


PRACTICAL

ELECTRONICS

DECEMBER 1980

65p

PE ENGINE TUNE-UP UNIT

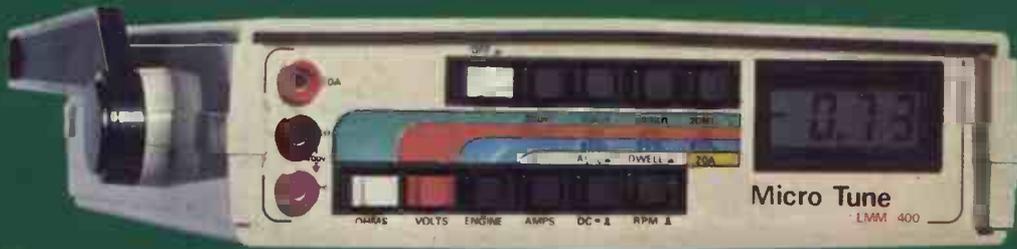

PE MASTER RHYTHM



Plus our Special Offer... **IN-CAR ENTERTAINMENT**

FREE INSIDE!

ELECTROVALUE Catalogue with all U.K. copies

COMP POCKET COMPUTER GREATEST BREAKTHROUGH YET

£99.90
+ VAT



COMPUTER
POWER THAT
ONCE FILLED A
ROOM CAN
NOW BE
CARRIED IN YOUR POCKET!

• Programs in BASIC • "QWERTY" Alphabetic Keyboard • 1.9K Random Access Memory • Long Battery Life.

Computer power that once filled a room can now be carried in your pocket! It's easy to load with ready-to-run software from cassette tape (interface and recorder optional) or program it yourself in easy-to-learn BASIC. 24 character liquid crystal readout displays one line at a time. Special feature is advanced non-volatile memory allows you to power on and off without losing the contents of memory. Note: Memory must be transferred to tape before changing batteries. Automatic statement compaction squeezes every ounce of memory space. Features power-off retention of programs and data. Powerful resident BASIC language includes multiple statements, math functions, editing, strings, arrays and much more. Multiple program loading capability subject to RAM availability. Carrying case and batteries included.

Program	Each	Program	Each
Real Estate	£13.95	Games 1	£8.95
Civil Engineering	£13.95	Business Statistics	£10.95
Aviation	£13.95	Business Financial	£10.95
Math Drill	£8.95	Personal Financial	£10.95

EXTENDED
WARRANTY BY
COMPCARE

We give a full one year's warranty on all our products.

EXTENDED
WARRANTY BY
COMPCARE

only £325 + VAT



TRS80
LEVEL 2 16K

Fully converted to UK T.V. Standard. Comes complete with easy to follow manuals. UK Power Supply - Cassette Leads - Sample tapes. Special box to enable you to plug into your own TV. Recommended for first time-buyers. Just plug in and go.

Interface to Centronics Parallel for TRS80 £75.00 + VAT

only £295 + VAT
Expand your TRS80 by 32K.
32K Memory on board.
Centronics parallel port.
Disk controller card. Real time clock. Requires Level II Basic Interface for 2 cassette decks complete with power supply.



THE VIDEO GENIE SYSTEM

EG3000
Series



16K
£289
+ VAT

WITH

• 16K user RAM
plus extended 12K Microsoft BASIC in ROM • Fully TRS-80 Level II software compatible • Huge

range of software already available • Self contained, PSU, UHF modulator, and cassette • Simply plugs into video monitor or UHF TV • Full expansion to disks and printer • Absolutely complete - just fit into mains plug.

NEW

TV GAME BREAK OUT

Has got to be one of the world's greatest TV games.

You really get hooked. As featured in ETI. Has also 4 other pinball games and lots of options. Good kit for up-grading old amusement games.

MINI KIT - PCB, sound & vision modulator, memory chip and de-code chip. Very simple to construct.

£14.90 + VAT

OR PCB £2.90 MAIN LSI £8.50 Both plus VAT

NEW REDUCED PRICES

8K £399
16K £499
32K £599

+ VAT

RRP £795 for 32K



EXTENDED
WARRANTY BY
COMPCARE

The PEDIGREE PETS

Very popular for home & business use. 8K Microsoft Basic in ROM. 8K Pet 32K & 16K with new improved keyboard. All with green screen.

Cassette Deck £55 extra. Full range of software available.

Interface PET IEEE - Centronics Parallel

Not decoded £49.00 + VAT Decoded £77.00 + VAT

NOW IN STOCK SUPER 80 COLUMN PET

only £825 + VAT

SPECIAL GET YOURSELF A SCOOP YOUR PET AND SAVE A FORTUNE

only £299 + VAT

Interface Cards £49

Full Pet Graphics including cables. Ready to go.

Interfaces with APPLE, PET, FXIDY, TRS80, COMPUKIT and NASCOM.

EX-STOCK.



EXTENDED
WARRANTY BY
COMPCARE

EUROPE'S FASTEST SELLING ONE BOARD COMPUTER COMPUKIT UK101

★ 6502 based system - best value for money on the market. ★ Powerful 8K Basic - Fastest around ★ Full Qwerty Keyboard. ★ 4K RAM Expandable to 8K on board. ★ Power supply and RF Modulator on board. ★ No Extras needed - Plug-in and go. ★ Kansas City Tape Interface on board. ★ Free Sampler Tape including powerful Disassembler and Monitor with each Kit. ★ If you want to learn about Micros, but didn't know which machine to buy then this is the machine for you.

40 pin Expansion Jumper Cable for CompuKit expansion £8.50 + VAT

Build, Understand and Program your own Computer for only a small outlay

KIT ONLY £179 + VAT
NO EXTRAS NEEDED

Available ready assembled, tested & ready to go £229 + VAT

NEW MONITOR FOR COMPUKIT UK101

• In 2K Eprom 2716 • Allows screen editing • Saves data on tape • Flashing cursor • Text scrolls down £22.00 + VAT

FOR THE COMPUKIT

Assembler/Editor	£14.90
Screen Editor Tape	£5.90

All Prices exclusive VAT

Game Packs		Super Space Invaders (8K)	£8.50
1. Four Games	£5.00	Space Invaders	£5.00
2. Four Games	£5.00	Chequers	£3.00
3. Three Games 8K only	£5.00	Real Time Clock	£3.00
		Case for CompuKit	£29.50

WE ARE NOW STOCKING THE APPLE II EUROPLUS AT REDUCED PRICES



16K £599
32K £649
48K £659

+ VAT

Getting Started APPLE II is faster, smaller, and more powerful than its predecessors. And it's more fun to use too because of built-in features like:

• BASIC - The Language that Makes Programming Fun.
• High-Resolution Graphics (in a 54,000-Point Array) for Finely-Detailed Displays.
• Sound Capability that Brings Programs to Life.
• Hand Controls for Games and Other Human-Input Applications.
• Internal Memory Capacity of 48K Bytes of RAM, 12K Bytes of ROM; for Big-System Performance in a Small Package.
• Eight Accessory Expansion Slots to let the System Grow With Your Needs.

You don't need to be an expert to enjoy APPLE II. It is a complete, ready-to-run computer. Just connect it to a video display and start using programs (or writing your own) the first day. You'll find that its tutorial manuals help you make it your own personal problem solver.

NOW OPEN

OUR NEW SHOWROOM & SALES CENTRE AT

311 Edgware Road,
London W2.

Telephone: 01-441 2922

THE ATARI VIDEO COMPUTER GAMES SYSTEM

Atari's Video Computer System now offers more than 1300 different game variations and options in twenty Game Program™ cartridges!


£83.00
+ VAT

Most Cartridges only £13.90 + VAT
Prices may vary with special editions. Basic Maths, Airsea Battle, Black Jack, Breakout, Surround, Spacwar, Video Olympics, Outlaw, Basketball, Hunt & Score*, Space War, Sky Diver, Air Sea Battle, Codebreaker*, Miniature Golf.

Extra Paddle Controllers - £14.90 + VAT

*Keyboard Controllers - £16.90 + VAT

SPACE INVADERS NOW IN STOCK £25

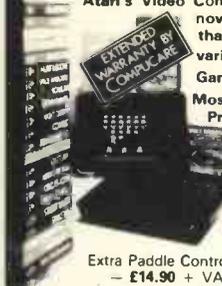

EXTENDED
WARRANTY BY
COMPCARE

Please add VAT to all prices - including delivery. Please make cheques and postal orders payable to **COMP SHOP LTD.**, or phone your order quoting **BARCLAYCARD, ACCESS, DINERS CLUB** or **AMERICAN EXPRESS** number.

CREDIT FACILITIES ARRANGED - send S.A.E. for application form.

MAIL ORDER AND SHOP:

14 Station Road, New Barnet, Hertfordshire, EN5 1QW (Close to New Barnet BR Station - Moorgate Line).
Telephone: 01-441 2922 (Sales) 01-449 6596 Telex: 298755 TELCOM G

NEW WEST END SHOWROOM:

311 Edgware Road, London W2. Telephone: 01-262 0387

OPEN - 10am - 7pm - Monday to Saturday

★ IRELAND: 80 Marlborough Street, Dublin 1. Telephone: Dublin 749933

★ COMPSHOP USA, 1348 East Edinger, Santa Ana, California, Zip Code 92705.
Telephone: 0101 714 5472526



"Europes Largest Discount
Personal Computer Stores"

COMP COMPUTER
COMPONENTS

(Part of the Compshop Ltd. Group)



PRACTICAL ELECTRONICS

VOLUME 16

No. 12

DECEMBER 1980

CONSTRUCTIONAL PROJECTS

PE MICROTUNE Part 1 <i>by Martin Kent</i>	26
A keep fit kit for your car	
PE MASTER RHYTHM Part 1 <i>by A. J. Boothman BSc.</i>	32
Programmable Rhythm Generator	
20mA LOOP <i>by Stephen Ibbs</i>	40
Opto-isolated power for the teletype selector magnet	
SPEECH SYNTHESIS <i>by Dr A. A. Berk</i>	44
Speech Board and interface designs	
SECURITY SENTINEL Part 2 <i>by W. C. Dickinson</i>	54
Construction and installation	
DISCO DESK Part 4 <i>by Ben J. Duncan</i>	60
12V subsystem; output routing and monitor switching	

GENERAL FEATURES

SEMICONDUCTOR UPDATE <i>by R. W. Coles</i>	23
IMS 1400 EF9365	
MICROBUS <i>by D.J.D.</i>	52
Six BASIC programs for the Sinclair ZX80	
INGENUITY UNLIMITED	64
Keyboard Switches—A True Peak-reading DC Voltmeter—Simple Pulse Generator	

NEWS AND COMMENT

EDITORIAL	17
MARKET PLACE	18
New Products	
INDUSTRY NOTEBOOK <i>by Nexus</i>	21
Our man in the know remains optimistic	
SPECIAL OFFER: IN CAR ENTERTAINMENT	24
Once again we bring you quality products at unbelievable prices	
COUNTDOWN	25
What to see; where and when to see it	
SPACEWATCH <i>by Frank W. Hyde</i>	43
The Shuttle Telescope—The Heart of a Supernova—The Solar Wind	
READOUT	50
Frank Hyde closes the correspondence on Velikovsky	
PATENTS REVIEW	59
Another installment in the chequered history of speaker design	
POINTS ARISING	59
NEWS BRIEFS	59
INDEX FOR VOLUME 16	66

OUR JANUARY 1981 ISSUE WILL BE ON SALE FRIDAY, 12 DECEMBER 1980
(for details of contents see page 31)

© IPC Magazines Limited 1980. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

WATFORD ELECTRONICS

33/35, CARDIFF ROAD, WATFORD, HERTS, ENGLAND
MAIL ORDER, CALLERS WELCOME. Tel. Watford 40588/9

ALL DEVICES BRAND NEW. FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O. OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS OFFICIAL ORDERS ACCEPTED (TELEPHONE ORDERS BY ACCESS NOW ACCEPTED Minimum order £10.00 please). TRADE AND EXPORT INQUIRY WELCOME. P & P ADD 40p to ALL ORDERS UNDER £10.00. OVERSEAS ORDERS POSTAGE AT COST.

VAT Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 15% to the total cost.

We stock many more items. It pays to visit us. We are situated behind Watford Football Ground, nearest Underground/Bus Rail Station: Watford High Street. Open Monday to Saturday 9 a.m.-6 p.m. Ample Free Car Parking space available.

POLYESTER CAPACITORS: (Axial Lead Type)
400V: 1nF, 1n5, 2n, 3n3, 4n7, 6n8, 10n, 15n, 9p; 18n 10p; 22n, 33n 11p; 47n, 68n 14p; 100n 17p; 150n, 220n 24p; 330n, 470n 41p; 680n, 470n; 1µF 64p; 2µF 82p; 4µF 85p.
1000V: 10n, 15n, 20n, 22n; 22p; 47n 26p; 100n 42p; 470n, 470n; 1µF 175p.

POLYESTER RADIAL LEAD CAPACITORS: 250V;
10n, 15n, 22n, 27n 6p; 33n, 47n, 68n, 100n 7p; 150n 10p; 220n, 330n 13p; 470n 17p, 680n 19p; 1µ 22p; 1µ5 30p; 2µ 34p.

TRANSISTORS		2N3442	
AC107	35	BC328	15
AC125	35	BC337	15
AC126	25	BC338	18
AC127	25	BC441	34
AC128	25	BC461	34
AC141	30	BC477	40
AC142	30	BC516	40
AC176	28	BC517	40
AC187	28	BC547	14
AC177	70	BC548	14
AC188	70	BC549	14
AC189	75	BC551	15
AC190	75	BC558	15
AC211	75	BC559	15
AC222	60	BC570	16
AC228	60	BC571	16
AC239	85	BD172	20
AD149	79	BD173	95
AD161	42	BD124	115
AD162	42	BD131	48
AF118	95	BD132	48
AF139	40	BD133	60
AF178	40	BD135	45
BC107	10	BD136	40
BC107B	12	BD137	40
BC108	10	BD138	40
BC108B	12	BD140	40
BC108C	12	BD141	198
BC108D	12	BD142	198
BC109B	12	BD205	10
BC109C	12	BD245	45
BC140	30	BD378	70
BC142	30	BD343	70
BC147	30	BD372	75
BC147B	10	BD695A	85
BC148	10	BD696A	85
BC148B	10	BDY60	160
BC148C	10	BDY61	160
BC149	35	BDY62	160
BC149C	27	BF167	29
BC153	27	BF177	25
BC154	13	BF178	35
BC157	10	BF179	35
BC158	10	BF180	35
BC159	11	BF194	12
BC160	45	BF195	12
BC167A	10	BF196	12
BC168A	10	BF197	12
BC169B	10	BF198	12
BC170	15	BF199	18
BC171	11	BF224	25
BC172	11	BF244A	29
BC173	11	BF244B	29
BC177	20	BF244	29
BC178	20	BF245	28
BC179	20	BF246	28
BC181	20	BF257	32
BC182	10	BF258	32
BC183	10	BF259	35
BC184	10	BF274	42
BC182L	10	BF336	40
BC183L	10	BF351	35
BC184L	10	BF594	30
BC187	26	BF595	30
BC187	26	BF596	30
BC187	26	BF597	30
BC187	26	BF838	30

It's faster and more thorough than classroom learning: you pace yourself and answer questions on each new aspect as you go. This gives rare satisfaction - you know that you are really learning and without mindless drudgery. With a good self-instruction course you become your own best teacher.

Understand Digital Electronics

In the years ahead digital electronics will play an increasing part in your life. Calculators and digital watches mushroomed in the 1970's - soon we will have digital car instrumentation, cash cards, TV messages from friends and electronic mail. After completing these books you will have broadened your career prospects and increased your knowledge of the fast-changing world around you.

DIGITAL COMPUTER LOGIC AND ELECTRONICS £7.00

This course is designed as an introduction to digital electronics and is written at a pace that suits the raw beginner. No mathematical knowledge is assumed other than the use of simple arithmetic and decimals and no electronic knowledge is expected at all. The course moves painstakingly through all the basic concepts of digital electronics in a simple and concise fashion: questions and answers on every page make sure that the points are understood.

Everyone can learn from it - students, engineers, hobbyists, housewives, scientists. Its four A4 volumes consist of:

- Book 1 Binary, octal and decimal number systems; conversion between number systems; conversion of fractions; octal-decimal conversion tables.
- Book 2 AND, OR gates; inverters; NOR and NAND gates; truth tables; introduction to Boolean algebra.
- Book 3 Positive ECL; De Morgans Laws; designing logic circuits using NOR gates; dual-input gates.
- Book 4 Introduction to pulse driven circuits; R-S and J-K flip flops; binary counters; shift registers; half-adders.



DESIGN OF DIGITAL SYSTEMS £12.50

This course takes the reader to real proficiency. Written in a similar question and answer style to Digital Computer Logic and Electronics, this course moves at a much faster pace and goes into the subject in greater depth. Ideally suited for scientists or engineers wanting to know more about digital electronics, its six A4 volumes lead step by step through number systems and Boolean algebra to memories, counters and arithmetic circuits and finally to an understanding of calculator and computer design.

Book 1 Octal, hexadecimal and binary number systems; conversion between number systems; representation of negative numbers; complementary systems; binary multiplication and division.


Book 2 OR and AND functions; logic gates; NOT, exclusive-OR, NAND, NOR and exclusive-NOR functions; multiple input gates; truth tables; De Morgans Laws; canonical forms; logic conventions; karnaugh mapping; three state and wired logic.

Book 3 Half adders and full adders; subtractors; serial and parallel adders; processors and arithmetic logic units (ALUs); multiplication and division systems.

Book 4 Flip flops; shift registers; asynchronous and synchronous counters; ring, Johnson and exclusive-OR feedback counters; random access memories (RAMs) and read only memories (ROMs).

Book 5 Structure of calculators; keyboard encoding; decoding display data; register systems; control unit; program ROM; address decoding; instruction sets; instruction decoding; control programme structure.

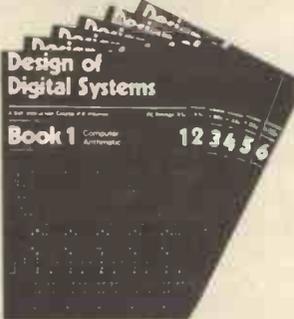Book 6 Central processing unit (CPU); memory organization; character representation; program storage; address modes; input/output systems; program interrupts; interrupt priorities; programming; assemblers; computers; executive programs; operating systems and time sharing.



Flow Charts and Algorithms

are the essential logical procedures used in all computer programming and mastering them is the key to success here as well as being a priceless tool in all administrative areas - presenting safety regulations, government legislation, office procedures etc.

THE ALGORITHM WRITER'S GUIDE £4.00

explains how to define questions, put them in the best order and draw the flow chart, with numerous examples.

GUARANTEE No risk to you.

If you are not completely satisfied, your money will be refunded upon return of the books in good condition.

CAMBRIDGE LEARNING LIMITED, UNIT 27
RIVERMILL SITE, FREEPOST, ST. IVES, HUNTINGDON,
CAMBS., PE17 4BR, ENGLAND.
TELEPHONE: ST. IVES (0480) 67446

All prices include worldwide postage (airmail is extra - please ask for prepayment invoice).

Please allow 28 days for delivery in U.K.

Microcomputers are coming - ride the wave! Learn to program.

Millions of jobs are threatened but millions more will be created. Learn BASIC - the language of the small computer and the most easy-to-learn computer language in widespread use. Teach yourself with a course which takes you from complete ignorance step-by-step to real proficiency with a unique style of graded hints. In 60 straightforward lessons you will learn the five essentials of programming: problem definition, flowcharting, coding the program, debugging, clear documentation. Harder problems are provided with a series of hints so you never sit glassy-eyed with your mind a blank. You soon learn to tackle really tough tasks such as programs for graphs, cost estimates, compound interest and computer games.



COMPUTER PROGRAMMING IN BASIC £9.00

Book 1 Computers and what they do well; READ, DATA, PRINT, powers, brackets, variable names; LET; errors; coding simple programs.

Book 2 High and low level languages; flowcharting; functions; REM and documentation; INPUT, IF...THEN, GO TO; limitations of computers, problem definition.

Book 3 Compilers and interpreters; loops. FOR...NEXT, RESTORE; debugging; arrays; bubble sorting; TAB.

Book 4 Advanced BASIC; subroutines; string variables; files; complex programming; examples; glossary.

THE BASIC HANDBOOK £11.50

This best-selling American title usefully supplements our BASIC course with an alphabetical guide to the many variations that occur in BASIC terminology. The dozens of BASIC 'dialects' in use today mean programmers often need to translate instructions so that they can be RUN on their system. The BASIC Handbook is clear, easy to use and should save hours of your time and computer time: A must for all users of BASIC throughout the world.

A.N.S. COBOL £5.90

The indispensable guide to the world's No. 1 business language. After 25 hours with this course, one beginner took a consulting job, documenting oil company programs and did invaluable work from the first day. Need we say more?

ORDER FORM

Please send me the following books:-

- Digital Computer Logic & Electronics @ £7.00
- Design of Digital Systems @ £12.50
- Algorithm Writer's Guide @ £4.00
- Computer Programming in BASIC @ £9.00
- BASIC Handbook @ £11.50
- ANS COBOL @ £5.90
- Your Booklist (Free)

I enclose a *cheque/PO payable to Cambridge Learning Ltd.

for £..... (*delete where applicable)
Please charge my:

*Access/American Express/Barclaycard/Diners Club/Eurocard/Visa/
Mastercharge/Trustcard

Credit Card No.....

Signature

Telephone orders from credit card holders accepted on 0480 67446 (Ansafone).

Overseas customers (incl. Eire) should send a bank draft in sterling drawn on a London bank, or quote credit card number.

Name

Address

.....

.....

Cambridge Learning Limited, Unit 27, Rivermill Site,
FREEPOST, St. Ives, Huntingdon, Cambs PE17 4BR, England.
(Registered in England, No. 1328762)

D.I.Y. KITS FOR SYNTHESISERS, SOUND EFFECTS



BASIC COMPONENTS SETS include all necessary resistors, capacitors, semiconductors, potentiometers and transformers. Hardware such as cases, sockets, knobs, keyboards, etc. are not included but most of these may be bought separately. Fuller details of kits PCBs and parts are shown in our lists.

LAYOUT DIAGRAMS are supplied free with all PCBs unless "as published".

PHONOSONICS

MAIL ORDER SUPPLIERS OF QUALITY PRINTED CIRCUIT BOARDS, KITS AND COMPONENTS TO A WORLD-WIDE MARKET

P.E. MINISONIC MK2 SYNTHESIZER

A portable mains operated miniature sound synthesiser with keyboard circuits. Although having slightly fewer facilities than the large Formant and P.E. synthesisers the functions offered by this design give it great scope and versatility.

Set of basic component kits (excl. KBD R's & tuning pots - see list for options available) and PCBs (incl. layout charts)
KIT 38-25 £80.14
 "Sound Design" booklet **£1.00**

P.E. 128-NOTE SEQUENCER

Enables a voltage controlled synthesiser to automatically play pre-programmed tunes of up to 32 pitches and 128 notes long. Programs are keyboard initiated and note length and rhythmic pattern are externally variable.

Set of basic comps, PCBs and charts **KIT 76-7 £35.56**
 Set of text photocopies **£1.36**

P.E. 16-NOTE SEQUENCER

Sequences of up to 16 notes may be programmed by the use of external panel controls and fed into most voltage controlled synthesisers.

Set of basic comps, PCBs and charts **KIT 86-5 £32.10**
 Set text photocopies **£1.84**

P.E. STRING ENSEMBLE

A multivoiced polyphonic string instrument synthesiser. Set of basic comps, PCBs & charts

KIT 77-8 £109.72

ELEKTOR PHASING & VIBRATO

Includes manual and automatic control over the rate of phasing & vibrato, and has been slightly modified to also include a 2-input mixer stage.

Set of basic comps, PCB & chart **KIT 70-2 £21.67**
 Text photocopy **67p**

ELEKTOR FORMANT SYNTHESIZER

A very sophisticated synthesiser for the advanced constructor who puts performance before price.

Set of basic comps, PCBs (as publ.) **KIT 66-14 £255.45**
 Set of text photocopies **£7.83**

ELEKTOR DIGITAL REVERB UNIT

A very advanced unit using sophisticated i.c. techniques instead of mechanical spring lines. The basic delay range of 24 to 90mS can be extended up to 450mS using the extension unit. Further delays can be obtained using more extensions.

Main unit basic comps and PCB (as publ.) **KIT 78-3 £49.95**
 Extension unit basic comps and PCB (as publ.) **KIT 78-4 £39.95**
 Text photocopy **86p**

ELEKTOR SEWAR

For use with Elektor Analogue Reverb to give greater flexibility to the reverb effects.

Basic comps, PCB (as publ.) **KIT 101-1 £18.19**
 Text photocopy **60p**

ELEKTOR RING MODULATOR

Compatible with the Formant & most other synthesisers. Set of basic comps & PCB (as publ.)

KIT 87-2 £6.84
 Text photocopy **38p**

ELEKTOR CHOROSYNTH

A 2 $\frac{1}{2}$ -octave Chorus synthesiser with an amazing variety of sounds ranging from violin to cello and flute to clarinet amongst many others. Experienced constructors can readily extend the octave coverage.

Basic comps, PCBs and charts but excl. sw's **KIT 100-8 £44.39**
 Text photocopy **70p**

ELEKTOR ANALOGUE REVERB

Using i.c.s instead of spring-lines the main unit has a maximum delay of up to 100mS, and the additional set extends this up to 200mS. May be used in either mono or stereo mode.

Main unit basic component set **KIT 83-4 £29.23**
 Additional Delay basic components **KIT 83-2 £20.07**
 PCB (as publ.) to hold both kits included in Kit 83-4 **67p**
 Text photocopy

ELEKTOR FUNNY TALKER

Incorporates a ring modulator, chopper & frequency modulator to produce fascinating sounds when used with speech & music signals.

Basic comps, PCB (as publ.) **KIT 99-1 £9.60**
 Text photocopy **40p**

ELEKTOR FREQUENCY DOUBLER

For use with guitars & other electronic instruments to produce an output one octave higher than the input. Inputs and outputs may be mixed to give greater depth.

Basic comps, PCB (as publ.) **KIT 98-1 £5.48**
 Text photocopy **20p**

P.E. SPLIT-PHASE TREMOLO

A simple but effective substitute for a rotary cabinet. The output of an internal generator is phase-split and modulated by an input signal from an electronic guitar or other instrument. Output amplitudes, depth & rate are variable. May be fed to one or two amplifiers.

Basic comps, PCB & chart **KIT 102-3 £17.68**
 Text photocopy **65p**

P.E. MINISONIC WAVEFORM CONVERTER

A simple converter that modifies the Minisonic sawtooth waveform to produce triangle and sine outputs. Ideally one should be used with each Minisonic VCO.

Basic comps, PCB & chart **KIT 96-1 £3.98**

P.E. GUITAR MULTIPROCESSOR

An extremely versatile sound processing unit capable of producing, for example, flanging, vibrato, reverb, fuzz and tremolo as well as other fascinating sounds. May be used with most electronic instruments.

Set of basic comps, PCBs & charts (excl. SWs) **KIT 85-5 £49.23**
 Set of text photocopies **£2.52**

P.E. PHASER

An automatically controlled 6-stage phasing unit with integral oscillator.

Basic components, PCB & chart **KIT 88-1 £10.91**
 2-Notch extension, PCB & chart **KIT 88-2 £6.38**
 Text photocopy **68p**

ELEKTOR ELECTRONIC PIANO

A touch-sensitive multiple-voicing piano using the latest integrated circuit techniques for the keying and envelope shaping, and virtually eliminating "bee-hive" noise hitherto inherent in previous electronic pianos.

5-octave set of basic comps and PCBs (as publ.) **KIT 80-9 £149.42**
 Additional 3-octave extension and basic parts and PCBs (as published) **KIT 80-10 £58.32**
 Set of text photocopies **£1.81**

P.E. GUITAR EFFECTS UNIT

Modulates the attack, decay and filter characteristics of a signal from most audio sources, producing 8 different switchable effects that can be further modified by manual controls.

Basic comps, PCB & chart **KIT 42-3 £10.60**
 Text photocopy **28p**

P.E. GUITAR OVERDRIVE

Sophisticated versatile fuzz unit incl. variable controls affecting the fuzz quality whilst retaining attack and decay, and also providing filtering. Usable with most electronic instruments.

Basic components, PCB & chart **KIT 56-3 £11.22**
 Text photocopy **68p**

P.E. SMOOTH FUZZ

Basic components, PCB & chart **KIT 91-1 £6.52**
 Text photocopy **55p**

TREMOLO UNIT

A slightly modified version of the simple P.E. unit.

Basic components, PCB & chart **KIT 54-1 £3.74**

GUITAR FREQUENCY DOUBLER

A slightly modified and extended version of the P.E. unit. Basic components, PCB & chart **KIT 74-1 £5.19**
 Text photocopy **39p**

P.E. GUITAR SUSTAIN

Maintains the natural attack whilst extending note duration.

Basic components, PCB & chart **KIT 75-1 £6.99**
 Text photocopy **38p**

P.E. AUTO-WAH UNIT

Automatically gives Wah or Swell sounds with each note played.

Basic components, PCB & chart **KIT 58-1 £10.11**
 Text photocopy **58p**

ELEKTOR WAVEFORM CONVERTER

Converts a saw-tooth waveform into sinewave, mark-space sawtooth, regular triangle, or square-wave with variable mark-space.

Basic comps, PCB & chart, but excl. sw's **KIT 67-1 £9.24**

P.E. SWITCHED TONE TREBLE BOOST

Provides switched selection of 4 preset tonal responses.

Basic components, PCB & chart **KIT 89-1 £4.34**
 Text photocopy **78p**

NEW MORE INFORMATIVE LIST NOW AVAILABLE

ADD: POST & HANDLING

U.K. orders: Keyboards add £2.70 each. Other goods: Under £5 add 50p, under £20 add 75p, over £20 add £1. Recommended insurance against postal mishaps: add 50p for cover up to £50, £1 for £100 cover, etc., pro-rata. Insurance must be added for credit card orders. N.B. Eire, C.I., B.F.P.O. and other countries are subject to higher export postage rates.

ADD 15% VAT

(or current rate if changed). Must be added to full total of kits, discount post & handling on all U.K. orders. Does not apply to Exports, or photocopies.

EXPORT ORDERS ARE WELCOME but to avoid delay we advise you to see our list for postage rates. All payments must be cash-with-order, in Sterling by International Money Order or through an English Bank. To obtain list - Europe send 35p, other countries send 75p. **Note that we do not offer a C.O.D. service and that our terms are payment in advance.**

PHONOSONICS · DEPT PE8D · 22 HIGH STREET · SIDCUP · KENT DA14 6EH

TERMS: C.W.O., MAIL ORDER OR COLLECTION BY APPOINTMENT (TEL 01-302 6184)

AND OTHER PROJECTS

PHOTOGRAPHS in this advertisement show two of our units containing some of the P.E. projects built from our kits and PCBs. The cases were built by ourselves and are not for sale, though a small selection of other cases is available.

LIST—Send stamped addressed envelope with all U.K. requests for free list giving fuller details of PCBs, kits and other components.

OVERSEAS enquiries for list Europe—send 35p; other countries—send 75p.



KIMBER-ALLEN KEYBOARDS AND CONTACTS

KIMBER-ALLEN KEYBOARDS as required for many published projects. The manufacturers claim that these are the finest moulded plastic keyboards available. All octaves are C to C, the keys are plastic, spring-loaded, fitted with actuators, and mounted on a robust aluminium frame.

3 Octave (37 notes) £25.50 4 Octave (49 notes) £32.25 5 Octave (61 notes) £39.75

CONTACT ASSEMBLIES (gold-clad wire) — 1 required for each KBD note:
Type GJ — SPCO 33p ea. Type GB — 2 pr N/O 37½p ea.

P.E. V.C.F.

A voltage controlled filter extracted from P.E. Minisonic project.

Basic comps, PCB & chart KIT 65-1 £8.45

P.E. RING MODULATOR

Extracted from P.E. Minisonic project.

Basic comps, PCB & chart KIT 59-1 £6.35

WIND & RAIN EFFECTS UNIT

A slightly modified version of the original P.E. unit.

Basic comps, PCB & chart KIT 28-1 £4.84

Text photocopy 28p

P.E. ENVELOPE SHAPER WITH VCA

Has an Integral Voltage Controlled Amplifier, and has full manual control over the A.D.S.R. functions.

Basic comps, PCB & chart KIT 50-1 £8.03

Text photocopy 58p

P.E. TRANSIENT GENERATOR

An ADSR envelope shaper without VCA, and additionally providing Repeat-triggering enabling a synthesiser to be programmed for mandolin or banjo effects.

Basic comps, PCB & chart KIT 63-2 £7.62

Text photocopy 58p

P.E. EXTERNAL-INPUT SYNTHESISER-INTERFACE

Allows external inputs such as guitars, microphone etc., to be processed by synthesiser circuits.

Basic comps, PCB & chart KIT 81-1 £3.90

P.E. TUNING FORK

Produces 84 switch-selected frequency-accurate tones with an LED monitor clearly displaying beat-note adjustments.

Set of basic components, incl. power supply, PCBs & charts KIT 46-3 £23.32

Text photocopy 97p

P.E. TUNING INDICATOR

A simple 4-octave frequency comparator for use with synthesisers and other instruments where the full versatility of KIT 46 is not required.

Basic components, PCB & chart, but excl. sw. KIT 69-1 £8.19

Text photocopy 58p

P.E. DYNAMIC RANGE LIMITER

Preset to automatically control sound output levels.

Basic comps, PCB & chart KIT 62-1 £5.31

P.E. CONSTANT DISPLAY FREQUENCY COUNTER

A 4-digit counter for 1Hz to 99kHz with 1Hz sampling rate. Readout does not count visibly or flicker due to blanking.

Basic components, PCB & chart KIT 79-4 £31.61

Text photocopy 78p

P.E. 6-CHANNEL MIXER

A high specification stereo mixer with variable input impedances.

Basic components, (excl. sw.'s), and set of PCBs and charts. KIT 90-8 £64.62

Extra 2-channel set with PCB KIT 90-9 £10.21

Set of Text photocopies £1.50

STEREO HEADPHONE AMPLIFIER

Extracted from P.E. 6-channel mixer.

Basic components, PCB & chart KIT 92-1 £5.68

DIGITAL EXPOSURE UNIT

Controls up to 750 watts in ½ second steps up to 10 minutes, with built-in audio alarm.

Basic components, PCBs & charts KIT 93-3 £23.45

Text photocopy £1.20

P.E. DISCOSTROBE

A 4-channel light show controller giving a choice of sequential, random, or full strobe mode of operation.

Basic components, PCB & chart KIT 57-3 £19.37

Text photocopy 78p

RHYTHM GENERATORS

Several available, including programmable 16 beat 64000 pattern, and pre-programmed 15 pattern using either M252 or M253 rhythm chips. A selection of effects instrument circuits is also available.

P.E. VOICE OPERATED FADER

For automatically reducing music volume during talkover — particularly useful for discos.

Basic components, PCB & chart KIT 30-1 £4.37

Text photocopy 28p

P.E. DYNAMIC NOISE LIMITER

Very effective stereo circuit for reducing the hiss found in most tape recordings.

Basic components, PCB & chart KIT 97-1 £8.07

Text photocopy 75p



TRAIN FOR SUCCESS

in Radio, Television & Electronics

ICS have helped thousands of ambitious people to move up into higher paid more secure jobs in the field of electronics — now it can be your turn. Whether you are a newcomer to the field or already working in the industry, ICS can provide you with the specialised training so essential to success.

Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful, is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

- Telecommunications Technicians
- Radio, T.V. Electronics Technicians
- Radio Amateurs
- Electrical Installation Work

Diploma Courses

- Colour T.V. Servicing
- CCTV Engineering
- Electronic Engineering & Maintenance
- Computer Engineering and Programming
- Radio, T.V. and Audio, Engineering & Servicing
- Electrical Engineering, Installations & Contracting

Other Career Courses

A wide range of other technical and professional courses are available including GCE.

FREE BOOK

Post this coupon or 'phone today for free Electronics careers guide.

Name _____

Address _____


Age _____

ICS To ICS, Dept 273B, Intertext House, London SW8 4UJ or telephone 01-622 9911 (all hours)

PRICES ARE CORRECT AT TIME OF PRESS. E. & O. E. DELIVERY SUBJECT TO AVAILABILITY.

PHONOSONICS

Pure ind

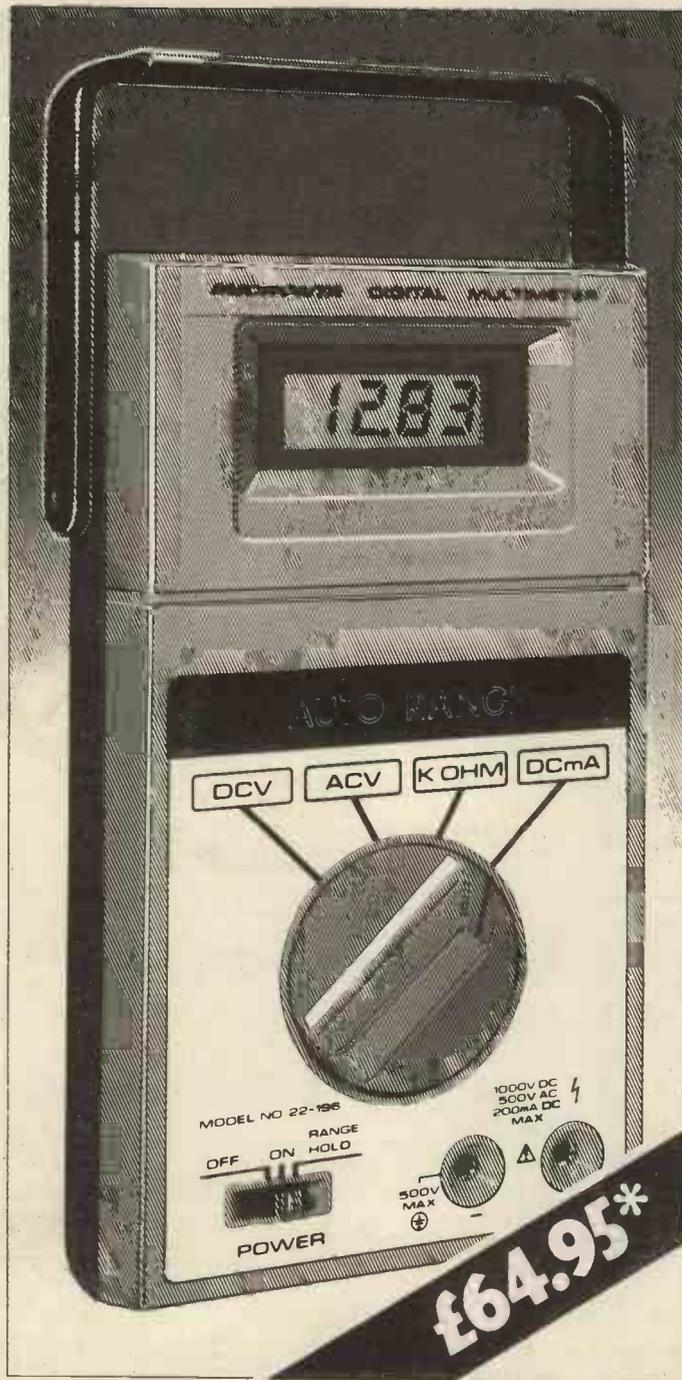

£64.95*

Micronta Auto Range Multimeter Gives you correct polarity, range and measurement — every time. Single function switch lets you choose DC 4 ranges; AC 4 ranges; DC current resistance. 4 ranges. LCD readout. Exclusive range hold facility. 22-196




£6.95*

Micronta 1000 Ohms/Volt Multimeter Very compact at 89 x 59 x 32 mm. Easy to read colour meter, pin jacks for all 8 ranges. Reads AC V, DC current and ohms. Mirrored scale. 20-027



£9.95*

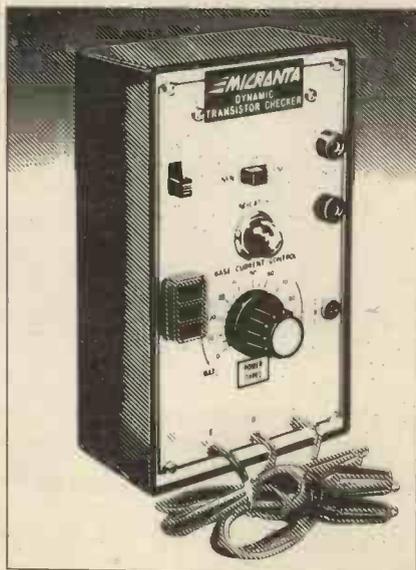Micronta Transistorized Signal Tracer Spot circuit troubles, check RF, IF and audio signals from aerial to speaker on all audio equipment. It has built in 5 cm speaker with volume control. 50 x 143 x 38 mm. 22-010




£9.95*

Micronta Dynamic Transistor Checker Shows current gain and electrode open and short circuit. Tests low medium or high power PNP or NPN types. Go/no-go tests from 5-50 mA on power types. "Quick-check" sockets. 22-024

Wiggenance.

Realistic Direct Entry Programmable Scanning Receiver Hear real-life drama on six exciting bands. With direct access to all frequencies, you can punch in actual frequencies for monitoring, storing in the computer's memory or just exploring. Big fluorescent display. Phase locked loop security. 20-9111

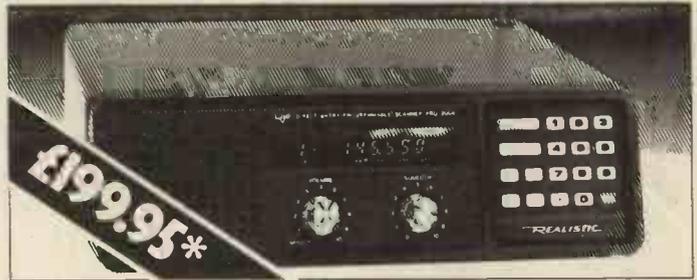TRS-80 Model I C.P.U.'s Ready to run from your TV monitor. Plug in and start computing. Contains 4096 bytes of user memory and can be expanded to 16K. 26-9051



- | | | | | | | |
|---|---|--|---|--|---|--|
| <p>ACCRINGTON
37 Union Street</p> <p>ALDRIDGE
15 Central Area Development</p> <p>BARNSELY
58 Market Street</p> <p>BASINGSTOKE
22 London Street</p> <p>BIRKENHEAD
Kwik Save Centre, Preston</p> <p>BRADFORD COMPUTER CENTRE
2/4, Forster Square</p> <p>BIRMINGHAM AREA</p> <p>BULL RING
528 Bridge Link Shopping Centre</p> <p>CAPE HILL
44-46, Cape Hill</p> <p>CITY CENTRE
80, Corporation Street</p> <p>DALE END
57-58, Dale End</p> <p>EDGBASTON COMPUTER CENTRE
Edgbaston Shopping Centre</p> <p>ERDINGTON
218 High Street</p> <p>HALESOWEN
57, Queensway</p> <p>NORTHFIELD
749 Bristol Road South</p> | <p>PERRY BARR
201 Briton Square</p> <p>SHELDON
2268 Coventry Road</p> <p>SHEFFIELD
44, 46 Cape Hill</p> <p>WARD END
887 Washwood Heath Road</p> <p>WEDNESBURY
Bilston Road</p> <p>BOLTON
5 Nelson Square</p> <p>BOSCOMBE
548 Christchurch Road</p> <p>BOLNISEMOUTH
132/4 Commercial Road</p> <p>BRADFORD
9 Petergate</p> <p>BRIGHTON
70 London Road</p> <p>BRISTOL AREA</p> <p>BISHOPSTON
13 Gloucester Road</p> <p>BRISTOL COMPUTER CENTRE
Colston Centre</p> <p>CLIFTON
146 Whitehalls Road</p> <p>DOWNEND
5 Badminton Road</p> <p>KNOWLE
Broadwalk Shopping Centre</p> <p>WITE
4 North Parade</p> | <p>BROMSGROVE
6-8 St. John Street</p> <p>BROWNHILLS
80 High Street</p> <p>BURY (Lancs)
91 The Rock</p> <p>CARLISLE
87 Merrion Centre</p> <p>CHELTEMPHAM
31 Cambray Place</p> <p>CHESTER
Kwik Save Centre</p> <p>SEALAND ROAD
COVENTRY</p> <p>4 Haies Street
CREWE</p> <p>12 Market Street
DARLINGTON</p> <p>15/16 Priestgate
DERBY</p> <p>33 Victoria Street
DONCASTER</p> <p>32/34 Kinggate
DUDLEY</p> <p>Trindle Road Roundabout
EASTBOURNE</p> <p>Largely Shopping Centre
EXETER</p> <p>13 Paris Street
GRIMSBY</p> <p>Riverhead Centre
HARROGATE</p> <p>34 Oxford Street
WITE</p> | <p>HUDDERSFIELD
Packhorse Shopping Centre</p> <p>HULL
Status City, Cough Road</p> <p>LEAMINGTON SPA
83 Warwick Street</p> <p>LEEDS
72 Merrion Centre</p> <p>LEEDS
3 Eastgate</p> <p>LEICESTER
Market Street</p> <p>LETONWORTH
25 Commerce Way</p> <p>LINCOLN
High Street</p> <p>LIVERPOOL AREA</p> <p>ALLERTON
90 Allerton Road</p> <p>BOOTLE
New Strand Precinct</p> <p>OLD SWAN
648 Prescott Road</p> <p>ST. JOHNS PRECINCT
168 Market Way</p> <p>LONDON AREA</p> <p>BARKING
8/10 North Street</p> <p>BAYSWATER
The Colonades</p> <p>Pochester Road
BECKENHAM</p> <p>144 High Street
CATFORD</p> <p>23 Catford Broadway
CHESHUNT</p> <p>92 Turners Hill
CHINGFORD</p> <p>3 Hall Lane
CLAPHAM</p> <p>84 Clapham High Street
COLLIER ROW</p> <p>27, Collier Row
CRUICKSHAW END</p> <p>42 The Broadway
DAGENHAM</p> <p>297 Heathway
EDGWARE</p> <p>128 Burnt Oak
EDMONTON</p> <p>23, North Mall
ENFIELD</p> <p>10 Colman Parade
HAMMERSMITH</p> <p>142/4 King Street
HENDON</p> <p>24 Sentinel Square
ORPINGTON</p> <p>5 The Walnuts
PALMERS GREEN</p> <p>375 Green Lanes
ROXFORD</p> <p>27 Collier Row Road
SEACDAL LANE</p> <p>1/2, Seacal Lane
STREATHAM</p> <p>254 Streatham High Road
TOTTENHAM</p> <p>455 High Road
WALTHAMSTOW</p> <p>123 High Street
WALLWORTH</p> <p>239 Watworth Road
WANDSWORTH</p> <p>107/9 High Street
WELLING</p> <p>7 Embassy Court
WIMBLEDON</p> <p>124/6 The Broadway
LUTON</p> <p>157 Dunstable Road
MANCHESTER AREA</p> <p>ARNDALE
Unit 71, Arndale Centre</p> <p>BRAMHALL
14/15 The Centre</p> <p>CHADDERTON
67 High Street</p> <p>CHEBLE
67, High Street</p> <p>DEANSGATE COMPUTER CENTRE
36, Market Place</p> <p>HYDE
4/8 The Mall</p> <p>RADCLIFFE
25, Bockburn Street</p> <p>SALE
The Mall</p> | <p>CITY CENTRE
Arndale Centre</p> <p>STRETTON
Arndale Centre</p> <p>NEWBURY
14 Bartholomew Street</p> <p>NORTHAMPTON
Weston Favel Shopping Centre</p> <p>WANDSWORTH
107/9 High Street</p> <p>WELLING
7 Embassy Court</p> <p>WIMBLEDON
124/6 The Broadway</p> <p>LUTON
157 Dunstable Road</p> <p>MANCHESTER AREA</p> <p>ARNDALE
Unit 71, Arndale Centre</p> <p>BRAMHALL
14/15 The Centre</p> <p>CHADDERTON
67 High Street</p> <p>CHEBLE
67, High Street</p> <p>DEANSGATE COMPUTER CENTRE
36, Market Place</p> <p>HYDE
4/8 The Mall</p> <p>RADCLIFFE
25, Bockburn Street</p> <p>SALE
The Mall</p> | <p>SHREWSBURY
20 Shop Latch</p> <p>SOUTHAMPTON
20 The Forum Shopping Centre</p> <p>SLOUGH
293 High Street</p> <p>SOUTHAMPTON
East St. Centre</p> <p>STAFFORD
6 Sheridan Shopping Centre</p> <p>ST. HELENS
Fingerpost Centre</p> <p>STURKE-OAK-TRENT
Hanley 16 Charles Street</p> <p>SUNDERLAND
4 Fawcett Street</p> <p>SURREY
205 High Street</p> <p>SUTTON (Surrey)
205 High Street</p> <p>TORQUAY
134 Lincoln Street</p> | <p>TYNE AND WEAR AREA</p> <p>NEWCASTLE
23 Newcastle Centre</p> <p>SHEFFIELD
19-20, Hillsborough Shopping Centre</p> <p>SHELDON ROAD
184/6 Sheldon Road</p> <p>WASHINGTON NEW TOWN
Galleries Shopping Centre</p> <p>WAKEFIELD
Kirkgate Shopping Centre</p> <p>WALSALL
74 Bradford Street</p> <p>WALLASEY
The Precinct</p> <p>WIGAN
8 St. Nicholas Street</p> <p>WORKSOP
7/9 Bridge Place</p> <p>YORK
5 Church Street</p> |
|---|---|--|---|--|---|--|

* All prices include VAT.

IT'S POSSIBLE, ONLY AT Tandy
Better Equipment. Lower Prices. No Middlemen!

Make sure of your Heathkit catalogue... write now.



Keep up to date with the world's finest electronic kits—with the Heathkit catalogue. 48 product packed pages contain photographs and specifications of the widest possible range of kits. Everything from doorbells to digital clocks, multimeters to microcomputers.

Heathkit make it easy to build, easy on your pocket, and as with 13 million Heathkit builders over 34 years, your success is guaranteed.

Make sure of your copy of the Heathkit catalogue. Send the coupon today, plus 25p in stamps and beat the demand.

To: Heath Electronics (U.K.) Limited, Dept (PE/12/80)
Bristol Road, Gloucester, GL2 6EE.

Please send me a copy of the Heathkit catalogue. (PE/12/80)
I enclose 25p in stamps.

Name _____

Address _____

Soldering
Iron offer
FREE

N.B. If you are already on the Heathkit mailing list you will automatically receive a copy of the Heathkit catalogue, without having to use this coupon. When you receive your catalogue you will get details of this free offer.

HEATHKIT

HEATH
ZENITH

DISCO LIGHTING KITS!!!

First class constructional projects, c/w glass fibre P.C.B.'s & full instructions. No extra components needed to make a top rate working unit.

LK1 3 channel sound-to-light.
£9.90 300 w/channel 1v - 100w input

LK3 2kW slider dimmer
£5.50 suitable for clubs/pubs.
A professional unit c/w face plate.

LK2 3 channel 3kW
£17.90 zero voltage firing
200mV - 100 watts input.


LK4 4 channel 4kW
£16.50 audio - forward/reverse
auto - two speed ranges.

ALL KITS C/W
circuit, comprehensive
instructions & full
parts guarantee



Carriage on above 70p

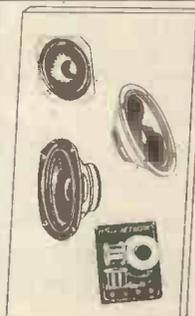Suitable case for
LK 1/2/4 **£3.50**
100w spots ES or BC
£1.50.
Coloured pigmy lamps
65p.



UNREPEATABLE HI-FI BARGAIN

3 WAY LOUDSPEAKER KIT C/W BAFFLE (pre-cut)

Comprises:

- ★ 6 1/2" linen surround bass unit
 - ★ 5" mid-range unit
 - ★ 3" tweeter
 - ★ 3 way crossover, fixing screws & baffle
 - ★ 20 watts handling capability.
- Full instructions provided
Must be heard to be believed!!

£10.50 or 2 kits for **£20.** Carr. **£1** per kit.

SAXON ENTERTAINMENTS

327-333 Whitehorse Rd., Croydon, Surrey CR0 2HS.
(01) 684 8007

Order by phone - Access/Barclaycard/C.O.D.
Open Mon. - Sat. 9am - 5pm.

MONITORS MONITORS MONITORS



Uncased from 3" to 12"
Cased from 5" to 20"

Semi professional or
professional available
from stock.

Monitor PCB's including
Transformers and Tubes
also in stock.

All Monitors available
with P4, P31 and P39
Tubes.

Phone or write for
details.

CROFTON ELECTRONICS

Crofton Electronics Limited
35 Grosvenor Road, Twickenham, Middx.
Tel: 01 891 1513

Britain's first com puter kit.

The Sinclair ZX80.

£79.95

Price breakdown
ZX80 and manual: £69.52
VAT: £10.43
Post and packing FREE

Please note: many kit makers quote VAT-exclusive prices.

You've seen the reviews... you've heard the excitement... now make the kit!

This is the ZX80. 'Personal Computer World' gave it 5 stars for 'excellent value.' Benchmark tests say it's faster than all previous personal computers. And the response from kit enthusiasts has been tremendous.

To help you appreciate its value, the price is shown above with and without VAT. This is so you can compare the ZX80 with competitive kits that don't appear with inclusive prices.

'Excellent value' indeed!

For just £79.95 (including VAT and p&p) you get everything you need to build a personal computer at home... PCB, with IC sockets for all ICs; case; leads for direct connection to a cassette recorder and television (black and white or colour); everything!

Yet the ZX80 really is a complete, powerful, full-facility computer, matching or surpassing other personal computers at several times the price.

The ZX80 is programmed in BASIC, and you can use it to do quite literally anything from playing chess to managing a business.

The ZX80 is pleasantly straightforward to assemble, using a fine-tipped soldering iron. It immediately proves what a good job you've done; connect it to your TV... link it to an appropriate power source*... and you're ready to go.

Your ZX80 kit contains...

- Printed circuit board, with IC sockets for all ICs.
- Complete components set, including all ICs—all manufactured by selected world-leading suppliers.
- New rugged Sinclair keyboard, touch-sensitive, wipe-clean.
- Ready-moulded case.
- Leads and plugs for connection to domestic TV and cassette recorder. (Programs can be SAVEd and LOAded on to a portable cassette recorder.)
- FREE course in BASIC programming and user manual.

Optional extras

- Mains adaptor of 600 mA at 9 V DC nominal unregulated (available separately—see coupon).
- Additional memory expansion boards allowing up to 16K bytes RAM. (Extra RAM chips also available—see coupon).

*Use a 600 mA at 9 V DC nominal unregulated mains adaptor. Available from Sinclair if desired (see coupon).

The unique and valuable components of the Sinclair ZX80.

The Sinclair ZX80 is not just another personal computer. Quite apart from its exceptionally low price, the ZX80 has two uniquely advanced components: the Sinclair BASIC interpreter; and the Sinclair teach-yourself BASIC manual.

The unique Sinclair BASIC interpreter offers remarkable programming advantages:

- **Unique 'one-touch' key word entry: the ZX80 eliminates a great deal of tiresome typing. Key words (RUN, PRINT, LIST, etc.) have their own single-key entry.**
- **Unique syntax check.** Only lines with correct syntax are accepted into programs. A cursor identifies errors immediately. This prevents entry of long and complicated programs with faults only discovered when you try to run them.
- **Excellent string-handling capability—takes up to 26 string variables of any length.** All strings can undergo all relational tests (e.g. comparison). The ZX80 also has string input-to request a line of text when necessary. Strings do not need to be dimensioned.
- **Up to 26 single dimension arrays.**
- **FOR/NEXT loops nested up to 26.**
- **Variable names of any length.**
- **BASIC language also handles full Boolean arithmetic, conditional expressions, etc.**
- **Exceptionally powerful edit facilities,** allows modification of existing program lines.
- **Randomise function,** useful for games and secret codes, as well as more serious applications.
- **Timer under program control.**
- **PEEK and POKE enable entry of machine code instructions.** USR causes jump to a user's machine language sub-routine.
- **High-resolution graphics with 22 standard graphic symbols.**
- **All characters printable in reverse under program control.**
- **Lines of unlimited length.**

Fewer chips, compact design, volume production—more power per pound!

The ZX80 owes its remarkable low price to its remarkable design: the whole system is packed on to fewer, newer, more powerful and advanced LSI chips. A single SUPER ROM, for instance, contains the BASIC interpreter, the character set, operating system, and monitor. And the ZX80's 1K byte RAM is roughly equivalent to 4K bytes in a conventional computer—typically storing 100 lines of BASIC. (Key words occupy only a single byte.)

The display shows 32 characters by 24 lines. And Benchmark tests show that the ZX80 is faster than all other personal computers.

No other personal computer offers this unique combination of high capability and low price.

Z80 A microprocessor—new, faster version of the famous Z-80 microprocessor chip, widely recognised as the best ever made.


Sockets for TV, cassette recorder, power supply.

SUPER ROM.

Clock. Rugged, flush, Sinclair keyboard.

RAM chips.

UHF TV modulator.

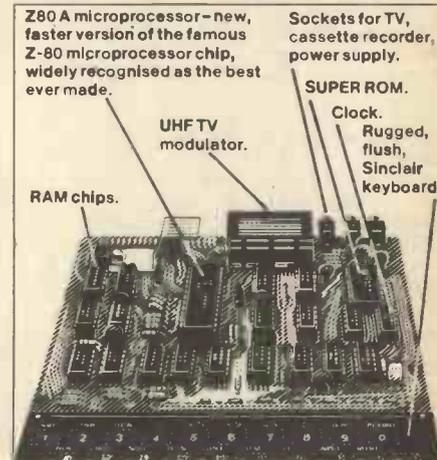

Marshall's

A. Marshall (London) Ltd., Kingsgate House,
Kingsgate Place, London NW6 4TA
Industrial Sales: 01-328 1009
Mail Order: 01-624 8582 24hr. service
Also retail shops: 325 Eridge Road, London W2
40 Cricklewood Broadway, London NW2 85 West Regent St., Glasgow
108A Stokes Croft, Bristol

We now supply the extremely reliable and cost conscious LEADER range of testgear.

SINGLE TRACE OSCILLOSCOPES		
LBO 510A 5" 4MHz 20mV		£125.00
LBO 512A 5" 10MHz 10mV		£170.00
LBO 513A 5" 10MHz 10mV		£215.00
LBO 507A 5" 20MHz 10mV		£739.00

DUAL TRACE OSCILLOSCOPES		
LBO 308S 3" 20MHz 20mV		£419.00
LBO 508A 5" 20MHz 10mV		£299.00
LBO 520A 5" 35MHz 5mV		£475.00
LBO 514 5" 10MHz 5mV		£265.00

TV RADIO TEST GEAR		
LSG 16 Signal Generator		£ 49.00
LSG 231 FM Stereo Signal Generator		£169.00
LCG 397U PAL B Pattern Generator		£189.00

AUDIO TEST GEAR		
LAG 26 Audio Generator		£ 60.00
LAG 120A Audio Generator		£119.00
LDA1 170 Distortion Meter		£225.00
LFA1 39A Wow Flutter Meter (Dist)		£249.00
LIA1 39A Wow Flutter Meter (Dist)		£299.00
LAV 191 Audio Tester		£249.00
LAG 125 Low Distortion Audio Generator		£229.00

GENERAL TEST GEAR		
LCR 740 LCR Bridge		£135.00
LTC 906A Transistor Checker		£ 90.00
LVT 72 FET Transistor Checker		£119.00
LTC 907 Transistor Checker		£139.00
LAT 47 Attenuator		£135.00
LAT 45 Attenuator		£ 75.00
LCG 1300 Sweep Function Generator		£299.00

AMATEUR RADIO		
LDM 815 DIP Meter		£ 43.00
LIM 870A Antenna Impedance Meter		£ 41.00
LPM 880 RF Power Meter		£ 69.00
LPM 885 SWR Watt Meter		£ 44.00
LAC 895 Antenna Coupler		£ 85.00
LAC 896 Antenna Coupler		£ 41.00
LAC 897 Antenna Coupler		£ 41.00

Please send large SAE for special catalogue. All prices exclusive VAT/carriage.

The new Marshall's 80/81 catalogue is now available. A veritable treasure house of components, test gear, tools, etc.



Lots of old friends, but also many new products including leader test gear, Crimson Hi Fi Modules, Rechargeable Ni Cad batteries and chargers (very competitive). More components including SN74ALS series, new tools etc. Available by post, UK 75p post paid: Europe 95p post paid: Rest of world £1.35 post paid.

SINCLAIR INSTRUMENTS

Digital Multimeter		
"	PDM35	£ 34.50
"	DM235	£ 52.50
"	DM350	£ 72.50
"	DM450	£ 99.00
Digital Frequency Meter		
"	PFM200	£ 49.80
Low Power Oscilloscope		
"	SC110	£139.00

NEW

TF200	Frequency Meter	
		£145.00
TGF105	Pulse Generator	
		£ 85.00

CRIMSON ELEKTRIK HI FI MODULES

CE608	Power Amp	£20.09
CE1004	"	£23.43
CE1008	"	£26.30
CE1704	"	£33.48
CE1708	"	£33.48
CPS1	Power Unit	£19.52
CPS3	"	£23.52
CPS6	"	£30.00
CPR1	Pre Amp	£32.17
CPR1S	Pre Amp	£42.52

All Prices + VAT + postage/packaging

Don't forget! We also carry an impressive range of semi-conductors, passive components, electro-mechanical components, tools etc.



TITAN TRANSFORMERS AND COMPONENTS
CENTRAL HALL CHAMBERS
GRIMSBY SOUTH HUMBERSIDE
MAIL ORDER ONLY
PAYMENT C.W.O. CHEQUES, POSTAL ORDERS
ALL PRICES INCLUDE 15% V.A.T.

PRINTED CIRCUIT BOARD TYPES

0-5v 0-5v

REF	AMPS	PRICE	P/P
TTP 448	0.5-2	1.79	50
TTP 447	0.75-2	2.14	60
TTP 449	1.0-2	2.38	70
TTP 450	2.08-2	2.99	85
TTP 451	4.18-2	4.57	120
TTP 452	8.33-2	5.68	120

0-9v 0-9v

REF	AMPS	PRICE	P/P
TTP 480	0.30-2	1.79	50
TTP 481	0.50-2	2.14	60
TTP 483	0.80-2	2.38	70
TTP 484	1.38-2	2.99	85
TTP 485	2.77-2	4.57	120
TTP 486	5.55-2	5.68	120

0v-12v 0v-12v

REF	AMPS	PRICE	P/P
TTP 467	0.25-2	1.79	50
TTP 468	0.38-2	2.14	60
TTP 470	0.50-2	2.38	70
TTP 471	1.04-2	2.99	85
TTP 472	2.08-2	4.57	120
TTP 473	4.18-2	5.68	120


0-15v 0-15v

REF	AMPS	PRICE	P/P
TTP 474	0.20-2	1.79	50
TTP 475	0.30-2	2.14	60
TTP 477	0.4-2	2.38	70
TTP 478	0.83-2	2.99	85
TTP 479	1.66-2	4.57	120
TTP 480	3.33-2	5.68	120

0-24v 0-24v

REF	AMPS	PRICE	P/P
TTP 495	0.13-2	1.79	50
TTP 496	0.19-2	2.14	60
TTP 498	0.25-2	2.38	70
TTP 499	0.52-2	2.99	85
TTP 500	1.04-2	4.57	120
TTP 501	2.08-2	5.68	120

TRANSFORMERS

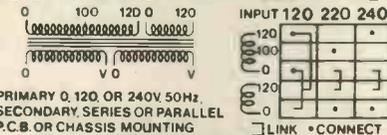

LINK *CONNECT

CHASSIS MOUNTING TYPES

REF	AMPS	PRICE	P/P
TTC 448	0.5-2	1.85	50
TTC 447	0.75-2	2.20	60
TTC 449	1.0-2	2.45	70
TTC 450	2.08-2	3.10	85
TTC 451	4.18-2	4.70	120
TTC 452	8.33-2	5.85	120

0v-9v 0v-9v

REF	AMPS	PRICE	P/P
TTC 467	0.25-2	1.85	50
TTC 468	0.38-2	2.20	60
TTC 470	0.50-2	2.45	70
TTC 471	1.04-2	3.10	85
TTC 472	2.08-2	4.70	120
TTC 473	4.18-2	5.85	120

0v-15v 0v-15v

REF	AMPS	PRICE	P/P
TTC 474	0.20-2	1.85	50
TTC 475	0.30-2	2.20	60
TTC 498	0.25-2	2.45	70
TTC 499	0.52-2	3.10	85
TTC 500	1.04-2	4.70	120
TTC 501	2.08-2	5.85	120

0-24v 0-24v

REF	AMPS	PRICE	P/P
TTC 495	0.13-2	1.85	50
TTC 496	0.19-2	2.20	60
TTC 498	0.25-2	2.45	70
TTC 499	0.52-2	3.10	85
TTC 500	1.04-2	4.70	120
TTC 501	2.08-2	5.85	120

MAINS ADAPTORS		
3 PIN 13AMP PLUG IN ADAPTORS, MADE IN U.K.		
REF	OUTPUT	PRICE P/P
TT 100	6-7.5-9v	3.85 40
TT 101	6-7.5-9v	4.70 80

COMPONENTS		
TYPE	QTY	PRICE P/P
BRIDGE 1A 50V	5	85 10
IN 4001	10	45 10
1000UF 25V	4	95 15
1000UF 16V	5	105 15
470UF 16V	5	85 15

SECURITY SENTRY/SENTINEL


If you are considering building either of these alarm systems save yourself time, aggravation and £££ by purchasing one of our kits. Each kit contains detailed step-by-step assembly and installation instructions and every item required to build an alarm control centre as illustrated in the articles. There are no extras to buy. Prices are all inclusive (U.K. only) and are valid for six months. Terms: CWO; Access and Barclaycard orders welcome.

SECURITY SENTRY (July Pe)	
SCA01	Security Sentry Alarm Control Centre. Includes: Silk screened and drilled case, drilled and tinned PCB, all PCB components, IC sockets, battery holder (less batteries) and all mounting hardware. £12.95
SCA/CPP01	Consists of the above kit and a caravan protection kit comprising: Siren, seven pin socket, magnet and reed switch, 20 Mtrs wire, wire staples & hardware. £26.70

SECURITY SENTINEL	
DAS01	Security Sentinel Alarm Control Centre. Comprising: silk screened & drilled case, silk screened, drilled & tinned PCB's, IC sockets, all PCB components, battery holder (less batteries), mains transformer, and all hardware. £45.95
DAS02	As above but includes nickel-cadmium batteries. £53.95
CS02	Siren Kit. (Can also be used with SCA01): Siren, 10 Mtrs wire, wire staples, and mounting hardware. £8.75
TMS01	Tri-Mode switch kit comprising: two magnet and reed switch assemblies, diode, resistors, & hardware. £1.95

Interested in a vehicle alarm system kit?? Write for details.
COMPU-TECH SYSTEMS
Laundry Loke Industrial Estate,
North Walsham, Norfolk
Tel: North Walsham 5600

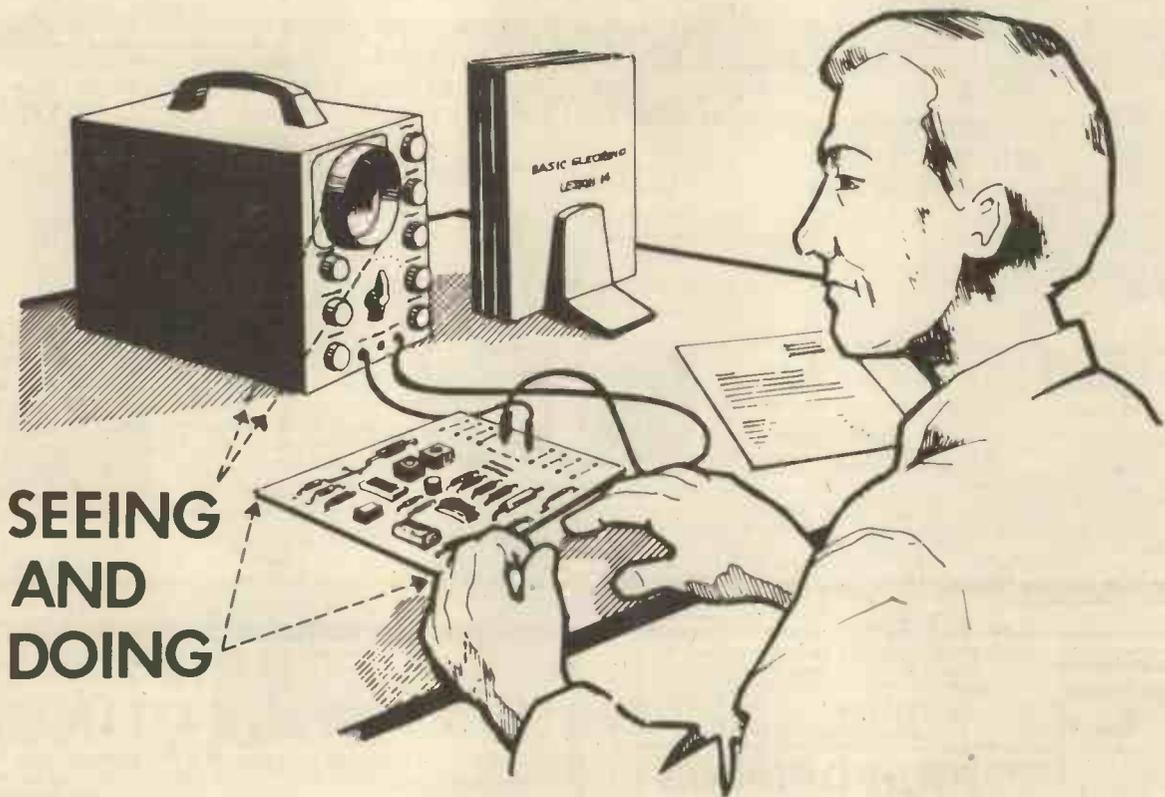Master Electronics the new Practical way.



SEEING
AND
DOING

Conquer the 'Chip' – Easy-Fast-Exciting !

AND MASTER ALL THE NEW TECHNIQUES
IN MODERN ELECTRONICS.

- Build an Oscilloscope.
- Carry out over 40 full experiments including work on Digital Electronic Circuits.
- Recognition of Electronic Components.
- Understand and draw Circuit Diagrams.
- Experience with handling Solid State Circuits and "Chips".
- Testing and Servicing of Radio, T.V., Hi-Fi and all types of modern computerised equipment.

Colour Brochure – without any obligation. Post to :-

PE/12/812

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL
4 Cleveland Road, Jersey, Channel Islands.

Name

Address

.....

.....

FREE

BLOCK CAPS PLEASE

NEW

PRACTICAL ELECTRONICS PROJECT 125 WATT POWER AMP KIT

SPECIFICATIONS

Max. Output power 125 watt RMS
 Operating voltage (DC) 50-80 Max.
 Loads 4-16 ohms
 Frequency response Measured at 100 watts 25Hz-20kHz
 Sensitivity for 100 watts 400mV @ 47K
 Typical T.H.D. @ 50 watts 4 ohms load 0.1 %
 Dimensions 205 x 90 and 180 x 36 mm

The P.E. power amp kit is a module for high power applications—disco units, guitar amplifiers, public address systems and even high power domestic systems. The unit is protected against short circuiting of the load and is safe in an open circuit condition. A large safety margin exists by use of generously rated components, the

output stage uses four 115 watt transistors normally only two would be used, result, a high powered rugged unit. The PC Board is backprinted, etched and ready to drill for ease of construction, and the aluminium chassis is preformed and ready to use, supplied with all parts and circuit diagrams.



£9.50 plus £1.00 p&p

125 watt power amp kit

ACCESSORIES

Suitable LS. coupling electrolytic

Suitable Mains Power Supply Unit sufficient for one power amp

£1.00 plus 20p p&p

£7.50 plus £2.75 p&p

AS FEATURED IN PRACTICAL ELECTRONICS OCTOBER ISSUE

DIY STEREO BARGAIN PACKS FEATURING FAMOUS BUILT MULLARD PREAMP MODULES

MULLARD STEREO PREAMP MODULES AND TWO 12 WATT POWER AMP KITS.



In easy to build form P.C.B.s backprinted, etched and drilled ready to use.

BUILD A 12 WATTS PER CHANNEL STEREO AMPLIFIER ACCESSORIES AND L.S. KIT EXTRA (not available separately)

£6.00

DIY PACK 1 2 x power amp kits LP1182/ preamp module, suitable for ceramic and auxiliary inputs

£6.00 plus £1.10 p&p

DIY PACK 2 2 x power amp kits LP1184 preamp module suitable for magnetic ceramic and auxiliary inputs.

£8.50 plus £1.15 p&p

DIY SPEAKER KIT Two 8" x 5" approx. 4 ohm bass.

£3.50 plus £1.70 p&p



DIY ACCESSORIES Mains transformer smoothing capacitor rectifier 4 x slider controls, for base, treble and volume.

£3.00 plus £1.60 p&p

ACCESSORIES: Available only at time of purchase of Bargain Packs

12 + 12 WATT AMPLIFIER KIT

NOTE: for use with 4 to 8 ohms speakers.

With up-to-the-minute features. To complete you just supply screws, connecting wire and solder. Features include din input sockets for ceramic cartridge, microphone, tape or tuner. Outputs—tape, speakers and headphones. By the press of a button it transforms into a 24 watt mono disco amplifier with twin deck mixing. The kit incorporates a Mullard LP1183 pre-amp module, plus 2 power amplifier assembly kits and mains power supply. Also featured 4 slider level controls, rotary bass and treble controls and 6 push button switches. Silver finish fascia panel with matching knobs. Easy to assemble teak simulate cabinet and ready made metal work. For further information instructions are available price 50p. Free with kit. Size 9 1/4" x 8 3/4" x 4" approx.

£13.95 plus £2.55 p&p

NOTE: for use with 4 to 8 ohms speakers.

BSR chassis record deck with manual set down and return, complete with stereo ceramic cartridge



£8.50 plus £2.75 p&p when purchased with amplifier. Available separately **£10.50** plus £2.75 p&p.

8" SPEAKER KIT. 2 Philips 8" approx. speakers **£4.75** per stereo pair plus £1.50 p&p when purchased with amplifier. Available separately **£6.75** plus £1.50 p&p.

STEREO MAGNETIC PRE-AMP CONVERSION KIT all components including P.C.B. to convert your ceramic input on the 12 + 12 amp to magnetic. **£2.00** when purchased with kit featured above. **£4.00** separately inc p&p.




BSR Manual single play record deck with auto return and cueing lever. Fitted with stereo ceramic cartridge 2 speeds with 45 rpm spindle adaptor ideally suited for home or disco use.



£12.25 OUR PRICE plus £2.75 p&p Size approx 13" x 11"

PHILLIPS RECORD PLAYER DECK GC037

Size approx 15 1/4" x 12 1/4"

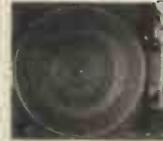

Hi Fi record player deck, 2 speed, damped cueing, auto shut-off, belt drive with floating sub chassis to minimise acoustic feedback. Complete with GP 401 stereo magnetic cartridge—LIMITED STOCK. UNBEATABLE OFFER AT

£27.50 complete plus £2.75 p&p

OFFER! SAVE MONEY by purchasing 12 + 12 amp kit, BSR record deck and speaker kit together for only **£25.50** p&p £4.50.

PRACTICAL ELECTRONICS CAR RADIO KIT

£10.50

(Constructors pack 7)

plus £1.75 p&p



2 WAVE BAND MW LW

- * Easy to build * 5 push button tuning
- * Modern styling design * All new unused components
- * 6 watt output * Ready etched & punched P.C.B.
- * Incorporates suppression circuits * Now with tape input socket

All the electronic components to build the radio, you supply only the wire and solder as featured in the Practical Electronics March issue. Features: Pre-set tuning with five push button options, black illuminated tuning scale, with matching rotary control knobs, one, combining on/off volume and tone-control, the other for manual tuning, each set on wood simulated fascia. The P.E. Traveller has a 6 watts output, neg ground and incorporates an integrated circuit output stage, a Mullard IF module LP1181 ceramic filter type, pre-aligned and assembled and a Bird pre-aligned push button tuning unit. The radio fits easily in or under dashboards.

Complete with instructions

CONSTRUCTORS PACK 7A

Suitable stainless steel fully retractable locking aerial and speaker (approx. 6" x 4") is **£1.95** per pack, available as a kit complete **£1.00** p&p £1.00

Pack 7A may only be purchased at the same time as Pack 7.

NOTE: Constructor's pack 7A sold complete with radio kit **£15.20** including p&p.

FEATURED PROJECT IN PRACTICAL ELECTRONICS.



30 + 30 WATT STEREO AMPLIFIER BUILT AND TESTED

Viscount IV unit in teak simulate cabinet silver finished rotary controls and pushbuttons with matching fascia, red mains indicator and stereo jack socket. Functions switch for mic magnetic and crystal pickups, tape and auxiliary. Rear panel features fuse holder, DIN speaker and input socket 30 + 30 watts. RMS 60 + 60 watts peak for use with 4 to 8 ohm speakers. Size 14 1/2" x 10" approx.

READY TO PLAY **£32.90** plus £3.30 p&p



323 EDGWARE ROAD, LONDON W2
 21B HIGH STREET, ACTON W3 6NG

ACTON: Mail Order only. No callers
ALL PRICES INCLUDE VAT AT 15%
 All items subject to availability. Prices correct at 1.10.80 and subject to change without notice.
 For further information send for instructions

NOTE: 20p plus stamped addressed envelope.
 Persons under 16 years not served without parent's authorisation.

BARGAIN OFFER!!



ARISTON PICK UP

Ariston pick-up arm manufactured in Japan. Complete with headshell. Listed price over £30.00

£11.95

OUR PRICE plus £2.50 p&p

100 WATT MONO DISCO AMPLIFIER

Brushed aluminium fascia and rotary controls. Size approx 14 1/2" x 4 1/2" x 10 1/2". Five vertical slide controls, master volume, tape level, mic level, deck level. PLUS INTER DECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre fade level controls (PRL) lets YOU hear next disc before fading it in. VU meter monitors output level. Output 100 watts RMS 200 watts peak.

£76.00 plus £4.00 p&p

50 WATT MONO DISCO AMPLIFIER

Size approx 13 1/2" x 5 1/2" x 6 1/2". 50 watts rms. 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume



£30.60 plus £3.20 p&p

BREADBOARD

PROVIDING there are no last minute production or distribution hiccups with this issue (after our industrial problems earlier in the year we only managed to get back on schedule last month) you could be reading this in time to make plans to visit Breadboard '80. Odd though the name is we are sure nearly every enthusiast will by now be aware that the Breadboard exhibition caters for all those interested in electronics as a hobby.

Once again *PE* will be exhibiting, in our own rather unpretentious manner. We will be very pleased to meet any readers that care to come along, and of course, we will have a number of projects on show—many of them operational. We will also be selling past (back to August '80) and present copies and our own book *PE Popular Projects*.

Some of the items we expect to have working are: *PE Teletext*, *PE Master Rhythm*, *PE Starspinner* (see page 31), a speech synthesiser (see page 44), *PE Congress Hi-Fi Amp*, *Compukit Sound Generator*, etc. We will also be showing many items of test gear including the *PE Microtune* (see page 26) and the range of in-car entertainment equipment from our special

offer on page 24 (this equipment **will not** be available to purchase from the stand). So if you want to see any of these items or if you just want to chat, come and find us on stands E3 and E4.

If last year is anything to go by, a weekday is best and make sure you bring earplugs and a loud voice! Might we suggest that you also bring plenty of money as there have been many exhibition offers on retailers stands in past years and you could find some bargains.

AVAILABILITY

Many readers have informed us that they have problems buying recent issues—some have been told that we have not published certain issues, one man even rang recently to ask if *PE* had ceased publication! Let us make it quite clear that we have published every issue this year—although some were more than a month late.

One of the problems is that these days the newsagents are watching their finances and are not prepared to stock more issues than they are sure they can sell. This means that they often sell out early and few spare copies of any issue are available. In order to make sure of your issue, may we suggest you place an order with your

newsagent and ask for your copy if it fails to arrive.

SPECIAL ISSUES

The availability problem becomes more acute when we have a special issue, gift or extra supplement etc.. This issue carries the Electrovalve catalogue free with all UK copies and next month the issue will carry a free 132 page Tandy catalogue, banded to it. These free catalogues do increase demand for issues so please don't miss out! You have been warned! We are also planning special issues for March, April, May and June and we expect our February issue to be in demand because we hope to cover the electronics incorporated in an entirely new and quite revolutionary luxury British car, which should be launched after Christmas.

For some time *PE* contributors have been involved in the development of instruments and a locking system for this £65,000 plus vehicle. We will be describing the development of these instruments and showing how to make similar items to fit rather more mundane vehicles. We can't reveal what the car is or what it looks like yet, but "stay tuned" for full details.

Mike Kenward

EDITOR

Mike Kenward

Gordon Godbold ASSISTANT EDITOR

Mike Abbott TECHNICAL EDITOR

David Shortland PROJECTS EDITOR

Jasper Scott PRODUCTION EDITOR

Jack Pountney ART EDITOR

Keith Woodruff ASSISTANT ART EDITOR

John Pickering SEN. TECH. ILLUSTRATOR

Isabelle Greenaway TECH. ILLUSTRATOR

Colette McKenzie SECRETARY

Editorial Offices:

Practical Electronics,
Westover House,
West Quay Road, Poole,
Dorset BH15 1JG
Phone: *Editorial* Poole 71191

We regret that lengthy technical enquiries cannot be answered over the telephone (see below).

Advertising Offices:

Practical Electronics Advertisements,
King's Reach Tower,
King's Reach, Stamford Street, SE1 9LS
Telex: 915748 MAGDIV-G

Make Up/Copy Dept.: 01-261 6601

ADVERTISEMENT MANAGER

D. W. B. Tilleard

SECRETARY **Christine Pocknell**

} 01-261 6676

AD. SALES EXEC. **Alfred Tonge** 01-261 6819

CLASSIFIED MANAGER **Colin Brown** 01-261 5762

Technical Queries

We are unable to offer any advice on the use or purchase of commercial equipment or the incorporation or modification of designs published in Practical Electronics.

All letters requiring a reply should be accompanied by a stamped, self addressed envelope and each letter should relate to one published project only.

Components are usually available from advertisers; where we anticipate supply difficulties a source will be suggested.

Back Numbers

Copies of most of our recent issues are available from: Post Sales Department (Practical Electronics), IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF, at 95p each including Inland/Overseas p&p.

Binders

Binders for *PE* are available from the same address as back numbers at £4.30 each to UK or overseas addresses, including

postage and packing, and VAT where appropriate. Orders should state the year and volume required.

Subscriptions

Copies of *PE* are available by post, inland or overseas, for £11.80 per 12 issues, from: Practical Electronics, Subscription Department, Oakfield House, Perrymount Road, Haywards Heath, West Sussex RH16 3DH. Cheques and postal orders should be made payable to IPC Magazines Limited.

Market Place


Items mentioned are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned. All quoted prices are those at the time of going to press.

by
David Shortland

and
Jasper Scott

ECONOMIC SCOPE

The new Model SB 3M oscilloscope from Albol Electronic will serve most purposes required by industrial, service and hobby engineers, and yet manages to keep on the right side of the significant £100 price barrier. With a bandwidth of 0 to 3MHz at -3 dB (extending to 6MHz at -6 dB), the SB 3M breaks new ground, in its class, by offering time-base automatic triggering by i.c. comparator control of the type usually fitted only to luxury scopes. A 10 mV signal is all that is needed for a firmly locked and triggered time-base.

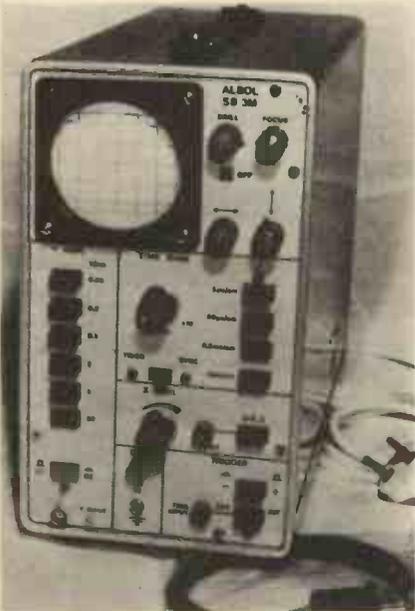

The measuring field on the c.r.t. is 50 by 60mm, and the deflection sensitivities are selectable (by push-button) from 0.05 to 20 V/cm. Calibration accuracy is ± 5 per cent. Albol say that the input characteristics are 1 megohm ± 5 per cent, and 30 pF ± 10 per cent. The time-base can be either automatically triggered or synchronised, and it has four switch-selectable calibration speeds, from 1 μ s/cm to 5 ms/cm. A six-stage attenuator, from $\times 1$ to $\times 10$, can be applied to each.

Triggering, which can be either internal or external, can be polarised positive or negative, in the range 10Hz to 500kHz. If internal synchronisation is used the range extends from 10Hz to 3MHz. The internal trigger threshold is 5 mV, and the external 100 mV.

The SB 3M takes about 20 watts from the 240V mains, weighs 4.5kg, and measures 150mm wide by 340mm deep by 280mm high. The price is £99.00, plus VAT; delivery is ex-stock.


Albol Electronic & Mechanical Products Ltd., 3 Crown Buildings, Crown St., London SE5 0JR (01-703 2311).

MICRO BREADBOARD

The first Eurocard size breadboarding system designed specifically for microprocessor based circuit designs will be launched at this year's Breadboard Exhibition by Boss Industrial Mouldings Ltd.

Comprising a central MPU Section capable of accommodating a mixture of 24, 28, 40 and 64 pin microprocessors, and flanked on both sides by Auxiliary breadboarding sections for RAM's, ROM's and peripheral chips, this 'world first' system enables complex designs to be rapidly built whilst keeping interconnection

link lengths to an absolute minimum. Dual and single bus strips on all sides, plus 5 incoming power line turret terminals all contribute to make this remarkably versatile and rugged breadboarding system. Easily replaceable, double sided, nickel silver contacts, rated at 1A and typically 10m ohms resistance will accept a wide range of lead sizes enabling d.i.l. i.c.'s transistors, resistors, capacitors and diodes etc to be readily plugged in. The rigid High Impact Polystyrene body is rated up to 75°C and has non-slip rubber backing for working stability.

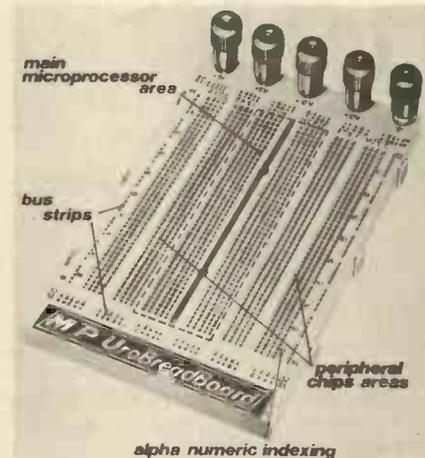


Capable of accepting .3", .4", .5" and .6" pitch d.i.l. packages without needlessly wasting auxiliary pin positions and breadboarding areas, every contact is alpha-numeric indexed, this being imperative for education and training applications where step-by-step build-up instructions are used.

Boss Industrial Mouldings Ltd, 2 Herne Hill Road, London SE24 0AU (01-731 2383).

SUPER STRIPPER

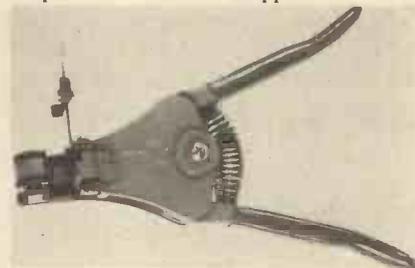Tele-Production Ltd. have recently come up with a simple but effective wire stripper, the Telpro Automatic Wire Stripper.




A single squeeze operation strips the insulation from single and stranded wires without damage. Its wide jaws permit fast and accurate stripping without any nicking or scraping of the wire and a gauge is supplied to ensure consistent lengths of stripping during fast production work. Five diameters of wire can be used on this tool, which has the following size cutter: 1.0, 1.6, 2.0, 2.6 and 3.2mm. Of an all metal construction, it is available ex stock priced £10.50.

Also available from Tele-Productions is a new p.c.b. holder with a quick release trigger which allows a p.c.b. to be removed and replaced in seconds. There is also a special attachment which when fitted to the holding arms of the unit can be repositioned to hold

small components such as switches etc., during soldering.

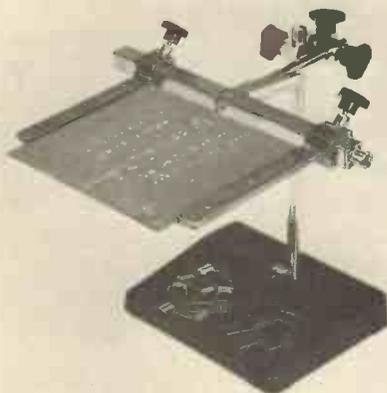The unit can hold boards up to 12in long and can revolve through 360 degrees. The quick release trigger works by spring tension which can be adjusted. The diecast base of the holder incorporates two trays for holding components.



The MPC 2 Holder is priced at £30.00 excluding VAT and p&p.

Tele-Production Tools, Stiron House, Electric Avenue, Westcliff-on-Sea, Essex SS0 9NW. (0702 352719).

4½ Digit DMM

The new 4½ digit multimeter from Thurlby Electronics has a scale length of 32,768 counts (± 15 bits). This extra resolution enables it to monitor a 1mV change in a 30 volt power rail, for instance, when a 4½ digit meter would be limited to 10mV, and a 3½ digit meter to 100mV. In addition, the high resolution virtually eliminates inaccuracy caused by digitising error since this is reduced by 0.003 per cent of full scale, compared to the basic accuracy figures of 0.05 per cent of reading.



Thirty measuring ranges are provided covering the five basic functions of d.c. and a.c. voltage, d.c. and a.c. current, and resistance. In addition, diode test and frequency measurement functions are included. Frequency measurement is achieved via a crystal controlled timebase, and is particularly useful for monitoring oscillators or checking microprocessor clock frequencies, etc. Maximum reading is 3999.9kHz with overflow to 7MHz.

The 1503 is housed in a high impact ABS case with a six-position tilt stand which doubles as a carrying handle. Although primarily intended as a laboratory instrument, very low

power circuitry gives it 200 hours of operation from batteries, enabling it to be used as a fully portable field service multimeter. This low power consumption circuitry also eliminates drifts caused by internal heat generation and improves long term stability.


The price of the 1503 is £139 ex VAT and p&p.

Thurlby Electronics Ltd. Coach Mews, St. Ives, Huntingdon, Cambs. PE17 4BN.

LUCKY DIPS

The latest range of dual-in-line sockets from OK Machine & Tool for pluggable packaging of integrated circuits includes 8, 14, 16, 18, 20, 24, 28, 36 and 40 pin configurations with standard 0.1in (2.54mm) in-line spacing.

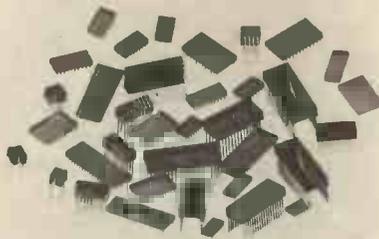Virtually all SS1, MS1 and LS1 devices can be accommodated and in the case of the wire wrap versions the pins are suitable for three-level wire wrapping. The insulations are made of glass filled thermoplastic polyester and contacts are phosphor bronze. Pins are gold plated over nickel.



These sockets are complemented by a range of cable assemblies of varying lengths, to provide a high number of contacts in the minimum of space, together with high density 28-pin input/output sockets and plugs conforming to the basic 0.01in x 0.01in grid layout.

For further information, contact: OK Machine & Tool (UK) Ltd., Dutton Lane, Eastleigh, Hants SO5 4AA. (0703 610944)

VERO CASE

A pocket, hand-held box, ideal for housing remote control handsets, instruments etc., is the latest addition to the Vero range of cases.

It incorporates a 20x50mm cut-out slot which may be used for fitting panels or switches and a 12x35mm recessed panel for labelling. A circuit board 71x107mm can be accommodated in the top section of the two



part body by the use of four self-tapping screws, whilst the bottom section will house a board of 56x105mm. The two sections snap together and are secured by four screws through the base. There is an integral battery compartment which will accept a PP3 or a nickel cadmium stack of 25x45mm, it has a slide-off cover which allows easy access.

The price of the case is £12.47 excluding VAT and p&p.

Vero Electronics Limited, Industrial Estate, Chandler's Ford, Eastleigh, Hants SO5 3ZR.

AMBIT

Four new compact modules from Ambit can provide the ideal solution to many MPU data output decoding and display requirements.

Two versions (DM180/1) provide simultaneous decoding and display from multiplexed b.c.d. inputs. Additional options allow for either Hex or Code B displays. The DM180/1 will operate over a voltage range of 3.5V to 6V at 20µA in either the 3.5 or 4 digit display format.



The DM182/3 provides decoding and display using serial data inputs compatible with many types of MPU. At operating voltages of 3V to 15V current consumption is typically 60µA.

The modules which are priced at £10.99 excluding VAT and p&p measure 60x30x7mm and 12.5mm l.e.d.s with integral backlighting can also be supplied.

Ambit International, 200 North Service Road, Brentwood, Essex. (0277 230909).

A TO D INTERFACE

The ADC 1660 is a high speed 16 channel analogue to digital interface board which will connect directly into a standard Acorn 64 DIN bus. The unit provides A to D conversion of 16 inputs at a rate of 16K conversions per second to 8-bit resolution.

To the processor the card appears as a block of 16 memory locations which by using 12 d.i.l. switches can be placed in any of 4000 positions in a 64K map. No special software is required to control the interface, a write pulse from the processor to any of the 16 memory locations loads the analogue multiplexer with the four low order address bits and initiates the conversion sequence. Sample and hold timing is carried out on board and 60 microseconds later the conversion is complete. The processor can time out or an interrupt from the card can inform it that data is available to be read from the same memory location that was written to.

At present the ADC 1660 is available in eurocard form with a 64 way indirect connector for the Acorn bus, but can be link programmed to suit any other 64 way bus.

The ADC 1660 costs £82.00 in kit form, or ready assembled and tested with front panel and 34 way connector for £110.00.

Stoneage Electronics, The Cottage, 70 Albion Drive, London, E8 4LX. (254 4727).


The NEW

VIDEOTONE

YOU CANNOT BUY CHEAPER - YOU CAN ONLY GET LESS FOR YOUR MONEY!

Introduces DIRECT SELLING - the Ultimate Discount!!!

DISCOUNT SELLING PRICE
£50.00

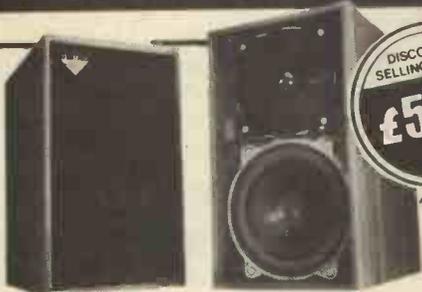

LOUDSPEAKERS

The complete fully reviewed range of Videotone Speakers which dominate within their class. Now at lowest ever prices.

D 100	£38
Minimax 11	£44
GB3	£50
GB2	£60
GBS	£207
D 93	£40

DISCOUNT SELLING PRICE
£68.00



ELECTRONICS

This new range of Electronics from Videotone redefines the words quality and value for money to a new high.

30 watt amp MC input SA4130	£75.00
Stereo Tuner ST4120	£68.00
Cassette full features SC3200	£98.00
50 Watt amplifier WA7700	£77.00
20 Watt amplifier LA2020	£58.00

DISCOUNT SELLING PRICE
£75.00

DISCOUNT SELLING PRICE
£9.69



HEADPHONES

HP 90 Headphone	£12.65
HP 80 Headphone	£9.69

Superbly made with top flight performance.

VIDEOTONE

ALL PRODUCTS ON DISPLAY & CONTINUOUS DEMONSTRATIONS

ALL PRICES INCLUDE VAT

CORAL CARTRIDGES

Fast becoming one of the top names

MOVING COIL

UK's No. 1 Cartridge

MC 81	£48.87
777EX	£35
777E	£25

MOVING MAGNET

555SX	£7.28
555E	£14.22
666E	£32.48



HEAD AMP

H300	£51.75
T100	£24.75

HEADSHELLS

S100	£6
S101	£7
S200	£4



MICROPHONES

MU 105-22	£29.30
MU 105-12	£22.25
MU 25 C	£17.39

TURNTABLES

Sansui SR222 Mk2	£69.00
JVC LA 11	£64.00
JVC SLQ 3	£140.00

A MESSAGE FROM VIDEOTONE


Dear Customer

You will find that the products advertised on this page are the best possible value for money. They are only low in price because we have eliminated large amounts of selling costs that other brands have to suffer. These savings are passed directly on to you. We have full brochures on any specific item you may be interested in and a competent realistic staff of engineers at our London Showrooms to help you in your choice. Our consumer protection packages are comprehensive and we offer every form of financing you may require. We carry out our own servicing and are dedicated to giving Value for Money. We are confident our products are unbeatable. You may purchase with confidence because our Engineers have specially selected them from competitive sources throughout the world and we import them directly ourselves. Remember, you have 21 days trial period on all products. That is the measure of our confidence.

Videotone

SEND FOR OUR LATEST FREE BROCHURE

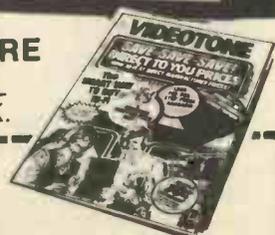AND DETAIL LIST OF LOCAL SALES OUTLETS IN THE U.K.




VIDEOTONE
98 CROFTON PARK ROAD,
CROFTON PARK, LONDON SE4
Tel: 01-690 8511/2

Please send me your Direct Selling Brochure and list of sales outlets.

Name _____

Address _____

PE/12/80

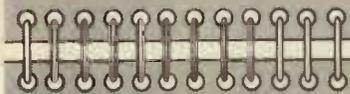

INDUSTRY NOTEBOOK

By Nexus



New Year

The political New Year which opened traditionally with the Political Party and Trade Union conferences has every promise of turbulence. Criticism of Government policy reached a new crescendo, as might be expected, but with a remarkable reversal of roles.

It takes a bit of getting used to when we see the more radical forces of the left becoming the new conservatives, with the reactionaries of the right making the pace in forcing radical change.

We all realise that politicians and trade union leaders need to make their views known in reasonable force but their choice of words and phrases is hardly consistent with fact. Thus, while everyone admits the need for change in industrial performance, we have seen the verbal description of such change progress from the neutral and moderate term rationalisation to restructuring, and now to the destruction of industry. Similarly, the population over the same period has moved from a comparatively mild state of misery, via suffering and sacrificing, to the ultimate crucifixion. The medical metaphor is also much in vogue, particularly on the delicate question of whether the cure will kill the patient.

Listening to the Jeremiahs you might imagine that the whole nation is in extremity whereas the truth is that the areas and industries most affected by the need for change have been problem areas and problem industries for decades and no government yet has found a satisfactory solution for them or is likely ever to do so.

On the broad economic front industry shows no sign of 'destruction' although, naturally, it is feeling the effect of economic squeeze at home and world recession abroad. Exports have been comfortably ahead of imports during past months and the aerospace and electronics industries are not only buoyant but have record order books. Overall, manufacturing industry output has declined seven percent over a

period of a year which embraced crippling strikes in engineering and steel. In the circumstances a creditable performance.

On crucifixion, incomes have kept ahead of inflation and personal savings are near, if not at, an all-time high. And those wanting a late continental holiday were disappointed to find planes fully booked. Of course there is inconvenience, even hardship, deserving of every sympathy and assistance in individual cases, but even these hardly merit the 'crucifixion' label.

Employment

Employment is the most emotive issue, especially when presented in lurid terms as unemployment in numbers of people rather than percentage of the total workforce. The electronics industry finds itself in a unique position in this delicate area by simultaneously creating new jobs in a new industry while destroying existing ones in long-established industries.

Every new advance in industrial automation developed by electronic engineers and fabricated in an electronics plant has had a single purpose, that of increasing productivity per unit cost elsewhere. Thus, to give but one example, a battery of programmable numerically-controlled machine tools could, in theory, be supervised by a single operator rather than having a skilled manual operator for each machine. One of the tragedies of British industry over the immediate past years is that the attitude to such changes in manufacturing practice has been little different from that of the Luddites of 169 years ago. Hence, the tardy progress in modernisation and excesses in over-manning which are now being rectified at considerable social cost to the individual and to the nation as a whole.

At the same time the electronics industry itself has had to readjust to new work patterns resulting in changes of technology as well as to variations in markets. On the latter, one notes that the small-boat radar business of Decca is being discontinued by Racal, new owners. This is no surprise and is a result of being unable to compete commercially with Asian manufacture. Some 350 jobs are said to be at stake but transfers to more profitable areas within the Racal group and imminent retirement of other Decca people will ease the blow and enable most to be absorbed.

Improved technology rather than lack of market is said to be the reason for Thorn cut-backs at their consumer electronics plant at Colwick. The TX9 and TX10 television chassis were designed for easier assembly. Not only are there far fewer components (through LSI) but automated insertion means that assembly is far less labour-intensive.

In fact the number of people in electronics goods manufacture is increasing but only at a fraction of the rate of growth of cash turnover. There is still an increasing demand for engineers and technicians but the armies of girl assemblers once needed for wiring up and soldering are no longer required. The circuits are now supplied already wired in the shape of ICs and LSI

from the semiconductor manufacturers, interconnected in PCBs, and are machine soldered in final assembly.

One can't help reflecting on the good fortune that the British electronics industry has remained comparatively free from Luddite attitudes, otherwise it would not and could not exist today.

Forecast

At the risk of treading hazardous ground I still forecast continuing prosperity for the electronics and aerospace industries. I include aerospace because of its huge electronic content. The two are interdependent, especially in the higher and more sophisticated branches of technology.

There will still be ups and downs, mainly in consumer electronics (a perennial problem) but taken as a whole, growth curve has got to be upwards.

I base this assessment on past and present performance of the larger well established companies on which, like the motor industry, many smaller companies feed, and on continuing investment such as the £8.5 million recently announced for expansion of GIM's plant at Glenrothes. There is also heartening news from Immos with a promising development in a 16k static ram although we must wait to see how technical design is converted to production and sales.

Another favourable indicator is the exhibition scene. The Farnborough Air Show was the best for many years. The production equipment Internecon show in its new home at the Brighton Conference Centre has 400 exhibitors, the greatest number yet. Also new to Brighton this year (from London) was the International Broadcasting Convention packed with professional studio and transmitting equipment from a whole gamut of companies from Acron Video to Zoom Television. Across the channel in Paris the British-run Automatic Testing 80 was also a success with a complete sell-out of space and record attendance.

There is every reason for cheer in high technology industries. They are actively doing, not just talking. They are also crying out for young numerate, literate and scientifically-minded recruits. And yet the National Union of Teachers and the Schools Council are reported as criticising the proposed core curriculum which calls for a minimum number of hours per week to be devoted to study—of what? You guessed right first time, the study of mathematics, English and science.

It is now abundantly clear that technology is the road forward. And this is the area where we can and do sell profitably to all countries including our own. Not only electronics but in other high technology areas, too.

I remain optimistic, at least for the technology-based industries. But even taken overall, for all industries, our export performance has consistently improved in cash terms over the years, more than doubling in the 'difficult' years of 1975-79. As I have often said in this column, the real high-fliers do well in good times and bad and there is plenty of life in the old dog yet.



MUSICAL MICRO 24 TUNE DOOR BELL



BUILD THE WORLD FAMOUS CHROMA-CHIME

Give your friends a warm welcome. Yes, think how delighted and amazed they will be to hear the musical Chroma-Chime play when they press your button!

The Chroma-Chime uses a microcomputer to play 24 well-known tunes. The kit is simplicity itself for ease of construction. Absolutely everything needed is supplied, including:

- ★ Resistors, Capacitors, Diodes, Transistors, I.C. Socket and all hardware
- ★ Texas Instruments TMS 1000 microcomputer
- ★ Comprehensive kit manual with full circuit details
- ★ Ready drilled and legended PCB included

**ONLY
£11.95
+ 75p p&p
UK ONLY**

Plays 24 well-known tunes including:

Star Spangled Banner, William Tell Overture, Greensleeves, Rule Britannia, Colonel Bogey, Oh come all ye faithful, plus many other popular tunes.

- ★ No previous microcomputer experience necessary
- ★ All programming retained is on chip ROM
- ★ Fully guaranteed
- ★ Ideal present any time

TMS 1000N



MP0027A Micro-computer chip available separately if required. Full 24 tune spec device fully guaranteed.

This unique chip can be used not only for electronic door chimes but for other projects requiring musical output:
Car Horns Musical Boxes Alarms
Amusement Machines Public Address etc
Free applications manual and data supplied with device
(10/200 components)

£4.95

ALL CHROMATRONICS PRODUCTS SUPPLIED WITH MONEY BACK GUARANTEE
PLEASE ALLOW 7-21 DAYS FOR DELIVERY
CHROMATRONICS, RIVER WAY, HARLOW, ESSEX.

Please send me:

TO: CHROMATRONICS, RIVER WAY, HARLOW, ESSEX.
Telephone (0279)418611

NAME _____ PE/12/80

ADDRESS _____

I enclose cheque/PO value £ _____
or debit my ACCESS/BARCLAYCARD account no. _____

Signature _____

CHROMATRONICS



Wilmslow Audio

THE firm for speakers!

SEND 50p FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST.

- AUDAX ● AUDIOMASTER ● BAKER ●
BOWER & WILKINS ● CASTLE ● CELESTION
● CHARTWELL ● COLES ● DALESFORD ●
DECCA ● EAGLE ● ELAC ● EMI ● FANE ●
GAUSS ● GOODMANS ● HARBETH ●
ISOPHON ● I.M.F. ● JORDAN ● JORDAN
WATTS ● KEF ● LOWTHER ● MCKENZIE ●
MISSION ● MONITOR AUDIO ● MOTOROLA
● PEERLESS ● RADFORD ● RAM ● ROGERS ●
RICHARD ALLAN ● SEAS ● SHACKMAN ● STAG
● TANNOY ● VIDEOTONE ● WHARFEDALE ●

**WILMSLOW AUDIO (Dept. P.E.)
SWAN WORKS, BANK SQUARE, WILMSLOW,
CHESHIRE SK9 1HF**

Tel: 0625 529599
FOR MAIL ORDER & EXPORT OF DRIVE UNITS, KITS ETC.
Tel: 0625 526213
(SWIFT OF WILMSLOW) FOR HI-FI & COMPLETE SPEAKERS

PARNDON ELECTRONICS LTD.

44 Paddock Mead, Harlow, Essex. CM18 7RR. Tel: 0279 32700 (Dept. No. 21)

RESISTORS: 1/4 Watt Carbon Film E24 range ± 5% tolerance. High quality resistors made under strictly controlled conditions by automatic machines. Banded/layered and colour coded
£1.00 per hundred mixed. (Min 10 per value)
£8.50 per thousand mixed. (Min 50 per value)
Special stock pack. 60 values. 10 off each £5.50

DIODES: IN4148 3p each. Min order quantity - 15 items
£1.60 per hundred

DIL SWITCHES: Gold plated contact in fully sealed base - solve those programming problems.
4 Way 86p each. 6 Way £1.00 each. 8 Way £1.20 each.

DIL SOCKETS: High quality, low profile sockets.
8 pin - 10p. 14 pin - 13p. 16 pin - 15p. 18 pin - 19p. 20 pin - 25p.
22 pin - 29p. 24 pin - 35p. 28 pin - 39p. 40 pin - 57p.

ALL PRICES INCLUDE V.A.T. & POST & PACKING - NO EXTRAS
MIN ORDER - UK. £1.00. OVERSEAS £5 CASH WITH ORDER PLEASE



THIS MONTH'S SNIP!

"Let us quote for your hard to get components for PE projects"

CLAIREX CL705HL — £4.50 ea.
PMI REF 02 — £4.00 ea.

RS ITEMS A SPECIALITY!

Send s.a.e. for priced parts list of PE projects
(max. 4) stating month and project title.

ACE MAILTRONIX LTD
Dept. PE, 3A Commercial St.
Bately, W. Yorks. WF17 5HJ



I enclose 30p* please send catalogue

name _____

address _____

*refundable with future order over £5.00

Semiconductor UPDATE...

FEATURING

IMS 1400 EF9365

R. W. Coles

THANKS FOR THE MEMORY

At last our very own "Silicon Valley" Company, Inmos, has lifted a corner of the veil to reveal a glimpse of the goodies to come.

In fact, the "Silicon Valley" tag with its California connections is not strictly accurate since the action is actually spread between plants in Colorado Springs, Colorado, U.S.A. and Bristol, Avon, U.K., with future production facilities scheduled for a site in South Wales. But apart from its geographical position(s) the Inmos outfit is every inch a progeny of "Silicon Valley", deeply engaged in the business of producing innovative yet practical microcircuits aimed at capturing a big slice of the billion dollar market of the 1980s. It would be terrifying really, if it were not for the fact that they are doing it all for us, the poor old British taxpayers! Everyone who knew anything about the deal must have been worrying a lot about the investment of all that hard earned money in a field where corporate fortunes are not only made, but lost. There was a lot of criticism when the deal was first announced, a lot of delay in making the second instalment of money available, and a long, long, wait before any hint of a return on the investment could be perceived—but now at last it begins to look like money well spent (Thank Goodness!)

The first device out of the Inmos stable, a 16K static RAM coded IMS 1400, looks like a real winner because it employs ingeniously different techniques to give a memory which has a larger capacity than any of its rivals, is faster, and is also potentially cheaper to produce. Innovation is the name of the game in the cut-throat memory market-place, as has been demonstrated by such giants as Intel and Mostek, but innovation alone is not enough, the clever new products have to be producible too, and producible in large enough volumes to swamp the competition. With the IMS 1400, Inmos appear to have made an excellent start. Until the IMS 1400, most memory improvements have been made by simply shrinking device geometries so that more and more cells could be squeezed onto a given area of silicon. While this has been an important process of improvement, it does mean that memories have been getting more and more difficult to produce. The Inmos approach does not depend on scaling but on changes to the circuit design

used for each memory cell which together produce a more efficient element which is, in manufacturing terms, actually *simpler* than rival chips of lower capacity. The performance of the IMS 1400 is adequate for all present and projected microprocessor and minicomputer applications, and it exceeds by a comfortable margin the performance of today's fastest (but smaller) 4K 2147 device.

The IMS 1400 is housed in a 20 pin 0.3 inch wide package which has an extended version of the 2147 4K pin-out. The chip runs from a single five volt line and has a very low power consumption of 375 milliwatts (active) and 35 milliwatts (standby). Perhaps the most significant performance feature is the access time of just 30 nanoseconds, *too* fast for most of today's microprocessors, but useful for other memory applications currently filled by exotic and expensive bipolar devices of much lower capacity. As if all this alone wasn't enough to make Inmos a blue chip investment, the designers in Colorado Springs have hedged their bets by building in *spare* columns of memory cells which can be selected after chip fabrication by means of fusible links which map one or more of the spares into the active area to replace defective columns discovered during wafer test.

If future Inmos devices are as ingenious, I think I for one will retire on the proceeds!

ELECTRIC DRAWING BOARD

You can draw pictures on a CRT in one of two basic ways, direct vector or raster scan. In the direct vector scheme, lines are drawn by tracing them onto the tube face with a moving beam of electrons, in a scheme somewhat similar to that employed by an oscilloscope. To draw a line from A to B the beam is turned on in position A and the correct waveforms are applied to the X and Y deflection plates or coils to move the beam so that its intersection with the display surface describes a straight line on the screen. In raster scan on the other hand, a beam of electrons is constantly scanning the screen in TV raster format and the drawing of a straight line involves no out-of-sequence movement of the electron beam at all. With raster graphics, the screen is arbitrarily divided up into picture elements as "pixels" each of which has a

unique bit reserved for it in the screen memory array. To draw a straight line, the start and end points are used to calculate which of the bit cells in the screen memory need to be "on". As the raster is built up, every memory location will be scanned in sequence, but only those bit cells which are "on" will cause the beam to excite the screen phosphors. The result is a line as before, although in this case the line may appear jagged if the screen memory resolution is limited.

The advantage of raster graphics lies in the fact that multicolour displays using readily available television monitors can be easily constructed, whereas direct vector systems need special long persistence tubes and cannot easily produce multicolour pictures.

Complete raster graphics systems are available from several manufacturers, and are widely used for engineering design and other similar applications where the cost is acceptable. Resolution is typically 512 x 512 pixels for a 625-line monitor, giving a memory requirement of at least 16K bytes per colour, a factor which has ruled out such desirable high definition graphics for home computer applications until now.

Thanks to cheap dynamic memory and a new chip from Thompson CSF, the EF 9365, all that is about to change and we can expect to see much wider application of the "Electric drawing board" in low cost systems. The new chip performs many of the functions currently performed by the proprietary raster display systems costing hundreds of pounds, yet it comes in a 40 pin package and will eventually cost less than £20! Teamed with a microprocessor and a group of dynamic RAM chips the EF 9365 will turn complex input specifications such as vectors, symbols, shapes and points of origin into the appropriate bit patterns in the screen refresh memory. To cater for the necessary but more mundane alphanumeric display requirement (to label graphics pictures for example) the Thomson device also has an on chip character generator for a full 96 character ASCII set. When drawing vectors on the screen, a mean writing rate of 1.36 milliseconds per pixel is possible, and when this device becomes freely available in 1981 we can expect to see a colourful revolution in microprocessor display peripherals.

SPECIAL OFFERS!

IN CAR ENTERTAINMENT

PE has taken a pride in bringing readers some excellent offers over the months. Offers arranged to enable the purchase of technical products at exceptional prices. Back in April we arranged a special offer on Videotone speakers. That offer was so successful that Videotone have again come up with exceptional prices, this time on in-car-

entertainment products, just for PE readers.

We believe these products represent incredible value for money, and that this is one of the best offers we have ever been able to arrange. The equipment and speakers on offer, shown and described here, are all covered by a full one year guarantee and money back facility if you are not satisfied.



**AS6123 20W HiFi
GRADE
SPEAKERS
WITH 3 DRIVE
UNITS ON
SWIVEL MOUNT**



£17.50
PER PAIR

£42

**AM/FM STEREO RADIO AND
AUTOREVERSING CASSETTE
PLAYER**



**AS4107 10W HIGH
QUALITY
WATERPROOFED
DOOR MOUNTING
SPEAKERS**



£10.50
PER PAIR

£17

**AC200 STEREO 10W per channel
(max.) CASSETTE PLAYER**



**AC100 STEREO 7W per channel
(max.) CASSETTE PLAYER**

**AS6111 15W WEDGE
TYPE SPEAKERS
WITH METAL
GRILLE**



£8.50
PER PAIR

£14.50

ALL PRICES INCLUDE POSTAGE PACKING & V.A.T.

BASIC SPEC. FOR THE RADIO/CASSETTE PLAYER

AM 540 – 1605kHz, 20µV sensitivity (at 20dB S/N), 455kHz i.f.
 FM 88 – 108MHz, 5µV sensitivity (at 30dB S/N), 10.7MHz i.f.,
 antenna impedance 75Ω unbalanced, i.e.d. stereo beacon,
 AM/FM/FM multiplex switch.

TAPE PLAYER Autoreversing, 4 track 2 channel stereo, wow and flutter <0.3% (WRMS), signal to noise >-40dB, crosstalk >-40dB, i.e.d. indication of tape direction, manual tape reverse button, fast forward and rewind.

GENERAL Output 7W per channel, frequency response 80Hz – 10kHz, output impedance 4 – 8Ω, supply voltage 12V (11 – 16V d.c.) **negative earth only**, tone, balance, volume and tuning controls, range switch, scale illumination, size 180 x 44 x 148mm deep, weight 1.9kg, supplied with fixings for in-dash mounting, in line fuse holder and fuse and instructions for mounting, wiring and operating the unit.

BASIC SPEC. FOR THE CASSETTE PLAYERS

Autostop, 4 track 2 channel stereo, wow and flutter <0.25% (AC200), <0.3% (AC100) WRMS, frequency response 50Hz – 12kHz, signal to noise <-45dB, fast forward time <180 sec. for C60 cassette, output impedance 4 – 8Ω, supply voltage 12V (11 – 16V d.c.) **negative earth only**, size 110 x 50 x 170mm deep (AC100), 110 x 55 x 170mm deep (AC200), loudness +7dB (AC200 only), supplied with fixing brackets, connecting plug, wire, in line fuse holder and fuse and instructions for mounting, wiring and operating, including circuit diagram.

To: Videotone Ltd. (PE Offer), 98 Crofton Park Road, Crofton Park, London SE4. Tel: 01-690 8511/2.

Please send me:

QUANTITY	DESCRIPTION	PRICE
	AM/FM RADIO CASSETTE at £42.00	
	AC200 10W CASSETTE at £17.00	
	AC100 7W CASSETTE at £14.50	
pr/s	AS6123 20W SPEAKERS at £17.50	
pr/s	AS4107 10W SPEAKERS at £10.50	
pr/s	AS6111 15W SPEAKERS at £8.50	

I enclose a cheque/P.O. No: for £

made payable to Videotone Ltd. (All quoted prices include post, packing and VAT.)

Name

Address

**Please allow 28 days for delivery
 OFFER CLOSES FRIDAY JANUARY 30 1981**

Name

Address

To: Videotone Ltd. (PE Offer), 98 Crofton Park Road, Crofton Park, London SE4. Tel: 01-690 8511/2.

Please complete both parts of the coupon in BLOCK CAPITALS

Countdown

Please check dates before setting out, as we cannot guarantee the accuracy of the information presented below.

- Semiconductor International** 80 Nov. 25–27. Metropole Convention Centre. **T1**
 - BEX** 80 Nov. 26–27. Exhibition Centre, Bristol. **K**
 - Breadboard** Nov. 26–30. Royal Horticultural Halls, Westminster. **T**
 - BEX** 81 Feb. 4–5. Pavilion, Bournemouth. **K**
 - Microsystems 81** (exhibition and conference) March 11–13. Wembley Conf. Centre, London. **Z1**
 - INSPEX 1981** March 16–20. NEC, Birmingham. **Z1**
 - Seminex 81** (seminars only) March 23–27. Imperial College, London. **H1**
 - BEX** 81 March 25–26. Metropole, Brighton. **K**
 - The Northern Electronic Test & Measurement Exhibition 81** March 31–April 2. Wythenshawe Forum, Manchester. **T**
 - Laboratory 81** April 1–2. Glasgow. **I**
 - BEX** 81 April 8–9. Centre Hotel, Liverpool. **K**
 - Laboratory 81** April 8–9. Manchester. **I**
 - All Electronics Show 81** April 22–24. Grosvenor Ho., Park Lane, London. **F1**
 - Computer Graphics 1981** April 28–30. The Barbican Centre, London. **O**
 - BEX** 81 April 29–30. Dragonara Hotel, Leeds. **K**
 - Entertainment 81** May 9–17 (weekday mornings trade only). NEC, Birmingham. **B2**
 - The European Consumer Electronics Show 81** May 10–13. Nuremberg, West Germany. **I**
 - The European Consumer Electronics Show 81** May 10–13, Nuremberg Fair Centre. W. Germany. (Trade) **I**
 - BEX Train** May 11–22. Calling at: Cambridge, Norwich, Leicester, Sheffield, Newcastle, Middlesbrough, Hull, Nottingham, Reading and Portsmouth. **K**
 - Defence Components Expo 81** May 12–14. Brighton Metropole. **I**
 - Scotex 81** June 2–4. Royal Highland Exhibition Hall, Ingleston, Edinburgh. **A1**
 - Semlab 81** June 2–5. Grand Hall, Olympia, London. The international scientific, educational; medical and industrial laboratory equipment exhibition. (Trade) **I**
 - Transducer Tempcon 81** June 9–11. Wembley Conf. Centre, London. **T**
 - Components 81** (Electronics Components Industry Fair) June 9–12. Earls Court, London. **I**
 - International Word Processing Exhibiton & Conf.** 81 June 23–26. Wembley Conf. Centre, London. **Z**
 - Solar Energy Exhibition** Aug. 23–28, 1981. Brighton. **M**
 - Laboratory 81** Sept. 8–10. Grosvenor Ho., Park Lane, London. **I**
 - International Business Show 81** Oct. 20–29. NEC, Birmingham. **A2**
 - Electronics 82** (Sub-titles' International Electronics Control and Instruments Exhibition) May 24–28, 1982. NEC. **I**
-
- I** Industrial Trade Fairs. ☎ 021-705 6707
 - K** Douglas Temple Studios. 1046 Old Christchurch Road, Bournemouth
 - M** Montbuild. ☎ 01-486 1951
 - O** Online Conferences. ☎ 0895 39262
 - T** Trident International Exhibitions. ☎ 0822 4671
 - A1** Institute of Electronics. ☎ 0706 43661
 - H1** Seminex Ltd. ☎ 0892
 - T1** Kiver Communications UK, Millbank House, 171–185 Ewell Road, Surbiton, Surrey KT6 6AX.
 - Z1** IPC Exhibitions Ltd., 40 Bowling Green Lane, London EC1R 0NE. ☎ 01-837 3636
 - A2** Hart Browne & Curtis Ltd., 29 Sackville Street, Piccadilly, London W1X 1DR. ☎ 01-439 8556
 - B2** Brintex Exhibitions Ltd., 178–202 Great Portland Street, London W1N 6NH. ☎ 01-637 2400

PE

MICROTUNE

MARTIN KENT

THE PE MICROTUNE is a general-purpose automotive tester which, as well as featuring *volts*, *amps* and *resistance* measurement, can also check *r.p.m.* and ignition *dwell angle*. The voltage and current ranges also have an a.c. function, making the meter extremely useful on car radios, cassettes etc., as well as being suitable for general electrical or electronic diagnostic use. The digital read-out gives a far higher accuracy than is attainable from analogue "pointer" type meters. Use of an l.c.d. display gives large, easily read digits, visible even in bright sunlight, and giving very long battery life.

A total of seven functions (DC Volts, AC Volts, DC Current, AC Current, Resistance, RPM, Dwell) and twenty ranges, makes this the most versatile car tester yet. It is suitable for use on positive or negative earth vehicles, fitted with normal or electronic ignition, and *four, six or eight* cylinder engines are catered for.

MICROTUNE BASICS

As with the PE DMM (July 1980), the Microtune uses the Intersil 7106 as the heart of the instrument, the single range voltmeter. This is a $3\frac{1}{2}$ digit analogue to digital converter, which drives an l.c.d. display directly. The July article outlined the operation of a dual-slope A/D Converter, so the explanation will not be repeated.

The heart of the Instrument is the single range 200mV voltmeter formed by IC1, the 7106. The input impedance is greater than $100M\Omega$, to ensure that negligible current is drawn from the circuit under test. An input filter to limit noise voltage is formed by C6 and R6; the latter also increases the overload protection by restricting the input currents. An on-chip reference voltage is provided at pin 32 of IC1, which is maintained at approximately 2.8V below the positive supply rail. The voltage reference is the critical part of any A/D converter as all inputs are compared against it. To optimise reference stability, a bandgap voltage reference IC3 is used, which operates from the on-chip 2.8V reference. The reference voltage output of bandgap devices depends inherently on the properties of transistor junction potentials. The V_{be} of a junction depends upon bulk properties and doping levels of the semiconductor material; its long

term stability being essentially unaffected by surface phenomena. A potential divider is formed by resistors R3, R4, R5, and VR1 to adjust the 1.2V output of IC3 and produce an extremely stable 100mV reference, while C7 eliminates any noise voltages.


The frequency of the interval clock oscillator is controlled by C5 and R2, the values chosen providing a frequency of approximately 48KHz, to produce a conversion rate of three readings per second with good rejection from 50Hz pick-up.

The A/D converter is inherently auto-zero in its' operation, such that when the inputs are shorted together the digital outputs are guaranteed to be zero, to eliminate the need for offset adjustments. The auto-zero capacitor C2 prevents noise voltages affecting the above function. The integrator time constant is set by C1 and R1.

DISPLAY REQUIREMENTS

The 7106 drives liquid crystal displays direct and the square wave backplane signal is provided at pin 21. L.c.d.s require a.c. drive signals since steady d.c. potentials can burn-in the segments. For a particular segment to be turned on, it must be driven by a signal of equal amplitude but opposite phase to the backplane signal.

Voltage comparator integrated circuits are designed to produce a logic "1" output when the difference between the inputs is positive and a logic "0" when the difference is negative. This is the basis of the auto-polarity circuitry within IC1 which drives the negative polarity bar directly from pin 20. Decimal points are selected by sections of the range switches S2-S5 and the correct l.c.d. drive is provided by dual-input EXCLUSIVE-OR gates within IC4. Examination of the truth table of an EXCLUSIVE-OR gate will show that the output is high if one or other of the inputs is high, but the output is low if both inputs are high. If one of the inputs is used as a control input, when it is low it will allow through the gate a high or low level, as applied to the second input. When the control input is high it will invert the level applied to the second input. Resistors R7, R8 and R9 hold the control inputs, pins 8, 13 and 6 of IC4, at a normally low level by using the test output, pin 37, of IC1. The backplane signal is applied to IC4 pins 9, 12, and 5. When a control input is

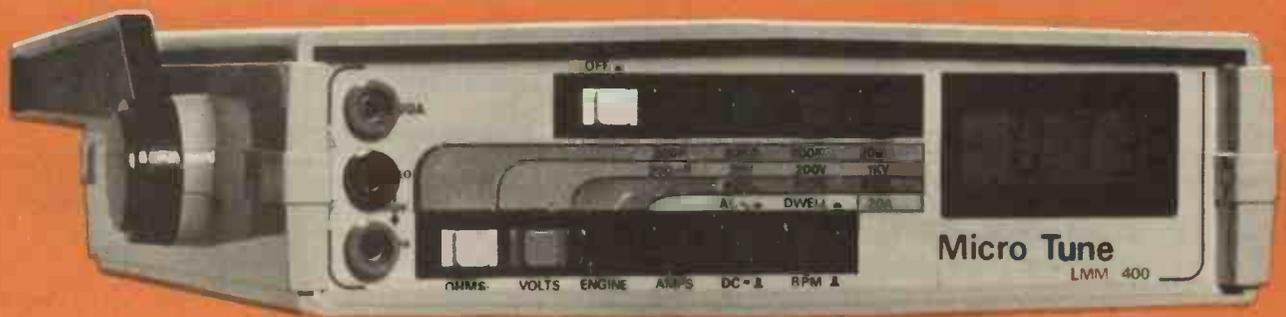

...ENGINE TUNE-UP UNIT

Part One



taken to a high level by the range switch, the respective gate acts as an inverter to provide an output in antiphase to the backplane input and so provide the required I.c.d. drive signal.

When using battery-operated instruments, it is important to know when the battery voltage is dropping to a level where performance of the instrument may be impaired. The liquid crystal displays supplied by Lascar have "LO-BAT" wording which can be turned on when the battery voltage has dropped such that 20 per cent of useful life remains. The operator therefore receives advance warning of battery failure while being able to maintain accurate readings until the battery can be changed.

A potential divider is formed across the supply rails by R10 and R11. When the supply voltage drops to approximately 7 Volts TR1 collector is taken high and IC4d becomes an inverter for the backplane signal, and turns on the low battery warning display segments.

INPUT CONDITIONING

All of the signal inputs to the Microtune must be converted to 0-200mV d.c. levels to ensure compatibility with the A/D convertor.

(a) D.C. VOLTAGE AND CURRENT MEASUREMENT

Four d.c. voltage ranges are provided with f.s.d. of 200mV, 20V, 200V and 1KV. The four range switches S2-S5 are interlocked with the Off Switch S1 such that any range selection switches the instrument on. Sections of the function switches then select appropriate areas of circuitry to minimise current drain in unwanted circuitry. Switch S1b also isolates the main signal input when the power is off to prevent damage to the A/D convertor. When the Voltage function is selected by S7, the input is applied to the 10MΩ attenuator formed by resistors R13-R18 which are extremely stable 0.25 per cent metal film types. On the 200mV range the input is routed directly to the A/D convertor, whereas the higher range switches select the appropriate attenuation point.

Voltage dependent resistors R21-R23 are connected across the input terminals to clamp any transient high voltage spikes which may otherwise cause damage to the instrument. A VDR normally exhibits extremely high resistance such that it does not affect measurement accuracy but when the threshold voltage is exceeded the device alters rapidly to a low resistance to shunt out transients.

A single current range of up to 20A is provided via a separate input terminal to avoid high currents flowing through the switches. To convert the input current to the required voltage requires a shunt resistor of value 10mΩ and whilst this value is available such resistors are very expensive. The cost of such resistors may be eliminated by using the p.c.b. track and recalling that the resistance of an element is given by its' resistivity (ρ), length and cross-sectional area.

$$\text{Resistance, } R = \frac{\rho l}{A} \text{ ohms}$$

The industrial standard copper laminate fibre-glass board used for p.c.b. manufacture uses 1oz. (0.035mm thick) copper coating. The track width was chosen first to restrict the temperature rise to 20 deg. C with 20A flowing, and then the cross sectional area was calculated. From the resistivity of annealed copper, the length of the required track for a resistance of 10mΩ was then calculated.

No protection is provided on the current range and care must be exercised when connecting this range in circuit.

The d.c. voltage developed across the shunt resistor R24 is switched by S9a, and the decimal point on the display is set for 19.99A by S9b.

(b) A.C. VOLTAGE & CURRENT MEASUREMENT

When a.c. functions are selected by S10, capacitor C8 is connected in series with the input to remove any d.c. component. Voltage inputs are fed through the 10MΩ attenuator as before and current input is applied to the shunt resistor.

Integrated circuit IC5 is a TL061 operational amplifier, connected as a precision rectifier. Alternating inputs are rectified by diodes D4 and D5 with the positive component

SPECIFICATION

FUNCTION	FSD	RESOLUTION	ACCURACY
VOLTS (DC)	200mV	0.1mV	0.5% ± 1 Digit
	20V	10mV	
	200V	100mV	
	1kV	1V	
CURRENT (DC)	20A	10mA	5% ± 2 Digits
VOLTS (AC)	200mV	0.1mV	0.75% ± 5 Digits
	20V	10mV	
	200V	100mV	
	1kV	1V	
CURRENT (AC)	20A	10mA	6% ± 5 Digits
RESISTANCE	200Ω	100mΩ	0.5% ± 1 Digit
	20kΩ	10Ω	
	200kΩ	100Ω	
	20MΩ	10kΩ	
RPM	20,000RPM (4, 6 or 8 cylinders)	10RPM	1% nominal ± 3 Digits
DWELL	200° (4, 6 or 8 cylinders)	0.1°	2% nominal ± 3 Digits

COMPONENTS . . .

Resistors

R1, R36	47k	Carbon film 5% (2 off)
R2, R20,		
R30	100k	Carbon film 5% (3 off)
R3, R5	1k	Carbon film 5% (2 off)
R4, R27,		
R28	18k	Carbon film 5% (3 off)
R6, R26	10M	Carbon film 5% (2 off)
R7-R10,		
R12, R25	1M	Carbon film 5% (6 off)
R11, R19	220k	Carbon film 5% (2 off)
R13	9M	Metal film 0.25%
R14	900k	Metal film 0.25%
R15	90k	Metal film 0.25%
R16	9k	Metal film 0.25%
R17	900R	Metal film 0.25%
R18	100R	Metal film 0.1%
R21	VDR	400V
R22	VDR	400V
R23	VDR	400V
R24	10mΩ	P.c.b. integral
R29	6k8	Carbon film 5%
R31	Thermistor	PTC, 1k, 260V a.c.
R32	100k	Carbon film 5%
R33	470R	Carbon film 5%
R34, R45	3k3	Carbon film 5% (2 off)
R35, R39,		
R41, R44,		
R46, R47	10k	Carbon film 5% (6 off)
R37, R38	27k	Carbon film 5% (2 off)
R40, R50	1k	Carbon film 5% (2 off)
R42	2k2	Carbon film 5%
R43	4k7	Carbon film 5%
R48	6k8	Carbon film 5%
R49	910k	Carbon film 5%

Variable Resistors

VR1	2k	Multiturn cermet
VR2-VR4	5k	Multiturn cermet (3 off)

Capacitors

C1, C14	220n	Polyester (2 off)
C2	470n	Polyester
C3,		
C10-C12,		
C15	100n	Polyester (5 off)
C4, C6	10n	Polyester (2 off)
C5	100p	Polystyrene
C7, C9,		

C13	10μ	Tantalum bead 16V (3 off)
C8	20n	Ceramic disc 2,000V
C16, C17	22μ	Tantalum bead 16V (2 off)

Semiconductors

D1	IN4004	
D2-D5,		
D8, D10,		
D11	IN4148	(7 off)
D6, D7	BZY88	5V6 (2 off)
D9	BZY88	2V7
TR1	BC237	
TR2	MPSA42	
IC1	ICL7106	
IC2	LCD106	
IC3	Teledyne	9491 or Ferranti ZN423
IC4	4070	
IC5	TL061	
IC6	LM2907-8	
IC7	LM324N	

Switches

S1-S5	4PDT	All interlocked, Bank 1	} Bank 2
S6	8PDT		
S7, S8	4PDT	All interlocked	
S9	DPDT		
S10	6PDT		
S11	DPDT		

Miscellaneous

Strips of 20-way soldercom pins (2 off)
 Nylon soldercon nests (2 off)
 20mm p.c.b. fuse clips + 2A fuse
 PP7 batteries and connectors (2 off)
 Printed circuit boards (3 off)
 15-way p.c.b. mounting socket
 10-way p.c.b. mounting plugs (2 with long pins) (4 off)
 Ribbon cable, 10-way with end sockets
 Through-board pins (22 off)
 4mm input terminals (2 red, 1 black) (3 off)
 Springs (2 off), nuts and screws etc.
 Case kit, comprising top, bottom, front panel, rear panel, sides/carrying handle, four feet with screws.

Constructors' Note

A complete kit of all parts for the PE Microtune, including batteries and test leads is available from Lascar Electronics Ltd., Unit 1, Thomasin Road, Burnt Mills, Basildon, Essex SS13 1LH, price £69.80 which includes p&p and VAT. A calibration and fault finding service will also be offered.

sampled by R26 then filtered by R30 and C12. The op-amp has a j.f.e.t. input resulting in high input impedance, and the supply current is typically 250μA, which makes it ideal for battery operation.

The circuit is mean-sensing and calibrated to indicate the r.m.s. value of sine wave inputs by adjustment of VR2.

(c) RESISTANCE MEASUREMENT

One method of measuring an unknown resistor is to apply a constant current and measure the voltage developed across the resistor. The PE DMM used such a method but the Microtune with its increased space to provide more intricate switching, uses a more streamlined method of resistance measurement. The Intersil 7106 analogue inputs are fully differential as are the reference voltage inputs. In the normal mode of operation a fixed reference voltage is applied to the 7106 and the signal input voltage is measured as a ratio of the reference voltage and the digital reading is $1000 \frac{V_{in}}{V_{ref}}$. So that with a 100mV reference, an input of 100mV would be read as 100.0. For resistance measure-

ment the arrangement shown in Fig. 2 may be used.

The bandgap reference IC3 forms a stable voltage source which is applied across the reference resistor R_r and the unknown resistor R_x.

The voltage developed across each resistor is dependent upon the ratio of the two resistors and the ratiometric method of operation of the 7106 permits the value of the unknown resistor to be read directly.

$$\text{Reading} = 1000 \frac{R_x}{R_r}$$

The reference resistor is selected from the input voltage attenuator resistors, to avoid expensive duplication, by S2-S5 and is in reverse order to the voltage settings. The value of R_x is 100Ω for the 200Ω range, 10kΩ for the 20kΩ range etc.

A simplified form of the instrument circuit with the 200Ω range selected for resistance measurement is shown in Fig. 3 to clarify the switching.

Resistance measurements should not be made on live circuits, however protection is included to prevent damage to


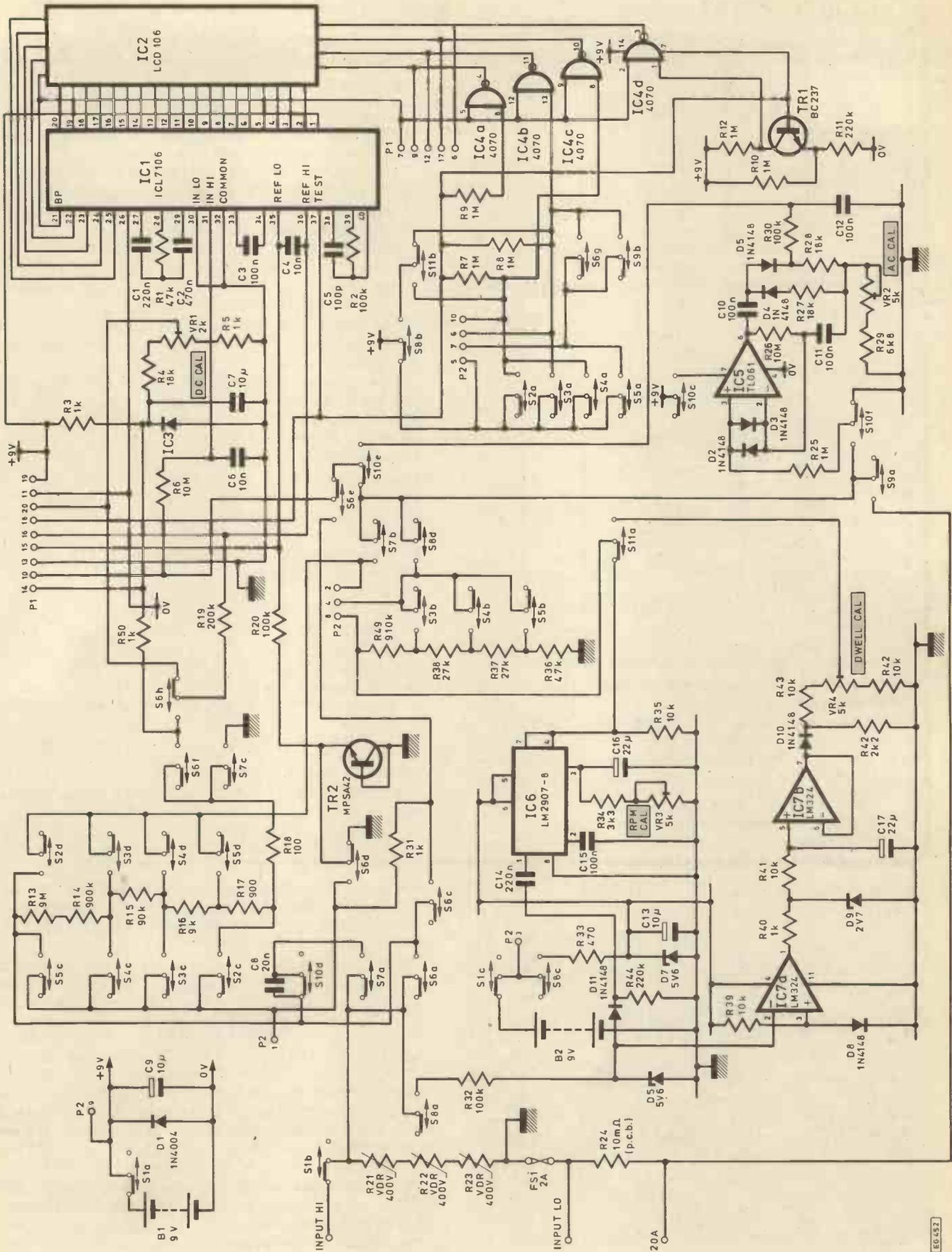


Fig. 1. Full circuit diagram.

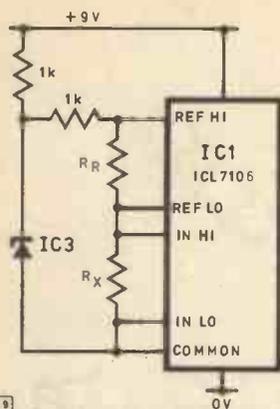

EG449

Fig. 2. Resistometric resistance measurement


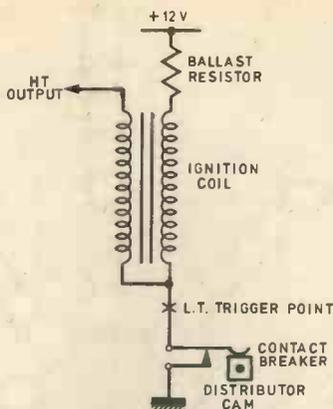


Fig. 4. Ignition system triggering

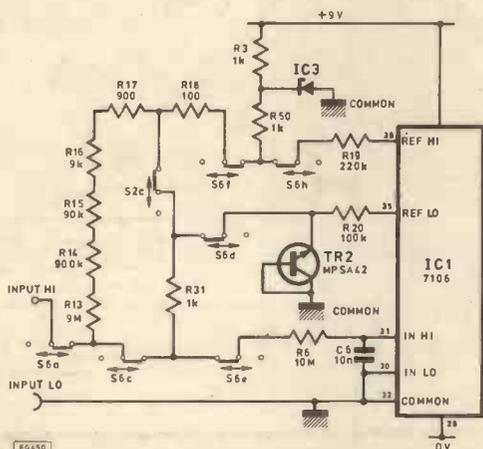

EG450

Fig. 3. Switch configuration for resistance 200Ω range

the instrument against applied high voltages. Transistor TR2 will turn on at approximately 10V and shunt the applied voltage. Thermistor R31 has a nominal value of 1kΩ at room temperature, but when TR2 draws current through R31 the thermistor temperature rises and due to the positive temperature coefficient the resistance increases so limiting the input current.

(d) R.P.M. MEASUREMENT

The measurement of engine r.p.m. can be very useful when servicing cars and we shall see later that specific tests carried out whilst monitoring the speed of an engine enable its efficiency to be optimised.

Although the internal combustion engine has changed very little over the years, there have been distinct changes in the area of the ignition system. A large number of new vehicles still employ the conventional contact breaker, driven from the distributor, to trigger the ignition coil and hence produce h.t. voltage to the sparking plugs. However, an increasing number of engines are being fitted with electronic ignition units usually triggered by the contact breaker, and capable of producing higher voltage at the sparking plugs from lower supply voltages. Some electronic ignition systems dispense with the mechanical contact breaker and are triggered by a Hall effect switch which detects the passing of a magnetic vane to control the timing. Amidst the variety of ignition systems, one component usually remains unchanged and that is the ignition coil. By monitoring the triggering of the ignition coil, measurement of engine r.p.m. may be made without the need for expensive transducers.

Fig. 4 shows the simplified ignition arrangement of a negative earth vehicle.

For a four-stroke engine, the distributor shaft rotates at half the speed of the crankshaft and the number of trigger pulses applied to the ignition coil is given by:

$$\text{Pulses/Min} = \frac{\text{r.p.m.} \times \text{number of cylinders}}{2}$$

alternatively,

$$\text{r.p.m.} = \frac{\text{Pulses/Min} \times 2}{\text{Number of cylinders}}$$

Therefore, for a given engine, the r.p.m. varies linearly with the pulses/min applied to the ignition coil.

Measurement of the pulse rate is most easily carried out by conversion to an analogue voltage with a frequency-to-voltage converter and then measuring the d.c. voltage on the 7106-based voltmeter.

The basic diode pump circuit is dependent upon pulse width and amplitude but may be improved by feeding it from monostable which delivers a pulse of fixed amplitude and duration each time the ignition coil is triggered.

Integrated circuit IC6 is a monolithic frequency-to-voltage converter based upon a charge pump whose output voltage is buffered by an op-amp.

Due to the ignition coil inductance, high transient voltages can be found superimposed upon the normal 12V trigger pulse on the coil primary and the input voltage to the f/v converter is clipped by R32 and D6. The input signal is fed through C14 as the comparator input is required to pass through zero to ensure correct triggering. The output voltage of the LM2907 is referenced to its power supply zero volt line but the 7106 input is not able to operate down to its zero volt line, therefore a separate supply is used for the tachometer section. Output voltage is proportional to timing capacitor C15 and load resistor R34 + VR3, whereas filter capacitor C16 suppresses ripple but will also lengthen the converter response time. Resistors R49 and R36-R38 form an attenuator to reduce the output voltage when switching between 4, 6 and 8 cylinders, since r.p.m. is inversely proportional to the number of cylinders as shown earlier. Full scale output of IC6 is set at 2V.

The normal range-switch selection of decimal points is overridden on engine functions by S8b, and S11b sets the d.p. for 19.99 (x 1000) r.p.m. for 4, 6 or 8 cylinders.

(e) DWELL MEASUREMENT

Each vehicle has a specific dwell angle quoted for the distributor and is the angle through which the contact breaker cam rotates whilst the points are closed. Adjustment of the dwell angle is very important to ensure correct combustion and the angle may be measured by comparing the points open time to points closed time, or duty cycle. The cam has a number of lobes equal to the number of cylinders such that a four cylinder engine will have four lobes spaced 90° apart and the dwell angle is usually slightly less than two-thirds of the cam lobe angle.


$$\text{Dwell angle} = \text{cam lobe angle} \times \frac{100\% - \text{Duty Cycle}}{100\%}$$

The instrument is connected to the same coil primary connection as used when measuring r.p.m. and the input voltage is fed to IC7 which is an LM 324 quad op-amp. The first stage acts as a comparator whose threshold voltage is set at approximately 1V by R39 and D8. The rectangular output of IC7a is an inversion of the input such that the points-closed time is active "high" and clipped to constant amplitude by R40 and D9.

The clipped signal is integrated by R41 and C17 to obtain the average value which is then buffered by IC7b and the 600mV offset is removed by D10. The output voltage is adjusted by R42, R43 and VR4 to produce a 2V f.s.d. proportional to dwell angle.

NEXT MONTH: Construction and Use.

NEXT MONTH
PE STARSPINNER

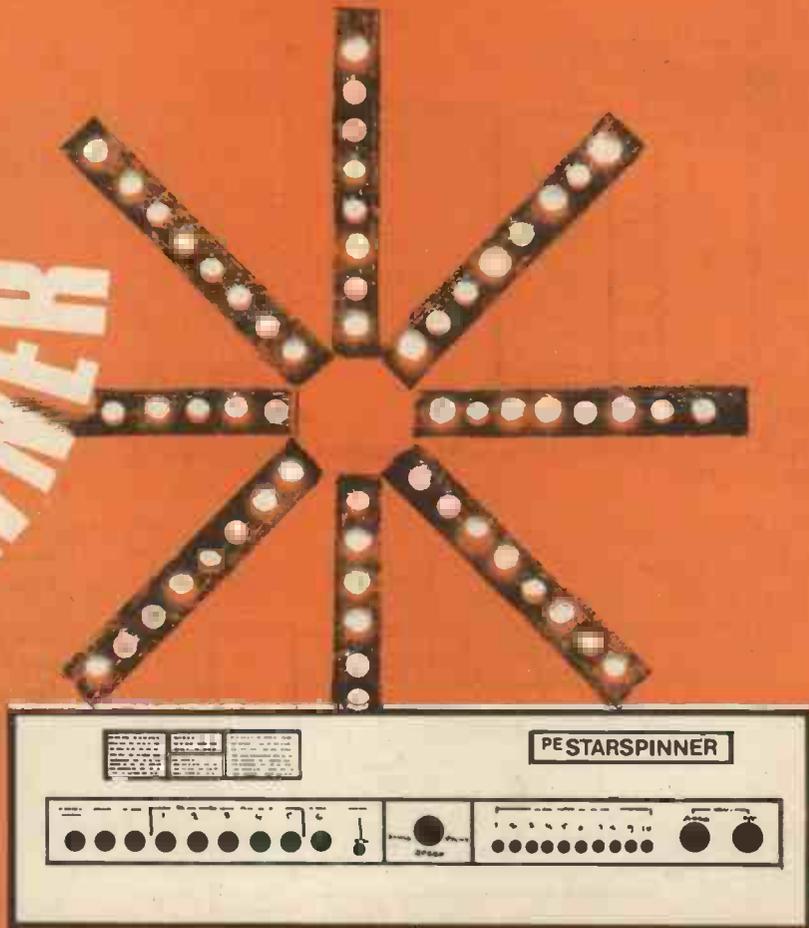

Most people have seen the fascinating rotating and radiating displays available from modern "zoning" or "matrixing" lighting systems. The *PE StarSpinner* can produce 62 dynamic effects of this type plus two static effects and a sound to light advance facility—full circuit and construction details start next month.

SOLAR POWER SATELLITES

Will solar power solve our energy problems? Can we build the satellites? How will they work? When will they be available? How much will it all cost?

For answers to these and other questions the SPS raise, see our article next month.

INTERFACING COMPUKIT

Computers make smashing toys but sooner or later they must pay for their keep by doing some real work. Next month we start a series on interfacing the UK101 with the outside world, using such things as joysticks, I.d.r.s, power controllers, D/A and A/D converters, etc.

FREE TANDY 132 PAGE CATALOGUE with every U.K. copy

PRACTICAL

ELECTRONICS

OUR JANUARY ISSUE WILL BE ON SALE ON FRIDAY, DECEMBER 12, 1980

PE

Master Rhythm

Part 1 A.J. Boothman B.Sc.

It is some twenty years since the first commercial attempts were made to simulate the role of a drummer using electronic principles, and despite continuous criticism of monotony and lack of instrument quality the utilisation of this type of musical aid has grown enormously to the present time where, in addition to almost universal incorporation into commercial electronic organs, it is used by Spanish guitarists in Tenerife, Greek singers in London restaurants, Scottish dancers and by practice musicians anywhere.

DEVELOPMENT

Basic design philosophy has changed little over the twenty years but the method of realisation has altered continuously along with the advances made in semiconductor technology. Ignoring tape playback systems early rhythm generators contained a limited number of simple patterns programmed during construction by a diode matrix. This type of system has had a long life and to many musicians its pattern simplicity is still preferable to many of the later "advancements". The advent of high capacity semiconductor memories seemed to provide the perfect answer to rhythm pattern generation—four, eight, twelve, sixteen rhythms on a single chip—then twenty four or more plus extra instruments and measures per bar using multiple chips.

All this looked marvellous, however the technique depended on the fixing of the patterns and instrument channels during the latter stages of manufacture of the integrated circuits and what i.c. manufacturer or commercial electronic

musical instrument design house could resist putting in the most complex patterns possible to give his equipment the gimmick appeal required by the general public. Hence the next generation of design realisation known as "Cancel Buttons". This allows a degree of low pass gimmick filtering and there present systems have rested.

The ability to leave the programming function to the musician has been restricted by the relatively slower development of read/write memories, commonly known as RAMs, as opposed to read only memories, or ROMs. This situation has only fairly recently changed in two important respects, the size of RAM available at an economic price and the standby power required to retain the patterns in an easily reprogrammable memory between periods of active use. The CMOS technique of semiconductor manufacture now gives reasonably low cost i.c.s which may be easily configured to give a 4096 bit capacity, similar to the common preprogrammed rhythm generator ROMs, with instant user programming and reprogramming capabilities and a standby data storage current of a few microamps.

The PE Master Rhythm makes use of this type of integrated circuit to give a small easily constructed rhythm generator on two p.c.b.s which is completely under the programme control of the musician. At the end of the series a full set of patterns will be given which may be used by the constructor to gain familiarity with the operation of the instrument. These are open to experiment and can be used as a base for further rhythms.



SPECIFICATION

Control Facilities

RHYTHM PATTERN SELECTION—Twelve Dual Section Positions.

Switch Positions

One to four
Five to eight
Nine and ten
Eleven and twelve

Measures Per Section (A and B)

Twelve or sixteen
Sixteen
Thirty two
Twenty four or thirty two

Section and Sequence Operation (Two switches)

Section	Sequence	Section
Switch	Switch	in
Position	Position	Operation
One	Any	A only
Two	Any	B only
Three	One	A then B
Three	Two	3A then B
Three	Three	7A then B

Cymbal Control (Three positions)

Switched—(1) Play programme, (2) Off, (3) Continuous.

Program Control (Ten positions)

Program (write) Tracks—Eight
Play (read) Mode—Two positions

Instrumentation (Three position control)

TRACK	STICK	BRUSH	L-A
Eight	Accent	Accent	Accent
Seven	Short Cymbal	Short Cymbal	Short Cymbal
Six	Long Cymbal	Long Cymbal	Long Cymbal
Five	Rim-Shot	Short Brush	Claves
Four	Snare Drum	Long Brush	High Bongo
Three	High Tom-Tom	High Tom-Tom	Low Bongo
Two	Low Tom-Tom	Low Tom-Tom	Conga Drum
One	Bass Drum	Bass Drum	Bass Drum

Memory Capacity—4,096 bits configured as 512 x 8

Power Source—4 x HP7 or similar

Operating Current—Typically less than 10mA

Standby Current—Typically less than 10µA

Nominal Output—100mV into 50kilohm

Approx. Dimensions—8½in x 5in x 2½in

SCOPE OF THE INSTRUMENT

This instrument is capable of storing between twelve and twenty four selectable rhythmic patterns, invented, modified, and entered by the operator onto eight instrument tracks. A three position "Instrumentation" control expands the number of instruments available to twelve, grouped into sounds typical of playing with drumsticks, brushes, or on Latin American bongos and claves. The incorporation of pattern sections containing twelve, sixteen, twenty four, and thirty two measures per section, coupled with dual section selection on the main "Rhythm Select" control which allows a continuous pattern of up to sixty four measures, a wide range of complex patterns may be reproduced.

RHYTHM CAPACITY

Each position of the "Rhythm Select" control selects a portion of the memory, split into two sections A and B. The "Section Selector" switch can isolate each section which may therefore contain totally different repeating patterns for a maximum capacity of twenty four discrete rhythms. However the two sections may be programmed with related rhythms, the B section for example containing a drum roll pattern or turn-round riff which will only be played if the "Section Selector" is set to the "B" or "Sequence" position. In the latter case the sequencer switch will determine how often the B pattern appears which on the first eight rhythms can be switched to alternate bars, four bar repetition, or eight bar repetition. Rhythm positions nine to twelve contain double length patterns—i.e. twenty four or thirty two measures per section, and whilst the longer sections may be used to give more measures per bar, they may also be programmed as two bars each which extends the maximum sequence to sixteen bars.

PLAY MODE

When the instrument is set in the play mode depression of the "Play" switch starts the rhythm sequence which continues until "Rest" is depressed. The start of the pattern is indicated by a pulse on the l.e.d. Restart will always be at the commencement of the pattern and sequence, and the "Section Selector" and "Sequence" switches may be altered at

any time during the play condition without disturbance to the synchronisation of the rhythm. The "Instrumentation" and "Cymbal" switch positions may also be altered during performance to introduce further variety as required.

INSTRUMENTATION

The memory system can be considered as an eight track digital recorder in which recording is executed one track at a time and playback occurs on eight simultaneously. Using the "Instrumentation" control the eight tracks may be fed to one of three groups of instruments as shown in the specification. The instruments will be familiar to the reader except possibly for "Accent" which allows a degree of dynamics to be introduced into rhythm patterns giving a more realistic result.

The "Cymbal" control normally selects the pattern contained on the relevant programmed track, but it also has positions to either cancel sound from the "Short Cymbal" or cause it to operate continuously—e.g. in a 16s mode.

PROGRAM MODE

The program mode is automatically attained by moving the "Program Control" to any of the eight instrument track positions. Prior to carrying out this operation the Master Rhythm should be run in the play mode and the "Rest" button depressed to ensure that the rhythm pattern is at its starting point. This will be indicated by illumination of the l.e.d. as the program mode is selected. During programming the "Sequence" control should be in the "A+B" position and the operator can choose to programme "A" and "B" either separately or together by the position of the "Section Select" control.

The "Instrumentation" and "Cymbal" switches can be set to any position during programming. Corresponding instrument sounds will be heard as the rhythm pattern is developed, but the sounds on playback will be determined by the switch settings at that time.

When an instrument track is selected on the "Program Control", depression of the "Play" button dictates that the relevant instrument will play during that measure of the pattern. Depression of the "Rest" button keeps the instrument

silent for the corresponding measure. Thus for four beats on sixteen measures per bar the pattern of one "Play" plus three "Rest" is pressed four times. In formulating a complete rhythm this action is repeated on each of the eight instrument tracks, an operation which soon becomes very quick. An individual track may be chosen for modification at any time without disturbing the other tracks. All instruments previously programmed plus the instrument under current modification, play during programming which allows a continuous audible check on the growing rhythm pattern.

PATTERN STORAGE

The play mode is automatically regained by turning the "Program Control" to either of its extreme switch positions, and the programmed information will be retained in the memory until modified, provided that the battery continues to give the required standing storage current of typically 5µA and does not fall below 2V, which represents virtually a shelf life condition for the battery. When a battery change becomes necessary, indicated by a loss of instrument quality, the battery may be removed for up to five minutes without the loss of the rhythm patterns.

MEMORY OPERATION

The heart of the unit is the block of four CMOS memories type 5101. These are 22 pin packaged devices each containing 1024 memory cells arranged as 256 rows four columns wide. By interconnecting the four integrated circuits in a series parallel configuration the final memory has 512 rows, eight columns wide.

Fig. 1 shows the operation of a single 5101 in simplified form, indicating that the chip consists of a set of memory cells plus control circuits. Each row in the memory has a unique address which can be selected by the voltages present on eight address lines due to the normal binary relationship of $2^8 = 256$. Thus for one combination of address input voltages only one row will be selected. In the unit some of the address lines are connected to the "Rhythm Select" switch which defines the row at which the pattern will start, whilst the others are connected, via the "Section" and "Sequence" switch logic, to a counter which automatically increments the row selection process up to the point at which the pattern is intended to be repeated.

When a row is selected the four corresponding memory cells are potentially available at both inputs and outputs. A read/write control line ensures that information can be put into the memory only when the control line voltage is low, and this is inserted on the rows (measures) as required using a positive voltage equal to the supply to indicate that an instrument requires to be played. On playback, with the read/write control line high, pulses will appear at the outputs to drive the instrument circuits when required.

Two chip selection control lines are also provided in the 5101, one of which, CE1, causes the chip to be active when its input is low and the other, CE2, when high. Unless both inputs are in the corresponding active states the chip presents an open circuit at its outputs preventing any influence on other chips which may be connected into the system. Thus CE1 is used in a similar manner to the address lines allowing selection of only the first pair of i.c.s with 256 rows and eight columns, or only the second pair of i.c.s with a further 256 rows giving 512 total. CE2 is used by the system clock which beats at one pulse per musical measure, to pulse the chosen address to give the output drive pulses to the instruments.

The remaining connections to the memory are its single supply and ground plus the grounding of pin 18, OD, which

is not used in this application. The relative timing and periods of various activities in this integrated circuit are important and are covered by the detailed circuitry.

SYSTEM OPERATION

A schematic of the system is given in Fig. 2, ignoring the detailed operation of the memory. The mode detector senses whether the "Program Control" switch is in either of the two play positions and signals the mode switching circuitry accordingly. This holds the read/write control voltage up to ensure that when the "Play" key is pressed, and its output latched, the clock will start and be fed through the counter, "Sequence" and "Section Select" switches, to the memory address inputs, coupled with the fixed starting address determined by the position of the "Rhythm Select" switch. A pulse is also transmitted to the chip select inputs CE2 for each measure within the rhythm pattern, and the down beat indicator is pulsed for each twelve or sixteen measure period. The memory output pulses are fed to the instruments via the "Instrumentation" and "Cymbal" selectors where applicable.

When the "Program Control" is in an instrument track position the mode detector gives a high output which sets the mode switching circuitry such that the counter is disconnected from the clock but increments on each depression of the "Play" or "Rest" key. High and low level signals corresponding to play and rest respectively pass through the "Program Control" switch to the instrument track selected and replace the level previously stored in that memory cell as a falling pulse is applied to the read/write control input from the mode switching network. The instrument tracks not selected at this time retain the previously recorded information due to the prior state feedback network.

CONTROL CIRCUITS

The complete control circuit detail is shown in Fig. 3. NAND gates IC1c and IC1d form the latch, one output of which is fed to the "Program Control" switch. Resistor network R17 and R18 produces a voltage of approximately 3V at the inputs to the two comparators which make up the mode detector, leading to a detector output of approximately 6V. However when the "Program Control" switch is in either of the "Play" positions the resistor network is overcome and the detector input becomes 0V or 6V dependent on the state of the latch connected to "Play" and "Rest" keys. In either case the detector output becomes zero which prevents any signals passing through IC2b to the write enable portion of the circuit. Under these circumstances the clock, which comprises IC1a and IC1b, is connected via IC2c and IC2d to

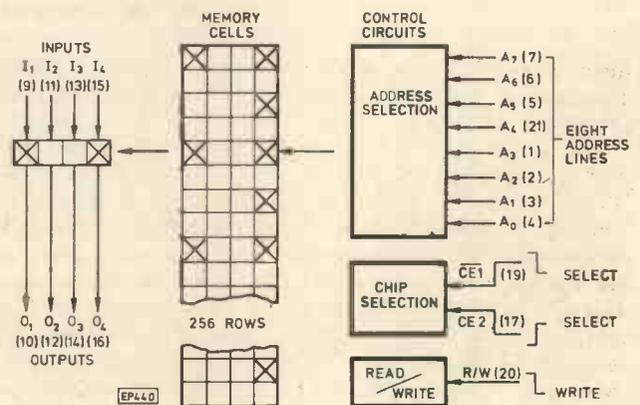


Fig. 1. Showing simplified operation of a 5101

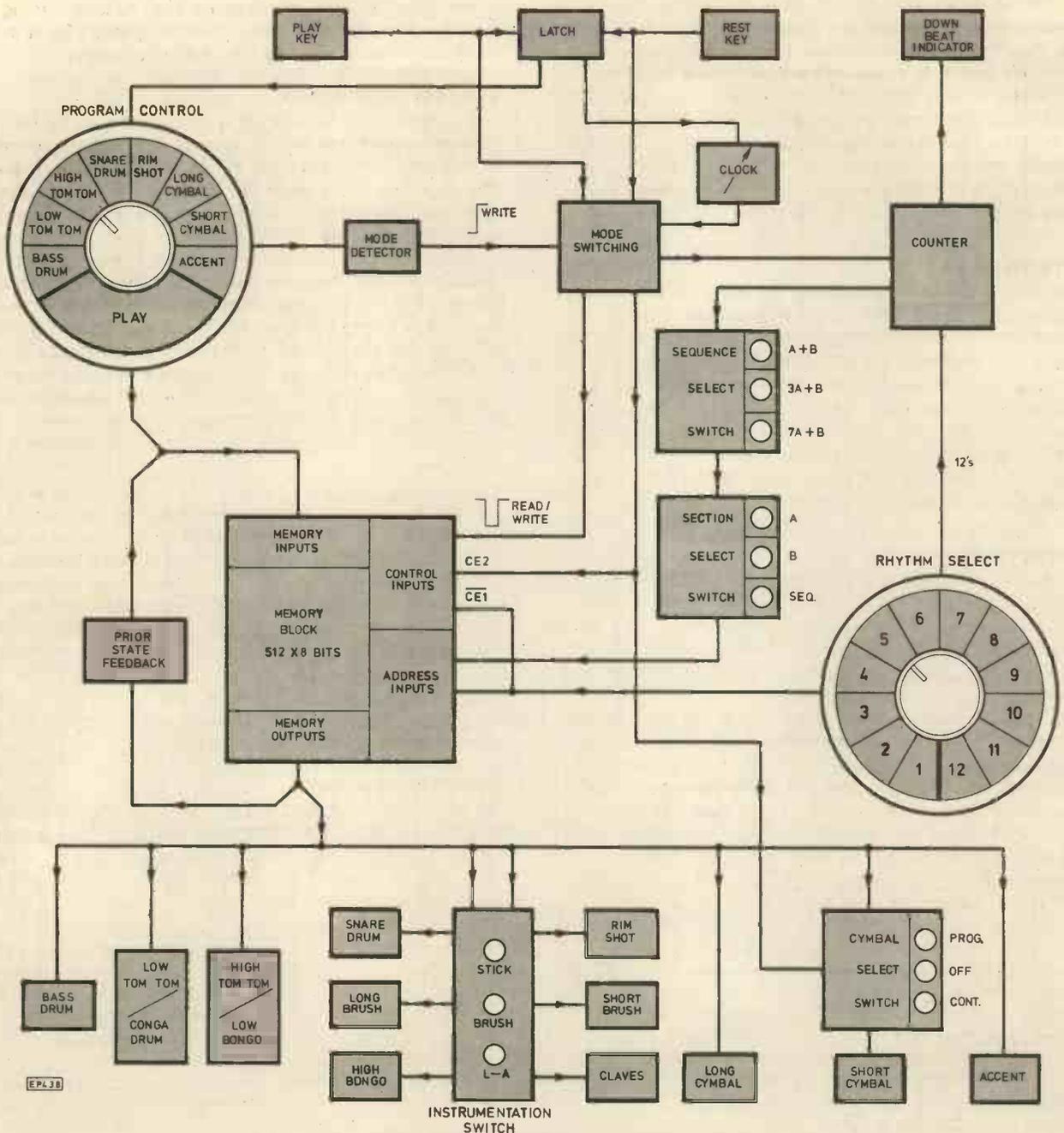



Fig. 2. Schematic of Master Rhythm

the counter input. Depression of the "Rest" key will reset the complete counter through IC3b, IC3a and D12, whilst the "Play" key will start the clock.

The counter consists of eight synchronously switched divider stages, the first four of which are decoded by diodes D5 to D8 to produce down beat indicator pulses in conjunction with D4. Outputs from the third and fourth dividers are decoded by diodes D10 and D9 to produce reset signals on the first four counters via D11 after every twelfth measure when R33 is raised by selection of a twelve measure category rhythm. The last four stages of the counter are decoded by diodes D13 to D20 which link with the "Sequence" select switch S5 to pass sequence address information via the "Section Select" switch S6. Counter outputs provide the incrementing address information required by the memory, whilst the fixed starting addresses are

provided through diodes D27 to D41 from the "Rhythm Select" switch. As described earlier the memories work in pairs, IC6 plus IC8 and IC7 plus IC9. The changeover chip enable signals $\overline{CE1}$ are provided in opposite sense through the inverter IC3c.

When the "Program Control" is in an instrument track position the high output from the mode detector prevents the passage of the clock through IC2c and enables IC2b to pass the pulses, which occur at the output of IC2a each time either the "Play" or "Rest" key is depressed, forward to IC2d and IC4c. The former provides the stepped clock required during the programming operation whilst the latter provides a negative sense write enable pulse timed by R6/C4 and R10/C5. The prior state feedback network consists of resistors R20 to R27 which protect the information on the non-operative tracks during programming.

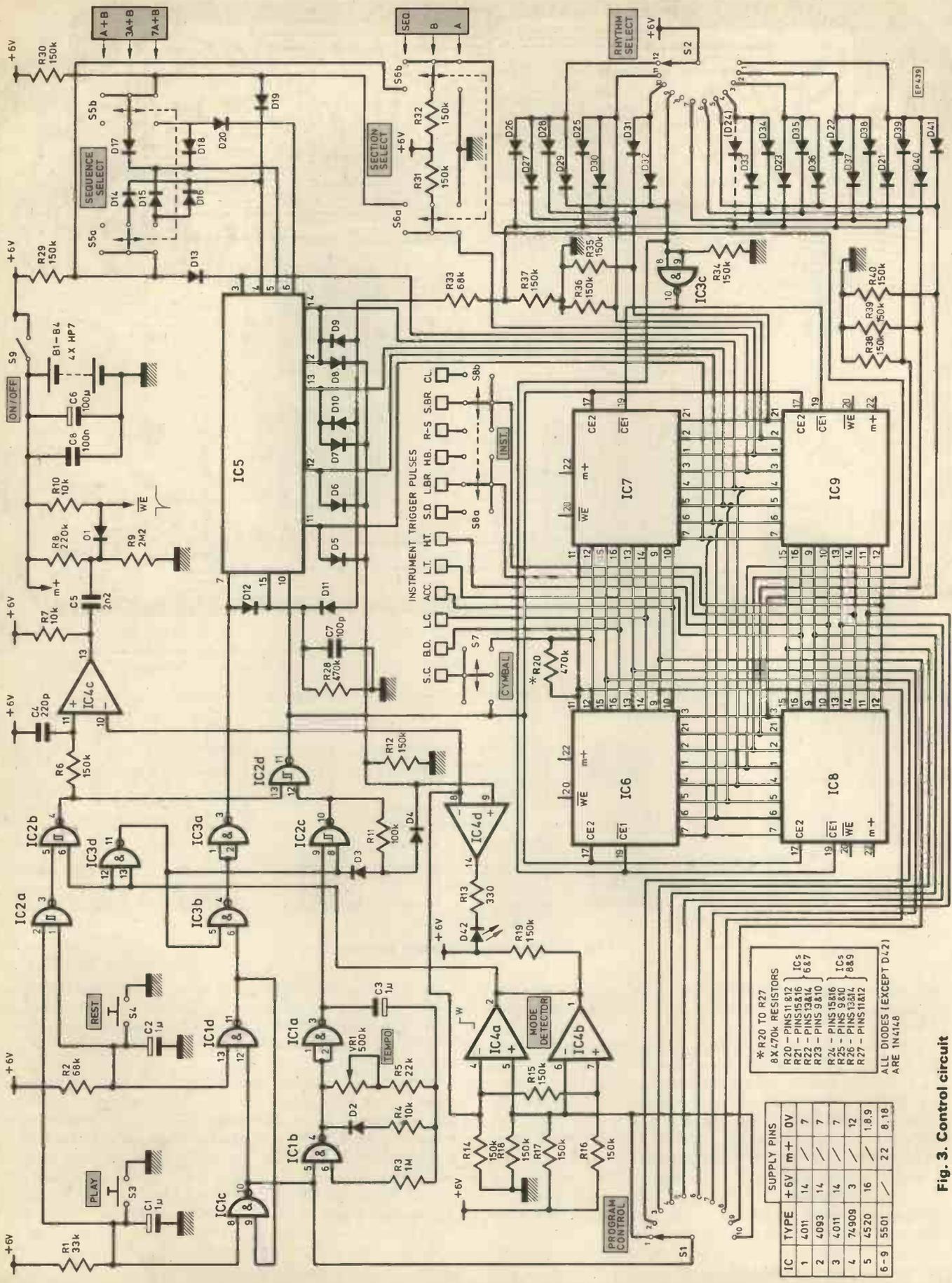

* R20 TO R27
 8x 470k RESISTORS
 R20 - PINS 11 & 12 ICs
 R21 - PINS 15 & 16 ICs
 R22 - PINS 13 & 14 ICs
 R23 - PINS 9 & 10 ICs
 R24 - PINS 15 & 16 ICs
 R25 - PINS 9 & 10 ICs
 R26 - PINS 13 & 14 ICs
 R27 - PINS 11 & 12 ICs
 ALL DIODES (EXCEPT D1,2)
 ARE 1N4148

IC TYPE	SUPPLY PINS	
	+6V	0V
1	4011	14
2	4093	14
3	4011	14
4	74909	3
5	4520	16
6-9	5501	22
		8,18

Fig. 3. Control circuit


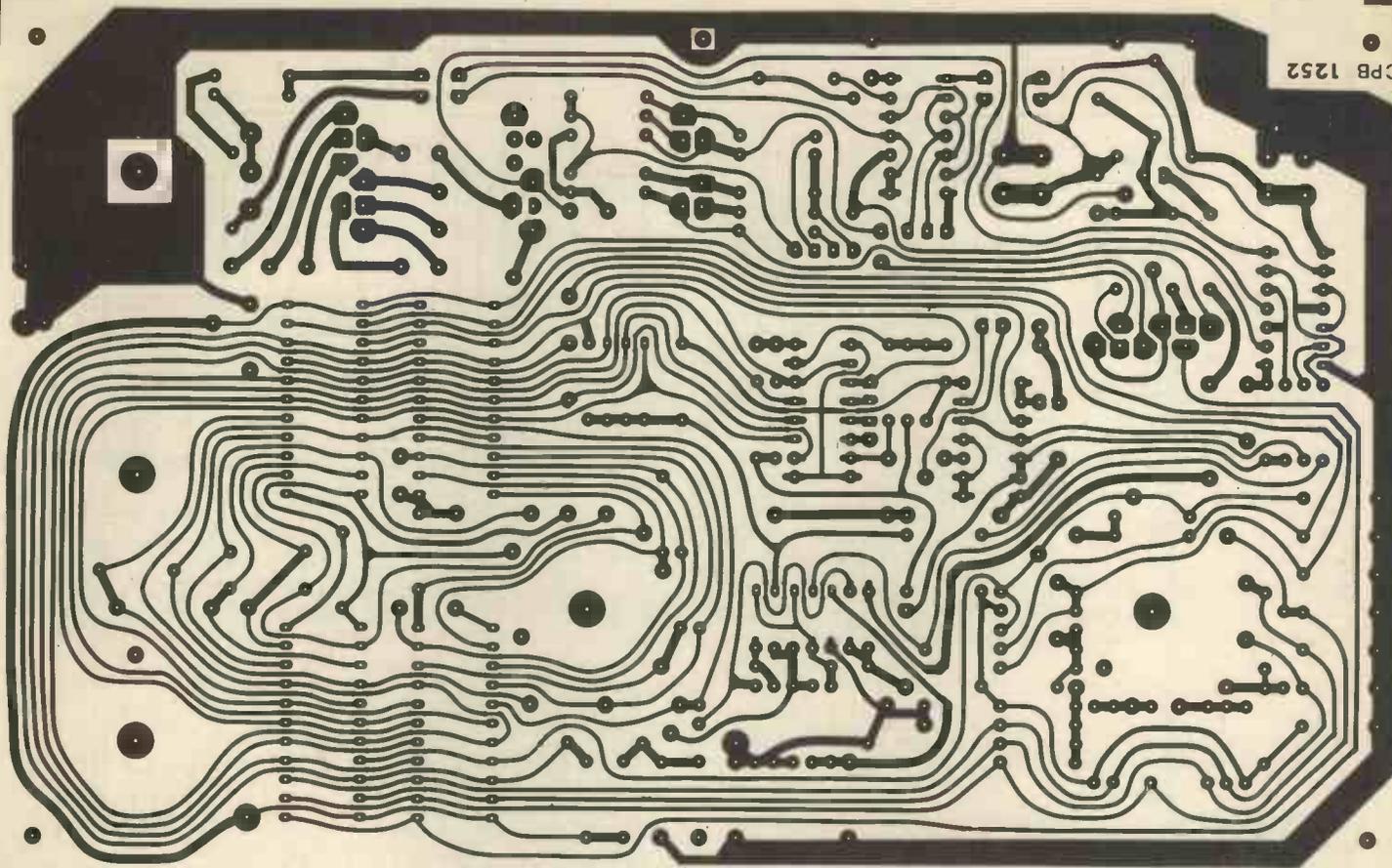


Fig. 4. Control p.c.b.

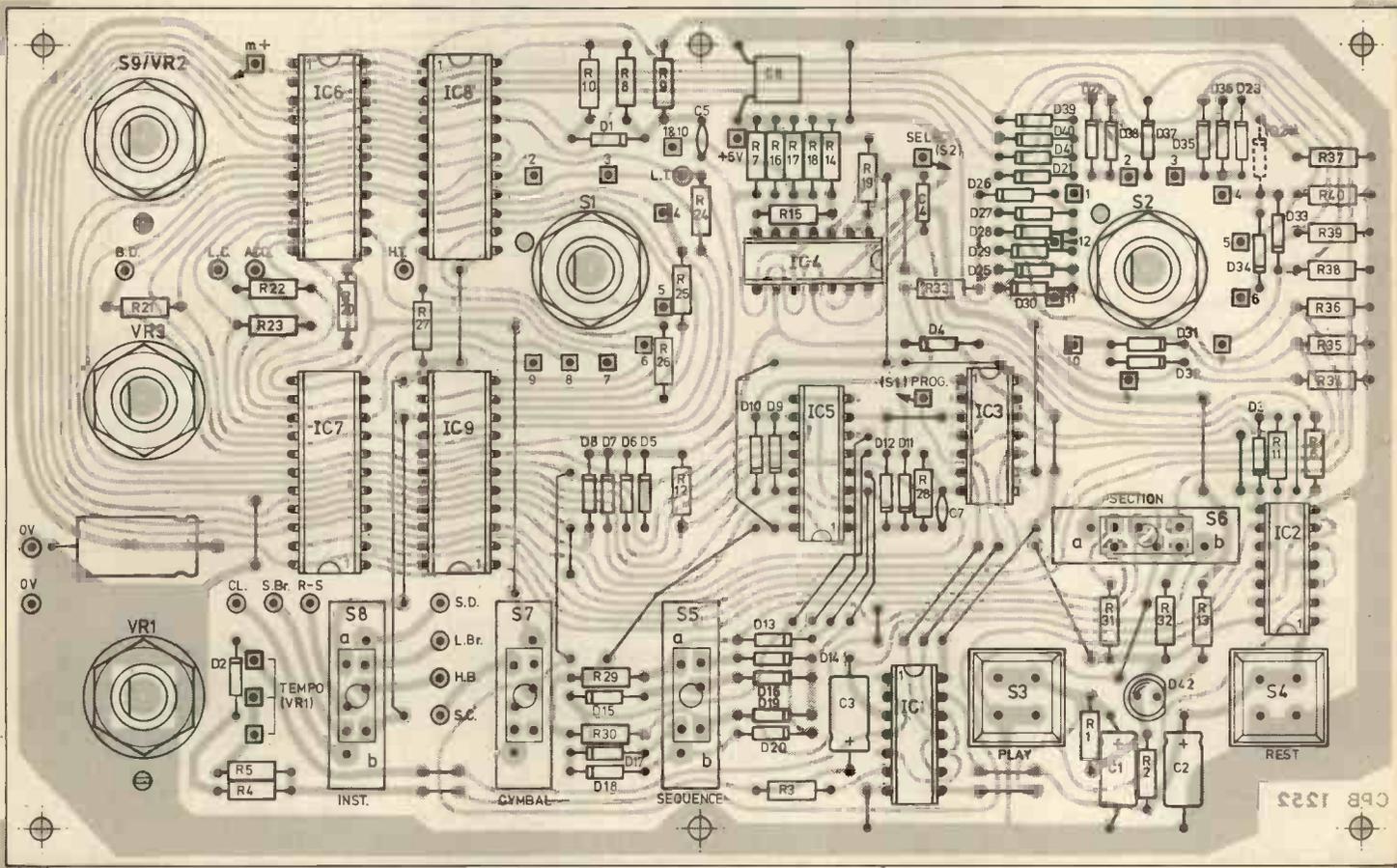

○ EXTERNAL CONNECTIONS
 ■ CONNECTIONS TO SWITCHES AND V.R.s

Fig. 5. Control board overlay

COMPONENTS

CONTROL BOARD

Resistors

R1	33k
R2	68k
R3	1M
R4	10k
R5	22k
R6	150k
R7	10k
R8	220k
R9	2M2
R10	10k
R11	100k
R12	150k
R13	330R
R14-19	150k (6 off)
R20-28	470k (9 off)
R29-32	150k (4 off)
R33	68k
R34-40	150k (7 off)
All resistors 0.25W, 5% carbon film	

Switches

S1	Single pole 10 way rotary
S2	Single pole 12 way rotary
S3-4	Single pole push-to-make (2 off)
S5-8	2 pole 3 way sliders (4 off)
S9	Single pole (see potentiometer VR2)

Capacitors

C1-C3	1 μ /16V axial electrolytic
C4	220p ceramic plate
C5	2n2 ceramic plate
C6	100 μ /16V axial electrolytic
C7	100p ceramic plate

Diodes

D1-41	1N4148 (41 off)
D42	i.e.d.

Integrated Circuits

IC1	CD4011
IC2	CD4093
IC3	CD4011
IC4	MM 74C909
IC5	CD4520
IC6-9	TC5501P (4 off)

Potentiometers

VR1	500k lin
VR2	25k log with switch
VR3	25k log

Miscellaneous

0.040in terminal pins 12 off
 22 pin i.c. sockets 4 off
 16 pin i.c. sockets 1 off
 14 pin i.c. sockets 4 off
 control knobs 1in dia 2 off
 control knobs $\frac{3}{4}$ in dia 3 off
 printed circuit board 1 off

A complete kit can be obtained from **Clef Products, 16 Mayfield Rd., Bramhall, Cheshire SK7 1JU**

CONTROL P.C.B.

From the photograph it can be seen that in addition to controlling the control circuitry the Control p.c.b. acts as a mechanical support for all switches and the "Level," "Tone," and "Tempo" potentiometers. Diode D24 is shown in brackets and is the twelve measure connection for position 4 on the "Rhythm Select" switch. Since the sample pattern given later for rhythm 4 is based on sixteen measures this diode is omitted. The corresponding twelve measure diodes for positions 1, 2, 3, 11 and 12 are D21, D22, D23, D25 and D26 respectively and may be omitted as required. Rhythms 5 to 10 inclusive are permanently arranged on a sixteen measure basis.

ASSEMBLING THE P.C.B.

The Control p.c.b. has a considerable number of interconnection tracks and it is advisable to inspect closely the p.c.b. before proceeding, particularly ensuring that bridges are not present between the memory tracks or the large switch pads. Figs. 4 and 5 show the track layout and component overlay for the p.c.b.

The twelve terminal pins should first be inserted in the board, note that many of the interconnections are made from the rear of the p.c.b. where pins are not required. All resistors and diodes can be inserted and soldered next. It is advisable to use a small soldering iron with a maximum bit size of 3/32in, and in particular it will be found to help if 22 s.w.g. solder is used rather than thicker varieties which aggravate the possibility of solder bridges. Wire links can be inserted after soldering the i.c. sockets, advisable throughout, followed by the capacitors.

The three position switches are pushed into the holes in the p.c.b. and are a tight fit. The "Sequence" switch requires two tags to be cut off before insertion and care should be taken not to damage the switches. However it is important for front panel alignment that the switches should seat on the p.c.b. and it may be necessary to slightly increase the size of the switch tag mounting holes due to the mechanical spread on the switches. To assist in later alignment of the front panel it is also suggested that at this stage the i.e.d. is soldered temporarily some 0.5in off the p.c.b. The "Play" and "Rest" keys should be easy to locate with the four pin fixing provided.

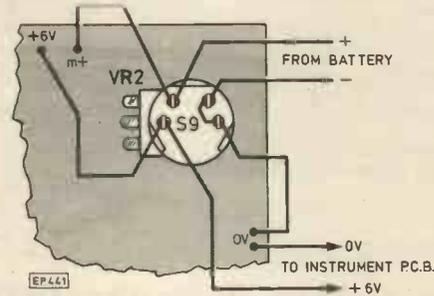


Fig. 6. Wiring connections to S9

ROTARY SWITCHES

The rotary switches are single pole, twelve position, and when supplied they have a small metal ring, concentric with the shaft, which can be repositioned to alter the switching compass. In the case of the "Rhythm Select" switch the ring should be removed completely to allow the full twelve positions to be used. The "Program Control" should be set to give ten positions by adjustment of the ring position to its second slot.

Wiring of the rotary switches to the p.c.b. is carried out from the track side using single core tinned wire of 22 s.w.g. The numbers enclosed by squares on the component ident side of the p.c.b. correspond with the switch tag numbers. Note that pins 1 and 10 on the "Program Control" switch are shorted together and that the connection points for the centre keys are some distance away requiring insulation. These are marked **SEL** for the Selector Switch and **PROG** for the "Program Control" switch. It is also worth noting that tag 8 on the "Rhythm Select" switch and tags 11 and 12 on the "Program Control" do not have connections to the p.c.b.

POTENTIOMETERS

The "Tempo" control is soldered to the three pads on the p.c.b. again using wire links, whereas the potentiometer sections of the "Level" and "Tone" controls are later connected to the instrument p.c.b. only. Fig. 6 shows all the connections, from the switch S9 integral with the "Level" control VR2, to the control p.c.b. supply points. These are important since they control the standby system in addition to switching on the main operating power.

Next Month: Instrumentation and setting up

At these sensational prices you can afford to give



CHRISTMAS TIME PRESENTS

Great gifts at giveaway prices. For your family. Your friends. Or yourself.

SEIKO QUARTZ CALCULATOR/ALARM

Only £49.95 + 85p p&p

Continuous display of hours, minutes, seconds with day, alarm indicators. Optional display: month, date, AM/PM with day indicator. Calculator (16 key) performs arithmetic, percentage, constant and power calculations. 12 hour alarm with AM/PM indication, rings twice a second for 10 seconds, then four times a second for 10 seconds. Display flashes as battery life nears end. Back light. Water resistant. Adjustable stainless steel strap.

MITRAD MD605 QUARTZ LADIES MUSICAL ALARM

CHRONO Only £11.95 + 85p p&p

Continuous display of hours, minutes, seconds. Optional display: day, date, month. Auto calendar. Chronograph with lap timing facilities to 1/10 sec. 24 hour alarm plays 30 seconds of Beethoven's 'Für Elise'. Back light. Infinitely adjustable stainless steel strap.

MITRAD MD610 QUARTZ GENTLEMAN'S MELODY

ALARM Only £16.95 + 85p p&p

Case thickness only 5mm. Continuous display of hours, minutes, seconds with date and mode indications. 'Running horse' chronograph to 1/10 sec. 12 hour alarm plays 30 seconds of 'Yellow Rose of Texas'. Back light. Infinitely adjustable stainless steel strap.

MITRAD PEN WATCH Only £11.15 + 85p p&p

Elegant stainless steel ballpoint pen combined with a quartz precision timepiece. The five function LCD watch displays hours, minutes, seconds, month and date and has a computerised four year date memory. In presentation case with spare pen refill.

From the collection of 12 month guaranteed leading make products offered through Mitrad's 7 day distribution system and backed by Mitrad's own service organisation. For complete product range, ring or write for catalogue. Trade price list available for bulk buyers.

MITRAD The Premier mail order house specialising in quality products and superior after-sales care.

To: Mitrad, 68-70 High Street, Kettering, Northants. Please send me:

- Seiko Calculator/Alarm at £50.80 inc. p&p MD605 at £12.80 inc p&p
 MD610 at £17.80 inc p&p Pen Watch(es) at £12.00 inc p&p

Total value of my order £ _____

I enclose cheque/PO or debit my Access/Barclaycard



No. _____ Signature _____

Name _____ (block letters please)

Address _____

PE/12/80

* Credit card holders may telephone (0536) 522024 24 hours a day stating card number for immediate attention. All orders despatched within 7 days. Delivery subject to availability. Full refund if not completely satisfied. Mitrad. Registered in England No. 2554356.



Mitrad, 68-70 High Street, Kettering, Northants.

20mA LOOP

S.A. WITHEY

OPTO-COUPLED RS232 INTERFACE

ALTHOUGH designed to interface a Nascom 1 microcomputer with a KSR33 Teletypewriter, this current loop needs very little or no modification to suit other printers and microcomputers with 20mA serial output. The circuit is in three sections; power supply, opto-isolator, and 20mA (or 60mA) current loop mounted on a single, easily drawn p.c.b.

POWER SUPPLY

On test it was found that 400mA at 9V was more than sufficient to activate the selector magnet of the teletype, normal being 500mA at 20V. A 14.5V 500mA transformer was chosen to power the circuit, as these are easily obtainable for a very modest outlay, as are the 1A bridge rectifier, 1000 μ F 40V electrolytic capacitor and 13.5V Zener diode, all of which provide a stabilised power supply. With the exception of the transformer, the components are mounted on the p.c.b.


OPTO-ISOLATOR

R1 is chosen to protect the i.e.d. and any resistance value between 470 and 1k should be sufficient. The reverse-parallel diode D5 bypasses negative peaks across the i.e.d. The light emitted by the i.e.d. causes current to flow through the photo-transistor, which is amplified by TR1 and TR2. The high gain causes a square wave to appear at the collector of TR2. VR1 is used to adjust the current to 20mA or 60mA as required. It also serves as a final adjustment to achieve 500mA at the output to the printer selector magnet.

Similar to those installed in converted teletypes, enhancing the price by anything up to £80, yet can be built for only a few pounds

CURRENT LOOP

TR3 and TR4 can be any power transistors of the 3053 and 3055 n.p.n. types respectively. D7 can be any 1 or 2A diode. Because of the heat generated around the junction of R9 and R10, R7, R8 and R9 should be 2 to 4 Watt wirewound resistors and R10 a 10 Watt wirewound. These resistors run much cooler when the selector magnet is connected than they do whilst under test before installation. R6 might require changing to adjust the current gain to produce 500mA at the output.

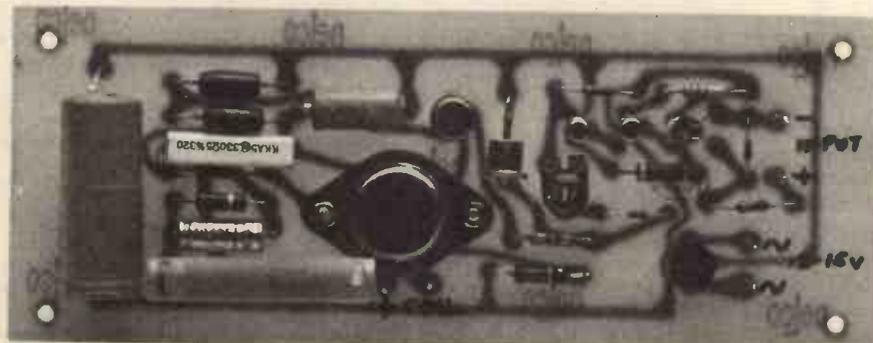

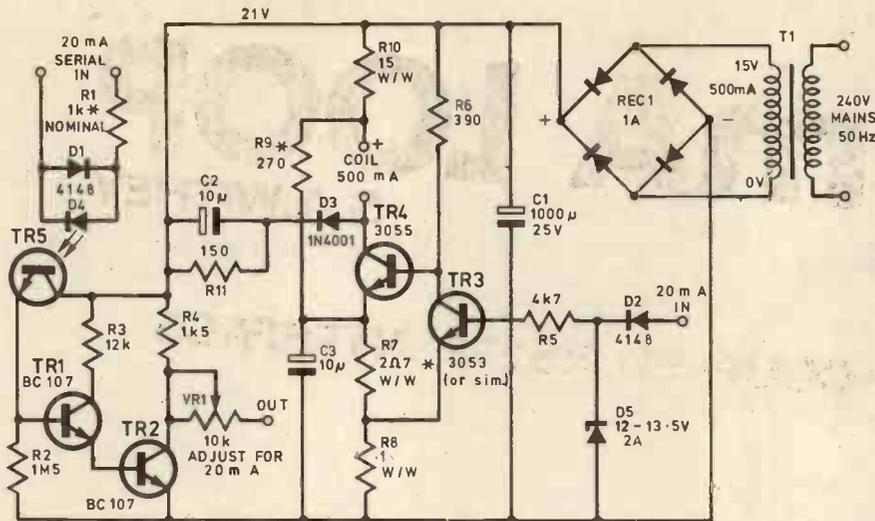


Fig. 1. Circuit diagram of opto-coupled 20mA loop. When in opto-isolated mode, the OUT from VR1 is connected to IN at D2 (as on p.c.b.) The input at D2 can be used as a non-isolated RS232 input

EG394

For a mark input a positive current is applied to the anode of D2. This provides a positive bias to the base of TR3 which overcomes the normal negative bias supplied through R5 and stabilised by D5. TR3 will turn off as the increasing positive current reaches one half of its final value. The collector of TR3 then goes negative and this negative potential is applied to the base of TR4 which turns TR4 on. R8 provides emitter bias to TR3 and supplies a regenerative action to the transistor.

The selector magnet of the teletype is connected between the collector of TR4 and the junction of R9, R10. On marks the current rises to 500mA and energises the magnet. On spaces the positive input bias decreases and TR3 is turned on at the half line current point by negative bias through R5. The collector of TR3 rises towards a zero potential, applying reverse bias to TR4, de-energising the magnet. The selector magnet opposes the change in current and applies a transient potential to the collector of TR4. D3 now conducts and passes the transient potential to C2 and R11 which limits the potential to a value well under the breakdown voltage of TR4, while selector magnet energy is being dissipated.

CONSTRUCTION

R10 gets very warm in operation and should be mounted away from the p.c.b. to aid heat dissipation.

D4 should be mounted on long leads and bent over the photo-transistor. They are joined with a short length of coaxial sleeving. The ends should be left open while tests are carried out so that room light shines through the end and activates the photo-transistor, thus preventing the printer from chattering. When the unit is connected to a 20mA current a plastic pen-cap makes a neat cover.

Should a photo-transistor not be available, the top can be carefully cut from a BC107 and the base exposed.★

COMPONENTS . . .

Resistors

R1	1k nom. see text
R2	1M5
R3	12k
R4	1k5
R5	4k7
R6	390 see text
R7	2R7 w.w. 2W
R8	1 w.w.
R9	270 w.w.
R10	15 10W
R11	150

All resistors $\frac{1}{2}$ W 5% unless otherwise stated

Capacitors

C1	100 μ /40V
C2, C3	10 μ /25V (2 off)

Transistors And Diodes

REC1	1A bridge rectifier
D1, D2	4148 or similar (2 off)
D3	4001 or similar
D4	0.2 in. red l.e.d.
D5	12V or 13V Zener 1.5W
TR1, TR2	BC107 (2 off)
TR3	2N3053
TR4	2N3055
TR5	n.p.n. photo-transistor

Transformer

T1	240V 50Hz prim. 14.5 to 20V 500mA sec.
----	--

Constructors' Note

A complete kit of components is available from Watford Electronics

20mA

LOOP

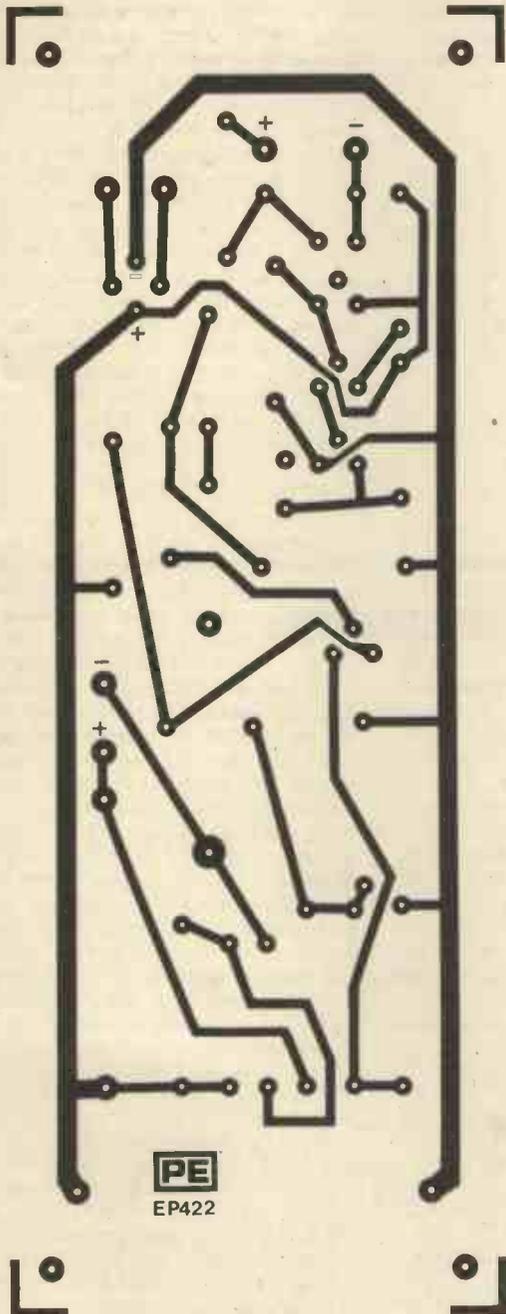


Fig. 2. Printed circuit (actual size)

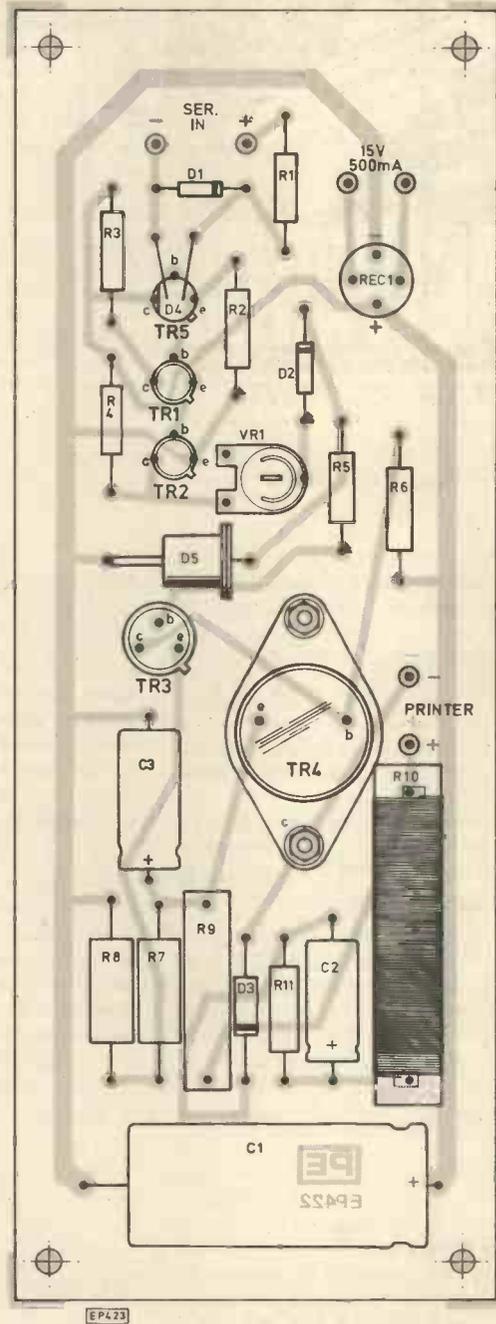


Fig. 3. Component layout



SPACEWATCH

FRANK W. HYDE

THE SHUTTLE TELESCOPE

This infrared instrument is a natural addition to the joint United States, United Kingdom and Netherlands venture, which is expected to be launched in 1982. Its full title is Shuttle Infrared Telescope Facility. It is an observatory 1-metre class instrument. It will be in operation outside the atmospheric difficulties such as the absorption and emission of radiation. This will mean that the degrading of quality, which is suffered by telescopes in lower orbits, can be avoided. In fact the limitations of the SIRTf will be due to the natural background of space.

To the techniques to be used in this mission, which is scheduled for 1987 or thereabouts, will be added the advantages of cryogenic control. Such control can provide considerably greater sensitivity. Part of this will be derived from the fact that the operational area will be outside that which limits sensitivity, namely below the wavelength of 30 micrometres and above 300 micrometres. The normal background in these ranges is spoiled by water vapour and carbon dioxide. It is possible to overcome some of this by the use of aircraft and balloons. However there is still the line of sight difficulty due to random absorption and emission: So important are data that can be retrieved in this part of the spectrum that pressure from astronomy has virtually demanded that the latest techniques are used. At the present time detectors are available which, in ground based telescopes, are limited only by photon background. Much of the noise and the atmospheric limitation is at a level several orders of magnitude above the sources to be studied. The use of cryogenic techniques enables this background to be overcome with the result that a cryogenic system outside the atmosphere will offer up to a 1,000 times increase in sensitivity above current equipment. For the first time it will be possible to study high-luminosity extra-galactic sources and stellar formations.

The value of scientific advantages such as the SIRTf lie in the ability to look forward in time as well as backward. The early history of the expansion of the Universe with the formation of galaxies may lie in this cosmological area because of the redshift. Once again the real workload lies with the electronics of control for which the specification is severe. It is required that there shall be a pointing accuracy ± 1 -arc/second and a guidance system to ensure a stability of 0.25-arc/second. Other requirements are that the primary mirror must be held below 12 Kelvin for the first half of each 7 to 14 day mission and thereafter below 16 Kelvin. The secondary mirror must also have a low temperature control at 10 Kelvin or less for the first part of missions and then 15 Kelvin maximum for the rest of the period.

For a nominal 14 day mission SIRTf would need to carry about 1,300 litres of supercritical gaseous helium. This will be held at a pressure of 6 atmospheres to cool the telescope optics and the body. There will be facilities to carry superfluid helium to cool the instrument chamber to a level of 2-Kelvin. There are current investigations to get the temperature down to a few tenths of a degree kelvin using the isotope helium 3. This is a case of the sword into ploughshares for Helium 3 is a byproduct of weapons technology.

There are difficulties in attaining the ultimate goals but already there are satisfactory signs of progress. For example the optical systems will be diffraction limited at 5 micrometers. This can be achieved using optical grade beryllium. There is a doubt as to whether that beryllium can attain the 2 micrometre diffraction. This figure is of importance for the observation of proto-galaxies, these are galaxies that are forming and would show a high redshift. Other materials are being investigated and these matters will be on-going during this continuing updating. The first flights will be about 14 hours duration rising to 30 hours. The reusable system is expected to reach mission durations of 30 days with a reusable condition free of replacement of any major part for 20 missions.

The aperture of the telescope is .85 metres in diameter and 9.2 metres in length. The cryogenic tanks, the electronics and the pointing systems are housed outside the main shell. There is a sun shield and a collapsible cover to reduce the off-axis radiation in to the telescope. This allows the main axis of the telescope to come within 45 degrees of the sun or the earth. The optical arrangement is that of a primary and secondary mirror arranged in what is known as the Ritchey-Chretien-Cassegrain configuration. The telescope can be used for over a wide range of studies which include:—

The observation of quasars, star formation, normal galaxies; objects in the solar system such as asteroids, comets and the satellites of the outer planets, also the observation of mass exchange between stars and the interstellar medium. It would also be possible to detect the massive halos of cool stars surrounding galaxies, with the identification of high redshift galaxies in formation.

THE HEART OF A SUPERNOVA

With optical activities growing all the while

it is easy to miss the new developments in radioastronomy. However the 5 kilometre radio telescope at the Mullard Radio Astronomy Observatory has been in operation investigating the Tycho Brahe supernova remnant. This was observed to explode in 1572. This is a Type I supernova, a most bright and energetic star explosion.

The discovery made at the observatory at Cambridge by Steve Gull and Guy Pooley was a very small but intense source of radiation at the centre of what remains of the supernova. Until now only one other nebula has been shown to have a Pulsar and this was the Crab Nebula which is within our own galaxy. The radiation of the Tycho remnant was detected at a wavelength of 11 cm. With the high resolution of this radio telescope the picture of the collapsed star can be built up in considerable detail. The observer's suggest that the pulsar or neutron star is in fact the collapsed star. It is not yet finally decided what the real answer is because there could be other reasons for the small star like object being present. If it is in fact the final 'bit' of the original star then it must be moving at 2000 k/ms a second. This is about 10 times faster than known pulsars. Other observatories are now checking on this star but it may be some time before it is confirmed.

THE SOLAR WIND

Back now to the Earth itself. There is a new collaboration of scientists from 11 countries which began in November. It is perhaps one of the more ambitious projects to undertake the study of the physics of the upper atmosphere. Some 200 scientists are involved. It is expected that nearly fifty rocket launches will be made and observations from 37 ground stations supplemented by satellites and balloons will provide data about the upper atmosphere. The main object of the exercise is to study the atmosphere from 80 to 200 kilometres above the Earth during a magnetic storm.

Magnetic storms are severe disturbances of the earth's magnetic field by the solar wind. There is a continuous radiation which forms the solar wind but this is enhanced by flares and sunspots. The magnetosphere round the earth becomes distorted and the tadpole like tail which appears on the side of the earth away from the sun is extended. The plasma which is composed of ionised particles mostly of hydrogen carries tremendous energy. The particles are dissipated in the upper atmosphere. The solar wind expelled radially from the sun is composed of protons and electrons. When they near the magnetosphere they are lured out of their straight paths and focussed towards the poles. As the denser part of the atmosphere at about 150 kilometres is reached larger protons are inhibited but the electrons move on. As a result there is a drift of high energy current in a westward direction. This leaks into the atmosphere away from the poles.

Following the article by Frank Hyde on Velikovsky in the April 1980 Spacewatch, we have received many letters from readers, expressing varying opinions. Frank Hyde's final reply to these letters is printed in Readout on page 50.

and revolve around numerical words such as "two", "thirty", "pounds" etc.

One of the advantages of the fixed-word approach is the extreme ease of interface with any logic system. To aid in the evaluation and addition of speech to any computer or logic device, the interface is described below, as a constructional article. The speech board is available separately, however, with a full technical specification for the user to design his own interface in any way he wishes.

TSI SPEECH SYNTHESIS BOARD

Telesensory Systems Inc (TSI) are the manufacturers of several products for the synthesis of human speech. They produce a talking calculator which has found obvious application for the blind. The units of particular interest, produced by TSI, are the fixed 24 and 64 English word units, consisting of a controller chip (called the CRC), and one or

speech synthesis


Dr A.A. Berk · part 2

LAST month, an introduction to the theory and history of speech synthesis was given as a precursor to this month's constructional article. An American speech board (manufactured by Telesensory Systems Inc.) is available through Modus Systems Ltd., and its interface to any general computer or logic system is described. The Comukit and Edukit are used to give examples of the interface, and hence provide readers with a practical demonstration of the way in which speech may be added to their own type of system.

INTRODUCTION

Converting the theory of last month's article into practice at the "one-off" small computer level, was, until recently, rather difficult. Texas Instruments, for instance, have not made their speech products available on this experimentation level, and most other companies are only interested in the large volume "OEM" buyer, who needs expensive customised speech sets. To experiment with the technology, the alternatives include some excellent, but relatively expensive phoneme analysis boards, whereby any word may be synthesised by sending it information of the phonemes which make it up. To "try out" speech synthesis, a far better approach is to use a cheap, mass produced fixed-word synthesiser giving digitally controllable speech on demand from any computer or logic system. If more than one speech set is also available then so much the better. It is with this in mind that Modus have imported a range of fixed-word speech synthesisers, for applications where a customised vocabulary is unnecessary. The words available are basic

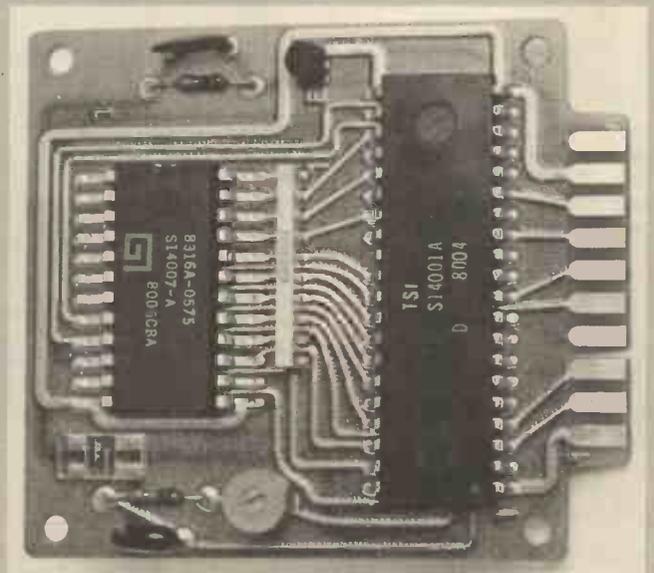two 2K ROMs, respectively. The photograph shows the chips mounted on a p.c.b. with one or two other discrete components, and a gold-flashed edge connector. The size of the board is 66x73x13mm, with 0.156in. pitch edge connector tracks. The 64-word versions have two ROMs on the board and are slightly larger.



TSI speech board

The CRC is a general speech synthesis chip which requires data of pronunciation, pitch, word-length etc. from a ROM to create the necessary sounds. To store the raw data of a word on a read only memory, a complex computer program accepts speech through a microphone and converts it to data suitable to the CRC. TSI have commissioned ROMs, by this method, for several different speech "fonts", and standard vocabularies in a number of different languages (German, French, Arabic etc). The words available here are detailed in Table 1.

S2A (Calculator type 24-words)	S2B (Standard English 64-words)	S2C (ASCII 64-words) space, X-point, quote, number, dollars, percent, and, apostrophe, left parent, right parent, star, plus, comma, minus, point, slash, zero, one, etc. nine, colon, semicolon, less than, equals, greater than, mark, at, A, B, C, (etc.) ... Z lower case, tone, upper case, up arrow, control
oh	Same as S2A plus:	
one	ten, eleven, etc.	
two	twenty, thirty, etc.	
three	hundred, thousand,	
four	zero, and, seconds,	
five	degrees, dollars,	
six	cents, pounds,	
seven	ounces, total,	
eight	please, feet,	
nine	metres, centimetres	
times-minus	volts, ohms, amps,	
equals	hertz, d.c., a.c.,	
percent	down, up, go,	
low	stop, low and high tones	
over		
root		
em(M)		
times		
point		
overflow		
minus		
plus		
clear		
swap		

N.B. The ASCII set is of course arranged in exact ASCII order to convert any standard binary code into a verbalisation of the corresponding ASCII character.

TABLE 1. Vocabulary of the three TSI speech boards available

The speech board acts by accepting a control word of six bits to identify the spoken word to be output, followed by a start pulse to tell it to begin speaking. The board is also equipped with a "busy" line to tell external devices that a word is in the process of being spoken. Fig. 2.1 shows a block diagram with timing signals to illustrate the process. The timing shows that the speech output itself does not occur until the "start" signal has fallen to zero. In a typical interface set-up, a set of six latches would feed the control word to the CRC, the "start" signal would fall after 140 micro seconds or more, and the output would be forthcoming. It must be noted that if the "start" line should rise at any time during the speech output, the output is stopped in mid flow. When the "start" line falls again, the word is started from the beginning. To assist in preventing this occurrence, the "busy" line should be monitored by the external system, and the "start" line only operated when the machine has finished talking.

INTERFACING

As is clear from the above, the logic interface requirements are straightforward, and the only problems arise from the rather strange power supply requirements, which are -5V and -15V. However, by a simple trick, the -5V level can be derived from the normal supply of a microcomputer, while the -15V supply must be derived separately.

The final requirement of the board is for audio circuitry of essentially two types, a filter and an amplifier. The sound is produced by the CRC via a digital to analogue converter

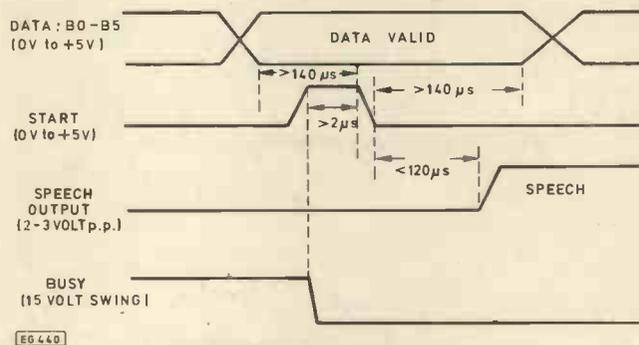
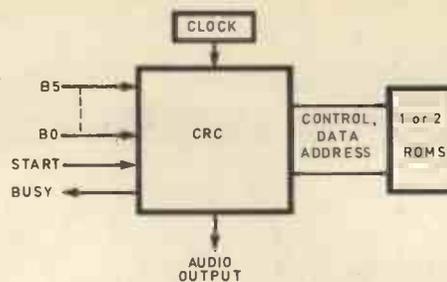


Fig. 2.1. TSI Speech Board

(DAC). This implies that the output waveform is not completely smooth. Its variation from level to level is by a set of steps. A sinewave derived from a DAC will have the form shown in Fig. 2.2. Note that the horizontal width of each step is constant, while the vertical steps vary to approximate the sinewave. This shows that the waveform thus formed may be viewed as a sinewave modulated by a constant frequency squarewave. However, a squarewave contains the elements of many frequencies mixed together (depending on how square it is), and hence the voice output must be passed through a band-pass filter allowing just the band of frequencies needed for voice to pass. To give an idea of the frequencies needed and some typical characteristics, Fig. 2.3 reproduces TSI's suggested op-amp filter response. The three decibel level is often used as a method of comparing such responses, and the frequencies at which this level cuts the graph are called the "corner frequencies". The reason for their importance is that at these frequencies, the incoming waveform's amplitude is exactly halved by passing through the filter.

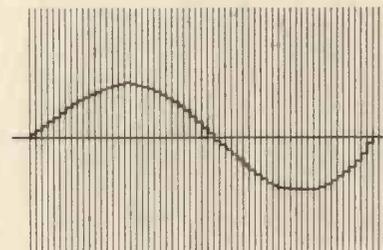


Fig. 2.2. Sine wave output from D to A converter

In considering the TSI output, however, it was found most advantageous to be able to vary the response to different ears, and for different loudspeaker arrangements. After much experimentation, a very simple single op-amp band-pass filter was selected, which, together with an integrated circuit power amplifier gave acceptable results. This circuit is

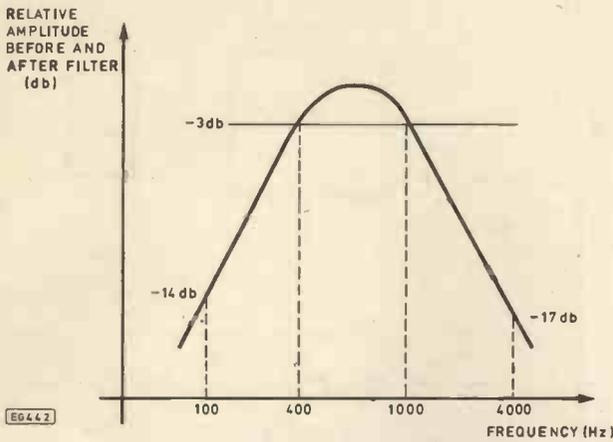


Fig. 2.3. Bandpass filter characteristics

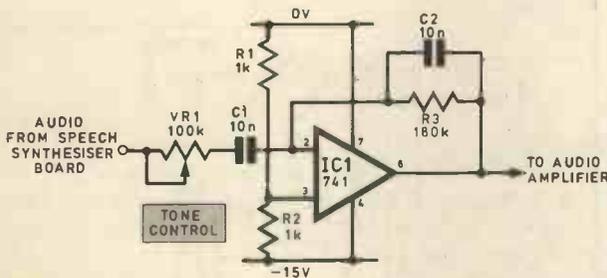


Fig. 2.4. Bandpass filter

shown in Fig. 2.4, and includes a tone control, which varies the filter's pass characteristics.

THE INTERFACE UNIT

As explained above, interfacing is dependent upon three main systems: logic, power and audio sections. All these are included on the interface board described here, along with such important details as the correct edge-connector into which the TSI speech unit plugs.

Fig. 2.5 shows a complete circuit diagram of the interface unit, which is designed to be as complete as possible. A separate 5-volt supply is needed for the logic, as well as a small 10 to 20 volt transformer (at around 250mA) and an 8 ohm speaker.

The word to be spoken is requested by supplying a set of bits (D0 to D5) along with a positive going "latch enable" pulse. The word is latched into IC2 and presented to the speech synthesis board. When the "start" line changes from high to low, and held there, an audio signal is output from the synthesiser. IC1 filters this audio signal in a manner partly determined by the setting of VR1. The filtered signal is a.c. coupled to a volume control and the i.c. power amplifier IC3 which feeds an 8 ohm speaker through C4. The power supply on the board adds 10 volts to the 5 volt supply from the external logic, and just requires an external mains transformer as indicated. The "busy" signal output swings through 15 volts and to convert this to a 5 volt swing, D5 and R5 are included.

CONSTRUCTION

The p.c.b. design and component layout for the unit is shown in Fig. 2.6.

Assembly of the unit is straightforward, and the sockets for the i.c.s should be inserted and soldered first, followed by the edge-connector and ribbon cable connector. Note that the ribbon cable connector has some spare pins for expansion. Discrete components and regulator should be fitted next, observing the correct polarities with great care. It is a very good idea to check that there are 10 volts between -5V and -15V lines from IC4, before proceeding. The 5 volt

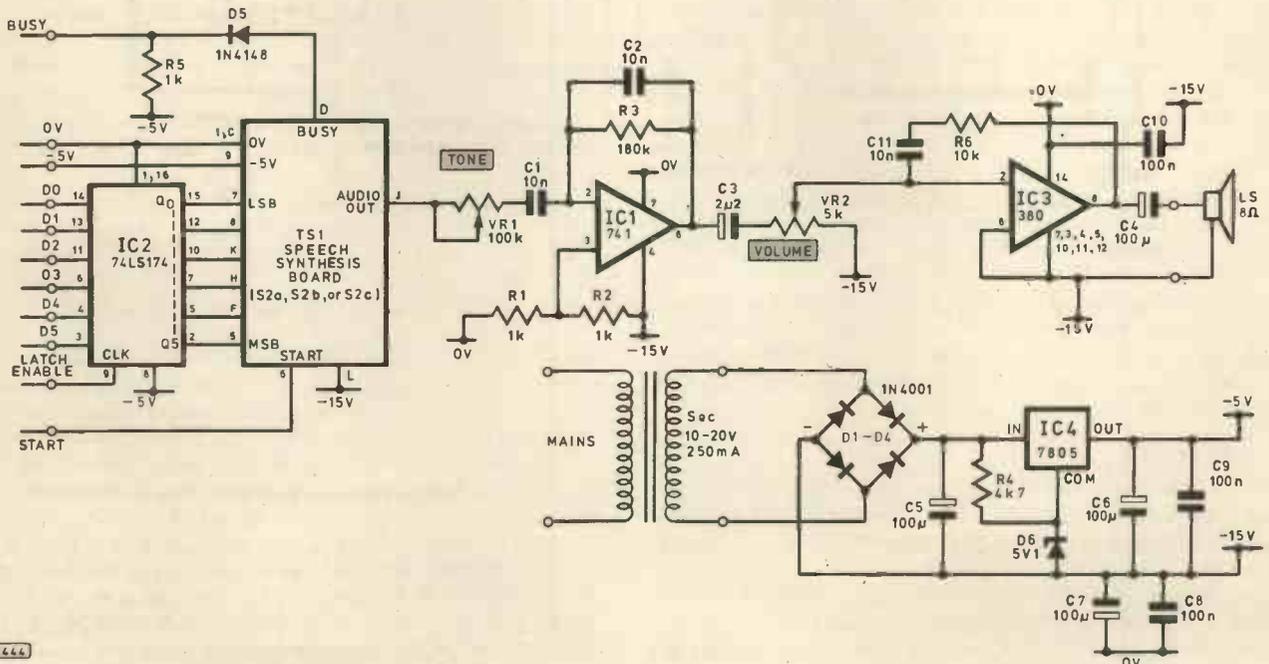


Fig. 2.5. Interface and speech board circuit diagram

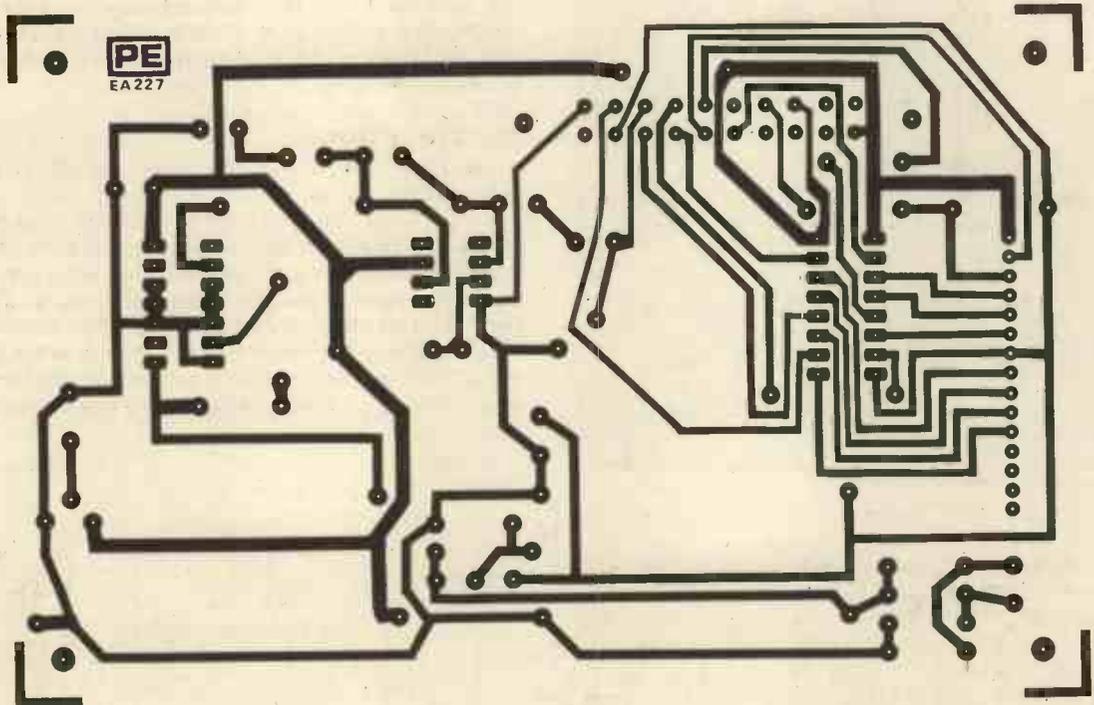
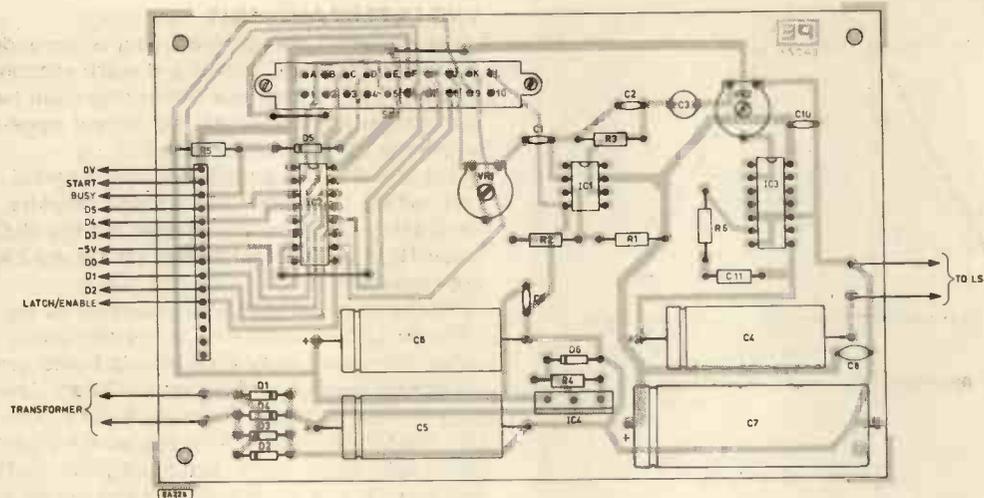


Fig. 2.6. P.c.b. design and component layout for the interface board (Copyright Modus Systems Ltd)

supply can then be connected and a check performed for 15 volts across IC1 and IC3 sockets. Check, also, that the correct supply levels are present at the speech synthesiser connector and IC2 socket. When you are fully satisfied, switch off and insert IC3. With the volume fully up, a hum should be audible at the loudspeaker when the wiper of VR2 is touched with a finger. Turn the volume down to ensure that this causes the hum to disappear. This will verify IC3's operation.

Next, insert IC1, IC2 (the correct way round) and the speech synthesiser board, with the component side inwards as shown. The unit will sound highly unstable unless the "start" line is held at "one" or "zero" (TTL levels). The line should be taken to zero (-5V) through a low resistance (100 ohm for

instance). The line may then be taken high and back to zero to check for word output. If none appears, connect all the inputs of IC2 to zero, and pulse the "latch enable" low, then high. This should load the word "Oh". VR1 and VR2 should be adjusted for the best sound. It is useful to note that the word's pitch may be adjusted by the pot on the speech synthesiser p.c.b.—the pot should be set at half way initially—the total number of turns for its full travel is about four and a half, the pot should be turned one way until obviously at its end, and a couple of turns added in the opposite direction. If no sound appears, use a logic probe, meter (or i.e.d. in series with a 1k resistor), to check that the data bits from IC2 to the speech synthesiser board are all zero. If nothing is forthcoming, power should be removed and the whole unit

COMPONENTS...

Resistors

R1, R2, R5	1k (3 off)
R3	180k
R4	4k7

All resistors $\frac{1}{4}$ W 5% carbon

Potentiometers

VR1	100k hor. preset
VR2	5k hor. preset

Capacitors

C1, C2	10n ceramic disc (2 off)
C3	2 μ 2 15V elect.
C4, C5, C6, C7	100 μ 15V elect. (4 off)
C8, C9, C10	100n disc ceramic (3 off)

Semiconductors

D1–D4	1N4001 (4 off)
D5	1N4148
D6	5V1 Zener BZY88
IC1	741
IC2	74LS174
IC3	LM380
IC4	7805

Miscellaneous

P.c.b.
 PL1 ribbon cable plug and connector
 SK1 edge connector socket (10 double way at 0.156in. pitch with polarising plug)
 Mains transformer 10–20V sec 250mA
 8 Ω loudspeaker
 S2A, S2B or S2C speech synthesis board
 i.c. sockets

Constructor's Note

All components including the speech boards are available from **Modus Systems Ltd., 29A Eastcheap, Letchworth, Herts, SG6 3DA (04626 74468/76392).**

The interface board (ex. transformer and loudspeaker) is £14.95 ex. VAT and p&p, and the S2A board is £39.95 ex. VAT and p&p.

checked with the greatest care for any incorrect soldering or component location.

When the unit is working, adjust the two pots on the interface, and the pot on the synthesis board for the best sound. Any tendency toward instability will almost certainly be removed by adding to the power supply decoupling capacitors. Experimentation with the loudspeaker mounting is very worthwhile. Try mounting the speaker in a closed cardboard box with just the speaker cone exposed through a hole of the same diameter. The prototype gave excellent results with a speaker in a transistor radio housing. The speaker should be around two inches or more in diameter for the best results, any smaller and the important base responses will be lost.

COMPUTER SPEECH

It is expected that a number of readers will want to attach the unit to a microcomputer and this section deals with its interface to the Compukit, and the Edukit. The interface requirements for the two machines are sufficiently different to provide an excellent illustration of the process.

In order to operate the speech board effectively, the host computer should have two output lines and one input, as well as the six data lines, usually derived from the data bus, to supply details of the exact word to be spoken. One of the


output lines is used to clock the six bit word into the data latch, the other output is used as a "start" signal to the speech board, and the input line is connected to the "busy" line and monitored by the computer to ensure that a new word is not requested before the current one is finished. This last line is not necessary if a delay loop is used by the computer to ensure that the next word is never output too soon.

The Edukit has several input and output lines for these purposes, and its interface is very straightforward. Fig. 2.7 shows a tried and tested arrangement. The Edukit is based around the RCA 1802 MPU which has a number of special and useful features for hardware control. One of its lines, called the Q line, is a flip-flop output whose condition may be set by a couple of dedicated machine-code instructions—one to set and one to reset. This output is used here as a "start" signal. The Edukit has a transistor connected to the Q line, and a couple of pins on the board give access to its collector (through a 100 ohm resistor). A load resistor (2k2 at least) should be connected across the pins, and the collector end of the resistor (pin nearest to the keyboard) should be connected, as shown, to the "start" line of the interface. Thus, the Q output from the 1802 is inverted, and starting of the speech output is effected by first setting Q (giving zero at the "start" line), resetting and setting Q again. This provides a short pulsed "one" on the "start" line.

The Edukit also has a number of input lines, called "External Flags" (EF lines). The states of these lines may be examined by a comprehensive set of jump instructions in the 1802. The "busy" line, therefore, may be examined by EF1, for instance, and the next word sent when the "busy" line returns to a "one".

To transfer data from the computer, the lower six data lines are used, and a further output line is necessary to latch these data bits into the interface's latches. Again, the 1802 is well designed to allow the presence of "output" data on the "data bus" to be signalled by a particular set of output lines (N0 and N2). On the Edukit, one of these lines is inverted and used to allow data to be shown on the digital display. The signal appears at pin 3 of the display drivers, (IC11 or IC12), and it is from here that the latch enable of the interface should be drawn.

To ensure that the unit is interfaced correctly, write a program to turn the Q line off, then on, then off again.

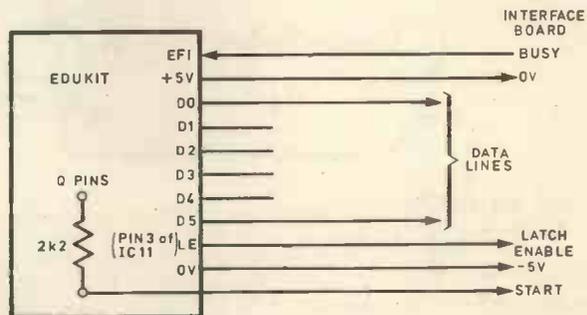

EQ445

Fig. 2.7. Edukit interface board

Whatever word is held on the latch (IC2) will now be heard when the program is run. If this is working, the hex equivalent of the word spoken will appear on the digital display.

Fig. 2.8 gives a flow chart of a typical piece of software to output all the words offered by the speech board. Either 24 or 64 words are offered on the board, and this will decide when the last word has been spoken. The routine starts by setting the Q line to a "one", and setting the contents of the

memory location (called "I" here) to the number 0, which is the first word to be spoken. The OUT instruction is then used exactly as for outputting to the digital display. "I" is then incremented and Q set to 0 for a short time. The word spoken should agree with the digital display reading. A loop is then entered which simply repeats until the "busy" line returns to a 1 level. When this happens, a check is done to determine whether the last word has been spoken; if not the process is repeated, otherwise the end is reached. This routine, of course, forms the basis for operating any system, though the exact manner in which the checks are made, and the data output, depends upon the hardware set-up involved.

Interfacing to the Compukit is a rather more difficult business as there are no I/O lines on the board. There are two approaches which may be considered. Which is chosen depends upon whether a quick experimental set-up is sufficient, or a fully operational unit capable of controlling the speech fully is required.

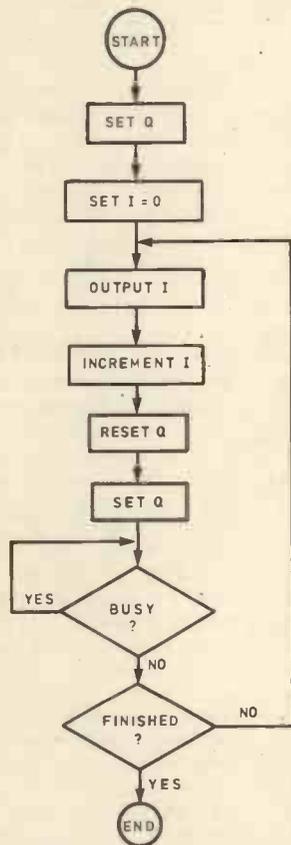


Fig. 2.8. Flow chart to output all the words offered by the speech board

A quick interface to the Compukit, which is by no means a finished set-up, but will give a flavour of the use of speech for a later more sophisticated approach is shown in Fig. 2.9. Here, the top 2K of RAM i.c.s are removed, and their "data" lines, "supply" lines and "chip select" lines are used to drive the speech unit. Notice that the RS lines from the Compukit need inverting before being able to drive the "start" line. The easiest solution is to use any small signal transistor for the job. This interface proved perfectly satisfactory, and should be realised by a couple of d.i.l. headers, rather than by soldering to the p.c.b. When the Compukit is reset and cold started, the Monitor does a memory test, and hence the RS lines are activated. This should cause a word to be output. The theory of operation of this interface is as follows. When a word is to be output, a POKE statement is performed to

any memory location in the top 1K of memory. This causes RS7 to go low when the "data bus" contains the desired word. The word is then latched by the speech interface. The next operation is to POKE any location in the next to last 1K of memory—any value will do. This causes RS6 to fall to a zero for a short time, which, via the transistor inverter,

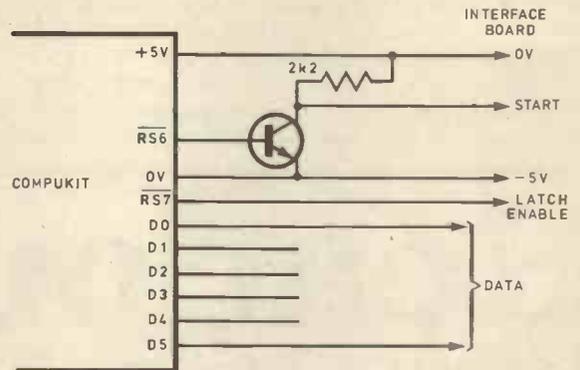


Fig. 2.9. Simple Compukit interface

causes the "start" line to rise for a short time and the speech board outputs the latched word. No provision is made for monitoring the "busy" signal, and if a string of words is to be output, then it is necessary to include a delay loop such as:

```
FOR I = 1 TO 1500 : NEXT I
```

between each word output.

The upper 1K of memory starts at decimal 7168, and the next 1K below at 6144. Thus, for instance, the following program will "say" all the words on the 24-word version of the speech board.

```

10 FOR J = 0 TO 23
20 POKE 7168,J
30 POKE 6144,0
40 FOR I = 1 TO 1500
50 NEXT I
60 NEXT J
  
```

The upper value in line 40 depends upon the frequency of the clock on the speech board, and hence may need to be adjusted to ensure that nothing is lost.

The above interface should not be viewed as a long term method of providing the Compukit with speech. The correct approach is to use a PIA type device such as that detailed in the PE Compukit articles. By this means, the "busy" signal can be used to ensure that nothing is lost, and the top 2K of RAM remains free. An excellent and general interface project for the Compukit is described in a set of articles by D. E. Graham, starting in the next issue of PE. The project is perfectly set up to control the speech board as well as many other things. Another advantage of this interface is that it allows the use of digital to analogue converters. The need for such devices, with reference to speech, is mentioned below.

GENERAL NOTES

Any digital device which displays decimal information, such as a digital clock, digital car instruments, test gear etc. should be able to be interfaced with the speech unit described here. Some demultiplexing may be required, and the on-board latch provides the basis of such circuitry. Though a major application is for computer speech, a computer is by no means necessary to drive the unit.

In using the speech unit, it is worth pointing out that any word spoken to the human ear out of context may be mis-

heard or misunderstood by the listener. It is therefore a good idea to listen through the complete vocabulary, at least once, while following a written copy. This should adequately attune the ear to the sound being produced.

To experiment with voice output fully, the pitch of the utterance must also be controlled in real time. The speech boards allow the clock frequency to be supplied from an external source, and an external D to A converter followed by a voltage controlled oscillator would be a method of allowing computer control of pitch. Volume could also be adjusted at IC3, and, along with pitch, ultimate control of the process would result. The next step would be to produce a piece of

software which automatically determines and controls the pitch and volume depending upon context and syntax of the utterance. Although the speech unit presented here is relatively simple, it is more than adequate for these and many other sophisticated experiments in speech synthesis. Indeed, the unit is actually useful, and provides the user with yet another source of output from electronic equipment. This is especially true when the eyes are busy with other tasks, but constant monitoring of numerical data is required.

Finally, the author would like to thank Mr. M. Terkow of Modus Systems for his assistance in prototyping and checking many of the ideas presented in these articles. ★

Readout...

A selection from our Postbag

Readers requiring a reply to any letter must include a stamped addressed envelope. Opinions expressed in Readout are not necessarily endorsed by the publishers of Practical Electronics.

Velikovsky: Frank Hyde Replies

I offered to answer specific questions from Mr. Austin but so far none have come to hand. However, since Messrs Warlow and Williams have added their criticisms on this matter it gives me an opportunity to assume that, certain main themes are themselves statements of belief if not scientific fact, accepted by these gentlemen.

First let me make it clear that I am dealing with the matter from my own original edition of Velikovsky's "Worlds in Collision". Most of the book consists of statements without any support other than quotations from random works of the past. Much of the support for his own ideas are drawn from the biblical text. It is here that quotation is regarded as confirmation of physical facts and as is all too common with this kind of "proof" is not sufficient to substantiate the claims.

Dominant among the statements which serve to antagonise physicists and astronomers are the claims that a comet was ejected from Jupiter. Let us take this as a starting point and I quote page 48 of "Worlds in Collision" "*In the middle of the second millennium before the present era, as I intend to show, the earth underwent one of the greatest catastrophes of its history. A celestial body that only a short while before had become a member of the solar system—a new comet—came very close to earth*". Then for some 14 pages of quotations of various happenings interspersed with statements such as "*the tails of comets are composed mainly of carbon and hydrogen gases. Lacking oxygen, they do not burn in flight, but the inflammable gases, passing through an atmosphere containing oxygen, will be set on fire*". Well the earth passed through the tail of Halley's comet in 1910 but no one noticed it nor was the tail visible, let alone on fire. It is perhaps wise to point out here that the "tail" of a comet appears as the comet approaches the body which determines

its perihelion passage. If the comet is large the "tail" will be produced in a direction away from the body it approaches and will continue as it passes round the body to point away from it. It may be that more than one "tail" appears. Sometimes the tail is insignificant and sometimes there is no visible "tail". Halley's comet is due in 1986 and between now and then there is to be a mission to observe the comet at first hand. Thus will all doubt as to the composition be settled. Beyond saying that there is an abundance of literature available about comets which when read will give some of the answers, I will leave the actual comet in order to test the statement by Velikovsky that Venus was originally a comet ejected from Jupiter. This he says occurred around the year 1500 BC. The Book of Exodus provides the details of what happened when the comet grazed the earth. Many very strange things are told such as, the houses of the Egyptian people were destroyed, the Nile ran red etc. The curious thing about it all was that the houses of the Israelites were not affected. After forty years the comet came back and caused further trouble, to go off and again return, and, after hitting the earth, again bringing it to a standstill before going on to upset Mars into its present orbit and itself settling down as Venus. The earth regained its place and continued on as it was, before all these events took place. All this supported by historical facts quoted from the Bible and other writings from various parts of the world. These are very far reaching statements and thus need careful examination. Many so-called scientific predictions have gone awry even when evidence appears to be adequate to make a forecast. However there are certain everyday facts of natural science which must be satisfied before new and astounding statements can be accepted. Let us then look at what the statements of Velikovsky imply in relation to comets.

The basis of many of the statements attends on "belief". Because many of the cometary orbits lie near Jupiter a number of people including Laplace and Pierre Simon put forward

the view that Jupiter might be the source of cometary bodies. However there are no writings in support of the fact nor indeed are there any sightings of it ever happening nor has Jupiter ever been observed to have unusual events occurring in its vicinity. One person, V. S. Vsekhsviatyky does believe that comets are ejected from volcanoes on the satellites.

I will not resort to writing out the mathematics in this reply but will give the consequences as are known and used in astronomical physics. Of course if anyone would like to have the full mathematics I will send them, if a stamped addressed envelope is supplied. The effect of projection of a portion of Jupiter of the density and size to end up as a planetary body like Venus, would be to raise the temperature of Jupiter several thousands of degrees centigrade. This would have melted the body being ejected and therefore it would probably be dispersed as dust or vapour. Thus it is unlikely that even a comet (assuming that a comet is not anything like current thinking) could exist or survive such an experience. There is another problem also. The escape velocity at Jupiter is of the order of 20km/second. Whatever the escape mechanism might be it would not be aware of this fact for if the velocity of escape was 70km/second the comet/planet would fall back into Jupiter, if it were 73km/second it would escape from the solar system. In either case it is more likely that Jupiter would be considerably changed and not its stable self as has been observed over a far longer period of time than as recently as 1500 BC.

There is still a further problem. This is the mass of Venus. It amounts to rather more than 5×10^{27} grammes. The total kinetic energy that would be required to propel Venus to the escape velocity of Jupiter is of the order of 10^{41} ergs. This poses an even greater problem than all the others put together for 10^{41} ergs is equivalent to all the radiation energy of the sun for a year. Or in other terms one hundred million times more powerful than the largest solar flare ever observed.

A final word on this situation, which is occupying more space than is justified. Velikovsky has quoted several rapidly occurring collisions involving planets yet the odds against it happening once in a millenium is 30,000 years. Surely unwritten folk stories and legends must defer to practical and demonstrable facts, for this is why David Birch was dismissive.

Frank W. Hyde, FSE, PEng, FRAS.

This correspondence is now closed—Ed.

Buy a microcomputer for under £1,000 and you could be on your own! Unless it's a Commodore PET.



Commodore produce Britain's number one microcomputer. But we don't stop there. We also insist on providing comprehensive support throughout our national dealer network.

Our dealers can examine your needs and demonstrate which hardware and software will suit you best. Their trained engineers are always at hand and a 24-hour field maintenance service is available. Your local dealer can tell you more about the following Commodore Services.

Commodore PET

The Commodore PET computer range covers everything from the self-contained unit at under £500 to complete business systems at under £2,500.

Commodore Business Software and Petpacks

Our software range covers hundreds of applications. Business software includes Sales and Purchase Ledgers, Accounting, Stock Control, Payroll, Word Processing and more. In addition over 50 Petpacks are available covering such titles as Strathclyde Basic Tutorial, Assembler Development System, Statistics, plus our Treasure Trove and Arcade series of games.

Commodore Approved Products

Compatible products of other manufacturers with Commodore's mark of approval are also available.

Commodore Courses

Commodore offer a range of residential training courses and one day seminars. An excellent start. And when you have installed your system the PET User's Club Newsletter can keep you informed of new ideas and latest developments.

LONDON AREA

Adda Computers Ltd.
W5, 01-579 5845
Advanced Management Systems.
EC2, 01-638 9319
Byteshop Computerland,
W1, 01-636 0647
C.S.S. (Business Equipment) Ltd.
E8, 01-254 9292
Capital Computer Systems.
W1, 01-636 3863
Centralx-London Ltd.
SE13, 01-318 4213
Cream Microcomputer Shop.
HARROW, 01-863 0833
Da Vinci Computer Shop.
EDGWARE, 01-952 0526
L & J Computers.
NW9, 01-204 7525
Home and Business Computers.
E12, 01-472 5107
Merchant Systems Limited.
EC4, 01-353 1464
Metyclean Ltd.
SW1, 01-828 2511
Micro Computation.
N14, 01-882 5104
Micro Computer Centre.
SW14, 01-878 3206
Sumlock Bondain Ltd.
EC1, 01-250 0505
Sumlock Bondain Ltd.
EC4, 01-626 0487
T.L.C. World Trading Ltd.
WC2, 01-839 3894
TOPS TV LTD.
SW1, 01-730 1795

HOME COUNTIES

G. M. Marketing.
ANDOVER, 790922
HSV Microcomputers.
BASINGSTOKE, 62444
MMS Ltd.
BEDFORD, 40601
Elex Systems Ltd.
BRACKNELL, 52929
DOM Direct Data Marketing Ltd.
BRENTWOOD, 229379
Amplicon Micro Systems Ltd.
BRIGHTON, 562163
RUF Computers (UK) Ltd.
T. BURGESS HILL, 45211
T & V Johnson (Microcomputers
Etc) Ltd, CAMBERLEY, 20446
Cambridge Computer Store.
CAMBRIDGE, 65334
Wego Computers Ltd.
CATERHAM, 49235
Dataview Ltd.
COLCHESTER, 78811
South East Computers Ltd.
HASTINGS, 426844
Alpha Business Systems.
HERTFORD, 57423
Brent Computer Systems.
KINGS LANGLEY, 65056
Isher-Woods Business Systems.
LUTON, 416202
South East Computers Ltd.
MAIDSTONE, 681263
Micro Facilities Ltd.
MIDDLESEX, 01-979 4546
J. R. Ward Computers Ltd.
MILTON KEYNES 562850
Sumlock Bondain (East Anglia) Ltd.
NORWICH, 26259
T & V Johnson (Microcomputers
Etc) Ltd, OXFORD, 721461
H.S.V. Microcomputers.
SOUTHAMPTON, 22131
Super-Vision.
SOUTHAMPTON, 774023
Xitan Systems Ltd.
SOUTHAMPTON, 38740
Stuart R Dean Ltd.
SOUTHEND-ON-SEA, 62707
The Computer Room.
SUNBRIDGE WELLS, 41645
Orchard Electronics.
WALLINGFORD 35529

Petalect Ltd.
WOKING, 63901
Oxford Computer Systems.
WOODSTOCK, 811976

MIDLANDS AND SOUTH HUMBERSIDE

Byteshop Computerland,
BIRMINGHAM, 622 7149
CPS (Data Systems) Ltd.
BIRMINGHAM, 707 3866
Camden Electronics,
BIRMINGHAM, 773 8240
Computer Services Midlands Ltd.
BIRMINGHAM, 382 4171
Catlans (Computers) Ltd.
BURTON-ON-TRENT, 812380
Itek Systems.
COVENTRY, 86449
Jondane Associates Ltd.
COVENTRY 664400
Davidson-Richards Ltd.
DERBY, 366803
Caddis Computer Systems Ltd.
HINCKLEY, 613544
H.B. Computers.
KETTERING, 83922
Taylor-Wilson Systems Ltd.
KNOWLE, 6192
Machsize Ltd.
LEAMINGTON SPA, 312542
Office Computer Techniques Ltd.
LEICESTER, 28631
Lowe Electronics,
MATLOCK, 2817
Betos (Systems) Ltd.
NOTTINGHAM, 48108
Byteshop Computerland,
NOTTINGHAM, 40576
Keen Computers Ltd.
NOTTINGHAM, 583254
Tekdata Computing.
STOKE-ON-TRENT, 813631
Systems Micros.
TELFORD, 460214
McDowell Knaggs & Associates.
WORCESTER, 427077

YORKSHIRE AND NORTH HUMBERSIDE

Ackroyd Typewriter & Adding
Machine Co. Ltd, BRADFORD, 31835
Allen Computers.
GRIMSBY, 40568
Microware Computers Ltd.
HULL, 562107
Microprocessor Services.
HULL, 23146
Holdens Ltd.
LEEDS, 459459

South Midlands Communications Ltd.
LEEDS, 782326

Yorkshire Electronics Services Ltd.
WORLEY, 522181
Computer Centre (Sheffield) Ltd.
SHEFFIELD, 53519
Electronic Services.
SHEFFIELD, 668767
Hallam Computer Systems Ltd.
SHEFFIELD, 663125

NORTH EAST

Dyson Instruments.
DURHAM, 66937
Currie & Maughan.
GATESHEAD, 774540
Wards (Office Supplies) Group.
GATESHEAD, 605915
Elfton Ltd.
HARTLEPOOL, 61770
Fiddes Marketing Limited.
NEWCASTLE, 815157
Newcastle Computer Services.
NEWCASTLE, 815325
Format Micro Centre.
NEWCASTLE, 21093
Tripont Associated Systems
Consultants Ltd.
SUNDERLAND, 73310

SOUTH WALES AND WEST COUNTRY

Radan Computational Ltd.
BATH, 318483
Computer Corner.
SHREWSBURY, 59788
Bristol Computer Centre.
BRISTOL, 23430
C.S.S. (Bristol) Ltd.
BRISTOL, 779452
T & V Johnson (Microcomputers
Etc) Ltd, BRISTOL, 422061
Sumlock Tabdown Ltd.
BRISTOL, 26685
Sigma Systems.
CARDIFF, 34869
Office and Business Equipment
(Chester) Ltd, DEESIDE, 817277
A.C. Systems.
EXETER, 71718
Micro Media Systems.
NEWPORT, 59276
J.M. Computer Services Ltd.
NEWQUAY, 2863
Devon Computers.
PAIGNTON, 526303
J.A.D. Integrated Services.
PLYMOUTH 62616
Business Electronics.
SOUTHAMPTON, 738248
Computer Supplies (Swansea).
SWANSEA, 290047

NORTH WEST AND NORTH WALES

Tharstern Ltd.
BURNLEY, 38481
B + B (Computers) Ltd.
BOLTON, 26644
Preston Computer Centre.
PRESTON, 57684
Catlans (Computers) Ltd.
WILMSLOW, 527166

LIVERPOOL

Aughton Microsystems Ltd.
LIVERPOOL, 548 7788
B.E.C. Computers.
LIVERPOOL, 263 5738
Rockcliff Brothers Ltd.
LIVERPOOL, 521 5830

MANCHESTER AREA

Byteshop Computerland.
MANCHESTER, 236 4737
Computatone Ltd.
MANCHESTER, 832 4761
Cytek (U.K.) Ltd.
MANCHESTER, 872 4682
Executive Reprographic Ltd.
MANCHESTER, 228 1637
N.S.C. Computer Shops Ltd.
MANCHESTER, 832 2269
Sumlock Electronic Services
(Manchester) Ltd.
MANCHESTER, 834 4233
Professional Computer Services Ltd.
OLDHAM, 624 4065
D. Kipping Ltd.
SALFORD, 834 6367
Automated Business Equipment Ltd.
STOCKPORT, 061-432 0708

SCOTLAND

Holdene Microsystems Ltd.
EDINBURGH, 668 2727
Microcentre.
EDINBURGH, 556 7354
Aethrol Consultancy Services.
GLASGOW, 641 7758
Byteshop Computerland,
GLASGOW, 221 7409
Robox Ltd.
GLASGOW, 221 5401
Mac Micro.
INVERNESS, 712203
Thistle Computers.
KIRK WALL, 3140

IRELAND

Softech Ltd.
DUBLIN, 784739
Medical & Scientific Computer
Services Ltd, LISBURN, 77533

To: Commodore Information Centre,
360 Euston Road, London W1 3BL. 01-388 5702

Please send me further information about the Commodore PET.

Name _____
Position _____
Address _____

Intended application _____ P.E.D.2
Do you own a PET? YES NO

Commodore

This list covers dealers participating in our advertising.

MICRO-BUS

Compiled by DJD.

Appearing every two months, Micro-Bus presents ideas, applications, and programs for the most popular microprocessors; ones that you are unlikely to find in the manufacturers' data. The most original ideas often come from readers working on their own systems; payment will be made for any contribution featured.

THIS month's Micro-Bus presents six BASIC programs for the Sinclair ZX80 microcomputer.

LARGE CHARACTERS

The ZX80 is unusual among microcomputers in that its character-set is stored in ROM alongside the BASIC interpreter, and characters are written to the display by software. Bob Sharp, of Corby, has discovered how to PEEK the ROM and produce displays of large characters. His three programs generate displays of 32, 8 or 2 characters of increasing size. They can give the alphanumeric characters and graphics symbols, together with the symbols "# \$: ?". As well as being extremely revealing about how the ZX80 works, the programs would be useful for creating large displays for teaching or shop-window advertising.

In the ZX80 the character set is stored, starting at address 448*8 in the ROM, as a sequence of 8 bytes per character. Each byte codes the bit pattern for one line of the character matrix. A "1" in that byte is displayed as a black dot, and a zero as a white dot. Thus, for example, the 8 lines for the character with code N can be printed, in decimal, by executing:

```
10 INPUT N
20 FOR R=0 TO 7
30 PRINT PEEK ((448+N)*8+R)
40 NEXT
```

Converting these decimal numbers to binary will then reveal the shape of the character.

HUGE EIGHT

The simplest program of the three to understand is Huge Eight, see Fig. 1, which generates 2 lines of 4 characters; for example, see Fig. 2. The Huge Eight program prints a space character, or an inverted space character, for each bit of the characters, thus giving characters 8 times larger than normal. For each line of 4 characters the character codes (plus 448) are stored in the array I(0) to I(3). Then, for each row in these characters (line 120) the ROM is PEEKed (line 140) and the bits are printed (line 160) starting with the high-order bit. A zero is printed as a space, code 0, and a one as an inverted space, code 128. The expression $(X/2^{**}(7-H))$ divides X, the row in the character matrix, by successive powers of 2. The low-order bit of the result determines whether, when the result is multiplied by 128, the code produced is 0 or 128.

```
10 REM HUGE 8
30 INPUT A$
60 FOR E=0 TO 1
70 DIM I(3)
80 FOR N=0 TO 3
90 LET I(N)=448+CODE(A$)
100 LET A$=TL$(A$)
110 NEXT N
120 FOR G=0 TO 7
130 FOR U=0 TO 3
140 LET X=PEEK(8*I(U)+G)
150 FOR H=0 TO 7
160 PRINT CHR$(128*(X/2**(7-H))
);
170 NEXT H
180 NEXT U
190 NEXT G
200 NEXT E
```

Fig. 1. Huge Eight program gives a display of eight large characters on a ZX80



Fig. 2. Display generated by the Huge Eight program

GIANT TWO

The Giant Two program, Fig. 3, converts each bit in the character matrix into a square of four spaces, or four inverted spaces, thus giving an enlargement of 16 times and filling the screen with two characters. The program works in a similar way to Huge Eight, except that now I(0) to I(7) hold the bytes of the character matrix for the first character, and I(8) to I(15) hold the matrix for the second character.

BIG THIRTY-TWO

The third of Bob Sharp's programs, shown in Fig. 4, gives four lines of eight characters, and is at first sight the most baffling to understand. It displays each block of four bits in the characters as the relevant graphics symbol, thus giving an enlargement of four times.

```
10 INPUT A$
20 DIM I(15)
30 FOR N=0 TO 15
40 IF N=8 THEN LET A$=TL$(A$)
50 LET I(2*N-15*(N/8))=PEEK(N+
8*(448+CODE(A$)-N/8))
60 NEXT N
70 FOR T=0 TO 7
80 FOR N=0 TO 1
90 PRINT
100 FOR A=0 TO 1
110 FOR I=0 TO 7
120 FOR G=0 TO 1
130 PRINT CHR$(128*(I(2*T+A)/2*
*(7-I)));
140 NEXT G
150 NEXT I
160 NEXT A
170 NEXT N
180 NEXT T
```

Fig. 3. Giant Two program gives a display consisting of two large characters

```
10 INPUT B$
20 FOR A=0 TO 3
30 FOR B=0 TO 3
35 LET A$=B$
40 FOR C=0 TO 7
50 FOR D=0 TO 3
55 LET Y=0
60 FOR E=0 TO 1
65 LET W=CODE(A$)
70 LET X=PEEK(8*((448+W)+2*B+E))
90 LET Y=4*Y+X/4**(3-D)-4*(X/4
**(4-D))
100 NEXT E
105 IF Y<8 THEN GO TO 120
110 LET Y=15-Y
115 LET E=0
120 LET Z$="07635B8D"
130 FOR N=0 TO Y
140 LET Z=CODE(Z$)
150 LET Z$=TL$(Z$)
160 NEXT N
170 IF Z>36 THEN LET Z=Z+119
175 IF E=0 THEN LET Z=Z+128
180 PRINT CHR$(Z-28);
190 NEXT D
200 LET A$=TL$(A$);
210 NEXT C
230 NEXT B
240 LET B$=A$
250 NEXT A
```

Fig. 4. Big Thirty-Two program displays four lines of enlarged characters on a ZX80

The program looks up two rows of each character, in lines 60 to 100, and calculates in Y a 4-bit binary number which specifies the

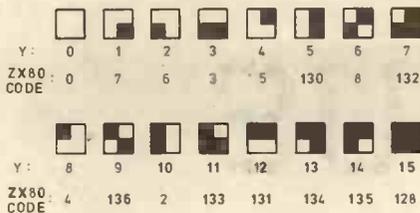


Fig. 5. The graphics symbols used by the Big Thirty-Two program, together with their ZX80 codes

states of the four squares in the graphics symbol. Thus $Y=0$ is a space, and $Y=15$ is an inverted space. However, finding the correct graphics symbol for the other values of Y is by no means an easy task, since the codes for the graphics symbols are apparently quite haphazard on the ZX80; the symbols and their ZX80 codes are shown in Fig. 5. Bob Sharp gets around this problem by providing a string, $Z\$,$ in line 120, whose characters specify the order of the first 8 graphics symbols. Lines 130 to 160 select the required character in this string, and then lines 170 to 180 convert this to the graphics symbol, and print it. The symbols for Y between 8 and 15 are obtained by inverting one of the first 8 graphics symbols in line 175.

This process is repeated to give the 32 graphics symbols for each line, and for the 16 lines of symbols, and the whole program takes almost two minutes to execute.

These three programs for generating large characters can be modified to give other punctuation and arithmetic signs, in addition to the alphanumeric characters, by replacing the reference to $CODE(A\$,)$ with: $121-ABS(121-CODE(A\$,))$.

MEMORY-MAPPED DISPLAY

Another unusual feature of the ZX80 is that there is not a precise mapping between the characters in memory and what is displayed on the screen; instead the display is generated from a "display file" which can reside anywhere in memory, and which can contain lines of different lengths so that trailing blanks do not have to be stored.

However, it is sometimes useful to be able to use the display as if it were memory-mapped, so that **POKE**ing to a specific memory location will cause the code for that character to appear at a predetermined position, and **PEEK**ing will read the code of the character at that position. The program of Fig. 6, submitted by *S. J. Duggins* of Birmingham, shows how to achieve this, and demonstrates its use by drawing lines, using inverted spaces, between two pairs of coordinates. The top left-hand corner of the screen has coordinates (1,1), and the bottom right-hand corner has coordinates (32,18). As an example, Fig. 7 shows four lines drawn by the program.

Mr. Duggins describes the operation of the program as follows: "The display file is first created in lines 20-40 by printing spaces. The coordinates are then entered as $X1,Y1,$ and $X2,Y2$. If 99 is entered as the first coordinate

the program will stop. The peculiar **LET** statements in lines 100 and 110 are used to save having to put four **IF** statements; their use is explained in the manual. The start address of the display file is then obtained in line 120 from the system variable $D-FILE$; since the file does not reside in a fixed area of memory the address is obtained before each **POKE** statement is executed, because even if a variable is assigned the display file will be moved. The reverse space is then **POKE**d in line 130 to the display position of the coordinates $X1,Y1$. Then $Y1$ coordinate (line number) is multiplied by 33 instead of the line width, 32, because a 32-character line does in fact contain 33 characters, the last one being inserted by the monitor as a newline marker. Line 140 checks to see if the second coordinates have been reached, and lines 150 and 160 increment or decrement the plotting coordinates to the next position.

```

10 LET N=16396
20 FOR A=1 TO 18*32
30 PRINT " ";
40 NEXT A
50 INPUT X1
60 IF X1=99 THEN STOP
70 INPUT Y1
80 INPUT X2
90 INPUT Y2
100 LET X=X1<X2 AND 1 OR X1>X2
AND -1
110 LET Y=Y1<Y2 AND 1 OR Y1>Y2
AND -1
120 LET D=PEEK(N)+PEEK(N+1)*256
130 POKE D+(Y1-1)*33+X1,128
140 IF X1=X2 AND Y1=Y2 THEN GO
TO 50
150 LET X1=X1+X
160 LET Y1=Y1+Y
170 GO TO 110

```

Fig. 6. Program draws lines by **POKE**ing to the ZX80 display file

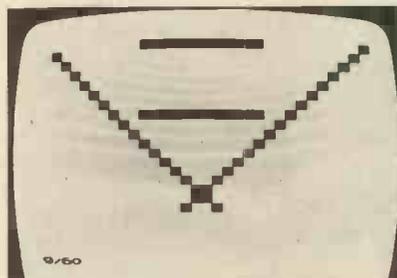


Fig. 7. Graphics drawn by the program of Fig. 6

Note that the program does not check that the coordinates are legal, and drawing to coordinates outside the display area may ruin the program."

STRING ARRAYS ON THE ZX80

Although the ZX80 provides strings and integer arrays, it does not provide string arrays, and this can be very tiresome when strings are being manipulated by a program. *Jeremy Ruston* of Kensington has devised an ingenious way around this restriction. A short routine, Fig. 8(a), sits below the main program and uses the string variables $A\$, B\$, C\$, \dots$ etc. as one string array of up to 25 elements. The number of the required element is passed in $Z,$ and the string is transferred in $Z\$.$ The

```

1 GO TO 12
2 LET Z$=C$
3 RETURN
4 LET C$=Z$
5 RETURN
6 POKE 16446,38+Z
7 GO SUB 4
8 RETURN
9 POKE 16436,38+Z
10 GO SUB 2
11 RETURN
12 GO TO 20
20 FOR Z=1 TO 10
30 INPUT Z$
40 GO SUB 6
50 NEXT Z
60 FOR Z=1 TO 10
70 GOSUB 9
80 PRINT Z$,
90 NEXT Z

```

Fig. 8. (a) Routine to implement a string array on the ZX80, and (b) a program to illustrate its operation

routine then **POKE**s the reference to $C\$,$ in line 2 or line 4 to alter it to the required string variable. On the ZX80 the first line of the program begins at address 16424, and the **POKE** addresses in lines 6 and 9 of the routine give the addresses of the "C"s in lines 4 and 2 respectively. Obviously the routine should not be altered without changing these **POKE** addresses.

The routine is used as follows. Instead of: $LET A\$(X)="HUGO DRAX"$ (which is illegal on the ZX80) you write:

```

LET Z=X
LET Z$="HUGO DRAX"
GO SUB 6

```

Similarly, to print an element, instead of:

```
PRINT A$(8)
```

you would write:

```

LET Z=8
GO SUB 9
PRINT Z$

```

The program in Fig. 8(b) gives a simple demonstration of how the routine can be used; it reads in ten strings, and then prints them all out.

MAZE

The final program of Fig. 9 is very simple, but quite fun; it was devised by *D. Stocqueler* of Cardiff, and it draws a random maze on the screen using the ZX80's graphics symbols. His instructions are:

"The object of the game is to try and find a path between the letters A, B, C, D, W, X, Y or Z. Note that the letters may be joined by black or white paths, or they may not be joined at all."

Note that the computer does not ensure that a path exists; this is a much harder task, possibly beyond the capability of an unexpanded ZX80.

```

10 REM MAZE
70 CLS
75 PRINT "A","B","C","D";
80 FOR A=1 TO 750
90 PRINT CHR$(RND(3));
100 NEXT A
105 PRINT
110 PRINT "W","X","Y","Z";

```

Fig. 9. Program to draw a random maze

SECURITY



SENTINEL...

Part 2 W.C. Dickinson

THE complete control centre is mounted on two p.c.b.s which are interconnected with ribbon cable. Connections to the sensor and alarm circuits are made via p.c.b. mounted terminal blocks.

CONSTRUCTION

The designs and component layouts for the two p.c.b.s is shown in Fig. 2.1. The Veropins should be soldered first then the rest of the components starting with the smallest. The terminal blocks, potentiometers, transformer and battery holder are all mounted on the track side of the p.c.b.s and should be soldered last. The l.e.d.s should be bent as shown in Fig. 2.2. before they are soldered in position.

When the ribbon cable has been soldered the battery holder can be secured to the p.c.b. via 4BA screws and 6mm spacers. The wires from the battery holder should be passed through the p.c.b. and soldered to the appropriate Veropins.

If nickel-cadmium batteries are used then the three links N1, N2 and N3 should be soldered. If alkaline batteries are to be used then the only link required is A1.

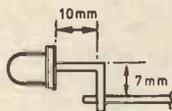



Fig. 2.2. Mounting details for the l.e.d.s. Note the orientation of l.e.d. 90 and 91 is different to the rest

EG461

Each channel of the Sentinel can provide either a delayed or immediate alarm signal when an intrusion is detected. The channels which will be used to monitor the normal entrances and exits should have a delayed alarm. Any channel will give an immediate alarm if D11, D21, D31, D41, D51 or D61 are soldered. So this diode should be omitted from any channel where a delayed alarm is required.

SETTING UP

Before carrying out the following adjustments ensure that the batteries are fully charged. Connect a 100kΩ resistor and a 1N4148 diode across each pair of alarm channel inputs with the cathode connected to the 'a' terminal as shown in Fig. 2.3.

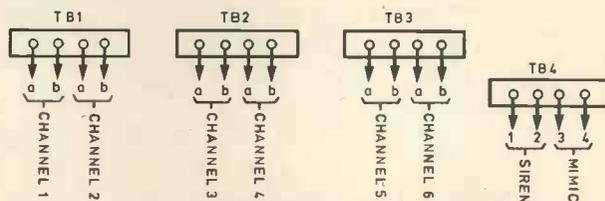


EG460

Fig. 2.3. Terminal block connections

Rotate VR10 to VR60 fully anti-clockwise (from the front of the p.c.b.). Insert the batteries depress all alarm channel select switches and release the activate switch. The 'operational' l.e.d. should illuminate in approximately three quarters of a second. None of the channel 'alarm' l.e.d.s should illuminate. Depress the 'system' switch to the 'defeat' position and using an insulated screwdriver adjust VR10 slightly clockwise. Release the 'system' switch to the 'activate' position. When the 'operational' l.e.d. illuminates depress the 'system' switch to the 'defeat' position. Repeat the above procedure until the channel 'alarm' l.e.d. illuminates when the 'system' switch is released to the 'activate' position. Back VR10 off slightly and release the 'system' switch to the 'activate' position. Repeat this procedure until the channel 'alarm' l.e.d. does not illuminate when the 'system' switch is released. Repeat this procedure for the remaining five alarm channels. If any channel displays an erroneous alarm adjust the preset of the offending channel slightly anti-clockwise until normal operation resumes.

REMOTE MIMIC

The remote mimic (Fig. 2.4.) should be installed near the door which is normally used to leave the house. If the pre-siren option is used then the system alarm l.e.d. cannot be used.


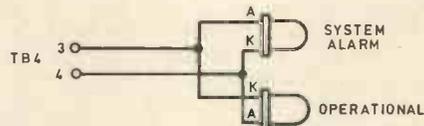


EG453

Fig. 2.4. Remote Mimic wiring

PRE-SIREN SIGNAL UNIT

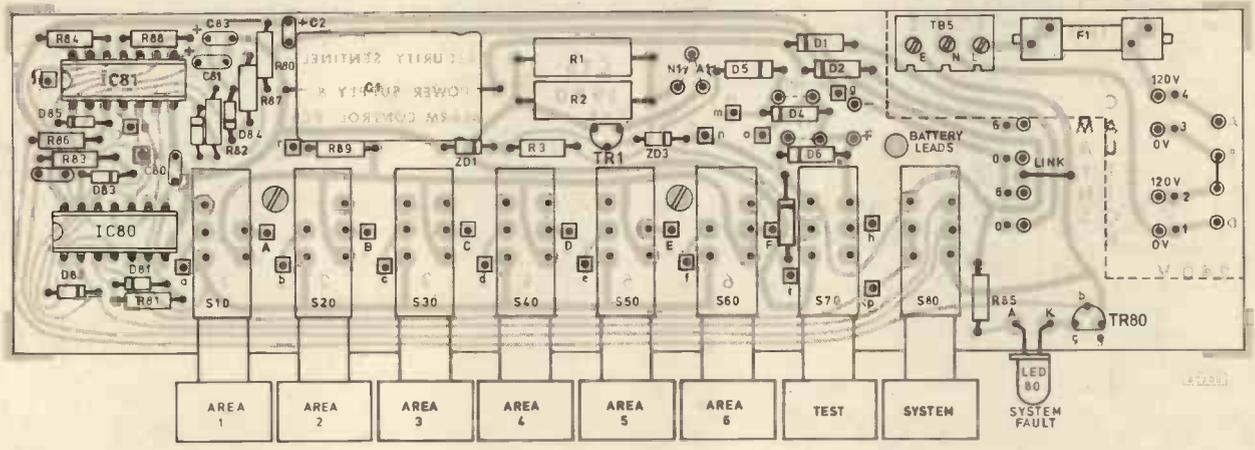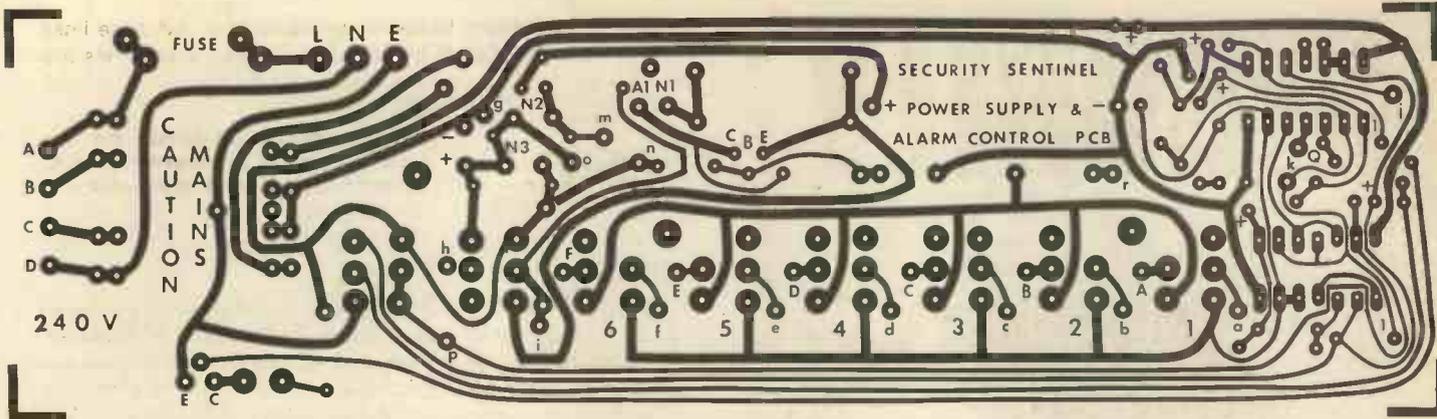A small piezoelectric sounder can be driven (Fig. 2.5.) instead of the remote system alarm l.e.d. The sounder can be



EO427 □ DENOTES INTERBOARD LINKS A TO A, B TO B, ETC.

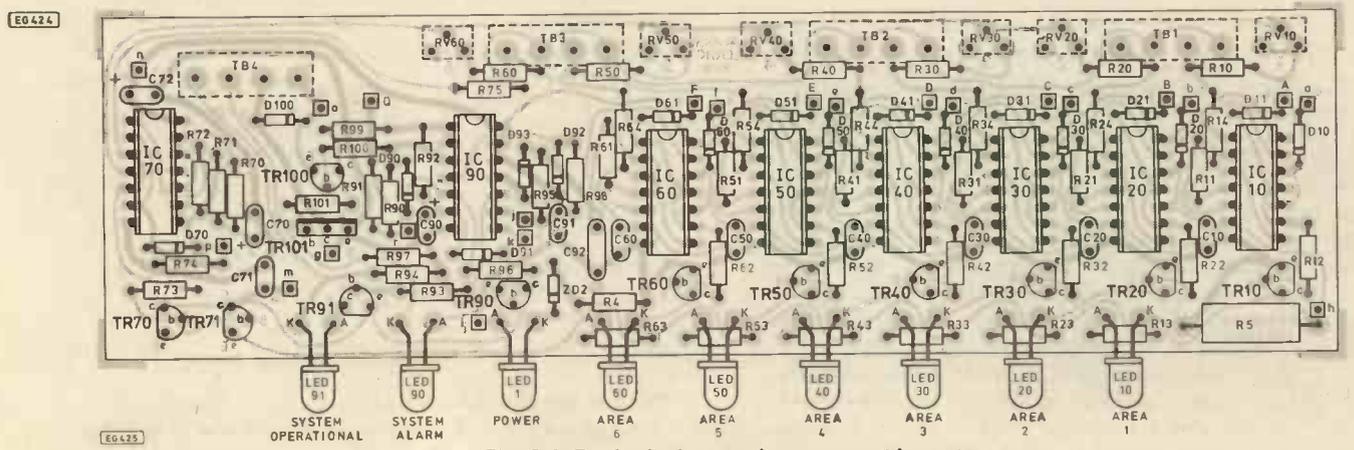
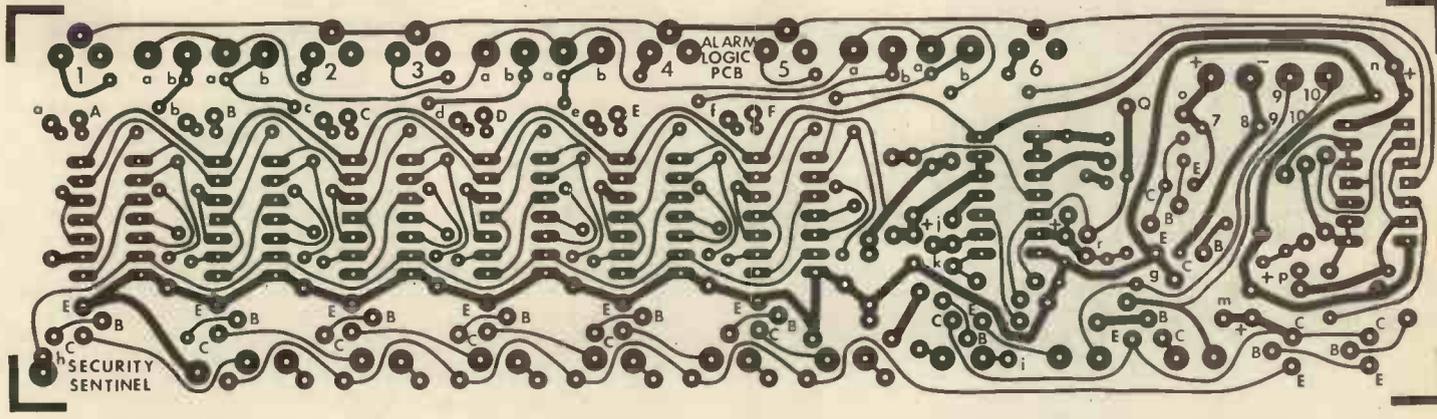


Fig. 2.1. P.c.b. designs and component layouts

used to provide an alarm in advance of the siren being triggered. If this option is used then the value of resistor R89 should be increased to 3M6 to increase the 'immediate alarm' delay time to 30 secs. This enables the system to be defeated before the siren is triggered.

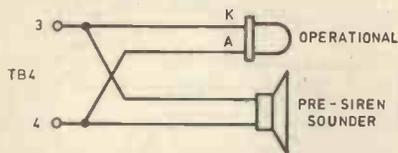


Fig. 2.5. Pre-signal unit wiring

SIREN

Selecting a location for the siren is just as important as selecting the location of the control centre. An ideal arrangement is to have one siren mounted inside the house in a secluded place and a second unit mounted in a high, inaccessible location outside the house. Most systems will only use one unit and this should be mounted near the eaves with the wiring routed through the loft.

ALARM LOOP INSTALLATION

The wiring of the alarm unit will be determined by the layout of the house and the degree of protection required.

SENSORS

Each alarm channel must include one 'tri-mode' sensor and can have up to a maximum of four. An unlimited number of 'bi-mode' sensors, conventional switches, window foils, trip wires and pressure pads may be incorporated in the loop together with fire sensors and 'panic switches'.

TRI-MODE SENSORS


These sensors provide protection against an opened door or window, a magnetically shunted or an electrically shorted sensor. All large windows and external doors should have 'tri-mode' sensors.

BI-MODE SENSORS

These sensors provide protection against an opened door or window and a magnetically shunted sensor. These sensors should be used on external doors and windows when the number of doors and windows in a loop exceed the number that can be protected by 'tri-mode' sensors. The 'tri-mode' sensors should be fitted to the most vulnerable windows and doors with 'bi-modes' fitted to the remainder.

CONVENTIONAL SENSORS

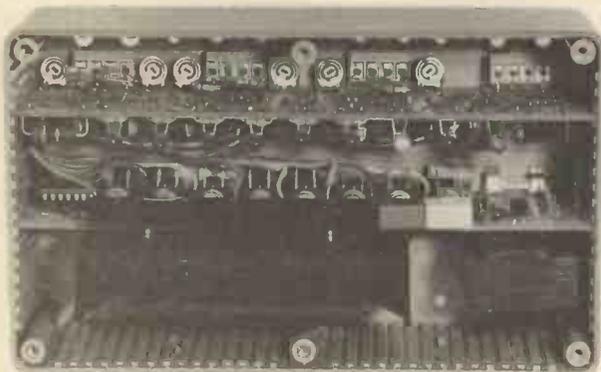Conventional sensors consist of magnet and reed switch combinations used alone. They can be fitted to windows on



Internal view of the Sentinel

first floors to reduce installation costs. They can also be used to provide back-up protection by fitting them to between adjoining rooms. This would however prevent the system being used when the house is occupied.

SHUNT DEVICES

Shunt devices normally take the form of pressure mats fitted under carpets. Magnet and reed switch combinations can also be used in this configuration if they are used to sense a door being closed. Pressure mats are normally fitted near windows, doors and passages between rooms. The use of shunt devices also prevents the system being used when the house is occupied.

WINDOW FOILS

Window foils are inexpensive and easy to install but are very conspicuous and easily shunted. If a 'tri-mode' switch is added to the middle of a foil loop it can be made virtually tamper-proof.

'TRI-MODE SWITCH ASSEMBLY

Before any 'tri-mode' switches are fitted into the system it should be decided how many are to be used in each channel (remember at least one per channel is required to establish the loop impedance). The number of switches will determine the value of resistor R_a (Table 1).

Number of 'tri-mode' switches (per channel)	Value of R_a
1	100k Ω
2	47k Ω
3	33k Ω
4	24k Ω

TABLE 1: All the 'tri-mode' switches in a particular channel should have the same value resistors.

The selected resistor R_a should first be soldered to a germanium diode (OA91) and then fitted into the reed switch assembly as shown in Fig. 2.6.

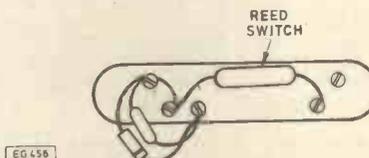


Fig. 2.6. After soldering, the resistor and diode should be fitted inside the switch. Note the reed switch is fitted inside the body of the switch and cannot be seen.

DESIGNING A LOOP

The basic principle of the alarm loop is that it presents a resistance of 100k Ω during one phase of the multi-vibrator. If the resistance of the loop decreases to 80k Ω or less an alarm is sensed. During the other phase of the multi-vibrator the loop should present a resistance less than 10k Ω . If the resistance of the loop increases to 100k Ω or greater an alarm is sensed. The first phase monitors the loop for short circuits and shunt sensors being activated the second phase monitors the loop of continuity of the series sensors.

When designing a loop there are three basic rules that must be followed:

- a) In order to maintain maximum noise immunity twin conductor wire should be used from sensor to sensor. This is important if the sensors are some distance

apart or the alarm wiring is in close proximity to the electrical wiring in the house. Wiring in one area, say around a large set of windows, can be separated into single cores whenever it is convenient to do so.

b) The reverse resistance of the loop should be approximately $100k\Omega$ when the loop is safe. This resistance is determined by the sum of the resistors in the 'tri-mode' sensors. (cathode of diode D positive with respect to its anode).

c) The forward resistance of the loop should be less than $10k\Omega$ when the loop is safe. This resistance is determined by the series resistance of the wire and the diodes in the 'tri-mode' sensors. (cathode of diode D negative with respect to its anode).

A basic system would take the form of a 'tri-mode' switch at the external door and at any windows which can be forced open to provide access for the average size person. 'Bi-mode' switches should be fitted to the remaining windows. Doors and windows which are in dark or secluded areas require extra attention as these areas will be the most likely points of attempted access. 'Tamper proof' window foils should be installed on all glass panes in these localities.

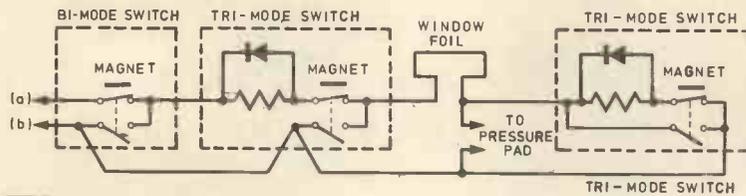


Fig. 2.7. Basic loop system. If a shunt device is used at the end of a loop then an extra wire is required. To overcome this problem each loop should end with a tri-mode switch

One of the major advantages of the 'tri-mode' concept which requires only one twin-conductor wire from the control panel to the area being protected is that only one 'tri-mode' switch need be fitted initially. When time and budget allow, the loop can be expanded without disturbing the existing installation. Wiring is also greatly simplified by this design.

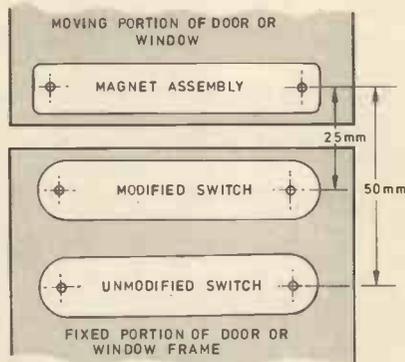


Fig. 2.8. Switch mounting details

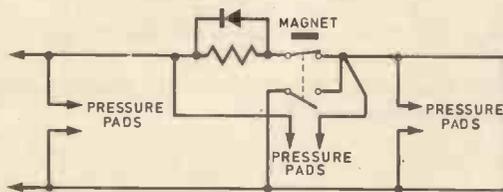


Fig. 2.9. Shunt sensors can be connected across the loop or across a 'tri-mode' sensor

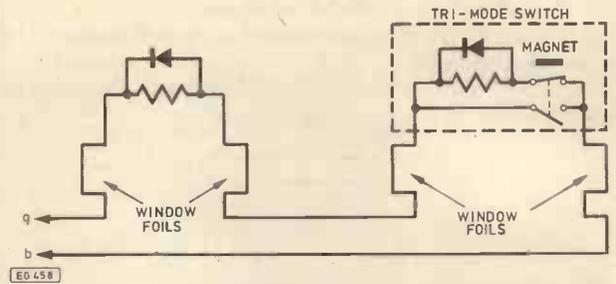


Fig. 2.10. Tamper-proof system for window foils.

TAMPER-PROOF FOILS

Because window foils are conspicuous and are easily shunted the basic type should only be used on fixed opaque glass such as those found in bathrooms. A tamper-proof arrangement for foils can be developed by using a resistor-diode combination from a tri-mode switch in the foil loop of a fixed window. If the window can be opened then it is better to incorporate a tri-mode switch into the loop, this ensures that the alarm will be triggered if either set of foil terminals is shunted.

An unlimited number of bi-mode switches can be developed from conventional switches and although bi-mode and tri-mode switches can be used in either leg it is easier to wire all the series devices in 'a' leg and use the 'b' leg as the return.


OPERATION OF THE SYSTEM

Operation of this system is straightforward due to the built-in automatic test facilities. When you are ready to leave the premises close all windows and doors that are monitored and release all of the channel selector switches to the 'activate' position. As you leave release the 'system' switch to the 'activate' position. When the 'operational' i.e.d. illuminates the system is completely clear of alarms and has initiated the exit delay. You now have one and a half minutes to make your exit and close the door behind you. If the system goes to 'fault' when it is activated the channel which is causing the alarm will be identified by the flashing channel 'alarm' i.e.d. If you wish you can depress the channel selector switch to 'defeat', cycle the 'system' switch to 'defeat' and then back to 'activate'. The system will now ignore the alarm sensed on this channel and you can make your exit. The facility to 'defeat' selected channels was provided for use mainly when you use the system to protect the house when it is occupied and you only wish to protect key areas of the premises. When the house is unoccupied the source of the alarm should be identified and corrected before you depart. When you return and re-enter the house you will trigger the system immediately. The entry delay timer allows you one minute to reach the control centre and depress the 'system' switch to 'defeat' before the siren is triggered. The 'operational' status when you depart and the 'system alarm' status when you re-enter are verified by the remote i.e.d. mimic as confirmation that the system is operating correctly. ★

AITKEN BROS

35, High Bridge, Newcastle upon Tyne

Tel: 0632 26729

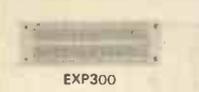

EXP300



PB6 Kit

EXP300

550 contacts with two 50-point BUS bars. Size 152x53mm. £6-95.

PROTO-BOARD 6 KIT

630 contacts, four 5 way binding posts, accepts up to 6 14 pin DIPs. £10-98.

CSC LOGIC PROBES

LP-2 ECONOMY PROBE

Min. pulse width 300 nanoseconds, 300 KΩ input impedance, tests circuits up to 1-5MHz. Detecting pulse trains or single-shot event in TTL, DTL, HTL, and CMOS circuits. £20-95.

LP-1 Memory Probe

£35-65

LP-3 High Speed Memory Probe

£56-75

CSC catalogue available. Please send S.A.E.

CALSCOPE SUPER 6 £186-30

A portable single beam 6MHz bandwidth oscilloscope with easy to use controls. High gain to 10 mv/cm and wide time base range from 1µs to 100 ms/cm. Full specification to request. Please send S.A.E. Professional scopes you can afford.

CALSCOPE SUPER 10 £251-85

A dual trace 10MHz instrument of the very highest performance and quality. It has an accuracy of 3% which is achieved by the use of built-in stabilised power supplies which keep the trace rock steady over a wide range of mains fluctuations. Full specification on request. Please send S.A.E.

SINCLAIR LOW POWER PORTABLE OSCILLOSCOPE SC110 £159-85

The SC110 has a 10MHz bandwidth and sensitivity down to 10mV per division. Full trigger facilities are provided, including bright line, auto with TV line and frame positions. Please send for full spec. and illustrated brochure.

TMK 500 MULTIMETER 30,000 o.p.v. AC volts 2.5, 10, 25, 100, 250, 500, 1000. DC volts 0.25, 1, 2.5, 10, 25, 100, 250, 1000. DC current 50µA, 5MA, 50MA, 12 amp. Resistance 0-6K, 60K, 6MEG, 60MEG. Decibels. -20 to + 56 db. Buzzer continuity test size, 160 x 110 x 55MM. Batteries, leads, and carrying case included. **PRICE £22-95.**

CSC EXPERIMENTOR BREADBOARDS

No soldering modular breadboards, simply plug components in and out of letter/number identified nickel-silver contact holes. Start small and simply snap lock boards together to build breadboards of any size.



SINCLAIR DM350

£83-95

SINCLAIR DM450

£114-95

Size 255x148x40mm.

DM350 3½ digit display DM450 4½ digit display. Both provide six functions in 34 ranges. D.C. voltage 10µV to 1200V (100µA on DM350) A.C. voltage 100µV to 750V. D.C. current 1nA to 10A. A.C. current 1nA to 10A resistance 10MΩ to 20MΩ (100mΩ on DM350). Accessories for DM350 & 450 as for DM235 below. Full spec. on request. Please send S.A.E.

Sinclair PFM200 frequency meter

Size 157x76x32mm.

Range 20Hz to 200MHz. Accessories and illustration as for PDM35 below. £57-95.

SINCLAIR PDM35

DIGITAL POCKET MULTIMETER

DC volts (4 ranges) 1mV to 1000V AC volts 1V to 500V DC current (6 ranges) 1nA to 200MA. Resistance (5 ranges) 1Ω to 20 MEG Ω. **PRICE £39.95 AC Adaptor £4-25 de luxe padded carrying case £1-95 MN 1604 Battery £1-28.** Size 157x76x32mm.

SINCLAIR DM235

BENCH-PORTABLE DIGITAL MULTIMETER.

DC volts (4 ranges) 1mV to 1000V AC volts (4 ranges) 1mV to 750V AC & DC current 1µA to 1000MA Resistance (5 ranges) 1Ω to 20 MEG Ω. **PRICE £60-98.** Carrying case **£8.95.** AC adaptor/charger. **£4-25.** Rechargeable Battery Pack. **£8-95.** Size 255x148x40mm.

PANEL METERS

DIMS 60MM x 45MM. 50µ amp, 100µ amp 1MA, 5MA, 10MA, 50MA, 100MA, 500MA, 1 amp, 2 amp, 25V dc, 30V dc, 50v AC, 300V ac. "S", "VU" 50-0-50µA, 100-0-100µA, 500-0-500µA. **PRICE £5-95.**

DESOLDERING TOOL

£6-45

SUCTION PUMP.

Education Establishment Orders Accepted.

PHONE OR SEND YOUR ACCESS OR

BARCLAYCARD NUMBER

ALL PRICES INCLUDE POSTAGE AND VAT.



DIGITAL VOLTMETER MODULE



Fully built and tested, ONLY

£11.95 + VAT

- ★ Reads positive and negative voltages with a sensitivity of 0 - +999mV and 0 - -99mV
- ★ Requires only single supply between 7 & 12 volts (220mA)
- ★ High accuracy +0.1% +1 digit
- ★ Large bright 0.43" high efficiency displays
- ★ 4 readings per second sampling rate
- ★ Size only 41 x 95 x 10mm
- ★ Supplied with full data & applications information

This brand new, quality module manufactured by Autona Limited (who are one of the U.K.'s largest module manufacturers) means you can build accurate test equipment, multi-meters, thermometers, etc. easily and at a fraction of the cost of ready-made equipment. Full details are provided showing how to measure A.C. voltage, current, resistance and temperature.

Send your cheque or P.O. (£11.95 + £1.79 V.A.T. + 50pp. & p. = £14.24) now to:-

Dept. P.E.3
RISCOMP LIMITED
21 Duke Street
Princes Risborough
Bucks. HP17 0AT

BUCKINGHAMSHIRE'S NEW
ELECTRONICS-CENTRE
8 miles off the M40
50 minutes from London
Telephone: (084 44) 6326

EX-STOCK DELIVERY

Rapid Electronics

■ Guaranteed same day Despatch

■ Quality Product

■ Free Catalogue

■ Vast Stocks


■ Competitive Prices

Pack		50p	Pack		90p
A10	10 PP3 battery leads	50p	F11	10 BC108 trans.	90p
A72	10 3.5mm jack plugs	80p	F26	10 2N3704 trans.	80p
A73	10 3.5mm jack sockets	80p	F27	10 2N3819 trans.	190p
A74	10 Std. jack plugs	130p	H11	20 1N4002 diodes	75p
A75	10 Std. jack sockets	170p	H50	20 0A91 diodes	110p
A84	10 5 pin 180 DIN plug	120p	H60	100 1N4148 diodes	180p
A85	10 5 pin 180 sockets	100p	H70	5 C106D thyristors	200p
C20	10 Min. slide switch	130p	J10	20 0.2in. red LEDs	170p
C30	10 Push to make sw.	130p	J15	50 0.2in. red LEDs	400p
C31	10 Push to break sw.	170p	J20	100 0.2in. red LEDs	750p
C40	Pair Ultrasonics	350p	J30	20 0.2in. green LEDs	280p
C32	Submin. SPST toggle	60p	J50	20 0.2in. yellow LEDs	280p
C33	Submin. DPDT toggle	80p	J80	4 FND500 CC displays	350p
C50	20 Texas 8 pin sockets	170p	K5	5 741 op amps.	90p
C51	20 Texas 14 pin sockets	200p	K40	1 LM324 op amp.	50p
C52	20 Texas 16 pin sockets	220p	K20	5 CA3140 op amps.	225p
E10	Resistor kit. 10 ea value 1/W	480p	K85	5 NE555 timers	110p
	4.7Ω, 1M, 650 resistors	480p	L8	5 4011 CMOS	130p
E34	10 10u 25V radial elec	50p	L9	4013 CMOS	40p
E37	10 100u 25V radial	75p	L11	4017 CMOS	75p
E44	10 1u 35V tantalum	100p	L19	4049 CMOS	45p
E54	10 0.1 C280 polyester	50p	M20	Dalo pen	80p

■ For quality components at competitive prices by return of post Rapid Electronics must be your first choice!

All prices include VAT. Please add 50p postage and packing on orders below £10. Send SAE for our complete catalogue.

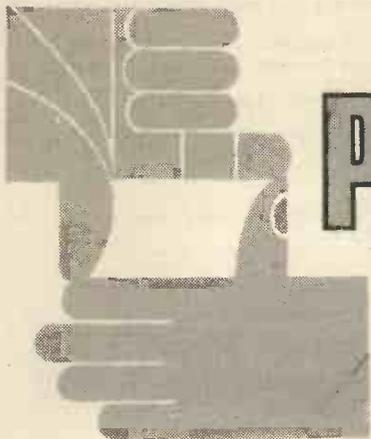Rapid Electronics Limited
Hillcroft House, Station Road, Eynsford, Kent



PATENTS REVIEW...

Copies of Patents can be obtained from:
the Patent Office Sales, St. Mary Cray, Orpington, Kent. Price 95p each.

BOSE SPEAKERS

European patent application no. 0 007 453 originates from the Bose Corporation of Framingham, Massachusetts. The aim of the invention is to provide the electronic equivalent of mechanical adjustments which are necessary on some of Bose loudspeakers. According to Bose design philosophy a loudspeaker should radiate more sound energy onto a reflecting surface, such as a room wall, than directly into the listening area. This is said to simulate the sound received in a concert hall where the listener receives significantly more reflected energy than direct energy from the sound source on the stage.

This (highly controversial) approach can result in an unnaturally broad sound image which spreads across the entire surface of the wall which is reflecting the indirect sound from the loudspeakers. Some control of the image spread is possible if the user physically adjusts the angle of the loudspeakers with respect to the nearest wall. But as Bose admit in the new patent application, this is "impractical in many situations". The new idea is to provide additional circuitry which enables the user to vary the image without altering the loudspeaker position.

The Bose 901 loudspeaker is shaped rather like a chunky slice of cake and (see Figure 4) four identical full range loudspeaker drivers 21-24 and 25-28 are

mounted on each of the two rearwardly facing and mutually angled panels 120 and 121. A single front facing driver 29 is mounted on the front panel 30 to fire directly into the listening area. The nine drivers are connected in series between loudspeaker terminals 31 and 32 with the junction of front driver 29 and inside rear driver 25 connected to an extra terminal 33. As shown in figure 5, the audio signal input 44 is split between an "inside" channel of amplifier 47, resistor R1 and amplifier 51 and an "outside" channel of amplifier 52, resistor R2 and amplifier 54. The gains of amplifiers 47 and 52 are of equal magnitude but opposite sense to provide phase reversal. Capacitor 55 couples the arm 42 of a potentiometer or "spatial control" 41 to earth. Central terminal 33 of the loudspeaker system is also connected to earth. In this way the spatial control alters the ratio of sound energy generated by the inside and outside panels, but only above a frequency of around 300Hz. Frequencies below 300Hz, which are largely non-

directional, are unaffected and radiated at equal level by both the inside and outside panels of the loudspeaker. Moreover the overall radiated power from both rear panels remains constant, irrespective of the changing ratio of radiation between panels. Adjustment of the potentiometer arm 42 should thus vary the perceived image without audible change of volume.

According to Bose the modification is immediately applicable to Model 901 loudspeakers which already have the necessary three terminals, but models 501 and 601 speakers will need some modification. It will be interesting to chart the progress of application no. 0 007 453 through the European Patent Office because the text contains self-congratulatory statements which are arguable and of a type normally inadmissible in a patent document, e.g. according to Bose the 901 system "has met with wide critical and consumer acclaim throughout the world, receiving an unprecedented series of rave reviews"!

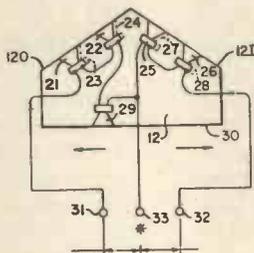


FIG. 4

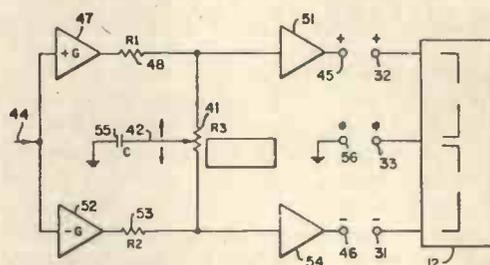


FIG. 5

POINTS ARISING

THE PERSONAL COMPUTER BOOK by Robin Bradbeer in *PE* October 1980 (Review)

NOTE: Input Two-Nine, the publisher of this book has been taken over by Gower. Those who read this review should note that the book is now available from: Gower Publishing Company, 1 Westmead, Farnborough, Hants, GU14 7RU.

News Briefs

LARGER PREMISES

ACE MAILTRONIX has moved into larger premises at 3A, Commercial Street, Batley, W. Yorks WF17 5HJ. The company specialises in Electronic Components for magazine projects in addition to its electronic component catalogue listing approx 1000 items available from stock by mail order. The catalogue is available now, priced 30p to mail order customers, and refundable with subsequent orders over £5. Callers are welcome during normal working hours Monday to Friday and on Saturday mornings, to whom the catalogue is free. Since its formation in 1977 Ace Mailtronix has helped many magazine project builders to find the more awkward components.

DISCO DESK

Part 4 BEN DUNCAN

IN this part the 12V subsystem, output routing and monitor switching, together with wiring, will be detailed.


PANEL WIRING

The mounting of the components and interwiring is a large task and must be approached systematically. All steps must be carefully checked, because the correction of small errors at a later stage can be very time consuming. A wiring colour code is extremely helpful provided you are not colour blind, in which case the choice of colours would be limited. A table (next month) gives a suitable colour code.

Begin by mounting components on the front panel. Set the rotary switch spigots for the appropriate number of switch positions. When mounting the slide pots and microphone transformer, ensure that the screws do not extend more than 1mm beyond the tapping, otherwise damage may result. The sliders are mounted on spacers so that a standard length screw may be used. Use Selotape to hold the spacers in place whilst the slider bezel, screws, panel and slide pot are aligned. Note that although the slider bezels specified are self-adhesive, they are drilled to accept the slide pot's fixing screws. Next, mount all the components on the edge panel. These can be wired directly to their respective barrier strips and the panel can be bolted in place. Then mount barrier strip no. 7 under the turntables. If the relays are mounted on a plate, then it is convenient to wire these up on the bench to their associated components, and then to mount the plate next to barrier strip no. 7 and complete the interwiring. At this stage all the wiring in Fig. 15 can be completed. When the front panel components are all mounted, this panel should be bolted to the console frame by means of hinges along the top edge. The panel should be arranged to sit in the position shown in dashed lines on this figure; this arrangement greatly eases the task of wiring up.

Before beginning the wiring, check the switch positions, ensure that the cards fit their respective edge connectors, especially when the panel is lowered and ensure that the edge connectors are the right way up, so that they connect with the card terminals when the components are facing you. Most important of all, the log sliders must be correctly orientated; pins 11 and 21 are 'earthy' and go to 0V, i.e. these are uppermost when the panel is hinged back.

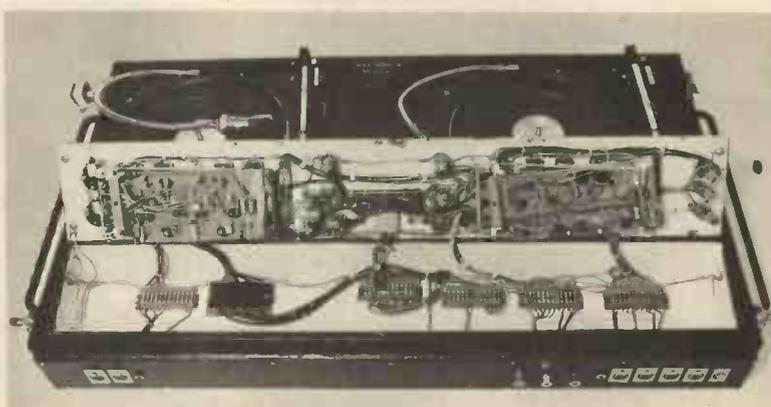Wiring begins with the 'chassis earths'. Unlike the 0V connections, these go directly to the mains earth from screens and all exposed metalwork, which must be permanently earthed. The 0V connections on the other hand can be 'ground-lifted' to prevent hum loops. It must be emphasised that the chassis and 0V earths should be regarded as being entirely separate. Connect all handles, panels, screens,



turntables, gooseneck arms and other exposed metalwork via 16/0.2 wire to the chassis earth commoning point.

12V SUBSYSTEM

The 12 volt subsystem should be wired next and the relays, lamps and monitor amplifier can be tested if a 12V supply is to hand. The lamps are normally wired via the spare contacts on each push-button switch. However, extra switch elements may need to be added to certain switches to ensure a consistent pattern, i.e. 'lamps on' = 'function on'. Also test for isolation between chassis earths and the 12V '0V' connections. Before wiring the left-hand edge connector socket, attach a generous length of wire to the VU meters. These will be wired later, but they are difficult to reach once the adjacent sockets are wired. Likewise, be sure that the 12V subsystem switches adjacent to the right-hand (Cards 3 and 4) edge connectors are correctly wired. Remove edge connector 2 and commence wiring connector 1. Sleeve alternate connections and cut off generous lengths of wire. It will only be possible to connect a few cables as yet, but route the cables as far as possible, using self-adhesive aluminium cable clips to hold them in place temporarily, in conjunction with re-usable cable ties.

When all the connections to the Card 1 edge connector have been made, replace edge connector No. 2 and recommence. As the work progresses, the cable looms will take shape and the loose ends will be tied up. However, where multiple connections are to be made, as on the routing switches and at the power supply bus-bars, the easiest course of action is to attach and solder all the connections simultaneously, and for this reason they are best left until the remainder of the wiring is completed.

Next Month: Completing the wiring

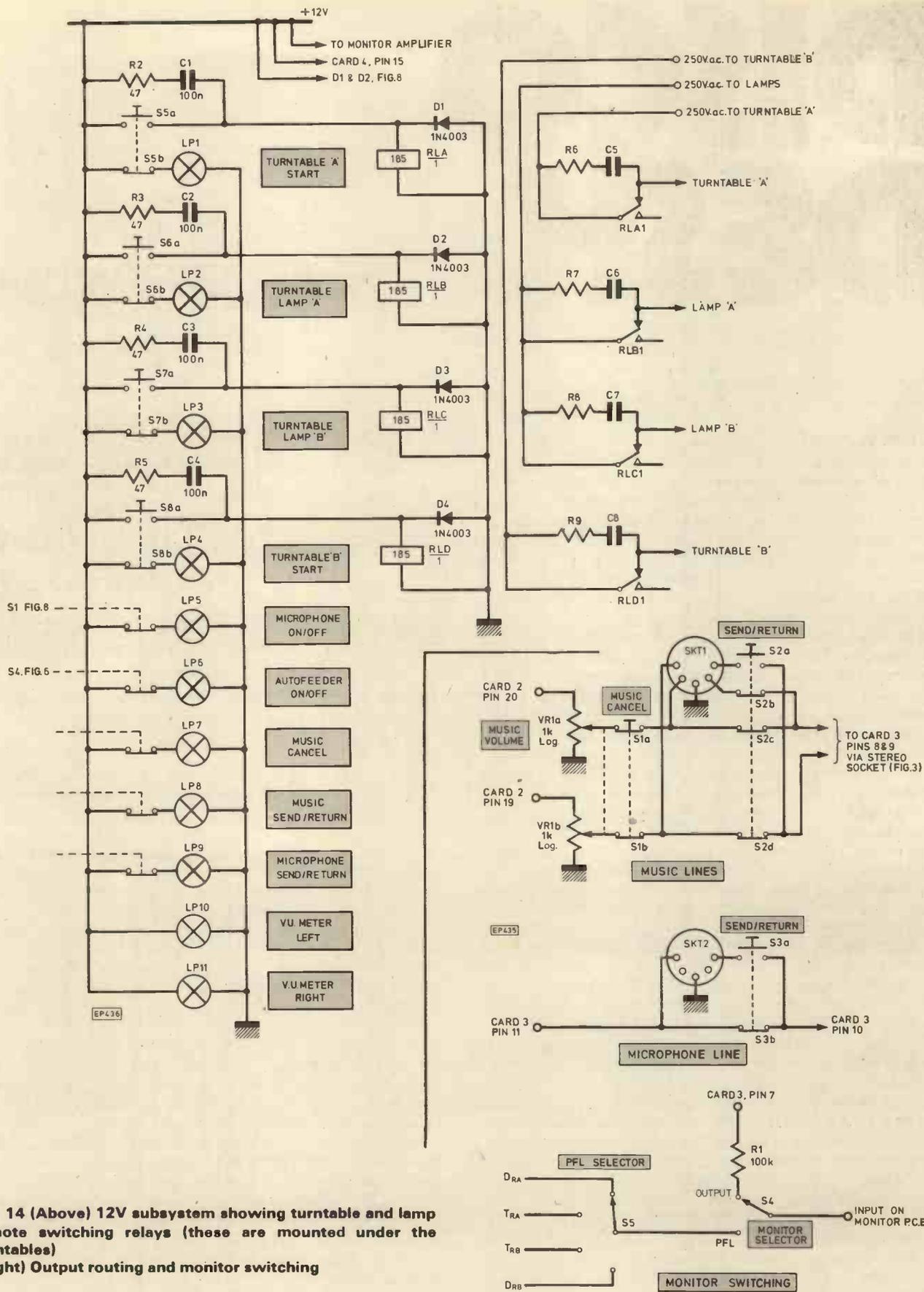


Fig. 14 (Above) 12V subsystem showing turntable and lamp remote switching relays (these are mounted under the turntables) (Right) Output routing and monitor switching

3 GREAT BARGAINS

PLUS-FREE GIFT WITH EACH ORDER!



TOOL PACK — consisting of the new WELLER 12W 240V MINI IRON, an XCELITE M60 MINI DRIVER KIT of 6 jeweller's type slotted and Phillips screwdrivers, plus torque amplifier handle and an XCELITE LIGHT AND MEDIUM DUTY KNIFE SET, including 10 assorted blades for a wide range of cutting, all designed to meet the need of today's electronics enthusiast.

£9.95 inc.VAT & P.P.

Plus Free pack of 3 soldering aid tools



PHILIPS ANALOGUE MULTIMETER — the Philips UTS 003, designed with the electronics enthusiast in mind. 20,000 Ω/V; DC voltage 300 mV — 1000V; AC Voltage 1.5V — 1500V; DC Current 50 μA — 2.5A; AC Current 250 μA — 2.5A; Resistance 0 — 1MΩ; Decibel range — 20dB — +65dB. Large easy to read scale and mirror to eliminate parallax errors; overload protected. Requires two penlite batteries (not supplied). Manufactured to IEC 348 standard.

£23.95 inc.VAT & P.P.

Plus Free Lufkin Ultralok 10ft/3m tape



INSTANT HEAT GUN KIT — containing the WELLER Instant Heat Gun, 2 spare copper soldering tips, one smoothing tip, one plastic cutting tip, soldering aid tool, flux brush, tip wrench, coil of 60/40 rosin core solder, all contained in a tough plastic carrying case. 100W 240V.

£15.95 inc.VAT & P.P.

Plus Free Xcelite Heavy duty hobby knife

I wish to order: _____ Quantity required _____

1st Offer £9.95 each _____

2nd Offer £23.95 each _____

3rd Offer £15.95 each _____

I enclose Cheque/Postal Order for

£ _____

Debit my Access/Barclaycard

Number _____

Name _____

Address _____

_____ Block Capitals

Philips Service.
Dept. CSO, 604 Purley Way, Waddon,
Croydon, CR9 4DR.


Philips Service.
604 Purley Way, Waddon, Croydon, CR9 4DR.

For immediate credit card orders —
Ring 01-688 3633 between 9.00am & 5.00pm,
Monday to Friday, quoting your Access/
Barclaycard number & we will post by return.

All prices include VAT & Post/Packing.
Gifts are offered subject to availability &
may be substituted by goods of a similar
value without prior notice.

These offers apply to all orders received
before 31st December 1980.

Philips Service

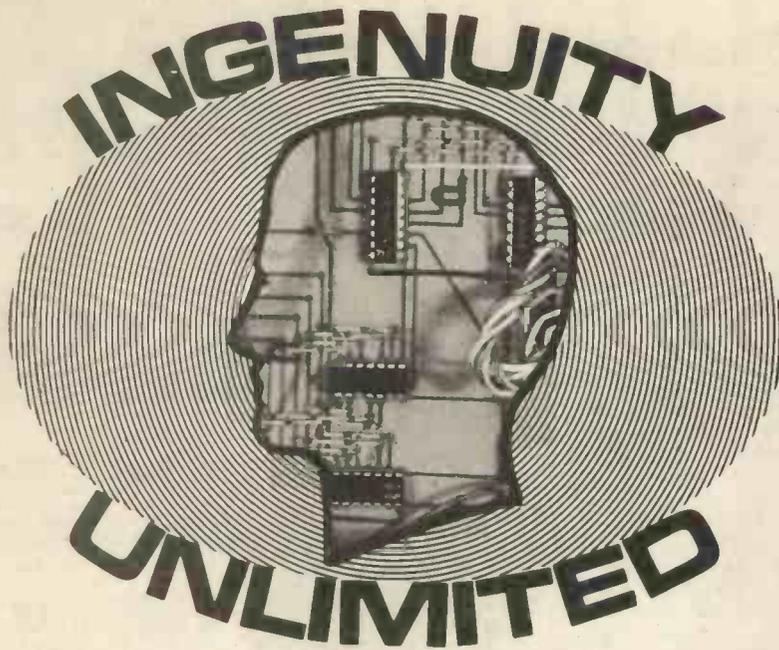

A selection of readers' original circuit ideas. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought.

Why not submit *your* idea? Any idea published will be awarded payment according to its merits.

Articles submitted for publication should conform to the usual practices of this journal, e.g. with regard to abbreviations and circuit symbols. Diagrams should be on separate sheets, not inserted in the text.

Each idea submitted must be accompanied by a declaration to the effect that it has been tried and tested, is the original work of the undersigned, and that it has not been offered or accepted for publication elsewhere.

HERE is an electronic substitute for a polyphonic electromechanical keyswitch assembly. The 4416 is a quad bilateral switch. When a logical '0' is applied to all control inputs, switches A and D are open and switches B and C are closed. When a logical '1' is applied to all control inputs, the reverse happens A and D are closed and B and C are open.


In my design there are two 4416 i.c.s for each keyboard contact. The keyboard can now use simple single pole contacts. When a keyboard contact is pressed, a logical '1'

is supplied to the 4416s of that keyboard contact activating the s.p.d.t. switches, and that particular voltage is supplied to VCO1 hold. If any further keys are pressed they will supply simultaneously the relevant voltages to the VCO holds and so on. The voltage divider is now situated between the i.c.s and not on the keyboard contacts. (Power supply connections are omitted from the figure for simplicity — all pin 14s to +9V, pin 7s to 0V.)


The system only uses three of the s.p.d.t. switches, but it can be expanded to

provide simultaneous programming for more. 8 or 10 notes played together might be feasible. Alternatively the unused s.p.d.t. switch can be used to provide the -ve voltage for the triggering of the envelope shapers etc. The ohmic resistance of the 4416 switches provides isolation for the VCO hold circuits. All the usual rules should be observed when handling CMOS i.c.s.

R. M. Pimlott,
Bexleyheath,
Kent.

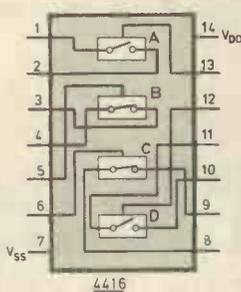

KEYBOARD SWITCHES

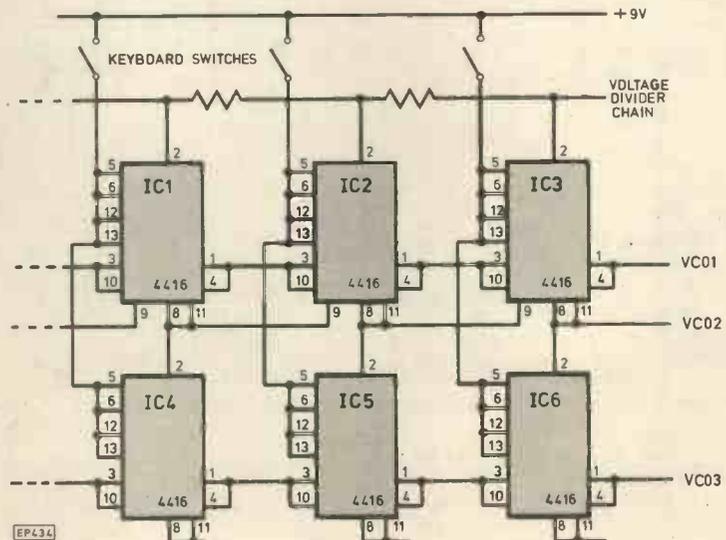

A TRUE PEAK-READING D.C. VOLTMETER


THE accompanying circuit shows a simple method of reading the peak rather than the average of a d.c. waveform. Of course, this may be applied to an a.c. signal simply by rectification prior to feeding the signal to this circuit. Two 741-type op amps are used, in this case in the form of a dual device. The peak voltage is held in a capacitor C_x , which is charged further whenever the comparator IC1a detects that the input voltage exceeds the value on C_x . D2 prevents reverse leakage into IC1a output, while D1 restores the d.c. offset caused by D2.

IC1b is a simple voltage follower to preserve the leakage resistance from C_x at a high value. In fact, this value will be of the order of 10 megohms. With a 0.22µF capacitor at C_x , the time constant is of the order of 1.5 seconds, giving a good

response to a music or audio signal. By using a value as high as 100µF (tantalum) at C_x , a "peak-hold" effect is obtained, with a time constant of some minutes. D.c. offset at the output has not been found to

exceed a couple of mV, when using 2 × PP3 for the supplies. Supply-line current drain is about 4mA.

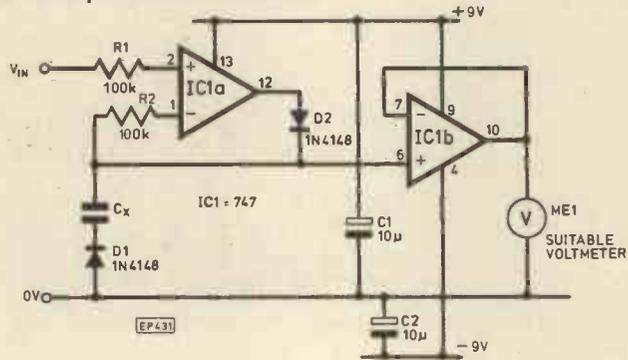R. J. Crowther,
Stourbridge,
West Midlands.



SIMPLE PULSE GENERATOR

SHOWN is the circuit of a simple pulse generator which is useful for testing the operation of digital circuits. It uses a type 4011 CMOS integrated circuit and functions as follows.

The monostable formed from IC1a and IC1b is triggered by momentarily grounding pin 6 through S1 and then generates a negative going pulse of duration T1, at output A, and a positive pulse, of duration T2, at output B. With the component values shown VR1 will set the duration T1 in the range 50 milliseconds to 1 second. If the triggering pulse or closure of S1 has duration T then for:

$$T < T1 \text{ then } T1 = T2$$

$$T > T1 \text{ then } T2 = T$$

Thus output B can also provide a "d.bounced" digital signal corresponding to the position of S1.

IC1c and d are interconnected to form an astable which can generate pulses of duration T3 varying from about 2 to 100 milliseconds depending on the setting of VR2. With S2 set to "Pulse" the astable is gated by output B and is therefore controlled by S1 to give either a train of N pulses, where $N \approx T2/T3$, or a continuous pulse train at output C. If S2 is set to "Run" then output C provides a continuous pulse train independent of S1.


When S2 is set to "Pulse" and VR1 at maximum, VR2 can be set so that $N = 1$ to 10. Output C can then be used to check a counter/decoder/display circuit, each momentary closure of S1 advancing the counter system by N pulses.

Alternatively, with S1 set to "Run", output C can be used as a source of "clock" pulses, whilst outputs A and B are used for "gate" or "data" pulses.

The supply voltage V+ should be equal

to that of the circuit under test and can conveniently be taken from the supply rails of the latter. Each output will drive two TTL or 20 CMOS inputs.

G. B. Wills,
Ealing.

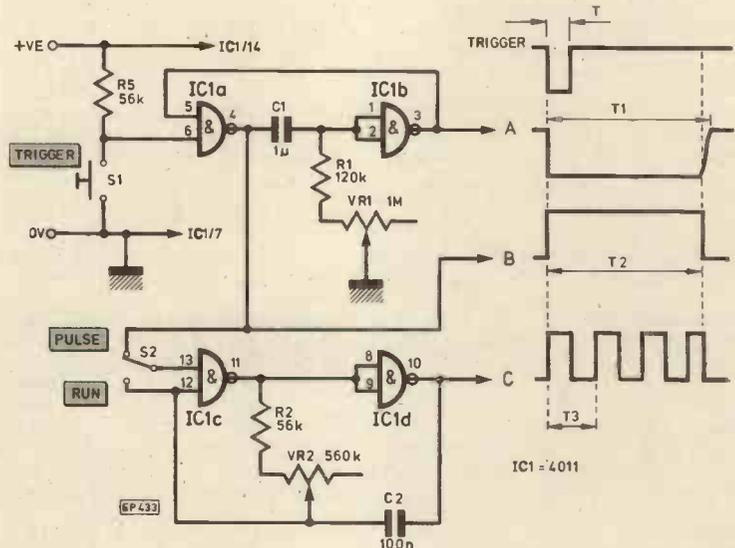

INDEX

JANUARY 1980 TO DECEMBER 1980

VOLUME 16

CONSTRUCTIONAL PROJECTS

- A Simple Conversation Aid by *J. M. Watt M.B., Ch.B.* March 62
- Acoustically Coupled Telephone Modem by *K. Amor* Feb. 39, March 54
- Alarm, Security Sentinel Nov. 32, Dec. 54
- Alarm, Security Sentry July 64
- Amplifier, Class "A" Sept. 58
- Amplifier, PE Congress April 38, May 26, June 26
- Amplifier, 125W Oct. 52
- Audio Isolator by *G. Davies* March 22
- Bench PSU by *J. P. MacCaulay* June 34
- Car Radio, PE Traveller March 40, April 70
- Chip Checker by *L. V. Cooper* April 25
- Cine Frame Counter by *Stephen Ibbs* Oct. 30
- Class "A" Amplifier by *K. Garwell* Sept. 58
- Cleaner, Ultrasonic Jan. 41
- Constant Current Sources by *I. Millar* Aug. 60
- Controller, Infra Red May 42
- Controller, Greenhouse Temperature June 58
- Controller, Soldering Iron Feb. 30
- Controller, 2 Wire Train April 72, May 66
- Conversation Aid, A Simple March 62
- Counter, Cine Frame Oct. 30
- Current Sources, Constant Aug. 60
- Desk, Disco Sept. 24, Oct. 62, Nov. 56, Dec. 60
- DFM, PE July 50
- Diamatic Update, PE Nov. 52
- Digital Frequency Meter by *M. Tooley B.A. and D. Whitfield B.A., M.Sc.* March 72
- Digital Frequency Meter, PE July 50
- Digital Multimeter, PE July 42
- Digital Tachometer by *G. I. Williams* June 64
- Disco Desk by *Ben J. Duncan* Sept. 24, Oct. 62, Nov. 56, Dec. 60
- DMM, PE July 42
- Doorbell Monitor by *J. A. Barrow* Aug. 30
- Dynamic Noise Limiter by *R. A. Penfold* Feb. 19
- Dynamic Semiconductor Tester by *M. Tooley B.A. and D. Whitfield B.A., M.Sc.* May 48
- Electrostat by *P. A. Dakin* Feb. 46
- Enlarger Timer by *R. Besson* March 33
- Eprom Programmer by *A. A. Berk B.Sc., Ph.D.* Jan. 55
- Filter, Scratch and Rumble Jan. 22
- Games Timer by *Stephen Ibbs* Nov. 23
- Generator, Programmable Sound Sept. 32
- Greenhouse Temperature Controller by *P. R. Williams* June 58
- Guitar, Mastertune June 39
- Infra Red Controller by *Malcolm Plant* May 42
- Isolator, Audio March 22
- Lead Tester by *Chris Lane* Oct. 36
- Loop, 20mA Dec. 40
- Master Rhythm by *A. J. Boothman B.Sc.* Dec. 32
- Mastertune, Guitar by *B. J. Hamill* June 39
- Memory, 4 Channel Digital Feb. 56
- Metal Locator, PE Magnum Aug. 51, Sept. 52
- Meter, Digital Frequency March 72
- Meter, PE Digital Frequency July 50
- Microtune Dec. 26
- Modem, Acoustically Coupled Telephone Feb. 39, March 54
- Monitor, Doorbell Aug. 30
- Multimeter, PE Digital July 42
- Noise Limiter, Dynamic Feb. 19
- PE Congress by *Graham Jackson* April 38, May 26, June 26
- PE Diamatic Update by *J. R. W. Ames and L. Blyth* Nov. 52
- PE DFM by *D. Mottram* July 50
- PE DMM by *Martin Kent* July 42
- PE Magnum Metal Locator by *Andy Flind* Aug. 51, Sept. 52
- PE Microtune by *M. Kent* Dec. 26
- PE Teletext by *D. J. Shortland* Aug. 38, Sept. 42, Oct. 56, Nov. 48
- Pendant, Scintillating Jan. 48
- Prescaler by *M. Tooley B.A. and D. Whitfield B.A., M.Sc.* April 34
- Programmable Sound Generator by *D. Coutts* Sept. 32
- Programmer, Eprom Jan. 55
- PSU, Bench June 34
- Radio PE Traveller, Car March 40, April 70
- R/C Servo Tester by *C. R. Francis B.Sc.* Jan. 50
- Rhythm, Master Dec. 32
- Scintillating Pendant by *Owen Bishop* Jan. 48
- Scratch and Rumble Filter by *R. A. Penfold* Jan. 22

Security Sentinel by William Dickinson	Nov. 32, Dec. 54
Security Sentry by William Dickinson	July 64
Soldering Iron Controller by M. S. Dhingra	Feb. 30
Speech Synthesis by Dr. A. A. Berk	Nov. 26, Dec. 44
Split Phase Tremolo by J. McCarthy	May 34
Synchroniser, Tape/Slide	July 34
Tachometer, Digital	June 64
Tape/Slide Synchroniser by R. A. Penfold	July 34
Teletext, PE	Aug. 38, Sept. 42, Oct. 56, Nov. 48
Tester, Dynamic Semiconductor	May 48
Tester, Lead	Oct. 36

Tester, R/C Servo	Jan. 50
Timer, Enlarger	March 33
Timer, Games	Nov. 23
Train Controller, 2 Wire	April 72, May 66
Tremolo, Split Phase	May 34
Ultrasonic Cleaner	Jan. 41
2 Wire Train Controller by J. Milne	April 72, May 66
4 Channel Digital Memory by C. Harding	Feb. 56
20mA Loop by Stephen Ibbes	Dec. 40
125W Amplifier	Oct. 52

GENERAL FEATURES

A True peak-reading d.c. voltmeter by R. J. Crowther	Dec. 65
Acorn Review by Dr. A. A. Berk	Aug. 22
Animated Graphics by P. Houghton	May 40
Calculator Chips as Logic Devices by P. A. Birnie	Jan. 69
Colour Blindness by Dr. Janet Voke	June 48
Compukit Update by Dr. A. A. Berk	March 68, June 71
Edukit Review by Mike Abbott	April 22
Electrochemistry by A. T. Kuhn M.A., D.Phil.	Aug. 35
INGENUITY UNLIMITED	Jan. 35, Feb. 60, March 58, April 64, May 58, June 52, July 58, Aug. 66, Sept. 66, Oct. 40, Nov. 68, Dec. 64
Accurate Kitchen Timer by David Ian	July 60
Alarm Clock Weekend Lockout by P. M. Jessop	Sept. 66
Appointment Reminder by A. M. Tucker	May 61
Automatic Car Aerial Control by D. A. Petty	Feb. 65
Battery Check by D. H. Halliday	Sept. 68
Car Anti-Theft Device by Alastair Mutch	Oct. 41
Car Battery Charge Indicator by A. Dames	May 59
Car Burglar Alarm by C. Guthrie	Jan. 36
Car Cassette Power Supply by N. Riddiford	Feb. 62
Car Courtesy Light Timer by A. Chadwick	May 62
Current/Voltage Regulator by A. J. Chadwick	May 61
Disco Cross Fader by Ben. J. Duncan	Jan. 38
Four Digit to Six Digit Clocks by P. Ratnam	Sept. 67
Four State Indicator by V. V. Shah	May 62
Frequency Tester/Missing Pulse Detector by P. R. Turner	June 55
Function Generator by M. Rodgers	Sept. 68
Glow Plug Supply by R. MacFarlane	Jan. 37
Guitar Tremolo by A. R. Curtis	March 59
Hex Keypad by D. Greaves	Aug. 66
Hexadecimal Display by R. G. Stubbs	March 60
Inexpensive A to D Converter by D. Greaves	Aug. 68
"Jacked Up" Regulator by J. A. Barrow	Feb. 61
Keyboard Scanner by A. Piper	Aug. 68
Keyboard Switches by R. M. Pimlett	Dec. 64
Lamp Flasher by P. F. Farthing	June 53
Light Triggered Variable Pulse by M. Miller	Nov. 69
Logic Probe by I. Mercer	Nov. 70
Low Noise Mic Pre-Amp by P. R. Williams	April 65
Low Pass Filter by J. J. Lambe	Jan. 38
Metal Detector by P. R. Williams	April 65
Model Railway Controller by J. O. Linton	April 64

Model Railway Signal Controller by C. R. Bray	June 54
Model Traffic Lights by M. J. Rendle	July 59
Motor Reversal by C. P. Finn	June 52
Moving Lights by A. W. Cunningham	July 58
Multiplexer by C. F. Shorto	Aug. 67
Noise Gate by C. Bishop	July 59
Op Amp Battery Supply by A. J. Flind	June 54
Op-Amp Tester by S. Callaghan	Nov. 71
Phased White Noise by R. Otterwell	Jan. 37
Portable Tennis by P. Bailey	Aug. 69
Quiz Win Indicator by J. Sarns	Sept. 67
R/C Failsafe and Servo Tester by J. R. Shield	Nov. 69
R/C Servo by N. Roche	Jan. 36
Rhythm Code Generator by E. J. Weremiuk	Feb. 65
Rhythm Generator for Minisonic by A. R. Bradford	May 58
Roulette Wheel by A. J. Kitching	Oct. 40
Scope Calibrator by A. Andrews	Feb. 66
Shoot Game by D. Johnson	Oct. 41
Shoot Game by L. Privett	Nov. 71
Simple Autofade by T. P. Hopkins	Jan. 35
Simple d.c. Power Controller by J. M. Lucas	May 60
Simple Pulse Generator by G. B. Wills	Dec. 65
Slave Flash Controller by R. C. Mackay	Sept. 68
Stepset Sequencer by P. R. Williams	July 61
Stereo Balance Meter by T. Austin	June 53
Tape/Slide Sync by R. N. Johnson	Feb. 60
TTL/CMOS Debounced Switch by A. F. Olivera	July 60
TTL Logic Tester by A. C. Twist	Nov. 68
TTL Staircase Generator by B. Bell	May 60
Voltage Sensitive Relay by M. S. Dhingra	Feb. 61
Waveform Converter for Minisonic by P. G. Ludgate	Feb. 62
Wah-Wah Pedal by Richard Fuller	March 58
3 Lamp 2 Wire Controller by J. P. Kemp	Feb. 66
200W Temperature Controller by D. Wedlake	March 59
555/556 Quick Tester by C. P. Finn	June 52
MICROBUS by D.J.D.	Feb. 53, April 60, June 68, Aug. 46, Oct. 24, Dec. 52
Micro Prompt	Feb. 23, Mar. 67, April 63, May 38, July 68, Sept. 40, Nov. 40
Power Supplies for MPU's by A. Clements	April 54, May 22
Resident Editor by N. A. Climpson	Nov. 43
SEMICONDUCTOR UPDATE by R. W. Coles	Jan. 26, Feb. 29, Mar. 25, April 24, June 32, July 27, Aug. 33, Sept. 20, Oct. 29, Nov. 39, Dec. 23

Intel 8294, Intel 2920, Plessey SL446A	Jan. 26
Ferranti ZN419CE, Intel 87C48, Texas MCM 68732	Feb. 29
Intel 8041/IBSC941	March 25
Llyis Electronics ZMOS F.E.T. (X520, X530) Traskert (AG 1000) Inmos (IU 101)	April 24
NEC mPD7801, Hewlett Packard HEDS-1000, Exar Integrated Systems XRL556, Mullard BT155	June 32
Intersil ICL7660, Thomson CSF TDA 1099 SP, LS1 Computer Systems Inc. LS7220	July 27
Epson America Inc. 7910, ITT UAA1003, Plessey MN9106	Aug. 33
Intel NSC800, Texas 74LS610, GEC MA537	Sept. 20
National Semiconductor LM1871, LM1872, Harris HM6564, National Semiconductor TO237, Motorola TDA1085A	Oct. 29

Hughes HNVM3008, National Semiconductor NM58174, Texas TLO11	Nov. 39 Dec. 27
Inmes IMS 1400, Thompson CSF EF 9365	Dec. 27
Softy Review by A. A. Berk B.Sc., PhD	Jan. 27
Sparkrite X5 Review	July 39
Speech Synthesis by Dr. A. A. Berk	Nov. 26, Dec. 44
Sinclair ZX80 Review by Mike Abbott	July 22
Strictly Instrumental by K. Lenton-Smith	Feb. 45, May 65, Aug. 26,
Surefire Electronic Ignition Review	May 33
Switching Regulators by D. L. H. Smith	Jan. 64
The Shape of Spacecraft by C. R. Francis B.Sc., Ph.D.	Oct. 44
The ULA by E. Fry B.Sc.	Feb. 34
Transistor Parameters by R. A. Hatton	March 29
UK101 Teleprinter Interface by J. J. Trevillion	Sept. 38
Video—The Slow Revolution by R. Miles	July 28
Video Information Centre by R. Miles	July 49
Wersi and Clef Sound Processor Kits Review	June 24
Wiegand Effect by B. Dance M.Sc.	Jan. 39

NEWS AND COMMENT

BOOK REVIEWS	Feb. 36, April 80, June 47, Oct. 68, Nov. 62
Breadboard Review	March 26
COUNTDOWN	Jan. 71, Feb. 28, March 63, April 71, May 73, June 47, July 37, Aug. 65, Sept. 21, Oct. 68, Nov. 51, Dec. 25
EDITORIAL	Jan. 17, Feb. 15, March 17, April 17, May 17, June 17, July 17, Aug. 17, Sept. 17, Oct. 19, Nov. 17, Dec. 17
INDUSTRY NOTEBOOK by Nexus	Jan. 47, Feb. 24, March 21, April 33, May 21, June 23, July 21, Aug. 21, Sept. 23, Oct. 23, Nov. 20, Dec. 21
MARKET PLACE	Jan. 18, Feb. 16, March 18, April 18, May 18, June 18, July 18, Aug. 18, Sept. 18, Oct. 20, Nov. 18, Dec. 18

NEWS BRIEFS	Jan. 66, Feb. 28, 55, March 30, 79, May 37, 41, 46, June 36, Aug. 59, Sept. 62, Oct. 55, 68, Nov. 44, Dec. 59
PATENTS REVIEW	Jan. 62, Feb. 38, March 64, April 79, May 53, June 62, July 73, Aug. 59, Sept. 51, Oct. 67, Nov. 55, Dec. 59
PE/Lektrokit Competition Results	Feb. 38
POINTS ARISING	Feb. 38, March 71, April 80, June 67, July 25, Aug. 31, Sept. 21, Oct. 67, Nov. 51, Dec. 59
READOUT	Jan. 63, March 80, April 80, May 74, June 46, July 63, Aug. 70, Nov. 61, Dec. 50
SPACEWATCH by F. W. Hyde	Jan. 32, Feb. 27, March 66, April 66, May 25, June 45, July 40, Aug. 49, Sept. 64, Oct. 32, Nov. 47, Dec. 43

SPECIAL SUPPLEMENTS AND OFFERS

Capacitor Offer	Aug. 45
Casio Watch Offer	July 33
Casio Watch Offer Correction	Sept. 65
Computer Case Offer	Feb. 37, March 81
Edukit Offer	May 63, June 31
How to Use Your Free Stickies	May 47
P.A. Loudspeaker Systems by Ben J. Duncan	March 44
Radio/Cassette Offer	Dec. 24

Seiko Watch Offer	Jan. 34
Speaker Offer	April 68
Special Offer—Auroranging DMM's	Sept. 57
Special Offer—PE Congress	Nov. 31
Turntable Offer	Oct. 35, Nov. 66
Video for Everyone by G. K. Gardner	April 44
Watch Offer	Mar. 65



The biggest name in solder worldwide

Products that help you make a better job of it.



Arax Multicore Solder.
Economy pack for general non-electrical use. Replaces solid wire and stick solder. (B.S. 219 Grade L). Econopak 200g reel of 3mm dia. Size 16A. **£4.14 per reel.**



Handy Dispensers	Per pack
PC115 for printed circuits.	£1.15
SV130 for radio and TV repairs.	£1.61
AR140 for non-electrical applications, except aluminium.	£1.38
SS160 for stainless steel and silver jewellery.	£2.53
19A for printed circuit boards – non-corrosive.	96p
AL150 for aluminium.	£1.93
BCA16 solder cream for stainless steel, jewellery and household products (non-electrical).	£3.22
BCR10 solder cream for electronic and electrical use.	£1.38
BCA14 all purpose solder cream, non-electrical jointing and repairing.	£1.38



Econopak
Ersin Multicore 5-core solder. Contains non-corrosive flux for electrical applications. 1.2mm dia. 200g Econopak. Size 13A. **£4.14 per reel.**



Toolbox Reels.
Multicore 5-core solder for general use. Suitable for electrical joints (B.S. 219 Grade C). 40/60 tin/lead. 1.6mm dia. Size 3. **£3.91 per reel.**

Savbit.
Multicore 5-core solder for radio, TV and similar work. Reduces copper erosion. Suitable for service engineers and manufacturers using small quantities of solder. 1.2mm dia. Size 12. **£3.91 per reel.**




Metal Soldering.
Arax Multicore 4-acid-core solder for metal fabrication (not aluminium) and repairs. 40/60 tin/lead 1.6mm dia. Size 11. **£3.91 per reel.**



Multicore Wick.
Multicore solder-wick for removing solder from virtually any joint. 1.7mm dia. Size AB10. **£1.38 per reel.**

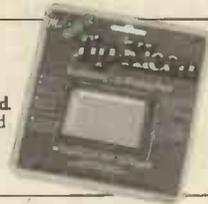Tip Kleen.
Multicore Tip Kleen, Soldering-Iron tip wiping pad. Replaces wet sponges. (Should not be used above 350°C). **81p per pack.**



TV and Radio Soldering.
Savbit Multicore for radio, TV and similar work. Reduces copper erosion. 1.2mm dia. Size 5. **90p per handy dispenser.**
Econopak.
General purpose solder suitable for all electrical joints. 40/60 alloy 1.2mm dia. Size 6. **58p per handy plastic dispenser.**



Aluminium Soldering.
Alu-Sol Multicore 4-core solder for soldering most types of aluminium. No extra flux needed. 1.6mm dia. Size 4. **£11.50 per reel.**



Soldering Flux Pastes.
Multicore soldering flux paste. Extra fast, non-corrosive, rosin-flux for electrical and general purpose soldering.
Rosin RF10. 35g net. **69p per pack.**
Multicore soldering flux paste for soft metals (except aluminium) and stainless steel. Non-electrical.
Arax A.F14. 35g **69p per pack.**



Wire Stripper and cutter.
Wire stripper and cutter with precision ground and hardened steel jaws. Adjustable to most wire sizes. With handle locking-catch and easy-grip plastic covered handles.
Ref. 9. **£2.69 per pair.**

Bib Hi-Fi Accessories Ltd., (Solder Division), Kelsey House, Wood Lane End, Hemel Hempstead, Hertfordshire HP2 4RQ. Telephone: (0442) 61291.

All recommended retail prices shown are inclusive of VAT. If you have difficulty in obtaining any of these products send direct with 40p for postage and packing. For free colour brochure send S.A.E.

BI-PAK SEMI CONDUCTORS,

CERAMIC PAK

16160 - 24 - 3 of each value - 22pf 27pf 33pf 39pf 47pf 68pf 82pf £0.89
 16161 - 24 - 3 of each value - 100pf 120pf 150pf 180pf 220pf 270pf 330pf 390pf £0.89
 16162 - 24 - 3 of each value - 470pf 560pf 680pf 820pf 1000pf 1500pf 2200pf £0.89
 16163 - 24 - 3 of each value - 4700pf 6800pf 01uf 015uf 022uf 03uf 047uf £0.89

ELECTROLYTIC PAKS

A range of paks each containing 18 first quality, mixed value miniatures.
 16201 - 47mFD-10mFD £0.69
 16202 - 10mFD-100mFD £0.69
 16203 - 100mFD-680mFD £0.69

CARBON RESISTOR PAKS

16213 - 60 mixed $\frac{1}{2}$ W 100 ohms - 820 ohms £0.69
 16214 - 60 mixed $\frac{1}{2}$ W 1K ohms - 82K ohms £0.69
 16215 - 60 mixed $\frac{1}{2}$ W 10K ohms - 83K ohms £0.69
 16216 - 60 mixed $\frac{1}{2}$ W 100K ohms - 820K ohms £0.69
 16217 - 40 mixed $\frac{1}{2}$ W 100 ohms - 820 ohms £0.69
 16218 - 40 mixed $\frac{1}{2}$ W 1K ohms - 82K ohms £0.69
 16219 - 40 mixed $\frac{1}{2}$ W 10K ohms - 82K ohms £0.69
 16220 - 40 mixed $\frac{1}{2}$ W 100K ohms - 820K ohms £0.69
 16230 - 60 mixed $\frac{1}{2}$ W 1 Meg 10 Meg ohms £0.69
 16231 - 40 mixed $\frac{1}{2}$ W 1 Meg - 10 Meg ohms £0.69

COMPONENT PAKS

16164 - 200 Resistor mixed value approx (Count by weight) £0.69
 16165 - 150 Capacitors mixed value approx (Count by weight) £0.69
 16166 - 50 Precision resistors. Mixed values £0.69
 16167 - 80 $\frac{1}{2}$ W resistors. Mixed values £0.69
 16168 - 5 pieces assorted ferrite rods £0.69
 16169 - 2 Tuning ganged MW LV VHF £0.69
 16170 - 1 Pack wire 50 metres assorted colours single strand £0.69
 16171 - 10 Reed switches £0.69
 16172 - 3 Micro switches £0.69
 16173 - 15 Assorted pots £0.69
 16174 - 5 metal jack sockets 3 x 3.5mm 2 x standard switch types £0.69
 16175 - 30 Paper condensers - mixed values £0.69
 16176 - 20 Electrolytics trans types £0.69
 16177 - 1 Pack assorted hardware - Nuts, bolts, gromets etc £0.69
 16178 - 5 Mains slide switches, assorted £0.69
 16179 - 20 Assorted tag strips and panels £0.69
 16180 - 15 Assorted control knobs £0.69
 16181 - 3 Rotary wave change switches £0.69
 16182 - 2 Relays 6-24V operating £0.69
 16183 - 1 Pak copper laminate approx 200 sq inches £0.69
 16184 - 15 Assorted Fuses 100mA 5 amps £0.69
 16185 - 50 metres PVC sleeving assorted size and colours £0.69

METAL FOIL CAPACITOR PAK

16204 - Containing 50 metal foil capacitor like Mullard C280 series - Mixed values ranging from 0.1uf-2.2uf. Complete with identification sheet £1.38

SLIDER PAKS

16190 - 6 slider mixed £0.69
 16191 - 6 slider 470 ohms £0.69
 16192 - 6 slider 10K ohms 1in £0.69
 16193 - 6 slider 22K ohms 1in £0.69
 16194 - 6 slider 47K ohms 1in £0.69
 16195 - 6 slider 47K ohms £0.69

TRANSISTORS

AC107	£0.25	AD182	£0.40	BC161	£0.25	BC441	£0.35	BF165	£0.55	2N1305	£0.21
AC113	£0.23	AD181/182	£0.41	BC162	£0.23	BC480	£0.44	BF187	£0.28	2N1308	£0.28
AC115	£0.23	AD1140	£0.83	BC163	£0.29	BC481	£0.44	BF173	£0.23	2N1307	£0.29
AC117	£0.35	AF124	£0.35	BC164	£0.22	BC477	£0.23	BF178	£0.44	2N1308	£0.35
AC117K	£0.39	AF126	£0.35	BC167	£0.12	BC478	£0.23	BF177	£0.30	2N1309	£0.35
AC121	£0.23	AF128	£0.35	BC168	£0.12	BC479	£0.23	BF178	£0.32	2N1711	£0.23
AC122	£0.18	AF127	£0.37	BC159	£0.12	BC547	£0.12	BF179	£0.35	2N2218	£0.23
AC125	£0.21	AF139	£0.40	BC160	£0.30	BC548	£0.12	BD238A/		2N2221	£0.23
AC128	£0.21	AF178	£0.89	BC181	£0.44	BC549	£0.12	240AMP	£1.16	2N2222	£0.23
AC127	£0.21	AF178	£0.89	BC187	£0.14	BC550	£0.16	BF180	£0.35	2N2388	£0.18
AC128	£0.18	AF180	£0.89	BC188	£0.14	BC556	£0.16	BF181	£0.35	2N2711	£0.26
AC128K	£0.30	AF181	£0.87	BC189	£0.10	BC557	£0.16	BF182	£0.35	2N2712	£0.26
AC132	£0.23	AF186	£0.98	BC190	£0.10	BC558	£0.16	BF183	£0.35	2N2714	£0.26
AC134	£0.23	AF239	£0.44	BC170	£0.10	BC559	£0.18	BF184	£0.23	2N2900	£0.21
AC137	£0.23	AL102	£1.38	BC171	£0.10	BC560	£0.18	BF185	£0.23	2N2905	£0.21
AC141	£0.24	AL103	£1.38	BC172	£0.10	BC211	£0.89	BF186	£0.30	2N2906	£0.18
AC141K	£0.36	AL104	£1.81	BC173	£0.10	BC212	£0.89	BF187	£0.30	2N2907	£0.23
AC142	£0.23	AL110	£1.81	BC174	£0.17	BD116	£0.58	BF188	£0.48	2N2923	£0.17
AC142K	£0.23	AF186	£0.98	BC175	£0.40	BD118	£0.92	BF189	£0.32	2N2924	£0.17
AC151	£0.23	BC107	£0.09	BC177	£0.18	BD121	£0.75	BF195	£0.12	2N2925	£0.17
AC153	£0.25	BC107A	£0.09	BC178	£0.18	BD123	£0.75	BF196	£0.12	2N2926	£0.10
AC153K	£0.35	BC107B	£0.10	BC179	£0.18	BD124	£0.81	BF197	£0.12	2N2928	£0.09
AC154	£0.23	BC107C	£0.12	BC180	£0.29	BD131	£0.40	BF198	£0.18	2N2929	£0.09
AC155	£0.23	BC108	£0.09	BC181	£0.10	BD132	£0.40	BF199	£0.18	2N2930	£0.09
AC156	£0.23	BC108A	£0.09	BC182	£0.25	BD131/132MP	£0.82	MJE340	£1.58	2N2935	£0.09
AC157	£0.20	BC108B	£0.10	BC182L	£0.10			MJE3855	£0.84	2N3051	£0.20
AC165	£0.23	BC108C	£0.12	BC183	£0.10			MJE3856	£0.89	2N3054	£0.48
AC166	£0.23	BC109	£0.09	BC183L	£0.10	BD133	£0.48	TIP28A	£0.48	2N3055	£0.48
AC167	£0.23	BC109B	£0.10	BC184	£0.10	BD136	£0.48	TIP29B	£0.48	2N3402	£0.24
AC168	£0.28	BC109C	£0.12	BC184L	£0.10	BD138	£0.40	TIP29C	£0.51	2N3403	£0.24
AC169	£0.23	BC113	£0.18	BC185	£0.25	BD137	£0.40	TIP30A	£0.48	2N3404	£0.33
AC171	£0.20	BC114	£0.18	BC187	£0.25	BD138	£0.41	TIP30B	£0.48	2N3405	£0.38
AC176	£0.21	BC126	£0.20	BC207	£0.13	BD139	£0.41	TIP30C	£0.51	2N3702	£0.09
AC176K	£0.30	BC128	£0.25	BC208	£0.13	BD140	£0.41	TIP31A	£0.48	2N3703	£0.09
AC178	£0.20	BC132	£0.21	BC209	£0.14	BD138/140MP	£0.92	TIP31B	£0.48	2N3704	£0.09
AC178	£0.28	BC134	£0.21	BC212	£0.10	BF116	£0.92	TIP31C	£0.51	2N3705	£0.09
AC180	£0.23	BC136	£0.17	BC212L	£0.25	BF122A	£0.25	TIP32A	£0.48	2N3706	£0.09
AC180K	£0.32	BC138	£0.21	BC213	£0.10	BF152	£0.29	TIP32B	£0.48	2N3707	£0.09
AC181	£0.23	BC137	£0.21	BC251	£0.17	BF153	£0.29	TIP32C	£0.51	2N3708	£0.09
AC181K	£0.32	BC139	£0.37	BC251A	£0.16	BF154	£0.25	TIP41A	£0.51	2N3709	£0.09
AC187	£0.21	BC140	£0.35	BC301	£0.32	BF165	£0.40	TIP41B	£0.53	2N3710	£0.09
AC187K	£0.32	BC141	£0.32	BC302	£0.33	BF166	£0.32	TIP41C	£0.55	2N3711	£0.09
AC188	£0.21	BC142	£0.25	BC303	£0.32	BF167	£0.32	TIP42A	£0.51	2N3772	£1.84
AC188K	£0.32	BC143	£0.25	BC304	£0.44	BF168	£0.32	2N708	£0.12	3N3773	£2.53
AD140	£0.69	BC145	£0.53	BC327	£0.16	BF169	£0.32	2N707	£0.55	2N3818	£0.40
AD142	£0.98	BC147	£0.08	BC328	£0.17	BF180	£0.35	2N708	£0.18	2N3820	£0.40
AD143	£0.88	BC148	£0.08	BC337	£0.17	BF182	£0.35	2M1302	£0.17	2N3821	£0.89
AD149	£0.89	BC149	£0.08	BC338	£0.17	BF183	£0.35	2N1303	£0.21	2N3823	£0.89
AD181	£0.40	BC150	£0.23	BC440	£0.35	BF184	£0.55	2N1304	£0.21	2N3903	£0.12

74 SERIES TTL IC'S

7400	£0.10	7422	£0.18	7448	£0.84	7489	£1.86	74123	£0.48	74175	£0.71
7401	£0.13	7423	£0.24	7449	£0.13	7490	£0.37	74126	£0.80	74178	£0.87
7402	£0.13	7425	£0.22	7451	£0.13	7491	£0.74	74141	£0.83	74177	£0.87
7403	£0.13	7426	£0.22	7453	£0.13	7482	£0.40	74145	£0.83	74180	£1.73
7404	£0.13	7427	£0.28	7454	£0.13	7483	£0.35	74150	£0.78	74181	£0.87
7405	£0.13	7428	£0.20	7450	£0.13	7454	£0.88	74151	£0.55	74182	£0.81
7406	£0.13	7429	£0.30	7451	£0.13	7455	£0.88	74152	£0.55	74184	£0.81
7407	£0.26	7432	£0.25	7472	£0.23	7456	£0.58	74154	£0.94	74190	£0.78
7408	£0.15	7433	£0.35	7473	£0.29	74100	£0.88	74155	£0.58	74191	£0.71
7409	£0.15	7437	£0.24	7474	£0.29			74156	£0.58	74192	£0.69
7410	£0.13	7438	£0.24	7475	£0.33	74104	£0.45	74157	£0.58	74193	£0.87
7411	£0.20	7440	£0.14	7478	£0.29	74105	£0.44	74180	£0.87	74174	£0.71
7412	£0.17	7441	£0.58	7480	£0.51	74107	£0.28	74181	£0.71	74185	£0.88
7413	£0.28	7442	£0.48	7481	£0.98	74110	£0.41	74182	£0.71	74186	£1.21
7414	£0.58	7443	£0.81	7482	£0.78	74111	£0.67	74183	£0.71	74187	£1.21
7415	£0.28	7444	£0.81	7483	£0.87	74112	£0.92	74184	£0.78	74188	£2.13
7416	£0.28	7445	£0.75	7484	£1.01	74113	£1.38	74185	£0.78	74189	£2.13
7417	£0.28	7446	£0.89	7485	£0.78	74121	£0.28	74186	£0.90		
7418	£0.23	7447	£0.55	7486	£0.25	74122	£0.45	74174	£0.75		

CMOS IC'S

CD4000	£0.16	CD4012	£0.22	CD4021	£0.94	CD4030	£0.55	CD4045	£1.81	CD4070	£0.20
CD4001	£0.16	CD4013	£0.22	CD4022	£0.94	CD4031	£2.12	CD4046	£1.81	CD4071	£0.20
CD4002	£1.08	CD4014	£0.94	CD4023	£0.22	CD4035	£1.38	CD4047	£1.00	CD4072	£0.20
CD4006	£1.06	CD4016	£0.89	CD4024	£0.75	CD4037	£1.09	CD4049	£0.55	CD4081	£0.20
CD4007	£0.20	CD4017	£0.94	CD4025	£0.22	CD4040	£1.01	CD4050	£0.55	CD4082	£0.25
CD4008	£1.06	CD4018	£0.88	CD4026	£1.38	CD4041	£0.87	CD4054	£1.27	CD4510	£1.27
CD4009	£0.52	CD4019	£0.88	CD4027	£0.58	CD4042	£0.83	CD4055	£1.15	CD4511	£1.44
CD4010	£0.26	CD4020	£0.15	CD4028	£0.78	CD4043	£0.87	CD4056	£1.55	CD4518	£1.15
CD4011	£0.23	CD4014	£0.92	CD4029	£0.98	CD4044	£0.84	CD4089	£0.20	CD4518	£1.15

LINEAR IC'S

CA3011	£1.12	CA3090	£4.14	MC1312	£2.19	UA709	£0.29	748P	£0.40	TBA800	£0.92
CA3014	£1.85	CA3123	£2.19	MC1360	£1.18	72709	£0.53	SN76013N	£1.97	SN7810	£1.73
CA3020	£0.75	CA3130	£1.01	MC1362	£1.81	709P	£0.29	SN76023N	£1.97	SN78115	£2.10
CA3028	£0.98	CA3140	£0.81	MC1469	£3.39	UA710C	£0.48	SL1414A	£2.24	SN7880	£0.88
CA3028	£0.92	CA3085E	£0.95	MC1498	£1.94	72710	£0.35	TAA5508	£		

**SEND YOUR ORDERS TO DEPT. PE12, PO BOX 6, WARE, HERTS.
VISIT OUR SHOP AT: 3 BALDOCK ST, WARE, HERTS. Tel: 0920 3182, Telex 817861**

EXPERIMENTOR BREADBOARDS

FROM 

No soldering breadboards. Simply plug components in and out of letter number identified.

Nickel-silver contact holes. Start small and simply snap-lock boards together to build a breadboard of any size.

All EXP Breadboards have two bus-bars as an integral part of the board. If you need more than two buses, simply snap on 4 more bus-bars with the aid of an EXP 4B.

EXP 325 The ideal breadboard for 1 chip circuits. Accepts 8, 14, 16 and up to 22-pin IC's. **ONLY £1.84**
48mm (1.9")

EXP 350 270 contact points with two 20-point bus-bars. **ONLY £3.62**
91mm (3.6")

EXP 300 550 contacts with two 40-point bus-bars. **ONLY £6.61**
152mm (6.0")

EXP 650 For Micro-processors. **ONLY £4.14**
91mm (3.6")

EXP 4B More bus-bars. **ONLY £2.65**
152mm (6.0")

EXP 600 As EXP 300 but accepts 24 pin DIL and over. **ONLY £7.25**
152mm (6.0")

All EXP 300 Breadboards mix and match with 600 series.

ANTEX IRONS

1943 15 watt quality soldering iron with 3/32" bit **£4.88**

1947 Replacement element for 1943 **£2.18**

1944 Iron coated bit 3/32" for 1943 **£0.53**

1945 Iron coated bit 1/8" for 1943 **£0.53**

1946 Iron coated bit 3/16" for 1943 **£0.53**

1948 18 watt iron with iron coated bit **£4.59**

1952 Replacement element for 1948 **£2.18**

1949 Iron coated bit 3/32" for 1948 **£0.53**

1950 Iron coated bit 1/8" for 1948 **£0.53**

1951 Iron coated bit 3/16" for 1948 **£0.53**

1931 X25 25 watt iron, ceramic shaft and another shaft of stainless steel to ensure strength **£4.88**

1935 Replacement element for 1931 **£1.84**

1932 Iron coated bit 1/8" for 1931 **£0.57**

1933 Iron coated bit 2/16" for 1931 **£0.57**

1934 Iron coated bit 3/32" for 1931 **£0.57**

1953 SK1 soldering Kit - contains 15 watt soldering iron with 3/16" bit plus two spare bits, a reel of solder, heat-sink and a booklet 'How to Solder' **£6.38**

1939 ST3 iron stand made from high grade bakelite chrom plated steel spring, suit all models - includes accommodation for six bits and two sponges to keep the iron bits clean **£1.86**

1724 Model MLX as X25 iron but 12 volts **£5.29**

CASES AND BOXES

VERO plastic case box. These boxes consist of top and bottom sections which include fixings points for horizontal mounting PC boards/chassis plates, the two sections are held together by four screws which enter through the base and are concealed by plastic feet.

No.	Length	Width	Height	Price
170	140mm	40mm	205mm	£4.35
171	140mm	75mm	205mm	£4.85
172	140mm	110mm	205mm	£6.30

INSTRUMENT CASES in two sections vinyl covered top and sides, aluminium bottom, front and back.

No.	Length	Width	Height	Price
155	8in	5 1/2in	2in	£2.01
156	11in	6in	3in	£3.10
157	6in	4 1/2in	1 1/2in	£1.93
158	9in	5 1/2in	2 1/2in	£2.59

ALUMINIUM BOXES made from bright anodized construction each box complete with half inch deep lid and screws.

No.	Length	Width	Height	Price
159	5 1/2in	2 1/2in	1 1/2in	£0.98
160	4in	4in	1 1/2in	£0.98
161	4in	2 1/2in	1 1/2in	£0.98
162	5 1/2in	4in	1 1/2in	£1.10
163	4in	2 1/2in	2in	£0.98
164	3in	2in	1in	£0.67
165	7in	5in	2 1/2in	£1.54
166	8in	6in	3in	£1.98
167	6in	4in	2in	£1.32

SLOPE front aluminium boxes with black vinyl base and sides & aluminium back, top & front - strong construction easily accessible.

No.	Length	Width	Height	Price
169	2 1/2in	5 1/2in	2 1/2in	£8.45
168	2 1/2in	7 1/2in	4in	£8.21

AUDIO MODULES

AMPLIFIERS

AL10	3 watt Audio Amplifier Module 22-32v supply	£3.63
AL20	5 watt Audio Amplifier Module 22-32v supply	£4.73
AL30A	7-10 watt Audio Amplifier Module 22-32v supply	£5.51
AL60	15-25 watt Audio Amplifier Module 30-50v supply	£8.81
AL80	35 watt Audio Amplifier Module 40-60v supply	£10.87
AL120	50 watt Audio Amplifier Module 50-70v supply	£17.38
AL250	125 watt Audio Amplifier Module 50-80v supply	£25.91

STEREO PRE-AMPLIFIERS

PA12	Supply voltage 22-32v input sensitivity 300mv suit: AL10/AL20/AL30	£9.63
PA100	Mag P.U., Suit: AL60/AL80	£20.30
PA200	Supply voltage 35-70v inputs: Tape, Tuner, Mag P.U., Suit: AL80/AL120/AL250	£20.98

MONOPRE-AMPLIFIERS

MM100	Supply voltage 40-65v inputs: Mag. P.U., Tape Microphone Max. output 500mv	£14.29
MM100G	Supply voltage 40-65v inputs: 2 Guitars, Microphones Max. output 500mv	£14.29

POWER SUPPLIES

PS12	24v Supply suit 2 x AL10, 2 x AL20, 2 x AL30 & PA12/25/450	£1.90
SPM80	33v Stabilised supply - suit 2 x AL60, PA100 to 15 watts	£5.57
SPM120/45	45v Stabilised supply - suit 2 x AL60, PA100 to 25 watts	£7.34
SPM120/55	55v Stabilised supply - suit 2 x AL80, PA200	£7.34
SPM120/65	65v Stabilised supply - suit 2 x AL120, PA200, 1 x AL250, PA200	£7.34
SG30	15-0-15 Stabilised power supply for 2 x GE100MKII	£4.37

MISCELLANEOUS

MPA30	Stereo Magnetic Cartridge Pre-Amplifier-Input 3.5mv Output 100mv	£3.76
S.450	Stereo FM Tuner Supply Voltage 20-30v - Varicap tuned	£29.39
STEREO30	Complete 7 watt per Channel Stereo Amplifier Board - includes amps, pre-amp, power supply, front panel, knobs etc - requires 2050 Transformer	£24.25
8P124	5 watt 12v max. - Siren Alarm Module	£4.43
GE100MKII	10 channel mono-graphic equaliser complete with sliders and knobs	£26.45
VPS30	Variable regulated stabilised power supply 2-30v 0-2 amps	£8.74

TRANSFORMERS

No.	Rating	Price	P & P
2034	1.7 amp 35v suit SPM80	£6.21	£1.21
2035	2 amp 55v	£7.30	£1.47
2036	750mA 17v suit PS12	£3.68	
2040	1.5 amp 0.45v-55v suit SPM120/45, SPM120/55v	£5.98	£1.21
2041	2 amp 0-55v-65v suit SPM120/55, SPM120/65v	£7.82	£1.47
2050	1 amp 0-20v suit Stereo 30	£3.74	£0.75
1725	150mA 15-0-15v suit SG30	£2.04	

ACCESSORIES

139	Teak Cabinet suit Stereo 30, 320, 235 - 81mm	£9.72
140	Teak Cabinet suit STA15 425 x 290 x 95mm	£8.97
FP100	Front Panel for PA100 & PA200	£2.07
BP100	Back Panel for PA100 & PA200	£1.84
GE100FP	Front Panel for one GE100MKII	£2.05
2240	Kit of parts including Teak Cabinet, chassis sockets, knobs to build 15 watt stereo amplifier	£22.94

VEROBOARD

2201	2.5"x5", .1 copper	£0.71	2211	2.5"x3.75", .15 copper	£0.53
2202	2.5"x3.75", .1 copper	£0.81	2212	3.75"x1.7", .15 copper	£2.39
2203	2.5"x1.7", .1 copper	£2.14	2213	3.75"x5", .15 copper	£0.90
2206	3.75"x3.75", .1 copper	£0.71	2217	3.75"x1.7", .1 Plain	£1.79
2208	3.75"x1.7", .1 copper	£2.76	2218	3.75"x2.5", .1 Plain	£0.44
2207	4.75"x1.7", .1 copper	£3.61	2219	5"x3.75", .1 Plain	£0.68
2208	2.5"x1", .15 in pack	£0.85	2223	2.5"x5", .15 Plain	£0.37
2204	3.75"x5", .1 copper	£0.79	2225	5"x7.5", .15 Plain	£0.56
2210	2.5"x5", .15 copper	£0.64			

METAL FOIL CAPACITOR PAKS

16204 - Containing 50 metal foil capacitor like Mullard C280 series - Mixed values ranging from 01uf - 2.2uf. Complete with identification sheet **£1.38**

TRIACS

2 amp	T05 case	Price	10 amp	Price	
100	TR12A/100	£0.36	100	TR110A/100	£0.88
200	TR12A/200	£0.89	200	TR110A/200	£1.06
400	TR12A/400	£0.82	400	TR110A/400	£1.29

6 amp	10 amp	Price
100	TR16A/100	£0.59
200	TR16A/200	£0.70
400	TR16A/400	£0.88
	BR100	£0.23
	D32	£0.23

SILICON RECTIFIERS

200mA	IS920 50V	£0.07	3 Amp	IN5400 50V	£0.16
	IS921 100V	£0.08		IN5401 100V	£0.17
	IS922 150V	£0.09		IN5402 200V	£0.18
	IS923 200V	£0.10		IN5404 400V	£0.19
	IS924 300V	£0.11		IN5406 600V	£0.24
				IN5407 800V	£0.28
				IN5408 1000V	£0.34

1 Amp	IN4001 50V	£0.05	10 Amp	IS10/50 50V	£0.21
	IN4002 100V	£0.06		IS10/100 100V	£0.24
	IN4003 200V	£0.07		IS10/200 200V	£0.26
	IN4004 400V	£0.08		IS10/400 400V	£0.40
	IN4005 600V	£0.09		IS10/600 600V	£0.48
	IN4006 800V	£0.10		IS10/800 800V	£0.58
	IN4007 1000V	£0.11		IS10/1000 1000V	£0.69
				IS10/1200 1200V	£0.79

1.5 Amp	IS1015 50V	£0.10	30 Amp	IS30/50 50V	£0.64
	IS1020 100V	£0.11		IS30/100 100V	£0.79
	IS1021 200V	£0.12		IS30/200 200V	£1.06
	IS1023 400V	£0.14		IS30/400 400V	£1.43
	IS1025 600V	£0.16		IS30/600 600V	£2.02
	IS1027 800V	£0.18		IS30/800 800V	£2.23
	IS1029 1000V	£0.23		IS30/1000 1000V	£2.65
	IS1031 1200V	£0.28		IS30/1200 1200V	£3.31

60 Amp	IS70/50 50V	£0.86	IS70/400 400V	£2.01
	IS70/100 100V	£0.96	IS70/600 600V	£2.87
	IS70/200 200V	£1.38	IS70/1000 1000V	£3.45

THYRISTORS

600ma	TO 18 Case	7 amp	TO 48 Case
Volts No.	Price	Volts No.	Price
10 THY600/10	£0.17	50 THY7A/50	£0.55
20 THY600/20	£0.18	100 THY7A/100	£0.59
30 THY600/30	£0.23	200 THY7A/200	£0.66
50 THY600/50	£0.25	400 THY7A/400	£0.71
100 THY600/100	£0.29	600 THY7A/600	£0.90
200 THY600/200	£0.44	800 THY7A/800	£1.06
400 THY600/400	£0.51		

10 amp	TO 48 Case
Volts No.	Price
50 THY10A/50	£0.59
100 THY10A/100	£0.66
200 THY10A/200	£0.71
400 THY10A/400	£0.81
600 THY10A/600	£1.14
800 THY10A/800	£1.40

16 amp	TO 48 Case
Volts No.	Price
50 THY16A/50	£0.62
100 THY16A/100	£0.67
200 THY16A/200	£0.79
400 THY16A/400	£0.89
600 THY16A/600	£1.04
800 THY16A/800	£1.60

30 amp	TO 94 Case
Volts No.	Price
50 THY30A/50	£1.38
100 THY30A/100	£1.54
200 THY30A/200	£1.87
400 THY30A/400	£2.06
600 THY30A/600	£4.03

5 amp	TO 66 Case
Volts No.	Price
50 THY5A/50	£0.41
100 THY5A/100	£0.52
200 THY5A/200	£0.58
400 THY5A/400	£0.66
600 THY5A/600	£0.73
800 THY5A/800	£0.93

5 amp	TO 220 Case
Volts No.	Price

CHROMASONIC electronics

48 JUNCTION ROAD, ARCHWAY, LONDON N19 5RD
TELEPHONE 01-883 3705 01-883 2289

50 YDS FROM ARCHWAY STATION & 9 BUS ROUTES

YOUR SOUNDEST CONNECTION IN THE WORLD OF COMPONENTS AND COMPUTERS


PETS & SYSTEMS

8N 8K RAM £399
16N 16K RAM £499
32N 32K RAM £599
CASSETTE DECK £55

✓ 343K Twin Floppy Disk
£895



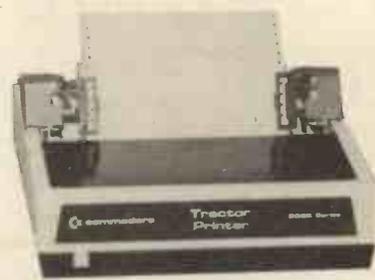NEW 32K with 80 col Screen **£825**
Twin Disk Drive 950K **£895**
All with new keyboard and green screen
Friction Feed Printer **£375** Tractor Feed Printer **£425**




COMPLETE 32K SYSTEM £1789

MEMORY EXPANSION KIT

Suitable for UK101, Super-board expansion using 2114's each board has 16K ram capacity kit contains:

- ★ On board power supply
- ★ 4K Eprom expansion
- ★ Fully buffered for easy expansion via 40 pin socket
- ★ 8K kit **£89.95**
- ★ 16K kit **£122.95**
- ★ Printed Circuit Board **£29.95**
- ★ 40 pin-40 pin header plug **£8.50**

NEW SHOP

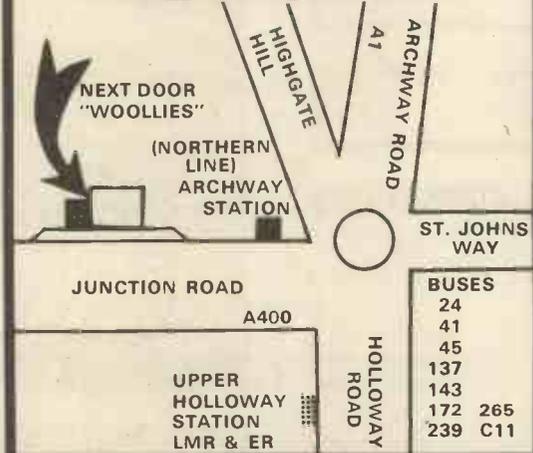

VIDEO GENIE



VIDEO GENIE
based on TRS80

Utilises Z80, 12K level II Basic, Integral Cassette Deck, UHF O/P, 16K RAM, all TRS80 features.

£289

CASES

Available for U.K. 101, Superboard Nascom, Appx. DIM. 17" x 15" 435 x 384 mm

PRICE £24.50

Post + Packing
£1.50

UK101 P.P.I.

Built & tested. Interfaces TX80 printer direct, can be programmed to operate relays, motors, various other peripherals. "Centronics compatible". Plugs into IC socket. LED binary display. Fully documented. **£29.95**

UK101


£179 IN KIT FORM
£229 READY BUILT & TESTED

£255 COMPLETE IN CASE (8x2114)


4K EXPANSION NOW ONLY £18.00

No extras required

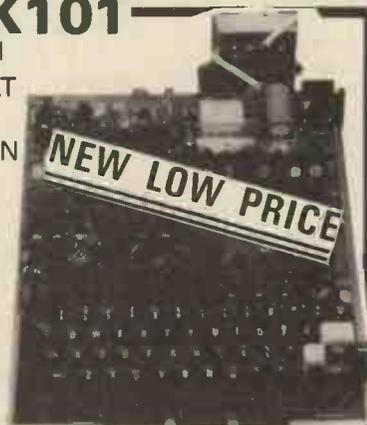- ★Free sampler tape
- ★Full Qwerty keyboard
- ★8K basic
- ★Ram expandable to 8K on board (4K inc.)
- ★Kansas City tape interface
- ★New monitor allows full editing & cursor control **£22.00**



PRINTERS

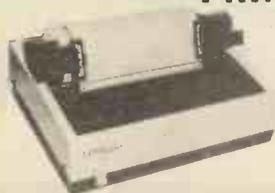

EPSON TX-80
£349

Dot-matrix printer with Pet graphics interface: Centronics parallel, options: PET, Apple and serial.



Please add VAT 15% to all prices. Postage on computers, printers and cassette decks charged at cost, all other items, P&P 30p. Place your order using your Access or Barclaycard (Min. tel order £5). Trade and export enquiries welcome, credit facilities arranged.



NEW SHOP & SHOWROOM NOW OPEN

TELEPHONE 01-883 3705 01-883 2289

UK101 SOUND

Sound generator and combined parallel in out port kit containing P.C.B., AY-3-8910, 6520 PIA, fully documented and demo tape.

£29.95

AY-3-8910 **£8.50**

UK101 SOFTWARE

	£ p
Space Invaders	6.50
Real Time Clock	5.00
Chequers	3.00
Othello	4.00
Game Pack I	5.00
Game Pack II	5.00
Game Pack III	5.00
Screen Monitor	4.00
Assembler Editor	14.90
10 x C12 Blank Tapes	4.00

MEMORY

D. RAMS	£ p
4027	2.75
4050 (350NS)	2.35
4060 (300NS)	2.39
4116	3.95

S. RAMS	
2102A	1.30
2102A2	1.69
2112A	2.75
2114/4045	2.75
4035	1.07
4044-5257	6.93
6810	3.50

BULK PURCHASE	
8x2114	18.00
8x4116	27.50
16x2114	34.00

EPROMS

2708	4.25
2716 (5v)	6.95
2532	29.95

ROM

2513 (UC)	5.95
-----------	------

CPU'S

Z80 2.5 Meg	7.95
Z80A 4 Meg	9.95
6502	6.95
6800	6.50
8080	4.75
9900	25.95

I.C. SOCKETS

	D.I.L.	W/W
8 pin	.09	.25
14 pin	.11	.35
16 pin	.12	.42
18 pin	.16	.50
20 pin	.20	.62
22 pin	.22	.65
24 pin	.24	.70
28 pin	.30	.80
36 pin	—	.99
40 pin	.40	1.10

SUPPORT CHIPS

Z80 CTC	5.95
Z80A CTC	6.95
Z80 PIO	5.95
Z80A PIO	6.95
6520	3.95
6522	6.85
6532	8.50
6821	4.25
6850	3.60
6852	4.35
8212	1.95
8216	1.95
8224	2.75
8228	3.75
8251	4.95
8253	9.75
8255	4.50
TM59901	13.16
TM59902	11.18
TM59904 (2465362)	4.21

BUFFERS

81LS95	1.25
81LS96	1.25
81LS97	1.25
81LS98	1.25
SN74365	.52
SN74366	.52
SN74367	.52
SN74368	.52
8T26	1.50
8T28	1.50
8T95	1.50
8T96	1.50
8T97	1.50
8T98	1.50

UARTS

AY-5-1013	3.95
AY-3-1015	4.75
MM5303	4.75
TMS6011	3.55

BAUD RATE GEN'S

MC14411	8.75
MM5307	8.75

**SEND S.A.E. FOR COMPLETE
PRICE LIST OR PHONE 01-883 3705**

All these advantages...


- Instant all-weather starting
- Smoother running
- Continual peak performance
- Longer battery & plug life
- Improved fuel consumption
- Improved acceleration/top speed
- Extended energy storage

..in kit form

SPARKRITE X5 is a high performance, top quality inductive discharge electronic ignition system designed for the electronics D.I.Y. world. It has been tried, tested and proven to be utterly reliable. Assembly only takes 1 1/2 hours and installation even less due to the patented 'clip on' easy fitting.

The superb technical design of the Sparkrite circuit eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current by 95% of the normal.

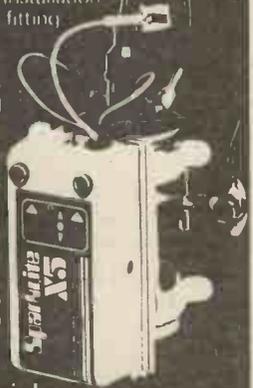There is also a unique extended dwell circuit which allows the coil a longer period of time to store its energy before discharging to the plugs. The unit includes built in static timing light systems function light and security changeover switch. Will work all rev counters.



**Fits all 12v negative-earth vehicles
with coil/distributor ignition up to 8 cylinders.**

THE KIT COMPRISES EVERYTHING NEEDED

Die pressed case. Ready drilled aluminium extruded base and heat sink, coil mounting clips and accessories. All kit components are guaranteed for a period of 2 years from date of purchase. Fully illustrated assembly and installation instructions are included.



Roger Clark the world famous rally driver says "Sparkrite electronic ignition systems are the best you can buy."

Sparkrite

HIGH PERFORMANCE
ELECTRONIC IGNITION

Electronics Design Associates, Dept. PE1179, 82 Bath St., Walsall, WS1 3DE

Electronics Design Associates, Dept. PE 12/80
82 Bath Street, Walsall, SW1 3DE. Phone: (0922) 614791

Name _____
Address _____

Phone your order with Access or Barclaycard

I enclose cheque PO's for

Inc. V.A.T. and P.P.

QUANTITY REQ'D

X5KIT £16.95

£

Cheque No.

ACCESS OR BARCLAY CARD No.

Send SAE if brochure only required

interface components

ALL PRICES ARE EXCLUSIVE OF VAT

TRANSISTORS		REGULATORS	
AC128 15p	BCY71 12p	7805 80p	74175 77p
AC187K 30p	BCY72 12p	7812 80p	4022 79p
AC188K 30p	BF179 25p	7815 80p	74180 84p
ADY17 90p	BF183 25p	7824 80p	4023 16p
AD149 55p	BF200 29p	7905 65p	74181 270p
AF127 35p	BF336 33p	7912 65p	74192 127p
ASZ17 120p	BFX30 32p	7915 65p	4026 169p
AU113 150p	BFX86 26p	7918 65p	74193 120p
BC107 7p	BFX88 22p	7924 65p	74194 99p
BC108 7p	BFY50 13p	LM309K 105p	74L500 11p
BC108A 7p	BFY51 13p	LM320T5 105p	74L501 11p
BC108C 7p	BFY64 28p	LM320T12 105p	74L502 12p
BC136 15p	BFY90 56p	LM320T15 105p	74L503 12p
BC140 28p	BSX19 80p	LM320T18 105p	74L504 12p
BC141 30p	BSY95A 16p	LM340T5 80p	74L510 19p
BC142 25p	BU204 149p	LM340T8 80p	74L511 20p
BC143 28p	BU208 150p	LM340T12 80p	74L520 18p
BC147 6p	OC29 89p	LM340T15 80p	74L530 24p
BC147B 6p	OC43 50p	LM340T18 80p	74L532 24p
BC149 7p	2N696 15p	LM340T21 80p	74L542 89p
BC149C 7p	2N930 20p	LM340T28 80p	74L551 24p
BC159 9p	2N1132 19p	LM340T38 80p	74L555 65p
BC160 35p	2N1304 40p	LM340T48 80p	74L574 39p
BC167A 10p	2N1613 12p	LM340T58 80p	74L575 46p
BC178 12p	2N1711 15p	LM340T68 80p	74L576 39p
BC179 12p	2N2217 20p	LM340T78 80p	74L585 99p
BC182 8p	2N2219A 20p	LM340T88 80p	74L590 46p
BC182L 9p	2N2221 18p	LM340T98 80p	74L593 79p
BC183 9p	2N2368 15p	LM340T108 80p	74L5114 49p
BC183L 9p	2N2369 14p	LM340T118 80p	74L5122 65p
BC184L 9p	2N2894A 20p	LM340T128 80p	74L5123 85p
BC186 20p	2N2904 15p	LM340T138 80p	74L5124 165p
BC212 9p	2N2904A 15p	LM340T148 80p	74L5132 89p
BC212L 9p	2N2905 15p	LM340T158 80p	74L5139 79p
BC213B 9p	2N2906 15p	LM340T168 80p	74L5151 89p
BC327 13p	2N2926Y 10p	LM340T178 80p	74L5155 91p
BC328 13p	2N2926O 10p	LM340T188 80p	74L5156 89p
BC337 16p	2N2926R 10p	LM340T198 80p	74L5159 91p
BC338 11p	2N3442 102p	LM340T208 80p	74L5165 89p
BC440 32p	2N3702 8p	LM340T218 80p	74L5167 69p
BC547 9p	2N3704 8p	LM340T228 80p	74L5168 195p
BC548 9p	2N3705 8p	LM340T238 80p	74L5174 140p
BC550 14p	2N3708 8p	LM340T248 80p	74L5175 99p
BC558 12p	2N3709K 8p	LM340T258 80p	74L5190 110p
BCY33 99p	2N3866 35p	LM340T268 80p	74L5192 115p
BCY34 99p	2N3906 10p	LM340T278 80p	74L5194 115p
BCY39 229p	2N4058 12p	LM340T288 80p	74L5195 115p
BCY58 16p	2N4427 60p	LM340T298 80p	74L5196 95p
BCY70 12p	Add VAT	LM340T308 80p	74L5197 125p

TTL

7400 9p	7401 9p	7402 9p	7403 9p	7404 10p	7405 14p	7406 45p	7407 45p	7408 17p	7410 12p	7412 17p	7413 25p	7414 45p	7416 25p	7417 25p	7420 14p	7427 28p	7430 14p	7432 22p	7438 26p	7442 70p	7447 95p	7450 15p	7451 15p	7470 40p	7472 25p	7474 32p	7475 50p	7480 50p	7482 70p	7486 30p	7491 80p	7492 55p	7493 55p	7494 90p	7495 63p	74100 120p	74107 30p	74121 40p	74122 52p	74123 90p	74145 85p	74154 137p	74157 60p	74161 92p
---------------	---------------	---------------	---------------	----------------	----------------	----------------	----------------	----------------	----------------	----------------	----------------	----------------	----------------	----------------	----------------	----------------	----------------	----------------	----------------	----------------	----------------	----------------	----------------	----------------	----------------	----------------	----------------	----------------	----------------	----------------	----------------	----------------	----------------	----------------	----------------	------------------	-----------------	-----------------	-----------------	-----------------	-----------------	------------------	-----------------	-----------------

CMOS

4000 14p	4001 14p	4002 14p	4006 86p	4007 16p	4008 79p	4009 36p	4010 36p	4011 19p	4012 16p	4014 79p	4015 73p	4016 42p	4017 79p	4018 79p	4019 45p	4020 89p	4021 99p
----------------	----------------	----------------	----------------	----------------	----------------	----------------	----------------	----------------	----------------	----------------	----------------	----------------	----------------	----------------	----------------	----------------	----------------

DIODES

AA119 10p	4A 400V 54p
BA154 9p	4A 600V 60p
BA156 9p	6A 400V 60p
IN4001 4p	6A 600V 66p
IN4002 4p	8A 400V 66p
IN4003 5p	8A 600V 72p
IN4005 5p	10A 400V 72p
IN4006 6p	10A 600V 84p
IN4007 6p	15A 400V 108p
IN4148 5p	15A 600V 126p
IS44 3p	

TRIACS

4A 400V 66p	4A 600V 75p	6A 400V 75p	6A 600V 90p	8A 400V 95p	10A 400V 95p	10A 600V 100p	15A 400V 120p	15A 600V 138p
-------------------	-------------------	-------------------	-------------------	-------------------	--------------------	---------------------	---------------------	---------------------

OPTO

Leds	125 Red 8p	125 Green 12p	125 Yellow 12p	2 Red 10p	2 Green 10p	Displays	704 110p	741 160p	747 160p	750 160p
------	------------------	---------------------	----------------------	-----------------	-------------------	----------	----------------	----------------	----------------	----------------

BRIDGE RECTIFIERS

50V	100V	200V	400V	600V
1.5A 34p	36p	38p	40p	54p
4A 40p	42p	44p	48p	64p
6A 48p	50p	54p	60p	74p
25A 130p	140p	150p	170p	220p

EPROMS

2708 650p	2716 1150p	2732 4850p
-----------------	------------------	------------------

CPU'S

Mk 3880 950p	Mk 3881 625p	Mk 3882 625p
--------------------	--------------------	--------------------

All advertised items available for immediate despatch while stocks last.

RETAIL SHOP AND MAIL ORDER WE STOCK A WIDE RANGE OF
 ★ Semiconductors ★ Resistors - Capacitors ★ Soldering Irons & tools ★ VERO products ★ OK Machine Tool Co. Products ★ Microcomputers & Peripherals including Nascom and Sharp. ★ Large range of Microcomputer books 35p P & P. VAT additional

INTERFACE COMPONENTS LIMITED, OAKFIELD CORNER, SYCAMORE ROAD, AMERSHAM, BUCKS HP6 6SU TELEPHONE: 02403 22307. TELEX: 837788
 Write, telephone or call. Access or Barclaycard accepted

- CLEF KITS -



P.E. MASTER RHYTHM

A User Programmable Rhythm generator for up to 24 selectable patterns on eight tracks. Three instrumentation settings select from twelve instruments, and sequence operation gives up to 16 Bar pattern groups.

COMPONENT KIT - £79

ELECTRONIC ROTOR
 Two speed organ rotor simulation plus a three phase chorus generator. Easily integrates with existing organ.

COMPONENT KIT - £89

KEYBOARDS (Square Front)
 49 NOTE C-C £23.80
 73 NOTE F-F £37.00
 88 NOTE A-C £45.00

All Keyboards are easily cut to provide your required length and compass. Quantity enquiries welcome.

BUILDING SERVICE
 We are specialists in Electronic Piano Manufacture and can build your Piano for you - see lists.

INFORMATION
 Please send S.A.E. quoting items of interest. Telephone BARCLAYCARD orders can be accepted, all prices include V.A.T., carriage & insurance.

SHOWROOM - 44a Bramhall Lane South.

EXPORT
 Enquiries welcome - in Australia please contact JAYCAR (Sydney).

Back up TELEPHONE advice is available from the Designer to supplement the clear instructions included with the above Kits.

High Quality Electronic Musical Instruments under the personal supervision of Specialist Designer A. J. BOOTHMAN.

JOANNA 72 & 88 PIANOS
 Six and 7½ Octave Electronic Pianos with unique Touch Sensitive Action as used in the P.E. JOANNA, which electronically simulates piano key inertia - a feature not available in any other design. Build this widely acclaimed professional instrument, for either domestic or Stage use, from our top quality Component Kits.

SIX OCTAVES - £207
7½ OCTAVES - £232

P.E. STRING ENSEMBLE
 The versatile String Synthesizer with a fantastic sound at an economic price. Split Keyboard facility with a range of impressive voices.

COMPONENT KIT - £169

P.A.'s - SPEAKERS - CABINETS
 Units can be supplied to add to the Piano Component Kits, including Domestic or Stage Cabinets and portable tubular legs.

CLEF PRODUCTS (ELECTRONICS) LIMITED

(Dept. PE) 16, Mayfield Road, Bramhall, Cheshire SK7 1JU. 061-439 3297



QUALITY REEL TO REEL & CASSETTE TAPE HEADS + MECHANISMS

POPULAR UNIVERSAL CASSETTE TAPE HEADS			
B12-01 Mono Playback.....	£1.89	C42RPH04 Stereo GLASS FERRITE R/P.....	£11.60
B12-02 Mono Record/Playback.....	£4.02	C42RPS18 Stereo TWIN GAP R/P.....	£25.21
B24-01 Stereo Playback.....	£3.30	E12-09 Mono/stereo erase.....	£ 1.85
B24-02 Stereo Record/Playback.....	£6.55	B22-02 Twin ¼ track R/P.....	£ 5.97
B24-07 Stereo R/P. (Dolby Sism).....	£7.87	C44RPH03 Quad ¼ track R/P.....	£13.17
C42RPH20 Stereo SENDUI R/P.....	£9.28	C44RPS01 Quad ¼ track combined R/P + Erase.....	£26.45
C42RPS01 Stereo combined R/P + Erase.....	£10.93	C22ES02 Twin half track erase.....	£ 4.72

SEND FOR OUR FULL CATALOGUE 50p including P. & P.

MONOLITH

THE MONOLITH ELECTRONICS CO. LTD. 5/7 CHURCH ST., CREWKERNE, SOMERSET, ENGLAND. (0450) 74321 ALL PRICES INCLUDE VAT



Top Priority for every constructor-HOME RADIO CATALOGUE

- About 2,000 items clearly listed.
- Profusely illustrated throughout.
- Large A-4 size pages.
- Bargain list, order form and 2 coupons each worth 25p if used as directed, all supplied free.

Price £1, plus 50p for post, packing and insurance.

Send cheque or P.O. for £1.50

HOME RADIO Components LTD
 Dept. PE, P.O. Box 92, 215 London Road, Mitcham, Surrey. 01-543 5659

GUARANTEED LOWEST PRICES – GUARANTEED QUALITY

We promise to BEAT any lower advertised price by an extra 2½% – Just send details and your remittance for the lower amount*

Casio and Seiko watches are water resistant and won't drown in the rain. They do not eat expensive batteries. The quality cases won't wear your cuffs away, nor will plating wear off in a few months. Unlike the usual plastic type, the mineral glass faces will not easily scratch or mark. The high quality modules have a failure rate of around 1% or less – not 25% or more. They are guaranteed accurate and functions do not interact. Spares and servicing are available after the guarantee expires from UK service departments.

THE ULTIMATE WATCHES

CASIO'S giant step forward in time.



Analogue Display



Digital Display

AA81

LCD ANALOGUE/DIGITAL Alarm Chronograph with countdown

Analogue. Independent hours and minutes with synchronous digital seconds. Dual time ability. Digital. Hours, minutes, seconds, day and date. Stopwatch. 1/100 second to 12 hours. Net, lap and 1st and 2nd place. Start/stop and 10 minute signals. Alarm. For 30 seconds with carousel display. Countdown Alarm. Normal and net times to 1 hour, with amazing "Star Burst" flashing display. Time signal. Half hourly and hourly chimes. Tone control. Lithium battery. Light. Water Resist case. 8.65mm thick. Mineral glass (£34.95).

ONLY £29.95
For around 40 functions.

12 MELODY ALARM CHRONOGRAPHS

Countdown alarm. Date memories.

Hours, minutes, seconds, am/pm, 12 or 24 hour. Day, date and month auto calendar. Alarm. 7 melodies, one for each day of the week. Hourly time signals. With "Big Ben" type tune. Date memory. Select either "Wedding March" or "Trinkled" to be played. Birthday and Christmas Memory. Countdown alarm. From 1 second to 1 hour. After zero, count continues positively. Stopwatch. 1/10 second to 1 hour. Net, lap etc. Picturesque moving display of notes played. Light Lithium. Glass. Water Resist. cases. M-12 resin, s/s trim. M-1200 all s/s 9.0mm, thick.



£24.95



£29.95

For around 40 functions.



£19.95



£32.50

For around 30 functions

A250. As above but with standard water resistant case. £T.B.A.

S220. As above but with dual time in lieu of alarms and chimes £25.00.

F300 Sports Chronograph (right). 8 digits, hours, minutes, seconds, date and day indicator. 1/100 second stopwatch; net, lap and 1st and 2nd place times, to 12 hours. Resin case. s/s trim. Water resist. glass. Light.

110QS-37B. Metal version £17.95.

F80E Alarm Chronograph (far right). 8 digit display of hours, minutes, seconds, am/pm and date. 24 hour alarm, hourly chimes. 1/10 second stopwatch to 12 hours; net, lap 1st and 2nd place. Resin case/strap. Water resist. Mineral glass. Nightlight.

83QS-41B. S/s jacket version £19.95.

100 METRE WATER RESISTANT

Alarm Chronographs with countdown.

Amazing 5 year lithium battery life. Hours, minutes, seconds, am/pm, day, date and month. 12 or 24 hour. Time is always visible regardless of display mode. Stopwatch. 1/100 second to 1 hour. Net, lap, 1st and 2nd. Start/top signal. 10 minute signal. Alarm. Sounds for 30 seconds. Countdowns Alarm. Normal and net times to 12 hours. Start/stop and 10 minute signals. Time signal. Half hourly and hourly chimes. W-100. All resin. W-150B. All s/s. W-150C (not illustrated) s/s case/resin strap £25.95.



£37.50

SEIKO ALARM CHRONOS

FROM £37.50.

DFT 048 (left). Alarm, countdown alarm, hourly chimes, stopwatch to 1/100 second; net, lap, 1st and 2nd. DFT 038 100 meter water resistant version

£49.95

DER 048 Solar powered (right). Weekly programmable alarm, 16 hour interval countdown alarm timer, hourly chimes. 1/100 second stopwatch.

£69.95



£52.50

OTHER CASIO WATCHES. Remember we will BEAT lower prices by 2½%.

8 digit basic watches. F7C £8.95. 111QS-34B £14.95.

Chronographs. 95QS-36B £19.95. 56QS-38B Digital/analogue £14.95.

Calculator/chronographs. C80 £24.95. C801 £29.95.

Alarm chronos. 81QS-35B £29.95. 81QS-35B all s/s £29.95. 83QS-41B Gold plated £29.95.

79QS-39B Calendar £29.95. 79CS-51B Calendar £39.95.

LADIES MODELS with stopwatch or dual time.

87QGL-13B Gold plated £24.95. 87QL-13B chrome £16.95.

Other ladies models from £10.95 to £34.95. Details on request.

*Providing the advertiser has stocks and we still make a small profit.

Send 25p for our illustrated catalogue of Casio and Seiko products.

Price includes VAT and P&P. Send your company order, cheque, P.O. or phone your ACCESS or BARCLAYCARD number to:

TEMPUS

Dept. PE, FREEPOST, 164-167 East Road, Cambridge CB1 1DB. Tel: 0223 312866

JOIN THE KEYBOARD REVOLUTION!

With the amazing new CASIOTONE 201.

A remarkable new concept in electronic keyboard instruments using a totally new technology. Pitch, timbre and harmonics of 29 instruments have been measured, digitalised and stored in electronic chip memory for faithful reproduction.

A 4-sound memory function allows switching between any 4 pre-selected instruments.

This polyphonic instrument can play full chords of up to 8 notes on its 29 white and 20 black keys spanning 4 octaves, Vibrato and tone switches. Foot volume and sustain pedal options. Echo jacks. 3x33x9½ inches. Weight 15lbs. Black or woodgrain finish. AC only.



ONLY £245 (r.r.p. £285)



CASIOTONE M-10

Four instruments on the move!

Polyphonic playing of piano, organ, violin and flute. 19 white and 13 black keys span 2½ octaves. Vibrato switch. 2x164x5½ inches. Weight 3.5lb. Integral speakers. O/p jack. Mains/battery.

ONLY £69 (r.r.p. £79)

THE SPACE INVADERS ARE BACK!


This time right in your pocket. An action-packed speed game that will give you hours of skilful entertainment and chair-grabbing excitement. Never another dull spare moment. Also an 11-note melody calculator, pre-programmed "When The Saints Go Marching In". Fully memory, %. Auto power off facility.

MG-880 (left)
1½x2½x4½"

£10.95 (£12.95)

MG-770 (right)
Kiss touch keys
5/32x3¼x2½"

(£14.95) **£12.95**

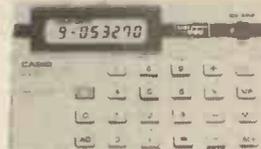

12 PRE-PROGRAMMED MELODIES

Clock, calendar, 11-note melody maker, calculator, square roots, %, Alarm 1; 7 tunes, one for each day, Alarm 2; a fixed tune. Hourly chimes. Date memories: 4 anniversary tunes. MQ-1200 (below). Desk or bedside. Built-in speaker. Volume control. Nightlight. Powered by three AA batteries. 1-9/16x6x2½ inches.



£19.95 (£22.95)

ML-90 (right)
Kiss keys. Stopwatch.
7/32x2½x4½"

(£22.95)

£19.95



Other Casio calculators, P.O.A. Remember, we will BEAT lower prices by 2½%*

DUO DISPLAY Analogue/digital watches from £57.50.

KEELMOOR Quality..

Keelmoor Ltd is a company which has been established for a long time – we supply the products you have often bought from other companies. Our precision watches and electrical goods are renowned for their superb quality and reliability.

We differ from other companies in that we import direct world-wide – that difference is passed on to you at unbeatable prices. You receive the goods faster and we provide a service and no catch guarantee of which we are justly proud.

We employ experts world-wide whose job it is to seek out products of the highest quality at the lowest possible prices. Illustrated here is just a tiny selection of our comprehensive range. Just compare these items with those seen elsewhere – we are confident the prices will amaze you. You can save ££££'s.

GENTS 5 FUNCTION LCD

A



This is the foundation of our range and is ideal for the man requiring the basic functions of hours, minutes and seconds, with month and date. A backlight is included and the stainless steel strap provided is fully adjusted to suit any size of wrist. Guaranteed for one year, this watch represents fantastic value at only

£4.95p

ILLUSTRATED BELOW IS THE LADIES 5 FUNCTION LCD. This watch has the same time and auto calendar functions as the basic gents model described above, together with backlight and adjustable strap to suit the daintiest of wrists. It's compact, pleasing appearance makes it a very practical day watch and it is also often used for boys and girls. Available in black or white face.

These are just a few of our fantastic offers remember. A free colour catalogue is posted with every order. Or just send large S.A.E. and we'll send you one.

B



£5.95p

C



GENTS LCD ALARM WATCH

This model represents fantastic, incredible value for money. The 6 digit display continuously shows hours, minutes and seconds, or may be changed at will to hours, minutes and date. Its effective alarm is extremely useful and may be set to any time within a 24 hr. period. In addition, there is an alarm indicator, 4 year calendar and snooze repeater.

£8.95p

FULLY GUARANTEED

We must emphasize all these items are fully guaranteed for one year. All electronic goods come complete with demonstration batteries which cannot be guaranteed. New batteries are available for only 60p.

BARCLAYCARD AND ACCESS CARD WELCOME. SEE COUPON.

HERE IS THE AMAZING 12/24 HOUR ALARM/CHRONOGRAPH

D



Along with the usual time and date displays, this multi-functional timepiece has a 24 hour alarm and a second stopwatch. The time may be set to operate in 12 or 24 hour mode and the date can be in English or American format. The day of the week is continuously indicated and the stopwatch display may, on command, be frozen to show split/laptime while the stopwatch continues to run. Stopwatch operation does not effect normal time keeping. £12.95 only for this model. Also available with solar energy panel to conserve energy during daylight hours for £14.95

FROM
£12.95p

From Watches to Clocks, from Calculators to Radios, from Binoculars to Tool Kits – KEELMOOR is the name for the right quality at the right price. Your personal catalogue will tell you more – free with every order.

E LADIES QUARTZ LCD DRESS WATCH

This attractive ladies model with the standard 5 functions of hours, minutes, seconds, month and date has literally sold in tens of thousands. Available in gold or silver colours with 'sugar cube' finish. Please state first and second choice of square, round or oval design.

£8.95p

THE ULTIMATE GENTS LCD CALCULATOR/ALARM WATCH

If you want a watch from the top end of the market this is the one for you. Full calculator functions plus memory and percentage are combined with time and alarm functions to make this item an outstanding buy. Manufactured in Japan at the same factory that produces models for probably the most famous name in the watch business, this device represents sheer quality at an unbelievable price. Comes complete with backlight and button operating tool carried in the strap clasp. We advise you to order quickly whilst stocks last.

£39.95p

F



at Keener Prices

FREE
With every order.
Big colourful
Keelmoor catalogue
featuring hundreds of
products at bargain
prices.

We don't think you'll find items of this quality anywhere else at the price we offer. Order now, Christmas is round the corner and this is the way to make gift buying easier – and cheaper too.

WE ARE PROUD TO INTRODUCE THE AMAZING
MELODY ALARM CHRONOGRAPH



**ACTUALLY
PLAYS
THE YELLOW
ROSE OF TEXAS**
BUT AS YOU CAN SEE
FROM THE DETAILS BELOW
THIS CHRONOGRAPH IS NO
MERE NOVELTY

Today's technology has produced this fine watch which incorporates a musical alarm which plays a complete verse of 'The Yellow Rose of Texas'. Other functions included are as for model number 1 with stop watch.

G
£14.95p

NEW TO OUR RANGE, WE COMBINE PRECISION
AND STYLE IN THIS—THE SUPER SLIM GENTS
5 FUNCTION CHRONOGRAPH



JUST TO GIVE YOU
AN IDEA OF THE
ULTRA SLIMNESS OF
THESE WATCHES WE
HAVE ILLUSTRATED
A SIDE VIEW OF THE
SUPERSLIM DIGITAL.
BELOW, WE HAVE
ELABORATED ON
SOME OF THE
TECHNICALITIES:—

These watches need no special functions to make them stand out in a crowd—their slimness serves that purpose. If you've been put off digital quartz watches in the past because you require an ultra-slim design, now is the time to change. Is equipped with standard 5 functions and backlight.

£9.95p

Keelmoor Ltd, 78 Castle Street, Melbourne, Derbyshire, DE7 1DY.

Every order
dispatched by
return, and is
sent by
recorded
delivery. That
is **Keelmoor's
Promise To
You.**

THE KEELMOOR PROMISE

Keelmoor have a tremendous reputation to uphold, both in the retail and wholesale trades and so, with every product sold, we automatically give the Keelmoor Promise. This includes:—

- **NO RISK GUARANTEE:** Try any of these items for 15 days and if you are not completely satisfied with the quality and value simply return it for a complete refund.
- **ONE YEAR'S FULL GUARANTEE** on all products
- **BACK UP SERVICE** second to none

MAINS DIGITAL ALARM CLOCK



A very practically sized mains operated digital alarm clock – this item is extremely well finished and looks equally at home by the bedside or in the living room. With snooze/repeater alarm you could not even buy the components to build your own for this price. Available at the amazingly low price of only

£8.95p

AND FINALLY, WHAT MUST BE THE ULTIMATE IN SQUEEZING A QUART INTO A HALF PINT POT! THE INCREDIBLE MINIATURE LCD TRAVEL/ALARM CLOCK



As you can see from the photograph above this device is tiny and yet it continuously displays hours and minutes with auto calendar and night light. Invaluable for the busy traveller or simply for use in the modern home, it comes complete with its own travelling case and can easily be carried in top pocket or the smallest of handbags. It has even got a stand for upright position on table, shelf or sleeping compartment. An unusual gift to yourself or others at only £10.95. **J**

15 DAY TRIAL COUPON.

To Keelmoor Ltd, 78 Castle Street, Melbourne, Derby DE7 1DY
Please send me the items indicated in the boxes below. I understand that if I am not completely satisfied, I may return the goods undamaged within 15 days and my money will be refunded in full.

A	B	C	D	E	F	G	H	I	J	Just indicate with a tick, item required, if more than one required tick plus number – i.e. 2's
										TOTAL AMOUNT = £

NAME Mrs, Miss, Ms, Mr
ADDRESS _____

POSTCODE _____

I enclose a cheque (P) to **KEELMOOR LTD**
(Or charge my Access or BARCLAYCARD (tick as applicable))

No _____

TOTAL — £ _____ Please add 50p per item P&P.
The advertisements to watch for quality precision at the right price.
All goods dispatched by return.

PE 6

3 CHANNEL SOUND/LIGHT CHASER

LB31000SLC **£29.90**



A high performance sound to light system which automatically switches to a chase when the music ceases. Super sensitive with an anti interference circuit, the unit will operate from practically any amp and control up to 1,000W/channel, 5Hz to 70K. Controls: bass/mid/treble/master sensitivity/chase speed.

STEREO DISCO MIXER/PREAMP

LBPA3
M - Magnetic
C - Ceramic



£30.70

Magnetic or ceramic deck versions - please state

NEW ADVANCED MODEL AVAILABLE

All the requirements of a stereo disco preamp on one board, left and right deck mixers/controls/mic mixer/tones/mic. auto fade over decks/and P.F.L. The unit can be used with either LB100/150/250. LBPA3PS - Regulated supply - £10.50. Full set of pots - £8.63 Sliders - £11.21

3 CHANNEL SOUND/LIGHT

LB31000SL



£21.40

All the advantages of the SLC without chase. Controls: bass/mid/treble/master sensitivity.

LPBA2 **£17.20**

A four channel mixer and tone stage for mics, guitars, etc. Can be used with any LB amps. Set of pots £2.74, sliders £5.23.

LBPA1 **£19.50**

A stereo hi-fi preamp and tone stage for mag. p.u./tape/tuner, etc. Set of pots £3.27, sliders £4.49.

2/4/8 CHANNEL CHASER

LB81000LC



£26.50

An all logic chase system for use with up to 8 channels at 1,000 watts each. Facilities include footswitch trigger and module cascading (16, 24, 32 channel, etc.), chase speed and re-cycle delay.

3-WAY ACTIVE CROSSOVER


LBACO1 **£17.90**



Bass/mid/treble active crossover with stage booster! Available with crossover points of 200 or 300Hz, and 2K or 3KHz (please specify) LBPSU1 supply for LBACO1.

4 CHANNEL SEQUENCER

LB41000LS

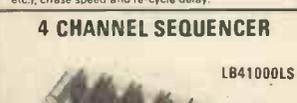

£17.50

A 4 channel sequence generator for banks of lamps up to 1,000W per channel. Two speed controls, cross effect to provide settings between seconds and rapid burst.

POWER AMPLIFIERS


Tough dealing power amps for use in sound systems. Open/short circuit protection and fused. Heavy gauge heatsinks and rugged o/p devices fall operate down to 4 ohms!

25W R.M.S.	100W R.M.S.	150W R.M.S.	250W R.M.S.
20Hz to 60K 0.07% THD	5Hz to 25K 0.1% THD	5Hz to 25K 0.1% THD	5Hz to 25K 0.1% THD
980B S/N LB25	1100B S/N LB100	1100B S/N LB150	1100B S/N LB250
£11.20	£18.20	£26.50	£39.50

Note all models are available with either 500mV or 775mV sensitivity. Please state when ordering.

1 AND 3 CHANNEL DIMMERS

LB31000LD

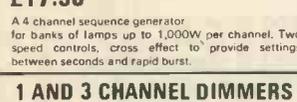


LB31000LD **£14.70**

Single channel version LB11000LD **£6.70**

Power dimmer units for theatre/stage applications up to 1,000W per channel, with on board suppressing. The unit is also available without rotary pots for use with sliders - LB31000LD (no pots) **£13.50** Sliders 75p each.

LBRLD1 **£5.70**

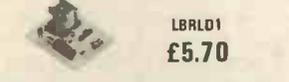

A de-thump unit for use with any LB power amps.

ROPE LIGHTS/DRIVER

LB41000LC-S **£22.70**



24 feet ropes Red/Yellow Blue/Green

ROPE LIGHTS £41.40

A four channel chaser up to 1,000W per channel, with a sound trigger facility. The music input signal modulates the speed of the chase giving an excellent sound/light effect. The unit will control up to 10 ropes with chase speed and trigger level control

POWER SUPPLIES

LB25PS	LB100PS	LB150PS	LB250PS
£11.20	£14.70	£18.00	£24.50
P/P £1.20	P/P £1.40	P/P £1.40	P/P £1.70

PIEZO HORNS £5.75

P/P 50p

CELESTION LOUDSPEAKERS (8 ohms)

G12-45 (12 inch 65W)	G12-100 (12 inch 100W)	G12-125 (12 inch 125W)
£20.70	£26.45	£46.00
P/P £1.70	P/P £1.70	P/P £2.00

NEW - MINI MODULES - NEW

Ingeniously designed mini pre-amplifier 'building blocks' for use in music and P.A. applications. You choose the type and number of units you require for your particular system and mount each module via its control direct onto your panel.

LBMM1 Pre-amp for mics, guitars etc.
LBMM2 Mixer for up to 6 LBMM1/2/3/4/5
LBMM3 Bass/boost/cut for either LBMM1/2/3/4/5
LBMM4 Mid-boost/cut for either LBMM1/2/3/4/5
LBMM5 Treble boost/cut for either LBMM1/2/3/4/5
LBPSU1 ± 15V supply for up to 8 modules
LBPSU ± 15V regulated for up to 50 modules

MM1 £4.50; MM2 £5.20; MM3 £5.70; MM4 £5.70; MM5 £5.70; PSU1 £6.20; RPSU £14.50. Discount on MM1/2/3/4/5 10 to 24 - 20%, 25+ - 30%

L & B ELECTRONIC MODULES

PROFESSIONAL ENGINEERING BY PROFESSIONALS

45 Wortley Road, West Croydon, Surrey CRO 3EB. Tel. 01-689 4138

Each module is manufactured from the highest quality components, fully tested, supplied with a connection and circuit diagram and guaranteed for twelve months.

All prices shown are VAT inclusive. Please include 50p post/packing except where individually stated. To mail order send cheque/P.O./registered cash/Barclaycard or Access number, C.O.D. service £1 extra. For the new Autumn catalogue send 50p. (Full spec. shown.)

MULLARD CAPACITORS

Special purchase of factory clearance capacitors enables us to offer: C280 Polyesters (Liquorice Allsorts) at £2 for 100 mixed. And Miniature Electrolytics at £1.50 for 100 mixed. Pack of each only £3.

These consist of spillages, floor sweepings, cosmetic imperfections etc. As we have no time to sort them they are magnificent value for the constructor.

HUMIDISTATS

Don't Let Your Environment Dehydrate You!

Buy our Honeywell Humidity Controller. Membrane actuated, very sensitive, 1/2" shaft, 250V, 3.75A. Contacts ideal for greenhouses, centrally heated homes, offices etc. Build your own humidifiers or alarms. Fraction of original cost 90p ea. 3 for £2.

20 ASSORTED ZENER DIODES

1 watt and 400mW. £1.50

100 MIXED DIODES

Includes: Zener, power, bridge, germanium, silicon etc. All full spec. £4.95

2" LED's

0-2" LEDs with 2 piece clips.

ULTRASONIC TRANSDUCERS

Transmitter and receiver 40 kHz 14 mm dia £3-25 pair.

MINIATURE REED SWITCHES

We are the cheapest! 12 for £1.00 100 for £4.20

G.E.C. UHF TRANSISTOR TV TUNERS

Rotary type with slow motion drive, leads and aerial socket £1.50 3 for £3.50 "for G.E.C. "2010" series etc."

DE LUXE FIBRE GLASS PRINTED CIRCUIT ETCHING KITS

Includes 150 sq. ins. copper clad 1/8" G board, 1 lb ferric chloride 1 dazo etch resist pen, Abrasive cleaner, Etch tray plus instructions. Special Price £4.95

1 lb FE. C1. To mil. spec. £1.25
5 lb FE. C1. To mil. spec. £5.00

150 sq. in. Single sided board £2.00
150 sq. in. Double sided board £3.00

MINIATURE MAINS TRANSFORMERS

Top quality. Split bobbin construction will give 4.5V-0-4.5V at 250 MA. 1 1/2" x 1 1/2" x 1 1/2". all sorts of uses. ONLY 90p, 3 for £2.20.

2,200 μ F 40V Radial, 1 1/2" x 2" 60p. 3 for £1.50.
1,000 μ F 100V Radial, 1 1/2" x 2" ONLY 70p. 3 for £1.50.

BD181 78 Watt T.O.3 Power Transistors. 50p ea. 3 for £1.44F1 Alternator Diodes. Ideal for making Battery Chargers etc. 4 make 50 amp bridge. 50p ea. -Ve or +Ve case 2 of ea. £1.50.

TRANSISTOR PACKS

100. Full spec. new and marked. Includes BC148, BC184L, MED412, BF274, BC154 etc. etc. £4.95

200 as above and includes AC128, 2N3055, 8FV50, 60131, BF200 etc. £9.95

Buy bulk and save money, these packs are worth at least double.

P/B SWITCH BANKS

These cost a fortune! Were made for various music centres. Includes independent and interdependent latching types multi pole etc etc. Can be modified. Can't be repeated. 3 Banks for £1

Knobs for P/B Switches. Fit 3 1/2" mm sq. shaft. 10 for £1. Chrome or Spun Aluminium Finish.

BULK BARGAINS. STOCK UP FOR SUMMER

300 mixed 1/2 & 3/4 watt resistors £1.50
150 mixed 1 & 2 watt resistors £1.50
300 mixed capacitors, modern, most types £3.75
100 mixed ceramic and plate caps £1.20
400 mixed film resistors £2.95
100 mixed polystyrene caps £2.20
25 pots and presets £1.50
25 presets, skeleton etc. £1.20
20 VDRs and thermistors £1.20
100 Hi-wattage resistors wirewound at £2.75
100 electrolytics, nice values £2.20
300 printed circuit resistors £1
300 printed circuit components £1.50

100K MINIATURE THUMBWHEEL SLIDER POTS

Very neat, can be banked side by side. Ideal for v. cap tuning, graphic equalisers etc. 10 for £1

MINIATURE LEVEL/BATT. METERS 200 μ A

F.S.D. as fitted to many cassette recorders 60p

50p P & P on all above items. Cheque or P.O. with order to:

SENTINEL SUPPLY, DEPT. P.E.
149A BROOKMILL RD., DEPTFORD, LONDON, SE8

A new book for the home electronics constructor

Microprocessors for Hobbyists

Ray Coles

- * An introduction to microprocessors based on two popular series in *Practical Electronics*
- * Covers the architecture of microprocessor chips and systems, programming memory, and input-output components
- * Describes home computers together with a comparison of different models and the appropriate software
- * Includes a comprehensive glossary of terms to explain the 'buzz-words' of the micro-processor scene

1980 96 pages £2.95 US \$7.50

Newnes Technical Books
Borough Green, Sevenoaks, Kent TN15 8PH

TRANSFORMERS + VAT 15%

30 VOLT RANGE (Split Sec)
Pri 220/240 Voltages available 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30V or 12V-0-12V or 15V-0-15V.

Ref.	Amps	Price	P&P
112	.5 1 15V	2.90	0.90
79	1 2 0	3.93	1.10
3	2 4 N	6.35	1.10
20	3 6 L	7.39	1.31
21	4 8 Y	8.79	1.31
51	5 10	10.86	1.52
117	6 12	12.29	1.67
88	8 16	16.45	1.89
88	10 20	18.89	1.89
90	12 24	21.09	2.24
91	15 30	24.18	2.39
92	20 40	32.40	O.A.

CONTINUOUS RATINGS

All voltages given are at full load

AUTO TRANSFORMERS

Voltages available 105, 115, 190, 200, 210, 220, 230, 240. Voltage for step up or step down.

Ref.	VA	£	P & P
113*	15	2.73	0.81
64	80	4.41	1.10
4	150	5.89	1.10
67	350	10.08	1.31
84	1000	20.64	2.39
93	1500	25.61	O.A.
95	2000	38.31	O.A.
73	3000	65.13	O.A.
80S	4000	84.85	O.A.
57S	5000	98.45	O.A.

50 VOLT RANGE (Split Sec)
Pri 220/240V Voltage available 5, 7, 8, 10, 13, 15, 17, 20, 33, 40 or 240V-0-20V or 25V-0-25V.

Ref.	Amps	Price	P&P
102	.5 1 25V	3.75	0.90
103	1 2 0	4.57	1.10
104	2 4 N	7.98	1.31
105	3 6 L	9.42	1.52
106	4 8 Y	12.82	1.73
107	6 12	16.37	1.89
118	8 16	22.29	2.39
119	10 20	27.48	O.A.
109	12 24	32.88	O.A.

MAINS ISOLATORS (SCREENED)
Pri 0-120; 0-100-120V (120, 220, 240V) Sec 60-55-0-55, 60 twice, to give 55, 60, 110, 115, 120, 125, 175, 180, 220, 225, 230, 235, 240.

Ref.	VA	Price	P & P
*07	20	4.54	0.91
149	60	7.37	1.10
150	100	8.38	1.31
151	200	12.28	1.31
152	250	14.81	1.73
153	350	18.07	2.15
154	500	22.52	2.47
155	750	32.03	O.A.
156	1000	40.92	O.A.
157	1500	58.52	O.A.
158	2000	87.99	O.A.
159	3000	95.33	O.A.

*Pri 0-220-240V Sec 115 or 240V. State sec. volts required.

CASED AUTO TRANSFORMERS
240V cable in 115V USA flat pin outlet.

VA	Price	P & P	Ref
20	6.85	1.03	56W
75	8.50	1.31	64W
150	11.00	1.31	4W
250	13.39	1.67	69W
500	20.13	1.89	67W
1000	30.67	2.65	84W
2000	48.97	O.A.	95W

12 OR 24V OR 12-0-12V
Pri 220-240 volts

Ref	12V	24V	Price	P&P
111	0.5	0.25	2.42	0.52
213	1.0	0.5	2.90	0.90
71	2	1	3.86	0.90
18	4	2	4.48	1.10
85	5	2.5	6.18	1.10
70	6	3	6.99	1.10
108	8	4	8.18	1.31
72	10	5	8.93	1.31
116	12	6	9.89	1.52
17	16	8	11.79	1.80
115	20	10	15.37	2.39
187	30	15	19.72	2.39
226	60	30	40.41	O.A.

Bridge Rectifier

100V	25A	£2.80
200V	4A	.52
200V	4A	.75
400V	4A	.98
400V	6A	£1.44
500V	PM7A6 12A	£3.75

20,000 ohm/V Multimeter
mirror. Scale ranges AC/DC to 1000V DC current to 250mA. Resistance to 3 M Ohms. 5" x 3 1/2" x 1 1/2" £14.36. P&P £1.00. VAT 15%

60 VOLT RANGE (Split Sec)
Pri 220/240V Voltages available 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 or 24-0-24V or 30V-0-30V.

Ref.	Amps	Price	P&P
124	.5 1 30V	4.27	1.10
124	1 2 0	6.50	1.10
124	2 4 N	8.36	1.31
124	3 6 L	12.10	1.31
124	4 8 Y	17.42	1.89
124	5 10	19.87	2.12
124	6 12	27.92	O.A.
124	8 16	27.92	O.A.
124	10 20	32.51	O.A.
124	12 24	37.47	O.A.

CONNECTORS
Thorn, Cannon, Plessey, Bendix, Greenpar now available.

Soldering Iron - 25W to BS spec. £1.75 + 30p P&P + VAT.

100W Solder Gun bulb for spot on vision and joints £7.50 + P&P 70p + VAT.

De-solder Pump - Spring loaded with quick action button release for one handed working. Large £5.10 + P&P 35p + VAT. Small £4.75 + P&P 30p + VAT. Replacement tips Small 65p + VAT. Large 86p + VAT.

AVO TEST METERS

Ref.	Price	Antex
8 MK5	£106.40	Soldering Irons
71	£43.10	15W.
73	£58.60	25W
MM5 minor	£36.90	£4.58.
Wee Megger 500V (WN4/3)	£87.00	Safety Stand
TT169 in circuit transistor tester	£45.00	£1.75
EM272 315KΩ per volt	£97.10	P&P
DA116 digital	£108.90	52p each.
BM7 Megger	£58.60	

All Avos Meggers and accessories available P&P £1.32 15% VAT

NEW RANGE TRANSFORMERS
0-36-48 twice to give 36-0-36 48-0-48V, 60V, 72V, 84V, 96V.

Amps	Ref	Price	P&P
0.5	430	4.88	0.76
1	431	8.12	0.99
2	432	13.35	1.31
3	433	16.17	1.40
4	434	20.65	2.11
5	435	29.30	2.47
6	436	36.69	O.A.
8	437	40.03	O.A.

TRANSFORMERS END OF LINE OFFERS

30-Isolator 240V:240V 200VA £4.54 £1.04

M616 - 240V: Screen 1) 13-0-13 1A. 2) 12V 150ma £1.50 60p

M489 - 240V: 1400V @ 150ma 6.3V @ 4A £5.50 £1.04

M708 - 8K to 3Ω matching transformer 5W 90p 40p

M679 - 120V x 2: 36V 1-6A £3.00 78p

M865 - 100V Line to 4Ω 10 watts £1.90 60p

M1020 - 0-240V 12-0-12V x 50ma 75p 41p

M1126 - 120/240V: 9-0-9V x 1A £1.75 11p

ABS Plastic Boxes: inset brass nuts, slots to take P.C. cards (boards) flush fitting lid.

PB1 - 80mm x 82 x 40 80p
 PB2 - 100mm x 75 x 40 90p
 PB3 - 120mm x 100 x 45 £1.04
 PB4 - 215mm x 130 x 85 £2.68

P&P 33p + VAT

Plus In Save Batteries - Plug into 13 amp socket 3-6-7.5, 9-12V @ 100ma to 400ma £4.60 + P&P 60p + VAT.

Metal Oxide Resistors 1/2 W 5% £1.00 per 100. A bargain. Use instead of Carbon Film! In 100's only. 30p P&P + VAT.

390Ω/470Ω/510Ω/560Ω/820Ω/1K/1K1/1K2
 1K6/1K8/2K/2K4/3K/16K/20K/22K/24K/47K/82K/
 100K/110K/120K/130K/180K/220K/270K/300K

U4315 Budget Meter
20Kv/Ω Ranges to 1000V, 2.5A AC/DC 500K Res. In steel case £15.85 P&P £1.32

SPECIAL OFFER Multimeter (20KΩ/V with combined audio/L.F. test oscillator at 1KHz, and 465 KHz AC/DC to 1000 volts. DC current to 500 MA resistance to 1M size 160x97x40mm £8.50. P&P £1.00. VAT 15%

Split Bobbin Type - 0-12-15-20-24-30V.
 Ref 009 - 1 Amp £2.98, P & P £1.10.
 Ref 010 - 2 Amp £4.65, P & P £1.10 open frame fixing. Other types available.

"Educational" Meters (Moving coil)
 0-10A, 0-2A, 0-15V, 0-30V.
 Free standing large scale easily read meters with top screw terminals for quick connections.

Size 75 x 78mm scale £4.50 P&P 66p + VAT

PANEL METERS

43mm 43mm	82mm 78mm		
0-50μA	6.20	0-50μA	6.70
0-500μA	5.95	0-500μA	6.70
0-1mA	5.95	0-1mA	6.70
0-30V	5.95	0-30V	6.70

VU ind. Panel 48mm x 45mm or 40mm x 40mm 250μA f.s.d. SV041 Edge VU centre zero f.s.d £2.80
 Carriage 76p. VAT 15%

Send 20p stamp for catalogue
 Prices correct 1/8/80

15V Range 0-36-48 twice to give 36-0-36 48-0-48V, 60V, 72V, 84V, 96V.

171 500mA	2-30	0.52
172 1A	3-26	0.92
173 2A	3-95	0.90
174 3A	4-13	0.99
175 4A	6-30	1.10

Burglar Alarm - Ultrasonic 20ft range no installation costs. Key operated; built in siren (external can be added). Looks like a speaker. £98.00 £2.00 P&P + VAT.

SCREENED MINIATURES

Ref	mA	Volts	£	P&P
238	200	3-0.3	2.83	0.63
212	1A, 1A	0-6-0.6	3.14	0.90
13	100	9-0.9	2.35	0.44
235	330, 330	0-9-0.9	2.19	0.44
207	500, 500	0-9-0.9-9	3.05	0.85
208	1A, 1A	0-8-0.8-9	3.88	0.90
236	200, 200	0-15-0.15	2.19	0.44
214	300, 300	0-20-0.20	3.08	0.90
221	700(DC)	20-12-0-12-20	3.75	0.90
206	1A, 1A	0-15-20-0-15-27	25.09	1.10
203	500, 500	0-15-27-0-15-20-24	39.11	1.40
204	1A, 1A	0-15-27-0-15-27-26	64.11	1.10
239	50	12-0-12	2.88	0.43
234	500	6	2.19	0.44

Barrie Electronics Ltd.
 3, THE MINORIES, LONDON EC3N 1BJ
 TELEPHONE: 01-488 3316/7/8
 NEAREST TUBE STATIONS: A1 GATGATE & LIVERPOOL ST


Guess who builds this great



Logic Probe...YOU! for only £11.92

With this easy-to-build Logic Probe Kit from CSC and just a few hours of easy assembly—thanks to our very descriptive step-by-step manual—you have a full performance logic probe.

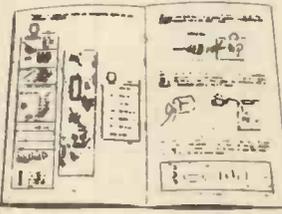With it, the logic level in a digital circuit is indicated by light from the Hi or Lo LED; pulses as narrow as 300 nanoseconds are stretched into blinks of the Pulse LED, triggered from either leading edge. You'll be able to probe deeper into logic with the LPK-1, one of the better tools from CSC.



Complete, easy-to-follow instructions help make this a one-night project.

See us on STAND F1 at LONDON BREADBOARD EXHIBITION

CONTINENTAL SPECIALTIES CORPORATION



C.S.C. (UK) Limited, Dept. 5Z
 Unit 1, Shire Hill Industrial Estate,
 Saffron Walden, Essex. CB11 3AQ.
 Telephone: Saffron Walden (0799) 21682
 Telex: 817477.

CONTINENTAL SPECIALTIES CORPORATION, DEPT. 5Z
 Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex.

Name _____
 Address _____
 Inc P&P and 15% VAT I enclose cheque/
LPK-1 £14.86 PO for £ _____ FREE Catalogue
 Phone your order with Access, Barclaycard tick box
 or American Express Card No. _____ Expiry date _____

24 HOUR CLOCK/APPLIANCE TIMER KIT



Switches any appliance up to 1KW on and off at preset times once per day. Kit contains: AY-5-1220 IC, 0.5" LED display, mains supply, display drivers, switches, LEDs, triac, PCBs & full instructions.

CT1000K Basic Kit £14.90
CT1000KB with white box (56/131x71mm) £17.40
Ready Built £22.50

MINI KITS

These Kits form useful subsystems which may be incorporated into larger designs or used alone. Kits include PCB, short instructions and all components.

MK1 TEMPERATURE CONTROLLER/THERMOSTAT
Uses LM3911 IC to sense temperature (80°C max) and triac to switch heater. 1KW £4.00

MK2 SOLID STATE RELAY
Ideal for switching motors, lights, heaters, etc. from logic. Opto-isolated with zero voltage switching. Supplied without triac. Select the required triac from our range. £2.60

MK3 BAR/DOT DISPLAY
Displays an analogue voltage on a linear 10-element LED display as a bar or single dot. Ideal for thermometers, level indicators etc. May be stacked to obtain 20 to 100 element displays. Requires 5-20V supply. £4.75

MK4 PROPORTIONAL TEMPERATURE CONTROLLER
Based on the TDA1024 Zero voltage switch, this kit may be wired to form a "burst fire" power controller or a "proportional temperature" controller enabling the temperature of an enclosure to be maintained to within 0.5°C. 3KW £5.55

MK5 MAINS TIMER
Based on the ZN1034E Timer IC this kit will switch a mains load on (or off) for a preset time from 20 minutes to 35 hours. Longer or shorter periods may be realised by minor component changes. Maximum load 1KW £4.50

TRIACS



400V Plastic Case (Texas)
3A 49p
8A 85p 16A 95p
12A 85p 25A 190p
6A with trigger 80p
8A isolated tab 65p
10A 18p

SPECIAL OFFER OVM THERMOMETER KIT

Based on the ICL 7106. This kit contains a PCB, resistors, presets, capacitors, diodes, IC and 0.5" liquid crystal display. Components are also included to enable the basic DVM kit to be modified to a Digital Thermometer using a single diode as the sensor. Requires a 3mA 9V supply (PP3 battery), closing date 31.12.80. Price £17.50

XMAS STOCKING FILLERS

(closing date 31.12.80)
6 x 555 ICs £1.00
15 x 8-pin sockets £1.00
12 x 14-pin sockets £1.00
10 x 16-pin sockets £1.00
15 x 8C182 £1.00
15 x 8C212 £1.00
2 x TIC2280 triacs £1.00
12 x Red LEDs 0.2"/0.1" £1.00
10 x Green LEDs 0.2"/0.1" £1.00
10 x Yellow LEDs 0.2"/0.1" £1.00
2 x LM380 2W audio amp. £1.50
1 x LM2917 + socket £1.50

INTEGRATED CIRCUITS

555 Timer 21p
741 Op. Amp. 19p
AY-5-1224 Clock £2.60
AY-5-1230/2 Clock/Timer £4.50
AY-3-1270 Thermometer £8.20
ICL7106 DVM (LCD drive) £7.00
LM377 Dual 2W Amp. £1.45
LM3795 Dual 6W Amp. £3.50
LM380 2W Audio Amp. 80p
LM382 Dual low noise Preamp £1.00
LM386 250mW low voltage Amp. 75p
LM1820 Fluid Level Detector £1.50
LM2907 f-v Converter (8 pin) £1.40
LM2917 f-v Converter (14 pin) £1.60
LM3909 LED Flasher/Oscillator 60p
LM3911 Thermometer £1.20
LM3914 Dot/Bar Driver £2.10
MM74C911 4 digit display controller £6.50
MM74C915 7 segment-BCD converter 95p
MM74C926 4 digit counter with 7 seg. o/p £4.50
S568B Touchdimmer £2.50
S9263 Touchswitch 16-way £2.50
SN76477 Complex Sound Generator £2.52
TBAB00 SW Audio Amp. 65p
TBA810AS 7W Audio Amp. £1.20
TDA1024 Zero Voltage Switch £1.20
TDA2020 20W Audio Amp. £2.85
ZN1034E Timer £1.80
All ICs supplied with data sheets.
Data Sheets only, 10p each device.

AND NOW A DIMMER THAT MAKES TOUCH DIMMERS OBSOLETE

Two years ago TK Electronics launched a touchdimmer kit, the TD300K, which made knob controlled dimmers obsolete. This was such a great success that many magazines and more retailers soon produced similar designs. SO THAT OTHERS MAY FOLLOW, TK have designed a touch dimmer kit with an infra red Remote Control, enabling you to switch and control the brightness of your lights from the comfort of your armchair etc. (as well as manually by touching the frontplate or by using the TDE/K extension kit).



We have designed the light dimmer unit to fit a standard wall box, the transmitter to fit your hand and the price to fit your pocket.

As with all our kits, these units come complete with all components, including RFI suppression, frontplate, a neon to help you find the switch in the dark and a neat box for the transmitter. The plastic frontplate has no metal parts to touch, ensuring complete safety and enabling the plate to be covered with a decorative finish to blend with your room decor.



In two years' time everyone will be selling remote control dimmers but you can have your TDRK300K kit NOW for only £14.30 for the dimmer unit and £4.20 for the transmitter. For the more athletic of you, the TD300K is still available at £6.50 and the TDE/K at £2.00.

DON'T FORGET to add 40p P&P and 15% VAT to your total purchase.

REMOTE CONTROL COMPONENTS

LD271 IR Emitting Diode 36p
SFH205 Photodiode Detector 95p
SL480 IC Pulse Amp. £1.70
SL490 32 command encoder/transmitter £2.40
ML922 10 channel receiver + 3 analogue outputs £4.20
ML926 16 channel receiver 4 momentary binary o/p £1.40
ML928 16 channel receiver 4 latched binary o/p £1.40
ML929 16 channel receiver 4 latched binary o/p £1.40
Data sheets per device 10p
These ICs can be used with infra red, ultrasonic or radio links, depending on range, cost and speed of operation.

RC500K KIT

If you do not require a sophisticated multi-channel remote control, we have developed a simple single-channel on/off infra red transmitter and receiver kit. The transmitter unit comes complete with a hand held box and requires a PP3 (9V) battery. The receiver includes a triac capable of switching up to 500W at 240V a.c. and comprises a pre-amplifier bistable latch and a mains power supply, making the unit completely self-contained. The small size of the receiver enables the unit to be "built into" all kinds of equipment from lamps to tape recorders. Range: approximately 20 ft. £12.50.

ALL COMPONENTS ARE BRAND NEW AND TO SPECIFICATION. ADD VAT AT CURRENT RATE TO ABOVE PRICES. 40p P&P MAIL ORDER - CALLERS WELCOME BY APPOINTMENT



TK Electronics
(P.E.), 11 Boston Road, London
W7 3SJ. TEL. 01-579 9794



FLADAR TRANSFORMERS

PRIMARY 0-240V 50Hz

SEND FOR OUR TRANSFORMER CATALOGUE PRICE £1.00 WHICH INCLUDES A 50p VOUCHER OFF YOUR FIRST PURCHASE.

Type	Voltage	Current	£	p/p	Type	Voltage	Current	£	p/p
06FE06	6+6	0.5A EACH	1.99	60p	08FE60	15-0-15	0.4A	1.95	60p
12FE06	6+6	1.6A EACH	2.66	75p	08FE60	15-0-9	1A	2.35	60p
20FE06	6+6	1.6A EACH	3.36	75p	08FE60	15-0-15	0.5A	2.35	60p
50FE06	6+6	3A EACH	4.02	90p	12FE40	9-0-9	1.5A	2.60	75p
60FE06	6+6	4A EACH	5.03	125p	12FE50	12-0-12	1A	2.60	75p
06FE09	9+9	0.3A EACH	1.99	60p	12FE60	15-0-15	0.8A	2.60	75p
08FE09	9+9	0.5A EACH	2.40	60p	20FE50	9-0-9	2A	3.30	75p
12FE09	9+9	0.7A EACH	2.66	75p	20FE60	12-0-12	1.6A	3.30	75p
20FE09	9+9	1A EACH	3.36	75p	20FE70	15-0-15	1.2A	3.30	75p
50FE09	9+9	2.5A EACH	4.02	90p	20FE80	20-0-20	1A	3.30	75p
60FE09	9+9	3A EACH	5.03	125p	20FE100	30-0-30	0.6A	3.30	75p
06FE12	12+12	0.2A EACH	1.99	60p	50FE50	9-0-9	5A	4.00	90p
08FE12	12+12	0.3A EACH	2.40	60p	50FE70	15-0-15	3A	4.00	90p
20FE12	12+12	0.8A EACH	3.36	75p	50FE80	20-0-20	2A	4.00	90p
50FE12	12+12	1.8A EACH	4.02	90p	50FE110	30-0-30	1.4A	4.00	90p
60FE12	12+12	2.5A EACH	5.03	125p	60FE70	15-0-15	4A	5.00	125p
80FE12	12+12	3A EACH	6.20	125p	60FE80	20-0-20	3A	5.00	125p
06FE15	15+15	0.2A EACH	1.99	60p	60FE100	28-0-28	2.2A	5.00	125p
08FE15	15+15	0.25A EACH	2.40	60p	60FE110	30-0-30	3A	5.00	125p
12FE15	15+15	0.4A EACH	2.66	75p	80FE40	12-0-12	6A	6-15	125p
20FE15	15+15	0.6A EACH	3.36	75p	80FE50	15-0-15	5A	6-15	125p
50FE15	15+15	1.5A EACH	4.02	90p	80FE60	20-0-20	4A	6-15	125p
60FE15	15+15	2A EACH	5.03	125p	80FE80	28-0-28	2.5A	6-15	125p
80FE15	15+15	3A EACH	6.20	125p	80FE70	24-0-24	3A	6-15	125p
06FE20	20+20	0.15A EACH	1.99	60p	80FE90	30-0-30	2.3A	6-15	125p
12FE20	20+20	0.25A EACH	2.66	75p	90FE50	15-0-15	5A	6-30	150p
20FE20	20+20	0.5A EACH	3.36	75p	90FE60	20-0-20	3A	6-30	150p
50FE20	20+20	1.2A EACH	4.02	90p	90FE90	30-0-30	3A	6-30	150p
60FE20	20+20	1.5A EACH	5.03	125p	100FE50	15-0-15	4A	6-60	150p
80FE20	20+20	2A EACH	6.20	125p	100FE26	26-0-26	3.5A	6-60	150p
06FE30	6-0-6	1.5A	1.95	60p	100FE28	28-0-28	3A	6-60	150p
08FE40	9-0-9	0.5A	1.95	60p	100FE30	30-0-30	3A	6-60	150p
08FE50	12-0-12	0.5A	1.95	60p	100FE36	36-0-36	3A	6-60	150p
150FE15	15-0-15	6A	8.20	160p	150FE15	15-0-15	6A	8.20	160p
150FE26	26-0-26	5A	8.20	160p	150FE26	26-0-26	5A	8.20	160p
150FE30	30-0-30	4A	8.20	160p	150FE30	30-0-30	4A	8.20	160p
150FE36	36-0-36	4A	8.20	160p	150FE36	36-0-36	4A	8.20	160p
150FE42	42-0-42	3A	8.20	160p	150FE42	42-0-42	3A	8.20	160p
250FE28	28-0-28	8A	9.02	200p	250FE28	28-0-28	8A	9.02	200p
250FE30	30-0-30	7A	9.02	200p	250FE30	30-0-30	7A	9.02	200p
250FE42	42-0-42	5A	9.02	200p	250FE42	42-0-42	5A	9.02	200p

FLADAR ELECTRIC
SOUTHVIEW DRIVE
P O BOX 19
WELSH CLIFF ON SEA
ESSEX O/02 613314


TRADE ENQUIRIES
WELCOME

PAYMENT TERMS:
C.W.O. Cheques,
Postal Orders
All Prices include 15% V.A.T.

OHIO SCIENTIFIC SUPERBOARD II

NEW GUARD BAND MODELS WITH FULL 32 x 32 DISPLAY

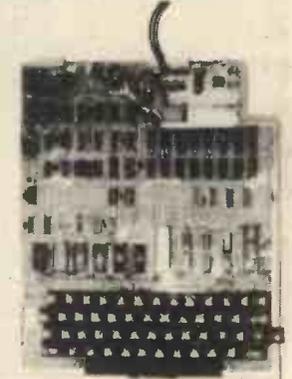50HZ BLACK AND WHITE SUPERBOARD II £159 + 15% VAT POST FREE
50HZ COLOURBOARD II £225 + 15% VAT.



THE UNIQUE SPECIAL OFFER YOU CANNOT RESIST

★ If bought with superboard or colour-board these items are at the reduced prices shown first. Also sold separately at the bracketed prices. Add 15% VAT. Modulator and power supply kit £8 (£25). 4k extra ram £20 (£24). Display expansion kit approx 30 lines x 54 characters £15 (£20). Case £23 (£26). Colour conversion board fully assembled £65 (£65). Cassette recorder £14 (£16). Extended memory £20 (£20). Assembler/Editor £25 (£25). 610 expansion board £160 (£160). Minifloppy with psu and 2 copies DOS £275 (£275).

SHARP COMPUTERS
Please add 15% VAT. MZ80K £438. MZ801/0 £96. MZ80P3 £515. MZ80FD £772. PC1211 £94. CE121 £13.

SUPER PRINT 800MST

The ideal impact matrix printer for Superboard, UK101, pet, apple, trs80, 80 lines/minute. 5 print densities of 72, 80, 96, 120 or 132 chr/line. Tractor and friction feed for up to 9 1/2" tractor paper. Graphics with user definable set in ram. RS-232 20ma. IEEE488 and centronics I/O. SPECIAL OFFER:- Supplied with free word processor program and interface components £359 + 15% VAT.

SINCLAIR PRODUCTS
ZX80 kit p.o.a. ZX80 assembled p.o.a. SC110 Oscilloscope £144.95. PFM200 £21.95. Microvision TV £89. PDM35 £34.23. DM235 £55.55. DM350 £76.70. DM450 £102.17. Enterprise prog calculator £19.95. TG105 £87. TF200 £150.

COMPUTER GAMES
Chess challenger 7 £79. Sensory chess challenger 8 £119. Atari video-computer £107. Cartridges £14.85 (except space invaders £27.80, chess £43.95 and backgammon £33.95).

SWANLEY ELECTRONICS

Dept. PE, 32 Goldsall Rd., Swanley, Kent BR8 8EZ.

Mail order only. Please add 35p postage. Prices include VAT unless stated. Lists 27p post free. Overseas customers deduct 13%. Official credit orders welcome.

IN EASY REACH OF ALL THE MAJOR NORTHERN ROUTES, (M1, M62, M61, M18, A1, A38 ETC.). NO PARKING PROBLEMS AS OUR MODERN SHOWROOM IS ADJACENT TO THE MAIN MULTI-STOREY CAR PARK. PHONE US, AND WE WILL DIRECT YOU PERSONALLY TO OUR DOOR!

AURA SOUNDS* WE'VE ALREADY BROUGHT YOU *



HELIOS

THE MODEL USED BY
KLAUS WUNDERLICH



COSMOS

REAL WERSI SOUND
AT A BUDGET PRICE



SATURN

THE NEW PROFESSIONAL
TWIN WERSIVOICE MODEL



ORION

SOUND COMPUTER[®]
HOME MODEL



CLASSICA

CLASSICAL CHURCH
MODEL

CENTRE OF THE NORTH

17, UPPER CHARTER ARCADE, METROPOLITAN CENTRE

BARNESLEY, SOUTH YORKSHIRE

TEL: 0226-5248

(CLOSED THURSDAYS)



COME AND
LET ALEX GOVIER
WERSI
DEMONSTRATOR SHOW
YOU HOW AND WHY
THE PROFESSIONALS
PLAY WERSI

AND WE
CAN SHOW YOU
THE INCREDIBLE

GALAXY TOO!

LET OUR TECHNICAL STAFF SHOW YOU HOW, WITH THE BENEFIT OF OUR UNIQUE TECHNICAL BACK UP SERVICE, EVEN A NEWCOMER TO ELECTRONICS CAN BUILD HIS OWN FAMOUS-SOUND WERSI ORGAN AT AN ENORMOUS SAVING ON FACTORY PRICES.

PLEASE SEND ME THE FULL WERSI INFORMATION PACKAGE, FOR WHICH I ENCLOSE £1.

NAME (BLOCK CAPITALS)

ADDRESS

PE12. PLEASE SEND TO PURLEY ADDRESS

HEAR WERSI IN THE SOUTH AT AURA SOUNDS LTD PURLEY

14-15 ROYAL OAK SHOPPING CENTRE, PURLEY, SURREY.
TEL: 01-668-9733 (CLOSED MONDAYS)



SIMPLY AHEAD
and staying there

The range grows bigger... better...

New Profile Amplifiers - Two New Series

MOSFET


CHOOSE AN I.L.P. MOSFET POWER AMP when it is advantageous to have a faster slew rate, lower distortion at higher frequencies, enhanced thermal stability, the ability to work with complex loads without difficulty and complete absence of cross-over distortion. I.L.P.'s exclusive encapsulation technique within fully adequate heatsinks has been taken a stage further with specially developed, computer-verified 'New Profile' extrusions. These ensure optimum operating efficiency from our new MOSFETS, and are easier to mount. Connections are via five pins on the underside. I.L.P. MOSFETS ARE IDENTICAL IN PERFORMANCE TO THE COSTLIEST AMPLIFIERS IN THIS EXCITING NEW CATEGORY BUT ARE ONLY A FRACTION OF PRICES CHARGED ELSEWHERE.

Model	Output Power RMS	Distortion Typical at 1KHz	Slew Rate	Rise Time	Signal/Noise Ratio DIN AUDIO	Price & VAT
MOS120	60W into 4-8Ω	0.005%	20V/μs	3μs	100dB	£25.88 + £3.88
MOS200	120W into 4-8Ω	0.005%	20V/μs	3μs	100dB	£33.46 + £5.02

BIPOLAR

CHOOSE AN I.L.P. BIPOLAR POWER AMP where power and price are first consideration while maintaining optimum performance with hi-fi quality and wide choice of models. From domestic hi-fi to disco and P. A., for instrument amplification, there is an I.L.P. Bipolar to fill the bill, and as with our new Mosfets, we have encapsulated Bipolars within our New Profile extrusions with their computer-verified thermal efficiency and improved mounting shoulders. Connections are simple, via five pins on the underside and with our newest pre-amps and power supply units, it becomes easier than ever to have a system layout housed the way you want it.

Model	Output Power RMS	Distortion Typical at 1KHz	Slew Rate	Rise Time	Signal/Noise Ratio DIN AUDIO	Price & VAT
HY30	15W into 4-8Ω	0.015%	15V/μs	5μs	100dB	£6.34 + 95p
HY60	30W into 4-8Ω	0.015%	15V/μs	5μs	100dB	£7.24 + £1.09
HY120	60W into 4-8Ω	0.01%	15V/μs	5μs	100dB	£15.20 + £2.28
HY200	120W into 4-8Ω	0.01%	15V/μs	5μs	100dB	£18.44 + £2.77
HY400	240W into 4Ω	0.01%	15V/μs	5μs	100dB	£27.68 + £4.15

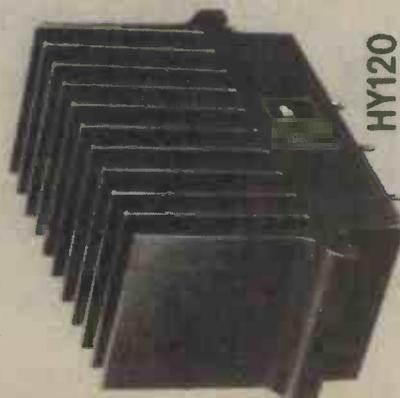


HY120




HY60

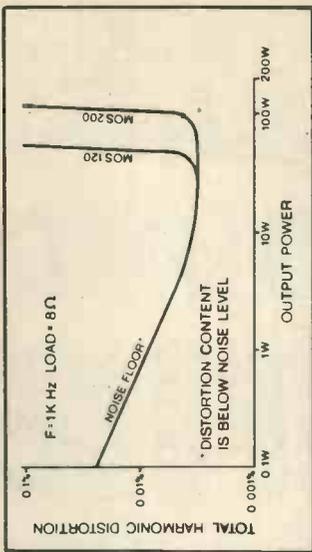
I.L.P. POWER AMPS ARE ENCAPSULATED FOR THERMAL STABILITY AND LONGER LIFE



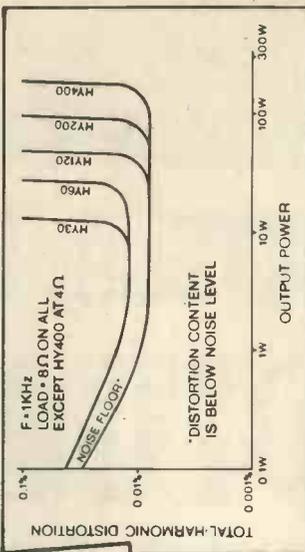Load impedance both models 4Ω-∞ Input sensitivity both models 100KΩ
4Ω-∞ Input sensitivity both models 15Hz-100KHz-3dB
Frequency response all models 15Hz-50KHz-3dB



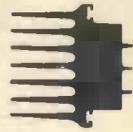Load impedance all models 4Ω-∞ Input impedance all models 100KΩ
Input sensitivity all models 500mV Frequency response all models 15Hz-50KHz-3dB



THE NEW PROFILE EXTRUSIONS
The introduction of standard heatsink extrusion for all I.L.P. power amplifiers achieves many advantages: - Research shows they provide optimum thermal dissipation and stability. Slotted shoulders allow easy mounting; standardisation enables us to keep our prices competitive. Surfaces are matt black, anodised for lower thermal conductivity. Extrusions vary in size according to module number.

NEW PRE-AMPS

HY6 (mono) and HY66 (stereo) are new to I.L.P.'s range of advanced audio modules. Their improved characteristics and styling ensure their being compatible with all I.L.P. power-amps both MOSFET and BIPOLAR, giving you chance to get the best possible reproduction from your equipment. HY6 and HY66 pre-amps are protected against short circuit and wrong polarity. Full assembly instructions are provided. Mounting boards are available as below.

Sizes - HY6 - 45 x 20 x 40 mm. HY66 - 90 x 20 x 40 mm. **Active Tone Control circuits provide ± 12 dB cut and boost.** **Inputs Sensitivity** - Mag. PU. -3mV; Mic - selectable 1-12mV; All others 100mV. **Tape O/P** - 100mV. **Main O/P** - 500mV. **Frequency response** - D.C. to 100KHz - 3dB.

HY6 mono £5.60 + 84p VAT Connectors included
 HY66 stereo £10.60 + £1.59 VAT Connectors included
 B6 Mounting Board for one HY6 78p + 12p VAT
 B66 Mounting Board for one HY66 99p + 15p VAT

NEW POWER SUPPLY UNITS

Of the eleven power supply units which comprise our current range, nine have toroidal transformers made in our own factory. Thus these I.L.P. power supply units are space-saving, more efficient and their better overall design helps enormously when assembly building. All models in the range are compatible with all I.L.P. amps and pre-amps with types to match whatever I.L.P. power amps you choose.

- PSU30 ± 15 V at 100mA to drive up to 12 x HY6 or 6 x HY66 £4.50 + 0.68p VAT
- PSU36 for use with 1 or 2 HY30's £8.10 + £1.22 VAT
- PSU60 for use with 1 or 2 HY60's £9.75 + £1.46 VAT
- PSU65 for use with 1 HY120 £9.75 + £1.46 VAT
- PSU70 for use with 1 or 2 HY120's £13.61 + £2.04 VAT
- PSU90 for use with 1 or 2 MOS120 £13.61 + £2.04 VAT
- PSU95 for use with 1 HY200 £14.75 + £2.21 VAT
- PSU180 for use with 1 HY400 or 2 HY200 £23.02 + £3.45 VAT
- PSU185 for use with 1 or 2 MOS200 £24.20 + £3.63 VAT

★ Freepost facility

When ordering or writing about I.L.P. products, you do not need to stamp the envelope. Mark it FREEPOST plus the code shown in the address below. We pay the postage for you.

★ TO ORDER


Send cheque or money order payable to I.L.P. Electronics Ltd and crossed. Or pay by ACCESS or BARCLAYCARD. Cash payments must be in registered envelope; if C.O.D. payment is wanted, please add £1.00 to TOTAL value of order.

ELECTRONICS LTD.

FREEPOST 2 Graham Bell House, Roper Close, Canterbury, Kent CT2 7EP.
 Telephone (0227) 54778 [Technical (0227) 64723] Telex 965780

Available also from MARSHALLS, WATFORD ELECTRONICS and certain other selected retailers

COMPATIBLE WITH ALL I.L.P. MODULES

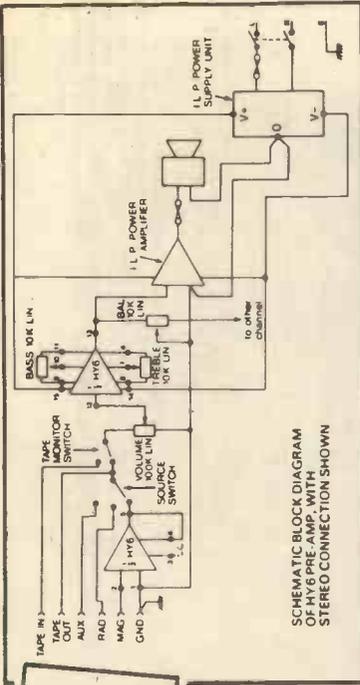

SCHEMATIC BLOCK DIAGRAM OF HY6 PRE-AMP, WITH STEREO CONNECTION SHOWN

- DISTORTION TYPICALLY 0.005 %
- S/N RATIO - 90dB (Mag. P.U. - 68 dB)
- 38 dB overload margin on Mag. P.U.
- LATEST DESIGN HIGH QUALITY CONNECTORS
- ONLY POTS, SWITCHES AND PLUGS/SOCKETS NEED ADDING
- NEEDS ONLY UNREGULATED POWER SUPPLY ± 15 to ± 60 V

IN A RANGE OF 11 MODELS USING LATEST TOROIDAL TRANSFORMERS

1971-1980 TEN YEARS OF PLANNED PROGRESS

When, in 1971, Ian L. Poits founded his now world-famous company, he saw the need for a different and more rational approach to exploiting to the full, the potential that lay in modular construction. New thinking was badly needed. The result was a range of modules revolutionary in concept. The rightness of this new thinking is shown by the size of the company today, its new factory, its vast exports, its acceptance by constructors as the modules to build with. The range grows bigger and better. Exciting new lines (in no way conflicting with existing ones) are well past drawing board stage. This is why I.L.P. are simply ahead and staying there.

BRITAIN'S FASTEST GROWING MODULE SUPPLIERS

To: I.L.P. ELECTRONICS LTD, CANTERBURY CT2 7EP

Please supply

Total purchase price £.....


I enclose Cheque Postal Orders International Money Order

Please debit my Access/Barclaycard Account No.....

NAME.....


ADDRESS.....

Signature.....

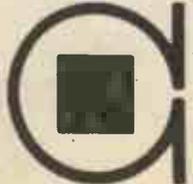

NO QUIBBLE 5 YEAR GUARANTEE
 7-DAY DESPATCH ON ALL ORDERS
 BRITISH DESIGN AND MANUFACTURE
 FREEPOST SERVICE

PSU

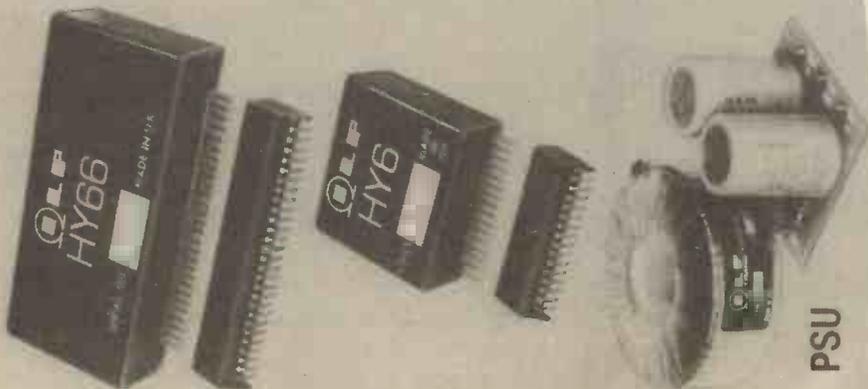


ALL UK ORDERS DESPATCHED POST FREE

SPECIAL PURCHASE



OF TOP QUALITY LCD MULTIMETERS

AC/DC
CURRENT
22
RANGES

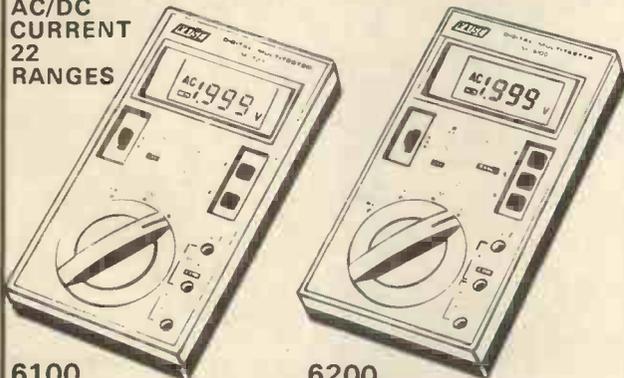

6100

6200

CHOOSE FROM FOUR MODELS

- 3½ digit autoranging (volts/Ohms)
- 200 hours battery life (2 pencils)
- 10 amp AC/DC (6220 & 6100)
- 1000v DC 600v AC
- 200 mA AC/DC (6200 & 6100)
- Range hold facility (6100 & 6110)
- Unit and range sign (6110 & 6220)
- Continuity buzzer (6100 & 6110)

RESOLUTION

100 µVDC, 1 mVAC
10 µA AC/DC, 0.1 Ohm
10 mA on 10A, AC/DC

ACCURACY 6100/6110

0.5% DC Volts
1% DC Current
1.2% AC Current
0.5% Resistance

OTHER FEATURES (ALL MODELS)

Low power Ohms range.
Zero Adjust key.
Battery Warning.

6200/6220

0.8% DC Volts
1.3% DC Current
1.4% AC Current
0.8% Resistance

In circuit resistance test.

Size 155 x 85 x 28 mm. 250 g.

- All prices include batteries/leads and UK VAT (UK c/p 65p)
- Order by post or telephone with Barclay or Access.

6200 **£39.95**

6220 **£49.95**

6100 **£64.95**

6110 **£74.95**

OR CALL IN AND SEE FOR YOURSELF

Prices correct at 1.11.80 E & OE

Cubegate Limited OPEN 9-6 SIX DAYS A WEEK

AUDIO ELECTRONICS

301 EDGWARE ROAD, LONDON, W2 1BN

TELEPHONE 01-724 3564



FREE CATALOGUE!

Send large SAE (175p UK)
Schools, Companies,
etc. free on request.

From Mr/Mrs/Miss (Block caps please)..... Ref P.E.:

Address

Please supply Qty Model(s)

I/We enclose (incl. 65p post).....

Chq/PO Value

Or debit Barclay/Access No.

2 SUPERB NEW KITS!

£2 OFF
SPECIAL OFFER



C300/ES200

high performance electronic ignition, to add power, economy, reliability, sustained smooth peak performance, instant all weather starting, to your car.

Surefire has sold in its thousands in ready made form from big name accessory firms, but it is now available in quality kit form to fit all vehicles with coil ignition up to 8 cylinders.

ES200. A high performance inductive discharge ignition incorporating a power integrated circuit (special selection); electronic variable dwell circuit (maximises spark energy at all speeds); pulse processor (overcomes contact breaker problems). Coil governor (protects coil). Long burn output. Negative earth only. Compatible with all rev. counters.

C300. In its ready built form (C3000) it came top of all systems tested by an independent national authority July '79. A high energy capacitive discharge ignition incorporating a high output short circuit proof inverter, top grade Swedish output capacitor, pulse processor circuit, transient overload protection. Fast rise bidirectional output ideal for fuel injection, sports carburation, oily engines. Compatible with most rev. counters. (Low cost adaptors available for rare cases. Application list enclosed with each kit. Note: Vehicles with Smiths/Jaeger rev. counters code RVI on dial will require adaptor type TCI).

What's in the kits. Surefire's own precision anodised aluminium extruded case. P.C. mounted security changeover switch, static timing light. Special selection Motorola semi-conductors. Capacitors, resistors etc. selected after 5 years experience. Glass fibre pcb, solder, complete down to last washer. Fully illustrated comprehensive instructions and full technical back up service.

SUREFIRE ELECTRONIC IGNITION

Suretron Systems (UK) Ltd.
Bayer Buildings, Lower Bristol Rd, Bath, BA2 3EF Dept. PE5
Tel: (0225) 332317

Name
Address

Phone order with Access/Barclaycard Quantity
VAT and P & P inc required

ES200: Neg	⊕	£13.95	£11.95	
C300: Pos	⊕	£17.95	£15.95	
C300: Neg	⊕	£17.95	£15.95	
Tacho Adapt. TCI			£3.90	

I enclose
chq/PO's
£
Chq No.


J. BIRKETT

(Partners: J. H. Birkett, J. L. Birkett)
Radio Component Suppliers
25 The Strait, Lincoln. LN2 1JF
Telephone: 20767

MAINS TRANSFORMER 250 Volt - Input, Out 43 Volt 50mA, 11 Volt, 2.5 Amp, 22-0-22 Volt 150mA, 16 Volt 120mA, 15 Volt 1.5 Amp, 20 Volt 275mA, at £3.90 (P&P £1.20).
TTL I.C.'s 7400 @ 20p, 74102 @ 22p, 7440 @ 22p, 74LS38 @ 30p, 74LS138 @ 40p.
5MHz CRYSTALS in 10X Case for 50p.
SUB-MINIATURE MULLARD DISCS. 1000pf 63v.w., at 25p doz.
10 WATT ZENER DIODES 4.7, 6.8, 7.5, 8.2, 12, 15, 18, 20, 24, 27, 30, 33, 36, 39, 43, 47, 51, 62, 68, 75, 82, 91, 100, 120, 130, 150, 180, 200 Volt All at 50p each.
5 WATT PLASTIC WIRE ENDED ZENER DIODES 3.6, 4.3, 5.6, 6, 6.2, 7.5, 8.2, 10, 11, 13, 14, 15, 16, 17, 18, 19, 20, 22, 27, 36, 39, 40, 47, 51, 56, 60, 62, 68, 87 Volt All at 30p each.
MINIATURE 6 To 12 VOLT S.P.C.O. RELAY with 5 Amp Contacts @ 60p.
MAINS TRANSFORMERS 250 Volt Input. Type 1. 24 Volt Tapped at 14 Volt 1 Amp @ £1.30 (P&P 25p). Type 2. 30-0-30 Volt 500mA @ £1.30 (P&P 25p). Type 4. 20 Volt 1 AmpX2, 10 Volt 1 AmpX2 @ £4.50 (P&P 95p). Type 5. 45 Volt 2 Amp, 45 Volt 500mA @ £3.50 (P&P 95p). Type 6. 16 Volt 2 Amp @ £1.60 (P&P 25p). Type 8. 30 Volt 1.75 Amp @ £1.60 (P&P 25p). Type 10. 24 Volt 2 Amp @ £1.60 (P&P 25p).
T.V. SAW FILTERS Untested at 3 for 50p.
IRON CORED L.F. CHOKE 2MH 4 AMP @ 50p (P&P 20p).
UNIUNCTION TRANSISTORS 2N 4871 @ 22p, MEV21 @ 22p, MU 4894 @ 22p, 4JD529 @ 22p, TIS 43 @ 20p.
WIRE WOUND POTENTIOMETERS 2 WATT 2K, 5K, 10K, 4 WATT 100K All at 30p each.
50. BC 107-8-9 TRANSISTORS Assorted untested @ 60p.
50. AC 128 TRANSISTORS Branded but untested @ 60p.
50. OC 71 TRANSISTORS untested @ 75p.
50. 2 WATT ZENERS Assorted untested @ 60p.
20. PHOTO TRANSISTORS AND DARLINGTONS assorted untested @ £1.
10. 20 AMP DIODES untested @ 60p.
20. 10 AMP DIODES untested @ 60p.
50. 1 AMP S.C.R.'s T05 Case untested @ £1.
METAL FILM RESISTORS 0.5% Tol. 32, 39, 39.2, 68, 82, 82.5, 100, 121, 150, 270, 330, 332, 360, 365, 470, 562, 619, 620, 680, 681, 700, 750, 820, 909 ohm, 1K, 2.15K, 2.2K, 3.01K, 3.9K, 5.1K, 6.2K, 18K, 75K, 150K, 200K, 392K, 597K, 600K, 1.21M All at 6p each.
MIDGIT MICRO SWITCHES with Lever SPCO @ 20p.
20 WAY LUCAR TAG CONNECTING BLOCK @ 60p.
POWER TRANSISTORS Germanium OC 20 @ £1, AL103 @ 75p, Silicon 2N 3789 @ 50p, BDY 57 @ £1.30, BDY 91 @ 80p, 2N 5039 @ £1.15, 2N 6354 @ £1.15, 2N 6495 @ £1.15, 2N 6496 @ £1.15.
PLASTIC BC 108 or BC 212 TRANSISTORS at 6 for 50p.
500Mtr. REEL OF PVC CABLE 13 Strands .019 @ £10.
9 VOLT ITRON 9 DIGIT SEVEN SEGMENT DISPLAY Type FG95A @ £1.80.
4500 PIV 2 Amp SILICON DIODES @ £1.50 each.

Please add 20p for post and packing, unless otherwise stated.

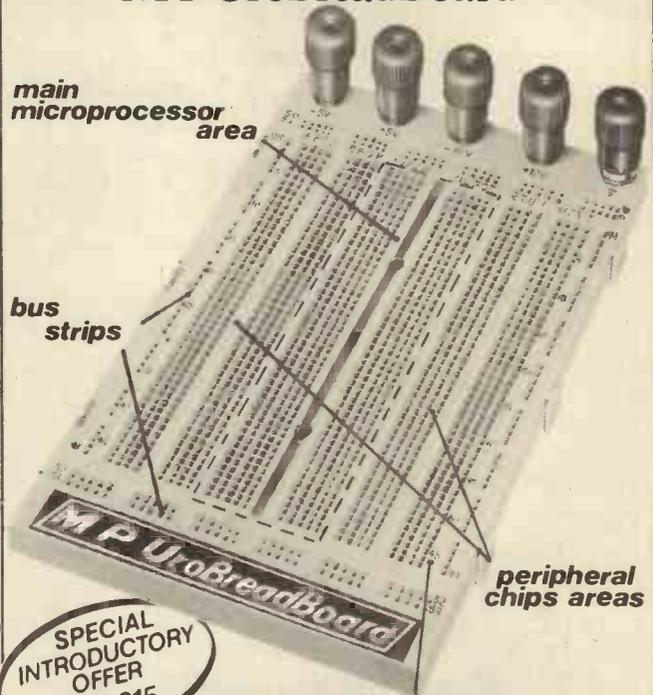If you're into MICROPROCESSORS then they should be into an M P UroBreadBoard



SPECIAL INTRODUCTORY OFFER ONLY £15

alpha numeric indexing

- * MPU Section accepts 24, 28, 40 & 64 pin DIL microprocessors
- * Auxiliary Areas accept any .3" or .6" RAM, ROM or peripheral chip
- * Power Bus Strips on all sides
- * 5 incoming turret Power Terminals
- * Component Support Bracket included
- * Over 1400 contact points
- * Alpha-Numeric column and row indexing
- * Eurocard size (160mm x 100mm)
- * Slots onto all BIMBOARDS
- * Non-Slip rubber backing
- * Ideal for schools and colleges
- * Long life, <10m.ohms, nickel silver contacts

The PROFESSIONALS breadboard that BEGINNERS can start on

BOSS INDUSTRIAL MOULDINGS LTD

2 Herne Hill Rd, London SE24 0AU, England
Telephone 01-737 2383 Telex 919693
Cables & Telegrams: LITZEN LONDON SE24

Please send me MPuroBreadBoard(s) at the special, limited period, introductory offer price of £15.00. This price includes VAT & PP, is applicable from Sept 1 1980 but please add 15% for Overseas Orders, make cheques/P.O. payable to BOSS Industrial Mouldings Ltd and allow 10 days for order processing and cheque clearance etc.

I enclose a cheque/P.O. to the value of £.....

Name

Company

Address

.....

.....

Telephone Number

PE 12

DORAM DORAM ELECTRONICS LTD

Fitzroy House, Market Place, Swaffham, Norfolk, PE37 7QH.

New Catalogue



40p

to be refunded with first order

FREE competition entry with catalogue

REF. Dept. PE

Please send me a copy of your new catalogue

NAME

ADDRESS

I enclose cheque/postal order for 40p

LOW COST

COMPUTER SPEECH

ADD VERBAL OUTPUT TO A COMPUTER OR LOGIC SYSTEM OF ANY KIND AT SPECIAL INTRODUCTORY PRICES:

24-WORD (ref. S2A - see below for spec.) speech synthesiser board: **£39.95** + 80p PP + VAT, INTERFACE KIT: **£14.95** + 80p PP + VAT

N.B. Full tech. spec. comes with speech board, prices can only be held definitely until end of Dec.

AS DESCRIBED IN THIS ISSUE OF P.E.


The basic speech boards which we offer provide fixed 24 or 64 word highly intelligible vocabularies at a remarkably low cost. The unit is based around the excellent Telesensory Instruments (TSI) speech products for which Modus is the sole UK distributor.

These boards require a TTL interface, binary latches, special power supply, audio band-pass filter, edge-connector, plug and socket to driving computer or logic system. All this is included on our interface kit: **£14.95** + 80p PP + VAT. All that is required is the speech synthesis board itself, a small transformer and an 8 ohm loudspeaker. Controls are included for frequency, volume and tone.

All speech synthesiser boards are supplied with full tech. specs, and their connection to any logic system (MPU or not) is very straight forward.

SPEECH SETS AND PRICES:

S2A (24 words) (calculator vocabulary) £39.95 + 80p PP + VAT "OH" "ONE" "TWO" "THREE" "FOUR" "FIVE" "SIX" "SEVEN" "EIGHT" "NINE" "TEN" "ELEVEN" "TWELVE" "THIRTY" etc. "HUNDRED" "THOUSAND" "AND" "SECONDS" "DEGREES" "DOLLARS" "CENTS" "POUNDS" "OUNCES" "TOTAL" "PLEASE" "FEET" "METRES" "CENTIMETRES" "VOLTS" "OHMS" "AMPS" "HERTZ" "DC" "AC" "DOWN" "UP" "GO" "STOP" high and low tones are also included.	S2B (64 words) (standard English set) £67.50 + 80p PP + VAT All words as for S2A board plus: "ZERO" "TEN" "ELEVEN" "TWELVE" etc. "TWENTY" "THIRTY" etc. "HUNDRED" "THOUSAND" "AND" "SECONDS" "DEGREES" "DOLLARS" "CENTS" "POUNDS" "OUNCES" "TOTAL" "PLEASE" "FEET" "METRES" "CENTIMETRES" "VOLTS" "OHMS" "AMPS" "HERTZ" "DC" "AC" "DOWN" "UP" "GO" "STOP" high and low tones are also included.	S2C (64 words) (ASC11 vocabulary) £67.50 + 80p PP + VAT "SPACE" "X-POINT" "QUOTE" "NUMBER" "DOLLARS" "PERCENT" "AND" "APOSTROPHE" "LEFT PAREN" "RIGHT PAREN" "STAR" "PLUS" "COMMA" "MINUS" "POINT" "SLASH" "ZERO" "ONE" "TWO" etc. "COLON" "SEMICOLON" "LESS THAN" "EQUALS" "GREATER THAN" "MARK" "AT" "A" "B" "C" etc. "LOWER CASE" "UPPER CASE" "UP ARROW" "CONTROL"
--	--	---

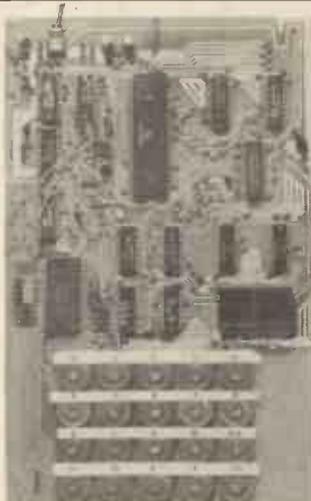

GET TO GRIPS WITH THE MICRO PROCESSOR ITSELF WITH

THE EDUKIT

you can even make it talk with our speech board!

FULL KIT: **£34.95** + 80p PP + VAT

Designed by Dr. A. A. BERK

(see P.E. review (April edition) & P.E. special-offer May and June)

TECHNICAL SPEC.

- CMOS 1802 Processor (RCA) - excellent MPU for control.
- 256 bytes of RAM - plenty for learning machine code.
- Hexadecimal display - large and readable.
- Full hex keyboard - positive "click" type switches.
- Full manual - starts at soldering, ends with control circuits.
- Loudspeaker output - simple audio experiments.
- Excellent for all ages from secondary school level upwards.

The EDUKIT has proven a great success providing an excellent introduction to silicon chip technology from the bottom upwards. Many schools and colleges are using the kit, and sales now extend world wide. The machine is not meant to form the basis of a large and expandable personal computer system. The EDUKIT teaches all those things which a purely BASIC running machine cannot, i.e. the basis of hardware electronic control, down-to-earth Bits and Bytes, Machine Code etc. - and all this at a really throw away price. The manual is written by Dr. A. A. Berk to impart educational understanding from the beginning.

1802 USER'S MANUAL (essential for full understanding of MPU used in EDUKIT) **£4.75** + 50p PP.

FULL SOCKET SET for EDUKIT: **£2.99** + VAT (PP included).

EPROM PROGRAMMER P.C.B. £8.95 (fully inc.)

(For 2708's & multi supply 2716's)

See P.E. Dec. '79 and Jan. '80 for full description of programmer, along with interface to COMPUKIT.

MODUS SYSTEMS LTD.

Phone: Letchworth (04626) 74468/76392.
29A Eastcheap, Letchworth, Herts SG6 3DA.

ELECTROVALUE OVERSEAS



Although originally organised to serve the U.K. market, thanks to our computer, we are able to meet the demands of a steadily growing number of customers overseas with speedy and reliable service. We make it as simple as possible for you to order from our EV Catalogue '81 which we shall be happy to send on request.

FOR A FREE COPY

send us your name and address without delay and we shall send you Catalogue '81 by surface mail by return. If you want Catalogue '81 sent by air, please include one U.S. dollar or equivalent with your instructions.

ELECTROVALUE

ELECTROVALUE LTD., 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB. TEL: (S.T.D. 0784) 33603. TELEX: 264475

PROGRESSIVE RADIO

31, CHEAPSIDE, LIVERPOOL L2 2DY
SEMICONDUCTORS. Texas R1038 TO3 power trans. 50p. 741 8 pin 22p. NE555 24p. TAG4443 SCR 45p. 723 14 PIN REGS. 35p. AD 161/2 MATCHED PAIRS 70p. 2N5062 SCR 18p. TL209 RED LED 10 for 75p. BD238 28p. BD438 28p. MPU131 P.U.T.'s 40v. 200mA 375MMW 15p each. 2K3733 £1.75. Infra Red OL2 LEDs 30p. Rectangular Red LED's 12p each. CA3020 I.C.'s 40p each. BY223 20p.
MINIATURE MAINS TRANSFORMERS. ALL 240VAC PRIMARY. 6-0-6 100mA. 9-0-9 75mA. 12-0-12 50mA/ all 75p each. 2V 200mA 75p. 12-0-12V, 250mA £1.25. 0-8V-0-8V 280mA £1.30.
PULSE TRANSFORMERS. 1:1 (GPO type) 30p. 1:1 plus 1 min. P.C. mounting 60p.
MINIATURE SOLID STATE BUZZER. 33x17x15mm. output at 3 feet 70db, only 15mA drain, operating voltage 2 types 6 or 12VDC 75p each.
LOUD BUZZER. 63x17x15mm. 63p. Rotary Alarm siren. 12VDC. Red plastic body and mounting bracket 68x75mm £4.95.
ALARM BELLS. motorised aluminium gong. output 80db at 3 mtrs. 12V DC 65mA £7.95p.
POCKET MULTIMETER. MODEL NM55 2,000 ohms per volt. 1,000 volts AC/DC, 100mA DC current. 2 resistance ranges to 1 meg £5.50p.
SOLDER SUCKER. High suction/teflon nozzle. £4.65p.
TRANSISTORS. 40kHz RECEIVER £3.50 pair.
MOTORS. 3V model type 22p. 6V cassette motor £1.20p. Replacement 12VDC 8 track motors 85p.
EX-EQUIP. B.S.R. RECORD DECK MOTORS. C128, C127 etc. 240V AC £1.20p.
AMPLIFIER COAX CONNECTORS. Plugs 47p. Sockets 42p. Elbows 90p. Reducers 13p. Back to back sockets 65p. Back to back plugs 65p.
HIGH IMPEDENCE HEADPHONES. mono 2,000 ohms Imp. transducer type, adjustable band and padded earpiece £2.75.
SPECIAL OFFER STEREO HEADPHONES. 8 ohms, adjustable, standard stereo plug only £2.95p.
INTERCOM UNITS (can be used as baby alarm) supplied with approx. 60' cable, call button, 2 wts £5.25 pair, 3 way £7.25p. **WIRELESS INTERCOM.** 2 units both operate on 240VAC and mains connected. AM frequency 180KHz. £29.95p.
MINIATURE TIE PIN MICROPHONE. Omni, 1K Imp., uses dead air battery (supplied) £4.95p. **LOW COST CONDENSER MIKE.** Stick type. Omni, 600 ohms, on/off switch, standard jack plug only £2.95p. **EM607 CONDENSER MICROPHONE.** Highly polished metal stick mike, uni directional, 600 ohms. 30-18KHz, on/off switch only £7.95p. **DYNAMIC STICK MIKE.** CARDIOD, dual imp., 600 ohms or 20K. 70-18KHz, attractive black metal case only £7.75p.
JACKSON'S C280 80p each. **VARIABLE CAPS.** 50p each. **MERCURY (TILT) SWITCH,** 1x1/2". 35p.
Special clearance offer of tools, (1) Side Cutters, (2) Long nosed Pliers, (3) Heavy duty pliers, Insulated handles, all at £1.00 each.
CRIMPING TOOL for standard terminals also 6 gauge stripper and wire cutter, insulated handles only £2.30.
Cash with order please, official orders welcome from schools etc., please add 30p post and packing, VAT inclusive, SAE for latest illustrated stock list. **ALL ORDERS DESPATCHED BY RETURN POST**



250 V d.c. working POLYESTER CAPACITORS

Prices per pack of five
 .01uF, .022uF, .047uF, .1uF 35p.
 .22uF-.47uF 60p.
 1.0uF-2.2uF £1.60.

SIGNAL INJECTORS with (pre-set) variable AF, which emits RF harmonics into the UHF band. Protected up to 300 volts dc. Complete with leads **£5.70 each.**
 All prices include VAT at 15%. P&P per order 30p. S.A.E. for leaflets. Access cards.

ELECTRONIC MAILORDER LTD,

62 Bridge Street, Ramsbottom,
Via Bury, Lancs. BL0 9AGT. Tel. Ramsbottom 3036.

AERIAL AMPLIFIERS

Aerial amplifiers can produce remarkable improvement on the picture and sound in fringe or difficult areas.

B45 - for mono or colour this is tunable over complete UHF television band.

B11 - for stereo or standard VHF/FM radio.


B12 - for VHF television band 1 & 3.

All amplifiers are complete and ready to use.

Battery type PP3 or 8v to 18v dc, next to the set type fitting. Prices **£6.70 each.**

say hi!
to the CS-1830

...and 'goodbye'
mediocrity.

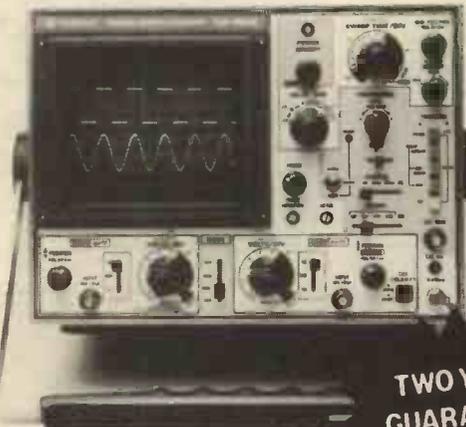

TWO YEAR
GUARANTEE.

Our dual trace CS-1830, from Trio, is no ordinary 30MHz oscilloscope.

Its domed mesh PDA rectangular c.r.t., with its internal graticule, gives outstanding brightness and clarity with only minimal parallax error.

It has a trigger delay function, which eases the measurement of complex waveforms; a 2mV/div. vertical sensitivity, to help measure ultra-weak signals; and a bandwidth of d.c. to 30MHz. And much, much more.

In short, the Trio CS-1830 is the means of measuring high frequency, pulsed, video, audio or digital signals. There are simply none more precise; and none more practical.

And 'hi!' to the rest of the Trio range.

- CS-1577A: dual-trace; d.c. to 35MHz
- CS-1566A: dual-trace; d.c. to 20MHz
- CS-1560A11: dual-trace; d.c. to 15MHz
- CS-1352: dual-trace; d.c. to 15MHz portable
- CS-1562A: dual-trace; d.c. to 10MHz
- CS-1575: dual-trace; d.c. to 5MHz
- CS-1559A: single-trace; d.c. to 10MHz
- and now, MS-1650: dual-trace; d.c. to 10MHz; digital storage.

hi!  **NONE BETTER.**
House of Instruments,
34-36 High Street,
Saffron Walden, Essex CB10 1EP.
Tel: (0799) 22612. Tlx: 81653.

GMT Freeport E **Birmingham** B19 1BR
ELECTRONICS 021-233-2400

- FREESTOP ON ORDERS
- VAT INCLUSIVE PRICES
- ADD 30p P&P
- 24 HR PHONE ANSWERING SERVICE
- ACCESS
- VISA
- CASH
- CHEQUE

ALL PRICES IN PENCE EACH UNLESS OTHERWISE STATED

C-MOS (BUFFERED)				LINEAR				SEMICONDUCTORS			
HEF4000	22	HEF4044	105	UA7457	136	CA3046	84	IN914	8	8C182L	12
HEF4001	22	HEF4046	133	HEF4516	127	CA3080E	77	IN4001	5	8C184	11
HEF4002	22	HEF4047	109	HEF4517	214	CA3130E	90	IN4002	5	8C184L	13
HEF4003	119	HEF4049	57	HEF4518	118	CA3140E	48	IN4004	7	8C212	11
HEF4007	22	HEF4050	57	HEF4519	69	CA3189E	293	IN4007	9	8C212L	12
HEF4008	100	HEF4051	87	HEF4520	116	LM301AN	34	IN4148	4	8C214	11
HEF4011	22	HEF4052	90	HEF4521	235	LM309A	78	IN4202	13	8C241	12
HEF4012	22	HEF4053	90	HEF4528	124	LM380N	104	2N2369	21	8C547	13
HEF4013	37	HEF4066	62	HEF4532	150	LM381AN	158	2N2646	46	8C548	11
HEF4014	105	HEF4067	475	HEF4534	338	LM3900N	75	2N2926G	13	8C549	12
HEF4015	100	HEF4068	22	HEF4539	138	MC3403P	156	2N3053	19	8C557	18
HEF4016	57	HEF4069	22	HEF4585	122	NE531	131	2N3054	55	8C558	16
HEF4017	100	HEF4070	22	HEF4574	214	NE581T	259	2N3056	55	8C570	15
HEF4018	100	HEF4071	23	HEF4097	113	NE555N	28	2N3102	9	8C571	15
HEF4019	58	HEF4072	23	HEF4098	92	NE568N	66	2N3104	9	8D131	39
HEF4020	112	HEF4073	23	HEF40106	78	NE586N	171	2N3105	10	8D132	39
HEF4021	107	HEF4075	23	HEF40140	149	NE570N	445	2N3173	297	8D138	39
HEF4022	103	HEF4076	130	HEF40192	149	NE571N	505	2N3819	22	8D140	39
HEF4023	22	HEF4077	22			RC8136	146	2N3820	39	8F180	333
HEF4024	76	HEF4078	23			TBA1205	86	2N3904	86	8F185	29
HEF4025	22	HEF4061	23			TD01022	713	2N6457	39	8F190	17
HEF4026	244	HEF4082	23			TD010348	239	2N6459	35	8F191	17
HEF4027	57	HEF4095	80			TL081CP	84	40673	86	8H139	50
HEF4028	97	HEF4086	60			TL081CN	156	8E107	14	8K120	21
HEF4029	113	HEF4093	63			UA741CN	20	8C108	14	8L896	280
HEF4030	58	HEF4074	219			UA7812CU	78	8C108L	18	8T131	49
HEF4031	250	HEF4104	206			UA7815CU	148	8C139	16	8T132	54
HEF4032	139	HEF4502	114			UA7912CU	97	8C109B	19	8T141C	76
HEF4040	107	HEF4505	714			UA7915CU	97	8C109C	20	8T142C	76
HEF4041	94	HEF4508	230			UA7810CS	38	8C148	10	8T195S	76
HEF4042	83	HEF4510	135			UA7811CS	38	8Z158/8Z159	10	8T195S	60
HEF4043	100	HEF4511	157			UA7815CS	38	+ Voltage	9	8T177	15

CAPACITORS				Polyester Radial Leads				Electrolytic Radial Leads						
Electrolytic Axial				Dipped Type, C200/352 Style				Cap 382						
-10% to +60% Tol.				Moulded Type, 10.2mm Pitch				+ Value						
Order Code	Cap 018	µF	±	Order Code	Cap 380	µF	±	Order Code	Cap 034	µF	±			
1.0	16	28	40	85	1.0	16	28	40	85	1.0	16	28	40	85
1.5	16	28	40	85	1.5	16	28	40	85	1.5	16	28	40	85
2.2	16	28	40	85	2.2	16	28	40	85	2.2	16	28	40	85
3.3	16	28	40	85	3.3	16	28	40	85	3.3	16	28	40	85
4.7	16	28	40	85	4.7	16	28	40	85	4.7	16	28	40	85
6.8	16	28	40	85	6.8	16	28	40	85	6.8	16	28	40	85
10	16	28	40	85	10	16	28	40	85	10	16	28	40	85
15	16	28	40	85	15	16	28	40	85	15	16	28	40	85
22	16	28	40	85	22	16	28	40	85	22	16	28	40	85
33	16	28	40	85	33	16	28	40	85	33	16	28	40	85
47	16	28	40	85	47	16	28	40	85	47	16	28	40	85
68	16	28	40	85	68	16	28	40	85	68	16	28	40	85
100	16	28	40	85	100	16	28	40	85	100	16	28	40	85
150	16	28	40	85	150	16	28	40	85	150	16	28	40	85
220	16	28	40	85	220	16	28	40	85	220	16	28	40	85
330	16	28	40	85	330	16	28	40	85	330	16	28	40	85
470	16	28	40	85	470	16	28	40	85	470	16	28	40	85
680	16	28	40	85	680	16	28	40	85	680	16	28	40	85
1000	16	28	40	85	1000	16	28	40	85	1000	16	28	40	85
1500	16	28	40	85	1500	16	28	40	85	1500	16	28	40	85
2200	16	28	40	85	2200	16	28	40	85	2200	16	28	40	85

RESISTORS				D.I.L. Sockets			
Carbon Film, Fixed				8 Pin Low Profile Socket Tin			
0.25W, E24 Values, 100-10M, 5% Tol.				12 DIL SKT 8			
100/100 (Multi 10/Value)				16 Pin Low Profile Socket Tin			
0.5W, E12 Values, 10R-4M, 10% Tol.				18 DIL SKT 16			
2 Pin				18 Pin Low Profile Socket Tin			
Metal Film, Fixed				P.C.B. Components			
0.5W, E24 Values, 5R-1M, 2% Tol.				Delta Fan, Blue Ink, Slow Drying			
2 Pin				80			
2.5W, E12 Values, 10R-21K, 5% Tol.							
8 Pin							
Metal Glass, Fixed							
0.5W, E24 Values, 1M-33M, 5% Tol.							
16 Pin							

MAINS TRANSFORMERS				Plastic Boxes - Boss Industrial Mouldings			
Secondary may be connected in series or parallel to give wider voltage range				Moulded Box and Clamp Fitting Flanged Lid			
Primary-use 0.20V, 240V				ABS Box, C/W Brass Bushes, and Lid in Orange			
6VA - Clamp Type Construction				Order Code			
Approx. 18% Regulation F.C. 54, H36, W35				L112 W82 D31 96 Case BIM2003 DR			
D-4.5V, 0.4 5V Secondaries				L150 W80 D50 131 Case BIM2005 DR			
0.5V, 0.8V				L180 W110 D80 223 Case BIM2008 DR			
0.12V, 0.12V							
0.15V, 0.15V							
0.17 5V, 0.17 5V							
0.20V, 0.20V							
20VA - Clamp Type Construction				Plastic Boxes with Metal Lids			
360 each				Recessed Top Box			
Approx. 16% Regulation F.C. 70, H48, W46				ABS Box, C/W Brass Bushes, In Orange			
D-4.5V, 0.4 5V Secondaries				Trim Aluminium Top Panel Painted Grey			
0.8V, 0.8V				Order Code			
0.12V, 0.12V				L85 W58 D78 112 Case BIM4003 DR			
0.15V, 0.15V				L111 W111 D42 150 Case BIM4004 DR			
0.17 5V, 0.17 5V				L161 W98 D53 208 Case BIM4005 DR			
0.20V, 0.20V							

VERO ELECTRONICS PRODUCTS				SWITCHES			
2.5" x 5" 1" pitch Veroboard				Miniature Toggle - Honeywell			
71				SPDT			
3.75" x 8" 1" pitch Veroboard				SPDT C/OH			
79				SPDT Double Bias To Centre			
2.5" x 1" 1" pitch Veroboard (B)				DPDT			
85/Pack				DPDT C/OH			
3.75" x 5" 1" pitch Plain Board				Miniature Push - C & K			
88				SP Push To Make, Momentary			
8.82" x 2.8" 1" pitch V-DIP Board				SP Push To Break, Momentary			
135				82 SW 8531			
Spot Face Cutter				99 SW 8A2081			
107				111 SW 8A2021			
Pin Insertion Tool for D40 type pin							
147							
D8 Pin, 040 (100)							
44/Pack							
SS Pin, 040 (100)							
44/Pack							
Verobase Kit (1) open, 2-mv, 75-comb							
454/Pack							
Verobase Combs (25)							
109/Pack							
Verobase Wire (2)							
109/Pack							

GMT ELECTRONICS PROJECTS	KIT	BUILT UP
FREE-STANDING COMPLETE TELETXT UNIT - FULL SPEC	E199-90	E275-00
TELETXT DECODER BOARD + REMOTE HAND CONTROL	E135-90	E160-00
TELETXT COMPATIBLE TUNER AND P. S. U.	E 46-90	E 57-00
TELETXT COMPATIBLE PAL ENCODER + MODULATOR	E 22-90	E 35-00
F. E. T. OUTPUT 100W MONO POWER AMPLIFIER MODULE	E 27-50	E 35-00
X-BAND DOPPLER RADAR ALARM MODULE - MARK II	E 35-90	E 44-00
ONE AMP P. S. U. MODULE (SPECIFY 5 OR 12 VOLTS)	E 7-50	E 10-00
SIMULATED INERTIA MODEL TRAIN CONTROLLER	E 22-50	E 35-00
SIMULATED INERTIA SLOT RACER CONTROLLER	E 27-50	E 40-00
MODEL TRAIN STEAM SOUND SIMULATOR MODULE	E N/A	E 5-00

GMT ELECTRONICS, P.O. BOX 290, HAMPTON STREET, BIRMINGHAM B19 3JR

STEVENSON

REGULATORS

7905	85p	7805	70p
7912	85p	7812	70p
7915	85p	7815	70p
TIC246	16A 400V Triac	115p	
C106D	4A 400V SCR	45p	

SPEAKERS

64mm 8Ω	110p
64mm 64Ω	110p
70mm 8Ω	140p
70mm 80Ω	170p
56mm 8Ω	100p
Pair of ultrasonic transducers	380p
Magnetic earphone + 3.5mm plug	17p
Crystal earphone + 3.5mm plug	48p

POTENTIOMETERS

Rotary 5K-1M Log or Lin	8p
Rotary 5K-1M stereo	33p
Slide 60mm travel 5K-500K log or Lin, single	110p
Suitable knobs for above with coloured caps in red, blue, green, grey, yellow and black. Rotary 16p. Slide 12p each.	65p

CONNECTORS

DIN	Plug	Chassis Socket	Line Socket
2 pin	9p	8p	12p
3 pin	12p	10p	12p
5 pin 180	13p	11p	16p
JACK	Plug	Scr. plug	Socket
2.5mm	10p	16p	9p
3.5mm	11p	18p	9p
std.	17p	30p	22p
Stereo	25p	39p	25p

SPECIAL OFFERS

2708 EPROM	490p	10 x TL081 op. amps	350p
AYS-1013 UART	290p	100 x 1N4148	180p
TDA1022 Delay line	550p	20 x 1N4001 diodes	70p
MM57160 STAC timer	500p	20 x 0.125 red LED's	150p
SN76477 Sound generator	180p	20 x 0.125 green LED's	260p
NE567 Tone decoder	100p	20 x 0.125 yellow LED's	260p
LM318 Op. amp.	70p	4 x HP7 rechargeable cells	500p
5 x C106D SCR	200p	3 x LM339 Quad comp.	140p
4 x FND500 displays	350p	10 x 2N3707 transistors	50p
3 x 7905 or 7912	150p	10 x BC157 transistors	60p
2 x CA3046 arrays	100p	10 x Miniature slide switches	150p
		20 x 8 pin DIL sockets	160p
		3 x 4P3W rotary switch	100p
		10 x T05 heatsinks	100p

Send 50p for your copy of our catalogue, containing 100 illustrated pages detailing over 3000 line items. You will receive:

- A mail order form to facilitate rapid despatch
- A 50p discount voucher.

All prices include VAT. Please add 50p carriage on all orders below £15. Minimum order £5.



Access & Barclaycard welcome
Sales office: 01-464 5770.



Mail orders to STEVENSON (Dept PE)

TRANSISTORS

AC127	25p	BC547	8p	TIP30C	70p
AC128	25p	8CY71	18p	TIP2955	65p
AD161	40p	BD131	35p	TIP3055	60p
AD162	40p	BD132	35p	ZTX107	12p
BC107	10p	BD139	35p	ZTX108	12p
BC108	10p	BD140	35p	ZTX109	12p
BC109C	12p	BFX29	25p	ZTX300	14p
BC147	9p	BFX84	26p	ZTX500	15p
BC178	16p	BFY50	23p	2N3053	25p
BC182	10p	BFY51	23p	2N3055	55p
BC182L	10p	MJ2955	98p	2N3702	9p
BC184	10p	TIP29C	60p	2N3703	9p
BC184L	10p			2N3704	9p
BC212	10p			2N3819	22p
BC212L	10p			2N3905	10p
BC214	10p			2N3905	98p
BC214L	10p			2N5777	50p

LINEAR

741	18p	LM324	52p	MM57160	650p
747	70p	LM339	55p	NE531	140p
748	40p	LM348	100p	NE555	23p
7106	850p	LM377	170p	NE556	60p
CA3046	70p	LM378	230p	NE567	120p
CA3080	75p	LM380	85p	RC4136	100p
CA3130	100p	LM381	140p	SN76477	230p
CA3140	60p	LM382	120p	TBA800	80p
LF347	170p	LM386	90p	TBA810	110p
LF351	45p	LM387	120p	TDA1022	630p
LF353	90p	LM1458	40p	TL081	45p
LF386	95p	LM1830	180p	TL082	85p
LM301A	30p	LM3900	60p	TL084	125p
LM318	85p	LM3909	72p	XR2206	390p
		LM3911	120p	ZN414	80p
		LM3914	320p	ZN425E	475p
		LM3915	320p		

PACKS

Specially designed packs intended for development work at a considerable saving.


- 1/4w resistors. 10 of each value 4.7ohm to 1 Mohm. a total of 650 resistors. 530p each.
- 1/2w resistors. 10 of each value 4.7ohm to 1 Mohm. a total of 650 resistors. 875p each.
- Presets. Pack of 5 of each value from 100ohms to 1 Megohm. a total of 65 presets. 390p each.
- LED's. Pack containing 10 of each colour LED 0.2 size. Total of 30 Led's + clips. 450p each.
- Zeners. Pack of 5 of each value from 2V7 to 33V a total of 130 zeners 780p each.

CMOS

4001	25p	4025	25p	4072	25p
4002	25p	4026	150p	4081	30p
4006	95p	4027	50p	4082	30p
4007	25p	4028	90p	4085	85p
4011	30p	4029	110p	4093	80p
4013	50p	4040	110p	4095	110p
4015	85p	4042	85p	4510	90p
4016	48p	4046	110p	4511	100p
4017	90p	4047	95p	4518	90p
4018	90p	4049	50p	4520	110p
4020	110p	4050	50p	4527	165p
4021	100p	4052	80p	4528	100p
4022	25p	4060	120p	4532	125p
4023	25p	4066	63p	4543	170p
4024	80p	4068	25p	4583	80p
		4069	25p	4585	115p
		4070	25p		
		4071	25p		

SKTS

8 pin	9p	22pin	20p
14pin	11p	24pin	22p
16pin	12p	28pin	26p
18pin	16p	40pin	38p
20pin	18p		

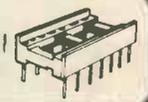

OPTO

Red	0.125in.	0.2in.	
Green	TIL209	TIL220	10p
Yellow	TIL211	TIL221	16p
Clips	TIL213	TIL223	16p
			3p
DL704	0.3in	CC	130p
DL707	0.3in	CA	130p
FND500	0.5in	CC	100p

CAPACITORS

TANTALUM BEAD	
0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1	
and 2.2uF @ 35V	12p
4.7, 6.8, 10uF @ 25V	20p
22 @ 16V, 47 @ 6V, 100 @ 3V	26p
POLYESTER (Mullard C280 series)	
0.01, 0.015, 0.022, 0.033, 0.047, 0.1	6p
0.15, 0.22	8p
0.33, 0.47	12p
RADIAL LEAD ELECTROLYTICS	
63V 0.47 1.0 2.2 4.7 10	7p
	22 33 47 9p
25V 10 22 33 47	7p
	100 9p
	470 20p
	1000 32p

NEED ENCLOSING?

Now, CSC are really in the hardware business, with a series of plastic cases ideally suited to applications ranging from hand-held probes to hi-fi equipment. CSC cases are moulded in robust plastic and come with all the necessary screws, covers and, where appropriate, battery compartments, connectors and transparent panels for displays. And CSC can provide customer-specified variations for large-quantity orders. Fill in the coupon for more details.

CSC (UK) Ltd, Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.
Telephone: (0799) 21682. Telex: 817477.

 CTP-Probe Case (£2.30 Nett) £3.50	 DMC-2 Design-Mate Case (£3.85 Nett) £5.29	 CBP-1 Portable Case (£5.75 Nett) £7.76
 CTH-1 Handheld Case (£3.00 Nett) £4.31	 DMC-1 Design-Mate Case (£4.25 Nett) £5.75	 CTB-1 Bench Topper Case (£7.15 Nett) £9.37

Bold prices include P & P and 15% VAT. Please deduct £1 postage from each additional order.

I enclose cheque/PO for £.....
or debit my Barclaycard, Access, American Express card

No..... Exp. date.....
or Tel: (0799) 21682 with your card number and your order will be in the post immediately.

NAME.....
ADDRESS.....
CONTINENTAL SPECIALTIES CORPORATION
CSC FREE catalogue tick box

Continental Specialties Corporation (UK) Limited, Dept. 5MM
Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.

TOMORROW'S TOOLS TODAY

ALCON

BRING YOU THE NEW

TESTER 20

20kΩ/V a.c. & d.c.

THE PROFESSIONAL SOLUTION TO GENERAL MEASUREMENT PROBLEMS

£43.06

Inc. VAT and complete with carrying case, leads and instructions.



The best instrument for the workshop, school, toolbox, TV shop and anywhere accurate information is needed quickly and simply.

Accuracy: d.c. ranges 2%, a.c. & Ω 3%.
d.c. V 100mV, 1.0V, 3.0V, 10.0V, 30V, 100V, 300V, 1000V. d.c. 1. 50μA, 100μA, 300μA, 1.0mA, 3.0mA, 100mA, 30mA, 100mA, 1.0A, 10A.
a.c. V 10V, 30V, 100V, 300V, 1000V.
a.c. 1. 3.0mA, 10mA, 30mA, 100mA, 1.0A, 10A.
Ω 0.5-0.0kΩ, 50kΩ, 500kΩ, 5.0MΩ, 50MΩ.
db from -10 to +61 in 5 ranges.

For details of this and the many other exciting instruments in the Alcon range, including multimeters, component measuring, automotive and electronic instruments please write or telephone:

ALCON Instruments Ltd.

19 MULBERRY WALK · LONDON SW3 6DZ · TEL: 01-352 1897 · TELEX: 918867

Base 2

MODEL 800MST

80 COLUMN HIGH PERFORMANCE
IMPACT PRINTER

- suitable for most Micros.

JUST LOOK AT THESE STANDARD FEATURES:-

*RS-232, 20mA, IEEE 488 and Centronics I/O
*15 Baud rates to 9,600 *100 Chrs. per second -
Bidirectional * 6 print densities 60, 72, 80, 96,
120 or 132 Chr/line * Self test switch * 96 Chrs.
ASC II Standard * Auxilliary User Defined Ch.
set * Tractor and fast paper feed/graphics
* 2k Buffer * Accepts 8½" max. paper pressure
feed and 9½" max. paper tractor feed.

FREE
INTERFACE
CABLE
WORTH
£25

ONLY
£359 + VAT

Compukit UK101 DISC DRIVES

with up to 32k RAM expansion

free
games
disc

NEW

* 9 Digit extended Basic

* Plugs straight into 8k Compukit requires
no hardware mods. (5v.5A required for 610)

610 Expansion (8k) ONLY £159 + VAT
Disc Drive with DOS ONLY £285 + VAT

VERBATIM 5¼" DISCS £1.85 each (min. 10) + VAT

STATIC RAM 2114 1-12 £3 each + VAT 13+ £2.50 each + VAT

EXATRON Stringy Floppy

COMBINES ECONOMY OF CASSETTE
WITH SPEED & RELIABILITY OF DISC

16k loads in approx. 24 secs. - Wafers to
75ft (48k approx.)

ONLY
£188
+ VAT

Versions for
PET
APPLE
TRS80

Stringy Floppy with 10 Wafers (Tapes)
BUS EX. 2 for 1. Machine Lang. Monitor

Ohio Superboard II & Challenger 1P with FREE RAM

- the no fuss start to Micro's.

* Ready Built * 8k Microsoft in ROM, 6 digit floating
point basic plus full features. 4k RAM - expandable to 32k



FREE
ADDITIONAL
4k RAM with
SII & CI
WORTH £24

All 50Hz
operation

SUPERBOARD II (24x24 format) £159 + VAT

SUPERBOARD II (48x32 format) £199 + VAT

POWER SUPPLY 5v.3A. £27 + VAT

CASE £29 + VAT

CHALLENGER 1P (24x24 format) £219 + VAT

CHALLENGER 1P (48x32 format) £259 + VAT
(Superboard is used in Challenger)

Mighty Micro

for a Mighty good deal !!!

Please add V.A.T. at 15%. Carriage extra, will advise at time of order. Official orders welcome.

61 NEW MARKET SQUARE, BASINGSTOKE, HAMPSHIRE. RG21 1HW

Telephone: Basingstoke (0256) 56468 and 56417

Buy in confidence. If on receipt of your order the goods do not meet with your satisfaction,
return within 7 days for full refund. Credit facilities arranged.



READ ALL ABOUT IT — all the latest on home entertainment equipment and ideas in . . .

HI FI YEARBOOK AND HOME ENTERTAINMENT 1981


Published again in November, this new 1981 edition in larger magazine
size means more comprehensive coverage of the whole range of home
entertainment equipment, from aerials to headphones, from microphones
to video recorders and from radios to electronic organs.

Backed by authoritative articles on developments in the world of Hi Fi,
plus details of stockists, Hi Fi Yearbook and Home Entertainment 1981 is
essential reading for enthusiasts and buffs.

Available from leading newsagents and bookshops from 1st November
1980. Price £3.00.

If you have difficulty in obtaining your copy order direct from the
publishers @ £3.50 inclusive.

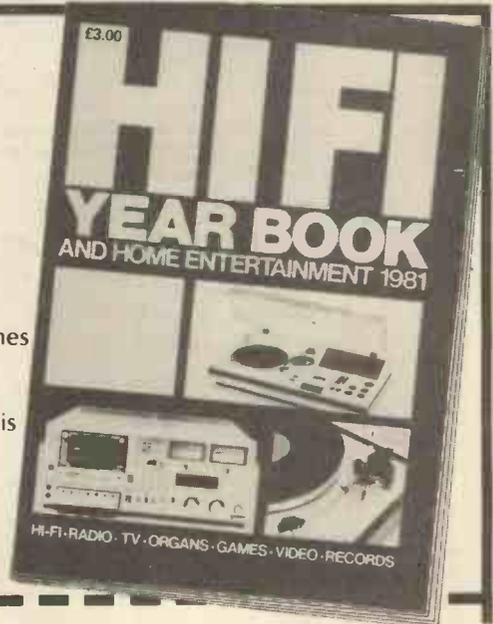General Sales Manager, Room 205, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS



ORDER FORM

To: General Sales Manager, Room 205, Quadrant
House, The Quadrant, Sutton, Surrey, SM2 5AS.

Please send me copy/copies of the Hi Fi
Yearbook and Home Entertainment 1981 @ £3.50
including postage and packing. Cheque/postal order
should be made payable to IPC Business Press Ltd.

Name _____
(please print)

Address _____

Registered in England No. 677128.

PE/1



When replying to Classified Advertisements please ensure:

- That you have clearly stated your requirements.
- That you have enclosed the right remittance.
- That your name and address is written in block capitals, and
- That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

RECEIVERS AND COMPONENTS

FLAT CABLE. Laminated, various sizes available. S.A.E. for list, Steve King, 61, Coldean Lane, Brighton, Sussex.

BRAND NEW COMPONENTS BY RETURN

Electrolytic Capacitors 18V, 25V, 50V.
 0.47, 1.0, 2.2, 4.7 & 10 Mfd. — 5p.
 22 & 47 — 5p. (50V — 6p), 100 — 7p. (50V — 8p).
 220 — 8p. (50V — 10p), 470 — 11p. (40V — 16p).
 1000/15p. 1000/25V — 18p. 1000/40V — 35p.

Subminiature bead Tantalum electrolytics.
 0.1, 0.22, 0.47, 1.0 & 35V, 4.7 & 6.3V — 14p.
 0.2/25V, 4.7/25V — 15p, 10/25V, 15/16V — 20p.
 22/16V, 33/10V, 47/6V, 68/3V & 100/3V — 30p.
 15/25V, 22/25V, 47/10V — 35p, 47/16V — 80p.

Subminiature Ceramic Caps. E12 Series 100V.
 2% 10 pf. to 47 pf. — 3p. 56 pf. to 330 pf. — 4p.
 10% 390 pf. to 4700 pf. — 4p.

Vertical Mounting Ceramic Plate Caps. 50V.
 E12 22 pf. to 1000 pf. E6 1500 pf. to 47000 pf. — 2p.

Polystyrene E12 Series 63V. Horizontal Mntg.
 10 pf. to 820 pf. — 3p. 1000 pf. to 10,000 pf. — 4p.

Miniature Polyester 250V Vert. Mtg. E6 Series.
 0.1 to 0.68 — 4p. 1 — 5p. 15, 22 — 6p. 33, 47 — 10p.
 .68 — 12p. 1.0 — 15p. 1.5 — 22p. 2.2 — 24p.

Mylar (Polyester) Film 100V. Vertical Mounting.
 .001, .0022, .0047 — 3p. .01, .022 — 4p. .04, .05, 0.1 — 5p.

Miniature Film Resistors Highest. E12 Ser. 5%.
 0.125W mixed carbon/metal 100 to 1MΩ — 1p.
 0.25W Carbon 1Ω to 10MΩ (10% over 1MΩ) — 1p.
 E24 Series av. in 1W C. Film 1Ω to 5MΩ (Q).
 0.25W, 0.5W & 1.0W Metal Film 100 to 2MΩ — 2p.
 1N4148 — 2p. 1N4002 — 4p. 1N4006 — 6p. 1N4007 — 7p.
 BC107/8/9, BC147/8/9, BC157/8/9, BF194 & 7 — 10p.
 8 Pin i.c.s. 741 Op. amp. — 18p. 555 Timer — 24p.
 DIL Holders 8 pin — 9p. 14 pin — 12p. 16 pin — 14p.
 LED's. 3 & 5mm. Red — 10p. Green & Yellow — 14p.
 Grommets for 3mm. — 1p. 2 pce. holders 5mm. — 2p.
 20mm. Q.B. Fuses. 15, 25, 5, 1, 2, 3 & 5A — 3p.
 20mm. Anti Surge 100mA. to 5.0A — 5p.
 20mm. Fuseholders P.C. or Chassis Mtg. — 5p.
 Solid A1. knobs 15mm. — 25p. 25mm. — 35p. 30mm. — 50p.
 400mW Zener diodes E24 series 2V7 to 33V — 8p.

Prices VAT Inclusive Post 15p. (Free over £5.00).

THE C. R. SUPPLY CO.

127, Chesterfield Rd., Sheffield S8 0RN.

BOURNEMOUTH/POOLE electronic components for the hobbyist, and friendly service. Why not pay us a visit, H & H Telelectrics Ltd., 353 Ashley Road, Parkstone, 742643.

YOUR OWN P.C.B.'s & FRONT PANELS EASILY MADE, NO COMPLICATED PROCESSES

Full details S.A.E.

Drafting packs: pcb £1.80; panel £2.25. Processing packs: pcb (3" x 4") £3.72, panel (5" x 6") £3.48. Drills, etchant, pcb board and all materials available.

WE ALSO SUPPLY R.S. QUALITY COMPONENTS

LYNWOOD ELECTRONICS

20, Stourcliffe Avenue,
Bournemouth, BH6 3PT.

TUNBRIDGE WELLS COMPONENTS, Ballard's, 108 Camden Road, Tunbridge Wells. Phone 31803. No Lists. Enquiries S.A.E.

SMALL ADS

The prepaid rate for classified advertisements is 24 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £8.00 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Electronics and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Practical Electronics, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

CLEARANCE PARCELS: Transistors, Resistors, Boards, Hardware, 10lbs only £5.80! 1,000 Resistors £4.25, 500 Capacitors £3.75. BC108, BC171, BC204, BC230, 2N5061, CV7497 Transistors 10 70p, 100 £5.80. 2N3055, 10 for £3.50. S.A.E. Lists: W.V.E. (2), 15 High Street, Lydney, Gloucestershire.

BOURNEMOUTH/BOSCOMBE. Electronic components specialists for 3 years. Forrester's (National Radio Supplies) Late Holdenhurst Rd. Now at 36, Ashley Rd., Boscombe. Tel. 302204. Closed Weds.

100 ASSORTED COMPONENTS 115p. 100 Assorted Resistors 60p. 100 Assorted capacitors 150p. 50 reed switches 200p. 10 mains neons 50p. 10 Micro switches 150p. Add 25p P&P. Durrants, 9 St. Mary's Street, Shrewsbury, Salop.

Electronic Components at very Low Prices

- * 32.768 KHz Watch Crystal £1.38 each
- * 25 KHz Ultrasonic Microphones: Transmitter/Receiver £2.56 per pair
- * 35 x 25 x 8 mm Microphone Insert
- Spec. Sensitivity — 58db at 1 KHz; Response 50-7 KHz; Capacity. 1.400pF £0.58p each.
- * 600 pf 500V — 20% Ceramic Caps £1.28 per 100.
- * 12V D.C. Coil Miniature Single Pole C/O Relay £1.15 each.

Minimum order value is £5

Post and Packing is 30p per order.

Send cheques or Postal order to:

IMPECTRON LTD.,
 Foundry Lane, Horsham,
 W. Sussex RH13 5PX.

TURN YOUR SURPLUS Capacitors, transistors, etc., into cash. Contact **COLES-HARDING CO.**, 103 South Brink, Wisbech, Cambs. 0945-4188. Immediate settlement.

MIXED. 100 transistors £3.50. 25 I.C.s £1.50. 100 Diodes £1. Post paid. Early radios. Valves. Interesting lists 15p. Sole Electronics. P.E. 37, Stanley Street, Ormskirk, Lancs. L39 2DH.

SERVICE SHEETS

SERVICE SHEETS from 50p and S.A.E. Catalogue 25p and S.A.E. Hamilton Radio, 47 Bohemia Road, St Leonards, Sussex.

G.T. TECHN. INFO. SERVICE

76 Church St, Larkhall, Lanarks ML9 1HE

Any single service sheet £1 + large SAE

1,000s of sheets/manuals always in stock.

Sole suppliers of all T.V. Repair Systems

Giant Diagram Manual for Washing Machines

Single tubs/twin tubs/auto — only £13.50

Repair Data any named T.V. £5.50 (with circuits, etc.

£7.00). SAE for newsletter, bargain offers etc.

Phone 0698 883334 after 4pm.

BELL'S TELEVISION SERVICES for Service Sheets on Radio, TV, etc £1.00 plus S.A.E. Colour TV Service Manuals on request. S.A.E. with enquiries to B.T.S. 190 Kings Road, Harrogate, N. Yorkshire, Tel: (0423) 55885.

SOFTWARE

UK101 SHORTHAND BASIC. Machine Code Program loaded from Basic enables a whole basic word to be typed one key (after command key). State old or new monitor and 8K or 4K memory size. Cassette and instructions for £5 + 30p P&P from P. P. Patay, 3 West View, Tandridge, Oxted, Surrey.

HP41C-PROGRAMMABLE CALCULATOR plus two memory modules and software. Five months old, the lot for £220. O.V.N.O. Telephone: Fareham 280642.

NOTICE TO READERS

Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser to check both prices and availability of goods before ordering from non-current issues of the magazine.

COMPUKIT SOFTWARE, Word Processor, Calendar Diary, Editor Mailing List, Line Renumber, 10000 Baud Cassette Routine etc. S.A.E. for details N. V. Davies, 11 Holloway, Haverfordwest, Dyfed.

INVASION. Exciting M/C game for UK101 with free pools predictor. Both use under 4K. Send £2.50 for tape to Mr. A. Pettitt, 2, Caburn View, Fittle, Lewes, Sussex.

OHIO SCIENTIFIC MEMORY test program from 2K to 48K in 1K blocks for basic in ROM versions. £1 for listing. SAE to K. Yeap, 71 North Grove, London N15.

THE ZX80 MAGIC BOOK £4.75

Edition 2, includes 15 plus programs, Music, Othello, Animals and others. Programming tips, Using USR. Hardware notes.

Timedata Ltd.,
 57, Swallowdale,
 Basildon,
 Essex.

ZX80 GAMES MAZE (1 & 11). Battleships, Pontoon, Slot machine, Maths quiz, Guess the Number. All on one cassette. Send £6.50 to P. Bramwell, 87, Anderson Crescent, Great Barr, Birmingham B43 7ST.

UK101 VIDE Hardware modification doubles video display giving 32 lines by 48 characters. BASIC writes to top 16 lines leaving bottom 16 lines for graphics etc. For detailed step by step instructions send £5 cheque or postal order to: D. Butler, 82 Banks Lane, Riddlesden, Keighley, W. Yorks.

EDUCATIONAL

CAREERS in Marine Electronics. Courses commencing September and January. Further details, The Nautical College, Fleetwood FY7 8JZ. Tel. 03917 79123.

CITY & GUILDS EXAMS

Study for success with ICS. An ICS homestudy course will ensure that you pass your C. & G. exams. Special courses for: Telecoms. Technicians, Electrical Installations, Radio, TV & Electronics Technicians, Radio Amateurs. Full details from:

ICS SCHOOL OF ELECTRONICS

Dept. 272B Intertext House, London SW8 4UJ

Tel. 01-622 9911 (all hours)

State if under 18

TECHNICAL TRAINING

Get the training you need to move up into a higher paid job. Take the first step now—write or phone ICS for details of ICS specialist homestudy courses on Radio, TV, Audio Eng. and Servicing, Electronics, Computers; also self-build radio kits. Full details from:

ICS SCHOOL OF ELECTRONICS

Dept. 272B Intertext House, London SW8 4UJ

Tel. 01-622 9911 (all hours)

State if under 18

COLOUR TV SERVICING

Learn the techniques of servicing Colour TV sets through new homestudy course approved by leading manufacturers. Covers principles, practice and alignment with numerous illustrations and diagrams. Other courses for radio and audio servicing. Full details from:

ICS SCHOOL OF ELECTRONICS

Dept. 272B Intertext House, London SW8 4UJ

Tel. 01-622 9911 (all hours)

State if under 18

SERVICE ENGINEERS

Take a look at Kodak



This is your opportunity to take a look at Kodak and find out about installing, maintaining and repairing an exciting range of equipment used in the photographic industry, including microfilers, processors and printers, on customers' premises throughout the U.K.

We are expecting a high standard from you. You will need a sound knowledge of practical electronics coupled with mechanical skills, preferably having had previous servicing experience. In return we can offer the rewards and promotion prospects expected when you join a large international company and potential earnings in the range £7,000 - £8,000 p.a. (under review) including some overtime,

allowances and company bonus plus plenty of attractive employee benefits.

We are looking for men or women aged 21 and over to join our teams of service engineers strategically placed around the U.K. to meet the service needs of our customers.

Full training on our equipment will be provided and on completion of training a Company vehicle is provided where it is needed to cover the territory.

Please write to Mr. C. Long, Personnel Department, A1t, Kodak Limited, P.O. Box 66, Station Road, Hemel Hempstead, Herts. HP1 1JU, giving details of education, experience and personal information.



Assistant Film Recordists

MANCHESTER

To work in sound transfer and dubbing areas operating sound recording and reproduction equipment for a wide range of programmes. Some mobile film recording work involved. Candidates must have professional experience and practical knowledge in this field, current driving licence and normal hearing.

Salary: £5,425-£6,725 p.a. (starting salary in accordance with qualifications and experience).

Candidates lacking experience may be considered for appointment as TRAINEES at a starting salary of £3,865 p.a.

Relocation expenses considered.

Contact us immediately for application form (quote ref. 2390/PE and enclose s.a.e.): **BBC** Appointments, London W1A 1AA. Tel. 01-580 4468 Ext. 4619.

BBC tv

Earn £20-£100 p.w. in your spare time

by introducing the revolutionary new Flip-Caller telephone to your friends. Features micro-chip controlled push-button dialling and memory re-call. Sells itself. Generous commission. For details write to Dept. 1P1

IDL SUPERPHONE

P.O. Box 31, Twickenham TW2 5NL



BOOKS AND PUBLICATIONS

ANY REQUESTED SERVICE SHEET £1 + Large S.A.E. Full repair data any named TV £5.50 (with circuits, layouts etc. £7). SAE brings newsletter, bargain offers, etc. AUSPEL, 76 Church St, Larkhall, Lanarks ML9 1HE.

MICROPROCESSORS. Application and reference manuals 8, 16 Bit. MOT T1 and AMD advanced micro device. SAE list. Steve King, 61, Coldean Lane, Brighton, Sussex.

FOR SALE

COMPUKIT UK101 8K. new monitor, built and cased, assembly tape etc. £300 o.n.o. Tel. 0280 702750.

30 NOTE ORGAN PEDAL BOARD solid oak, fully sprung £45. Eastleigh 619295.

BACK ISSUES: P.E. Vol 9 (bound), Vols 10, 11 (unbound). P.W. Vols 46, 47, 48 (bound) 49, (unbound). Television Vols 22, 23, (bound) 24, 25, (unbound). Offers please, Poynter, 26 Hanbury Close, Chesterfield, Derbyshire.

ACORN Microcomputer with edge connector, extra programs and monitor commentary. £50. Tel. 0277 822691.

COMPUKIT 4K ALIEN INVADERS CASSETTE £2.00. Steven Hall, 14, Christchurch Lane, Lichfield, Staffs.

NEW BACK ISSUES of 'Practical Electronics' available 90p each Post Free. Cheque or uncrossed p/o returned if not in stock - BELL'S TELEVISION SERVICES, 190 Kings Road, Harrogate. N. Yorks. Tel: (0423) 55885.

PLEASE
MENTION
PRACTICAL
ELECTRONICS
WHEN
REPLYING
TO
ADVERTISE-
MENTS

MISCELLANEOUS

VIDEO MUSIC

The amazing Videograph, as featured recently in Electronics Today International, links your Hi-Fi with any Colour TV to produce a Fantasia of hypnotic visual effects. The system displays stereo music as brilliantly coloured waveforms against an ever changing background. For the technically-minded, a square-wave signal generator is built-in, permitting advanced demonstrations of transient response etc. Truly the ultimate accessory for any Hi-Fi system!

DIY KIT ONLY £33.95
Case & Controls £15.95
or **READY BUILT £69.95**

All prices include VAT and postage

WILLIAM STUART SYSTEMS Ltd
Owler House, Billerica Road, Herongate, Brentwood, Essex CM13 3SD. Telephone: Brentwood (0277) 810244

OPTICAL FIBRES. Carry light. Tough, wire-like, excellent for communications, lighting, electrical isolation, etc. Introductory pack totals sixteen feet of four assorted types, plus illustrated guide. Send £3.55. Quantum Jump Ltd., 53, Marlborough Road, Tuebrook, Liverpool.

Cabinet and Flightcase Fittings

Fretcloths, Coverings, Handles, Castors etc., Jacks and Sockets, Cannons, Bulgins, Reverb Trays, Emilia Compression Drivers, AKG Mics, Celestion Speakers, ASS, Glassfibre Horns.

Send 30p Postal Order for illustrated catalogues to:-

ADAM HALL (P. E. SUPPLIES)

Unit G, Carlton Court, Grainger Road, Southend-on-Sea, Essex SS2 5BZ.

GUITAR/PA MUSIC AMPLIFIERS

100 watt superb treble/bass overdrive. 12 months guarantee. Unbeatable! £49; 60 watt £42; 200 watt £68; 100 watt twin channel sep. treble/bass per channel £62; 60 watt £52; 200 watt £78; 100 watt four channel sep. treble/bass per channel £75; 200 watt £98; slaves 100 watt £34; 200 watt £56; fuzz boxes, great sound £12.00; bass fuzz £12.50; overdriver fuzz with treble and bass boosters £22; 100 watt combo superb sound overdrive, sturdy construction, castors, unbeatable £98; twin channel £110; bass combo £112; speakers 15in. 100 watt £36; 12in. 100 watt £24; 60 watt £16; microphone Shure Unidyne B £25; 3-Channel sound/Alight £26.

Send cheque or P.O. to:

WILLIAMSON AMPLIFICATION

62 Thornclyffe Avenue, Dukinfield, Cheshire.
Tel: 061-308 2064

SUPERB INSTRUMENT CASES BY BAZELLI, manufactured from P.V.C. Faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range. Competitive prices start at a Low £1.05. Chassis punching facilities at very competitive prices. 400 models to choose from. Suppliers only to Industry & The Trade. BAZELLI (Dept. No. 23), St. Wilfrids, Foundry Lane, Halton, Lancaster, LA1 6LT.

RECHARGEABLE BATTERIES

TRADE ENQUIRIES WELCOME

FULL RANGE AVAILABLE. SAE FOR LISTS. £1.45 for Booklet "Nickel Cadmium Power" plus Catalogue. Write or call: Sandwell Plant Ltd., 2 Union Drive, BOLDMERE, SUTTON COLDFIELD, WEST MIDLANDS, 021-354 9764.

TEMPERATURE GAUGES. 0-120°C Black dial. Chrome bezel. Remote sensor on 38" capillary, Snap fitting in 55mm hole. £1.85 (incl. P&P) L.E.M. Services, 239, Rugby Road, Leamington Spa, Warwickshire. 0926-30622.

GLOBAL ELECTRONIC CONSTRUCTION KITS

Using the super radio chip Ferranti ZN414. This powerful little radio is ideal for the inexperienced constructor as it is so easy to build and operate. Makes a great pocket radio and works for months on a simple 1.5v battery. Complete with earpiece, ferrite rod aerial, tuning capacitor, volume control, ZN414 integrated circuit and one transistor for really super reception. Complete with ready drilled case size 105mm x 70mm x 40mm. All necessary parts to build the kit including baseboard and pictorial plans. Price £6.95, p&p 56p.

SUPER CHIP 2.
The same super radio as above, but has an LCZ414 plus two transistors added plus a loudspeaker to make a nice little pocket loudspeaker receiver. Also very easy to construct from the plans and parts supplied. Complete kit of parts including plans and ready drilled case 10mm x 75mm x 33mm. Price £8.25, p&p 65p.

Super AM/FM MW/Aircraft Radio. Ready built pocket receiver. Fully tested and operational. Price £10.25, p&p 60p.
Cheques and P.O.'s made payable to
GLOBAL ELECTRONIC ENTERPRISES
St. John's Works, St. John's, Bedford, Beds.
Free catalogue sent with order or 45p on request.

MK14 CORNER. Interface Board, includes flag driven mains relays, LED Indicators for all serial I/O, A/D and single step chips, and prototype area; also suitable for other Microcomputers; PCB and circuit £3.95. Replace calculator display with 1/2" FND 500's; PCB, filter instructions £1.95 Ready Built replacement Keyboard £11. Useul notes on MK14 75. Rayner, 'Kismet' High Street, Colnbrook, Bucks.

RYDER ORGAN SYSTEM REVERBERATION

A new design for organs gives smooth, natural sound. Demo r-to-r, or cassette, on loan, deposit £1.50, refund £1.00 (UK only).

HIYKON LTD. (P.),
Woodsie Croft, Ladybridge Lane,
Bolton BL1 5ED.

THE SCIENTIFIC WIRE COMPANY PO Box 30, London E.4

ENAMELLED COPPER WIRE

SWG	1lb	8oz	4oz	2oz
8 to 29	2.76	1.50	0.80	0.60
30 to 34	3.20	1.80	0.90	0.70
39	3.40	2.00	1.10	0.80
40 to 43	4.75	2.60	2.00	1.42
47	8.37	5.32	3.19	2.50
48 to 49	15.96	9.58	6.38	3.69

SILVER PLATED COPPER WIRE

14 to 30 6.50 3.75 2.20 1.40

TINNED COPPER WIRE

14 to 30 3.85 2.36 1.34 0.90


Prices include P&P, VAT and wire Data.

SAE for list. Dealer enquiries welcome.

Reg office 22 Coningsby Gardens.

NEAT! TIDY!
HANDY! 1D 2D 3D 6D

INTERLOCKING PLASTIC STORAGE DRAWERS

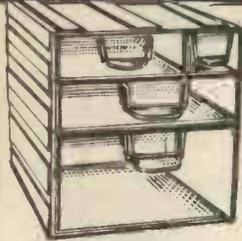

**AS SUPPLIED:
TO POST OFFICE
& GOVT DEPTS**

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units

interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. 1D and 2D have space dividers. Build up any size cabinet for wall, bench or table top.

SINGLE UNITS (1D) (5in+2½in+2½in) £4.90 DOZEN
DOUBLE UNITS (2D) (5in+4½in+2½in) £7.50 DOZEN
TREBLE (3D) £7.50 for 8.
DOUBLE TREBLE 2 drawers, in one outer case (6D2), £10.90 for 8.

Extra large size (6D1) £8.50 for 8.

PLUS QUALITY DISCOUNTS

Orders over £60, less 5%. Packing/Postage/Carriage: Add £1.30 to all orders under £10. Orders £10 and over, please add 10% carriage.

QUOTATIONS FOR LARGER QUANTITIES

Please add 15% V.A.T. to total remittance.

All prices correct at time of going to press.

**FLAIRLINE
SUPPLIES**

(PE12) 124 Cricklewood
Broadway, London
N.W.2. Tel: 01-450
4844.

£99 SYNTHESISER DIY. Professional results easy-build. SAE. Dewtron. 254 Ringwood Road, Ferndown, Dorset, BH22 9AR.

DIGITAL WATCH BATTERY REPLACEMENT KIT



These watches all require battery (power cell) replacement at regular intervals. This kit provides the means. We supply eyeglass, non-magnetic tweezers, watch screwdriver, case knife and screwback case opener, also one doz. assort. push pieces, full instructions and battery identification chart. We then supply replacement batteries—you fit them. Begin now. Send £9.00 for complete kit and get into a fast growing business. Prompt despatch.



**BOLSTER INSTRUMENT CO.
(PE19)**

11 Percy Avenue, Ashford, Middx. TW15 2PB.

AMAZING ELECTRONIC PLANS: Lasers—burning, cutting, rifle, light shows. Ultrasonic Force Fields—weaponry, satellite, T.V., giant tesla, split the atom; lots more. Catalogue 75p. Plan Centre, St John Street, Bridgnorth, Shropshire.

TIME RIGHT?

MSF CLOCK is ALWAYS CORRECT—never gains or loses, self setting at switch-on, 8 digits show Date, Hours, Minutes and Seconds, larger digit Hours and Minutes for easy QUICK-GLANCE time, auto GMT/BST and leap year, also parallel BCD output and audio to record and show time on playback, receives Rugby 60KHz atomic time signals, built-in antenna, 1000Km range, now ABSOLUTE ACCURACY, £54.80.

V.L.F. 7 EXPLORE 10-150KHz. Receiver £13.70.
60KHz RUGBY RECEIVER, as in MSF Clock, serial data and audio outputs, £15.70.

Each fun-to-build kit includes all parts, printed circuit, case, postage etc, money back assurance so GET one NOW.

CAMBRIDGE KITS

45 (FM) Old School Lane, Milton, Cambridge.

CLEARING LABORATORY: scopes, generators, P.S.U.'s, bridges, analysers, meters, recorders, etc. 0403-76236.

UK101

NASCOM 1 & 2

ADD-ON COLOUR SYSTEM



DAZZLING COLOUR GRAPHICS FOR UK101 & NASCOM

- Professional bit-addressable 'pixel' system
- 3072 colour cell definition
- 8 Colours foreground + 8 background
- FREE SOFTWARE: Plot, Line, Circle (Basic + Z80)
- Animated Demonstration Program
- Modulator Included for use with normal TV

KIT: only **£45** Built & Tested: only **£60**

Also available separately:

COLOUR MODULATOR

- R G B inputs, PAL/UFH output
- Unlimited colour combinations
- TTL etc interface details supplied
- 1000's already in use!



KIT: only **£12** Built & Tested: only **£18**

— please add VAT at 15% to all prices
— Barclay/Access orders accepted by telephone

**WILLIAM
STUART
SYSTEMS Ltd**

Dower House, Billericay Road,
Herongate, Brentwood,
Essex CM13 3SD. 
Telephone: Brentwood (0277) 810244

MAKE YOUR OWN PRINTED CIRCUITS
Etch Resist Transfers—Starter pack (5 sheets, lines, pads, I.C. pads) £2.00. Large range of single sheets in stock at 43p per sheet.

Master Positive Transparencies from P.C. layouts in magazines by simple photographic process. Full instructions supplied. 2 sheets (20 x 25cm) negative paper and 2 sheets (18 x 24cm) positive film £1.80. Drafting film (30 x 21cm) 22p per sheet.

17p stamp for lists and information. P & P 30p/order

P.K.G. ELECTRONICS
OAK LODGE, TANSLEY, DERBYSHIRE.

Readily available Hardware and Accessories for Home Constructors, Dev Engineers, Modelmakers. Selected range of quality components. Drawing materials for p.c. boards. Reliable resist coated epoxy glass laminate, no unusual chemicals. Printed circuit boards, top quality to personal designs, prompt service. Photography for p.c.b. Solid tungsten carbide drills. All immediately available. Catalogue 15p stamps please to:

RAMAR CONSTRUCTOR SERVICES,
Masons Rd. Stratford on Avon
Warwks. CV37, 9NF 0789-4879

BURGLAR ALARM EQUIPMENT. Latest Discount Catalogue out now! Phone C.W.A.S. Alarm 0274 682674.

PSYCHOTRONIC GENERATORS, gravity lasers, electrokinesis, electrophotography, skinvision. SAE 4x9" Paralab, Downton, Wilts.

PRACTICAL ELECTRONICS P.C.B.'s

- Apr. 80 Wire Train Controller EP320 £2.93
- May 80 Two Wire Train Controller EP326 £3.02
- EP328/30 £1.20 pair
- Dynamic Semiconductor Tester EG311/2 £1.83 pair
- MasterTune EP343 £3.80 (Not plated through)
- Greenhouse Temp. Control EP358 £1.90
- Jul. 80 Tape Slide Synch EG353 £1.28
- Sept. 80 DISCO deck EP365 £3.26
- Sound Gen. EC14 £2.53
- Oct. 80 Disco deck AE202 £3.11
- Cine frame Counter EG408 98p

For full list and current pcb's please send SAE. Pcb's also produced to customer's own masters. Trade enquiries welcomed. Please write for quota. CWO Please Postage.—Please add 30p postage and packing to complete order. Europe 65p.

PROTO DESIGN

14 Downham Road, Ramsden Heath
Billericay, Essex CM11 1PU
Telephone 0268-710722

CREED TELEPRINTED. 75R Mk 2 £55. ICL Keyboard 76 keys £25. Solartron scope CD78. 2 beam E.H.T. fault. £30 Variacs, all sizes. 01-669 4528.

SEEN MY CAT? 5000 Odds and ends. Mechanical. Electrical. Cat. free. Whiston Dept. PRE. New Mills, Stockport.

ULTRASONIC TRANSDUCERS. £2.85 per pair + 25p P&P. Dataplus Developments, 81 Cholmeley Road, Reading, Berks.

NATIONAL Personal Computer Users Association, 11 Spratling Street, Manston, Ramsgate, Kent (S.A.E. Details).

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Practical Electronics for

insertions. I enclose Cheque/P.O. for £

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Practical Electronics)

NAME

ADDRESS

Company registered in England. Registered No. 53626. Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS.

Send to: Classified Advertisement Manager
PRACTICAL ELECTRONICS
GMG, Classified Advertisements Dept., Room 2337,
King's Reach Tower, Stamford Street,
London SE1 9LS. Telephone 01-261 5846
Rate:
24p per word, minimum 12 words. Box No. 60p extra.

I.L.P. Toroidal

**TRANSFORMERS
IN A RANGE OF
75
TYPES**



We use advanced winding technology to make our toroidal transformers. They have only half the weight and height of their laminated equivalents and are appreciably more efficient. Our toroidals cost virtually the same as the older types which they are rapidly replacing. Induced hum is reduced by a factor of ten. Supplied with rigid mounting kit with centre bolt, steel and neoprene washers.

30VA 70mm dia. x 30mm Weight 0.45 Kg **£4.71**
(+£1.00 p.p. +0.86 VAT)

TYPE	SECONDARY RMS VOLTS	SECONDARY RMS CURRENT
1X010	6+6	2.50
1X011	9+9	1.66
1X012	12+12	1.25
1X013	15+15	1.00
1X014	18+18	0.83
1X015	22+22	0.68
1X016	25+25	0.60
1X017	30+30	0.50

50VA 80mm dia. x 35mm Weight 0.9 Kg **£5.19**
(+£1.10 p.p. +0.94 VAT)

2X010	6+6	4.16
2X011	9+9	2.77
2X012	12+12	2.08
2X013	15+15	1.66
2X014	18+18	1.38
2X015	22+22	1.13
2X016	25+25	1.00
2X017	30+30	0.83
2X028	110	0.45
2X029	220	0.22
2X030	240	0.20

80VA 90mm dia. x 30mm Weight 1 Kg **£5.76**
(+£1.20 p.p. +£1.04 VAT)

3X010	6+6	6.64
3X011	9+9	4.44
3X012	12+12	3.33
3X013	15+15	2.66
3X014	18+18	2.22
3X015	22+22	1.81
3X016	25+25	1.60
3X017	30+30	1.33
3X028	110	0.72
3X029	220	0.36
3X030	240	0.33

120VA 90mm dia. x 40mm Weight 1.2 Kg **£6.72**
(+£1.30 p.p. +£1.20 VAT)

4X011	9+9	6.66
4X012	12+12	5.00
4X013	15+15	4.00
4X014	18+18	3.33
4X015	22+22	2.72
4X016	25+25	2.40
4X017	30+30	2.00
4X028	110	1.09
4X029	220	0.54
4X030	240	0.50

160VA 110mm dia. x 40mm Weight 1.8 Kg **£8.88**
(+£1.40 p.p. +£1.54 VAT)

TYPE	SECONDARY RMS VOLTS	SECONDARY RMS CURRENT
5X012	12+12	6.66
5X013	15+15	5.33
5X014	18+18	4.44
5X015	22+22	3.63
5X016	25+25	3.20
5X017	30+30	2.66
5X018	35+35	2.28
5X028	110	1.45
5X029	220	0.72
5X030	240	0.66

225VA 110mm dia. x 45mm Weight 2.2 Kg **£10.59**
(+£1.50 p.p. +£1.81 VAT)

6X014	18+18	6.25
6X015	22+22	5.11
6X016	25+25	4.50
6X017	30+30	3.75
6X018	35+35	3.21
6X026	40+40	2.81
6X028	110	2.04
6X029	220	1.02
6X030	240	0.93

300VA 110mm dia. x 50mm Weight 2.6 Kg **£12.27**
(+£1.60 p.p. +£2.08 VAT)

7X016	25+25	6.00
7X017	30+30	5.00
7X018	35+35	4.28
7X026	40+40	3.75
7X025	45+45	3.33
7X028	110	2.72
7X029	220	1.36
7X030	240	1.25

500VA 140mm dia. x 60mm Weight 4 Kg **£16.35**
(£1.70 p.p. +£2.71 VAT)

8X017	30+30	8.33
8X018	35+35	7.14
8X026	40+40	6.25
8X025	45+45	5.55
8X033	50+50	5.00
8X028	110	4.54
8X029	220	2.27
8X030	240	2.08

● I.L.P. TOROIDAL TRANSFORMERS ARE GUARANTEED FOR 5 YEARS

CHOICE OF 3 PRIMARY INPUTS

I.L.P. Toroidal Transformers are available in choice of 110V, 220V, 240V, coded as follows: (Secondaries can be connected in series or parallel)

For 110V Primary insert 0 in place of "X" in type number.
For 220V Primary (Europe) insert 1 in place of "X" in type number.
For 240V Primary (U.K.) insert 2 in place of "X" in type number.

Example - 120VA 240V 15+15V. 4A = 42013.

* CUSTOMER DESIGN ENQUIRIES INVITED.
QUANTITY PRICE LIST AVAILABLE.

FREEPOST facility.(U.K. only).

Simply address envelope to **FREEPOST** to address below. **NO STAMP REQUIRED.**

TO ORDER Enclose cheque/Postal Order/Money Order payable to I.L.P. Electronics Ltd or quote your **ACCESS** or **BARCLAYCARD** account No. To pay C.O.D. add £1 extra to **TOTAL** value of order. Also available from **ELECTROVALUE** and **MARSHALLS**.

I.L.P. TRANSFORMERS
A division of I.L.P. ELECTRONICS LTD.
FREEPOST T2 GRAHAM BELL HOUSE ROPER CLOSE
CANTERBURY CT2 7EP

Phone (0227) 54778. Technical (0227) 64723. Telex 965 780

TUNE IN to the new-look

DECEMBER 1980

Practical Wireless

65p

ree
TWEEZERS

'TWINHAM'
analogue/digital
multimeter
Part 1

'FIRST YL'
VOLUME 56
YAESU
RECEIVER

FREE
all-purpose

WORKSHOP TWEEZERS

● THE FIRST YL

One of the most active of the early amateur YL operators was Barbara Dunn 6YL (later G6YL), who was involved in monitoring the famous Southern Cross on its transatlantic flight 50 years ago. Ron Ham recounts 6YL's achievements.

● PW 'TWINHAM' ANALOGUE DIGITAL MULTIMETER

Combining two instruments seems an attractive idea - until you want to measure, say, voltage and frequency together. The PW 'Twinham' is a mains-powered multimeter which gives you simultaneous analogue and digital readouts for both accuracy and trendwatching. Full instructions are given for making this useful device.

PRACTICAL WIRELESS

December issue OUT NOW 65p

INDEX TO ADVERTISERS

Ace Mailtronix	22
Adam Hall (P.E. Supplies)	92
Altken Bros	58
Alcon	88
Audio Elec	84
Aura	81
Barrie Electronics	79
BBC Appointments	92
BIB Hi-Fi Accessories	69
Bi-Pak	70-71
Birkett J.	85
Bolster Instruments Co	93
Boss Industrial Mouldings	85
British National Radio & Electronics School	15
Butterworths	78
Cambridge Kits	93
Cambridge Learning	5
Chromasonic Electronics	72, 73
Chromatronics	22
Clef Products	74
Codespeed	4
Commodore	51
Computech	14
Computer Components (Teleplay)	Cover II
Continental Spec.	79, 88
Crofton Electronics	10
C.R. Supply Co.	90
Doram	85
E.D.A.	73
Electronic Mail Order	86
Electrovalve	86
Fladar	80
Flairline Supplies	93
Global	92
GMT	87
GT Technical Information Service	90
Heathkit	10
Hi-Fi Year Book	89
Hiykon Ltd	92
Home Radio	74
House of Instruments	87
I.C.S. Intertex	7, 90
I.L.P. Electronics	82, 83, 94
Impectron Ltd.	90
Intercity Distributors	92
Interface Components	74
Jayen Developments	4
Keelmoor	76, 77
Kodak Ltd.	91
L & B Electronics	78
Lynwood Electronics	90
MacIn-Zand	4
Maplin Electronics	Cover IV
Marshall, A.	14
Micro Circuits	11
Midland Trading	11
Mighty Micro	89
Modern Book Co	96
Modus Systems	86
Monolith	74
Parndon	22
Philips	63
Phonosonics	6, 7
PKG Electronics	93
Progressive Radio	86
Proto Design	93
Radio Component Specialists	95
Radio & T.V. Components	16
Ramar Constructor Service	93
Rapid Electronics	58
Riscomp Ltd	58
Sandwell Plant Ltd.	92
Saxon Entertainments	10
Science of Cambridge	12, 13
Scientific Wire Co	92
Service Trading	Cover III
Sentinel Supply	78
Stevenson	88
Suretron	84
Swanley Electronics	80
Tandy	8, 9
Tempus	75
Timedata Ltd	90
Titan	14
T.K. Electronics	80
Technomatic	96
Vero	3
Videozone	20
Watford Electronics	2, 3
Williamson Amplification	92
William-Stuart Systems	92, 93
Wilmslow Audio	22

VIDEOTEX

— the new television —

telephone information services
by R. Woolfe price: £8.00

ELECTRONIC TEST EQUIPMENT CONSTRUCTION
by F. G. Rayer price: £2.00

ELECTRONIC MUSIC SYNTHESIZERS
by D. T. Horn price: £4.00

POWER SUPPLY PROJECTS
by R. A. Penfold price: £2.00

99 PRACTICAL ELECTRONIC projects
by H. Friedman price: £3.60

1001 THINGS TO DO WITH YOUR PERSONAL COMPUTER
by M. Sawusch price: £5.75

LC CIRCUITS
by R. P. Turner price: £4.15

DESIGN OF TRANSISTOR CIRCUITS WITH EXPERIMENTS
by Dr. K. A. Pullen, Jr. price: £9.40

THE MASTER IC COOKBOOK
by C. L. Hallmark price: £7.00

RADIO & T.V. SERVICING 1979/80 MODELS
by R. N. Wainwright price: £15.60

ALL PRICES INCLUDE POSTAGE

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST
of British and American Technical Books

19-21 PRAED STREET
LONDON W2 1NP

Phone 01-402 9176
Closed Saturday 1 p.m.

PLEASE MENTION PRACTICAL ELECTRONICS

When replying to Advertisements

BAKER 50 WATT AMPLIFIER £69

Post £2



Superior quality ideal for Halls/PA systems. Disco's and Groups. Two inputs with Mixer Volume Controls. Master Bass. Treble and Gain Controls. 50 watts RMS. Three loudspeakers outlets 4, 8, 16 ohm. AC 240V (120V available). White wording on black cabinet.

BAKER 150 Watt AMPLIFIER 4 Inputs £89
DRILL SPEED CONTROLLER/LIGHT DIMMER KIT. Easy to build kit. Controls up to 480 watts AC mains. Printed Circuit. £3

DELUXE MODEL R ready built. 800 watts £4
STEREO PRE-AMP KIT. All parts to build this pre-amp. 3 inputs for high medium or low gain per channel, with volume control and P.C. Board. Can be ganged to make multi-way stereo mixers. £2-95

R.C.S. SOUND TO LIGHT DISPLAY MK 2

Complete kit of parts with R.C.S. printed circuit. Three channels. Up to 1,000 watts each. Will operate from 200MV to 100 watts signal source. Suitable for home Hi-Fi and all Disco Amplifiers. Cabinet extra £4.50. Post 50p
200 Watt Rear Reflecting White Light Bulbs. Ideal for Disco Lights. Edison Screw 75p each or 6 for £4. or 12 for £7.50.

MAINS TRANSFORMERS Primary 240V A.C. ALL POST 99p
250-0-250V 70mA. 6-3V 2A..... £3-45
250-0-250V 80mA. 6-3V 3-5A. 6-3V 1A..... £4-60
330-0-330V 200mA. 6-3V 3A+6-3V 2A+6-3V 2A..... £12-00
300-0-300V 120mA. 2x6-3V 2A C.T.: 5V 2A..... £10-00
220V 45mA. 6-3V 2A..... £2-50

GENERAL PURPOSE LOW VOLTAGE.
Tapped outputs available
2 amp 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 25 and 30V..... £6-00
1 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60..... £6-00
2 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60..... £9-50
3 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60..... £12-50
5 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60..... £16-00
6V, 500mA..... £2-00
12V, 100mA..... £1-30
12V, 750mA..... £1-75
10-0-10V 2 amp..... £3-00
30V, 5 amp and 17V-0-17V..... £3-25
2 amp..... £4-00
0-5, 8, 10, 16V, 1 amp..... £2-50
9V, 3 amp..... £3-50
15-0-15v 2 amp..... £3-75
30V, 2 amp..... £3-50
30V, 1 1/2 amp..... £3-30
6-0-6V, 100mA..... £1-50
20V, 40V, 60V, 1 amp..... £4-00
12V, 3 amp..... £3-50
10V, 30V, 40V, 2 amp..... £3-50
12V, 2 amp..... £3-25
20V, 1 amp..... £3-00
30V, 0-30V, 2 amp..... £8-00
2 of 18V, 6 amp, each..... £11-00
12-0-12V, 2 amp..... £3-50
9V, 1 amp..... £1-50

AUTO TRANSFORMERS 115V to 240V 500W £10.00
CHARGER TRANSFORMERS - CHARGER RECTIFIERS
6-12V-3a..... £4.00
6-12V-4a..... £6.50
6-12V-2a..... £1.00
6-12V-4a..... £2.00

R.C.S. LOUDSPEAKER BARGAINS

3 ohm. 6x4in. £1-50. 7x4in. £1-50. 8x5in. £2-50. 6 1/2in. £2-20. 8in. £2-60. 10in. £3-50. 12in. £4-50.
8 ohm. 2 1/2in. £1-50. 3in. £1-50. 5in. £2-20. 8in. £2-60. 10in. £3-50. 12in. £4-50. 16 ohm 6 x 4in. £1-50. 7 x 4in. £1-50. 5in. £1-50. 8in. £3-10in. £3-50. 12in. £4-50. 10 x 6in. £3-50.

R.C.S. LOW VOLTAGE STABILISED POWER PACK KITS 90-100 mA Post 50p £2-95

All parts and instructions with Zener diode printed circuit, rectifiers and double wound mains transformer in input 200-240 a.c. Output voltages available 6 or 7.5 or 9 or 12V d.c. up to 100mA. State voltage.


PP BATTERY ELIMINATOR. BRITISH MADE
Mains power pack 9 volt 400 ma stabilised, with overload protection. Size 2x3 1/2 x 2 1/2 price £4.50 post 50p.

THE "INSTANT" BULK TAPE ERASER
Suitable for cassettes, and all sizes of tape reels.
A.C. mains 200/240V.
Leattel S.A.E. £7-50 Post 50p



HEAD DEMAGNETISER PROBE £5-00

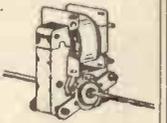A.C. ELECTRIC MOTORS POST 50p.
2 Pole, 240V, .2 Amp. Spindle - 1-4 x 0-212in. £1-75. 2 pole, 240V, .15 Amp. Double spindle - 1-75 x 0-16in. Each £1-50. 2 Pole, 120V, .5 Amp. Spindle - 0-75 x 0-2in. Two in series=240V. 75p each. Brush Motor. From a Food Mixer 240V, .3 Amp. High Speed and Powerful. Spindle - 0-5 x 0-25in. £2-95



BLANK ALUMINIUM CHASSIS, 18 s.w.g. 2 1/2in. sides. 6 x 4in. 95p.
8 x 6in. £1-40. 10 x 7in. £1-55. 14 x 9in. £1-90. 16 x 6in. £1-85. 12 x 3in. £1-20. 16 x 10in. £2-20. 12 x 8in. £1-70.

ALUMINIUM PANELS, 18 s.w.g. 6 x 4in. 24p. 6 x 6in. 38p.
10 x 7in. 54p. 12 x 5in. 44p. 12 x 8in. 70p. 16 x 6in. 70p. 14 x 9in. 94p. 12 x 12in. £1. 16 x 10in. £1.16.
ALUMINIUM ANGLE BRACKETS 6 x 1/2 x 1/2in. 25p.
ALUMINIUM BOXES, MANY SIZES IN STOCK.
4 x 2 x 2in. £1.00. 3 x 2 x 1in. 80p. 6 x 4 x 3in. £1.30. 8 x 6 x 3in. £2.10. 12 x 5 x 3in. £2.30. 6 x 4 x 3in. £1.60. 10 x 7 x 3in. £2.50.

HIGH VOLTAGE ELECTROLYTICS
8/800V.....£1-20
50/500V.....£1-20
16/500V.....75p
32/500V.....75p
50/500V.....£1-20
220/450V.....95p
8+16 450.....75p
32+32/350V.....50p
50+50/500V.....£1-80
40+80/500V.....£2
16+32+32/500V.....£2

DE LUXE BSR HI-FI AUTOCHANGER

Plays 12in., 10in., or 7in records
Auto or Manual. A high quality unit backed by BSR reliability with 12 months guarantee. A.C. 200/250V. Size 13 1/2 x 11 1/2in. Above motor board 3 1/2in. Below motor board 2 1/2in. With CERAMIC STEREO CARTRIDGE



BSR Single Player P207 cueing device, ceramic cartridge. £15

Garrard Single Player 6-200 metal turntable, cueing device, aluminium arm. Stereo cartridge. £22

BSR P182 Snake arm, flared Aluminium Turntable ADC QLM30 Magnetic Cartridge. £30

B.S.R. Auto Changer. 11in. Turntable. Budget price. £17-50
Stereo ceramic, reliable unit, 3-speed.

R.C.S. Disco Deck 3 speed stereo £9-95 or £18 pair
Rapid Mail Order 50p minimum postage. Callers Welcome. Access- Visa. Lists 20p. Closed Wed.

Radio Components Specialists
337, WHITEHORSE ROAD
CROYDON, SURREY, U.K. TEL: 01-684 1665.

TTLs by TEXAS	74180 93p	4000 SERIES	93 SERIES	VEROBARD	TRANSISTORS	*BFR80 25p	*IP33A 50p	*2N3708/7 10p	*DIODES	*ZENEERS
7400 11p	74181 80p	4000 18p	9301 160p	0.1	AC126 25p	TIP33C 11p	*2N3773 300p	*BY127 9p	*2N7 9p	2.7V 33V 8p
7401 12p	74184A 150p	4001 22p	9302 175p	(copper clad)	AC176 25p	TIP33A 115p	*2N3819 25p	*OA81 15p	*OA7 9p	400mW 9p
7402 12p	74185 150p	4002 20p	9308 316p	21 x 3 1/2 65p	AC187 25p	BFX30 30p	*2N3820 50p	*OA85 15p	*OA8 15p	1W 15p
7403 15p	74186 500p	4006 95p	9310 275p	3 1/2 x 5 75p	AF116/7 50p	BFX84/5 30p	*2N3820 50p	*OA90 9p	*OA9 9p	
7404 14p	74186 500p	4007 25p	9311 160p	3 1/2 x 3 1/2 75p	AD149 70p	BFX88/7 30p	*2N3866 90p	*OA91 9p		
7405 60p	74190 90p	4008 80p	9312 160p	2 1/2 x 1 1/2 320p	AD161/2 45p	BFX88 30p	*2N3866 90p	*OA95 9p		
7406 36p	74192 90p	4009 40p	9314 165p	3 1/2 x 1 1/2 410p	AU107 250p	BFY50 30p	*2N3906/2 20p	*OA95 9p		
7407 35p	74193 90p	4010 50p	9316 225p	3 1/2 x 1 1/2 410p	BC107/8 11p	BFY51/2 30p	*2N4037 65p	*OA202 10p		
7408 17p	74194 90p	4012 15p	9322 150p	3 1/2 x 1 1/2 410p	8C109 11p	BFY90 90p	*2N4058/9 12p	*IN194 4p		
7409 19p	74195 95p	4013 50p	9334 340p	Spot face cutler/5p	*BC117 20p	BRV39 45p	*2N4060 12p	*IN196 7p		
7410 15p	74196 95p	4014 84p		Pin insertion	*BC147/8 9p	TIP295 75p	*2N4061/2 18p	*IN148 4p		
7411 24p	74198 150p	4015 84p	LINEAR I.C.s	tool 99p	BC149 10p	TIP295 75p	*2N4123/4 27p	*IN4001/2 5p		
7412 20p	74199 150p	4016 45p	*AY1-0212 600p	VERO WIRING	*BC151/8 11p	TIP295 75p	*2N4126/7 27p	*IN4003/4 5p		
7413 30p	74200 150p	4017 70p	*AY1-1313 668p	Plus spool 325p	*BC151/9 11p	TIP295 75p	*2N4126/7 27p	*IN4005 6p		
7414 40p	74221 160p	4018 89p	*AY1-1320 320p	(Wire spool 80p)	*BC159 11p	TIP295 75p	*2N4126/7 27p	*IN4006 6p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p	Combes 7p each	*BC169C 12p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC172 12p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC172/7 12p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC182/3 10p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC184 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187 30p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/12 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/13 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/14 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/15 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/16 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/17 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/18 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/19 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/20 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/21 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/22 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/23 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/24 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/25 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/26 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/27 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/28 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/29 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/30 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/31 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/32 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/33 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/34 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/35 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/36 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/37 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/38 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/39 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/40 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/41 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/42 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/43 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/44 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/45 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/46 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/47 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/48 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/49 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/50 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/51 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/52 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/53 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/54 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/55 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/56 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/57 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/58 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/59 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/60 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/61 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/62 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/63 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/64 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/65 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/66 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/67 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/68 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/69 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/70 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/71 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		
7414 30p	74221 160p	4018 89p	*AY1-1320 320p		*BC187/72 11p	TIP295 75p	*2N4126/7 27p	*IN4007 7p		

The new MAPLIN CATALOGUE is out on December 5th

A massive new catalogue from Maplin that's bigger and better than ever before. If you ever buy electronic components this is the one catalogue you must not be without. Over 300 pages, it's a comprehensive guide to electronic components with thousands of photographs and illustrations and page after page of invaluable data. We stock just about every useful component you can think of. In fact, well over 5000 different lines, many of them hard to get from anywhere else. Hundreds and hundreds of fascinating new lines, more data, more pictures and a new layout to help you find things more quickly.

MAPLIN

Maplin Electronic Supplies Ltd.
 All mail to: P.O. Box 3, Rayleigh, Essex SS6 8LR.
 Telephone: Southend (0702) 554155. Sales (0702) 552911.
 Shops:
 159-161 King Street, Hammersmith, London W6. Telephone: (01) 748 0926.
 284 London Road, Westcliff-on-Sea, Essex. Telephone: Southend (0702) 554000.
 Both shops closed Mondays.



On sale
 in all branches
 of W H Smith
 from Dec 5th
 price £1

Breadboard 1980
 26th to 30th November
 Open 10 a.m. till 6 p.m. (and till 8 p.m. Thursday, 4 p.m. Sunday)
 Royal Horticultural Halls,
 Elverton Street, London
 (Nr. St. James's Park Underground)
 Visit our huge stand and see our new 'single-chip' organ, a new sequencer/composer, and lots more. Don't miss it!!

Post this coupon now for your copy of our 1981 catalogue price £1.
 Please send me a copy of your 320 page catalogue. I enclose £1 (Plus 25p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the UK send £1.68 or 12 International Reply Coupons.
 I enclose £1.25

Name _____

Address _____

12 5mm