

Australia \$1.10 New Zealand \$1.20 Malaysia \$4.50

PRACTICAL

# ELECTRONICS

APRIL 1981

65p

## PE DIGISOUNDER



### **SPEECH PROCESSOR**

Adds talk power.... aids intelligibility

### **ULTRASONIC INTRUDER ALARM**

Doppler shift system....easy installation

## THE ATARI VIDEO COMPUTER GAMES SYSTEM

Atari's Video Computer System now offers more than 1300 different game variations and options in twenty Game Program™ cartridges!

**Most Cartridges only £13.90 + VAT**  
**Prices may vary with special editions** Basic Maths, Airsea Battle, Black Jack, Breakout, Surround, Spacewar, Video Olympics, Outlaw, Basketball, Hunt & Score™, Space War, Sky Diver, Air Sea Battle, Codebreaker™, Miniature Golf.

Extra Paddle Controllers — £14.90 + VAT  
 Keyboard Controllers — £16.90 + VAT

**SPACE INVADERS NOW IN STOCK £25**

**EXTENDED WARRANTY BY COMPLIANCE**

only **£325** + VAT



**TRS80 LEVEL 2 16K**

Fully converted to UK TV Standard. Comes complete with easy to follow manuals, UK Power Supply, Cassette leads, Sample tapes. Special box to enable you to plug into your own TV. Recommended for first time buyers. Just plug in and go.

Full Range of Software Available

Interface to Centronics Parallel for TRS80 **£75.00 + VAT**

only **£295** + VAT



**TRS80 EXPANSION INTERFACE**

Expand your TRS80 to 32K  
 32K Memory on board  
 Centronics parallel port  
 Disk controller card  
 Real-time clock. Requires Level 2 Basic. Interface for 2 cassette decks complete with power supply.

## THE VIDEO GENIE SYSTEM

Ideal for small businesses, schools, colleges, homes, etc. Suitable for the experienced, inexperienced, hobbyist, teacher, etc.

**EG3000 Series**

**WITH NEW EXTRA KEYS!**

**16K £299** + VAT

• 16K user RAM plus extended 12K Microsoft BASIC in ROM • Fully TRS-80 Level II software compatible • Huge range of software already available • Self contained, PSU, UHF modulator, and cassette • Simply plugs into video monitor or UHF TV • Full expansion to disks and printer • Absolutely complete — just fit into mains plug

**EXTENDED WARRANTY BY COMPLIANCE**

## NASCOM 2 GAMES TAPE £7.50

featuring Space Invaders and Android Nim, Re-numbering program and other goodies! + VAT

## SPECIAL SCOOP GET YOURSELF A PRINTER FOR YOUR PET AND SAVE A FORTUNE

only **£299** + VAT

Interface Cards for Apple, Pet, TRS80, Nascom and CompuKit — **£49 + VAT**

Full Pet Graphics including cables. Ready to go **EX-STOCK.**

**EXTENDED WARRANTY BY COMPLIANCE**

We give a full one year's guarantee on all our products.

Send £1 and S.A.E. for the **1981 SPRING CATALOGUE**

## HITACHI PROFESSIONAL MONITORS

9" — ~~£129~~ **£99.95**  
 12" — ~~£199~~ **£149**

- Reliability Solid state circuitry using an IC and silicon transistors ensures high reliability
- 500 lines horizontal resolution Horizontal resolution in excess of 500 lines is achieved in picture center
- Stable picture Even played back pictures of VTR can be displayed without jittering
- Looping video input Video input can be looped through with built-in termination switch
- External sync operation (available as option for U and C types)
- Compact construction Two monitors are mountable side by side in a standard 19-inch rack

**EXTENDED WARRANTY BY COMPLIANCE**

## EUROPE'S FASTEST SELLING ONE BOARD COMPUTER COMPUKIT UK101

- ★ 6502 based system — best value for money on the market.
- ★ Powerful 8K Basic — Fastest around
- ★ Full Qwerty Keyboard
- ★ 4K RAM Expandable to 8K on board.
- ★ Power supply and RF Modulator on board.
- ★ No Extras needed — Plug-in and go.
- ★ Kansas City Tape interface on board
- ★ Free Sampler Tape including powerful Disassembler and Monitor with each Kit.
- ★ If you want to learn about Micros, but didn't know which machine to buy then **this is the machine for you.**

**40 pin Expansion Jumper Cable** for CompuKit expansion **£8.50 + VAT**

Build, Understand and Program your own Computer for only a small outlay.

**KIT ONLY £179 + VAT**  
**NO EXTRAS NEEDED**

Available ready assembled, tested & ready to go **£229 + VAT**

**NEW MONITOR FOR COMPUKIT UK101**

- In 2K Eprom 2716
- Allows screen editing
- Saves data on tape
- Flashing cursor
- Text scrolls down

**£22.00 + VAT**  
**Special Bonus SAVE £22.** New Super Monitor inc. in each kit or sold separately for **£22 + VAT**

FOR THE COMPUKIT	Game Packs	Super Space Invaders (8K)	£8.50
Assembler/Editor <b>£14.90</b>	1 Four Games <b>£5.00</b>	Space Invaders	<b>£5.00</b>
Screen Editor Tape <b>£5.90</b>	2 Four Games <b>£5.00</b>	Chequers	<b>£3.00</b>
	3 Three Games 8K only <b>£5.00</b>	Real Time Clock	<b>£3.00</b>
		Case for CompuKit	<b>£29.50</b>

All Prices exclusive VAT

## NEW REDUCED PRICES

8K **£399**  
 16K **£449**  
 32K **£499**

RRP £795 for 32K

**The PEDIGREE PETS**

Very popular for home & business use. 8K, 16K, 32K, 64K, 128K, 256K, 512K, 1024K, 2048K, 4096K, 8192K, 16384K, 32768K, 65536K, 131072K, 262144K, 524288K, 1048576K, 2097152K, 4194304K, 8388608K, 16777216K, 33554432K, 67108864K, 134217728K, 268435456K, 536870912K, 1073741824K, 2147483648K, 4294967296K, 8589934592K, 17179869184K, 34359738368K, 68719476736K, 137438953472K, 274877906944K, 549755813888K, 1099511627776K, 2199023255552K, 4398046511104K, 8796093022208K, 17592186044416K, 35184372088832K, 70368744177664K, 140737488355328K, 281474976710656K, 562949953421312K, 1125899906842624K, 2251799813685248K, 4503599627370496K, 9007199254740992K, 18014398509481984K, 36028797018963968K, 72057594037927936K, 144115188075855872K, 288230376151711744K, 576460752303423488K, 1152921504606846976K, 2305843009213693952K, 4611686018427387904K, 9223372036854775808K, 18446744073709551616K, 36893488147419103232K, 73786976294838206464K, 147573952589676412928K, 295147905179352825856K, 590295810358705651712K, 1180591620717411303424K, 2361183241434822606848K, 4722366482869645213696K, 9444732965739290427392K, 18889465931478580854784K, 37778931862957161709568K, 75557863725914323419136K, 151115727451828646838272K, 302231454903657293676544K, 604462909807314587353088K, 1208925819614629174706176K, 2417851639229258349412352K, 4835703278458516698824704K, 9671406556917033397649408K, 19342813113834066795298816K, 38685626227668133590597632K, 77371252455336267181195264K, 154742504910672534362390528K, 309485009821345068724781056K, 618970019642690137449562112K, 1237940039285380274899124224K, 2475880078570760549798248448K, 4951760157141521099596496896K, 9903520314283042199192993792K, 19807040628566084398385987584K, 39614081257132168796771975168K, 79228162514264337593543950336K, 158456325028528675187087900672K, 316912650057057350374175801344K, 633825300114114700748351602688K, 1267650600228229401496703205376K, 2535301200456458802993406410752K, 5070602400912917605986812821504K, 10141204801825835211973625643008K, 20282409603651670423947251286016K, 40564819207303340847894502572032K, 81129638414606681695789005144064K, 162259276829213363391578010288128K, 324518553658426726783156020576256K, 649037107316853453566312041152512K, 1298074214633707107132624082305024K, 2596148429267414214265248164610048K, 5192296858534828428530496329220096K, 10384593717069656857060992658440192K, 20769187434139313714121985316880384K, 41538374868278627428243970633760768K, 83076749736557254856487941267521536K, 166153499473114509712975882535042672K, 332306998946229019425951765070085344K, 664613997892458038851903530140170688K, 1329227995784916077703807060280341376K, 2658455991569832155407614120560682752K, 5316911983139664310815228241121365504K, 10633823966279328621630456482242731008K, 21267647932558657243260912964485462016K, 42535295865117314486521825928970924032K, 85070591730234628973043651857941848064K, 170141183460469257946087303715883696128K, 340282366920938515892174607431767392256K, 680564733841877031784349214863534784512K, 13611294676837540635686984297270695681024K, 27222589353675081271373968594541391248256K, 5444517870735016254274793718908278248512K, 10889035741470032508549587437816556497024K, 21778071482940065017099174875633112994048K, 43556142965880130034198349751266225988096K, 87112285931760260068396699502532451976192K, 17422457186352052013679339900506490354304K, 34844914372704104027358679801012980708608K, 69689828745408208054717359602025961417216K, 13937965749081641610943471920405192284432K, 27875931498163283221886943840810384568864K, 55751862996326566443773887681620771137728K, 11150372599265313288754777536324154551552K, 22300745198530626577509555072648309103104K, 44601490397061253155019110145296618206208K, 89202980794122506310038220290593236412416K, 178405961588245012620076440581186472824832K, 356811923176490025240152881162372945649664K, 713623846352980050480305762324745891299328K, 1427247692705960100960611524649491782598656K, 2854495385411920201921223049298983565197312K, 5708990770823840403842446098597967130394624K, 1141798154164768080768489219719593426078928K, 2283596308329536161536978439439186852157856K, 4567192616659072323073956878878377044355712K, 9134385233318144646147913757756754088711424K, 18268770466636289292295827515513508177422848K, 3653754093327257858459165503102701634885792K, 730750818665451571691833100620540326971584K, 1461501637330903143383666201241080653943168K, 2923003274661806286767332402482161307886336K, 5846006549323612573534664804964322615772704K, 11692013098647225147069329699928645231545408K, 23384026197294450294138659399857290463090816K, 467680523945889005882773187997145809261821328K, 935361047891778011765546375994291618523642656K, 1870722095783556023531092751988583237047285312K, 3741444191567112047062185503977166474094570624K, 7482888383134224094124371007954332941889141248K, 1496577676626844818824874201590866588377828256K, 299315535325368963764974840318173317675565552K, 59863107065073792752994968063634663535111104K, 119726214130147585505989936127269327070222208K, 239452428260295171011979872254538654140444416K, 478904856520590342023959744509077308280888832K, 957809713041180684047919489018154616561777664K, 191561942608236136809583897803629123312355328K, 383123885216472273619167795607258246624711056K, 766247770432944547238335591214516493244222112K, 1532495540865889094476671182429032986488444224K, 306499108173177818895334236485806597297688848K, 612998216346355637790668472971613194595377792K, 1225996432692711275581336945943226911190755536K, 2451992865385422551162673891886453822381511072K, 4903985730770845102325347783772907644763022144K, 98079714615416902046506955675458152895260448K, 196159429228833804093013911350963057790520896K, 39231885845766760818602782270192611558104192K, 78463771691533521637205564540385223116208384K, 156927543383067043274411129080770462232416768K, 313855086766134086548822258161540924464833536K, 627710173532268173097644516323081848928667104K, 1255420347064536346195289032646163777977322208K, 2510840694129072692390578065292327555954644512K, 5021681388258145384781156130584655111909289024K, 10043362776516290769562312261169310223818778048K, 20086725553032581539124624522338620447637556096K, 40173451106065163078249249044677240895275121152K, 80346902212130326156498498089354481790550222304K, 160693804424260652312996976178708963581100444512K, 321387608848521304625993952357417927162200889248K, 64277521769704260925198790471483585424401777856K, 128555043539408521850397580942967170848803555712K, 257110087078817043700795161885934341697607111424K, 514220174157634087401590323771868683395214222848K, 102844034831526817480318064754373676679048445568K, 205688069663053634960636129508747353358096891136K, 411376139326107269921272259017494706716193782272K, 822752278652214539842544518034989413432387545544K, 164550455730442907968508903606997826864751111088K, 329100911460885815937017807213995653729502222176K, 658201822921771631874035614427991307459004444352K, 1316403645843543263748071228855982614918008888704K, 2632807291687086527496142457711965229836017777408K, 5265614583374173054992284915423930579672035554816K, 10531229166743546109985698228847661159344071111072K, 2106245833348709221997139645769532239868814222224K, 4212491666697418443994279291539064479737728444448K, 842498333339483688798855858307812899475556888896K, 1684996666778967377597711716615657989451113777776K, 3369993333557934755195423433231315979902227555552K, 6739986667115869510390846866462639599804451111104K, 134799732342317390207816937329252791996089022222176K, 269599464684634780415633874658505583992178044444352K, 539198929369269560831267749317011179984360088888704K, 107839785873853912166253549863402359968720177777408K, 215679571747707824332507099726804719937440355555176K, 431359143495415648665014199453609439874880711111352K, 862718286990831297330028398907218879749761422222704K, 1725436573981662594660056797814437759499522844444352K, 345087314796332518932011359562887519899905688888704K, 69017462959266503786402271912577439799981137777408K, 138034925918533007572804543825154679599962275555176K, 27606985183706601514560908765030939199992451111352K, 55213970367413203029121817530061878399984902222704K, 11042794073482640605824363506012357679996884444352K, 22085588146965281211648727012024715359993768888704K, 44171176293930562423297454024049426719997537777408K, 88342352587861124846594908048098853439995075555176K, 17668470517572224969318981609619766887999015111352K, 35336941035144449938637963219239533775999802222704K, 70673882070288899877275926438479067551999604444352K, 14134776414057779975455185287695813113999208888704K, 28269552828115559950910370575391626227999417777408K, 56539105656231119901820741150783252455999835555176K, 11307821131246223980364148230156504911199967111352K, 226156422624924479607282964603130098223999342222704K, 452312845249848959214565929206260194447999684444352K, 9046256904996979184291318584125203888999368888704K, 18092513809993958368582637168250407777999737777408K, 36185027619987916737165274336500815555999475555176K, 7237005523997583347433054867300161111199995111352K, 1447401104799516669486610974600322223999902222704K, 2894802209599033338973221949200644447999804444352K, 57896044191980666779464438984012888999608888704K, 1157920883839613335589288779680257779992137777408K, 2315841767679226671178577559360515559994275555176K, 463168353535845334235715511872103111199985111352K, 9263367070716906684714302375442062223999702222704K, 1852673414143381336942860475088412447999404444352K, 3705346828286762673885720950176824999808888704K, 7410693656573525347771441900353649996177777408K, 1482138731314705069554288380070729992355555176K, 296427746262941013910857676014145999471111352K, 592855492525882027821715352028291999942222704K, 118571098505176405564343070405583999844444352K, 23714219701035281112868614081116799968888704K, 47428439402070562225737228162335999377777408K, 94856878804141124451474456324671999755555176K, 18971375760828224890294891264934399951111352K, 37942751521656449780589785289868799902222704K, 7588550304331289956

# PRACTICAL ELECTRONICS

VOLUME 17

No. 4

APRIL 1981

## CONSTRUCTIONAL PROJECTS

<b>PE DIGISOUNDER</b> Part 1 <i>by Brian Currie</i> .. .. .	<b>30</b>
Digital depth sounder for boats	
<b>SPEECH PROCESSOR</b> <i>by Michael Tooley BA and David Whitfield BA, MSc</i> .. .. .	<b>38</b>
Improves the intelligibility of voice signals	
<b>DRILL PSU</b> <i>by Chris Lare</i> .. .. .	<b>44</b>
Includes a p.w.m. controller for variable speed capability	
<b>ULTRASONIC INTRUDER ALARM</b> <i>by Gilbert Davies</i> .. .. .	<b>52</b>
Updated protection system	
<b>INTERFACING COMPUKIT</b> Part 4 <i>by D. E. Graham</i> .. .. .	<b>56</b>
Analogue board—construction and theory	

## GENERAL FEATURES

<b>CONSUMER ELECTRONICS SHOW</b> .. .. .	<b>22</b>
Latest developments are seen at Las Vegas	
<b>OSCILLOSCOPES . . . HOW THEY WORK</b> Part 1 <i>by Ian Hickman</i> .. .. .	<b>26</b>
The cathode-ray tube	
<b>SEMICONDUCTOR UPDATE</b> <i>by R. W. Coles</i> .. .. .	<b>49</b>
ICM 7242 L290, 1&2 4118, 4801&4802	
<b>MICROBUS</b> <i>by D.J.D.</i> .. .. .	<b>50</b>
Program loader and other software for ZX80, plus 3-D plotting for Acorn Atom	
<b>INGENUITY UNLIMITED</b> .. .. .	<b>66</b>
'Day to Remember' clock—Bargraph Thermometer—L.F. Analogue Monitor— Envelope Differentiator—Synth Processor—TVC for Synths	

## NEWS AND COMMENT

<b>EDITORIAL</b> .. .. .	<b>17</b>
<b>MARKET PLACE</b> .. .. .	<b>18</b>
New Products	
<b>INDUSTRY NOTEBOOK</b> <i>by Nexus</i> .. .. .	<b>21</b>
The painful implementation of new technology	
<b>SPACEWATCH</b> <i>by Frank W. Hyde</i> .. .. .	<b>35</b>
Prospects for the next decade	
<b>COUNTDOWN</b> .. .. .	<b>42</b>
What to see; where and when to see it	
<b>POINTS ARISING</b> .. .. .	<b>42</b>
27/28MHz Converter, Microbus	
<b>READOUT</b> .. .. .	<b>63</b>
A bumper batch of readers' opinions, including more views on CB	
<b>PATENTS REVIEW</b> .. .. .	<b>65</b>
Pulse rate loggers for overweight joggers	

**OUR MAY ISSUE WILL BE ON SALE FRIDAY, 10 APRIL 1981**  
(for details of contents see page 36)

© IPC Magazines Limited 1981. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

# WATFORD ELECTRONICS

33/35, CARDIFF ROAD, WATFORD, HERTS, ENGLAND  
MAIL ORDER CALLERS WELCOME Tel. Watford 40588/9

ALL LEADING BRAND NEW, FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O. OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS OFFICIAL ORDERS ACCEPTED TELEPHONE ORDERS ACCESS ONLY. ACCEPTED (Minimum £10.00 please). TRADE AND EXPORT INQUIRIES WELCOME. P. ADD 50p to ALL ORDERS UNDER £10.00. OVERSEAS ORDERS POSTAGE AT COST.

**VAT** Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 15% to the total cost.

We stock many more items. It pays to visit us. We are situated behind Watford Football Ground, Nearest Underground/Br. Rail Station: Watford High Street. Open Monday to Saturday 9 a.m. - 6 p.m. Ample Free Car Parking space available.

## POLYESTER CAPACITORS:

400V: 1nF, 1.5n, 2n2, 3n3, 4n7, 6n8 11p; 10n, 15n, 18n, 22 12p; 33n, 47n, 68n 16p; 100n, 150n, 200n, 220n, 330n, 470n, 52p; 680n 60p; 1µF 68p; 2µF 47 85p.  
160V: 10nF, 12n, 100n 11p; 150n, 220n 17p; 330n, 470n 30p; 680n 38p; 1µF 42p; 1.5µF 45p; 2µF 48p; 4µF 58p.  
1000V: 1nF 17p; 10nF 30p; 15n 40p; 22n 36p; 33n 42p; 47n, 100n 50p; 147n 99p.

## POLYESTER RADIAL LEAD CAPACITORS: 250V:

100n, 15n, 22n, 27n 8p; 33n, 47n, 68n, 100n 7p; 150n, 220n 10p; 330n, 470n 13p; 680n 19p; 1µF 23p; 1.5µF 40p; 2µF 46p.

## ELECTROLYTIC CAPACITORS (Values in µF):

500V: 10 52p; 47 73p; 250V: 100 65p; 63V: 0.47, 1.0, 1.5, 2.2, 3.3, 8p, 4.7 9p; 6.8, 10 10p; 15, 22 12p; 33, 47 12p; 100 19p; 1000 70p; 50V: 47 12p; 68 20p; 220 24p; 470 32p; 2200 90p; 40V: 4.7, 15, 22, 9p; 33 9p; 47 10p; 25V: 0.5, 6.8, 10, 22, 33 9p; 33 9p; 47 10p; 100 11p; 150 12p; 220 15p; 330 22p; 470 25p; 680, 1000 34p; 2000 50p; 3300 76p; 4700 92p; 16V: 40, 47, 100 9p; 125 12p; 220 13p; 470 20p; 680 34p; 1000 27p; 1500 31p; 2200 36p; 3300 74p; 4700 79p.

## TANTALUM BEAD CAPACITORS:

0.5V 10µ, 0.22, 0.33 15p; 0.47, 0.68, 1.0, 1.5 16p; 2.2, 3.3 18p; 4.7, 6.8 22p; 10 28p; 16V: 2.2, 3.3 16p; 4.7, 6.8, 10 18p; 15 30p; 22 30p; 33, 47 40p; 100 75p; 10V: 15, 22 26p; 33, 47 35p; 100 55p.

## MYLAR FILM CAPACITORS:

100V: 1nF, 2n, 4n, 4n7, 10 8p; 15nF, 22n, 30n, 40, 47 7p; 56, 100n, 200 9p; 470n 50V: 12p.

## CERAMIC CAPACITORS: (50V)

Range 0.5pF to 10nF 4p  
15nF 22nF, 33nF, 47nF 5p  
100nF/30V 7p, 220nF/6V 8p

## POLYSTYRENE CAPACITORS:

10pF to 1nF 8p 1.5nF to 12nF 10p.

## SILVER MICA (pF)

2, 3, 3.4, 7, 6.8, 8, 2, 10, 12, 18, 22, 27, 33, 39, 47, 56, 68, 75, 82, 85, 100, 120, 150, 180

## TRIMMERS miniature

2-6pF 2-10pF 20p  
2-25pF, 5-56pF 22p  
10-80pF 35p

## COMPRESSION

3-40pF, 10-80pF 20p  
20-250pF 28p  
100-580pF 38p  
400-1250pF 49p

## POTENTIOMETERS: Carbon Track.

0.25W Log & Linear Values  
500Ω, 1K & 2K (LIN ONLY) Single 29p  
5KΩ, 2MΩ single gang 25p  
5KΩ, 2MΩ single gang D/P switch 69p  
5KΩ, 2MΩ dual gang stereo 88p  
1W Wire-wound 50Ω-20K 115p

## SLIDER POTENTIOMETERS

0.25W log and linear values 60mm track  
5KΩ, 500KΩ Single gang 70p  
10KΩ, 500KΩ Dual gang 110p  
Self-Stick graduated Alum. Bezels 36p

## PRESET POTENTIOMETERS

0.1W 50Ω-2.2M Mini Vert. & Horiz. 7p  
0.25W 22Ω-3.3M Horz. larger 10p  
0.25W 250Ω-4.7MΩ Vert. 10p  
Precision Cermet 1W 100Ω-100K 80p

## RESISTORS—Erie make 5% carbon

Miniature High Stability, Low Noise.  
RANGE Val. 1-99 100-1000  
0.25W 202-4 M7 E24 2p 1p  
0.5W 202-4 M7 E24 2p 1p  
1W 202-10M E12 2p 1p  
2% Metal Film 100-1M 6p 4p  
1% 0.5W 51Ω-1M24 8p 6p  
100+ price applies to Resistors of each type not mixed values.

TRANSISTORS		74LS		CMOS					
AC107	35	BC327	15	BFX84	26	TIP32C	60	2N3054	58
AC125	35	BC328	15	BFX85	26	TIP33A	65	2N344	40
AC126	35	BC329	15	BFX86	26	TIP33B	65	2N3614	199
AC127	25	BC338	15	BFX87	28	TIP33A	74	2N3615	199
AC128	25	BC441	34	BFX88	28	TIP34C	88	2N3663	15
AC141	30	BC461	34	BFY50	23	TIP35A	160	2N3702	10
AC142	30	BC477	40	BFY51	23	TIP35C	185	2N3703	10
AC176	28	BC516	40	BFY52	23	TIP36A	170	2N3704	10
AC177	28	BC517	40	BFY53	23	TIP36B	195	2N3705	10
AC178	28	BC518	40	BFY54	35	TIP41A	55	2N3706	10
AC179	28	BC519	40	BFY81	120	TIP41B	60	2N3707	10
AC180	28	BC520	40	BFY82	120	TIP42A	60	2N3708	10
AC181	28	BC521	40	BFY83	120	TIP42B	75	2N3709	10
AC182	28	BC522	40	BFY84	120	TIP42C	75	2N3710	10
AC183	28	BC523	40	BFY85	120	TIP42D	75	2N3711	10
AC184	28	BC524	40	BFY86	120	TIP42E	75	2N3712	10
AC185	28	BC525	40	BFY87	120	TIP42F	75	2N3713	10
AC186	28	BC526	40	BFY88	120	TIP42G	75	2N3714	10
AC187	28	BC527	40	BFY89	120	TIP42H	75	2N3715	10
AC188	28	BC528	40	BFY90	120	TIP42I	75	2N3716	10
AC189	28	BC529	40	BFY91	120	TIP42J	75	2N3717	10
AC190	28	BC530	40	BFY92	120	TIP42K	75	2N3718	10
AC191	28	BC531	40	BFY93	120	TIP42L	75	2N3719	10
AC192	28	BC532	40	BFY94	120	TIP42M	75	2N3720	10
AC193	28	BC533	40	BFY95	120	TIP42N	75	2N3721	10
AC194	28	BC534	40	BFY96	120	TIP42O	75	2N3722	10
AC195	28	BC535	40	BFY97	120	TIP42P	75	2N3723	10
AC196	28	BC536	40	BFY98	120	TIP42Q	75	2N3724	10
AC197	28	BC537	40	BFY99	120	TIP42R	75	2N3725	10
AC198	28	BC538	40	BFY00	120	TIP42S	75	2N3726	10
AC199	28	BC539	40	BFY01	120	TIP42T	75	2N3727	10
AC200	28	BC540	40	BFY02	120	TIP42U	75	2N3728	10
AC201	28	BC541	40	BFY03	120	TIP42V	75	2N3729	10
AC202	28	BC542	40	BFY04	120	TIP42W	75	2N3730	10
AC203	28	BC543	40	BFY05	120	TIP42X	75	2N3731	10
AC204	28	BC544	40	BFY06	120	TIP42Y	75	2N3732	10
AC205	28	BC545	40	BFY07	120	TIP42Z	75	2N3733	10
AC206	28	BC546	40	BFY08	120	TIP42AA	75	2N3734	10
AC207	28	BC547	40	BFY09	120	TIP42AB	75	2N3735	10
AC208	28	BC548	40	BFY10	120	TIP42AC	75	2N3736	10
AC209	28	BC549	40	BFY11	120	TIP42AD	75	2N3737	10
AC210	28	BC550	40	BFY12	120	TIP42AE	75	2N3738	10
AC211	28	BC551	40	BFY13	120	TIP42AF	75	2N3739	10
AC212	28	BC552	40	BFY14	120	TIP42AG	75	2N3740	10
AC213	28	BC553	40	BFY15	120	TIP42AH	75	2N3741	10
AC214	28	BC554	40	BFY16	120	TIP42AI	75	2N3742	10
AC215	28	BC555	40	BFY17	120	TIP42AJ	75	2N3743	10
AC216	28	BC556	40	BFY18	120	TIP42AK	75	2N3744	10
AC217	28	BC557	40	BFY19	120	TIP42AL	75	2N3745	10
AC218	28	BC558	40	BFY20	120	TIP42AM	75	2N3746	10
AC219	28	BC559	40	BFY21	120	TIP42AN	75	2N3747	10
AC220	28	BC560	40	BFY22	120	TIP42AO	75	2N3748	10
AC221	28	BC561	40	BFY23	120	TIP42AP	75	2N3749	10
AC222	28	BC562	40	BFY24	120	TIP42AQ	75	2N3750	10
AC223	28	BC563	40	BFY25	120	TIP42AR	75	2N3751	10
AC224	28	BC564	40	BFY26	120	TIP42AS	75	2N3752	10
AC225	28	BC565	40	BFY27	120	TIP42AT	75	2N3753	10
AC226	28	BC566	40	BFY28	120	TIP42AU	75	2N3754	10
AC227	28	BC567	40	BFY29	120	TIP42AV	75	2N3755	10
AC228	28	BC568	40	BFY30	120	TIP42AW	75	2N3756	10
AC229	28	BC569	40	BFY31	120	TIP42AX	75	2N3757	10
AC230	28	BC570	16	BU105	170	TIP42AY	75	2N3758	10
AC231	28	BC571	16	BU205	190	TIP42AZ	75	2N3759	10
AC232	28	BC572	20	BU208	200	TIP42BA	75	2N3760	10
AD161	42	BD121	95	E421	250	TIP2955	60	2N3879	22
AD162	42	BD123	98	MJ2955	250	TIP3055	60	2N3820	22
AF118	95	BD124	115	MJ2955	90	TIS43	32	2N3822	65
AF139	40	BD131	48	MJE340	54	TIS44	45	2N3823	65
AF178	75	BD132	48	MJE370	100	TIS45	45	2N3866	90
BC107	10	BD133	60	MJE371	100	TIS90	30	2N3903	18
BC107B	12	BD135	45	MJE525	95	TIS91	32	2N3904	15
BC108	10	BD136	40	MJE525	95	UC73A	61	2N3906	17
BC109	10	BD137	40	MJE525	95	ZT1027	11	2N3906	17
BC108C	12	BD138	40	MPF102	66	ZTX108	11	2N4037	46
BC109	10	BD139	40	MPF103	36	ZTX109	12	2N4058	10
BC109B	12	BD140	40	MPF104	36	ZTX122	28	2N4061	10
BC109C	12	BD144	198	MPF105	36	ZTX300	13	2N4062	10
BC140	30	BD205	40	MPF106	40	ZTX300	16	2N4069	45
BC142	30	BD245	45	MPSA05	58	ZTX325	16	2N4227	80
BC143	30	BD378	70	MPSA06	25	ZTX303	25	2N4859	78
BC147	9	BD434	55	MPSA12	32	ZTX304	17	2N4871	55
BC147B	10	BD517	75	MPSA55	30	ZTX314	25	2N5135	20
BC148	9	BD598A	85	MPSA56	30	ZTX320	30	2N5136	20
BC148C	10	BD598B	85	MPSU02	58	ZTX325	16	2N5138	18
BC149	9	BDV56	180	MPSU05	55	ZTX334	30	2N5172	18
BC149C	9	BDV61	160	MPSU06	55	ZTX500	14	2N5179	45
BC153	27	BF115	35	MPSU52	65	ZTX501	15	2N5180	45
BC154	27	BF125	29	MPSU55	60	ZTX502	15	2N5191	75
BC157	10	BF177	20	OC2	10	ZTX503	18	2N5305	24
BC158	10	BF178	30	OC26	170	ZTX531	25	2N5458	36
BC159	11	BF179	35	OC28	130	ZTX550	25	2N5459	36
BC160	45	BF180	38	OC34	125	ZN697	23	2N5485	36
BC167A	10	BF194	12	OC36	120	ZN698	45	2N5777	45
BC168	10	BF195	12	OC37	120	ZN699	48	2N6102	32
BC169	10	BF196	12	OC42	120	ZN706A	19	2N6109	60
BC170	10	BF197	12	OC44	120	ZN708	19	2N	

# WATFORD ELECTRONICS

(Continued from opposite side)

DIODES	
AA119	15
8A100	8
BY100	24
BY126	12
BY127	12
CR033	250
OA9	40
OA47	12
OA70	12
OA79	15
OA85	15
OA90	8
OA91	8
OA95	8
OA200	8
OA202	8
1N914	4
1N916	5
1N4001/2	5
1N4003	6
1N4004/5	6
1N4006/7	7
1N4148	4
1N5401	15
1N5404	16
1N5406	17
1N5408	19
1544	9
15921	9
6A100V	40
6A400V	50
6A800V	65
SCR's Thyristors	
0-8A-100V	32
1A/200V	58
1A/400V	70
5A/300V	38
5A/400V	40
5A/600V	48
8A/300V	60
8A/400V	65
8A/600V	78
12A/100V	78
12A/400V	95
12A/800V	188
8T116	150
8T116	180
CT106D	38
TIC44	24
TIC45	29
TIC47	35
2N5062	32
2N5064	38
2N4444	130
BRIDGE RECTIFIERS	
(plastic case)	
1A/50V	20
1A/100V	22
1A/400V	29
1A/600V	34
2A/50V	35
2A/200V	40
2A/400V	46
2A/600V	65
6A/100V	83
6A/400V	95
6A/600V	125
10A/200V	215
10A/600V	250
25A/200V	240
25A/600V	395
3Y164	56
VM18	50
ZENERS	
Range 2V7 to 39V	400mW
8p each	
Range 3V3 to 33V	1.3W
15p each	
VARICAPS	
MVAM2	165
MVAM115158	158
8A102	30
8B105B	40
8Y164	56
BB106	40
Noise Diode	
Z5J	180
TRIACS	
3A/100V	48
3A/400V	56
3A/800V	85
8A/100V	60
8A/400V	69
8A/800V	115
12A/100V	78
12A/400V	82
12A/800V	135
16A/100V	103
16A/400V	105
16A/800V	220
25A/400V	185
25A/800V	295
25A/1000V	
COPPER CLAD BOARDS	
Fibre Single	SRBP
Glass sided	9.5" x 8.5"
6" x 6"	90p
6" x 12"	150p
DIAC	
ST2	25

OPTO ELECTRONICS	
LEDS Plus Clip	13
TIL209 Red 125"	18
TIL211 Green 125"	18
TIL212 Yellow	18
TIL220 2" Red	15
0.2" Yel. Grn. Amber	18
Red, Green and Yellow	29
Rectangular LEDS	28
0.2" Red/green LED	46
0.2" Red High Bright	48
2N5777 45	120
OCPT71	20
LD271 Infra Red (emit)	41
LD271 Infra Red (R&G)	41
SF1205 (detector)	91
TIL78 (detector)	60
7 Segment Displays	
LM3008	115
TIL322 5" C.th	115
DL704 3" C. Cath	99
DL707 3" C. Anod	99
DL747 6" C. Cathod.	180
8" Orange CA.	250
FND357 or 500	120
3" Green CA.	140
±1.3" Red or Green	150
Bargraph 10 seg. Red	225
Liquid Crystal Display	
3 1/2 digit 675p; 4 digit 750p	
6 Digit LCD	850p
VO Board	150p
DIP Board	330p
Verob Strip	144p
PROTO-DECs	
Veroblock	375p
S-Dec	350p
Eurobreadboard	520p
PCB Board 1	785p
Superstrip SS2	998p
VERO WIRING PEN and Spool	
Spare Wire (Spool) 65p;	
Combs 6p ea.	
FERRIC CHLORIDE	
1 lb bag Anhydrous	195p
+ 40p p&p	
DALO ETCH RESIST	
Pen + Spare tip	90p
ALFAC TRANSFERS	
Etch Resist	
Full range available	
35p a sheet	
SOLDERCON PINS	
100 pins 60p	
500 pins 275p	

VOLTAGE REGULATORS	
1A T03 +ve	-ve
5V 7805 145p	7905 220p
12V 7812 145p	7912 220p
15V 7815 145p	7915 220p
18V 7818 150p	—
TO220 Plastic Casing	
5V 7805 60p	7905 65p
12V 7812 60p	7912 65p
15V 7815 60p	7915 65p
18V 7818 60p	7918 65p
24V 7824 60p	—
100mA TO22 Plastic Casing	
5V 78L05 30p	79L05 65p
6V 78L62 30p	—
8V 78L82 30p	—
12V 78L12 30p	79L12 65p
15V 78L15 30p	79L15 65p
CA3085	95
LM300H	170
LM305H	140
LM309K	135
78H05 5V/5A	595p
78H05-5 to +24V 5A	650p
79H-2 2.25V to -24V 5A	850p
LM317K	350
LM323K	625
LM325N	240
LM328N	240
LM327N	270
LM723	39
T8A6258	85
SWITCHES	
SLIDE 250V	
1A DPDT	14
1A DPDT C/OFF 15	33
1A DPDT	44
1A DPDT	23
4 pole 2-way	14
4 pole on off	54
TOGGLE 2A 250V	
SPST	33
DPDT	44
4 pole on off	54
PUSH BUTTON	
Spring loaded	
Latching or Momentary 6A	
SPDT c/over	99
DPDT c/over	145
MINIATURE	
Non Locking	
Push to make	15p
Push break	25p
SUB-MIN TOGGLE	
SP changeover	60
SPST on off	54
SPDT c/over	85
SPDT Biased	105
6 tags	75
DPDT C/OFF	88
DPDT Biased	145
4 pole c/over	205
ROCKER	
5A, 250V SPST	28p
(white) 10A 250V SPDT	28p
changeover	
ROCKER: With neon lights red when on	65p
10A 250V DPST	85p
ROCKER: (White) 10A/250V DPDT	72p
ROTARY: "Make-A-Switch"	
Make your own multiway Switch as required. Shaft-assembly has adjustable stop. Accommodates up to 6 Wafers. Break before make Wafers. Silver contacts.	
1 pole/12 way, 2 pole/6 way, 3 pole/4 way, 4 pole/3 way, 6 pole/2 way	90p
Mains DPST Switch to fit	45p
Screen & Spacers	6p
ROTARY: (Adjustable Stop Type)	
1 pole/2 to 12 way, 2p/2 to 6 way, 3 pole/2 to 4 way, 4 pole/2 to 3 way	45p
ROTARY: Mains 250V AC, 4 Amp	56p


CRYSTALS		
100KHz	300	
455KHz	370	
1MHz	295	
1.008M	295	
1.6432M	300	
2.0MHz	305	
2.4576M	305	
3.2768M	290	
3.57954M	150	
4.0MHz	290	
4.032M	290	
4.194304M	270	
4.433619M	150	
5.0MHz	290	
5.185M	300	
5.24288M	390	
6.0MHz	290	
6.144M	295	
6.5536M	290	
7.168M	290	
7.68MHz	300	
8.0MHz	290	
8.867237MHz	270	
10.0MHz	290	
10.7MHz	270	
12.0MHz	290	
14.31818M	320	
16.0MHz	290	
18.0MHz	290	
18.432M	290	
26.69M	290	
27.648M	330	
38.66667MHz	290	
48.0MHz	270	
100.0MHz	375	
DIL PLUGS (Headers)		
14 pin 44p;	24 pin 88p	
16 pin 49p;	40 pin 295p	
(DIL Sockets on opp. page)		
'D' CONNECTORS (Cannon type)		
	Plugs Sockets Covers plastic	
9 way	90p 118p	150p
15 way	120p 167p	170p
25 way	180p 280p	170p
37 way	268p 390p	185p
DIL switches (SPST)		
4 way	85p	
6 way	82p	
8 way	98p	
115p		
10 way	115p	
175p		
(SPDT)	197p	
4 way	195p	
2x43 way	250p	
EDGE CONNECTORS double type		
	1 156	
2 x 10 way	82p	
2 x 15 way	98p	
2 x 18 way	140p 120p	
2 x 22 way	150p 125p	
2 x 25 way	165p 160p	
2 x 30 way	188p	
2 x 36 way	197p	
2 x 40 way	205p	
2 x 43 way	250p	
TRANSFORMERS (mains Prim. 220-240V)		
6-0-6V 100mA, 9-0-9V 75mA, 12-0-12V 75mA	98p	
8VA type: 6V-5A 6V-5A 9V-4A 9V-4A 12V-3A 12V-3A 15V-25A 15V-25A 220p		
12VA: 4.5-1.3A 4.5V-1.3A 6V-1.2 6V-1.2A 12V-1A 12V-1A 15-8A 15-8A 20V-6A 20V-6A 310p (44p p&p)		
24VA: 6V-1.5A 6V-1.5A 9V-1.2A 9V-1.2A 12V-1A 12V-1A 15V-1.5A 15V-1.5A 20V-1.2A 20V-1.2A 25V-1A 25V-1A 30V-8A 30V-8A 365p (60p p&p)		
100VA: 12V-4A 12V-4A 15V-3A 15V-3A 20V-2.5A 20V-2.5A 30V-1.5A 30V-1.5A 40V-1.25A 40V-1.25A 50V-1A 50V-1A 820p (60p p&p)		
JUMPER LEADS Ribbon Cable Assembly		
Single ended DIP, 24" length Cable		
14 pin 145p	16 pin 165p;	
24 pin 240p;	40 pin 380p.	

COMPUTER CORNER	
● SUPERBOARD II: (Series II New Version) Ready-built and tested: 50Hz.	Only £149
● PSU 5V/3A for above incl. UHF Mod. 610 Expansion Board (8K)	£150
● Plastic Case for Superboard, fits UK101, NASCOM etc.	£25
● Space Invaders for Superboard (4K)	£5
● PRINTER 800. Ideal for PET, Apple, TRS80, Superboard etc.	Only: £299
● SEIKOSHA GP80A Unihammer dot-matrix Printer. Gives normal and double width characters as well as Dot resolution Graphics.	£225
● EPSON TX80 80 column dot matrix printer available in tractor feed or friction feed.	£295
● VIDEO GENIE based on TRS80 16K RAM NEW VERSION	Only: £289
● SOFTY. Intelligent EPROM Programmer Kit Ready-Built & Tested PSU for above (Built)	£99 £120 £20
● TEX UV EPROM Eraser. Erases up to 32 ICs in 15-30 min.	£33
● UHF MODULATOR 6MHz	280p
● UHF MODULATOR 8MHz	450p
● KEYPADS 4x4 matrix	350p
● Model 756 ASCII Keyboard	£40
● 10x C12 Cassettes in stockable racks	£5.50
We stock a wide selection of Computer Books.	

# A Healthy Pulse Rate

## \* £95 for 0.5Hz to 5MHz


Here's a precision digital pulse generator with fast rise and fall times covering 0.5Hz to 5MHz in five overlapping ranges. With pulse width and pulse spacing each independently variable from 100 nsec to 1 sec for an amazing 10<sup>7</sup>:1 duty cycle range. You'll find the 4001 delivers the pulse modes you need: Continuous, One-Shot, Triggered, Gated, Square Wave, even a Complement mode. The Trigger/Gate input, 50 ohm variable output, TTL-level output and Sync output connectors are BNCs.

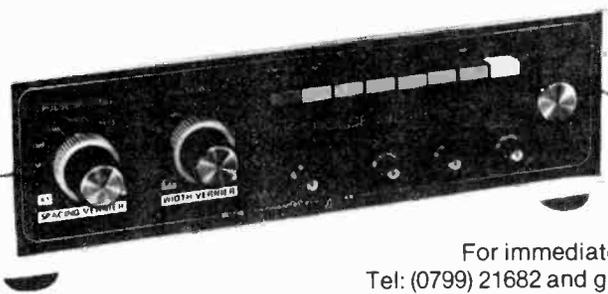

The 4001. A specification to get your pulse racing.

For immediate action — The G.S.C. 24 hour, 5 day a week service Tel: (0799) 21682 and give us your Access, American Express, Barclaycard number and your order will be in the post immediately or just clip out the coupon.

### GLOBAL SPECIALTIES CORPORATION

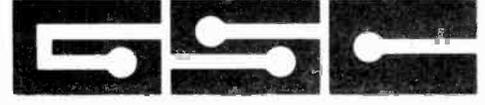

G.S.C. (UK) Limited, Dept 25GG, Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ. Tel: Saffron Walden (0799) 21682 Telex: 817477.

Global Specialties Corporation (UK) Limited, Dept 25GG Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.			
Model 4001 Ultra Variable Pulse Generator	£110.97 (inc. P&P and 15% VAT)	Qty Reqd.	For FREE catalogue tick box <input type="checkbox"/>
Name .....	Address .....		
I enclose PO/Cheque for £..... or debit my Barclaycard/Access/American Express No ..... exp date.....			

# CHROMASONIC electronics

48 JUNCTION ROAD, ARCHWAY, LONDON N19 5RD  
TELEPHONE 01-263 9493 01-263 9495

100 YDS FROM ARCHWAY STATION & 9 BUS ROUTES

**YOUR SOUNDEST CONNECTION IN THE WORLD OF COMPONENTS AND COMPUTERS**


## PETS & SYSTEMS

- 8N 8K RAM** £399
- 16N 16K RAM** £499
- 32N 32K RAM** £599
- CASSETTE DECK** £55  
343K Twin Floppy Disk  
£695



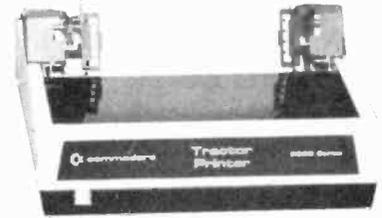**COMPLETE 32K SYSTEM £1789**

- NEW** 32K with 80 col Screen £825  
Twin Disk Drive 950K £895  
All with new keyboard and green screen
- Friction Feed Printer £375
  - Tractor Feed Printer £425




### MEMORY EXPANSION KIT

Suitable for UK101, Super-board expansion using 2114's each board has 16K ram capacity kit contains:

- ★ On board power supply
- ★ 4K Eprom expansion
- ★ Fully buffered for easy expansion via 40 pin socket
- ★ 8K kit £89.95
- ★ 16K kit £122.95
- ★ Printed Circuit Board £29.95
- ★ 40 pin-40 pin header plug £8.50

### NEW SHOP

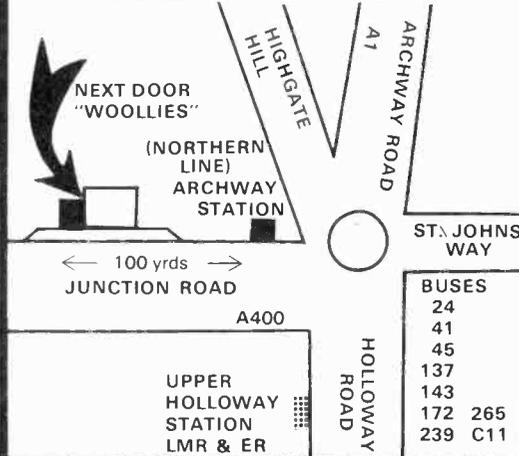

### VIDEO GENIE



**VIDEO GENIE based on TRS80**

Utilises Z80, 12K level II Basic, Integral Cassette Deck, UHF O/P, 16K RAM, all TRS80 features.

**£289**

### CASES

Available for U.K. 101, Superboard Nascom, Appx. DIM. 17" x 15" 435 x 384 mm

**PRICE £24.50**

Post + Packing £1.50

### UK101 P.P.I.

Built & tested. Interfaces TX80 printer direct, can be programmed to operate relays, motors, various other peripherals. "Centronics compatible". Plugs into IC socket. LED binary display. Fully documented. **£29.95**

### UK101

**£179** IN KIT FORM  
**£229** READY BUILT & TESTED

**£255** COMPLETE IN CASE (8x2114)

4K EXPANSION NOW ONLY **£18.00**

No extras required


- ★ Free sampler tape
- ★ Full Qwerty keyboard
- ★ 8K basic
- ★ Ram expandable to 8K on board (4K inc.)
- ★ Kansas City tape interface
- ★ New monitor allows full editing & cursor control **£22.00**


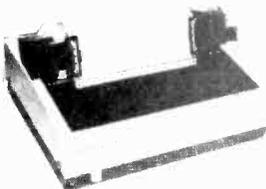
### PRINTERS

**EPSON MX-80**  
**£359**

Dot-matrix printer with Pet graphics interface: Centronics parallel and serial options: PET & Apple compatible.



Please add VAT 15% to all prices. Postage on computers, printers and cassette decks charged at cost, all other items, P&P 30p. Place your order using your Access or Barclaycard (Min. tel order £5). Trade and export enquiries welcome, credit facilities arranged.



# NEW SHOP & SHOWROOM NOW OPEN

TELEPHONE 01-263 9493 01-263 9495

## UK101 SOUND

Sound generator and combined parallel in out port kit containing P.C.B., AY-3-8910, 6520 PIA, fully documented and demo tape.

**£29.95**

AY-3-8910

**£8.50**

## UK101 SOFTWARE

	£ p
Space Invaders	6.50
Real Time Clock	3.00
Chequers	3.00
Othello	4.00
Game Pack I	5.00
Game Pack II	5.00
Game Pack III	5.00
Screen Monitor	4.00
Assembler Editor	14.90
10 x C12 Blank Tapes	4.00

## CPU'S

Z80 2.5 Meg	7.95
Z80A 4 Meg	9.95
6502	6.95
6800	6.50
8080	4.75
9900	25.95

## SUPPORT CHIPS

Z80 CTC	5.95
Z80A CTC	6.95
Z80 PIO	5.95
Z80A PIO	6.95
6520	3.95
6522	6.85
6532	8.50
6821	4.25
6850	3.60
6852	4.35
8212	1.95
8216	1.95
8224	2.75
8228	3.75
8251	4.95
8253	9.75
8255	4.50
TMS9901	13.16
TMS9902	11.18
TMS9904 (74LS362)	4.21
DM8123	1.75
MC1483	.90
MC1489	.90

## UARTS

AY-5-1013	3.95
AY-3-1015	4.75
MM5303	4.75
TMS6011	3.55

## MEMORY

D. RAMS	£ p
4027	2.75
4050 (350NS)	2.35
4060 (300NS)	2.39
4116	3.95

S. RAMS	£ p
2102A	1.30
2102A2	1.69
2112A	2.75
2114/4045	2.75
4035	1.07
4044-5257	6.93
6810	3.50

BULK PURCHASE	£ p
8x2114	18.00
8x4116	27.50
16x2114	34.00

## EPROMS

2708	4.25
2716 (5v)	6.95
2532	29.95

## ROM

2513 (UC)	5.95
-----------	------

## I.C. SOCKETS

	D.I.L.	W/W
8 pin	.09	.25
14 pin	.11	.35
16 pin	.12	.42
18 pin	.16	.50
20 pin	.20	.62
22 pin	.22	.65
24 pin	.24	.70
28 pin	.30	.80
36 pin	—	.99
40 pin	.40	1.10

## BUFFERS

81LS95	1.25
81LS96	1.25
81LS97	1.25
81LS98	1.25
SN74365	.52
SN74366	.52
SN74367	.52
SN74368	.52
8T26	1.50
8T28	1.50
8T95	1.50
8T96	1.50
8T97	1.50
8T98	1.50

## BAUD RATE GENS

MC14411	8.75
MM5307	8.75

**SEND S.A.E. FOR COMPLETE  
PRICE LIST OR PHONE 01-263 9495**

# TRAIN FOR SUCCESS

in Radio, Television & Electronics

ICS have helped thousands of ambitious people to move up into higher paid more secure jobs in the field of electronics — now it can be your turn. Whether you are a newcomer to the field or already working in the industry, ICS can provide you with the specialised training so essential to success.

## Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful, is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

## City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

Telecommunications Technicians  
Radio, T.V. Electronics Technicians  
Radio Amateurs  
Electrical Installation Work

## Diploma Courses

Colour T.V. Servicing  
CCTV Engineering  
Electronic Engineering & Maintenance  
Computer Engineering and Programming  
Radio, T.V. and Audio, Engineering & Servicing  
Electrical Engineering, Installations & Contracting

## Other Career Courses

A wide range of other technical and professional courses are available including GCE.

**FREE  
BOOK**

Post this coupon or 'phone today for free Electronics careers guide.

Name \_\_\_\_\_

Address \_\_\_\_\_

Age \_\_\_\_\_

**ICS**


To ICS, Dept 273F, Intertext House,  
London SW8 4UJ  
or telephone 01-622 9911 (all hours)

# BLACK MAGIC!

FOR ALL YOU HEAVY HEAVY SOUND MEN  
THE FIRST EVER COMMERCIALY AVAILABLE QUALITY SOUND  
MIXER DESIGNED SPECIFICALLY FOR REGGAE MUSIC - LOOK  
AT ALL THESE FEATURES:

\* Mono mixing with split weight & treble outputs. \* Maximum output  
bass 4v: treble 3½v. \* Mic input with vol, treble and bass controls \* Aux  
input with vol control. \* Ceramic input & Mag input with vol control.

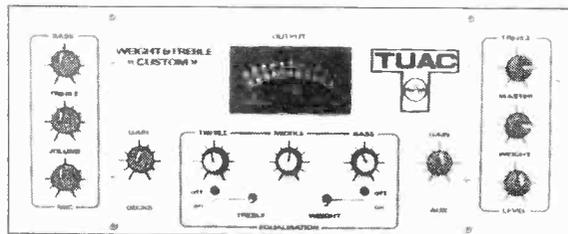\* Weight & treble on/off effects switches and LED indicators. \* Treble, middle & bass controls plus master volume  
master treble & master bass controls. \* Stereo LED VU meter to monitor weight & treble levels. \* All connections  
via standard ¼" jacks mounted on rear panel. 240v mains operated power supply included. \* Size 15"x6"x3".



£129 inc VAT.

## TD 500



This superb power amplifier module is a dual mode  
output configuration i.e. class AB low power primary  
power output stage, dumping power into a  
rugged class B 6 transistor output stage with inbuilt  
protection against open & short circuits and thermal  
overload. This unit is ideal for high power and high  
quality applications.

### Technical specifications

\* 500W RMS into 2 ohms. \* Input sensitivity  
.775v RMS (0dB) at 25K ohms. \* Frequency response  
30Hz - 25KHz - 1dB at full power. \* Quiescent  
current 45mA. \* Hum and noise - 105dB relative  
full output. \* T.H.D. at full power .1%. \* Power re-  
quirements 60 - 0 - 60v D.C. at 8 amps. \* Size:  
7"x6½"x1¼".

£57 inc VAT.

300W version £47 inc VAT.

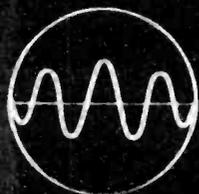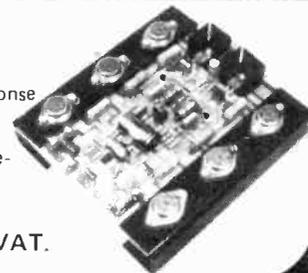

# TUAC

TUAC LTD 119 Charlmont Road, SW17.  
Tel 01-672 3137/9080

PRICE INCLUDES VAT. P+P FREE

TO ORDER BY POST. Money orders/P.O.s payable to TUAC LTD. or quote  
Access/Barclaycard No. and post to TUAC LTD, 119 Charlmont Road, London  
SW17 9AB. We accept telephone orders from Access/Barclaycard Holders.

### TUAC MAIN DISTRIBUTORS

Birmingham, George Matthews, 85/87  
Hurst St, (Tel: 622 1941)  
Buckinghamshire, Disco Barn Iver,  
20 Thorney Lane South, (Tel: 6531711).  
Canterbury, SocoDi Music, 9 The Friars,  
(Tel: 60948).  
Cheshire, Cookies Disco Centre, 126  
West St, Crewe, (Tel: 0270 214739).  
Edinburgh, Cruiser Sound Supplies, 13  
Ferry Rd, Leith, (Tel: 554993).  
Exeter, Electrore Ltd, Fore St,  
(Tel: 56687).  
France, Delta Vision, 28 Rue de  
Leningrad, 75008 Paris, (Tel: 522.11.75).

Glasgow, Rock Electronics, 149 Glasgow  
Rd, Dumbarton, (Tel: 32588).  
London, Session Music, 163 Mitcham  
Rd, Tooting SW17, (Tel: 01-672 3413).  
Kingston, ABC Music, 56 Surbiton Rd,  
(Tel: 01-546 9877).  
Luton, Luton Disco Centre, 88  
Wellington St, (Tel: 411733).  
Manchester, A1 Music, 88 Oxford St,  
(Tel: 236 0340).  
Middlesborough, Salcogien, 43  
Borough Rd, (Tel: 242851).  
Swansea, Burns Electronic Amplificat-  
ion, 63 Ridgeway, Killay, (Tel: 27915).

# INTRUDER ALARMS

## BRANDED INTRUDER ALARMS AT DISCOUNT PRICES FOR LIMITED PERIOD ONLY

Alarm with self-contained siren. Keyed and timed entry, using  
minimal power consumption on stand-by. With circuit fault  
indicator, 3 reed switches, 1 pressure mat, wire and full  
installation instructions. **£36.80**

Siren extension unit to increase range **£11.75**

Self-powered siren (sounds if separately attacked) **£25.00**

Self-powered bell (sounds if separately attacked) **£29.00**

Reed switches (surface) **£1.00**

Reed switches (flush) **£0.90**

Pressure Pad - 27" x 15" **£2.20**

Pressure Pad - 22½" x 6¾" **£1.60**

All above prices inclusive of V.A.T. and postage. Terms: Cash with order.  
Write to Yale Security Products, Wood Street, Willenhall,  
West Midlands WV13 1LA. Telephone: 0902 66911. Telex: 338251.

TRAIN AT HOME

# Be an ELECTRONIC ENGINEER

Do something PRACTICAL about your future.  
Firms all over Britain are crying out for qualified people. With  
the right training, you could take your pick of these jobs.

Now, the British Institute of  
Engineering Technology will train  
you in your spare time to be an  
Electrical Engineer.

You risk nothing! We promise  
to get you through your  
chosen course—or refund your  
fee!

So, join the thousands who  
have built a new future through  
home study Engineering courses.

Courses in  
C & G Elect. Technicians  
C & G Elect. Installations  
Telecomms. Technicians Exams  
Television Servicing  
Radio Maint. & Repairs (BIET)  
Pract. Radio & Electronics  
Plus over 60 other  
home study courses.

## POST COUPON FOR FREE 44 PAGE GUIDE

### BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Aldermaston Court, Dept TPE10, Reading RG7 4PF.

NAME (Block capitals please) \_\_\_\_\_

ADDRESS \_\_\_\_\_

POSTCODE \_\_\_\_\_

Other Subjects \_\_\_\_\_ AGE \_\_\_\_\_

Accredited by CACC

Member of ABCC

Dept. PE8, Unit 9/10, 1st Floor, East Block, 38 Mount Pleasant, London WC1X 0AP. Tel: 01-837 1165, 01-278 7369. Telex: 8953084 Maclin G.

All our microchips are at micro prices. Don't be fooled by low prices. We do not offer for sale surplus, sub-spec or rebranded devices. All our parts are guaranteed new, first quality, factory prime, full spec devices. It is also our policy to offer you the best of new devices that become available and these are featured regularly. Prices are exclusive of p&p and VAT - please refer to "Ordering Information" before ordering. Official order to schools, colleges, universities and Gov. authorities accepted.

## NEW, LOW, LOW PRICES ON MEMORIES!!!

Compare our prices before you buy elsewhere! All devices are brand new. Factory prime, full spec and fully guaranteed! All prices exclude p&p and VAT. Please refer to Ordering Information before ordering. DON'T DELAY - BUY TODAY - SUCH LOW PRICES DON'T LAST FOR EVER!!!

<b>STATIC RAMS</b>	1-24	25-99	100+
2114L 450 NS	195p	175p	150p
2114L 200 NS	225p	195p	175p
2114L 200 NS	250p	225p	195p
4118 250 NS 8K			
NEW!!!			
HM6116 16K (2K x 8)	895p	795p	695p
150 NS 24 pin NEW!!!	£19.95	£17.95	£15.95
<b>DYNAMIC RAMS</b>			
4116 200 NS Ceramic	195p	175p	150p

4116 150 NS	375p	350p	325p
HM4864 64K			
(65K x 1) 200 NS			
Single + 5V supply			
16 pin NEW!!!	£29.95	£24.95	£19.95
<b>CMOS RAMS</b>			
5101 1K (256 x 4)			
450 NS	350p	325p	295p
4315 4K (4K x 1) 450 NS	995p		
TC5514P 4K (1K x 4)	495p	450p	395p
450 NS			
HM6116 16K (2K x 8)			
150 NS 24 pin NEW!!!	£19.95	£17.95	£15.95
<b>EPROMS</b>			
2708 450 NS	350p	325p	295p
2716 5V 450 NS	475p	450p	395p
2532 Single 5V 450 NS	£14.95	£12.95	£11.95
2732 Intel type 450 NS	£14.95	£12.95	£11.95
2564 64K (8K x 8) 450			
NS 28 pin	£99	£95	£90

Ordering information. Unless otherwise stated, all orders under £50 add 50p p&p. Add 15% VAT to total (no VAT on books). All devices are brand new, factory prime and full spec and subject to prior sales and availability. Prices subject to change without notice. Minimum telephone order using ACCESS, is £10. If ordering by post with ACCESS, include name, address and card no. written clearly. Please allow 4/6 weeks delivery on books.



### DTL

830	55p	74LS112	75p	4042	73p
935	65p	74LS123	63p	4043	86p
937	55p	74LS125	50p	4044	86p
944	65p	74LS126	50p	4045	160p
946	55p	74LS132	75p	4047	99p
947	55p	74LS138	69p	4048	56p
962	55p	74LS139	75p	4049	38p
9099	90p	74LS148	170p	4050	40p
		74LS151	75p	4051	69p
		74LS153	75p	4052	75p
		74LS155	65p	4053	73p
		74LS157	74p	4054	111p
		74LS160	115p	4055	121p
		74LS161	78p	4056	121p
		74LS163	90p	4059	560p
		74LS164	90p	4060	112p
		74LS165	100p	4063	112p
		74LS168	190p	4065	56p
		74LS173	100p	4067	422p
		74LS174	99p	4068	19p
		74LS175	99p	4069	19p
		74LS181	280p	4070	28p
		74LS190	110p	4071	25p
		74LS195	87p	4072	25p
		74LS196	100p	4075	20p
		74LS221	110p	4076	88p
		74LS240	210p	4077	23p
		74LS241	200p	4078	29p
		74LS242	220p	4081	23p
		74LS244	175p	4082	25p
		74LS245	220p	4085	86p
		74LS251	120p	4086	68p
		74LS252	120p	4089	130p
		74LS257	110p	4093	68p
		74LS260	90p	4094	225p
		74LS273	175p	4095	99p
		74LS290	95p	4096	325p
		74LS293	120p	4098	110p
		74LS366	57p	4099	180p
		74LS373	170p	4501	25p
		74LS374	170p	4502	112p
		74LS375	140p	4503	69p
		74LS393	135p	4507	52p
		74LS490	140p	4508	288p
		74LS670	260p	4510	76p
				4511	125p
				4512	75p
				4514	250p
				4515	290p
				4516	109p
				4518	99p
				4520	99p
				4521	230p
				4526	105p
				4527	130p
				4528	99p
				4529	140p
				4531	150p
				4532	125p
				4533	69p
				4538	150p
				4543	160p
				4556	70p
				4560	225p
				4572	46p
				4584	74p
				4585	125p

### 7400

7400	11p
7401	12p
7402	12p
7403	13p
7404	17p
7409	18p
7410	18p
7411	18p
7412	18p
7413	28p
7420	16p
7430	15p
7432	25p
7440	16p
7442	68p
7448	75p
7473	32p
7474	32p
7475	40p
7476	40p
7480	35p
7492	50p
7493	45p
7496	45p
74121	35p
74123	45p
74154	90p
74157	55p
74122	45p
74125	50p
74195	100p
74196	100p
74283	140p
74290	120p
74365	90p
74365	90p

### 74LS

74LS00	12p
74LS01	12p
74LS02	13p
74LS03	13p
74LS04	13p
74LS08	20p
74LS10	19p
74LS11	20p
74LS12	20p
74LS13	35p
74LS14	60p
74LS15	39p
74LS20	19p
74LS21	30p
74LS22	30p
74LS26	45p
74LS27	45p
74LS30	18p
74LS32	23p
74LS37	35p
74LS38	35p
74LS40	25p
74LS42	56p
74LS47	78p
74LS49	99p
74LS73	30p
74LS74	30p
74LS75	42p
74LS85	98p
74LS86	39p
74LS90	35p
74LS93	70p
74LS96	150p
74LS107	40p

### 74LS

74LS00	12p
74LS01	12p
74LS02	13p
74LS03	13p
74LS04	13p
74LS08	20p
74LS10	19p
74LS11	20p
74LS12	20p
74LS13	35p
74LS14	60p
74LS15	39p
74LS20	19p
74LS21	30p
74LS22	30p
74LS26	45p
74LS27	45p
74LS30	18p
74LS32	23p
74LS37	35p
74LS38	35p
74LS40	25p
74LS42	56p
74LS47	78p
74LS49	99p
74LS73	30p
74LS74	30p
74LS75	42p
74LS85	98p
74LS86	39p
74LS90	35p
74LS93	70p
74LS96	150p
74LS107	40p

### 74LS

74LS00	12p
74LS01	12p
74LS02	13p
74LS03	13p
74LS04	13p
74LS08	20p
74LS10	19p
74LS11	20p
74LS12	20p
74LS13	35p
74LS14	60p
74LS15	39p
74LS20	19p
74LS21	30p
74LS22	30p
74LS26	45p
74LS27	45p
74LS30	18p
74LS32	23p
74LS37	35p
74LS38	35p
74LS40	25p
74LS42	56p
74LS47	78p
74LS49	99p
74LS73	30p
74LS74	30p
74LS75	42p
74LS85	98p
74LS86	39p
74LS90	35p
74LS93	70p
74LS96	150p
74LS107	40p

### 74LS

74LS00	12p
74LS01	12p
74LS02	13p
74LS03	13p
74LS04	13p
74LS08	20p
74LS10	19p
74LS11	20p
74LS12	20p
74LS13	35p
74LS14	60p
74LS15	39p
74LS20	19p
74LS21	30p
74LS22	30p
74LS26	45p
74LS27	45p
74LS30	18p
74LS32	23p
74LS37	35p
74LS38	35p
74LS40	25p
74LS42	56p
74LS47	78p
74LS49	99p
74LS73	30p
74LS74	30p
74LS75	42p
74LS85	98p
74LS86	39p
74LS90	35p
74LS93	70p
74LS96	150p
74LS107	40p

### 74LS

74LS00	12p
74LS01	12p
74LS02	13p
74LS03	13p
74LS04	13p
74LS08	20p
74LS10	19p
74LS11	20p
74LS12	20p
74LS13	35p
74LS14	60p
74LS15	39p
74LS20	19p
74LS21	30p
74LS22	30p
74LS26	45p
74LS27	45p
74LS30	18p
74LS32	23p
74LS37	35p
74LS38	35p
74LS40	25p
74LS42	56p
74LS47	78p
74LS49	99p
74LS73	30p
74LS74	30p
74LS75	42p
74LS85	98p
74LS86	39p
74LS90	35p
74LS93	70p
74LS96	150p
74LS107	40p

### 74LS

74LS00	12p
74LS01	12p
74LS02	13p
74LS03	13p
74LS04	13p
74LS08	20p
74LS10	19p
74LS11	20p
74LS12	20p
74LS13	35p
74LS14	60p
74LS15	39p
74LS20	19p
74LS21	30p
74LS22	30p
74LS26	45p
74LS27	45p
74LS30	18p
74LS32	23p
74LS37	35p
74LS38	35p
74LS40	25p
74LS42	56p
74LS47	78p
74LS49	99p
74LS73	30p
74LS74	30p
74LS75	42p
74LS85	98p
74LS86	39p
74LS90	35p
74LS93	70p
74LS96	150p
74LS107	40p

### 74LS

74LS00	12p
74LS01	12p
74LS02	13p
74LS03	13p
74LS04	13p
74LS08	20p
74LS10	19p
74LS11	20p
74LS12	20p
74LS13	35p
74LS14	60p
74LS15	39p
74LS20	19p
74LS21	30p
74LS22	30p
74LS26	45p
74LS27	45p
74LS30	18p
74LS32	23p
74LS37	35p
74LS38	35p
74LS40	25p
74LS42	56p
74LS47	78p
74LS49	99p
74LS73	30p
74LS74	30p
74LS75	42p
74LS85	98p
74LS86	39p
74LS90	35p
74LS93	70p
74LS96	150p
74LS107	40p

### 74LS

74LS00	12p
74LS01	12p
74LS02	13p
74LS03	13p
74LS04	13p
74LS08	20p
74LS10	19p
74LS11	20p
74LS12	20p
74LS13	35p
74LS14	60p
74LS15	39p

# BI-PAK NEW EXTENDED 1981 RANGE

## TRANSISTORS

AC107	25	BC107B	11	BC173	09	BC549	11	BD200	99	BF163	30	BFR52	25	MP5A05	20	TIP30A	40	2N707	48	2N2714	22	2N3823	60
AC125	30	BC107C	12	BC174	15	BC550	14	BD201	80	BF164	50	BFR62	24	MP5A06	20	TIP30B	42	2N708	14	2N2904	24	2N3823	60
AC126	22	BC108	10	BC175	35	BC556	14	BD202	80	BF165	50	BFR79	28	MP5A55	20	TIP30C	44	2N711	30	2N2904A	24	2N3903	12
AC127	20	BC108B	11	BC177	14	BC558	13	BD201/202	1.70	BF167	24	BFR80	28	MP5A56	20	TIP31	38	2N717	30	2N2905	24	2N3904	12
AC128	20	BC108B	11	BC178	14	BC559	14	BD203	80	BF176	24	BFW10	55	ND120	18	TIP31A	40	2N718	25	2N2905A	24	2N3905	12
AC128K	37	BC108C	12	BC179	14	BC559	14	BD204	80	BF177	24	BFX30	30	OC20	1.85	TIP31C	44	2N726	18	2N2906	18	2N3906	12
AC132	26	BC109	10	BC180	12	BCY30	80	BD204	80	BF177	24	BFX30	30	OC20	1.85	TIP32	38	2N727	29	2N2907	20	2N4058	12
AC141	26	BC109A	11	BC181	10	BCY31	80	BD203/204	80	BF178	25	BFX84	24	OC22	1.50	TIP32A	40	2N743	20	2N2907A	22	2N4060	14
AC141K	40	BC109B	11	BC182	10	BCY32	85	BD205	80	BF179	30	BFX85	26	OC23	1.50	TIP32B	42	2N744	20	2N2923	15	2N4061	12
AC142	50	BC109C	12	BC182L	10	BCY33	80	BD206	80	BF180	30	BFX86	26	OC24	1.35	TIP32C	44	2N914	20	2N2924	15	2N4062	12
AC142K	24	BC113	16	BC193	10	BCY34	80	BD207	80	BF182	30	BFX88	26	OC25	1.00	TIP41A	44	2N918	20	2N2925	15	2N4220	12
AC176K	40	BC115	18	BC184	10	BCY71	15	BD208	80	BF183	30	BFX90	55	OC28	90	TIP41B	46	2N929	20	2N2926	15	2N4221	12
AC187	25	BC116	19	BC184L	10	BCY72	15	BD222	47	BF184	22	BFY50	20	OC29	95	TIP41C	48	2N930	18	2N2926Y	09	2N4284	28
AC187K	40	BC116A	20	BC186	15	BCZ10	70	BD225	47	BF185	22	BFY51	20	OC36	90	TIP42A	44	2N946	40	2N2926O	09	2N4285	28
AC188	25	BC117	22	BC187	18	BCZ11	70	BD232	85	BF186	26	BFY52	20	OC36	90	TIP42B	46	2N1131	24	2N2926R	09	2N4286	28
AC188K	40	BC118	17	BC207	11	BCZ12	70	BD233	85	BF187	26	BFY53	20	OC41	20	TIP42C	48	2N1132	24	2N2926S	09	2N4287	28
AC189	25	BC118	17	BC207	11	BCZ12	70	BD234	85	BF188	26	BFY54	20	OC42	20	TIP2955	50	2N1302	25	2N3010	20	2N4288	28
AC189K	40	BC118	17	BC207	11	BCZ12	70	BD235	85	BF189	26	BFY55	20	OC43	20	TIP3055	50	2N1303	25	2N3011	20	2N4289	28
AC197	50	BC119	29	BC208	11	BD106	50	BD236	58	BF190	10	BI20	38	OC45	20	TIS43	22	2N1304	28	2N3053	22	2N4290	28
AC198	50	BC120	35	BC209	12	BD115	50	BD237	65	BF196	12	BI20	38	OC70	24	TIS90	20	2N1305	28	2N3054	22	2N4291	28
AC198K	40	BC120	35	BC209	12	BD115	50	BD238	65	BF197	12	BI20	38	OC70	24	TIS91	22	2N1306	35	2N3055	22	2N4292	28
AC199	50	BC125	25	BC212	10	BD116	50	BD239A	65	BF198	12	BI20	38	OC71	24	TIS92	22	2N1307	35	2N3402	21	2N4293	28
AC200	50	BC126	30	BC212L	10	BD123	65	BD239A	65	BF199	12	BI20	38	OC72	24	TIS93	22	2N1308	35	2N3403	21	2N4294	28
AC201	50	BC134	18	BC213	10	BD123	65	BD240A	50	BF199	12	BI20	38	OC73	24	TIS94	22	2N1309	35	2N3404	21	2N4295	28
AD130	75	BC135	18	BC214	10	BD131	35	BD240A	50	BF199	12	BI20	38	OC74	24	TIS95	22	2N1310	35	2N3405	21	2N4296	28
AD140	70	BC136	20	BC214L	10	BD132	35	BD239A	65	BF200	30	BSX20	21	OC75	30	ZTX107	10	2N1309	40	2N3406	21	2N4300	28
AD142	85	BC137	20	BC225	26	BD131/132	35	BD240A	50	BF200	30	BSX20	21	OC76	35	ZTX108	10	2N1599	35	2N3405	21	2N4301	28
AD143	85	BC138	28	BC226	36	BD133	35	BD241	45	BF224	20	BSY95	13	OC77	50	ZTX109	10	2N1613	28	2N3416	16	2N5135	10
AD149	85	BC139	32	BC227	11	BD136	35	BD242	45	BF240	17	BSY95A	13	OC79	40	ZTX300	12	2N1711	30	2N3415	16	2N5136	10
AD161	40	BC140	25	BC238	38	BD136	35	BD243	45	BF241	17	BSY95A	13	OC79	40	ZTX300	12	2N1711	30	2N3415	16	2N5136	10
AD162	40	BC141	28	BC239	15	BD136	35	BD244	45	BF241	17	BSY95A	13	OC79	40	ZTX300	12	2N1711	30	2N3415	16	2N5136	10
AD161/162	80	BC142	25	BC251	15	BD137	35	BD245	45	BF241	17	BSY95A	13	OC79	40	ZTX300	12	2N1711	30	2N3415	16	2N5136	10
M/P	80	BC143	25	BC251A	16	BD138	36	BD246	45	BF241	17	BSY95A	13	OC79	40	ZTX300	12	2N1711	30	2N3415	16	2N5136	10
AF14	50	BC145	46	BC260	11	BD139	38	BD247	45	BF241	17	BSY95A	13	OC79	40	ZTX300	12	2N1711	30	2N3415	16	2N5136	10
AF115	50	BC145	46	BC260	11	BD139	38	BD248	45	BF241	17	BSY95A	13	OC79	40	ZTX300	12	2N1711	30	2N3415	16	2N5136	10
AF116	50	BC147	09	BC301	28	BD139/140	38	BD249	45	BF241	17	BSY95A	13	OC79	40	ZTX300	12	2N1711	30	2N3415	16	2N5136	10
AF117	50	BC148	09	BC302	29	M/P	80	BD250	45	BF241	17	BSY95A	13	OC79	40	ZTX300	12	2N1711	30	2N3415	16	2N5136	10
AF118	65	BC149	09	BC303	28	BD155	50	BD251	45	BF241	17	BSY95A	13	OC79	40	ZTX300	12	2N1711	30	2N3415	16	2N5136	10
AF124	50	BC150	20	BC304	28	BD175	60	BD252	45	BF241	17	BSY95A	13	OC79	40	ZTX300	12	2N1711	30	2N3415	16	2N5136	10
AF125	50	BC151	20	BC307	13	BD176	60	BD253	45	BF241	17	BSY95A	13	OC79	40	ZTX300	12	2N1711	30	2N3415	16	2N5136	10
AF126	50	BC152	20	BC327	13	BD177	60	BD254	45	BF241	17	BSY95A	13	OC79	40	ZTX300	12	2N1711	30	2N3415	16	2N5136	10
AF127	50	BC153	25	BC328	13	BD178	68	BD255	45	BF241	17	BSY95A	13	OC79	40	ZTX300	12	2N1711	30	2N3415	16	2N5136	10
AF139	38	BC154	19	BC337	13	BD179	75	BD256	45	BF241	17	BSY95A	13	OC79	40	ZTX300	12	2N1711	30	2N3415	16	2N5136	10
AF239	42	BC157	10	BC338	13	BD180	75	BD257	45	BF241	17	BSY95A	13	OC79	40	ZTX300	12	2N1711	30	2N3415	16	2N5136	10
AS102	1.90	BC158	10	BC384	14	BD185	68	BD258	45	BF241	17	BSY95A	13	OC79	40	ZTX300	12	2N1711	30	2N3415	16	2N5136	10
AS103	1.80	BC159	10	BC385	14	BD186	68	BD259	45	BF241	17	BSY95A	13	OC79	40	ZTX300	12	2N1711	30	2N3415	16	2N5136	10
AS126	50	BC160	26	BC441	30	BD187	68	BD260	45	BF241	17	BSY95A	13	OC79	40	ZTX300	12	2N1711	30	2N3415	16	2N5136	10
AS27	50	BC161	38	BC460	32	BD188	75	BD261	45	BF241	17	BSY95A	13	OC79	40	ZTX300	12	2N1711	30	2N3415	16	2N5136	10
AS28	50	BC167	11	BC461	32	BD189	78	BD262	45	BF241	17	BSY95A	13	OC79	40	ZTX300	12	2N1711	30	2N3415	16	2N5136	10
AS29	50	BC168	10	BC477	20	BD190	78	BD263	45	BF241	17	BSY95A	13	OC79	40	ZTX300	12	2N1711	30	2N3415	16	2N5136	10
AU104	1.90	BC169	10	BC478	20	BD191	80	BD264	45	BF241	17	BSY95A	13	OC79	40	ZTX300	12	2N1711	30	2N3415	16	2N5136	10
AU110	1.90	BC170	09	BC479	20	BD192	80	BD265	45	BF241	17	BSY95A	13	OC79	40	ZTX300	12	2N1711	30	2N3415	16	2N5136	10
AU113	1.90	BC170	09	BC479	20	BD192	80	BD266	45	BF241	17	BSY95A	13	OC79	40	ZTX300	12	2N1711	30	2N3415	16	2N5136	10
BC107	10	BC171	09	BC547	10	BD198	95	BD267	45	BF241	17	BSY95A	13	OC79	40	ZTX300	12	2N1711	30	2N3415	16	2N5136	10
BC107A	11	BC172	09	BC548	10	BD199	99	BD268	45	BF241	17	BSY95A	13	OC79	40	ZTX300	12	2N1711	30	2N3415	16	2N5136	10

## DIODES


AA119	08	BB104	30	BY176	75	OA79	10
AA120	08	BAX13	07	BY206	30	OA81	10
AA129	09	BAX16	08	BY210/6009	30	OA85	10
AA130	09	BY100	22	BY210	45	OA90	07
AA131	09	BY101	22	BY211	45	OA91	07
AA132	09	BY102	22	BY212	40	OA95	07
BA100	10	BY114	22	BY213	40	OA182	13
BA102	20	BY124	22	BY216	41	OA200	08
BA149	09	BY126	11	BY217	36	OA202	08
BA148	15	BY127	12	BY218	36	IN34A	07
BA154	14	BY128	16	BY219	36	IN34A	07
BA155	14	BY130	17	OA5	60	IN914	04
BA156	14	BY133	21	OA10	35	IN916	05
BA173	15	BY156					



CHOOSE FROM OVER  
20 TOP QUALITY  
MODULES


## AL20A-30A

AUDIO  
AMPLIFIER  
MODULES

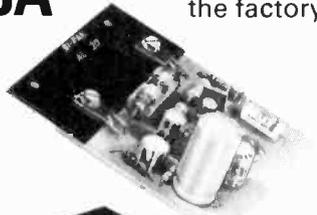

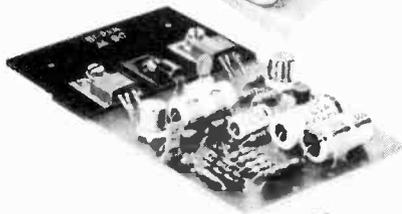
## AL80

AUDIO  
AMPLIFIER  
MODULE  
35 Watts RMS



## AL120


AUDIO AMPLIFIER  
50W RMS

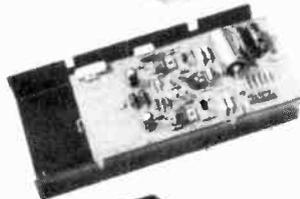
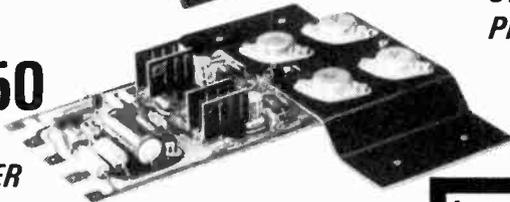
## AL250


POWER  
AMPLIFIER

With integral heat  
sink and short-  
circuit protection



## Stereo 30

COMPLETE  
AUDIO  
CHASSIS

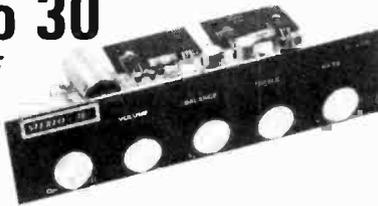


BI-PAK Audio Modules are famous for their variety, quality of design and ruggedness. For over 10 years BI-PAK have been suppliers to manufacturers of high quality audio equipment throughout the world – to date, well over 100,000 modules have been sold – this is why discerning amateur enthusiasts insist on using BI-PAK modules in their equipment. They know that every item is designed and tested to do the job for which it is intended before it leaves the factory. Whatever you are building, there is a kit or module

in the BI-PAK range to suit your every need from 5 watts to 125 watts, from amplifiers to equalisers. AND if you cannot see what you require in this

advertisement, just write or phone us – we are waiting to help you!
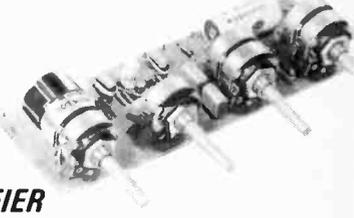
## AL60

AUDIO  
AMPLIFIER  
MODULE  
25 Watts RMS




## PA12

STEREO  
PRE-AMPLIFIER

## PA100 & PA200

STEREO  
PRE-AMPLIFIER

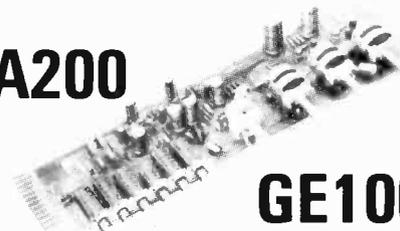

## GE100

10 CHANNEL  
MONOGRAPHIC

### Latest addition

MM100 Suitable for disco mixer.

MM100G Suitable for guitar pre-amp-mixer.



**£12.43**  
each

# BI-PAK

COMPLETELY  
GUARANTEED

### AMPLIFIERS

AL10. 3 watt Audio Amplifier Module 22-32v supply.	<b>£3.08</b>
AL20. 5 watt Audio Amplifier Module 22-32v supply.	<b>£3.57</b>
AL30A. 7-10 watt Audio Amplifier Module 22-32v supply.	<b>£4.16</b>
AL60. 15-25 watt Audio Amplifier Module 30-50v supply.	<b>£5.15</b>
AL80. 35 watt Audio Amplifier Module 40-60v supply.	<b>£8.07</b>
AL120. 50 watt Audio Amplifier Module 50-70v supply.	<b>£13.14</b>

AL250. 125 watt Audio Amplifier Module 50-80v supply. **£19.60**

### STEREO PRE-AMPLIFIERS

PA12. Supply voltage 22-32v input sensitivity 300mv. Suit: AL10/AL20/AL30.	<b>£8.55</b>
PA100. Supply voltage 24-36v inputs: Tape, Tuner, Mag P.U. Suit: AL60, AL80.	<b>£17.65</b>
PA200. Supply voltage 35-50v inputs: Tape, Tuner, Mag P.U. Suit: AL80/AL120/AL250.	<b>£18.24</b>

## BI-KITS

- STA5.** 5 watts per channel Stereo Amplifier. Kit consisting of: 2xAL20 amplifiers, 1xPA 12 pre-amplifier, 1xPS12 power supply, 1x2036 transformer and necessary wiring diagram. **£19.52**
- STA10.** 10 watts per channel Stereo Amplifier. Kit consisting of: 2xAL30 amplifiers, 1xPA12 pre-amplifier, 1xPS12 power supply, 1x2036 transformer and necessary wiring diagrams. **£20.63**
- STA15.** 15 watts per channel Stereo Amplifier. Kit consisting of: 2xAL60 amplifiers, 1xPA100 pre-amplifier, 1xSPM80 power supply, 1x2034 transformer, 2x coupling capacitors for 8 ohms 470mfd 30v and necessary wiring diagram. **£36.76**

## BI-KITS

- STA25.** 25 watts per channel Stereo Amplifier. Kit consisting of: 2xAL60 amplifiers, 1xPA100 pre-amplifier, 1xSPM120/45 power supply, 1x2040 transformer, coupling capacitors for 8 ohms 470 mfd 45v, 1xreservoir capacitor 2200mfd 100v and necessary wiring diagram. **£40.50**
- STA35.** 35 watts per channel Stereo Amplifier. Kit consisting of: 2xAL80 amplifiers, 1xPA200 pre-amplifier, 1x2035 transformer, 2x coupling capacitors 470mfd at 50v for 8 ohms, 1xreservoir capacitor 2200mfd 100v and necessary wiring diagram. **£45.76**


## BI-KITS

- STA50.** 50 watts per channel Stereo Amplifier. Kit consisting of: 2xAL120 amplifiers, 1xPA200 pre-amplifier, 1x2041 transformer, 2xcoupling capacitors 1000mfd 63v, 1xSPM120/65, 1xreservoir capacitor 3300mfd 100v and necessary wiring diagram. **£59.89**
- STA100.** 100 watts per channel Stereo Amplifier. Kit consisting of: 2xAL250 amplifiers, 1xPA200 pre-amplifier, 2xSPM120/65 power supplies, 2x2041 transformers, 2xcoupling capacitors 1000mfd 100v and necessary wiring diagram. **£84.68**

## PS12 POWER SUPPLY MODULE




## SPM80 STABILISED POWER SUPPLY

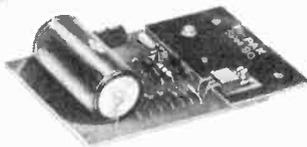

## SPM120 STABILISED POWER SUPPLY



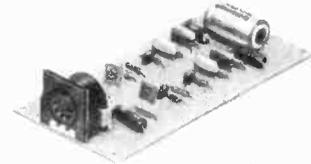
## MPA30 MAGNETIC CARTRIDGE PRE-AMPLIFIER




## BP124 SIREN ALARM MODULE


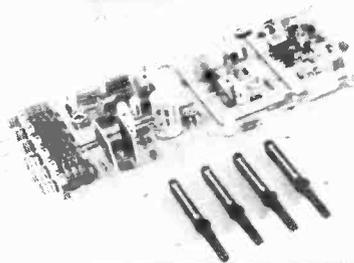
## S450 STEREO FM TUNER Fitted with phase lock-loop



## Mk II

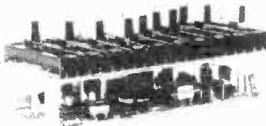

## EQUALISER

### MONO PRE-AMPLIFIERS

- MM100. Supply voltage 40-65v inputs: Tape, Mag P.U. Microphone Max output 500mv. **£12.43**
- MM100G. Supply voltage 40-65v inputs: 2 Guitars. Microphones Max output 500mv. **£12.43**

### POWER SUPPLIES

- PS12. 24v Supply. Suit: 2xAL10, 2xAL20, 2xAL30 & PA12/S.450. **£1.65**
- SPM80. 33v Stabilised supply. Suit: 2xAL60, PA100 to 15 watts. **£4.84**
- SPM120/45. 45v Stabilised supply. Suit: 2xAL60, PA100 to 25 watts. **£6.38**
- SPM120/55. 55v Stabilised supply. Suit: 2xAL80, PA200. **£6.38**
- SPM120/65. 65v Stabilised supply. Suit: 2xAL120, PA200, 1xAL250. **£6.38**
- SG30. 15-0-15 Stabilised power supply for 2xGE100MK11. **£3.80**

### MISCELLANEOUS


- MPA30. Stereo Magnetic Cartridge Pre-Amplifier - input 3.5mv Output 100mv. **£3.27**
- S.450. Stereo FM Tuner Supply Voltage 20-30v - Varicap tuned. **£25.56**
- STEREO 30. Complete 7 watt per channel Stereo Amplifier 80ard - includes amps, pre-amp, power supply, front panel, knobs etc - requires 2039 Transformer. **£21.09**

Transformers are not included with power supplies.  
SPM120 Range also require reservoir and output capacitors.

BP124. 5 watt 12v max. - Siren Alarm Module. <b>£3.85</b>	2041. 2 amp 0-55v-65v. Suit: SPM120/55, SPM120/65v. <b>£8.46</b>
GE100MK11. 10 channel mono-graphic equaliser, complete with sliders and knobs. <b>£23.00</b>	2039. 1 amp 0-20v. Suit Stereo 30. <b>£3.50</b>
VPS30. Variable regulated stabilised power supply 2-30v 0-2 amps. <b>£7.60</b>	2043. 150mA 15-0-15v. Suit: SG30. <b>£2.40</b>
PS250. Consists - 1 capacitor & 4 diodes for constructing unstabilised power supply for AL250 to 125 watts. <b>£2.90</b>	
	<b>ACCESSORIES</b>
<b>TRANSFORMERS</b>	139. Teak Cabinet. Suit: Stereo 30, 320x235x81mm. <b>£7.00</b>
2034. 1.7 amp 35v. Suit SPM80. <b>£4.90</b>	140. Teak Cabinet. Suit: STA15, 425x290x95mm. <b>£9.50</b>
2035. 2 amp 55v. <b>£6.65</b>	FP100. Front Panel for PA100 & PA200. <b>£1.80</b>
2036. 750mA 17v. Suit: PS12. <b>£2.85</b>	BP100. Back Panel for PA100 & PA200. <b>£1.60</b>
2040. 1.5 amp 0-45v-55v. Suit: SPM120/45, SPM120/55v. <b>£6.45</b>	GE100FP. Front Panel for one GE100MK11. <b>£1.75</b>
	2240. Kit of parts including Teak Cabinet, Chassis, Sockets and Knobs etc. (To house STA15 Amplifier.) <b>£19.95</b>

Full data sheets are available FREE on request, please enclose a S.A.E.
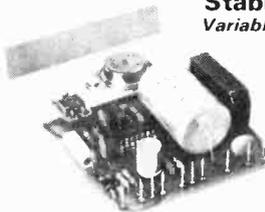
## VPS30 REGULATED VARIABLE STABILISED POWER SUPPLY



### Stabilised Power Supply Kit Variable from 2-30 volts and 0-2 Amps

#### Kit includes:

- 1 - VPS30 Module.
- 1 - 25 volt 2 Amp transformer.
- 1 - 0-50v 2" Panel Meter.
- 1 - 0-2 Amp 2" Panel Meter.
- 1 - 470 ohm wirewound potentiometer.
- 1 - 4K7 ohm wirewound potentiometer.

Wiring Diagram Included.

### KIT £20 + V.A.T.

Access and Barclaycards accepted - just telephone our Orderline - Ware (STD 0920) 3182. All prices exclude V.A.T., add 50p. postage per order. Terms: C.W.O., cheques, Postal Orders payable to Bi-Pak.

# BI-PAK – SATISFACTION OR YOUR MONEY BACK!

## PLUGS AND SOCKETS

1625	2mm Plug RED	£0.16
1626	2mm Plug BLACK	£0.16
1628	2mm Socket RED	£0.16
1629	2mm Socket BLACK	£0.16
1634	4mm Plug BLACK	£0.16
1637	4mm Plug RED	£0.16
1640	4mm Socket BLACK	£0.16
1643	4mm Socket RED	£0.16
1652	2 Pin DIN Chassis Socket	£0.08
1654	5 Pin 180° DIN Chassis Socket	£0.12
1655	5 Pin 240° DIN Chassis Socket	£0.12
1656	2.5mm Chassis Socket	£0.10
1657	3.5mm Chassis Socket	£0.18
1658	Metal Std. Jack Chassis Socket (mono)	£0.24
1659	Metal Std. Jack Chassis Socket (stereo)	£0.09
1660	Single Phono socket	£0.12
1661	Double Phono Socket	£0.22
1662	Coax surface socket	£0.22
1663	Coax Flush Socket	£0.20
1664	Plastic Std. Jack Socket (mono)	£0.32
1665	Plastic Std. Jack Socket (stereo) for headphones	£0.18
1666	Car Aerial Chassis Socket	£0.16
1667	AC Chassis Socket	£0.22
1668	4 Way Phono Chassis Socket	£0.32
1669	Plastic Std. Jack Chassis socket stereo switched	£0.32
1670	AC switched non rev. socket	£0.10
1672	2 Pin DIN line socket	£0.17
1674	5 Pin 180° DIN line socket	£0.20
1675	5 Pin 240° DIN line socket	£0.12
1676	2.5mm Plastic line socket	£0.12
1677	3.5mm Plastic line socket	£0.17
1678	Std. jack plastic line socket (mono)	£0.30
1679	Std. jack metal line socket (mono)	£0.22
1680	Std. jack plastic line socket (stereo)	£0.38
1681	Std. jack metal line socket (stereo)	£0.16
1682	Phono in line metal socket	£0.34
1684	Coax line socket	£0.14
1685	Coax back-back socket	£0.18
1686	AC linesocket (2 pin USA Type)	£0.12
1687	Phono in line plastic socket	£0.20
1688	Phono back-back socket	£0.10
1689	2 Pin DIN plug	£0.14
1692	5 Pin 180° DIN plug	£0.15
1693	5 Pin 240° DIN plug	£0.25
1696	2.5mm Plug (Metal)	£0.12
1697	3.5mm Plug (Plastic)	£0.16
1698	3.5mm Plug (Metal)	£0.16
1699	Std. Plastic Jack Plug (Mono)	£0.30
1700	Std. Metal Jack Plug (Mono)	£0.35
1701	Std. Metal Jack Plug (Stereo)	£0.21
1702	Plastic Phono Plug	£0.22
1703	Car Aerial Plug	£0.20
1704	Coax TV Plug	£0.12
1705	Right Angle Jack Plug (Mono)	£0.22
1706	2.5mm Plastic Plug	£0.22
1707	Std. Plastic Jack Plug (Stereo)	£0.12
1708	Metal Phono Plug	£0.22
1709	2.1mm DC Plug	£0.12
1710	2.5mm DC Plug	£0.16
1711	AC Plug (2 pin USA Type)	£0.17
1712	AM Aerial Plug	£0.15
1713	Cassette AC Input Plug	£0.13
1714	FM Aerial Plug	£0.40
1715	PL 259 Plug	£0.40
1716	SO239 Socket 4 hole fixing	£0.40
1717	SO239 Socket single hole fixing	£0.40
1718	PL258 Double Ended Female Coupler	£0.16
1719	NC555 Reducer for PL259 (Small)	£0.16
1720	NC556 Reducer for PL259 (Large)	£0.75
1721	M359 Right Angle Coupler PL259 SO239	£0.85
1722	M358 T Connector Female-Male-Female	£0.60
1723	NC563 In-line Coupler PL259 x 2	£0.64
1724	BNC15 50 ohm standard plug	£0.75
1725	BNC1502 Chassis mounting socket	£0.70
1726	BNC1503 Chassis mounting socket single hole fixing	£0.85
1727	BNC1520 BNC male to SO239 female	£0.85
1728	BNC1521 BNC female to PL259 male	£0.80
1729	Junction Box one in two out	£1.00
1730	Low loss splitter	£0.00

## BREADBOARD

2195	EXP325	£1.84
2196	EXP350	£3.62
2197	EXP650	£4.14
2198	EXP300	£6.61
2199	EXP48	£2.65
2200	EXP600	£7.25

## VEROBOARD

2201	2.5" x 5" .1 copper	£0.76
2202	3.5" x 3.75" .1 copper	£0.66
2203	2.5" x 17" .1 copper	£2.28
2204	3.75" x 5" .1 copper	£0.86
2205	3.75" x 3.75" .1 copper	£2.96
2206	3.75" x 17" .1 copper	£3.90
2207	4.75" x 17.9" .1 copper	£0.92
2208	2.5" x 1" 5 in pack	£1.92
2209	3.75" x 17" .1 Plain	£0.48
2210	3.75" x 2.5" .1 Plain	£0.72
2211	5.0" x 3.75" .1 Plain	£0.52
2212	vero pins Double sided .040mm .1" (in 100's)	£0.52
2213	vero pins Single sided .040mm .1" (in 100's)	£3.26
2214	DIP Breadboard	£1.06
2215	Vero Cutter	£1.46
2216	Insertion Tool .1	£7.00
2218	12 volt mini drill	£0.07
2219	Right Angle Bracket 1 1/2" x 1 1/2"	£0.06
2220	Right Angle Bracket 1 1/2" x 3/4"	£0.06

## EARPIECES & BUZZERS

500	Solid State Buzzer 4-25v	£0.75
501	Crystal Earpiece	£0.42
502	8 ohm Earpiece 2.5mm Plug	£0.18
503	8 ohm Earpiece 3.5mm Plug	£0.18
505	200 ohm Earpiece 3.5mm Plug	£0.44

## COMPONENT PACKS

C26	300 Preformed carbon resistors mixed 1/4-w	£1.00
C27	502-10 watt wire wound resistors mixed	£1.00
C28	300 Approx Resistors mixed values (count by weight)	£1.00
C29	2000 Approx Capacitors mixed values and types (count by weight)	£1.00
C30	60 Precision Resistors 1-5% tol.	£1.00
C31	100 Approx 1/8 watt min Resistors mixed values	£1.00
C32	6 Pieces Ferrite beads	£1.00
C33	60 Metres Single strand wire assorted colours	£1.00
C34	15 Reed switches glass type	£1.00
C35	5 Micro switches assorted types including min.	£1.00
C36	6 Assorted Audio jack sockets and plugs	£1.00
C37	100 Disc ceramic caps mixed values	£1.00
C38	20 Assorted pots	£1.00
C39	40 C280 type capacitors metal foil	£1.00
C40	60 Electrolytics assorted	£1.00
C41	50 Assorted polyester/polystyrene	£1.00
C42	60 Low voltage Electrolytics mixed values up to 10v.	£1.00
C43	15 Assorted slider pots	£1.00
C44	10 Dual gang pots log and lin assorted	£1.00
C45	1 Pack assorted Hardware nuts/bolts etc.	£1.00
C46	10 Assorted switches slide/rocker/mains	£1.00
C47	3 Relays 24v coil	£1.00
C48	20 Assorted knobs push, screw and slider types	£1.00
C49	10 Assorted Tag strips and panels	£1.00
C50	4 Wave change switches rotary	£1.00
C51	1 Pack of assorted PVC sleeving and markers	£1.00
C52	100 1/2 watt resistors mixed values	£1.00
C53	35 Presets assorted type and values	£1.00
C54	40 Metres stranded wire assorted colours	£1.00
C55	10 Assorted Din/sockets/Coax/speakers/phone	£1.00
C56	10 Assorted plugs Din/coax/speakers/etc.	£1.00
C57	10 Metres assorted cable. Mains/speaker/coax/microphone	£1.00
C58	100 sq in copper clad board single side paper	£1.00
C59	75 sq in copper clad fibreglass board	£1.00
C60	15 Assorted IC sockets 8, 14, 16 pin	£1.00

## BUDGET STEREO HEADPHONES

BLACK WITH PADDED EARCUPS  
IMPEDANCE 8 ohms  
FREQUENCY RESPONSE  
30-18,000 HZ  
WEIGHT 300gms  
**£4.20**

## GOOD QUALITY STEREO HEADPHONES

DOUBLE PADDED HEAD BAND  
CIRCULAR VENTED PADDED  
EARPIECES  
BLACK AND ALUMINIUM FINISH  
IMPEDANCE 8 ohms  
FREQUENCY RESPONSE  
20-19,000 HZ  
WEIGHT 350gms  
**£8.25**

## SUPERIOR QUALITY STEREO HEADPHONES

WIDE BLACK PADDED HEAD  
BAND AND MATT  
ALUMINIUM EARCUPS  
IMPEDANCE 8 ohms  
FREQUENCY RESPONSE  
15-25,000 HZ  
WEIGHT 290gms  
**£15.85**

## BABANI BOOKS

No	TITLE	PRICE
BP160	Coil Design and Construction Manual	1.25
BP202	Handbook of Integrated Circuits (IC's) Equivalents & Substitutes	1.45
BP205	First Book of Hi-Fi Loudspeaker Enclosures	0.95
BP207	Practical Electronics Science Projects	0.75
BP208	Practical Stereo and Quadrophony Handbook	0.75
BP211	First Book of Diode Characteristics Equivalents and Substitutes	1.25
BP212	Electronic Circuits for Model Railways	1.00
BP213	Audio Enthusiasts Handbook	0.85
BP218	Build Your Own Electronic Experiments Laboratory	0.85
BP219	Solid State Novelty Projects	0.85
BP220	Build Your Own Solid State Hi-Fi and Audio Accessories	1.25
BP221	28 Tested Transistor Projects	1.25
BP222	Solid State Short Wave Receivers for Beginners	1.25
BP223	50 Projects Using IC CA3130	1.25
BP224	50 CMOS IC Projects	1.25
BP225	A Practical Introduction to Digital IC's	1.20
BP226	How to Build Advanced Short Wave Receivers	1.25
BP227	Beginners Guide to Building Electronic Projects	1.25
BP228	Essential Theory for the Electronics Hobbyist	0.70
BP6	Engineers and Machinists Reference Tables	0.35
BP7	Radio and Electronic Colour Codes and Data Chart	1.10
BP14	Second Book of Transistor Equivalents and Substitutes	0.75
BP23	First Book of Practical Electronic Projects	0.60
BP24	52 Projects Using IC741	0.60
BP27	Giant Chart of Radio Electronic Semiconductor and Logic Symbols	0.60
BP28	Resistor Selection Handbook (International Edition)	0.85
BP29	Major Solid State Audio Hi-Fi Construction Projects	1.35
BP32	How to Build Your Own Metal and Treasure Locators	1.25
BP33	Electronic Calculator Users Handbook	1.25
BP34	Practical Repair and Renovation of Colour TVs	1.25
BP35	Handbook of IC Audio Pre-amplifier & Power Amplifier Construction	0.75
BP36	50 Circuits Using Germanium, Silicon and Zener Diodes	1.25
BP37	50 Projects Using Relays, SCR's and TRIACs	0.75
BP38	Fun and Games with Your Electronic Calculator	1.50
BP39	50 (FT) Field Effect Transistor Projects	2.50
BP40	Digital IC Equivalents and Pin Connections	2.75
BP41	Linear IC Equivalents and Pin Connections	0.95
BP42	50 Simple L.E.D. Circuits	1.50
BP43	How to Make Walkie-Talkies	1.75
BP44	IC555 Projects	1.75
BP45	Projects in Opto-Electronics	1.35
BP46	Radio Circuits Using IC's	1.35
BP47	Mobile Discotheque Handbook	1.35
BP48	Electronic Projects for Beginners	1.45
BP49	Popular Electronic Projects	1.35
BP50	IC LM3900 Projects	1.50
BP51	Electronic Music and Creative Tape Recording	1.50
BP52	Long Distance Television Reception (TV-DX) for the Enthusiast	1.95
BP53	Practical Electronic Calculations and Formulae	2.25
BP54	Your Electronic Calculator and Your Money	1.35
BP55	Radio Stations Guide	1.75
BP56	Electronic Security Devices	1.45
BP57	How to Build Your Own Solid State Oscilloscope	1.50
BP58	50 Circuits Using 7400 Series IC's	1.35
BP59	Second Book of CMOS IC Projects	1.50
BP60	Practical Construction of Pre-amps, Tone Controls, Filters & Attn.	1.45
BP61	Beginners Guide to Digital Techniques	0.95
BP62	Elements of Electronics - Book 2	2.25
BP63	Elements of Electronics - Book 2	2.25
BP64	Elements of Electronics - Book 3	2.25
BP65	Single IC Projects	1.50
BP66	Beginners Guide to Microprocessors and Computing	1.75
BP67	Counter, Driver and Numerical Display Projects	1.75
BP68	Choosing and Using your Hi-Fi	1.65
BP69	Electronic Games	1.75
BP70	Transistor Radio Fault-Finding Chart	0.50
BP71	Electronic Household Projects	1.75
BP72	A Microprocessor Primer	1.95
BP73	Remote Control Projects	1.75
BP74	Electronic Music Projects	1.75
BP75	Electronic Test Equipment Construction	1.75
BP76	Power Supply Projects	1.75
BP77	Elements of Electronics - Book 4	2.95
BP78	Practical Computer Experiments	1.75
BP79	Radio Control for Beginners	1.75
BP80	Popular Electronic Circuits - Book 1	1.95

## LAST MINUTE ITEMS

PRICE

*We offer the following Fairchild Power Transistors at much reduced prices*

TYPE	Pol	£ p
2N3054	PNP	0.32
2N3713	PNP	0.35
2N3714	PNP	0.36
2N3716	PNP	0.36
2N3767	PNP	0.34
2N3789	PNP	0.45
2N4901	PNP	0.40
2N4903	PNP	0.42
2N4910	PNP	0.25
2N4911	PNP	0.27
2N4912	PNP	0.30
2N4913	PNP	0.30
2N4914	PNP	0.32
2N4915	PNP	0.34
2N5630	PNP	0.50
2N5631	PNP	0.60
2N5838	PNP	0.60
2N5886	PNP	0.60
2N6031	PNP	0.70
2N6123	PNP	0.25
2N6129	PNP	0.25
2N6130	PNP	0.30
2N6131	PNP	0.32
2N6133	PNP	0.32
2N6134	PNP	0.35
2N6487	PNP	0.35
2N6490	PNP	0.40
BD220	PNP	0.25
BD223	PNP	0.30
BD225	PNP	0.30
FT49	NPN	0.25
FT317a	PNP	0.28
FT417a	PNP	0.32
FT417b	PNP	0.34
FT423	PNP	0.40
MJ802	PNP	0.45
TIP61A	NPN	0.25
TIP61B	NPN	0.26
TIP62A	PNP	0.28
TIP62B	PNP	0.28
TIP110	PNP	0.30
TIP111	PNP	0.32
TIP112	PNP	0.35

## BRIDGE RECTIFIERS

10 Amp RMS	1.40
BR10/50v	1.40
BR10/100v	1.50
BR10/200v	1.60
BR10/400v	1.90
25 Amp RMS	1.85
BR25/50v	1.85
BR25/100v	1.95
BR25/200v	2.05
BR25/400v	2.90
BY164	51

Access and Barclaycards accepted – just telephone our Orderline – Ware (STD 0920) 3182. All prices exclude V.A.T., add 50p postage per order. Terms: C.W.O., cheques, Postal Orders payable to Bi-Pak.

# THE BI-PAK OPTO SHOW

## LED's

1501	TIL209 Red LED .125"	£0.10
1502	TIL211 Green LED .125"	£0.18
1503	TIL213 Yellow LED .125"	£0.18
1504	FLV117 Red LED 2"	£0.10
1505	FLV310 Green LED 2"	£0.18
1506	FLV410 Yellow LED 2"	£0.18
1507	2nd Grade LED pack 10 assorted	£0.80
1522	MIL32 Clear Illuminating Red LED .125"	£0.12
1523	FLV111 Clear Illuminating Red LED 2"	£0.12
1524	COX21 Red Flashing LED	£0.65
1525	COX95 two colour LED	£0.75

## OPTO-ISOLATORS

1515	Opto-isolator IL74 Single	£0.55
1516	Opto-isolator LD74 Dual	£1.18
1517	Opto-isolator LQ74 Quad	£2.10

## 7 SEGMENT LED DISPLAYS

1508	BDL307 7 segment LED display .3"	£0.80
1509	BDL527 dual 7 segment LED display .5"	£1.80
1510	BDL707 7 segment LED display .3"	£0.98
1511	BDL747 7 segment LED display .6"	£1.75
1512	BDL727 dual 7 segment LED display .5"	£1.90

## MISCELLANEOUS

1514	ORP12 Light Dependent Resistor	£0.60
1518	Photo transistor P20 NPN	£0.60
1519	Photo Darlington MEL11 NPN	£0.26
1520	Photo transistor OCP71 PNP	£0.40
1526	FPE100 Infra Red Emitter	£0.38
1527	CQY89 Infra Red LED	£0.38

## Beginners Pak: No. 1

### 100 Transistors

A pack of well known transistors. As used in many popular projects. A must for beginners (and very useful to experienced constructors too).

10	BC107/B	T018	Metal	NPN
10	BC237	T092	Plastic	NPN
5	BC177/B	T018	Metal	PNP
5	BC251	T092	Plastic	PNP
10	BFY51-BC141	T039	Metal	NPN
5	BC160	T039	Metal	PNP
5	2N3055	T03	Metal	NPN
2	BD312/MJ2955	T03	Metal	PNP
5	TIP29-31	T0220	Plastic	NPN
2	TIP30-32	T0220	Plastic	PNP
10	OC71-76	Germanium	Metal	PNP
5	AC128-188	Germanium	Metal	PNP
5	AC176	Germanium	Metal	PNP
5	OC44-45	Germanium	Metal	PNP
5	TIS43-UT46	Unijunction	Plastic	F.E.T.
5	2N3819	F.E.T.		
2	MEL11	Photo Transistor	Plastic	NPN
2	BD131	T0126	Plastic	PNP
2	BD132	T0126	Plastic	PNP

100 TOTAL

All devices - brand new and full spec as per device coding. Data and lead out details included in pak.

Normal Retail Value £23.00

Our Special Offer Price £15.00

## Beginners Pak: No. 2

### 100 Rectifiers, SCR's, Triacs, Diodes.

20	IN4001-IN4007	1Amp Silicon Rectifier
20	IN5401-IN5407	3Amp Silicon Rectifier
20	IN4148	Fast switch diodes Silicon
10	OA200 BAX13-6	General Purpose Diode Silicon
5	C106D	Thyristor 400v T0202 Case
2	10Amp Triacs 400v T0220	Case Isolated Tab
2	4Amp Triacs 400v T0220	Case Non-isolated Tab
10	Assorted 3Amp Thyristors	50-600volts T064-T066 Case
5	Assorted 1Amp Thyristors	50-600volts T039 Case
6	OAB1-91	General Purpose Germanium Diodes

100 TOTAL

All devices brand new and full spec Data and lead out details included.

Normal Retail Value £17.00

Our Special Offer Price £11.00

## UNTESTED SEMICONDUCTOR PAKS


U1	150 germ Gold Bonded Diodes OA47	£1.00
U2	150 germ point contact diodes OA81	£1.00
U3	150 Silicon G.P. 200mA Diodes OA200	£1.00
U4	150 Silicon Fast Switch Diodes IN4148	£1.00
U5	25 Stud type Silicon Rectifiers up to 10A	£1.00
U6	10 SCR's 5Am- T066	£1.00
U7	40 Sil Trans NPN T018 Case BC107/B/9	£1.00
U8	40 Sil Trans PNP T018 Case BC177/B/9	£1.00
U9	40 Sil Trans NPN T018 Case 2N706	£1.00
U10	40 Sil Trans NPN T05/39 2N697/2N1711	£1.00
U11	40 Sil Trans PNP T05/39 2N2905/1132	£1.00
U12	30 Sil Trans NPN T039 BFY51-BC141	£1.00
U13	30 Sil Trans PNP T039 BC160-161 etc	£1.00
U14	10 Sil Trans NPN T03 2N3055	£1.00
U15	10 Sil Trans NPN T0220 TIP29-31-33	£1.00
U16	10 Sil Trans PNP T0220 TIP30-32-34	£1.00
U17	30 Sil Trans NPN T039 High Vols. 8F258/115	£1.00
U18	40 Sil Trans T092 BC237/B	£1.00
U19	40 Sil Trans T092 BC251	£1.00
U20	40 Sil Trans NPN T092 BC183-4	£1.00
U21	40 Sil Trans PNP T092 BC257 BC212L	£1.00

Code No's mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally unmarked.

## ELECTROLYTIC PAKS

A range of paks each containing 25 first quality, mixed value miniature electrolytics		
EC1	Values from 46mFD-10mFD	£1.00
EC2	Values from 10mFD-100mFD	£1.00
EC3	Values from 100mFD-1000mFD	£1.00

## NEW SHAPE LED's

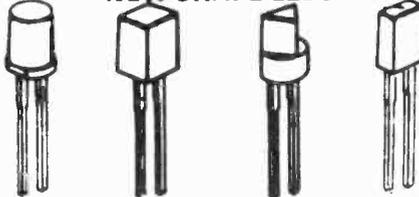

1561	3mm Cylindrical LED Red	£0.26
1562	3mm Square LED Red	£0.26
1563	3mm Triangular LED Red	£0.26
1564	5mm Rectangular LED Red	£0.26
1565	5mm Cylindrical LED Red	£0.26
1566	5mm Square LED Red	£0.26
1567	5mm Triangular LED Red	£0.26
1568	3mm Cylindrical LED Green	£0.28
1569	3mm Square LED Green	£0.28
1570	3mm Triangular LED Green	£0.28
1571	5mm Rectangular LED Green	£0.28
1572	5mm Cylindrical LED Green	£0.28
1573	5mm Square LED Green	£0.28
1574	5mm Triangular LED Green	£0.28
1575	3mm Cylindrical LED Yellow	£0.28
1576	3mm Square LED Yellow	£0.28
1577	3mm Triangular LED Yellow	£0.28
1578	5mm Rectangular LED Yellow	£0.28
1579	5mm Cylindrical LED Yellow	£0.28
1580	5mm Square LED Yellow	£0.28
1581	5mm Triangular LED Yellow	£0.28

## CERAMIC PAKS

Containing a range of first quality miniature ceramic capacitors.

MC1	40 miniature ceramic capacitors: 5 of each value: 22pf, 27pf, 33pf, 39pf, 47pf, 56pf, 68pf, 82pf.	£1.00
MC2	40 miniature ceramic capacitors: 5 of each value: 100pf, 120pf, 150pf, 180pf, 220pf, 270pf, 330pf, 390pf.	£1.00
MC3	40 miniature ceramic capacitors: 5 of each value: 470pf, 560pf, 680pf, 820pf, 1000pf, 1500pf, 2200pf, 3300pf.	£1.00
MC4	35 miniature ceramic capacitors: 5 of each value: 4700pf, 6800pf, .01uf, .015uf, .022uf, .033uf, .047uf.	£1.00

## SPEAKERS AND CROSSOVERS

1901	Dome Tweeter 3 1/2" 8 ohms 50w	£3.20
1902	Dome Tweeter 3 1/2" 8 ohms 20w	£2.60
1903	Flared Horn Tweeter 8 ohms 30w	£3.80
1904	2 way crossover 15w 8 ohms	£1.24
1905	2 way crossover 40w 8 ohms	£2.70
1906	3 way crossover 60w 8 ohms	£3.50
1907	Pi-zo Tweeter	£5.20
1914	70mm 80 ohm speaker	£1.20
1915	70mm 8 ohm speaker	£0.95
1916	56mm 8 ohm speaker	£0.65
1917	2 1/2" 8 ohm speaker	£0.75
1918	2 1/2" 64 ohm speaker	£0.82
1919	5" woofer 4 ohms 10w	£3.90
1920	5" woofer 8 ohms 10w	£3.90
1921	5" Dual cone wide range 8 ohms	£5.80
1922	8" Dual cone long throw 8 ohms 15w	£4.84
1923	8" woofer dual 4 + 8 ohms rubber edge 20w	£7.80


## DIL SOCKETS

1602	14 Pin	£0.11	1606	22 Pin	£0.24
1603	16 Pin	£0.12	1607	24 Pin	£0.28
1604	18 Pin	£0.18	1608	28 Pin	£0.32
1605	20 Pin	£0.20	1609	40 Pin	£0.36

## LATE ADDITIONS - High Current

Transistors				
BFT32	VCEO 60	VCBO 80	I.C. Max 3A	£0.60
BFT33	80	100	3A	£0.62
BFT34	100	120	3A	£0.65
BFT37	100	120	3A	£0.95
RPY76A	Infra Red Detector			£0.65

## LED CLIPS AND HOUSINGS

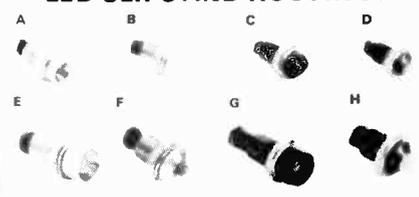

1548	LED Plastic clips .125"	£0.15
1549	LED Plastic clips .2"	£0.18
1550	LED Housing (nickel plated) .125"	£0.28
1551	LED Housing (nickel plated) .125"	£0.22
1552	LED Housing (matt black) .125"	£0.37
1553	LED Housing (matt black) .125"	£0.31
1554	LED Housing (nickel plated) .2"	£0.34
1555	LED Housing (nickel plated) .2"	£0.28
1556	LED Housing (matt black) .2"	£0.44
1557	LED Housing (matt black) .2"	£0.38

## BULBS AND NEONS

1534	LES Bulb 6v 0.36w	£0.24
1535	LES Bulb 6.5v 1w	£0.24
1536	LES Bulb 14v 0.75w	£0.24
1538	MES Bulb Round 6v .04A	£0.24
1539	MES Bulb Round 6.5v .15A	£0.20
1540	MES Bulb Round 6.5v .3A	£0.20
1541	MES Bulb Round 12.0v .1A	£0.20
1542	MES Bulb Round 12.0v 2.2w	£0.20
1543	Neon Red Round 240v	£0.34
1544	Neon Red Rectangular 240v	£0.34
1545	Neon Orange Rectangular 240v	£0.34
1546	Neon Green Rectangular 240v	£0.34
1547	MES Batten Holder	£0.18

## CARBON FILM RESISTOR PAKS

These paks contain a range of Carbon Film Resistors, assorted into the following groups:

R1	80 Mixed 1/4w 100 ohms-820 ohms	£1.00
R2	80 Mixed 1/4w 1K ohms-8.2K ohms	£1.00
R3	80 Mixed 1/4w 10K ohms-8.2K ohms	£1.00
R4	80 Mixed 1/4w 100K ohms-1M	£1.00
R5	60 Mixed 1/2w 100 ohms-820 ohms	£1.00
R6	60 Mixed 1/2w 1K ohms-8.2K ohms	£1.00
R7	60 Mixed 1/2w 10K ohms-8.2K ohms	£1.00
R8	60 Mixed 1/2w 100K ohms-1M	£1.00

## TANTALUM BEAD CAPACITORS

401	0.1uf 16v	£0.11	414	47.0uf 16v	£0.55
402	0.22uf 16v	£0.11	415	100uf 10v	£0.62
403	0.33uf 16v	£0.11	416	1uf 35v	£0.12
404	0.47uf 16v	£0.11	417	22uf 35v	£0.12
405	0.68uf 16v	£0.11	418	33uf 35v	£0.12
406	1.0uf 16v	£0.11	419	47uf 35v	£0.12
407	2.2uf 16v	£0.12	420	68uf 35v	£0.12
408	3.3uf 16v	£0.13	421	1.0uf 35v	£0.12
409	4.7uf 16v	£0.14	422	2.2uf 35v	£0.13
410	6.8uf 16v	£0.15	423	3.3uf 35v	£0.15
411	10.0uf 16v	£0.16	424	4.7uf 35v	£0.18
412	22.0uf 16v	£0.28	425	6.8uf 35v	£0.20
413	33.0uf 16v	£0.50	426	10.0uf 35v	£0.38

## FAIRCHILD/DARLINGTON

TYPE	Pol	VCEO	VCBO	I.C.	HFE	CASE	£ p
2N6052	PNP	-100v	-100v	12A	750-18K	T03	1.50
2N6282	PNP	60v	60v	20A	750-18K	T03	1.25
MJ3000	NPN	60v	60v	10A	1KMN	T03	1.00
SE9300	PNP	60v	60v	10A	1000	T0220	0.95
SE9031	PNP	80v	80v	10A	1000	T0220	0.95
SE9304	PNP	80v	80v	10A	1000	T03	0.95
SE9305	PNP	100v	100v	10A	1000	T03	1.00
SE9401	PNP	-80v	-80v	10A	1000	T0220	1.10
TIP115	PNP	-60v	-60v	2A	1A	T0220	0.40
TIP117	PNP	-100v	-100v	2A	1K	T0220	0.50
TIP120	NPN	60v	60v	5A	1K	T0220	0.60
TIP121	NPN	80v	80v	5A	1K	T0220	0.65
TIP122	NPN	100v	100v	5A	1K	T0220	0.88
TIP126	PNP	-80v	-80v	5A	1K	T0220	0.70
TIP127	PNP	-100v	-100v	5A	1K	T0220	0.72

## POWER SUPPLIES

137	AC-DC Adaptor 6.7 1/2, 9 & 12 volts	£3.75
138	DC-AC Adaptor 6.7 1/2, 9 volts	£2.70

## CABINETS

139	Teak 30 Case	£7.00
140	Teak 60 Case	£9.50

Access and Barclaycards accepted - just telephone our Orderline - Ware (STD 0920) 3182.

All prices exclude V.A.T., add 50p postage per order. Terms: C.W.O., cheques, Postal Orders payable to Bi-Pak at addresses below.



**SEMICONDUCTORS**  
Dept. PE4, P.O. BOX 6, WARE, HERTS.  
Tel: Ware (STD 0920) 3442. Telex: 817861.  
Giro No. 3887006.  
Visit our shop at: 3, Baldock St, Ware, Herts.

BARCLAYCARD



Only buy the complete kit

+ 50p P&P

+ 15% VAT

# SPRING TIME IS SALE TIME

Closing date 31.4.81

6 x 555	1.00	LEDs 0.2"	15 x BC182	1.00
6 x 741	.90	10 each red, green, yellow	15 x BC212	1.00
IC Sockets	LM3915 + 10-element LED	3.20	4 x C106D SCR	1.10
15 x 8 pin	1.00	display	6 x CD4011 (CMOS)	1.00
12 x 14 pin	1.00	Liquid Crystal Display, 3 1/2	<b>Voltage Regulators</b>	
10 x 16 pin	1.00	0.5" digits, d.i.l.	2 x 7805	1.00
8 x 18 pin	1.00	2 x TIC226D 8A/400V Triacs	2 x 7812	1.00
6 x 22 pin	1.00	2 x TIC236D 12A/400V Triacs	2 x 7815	1.00

BONUS: A further 5% discount if you buy the lot. (£24.75 - VAT).

## ARE YOU SITTING COMFORTABLY?

Our new TDR300K Touch Dimmer Kit will ensure that you are... Based on our highly successful TD300K touch controlled dimmer kit, the TDR300K incorporates an infra red receiver, enabling the lamp brightness to be varied and switched on or off by touch or remotely by means of a small hand held transmitter.



The complete kit, which includes easy to follow instructions, will fit into a plaster depth box and the plastic front plate has no metal pads to touch, ensuring complete safety. Even a neon is included to help you locate the switch in the dark.

In years to come everyone will be selling remote control dimmers, but you can have your TDR300K kit now for ONLY £14.30 for the dimmer unit and £4.20 for the transmitter. For the more athletic of you, the TDK300K Touchdimmer kit is still available at £6.50 and the TDE/K Extension kit, for 2-way switching etc. is £2.00. DON'T FORGET to add 50p P&P and 15% VAT to your total purchase.

## CT4000 CLOCK/APPLIANCE TIMER KIT

The CT4000 has been designed to preset the state (on or off) of four outputs at four times per day for up to 7 days in advance, enabling the unit to control tape recorders, appliances, central heating, lights, etc. The times are set on a 0.1" high red LED display by means of a keyboard and the output states are displayed on four LEDs. Each output can switch up to 20mA at 9V. For mains loads use our Solid State Relay Kit (MK2). The kit includes a PCB, keyswitches, I.C., 4 digit LED display, transformer, plus all other components and a screen printed and drilled box which can also accommodate up to 4 Solid State Relay Kits.



£25.25

Size: 10x12x4.5 cms. Colour: Black.



## THE REMOTE CONTROL STORY



ONCE UPON A TIME, if you wanted to control any equipment remotely you had to buy a dozen logic ICs, chase around the shops for crystals and expensive ultrasonic transducers and then spend a few days getting the unit to work. Then one day TK began stocking a new system. All you required was one IC, a couple of transistors, resistors and a keyboard for the transmitter and a couple of ICs plus a few capacitors for the receiver, to give you up to 16 on/off (digital) outputs or 10 channels plus three analogue (0-10V) outputs. The SL490 transmitter/encoder accepts inputs from a keyboard (up to 32 way) and encodes these into a pulse train which may be transmitted using infra red, ultrasonic, radio or even wire links. For the receiver you may use the SL480 pre-amplifier if you want an infra red link or a suitable pre-amplifier for ultrasonic or radio links, and one of the ML920 series decoders depending on the number and type of outputs required. The only adjustment you need to make is to set one preset frequency or with a scope and that's all.

LD271	IR Emitting Diode	£0.36	ML926	16-channel receiver, 4 momentary binary outputs	£1.40
SFHZ05	Photodiode Detector	£0.90	ML928	16-channel receiver, 4 latched binary outputs	£1.40
SL480	10 Pulse Amp	£1.70	ML929	16-channel receiver, 4 latched binary outputs	£1.40
SL490	32 Command Encoder/transmitter	£2.40		Clip-on Plastic Reflector for IR LEDs, increases range	£0.20
ML922	16-channel receiver	£4.20			

**NEW ML925.** A decoder designed for model/toy control, providing a 2-speed drive motor and three position latched steering system or a vehicle with momentary action steering and a third motor, eg gun turret, winch, etc. Outputs also available for other facilities such as horn, turn indicators, headlights, etc. £2.10.

To make things EVEN EASIER we have designed several new kits:-

**MK6** Simple Infra Red TRANSMITTER. A pulsed infra red source which comes complete with a hand held plastic box. Requires a 9V battery. £4.20.

**MK7** 16-Channel RECEIVER. Single channel, range approximately 20 ft. Mains powered with a triac output to switch loads up to 500W at 240V ac, but can be modified for use with 5 to 15V dc supplies and transistor or relay outputs. £9.00.

**SPECIAL PRICE** MK6 and MK7 together. Order as RC500K. £12.50.

**MK8** Code Infra Red TRANSMITTER. Based on the SL490, the kit includes 2 IR LEDs, measures only 8 x 2 x 1.3 cms. and requires a 9V (PP3) battery. £5.90.

**MK9** 4-Way KEYBOARD. For use with the MK8 kit, to make a 4-channel remote control transmitter. For use with ML926 or ML928 Based Receivers. £1.90.

**MK10** 16-Way KEYBOARD. For use with the MK8 kit, to generate 16 different codes for decoding by the ML928 or ML926 receiver (MK12) kit. £5.40.

**MK11** 10 On-Off Channel IR RECEIVER with three analogue outputs (0-10V) for controlling such functions as lamp brightness, volume, tone, etc. Other functions include an on/standby output and a toggle output, which may be used for sound muting. Based on ML922 decoder IC. Includes its own mains supply. £12.00.

**MK12** 16-Channel IR RECEIVER. For use with the MK8 kit with 16 on/off outputs which with further interface circuitry, such as relays or triacs, will switch up to 16 items of equipment on or off remotely. Outputs may be latched or momentary, depending on whether the ML926 or ML928 is specified. Includes its own mains supply. £11.95.

**MK13** 11-Way KEYBOARD. For use with MK8 and MK11 kits. Transmits programme step + and - analogue - and 10V mute - normalise analogue outputs, and on/standby. £4.35.

Now you can buy all the components you require for your infra red system or complete kits from one supplier, at unbeatable prices, and live happily ever after.

ALL COMPONENTS ARE BRAND NEW AND TO SPECIFICATION. ADD 50p P&P and 15% VAT TO TOTAL. OVERSEAS CUSTOMERS ADD £1.50 (Europe) £4 (elsewhere) for P&P. Send see for price list and with all enquiries. Callers welcome 9.30-5.00 (Mon-Fri) 10.00-4.00 (Sat.).



**TK Electronics**  
(P.E.), 11 Boston Road, London W7 3SJ. TEL. 01-579 9794



# Conquer the chip.

Be it a career, hobby or interest, like it or not the Silicon Chip will revolutionise every human activity over the next ten years.

Knowledge of its operation and its use is vital. Knowledge you can attain, through us, in simple, easy to understand stages.

Learn the technology of the future today in your own home.

## MASTER ELECTRONICS LEARN THE PRACTICAL WAY BY SEEING AND DOING

- Building an oscilloscope. ● Recognition of components.
- Understanding circuit diagrams. ● Handling all types Solid State 'Chips'.
- Carry out over 40 experiments on basic circuits and on digital electronics.
- Testing and servicing of Radio, T.V., Hi-Fi and all types of modern computerised equipment.


## MASTER COMPUTERS

LEARN HOW TO REALLY UNDERSTAND COMPUTERS, HOW THEY WORK - THEIR 'LANGUAGE' AND HOW TO DO PROGRAMS.

- Complete Home Study library. ● Special educational Mini-Computer supplied ready for use. ● Self Test program exercise.
- Services of skilled tutor available.
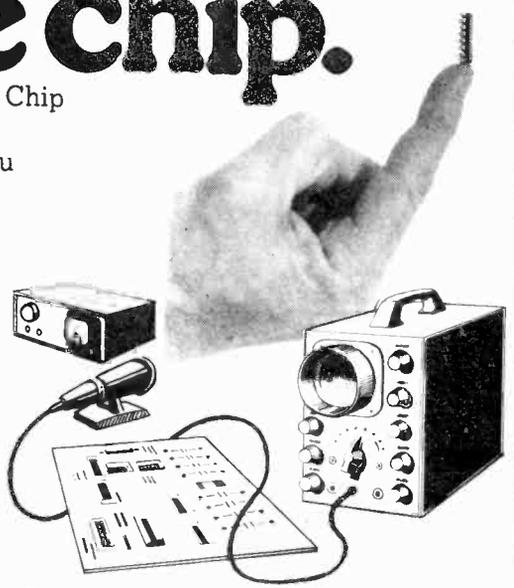
## MASTER THE REST

- Radio Amateurs Licence. ● Logic/Digital techniques.
- Examination courses (City & Guilds etc.) in electronics.
- Semi-conductor technology.
- Kits for Signal Generators - Digital Meters etc.



Please send your **FREE** brochure without obligation to:-

Name \_\_\_\_\_

Address \_\_\_\_\_

BLOCK CAPS PLEASE

I am interested in -

PRACTICAL ELECTRONICS

COMPUTER TECHNOLOGY

OTHER SUBJECTS (please state your interest)

PE/4/813

**BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL**


**4 CLEVELAND ROAD, JERSEY, CHANNEL ISLANDS.**

**3 CHANNEL SOUND/LIGHT CHASER**  
LB31000SLC **£32.70**



A high performance sound to light system which automatically switches to a chase when the music ceases. Super sensitive with an anti interference circuit, the unit will operate from practically any amp and control up to 1,000W/channel, 5Hz to 70K. Controls: bass/mid/treble/master sensitivity/chase speed.

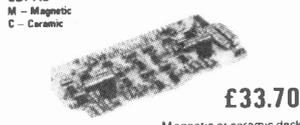**STEREO DISCO MIXER/PREAMP**  
LBPA3 **£33.70**  
M - Magnetic  
C - Ceramic



Magnetic or ceramic deck versions - please state

All the requirements of a stereo disco preamp on one board left and right deck mixers/tones controls/mic mixer/tones/mic auto fade over decks/and P.F.L. The unit can be used with either LB100/150/250.

Full set of pots — **£8.63**

**3 CHANNEL SOUND/LIGHT**  
LB31000SL **£22.70**



All the advantages of the SLC without chase Controls: bass/mid/treble/master sensitivity

**LBPA2 £17.20** **LBPA1 £19.50**

A four channel mixer and tone stage for mics, guitars etc. Can be used with any LB amps. Set of pots £2.74.

A stereo hi-fi preamp and tone stage for mag. p.u./tape/tuner etc. Set of pots £3.27.

**3-WAY ACTIVE CROSSOVER**  
LBACO1 **£17.90**



LBPSU1 **£7.20**

Bass/mid/treble active crossover with stage booster! Available with crossover points of 200 or 300Hz and 2K or 3KHz (please specify) LBPSU1 supply for LBACO1. (1 or 2).

**2/4/8 CHANNEL CHASER**  
LB81000LC **£28.00**



An all logic chaser system for use with up to 8 channels at 1,000 watts each. Facilities include footswitch trigger and module cascading (16 24 32 channel, etc.), chase speed and re-cycle delay.

**POWER AMPLIFIERS**


Tough dealing power amps for use in sound systems. Open/short circuit protection and fused. Heavy gauge heatsinks and rugged o/p devices (all operate down to 4 ohms)

25W R.M.S.	100W R.M.S.	150W R.M.S.	250W R.M.S.
20Hz to 60K 0.07% THD	5Hz to 25K 0.1% THD	5Hz to 25K 0.1% THD	5Hz to 25K 0.1% THD
960B S/N LB25	1100B S/N LB100	1100B S/N LB150	1100B S/N LB250

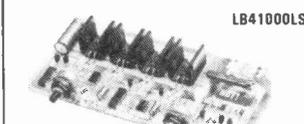**£11.20 £19.70 £29.20 £43.50**

Note: All models are available with either 500mV or 775mV sensitivity. Please state when ordering.

**4 CHANNEL SEQUENCER**  
LB41000LS **£19.20**



A 4 channel sequence generator for banks of lamps up to 1,000W per channel. Two speed controls cross effect to provide settings between seconds and rapid burst.

**LBRD1 £6.20**

A die thruamp unit for use with any LB power amps

**1 AND 3 CHANNEL DIMMERS**  
LB31000LD **£16.20**



Single channel version LB11000LD **£7.20**

Power dimmer units for theatre/stage applications up to 1,000W per channel, with on board suppressing. The unit is also available without rotary pots for use with sliders —

LB31000LD (no pots) **£15.00** Sliders **75p** each

**POWER AMP POWER SUPPLIES**

LB25PS	LB100PS	LB150PS	LB250PS
<b>£11.20</b>	<b>£16.20</b>	<b>£19.00</b>	<b>£26.50</b>
P.P. £1.20	P.P. £1.40	P.P. £1.40	P.P. £1.70

**FOR GUITARS, P.A. AND DISCO**



**PIEZO HORNS £5.75**  
P.P. 50p

**ROPE LIGHTS/DRIVER**  
LB41000LC-S **£24.20**



24 feet ropes Red/Yellow/Blue/Green

**ROPE LIGHTS £45.40**

A four channel chaser up to 1,000W per channel with a sound trigger facility. The music input signal modulates the speed of the chase giving an excellent sound/light effect. The unit will control up to 10 ropes with chase speed and trigger level control.

**CELESTION LOUSPEAKERS (ALL STANDARD CONE 8 OHMS)**

G19-50	G12-65	G12-100	G15-100
(10 inch 50W)	(12 inch 65W)	(12 inch 100W)	(15 inch 100W)
<b>£14.70</b>	<b>£20.70</b>	<b>£26.45</b>	<b>£36.45</b>
P.P. £1.70	P.P. £1.70	P.P. £1.70	P.P. £2.00

**NEW - MINI MODULES - NEW**

Ingeniously designed mini pre-amplifier building blocks for use in music and P.A. applications. You choose the type and number of units you require for your particular system and mount each module via its control direct onto your panel.

LBMM1 Pre-amp for mics, guitars etc.  
LBMM2 Mixer for up to 6 LBMM1/2/3/4/5  
LBMM3 Bass/boost/cut for either LBMM1/2/3/4/5  
LBMM4 Mid-boost/cut for either LBMM1/2/3/4/5  
LBMM5 Treble boost/cut for either LBMM1/2/3/4/5  
LBPSU1 ± 15V supply for up to 12 modules  
LBPSU2 ± 15V regulated for up to 50 modules

MM1 £4.50; MM2 £5.20; MM3 £5.70; MM4 £5.70; MM5 £6.70; PSU1 £7.20; RPSU £14.50.  
Discount on MM1/2/3/4/5 10 to 24 - 20%, 25+ - 30%

**L & B ELECTRONIC MODULES**

PROFESSIONAL ENGINEERING BY PROFESSIONALS

45 Wortley Road, West Croydon, Surrey  
CRO 3EB. Tel. 01-689 4138

Each module is manufactured from the highest quality components fully tested, supplied with a connection and circuit diagram and guaranteed for twelve months.

All prices shown are VAT inclusive. Please include 50p post/packing except where individually stated. To mail order send cheque/P.D./registered cash or Access number COD service £1 extra. For the new Autumn catalogue send 50p (full spec shown).

PLEASE NOTE THIS COMPANY HAS NO CONNECTION WITH LB ELECTRONICS OF HILLINGDON

**L.P. Toroidal TRANSFORMERS**  
IN A RANGE OF **76 TYPES**



We use advanced winding technology to make our toroidal transformers. They have only half the weight and height of their laminated equivalents and are appreciably more efficient. Our toroidals cost virtually the same as the older types which they are rapidly replacing. Induced hum is reduced by a factor of ten. Supplied with rigid mounting kit with centre bolt, steel and neoprene washers.

**30VA** 70mm dia. x 30mm **£4.71**  
Weight 0.45 Kg  
(+£1.20 p.p. + 0.89 VAT)

**160VA** 110mm dia. x 40mm **£8.88**  
Weight 1.8 Kg  
(+£1.80 p.p. + £1.60 VAT)

TYPE	SECONDARY RMS VOLTS	SECONDARY RMS CURRENT
1X010	6 + 6	2.50
1X011	9 + 9	1.66
1X012	12 + 12	1.25
1X013	15 + 15	1.00
1X014	18 + 18	0.83
1X015	22 + 22	0.68
1X016	25 + 25	0.60
1X017	30 + 30	0.50

TYPE	SECONDARY RMS VOLTS	SECONDARY RMS CURRENT
5X012	12 + 12	6.66
5X013	15 + 15	5.33
5X014	18 + 18	4.44
5X015	22 + 22	3.63
5X016	25 + 25	3.20
5X017	30 + 30	2.66
5X018	35 + 35	2.28
5X028	110	1.45
5X029	220	0.72
5X030	240	0.66

**50VA** 80mm dia. x 35mm **£5.19**  
Weight 0.9 Kg  
(+£1.30 p.p. + 0.97 VAT)

2X010	6 + 6	4.16
2X011	9 + 9	2.77
2X012	12 + 12	2.08
2X013	15 + 15	1.66
2X014	18 + 18	1.38
2X015	22 + 22	1.13
2X016	25 + 25	1.00
2X017	30 + 30	0.83
2X028	110	0.45
2X029	220	0.22
2X030	240	0.20

**225VA** 110mm dia. x 45mm **£10.59**  
Weight 2.2 Kg  
(+£1.90 p.p. + £1.87 VAT)

6X014	18 + 18	6.25
6X015	22 + 22	5.11
6X016	25 + 25	4.50
6X017	30 + 30	3.75
6X018	35 + 35	3.21
6X026	40 + 40	2.81
6X028	110	2.04
6X029	220	1.02
6X030	240	0.93

**80VA** 90mm dia. x 30mm **£5.76**  
Weight 1 Kg  
(+£1.50 p.p. + £1.09 VAT)

3X010	6 + 6	6.64
3X011	9 + 9	4.44
3X012	12 + 12	3.33
3X013	15 + 15	2.66
3X014	18 + 18	2.22
3X015	22 + 22	1.81
3X016	25 + 25	1.60
3X017	30 + 30	1.33
3X028	110	0.72
3X029	220	0.36
3X030	240	0.33

**300VA** 110mm dia. x 50mm **£12.27**  
Weight 2.6 Kg  
(+£2.00 p.p. + £2.14 VAT)

7X016	25 + 25	6.00
7X017	30 + 30	5.00
7X018	35 + 35	4.28
7X026	40 + 40	3.75
7X025	45 + 45	3.33
7X028	110	2.72
7X029	220	1.36
7X030	240	1.25

**120VA** 90mm dia. x 40mm **£6.72**  
Weight 1.2 Kg  
(+£1.60 p.p. + £1.25 VAT)

4X010	6 + 6	10.00
4X011	9 + 9	6.66
4X012	12 + 12	5.00
4X013	15 + 15	4.00
4X014	18 + 18	3.33
4X015	22 + 22	2.72
4X016	25 + 25	2.40
4X017	30 + 30	2.00
4X028	110	1.09
4X029	220	0.54
4X030	240	0.50

**500VA** 140mm dia. x 60mm **£16.35**  
Weight 4 Kg  
(£2.10 p.p. + £2.77 VAT)

8X017	30 + 30	8.33
8X018	35 + 35	7.14
8X026	40 + 40	6.25
8X025	45 + 45	5.55
8X033	50 + 50	5.00
8X028	110	4.54
8X029	220	2.27
8X030	240	2.08

• I.L.P. TOROIDAL TRANSFORMERS ARE GUARANTEED FOR 5 YEARS

**CHOICE OF 3 PRIMARY INPUTS**

I.L.P. Toroidal Transformers are available in choice of 110V, 220V, 240V, coded as follows: (Secondaries can be connected in series or parallel)

For 110V Primary insert 0 in place of "X" in type number.  
For 220V Primary (Europe) insert 1 in place of "X" in type number.  
For 240V Primary (U.K.) insert 2 in place of "X" in type number

Example - 120VA 240V 15 + 15V. 4A = 42013.

• CUSTOMER DESIGN ENQUIRIES INVITED. QUANTITY PRICE LIST AVAILABLE.

**FREEPOST facility. (U.K. only).**

Simply address envelope to **FREEPOST** to address below. NO STAMP REQUIRED.

**TO ORDER** Enclose cheque/Postal Order/Money Order payable to I.L.P. Electronics Ltd or quote your ACCESS or BARCLAYCARD account No. To pay C.O.D. add £1 extra to TOTAL value of order. Also available from ELECTROVALUE and MARSHALLS.

**L.P. TRANSFORMERS**  
A division of I.L.P. ELECTRONICS LTD.

FREEPOST T2 GRAHAM BELL HOUSE ROPER CLOSE  
CANTERBURY CT2 7EP  
Phone (0227) 54778 Technical (0227) 64723 Telex 965 780

# HIGH POWER MODULE KITS

**125 WATT MODEL £10.50** plus £1.15 p&p (Illustrated)  
**200 WATT MODEL £14.95** plus £1.15 p&p

## SPECIFICATIONS

Max. Output power 125 watt RMS  
 Operating voltage (DC) 50-80 Max.  
 Loads 4-16 ohms  
 Frequency response measured at 100 watts 25Hz-20KHz  
 Sensitivity for 100 watts 400mV @ 47K  
 Typical T.H.D. @ 50 watts 4 ohms load 0.1%  
 Dimensions 205 x 90 and 190 x 36 mm  
 The P.E. power amp kit is a module for high power applications—disco units, guitar amplifiers, public address systems and even high power domestic systems. The unit is protected against short circuiting of the load and is safe in an open circuit condition. A large safety margin exists by use of generously rated components, result, a high powered rugged unit. The PC Board is backprinted, etched and ready to drill for ease of construction, and the

aluminium chassis is preformed and ready to use. Supplied with all parts, circuit diagrams and instructions.

## ACCESSORIES

Suitable LS coupling electrolytic for 125W model **£1.00** plus 25p p&p  
 Suitable LS coupling electrolytic for 200W model **£1.25** plus 25p p&p  
 Suitable Mains Power Supply Unit for 125W model **£7.50** plus £3.15 p&p  
 Suitable Twin Transformer Power Supply for 200W model **£13.95** plus £4.00 p&p

## PRACTICAL ELECTRONICS CAR RADIO KIT (Constructors pack 7)



**2 WAVE BAND MW LW**  
 \* Easy to build \* 5 push button tuning  
 \* Modern styling design \* All new unused components  
 \* 6 watt output \* Ready etched & punched P.C.B.  
 \* Incorporates suppression circuits \* Now with tape input socket

All the electronic components to build the radio, you supply only the wire and solder as featured in the Practical Electronics March issue. Features: Pre-set tuning with live push button options, black illuminated tuning scale, with matching rotary control knobs, one, combining on/off volume and tone-control, the other for manual tuning, each set on wood simulated fascia. The P.E. Traveller has a 6 watts output, neg ground and incorporates an integrated circuit output stage, a Mullard IF module LP1181 ceramic filter type, pre-aligned and assembled and a Bird pre-aligned push button tuning unit. The radio fits easily in or under dashboards.

**£10.50**

Complete with instructions  
**CONSTRUCTORS PACK 7A** plus £2.00 p&p  
 Suitable stainless steel fully retractable locking aerial and speaker (approx. 6" x 4") is available as a kit complete **£1.95** per pack, £1.15 p&p



## 30 + 30 WATT STEREO AMPLIFIER BUILT AND TESTED


Viscount IV unit in teak simulate cabinet silver finished rotary controls and pushbuttons with matching fascia, red mains indicator and stereo jack socket. Functions switch for mic magnetic and crystal pickups, tape and auxiliary. Rear panel features fuse holder, DIN speaker and input socket 30 + 30 watts. RMS 60 + 60 watts peak for use with 4 to 8 ohm speakers. Size 14 1/2" x 10" approx.

**READY TO PLAY £32.90** plus £3.80 p&p
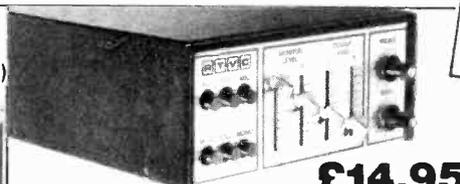
## HI FI STEREO AMPLIFIER MODULES



- Mullard LP1183 built preamplifier suitable for ceramic and auxiliary inputs. £1.95 plus 70p p&p.
- Mullard LP1184 built preamplifier suitable for magnetic/ceramic and auxiliary inputs. £4.95 plus 80p p&p
- Matching I.C. 10 + 10 Stereo Power amplifier kit. £3.95 plus £1.15 p&p
- Matching power supply kit with transformer. £3.00 plus £1.96 p&p
- Matching set of 4 slider controls complete with knobs for bass, treble and volumes. £1.70 plus 80p p&p.
- Complete with application notes.



## 10+10 WATT STEREO AMPLIFIER KIT

**£14.95** plus £2.90 p&p

- Featuring latest SGS/ATES TDA 2006 10 watt output I.C.'s with in-built thermal and short circuit protection.
- Mullard Stereo Preamplifier module.
- Attractive black vinyl finish cabinet. Size 9" x 8 1/2" x 3 3/4" approx.
- Converts to a 20 watt Disco amplifier.

To complete you just supply connecting wire and solder. Features include din input sockets for ceramic cartridge, microphone, tape or tuner. Outputs—tape, speakers and headphones. By the press of a button it transforms into a 20 watt mono disc amplifier with twin deck mixing. The kit incorporates a Mullard LP1183 pre-amp module, plus power amplifier assembly kit and mains power supply. Also featured 4 slider level controls, rotary bass and treble controls and 6 push button switches. Silver finish fascia panel with matching knobs and contrasting ready made black vinyl finish cabinet and ready made metal work. For further information instructions are available price 50p. Free with kit.

## SPECIFICATIONS

Suitable for 4 to 8 ohms speakers  
 Frequency response 40Hz — 20KHz  
 P.U. 150mV Aux. 200mV Mic. 1.5mV  
 Input Sensitivity  
 Tone controls  
 Distortion  
 Mains supply

**BSR** chassis record deck with manual set down and return, complete with stereo ceramic cartridge. **£8.50** plus £3.15 p&p when purchased with amplifier. Available separately **£10.50** plus £3.16 p&p



**8" SPEAKER KIT** 2 8" approx. twin cone domestic use speakers. **£4.75** per stereo pair plus **£1.70** p&p when purchased with amplifier. Available separately **£6.75** plus **£1.70** p&p.

## STEREO MAGNETIC PRE-AMP CONVERSION KIT.

All components including P.C.B. to convert your ceramic input on the 10+10 amp to magnetic. **£2.00** when purchased with kit featured above. **£4.00** separately inc. p&p.

**RTVC**  
 323 EDGWARE ROAD, LONDON W2  
 21 BHIGH STREET, ACTON W3 6NG

ACTON: Mail Order only. No callers

**ALL PRICES INCLUDE VAT AT 15%**


All items subject to availability. Price correct at 5.2.81 and subject to change without notice.

For further information send for instructions

20p plus stamped addressed envelope.

**NOTE:** Goods despatched to mainland and N. Ireland only. Persons under 16 years not served without parent's authorisation.

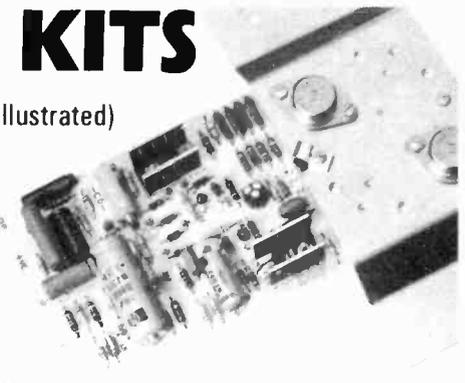
RTVC LTD. reserve the right to alter, update or improve their products without notice.



## MULLARD LP1183 STEREO PREAMP

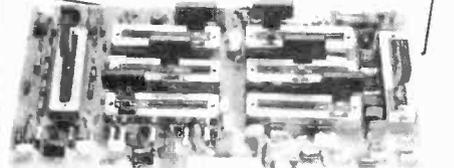**FREE!**

Original listed price over £5.00. Suitable for ceramic and auxiliary inputs, when you purchase 2 power module kits.




## STEREO DISCO PREAMPLIFIER

matching above modules, suitable for twin deck mixing with P.F.L. output and Mic/Tape input.

Ready built, ready to play with circuit diagram and application notes to suit our power module kits. **£21.95** plus £1.72 p&p

## 100 WATT MONO DISCO AMPLIFIER

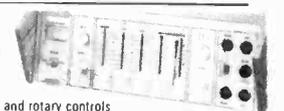

Brushed aluminium fascia and rotary controls

Size approx 14" x 4" x 10 1/2". Five vertical slide

controls, master volume, tape level, mic level, deck

level, PLUS INTER DECK FADER for perfect graduated change

from record deck No. 1 to No. 2, or vice versa. Pre fade level

controls (PRL) lets YOU hear next disc before

fading it in. VU meter monitors output level.

Output 100 watts RMS 200 watts peak. **£76.00**

plus £4.60 p&p

## 50 WATT MONO DISCO AMPLIFIER

Size approx 13 1/2" x 5 1/4" x 6 3/4". 50 watts rms. 100 watts peak

output. Big features include two disc inputs, both for ceramic

cartridges, tape input and microphone input. Level mixing controls

fitted with integral push-pull switches.

Independent bass and treble controls

and master volume.



**£30.60**

plus £3.68 p&p

## BSR Manual single play

record deck with auto return and

cueing lever. Fitted with stereo

ceramic cartridge 2 speeds with 45

rpm spindle adaptor ideally suited

for home or disco use.

**£12.25** OUR PRICE

plus £3.16 p&p



Size approx 13" x 11"

## PHILLIPS RECORD PLAYER

DECK GC037

Size approx 15 1/4" x 12 1/4"

Hi Fi record player deck, 2 speed,

damped cueing, auto shut-off, belt

drive with floating sub chassis to

minimise acoustic feedback. Complete

with GP401 stereo magnetic

cartridge—LIMITED STOCK.

UNBEATABLE OFFER AT

**£27.50** complete plus £3.16 p&p

## A GOOD CASE . . .

THOSE of you who have already looked further into your copy will by now be aware that our May issue is a very special one (others turn to page 36—when you have finished this piece please!) When planning our free case one of our intentions was to present as wide a variety of digital projects to fit in the case as possible. Another factor that influenced our decision to go ahead with this rather expensive gift, in the face of the present recession, was the relatively simple construction of each project.

The use of what is probably the first of a new generation of panel meters has resulted in very high performance projects which are not expensive, are readily constructed and neatly housed. The free case was designed especially for PE by Lascar Electronics and, as far as we know, is the only case of this type available in the UK at the present time. Because you will get one free you will save over £2.00 on the project cost and our *DPM Special Offer* will save you a further £3.00 on the normal price.

Taking all these factors into account we believe that we can appeal to the

widest possible range of readership and thus make the most of our primary intention—to sell more copies. Yes, it's a hard world and we do publish to make money, although we can easily lose sight of that fact in our enthusiasm for electronics and for PE in particular. Of course we believe PE is excellent value for money anyway, but on this special occasion it will be even more attractive, so please make sure of your copy by ordering it now.

## . . . LAID BEAR!

Having just worked our way through that lot of (hopefully) logical thinking and confidently believing we can introduce some new readers to PE, we received the following letter trusted to the tender care of a Paddington Bear envelope:

*"Dear Sir or Madam,*

*In November 1974's Practical Electronics you published the "PE Minisonic" by G. D. Shaw.*

*My dad has a collection of your magazines, but unfortunately has not got all the parts. So could you please send me the circuit diagram for this very good battery operated synthesiser.*

*I enclose a stamped addressed envelope for your reply.*

*Yours sincerely,  
Robert Brooks.*

*PS. I am twelve years old."*

Thank you Robert for an excellent letter, unlike many older readers you have given your name and address clearly—you'd be surprised how many people forget all, or part of it—supplied a stamped addressed (Paddington) envelope—without any marmalade on it—set out your letter clearly, kept to one subject and even given us a little praise—all others please follow Robert's example.

The only thing that worries us is why do we bother about easy to build projects to interest new readers if you are building the *PE Minisonic* at the age of 12? You have just messed up all that logical thinking!

We would be interested in hearing from other young readers, we cannot promise to answer all the letters, but why not tell us how you first started reading PE and what type of projects and articles you like.

*Mike Kenward*

PS. I'm not telling you my age.

## EDITOR

Mike Kenward

Gordon Godbold ASSISTANT EDITOR

Mike Abbott TECHNICAL EDITOR

David Shortland PROJECTS EDITOR

Jasper Scott PRODUCTION EDITOR

Jack Pountney ART EDITOR

Keith Woodruff ASSISTANT ART EDITOR

John Pickering SEN. TECH. ILLUSTRATOR

Isabelle Greenaway TECH. ILLUSTRATOR

Colette McKenzie SECRETARY

## ADVERTISEMENT MANAGER

SECRETARY

AD. SALES EXEC.

CLASSIFIED MANAGER

D. W. B. Tilleard

Christine Pocknell

Alfred Tonge 01-261 6819

Colin Brown 01-261 5762

01-261 6676

### Editorial Offices:

Practical Electronics,  
Westover House,  
West Quay Road, Poole,  
Dorset BH15 1JG  
Phone: Editorial Poole 71191

**We regret that lengthy technical enquiries cannot be answered over the telephone (see below).**

### Advertising Offices:

Practical Electronics Advertisements,  
King's Reach Tower,  
King's Reach, Stamford Street, SE1 9LS  
Telex: 915748 MAGDIV-G

**Make Up/Copy Dept.: 01-261 6601**

### Technical Queries

We are unable to offer any advice on the use or purchase of commercial equipment or the incorporation or modification of designs published in Practical Electronics.

All letters requiring a reply should be accompanied by a stamped, self addressed envelope and each letter should relate to one published project only.

Components and p.c.b.s are usually available from advertisers; where we anticipate difficulties a source will be suggested.

### Back Numbers

Copies of some of our recent issues are available from: Post Sales Department (Practical Electronics), IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF, at 95p each including Inland/Overseas p&p.

### Binders

Binders for PE are available from the same address as back numbers at £4.30 each to UK or overseas addresses, including

postage and packing, and VAT where appropriate. Orders should state the year and volume required.

### Subscriptions

Copies of PE are available by post, inland or overseas, for £11.80 per 12 issues, from: Practical Electronics, Subscription Department, Oakfield House, Perrymount Road, Haywards Heath, West Sussex RH16 3DH. Cheques and postal orders should be made payable to IPC Magazines Limited.

# Market Place


Items mentioned are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned. All quoted prices are those at the time of going to press.

by  
**David Shortland**

and  
**Jasper Scott**
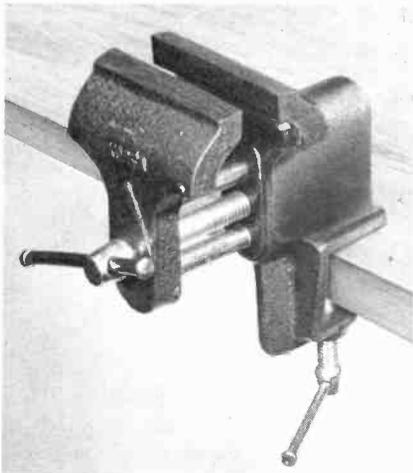
## BUDGET VICE

This portable bench vice, pictured below, is now available from Home Radio. The jaws open to a maximum of 32mm and it can be fitted to benches up to 24mm thick, so it should be suitable for most light constructional work.




The price including VAT and p&p is £3.87.  
**Home Radio (Components) Ltd, PO Box 92, 215 London Road, Mitcham, Surrey (01-543 5659)**

## DRILLMASTER

Two new mini drills ideal for use with our minidrill p.s.u. are being marketed by Microflame together with a complete range of accessories which include a drill stand with a built in magnifying glass.

The junior model features a detachable

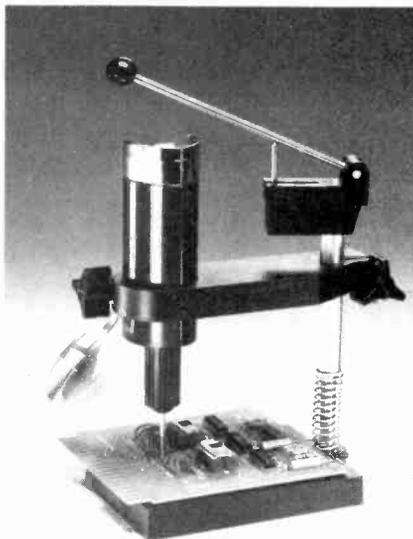chuck finger shield for close control and the chuck itself has four precision cut steel collets (0.6, 1.2, 1.8 and 2.4mm). An automatic 3-jaw chuck is available as an optional extra.



The senior model is supplied with an automatic 3-jaw chuck and a precision chuck with 5 collets is available as an optional extra (0.6, 1.2, 1.8, 2.4 and 3.2mm).

The price of the junior model is £10.00 and the senior model is £17.35. All prices exclude VAT and p&p.

**Microflame (UK) Limited, Vincas Road, Diss, Norfolk (0379 4813).**

## SOAR DFM

Many people who consider digital frequency meters just too expensive to be considered for inclusion in their range of test equipment will be interested to hear about the Soar DFM. The importers of this Japanese instrument claim they have done so because of the non-availability of a low priced high quality UK meter.




The unit which measures only 100x32x120mm has a frequency range of 10Hz to 50MHz and can measure up to 500MHz with a prescaler. Powered by either 4 penlight batteries or an external d.c. supply (8 to 11V) the instrument has a 4 digit display and a resolution of 10Hz/10kHz with a maximum input of 20V.

The DFM is priced at £39.99 including VAT. For £43.58 the DFM is available with batteries, input lead carriage and insurance.

**Holdings, Mincing Lane, Darwen Street, Blackburn BB2 2AF (0254 59595).**
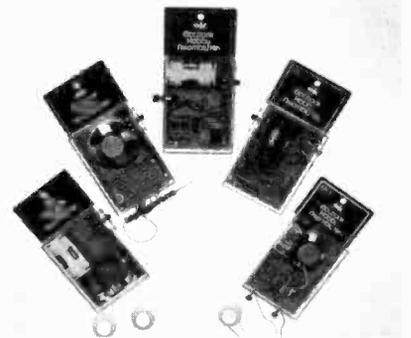
## KITS FOR BEGINNERS

A range of simple chip based hobby kits with step-by-step instructions has been introduced by OK Machine & Tool. OK say that the kits are suitable for 12 year olds upwards, with descriptions of the various terms and components used in electronics included in the instructions. Once assembled, the kits fit into their original plastic packaging containers.



Five kits are available. Quick Reaction (£5.80), Electronic Dice (£7.98), Digital Roulette (£8.60), Morse Code (£3.99) and Electronic Organ (£6.70). All prices include VAT and p&p and items are available by mail order or by placing a credit card order over the telephone. Prices do not cover batteries or tools.

**OK Machine & Tool (UK) Ltd., Dutton Lane, Eastleigh, Hants SO5 4AA (0703 610944)**

## CATALOGUES

Howard Associates have just released a short form catalogue which covers a range of PE projects such as the Solid State Car Instruments, Speech Processor, 27/28MHz Converter, DFM, Sound Operated Switch and the Dynamic Semiconductor Tester.

Part kits are available and Howard can also provide individual component price lists.

The catalogue is available from **Howard Associates, 59 Outlands Avenue, Weybridge, Surrey KT13 9SU.**

Another shortform catalogue just available is from Lascar Electronics. It contains their complete range of digital panel meters, counter timers and portable instruments. Also listed is a 12/24hr clock module and l.c.d. and l.e.d. thermometers which will measure temperatures between  $-55^{\circ}$  to  $+150^{\circ}\text{C}$  with a resolution of  $0.1^{\circ}\text{C}$ .

**Lascar Electronics, Unit 1, Thomasin Road, Basildon, Essex (0268 727383)**

## KEYBOARD CONSOLES

Boss Industrial Mouldings have recently introduced three medium sized keyboard consoles into their BIM 7400 range. This range now consists of six case sizes from 355 to 508mm wide by either 178 or 254mm deep and with a rear panel depth of 102mm. The front panel is inclined by 10 to 15 degrees for easier key operation.



The consoles are of all aluminium construction and incorporate ventilation slots in both rear and bottom panels with a gasket fitted between the panels to reduce vibration.

Prices for the range are from £16.05 to £26.33 excluding VAT.

**Boss Industrial Mouldings Ltd., 2 Herne Hill Road, London (01-737 2383).**

## DRAUGHTING AIDS

Constructors who like to produce their own p.c.b.s will be interested in the latest range of etch resistance transfers from Ace Mailtronix. The transfers which include straight or curved tracks, transistor, d.i.l. solid, oval, square and terminal pads are available either in sets of five sheets of a type or a mixed bag of six sheets including an introduction sheet. The transfers which are printed on  $115 \times 105\text{mm}$  sheets are available in a 1:1 scale for use directly onto copper clad boards or in a 2:1 scale for those

with photographic reduction facilities. Ace can also supply black crepe paper track tape in various widths for constructors with UV light boxes.

For a free catalogue of the complete range send a stamped addressed envelope ( $9 \times 4\text{ins}$ ).

**Ace Mailtronix Ltd., 3A Commercial Street, Batley, West Yorkshire, WF17 5HJ.**

## AUDIO-SAFE

The latest protection system for cars is the audio-safe unit which the makers claim makes the unauthorised removal of an in-car entertainment system virtually impossible.

The unit is a two part system: a base plate which replaces the usual dashboard trim plate and a cast aluminium cover that fits over the equipment and is secured to the replacement




panel by means of an individual locking key.

When locked together access to the mounting nuts, securing the equipment, is prevented. In fact the equipment itself cannot be seen.

The audio-safe will sell for around £25.00 from retailers.
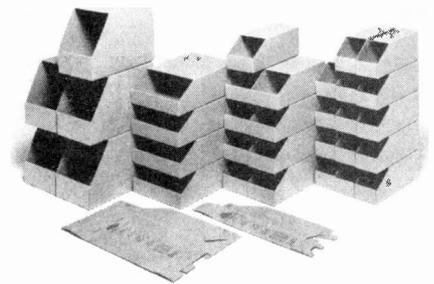
## STORAGE CASES

A new range of component containers has been added to the large range already carried by Trade Aids. The containers which are made of laminated board are light, strong and easily folded flat for storage. They are available in four sizes from  $380 \times 100 \times 133\text{mm}$




to  $380 \times 210 \times 266\text{mm}$  with prices ranging from 24p to 50p ex. VAT and p&p.

**Trade Aids, 54-56 Hawkes Road, Kingston upon Thames, Surrey, KT1 3FF. (01-549 2137)**
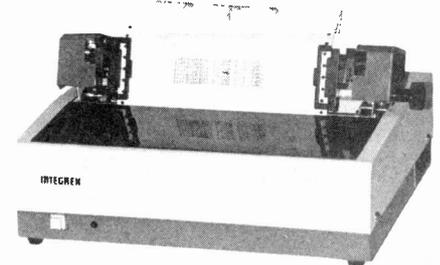
## COLOUR PRINTER

Integrex have recently announced the introduction of their new low cost impact Colour Matrix Printer, model CX80.

Printing in 7 colours (with simple control codes) and with 96 ASCII plus 64 graphics characters in ROM, the CX80 is fully dot ad-



dressable, has 15 user programmable characters together with double length and reverse character printing.

The retail price is £895 plus VAT, and further information is available from:

**Integrex Ltd., Portwood Industrial Estate, Church Gresley, Burton on Trent, Staffs. (0283 215432)**

## FUELSTRETCHER

The latest in-car monitor is the Fuelstretcher Drive Computer which will give an instantaneous m.p.g. indication as well as helping with route planning, record keeping and trip scheduling.

The computer processes and stores information received from the fuel flow and speed sensors. This information which is given on a 4 digit l.e.d. display shows the driver how much fuel has been used, elapsed time and distance travelled on a particular trip or on a weekly or monthly basis.

The makers claim the unit is as easy to install as a car stereo and should take no more than two hours. All the motorist has to do is to fit the fuel sensor into the fuel line, speed sensor to the drive shaft and then connect both to the computer unit.

The computer, complete with wiring, optional mounting bracket, instruction manual, fuel flow and speed sensors can be obtained directly from EnviroSystems for just over £80.00.


**EnviroSystems Ltd., Hampsfell Road, Grange-over-Sands, Cumbria, LA11 6BE (044 84 4233).**


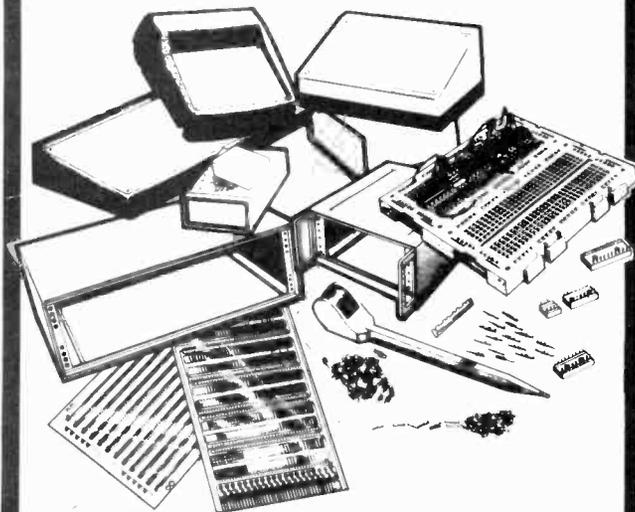
# ARE YOU INTERESTED IN ELECTRONICS?

THEN YOU SHOULD KNOW ABOUT VERO.

We manufacture a wide range of products for the electronics industry and can make available to you a selection suitable for project work. We offer you a large choice of Veroboard and circuit board accessories, including the latest solderless breadboard — VEROBLOC, which enables you to use those valuable components time and time again. Use a piece of Veroboard to save a successfully completed circuit and choose a box or instrument case from our vast range to give your project that professional touch.



For further details and a copy of the brochure please fill in the coupon below.

Veroboard Ltd.  
Retail Department.  
Industrial Estate,  
Chandler's Ford.  
Hampshire. SO5 3ZR.  
Tel. (042 15) 62829

**vero  
vero**

Veroboard Hobbyist Brochure.  
I enclose 40p. for package and postage

Name \_\_\_\_\_

Address \_\_\_\_\_



## Wilmslow Audio

THE firm for speakers!

SEND 50p FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST.

AUDAX ● AUDIOMASTER ● BAKER ● BOWER & WILKINS ● CASTLE ● CELESTION ● CHARTWELL ● COLES ● DALESFORD ● DECCA ● EAGLE ● ELAC ● EMI ● FANE ● GAUSS ● GOODMANS ● HARBETH ● ISOPHON ● I.M.F. ● JORDAN ● JORDAN WATTS ● KEF ● LOWTHER ● McKENZIE ● MISSION ● MONITOR AUDIO ● MOTOROLA ● PEERLESS ● RADFORD ● RAM ● ROGERS ● RICHARD ALLAN ● SEAS ● SHACKMAN ● STAG ● TANNOY ● VIDEOTONE ● WHARFEDALE ●

WILMSLOW AUDIO (Dept. P.E.)  
35/39 CHURCH STREET, WILMSLOW,  
CHESHIRE

Tel: 0625 529599

FOR MAIL ORDER & EXPORT OF DRIVE UNITS, KITS ETC.

Tel: 0625 526213

(SWIFT OF WILMSLOW) FOR HI-FI & COMPLETE SPEAKERS

IN  
KIT FORM

### FORGESTONE 500 TELETEXT

High quality colour television receiver  
NEW INFRA-RED FULL FEATURE  
REMOTE CONTROL TELETEXT

- ★ Pin diode tuner
- ★ Glass epoxy printed circuit panels
- ★ Full technical construction manual
- ★ Hi-Bri tube
- ★ Eleven integrated circuits
- ★ Ready built and aligned IF module
- ★ High quality components
- ★ Modern cabinets
- ★ All solid state
- ★ Fully isolated & protected power supply
- ★ Diode split L.O.P.T.
- ★ Low consumption

The ultimate in large screen 22" & 26" television receiver kits. Deluxe full spec. Teletext, 7 channel + VCR. Also video and audio in/out. 6 models in the 500 range.

Buy as you build. All Forgestone Kits are for the constructor of today, sections of the Kit are available separately. Please send stamp for further details of these quality products.

Telephone or Mail Orders accepted on Access/Barclaycard

**forgestone colour developments limited**

Ketteringham, Wymondham, Norfolk, NR18 9RY

Telephone: Norwich (0603) 810453

### PARNDON ELECTRONICS LTD.

Dept No 21 44 Paddock Mead, Harlow, Essex. CM18 7RR Tel: 0279 32700

**RESISTORS:** 1/4 Watt Carbon Film E24 range  $\pm 5\%$  tolerance. High quality resistors made under strictly controlled conditions by automatic machines. Bandoliered and colour coded.

£1.00 per hundred mixed (Min 10 per value)

£8.50 per thousand mixed (Min 50 per value)

Special stock pack 60 values. 10 off each £5.50

**DIODES:** IN4148 3p each. Min order quantity - 15 items  
£1.60 per hundred


**DIL SWITCHES:** Gold plated contact in fully sealed base - solve those programming problems  
4 Way 86p each 6 Way £1.00 each 8 Way £1.20 each

**DIL SOCKETS:** High quality, low profile sockets.

8 pin - 10p. 14 pin - 13p. 16 pin - 15p. 18 pin - 19p. 20 pin - 25p.

22 pin - 29p. 24 pin - 35p. 28 pin - 39p. 40 pin - 57p.

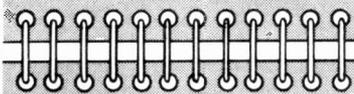ALL PRICES INCLUDE V.A.T. & POST & PACKING — NO EXTRAS  
MIN. ORDER - UK. £1.00. OVERSEAS £5 CASH WITH ORDER PLEASE



# INDUSTRY NOTEBOOK

By Nexus



## New Style Office

"----- a transition to twentieth century from nineteenth century office technology is not easily or quickly achieved."

You might suppose the quotation above was taken from a text written, say, in 1905 and referring to then new-fangled ideas like the telephone. Actually, it was written in 1980 and published in January 1981 and is from a case history on the introduction of word processing. It implies that office methods haven't changed much in over 80 years and carries a stern warning of hazards ahead.

Word processing is now a boom area for manufacturers and equipment suppliers. But the potential user had better be wary. It is all too easy to stumble into the trap experienced by those bold enough to invest in data processing in the 1960s. In those days persuasive sales talk and extravagant claims for economy as well as efficiency only too frequently led to hasty installations, muddle, inefficiency and high costs. The jokes about computers all but disappeared as computer science attained maturity. Early hilarity has been supplanted by the menace of computer fraud—no laughing matter.

Now that we are all accustomed to, even conditioned to, data processing, a transition to word processing ought to be comparatively easy and painless. And, one would have thought, demonstrably so as an office has a well understood structure and purpose.

Not so, according to this case history. The authors went back to first principles and asked themselves what an office is and what it does. They found that in their own case that different departments organised their affairs quite differently and often to suit the personal needs of executives and

secretaries as well as particular characteristics of the work undertaken.

There were more than 20 departments employing some 1,500 staff, half in London, originating over 1.2 million pages of text on A4 paper per year. When they looked at what people did they discovered that 150 person-years of time which should have been available for profit-earning professional tasks was being frittered away on internal administration. In fact the biggest savings would not be in reduction of secretarial costs but in gains of management time.

When it came to selecting a system it was found that over 30 suppliers offering over 50 different systems were available. Whittling these down to a short-list and final selection was no easy task.

The investment was eventually some £700,000 for the London office and an equal amount for the provincial offices, making a grand total of £1.4 million. The payback period was calculated as two years or less.

There is no space to describe all the development of software, training of staff, integration of the system with existing data processing facilities, or possible future expansion of the word processing system in terms of both size and newer technology as it becomes available. Or of how the system was progressively introduced, section by section, of 85 work stations without disruption of the daily work schedule.

The conclusion is that word processing is available now and is cost-effective. There is no mention of staff redundancy so that one assumes that payback in this case is added capacity for throughput which can only pay with an increase in business. In other words, while there are no immediate redundancies there should be no need to expand the staff for a long time ahead.

While this picture looks bleak for office workers, the other side of the coin is a huge new market for the electronics industry in manufacturing, installation, servicing and, eventually, a substantial replacement market, not to mention armies of software specialists.

Albert Einstein is recorded as having said: "If we look hopefully upon the shape of things to come, we can visualise automation as the greatest blessing mankind has ever known." I can only add that it seems a pity that the implementation of such a blessing is so painful.

## Inertia

As a counterweight to the above an eminent engineer last year was remarking that although technology continues to advance it was slow in introduction and had had little real effect on our daily life pattern. As examples he quoted that people still commuted every day in great discomfort and read newspapers produced and distributed in the same manner as in the early part of the century.

How true! But he, too, is expecting big changes. What he was describing was that today there is practically no technical limitation to what can be achieved. The

only real barrier to change is that people are conservative by nature.

## Expansion

Ten years ago Aberdeen Airport was a busy terminal handling 30,000 aircraft movements per year of which 4,000 were helicopters. This year the projected movements are 130,000 including 53,000 helicopter movements. A new runway was laid down in 1977 and a new control tower added in 1979. Latest addition is a comprehensive CCTV system for monitoring apron parking, refuelling and baggage handling areas.

Such has been the impact of North Sea oil. The spin-off for the electronics industry is substantial and not only at Aberdeen.

Exploration, drilling, pumping, data logging, communications at sea are all huge markets benefiting the industry. It is interesting to note that in an analysis of the performance of the FT 30 Ordinary Share Index over the past three years that the oil giant BP is a notable high flyer with a gain of 90 per cent showing the strength of oils. But BP comes only third. Runaway winner is Plessey with a gain of 170 per cent since 1978 and GEC a creditable second-placer up 117 per cent.

There are some doubts on whether the government can maintain the promised level of defence spending and this could have an effect on both GEC and Plessey prospects with some major projects. But both these companies have a wide spread of activities and any programme reductions or delays are not likely to have a great effect.

In fact the outlook for electronics has never been brighter. One market analyst, Mackintosh, is forecasting an overall European growth rate of 12 per cent through to 1984 and that the UK will increase its market share.

The British Electrical and Allied Manufacturers' Association (BEAMA), which includes heavy electricals as well as electronics firms in membership, reported a 17 per cent rise in exports over the first nine months in 1980. In the same period, imports were up only 10 per cent.


## ATE.

Automatic test equipment (ATE) continues to thrive. Marconi Space and Defence Systems are supplying equipment for the Middle Eastern military base workshop. The contract is worth £2.5 million and the equipment supplied will be used to check out 150 p.c.b.s, sub-assemblies and other electronic units on main battle tanks.

On a more modest scale a Racal ATE worth £64,000 has gone into service with audio engineers Neve, who make sound mixing consoles for broadcasting and other high quality applications. Manual testing of a complex Neve p.c.b. takes as long as 3½ hours. The Racal ATE does the same job in five minutes.

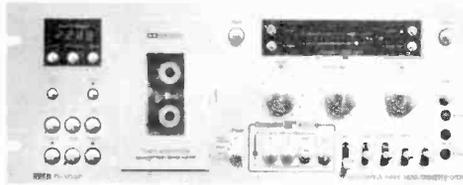
# CONSUMER ELECTRONICS SHOW

A gallery of impressions from the Consumer Electronics Show held in Las Vegas, January 1981.




Claimed to be the world's first computer connectable cassette deck, the Eumig FL-100. Built-in microprocessor enables on-tape indexing of sound tracks.

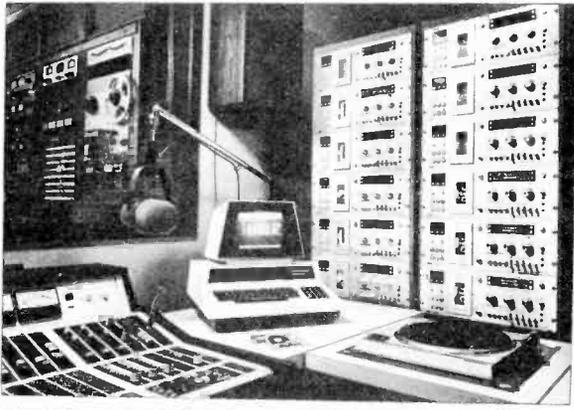Twelve FL-1000s under computer control in an automated broadcast. Photos courtesy of Eumig.



New Revox B795 direct drive turntable with Linatrak tangential tracking system. Motors are controlled by Hall effect sensors via quartz-referenced phase locked loops. Courtesy Studer Revox America Inc.

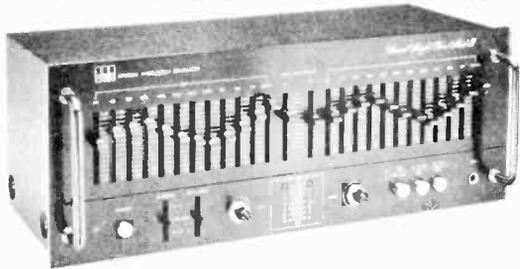More conventional than the deck shown above—or is it? All operations are computer supervised, and controlled entirely at the fascia so that the dust cover stays down. The new FR-D45 turntable, courtesy of Sansui.



BSR's ADC Sound Shaper Two Mark III, with i.e.d. slide controls, each with defeat switch for individual on/off. Unit includes 12 frequency controls of 24dB range per channel. Courtesy BSR (USA) Ltd.


Not a two-faced grandfather clock, but the Revox Audio Rack. Galvanized steel to give strength, oak veneer to give finish. Courtesy of Studer Revox.



The world's most expensive stereo receiver, or so it is claimed, is the Revox B780. Incorporating a 70W per channel amplifier and quartz-controlled synthesizer FM tuner, the entire system is based on advanced technology. The unit also uses a microprocessor to manage the 18-station recall memory (with back-up battery). Specification is top line, and a Dolby FM circuit card can be user-installed. Suggested list: \$2699.



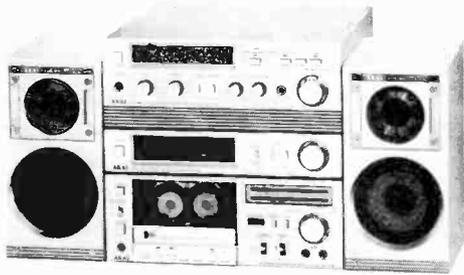Ultra-lightweight headphones by Mura. Weighing just 1.6 oz, the "Red Set" phones employ samarium-cobalt drivers. Courtesy of Mura Corp.



The Akai mini-component system, UC-3. The amplifier produces 45W of power per channel. *Courtesy of Akai America Ltd.*

**Dimensions**

UC-U3 mini-amp:  
11 in. wide, 4 in. high, 10 in. deep  
Cassette deck:  
11 in. wide, 4 in. high, 10 in. deep  
UC-S4 AM/FM  
digital tuner:  
11 in. wide, 2 in. high, 10 in. deep




Put a tape of any oxide formulation into this cassette deck, and the on-board computer will have adjusted to correct bias, equalisation and sensitivity within seconds. Functions are solenoid (logic) controlled. The fluorescent bar meter allows for peak hold, and Dolby noise reduction is included in the GX-F95. *Akai America Ltd.*




Selling the concept of psychoacoustics, "Doc" Cavalier of Omnisonix Ltd. says of his Imager... "far more dramatic than the performance of a dynamic range expander". Shown here is the 801-A, intended for automobile hi-fi. *Courtesy of Omnisonix Ltd.*

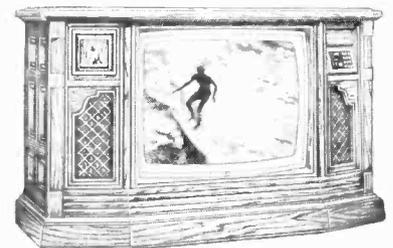The Bearcat 150 synthesised scanner, featuring 10-channel memory, fluorescent display and membrane keypad operation. Frequency ranges from 30 to 512 MHz, covering 5 bands.



Leading edge technology concealed in a "Mediterranean" styled colour TV. Model 5056 in Pecan, by *Magnavox*.

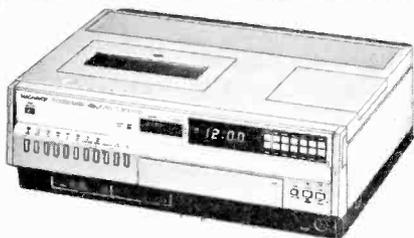

Magnavox 14-day programmable touch-tune VHS VCR, model 8340 portable. Features frame by frame advance, variable slow motion, stop action, fast motion and picture search; fascia or remote control.

Described as the *unconventional* colour video camera, Akai's VC-X1 features auto-focus, whereby the camera adjusts itself relative to the main subject matter. The equipment can handle close-up and low light level work. *Photo courtesy of Akai.*




Magnavision laser-optical videodisc player. Forward, reverse, speed and search facilities, plus choice of bi-lingual-or-stereo, are built in. Video discs are immune to dust and scratches. *Courtesy of Magnavox.*





Today's look in television. The CB-954 is one of the latest family of 19 inch sets from Toshiba. Picture improvement results from the following: Electronic Noise Canceller, Automatic Dark Picture Intensifier, and a White Detail Purifier. Photo courtesy of Toshiba America Inc.

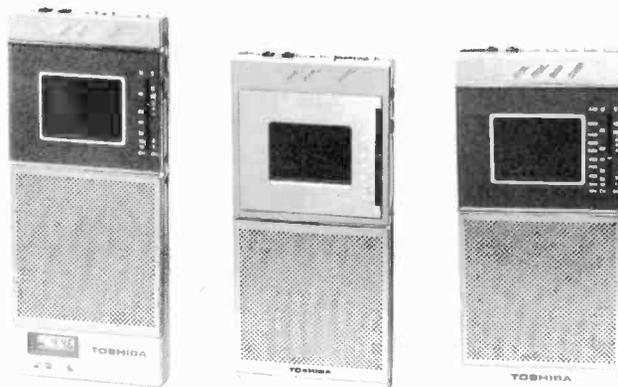
### POCKET TELEVISION WITH LIQUID CRYSTAL SCREEN



The star revelation at Las Vegas was undoubtedly three hand-held UHF-VHF TVs, whose monochrome pictures are produced on flat-screen l.c.d.s. Each unit measures an amazing 6.8 x 3.2 x 0.7 inches thick, and weighs just 10.5 ounces. The screen system used measures 1.2 x 1.6 inches (2 in. diagonal). One model incorporates a digital clock, and another, a radio. All three televisions can double the image size by zooming in on the centre area of the screen.

This is the way Toshiba describe the operation of their breakthrough: "The screen comprises a liquid crystal matrix panel filled with liquid crystal in a gap between the integrated circuit and the front glass. A picture is the end result of brightness differences on the crystal created by voltage differentials."

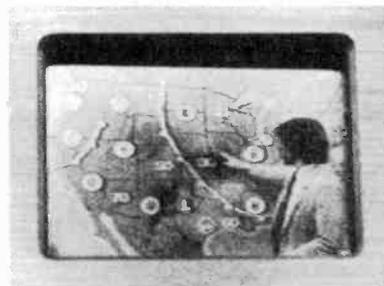Photographs courtesy of Toshiba Consumer Electronics Divn.




Computers disguised as animals aid development in thinking and co-ordination in the very young.




Mattel Electronics, a pioneer of hand-held electronic games, is expanding in the computerised video games field. Some of these games are shown below.


OUTLAW

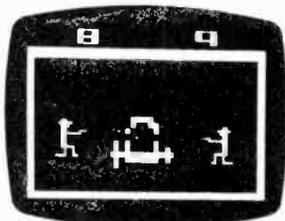


BOWLING

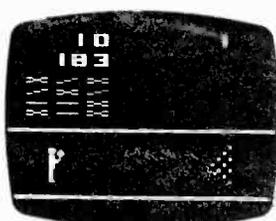

FLAG CAPTURE

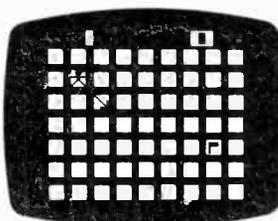

HUMAN CANNONBALL

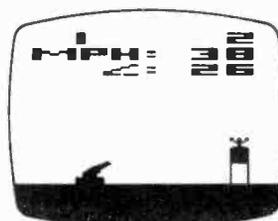

A unique three-dimensional game called Cosmos. In addition to what are described as "Holoptic" images, this sophisticated l.e.d. game incorporates novel sound effects.





The EL-7001 Memowriter is an alphanumeric typewriter/calculator with 40 word-memories, by Sharp.



The Imagination Machine II with 27K RAM, 14K ROM, is a small business system with r.r.p. \$1,199. It features up to eight video colours, sound synthesiser, BASIC or 6800 m/c, object orientated and point resolution graphics. Photo shows floppy interface module inserted. *Courtesy of APF Electronics.*



Praxis 35 portable electronic typewriter. Automatic correction of last ten characters via memory. *Courtesy of Olivetti.*

Mura claim this is one of the lowest priced digital VOMs. The LCD-200 features easy-to-read  $\frac{1}{2}$  inch high digits, and is intended for hobbyists and engineers.



Banana plugs are used in preference to pin contacts, and all ranges are switched, obviating the need to change the probe leads from one socket to another, as is often the case with cheaper units. *Photo courtesy of Mura Corporation.*



The "jewelry look" has come to calculators. This charcoal grey case with raised chrome numeral keys and l.c.d. display should suit some executives.



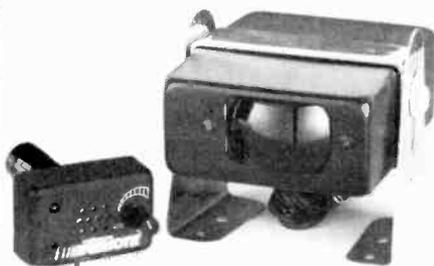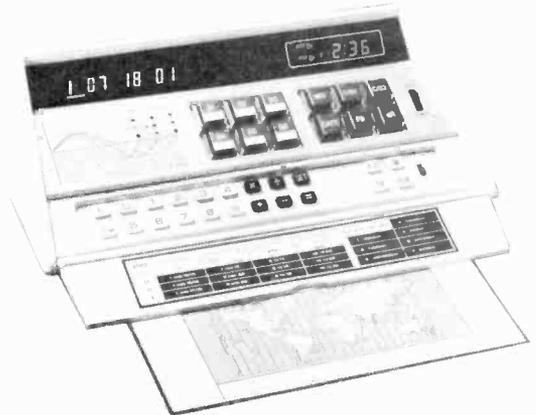
The Kosmos biorhythm unit and world time clock will display data on six people. It also has a stopwatch. *Courtesy of Kosmos International of Atlanta.*




Fuzzbuster's radar detector for cars. The remote portion, utilising dielectrically coupled waveguide technology, fits behind the radiator grill. *Electrolert Inc.*

A few of the very many Atari games on offer. *Pictures courtesy of Atari Consumer Divn.*


GOLF

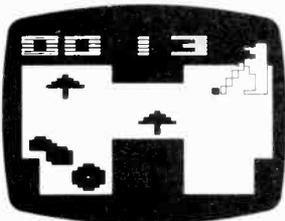


SKYDIVER

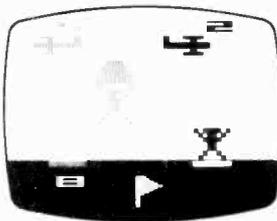

TIC-TAC-TOE

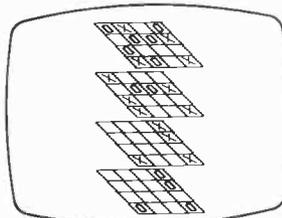


ADVENTURE

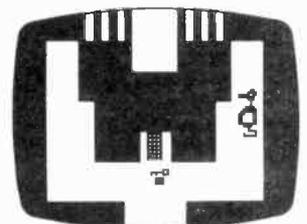

CONSUMER ELECTRONICS SHOW

# Oscilloscopes

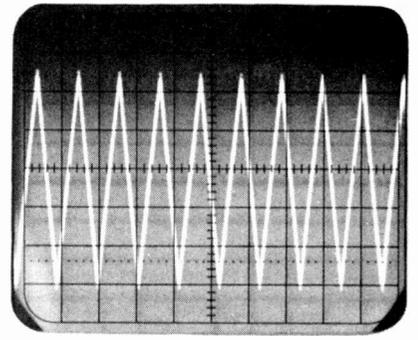

## ....HOW THEY WORK

### Part One...The Cathode Ray Tube...by Ian Hickman

**This two-part feature is taken from the last two chapters of a new book by this well-known author. Published by Newnes Technical Books the paperback is entitled *Oscilloscopes. How to use them. How they work.***

THE cathode-ray tube is the main component of an oscilloscope. A cathode-ray tube consists basically of an electrode assembly mounted in an evacuated glass vessel (Fig. 1). The electrodes perform the following functions:

1. A triode assembly generates the electron beam, originally called the "cathode ray". It consists of a cathode K heated by a filament F, a control grid G and the first beam-acceleration electrode (2).
2. An electrode (1) focuses the beam.
3. The beam is then further accelerated before reaching the deflection plates.
4. The vertical deflection plates change the direction of the beam in proportion to the potential difference between them. When this is zero, i.e. the two plates are at the same potential, the beam passes through undeflected. The vertical deflection plates are so called because they can deflect the beam in the vertical direction, so that it hits the screen at a higher or a lower point; they are actually mounted horizontally above and below the beam, as shown in Fig. 1. Similarly the horizontal deflection plates permit the beam to be deflected to left or to right.
5. The deflected beam then hits the fluorescent coating on the inner surface of the glass screen of the c.r.t. The coating consists of a thin layer of "phosphor", a preparation of

very fine crystals of metallic salts deposited on the glass. The "spot" or point of impact of the beam glows, emitting light in all directions including forwards. Modern c.r.t.s are aluminised, i.e. a thin layer of aluminium is evaporated on to the rear of the coated screen. The electrons pass through this with little retardation, causing the phosphor to glow as before, but now the light emitted rearwards is reflected forwards, almost doubling the useful light output.

The potential at the focus electrode is adjusted to obtain a very small round spot on the end of the tube. Unfortunately, if no other control were provided, it would often be found that the focus control setting for minimum spot widths was different from that for minimum spot height. This is avoided by providing an astigmatism control. In the case of a simple cathode-ray tube this consists of a potentiometer that adjusts the voltage on the final anode and screen relative to the deflection plate voltages. Alternate adjustments of the focus and astigmatism controls then permit the smallest possible spot size to be achieved. With more complicated tubes using a high "post-deflection acceleration ratio" another electrode is often needed. This is a "geometry" electrode and is connected to another preset potentiometer, which is adjusted for minimum "pincushion" or "barrel" distortion of the display.

When an electron beam passes between two horizontal plates

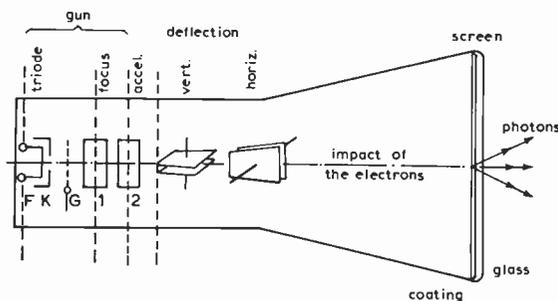


Fig. 1. Basic oscilloscope (electrostatic) cathode-ray tube (courtesy Enertec Instrumentation Ltd.)

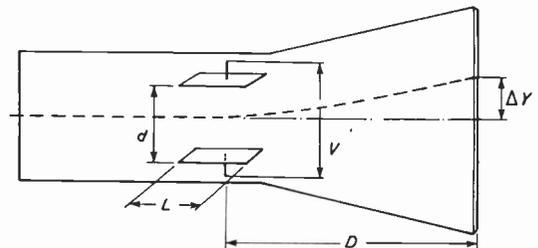


Fig. 2. Y-deflection sensitivity: see text (courtesy Enertec Instrumentation Ltd.)

that have a potential difference of  $V$  volts between them (Fig. 2) it is deflected vertically by an amount:

$$\Delta Y = \frac{KVLD}{2V_a d}$$

- where  $L$  = length of the plates  
 $D$  = distance between the plates and the point on the axis where the deflection is measured  
 $d$  = distance between the plates  
 $V_a$  = acceleration voltage applied to the beam at the level of the plates  
 $K$  = a constant relating the charge of an electron to its mass.

The Y deflection sensitivity of a c.r.t. is defined by  $\Delta Y/V$  and is expressed in cm/V. However, in practice the inverse relationship is normally used:  $V/\Delta Y$ , in V/cm, i.e. the differential deflection-plate voltage necessary to achieve a spot deflection of 1cm.

Brilliance or intensity modulation (also called Z modulation) is obtained by the action of a potential applied to the cathode or grid that controls the intensity of the beam. Generally, a change of 5V will produce a noticeable change of brightness, while a swing of about 50V will extinguish a maximum-intensity trace. The beam is normally extinguished during "flyback" or "retrace"; see Part 2. This may alternatively be achieved in some c.r.t.s by means of an auxiliary "blanking" electrode, which can deflect the beam so that it no longer passes through the deflection plates and hence does not reach the screen.

### TUBE SENSITIVITY

The deflection plates of a c.r.t. are connected to amplifiers, which can be of relatively simple design when the required output amplitude is low; it is therefore desirable for the tube sensitivity to be as high as possible. To enable the amplifier to have a wide bandwidth, the capacity between the plates must be kept low, so they must be small and well separated. On the other hand, in order to obtain a suitably clear trace of a signal with low repetition frequency (or single-shot) the energy of the beam must be high. But the ideal tube must be:

1. Short (not cumbersome):  $D$  small
2. Bright (high acceleration voltage):  $V_a$  large
3. And with low deflection-plate capacity:  $L$  small,  $d$  large

This gives a tube with very low sensitivity, considering the formula:

$$\text{Sensitivity} = \frac{\Delta Y}{V} = \frac{KLD}{2V_a d}$$

The requirements for high sensitivity contradict the terms of the equation. Practical cathode-ray tubes are therefore the result of a compromise. However, techniques have been developed to improve a selected parameter without prejudice to the others. Post-deflection acceleration (p.d.a.) is one of these; see Fig. 3. To improve the trace brightness while retaining good sensitivity, it is arranged that the beam passes through the deflection system in a low energy condition (relatively low initial acceleration); post-deflection acceleration is then applied to the electrons. This is achieved by applying a voltage of several kilovolts to the screen of the c.r.t.

Spiral p.d.a., Fig. 4, is a development of the basic p.d.a. technique, and consists of the application of the p.d.a. voltage to a resistive spiral (500M $\Omega$ ) deposited on the inner tube surface between the screen and the deflection system. The uniformity of the electric field is improved, which reduces distortion. In addition the effect of the p.d.a. field between the deflection plates is weaker, so the loss in sensitivity caused by this field is reduced.

The use of a field grid—Fig. 5a—avoids any reduction in sensitivity caused by the effect of the post-deflection acceleration field. A screen is interposed between the deflection system and

the p.d.a.; this makes the tube sensitivity independent of the p.d.a., a significant benefit. The screen must, of course, be transparent to the electrons and is formed from a very fine metallic grid. With this system we reach the domain of modern cathode-ray tubes.

The next development is the electrostatic expansion lens—Fig. 5b. By modifying the shape of the field grid (e.g. a convex grid) it is possible to create, with respect to the other electrodes, an electric field that acts on the electron beam in the same way as a lens acts on a light beam. It is therefore possible to increase the beam deflection angle, for example by a factor of two, which improves the sensitivity by the same amount.

The field can also be formed by quadripolar lenses. So, for example, if the sensitivity of a spiral tube is 30V/cm in the X axis and 10V/cm in the Y axis, then the sensitivity of a lens-fitted tube, for the same trace brightness, may be 8V/cm in X and 2V/cm in Y or even better.

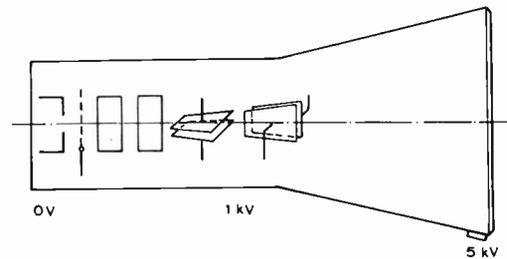


Fig. 3. Single-stage post-deflection acceleration (courtesy Enertec Instrumentation Ltd.)

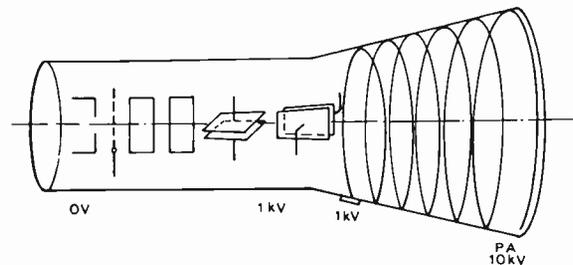


Fig. 4. Spiral p.d.a. (courtesy Enertec Instrumentation Ltd.)



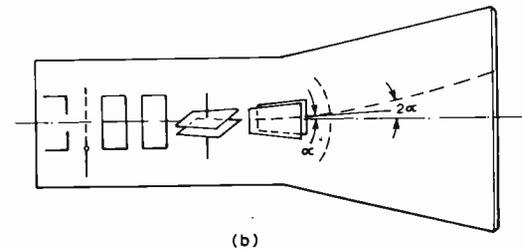
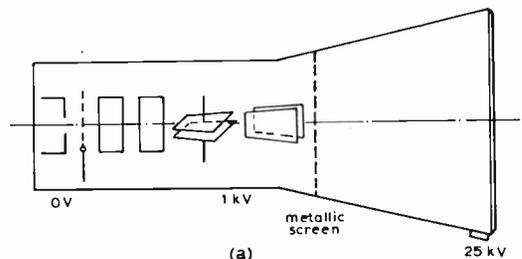



Fig. 5. (a) Mesh p.d.a.; (b) As (a) combined with expansion lens (courtesy Enertec Instrumentation Ltd.)

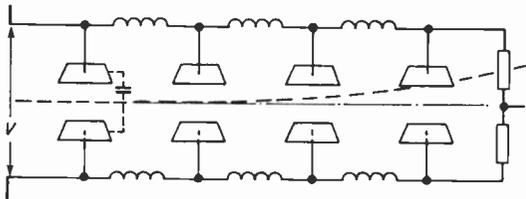


**Fig. 6. Delay-line Y-deflection plates (courtesy Enertec Instrumentation Ltd.)**

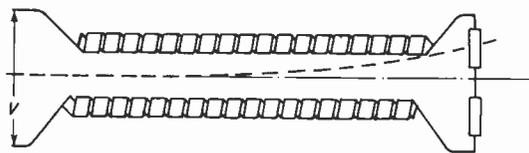

**Fig. 7. Travelling-wave Y-deflection plates (courtesy Enertec Instrumentation Ltd.)**

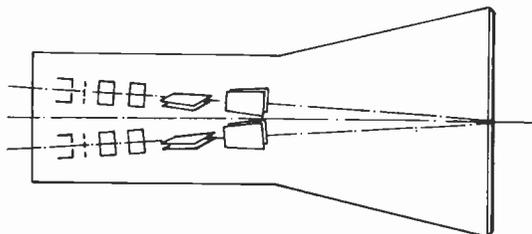

(a)

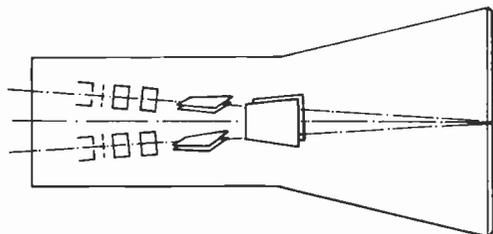

(b)

**Fig. 8. (a) Dual-gun tube; (b) Dual-gun tube with common X-deflection plates (courtesy Enertec Instrumentation Ltd.)**

To improve the sensitivity by modifying the deflection system it is necessary to do one of two things:

1. Reduce the distance between the plates, increasing the capacity between them; in addition it must be possible to deflect the beam without it striking them.
2. Lengthen the plates, again increasing the capacity; however, the transit time involved limits the application of this idea.

The transit time is the time taken for an electron to pass through the deflection system:  $t_0 = L/\text{electron speed}$ . Suppose that a sinusoidal voltage of period  $t_0$  is applied to the deflection plates. An electron leaving the plates will be in the same position as one entering the system, because the instantaneous value of the voltage applied to the plates will be the same (one period between the input and the output) and there will be no deflection. To enable the beam to be deflected so as to trace the outline of the applied signal, the length of the plates must be small compared with the distance the electrons travel during the period of one cycle of the signal. So for high-frequency work the plates must be short, which again reduces the sensitivity.

This problem can be circumvented by the use of sectional plates (Fig. 6). To improve the sensitivity several plates are placed in series, connected by a delay line. As the propagation velocity of the line is made equal to the speed of the electrons in the beam, the deviation accumulates successively. On the other hand the parasitic capacitance of the plates is incorporated in the delay line, which must be terminated in its characteristic impedance. The design of the line is entirely determined by its stray capacitance and the propagation time. This brings us to delay-line deflection plates (Fig. 7). Here, the dimensions of the plates have been reduced and their number increased. Two flattened helices are used, each spiral acting as a deflection plate. The helix is constructed in such a way that its propagation velocity corresponds to the speed of the electron beam. These deflection systems, together with field grids or quadripolar lenses (or both), permit the construction of very high-performance tubes.


#### OTHER TUBE CHARACTERISTICS

To be suitable for use at high frequencies a c.r.t. must, as already discussed, have a highly developed deflection system.

But this alone is not sufficient when it is required to observe and photograph fast pulses with low repetition rates or single-shot phenomena. The brilliance of the display must also be adequate. This is why "writing speed" is an important feature in these conditions. Writing speed is defined as the maximum speed at which a spot, passing once across the tube face, can be photographed under specified conditions (camera, aperture, image/object, film sensitivity).

On the occasions when it is necessary to compare several fast, single-shot phenomena occurring simultaneously, the only solution is to use an oscilloscope equipped with a c.r.t. with several beams. There are a number of different types available:

1. Multi-gun tubes. Fig. 8a shows a c.r.t. with several cathode-ray assemblies mounted in a single tube. Fig. 8b shows a tube where each gun or triode assembly has its own vertical deflection system but shares common horizontal deflection plates. All phenomena are displayed with the same sweep speed.

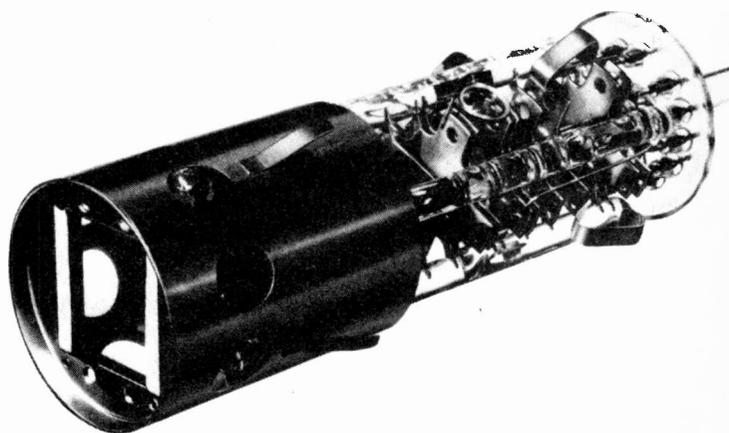

**Fig. 9. Electrode assembly of Brimar mesh p.d.a. c.r.t. type D13-51GH (courtesy Thorn Brimar Ltd.)**

2. Multi-beam tubes. There is a single electron gun for the different deflection systems, typically two. The beam is shared between each deflection system by means of a splitter plate. This type of tube is more economical because there is a single gun assembly. However, there is reaction between the two systems, and the brilliance of the displays cannot be adjusted separately.

## CONSTRUCTION

The construction of the electrode assembly of a mesh p.d.a. cathode-ray tube is shown in Fig. 9. The deflection plates are within the cylindrical shield and the mesh covers the square opening at the end. The wires of which the mesh is woven are so fine that it is invisible; this also ensures that it is transparent to the beam of electrons. Fig. 10 shows a high-performance oscilloscope c.r.t. with side connectors to the deflection plates for minimum capacitance, spiral p.d.a., internal graticule, bonded implosion guard and light guide for graticule illumination.

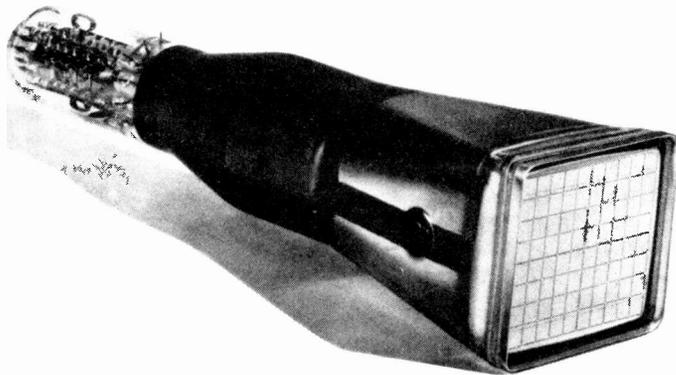


Fig. 10. Brimar spiral p.d.a. c.r.t. type D14-210GH/82 with internal graticule (courtesy Thorn Brimar Ltd.)

All the measures to maximise the bandwidth of a c.r.t. mentioned previously—p.d.a., delay-line deflection plates, scan expansion lenses—have been put together in the cathode-ray tube used in the Tektronix type 7104 oscilloscope. This instrument boasts a 1GHz real-time bandwidth, this limit being set by the Y amplifier rather than the c.r.t. itself. The latter could display signals up to 2.5GHz, were it possible to design suitable wide-band drive circuitry. Also, notwithstanding the conflict, explained earlier, between tube design parameters for optimum bandwidth and maximum writing speed, this tube achieves the remarkable writing speed of 20,000cm/μs, using ASA 3000 film without fogging. (In fact, single-shot events at that speed can also be seen comfortably with the naked eye.) The secret is revealed in Fig. 11, which shows that in addition to the measures already mentioned, the c.r.t. incorporates a microchannel electron multiplier plate. This consists of thousands of short parallel tubes, each coated internally with a high-resistance film. Each individual tube acts as an electron multiplier by virtue of secondary emission, resulting in 10,000 electrons hitting the phosphor for each electron in the beam. Owing to the small spacing between the microchannel plate output side and the aluminised phosphor, together with the high potential difference between them, there is negligible spreading of the output of each microchannel tube, maintaining a small sharp spot size.

**NEXT MONTH: the oscilloscope circuitry.**

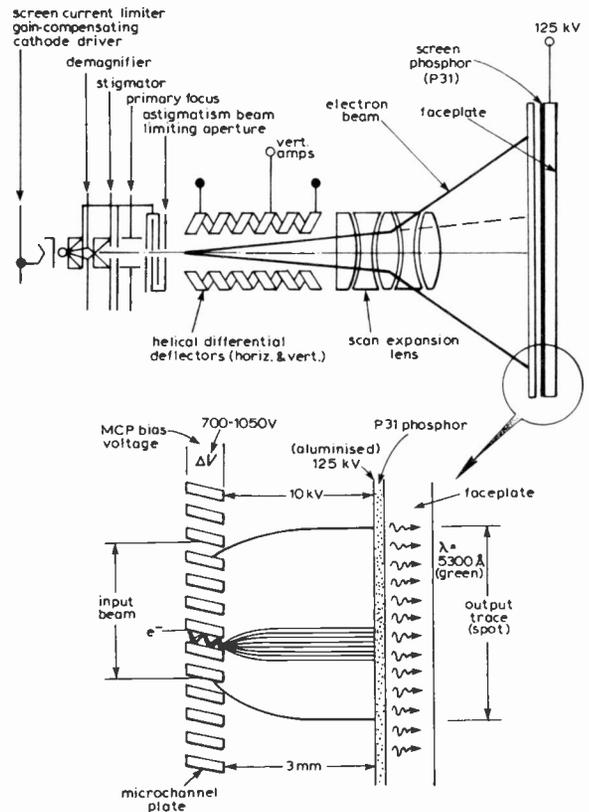


Fig. 11. Cathode-ray tube used in Tektronix oscilloscope type 7104 (courtesy Tektronix UK Ltd.)

# Oscilloscopes

Look  
new  
book

How to use them  
How they work

Ian Hickman

Explains from first principles what the oscilloscope does and how it works. The capabilities of both basic and advanced scopes and related instruments are examined. Essential reading for all users and potential users of these vital electronic tools.

216 x 138mm 128 pages Illustrated  
0 408 00472 X £3.45 Paperback

Available from your local bookseller or in case of difficulty from the publisher.

ORDER NOW. Cut out this coupon and return it to Patricia Davies at the address below.

Please send me \_\_\_\_\_ copy/ies of **Oscilloscopes** (Hickman) 0 408 00472 X @ £3.45 Paperback

I enclose a cheque/PO for £. \_\_\_\_\_ in total payment

From \_\_\_\_\_

Address \_\_\_\_\_

(PE/4 81)

**Newnes Technical Books**  
Borough Green, Sevenoaks, Kent TN15 8PH

# PE DIGISOUNDER

PART 1

BRIAN CURRIE

THE PE Digisounder is a digital depth gauge suitable for all types of small vessels. The l.c.d. read-out gives a clear unambiguous display, drawing only a small operating current. This makes it particularly suitable for sailing boats where power is often at a premium. The 'Digisounder' also includes an internally pre-settable alarm which gives an audible warning if the depth of water below the hull drops under a certain level.

Assuming sufficient interest a synthesised speech board will be featured in a future issue. This will utilise a small loudspeaker and actually call out the depth indicated on the Digisounder. This facility will be particularly useful to single-handed sailors or when sailing at night. It will fit inside the 'Digisounder' case and outputs are provided ready for it.

The 'Digisounder' can be constructed at a fraction of the cost of similar commercial equipment and will replace the 'Seafarer' type fitted in many boats, as it utilises the same ultrasonic transducer.

## 'DIGISOUNDER' BASICS

The principle is similar to radar in that a pulse is transmitted, and the time taken for the reflection to return is propor-

tional to the distance the pulse has travelled. With radar the pulse is electromagnetic and travels at 300,000km per second approximately. The Digisounder uses an ultrasonic pulse of usually 150kHz, which travels approximately 1.5km per second in water. So typically, we will expect time durations in the order of tens of milliseconds.

Conventional depth sounders usually have a rotor with an l.e.d. or neon, which flashes as the pulse is transmitted and flashes again when it is received. By this time, the rotor has moved further round the clock face scale, giving an approximate indication of depth. This system, besides being sometimes hard to read, is very wasteful of power as the rotor consumes power as it turns, and to give an apparently continuous display, the pulse must be transmitted and l.e.d. flashed several times a second.

The Digisounder only transmits one pulse of 500 microseconds duration per second and the l.c.d. display consumes negligible power, so the overall consumption from a 9V battery is around 7mA, compared with 250mA for the conventional type.

The overall operation can be seen from the block diagram, in Fig. 1.1. Although the circuit contains certain extra

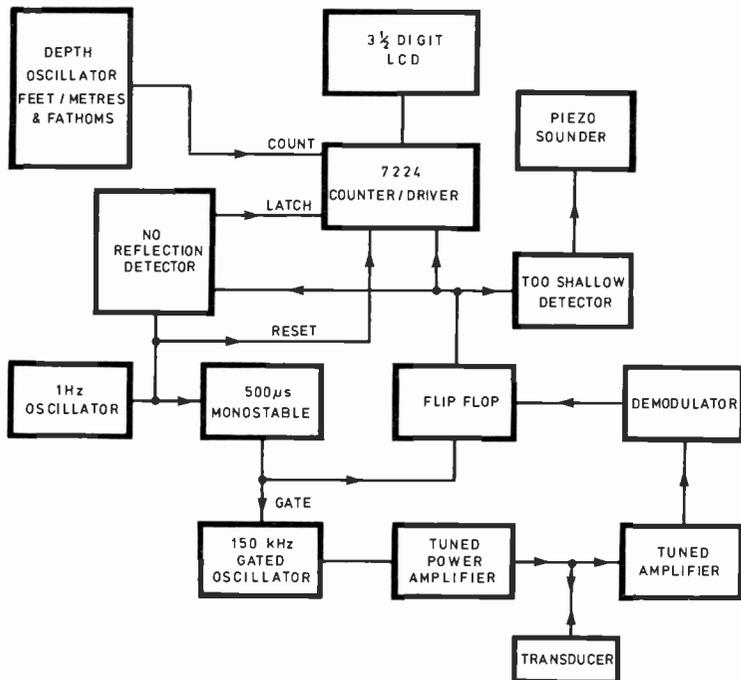



Fig. 1.1. Block diagram of the Digisounder

features, the basic operation is to pulse an electronic transducer. At the same time, a counter is reset to zero and the counter input is held open. An oscillator input is fed into the counter, which will commence to count. The counter is stopped and the resultant count displayed on receipt of the transmitted pulse. This count is dependant on the depth of water below the transducer. Varying the oscillator frequency means that the read-out can be in feet, metres or fathoms.
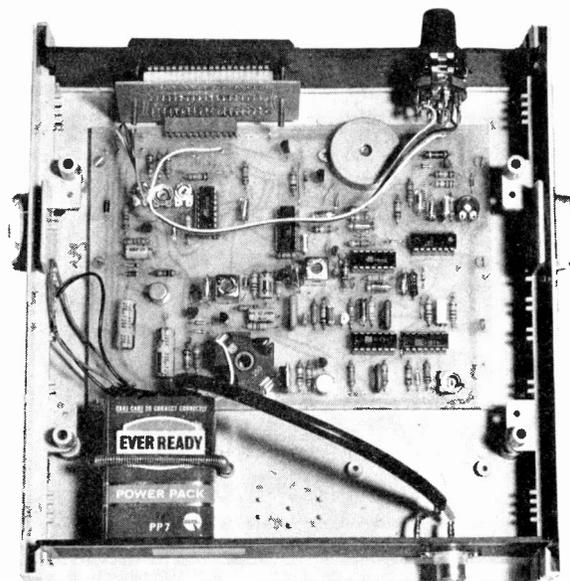
### CIRCUIT DESCRIPTION

The complete circuit diagram of the Digisounder is shown in Fig. 1.2. The 1Hz oscillator IC1d, e, f controls the timing of the circuit. It initiates the cycle of firing the 500μs monostable IC2e, IC2f which gates the 150kHz oscillator IC1a, IC1b, IC1c, "on" (for 500μs). The tuned power amplifier TR3, TR4, TR5 amplifies this 9V pk-pk square wave to about 400V pk-pk. The waveform at this stage is approximately sinusoidal because of the tuning. When this 400V signal is applied to the transducer, the crystal turns the electrical signal into an acoustic one, which travels down to the seabed where it is reflected. On returning to the transducer, it is converted back to an electrical signal (typically tens of microvolts).

The tuned amplifier TR8, TR10 has a time dependant automatic gain control TR6, TR7. The 1Hz oscillator turns the gain down during transmission and raises it again over the following 30 milliseconds. As the transducer is fired, a positive going pulse appears at the output of IC3b, switching on TR7, discharging C9. Which then charges exponentially through R15, R16 and this changing level is fed via emitter follower TR6 to supply the first tuned stage of the receiver, TR9. The purpose of this is to reduce the risk of a false reflection from air bubbles or debris, which if they are near the transducer can cause large receiver signals and hence an incorrect depth reading. As the gain of the tuned amplifier is very high, it is susceptible to all sorts of interference, hence the need to turn the 150kHz oscillator off by D2 when it is not driving the transducer (if it were not turned off, some small amount of 150kHz might get through and saturate the amplifier).



Internal view of the Digisounder

### COUNTER

The heart of the unit is the main counter, which receives pulses from the oscillator. The gate of the counter is held open from the moment the transmitter is fired until the returned pulse 'disables' the counter, and operates the latch, updating the display. The time the gate is held open is proportional to depth of water and the frequency of pulses fed in during this time determines the ultimate displayed figure. Therefore, by feeding in different frequencies, the counter will display feet, metres or fathoms. As an example, the 'feet' oscillator is exactly six times the frequency of the 'fathoms' input. This automatically converts the reading into fathoms.


The counter used is the Intersil 7224, a 4½ digit counter that will drive an l.c.d. directly. Although 3½ digits are sufficient, this i.c. was chosen as being the most convenient method of implementing the required function. It features low power operation, direct 7-segment l.c.d. drive, latch and reset inputs and a count inhibit (enable/disable) control.

### "NO REFLECTION" DEFLECTION

The flip-flop IC4a, IC4b is set by the 1Hz oscillator at the beginning of the transmit pulse and reset by the demodulator IC3e when a reflection is detected (so the output is high for a time proportional to the depth of the water, and this signal is used to 'enable' the 7224 counter). If the bottom has soft mud or substantial weed growth, it is possible that no reflection will be detected. IC5a, IC5b another flip-flop is set on transmission, and stays in this position as long as reflections are received. If, however, after approximately 0.5 seconds, no reflection is received, IC5d resets it. IC5a output goes low, which resets the main flip-flop (IC4a, IC4b) and prevents the latch pulse being transmitted by IC4d. TR11 turns on, and pulls the reset and latch inputs of the 7224 low. This makes the display show a zero reading indicating that no reflection has been received. As soon as a correct reflection arrives, normal operation recommences.
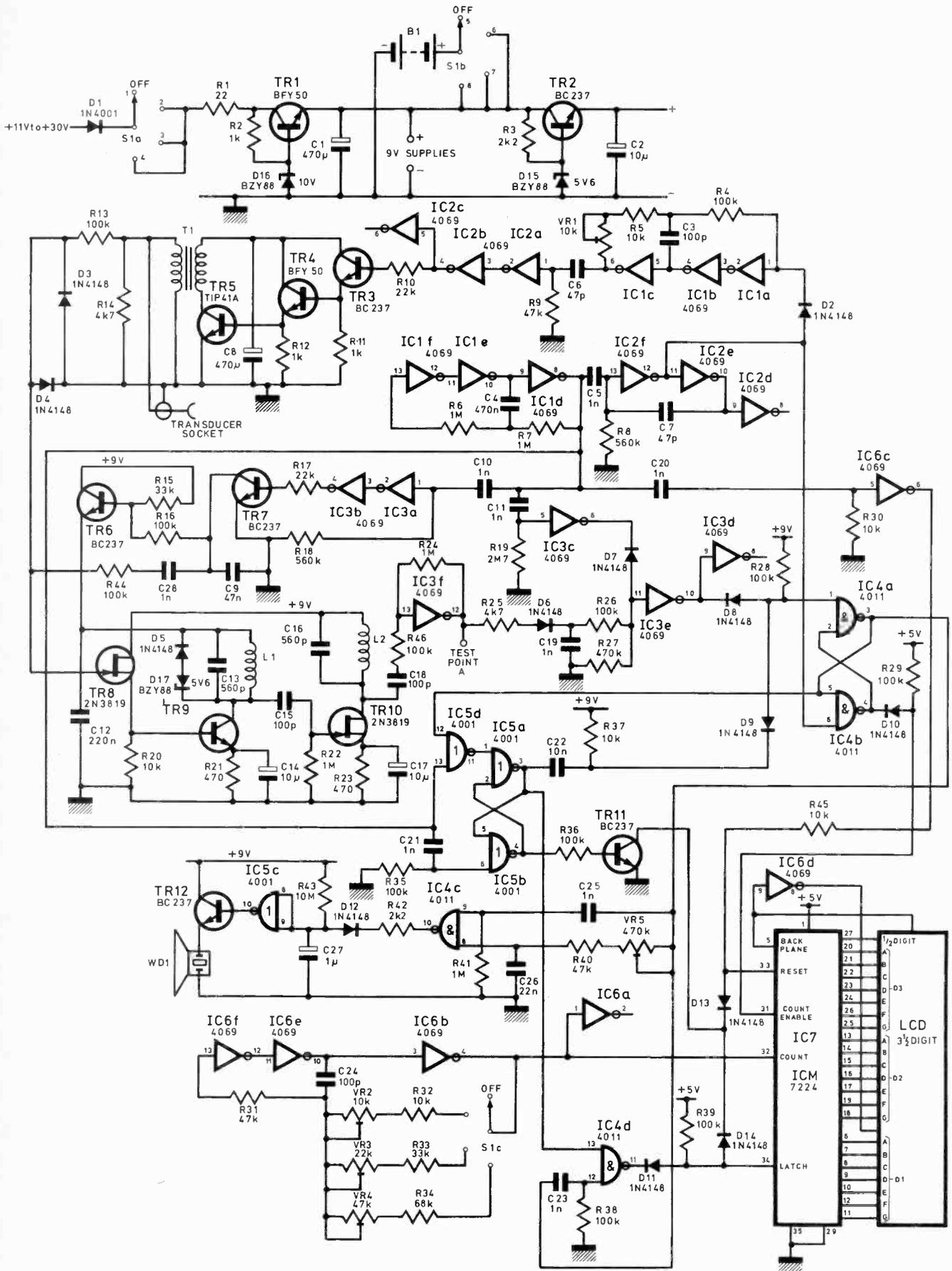
### DEPTH OSCILLATOR

By varying the rate of the oscillator IC6b, IC6e, IC6f applied to the count input of the 7224, it is possible to arrange the display to show the depth in any desired unit — feet,



## COMPONENTS . . .

### Resistors

R1	22
R2, R11, R12	1k (3 off)
R3, R42	2k2 (2 off)
R4, R13, R16, R26, R28, R29, R35, R36, R38, R39, R44, R46	100k (12 off)
R5, R20, R30, R32, R37, R45	10k (6 off)
R6, R7, R22, R24, R41	1M (5 off)
R8, R18	560k (2 off)
R9, R31, R40	47k (3 off)
R10, R17	22k (2 off)
R14, R25	4k7 (2 off)
R15, R33	33k (2 off)
R19	2M7
R21, R23	470 (2 off)
R27	470k
R34	68k
R43	10M

All resistors  $\frac{1}{2}$ W 5% carbon

### Potentiometers

VR1, VR2	10k per min. (2 off)
VR3	22k per min.
VR4	47k per min.
VR5	470k per min.

### Capacitors

C1, C8	470 $\mu$ 16V (2 off)
C2, C14, C17	10 $\mu$ 16V (3 off)
C3, C15, C18, C24	100p (4 off)
C4	470n
C5, C10, C11, C19, C20, C21, C23, C25, C28	1n (9 off)

C6, C7	47p (2 off)
C9	47n
C12	220n
C13, C16	560p (2 off)
C22	10n
C26	22n
C27	1 $\mu$

### Semiconductors

D1	IN4001
D2-D14	1N4148 (13 off)
D16	BZY88 10V Zener
D15, D17	BZY88 5V6 Zener (3 off)
TR1, TR4	BFY50 (2 off)
TR2, TR3, TR6, TR7, TR9, TR11, TR12	BC237 (7 off)
TR5	TIP41A
TR8, TR10	2N3819 (2 off)
IC1, IC2, IC3, IC6	4069 (4 off)
IC4	4011
IC5	4001
IC7	ICM7224

### Miscellaneous

3 pole 4 way switch
3 $\frac{1}{2}$ digit l.c.d.
PP7 battery and connector
15 way p.c.b. plug and socket
Case Pac Tec 60119-1
UHF socket
Rm10 (AL250) pot core kit (RS228-242)
YXNS 30450NK 2mH choke (2 off)
22 s.w.g. enamelled wire
36 s.w.g. enamelled wire
Ultrasonic transducer
Soldercon pins
WD1 Piezo-Electric Sounder

### Constructor's Note

A complete set of parts for the Digisounder is available from **Lascar Electronics, Unit 1, Thomasin Road, Basildon, Essex (0268 727383)**. Price £69.80 (transducer extra)

metres, fathoms, inches etc. For the purpose of this design, the first three are used.

Those who know the ICM 7224 will, no doubt, realise that it is a 4 $\frac{1}{2}$  digit counter, but here it is only being used to drive a 3 $\frac{1}{2}$  digit display. This is because there is little point in measuring to an accuracy of 0.01 feet ( $\frac{1}{8}$ th of an inch) when the boat will be moving up and down substantially more than that, due to the movement of the water. A 3 $\frac{1}{2}$  digit display is easier and cheaper to obtain with larger digits for the same glass size.

### "TOO SHALLOW" DETECTOR

As the current consumption is so low, there is no reason why the instrument should not be left on all the time, in which case the shallow water detector IC4c comes into its own. If there are three consecutive readings below a preset level (adjustable by altering resistor VR5 on the p.c.b.) an alarm sounds, so you can sleep in confidence that if the tide goes out, you will be woken up before it is too late! Three consecutive readings are required, as you might get an occasional low reading from a fish or piece of debris near the transducer. The output from IC4a is taken low when the transmitter fires and stays low until the flip-flop is reset by the returning signal. When the output first goes low, C26 discharges at a rate set by VR5. If the main flip-flop is reset before the voltage on C26 is below the CMOS threshold (approximately 4.5V) due to shallow water, then a negative go-

ing pulse on the output of IC4c partially discharges C27. This is normally being charged via R43. However, the circuit is arranged so that three consecutive 'low level' readings discharge C24 to the point where IC5c switches on TR12, activating the alarm. VR5 allows setting of any depth between 2-3 feet and 25 feet.

If the depth sounder is to be used on a boat with an engine, it is imperative that the engine is properly suppressed, otherwise it will produce interference, giving random depth indications.

### POWER SUPPLY

The instrument operates from a 9V supply, from which is derived a 5V supply for the logic circuitry. The 9V supply can be from the internal PP7 battery, or external in the range 12V to 30V. The external input is regulated down to approximately 9V by D16, TR1. D15 and TR2 regulate the 9V input down to 5V. Diode D1 protects against reverse polarity connection of external supply.

The instrument can be powered from either a supply in the range 12V to 30V or an internal 9V battery, but not both at the same time, because the 9V battery may leak corrosive chemicals as a result of having charge pushed into it. If external supply is used, the internal 9V battery should be removed.

**NEXT MONTH: Construction, Testing and Installation**





**FRANK W. HYDE**

## THE NEXT DECADE

The Calendar for the next decade is a very full one. It is hoped that it will begin with the first trials of the Space Shuttle, Columbia. This issue of *Spacewatch* should be in your hands for the date set for the launch, which is the 17th of March 1981.

At the present time of writing Columbia is set up on its launch platform at the Kennedy Space Centre in Florida. The vehicle was powered up from the ground using ground based power. Engineers have since January 5th been making the final inspections and the exhaustive check of the systems.

On January 6th the prime team of astronauts, John Young and Robert Crippen together with the back-up crew practised the escape routines. The back-up team are Joe Engel and Richard Truly. There are complete safeguards for the crew from the moment of count-down. A quick exit is possible during the final hours of count-down if an emergency should arise.

The first orbital flight will last for 54 hours. During this flight the crew will test all the systems including the opening and the closing of the 59 feet long doors which cover the payload bay (where the spacecraft to be launched will be carried) and the space which is provided for other instruments.

The Shuttle with its boosters will be launched vertically and will later re-enter the atmosphere to glide in an un-powered condition to the NASA Dryden Flight Research centre in Edwards, California. If an emergency should arise the crew can also land in Florida or at the White Sands Missile Base near Las Cruces, Mexico.

## PROSPECTS FOR THE NEXT DECADE

August 1981 will see the encounter with Saturn by Voyager 2. Plans are already being finalised for this event. The success or

otherwise is dependent on the state of the vehicle when it arrives in the area of Saturn, before going on to Uranus.

The Soviet Union have a planetary programme which will involve four Venus probes. Venera Nos. 13 and 14 will be launched in November this year with an encounter date in the spring of 1982. Two more Venera craft nos. 15 and 16 will be launched around June or July 1985.

The missions will be "landers" and will very likely be similar to the Viking landers used by NASA on Mars. The two vehicles 13 and 14 will land March/April 1982 to examine the surface of Venus and, no doubt will be making the details of the project available. The 1984 mission will be a joint mission with France. Venera 15 and 16 will carry two balloons and two landers. These balloons at present being developed will carry instruments for the study of the Venusian atmosphere at a height of 56 km over a period of about six days. The landers will be carrying out observations from the surface at the same time. It is not known at present whether the vehicles themselves will orbit or flyby, but one will leave for an encounter with Halley's comet. This will be in 1986. This vehicle will be equipped with a specially developed camera supplied by the French.

The European Space Agency is preparing the Exosat which will be an additional satellite to cover the X-ray spectrum. At the moment this is the province of the Einstein satellite of NASA. An additional booster will be added to the Ariane launcher in order to get the required power to lift the Exosat to its eccentric orbit, taking it some 200,000km above the North Pole. The vehicle is equipped to study the position, structure and spectra of the sources emitting X-rays in the energy range up to 1.5keV. This satellite will operate as an observatory so that the groups of observers can share the time. The date set for the launch is November 1981.

A joint European/United States venture for the launching of an astronomical Satellite in August 1982 will go ahead, but at a higher cost due to certain technical problems. Its task is to study the infra-red wavelengths, which cannot be done satisfactorily from ground based telescopes, because of the carbon dioxide and water in the Earth's atmosphere. This satellite is the IRAS.

Another joint NASA/ESA venture will be the Space Telescope. This is due to be launched by the Space Shuttle in December 1983. The exact date of launch will of course depend on the progress and time table of the Shuttle programme. The telescope will have a primary mirror of 2.4m diameter, and will carry a number of instruments for the task to be undertaken. The benefit of this telescope will be that it will be some 500km above the atmosphere and will in consequence produce results of the order of 10 times greater than the largest of the earth based instruments.

In 1984, during March, the Galileo probe is due to be launched. This vehicle has also had a number of difficulties due to the financial troubles that have beset NASA. The plan is to send a probe deep into the atmosphere of Jupiter and an orbiter to go round the planet.

The orbiter would be sent ahead of the probe and will circle the planet for 20 months make close observations of the conditions of the atmosphere. The probe will study the atmosphere down to a level where the pressure is more than 10 times that of the Earth. Both vehicles will encounter the planet in July 1987.

Still another joint mission is the International Solar Polar Mission. The object of this mission is to explore that part of the solar system away from the ecliptic. It will be the first time that any spacecraft explore that part of the solar system about which we know nothing. The orbit will be over the poles of the Sun. Two spacecraft will be despatched toward Jupiter and "flicked" round in the planet's gravitational field toward the Sun. They will be launched in such a way that they pass over each of the solar poles, that is, they will travel in opposite directions.

Their task is to study the high energy particles of the solar wind and study the solar magnetic field. This is a most important mission to which the European space agency has already allocated £30 million.

In 1986 the Venus Orbiting Imaging Radar mission will be launched from the Space Shuttle. The object, as its name implies, will be to obtain radar pictures of the surface of Venus. The system of imaging that has been successfully developed will enable distances down to 150m to be resolved through the thick cloud cover. This vehicle will be despatched in May or August depending on which trajectory is chosen. It will arrive at Venus in December of the same year.

Another special mission is that of Giotto. This is to be launched by an Ariane vehicle in July 1985 on a trajectory to intercept Halley's comet in March 1986. Attempts will be made to obtain imaging of the nucleus and measure the gas and dust of the coma. There is a great deal at stake in this mission, for an accurate knowledge of the composition of comets is very necessary to qualify present theories of cosmology.

The United States will carry out a plan to extend Gamma-Ray astronomy. The observatory will be launched in August 1985. The Shuttle will also be the vehicle for this mission. The observatory will examine, from an orbit 400-500km above the Earth, the very short wavelengths below  $10^{-13}$ m. It is hoped that these observations will help to provide clues as to the nature of Pulsars, Quasars and Supernova.

To make a new map of the sky a special satellite, Hipparcos, is to be launched in 1986/1987. This was put back in favour of Giotto to ensure that at least one spacecraft was able to rendezvous with Halley's comet. Hipparcos' mission is an extremely important one for the same reasons that Giotto was important: further accurate knowledge of the universe.

Hipparcos will measure the positions and motions of 100,000 stars with an accuracy that is not possible from Earth. The measurements will also provide better evidence of the quasars and sources near the edge of the observable universe.

# SPECIAL NEXT MONTH...

## THIS FREE CASE

*Cover mounted on every issue*

# WORTH OVER £2

ACTUAL  
SIZE

**ALSO... The first two projects designed to fit the case**




**Precision Digital Multimeter;** five functions; four ranges per function; diode check; fully protected;  $\pm 0.5\%$  basic accuracy (d.c. volts). No calibration required.



**Precision Digital Thermometer;**  $-55^{\circ}\text{C}$  to  $+150^{\circ}\text{C}$ ; stainless steel probe; laser trimmed i.c. sensor giving excellent linearity and easy calibration.

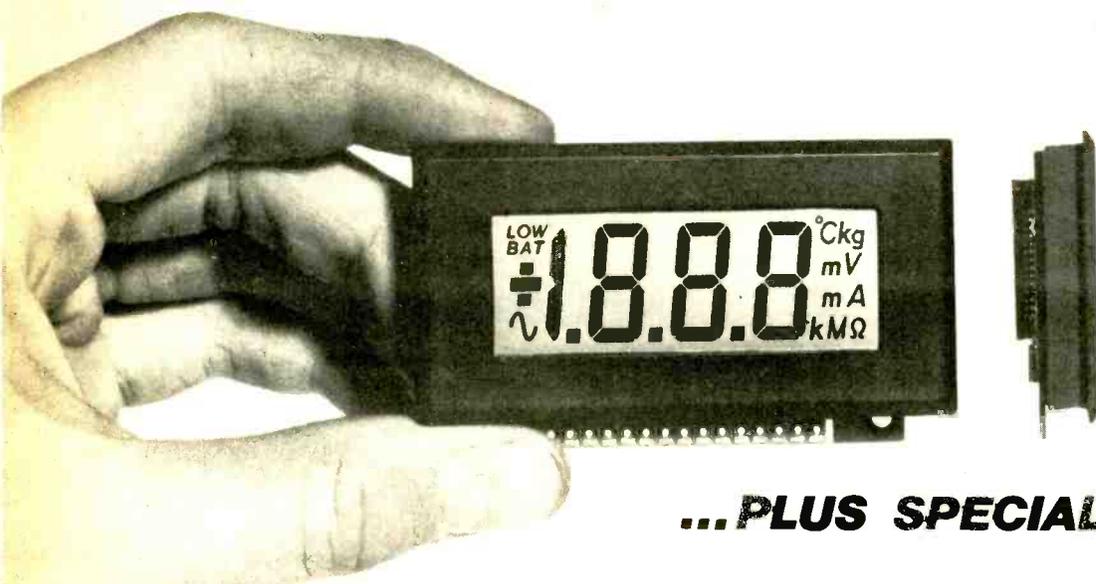*... These will be followed in the June and July issues by at least 6 more projects designed to fit in the case*



## ...PLUS SPECIAL DPM OFFER

**T**O match the free case we will also have a special offer on this brand new i.c.d. digital panel meter. The meter employs watch manufacturing techniques to reduce the depth to a minimum. The current drain has been reduced to only 200 $\mu$ A which means a PP3 battery can power the display for typically two years if used 8 hours a day.

Other features include 15mm digits, digital hold facility, auto-zero, auto-polarity, single rail 5–15V supply, programmable decimal points and 200mV full scale deflection.

The meter will fit neatly into our free case and all our projects will use it. An exclusive special offer price has been arranged for PE readers—full details next month.

## EXTRA CASES...

We will be presenting "PE Case Vouchers" in subsequent issues so that regular UK readers can obtain extra cases for a fraction of the normal cost. With at least eight different projects we think you will want another case!

*Make Sure of Your Copy Now!*

We do not want our regular readers to miss out due to the heavy demand this issue is bound to attract, so please order a copy from your newsagent NOW!

PRACTICAL  
**ELECTRONICS**

MAY ISSUE ON SALE FRIDAY 10 APRIL 1981

# Simple Speech Processor



Michael Tooley B.A.  
David Whitfield B.A.M.Sc.

A SPEECH processor is essentially a device which improves the intelligibility of a voice signal. This is particularly important where the wanted signal is contaminated by noise or where the signal varies over a wide range. Several different types of processor are possible and these vary considerably in complexity and effectiveness.

The unit to be described not only provides an increase in signal level but also reduces the dynamic range of the signal. It is therefore eminently suited to applications where a consistently high level of output is required from a signal which varies in amplitude. The unit employs an active limiter and therefore avoids some of the time constant problems associated with dynamic speech compressors. Active filter techniques further enhance the output signal by reducing noise and harmonic distortion.

The circuit uses only one integrated circuit, a FET input quad operational amplifier, and may be readily inserted in the signal path of such equipment as public address amplifiers, tape recorders, transmitters and transceivers.

## CHARACTERISTICS OF SPEECH

Very large variations in instantaneous signal are present in speech waveforms. This can often be an important consideration in the design of equipment for use with voice signals including public address amplifiers, transceivers etc. The 'peak factor' is defined as the ratio of peak to RMS sound pressure over a specified bandwidth. For unfiltered speech the peak values exceed the RMS values by typically some 10dB or more over a time which is equivalent to the length of an average syllable. Over a longer period of time, however, this value is greatly increased and the peak factor is typically some 20dB. Thus, if a public address amplifier is producing, for example, an average power of 1W from a given source it must be capable of a peak power of around 100W if the signal is to be reproduced faithfully.

In many applications, however, the important consideration is intelligibility rather than accuracy of reproduction. Here we are concerned not with the absolute signal power but more with the ratio of signal to noise power. This can be increased by either reducing the transmission channel bandwidth or by raising the average level of the signal whilst the noise in the transmission medium or recording system remains constant. The latter technique has the effect of

## SPECIFICATIONS

**Maximum limiting** 3dB change in output for 20dB change in input

**Input signal range** 2mV to 2V peak-peak

**Output signal range** 20mV to 6V peak-peak

**Minimum input signal for onset of limiting** 6mV peak-peak

**Input impedance** 10k typical

**Output impedance** 150R typical

Supply 6 to 9V at 12 to 20mA

reducing the dynamic range of the signal or, to put it in simple terms, making the quieter sounds louder whilst the louder sounds stay loud!

A further consideration is that, for a given system, there is often a maximum signal level that should not be exceeded. This is important in, for example, such applications as broadcast transmitters where overmodulation of the carrier results in a signal having an excessive bandwidth.

## SPEECH PROCESSING TECHNIQUES

The two principal methods for restricting the dynamic range of a signal are amplitude limiting or clipping and dynamic compression. The former method has the advantage that it is simple and fast to act, but has the disadvantage that harmonic distortion is introduced by the limiting action. Dynamic compressors are relatively distortion free but are somewhat more complex. They also have considerable drawbacks associated with attack and decay time constants of the AGC system employed; the compressor may not operate quickly enough to respond to a rapid transient and, furthermore, may be slow to recover once the compression action has been started. Fig. 1a shows the general block schematic of an amplitude limiter whilst, for comparison, Fig. 1b shows the arrangement of a dynamic compressor.

The circuit described in this article uses an active limiting arrangement. As with all limiters some distortion is inevitable. This is primarily due to the generation of harmonics caused by the non-linearity of the transfer characteristic. Harmonics of the lower frequency components (say below 1kHz) of the input signal are more significant because they

fall within the frequency range of the speech signal. At middle and high frequencies (say above 2kHz) the harmonics generated fall outside the speech signal frequency range and can be attenuated by means of a suitably designed filter.

The transfer characteristics for various degrees of amplitude limiting are shown in Fig. 2. 'Hard-limiting' occurs very abruptly, there being no perceptible increase in the output signal amplitude beyond a certain input level. 'Soft-limiting', as its name implies, is somewhat more gentle and the slope of the transfer characteristic is made to fall progressively as the input signal amplitude increases above

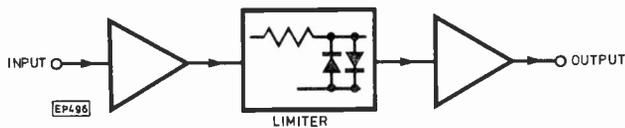


Fig. 1a Amplitude limiter block schematic

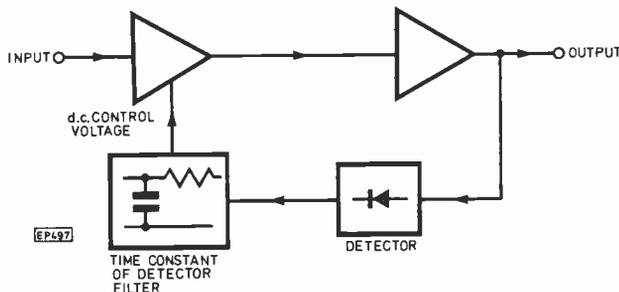


Fig. 1b Dynamic compressor block

a certain threshold level. 'Soft-limiting' offers some advantages over 'hard-limiting' as regards the generation of unwanted harmonics of the input signal. These are considerably reduced with the result that the output signal is less harsh and consequently more pleasant to listen to. Also, due to the reduction in harmonic content, less stringent requirements are imposed on the subsequent filter stage. Typical signal waveforms obtained with 'hard' and 'soft-limiting' are shown in Fig. 3.

The degree of limiting employed depends largely upon the particular application. A change in output of, say, 3dB for a change in input of 20dB may be eminently suitable for voice communications over a noisy radio channel, however, for public address and tape recording of speech signals a somewhat less severe 6dB change in output for a 12dB change in input will be more suitable. An essential requirement, therefore, of a general purpose speech processor employing amplitude limiting techniques is that the degree of limiting should be adjustable over a wide range. In practice, and since the input signal level may vary from one source to another, this means that the signal level both preceding and following the limiter stage must be made variable. By careful adjustment a wide range of limiting can be achieved and a variety of input and output signal levels can be catered for.

The block schematic of the speech processor is shown in Fig. 4. The first stage is an amplifier with a voltage gain which is adjustable from approximately 1 to 100. The limiter stage which follows has a fixed voltage gain of 2 for small signals and this falls dramatically as the signal level increases. The active low pass filter has an upper cut-off frequency of approximately 4kHz and significantly reduces the harmonic content of the output signal from the limiter. The final stage is another amplifier, the gain of which may be adjusted over the range of 0.05 to 4.5.

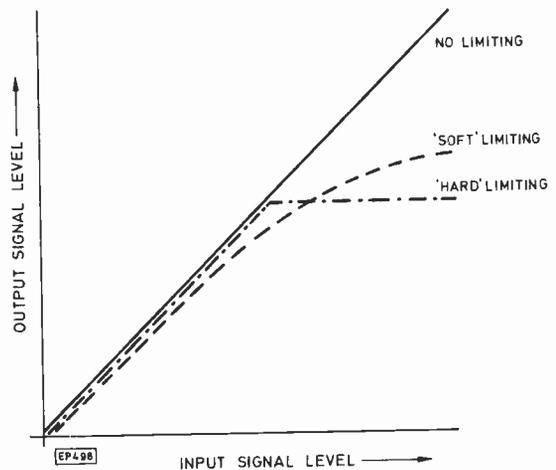


Fig. 2 Transfer characteristics for various degrees of amplitude limiting

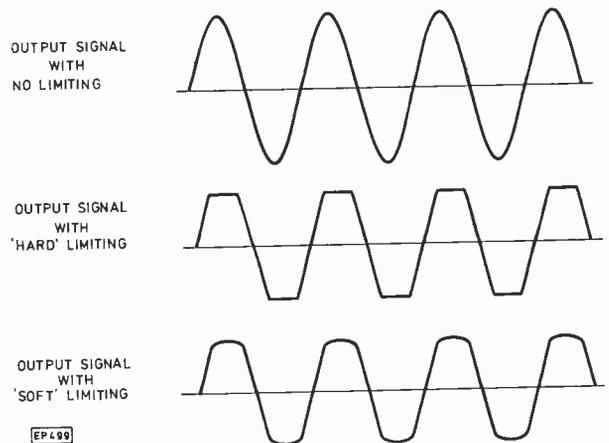


Fig. 3 Effect upon signal waveforms of the limiting characteristics depicted in Fig. 2


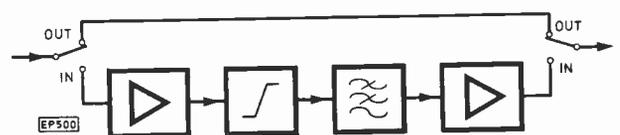


Fig. 4 Block schematic of the Speech Processor

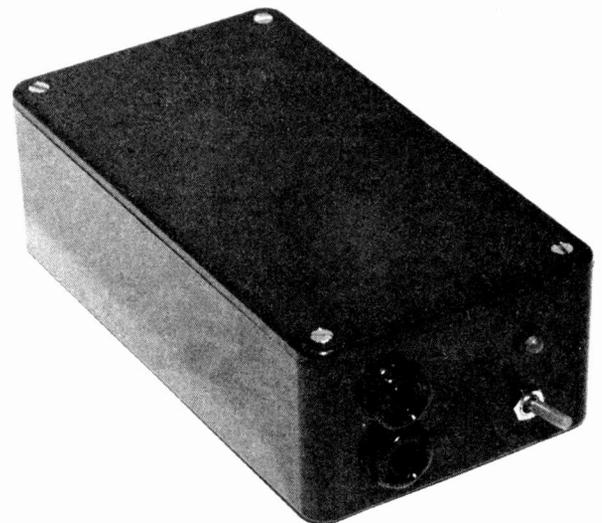

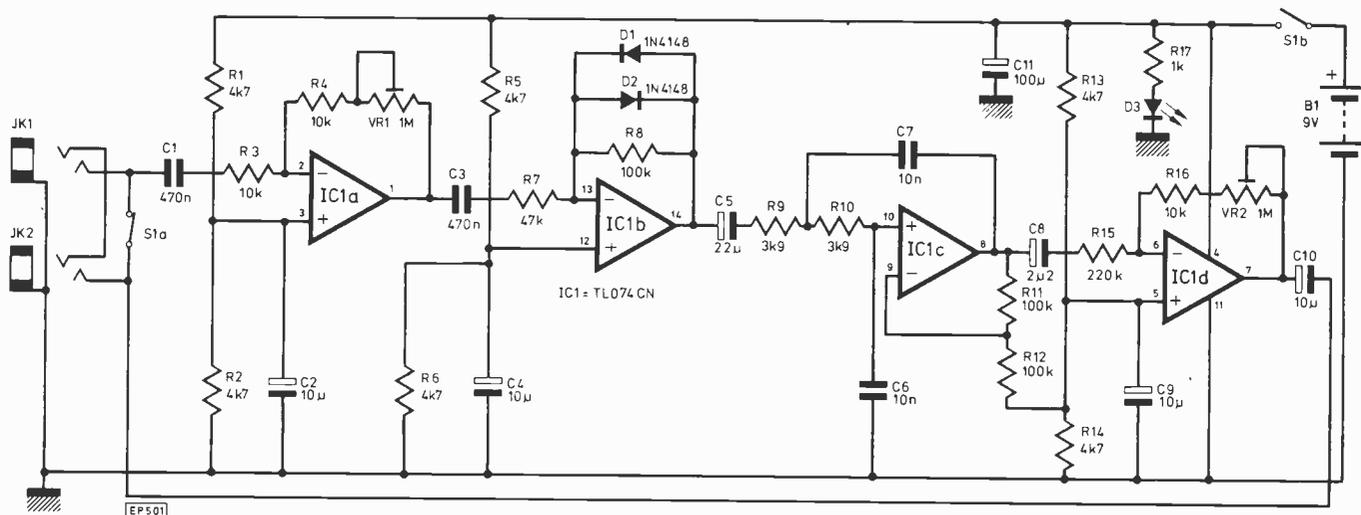


Fig. 5 Circuit of Speech Processor

Resistors		COMPONENTS.		Capacitors	
R1	4k7	<b>Potentiometers</b> VR1 1M miniature horizontal preset VR2 1M miniature horizontal preset	<b>Semiconductors</b> IC1 TL074CN D1 1N4148 D2 1N4148 D3 l.e.d.	C1	470n polyester
R2	4k7			C2	10µ 16V tantalum
R3	10k			C3	470n polyester
R4	10k			C4	10µ 16V tantalum
R5	4k7			C5	22µ 25V tubular
R6	4k7			C6	10n polyester
R7	47k			C7	10n polyester
R8	100k			C8	2µ2 35V tantalum
R9	3k9			C9	10µ 16V tantalum
R10	3k9			C10	10µ 16V tantalum
R11	100k			C11	100µ 16V p.s. mounting tubular
R12	100k				
R13	4k7				
R14	4k7				
R15	220k				
R16	10k				
R17	1k				
All fixed resistors ¼W 5% carbon					

**Miscellaneous**  
 Printed circuit board plastic case measuring approx. 150 x 80 x 50 mm DPDT miniature toggle switch, sockets (2 off) 3-pole jack or similar, battery connector—snap fit to PP3 battery, low profile 14-pin DIL socket

Components and p.c.b. available from **Howard Associates, 59, Otlands Avenue, Weybridge, Surrey.**

**CIRCUIT DESCRIPTION**

IC1a operates as a conventional inverting voltage amplifier, the gain of which is controlled by the negative feedback resistor, VR1. The voltage at the non-inverting input is set by means of R1 and R2 at approximately half the supply voltage with C2 providing decoupling at signal frequencies. A similar arrangement is used for setting the non-inverting input on each subsequent stage. The active limiter is formed by IC1b, D1, D2 and associated components. Since D1 and D2 are silicon devices, a peak-peak voltage of approximately 1.2V at pin 14 of IC1 will cause D1 and D2 to conduct on alternate half-cycles and this will, in turn, provide a low impedance shunt path across the feedback component, R8.

IC1c and associated entry circuit forms a low-pass Sallen and Key filter. This is a simple, yet effective, second order filter, and cut-off frequency being determined by R9, R10 and C6, C7. The ratio of R9 to R10 and C6 to C7 being kept constant to provide fixed filter characteristics. The final stage, IC1d, is an inverting voltage amplifier, similar in configuration to IC1a. VR2 and R16 set the voltage gain of this stage, the values being chosen so that the stage can provide attenuation as well as amplification. S1a provides a direct signal path between input and output when S1b is in the 'off' position. A conventional LED and current limiting

resistor is used to provide visual indication that the processor is in use.

**CONSTRUCTION**

The speech processor is built on a single sided p.c.b., the copper foil layout of which is shown in Fig. 6. The components are arranged on the top side of the p.c.b., as shown in Fig. 7.

It is recommended that IC1 be mounted in a low-profile 14-pin DIL socket and that, as far as possible only miniature components are used. The completed p.c.b. should be carefully checked and then mounted in a small plastic case using stand-off pillars. The layout of the input and output sockets, on/off switch and l.e.d. being entirely a matter for the individual constructor's preference. The connections to the p.c.b. together with associated wiring are shown in Fig. 8.

**INITIAL TESTS AND ADJUSTMENTS**

Connect a suitable battery (PP3, PP6 or similar) and check the supply current. This should be in the region of 12 to 20 mA. Set VR1 and VR2 to mid-position and connect a microphone to SK1. The output signal should then be checked using an amplifier or tape recorder connected to

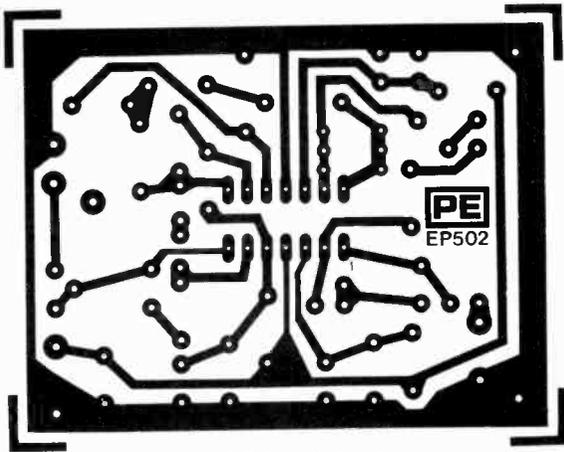


Fig. 6 Printed circuit

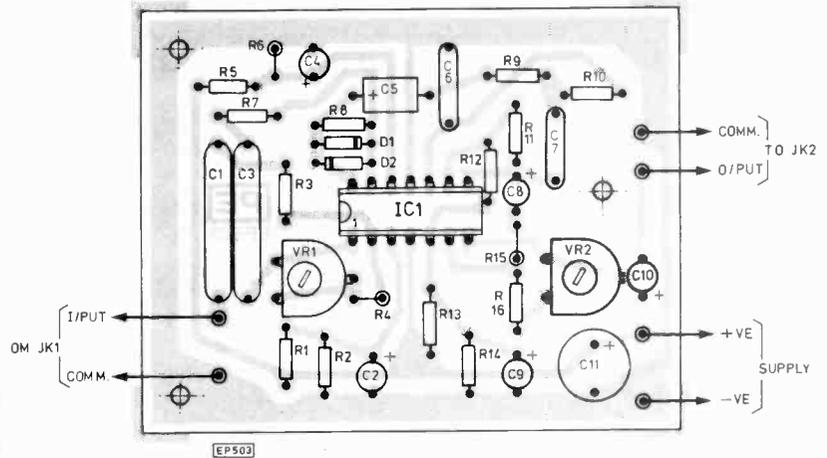


Fig. 7 Component layout

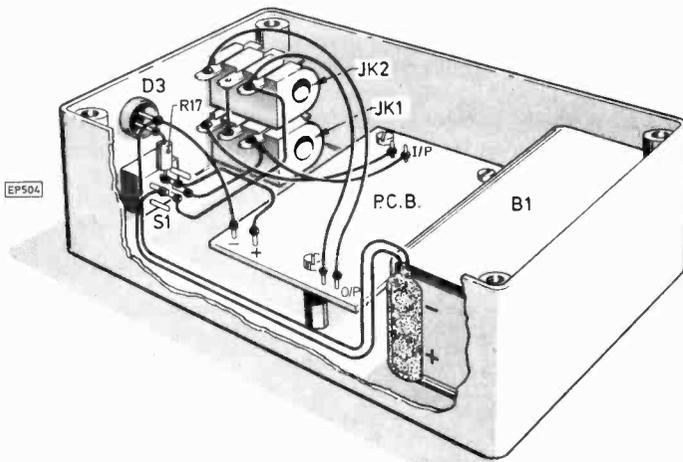


Fig. 8 Interior layout and wiring

SK2. The effect of varying the settings of VR1 and VR2 should be noted. If VR1 and VR2 fail to have any effect, or if the output signal is not obtained, the p.c.b. should again be carefully checked and, if this does not reveal any errors, d.c. voltages should be measured and reference made to the table of test voltages.

When experimenting initially with the speech processor it is recommended that VR1 and VR2 be set almost fully clockwise. This will produce similar input and output levels when using a low impedance dynamic microphone and limiting should occur when 'close-talking' into the microphone. Where an appreciable amount of gain is required, as would be the case when speaking at some distance from the microphone, the settings of both VR1 and

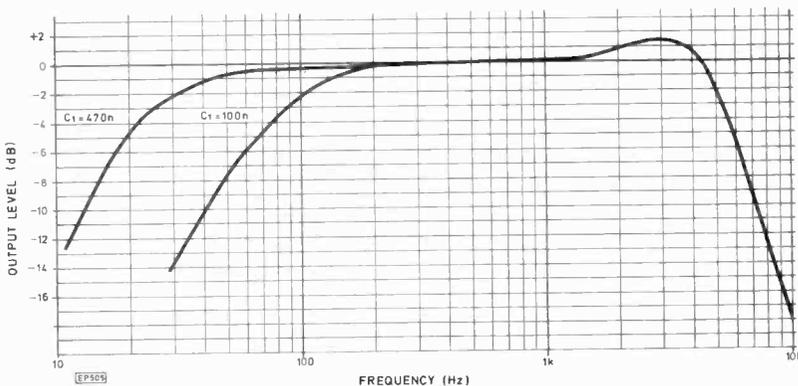


Fig. 9 Frequency response of the Speech Processor with  $C_1 = 470n$  and 'rolled-off' at LF below 200Hz with  $C_1 = 100n$

VR2 may be increased to around mid-position.

Note that this may have the undesirable side-effect of amplifying unwanted extraneous noises to such a level that their presence is annoying. The settings of VR1 and VR2 are best determined by experiment in conjunction with the actual microphone or signal source which is to be used. It is then a fairly easy matter to determine the optimum settings for any particular application.

## APPLICATIONS

### Radio transmitters/transceivers

The addition of a speech processor will enhance the performance of most transmitters and transceivers. The extra "talk-power" often making the difference between a signal which is readable and one which is lost in noise. Air tests under marginal conditions show an effective 3 to 4dB increase over a signal without speech processing. The device is suitable for use with most types of transmitter and transceiver and, being merely inserted in the microphone connection, requires no internal modifications whatsoever. The processor may be switched in and out as required; a direct path from microphone to transceiver being provided in the latter case. Since processed speech tends to be somewhat less pleasant to the ear this facility is useful for restoring normal operation for local contacts; the speech processor being primarily intended for chasing DX! When used with mobile equipment the speech processor will allow


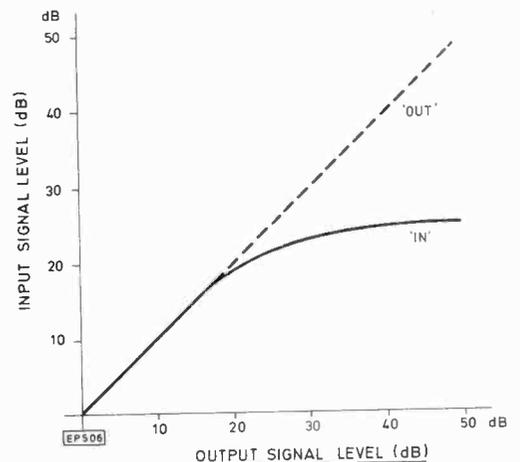


Fig. 10 Transfer characteristic

### Test voltages

IC1 pin	1 4.5V	8 4.5V
	2 4.5V	9 4.5V
	3 4.5V	10 4.5V
	4 9.0V	11 0V
	5 4.5V	12 4.5V
	6 4.5V	13 4.5V
	7 4.5V	14 4.5V

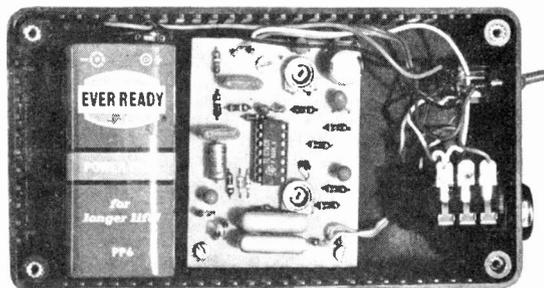All the above voltages were measured with a 10mΩ input d.c. voltmeter. The d.c. supply was 9V.



the operator to talk at some distance from the microphone thus permitting the use of a gooseneck or tie-clip microphone. This is much safer in use than the usual hand-held microphone!

### Public address

The speech processor is particularly useful as a means of compensating for the variation in signal level which is often experienced when a fixed microphone (on either a floor or table stand) is employed. The processor then allows the speaker to vary his position relative to the microphone without appreciable loss of amplification.

### Tape recording

The speech processor may be used to replace the AGC system used on some cassette tape recorders when recording speech. There is no annoying 'recovery time' and the processor is useful in clarifying signals contaminated by noise as would be the case when recording from short wave receivers. The unit is also suitable for dictation, freeing the user from the need to hold the microphone and allowing him or her to talk at some distance from the recording machine.

And finally, although the processor is not generally suitable for music (the distortion introduced being quite noticeable) it may prove to be of some interest to those who wish to experiment with musical effects. The speech processor makes a very effective "fuzz-box" with VR1 and VR2 suitably adjusted!

## Countdown

- BEX** March 25-26. Metropole, Brighton. **K**  
**The Northern Electronic Test & Measurement Exhibition** March 31-April 2. Wythenshawe Forum, Manchester. **T**  
**Laboratory** April 1-2. Glasgow. **I**  
**BEX** April 8-9. Centre Hotel, Liverpool. **K**  
**Laboratory** April 8-9. Manchester. **I**  
**London Computer Fair** April 14-16. North London Polytechnic **B5**  
**All Electronics Show** April 22-24. Grosvenor House, Park Lane, London. **F1**  
**Computer Graphics** April 28-30. The Barbican Centre, London. **O**  
**BEX** April 29-30. Dragonara Hotel, Leeds. **K**  
**Entertainment** May 9-17 (weekday mornings trade only). NEC, Birmingham. **B2**  
**The European Consumer Electronics Show** May 10-13. Nuremberg, West Germany. **I**  
**BEX Train** May 11-22. Calling at: Cambridge, Norwich, Leicester, Sheffield, Newcastle, Middlesbrough, Hull, Nottingham, Reading and Portsmouth. **K**  
**Defence Components Expo** May 12-14. Brighton Metropole. **I**  
**East Suffolk Wireless Revival** May 24. Sports ground of Ipswich Civil Service Sports Association, Straight Road, Ipswich. **VI**  
**Scotalex** June 2-4, Royal Highland Exhibition Hall, Ingleston, Edinburgh. **A1**  
**Semlab** June 2-5, Grand Hall, Olympia, London. The international scientific educational, medical and industrial laboratory equipment exhibition. (Trade). **I**  
**Transducer Tempcon** June 9-11. Wembley Conf. Centre, London. **T**  
**Components** (Electronics Components Industry Fair) June 9-12. Earls Court, London. **I**  
**International Word Processing Exhibition & Conf.** June 23-26. Wembley Conf. Centre, London. **Z**  
**BEX**—Portsmouth June 24-25. Centre Hotel. **K**

- Solar Energy Exhibition** Aug. 23-28, 1981. Brighton. **M**  
**Laboratory** Sept 8-10. Grosvenor House, Park Lane, London. **I**  
**International Business Show** Oct. 20-29. NEC, Birmingham. **A2**  
**BEX**—Southampton Nov. 4-5. Polygon Hotel. **K**  
**Electronics 82** (Sub-titled International Electronics Control and Instruments Exhibition) May 24-28, 1982. NEC. **I**

- I** Industrial Trade Fairs. ☎ 021-705 6707  
**K** Douglas Temple Studios, 1046 Old Christchurch Road, Bournemouth  
**M** Montbuild. ☎ 01-486 1951  
**O** Online Conference. ☎ 0895 39262  
**T** Trident International Exhibitions. ☎ 0822 4671  
**A1** Institute of Electronics. ☎ 0706 43661  
**VI** Jack Tootill, Ipswich. ☎ 0473 44047  
**A2** Hart Browne & Curtis Ltd., 29 Sackville Street, Piccadilly, London W1X 1DR. ☎ 01-439 8556  
**B2** Brintex Exhibitions Ltd., 178-202 Great Portland Street, London W1N 6NH. ☎ 01-637 2400  
**B5** Dept. Electronic & Communication Eng., Polytechnic of N. London.

## POINTS ARISING

### 27/28MHz CONVERTER (March '81)

The following coil winding details were omitted from Fig. 6:

L1 3 turns 26 s.w.g. wound over L2.

L2 15 turns 30 s.w.g. close wound.

L3 & L4 12 turns 30 s.w.g. close wound.

L5 18 turns 30 s.w.g. close wound.

In Fig. 5, D5 Anode should be connected to C21 which is non elect.

**MICROBUS** (Feb '81)

There was an error in one of the ZX80 programs. See *Readout* on page 64.

# VIDEOTONE

**BUY DIRECT FROM US AND  
GET THE SAME HIGH  
QUALITY AT LOW PRICES!**




DISCOUNT  
SELLING PRICE  
**£50.00**

## LOUDSPEAKERS

The complete fully reviewed range of Videotone Speakers which dominate within their class. NOW AT LOWEST EVER PRICES.

D100	£38.00
Minimax 11	£44.00
GB3	£50.00
GB2	£60.00
GBS	£207.00
D 93	£40.00

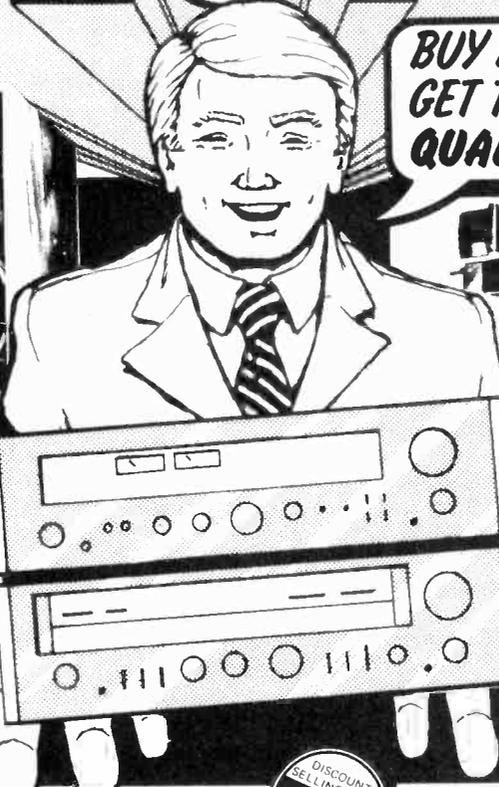

## CORAL CARTRIDGES

Fast becoming one of the top names

<b>MOVING COIL</b>	<b>MOVING MAGNET</b>
UK's No. 1 Cartridge	
MC 81 £48.87	555SX £7.28
777EX £35.00	555E £14.22
777E £25.00	666E £32.48
<b>HEAD AMP</b>	<b>HEADSHELLS</b>
H300 £51.75	S100 £6.00
T100 £24.75	S101 £7.00
	S200 £4.00

## TURNTABLES

Sansui SR222 Mk2	£69.00
Sansui P50S	£69.00

## AMPS-TUNER-CASSETTE

30 watt amp MC input SA4 130	£75.00
Stereo Tuner ST 4120	£68.00
Cassette full features SC 4200	£95.00
50 watt amplifier WA7700	£77.00
20 watt amplifier LA2020	£58.00

This new range of Electronics from Videotone redefines the words quality and value for money to a new high.



DISCOUNT  
SELLING PRICE  
**£68.00**

DISCOUNT  
SELLING PRICE  
**£75.00**

### \* A MESSAGE FROM VIDEOTONE \*

Dear Customer  
You will find that the products advertised on this page are the best possible value for money. They are only low in price because we have eliminated large amounts of selling costs that other brands have to suffer. These savings are passed directly onto you. We have full brochures on any specific item you may be interested in and a competent realistic staff of engineers at our London Showrooms to help you in your choice. Our consumer protection packages are comprehensive and we offer every form of financing you may require. We carry out our own servicing and are dedicated to giving Value for Money. We are confident our products are unbeatable. You may purchase with confidence because our Engineers have specially selected them from competitive sources throughout the world and we import them directly ourselves. Remember, you have 21 days trial period on all products. That is the measure of our confidence.

*Cliff Hardcastle*  
Cliff Hardcastle, Managing Director.

## MICROPHONES

MU 105-22	£29.30
MU 105-12	£22.25
MU 25 C	£17.39



## HEADPHONES

Superbly made with top flight performance

HP90	£12.65
HP80	£9.69



Quality plus value ~ always

# VIDEOTONE

ALL  
PRICES  
INCLUDE  
VAT

ALL PRODUCTS  
ON DISPLAY &  
CONTINUOUS  
DEMONSTRATIONS

98 CROFTON  
PARK ROAD  
LONDON SE4  
TEL: 01-690 8511/2

SEND FOR OUR LATEST  
FREE BROCHURE  
AND DETAIL LIST OF LOCAL  
SALES OUTLETS IN THE U.K.

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
\_\_\_\_\_



PE

## ***P.s.u. and controller design for mini-drills employing p.w.m. to vary the speed***


**N**EARLY everyone who regularly produces printed circuit boards at home will own a miniature drill of some sort. These drills normally require a power supply of 14 volts, capable of giving 2–3 amps. The supply will allow the drill to give a better performance if it is regulated, since the 14 volts will be maintained when the drill is under load. Also, if the drill is to be used for other purposes than drilling (which should always be done at the fastest possible speed) a variable speed power supply/controller is desirable. The most notable time when a slower speed is required is when using a burr bit to scratch out a p.c.b. track, at full speed the burr tends to skid or bite making the job very difficult. The design presented here is for a suitable power supply and controller, employing pulse width modulation to give the variable speed capability.

### **PULSE WIDTH MODULATION**

The easiest way to control the speed of a small d.c. motor (as are most drills) is to vary the power supply voltage. However, the torque developed by the motor falls off very quickly as the supply is reduced, making the slower speeds useless. This problem can be overcome by using a square wave drive with variable 'on' and 'off' time. (Fig. 1). When the 'on' time is a small percentage of the 'off' time the motor will obviously run more slowly since less energy is supplied, but since the motor is pulsed by a full power surge the torque remains fairly high. Obviously the speed is increased by increasing 'on' time. It is usual to keep the frequency of the system constant and vary the width of the 'on' pulse, hence the name of pulse width modulation.

### **THE CIRCUIT**

The circuit is shown in Fig. 2. The power supply is fairly conventional, except that a great deal of decoupling is employed. This should not be omitted because the drill generates a lot of spikes which will cause faulty operation of the timing circuit. It is important that all the power supply components are rated to sufficient current.

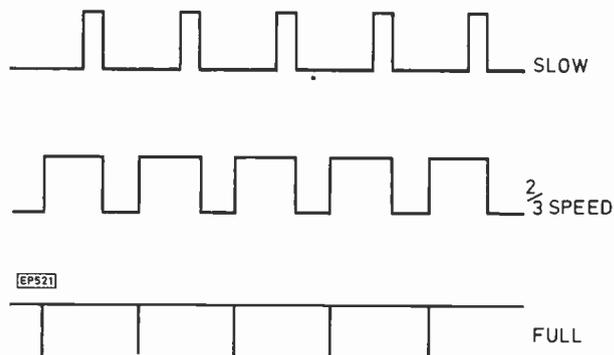

**Fig. 1. Pulse width speed control**

A 20 volt transformer was used in the prototype to give plenty of spare capacity. The output from this transformer is fed to C2 via a 6 amp bridge. Transistor TR1 and R1, D1 form a simple series regulator for the timing circuit. The voltage generated by this supply also determines the final output voltage and thus should be chosen to suit the drill concerned. A 15 volt Zener was used in the prototype, when reduced by three base/emitter drops the resultant 13.2 volt final drive is ideal for a 14 volt drill.


The timing is generated by two 555 timers in a double package (556). The first timer is connected as an astable, of 60Hz frequency. However, the output from this is in the form of a short pulse, this being ensured by making R2 much greater than R3. The pulse output is used to trigger the second 555, which is connected in monostable mode. C8 and R4 act as a pulse differentiator which increases the noise immunity of the circuit.

The monostable period can be varied by VR2, between short and long periods. Since the maximum period required is just less than the frequency of the first 555 VR3 is included to allow this period to be accurately set; similarly VR1 sets the shortest time available—or the slowest speed. A footswitch facility is provided by using the reset of the monostable; this simply inhibits its operation.

The output from the monostable is fed to a Darlington pair, of which the 2N3055 should be mounted on a heatsink. The output from the 2N3055 is fed directly to the drill, although considerable decoupling in the form of C11, C12 and R10 should be added.

# mini drill P.S.U.

**CHRIS LARE**

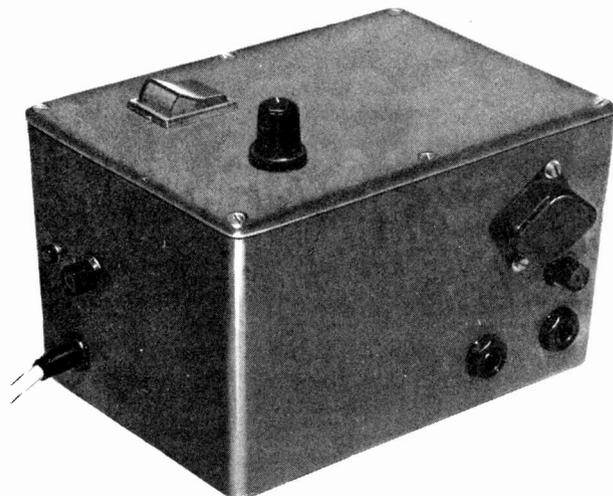

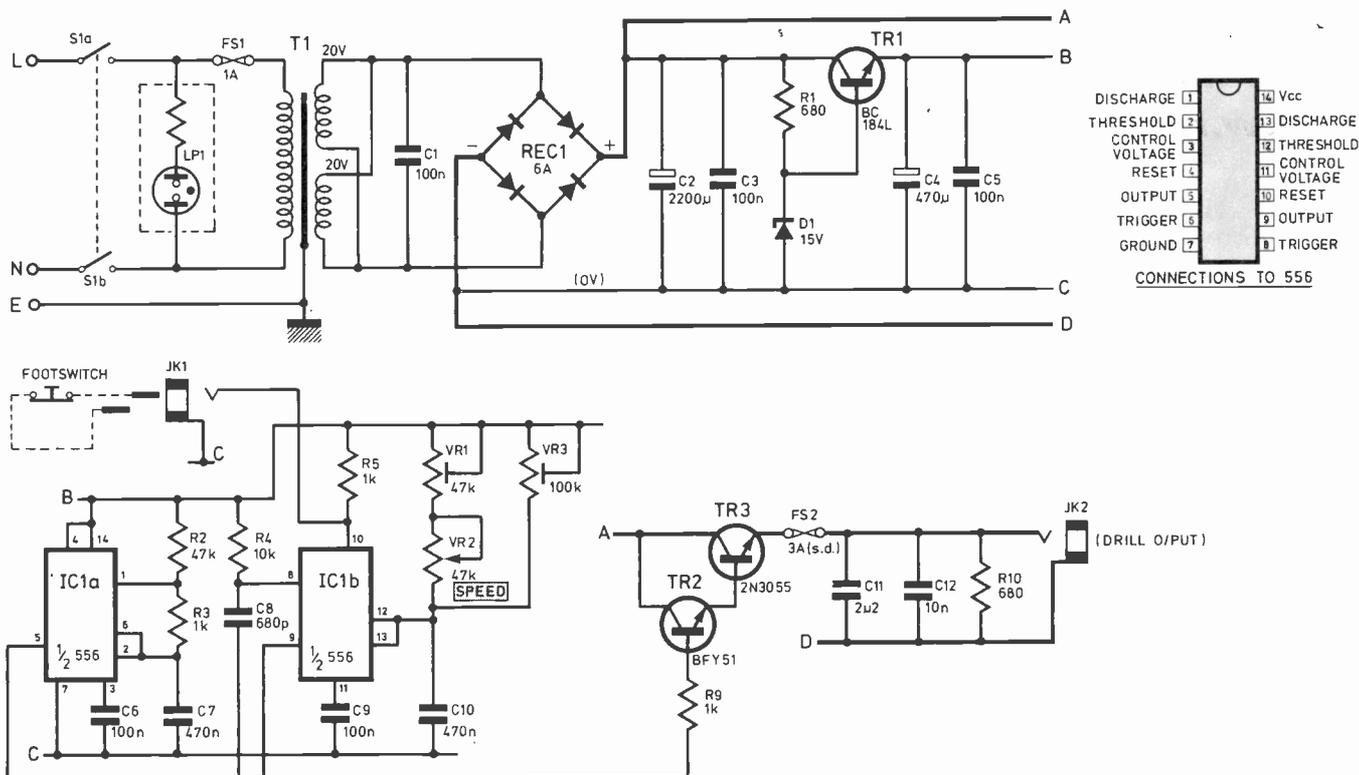


Fig. 2. Circuit diagram

### Resistors

R1, 10	680R
R2	47k
R3, 5, 9	1k
R4	10k
VR1	47k miniature preset
VR2	47k potentiometer
VR3	100k miniature preset

### Capacitors

C1, 3, 5, 6, 9, 12	0.1µ Mullard C280
C2	2200µ 63 Volt electrolytic
C4	470µ 25 Volt electrolytic
C7, 10	0.47µ Mullard C280
C8	680p polystyrene
C11	2.2µ Mullard C280
C12	0.01 disc ceramic 750V

## COMPONENTS ...

### Semiconductors

D1	15V 400mW Zener
TR1	BC184L
TR2	BFY51
TR3	2N3055
IC1	555

### Miscellaneous

REC1-6A bridge; T1-20V transformer 2.4A; double pole single throw illuminated switch; 1A fuse & holder; 3A fuse & holder (optional); 2 mono jack sockets; plugs; die cast aluminium box; p.c.b.; footswitch (Watford PB12); insulation kit for 2N3055; cover for 2N3055; nuts, bolts etc.; sticky feet; mains supply neon (optional).

## CONSTRUCTION

The physical construction is not critical, but the wiring diagram should be closely adhered to so as to avoid noise problems.

The prototype circuit was built on a printed circuit board, produced with an etch-resist pen. Veroboard is not recommended due to the possible noise problems. The circuit board, together with the other parts was housed on a large die-cast aluminium box, chosen for its good heatsink properties. The 2N3055 transistor was mounted on the box part and fitted with a cover to prevent accidents with wandering screwdrivers. A double pole illuminated switch for the mains supply and the speed control were mounted on the lid of the box.

Standard quarter inch jack sockets were used to connect the drill and footswitch. Note that the footswitch should have closed contacts when released. Most footswitches are connected the other way round, but the one used in the prototype had a standard changeover micro switch inside,

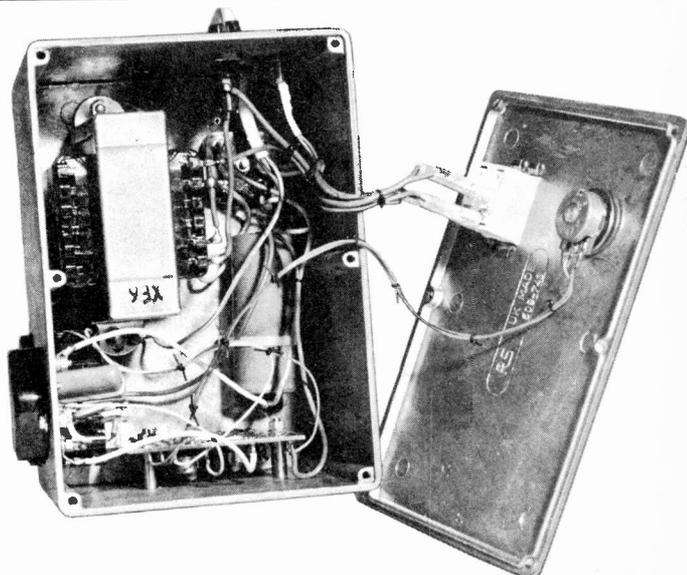


Fig. 3. P.c.b. and assembly details

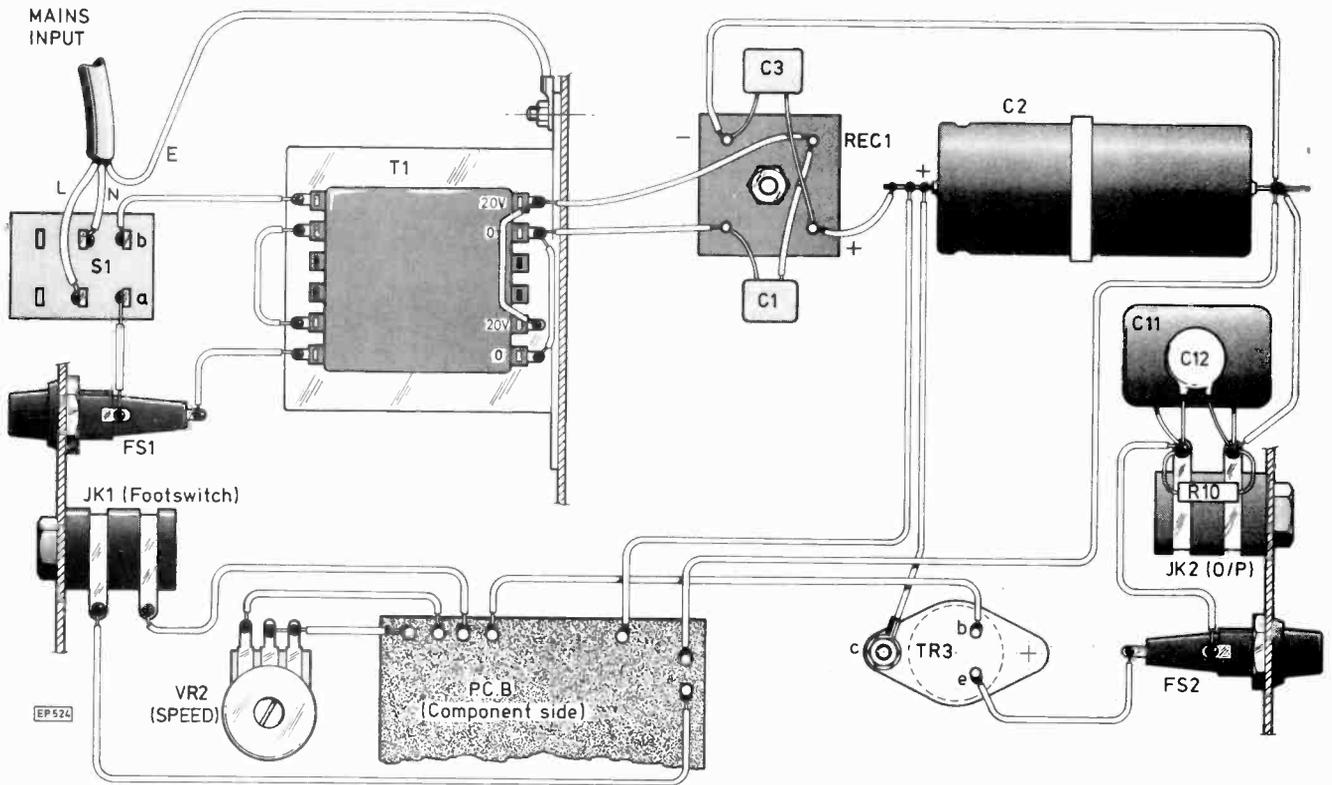
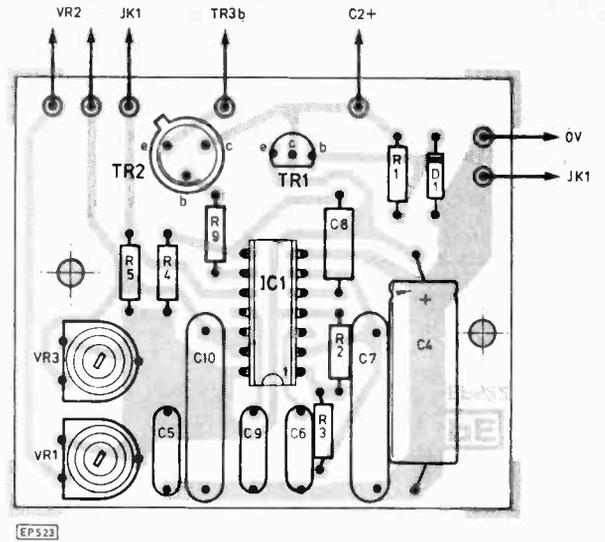
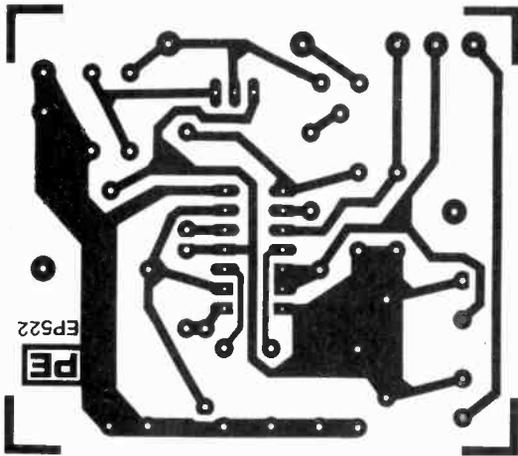


Fig. 4. Interwiring detail

and it was a simple matter to alter the connections. The main capacitor and bridge were mounted on the bottom of the box, and the output decoupling components were mounted directly on the output jack socket.

Four stick on plastic feet completed the unit.

### TESTING

If an alternative current limited supply is available it is a good idea to test the board with that, since a major failure will almost certainly destroy TR1 and probably D1 as well. Set the supply for about 17 volts. After re-checking the wiring switch on. Check the regulator works. Check that a pulse output is present on pin 5, and also on pin 9. Set both presets to half travel and connect a drill up and it should run. Increase the speed control to full, and the drill should speed up. If it starts to run roughly, and slows down, do not

worry—it is simply the monostable over running. Adjust VR3 with the speed control at maximum until the motor runs at its fastest. Turn the speed control to minimum and adjust VR1 until a suitable speed is obtained, then re-adjust VR3 with the speed control at maximum.

### IN USE

All drilling should be performed with the speed control at maximum. Slow drilling will wear the drill bits out more quickly, as well as taking longer. For other uses, burring, polishing, etc. the best advice is trial and error, but around half speed seems to be the best.

The footswitch is a definite improvement. It is particularly useful if the drill stalls because the drive can be released quickly, and when drilling over a centre point because the drill can be positioned and then started. ★



# Multicore makes for a better job...

The biggest name in solder worldwide




### Tool Box Reels

3 flux-cored solders that cover a range of electrical and non-electrical applications. ARAX 40/60 tin/lead size 11 £3.91 each. ALU-SOL size 4 £6.90 each. ERSIN 40/60 tin/lead size 3 £3.91 each.
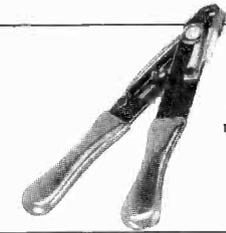
### Solder Cream

For precision soldering, Solder Cream is a mixture of solder powder and flux. Electrical/electronic ("Ersin" flux) size BCR10 £1.38. Metal joining ("Arax" flux) size BCA14 £1.38. Stainless steel and jewellery ("Arax" flux) size BCA16 £3.22.



### Wire Strippers & Cutters

No tool box is complete without this handy wire stripper which will adjust to most sizes of flex and cable. Easy grip plastic coated handles. Automatic opening. Handle locking device. Ref 9 £2.69.



### Handy Dispensers

Size 19A 5-core solder Ersin flux 1.22mm dia for electrical work £0.97.  
Size PC115 extra thin gauge for small electrical components £1.15  
Size SV130 5-core Savbit specially for copper bits and wires £1.61  
Size AR140 Arax solder for all metal repairs except aluminium £1.38.  
Size AL150 Alu-sol for most metals especially aluminium £1.93.  
Size SS160 for stainless steel and silver jewellery £2.53.

**Soldering Flux Paste - Ersin**  
A fast, non corrosive rosin flux for general and electrical soldering applications. Use with Ersin Multicore solder. Size RF10 £0.69.

Arax soldering flux paste also available for general metal working. Size AF14 £0.69.



**Ersin 5-core Dispenser**  
Handy dispenser for all electrical and electronic applications. Size 6 £0.58.

### Savbit Dispenser

Handy dispenser ideal for radio, TV and similar work. Reduces copper erosion. Size 5 £0.90.




# ... Bib makes for a better sound


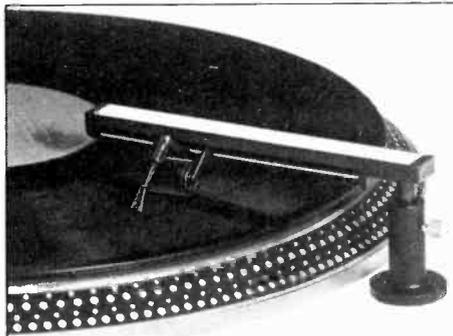
### Electronic Cassette Head Demagnetizer

Demagnetizes the tape heads to improve performance and reduce background noise. Audible tone indicates demagnetizing action. Works on all cassette machines including in-car. No external power needed. Ref 23 £10.49.



### Bib Groove-Kleen

For single play turntables. Velvet pad and tracking brush track across the record as it plays picking up harmful dust to improve sound performance. Ref. 101B £4.69 British Patent Number 1519881



### Cassette Tape Hand Winder

Winds a C90 cassette in 60 seconds - faster than most cassette machines. Especially ideal for battery powered recorders to save consumption when used on fast wind. Ref 78 £1.66. British Patent Number 1443628



### Bib Groove-Guard-XL-2

Unique formula liquid, when applied to record, gives anti-static protection and helps reduce friction between stylus tip and groove. Complete with pump spray dispenser and special cleaning pad. Treats up to 12 LPs. Ref 27 £2.60.



### Record Valet and Liquid

Handy kit contains special anti-static fluid and velvet record cleaning pad. Ideal to remove dust and other particles from records and provides an anti-static effect to help keep your records clean. Ref 47 £3.45.



### Tape Head Cleaning Kit

Contains everything needed to clean and maintain the heads, capstan and pinch wheel on all types of cassette and tape machines. Kit includes cleaning and polishing pad, special liquid and handy inspection mirror. Ref 25 £2.48. British Patent Number 1485069.



**Bib Hi-Fi Accessories Ltd.**  
Kelsey House, Wood Lane End,  
Hemel Hempstead,  
Hertfordshire HP2 4RQ.  
Telephone: (0442) 61291.

All prices given are recommended retail including VAT. If you have difficulty in purchasing your Multicore solder product or Bib Hi-Fi accessory, send direct to the address above quoting the reference number and including your remittance plus 40p P&P. Send SAE for free colour catalogue showing complete range.

# Crompton Instruments

## Type 33 Analogue Multimeter

**A Superior Electronics Test Meter for home or service use**



**New low price - only £22.95**  
(inc. VAT and p & p in U.K.)

- ★ 31 ranges - DC, AC, OHMS, dB etc.
- ★ Test leads, batteries & wallet supplied
- ★ High accuracy - 20KΩ /Vdc
- ★ Mirror scale + knife-edge pointer
- ★ 2 fuses + diode protection
- ★ Colour coded switches/scales
- ★ Tough stylish case
- ★ 12 months guarantee
- ★ 5 U.K. Service Centres

### 31 Switched Measuring Ranges:

DC Volts:	100mV, 0.5, 2, 10, 50, 200, 500, 1000V
DC Current:	50, 500μA, 5, 50, 500mA, 5A
AC Volts:	2.5, 10, 50, 250, 1000V (50 - 10,000Hz)
AC Current:	250μA, 2.5, 25, 250mA, 2.5A
Resistance:	1Ω - 5KΩ, 50, 500kΩ, 5MΩ (+50MΩ)
Capacitance:	100pF - 50nF, 10,000pF - 50μF
dB Ratios:	-12 to +40 dB

**HAWKER SIDDELEY**  
**CROMPTON INSTRUMENTS**  
CROMPTON INSTRUMENTS, U.K. MARKETING  
8 SAFFRON WAY, LEICESTER LE2 6UP  
Hawker Siddeley Group supplies electrical and mechanical equipment with world-wide sales and service.


Please send me ..... Crompton Type 33 Multimeter(s) at £22.95 each.

I enclose cheque/money order/postal order for £ ..... made payable to Crompton Parkinson Ltd.

NAME (Please print) .....


ADDRESS .....

# CROFTON STAR OFFER

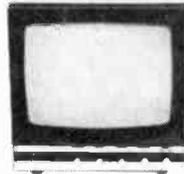

## 9" Aztec Monitor

P4 White £55.75 P31 Green £69.00

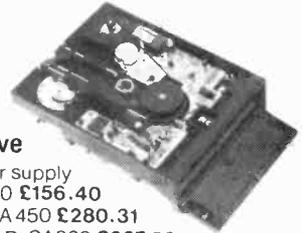

## Floppy Disk Drive

No case, no power supply  
5 1/4" S.S.S.D. SA400 £156.40  
5 1/4" D.S.S.D. SA450 £280.31  
8" S.S.S.D. SA800 £337.52



## Sony Colour Camera

2010P 12v operation  
IV composite output £298.50

The above prices include VAT  
Carriage will be charged at cost.



All major credit cards accepted



Ask for Crofton Mail Order Catalogue.

Phone or write to

## CROFTON ELECTRONICS LIMITED

35 Grosvenor Road, Twickenham, Middlesex TW1 4AD. Tel: 01.891 1923/1513

# Rapid Electronics

Pack No.		Price	Pack No.		Price
A10	10 PP3 battery leads	50p	F331	1 BD139 transistor	45p
A72	10 3.5mm jack plugs	80p	F421	1 MJ2955 transistor	110p
A73	10 3.5mm jack sockets	80p	F43	5 78L05 regulators	130p
A74A	5 Standard jack plugs	80p	F46A	1 7805 regulator	70p
A75A	5 Std. jack sockets	90p	F47A	1 7812 regulator	70p
A84A	5 5 pin 180 DIN plugs	70p	F49A	1 7905 regulator	75p
A85A	5 5 pin 180 DIN sockets	55p	F53	1 LM317T variable reg.	200p
C21	5 Min. slide switches	75p	F54	1 LM323K 3A 5V reg.	500p
C28	5 Push to make switches	70p	H11	20 1N4002 diodes	75p
C29	5 Push to break switches	90p	H30	2 W005 bridge rectifiers	45p
C50	20 8 pin DIL sockets	170p	H60	100 1N4148 diodes	180p
C51	20 14 pin DIL sockets	200p	H73	2 C106D thyristors	90p
C52	20 16 pin DIL sockets	220p	J5	10 0.2in red LEDs	100p
E10	Resistor kit. 650 resistors 1/4W 10 ea value 4.7 to 1M	480p	J25	10 0.2in green LEDs	150p
—	Single potentiometers		J45	10 0.2in yellow LEDs	150p
—	5K-1M log or lin	35p	J70	20 0.2in LED clips	60p
—	Slide potentiometers. 60mm travel. 5K-500K log or lin	65p	J7	10 0.125in red LEDs	100p
E26	10 100K min. presets	70p	J27	10 0.125 green LEDs	150p
E31	10 1u 63V electrolytics	50p	J47	10 0.125 yellow LEDs	150p
E33	10 4u7 63V radial elec.	50p	J72	20 0.125 LED clips	60p
E34	10 10u 25V radial elec.	50p	K5	5 741 op amps.	90p
E37	10 100u 25V radial elec.	75p	K20	5 CA3140 op amps.	225p
E44	10 1u 35V bead tants.	100p	K30	5 LM301A op amps.	140p
E50	10 0.01 C280 polyester	50p	K40	1 LM324 op amp.	50p
E54	10 0.1 C280 polyester	50p	K50	1 LM380 2W amp.	70p
E10	10 BC107 transistors	90p	K75	1 LM3914 LED bar graph	320p
F11	10 BC108 transistors	90p	K85	5 NE555 timers	110p
F12	10 BC109 transistors	90p	K90	1 NE556 timer	50p
F17	10 BC214L transistors	90p	K100	5 TL081 op amps.	175p
F27A	5 2N3819 transistors	100p	L8	5 4011 CMOS	130p
F311	1 BD131 transistor	45p	L9	1 4013 CMOS	40p
F312	1 BD132 transistor	45p	L11	1 4017 CMOS	75p
			L22	1 4049 CMOS	45p

All prices include VAT. Please add 50p postage and packing. Send SAE for our complete catalogue.

**Rapid Electronics Limited**  
Hillcroft House, Station Road, Eynsford, Kent

# Semiconductor UPDATE...

FEATURING ICM 7242 L290, 1 & 2 4118, 4801 & 4802 R. W. Coles

## DIGITAL 555

Probably the most universally useful and successful integrated circuit ever made is the ubiquitous 555 timer. You find them in the most unlikely places, often doing unlikely jobs which the manufacturers never dreamed of when they introduced the design back in the early 'seventies. First came useful dual and quad versions in 14 and 16 pin packages, and more recently came the CMOS versions, all helping to expand the area of application, but never really eclipsing the original design with its cheap, simple and robust reputation. All of the "improved" 555 devices have been covered in this column over the years, and this month I am able to report on yet another device intended to replace 555s in certain timing applications.

One area where all previous 555 circuits have run out of steam has been in the construction of simple timers capable of long delay periods of seconds or even minutes duration. The trouble is that the 555 relies on a single CR period to set time duration, and this means going to large electrolytic capacitors when long time-outs are needed. The use of electrolytic capacitors brings the usual bogies of poor tolerance, high leakage, and temperature sensitivity, and for critical applications the solution has been to run the 555 as a higher frequency astable and follow it with a multi stage binary counter such as the CMOS 4040.

To make the job of constructing long duration timers and low frequency oscillators easier, Intersil have introduced the ICM 7242 which puts the oscillator and the counter all in one 555-like 8 pin package. A single external resistor and capacitor set the basic oscillator frequency, and the oscillator output is fed to the internal 8 stage binary divider chain whose final stage therefore gives an output frequency 1/256th that of the oscillator. Also in the package is a control flip-flop which is set by a TRIGGER input, and starts the count sequence, and reset by a RESET input which stops the count and zeroes the counter chain. With the

RESET line disconnected the 7242 can be used as an LF oscillator, with the RESET line connected to the final count stage output the 7242 works like a monostable or timer.

For additional flexibility the basic RC oscillator output is brought out, as is the first stage of the count chain which gives a symmetrical square wave at half the oscillator frequency. This is a very useful device for those occasional long time/low frequency applications, but it won't replace the 555, take my word for it!

## ROBOT MUSCLE

Robots, like people, need muscles to enable them to move their "arms". Animal muscles can be precisely controlled, are efficient, and are very complex. The poor old robot, on the other hand, has to rely on electric motors, gears, and drive belts, not to mention feedback pots, servo amplifiers, and power supplies.

Really useful muscle analogues seem as far away as ever, but perhaps a new chip set from SGS-ATES can at least help to streamline existing d.c. servomotor "muscle" technology to make it more efficient and compact. With the addition of a d.c. motor and an optical position encoder, and under the control of a microprocessor, the L290, L291 and L292 trio make up a compact and powerful servo system for position control in robots or any other industrial machine. The L290 comes in a 16 pin plastic d.i.p. and contains the circuitry to interface the optical position encoder to the microprocessor by means of derived position and velocity signals. This chip also provides a compensated reference for the L291, which accepts parallel binary data from the microprocessor and converts this into an analogue servo demand signal using a D to A converter. This chip also contains a position amplifier, mode/direction switches, and is housed in another 16 pin d.i.p. The L292 is the motor driver, able to handle up to 2 amps at 36 volts using an overload protected bridge circuit. The L292 operates in the "switched" mode, and in keeping with the application, it is housed in a 15

lead Multiwatt power package.

When interconnected, the servo components operate in two modes. In order to slew rapidly to a new demanded position the servo loop can initially employ velocity control only, but as the target position is approached, a change to precise position control is made.

## PUTTING THE BYTE ON

If you are shovelling together a new microprocessor system and can't make up your mind what to do about memory, it's probably time you had a look at the "Bytewyde" concept championed by Mostek.

Bytewyde is not a reference to a single memory device, but is the name given to a whole family of devices, including some you will already be very familiar with, like the 2716 EPROM. What makes the concept special is the plug-in interchangeability of ROM and RAM memory devices in the same socket by utilising the pin configuration made standard by 24 pin UV erasable EPROMs and compatible masked ROMs. To launch the concept, Mostek introduced the 4118, a 1K x 8 static RAM in a 24 pin package which would have been a useful hunk of memory even *without* EPROM compatibility! Things didn't stop there however, and now there are bigger chips and several new manufacturers joining in. Mostek have introduced another 1K x 8, the 4801 which is faster than the 4118, and are now offering the 4802 which is faster and has a 2K x 8 capacity to boot. The Mostek chips are all NMOS, but in the land of the rising sun they are turning out CMOS memories in the Bytewyde mould, such as the MSM 2128-1 from OKI Semiconductor, another 2K x 8 device.

If you adopt Bytewyde, you can lay your boards out with standard 24 pin sockets and then by changing links to just two of the pins, you can plug in your choice of 1K x 8, 2K x 8 or 4K x 8 EPROMs, or 1K x 8 or 2K x 8 RAMs. If you use 28 pin sockets instead, you will be ready for all of the above plus the new generation of 8K x 8 EPROMs and those giant RAM chips which are just around the corner!

# MICRO-BUS

Compiled by DJD.

Appearing every two months, Micro-Bus presents ideas, applications, and programs for the most popular microprocessors; ones that you are unlikely to find in the manufacturers' data. The most original ideas often come from readers working on their own systems; payment will be made for any contribution featured.

THIS month's Micro-Bus presents an automatic program loader for the ZX80, and a three-dimensional plotting program for the Acorn ATOM. But first here are three ingenious programs for the ZX80 devised by Lars Silen of Finland. They provide ways of concatenating strings, transferring the last character from one string to another, and reading from the ZX80's keyboard.

## CONCATENATING STRINGS

The ZX80 has no built-in function for concatenating two strings; so you cannot, for example, add the two strings A\$="STUV" and B\$="WXYZ" by writing A\$=A\$+B\$ as you can on some BASICs. The routine shown in Fig. 1 overcomes this limitation by providing a way of concatenating any two different string variables, and it is called as follows:

```
LET A$=A$
LET B$=B$
GO SUB 1000
```

With the examples given above A\$ would end up with the value "STUVWXYZ" and B\$ would have the value "" (the null string). The references to A\$ and B\$ in the two seemingly redundant LET statements may be changed to any two different string variables that are to be concatenated. Note that no variables should be used between these two LET statements and the subroutine call, as this may cause the interpreter to hang up.


```
1000 REM STRING ADDER
1010 LET AD=PEEK(16394)+256*PEEK(16395)-3
1020 LET AD=AD-1
1030 IF NOT PEEK(AD)=1 THEN GO TO 1020
1035 LET TP=PEEK(AD+1)
1040 POKE AD,0
1050 POKE AD,PEEK(AD+2)
1060 LET AD=AD+1
1070 IF NOT PEEK(AD+2)=1 THEN GO TO 1050
1080 POKE AD+1,TP
1090 POKE AD,1
1100 RETURN
```

Fig. 1. Program to concatenate two strings on the ZX80

## PROGRAM OPERATION

The program depends, for its operation, on the way strings are assigned in the ZX80; when a string variable is assigned to, the old version is deleted and a new version is created at the end of the list of variables. The two LET statements above have the effect of moving the

strings A\$ and B\$ to the end of the list of variables, so that they are positioned in memory as shown in Fig. 2 (a).

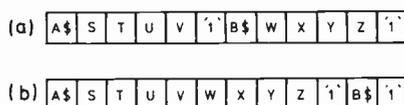

EG523

Fig. 2. Diagram showing two strings (a) before and (b) after running the String Adder program of Fig. 1

Locations 16394 and 16395 contain the address of the top of the list of variables; the program reads backwards from this address, through string B\$, until the terminating byte '1' is found at the end of A\$ (lines 1020 to 1030). Then the characters of B\$ are shuffled down onto the end of A\$ (lines 1050 to 1070), and finally B\$ is recreated as a null string (lines 1080 to 1090). The result is shown in Fig. 2 (b).

## TR\$ FOR THE ZX80

The following routine is very much like the ZX80's TL\$ function, but instead of cutting off the leftmost character from a string, it cuts off the rightmost character; it could therefore be called TR\$. The routine is shown in Fig. 3, and uses much the same technique as the program to concatenate strings. Again, the routine is called by executing:

```
LET A$=A$
LET B$=B$
GO SUB 1000
```

The effect is to cut off the last character from A\$ and add it as the first character of B\$. Thus if initially A\$="STUV" and B\$="WXYZ" the result would be A\$="STU" and B\$="VWXYZ". B\$ may initially be a null string.

```
1000 REM TR$
1010 LET AD=PEEK(16394)+256*PEEK(16395)-3
1030 LET AD=AD-1
1040 IF NOT PEEK(AD)=1 THEN GO TO 1030
1050 POKE AD,PEEK(AD+1)
1060 POKE AD+1,PEEK(AD-1)
1070 POKE AD-1,1
1080 RETURN
```

Fig. 3. Program for the ZX80 moves the last character from one string to another

## ZX80 KEYBOARD ROUTINE

One shortcoming of the ZX80 is that the keyboard and display are effectively dead during execution of a program. However, with the help of the following simple machine-code routine it is relatively easy to read keys at any desired time:

```
IN A,0 : read port 0 into accumulator
LD L,A : save result in LSB of HL
LD H,0 : zero MSB of HL
RET : return to BASIC, result in HL
```

Since there is always a risk that a machine-code routine located in the ZX80's RAM will be overwritten by the display file, the routine is written into a string which must not therefore be used elsewhere in the program. The program of Fig. 4 sets up the machine-code routine, and is called using the USR function:

```
LET K=USR(O)
```

where K is given the value of the key pressed. Note that this function, and lines 20 to 90 in the program, refer to the variable "O", not the digit zero.

```
10 REM READER
20 LET O$="XXXXXX"
30 LET O=PEEK(16392)+256*PEEK(16393)+1
40 POKE O,219
50 POKE O+1,0
60 POKE O+2,111
70 POKE O+3,38
80 POKE O+4,0
90 POKE O+5,201
```

Fig. 4. Program sets up a machine-code routine to read the ZX80's keyboard

## AUTOMATIC PROGRAM LOADER

It is often convenient to record a large number of seldom-used programs onto one cassette, but then it can be a lengthy business retrieving the particular one you want. The following system automatically searches a tape for the correct program, by skipping the correct number of earlier programs on the tape. It was developed by Trevor Toms of Phipps Associates, for use with the cassettes of programs that accompany their excellent "ZX80 Pocket Book", and they have kindly given permission for it to be included in Micro-Bus.

The automatic loading is performed by a header program, stored at the beginning of

each tape. This is loaded first, and it prints out a list of all the other programs on that tape. All you need to do is type the number of the program you want, and the header program will locate it and load it.

### MACHINE-CODE ROUTINE

The first stage in writing the header program is to create a machine-code routine that will skip past a program on the tape. This is best done using a BASIC program, as in Fig. 5. First, line 2 reserves 100 bytes for the machine-code by dimensioning an array C, and the address of this array is calculated and stored in the variable C (line 10). To avoid having to write the entire cassette routine from scratch, the ZX80's LOAD subroutine is copied out of the relevant part of the monitor ROM in lines 30 to 70, and then "patched" to do the required task by modifying certain bytes. The patches are as follows:

Lines 110 to 230 converts the routine into a subroutine, rather than part of the main command-entry loop, and make it read program bytes from tape until a byte containing 128 (or 80 in hex) is detected. This byte denotes the end of the program and program variables. Lines 240 to 260 make the routine ignore the system variables, which are stored as 40 bytes before the program text and program variables. Finally, the routine is patched so that if the BREAK key is pressed the USR function will return a value of -1 (lines 330 to 390). Any other value returned indicates that a program has been successfully skipped over.

```

1 REM CREATE CASSETTE HEADER
2 DIM C(50)
10 LET C=PEEK(16392)+PEEK(1639
3)*256+2
20 LET Y=C+1
40 FOR X=504 TO 597
50 POKE Y,PEEK(X)
60 LET Y=Y+1
70 NEXT X
100 REM PATCH LOAD SUBROUTINE
110 POKE C+1,21
120 POKE C+2,32
130 POKE C+3,5
140 POKE C+4,126
150 POKE C+5,254
160 POKE C+6,128
170 POKE C+7,22
180 POKE C+8,1
190 POKE C+9,0
200 POKE C+10,0
210 POKE C+11,32
220 POKE C+12,28
230 POKE C+13,201
240 POKE C+14,6
250 POKE C+15,40
260 POKE C+25,57
270 POKE C+35,42
280 POKE C+36,8
290 POKE C+37,64
300 POKE C+38,35
310 POKE C+39,35
320 POKE C+40,80
330 POKE C+49,33
340 POKE C+81,24
350 POKE C+82,174
360 POKE C+83,33
370 POKE C+84,255
380 POKE C+85,255
390 POKE C+86,201
400 STOP

```

**Fig. 5. Program to set up a machine-code routine to skip a program on tape**

Having typed in the program of Fig. 5, and saved it on tape in case it crashes, run it to create the machine code in array C. Now delete every line in the program, being extremely careful to avoid pressing RUN or CLEAR which would destroy the contents of array C. Now type in the header program of Fig. 6; this contains, in lines 100 to 200, a list of the programs to be saved on the tape, and these lines should obviously be altered to suit the programs to be stored. Line 20 calculates the address of the skip subroutine created earlier, which still exists in memory although there is no longer any reference to it. The subroutine is called by the function USR(C+14).

```

1 REM *** "GOTO 1" ***
2 REM *** DO NOT "RUN" ***
10 LET MAXPROGS=3
20 LET C=PEEK(16392)+PEEK(1639
3)*256+2
30 PRINT "PROGRAM SELECTION:"
40 PRINT
100 PRINT "1. MASTERMIND",,"1K"
100 PRINT "2. HANGMAN",,"1K"
120 PRINT "3. HUNT THE WUMPUS",
"3K"
200 PRINT
210 PRINT "REWIND TAPE, ENTER S
ELECTION"
220 PRINT "PRESS PLAY/NEWLINE T
OGETHER"
300 INPUT N
310 IF N<1 OR N>MAXPROGS THEN G
OTO 1
320 IF N=0 THEN LOAD
330 IF USR(C+14)=-1 THEN GO TO
400
340 LET N=N-1
350 FOR Y=1 TO 400
360 NEXT Y
370 REM SMALL SETTLE LOOP 4 SEC
S
380 GO TO 320
400 PRINT "BREAK..."
9999 STOP

```

**Fig. 6. Header program for the ZX80 loads a specified file from a tape**

Having entered the header program, save it at the start of the tape, and you are then ready to fill up the tape with programs you wish to archive. Note that about 10 seconds of blank should be allowed after recording the header program, so that it can be updated and re-recorded if more programs are added to the end of the tape at a later stage.

### USING THE PROGRAM

In use, the header program is first loaded from the start of the cassette, and executed using "GOTO 1" since RUN would destroy array C containing the machine-code routine. Having selected a program from the menu, and entered its number, the tape is rewound and played again, while typing NEWLINE. The automatic loader will then skip the header program, and all the intermediate programs, finally loading the program that was chosen.

### 3-D PLOTTING

The simple program in Fig. 7 plots a three-dimensional curve using high-resolution graphics. It is designed for an Acorn Atom

with a floating-point extension. The program avoids plotting lines that would be hidden by the perspective from which the curve is being viewed; see Fig. 8.


The program uses a mixture of integer and floating-point variables: the floating-point variables are prefixed by a "%" sign, and are

```

5 REM 3-D PLOT
10 CLEAR 4
20 A=128;B=A*A;C=96;D=96
30 FOR X=0 TO A
40 S=X*X
50 %P=SQR(B-S)
60 %I=-%P
65 DO
70 %R=SQR(S+%I*%I)/A
80 %Q=(%R-1)*SIN(24*%R)
90 %Y=%I/3+%Q*D
95 FIF %I=-%P %M=%Y;GOTO b
100 FIF %Y>%M %M=%Y;GOTO a
105 FIF %Y>=%N GOTO c
110 %N=%Y
115 a %Y=C+%Y
120 PLOT 13,(A-X),%Y
130 PLOT 13,(A+X),%Y
135 c %I=%I+4
140 FUNTIL %I>=%P
145 NEXT X
150 END

```

**Fig. 7. Three-dimensional plotting program for Atom BASIC with floating-point**

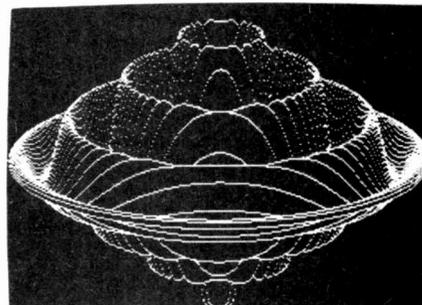

**Fig. 8. High-resolution graphics curve produced by 3-D Plot program**

totally separate from the normal integer variables. A second version of the IF statement, FIF, is provided for floating-point comparisons; similarly the integer DO...UNTIL loop, which gives repeated execution of a section of statements until the condition in the UNTIL statement is satisfied, has as its counterpart the floating-point DO...FUNTIL loop. The lower-case letters are labels, used by the GOTO statements instead of line numbers.

The graphics command 'CLEAR 4' sets up the display for 256 x 192 points, and the statement 'PLOT 13,X,Y' plots a point at coordinates X,Y. Hidden-line removal is performed by keeping a record of the highest point plotted, in %M, and the lowest point plotted, in %N; only points greater than %M and less than %N are plotted. Line 90 determines the perspective at which the curve is viewed. The function for evaluation is given in line 80, as the height %Q in terms of the radius %R, and this line can be changed to give plots of other functions.

# ULTRASONIC INTRUDER ALARM

GILBERT DAVIES

**T**HIS Ultrasonic Intruder Alarm is an updated version of the design published in *PE December 1979*. Modifications to the original circuit include the use of a sensitivity control which will also preset the detection range and a steady alarm output. The complete unit has been redesigned to fit onto a single p.c.b.

## CIRCUIT DESCRIPTION

The complete circuit diagram of the Intruder Alarm is shown in Fig.1. The 555 timer (IC2) is connected as a 40kHz square wave generator which can be fine tuned by VR1. The square wave output is filtered by R22 and C16 before being used to drive the ultrasonic transmitter X1. The 40kHz signal sets up a sound pattern in the protected room and if an object moves within the field a frequency shift occurs (due to the Doppler effect) to the waves which are reflected from the moving object. The transducer X2 will receive two different frequencies (40kHz and the shifted frequency which can be higher or lower than 40kHz); these will combine to produce a beat note. The frequency of this audio or sub-audio beat note will be the difference between the two ultrasonic frequencies. This beat frequency is then amplified filtered and used to operate the alarm. The received sound from X1 feeds the 40kHz amplifier IC3 the gain being determined by VR2, R6 and C6. VR2 adjusts the voltage gain from 1 to X100.

The output of this stage is fed to the envelope detector to remove the 40kHz signal and detect the Doppler frequencies from the received signal. IC4 forms a Doppler frequency amplifier the gain being set by R10, R9, and C8 this increases the signal sufficiently to drive the diode pump detector C9, D7, D8, C10 and R11 to convert the Doppler frequency into a d.c. level.

This d.c. level feeds the unit 'on' and 'movement' indicator formed by IC5, D9 and R12. The diode D9 glows when the unit is on and increases in brightness as a movement is detected, the brightness being dependent upon the voltage at the output of IC5 which causes current to flow through D9 and R12. The diode D9 also acts as a 1.2V level shifter for better matching to the next stage.


The d.c. level from IC5 is filtered by R13 and C11 (to form

a 1 second invalid movement delay to prevent false triggering) before feeding IC6a and b which form a bistable reset at switch on by C12, D11 and R19 (D10 forms a discharge path at switch off for C12). When the bistable is triggered by pin 13 going high the output of pin 10 goes high charging C13 via R14. When the voltage across C13 reaches the upper threshold of the Schmitt trigger formed by IC6c and d, R15 and R16 the output of pin 4 goes high driving TR1 via resistor chain R17 and R18, the collector of TR1 drives RLA and D12. Resistor R21 and C15 provide sufficient current to energise the relay with a low holding current to minimise the power taken by the relay. When pin 4 is high C12 is discharged by R19 and R20 causing the voltage at pin 9 to rise, which resets the bistable causing pin 10 to go low discharg-

## FEATURES

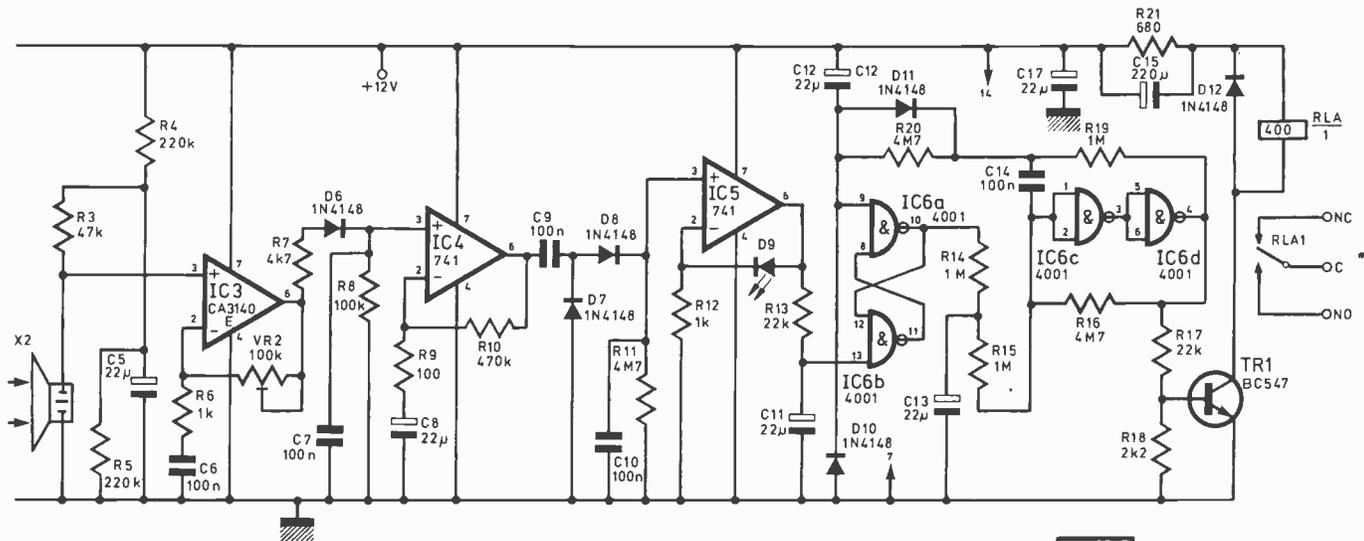- (1) Screw connections for 240V a.c. supply and remote alarm sounder.
- (2) 1BV battery back up option in case of mains failure. Ni-cads can provide up to 5 hours of protection.
- (3) Internally preset detection range (normally preset to 15 feet with built and tested alarms)
- (4) Half second system test at switch on—acts as an alarm on reminder for the user
- (5) Twenty seconds delay at switch on—to allow the building to be left without sounding the alarm.
- (6) Twenty second delay on entry—to allow the alarm to be cancelled without sounding.
- (7) One second invalid movement delay—to prevent false alarms by plants etc.
- (8) Two minute self cancelling alarm—to provide repeated protection whilst away for long periods.

The alarm is most sensitive to moving objects in front of the unit and towards the unit. A red lamp glows on the front of the unit when power is connected and increases in brightness as movement is detected.



ing C13 via R14 and when the lower threshold of the Schmitt trigger is reached pin 4 goes low turning off TR1 and de-energising RLA. If relay RLA is removed and R21 linked TR1 can drive a low power high efficient piezo sounder such as the ITT U250-RHA which requires 12V d.c. at 18mA to produce a 105dB 2.7kHz at 1 metre.

R1 and D5 form a suitable charging circuit for ni-cad battery back up. If dry cells are used the charge resistor R1 should be removed. The mains power to the unit and battery feed should both be switched.

The power supply consists of T1, D1, D2, D3, D4, smoothing capacitor C1 i.e. regulator IC1 and decoupling capacitors C2 and C17.

The switch on test is provided by C14 causing pins 1 and 2 of IC6 to go high whilst charging through path C12. D11, R15 and C13 causing pin 4 to go high turning on TR1 and energising RLA.

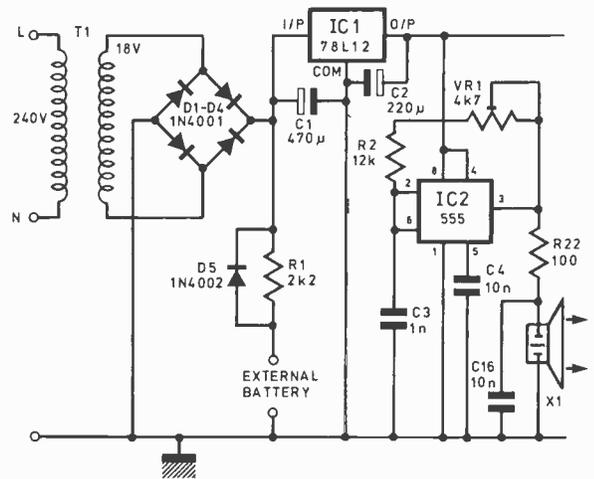


Fig. 1. Complete circuit diagram of the Intruder Alarm

## COMPONENTS . . .

### Resistors

R1, R18	2k2 (2 off)
R2	12k
R3	47k
R4, R5	220k (2 off)
R6, R12	1k (2 off)
R7	4k7
R8	100k
R9, R22	100 (2 off)
R10	470k
R11, R16, R20	4M7 (3 off)
R13, R17	22k (2 off)
R14, R15, R19	1M (3 off)
R21	680

All resistors  $\frac{1}{4}$ W 5% carbon

### Potentiometers

VR1	4k7 min. hor.
VR2	100k min. hor.

### Capacitors

C1	470µ 25V elect.
C2, C15	220µ 16V elect. (2 off)
C3	1n polyester

C4, C16	10n ceramic (2 off)
C5, C8, C11, C12, C13, C17	22µ 16V elect. (6 off)
C6, C7, C9, C10, C14	100n polyester (5 off)

### Semiconductors

D1-D4	1N4001 (4 off)
D5	1N4002
D6, D7, D8, D10, D11, D12	1N4148 (6 off)
D9	Red l.e.d.
TR1	BC547
IC1	78L12
IC2	NE555
IC3	CA3140E
IC4, IC5	741 (2 off)
IC6	4001

### Miscellaneous

T1	Mains transformer 18V sec
X1	MA40LIS
X2	MA40LIR
	20mm grommets (2 off)
	9mm grommets (2 off)
	ABS box 115 x 95 x 45mm
	Relay Omron LC1N-E
	Piezo sounder ITT 250 RHA, p.c.b.
	3-way terminal block p.c.b. type (2 off)

### Constructor's Note

A complete kit of parts for the Intruder Alarm is available from **GJD Electronics, 105 Harper Fold Road, Radcliffe, Manchester M26 0RQ.**

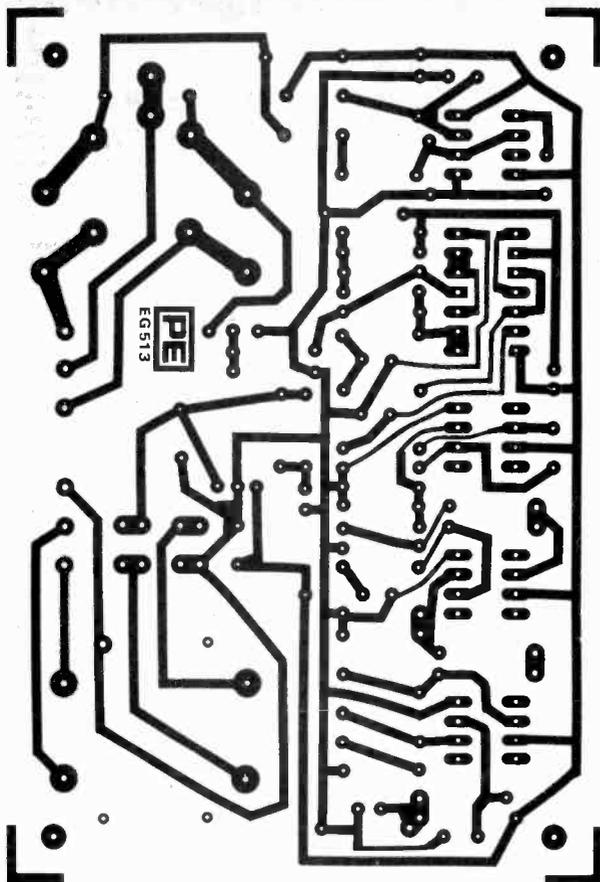


Fig. 2. P.c.b. design

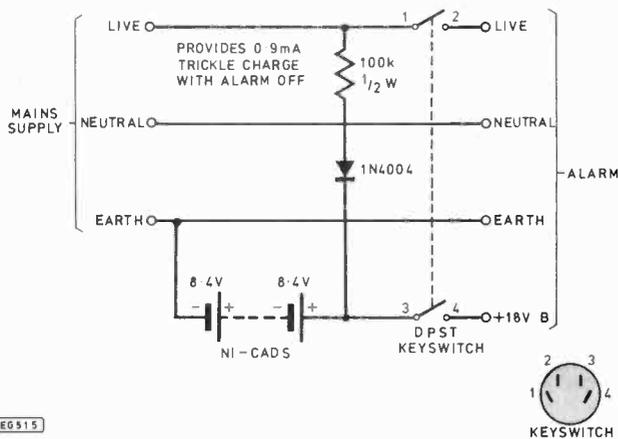


Fig. 4. Circuit for ni-cad conversion



Internal view of the alarm

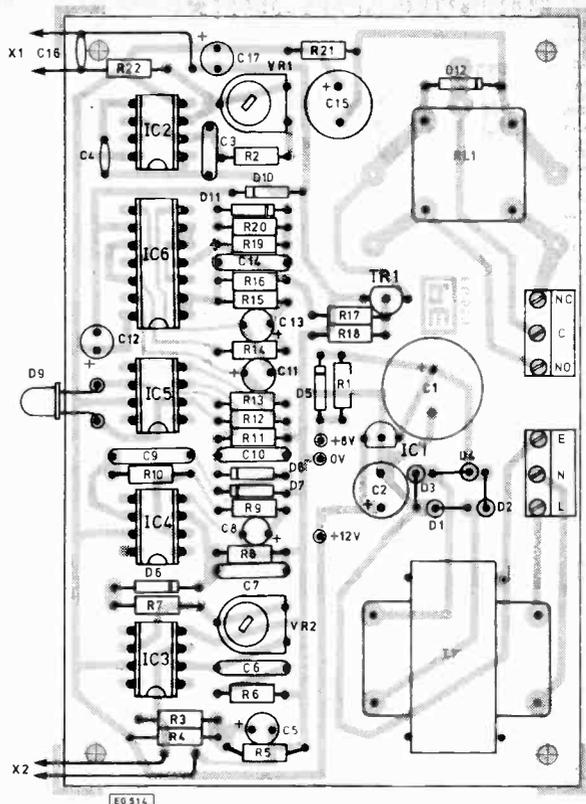


Fig. 3. Component layout

### CONSTRUCTION

The p.c.b. design for the alarm unit is shown in Fig. 2 with the component layout shown in Fig. 3. After all the components have been soldered onto the p.c.b. and checked then the case can be drilled. On the prototype the two transducers were fitted into 20mm grommets. The front panel should also be drilled for the movement detector i.e.d. Grommets should also be fitted to the two holes at the rear of the case used for the mains lead and relay connections.

With the transducers fitted into the case and the p.c.b. mounted, then C16 and the other end of R22 should be soldered onto the ultrasonic transducer X1.

### SETTING UP

Point the alarm into the room. Turn VR2 fully clockwise and measure the voltage at IC4 pin 3 which should be at around 5.5V d.c. Adjust VR1 until the maximum voltage is obtained, reduce this setting of VR2 for the required sensing range. It is always best to use the minimum range required to reduce the possibility of a false alarm.

### INSTALLATION

The alarm is prone to both vibration and air currents therefore the points below should be observed to avoid false triggering of the alarm.

- (1) Do not place the alarm on a vibrating surface.
- (2) Close all doors and windows.
- (3) Do not point the alarm at a radiator or convector heater.
- (4) Cats, dogs and large insects should be considered.
- (5) If more than one alarm is to be used ensure that the ultrasonic sound emitted by one alarm does not interact with the second alarm.
- (6) Try to install away from telephones as some bells can produce high frequency sound similar to that of the alarm








outputs of a 7475 quad latch. The output voltage would range from a fraction of a volt for zero data to about 4 volts for the decimal value 15. The resistors would need to be one per cent tolerance types to avoid abrupt changes in voltage occurring when different sections of the chain are brought into play, as in the major transition which occurs from 7 to 8 for example.

The configuration could be doubled up to produce an 8 bit converter, but resistor tolerances would become more

critical. Also, if a PIA port was to be used with such a converter, higher value resistors would be required because of the relatively low drive capability of its output. This would further necessitate the use of a d.c. amplifier to produce a usable analogue output.
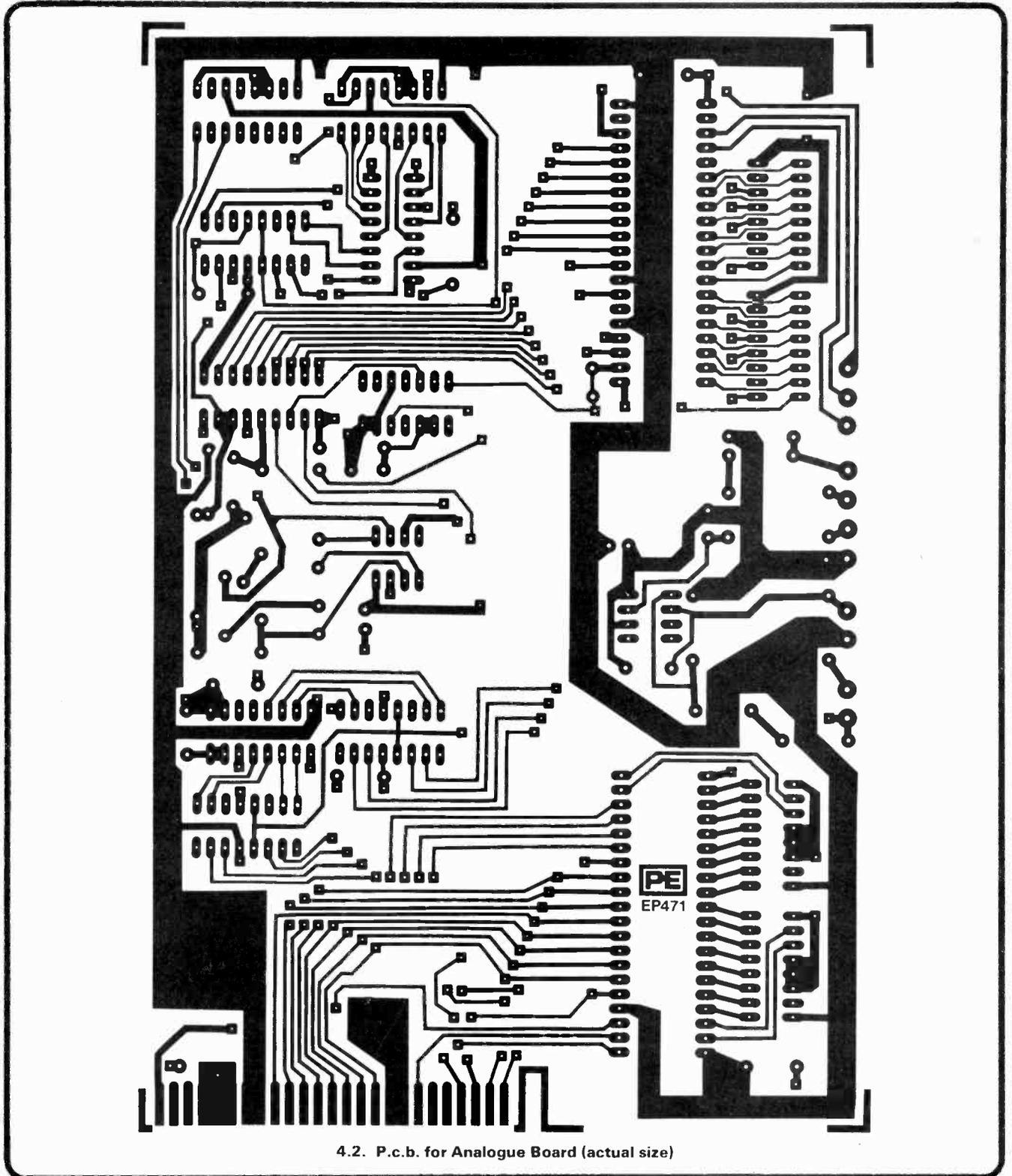
#### ZN425 MONOLITHIC CONVERTER

It is of course possible to get around these problems, and particularly the problem of conversion accuracy, by using a



4.2. P.c.b. for Analogue Board (actual size)

**Table 4.1 Connections Between SK1 of Analogue board and SK6 of Decoding Module.**

SK1 pin number	Upper		Lower	
	SK6 pin number (upper)	Function	SK6 pin number (lower)	Function
1	1	Vgg(-5V)	1	RESET
2	2	Ø2	2	W7
3	3	1RQ	3	W8
4	4	BC1	4	R7
5	5	BDIR	—	NC
6	—	NC	—	NC
7	—	NC	7	R/W
8	—	NC	8	GND
9	—	NC	9	GND
10	—	NC	10	D7
11	11	W7	11	D6
12	—	NC	12	D5
13	13	A3	13	D4
14	14	A2	14	D0
15	15	A1	15	D1
16	16	A0	16	D2
17	17	GND	17	D3
18	18	GND	18	Vcc
19	19	GND	19	Vcc
20	—	NC	20	GND
21	—	NC	21	GND
22	—	NC	22	GND
23	—	NC	—	NC
24	—	NC	—	NC
25	25	NMI	25	BL2

monolithic D/A converter i.c. From the variety of such devices on the market we have chosen to use the Ferranti ZN425 for a number of reasons. In particular it is readily available at a reasonable price, and operates from a 5 volt supply.

Fig. 4.6 gives a block diagram of the sections of the 425 used in D/A conversion. Essentially it consists of 8 data switches which are activated by an external port or latches. These switch a precision R-2R network to an on-chip 2.5 volt reference source to produce an analogue output on pin 14. This is typically 2.555 volts for all bits on, and 3mV for all bits off.

### PRACTICAL D/A CIRCUIT

Fig. 4.7 gives the full circuit of the D/A section of the Analogue Board. This consists of a pair of 74LS75s wired to form an 8 bit data latch. The latch enables are taken to the W line on the Decoding Module, which corresponds to an address of 61320. The 8 parallel outputs of the latch are connected directly to the ZN425, which performs the conversion of the latched data within 1µ sec. The analogue output (DA) appears at pin 14 of the 425, and is fed to the non-inverting input of IC11, a 741 operational amplifier. Both DA, and the output of the op. amp. (DAA) are taken out to SK7, which also carries both polarity supply connections and ground.

The op. amp. circuit has two associated variable resistors. VR1 is used for zeroing, and has been given an extended offset capability, and VR2, which controls the gain between about 1 and 2.


To test the converter, connect a voltmeter between pin 14 of SK7 and earth (pins 1, 5 or 6 of SK7). Execute the command **POKE 61320, 0**, and adjust VR1 to give zero volts on the meter. Now execute **POKE 61320, 255**. This should cause the meter to read somewhere between 2.5 and 4 volts, depending on the setting of VR2. The system is now operational, and POKing intermediate values to 61320 should yield intermediate voltage readings with a linear correspondence (providing the gain has not been set too high).

If the voltage does not vary with differing data, a voltage check should be made on the DA output of the converter (pin 14 of IC6, or pin 16 of SK7). If this does not alter when data is POKed to 61320, then checks should be made on the outputs of the two latches IC4 and 5. These should also change when different values are POKed to 61320.
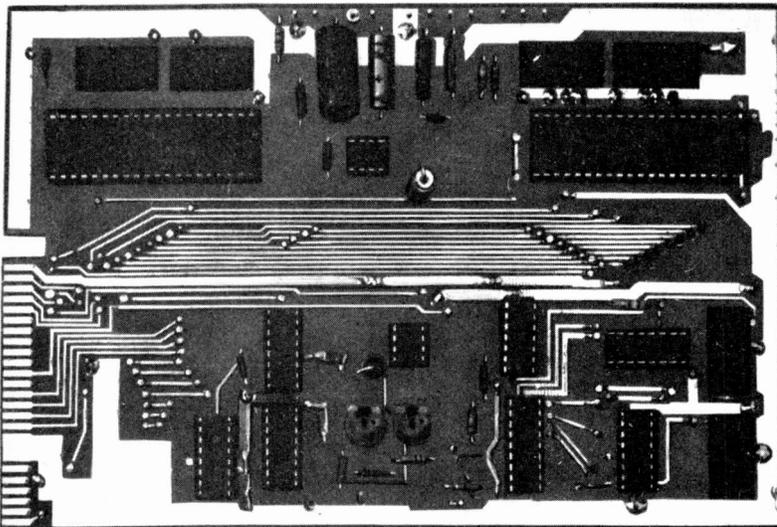
### APPLICATIONS OF THE D/A CONVERTER

The DAA output of the converter unit at pin 14 of SK7 may be used in a wide variety of different applications. It could be used for example to feed a servo amplifier controlling a d.c. motor which could variously drive a graph plotter, a steering mechanism, or a robot's left leg.

More simply it may be used to drive power controllers of one kind or another. For low power d.c. operation, a simple current amplifier of the type shown in Fig. 4.8 may be connected to the DAA output of the converter unit. This will vary the brightness of a 2.5V lamp according to the data POKed to 61320. To set this up, first execute **POKE 61320, 0**, and adjust the zero offset (VR1) so that the bulb is just extinguished. Then execute **POKE 61320, 255**. This should



### CONSTRUCTOR'S NOTE: NEW MONITOR IN EPROM

During the development of this series the screen editor written by Nigel Climpson and published in PE was found to be extremely useful. This editor is now available as the CE1 monitor in a 2716 EPROM for £12.50 + VAT and p&p, from Technomatic Ltd. It replaces the UK101 2K monitor ROM, and also contains useful routines such as a rapid screen clear.

illuminate the lamp brightly, and VR2 may then be adjusted to achieve best control over the full range of data.

A program of the type listed below will be found useful in setting up the converter for the above, and for other applications:

**80 REM TEST ROUTINE FOR A/D CONVERTER**

```
100 A=61320
120 INPUTX
140 POKEA,X
160 GOTO100
```

It simply requests a number, which should be an integer between zero and 255, and POKEs this to the converter.

**TRIAC CONTROLLER**

If a.c. or pulsed d.c. control is required, then the converter may be used to drive a Triac or Thyristor. There are many ways in which this may be achieved, but perhaps the most straightforward is to use the DAA output of the converter to vary the brightness of a l.e.d. indicator, which itself illuminates a light dependent resistor placed at a strategic

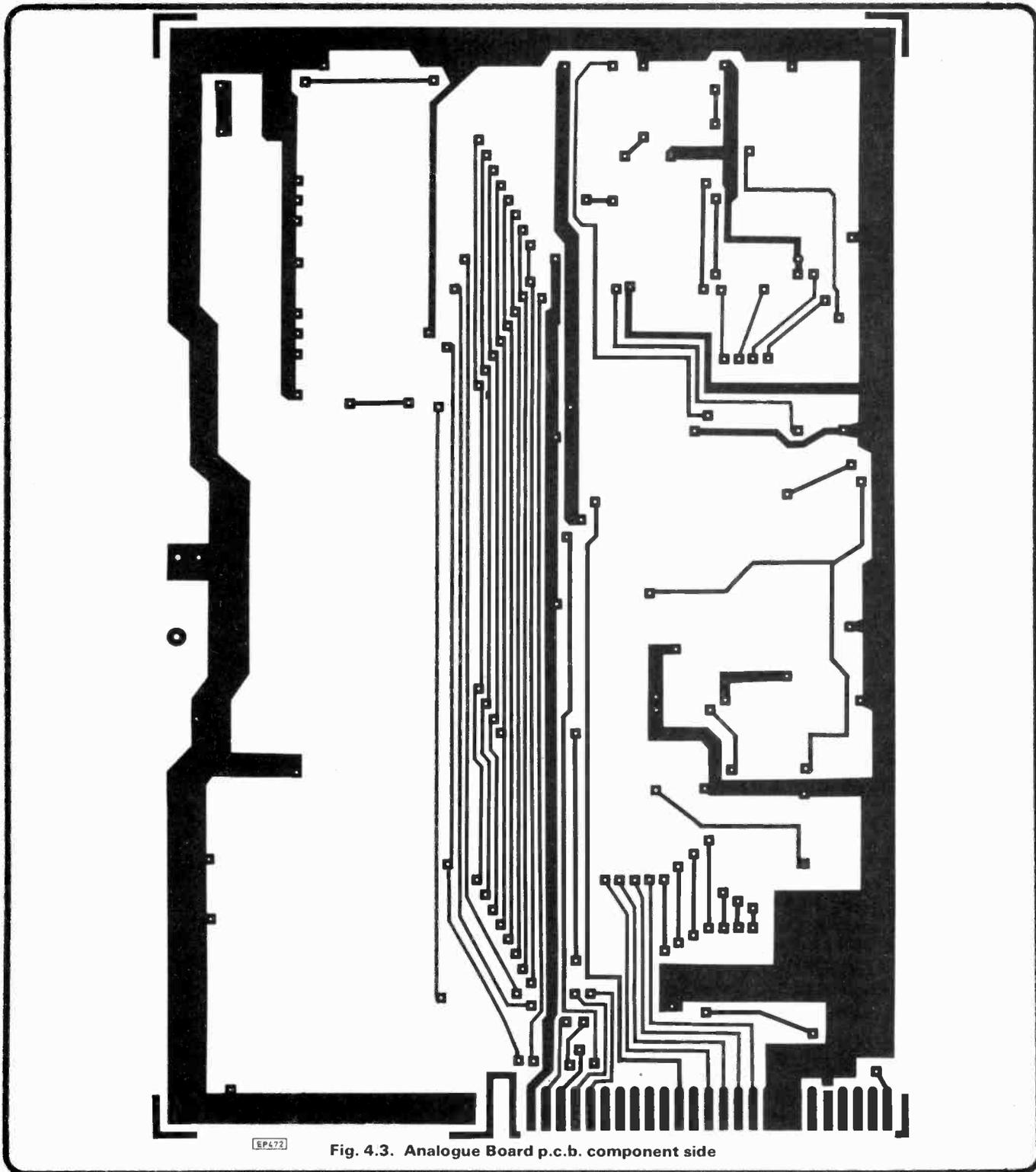


Fig. 4.3. Analogue Board p.c.b. component side

point in a triac or thyristor controller circuit. This has the great advantage of completely isolating the computer system from the mains. Alternatively, a patent opto-isolator such as the TIL112 may be used. In either case the l.e.d. may be directly driven by the DAA output of the converter as in Fig. 4.9.

Fig. 4.10 gives an experimental circuit for a power controller using the l.d.r. method. The phase shift for the triac is produced by the R1/C1 network, with the l.d.r. altering the

charge time of C1. R2, R3, and C2 help to reduce hysteresis and flicker, common diseases of this type of controller, though the latter is *not* completely eliminated. L1 and L2 are inductors each formed by winding about 100 turns of wire of a half inch former. Perhaps the most vital part of the circuit is the R4/C3 network. This prevents spikes in the supply line from destroying the triac.

The l.e.d. and series resistor are connected between the DAA output of the converter and Vcc. The l.e.d. should be

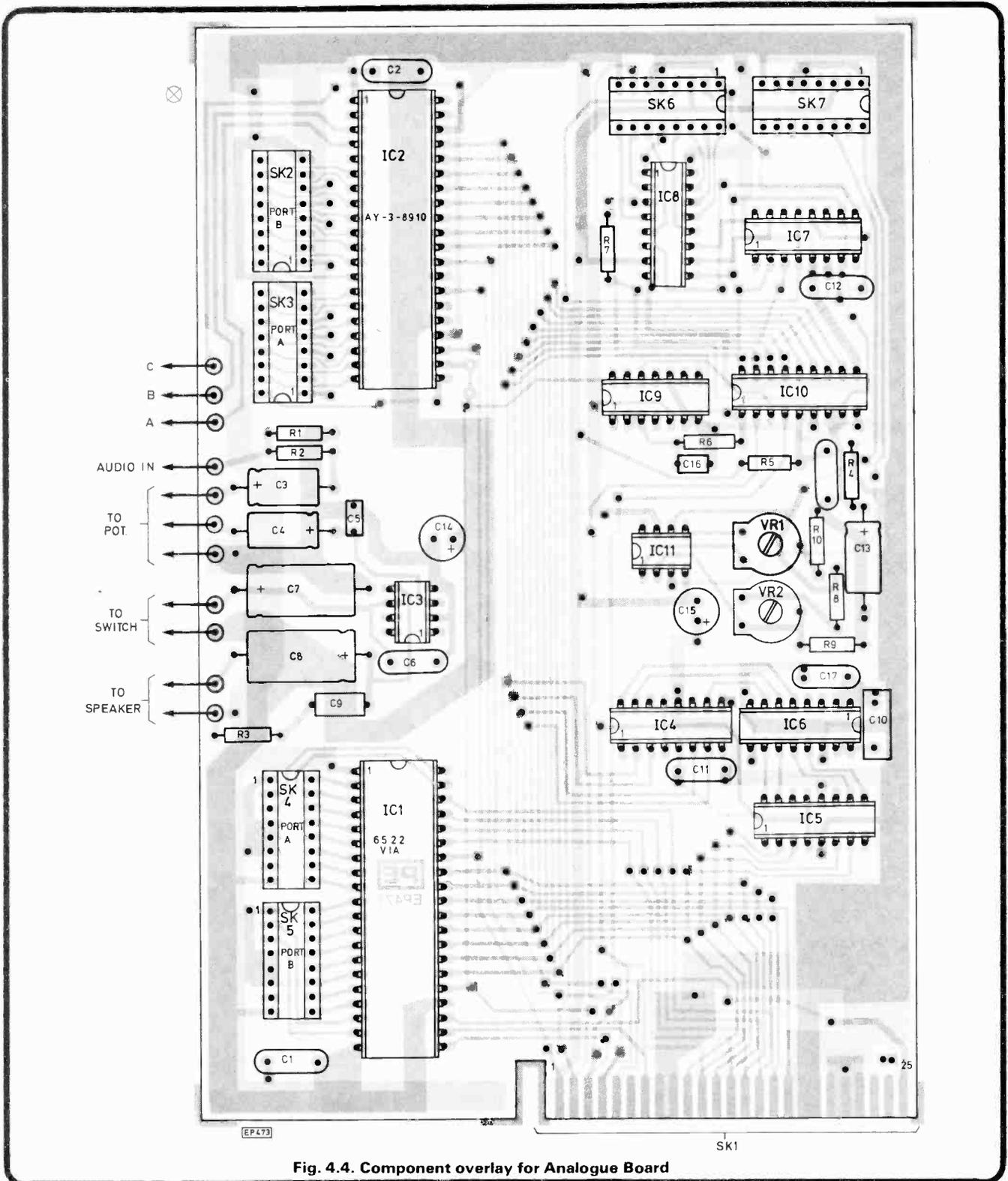


Fig. 4.4. Component overlay for Analogue Board

taped to the l.d.r., and the pair mounted in a *completely* light-tight container.


To set up the circuit, VR1 of the converter should be set to give zero volts between DAA and ground on execution of POKE 61320, 0. VR2 should then be adjusted to give a smooth range of control. Some adjustment of R1, 2 and 3 may be necessary to effect this.

### THYRISTOR CONTROLLER



In the author's experience, far more satisfactory power control is achieved using thyristors rather than triacs. One advantage of the thyristor is the ease with which unijunction transistor delay circuits may be used with them; and secondly they cannot suffer from asynchronous firing in the two directions of current flow, as may occur with the triac, and which is indeed one of the factors causing flicker in the controller of Fig. 4.10.

Fig. 4.11 gives the circuit of a thyristor controller which may be used to vary the power to some 12 volt d.c. device for currents up to two or three amperes. Control using the 500k resistor is smooth and flicker-free. An l.d.r. driven by an i.e.d. from the D/A converter may be introduced in a number of ways into this circuit. About the simplest is to take the l.d.r. from point X to earth via a resistor in the range 20 to 100k. To obtain smooth control it will be necessary to adjust the 500k pot in conjunction with VR1 and VR2 on the Analogue Board. Again, however, it should be stressed that this is an experimental circuit, and some adjustment of values may be necessary to obtain the best performance.

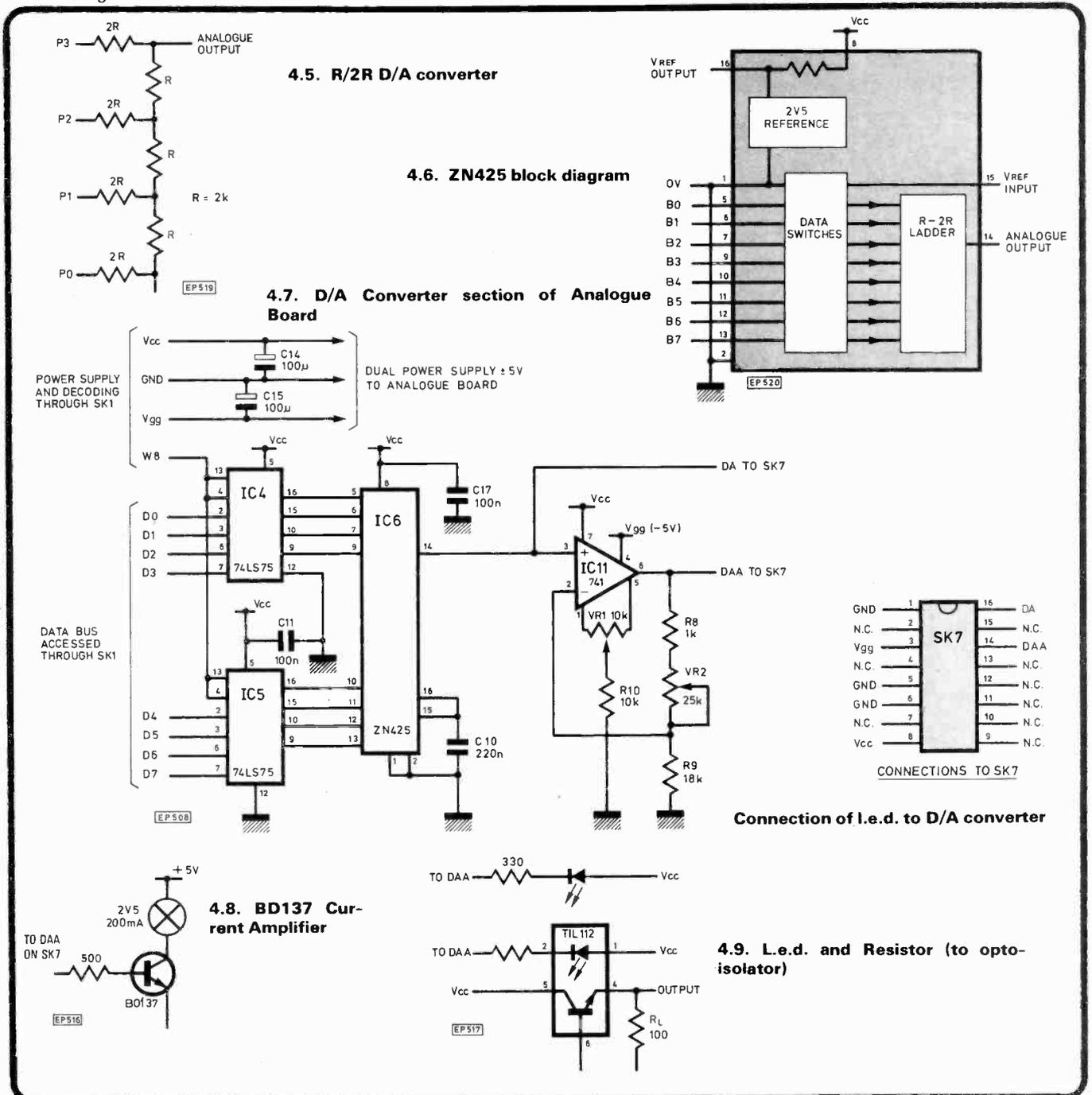
If it is desired to use this circuit for power control at a higher voltage, then it should be possible to increase the supply voltage, and adjust the Zener diode dropper resistor R1 accordingly. If a.c. control is required, then the load



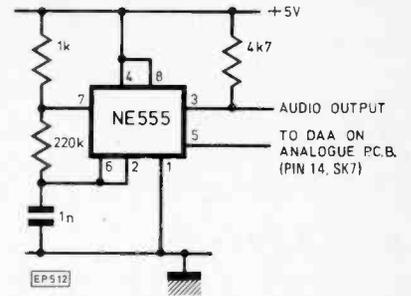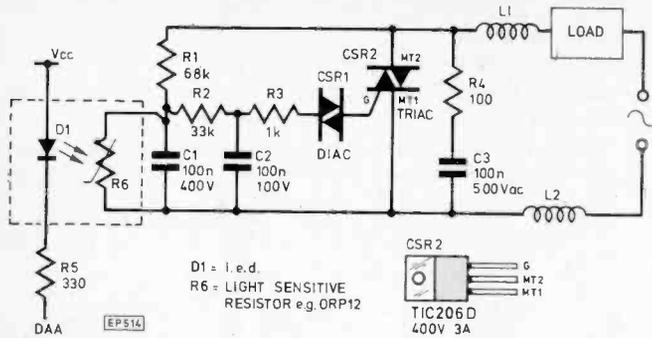
#### 4.10. Triac Power Controller. All resistors are 1 Watt



4.12. NE555 signal generator

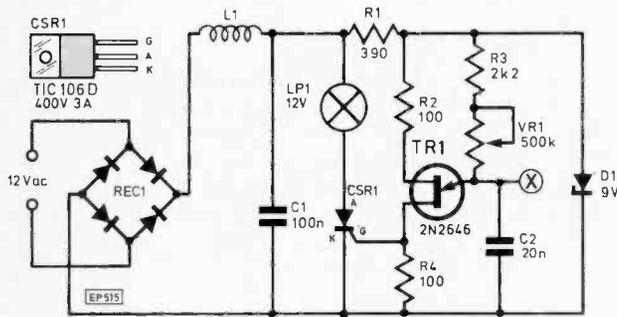

4.11. Thyristor Power Controller

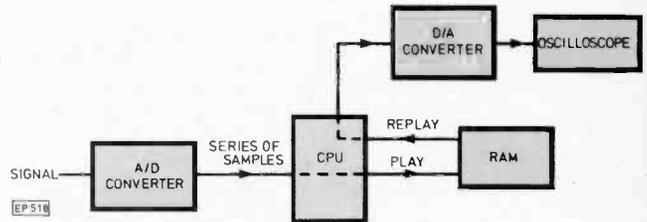

4.13. Block diagram of storage oscilloscope

## COMPONENTS . . .

### Resistors

R1, R6, R8	1k (3 off)
R2	100k
R3	10
R4	390
R5	82k
R7	3k9
R9	18k
R10	10k

### Potentiometers

VR1	10k preset
VR2	25k preset
VR3	100k log + switch

### Capacitors

C1, C2, C6, C11, C12, C17	100n disc ceramic (6 off)
C3, C4, C13	10µ/10V (3 off)
C5	1n
C7, C14, C15	100µ/10V (3 off)
C8	200µ/10V
C9	47n mylar
C10	220n mylar
C16	50n mylar

### Integrated Circuits

IC1	6522
IC2	AY-3-8910
IC3	LM386
IC4, IC5, IC7	74LS75 (3 off)
IC6	ZN425
IC8	4051
IC9	74LS90
IC10	ZN427
IC11	741

### Miscellaneous

P.c.b.	
SK1	2 x 25 0.1in. edge connector
SK2-SK7	16-pin d.i.l. sockets (6 off)
	40-pin d.i.l. sockets (2 off)
	16-pin d.i.l. sockets (5 off)
	8-pin d.i.l. sockets (2 off)
	14-pin d.i.l. sockets
	14-pin d.i.l. sockets
	length of 40 strand ribbon cable

### Constructors' Note

A complete kit of parts, excluding loudspeaker, is obtainable from **Technomatic Ltd., 17 Burnley Road, London NW10**

should be placed in series with the a.c. supply feeding the bridge rectifier. Additionally the reader is referred to the many power control circuits that have appeared in *P.E.* in the past, and to the useful book on the subject by *D. Marsden*, entitled *110 Thyristor Projects*. The use of one of these with a controlling l.d.r. or opto-isolator should meet most individual requirements; though it should be noted that the recently published circuit for the *Slave Light Dimmer (P.E. Feb. 1981)* is not suitable for this purpose.

### AUDIO OUTPUT

For some purposes it may be found useful to run an audio generator from the Analogue Board D/A converter, or from a R-2R converter running from an unused port, and buffered with an operational amplifier similar to that used on the Analogue Board. In either case the DAA output (or similar) may be used directly with i.c.s such as the NE566 function generator or the NE555 timer. Fig 4.12 gives a circuit for audio production using the 555. The DAA line from pin 14 of SK7 is used to directly drive the control pin (pin 5) of the 555. With the components specified this will give outputs in the range 5 to 10kHz. VR1 should be set to null output for zero data, and VR2 to maximum gain. This will result in outputs of about 10kHz for 255, and about 5kHz for data of around 80. If zero is POKEd to the converter, the generator ceases to oscillate, so providing a convenient means of switching off audio output.

### FURTHER APPLICATIONS

The D/A converter on the Analogue Board may also be used for directly handling audio and other waveforms. It can, for example, be used in the direct generation of virtually any conceivable waveform. The program below produces a stair-

case output at the DA and DAA pins of the converter:

```
100 A=61320
110 INPUT "SAMPLE RATE: TRY 5"; C
120 FOR B=1 TO 255 STEP C
130 POKE A, B
140 NEXT
150 GOTO 120
```

Using BASIC for this purpose limits the output frequency of any waveform generated to a few Hz or so. For higher frequency outputs, the program would have to be executed in 6502 code. It would be a relatively simple matter to write a short routine in 6502 code that successively output the contents of a block of memory to the D/A converter. The block could then be filled beforehand, using a POKE routine in BASIC, with any desired waveform, e.g. sin, square, triangular step, etc. The short 6502 code program could then be accessed via the USR(X) call to output the data at any given speed.

Using similar techniques in conjunction with an A/D converter it would be possible to write software for a storage facility for an oscilloscope. The A/D converter would sample a given waveform, and store the data in a given block of RAM. The D/A converter could then be used to output the sequence repeatedly, and at any frequency and repetition rate, so as to provide a permanent display, with the option of recall facilities, etc. See Fig. 4.13.

**Next month** we will look at the use of the PSG on the Analogue Board, and discuss applications such as a 14-note organ operated from the UK101 keyboard. Details will also be given on the use of the Programmable Sound Generator as a 3-channel D to A converter

# Readout...

## A selection from our Postbag

Readers requiring a reply to any letter must include a stamped addressed envelope. Opinions expressed in Readout are not necessarily endorsed by the publishers of Practical Electronics.

### Excellent Combination

Sir—I have recently constructed a *PE* Congress amplifier from a kit supplied by Wicca, as a re-introduction to electronics after a fifteen year break. Apart from bridging two tracks in the phono stage, the unit worked first time. I must congratulate the designer(s) on the performance of this design—it really is incredibly good to listen to, and is capable of 'demolishing' a number of commercial units with a higher 'paper' performance.

I have only two small points of criticism. Firstly, the effectiveness of the balance control can only be described as minimal. I can find no fault in the construction, so can you advise? The second problem (about which I intend to speak to Wicca) is transformer hum, which, in an amplifier that generates so little noise internally, is very noticeable. Perhaps a toroidal unit would have been worthwhile?

My second reason for writing is to give a pat on the back to a company which has given me superb service. Some six months ago, I purchased a pair of Videotone GB3 speakers through the *PE* Special Offer. These were used a few times on an old stereo record player which at best could be described as poor, but did play old records, so I took little notice of the poor sound. When I had completed the Congress, I connected the GB3 units, and with a decent input to them, it was immediately obvious that one tweeter was inoperative.

I telephoned Videotone and explained the problem, which they suggested may have been caused by clipping on the old amplifier (which I doubt as I treated the unit very carefully in deference to its meagre output), but they took my address and offered to supply a new tweeter under warranty. It duly arrived and was installed, and the speakers were connected. The performance of those tiny (and cheap) boxes is a revelation. There is ample bass during the day with a little boost, but the

real beauty is at night. With the bass rolled off a little, the sound quality is retained without annoying the neighbours. Try doing that with the bus-sized speakers that so many people seem to think necessary. In any normal residence, the Congress and GB3 pairing will be found capable of generating excruciating volume without distortion, even to those with 'disco-ears'.

To any reader who may have built a Congress, I would say without hesitation, "hang on a pair of GB3s, you will not believe your ears". I bought the GB3s on the strength of an earlier auditioning of the older 'Minimax', which was very good, but not, I believe, in the same class as the GB3. As for the service from Videotone, what can I say except "thank you".

S. G. West,  
Northampton.

### Noddy Radio

Sir—As a reader of your magazine I would be quite content if the sickeningly over-exposed letters "CB" appeared never again. I have no enthusiasm for citizens band radio, and I suspect that 99% of the population of this country is similarly disinterested.

What we have is a verbose minority creating a furore over what is, after all, Noddy radio. I am prepared to tolerate occasional breakthrough on my domestic equipment when it is the police going discreetly about their business—or even a local taxi firm.

However, I see no reason why I should endure prolonged breakdowns when I am trying to take in the news, just so that an immature "citizen" can tell the world he is called Rubber Duck and he doesn't like "bears".

I have no doubt that should this band be allowed, every ten years or so it will become involved in some small way with a murder hunt, and then we shall hear of the wonderful contribution CB makes to society. Why should a respectable magazine like *Practical Electronics* jump on this bandwagon?

As far as I'm concerned, CB should be allowed only on microwave at 1mW so that nobody can use it!

Peter Bleck,  
London.

Sir—I see that you have published a CB converter in your March issue. I already have a converter and I see from your editorial in the February issue that I need a licence to listen to it. As I cannot obtain a licence to listen to CB, how can I be prosecuted for not having something I cannot obtain anyway?

It is also illegal to transmit on CB, so therefore there is nothing to listen to. So how can I be prosecuted for listening to something that is not there in the first place?

This seems to me to be a ridiculous situation and the sooner the government comes up with some *sensible* licensing ideas, the sooner it will be getting more money to help with the running of the country.

Little T,  
Leicester.

Sir—Your editorial seeking views on listening to—for example—CB on 27 MHz raises a wider question. Has any government the moral right to forbid us to listen to any available radio transmission? There may be perfectly justifiable reasons for restricting *transmission* (e.g. CB) but it must surely be a fundamental right to *listen* to any broadcast information in an intelligible form.

The obvious exception is on security grounds, e.g. police radio—but the enterprising criminal is hardly likely to be deterred by the Wireless Telegraphy Acts more than, say, the Theft Act!

If the originator of a message chooses an inherently public medium such as radio the onus is on him to adopt a cryptic method of transmission. If an illicit broadcaster gets on the air it is the business of the authorities to stop him, not to tell us not to listen, as do totalitarian regimes. Even those who practice press censorship tend to go for the publisher rather than the reader!

D. B. Lyall,  
Cheltenham.

## Alive and Kicking

Sir—As the new chairman of the Amateur Computer Club I would like to clarify the current position of the ACC, and in particular its future. I feel that your readers, many of whom are interested in home computing will be interested to learn of the current position of the ACC.

I am pleased to announce that the ACC is now very much alive and kicking following a somewhat dormant period last year. The ACC is a national organisation to promote interest in amateur computers and computing, to facilitate the exchange of information and ideas, and to help members with their home computer systems. Annual membership is £4.50.

I would also like to mention a few other points. Firstly, last year the ACC year was extended to September '80. The new year started on October 1st and runs until 30th September '81. Secondly, it is hoped to set up regular contact with the journals and to keep them informed of the activities of the ACC.

Peter Whittle,  
Chairman—ACC,  
1 Blinco Road,  
Urmston,  
Manchester.

## Micro Bus Error

Sir—Congratulations for your excellent 'Micro Bus' series, but why not every month? Having tried the *Draughts Board* game in *February 81* issue (for the ZX80) I would like to point out a couple of small (but very important) errors (probably printing errors!):

Line 30 should read: **PRINT "12345678"**  
*Space after the eight, and Line 300 . . . OR (X=13 AND TL\$(A\$)="R") OR NOT... Bracket close after "R"*

Having just spent a Sunday afternoon finding the missing space, I hope this might save someone else the trouble. There has been some gain though, at least I now know how the program works, which I admit I wouldn't have if it had worked straight away!

P. Holton,  
Upper Norwood,  
London.

## PE Microtune

Sir—I have read with interest your project Microtune, in the Dec-Jan editions of your magazine, and was impressed by the technical specifications and useful functions available on what is quite a reasonably priced machine.

It is good to note that your magazine is aware of the importance of the correct adjustments to the ignition system of the modern motor car and that this equipment makes such adjustments an easy task. Using this equipment carefully should enable the builder to recover the cost of it in improved fuel consumption and smoother running in a very short time.

On reading the section "USING THE MICROTUNE", I would like to comment on a few points that I feel may cause confusion with an operator who is not fully conversant with car electrical systems and I hope that my comments may be of use.

In the section "Battery Checking" the test that is suggested is a good test but I feel that the duration of the test should be limited to 15 seconds as the time of 30 seconds quoted I consider too long and could result in the premature condemning of a serviceable battery. An extra check that could be incorporated into this section is a check on coil SW

voltage. On a 12 volt coil system the voltage at the SW terminal should be no more than 0.5 volt lower than the battery voltage. A higher volt loss could be due to a faulty ignition switch or connections in the coil feed. On a ballast system the voltage should be between 5 and 8 volts; a reading higher or lower could indicate a wrong coil fitted or a high resistance in ballast resistor or wiring. These checks are carried out with the contacts closed and ignition on. With the engine being cranked over, this voltage at the SW terminal should be a minimum of 9 volts. With a ballast system a voltage of, say, 5 volts would indicate a fault in the boost circuit between solenoid and coil.

Coil resistance tests are extremely useful, particularly when trying to find out if a car has the right coil fitted. The most usual figures are 3 to 3.5 ohms for a 12 volt coil and 1.5 ohms for a ballast coil. Most ballast resistors are 1.5 ohms and on some cars it is possible to check this also.

The section on points resistance is perhaps the most useful section, and it is important to get this figure down as low as possible. The figures quoted by distributor manufacturers vary between 0.1 volt and 0.4 volt. The Lucas figure of 0.2 volt can be considered as one to aim for. Good starting and coil output depend on a low volt loss here and to some extent condenser performance can also be affected. Things to look for are faults in plug-in connectors in the wiring, burnt or dirty contacts and distributor base plate earth faults.

Dwell angle on modern cars is around 50° and typical figures quoted are Motorcraft 48 to 52° on Ford vehicles, 46 to 56° by Lucas on most Leyland vehicles and 49 to 51° by Delco fitted to Vauxhall cars. These figures are all for 4 cylinder engines. Owing to the fact that altering the dwell angle by 5° alters the ignition timing by 5°, it is important to check and adjust the ignition timing after any distributor adjustments.

M. J. Stacey,  
TI Transport,  
PO Box 8,  
High March,  
Daventry,  
Northants.

## Going too far?

Sir—In view of the recent interest in CB, I think you may be interested to learn of an article which appeared in a recent issue of the medical newspaper *Doctor*.

The article concerns an incident in Preston, when a CB group donated £560 to the intensive care unit of a local hospital to buy some urgently needed equipment. The doctor who had accepted the donation was shocked when the hospital management refused the gift and ordered inquiries into the donors.

The article states: "An embarrassed Dr Saltpepper said 'After the DMT's final decision I was informed that it is not advisable for members of staff to associate with unlawful organisations.' He had not realised that the CB group—many of whom are ambulancemen—was unrecognised as a charitable body because CB radio is illegal."

D. M. Broughton,  
Leeds.

# PATENTS REVIEW...

Copies of Patents can be obtained from:  
the Patent Office Sales, St. Mary Cray, Orpington, Kent. Price £1.25 each.

## FINGER ON THE PULSE

The national obsession with jogging, and the health risks involved, is producing a spate of patents for gadgets which monitor the wearer's pulse rate and heart beat. The latest, British patent application 2 039 434, from Patrick Wright of Woking, Surrey and Julian Lynn-Evans of Chichester, Sussex, describes a sophisticated monitor which is worn like a watch on the wrist to give a constant digital readout of heart beat and sound an alarm if a dangerously high rate is reached.

The unit shown in Figures 1 & 2 has a transducer 16 and pressure sensor 13 on the rear face which lies over the wrist pulse point. Normal pulse rate is around 72 pulses per minute and the inventors suggests that in general, exercise should be controlled to keep the rate down to below 120ppm.

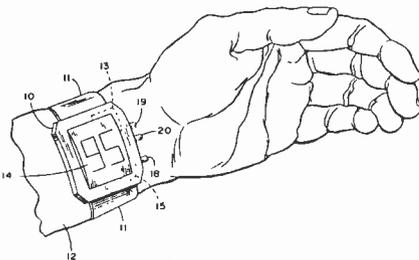


Figure 1

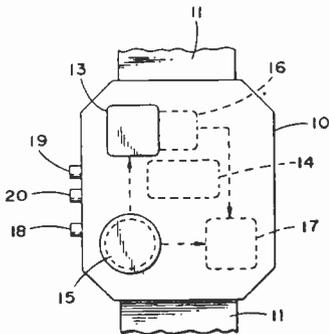


Figure 2

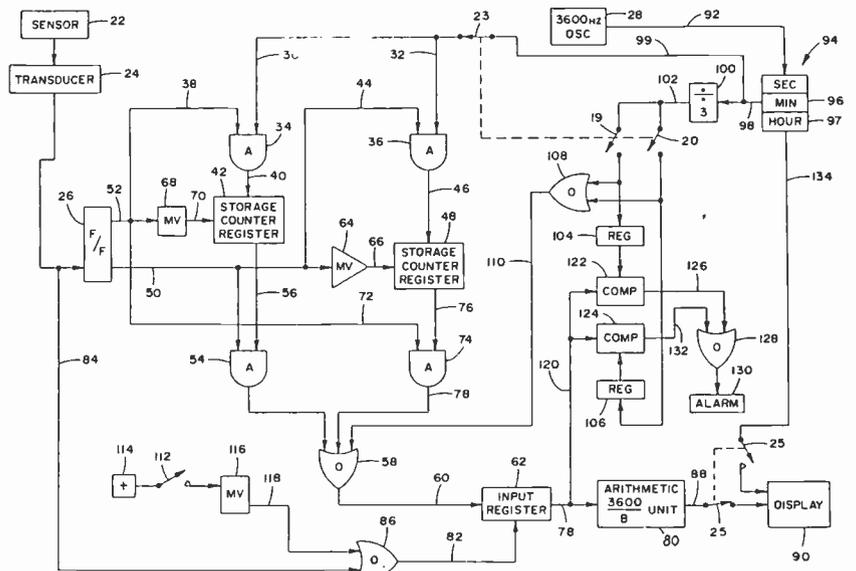


Figure 3

Figure 3 shows the basic circuit for utilising the pressure sensor output. Oscillator 28 produces a 3600Hz signal on line 92 coupled to clock 94. Heart beat rate is determined by the formula

$$H = \frac{3600}{B}$$

where H = heartbeat rate and B = the number of oscillator pulses stored between heart beats. So if 60 pulses are stored between heart beats, a rate H, of 60 beats per minute is represented and if 120 are stored between beats a rate H, of 30 beats per minute, is represented. Clock circuit 94 is a conventional second, minute, hour, clock and its 60 pulse per second output on line 98 is fed to AND gates 34, 36. These gates are enabled by a signal from flip-flop 26 which changes state each time a pulse is received from transducer 24. When the sensor 13 is in contact with the wearer's pulse pressure point it produces a pulse each time a heart beat is detected so flip-flop 26 changes state with the wearer's heart beat.

With the appearance of each heart beat one of two counters 42, 48 begins to store pulses from oscillator 28 until the next heart beat is sensed. At that instant the 60Hz pulses from clock 94 are transferred from the first counter to the second counter, while the output of the first counter is coupled to input register 62. So the number

of pulses occurring between heart beats is stored alternately in counters 42, 48 and transferred alternately to input register 62. Arithmetic unit 80 is programmed to divide 3600 by whatever count is stored in register 62. The output of unit 80 is coupled to numerical display 90. So the wrist watch unit provides a constant monitor of heart beat rate.

To sound the alarm for an excessively high rate, a pre-set number of oscillator pulses is stored in a register for comparison with the sensed rate. Switches 19, 20 couple the output of divider circuit 100 to storage register 104 and 106. As these switches are held closed, pulses are fed into the registers at 20 pulses per second and until required upper and lower limit heart beat rates are stored. Switch 19 is depressed to store the upper rate and switch 20 is depressed to store the lower rate.

Comparators 122, 124 receive the same input signals as arithmetic unit 80 from input register 16. Comparator 122 produces an output for OR gate 128 if the monitored heart beat is greater than the number of pulses stored in register 104. Likewise if the monitored number of pulses is less than the number stored in register 106, comparator 124 produces an output for OR gate 128. In each case an alarm 130 is activated to warn the wearer.



A selection of readers' original circuit ideas. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought.

Each idea submitted must be accompanied by a declaration to the effect that it has been tried and tested, is the original work of the undersigned, and that it has not been offered or accepted for publication elsewhere.

Why not submit your idea? Any idea published will be awarded payment according to its merits.

Articles submitted for publication should conform to the usual practices of this journal, e.g. with regard to abbreviations and circuit symbols. Diagrams should be on separate sheets, not inserted in the text.

## 'DAY TO REMEMBER' CLOCK


THIS circuit is an add on unit to D. E. Clarke's Digital Calendar published in *PE* June 1976. It provides a 'Day To Remember' alarm for birthdays, anniversaries, etc.

The NOR gates inputs are wired up to the required outputs from the 74154 on the digital calendar and the 7442. I have divided the unit up into three groups of three NOR gates, DAY/UNIT/MONTH, DAY/TENS/MONTH, DAY/TWENTIES/MONTH. If the day to remember is the 16th March, then the middle set of gates would have one of its inputs connected to the 3rd output on the 74154 and the other input connected to the 6 output on the 7442.

When the clock indicates this date both inputs would go to '0', feeding a '1' to the 7410 gate, as the date is the 16th, and not the 6th, or the 26th, 'except tens' will be at '1' and the 'inhibit 30' will also be at '1', then a '0' will be fed through and trigger the 7473. This will remove the inhibit from the 7440 and let the 1 sec. pulse through to switch the l.e.d.s on and off. The 7473 is reset by a '0' on pin 6: this will cause pin 9 to restore the inhibit and stop the l.e.d.s switch on and off.

Obviously it would be of no point in setting up the clock to indicate the day on which the birthday or anniversary falls, therefore I have set my clock up for the alarm to come on 5 days before the event.

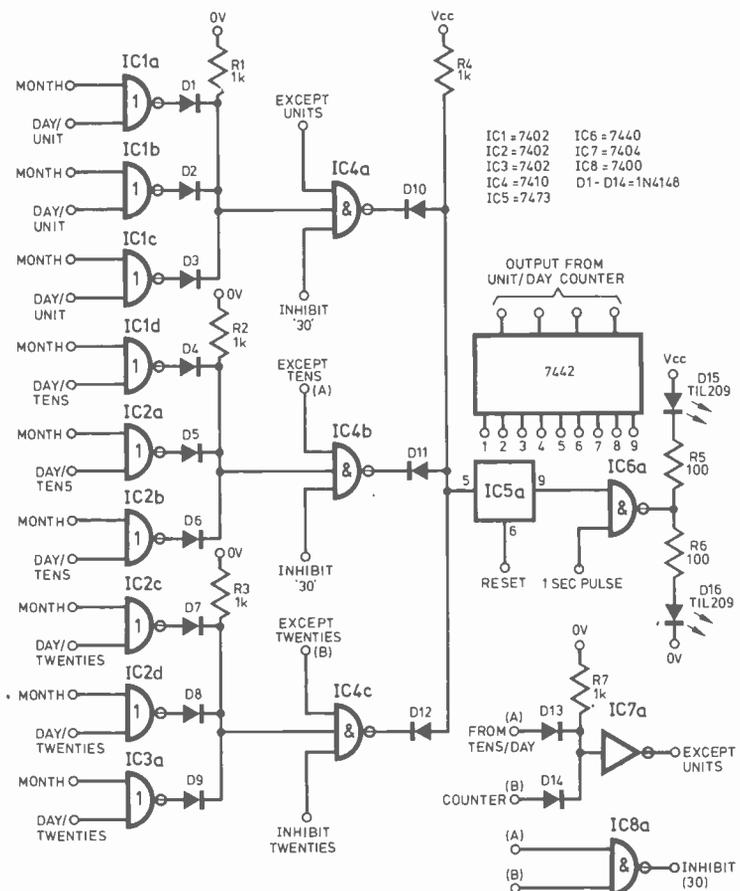C. T. Chantler,  
Grimsby,  
South Humberside.



THE thermometer circuit shown will measure temperature in the range  $-25^{\circ}\text{C}$  to  $+85^{\circ}\text{C}$ . The LM3911 is used to sense the temperature and provides an output of  $10\text{mV}/^{\circ}\text{K}$  ( $10\text{mV}/^{\circ}\text{C}$ ). Therefore at  $-25^{\circ}\text{C}$  ( $248^{\circ}\text{K}$ ) the output is  $2.48\text{V}$  and at  $+85^{\circ}\text{C}$  ( $358^{\circ}\text{K}$ )  $3.58\text{V}$ .


This output, though, goes negative on temperature increase, and is so inverted by the 741 op-amp. VR1 can be used to adjust the final reading on the display.

The LM3914 is an i.c. that senses analogue voltage levels and drives to l.e.d.s, providing a linear analogue display. The current for each l.e.d. is programmable and in this case is set at approximately  $10\text{mA}$ . The i.c. uses a resistive divider network, one end of which is set to the high reference, the other end to the low reference. For this application they are set to  $3.58\text{V}$  and  $2.48\text{V}$  respectively. These being adjustable by VR2. The divider therefore has  $1.1\text{V}$  across it which means that another l.e.d. will light for every  $110\text{mV}$  input, which corresponds to an  $11^{\circ}\text{C}$  temp. rise. The first l.e.d. will switch on at  $-14^{\circ}\text{C}$ , the second at  $-30^{\circ}\text{C}$  and so on up to  $+85^{\circ}\text{C}$ .

The mode switch selects whether previously lit l.e.d.s remain on as temp. increases, or whether only one l.e.d. remains on.


R. Eley,  
Keynsham,  
Bristol.

## BARGRAPH THERMOMETER

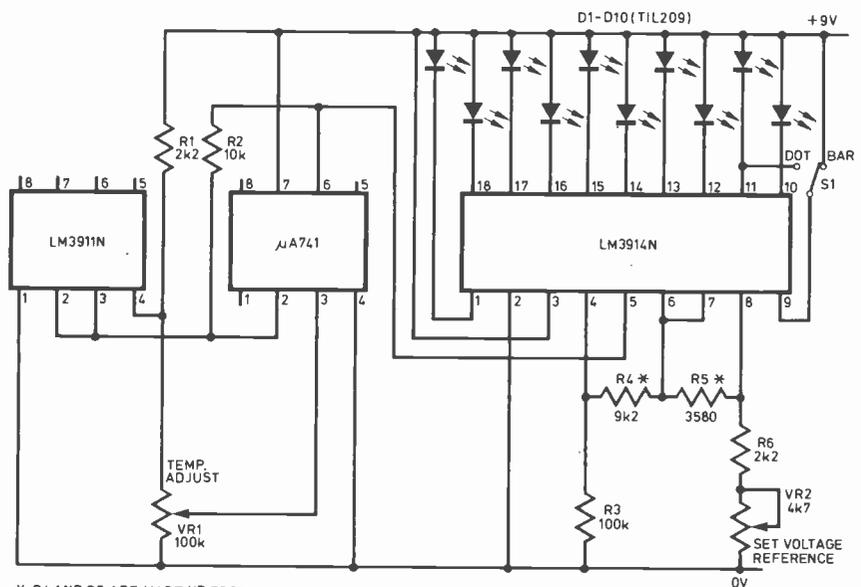

\* R4 AND R5 ARE MADE UP FROM  
8k2 AND 1k (R4) AND 3k3, 270, 10 (R5)  
FOR DIFFERENT SUPPLY VOLTAGES  
 $R1 = (V^* - 6.8)\text{k}$

## L.F. ANALOGUE MONITOR

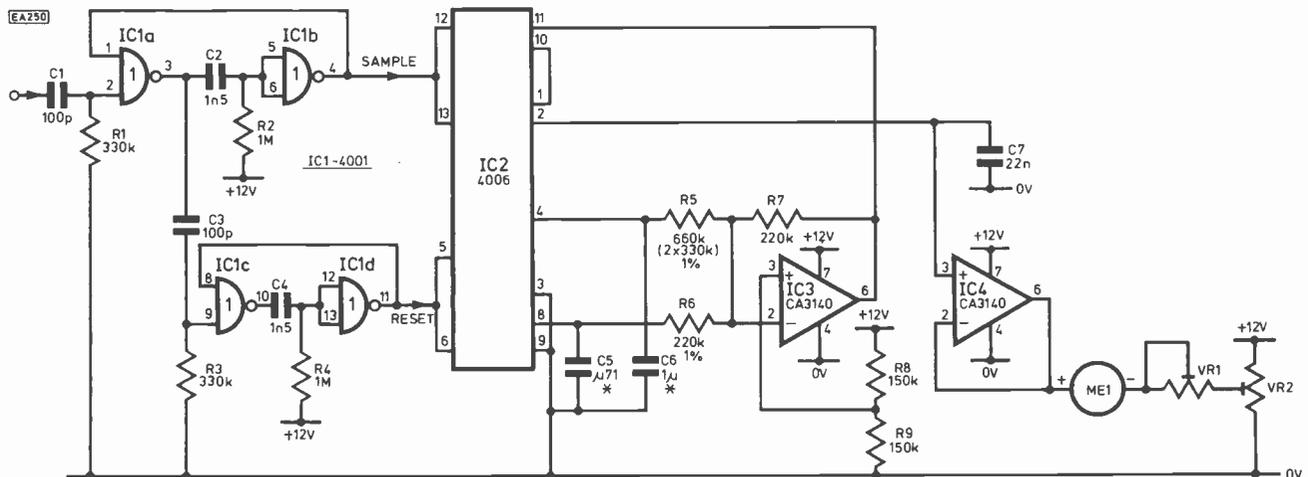

MOST low frequency measurements, e.g. the human pulse rate, involve a compromise between a slow response and a pulsating output. This can be avoided by calculating the reciprocal of the interval between pulses. Done digitally, this is elegant, but costly enough in itself to increase the pulse rate!

My simple analogue circuit gives excellent linearity over a 4:1 or more frequency range. It relies on the fact that a CR charge will approximate a reciprocal. Combining two charge currents of different time constants in the right ratio gives a good approximation to linearity.

Here, R5, R6, C5 and C6 form the two

RC networks, C5 and C6 charging towards an aiming potential  $V_{DD} \times R9/(R8 + R9)$ .

IC3 produces an output voltage proportional to the sum of the currents in R5 and R6. This is sampled and held, to drive the meter via IC4, each time a positive going pulse appears at the input to IC1a. Each such input pulse develops, via IC1a to d, a sample pulse for this purpose, followed by a reset pulse to discharge C5 and C6 and recommence the cycle.

The 4 channel switch IC2 performs the discharge and sampling. Sampling is via two gates in series to maximise leakage resistance. C8, which provides a double in-

tegrator in the open gate condition via the gate leakage resistances, is not needed at pulse rates higher than 30 per minute.

VR1 and 2, which control sensitivity and zeroing, can with many meter scales be set up for a direct indication of frequency.

The ratios  $R5/R6$  and  $R5C5/R6C6$  should ideally to correct within about 1%.

The supply voltage is not critical but should be reasonably stable since it affects sensitivity to some extent.

C. J. Collins,  
Letchworth,  
Herts.



## ENVELOPE DIFFERENTIATOR

MOST monophonic lead line synthesisers have provision for modulation of the VCOs by other oscillators to give vibratos and trills, but few use the ADSR envelope output because of the difficulty in tuning caused by sustained portions of the envelope. The circuit described here converts an ADSR envelope into an AD envelope, giving a 'chirp' at the beginning of every new envelope.

Capacitor C1 'differentiates' the changing envelope voltages, whilst diodes D1

and D2 ensure that only negative going AD envelopes reach the VCOs. VR1 controls the depth of VCO modulation. Rx is a resistor chosen to give acceptable maximum levels of modulation. For use in the PE Minisonic suitable values range from 100k to 470k, depending on individual tastes.

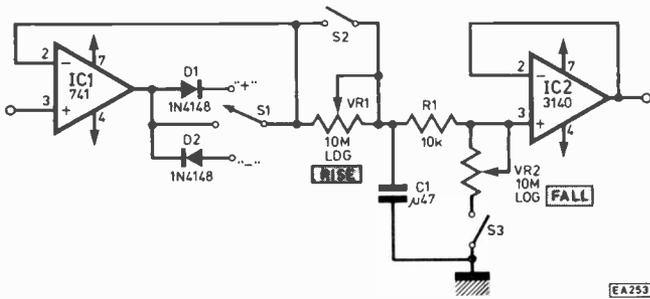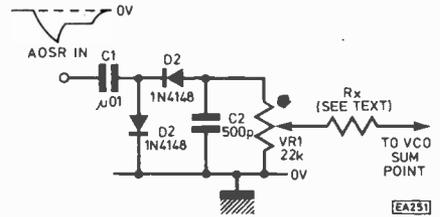Martin Russ,  
Fallowfield,  
Manchester.



## SYNTH PROCESSOR

S3 are closed and VR2 is set to its minimum value, the circuit acts as a voltage follower.

There are many applications of this circuit. In a voltage-controlled synthesiser, the lag processor and voltage follower are useful control-voltage modifiers, using the peak hold with a keyboard voltage can give unusual effects such as unidirectional portamento, where the glide speed varies with the direction of playing on the keyboard. For low frequency a.c. applications the circuit can be used as a rectifier and filter unit with the output being proportional to the 'average' of the input in a similar manner to the operation of an envelope follower.

Martin Russ,  
Fallowfield,  
Manchester.

THIS circuit was originally designed for use in a voltage-controlled synthesiser as a multi-purpose voltage processor, but it can be applied to many other uses.

The circuit consists of a peak detector made up of IC1 and the associated components, and a memory circuit made up of IC2 and the associated components.

Switches S2 and S3 are used to control the operation mode of the circuit. Controls

VR1 and VR2 control the rate of change of the output voltage. Switch S1 controls the direction in which the circuit holds the peaks of the input voltage.

With S2 open the rise time of the circuit is determined by VR1 and the circuit now behaves as 'lag' circuit or integrator. If S3 is closed the fall time of the circuit is determined by VR2. S3 is opened for a memory hold or peak detector function. If S2 and

## TVC FOR SYNTHS

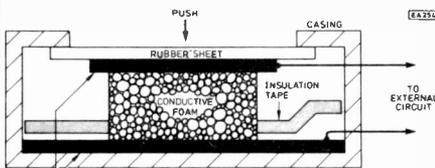


Fig. 1. ▲

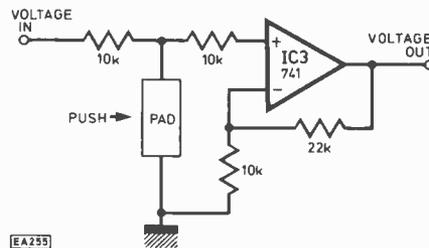


Fig. 2. ▲

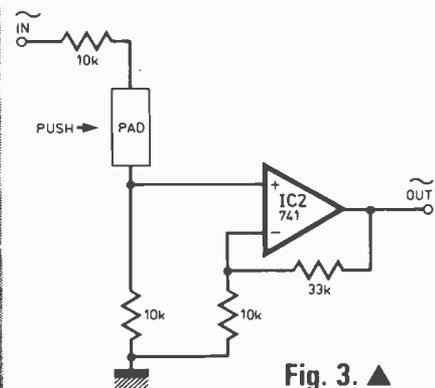


Fig. 3. ▲

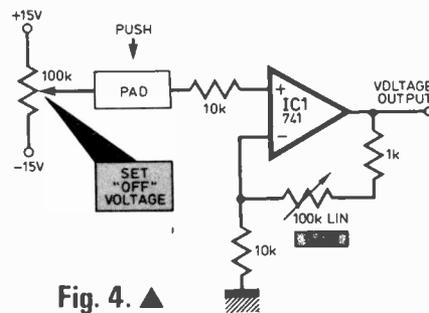


Fig. 4. ▲

COMMERCIAL performance synthesisers use many forms of man/machine interface. Of these, the pitch-pad is rarely seen on home produced synthesisers. The touch voltage control (TVC) pad idea to be applied to almost any synthesiser.

The basis of the circuit is the 'conductive' black foam used to pack CMOS i.c.s. By using a piece about 3 cms square, sandwiched between two metal sheets, it is possible to make a resistor whose value changes with pressure, from about 100k or more down to about 200 ohms.

Mechanical and electrical construction of the TVC pad is shown in Fig. 1. The prototype was constructed in a PP3 battery case from which the insides were removed and a rectangular hole cut in the side.

The pad can be used to replace any resistor in the control circuitry of the synthesiser, a few ideas are given in Figs. 2, 3 and 4. These are a voltage controller, volume control and attenuator respectively.

Martin Russ,  
Manchester.

- ORDER BY POST OR TELEPHONE WITH BARCLAYCARD/ACCESS
- ELECTRONIC TEST EQUIPMENT SPECIALISTS
- ALL PRICES INCLUDE VAT


# AUDIO ELECTRONICS

- ALL MODELS ON DISPLAY
- RETAIL - MAIL ORDER - EXPORT - INDUSTRIAL
- OPEN SIX DAYS A WEEK
- CALL IN AND SEE FOR YOURSELF

ALL PRICES INCLUDE VAT
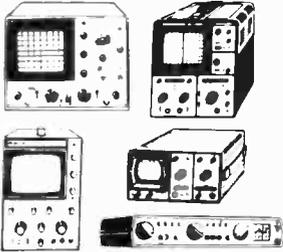
## SCOPES

A range of Scopes in stock from 5mHZ Single Trace to 50mHZ Dual Trace. Mains and Battery/Mains Portables. Many on demonstration.



HAMEG ● TRIO ● LEADER ● SINCLAIR ● HITACHI

### SINGLE TRACE (UK c/p etc £2 50)

Hm 307-3 10mHZ, 5mV, 6 x 7cm display plus component Test	£158-78
C01303D 5mHZ, 10mHZ, 7 x 7cm display	£109-25
SC110 10mHZ Battery portable, 10mV, 3.2 x 2.6cm display (Optional case £8-86, Nicads £8-63, Mains unit £4-00)	£158-95
*LB0512A 10mHZ, 10mV, 5" display	£195-50
CS1559A 10mHZ, 10mV, 5" display	£232-00
*V151 15mHZ, 1mV, 5" display	£241-50

### OPTIONAL PROBES (ALL MODELS)

X1 £6-50, X10 £8-50, X100 £12-95, X1-X10 £10-95

\*PRICES INCLUDE FREE PROBE(S)

### DUAL TRACE (UK c/p etc £3 50)

CS1562A 10mHZ, 10mV, 5" display	£267-00
CS1575 5mHZ, 1mV, 5" display	£284-00
Hm 312-8 20mHZ, 5mV, 8 x 10cm display	£253-00
CS1566A 20mHZ, 5mV, 5" display	£339-00
*LBO3085 70mHZ, 2mV, 5 x 6.3cm display. Battery/Mains portable, built in Nicads	£482-00
Hm 412-4 20mHZ, 5mV, 8 x 10cm display plus Sweep Delay	£399-50
CS1577A 35mHZ, 2mV, 5" display	£478-00
CS1830 30mHZ, 2mV, 5" display plus Sweep Delay/Line/New Model	£569-00
Hm 512-8 50mHZ, 5mV, 10 x 8cm display, Delay Sweep	£667-00
*LB0514 10mHZ, 1mV (5mV), 5" display	£294-00
*V152 15mHZ 1mV 5" display	£326-60
*V302 30mHZ 1mV 5" display	£447-35
*V550 50mHZ 1mV 10 x 8cm Delay sweep + 3 channel display	£799-25

## GENERATORS (UK C-P £1.75)



TRIO ● LEADER ● CSC ● SINCLAIR ● LEVELL

### RF

A range of signal generators to cover audio RF and pulsing. Mains operated (TG series battery)	
SG402 100KHZ-30mHZ with AM modulation	£68-00
LSG16 100KHZ-100mHZ (300mHZ on Harmonics)	£63-25
SG2030 250KHZ-100mHZ low cost range	£46-95
ARF300 18HZ-200mHZ Low cost range	£76-95

### PULSE

2001 1HZ-100KHZ (Function)	£89-70
TG105 5HZ-5mHZ	£92-50
4001 0 5HZ-5mHZ	£109-25
TT100 (Function 10KHZ)	£90-85

### AUDIO (All sine/square)

AG202A 20HZ-200KHZ	£69-00
LAG26 20HZ-200KHZ	£73-60
AG203 10HZ-1mHZ Sine/Square	£126-75
LAG120A 10HZ-1mHZ	£146-00

## LOGIC PROBES/ MONITORS

Logic probes indicating high/low, etc. states that scopes can miss. All circuit powered for all IC's.


LP3 50 mHZ logic probe	£55-95
LP1 10 mHZ logic probe	£35-50
LP2 1 1/2 mHZ logic probe	£19-95
LM1 Logic monitor	£51-00
LDP 50 mHZ Logic probe with case	£51-00
Also in stock range of Protoboard kits and breadboards.	
<b>PRO MULTIMETERS</b>	
M1200 100K/Volt 30 range plus AC/DC 15 amp	£67-00
K1400 20K/Volt 23 range large scale AC/DC 10 amp	£79-95
M1500 20K/Volt 42 range plus AC/DC 10 amp	£53-50
(UK c/p £1-20)	
K200 38 range FET 10m ohm input 20Hz to 30 MHz	£95-00
(UK c/p £1-50)	

## SWR/FS AND POWER METERS

Range in stock covering up to 150mHZ and up to 1K watt power. PL239 sockets. 250uHZ Grid Dip.	
SWR9 SWR/S 3-150mHZ	£9-50
SWR50 SWR/Power meter 3 1/2-150mHZ 0-1000 watts	£13-95
110 SWR/Power 1 1/2-144mHZ 0/10/100 watts	£11-50
171 As 110 Twin meter plus FIS	£14-50
Plus large range of BNC/PL259/etc leads / plugs / adaptors / connectors always in stock.	
176 SWR Power FS 1 1/2-144mHZ, 5-50 watt	£16-60
KDM6 Grid Dip 1 1/2-250mHZ	£38-50

## DIGITAL MULTIMETERS

KAISE ● SINCLAIR ● LASCAR ● THURLBY

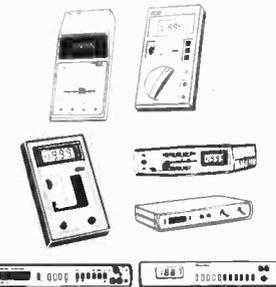

### HAND HELD (UK post etc 85p)

TM352 3 1/2 Digit LCD plus 10ADC and Hfe checker	£54-95
TM354 3 1/2 digit LCD 2A AC/DC	£46-94
ME502 3 1/2 Digit LED plus 10A DC and Hfe checker	£43-95
LM2001 3 1/2 Digit LCD 2 amp AC/DC 0-1%	£51-70
6200 3 1/2 Digit LCD 0-2A AC/DC, Auto range	£45-95
6220 As 6200 plus 10A AC/DC	£55-95
6100 As 6200 plus Cont. test/ range hold	£69-95
6110 As 6100 plus 10A AC/DC	£85-95
GL35C 3 1/2 digit LCD 1A AC/DC with case	£37-50


A range of LED and LCD Bench and Hand DMM's battery operated with optional Mains Adaptors—some with optional Nicads. All supplied with batteries and leads.

### BENCH PORTABLES (UK c/p £1-00)

DM235 3 1/2 Digit LED 21 ranges, 0-5% AC/DC 2A	£60-38
DM350 3 1/2 Digit LED 34 ranges, AC/DC 10A	£83-38
TM353 3 1/2 Digit LCD AC/DC 2 amp	£96-60
TM351 3 1/2 Digit LCD AC/DC 10 amp	£113-85
LM100 3 1/2 Digit LCD AC/DC 2 amp	£86-50
DM450 4 1/2 Digit LED 34 ranges, AC/DC 10 amp	£113-85
(DM series options: Carry case £8-86, Nicads £8-63, Mains adaptor £4-00)	


## MULTIMETERS

(UK post etc 75p)

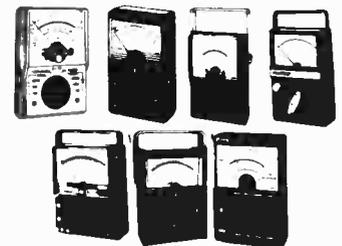

KRT101 1K/Volt 10 range pocket	£4-60
ATM1/LTI 1K/Volt 12 range pocket	£5-98
NH55 2K/Volt 10 range pocket	£6-50
ATI 2K/Volt 12 range pocket de luxe	£7-75
NH56 20K/Volt 22 range pocket	£11-95
YN360TR 20K/Volt 19 range pocket plus hfe test	£13-50
AT1020 20K/Volt 19 range de luxe plus hfe test	£16-95
7081 50K/Volt 36 range plus 10 amp DC	£20-80
TR303TR 20K/Volt + 12A DC + HFE test	£15-95
AT20 20K/Volt 21 range de luxe plus 10A DC and SKV DC	£21-95
AT205 50K/Volt 21 range de luxe plus 10A DC	£24-95
7080 20K/Volt 26 range large scale, 10A DC plus 5KV AC/DC	£26-95
AT2050 50K/Volt 18 range de luxe plus hfe test	£28-50
AT210 100K/Volt 21 range de luxe 12A AC/DC	£29-95
360TR 100K/Volt 23 range plus hfe checker and AC/DC 10 amps	£34-95

## FREQUENCY COUNTERS

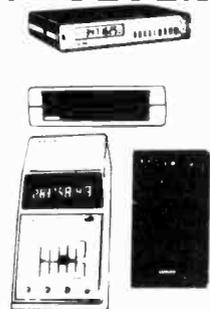

Portable and Bench LCD and LED Counters up to 600mHZ. Prices include batteries and leads.

### HAND HELD (UK post etc 85p)

PFM200 20HZ to 200mHZ 8 Digit LED	£52-27
MAX50 100HZ to 50mHZ 6 Digit LED	£61-00
MAX550 30KHZ to 550mHZ 6 Digit LED	£106-00

### BENCH PORTABLES (UK c/p £1-00)

MAX100 8 Digit LED 5HZ to 100mHZ	£89-00
TF200 8 Digit LCD 10HZ to 200mHZ	£166-75
7010A 9 Digit LED 10HZ to 600mHZ	£169-00
200SPC 6 Digit 100mHZ LED built into 0-002HZ to 5-5mHZ pulse generator	£437-00
TP600 600mHZ Prescaler for TF200	£43-13
TF040 8 digit LCD 20 MHz	£126-50

CSC ● SINCLAIR ● SPC ● OPTO ELECTRONICS

## SOLDERLESS BREADBOARD AND KITS

EXP350	£3-45
EXP300	£5-95
EXP650	£3-95
EXP600	£6-50
<b>KITS</b>	
PB6	£9-95
PB100	£12-95
PB101	£17-95
(UK c/p - EXP's 30p. KITS 55p)	

## MINI DRILLS AND KITS

(9-12 Volt 1/4" chucks)	
Small Drill plus 3 collets	£7-25
Medium Drill plus 3 collets	£10-50
Small Drill plus 20 tools	£14-95
Medium Drill plus 20 tools	£17-95
Mains Drill	£13-95
Mains Drill plus 20 tools	£21-50

CHOOSE FROM THE UK'S LARGEST SELECTION

Stockists of electronic equipment, speakers/kits, PA equipment plus huge range of accessories ● UK carriage/packing as indicated ● Export - prices on request ● All prices correct at 1.2.81 E & OE ● All prices include VAT.

**AUDIO ELECTRONICS** Cubegate Limited  
301 EDGWARE ROAD, LONDON, W2 1BN, ENGLAND. TELEPHONE 01-724 3564

OPEN SIX DAYS A WEEK




**FREE CATALOGUE!**  
Send large SAE (17/5p UK) Schools, Companies, etc. free on request.

## JOIN THE KEYBOARD REVOLUTION!

With these amazing new CASIOTONE instruments.

A remarkable new concept in electronic keyboards using a totally new technology. Pitch, timbre and harmonics of a variety of instruments have been measured, digitalised and stored in electronic chip memory for faithful and exciting reproduction.

### CASIOTONE 401

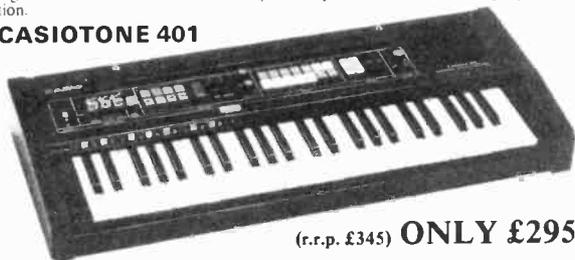

(r.r.p. £345) **ONLY £295**

**Polyphonic.** 8 note playing of 14 instruments and sounds over 4 octaves.  
**Rhythm accompaniment.** 16 different rhythms with full-in auto-rhythm.  
**Casio Auto Chord.** Allows one finger accompaniment. Just press a key with a single finger and play major, minor and seventh chords and bass accompaniment automatically. Combines with auto-rhythm for professional sounds.  
**Vibrato, delayed vibrato, sustain and hold** are incorporated in the at-a-glance, simple to use operational panel. Pitch control makes tuning easy with groups.  
**Compact** 4 1/2 x 31 1/2 x 12 1/2 inches with integral amplifier and speaker. The lightweight (28.2lb) allows playing anywhere there is an A.C. socket. **Stand £39.**  
**301.** Similar to above but without Auto Chord, sustain and hold. **£245.**

### CASIOTONE MT-30




(r.r.p. £115) **ONLY £95**

**Polyphonic** playing of 22 instruments and sounds over 3 octaves.  
**4-position sound memory** lets you switch between pre-selected sounds without pause.  
**Built-in vibrato and sustain functions** greatly enhance the overall musical effect.  
**Compact** 2 1/2 x 22 1/2 x 6 1/2 inches, with built-in amplifier and loudspeaker.  
**Battery/mains** power source and light weight (6lb) allows playing anywhere.
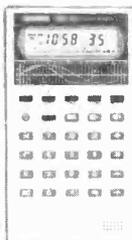
## BIOLATOR & WATCH

Clock, calendar, two alarms, countdown alarm, stopwatch, time memory, three date memories. Calculator with date calculations and BIORHYTHM CALCULATIONS.

Forecast your physical, emotional and intellectual performance potential. Chart your peak, ebb and critical days and reschedule to avoid mistakes. 2 silver oxide batteries last approx. 1 year.  
 Dims: (x2 7 1/16 x 4 1/4 inches).  
 Supplied with leatherette wallet.



OTHER CASIO CALCULATORS. Lowest prices\*. Send for details.

## BEST SELLING CASIO ALARM CHRONOGRAPHS



AA81

All have 4 year auto calendar, alarm, countdown alarm, hourly chimes, stopwatch, night light, long-life lithium battery, water resistant cases and mineral glass real quality watches.  
**LCD analogue/digital**  
 AA 81 (Chrome). AA 81G (Gold) **£49.95.** AA 82 (S/-) **£39.95.**  
**12 melody alarms and date memories**  
 M 12 (Resin case/strap) **£24.95.** M 1200 (S/s) **£29.95.**  
**100 metre water resistant**  
 W 100 (Resin case/strap) **£19.95.** W 150C (S/s case/resin strap) **£25.95.** W 1508 (all s/s) **£32.50.**

**CASIO watches. Lowest prices\*.**  
 Send for details.  
**SEIKO selected watches. Send for details.**

SEND 20p (postage) for details of Casiotone, Casio and Seiko products.

### \*PRICES

We will beat lower advertised price by 5% providing we still make a profit! Prices include VAT, P.&P. Offers subject to availability.

Send your cheque, P.O. or phone your ACCESS or B'CARD number to:

**TEMPUS**

Dept. PE, Beaumont Centre, 164-167 East Rd, Cambridge CB1 1DB. Tel: 0223 312866.

## DISCO LIGHTING KITS!!!

First class constructional projects, c/w glass fibre P.C.B.'s & full instructions. No extra components needed to make a top rate working unit.

**LK1** 3 channel sound-to-light.  
**£9.90** 300 w/channel 1v - 100w input

**LK3** 2kW slider dimmer  
**£8.90** suitable for clubs/pubs.  
 A professional unit c/w face plate.

**LK2** 3 channel 3kW  
**£17.90** zero voltage firing  
 200mV - 100 watts input.

**LK4** 4 channel 4kW  
**£16.50** audio - forward/reverse auto - two speed ranges.

ALL KITS C/W

circuit, comprehensive instructions & full parts guarantee



Carriage on above 70p

Suitable case for LK 1/2/4 **£3.50**  
 100w spots ES or BC **£1.50.**  
 Coloured pigmy lamps **65p.**


## UNREPEATABLE HI-FI BARGAIN

### 3 WAY LOUDSPEAKER KIT C/W BAFFLE (pre-cut)

Comprises:

- ★ 6 1/2" linen surround bass unit
  - ★ 5" mid-range unit
  - ★ 3" tweeter
  - ★ 3 way crossover, fixing screws & baffle
  - ★ 20 watts handling capability.
- Full instructions provided  
 Must be heard to be believed!!

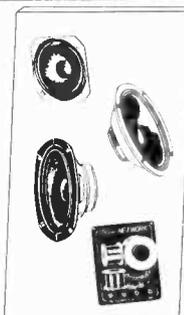**£10.50** or 2 kits for £20. Carr. £1 per kit.



## SAXON ENTERTAINMENTS

327-333 Whitehorse Rd., Croydon, Surrey CR0 2HS.

(01) 684 8007

Order by phone - Access/Barclaycard/C.O.D.  
 Open Mon. - Sat. 9am - 5pm.



68 LARGER PAGES

The larger Catalogue that means **FREE POSTAGE IN U.K.**

ADDITIONAL DISCOUNTS

KEEN PRICES

GUARANTEED SATISFACTION

GOOD STOCKS  
 GOOD DELIVERY

We Pay Postage

Semi-Conductors • I.C.s • Opto-devices • Rs and Cs in great variety • Pots • Switches • Knobs • Accessories • Tools • Materials • Connectors

**ELECTROVALUE**

**FREE FOR THE ASKING**

ELECTROVALUE LTD. (PE3),  
 28 St. Jude's Road, Englefield Green, Egham, Surrey TW20 0HB.  
 Phone: 33603 (London 87) STD 0784. Telex 264475.  
 NORTHERN (Personal Shoppers Only): 680 Burnage Lane, Burnage, Manchester M19 1NA. Phone (061) 432 4945.


# JOIN UP WITH LITESOLD

New 'L' Series soldering irons, designed to latest safety standards. Outstanding performance, lightweight and easy maintenance. Heating elements enclosed in stainless steel shafts and insulated with mica and ceramic. Non-seize interchangeable bits, 'Copper' or 'Long-Life', fit over heating elements for high efficiency. Non-roll GRP handles and screw-connected 3-core mains leads.

Order direct at these special prices or send 25p for 4-page colour leaflet, or 60p for 16-page colour catalogue.

**Model LC18** General purpose 18 watt iron for virtually all electronics assembly and servicing. Normally 240 volts but also available in 12 and 24 volt. Iron fitted with 3.2mm copper bit: £5.23. Iron with 3 spare bits 1.6, 2.4 and 4.7mm: £7.11

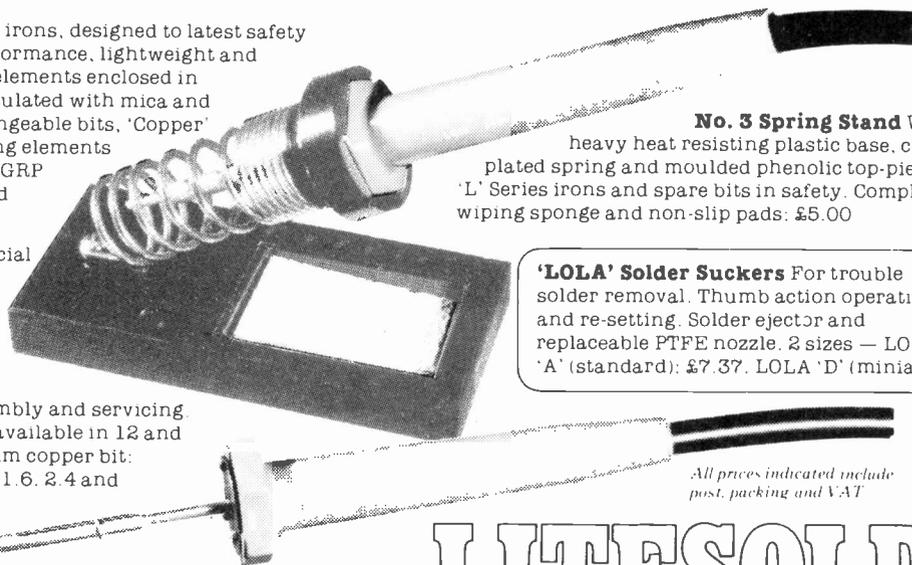**Model LA12** Intended mainly for fine work this 12 watt iron has a slimmer shaft and smaller bits. Normally 240 volts but available in 6, 12 and 24 volts. Iron with 2.4mm copper bit: £5.19. Iron with 2 spare bits 1.2 and 3.2mm: £6.29



**No. 3 Spring Stand** With heavy heat resisting plastic base, chromium plated spring and moulded phenolic top-piece. Holds 'L' Series irons and spare bits in safety. Complete with wiping sponge and non-slip pads: £5.00

**'LOLA' Solder Suckers** For trouble free solder removal. Thumb action operation and re-setting. Solder ejector and replaceable PTFE nozzle. 2 sizes — LOLA 'A' (standard): £7.37. LOLA 'D' (miniature).

All prices indicated include post, packing and VAT

## LITESOLD

LIGHT SOLDERING DEVELOPMENTS LTD

DEPT. PE1, 97-99 GLOUCESTER ROAD, CROYDON, SURREY CR0 2DN. TELEPHONE: 01-689 0574. TELEX 8811945.

**DMM  
BREAKTHROUGH!**



The Incredible 6200

## If you want an Autoranging, Auto Unit Display, 3½ digit LCD DMM.

# For only £45.95

(inc VAT)

## We've got to hand it to you!

Introducing the latest professional state-of-the-art 3½-digit DMM — at really old-fashioned prices! From just an unbelievable £45.95 inc. VAT!

- \* 1mV, 100µA and 0.1Ω resolution!
- \* Measures AC voltage to 600V!
- \* Measures DC voltage to 1000V!
- \* Measures resistance to 2 Megohms!
- \* Low power Ohm ranges!
- \* Displays mV, V and mA!
- \* 0.8% accuracy!
- \* Zero adjustment!
- \* 3 other models too!

This one-off price is so unbelievably low because the A/D converter and display are custom-built. This is a genuine, no corners cut top-spec DMM, that gives you all the features above and 200 hrs continuous battery life on the 3½-digit LCD display auto 'Batt. warning, pair of test leads, batteries, spare fuse and 6 months' guarantee! This offer can't last for ever, so buy now. Remember, a DMM in the hand

**Plus three other DMMs in the range!**

6220 As the 6200, plus 10 Amp AC/DC measurement! ONLY £55.95 inc VAT!

6100 With Continuity check plus 10 Amp AC/DC measurement! ONLY £85.95 inc VAT!

Maclin-Zand Electronics Ltd., 38 Mount Pleasant, London, WC1X 0AP.

I believe you! Please send me the DMMs as marked

\_\_\_\_\_ 6200 @ £45.95 each, inc VAT. Total price £ \_\_\_\_\_  
 \_\_\_\_\_ 6220 @ £55.95 each, inc VAT. Total price £ \_\_\_\_\_  
 \_\_\_\_\_ 6110 @ £85.95 each, inc VAT. Total price £ \_\_\_\_\_

Total cash cheque enclosed £ \_\_\_\_\_  
 Cheques payable to  
 Maclin-Zand Electronics Ltd., please  
 38 Mount Pleasant, London WC1X 0AP  
 Tel. 01-837 1165/01-278 7369



## Maclin-Zand

Making state-of-the-art affordable


ACCESS orders taken. Please write card no. and signature.

ACCESS NO. \_\_\_\_\_  
 Name \_\_\_\_\_  
 Address \_\_\_\_\_  
 \_\_\_\_\_  
 Signed \_\_\_\_\_

To: Maclin-Zand Electronics Ltd., 38 Mount Pleasant, London WC1X 0AP.  
 For overseas orders, please add £2 Europe, £5 outside Europe, to total order value.

PE9
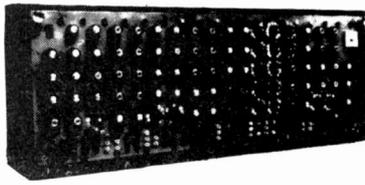
# D.I.Y. KITS FOR SYNTHESISERS, SOUND EFFECTS



**BASIC COMPONENTS SETS** include all necessary resistors, capacitors, semiconductors, potentiometers and transformers. Hardware such as cases, sockets, knobs, keyboards, etc. are not included but most of these may be bought separately. Fuller details of kits PCBs and parts are shown in our lists.

**LAYOUT DIAGRAMS** are supplied free with all PCBs unless "as published".

# PHONOSONICS

MAIL ORDER SUPPLIERS OF QUALITY PRINTED CIRCUIT BOARDS, KITS AND COMPONENTS TO A WORLD-WIDE MARKET

## P.E. MINISONIC MK2 SYNTHESIZER

A portable mains operated miniature sound synthesizer with keyboard circuits. Although having slightly fewer facilities than the large Formant and P.E. synthesizers the functions offered by this design give it great scope and versatility.

Set of basic component kits (excl. KBD R's & tuning pots - see list for options available) and PCBs (incl. layout charts)  
 KIT 3B-25 **£80.14**  
 "Sound Design" booklet **£1.00**

## P.E. 128-NOTE SEQUENCER

Enables a voltage controlled synthesiser to automatically play pre-programmed tunes of up to 32 pitches and 128 notes long. Programs are keyboard initiated and note length and rhythmic pattern are externally variable.

Set of basic comps, PCBs and charts **KIT 7B-7 £35.56**  
 Set of text photocopies **£1.36**

## P.E. 16-NOTE SEQUENCER

Sequences of up to 16 notes may be programmed by the use of external panel controls and fed into most voltage controlled synthesizers.

Set of basic comps, PCBs and charts **KIT 8B-5 £32.10**  
 Set text photocopies **£1.84**

## P.E. STRING ENSEMBLE

A multivoiced polyphonic string instrument synthesiser. Set of basic comps, PCBs & charts

**KIT 77-8 £109.72**

## ELEKTOR PHASING & VIBRATO

Includes manual and automatic control over the rate of phasing & vibrato, and has been slightly modified to also include a 2-input mixer stage.

Set of basic comps, PCB & chart **KIT 70-2 £21.67**  
 Text photocopy **67p**

## ELEKTOR FORMANT SYNTHESIZER

A very sophisticated synthesiser for the advanced constructor who puts performance before price.

Set of basic comps, PCBs (as publ.) **KIT 86-14 £255.45**  
 Set of text photocopies **£7.83**

## ELEKTOR DIGITAL REVERB UNIT

A very advanced unit using sophisticated i.c. techniques instead of mechanical spring lines. The basic delay range of 24 to 90mS can be extended up to 450mS using the extension unit. Further delays can be obtained using more extensions.

Main unit basic comps and PCB (as publ.) **KIT 7B-3 £49.95**  
 Extension unit basic comps and PCB (as publ.) **KIT 7B-4 £39.95**  
 Text photocopy **86p**

## ELEKTOR SEWAR

For use with Elektor Analogue Reverb to give greater flexibility to the reverb effects.

Basic comps, PCB (as publ.) **KIT 101-1 £18.19**  
 Text photocopy **60p**

## ELEKTOR RING MODULATOR

Compatible with the Formant & most other synthesizers.

Set of basic comps & PCB (as publ.) **KIT B7-2 £6.84**  
 Text photocopy **38p**

## ELEKTOR CHOROSYNTH

A 2 $\frac{1}{2}$ -octave Chorus synthesizer with an amazing variety of sounds ranging from violin to cello and flute to clarinet amongst many others. Experienced constructors can readily extend the octave coverage.

Basic comps, PCBs and charts but excl. sw's **KIT 100-8 £44.39**  
 Text photocopy **70p**

## ELEKTOR ANALOGUE REVERB

Using i.c.s instead of spring-lines the main unit has a maximum delay of up to 100mS, and the additional set extends this up to 200mS. May be used in either mono or stereo mode.

Main unit basic component set **KIT 83-4 £29.23**  
 Additional Delay basic components **KIT 83-2 £20.07**  
 PCB (as publ.) to hold both kits included in Kit 83-4  
 Text photocopy **67p**

## ELEKTOR FUNNY TALKER

Incorporates a ring modulator, chopper & frequency modulator to produce fascinating sounds when used with speech & music signals.

Basic comps, PCB (as publ.) **KIT 99-1 £9.60**  
 Text photocopy **40p**

## ELEKTOR FREQUENCY DOUBLER

For use with guitars & other electronic instruments to produce an output one octave higher than the input. Inputs and outputs may be mixed to give greater depth.

Basic comps, PCB (as publ.) **KIT 98-1 £5.48**  
 Text photocopy **20p**

## P.E. SPLIT-PHASE TREMOLO

A simple but effective substitute for a rotary cabinet. The output of an internal generator is phase-split and modulated by an input signal from an electronic guitar or other instrument. Output amplitudes, depth & rate are variable. May be fed to one or two amplifiers.

Basic comps, PCB & chart **KIT 102-3 £17.68**  
 Text photocopy **65p**

## P.E. MINISONIC WAVEFORM CONVERTER

A simple converter that modifies the Minisonic sawtooth waveform to produce triangle and sine outputs. Ideally one should be used with each Minisonic VCO.

Basic comps, PCB & chart **KIT 96-1 £3.98**

## P.E. GUITAR MULTIPROCESSOR

An extremely versatile sound processing unit capable of producing, for example, flanging, vibrato, reverb, fuzz and tremolo as well as other fascinating sounds. May be used with most electronic instruments.

Set of basic comps, PCBs & charts (excl. SWs) **KIT 85-5 £49.23**  
 Set of text photocopies **£2.52**

## P.E. PHASER

An automatically controlled 6-stage phasing unit with integral oscillator.

Basic components, PCB & chart **KIT 88-1 £10.91**  
 2-Notch extension, PCB & chart **KIT 88-2 £6.36**  
 Text photocopy **68p**

## ELEKTOR ELECTRONIC PIANO

A touch-sensitive multiple-voicing piano using the latest integrated circuit techniques for the keying and envelope shaping, and virtually eliminating "bee-hive" noise hitherto inherent in previous electronic pianos.

5-octave set of basic comps and PCBs (as publ.) **KIT 80-9 £149.42**  
 Additional 3-octave extension and basic parts and PCBs (as published) **KIT 80-10 £58.32**  
 Set of text photocopies **£1.81**

## P.E. GUITAR EFFECTS UNIT

Modulates the attack, decay and filter characteristics of a signal from most audio sources, producing 8 different switchable effects that can be further modified by manual controls.

Basic comps, PCB & chart **KIT 42-3 £10.60**  
 Text photocopy **28p**

## P.E. GUITAR OVERDRIVE

Sophisticated versatile fuzz unit incl. variable controls affecting the fuzz quality whilst retaining attack and decay, and also providing filtering. Usable with most electronic instruments.

Basic components, PCB & chart **KIT 56-3 £11.22**  
 Text photocopy **68p**

## P.E. SMOOTH FUZZ

Basic components, PCB & chart **KIT 91-1 £6.52**  
 Text photocopy **55p**

## TREMOLO UNIT

A slightly modified version of the simple P.E. unit. Basic components, PCB & chart **KIT 54-1 £3.74**

## GUITAR FREQUENCY DOUBLER

A slightly modified and extended version of the P.E. unit. Basic components, PCB & chart **KIT 74-1 £5.19**  
 Text photocopy **39p**

## P.E. GUITAR SUSTAIN

Maintains the natural attack whilst extending note duration. Basic components, PCB & chart **KIT 75-1 £6.99**  
 Text photocopy **38p**

## P.E. AUTO-WAH UNIT

Automatically gives Wah or Swell sounds with each note played. Basic components, PCB & chart **KIT 58-1 £10.11**  
 Text photocopy **58p**

## ELEKTOR WAVEFORM CONVERTER

Converts a saw-tooth waveform into sinewave, mark-space saw-tooth, regular triangle, or square-wave with variable mark-space. Basic comps, PCB & chart, but excl. sw's **KIT 67-1 £9.24**

## P.E. SWITCHED TONE TREBLE BOOST

Provides switched selection of 4 preset tonal responses. Basic components, PCB & chart **KIT 89-1 £4.34**  
 Text photocopy **78p**

**NEW MORE INFORMATIVE LIST NOW AVAILABLE**

### ADD: POST & HANDLING

U.K. orders: Keyboards add £2.70 each. Other goods: Under £5 add 50p, under £20 add 75p, over £20 add £1. Recommended insurance against postal mishaps: add 50p for cover up to £50, £1 for £100 cover, etc., pro-rata. Insurance must be added for credit card orders. N.B. Eire, C.I., B.F.P.O. and other countries are subject to higher export postage rates.

### ADD 15% VAT

(or current rate if changed). Must be added to full total of kits, discount post & handling on all U.K. orders. Does not apply to Exports, or photocopies.

**EXPORT ORDERS ARE WELCOME** but to avoid delay we advise you to see our list for postage rates. All payments must be cash-with-order, in Sterling by International Money Order or through an English Bank. To obtain list - Europe send 35p, other countries send 75p. Note that we do not offer a C.O.D. service and that our terms are payment in advance.

**PHONOSONICS · DEPT PE8D · 22 HIGH STREET · SIDCUP · KENT DA14 6EH**

**TERMS: C.W.O., MAIL ORDER OR COLLECTION BY APPOINTMENT (TEL 01-302 6184)**

# AND OTHER PROJECTS

**PHOTOGRAPHS** in this advertisement show two of our units containing some of the P.E. projects built from our kits and PCBs. The cases were built by ourselves and are not for sale, though a small selection of other cases is available.

**LIST**—Send stamped addressed envelope with all U.K. requests for free list giving fuller details of PCBs, kits and other components

**OVERSEAS** enquiries for list Europe—send 35p; other countries—send 75p.



## KIMBER-ALLEN KEYBOARDS AND CONTACTS

**KIMBER-ALLEN KEYBOARDS** as required for many published projects. The manufacturers claim that these are the finest moulded plastic keyboards available. All octaves are C to C, the keys are plastic, spring-loaded, fitted with actuators, and mounted on a robust aluminium frame.

3 Octave (37 notes) **£25.50** 4 Octave (49 notes) **£32.25** 5 Octave (61 notes) **£39.75**

**CONTACT ASSEMBLIES** (gold-clad wire) — 1 required for each KBD note:  
Type GJ — SPCO 33p ea. Type GB — 2 pr N/O 37½p ea.

### P.E. V.C.F.

A voltage controlled filter extracted from P.E. Minisonic project

Basic comps, PCB & chart KIT 65-1 **£8.45**

### P.E. RING MODULATOR

Extracted from P.E. Minisonic project

Basic comps, PCB & chart KIT 59-1 **£6.35**

### WIND & RAIN EFFECTS UNIT

A slightly modified version of the original P.E. unit.

Basic comps, PCB & chart KIT 28-1 **£4.84**

Text photocopy **28p**

### P.E. ENVELOPE SHAPER WITH VCA

Has an integral Voltage Controlled Amplifier, and has full manual control over the A.D.S.R. functions.

Basic comps, PCB & chart KIT 50-1 **£8.03**

Text photocopy **58p**

### P.E. TRANSIENT GENERATOR

An ADSR envelope shaper without VCA, and additionally providing Repeat-triggering enabling a synthesiser to be programmed for mandolin or banjo effects.

Basic comps, PCB & chart KIT 63-2 **£7.62**

Text photocopy **58p**

### P.E. EXTERNAL-INPUT SYNTHESISER-INTERFACE

Allows external inputs such as guitars, microphone etc., to be processed by synthesiser circuits.

Basic comps, PCB & chart KIT B1-1 **£3.90**

### P.E. TUNING FORK

Produces 84 switch-selected frequency-accurate tones with an LED monitor clearly displaying beat-note adjustments.

Set of basic components, incl. power supply, PCBs & charts **£23.32**

Text photocopy **97p**

### P.E. TUNING INDICATOR

A simple 4-octave frequency comparator for use with synthesisers and other instruments where the full versatility of KIT 46 is not required.

Basic components, PCB & chart, but excl. sw. KIT 69-1 **£8.19**

Text photocopy **58p**

### P.E. DYNAMIC RANGE LIMITER

Preset to automatically control sound output levels.

Basic comps, PCB & chart KIT 62-1 **£5.31**

### P.E. CONSTANT DISPLAY FREQUENCY COUNTER

A 4-digit counter for 1Hz to 99kHz with 1Hz sampling rate. Readout does not count visibly or flicker due to blanking.

Basic components, PCB & chart **£31.61**

Text photocopy **78p**

### P.E. 6-CHANNEL MIXER

A high specification stereo mixer with variable input impedances.

Basic components, (excl. sw.'s), and set of PCBs and charts **£64.62**

Extra 2-channel set with PCB **£10.21**

Set of Text photocopies **£1.50**

### STEREO HEADPHONE AMPLIFIER

Extracted from P.E. 6-channel mixer.

Basic components, PCB & chart **£5.68**

Text photocopy **£1.20**

### DIGITAL EXPOSURE UNIT

Controls up to 750 watts in ½ second steps up to 10 minutes, with built-in audio alarm.

Basic components, PCBs & charts **£23.45**

Text photocopy **£1.20**

### P.E. DISCOSTROBE

A 4-channel light show controller giving a choice of sequential, random, or full strobe mode of operation.

Basic components, PCB & chart **£19.37**

Text photocopy **78p**

### RHYTHM GENERATORS

Several available, including programmable 16 beat 64000 pattern, and pre-programmed 15 pattern using either M252 or M253 rhythm chips. A selection of effects instrument circuits is also available.

### P.E. VOICE OPERATED FADER

For automatically reducing music volume during talkover — particularly useful for discos.

Basic components, PCB & chart **£4.37**

Text photocopy **28p**

### P.E. DYNAMIC NOISE LIMITER

Very effective stereo circuit for reducing the hiss found in most tape recordings.

Basic components, PCB & chart **£8.07**

Text photocopy **75p**

# KEELMOOR Quality.. at Keener Prices

### LADIES WATCHES

5 function — Hours, mins, secs, day, date, back light, auto calendar. Only 6mm thick. Elegant matching metal bracelet. Dress **£8.95** Day **£5.95**

**QUARTZ LCD Slim Chronograph.** 11 function. hours, mins, secs, 6 digit-month, date, day of week. 1/100 sec stop watch split and lap modes, back-light. **ONLY £7.95**

**QUARTZ LCD ALARM.** 6 digit hours, mins, secs, day, date. 24-hour alarm with on/off indicator. **ONLY £8.95**

**ONLY £8.95**



**ONLY £8.95**

Send s.a.e. for colour Brochure of 120 other bargains.

**MELODY LCD, Alarm/chronograph plays Yellow Rose of Texas date, stop-watch, dual time. ONLY £14.95**

**ALL WATCHES CARRY A 1 YEAR GUARANTEE.** They come complete with fully adjustable, matching, stainless steel straps and demonstration battery fitted (this battery is not guaranteed). Please add 60p for each spare battery required. Send cheques/P.O.'s, quoting watch/watches required to

**QUARTZ LCD Alarm / Chronograph.** 22 functions. Hours, mins, secs, day, date, month, 1/10 sec stopwatch, split & lap modes, 12 & 24 hour modes, 24 hour alarm. **ONLY £12.95**



PRICES ARE CORRECT AT TIME OF PRESS. E. & O. DELIVERY SUBJECT TO AVAILABILITY.

**PHONOSONICS**



**78 CASTLE STREET, MELBOURNE, DERBY, DE7 1DY**

Please add 50p & p per order.

# Why the Sinclair ZX80 is Britain's best-selling

## Built: £99.95

Including VAT, post and packing, free course in computing, free mains adaptor.

## Kit: £79.95

Including VAT, post and packing, free course in computing.

This is the ZX80. A really powerful, full-facility computer, matching or surpassing other personal computers at several times the price. 'Personal Computer World' gave it 5 stars for 'excellent value'. Benchmark tests say it's faster than all previous personal computers.

Programmed in BASIC – the world's most popular language – the ZX80 is suitable for beginners and experts alike. And response from enthusiasts has been tremendous – over 20,000 ZX80s have been sold so far!

### Powerful ROM and BASIC interpreter


The 4K BASIC ROM offers remarkable programming advantages:

- \* Unique 'one-touch' key word entry: the ZX80 eliminates a great deal of tiresome typing. Key words (RUN, PRINT, LIST, etc.) have their own single-key entry
- \* Unique syntax check. A cursor identifies errors immediately.
- \* Excellent string-handling capability – takes up to 26 string variables of any length. All strings can undergo all relational tests (e.g. comparison)
- \* Up to 26 single dimension arrays.
- \* FOR/NEXT loops nested up to 26.
- \* Variable names of any length.
- \* BASIC language also handles full Boolean arithmetic, condition expressions, etc.
- \* Randomise function, useful for games and secret codes, as well as more serious applications.
- \* Timer under program control.
- \* PEEK and POKE enable entry of machine code instructions.
- \* High-resolution graphics
- \* Lines of unlimited length.
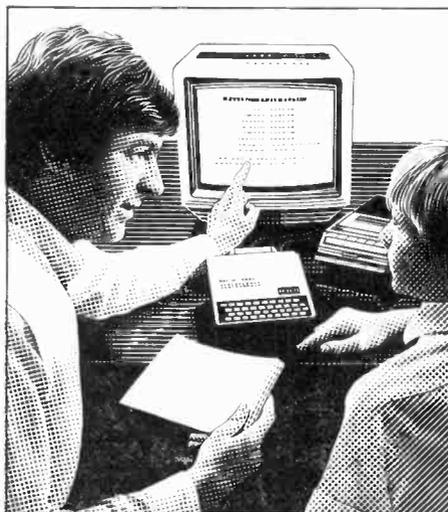
### Unique RAM

The ZX80's 1K-BYTE RAM is the equivalent of up to 4K BYTES in a conventional computer – typically storing 100 lines of BASIC.

No other personal computer offers this unique combination of high capability and low price.



The ZX80 as a family learning aid. Children of 10 years and upwards are quick to understand the principles of computing – and enjoy their personal computer.

### The Sinclair teach-yourself BASIC manual

If the specifications of the Sinclair ZX80 mean little to you – don't worry. They're all explained in the specially-written 128-page book (free with every ZX80). The book makes learning easy, exciting and enjoyable, and represents a complete course in BASIC programming – from first principles to complex programs.


### Kit or built – it's up to you

In kit form, the ZX80 is pleasantly easy to assemble, using a fine-tipped soldering iron. And you may already have a suitable mains adaptor – 600 mA at 9V DC nominal unregulated. If not, see the coupon.

Both kit and built versions come complete with all necessary leads to connect to your TV (colour or black and white) and cassette recorder. Plug in and you're ready to go. (Built versions come with mains adaptor.)

# personal computer.
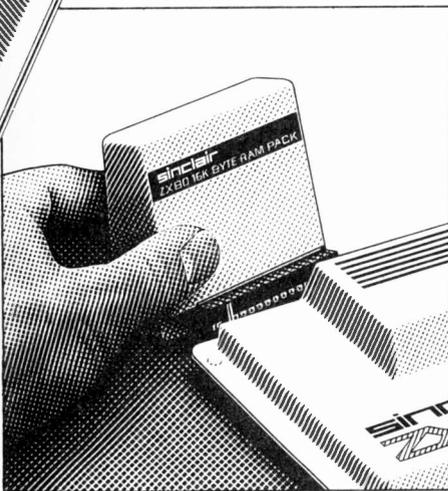
## Now available for the ZX80... New 16K-BYTE RAM pack



### Massive add-on memory. Only £49.95.

The new 16K-BYTE RAM pack is a complete module designed to provide you – and your Sinclair ZX80 – with massive add-on memory. You can use it for those really long and complex programs – or as a personal database. (Yet it can cost as little as half the price of competitive add-on memory for other computers.)

For example, you could write an interactive or 'conversational' program to show people what your ZX80 can do. With 16K-BYTES of RAM, they could be talking to your computer for hours!

Or you can store a mass of data – perhaps in a fairly simple program – such as a name and address list, or a telephone directory.

And by linking a number of separate programs together into one giant, but modular, program, you can achieve the same effect as loading several programs at once.


We're also confident that it won't be long

before you can buy cassette-based software using the full 16K-BYTE RAM. So keep an eye on the personal computer magazines – and brush up your chess perhaps!

The RAM pack simply plugs into the existing expansion port on the rear of the ZX80. No wires, no soldering. It's a matter of seconds and you don't need another power supply. You can only add one RAM pack to your ZX80 – but with 16K-BYTES who could want more!
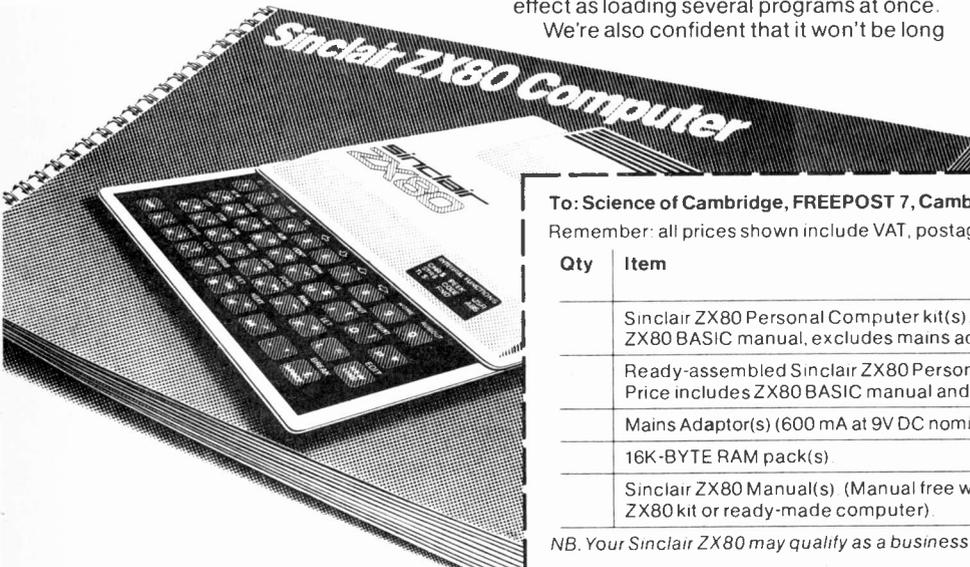
### How to order

Demand for the ZX80 exceeds all other personal computers put together! So use the coupon to order today for the earliest possible delivery. All orders will be despatched in strict rotation. We'll acknowledge each order by return, and tell you exactly when your ZX80 will be delivered. If you choose not to wait, you can cancel your order immediately, and your money will be refunded at once. Again, of course, you may return your ZX80 as received within 14 days for a full refund. We want you to be satisfied beyond all doubt – and we have no doubt that you will be.



To: Science of Cambridge, FREEPOST 7, Cambridge CB2 1YY.

Remember: all prices shown include VAT, postage and packing. No hidden extras. Please send me

Qty	Item	Code	Item price £	Total £
	Sinclair ZX80 Personal Computer kit(s). Price includes ZX80 BASIC manual, excludes mains adaptor	02	79.95	
	Ready-assembled Sinclair ZX80 Personal Computer(s). Price includes ZX80 BASIC manual and mains adaptor	01	99.95	
	Mains Adaptor(s) (600 mA at 9V DC nominal unregulated)	03	8.95	
	16K-BYTE RAM pack(s)	18	49.95	
	Sinclair ZX80 Manual(s) (Manual free with every ZX80 kit or ready-made computer).	06	5.00	

NB. Your Sinclair ZX80 may qualify as a business expense

**TOTAL: £**

I enclose a cheque/postal order payable to Science of Cambridge Ltd for £ \_\_\_\_\_  
Please print

Name: Mr/Mrs/Miss \_\_\_\_\_

Address \_\_\_\_\_

**FREEPOST – no stamp needed.**

PRE04

# sinclair ZX80

Science of Cambridge Ltd.

6 Kings Parade, Cambridge, Cambs., CB2 1SN.  
Tel: 0223 311488.



NOW

# DOUGLAS TRANSFORMERS FROM TITAN

NEW FRANCHISE AT FANTASTIC PRICES - EX STOCK

WE GUARANTEE THESE PRICES TO BE UNBEATABLE ANYWHERE!!

12/24V RANGE PRI 220/240V					15/30V RANGE PRI 220/240V					25/50V RANGE PRI 120/220/240V					30/60V RANGE PRI 120/220/240V					
SEC. 0 12V 24V					SEC. 0V 12V 15V 0V 5V 9V 15V					SEC. 0V 20V 25V 0V 8V 15V 25V					SEC. 0V 24V 30V 0V 10V 15V 30V					
VOLTS 12=1-48 0-48					VOLTS AVAILABLE 3=15-0-15					VOLTS OUT 5=25-0-25					VOLTS 6=30-0-30					
TYPE	amps	price	p-p		TYPE	amps	price	p-p		TYPE	amps	price	p-p		TYPE	amps	price	p-p		
	12v	24v	£	£		15v	30v	£	£		25v	50v	£	£		30v	60v	£	£	
242	0.3	0.15	1.70	0.40	112	1	0.50	2.47	0.95	102	1	0.50	2.88	1.43	124	1	0.5	2.92	1.43	
213	1	0.50	2.32	0.70	79	2	1.0	3.16	0.95	103	2	1.0	3.60	1.43	126	2	1	5.78	1.43	
71	2	1	2.51	0.90	3	4	2	5.64	1.43	104	4	2	7.04	1.73	127	4	2	7.13	1.73	
18	4	2	3.24	1.43	20	6	3	6.59	1.73	105	6	3	8.33	1.90	125	6	3	10.73	1.90	
68	3	1.5	3.15	1.43	21	8	4	7.80	1.73	106	8	4	11.18	1.90	123	8	4	12.28	2.20	
85	5	2.5	5.52	1.43	51	10	5	9.68	1.90	107	12	6	14.79	2.20	40	10	5	15.55	2.20	
70	6	3	6.26	1.43	117	12	6	10.97	2.05	118	16	8	20.49	2.55	120	12	6	17.72	2.35	
108	8	4	7.36	1.73	88	16	8	14.65	2.20	119	20	10	24.52	2.55	121	16	8	25.09	2.65	
72	10	5	8.05	1.65	89	20	10	16.93	2.35	109	24	12	29.39	3.50	122	20	10	29.07	4.00	
116	12	6	8.57	1.90	90	24	12	18.84	2.55					189	24	12	33.51	4.60		
17	16	8	10.53	2.05	91	30	15	21.56	2.65											
115	20	10	13.69	2.05	92	40	20	30.08	3.50											
187	30	15	17.62	2.45																

48/96V RANGE PRI 120/220/240V					AUTOTRANSFORMERS 240/220-115V					CASED AUTOTRANSFORMERS					LINE ADJUSTMENT AUTOTRANSFORMERS				
SEC. 0V 36V 48V 0V 36V 48V					SEC. 0V 115V 220V 240V					240V LEAD IN 115V 2PIN SOCKET OUT					0 200 210 220 230 240 250				
VOLTS 12=148 0-48																			
TYPE	amps	price	p-p		TYPE	va	price	p-p		TYPE	va	price	p-p		TYPE	va	price	p-p	
	48v	96v	£	£		25	65	3.82	1.10		56W	20	5.52	0.58		415C	50	2.13	0.58
430	1	0.5	4.14	1.43	64	80	4.40	1.10		64W	80	7.63	1.43		416C	100	3.13	1.10	
431	2	1	7.22	1.73	4	150	5.64	1.43		4W	150	9.63	1.73		417C	200	3.65	1.43	
432	4	2	11.87	2.05	69	250	7.13	1.73		69W	250	11.98	1.90		418F	350	5.63	1.43	
433	6	3	14.77	2.20	53	350	8.97	1.90		67W	500	18.67	2.20		419F	500	6.13	1.73	
434	8	4	18.43	2.45	67	500	11.09	2.20		84W	1000	26.90	2.65		420E	750	7.60	1.90	
435	10	5	26.16	2.65	83	750	12.42	2.20		73W	3000	69.18	8.00		421F	1000	10.55	2.05	
436	12	6	32.75	4.00	84	1000	16.88	2.65											
437	16	8	35.77	4.60	95	2KVA	31.26	4.00											
					73	3	61.27	4.75											
					57	5	87.42	6.60											
					101	10	159.45	13.00											

MAINS ISOLATORS (SAFETY SCREEN)					MAINS ISOLATORS (SAFETY SCREEN)					MAINS ADAPTORS				
PRI 120/220/240V SEC 60V 55V 0V 55V 60V 60V 55V 0V 55V 60V					PRI 380/416/480V SEC 60V 55V 0V 55V 60V 60V 55V 0V 55V 60V					13 amp plug in type. Reversible spider jack lead.				
TYPE	va	price	p-p		TYPE	va	price	p-p		TYPE	va	price	p-p	
		£	£				£	£		100	6-7.5-9v	250	3.85	0.58
149F	60	7.35	1.73		243F	60	7.35	1.43		Regulated	300	4.70	0.58	
150F	100	8.61	1.73		244F	100	8.61	1.73						
151F	200	12.15	2.05		245F	200	12.15	2.05						
152F	250	14.75	2.20		246F	250	14.75	2.20						
153F	350	18.22	2.55		247F	350	18.22	2.55						
154F	500	22.70	2.65		248F	500	22.70	2.65						
155F	750	32.08	7.00		249F	750	32.08	7.00						
156F	1000	41.26	7.00		250F	1000	41.26	8.00						

SEND TODAY 50p (REFUNDABLE WITH FIRST ORDER) FOR CATALOGUE  
**TITAN TRANSFORMERS AND COMPONENTS**  
 CENTRAL HALL CHAMBERS GRIMSBY S. HUMBERSIDE  
 MAIL ORDER ONLY - PRICES INCLUDE 15% VAT

## AITKEN BROS

35, High Bridge, Newcastle upon Tyne  
 Tel: 0632 26729



**EXP300**



**PB6 Kit**

**EXP300**  
550 contacts with two 50-point BUS bars. Size 152x53mm. £6-95.


**PROTO-BOARD 6 KIT**  
630 contacts, four 5 way binding posts, accepts up to 6 14 pin DIPs. £10-98.

**CSC LOGIC PROBES**  
**LP-2 ECONOMY PROBE**  
 Min. pulse width 300 nanoseconds, 300 KΩ input impedance, tests circuits up to 1.5MHz. Detecting pulse trains or single-shot event in TTL, DTL, HTL, and CMOS circuits. £20-95.  
**LP-1 Memory Probe** £35-85  
**LP-3 High Speed Memory Probe** £56-75  
 CSC catalogue available. Please send S.A.E.

**CALSCOPE SUPER 6 £186-30**  
 A portable single beam 6MHz bandwidth oscilloscope with easy to use controls. High gain to 10 mv/cm and wide time base range from 1µs to 100 ms/cm. Full specification to request. Please send S.A.E. Professional scopes you can afford.

**CALSCOPE SUPER 10 £251-85**  
 A dual trace 10MHz instrument of the very highest performance and quality. It has an accuracy of 3% which is achieved by the use of built-in stabilised power supplies which keep the trace rock steady over a wide range of mains fluctuations. Full specification on request. Please send S.A.E.

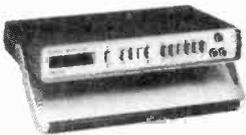**SINCLAIR LOW POWER PORTABLE OSCILLOSCOPE SC110 £159.85**  
 The SC110 has a 10MHz bandwidth and sensitivity down to 10mV per division. Full trigger facilities are provided, including bright line, auto with TV line and frame positions. Please send for full spec. and illustrated brochure.



**SINCLAIR DM350 £83-95**  
**SINCLAIR DM450 £114-95**  
 Size 255x148x40mm  
 DM350 3½ digit display DM450 4½ digit display. Both provide six functions in 34 ranges. D.C. voltage 10µV to 1200V (100µV on DM350) A.C. voltage 100µV to 750V. D.C. current 1nA to 10A. A.C. current 1nA to 10A resistance 10mΩ to 20MΩ (100mΩ opt DM350). Accessories for DM350 & 450 as for DM235 below. Full spec. on request. Please send S.A.E.

**Sinclair PFM200 frequency meter**  
 Size 157x76x32mm.  
 Range 20Hz to 200MHz. Accessories and illustration as for PDM35 below. £57-95.

**SINCLAIR PDM35 DIGITAL POCKET MULTIMETER**  
 DC volts (4 ranges) 1mV to 1000V AC volts 1V to 500V DC current (6 ranges) 1nA to 200mA. Resistance (5 ranges) 1Ω to 20 MEGΩ. PRICE £39.95 AC Adaptor £4-25 de luxe padded carrying case £1-95 MN 1604 Battery £1-28.  
 Size 157x76x32mm.

**SINCLAIR DM235 BENCH-PORTABLE DIGITAL MULTIMETER.**  
 DC volts (4 ranges) 1mV to 1000V AC volts (4 ranges) 1MV to 750V AC & DC current 1µa to 1000MA Resistance (5 ranges) 1Ω to 20 MEG Ω. PRICE £60-98. Carrying case £8.95. AC adaptor/charger £4-25. Rechargeable Battery Pack. £8-95.  
 Size 255x148x40mm.

**PANEL METERS**  
 DIMS 60MM x 45MM. 50µ amp, 100µ amp 1MA, 5MA 10MA 50MA, 100MA, 500MA, 1 amp, 2 amp, 25V dc, 30V dc, 50V AC, 300V ac, 'S' 'VU' 50-0-50µa, 100-0-100µa, 500-0-500µa. PRICE £5-95.

**DESOLDERING TOOL SUCTION PUMP. £6-45**  
 Education Establishment Orders Accepted.  
 PHONE OR SEND YOUR ACCESS OR BARCLAYCARD NUMBER  
 ALL PRICES INCLUDE POSTAGE AND VAT.

**CSC EXPERIMENTOR BREADBOARDS**  
 No soldering modular breadboards, simply plug components in and out of letter/number identified nickel-silver contact holes. Start small and simply snap lock boards together to build breadboards of any size.



# P.E. STAR SPINNER

A FULL KIT OF PARTS AND ALSO INDIVIDUAL ITEMS ARE AVAILABLE AS FOLLOWS FROM FELTGLow LTD, 105B LONDON ROAD, BEXHILL, E. SUSSEX

DESIGNER APPROVED PARTS FOR THIS EXCITING PROJECT

P.C.B. Drilled & Tinned	£6.45
MM2708 Ready Programmed	£11.85
Mains Transformer	£11.75
Set 20 TRIACS	£28.50
Set 20 Darlington Opto's	£19.40
Complete set of I.C.'s (other than above) & Holders	£9.80
Set of Resistors, Caps, etc.	£4.80
Set of Fuse Holders/Fuses/Switches/LEDs	£10.65
Complete Set of Metalwork comprising: Printed Front Panel Printed Chassis Lid & Heatsinks & Grommets Chrome Front Screws & Internal Fixings	£14.75
Set of DIN Rail Terminals & Rail	£8.60

If Purchased Separately £126.55

**SPECIAL OFFER FULL KIT PRICE OF £109.95**

SAVING £16.60 OVER INDIVIDUAL PRICES.

COMPLETE KIT INCLUDES FULL CONSTRUCTIONAL DETAILS

PRICES INCLUDE VAT - ADD POST & PACKING 60p ON INDIVIDUAL ITEMS - COMPLETE KIT P&P FREE


Send Cheque or Crossed P.O.'s or Write/Phone your Card No.



**FELTGLow LTD.**  
105B LONDON ROAD,  
BEXHILL, E. SUSSEX.  
(0424) 221686.



# IT'S AS EASY AS A,B,C...

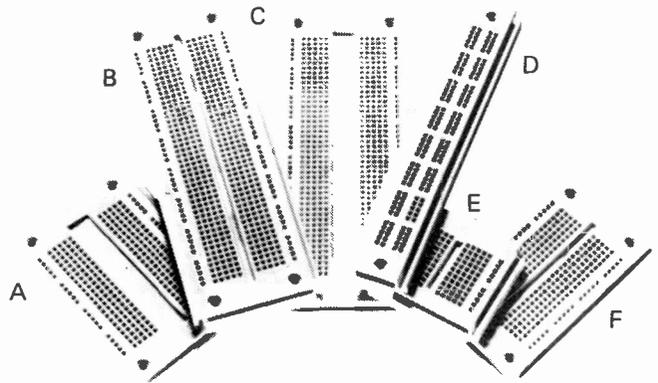

- A EXP 650 For microprocessor chips. £3.60
- B EXP 300 The most widely sold breadboard in the UK; for the serious hobbyist. £5.75
- C EXP 600.6" centre channel makes this the Microprocessor Breadboard. £6.30
- D EXP 4B An extra 4 bus-bars in one unit. £2.30
- E EXP 325 Built in bus-bars accepts 8, 14, 16 and up to 22 pin ICS. £1.60
- F EXP 350 270 contact points, ideal for working with up to 3 x 14 pin DIPS. £3.15
- G PB6 Professional breadboard in easily assembled kit form. £9.20 (Not illustrated.)
- H PB 100 Kit form breadboard recommended for students and educational uses. £11.80 (Not illustrated.)

& IT'S AS EASY AS 1,2,3 with THE EXPERIMENTOR SYSTEM

SCRATCHBOARD  
-BREADBOARD  
-MATCHBOARD

1. EXP 300PC which includes one item. A matchboard pre-drilled PCB - £1.20
2. EXP 302 which includes three items. Three 50-sheet scratchboard workpads - £1.50
3. EXP 303 which includes three items. Two matchboards and an EXP 300 solderless breadboard - £7.60
4. EXP 304 which includes four items. Two matchboards and EXP 300 breadboard and a scratchboard workpad - £8.70

The above prices do not include P&P and 15% VAT

## Now, for every Atom owner... Atomic games!

Make even more of your Acorn Atom with these, the first in a fast-growing range of imaginative, challenging and sophisticated games!

### Games Pack 1

ASTEROIDS. Shoot them down before you collide.  
SUB HUNT. Choose your course and speed to catch enemy subs.  
BREAKOUT. Score points for knocking bricks from wall.

### Games Pack 2


DOGFIGHT. Shoot down your opponent without crashing into stars.  
MASTERMIND. Guess the computer's code.  
ZOMBIE. Lure all the zombies into the swamp to survive.

### Games Pack 3

RAT TRAP. Entangle your opponent before he entangles you. Action replay feature.  
LUNAR LANDER. Altitude, fuel, drift velocity.  
BLACK BOX. Deduce the position of four invisible objects.
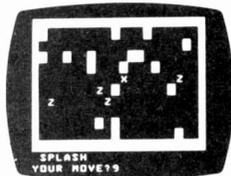
### Games Pack 4

STAR TREK. The classic computer game. The Universe versus the Klingons.  
FOUR ROW. Beat the computer to get four marbles in a row.  
SPACE ATTACK. Save the earth from invasion.



### Utility Pack 1

SOFT VDU. Replaces the Atom VDU to give 128 characters, upper and lower case, mathematical symbols, etc.

### Order today!

Just send a cheque or money order for £11.50 (inc VAT and p&p) per Pack, stating which Pack you want, or write for full details to Acorn Soft Limited, 4a Market Hill, Cambridge. Allow 14 days for delivery.

**ACORNSOFT**

## TOMORROW'S TOOLS TODAY

GLOBAL SPECIALTIES CORPORATION

G.S.C. (UK) Limited, Dept. 5H,  
Unit 1, Shire Hill Industrial Estate,  
Saffron Walden, Essex CB11 3AQ.  
Tel: Saffron Walden (0799) 21682.  
Telex: 817477.



NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

I enclose cheque/PO for £ \_\_\_\_\_  
or debit my Barclaycard, Access, American Express card  
No. \_\_\_\_\_ Exp. date \_\_\_\_\_  
or Tel: (0799) 21682 with your card number and your order will be in the post immediately.

A EXP 650 £5.00	Qty. Reqd.	B EXP 300 £7.76	Qty. Reqd.
C EXP 600 £8.39	Qty. Reqd.	D EXP 4B £3.50	Qty. Reqd.
E EXP 325 £2.70	Qty. Reqd.	F EXP 350 £4.48	Qty. Reqd.
G PB6 £11.73	Qty. Reqd.	H PB 100 £14.72	Qty. Reqd.

Experimenter System

1 EXP 300 PC £2.25	Qty. Reqd.	2 EXP 302 £2.58	Qty. Reqd.
3 EXP 303 £9.90	Qty. Reqd.	4 EXP 304 £11.15	Qty. Reqd.

Boxed prices include P & P and 15% VAT  
If no dealer in your area contact GSC direct.

FREE catalogue  
tick box

Global Specialties Corporation (UK) Limited, Dept. 5H,  
Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.



## RECEIVERS AND COMPONENTS

### BRAND NEW COMPONENTS BY RETURN

**Electrolytic Capacitors 16V, 25V, 50V.**  
 0.47, 1.0, 2.2, 4.7 & 10 Mfd. — 5p.  
 22 & 47 — 6p. 100 — 7p. (50V — 8p). 220 — 8p.  
 (50V — 10p). 470 — 11p. (40V — 18p). 1000/15V — 15p.  
 1000/25V — 18p. 1000/40V — 35p.

**Subminiature bead Tantulum electrolytics.**  
 0.1, 0.22, 0.47, 1.0 & 35V, 4.7 & 6.3V — 14p.  
 2/2/35V. 4.7/25V — 15p. 10/25V. 15/16V — 20p.  
 22/16V. 33/10V. 47/6V. 68/3V & 100/3V — 30p.  
 15/25V. 22/25V. 47/10V — 35p. 47/16V — 80p.

**Subminiature Ceramic Caps. E12 Series 100V.**  
 2% 10 pf. to 47 pf. — 3p. 56 pf. to 330 pf. — 4p.  
 10% 390 pf. to 4700 pf. — 4p.

**Vertical Mounting Ceramic Plate Caps. 50V.**  
 E12 22 pf. to 1000 pf. E6 1500 pf. to 47000 pf. — 2p.

**Polystyrene E12 Series 63V. Horizontal Mntg.**  
 10 pf. to 820 pf. — 3p. 1000 pf. to 10,000 pf. — 4p.

**Miniature Polyester 250V Vert. Mtg. E6 Series.**  
 01 to 06B — 4p. 1 — 5p. 15, 22 — 6p. 33, 47 — 10p.  
 68 — 12p. 10 — 15p. 1.5 — 22p. 2.2 — 24p.

**Mylar (Polyester) Film 100V. Vertical Mounting.**  
 .001, .0022, .0047 — 3p. .01, .022 — 4p. .04, .05, 0.1 — 5p.

**Miniature Film Resistors Highstab. E12 Ser. 5%.**  
 0.125W mixed carbon/metal 10Q to 1MΩ — 1p.  
 0.25W Carbon 1Q to 10MΩ (10% over 1MΩ) — 1p.  
 (E24 Series av. in 1/4W C. Film 1Q to 5M6Q).

**0.25W 0.5W & 1.0W Metal Film 10Q to 2M2Q — 2p.**  
 1N4148 — 2p. 1N4002 — 4p. 1N4006 — 6p. 1N4007 — 7p.  
 BC107/8/9. BC147/8/9. BC157/8/9. BF195 & 7 — 10p.  
 9 Pin I.C.s. 741 Op. amp. — 18p. 555 Timer — 24p.  
 DIL Holders 8 pin — 9p. 14 pin — 12p. 16 pin — 14p.  
 LED's. 3 & 5mm. Red — 10p. Green & Yellow — 14p.  
 Grommets for 3mm. — 1 1/2 p. 2 pce. holders 5mm. — 2 1/2 p.  
 20mm. Q.B. Fuses 15, 25, 5, 1, 2, 3 & 5A — 3p.  
 20mm. Anti Surge 100mA. to 5.0A — 5p.  
 20mm. Fishholders P.C. or Chassis Mtg. — 5p.  
 Solid A1. knobs 15mm. — 25p. 25mm. — 35p. 30mm. — 50p.  
 400mW Zener diodes E24 series 2V7 to 33V — 8p.

Prices VAT inclusive Post 15p. (Free over £5.00).

### THE C. R. SUPPLY CO.

127, Chesterfield Rd., Sheffield S8 0RN.

**100 TRANSISTORS £5.** (New mix) prewar onward wireless, valves. SAE. Sole Electronics. (PE) 37, Stanley Street, Ormskirk, Lancs.

### PC WHOLESALE

3, Thornhill, Romsey Road, Whiteparish, Salisbury, SP5 2SD.

All goods new full spec — prices are for minimum 100 any one type. Minimum Order £10 + 50p post. No VAT. SAE for full list.

AC138	.14	2N3702/8	.045	Diodes	
AC176	.14	2N3819	.14	1N4148	.02
AD161/2	.45	2N5401	.17	1k	.012
BC107	.07	40673	.45	10k	.008
BC108	.08	IC's	1k	.013	
BC109C	.08	4001B	.10	10k	.009
BC114	.05	4011B	.10	1N4002	.02
BC147/8/9	.05	4013AF	.30	1k	.024
BC171/2	.05	4017A	.35	10k	.020
BC177	.07	4025A	.12	1N4003	.034
BC182B	.045	4029A	.50	1k	.025
BC193L	.04	4049A	.25	10k	.021
BC212B	.045	4060B	.60	1N4006	.046
BC237/8/9	.05	4069B	.12	1k	.034
BC308B	.05	4511B	.60	10k	.028
BC320	.07	400148	.50		
BC327/8	.07	2114N-L	1.50		
BC441	.19	2708 450ns		Capacitors	
BC461	.20	741	2.80	cropped lead	
BC557/8/9	.06	555	.17	PCB mntg.	
BD246	.30	LED's			
BD433	.32	3mm red	.055	0.47/50	.022
BF181	.15	yellow	.080	1/50	.024
BF259	.20	green	.080	2/2/50	.024
BFY50	.15	5mm red	.060	4.7/25	.022
BFY51/2	.13	green	.080	10/16	.021
PBC108	.05	yellow	.060	10/40	.023
PN109	.05	green	.080	22/25	.023
TIP2955	.46	Clips	.02	47/16	.024
TIP3055	.45	Zeners, 400mW		47/40	.028
2N1132	.16	2V4 3V6 4V7		100/16	.022
2N1711	.18	5V6 6V2 6V8		100/25	.025
2N2369	.12	7V5 8V2 9V1		100/40	.027
2N2646	.34	11V 12V 14V		220/63	.037
2N2926R	.045	18V 24V		1000/16	.060
2N3053	.15	All at	.03	2200/40	.320
2N3055	.30				

**TURN YOUR SURPLUS** Capacitors, transistors, etc., into cash. Contact COLES HARDING CO., 103 South Brink, Wisbech, Cambs, 0945 4188. Immediate settlement.

# SMALL ADS

The prepaid rate for classified advertisements is 28 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £9.50 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Electronics and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Practical Electronics, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

**BOURNEMOUTH/BOSCOMBE.** Electronic components specialists for 33 years. Foresters (National Radio Supplies). Late Holdenhurst Road. Now at 36, Ashley Road, Boscombe. Tel. 302204. Closed Weds.

## £1 BARGAIN PACKS

All packs £1 each: any 12 for £10. Post 25p. All top-grade new components — no rubbish.

PC1 12 BC107	PC9 10 T03 sockets
PC2 14 BC108	PC10 15 0-1/35V tants
PC3 12 B8C109	PC11 14 3mm red LEDs
PC4 3 2N3055	PC12 12 5mm red LEDs
PC5 7 BFV51	PC13 8 741
PC6 16 BC182	PC14 6 555
PC7 60 1N4148	PC15 15 12V zeners
PC8 25 1N4003	PC16 200 1k 1W 5% Rs

Send S.A.E. for 8-page list/enquiries.

**PC ELECTRONICS, 3 Thornhill, Romsey Road Whiteparish, Salisbury, SP5 2SD**

**CLEARANCE PARCELS:** Transistors, Resistors, Boards, Hardware. 10lbs only £5.80! 1,000 Resistors £4.25, 500 Capacitors £3.75. BC108, BC171, BC204, BC230, 2N5061. CV7497 Transistors 10 70p, 100 £5.80, 2N3055, 10 for £3.50. S.A.E. Lists: W.V.E. (2), 15 High Street, Lydney, Gloucestershire.

**BALLARD'S OF TUNBRIDGE WELLS** have moved to 54, Grosvenor Road, no lists. S.A.E. all enquiries phone Tunbridge Wells 31803.

## SOFTWARE

**COMPUKIT SOFTWARE. FIRMWARE. INFORMATION.** Switched 16/32 Line display conversion, simple PIA interface, word processor program on Prom or Cassette, high speed cassette save/load, new enhanced basic monitor & toolkit, Prom Programming service. S.A.E. for details. N. V. Davies, 11 Holloway, Haverfordwest, Dyfed.

**ZX80 MAZE (I&II), Battleships.** Slot machine, Maths test, Guess number, pontoon. All on one cassette (for 1K) — £2.50. TRS 80 (II 16K). Space Invaders. Digital clock (with alarm facility) on one cassette — £2.50. From: P. Bramwell, 87, Anderson Crescent, Great Barr, Birmingham B43 7ST.

## UK 101 Software on Tape

8K Nuclear Holocaust	8K Asteroid Runner
8K Home Finance	5K Space Defender
4K Alien Invaders	4K Snakes and Ladders
4K UK 101 Breakout	4K Drawing Machine
4K The M. M. Y. Game	4K Fruit Machine

£3.00 each or £2.50 each for two or more  
 8K Quest For The Golden Crown £5.50.  
 A graphics 'Adventure' game, with instruction booklet

## UK 101 Hardware

**Programmable Sound Generator**  
 Add another dimension to your UK 101 with our sound unit using the AY 3-8910. We will supply the P.C.B. manual containing list of parts, Hardware, Software and construction details, and software on tape. All for only £9.50.

Imagine a sound — Program it!

Cheque, P.O. or just S.A.E. for details to:

**MARICK, Dept 12, 1 Branksome Close, Paignton, Devon.**

**ZX80 (4K) SOFTWARE.** Make sure your junior school child has a sound background in English, Maths, General Knowledge and Reasoning. Fun but thorough coaching on cassette £4.50. Rose Cassettes, 148 Widney Lane, Solihull, West Midlands B91 3LH.

**COMPUKIT 4K DRAUGHTS CASSETTE £1.50.** Beat the computer. Simon Monk, 16, Richmond Road, Wolverhampton, WV3 9HY.

**4K COMPUKIT CASSETTE.** Alien Invaders £2.50, 10 x 10 Maze Escape 3D graphics £2.50 both £4.00. Steven Hall, 14, Christchurch Lane, Lichfield, Staffs.

**UK101 PROGRAMMERS AID.** Features. Find, Trace, Delete, Renumber, Variables list and more. Super-board Compatible (2K machine code) 021-308 7012 (Richard).

## NOTICE TO READERS

*Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser to check both prices and availability of goods before ordering from non-current issues of the magazine.*

**COMPUKIT UK101** can handle dimensioned string arrays without any hangups. Simply fit a modified Basic 3 chip (5v 2716) as published by OSI UK user group, only £12. Other programming services considered. M. Spalton, 9, Willowfields, Hilton, Derby DE6 5GU.

## BOOKS AND PUBLICATIONS

**ANY SINGLE SERVICE SHEET £1 L.S.A.E.** Thousands different repair/service manuals/sheets in stock. Repair data your named T.V. £6 (with circuits £8). S.A.E. Newsletter, pricelists, quotations. AUS (PE), 76 Church Street, Larkhall, Lanarkshire. (0698 883334).

## EDUCATIONAL

**CAREERS** in Marine Electronics. Courses commencing September and January. Further details, the Nautical College, Fleetwood FY7 8JZ. Tel. 03917 79123.

## CITY & GUILDS EXAMS

Study for success with ICS. An ICS homestudy course will ensure that you pass your C. & G. exams. Special courses for: Telecoms. Technicians, Electrical Installations, Radio, TV & Electronics Technicians, Radio Amateurs. Full details from:

## ICS SCHOOL OF ELECTRONICS

Dept. 272F Intertex House, London SW8 4UJ

Tel. 01-622 9911 (all hours)

State if under 18

## TECHNICAL TRAINING

Get the training you need to move up into a higher paid job. Take the first step now — write or phone ICS for details of ICS specialist homestudy courses on Radio, TV, Audio Eng. and Servicing, Electronics, Computers; also self-build radio kits. Full details from:

## ICS SCHOOL OF ELECTRONICS

Dept. 272F Intertex House, London SW8 4UJ

Tel. 01-622 9911 (all hours)

State if under 18

## COLOUR TV SERVICING

Learn the techniques of servicing Colour TV sets through new homestudy course approved by leading manufacturers. Covers principles, practice and alignment with numerous illustrations and diagrams. Other courses for radio and audio servicing. Full details from:

## ICS SCHOOL OF ELECTRONICS

Dept. 272F Intertex House, London SW8 4UJ

Tel. 01-622 9911 (all hours)

State if under 18

## COURSES

**SUMMER SCHDOL** in Personal Computing July 1981 two weeks residential at the University College of Wales Aberystwyth. Details from: PC Summer School, Sandmarsh, Queens Road, Aberystwyth SY23 2HH. 0970 617749.

## AERIALS

**ALMAG INDOOR TV AERIAL.** New design. All groups £2.50 + 50p P&P refundable. Murphy, 6, London Road, Dalkeith, Midlothian.

## SERVICE SHEETS

**BELL'S TELEVISION SERVICES** for Service Sheets on Radio, Tv, etc £1.00 plus S.A.E. Colour TV Service Manuals on request. S.A.E. with enquiries to B.T.S. 190 Kings Road, Harrogate, N. Yorkshire, Tel: (0423) 55885.

**JAPANESE TV SERVICE SHEET** specialists catalogue 25p plus SAE. SANDHURST PUBLICATIONS, Camberley, Surrey.

## FOR SALE

**P.E. COMPLETE SET** Vol 1 No. 1. To present over 170 magazines. Offers Box 85.

**NEW BACK ISSUES** of 'Practical Electronics' available 90p each Post Free. Cheque or uncrossed p/o returned if not in stock - BELL'S TELEVISION SERVICES, 190 Kings Road, Harrogate, N. Yorks. Tel: (0423) 55885.

**UK101 COMPUKIT** 8K Case Cassette Unit, TV-set, programs, manuals etc. Fully working, built by engineer. Tel. 0245 469370. £200.

**SET OF "PRACTICAL ELECTRONICS" 1965 TO 1981.** Offers invited. Telephone Wigan 41850.

**PRACTICAL ELECTRONICS,** May 1969 to May 1980 inclusive, offers 051 645 5247.

**SUPERBOARD II COMPUTER,** Cased. Including power supply, Cassette Recorder, Cassette and Manuals. Costs £226, Only £175. Phone Ingrebourne 46565.

**E.T.I. 4600 SYNTHESISER,** Offers over £500. Tel. 09323 44531 evenings or 09323 41199 Ext. 2264 daytime.

**EARLY PRACTICAL ELECTRONICS,** November 1964 to January 1973. Offers? Shottisham (0394) 411000.

## MISCELLANEOUS

**DIGITAL WATCH BATTERIES.** Any sort 75p each + P&P. Send S.A.E. or 15p with number or old battery to Dislec, Y. 511, Fullbridge Road, Werrington, Peterborough PE4 6SB.

### PE ULTRASONIC ALARM KITS

designer approved

KITS	INC	F/G	PCB	DRILLED	ABS	BOX	
HARDWARE - ALL COMPS							
IC Ultrasonic Alarm - Piezo Drive Output							£16.95
IC Ultrasonic Alarm - Relay Output - 3A 240V							£19.65
Piezo Sounder 12V 18mA 2.7kHz 105db @ 1 mtr							£9.20
Slave Dimmer (FEB 81) phototransistor input							£12.95
Audio Isolator (MAR 80) via infrared beam							£6.95
All prices inclusive - CWO - UK mail order							
GJD ELECTRONICS, 105 Harper Fold Road, Radcliffe, Manchester M26 0RQ.							

**CLEARING LABORATORY:** scopes, generators, P.S.U.'s, bridges, analysers, meters, recorders, etc. 0403-76236.

## Cabinet and Flightcase Fittings

Fretcloths, Coverings, Handles, Castors etc., Jacks and Sockets, Cannons, Bulgins, Reverb Trays, Emilar Compression Drivers, AKG Mics, Celestion Speakers, ASS, Glassfibre Horns.

Send 30p Postal Order for illustrated catalogues to:-

### ADAM HALL (P. E. SUPPLIES)

Unit G, Carlton Court, Grainger Road, Southend-on-Sea, Essex SS2 5BZ.

**PRINTED CIRCUITS.** Make your own simply, cheaply and quickly! Golden Fotolak Light Sensitive Lacquer - now greatly improved and very much faster. Aerosol cans with full instructions £2.25. Developer 35p. Ferric Chloride 55p. Clear Acetate sheet for master 14p. Copper-clad Fibreglass. Board approx. 1mm thick £1.70 sq. ft. Post/packing 75p. WHITE HOUSE ELECTRONICS, P.O. BOX 19, Castle Drive, Penzance, Cornwall.

## BIG EARS

SPEECH  
INPUT  
FOR  
YOUR  
COMPUTER!



**BIG EARS** opens the door to direct man-machine communication. The system comprises analogue frequency separation filters, preamps and signal conversion, together with a quality microphone and extensive software. Words, in any language, are stored as "voice-prints" by simply repeating them a few times in "learn" mode. Using keyword selection techniques, large vocabularies can be constructed.

Use **BIG EARS** as a front end for any application: data enquiry, robot control, starwars - the possibilities are unlimited...

**BUILT, TESTED & GUARANTEED ONLY £45!**

PRICE INCLUDES POSTAGE & PACKING. PLEASE ADD VAT AT 15%  
PLEASE STATE COMPUTER, UK101 SUPERBOARD, NASCOM2,  
PET, TRS80, ETC.

### MICROGRAPHICS

Colour Conversion for  
UK101/NASCOM 1 & 2/ Superboard.  
(Modulator included)

KIT £45  
BUILT £60

### COLOUR MODULATOR

RGB in, PAL/UHF out

KIT £12  
BUILT £18

Please add VAT at 15% to all prices  
Barclay/Access orders accepted on telephone

WILLIAM STUART SYSTEMS Ltd  
Dower House, Billericay Road, Herongate, Brentwood, Essex CM13 3SD  
Telephone: Brentwood (0277) 810244

**SUPERB INSTRUMENT CASES BY BAZELLI,** manufactured from P.V.C. Faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range. Competitive prices start at a Low £1.05. Chassis punching facilities at very competitive prices, 400 models to choose from. Suppliers only to Industry & The Trade. BAZELLI (Dept. No. 23), St. Wilfrids, Foundry Lane, Halton, Lancaster, LA1 6LT.

## GUITAR/PA/ MUSIC AMPLIFIERS

100 watt superb treble/bass overdrive. 12 months guarantee. Unbeatable at £50; 60 watt £44; 200 watt £68; 100 watt twin channel sep. treble/bass per channel £65; 60 watt £52; 200 watt £78; 100 watt four channel sep. treble/bass per channel £75; 200 watt £98; slaves 100 watt £34; 200 watt £60; 250 watt £70; 500 watt £140; fuzz boxes £12.00; bass fuzz £12.90; overdrive fuzz £22; 100 watt combo superb sound overdrive, sturdy construction, castors, unbeatable £98; twin channel £115; bass combo £118; speakers 15in. 100 watt £36; 12in. 100 watt £24; 60 watt £16; microphone Shure Unidyne B £25; 3-Channel sound/light £26.

Send cheque or P.O. to:

**WILLIAMSON AMPLIFICATION**  
62 Thorncliffe Avenue, Dukinfield, Cheshire.  
Tel: 061-308 2064

**ULTRASONIC TRANSDUCERS.** £2.85 per pair + 25p P. & P. Dataplus Developments, 81 Cholmeley Road, Reading, Berks.

## MAKE YOUR OWN PRINTED CIRCUITS

Etch Resist Transfers - Starter pack (5 sheets lines, pads, I.C. pads) £2.00. Large range of single sheets in stock at 43p per sheet.

**Master Positive Transparencies** from P.C. layouts in magazines by simple photographic process. Full instructions supplied. 2 sheets (20 x 25cm) negative paper and 2 sheets (18 x 24cm) positive film £1.80. Drafting film (30 x 21cm) 22p per sheet.

20p stamp for lists and information. P&P 35p/order

**P.K.G. ELECTRONICS**  
OAK LODGE, TANSLEY, DERBYSHIRE

**BURGLAR ALARM EQUIPMENT.** Latest Discount Catalogue out now! Phone C.W.A.S. Alarm 0274 682674.

## RYDER ORGAN SYSTEM

The WW classical design for full-size keyboards, including couplers. Expanded range of p.c. boards & data available includes chorus, vibrato, combination stop control.

**Reverberation.** A new compact solid-state unit gives smooth natural sound. Demo cassette, on loan, deposit £1.50, refund £1.00. (Prices UK only).

**HIYKON LTD. (P), Woodside Croft, Ladybridge Lane, Bolton BL1 5ED.**

## ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Practical Electronics for .....

insertions. I enclose Cheque/P.O. for £ .....

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Practical Electronics)


NAME .....

ADDRESS .....

Company registered in England. Registered No. 53626. Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS.

Send to: Classified Advertisement Manager

**PRACTICAL ELECTRONICS**  
GMG, Classified Advertisements Dept., Room 2337,  
King's Reach Tower, Stamford Street,  
London SE1 9LS. Telephone 01-261 5846

Rate:

28p per word, minimum 12 words. Box No. 60p extra.

## TIME EXACT?

**MSF CLOCK** is ALWAYS CORRECT - never gains or loses, self setting at switch-on, 8 digits show Date, Hours, Minutes and Seconds, larger digit Hours and Minutes for easy QUICK-GLANCE time, auto GMT/BST and leap year, can expand to years and milliseconds, also parallel BCD output for computer or millisecond and audio to record and show time on playback, receives Rugby 60KHz atomic time signals, built-in antenna, 1000Km range, fun-to-build kit **£54.80** includes all parts, printed circuit, case, postage etc, money back assurance, ABSOLUTE ACCURACY so GET yours NOW.


## CAMBRIDGE KITS

45 (FR) Old School Lane,  
Milton, Cambridge.

**BURGLAR ALARM EQUIPMENT.** - Brand new, top quality. Free catalogue and price list: Sigma Security Systems, 13 St. Johns Street, Oulton, Leeds LS26 8JT.

**SEEN MY CAT?** 5000 odds and ends. Mechanical, electrical. Cat free. Whiston Dept. PRE, New Mills, Stockport.
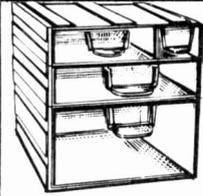
## NEAT! TIDY! HANDY! 1D 2D 3D 6D INTERLOCKING PLASTIC STORAGE DRAWERS



AS SUPPLIED:  
TO POST OFFICE  
& GOVT DEPTS

Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. 1D and 2D have space dividers. Build up any size cabinet for wall, bench or table top.

SINGLE UNITS 1101 (5in. x 2 1/2in. x 2 1/2in) £4.80 DOZEN  
DOUBLE UNITS 1201 (5in. x 4 1/2in. x 2 1/2in) £7.50 DOZEN  
TREBLE 1301 £7.50 for 8  
DOUBLE TREBLE 2 drawers, in one outer case (602), £10.90 for 8  
Extra large size (601) £8.50 for 8  
Orders over £60, less 5%. Packing/Postage/Carriage: Add £1.30 to all orders under £10. Orders £10 and over, please add 10% carriage.

Please add 15% V.A.T. to total remitance.  
All prices correct at time of press.

**FLAIRLINE SUPPLIES** (Dept PE4), 124 Cricklewood Broadway, London NW2. Tel: 01-450 4844.

## THE SCIENTIFIC WIRE COMPANY PO Box 30, London E.4. 01-531 1568.

### ENAMELLED COPPER WIRE

SWG	1lb	8oz	4oz	2oz
8 to 29	2.76	1.50	0.80	0.60
35 to 39	3.20	1.80	0.90	0.70
40 to 43	3.40	2.00	1.10	0.80
44 to 47	4.75	2.60	2.00	1.42
47	8.37	5.32	3.19	2.50
48 to 49	15.96	9.58	6.38	3.69

### SILVER PLATED COPPER WIRE

14 to 30	6.50	3.75	2.20	1.40
----------	------	------	------	------

### TINNED COPPER WIRE

14 to 30	3.85	2.36	1.34	0.90
----------	------	------	------	------

Prices include P&P, VAT and wire Data.

Orders under £2 please add 20p.

SAE for List. Dealer enquiries welcome.

Reg. Office: 22 Coningsby Gardens.

**PSYCHOTRONIC GENERATORS.** gravity lasers, electrokinesis, electrophotography, skinvision. S.A.E. 4" x 9" Paralab, Downton, Wilts.

**BURGLAR ALARM EQUIPMENT,** wide selection at competitive prices. Sae for price list. A. Barton (PE), 27, Gunville Road, Newport, I.W.

## DIGITAL WATCH BATTERY REPLACEMENT KIT



These watches all require battery (power cell) replacement at regular intervals. This kit provides the means. We supply eyeglass, non-magnetic tweezers, watch screwdriver, case knife and screwback case opener, also one doz. assort. push pieces, full instructions and battery identification chart. We then supply replacement batteries—you fit them. Begin now. Send **£9.00** for complete kit and get into a fast growing business. Prompt despatch.

### BOLSTER INSTRUMENT CO. (PE23)

11 Percy Avenue, Ashford, Middx. TW15 2PB.

## VIDEO MUSIC



The amazing Videograph, as featured recently in Electronics Today International, links your Hi-Fi with any Colour TV to produce a Fantasia of hypnotic visual effects. The system displays stereo music as brilliantly coloured waveforms against an ever changing background. For the technically-minded, a square-wave signal generator is built-in, permitting advanced demonstrations of transient response etc. Truly the ultimate accessory for any Hi-Fi system!

### DIY KIT ONLY £33.95

Case & Controls £15.95  
or READY BUILT £69.95

All prices include VAT and postage

**WILLIAM STUART SYSTEMS LTD**

Dower House, Billericay Road, Herongate, Brentwood, Essex CM13 3SD  
Telephone Brentwood (0277) 810244

## PRACTICAL ELECTRONICS P.C.B.'s

Drilled, 1.5mm Glass fibre Fry's Roller Tinned	
JUNE 80 Greenhouse temp controller EP358	£1.90
JULY 80 Tape slide synch EG353	£1.28
SEPT 80 Sound gen EC14	£2.53
OCT 80 Cine frame counter EG408	98p
NOV 80 Disco desk, set of 5 pcb's	£12.50
Dramatic update EP416 95p. Games timer EP424	£1.32
DEC 80 20mA current loop EP422	£1.95
FEB 81 Dimmer EG485 £1.33 Lapsed hour meter set of 3	£3.45
MAR 81 27/28 MHz converter EA236	£1.44
Digital counter timer EG505/7/9	set £5.29

For full list and current pcb's please send SAE Pcb's also produced to customers own masters. Trade enquiries welcomed. Please write for quote. CWO Design. Postage. - Please add 35p postage and packing to complete order. Europe 70p.

### PROTO DESIGN

14 Downham Road, Ramsden Heath  
Billericay, Essex CM11 1PU  
Telephone 0288-710722

### MULLARD CAPACITORS

Special purchase of factory clearance capacitors enables us to offer **£280** Polystyrene (Liquonac Allsorts) at £2 for 100 mixed. And Miniature Electrolytics at £2 for 200 mixed. Pack of each only **£3.50**. These consist of spillages, floor sweepings, cosmetic imperfections etc. As we have no time to sort them they are magnificent value for the constructor

### T.V. GAME BOARDS

New, but incomplete. Contains CMOS ICS, transistors, diodes, switches, etc. etc. All modern components. 5 assorted boards only **£3.50**. Superb value.

### U.H.F. MODULATORS

Video in - UHF out, calibrated to CH. 36 (625 line UHF). Housed in metal box 2 1/2" x 2" x 1 1/2" with 9' coaxial lead, TV plug and connection data £2.50 each 3 for £6.

### G.E.C. UHF TRANSISTOR TV TUNERS

Rotary type with slow motion drive, leads and aerial socket. **£1.50** 3 for **£3.50** for G.E.C. "2010" series etc."

### DE LUXE FIBRE GLASS PRINTED CIRCUIT ETCHING KITS

Includes 150 sq. ins. copper clad F/G board, 1 lb ferric chloride, 1 dalo etch resist pen, Abrasive cleaner, Etch resist tweezers Etch tray plus instructions. Special Price: **£5.95**.

### 1 1/2 FE. C1. To mil spec £2.25

150 sq. in. Single sided board **£2.00**  
150 sq. in. Double sided board **£3.00**

### MINIATURE MAINS TRANSFORMERS

Top quality. Split bobbin construction will give 4.5V-0-4.5V at 250 MA 1 1/2" x 1 1/2" x 1 1/2", all sorts of uses. **ONLY 90p.** 3 for **£2.20**.

**BD181 78 Watt T.O.3 Power Transistors.** 50p ea. 3 for **£1.44P1 Alternator Diodes.** Ideal for making **Battery Chargers** etc. 4 make 50 amp 150V bridge. -Ve or +Ve case. 2 of each **£2.00**.

### TRANSISTOR PACKS

100. Full spec, new and marked Includes BC148, BC183L, MED412, BF274, BC154 etc. **£4.95**  
200 as above and includes AC128, 2N3055, BFY50, BD131, BC338 and PBC108 etc **£9.95**. Buy bulk and save money, these packs are worth at least double.

**100K MINIATURE THUMBWHEEL SLIDER POTS** Very neat, can be banked side by side. Ideal for v. cap tuning, graphic equalizers etc. 10 for **£1**

50p P & P on all above items. Cheque or P.O. with order to:

**SENTINEL SUPPLY, DEPT. P.E.**  
149A BROOKMILL RD., DEPTFORD, LONDON, SE8

### P/B SWITCH BANKS

These cost a fortune! Were made for various music centres. Includes independent and interdependent latching types multi pole c/o etc. Can be modified. Can't be repeated. 3 Banks for **£1**. Knobs for P/B Switches. Fit 3 1/2 mm sq. shaft. 10 for **£1**. Chrome or Saun Aluminium Finish.

### MINIATURE LEVEL/BATT. METERS 200µA F.S.D. as fitted to any cassette recorder 90p.

### BULK BARGAINS. STOCK UP FOR WINTER

300 mixed 1/2 & 1/4 watt resistors **£1.95**  
150 mixed 1/2 & 2 watt resistors **£1.95**  
300 mixed capacitors, modern, most types **£3.95**  
100 mixed ceramic and plate caps **£1.20**  
100 mixed polystyrene caps **£2.20**  
25 assorted pots **£1.50**  
25 presets, skatlon etc. **£1.20**  
20 VDRs and thermistors **£1.20**  
100 Hi wattage resistors wirewound at **£2.75**  
100 electrolytics, nice values **£2.20**  
300 printed circuit resistors **£1.45**  
300 printed circuit components **£1.95**

### 20 ASSORTED ZENER DIODES

1 watt and 400mW. **£1.50**  
100 MIXED DIODES  
Includes Zener, power, bridge, germanium, silicon etc  
All full spec **£4.95**

PP3 Battery Connectors 10 for 50p.  
Miniature Press to Make Switches, Red knob, 3 for 50p.  
Subminiature S.P.C.O. Slide Switches, 6 for 50p.  
Miniature D.P.C.O. Slide Switches 6 for 50p.  
Standard 2P. 3 Position Slide Switch 4 for 50p.  
4 x HP11 Battery Holders (2 x 2 Flat type) with leads. 2 for 50p.

Assorted Fuse Holders including 20mm P.C. Panel and chassis types Pack of 7 for 50p.  
3.5mm Jack Sockets, switched. Enclosed type. P.C. or panel mounting. With nuts and washers. 4 for 50p.  
9" Section, Chrome on Brass Telescopic Aerial. Plugs into any 3.5mm socket Approx 2'6" extended **£1** each. 3 for **£2.50**.

### R.C. SUPPRESSORS

250V 1" x 1" x 1" Ideal for fluorescent light suppression, car, and relays Also for snubber networks. 50p each, 3 for **£1**.

### MINIATURE REED SWITCHES

We are the cheapest 20 for **£1.00** 100 for **£3.30**.

### SUBMINIATURE REED SWITCHES

10 for **£1.00**, 100 for **£8.00**.

### RED LEDs. 0.125" TL209 12 for £1.

20 Miniature Tantalum Capacitors at least 6 types per pack **£1.20**.

## Top Priority for every constructor-HOME RADIO CATALOGUE

- About 2,000 items clearly listed.
- Profusely illustrated throughout.
- Large A-4 size pages.
- Bargain list, order form and 2 coupons each worth 25p if used as directed, all supplied free.

Price £1, plus 50p for post, packing and insurance.

*Send cheque or P.O. for £1.50*

**HOME RADIO Components LTD**  
Dept. PE, P.O. Box 92, 215 London Road, Mitcham, Surrey. 01-543 5659

## PRACTICAL ELECTRONICS PROJECTS

PHASER UNIT (April 1979) Complete kit as specified inc. box	£16.95
SUSTAIN UNIT (Oct. 1977) Complete kit as specified inc. box	£8.95
SMOOTH FUZZ (Sept. 1979) Complete kit as specified inc. box (All parts available separately. Send S.A.E. for list)	£8.95
ORION AMPLIFIER Complete set of semiconductors	£9.75
Quality glass fibre p.c.d. printed with component locations	£3.50
PE TV SOUND SEPARATOR Complete set of semiconductors	£2.30
High quality glass fibre p.c.d.	£1.50
Murata filters: SFE6 OMA 50p, CDA6 OMC 50p.	

POSTAGE & PACKING 25p per order.  
Orders over £10.00 post free.

PRICES DO NOT INCLUDE VAT. Add 15% to all prices.

MAIL ORDER ONLY CALLERS BY APPOINTMENT

## DAVIAN ELECTRONICS

13 DEEPDALE AVENUE, ROYTON, OLDHAM OL2 6XD.

## PROJECT PACKS

<b>Pools predictor (79053)</b> An analogue computer that may win you a fortune	£8.15
<b>Talk Funny (80052)</b> A ring modulator circuit that produces very strange results when fed with a human voice	£9.60
<b>Pest Pester (80130)</b> An electronic insect repellent.	£2.35
<b>Steam train sound effects (80019)</b> Simulates the sound of steam and whistle.	£6.50
<b>Electronic Nuisance (80016)</b> Makes an annoying noise, but only in the dark!	£3.85
<b>Cackling Egg timer (9985)</b> An egg timer with a difference, it clucks like a hen.	£8.35
<b>Chorosynth (80060)</b> A cheap mini synthesizer. Send for details.	£57.90
<b>Elektor Vocoder (80060)</b> The first Vocoder designed to be built in kit form. 10 Channel modular construction.	£162.50
<b>Analogue Reverberation Unit (9973)</b> Uses a SAD 1024 which can produce a delay up to 100ms.	£27.70
<b>Guitar Preamp (77020)</b> With three tone controls.	£6.50
<b>Linear Thermometer (80127)</b> Simple but effective meter reading thermometer using a diode as sensor.	£13.45
<b>Precision Power Unit (80514)</b> Produces accurate reference voltages at presettable current limits up to 2 Amps.	£48.65
<b>Top-preamp (80031)</b> Mini, all IC preamplifier for use with most power amplifiers.	£34.40
<b>Programmable Slide Fader (81002)</b> Mixes audio signals on tape with operation of two slide projectors.	£46.50
<b>Stereo dynamic Preamp (80532)</b> A low noise high quality disc preamplifier.	£5.20
<b>STAMP (80543)</b> Super tiny amplifier with up to 1 Watt output.	£3.75
<b>Transistor Ignition (80082)</b> The most significant advantages of other systems combined in one.	£20.45
<b>Dipstick Probe (80102)</b> Direct warning of high oil temperature. State long or short dipstick required.	£11.25
<b>Intelligent Wiper Delay (80086)</b> Can be set to produce delayed wipes at any predetermined interval.	£15.85
<b>Fuel Economiser (81013)</b> Audible guide to cheaper driving.	£8.05
<b>Disco Projects.</b>	Send for details
<b>Minimixer (8106)</b> 5 Channel High Quality Stereo Mixer.	£37.50
<b>Bath Thermometer (81047)</b> LED display of your bath temperature.	£6.85
<b>Process Timer (81101)</b> Versatile photographic development timer.	£18.20

Our Project Packs include the electronic components, the PCB, sockets and solder together with assembly instructions. Cases, knobs etc can be supplied as extra items if required. This is only part of our wide range of projects. See our catalogue for details of other projects that we can supply. You can also ring our number between 12.30 p.m. and 1.30 p.m. any weekday for a recorded announcement of any new items we have available.

To order: send cheque or postal order + 40p P&P to DORAM ELECTRONICS LTD All prices include VAT.  
a de boer company TELEPHONE: (0760) 21627 TELEX: 817912




### OHIO SCIENTIFIC NEW SUPERBOARD 3




New Series 2 Challenger C1P— cheapo 4K version £202, Ohio version 8K (illustrated) £259. The special offer of the century. (Only Swanley could do it!). For just £159 we will supply Superboard 3 with a free power supply and modulator kit and our free guard band kit (a brilliant breakthrough in itself for this kit extends the display to 32 x 32, gives 1200 and 300 Baud tape speeds, increases the computing speed by 50% and converts the display to 50Hz for flicker free viewing). Guard band kit also supplied separately for £10. 4K extra ram £16.95. Case £27. Cassette recorder £16. Cegmon improved monitor rom £29.50. Assembler/Editor tape £25. Word processor program £10. Display expansion kit 30 lines x 54 characters for Superboard 2 (not 3) £20. Cheapo memory expansion offer— buy a 610 expansion board with 8K ram on board and space for another 16K for £159 and get a free 5V 4A power kit and any extra ram you want for £3/K. Buy a minifloppy disc drive + case + power supply + DOS for £275 and we will do the extra ram for £2/K (max 16K).

### PRINTERS

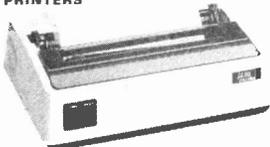

Buy any of the below and get a free interface kit and word processor program for UK101 or Superboard 2— OKI Microline 80 (illustrated) £329. Base 2 800 MST £299. Seikoso GP80 £225.

### SHARP MZ80K COMPUTERS

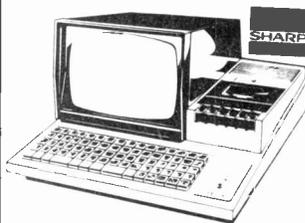

With Basic tape and a free tape of approx. 50 programs— 20K £415. 36K £437. 48K £459.

### SINCLAIR PRODUCTS\*

SC110 Oscilloscope £144.95. PFM200 £51.95. Microvision TV £89, adaptor £6.88. Enterprise prog calculator £19.95. PDM 35 £32.50. DM235 £55.55. DM450 £109.11.

### BATTERY ELIMINATORS\*

3-way type 6/7 1/2 9V 300ma £3.50. 100ma radio types with press studs 9V £4.77. 9 x 9V £5.99. Car converter 12V input, output 4 1/2 6/7 1/2 9V 800ma £3.04.

### BATTERY ELIMINATOR KITS\*

100ma radio types with press-studs 9V £1.64. 9 x 9V £2.30. Stabilised 8-way types 3/4 1/2 6/7 1/2 9V 12V 15V 19V 100 ma £3.12. 1 Amp £8.10. Stabilised power kits 2-18V 100ma £3.12. 1-30V 1A £8.30. 1-30V 2A £14.82. TTL and computer supplies 5V stabilised 1 1/4 £9, 3A £12. 12V car converters 6/7 1/2 9V 1A £1.62.

### TV GAMES\*

Stunt cycle chip + kit £20.95. AY-3-8600 + kit £12.98. AY-3-8550 + kit £9.26.


### MEMORIES

2114 450ns £2.15. 4116 200ns £2.83. 4027 £1.30. All low current.

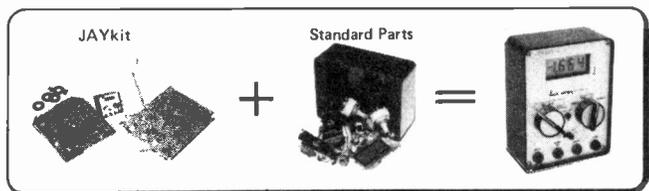
## SWANLEY ELECTRONICS

Dept. PE, 32 Goldsel Road, Swanley, Kent BR8 8EZ.

Telephone Swanley 64851. Please add 45p postage. Please add VAT except on sections marked with a \* which already include it. Lists 27p post free. No VAT on overseas orders which are a speciality. Official orders welcome.




### DM-2

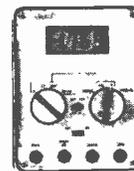

DIGITAL  
MULTIMETER

- ★ DC Volts . . . . . 1mV to 1000V
- ★ AC Volts . . . . . 1V to 500V
- ★ DC Current . . . . . 0.1mA to 0.2A
- ★ Resistance . . . . . 1Ω to 20MΩ
- ★ 3 1/2 digit LCD
- ★ Auto Low Battery indication
- ★ Auto Polarity & Zero
- ★ 1% accuracy (DC volts)
- ★ Designed around Intersil 7106 IC
- ★ Total cost around £30 (incl. case)

### FG-1a

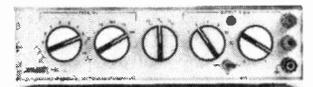

FUNCTION GENERATOR

- ★ 30mV to 10V pk-pk
- ★ 1Hz to 100kHz
- ★ DC coupled
- ★ Sine, Square & Triangle
- ★ Separate TTL output
- ★ Designed around Intersil 8038 IC
- ★ Total cost around £30 (incl. case)

Provided in a JAYkit is a Printed Circuit Board, a punched and lettered Front Panel overlay, a Circuit Diagram and Instruction Sheet and a comprehensive and up to date Component List showing suppliers and current prices. Difficult to obtain pieces of hardware are supplied with the kit.

Jayen Developments, 21 Gladeside, Bar Hill, Cambridge CB3 8DY

To: JAYEN Developments  
21 Gladeside, Bar Hill,  
Cambridge CB3 8DY  
Tel: (0954) 80285

Name \_\_\_\_\_

Address \_\_\_\_\_

Please send:

- DM-2 @ £5.45  
 FG-1a @ £4.95  
(Incl. VAT and P&P)

Money to be refunded if the kit is returned within 10 days.

# JAYkits



**SIMPLY AHEAD**  
and staying there

# The range grows bigger... better...

## New Profile Amplifiers - Two New Series

### MOSFET

CHOOSE AN I.L.P. MOSFET POWER AMP when it is advantageous to have a faster slew rate, lower distortion at higher frequencies, enhanced thermal stability, the ability to work with complex loads without difficulty and complete absence of cross-over distortion. I.L.P.'s exclusive encapsulation technique within fully adequate heatsinks has been taken a stage further with specially developed computer-verified 'New Profile' extrusions. These ensure optimum operating efficiency from our new MOSFETS, and are easier to mount. Connection is via five pins on the underside. I.L.P. MOSFETS ARE IDENTICAL IN PERFORMANCE TO THE COSTLIEST AMPLIFIERS IN THIS EXCITING NEW CATEGORY BUT ARE ONLY A FRACTION OF THE PRICES CHARGED ELSEWHERE.


Model	Output Power RMS	Distortion Typical at 1kHz	Slew Rate	Rise Time	Signal/Noise Ratio DIN AUDIO	Price & VAT
MOS120	60W into 4-8Ω	0.005%	20V/μs	3μs	100dB	£25.88 + £3.88
MOS200	120W into 4-8Ω	0.005%	20V/μs	3μs	100dB	£33.46 + £5.02

### BIPOLAR


#### STANDARD O/P TRANSISTORS

CHOOSE AN I.L.P. BIPOLAR POWER AMP where power and price are first consideration while maintaining optimum performance with hi-quality and wide choice of models. From domestic hi-fi to disco and P.A., for instrument amplification, there is an I.L.P. Bipolar to fill the bill, and as with our new Mosfets, we have encapsulated Bipolars within our New Profile extrusions with their computer-verified thermal efficiency and improved mounting shoulders. Connections are simple - via five pins on the underside and with our newest pre-amps and power supply units, it becomes easier than ever to have a system layout housed the way you want it.

Model	Output Power RMS	Distortion Typical at 1kHz	Slew Rate	Rise Time	Signal/Noise Ratio DIN AUDIO	Price & VAT
HY30	15W into 4-8Ω	0.015%	15V/μs	5μs	100dB	£7.29 + £1.09
HY60	30W into 4-8Ω	0.015%	15V/μs	5μs	100dB	£8.33 + £1.25
HY120	60W into 4-8Ω	0.01%	15V/μs	5μs	100dB	£17.48 + £2.62
HY200	120W into 4-8Ω	0.01%	15V/μs	5μs	100dB	£21.21 + £3.18
HY400	240W into 4Ω	0.01%	15V/μs	5μs	100dB	£31.83 + £4.77

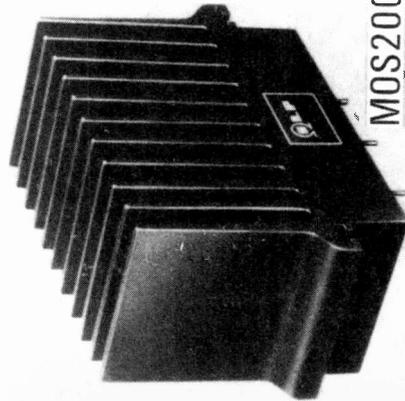


MOS200

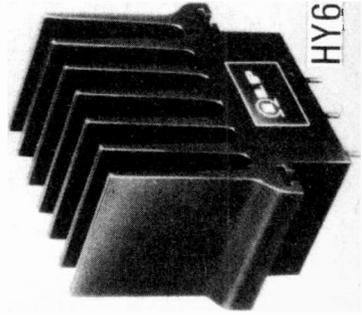


HY60

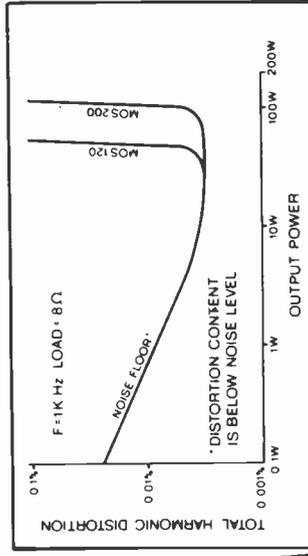**I.L.P. POWER AMPS ARE ENCAPSULATED FOR THERMAL STABILITY AND LONGER LIFE**



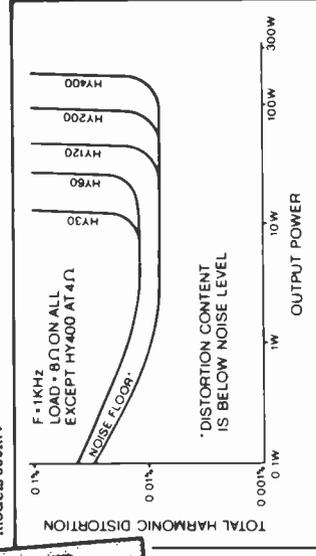Load impedance both models 4Ω - ∞ Input sensitivity both models 500mV  
Input impedance both models 100KΩ  
Frequency response both models 15Hz-100KHz - 3dB



Load impedance all models 4Ω - ∞ Input impedance all models 100KΩ  
Input sensitivity all models 500mV  
Frequency response all models 15Hz-50KHz - 3dB

#### THE NEW PROFILE EXTRUSIONS

The introduction of standard heatsink extrusion for all I.L.P. power amplifiers achieves many advantages. Research shows they provide optimum thermal dissipation and stability. Slotted shoulders allow easy mounting; standardisation enables us to keep our prices competitive. Surfaces are matt black, anodised for higher thermal conductivity. Extrusions vary in size according to module number.



# I.L.P. PRE-AMPS

HY6 (mono) and HY66 (stereo) are new to I.L.P.'s range of advanced audio modules. Their improved characteristics and styling ensure their being compatible with all I.L.P. power-amps both MOSFET and BIPOLAR, giving you chance to get the best possible reproduction from your equipment. HY6 and HY66 pre-amps are protected against short circuit and wrong polarity. Full assembly instructions are provided. Mounting boards are available as below.

Sizes - HY6 - 45 x 20 x 40 mm. HY66 - 90 x 20 x 40 mm. Active Tone Control circuits provide  $\pm 12$ dB cut and boost. Inputs Sensitivity - Mag. P.U. - 3mV. Mic. - selectable 1-12mV. All others 100mV. Tape O/P - 100mV. Main O/P - 500mV. Frequency response - D.C. to 100kHz - 3dB.

HY6 mono £6.44 + 97p VAT Connectors included

HY66 stereo £12.19 + £1.83 VAT Connectors included

B6 Mounting Board for one HY6 78p + 12p VAT

B66 Mounting Board for one HY66 99p + 15p VAT

# I.L.P. POWER SUPPLY UNITS


Of the eleven power supply units which comprise our current range, nine have toroidal transformers made in our own factory. Thus these I.L.P. power supply units are space-saving, more efficient and their better overall design helps enormously when assembly building. All models in the range are compatible with all I.L.P. amps and pre-amps with types to match whatever I.L.P. power amps you choose.

- PSU30  $\pm 15$ V at 100mA to drive up to 12 x HY6 or 6 x HY66 £4.50 + 0.68p VAT
- THE FOLLOWING WILL ALSO DRIVE I.L.P. PRE-AMPS £8.10 + £1.22 VAT
- ALL THE FOLLOWING USE TOROIDAL TRANSFORMERS
- PSU50 for use with 1 or 2 HY60's £10.94 + £1.64 VAT
- PSU60 for use with 1 HY120 £13.04 + £1.96 VAT
- PSU65 for use with 1 MOS120 £13.32 + £2.00 VAT
- PSU70 for use with 1 or 2 HY120's £15.92 + £2.39 VAT
- PSU75 for use with 1 or 2 MOS120 £16.20 + £2.43 VAT
- PSU90 for use with 1 HY200 £16.20 + £2.43 VAT
- PSU95 for use with 1 MOS200 £16.32 + £2.45 VAT
- PSU180 for use with 1 HY400 or 2 HY200 £21.34 + £3.20 VAT
- PSU185 for use with 1 or 2 MOS200 £21.46 + £3.22 VAT
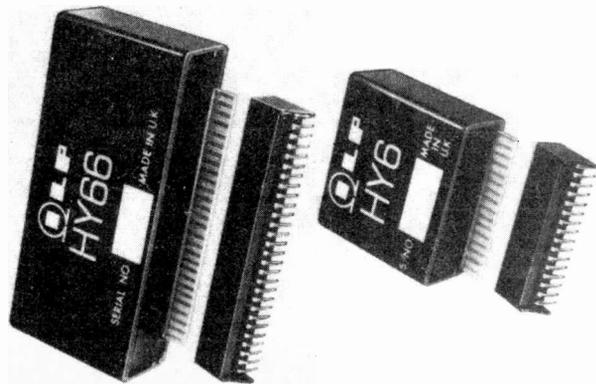
## ★ Freepost facility


When ordering or writing about I.L.P. products, you do not need to stamp the envelope. Mark it FREEPOST plus the code shown in the address below. We pay the postage for you.

★ TO ORDER Send cheque or money order payable to I.L.P. Electronics Ltd and crossed. Or pay by ACCESSOR/BARCLAYCARD Cash payments must be in registered envelope; if C.O.D. payment is wanted, please add £1.00 to TOTAL value of order.



PSU

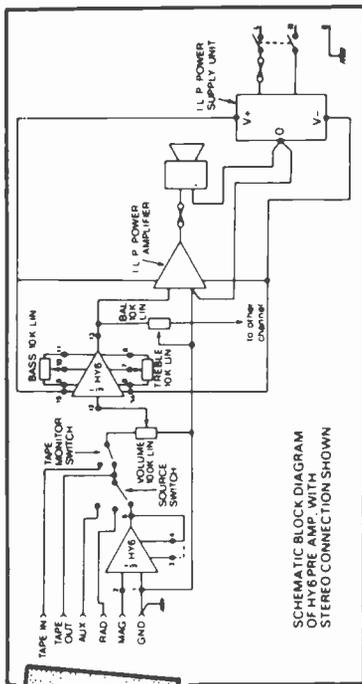**NO QUIBBLE 5 YEAR GUARANTEE  
7-DAY DESPATCH ON ALL ORDERS  
BRITISH DESIGN AND MANUFACTURE  
FREEPOST SERVICE**



SCHEMATIC BLOCK DIAGRAM OF HY6 PRE-AMP WITH STEREO CONNECTION SHOWN

- DISTORTION TYPICALLY 0.005%
- S/N RATIO - 90dB (Mag. P.U. - 68 dB)
- 38 dB overload margin on Mag. P.U.
- LATEST DESIGN HIGH QUALITY CONNECTORS
- ONLY POTS, SWITCHES AND PLUGS/SOCKETS NEED ADDING
- NEEDS ONLY UNREGULATED POWER SUPPLY  $\pm 15$  to  $\pm 60$ V

**IN A RANGE OF 11 MODELS USING LATEST TOROIDAL TRANSFORMERS**

# 1971-1980 TEN YEARS OF PLANNED PROGRESS

When in 1971, Ian L. Potts founded his now world-famous company, he saw the need for a different and more rational approach to exploiting to the full the potential that lay in modular construction. New thinking was badly needed. The result was a range of modules revolutionary in concept. The rightness of this new thinking is shown by the size of the company today, its new factory, its vast exports, its acceptance by constructors as the modules to build with. The range grows bigger and better. Exciting new lines (in no way conflicting with existing ones) are well past drawing board stage. This is why I.L.P. are simply ahead and staying there.

# BRITAIN'S LEADING QUALITY MODULE SUPPLIERS

To: I.L.P. ELECTRONICS LTD, CANTERBURY CT2 7EP

Please supply..... Total purchase price £.....

I enclose Cheque  Postal Orders  International Money Order

Please debit my Access/Barclaycard Account No. ....

NAME.....

ADDRESS.....

Signature.....

# ELECTRONICS LTD.

FREEPOST 2 Graham Bell House, Roper Close, Canterbury, Kent CT2 7EP. Telephone (0227) 54778 Technical (0227) 647231 Telex 965780

Available also from MARSHALLS, WATFORD ELECTRONICS and certain other selected retailers



ALL U.K. ORDERS DESPATCHED POST FREE

# Enter the 80's with SAXON

**£30 FREE!**

## STEREO DISCO SYSTEMS WITH LIGHT SHOW & DISPLAY

### STANDARD CENTAUR 100W

£299 incl VAT Deposit £60

### SUPER CENTAUR 200W

£399 incl VAT Deposit £80

### GXL 200W with PDF BINS (illus)

£489 incl VAT Deposit £99

### CUSTOM CENTAUR 400/600W with four PDF 100A Bins

£899 incl VAT Deposit £180

### MINI DISCO 100W MONO

£249 incl VAT Deposit £50



- Headphone monitor/cue light
- Full mixing/crosstape
- Tape & mic inputs
- Top Quality
- 4 channel soundlight

All systems complete  
with loudspeakers, leads,  
& 2 years warranty

Typical Apr. 38%

**20%  
DEPOSIT  
CREDIT  
TERMS**

### P.A SYSTEMS C/W LOUSPEAKERS

Vouchers with our new catalogue over 200 items of disco systems, lighting and accessories. Send **£1.00** now.

#### EXAMPLES:

Fuzz lights	£26.75
Projectors from	£55.50
Strobes	£35-£220
Quality Rope lights 8 mt	£59
Disco stands	£29.75
Echo chambers from	£77.50
100W speaker 12"	£29.50
10 way programmed chaser	£199
100W twin horn	£125
800W spot bank	£55

Mixers, mics, amplifiers, goosenecks, light units, bubble machines, mirror balls, helicopters, bins, consoles, and much more.

CARRIAGE ON COMPLETE SYSTEMS  
IN U.K. £19

100 WATT  
£229 incl VAT  
Dep. £46

- Four mixing inputs & master
- Bass & treble controls
- Sturdy construction
- Twin Piezo cabinets

200 Watts £349 incl VAT  
• Twin 200W cabinets  
• Six inputs—three channels  
Dep. £70



### JUST PLUG IN AND GO!!

AP100  
AMPLIFIER £67.50  
AP200 AMPLIFIER £119

**AND IF WE HAVEN'T GOT  
IT - WE'LL GET IT!**

Full range of Pluto, D.J.  
Lightmotion products in  
stock  
Send £1 now for your  
catalogue - worth £30!!!

SAXON  
ENTERTAINMENTS  
333 WHITEHORSE ROAD  
CROYDON  
SURREY CR0 2HS  
Mon-Sat 9am-5pm

ALL MAIL & CREDIT ENQUIRIES TO  
CROYDON TO ORDER  
Send cheque/crossed POS or Telephone (01) 684 8007  
Access/Barclaycard. Telephone orders accepted  
For Credit Sales & Enquiries Ring  
SUE ABEGG ON (01) 684 8007.

LICENSED  
CREDIT  
BROKERS

## COMPUTER USER AIDS Incorporating the UK101 User Group UK101 & SUPERBOARD USERS

Is your regulator too hot?  
Is your cassette unreliable?  
Don't know where to buy cheap RAM?  
Can't find good quality low price software?

Then perhaps we can help. Computer Aids runs the UK 101 User Group which produces a quarterly newsletter that is despatched to members all over the world. This contains many soft & hardware tips and hints that answer most of the common questions about the 101. Advice reviews etc.

Our software sales and hardware kits all carry a 15% discount for members:

Programs from £3.00 + VAT - Non members £3.45 + VAT  
Sound Board @ £34.95 + VAT - Non members £40.20 + VAT

Details of tapes and kits on request, including our latest Programmable Graphics Generator.  
Membership is £4.60 inc. VAT per 6 months.  
9 MOSS LANE, ROMFORD, ESSEX.

Tel. Romford 64954.

## OVERSEAS ORDERS

Overseas readers are reminded that unless otherwise stated, postage and packing charges published in advertisements apply to the United Kingdom only.

Readers wishing to import goods from the United Kingdom are advised to first obtain from the advertiser(s) concerned an exact quotation of the cost of supplying their requirements carriage paid home.

**PROGRESSIVE RADIO** 31, CHEAPSIDE, LIVERPOOL L2 2DY  
SEMICONDUCTORS. Texas R1038 TO3 power trans 50p, 741 8 pin 22p, NE555 24p, TAG4443 SCR 45p, 723 14 PIN REGS 30p, AD 161/2 MATCHED PAIRS 70p, 2N5062 SCR 18p, TL209 RED LEDS 10 for 75p, BD238 28p, BD438 28p, MPU131 P U T s 40V 200mA, 375MWV 15p each, 2N3733 £1.75 Infra Red 0.2" LEDs 30p, Rectangular Red LED's 12p each, CA3020 I.C.'s 40p each, BY223 20p.  
MINIATURE MAINS TRANSFORMERS. ALL 240VAC PRIMARY, 6-0-6 100mA, 9-0-9 75mA, 12-0-12 50mA, all 75p each, 12V 200mA 75p, 12-0-12V, 250mA £1.25, 0-6V-0-6V 280mA £1.30.  
PULSE TRANSFORMERS. 1.1 (GPO type) 30p, 1.1 plus 1 min P C mounting 60p.  
MINIATURE SOLID STATE BUZZER. 33 x 17 x 15mm output at 3 feet 70db only 15mA drain operating voltage 2 types 6 or 12VDC 75p each.  
LOUD BUZZER. 6 x 1 1/2 volts 63p. Rotary Alarm siren, 12VDC, Red plastic body and mounting bracket 68 x 75mm £4.80p. ALUMINUM BUBBLES, moltened aluminium gong, output 8db at 3 mtrs, 12V DC 65mA, £7.95p.  
POCKET MULTIMETER. MODEL NH55 2,000 ohms per volt 1,000 volts AC/DC, 100mA DC current, 2 resistance ranges to 1 meg £5.50p.  
SOLDER SUCKER. High suction/teflon nozzle, £4.65p.  
TRANSDUCERS. 40KHz REC'SENDER £3.50 pair  
MOTORS. 3V model type 22p, 6V cassette motor £1.20p, Replacement 12VDC 8 track motors 55p.  
EX-EQUIP. B.S.R. RECORD DECK MOTORS, C129, C127 etc, 240V AC £1.20p.  
AMPHENOL COAX CONNECTORS. Plugs 47p, Sockets 42p, Elbows 90p, Reducers 13p. Back to back sockets 65p, Back to back plugs 65p.  
HIGH IMPEDANCE HEADPHONES, mono 2,000 ohms imp transducer type, adjustable band and padded ear-piece £2.75.  
SPECIAL OFFER STEREO HEADPHONES, 8 ohms, adjustable, standard stereo plug only £2.95p  
INTERCOM UNITS (can be used as baby alarm) supplied with approx 60' cable, call button 2 was £5.25 pair, 3 way £7.25p. WIRELESS INTERCOM, 2 units both operate on 240VAC and mains connected. AM frequency 180KHz, £29.95p.  
MINIATURE TIE PIN MICROPHONE. Omni, 1K imp., uses deaf aid battery (supplied) £4.95p. LOW COST CONDENSER MIKE. Stick type Omni, 600 ohms, on/off switch, standard jack plug only £2.95p. EM607 CONDENSER MICROPHONE. Highly polished metal stick mike, uni directional, 600 ohms, 30-18KHz, on/off switch only £7.95p. DYNAMIC STICK MIKE. CARDIO, dual imp., 600 ohms or 20K 70-15KHz attractive black metal case only £7.75p.  
JACKSONS C280 £3.50p each. VARIABLE CAPS. 50p each. MERCURY (TILT) SWITCH, 1"x1", 35p. Special clearance offer of tools: (1) Side Cutters, (2) Long nosed Pliers, (3) Heavy duty pliers, insulated handles, all at £1.00 each.  
CRIMPING TOOL, for standard terminals also 6 gauge stripper and wire cutter, insulated handles only £2.30.  
Cash with order please, official orders, welcome from schools etc, please add 30p post and packing. VAT inclusive. SAE for latest illustrated stock list. ALL ORDERS DESPATCHED BY RETURN POST!

# Get a great deal from Marshall's

## CRIMSON ELEKTRIK HI FI MODULES

CE 608	Power Amp	£20.09
CE 1004	Power Amp	£23.43
CE 1008	" "	£26.30
CE 1704	" "	£33.48
CE 1708	" "	£33.48
CPS 1	Power Unit	£19.52
CPS 3	" "	£23.52
CPS 6	" "	£30.00
CPR 1	Pre Amp	£32.17
CPR 1S	" "	£42.52

## SINCLAIR INSTRUMENTS

Digital Multimeter	
	PDM35 £34.50
" "	DM235 £52.50
" "	DM350 £72.50
" "	DM450 £99.00
Digital Frequency Meter	
	PFM200 £49.80
Low Power Oscilloscope	
	SC110 £139.00
TF200 Frequency Meter	£145.00
TGF 105 Pulse Generator	£85.00

## NEW

LCD Multimeter	TM351	£99.00
LCD Multimeter	TM352	£49.95
Prescaler	TP600	£37.50

## ILP HI FI MODULES

Power Amplifiers	
HY30	£7.29
HY60	£8.33
HY120	£17.48
HY200	£21.21
HY400	£31.83

Pre Amplifiers	
HY6	£6.44
HY66	£12.19

Power Supplies	
PSU30	£4.50
PSU36	£8.10
PSU60	£4.75
PSU70	£13.04
PSU180	£21.34

## MULTIPLEX NICKEL CADMIUM CELLS


Type S101 (HP4)	£0.98
Type SubC (HP11)	£1.75
Type SubD (HP2)	£1.95
Friwo Chargers for above Penlight	
4: accommodates 1-4 size HP7	£5.50
Combibox FW611: accommodates	
HP7, HP11	£13.25

**NOTE ALL PRICES NET.  
EXCLUDING VAT.  
POSTAGE/PACKING**

## New

- Presensitised PC Boards, Developer. U.V. units, Toyo miniature Fans 230v AC £9.95
- Mini Metal Detector/Voltage Tester for locating cable under plaster £9.95
- Flow/Speed Sensors for monitoring fuel consumption electronically in vehicles

## Just one of the exciting Leader range

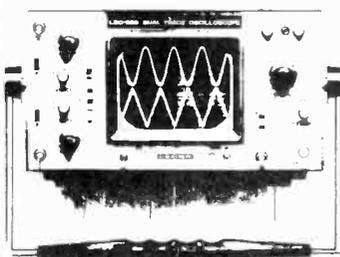

**LBO508A  
OSCILLOSCOPE**  
With 20MHz DC bandwidth and 10 mv input sensitivity on a 5" screen this universal oscilloscope is suitable for a wide range of applications.

## Send SAE for details of full range.

Marshall's 80/81 catalogue is now available by post, UK 75p post paid Europe 95p post paid: Rest of world £1.35 post paid.

A. Marshall (London) Ltd., Kingsgate House,  
Kingsgate Place, London NW6 4TA.  
Industrial Sales: 01-328 1009

Mail Order: 01-624 8582 24hr service. Glasgow. 108A Stokes Croft, Bristol.


Also retail shops: 325 Edgware Road, London W2.  
40 Cricklewood Broadway, London NW2. 85 West Regent St.  
Glasgow. 108A Stokes Croft, Bristol.

# CAMBRIDGE LEARNING ENTERPRISES

# Self Instruction Courses
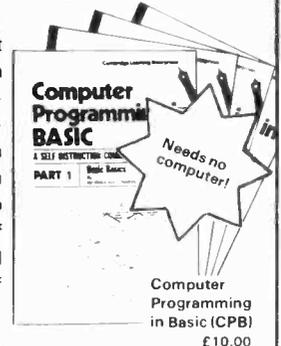
## Microcomputers are coming - ride the wave! Learn to program.

Millions of jobs are threatened but millions will be created. Learn BASIC - the language of the small computer and the most easy-to-learn computer language in widespread use. Teach yourself with a course which takes you from complete ignorance step-by-step to real proficiency, with a unique style of graded hints. In 60 straightforward lessons you will learn the five essentials of programming: problem definition, flowcharting, coding the program, debugging, and clear documentation.




**BOOK 1** Computers and what they do well; **READ, DATA, PRINT**, powers, brackets, variable names; **LET**, errors, coding simple programs. **BOOK 2** High and low level languages; flowcharting, functions, **REM** and documentation; **INPUT, IF...THEN, GO TO**; limitations of computers, problem definition. **BOOK 3** Compilers and interpreters, loops, **FOR...NEXT, RESTORE**; debugging; arrays, bubble sorting; **TAB BOOK 4** Advanced BASIC; subroutines; strings; files; complex programming; examples; glossary.

Also **THE BASIC HANDBOOK (BHB) £11.50** An encyclopaedic guide to the major BASIC dialects. A must if you use other peoples' programs

and: **ALGORITHM WRITER'S GUIDE (AWG) £4.00** Communicate by flow chart! Learn to use Yes/No questions for: procedures, system design, safety, legislation etc.
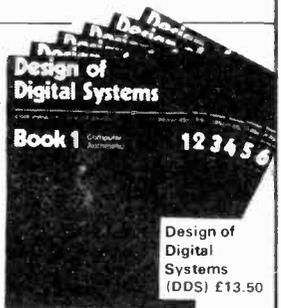
## Understand Digital Electronics

Written for the student or enthusiast, this course is packed with information, diagrams, and questions designed to lead you step-by-step through number systems and Boolean algebra to memories, counters, and simple arithmetic circuits; and finally to an understanding of the design and operation of calculators and computers.



**BOOK 1** Decimal, Octal, hexadecimal, and binary number systems and conversion between number systems; negative numbers; complementary systems. **BOOK 2** OR and AND functions; multiple input gates; truth tables; De Morgan's Laws; canonical forms; logic conventions; Karnaugh mapping; three-state and wired logic. **BOOK 3** Half, full, serial, and parallel adders; subtraction; processors and ALU's; multiplication and division. **BOOK 4** flip flops; shift registers; asynchronous, synchronous, ring, Johnson, and exclusive-OR feedback counters; ROMs and RAMS. **BOOK 5** Structure of calculators; keyboard encoding; decoding display-data; register systems; control unit; PROM; address decoding. **BOOK 6** CPU, memory organisation character representation; program storage; address modes; input/output systems; program interrupts; interrupt priorities; programming, assemblers, computers; executive programs; operating systems.

**DIGITAL COMPUTER LOGIC & ELECTRONICS. (DCL) £7.50**  
A course covering the material in italics above, but at a slower pace. (4 vols)

**GUARANTEE** - No risk to you. If you are not completely satisfied your money will be refunded without question, on return of the books in good condition.

**CAMBRIDGE LEARNING LIMITED, UNIT 21, RIVERMILL SITE, FREEPOST, ST. IVES, HUNTINGDON PE17 4BR.**

PLEASE SEND ME: - CPB (10.00)  
BHB (£11.50)  
AWG (£4.00)  
DDS (£13.50)  
DCL (£7.50)

Quantity

### FOUR WAYS TO PAY:

- 1) A U.K. cheque or a U.K. postal order (Not Eire or overseas)
- 2) A bank draft, in sterling on a London bank (available at any major bank)
- 3) Please charge my Access/M Ch  Barclay/TrustC/Visa  Am. Exp.  Diners
- 4) Or phone us with these credit card details - 0480 67446 (ansaphone) 24 hour service.

Expiry date.....

Card No.....Signed.....

**THESE PRICES COVER THE COST OF SURFACE MAIL WORLDWIDE AIRMAIL:**  
Eur, N.Af, Mid.E. add ½ to price of books: Jpn, Aus, N.Z. Pfc add ¾; elsewhere add ½

Name.....  
Address.....

Cambridge Learning Limited, Unit 21, Rivermill Site, FREEPOST, St. Ives, Huntingdon, Cambs PE17 4BR England. U.K. Delivery: up to 28 days

Reg. in Eng. No. 1328762

**THE SHAPE OF THINGS TO COME!**

# MOTOR CYCLING

April issue on sale Sat., March 14.

**Keep in touch with the dramatic changes in the motorcycling world by reading our great value-for-money magazine, every month.**

*In the April issue.*

## SPRING BIKE BUYERS GUIDE

What to look for in performance and economy when choosing a new or second hand bike.

## SUZUKI SPECIAL

Off-road sports plans for 1981 and a road test of their GSX 400 and GSX 550LT models.

## TOOLS OF THE TRADE

Home servicing pays if you've got the right equipment for a basic workshop.



## THREE BIKE TRAIL TEST

An off-road, rough rider look at the BMW R80 G/S, Can-Am 350 and Kawasaki KE 125. How do they cope when the going gets rough.

and all your regular features and tests!  
Motorcycling out every month...  
everything for the motorcyclist.  
Place a regular order! 60p.

# — CLEF KITS —

# FIRST

FOR PIANOS  
FOR STRINGS  
FOR ROTORS  
FOR RHYTHM

**IF MUSIC IS YOUR INTEREST**

Since 1972 Clef Products have consistently produced leading designs in the field of Electronic Musical Instruments, many of which have been published under the authorship of A. J. Boothman. With musical quality of paramount importance new techniques have been evolved and the latest musically valid technology has been incorporated into projects which have been successfully completed by constructors over a wide range of technical capability.

## PIANOS

Kits or Manufactured  
**SPECIALISTS SINCE 1972**



The most advanced form of Touch Sensitive action simulating piano key inertia by patented technique.

### SIX OCTAVES £207

(component kits include keyboard and may be purchased in four stages)

### 7 1/4 OCTAVES £232

Four mixable voices for serious tone variation plus electronic chorus and flanger effects. See lists for Cabinets, P.A. & Manufactured Pianos.

Back up **TELEPHONE** advice to our customers is available direct from the Designer of all kits advertised.

## STRINGS

### P.E. STRING ENSEMBLE

Versatile String Synthesizer with split keyboard facility and impressive voices. 49 note organ diode keyswitch system with four pitches plus two phase Chorus generator. Kit includes Swell Pedal.

**COMPONENT KIT £169**

## ROTOR-CHORUS


Comprehensive two speed organ rotor simulator plus a three phase chorus generator on a single 8" x 5" p.c.b. The kit includes all components for mains operation and a stereo headphone driver p.c.b. Easily integrated with existing organ/amplifier system.

**COMPONENT KIT £89.00**
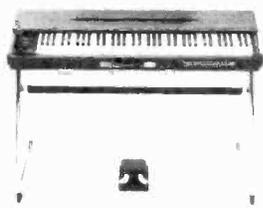
## KEYBOARDS

Our Square Front Keyboards are chosen for their superior feel to the discerning musician whilst giving adequate physical strength for the high impact playing present in the Piano application.

**49 NOTE C-C £25.00 QUANTITY**  
**73 NOTE F-F £39.00 ENQUIRIES**  
**88 NOTE A-C £47.00 WELCOME**



## MASTER RHYTHM

As published in Practical Electronics

**FULLY PROGRAMMABLE  
TWENTY-FOUR PATTERNS  
EIGHT PARALLEL TRACKS  
TWELVE INSTRUMENTS  
SEQUENCE OPERATION**



Kit includes all components to build this comprehensive User Programmable Rhythm Generator in an attractive metal case with finished case, hardware and wire.

**KIT - £79.00 BUILT - £114.00**

### OUR PRICES INCLUDE V.A.T., CARRIAGE & INSURANCE

Please send S.A.E. for complete lists or use our telephone BARCLAYCARD service. Very competitive **EXPORT** rates - in Australia please contact JAYCAR in Sydney.

**ALL INSTRUMENTS MAY BE SEEN IN OUR SHOW ROOM.**

## CLEF PRODUCTS (ELECTRONICS) LIMITED

(Dept. P.E.) 44A Bramhall Lane South, Bramhall,  
Stockport, Cheshire SK7 1AH 061-439-3297



TTL by TEXAS	74180	93p	4000 SERIES	93 SERIES	160p	VEROBOARD	TRANSISTORS	6FR80	25p	TIP33A	90p	*2N3706/7	14p
	7400	11p	74182	10p	4000	12p	AC126	25p	TIP37	11p	*2N3708/9	12p	<b>SOFTY</b>
7401	12p	74184A	150p	21p	28p	AC176	25p	BFX20	30p	TIP34A	115p	*2N3773	300p
7402	12p	74185	150p	21 x 3	65p	AC176	25p	BFX30	34p	TIP34C	160p	*2N3819	25p
7403	12p	74186	500p	9310	275p	AF116/7	50p	BFX84.5	30p	TIP35A	225p	*2N3820	50p
7404	14p	74186	500p	9311	275p	AF116/7	50p	BFX86/7	30p	TIP35C	225p	*2N3823	70p
74504	60p	74190	90p	9312	160p	AD149	70p	BFX88	30p	TIP36A	270p	*2N3866	90p
7405	18p	74191	90p	9316	165p	AD149	70p	BFX90	30p	TIP36B	270p	*2N3867	90p
7406	36p	74192	90p	9316	165p	AU107	250p	BFY50	30p	TIP36C	340p	*2N3903/4	18p
7407	11p	74193	90p	9321	225p	BC107/8	11p	BFY51/2	30p	TIP41A	65p	*2N3905/6	20p
7408	17p	74194	90p	9322	150p	BC109	11p	BFY56	33p	TIP41C	78p	*2N4037	65p
7409	19p	74195	95p	9334	340p	BC111	20p	BFY90	30p	TIP42A	70p	*2N4058/9	12p
7410	15p	74196	95p			BC147/8	9p	BFY90	30p	TIP42C	82p	*2N4060	12p
7411	24p	74197	90p	<b>LINEAR I.C.s</b>	600p	BC149	9p	BFY90	30p	TIP42D	82p	*2N4061/2	18p
7412	20p	74198	100p	*AY1 0212	600p	BC157/8	10p	BS119/20	20p	TIP3053	70p	*2N4123/4	27p
7413	20p	74199	150p	*AY1 1313	668p	BC159	11p	BU104	225p	TIS43	34p	*2N4125/27	27p
7414	30p	74201	150p	*AY1 3200	320p	BC169C	12p	BU108	250p	TIS93	30p	*2N4271	90p
7414	30p	74221	160p	*AY1 5050	1400p	BC172	12p	BU109	225p	*TX108	12p	*2N4871	60p
74C14	90p	74C221	150p	AY3-8910	800p	BC177/8	17p	BU109	225p	*TX300	13p	*2N5087	27p
7416	27p	74251	140p	AY3-8912	650p	BC182/3	10p	BU208	200p	ZTX500	15p	*2N5092	27p
7417	27p	74259	250p	AYS-1224A	240p	NE556	60p	BU208	200p	*TX502	18p	*2N5199	90p
7420	17p	74265	90p	*AYS 1315	775p	NE556	60p	*E300	50p	*TX504	30p	*2N5199	90p
7421	22p	74279	110p	*AYS-1317A	800p	NE564	425p	*J310	50p	*2N457A	250p	*2N5191	83p
7423	34p	74283	160p	CA3028A	90p	NE565	130p	*M2950	225p	*2N696	35p	*2N5194	90p
7425	30p	74284	180p	*CA3046	70p	NE566	150p	*M2951	90p	*2N698	45p	*2N5245	40p
7426	40p	74285	400p	*CA3048	225p	NE567	1425p	*M2952	90p	*2N698	45p	*2N5286	50p
7427	34p	74290P	400p	*CA3080E	72p	NE571	425p	*M3000	225p	*2N706A	20p	*2N5401	50p
7428	36p	74291	400p	RC436	170p	NE571	425p	*M3000	225p	*2N706A	20p	*2N5457/8	40p
7430	17p	74294	200p	RC436E	170p	NE553A	25p	*M3000	225p	*2N930	18p	*2N5459	40p
7431	30p	74298	200p	*CA3090E	275p	NE553A	25p	*M3000	225p	*2N930	18p	*2N5460	60p
7432	30p	74365	150p	CA3130E	100p	RC4195	400p	*M3000	225p	*2N930	18p	*2N5485	44p
7433	40p	74366	150p	CA3140E	50p	RC4195	400p	*M3000	225p	*2N930	18p	*2N5485	44p
7437	35p	74368	150p	CA3160E	100p	S5668	275p	*M3000	225p	*2N930	18p	*2N5485	44p
7438	35p	74369	150p	CA3160E	100p	*SAD1024A	1250p	*M3000	225p	*2N930	18p	*2N5485	44p
7439	35p	74390	160p	CA3162E	140p	SFF96364	1100p	*M3000	225p	*2N930	18p	*2N5485	44p
7440	17p	74393	160p	CA3189E	300p	SN76477	75p	*M3000	225p	*2N930	18p	*2N5485	44p
7441	70p	74490	225p	CA3189E	300p	TA7205	75p	*M3000	225p	*2N930	18p	*2N5485	44p
7442A	60p	74490	225p	CA3189E	300p	TA7205	75p	*M3000	225p	*2N930	18p	*2N5485	44p
7443	112p	74LS SERIES	40p	HA1388	260p	*TA661A1811	225p	*M3000	225p	*2N930	18p	*2N5485	44p
7444	112p	74LS02	14p	ICL7106	850p	*TA8651	200p	*M3000	225p	*2N930	18p	*2N5485	44p
7445	100p	74LS04	14p	ICL7106	850p	*TA8651	200p	*M3000	225p	*2N930	18p	*2N5485	44p
7446A	93p	74LS05	25p	ICM7555	55p	*TA8651	200p	*M3000	225p	*2N930	18p	*2N5485	44p
7447A	75p	74LS05	25p	LF351	45p	*TA8651	200p	*M3000	225p	*2N930	18p	*2N5485	44p
7448	80p	74LS08	25p	LF356	95p	*TA8651	200p	*M3000	225p	*2N930	18p	*2N5485	44p
7450	17p	74LS10	20p	LM301A	27p	*TA8651	200p	*M3000	225p	*2N930	18p	*2N5485	44p
7451	17p	74LS11	40p	LM311	70p	*TA8651	200p	*M3000	225p	*2N930	18p	*2N5485	44p
7453	17p	74LS14	60p	LM318	200p	*TA8651	200p	*M3000	225p	*2N930	18p	*2N5485	44p
7454	17p	74LS14	60p	LM319	70p	*TA8651	200p	*M3000	225p	*2N930	18p	*2N5485	44p
7460	17p	74LS20	20p	LM324	70p	*TA8651	200p	*M3000	225p	*2N930	18p	*2N5485	44p
7470	36p	74LS21	40p	LM339	75p	*TA8651	200p	*M3000	225p	*2N930	18p	*2N5485	44p
7472	30p	74LS27	38p	LM339	75p	*TA8651	200p	*M3000	225p	*2N930	18p	*2N5485	44p
7473	34p	74LS30	20p	LM348	95p	*TA8651	200p	*M3000	225p	*2N930	18p	*2N5485	44p
7474	24p	74LS32	27p	LM377	175p	*TA8651	200p	*M3000	225p	*2N930	18p	*2N5485	44p
7475	30p	74LS33	36p	LM380	105p	*TA8651	200p	*M3000	225p	*2N930	18p	*2N5485	44p
7475	30p	74LS33	36p	LM381A	180p	*TA8651	200p	*M3000	225p	*2N930	18p	*2N5485	44p
7475	30p	74LS38	36p	LM386	95p	*TA8651	200p	*M3000	225p	*2N930	18p	*2N5485	44p
7476	35p	74LS42	70p	LM386	95p	*TA8651	200p	*M3000	225p	*2N930	18p	*2N5485	44p
7480	50p	74LS47	70p	LM709	36p	*TA8651	200p	*M3000	225p	*2N930	18p	*2N5485	44p
7481	100p	74LS55	30p	LM710	50p	*TA8651	200p	*M3000	225p	*2N930	18p	*2N5485	44p
7482	84p	74LS57	50p	LM715	35p	*TA8651	200p	*M3000	225p	*2N930	18p	*2N5485	44p
7483A	70p	74LS74	40p	LM733	100p	*TA8651	200p	*M3000	225p	*2N930	18p	*2N5485	44p
7484	100p	74LS75	40p	LM741	100p	*TA8651	200p	*M3000	225p	*2N930	18p	*2N5485	44p
7485	100p	74LS76	48p	LM747	70p	*TA8651	200p	*M3000	225p	*2N930	18p	*2N5485	44p
7486	30p	74LS83	70p	LM748	35p	*TA8651	200p	*M3000	225p	*2N930	18p	*2N5485	44p
7489	210p	74LS85	80p	LM748	35p	*TA8651	200p	*M3000	225p	*2N930	18p	*2N5485	44p
7490A	38p	74LS86	40p	LM748	35p	*TA8651	200p	*M3000	225p	*2N930	18p	*2N5485	44p
7491	80p	74LS90	50p	LM748	35p	*TA8651	200p	*M3000	225p	*2N930	18p	*2N5485	44p
7492A	46p	74LS93	60p	LM748	35p	*TA8651	200p	*M3000	225p	*2N930	18p	*2N5485	44p
7493A	38p	74LS107	45p	LM748	35p	*TA8651	200p	*M3000	225p	*2N930	18p	*2N5485	44p
7494	84p	74LS112	100p	LM748	35p	*TA8651	200p	*M3000	225p	*2N930	18p	*2N5485	44p
7495A	70p	74LS123	80p	LM748	35p	*TA8651	200p	*M3000	225p	*2N930	18p	*2N5485	44p
7496	65p	74LS123	80p	LM748	35p	*TA8651	200p	*M3000	225p	*2N930	18p	*2N5485	44p
7497	180p	74LS125	80p	LM748	35p	*TA8651	200p	*M3000	225p	*2N930	18p	*2N5485	44p
74100	130p	74LS126	80p	LM748	35p	*TA8651	200p	*M3000	225p	*2N930	18p	*2N5485	44p
74104	65p	74LS132	80p	LM748	35p	*TA8651	200p	*M3000	225p	*2N930	18p	*2N5485	44p
74105	65p	74LS133	80p	LM748	35p	*TA8651	200p	*M3000	225p	*2N930	18p	*2N5485	44p
74110	55p	74LS136	80p	LM748	35p	*TA8651	200p	*M3000	225p	*2N930	18p	*2N5485	44p
74111	70p	74LS151	100p	LM748	35p	*TA8651	200p	*M3000	225p	*2N930	18p	*2N5485	44p
74116	200p	74LS153	80p	LM748	35p	*TA8651	200p	*M3000	225p	*2N930	18p	*2N5485	44p
74118	130p	74LS154	200p	LM748	35p	*TA8651	200p	*M3000	225p	*2N930	18p	*2N5485	44p
74119	210p	74LS155	200p	LM748	35p	*TA8651	200p	*M3000	225p	*2N930	18p	*2N5485	44p
74120	110p	74LS155	200p	LM748	35p	*TA8651	200p	*M3000	225p	*2N930	18p	*2N5485	44p
74121	28p	74LS158	90p	LM748	35p	*TA8651	200p	*M3000	225p</				

# SERVICE TRADING CO

## FT3 NEON FLASH TUBE

High intensity multi turn high voltage, neon glow discharge flash tube. Design for ignition timing etc. £1.50. P & P 25p (£2.01 inc. VAT) 3 for £3. P & P 50p (£4.03 inc. VAT & P).

## WHY PAY MORE?

MULTI RANGE METER Type MF15A a.c. d.c. volts 10 50 250 500 1000 Ma 0.5 0.10 0.100 Sensitivity 2000V 24 range diameter 133 by 93 by 46mm including test leads. Price £7.00 plus 50p P & P (£8.63 inc. VAT & P).




## METERS (New) - 90 mm DIAMETER

A.C. Amp., Type 62T2, 0-1A, 0-5A 10A, 0-20A, 50A  
A.C. Volt. 0-150V, 0-300V  
D.C. Amp., Type 65C5 0-2A, 5A 0-10A, 0-20A, 0-50A, 0-100A  
D.C. Volt. 15V, 30V

All types £3.50 ea. + P & P. 50p (£4.60 inc. VAT), except 0-50A, 0-100A D.C. price £5.00 + P & P (£6.33 inc. VAT).
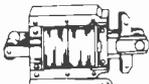
## HEAVY DUTY SOLENOID, mf by

Magnetic Devices. 240V. A.C. intermittent operation. Approx 20 lb pull at 1.25 in. Ex-equip. Tested. Price £5.50 - 75p. P & P (£7.19 inc. VAT & P).



## 12V D.C. SOLENOID

12V D.C. heavy duty Solenoid 4 Kp. pull. Easily removable from plate. Ali chassis containing 4.24V D.C. Push Solenoids (1 1/2 lb. approx) 5-filg Counter 6 min photo cells, Sub-min. Micro-switches etc. etc. Ex-equip. London Transport Printer. Price: £9.00 £1.00 p & p (total incl. VAT £11.50).

12V D.C. Solenoid approx 1lb pull. Price £1.40 + p & p 30p (total incl. VAT £1.96).

## SOLENOIDS

WESTOOL SERIES D6 Model A3 24V D.C. Price £1.50 - 50p p & p. (Total incl. VAT £2.30)

WESTOOL SERIES D4 Model A, 24V, D.C. Price £1.00 - 30p p & p. (Total incl. VAT £1.50)

AG/GT 24V, D.C. 70 ohm Coil Solenoid Push or Pull. Adjustable travel to 3/16 in. Fitted with mounting brackets and spark suppressor. Size: 100 x 65 x 25 mm. Price: 3 for £2.40 - 30p. P & P. (min 3 off) (£3.11 inc. VAT & P).

## 800 WATT DIMMER SWITCH

Easily fitted. Will control up to 800 W. of all lights except fluorescent at mains voltage. Price: £3.90 - 50p p & p. (£5.06 inc. VAT).

REED SWITCHES. Size 28mm x 4mm dia. Price: 10 for £1.00 - p & p. 20p. (total incl. VAT £1.38). 100 for £8.00 - o & p. 30p. (total incl. VAT £9.55).

## MICRO SWITCHES

Sub. Min Honeywell Lever m/s type 3115m 906ft. 10 for £3.50 post paid (£4.03 incl. VAT)

Button type (Pye) 10 for £3.00 (£3.45 incl. VAT)

Short Lever type 16amp rating (Grouzet) £4.00 (£4.60 incl. VAT)

Roller Type (Bonnella) 10 for £3.50. (£4.03 incl. VAT) N.M.S. D.P. C/O lever m/s switch mfg. by Cherry Co. USA. Precious metal low resistance contacts. 10 for £2.25 P. & P. 30p. Total incl. VAT £2.93 (min 10).

## LOCAL STATE EHT UNIT

Input 230V ac. Fully isolated output 10mm spark. Approx. 15Kv Built in 10 sec Timer. Easily modified for 20 sec. 30 sec. to a continuous operation. Designed for boiler ignition. Dozens of uses in the field of physics and electronics, eg. supplying neon or argon tubes etc., EHT. starter or laser xenon. CSR lamps VAN de GRAFF generator, loss of vacuum detector, OJDINI coils etc. Size: Length 155mm, width 85mm, height 50mm. Weight 530 grammes. Price £5.00 - 75 pence post & packing. Total incl. VAT £6.61.

## A.E.G. CONTACTOR

Type L56/L11 Coil 240V 50 Rs. Contacts - 3 make- 600V 20amp 1 break; 600V 20 amp. Price: £5.50 + 50p P. & P. (£6.90 inc. VAT & P).

ARROW-HART MAINS CONTACTOR, Cat. No. 130A/30 Coil 250V, or 500V. A.C. Contacts, 3 make 50 amp up to 660V. A.C. 20 h.p. at 440V, 3 phase 50 Hz. Price: £7.75 + p & p. £1.00 (incl. VAT, total £10.06). N.M.S.

## SMITH BLOWER

Type FB. 1705. Small, quiet, smooth running, 240V. A.C. operation. Output aperture 45x40cm. Overall size 135x165 cm. Flange mounting. Price: £4.25. P & P. 75p. (Total: £5.75 inc. P. & VAT. N.M.S.)

## CENTRIFUGAL BLOWER UNIT

Powered by GEC 230/250V, 2850 r.p.m. motor producing approx. 120 c.f.m. Aperture 65-90mm. Overall size 222 x 225 x 195mm incl. Starter. Capac. Price: £16.00 - £2.00 p & p. (Total incl. VAT £20.70)

## 24 volt. D.C. BLOWER UNIT

Precision 24 volt D.C. 0.8 amp Blower that works well on 12V 0.4 amp D.C. Producing 30 cu ft. min at normal air pressure. £4.50 P & P 75p (incl. VAT £6.04) N.M.S.

## INSULATION TESTERS NEW!

Test to I.E. Spec Rugged metal construction suitable for bench or field work constant speed clutch Size L 8in W 4in H 6in weight 6lb. 500V, 500 megohms. £49.20 80p (£57.27 incl. VAT & P.) 1,000V 1,000MΩ, £55. Post 80p (£64.17 incl. VAT & P. SAE for leaflet).

Yet another outstanding offer.

IMFD 600V Dubilier wire ended capacitors. N.M.S. 10 for £1.50 p & p 50p (£2.30 inc. VAT + p & p) (Min 10).

## VARIABLE VOLTAGE TRANSFORMERS

### INPUT 230/240V a.c. 50/60 OUTPUT 0-260V

200 watt (1 amp inc. a.c. voltmeter)	£14.50
0.5 KVA (2 1/2 amp (MAX))	£18.00
1 KVA (5 amp MAX)	£24.00
2 KVA (10 amp MAX)	£39.00
3 KVA (15 amp MAX)	£47.00
5 KVA (25 amp MAX)	£76.00
10 KVA (50 amp MAX)	£168.00
15 KVA (75 amp MAX)	£260.00



### 3-PHASE VARIABLE VOLTAGE TRANSFORMERS

Dual Input 200-240V, or 380-415V. Star connected.  
3KVA 5 amp per phase max. £106.43 Carriage, packing & VAT extra.  
6KVA 10 amp per phase max. £159.37  
10KVA 16 amp per phase max. £327.43

### LT TRANSFORMERS

13 0 13V at 1 amp £2.50 P & P 50p (£3.45 inc. VAT)  
0-15V 24 amp 0-30 at 12 amp £20.40. plus P. & P. £2.30. Total incl. VAT £26.11.  
0-6V/12V at 20 amp £16.20 P & P £1.00 (£19.78 inc. VAT)  
0-12V at 20 amp or 0-24V at 10 amp £14.90 P & P. £1.50 (£18.86 inc. VAT & P)  
0-6V/12V at 10 amp £9.10 P & P £1.50 (£12.19 inc. VAT)  
0-6V/12V/17V/18V/20V at 20 amp £20.90 P & P. £2.00 (£26.34 inc. VAT & P)  
0-10V/17V/18V at 10 amp £11.55 P & P £1.80 (£15.35 inc. VAT)  
Other types in stock. phone for enquiries or send sae for leaflet

### HY-LIGHT STROBE KIT MK IV

Latest type Xenon white light flash tube. Solid state timing and triggering circuit 230/240V a.c. operation. Designed for larger rooms, halls, etc. Speed adjustable 1-20 f.p.s. Light output greater than many ISO called 4 joule strobes. Hy-Light Strobe Kit Mk IV. £22.00 - £1.50 P & P (incl. VAT total £27.03). Specially designed case and reflector for Hy-Light. £9.00. Post £1.50 (£12.08 incl. VAT & P.) Super Hy-Light Strobe (approx. 16 joules) Price £33. P & P £1.50 (incl. VAT total £39.68). Suitable case £11.00 + £1.50 P & P (£14.38 incl. VAT & P & P.) Super Hy Light Strobe Kit. details on receipt of foolscap sae.

### XENON FLASHGUN TUBES

Range available from stock. S.A.E. for details.

### ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES

4ft. 40 Watt £8.70. inc. VAT £10.00 (callers only).  
2ft. 20 Watt £6.20. Post 75p (£7.99 inc. VAT + P.) (For use in stan bi-pin fittings).  
12in. 8 watt £2.80. Post 35p (£3.62 inc. VAT + P.)  
9in. 6 watt £2.25. Post 35p (£2.99 inc. VAT + P.)  
6in. 4 watt £2.25. Post 35p (£2.99 inc. VAT + P.)  
Complete ballast unit, for either 6", 9" or 12" tube 230V AC op £4.50. Post 45p (£5.69 inc. VAT + P.) Also available for 12V DC op £4.50. Post 45p (£5.69 inc. VAT + P.)  
400 watt UV lamp and ballast complete £38.00. Post £3.50 (£47.73 incl. VAT + P.) 400 watt UV lamp only £14.00. Post £1.50 (£17.83 incl. VAT + P.)

### PROGRAMME TIMERS

240V A.C. operation. 12 individually adjustable cams. £7.50 + 75p P. & P. (£9.49 inc. VAT). R.T.  
6 adjustable 6 fixed cams. Price £6.00 - 75p p & p. (£7.76 inc. VAT) R & T

### Superior Quality Precision Made NEW POWER RHEOSTATS

New ceramic construction embedded winding heavy duty brush assembly. continuously rated.  
15W WATT 10/25 50, 100/250/500/1kΩ/1.5kΩ. £2.90. Post 20p (£3.45 inc. VAT & P.)  
50 WATT 250Ω £2.90. Post 25p (£3.62 inc. VAT & P.)  
100 WATT 1.5, 10, 25, 50, 100, 250/500/1kΩ/1.5kΩ/2.5kΩ/3.5kΩ £6.90 p & p. 35p (£8.34 incl. VAT).  
Black, Silver, Skirted knob calibrated in Nos 1.9 1 1/2 in dia brass bush. Ideal for above Rheostats 24p each

### RELAYS

Wide range of AC and DC relays available from stock. Phone or write in your enquiries.  
Other types available - phone for details. N.M.S.  
230/240V A.C. Relays: Arrow 2 c/o 15amp £1.50 (£1.96 inc. VAT & P.)  
Open type 3 c/o. 10 amp £1.10 (£1.50 incl. VAT & P.)  
230/240V A.C. 3Co. 11 pin base. Sealed, 5 amp contacts £1.35 plus P & P. 20p. Total incl. VAT £1.78.  
D.C. Relay, sealed 6/12V. D.C. 2Co. 10 amp contacts. Single hole fixing. Push on contacts. £1.30 plus P. & P. 20p. Total incl. VAT £1.73.  
12V D.C. 2Co. open type 10 amp contacts £1.25 plus P. & P. 20p. Total incl. VAT £1.67.  
24V D.C. 2Co. 7 amp contacts. Sealed, octal base. £1.30 plus P. & P. 20p. Total incl. VAT £1.73.  
Mercury Wetted contact relay mfg. by Clare. Type HGSM 1003 18/24V D.C. lco. £2.00 plus P. & P. 20p. Total incl. VAT £2.53.  
Reed Relay mfg. by Alma Type CPR1/D 6/9V D.C. 700 ohm. coil. 5 for £2.50 plus P. & P. 50p. Total incl. VAT £3.45.  
D.C. Relays: Sealed 12V. 1 c/o 7 amp octal base £1.00 (£1.38 inc. VAT & P.) Sealed 12V. 3 c/o 7 amp 11-pin £1.35 (£1.78 inc. VAT & P.) 24V. Sealed 3 c/o 7 amp 11-pin £1.35 (£1.78 inc. VAT & P.) lamps contact rating) P & P on any Relay 20p.  
KMKI Relay. 230V. A.C. 1 c/o. open type 10 amp contact. mf by "keyswitch" 80p. + 20p. p & p. (£1.15 incl. VAT). 5 for £3.75 postpaid (£4.32 incl. VAT).  
Hellermann Deutsch. Hermetically sealed sub-min. Relay 12-24V. D.C. 2 c/o. 850 ohm coil. 0.2 pitch. P.C. mounting. L 20mm W. 10mm. H. 12mm. Fraction of maker's price. £2.50 postpaid (£2.88 incl. VAT). N.M.S.

## GEARED MOTORS

7 1/2 rpm KLAXON motors approx. 25lb inch  
28rpm WYNSCALE motors approx. 20lb inch  
7 1/2 rpm WYNSCALE motor approx. 10lb inch  
Above three motors are designed for 110V. A.C. supplied with auto transformer 240V. A.C. operation. £9.25 p & p 75p. Total incl. VAT £11.50. N.M.S.



56 rpm 240V a.c. 50lb in 50Hz  
0.7 amp Shaft length 35mm Dia 16mm Wt 6kg 600g mf FRACMO.  
Price £15.00 + £1.50 P & P (£18.98 incl. VAT) N.M.S.



100 rpm 110V a.c. 115lb in 50Hz 28 amp single phase split capacitor Immense power



Totally enclosed. In-line gearbox. Length 250mm. Dia. 135mm. Spindle dia. 15.5mm. length 145mm. Tested. Price: £12.00 + £1.50 P & P. (£15.53 incl. VAT). R. & T. Suitable Transformer for 230/240V operation. Price £8.00 + 75p. P & P (£10.60 inc. VAT).

200 rpm 35 lbs in 115V 50Hz  
Pncr £16.00 + £1.50 P & P (£20.13 incl. VAT) N.M.S.  
Suitable Transformer for 230 240V a.c. Price £8.00 + £1.00 P & P (£10.35 incl. VAT) N.M.S.

1 rpm 230/240V. a.c. Synchronous geared Motor, mf. HAYDON.  
2 rpm 230/240V. a.c. Synchronous geared Motor, mf. CROUZET. Either type £3.90 - 30p. P & P. (£4.83 inc. VAT).



N.E.C. geared Motor 152 R.P.M. 200lb. inch. 230 A.C. 50Hz. Ratio 9.2 to 1 Non reversible. Incl. capacitors Fraction of makers Price £35.00 plus carriage and VAT. Also available 230A C 60Hz 182 R.P.M. 20lb in as above.  
42 R.P.M. 110 A.C. 50Hz. 100lb incl reversible will operate on 230A C Speed remains at 42R.P.M but torque reduces by 50%. Price £16.00. P & P. £1.00 (total incl. VAT & p. £19.55) N.M.S.

### INCREDIBLE OFFER

Geared Motor 120 rpm approx. 15 lb.in. 230V A.C. Cont. Rating Non-reversible. Size 150mm - 90mm - 85mm spindle 8mm dia - 30 mm long. Complete with capacitor and relay for max. load starting. Offered at mere fraction of mfrs price - £11.50 incl. of p. & p & VAT



### 24V. D.C. GEARED MOTOR

24V. D.C. 200 rpm 10lbs/in. continuously rated geared Motor mfg. by either Parvalux or Carter. Easily removable from heavy ali chassis containing 9-24V D.C. Solenoids, microswitches, friction clutch precision gearing etc. Ex-equipment London Transport Ticket Printer. Price: £11.00 - £2.00 p & p (total incl. VAT £14.95).

### 24V. D.C. REVERSIBLE MOTOR

Parvalux type SD12L 24 D.C. shunt wound Motor, either 133 rpm 65lbs in Gearbox ratio 30:1 Current 6.8 amp. Rating continuous Will operate on reduced power and speed at 9V D.C. or less Size Dia. 16mm. Width 150mm. Shaft dia. 16mm Price £16.00 £2.00 p & p (£20.70 incl. VAT) N.M.S. or 60 rpm 100lb in rating Price as above. N.M.S.  
100W Rheostat 1 ohm speed control available £6.90 (£7.94 incl. VAT).

### 230V a.c. FAN ASSEMBLY.

Powerful continuously rated a.c. motor complete with 5 blade 6 in or 4 blade 3 in aluminium fan. Price £3.50. P & P 65p (£4.77 incl. VAT & P.)



### ROTARY CARBON VANE VACUUM & COMPRESSOR.

Direct coupled to 1/3 hp 110/115V. A.C. Motor 4.2 amp 1380 rpm Motor manu. by A.E.I. or G.E.C. Pump by Williams Max Vac 25" Hg. Max. pressure cont 10 p.s.i. Int. 15 p.s.i. Max air-flow 3 c.f.m. at 0 HG Price: £30.00 - £3.00 P & P. (£37.95 incl. VAT) N.M.S.

Suitable transformer for 240V. op £10.00 P & P £2.00 (£13.80 incl. VAT) N.M.S.

### A.C. Wkg. TUBULAR CAPACITORS.

Fraction of makers price. Motor start etc.			
15 mfd. 440V A.C.	60p	5.4 mfd 280V. A.C.	75p
2 mfd. 250V A.C.	60p	6.5 mfd 280V A.C.	£1.00
2 mfd. 450V A.C.	75p	7.5 mfd 200V A.C.	£1.00
2.2 mfd 440V. A.C.	75p	10 mfd. 250V A.C.	£1.00
3 mfd 440V. A.C.	£1.00	19 mfd 280V. A.C.	£2.00
4.1 mfd 440V. A.C.	£1.00	20 mfd 250V A.C.	£2.25
5 mfd 400V A.C.	£1.25		
5.3 mfd 160V A.C.	60p		

P & P. up to 2.5 mfd 25p 3 mfd tp 20 mfd 50p All plus V.A.T. N.M.S.

### Time Switch Venor Type

ERD Time switch 200/250V a.c. 30 amp contact 2 on/2 off every 24 hrs. at any manually pre-set time 36 hour Spring Reserve and day omitting device. Built to highest Electricity Board specification. Price £9.00. P. & P. 75p (£11.21)



### SANGAMO WESTON TIME SWITCH

Type S251 200 250V a.c. 2 on 2 off every 24 hours 20 amps contacts with override switch dia 4 x 3 price £8.50 P & P 50p inc. VAT £10.35. Also available with Solar dial R & T

N.M.S. New Manufacturers Surplus R & T Reconditioned and Tested

# SERVICE TRADING CO


57 BRIDGMAN ROAD, CHISWICK, LONDON W4 5BB 01-995 1560

ACCOUNT CUSTOMERS MIN. ORDER £10-00

All Mail Orders Callers Ample Parking Space Showroom open Mon-Fri.

Personal callers only Open Saturdays 9 Little Newport Street, London WC2H 7JJ Phone 01-437 0576

# Make it for a Song!

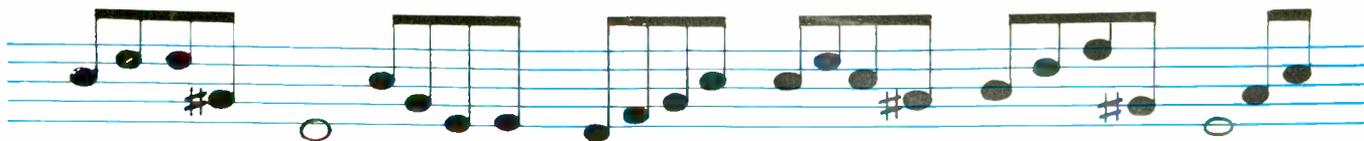


## The New **Maplin Matinée**

**Amazing Value**  
**For Only** **£299.95** + £99.50 for cabinet if required.

Easy to build. Latest technology – means less cost, less components and 80% less wiring. Comparable with organs selling for up to £1,000.00. Two 49-note manuals. 13-note pedalboard. All organ voices on drawbars. Preset voices: Banjo, Accordion, Harpsichord, Piano, Percussion. Piano sustain Sustain on both manuals, and pedalboard.

Electronic rotor, fast and slow. Vibrato and Delayed vibrato. Reverb. Manual and Auto-Wah. Glide (Hawaiian Guitar Sound). Single finger chording plus memory. 30 Rhythms! 8-instrument voicing. Major, Minor and Seventh chords. Unique walking bass lines with each rhythm. Unique countermelody line with each rhythm. Truly amazing value for money.

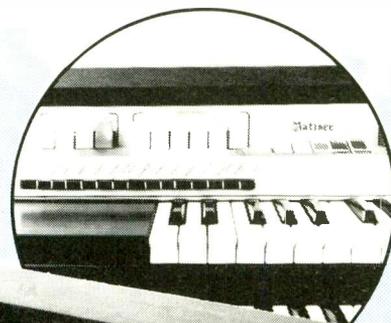For full construction details contact  
Maplin Electronic Supplies Ltd.



The complete buyers' guide to electronic components. With over 300 pages, it's a comprehensive guide to electronic components with thousands of photographs and illustrations and page after page of invaluable data. Get a copy now – it's the one catalogue you can't afford to be without.

Post this coupon now for your copy of our 1981 catalogue price £1  
Please send me a copy of your 320 page catalogue. I enclose £1 (Plus 25p p&p) If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the UK send £1.68 or 12 International Reply Coupons I enclose £1.25

Name \_\_\_\_\_

Address \_\_\_\_\_

PE.4.81

# MAPLIN

Maplin Electronic Supplies Ltd  
All mail to P.O. Box 3, Rayleigh, Essex SS6 8LR  
Telephone: Southend (0702) 554155 Sales (0702) 552911  
Shops:  
159-161 King Street, Hammersmith, London W6 Telephone: (01) 748 0926  
284 London Road, Westcliff on Sea, Essex Telephone: Southend (0702) 554000  
Both shops closed Mondays.

Catalogue now on sale in all branches of WHSMITH  Price £1.00