

PRACTICAL

ELECTRONICS

MARCH 1982

75p

Use Your
FREE




TRANSISTORS


with the

6 PROJECTS

in this issue!!

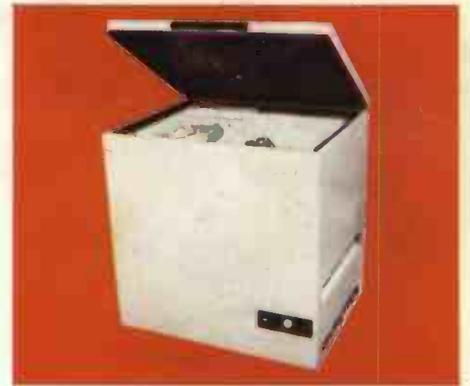

What does
it cost
to run??

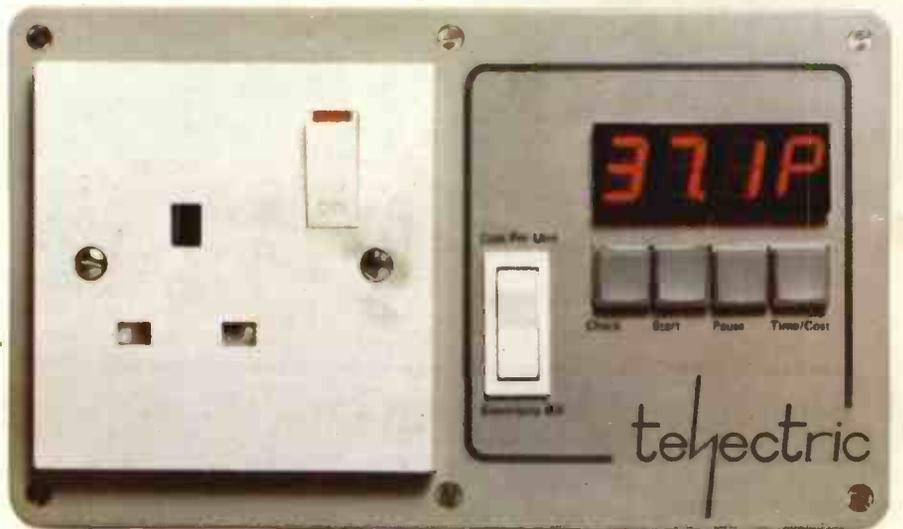

telectric Cost Monitor

Plus... **EMERGENCY LIGHT**

Much more than just kits quite simply the best way to make music . . .

The smart contemporary styling of the 'black-boxes' contain the easy-to-build advanced electronics that produce everything from high grade amplification to complex lighting effects. These units are among the finest of their kind available and combine, as do all the Powertran kits, constructional ingenuity with high grade performance capability.

The finest materials and components are used throughout and the easy-to-follow fully illustrated and diagrammed manuals make building as pleasurable as operating.

Each unit can, of course, perform its independent function – but it is compatible with its fellows (same cabinet sizes and the same quality and professional finish) to enable you to assemble an impressive bank of wholly controllable power.



MPA 200 – a 100W amplifier with professional finish and performance at an exceptionally low price. Adaptable inputs mixer accepts a variety of sources. Straightforward construction – an excellent beginners kit. **COMPLETE KIT £49.90 (+ VAT)**


CHROMATHEQUE 5000 – 5 channel lighting effect system. Sound to light, strobe to music level, random or sequential effects – each channel handles up to 500W yet minimal wiring is needed with our single-board design. **COMPLETE KIT £49.50 (+ VAT)**

ETI VOCODER – 14 channel for maximum versatility and high intelligibility; each channel has independent level control. 2 input amplifiers – for speech/external excitation – each with level control and tone control. The Vocoder is a superb machine capable of infinite variety of operation. Construction with our easy to follow, comprehensive builders' manual – is challenging yet within the scope of most enthusiasts. **COMPLETE KIT £175 + VAT)**

SP2 200 – 2 channel 100W amplifier. Two of the rugged, reliable and economic amplifiers from the MPA200 are fed by separate power supplies from a common toroidal transformer. Fully finished metalwork, fibreglass PCBs, controls, wire – everything you need to make this powerful unit. **COMPLETE KIT £64.90 + VAT)**



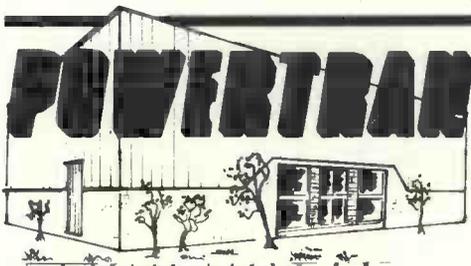DJ90 STEREO MIXER – a versatile new mixer with 2 stereo inputs for magnetic cartridges, a stereo auxiliary input and mike input. Auto planning for fast or slow, slider controls, multi-mixing, ducking, interrupt, input modulation – everything . . . yet still under £100! (Our console below shows the mixer neatly teamed with a Chromatheque and SP2 200) **COMPLETE KIT £97.50 + VAT)**



PRICE STABILITY: Order with confidence. Irrespective of any price changes we will honour all prices in this advertisement until April 30th, 1982, if this month's advertisement is mentioned with your order. Errors and VAT rate changes excluded.

EXPORT ORDERS: No VAT. Postage charged at actual cost plus £1 handling and documentation.

U.K. ORDERS: Subject to 15% surcharge for VAT. No charge is made for carriage, or at current rate if changed.

SECURICOR DELIVERY: For this optional service (U.K. mainland only) add £2.50 (VAT inclusive) per kit. FREE ON ORDERS OVER £100.

SALES COUNTER: If you prefer to collect kit from the factory, call at Sales Counter. Open 9 a.m.–12 noon, 1–4.30 p.m.

Monday-Thursday.



POWERTRAN ELECTRONICS, PORTWAY INDUSTRIAL ESTATE, ANDOVER, HAMPSHIRE SP10 3WN. Telephone Andover (0264) 64455

MORE SUPERB KITS IN OUR CATALOGUE



PRACTICAL ELECTRONICS

VOLUME 18

No. 3

MARCH 1982

CONSTRUCTIONAL PROJECTS

TELETRIC ELECTRICITY COST MONITOR Part 1 by <i>Stephen Day BSc Eng MIEE</i>	22
Can provide instant and long-term cost monitoring of almost any electrical appliance	
EMERGENCY LIGHT by <i>Stephen Ibbs</i>	28
Rechargeable, with automatic cut-in	
FREE TRANSISTOR PROJECTS	32
Six circuits specially designed around your free transistors	
AUTO LIGHT, CAR BATTERY CONDITION INDICATOR, AF/RF GENERATOR, BENT WIRE GAME, DOUBLE SIREN, LIQUID ALARM	
INFRA-RED REMOTE CONTROL Part 2 by <i>Bart Trepak</i>	40
Construction and applications	
PE RANGER BASE STATION Part 3 by <i>Michael Tooley BA and David Whitfield MA MSc</i>	44
Testing and alignment	
PE ROBOTS Part 5 by <i>Richard Becker, Tim Orr and Richard Monkhouse</i>	56
Resume, completion of hardware, and software prologue	
TV CAMERA Part 3 by <i>Philip Gaffney</i>	62
Assembly and setting up	

GENERAL FEATURES

DIGITAL DESIGN TECHNIQUES Part 8 by <i>Tom Gaskell BA</i>	48
Memories and Microelectronics	
MICROBUS by <i>D.J.D.</i>	60
Use of micros in amateur radio	
SEMICONDUCTOR UPDATE by <i>R. W. Cples</i>	66
Featuring LM1035 99000 Series 8X60	

NEWS AND COMMENT

EDITORIAL	17
NEWS & MARKET PLACE	18
Including Countdown	
INDUSTRY NOTEBOOK by <i>Nexus</i>	21
Reflections on the past year	
PATENTS REVIEW	64
New ideas from around the world	
SPACEWATCH by <i>Frank W. Hyde</i>	68
Extra-terrestrial activities chronicled	

OUR APRIL ISSUE WILL BE ON SALE FRIDAY, 12th MARCH 1982
(for details of contents see page 39)

© IPC Magazines Limited 1982. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

WATFORD ELECTRONICS

33/35, CARDIFF ROAD, WATFORD, HERTS WD1 8ED, ENGLAND
Tel. Watford (0923) 40588. Telex: 8956095 WAELC

ALL DEVICES BRAND NEW. FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O. OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS OFFICIAL ORDERS ACCEPTED (TELEPHONE ORDERS BY ACCESS NOW ACCEPTED Minimum £10.00 please). TRADE AND EXPORT INQUIRY WELCOME. P & P ADD 50p TO ALL ORDERS UNDER £10.00 EXCL. VAT. OVERSEAS ORDERS POSTAGE AT COST.

VAT Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 15% to the total cost incl. p&p. We stock many more items. It pays to visit us. We are situated behind Watford Football Ground. Nearest Underground/Br. Rail Station: Watford High Street. Open Monday to Saturday 9 a.m. - 6 p.m. Ample Free Car Parking space available.

POLYESTER CAPACITORS: (Axial Lead) 400V: 1nF, 1n5, 2n2, 3n3, 4n7, 6n8 11p; 10n, 15n, 18n, 22n 12p; 33n, 47n, 68n 16p; 100n, 150n 20p; 220n 30p; 330n 42p; 470n 52p; 680n 60p; 1µF 68p; 2µF, 4µF 85p. 160V: 10nF, 12n, 100n 11p; 150n, 220n 17p; 330n, 470n 30p; 680n 39p; 1µF 42p; 1µ5 45p; 2µF 48p; 4µF 58p. 1000V: 1nF 17p; 10nF 30p; 15n 40p; 22n 36p; 33n 42p; 47n, 100n 80p.

POLYESTER RADIAL LEAD CAPACITORS: 250V: 10n, 15n, 22n, 27n 6p; 33n, 47n, 68n, 100n 7p; 150n, 220n 10p; 330n, 470n 13p; 680n 19p; 1µ 23p; 1µ5 40p; 2µ 48p.

ELECTROLYTIC CAPACITORS (Values in µF): 500V: 10 82p; 47 78p; 63V: 0.47, 1.0, 1.5, 2.2, 3.3, 4.7, 7.9p; 6.8, 10 10p; 15, 22 12p; 33 15p; 47 12p; 100 15p; 1000 70p; 50V: 4.7, 10 12p; 68 20p; 220 24p; 470 32p; 2200 90p; 40V: 4.7, 15, 22, 33p; 330 90p; 4700 120p; 25V: 1.5, 6, 8, 10, 22 8p; 33 9p; 47 10p; 100 11p; 150 12p; 220 13p; 330 22p; 470 26p; 680 34p; 2200 50p; 3300 76p; 4700 120p; 18V: 4.7, 10 9p; 100 9p; 125 12p; 220 13p; 470 20p; 680 34p; 1000 27p; 1500 31p; 2200 36p; 3300 74p; 4700 79p.

TAG-END TYPE: 70V: 4700 245p; 64V: 3300 198p; 2200 139p; 50V 3300 154p; 2200 110p; 40V: 4700 160p; 25V: 1000 320p; 15000 345p.

TANTALUM BEAD CAPACITORS: 35V: 0.1µ, 0.22, 0.33 15p; 0.47, 0.68, 1.0, 1.5 16p; 2.2, 3.3 18p; 4.7, 6.8 22p; 10 28p; 16V: 0.22, 0.33, 16p; 0.47, 6.8, 10 18p; 15, 30p; 22p; 33p; 33, 47 40p; 100 75p; 220 88p; 10V: 15, 22 26p; 33, 47 33p; 100 55p.

SILVER MICA (pF)
2, 3, 3.4, 4.7, 6.8, 8.2, 10, 12, 15, 18, 10K 10p; 22, 33, 39, 47, 50, 56, 68, 75, 82, 85, 100, 120, 150, 180, 180 15p each
220, 250, 270, 330, 360, 390, 470, 600, 800, 800 & 820pF 21p each
1000, 1200, 1800 30p each
3300, 4700 60p each

SIEMENS multilayer miniature capacitors.
50V: 1nF, 1n5, 2n2, 3n3, 4n7, 6n8, 8n2, 10n, 12n, 15n, 22n 3p; 15n, 27n, 33n, 47n 8p; 39p, 56n, 68n 9p.
100V: 100n, 120n, 10p; 150n 11p; 220n 13p; 330n 18p; 470n 23p; 680n 30p; 1µF 30p; 2µF 50p.

MYLAR FILM CAPACITORS
100V: 1nF, 2n, 4n, 4n7, 10 7p
15nF 22, 30, 40, 47n 8p
56V: 100, 200n 5p
50V: 470nF 12p

CERAMIC Capacitors: 50V
Range 1pF to 6800pF
10nF, 15n, 22, 33, 47nF 5p
100n/30V 7p; 220n/6V 8p

POLYSTYRENE Caps:
10pF to 1nF 8p
1n5 to 12nF 10p

Sound Generator AY-3-8910 £6
Special Booklet for above £2.50

RESISTORS - Hi-stab, Miniature, 5% Carbon.
1W 1/4 199 100+
0.25W 202-4-M7 E24 2p 1p
0.5W 202-4-M7 E12 2p 1p
1W 202-10M E12 5p 3p
2% Metal Film 100-1M 8p 4p
1% Metal Film 51-1M 8p 6p

RESISTORS - Hi-stab, Miniature, 5% Carbon.
100+ price applies to Resistors of each type not mixed values.

555 CMOS	80	LF351	150	NE544	210	TL081CP	25	6545 CRTC	1450
702	75	LF355	85	NE555	16	TL082CP	45	6551 ACIA	785
709C 8 pin	15	LF359	100	NE556D	45	TL083CP	75	6592 PC	£20
710	48	LF357	110	NE560	325	TL084CP	95	6800	300
741	14	LM10	425	NE561	410	TL170	50	6803	£12
747C 14 pin	65	LM301A	26	NE564	420	UA2240	245	6804	160
748C 8 pin	36	LM309	85	NE565A	120	UA1170	170	6805	670
753 D	185	LM311	70	NE566	155	UA180	170	6808	520
758 8 pin	15	LM317	200	NE567	140	UA1003-3	335	6809	999
9400CJ	350	LM319	215	NE568	120	ULN1003	330	6810	120
AY-1-0212	675	LM324	30	NE569	120	ULN1004	90	6820	175
AY-1-1313A	660	LM335	128	NE570	150	ULN2283	100	6821	125
AY-1-1320	225	LM339	54	NE571	120	UPC755	350	6840	420
AY-1-5050	160	LM348	64	NE572	140	UPC1025H	375	6843	£14
AY-1-6720	210	SAB320	425	NE573	120	UPC1182	330	6845	975
AY-3-1270	840	SAB321	100	NE574	120	UPC1159H	290	6847	850
AY-3-8500	390	LM358	65	NE575	150	XR2200	300	6850	150
AY-3-8910	600	LM377	175	NE576	150	XR2207	375	6852	255
AY-5-1224A	235	LM379	480	NE577	150	XR2211	575	6875	500
AY-5-1230	450	LM392	320	NE578	150	XR2216	675	8080A	350
AY-5-1317A	630	LM394	325	NE579	150	XR2240	245	8085	550
AY-5-1376A	300	LM395	325	NE580	150	XR2266	750	81S595	950
AY-5-4007D50	775	LM397	415	NE581	150	ZN414	88	81LS96	90
AY-5-8100	775	LM382	125	NE582	150	ZN419C	190	81LS97	90
CA3011	140	LM384	140	NE583	150	ZN423C	138	8166	00
CA3012	175	LM385	140	NE584	150	ZN424E	130	8123	125
CA3014	157	LM387	120	NE585	150	ZN425F	80	8202	£25
CA3018	68	LM389	95	NE586	150	ZN426E-8	600	8214	425
CA3019	70	LM393	100	NE587	150	ZN428E	478	8216	70
CA3020	186	LM394C	290	NE588	150	ZN429E-8	210	8224	200
CA3023	130	LM397	290	NE589	150	ZN430E	210	8226	250
CA3028A	120	LM398	290	NE590	150	ZN431E	210	8228	320
CA3035	235	LM399	290	NE591	150	ZN432E	210	8230	320
CA3036	115	LM399	85	NE592	150	ZN433E	210	8232	320
CA3043	275	LM399	125	NE593	150	ZN434E	210	8234	320
CA3045	365	LM399	125	NE594	150	ZN435E	210	8236	320
CA3046	70	LM399	125	NE595	150	ZN436E	210	8238	320
CA3048	214	LM399	220	NE596	150	ZN437E	210	8240	320
CA3059	225	LM399	220	NE597	150	ZN438E	210	8242	320
CA3075	213	LM399	220	NE598	150	ZN439E	210	8244	320
CA3080E	85	M525AA	625	NE599	150	ZN440E	210	8246	320
CA3081	190	M533AA	1150	NE600	150	ZN441E	210	8248	320
CA3086	48	M5151L	320	NE601	150	ZN442E	210	8250	320
CA3089E	215	M5151L	230	NE602	150	ZN443E	210	8252	320
CA3090A0	375	M5376A	440	NE603	150	ZN444E	210	8254	320
CA3123	150	MC1303	88	NE604	150	ZN445E	210	8256	320
CA3130	90	MC1304P	260	NE605	150	ZN446E	210	8258	320
CA3140	48	MC110P	100	NE606	150	ZN447E	210	8260	320
CA3160	95	MC145	150	NE607	150	ZN448E	210	8262	320
CA3161E	135	MC145	150	NE608	150	ZN449E	210	8264	320
CA3162E	450	MC149A	694	NE609	150	ZN450E	210	8266	320
CA3189	220	MC149B	625	NE610	150	ZN451E	210	8268	320
CA3240	110	MC149C	350	NE611	150	ZN452E	210	8270	320
LA1336W	240	MC158E	225	NE612	150	ZN453E	210	8272	320
ICL7106	750	MC1648	290	NE613	150	ZN454E	210	8274	320
ICL7107	975	MC1709G	90	NE614	150	ZN455E	210	8276	320
ICL8038CC	300	MC3302	150	NE615	150	ZN456E	210	8278	320
ICL8211	450	MC3340P	120	NE616	150	ZN457E	210	8280	320
ICM7204	850	MC3309B	625	NE617	150	ZN458E	210	8282	320
ICM7205	1150	MC3401	65	NE618	150	ZN459E	210	8284	320
ICM7207	475	MC3403	110	NE619	150	ZN460E	210	8286	320
ICM7215	1050	MC3405	150	NE620	150	ZN461E	210	8288	320
ICM7216A	1950	MC4016	100	NE621	150	ZN462E	210	8290	320
ICM7216B	1950	MC8040	97	NE622	150	ZN463E	210	8292	320
ICM7217A	750	MC8098	625	NE623	150	ZN464E	210	8294	320
ICM7224	785	MC5303	635	NE624	150	ZN465E	210	8296	320
ICM7555	80	MM5307	1275	NE625	150	ZN466E	210	8298	320
ICM7556	00	MM5374	475	NE626	150	ZN467E	210	8300	320
LA3350	250	MM5526	820	NE627	150	ZN468E	210	8302	320
LA4031P	340	NE515	278	NE628	150	ZN469E	210	8304	320
LA4032	295	NE515	278	NE629	150	ZN470E	210	8306	320
LA4400	440	NE531	100	NE630	150	ZN471E	210	8308	320
LC1720	300	NE543	225	NE631	150	ZN472E	210	8310	320

COMPUTER IC's

1702	299	1802CP	700
201-2	110	211-2	270
2114-300n	85	2114-200n	87
2118-4	250	2147-3	425
2532-450n	450	2564	£20
2708	175	2718-5V	210
2742-450n	420	2764	£19
4027	240	4116-150	95
4116-200	75	4118-250	400
4118-250	400	4315-4K	625
4334-3	310	(CMOS 2114)	325
4864-3 64K	785	6116-3	500
6116-3	500	6502 CPU	399
6502 CPU	399	6503	600
6504-25A	550	6505	600
6505	600	6520 PIA	175
6520 PIA	175	6522 VIA	320
6522 VIA	320	6530 RIOT	1350
6530 RIOT	1350	6532 RIOT	670

TRANSISTORS

AC107	35	BC307B	16	BFX29/84	28	TP300C	58	2N1131/2	24	2N5777	45
AC125/35	35	BC327/8	15	BFX85/86	28	TP131A	45	2N1303/4	65	2N6027	32
AC127/8	30	BC337/8	15	BFY30/51	18	TP132	45	2N1305/7	60	2N6109	60
AC141/2	30	BC441	34	BFY56	32	TP23C	60	2N1613	30	2S415	60

SPEAKERS	
8Ω, 0.3W, 2"; 2.25", 2.5", 3"	80p
0.3W, 2.5" 40Ω; 64Ω or 80Ω	80p

DIODES	
AA119	15
BA100	25
8Y100	24
8Y126	12
8Y127	12
CR033	250
CA19	40
OA47	12
OA70	12
OA79	15
OA85	15
CA190	8
OA91	8
OA95	8
OA200	8
OA202	8
IN914	4
IN546	6
IN4001/2	6
IN4003	6
IN4004/5	6
IN4006/7	6
IN4148	4
IN5401	15
IN5404	16
IN5408	17
IN5408	19
IS44	9
IS921	9
6A100V	40
6A400V	50
6A800V	65

Noise Diodes	
Z5J	195

SCR's	
0.5A/100V	32
1A/200V	58
1A/400V	78
5A/300V	38
5A/400V	40
5A/600V	48
8A/300V	60
8A/400V	65
8A/600V	95
12A/100V	78
12A/200V	78
12A/400V	88
12A/600V	188
BT106	150
BT116	180
C106D	38
TIC44	24
TIC45	29
TIC47	35
2N5062	32
2N5064	38
2N4444	130

DIAC	
SR12	25

OPTO ELECTRONICS	
LEDS including Clips	
TL1209 Red 125°	13
TL1210 Green 125°	18
TL1212 Yellow	18
TL1220 2° Red	15
0.2" Yel, Grn, Amber	18
Red, Green and Yellow	
Rectangular LEDs	29
Triangular LEDs R&G	18
0.2" Flashing LED Red	55
0.2" Bi colour LEDs	55
Red/Green	65
Green/Yellow	65
0.2" Tri colour LEDs	85
Red/Green/Yellow	85
LD271 Infra Red (emit)	46
TL132 Infra Red (emit)	52
SFH205 (detector)	91
TL178 (detector)	54
TL100	90

7 Segment Displays	
TL131 5.1" C.An	115
TL1322 5.1" C.Th	115
DL704 0.3" C.H	99
DL707 0.3" C.Anod	99
DL747 0.6" C.Cathod	180
0.3" Orange C.A.	250
FND357 or 500	120
0.3" Green C.A.	140
±1.3" Red or Green	150
Bargraph 10 seg. Red	225

FERRIC CHLORIDE	
1 lb bag Anhydrous	210
195p + 50p p&p	

DALO ETCH RESIST	
Pen + Spare tip	90p

COPPER CLAD BOARDS	
Fibre Single-sided	SRBP
Glass Double-sided	9.5"x8.5"
6"x6"	90p
6"x12"	110p
6"x12"	150p

SOLDERCON PINS	
100 pins 70p	500 pins 325p

VEROBOARDS 0.1"	
VQ Board	150
'DIP' Board	330
Verob Strip	144
'S100 Board	£14

PROTO-DECs	
Veroblock	375
S-Dec	350
Eurobreadboard	520
Bimboard 1	695
Superstrip SS2	1350

VERO WIRING PEN and Spool	
Spare Wire (Spool) 75p	310p
Combs 8p ea.	

SPECIAL OFFER	
NE555	1 + 50+
2114L-3	16p 14p
2114L-2	87p 80p
2708	87p 80p
2532	175p 160p
2716	450p 375p
2732	210p 195p
4116	400p 375p
6116	75p 68p
6522	580p 550p
7805 1A/5V	350p 320p
	45p 35p

CUSTOMER: How can Watford sell full spec devices so cheaply? WATFORD: It's simple. By bulk buying (direct from manufacturers where possible), low overheads and smaller margins which give us an edge over our competitors.

ANTEX Soldering Irons	
C15W	410
CX17W	425
CCN15W	425
K25W	440
Spare bits	50
Elements	200
Iron stands	160
Heat Shunt	25

GAS & SMOKE DETECTORS	
TGS12 & B13	575
Sockets	40

ULTRASONIC TRANSDUCERS	
40KHz Transmitter & Receiver	395p/pair

DIL SOCKETS (TEXAS)	
Low profile	Wire wrap
8 pin	8p 25p
14 pin	10p 35p
16 pin	10p 42p
18 pin	16p 52p
20 pin	22p 60p
22 pin	25p 70p
24 pin	25p 70p
28 pin	28p 80p
36 pin	30p 105p
40 pin	30p 99p

DIL PLUGS (Headers)	
14 pin	44
16 pin	48
24 pin	58
40 pin	265

SPEAKING CLOCK	
Full Kit of parts now available	Only: £37.50

ZERO Insertion Force DIL Sockets	
24 way 595p; 28 way 850p; 40 way 975p	

'D' CONNECTORS mini. (Cannon type) Solder Bucket		
Plugs	Sockets	Covers plastic
9 way	95p	125p
15 way	135p	198p
15 way	170p	230p
37 way	290p	398p

PCB Pins	
25 way 200p	245p

PCB Pins (right angle)	
25 way 210p	275p

Amphenol Plugs	
24 way IEEE	575p

EDGE CONNECTORS	
Two rows	1
2x10 way	135p
2x15 way	140p
2x18 way	180p
2x22 way	190p
2x25 way	225p
2x30 way	245p
2x36 way	295p
2x40 way	315p
2x43 way	395p

WATFORD'S Ultimate Monitor IC.

A 4K Monitor Chip specially designed to produce the best from your Superboard Series I & II, Enhanced Superboard & UK101. As reviewed by Dr. A. A. Berk in Practical Electronics, June 1981. Price only £15.95 + 50p P&P.

EPSON MX Series PRINTERS

Now available from stock at very competitive prices.

- **MX80T 10" Tractor Feed, 9x9 matrix, 80 column Speed 80 CPS bi-directional. Centronics Interface, Baud rate 110-9600 (RS232) £340**
- **MX80FT Has Friction & Tractor Feed plus all the MX80T's facilities £375**
- **MX80FT2 Has high resolution Graphics option plus all the MX80T's facilities £420**
- **MX100 132 Column plus all the facilities of MX80FT2. Value for money. £550**

TRANSFORMERS (mains Prim. 220-240V)	
6.0-6V 100mA; 9.0-9V 75mA; 12.0-12V 75mA	98p
6VA type: 6V-5A 6V-5A; 9V-4A 9V-4A; 12V-3A 12V-3A; 15V-2.5A 15V-2.5A 220p	
12VA: 4.5-1.3A 4.5V-1.3A; 6V-1.2A 6V-1.2A; 12V-0.5A 12V-0.5A 275p (30p p&p)	
24VA: 6V-1.5A 6V-1.5A; 9V-1.2A 9V-1.2A; 12V-1A 12V-1A; 15-8A 15-8A; 20V-6A 20V-6A 320p (44p p&p)	
50VA: 6V-4A 6V-4A; 9V-2.5A 9V-2.5A; 12V-2A 12V-2A; 15V-1.5A 15V-1.5A; 20V-1.2A 20V-1.2A; 25V-1A 25V-1A; 30V-8A 30V-8A 395p (60p p&p)	
100VA: 12V-4A 12V-4A; 15V-3A 15V-3A; 20V-2.5A 20V-2.5A; 30V-1.5A 30V-1.5A; 40V-1.25A 40V-1.25A; 50V-1A 50V-1A 920p (80p p&p)	

JUMPER LEADS Ribbon Cable Assembly	
Single ended DIP, 24" length Cable	
14 pin 145p	16 pin 165p;
24 pin 240p;	40 pin 380p.
Double ended DIP	
6" 14 pin	16 pin 24 pin 40 pin
6" 185p	20p 300p 465p
12" 198p	215p 315p 490p
24" 210p	235p 345p 540p
36" 230p	250p 375p 595p

COMPUTER CORNER

- **VIC 20 MICROCOMPUTER.** Connects directly to a colour TV. 5K RAM expandable to 32K PET type graphics. **£165**
- **CASSETTE DECK for VIC20** including a free 6 programme Cassette. **£34**
- **EPSON MX SERIES PRINTERS:** see top right hand side of this advertisement.
- **SEIKOSHA GP80A** - Unihammer Printer, gives normal and double width characters as well as dot resolution graphics 8" Tractor feed. Parallel Interface standard. **£195**
- **SOFTY-2.** As reviewed in PE September 1981. The complete microprocessor development system for Engineers & Beginners. New powerful instruction. Accepts any 24 pin 5V single rail EPROM. Supplied fully built, tested & enclosed in a black ABS case. Price incl. encapsulated plug in power supply. **£169**
- **VIDEO MONITOR 9"** fully cased. B&W. Fully guaranteed. Excellent value for money at only **£69**
- **TEX EPROM ERASER.** Erases up to 32 ICs in 15-30 min. **£33**
- **TEX EPROM ERASER** with integral 30 min. Electronic timer **£45**
- **Spare UV lamp bulbs** **£9**
- **5V/5A PSU** Ready built and tested **£25**
- **Attractive Beige/Brown ABS CASE** for Superboard/UK101 or Home Brew **£26**
- **Extra 4K of RAM** (8 off 2114L-300N5) **£7**
- **Space Invaders** for Superboard **£6**
- **Full ASC11** coded keyboard type '756' **£39**
- **4 x 4 matrix keypad** (reed switch assembly) **£4**
- **C12 Cassettes** in Library Cases **40p**
- **8 1/2 Fan fold paper** (500 sheets) (no VAT) **£6**
- **9 1/2 Fan fold paper** (500 sheets) (no VAT) **£6**
- **Teletypewriter Roll** (no VAT) **£3.50**

(P&P on most of the above items is extra)
Call in at our shop for demonstration of any of the above items. Be satisfied before you buy.

VOLTAGE REGULATORS

1A T03 +ve	-ve
5V 7805 145p	7905 220p
12V 7812 145p	7912 220p
15V 7815 145p	7915 220p
18V 7818 150p	
1A T0220 Plastic Casing	
5V 7805 50p	7905 55p
12V 7812 50p	7912 55p
15V 7815 50p	7915 55p
18V 7818 50p	7918 55p
24V 7824 50p	
100mA T092 Plastic Casing	
5V 7805 30p	7905 60p
6V 7812 30p	
8V 7818 30p	
12V 7812 30p	7912 60p
15V 7815 30p	7915 60p
LM300H	170
LM304H	160
LM305H	140
78H05 5V/5A	550p
78HG+5 to +24V 5A	599p
78HC -2.25V	1M723 35
-24V 5A	785p
LM309K	135
LM309KP	99
LM317H	280
LM317K	350
LM323K	500
LM326N	240
LM327N	270
LM723	35
TBA625B	75

SWITCHES

SLIDE 250V	TOGGLE 2A 250V
1A DPDT	14 SPST
1A DPDT/COFF	15 DPDT
1A DP on/on/on	40 4 pole on off

PUSH BUTTON	
Latching or Momentary 6A	SP SPST or SPST on off
SPDT c/over	99 SPST on off
DPDT c/over	145 SPDT c/off

SUB-MIN TOGGLE	
SPST changeover	60
SPST on off	54
SPDT c/off	85
SPDT Biased	105
DPDT 6 pgs	75
DPDT C/OFF	88
DPDT Biased	145
3 pole c/over	205

ROCKER: 5A, 250V, SPST	
ROCKER: (white) 10A 250V	SPST 39p

ROCKER: With neon lights red when on.	
10A 250V, DPST	85p
ROCKER: (White) 10A/250V DPDT	72p

ROTARY: Make your own Multiway Switch. Shafting Assembly accommodates up to 8 wafers.	
Break before make Wafers. Silver contacts.	
1 pole/12 way; 2 pole/6 way; 3 pole/4 way; 4 pole/3 way; 6 pole/2 way	85p
Mains DPST Switch to fit Screen & Spacers	45p
Rotary: (Adjustable Stop Type)	
1 pole/2 to 12 way; 2p/2 to 6 way; 3 pole/1 to 4 way; 4 pole/2 to 3 way	90p
ROTARY: Mains 250V AC, 4 Amp	50p

DIL SWITCHES: (SPST) 4 way 70p; 6 way 85p; 8 way 90p; 10 way 145p; (SPDT) 4 way 190p.	
----------------------------------------------------------------------------------------------	--

WATFORD'S UNIVERSAL MICRO EXPANSION SYSTEM

Designed by Watford Electronics, this extremely versatile and economical Expansion System as published in E.T.I., starting from Dec., 81 issue, offers a low cost flexible expansion facility for ZX81, UK101, SUPERBOARD, ACORN ATOM, PET, TANGERINE, VIDEO GENIE, ECT.

The Motherboard (Interfaces with the Computer) has capacity to accept up to five daughter cards and can be paralleled for even more daughter cards.

All PCBs are of Computer grade finish and are supplied in Kit form.

- Just look at the expansion possibilities:**
- **MOTHERBOARD** - Accepts up to five Daughter Cards **Full Kit: £36.50**
 - **SOUND CARD** - Utilising up to three AY-3-8910 Sound chips. (one supplied with every Kit) **Full Kit: £24.95**
 - **PIO CARD** - Using two 6520 PIA chips, this Board offers Centronics parallel printer driver, digital to analogue converter and a host of other out-put facilities. **Full Kit: £19.95**
 - **PROM PROGRAMMER** - This simple but extremely useful card can blow 2716 or 2732 single rail EPROMS. **Full Kit: £19.95**
 - **PROM CARD** - P.C.B. cards for housing four 2716 or two 2732 EPROMS. **Full Kit: £9.95**
 - **RAM CARD** - 8K RAM card. Accepts 16x2114 RAMs. The Board is supplied fully populated. **Full Kit: £28.50**

(N.B. PCBs may be bought separately)

WATFORD ELECTRONICS
Tel. (0923) 40588 Telex. 8956095

EXCITING OFFERS!

DIGITAL VOLTMETER MODULE

Fully built & tested



- Positive and negative voltages with an FSD of 999mV which is easily extended.
- Requires only single supply 7 - 12V.
- High overall accuracy $\pm 0.1\% + 1$ digit.
- Large bright 0.43" (11mm) LED displays.
- Supplied with full data and applications information.

ONLY
£11.95
+VAT

Using this fully built and calibrated module as a basis now means that you can easily build a wide range of accurate equipment such as multimeters, thermometers, battery indicators, etc. etc. at a fraction of the cost of ready-made equipment. Full details are supplied with each module showing how to easily extend the voltage range and measure current, resistance and temperature. Fully guaranteed, the unit has been supplied to electricity authorities, Government departments, universities, the P.O. and many companies.

Temperature Measurement £2.15 +VAT

An easily constructed kit using an I.C. probe providing a linear output of 10mV/°C over the temperature range from -10°C to +100°C. The unit is ideal for use in conjunction with the above DVM module providing an accurate digital thermometer suitable for a wide range of applications.

Power Supply £4.95 +VAT

This fully built mains power supply provides two stabilised isolated outputs of 9V providing current levels of up to 250mA each. The unit is ideally suited for powering the DVM and the Temperature Measurement module.

ULTRASONIC ALARM MODULE

Fully built & tested

ONLY
£10.95
+VAT

Power Supply & Relay Unit £3.95 +VAT

Incorporating a stabilised 12V supply and a s.p.c.o. relay with 3A contacts, this unit is designed to operate in conjunction with the above ultrasonic unit. Fully built and tested, its compact size makes it ideal for constructing the smallest of units.



Range adjustable from 5' - 25'

A really effective fully built module which contains both ultrasonic transmitter and receiver, together with the necessary circuitry for providing the appropriate delays and false alarm suppression. Using this module with a suitable 12V power supply and relay unit such as that shown, a really effective though inexpensive intruder alarm may be constructed. The module, which is supplied with a comprehensive data sheet, is easily mounted in a wide range of enclosures. A ready drilled case, together with all the necessary hardware, is available below.

Siren Module

£2.57 +VAT

Producing a very loud and penetrating wailing sound, this module operates from 9-15 volts, capable of driving one or two 8 ohm speakers. Suitable horn speakers available at £4.30 each plus VAT.

Hardware Kit £3.95 +VAT

A suitable ready drilled case together with the various mounting pillars, nuts and bolts, and including a mains switch and 2mm sockets designed to house the ultrasonic alarm module, together with its associated power supply. Size 153mm x 120mm x 45mm.

In addition to the above a wide range of competitively priced electronic components is stocked. Please telephone your specific requirements.



RISCOMP LIMITED

Dept. PE5,
21 Duke Street,
Princes Risborough, Bucks.
Tel: Princes Risborough (084 44) 6326

- V.A.T. must be added on all items.
- Shop hours 9 - 5.30 (Weds. 9 - 1)
- ex-stock delivery on all items.
- Units on demonstration, callers welcome.
- Post and packing charge 50p per order.
- S.A.E. with all enquiries please.

MASTER ELECTRONICS NOW! The PRACTICAL way!


This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to start or further a career in electronics or as a self-employed servicing engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write personally at any time, for advice or help during your work. A Certificate is given at the end of every course.

You will do the following:

- Build a modern oscilloscope
- Recognise and handle current electronic components
- Read, draw and understand circuit diagrams
- Carry out 40 experiments on basic electronic circuits used in modern equipment
- Build and use digital electronic circuits and current solid state 'chips'
- Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-Fi and microprocessor/computer equipment.

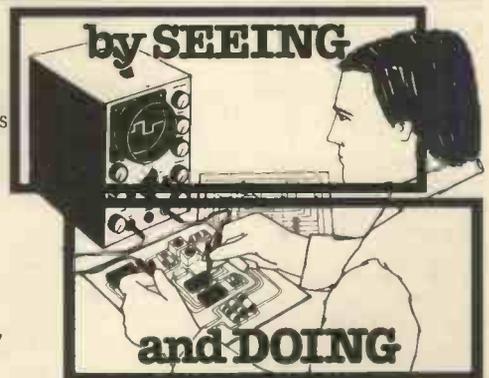

New Job? New Career? New Hobby? Get into **Electronics** Now!

FREE!
COLOUR BROCHURE



POST NOW TO:

Please send your brochure without any obligation to

NAME _____

ADDRESS _____

I am interested in:

- COURSE IN ELECTRONICS as described above
- RADIO AMATEUR LICENCE
- MICROPROCESSORS
- LOGIC COURSE

OTHER SUBJECTS _____

PE/3/82

BLOCK CAPS PLEASE

British National Radio & Electronics School Reading, Berks. RG1 7BR

KITS, COMPONENTS MICROS & PARTS

THE GARAGE DOOR AT YOUR COMMAND

At last, a kit to enable your motorised garage door to be opened without setting foot from your car, and also enable the lights in your garage and drive to be switched on or off at the touch of a button. A momentary relay output operating the door controller is switched only while a valid code is transmitted. A momentary relay switching 240V a.c. mains loads via remote opto-isolated solid state switches (1kW maximum). A hand-held transmitter for 9V PP3 battery operation constituting a range of approximately 40 feet is included. As a general purpose remote control in the home for switching lights, television and other appliances. This unit is ideal for the aged or disabled.

ALL PRICES
EXCLUDE VAT

£23.75

DISCO LIGHTING KITS

DL1000K
This value-for-money kit features a bi-directional sequence, speed of sequence and frequency of direction change, being variable by means of potentiometers and incorporates a master dimming control. Only £14.60



DL21000K
A lower cost version of the above, featuring unidirectional channel sequence with speed variable by means of a pre-set pot. Outputs switched only at mains zero crossing points to reduce radio interference to a minimum. Only £8.00

Optional opto input DLA1 60p
Allowing audio ("beat")—light response.

DVM/ULTRA SENSITIVE THERMOMETER KIT

This new design is based on the ICL7126 (a lower power version of the ICL7106 chip) and a 3½ digit liquid crystal display. This kit will form the basis of a digital multimeter (only a few additional resistors and switches are required—details supplied), or a sensitive digital thermometer (-50°C to +150°C) reading to 0.1°C. The basic kit has a sensitivity of 200mV for a full scale reading, automatic polarity indication and an ultra low power requirement—giving a 2 year typical battery life from a standard 9V PP3 when used 8 hours a day, 7 days a week. Price £15.50



DO YOU LONG TO HEAR YOUR DOORBELL RING?

Our latest kit gives you a pleasing three-note harmonically related tone sequence (not a microprocessor controlled buzz or the same old ding dong) at a touch of a button.

This kit, based on a new integrated circuit, is supplied complete with a printed circuit board, loudspeaker and drilled box and requires only 9V battery and push button common to most households.

It may also be switched by logic in such applications as car alarms, clocks, toys, P.A. systems, etc. The unit produces a 150mW output and draws less than one 1uA from a PP3 battery when the tone ceases. Supplied complete with circuit and assembly instructions. IDEAL PROJECT FOR BEGINNERS—ONLY £5.00



TRIACS

400V Plastic Case (Texas) 3A TIC206D 49p
8A TIC226D 58p
12A TIC236D 85p
16A TIC246D 96p
25A TIC263D 190p
6A with Trigger Q4006LT 85p
8A Isolated tab TXAL228B 65p
Diac 18p
Opto Isolated triac MOC3020 0.6A/400V 110p



IF YOU CAN'T (REMOTE) CONTROL YOURSELF . . .

Published remote control systems tend to be quite complex, requiring difficult-to-get components and a well-equipped lab to get them to work. If this has put you off making your own system we have just the kits for you. Using infrared, our KITS range from simple on/off controllers to coded transmitter/receivers with 16 on/off outputs or three analogue outputs for controlling, e.g., TV or Hi-Fi systems. The kits are easy to build and simple to set up—and they are extremely versatile, controlling anything from garage doors to room lighting just by adding the required output circuits, i.e. relays, triacs, etc.




If you can design your own system, we stock a wide range of remote control components at very competitive prices.

We have compiled a booklet on remote control, containing circuits, hints, data sheets and details of our remote control kits and components. So don't control yourself—SEND US 30p and a stamped addressed envelope for your copy TODAY!

THE MULTI-PURPOSE TIMER HAS ARRIVED

Now you can run your central heating, lighting, hi-fi system and lots more with just one programmable timer. At your selection it is designed to control four mains outputs independently, switching on and off at pre-set times over a 7 day cycle, e.g. to control your central heating (including different switching times for weekends), just connect it to your system programme and set it and forget it—the clock will do the rest.

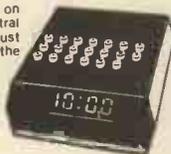

FEATURES INCLUDE—

- ★ 0.5" LED 12 hour display.
 - ★ Day of week, am/pm and output status indicators.
 - ★ 4 zero voltage switched mains outputs.
 - ★ 50/60Hz mains operation.
 - ★ Battery backup saves stored programmes and continues time keeping during power failures. (Battery not supplied).
 - ★ Display blanking during power failure to conserve battery power.
 - ★ 18 programme time sets.
 - ★ Powerful "Everyday" function enabling output to switch every day but use only one time set.
 - ★ Useful "sleep" function—turns on output for one hour.
 - ★ Direct switch control enabling output to be turned on immediately or after a specified time interval.
 - ★ 20 function keypad for programme entry.
 - ★ Programme verification at the touch of a button.
- THERE HAS NEVER BEEN A CLOCK CAPABLE OF SO MUCH AT SUCH A LOW PRICE—ONLY £45.00
(Including components, assembly and programme instructions in an attractive case).

EDUCATIONAL EXPANSION WITH SOFTY 2

Plug SOFTY 2 into the EPROM socket of your micro (Z80, 6800, 8035, etc.) prototype system and SOFTY 2 will operate as the ROM in your system but enable you to write data into any location, observe memory contents on a black & white TV and store the programme on a cassette recorder if required.


Various editing facilities are also available, permitting bytes or blocks of code to be changed, inserted, deleted, etc., enabling the programme to be developed and run on the host computer.

After "debugging" SOFTY 2 may be used to programme an EPROM (2716 or 2732). You can also use it as an Intelligent EPROM programmer to copy EPROMs from a master or to/from tape.

Housed in a black ABS case SOFTY 2 comes complete with a mains supply cable and 24-pin d.i.l. plug for connection to your prototype system and TV lead.

FULLY BUILT AND TESTED—ONLY £169.00

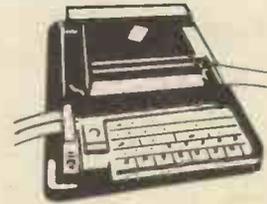For further details of SOFTY 2 and the new Z80 Assembler/Micro Controller-Menta available at just £115.00 please send stamped addressed envelope.




THE PERFECT AID FOR "LAZYITIS"

Our Lamp Dimmer Kit with INFRARED REMOTE CONTROL will enable you to switch the lights on or off, and set the brightness, at a push of a button without leaving your armchair, water-bed, etc. Not only will you save time but it has also been estimated that the savings in shoe leather and carpet wear alone would pay for this unit in approximately 1.3697 years or more!



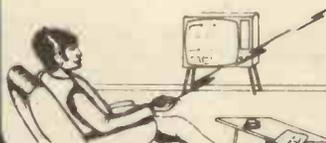
This unit has considerable practical uses, especially for the old, infirm and disabled. It works like a conventional dimmer, enabling you to switch the lights on or off, or to dim them to whatever brightness you require, by touch or using the hand-held infra red transmitter. When assembled, it fits into a plaster depth box to replace your conventional switch or dimmer with no rewiring.



TDR300K Dimmer Kit £14.30
MK6 Transmitter Kit £4.20
We also still sell our highly popular TD300K Touch Dimmer Kit at £7.00 and the LD300K rotary controlled Dimmer Kit at only £3.50
All kits contain all necessary components and full instructions. You only need a soldering iron and cutters.

24 HOUR CLOCK/APPLIANCE TIMER KIT

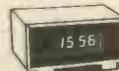Switches any appliance up to 1kW on and off at present times once per day. Kit contains: AY-5-1230 IC, 0.5" LED display, mains supply, display drivers, switches, LEDs, triacs, PCBs and full instructions.



CT1000K Basic Kit £14.90
CT1000K with white box (56/131 x 71mm) £22.50
(Ready Built).

Add 50p postage & packing + 15% VAT to total.
Overseas Customers:
Add £1.50 (Europe), £4.00 (elsewhere) for p & p.
Send S.A.E. for further STOCK DETAILS.
Goods by return subject to availability.
9am to 5pm (Mon to Fri)
OPEN 10am to 4pm (Sat)

FAST SERVICE - TOP QUALITY - LOW LOW PRICES

No circuit is complete without a call to—

PRactical ELECTRONICS

11 Boston Road
London W7 3SJ



Telephone:
01-579 9794/2842



CLEF ELECTRONIC MUSIC

ELECTRONIC PIANOS

SPECIALISTS SINCE 1972
Clef Pianos adopt the most advanced form of Touch Sensitive action which simulates piano Key inertia using a patented electronic technique.

7 1/4 OCTAVE DOMESTIC MODEL COMPONENT KIT £244 COMPLETE KIT £395.70 MANUFACTURED £675

Two Domestic Models are available including the 88-note full-size version. Four intermixable Voice Controls may be used to obtain a wide variation of Piano tone, including Harpsichord. Both Soft and Sustain Pedals are incorporated in the Design and internal Effects are provided in the form of Tremolo, Honky-Chorus, and Phase/Flanger. A power amplifier integrates into the Piano top which may be removed from the Base for easy transportation.

SIX OCTAVE DOMESTIC MODEL COMPONENT KIT £217 MANUFACTURED £595

Component Kits include Keyboard, Key-switch hardware, and all electronic components and may be purchased in four stages at no extra cost. Complete Kits further contain Cabinets, wiring harness, Pedals and in the case of Domestic Models both Power Amplifier and Speaker. The Six Octave Stage Piano has the same range of Voices and Effects and is designed for use with an External Amplifier and Speaker.

SIX OCTAVE STAGE MODEL COMPONENT KIT £217 MANUFACTURED £530

Since 1972 Clef Products have consistently produced leading designs in the field of Electronic Musical Instruments, many of which have been published in technical magazines. With musical quality of paramount importance, new techniques have been evolved and the latest musically valid technology has been incorporated into projects which have been successfully completed by constructors over a wide range of technical capability. Back-up TELEPHONE advice to our customers is available from the Designer of all Kits advertised.

STRING ENSEMBLE

(As Published in conjunction with "Practical Electronics")
A very popular Keyboard Synthesizer Kit, for Group or Home use, with a four octave compass and split Keyboard facility.

The instrument is fully polyphonic and has two rich Multi-String Voices plus Woodwind and Brass Effects for individual or Mixed use. Variable Attack and Sustain Controls give a good Orchestral Mix with the added concert hall reverberation effect produced by sustain coupled with phase modulation in the Chorus Unit. The Component Kit includes Keyboard, Key-switch hardware, and all electronic components plus tone generator linking wire and Volume Pedal. A copy of the P.E. project series can be supplied for £3.00 inc. post.

COMPONENT KIT £179.00

ROTOR-CHORUS

Comprehensive two speed organ rotor simulator plus a three phase chorus generator on a single 8" x 5" pcb. The kit includes all components for mains operation and a stereo headphone driver pcb. Easily integrated with existing organ/amplifier system.

COMPONENT KIT £89.00

KEYBOARDS

Our Square Front Keyboards are chosen for their superior feel to the discerning musician whilst giving adequate physical strength for the high impact playing present in the Piano application.

**88 NOTE (A-C) £57.00
73 NOTE (F-F) £47.00
FIVE OCTAVE £38.00
FOUR OCTAVE £28.75**

EXPERIMENTERS

A number of our Sub-Kits are of interest to Electronic Music and COMPUTER Experimenters. These include the 6502 based MICRO-CONTROLLER and Music system kit used in the BAND-BOX, plus a 49 note four pitch diode Keyswitch system. See our lists for Sub-Kit prices.

PRICES INCLUDE VAT, UK CARRIAGE & INSURANCE (CARRIAGE EXTRA ON MFD PIANOS). Please send S.A.E. for our complete lists, or use our telephone VSA/ACCESS Service. Competitive quotations can be given for EXPORT orders - in Australia please contact JAYCAR in Sydney.

CLEF PRODUCTS (ELECTRONICS) LIMITED

(Dept. P.E.) 44A Bramhall Lane South, Bramhall, Stockport, Cheshire SK7 1AH 061-439-3297

"THE ELECTRONIC BAND-BOX" CURRENTLY IN "PRACTICAL ELECTRONICS"

COMPLETE KIT £289

£399 MANFD.



PRICES INCLUDE MASTER RHYTHM

A revolution in the field of Computer Music Generation!

A MUSICIANS INSTRUMENT FOR: SOLOISTS - SINGERS - RECORDING - PRACTICE LIVE PERFORMANCE - COMPOSITION

The BAND-BOX provides an Electronic Backing Trio consisting of Drums, Bass, and a Chord Instrument (one of 16 Waveform/Envelope combinations), with the capacity to store over 3,000 User Programmable Chord Changes on more than 120 different Chords. Using advanced Microprocessor technology, Playback of 50-100 Scores can be executed in any Key and at chosen Tempo. Complete Music Pad is electronically Indexed and stored on secondary battery back-up. Facility exists for composition of Intro, Repeat Chorus, and Coda sections including Multiple Score Sequences. Sockets are provided for Volume Pedal and Footswitch plus separate and mixed Instrument Outputs. Total size 19" x 11" x 4 1/2" incorporating Master Rhythm.

THE Programmable DRUM MACHINE

(As Published in conjunction with "Practical Electronics")

EIGHT TRACK PROGRAMMING / TWENTY FOUR PATTERNS / TWELVE INSTRUMENTS SEQUENCE OPERATION. COMPLETE KIT £79.00 MANFD. £119.00



The Clef Master Rhythm is capable of storing 24 selectable rhythmic drum patterns, invented, modified, and entered by the Operator on to Eight Instrumentation tracks. A three position Instrumentation control expands the number of instruments available to twelve, grouped into sounds typical of playing with Drumsicks, Brushes, or Latin American Bongos and Claves. Sequence operation allows two rhythm sections to be coupled with the second (B) section appearing at four, eight or sixteen Bar repetition. All drums can be adjusted for level and resonance on internal controls to suit individual taste, thus producing good musical sounds in a battery driven unit 8 1/2" x 5" x 2 1/2".

PE CAR COMPUTER



This unit was described by Practical Motorist as: "One of the neatest, most comprehensive and most useful of these car computers that we have yet come across..."

The PE Car Computer was designed to exceed the specification of all others, both for number of functions and accuracy. As well as the usual functions, it can perform eleven "remaining" type calculations, has a unique "start-stop" mode (used for acceleration timing and the like) and has a combination lock for driving an alarm or ignition cut-out.

The unit is housed in a custom designed box with high quality printed panels having an overall size of 165 x 50 x 80mm deep, and can be fitted above or below the dashboard. The display is liquid crystal for clarity in all lighting conditions.

The kit includes all sensors, wiring, etc and is suitable for all cars except those fitted with diesel or fuel injection engines.

Kit price: £78.50 Assembled Price: £88.50 + £1 p&p includes VAT.

Send S.A.E. for list of separately available parts.

Please allow 14 days for delivery.



PIMAC SYSTEMS LTD
20 Bloomfield Road, Moseley,
Birmingham B13 9BY.

Tel: 021-449 0384

"SEE SCAN" (PRINTOID LTD)

**FREEPOST,
20/21 ALFRIC SQUARE,
PETERBOROUGH PE2 0BR**

The designers and manufacturers of the PE Camera Project offer technical club membership/certification to project enthusiasts.

Camera technical support and circuit testing/alignment service available. Various kits and projects always on hand (simple/intermediate/advanced).

Write for full parts list/club application forms (camera/electronics/security products) or ring:

**Project "C" Engineer
on 0733 239111 (4 lines)**


Access/Barclaycard accepted.

MICROCOMPUTER COMPONENTS AND SYSTEMS

LOWEST PRICES FASTEST DELIVERY

NEC 12" MONITOR

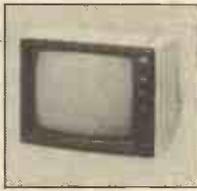- ★ GREEN DISPLAY
- ★ BUILT IN AMPLIFIER AND SPEAKER
- ★ £149.95 each excluding carriage (£10.00) and V.A.T. (15%)
- ★ EX-STOCK*



The NEC JB1201M is a 12" Video Monitor optimised for use as a computer video display terminal (unlike most CCTV monitors available). The green phosphor CRT display greatly reduces eyestrain. The built in audio amplifier and speaker make it specially suitable for personal computers.

EPROM PROGRAMMERS AND ERASER


EP4000 EMULATING PROGRAMMER

- ★ COPY/PROGRAMME/EMULATE 2704/2708 2716/2508/2516/2532/2732 EPROMS
- ★ 4K x 8 STATIC RAM
- ★ VIDEO O/P AND 8 DIGIT LED DISPLAY
- ★ POWERFUL EDITING FACILITIES
- ★ COMPREHENSIVE I/O AS STD (RS232, TTL, 20mA PARALLEL, DMA)
- ★ £545.00 excluding carriage (£10.00) and V.A.T. (15%)
- ★ EX-STOCK*



P4000 PRODUCTION PROGRAMMER

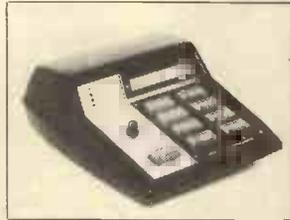- ★ PROGRAMME UP TO 8 EPROMS SIMULTANEOUSLY
- ★ COVERS SAME EPROMS AS EP4000
- ★ INDEPENDANT BLANK CHECK/VERIFY PROGRAM MODES
- ★ SIMPLE TO USE
- ★ £545.00 excluding carriage (£10.00) and V.A.T. (15%)
- ★ EX-STOCK*



UV141 EPROM ERASER

- ★ 14 EPROM CAPACITY
- ★ SAFETY INTERLOCKED
- ★ ELECTRONIC TIMER
- ★ £78.00 excluding Carriage (£5.00) and V.A.T. (15%)
- ★ EX-STOCK*



KEYBOARD AND ENCLOSURE

CASE Attractively styled personal computer enclosure constructed of structured foam top and steel base (similar to the top selling Apple). Finished in charcoal and black.
£49.95 excluding carriage (£10.00) and V.A.T. (15%)

KEYBOARD High quality electromechanical ASCII Encoded keyboard which can be fitted in above case or used separately. Full upper and lower case provided.
£49.95 excluding carriage (£2.00) and V.A.T. (15%).



TRANSFORMER Mains transformer suitable for +5V at 2.5A and ±12V at 1A. Mounts on special lugs inside enclosure.
£10.95 excluding carriage (£1.00) & V.A.T. (15%)

HEATSINK Heatsink for T03 Regulators which mounts inside rear of enclosure.
£2.50 excluding V.A.T. (15%)

SPECIAL PRICE FOR CASE, KEYBOARD, TRANSFORMER & HEATSINK IF PURCHASED TOGETHER:
£99.95 excluding carriage (£15.00) & V.A.T. (15%)

Device	Price	Device	Price	Device	Price	Device	Price	Device	Price
MEMORIES		LM555CN	0.16	CMOS 4000 'B' SERIES	4543	0.99	74LS190	0.49	
2114L-200ns	1+0.93	LM556CN	0.49	4000	0.11	4553	2.90	74LS191	0.49
2114L-300ns	25+0.89	LM725CN	3.20	4001	0.11	4555	0.39	74LS192	0.49
(FOR ACORN ATOM)	1.55	LM741CN	0.14	4001	0.11	4556	0.44	74LS193	0.46
2708 450ns	1+1.75	LM747CN	0.70	4002	0.13	4585	0.62	74LS194	0.39
		LM748CN	0.34	4006	0.60			74LS195	0.39
2716 450ns	25+1.68			4007	0.15	74LS SERIES		74LS196	0.59
(single +5V)	1+2.49	REGULATORS		4008	0.55	74LS00	0.10	74LS197	0.65
2716 350ns	25+2.25	7805	0.39	4009	0.28	74LS01	0.11	74LS221	0.54
2532 450ns	6.95	7812	0.39	4010	0.35	74LS02	0.12	74LS240	0.89
	1+4.50	7815	0.39	4011	0.12	74LS03	0.12	74LS241	0.89
	25+4.25	78L05	0.29	4012	0.15	74LS04	0.12	74LS242	0.79
2732 450ns	1+3.99	78L12	0.29	4013	0.29	74LS05	0.13	74LS243	0.79
	25+3.80	78L15	0.29	4014	0.58	74LS08	0.12	74LS244	0.65
2732 350ns	7.50	7905	0.55	4015	0.58	74LS09	0.12	74LS245	0.89
4116 200ns	1+0.74	7912	0.55	4016	0.25	74LS10	0.12	74LS247	0.63
	25+0.70	7915	0.55	4017	0.45	74LS11	0.12	74LS248	0.63
	100+0.67			4018	0.58	74LS12	0.12	74LS249	0.63
4116 150ns	1+0.93	79L05	0.59	4019	0.29	74LS13	0.22	74LS251	0.40
	25+0.89	79L12	0.59	4020	0.58	74LS14	0.39	74LS253	0.39
4118 200ns	1+3.90	79L15	0.59	4021	0.60	74LS15	0.12	74LS257	0.44
	25+3.45	LM309K	1.30	4022	0.62	74LS20	0.12	74LS258	0.39
4118 150ns	6.00	LM317K	3.20	4023	0.17	74LS21	0.12	74LS259	0.79
5516 200ns	12.50	LM323K	4.95	4024	0.35	74LS22	0.12	74LS261	1.95
6116 200ns	7.95	LM338K	4.75	4025	0.16	74LS26	0.15	74LS266	0.23
6116LP 200ns	9.50	Z80 FAMILY		4026	0.99	74LS27	0.12	74LS273	0.75
6116LP 150ns	9.95	Z80 CPU	3.49	4027	0.30	74LS28	0.15	74LS279	0.39
		Z80A CPU	3.99	4028	0.55	74LS30	0.12	74LS283	0.44
		Z80 CTC	2.99	4031	1.65	74LS32	0.12	74LS290	0.54
CRT CONTROLLERS		Z80A CTC	3.49	4033	1.60	74LS33	0.16	74LS293	0.63
EF6845P	9.50	Z80 DART	10.00	4034	1.55	74LS37	0.15	74LS298	0.34
EF9364P	5.94	Z80 DART 10.00	4035	0.72	4038	0.12	74LS366	0.36	
EF9365P	62.90	Z80 DART 12.00	4040	0.54	74LS40	0.12	74LS367	0.34	
EF9366P	62.90	Z80 DMA	9.95	4041	0.69	74LS42	0.34	74LS368	0.49
EF9365/6 DATA AND APPLICATIONS	2.00	Z80A DMA	11.95	4042	0.54	74LS47	0.39	74LS373	0.74
		Z80 PIO	3.49	4043	0.59	74LS48	0.60	74LS374	0.74
		Z80A PIO	3.75	4044	0.64	74LS49	0.59	74LS375	0.47
BUFFERS		Z80 SIO-0	10.99	4045	1.65	74LS51	0.14	74LS377	0.89
81LS95	0.90	Z80A SIO-0	11.99	4046	0.68	74LS54	0.15	74LS378	0.69
81LS96	0.90	Z80 SIO-1	10.99	4047	0.68	74LS55	0.15	74LS379	0.64
81LS97	0.90	Z80A SIO-1	11.99	4048	0.54	74LS73	0.19	74LS386	0.28
81LS98	0.90	Z80 SIO-2	10.99	4049	0.26	74LS74	0.16	74LS390	0.54
8128A	1.20							74LS393	0.59
8128B	1.40								
8195	1.35								
8197A	1.35								
8198	1.45								

2114
Low Power
200ns
0.84

OFFER VALID 1/2/82 - 31/3/82

Device	Price
DATA CONVERTERS	
ZN425E-8	3.45
ZN426E-8	3.00
ZN427E-8	5.99
ZN428E-8	4.75
ZN429E-8	2.10
ZN432CJ-10	28.09
ZN433CJ-10	2.59
ZN440	56.63
ZN432E-10	14.75
ZN447	9.14
ZN448	6.85
ZN449	3.20

Device	Price
NEW FLOPPY DISC CONTROLLERS	
FD1771	17.12
FD1791	32.61
FD1793	32.61
FD1795	35.33
WD1391	45.50
WD1393	45.50
WD1395	45.50
WD1397	45.50
WD2143-01	5.45
WD1691	10.87

Device	Price
MISCELLANEOUS SUPPORT CHIPS	
AY-3-1015	3.25
AY-3-1270	7.95
AY-3-8910	6.95
AY-5-1013	3.45
AY-5-3600	7.95
AY-5-2376	6.95
DP8304	4.50
MC1488	0.59
MC1489	0.59
MC3446	2.95
MC3448A	4.25
MC3480	7.95
MC3487	2.95
MC14411	6.94
MC14412	7.99
RO-3-2513L	7.25
RO-3-2513U	5.99
ULN2803A(L203)	0.84

Device	Price
OVN CHIPS	
ZN450E	7.61
ZN450E OVM KIT	25.00

Device	Price
NEW LINEARS	
LM301AN	0.25
LM308N	0.89
LM311N	0.89
LM319N	2.20
LM324N	0.30
LM348N	0.59

Z80A SIO-2	11.99	4050	0.26	74LS75	0.24
MK 3886	11.00	4051	0.59	74LS76	0.20
MK 3886-4	14.47	4052	0.68	74LS78	0.19
		4053	0.59	74LS83	0.44
		4054	1.20	74LS85	0.65
8080 FAMILY		4055	1.20	74LS86	0.15
8800	2.99	4056	0.79	74LS90	0.30
8802	3.99	4060	0.95	74LS91	0.75
8803C	11.80	4063	0.34	74LS92	0.34
8809	9.99	4066	0.17	74LS93	0.34
8810	1.25	4068	0.17	74LS95	0.43
8821	1.25	4069	0.17	74LS96	0.43
8840	4.20	4070	0.17	74LS109	0.21
8850	1.50	4071	0.17	74LS112	0.21
8862	6.91	4072	0.17	74LS113	0.23
8871ATT	18.70	4073	0.19	74LS114	0.19
8880	1.07	4075	0.17	74LS122	0.39
8887	0.80	4076	0.62	74LS123	0.39
88488	9.11	4077	0.22	74LS124	0.99
8675	4.18	4078	0.24	74LS125	0.25
8643	13.99	4081	0.14	74LS126	0.25
86800	4.70	4082	0.19	74LS132	0.45
86802	19.11	4085	0.63	74LS136	0.28
86821	2.29	4086	0.69	74LS138	0.34
86810	2.00	4093	0.39	74LS139	0.35
86840	4.70	4092	0.60	74LS145	0.47
86850	2.15	4507	0.39	74LS148	0.80
86000C4	110.00	4508	1.90	74LS151	0.39
		4510	0.80	74LS153	0.29
		4511	0.49	74LS155	0.39
6500 FAMILY		4512	0.60	74LS156	0.38
6502	4.25	4514	1.49	74LS157	0.31
6520	2.99	4514	1.49	74LS158	0.31
6522	4.75	4515	1.49	74LS160	0.39
6532	6.95	4516	0.69	74LS162	0.39
		4518	0.40	74LS161	0.39
		4519	0.28	74LS162	0.39
8080 FAMILY		4520	0.69	74LS163	0.39
8085A	5.50	4521	1.49	74LS164	0.47
8212	1.70	4522	1.20	74LS165	0.99
8216	0.99	4522	0.70	74LS166	0.84
8224	1.95	4526	0.89	74LS173	0.70
8228	3.95	4527	0.89	74LS174	0.47
8251	3.60	4528	0.70	74LS174	0.47
8253	7.95	4532	0.85	74LS175	0.49
8255	3.60	4541	0.99	74LS181	1.28

DIL SOCKETS	LOW PROFILE - TIN
8 pin	0.07
14 pin	0.09
16 pin	0.09
18 pin	0.13
20 pin	0.14
22 pin	0.17

Beginners' luck

30% OFF
10 selected kits
for first-time
builders




Shortwave
Listener's
Receiver

With Heathkit, you're all set for a great deal. And not just big savings.

Whichever kit you choose, you'll find it easy to build. Simple, but detailed instructions take you through every stage. Everything is included. Even the solder you need

Digital Clock

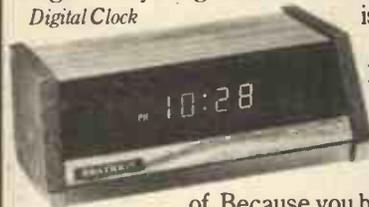

is there. Follow the steps and you'll end up with a hand-crafted, well-designed piece of equipment. One you'll be proud of. Because you built it yourself.

There are 10 great kits to start you off. An interesting choice of a digital clock to a metal locator, including a short wave listener's receiver, windspeed and direction indicator, digital readout electronic scale and five more useful kits.

All at 30% off to first-timers. Send for your catalogue right now for a start.

Follow the steps and you'll end up with a hand-crafted, well-designed piece of equipment. One you'll be proud of. Because you built it yourself.



Metal
Locator



Windspeed and Direction
Indicator

To Heath Electronics
(UK) Limited, Dept (PE3),
Bristol Road, Gloucester GL2 6EE.

PE3

To start me off, please send me a copy of the Heathkit catalogue. I enclose 28p in stamps.

Name _____

Address _____



HEATH **You build on our experience**
HEATHKIT

BI-PAK

CB users. Home base POWER SUPPLY 3A

Rugged Powerful British Made

FEATURES ★ Safe 3 Amp operation ★ 13.8V Fully regulated ★ Electronic short circuit & overload protected ★ Latest technology I.C. design ★ Attractive compact case ★ Competitively priced

SPECIFICATIONS ★ Input voltage — 240 V.a.c. 50Hz ★ Output voltage — 13.8V d.c. ± 1% Maximum with mains input variation ± 10% load 0-2.5A ★ Output current — 0-3Amp ★ Ripple — less than 2mV up to full load ★ Dimensions — 175ig x 100w x 75h (mm)

OUR PRICE **only £15.00** ORDER NO. 3GA

CB Rigs and Accessories in stock. Send S.A.E. for full listings.

8 Bit MICROPROCESSOR

National INS8080AN 40 Pin DIL N. Channel Silicon GATE MOS TECHNOLOGY As used in Nationals 18080 Micro Computer Family

Instruction Cycle Time 2 us
Supplied with functional Block Diagram

BRAND NEW —

NOT seconds or reclaims

100% perfect ORDER NO. SX8080

Normal Sell price £4.50 each

Our BI-PAK Special Price

only £2.00

SO HURRY — LIMITED STOCKS



40 Pin IC Socket to fit SX8080 Offer price
ORDER NO. 1609 **30p**

TECASBOTY

The Electronic Components and Semiconductor Bargain of the Year. A host of Electronic components including potentiometers — rotary and slider, presets — horizontal and vertical. Resistors of mixed values 220ohms to 2M Ω — 1/8 to 2 Watt. A comprehensive range of capacitors including electrolytic and polyester types plus disc ceramics etcetera. Audio plugs and sockets of various types plus switches, fuses, heatsinks, wire, nuts/bolts, gromets, cable clips and lyes, knobs and P.C. Board. Then add to that 100 Semiconductor devices to include transistors, diodes, SCR's opto's, all of which are current everyday usable devices. In all a Fantastic Parcel. No rubbish all identifiable and valued in current catalogues at well over £25.00. Our Fight Against Inflation

— Beat the Budget

— Down with Depression

Price
JUST £6.50.

ORDER NO. SX 85

Fantastic Audio Bargains

15 watts per channel stereo amplifier kit

Consisting of — ORDER NO. STA15

- 2 x AL60 amplifiers
 - 1 x PA100 pre-amplifier
 - 1 x SPM80 power supply
 - 1 x 2034 transformer
 - 2 x coupling capacitors for 8 ohms 470mfd
 - 50v and necessary wiring diagrams
- now only

Save over £10 on this kit **£26.00**

5 watt (RMS) Audio Amp

High Quality audio amplifier Module. Ideal for use in record players, tape recorders, stereo amps and cassette players, etc. Full data and back-up diagrams with each module.

Specification:
● Power Output 5 watts RMS ● Load Impedance 8-16 ohms ● Frequency response 50Hz to 25 KHz — 3db ● Sensitivity 70 mv for full output ● Input Impedance 50k ohms ● Size 85 x 64 x 30mm ● Total Harmonic distortion less than 5%

BI-PAK'S give away price

£2.25

You could not Build one for this price.


COMPLETE AUDIO CHASSIS

STEREO 30 Complete 7 watt per channel Stereo amp board — includes amps, pre-amp, power supply, front panel, knobs and Transformer

Almost 1/2 PRICE

£12.50

ORDER NO. ST30

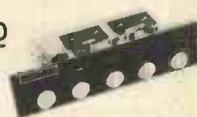

MONO PRE-AMPLIFIERS

MM100 suitable for disco mixer, MM100G suitable for guitar pre-amp mixer.

The MM100 and MM100G mono pre amplifiers are compatible with the AL60, AL80, AL120 and AL250 power amplifiers and their associated power supplies.

MM100 Supply voltage 40-65v inputs. Tape Mag P.U. Microphone Max output 500mV **£12.45** MM100G Supply voltage 40-65v inputs: 2 Guitars, Microphones Max output 500mV

£12.45
each **£10**

Silicon NPN'L' Type Transistors

T0-92 Plastic centre collector
Like BC182L — 183L — 184L
VC80 45 VCE0 30 IC200mA Hfe 100-400

ALL perfect devices — uncoded ORDER AS SX183L
50 off 100 off 500 off 1000 off
£1.50 £2.50 £10.00 £17.00

PNP SILICON TRANSISTORS:

Similar ZTX500 — ZTX214 — E-Line
VCE0 40 VCB0 35 Ic 300mA Hfe 50-400

Brand New — Uncoded — Perfect Devices
50 off 100 off 500 off 1000 off
£2.00 £3.50 £15.00 £25.00
Order as ZTXPNP

Send your orders to Dept PE3
BI-PAK, 3 BALDOCK ST.,
WARE, HERTS.



Use your credit card. Ring us on Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail.
Remember you must add VAT at 15% to your order Total. Postage add 50p per Total order.

BI-PAK BARGAINS



5T21 SCREWDRIVER SET
6 precision screwdrivers in hinged plastic case. Sizes - 0.8, 1.4, 2.2, 2.9 and 3.8mm. **£1.75**

5T31 NUT DRIVER SET
5 precision nut drivers in hinged plastic case. With turning rod. **£1.75**

Sizes: - 3, 3.5, 4, 4.5 and 5mm.


5T41 TOOL SET
5 precision instruments in hinged plastic case. Crosspoint (Philips) screwdrivers: - H 0 and H 1 Hex key wrenches. - 1.5, 2 and 2.5mm. **£1.75**

5T51 WRENCH SET
5 precision wrenches in hinged plastic case. Sizes: - 4, 4.5, 5, 5.5 and 6mm. **£1.75**


BUY ALL FOUR SETS: 5T21, 5T31 and get HEX KEY SET FREE
HEX KEY SET ON RING
Sizes: 1.5, 2, 2.5, 3, 4, 5, 5.5 and 6mm.
Made of hardened steel.
HX/1. **£1.25**



BI-PAK PCB ETCHANT AND DRILL KIT
Complete PCB Kit comprises
1 Expo Mini Drill 10,000RPM 12v DC incl 3 collets & 1 x 1mm Twist bit
1 Sheet PCB Transfers. 210mm x 150mm.
1 Etch Resist Pen.
1 1/2 lb pack FERRIC CHLORIDE crystals.
3 sheets copper clad board
2 sheets Fibreglass copper clad board.
Full instructions for making your own PCB boards.
Retail Value over **£15.00**
OUR BI-PAK SPECIAL KIT PRICE **£9.75**
ORDER NO. SX81

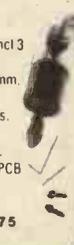

BI-PAK SOLDER-DESOLDER KIT
Kit comprises ORDER NO. SX80
1 High Quality 40 watt General Purpose Lightweight Soldering Iron 240v mains incl 3/16" (4.7mm) bit.
1 Quality Desoldering pump. High Suction with automatic ejection. Knurled, anti-corrosive casing and teflon nozzle.
1.5 metres of De-soldering braid on plastic dispenser
2 yds (1.83m) Resin Cored Solder on Card.
1 Heat Shunt tool tweezer Type.
Total Retail Value over **£12.00**
OUR SPECIAL KIT PRICE **£8.95**

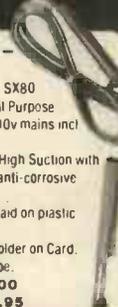


BRAND NEW LCD DISPLAY MULTITESTER.
RE 188m
LCD 10 MEGOHM INPUT IMPEDANCE
*3 1/2 digit *16 ranges plus hFE test facility for PNP and NPN transistors *Auto zero auto polarity *Single-handed, pushbutton operation *Over range indication *12.5mm (1/2-inch) large LCD readout *Diode check *Fused circuit protection *Test leads, battery and instructions included
Max indication 1999 or - 1999
Polarity indication Negative only
Positive readings appear without + sign
Input impedance 10 Megohms
Zero adjust Automatic
Sampling time 250 milliseconds
Temperature range -5°C to 50°C
Power Supply 1 x PP3 or equivalent 9V battery
Consumption 20mW
Size 155 x 88 x 31mm

RANGES
DC Voltage 0-200mV
0-2-20-200-1000V Acc 0.8%
AC Voltage 0-200-1000V
Acc 1.2% DC Current 0-200uA
0-2-20-200mA 0-10 A. Acc 1.2%
Resistance 0-2-20-200K ohms
0-2 Megohms Acc: 1%
BI-PAK VERY LOWEST POSSIBLE PRICE **£35.00** each



MINI VICE
This small cast iron quality made vice will clamp on to any bench or table having a max thickness of 1 1/2". The 2 1/2" jaws open to max of 1 1/2". Approx size 80 x 120 x 66mm.
Bi-Pak's Mini Vice at a Mini Price only
£2.
ORDER NO. SX82

The Third and Fourth Hand...
.... you always need but have never got "until now".
This helpful unit with Rod mounted horizontally on Heavy Base. Crocodile clips attached to rod ends. Six ball & socket joints give infinite variation and positions through 360° also available attached to Rod a 2 1/2" diam magnifier giving 2.5 x magnification. Helping hand unit available with or without magnifier. Our Price with magnifier as illustrated ORDER NO. T402 **£5.50**
Without magnifier ORDER NO. T400 **£4.75**

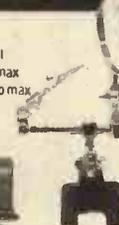EXPERIMENTER BOXES - ALUMINIUM - PLASTIC
ALUMINIUM BOXES
Made with Bright Aluminium folded construction with deep lid and screws

SIZE	L	W	H	Order No.	Price
	5 1/2	2 1/4	1 1/2	159	83p
	4	2 1/4	1 1/2	161	83p
	4	2 1/2	2	163	83p
	3	2	1	164	57p
	8	6	3	166	£1.68
	6	4	2	167	£1.12


All measurements for boxes are shown in inches. L = Length. W = Width. H = Height



Plastic Boxes
Coloured Black. Close fitting. Flanged Lid, fixing screws into brass bushes.

SIZE	L	W	H	Order No.	Price
	4	2	1	141	£1.10
	4	2 1/2	1 1/2	143	£1.30
	6	3 1/2	2	144	£1.50

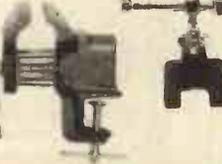Plastic as above but with aluminium top panel
4 2 1/4 1 1/2 **£1.40**
Plastic sloping front
5 1/2 4 1/4 2 1/4 slope to 1 1/2 **£2.14**



MW398 NI-CAD CHARGER
Universal Ni-Cad battery charger. All plastic case with lift up lid. Charge/Test switch. LED indicators at each of the five charging points.

Charges -	Power -
PP3 (9V)	220-240V AC
U12 (1.5V penlite)	Dim's -
U11 (1.5V "C")	210 x 100 x 50mm
U2 (1.5V "D")	£6.95

POWER SUPPLY OUR PRICE £3.25
Power supply fits directly into 13 amp socket. Fused for safety. Polarity reversing socket. Voltage switch. Lead with multi plug
Input: - 240V AC 50HZ Output: - 3, 4.5, 6, 7.5, 9 & 12V DC Rating: - 300 ma MW88



"IRRESISTABLE RESISTOR BARGAINS"

Pak No.	Qty	Description	Price
SX10	400	Mixed "All Type" Resistors	£1
SX11	400	Pre formed 1/2 watt Carbon Resistors	£1
SX12	200	1/2 watt Carbon Resistors	£1
SX13	200	1/2 watt Carbon Resistors	£1
SX14	150	1/2 watt Resistors 22 ohm	£1
SX15	100	Zn2 Mixed Land 2 watt Resistors 22 ohm 2m2 Mixed	£1

Paks SX12-15 contain a range of Carbon Film Resistors of assorted values from 22 ohms to 2.2 meg. Save cover your projects
Quantities approximate. count by weight.

"CAPABLE CAPACITOR PAKS"

Pak No.	Qty	Description	Price
SX16	250	Capacitors Mixed Types	£1
SX17	200	Ceramic Capacitors Mixture	£1
SX18	100	Mixed	£1
SX19	100	Mixed Ceramics 1pf-5 pf	£1
SX20	100	Mixed Ceramics 68pf-0.01mf	£1
SX21	60	Assorted Polyester/Polystyrene Capacitors	£1
SX22	100	Mixed C280 type capacitors metal foil	£1
SX23	50	Electrolytics, all sorts	£1
SX24	20	Quality Electrolytics 50-1000mf Tantalum Beads mixed	£1

Quantities approximate. count by weight.

AUDIO PLUGS, SOCKETS AND ACCESSORIES

25 pieces of Audio Plugs, Sockets and Connectors to include DIN 180 "240", Inline 3-6 Pin at well over £3 normal Order No. SX25 Our Price £1.50 per pak Guaranteed to save you money

SX26	3 Pcs of 6 pin 240 DIN Plugs and Chassis Sockets	£1
SX38	100 Silicon NPN Transistors - all perfect Coded mixed types with data and eqvt sheet. No rejects. Real value	50p
SX39	100 Silicon PNP Transistors - all perfect Coded mixed types with data and eqvt sheet. No rejects. Fantastic value	£2.50

TRIACS - PLASTIC

4 AMP - 400v - T0202 - TAG 136G		
1 OFF	10 OFF	100 OFF
40p	£3.75	£17.50
8 AMP 400v - T0220 - TAG 425		£30.00
60p	£5.75	£27.50
		£50.00

MOTOROLA PIEZO ELECTRIC TWEETER

Maximum Ratings:
25 volts rms which is equal to 200 watts across 4 ohms
100 watts across 8 ohms
50 watts across 16 ohms
BI-PAK SPECIAL OFFER PRICE **£4.85**
ORDER NO. 1907

DOMTWEETER
Dome tweeter for systems up to 50w.
Impedance: 8 ohms
Frequency Response: 2000-20,000Hz
Dims 98mm diam. x 31mm deep
Our Price **£2.85** OMT200



BI-PAK'S COMPLETELY NEW CATALOGUE

Completely redesigned. Full of the type of components you require plus some very interesting ones you will soon be using and of course, the largest range of semiconductor for the Amateur and Professional you could hope to find

There are no wasted pages of useless information so often included in Catalogues published nowadays. Just solid facts i.e. price, description and individual features of what we have available. But remember, Bi-Pak's policy has always been to sell quality components at competitive prices and THAT WE STILL DO.

BI-PAK'S COMPLETELY NEW CATALOGUE is now available to you. You will be amazed how much you can save when you shop for Electronic Components with a Bi-Pak Catalogue. Have one by you all the time-it pays to buy BI-PAK

To receive your copy send **75p** plus 25p p&p



Everyday Electronics

Teach in '81 Kit 1 £15.65 (Kits 1 & 2 combined price £23.00)

IC SOCKETS
The lowest price ever.

The more you buy the cheaper they come!

Pin	10 off	50 off	100 off
8	75p	£3.00	£5
14	80p	£3.25	£5.50
16	80p	£3.25	£5.50

VOLTAGE REGULATORS T0220

	Positive +	Negative -	(please state voltage required)
	7805 - 50p	7905 - 55p	
	7812 - 50p	7912 - 55p	
	7815 - 50p	7915 - 55p	
	7824 - 50p	7924 - 55p	

Other types: LM340K - 6 volt - 18 volt - 24 volt
T03 - 40p, UA723 - 14 pin OIL - 40p

Guarantee
We guarantee satisfaction or your money back. This has been BI-PAK'S GUARANTEE and it still is. All these sale items are in stock in quantities and we will dispatch in the same day as your order is received.

BI-PAK Send your orders to Dept PE3, BI-PAK PO BOX 6 WARE HERTS SHOP AT 3 BALDOCK ST WARE HERTS
TERMS CASH WITH ORDER SAME DAY DESPATCH ACCESS
BARCLAYCARD ALSO ACCEPTED TEL (0920) 3182 GYRO 388 7006
ADD 15% VAT AND 50p PER ORDER POSTAGE AND PACKING.

Use your credit card. Ring us on Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail.
Remember you must add VAT at 15% to your order
Total Postage add 50p per Total order.



CAMBRIDGE LEARNING

SELF-INSTRUCTION COURSES

A PRACTICAL DIGITAL ELECTRONIC KIT FOR ★ LESS THAN £20 ★



SUITABLE FOR BEGINNERS

Learn the wonders of digital electronics and see how quickly you are designing your own circuits. The kit contains: seven LS TTL integrated circuits, breadboard, LEDs, and all the

DIL switches, resistors, capacitors, and other components to build interesting digital circuits; plus a very clear and thoroughly tested instruction manual (also available separately). All this comes in a pocket size plastic wallet for only £19-90p inc VAT and p&p. This course is for true beginners:

- needs no soldering iron.
- asks plenty of questions, but never leaves you stuck and helpless.
- teaches you about fault-finding, improvisation, and subsystem checking.
- the only extra you need is a 4½V battery (Ever Ready 1289, or similar), or a stabilised 5V power supply.

Using the same breadboard you may construct literally millions of different circuits.

This course teaches boolean logic, gating, R-S and J-K flipflops, shift registers, ripple counters, and half-adders. Look out for our supplementary kits which will demonstrate advanced arithmetic circuits, opto-electronics, 7-segment displays etc.

Other self-instruction courses from Cambridge Learning Ltd include:

COMPUTER PROGRAMMING IN BASIC	£10.50
DIGITAL COMPUTER LOGIC AND ELECTRONICS	£ 8.50
DESIGN OF DIGITAL SYSTEMS	£14.00

Please send for full details (see coupon below).

GUARANTEE No risk to you. If you are not completely satisfied, your money will be refunded upon return of the item in good condition within 28 days of receipt.

CAMBRIDGE LEARNING LIMITED, UNIT 23, RIVERMILL SITE, FREEPOST, ST IVES, CAMBS, PE17 4BR, ENGLAND.
TELEPHONE: ST IVES (0480) 67446. VAT No. 313026022

All prices include worldwide postage (airmail is extra - please ask for prepayment invoice). Giro A/c No 2789159.

Please allow 28 days for delivery in UK



Please send me:

.....SUPERKIT(S) @ £19.90

.....Free details of your other self-instruction courses.

I enclose a *cheque/PO payable to Cambridge Learning Ltd for £..... (*delete where applicable)

Please charge my:

*Access / American Express / Barclaycard / Diners Club
Eurocard / Visa / Mastercharge / Trustcard

Expiry Date..... Credit Card No

Signature.....

Telephone orders from card holders accepted on 0480 67446
Overseas customers (including Eire) should send a bank draft in sterling drawn on a London bank, or quote credit card number.

Name.....


Address.....

Cambridge Learning Limited, UNIT 23, Rivermill Site, FREEPOST, St Ives, Huntingdon, Cambs, PE17 4BR, England. (Registered in England No. 1328762).

COMPUTER USER AIDS

APPROVED VIDEO GENIE DEALERS

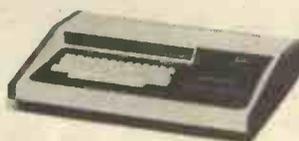We now stock the Superb new GENIE I computer. With all the features that make it one of the best value for money machines on the market.




- ★ Extended Basic including Renumber
- ★ Full upper and lower case
- ★ Internal Sound unit
- ★ Machine language monitor
- ★ 16K Ram, 12K Rom
- ★ Fully TRS80 software Compatible

PRINTERS FROM £279

A range of the best and most popular printers all at greatly reduced prices. Many include FREE paper and FREE delivery to mainland UK.

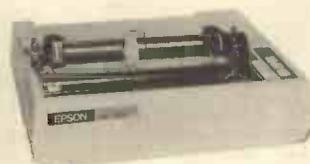- ★ Epson MX80 FT and T
- ★ Epson MX82 and MX100
- ★ OKI Microline 80, 82a and 83a
- ★ Range of interfaces for PET APPLE, UK101 etc.
- ★ Paper just £15.00 per 2000 sheets inc VAT
- ★ Contact us now for the lowest possible prices.



WE ALSO STOCK

- 2114 - £1.00 + VAT
- 4116 - £1.00 + VAT
- 2716 - £3.00 + VAT
- 2732 - £5.10 + VAT
- 40 pin jumper £5.20 + VAT

- 8T28 Buffers £1.00 + VAT
- C12 tapes £3.50 + VAT
- UK101 Graphics Board £45.00 + VAT

MAIL ORDER or why not call into our shop in Romford.
We are open Monday to Saturday 9-6 p.m.

14 CARLTON ROAD, ROMFORD, ESSEX
0708-64954

So you've fancied some WHARFEDALE E90 speakers -

But the bank manager won't co-operate! Don't despair - now there are Wilmslow Audio flat-pack kits for the Wharfedale E50, E70 and E90. A few hours of easy and interesting work will complete your speakers at a very considerable saving on buying 'assembled' systems.



The kits contain all cabinet components - accurately machined for easy assembly - all drive units, crossover networks, acoustic wadding, reflex port trim, nuts, bolts, terminals, grille fabric, etc. The cabinets can be painted or stained or finished with iron-on veneer. Easy, foolproof assembly instructions are supplied - no electronic or woodworking knowledge necessary.

- Prices: E50 kit £182 per pair including VAT, carriage and insurance £ 8
 - E70 kit £220 per pair including VAT, carriage and insurance £ 8
 - E90 kit £330 per pair including VAT, carriage and insurance £10
 - Pro E90 kit £369 per pair including VAT, carriage and insurance £10
- Credit terms available: Deposit 20%, balance over 12 months (charges currently 31.2 APR)



0625 529599

35/39 Church Street, Wilmslow, Cheshire SK9 1AS



Lightning service on telephoned credit card orders!
Please allow 7 days for delivery



The Proto-Board[®]

Now circuit designing is as easy as pushing a lead into a hole . . .
 No soldering
 No de-soldering
 No heat-spoilt components
 No manual labour
 No wasted time



For quick signal tracing and circuit modification
 For quick circuit analysis and diagramming
 With or without built-in regulated power supplies
 Use with virtually all parts — most plug in directly, in seconds.
 Ideal for design, prototype and hobby

NO	MODEL NO	NO OF SOLDERLESS TIE POINTS	IC CAPACITY (14 pin DIP 5)	UNIT PRICE	PRICE INC P&P 15% VAT	OTHER FEATURES
1	PB 6	630	6	9.20	11.73	Kit
2	PB 100	760	10	11.80	14.72	Kit
3	PB 101	940	10	17.20	21.21	
4	PB 102	1240	12	22.95	27.83	
5	PB 103	2250	24	35.95	43.06	
6	PB 104	3060	32	47.95	56.86	
7	PB 203	2250	24	59.95	70.66	5V @ 1A
8	PB 203A	2250	24	85.00	99.47	5V ± 15V
9	PB 203AK	2250	24	69.00	81.07	5V ± 15V & Kit

Tomorrow's tools for today's problems

Goods despatched within 48 hours.

GLOBAL SPECIALTIES CORPORATION



G.S.C. (UK) Limited, Dept. 5U
 Unit 1, Shire Hill Industrial Estate,
 Saffron Walden, Essex. CB11 3AQ.
 Telephone: Saffron Walden (0799) 21682
 Telex: 817477

G.S.C. (UK) Limited, Dept. 5U, Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.

1 Qty Req 2 Qty Req 3 Qty Req 4 Qty Req 5 Qty Req 6 Qty Req 7 Qty Req 8 Qty Req 9 Qty Req

Name _____ Address _____

I enclose Cheque/P.O. for £ _____ or debit my Barclaycard, Access,

American Express card no. _____ exp. date _____

FOR IMMEDIATE ACTION — The G.S.C. 24 hour 5 day a week service Telephone (0799) 21682 and give us your Barclaycard, Access, American Express number and your order will be in the post immediately

For FREE catalogue tick box

Sinclair ZX81 Personal Computer the heart of a system that grows with you.

1980 saw a genuine breakthrough – the Sinclair ZX80, world's first complete personal computer for under £100. Not surprisingly, over 50,000 were sold.

In March 1981, the Sinclair lead increased dramatically. For just £69.95 the Sinclair ZX81 offers even more advanced facilities at an even lower price. Initially, even we were surprised by the demand – over 50,000 in the first 3 months!

Today, the Sinclair ZX81 is the heart of a computer system. You can add 16-times more memory with the ZX RAM pack. The ZX Printer offers an unbeatable combination of performance and price. And the ZX Software library is growing every day.

Lower price: higher capability

With the ZX81, it's still very simple to teach yourself computing, but the ZX81 packs even greater working capability than the ZX80.

It uses the same micro-processor, but incorporates a new, more powerful 8K BASIC ROM – the 'trained intelligence' of the computer. This chip works in decimals, handles logs and trig, allows you to plot graphs, and builds up animated displays.

And the ZX81 incorporates other operation refinements – the facility to load and save named programs on cassette, for example, and to drive the new ZX Printer.



New BASIC manual

Every ZX81 comes with a comprehensive, specially-written manual – a complete course in BASIC programming, from first principles to complex programs.

Kit: £49.⁹⁵

Higher specification, lower price – how's it done?

Quite simply, by design. The ZX80 reduced the chips in a working computer from 40 or so, to 21. The ZX81 reduces the 21 to 4!

The secret lies in a totally new master chip. Designed by Sinclair and custom-built in Britain, this unique chip replaces 18 chips from the ZX80!

New, improved specification

- Z80A micro-processor – new faster version of the famous Z80 chip, widely recognised as the best ever made.
- Unique 'one-touch' key word entry: the ZX81 eliminates a great deal of tiresome typing. Key words (RUN, LIST, PRINT, etc.) have their own single-key entry.
- Unique syntax-check and report codes identify programming errors immediately.
- Full range of mathematical and scientific functions accurate to eight decimal places.
- Graph-drawing and animated-display facilities.
- Multi-dimensional string and numerical arrays.
- Up to 26 FOR/NEXT loops.
- Randomise function – useful for games as well as serious applications.
- Cassette LOAD and SAVE with named programs.
- 1K-byte RAM expandable to 16K bytes with Sinclair RAM pack.
- Able to drive the new Sinclair printer.
- Advanced 4-chip design: micro-processor, ROM, RAM, plus master chip – unique, custom-built chip replacing 18 ZX80 chips.



Built: £69.⁹⁵

Kit or built – it's up to you!

You'll be surprised how easy the ZX81 kit is to build: just four chips to assemble (plus, of course the other discrete components) – a few hours' work with a fine-tipped soldering iron. And you may already have a suitable mains adaptor – 600 mA at 9 V DC nominal unregulated (supplied with built version).

Kit and built versions come complete with all leads to connect to your TV (colour or black and white) and cassette recorder.



Computer-



Available now - the ZX Printer for only £49.⁹⁵

Designed exclusively for use with the ZX81 (and ZX80 with 8K BASIC ROM), the printer offers full alpha- numerics and highly sophisticated graphics.

A special feature is COPY, which prints out exactly what is on the whole TV screen without the need for further instructions.

At last you can have a hard copy of your program listings - particularly

useful when writing or editing programs.

And of course you can print out your results for permanent records or sending to a friend.

Printing speed is 50 characters per second, with 32 characters per line and 9 lines per vertical inch.

The ZX Printer connects to the rear of your computer - using a stackable connector so you can plug in a RAM pack as well. A roll of paper (65 ft long x 4 in wide) is supplied, along with full instructions.

16K-byte RAM pack for massive add-on memory.

Designed as a complete module to fit your Sinclair ZX80 or ZX81, the RAM pack simply plugs into the existing expansion port at the rear of the computer to multiply your data/program storage by 16!

Use it for long and complex programs or as a personal database. Yet it costs as little as half the price of competitive additional memory.

With the RAM pack, you can also run some of the more sophisticated ZX Software - the Business & Household management systems for example.

How to order your ZX81

BY PHONE - Access, Barclaycard or Trustcard holders can call 01-200 0200 for personal attention 24 hours a day, every day.

BY FREEPOST - use the no-stamp-needed coupon below. You can pay

by cheque, postal order, Access, Barclaycard or Trustcard.

EITHER WAY - please allow up to 28 days for delivery. And there's a 14-day money-back option. We want you to be satisfied beyond doubt - and we have no doubt that you will be.

To: Sinclair Research Ltd, FREEPOST, Camberley, Surrey, GU15 3BR.				Order
Qty	Item	Code	Item price £	Total £
	Sinclair ZX81 Personal Computer kit(s). Price includes ZX81 BASIC manual, excludes mains adaptor.	12	49.95	
	Ready-assembled Sinclair ZX81 Personal Computer(s). Price includes ZX81 BASIC manual and mains adaptor.	11	69.95	
	Mains Adaptor(s) (600 mA at 9 V DC nominal unregulated).	10	8.95	
	16K-BYTE RAM pack.	18	49.95	
	Sinclair ZX Printer.	27	49.95	
	8K BASIC ROM to fit ZX80.	17	19.95	
	Post and Packing.			2.95

Please tick if you require a VAT receipt

TOTAL £

*I enclose a cheque/postal order payable to Sinclair Research Ltd, for £

*Please charge to my Access/Barclaycard/Trustcard account no.

*Please delete/complete as applicable.

Please print.

Name: Mr/Mrs/Miss

Address:

sinclair ZX81

6 Kings Parade, Cambridge, Cambs., CB2 1SN.
Tel: (0276) 66104 & 21282.

FREEPOST - no stamp needed. Offer applies to UK only.

PRE 03

CMOS																			
4000	0.11	4077	0.18	4705	4.24	7447N	0.62	74153N	0.55	74366N	0.85	74LS109N	0.20	74LS248N	1.35	74CXX		Processors	
4001	0.11	4078	0.18	4706	4.50	7448N	0.56	74154N	0.55	74367N	0.85	74LS112N	0.20	74LS249N	1.35	74C00	0.20	8080 series	
4002	0.12	4081	0.12	4720	4.00	7450	0.14	74155N	0.55	74368N	0.85	74LS113N	0.20	74LS251N	0.35	74C02	0.20	8080AFC/2	£7.30
4007	0.13	4082	0.18	4723	0.95	7451N	0.14	74156N	0.55	74390N	1.85	74LS114N	0.18	74LS253N	0.35	74C04	0.20	8212	2.30
4008	0.13	4093	0.30	4724	0.95	7453N	0.14	74157N	0.55	74393N	1.85	74LS124N	0.35	74LS257N	0.40	74C08	0.20	8214	3.50
4008AE	0.80	4099	0.80	4725	2.24	7454N	0.14	74159N	0.90	74490N	1.95	74LS123N	0.35	74LS258N	0.40	74C10	0.20	8216	1.85
4009	0.25	4502	0.80	40014	0.54	7460N	0.14	74160N	0.55			74LS124N	1.80	74LS259N	0.60	74C10	0.20	8224	3.50
4010	0.30	4503	0.50	40085	0.99	7470N	0.28	74161N	0.55			74LS125N	0.24	74LS260N	0.50	74C14	0.55	8251	6.21
4011AE	0.24	4503	0.50	40098	0.54	7472N	0.27	74162N	0.55			74LS126N	0.24	74LS266N	0.22	74C20	0.20	8255	5.40
4011AE	0.24	4506	0.70	40106	0.69	7473N	0.28	74163N	0.55			74LS132N	0.42	74LS273N	0.70	74C30	0.20		
4011	0.11	4507	0.37	40160	1.05	7474N	0.28	74164N	0.55			74LS133N	0.24	74LS275N	3.20	74C32	0.20	6800/6809	
4013	0.25	4508	1.50	40161	1.05	7475N	0.35	74165N	0.55			74LS136N	0.20	74LS279N	0.35	74C42	0.80	6800P	£2.80
4015	0.50	4510	0.55	40162	1.05	7476N	0.30	74166N	0.70			74LS138N	0.30	74LS280N	2.50	74C48	1.03	68A00	4.25
4016	0.22	4511	0.45	40163	1.05	7480N	0.26	74167N	1.25			74LS139N	0.30	74LS283N	0.42	74C73	0.50	68B00	4.85
4017	0.40	4512	0.55	40174	1.05	7481N	0.20	74170N	1.25			74LS145N	1.20	74LS290N	0.50	74C74	0.50	6802	3.50
4019	0.38	4514	1.25	40175	1.05	7482N	0.75	74173N	1.10			74LS149N	0.12	74LS293N	0.40	74C76	0.48	6809	£8.75
4020	0.55	4515	1.25	40192	1.08	7485N	0.75	74174N	0.75			74LS109N	0.12	74LS296N	1.50	74C83	0.98	6810	1.25
4021	0.55	4516	0.60	40193	1.08	7486N	0.24	74175N	0.75			74LS111N	0.12	74LS298N	0.78	74C85	0.98	68A10	1.85
4022	0.55	4518	0.35	40194	1.08	7489N	1.05	74176N	0.75			74LS112N	0.12	74LS305N	0.32	74C86	0.26	68B10	2.04
4023	0.15	4520	0.80	40195	1.08	7490N	0.30	74177N	0.75			74LS131N	0.20	74LS306N	0.34	74C89	2.68	6820	1.95
4024	0.33	4521	1.30			7491N	0.55	74178N	0.90			74LS141N	0.30	74LS307N	0.32	74C90	0.80	6821	1.25
4025	0.15	4522	0.95			7492N	0.35	74179N	1.35			74LS151N	0.12	74LS308N	0.35	74C93	0.80	68A21	2.10
4026	1.05	4527	0.80	7400N	0.10	7493N	0.35	74180N	0.75			74LS152N	0.12	74LS313N	0.70	74C95	0.94	68B21	2.25
4027	0.26	4528	0.85	7401N	0.10	7494N	0.70	74181N	1.22			74LS154N	0.98	74LS317N	0.70	74C107	0.48	6840	4.25
4028	0.50	4529	0.70	7402N	0.20	7495N	0.60	74182N	0.70			74LS160N	0.37	74LS318N	0.70	74C151	1.52	68A40	4.55
4029	0.55	4531	0.65	7403N	0.11	7496N	0.45	74184N	1.20			74LS161N	0.37	74LS322N	0.37	74C154	2.26	68B40	4.85
4030	0.35	4532	0.80	7404N	0.12	7497N	1.40	74185N	1.20			74LS162N	0.37	74LS326N	0.37	74C157	1.52	6850	1.50
4035	0.67	4534	4.00	7405N	0.12	74100	1.10	74188N	3.00			74LS163N	0.37	74LS327N	0.12	74C160	0.80	68B50	2.13
4040	0.50	4536	2.50	7406N	0.22	74104	0.62	74190N	0.55			74LS164N	0.40	74LS328N	0.15	74C161	0.80	6852	2.85
4042	0.50	4538	0.85	7407N	0.22	74105	0.62	74191N	0.55			74LS165N	0.80	74LS329N	0.80	74C162	0.80	68A52	2.75
4043	0.50	4539	0.80	7408N	0.15	74107	0.26	74192N	0.55			74LS166N	0.80	74LS334N	2.50	74C163	0.80	68B52	2.95
4043AE	0.93	4543	0.80	7409N	0.15	74107	0.26	74192N	0.55			74LS168N	0.70	74LS335N	2.05	74C163	0.80	68488	5.25
4044	0.60	4549	3.50	74109N	0.35	74109N	0.35	74193N	0.55			74LS169N	0.85	74LS336N	0.29	74C164	0.80		
4046	0.60	4553	2.70	74110N	0.12	74110N	0.54	74194N	0.55			74LS170N	0.80	74LS339N	0.68	74C165	0.84		
4047	0.68	4554	1.20	74111N	0.18	74111N	0.68	74195N	0.55			74LS173N	0.80	74LS340N	0.61	74C173	0.72	Z80 series	
4049	0.24	4555	0.35	74112N	0.19	74112N	1.70	74196N	0.55			74LS174N	0.40	74LS341N	0.61	74C174	0.72	Z80A	£3.75
4050	0.24	4556	0.40	74113N	0.27	74116N	1.98	74197N	0.55			74LS175N	0.40	74LS342N	0.99	74C175	0.72	Z80ADP	7.50
4051	0.55	4557	2.30	74114N	0.51	74118N	0.85	74198N	0.85			74LS181N	1.05	74LS343N	2.75	74C176	0.72	Z80APIO	3.80
4052	0.55	4558	0.80	74116N	0.27	74119N	1.20	74199N	1.00			74LS183N	1.75	74LS344N	2.30	74C192	0.80	Z80ASIO/1	11.00
4053	0.55	4559	3.50	74120N	0.27	74120N	0.95	74211N	1.00			74LS189N	1.28	74LS345N	1.40	74C193	0.80	Z80ASIO/2	11.00
4054	1.30	4560	2.50	74121N	0.13	74121N	0.34	74246N	1.50			74LS190N	0.45	74LS347N	1.95	74C195	0.80	Z80ASIO/3	9.85
4055	1.30	4561	1.00	74122N	0.28	74122N	0.34	74247N	1.51			74LS191N	0.45	74LS348N	1.10	74C200	4.52	Z80ACTC	4.00
4056	1.30	4562	2.50	74123N	0.22	74123N	0.40	74248N	1.89			74LS192N	0.45	74LS349N	1.10	74C202	0.38	Z80AIO/4	6.50
4059	5.75	4566	1.20	74125N	0.22	74125N	0.40	74249N	1.11			74LS193N	0.45	74LS350N	1.05	74C204	0.38		
4060	0.75	4568	1.45	74126N	0.22	74126N	0.40	74250N	1.05			74LS194N	0.35	74LS351N	1.05	74C207	0.38		
4063	1.15	4569	1.70	74127N	0.12	74128N	0.65	74255N	0.66			74LS195N	0.35	74LS352N	1.70	74C209	0.38		
4066	0.30	4572	0.22	74132N	0.23	74132N	0.50	74273N	2.67			74LS196N	0.55	74LS353N	1.70	74C212	0.38		
4067	4.30	4580	3.25	74133N	0.23	74136N	0.65	74278N	2.49			74LS197N	0.50	74LS354N	1.70	74C213	0.38		
4068	0.16	4581	1.40	74137N	0.22	74141N	0.45	74279N	0.89			74LS198N	0.40	74LS355N	3.40	74C214/2	1.49		
4069AE	0.14	4582	0.70	74138N	0.22	74142N	1.85	74283N	1.30			74LS200N	3.40	74LS356N	3.40	74C217	5.78		
4070	0.16	4583	0.80	7440N	0.14	74143N	2.50	74284N	3.50			74LS202N	3.40	74LS357N	3.40	74C219	1.52		
4071	0.16	4584	0.27	7441N	0.54	74144N	2.50	74285N	3.50			74LS221N	0.50	74LS358N	3.40	74C221	1.06		
4072	0.16	4585	0.45	7442N	0.42	74145N	0.75	74290N	1.00			74LS240N	0.80	74LS359N	3.40	74C227	1.06		
4073	0.16	4702	4.50	7443N	0.62	74147N	1.50	74293N	1.05			74LS241N	0.80	74LS360N	3.40	74C228	1.06		
4075	0.16	4703	4.48	7444N	0.62	74148N	1.09	74297N	2.36			74LS242N	0.70	74LS361N	3.40	74C229	1.06		
4076	0.55	4704	4.24	7445N	0.62	74150N	0.79	74298N	1.85			74LS243N	0.70	74LS362N	3.40	74C232	1.06		
				7446N	0.62	74151N	0.55	74305N	0.85			74LS244N	0.80	74LS363N	3.40	74C235	4.32		
								74365N	1.85			74LS245N	0.80	74LS364N	3.40	74C236	4.32		
												74LS247N	1.35	74LS365N	3.40	74C237	4.32		

TELEPHONE (STD 0277) 230909 TELEX 995194 AMBIT G POSTCODE CM14 4SG
AMBIT international 200 North Service Road, Brentwood, Essex



Metal cased 9"
CROFTON MONITOR

10 MHZ Bandwidth
 P4 Standard
 £59.50 + VAT (£68.42)
 plus carriage £3.00
 For P31 (green) high
 resolution tube add £12.50 + VAT (£14.38)

Plastic cased 12"
NEW PRINCE MONITOR



High resolution
 24 MHZ Bandwidth
 P31 (green) Standard
 for only
 £78.00 + VAT
 (£89.70) plus
 carriage £3.00

ALL MAJOR CREDIT CARDS
 ACCEPTED - Small surcharge
CROFTON ELECTRONICS LTD
 35 Grosvenor Road, Twickenham, Middx TW1 4AD
 01-891 1923/1513


Now the time can tell you! . . .

New - from Silicon Speech Systems (a Powertran subsidiary) - the first ever easy-to-build kit that will give a whole new meaning to the 'speaking clock'! Electronics and quartz technology combine to enable you to construct a talking timepiece that is interesting to build - fun to have!

Full instructions make this a kit with equal appeal to the beginner or experienced constructor.

I AM ONLY
£24.50
 (includes VAT and Post & Pkg)

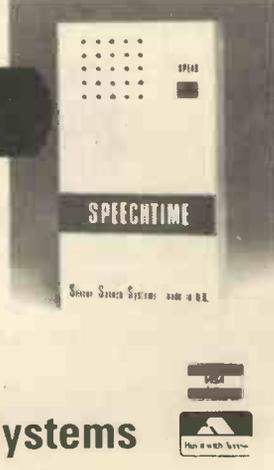- Accurate to a minute a year
- Adjustable voice pitch
- Grained stainless-steel case
- Pocket size - approx. 5in. x 2½in. x 1in.
- Useful in the home or office
- As heard on BBC radio




Silicon Speech Systems
 (A Powertran Subsidiary)

PORTWAY INDUSTRIAL ESTATE, ANDOVER, HANTS., SP10 3WN
 TELEPHONE ORDERING FOR ACCESS/BARCLAY CARD CUSTOMERS IS NOW AVAILABLE.
 JUST PHONE YOUR ORDER AND GIVE YOUR CARD NO.
 RING ANDOVER (0264) 64455.

Goods normally despatched 7 days

ELECTRONIC IGNITION KIT

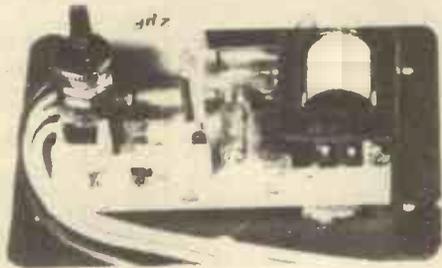

TOTAL ENERGY DISCHARGE electronic ignition gives all the well known advantages of the best capacitive discharge systems.

PEAK PERFORMANCE — higher output voltage under all conditions.

IMPROVED ECONOMY — no loss of ignition performance between services.

FIRES FOULED SPARK PLUGS no other system can better the capacitive discharge system's ability to fire fouled plugs.

ACCURATE TIMING — prevents contact wear and arcing by reducing load to a few volts and a fraction of an amp.

SMOOTH PERFORMANCE — immune to contact bounce and similar effects which can cause loss of power and roughness.

PLUS

SUPER POWER SPARK — 3½ times the energy of ordinary capacitive systems — 3½ times the power of inductive systems.

OPTIMUM SPARK DURATION 3 times the duration of ordinary capacitive systems — essential for use on modern cars with weak fuel mixtures.

BETTER STARTING — full spark power even with low battery.

CORRECT SPARK POLARITY unlike most ordinary C.D. systems the correct output polarity is maintained to avoid increased stress on the H.T. system and operate all voltage triggered tachometers.

L.E.D. STATIC TIMING LIGHT for accurate setting of the engine's most important adjustment.

LOW RADIO INTERFERENCE fully suppressed supply and absence of inverter 'spikes' on the output reduces interference to a minimal level.

DESIGNED IN RELIABILITY an inherently more reliable circuit combined with top quality components — plus the 'ultimate insurance' of a changeover switch to revert instantly back to standard ignition.

IN KIT FORM

it provides a top performance electronic ignition system at less than half the price of competing ready-built systems. The kit includes everything needed, even a length of solder and a tiny tube of heatsink compound. Detailed easy-to-follow instructions, complete with circuit diagram, are provided — all you need is a small soldering iron and a few basic tools.

AS REVIEWED IN

ELECTRONICS TODAY INTERNATIONAL JUNE '81 ISSUE
and **EVERYDAY ELECTRONICS DECEMBER '81 ISSUE**

FITS ALL NEGATIVE EARTH VEHICLES,
6 or 12 volt, with or without ballast

OPERATES ALL VOLTAGE IMPULSE TACHOMETERS

Some older current impulse types (Smiths pre '74) require an adaptor —
PRICE £2.95

STANDARD CAR KIT £14.85

ASSEMBLED AND TESTED £24.95

PLUS £1

TWIN OUTPUT KIT £22.94

For MOTOR CYCLES and CARS with twin ignition systems

ASSEMBLED AND TESTED £34.70

U.K. P.&P.

Prices include V.A.T.

ELECTRONIZE DESIGN Dept. B

Magnus Road, Wilnecote,

Tamworth. B77 5BY

Phone 0827-281000

BARCLAYCARD

VISA

DIMENSIONS:
Length 12.5 cm
Width 8.9 cm
Height 4.3 cm
Lead length 100.0 cm

TECHNICAL DETAILS

The basic function of a spark ignition system is often lost among claims for longer 'burn times' and other marketing fantasies. It is only necessary to consider that, even in a small engine, the burning fuel releases over 5000 times the energy of the spark, to realise that the spark is only a trigger for the combustion. Once the fuel is ignited the spark is insignificant and has no effect on the rate of combustion. The essential function of the spark is to start that combustion as quickly as possible and that requires a high power spark.

The traditional capacitive discharge system has this high power spark but, due to its very short spark duration and consequential low spark energy, is incompatible with the weak air/fuel mixtures used in modern cars. Because of this most manufacturers have abandoned capacitive discharge in favour of the cheaper inductive system with its low power but very long duration spark which guarantees that sooner or later the fuel will ignite. However, a spark lasting 2000µs at 2000 rev/min. spans 24 degrees and 'later' could mean the actual fuel ignition point is retarded by this amount.

The solution is a very high power, medium duration, spark generated by the **TOTAL ENERGY DISCHARGE** system. This gives ignition of the weakest mixtures with the minimum of timing delay and variation for a smooth efficient engine.

SUPER POWER DISCHARGE CIRCUIT A brand new technique prevents energy being reflected back to the storage capacitor, giving 3½ times the spark energy and 3 times the spark duration of ordinary C.D. systems, generating a spark powerful enough to cause rapid ignition of even the weakest fuel mixtures without the ignition delay associated with lower power 'long burn' inductive systems.

HIGH EFFICIENCY INVERTER A high power, regulated inverter provides a 370 volt energy source — powerful enough to store twice the energy of other designs and regulated to provide sufficient output even with a battery down to 4 volts.

PRECISION SPARK TIMING CIRCUIT This circuit removes all unwanted signals caused by contact volt drop, contact shuffle, contact bounce, and external transients which, in many designs, can cause timing errors or damaging un-timed sparks. Only at the correct and precise contact opening is a spark produced. Contact wear is almost eliminated by reducing the contact breaker current to a low level — just sufficient to keep the contacts clean.

TYPICAL SPECIFICATION

	TOTAL ENERGY DISCHARGE	ORDINARY CAPACITIVE DISCHARGE
SPARK POWER (PEAK)	140 W	90 W
SPARK ENERGY (STORED ENERGY)	36 mJ	10 mJ
SPARK DURATION	135 mJ	65 mJ
OUTPUT VOLTAGE (LOAD 50pF EQUIVALENT TO CLEAN PLUGS)	500 µs	160 µs
OUTPUT VOLTAGE (LOAD 50pF + 500 KΩ EQUIVALENT TO DIRTY PLUGS)	38 KV	26 KV
VOLTAGE RISE TIME TO 20 KV (Load 50pF)	26 KV	17 KV
	25 µs	30 µs

TOTAL ENERGY DISCHARGE should not be confused with low power inductive systems or hybrid so called reactive systems.

Goods normally despatched within 7 days.




NEW

PRACTICAL ELECTRONICS - STEREO TUNER KIT

This easy to build 3 band stereo AM/FM tuner kit is designed in conjunction with Practical Electronics (July issue). For ease of construction and alignment it incorporates three Mullard modules and an I.C. IF. System.

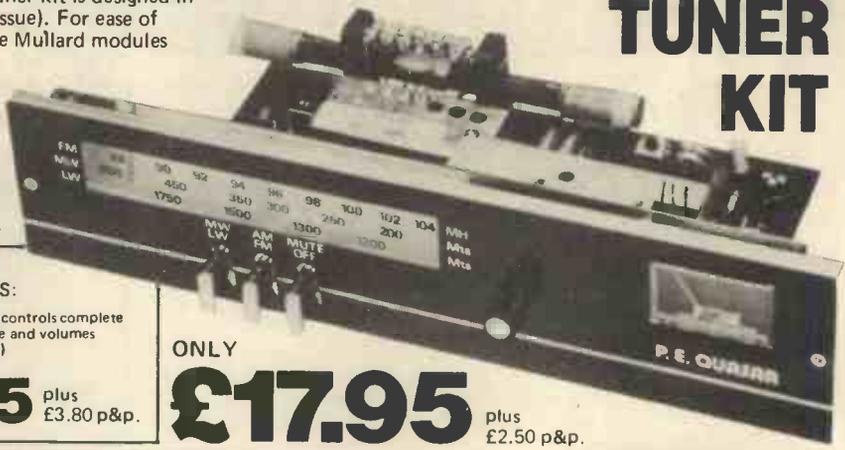FEATURES: VHF, MW, LW Bands, interstation muting and AFC on VHF. Tuning meter. Two back printed PCB's. Ready made chassis and scale. Aerial: AM - ferrite rod, FM - 75 or 300 ohms. Stabilised power supply with 'C' core mains transformer. All components supplied are to P.E. strict specification. Front scale size 10½" x 2½" approx. Complete with diagrams and instructions.



SPECIAL OFFER! TUNER KIT PLUS:


- Matching I.C. 10+10 Stereo Power amplifier kit (usually £3.95 + £1.15 p&p)
- Mullard LP1183 built preamp. suitable for magnetic/ceramic and auxiliary inputs (usually £1.95 + 70p p&p)
- Matching power supply kit with transformer (usually £3.00 + £1.95 p&p)

- Matching set of 4 slider controls complete with knobs for bass, treble and volumes (usually £1.70 + 80p p&p)

£21.95 plus £3.80 p&p.

ONLY

£17.95 plus £2.50 p&p.

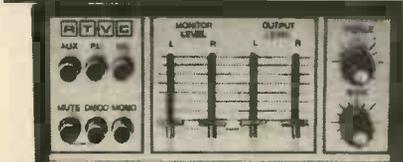

STEREO AMPLIFIER KIT

- Featuring latest SGS/ATES TDA 2006 10 watt output IC's with in-built thermal and short circuit protection.
- Mullard Stereo Pre-amplifier Module.
- Attractive black vinyl finish cabinet, 9" x 8½" x 3½" (approx)
- 10+10 Stereo converts to a 20 watt Disco amplifier.

To complete you just supply connecting wire and solder. Features include din input sockets for ceramic cartridge, microphone, tape or tuner. Outputs - tape, speakers and headphones. By the press of a button it transforms into a 20 watt mono disco amplifier with twin deck mixing. The kit incorporates a Mullard LP1183 pre-amp module, plus power amp assembly kit and mains power supply. Also features 4 slider level controls, rotary bass and treble controls and 6 push button switches. Silver finish fascia with matching knobs and contrasting cabinet. Instructions available, price 50p. Supplied FREE with the kit.

£14.95 Plus £2.90 p&p.

SPECIFICATIONS: Suitable for 4 to 8 ohm speakers. 40Hz - 20KHz. P.U. 150mV. Aux. 200mV. Mic. 1.5mV.

Tone controls

Distortion
Mains supply

STEREO MAGNETIC PRE-AMP CONVERSION KIT
Includes FREE Magnetic cartridge with diamond styli. All components including p.c.b. to convert your ceramic input on the 10+10 to magnetic. Only available with 10+10 amp. **£2.00** includes p&p.

8" SPEAKER KIT Two 8" twin cone domestic speakers. £4.75 per stereo pair plus £1.70 p&p. when purchased with amplifier. Available separately £6.75 plus £1.70 p&p.

PRACTICAL ELECTRONICS CAR RADIO KIT SERIES II

2 WAVE BAND MW - LW

- Easy to build
- 5 push button tuning
- Modern design
- 6 watt output
- Ready etched and punched PCB
- Incorporates suppression circuits.

All the electronic components to build the radio, you supply only the wire and the solder, featured in Practical Electronics March issue. Features: pre-set tuning with 5 push button options, black illuminated tuning scale. The P.E. Traveller has a 6 watt output neg. ground and incorporates an integrated ceramic filter type pre-aligned and assembled, and a Bird pre-aligned push button tuning unit.

£10.50 Plus £2.00 p&p.

Suitable stainless steel fully retractable aerial (locking) and speaker (6" x 4" app.). available as a kit complete. **£1.95/pack.** Plus £1.15 p&p.

HIGH POWER AMPLIFIER MODULES

READY BUILT OR IN KIT FORM

	KIT	BUILT
125 WATT MODEL	£10.50 Plus £1.15 p&p	£14.25 Plus £1.15 p&p.
200 WATT MODEL	£14.95 Plus £1.15 p&p	£18.95 Plus £1.15 p&p.

SPECIFICATIONS:	125 W Model	200 W Model
Max. output power (RMS)	125 watts	200 watts
Operating voltage (DC)	50 - 80 max.	70 - 95 max.
Loads	4 - 16 ohms	4 - 16 ohms
Frequency response measured @ 100 watts	25Hz - 20KHz	25Hz - 20KHz
Sensitivity for 100 watts	400mV @ 47K	400mV @ 47K
Typical T.H.D. @ 50 watts, 4 ohms	0.1%	0.1%
Dimensions (both models)	205 x 90 and 190 x 36mm.	

The power amp kit is a module for high power applications - disco units, guitar amplifiers, public address systems and even high power domestic systems. The unit is protected against short circuiting of the load and is safe in an open circuit condition. A large safety margin exists by use of

generously rated components, result, a high powered rugged unit. The PC Board is back printed, etched and ready to drill for ease of construction and the aluminium chassis is preformed and ready to use. Supplied with all parts, circuit diagrams and instructions.

ACCESSORIES:

- Suitable LS coupling electrolytic for 125W model **£1.00** plus 25p p&p.
- Suitable LS coupling electrolytic for 200W model **£1.25** plus 25p p&p.
- Suitable mains power supply unit for 125W model **£7.50** plus £3.15 p&p.
- Suitable Twin transformer power supply for 200W model **£13.95** plus £4.00 p&p.



30+30 WATT STEREO AMPLIFIER

Viscount IV unit in teak simulate cabinet, silver finished rotary controls and pushbuttons with matching fascia, mains indicator and stereo jack socket. Functions switch for mic magnetic and crystal pickups, tape and auxiliary. Rear panel features fuse holder, DIN speaker and input socket 30+30 watts RMS, 60+60 watts peak. For use with 4 to 8 ohm speakers. Size 14½" x 10" approx. **£32.90** Plus £3.80 p&p.

TV SOUND TUNER KIT

as featured in E.T.I. December '81 issue. Kit of parts including PCB, UHF tuner, I.C.'s, all components excluding case, and selector switch. **£11.45 + £1.50 p&p.**



• Transformer £1.50 + £1.50 p&p (p&p free on transformer if ordered with kit). • Ready built LP1183 Module for simulated stereo operation **£1.95 + 75p p&p.**

MONO MIXER AMPLIFIERS



50 WATT Six individually mixed Inputs for two pick ups (Cer. or Mag.), two moving coil microphones and two auxiliary for tape, tuner, organs, etc. Eight slider controls - six for level and two for master bass and treble, four extra treble controls for mic and aux inputs. Size: 13½" x 6½" x 3½" app. Power output 50 watts R.M.S. (continuous) for use with 4 to 8 ohm speakers. Attractive black vinyl case with matching fascia and knobs. Ready to use. **£39.95** Plus £3.70 p&p.



100 WATT Brushed Aluminium fascia and rotary controls. Size: approx. 14" x 4" x 10½". Five vertical slider controls, master volume, tape level, mic level, deck level, PLUS INTERDECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre fade level controls (PFL) lets YOU hear the next disc before fading it in. VU meter monitors output. **£76.00** Plus £4.60 p&p.



CALLERS ONLY

323 Edgware Rd, London W2. Tel: 01-723 8432. Open 9.30am - 5.30pm. Closed all day Thursday. Persons under 16 not served without parents authorisation. **ALL PRICES INCLUDE VAT AT 15%.**

MAIL ORDER ONLY

21B HIGH STREET, ACTON, W3 6NG. Note: Goods despatched to UK postal addresses only. For further information send for instructions 20p plus stamped addressed envelope. All goods delivered within 14 days of receipt of order.

All items subject to availability. Prices correct at 1/12/81 and subject to change without notice. RTVC Limited reserve the right to update their products without notice.

FREE

While reading the local paper recently, the thought occurred that there must be hundreds of electronics hobbyists with odd bits of test gear, audio equipment, or components stacked away that they could sell in an "under a tenner" column of the type now found in many local papers. During discussions in the editorial office it was thought to be an excellent idea and that we could run advertisements with no price limit, provided the service was only available to private readers and not to the trade or anyone making money from buying and selling anything to do with electronics. After all, the trade can advertise in our pages or take a classified space, but with the cost of classifieds rising it is not a viable proposition for the reader who would like to sell a few components, a speaker or a meter.

We think a readers free ad. page will be of interest to most readers, will encourage an interface between hobbyists and could realise some cash to help with our hobby. We want to encourage you to buy, sell or swap anything to do with electronics from a bag of resistors to a printer, computer, organ, TV or oscilloscope but we have

decided that we cannot accept ads. for computer software. After all, if you're writing and selling software you are "in business" and if you're selling someone else's you're probably infringing their copyright!

PE BAZAAR

We have decided to call the feature *PE Bazaar* as we feel this term describes perfectly just what it's all about. As we have said it is for **PE readers only** and we have thus instigated a coupon system for sending in ads. This means that you must have an up to date issue to send in your ad. and you must sign a declaration to say you are not running a business dealing with electronics in any way. We have reserved the right to refuse ads. if we are worried about the contents or the private reader/business situation.

In order to give everyone a chance we can only accept one ad. per coupon and we have limited the number of words in each ad. so that we can get a good variety on a page, or in any small space we may have—say at the end of an article. Full details of *PE Bazaar* and the first ad. coupon can be found on page 31. If we get some ads. back very soon after the publication of this issue,

we hope to be able to get them in next month—it's first come, first served.

RESPONSIBILITY

One final point, we must make it quite clear that PE cannot be held responsible for any errors in the free ads. or for any transactions that take place between readers as a result of a free ad. We will not enter into correspondence concerning free advertisements, their contents or transactions.

However, we must say that in our editorial dealings with our readers we have found you to be a wonderfully reliable, trustworthy and honest lot. We have often sent odd items to readers, requesting payment on receipt and almost without exception have received prompt payment. We would like to take this opportunity to thank you—it saves us all time, trouble and money when things work in this way. Let's hope *PE Bazaar* is popular, helps as many of you as possible and leads to some useful exchanges and friendships within our hobby. It's up to you now!

Like everything else, it seems to be such a good idea, we wonder why we didn't think of it months ago?

Mike Kenward

EDITOR Mike Kenward

Gordon Godbold ASSISTANT EDITOR

Mike Abbott TECHNICAL EDITOR

David Shortland PROJECTS EDITOR

Jasper Scott PRODUCTION EDITOR

Jack Pountney ART EDITOR

Keith Woodruff ASSISTANT ART EDITOR

John Pickering SEN. TECH. ILLUSTRATOR

Isabelle Greenaway TECH. ILLUSTRATOR

Colette McKenzie SECRETARY

Editorial Offices:

Practical Electronics,
Westover House,
West Quay Road, Poole,
Dorset BH15 1JG

Phone: **Editorial Poole 71191**

We regret that lengthy technical enquiries cannot be answered over the telephone (see below).

Advertising Offices:

Practical Electronics Advertisements,
King's Reach Tower,
King's Reach, Stamford Street, SE1 9LS
Telex: 915748 MAGDIV-G

ADVERTISEMENT MANAGER

SECRETARY

AD. SALES EXEC.

CLASSIFIED SUPERVISOR

AD. MAKE-UP/COPY

D. W. B. Tilleard

Christine Pocknell

Alfred Tonge

Barbara Blake

Ian Sweeney

} 01-261 6676

01-261 6819

01-261 5897

01-261 6601

Technical Queries

We are unable to offer any advice on the use or purchase of commercial equipment or the incorporation or modification of designs published in PE. All letters requiring a reply should be accompanied by a stamped, self addressed envelope, or international reply coupons, and each letter should relate to **one published project only**.

Components and p.c.b.s are usually available from advertisers; where we anticipate difficulties a source will be suggested.

Back Numbers

Copies of most of our recent issues are available from: Post Sales Department (Practical Electronics), IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF, at 95p each including Inland/Overseas p&p.

Binders

Binders for PE are available from the same address as back numbers at £4.60 each to UK or overseas addresses, including

postage and packing, and VAT where appropriate. Orders should state the year and volume required.

Subscriptions

Copies of PE are available by post, inland or overseas, for £13.00 per 12 issues, from: Practical Electronics, Subscription Department, Oakfield House, Perymount Road, Haywards Heath, West Sussex RH16 3DH. Cheques and postal orders should be made payable to IPC Magazines Limited.

NEWS &

Edited by
Jasper Scott

Public consultation on radio frequencies

Wider public consultation on proposals which could affect frequency allocations for some aircraft and shipping radio services has been announced by the Home Office.

The Home Secretary was giving details of the United Kingdom's preparations for the 1983 World Administrative Conference for Mobile Telecommunications, to be held in Geneva, in answer to a Parliamentary Question from Mr. Peter Viggers MP. The decisions made at the Geneva Conference will govern frequency allocations for certain maritime and aeronautical mobile radio services.

The Home Secretary pointed out that non-government organisations had already been consulted about the UK's provisional proposals for the conference, but he had decided that views should be sought from a broader public so that no significant point was overlooked.

The UK proposals deal mainly with two major items:

Regulatory provisions for the introduction and development of the Inter-Governmental Maritime Consultative Organisation's Future Global Distress and Safety System; and the drawing-up of channelling plans for the maritime mobile service in the medium-frequency (MF) and high-frequency (HF) bands. Other UK proposals seek improvements in the regulation of the aeronautical mobile service, and cover miscellaneous points on the agenda.

Copies of the proposals can be obtained from: Home Office Radio Regulatory Department, Room 804, Waterloo Bridge House, Waterloo Road, London SE1 8UA.

Grand Prize

British Telecom's Prestel world viewdata service is offering a £1000 prize to the designer of the best Prestel adaptor for the top-selling Sinclair ZX81 personal computer.

Sinclair Research, which is to provide one of the judges, strongly supports the competition and believes that a successful design will offer its established 150,000 UK users a valuable new application. Although a number of microcomputers can already receive Prestel, these numbers would mark a very significant service extension for British Telecom.

Telesoftware—computer programs distributed via teletext or viewdata to computers in schools, homes and offices—is now a major Prestel growth area, and many program publishers are becoming active and establishing libraries that can hold up to 1,000 pages following the Department of Industry's initiative in funding the Educational Telesoftware Project.

The prize will be awarded to the adaptor which best combines 'low price, elegant design

and practical robustness', and the working design submitted must be capable of being modified to receive approval for attachment to the telephone network.

Closing date is March 14th, 1982, and further details, specification and entry forms are available from Tony Sweet, Prestel Headquarters, Telephone House, Temple Avenue, London EC4 0HL (01-583 9811).


AM CB: AN APRIL FOOL

Following numerous rumours that the Government is considering legalising CB on 27MHz AM, the Home Office has issued the following statement:

"Don't be misled by unfounded rumours claiming that the use of illicit 27MHz AM sets will be legalised. The Government has no intention of making any changes to the new legal 27MHz FM CB service."

Reports abound of AM sets carrying labels stating that the apparatus cannot be used "until April 1982". Any such stickers are quite simply hoaxes.

POCKET MICROSCOPE

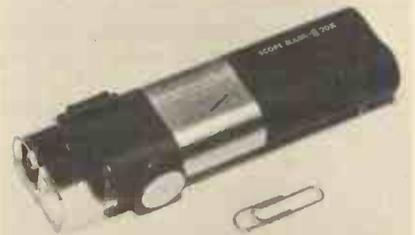

Can't quite make out that dry joint or broken p.c.b. track? What you may need is a pocket microscope, and Stotron Ltd. have recently introduced one which could be just what you need. With 20X magnification and a graticule showing linear and angular measurements, the unit is only 125mm long. Illumination is powered by standard 1.5V penlight batteries, and a micro-stand with spring clips for sample slides is also available, so the microscope can be used like a conventional model.

Priced at £16.99 plus £2.80 for the stand, the 'scope is available from Stotron Ltd., Unit 1, Haywood Way, Ivyhouse Lane, Hastings, East Sussex (0424 442160).

CAR COMPUTER



Pimac Systems Ltd., who supply kits for the PE Car Computer, inform us that they have been able to reduce the price for the complete kit to £78.50 plus £1 p&p. The unit is also available ready built, price £88.50 plus £1 p&p. Both prices include VAT. Pimac Systems Ltd., 20 Bloomfield Road, Moseley, Birmingham B13 9BY.

MARKET PLACE

Items mentioned are available through normal retail outlets unless otherwise specified. Prices correct at time of going to press.

Briefly...

This year, the All-Electronics/ECIF show will be doubled in size and held at the Barbican Exhibition Centre in the City of London. It will run from Tuesday April 20th to Thursday April 22nd, and, say the organisers, will offer the largest and most comprehensive display of the electronics industry that the capital has seen for many years.

Tempus—often featured in these pages as suppliers of Casio products—have moved from their premises in East Road, Cambridge. Their new address is: 38 Burleigh Street, Cambridge CB1 1DG.

Barrie Electronics Ltd. inform us that they have been appointed a franchised distributor for the "budget range" of toroidal transformers manufactured by Cotswold Electronics Ltd.

The fifty-eight toroidal transformers will complement the 150 stacked laminated types stocked by Barrie Electronics on an off-the-shelf basis.

Barrie Electronics Ltd., 3 The Minories, London EC3N 1BJ (01-488 3316).

PCB DRILL OFFER

Due to demand for this exceptionally priced tool which was on Special Offer in our January issue, the offer closing date has been extended to March 26th 1982. Please contact Watford Electronics to ensure supply. Price is £8.60 inclusive.

Countdown...

Please check dates before setting out, as we cannot guarantee the accuracy of the information presented below.

BEX Bournemouth Feb. 17-18. K
Microsystems Feb. 24-26. West Centre Hotel, London. Z1
Seminex Mar. 29-Apr. 2. Imperial College, London. H1
Laboratory Edinburgh Mar. 30-31. Ass. Rooms, Edinburgh. E
CAD Mar. 30-Apr. 1. Metropole, Brighton. Z1
Sensors & Systems Mar. 30-Apr. 1. The Forum, Wythenshawe, Manchester. T
ETM Mar. 30-Apr. 1. The Forum, Wythenshawe. T
Peripherals Mar. 31-Apr. 2. West Centre Hotel, London. Z1
Laboratory Manchester Apr. 7-8. New Century Hall, Manchester. E
All Electronics Show Apr. 19-21. Barbican Centre, London. E

WERSI'S COMET



Recently unveiled by Aura Sounds in London, the Wersi Comet is the latest addition to the increasingly popular range of Wersi Organs. The Comet is a completely new model—not a modification or development of any other Wersi organ, and has been designed to give the best possible sound quality and features at a budget price.

As well as traditional drawbar and orchestral sounds, the Comet provides a wide range of other voices, including various guitars, synthesiser and percussion. Numerous effects are incorporated, including three way vibrato, slalom and the Wersivoice rotating speaker sound. A totally new feature is the Comet's facility to accept connection of up to four 'satellite' keyboards, so that up to five musicians can play the one organ together.

As with all other Wersi instruments, the Comet is available ready built or as a kit. If you choose to build a Comet yourself (which is a very straightforward operation estimated to take only 100 hours, due to the use of plug-in circuit boards and ribbon cable wiring) you can save almost half the cost of the ready built unit.

The Comet is available either as a home console model (W10S) or as a portable unit with detachable legs (W10T). Prices are as follows: W10S £3,620—ready built; £1,899—complete kit. W10T £3,592—ready built; £1,971—complete kit. Further information is available from Aura Sounds Ltd., 14-15 Royal Oak Centre, Brighton Road, Purley, Surrey (01-668 9733).

BEX Brighton Apr. 28-29. K
Compec Europe May 4-6. Centre Int. Rogier, Brussels. Z1
Scotalex. Jun. 8-10. Roy. Highland Ex. Hall, Inghliston, Edinburgh. A1
BEX Leeds Jun. 9-10. K
Transducer/Tempeon Jun. 29-Jul. 1. Wemb. Conf. Centre. T
BEX Croydon Jun. 30-Jul. K
Leeds Electronics Show Jul. 6-8. University. E
Laboratory London Sep. 14-16. Grosvenor House. E

A1 Institute of Electronics, Rochdale, Lancs.
E Evan Steadman, Saffron Walden ☎ 0799 22612
H1 Seminex Ltd., Tunbridge Wells ☎ 0892 39664
K Douglas Temple, Bournemouth ☎ 0202 20533
L1 World Trade Centre ☎ 01-488 2400
T Trident Tavistock ☎ 0822 4671
V SDL ☎ Dublin 763871
Z1 IPC Exhibitions, Sutton ☎ 01-643 8040

introducing

The WERSI Comet



CLOSE UP OF COMET KEYBOARD

Aura Sounds have pleasure announcing the Comet, the "Band in One" organ, is now available through our branches. Once again the Comet achieves the optimum performance in its class.

It offers:-

- Numerous realistic and interesting tonal colours with guitar voices, synthesiser and other modern sounds together with the more traditional drawbar and orchestral sounds
- Playing aids include chord memory, WRS, Keyboard Selector, Wersiomatic rhythm and automatic accompaniment section plus much, much more



THE COMET TRANSPORTABLE W10 T

• Comet can accept up to four satellite keyboards (in addition to the 2 keyboards on the organ — a five man band can play on one instrument)

• Wersi have simplified self assembly even more, with plug in circuits etc.

• Ergonomic playing table eases operation. The Comet is available in the elegant lines of the spinet (W10 S) and with chromed steel legs (W10 T) for transportability

The Comet, the Organ to see through the eighties — available now.

For more details of this superb organ, ring us now on 01-668 9733 or write to Aura Sounds Ltd. at the Purley Branch.



THE COMET SPINET W10 S

AURA SOUNDS LTD.
 are the first company to successfully market WERSI organs and kits in the U.K.
 We have modern show-rooms, where we pride ourselves you will receive a friendly welcome. Why not pop in and see the WERSI range for yourself — we can always arrange a free demonstration. We also offer a free technical telephone support service which is second to none.

Alternatively, fill in the coupon below for free details. For immediate action telephone 01-668 9733 24 hour answering service.


AURA SOUNDS LTD.
 14-15 Royal Oak Centre, Brighton Road, Purley, Surrey.
 Tel: 01-668 9733
 17 Upper Charter Arcade, Barnsley, Yorkshire.
 Tel: (0226) 5248
 1729 Coventry Road, Sheldon, Birmingham.
 Tel: 021-707 8244
 Micro Centre, Albany Road, Newquay, Cornwall.
 Tel: Newquay 5953

Please send me FREE, all the details of The Comet and Wersi Range

NAME _____

ADDRESS _____

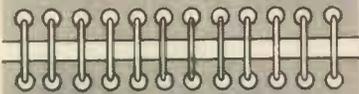Send to Aura Sounds Ltd., 14/15 Royal Oak Centre, Brighton Road, Purley, Surrey.



INDUSTRY NOTEBOOK

By Nexus



Salaries

A new year always brings thoughts of what lies ahead and reflection on the past. A main preoccupation is the personal one of jobs and salaries. On the broader front there is the anxiety that political hot-heads will rock the industrial boat and put all our jobs at risk. But assuming, hopefully, that militants can be bought off or otherwise contained then 1982 could still be a good year for recovery.

Barring political upheaval, any competent person in electronics can expect to hold his job. The adventurous may well rapidly improve their position and prospects by changing jobs. There are plenty of openings available and industry personnel managers are still complaining that good people are hard to find and how much it costs in advertising and interview time to find them.

The lowest advertised salary I have spotted recently is for R & D engineers at £5,176 for a junior starting post. But this was in Government service carrying some advantage in security and rising to £8,589.

A BBC call for transmitter and planning engineers gave a range of £9,000 to £11,000. An instrument engineer in South Wales is offered circa £9,000, another similar post in Essex up to £12,000. A development engineer in television was promised £10,000, his laboratory supervisor £16,000.

Overseas the salaries are higher and most enjoy tax advantages. A quick sample threw up a salesman (Middle East) £18,000, telecomms engineer (Saudi Arabia) £20,000 tax free, electronics lecturers (Hong Kong) circa £20,000, branch manager (Iraq) up to £24,000.

Everyone will hold his own views on the value of the salaries in relation to environmental factors, separation from family etc. I have known people move job to a lower salary in a different area to secure better education for their children. It seems that salaries in general are holding up well and that the variety of jobs and locations in

electronics gives far more choice and opportunity than most other industries.

Backward Glance

Last year was pleasurable in the number of success stories I was able to record. And it finished up with the giants of the industry continuing to improve not only their sales (including exports) and profits but also their order books. GEC-Marconi, for example, managed another scoop with a £500 million contract for the Royal Navy's heavyweight torpedo. On the technological front there were also gains with many new equipments and systems on offer.

Personality of the year was unquestionably Sir Ernest Harrison, mastermind of the Racal Electronics Group, who was heaped with honours, principally a well-deserved Knighthood but also Honorary Doctorates from Cranfield Institute of Technology and the University of Surrey. He finished the year with a flourish, winning the Businessman of the Year Award.

The citation of the latter mentioned the acquisition and subsequent turn-round in fortune of Decca but I think the last part would have pleased Sir Ernest best. It added, "And for providing a rallying point for industry, a much-needed demonstration that where the will is present, British companies, their managements and their products can equal the best in the world, even in the toughest high-technology markets which are too often considered to be the preserve of Japan and the USA."

Another well-deserved honour, the Gold Medal of the Royal Aeronautical Society, went to J.E. (Jack) Pateman for 'building-up British technical and industry leadership in the avionics field'. Pateman is managing director of Marconi Avionics and in ten years he created 8,000 new jobs, tripling the size of the company to become Europe's largest producer and top exporter of aviation electronics.

In case you imagine these men are nothing but workaholics I should mention that Jack Pateman enjoys gardening and sailing and Sir Ernest shares Jack's enthusiasm for gardening but also lists wild-life, all sports, but particularly soccer (I recall he was an Arsenal fan at one time and maybe still) among his interests.

Up North

With the great bulk of the electronics industry concentrated in the South and South East, the Midlands and Northern regions get less attention than they deserve. I recently had the opportunity of visiting three companies in regions which are generally described as depressed. This is certainly true of the inner city areas I saw on the trip but there was nothing depressing in the companies.

Maybe I was lucky in my choice but all three had expanded during the recession, had new products and services in planning, and all believed in a great future. One of the companies, to my astonishment, had been running three shifts round the clock throughout the whole of the recession.

None of them had had an easy time but there were no complaints. Just enthusiasm to get on with the job.

Energy

It seems only yesterday that we were all talking of the energy famine. Today we have a glut of oil and coal. But yesterday's scare triggered a surge of activity in developing alternative sources of energy.

One result is IBA's experimental sun-and-wind powered TV relay station at Bossiney on the north Cornish coastline. All power for the transposers and receivers come from natural sources. The idea of a hybrid sun-and-wind system is that if the sun isn't shining there is more than a fair chance that the wind will be blowing, and often both will be generating at the same time. When nature is not generous the system is backed up by a reservoir of three dozen lead-acid batteries with a capacity of 1,000Ah. The windmill produces 150W at wind speeds of 15 m.p.h. and 864 solar cells produce up to 780W in peak sunlight. The TV relay equipment consumes 150W.

To get Channel Four available to a target of 99.9 percent of the population some extra hundreds of such low power relay stations will be needed. But energy conservation is only part of the reason for the self-contained station. The other, often more compelling, reason is that these low-power relays, sometimes serving as few as 500 people or less, are on difficult and remote sites where the capital cost of running power lines to them is out of proportion.

Inmos

The Inmos factory at Newport, Gwent, some 85,000 sq.ft. of it, is now becoming a reality. Building has been in progress for a full year and the 30,000 sq.ft. clean area should be installed by March.

The Newport plant appears to be definitely scheduled for wafer fabrication and an eventual workforce of 1,000 is still envisaged. But assembly might still take place in the Far East.

A number of questions still overshadow the Inmos project, not least the departure of Paul Schroedor who as Executive Director, corporate development, was clearly a key man. The product strategy and future funding remain unclear. Obviously there are elements of commercial security involved. Anyway, with so much now invested and a tentative foothold in the market we can do no more than wish Inmos the best of British luck.

Vigorous ATE

Automatic Test Equipment (ATE) is still a blossoming market under vigorous attack by all the leading manufacturers. Typical is Marconi Instruments System 80X, unveiled at the ATE Exhibition in Brighton last December. The 80X has been designed with the US market in mind and MI has opened an ATE facility at Sunnyvale in an attempt to gain a larger market share. Prices start at £80,000 and rise to £150,000 for a complex system with up to 2,000 test points.

THE cost of electrical energy consumption has become increasingly significant in recent years as the price of primary fuels has risen more quickly than the average increase in the cost of living. In order to control costs in the house, it is necessary to know which appliances cost the most to use and to what extent savings can be made by reduced usage, turning thermostats down, etc. The watt-hour meter provided by the electricity supply authority does give a means of calculating total consumption and hence the staggering quarterly bill. However, it gives no indication of the rate at which costs are being incurred or which appliances are consuming energy at the greatest rate and what the individual cost is.

All appliances are supplied with a label indicating their power rating but to calculate the cost of running a washing machine through a 45 minute cycle with intermittent motor running, thermostatically controlled heating, pumping and spinning would be almost impossible for the average person.

The device described in this article continuously measures the current being consumed by such an appliance and having previously had the latest cost per unit of electricity keyed into it, displays the charge as it is being incurred. It was designed about three years ago and is the subject of a UK Patent application. Only recently has the cost of the components used reduced to the level where a home construction kit has become an attractive proposition.

TELECTRIC BASICS

The basic operation of the Telectric can be explained with reference to the block diagram of Fig. 1. The current consumed by the appliance plugged into the 13A socket flows through the primary turns of the current transformer and the secondary voltage induced forms the input to IC3 in order to measure this current. The PSU provides a 5 volt supply and also a sync pulse which occurs at the zero crossing of the a.c. mains voltage. The microprocessor reads the control keys, provides the display drive and multiplexing and samples the output of IC3 at the peak of the mains voltage waveform on both negative and positive half cycles. From the stored value of the cost per unit the incremental cost per half cycle is calculated and added to the running total for display.

There is one control switch and four push button keys. When the switch is in the cost per unit position the display initially reads Ent. and a single push of any key increments the display digit directly above it in order to enter the cost per unit in pence to three decimal places. When the control

switch is in the electricity bill position the four push buttons assume their control functions. These are:

Start Resets the accumulated charge and elapsed time to zero and starts new sequence.

Pause Holds the current reading of charge and time. A second push of this key restarts from the previous readings.

Time/Cost Toggles the display between displaying time and charge.

Check Whilst held down, the current value of the cost per unit is displayed as a check on operation.

DISPLAY FORMAT

In the cost per unit position the decimal point is located between the two left hand digits and the display indicates the unit cost in pence.

With the control switch in the electricity bill position the display is auto ranging, the device having been designed to accumulate up to £99.9 in cost and 99.9 days in time. The ranges and examples of their display formats are as follows:

Cost

up to 9.99p	e.g. 2.14P	pence and decimals of
10p to 99.9p	e.g. 47.1P	pence
£1.0 to £9.99	e.g. L7.85	pounds and pence
£10.0 to £99.9	e.g. L90.6	pounds and decimals of
		pounds

Time

1 second to 1 hour	minutes and seconds
e.g. 27.59	
1 hour to 1 day	hours and minutes
e.g. 14.27	
1 day to 99 days	days and decimals of days
e.g. 9.9d	

CIRCUIT DESCRIPTION

All the circuitry in the device uses a 5 volt supply and the circuit diagram is divided into two parts; Fig. 2 showing the power supply and sync pulse generator and Fig. 3 showing the processor, etc. The 5 volts is generated using a 9V (6VA) transformer, bridge rectifier and a 7805 i.c. regulator. The sync pulse generation can be described with reference to Fig. 5 which shows the waveforms through IC8. The full wave rectified input to IC8a is inverted and produces a positive going pulse about 2ms wide and symmetrical about the zero crossing of the a.c. mains waveform. This is delayed by R21, C6. The output of IC8b is a negative going 2ms pulse with its leading edge corresponding approximately



SPECIFICATION

Display

4 digit 7 segments l.e.d.s 0.5" high with decimal points.

Controls

S1 Cost per Unit/Electricity Bill
Output socket power switch (No effect on metering function)

S2-S5

Functions

A) Switch in 'Cost per Unit' position

S2 Most significant digit increments every time key is pressed, 0-9
S3, 4, 5 As S2 for digits 2, 3, 4 of pence per unit figure. This position of the switch serves only to enter the pence per unit figure. The decimal point second from left is illuminated. The electricity cost is not monitored. Cost and elapsed time functions are set to zero



B) Switch in 'Electricity Bill' position

S2 ('Check') While pressed pence per unit is displayed (operational check)
Otherwise S5 controls display
S3 ('Start') Each depression of key zeroes electricity bill and time elapsed. Electricity bill begins to total from moment of depression
Subsequent depression zeroes and restarts.
S4 ('Pause') Depression of key halts totalling of cost and elapsed time
Subsequent depression restarts from previous reading without zeroing
S5 ('Time/Cost') Display shows electricity bill initially. First depression causes display to show elapsed time. Second depression electricity bill, etc.

Maximum cost per unit 9.999 pence
Maximum electricity bill total £99.9
Maximum elapsed time 99.9 days
Accuracy better than 1% for 13A load

with the zero crossing. IC8c speeds up these edges and C8 couples them to IC8d which is biased below its threshold by R22 and R23. Thus the output from IC8d is a negative pulse approximately 20µs wide corresponding to the zero crossing and this forms a synchronising pulse.

The microprocessor controlling the Telectric is the 8035 which contains its own clock generator, reset, and interrupt input pins. It has 64 bytes of on chip RAM, an 8 bit data/address bus, two 8 bit I/O ports and external memory read and write timing signals. It also has an on chip timer which is used to time the ADC sampling at the peak of the a.c. voltage waveform.

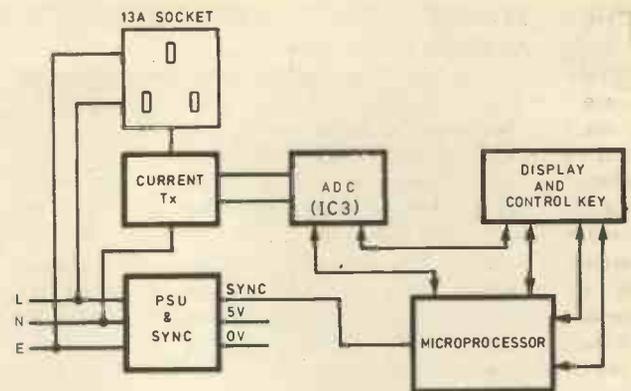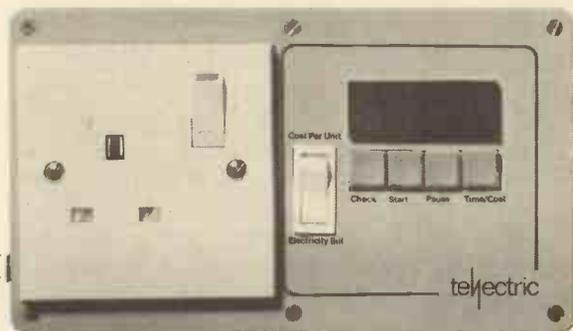

EG 7.80


Fig. 1. Block diagram

Details of the microprocessor, bus timing and software will follow next month, however, it is worth mentioning that the displays are of the common anode l.e.d. type and their pin connections are shown in Fig. 4. Pnp transistors are used to drive the common anode of each display and the multiplex frequency is 200Hz. The cathodes of the individual segments are driven via open collector gates and the microprocessor controls the display decoding in order to provide the special characters not normally available in a standard decoder.

CURRENT MEASUREMENT

In measuring mains current, the simplest way would be to use a series resistor but this has several drawbacks. The ADC requires a 5 volt peak-to-peak voltage waveform at its input for maximum current corresponding to a 40 amp peak to peak sinusoidal current or 14.14 amps r.m.s. The power developed in such a resistor would be 25 watts at peak load which is obviously not desirable. A smaller resistor could be used with an op-amp to multiply up the voltage generated but this technique still requires the circuitry to be connected to the mains and faults could be catastrophic. It was therefore decided to use a current transformer to provide full isolation.

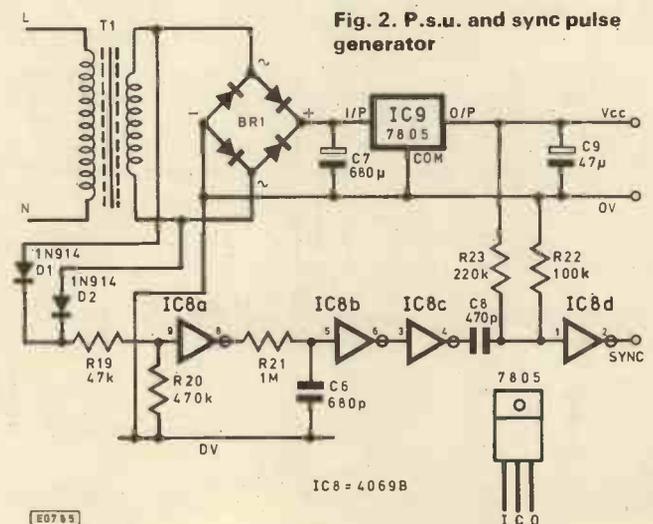
Purpose designed current transformers are quite expensive and so a 3VA mains to low voltage transformer is used in the Telectric. This has its low voltage winding removed to enable one and a half turns of the mains neutral lead to be threaded onto the transformer before connection to the output socket.



E0785


Fig. 2. P.s.u. and sync pulse generator

Fig. 4. The pin connections to a display digit

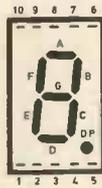


Pin	FUNCTION
1	E CATHODE
2	O CATHODE
3	COMMON ANODE
4	C CATHODE
5	DP CATHODE
6	B CATHODE
7	A CATHODE
8	COMMON ANODE
9	F CATHODE
10	G CATHODE

EG7&7

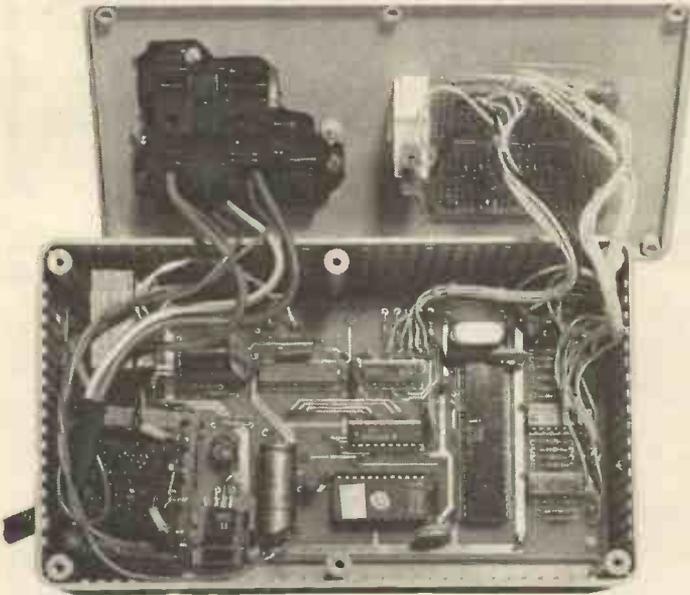

Internal assembly

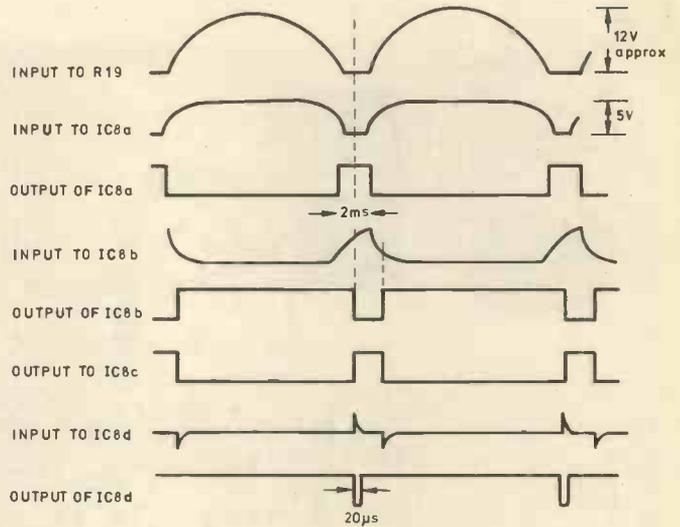


EG7&8

Fig. 5. Showing the waveforms through IC8

CONSTRUCTION

All of the components except the display and switches are mounted on the main p.c.b. which is double sided. The foil layouts are shown in Figs. 6 and 7 and the component layout in Fig. 8. Although the p.c.b. is double sided it has been designed with no through connections on i.c. pins and the position of these is shown by large dots in Fig. 8. Also shown are some extra decoupling capacitors which do not appear as components in the circuit diagrams. The p.c.b. should preferably be assembled using i.c. sockets for all i.c.s so that faults can be easily rectified.

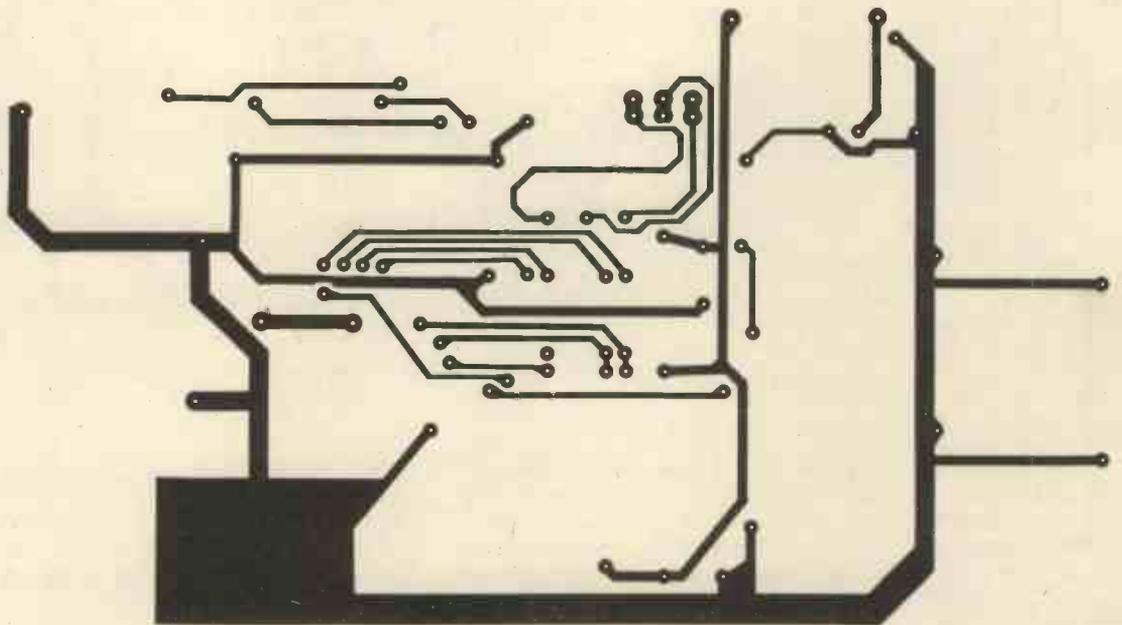

EP799

Fig. 6. Topside of p.c.b.

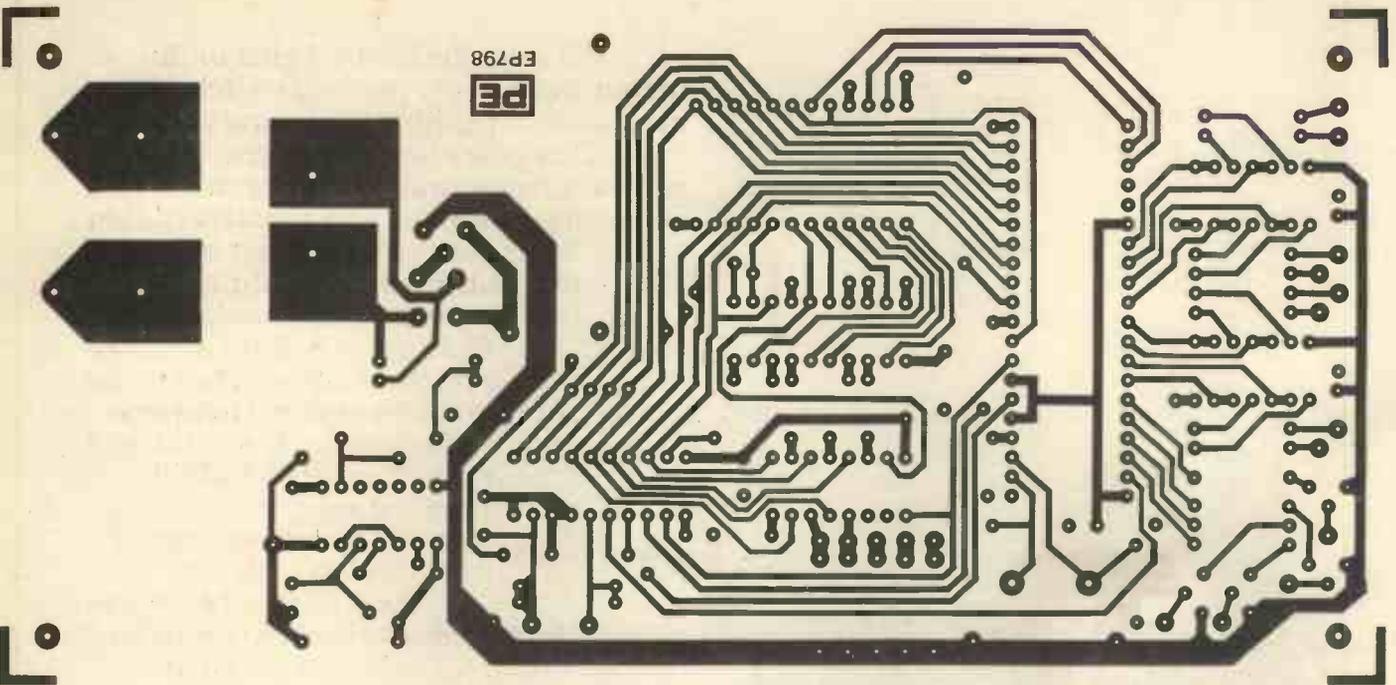


Fig. 7. Underside of p.c.b.

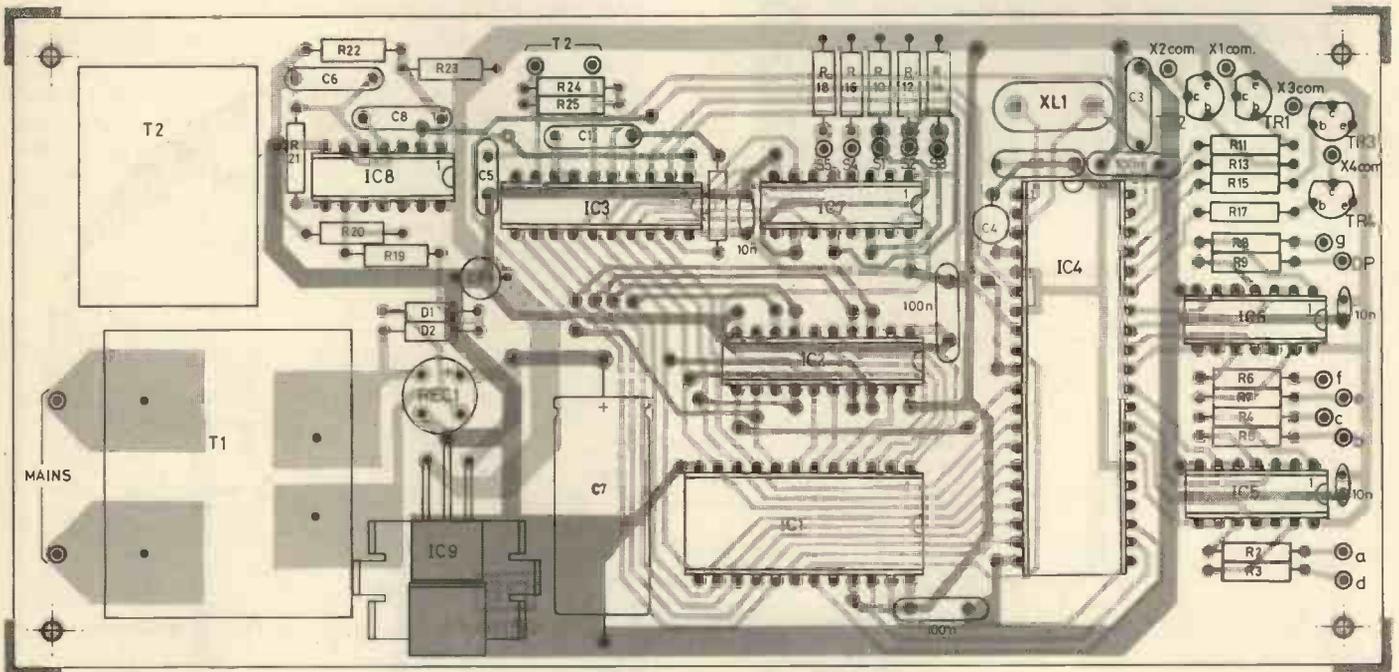


Fig. 8. Assembly details of board

The pads for the mains transformer have been made quite large to accommodate a variety of pin arrangements. The current transformer load resistors must be fitted before the ADC is plugged into the circuit. Without these resistors a high voltage may be generated which could damage or destroy the ADC. The values of R24 and R25 are found experimentally (they are supplied correct value with the kits) by using a one kilowatt load such as an electric fire. The exact current is measured with an Avo or similar and will be around 4 amps r.m.s. The voltage across the load resistors is

then given by the relationship $V(\text{r.m.s.}) = I \times 0.125 \text{ volts}$, where I is the exact current. R24 can now be selected to produce a slightly high voltage reading and R25 will be a higher value resistor to provide the final trim. (R24 may be 390 and R25 10k giving a total equivalent load of 376).

NEXT MONTH Detailed discussion of the microprocessor circuitry and software and more construction details.

All eight Beckman digital multi-meters have a very positive switch, giving no chance of pushing the wrong button.

Plus guaranteed long-term high accuracy, five ac and dc current ranges and six resistance ranges, and a battery life ten times longer than most competitive instruments (2000hr, hand held; 12000hr, bench models).




Options vary from a simple buzzer on the continuity test to the sophistication of direct temperature measurement, true RMS and even complete submersibility without damage.

Analogue multimeters were good in their day.

But today's professional demands a digital LCD display with CMOS chip technology. And that's Beckman.

Send for our multimeter family brochure and see if it's the time to make a positive switch yourself.

The switch is easy.

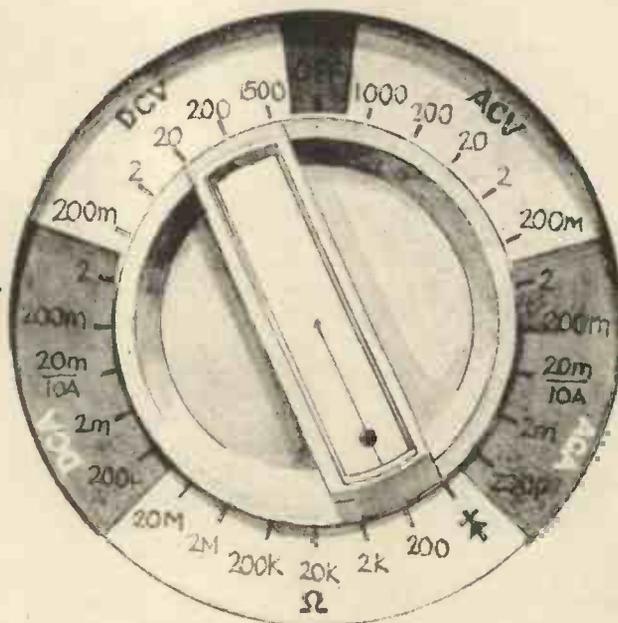

BECKMAN

Beckman Instruments Limited

Electronic Components UK Sales & Marketing Organisation
Mylen House, 11 Wagon Lane, Sheldon, Birmingham B26 3DU.

Tel: 021-742 7761 Telex: 336659.

EMERGENCY LIGHT

STEPHEN IBBS

WHERE WERE YOU WHEN THE LIGHTS LAST WENT OUT?

For around £20 and a little d.i.y. you could be *automatically* cut into the limelight with our rechargeable Emergency Lamp! Alternative? The next power cut might be your darkest hour.

IT IS likely that most householders will experience at least one power failure. This can be very inconvenient, because it is *then* that the candles and matches can't be found, *because of the dark!* However, such a failure can be more serious, as the author found when carrying a tray of crockery on the stairs at the moment of failure. The shock alone was enough to send both flying, resulting in a painful fall. The idea for this project was thus conceived during convalescence. It obviously needed to be automatic, pleasing and cheap.

The project described here is intended to enable constructors to build a ni-cad powered emergency light, drawing no battery current in its quiescent state (less than 1mA from the rectified supply), switching on automatically in the event of a mains failure. When mains is restored, the ni-cad can then be recharged, and a built-in timer lights an l.e.d. when the batteries should be charged (assuming they were fully exhausted to start with). Two switches are provided, one to act as an on/off control and as a reset switch, the other to activate the charging and timing circuits.

HOW IT WORKS

Mains voltage is reduced by the transformer, and then rectified by the diodes D4-5 (4-7). The resulting d.c. is then smoothed to a degree by C1 and flows via R1 to light l.e.d. 1. This d.c. also ensures that pins 1 and 2 of IC1a (used as an inverter) remain high, so that its output pin 3 is low, preventing the thyristor from turning on. When the mains does fail C1 rapidly discharges with R1, l.e.d. 1, R2 and R3, and pin 3 goes high, providing gate voltage to the thyristor which then fires, allowing current to flow via the three bulbs. C1 has to be relatively low in value, otherwise it would take a long time to discharge, causing a delay before the light came on. S1 now acts as a simple on/off switch. When mains is restored the lights will stay on, because once fired, gate voltage can be removed from a thyristor. However, briefly opening S1 disconnects the anode from the battery which does reset the thyristor ready for the next failure.

When S2 is closed current flows through R5, which acts as a current limiting resistor to protect the batteries. D1 prevents battery voltage from reaching pins 1 and 2, as does D2. The purpose of D2 and D3 is to provide voltage to the supply pins of the i.c.s. Because the rectified d.c. voltage is higher than the battery voltage, D3 is normally reverse-biased, so no current flows out of the battery. However, in the event of a mains failure D3 is now forward biased, maintaining supply to the i.c.s.


The closing of S2 also gates the slow oscillator constructed around IC1c and d. The frequency is adjustable to a certain extent by VR1. The output clocks IC2, a ripple counter, and after 16384 pulses pin 3 goes high, lighting l.e.d.s.

CONSTRUCTION

Assembly of the p.c.b. is straightforward. The plastic case used is the widely available Pifco "Everywhere Wall Light". It is first necessary to modify this case in the following way: The large bulb holder must be removed by drilling out its mounting rivets. Next, drill out the cord operated on/off switch. Drill two holes to accommodate the miniature toggle switches (see Fig. 1). These holes should be one above the other in the side of the case, directly opposite the "cord hole". This cord hole will be used to admit the mains cable. Two holes should also be drilled into the lens cover to take the l.e.d.s and (preferably) their bezels. Similarly, two further holes will need to be drilled through the internal diffuser to pass the l.e.d. wires (these wires should be fairly lengthy for lid removal). Hole diameters are dependent on switch and l.e.d. sizes, the former being subminiature types.

Only three nickel-cadmium cells are to be used, the mains transformers taking up one of the former battery positions. Various small transformers of the type needed are frequently seen advertised for as little as £1, therefore this component has not been rigidly specified. For this reason the rectification system has been made versatile to accommodate differing types, but the space available and the dimensions of the transformer must be taken into account. A little more spatial

Fig. 1. Circuit diagram. The PSU section may incorporate either a centre-tapped or single-winding secondary transformer. The appropriate wiring points on the p.c.b. are indicated in circles. The timer section, which drives D7 (green), indicates the necessary full-charge period for the ni-cads.

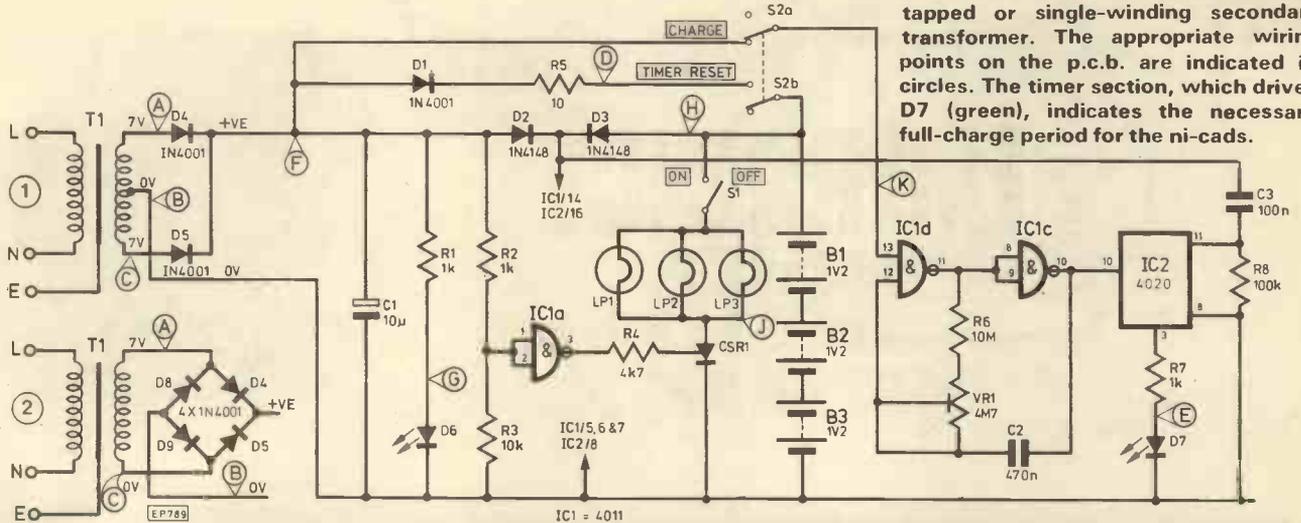

★ Components

Resistors

R1, R2, R7	1k (3 off)
R3	10K
R4	4k7
R5	10.2 watts
R6	10M
R8	100k

All resistors $\frac{1}{4}$ watt 5% unless otherwise specified

Potentiometers

VR1	4M7
-----	-----

Capacitors

C1	10µ 16V electro.
C2	470n polyester
C3	100n polyester

Semiconductors

D1	1N4001
D2, D3	1N4148 (2 off)
D4-5 (4-7)	1N4001 (2 off)
D6-7	i.e.d.s (2 off)
IC1	4011
IC2	4020
SC1	C106

Miscellaneous

3 bulb holders (cat. No. PLH2 Home Radio)
 3 torch bulbs 3V5
 3 x 4AL V2 equiv. ni-cads
 1 SPST) } miniature toggles
 1 DPST) }
 p.c.b.
 Transformer 7-0-7 Volts at 200mA
 Pifco Everywhere Wall Light, Model No. 1644

Constructors' note

The MES bulb holders are available from: Home Radio Components, 240 London Rd., Mitcham, Surrey, CR4 3HD. They may be second-sourced from: Electrovalue, 28 St. Judes Road; Englefield Green, Egham, Surrey, TW20 0HB. (Order skeleton lampholder type MSS36.)

The transformer's electrical requirements are less critical than its physical dimensions. For example, a 6-0-6V 250mA transformer will suffice so long as its measurements do not exceed 55mm wide, by 40mm high, by 35mm (the latter dimension to include any tags etc.).

If a 0-6V or 0-7V single-winding secondary transformer only, can be found, then the bridge rectifier arrangement may be used (insert D8 and D9 on p.c.b.). The Pifco lamp is available in high street shops.



Pifco Wall Light before modification, showing the lens cover and its removable diffuser/reflector.

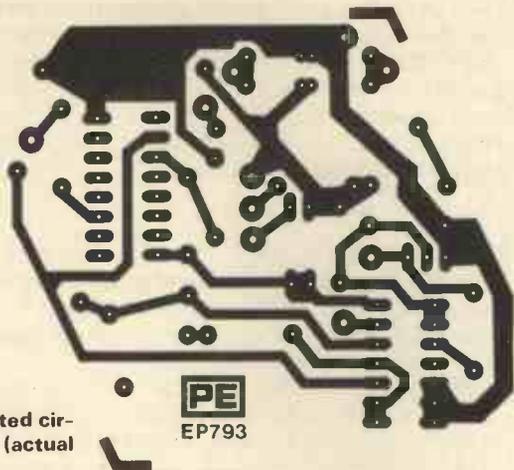


Fig. 2. Printed circuit board (actual size)

Prototype Emergency Lamp. This has been substantially rearranged mechanically, and serves as a guide only.



Skeleton MES bulb-holders which have been bent to the dimensions shown below.


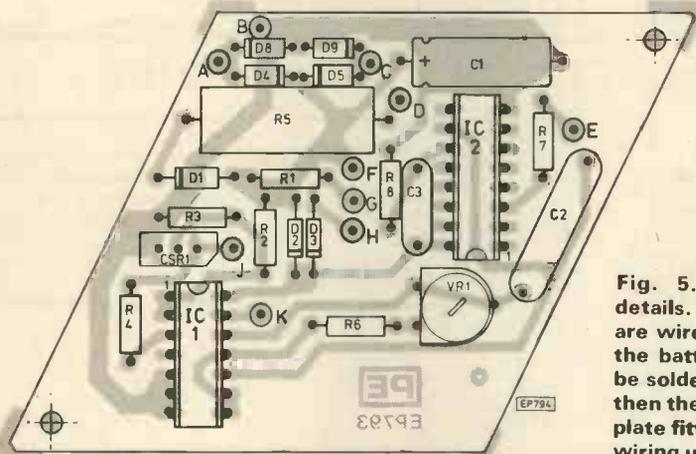
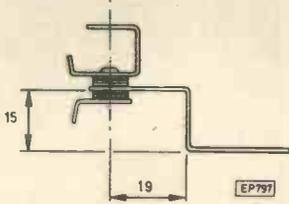
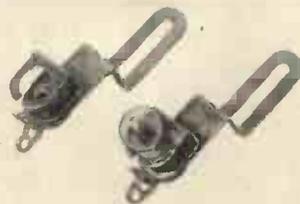
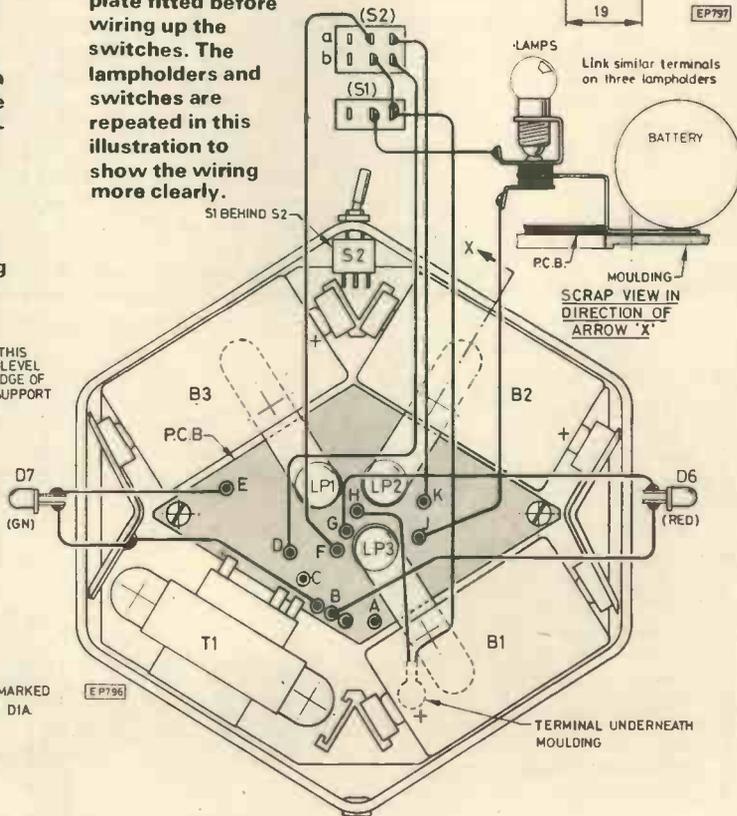


Fig. 3. Component layout for the p.c.b. If T1 has a centre-tapped secondary, leave D8 and D9 off the board. If T1 has a single-winding secondary, use terminals A and C only, and include D8 and D9.

Fig. 5. Wiring and layout details. The three MES bulbs are wired in parallel. Wires to the battery base-plate should be soldered first, then the base-plate fitted before wiring up the switches. The lampholders and switches are repeated in this illustration to show the wiring more clearly.

Fig. 4. The Pifco "Everywhere Wall Light" showing the necessary modifications to be made.

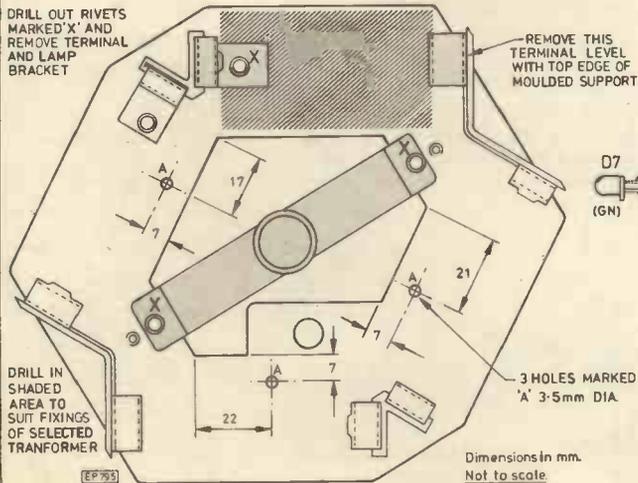

flexibility will be allowed if the two contact springs originally intended for the battery, are snipped out. Be careful how this is done. Do not remove the part which provides anchorage!

The three skeleton bulb-holders should be formed to the shape illustrated, and fixing holes drilled through the battery base-plate for mounting these. This shape has been conceived to aid the retention of the heavy nickel-cadmium cells. The round hole at the centre of the diffuser will not be large enough to clear the three MES bulbs in our new system, and therefore should be opened out using a knife or abra-file. It may be found necessary to bore some ventilation holes in the vicinity of the transformer to prevent gradual discoloration of the plastic.

When wired, the bulbs should light if S1 is closed. Switch on the mains, and the light should stay on; however, briefly opening S1 will extinguish them. Ensure that S1 is left in the closed (on) position, turn off the mains and the light should come back on.

To check that the batteries receive charge when S2 is closed, the most simple technique is to push a small piece of double sided p.c.b. in between the +ve of the battery and the

battery holder. Attach pulses from a current meter (black to the +ve battery side because charge should be flowing from the more positive rectified d.c. side into the battery) and check that charging is taking place. Also check that when the mains is on S2 is open, that no current flows out of the battery (with the lights out of course!) To set the timer for 18 hours, monitor pin 7, which should change state every 63 seconds (63-27 secs—approx!)

CONCLUSION

One of these lights at the head of the stairs is a real safety feature at home. It makes an ideal present, perhaps particularly for elderly people who may find a sudden blackout more difficult to cope with.

The only component possibly to cause problems when purchasing the parts is the case. It is manufactured by PIFCO and is called the "Everywhere Light" (model 1644) though other cases may, of course, be used. Because the batteries are not being trickle-charged, it is good practice to check the state of charge every so often. ★

FREE! READERS' ADVERTISEMENT SERVICE

PE BAZAAR

RULES

Maximum of 16 words plus address and/or phone no. Private advertisers only (trade or business ads. can be placed in our classified columns). Items related to electronics only. No computer software. PE cannot accept responsibility for the accuracy of ads. or for any transaction arising between readers as a result of a free ad. We reserve the right to refuse advertisements. Each ad. must be accompanied by a valid "date corner".

FREE READERS' ADVERTISEMENT SERVICE

We on PE believe that many readers have spare components, test gear, unused projects, etc., that could be turned into cash. Now we give you the chance to buy, sell or swap anything to do with electronics in our free ad. service.

Advertise your spare parts, test gear, tools, computers, printers, instruments, synthesisers, organs, books, etc., FREE. Yes, we will accept adverts from readers, *NOT TRADE*, on a one-off basis to be published in the first available issue. Not only can you advertise parts for sale but your wanted or swap ad. will also be acceptable. The rules are straightforward but please read them and make sure you send in a valid "date corner" cut from the issue.

If you have a few components, a Compukit or a computer organ we can help sell them for you. We reserve the right not to publish anything unacceptable to us or any ad. we believe is from a trader or anyone running a business involved in electronics; **it's a private readers only service. We cannot accept ads. for computer software.**

Please publish the following small ad. FREE in the next available issue. I am not a dealer in electronics or associated equipment.

Signature

Date

Please read the **RULES** then write your advertisement here— one word to each box. Then add your name, address and/or phone no. Maximum of 16 words plus address.

COUPON VALID FOR POSTING BEFORE 12 MARCH, 1982. (One month later for overseas readers.)


SEND TO: PE BAZAAR, PRACTICAL ELECTRONICS, WESTOVER HOUSE, WEST QUAY ROAD, POOLE, DORSET BH15 1JG.

BLOCK CAPITALS PLEASE

Name & Address:			

For readers who don't want to damage the issue send a photostat or copy of the coupon (filled in of course) with a cut-out valid "date corner".

FREE TRANSISTOR PROJECTS...

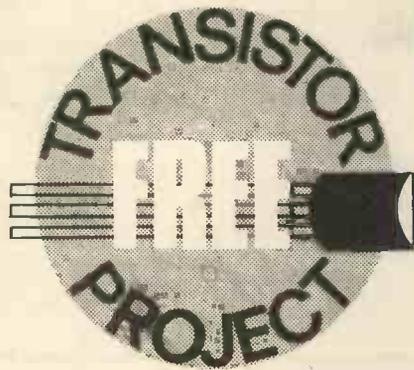

AUTOLIGHT

The 'in' thing for absent residents

HERE is a light that will deter a burglar in your absence as it automatically switches on at dusk and off at dawn. As such, it is ideally suited as a porch light, giving the impression that the premises are occupied.

Whilst the supply requirements are low, the period when the unit is in operation is long, so the use of the mains voltage was considered imperative and anyway, if the light was not powered from the mains it would probably give the game away.

CIRCUIT

In Fig. 1, a mains transformer T1 is used to step down the 240V supply to the operating potential. The secondary winding supplies the rectifier pair D1/D2 to provide rough d.c. which is further smoothed by the electrolytic capacitor C1.

TR1 is used as a switching transistor having the relay coil as its load. The diode strapping this is to suppress the transient high reverse voltage which would normally develop when the relay is switched off. Its action is to simply short circuit the high voltage spike, which could damage the transistor, reducing it to a value of about half a volt.

Bias is provided to the switching transistor by a resistive chain which includes a cadmium sulphide light dependent resistor, the resistance of which reduces as the light falling

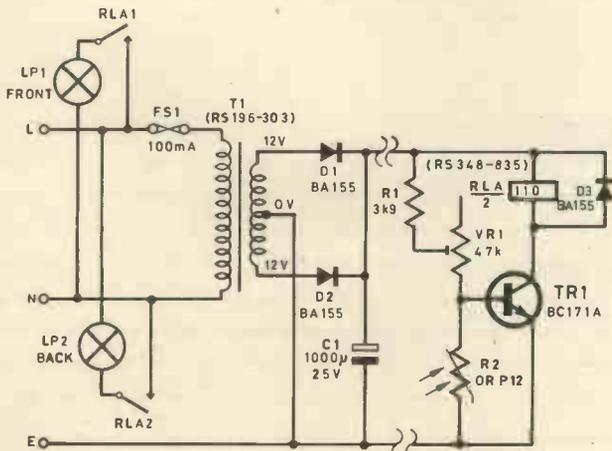


Fig. 1. Circuit of Autolight


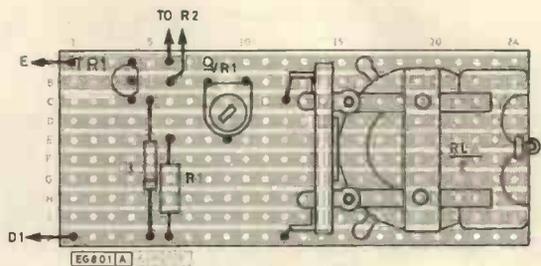


Fig. 2. Veroboard layout


on the device increases. Typically, for an ORP12 this resistance ranges from 10M in total darkness to less than 100 ohms in bright conditions, and around a few kilohms for a cloudy day.

COMPONENTS

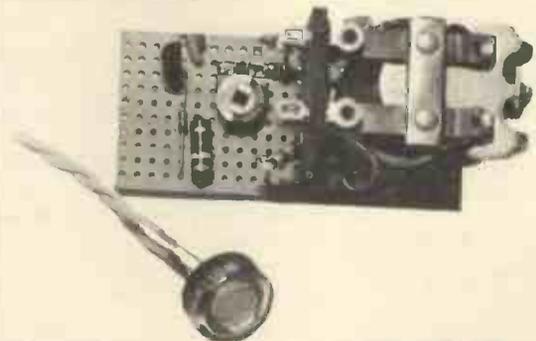

Resistors		Variable Resistor	
R1	3k9	VR1	47k
Capacitors		Light Dependent Resistor	
C1	1000µ 25V	R2	ORP 12
Semiconductors		Transformer	
D1-D3	BA155	T1	12-0-12V (RS 196-303)
TR1	BC171A	Relay	
Transformer		RLA	110
Relay		Fuse	
RLA	110	FS1	100mA
Lamps			
LP1-LP2			

LIQUID ALARM

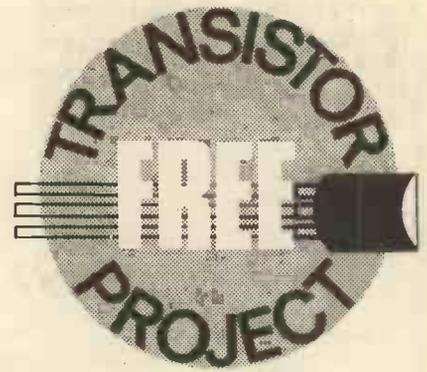

A sensor that sounds for liquid or vapour

ONE of the simplest and most versatile of direct coupled circuits is the super-alpha or Darlington pair. Super alpha derives from the gain multiplication produced by connecting transistors this way, so that the composite pair shown in Fig. 1 have a very high current amplification which for the transistors being used approximates to 125^2 .

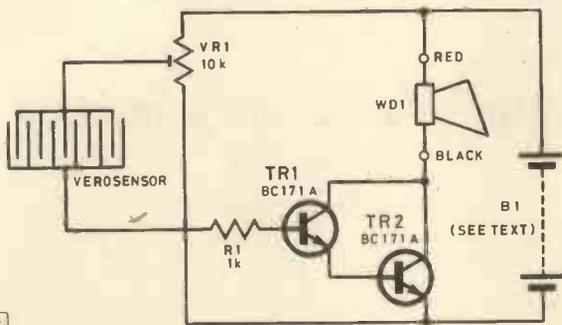


Fig. 1. Circuit of Alarm

VEROSWITCH

A piece of 0.1in matrix Veroboard with the alternate track layers commoned (Fig. 1) makes an ideal sensor as liquid or vapour bridging these will form a base input to TR1.

In the initial setting up, the sensitivity of the device is set by VR1. If steam is applied to the parallel copper strips of the sensor, VR1 is rotated until the alarm sounds. At this point the adjustment is for maximum sensitivity.

In its appointed role as a laundry protector, obviously the housewife will only be concerned with rain that has started falling so that she can make the quick rescue, so a high sensitivity adjustment should be made.

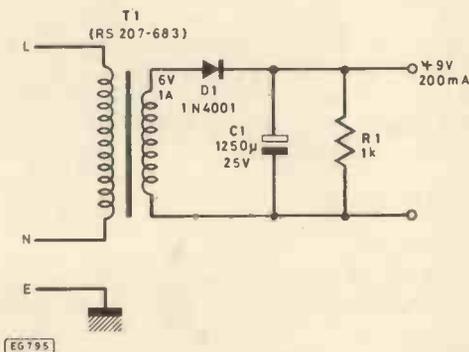


Fig. 2. A mains supply that can be used

LIQUID LEVEL

If a liquid level switch is intended, where two stiff conductive probes are substituted for the Veroboard, then the simple expedient is to use lengths of 16 s.w.g. tinned copper wire for the probes, these being terminated with the input connections to the device.

The retainer for these stiff wires could be a five-way terminal so that adjustment for probe separation, and therefore liquid level, would reduce to loosening the screws of the block and moving the wires relatively as required.

To complete the assembly, the two outer connectors of the block could retain a suspension hook of wire.

Obviously the probes could be manually adjusted for any liquid level rise or simply left with the tips adjacent to detect a level.

ALARM

The choice of supply was deliberately kept low for battery conservation, as the current consumption of the alarm rises almost linearly with the voltage applied. For the circuit shown and the alarm arranged for pulsed tone operation (3.2kHz approximately pulsed at 5Hz), the current is an intermittent 10ma. Nevertheless, sound output is strident and will almost certainly be heard anywhere around the house. However, if you do need a bigger output then you can simply raise the supply voltage to 9V. There are no circuit changes to be made, but remember, whilst the db output level rises so does the current consumption.

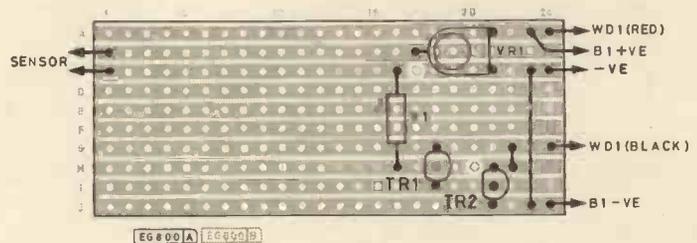


Fig. 3. Veroboard layout

OUTPUT ALTERNATIVES

With the alarm specified the output alternatives are continuous or pulsed tone depending on whether the yellow sense lead is connected. The instruction for this is to leave it unconnected for pulsed operation or to connect to battery negative for a continuous tone. The remaining two leads (red and black) are connected as shown in the circuit.

With its obvious long-term utility there is a need to substitute a simple mains supply for batteries and a suitable 9V circuit is given in Fig. 2.

COMPONENTS

Resistors

R1 1k
10% 1/4 watt carbon

Potentiometer

VR1 10k preset

Transistors

TR1-TR2 BC171A (2 off)

Warning Device


WD1—Surface mounting audible alarm (RS 248-788)

Battery

B1—see text




DOUBLE SIREN

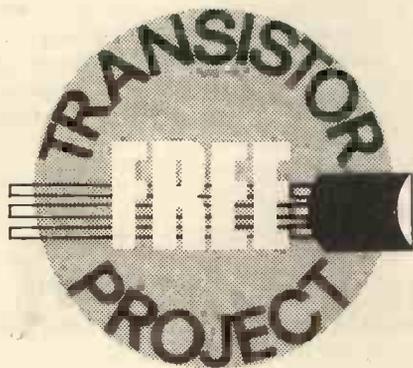

Alarm options with one transistor

THIS project makes use of only one of the free transistors but offers two siren options: an American police siren with the characteristic short rise and longer fall and alternatively the urgent rising bursts of sound reminiscent of the alarm status signals of the starship Enterprise. It should be noted that although the component count is small the sound output is large.

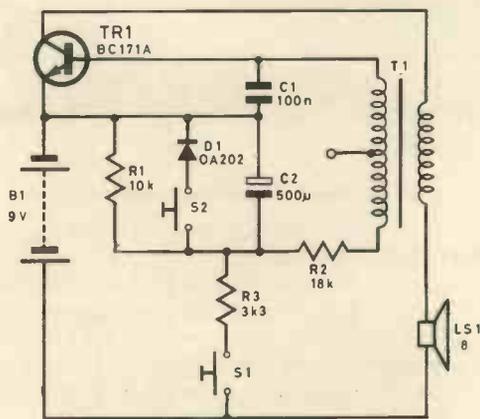

EG791

Fig. 1. Circuit of Siren

BLOCKING OSCILLATOR

Both these sounds are initiated by S1 and S2 respectively, but for the starship alarm S1 must be kept closed while pressing S2. Power consumption is relatively low—about 24mA—but if batteries are heavy on the pocket then there is the simple expedient of knocking up the simple 9V power supply given previously in this supplement.

This circuit has the rather formidable description of a blocking oscillator. Here, the transformer provides regenerative feedback by phase inversion from the collector to the base of TR1; so remember, if your unit does not work just reverse the connections to the primary or secondary of T1.

When S1 is pressed the tone produced through components C1, T1, R1 and R2 is raised by the charging of C2 through R3. When S1 is released the charge in the electrolytic capacitor leaks away so that the tone gradually falls. By introducing the diode with the switch S2, C2 is very rapidly discharged so that with operation of this switch you only have a series of rising tones.

OUTPUT

In introducing this project it was stated that the sound output is large. This statement is true if a large speaker is used, anyway, you can have fun experimenting. I used a 4in type and found the output adequate.

Since sound expansion has been touched upon there

COMPONENTS

Resistors

R1	10k
R2	18k
R3	3.3k
All $\frac{1}{4}$ W 10% carbon	

Capacitors


C1	100n
C2	500 μ 25V elect

Switches

S1-S2	Press switches
-------	----------------

Transformer

T1	T/T7 output (RS)
----	------------------

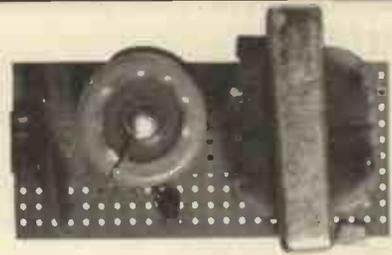

Transistor

TR1	BC171A
-----	--------

Loudspeaker

LS1	4in 8 Ω
-----	----------------

Battery

B1-9V	
-------	--


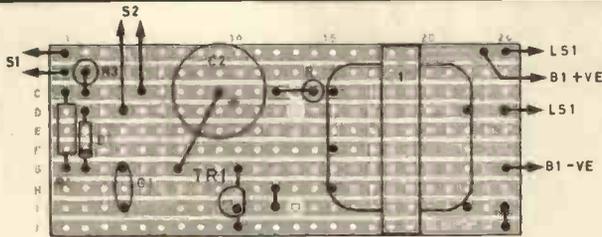


Fig. 2. Board assembly

could possibly be a requirement for changing the decay period or frequency. Although I have endeavoured to simulate the sounds set out in the introduction, I certainly am not gifted with perfect pitch so there might be some among you who require a little more accuracy in the reproduction, then the guidelines for sound tailoring are that increasing R1 will increase the siren's fall period and increasing C2 will lower the frequency and, of course, vice versa.

AF/RF GENERATOR

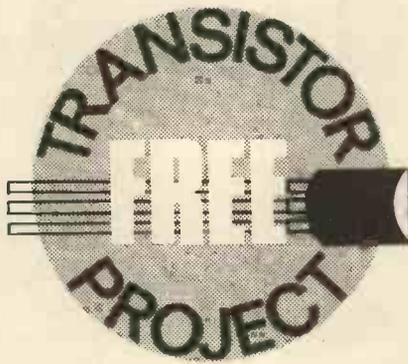

Broad band signal source

THIS little generator makes no pretensions towards a high specification, but with it you could quite easily trouble-shoot a radio covering the medium and long wavebands, which includes the r.f. and a.f. components, or any audio entertainment equipment.


FREE RUNNING

The circuit shown in Fig. 1 is a free running square wave generator which produces a basic tone of frequency $1/(1.4CR)$ cycles where C is the single coupling capacitance (farads) and R the base bias resistance (ohms), which works out to 1kHz.

To reduce signal output the simple expedient of starving the circuit is used via VR1.

ACTION

When power is first applied to the circuit from the battery, since there is no means of maintaining a permanent voltage at the base of either transistor the circuit has no stable state. The unbalance between each half of the circuit induces one transistor towards current cut-off and the other towards full conduction. However, there is no d.c. stable state and the current alternates between the two quasi-stable states at the previously mentioned rate fixed by the 200k/5n pairs. As the value of these are equal the output forms a symmetrical square wave.

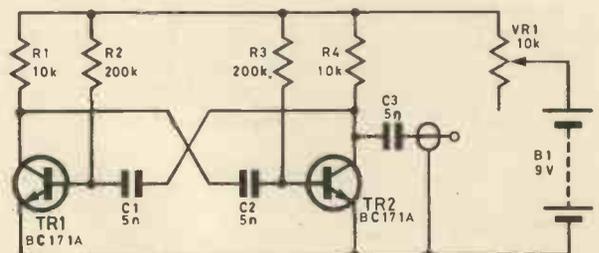

EG790

Fig. 1. Circuit of Generator

HARMONICS

The harmonics produced to cover the r.f. bands mentioned are the normal components of a square wave. How far they extend upward being set by the characteristic of the wavefront. The shorter the time of the rise the higher the harmonics extend upwards.

OUTPUT

Since the transistors are switched hard on the output voltage is that of the supply. To vary this output it is convenient to vary the supply with the potentiometer VR1, since the current drawn from the battery is extremely low. In fact, the generator will work with nothing more than a meagre 0.5V.

The output coupling capacitor C3 has a working voltage which has been chosen deliberately high for any valve circuit applications. Make sure the signal lead from this is coax suitably terminated with crocodile clips.

USING IT

Assuming you have no test equipment, when applying the

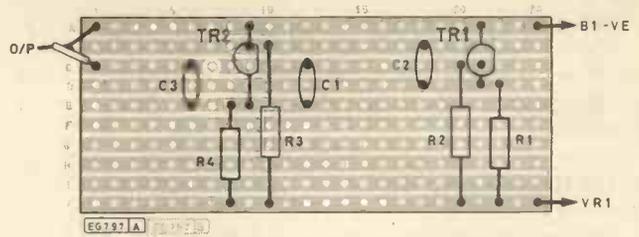


Fig. 2. Showing board assembly

generator to entertainment equipment fitted with its own loudspeaker the rule is always to work back from the output stage to the input. The evidence of stage and then component failure in proceeding in this logical manner is loss of signal.

With, say, a radio, this should be tuned off a station with the volume turned up. You should then work back through the a.f., i.f., and r.f. stages to locate the faulty component. A good set will produce a loud tone if the generator output is brought close to the ferrite aerial.

COMPONENTS

Resistors

R1	10k
R2	200k
R3	200k
R4	10k
·All $\frac{1}{4}$ W 10% carbon	


Capacitors

C1-C2	5n
C3	5n


Transistors

TR1-TR2

BC171A (2 off)

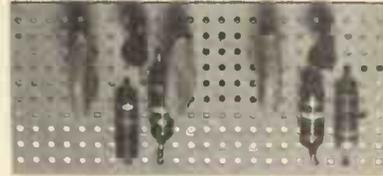

BENT WIRE GAME

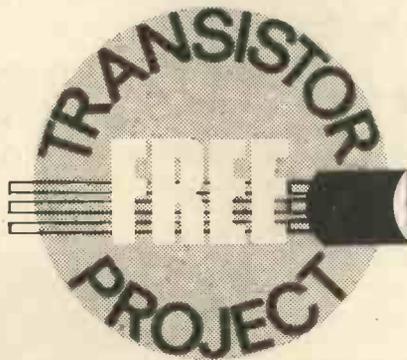

Touch tournament with a memory

HERE is a constructional variation of the old 'steady hand' game where a loop of wire has to be run along another piece of wire bent into an irregular pattern. The object of the game is to run the loop from one end of the shaped wire to the other without making contact between them. If this is done, then the loop is returned to the start and the next competitor makes his move.

Since any number of people can compete and presumably complete the course, the winner must be the one who does it in the shortest time.

MORE DIFFICULT

The difficulty of the game can be improved upon by any

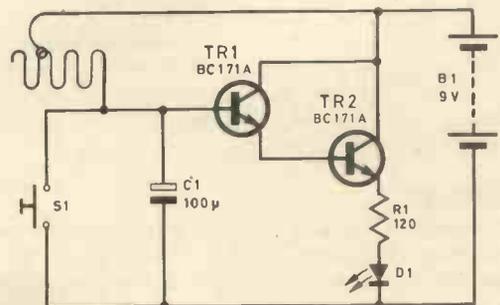


Fig. 1. Circuit of Game

one of the following changes, which are a) making the curves of the wire length more irregular, b) lengthening the run, and c) decreasing the diameter of the loop. These are all variations which can be tailored to suit the age and skill of the competitors and which cost very little in time or money to arrange.

HOW IT WORKS

The circuit shown in Fig. 1 is that of a compound emitter follower which has a characteristically high input impedance seen from the base of TR1 and the cathode of D1.

If, say, there was a short between the competitor's loop and the shaped wire the light emitting diode would switch on and in the absence of the electrolytic capacitor C1 this would switch off as soon as contact was broken.

You can imagine, then, the argument that would ensue if the offending party refused to own up to the instantaneous flicker, so C1 was introduced to remove any conflict.

In practice, the l.e.d. will remain lit for periods in excess of five minutes for the slightest touch so it does arbitrate conclusively. The switch S1 discharges C1 in preparation for a new game.

CONSUMPTION

The unit consumes no current in the stand-by condition and 40mA when switched on. This is, in fact, the maximum forward current of the l.e.d. specified and if a battery is to be used some might like to conserve power with a reduction of light emission.

To do this, resistors from the one specified up to a value of 1k can be used. The 1k limit provides a visible lamp but considerably reduces the consumption to about 5mA.

POWER SUPPLY

Once again we can solve the problem of battery cost by building the p.s.u. shown in the Liquid Alarm project.

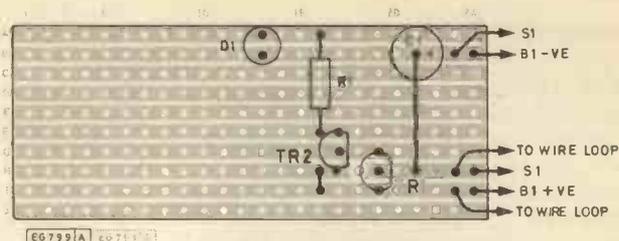


Fig. 2. Board assembly

COMPONENTS



Resistor

R1 120
All $\frac{1}{4}$ W 10% carbon

Capacitor

C1 100 μ 15V

Transistors

TR1-TR2 BC171A


Diode

D1 0.2in green l.e.d.
(RS 586-481)

Battery

B1-9V

CAR BATTERY CONDITION INDICATOR

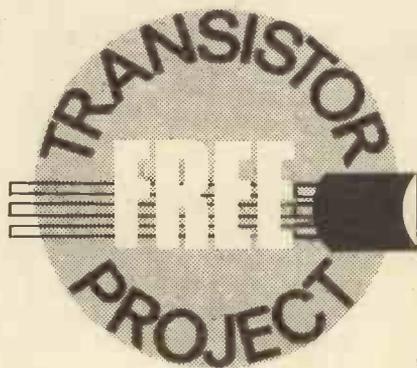

Lights the way to happy motoring

Just over a generation ago the voltmeter and ammeter were standard equipment for the motorist so that he was constantly aware of what was happening to the battery, dynamo and regulator when the vehicle was started or running.

Today's economies reduces all electrical awareness of a satisfactory circuit to the standard ignition warning light, which, apart from a perfunctory introductory glow, tells you nothing about the battery state of charge.

FULL INDICATION

This three l.e.d. alternative will continuously monitor the general state of the battery from 'poor' (red l.e.d. lights), when suspicion should be cast on the battery voltage regulator or dynamo or combination of these. For this condition the battery voltage is below 11.6V.

MOST car manufacturers pay scant attention to dashboard indicators in the charging department. A red light that comes on and goes off when you start the journey leaves you electrically ignorant in its absence until something like a broken fan belt occurs.

A battery terminal voltage above this would light D4, the yellow l.e.d. This condition warrants an investigation if it does not charge up after a few minutes and is marked 'fair' on the circuit.

Indication of a satisfactory circuit with a battery voltage of above 12.6V is given by the green l.e.d. lighting. This is labelled 'good' in Fig. 1.

There are transitional states between these as when the yellow lamp reduces in brilliance and transfers to a brightening green lamp, as a battery is charging, and vice-versa as it is discharging.

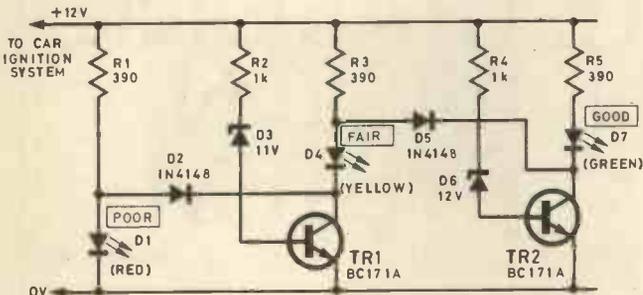


Fig. 1. Circuit of Indicator

IN GENERAL

Broadly, the green light on indicates all is well; red, the battery is defunct and yellow the output voltage is low which will be confirmed by poor light from the lamps, low hydrometer reading and lack of power to the starter motor when the battery is switched in.

This condition may be due to the dynamo not charging or giving a low or intermittent output in which case D4 will flicker.

POSSIBLE REMEDY

To remedy this latter condition the charging and field circuit wiring should be examined. Tighten any loose connections, particularly those at the battery, also renew any damaged cables. Check the tension of the dynamo driving belt also the regulator setting and adjust if necessary.

MOUNTING

The small board can be mounted directly on the car dashboard using the black panel clips supplied with each l.e.d. These suit a 6.35mm (0.25in) panel and will retain the circuit board when fitted.

A layout with equally spaced light emitting diodes is shown in Fig. 2. The viewing angle for the specified l.e.d.s is 30° which might produce a relatively low light output in bright conditions, so I am proposing an alternative device, the 'stackable l.e.d.' from RS Components, which has a viewing angle of 100° and provides a clear colour contrast when viewed at even oblique angles.


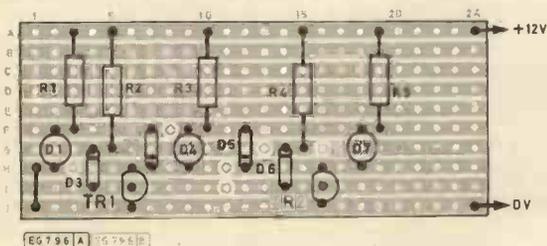


Fig. 2. Veroboard layout

COMPONENTS

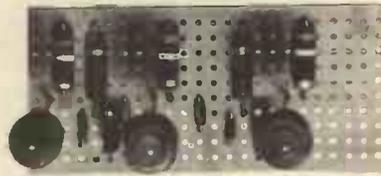

Resistors

R1	390
R2	1k
R3	390
R4	1k
R5	390
All ½W 10% carbon	

Semiconductors

D1	Red 0.2in l.e.d. (RS 586-475)
D4	Yellow 0.2in l.e.d. (RS 586-497)
D7	Green 0.2in l.e.d. (RS 586-481)
D2, D5	IN4148 (2 off)
D3	11V 500mW Zener
D6	12V 500mW Zener
TR1, TR2	BC171A (2 off)

ANOTHER ADVANTAGE

An additional advantage of this indicator is that being 'in circuit' continuously means that the battery condition can be tested as different loads are applied such as operation of car lights, starter motor, accessory items, etc. This way one can readily keep an eye on a deteriorating battery and know the time for replacement rather than be caught unawares.

CIRCUIT ACTION

In the circuit, at voltages below 11.6V, the brightness of the l.e.d. D1 is set by R1. As 11.6V is approached then D4 starts to light as TR1 conducts, the latter subtracting current from D1 causing it to extinguish.

This same procedure is repeated as the line voltage moves up to 12.6V when D7 will be lit. So you can see that there is always a continuous visual indication of battery state, and in living with it you should become extremely adept at interpreting impending problems.

CHECKING IT

When checking over the completed unit a variable power supply is useful to make sure the unit is switching through its ranges.

If dry batteries are used for this purpose it should be borne in mind that for a 'good' indication the total current drawn is around 80mA, which is largely made up of shunt current through D5.

The l.e.d.s chosen for this project are for panel mounting and could be attached to the car dashboard but first you should view these in daylight when the unit is powered up (take the 12V line from the ignition switch) for optimum positioning as brightest viewing is directly over the lens.


From
HAMEG...

HM307



£138
UK LIST
EX VAT

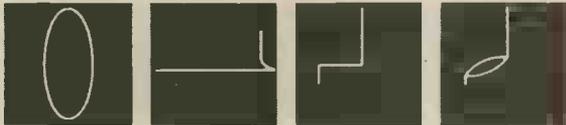The first portable scope with a component tester.



Capacitor 33uF Transistor E-C Transistor B-E B-E 1uF + 68ohms

Oscilloscope Specifications:

Y Deflection

Bandwidth: DC - 10 MHz (-3dB)
Overshoot: Less than 1%
Sensitivity: 5 mV - 20 V/cm
Input Imp: 1 M ohm // 25pf

X Deflection

Timebase: 0.2s - 0.2µs/cm
Triggering: 2 Hz - 30 MHz (3mm)
Auto + level control
Bandwidth: 2Hz - 1 MHz

General Information

Component Tester:	For single components and in circuit
Calibrator:	0.2V ± 1% for probe alignment
Power Supplies:	Regulated including high voltage
A.C. Input:	110, 127, 220, 237, V.A.C., 50 - 60 Hz
Weight:	8-¼ Lbs.
Size:	4-½"H x 8-3/8"W x 10-7/16"D

For further information on HAMEG's full range of top performance oscilloscopes, contact:

HAMEG LTD.
74-78 Collingdon Street, Luton, Beds. LU1 1RX
Tel: (0582) 413174

NEXT MONTH

ULTRASONIC VISION SYSTEM

This project is an advanced ultrasonic vision system which is within the means of the amateur constructor, yet is sophisticated enough to enable experimentation with computer measurement, image recognition, object tracking, and robot vision.

STEREO CASSETTE DECK

The PE Quasar stereo cassette deck is a versatile low cost system designed around a single p.c.b. which features a variable bias control for optimum recording of all tapes, a gate noise reduction system, twin VU meters and electronic switching.


PLUS...
6 More Projects to build with your FREE Transistors

PRACTICAL
ELECTRONICS

APRIL ISSUE ON SALE FRIDAY, MARCH 12th

IR REMOTE CONTROL

Part 2 — Bart Trepak

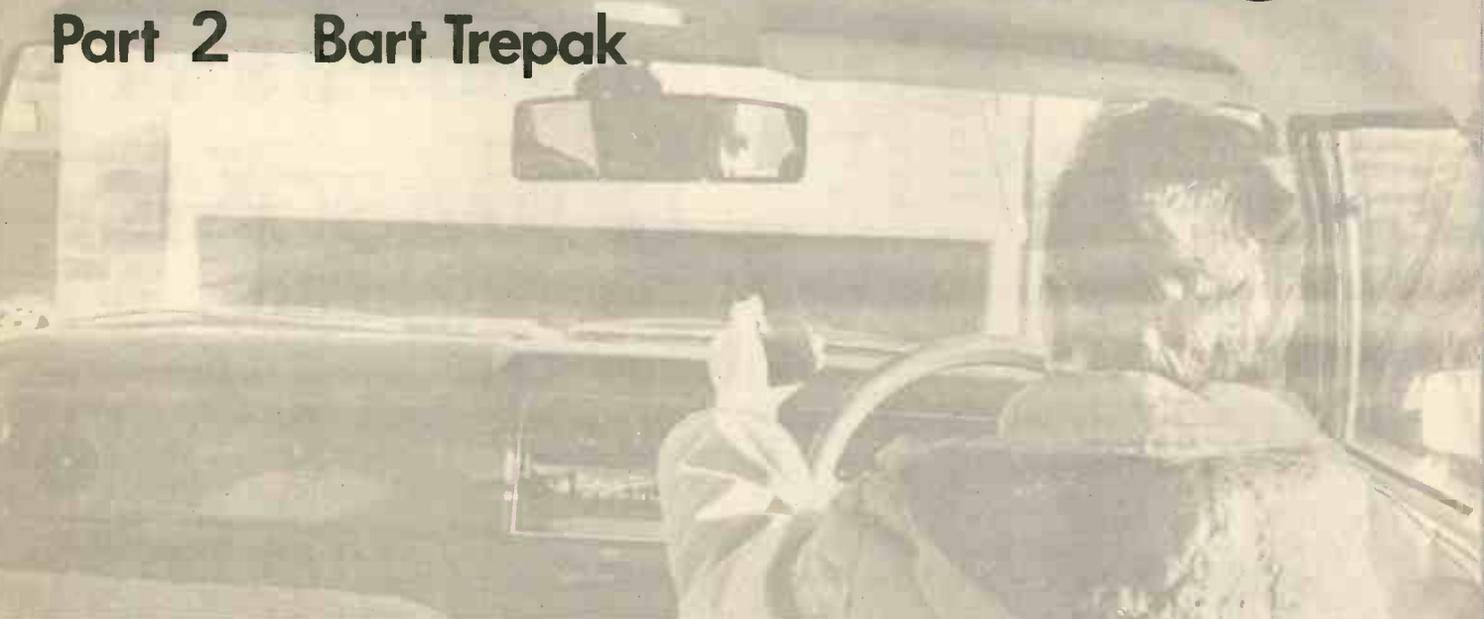


THE transmitter circuit is built on a small printed circuit board as shown in Figs. 1 and 2 which holds all the components except the l.e.d.s and the push switches. Care should be taken to ensure that transistors and electrolytic capacitors are mounted the correct way around. Although the i.c. is a bipolar device and, therefore, not prone to static damage, it is wise to mount this in a socket. If only one switch is to be used, a panel mounted push to make type may be fitted directly on to the box and connected to the appropriate pads on the transmitter board by wires. If more than one switch is required, these should be mounted on the switch board (Fig. 3), which is designed to fit "piggy back" style on the transmitter board using four stiff wires (pins). Care should be taken to ensure that the switches are positioned as shown in Fig. 4 and firmly seated on the p.c.b. before soldering.

The complete circuit may be housed in a small box together with the battery. The l.e.d.s should be mounted on the front of the box using l.e.d. clips or the reflectors if a greater range is required. If the box specified is used then these would be mounted on the aluminium front panel and soldered to the p.c.b. using flexible wires. The wires to the l.e.d.s should be kept as short as possible as relatively large

currents will flow in these leads and any inductance will have a detrimental effect on the range. Since there are no heavy components on the p.c.b., the transmitter circuit may be secured to the box with a double-sided adhesive pad. The distance between the main p.c.b. and the keyboard will have to be carefully chosen to ensure that the switches are free to move when the box is clipped together. If the assembly is made too high, one or more of the switches may be depressed permanently, which would, of course, result in the transmitter operating continuously. When the correct height has been ascertained, the connections between the two p.c.b.s may be made using tinned copper wire or discarded component leads. The two p.c.b.s have been designed so that the holes for the interconnections line up when the two assemblies are mated. Only the connections for which holes are provided should be made, the spare holes on the main p.c.b. (which are for use with other keyboards) should be ignored.

The battery clips should be assembled in the box battery compartment and connected to the p.c.b. pads marked + and - with wires. If there is any danger of incorrect battery connection, it is wise to place a diode (type 1N4001) in the positive lead to avoid damage. The circuit is powered by a 9V PP3 battery and draws an average current of 20mA when operating. Since the standby current consumption is only a few micro-amps, no on/off switch is required. A piece of polystyrene or similar material may be required to hold the battery in place within the battery compartment.

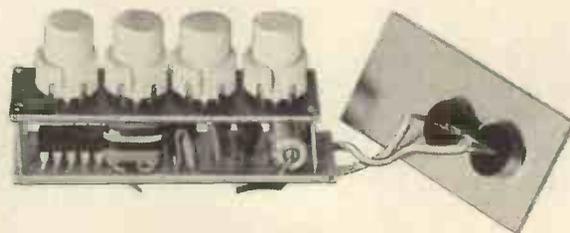

Switch assembly

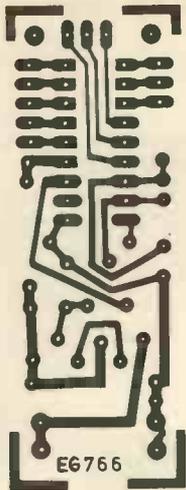


Fig. 1. P.c.b. design for the transmitter

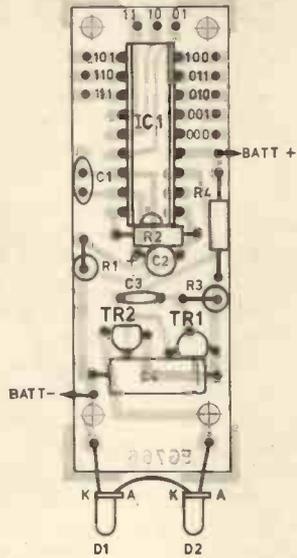


Fig. 2. Component layout

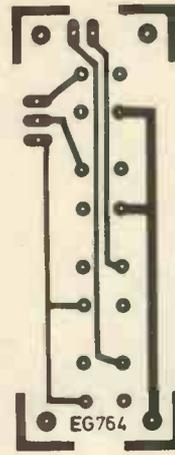


Fig. 3. Switch p.c.b.

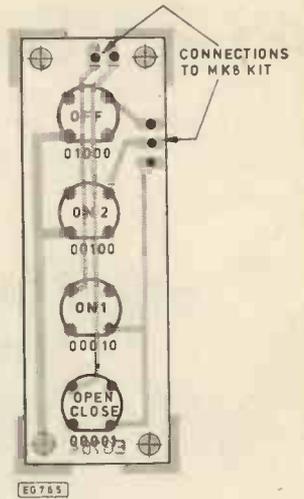


Fig. 4. Switch layout

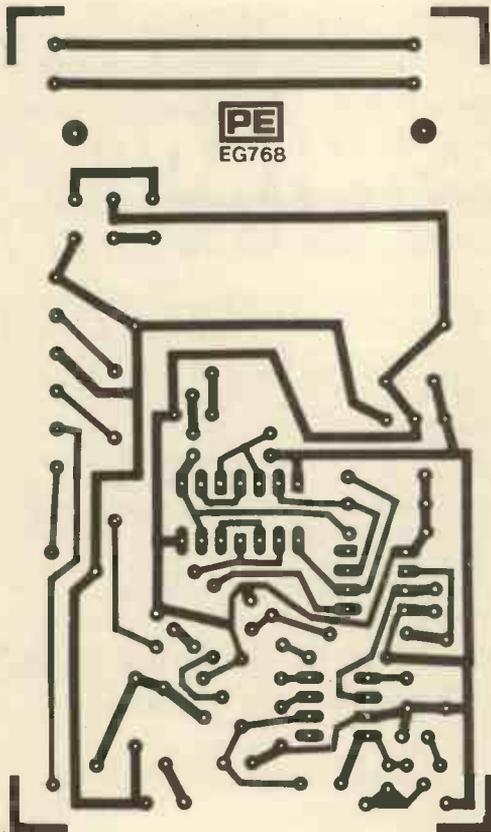


Fig. 5. P.c.b. design for the Receiver board


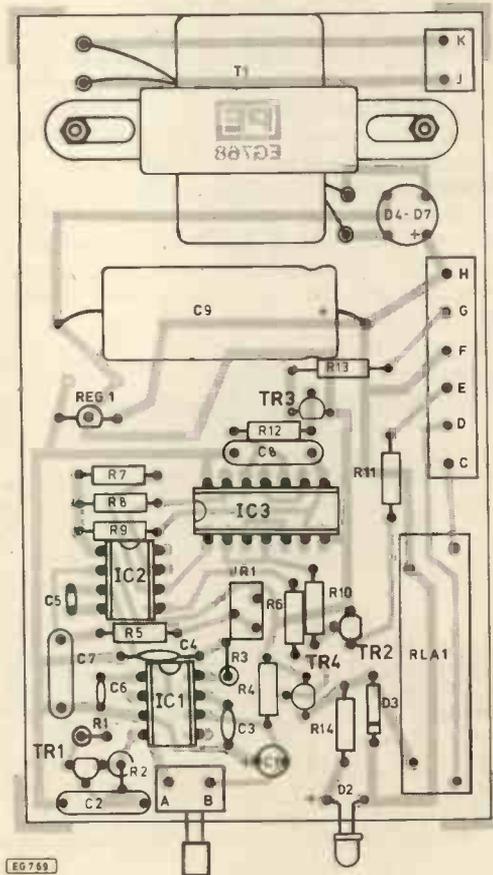


Fig. 6. Component layout

The receiver is built on one printed circuit board as shown in Figs. 5 and 6 with all the components, including the transformer, mounted on it. (Construction on Veroboard or other p.c. layouts is not recommended as the high gain amplifier IC1 may become unstable.) Only D1 and the opto isolator and triac are mounted remotely. D1 may be connected to the p.c.b. with wires although the length of these should be kept as short as possible to avoid noise pickup. A screened lead is best although the length should be kept to less than 6 inches as any capacitance across the photodiode will reduce the sensitivity of the circuit to the transmitted IR pulses. As the photodiode will need to be mounted externally, some form of protection from the weather will be needed.

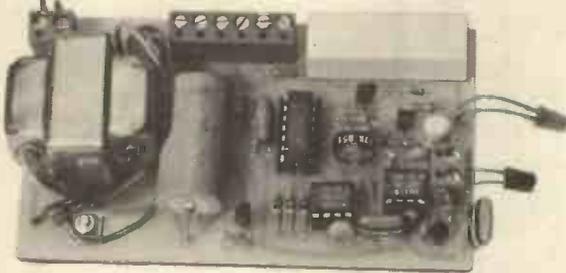

The sensitive face of the diode is the curved one and this should be arranged to face in the direction from which the IR radiation is expected. Any transparent or translucent enclosure of the type supplied for panel mounted neons would be suitable provided the diode is mounted against the front of the moulding to avoid making the unit too directional. If the unit is to be used in a room to control lamps or appliances, the photodiode mounting will not be so critical as multiple reflections occur from walls and ceilings making the controller largely non-directional.

The unit may be tested by connecting the mains to terminals J and K and transmitting the open/close code. VR1 should be adjusted until l.e.d. D2 lights and remains lit while the transmitter button is pressed. The other codes may be tested by connecting l.e.d.s directly to terminals E F and G H, with the l.e.d. cathodes connected to E and G. Transmitting ON 1 and ON 2 will switch each l.e.d. on while pressing OFF will cause both l.e.d.s to switch off.

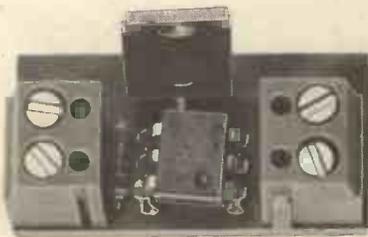


Fig. 7. P.c.b. mains switch

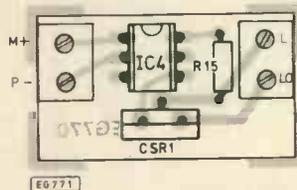


Fig. 8. Component layout

The layout of the mains switch is shown in Figs. 7 and 8. The triac CSR1 specified is an 8 Amp device which can control up to 2kW at 240V a.c., although a suitable heatsink will be required to keep the triac case temperature to below 70°C. Without a heatsink, a load of up to 1.5A (300W) may

be switched. If higher power loads are to be controlled a TIC236D (12A r.m.s.), TIC246D (16A r.m.s.) or TIC263D (25A r.m.s.) may be fitted without any circuit modifications. Note that the load must be connected in series with terminal Lo. Since the input is an l.e.d., the correct polarity must be observed with terminal M connected to the positive line, i.e. F or H.

APPLICATIONS

The obvious application for the unit and indeed the purpose of the design is in the control of motorised garage doors. In this context the momentary output would be used to trigger the open or close sequence while the two latched outputs could control mains lamps (via the slave switches) to illuminate the drive and garage if required.

The circuit could of course be used for a multitude of other functions around the house. As mentioned, the ON/OFF outputs could be used to switch virtually any appliance on or off such as radios, tape recorders, lamps, etc. The momentary output controlled by the open/close button could be used to change the channel on a suitably modified TV receiver. An interesting application would be to control room lighting. Many modern touch controlled lamp dimmers incorporate an input for connecting to slave touch plates. These normally require a momentary low current connection to the live terminal to effect switching or dimming of the light.

For the elderly or disabled, the unit could be used to control heating or lighting. Since the connections to the power switch of Fig. 4, shown last month, need only to be low voltage/low current wires, it would be easy to arrange for the controller to be situated in one room and control an appliance in another location, enabling, for example, the central heating or an electric blanket to be switched on or off without the necessity of leaving the living room. ★

EASIBINDERS

Quick, neat and easy!

It's so easy and tidy with the Easibind binder to file your copies away. Each binder is designed to hold 12 issues and is attractively bound and blocked with the PRACTICAL ELECTRONICS logo. Price U.K. £4.60 including postage, packing and V.A.T. Overseas orders add 25p.

Please allow 3/4 weeks for fulfilment of order. Why not place your order now? Send the completed coupon below with remittance payable to:—I.P.C. Magazines Ltd., Post Sales Dept., Lavington House, 25 Lavington Street, London SE1 0PF.

Order Form PRACTICAL ELECTRONICS

I enclose P.O./cheque value for binders.

Years required

BLOCK LETTERS PLEASE

Name

Address

Date

eb


hi! reliability hi! service hi! performance hi! competitive hi!

Low cost excellence

with a 2 YEAR guarantee


hi! reliability hi! service hi! performance hi! competitive hi! reliability hi! service hi!

reliability hi! service hi! performance hi! competitive hi! reliability hi! service

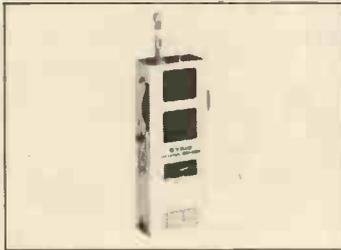


**DM 801
DIP METER**
£55

DM 801 DIP Meter — 700 KHz to 250 MHz in 7 bands — Inductive and Capacitive coupling with an 'RF Searcher' — high sensitivity — absorption Frequency Meter — Xtal tester — Marker generator — CW and AM monitor.
FC 754A Digital Frequency Counter — 6 digit — 10 Hz to 250 MHz
FC 756 — 10 Hz to 500 MHz.
DF 760 — Combined 7 digit Frequency Counter and 3½ digit DMM.

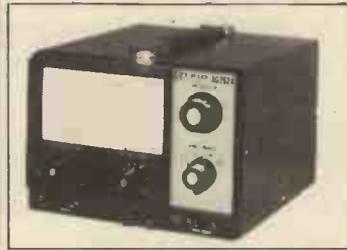


**AG 202A
SINE-SQUARE
OSCILLATOR**
£68

AG202A 200KHz R.C. Oscillator — 20Hz to 200KHz in 4 ranges — Sine and Squarewave — Flat O/P to 10V r.m.s. from 600 ohms — < 0.5% distortion — > 60dB of variable O/P atten — Ext. Sync. — Large easy to read single dial with smooth precise tuning control —
AG203 Low Distortion Oscillator — < 0.1% distortion — 10Hz to 1MHz in 5 ranges.

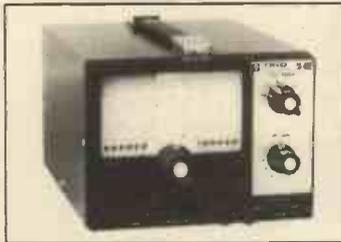


**SG 402
30 MHz A.M.
SIG. GEN.**
£59

SG402 A.M. Signal Generator — 100KHz to 30MHz in 6 bands — 100mV of O/P with variable attenuator — Int. and Ex. A.M. — Solid State — Lightweight and portable — Large clear easy to read frequency dial.

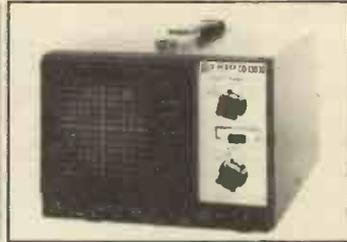

**CO 1303D
5 MHz
OSCILLOSCOPE**
£108

CO1303D, DC to 5MHz Oscilloscope — 10mV/div sensitivity with variable atten. — Int. variable sweep frequency in 4 ranges from 10Hz to 100KHz — Int. and Ext. sync. — Direct deflection terminals can monitor R.F. up to 450MHz. CO1303G as above, plus 1:8 to 54MHz monitor freq. range from 1 to 500W direct coupling — Two Tone gen. 1KHz and 1.575KHz — ideal for SSB, A.M. C.W. etc.

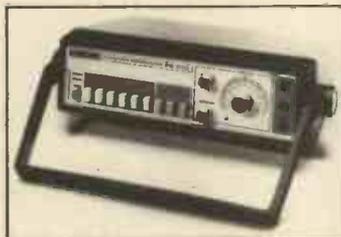

**FG 270
FUNCTION GEN.**
£139

FG270, Function Generator — 0.1Hz to 1MHz in 6 ranges — sine, square and triangle — 20V p-p open circuit output — < 1% distortion — D.C. offset — TTL O/P — Ext. VCO for sweep tests. FG271 as above plus 0.02Hz to 2MHz in 7 ranges — Int. sweep — Pulse, Tone Burst and A.M.



**DL 705
3½ DIGIT
DMM**
£92

DL 705 3½ Digit LED DMM — 2V FS 1000V FS (DC and AC) — 20A FS to 200 mA FS (DC) — 2 ohms FS to 20 M ohms FS — Accuracy 0.5% of reading — Compact, reliable and easy to use.
DL706 3½ Digit Auto Ranging and Zero — 0.1% of reading — 100µV resolution — AC Amps.
DL 720 4½ Digit — 0.03% of reading.

Plus many other Trio Products such as high sensitivity electronic voltmeters, Wow and Flutter meters, DIP meters and of course the main range of Trio scopes up to 100MHz — JUST ASK FOR THE CATALOGUE



TRIO®



House of Instruments Ltd.,
Clifton Chambers,
62, High Street,
Saffron Walden,
Essex CB10 1EE.

Telephone: (0799) 24922
Telex: 81653.

hi!
House of Instruments Ltd.

performance hi! competitive hi! reliability hi!

PE RANGER BASE STATION

Michael Tooley B.A.
David Whitfield M.A. M.Sc.
PART THREE



THE purpose of the S-meter module is to provide a d.c. output proportional to the amplitude of the 455kHz IF signal. The module samples the level of the IF signal in the Ranger preceding the amplitude limiting stages within IC100. At this point (the output of FL100) the IF signal is only at a relatively low level and hence some amplification is essential before detection. To prevent instability the module must be housed within the Ranger transceiver and its output taken via the 7-way ancillary connector to the Base and Mobile Adaptor. Where signal strength indication is not required, the S-meter module may, of course, be omitted. In this case there will simply be no meter indication on 'receive' but otherwise the performance and operation of the unit will remain unchanged.

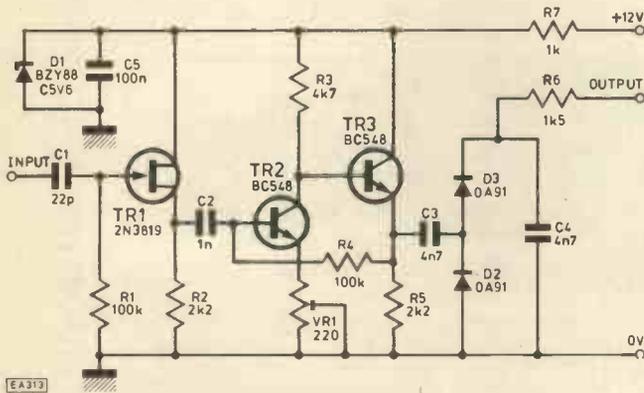


Fig. 3.1. Circuit diagram of the S-meter module

The circuit diagram of the S-meter module is shown in Fig. 3.1. Source follower, TR1, provides impedance matching and its high value of input impedance minimises loading of the IF amplifier at the point where the signal is derived. This is an important consideration as the filter needs to be accurately matched in order to obtain optimum performance. TR2 and TR3 form a voltage amplifier with gain adjustable by means of VR1, D2 and D3 rectify the amplified IF signal and the supply voltage is held constant by means of D1.

The S-meter module is assembled on a small single sided p.c.b. for which the foil layout is given in Fig. 3.2. The corresponding component layout is shown in Fig. 3.3. The

completed p.c.b. should be wrapped in a polythene sleeve and located at right angles to, and on the right hand side of, the main p.c.b. in the area adjacent to IC100 and IC101. Only four connections need to be made to the Ranger and these should again be kept as short and direct as possible.



Fig. 3.2. P.c.b. design for the S-meter module

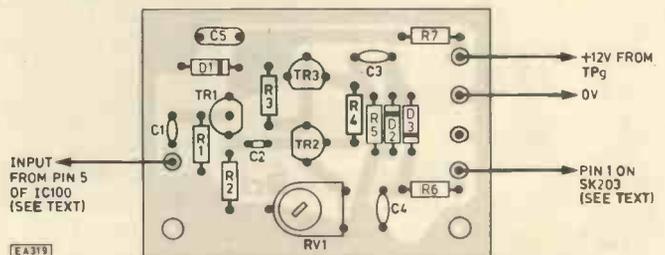


Fig. 3.3. Component layout for the S-meter module

The input is taken from the junction of R111 and FL100. This connection may most conveniently be made by soldering to the left-hand end of R111 (the end nearest FL100) on the top side of the p.c.b. The positive supply is derived from test point G and the common rail is taken from pin-2 of SK203 (or any other convenient 0V point). The output of the module is taken to pin-1 of SK203 and note that, regardless of whether the S-meter module is fitted or not, some minor modifications to the wiring of SK203 are necessary and these are covered in the next section.

TESTING AND ALIGNMENT

During the test and alignment procedure it is recommended that a current limited regulated d.c. power supply be

used. The supply should be set to give 12V d.c. ($\pm 0.5V$) and its current trip set to 1A ($\pm 100mA$). The Base and Mobile Adaptor does have its own internal 1A fuse but this should not be relied upon in the initial stages. Protection is essential in order to minimise the risk of damage to both the external power supply and to the Base and Mobile Adaptor in the event of incorrect component connection or faulty assembly (e.g. solder bridges between p.c.b. tracks). Under no circumstances should the external supply be allowed to exceed 17V as this may result in permanent damage to both the Ranger and the Adaptor.

Two interconnecting leads are required. Both need be no more than 160mm long since it is envisaged that the two units will normally be operated 'piggy-back' rather than 'side-by-side'. Constructors should, however, make the connecting cables long enough to allow the two units to be operated 'side-by-side' during the setting-up process. The RF connecting lead (at the front of the set) should use good quality 50ohm coaxial cable. (e.g. UR43 or UR76) terminated with PL259 plugs. The correct method for fitting these plugs is shown in Fig. 3.4. and 3.5. The control lead (at the rear of the set) has seven ways and should be terminated with 7-pin DIN plugs. Care must be taken to ensure that the pins are correctly linked and this is best done by checking pins 1 to 6 with an ohm-meter both for continuity and for the presence of short circuits between adjacent pins.

Make the following adjustments and connections in the order given before connecting the external d.c. supply:

- Ensure that the interconnecting leads are in place.
- The channel selector should be switched to channel 14.
- The 10dB attenuator should be switched 'off'.
- The RF gain control should be set to maximum (fully clockwise).
- VR1 should be set to minimum resistance.
- The cores of L1/L2 and L3 should all be set two full turns from the furthest position into the former.

COMPONENTS . . .

S-Meter Module

Resistors

R1, R4	100k (2 Off)
R2, R5	2k2 (2 off)
R3	4k7
R6	1k5
R7	1k

All resistors $\frac{1}{4}W$ 5% Carbon.

Capacitors

C1	22p
C2	1n
C3, C4	4n7 (2 off)
C5	100n

All capacitors ceramic disc or plate

Semiconductors

D1	BZY 88 C5V6
D2, D3	OA91 (2 off)
TR1	2N 3819
TR2, TR3	BC 548 (2 off)

Miscellaneous

VR1	220 min preset skeleton (hor)
-----	-------------------------------

- The variable capacitors should be set as follows:
VC1 and VC2; plates 20% meshed.
VC3 and VC4; plates 50% meshed.
- If the filter modules have been fitted they should be temporarily removed and replaced by shorting links.
- Connect an external loudspeaker (of between 4 and 16 ohms impedance) to the Adaptor via SK3.
- Switch the 'squelch' on the Ranger 'off'.
- Connect a matched 50ohm aerial to the Adaptor.


The external d.c. supply should now be connected and the steps which follow should permit alignment of the Base and Mobile Adaptor:




Cut end of cable clean. Remove outer covering 19mm from the end.



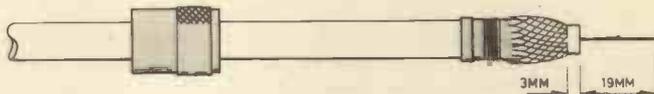Slide coupling ring and reducer onto cable.



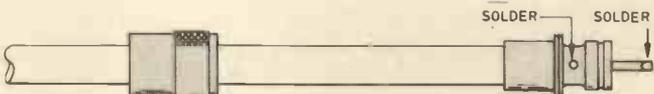Bare 19mm of centre conductor. Fan braid slightly and fold back over reducer.




Screw plug body onto reducer and tighten. Solder braid through holes and ensure that a good electrical contact is made. Solder centre conductor.




Final plug assembly with coupling ring free to mate with a socket.

Fig. 3.4. Method of fitting PL 259 connector and reducer to RG 58/U, UR76 or similar 0.2in diameter coax cables.

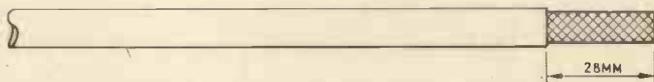

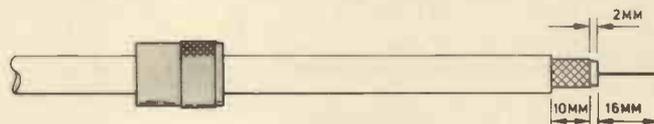
Cut end of cable clean. Remove outer covering 28mm from end.



Bare 16mm of centre conductor. Trim braid to 12mm. Slide coupling ring onto cable. Tin centre conductor.

STEP NUMBER	PROCEDURE	NOTES
1	Switch 'on' the external d.c. supply. Switch 'on' the Ranger and the Adaptor unit.	The 'receive' i.e.d. indicator on the Adaptor should be illuminated and noise should be heard from the Adaptor's loudspeaker when the volume control on the Ranger is advanced
2	Adjust the core of L1/L2 for maximum indication on the S-meter using the signal from a fairly strong local station. If a full-scale reading has been obtained reduce the setting of the RF gain control and continue to adjust L1/L2.	If the S-meter is not fitted adjust for minimum background noise (maximum quieting).
3	Select a channel on which there is a weak but stable signal. Adjust the RF Gain control to provide a reading of about $\frac{1}{3}$ to $\frac{1}{2}$ scale. Re-peak L1/L2 for maximum.	Only a slight adjustment, if any at all, should be necessary.
4	Disconnect the RF (coaxial) cable linking the Ranger and Adaptor. Connect the aerial directly to the Ranger thus bypassing the Adaptor. Note the S-meter reading obtained when a weak but stable signal is present.	
5	Re-connect the Adaptor and note the new S-meter reading with the RF gain control turned to maximum. (The same signal should be present as in step 4.)	If the RF stage has been correctly aligned and is working properly there should be an increase of approximately two S-units (around 12dB). If no discernible change is obtained or if there is a reduction in signal strength check the RF stage and repeat steps 1 to 5.
6	Replace the aerial with a 50ohm resistive dummy load capable of dissipating 5W. (Such devices are available from most CB accessory stockists.) Operate the Ranger on 'transmit' by either using the 'press-to-talk' facility on the microphone or by using a shorting link as described in the Ranger alignment procedure.	The 'transmit' indicator i.e.d.'s should be illuminated on both the Ranger and the Adaptor, and the noise from the loudspeaker should cease.
7	Adjust VC1, VC2, L3, VC1 and VC2 in the sequence given for maximum output power indication from the meter. Repeat several times and adjust the setting of VR1 to reduce the indication on the meter if necessary.	The adjustments are fairly critical and there is interaction between them.
8	Adjust VC3 and VC4 for maximum meter indication. Repeat several times for maximum output. Again adjust VR1 if necessary.	These adjustments are fairly broad with some interaction between them.
9	If an RF power meter (or SWR bridge which incorporates power measuring facilities) is available, check the output power delivered to the load. This should be between 3W and 6W. (See Fig. 3.6.)	If this is not the case repeat steps 7 to 9 inclusive.
10	Insert the filter modules and carefully adjust the ferrite cores for maximum output. Some minor re-adjustment of VC3 and VC4 may be beneficial.	The output power will be somewhat less than that obtained previously and should be typically between 2W and 5W.
11	Adjust VR2 in the Ranger for an output power of 4W.	Slight adjustment to the output stage and/or filter in the Ranger may help improve the drive level if necessary.
12	Switch the 10dB attenuator 'on' and note the effect on the output power. This should fall to approximately 400mW.	If the output power is greater than 500mW the value of R9 should be increased to 100 ohm 2W. If the output power is less than 300mW the value of R9 should be decreased to 47ohm 2W.
This completes the setting-up procedure and the Adaptor is now ready for 'air-testing'.		

Testing and Alignment procedure

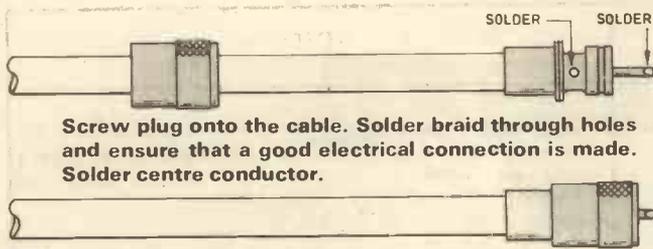

Screw plug onto the cable. Solder braid through holes and ensure that a good electrical connection is made. Solder centre conductor.

EA321


Final plug assembly with coupling ring free to mate with a socket.

Fig. 3.5. Method of fitting PL259 connector to RG 8/U, UR67 or similar 0.4in diameter coax cables.

AERIAL MATCHING UNIT


There will doubtless be many occasions where, for one reason or another, it is not possible to achieve a good match between the transceiver and an aerial system. Usually this is because the radiating element is not cut to the correct length; either it is too long or too short. Aerials with adjustable radiating elements are obviously to be preferred but they can be tiresome and inconvenient to adjust, particularly when they are mounted at some considerable distance from the rig. A most useful accessory, therefore, is a device for accurately matching the transceiver to any aerial system. The effect of providing an accurate match between the transceiver, feeder and aerial is to guarantee a low value of SWR. This helps to improve the radiation efficiency by eliminating additional SWR losses in the feeder and maintains the performance specification of the transceiver itself. The matching unit consists simply of a pi-network of two variable capacitors and a fixed inductor. An added bonus is the reduction of harmonic radiation associated with the low-pass characteristic of the network.

The circuit diagram of the aerial matching unit is shown in Fig. 3.7 together with an internal layout and wiring diagram

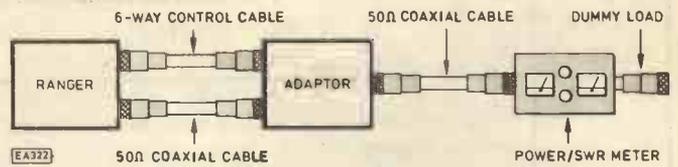


EA322

Fig. 3.6. Arrangement used for output power measurement

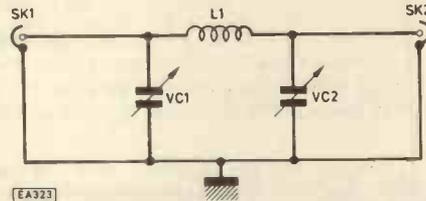


EA323

Fig. 3.7. Circuit diagram of the aerial matching unit

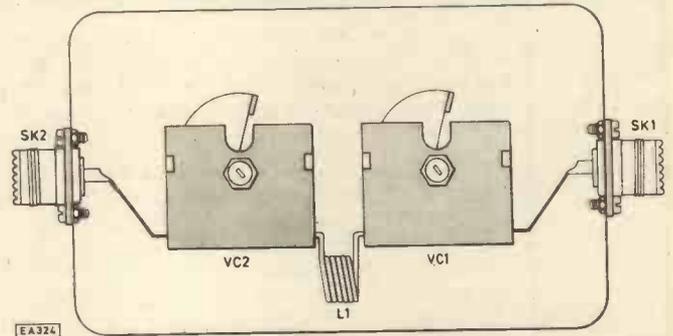

EA324

Fig. 3.8. Internal layout of the aerial matching unit

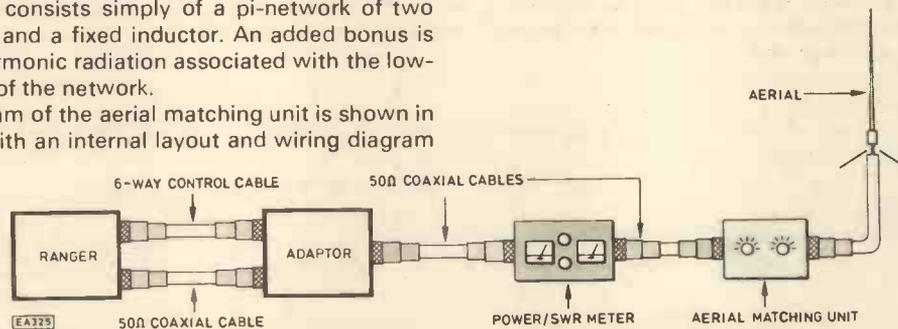

EA325

Fig. 3.9. Use of an aerial matching unit to improve SWR (Note. The matching unit should be mounted as close to the aerial as possible in order to reduce feeder SWR losses)

COMPONENTS . . .

Aerial Matching Unit

- | | |
|----------|--------------------------------------------------------------------------------------------|
| SK1, SK2 | S0239 sockets (2 off) |
| VC1, VC2 | Air spaced variable, max. capacity in the range 365 to 500pF, see text |
| L1 | 8 turns 18 s.w.g. enamelled copper wire, inside diameter 10mm, winding length 10mm approx. |
| | Metal case or diecast box |
| | Pointer knobs (2 off) fitted with '0-10' scale, see text |

in Fig. 3.8. A metal screening enclosure is essential to the correct operation of the matching unit and this can take the form of a diecast or aluminium box measuring approximately 150x80x50mm. The variable capacitors may be difficult to obtain but fortunately their exact maximum value is unimportant and can be anywhere between 365pF and 500pF. The prototype employed dual gang 176 and 208pF

capacitors with the two gangs connected in parallel to make a total maximum value of approximately 384pF. Capacitors of this type were commonplace in AM (medium and long wave) transistor portable radios of some 10 to 20 years vintage. Whatever type of capacitor is used they MUST be air spaced types and should be fitted with a pointer knob and scale. This is important for providing accurate reference points for re-setting the matching unit when it is to be used with several aerial systems. The unit should preferably be fitted as close to the aerial as possible. This is particularly important when a high SWR (greater than 2:1) is present. In many situations, however, this may not be practicable and it will be necessary to place the unit in the vicinity of the transceiver and SWR bridge. This is a less efficient arrangement (due to the high SWR in the feeder) but it will at least provide a reasonable match for the transceiver. A typical arrangement is shown in Fig. 3.9 and the aerial matching unit is simply adjusted for minimum VSWR. In practice, and with careful adjustment (both controls need to be used) it is possible to obtain an SWR of 1.1:1 or better with even the most difficult aerial systems. ★

Digital Design Techniques...

Tom Gaskell B.A.(HONS) ELEC. ENG.

Part 8 Memories & Microelectronics

IN the series so far we have looked at the design of logic systems, from simple combinational and sequential circuits up to multiplexing and bus-orientated networks. It's only a small step now into the world of microcomputing and microprocessors. We need only one more 'building block' of circuitry; the memory.

BASIC REQUIREMENTS OF MEMORY

Essentially, 'memory' is a collection of logic 1's and 0's which are stored in a system. There must be some way to 'write' these logic states into the memory, and some way to 'read' the logic states out of the memory and into other circuitry.

In some cases it might not be necessary to write information into the memory more than once. If a fixed set of binary numbers was to be stored, always the same and never requiring modification, then a 'Read Only Memory' or 'ROM' could be used; in its simplest form this would be a set of wire links or switches permanently set to give a logic 0 or logic 1 where required. In many cases, though, it is necessary to be able to frequently write information into the memory, as well as being able to read it. Such a memory is known as a 'RAM', which stands for 'Random Access Memory', meaning that all bits stored in the memory can be directly and independently written into, or read from. 'RAM' is actually a bad name for the device; all bits can be accessed randomly in a ROM, too. Unfortunately, this is a terminology that we'll have to live with!

In both ROMs and RAMs we want to be able to choose a specific point in the memory, known as the 'address', and read (or write) the information present there into the rest of our system. The memory device, therefore, will have a number of binary inputs which together form the address, and a number of binary outputs (or inputs/outputs in the case of RAM) which together form the data output (or input). Each value of the binary number on the address inputs is known as an address 'word'. In the case of RAMs, there is a read/write control input, and in many devices an 'enable' input is provided, to allow all functions of the device to be turned on or off. The timing of the logic signals can be very important; in many memory systems there must be certain minimum time periods allowed between data changing and the logic state of the read/write control being changed. Failure to observe this can cause incorrect data storage and retrieval, and is an important consideration when designing with many different types of memory device.

STORAGE DURATIONS

Systems which lose their information when the power supply is turned off are known as 'volatile', while those that

retain their information are 'non-volatile'. In some cases it is possible to use battery back-up supplies with a volatile memory to provide short term storage with the power off. In other instances it is possible to specifically design non-volatile memories, although this is usually done at the expense of performance or memory cost.

Frequently, the use of memories can be broken down into 'bulk storage', and temporary or general purpose storage, often known as 'scratchpad memory'. The former is usually a non-volatile technology, often with relatively slow access or operating speed but capable of holding a massive amount of information for permanent records, storage, filing, etc. The latter is used on a 'day-to-day' basis by the circuitry it serves, mostly for short term storage of information, rather in the manner of a jotter or scribble pad on a writing desk. (Hence the term 'scratchpad' memory). In order to avoid slowing down the surrounding circuitry, this memory has to be a fairly high speed type, although it does not usually need to store a very large amount of information.

MEMORY TECHNOLOGIES

Memories can be implemented by using various different technologies; electromechanical devices (relays, uniselectors, and the like) being one of the simplest, although these are far too slow, bulky, and cumbersome for the majority of applications. In early computers the non-volatile 'magnetic core' was used. This consisted of a large number of small ferrite rings with wires passing through their centres. By passing impulses of current through selected wires, the ferrite rings could be magnetically saturated and hence these cores were written into. By passing current pulses of the opposite polarity into the selected wires, and measuring the resulting e.m.f., the saturation of the cores could be determined and the memory could be read. Although a widely used technique several years ago, the magnetic core has now all but disappeared. More recent magnetic technologies are those of tape, disc, and bubble.

Magnetic tape is familiar to us in the form of audio cassettes, and indeed these are often used in small 'personal' computers as bulk storage, with differing frequencies of tone being recorded in bursts to indicate logic 0's and logic 1's as appropriate. Larger computers use larger tape; many times the thickness, width and length of cassette tape, running at very high speed, and with many tracks used in parallel to increase the speed of reading and writing of the memory.

Magnetic tape can store fantastic amounts of information, but is inherently very slow; if the data that you want is at the opposite end of the tape it can take several minutes to get there! A natural progression, therefore, was to use a

magnetic disc. With this system, a circular disc coated with a thin ferromagnetic material (similar to that used on tape) is continuously rotated at high speed. In the large, solid, 'hard' disc units, the read and write heads float on an air cushion fractionally above the disc, whereas in the case of the smaller flexible 'floppy' discs, the head and disc actually touch, the disc being coated with a lubricating material to reduce friction.

Information recorded anywhere on the disc can be accessed in a fairly short time by moving the heads inwards or outwards along a radius from the centre of the disc, and then by waiting for the disc to rotate sufficiently to bring the required information directly underneath the heads. In this respect, the disc is analogous to an LP record; you don't have to play the whole LP to reach a track that you want to hear—the pickup can be placed on that track directly, manually, saving a great deal of time. This method of bulk storage is fairly fast, and can store large amounts of data; typically between 0.1 and 1 Megabytes (a 'byte' is a group of eight bits) for a floppy disc and over 10 Megabytes for a hard disc.

A fairly recent development in non-volatile bulk storage is the 'Bubble Memory'. This device consists of a very thin layer of garnet crystal, grown on a non-magnetic substrate, wrapped with flat wire coils, and enclosed within a pair of permanent magnets. A large number of geometric 'shapes' are deposited on the surface of the garnet, in a soft magnetic material. Tiny magnetic 'bubbles' can be generated in the garnet; these are small areas only a few micro-metres in diameter, in which the magnetic field is opposite to that in the rest of the crystal. Magnetic fields generated by the coils produce and control the magnetic polarisation of the deposited geometric 'shapes', which in turn manipulate the bubbles. The presence of a bubble represents a logic 1, and the absence of one a logic 0.

Bubbles can be sensed by monitoring the resistance of extra 'detector' shapes. As the bubbles pass under these detectors, the resistance of the deposited shapes changes, and this can be amplified by a suitable detection circuit. The circuitry needed to control a bubble memory is complex and expensive, and the whole technology at the moment is a rather specialised one. In its favour, it is fairly compact, non-volatile, low power, and has reasonable speed performance. Of all the memory technologies in current use, it has perhaps the greatest potential for improvement and developments.

The memories that we've looked at so far have had attractions for bulk storage, but even the fastest floppy discs or bubble memories are much slower in operation than most logic families. The problem is not so much the rate of transfer of data, but rather the 'access time', i.e. the time taken between deciding that you wish to read or write to a specific location in memory, and actually being able to read or write that data. Although discs may be able to transfer data at many hundreds of thousands of bytes per second, it can take many tens of milliseconds to begin that data transfer. This is an unacceptably long time if it is to be repeated often within a system. As a result of this, extensive use is made of a much faster accessing memory technology.

SEMICONDUCTOR MEMORIES

Looking first at the RAM, its implementation is very straightforward since all that is required is an array of flip-flops or latches! Any flip-flop or latch can be used to store a 1 or a 0, can be written into (by changing the logic state of the clock), and can be read from by simply looking at the logic state of the Q output. However, the design of typical CMOS flip-flops and latches is rather over-complex for a large memory system; too much space on the i.c. 'chip'

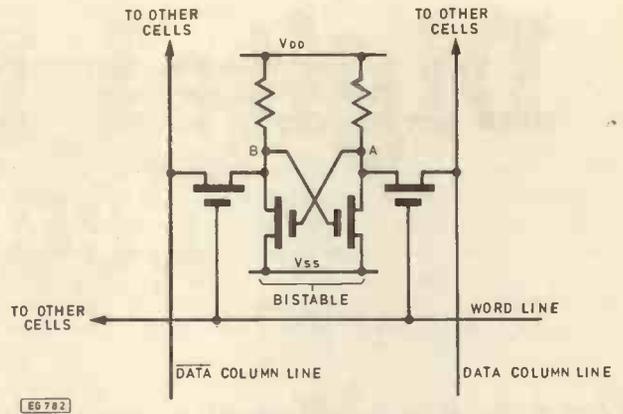


Fig. 8.1. The static memory cell

would be taken up with each device, and the total power consumption of the large numbers of devices involved would be prohibitive. As a result, a far simpler design of memory element or 'cell' is used, based on the 'bistable' circuit design. This is shown in Fig. 8.1, and is known as a 'static' RAM cell. ('Static' refers to the fact that data is stored in the cell for as long as power is applied; there is no decaying away of charge, or any other effect which may cause the cell to lose its data after a time.)

The memory is arranged in a matrix form; rows and columns of cells selected by control logic. To write a logic 1 into the static cell, the DATA column line for the column in question is taken to logic 1, and the $\overline{\text{DATA}}$ column line to logic 0. The word line, which determines the row in which the cell sits, is pulsed to logic 1, then back to 0 again. This forces the bistable into the state where point A is at logic 1 and point B at 0. (To write a logic 0, $\overline{\text{DATA}}$ column line = 1, DATA column line = 0, and again the word line is pulsed from 0 to 1 and back again). To read from the memory cell, the word line is pulsed again, but this time the logic states on the relevant column lines are monitored. If the DATA column line pulses to logic 1, then the bit stored was a logic 1. If the $\overline{\text{DATA}}$ column line pulses to logic 1, then the bit stored was a logic 0.

DYNAMIC MEMORY

The static memory cell contains four MOS transistors and two 'resistors' (also formed from MOS transistors), and hence is fairly bulky when used in quantity on an i.c. 'chip'. Supply current requirements are also relatively high, and this also restricts how closely packed the cells can be; too close together, and the resultant heat generated cannot be dissipated by the i.c. package, causing heat damage. Because of these restrictions, a lower power and more compact memory design is frequently used; the 'Dynamic' memory cell, as shown in Fig. 8.2.

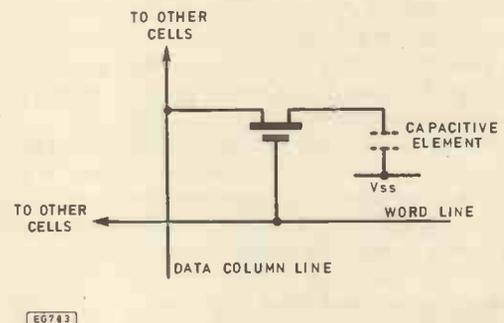


Fig. 8.2. The dynamic memory cell

To write a logic 1 into the cell, the DATA column line is held at logic 1, and the word line is pulsed from logic 0 to 1 then back to 0 again. This stores a charge on the 'capacitive element', which is actually another MOS transistor since capacitors are very difficult to fabricate effectively on an i.c. chip. To write a logic 0, the process is repeated with the DATA column line at logic 0. To read from the cell, the word line is again pulsed and the logic state of the DATA column line is monitored; if it pulses to logic 1, the stored bit was also a 1, if it does not change at all then the stored bit was a 0. (The logic 1 pulse is caused by the 'logic 1 charge' on the capacitive element discharging, via the MOS transistor, into the circuitry monitoring the DATA column line).

There are two inherent weaknesses of this design. The first is that, unlike the static cell, reading is 'destructive'; any charge stored on the capacitive element is discharged into the control circuitry upon readout, so the memory has been lost. The second weakness is that the charge on the capacitive element leaks away after a very short time (the actual capacitance value is very small), so the memory is lost after a short time anyway—well under a second! To overcome both these problems, 'refresh' circuitry is used to re-write any memory which has just been read with its 'own' data again, and to continually re-write all the data out of the memory and back into it again. These days, many popular dynamic RAMs have all the refresh circuitry built in, so they appear to the user to be static; no external refreshing is necessary.

THE ROM

Although the ROM is supposedly little more than a large array of pre-set switches, in practice it has a complexity similar to that of the RAM. This is necessary, to ensure that it can be addressed in a similar way to the RAM, that it can have a very high speed (i.e. the data should be fed out of the i.c. as soon as possible after the address has been selected), and in many cases that it can be programmed; it becomes a programmable read only memory, or 'PROM'. Naturally all ROMs have to be programmed at some time or other, so the term ROM is used for 'Mask Programmed' devices, i.e. those which have fixed programs built in during manufacture, and which are unalterable. 'PROM' refers to a device which is purchased 'blank', and is then written into; by applying high-voltage pulses into the device at the relevant address, the memory locations can be 'blown', rather like fuse links, to create the required pattern of 0's and 1's. Because it is easy to make errors while programming in this way, most PROMS are made erasable; 'EPROMS'. Erasing such devices restores all the 'fuse links', enabling the programmer to start again from scratch, and is most usually done by exposing the i.c. chip, via a transparent window in the top of the i.c. package, to a specific wavelength of ultra violet light for typically between 10 minutes and an hour. This sets all the bits to a logic 1 state; when memory locations are subsequently 'blown', this sets the bits in question to logic 0 states. 'EEPROMS', or electrically erasable PROMs, have recently started becoming available, and use electrical erase signals; they become, in effect, a non-volatile semiconductor memory of fairly large size, although their erase and write times can be very long.

Non-volatile semiconductor stores are available in their own right, the Plessey 'NOVOL' range being a prime example. This is a range of counters, counters with 7-segment decoders, and one latch circuit, which have non-volatile circuit elements built in to retain the last logic states of the device for up to one year in the absence of power. In these devices, of course, only small numbers of bits are involved, so they are only a very small-scale memory in terms of ROM, RAM and bulk storage techniques.

MEMORY ORGANISATION


Most semiconductor memories are organised in terms of 1 bit, 4 bits, or 8 bits per address word. Hence, a memory device which claimed to be 256 words x 8 bits would have a total of 2048 cells within it, i.e. a total storage of 2048 bits. We refer to a unit of 1024 bits as '1K' bits (1024 being equal to 2^{10}); hence, 2048 is 2K bits, 4096 is 4K bits etc. When memory devices are grouped together in a microprocessor or microcomputer system, we arrange them to suit the number of bits that the microprocessor uses. For example, the majority of microprocessors today work on an 8 bit system, so our memory will be arranged to be 8 bits 'wide' also. (By putting two 4-bit memories side by side, with common address lines, or eight 1-bit memories, etc.) Each set of eight bits is known as a 'BYTE', so a 4K Byte memory consists of $4 \times 1024 \times 8$ bits i.e. 32,768 bits. Often, computer jargon shortens the term '4K bytes' to just '4K', which could cause confusion with 4K bits. It is usual to talk about individual memory i.c.s. in terms of bits, but assemblies of memory devices, memory systems, and microcomputers in terms of bytes. Typical 'personal' or 'home computers' are available with between 1K and 48K (bytes) of RAM, and up to 12 or 16K (bytes) of ROM.

THE MICROPROCESSOR

The 'micro', as it is known, is a very complex and technically advanced electronic device, and there certainly isn't room in this article to go into detail about its design and operation. However, we can take a look at the basics, to give an idea about the way that the technology is used, and the sort of facilities that can be provided. Two months ago, we looked at bus-orientated systems, and gave an example of some data manipulation in an A.L.U. using such a system. Let's now take those principles further, and look at a greatly simplified 8-bit microprocessor system. (Note that a microprocessor will often be referred to as a 'Central Processing Unit' or CPU.)

A block diagram of a simplified microprocessor is shown in Fig. 8.3. The internal 8-bit data bus, ALU, accumulator, and general purpose registers have all been met before in Part 6 of this series. The data and address bus controllers are basically bi-directional register and latch arrangements to permit the feeding of data and addresses to and from external switches, transducers, bulk memory, displays, etc. The address bus controller normally uses 16 bit words, which are made up from two separate 8 bit words obtained from the internal 8 bit data bus. Most of the general purpose registers are 8 bit, but there are some specific exceptions; the 'Program Counter' and 'Stack Pointer' registers are both 16 bit, for example.

The 'Instruction Register' is used, together with the Control Unit, to identify and verify specific binary numbers called 'Instruction Codes', which are fed into the microprocessor from the program written in the external ROM or RAM. These numbers provide specific instructions to the microprocessor; 'reset the accumulator' or 'increment' (add 1 to) register B, etc. When identified and decoded by the control unit, each instruction causes a specific number of control and timing signals to be sent out to the relevant registers and areas of circuitry, in order to cause that instruction to be implemented. The number of different instructions that can be performed by a micro is a very good indication of the 'power' of that micro, along with the number of registers that it makes available to the user. The popular Intel 8080A, for example, has 78 instructions in its instruction set, whereas the Zilog Z80 (acknowledged as one of the most powerful 8 bit microprocessors available) has 158 instructions, including all 78 of the 8080. The Z80 is also well sup-

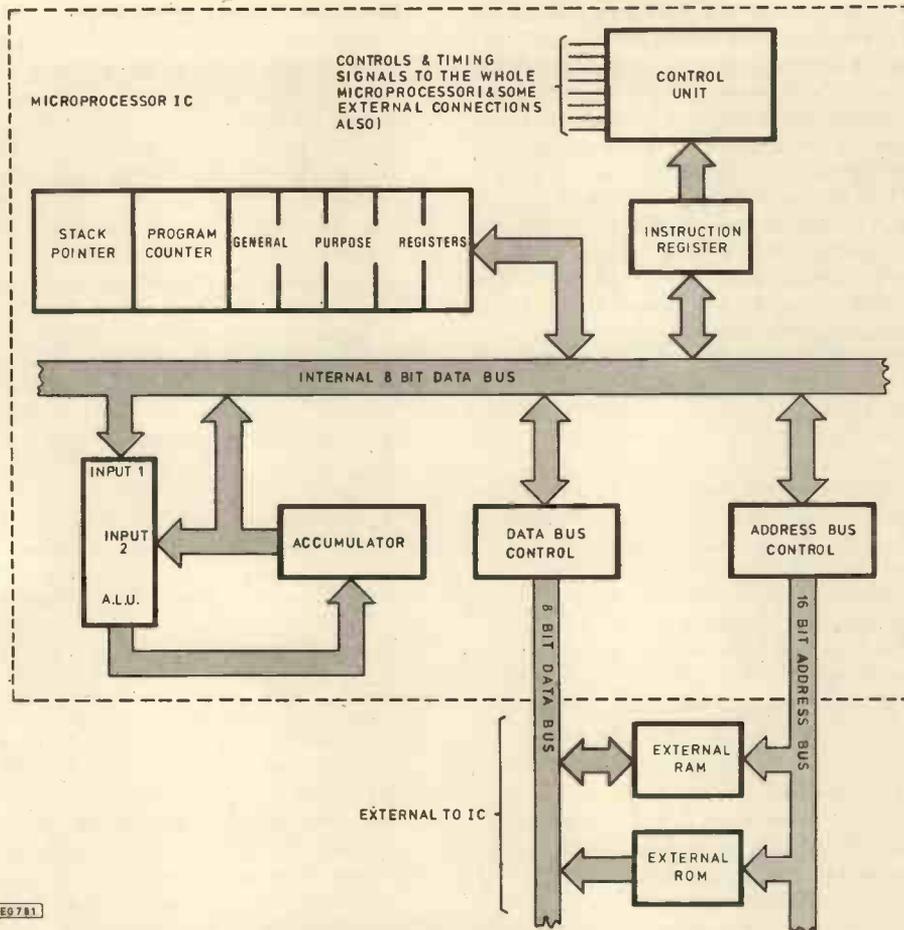

E0781

Fig. 8.3. Simplified 8-Bit microprocessor block diagram

ported with registers; a total of 18 8-bit and 4 16-bit registers are provided.

Unlike a conventionally designed piece of circuitry, the microprocessor based system is incapable of functioning, even when mechanically complete and apparently finished. The mechanics—p.c.b., power supply, i.c.s resistors, etc., are collectively known as 'hardware'. What is needed is a 'program'; a set of binary numbers which instruct the microprocessor what to do, and how to do it. Such programs or lists are known collectively as 'software', they are, in effect, the paperwork involved in the system. Programs, of course, can be written into ROM, RAM, or bulk storage. In this case, these devices consist of both hardware and software, and so any memory device containing a program is known as 'Firmware'; half way between being hard and soft!

PROGRAMMING

A program contains a series of instructions, and often data too, although in many systems the data is provided externally by switches, transducers, etc. The microprocessor executes each instruction in sequence, one at a time, although there can be built-in jumps such that upon receipt of a specific instruction the microprocessor will 'move' to a different area of the program, before or after the point which it has just 'left' and continue executing the program from there. The sequence of instructions given at the end of Part 6 of this series, covering the addition of two numbers together and the putting of the result in register 'D', is an example of part of a very simple program.


Programs can be shown diagrammatically by a 'flow chart'; a set of symbols and text, which is the software equivalent of a block diagram used to represent the hardware. Let us take,

as an example, the requirement to flash an l.e.d. on and off for a certain number of times as determined by a thumbwheel switch. The simplified flow chart for this program is shown in Fig. 8.4. The 'loop' is gone round as many times as the l.e.d. is flashed on. The type of instruction causing the program to jump from the question "is the content of register B zero?", to the "turn on l.e.d." sequence is known simply as a 'jump' instruction. In fact, the probable instruction would be "jump if not zero", which is an example of a 'conditional' jump. These conditional jumps make programming very much easier, because they effectively test for a specified condition ("accumulator = zero", or "a certain logic state = 1", etc.,) then either jump to a different part of the program, or continue to the next program step in the list, depending on the result.

The turning on of the l.e.d. would be accomplished by an external circuit driven from the microprocessor's 8 bit data bus, and the thumbwheel input would likewise be fed into the micro. The half second delay could be created by using an external monostable circuit, again, via the data bus, or by software methods; the computer takes a finite time to perform each program step, so by making it do a 'trivial' exercise a few tens of thousand of times, then time can be wasted, and a suitable delay created. In all programs, the most important thing to remember is that within the circuitry in question, both the instructions and the data are being represented as logic 0's and 1's; simple binary numbers.

THE USE OF MICROPROCESSORS

There are, essentially, two ways of using a 'micro' within a system. The first is 'dedicated' usage; the microprocessor has a single fixed program held in ROM, which it always per-

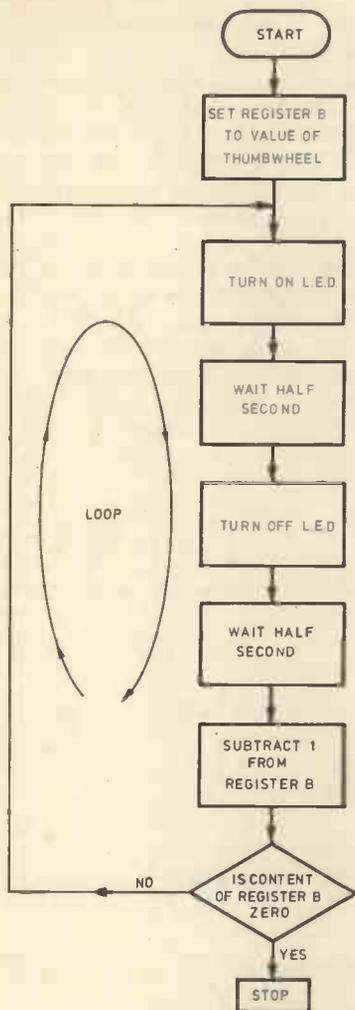

EG779

Fig. 8.4. Simplified flow chart of I.e.d. flasher


forms in the same way, while using small amounts of RAM for temporary storage if necessary. The user will have no means of re-programming this device. The microprocessor in this application is simply replacing large amounts of conventional logic circuitry. Test instruments, hand held electronic games, sewing machines, washing machines, cassette recorders; etc., whenever they use a microprocessor, they do so on a dedicated basis, and in each case the micro gives a fixed set of responses to a fixed set of stimuli, or inputs.

'Non-dedicated' use introduces us to the domain of the microcomputer, where the full performance, instructions, and capabilities of the microprocessor are fully at our disposal.

THE MICROCOMPUTER

The term 'microcomputer' means more than just a small computer. It is a computer in which the CPU is manufactured as a single i.c.; a microprocessor. Unlike the dedicated micro-based systems, it requires definite operator interaction before it can be of very much use at all! It is a programmable device, so without the program written into it, it can do very little. The constituent parts diagram of a typical microcomputer is shown in Fig. 8.5.

The video output of the microcomputer is normally in the form of a 9 to 12 inch CRT; often a portable domestic television set. This video monitor is usually arranged to display a number of ASCII characters corresponding to the binary numbers held in a particular part of the memory. Imagine the

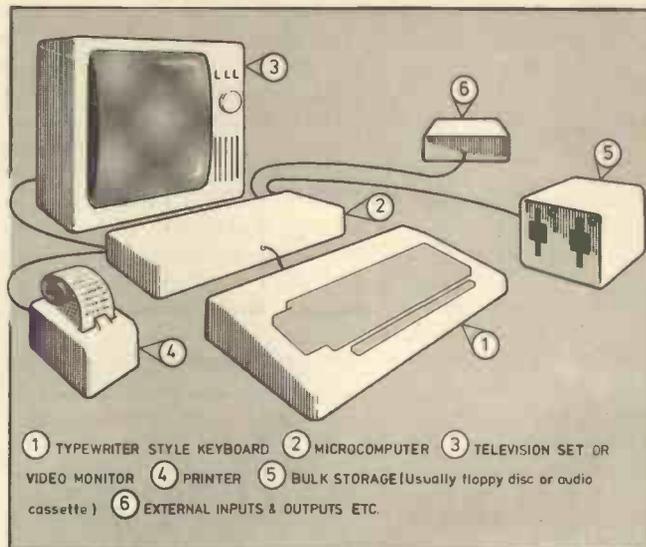

EP792

Fig. 8.5. Constituent parts diagram of a microcomputer system

screen being divided up into a matrix of squares, with each square having a specific and unique address. There are typically around one thousand (1K) of these. Part of the RAM known as the 'Video RAM' is usually dedicated for this use, and the display is then known as 'memory mapped'. The keyboard enters ASCII codes into the computer, which are normally fed up onto the screen as the program is being written. The bulk storage, printer, and external outputs and inputs are all fairly self-explanatory.

The microprocessor has many extra circuits and devices surrounding it; encoders and multiplexers to feed the keyboard information in, character generators and modulators to enable the memory to be displayed on the screen, and (of course) ROM and RAM. The ROM in a microcomputer normally carries the 'monitor program' (not to be confused with the video monitor); this is the 'apparent intelligence' of the computer, and is the interface point between the microprocessor logic, and the human operator and keyboard. Depending on the size and complexity of this monitor program, the facilities offered to the user can be considerable. The monitor contains basic and fundamental information within the computer, to tell it to scan the keyboard for any keys pressed, then to feed the ASCII character corresponding to the key pressed into the section of video RAM corresponding to the relevant position on the screen. It also enables, editing of the video RAM; deletion of characters, moving the display up and down ('scrolling'), etc.

Although the microprocessor operates on binary numbers, known as 'machine code', the human operator can program the computer in the hexadecimal equivalent to those binary numbers, making it quicker to type in, and easier to understand. This hexadecimal listing is known as 'object code'. Some systems help still further, by allowing the program to be written in 'mnemonics', which is a means of writing hex instructions in an abbreviated English language format. For example, 'JP' could be used to represent a jump instruction, the hex code for which might be C3, or 'INC B' might be used to represent the instruction 'increment the contents of register B', who's hex code might be 04. By using mnemonics (pronounced 'nimonics'), the program (when written down or typed in) can be much easier to follow and understand; the instructions all mean something and are no longer a collection of fairly arbitrary looking letters and numbers!

To produce machine code from the mnemonic program, an 'assembler' program must be used, which acts as a 'converter' between mnemonic and binary. (To translate back from binary to mnemonic, a program called a 'disassembler' is brought into use.) Much of the programming for dedicated microprocessors is written on microcomputers in object code or mnemonics, because this level of computer operation is very fast; the computer operates very efficiently when using these codes. However, programming can still be a complex, slow, and difficult task, as the detailed internal operation of the microprocessor is still dominant; programs are written in terms of registers, clock signals, ALUs, flags, etc. To bring the program one step higher in level, to a nearer approximation to the English Language, we must use a 'high level language'.

HIGH LEVEL LANGUAGES

The high level language raises programming to a fairly easily understood level. Instruction such as 'GO TO', 'PRINT', and 'IF X = Y . . . ' are used, and enable people who are not immediately familiar with the computer or program in use to make sense of it all fairly quickly. There are many different languages; FORTRAN, COBOL, ALGOL, BASIC, PASCAL, FORTH, etc., the most commonly used of these (in the case of microcomputers) being BASIC, which stands for 'Beginners Allpurpose Symbolic Instruction Code'. Although there are several 'dialects' of BASIC they all share many common properties, and BASIC programs for one make of computer can usually be run on other computers with only a small amount of modification, if any at all. The opposite is true of object code and mnemonics, since these are specific to the microprocessor and monitor program in use, and can be quite difficult to translate for other systems. A special program must be used within the computer to convert programs, written by the user in BASIC, into machine code, and to convert machine code 'replies' from the computer back into the relevant BASIC statements and comments. This special program is normally held in a ROM, as firmware.

High level languages, because of the extra complexity involved, are relatively slow in use; each step of the program takes longer to execute than in the case of machine code based programs. Even so, the operation can be fast enough for all but the most demanding applications.

GETTING TO GRIPS WITH THE 'MICRO'

Unfortunately, the microprocessor is not something that you can just 'dabble' at; you can read all that you like about it, but until you get 'hands on' experience with a micro-based system you will still know very little about the practicalities of the subject. By far and away the best learning aid is a microcomputer itself, which will cost a significant amount of money, so it is important to shop wisely. There are microcomputers on the market that may seem attractive because of their very low cost, and some good publicity. Indeed, they demonstrate considerable engineering achievement in squeezing so much circuitry into remarkably small spaces, for a reasonable price. However, they can be very restricting in performance; the keen user will find that the capabilities of the machine, even with 'expansion' (more memory), can be very limiting. For what they are, they are excellent, but they are not fully fledged microcomputers in the same class as machines costing over £200. It is strongly suggested that if you are serious about learning about microprocessing and computing, you spend more money to avoid disappointment in the very near future. As a compromise, some computers in kit form can enable you to start off with a simple and inexpensive system (working on the object code level), then build it up slowly, and add a high

level language, to finish up with a system which is worth several hundred pounds.

The machine to buy is very much a personal choice, to be made in combination with a study of magazine reviews, advice gleaned from other, more experienced microcomputer users, and a trip or two to your local dealer. Obviously, you get what you pay for, but to a certain extent you can pick and choose your approach. For those interested in the hardware side of the subject, the kit computers mentioned earlier can be a good starting point, but only if your standard of construction, especially soldering, is very good. Kit computers are NOT for beginners! Nascom 1, Nascom 2 and Tangerine products, amongst others, can certainly be recommended. Ready-built computers are for those less confident in the hardware side; Tangerine, Video Genie, Sharp and Tandy all have ready-built products, and the new 'BBC micro' is attracting a lot of attention at the moment, although at the time of writing it is not yet on the market. Paying out still more can provide small business computers such as the PET, APPLE or Tandy, but these represent a considerable investment and are not necessary unless you are likely to need their very advanced facilities later. A choice in the microprocessors used comes down to 6502 versus Z80 in the case of most microcomputers mentioned. The Z80 is undoubtedly more powerful, but the 6502 is somewhat more widely used, so once again the choice is a personal one.

Another point to make is in the interest of domestic harmony! Computing can take up a surprising amount of time. 'De-bugging' programs has kept most people busy into the early hours on a number of occasions, and you should be aware that demands on your time can be considerable, especially at first. Computing is not something that you can do a little at a time; several hours at a stretch is needed to get to grips with the problems, and preferably in peace and quiet, too. Don't let this put you off, though—it's a useful and fascinating subject, and well worth spending time and effort on!

In conclusion, if microcomputing or microprocessors are of interest to you, then the only real way to learn is to buy a microcomputer, and spend some time with it. Before committing yourself, why not see if the local school or technical college has evening classes in computing or microprocessors, or even runs a suitable club? This would enable you to try out various machines before buying, learn more about the subject, and ask the advice of other enthusiasts.

IC TECHNOLOGY

As technology has advanced through the years, so the number of active devices on an i.c. chip has increased. We can define the 'scale' of integration as follows (remember that each gate is made up of a number of transistors or MOS devices):

Small Scale Integration (SSI); up to 12 gates per i.c. Most NAND, NOR, inverter, and similar combinational logic i.c.s. fall into this category.

Medium Scale Integration (MSI); from 12 to 100 gates per i.c. This covers the range of counters, registers, decoders, flip-flops, etc.

Large Scale Integration (LSI); from 100 to several hundred gates per i.c. Multiplexed counter/driver i.c.s. digital clock i.c.s. and similar complex devices all fall into this category.

Very large Scale Integration (VLSI); from several hundred to several thousand gates per i.c. This is the realm of the microprocessor and the large memory i.c.s. Some micros even have memory i.c.s. both ROM and RAM, built in! Many 'accessory' i.c.s to the microprocessor are needed, such as

programmable timers, peripheral management devices, memory controllers, input/output controllers, etc., and most of these are LSI or VLSI devices in their own right. In many cases, the microprocessor is only a very small part of the whole system; its support i.c.s can take up a lot more space and cost more than it does itself!

To help cut down on the number of 'accessory' i.c.s in any logic circuit or system, the 'Uncommitted Logic Array', or 'ULA' has been developed. This is a very large collection of logic gates which have no pre-determined interconnections. By designing a suitable pattern of interconnections of these gates, a custom-built i.c. can be created which will do the job of a large number of 'off the shelf' devices. Because the ULA is a standard device, with only the final interconnection layer being customised for each application, it is considerably cheaper than having an entire i.c. designed and built, and this approach, therefore, holds great promise for further miniaturising circuit designs in the years to come.

DIGITAL ELECTRONICS IN THE FUTURE

The pace of technological advance is so fast at the moment that it is difficult, if not impossible, to predict developments in the medium or long term future. However, it is possible to extrapolate current trends and developments, and to fairly accurately assess the changes that we can expect to see in the next few years.

In terms of microprocessors, the trend is towards larger and larger numbers of bits being used in a device. The industry 'standard' is currently 8 bits. 16 bit micros are now readily available and are starting to be used in large quantities, yet already we have seen the first appearances of the 32 bit micro; an incredibly powerful i.c. which will enable us to out-perform the much larger 'mini-computers' with single board VLSI microcomputer systems. 64 bits is still long way off, but is far from being an unrealistic or impossible dream. To keep pace with the speed and power of these large devices, memory manufacturers will continue increasing the number of cells per chip, and increasing their operating speeds, probably with dynamic RAM, EEPROMS, and bubble memories showing the greatest improvements.

The 'in' subject at the moment is voice synthesis and speech recognition systems. Cheap, high quality synthesis i.c.s are readily available at low cost but have the severe restriction of a very limited vocabulary. Infinitely variable 'phonetic' synthesisers are more expensive, and most of them suffer from a very poor quality of speech. However, the i.c. manufacturers and designers seem determined to thrust the 'talking hot drink vending machine', and similar ideas, upon us, so this is sure to be an area of considerable future expansion! Speech recognition is a much more difficult task, due to the subtle nuances, inferences, dialects and idiosyncrasies that punctuate the speech of all of us. Again, systems are available with limited performance, and these will be improved upon considerably in the years to come.

Combining speech synthesis and recognition will allow direct communication between the computer and the 'man-in-the-street', which offers vast scope for technological advance and integration of the computer into our everyday life. From the other angle, the man-in-the-street is becoming more familiar with the subject of computing in its own right. All British schools are being equipped with at least one microcomputer, and already many schoolchildren are achieving stunning levels of proficiency and knowledge about computing. The 'electronic office' is with us; word processing, facsimile machines, electronic filing, and data transfer systems are all available and are being used in many of the large companies. Expensive, yes, at the moment, but as with most electronic goods a continued demand will

result in dramatically lowered costs.

Returning to technological advances at the device level, the Uncommitted Logic Array, as mentioned earlier, will help in the miniaturisation of circuit assemblies, which in turn will increase the number of everyday products which have electronics incorporated into them. Speed limitation is a major problem in many microprocessors and computers, and advances are already being made towards providing the technological basis for the next generation of devices. Gallium Arsenide semiconductors, and those using the 'Josephson Junction', both of which need very low temperature cooling systems to operate, offer considerable decreases in gate propagation delays, with the resultant increase in computing speeds, and show great potential for the future. The one thing that seems certain about the times ahead is that they will be filled with change, challenge, and interest, just as the last few years have been. The profession, and hobby, of electronic engineering is guaranteed to have a colourful future for many years to come!

DIGITAL DESIGN TECHNIQUES

We now conclude this series on digital design techniques; there's no 'mini-project' this month because of the level of complexity that we have now reached, and the resultant limitations of space, so for the final project see next month's issue. In the past few months we have worked through from binary logic and combinational gates, all the way up to microprocessors. The pace has been swift, and to get full benefit from the series it is strongly suggested that you follow up the points made, and do further reading, experimenting, and designing of your own. There is much to be learnt and a great deal of fun and enjoyment to be had, so start putting together your own projects today!

ACKNOWLEDGEMENT

I would like to express my grateful thanks to my father, Peter Gaskell, and to my friend and colleague John Miller, for all their help, criticism, and suggestions in the preparation of this series.

T.A.G.

PE POPULAR PROJECTS...

Our book *PE Popular Projects* containing a selection of popular projects is now available. The book costs £1.25 from retail outlets and is also available for £1.50, UK post paid, or £1.80 overseas surface post paid, from Post Sales Department (PE Popular Projects), IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF.

The book contains the following projects:

Battery Voltage Indicator, Rev. Counter, Ammeter, Engine Temperature Meter, Dwell Meter, Headlight Warning, Automatic Car Aerial, Digital Temperature Controller, Ultrasonic Burglar Alarm, Home Freezer Alarm, PE Diatomic, Digital Exposure Timer, Smooth Fuzz, Phaser, Guitar Sound Multiprocessor, R.C. Failsafe, Waveform Generator and Pulse Generator.

Step-by-step fully illustrated assembly and fitting instructions are included together with circuit descriptions. Highest quality components are used throughout.

Sparkrite


BRANDLEADING ELECTRONICS

NOW AVAILABLE IN KIT FORM





SX1000 Electronic Ignition

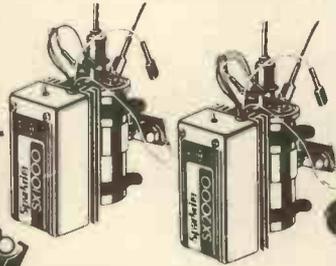- Inductive Discharge
- Extended coil energy storage circuit
- Contact breaker driven
- Three position changeover switch
- Over 65 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles.





SX2000 Electronic Ignition

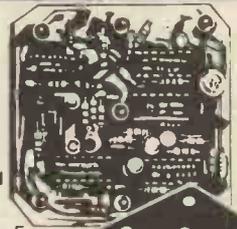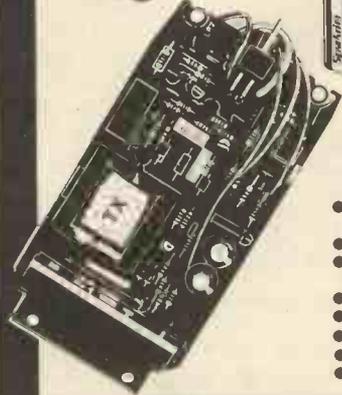- The brandleading system on the market today
- Unique Reactive Discharge
- Combined Inductive and Capacitive Discharge
- Contact breaker driven
- Three position changeover switch
- Over 130 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles



MAGIDICE Electronic Dice

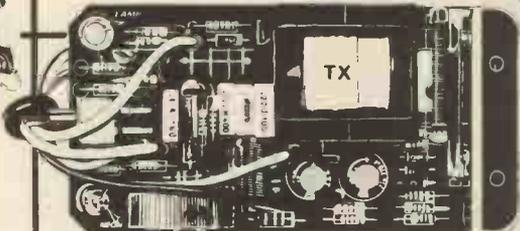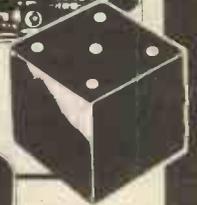- Not an auto item but great fun for the family
- Total random selection
- Triggered by waving of hand over dice
- Bleeps and flashes during a 4 second tumble sequence
- Throw displayed for 10 seconds
- Auto display of last throw 1 second in 5
- Muting and Off switch on base
- Hours of continuous use from PP7 battery
- Over 100 components to assemble





TX2002 Electronic Ignition

- The ultimate system ● Switchable contactless. ● Three position switch with Auxiliary back-up inductive circuit.
- Reactive Discharge. Combined capacitive and inductive. ● Extended coil energy storage circuit. ● Magnetic contactless distributor triggerhead. ● Distributor triggerhead adaptors included.
- Can also be triggered by existing contact breakers.
- Die cast waterproof case with clip-to-coil fitting ● Fits majority of 4 and 6 cylinder 12v neg. earth vehicles.
- Over 150 components to assemble



VOYAGER Car Drive Computer

- A most sophisticated accessory. ● Utilises a single chip mask programmed microprocessor incorporating a unique programme designed by EDA Sparkrite Ltd. ● Affords 12 functions centred on Fuel, Speed, Distance and Time. ● Visual and Audible alarms warning of Excess Speed, Frost/Ice, Lights-left-on. ● Facility to operate LOG and TRIP functions independently or synchronously.
- Large 10mm high 400ft-L fluorescent display with auto intensity. ● Unique speed and fuel transducers giving a programmed accuracy of + or - 1%. ● Large LOG & TRIP memories. 2,000 miles. 180 gallons. 100 hours. ● Full Imperial and Metric calibrations. ● Over 300 components to assemble. A real challenge for the electronics enthusiast!

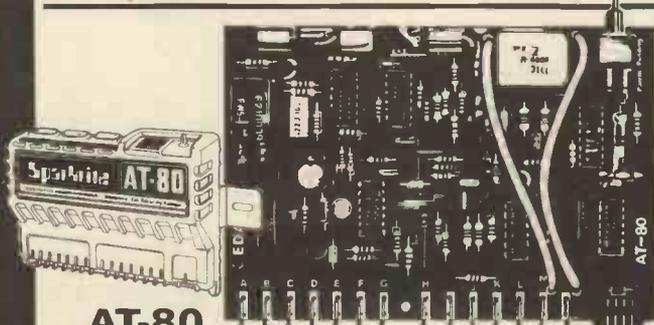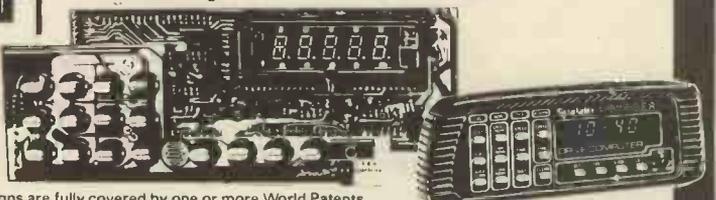

AT-80 Electronic Car Security System

- Arms doors, boot, bonnet and has security loop to protect fog/spot lamps, radio/tape, CB equipment
- Programmable personal code entry system
- Armed and disarmed from outside vehicle using a special magnetic key fob against a windscreen sensor pad adhered to the inside of the screen ● Fits all 12V neg earth vehicles
- Over 250 components to assemble

All EDA-SPARKRITE products and designs are fully covered by one or more World Patents.

EDA SPARKRITE LIMITED 82 Bath Street, Walsall, West Midlands, WS1 3DE England. Tel: (0922) 614791

Please allow 28 days for delivery

NAME _____ PE/3/82

ADDRESS _____

I ENCLOSE CHEQUE(S)/POSTAL ORDERS FOR

£ _____ KIT REF. _____

CHEQUE NO. _____
 -24hr. Answerphone
 PHONE YOUR ORDER WITH ACCESS/BARCLAYCARD
 SEND ONLY SAE IF BROCHURE IS REQUIRED

	SELF ASSEMBLY KIT	READY BUILT UNITS
--	-------------------	-------------------

SX 1000	£12.75	£25.90
SX 2000	£19.95	£39.90
TX 2002	£29.95	£59.90
AT. 80	£29.95	£59.90
VOYAGER	£59.95	£119.90
MAGIDICE	£9.95	£19.90

PRICES INC. VAT. POSTAGE & PACKING

BRANDLEADING BRITISH ELECTRONICS



CUT OUT THE COUPON NOW!

SS

PE ROBOTS

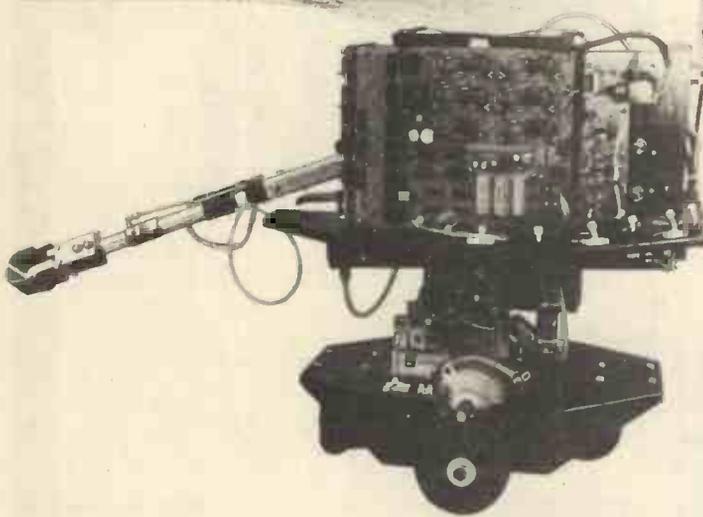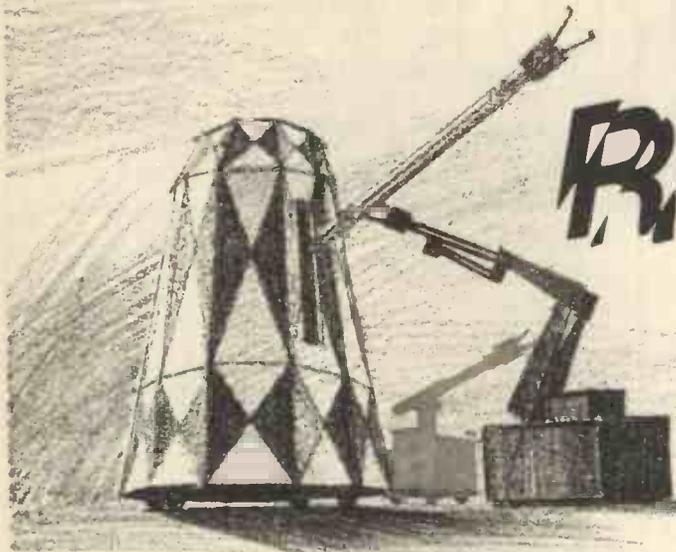PART 5

**RICHARD BECKER · TIM ORR
RICHARD MONKHOUSE**



Two photographs are shown here; one of the Genesis Mobile unit, M101, and the lower photograph which illustrates through multiple exposure photography, the level of robot technology with us today, by way of the Cincinnati Milacron machine. This latter machine (photo courtesy of Cincinnati) is in a somewhat prohibitive price range for the student. *Education* is quoted as an ideal application for the Genesis robots because they are *inexpensive* reprogrammable multi-tasking machines: and *light industry* because they are also engineered to a professional standard.

RÉSUMÉ

Genesis is a series of hydraulic computer controlled robots ideal for education, light industry and as microcomputer peripherals.

Features are: extremely low cost, up to six controllable axes, positional sensing, servo control, continuous path motion, learning ability, RS232 interface, and IR remote control for the mobile unit.



Constructor's Note

Complete kit of parts for this project can be obtained from Powertran Cybernetics, Portway Industrial Estate, Andover, Hants SP10 3WN. ☎ Andover (0264) 64455.

Prices are as follows . . .

<i>Genesis M101 4 axis model (excluding wheel base)</i>	£295.00
<i>Genesis M101 5 axis model (excluding wheel base)</i>	£345.00
<i>Genesis M101 wheel base</i>	£79.00
<i>Genesis P101 4 axis model</i>	£450.00
<i>Genesis P101 6 axis model</i>	£545.00
<i>Genesis S101 4 axis model</i>	£355.00
<i>Genesis S101 5 axis model</i>	£405.00
<i>Position detector coil set for M101, S101 4 axis models</i>	£15.00
<i>Position detector coil set for M101, S101 5 axis models</i>	£19.00
<i>Position detector coil set for P101 4 axis model</i>	£15.00
<i>Position detector coil set for P101 6 axis model</i>	£24.00
<i>Position detector board for M101, S101 4, 5 axis models</i>	£6.50
<i>Position detector board for P101 4, 6 axis models</i>	£7.50
<i>Motor drive board for M101 wheel base (2 required per machine)</i>	£11.50
<i>Control electronics for M101 (microprocessor board, interface board, display board and mounting bracket)</i>	£135.00
<i>Processor box for S101, P101 (microprocessor board, interface board, display board, power supply, interface cables, conduit, cabinet)</i>	£175.00
<i>Parts for RS232C interface (fits on microprocessor board)</i>	£14.50
<i>Hand held controller box for M101 (includes infra red transmitter and rechargeable battery)</i>	£47.00
<i>Hand held controller box for S101</i>	£33.00
<i>Hand held controller box for P101</i>	£33.50

All prices subject to 15% V.A.T.

Components . . .

CONTROL BOX (MOBILE)

Resistors

R1, R4, R6	180k (3 off)
R2	120k
R3, R5, R23, R29	47k (4 off)
R7	470
R8	3k9
R9, R12, R14, R15, R28	10k (5 off)
R10, R11	1M (2 off)
R13	2k2
R16	33
R17	1
R18, R22, R24	100k (3 off)
R21, R27	560k (2 off)
R19, R20, R25, R26	12k (4 off)

All resistors $\frac{1}{4}$ W 5%

Potentiometers

VR1	100k slider (linear)
VR2	47k slider & centre indent (linear)
VR3	470k preset
VR4, VR5	1M preset (2 off)
VR6, VR7	100k preset (2 off)

Capacitors

C1	1n Siemens B32560
C2	10n ceramic Piher
C3, C4	39p ceramic Piher (2 off)
C5, C6	100 μ /16V elect. Axial lead (2 off)
C7, C8	10n Siemens B32560 (2 off)

Transistors and Diodes

TR1	BC184L
TR2	TIP31A
TR3, TR4, TR5	BC182L (3 off)
D1-6, D9-14, D17, D18, D21, D25-30, D33-38, D43	1N4148 (28 off)
D41, D42	TIL 38 (2 off)
D44, D45	9491BJ (1V2 Band Gap) or LM385 (2 off)

Integrated Circuits

IC1, IC2	4051B (2 off)
IC3	4024B
IC4, IC9	4013B (2 off)
IC5	40106B
IC6	4023B
IC7	4011B
IC8	LM324
IC10	ICM7555 IPA
IC11	10k s.i.p.

Miscellaneous

Printed circuit board (RTX)
M101 metal cabinet and fixing screws
PP3 stud connector
PP3 rechargeable battery
Slider knob
Pot knob
8-pin d.i.l. socket
14-pin d.i.l. socket (7 off)
16-pin d.i.l. socket (2 off)
Switches (27 off)
Slide switch
3.5 jack socket
Jack-to-jack lead (1 metre)

COMPONENTS . . .

CONTROL BOX (P101 & S101)

Resistors

R1, R4, R6	180k (3 off)
R2	120k
R3, R5	47k (2 off)
R7	470
R10, R11	1M (2 off)
R12	10k
R13	2k2

All resistors $\frac{1}{4}$ W 5%

Capacitors

C1	1n Siemens B32560
C2	10n ceramic Piher
C3, C4	39p ceramic Piher
C5	100 μ /16V axial lead

Transistors and Diodes

D1-6, D9-14, D18, D21, D25-30, D33-38, D43	1N4148 (27 off)
D46	5V6 Zener
TR3	BC182L

Integrated Circuits

IC1, IC2	4051B
IC3	4024B
IC4	4013B
IC5	40106B
IC6	4023B
IC7	4011B
IC10	ICM75551PA
IC11	10k SIP

Miscellaneous

Metal cabinet and fixing screws
Printed circuit board
DIN plug 5-pin 240°
5-way cable (3 metres)
Slide switch
push-button switches
8-pin d.i.l. socket
14-pin d.i.l. socket (5 off)
16-pin d.i.l. socket (2 off)

Note: In part 2, Interface board components list, under Miscellaneous—SIP1 and SIP2 should be considered as IC22 and IC23. SIP3 is IC24.

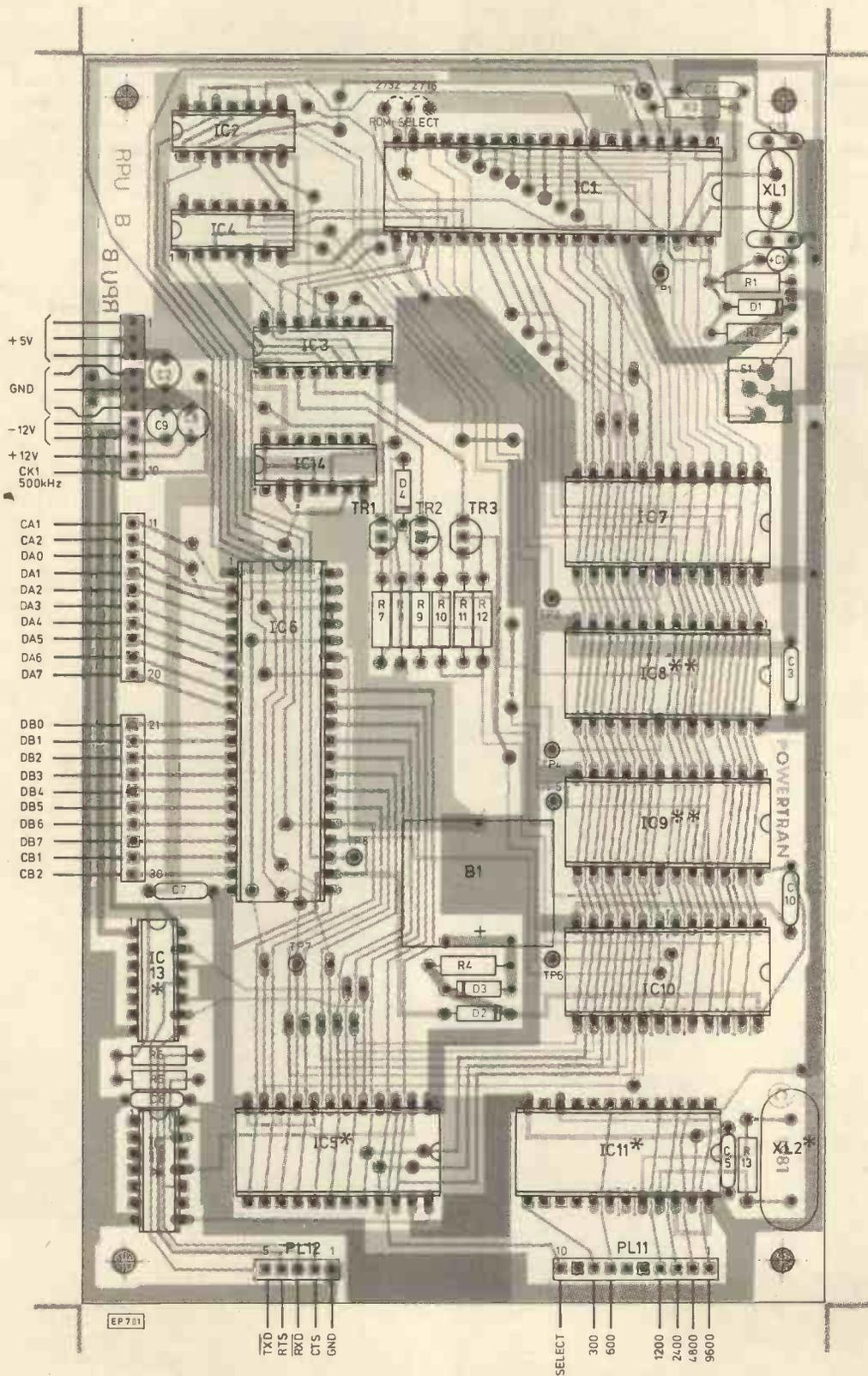


Fig. 1. Robot controller *RS232 version only. **Not used at present

INTERFACE BOARD

The Robot requires many more than the 20 I/O lines available from one PIA. To obtain these without going to multiple PIA's, the interface board uses a secondary 8 bit bus connected to one side of the PIA whilst the other side generates latch clocks for output latches or output enables for system inputs. Although careful attention to detail was necessary in the software to avoid bus clashes, this method makes efficient use of board space and means that the software can be debugged easily from an external computer.

The outputs from the expanded I/O scheme comprise two sets of 8 bits for controlling the solenoids and the motors, 8 bits for the display and bleeper and 8 bits for extra devices. On the input side there are 2 bits for the keyboard decoder interface one bit to signify RS232 connection and 5 bits for extra inputs.

SYSTEM DESCRIPTION

On manual control which is available in the EDIT mode, the robot arms can be moved around using the appropriate control buttons on the control box. There is logic to prevent both solenoids for an axis being activated simultaneously. The robot is taught by being moved under manual control to the desired position. Pressing the INSERT button enters the position and the microprocessor stores it in the battery backed-up CMOS RAM.

When a position is to be remembered, a combination of an analogue multiplexer and an eight bit analogue-to-digital converter (interface board — IC25 and IC24) selects each of the 5 transducer voltages in turn, and digitises them.

On replay, the ADC/multiplexer combination is constantly

scanning the 5 inputs under software control, the measured positions of the five axes being compared by the microprocessor with the current target positions. These comparisons are used to activate the correct solenoids to achieve the target positions.

Manual control of the drive motors (on the mobile unit) is made variable by mark/space modulation of the motor drive switching transistors. These mark/space modulation timings are derived by the program from an internal look-up table that gives the mark/space ratios for the left and right motors from the position of the panel Speed slider and the Steering pot. These timings are themselves also generated by the microprocessor.

RS232 input

To control the robot from an external computer, an RS232 input is provided. If the RS232 lead is plugged in when the unit is powered up, the unit will ignore the keyboard and wait for a command from an external computer.


A move command is simply sent as a string of ASCII characters. The format consists of an "M" followed by six pairs of hexadecimal digits (each pair representing a number between 0 and 255 — the desired position for each axis). The last pair is the jaw command, and should be 00 for "jaws open", and FF for "jaws closed", e.g. M8080808080FF will move all axes to a central position and close the jaws.

When the move has been completed the robot will send back a "*" down the RS232 line to inform this to the sending computer.

On five axis units, the format is the same, but the last-but-one pair of digits is ignored.

P.E. ROBOTS

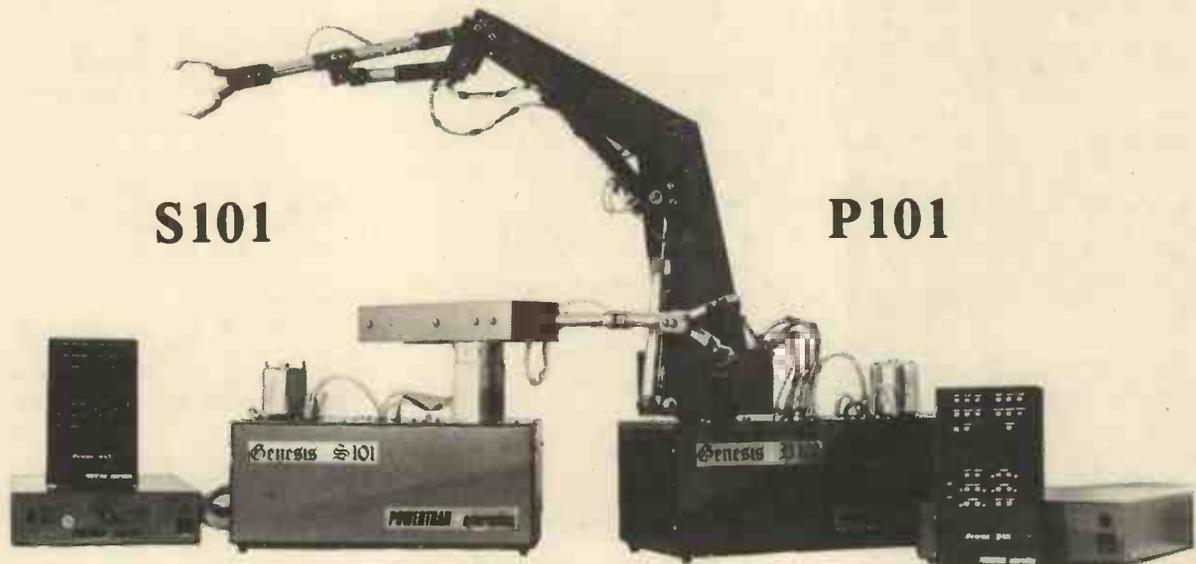This concludes the hardware and control of the robots. NEXT MONTH we embark on the software description and routines, and final constructions.



MICRO-BUS

Compiled by DJD.

THE TWO topics in this month's Micro-Bus show how micros can be used in amateur radio. The first program receives fax transmissions, and displays them on a computer screen. The second program acts as a Morse-code tutor, for those trying to learn Morse code. Both programs were developed by *Steve Platt*, a radio amateur in Cambridge (G6AZI).

RECEIVING FACSIMILE PICTURES

Pictures can be transmitted over channels normally used for speech, such as the telephone, or over the air by radio, using a system known as 'facsimile' or 'fax'. This system is used by radio amateurs to send diagrams such as weather maps and charts on the HF and VHF bands, but one problem faced by amateurs wishing to try their hand at fax is displaying the received pictures without expensive equipment.

The program to be described solves the problem by using the high-resolution four-colour graphics on an Acorn Atom computer to display fax transmissions on a TV screen straight off the air from a receiver. It was developed by *Steve Platt* of Cambridge (G6AZI), and what follows is based on his description.

"Radio amateurs generally use fax on the HF bands (short waves) where many commercial transmissions can be received. Fax is also used on the popular VHF 'two-metre' band where the calling frequency is 144.700MHz. A sample fax picture, of a street scene, is shown in Fig. 6; it is composed of three brightness levels, and has a total resolution of 128 x 192. It was received on 144.675MHz FM using the program of Fig. 7 with the receiver output connected directly to the Atom's cassette input!



Fig. 1. Facsimile picture decoded and displayed by the program of Fig. 2

```

10 DIM LL(18),JJ(3),B(100)
20 DIM D(100)
30 FOR N=0TO18; LLN=TOP; NEXT
40 FOR N=0TO3; JJN=TOP; NEXT
105 PRINT $12,"FAX"
110 PRINT "ENTER COUNT AND SYNC"
115 PRINT "TRY 77 & 8"
120 INPUT C,S
125 GOSUB 2000
130 FOR N=0 TO S; B?N=2; NEXT
140 B?(S+1)=0
150 FOR N=S+2 TO 100; B?N=3; NEXT
200 REM DO IT !
210 CLEAR4; COLOUR 1
220 DO
225 DO UNTIL?#B001<>#FF
230 ?#84=0; ?#85=#80; LINKJJ3
240 UNTIL 0
2000 REM - COUNT CYCLES
2004 PRINT $21
2005 FOR N=1 TO 2
2007 DIM P(-1)
2010 [
2020:LL1 LDA #0
2030 STA #82; LDA #C; STA #80
2035 LDA #1; STA #81
2040 LDA #820
2050 BIT #B002
2060 BEQ LL2
2070:LL4 DEC #80
2080 BEQ LL9
2090 NOP
2100 JMP LL10
2110:LL10 JMP LL11
2120:LL9 DEC #81
2130 BEQ LL3
2140:LL11 LDA #820
2150 BIT #B002
2160 BEQ LL6
2170 JMP LL15
2180:LL15 JMP LL5
2190:LL5 JMP LL4
2200:LL6 INC #82
2210 JMP LL2
2220:LL2 DEC #80
2230 BEQ LL12
2240 NOP
2250 JMP LL13
2260:LL13 JMP LL14
2270:LL12 DEC #81
2280 BEQ LL3
2290:LL14 LDA #820
2300 BIT #B002
2310 BNE LL7
2320 JMP LL16
2330:LL16 JMP LL8
2340:LL8 JMP LL2
2350:LL7 INC #82
2360 JMP LL4
2370:LL3 LDA #82
2380 RTS
2400:LL17 LDX #0
2410:LL18 LDA #C;STA #80
2420 LDA #1; STA #81
2430 JSR LL1
2440 STA D,X; INX
2450 CPX #101
2460 BNE LL18
2470 RTS
2500:JJ3 JSRLL1; CMP#S; BCC JJ3
2505:JJ2 JSRLL1; CMP#S; BCS JJ2
2510:JJ0 LDX #4
2520:JJ1 JSR LL1; TAY; LDA B,Y
2530 RORA; ROL#83; RORA; ROL#83
2540 DEX; BNEJJ1
2550 LDA#83; STA(#84,X); INC#84
2560 LDA#84; AND#31; BNEJJO
2570 LDA#84; BNE JJ3; INC#85
2580 LDA#85; CMP#898; BNE JJ3
2590 RTS
2960 ]
2970 NEXT N
2980 PRINT $6
2990 RETURN
3000 END

```

Fig. 2. Program for the Atom displays facsimile pictures

"The picture was transmitted (by G8RYL) using a surplus fax machine fed into the transmitter microphone socket. The picture is wrapped around a rotating drum, and scanned with a photocell. The photocell moves slowly along the drum to give a vertical scan, while the drum's rotation provides the horizontal scan. The output from the photocell is then used to vary the frequency of an oscillator with the brightness of the picture. Drum speeds of 60, 90, 120 and 240rpm are most popular; the program to be described works with 120rpm. The picture's "aspect ratio" is varied by setting the number of drum rotations for each inch that the photocell moves. Further details may be found in *Radio Communication*, August 1978, and *Wireless World*, December 1976 and March 1977.

PROGRAM DESCRIPTION

"The main task of the program is to determine the audio frequency of the incoming fax signal. This is done by counting "zero-crossings" during fixed intervals of time. The number of zero crossings is then related to a scale of brightness levels, and a point of the corresponding brightness is put on to the Atom screen by poking directly into the graphics memory.

"First the vectors and labels are declared, and the labels are cleared (lines 10 to 40). Variables C and S are parameters which can be varied to tune the program to the machine being received; the values given, C = 77 and S = 8, seem to work best. The time interval over which zero crossings are counted is determined by C, and S determines the number of zero crossings that correspond to the fax sync-pulse level; i.e. the lightest part of the picture. The call to subroutine 2000 in line 125 assembles the machine code; note that this code uses C and S as constants, so these must be set before assembly.

"Vector B is a look-up table of brightness values. If X zero-crossings are counted, the colour of the point plotted will be B?X. Values of 2, 0 and 3 correspond to white, grey and black respectively. The brightness levels are set up in lines 130 to 150, based on the value of S selected.

"The main program loop, in lines 210 to 240, first waits for a key-press; locations # 84 and # 85 are then pointed to the start of the screen memory (line 230), and the machine-code routine JJ3 fills the screen.

ASSEMBLER ROUTINE

"Lines 2000 to 3000 constitute the assembler routines to receive a fax transmission, and display it in three brightness levels on an Atom screen. Routine LL1, from 2020 to 2380, is the key subroutine and is actually

much simpler than it looks; it acts as a software frequency meter, counting the number of zero crossings on the cassette input in a fixed time interval.

"Each time the main loop is executed it reads the cassette input, and increments location # 82 if the input has changed. The main loop takes 32 usec, and is balanced with NOPs so that each decision branch takes the same number of cycles. The number of times the loop is executed is determined by locations # 80 and # 81; these are set to C in lines 2030 and 2035, and although in the present application C was only 77, a two-byte counter was used to allow expansion to longer measurement times. With this value of C the routine counts zero crossings for about 2.5 msec, before returning with number of zero crossings in location # 82.

"As a debugging aid, lines 2400 to 2470 will dump 100 samples of the input frequency in the vector D. Typing:

LINK LL17

followed by printing the values D?0, D?1 . . . D?100 will allow the input to be checked. If the values are not the range 7 to 12 the value of S may need to be changed.

DISPLAY ROUTINE

"The display routine, JJ3 in lines 2500 to 2590, is called from the main BASIC loop. It waits for the synchronising pulse which precedes each line of video information (lines 2500 and 2505), and then fills a line on the screen. To do this it calls the LL1 routine to sample the input frequency, then looks up the corresponding brightness value in vector B (line 2520). This is a 2-bit pixel value which is shifted into the screen memory via a work byte, # 83, in line 2530. When four pixels have been packed the byte is updated in the graphics area (line 2550). At the end of a line (when the address is a multiple of 32-line 2560) the program goes back to wait for another sync pulse.

"The remaining part of the routine updates the upper byte of the screen address, and checks for reaching the bottom of the screen, address # 9800 (line 2580).

POSSIBLE EXTENSIONS

"The facsimile system described above is similar to the slow-scan television (SSTV) system used by amateurs, employing modified TV cameras, and the same program has been used, with slight modification, to receive SSTV "conversations" on the HF bands. Since the sync levels are reversed, lines 2500 and 2505 should be exchanged, and the values of C and S may need to be altered.

"Thought is also being given to an Atom-based fax transmission system built around some sort of art/graphics sketchpad program. This would allow the user to sketch a pictorial reply to the received image on the Atom screen, using keyboard input.

MORSE-CODE TUTOR

Many radio amateurs are put off from using the short-wave bands because of the need to learn Morse code to obtain a licence, and the main problem is finding a source of slow Morse to learn from. The program for the Acorn Atom, shown in Fig. 3, acts as a Morse tutor by producing a continuous stream of letters in Morse code.

The Tutor program lets you learn a subset of the alphabet, starting with the letters which have the shorter codes. In addition, the speed and spacing of the Morse produced can be varied to cater for different abilities. The program presents letters in groups of five, separated by a single space. This is similar to the test format used in the amateur radio examination, and so the program can be used to test whether the required standard has been reached. The program can also be used to learn letters, by watching the words on the screen as the Morse is played.

Many people have their own theories as to the best way of learning Morse code. Generally it is thought to be better to hear the letters at full speed from the beginning. This way you identify the sound of each letter without thinking of a written pattern of dots and dashes, which can be a distraction when trying to gain speed! It is therefore best to start with the speed set to your target speed, and have extra time between letters, over and above the normal spacing. The Post Office test for radio amateurs requires a speed of 12 words per minute, where words are defined as having five letters; other tests may need less.

CODE STORAGE

The code for each letter occupies two bytes, in vectors C and L. The byte in C holds a binary sequence which gives the code for that letter, with '0' for a dot (short bleep) and '1' for a dash (long bleep), starting with the lowest bit. The byte in L gives the total length of the code; i.e. how many bits to use from C. As an example, take the letter Z, which is letter 26. The value of L?26 is 4, so taking the bottom 4 bits of C?26 we have 0011. Thus the Morse code for Z is:

— — . .

Only the codes for the letters are stored, although the program could easily be extended to numerals and punctuation.

PROGRAM DESCRIPTION

Lines 10 to 25 allocate space for vectors, C, L, S, and A, for labels VV0 to VV8, and for the machine code at P. The values of C and L for the Morse codes of the letters A to Z are set up in lines 100 to 170, and the assembly code is then assembled (line 180). The string S contains the alphabet in the order of shortest letters first; i.e. in rough order of difficulty. The program presents subsets of the alphabet starting with the first letter, S?1.

The main control loop of the program, from line 200 to line 295, determines how the codes are presented, and this could be altered to suit individual requirements. For example, the program could present codes one letter at a time, with you typing in your guess. K determines how many different letters from string S are being taught; thus, with K = 3, only letters E, T, and A are presented. G can be set to a value greater than 0 to give extra spaces between letters when learning (line 205). The program then presents a total of 24 'words', each of which is a 5-letter group (lines 210 and 220) picked at random from the first K letters in string S (lines 240 and 250). Each letter is 'bleeped' in Morse code by subroutine 'c' (line 260), followed by any extra spaces wanted between letters (line 265). After each word

there is an extra space (line 275), and the word is printed to the screen (line 280).

BLEEP ROUTINE

The assembler code in lines 900 to 995 of Fig. 3 is a routine to bleep the Atom's speaker, and is similar to the one in the Atom operating system. Location # 80 gives the pitch of the tone and location # 81 the length. The same routine is used for dots, dashes, and gaps, with location # 82 set to 4 for a tone and to 0 for silence; this ensures that tones and gaps are all exactly the right length.

An additional assembler routine at VV3 (line 982) gets the ASCII value of the next key pressed in location # 83.

```

5 PRINT $12,"MORSE TUTOR"
10 DIM C(26),L(26),S(27)
25 DIM A(5),VV(8),P(-1)
100 REM SETUP TABLES
110 C10=#5010200;L10=#4040200
120 C14=#3040001;L14=#3040103
130 C18=#50E0000;L18=#3040204
140 C12=#7010302;L12=#3020204
150 C16=#0020B06;L16=#3030404
160 C120=#6080401;L120=#3040301
170 C124=#30D09;L124=#40404
180 GOSUB 900; REM ASSEMBLE BLEEP
190 SS=" ETANIMSRWDGKHVFLPJXKCYZQ"
195 INPUT "SPEED (WORDS PER MINUTE)",W
196 T = 1059/W - 10
197 IF T<3:255 THEN PRINT"TOO SLOW";GOTO 195
200 INPUT "HOW MANY LETTERS DO YOU WANT TO LEARN",K
205 INPUT "HOW MANY SPACES BETWEEN LETTERS",G
210 FOR W=1 TO 24
220 FOR J=1 TO 5
240 I = ABS(RND)*8K+1
250 A?J=S?I; I=A?J - 64
260 GOSUB C
265 IF G>0 THEN I=0;FOR B=1 TO G;GOSUB c;NEXT B
270 NEXT J
275 I=0; GOSUB C
280 FOR J=1 TO 5:PRINT A?J;NEXT J
290 PRINT " "; NEXT W
295 GOTO 200
900 P.$1;I
910:VV0 LDA #B002
915 LDY #81
920:VV1 LDX #80
930:VV2 DEX
940 BNE VV2
950 EOR #82
960 STA #B002
965 DEY
970 BNE VV1
980 RTS
982:VV3 JSR #FFE3; STA #83; RTS
985); P.$6
990 ?#80-200
995 RETURN
1000:REM O/P MORSE CHAR "I"
1003 IF I<10R 1>26;?#81-2?T;?#82=0;LINK VV0; RETURN
1005 M=C?I; IF L?I<1 RETURN
1010 FOR N=1 TO L?I
1020 IF M?2=1 GOTO b
1025 ?#81-T
1030 ?#82=4; LINK VV0
1040 GOTO d
1050b ?#81-3*T
1052 ?#82=4; LINK VV0
1060d M=M/2
1065 ?#81=T
1070 ?#82=0; LINK VV0
1075 NEXT N
1080 ?#81-2*T
1085 ?#82=0; LINK VV0
1090 RETURN

```

Fig. 3. Morse-code tutor for the Atom

MORSE CODE OUTPUT

The final routine, 'c', outputs the code for the letter in I, where I = 1 gives A, up to I = 26 for Z; any value outside this range is treated as a space (inter-letter gap). The routine uses vectors C and L, set up as described above. Each dot is a bleep of length T (lines 1025-1040), and each dash a bleep of length 3*T (lines 1050-1052). There is a gap of length T between each dot or dash (lines 1065-1070), and a gap of length 3*T at the end of the letter (lines 1065-1085).

This routine could form the basis of a program to generate automatic Morse code from messages typed in at the keyboard. However, writing the complementary program to receive and decode Morse is a much tougher problem, and this would provide an interesting challenge to any radio amateurs with micros.

TV CAMERA

PHILLIP GAFFNEY

Part 3

IN THIS, the final part of the camera, we first catch up on some Logic Board constructional notes. The f.e.t. TR20 (VN66AF) should have its heatsink doubled over, as shown in Fig. 3.1, to clear its headroom.

Scrape a small amount of track off the top-right hole where the coil is situated on the p.c.b. Link the coil to the casing as shown in Fig. 3.2. There are two links, and C50 (15 μ /16V) to be mounted. The coil board is then mounted with C50 going to the lower part of the board (near IC3).

FINAL ASSEMBLY INSTRUCTION

Having completed the construction of the individual boards of the camera, the final assembly consists of fitting the boards together and making the necessary interconnections. The vidicon tube and scan coil assembly is supplied complete with connecting wires to make assembly simpler.

The individual component boards may be sent for testing and setting up to Security Electronics and Engineering (Printoid Ltd.), 20/21 Alfric Square, Woodston, Peterborough. ☎ 0733 329111. All components are available separately. Technical and supply problems should be sent direct to: PE/Seescan Camera Project, Security Electronics and Engineering, 20/21 Alfric Square, etc.



Fig. 3.1. Reshaping the heatsink of TR20

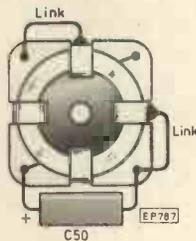


Fig. 3.2. Coil sub-assembly

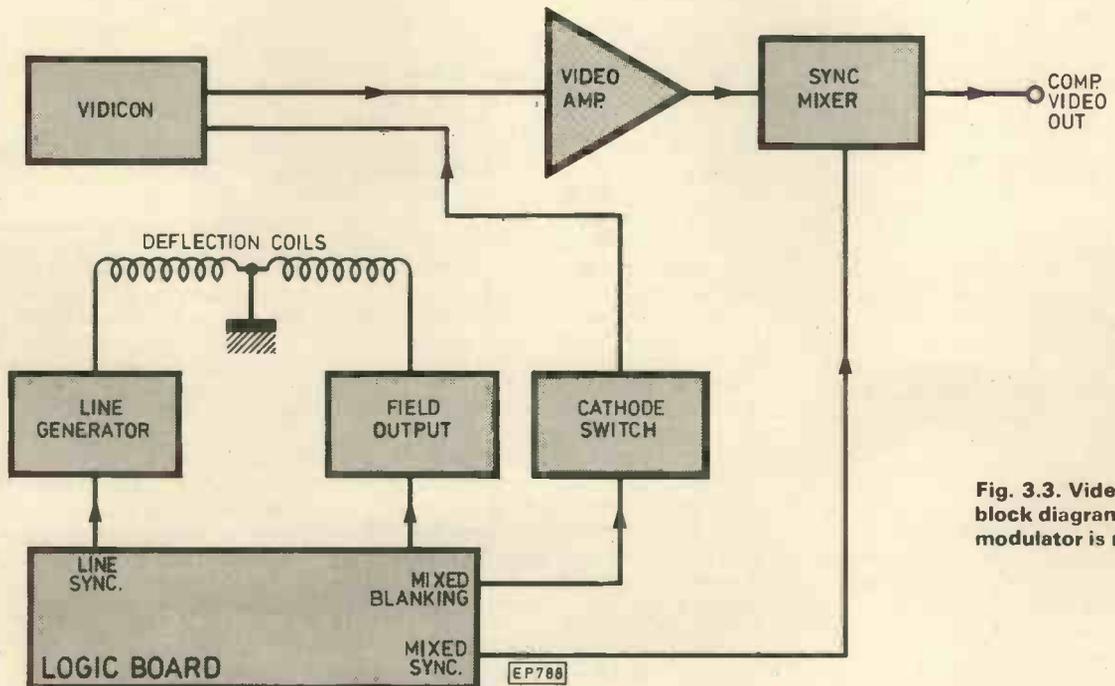


Fig. 3.3. Video and logic block diagram. The UHF modulator is not shown

Connect the four boards together using the varelco connectors—these are polarised so that the connectors will only mate correctly in one position. Check that all connectors are making good contact.

Mount the inner rear panel to the rear of the camera chassis using four M3 6mm screws. Mount the co-axial socket on the inner face of the rear panel using two counter-sunk M3 screws, one tag washer and two M3 nuts. The tag washer fits on the screw in the red hole.

Using heavy gauge tinned copper wire, connect the co-axial socket core and the tag washer to the points indicated on the diagram of Fig. 3.4.

Connect the three wire plug from the video board to the logic board so that the black wire is near pin 8 or IC9 on the logic board.

Mount the tube/coil assembly onto the front of the camera chassis using four M3 20mm screws with M3 nuts, ensuring that the coil and tube are orientated as shown in Fig. 3.5.

Plug the scan coil connector onto the logic board so that the blue wire is nearest to the scan coils.

Fit the tube base connector to the tube ensuring that the short tube pin fits in the unnumbered hole of the connector.

Solder the earthing connections from the scan coil assembly to the earth rail on the video board, as shown in Fig. 3.6.

Solder the screened target connection to the video board as shown.

Screw the lens into the front of the camera. The camera chassis is now complete.

SETTING UP

The general description of the camera electronics, and of the methods of setting up have been left until last, as it was felt that it would be easier to visualise the camera as a whole once the individual sub-assemblies had been constructed. In making final adjustments to the camera, it is essential that a clear understanding of the function of each control has been achieved.

We hope to show how these units inter-connect and work together to form a high quality black and white television camera.

VIDICON TUBE

The inverter and high voltage power supply boards provide all the necessary dc voltages for the correct operation of the vidicon tube. When correctly adjusted, the vidicon will produce a voltage at its target ring which will be proportional to the intensity of light falling on the centre of the target window. In the absence of scanning wave-forms, the electron beam will produce a focussed spot near the centre of the target window. *On no account should the tube ever be allowed to operate in this fashion as it will result in a spot being burnt onto the vidicon target.*

If the video amplifier were connected to the target ring, it would amplify this smaller voltage, and an amplified signal would be fed to the UHF modulator. The purpose of the logic/scan board is twofold. First, it scans the electron beam across the target of the vidicon tube. Line scan moves the beam from left to right, field scan from top to bottom. These two scan waveforms are precisely locked together, and are carried out at the same speed as the electron beam moves across the monitor screen. Therefore, the voltage at the target ring of the vidicon will be continually changing—at any instant being proportional to the intensity of light at a particular spot over the surface of the vidicon target upon

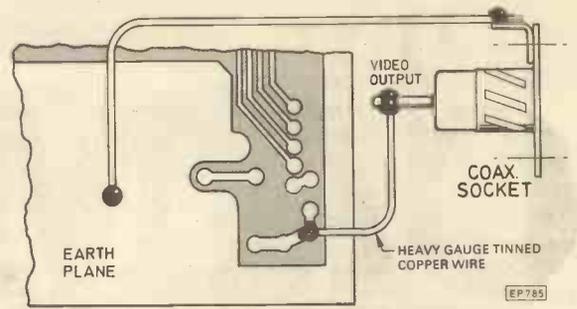


Fig. 3.4. Connection to the VHF modulated video output socket

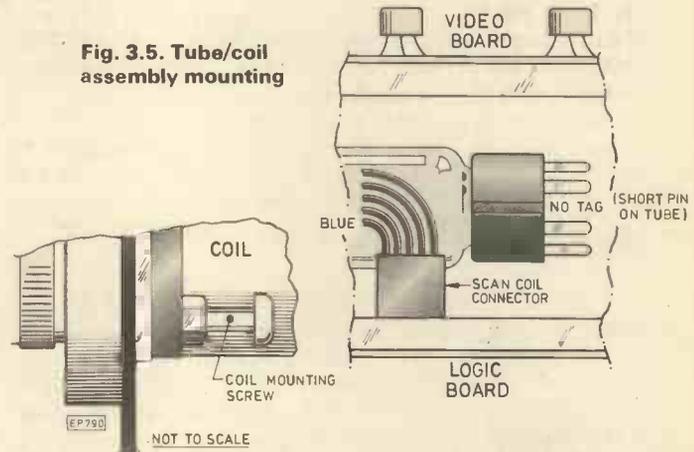


Fig. 3.5. Tube/coil assembly mounting

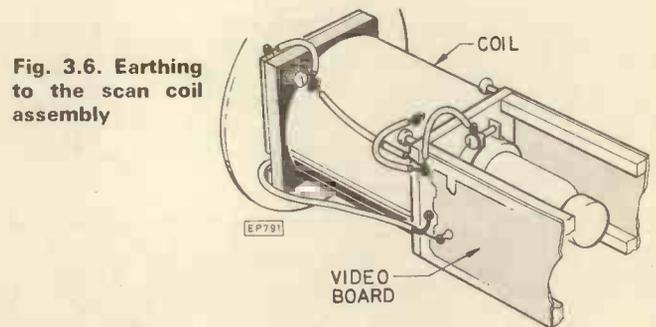


Fig. 3.6. Earthing to the scan coil assembly

which the optical image of the scene is focussed. We now therefore have picture information available at the output of the video amplifier ready to send to the monitor. However, at the moment, the scanning of the vidicon tube is not linked to the scanning of the monitor cathode ray tube. We need to ensure that when the camera starts a scan at the top left hand corner of the picture the monitor is also scanning at the top left hand corner. To do this we send out a pulse (called a sync. pulse) at the start of each line and field. The monitor is forced to keep in step by these pulses, ensuring that a stable fully locked picture is obtained. Our line and field sync. pulses are obtained from the logic board, and are mixed with the video signal in the video amplifier. The waveform handled by the last two stages of the video amplifier, and then fed to the modulator is a composite containing both the video signal and synchronisation pulses. As mentioned in part four, blanking signals are also added to prevent the electron beam retracing its steps across the picture when it rapidly flies back to start the next line or field. These signals

fed to the cathode of the vidicon tube cut off the electron beam between lines and at the end of fields preventing it reaching the rear of the target surface.

In testing the camera, it is important to ensure systematically that each of the sub-assemblies are correctly working.

PRESET CONTROLS	
Logic Board	Master clock oscillator Width Magnetic focus Height
Video Board	Automatic light control Pedestal Sync DC level
High Voltage Power Supply Board	Target Beam Electrostatic focus

SETTING UP

Before applying power, turn all presets to midway position, with the exceptions of beam current, target voltage and automatic light control. The beam control should be adjusted for maximum negative voltage on its wiper, the target control turned fully anticlockwise until zero volts is on the wiper. The automatic light control should be fully anticlockwise. With these settings, the vidicon tube is fully cut off, and it will not be possible to damage the face of the tube in the event that the scan waveforms are incorrect.

Switch camera on; line frequency whistle should be heard immediately from the inverter transformer; if not, switch off and recheck connections. Set the height and width controls to maximum, i.e. fully clockwise. At this stage, if the camera is connected to a TV set tuned to channel 36 a pattern of lines should be seen on the screen. Adjust the master oscillator control to stabilise the pattern as far as possible. If no pattern is visible, just a blank, noise free raster, try altering the position of the pedestal black level control. Place a finger on the target connection; a great deal of noise (random patterns) should be visible on the TV screen. Adjust the pedestal control for the strongest display. Use an oscilloscope to check that correct scan wave forms are present at coil plug. See Fig. 2.11.

Set beam current control to give 30V at its wiper, and target control to $\frac{3}{4}$ maximum. By adjusting the beam control carefully, it should now be possible to detect some sensitivity to light when the camera lens is wide open. Now set the camera lens to about f.8 in normal illumination, then adjust the electrostatic focus control to give the crispest image. Aiming at an object 2 metres away, with a lens set at 2 metres, slacken off the tube retaining clamp and slide the tube carefully backwards and forwards to obtain the sharpest focus. Adjust the height and width controls until the edges of the picture just exclude the target windows; readjust the electrostatic focus, and beam controls, for the best picture. Trim the pedestal control for best picture with no crushing of dark greys into blacks. Adjust sync. control for best contrast and stability; or use oscilloscope and set up video output wave-form to CCIR standard. Adjust all the presets one at a time for optimum picture quality. Finally, advance the automatic light control preset until it just has an effect on the picture; back off this setting slightly. This is the correct setting for normal use. ★



PATENTS REVIEW...

JAPANESE IDEAS

The Nissan Motor Company of Japan has been toying with the idea of building a factory in Britain to make cars. Already the company is filing patents in Britain. The latest (British patent application 2 074 313) suggests an interesting new application from Nissan for light links.

Currently any switches on the steering wheel of a motor car, for instance the horn button, produce electrical control signals. These are fed to the main car wiring harness via electro-mechanical slip rings between the moveable steering wheel and stationary steering wheel column. But slip rings suffer from wear. Also the contacts are bulky, and this limits the number of connection paths and thus the number of

switches which can be accommodated on the steering wheel. Nissan proposes replacing this electrical path with a light path.

Figure 1 shows the basic layout. A bank of switches 17 on the steering wheel 13 controls the engine or ancillary equipment. The electrical output of the switch bank is encoded at 21 to control the pulsing of a LED 22. The pulsed light is beamed at light-transmitting ring 23, made for instance of acrylic or polycarbonate. Light pulses emerging from the ring are picked up by photo-diode 24 which is secured to the steering wheel column. The electrical output diode 24 is amplified at 25, shaped at 26, decoded at 27 and fed to drive circuit

28 for control of the appropriate car function. This could for instance be the wave-band change and volume control of a radio.

Light fibre links can be used to improve optical coupling. The ring 23 is shaped to allow light from the diode to propagate inside the ring and escape only at the face adjacent the photo sensor.

The transmission code relies on pulses of 2.78 milli/sec width at a frequency of 180Hz and a duty factor of 50%. This enables a full message to be transmitted in 15 millisecc. Because the switch is likely to be depressed for at least 100 millisecc, each coded message is transmitted at least twice for safety.


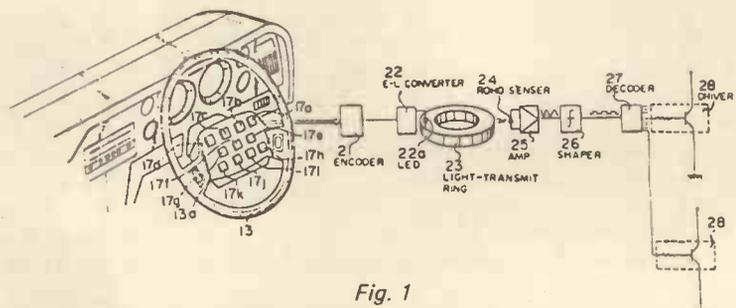


Fig. 1

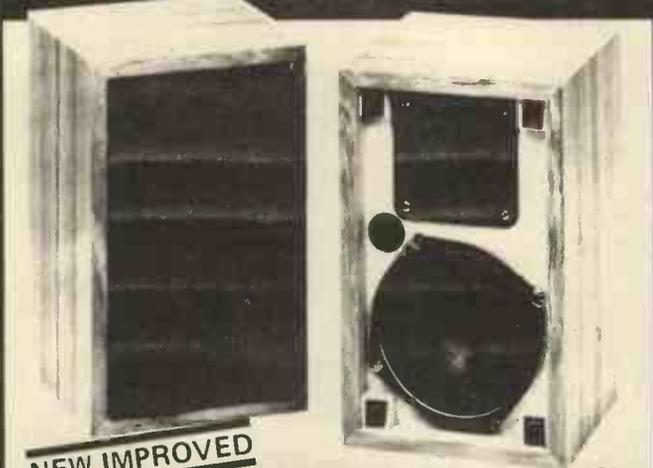Has seven years of success gone to our heads?



NEW IMPROVED

MINIMAX 2

With the Minimax II, Videotone revolutionised the market by establishing an opening for small, high quality speakers. Natural evolution has brought about the new Minimax 2, retaining all the qualities of clarity and sensitivity. This ideal combination of size and performance is a proven success, acclaimed by the press and public for seven years.

POPULAR HI-FI

"Switching to the Minimaxes' from any of the others produced an open and natural sound as though something had been taken away. It had, the colouration had gone." Comparative test OCTOBER 1975.

HI-FI ANSWERS

Their modest appearance and price disguise their startling abilities. Never have we heard such a small speaker sound so big!" JANUARY 1975.

PRACTICAL HI-FI & Audio

"The depth, clarity and openness of sound produced is quite astonishing". JUNE '75

WHAT HI-FI

"... the ability of the Mini-

max to take a lot of power and still sound good could be decisive" — Comparative test, APRIL 1977.

PRACTICAL HI-FI

The little Videotone scored highly for such a small inexpensive loudspeaker". JANUARY 1981.

Specification:

Recommended amplifier power: 10 to 40 watts rms into 8 ohms.
Frequency Response: 80Hz — 20KHz±5dB.
Finish: natural teak, veneer with black frets.
Size: 10 7/8" high, 6 3/4" wide, 7 1/2" deep.
Weight: 4.1 Kgs (9 lbs) each.

ONLY £69.95 A PAIR

- We welcome callers to our South London Showroom for demonstrations.
- Enquiries and information phone: 01-690 8511, Ex. 32.
- All products are only available direct or from selected authorised dealers throughout the U.K.

VIDEOTONE 98 CROFTON PARK ROAD LONDON SE4.

Send for our free brochure and details of outlets in the U.K.

Post to: Videotone, Crofton Park Road, London SE4. PE3

NAME _____

ADDRESS _____

ILP TOROIDALS UNBEATABLE VALUE FOR MONEY!

New production capacity at Canterbury has increased our range, decreased our prices, improved our special customer design service. Choose from toroidal transformers in a range of 98 types.



Order using the FREEPOST coupon below.

Trade enquiries are welcome.

Supplied with rigid mounting kit with centre bolt, steel and neoprene washers. GUARANTEED 5 YEARS.

TYPE	SERIES No	SECONDARY Volts	RMS Current	PRICE inc. VAT	PRICE ex VAT
30 VA 10 x 30mm 0.45 Kg Regulation 18"	1X010	6+6	1.50	£5.78 + £0.870 P.P.	£4.48 + £1.00 P.P.
	1X011	9+9	1.66		
	1X012	12+12	1.74		
	1X013	15+15	1.00		
	1X014	18+18	0.83		
	1X015	22+22	0.68		
50 VA 80 x 35mm 0.9 Kg Regulation 13"	2X010	6+6	1.16	£5.83 + £1.10 P.P.	£4.93 + £1.10 P.P.
	2X011	9+9	2.77		
	2X012	12+12	2.08		
	2X013	15+15	1.66		
	2X014	18+18	1.38		
	2X015	22+22	1.13		
80 VA 90 x 30mm 1 Kg Regulation 12"	3X010	6+6	6.64	£6.51 + £1.43 P.P.	£5.47 + £1.43 P.P.
	3X011	9+9	4.44		
	3X012	12+12	3.33		
	3X013	15+15	2.66		
	3X014	18+18	2.22		
	3X015	22+22	1.81		
120 VA 90 x 40mm 1.2 Kg Regulation 11"	4X010	6+6	10.00	£7.55 + £1.43 P.P.	£6.38 + £1.43 P.P.
	4X011	9+9	6.66		
	4X012	12+12	5.00		
	4X013	15+15	4.00		
	4X014	18+18	3.33		
	4X015	22+22	2.77		
160 VA 110 x 40mm 1.8 Kg Regulation 9"	5X010	12+12	8.89	£9.97 + £1.43 P.P.	£8.44 + £1.43 P.P.
	5X011	15+15	6.66		
	5X012	18+18	5.33		
	5X013	22+22	3.70		
	5X014	27+27	3.00		
	5X015	33+33	2.56		
225 VA 100 x 45mm 2.7 Kg Regulation 7"	6X010	12+12	9.38		
	6X011	15+15	7.50		
	6X012	18+18	6.25		
	6X013	22+22	5.11		
	6X014	25+25	4.50		
	6X015	30+30	3.75		
300 VA 110 x 50mm 2.6 Kg Regulation 6"	7X010	15+15	10.00		
	7X011	18+18	8.33		
	7X012	22+22	6.82		
	7X013	25+25	6.00		
	7X014	30+30	5.00		
	7X015	35+35	4.28		
500 VA 140 x 60mm 4 Kg Regulation 4"	8X010	25+25	10.00		
	8X011	30+30	8.33		
	8X012	35+35	7.14		
	8X013	40+40	6.25		
	8X014	45+45	5.56		
	8X015	50+50	5.00		
625 VA 140 x 75mm 5 Kg Regulation 4"	9X010	30+30	10.41		
	9X011	35+35	8.97		
	9X012	40+40	7.81		
	9X013	45+45	6.94		
	9X014	50+50	6.25		
	9X015	55+55	5.68		

IMPORTANT: Regulation — All voltages quoted are FULL LOAD. Please add regulation figure to secondary voltage to obtain full load voltage.

The benefits of ILP toroidal transformers

ILP toroidal transformers are only half the weight and height of their laminated equivalents, and are available with 110V, 220V or 240V primaries coded as follows:

For 110V primary insert "0" in place of "X" in type number.

For 220V primary (Europe) insert "1" in place of "X" in type number.

For 240V primary (UK) insert "2" in place of "X" in type number.

How to order Freepost:

Use this coupon, or a separate sheet of paper, to order these products, or any products from other ILP Electronics advertisements. No stamp is needed if you address to Freepost. Cheques and postal orders must be crossed and payable to ILP Electronics Ltd. cash must be registered. C.O.D. — add £1 to total order value. Access and Barclaycard welcome. All UK orders sent within 7 days of receipt of order for single and small quantity orders.

Also available at Electrowave, Maplin, Marshalls, Technomatic and Watford Electronics. ILP Electronics Ltd., Freepost 2, Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent.

Please send me the following ILP modules PE 1/3

Total purchase price _____

I enclose Cheque Postal Orders Int. Money Order

Please debit my Access / Barclaycard No. _____

Name _____

Address _____

Signature _____

Post to: ILP Electronics Ltd, Freepost 2, Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent, England. Telephone (0227) 54778 Technical (0227) 64723 Telex 965780.



Semiconductor UPDATE...

FEATURING

LM1035

99000 SERIES

8X60

R. W. Coles

REMOTE CONTROL

In days of yore, when I ran a sort of audio amplifier assembly facility in my back shed, I became well versed in the tricky business of connecting sensitive volume, bass, and treble pots into the rest of the circuitry using carefully screened and earthed leads. Of course, these amplifiers used transistors or even valves (Ah! Pentodes!) which always needed an element of black-magic to ensure success anyway, but in today's chip orientated circuitry, electronic sorcery at the soldering iron stage seems out of place somehow. My own special witches' brew for amplifier control connections has been rendered obsolete overnight by a new chip from National, the LM1035.

The trouble with the old method of connecting amplifier controls was the fact that the pots had to be on the front panel while the amplifier itself was several inches away, and the interconnections made marvellous transmitting or receiving aerials for cross-talk, noise, mains hum, and even Radio Luxembourg. What National have done is to provide electronic control circuits which are controlled directly by d.c. voltage levels, so that the sensitive audio signal path never has to leave the chip. Pots are still used of course, but now they are used to get, not a signal level, but a d.c. level which can be slugged with a big electrolytic capacitor to remove any stray signals which could interfere. Inside the chip are two signal channels (for stereo) which have individual electronic attenuators for gain and balance, and individual voltage controlled filters for treble and bass control with each feature being controlled by a single voltage level so that there is no longer a need for expensive ganged pots!

The LM1035 has a distortion level of 0.02% at 1kHz and gives a volume control range of 80dB with 22dB of balance range. Maximum bass and treble boost or cut is 15dB, channel tracking is good to within 1dB and channel separation is -60dB at 1kHz. An on-chip voltage regulator is provided to allow the device to operate on unbalanced supply rails of from 8 to 20 volts, and the whole thing lives in a tiny 20 pin package.

SUPERCHARGED 9900

When Texas Instruments introduced the first true 16 bit microprocessor, the 9900, they claimed that it spelled "The end of the two-bit eight-bit" and sat back to watch their tall-in-the-saddle processor steal sockets from Intel and Motorola who were then still clinging to their puny 8 bit devices. Unfortunately the market was not really ready for a 16 bit chip, and although the 9900 was reasonably successful, it cer-

tainly did not sweep the other 8 bit chips off the board, and even found itself a poor second when Intel, Zilog, and then Motorola introduced their own 1000 series 16 bitters several years later.

Well Texans don't take a licking easily, and so after a long cool analysis of the opposition, Texas have supercharged their 9900 design and brought out a new bit slinger family which appears to have the drop on those upstarts from the competition. Their new chip is still a sixteen biter and is downwards compatible with the instruction set of the 9900, but there the similarity ends because the 99000 series offers some real innovations which increase its speed and power far beyond that of its ancestor and even beyond the fast guns of the Motorola 68000. First to hit the streets will be the 99105 which has 82 basic instructions including multiprecision arithmetic, stack operations, memory bit manipulations, and parallel I/O instructions to overcome the limitations of the weird serial-only scheme of the 9900. Next will be the 99110 which has the great additional feature of an on-chip floating point arithmetic library which allows it to add, subtract, multiply, divide, move and convert real variables in the IBM format, a feat which has hitherto required substantial external software.

Fundamental to all members of the new processor family will be a clock speed of 24 MHz (almost v.h.f.l) which is twice as fast as the competition and means that with a memory cycle time of just 167 nS it will be necessary to choose the faster memory chips to take advantage of the power available. Inherent in the architecture of the family is a main memory address range of 256K bytes, and a separate "Macro-Store" address range of 120K bytes which can be used to augment the instruction set of the basic processor without the need to use main memory. The 99110 has its floating point arithmetic instructions implemented in Macro store space and actually uses a special on-chip 1K ROM and 32 byte RAM for this purpose. In the future other family members will use this same on-chip store to provide other high level features such as a real-time operating system or special I/O control routines. Unlike the 9900 which used a monster 64 pin package, the first members of the 99000 family both use 40 pin packages and have multiplexed data and address buses to suit.

FIFO

If you have a pet micro with a printer you probably get frustrated waiting for it to output listings at a rather pedestrian rate, during which it studiously ignores its keyboard and refuses to do anything else. One way

round this problem is to create a spooler program which runs under interrupt control to give apparently simultaneous service to both the printer and the keyboard so that you can go on typing in more code while the listing is printed. This scheme relies on the fact that it takes a short time to send a character to the printer but it takes a much longer time for the printer to actually print it. Since the micro is only involved in the sending operation the spare time can be used to service other tasks.

Unfortunately, all the spooler programs I have seen implemented on micros have suffered from shortcomings such as missed keyboard characters while printing, and of course there is the complication of running under interrupt control which needs careful attention while writing programs. A much simpler solution is possible which is used already on many printers such as the Nascom Imp and involves the use of a character buffer store implemented in hardware and not under the control of the microcomputer itself. In this case the micro "sees" an apparently very fast printer and dumps whole pages of text in next to no time. If the listing will fit entirely within this print buffer then no waiting is involved, and with memory prices dropping all the time a big print buffer looks economically feasible.

The buffer can be fitted between a micro and a printer, and needs to be organised as a FIFO (First In First Out), which raises the problem of how to control the two memory address pointers required to control writing at one rate and reading at a different rate. The Nascom printer uses a microprocessor to control this feature, but this starts to look a bit complicated for a stand alone buffer unit which is why, to my knowledge, no designs have been published. Fortunately the concept has now become much more practical thanks to a new chip from Signetics called the 8X60 FIFO controller.

This 28 pin device contains all the arbitration and control logic and two 12 bit address pointer registers to handle a buffer RAM array of up to 4K characters, quite adequate for the majority of day to day printouts. If you used a couple of 2K by 8 static RAMs you could make the heart of a print buffer with just three chips, with additional devices probably required to handle interfacing to the micro and the printer. The exact form of any interface would depend upon whether serial or parallel drive is required. In the case of a serial in-serial out link two UARTs would be needed, but a Centronics parallel interface would be much simpler.

In addition to Read and Write strobe inputs and address outputs, the 8X60 also has outputs to say whether the buffer is full, half full, or empty.

TRAIN FOR SUCCESS

in Radio, Television & Electronics

ICS have helped thousands of ambitious people to move up into higher paid more secure jobs in the field of electronics — now it can be your turn. Whether you are a newcomer to the field or already working in the industry, ICS can provide you with the specialised training so essential to success.

Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful, is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

Telecommunications Technicians
Radio, T.V. Electronics Technicians
Radio Amateurs
Electrical Installation Work

Diploma Courses

Colour T.V. Servicing
CCTV Engineering
Electronic Engineering & Maintenance
Computer Engineering and Programming
Radio, T.V. and Audio, Engineering & Servicing
Electrical Engineering, Installations & Contracting

Other Career Courses

A wide range of other technical and professional courses are available including GCE.

FREE BOOK

Post this coupon or 'phone today for free Electronics careers guide.

Name _____

Address _____

Age _____

ICS

To ICS, Dept 273S, Intertext House,
London SW8 4UJ
or telephone 01-622 9911 (all hours)

YOU CAN'T BEAT ILP BIPOLAR POWER AMPS FOR POWER AND PRICE

Get maximum power at minimum price, yet still with hi-fi specifications and a wide choice of outputs. ILP Bipolar power amps, now with or without heatsinks are unbeatable value for domestic hi-fi — but for disco, guitar amplifiers and PA choose the new range of heavy duty power amps, again with or without heatsinks, with protection against permanent short circuit, added safety for the disco or group user. Connection in all cases is simple — via 5 pins.



Every item has a 5 year no quibble guarantee and includes full connection data. So send your order FREEPOST today!

Load impedance, all models, 4 ohm — infinity. Input impedance, all models 100k ohm. Input sensitivity, all models, 500 mV. Frequency response, all models 15Hz-50kHz-3db.

BIPOLAR Standard, with heatsinks

Model No.	Output power Watts rms	DISTORTION		Supply voltage Typ/Max	Size mm	Wt gms	Price inc VAT	Price ex VAT
		T.H.D. Typ at 1kHz	I.M.D. 50Hz/7kHz 4:1					
HY 30	15w/4-8Ω	0.015%	<0.006%	±18±20	76 x 68 x 40	240	£8.28	£7.29
HY 60	30w/4-8Ω	0.015%	<0.006%	±25±30	76 x 68 x 40	240	£9.58	£8.33
HY 120	60w/4-8Ω	0.01%	<0.006%	±35±40	120 x 78 x 40	410	£20.10	£17.48
HY 200	120w/4-8Ω	0.01%	<0.006%	±45±50	120 x 78 x 50	515	£24.39	£21.21
HY 400	240w/4Ω	0.01%	<0.006%	±45±50	120 x 78 x 100	1025	£36.60	£31.83

BIPOLAR Standard, without heatsinks

HY 120P	60w/4-8Ω	0.01%	<0.006%	±35±40	120 x 26 x 40	215	£17.83	£15.50
HY 200P	120w/4-8Ω	0.01%	<0.006%	±45±50	120 x 26 x 40	215	£21.23	£18.46
HY 400P	240w/4Ω	0.01%	<0.006%	±45±50	120 x 26 x 70	375	£32.58	£28.33

Protection: Load line, momentary short circuit (typically 10 sec). Slew rate 15V/μs Rise time: 5μs, S/N ratio 100db. Frequency response (-30dB): 15Hz-50kHz. Input sensitivity 500mV rms. Input impedance 100kΩ. Damping factor (8Ω/100Hz)>400.

ILP Electronics Ltd, Freepost 2, Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent. HEAVY DUTY with heatsinks

Model No.	Output power Watts rms	DISTORTION		Supply voltage Typ/Max	Size mm	Wt gms	Price inc VAT	Price ex VAT
		T.H.D. Typ at 1kHz	I.M.D. 50Hz/7kHz 4:1					
HD 120	60w/4-8Ω	0.01%	<0.006%	±35±40	120 x 78 x 50	515	£25.85	£22.48
HD 200	120w/4-8Ω	0.01%	<0.006%	±45±50	120 x 78 x 60	620	£31.49	£27.38
HD 400	240w/4Ω	0.01%	<0.006%	±45±50	120 x 78 x 100	1025	£44.42	£38.63

HEAVY DUTY without heatsinks

HD 120P	60w/4-8Ω	0.01%	<0.006%	±35±40	120 x 26 x 50	265	£22.82	£19.84
HD 200P	120w/4-8Ω	0.01%	<0.006%	±45±50	120 x 26 x 50	265	£27.17	£23.63
HD 400P	240w/4Ω	0.01%	<0.006%	±45±50	120 x 26 x 70	375	£39.42	£34.28



Protection: Load line, PERMANENT SHORT CIRCUIT (ideal for disco/group use should evidence of short circuit not be immediately apparent). The Heavy Duty range can claim additional output power devices and complementary protection circuitry with performance specs as for standard types.

How to order Freepost: Use this coupon, or a separate sheet of paper, to order these products, or any products from other ILP Electronics advertisements. No stamp is needed if you address to Freepost. Cheques and postal orders must be crossed and payable to ILP Electronics Ltd; cash must be registered. C.O.D. — add £1 to total order value. Access and Barclaycard welcome. All UK orders sent post free within 7 days of receipt of order.

Please send me the following ILP modules

PE 2/3

Total purchase price

I enclose Cheque Postal Orders Int. Money Order

Please debit my Access/Barclaycard No. _____


Name _____

Address _____

Signature _____

Post to: ILP Electronics Ltd, Freepost 2, Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent, England
Telephone (0227) 54778 Technical (0227) 64723; Telex 965780

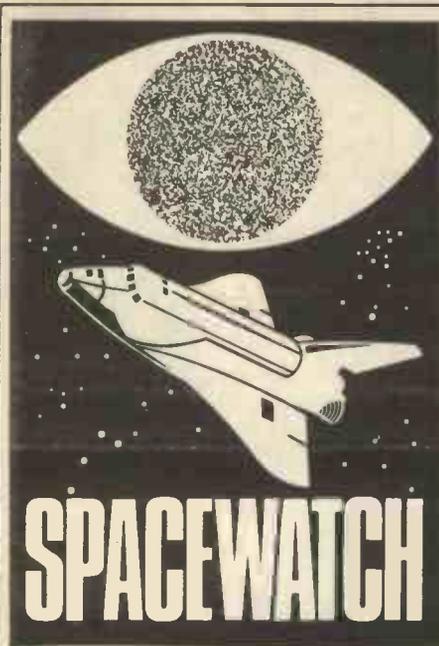ILP ELECTRONICS LTD
STAY AHEAD. STAY WITH US



FRANK W. HYDE

TIME FOR DATA PROCESSING

A major problem has been forcing its attention upon the groups who examine and analyse the data from satellites and probes. As usual the basic delay is funding. The amount of data has been so great that a very systematic priority clamp has had to be imposed upon some important sections of this work. It is of course readily understood that certain political requirements are involved and what might be considered by many of us as of humanitarian areas of priority are only of secondary consideration. With the present recession brought about indeed by the wrong priorities in many cases it could be deemed prudent to take an honest look at the terms of priorities. This requires a state of mental honesty extremely difficult to achieve when judged by action. A great many researchers all over the globe are seeking ways to improve the lot of mankind but work under conditions that demand for the continuance of their activities a constant campaign of begging donations from private resources for the funds to continue. So the inverse spiral of illogical thought publicly eulogises the endeavours of those engaged in these humanitarian works but denies them at the same time the means to forward them.

Now is the time to remember that the whole Earth and its environs is a system which is self generating or perhaps more correctly, regenerating and that every individual part is also the whole. Only now are some of the answers beginning to emerge. Much of the data could come from the environment of the atmosphere. Many false notions are still being bandied about such as that increasing carbon dioxide in the atmosphere will sooner or later make life impossible on Earth. Strange ideas about man's destruction of his environment AND EVEN HIMSELF is a tribute to vertical thinking and dealing in doom-mongering is an idiot course of action. Lateral thinking and a proper assessment with complete mental honesty in every phase of human activity is required to bring some impetus to those with vi-

sion and a certainty that the resources of the Earth are for the people of the Earth and should be brought into active use for their wellbeing. The mass of data requires funding and its ultimate benefit can be decided by the stroke of a pen in a political hand, which could deny the benefit of health to millions.

HIGH ALTITUDE EXPLORER SATELLITE

Explorer DE-1 has brought details of the aurora and the flow of solar energy and other matter from space. The interesting thing about the results provided by DE-1 and its companion DE-2 in a lower orbit which were equipped with instruments to provide data about the electric currents, fields and plasma between the magnetosphere, the ionosphere and the atmosphere is that it repeats history in the sense of 'it's been done before'. It is perhaps pertinent to point out that it is some fifty years since the basis of these phenomena were laid down and the archives contain records of papers on the subject of aurora.

In the latter part of the 1920's before the popularisation of the superheterodyne receiver multistage high frequency 'front ends' were used. Sometimes there were up to four stages. The coupling between stages was by HF transformers which looked like balls of string. Some of us searched in vain for the solution to what appeared to be instability. It appeared spasmodically and took the form of whistles sometimes rising in cadence and in other cases falling. Eventually there appeared headlines in the press to the effect that electrons shuttled backwards and forwards between the auroral points because they were trapped in the Earth's magnetic field. It was announced with some gusto that by timing some of these they followed lines of magnetic force more than 800m from the earth. These whistlers became the happy hunting ground for many post-graduates. Some of these 'whistlers' were given names like 'nose, lips, profile etc.' based on the shape which the graphs took as a result of the changing frequency. It would be interesting to know how many readers remember those days.

Now all this has been brought up to date as a result of DE-1 and DE-2 activity. The orbits of the satellites are:

DE-1 an eccentric orbit apogee 15,000 mi. perigee 354mi.

DE-2 apogee 628mi. perigee 192mi.

The arrangement of these two spacecraft allows the bracketing of the region of the leaking of low energy plasma into the magnetic field cusp from space where it is transformed into the high energy stream which initiates the aurora. It is well known now that the aurora is formed at a level which varies from 3,000 to 12,000 miles several times in 24 hours. At these levels the electrons trapped in the magnetic field are reflected back along the field lines and may continue this oscillating activity until their energy falls below a certain level.

The imaging system of DE-1 consists of three spin-scan photometers which permit daytime viewing of the aurora. The images are built up from line scans of the earth at the rate of one line per rotation of the spin stabilised satellite. This system uses 'super-reflecting' mirrors to avoid the light scatter which pre-

vents the use of lenses for this work. Two cameras operate in the visual part of the spectrum and a third operates in the ultra-violet. This imaging system is being used for other tasks also which include ozone observations, a special search for marine bioluminescence from space and the observation from high polar altitudes of the Earth-glow which is now called the geo-corona.

As the DE-1 apogee moves towards the Earth's equatorial region it is hoped that the cameras will be able to observe the red-glow bands that circle the Earth to the north and south of the equator. The drifting of the apogee will later enable the south polar regions to be observed. DE-2 carries instrumentation for the observation of particle and wave field environments. The instruments are capable of providing details of electron velocity every 2km.

A report by S. D. Shawhan on the radio waves generated in the auroral regions revealed that the more powerful emissions are associated with auroral storms. The frequencies are of the order 100-200kHz though sometimes as high as 800kHz (this was the range of whistlers). They are directed away from Earth and have powers of the order of billions of watts and can be picked up more than 15,000 miles from the auroral zones. This is of the same order as the radiations from Jupiter. They are characterised by rising and falling tones, each burst lasting about a second and changing in frequency by 1kHz. Detailed measurements of these waves have been made by DE-1. Its plasma instrument which monitors frequencies from a few Hertz to 400MHz detects the most intense waves when the spacecraft crosses magnetic field lines that pass through the aurora. Waves were detected by both satellites in the audio range, that is below 20kHz. This suggests that these waves must be guided away from the power source by the Earth's magnetic field.

High winds and high temperatures have also been recorded by DE-2. Data reveals that there are winds in the auroral zone which are of the order of hundreds of miles per hour and at times over 1,000 miles an hour. Temperatures have reached the order of 1,500 to 2,000K.

It is not possible to resist commenting that the Earth is far from approachable by alien spacecraft.


UNMANNED LAUNCH VEHICLE

The Boeing Aerospace Company has been selected to conduct a one year study for the National Aeronautics and Space Administration of an unmanned launch vehicle.

The vehicle which is designated SRB-X is being considered as a means of augmenting the space shuttle when payload and space is not immediately available in the shuttle orbiter. It will be capable of boosting a 65,000lb payload into low earth orbit or 12,000lb into a geosynchronous orbit. The SRB-X would be built from tried components with minimum modifications to boosters and launch facilities.

There are also three other studies—a liquid rocket booster and a side mounted shuttle derived cargo vehicle, studied by Martin Marietta; and another shuttle derived cargo vehicle—in line version, under study by Boeing.

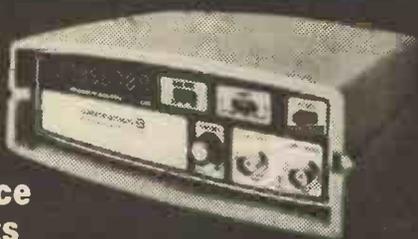An entire range of low-cost high-performance instruments



sabtronics

'Making Performance Affordable'

- | | | | |
|--------|--------------------------------------------------------|--------|-----------------------------------------|
| *2010A | 3½-Digit L.E.D. Bench DMM | 5020A | 1Hz-200KHz Function Generator |
| *2015A | 3½-Digit L.C.D. Bench DMM | *8110A | 100MHz 8-Digit Frequency Meter |
| 2020 | 3½-Digit L.E.D. Bench DMM with Microcomputer Interface | *8610A | 600MHz 8-Digit Frequency Meter |
| 2033 | 3½-Digit L.C.D. Hand DMM | *8610B | 600MHz 9-Digit Frequency Meter |
| *2035A | 3½-Digit L.C.D. Hand DMM | 8000B | 1GHz 9-Digit Frequency Meter |
| *2037A | 3½-Digit L.C.D. Hand DMM with Temp. | 8700 | 10MHz Universal Frequency Counter/Timer |
| LP-1 | 10MHz Logic Probe | PSC-65 | 600MHz Prescaler |
| | | 9005 | 5MHz Single Trace Oscilloscope |

Test our low priced test equipment. It measures up to the best. Compare our specs and our prices - no-one can beat our price/performance ratio.

Full colour illustrated brochure and price list from: **BLACK STAR LTD.**, 9a Crown Street, St. Ives, Cambs. PE17 4EB
Tel: (0480) 62440. Telex 32339



WHY AN ILP MOSFET POWER AMP?


Because ILP MOSFET power amps give you ultra-fi performance without costing big money. Performance you thought you couldn't afford at a price you know you can.

All ILP modules are compatible with each other - you'll find many more in other ILP ads in this magazine. Choose ILP MOSFET power amps when you need the fastest possible slew rate, low distortion at high frequencies, better thermal stability. MOSFET power amps work with complex loads without difficulty and without crossover distortion. Connection is simple - via 5 pins. With other ILP modules you can create almost any audio system, whatever your age or experience.



ILP MOSFET power amps are now available with integral heatsink (no extra heatsink required), or ready for mounting on to your own heatsink or chassis. Full dissipation detail on data sheet, available on request. Each carries a 5 year no quibble guarantee and comes with full connection data.

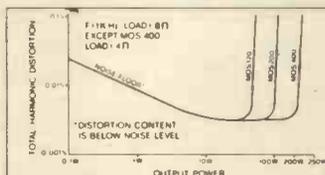Send your order FREEPOST today on the coupon at the foot of this ad.



Load impedance, all models, 4 ohm - infinity
Input impedance, all models 100k ohm
Input sensitivity, all models, 500 mV
Frequency response, all models 15Hz-50kHz-3db

MOSFET Ultra-Fi, with heatsinks

Model No.	Output power Watts rms	DISTORTION T.H.D. Typ at 1kHz	I.M.D. 50Hz/7kHz 4:1	Supply voltage Typ/Max	Size mm	Wt gms	Price inc VAT	Price ex VAT
MOS 120	60w/4-8Ω	<0.005%	<0.006%	+45±50	120 x 78 x 40	420	£29.76	£25.88
MOS 200	120w/4-8Ω	<0.005%	<0.006%	+55±60	120 x 78 x 80	850	£38.48	£33.46
MOS 400	240w/4Ω	<0.005%	<0.006%	+55±60	120 x 78 x 100	1025	£52.20	£45.39

MOSFET Ultra-Fi without heatsinks

Model No.	Output power Watts rms	DISTORTION T.H.D. Typ at 1kHz	I.M.D. 50Hz/7kHz 4:1	Supply voltage Typ/Max	Size mm	Wt gms	Price inc VAT	Price ex VAT
MOS 120P	60w/4-8Ω	<0.005%	<0.006%	+45±50	120 x 26 x 40	215	£26.82	£23.32
MOS 200P	120w/4-8Ω	<0.005%	<0.006%	+55±60	120 x 26 x 80	420	£32.81	£28.53
MOS 400P	240w/4Ω	<0.005%	<0.006%	+55±60	120 x 26 x 100	525	£44.75	£38.91

Protection:

Able to cope with complex loads, without the need for very special protection circuitry (fuses will suffice).

Ultra-fi specifications:

Slew rate 20V/μs. Rise time 3μs. S/N ratio 100db. Frequency response (-3dB) 15Hz-100kHz. Input sensitivity 500mVrms. Input impedance 100k. Damping factor (8Ω/100Hz) >400.

How to order Freepost:

Use this coupon, or a separate sheet of paper, to order these products, or any products from other ILP Electronics advertisements. No stamp is needed if you address to Freepost. Cheques and postal orders must be crossed and payable to ILP Electronics Ltd. cash must be registered. C.O.D. - add £1 to total order value. Access and Barclaycard welcome. All UK orders sent post free within 7 days of receipt of order.

ILP Electronics Ltd, Freepost 2, Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent.

Please send me the following ILP modules

PE 3/3

Total purchase price

Enclose Cheque Postal Orders Int. Money Order


Please debit my Access/Barclaycard No. _____

Name _____

Address _____

Signature _____

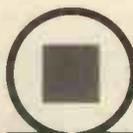Post to: ILP Electronics Ltd, Freepost 2, Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent, England
Telephone (0227) 54778 Technical (0227) 64723. Telex 965780



ILP ELECTRONICS LTD

STAY AHEAD. STAY WITH US

HOW WOULD YOU LIKE YOUR ZX81 TO LOOK LIKE THIS?



IT COULD WITH THE CROFTON ZX81 ADAPTAKIT.

ONLY £35.00 plus VAT - total £40.25 plus £2.65 P&P. AND IT ALSO HAS A VIDEO OUTPUT TO DRIVE A STANDARD MONITOR.

SEND FOR DETAILS.

CROFTON ELECTRONICS LIMITED

35 Grosvenor Road, Twickenham, Middlesex TW1 4AD. Tel: 01.891 1923/1513 Telex: 295093.


THE SENSATION OF THE JAPANESE MUSIC FAIR

Designed by a genius, Controlled by a computer, Programmed by a laser. Played by amateurs professionally and by professionals superbly.

THE NEW CASIOTONE 701

"... what is going to become THE instrument of 1982... probably the best instructive keyboard I have come across. But it is also a top line musical instrument capable of satisfying even the most proficient musician... I suggest you place your orders now." (*Keyboard & Music Player*)

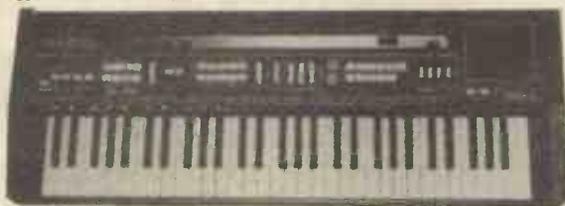"... opens up home music making for all the family... one of the most advanced music teaching aids so far developed... this instrument is going to be one of the biggest sellers of 1982." (*Electronics & Music Maker*)



Complete Programmable Polyphonic Keyboard (RRP £555) ONLY £495


- ★ Input an entire piece of music, specially scored in bar code and read by a light pen attached to the instrument.
- ★ Alternatively, program your own melodies, chords and tempo, from the keyboard, into the extensive memory, (up to 5 minutes playing or more) with full editing facilities.
- ★ 3-WAY PLAYBACK.
 1. Automatic playback of the entire piece; melody, chord, bass and rhythm with arpeggio. Follow the melody as it plays via lamps above each individual key.
 2. Manual melody playing, guided by the keyboard lamps, with automatic bass and rhythm accompaniment.
 3. ONE KEY PLAY facility, allows the melody line to be played, simply by stroking one key. Non-players can become Instant Musicians!
- ★ The 5 octave, 8-note polyphonic keyboard can be split into 2 & 3 octaves and a different voice can be selected for the accompaniment.
- ★ 20 "breath-takingly clear and bright" pre-set instruments and voices.
- ★ 3-way chord section:- Fingered, Memory and Casiochord auto accompaniment.
- ★ 16 rhythm accompaniments with "fill in" variation and two percussion effect buttons. Start/Stop, Synchro, Tempo and Balance controls.
- ★ Variable Vibrato and Sustain. Output jack. Foot pedal input jacks. Music book. AC only. Optional extras: Foot pedals, Hard Case.

FREE

CREDIT. 0% interest, † deposit, 12 monthly repayments. (Not MT-31, MT-40, or VL-1), or reduced rates for longer period.
INTEREST (0%) on ACCESS, B'CARD or VISA for first 6 months, for any keyboard purchase over £90.

NEW PORTABLE KEYBOARDS


CASIOTONE MT-40

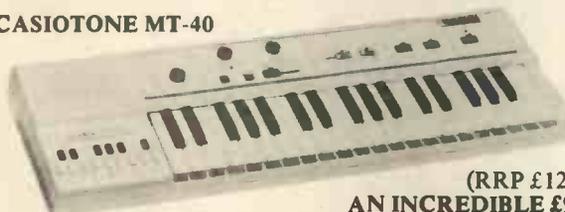

(RRP £125)
AN INCREDIBLE £99

- ★ 8-note polyphonic playing of this 37 key, 3 octave keyboard.
 - ★ 15 key bass keyboard with automatic synchronised bass function.
 - ★ 22 lively and realistic built-in instrument sounds and voices.
 - ★ 6 built-in auto rhythms, with dual "Fill-in" rhythmic interludes.
 - ★ Sustain, Vibrato and Pitch controls. Line out and Headphone jacks.
 - ★ Integral amplifier and speaker. Battery powered, or optional AC adaptor.
- Dims: 61.6x584x178mm (2-7/16x23x7"). Weight: 2.2kg (4.9lb).

CASIOTONE MT-31

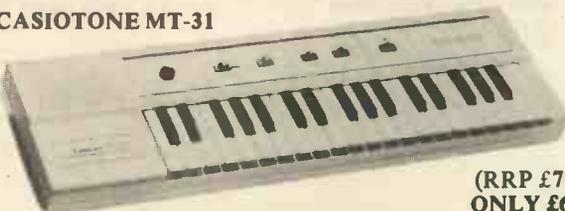

(RRP £79)
ONLY £69

"... basically a revision of the MT-30 (one of my all time favourite electronic keyboards)." *Electronics & Music Maker*.
Similar to the MT-40 but without the rhythm box, bass and auto functions.
Dimensions: As MT-40. Weight: 2.0kg (4.4lb) including batteries.

OTHER CASIOTONES

CT-101 £195. CT-202 £275. CT-403 £275. VL-TONE £35.95. Lists on request.

DELIVERY NORMALLY BY RETURN OF POST.

WE WILL BEAT ANY LOWER ADVERTISED PRICE BY 5%

providing the advertiser has stocks.

We regret that free offers are excluded when price beating.

World's Fastest Programmable?

FX-602P



- ★ LCD alpha/numeric (dot matrix) scrolling display.
- ★ Variable input from 32 program steps with 88 memories, to 512 steps with 22 memories.
- ★ Memory and program retention when switched off.
- ★ Up to 10 pairs unconditional jumps (GOTO).
- ★ Conditional jumps and count jumps. Indirect addressing. Manual jump.
- ★ Up to 9 subroutines, up to 9 levels.
- ★ 50 scientific functions, all usable in programs.
- ★ PAM (Algebraic) with 33 brackets at 11 levels.
- ★ Program and data storage on cassette tape using optional FA-2 remote control adaptor, £19.95.
- ★ Compatible with the FX-501P and FX-502P.
- ★ 9.6x71x141.2mm. 100g.

ONLY £74.95 (RRP £84.95)

Plus FREE MiCROL Professional Programming pack* (RRP £9.95)

FX-3600P

38 program steps, 7 memories. INTEGRALS & REGRESSION. **£22.95**


World's Most Powerful BASIC Pocket Computer?

CASIO FX-702P


(RRP £134.95)

ONLY £119.95

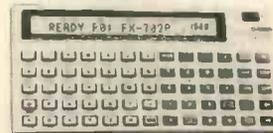Plus FREE MiCROL Professional Programming Pack (RRP £9.95)



Alpha/numeric dot matrix scrolling LCD. Variable input from 1680 steps, 26 memories, to 80 steps, 226 memories, all retained when switched off. Up to 10 programs. Subroutines; 10 levels. FOR:NEXT looping; 8 levels. Debugging and Editing. 55 built-in functions, including Regression and Correlation, all usable in programs. Program/Data storage on cassette via optional FA-2 adaptor (£19.95). Auto Power Off. 17x165x82mm. 176g.

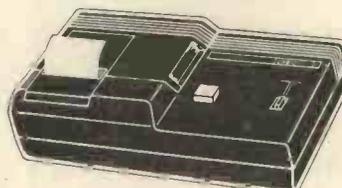

NEW CASIO FP-10 MINI PRINTER

(RRP £49.95)

AN INCREDIBLE £44.95

Plus FREE pack worth £5

Compatible with the FX-501P, FX-502P, FX-601P, FX-602P and FX-702P

Manual and program results printout. Memory and program listing. Electric discharge printer gives a remarkably legible 5x7 dot matrix printout of 20 characters per line. Stores up to 30 characters with printout over 1 1/2 lines, with overload symbol. Fast 2 lines per second print speed. Aluminium paper rolls are approx 2,500 lines (30 feet) long and cost £2.50 per pack of 5. FP-10 connects directly to the calculator or via FA-2 remote control cassette interface. Four AA batteries will print approx 6,000-9,600 lines. Rechargeable pack, NP-4M prints approx 13,000 lines, (£6.90). AC adaptor, AD-4150, recharges NP-4M in situ, (£5). Dims: 43.5Hx157.5Wx82.5D. (1 1/2 x 6 1/4 x 3 1/4"). Weight: 372g (13.1oz), incl. batteries.

MiCROL PROCOS Professional Computing Solutions on cassette. Save up to 90% of programming time with this electronic equivalent of pen and paper. "Visicalc-type" system. Answer "what if" questions & analyse trends. £24.95

Discounts on software when you purchase your hardware from us.

World's most versatile watch

CASIO AX-210

10 alternative displays; over 60 functions. LCD ANALOG display of time, plus: DIGITAL display of: Time (12 or 24 hour); Calendar; Full month calendar (this month and next month); Dual time (12 or 24 hour); Alarm time; Countdown alarm timer with memory function; Professional 1/100 second stopwatch with laps, etc. Hourly time signal. Alarm - electronic buzzer or 3 selectable melodies. Rapid forward/backward setting. 9.4x35.4x36mm.

(RRP £34.95) **ONLY £29.95**



CATALOGUE ON REQUEST
14p stamp appreciated

Price includes VAT and P&P. Send cheques, PO, or phone your ACCESS, VISA or B'CARD number to:

TEMPUS

LEADING CASIO SPECIALISTS
Dept. PE,
38 Burreleigh Street, Cambridge CB1 1DG
Telephone: 0223 312866

MUSIC KITS

ALL WITH PRINTED CIRCUIT BOARDS!

128-NOTE SEQUENCER

A digital, kbd controlled unit for most synths.
Kit incl kbd = SET-76 £120.45

16-NOTE SEQUENCER

Analogous, panel controlled unit for most synthesizers = SET-86 £64.63

3-CHANNEL STEREO MIXER

With left, right & master level controls & headphone monitor = SET-107 £21.50

3-MICROPHONE STEREO MIXER

Improves stereo reality = SET-108 £12.99

6-CHANNEL MIXER

High spec mixer with variable impedances = SET-90 From £96.67

AUDIO EFFECTS UNIT

Variable siren gen = SET-105 £15.12

AUTOWAH UNIT

Automatic Wah & Swell sounds from each guitar note played = SET-58 £14.01

CHOROSYNTH

30-Note chorus synth with wide variety of voices. Kit incl kbd = SET-100 £125.04

COMPRESSOR

With level & decay-rate controls, line & mic inputs with mixer = SET-120 £25.05

DISCOSTROBE

4-Chan 200W unit for sequential, random or full strobe use = SET-57 £39.78

DRUM SYNTHESIZER

Extremely versatile synthesizer for conventional & extraordinary drum sounds. = SET-119 From £50.11

DYNAMIC NOISE LIMITER

Helps clean up noisy recordings. = SET-97 £16.96

ENVELOPE SHAPER

ADSR unit with own VCA = SET-50 £14.96

KIMBER-ALLEN KEYBOARDS

Details in lists = From £32.43

P. E. MINISONIC SYNTH*

Excellent 3-Oct multi-module portable synth. Kit incl kbd = SET From £181.56

PHASER

6-Stage automatic unit with variable control = SET-88 £21.08

PHASING & VIBRATO

Manual & auto control producing superb full sounds = SET-70 £36.25

PULSE GENERATOR

Pulse width 100NS-2secs, freq 0.1 HZ-100KHZ = SET-115 £24.84

RHYTHM GENERATORS

Several in list = From £61.71

RING MODULATOR

Usable with most synths = SET-87 £13.62

SIGNAL TRACER & GENERATOR

Aids circuit testing. With frequency & level controls = SET-109 £17.50

SMOOTH FUZZ

As the name implies! = SET-91 £11.68

SPEECH PROCESSOR

Improves intelligibility of C.B. or P.A. speech signals = SET-110 £12.18

SPLIT-PHASE TREMOLO

Modulation, depth, rate & level under full control = SET-102 £29.98

SWITCHED TREBLE BOOSTER

4 Switchable preset tone changes = SET-89 £21.51

SYNTHESIZER INTERFACE

Enables guitars, mics etc to be synthesizer processed = SET-81 £9.49

LOTS OF NEW ILP ENCAPSULATED PRE-AMPS— COMPATIBLE WITH ALL ILP MODULES

Suddenly, instead of two ILP encapsulated pre-amps, there are eight! — everything from the simple mono pre-amp (HY6), through mixing mono pre-amps (HY12 and HY69), to a dual stereo pre-amp (HY71). Plus a new guitar pre-amp (HY73).

Each gives the very best reproduction from your equipment that your money can buy, and all are protected against short circuit and wrong polarity.

All ILP modules are compatible with each other — combine them to create almost any audio system. Every item carries a 5 year no quibble guarantee and includes full connection data.

So send your order today — the Freepost coupon needs no stamp.

ILP Electronics Ltd., Freepost 2, Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent. PRE-AMPS



Model No.	Module	What it does	Current required	Price inc. VAT	Price ex. VAT
HY 6	Mono pre-amp	Provides inputs for mic/mag. cartridge/tuner/tape/auxiliary, with volume/bass/treble controls.	10 mA	£7.41	£6.44
HY 9	Stereo pre-amp	Two channels, mag. cartridge, mic + volume control.	10 mA	£7.71	£6.70
HY 12	Mono pre-amp	Mixes two signals into one, with bass/mid-range/treble controls.	10 mA	£7.71	£6.70
HY 66	Stereo pre-amp	Two channels, with inputs for mic/mag. cartridge/tape/tuner/auxiliary, with volume/bass/treble/balance.	20 mA	£14.02	£12.19
HY 69	Mono pre-amp	Two input channels, mag. cartridge mic, with mixing and volume/treble/bass controls.	20 mA	£12.02	£10.45
HY 71	Dual stereo pre-amp	Provides four channels for mag. cartridge/mic with volume control.	20 mA	£12.36	£10.75
HY 73	Guitar pre-amp	Provides for two guitars (bass + lead) and mic with separate volume/bass/treble and mixing.	20 mA	£14.09	£12.25
HY 75	Stereo pre-amp	Two channels, each mixing two signals into one with bass/mid-range/treble controls.	20 mA	£12.36	£10.75



For easy mounting we recommend, B 6 mounting board for modules HY6-HY13 £0.90 inc. VAT, (0.78 ex. VAT) B 66 mounting board for modules HY66-HY77 £1.12 inc. VAT (0.99 ex. VAT.). All modules are encapsulated and include clip on edge connectors. All operate from +15V minimum to +30V maximum, needing dropper resistors for higher voltages. Modules HY6 to HY13 measure 45 x 20 x 40mm. HY66 to HY77 measure 90 x 20 x 40mm.

How to order Freepost:

Use this coupon, or a separate sheet of paper, to order these products, or any products from other ILP Electronics advertisements. No stamp is needed if you address to Freepost. Cheques and postal orders must be crossed and payable to ILP Electronics Ltd; cash must be registered.

C.O.D. — add £1 to total order value. Access and Barclaycard welcome. All UK orders sent post free within 7 days of receipt of order.

Please send me the following ILP modules

PE 4/3

Total purchase price

Enclose Cheque Postal Orders Int. Money Order

Please debit my Access/Barclaycard No.

Name

Address

Signature

Post to: ILP Electronics Ltd, Freepost 2, Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent, England. Telephone (0227) 54778 Technical (0227) 64723 Telex 965780



10% OFF 10% OFF U.K. C.W.O. ORDERS OVER £20 FROM THIS AD UNTIL END OF MONTH ON COVER. (5% OFF FOR CREDIT CARDS). THIS COUPON MUST ACCOMPANY ORDER. CODE PE23.

EXPOSURE TIMER

Range up to 10 mins in 0.5sec steps, with audio alarm = SET-93 £39.22

FORMAT SYNTHESIZER*

Advanced 3-oct synth with multiple modules. Kit incl kbd = SET-66 From £342.71

FUNNY TALKER

Fascinating sounds when used with speech & music = SET-99 £16.55

GUITAR EFFECTS

8-mode filter & envelope shaper for most instruments = SET-42 £16.92

GUITAR FREQUENCY DOUBLER

Orig & doubled signals can be mixed for greater depth = SET-98 £11.76

GUITAR MULTIPROCESSOR

Extremely versatile sound processor. Details in list.

GUITAR OVERDRIVE

Sophisticated fuzz with filter & shape controls = SET-56 £21.17

GUITAR PRACTISE AMPLIFIER

3-Watt practise or test-monitor amp. = SET-106 £22.16

GUITAR SUSTAIN

Retains natural attack whilst extending note duration = SET-75 £11.77

HEADPHONE AMPLIFIER

For most pick-ups, decks, tuners & headphones. RIAA specs = SET-104 £21.15

METRONOME

Variable for 40-240 beats per minute = SET-118 £10.58

EXPORTS WELCOME!

Sterling payment with order please. Postage rates in our lists. Europe send 50p for lists, other countries send £1.

TRANSIENT GENERATOR

Facilitates mandolin, banjo sounds etc. From a synthesizer = SET-63 £16.86

TREMOLO UNIT

For most instruments. Incl speed, depth & by-pass controls = SET-116 £13.47

TUNING FORK

Eases tuning of acoustic & electronic instruments = SET-46 £37.04

VOICE OPERATED FADER

Automatically reduces music volume during disco talk-over = SET-30 £9.85

VOICE SCRAMBLER

for coding or decoding speech signals for greater security. See list for details = SET-117 £21.81

WAVEFORM CONVERTER

Allows 5 different waveforms from synthesizer VCO = SET-67 £21.98

WAVEFORM GENERATOR

3 Waveforms, range 1HZ to 100KHZ, up to 10V P-P = SET-112 £23.13

WIND & RAIN EFFECTS

As the name says! = SET-28 £11.39

KIT CONTENTS

Sets include PCBs, U.K. P&P, 15% VAT, Res. Caps, S.c.s, Pts, Knobs, SW's, Skts, Wire, Solder, Photocopy of orig text, & a case unless marked *. Most are battery operated, but PSU units are also available. Most parts can be bought separately. Fuller details & more great kits in our catalogue. Send S.A.E. for free copy. Prices correct at press, E. & O.E., subject to stock. Despatch usually 24hrs on all ex-stock items.

Access, Barclay & Am-Express Credits Welcome.

PHONOSONICS

Dept. PE23, 22 High Street, Sidcup, Kent, DA14 6EH.

Telephone: 01-302 6184

THE PE RANGER

27FM CB PORTABLE

CB
27/81

BRITISH MADE
FOR U.K. MARKET
(Project described in
Practical Electronics, Sept
issue onwards)

THE RANGER CB rig has been designed to fit the new legal Home Office specification, and starts off as a hand held unit complete with aerial, mic., and rechargeable batteries.

The unit plugs into the mains, 12V car outlet, or runs on built-in re-chargeable batteries (built-in charger). EXCELLENT range in town to keep in touch with family and friends.

☆ FEB. SPECIAL OFFER ☆

Kit including all six channels including V.A.T.

£49.95
(P&P £2.85)

£97/matched pair
(INC. VAT + £5.90 P.P.)

This offer price includes rechargeable batteries, mic., aerial, mains lead and 6 channels.

Extra aerials £3.95 each + 80p P.P. + VAT
(Postage free with kit)

Tuneable Whip aerial magnetic or permanent
car amount (state which)

Permanent £13.95 - P.P. £1.00 + V.A.T.

Magnetic £15.95 - P.P. £2.00 + V.A.T.

SPEC.

R.F. Power Output $\frac{1}{2}$ Watt approx.
AF (internal speaker) $\frac{1}{2}$ Watt
Modulation: FM: freq. 27.6MHz-28MHz
(CB Band) (excellent speech quality)
No. of channels (max): 6
Fully protected against bad aerial
connection.

BASE STATION KIT ★ NOW AVAILABLE ★

£19.50
plus £2 p&p (inc. VAT)
**12V (NOMINAL) MAINS
ADAPTOR KIT £5.50**
plus £1.50 p&p

Despatch within 14 to 21 days

(SAE FOR FURTHER DETAILS)

PHONE YOUR ACCESS/BARCLAYCARD ORDER FOR FAST SERVICE



Ready Built Units £64.95
Available Now. Ring for Details

Autumn Products Ltd.
Park Drive, Baldock, SG7 6EW. Telephone, Baldock (0462) 894848

	Quant.	Unit Price
Universal Counter Timer Digital 10MHz-5MHz Rascal 9903	3	£400
Dual trace Oscilloscope 100MHz Tektronix 465	1	£1517
Continuity Tester Megger Evershed 40022 Type BM6 0-200-5M-200M ohms	3	£50
Range Switch for Megger Tester Series 2. Evershed	1	£15
Megger Test Set Avo MJ4	1	£127
Communicating Instrument LT Power Board Weyfringe Type 191	5	£142
Power Module 35W Tektronix TM501 for Sig Generator SG504	1	£102
Attenuator 3dB DC 18GHz Hewlett Packard HP8491B/003	1	£45
Step Attenuator Coaxial (Man) 0-12, 1dB steps, DC 1GHz Hewlett Packard HP355C	1	£142
Step Attenuator Coaxial (Man) 0-120, 10dB steps, DC 1GHz Hewlett Packard HP355D	1	£142
Power sensor 3W, 50 ohms, 10MHz-18GHz Hewlett Packard HP8481H	1	£341
Frequency Meter 0.96-4.2GHz coaxial type 'N' Hewlett Packard 536A	1	£488
Oscilloscope 200MHz Hewlett Packard 1710B	1	£1400
Integrated circuit Texas TL702C	89	£21
Capacitor fxd. Mica silvered 560 P00-G $\pm 2.0\%$ 350V DC insul. with wires. London Elec. MS611/R/1NG/350	4000	£0.40
Braided Copper Wire Tin $\frac{1}{4}$ in dia.	588 m.	£3
Braided Copper Wire flat 0.50in wide x 0.04in thick	271 m.	£0.22

PLESSEY RADAR LIMITED

Cowes, Isle of Wight PO31 8PF
Tele: (0983) 294141 Extn. 153

Packing & Carriage Extra. Plus VAT 15%.

MIGHTY NINETY PACKS

SUPER VALUE PACKS ALL AT 90p each. BUY SIX PACKS AND GET A SEVENTH - FREE

Please add 15p per pack postage. Please allow 7 days delivery.

MN2. 200 $\frac{1}{4}$ & $\frac{1}{2}$ -watt Resistors.	MN20. 1 240-110 to 12-volt. 100ma Transformer.	MN46. 15 asstd Zener diodes.
MN3. 100 1 & 2-watt Resistors.	MN21. 1 240-110 to 24-volt 100ma Transformer.	MN48. 200 Items 4BA asstd length screws, nuts & washers.
MN4. 50 Wirewound Resistors.	MN22. 8 2" Led's with clips, 4 red, 2 yellow, 2 green.	MN49. 200 Items 6BA asstd length screws nuts & washers.
MN5. 100 metal oxide Resistors. 1%, 2% and 5%.	MN23. 300 asstd screws, nuts, washers, self-tappers etc.	MN50. 3 pieces of veroboard useful sizes, min total 35 sq inch.
MN6. 12 asstd potentiometers.	MN24. 100 asstd small springs.	MN51. 10 x 0-2" red LED.
MN7. 25 asstd skeleton pre-set Resistors.	MN27. 200 Items, grommets, spacers, cable markers, plastic screws, sleeving, tie wraps etc.	MN52. 10 x 0-125" red LED.
MN8. 50 asstd Electrolytic Capacitors.	MN29. 75mts equipment wire, asstd colours and sizes.	MN53. 20 x 0-1 mfd 25v ceramic disc caps.
MN9. 100 asstd Ceramic Capacitors Pflc. disc. tub and monolithic etc.	MN35. 10 asstd switches, toggle, slide, micro etc.	MN54. 20 x 0-01 mfd 25v ceramic disc caps.
MN10. 100 mixed capacitors. Polyester. Polystyrene. Metallised, Radial and Axial types.	MN36. 10 sub-min SP. C/O slide switch.	MN55. 10 watt audio amp board with circuit.
MN11. 20 asstd Silver Mica Capacitors.	MN37. 10 asstd audio connectors, Din phono etc.	MN56. 10 14 pin low profile IC skt DIL.
MN12. 8 Tantalum Bead Capacitors (useful values).	MN40. 50 Polystyrene capacitors.	MN57. 10 16 pin low profile IC skt DIL.
MN13. 20 asstd Transistors. BC, 2N Series + Power etc.	MN41. 12 BC549C (plastic BC109C) transistors.	MN58. 2 x CA723 Voltage Regulator.
MN14. 40 IN4148 Diodes.	MN42. 10 BC107 Transistors.	MN59. 1 x LM380 2 watt audio amp IC + 555 timer IC.
MN16. 20 min. wire-ended Neons.	MN43. 10 BC108 Transistors.	MN60. 10 asstd TTL IC's.
MN17. 2 12-volt Relays. Ex nearly new equip.	MN44. 10 Screwfix S.P.C.O. min. slide switches.	MN63. 50 mixed polyester caps C280, Semlens etc.
MN18. 3 Encapsulated Reed Relays 9-12v coil, d-pole and l-pole.	MN45. 35 asstd diodes Zener, rect, signal, switching.	MN64. 5 Press to make min switches.
		MN65. 4 min push to break switch.
		MN71. IZN414 RADIO IC.

CHORDGATE LIMITED

75 FARINGDON ROAD, SWINDON, WILTS. Tel. (0793) 33877.

Retail shop at above address.

Schools, Colleges, official orders welcome.

JOIN UP WITH LITESOLD

Litesold's new 'L' Series soldering iron - now at a bargain price.

Outstanding performance. Lightweight. Easy to maintain.

Elements are enclosed in Stainless Steel shafts.

Insulated with mica and ceramic. Non-seize

interchangeable bits, choose from

'copper' or 'long life'. A very special

tool at a very special 'direct' price.

Just £5.22 for iron fitted with 3.2mm

copper bit. Just £2.27 for 3 spare

copper bits (1.6: 2.4: 4.7).

A mere £4 for

professional spring

stand! Or buy the

lot for £10.34

and save 10%.



£5.22

LITESOLD
LIGHT SOLDERING
DEVELOPMENTS LTD

All prices Inc. VAT P & P.

Please allow 14 Days Delivery

Write today. Send Cheque/P.O. to Litesold, 97-99 Gloucester Road, Croydon CR0 2DN

or phone 01-689 0574 for Barclaycard/Access sales.

MIXERS, FADERS, VU METER DRIVERS AND MORE - ALL NEW FROM ILP!

Just some of the 28 new amazingly compact modules from ILP Electronics, Britain's leader in electronics modules - you'll find more new products in the amps and pre-amps advertisements.

All ILP modules are compatible with each other - you can combine them to create almost any audio system. Together they form the most exciting and versatile modular assembly system for constructors of all ages and experience.

Every item from ILP carries a 5 year no quibble guarantee and includes full connection data. So send your order on the Freepost coupon below today!

Model No	Module	What it does	Current required	Price inc VAT	Price ex VAT
HY 7	Mono mixer	Mixes eight signals into one.	10 mA	£5 92	£5 15
HY 8	Stereo mixer	Two channels, each mixing five signals into one.	10 mA	£7 19	£6 25
HY 11	Mono mixer	Mixes five signals into one - with base/treble controls	10 mA	£8 11	£7 50
HY 68	Stereo mixer	Two channels, each mixing ten signals into one	20 mA	£9 14	£7 95
HY 74	Stereo mixer	Two channels, each mixing five signals into one - with treble and bass controls.	20 mA	£13 17	£11 45

AND OTHER EXCITING NEW MODULES

Model No	Module	What it does	Current required	Price inc VAT	Price ex VAT
HY 13	Mono VU meter	Programmable gain/LED overload driver	10 mA	£6 84	£5 95
HY 67*	Stereo headphone driver	Will drive stereo headphones in the 4 ohm-2K ohm range.	80 mA	£14 20	£12 35
HY 72	Voice operated stereo fader	Provides depth/delay effects.	20 mA	£15 07	£13 10
HY 73	Guitar pre-amp	Handles two guitars (bass and lead) and mic with separate volume/bass/treble and mix.	20 mA	£14 09	£12 25
HY 76	Stereo switch matrix	Provides two channels, each switching one of four signals into one.	20 mA	To be announced	
HY 77	Stereo VU meter driver	Programmable gain/LED overload driver.	20 mA	£10 64	£9 25

For easy mounting we recommend:

B 6 mounting board for modules HY6 -HY13 £0.90 inc. VAT (0.78 ex. VAT.)

B 66 mounting board for modules HY66-HY77 £1.12 inc. VAT. (0.99 ex. VAT.)

*All modules are encapsulated and include clip-on edge connectors. All operate from ±15V minimum to ±30V maximum, needing dropper resistors for higher voltages. HY67 can be used only with the PSU 30 power supply unit. Modules HY6 to HY13 measure 45x20x40mm. HY66 to HY77 measure 90x20x40mm.

FP 480 BRIDGING UNIT FOR DOUBLING POWER

Designed specially by ILP for use with any two power amplifiers of the same type to double the power output obtained and will function with any ILP power supply. In totally sealed case, size 45x50x20mm with edge connector. It thus becomes possible to obtain 480 watts rms (single channel) into 8Ω. Contributory distortion less than 0.005%. Price: £5.51 inc. VAT. (Ex. VAT £4.79.)

How to order Freepost:

Use this coupon, or a separate sheet of paper, to order these products, or any products from other ILP Electronics advertisements. No stamp is needed if you address to Freepost. Cheques and postal orders must be crossed and payable to ILP Electronics Ltd; cash must be registered. C.O.D. - add £1 to total order value. Access and Barclaycard welcome. All UK orders sent post free within 7 days of receipt of order.

ILP Electronics Ltd, Freepost 2, Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent.

Please send me the following ILP modules PE 5/3

Total purchase price

I enclose Cheque Postal Orders Int. Money Order

Please debit my Access/Barclaycard No.

Name

Address

Signature

Post to: ILP Electronics Ltd, Freepost 2, Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent, England
Telephone (0227) 547776 Technical (0227) 64723 Telex 965780



ACORN ATOM

Kit £120. Built £150. Power supply £8.87.

UK101 AND SUPERBOARD


UK101 with 1K and free power supply and modulator built £149. The below accessories suit both the UK101 and superboard:- Extra ram £2.70 per K. 16K memory expansion complete kit £50, built £58. 32K memory expansion kit £74, built £82. Case £27. Cassette recorder £19. Cesmon £22.50. Wemton £19.95. Word processor program £10. Centronics interface kit £10. 610 expansion board £179. Cased minifloppy drive with DOS £275. The below suit only superboard:- Colour adaptor board built £45. Assembler/Editor tape £25. Guard band kit £10. Series 1 only 30 lines x 50 characters display expansion kit £14. UK101 display expansion kit £14.

VIDEO GENIE £299

EG3014 Expansion box with 16K/32K ram £199/£213. Disk drive £220. Colourboard £36. Parallel printer interface £36. Monitors:- EG100 white £69, OVM9PGR green £99.



PRINTERS

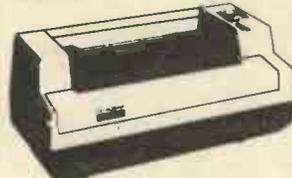

Buy any of the below and get a free interface kit and word processor program for UK101 or Superboard:- Epson MX70 £259. Epson MX80T £359. Epson MX80F/T1 £359. Epson MX80F/T2 £449. OKI Microline 80 £295. OKI Microline 82A £399. Centronics 737 £355. Seikosha GP80A £199.

SINCLAIR PRODUCTS*

Z801 built + mains adaptor £69.95 (post £2.95 extra). SC110 Oscilloscope £139. PFM200 £49. PDM35 £32.95. DM450 £116. Microvision TV £69.

BATTERY ELIMINATORS*

3-way type 6/7.5/8V 300ma £3.50. 100ma radio types with press studs 9V £4.95. 9+9V £8.25. Car converter 12V input, output 3/4.5/6/7.5/9V 800ma £3.04.

BATTERY ELIMINATOR KITS*

100ma radio types with press-studs 9V £179. 9+9V £2.50. Stabilized 8-way types 3/4.5/6/7.5/9/12/15/18V 100ma £3.12. 1 Amp £8.50. Stabilized power kits 2-18V 100ma £3.12. 1.30V 1A £8.50. 1-30V 2A £15.30. TTL and computer supplies 5V stabilized 1.5A £9. 3A £14. 6A £23. 12V car converters 6/7.5/9V 1A £1.62.

TV GAMES*

AY-3-8600*kit £12.98. AY-3-8550*kit £9.26.

BI-PAK AUDIO MODULES*

AL30A £4.35. PA12 £9.31. PS12 £1.75. T538 £2.90. S450 £27.90. AL60 £5.62. PA100 £19.24. SPMB0 £5.26. B1MT80 £6.36. Stereo 30 £21.00. AL20 £8.56.

VIC 20 COMPUTER

VIC 20 £185. Cassette recorder £39.09. Kit to allow the use of a normal cassette recorder £6. 3K ram £26.04. 8K ram £39.09. 16K ram £65.17. Vic printer £199.



COMPONENTS*

1N4148 1.5p. 1N4002 3.7p. NE555 8 dll 22p. 741 8 dll 16p. 2114 low current 300ns £1.35. BC112. BC134. BC212. BC214. BC547. BC549 8p. Resistors 5% 1/4 watt E12 10R to 10M 1p, 0.8p for 50+ of one value. Polystyrene capacitors E12 63V 10 to 1000pf 4p; 1n2 to 10n 8p. Ceramic capacitors 50V; E6 22pf to 47n 2.5p. Electrolytic capacitors 50V; 5. 1.2mf 6p; 25V 5. 10mf 6p; 16V 22. 33mf 6p; 47mf 4p; 100mf 7p; 330. 470mf 9p. Zeners 400mw E24 2v7 to 33v 7p. Preset pots subminiature 0.1W horiz or vert 100 to 2M2 8p. IC sockets 8 dll 8.7p, 14 dll 10.1p, 16 dll 12p.

Postage £3.50 on computers. £4.50 on printers and 45p on other orders. Lists 27p post free. Please add VAT to all prices except those sections marked with a * which already include it. Overseas and official credit orders welcome.

SWANLEY ELECTRONICS,

Dept. PE, 32 Goldsial Rd., Swanley, Kent BR8 8EZ. Tel. Swanley (0322) 64851.

TRANSFORMERS



MARCO TRADING

British made transformers at very attractive prices.

Primary	Secondary	Current	1+	10+	100+
240v:	4.5-0-4.5v	400ma	50p	45p	35p
240v:	6-0-6v	100ma	58p	52p	43p
240v:	6-0-6v	500ma	65p	60p	48p
240v:	9-0-9v	200ma	75p	70p	58p

Manufacturers note: We can supply FROM STOCK, 1000+ quantities of the above transformers and adaptors below.

These very high quality British made two pin European adaptors are ideal for driving Radios, cassette recorders, TV games, calculators etc. The adaptors fit the UK shaver socket.

REF.	D.C. Voltage	Current	1+	10+	100+
E08	4.5V	200ma	50p	45p	32p
EM3	6V	200ma	£1.00	80p	55p
E09	6V	400ma	£1.50	£1.25	85p
ET4	9V	150ma	£1.50	£1.25	85p

Please note that there is no extra P/P charge on the above transformers and adaptors. Export please add S&A/air mail at cost. Callers welcome Mon-Fri 9-5.

This advert is only a fraction of our range, send 25p for our latest catalogue. Please add 35p P/P to all orders. (Free over £5.00). Add 15% VAT to total. Send orders to:

Dept. PE1, MARCO TRADING,

The Old School, Edstaston, WEM, Shropshire SY4 5RJ.

Special Offer Test Equipment Catalogue available upon request. Send S.A.E. or Telephones. All order despatched by return of mail. Tel: (094872) 464

ELECTROVALUE

CATALOGUE '82

ESSENTIAL READING FOR:
THE ELECTRONICS
ENTHUSIAST
THE COMPUTING FREAK
THE EQUIPMENT
MANUFACTURER



PACKED WITH INFORMATION
ON MORE THAN 6,000 STOCK
ITEMS: ACTIVE AND PASSIVE
COMPONENTS, BOXES, CASES,
COMPUTER HOUSINGS,
KNOBS, POTS, SWITCHES,
RELAYS,
EVERYTHING FROM R's AND
C's TO COMPUTING SYSTEMS

FOR YOUR COPY OF CATA-
LOGUE 82 please send 70p
(includes 70p voucher to be re-
claimed against orders valued
£10.00 or over).

ALL ITEMS BRAND NEW
AND GUARANTEED
SPEEDY MAIL ORDER
SERVICE

No P/P charges on U.K. C.W.O.
orders over £5.75 Inc. V.A.T.
(add 40p handling charge if
under).

PLEASE ADD 15% V.A.T. TO
TOTAL VALUE OF ALL
ORDERS

FOR EV BARGAINS LIST and
useful News Sheet send S.A.E.

4000BE SERIES	74LS00 SERIES	74LS193	90p
4000BE	74LS00	74LS195	87p
4001BE	74LS02	74LS196	90p
4002BE	74LS04	74LS197	85p
4006BE	74LS05	74LS253	90p
4007BE	74LS08	74LS257	75p
4008BE	74LS10	74LS259	160p
4009BE	74LS11	74LS266	31p
4010BE	74LS14	74LS273	130p
4011BE	74LS20	74LS279	76p
4012BE	74LS30	74LS299	295p
4013BE	74LS32	74LS367	58p
4014BE	74LS37	74LS368	55p
4015BE	74LS38	74LS373	150p
4016BE	74LS42	74LS374	150p
4017BE	74LS47	74LS378	84p
4018BE	74LS51	74LS383	85p
4019BE	74LS73		
4020BE	74LS74		
4021BE	74LS75		
4022BE	74LS76		
4023BE	74LS85		
4024BE	74LS86		
4025BE	74LS90		
4026BE	74LS92		
4027BE	74LS93		
4028BE	74LS107		
4029BE	74LS112		
4030BE	74LS123		
4041BE	74LS125		
4042BE	74LS126		
4043BE	74LS132		
4044BE	74LS136		
4045BE	74LS137		
4049BE	74LS138		
4050BE	74LS139		
4060BE	74LS145		
4069BE	74LS148		
4070BE	74LS151		
4071BE	74LS153		
4072BE	74LS155		
4081BE	74LS156		
4082BE	74LS157		
4093BE	74LS161		
4510BE	74LS163		
4511BE	74LS164		
4514BE	74LS165		
4516BE	74LS166		
4518BE	74LS173		
4520BE	74LS174		
4543BE	74LS175		
4563BE	74LS191		

Computing IC's	2114	£1.50
4118	£7.90	
4116 200nS	£1.30	
4116 250nS	£1.30	
4116 300nS	£0.90	
Z80A CPU	£6.00	
Z80A P10	£6.00	
Z80A CTC	£6.00	
6402 UART	£4.50	
Special Offer!		
25 x 4116 (300nS)	£16.00 only	

Regulators	7805/12/15/24	65p
7805/12/15/24	55p	
7805/12/15/24	32p	
7805/12/15/24	67p	
723 (14 pin)	36p	
78H05	£5.55	
78HGKC	£7.20	
78HGKC	£12.15	
LM317K	£12.78	

Low Profile IC Holders - BICC	pins 1 off,	25 off
8	8p	£1.60
14	12p	£2.40
16	14p	£2.30
18	16p	£3.20
20	18p	£3.20
25	22p	£3.60
22	21p	£4.20
24	21p	£4.20

SHOP HOURS 9.5-3.0 p.m. (1 p.m. Sat.) Please mention this journal when writing or ordering by post.

ELECTROVALUE LTD

Dept. PE. 2, 28 St Jude's Rd., Englefield Green, Egham, Surrey TW20 0HB. Phone Egham 33603 (STD 0874 - London 87) Telex 264475, Northern Branch (personal shoppers only) 680 Burnage Lane, Burnage, Manchester M19A 1MA. Phone (061) 4324945.

NICADS AND CHARGERS

by Sanyo Cadnica
N450AA (AA size) 99p
N1800C (C size) £2.27
N3500D (D size) £3.78
6N75P (PP3 size) £4.10
CHARGERS:
NC75G (PP3) £4.95
NC450S (4 x AA) £4.95
NC1230 (A.A., C.D) £7.60

COMPONENT PACKS

Buy in quantity for best value
CPI: 100 ceramic capacitors from 1p8 to 1µF
Selection determined by relative popularity
Pack Price £4.20

RESISTOR DECADE PACKS

1W, 5% tolerance, each pack 100 items from one decade. Selection determined by popularity of each value.
RD1: 1R0-8R2; RD2: 10R-82R; RD3: 100R-820R
RD4: 1K-82K; RD5: 10K-82K; RD6: 100K-820K; RD7: 1M-10M, each decade pack £1.50

SEMICONDUCTOR PACKS

LD30A-2.9mm red LED's 25 for £1.58
LS1RD-5mm red LED's 25 for £1.58
1N4148 Diodes 25 for 88p
1N4001-1A 100V Diodes 25 for £1.30
1N5402-3A 200V Diodes 25 for £2.80
BC107/BC108/BC109 25 for £2.98
BC182/182L/183/183L/184/184L 25 for £1.88
BC212/212L/214/214L 25 for £1.88

TRANSISTOR SELECTION

2N3053 23p
2N3054 75p
2N3055 75p
BC327 11p
BC327 11p
BD130 45p
BD131 77p
BD139 30p
BD140 32p
BD679 53p
BD680 55p
BF500 28p
MJE2955 £1.20
MJE3055 87p
TIP31A 44p
TIP32A 44p
TIP41A 45p
TIP42A 45p
TIP2955 53p
TIP3055 55p

ANALOGUE IC SELECTION

741C8 18p
748C8 35p
7555 88p
CA3080E 16p
CA3130E 99p
CA3140E 40p
LM380N 99p
LM381 11p
LM3914N £2.68
NE555V 23p
NE556A 79p
TDA2030 £1.45
TL071CP 45p
TL072CP 75p
TL074CN £1.20
UA1170 £1.52
XR2206 £4.60
ZN414 £1.22
ZN425E £3.90

SPECIAL NASCOM OFFER

Quantity purchase enables us to offer superb NASCOM Microcomputer system at a much reduced price. The system comprises:
NASCOM 2 kit
RAM B kit with 16k Dynamic RAM and sockets for a further 32k.
3A PSU kit.
NASSYS 3—the new NASCOM Monitor.
Graphics ROM—block graphics.
Programmers Aid—BASIC toolkit.
Mini-Motherboard.

Special price £340.00 + VAT

STOP PRESS

SHARP MZ80K WITH HI-RES GRAPHICS PACKAGE
ONLY £445.00 + VAT.

NEW SABTRONICS

Frequency Meter
Model 800B: 9-digit 1GHz Frequency Meter.
Professional specification: £160.00

OTHER SABTRONICS EQUIPMENT

2015A Bench DMM (LCD) £83.00
2035A Hand-Held DMM (LCD) £82.00
8110A 8 digit 100MHz DFM £67.00
8610A 8 digit 600MHz DFM £82.00
5020A 1-200KHz Function Generator, Sine, Square, Triangle and separate TTL Square £79.00
90wave outputs

PARNDON ELECTRONICS LTD.

Dept. No. 21 44 Paddock Mead, Harlow, Essex, CM18 7RR. Tel: 0279 32700

RESISTORS: 1/4 Watt Carbon Film E24 range ± 5% tolerance. High quality resistors made under strictly controlled conditions by automatic machines. Banded and colour coded.
£1.00 per hundred mixed. (Min 10 per value)
£8.50 per thousand mixed. (Min 50 per value)
Special stock pack: 60 values. 10 off each £5.50


DIODES: 1N4148 3p each. Min order quantity - 15 items.
£1.60 per hundred

DIL SWITCHES: Gold plated contact in fully sealed base - solve those programming problems.
4 Way 86p each. 6 Way £1.00 each. 8 Way £1.20 each.

DIL SOCKETS: High quality, low profile sockets.
8 pin - 10p. 14 pin - 11p. 16 pin - 12p. 18 pin - 19p. 20 pin - 21p.
22 pin - 23p. 24 pin - 25p. 28 pin - 27p. 40 pin - 42p.

ALL PRICES INCLUDE V.A.T. & POST & PACKING - NO EXTRAS
MIN. ORDER - U.K. £1.00. OVERSEAS £5 CASH WITH ORDER PLEASE
EX-STOCK ITEMS BY RETURN OF POST

STORAGE CABINETS

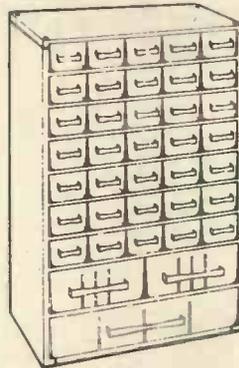

Type 1838

Metal Cabinets 12" wide x 5 3/4" deep, finished blue with transparent plastic drawers.

Type	H. (ins)	No. of Drawers	Price
1118	11	15 2 1	£10.75
1633	16	30 2 1	£13.95
1838	18	35 2 1	£15.95
2236	22	30 4 2	£18.55
2260	22	60 - -	£18.55

Access/Barclaycard welcome
Prices include VAT and Post. Cheque/P.O. to:
Millhill Supplies (Tools),
35 Preston Crowmarsh, Benson,
Oxon OX9 6SL.
Tel: Wallingford (0491) 38653
Goods by return of post.

EPROM PROGRAMMER

- 2716 ● HEX KEY PAD
- 2732 ● POWERFUL EDITOR
- 2532 ● TV (MONITOR) DISPLAY
- SERIAL/PARALLEL I/O
- CASSETTE BACK-UP
- ROMULATOR

SOFTY STANDS ALONE

£169 + VAT, EX-STOCK, BY RETURN

DATAMAN DESIGNS, LOMBARD HOUSE,
DORCHESTER, DORSET, DT1 1RX. (0305) 68066

THIS MONTH'S SNIP!

ACE MAILTRONIX LTD
Dept. PE. 3A Commercial St. Batley, W. Yorks. WF17 5HJ

NEW 1982 CATALOGUE
for your carefree component purchasing
COMPONENTS - Over 1,000 types in stock.
SERVICE - Same day despatch.
QUALITY - All guaranteed products.

"Let us quote for your hard to get components for PE projects"

I enclose 30p: please send catalogue

name _____
address _____

INTERESTED IN ELECTRONICS?

TRY A ZEDPACK! COMPONENTS AT A PRICE EVERYONE CAN AFFORD

- Z1 300 mixed 1 and 1/2 watt resistors £1-95
 - Z2 150 mixed 1 and 2 watt resistors £1-50
 - Z3 300 mixed capacitors, most types £3-95
 - Z4 100 mixed electrolytics £2-20
 - Z5 100 mixed polystyrene caps £2-20
 - Z6 300 mixed printed circuit components £1-95
 - Z7 300 mixed printed circuit resistors £1-45
 - Z9 100 mixed miniature ceramic and plate caps £1-20
 - Z10 25 assorted pots. £1-50
 - Z11 25 assorted presets, skeleton etc. £1
 - Z12 20 assorted vdr's and thermistors £1-20
 - Z13 11b mixed hardware. Nuts, bolts, self-tappers, sleeving, etc. £1-20
 - Z14 100 mixed, new and marked, full spec. translators. Pack Includes:— BC148, BF154, BF274, BC212L, BC238, BC184L, PBC108 and, or lots of similar types £4-95
 - Z15 100 mixed diodes Including:—zener, power, bridge, signal, germanium, silicon etc. All full spec. £4-95
 - Z16 20 1N4148 £1
 - Z17 20 1N4003/1002 £1
 - Z18 20 assorted zeners, 1 watt and 400mw £1-50
 - Z19 12 -125" TIL 209 RED. LED'S £1
 - Z20 10 Assorted switches, including push button, slide, multipole, miniature etc. Fantastic value, £1-20.
- UHF MODULATORS**
Video in UHF out. Calibrated to channel 36 (625 line UHF) housed in metal box 2 1/2" x 2" x 1 1/2" with 9' coaxial lead, TV plug and connection data. £2-50 ea. 3 for £6.
- 200µA** Miniature level/batt. meters, as fitted to many cassette recorders. 90p
- Deluxe FIBREGLASS** printed circuit etching kits.
Includes 150 sq ins. of copperclad F/G board, 1lb ferric chloride, (made for U.S. army to MIL SPEC), 1 dalo etch resist pen, abrasive cleaner, tweezers, etch resist dish and instructions. **OUR PRICE £5-95** 1lb of FeCl₂. £2-25.

To: "GEMINI ELECTRONIC COMPONENTS" DEPT PE "THE WAREHOUSE" SPEEDWELL ST. LONDON S.E.8.

Where shown, Send Cheque* or Postal Order. Plus 60p P&P. and 15% VAT. Please Quote ZED Code. SEND OFFICIAL ORDER ZED PACKS now available for Callers at 50 Deptford Broadway, London, S.E.8. Please allow 7 days for delivery. Send large S.A.E. for fuller list.

- 100 Miniature reed switches. £2-30
- 100 Subminiature Reed Switches. £4-20

SMALL MAGNETS

With hole in 6 for £1

P/B SWITCH BANKS

These cost a fortune! Were made for various music centres, includes independent and interdependent latching type, multi pole c/o etc. Can be modified. Can't be repeated. 3 Banks for £1. KNOBS for Switch Banks 10 for £1. Chrome or spun aluminium finish.

MINIATURE MAINS TRANSFORMERS

Top quality. Split bobbin construction will give 4-5V-0-4-5V at 250MA, 1 1/2" x 1 1/2" x 1 1/2", all sorts of uses. ONLY £1 3 for £2-50.

PP3 Battery Connectors 10 for 50p. Miniature Press to Make Switches, Red knob. 3 for 50p. Subminiature S.P.C.O. Slide Switches. 6 for 50p.

Miniature D.P.C.O. Slide Switches. 6 for 50p. Standard 2P. 3 Position Slide Switch. 4 for 50p.

TBA810P 7 Watt Amp. I.C. with circuits and data. only £1

MFC8010 1 Watt I.C. with data and circuits. 60p, 2 for £1

555 Timers. 30p ea. 4 for £1

6A 100V Bridge Rectifier. Small. 80p ea. 3 for £2

ZN3055H. RCA. 60p, 3 for £1.50

9 Section. Chrome on Brass Telescopic Aerial. Plugs into any 3.5mm socket. Approx 25" extended £1 each. 3 for £2-50.

Hi Power Infra Red Transmitter 5mm LED. TIL 38 60p ea. 3 for £1-50.

Crystal Clear 3mm LED'S very pretty Red, Green, Yellow. 10 of one colour £1. 10 of each £2-50.

ALTERNATOR RECTIFIERS

Make lovely 60 amp bridges. Ideal for High Power Battery Chargers. Type 4AF1. Set of 4 (2 neg. case + 2 pos. case) £2.

Special Purchase enables us to offer Mullard C280 Polyester Capacitors (Liquorice Allsorts) at the unbeatable price of £2 for 100 mixed. £15 for 1000. These consist of factory clearance lots i.e. spillages, floor sweepings, cosmetic rejects etc. Also, Mullard Miniature Electrolytics. 200 mixed £2.

ILP POWER SUPPLIES - MOST WITH ILP TOROIDAL TRANSFORMERS



Space-saving, efficient ILP power supplies are designed to give you flexibility in planning audio assemblies. Nine of the eleven models have toroidal transformers, manufactured on new cost-efficient high technology machines in our own factory. So we keep the quality up, and the price down.

ILP power supplies are compatible with all other ILP modules — combine them to produce almost any audio system. All carry the ILP 5 year no quibble guarantee and include full connection data. So send your order on the Freepost coupon below today!

POWER SUPPLY UNITS

Model No	For use with	Price inc. VAT	Price ex VAT
PSU 30	±15V combinations of HY6/66 series to a maximum of 100 mA or one HY67	£5.18	£4.50
	The following will also drive the HY6/66 series except HY67 which requires the PSU 30.		
PSU 36	1 or 2 HY 30.	£9.32	£8.10
PSU 50	1 or 2 HY 60.	£12.58	£10.94
PSU 60	1 x HY 120/HY 120P/HD 120/HD 120P.	£15.00	£13.04
PSU 65	1 x MOS 120/1 x MOS 120P	£15.32	£13.32
PSU 70	1 or 2 HY 120/HY 120P/HD 120/HD 120P	£18.31	£15.92
PSU 75	1 or 2 MOS 120/MOS 120P.	£18.63	£16.20
PSU 90	1 x HY 200/HY 200P/HD 200/HD 200P.	£18.63	£16.20
PSU 95	1 x MOS 200/MOS 200P.	£18.77	£16.32
PSU 180	2 x HY 200/HY 200P/HD 200/HD 200P or 1 x HY 400/1 x HY 400P/HD 400/HD 400P.	£24.54	£21.34
PSU 185	1 or 2 MOS 200/MOS 200P/1 x MOS 400 1 x MOS 400P.	£24.66	£21.46

All models incorporate ILP toroidal transformers except PSU 30 and PSU 36 which include our own laminated transformers.

How to order Freepost:

Use this coupon, or a separate sheet of paper, to order these modules, or any products from other ILP Electronics advertisements. No stamp is needed if you address to Freepost. Cheques and postal orders must be crossed and payable to ILP Electronics Ltd: cash must be registered. C.O.D. — add £1 to total order value. Access and Barclaycard welcome. All UK orders sent post free within 7 days of receipt of order. ILP Electronics Ltd, Freepost 2, Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent.

PE 6/3

Please send me the following ILP modules

Total purchase price _____

I enclose Cheque Postal Orders Int. Money Order

Please debit my Access/Barclaycard No. _____

Name _____

Address _____

Signature _____

Post to ILP Electronics Ltd, Freepost 2, Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent, England Telephone (0227) 54778 Technical (0227) 64723 Telex 965780



STAY AHEAD. STAY WITH US

DIY BURGLAR ALARMS WE'RE BACK!

Following major reorganisation we offer DIY security equipment and kits with fully illustrated, step-by-step, instructions.

- PLUS Better Prices! Better Delivery! Better Service!**
- Kits £32, £50, £75, £85 ● Control Panels £18, £23, £29, £37
 - Bell Boxes £6.25, £7.50 ● Pressure Pads £1.06, £1.45, £1.95
 - Sirens £7.50 ● Contacts 72p, 74p, 76p ● 4 Core Cable (100m) £8.00
 - Door Phones £49.42 ● Ultrasonics £34.50. ●

AND MUCH, MUCH MORE!

Send SAE or 'Phone for FREE Illustrated Catalogue.

AD ELECTRONICS, 217 Warbreck Moor, Aintree, Liverpool, L9 0HU. Tel. 051 523 8440 ● All prices include carriage ● VAT extra.

TRADE ENQUIRIES WELCOME

NICKEL CADMIUM BATTERIES

	AA (HP7) 0.5Ahr	SUB 'C' 1.2Ahr	'C' (HP11) 1.65Ahr	'C' (HP11) 2.0Ahr	'D' (HP2) 4.0Ahr	PP3 0.1Ahr
1-24	£0.85	£1.38	£1.69	£2.25	£2.37	£3.79
25-49	£0.75	£1.28	£1.58	£2.10	£2.77	
50-99	£0.65	£1.24	£1.52	£2.02	£2.67	
100 up	£0.59	£1.15	£1.41	£1.87	£2.47	

All cells are brand new full spec devices from reputable mfrs. All Nickel Cadmium cells (except PP3) are supplied complete with solder tags and are "VENTED" devices suitable for fast charge.

CHARGERS — single or dual O/P to charge PP3, AA or SUB 'C' cells in 12-14 hrs (chargers will charge 'C' and 'D' cells but with longer charging time). Units supplied complete in plug top case with flying leads. Number of cells (10 max) in series and type must be specified for each required O/P when ordering.

SINGLE O/P CHARGER £5.04
DUAL O/P CHARGER £5.72

TRANSFORMERS — as used in chargers. 2 x 12 volt 0.25 amp secondaries 240v primary, tag connections £1.57 each.

Data and charging circuits free with orders over £10 otherwise 30p post. P&P 10% if order less than £10, 5% if order over £10. Prices DO NOT INCLUDE VAT and this should be added to the total order. All advertised goods are ex-stock and normally despatched within 7 days.

Cheques, P.O.'s Mail Order to:—
SOLID STATE SECURITY,
Dept. (PE), Bradshaw Lane,
Parbold, Wigan, Lancs.
Telephone 02576-3018.



RECEIVERS AND COMPONENTS

300 SMALL COMPONENTS, Transistors, diodes £1.70. 7lbs assorted components £4.25. 10lbs £5.75. 20 wire ended neons £1. Forty 74 series ICs on panel £1.70. 500 capacitors £3.20. List 20p refundable. Post 60p, optional insurance 20p. JWB Radio, 2, Barnfield Crescent, Sale, Cheshire M33 1NL.

BRAND NEW COMPONENTS BY RETURN

Electrolytic Capacitors 16V, 25V, 50V.
0.47, 1.0, 2.2, 4.7 & 10 Mfds. — 5p.
22 & 47 — 6p. 100 — 7p. (50V — 8p). 220 — 8p.
(50V — 10p). 470 — 11p. (40V — 16p). 1000/15V — 15p.
1000/25V — 25p. 1000/40V — 35p.
Subminiature bead tantalum electrolytics.
0.1, 0.22, 0.47, 1.0 & 35V, 4.7 & 6.3V — 14p.
2.2/35V, 4.7/25V — 15p. 10/25V, 15/16V — 20p.
22/16V, 33/10V, 47/6V, 68/3V & 100/3V — 30p.
15/25V, 22/25V, 47/10V — 35p. 47/16V — 30p.
Subminiature Ceramic Caps. E12 Series 100V.
2% 10 pf. to 47 pf. — 3p. 56 pf. to 330 pf. — 4p.
10% 390 pf. to 4700 pf. — 4p.
Vertical Mounting Ceramic Plate Caps. 50V.
E12 22 pf. to 1000 pf. E6 1500 pf. to 47000 pf. — 2p.
Polystyrene E12 Series 63V. Horizontal Mntg.
10 pf. to 820 pf. — 3p. 1000 pf. to 10,000 pf. — 4p.
Miniature Polyester 250V Vert. Mtg. E6 Series.
.01 to .068 — 4p. .1 — 5p. 15, 22 — 6p. 33, 47 — 10p.
.88 — 12p. 1.0 — 15p. 1.5 — 22p. 2.2 — 24p.
Mylar (Polyester) Film 100V. Vertical Mounting.
.001, .0022, .0047 — 3p. .01, .022 — 4p. .04, .05, 0.1 — 5p.
Miniature Film Resistors Highstab. E12 Ser. 5%
0.125W mixed carbon/metal 100 to 1MΩ — 1p.
0.25W Carbon 1Ω to 10MΩ (10% over 1MΩ) — 1p.
(E24 Series av. in 1W C. Film 1Ω to 5M60Ω).
0.25W, 0.5W & 1.0W Metal Film 10Ω to 2M2Ω — 2p.
1N4148 — 2p. 1N4002 — 4p. 1N4006 — 6p. 1N4007 — 7p.
BC107/8/9, BC147/8/9, BC157/8/9, BF195 & 7 — 10p.
8 Pin Ics. 741 Op. amp. — 18p. 555 Timer — 24p.
Dil Holders 8 pin — 9p. 14 pin — 12p. 16 pin — 14p.
LED's. 3 & 5mm. Red — 10p. Green & Yellow — 14p.
Grommets for 3mm. — 13p. Grommets for 5mm. — 2p.
20mm. Q.B. Fuses -15, -25, .5, 1, 2, 3 & 5A — 3p.
20mm. Antl. Surge 100mA. to 5.0A — 5p.
20mm. Fuseholders P.C. or Chassis Mtd. — 5p.
Battery Snaps (pairs) PP3 — 5p. PP9 — 10p.
400mW Zener diodes E24 series 2V7 to 33V — 8p.

Prices VAT inclusive Post 15p. (Free over £5.00).

THE C. R. SUPPLY CO.

127, Chesterfield Rd., Sheffield S8 0RN.

TURN YOUR SURPLUS Capacitors, transistors, etc., into cash.
Contact COLES-HARDING CO., 103 South Brink,
Wisbech, Cambs. 0945-4188. Immediate settlement.

PE MINIATURE SCORPIO Capacitive Discharge Electronic Ignition Unit

Full kit of parts, including ready drilled pcb & metalwork, as specified in PE for only £14.85 including VAT & Postage. Wound transformer £2.00 extra. PCB only, £1.75 inclusive.

SAE for full price list.

Dept. PE,

Microstate Limited,
5 Northfield Close, Fernhill Heath,
Worcester WR3 7XB.

SMALL ADS

The prepaid rate for classified advertisements is 32 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £10.70 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Electronics and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Practical Electronics, Room 2612, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

T & J ELECTRONIC COMPONENTS — quality components, competitive prices. Illustrated catalogue 45p. 98 Burrow Road, Chigwell, Essex.

NOSTALGIA THE VINTAGE COLLECTING WIRELESS COMPANY 1920 to 1955

Receivers, valves, components, service data, historical research books, magazines, repairs and restorations. A complete service for the collector and enthusiast of vintage radio.

S.a.e. with enquiries and for monthly newsletter.

THE VINTAGE WIRELESS COMPANY, 64, Broad Street, Staple Hill, Bristol BS16 5NL. Tel. Bristol 565472.

B.R.B. PRINTED CIRCUITS for "P.E." Projects. Roller Tinned, drilled, and postage paid. "Space Evaders" — set £7.00. Trade enquiries — Customers own masters — etc. welcome. B.R.B., 109, Potter Street, Worksop, Notts. S80 2HL.

BULK OFFERS

All new full spec. devices. No rubbish. SAE list. Prices per 100. Minimum order £10. Post £1. No VAT.

4001B	£9	POLYESTER CAPS, 100V IIT:	
4007A	£9	470R, 2K2, 4K7, 10K, 22K, 47K,	
4011B	£9	100K. All £3/100.	
4017A	£20	0.1W presets, horiz. mntg:	
4035B	£40	470R, 2K2, 4K7, 10K, 22K, 47K,	
4503B	£22	33/10, 47/6, 68/3 £8.	
4511B	£35		
LN380N	£45	Tants: 0.1/35, 1.5/35, 2.2/16, all £4;	
74LS112	£8	33/10, 47/6, 68/3 £8.	
709 14 DIL	£6		
C106F (No Tab)	£6	PC ELECTRONICS, 2, Thornhill,	
TBA120C	£15	Romsay Road, Whiteparish,	
MC857	£16	Salisbury SP5 2SD.	

BOURNEMOUTH/BOSCOMBE. Electronic components specialists for 33 years. Foresters (National Radio Supplies), Late Holdenhurst Road. Now at 36, Ashley Road, Boscombe. Tel. 302204. Closed Weds.

BOOKS AND PUBLICATIONS

ANY SINGLE SERVICE SHEET £1/L.S.A.E. Thousands different repair/service manuals/sheets in stock. Repair data your named T.V. £6.50, (with circuits £8.50). S.A.E. Newsletter, price lists, quotations. AUS (PE), 76 Churches, Larkhall, Lanarkshire. (0698 883334).

NOTICE TO READERS

Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser to check both prices and availability of goods before ordering from non-current issues of the magazine.

SOFTWARE

EPROMS PROGRAMMED. 25/2716 £8.50, 25/2732 £16.00. Wilkinson, 3 Wedgwood Drive, Leeds LS8 1EF. Sae details, 667183.

7 x 81 TEMPERATURE SENSORS (plug-in compatible), including UK P & P £17.95. Leaflet, Cheshire Micro Design, 66 Close Lane, Alsager, Stoke-on-Trent.

FREE CATALOGUE. Everything for microcomputer users. Phone Croydon Computer Centre, 29A Brigstocker Road, Thornton Heath, Surrey. 01-689 1280.

UK101 SOFTWARE ON TAPE from the guy who wrote "Le Passe-Temps"

GALACTIC HITCHHIKER (8K). An adventure, all in machine code. A beauty! (£7.00)

SUPERTREK (8K). Sail boldly through the universe zap-ping moving Klingons in real time. Superb graphics. (£7.00)

STARTREK (8K). The old favourite, beautifully presented. (£6.00)

LUNAR LANDER. A real challenge. You won't get down in less than 3 hours. (£3.00)

HANGMAN. Excellent graphics. P.E. said so! (£3.00)

BASIC TUTOR (8x4K). The only way to learn — at the keyboard. (£12.00)

LE PASSE-TEMPS. You NEED this, if you haven't already got it. (£3.00)

MAD MONK (8K). It's ready at last! A machine code adventure with some truly remarkable graphics, this programme is in a class by itself. (£9.50)

These ORIGINAL PROGRAMS are compatible all 2K Monitors and are available for 16x48 and 32x48 displays (including enhanced Superboards).

HARDWARE

These kits are complete in every way — Fully socketted high quality PCB, all components, switches etc, plus preformed cable assembly for easy interconnection to J1, or our

MOTHERBOARD SYSTEM. Now you can add on all those extras easily. Provides eight, yes EIGHT, fully buffered J1 type sockets. (£19.50)

8K STATIC RAM BOARD. (£39.50)

HI-SPEED CASSETTE INTERFACE. At last, a system that works. COMPLETELY RELIABLE 4000 baud (8000 with reasonable cassette) plus software for named file handling. A delight to use. (£19.50). For software in EPROM, add £6.00

VIDEO ENHANCEMENT. Switch selectable 16x48 or 32x48 displays without butchering your computer. (£19.50)

Monitor EPROMS re-blown to suit for just £2.50

8K EPROM BOARD (£19.50). A 2K Extended Monitor is available in EPROM for £12.00 plus, coming soon.

TOOLKIT in EPROM and BASIC V.

MONITOR BOARD. Plug into Monitor socket to provide switch selection of up to 4 EPROMS. (£9.50)

AVAILABLE SHORTLY: EPROM Programmer, PIA/Sound Board. Analogue Board and something rather nice on the graphics side...

All inclusive prices — absolutely no hidden extras. Please write or phone for further details:

A. KNIGHT (Dept. PE),
28 Simonside Walk,
Ormsby,
Cleveland,
Tel. (0642) 321266.

When replying to Classified Advertisements please ensure:

- That you have clearly stated your requirements.
- That you have enclosed the right remittance.
- That your name and address is written in block capitals, and
- That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

COURSES

SOUND ENGINEERS

If you're following a career in Sound Engineering or interested in learning all aspects of recording studios you should attend one of our weekend studio courses.

Topics covered include:

- A. The basics of studio construction, wiring and materials used.
- B. Types of microphones uses, techniques, and limitations.
- C. Use of 2" 16 track machine, lining up, remotes etc.
- D. Use of 24 Channel Desk and all controls.
- E. Effect equipment, ADT, reverb, Echo, etc.
- F. Ancilliary equipment.
- G. Mixing and Editing.

There are a maximum number of 8 students on each course and every one is tutored to their own level of knowledge with regard to their needs and interest. The cost is £98 for the weekend including hotel accommodation overnight. Details please phone 01-580 4720 or 01-636 5308 during office hours.

EDUCATIONAL

CAREERS IN MARINE ELECTRONICS. Courses commencing September and January. Further details, The Nautical College, Fleetwood FY7 8JZ. Tel. 03917 79123.

TELEVISION COMPUTER RADIOCOMMUNICATIONS & RADAR SERVICING

2 1/3 YEAR full-time Modular Diploma course to include a high percentage of practical work.

- ELECTRONIC PRINCIPLES
- MONO TV & CCTV
- COLOUR TV & VCR
- MICROELECTRONICS & DIGITAL TECHNIQUES
- MICROPROCESSORS & COMPUTERS
- RADIOCOMMUNICATIONS & RADAR

Each of the above Modules are 13 weeks in duration. Individual Modules can be arranged for applicants with suitable electronics background.

Subject to approval, students will be awarded a TEC Diploma in Electronics & Communication Engineering on Completion of the full course.

Next session starts April 19th

Prospectus from:

LONDON ELECTRONICS COLLEGE

Dept: AA, 20 Penywern Road, London SW5 9SU. Tel: 01-373 8721.

FOR SALE

NEW BACK ISSUES OF 'PRACTICAL ELECTRONICS' available 90p each Post Free. Cheque or uncrossed P/O returned if not in stock - **BELL'S TELEVISION SERVICES**, 190 Kings Road, Harrogate, N. Yorks. Tel: (0423) 55885.

BK UK101 - £125. Transcendent 2000 synthesiser - £195.6 St. Lawrence Avenue, Ramsgate, Kent. (0843) 583581.

UK101 BK CASED. Super Space Invaders, Disassembler. £150 o.n.o. Tel. Wickford 5787.

UK101, 32 x 48, 24K, cased, CEGMON, WEMON joystick, software, £220. Telephone Sedgley 74804.

FRG-7. Mint condition, complete with C.L. 22 coupler £145. Guisborough (0287) 22213.

5mw LASER. Suit Disco etc., + some components, must be £120. Call Weybridge 51790 day.

SERVICE SHEETS

SERVICE SHEETS £1 each plus SAE. Individual T.V. repair data £6.50 (with circuits £8.50). Free electronics newsletter, pricelists unique publications. Auspe, 76 Churches, Larkhall. Lanarkshire ML9 1HE.

BELL'S TELEVISION SERVICES for Service Sheets on Radio, Tv, etc £1.25 plus S.A.E. Colour TV Service manuals on request. S.A.E. with enquiries to B.T.S. 190 Kings Road, Harrogate, N. Yorkshire, Tel: (0423) 55885.

PERSONAL

CHRISTIAN SINGLES. Friendship, contacts. 1982 holidays. Weekend houseparties. - C.F.F., Dept N46, Edenthorpe, Doncaster.

MISCELLANEOUS

PRINTED CIRCUIT BOARDS. Glass Fibre tinned and Drilled Prototypes to batch runs. Quick turn-round, competitive prices. Send s.a.e. for quotations: R. D. Electronics, 12 Whiteoaks Road, Oadby, Leicester. 0533 716273.

PARAPHYSICALS JOURNAL (Russian translations): Psychotronic Generators, Kirlianography, Gravity Lasers, Telekinesis. Details: SAE 4 x 9", Paralab, Downton, Wilts.

*** BIG EARS * STOP GO! LEFT! RIGHT!**

SPEECH INPUT FOR ANY COMPUTER



Hugely successful Speech Recognition System, complete with microphone, software and full instructions.

BUILT TESTED & GUARANTEED ONLY £49
PLEASE STATE COMPUTER: UK101, SUPERBOARD, NASCOM2, ZX80/81, PET, TRS80, MZ80K, APPLE II

ZX80 ZX81 MUSIC SYNTHESISER + 16 LINE CONTROL PORT



Play 3-part music, sound effects, drums etc. Full control of attack, decay and frequency. Input/Output lines provide control and monitor facility for Home Security, Robot Control, Model Railway, etc. etc. Works with or without 16K RAM

Add keyboard to make a five performance polyphonic synthesiser! Full instructions/software included.

AMAZING VALUE AT ONLY £19.50 (KIT) £25.00 (BUILT)

COLOUR MODULATOR	KIT £12
RGB In, PAL/UMF out	BUILT £18
UK101/NASCOM COLOUR GRAPHICS	KIT £45
Inc. Modulator. Still the best selling system!	BUILT £60

Please add VAT at 15% to all prices. Barclay/Access orders accepted by telephone.

WILLIAM STUART SYSTEMS Ltd
Dower House, Billerica Road, Harrogate, Brentwood, Essex CM13 3SD
Telephone: Brentwood (0277) 810244

SECURITY ALARMS KITS FROM £37. Full range of accessories. MFP Ltd., Harrison Road, Erdington, Birmingham B24 9AB. 021-373 0450.

RECHARGEABLE BATTERIES

Private & Trade Enquiries Welcome

FULL RANGE AVAILABLE. SAE FOR LISTS. £1.45 for Booklet. Nickel Cadmium Power plus Catalogue. Write or call: Sandwell Plant Ltd, 2 Union Drive, BOLDMERE, SUTTON COLDFIELD, WEST MIDLANDS. 021 354 9764. After hours 0977 84093.

NEW SEALED LEAD RANGE AVAILABLE

DIGITAL WATCH BATTERIES. Any type £1.20 each. Send S.A.E. or 15p with number or old battery to: DISCLEC Y, 511, Fulbridge Road, Werrington, Peterborough.

CLEARING LABORATORY: scopes, generators, P.S.U's, bridges, analysers, meters, recorders, etc. 0403-76236.

Cabinet and Flightcase Fittings

Fretcloths, Coverings, Handles, Castors etc., Jacks and Sockets, Cannons, Bulgins, Reverb Trays, Emilar Compression Drivers, P&N Stands, Celestion Speakers, ASS, Glass-fibre Horns.

Send 30p Postal Order for illustrated catalogues to:-

ADAM HALL (P. E. SUPPLIES)
Unit G, Carlton Court, Grainger Road, Southend-on-Sea, Essex SS2 5BZ.

ULTRASONIC TRANSDUCERS. miniature, 40KHZ, £2,85p/pair + 25p p&p. Dataplas Developments, 81, Cholmeley Road, Reading, Berks.

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Practical Electronics for.....

insertions. I enclose Cheque/P.O. for £.....

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Practical Electronics).

NAME.....

ADDRESS.....

Company registered in England. Registered No. 53626. Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS.

Send to: Classified Advertisement Manager
PRACTICAL ELECTRONICS
Classified Advertisements Dept., Room 2612
King's Reach Tower, Stamford Street,
London SE1 9LS. Telephone 01-261 5846
Rate:
32p per word, minimum 12 words. Box No. 60p extra.

MISCELLANEOUS - CONTD.

SECURITY SYSTEMS KITS ... All components and full instructions. Send large SAE for latest catalogue of advanced projects for car, caravan and home. Computech Systems, Ind. Est., N. Walsham NR28 0AN. Tel: (0692) 5600.

THE SCIENTIFIC WIRE COMPANY
PO Box 30, London E.4. 01-531 1568.

ENAMELLED COPPER WIRE

SWG	1lb	8oz	4oz	2oz
8 to 29	2.76	1.50	0.80	0.60
30 to 34	3.20	1.80	0.90	0.70
35 to 39	3.40	2.00	1.10	0.80
40 to 43	4.75	2.60	2.00	1.42
44 to 47	5.90	3.40	2.39	2.00
48 to 49	15.96	9.58	6.38	3.69

SILVER PLATED COPPER WIRE
14 to 30 6.50 3.75 2.20 1.40

TINNED COPPER WIRE
14 to 30 3.85 2.36 1.34 0.90

Prices incl P&P, VAT.
Orders under £2 please add 20p.
SAE for List of Copper/Resistance Wire. Dealer enquiries welcome.
Reg. Office, 22 Coningsby Gardens.

CENTURION BURGLAR ALARM EQUIPMENT. Send SAE for free list or a cheque/PO for £11.50 for our special offer of a full sized signwritten bell cover, to Centurion Dept PE, 265 Wakefield Road, Huddersfield, W. Yorkshire, Access & Barclaycard telephone orders on 0484-35527.

REVERBERATION

The Ryder solid-state unit, specially designed for organ use, gives smooth, natural sound. Demo cassette, on loan, deposit £1.50, refund £1.00. (Prices UK only).

HIYKON LTD. (P),
Woodside Croft, Ladybridge Lane,
Bolton BL1 5ED.

WRONG TIME?

MSF CLOCK IS ALWAYS CORRECT - never gains or loses, SELF SETTING at switch-on, 8 digits show Date, Hours, Minutes and Seconds, auto GMT/BST and leap year, also parallel BCD output for computer or alarm etc, second-in-month. STOPCLOCK, receives Rugby 60KHz atomic time signals, built-in antenna, 1000Km range, GET THE RIGHT TIME, £62.80.
V.L.F. 7 EXPLORE 10-150KHz, Receiver £16.50. Each fun-to-build kit includes all parts, printed circuit, case, instructions, postage etc, money back assurance so GET yours NOW.

CAMBRIDGE KITS

45 (FC) Old School Lane, Milton, Cambridge.

MICRO TRANSMITTER, VHF/FM, matchbox size, variable 70-150 MHz, complete kit, £4.50. Microtronic, 9, Tennant, Simonside, South Shields.

MAKE YOUR OWN PRINTED CIRCUITS

Etch Resist Transfers - Starter pack (5 sheets, lines, pads, I.C. pads) £2.00. Large range of single sheets in stock at 43p per sheet.
Master Positive Transparencies from P.C. layouts in magazines by simple photographic process. 2 sheets negative paper, 2 sheets positive film (A4) £2.10. Photo-resist spray (200 ml) £3.25 (p+p 55p). Drafting Film (A4) 25p. Precision Grids (A4) 85p.
20p stamp for lists and information. P&P 35p per order except where indicated.

P.K.G. ELECTRONICS
OAK LOOGE, TANSLEY, DERBYSHIRE.

ENAMELLED COPPER WIRE. 10 swg to 45 swg. S.A.E. for quotation by return, cheapest prices. 102 Parrswood Road, Manchester 20.


P.E. AND PROTOTYPE PCBs PLUS P.E. PHOTOCOPIES

LOW COST SERVICE FOR HOME ENTHUSIASTS
Send S.A.E. for lists

PRINTRONIX, 8 Back Road,
Sidcup, Kent, DA14 6HA.

DIGITAL WATCH BATTERIES one type equivalent to RW47, Renata 2, Ucar 392, 75p each. Two £1.30 payable S. Bath, Send, Carlton, The Square, Sittihians, Truro.

ANNOUNCING - THE SENSATIONAL VIBROSCOPE

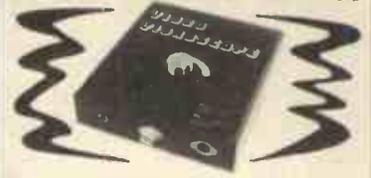

Once again, Stuart Systems have astounded the world with a totally new concept. The Video Vibroscope produces a fantastic multi-colored display on any TV. The picture is controlled by music, using microphone or other direct input, and forms an exciting, pulsating and rhythmic experience which cannot fail to turn them on! A must for parties, discos, etc.

NOW AVAILABLE FOR ONLY £49.95
9v POWER UNIT £4.95. PLEASE ADD VAT AT 15%. (POST & PACKING INCLUDED)

Barclay/Access orders accepted on telephone
WILLIAM STUART SYSTEMS Ltd
Dover House, Billericay Road, Herongate, Brentwood, Essex CM13 3SD. Telephone: Brentwood (0277) 810244

BURGLAR ALARM EQUIPMENT. Ring Bradford (0274) 308920 for our catalogue or call at our large showrooms opposite Odsal Stadium.

PRACTICAL ELECTRONICS P.C.B.'s

Drilled. 1-3mm Glass fibre Fry's Roller Tinned

NOV 81 UK 101 Monitor change EP640 £1.87

DEC 81 Space Invaders EA303 EA305 £6.91 a pair

For full list and current pcb's send SAE. Pcb's also produced to customers own masters. Trade enquiries welcomed. Write for quote. CWO Please. Postage - add 35p postage and packing to complete order. Europe 70p

PROTO DESIGN

14 Downham Road, Ransden Heath, Billericay, Essex CM11 1PU. Telephone 0268-710722

TRANSFORMERS + VAT 15%

30 VOLT RANGE (Split Sec)
Sec Voltages available 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30V or 12V-0-12V or 15V-0-15V.

Ref.	Amps	Price	P&P
112	30V 15V	2.90	1.00
79	1 2	3.93	1.00
3	2 4	6.35	1.20
20	3 6	7.39	1.44
21	4 8	8.79	1.60
51	5 10	10.98	1.60
117	6 12	12.29	1.72
88	8 16	16.45	1.96
89	10 20	18.98	1.84
90	12 24	21.09	O.A.
91	15 30	24.18	O.A.
92	20 40	32.40	O.A.

50 VOLT RANGE (Split Sec) Pri 120/240V
Sec Voltages available 5, 7, 8, 10, 13, 15, 17, 20, 33, 40 or 20V-0-20V or 25V-0-25V

Ref.	Amps	Price	P&P
102	5V 25V	3.75	1.20
103	1 2	4.57	1.20
104	2 4	7.88	1.44
105	3 6	9.42	1.60
106	4 8	12.82	1.72
107	6 12	16.37	1.84
118	8 16	22.29	2.20
119	10 20	27.48	O.A.
109	12 24	32.88	O.A.

MAINS ISOLATORS (SCREENED)
Pri 0-120; 0-100-120V (120, 220, 240V) Sec 0-CT-120V twice.

Ref.	VA	Price	P & P
*07	20	4.84	1.20
149	60	7.37	1.20
150	100	8.38	1.44
151	120	12.28	1.72
152	250	14.61	2.04
154	500	22.52	2.20
155	750	33.03	O.A.
156	1000	40.92	O.A.
157	1500	56.52	O.A.
158	2000	67.99	O.A.
159	3000	95.33	O.A.

*Pri 0-240V Sec 115 or 240V only. State sec. volts required.

CASED AUTO TRANSFORMERS
240V cable in 115V USA flat pin outlets

VA	Price	P & P	Ref
20	6.55	0.95	56W
75	8.50	1.20	64W
150	11.00	1.44	4W
250	13.39	1.44	69W
500	20.13	2.04	67W
1000	30.67	2.20	84W
2000	54.97	O.A.	95W

UK Postages. Overseas extra.

Voltages stated are on full load
Continuous Ratings

60 VOLT RANGE (Split Sec)
Pri 120/240V. Voltages available 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 or 24V-0-24V or 30V-0-30V.

Ref.	Amps	Price	P&P
124	60V 30V	4.27	1.20
126	1 2	6.50	1.20
127	2 4	8.36	1.60
125	3 6	12.10	1.72
123	4 8	13.77	1.96
40	5 10	17.42	1.84
120	6 12	19.87	2.04
121	8 16	27.92	O.A.
122	10 20	32.51	O.A.
189	12 24	37.47	O.A.

12 OR 24V OR 12-0-12V
Pri 220-240 volts

Ref.	12V	24V	Price	P&P
111	0 5	0 25	2.42	0.95
213	1 0	0 5	2.90	1.00
71	2 1	2	3.86	1.00
18	4 2	1	4.46	1.20
85	0 5	2 5	6.18	1.20
70	6 3	4	6.99	1.20
108	8 4	4	8.16	1.44
72	10 5	5	8.93	1.60
116	12 6	6	9.89	1.60
17	16 8	8	11.79	1.72
115	20 10	10	15.87	1.84
187	30 15	15	19.72	2.04
226	60 30	30	40.41	O.A.

SCREENED MINIATURES

Ref.	mA	Volts	£	P&P
238	200	3-0-3	2.83	0.50
212	1A	0-5-0-6	3.14	1.00
13	100	9-0-9	2.35	0.50
235	330	330-0-9-0-9	2.19	0.60
207	500	500-0-8-9-0-8-9	3.05	0.95
208	1A	0-8-9-0-8-9	3.88	1.20
236	200	200-0-15-0-15	2.19	0.60
214	300	300-0-20-0-20	3.08	1.00
221	700	700-12-0-12-0-12	3.75	1.00
206	1A	0-15-20 (x2)	5.09	1.20
203	500	500-0-15-27 (x2)	4.39	1.20
204	1A	0-15-27 (x2)	6.84	1.20
239	50	12-0-12	2.88	0.50
234	500	6-0-6	2.19	0.44

Send 20p stamps for Catalogue. Prices correct 21/4/81. Goods By Return

AUTO TRANSFORMERS
Voltages available: 105, 115, 190, 200, 210, 220, 230, 240, for step up and step down.

Ref.	VA (Watts)	£	P&P
113*	15	2.73	1.00
64	30	4.41	1.20
4	150	5.89	2.20
53	350	10.00	1.44
67	500	12.09	1.84
84	1000	20.64	2.20
93	1500	25.61	O.A.
95	2000	38.31	O.A.
73	3000	65.13	O.A.
80	4000	84.55	O.A.
57	5000	98.45	O.A.

*0.115, 220, 240.

Constant Voltage Transformers (1%)
Clean mains to computers/peripherals

250 VA.....	£103.00
500 VA.....	£136.40
1000 VA.....	£162.20

Also I.C. "sensing types" for low mains voltage fluctuations.

15V CT Range (7.5V-0-7.5V)

Ref.	500 mA	2.30	P & P
172	1A	3.26	1.00
173	2A	3.95	1.00
174	3A	4.13	1.20
175	4A*	6.30	1.20

96/48/36V RANGE
Pri 0 120/240V
Sec 2 windings 0-36-48V to give 36-0-36V or 48-0-48V or 72V or 96V.

Amps	Ref.	Price	P&P
72v/96v	36v/48v		
2	4	431	8.12 1.44
1	2	432	13.35 1.22
3	6	433	16.17 1.96
4	8	434	20.85 2.04
5	10	435	29.30 2.20
6	12	436	38.69 O.A.
8	16	437	40.03 O.A.

Split Bobbin Type. Sec Voltages available 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30V, or 12-0-12V or 15-0-15V, 1 amp (09) £2.06 + 98p. PP 2 amp (10) £4.11. £1.10pp + VAT.

BBC ACORN COMPUTER NOW AVAILABLE

OTHER PRODUCTS

AVO TEST METERS

AVO 8 MK5. Latest Model.....	£122.10
AVO 71 Electronics &.....	£45.40
AVO 73 TV Service.....	£63.90
AVO MMS Minor.....	£40.50
AVO EM272 316KQ/rot input 2.....	£67.10
AVO DA116 L.C.D. Digital.....	£121.70
AVO DA211 L.C.D. Digital (Hand.....)	£58.50
AVO DA212 L.C.D. Digital (Held.....)	£81.90
Battery MEGGER 8M7/500V.....	£65.30
Wee MEGGER hand crank.....	£97.20
Plus P&P £1.32 + VAT 15%	

All Avos Meggers & accessories available.

Toroidal Transformers Now Available
30VA, 60, 100, 160, 250, 330, 530VA.
Send stamp for list.

SPECIAL OFFER
25W Soldering Iron to BS Spec. £1.75 P&P 30p + VAT 15%.

TUMBLER SWITCHES. 30 amp 240V 4 pole on-off switch £6.50. P&P 90p+VAT. 16 amp 250V AC/DC 4 pole rotary switch £5.20+90p P&P.

ANTEX 15W CN240/CN 240 £4.58 + P&P + VAT. 25W x 25 £4.74 + 62 P&P + VAT.

P.W. Purbeck oscilloscope transformer 250-0-250; 6-3V; 12-9V (author approved) £9.42 £1-04

Precision De-Solder Pumps - Spring loaded quick action button release for one hand working. Large £5.86 P&P 35p+VAT. Small £5.17 P&P 30p+VAT. Replacement tips Small 65p+VAT. Large 85p+VAT.

Telephones - Bargain many types available. 2 tone grey model 748. £11.50. £1.20 P&P + VAT 15%.

METAL OXIDE RESISTORS £1 per 100 (Electrolin) TR4 5% 470/750/1800/3600/4300/4700/5100/5600/8200/1K/1K1/1K2/1K3/1K6/1K8/2K/2K4/3K/16K/20K/22K/24K/47K/82K/100K/110K/120K/130K/180K/220K/270K/300K. P&P 50p + VAT.

100W Soldering Gun includes bulb for spot-on joints £5.39 + VAT.

MAINS BATTERY ELIMINATORS
Plugs into 13A socket 3, 6, 7.5, 9, 12V DC @ 300-1400mA output
£5-10 P&P 60p + VAT.
6, 7.5, 9v 300mA £4.60

BRIDGE RECTIFIERS

100V 25A	£1.80	500V	
100V 50A	£2.20	PM7A6	
200V 2A	£0.52	12A	
200V 4A	£0.75	£3.75	
400V 1A	£0.25		
400V 4A	£0.98	P&P 20p	
400V 6A	£1.44		

It's easy to complain about advertisements.

Every week, millions of advertisements appear in the press, on posters or in the cinema.

Most of them comply with the rules contained in the British Code of Advertising Practice and are legal, decent, honest and truthful.

But if you find one that, in your opinion, is wrong in some way, please write to us at the address below.

We'd like you to help us keep advertising up to standard.

The Advertising Standards Authority.

A.S.A. Ltd., Brook House, Torrington Place, London WC1E 7HN.

WORLD RADIO T.V. HANDBOOK

1982 ed. Price: £11.00

AMATEUR RADIO HANDBOOK 1982

by A.R.R.L. Price: £8.00

UNDERSTANDING MICROPROCESSORS

by D. L. Cannon Price: £4.50

PRACTICAL ELECTRONICS H/B

by I. Sinclair Price: £4.35

THE CATHODE-RAY OSCILLOSCOPE & ITS USE

by G. N. Patchett Price: £4.00

INTRODUCING AMATEUR ELECTRONICS

2nd ed. by I. R. Sinclair Price: £4.00

INTRODUCING MICROPROCESSORS

by I. R. Sinclair Price: £5.00

H/B OF BASIC ELECTRONIC TROUBLESHOOTING

by J. D. Lenk Price: £4.65

67 READY TO RUN PROGRAMS IN BASIC: GRAPHICS, HOME & BUSINESS, EDUCATION, GAMES

by Wm. S. Watson Price: £4.60

COMPUTER PROGRAMMING IN BASIC

by P. Bishop Price: £3.50

* ALL PRICES INCLUDE POSTAGE *

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST of British and American Technical Books

19-21 PRAED STREET LONDON W2 1NP

Phone 01-402 9176 Closed Saturday 1 p.m. Please allow 14 days for reply or delivery.

BAKER LOUDSPEAKERS "SPECIAL PRICES" POST £2

Model	Ohms	Inch	Watts	Type	Price
Major	4, 8, 16	12	30	Hi-Fi	£14
Deluxe Mk II	8	12	15	Hi-Fi	£14
Superb	8, 16	12	30	Hi-Fi	£24
Auditorium	8, 16	12	45	Hi-Fi	£22
Auditorium	8, 16	15	60	Hi-Fi	£34
Group 45	4, 8, 16	12	45	PA	£22
Group 75	4, 8, 16	12	75	PA	£22
Group 100	8, 16	12	100	PA	£24
Group 100	8, 16	15	100	PA	£32
Disco 100	8, 16	12	100	Disco	£24
Disco 100	8, 16	15	100	Disco	£32

DE-LUXE DISCO MIXER. 240V, 4 stereo channels, 2 magnetic, 2 ceramic/tape, 1 mono mic channel, twin v.u. meters, headphone monitor outlet, slider controls, suitable for panel or desk mounting, attractive grained aluminium fascia, silver knobs. £40. Post £1.

2 CHANNEL STEREO MIXER. 9 volt operated £9.50 p&P 85p.

MINI MODULE LOUDSPEAKER KIT

15 x 8 1/2in. 3-way Baffle, 5in. EMI. Bass, 5in. EMI. Middle, 3in. EMI. Tweeter; 3-way Crossover. Full assembly instructions supplied. Response 60 to 20,000 c.p.s. 12 watt RMS 8 ohms £10 per kit. Two kits £18.50. Suitable Bookshelf Cabinet £10.50 each. Post £2.

GARRARD 6-200 SINGLE PLAYER DECK

Brushed Aluminium Arm with stereo ceramic cartridge and Diamond Stylus, 3-speeds. Manual and Auto Stop/Start. Large Metal Turntable. £22. Post £2.

METAL PLINTH CUT FOR GARRARD

Size: 16 x 14 x 3in. £3.00. Silver or Black finish. Post £2.

B.S.R. SINGLE PLAYER

Battery operated deck. 9 volt D.C. motor. Ceramic stereo cartridge. 'S' shaped arm, cueing device. £20. Post £1.

B.S.R. SINGLE PLAYER P170/2 £20.00

3-speeds 11in. aluminium turntable, "slim" arm, cueing device, stereo ceramic cartridge, silver trim, bias compensator, adjustable stylus pressure, plays all records, spring suspension, 240V AC. Post £2.

B.S.R. DE-LUXE AUTOCHANGER £20

with stereo cartridge, plays all size records. Post £2

DECCA B.S.R. TEAK PLINTH 18 1/2 x 14 1/2 x 4in.

Space for small amplifier. Special price £5.95 post paid. Ditto with Garrard Board £4.95 post paid.

TINTED PLASTIC COVERS POST £2

Sizes: 14 1/2 x 12 1/2 x 3in. £5. 17 1/2 x 9 1/2 x 3 1/2in. £3. 14 x 13 x 3 1/2in. £5. 18 x 12 1/2 x 3in. £6. 16 1/2 x 13 x 4in. £6. 17 1/2 x 13 1/2 x 4 1/2in. £6. 2 1/2 x 14 1/2 x 2 1/2in. £6.

R.C.S. LOW VOLTAGE STABILISED POWER PACK KITS £2-95 Post 85p

All parts and instructions with Zener diode printed circuit, mains transformer 240V a.c. Output 6 or 7 1/2 or 9 or 12V d.c. up to 100mA or less. Please state voltage required.

PP BATTERY ELIMINATOR BRITISH

Mains stabilized power-pack 9 volt 400mA max. with overload cut out. Size 5 x 3 1/2 x 2 1/2in. £4.50. Post £1. Switched 3; 6; 7 1/2; 9 volt 400mA. Stabilized. £7.50. Post £1.

MAINS TRANSFORMERS

Model	Price	Post
250-0-250V 70mA 6-3V, 2A	£4.50	£2
250-0-250 80mA 6-3V, 3-5A, 6-3V 1A	£5.00	£2
350-0-350V 250mA 6-3V 6 amp.	£14.50	£2
300-0-300 120mA 2 x 6-3V 2A C.T., 6-3V 2A	£12.00	£2
220V 45mA, 6-3V 2A	£2.50	£1
250V 60mA, 6-3V 2A	£2.75	£1

GENERAL PURPOSE LOW VOLTAGE

Model	Price	Post
2A, 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30V	£6.00	£2
1A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£6.00	£2
2A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£10.50	£2
3A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£12.50	£2
5A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£18.00	£2
TOROIDAL 30-0-30V 4A + 20-0-20V 1A.	£10.00	£2

AUTO TRANSFORMER 115V to 240V 500W £12.00 £2-00

Model	Price	Post
6V 1/2 amps	£2.00	£1
6-0-6V, 1 1/2 amps	£3.50	£1
9-0-9V 250ma.	£1.50	80p
9V 3 amps	£3.50	£1
9-0-9V 50ma.	£1.50	80p
10-30-40V 2 amps	£3.50	£1
12V 3 amps	£3.50	£1
6-0-6V 1 1/2 A	£3.50	£1

CHARGER TRANSF. Post RECTIFIERS

Model	Price	Post
6-12v-3A	£4.00	£2
6-12v-4A	£5.50	£2
6-12v-6A	£8.50	£2
6-12v-1A	90p	80p
6-12v-2A	£1.10	80p
6-12v-4A	£2.00	80p

BLANK ALUMINIUM CHASSIS. 6 x 4in. £1.45; 8 x 6in. £1.80; 10 x 7in. £2.30; 12 x 8in. £2.60; 14 x 9in. £3.00; 16 x 6in. £2.90; 16 x 10in. £3.20. All 2 1/2in. deep. 18 swg.

ANGLE ALI. 6 x 3 x 3/4in. 18 swg. 25p.
ALUMINIUM PANELS. 18 swg. 6 x 4in. 45p; 8 x 6in. 75p; 14 x 3in. 75p; 10 x 7in. 95p; 12 x 8in. £1.10; 12 x 5in. 75p; 16 x 6in. £1.10; 14 x 9in. £1.45; 12 x 12in. £1.50; 16 x 10in. £1.75.

PLASTIC AND ALI BOXES IN STOCK. MANY SIZES ALUMINIUM BOXES. 4 x 4 x 1 1/2in. £1. 4 x 2 1/2 x 2in. £1. 3 x 2 x 1in. £1. 6 x 4 x 2in. £1.30. 7 x 5 x 3in. £2.40. 8 x 6 x 3in. £2.50. 10 x 7 x 3in. £3. 12 x 5 x 3in. £2.75. 12 x 8 x 3in. £3.60. All 18 swg with lids.

HIGH VOLTAGE ELECTROLYTICS

Model	Price	Post
8/450V	45p	8+8/450V 75p
16/350V	45p	8+16/450V 75p
32/500V	75p	32+32/500V £1.10
50/500V	£1.20	32+32/450V £1.20
8/800V	£1.20	32+32/350V 75p
		150+200/275V 70p
		220/450V 95p

HEATING ELEMENTS, WAFER THIN

Size 11x9x1/4in. Operating voltage 240v, 250w approx. Suitable for Heating Pads, Food Warmers, Convector Heaters, Propagation, etc. Must be clamped between two sheets of metal, etc. ONLY 60p EACH (FOUR FOR £2) ALL POST PAID.

Radio Component Specialist's

337, WHITEHORSE ROAD CROYDON, SURREY, U.K. TEL: 01-884 1665
Post 65p Minimum. Callers Welcome. Closed Wed.
Phone orders with Access-Barclay-Visa.
Lists 28p Stamps. Same day despatch.

INDEX TO ADVERTISERS

Ace Mailtronix	74	Litesold	73
Adam Hall Supplies	77	London Electronics College	77
A.D. Electronics	75		
Ambit	14	Maplin Electronics	Cover IV
Aura	20	Marco Trading	73
Autumn Products	72	Microstate Ltd.	76
		Midwich Computer	7
Barrie	78	Millhill	74
Beckman Instruments	27	Modern Book Co	79
Bi-Pak	8, 9	Musicraft	80
Blackstar	69		
British National Radio & Electronics School		Parndon	74
		P.C. Electronics	76
Cambridge Kits	78	Phonosonics	71
Cambridge Learning	10	Pimac	6
Chordgate	72	P.K.G. Electronics	78
Clef Products	6	Plessey Radar	72
C.R. Supply Co.	76	Powell T.	80
Crofton Electronics	14, 69	Powertran	Cover II, 14
C.U.A.	10	Printoid Ltd.	6
		Printronic	78
Dataman Design	74	Proto Design	78
		Radio Components Specialists	79
E.D.A.	55	Radio & T.V. Components	16
Electronize Design	15	Riscomp Ltd.	4
Electrovalve	74		
		Scientific Wire Co.	78
Gemini	75	Sinclair Research	12, 13
Global Specialities Corporation	11	Solid State	75
		Swanley	73
Hameg Limited	39	Technomatic	80, Cover III
Heathkit	8	Tempus	70
Hiykon Ltd.	78	T.K. Electronics	5
House of Instruments	43		
		Videotone	65
ICS Intertext	67	The Vintage Wireless Co.	76
ILP Electronics	65, 67, 69, 71, 73, 75		
		Watford Electronics	2, 3
JSO Studios	77	William Stuart Systems (Big Ears)	77
		William Stuart Systems (Vibro-scope)	78
Knight A.	76	Wilmslow Audio	10

Switch on to Television

If you're an electronics man interested in the coverage of TV technology, TELEVISION is just the magazine for you. Coverage includes the latest developments in circuitry, video and long distance Television...including in the March issue a look at Video cameras and their compatibility with VCR's – and a TV sound adaptor. As a companion read with Practical Electronics it would be invaluable

TELEVISION

Well worth a closer look!

IONISER KIT (MAINS OPERATED)

This negative ion generator gives you the power to saturate your home or office with millions of refreshing ions. Without fans or moving parts it puts out a pleasant breeze. A pure flow of ions pours out like water from a fountain, filling your room. The result? Your air feels fresh, pure, crisp and wonderfully refreshing.

All parts, PCB and full instructions **£12.50**
A suitable case including front panel, neon switch, etc. **£6.50**

HOURS:

Mon. to Fri. 9-5 pm.
Sat. 9-4.30 pm.


Price includes post & VAT.
Barclay/Access Welcome

T. POWELL,
Advance Works, P.E.,
44 Wallace Road,
London N1 1PQ.
Tel. 01-226 1489.

Please allow 28 days for delivery.

CELESTION

RICHARD ALLAN

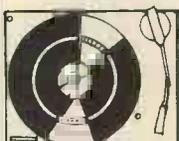

CB Antenna & Accessories in stock now!!

Stockists of leading makes of Disco Units & Lighting Equipment.
CITRONIC, FAL, TK, ICE, OPTIKINETICS, PLUTO.

Give your cabinets the professional finish.

Send 2 x 14p stamps for illustrated catalogue.

Please allow 14 days for delivery.

CROSSOVERS

100W	8 ohm	2 way
100W	8 ohm	3 way
80W	8 ohm	4 way
60W	8 ohm	2 way

All prices include VAT at 10%. Mail Orders welcome

MUSICRAFT
303 EDGWARE ROAD,
LONDON W.2. ENGLAND
TELEPHONE: 01-402 9729 / 01-402 2898

TECHNOMATIC TECHNOMATIC TECHNO

★ SPECIAL OFFER ★

2114 Low Power 450nS	1-24	25-99	100+
2114 Low Power 200nS	0.95	0.90	0.85
4116 200nS	1.00	0.95	0.90
2718 (+5v)	0.75	0.70	0.65
2732 (+5v)	2.20	2.00	1.90
6116	4.50	4.00	3.75
	6.00	5.75	7.00

CONNECTOR SYSTEM

I.D. CONNECTORS				25 WAY MINI D-CONNECTORS			DIL HEADER PLUGS		
HEADER	RECEP-	EDGE	CABLES	Solder	Solder	Solder	Solder		
PLUG	TAGLE	CONN		Bucket	Pin	Pin	type		
10 Way	220p	180p	65p			(angled)	14 pin	50p	130p
28 Way	350p	280p	390p	200p	215p	265p	16 pin	60p	140p
34 Way	450p	325p	450p	245p	255p	310p	24 pin	100p	200p
40 Way	525p	370p	280p				40 pin	275p	285p
50 Way	575p	450p	330p		100p. Locking Lever	100p			

JUMPER LEADS				EDGE CONNECTOR		EURO CONNECTORS		
24" Ribbon Cable with headers				0.1"	0.156"	DIN STD	PLUG	SKT
14 pin	16 pin	24 pin	40 pin	2x18 Way	150p	41617 31 Way	200p	200p
145p	165p	240p	380p	2x22 Way	310p	41612 2x32 Way	300p	350p
210p	230p	345p	540p	2x23 Way	335p	2x32 Way (angled)	350p	400p
Cable with Sockets				2x25 Way	350p	41612 3x32 Way	370p	420p
20 pin	26 pin	34 pin	40 pin	1x43 Way	260p	3x32 Way (angled)	450p	
160p	210p	270p	300p	2x43 Way	450p	(for 2x32 way please specify a+b or a+c)		
290p	385p	490p	540p	2x50 Way	400p			
				1x77 Way	700p			

BOOKS (NO VAT) (P&P £1.00 per book)

The Pascal Handbook	£10.06	TTL Cookbook	£7.15
CRT Controller Handbook	£5.95	CMOS Cookbook	£7.95
Understanding Microprocessors	£3.50	TTL Data Book	£7.50
Micros - Interfacing Techniques	£12.10	Video Cookbook	£5.95
Introduction to Micro Computers	£10.95	Z-80 Interfacing (1)	£7.95
6502 Assy. Lang. Prog.	£12.10	Z-80 Interfacing (2)	£9.75
8080A/8085 Assy. Lang. Prog.	£11.60	Prog. the Z80	£11.50
		Prog. the 6502	£10.25
		6502 Applications	£10.25

Please add £1.00 P&P per book

ADD SOUND - ★ ZX80/81 USER PORT ★

(As described in Oct/Nov PCW)

Port module plugs directly into ZX80/81 to provide 8 input and 8 output lines. These allow input of data from switches, photocells, sensors, joysticks etc and control of 8 relays. Also 7 segment displays and LED may be used - "VARIABLE TONE AUDIO OUTPUT CAN PRODUCE YOUR OWN SOUND EFFECTS." Port access is by simple PEEK & POKE COMMANDS. Kit £11.50.

READY BUILT AND TESTED UNIT £14.95 + 70p P&P

Reprint of PCW Oct/Nov, articles £1 + large SAE

For ZX81 users: Extender cord provided f.o.c. to enable to be plugged directly.

EXPERIMENT WITH COMPUTER VISION

★ ATOM ULTRASONIC VISION ★

Module connects to the ATOM printer port to give an ultrasonic radar picture of the surroundings, eg. room, furnishings, people. Experiment with computer measurement, image recognition, movement tracking, robot vision. Project to be described in PRACTICAL ELECTRONICS April/May 81.

★ UK101: INTERFACING SYSTEM ★

Two board interface system plugs directly into computer expansion socket to provide wide facilities accessible from BASIC or MACHINE CODE.

1) **DECODING MODULE:** Providing a dual 5v supply, 16 bit programmable I/O port, plus extensive address decoding for a wide variety of interfaces, including full decoding for a programmable sound generator, and also a 40 pin skt for further expansion.
2) **ANALOGUE BOARD:** Plugs into the decoding module to provide D/A converter, 8 channel multiplexed A/D converter with 20nS conversion time, AY3-8910 SOUND GENERATOR plus 6522 V/A provide complex timing & counting functions and additional 16 bit port.

DECODING MODULE KIT £27.50 ANALOGUE BOARD £39.95
P&P 0.75p/Kit

ACORN ATOM

A personal computer with full size QWERTY board and a built in UHF modulator to allow direct connection to domestic TV. A simple to build, simple to operate computer with all the features found in machines twice the price but with the advantage of expandability. Basic ATOM has 2K RAM and 8K ROM and on board expansion capability up to 12K + 12K.
Basic built £135, Built & Fully Expanded £185. P&P £3. 4K Floating Point ROM £20, 1K RAM (2 x 1141) £2. NEW 3A 5v Regulated Power Supply £22 + £1.50 P&P.

ATOM CONNECTORS	PLUG	SOCKET	ATOM SOFTWARE	
2x32 Way	£3.00	£4.00	Games Pack 1-10	£10 each
28 Way	£2.00	£2.00	Ft. Machine, Breakout, UFO Bomber, Disassembler	£3.50 each
10 Way	£1.20	£1.20	Prog Tool Box ROM	£25.00

Suitable high quality printers available soon, watch for details. Send SAE for ATOM memory expansion system
13K RAM or 64K DRAM.

BOOKS: Getting Acquainted with ATOM £7.95; ATOM Business £7.00; ATOM Magic Book £5.95.

UV EPROM ERASERS

UV1B (upto 6 EPROMS)	£42.00
UV14D (upto 14 EPROMS)	£61.50
UV141 (as UV14D but with timer)	£78.00

ALL ERASERS with built in safety devices.

SOFTY

PROM PROGRAMMER & ROMULATOR
Software development tool
MK11 (for 2516/2716/2532/2732). Built complete with psu £189.00 + £2 p&p

TECHNOMATIC TECHNOMATIC TECHNO

Published approximately on the 15th of each month by IPC Magazines Ltd., Westover House, West Quay Road, Poole, Dorset BH15 1JG. Printed in England by Chapel River Press, Andover, Hants. Sole Agents for Australia and New Zealand - Gordon & Gotch (A/sia) Ltd.; South Africa - Central News Agency Ltd.

Subscriptions INLAND and OVERSEAS £13.00 payable to IPC Services, Oakfield House, Perryment Road, Haywards Heath, Sussex.
Practical Electronics is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

MAPLIN the people for Atari



3 Consoles available:

Atari 400 with 16K RAM (AF36P) £345

Atari 400 with 32K RAM (AF37S) £395

Atari 800 with 16K RAM (AF02C) £645

Lots of other hardware:

Cassette Recorder	(AF28F)	£50.00
Disk Drive	(AF06G)	£345.00
Thermal Printer	(AF04E)	£265.00
Printer Interface for 400	(AF41U)	£49.95
Printer Interface for 800	(AF42V)	£49.95
Interface Module	(AF29G)	£135.00
Versawriter	(AF43W)	£169.00

16K RAM Module	(AF08J)	£64.00
32K RAM Module	(AF44X)	£125.35
32K Upgrade for 400	(AF45Y)	£75.00
Floppy Disk	(YX87U)	£2.75
Le Stick	(AC45Y)	£24.95
Joystick Controllers	(AC37S)	£13.95

For full details ask for our hardware leaflet (XH54J) SAE appreciated



NOW YOU CAN JOIN THE U.K. ATARI COMPUTER OWNER'S CLUB. An independent user's group. Four issues of the club magazine for only £1.60! Address your subscription to Graham.

THE CHOICEST GEMS OF ATARI SOFTWARE FROM MAPLIN

Adventure Games

Star Warrior	C-32K (B024B)	£28.95
Rescue At Risk	C-32K (B021X)	£22.45
Invasion Orion	C-32K (B023A)	£18.95
Dalstones of Ryn	C-32K (B022Y)	£14.95
Galactic Empire	C-24K (B014D)	£14.95
Hi-Res Adventure #2	D-48K (B025C)	£24.95
Analog Adventure	D-32K (B033L)	£24.95
Adventure Land	C-24K (B000A)	£14.95
Pirates Adventure	C-24K (B001B)	£14.95
Mission Impossible	C-24K (B003D)	£14.95
Voodoo Castle	C-24K (B004E)	£14.95
The Count	C-24K (B005F)	£14.95
Strange Odyssey	C-24K (B006G)	£14.95
Mystery Fun House	C-24K (B007H)	£14.95
Pyramid of Doom	C-24K (B008J)	£14.95
Ghost Town	C-24K (B009K)	£14.95
Savage Island I	C-24K (B010L)	£14.95
Savage Island II	C-24K (B011M)	£14.95
Golden Voyage	C-16K (YG53H)	£8.95
Energy CZar	C-8K (YG55K)	£8.95
Kingdom	C-8K (YG55K)	£8.95

Teach-Yourself Programs

Conversational French	SC-16K (YG44X)	£22.50
Conversational German	SC-16K (YG45Y)	£32.50
Conversational Spanish	SC-16K (YG46A)	£32.50
Conversational Italian	SC-16K (YG47B)	£32.50
Touch Typing	2C-16K (YG49D)	£34.95
States & Capitals	C-24K (YG56L)	£8.95
European Countries & Capitals	C-16K (YG57M)	£8.95

Learn Programming

Invitation to Programming	C-8K (YG43W)	£11.95
Basics of Animation	C-32K (B057M)	£9.95
Basics of Animation	D-32K (B058N)	£10.95
Player Missile Graphics	C-16K (B059P)	£18.95
Player Missile Graphics	D-24K (B060Q)	£19.95
Display Lists	C-16K (B051F)	£9.95
Display Lists	D-24K (B052G)	£10.95
Horiz/Vertical Scroll	C-16K (B053H)	£9.95
Horiz/Vertical Scroll	D-24K (B054J)	£10.95

Page Flipping	C-16K (B055K)	£9.95
Page Flipping	D-24K (B056L)	£10.95
Master Memory Map	Walchart (XH57M)	£4.00

Business Programs

Visicalc	D-32K (YL39N)	£119.95
Word Processor	D-32K (YG42V)	£85.00
Calculator	D-24K (YG50E)	£16.95
Graph-It	C-16K (YG51F)	£11.95
Statistics	C-16K (YG52G)	£11.95

Arcade Games

Star Raiders	E-8K (YG66W)	£29.95
Asteroids	E-8K (YG60O)	£29.95
Space Invaders	E-8K (YG70M)	£24.50
Missile Command	E-8K (YG64U)	£29.95
Super Breakout	E-8K (YG67X)	£29.95
Tari Trek	C-24K (YL36P)	£8.95
Tari Trek	D-32K (YL37S)	£11.95
Star Trek 3.5	C-32K (B015R)	£14.95
Race In Space	C-16K (B035O)	£14.95
Shooting Gallery	C-16K (B036P)	£14.95
Mountain Shoot	C-16K (B012N)	£10.95
Jawbreaker	D-48K (B026D)	£22.95
Basketball	E-8K (YG61R)	£29.95
Tank Trap	C-16K (YL34M)	£8.95
Tank Trap	D-32K (YL35O)	£11.95

Home Game Programs

Scram	C-16/24K (YG58N)	£12.95
Cypher Bowl	C-32K (B020W)	£22.45
Thunder Island	C-16K (B037S)	£10.95
Rotating Tilt	C-16K (B048C)	£14.95
Lunar Lander	C-16K (B016S)	£10.95
Jumbo Jet Lander	C-16K (B046A)	£29.95
Submarine Commander	C-16K (B047B)	£24.50
Sunday Golf	C-16K (B013P)	£10.95
Darts	C-16K (B042V)	£19.95
Tournament Pool	C-16K (B045Y)	£19.95
Snookey & Billiards	C-16K (B044X)	£19.95
Chess	E-8K (YG63T)	£29.95
Microchess	C-16K (YL40T)	£15.95
Checker King	C-16K (YL41U)	£15.95
Cribbage & Dominoes	C-16K (B043W)	£14.95

Poker Solitaire	C-16K (B017T)	£10.95
Blackjack	C-8K (YG62S)	£8.95
Fast Gammon	C-8K (YL33L)	£9.95
Reversi (Othello-type)	C-16K (B019V)	£14.95
Gomoko	C-16K (B018U)	£14.95
Hangman	C-8K (YG54J)	£8.95
Humpty Dumpty & Jack & Jill	C-16K (B038R)	£19.95
Hickory Dickory Dock	C-16K (B039N)	£19.95
British Heritage		
Jig-Saw Puzzles	C-16K (B040T)	£19.95
European Scene		
Jig-Saw Puzzles	C-16K (B041U)	£19.95
Atari Safari (25 Programs)	C-16K (B049D)	£18.95
Atari Safari (25 Programs)	D-16K (B050E)	£24.95
Mind Beggars (3 Programs)	C-16K (YL38R)	£8.95

Music Programs

Music Composer	E-8K (YG48C)	£32.50
Movie Themes (use with Music Composer)	C-16K (B034M)	£9.95

Computer Languages

Basic A +	D-48K (B031J)	£52.50
Operating System A +	D-48K (B030H)	£52.50
Basic A + &		
Operating System A +	D-48K (B032K)	£99.50
OS Forth	D-24K (YL29G)	£44.90
Pilot	E&C-8K (YG69A)	£49.50

Utilities

3D-Super Graphics	D-48K (B028F)	£29.95
3D-Super Graphics	C-48K (B029G)	£29.95
Atari World (Graphics)	D-48K (B027E)	£43.95
Assembler Editor	E-8K (YG68Y)	£34.50
Assembler	C-16K (YL32K)	£14.95
6502 Disassembler	C-8K (YL30H)	£8.95
6502 Disassembler	D-8K (YL31J)	£11.95
Character Generator	C-16K (YL27E)	£9.97
Character Generator	D-16K (YL28F)	£12.50
Telelink	E-8K (YG59P)	£14.95

Key: C = Cassette, D = Disk, E = Cartridge, 2C = 2 Cassettes etc. 8K: 16K etc. shows minimum memory requirement.

Send see now for our new software leaflet with details of all the above programs. Order As XH52G — Issue 2.

Lots of exciting new software titles available soon. Keep in touch with Maplin!

Subscribe now to America's leading Atari-only magazine — Analog — 6 issues per year for just £9.00. Order as GG24B.

MAPLIN

Maplin Electronic Supplies Ltd
P.O. Box 3, Rayleigh, Essex.
Tel: Southend (0702)
552911/554155.

Demonstrations at our shops NOW
See the amazing Atari's in action at
159-161 King St., Hammersmith W6
Tel: 01-748 0926
or at 284 London Road,
Westcliff-on-Sea, Essex.
Tel: (0702) 554000

Note: Order codes shown in brackets. Prices firm until 15th May, 1982 and include VAT and Postage and Packing (Errors excluded).