

PRACTICAL

ELECTRONICS

DECEMBER 1982

Australia \$1.35 Malaysia \$4.95 IR £1.26 (inc. VAT)

85p

PE

Micrograsp



Stylochord

Also... **MICRO-FILE Pull-out**
MICROPROCESSOR DATA

**ELECTRONIC
HOBBIES FAIR**

50p Coupon Inside

POWER PACKED — by POWERTRAN

Powertran's black boxes are packed with punch. Not only are they superb kits to buy and build they really do the job! Imaginative and ingenious design goes hand in hand with top quality materials and outstanding performance capability. With their smart black styling the kits harmonise visually as well as musically. You can build each unit independently for its set task and then gradually increase your array until you have a complete bank of formidable controllable power.

THE FIRST
WORDS AND
THE LAST
WORD IN
ELECTRONIC
KITS




Complete Kit — £49.90 + VAT

MPA 200 — is a low price, high power 100W amplifier. Its smart styling, professional appearance and performance, make it one of our most popular designs. Adaptable inputs mixer accepts a variety of sources yet straightforward construction makes it ideal for the first-time builder.



Complete Kit — £49.50 + VAT

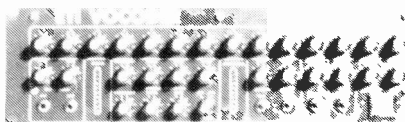Chromatque 5000 — a 5-channel lighting system powerful enough for professional discos yet controllable for home-effects. Sound to light, strobe to music level, random or sequential effects — each channel can handle up to 500W yet minimal wiring is needed with our unique single board design.




Complete Kit — £175.00 + VAT

ETI Vocoder — 14 channels, each with independent level control, for maximum versatility and intelligibility, two input amplifiers — speech/external — each with level and tone control. The Vocoder is a powerful yet flexible machine that is interesting to build and, thanks to our easy to follow construction manual, is within the capability of most enthusiasts.




Complete Kit — £64.90 + VAT

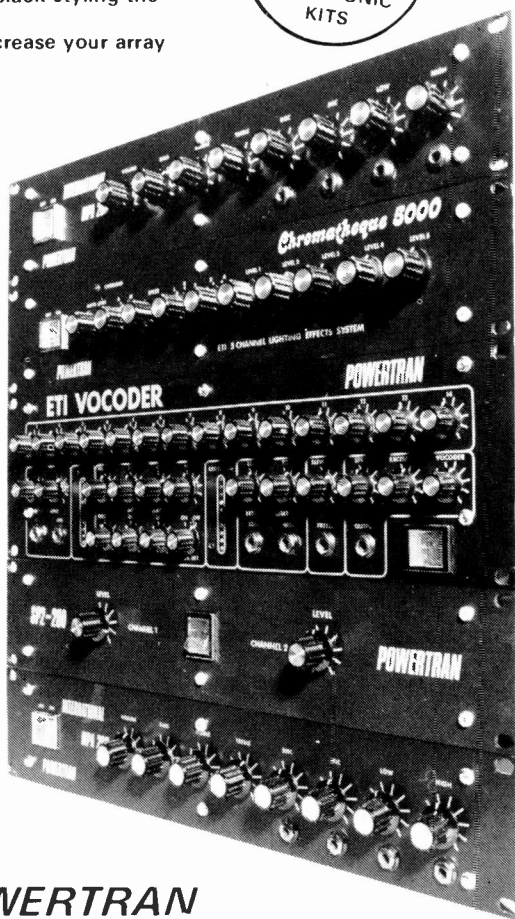SP2 2000 — twice the power with two of the reliable, durable and economic amps from the MPA 200, fed by separate power supplies from a common toroidal transformer. Superb finish and quality components throughout — up to (even over!) the standard of high priced factory-built units.



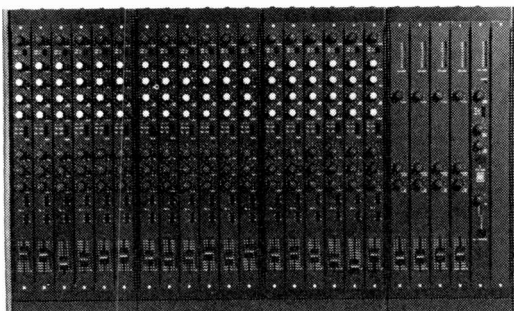STOP PRESS: NEW FROM POWERTRAN DESTINY Modular Mixer AS BEING FEATURED IN THIS MAGAZINE!



This versatile modular mixer, featured as a constructional article in this magazine can be built up to a maximum of 24 inputs, 4 outputs and an auxiliary channel. Each input channel has Mic and Line inputs, variable gain, bass and treble controls and a parametric middle frequency equalizer. There are send and return jacks, auxiliary, pan and fader controls and output group switching. The output channels have PPM displays and record and studio outputs. The auxiliary channel also has a PPM display and there is a headphone monitor jack and a built-in talk-back microphone. The mixer modules plug into base units each of which takes up to 6 channels. To eliminate hum, the power supply is in a separate cabinet.

Kit Prices:			
Input channel	£19.90	Base unit and wooden front	£27.50
Output channel	£18.50	Pair of mahogany end cheeks	£12.50
Auxiliary channel	£22.50	Power Supply and cabinet	£19.50
Blank Panel	£3.00	All prices are VAT exclusive	

.... Quite simply the best way to make music



PORTWAY INDUSTRIAL ESTATE, ANDOVER, HANTS SP10 3WN
(0264) 64455.

PRICE STABILITY: Order with confidence. Irrespective of any prices changes we will honour all prices in this advertisement until Jan. 31st 1983. If this month's advertisement is mentioned with your order. Errors and VAT rate changes excluded.

EXPORT ORDERS: No VAT. Postage charged at actual cost plus £1 handling and documentation.

U.K. ORDERS: Subject to 15% surcharge for VAT. No charge is made for carriage, or at current rate if changed.

SECURICOR DELIVERY: For this optional service (U.K. mainland only) add £2.50 (VAT inclusive) per kit. FREE ON ORDERS OVER £100.

SALES COUNTER: If you prefer to collect kit from the factory, call at Sales Counter. Open 9 a.m.-12 noon, 1-4.30 p.m. Monday-Friday.



MORE SUPERB KITS IN OUR
CATALOGUE



PRACTICAL ELECTRONICS

CONSTRUCTIONAL PROJECTS

STYLOCHORD by <i>Stephen Ibbs</i>	22
Twin probe stylus organ	
MICROGRASP PART 1 by <i>Richard Becker</i>	30
Computer controlled robot arm	
ULTIMUM PART 2	36
RAM and battery back-up boards	
SEMI-PROFESSIONAL MIXING DESK PART 3	44
P.S.U. and using the Desk	
MICROCONTROLLER PART 2 by <i>M. Tooley BA and D. Whitfield MA, MSc</i>	50
P.S.U., Disbug and 6800 programming	

GENERAL FEATURES

SEMICONDUCTOR UPDATE by <i>R. W. Coles</i>	49
Featuring the MC1468705G2, D60T, OP-22	
INGENUITY UNLIMITED	61
Universal Probe—Disco Lights Sequencer	

NEWS AND COMMENT

EDITORIAL	17
NEWS AND MARKET PLACE	18
Including Countdown and Points Arising	
SPACEWATCH by <i>F. W. Hyde</i>	29
Extra-terrestrial activities chronicled	
BAZAAR	35, 46, 47, 62
Free readers' advertisements	
INDUSTRY NOTEBOOK by <i>Nexus</i>	42
News and views on the electronics industry	
SPECIAL OFFER—DIGITAL PULSER KIT	43
All-purpose pulser for TTL and CMOS	
SPECIAL OFFER—CASSETTES	57
Bargain offer on high quality cassettes	
PATENTS REVIEW	59
PIN bulletins and hi-fi	
INDEX FOR VOLUME 18	64

SPECIAL SUPPLEMENT

MICRO-FILE by <i>R. W. Coles</i>	between pages 42 & 43
---	-----------------------

OUR JANUARY ISSUE WILL BE ON SALE FRIDAY, DECEMBER 10th, 1982
(for details of contents see page 66)

© IPC Magazines Limited 1982. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

Practical Electronics December 1982

SPEAKERS

BQ. 0.3W. 2". 2.25". 2.5". 3". 80p

0.3W. 2.5" 40Q. 64Q or 80Q 80p

DIODES

AA119	15	1A 100V	18
AA129	20	1A 100V	25
AA130	15	1A 100V	25
BA100	15	1A 100V	25
BA130	24	1A 100V	25
BY100	24	1A 100V	25
BY126	12	1A 100V	34
BY127	12	2A 50V	30
CR033	250	2A 200V	46
CR033	40	2A 400V	46
OA47	12	2A 600V	65
OA70	12	6A 100V	83
OA79	15	6A 100V	95
OA81	20	6A 100V	95
OA85	15	10A 200V	215
OA90	15	10A 600V	298
OA91	8	25A 200V	240
OA95	8	25A 600V	395
OA200	8	BY164	56
OA202	8	VM18	50
IN914	4		
IN916	4		
1N4001/2	5		
1N4003	6		
1N4004/5	6		
1N4006/7	6		
1N4148	4		
1N5401	15		
1N5404	16		
1N5406	17		
1N5408	19		
1S44	9		
1S921	4		
6A100V	40		
6A400V	50		
6A800V	65		
Noise Diode	25J		195

SCR's

Thyristors

0.8A-100V	32	3A 100V	48
5A/300V	38	3A 800V	55
5A/400V	40	3A 100V	60
5A/600V	48	8A 400V	69
8A/300V	68	8A 800V	115
8A/600V	95	12A 100V	78
12A/100V	78	12A 400V	82
12A/400V	95	12A 800V	135
12A/800V	188	16A 100V	103
BT108	150	16A 400V	105
BT116	180	16A 800V	180
CI068	38	25A 400V	185
TIC44	24	25A 800V	295
TIC45	29	25A 100V	295
TIC47	35	30A 400V	480
2N5062	32	30A 400V	480
2N5064	38	12A 800V	120
2N4444	130		

DIAC

ST2 25 100 70p 500 325p

OPTO ELECTRONICS

LEDs including Clips

TIL209 Red 3mm	10
TIL211 Green 3mm	14
TIL212 Yellow	12
TIL220 2" Red	14
2" Yel. Grn. Amber	14
Rectangular LEDs with two part clip. R. G & Y	18
Rectangl. Stackable LEDs	18
Triangular LEDs R&G	18
0.2" Flashing LED Red	55
0.2" Bi colour LEDs	59
Red/Green	65
Green/Yellow	80
0.2" Tri colour LEDs	85
Red/Green/Yellow	85
0.2" Infra Red Bright	25
LD271 Infra Red (emit)	46
TIL32 Infra Red (emit)	52
SFH205 (detector)	118
TIL78 (detector)	54
TIL38	82
TIL8	82
TIL100	82

0.5" LIQUID CRYSTAL DISPLAYS

3 1/2 digit	495
4 digit	530
6 digit	625

8PX21

8PX21	195
8PW21	295
8PX65	270
IL74	45
IL74	99
ILQ74	185
TIL111	75
OC7P1	120
ORP12	78
ORP81	85
2N577	85
4N33	135

OPTO SWITCH

52 Reflective	118
TIL139	170
54 Slotted similar	170
10 RS	186

ALUM. BOXES

3x2x1	65
4x2x1	85
4x2x2	103
4x4x2	120
5x4x2	105
5x2x1	90
5x2x2	130
5x4x1	99
5x4x2	120
6x4x2	120
6x4x3	150
7x5x3	180
8x6x3	210
10x4x1	240
10x7x3	275
12x5x3	260
12x8x3	295

7 Segment Displays

TIL322 5" C.A.	115
TIL322 5" C.Ch	115
DL704 3" C.Ch	99
DL707 3" C.A.	99
FND357 or 500	120
3" Green C.A.	140
±1 3" Red or Green	150
Bargraph 10 seg.	225
Bargraph NSM3914	500

FERRICHLORIDE

1lb bag Anodup 15p

1lb bag 50pp&p

DALOETCH RESIST

Pen - Spare tip 90p

COPPER CLAD BOARDS

Fibre Single	Double	SRBP
6"x6"	90p	110p
6"x12"	150p	195p

VERO BOARDS

1" VQ Board	180
2"x3 1/2" Clad	374
2"x3 1/2" Plain	144
2"x5" C.C.H	91p
3"x3 1/2" C.C.H	91p
3"x5" 105p	87p
3"x7 1/2" 360p	232p
4"x18" 470p	
Pkt. of 100 pins	50p
Spot Face Cutter	135p
Pin Insertion Tool	178p

VERO WIRING PEN and Spool

Spare Wire (Spool) 75p

Wire Wrapping Stakes 100

SPECIAL OFFER

2114L-2 90p 2532 350p 2716 215p 2732 350p 4116 85p 4816-100ns 225p 6116-150ns 290p 6520/21 115p 6522 300p 6820/6821 100p

PRINTERS

● **MX80T** 10" Tractor Feed, 9x9 matrix, 80 column, 80 CPS, Bi-directional, Centronic Interface. Baud Rate 110-9600. £275

● **MX80FT/3** Tractor & Friction feed. Has hi-resolution, bit image graphics, Subscript & Superscript, italics & underlining facility plus all the MX80FT features. £325

● **NEC PC-8023BE-C**, 100CPS bi-directional, logic seeking, 80 column, 7x9 Dot matrix, super/subscript, underlining, true decoders Tractor/Friction, Hi-Res, 2K Buffer, Proportional Spacing, at a Special Price £295

ANTEX Soldering Irons

C15W	450
CC17W	475
CXN15W	490
X25W	500

Spare bits 85

Elements 210

Iron stands 165

Heat Shunt 30

ASTECUHF MODULATORS

6MHz 280p

8MHz Wide 280p

Bandwidth 425p

ULTRASONIC TRANSDUCERS

40KHz Transmitter & Receiver 325p/pair

DIL SOCKETS

Low profile	Wire wrap
8 pin	8p 25p
14 pin	10p 35p
16 pin	10p 42p
18 pin	18p 52p
20 pin	20p 60p
22 pin	22p 65p
24 pin	25p 70p
28 pin	28p 80p
40 pin	30p 99p

ZIF DIL SOCKET

16 way	475p
24 way	575p
28 way	850p
40 way	975p

DIL PLUGS (Headers)

Pins	Solder	IDC
14	38p	95p
16	42p	100p
24	88p	138p
40	195p	218p

RIBBON CABLE

Ways	Price per foot
10	12p
20	25p
20	25p
26	35p
34	48p
40	55p
60	75p

'D' CONNECTORS:

Miniature

Pins	9	15	25	37
Male	80p	110p	160p	240p
Female	150p	210p	250p	350p
Strait	170p	160p	220p	310p
Strait	105p	160p	200p	338p
Strait	165p	215p	290p	440p
Strait	175p	200p	300p	420p

COVERS Top & Side Entry

95p 90p 100p 110p

IDC 25 way Pin 385p, Skt. 450p

Amphenol Plugs

24 way	156p
2x10 way	135p
2x15 way	140p
2x18 way	180p
2x22 way	199p
2x23 way	210p
2x25 way	225p
2x28 way	210p
2x30 way	235p
2x36 way	315p
2x40 way	315p
2x43 way	395p
2x75 way	550p

EDGE CONNECTORS

Two rows

24 way	156p
2x10 way	135p
2x15 way	140p
2x18 way	180p
2x22 way	199p
2x23 way	210p
2x25 way	225p
2x28 way	210p
2x30 way	235p
2x36 way	315p
2x40 way	315p
2x43 way	395p
2x75 way	550p

JUMPER LEADS

Ribbon Cable Assembly

DIL Plug (Headers)

Single Ended Lead, 24" long

Length	14pin	16pin	24pin	40pin
24"	145p	165p	240p	380p

Double Ended Leads:

Length	14pin	16pin	24pin	40pin
12"	185p	205p	300p	485p
18"	198p	215p	315p	490p
24"	210p	235p	345p	540p
36"	230p	250p	375p	595p

ID HEADER SOCKET Jumper Leads 24"

Length	20pin	26pin	34pin	40pin
1 end	160p	200p	260p	300p
2 ends	290p	370p	480p	525p

COMPUTER CORNER

● **EPSON MX Series Printers.** Full range available. See box above for details.

● **SEIKOSHA GP100A** - Unihammer Printer, normal & double width characters, dot resolution graphics 10" Tractor feed, parallel interface standard. FREE 500 Sheets £175

● **EPSON HX20** Microcomputer. Portable, Full size Keyboard, LCD Virtual Screen, 5x7 Dot Matrix Printer incorporated £1299

● **SOFTY-2.** The complete Microprocessor development system. New powerful instructions. Accepts any 24 pin 5V single rail EPROM. Supplied fully built & tested. Price includes plug-in PSU, Watford's extended warranty & a FREE 2732. £169

● **WEMON.** Watford's 3K Ultimate Monitor IC for Superboard & UK101. £10

● **VIDEO MONITOR 9"** fully cased. B&W. Fully guaranteed. 15MHz bandwidth value for money. £69

● **TEX EPROM ERASER.** Erases up to 32 ICs in 15-30 min. £33

● **TEX EPROM ERASER** with the Solid-State 30 minute Electronic Timer. £43

● **Spare UV lamp bulbs** £9

● **5V/5A PSU** Ready built and tested £25

● **MULTIRAIL PSU KIT.** Output: +5V/5A; +12V; +25V; -5V; -12V @ 1A. £40

● **Attractive Beige/Brown ABS CASE** for Superboard/UK101 or Home Brew £29

● **Full ASC11** coded keyboard type '756' £39

● **4 x 4 matrix keypad** (reed switch assembly) £4

● **C12 COMPUTER Grade Cassettes** in Library Cases 40p

● **STACK-PACK.** Unique 10 section stackable Drawers rack including 10 x C12 Computer grade Cassettes. 550p

● **8" Fan fold paper** (1000 sheets) (no VAT) £7

● **9 1/2" Fan fold paper** (1000 sheets) (no VAT) £7

● **Teleprinter Roll** (no VAT) £3.50

(P&P on some of the above items is extra)
Call in at our shop for demonstration of any of the above items. Be satisfied before you buy.

VOLTAGE REGULATORS

1A	T03	+ve	-ve	220p
5V	7805	145p	7905	220p
12V	7812	145p	7912	220p
15V	7815	145p	7915	220p
18V	7818	150p		

1A T0220 Plastic Casing

5V	7805	40p	7905	45p
12V	7812	40p	7912	45p
15V	7815	40p	7915	45p
18V	7818	40p	7918	45p
24V	7824	40p		

100mA T092 Plastic Casing

5V	78L05	30p	79L05	60p
6V	78L6	30p		
8V	78L8	30p		
12V	78L12	30p	79L12	60p
15V	78L15	30p	79L15	60p

LM300H 170 LM305H 140 LM304H 160 LM309H 135 LM305 5V/5A 550 LM317K 320 LM3712 12V/5A 580 LM317P 99 LM378-5 10 LM323K 500 LM378-5 10 LM337T 175 LM378-5 10 LM723 35 LM378-5 10 LM723 35 LM378-5 10 LM723 35

SWITCHES

SLIDE 250V

1A DPDT	14
1A DPDT C/OFF	15
1A DP on/on/off	40
4 pole d/c over	240

PUSH BUTTON

Spring loaded

Latching or Momentary 6A

SPDT c/c over 99

OPDT c/c over 145

SUB-MIN TOGGLE

SP changeover 60

SPST on/off 54

SPST c/c over 85

SPDT Biased 105

DPDT 6 wags 75

OPDT c/c over 88

DPDT on/on/off 185

DPDT Biased 145

3 pole c/c over 205

ROCKER: 5A 250V SPST 28p

ROCKER: 10A 250V SPST 28p

ROCKER: With neon lights red when on 85p

ROCKER: (White) 10A 250V DPDT 72p

ROTARY: Make your own Multiway Switch Shifting Assembly accommodates up to 6 wafers 90p

Break before make Wafers. Silver contacts

1 pole 12 way, 2 pole 6 way, 3 pole 4 way, 4 pole 3 way, 6 pole 2 way 45p

Mains DPST Switch to fit Screen & Spacers 6p

ROTARY: (Adjustable Stop Type)

1 pole 2 to 12 way, 2 pole 2 to 6 way, 3 pole 2 to 4 way, 4 pole 2 to 3 way 45p

ROTARY: Mains 250V AC 4 Amp 56p

DIL SWITCHES: (SPST)

4 way 65p

6 way 80p; 8 way 87p; 10 way 135p; (SPDT) 4 way 190p

THUMBWHEEL

Mini front mounting

Decade Switch Module 250p

B.C.D. Switch Module 275p

Mounting Cheeks (pair) 75p

PROXIMITY Switch with magnet 125p

CRYSTALS

3.576KHz	100
100KHz	235
200KHz	268
455KHz	370
1MHz	275
1.068MHz	392
1.8MHz	275
1.5MHz	420
1.6MHz	395
1.8MHz	395
1.8432M	200
2.4576M	225
2.5MHz	225
3.2768M	150
3.57954M	98
3.6864M	300
4.0MHz	150
4.032M	290
4.194304M	200
4.433619M	100
4.608MHz	200
4.8MHz	200
5.0MHz	175
5.185MHz	300
5.24288M	390
6.0MHz	140
6.144MHz	150
6.5536MHz	200
7.0MHz	150
7.168MHz	250
7.68MHz	200
8.0MHz	150
8.8333M	395
8.86727M	175
9.00MHz	200
9.375MHz	375
10.0MHz	150
10.5MHz	250
10.7MHz	150
10.24MHz	200
12.0MHz	175
12.58MHz	300
14.31818M	170
14.765MHz	250
15.0MHz	200
16.0MHz	180
18.432M	150
19.68MHz	150
20.0MHz	200
24.0MHz	170
24.930MHz	325
26.69M	150
26.670MHz	325
27.125MHz	295
27.45M	190
27.648MHz	330
38.66667M	175
48.0MHz	175
55.5MHz	400
100.0MHz	375
116.0MHz	300
145.8MHz	225

SPECIAL OFFER

TEX EPROM ERASER with SAFETY Switch £35

Electroni Solid-State TIMER for above £12

BBC MICRO UPGRADE KITS

Upgrade your BBC Micro with our upgrade kit and save yourself £ s s s . . .



- 16K MEMORY (8x4816-100ns) BBC1 £18.00
- Printer User I/O Port BBC2 £8.20
- SK10 with 36" Cable £2.00
- Complete Printer Cable 36" £12.00
- SK9 with 36" Cable £3.00
- Disc Interface Kit BBC3 £41.00
- Analogue I/O Kit BBC4 £6.75
- Serial I/O Kit BBC5 £7.50
- Expansion Bus Kit BBC6 £6.50
- SK11 with Cable 36" £3.00
- SK12 with Cable 36" £3.75
- Complete Upgrade Kit from Model A to B £45
- Complete range of Cables & Connectors for BBC Micro available. Send SAE for list.

FLOPPY DISC DRIVES

- TEAC Single FD-50A uncased £125
- TEAC Single FD-50A cased with PSU £180
- TEAC Twin FD-50A cased with PSU £335
- TEAC Single FD-50E 80 track cased with PSU £238
- SIEMENS FDD 100-5 Cased, Head, Motors, track zero micro switch & motor control PCB with read, write & control electronics plus cable (Ideal for Apple) £215
- Apple II Interface Card for above. £39
- 10 Floppy Diskettes 5 1/4" S.D. Verbatim £22
- 10 Floppy Diskettes 5 1/4" D.D. Verbatim £30


WATFORD ELECTRONICS
Tel. (0923) 40588 Telex. 8956095

GET BIG POWER

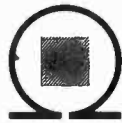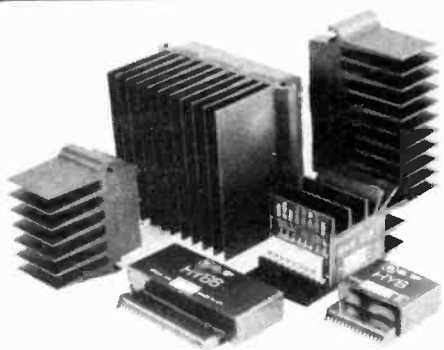

Modular Amplifiers the third generation

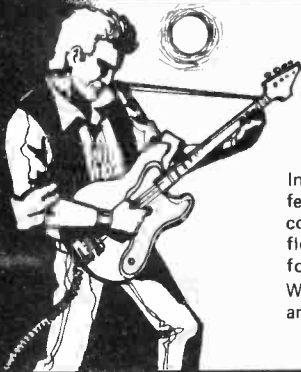Due to continuous improvements in components and design ILP now launch the largest and most advanced generation of modules ever.



WE'RE INSTRUMENTAL IN MAKING A LOT OF POWER

In keeping with ILP's tradition of entirely self-contained modules featuring, integral heatsinks, no external components and only 5 connections required, the range has been optimized for efficiency, flexibility, reliability, easy usage, outstanding performance, value for money.

With over 10 years experience in audio amplifier technology ILP are recognised as world leaders.



BIPOLAR MODULES

Module Number	Output Power Watts rms	Load Impedance Ω	DISTORTION T.H.D. Typ at 1KHz	I.M.D. 60Hz/7KHz 4:1	Supply Voltage Typ	Size mm	WT gms	Price inc. VAT
HY 30	15	4-8	0.015%	<0.006%	± 18	76 x 68 x 40	240	£8.40
HY 60	30	4-8	0.015%	<0.006%	± 25	76 x 68 x 40	240	£9.55
HY 120	60	4-8	0.015%	<0.006%	± 25	120 x 78 x 40	420	£18.69
HY 124	60	4	0.01%	<0.006%	± 26	120 x 78 x 40	410	£20.75
HY 128	60	8	0.01%	<0.006%	± 35	120 x 78 x 40	410	£20.75
HY 244	120	4	0.01%	<0.006%	± 35	120 x 78 x 50	520	£25.47
HY 248	120	8	0.01%	<0.006%	± 50	120 x 78 x 50	520	£25.47
HY 464	180	4	0.01%	<0.006%	± 45	120 x 78 x 100	1030	£38.41
HY 468	180	8	0.01%	<0.006%	± 60	120 x 78 x 100	1030	£38.41

Protection: Full load line. Slew Rate: 15V/ μ s. Rise time: 5 μ s. S/N ratio: 100db. Frequency response (-3dB): 15Hz - 50KHz. Input sensitivity: 500mV rms. Input Impedance: 100K Ω . Damping factor: 100Hz > 400.

PRE-AMP SYSTEMS

Module Number	Module	Functions	Current Required	Price inc. VAT
HY 6	Mono pre-amp	Mic/Mag. Cartridge/Tuner/Tape/Aux. + Vol/Bass/Treble	10mA	£7.60
HY 66	Stereo pre-amp	Mic/Mag. Cartridge/Tuner/Tape/Aux. + Vol/Bass/Treble/Balance	20mA	£14.32
HY 73	Guitar pre-amp	Two Guitar (Bass Lead) and Mic + separate Volume Bass Treble + Mix	20mA	£15.36
HY 78	Stereo pre-amp	As HY66 less tone controls	20mA	£14.20

Most pre-amp modules can be driven by the PSU driving the main power amp. A separate PSU 30 is available purely for pre-amp modules if required for £5.47 (inc. VAT). Pre-amp and mixing modules in 18 different variations. Please send for details.

Mounting Boards

For ease of construction we recommend the B6 for modules HY6-HY13 £1.05 (inc. VAT) and the B66 for modules HY66-HY78 £1.29 (inc. VAT).

POWER SUPPLY UNITS (Incorporating our own toroidal transformers)

Model Number	For Use With	Price inc. VAT
PSU 21X	1 or 2 HY30	£11.93
PSU 41X	1 or 2 HY60, 1 x HY6060, 1 x HY124	£13.83
PSU 42X	1 x HY128	£15.90
PSU 43X	1 x MOS128	£16.70
PSU 51X	2 x HY128, 1 x HY244	£17.07

MOSFET MODULES

Module Number	Output Power Watts rms	Load Impedance Ω	DISTORTION T.H.D. Typ at 1KHz	I.M.D. 60Hz/7KHz 4:1	Supply Voltage Typ	Size mm	WT gms	Price inc. VAT
MOS 128	60	4-8	<0.005%	<0.006%	± 45	120 x 78 x 40	420	£30.41
MOS 248	120	4-8	<0.005%	<0.006%	± 55	120 x 78 x 80	850	£39.86
MOS 364	180	4	<0.005%	<0.006%	± 55	120 x 78 x 100	1025	£45.94

Protection: Able to cope with complex loads without the need for very special protection circuitry (fuses will suffice).

Slew rate: 20V/ μ s. Rise time: 3 μ s. S/N ratio: 100db. Frequency response (-3dB): 15Hz - 100KHz. Input sensitivity: 500mV rms. Input impedance: 100K Ω . Damping factor: 100Hz > 400.

'NEW to ILP' In Car Entertainment

C15

Mono Power Booster Amplifier to increase the output of your existing car radio or cassette player to a nominal 15 watts rms.

Very easy to use.

£9.14 (inc. VAT)

Robust construction.

Mounts anywhere in car.

Automatic switch on.

Output power maximum 22w peak into 4 Ω .

Frequency response (-3dB): 15Hz to 30KHz. T.H.D. 0.1% at 10w 1KHz.

S/N ratio (DIN AUDIO) 80dB. Load Impedance 3 Ω .

Input Sensitivity and impedance (selectable) 700mV rms into 15K Ω 3V rms into 8 Ω .

Size 95 x 48 x 50mm. Weight 256 gms.

C1515

Stereo version of C15.

£17.19 (inc. VAT)

Size 95 x 40 x 80. Weight 410 gms.

Please note: X in part no. indicates primary voltage. Please insert "0" in place of X for 110V, "1" in place of X for 220V, and "2" in place of X for 240V.

WITH A LOT OF HELP FROM **ILP** ELECTRONICS LTD

PROFESSIONAL HI-FI THAT EVERY ENTHUSIAST CAN HANDLE...

Unicase

Over the years ILP has been aware of the need for a complete packaging system for its products, it has now developed a unique system which meets all the requirements for ease of assembly, adaptability, ruggedness, modern styling and above all price.

Each Unicase kit contains all the hardware required down to the last nut and bolt to build a complete unit without the need for any special tools.

Because of ILP's modular approach, "open plan" construction is used and final assembly of the unit parts forms a compact aesthetic unit. By this method construction can be achieved in under two hours with little experience of electronic wiring and mechanical assembly.

Hi Fi Separates

UC1 PRE AMP UNIT: Incorporates the HY78 to provide a "no frills", low distortion, ($<0.01\%$), stereo control unit, providing inputs for magnetic cartridge, tuner, and tape/monitor facilities. This unit provides the heart of the hi fi system and can be used in conjunction with any of the UP Unicase series of power amps. For ultimate hum rejection the UC1 draws its power from the power amp unit.

POWER AMPS: The UP series feature a clean line front panel incorporating on/off switch and concealed indicator. They are designed to compliment the style of the UC1 pre-amp. Performance for each unit which includes the appropriate power supply, is as specified on the facing page.




Power Slaves

Our power slaves, which have numerous uses i.e. instrument, discotheque, sound reinforcement, feature in addition to the hi fi series, front panel input jack, level control, and a carrying handle. Providing the smallest, lowest cost, slave on the market in this format.

UNICASES

HiFi Separates						Price inc. VAT
UC1	Preamp					£29.95
UP1X	30 + 30W/4-8Ω	Bipolar	Stereo	Hi-Fi		£54.95
UP2X	60W/4Ω	Bipolar	Mono	Hi-Fi		£54.95
UP3X	60W/8Ω	Bipolar	Mono	Hi-Fi		£54.95
UP4X	120W/4Ω	Bipolar	Mono	Hi-Fi		£74.95
UP5X	120W/8Ω	Bipolar	Mono	Hi-Fi		£74.95
UP6X	60W/4-8Ω	MOS	Mono	Hi-Fi		£64.95
UP7X	120W/4-8Ω	MOS	Mono	Hi-Fi		£84.95
Power Slaves						
US1X	60W/4Ω	Bipolar	Power	Slave		£59.95
US2X	120W/4Ω	Bipolar	Power	Slave		£79.95
US3X	60W/4-8Ω	MOS	Power	Slave		£69.95
US4X	120W/4-8Ω	MOS	Power	Slave		£89.95

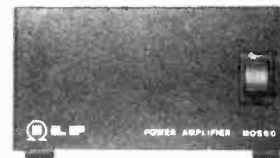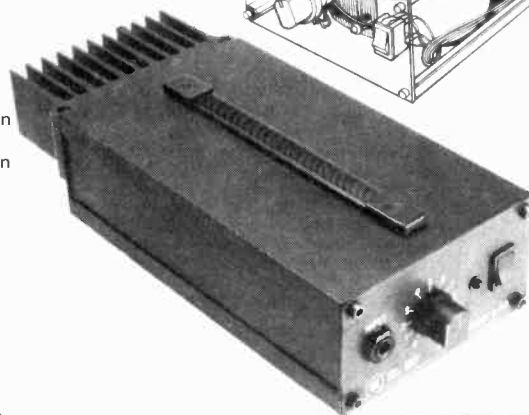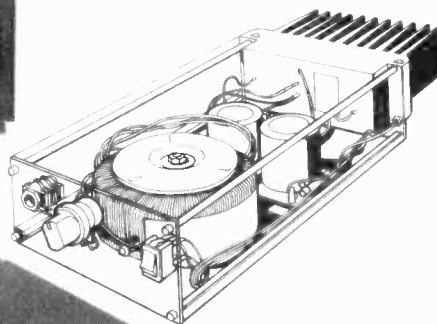Please note X in part number denotes mains voltage. Please insert '0' in place of X for 110V, '1' in place of X for 220V (Europe), and '2' in place of X for 240V (U.K.). All units except UC1 incorporate our own toroidal transformers.



TO ORDER USING OUR FREEPOST FACILITY

Fill in the coupon as shown, or write details on a separate sheet of paper, quoting the name and date of this journal. By sending your order to our address as shown at the bottom of the page opposite, with FREEPOST clearly shown on the envelope, you need not stamp it. We pay postage for you. Cheques and money orders must be crossed and made payable to I.L.P. Electronics Ltd, if sending cash, it must be by registered post. To pay C.O.D. please add £1 to TOTAL value of order.

PAYMENT MAY BE MADE BY ACCESS OR BARCLAYCARD IF REQUIRED



Post to: ILP Electronics Ltd, Freepost,
Graham Bell House, Roper Close,
Canterbury, CT2 7EP, Kent, England.
Telephone (0227) 54778
Technical (0227) 64723
Telex 965780

Please send me the following _____

Total purchase price _____

I enclose Cheque ☐ Postal Orders ☐ Int. Money Order ☐

Please debit my Access/Barclaycard No. _____

Name _____

Address _____

Signature _____

BI-PAK BARGAINS



5121 SCREWDRIVER SET

6 precision screwdrivers in hinged plastic case. Sizes — 0.8, 1.4, 2.2, 2.9 and 3.8mm. **£1.75**

5131 NUT DRIVER SET

5 precision nut drivers in hinged plastic case. With turning rod. Sizes — 3, 3.5, 4, 4.5 and 5mm. **£1.75**

5141 TOOL SET

5 precision instruments in hinged plastic case. Crosspoint (Phillips) screwdrivers — H 0 and H 1 Hex key wrenches — 1.5, 2 and 2.5mm. **£1.75**

5151 WRENCH SET

5 precision wrenches in hinged plastic case. Sizes — 4, 4.5, 5, 5.5 and 6mm. **£1.75**

BUY ALL FOUR SETS 5121-5151 and get HEX KEY SET FREE

HEX KEY SET ON RING

Sizes 1.5, 2, 2.5, 3

4, 5, 5.5 and 6mm

Made of hardened steel

HX/1 **£1.25**



"IRRESISTABLE RESISTOR BARGAINS"

Pak No.	Qty.	Description	Price
SX10	400	Mixed All Type Resistors	£1
SX11	400	Pre-formed 1/4 watt Carbon Resistors	£1
SX12	200	1/4 watt Carbon Resistors	£1
SX13	200	1/4 watt Carbon Resistors	£1
SX14	150	1/4 watt Resistors 22 ohm-2M Mixed	£1
SX15	100	1 and 2 watt Resistors 22 ohm-2M Mixed	£1

Paks SX12-15 contain a range of Carbon Film Resistors of assorted values from 22 ohms to 2.2 meg. Save pounds on these resistor paks and have a full range to cover your projects.

*Quantities approximate, count by weight

25 pieces of Audio Plugs, Sockets and Connectors to include DIN 180, 240, 240 Pin, Speakers, Phono, Jack Stereo and Mono etc Valued at well over £3 normal! Order No. SX25. Our Price **1.50** per pak.

Guaranteed to save you money

SX26 3 Pcs of 6 pin 240 Pin Plugs and Chassis Sockets 50p

SX27A 60 Assorted Polystyrene Bead Capacitors Type 9500 Series PPD £1.00

SX28A 50 Assorted Silver Mica Caps 5.6pF-150pF £1.00

SX29A 50 Assorted Silver Mica Caps 180pF-470pF £1.00

SX30A 50 High Voltage Disc Ceramics 750v min up to 8KV Assorted useful values £1.00

SX31A 50 Wirewound 9 watt (avg) Resistors Assorted values 10hm-12K £1.00

"CAPABLE CAPACITOR PAKS"

Pak No.	Qty.	Description	Price
SX16	250	Capacitors Mixed Types	£1
SX17	200	Ceramic Capacitors Miniature Mixed	£1
SX18	100	Mixed Ceramics 1pf-56pf	£1
SX19	100	Mixed Ceramics 68pf-0.5mF	£1
SX20	100	Assorted Polyester/Polystyrene Capacitors	£1
SX21	60	Mixed C280 type capacitors metal foil	£1
SX22	100	Electrolytics, all sorts	£1
SX23	50	Quality Electrolytics 50 1000mF	£1
SX24	20	Tantalum Beads, mixed	£1

*Quantities approximate, count by weight

BARGAINS

SX91	20 x Large, 2" RED LED	£1
SX42	20 small 125 Red LEDs	£1
SX43	10 Rectangular Green LEDs 2	£1
SX46	30 Assorted Zener Diodes 250mw-2 watt mixed voltages, all coded New	£1
SX47	4 Black Instrument Knobs—winged with pointer 1/4" Standard screw. Fit size 29 x 20mm	50p
SX49	20 Assorted Slider Knobs Black/Chrome, etc	£1
SX80	12 Neons and Filament Lamps. Low voltage and mains — various types and colours — some panel mounting	£1

BRAND NEW LCD DISPLAY MULTITESTER.

RE 188m
LCD 10 MEGOHM INPUT IMPEDANCE
*3 1/2 digit * 16 ranges plus HFE test facility for PNP and NPN transistors * Auto zero, auto polarity * Single handed pushbutton operation * Over range indication * 12 5mm (1/2-inch) large LCD readout * Diode check * Fast circuit protection * Test leads, battery and instructions included

Max indication 1999 or — 9999

Polarity indication Negative only

Positive readings appear without + sign

Input impedance 10 Megohms

Zero adjust Automatic

Sampling time 250 milliseconds

Temperature range —5°C to 50°C

Power Supply 1 x PP3 or equivalent 9v battery

Consumption 20mW

Size 155 x 88 x 31mm

RANGES

DC Voltage 0-200mv

0-2-20-200-1000V Acc. 0.8%

AC Voltage 0-200-1000V


Acc. 1.2% OC Current 0-200uA

0-2-20-200mA 0-10 A Acc. 1.2%

Resistance 0-2-20-200k ohms

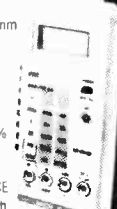0-2 Megohms Acc. 1%

BI-PAK VERY LOWEST POSSIBLE PRICE **£35.00** each




MINI VICE

This small cast iron quality made vice will clamp on to any bench or table having a max thickness of 1 1/2". The 2 1/2" jaws open to max of 1 1/2". Approx size 80 x 120 x 66mm

Bi-Pak's Mini Vice at a Mini Price only

£2.50

ORDER NO. SX82

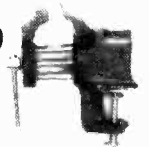

The Third and Fourth Hand...

... you always need

but have never got until now

This helpful unit with Rod mounted

horizontally on Heavy Base. Crocodile clips

attached to rod ends. Six ball & socket joints

give infinite variation and positions through

360° also available attached to Rod a 2 1/2" diam

magnifier giving 2.5 x magnification. Helping

hand unit available with or without magnifier

Our Price with magnifier as illustrated ORDER

NO. T402 **£5.50**

Without magnifier ORDER NO. T400 **£4.75**



BI-PAK SOLDER-DESOLDER KIT

Kit comprises ORDER NO. SX80

1 High Quality 40 watt General Purpose

Lightweight Soldering Iron 240v mains incl

3/16" (4.7mm) bit

1 Quality Desoldering pump. High Suction with

automatic ejection. Knurled, anti-corrosive

casing and teflon nozzle

1.5 metres of De-soldering braid on plastic


dispenser

2 yds (1.83m) Resin Cored Solder on Card

1 Heat Shunt tool tweezers Type

Total Retail Value over **£12.00**

OUR SPECIAL KIT PRICE **£8.95**

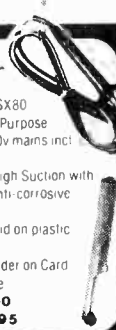

BI-PAK PCB ETCHANT AND DRILL KIT

Complete PCB Kit comprises

1 Expo Mini Drill 10 000RPM 12v DC incl 3

collets & 1 x 1mm Twist bit

1 Sheet PCB Transfers 210mm x 150mm

1 Etch Resist Pen

1 1/2 lb pack FERRIC CHLORIDE crystals

3 sheets copper clad board

2 sheets Fibreglass copper clad board


Full instructions for making your own PCB

boards

Retail Value over **£15.00**

OUR BI-PAK SPECIAL KIT PRICE **£9.75**

ORDER NO. SX81

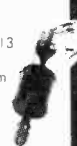

PROGRAMMABLE UNIJUNCTION TRANSISTOR
PUT case T0106 plastic MEU22 Similar to 2N6027/6028 PNP Silicon
Price 1-9 10-49 50-99 100- Normal Retail
Each 20p 18p 15p 13p Price £0.35 each

SX33A	6 small (min) (SDST/SPDT Toggle Switches 240v 5amp	£1.00
SX35A	6 small (min) Rocker Switches 240v 5amp	£1.00
SX32A	12 Assorted Jack & Phono plugs, sockets and adaptors. 2.5m, 3.0mm and standard sizes 50 "C108" Fallouts. Manufacture's out of spec on volts or gain. You test!	£1.00
SX71	A mixed bundle of Copper clad Board Fibreglass and paper. Single and double sided. A fantastic bargain	£1.00
SX72		£1.00

SX38 100 Silicon NPN Transistors—all perfect Coded mixed types with data and eqvt sheet. No rejects. Real value. **£3.00**

SX39 100 Silicon PNP Transistors—all perfect. Coded mixed types with data and eqvt sheet. No rejects. Fantastic value. **£3.00**

2N3055 The best known Power Transistors in the World — 2N3055 NPN 115w. Our Bi-Pak Special Offer Price:
10 off 50 off 100 off
£3.50 £16.00 £30.00

BD312 COMPLIMENTARY PNP POWER TRANSISTORS TO 2N3055
Equivalent M12955 — BD312 — 103
SPECIAL PRICE **£0.70** each 10 off **£8.50**



5 watt (RMS) Audio Amp

High Quality audio amplifier Module. Ideal for use in record players, tape recorders, stereo amps and cassette players, etc. Full data and back up diagrams with each module

Specification

• Max Power Supply 30v • Power Output 5 watts

RMS • Load Impedance 8-16 ohms • Frequency

response 50Hz to 25KHz — 3db • Sensitivity 70mv

for full output • Input Impedance 50k ohms • Size


85 x 64 x 30mm • Total Harmonic

distortion less than 5%

BI-PAK'S give away price

£2.25

You could not Build one for this price.

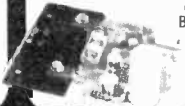

TECASBOTY

The Electronic Components and Semiconductor Bargain of the Year. A host of Electronic components including potentiometers — rotary and slider, presets — horizontal and vertical Resistors of mixed values 22ohms to 2M2 — 1/8 to 2 Watt. A comprehensive range of capacitors including electrolytic and polyester types plus disc ceramics etcetera. Audio plugs and sockets of various types plus switches, fuses, heatsinks, wire, nuts, bolts, gromets, cable clips and yes, knobs and P.C. Board. Then add to that 100 Semiconductors to include transistors, diodes, SCR's opto's, all of which are current everyday usable devices. In all a Fantastic Parcel! No rubbish! all identifiable and valued in current catalogues at well over £25.00. Our Fight Against Inflation Price —

— Beat the Budget
— Down with Depression
JUST £6.50.



BI-PAK

Send your orders to Dept PE12 BI-PAK PO BOX 6 WARE HERTS
SHOP AT 3 BALDOCK ST. WARE HERTS
TERMS: CASH WITH ORDER, SAME DAY DISPATCH, ACCESS,
BARCLAYCARD ALSO ACCEPTED. TEL 0920 3182. GIRD 388 7006
Add 15% VAT and 75p PER ORDER POSTAGE AND PACKING



Use your credit card! Ring us on Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail.
Remember you must add VAT at 15% to your order.
Total Postage add 75p per total order.

BI-PAK BARGAINS

TRIACS — PLASTIC

4 AMP — 400v — T0202 — TAG 136G	10 OFF	50 OFF	100 OFF
60p	£3.75	£17.50	£30.00
8 AMP 400v — T0220 — TAG 425	60p	£5.75	£27.50
			£50.00

SLIDER POTENTIOMETERS

SX63 5 x 470 ohms Lin	SX67 5 x 47k Lin
SX64 5 x 1k Lin	SX68 5 x 47k Log
SX65 5 x 22k Lin	SX69 5 x 100 Lin
SX66 5 x 22k Log	SX70 5 x 1 meg Lin

ALL AT
50p
PER PAK

SX40 250 Silicon Diodes—Switching like IN4148 00.35 All good—uncoded Worth double price 45v/75mA £1.25
SX41 250 Silicon Diodes—General Purpose like OA200/202 BAX13/16 Uncoded 30-100v/200mA DO-7 £1.25

SX44 10 5A SCR's T064 3 x 50v 3 x 100v 2 x 200v 2 x 400v Super value less than 1/2 price £1
SX45 10 5A SCR's T066 2 x 50v 2 x 100v 4 x 200v 2 x 400v All coded Brand new a give away at £1

MINIATURE TOOLS FOR HOBBYISTS

Miniature round nose side cutters — insulated handles 4 1/2 inch length. Order No Y043.

Miniature long nose pliers — insulated handles 5 1/2 inch length. Order No Y044.

Miniature bend nose pliers — insulated handles 5 1/2 inch length. Order No Y045.

Miniature end nippers — insulated handles 4 1/2 inch length. Order No Y046.

Miniature snipe nose pliers with side cutter and serrated jaws — insulated handles 5 inch length. Order No Y042.

ALL AT
1.25
each

All with insulated handles

FLEXKEY DRIVER

A flexible shaft screwdriver for those awkward to get at screws. Overall length 8 1/2 inch. Order No FS-1 Flat blade 4mm FS-2 Cross point no 1 **£1.75** each.

GRIP DRIVER
6 inch long screwdriver with spring loaded grip on end to hold screws in position while reaching into those difficult places. Order No SD-1 Flat blade 4mm SD-2 Cross point no 0. **95p** each.

INEXPENSIVE TOOLS OF IMMENSE VALUE

Combined wire stripper, cutter, crimper incl. 25 ass't terminals for crimping. Order No WS2. Our low price **£1.20** each.

BA NUT DRIVER SET

Set of 5 BA spanner shafts plus universal handle in roll-up wallet. Sizes 0BA 2-4-6-8BA Order no T192

£2.75 set

NEON SCREWDRIVER

7 1/2 inch blade order no NS1 **£0.85p** each
5 1/2 inch blade order no NS2 **£0.50p** each

Guarantee

Satisfaction or your money back has always been BI-PAK's GUARANTEE and it still is. All these Sale items are in stock in quantity and we will despatch the same day as your order is received.

IC SOCKETS

The lowest price ever.

Pin	10 off	50 off	100 off
8 pin	85p	£3.50	£6.00
14 pin	90p	£3.75	£6.50
16 pin	95p	£4.00	£7.00

VOLTAGE REGULATORS

T0220	Positive +	Negative -
	7805 — 50p	7905 — 55p
	7812 — 50p	7912 — 55p
	7815 — 50p	7915 — 55p
	7824 — 50p	7924 — 55p

BI-PAK'S OPTO 83 SPECIAL

A selection of Large & Small size LED's in Red, Green, Yellow and Clear, plus shaped devices of different types. 7 Segment displays, photo transistors, emitters and detectors. Types like MEL11, FPT100 etc. Plus Cadmium Cell ORP12 and germ photo transistor OCP71.

D/N0 SX57A
Valued Normal Retail £12.00
Our Price
£5.00

SEMICONDUCTORS FROM AROUND THE WORLD

100
A Collection of Transistors, Diodes, Rectifiers, Bridges, SCR's, Triacs, IC's both Logic and Linear plus Opto's all of which are current everyday usable devices.

Guaranteed Value over £10 at Normal Retail Price

£4.00
Data etc in every pak
Order No SX56

MW398 NI-CAD CHARGER

Universal Ni-Cad battery charger. All plastic case with lift up lid. Charge/Test switch. LED indicators at each of the five charging points.

Charges	Power
PP3 (9V)	220-240V AC
U12 (1.5V penlite)	Dims
U11 (1.5V C)	210 x 100 x 50mm
U2 (1.5V D)	£6.95

POWER SUPPLY OUR PRICE £3.25

Power supply fits directly into 13 amp socket. Fused for safety. Polarity reversing socket. Voltage switch. Lead with multi plug. Input — 240V AC 50HZ Output — 3 3.5 6 7.5 9 12V DC Rating — 300 ma MW88

1 Amp SILICON RECTIFIERS

Glass Type similar IN4000 SERIES IN4001-IN4004 50 — 500v — uncoded — you select for VLTS. ALL perfect devices — NO duds Min 50v 50 for **£1.00** — worth double ORDER NO SX76

Silicon General Purpose NPN Transistors T0-18 Case. Lock fit leads — coded CV7644 Similar to BC147 — BC107 — 2789 ALL NEW! VCE 70v IC500mA Hfe 75-250 50 off 100 off 500 off 1000 off
PRICE **£2.00 £3.80 £17.50 £30.00**

Silicon General Purpose PNP Transistors T0-18 Case. Lock fit leads coded CV9507 similar 2N2905A to BF130 VCE 60v IC 600mA Min Hfe 50 ALL NEW! 50 off 100 off 500 off 1000 off
PRICE **£2.50 £4.00 £19.00 £35.00**

Silicon NPN 'L' Type Transistors

T0-92 Plastic centre collector. Like BC182L — 183L — 184L. VCEO 45 VCE 30 IC 200mA Hfe 100-400. ALL perfect devices — uncoded ORDER AS SX183L 50 off 100 off 500 off 1000 off
PRICE **£1.50 £2.50 £10.00 £17.00**

PNP SILICON TRANSISTORS:

Similar ZTX500 — ZTX214 — E-Line. VCEO 40 VCE 35 IC 300mA Hfe 50-400. Brand New — Uncoded — Select Devices. 50 off 100 off 500 off 1000 off
PRICE **£2.00 £3.50 £15.00 £25.00**

DIGITAL VOLT METER MODULE

3 x 7 segment displays Basic Circuit 0.2V± instructions provided to extend voltage & current ranges. Operating voltage 9/12v. Typ. Power Consumption 50mA. D/N0 SX99 Once only price **£9.95**

ELECTRONIC SIREN 12v DC

Red plastic case with adjustable living bracket. Emits high pitched wailing note of varying pitch. 100 cycles per minute. Dims 90mm (dia) 60mm (depth). Power 12 v DC. Our Price: **£5.50**

8 Bit MICROPROCESSOR

National INS8080AN 40 Pin DIL N Channel Silicon GATE MOS TECHNOLOGY As used in Nationals N8080 Micro Computer Family. Instruction Cycle Time 2 µs. Supplied with functional Block Diagram. BRAND NEW — NOT seconds or reclaims. 100% perfect ORDER NO SX8080 Normal Sell price £4.50 each. Our BI-PAK Special Price **£2.00** SO HURRY — LIMITED STOCKS

40 Pin IC Socket to fit SX8080. Offer price ORDER NO 1609 **30p**

MULTITESTERS

30,000 opv Including test leads and case. AC volts — 0.25-10-25-100-250-500-1,000. DC volts — 0.025-1-2.5-10-25-100-250-1,000. DC current — 0-50ua 0-5ma-50ma 0-12amps. Resistance — 0-6K ohms-70K ohms-6meg ohms-60meg ohms. Decibels — -20db to plus 56db. Short test — Internal buzzer. Dims — 160 x 110 x 50mm.

O/N0. 1315. OUR PRICE **ONLY £24.75**

1,000 opv Including test leads & Battery. AC volts — 0-15-150-500-1,000. DC volts — 0-15-150-500-1,000. DC currents — 0-1ma-150ma. Resistance — 0-2.5 K ohms 100 K ohms. Dims — 90 x 61 x 30mm.

O/N0. 1322. OUR PRICE **£6.50 ONLY**

BI-PAK'S COMPLETELY NEW CATALOGUE

Completely re-designed. Full of the type of components you require, plus some very interesting ones you will soon be using and of course, the largest range of semiconductors for the Amateur and Professional you could hope to find.

There are no wasted pages of useless information so often included in Catalogues published nowadays. Just solid facts: i.e. price, description and individual features of what we have available. But remember, BI-PAK's policy has always been to sell quality components at competitive prices and THAT WE STILL DO.

BI-PAK'S COMPLETELY NEW CATALOGUE is now available to you. You will be amazed how much you can save when you shop for Electronic Components with a BI-PAK Catalogue. Have one by you all the time—it pays to buy BI-PAK.

To receive your copy send **75p** plus 25p p&p

BI-PAK

Send your orders to Dept PE12 BI-PAK PO BOX 6 WARE HERTS. SHOP AT 3 BALDOCK ST. WARE HERTS. TERMS: CASH WITH ORDER. SAME DAY DESPATCH. ACCESS, BARCLAYCARD ALSO ACCEPTED. TEL (0920) 3182. GIRD 388 7006. Add 15% VAT AND 75p PER ORDER POSTAGE AND PACKING.



Use your credit card. Ring us on Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail. Remember you must add VAT at 15% to your order. Total Postage add 50p per Total order.

HOME LIGHTING KITS

These kits contain all necessary components and full instructions & are designed to replace a standard wall switch and control up to 300w of lighting.

- TDR300K Remote Control Dimmer £14.30
MK6 Transmitter for above £4.20
- TD300K Touchdimmer £7.00
- TDE/K Extension kit for 2-way switching for TD300K £2.00
- LD300K Rotary Controlled Dimmer £3.50



HOME CONTROL CENTRE

This New Remote Control Kit enables you to control up to 16 different appliances anywhere in the house from the comfort of your armchair. The transmitter injects coded pulses into the mains wiring which are received by receiver modules connected to the same mains supply and used to switch on the appliance addressed. Receivers are addressed by means of a 16-way keyboard, followed by an on or off command. Since pushing buttons can become rather boring, the transmitter also includes a computer interface so you can programme your favourite micro to switch lights, heating, electric blanket, make your coffee in the morning, etc., without rewiring your house. JUST THINK OF THE POSSIBILITIES. The KIT includes all PCBs and components for one transmitter and two receivers, plus a drilled box for the transmitter.

Order as XK112. £42.00

Additional Receivers XK111 £10.00

ELECTRONIC LOCK KIT XK101

This KIT contains a purpose designed lock IC, 10-way keyboard, PCBs and all components to construct a Digital Lock, requiring a 4-key sequence to open and providing over 5000 different combinations. The open sequence may be easily changed by means of a pre-wired plug. Size: 7 x 6 x 3 cms. Supply: 5V to 15 V d.c. at 40uA. Output: 750mA max. Hundreds of uses for doors and garages, car anti-theft device, electronic equipment, etc. Will drive most relays direct. Full instructions supplied.

ONLY £10.50

Electric lock mechanism for use with latch locks and above kit

£13.50

THE MULTI-PURPOSE TIMER HAS ARRIVED

Now you can run your central heating, lighting, hi-fi system and lots more with just one programmable timer. At your selection it is designed to control four mains outputs independently, switching on and off at pre-set times over a 7 day cycle, e.g. to control your central heating (including different switching times for weekends), just connect it to your system programme and set it and forget it—the clock will do the rest.

FEATURES INCLUDE:

- 0.5" LED 12 hour display
- Day of week, am/pm and output status indicators
- 4 zero voltage switched mains outputs
- 50/60Hz mains operation
- Battery backup saves stored programmes and continues time keeping during power failures. (Battery not supplied)
- Display blanking during power failure to conserve battery power
- 18 programme time sets
- Powerful "Everyday" function enabling output to switch every day but use only one time set
- Useful "sleep" function—turns on output for one hour
- Direct switch control enabling output to be turned on immediately or after a specified time interval
- 20 function keypad for programme entry
- Programme verification at the touch of a button

(Kit includes all components, PCB, assembly and programming instructions). ORDER AS CT5000



FREE

SHORT FORM CATALOGUE — send SAE (6" x 9"). We also stock Vero, Books, Resistors, Capacitors, Semi-Conductors etc.

CHRISTMAS PRESENTS GALORE



STOCKING FILLERS

- PACK (1) 650 Resistors 47 ohm to 10 Mohm - 10 per value £4.00
- PACK (2) 40 x 16V Electrolytic Capacitors 10uF to 1000uF - 5 per value £3.25
- PACK (3) 60 Polyester Capacitors 0.01 to 1uF/250V - 5 per value £5.55
- PACK (4) 45 Sub-miniature Presets 100 ohm to 1 Mohm - 5 per value £2.90
- PACK (5) 30 Low Profile IC Sockets 8, 14 and 16 - pin - 10 off each £2.40
- PACK (6) 25 Red LEDs (5mm dia.) £1.25
- PACK (7) 20 BC182 NPN General Purpose Transistors £1.20
- PACK (8) 20 BC212 PNP General Purpose Transistors £1.20

All full spec. branded devices

BUY ANY 5 PACKS AND WE WILL SEND YOU 10 RED LEDs

FREE

ALL PRICES EXCLUDE VAT



DVM/ULTRA SENSITIVE THERMOMETER KIT

This new design is based on the ICL7126 (a lower power version of the ICL7106 chip) and a 3 1/2 digit liquid crystal display. This kit will form the basis of a digital multimeter (only a few additional resistors and switches are required—details supplied), or a sensitive digital thermometer (-50°C to +150°C) reading to 0.1°C. The basic kit has a sensitivity of 200mV for a full scale reading, automatic polarity indication and an ultra low power requirement—giving a 2 year typical battery life from a standard 9V PP3 when used 8 hours a day, 7 days a week.

Price £15.50

DISCO LIGHTING KITS

DL1000K This value-for-money kit features a bi-directional sequence, speed of sequence and frequency of direction change, being variable by means of potentiometers and incorporates a master dimming control. £14.60

DL2100K A lower cost version of the above, featuring unidirectional channel sequence with speed variable by means of a pre-set pot. Outputs switched only at mains zero crossing points to reduce radio interference to a minimum. Optional opto input DLA1. Only £8.00

DL3000K This 3 channel sound to light kit features zero voltage switching, automatic level control & built in mic. No connections to speaker or amp required. No knobs to adjust — simply connect to mains supply & lamps. Only £11.95 (1Kw/Channel)

"OPEN-SESAME"

The XK103 is a general purpose infra-red transmitter/receiver with one momentary (normally open) relay contact and two latched transistor output. Designed primarily for controlling motorised garage doors and two auxiliary outputs for drive/garage lights at a range of up to 40 ft. The unit also has numerous applications in the home for switching lights, TV, closing curtains, etc. Ideal for aged or disabled persons.

The kit comprises a mains powered receiver, a four button transmitter, complete with pre-drilled box, requiring a 9V battery and one opto-isolated solid state switch kit for interfacing the receiver to mains appliances. As with all our kits, full instructions are supplied.

ONLY £23.75

REMOTE CONTROL KITS

MK6 SIMPLE INFRA RED TRANSMITTER Pulsed infra red source complete with hand-held plastic box. Requires a 9V battery £4.20

MK7 INFRA RED RECEIVER Single channel, range approx. 20ft. Mains powered with a triac output to switch loads up to 500W at 240V ac. £9.00

MK8 CODED INFRA RED TRANSMITTER Based on the SL480, the kit includes all components to make a coded transmitter and only requires a 9V (PP3) battery and keyboard. 8 x 2 x 1.3cms £5.90

MK10 16-WAY KEYBOARD For use with MK8 and MK18 to generate 16 different codes for decoding by the ML928 or ML926 receiver (MK12) kit. £5.40

MK11 10-Channel + 3 Analogue o/p IR Receiver Based on ML922 decoder IC. Functions include on/standby output, toggle, control of volume, tone and lamp brightness. Includes its own mains supply. £12.00

MK12 16-CHANNEL IR RECEIVER For use with MK8 kit with 16 on/off outputs, which with further interface circuitry, such as relays or triacs, will switch up to 16 items of equipment on or off remotely. Latched or momentary outputs — please specify when ordering. Includes its own mains supply. £11.95

MK13 11-WAY KEYBOARD For use with MK8, MK18 and MK11 kits. £4.35

MK18 Mains Powered IR Transmitter Mains powered for continuous operation — single channel, for applications such as burglar alarms, automatic door openers, etc. Range approx. 6 ft. £2.50

MK17 12V d.c. IR RECEIVER For use with MK6 or MK16. Relay output with DP 3 Amp change over contacts, may be used as latched, momentary or "break beam" receiver. Operates from 6.13V d.c. £9.50

MK18 HIGH POWER IR TRANSMITTER Similar to MK8 but with range of approx. 60ft. £6.20

Ancillary Kits: MK2 Solid State Relay Opto-isolated with zero voltage switching. No triac supplied. £2.60

MK15 DUAL LATCHED SOLID STATE RELAY Comprises 2 x solid state relays and latch for use with momentary version of the MK12. 2 output. triacs required (not supplied). £4.50

Switches any appliance up to 1kW on and off at present times once per day. Kit contains: AY-5-1230 IC, 0.5" LED display, mains supply, display drivers, switches, LEDs, triacs, PCBs and full instructions.

CT1000K Basic Kit £14.90

CT1000K with white box (56/131 x 71mm) £17.40

(Ready Built) £22.50

Add 55p postage & packing + 15% VAT to total.

Overseas Customers; Add £2.50 (Europe), £6.00 (elsewhere) for p&p.

Send S.A.E. for further STOCK DETAILS.

Goods by return subject to availability.

24 HOUR CLOCK/APPLIANCE TIMER KIT

CT1000K Basic Kit £14.90

CT1000K with white box (56/131 x 71mm) £17.40

(Ready Built) £22.50

Add 55p postage & packing + 15% VAT to total.

Overseas Customers; Add £2.50 (Europe), £6.00 (elsewhere) for p&p.

Send S.A.E. for further STOCK DETAILS.

Goods by return subject to availability.

OPEN

9am to 5pm (Mon to Fri)

10am to 4pm (Sat)

FAST SERVICE · TOP QUALITY · LOW LOW PRICES

No circuit is complete without a call to —

ELECTRONICS PE

11 Boston Road
London W7 3SJ

ACCESS
AND
BARCLAYCARD
welcome

TEL: 01-567 8910 ORDERS
01-579 9794 ENQUIRY
01-579 2842 TECHNICAL AFTER 3PM



NEW T.V. SOUND TUNER BUILT AND TESTED



£22.95 + £2.00 p&p.

In the cut-throat world of consumer electronics, one of the questions designers apparently ponder over is "Will anyone notice if we save money by chopping this out?" In the domestic TV set, one of the first casualties seems to be the sound quality. Small speakers and no tone controls are common and all this is really quite sad, as the TV companies do their best to transmit the highest quality sound. Given this background a compact and independent TV tuner that connects direct to your Hi-Fi is a must for quality reproduction. This TV SOUND TUNER offers full UHF coverage with 5 pre-selected tuning controls. It can also be used in conjunction with your video recorder. Dimensions: 11 1/4" x 8 1/2" x 3 3/4".

PRACTICAL ELECTRONICS STEREO CASSETTE RECORDER KIT



£32.95
+ £2.75 p&p.

• NOISE REDUCTION SYSTEM. • AUTO STOP. • TAPE COUNTER. • SWITCHABLE E.Q. • INDEPENDENT LEVEL CONTROLS. • TWIN V.U. METER. • WOW & FLUTTER 0.1%. • RECORD/PLAYBACK I.C. WITH ELECTRONIC SWITCHING. • FULLY VARIABLE RECORDING BIAS FOR ACCURATE MATCHING OF ALL TAPES

Kit includes tape transport mechanism, ready punched and back printed quality circuit board and all electronic parts. i.e. semiconductors, resistors capacitors, hardware top cover, printed scale and mains transformer. You only supply solder and hook-up wire.

Featured in April issue P.E.
Reprint 50p. Free with kit

Self assembly simulated wood cabinet - ONLY £4.50 plus £1.50 p&p.

ELECTRONICS ONLY!

Ideal for updating your existing cassette. Includes pcb diagram, all semiconductors, IC's, Capacitors, resistors.

£18.95

+£1.40p&p.

PRACTICAL ELECTRONICS CAR RADIO KIT SERIES II

2 WAVE BAND
MW -- LW


• Easy to build
• 5 push button tuning
• Modern design
• 6 watt output • Ready etched and punched PCB • Incorporates suppression circuits.

All the electronic components to build the radio, you supply only the wire and the solder, featured in Practical Electronics March issue. Features: pre-set tuning with 5 push button options, black illuminated tuning scale. The P.E. Traveller has a 6 watt output neg. ground and incorporates an integrated circuit output stage, a Mullard IF Module LP1181 ceramic filter type pre-aligned and assembled, and a Bird pre-aligned push button tuning unit.

Suitable stainless steel fully retractable aerial (locking) and speaker (6"x4"app.). available as a kit complete. **£12.95** Plus £2.00 p&p. **£2.50/pack.** + £1.50 p&p.



P.E. STEREO TUNER KIT

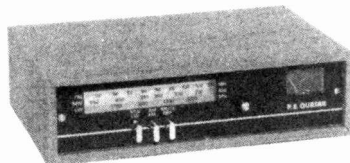

This easy to build 3 band stereo AM/FM tuner kit is designed in conjunction with Practical Electronics (July '81 issue). For ease of construction and alignment it incorporates three Mullard modules and an I.C. IF. System. FEATURES: VHF, MW, LW Bands, interstation muting and AFC on VHF. Tuning meter. Two back printed PCB's. Ready made chassis and scale. Aerial: AM - ferrite rod, FM - 75 or 300 ohms. Stabilised power supply with 'C' core mains transformer. All components supplied are to P.E. strict specification. Front scale size: 10 1/2" x 2 1/4" approx. Complete with d diagram and instructions.

£17.95


Plus £2.50 p&p.

Self assembly simulated wood cabinet sleeve to suit tuner only. Finish size: 11 1/4" x 8 1/2" x 3 3/4" **£3.50** Plus £1.50 p&p.

TV SOUND TUNER KIT

£11.45

+ £2.00 p&p.

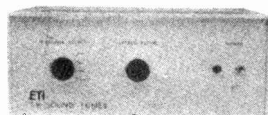

As featured in E.T.I. December '81 issue. Kit of parts including PCB, UHF tuner and selector switch with all components excluding case. + Transformer £1.50 + £1.50 p&p (p&p free on transformer if ordered with kit).

BIRD AUDIO STEREO CAR RADIO BOOSTER

To boost your car radio or radio cassette to 15W r.m.s. per channel.

£9.95 + £1.50 p&p.



125W HIGH POWER AMP MODULES


KIT **£10.50**
+ £1.15 p&p

BUILT **£14.25**
+ £1.15 p&p

The power amp kit is a module for high power applications - disco units, guitar amplifiers, public address systems and even high power domestic systems. The unit is protected against short circuiting of the load and is safe in an open circuit condition. A large safety margin exists by use of generously rated components, result, a high powered rugged unit. The PC board is back printed, etched and ready to drill for ease of construction and the aluminium chassis is preformed and ready to use.

Supplied with all parts, circuit diagrams and instructions.

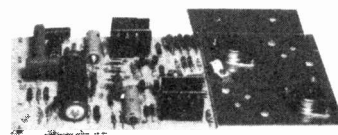ACCESSORIES: Suitable mains power supply kit with transformer: £8.00 plus £2.00 p&p. Suitable LS coupling electrolytic: £1.00 plus 25p p&p.



SPECIFICATIONS:

Max. output power (RMS): 125W.
Operating voltage (DC): 50 - 80 max.
Loads: 4 - 16 ohms.
Frequency response measured @ 100 watts: 25Hz - 20KHz.
Sensitivity for 100 watts: 400mV @ 47K.
Typical T.H.D. @ 50 watts, 4 ohms: 0.1%.
Dimensions: 205 x 90 and 190 x 36 mm.


HI-FI SPEAKERS AT BARGAIN PRICES

GOODMANS TWEETERS

8 ohm soft dome radiator tweeter (3 1/2"sq.) for use in up to 40W systems; with 2 element crossover.

£3.95 each (p&p £1) or

£6.95 each (p&p £1.50)

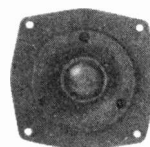


35 WATT MICRO 2-WAY SPEAKER SYSTEM

Unit comprises one 50w (4"app.) Audax soft dome tweeter HD100. And one 5" Audax bass/midrange 35w driver HIF11JSM. Complete with 2 element crossover. Total impedance of system 4 ohms.

£8.95

PER SET + £2.70 p&p.

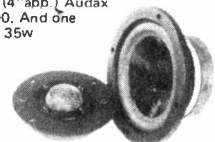


MONO MIXER AMP

Ideal for Church halls & Club houses.

£45.00

+ £2.00 p&p.

50 WATT Six individually mixed inputs for two pick ups (Cer. or mag.), two moving coil microphones and two auxiliary for tape tuner, organs, etc. Eight slider controls - six for level and two for master bass and treble, four extra treble controls for mic. and aux. inputs. Size 13 1/4"x6 1/2"x3 3/4"app. Power output 50 watts R.M.S. (cont.) for use with 4 to 8 ohm speakers. Attractive black vinyl case with matching fascia and knobs. Ready to use.

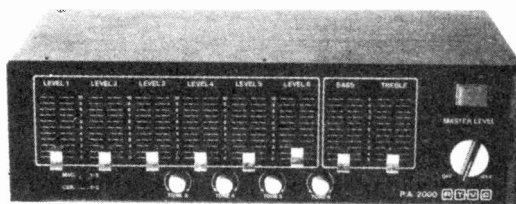

All mail to:
21B HIGH STREET, ACTON, W3 6NG.
Note: Goods despatched to U.K. postal addresses only. All items subject to availability. Prices correct at 30/10/82 and subject to change without notice. Please allow 7 working days from receipt of order for despatch. RTVC Limited reserve the right to up-

date their products without notice. All enquiries send S.A.E.

ALL CALLERS TO: **323 EDGWARE ROAD, LONDON W2.** Telephone: **01-723 8432.** (5 minutes walk from Edgware Road Tube Station) Now open 6 days a week 9 - 6. Prices include VAT.

Telephone or mail orders by ACCESS welcome.



BEGINNERS GUIDE TO MICROPROCESSORS

by Parr E. A.

Price: £4.50

ELECTRONIC DEVICES & COMPANIES

by Seymour J.

Price: £10.50

A PRACTICAL INTRO TO ELECTRONIC CIRCUITS

by Jones M.

Price: £7.50

ESSENTIAL ELECTRONIC AN A-Z GUIDE

by Loveday G.

Price: £6.75

ADVENTURES WITH DIGITAL ELECTRONICS

by Duncan T.

Price: £3.25

PRINCIPLES OF INTERACTIVE COMPUTER GRAPHICS

by Sproull R.

Price: £10.75

MICROCOMPUTER TECHNOLOGY AN INTRO

by Ullman J.

Price: £5.75

COMPLETE HANDBOOK OF MAGNETIC RECORDING

by Jorgensen F.

Price: £8.50

COMPLETE HANDBOOK OF VIDEO

by Owen D.

Price: £10.00

H.F. ANTENNAS FOR ALL LOCATIONS

by Moxan L.

Price: £7.50

★ ALL PRICES INCLUDE POSTAGE ★

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST
of British and American Technical Books

19-21 PRAED STREET
LONDON W2 1NP

Phone 01-402 9176 Closed Saturday 1 p.m.
Please allow 14 days for reply or delivery.

OVERSEAS ORDERS

Overseas readers are reminded that unless otherwise stated, postage and packing charges published in advertisements apply to the United Kingdom only.

Readers wishing to import goods from the United Kingdom are advised to first obtain from the advertiser(s) concerned an exact quotation of the cost of supplying their requirements carriage paid home.

STOCKING PARTS OTHER STORES CANNOT REACH

SUPERIOR QUALITY CARBON FILM RESISTORS. HISTAB LOW NOISE

1W 10C2-1M2 5% E24	2p
1W 10C2-1M2 5% E12	3p
1W 10C2-1M2 5% E12	6p
2W 10C2-1M2 5% E12	15p

METAL OXIDE FILM RESISTORS

Very high thermal & electrical stability. Extremely low noise
0.4W 10C2-1M2 5% E24 5p
0.4W 10C2-1M2 5% E12 8p

LOW OHMIC VALUE RESISTORS

0.22C2-8 2C2 E12 11p

WIRE WOUND RESISTORS 5%

2-3W 0.2C2-33C2-E12	28p
4-7W 0.4C2-6K 8 E12	33p
10-11W 1.0C2-33K E12	37p

LOW NOISE ROTARY POTS E3 Series

47K-2m Lin 32p	Veroboard 0.1"
47K-2m Log 32p	Copper Clad
As above with 32p	25x3.75 80p
DP switch 80p	25x5 90p
As above but stereo into switch 90p	3.75x3.75 1.03
	25x17 2.80
	4.75x17 4.55
	VO Board 1.80
	Drill Board 3.75
	Track Cutter 1.35
	Pin Isolator 1.75
	100 Pins 52p
	Verobloc 3.99
	Vero Wiring
	Pen+Spool 3.50
	Splice Strip 72p
	Combs 6p

MICRO MINI 100V CERAMIC PLATE ORs or better

E12 Series 7p
1p/10m 7p

DISCOUNTS ON QUANTITY PLEASE PHONE

SIEMENS POLY-C 5% 75mm 250W

Mini Vert 14p
Mini Horiz 14p
Standard Vert 17p
Standard Horiz 17p
Thumbwheel of 4" Spindle for Standard Pre-seals only 8p

QUALITY ELECTROLYTICS BY MATSUSHITA OR SIEMENS AXIALS

ufd V 8p
47 100 9p
47 350 30p
1 63 8p
1 100 9p
1 500 40p
2.2 25 8p
2.2 63 9p
2.2 100 11p
2.2 350 30p
3.3 25 10p
3.3 40 11p
3.3 63 12p
3.3 100 13p
4.7 16 12p
4.7 25 13p
10 16 11p
10 25 12p
15 16 11p
15 25 13p
22 16 11p
22 25 13p
33 16 11p
33 25 13p
100 33 17p

TANTALUM BEADS

1/35V 17p
22/35V 17p
33/35V 17p
47/35V 17p
68/35V 17p
10/35V 17p
22/16V 17p
22/35V 22p
33/35V 22p
47/16V 22p
47/35V 24p
68/35V 25p
10/16V 25p
10/35V 34p
15/10V 22p
15/16V 32p
15/25V 32p
22/16V 32p
33/10V 36p
47/16V 43p
100/35V 37p

Feedthrough Capacitor 1000pf 500V 7p

MINI FILM MULLARD TRIMMERS

1.4-5.5pf (800MHz) 23p
2-10pf (600MHz) 27p
2-22pf (400MHz) 29p
5-5.5pf (200MHz) 36p
Cermet 20
Precision Pre-sets 33p
50C2, 100C2, 200C2, 500C2, 1K, 2K, 5K, 10K, 20K, 50K, 100K, 99p each

RAINBOW RIBBON CABLE

10 Way 65p
24 Way 1.50
40 Way 2.10

ANTEX SOLDERING IRONS

C240 (15W) 4.59
X25 (25W) 4.99
Iron Stand 1.65
C240 Element 1.99
X25 Element 2.05
No 2 (Small) 65p
No 3 (Med) 65p
No 6 (Micro) 65p
Bays 18 30p
Bays 19 15p
Bays 20 15p

DIODES

IN34 30p
IN40 30p
IN41 30p
IN42 30p
IN43 30p
IN44 30p
IN45 30p
IN46 30p
IN47 30p
IN48 30p
IN49 30p
IN50 30p
IN51 30p
IN52 30p
IN53 30p
IN54 30p
IN55 30p
IN56 30p
IN57 30p
IN58 30p
IN59 30p
IN60 30p
IN61 30p
IN62 30p
IN63 30p
IN64 30p
IN65 30p
IN66 30p
IN67 30p
IN68 30p
IN69 30p
IN70 30p
IN71 30p
IN72 30p
IN73 30p
IN74 30p
IN75 30p
IN76 30p
IN77 30p
IN78 30p
IN79 30p
IN80 30p
IN81 30p
IN82 30p
IN83 30p
IN84 30p
IN85 30p
IN86 30p
IN87 30p
IN88 30p
IN89 30p
IN90 30p
IN91 30p
IN92 30p
IN93 30p
IN94 30p
IN95 30p
IN96 30p
IN97 30p
IN98 30p
IN99 30p
IN100 30p

SCREENED CABLE

Single 14p
Stereo 27p
Mini Single 15p
Mini Stereo 15p
4 Core 4 Screens 44p
4 Core 1 Screen 54p
8 Core 61p
12 Core 80p

AERIAL CABLE

50S1 RG58A 36p
75S1 LH 36p
75S1 VHF 14p
100S1 Flat 14p

RAINBOW RIBBON CABLE

10 Way 65p
24 Way 1.50
40 Way 2.10

ANTEX SOLDERING IRONS

C240 (15W) 4.59
X25 (25W) 4.99
Iron Stand 1.65
C240 Element 1.99
X25 Element 2.05
No 2 (Small) 65p
No 3 (Med) 65p
No 6 (Micro) 65p
Bays 18 30p
Bays 19 15p
Bays 20 15p

DIODES

IN34 30p
IN40 30p
IN41 30p
IN42 30p
IN43 30p
IN44 30p
IN45 30p
IN46 30p
IN47 30p
IN48 30p
IN49 30p
IN50 30p
IN51 30p
IN52 30p
IN53 30p
IN54 30p
IN55 30p
IN56 30p
IN57 30p
IN58 30p
IN59 30p
IN60 30p
IN61 30p
IN62 30p
IN63 30p
IN64 30p
IN65 30p
IN66 30p
IN67 30p
IN68 30p
IN69 30p
IN70 30p
IN71 30p
IN72 30p
IN73 30p
IN74 30p
IN75 30p
IN76 30p
IN77 30p
IN78 30p
IN79 30p
IN80 30p
IN81 30p
IN82 30p
IN83 30p
IN84 30p
IN85 30p
IN86 30p
IN87 30p
IN88 30p
IN89 30p
IN90 30p
IN91 30p
IN92 30p
IN93 30p
IN94 30p
IN95 30p
IN96 30p
IN97 30p
IN98 30p
IN99 30p
IN100 30p

SCREENED CABLE

Single 14p
Stereo 27p
Mini Single 15p
Mini Stereo 15p
4 Core 4 Screens 44p
4 Core 1 Screen 54p
8 Core 61p
12 Core 80p

AERIAL CABLE

50S1 RG58A 36p
75S1 LH 36p
75S1 VHF 14p
100S1 Flat 14p

RAINBOW RIBBON CABLE

10 Way 65p
24 Way 1.50
40 Way 2.10

ANTEX SOLDERING IRONS

C240 (15W) 4.59
X25 (25W) 4.99
Iron Stand 1.65
C240 Element 1.99
X25 Element 2.05
No 2 (Small) 65p
No 3 (Med) 65p
No 6 (Micro) 65p
Bays 18 30p
Bays 19 15p
Bays 20 15p

DIODES

IN34 30p
IN40 30p
IN41 30p
IN42 30p
IN43 30p
IN44 30p
IN45 30p
IN46 30p
IN47 30p
IN48 30p
IN49 30p
IN50 30p
IN51 30p
IN52 30p
IN53 30p
IN54 30p
IN55 30p
IN56 30p
IN57 30p
IN58 30p
IN59 30p
IN60 30p
IN61 30p
IN62 30p
IN63 30p
IN64 30p
IN65 30p
IN66 30p
IN67 30p
IN68 30p
IN69 30p
IN70 30p
IN71 30p
IN72 30p
IN73 30p
IN74 30p
IN75 30p
IN76 30p
IN77 30p
IN78 30p
IN79 30p
IN80 30p
IN81 30p
IN82 30p
IN83 30p
IN84 30p
IN85 30p
IN86 30p
IN87 30p
IN88 30p
IN89 30p
IN90 30p
IN91 30p
IN92 30p
IN93 30p
IN94 30p
IN95 30p
IN96 30p
IN97 30p
IN98 30p
IN99 30p
IN100 30p

SCREENED CABLE

Single 14p
Stereo 27p
Mini Single 15p
Mini Stereo 15p
4 Core 4 Screens 44p
4 Core 1 Screen 54p
8 Core 61p
12 Core 80p

AERIAL CABLE

50S1 RG58A 36p
75S1 LH 36p
75S1 VHF 14p
100S1 Flat 14p

RAINBOW RIBBON CABLE

10 Way 65p
24 Way 1.50
40 Way 2.10

ANTEX SOLDERING IRONS

C240 (15W) 4.59
X25 (25W) 4.99
Iron Stand 1.65
C240 Element 1.99
X25 Element 2.05
No 2 (Small) 65p
No 3 (Med) 65p
No 6 (Micro) 65p
Bays 18 30p
Bays 19 15p
Bays 20 15p

CRICKLEWOOD ELECTRONICS LTD

No 51 (Med) 65p

No 52 (Lge) 65p

DIL SOCKETS

Lo W.Wp 10p
Pins prof 10p
8 9p 25p
14 9p 35p
16 10p 40p
18 16p 50p
20 20p —
22 22p —
24 24p 70p
28 28p 79p
40 30p 99p

Beautiful Mini Radial Low Voltage Matsushita only

ufd V 6p
10 16 6p
22 10 6p
22 16 7p
47 10 7p
47 16 8p
100 10 8p
100 16 10p
220 10 11p
220 16 12p
470 10 17p
470 16 18p
1000 10 20p
1000 16 24p
2200 10 34p
2200 16 44p

ETCH RESIST TRANSFERS

1. Thin lines
2. Thick lines
3. Thin bends
4. Thick bends
5. DIL pads
6. Transistor pads
7. Dots & holes
8. 0.1" edge comp.
9. Mature Any sheet of above 30p
Set of 13 sheets 3.00

Ferric Chloride 60% Solution 250ml bottle

£1.60

Wire & Cable

Prices per metre
Solid Hook up Wire
Any colour 5p

Mains/Spaker Cable (per metre)

Twin 1 amp 14p
Twin 2 1/2 amp 16p
3 Core 2 1/2 amp 18p
3 Core 6 amp 31p
3 Core 13 amp 56p

Solid Multicore

4 Core 33p
8 Core 39p
12 Core 46p
50 Core 1.37

Screened Cable

Single 14p
Stereo 27p
Mini Single 15p
Mini Stereo 15p
4 Core 4 Screens 44p
4 Core 1 Screen 54p
8 Core 61p
12 Core 80p

Aerial Cable

50S1 RG58A 36p
75S1 LH 36p
75S1 VHF 14p
100S1 Flat 14p

RAINBOW RIBBON CABLE

10 Way 65p
24 Way 1.50
40 Way 2.10

ANTEX SOLDERING IRONS

C240 (15W) 4.59
X25 (25W) 4.99
Iron Stand 1.65
C240 Element 1.99
X25 Element 2.05
No 2 (Small) 65p
No 3 (Med) 65p
No 6 (Micro) 65p
Bays 18 30p
Bays 19 15p
Bays 20 15p

DIODES

IN34 30p
IN40 30p
IN41 30p
IN42 30p
IN43 30p
IN44 30p
IN45 30p
IN46 30p
IN47 30p
IN48 30p
IN49 30p
IN50 30p
IN51 30p
IN52 30p
IN53 30p
IN54 30p
IN55 30p
IN56 30p
IN57 30p
IN58 30p
IN59 30p
IN60 30p
IN61 30p
IN62 30p
IN63 30p
IN64 30p
IN65 30p
IN66 30p
IN67 30p
IN68 30p
IN69 30p
IN70 30p
IN71 30p
IN72 30p
IN73 30p
IN74 30p
IN75 30p
IN76 30p
IN77 30p
IN78 30p
IN79 30p
IN80 30p
IN81 30p
IN82 30p
IN83 30p
IN84 30p
IN85 30p
IN86 30p
IN87 30p
IN88 30p
IN89 30p
IN90 30p
IN91 30p
IN92 30p
IN93 30p
IN94 30p
IN95 30p
IN96 30p
IN97 30p
IN98 30p
IN99 30p
IN100 30p

SCREENED CABLE

Single 14p
Stereo 27p
Mini Single 15p
Mini Stereo 15p
4 Core 4 Screens 44p
4 Core 1 Screen 54p
8 Core 61p
12 Core 80p

AERIAL CABLE

50S1 RG58A 36p
75S1 LH 36p
75S1 VHF 14p
100S1 Flat 14p

RAINBOW RIBBON CABLE

10 Way 65p
24 Way 1.50
40 Way 2.10

ANTEX SOLDERING IRONS

C240 (15W) 4.59
X25 (25W) 4.99
Iron Stand 1.65
C240 Element 1.99
X25 Element 2.05
No 2 (Small) 65p
No 3 (Med) 65p
No 6 (Micro) 65p
Bays 18 30p
Bays 19 15p
Bays 20 15p

DIODES

IN34 30p
IN40 30p
IN41 30p
IN42 30p
IN43 30p
IN44 30p
IN45 30p
IN46 30p
IN47 30p
IN48 30p
IN49 30p
IN50 30p
IN51 30p
IN52 30p
IN53 30p
IN54 30p
IN55 30p
IN56 30p
IN57 30p
IN58 30p
IN59 30p
IN60 30p
IN61 30p
IN62 30p
IN63 30p
IN64 30p
IN65 30p
IN66 30p
IN67 30p
IN68 30p
IN69 30p
IN70 30p
IN71 30p
IN72 30p
IN73 30p
IN74 30p
IN75 30p
IN76 30p
IN77 30p
IN78 30p
IN79 30p
IN80 30p
IN81 30p
IN82 30p
IN83 30p
IN84 30p
IN85 30p
IN86 30p
IN87 30p
IN88 30p
IN89 30p
IN90 30p
IN91 30p
IN92 30p
IN93 30p
IN94 30p
IN95 30p
IN96 30p
IN97 30p
IN98 30p
IN99 30p
IN100 30p

SCREENED CABLE

Single 14p
Stereo 27p
Mini Single 15p
Mini Stereo 15p
4 Core 4 Screens 44p
4 Core 1 Screen 54p
8 Core 61p
12 Core 80p

AERIAL CABLE


50S1 RG58A 36p

40 Cricklewood Broadway, London NW2 3ET. Tel: 01-452 0161. Telex: 914977
 This is a small list from our vast stocks. Full price list free on request. You may order by phone, quoting Access, Visa or American Express no., or by normal mail order. Delivery welcome. All in stock items (95% ex stock) go out same day. Please add 15% VAT & 70p p.p. Govt. Dept. Excess. Excess orders welcome. Overseas orders add 10% VAT but allow extra p.p. Quantity discounts negotiable.

CRICKLEWOOD - STOCKING PARTS OTHER STORES CANNOT REACH!

3M143	2.85	3M147	13p	3M148	13p	3M149	13p	3M817	13p	3M818	13p
-------	------	-------	-----	-------	-----	-------	-----	-------	-----	-------	-----

IT'S AS EASY AS 1,2,3...

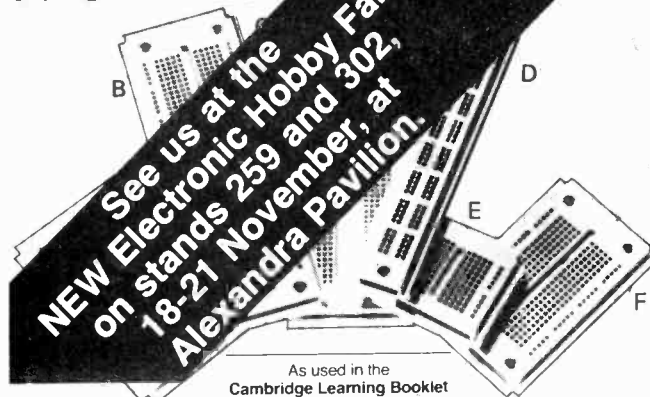

See us at the
NEW Electronic Hobby Fair
on stands 259 and 302,
18-21 November, at
Alexandra Pavilion.

As used in the
Cambridge Learning Booklet

- A EXP 650 For microprocessor chips. **£3.75**
- B EXP 300 The most widely sold breadboard in the UK; for the serious hobbyist. **£6.00**
- C EXP 600.6" centre channel makes this the Microprocessor Breadboard. **£6.60**
- D EXP 4B An extra 4 bus-bars in one unit. **£2.40**
- E EXP 325 Built in bus-bars accepts 8, 14, 16 and up to 22 pin ICS. **£1.65**
- F EXP 350 270 contact points, ideal for working with up to 3 x 14 pin DIPs. **£3.30**
- G PB6 Professional breadboard in easily assembled kit form. **£9.75** (Not illustrated.)
- H PB 100 Kit form breadboard recommended for students and educational uses. **£12.50** (Not illustrated.)

& IT'S AS EASY AS 1,2,3 with THE EXPERIMENTOR SYSTEM

SCRATCHBOARD

-BREADBOARD

-MATCHBOARD

1. EXP 300PC which includes one item. A matchboard pre-drilled PCB — **£1.20**
2. EXP 302 which includes three items. Three 50-sheet scratchboard workpads — **£1.50**
3. EXP 303 which includes three items. Two matchboards and an EXP 300 solderless breadboard — **£7.60**
4. EXP 304 which includes four items. Two matchboards and EXP 300 breadboard and a scratchboard workpad — **£8.70**

The above prices do not include P&P and 15% VAT.

TOMORROW'S TOOLS TODAY

GLOBAL SPECIALTIES CORPORATION G.S.C. (U.K.) Limited, Dept. 5H,
Unit 1, Shire Hill Industrial Estate,
Saffron Walden, Essex CB11 3AQ.
Tel: Saffron Walden (0799) 21682.
Telex: 817477.

NAME _____

ADDRESS _____

I enclose cheque/PO for £ _____

or debit my Barclaycard, Access, American Express card

No. _____ Exp. date _____

or Tel: (0799) 21682 with your card number and your order will be in the post immediately.

A EXP 650 £5.17	Qty. Req.	B EXP 300 £8.05	Qty. Req.
C EXP 600 £8.74	Qty. Req.	D EXP 4B £3.62	Qty. Req.
E EXP 325 £2.76	Qty. Req.	F EXP 350 £4.65	Qty. Req.
G PB6 £12.36	Qty. Req.	H PB 100 £15.52	Qty. Req.

Experimentor System


1 EXP 300 PC £2.25	Qty. Req.	2 EXP 302 £2.58	Qty. Req.
3 EXP 303 £9.40	Qty. Req.	4 EXP 304 £11.15	Qty. Req.

Boxed prices include P & P and 15% VAT

FREE catalogue
tick box ☐

Global Specialties Corporation (UK) Limited, Dept. 5H,
Unit 1, Shire Hill Industrial Estate, Saffron Walden Essex CB11 3AQ

The WERSI Concept...

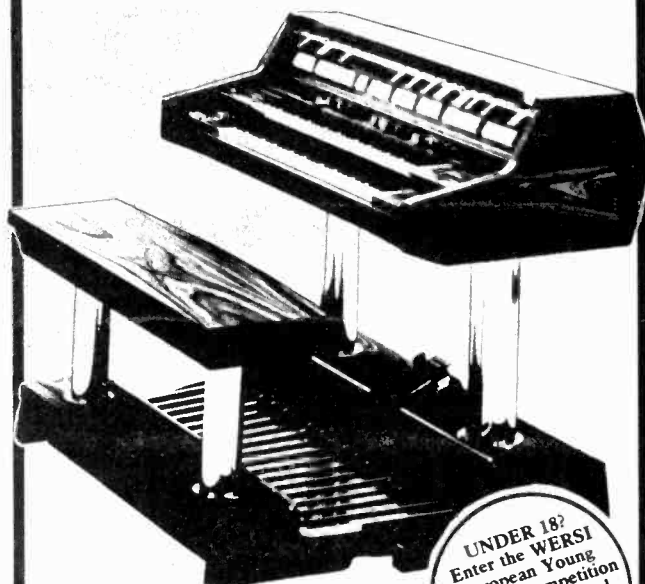

UNDER 18?
Enter the WERSI
European Young
Organist Competition
Over £9,000 Total
Prize Money.
Send for details
NOW!



Now you can indulge your ambition to spend more time playing music. At the same time you can build a superb organ at home, yourself, and it will cost you less than half the ready assembled price. You need no previous experience in electronics or carpentry — WERSI makes it easy.

Do you have to be a virtuoso or a music lover to benefit from building a WERSI organ? No... this would mean failure to recognize the sense of the hobby. Even after your project is completed you will be able to discover new excitement from the world of music. Whether you play haunting blues stomping disco, liturgical hymns or classic renditions the new generation of WERSI organs will make your life more enjoyable. Want to know more? Just fill in the coupon below, and we'll send you all the information.

WERSI

ORGANS & PIANOS
WERSI ORGANS & PIANOS LTD
14-15 Royal Oak Centre, Brighton Road,
Purley, Surrey. Tel: 01-668 9733.

PLEASE SEND ME FURTHER DETAILS OF THE WERSI RANGE

NAME _____

ADDRESS _____

Send to WERSI ORGANS & PIANOS LTD.,
14-15 Royal Oak Centre, Brighton Road, Purley, Surrey

PE

MASTER ELECTRONICS NOW!

The PRACTICAL way!

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to start or further a career in electronics or as a self-employed servicing engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write personally at any time, for advice or help during your work. A Certificate is given at the end of every course.

You will do the following:

- Build a modern oscilloscope
- Recognise and handle current electronic components
- Read, draw and understand circuit diagrams
- Carry out 40 experiments on basic electronic circuits used in modern equipment
- Build and use digital electronic circuits and current solid state 'chips'
- Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-Fi and microprocessor/computer equipment.



New Job? New Career? New Hobby? Get into **Electronics** Now!

FREE!

COLOUR BROCHURE



Please send your brochure without any obligation to

I am interested in:

PE/12/820

NAME

- ☐ COURSE IN ELECTRONICS as described above
- ☐ RADIO AMATEUR LICENCE
- ☐ MICROPROCESSORS
- ☐ LOGIC COURSE

ADDRESS

OTHER SUBJECTS

POST NOW TO:

BLOCK CAPS PLEASE

British National Radio & Electronics School Reading, Berks. RG1 1BR.

VIDEOTONE

Quality plus value ~ always

"The legendary
"MINIMAX"
— the small
speaker produc-
ing "Large
speaker" sounds.
Peak handling
100 watts.

ONLY £74.95
A PAIR!!!

NEW IMPROVED


MINIMAX 2

VIDEOTONE — For full range of loudspeakers, in-car, C.B.,
Video, audio & video cassettes, etc. Write for full details.

VIDEOTONE

98 CROFTON PARK ROAD,
LONDON SE4.
Tel: 01-690 8511. ext. 32.

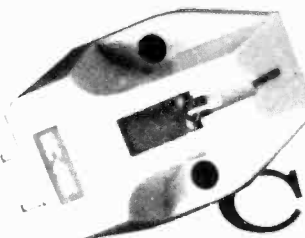Send for our free brochure and
details of outlets in the U.K.



the MC88E from CORAL

Moving Coil Cartridge — The MC88E is a high output cartridge
— so you do not need to use a head amp. EXCEPTIONAL
VALUE AT ONLY £24.95

Seoum Hi-Fi rep-
resents EXCELLENT
QUALITY AT A
REALISTIC PRICE!
The range offers a
choice of amplifiers,
tuner/amplifier, tuner,
and the excellent
SC4200 stereo cas-
sette recorder.



THE SCIENCE OF AUDIO

seoum

Post to: Videotone, Crofton Park Road, London SE4.


NAME _____

ADDRESS _____

MODULES FOR SECURITY & MEASUREMENT

AS FEATURED
IN
PRACTICAL
ELECTRONICS

INTRUDER ALARM CONTROL UNIT CA 1250

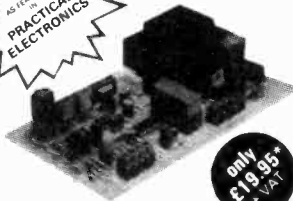

This exciting new module offers all the possible
features likely to be required when building an
intruder alarm system. Whether used with only 1 or
2 magnetic switches or in conjunction with several
ultrasonic alarm modules or infra-red units, a really
effective system can be constructed at a fraction of
the cost of comparable ready-made units. Supplied
with a fully explanatory Data Sheet that makes
installation straight forward, the module is fully
tested and guaranteed.

*available in kit form £16.95 plus VAT.

- Built-in electronic siren drives 2 loud speakers
- Provides exit and entrance delays together
with fixed alarm time
- Battery back-up with trickle charging facility
- Operates with magnetic switches, u/sonic or
I.R. units
- Anti-tamper and panic facility
- Stabilised output voltage
- 2 operating modes - full alarm/anti-tamper and
panic facility
- Screw connections for ease of installation
- Separate relay contacts for switching external
loads
- Test loop facility

only
£19.95
+ VAT

DIGITAL VOLTMETER MODULE DVM 314

Fully built & tested



- Positive & negative voltage with an FSD of
999mV which is easily extended
- Requires only single supply 7-12V
- High overall accuracy - 0.1% + 1 digit
- Large bright 0.43" LED displays
- Supplied with full applications data

only
£11.95
+ VAT

With this fully built and calibrated module a wide range of accurate equipment such as multimeters,
thermistors, battery indicators etc. can be constructed at a fraction of the cost of ready-made units. Full
details are supplied for extending the voltage range, measuring current, resistance and temperature.
Fully guaranteed, the unit has been supplied to electricity authorities, Government departments, etc.

Temperature Measurement Kit DT.10

£2.25 + VAT

Using the I.C. probe supplied, this kit provides a linear output of 10mV/°C over the temperature range
from 10°C to +100°C. The unit is ideal for use in conjunction with the DVM module providing an
accurate digital thermometer.

Power Supply PS.209

£4.95 + VAT

This fully built, mains power supply provides two stabilised isolated outputs of 9V, 250mA each. The unit
is ideally suited for operating the DVM and Temperature Measurement module.

ULTRASONIC ALARM MODULE

US 4012
Fully built
& tested

only
£10.95
+ VAT



Adjustable range
from 5ft. to 25ft.

A really
effective fully built
module containing both
ultrasonic transmitter and
receiver and circuitry for providing
false alarm suppression. This module,
together with a suitable 12V power supply
and relay unit as shown, forms an effective
though inexpensive intruder alarm. Supplied with
comprehensive Data Sheet, it is easily mounted in a
wide range of enclosures. A ready-drilled case and necessary
hardware is available below.

Power Supply & Relay Units PS 4012

£4.25 + VAT

Provides a stabilised 12V output and relay with 3A
contacts. The unit is designed to operate one or two
of the above ultrasonic units. Fully built and tested.

Hardware Kit HW 4012

£4.25 + VAT

A suitable ready-drilled case with the various mount-
ing pillars, mains switch socket and nuts and bolts.
Designed to house the ultrasonic alarm module
together with its power supply.
Size: 153mm x 120mm x 45mm

Siren Module SL 157

£2.95 + VAT

Produces a loud and penetrating sliding tone operat-
ing from 9-15V. Capable of driving 2 off 8 ohm
speakers to SPL of 110db at 2M.
Contains an inhibit facility for use with shop lifting
loops or other break to activate circuits.

★ ACCESSORIES ★

- 3-position Key Switch for use with
CA 1250, supplied with 2 keys £3.43
- Magnetic switch (with magnet) £1.17
- 5" Horn speaker for use with CA 1250
and SL 157 £4.95

Add VAT & 50p post and packing
to all orders.

Shop hours 9.00 - 5.30 p.m.

(Wed. 9.00 - 1.00 p.m.)

Units on demonstration - callers
welcome. S.A.E. with all
enquiries.



RISCOMP LIMITED

Dept: PE 12

21 Duke Street,
Princes Risborough, Bucks.

Princes Risborough (084 44) 6326

Please allow 7 days for delivery

Rapid Electronics

Tel: 0206 36412
Hillfarm Industrial Estate
Boxed
Colchester Essex CO4 5RD



CMOS		*4017	30	*4036	249	*4055	80	*4082	12	*4502	60	*4529	150
4000	10	4018	45	4039	280	4059	430	4085	48	4503	32	4532	60
*4001	10	4019	25	4040	40	4060	42	4086	50	4507	35	4534	40
4002	12	4020	42	4041	40	4063	80	4089	125	4508	125	4538	110
4003	12	4021	40	4042	38	4066	22	4093	18	4510	45	4543	70
4006	50	4022	45	4043	40	4068	225	4094	58	4511	45	4549	360
4007	14	4023	23	4044	40	4068	14	4095	65	4512	50	4553	245
4008	36	4024	33	*4046	50	4069	13	4097	290	4514	120	4555	35
4009	24	4025	16	4047	45	4070	13	4098	70	4515	120	4556	35
4010	24	*4026	75	4048	38	4071	13	4099	70	4516	55	4559	390
*4011	11	4027	20	*4049	21	4072	13	4100	40	4518	40	4560	175
*4012	15	4028	40	4050	21	4073	13	4103	110	4520	50	4564	40
*4013	20	4029	45	4051	42	4074	13	4104	60	4521	130	4565	60
4014	45	4030	14	4052	48	4076	45	4107	100	4526	60	4724	140
4015	40	4031	125	4053	48	4077	14	4108	75	4527	50		
4016	20	4034	140	4054	78	4081	12	4109	65	4528	50		

LS TTL		LS21	12	LS76	17	LS125	24	LS161	35	LS221	50	LS365	28
*LS00	11	LS22	12	LS78	17	LS126	25	LS162	35	LS240	60	LS366	28
LS01	11	LS23	12	LS79	17	LS127	35	LS163	35	LS241	60	LS367	28
LS02	11	LS27	12	LS85	48	LS136	26	LS164	40	LS242	55	LS368	29
LS03	11	LS22	12	LS86	16	*LS138	30	LS165	55	LS243	55	*LS373	60
LS04	12	LS23	12	LS89	24	*LS139	30	LS166	60	LS244	55	LS374	60
LS05	12	LS27	13	LS90	25	LS140	70	LS167	75	*LS245	70	LS375	60
LS06	12	LS38	15	*LS93	24	LS147	150	LS173	60	LS247	48	LS377	60
LS08	12	LS40	13	LS95	38	LS148	75	LS174	45	LS251	28	LS378	57
*LS09	12	*LS42	13	LS96	38	LS149	75	LS175	45	LS252	28	LS379	57
LS10	12	*LS47	35	LS107	30	LS153	78	LS190	35	LS258	32	LS393	45
LS11	12	LS48	45	LS109	21	LS154	75	LS191	35	LS259	55	LS399	156
LS12	12	LS51	14	LS112	21	LS155	33	LS192	35	LS266	58	LS454	78
LS13	12	LS52	14	LS113	21	LS156	33	LS193	35	LS267	58	LS455	78
LS14	12	LS53	14	LS114	21	LS157	33	LS194	35	LS268	58	LS456	78
LS107	12	LS146	14	LS207	21	LS250	33	LS287	35	LS361	58	LS549	78
LS108	12	LS147											



ELECTRONIC HOBBIES FAIR

Alexandra Pavilion London November 18–21 1982
**The biggest and best event ever to be
staged for the
electronic hobbies enthusiast!**

Walk into a whole world of electronic equipment. – Everything from resistors, IC's to home computers, transmitting and receiving units, citizens band radio and peripheral equipment, video games, musical instruments, radio control models. . . . In fact whatever your particular electronic hobby you'll find this show will be the most interesting and informative way to discover all the latest developments in your particular field.

Other attractions will include radio and TV transmission, electric vehicles, radio controlled models, and demonstrations by local and national organisations.

This is the age of the train – British Rail are offering a cheap rate rail fare from all major

stations in the country direct to Alexandra Palace – a bus will be waiting on your arrival to take you to the show. Ticket price also includes admission to the exhibition – so let the train take the strain to the Electronic Hobbies Fair.

Ticket prices at the door are £2 for adults, £1 for children but party rates are available for 20 people or more. To find out more, contact the Exhibition Manager, Electronic Hobbies Fair, IPC Exhibitions, Surrey House, 1 Throwley Way, Sutton, Surrey SM1 4QQ. Tel: 01-643 8040.

Electronic Hobbies Fair is sponsored by Practical Electronics, Everday Electronics and Practical Wireless and is organised by IPC Exhibitions Ltd.


OPENING TIMES

Thursday 18 Nov. – 10.00-18.00

Friday 19 Nov. – 10.00-18.00

Saturday 20 Nov. – 10.00-18.00

Sunday 21 Nov. – 10.00-17.00

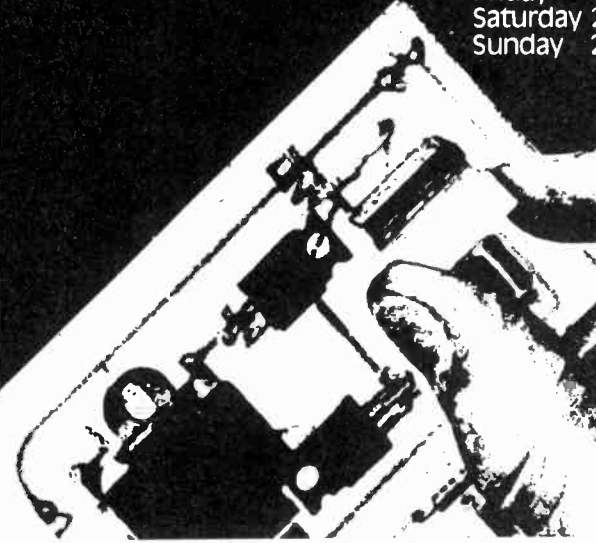

50p OFF

admission if you produce this coupon
at the door of Electronic Hobbies Fair.
Valid one per person only any day.

E.H.F.

JUST one last reminder re. **Electronic Hobbies Fair** (November 18th to 21st Alexandra Pavilion), this will be the best event ever for the hobbyist in this country. Just about all the top names in the retail supply business will be there—some are arranging special offers for the Fair, our own 50p off coupon is on the opposite page. In addition to the trade stands there will be a number of special attractions; like the Luxor satellite TV receiver mentioned last month; a display of electric vehicles built by members of the Battery Vehicle Society (more about them later); a demonstration of holography by Holographic Developments (you will be able to purchase some examples); some working radio controlled models; an exhibit by the Royal Signals and an amateur radio talk-in station operating on the 2m band, channel S22 (145.55MHz).

You will be able to try out computers have a go at the latest video games and much, much more. There will be stands representing clubs and organisations—like the RSGB—and plenty to buy.

On the PE stand Editorial staff will be waiting to meet you and discuss the

various projects on display. Among other things we will be showing *Micro-grasp*, *Microsynth*, *Microcontroller* our *Semi-Professional Mixing Desk*, *Ultimum* and one or two future projects. The other sponsoring magazines PW and EE will have similar stands and the following IPC magazines will also have a presence at the Fair; Practical Hi-Fi, Television, Wireless World, Practical Computing, Your Computer, and CB World.

ACCESS

Access to the show is easy—there's plenty of car parking and a park-and-ride bus. The Victoria and Piccadilly lines provide fast access to and from the West End and British Rail main line stations—King's Cross, St. Pancras, Euston and Victoria. Finsbury Park and Wood Green underground stations are linked to Alexandra Pavilion by the London Transport W3 bus service which runs every 7 to 10 minutes on all the Fair days. Also Alexandra Palace British Rail station will be linked to the show by a free bus shuttle service; this station is close to Wood Green underground station and is on the BR main and suburban lines from King's Cross and Moorgate.

Special fares are available from all

major British Rail stations direct to Alexandra Palace station and ticket price will include admission to the show—over 300 stations in the U.K. can provide access to Alexandra Palace with only one change of train. Through tickets to BR Alexandra Palace are available at underground ticket offices.

B.V.S.

Finally, a word about the Battery Vehicle Society. The B.V.S. was founded in 1973 to promote battery electric vehicles in all their forms and to provide a forum for everyone interested in this form of transport. The Society publishes a monthly magazine, *Battery Vehicle Review*, containing articles on the history, development and use of battery vehicles.

Following the 1979 Lucas 'How far can you get' competition for design and construction of lightweight electric vehicles, the B.V.S. competition section has monthly runs where the creations of members challenge each other to make the best of 56lbs of lead/acid battery. Some of these vehicles will form the special B.V.S. display at Electronic Hobbies Fair—see you there.

Mike Kenward

EDITOR Mike Kenward

Gordon Godbold ASSISTANT EDITOR

David Shortland ASSISTANT EDITOR/PRODUCTION

Mike Abbott TECHNICAL EDITOR

Jack Pountney ART EDITOR

Keith Woodruff ASSISTANT ART EDITOR

John Pickering SEN. TECH. ILLUSTRATOR

Isabelle Greenaway TECH. ILLUSTRATOR

Jenny Tremaine SECRETARY

ADVERTISEMENT MANAGER

D. W. B. Tilleard

SECRETARY Christine Pocknell

01-261 6676

AD. SALES EXEC. Alfred Tonge 01-261 6819

CLASSIFIED SUPERVISOR Barbara Blake 01-261 5897

AD. MAKE-UP/COPY Ian Sweeney 01-261 6601

Technical and Editorial queries and letters (see note below) to:

Practical Electronics,
Westover House,
West Quay Road, Poole,
Dorset BH15 1JG

Phone: Editorial Poole 671191

We regret that lengthy technical enquiries cannot be answered over the telephone

Queries and letters concerning advertisements to:

Practical Electronics Advertisements,
King's Reach Tower,
King's Reach, Stamford Street, SE1 9LS
Telex: 915748 MAGDIV-G

Letters and Queries

We are unable to offer any advice on the use or purchase of commercial equipment or the incorporation or modification of designs published in PE. All letters requiring a reply should be accompanied by a stamped, self addressed envelope, or addressed envelope and international reply coupons, and each letter should relate to **one published project only**.

Components and p.c.b.s are usually available from advertisers; where we anticipate difficulties a source will be suggested.

Back Numbers

Copies of most of our recent issues are available from: Post Sales Department (Practical Electronics), IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF, at £1 each including Inland/Overseas p&p. Please state month and year of issue required.

Binders

Binders for PE are available from the same address as back numbers at £4.60 each

to UK or overseas addresses, including postage and packing, and VAT where appropriate. Orders should state the year and volume required.

Subscriptions

Copies of PE are available by post, inland or overseas, for £13.00 per 12 issues, from: Practical Electronics, Subscription Department, Oakfield House, Perry Mount Road, Haywards Heath, West Sussex RH16 3DH. Cheques and postal orders should be made payable to IPC Magazines Limited.

Items mentioned are available through normal retail outlets unless otherwise specified. Prices correct at time of going to press.

...NEWS &

'Now is the Winter for Public Debate'

Both the IBA and the BBC are concerned about the affects unregulated cable TV could have on the standard of British Broadcasting. The Independent Broadcasting Authority has called for a winter of public debate on the expansion of cable and satellite broadcasting. After its first Autumn meeting the IBA made the following statement.

"The Independent Broadcasting Authority recognises the Government's commitment to the establishment of a national information grid through the expansion of broadcasting in the United Kingdom; and it is eager to use its many years of experience to contribute to the opportunities presented by this expansion of communications in the 80s while maintaining the high standards of British broadcasting. The unique quality of output which has earned a world-wide reputation for British programme-makers must not be eroded.


"The proposals of the Hunt Committee will be crucial to the expansion of broadcasting. Mistakes made now would take years to correct. It is for this reason that the Authority calls for a winter of public debate before the final decisions are taken. The Authority has no wish to delay the changes which clearly are on the way—on the contrary, the Authority believes that the creation of Channel Four was far too long delayed—but it believes that it is crucial to lay down the best possible framework for new developments and to ensure that meeting the challenge of wider choice need

not mean lower standards."

Meanwhile the BBC in its evidence to the Hunt Committee said that unregulated cable TV would be "socially divisive, sacrifice hard won programme standards and coarsen popular taste". It also warns that it might lead to the disappearance of big sporting events such as the FA Cup Final and the Olympic Games from BBC and ITV screens because the BBC says cable operators concentrating their resources on 'blockbuster' attractions might well be in a position to outbid the BBC and ITV in the areas of sport and entertainment, thus posing the public service broadcasters with a cruel dilemma. "They must either commit a disproportionate amount of their resources to matching the bids of the cable operators—thus impoverishing other areas of programming—or see the majority deprived of such star attractions in favour of a paying minority". The BBC also pointed out that perhaps no more than 50% of British viewers will have access to the proposed cable systems and that individuals will have no power to affect the issue because access will be determined by economic or geographical status.

POWER MODULE

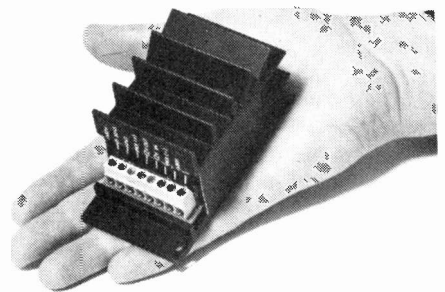The C15 mono power booster amplifier from ILP is designed to increase the output of any in-car entertainment system to a nominal 15W r.m.s. The amplifier is encapsulated into an integral heatsink making it a very compact, robust unit.



The system features automatic supply switch-on which is activated when the radio or cassette is turned on. It also has a selectable input level facility so it can be driven from either the low signal levels of a pre-amp or straight from the existing units speaker leads. If stereo operation is required then two units can be used.

Priced at £9.14 inclusive of VAT and p&p the C15 is available from ILP Electronics Ltd., Graham Bell House, Roper Close, Canterbury, CT2 7EP (0227 54778).

AVO 2000

A new British design concept in hand-held digital multimeters—for a wide range of electrical maintenance, field servicing and vehicle testing applications—has been launched by THORN EMI Instruments Limited.


With the AVO 2000 Series the company has concentrated on providing a design offering a host of 'ease-of-use' features.

Initially, the AVO 2000 Series comprises three instruments for specific applications: the AVO Digiminor 2000; the AVOMeter 2001 and the AVO Vehicle Test 2002.

Each is housed in a tough ABS case and fitted with non-slip safety pads, the important new features of all three instruments include: Direct entry prods—giving true one-hand operation; A $3\frac{1}{2}$ digit l.c.d. readout at the

base of the housing; Positive action slide switching with dustproof, positive range selection; Improved safety, with fully shrouded plugs for the lead set; and a three-position stand—the instrument can be used in the hand, on a bench or while hung from a hook.

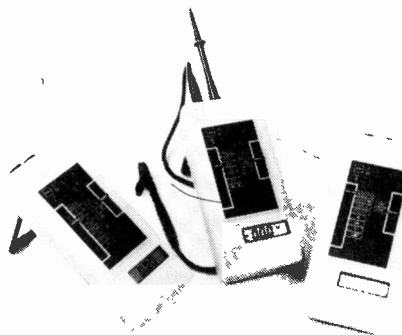Ideally suited to maintenance applications, the Digiminor 2000 incorporates a special buzzer socket for sim-



ple continuity testing without reference to the display.

The AVOMeter 2001 is designed primarily for field servicing applications. Featuring more comprehensive ranges than the Digiminor 2000, it ensures correct mode and range selection by the inclusion of an audible alarm which signals any discrepancy. Both the unit and mode of measurement are displayed on the l.c.d.

The AVO Vehicle Test 2002 is unique: it is the first digital multimeter of its kind designed specifically to simplify the testing of electrical circuits of any road vehicle from a small saloon car to HGV.


The AVO Digiminor 2000 is priced at £69.40, the 2001 at £85.40 and the 2002 at £97.00. Each multimeter is supplied with the appropriate lead sets, battery and operating instructions.

Thorn EMI Instruments Ltd., Archcliffe Road, Dover, Kent (0304 202620).

MARKET PLACE

CAPACITANCE METER

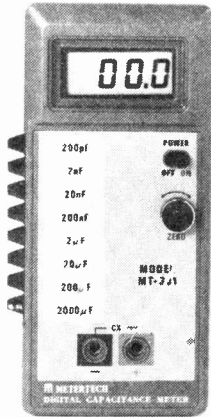The Metertech model MT301 is a low cost hand held digital capacitance meter which is battery operated with a 3½ digit liquid crystal display capable of measuring



capacitance values from 0.1pF to 2000µF over 8 push button ranges.

The unit is priced at £69 and is available from Centemp Instrument Co., 62 Curtis Road, Hounslow, Middlesex (01-894 2723).

ENERGY SAVER

The Velleman Heating Controller is designed to control the temperature inside offices, factories, houses etc., enabling central heating systems to work more economically.

It provides a 4 program daily cycle controlling the temperature at any given period. The programs are totally independent and therefore it is possible to select day and night temperatures separately.

The display functions as a clock as well as a thermometer with the device replacing conventional mechanical thermostats without additional wiring. The unit can be manually over-ridden at any time without disturbing any of the preselected programs.

The system is available in kit form (£75.00 ex VAT) and also as a built and tested unit.

Velleman (UK) Limited, P.O. Box 30, St. Leonards on Sea, East Sussex, TN37 7NL. (0424 753246).



CHIP LEG HAND TOOL

A simple hand tool that restores splayed-out legs on integrated circuits to the correct spacings has just been introduced by Aries Electronics. Called the DIP-R-SIZER, the new tool can handle integrated circuits with either 0.300in or 0.600in leg spacing.

When manufactured, the legs on integrated circuits are often outside the tolerances specified for centre spacings. The nominal 0.300in and 0.600in centres have a maximum tolerance of +0.020in. In practice a considerable proportion of integrated circuits leave the factory with spacings up to 0.095in above the nominal centre spacing. Particularly with high pin-count devices, attempts to insert out-of-tolerance legs into integrated circuit sockets or printed circuit boards often results in damage to the legs, the contacts in the socket or the holes in the printed circuit board.

The tool which has a pair of jaws hinged at one end is held open with a spring at the other. An anvil between the jaws is contoured to the correct angle and spacing for the integrated circuit legs. One side of the anvil takes 0.300in centre devices while the other takes the 0.600in size. To rectify splayed legs, the device is placed on the appropriate side of the anvil and the jaws squeezed lightly together. This presses the legs against the anvil, and brings them automatically into tolerance. While inten-



ded primarily for correcting leg spacings as received from the manufacturer, the tool can also be used to rectify legs put out of tolerance through mishandling. However, it cannot restore damaged devices where the legs have been displaced longitudinally—that is where the pitch between individual pins have been disturbed.

The tool which is priced at £10.50 including VAT and p&p. is available from Aries Electronics (Europe) Ltd., Metrostore House, Eastways, Witham, Essex CM8 3YQ. (0376 519318).

SUPERSWITCH HOME COMMAND CENTRE

The Superswitch Command Centre has been developed for the remote control of lamps and electrical appliances.

The unit which transmits high frequency coded signals along existing mains wiring is capable of controlling up to 16 appliances either manually or automatically. The centre can be pre-programmed up to 7 days in advance with a maximum of 24 programs.

The coded signals are received by modules which plug into the 13A socket outlets. Appliance modules operate electrical loads up to 13A whereas lamp modules can control Tungsten lighting loads up to 400W.


Other features of the unit include the manual dimming and brightening of lamps, battery back-up and the ability to turn on all lamps simultaneously. The Command Centre is priced at £73.70 with the appliance and lamp modules priced at £24.00 each.

Another Superswitch system which uses mains wiring is the Plug-In Intercom. This FM unit can plug into any 13A socket anywhere on a ring main, and send messages

using the mains wiring.


Up to 5 units can be used in conjunction with each other or a private conversation can be carried out between two units without the others on the system being able to hear. The intercom is priced at £37.45 per unit.

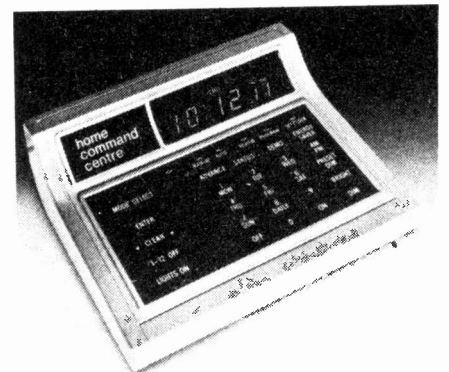Superswitch, 7 Station Trading Estate, Blackwater, Camberley, Surrey.



CHESSE SENSOR

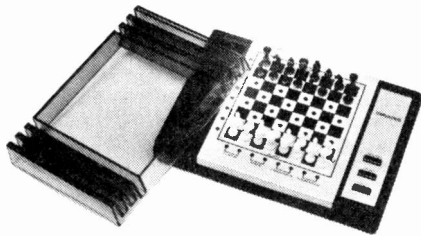The CG1 Sensor Computer chess game from Systema has 8 levels and is priced under £30. The unit measures only 175x120x47mm and can be either battery powered for up to 50 hours from a standard PP3 or mains operated.



The unit has a built-in sensory board which is operated by pressing down on the piece you are moving, a light shows your 'from' position and pressing down the piece on your 'to' position. The computer then records your move and indicates its reply.

Other features include changeable levels during play, side changes during play, en-passant captures, castling and pawn promotion.

Systema (UK) Limited, 25 King's Road, Reading, Berkshire.

Sensalite

An automatic light switch called Sensalite enables a room light to be automatically switched on when someone enters a room where lights are needed and then automatically switches the lights off when the room is vacated.

The unit operates by looking for movement and then at the prevailing lighting condition.



When the unit detects movement it checks the natural light level and, if required, switches on the light. The level at which the lights are energised can be set by the user.

Sensalite, a 100mm cube which is linked into the existing lights has provision for an additional burglar alarm module.

The unit is priced at £85 including VAT. Leading Edge Technologies Ltd., 1-4 Kings Parade, Croydon, Surrey (01-686 0255).



A new 16K RAM pack for the ZX81 which overcomes the "wobble" or disconnection problems associated with many add-on units is also available with a keyboard sounder as an optional extra. The sounder enables a faster entry of programs from the keyboard by giving an audible feedback when a key is pressed.

The RAM pack is priced at £19.95 and with a keyboard sounder is priced at £24.95.

Ground Control, Alfreda Ave, Hullbridge, Essex, (0702 2303 24).

POINTS ARISING . . .

COMBO AMPLIFIER (Sept. '82)

The following winding details should accompany L1 in Fig. 2.8: Three layers of ten turns each (30 turns total) should be wound using 18 s.w.g. enamelled copper wire. Resistor R13 should be 15k. The drain and source annotations of TR8 and TR9 in Fig. 2.1 should each be transposed.

Countdown . . .

Please check dates before setting out, as we cannot guarantee the accuracy of the information presented below. Note: some exhibitions may be trade only. If you are organising any electrical/electronics, radio or scientific event, big or small, we shall be glad to include it here. Address details to Mike Abbott.

Compec Nov. 16-19. Olympia. Z1

Electronic Hobbies Fair Nov. 18-21. Alexandra Pavilion, London. Z1

INTRON Nov. 23-25. RDS Dublin, Ireland. V

BEX Bristol Nov. 24-25. Holiday Inn. K

Northern Computer Fair Nov. 25-27. Belle View, Manchester. Z1

Christmas Holography (+items for sale) Dec. 2-Mar. (1983) Light Fantastic Gallery, London. A8

ElectroNORTH Dec. 7-9. Harrogate Supercenter. Q

IT82 (Information Technology Year Conf.) Dec. 8-9. Barbican. O

Continuous exhibitions at the National Microprocessor & Electronics Cntr. (nr. tower of London). L1

Peripherals Feb 2-4 1983. Cunard Int. Hotel, Hammersmith, London. Z1

BEX Bournemouth Feb. 9-10 1983. The Pavilion. K

Microsystems Feb. 23-25 1983. West Cntr. Hotel, Fulham, London. Z1

CAD North Mar. 1-3 1983. Belle Vue Ex. Cntr., Manchester. Z1

Mailing Efficiency Mar. 1-3 1983. Bloomsbury Cntr. Hotel, London. Z

Local Networks Mar. 8-10 1983. Royal Lancaster Hotel, London. O

Laboratory Edinburgh Mar. 16-17 1983. Assembly Rooms, George St. E

Brighton Electronics March 1983. T

BEX Leeds Mar. 16-17 1983. Dragonara Hotel. K

INSPEX Mar. 21-25 1983. National Exhibition Cntr. Birmingham International. Z1

Sensors & Systems Mar. 22-24 1983. The Forum, Wythenshawe. T

Compec Wales Mar. 22-24 1983. Cardiff University. Z1

ETM (Electronic Test/Masurement) Mar. 22-24 1983. The Forum, Wythenshawe, Manchester. T

Laboratory Manchester Mar. 23-24 1983. New Century Hall, Corporation St. E

American Holography Mar.-June inc. Light Fantastic Gallery, Covent Garden, London. A8

All Electronics Show April 19-21 1983. Barbican Cntr. London. E

Fibre Optics April 19-21 1983. Porter Tun Rooms, The Brewery (!), Chiswell St., London EC1. E

International Materials Handling April 19-26 1983. Earls Court. I

International Packaging Exhibition April 25-29 1983. NEC B/ham. I

A8 Holographic Exhibitions ☎01-836 6423

E Evan Steadman ☎0799 22612

K Douglas Temple Studios ☎0202 20533

L1 World Trade Cntr., Europe Ho., London E1

O Online ☎09274 28211


Q Exhibitions For Industry ☎08833 4371

T Trident ☎0822 4671

Z BETA Exhibitions ☎01-405 6233

Z1 IPC Exhibitions ☎01-643 8040

Jupiter ACE

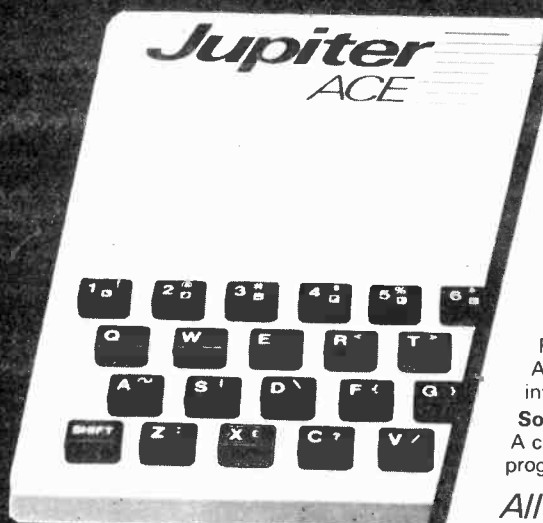

only
£89.95

All inclusive price

For £89.95 you receive your Jupiter Ace, a mains adaptor, all the leads needed to connect to most cassette recorders and T.V.s (colour or black and white), a software catalogue and a manual.

The manual is a complete introduction to the world of personal computing and a course in FORTH programming on the Ace.

Even if you are a complete newcomer to computers, the manual will guide you step by step from first principles to confident programming.

The price includes postage, packing and V.A.T.

The Jupiter Ace is backed by a full 12 month warranty.

The Jupiter Ace is available only by mail order. Please allow up to 28 days for delivery. Send cheque or postal order with the form to:—
JUPITER CANTAB, 22 FOXHOLLOW
BAR HILL, CAMBRIDGE CB3 8EP

The Jupiter Ace uses FORTH

The Jupiter Ace personal computer runs in FORTH, an easily understood language, typically four times as compact and ten times as fast as BASIC. Before the Ace all personal computers used BASIC and FORTH was only available to a privileged few. The Jupiter Ace also features a full-size moving-key keyboard, high-resolution graphics, sound, floating point arithmetic, a fast and reliable cassette interface and 3K of RAM.

Available soon

Plug-on parallel printer interface.

For around £20.00 this will connect your Jupiter Ace to anything from high-speed dot matrix to letter-quality daisy wheel printers.

Plug-on 16K Memory Expansion

For around £30.00 you will increase the memory of your Jupiter Ace to 19K giving you instant access to enormous amounts of information.

Software

A catalogue will be sent with every machines, and includes, initially, programs for education and entertainment.

Technical Information

Hardware

Z80A running at 3.25 MHz.
8K bytes ROM
3K bytes RAM

Keyboard 40 Moving-key keyboard with auto repeat on every key and Caps Lock.

Screen Memory mapped 32 column x 24 line flicker-free display with upper and lower case ascii character set.

Graphics Chunky graphics (64 x 46 pixels) may be plotted, unprinted or over-plotted (XOR operation). Also, the entire character set (128 characters and their video inverses) may be redefined allowing intricate shapes to be drawn with a resolution equivalent to 256 x 192 pixels.

Sound Internal loudspeaker may be programmed to operate over the entire audio spectrum.

Cassette Programs and data in the compact dictionary format may be saved, verified, loaded and merged. Blocks of memory can be saved, verified, loaded and relocated. All tape files are named. Running at 1500 baud, the Ace will connect to most portable tape recorders.

Expansion Port Contains D.C. power rails and full Z80 Address, data and control signals. May be used to connect extra memory and other peripherals. IN and OUT words allow port-based peripherals to be addressed.

Data Structures Integer, Floating point and String data may be held as constants, variables or arrays with multiple dimensions and mixed data types. There are no restrictions on names.

Control Structures IF-ELSE-THEN, DO-LOOP DO-+LOOP, BEGIN-WHILE-REPEAT, BEGIN-UNTIL, all may be mixed and nested to any depth.

The Jupiter Ace closely follows the FORTH 79 standard with extensions for floating point, sound and cassette. It has a unique and remarkable editor that allows you to list and alter words that have been previously compiled into the dictionary. This avoids the need to store screens of source, allowing the dictionary itself to be saved on cassette. Comprehensive error checking removes the worry of accidentally crashing your programs.

ORDER NOW!

Please send me:—

☐ JUPITER ACE MICROCOMPUTER(S) @ £89.95.

Name. Mr/Mrs/Miss _____

Address _____

_____ PE

Designed by Jupiter Cantab

Computer Designers Steven Vickers and Richard Altwasser played a major role in creating the ZX Spectrum and then formed Jupiter Cantab to develop advanced ideas in personal computing. The Ace is the result, another all-British computer to lead the world.

STYLOCHORD

Stephen Ibbs



HOW IT WORKS

The main i.c. being used is the 5024 top-octave-generator, (also coded S50240 by Tandy). From a single frequency input of 2.0024 MHz it will produce thirteen semitones, equally tuned. This frequency is generated by the astable multivibrator IC1a and b, adjustment being made by VR1. If the input frequency is halved, the 13 outputs will also be halved, sounding an octave lower. Consequently IC2b (part of a 4013), is connected as a $\div 2$ divider which feeds 1.0012 MHz into another 5024 to give another lower octave of notes. The 4013 is a dual D type flip-flop, and contains two identical circuits. If the data pin is connected to the $\bar{Q}$ pin, and the set and reset pins are connected to earth it will divide the incoming frequency by two. See Fig. 2 for details. Thus half of the 4013 was still unused, and this can be utilised to divide the output of the multivibrator prior to entry into IC2b and IC3, giving the unit an octave-down shift. Originally IC1a and b fed IC2b and IC3 direct, but it was found during development that switching in the octave shift caused a slight shift in frequency, affecting the tuning, so IC1d was included to act as a buffer, and this cured the problem.

The outputs from the top-octave-generators are connected to the appropriate keys, (see Fig. 3) and selected by either of the stylii, with S2 selecting whether one or both of IC5 and 6 are connected to each stylus. R2 and R3 are included to make sure that the inputs of IC5 and 6 are grounded when not in use. These i.c.s further divide the frequencies to bring them into the required audio octave range. Four outputs of each can be selected by the switch bank S3-S6, being square waves from IC5 and triangular waves from IC6, the change in waveform shape being accomplished by the resistors R8-R15, and capacitors C2-C5.


If pin 12 of IC6 is taken as an example, a square wave comes out, but R8 controls the charging rate of C2, giving a slope to the leading edge of the square wave; and R12 controls the discharge rate, giving a slope to the trailing edge resulting in an approximate triangular waveform. None of these values are critical and constructors should experiment to find the most satisfactory result. Different values will affect the waveform shape and the amplitude (loudness) of each voice.

TWIN PROBE STYLUS ORGAN


THE instrument popularised by Rolf Harris some years ago generated a plethora of similar designs, and many people clearly derived a great deal of enjoyment from these ingenious devices. With the inexorable march of progress, many i.c.s have developed, and become cheap enough for new improved designs to be produced. However, all the designs seen by the author demanded accurate resistor chains, or several presets, making the tuning of the instrument difficult. They were also limited in the sound they could produce.

The project described here is a two octave keyboard, with only one tuning preset, no resistor chains, and eight different voices: 16', 8', 4', 2' Square-wave, and 16', 8', 4', 2' triangular wave. The footages refer to the approximate physical length of organ pipes, but are used to indicate octave pitch, 8' being the standard, 16' being an octave lower, and 4' and 2' being one and two octaves higher respectively. The whole instrument can be transposed by an octave by means of a switch, and so the unit has a total range of six octaves. It contains two stylii, each controlling four voices, to enable the playing of two notes at a time, and a further switch decides whether one stylus plays one or both waveforms. See Fig. 1 for a simplified block diagram. Regular readers will note that the project is a development from the 'Instrument Tuner' (July 82).

Fig. 1. Block diagram of the Stylochord


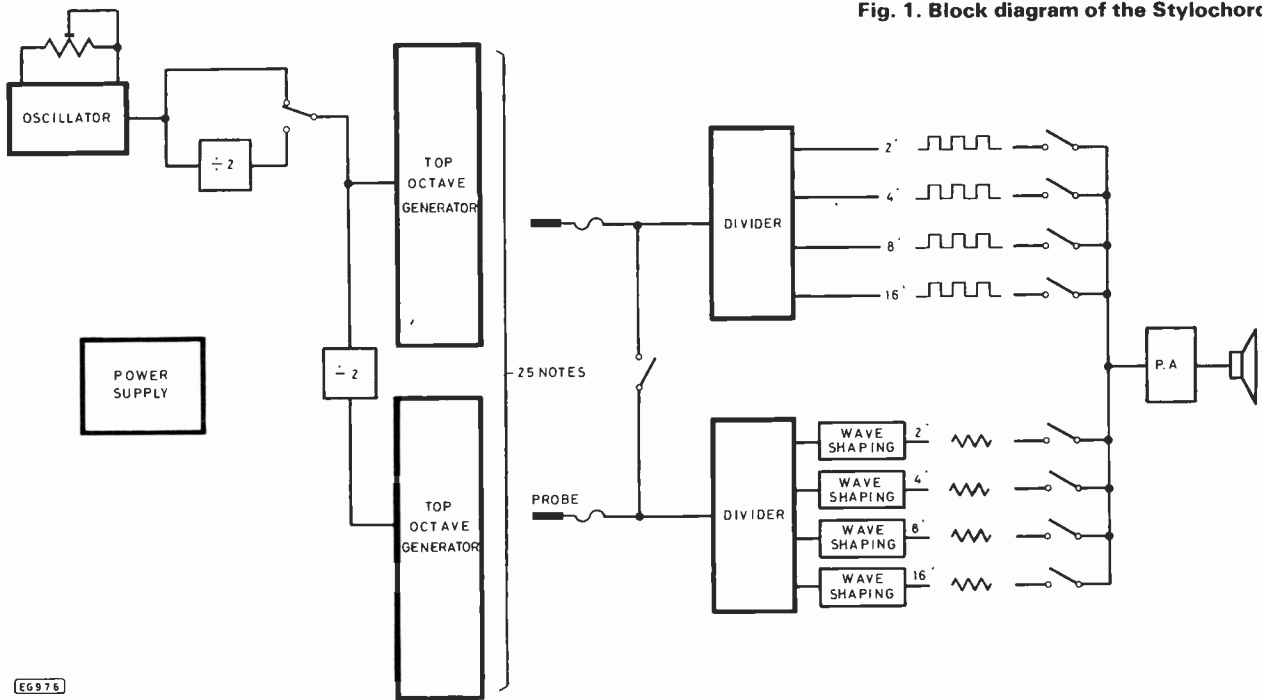


EG976

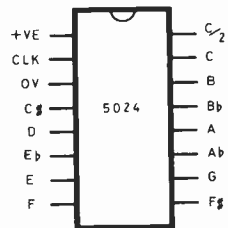


EG 972

Fig. 2. 4013 in ÷2 mode (right)

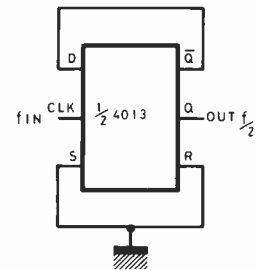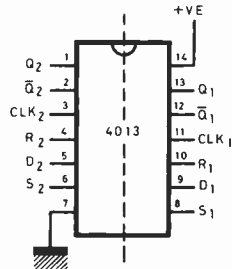

EG975

Fig. 3. Circuit diagram

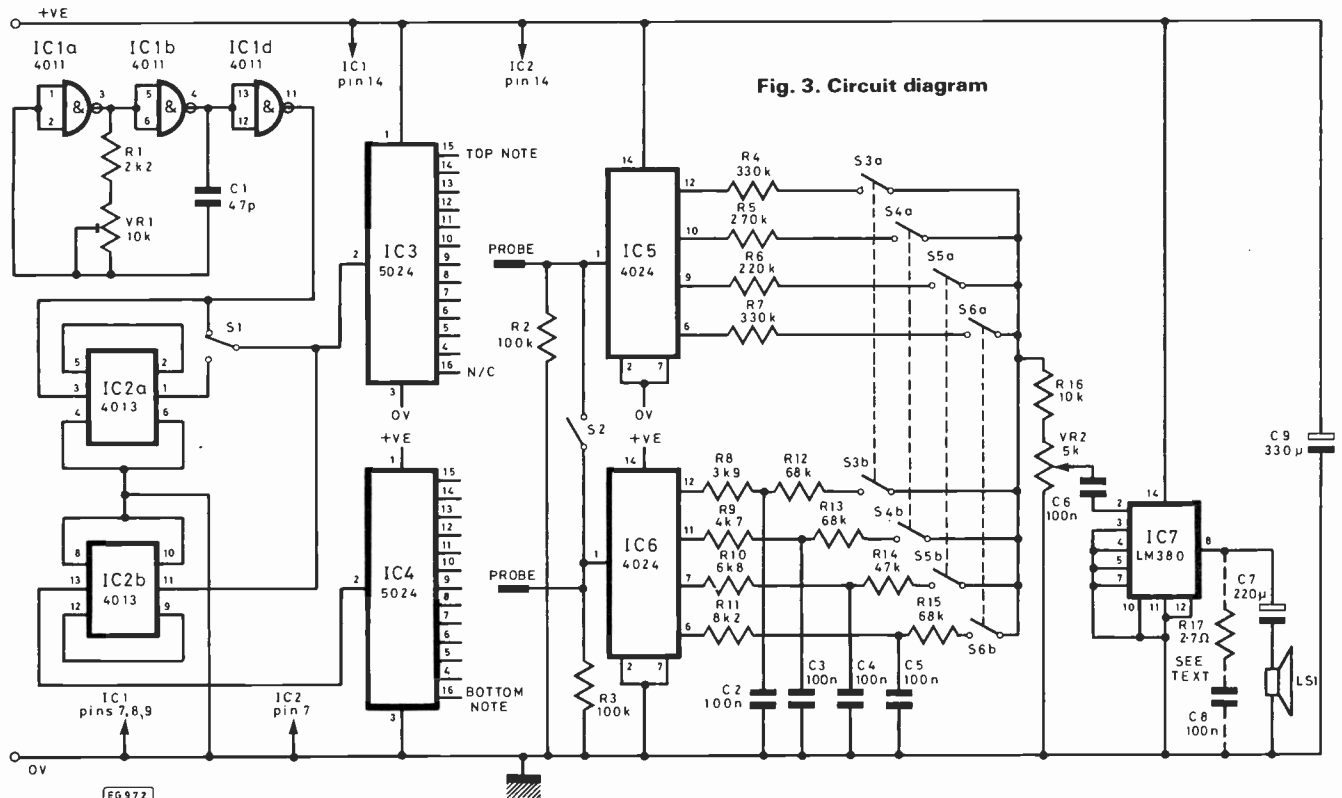

EG977

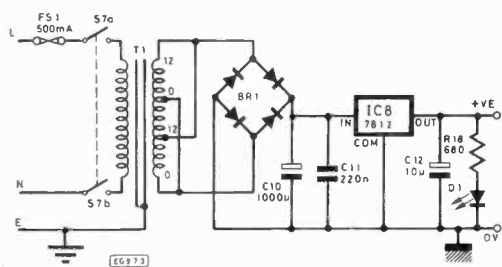


Fig. 4. PSU circuit diagram

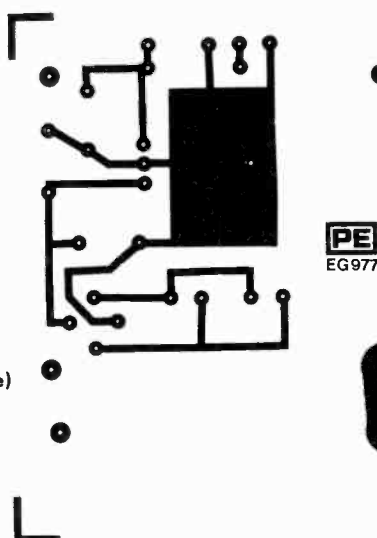


Fig. 5. PSU printed circuit (actual size)

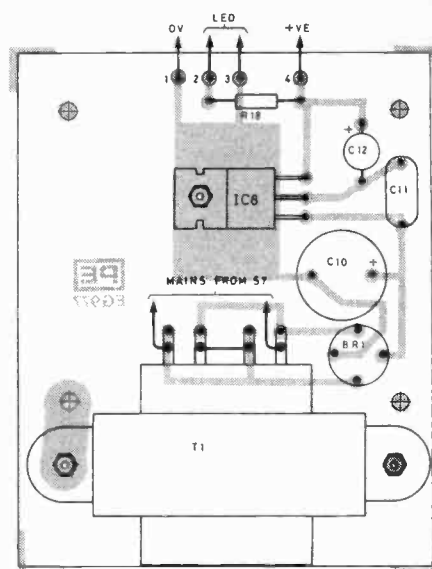


Fig. 6. PSU component layout (right)

The outputs can be switched in via S3-S6 and the result goes via the potential divider VR2 acting as a volume control to the audio amp. IC7, an LM380 2 watt i.c. If high frequency oscillation occurs, a Zobel network consisting of a 2.7 ohm resistor and a 1μ polyester capacitor in series from pin 8 to earth can be inserted, but this was not found to be necessary in the prototypes. However, space is made for these two components on the p.c.b.

The inclusion of a mains power supply may seem strange

to readers, but there are several reasons for it. IC3 and 4 require 11-16 volts, so the convenient PP range of batteries couldn't be used, and with the volume control turned up, the battery drain would be quite high. Also a mains powered regulated supply ensures a reliable voltage source, preventing frequency stability problems. Readers can, of course, omit the power supply and replace it with batteries, and it is for this reason that the power supply p.c.b. is separate.

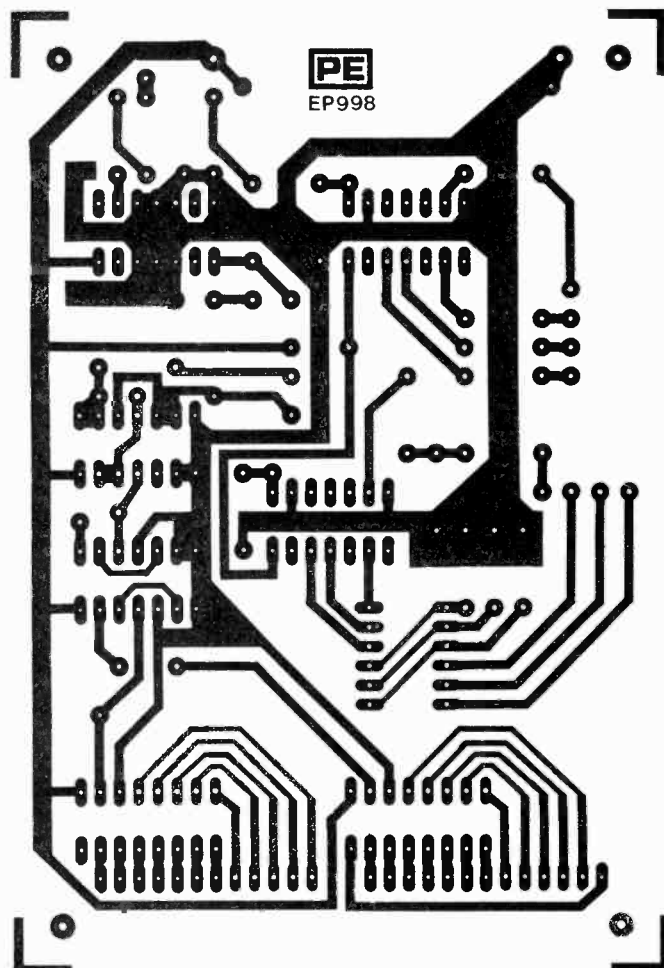


Fig. 7. Stylochord p.c.b. (actual size)

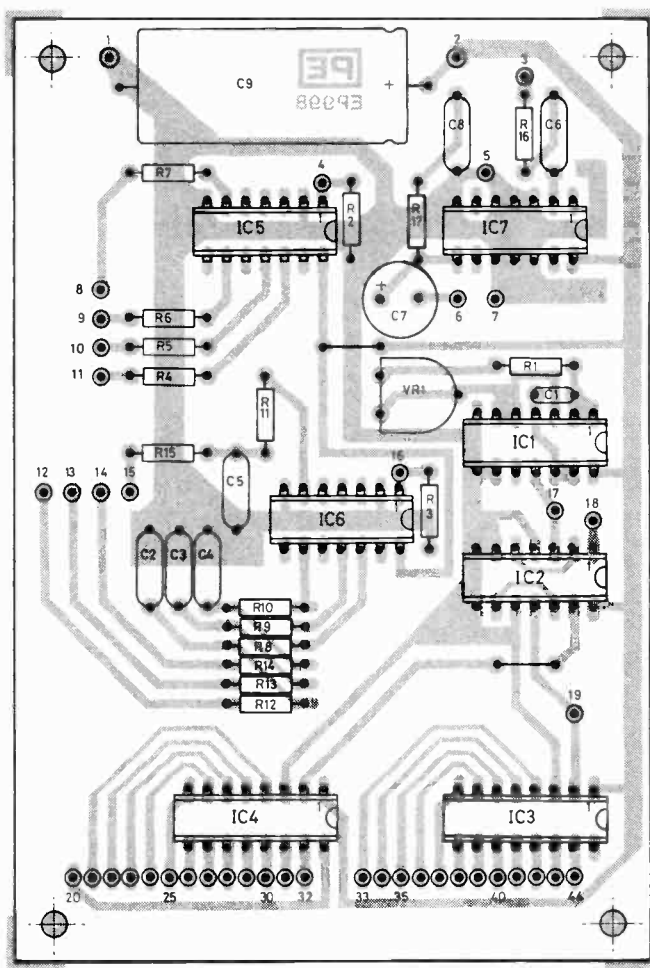


Fig. 8. Stylochord component layout

COMPONENTS . . .

Resistors

R1	2k2
R2, R3	100k (2 off)
R4, R7	330k (2 off)
R5	270k
R6	220k
R8	3k9
R9	4k7
R10	6k8
R11	8k2
R12,13,15	68k (3 off)
R14	47k
R18	680Ω
R16	10k
R17	2.7 Ohm (see text)

Capacitors

C1	47p ceramic
C2-C6	100n polyester (5 off)
C7	220μ elect.
C8	100n poly (see text)
C9	330μ elect 16V
C10	1000μ elect. 25V
C11	220n polyester
C12	10μ elect. 16V

Potentiometers

VR1	10k min horiz
VR2	5k log

Integrated Circuits

IC1	4011
IC2	4013
IC3,4	5024 (S50240 Tandy) (2 off)
IC5, 6	4024 (2 off)
IC7	LM380
IC8	7812

Miscellaneous

8 Ohm loudspeaker
 0-12, 0-12V transformer (RS 196-303 for example)
 Bridge rectifier (e.g. RS 262-141)
 2 probes
 6 off 2 pole *latching push-button* switches } SUE series
 8 way bracket, 15mm spacing } (AMBIT)
 6 knots 'A' (4 red, 2 black)
 L.e.d. + Holder
 Vero case (Order Code 75-1715G)
 D.p.d.t. toggle switch
 Knob
 20mm fuseholder and 500mA fuse
 P.c.b.s
 Ribbon cable
 Veropins, grommet, nuts and bolts etc.

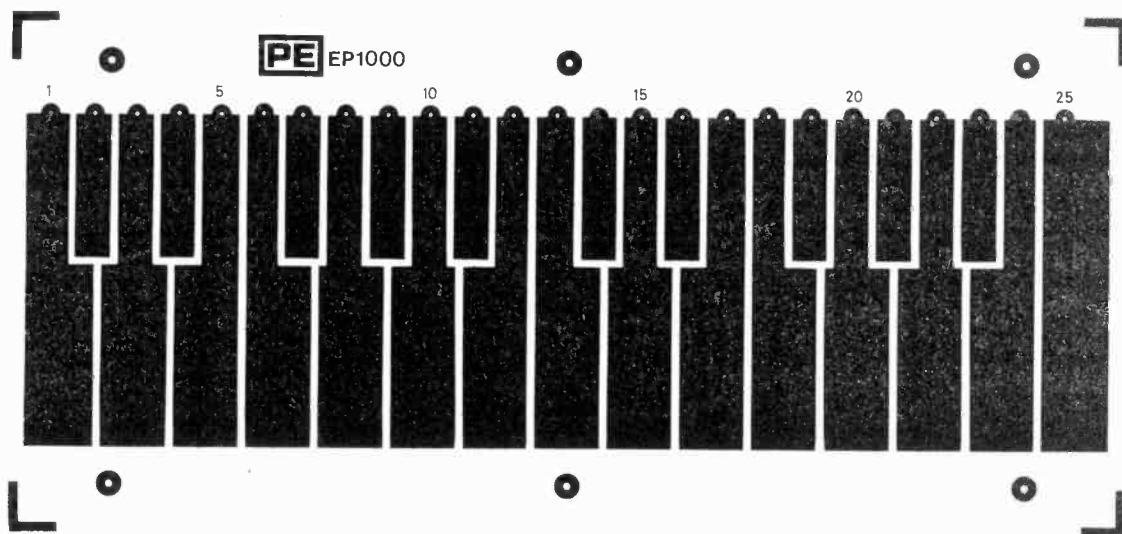


Fig. 9. Keyboard printed circuit

CONSTRUCTION

Readers are advised to use p.c.b.s, designs for which are given in Figs. 6 and 7, as this makes construction easier. There are quite a lot of interconnections to be made, and the prototype used ribbon cable, so that each wire is individually colour-coded and therefore easily traceable. Assemble the components, making sure that the i.c.s, diode, capacitors, and voltage regulator etc. are the correct way round. It is recommended that single-sided Veropins be used as solder terminals for all the wires.

The main p.c.b. and the power-supply p.c.b. are bolted to the base panel of the case, and the plastic housing is drilled to accept the cable retention grommet, fuseholder, speaker holes, switches, l.e.d., pot and probe sockets, see drilling details in Fig. 10.

The aluminium panel for the keyboard is cut and the keyboard mounted behind this with small spacers, nuts and bolts. The smaller aluminium panel is drilled to accept the switch bank. These switch modules are much cheaper than miniatures toggle switches, and the finished result looks extremely professional. Slot them into the 8-way bracket (positions 2 and 7 are left blank), bend the small tabs over to retain them, and then mount the unit behind the panel.

Make all wire interconnections (except those connecting the power supply to the main p.c.b.), taking care, as there are a number of them. See Fig. 11. Shielded audio lead was used where necessary, to avoid hum pick-up, and the case of the pot was earthed. When a final check has been made, turn on the mains and check that 12V is delivered by the regulator, and if so, turn off, connect up the two p.c.b.s

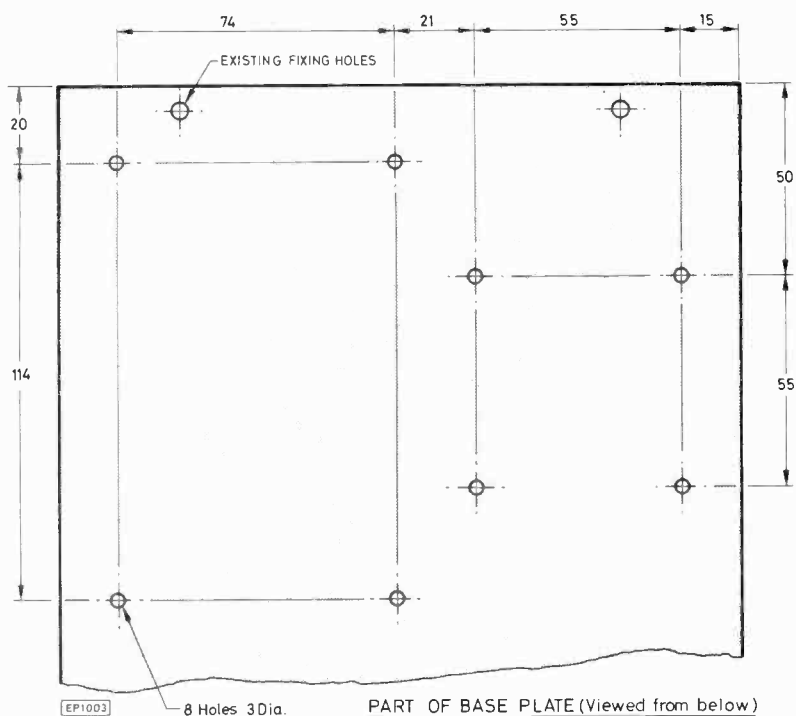


Fig. 10(a). Base plate drilling details

Fig. 10(b). Switch fascia drilling details

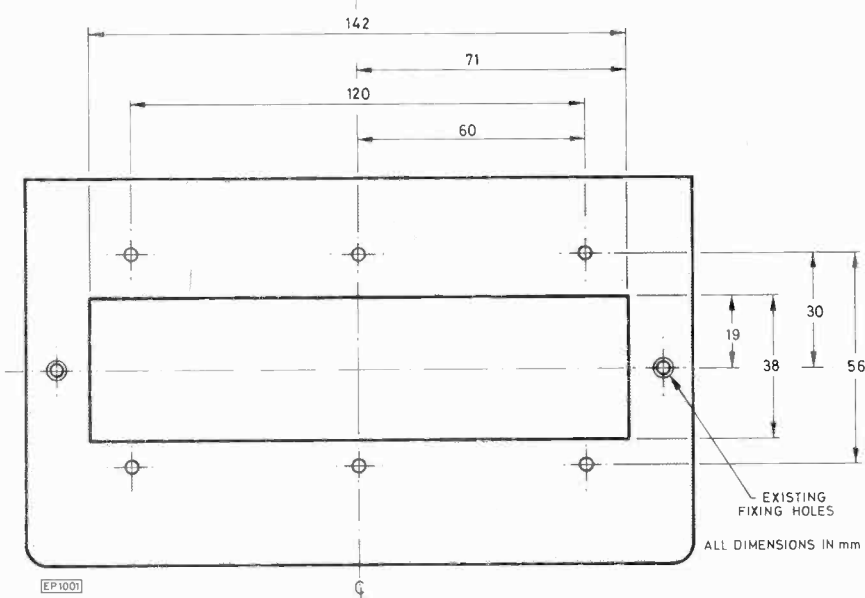
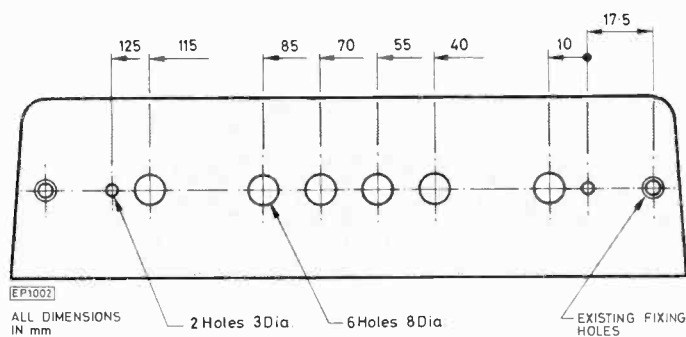


Fig. 10(c). Keyboard bezel details


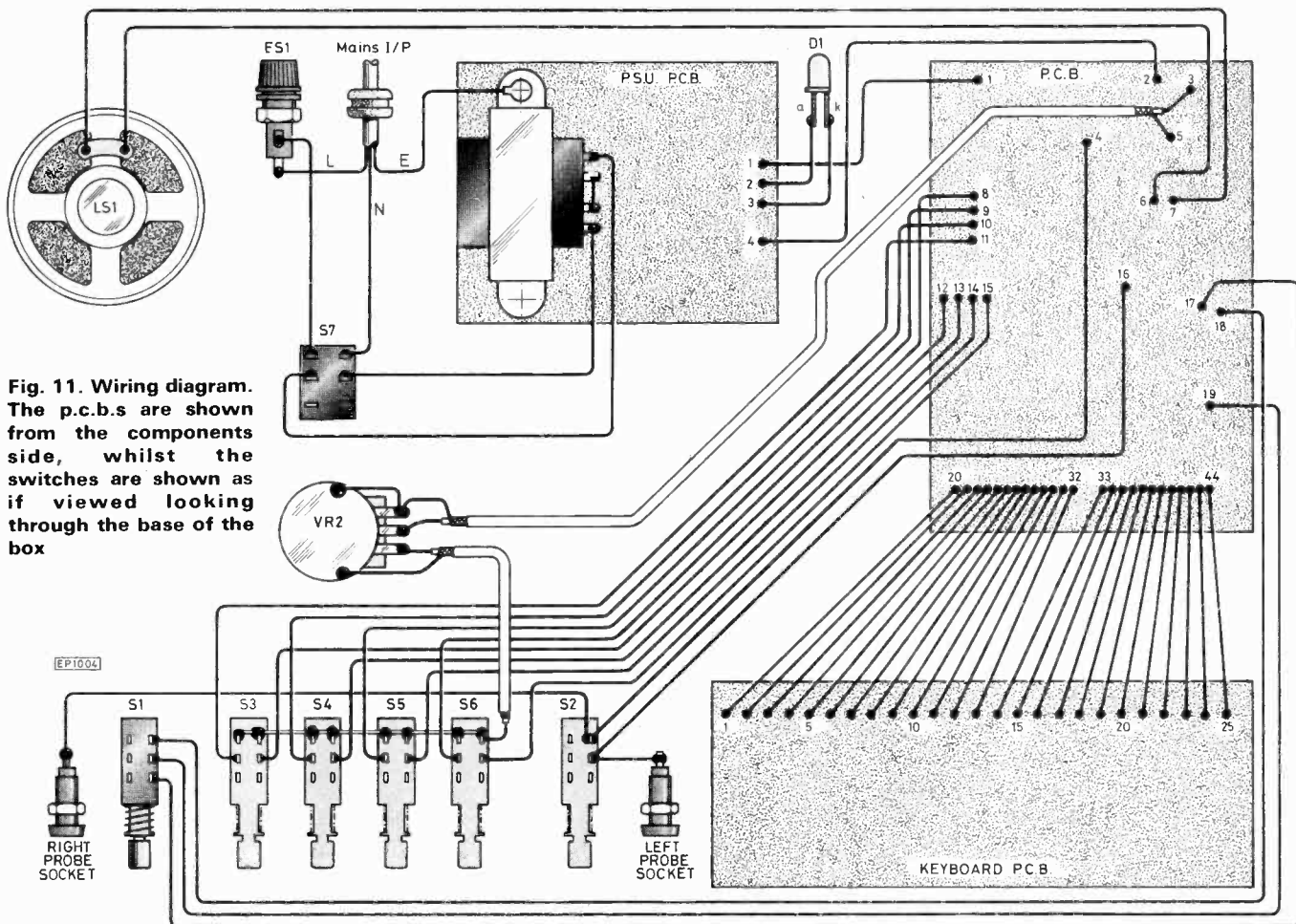


Fig. 11. Wiring diagram. The p.c.b.s are shown from the components side, whilst the switches are shown as if viewed looking through the base of the box

and turn on once more. Adjust the preset VR1 to tune the whole instrument up or down as necessary, and if all is well, bolt the unit together. You are now ready to start playing. If the probe switch is closed you cannot use both probes as you will try to put two different frequencies into ICs 5 and 6. A nasty sound will result!

CONCLUSION

The author has a prejudice against the vibrato effect, and so did not include one, but readers who are adventurous enough will find scope for development in this instrument, such as adding a phaser or a delay unit. However, the unit as described should give many hours of enjoyment, with various combinations of voices and stylis being possible. For greater variety, switches S3-S6 can be separated 'a' and 'b' to give e.g. 16' square with 2' triangular ... a *pig-and-whistle* effect! ★

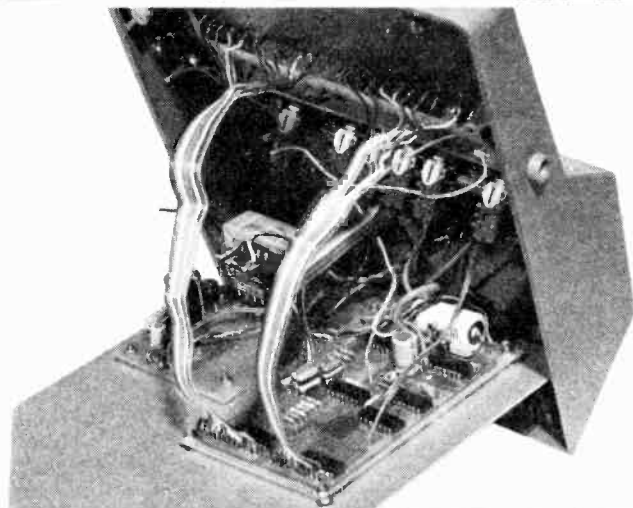

This coupon entitles the bearer to

£2 OFF

the price of a Hi-Style Desk Top Case as featured in Practical Electronics **STYLOCHORD** project. This coupon is valid until 31st December 1982

To the Retailer:—

Please accept the above coupon against the purchase of the stated case only. Send your vouchers to BICC-Vero Electronics as part payment of your monthly account, valid until 31st January 1983

New developments in UK Robotics


ADVANCED DESIGNS FOR EDUCATION, INDUSTRY AND THE HOME CONSTRUCTOR

Robotic experience is becoming as essential a subject as computing. MICROGRASP provides the lowest cost means of acquiring that experience but despite its ultra low price the robot has considerable versatility. There are 5 axes each using a servo motor and there is feedback from each of the arm movements. Control is by any computer with an expansion bus – the ZX81 being particularly suitable. Servoing is achieved with hardware on the interface board to keep programming simple and the robot is operated under BASIC commands with no computer-specific software required. The interface board is memory mapped using only 64 bytes at any of 1024 switch selectable locations.

MICROGRASP robot kit with power supply	£125.00
Universal computer interface board kit	£48.50
23 way edge connector	£2.50
ZX81 peripheral/RAM Pack splitter board	£3.00


HEBOT II is a turtle-type robot which takes programming out of the two dimensional world of the VDU into the real three dimensional world. Given a DC supply of 9-15V it can perform a bewildering number of moves under computer control – forwards, backwards, left and right – with each wheel independently controlled. It has blinking eyes, beeps with a choice of two tones and has a solenoid operated pen to chart its progress. Touch sensors coupled to its shell return data, about its environment, to the computer for it to calculate evasive or exploratory action. Hebot II connects directly to an I/O port or alternatively with the universal interface board to the expansion bus of a ZX81 or other computer.

Hebot II kit	£75.00
Universal computer interface board	£10.00
23 way edge connector	£2.50
ZX81 peripheral/RAM Pack splitter board	£3.00

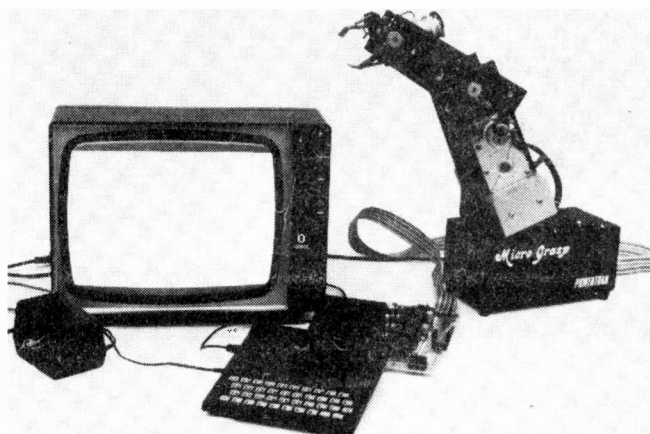


MICROGRASP, INTERFACE BOARD AND ZX81

'HIGH-TECH' FROM HANTS . . .

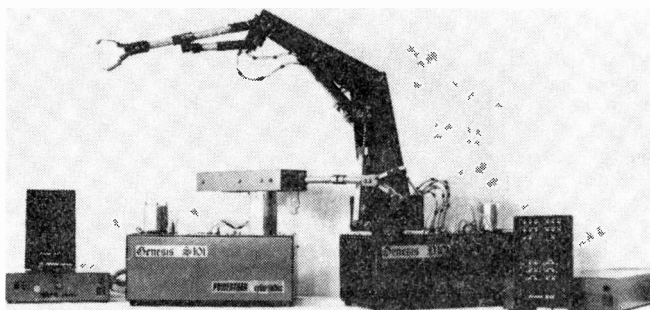

GENESIS S101 AND GENESIS P101 WITH PROCESSOR BOXES AND HAND-HELD CONTROLLERS

With prices starting below £1,000 the Genesis range of general purpose robots provide a first rate introduction to robotics for both education and industry. Each has a self-contained hydraulic power source, which enables loads of several pounds to be smoothly handled. The system operates from a single phase 240 or 120V AC supply or a 12V DC supply. The machine can be supplied with up to 6 axes each of which is fully independent but capable of simultaneous operation. Position control is achieved by means of a closed-loop feedback system based around a dedicated microprocessor. Movement sequences can be entered, stored and replayed by use of a hand held controller, alternatively the systems can also be interfaced to an external computer via a standard RS 232C link.

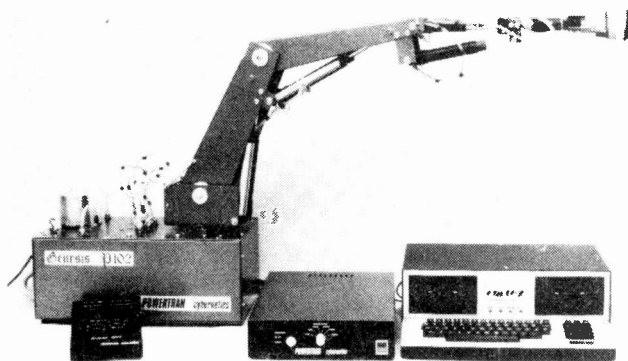

GENESIS P102 PROCESSOR BOX, HAND HELD CONTROLLER AND CORTEX COMPUTER

Top of the range is the Genesis P102 which has dual speed control, continuous servo operation and double acting cylinders for increased torque on the wrist and arm rotation joints. The microprocessor based control system has additional memory, position interrogation via the RS232C interface increasing the versatility of computer control and inputs are provided for machine tool interfacing.

6 axis system READY BUILT	£1950.00
Powertran CORTEX 16 bit 64K computer Kit	£295.00;
READY BUILT £395.00	
(Electronics Today International December issue on CORTEX)	

Example prices and specifications

Genesis S101

Base: 19.5" x 11" x 7.5"
Lifting capacity: 1500gm
Arm lift: 6.6"
Weight: 29Kg

4 axis model in kit form £390
5 axis model in kit form £445
5 axis model READY BUILT £790

Genesis P101

Base: 19.5" x 11" x 7.5"
Lifting capacity: 2000gm
Arm lengths between axes: 14.0"
Weight: 34Kg

4 axis model in kit form £495
6 axis model in kit form £595
6 axis model READY BUILT £950

COMPLETE SYSTEMS AS SHOWN IN PHOTOGRAPH ABOVE

Genesis S101

4 axis system in kit form £635.50
5 axis system in kit form £695.00
5 axis system READY BUILT £1355.00

Genesis P101


4 axis system in kit form £742.00
6 axis system in kit form £852.00
6 axis system READY BUILT £1525.00

As featured in this journal November '81–April '82 issues.

ALL PRICES EXCLUSIVE OF VAT

PORTWAY INDUSTRIAL ESTATE, ANDOVER, HANTS SP10 3WN
Telephone: ANDOVER (0264) 64455

POWERTRAN
cybernetics

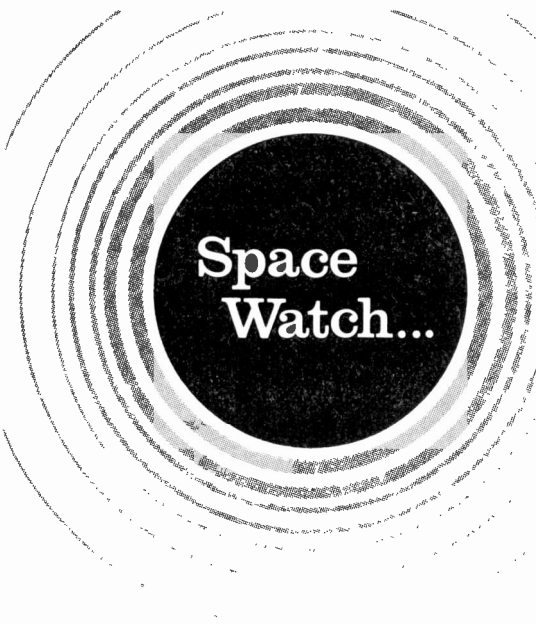

Space Watch...

ASTRONOMICAL OBSERVATIONS BY REMOTE CONTROL

Astronomers of the Royal Observatory of Edinburgh have achieved a technological superiority by remotely controlling the UKIRT (United Kingdom Infra Red Telescope) on the 14,000ft. high peak of Mauna Kea, Hawaii, from a computer terminal in Edinburgh. This experiment will lead to improved flexibility in the use of major astronomical facilities.

When this project was in its early stages there was great concern about the high cost of the movement of personnel to attain the best advantage from the site. Not only is it the best site from the reason of *seeing* but it has special advantages because of its height above sea level. The disadvantages lay in the cost of personnel movement, the difficulty of working at the height, even after long acclimatisation for any length of time and the limited hours that could be devoted to observations. Now this problem is solved and not only will personnel benefit but far more time will be available for the operation of UKIRT. For example all operations can be carried out from sea level and it will be possible to operate the telescope from Edinburgh during normal office hours for night time activities in Hawaii. The reason for this is, that the observers will be able to operate from any terminal connected to the SERC computer network, including all users of the STARLINK network.

Other advantages are that when unusual weather is prevailing the special observations, which can only be made at these times, may be undertaken. All this is now possible at a cost of normal leased lines and networks. Once again necessity provides not only the solution but also the expertise. It is perhaps worth noting that no longer can the cry of no money for essentials be raised. The remote control facility provides two levels of operation at the 1.8 metre UKIRT site. Almost all the operations that can be carried out at the Hilo laboratory in Hawaii including television reception are already available to the remote user via a 2-channel 9600bit/sec lines to the

telescope. This facility is expected to be in use for extensive observations at the longer infra-red wavelengths and also sub-millimetre wavelengths during daytime hours. The second level of operation, pioneered by the first breakthrough of this system, is a 1200 bit/sec intercontinental link to any United Kingdom astronomer with a terminal of the SERC computer network SERCNET.

For the purpose of the first experimental observations the terminal was linked via the GEC 4090 computer at the Royal Observatory in Edinburgh to the Regional centre then via SERCNET to the Rutherford Appleton Laboratory in Oxfordshire. Thence by the British Telecom PSS (Packet Switching Service) to the IPSS (international Packet Switching Service) through a transatlantic common carrier by TELENET. The nearest node centre of TELENET is at Honolulu. From there to the Hilo Laboratory of UKIRT by leased telephone lines. Though this sounds a little complicated the delay is only between 3 and 6 secs. This did not prove to be a difficulty in the first experiment. The entire communications during the preparation times were quite good according to the staff astronomers at Hilo, David Beattie and Dr. Ian Gatley. A significant point to be made here is that the total cost was some £80. The establishment of the remote facility had been achieved through the work of Peter Thanisch and Dr. Peredur Williams under the direction of Dr. Terry Lee in Hawaii, B. McNally at the Royal Observatory Edinburgh and Dr. P. Bryant at the Rutherford and Appleton Laboratory.

The Historic experiment took place on the 6th September this year when Malcolm Stewart secured an infrared photometric measurement and a spectrophotometric scan of the star HR 8824.

ARIANE

Following the great hopes, the Ariane launcher has again failed. There has now arisen a situation that the Insurance companies must face with current claims against losses having already reached very high figures. This is another of those hiccups which are usually very firmly pushed into the background. Such a long record of failure has dogged this enterprise that it is not easy to continue to hope for success. Is there perhaps a lesson to be learned from the history of the whole project? Are such questions as "is it wise to adopt the composite philosophy for the motors of a launcher" justified?

From an observer's point of view this seems pertinent enough, yet is it perhaps unfair to speculate without a great deal more first hand information. This is not just "one of those things", too many things seem to happen to this project. It suggests that there are areas of incompatibility. Is it concerned with the materials or components. Are there different standards under the same specification. Is the real cause satisfactorily diagnosed. This raises many other questions also. Is the launching site viable. It would seem timely to begin some horizontal thinking. If as was stated, the vehicle was fully qualified at what stage did the onset of failure occur?

Other failures are also continuing in other places and if Insurer's raise the premiums or the operators under-insure then developing industries may fail. What of the computer

modelling. How much of such technology has been applied. Many fantastic claims for such steps have been made especially *after* the events. Why not fund one of the claimants that continually pour out pamphlets, set up seminars at high cost and show little in practice. Is there too little hard practical engineering skill being applied. It is easy to cry wolf. This is true but perhaps such an emotional approach may inspire a defence.

TWENTY FIVE YEARS OF SPACE ACTIVITIES

For twenty-three years of this period the United States has made successful launchings of 44 vehicles for communications, weather and navigational activities. In addition there have been some 62 launches of a similar nature under International agreements. These particular satellites by the use of microwave techniques are able to function by line of sight since neither the atmosphere nor the curvature of the Earth are obstacles. Moving in straight lines, the signals can be acquired by earth based stations and passed on, or linked with other satellites. The now famous early suggestions by Arthur C. Clarke, made in the early forties and which earned him the universal credit for the invention of satellite communication systems, have become an active reality.

The most economic distance for profitable use, both technically and financially, is between 800 and 1,000 kilometres. The famous *Early Bird* was launched in 1965 and was the first of the communications satellites. *Early Bird* now renamed Intelsat 1, had a capacity for 240 channels of data or telephone and also had one television channel. The satellite had a life of three years and weighed 60 kilogrammes. Twenty five satellites later the Intelsat series 5 was launched in December 1980 and weighs 1,870 kilogrammes. Its life will be seven years and has 12,000 voice circuits and two television channels. Intelsat has 106 member countries and provides communications services to more than 150 countries.

The regulations of the United States Government prohibit the use of domestic satellites for overseas communications. All overseas communications in the Comsat network have to use the Intelsat network for the overseas link. It is getting crowded now and serious attention is being given to the difficulty which is a matter of rearranging the separation distances. This will be one of the subjects of the next issue of SPACEWATCH.

INDIA & SPACE

Russia has been assisting India to design and launch satellites for scientific studies including remote sensing and communications. During the late Yuri Gagarin's visit to India, soon after his epic mission, India determined she would have a cosmonaut. Nothing was done about it though it was discussed at a meeting in Moscow in 1978 with Moraji Desai, the Prime Minister of India at the time. Now some 8 Indian pilots are queuing for a cosmonaut assignment.

Frank W. Hyde

MICROGRASP was designed to be priced at under £200 inclusive of power supply, computer interface board and even VAT! However, despite that restriction, it has some very powerful features. Driven by a simple computer, the ZX81 being eminently suitable, Micrograsp has an articulated arm jointed at shoulder, elbow and wrist positions. The entire arm rotates about the base and there is a motor-driven gripper. Each of the arm movements is servo controlled i.e. there are position sensors feeding back information to the interface board, where it is compared with the programmed-in intended position, and automatically taking corrective action. This servo action is independent of the computer, greatly simplifying the software to drive the robot and all programming is carried out with a small number of Basic commands.

MECHANICAL OPERATION

For each of the five axes there is a motor with integral gearbox. For the wrist and gripper motors small in-line gearboxes are used. The other axes use more powerful gearboxes in heavy duty zinc alloy castings. The shoulder and elbow joints are driven directly from the motors gearboxes with both motors mounted on the lower arm (Fig. 1). On the upper arm and the shoulder support bracket are steel bushes clamping the gearbox shaft so that when the motors are driven there is relative movement between the lower arm and the upper arm and the support bracket.


Also on the lower arm are the position sensing potentiometers. On the bushes of these are plastic bushes on which the arm rotates. The shaft of each potentiometer is held in the steel bush fitted to the upper arm or support bracket.

For rotating the arm (axis 0) it is not possible to have the gear box shaft, the potentiometer and the shoulder support bracket all in line so the power is taken from the gearbox (Fig. 2) by a pair of spur gears which being of 2:1 ratio result in a doubling of torque. For this axis the gearbox shaft is taken out from the motor side of the gearbox.

For raising and lowering the wrist (axis 3) the gearbox shaft rotates a bar to which the potentiometer shaft and gripper mounting plate are fitted (Fig. 3). Through this bar the drive shaft for the gripper lead screw passes. When the

The Genesis range of robots published in these pages last winter have most effectively filled their role of providing a low cost introduction to robotics. Although their price is well within the budgets of further education establishments, industrial production and research and development departments; state run schools and home constructors have found it more of a struggle to raise the funds. In order to provide them with hands-on-experience of robotics we have created the ultra low cost Micrograsp.

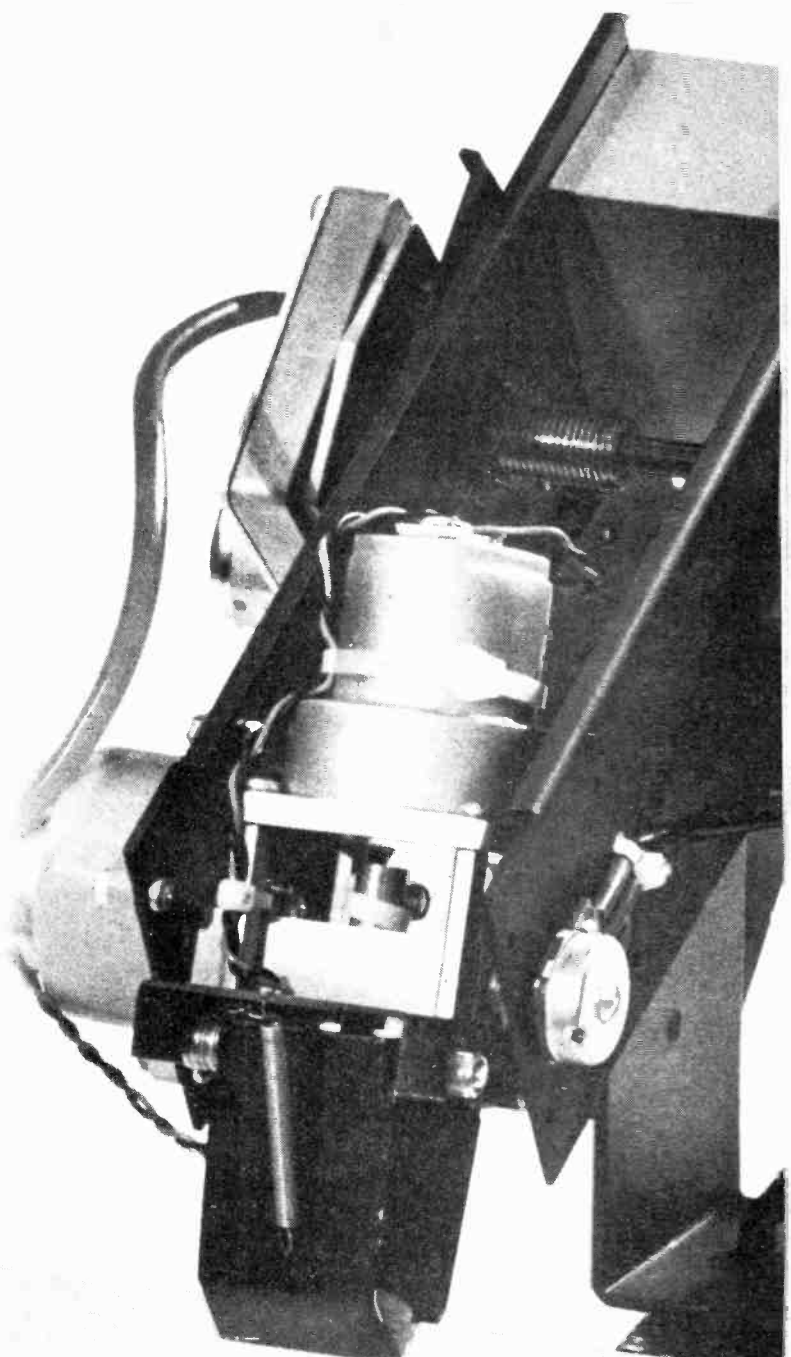At the same time further development of the Genesis P101 has resulted in P102, a higher performance version.



PE
MICROGRASP
PART 1
RICHARD BECKER

screw turns clockwise the disc nut is moved in pulling the jaws together (Fig. 4). On turning anticlockwise the disc nut moves out and the springs pull the jaws apart.

The arms for the robot each have counterbalance weights so that no voltage needs to be applied to the motors to hold the arm in the desired position. This improves the accuracy of the servoing. Without balancing an error signal would

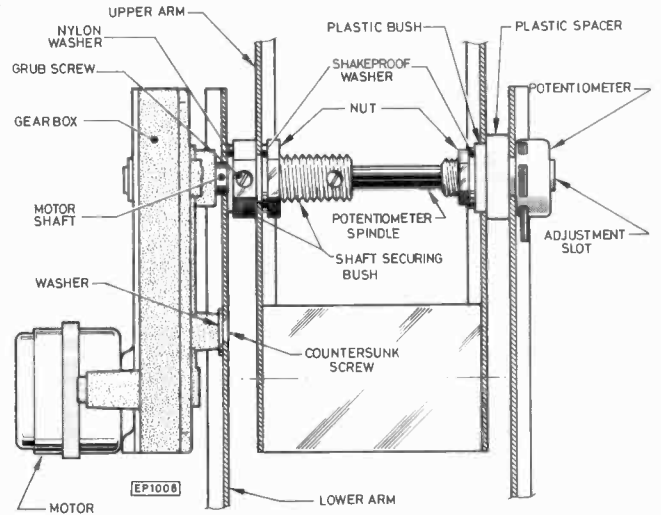


Fig. 1 Linkage between the motor, arms and potentiometer for axis 2 movement. Axis 1 operation is similar

(Left) Showing central position of the above linkage assembly

(Below) Interior of robot base showing Fig. 2 linkage and power supply

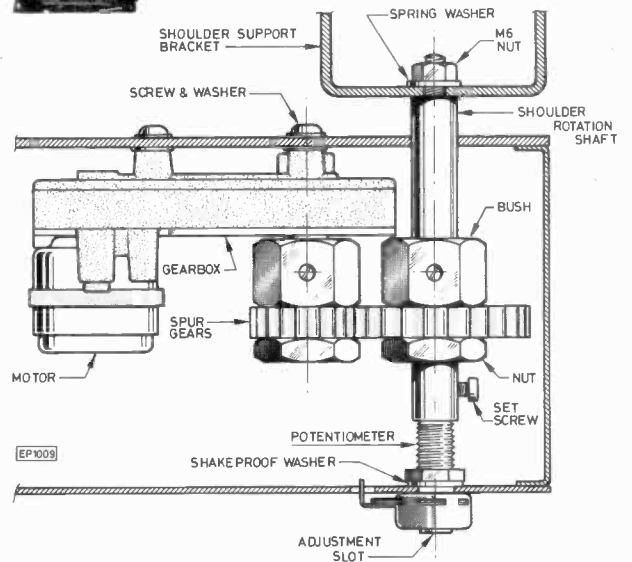
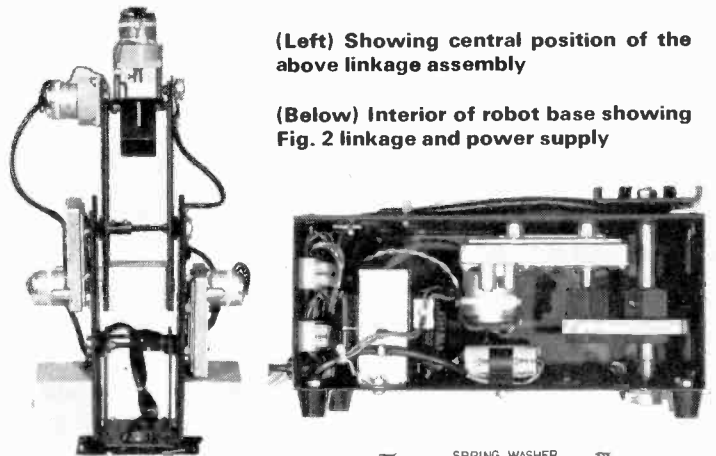


Fig. 2 Linkage between motor, spur gears, shoulder support bracket and potentiometer for axis 0 movement

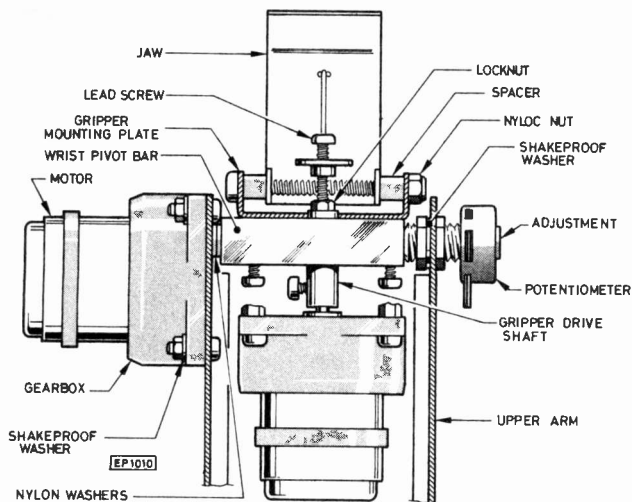


Fig. 3 Linkage between motor, gripper mounting bar and potentiometer for axis 3 movement

always be required for the arm to be motionless and a considerable torque would also have to be provided by the gearboxes causing an undue strain upon them.

CIRCUIT OPERATION

The interface board is designed to operate as a memory mapped peripheral of the controlling computer which generates the positional and manipulative commands whilst servoing is taken care of by linear circuitry on the interface board greatly simplifying the work of the computer and avoiding the requirement for extensive software specific to each type of machine. Some computers have I/O ports by which data could be sent to the robot, however the commonest and cheapest computer on the market, the ZX81 does not have this facility. It does however have an expansion bus giving access to all the address, data and control lines. Virtually all other micro computers also have this facility making practical a universal interface. The signals required are the address bus, data bus, Write and Mem REQuest. The connector format choice could have been arbitrary but in view of the particular cost effective suitability of the ZX81 the layout of that machine was selected and by using two back-to-back 23 way double sided connectors, a very neat connection with no wires can be made.

For any other computer a 23 way connector would be wired to one of the type recommended by that computers

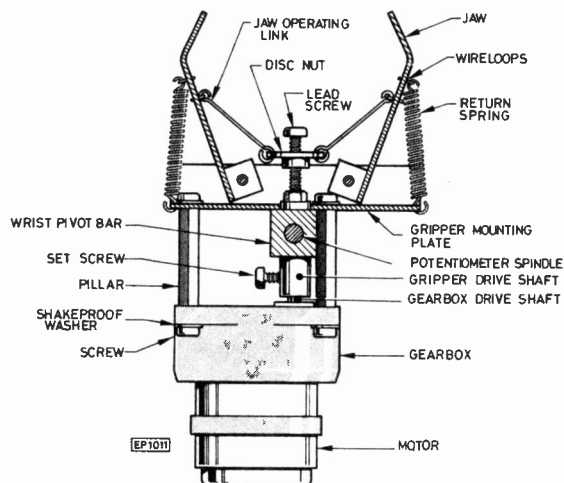


Fig. 4 Operating mechanism for the gripper

manufacturer. Using back-to-back connectors does however prevent the use of the 16K RAM pack limiting program length to about 30-60 lines. This restriction is avoided by use of the three way adaptor p.c.b. (Fig. 5) whereby the RAM pack lies neatly on top of the computer.

By setting the ten bank DIL switch (Fig. 6) any one of 1024 blocks of 64 bytes of the memory area can be selected. Actually only six bytes are required but to narrow down the memory area used would call for extra circuitry and with memory costs per byte of around 0.15p or less such extra complexity is pointless. IC2 is a ten bit comparator. The ten most significant address lines are compared with the +5V or 0V levels set up by the switch and when there is a match, i.e. when the computer selects an address within the 64 byte block, pin 13 goes high. The three least significant address lines are connected to IC3, a three into eight decoder, to select which axis is to be given a fresh command.

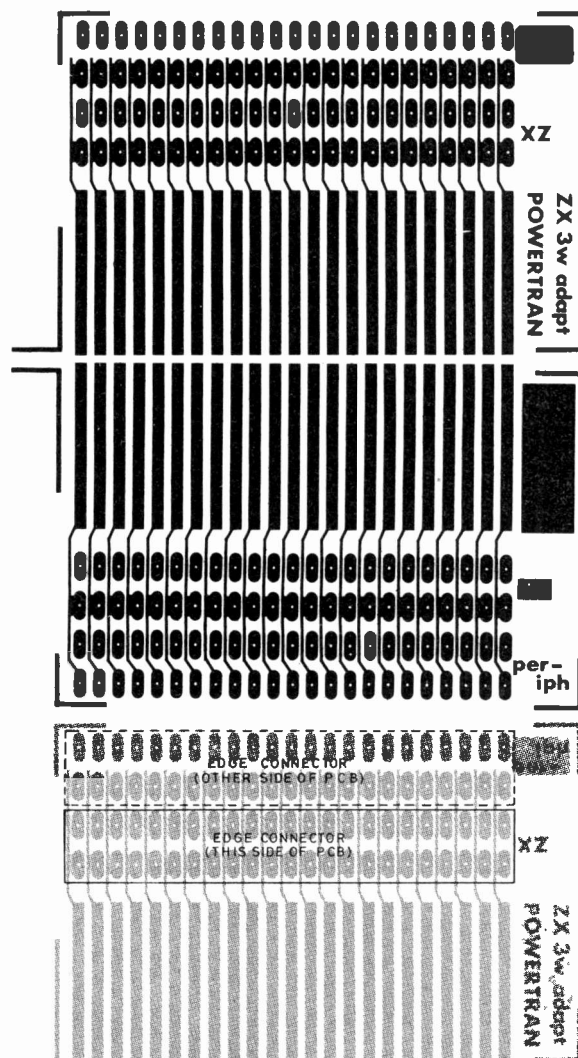


Fig. 5 Printed circuit of three way adaptor

The output of the decoder is enabled only when WR and MREQ are low and IC2 pin 13 is high i.e. when the computer is addressing the chosen axis as if it were a memory location into which data is to be written. For example if the top of the address space is to be used all the switches would be set to be open therefore addresses 65472-65535 are allocated to the robot. To move the rotation axis (servo circuit A) to the centre position the command would be POKE 65472, 128. 128 being the centre of the range of positions defined as 0

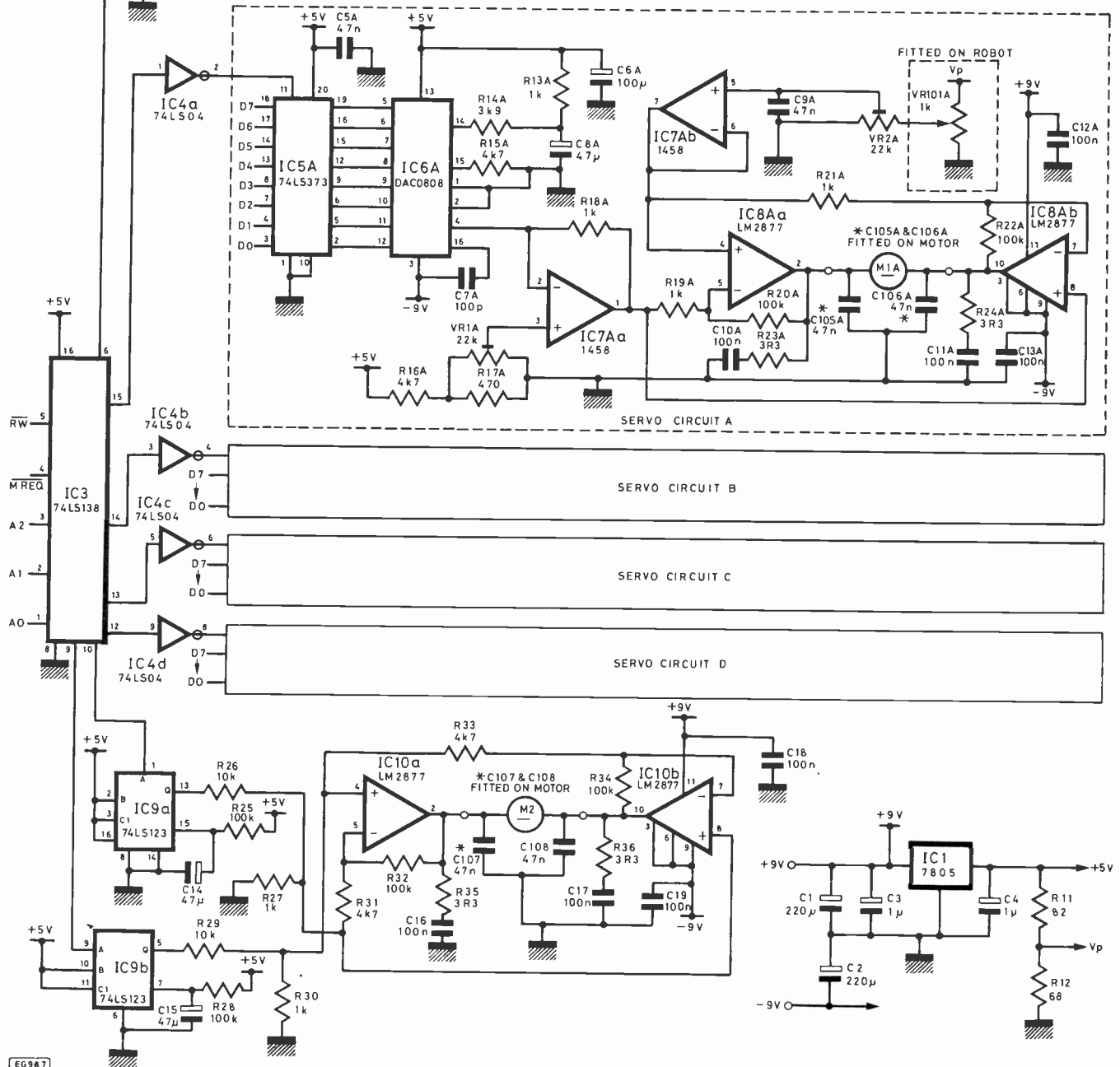
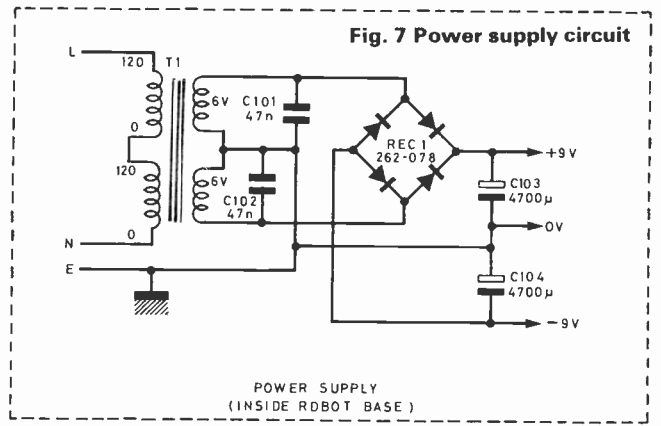
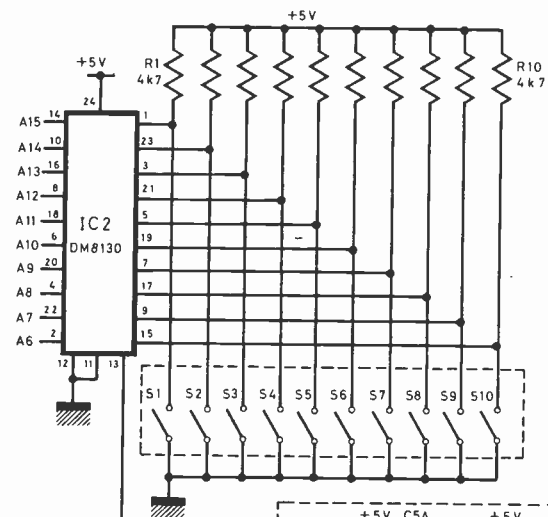


Fig. 6 Circuit of computer interface

COMPONENTS

INTERFACE BOARD

Resistors

R1, R2, R15A-D, R16A-D, } R31, R33	4k7 (12 off)
R3-10	4k7 SIL network
R11	82R
R12	68R
R13A-D, R18A-D, R19A-D, } R21A-D, R27, R30	1k (18 off)
R14A-D	3k9 (4 off)
R17A-D	470R (4 off)
R20A-D, R22A-D, R25, R28, } R32, R34	100k (12 off)
R23A-D, R24A-D, R35, R36	3R3 (10 off)
R26, R29	10k (2 off)

Potentiometers

VR1A-D, VR2A-D	22k preset (8 off)
----------------	--------------------

Capacitors

C1, 2	220µ/16V vertical electrolytic (2 off)
C3, 4	1µ/16V tantalum (2 off)
C5A-D	47n ceramic (4 off)
C6A-D	100µ/10V vertical electrolytic (4 off)
C7A-D	100p ceramic (4 off)
C8A-D	47µ/10V vertical electrolytic (4 off)
C9A-D	47n polyester (4 off)
C10A-D, C11A-D, } C12A-D, C13A-D, }	100n polyester (20 off)
C16-19	
C14, C15	47µ/6V3 tantalum (2 off)

Integrated Circuits

IC1	7805
IC2	DM8130
IC3	74LS138
IC4	74LS04
IC5A-D	74LS373 (4 off)
IC6A-D	DAC0808 (4 off)
IC7A-D	1458 (4 off)
IC8A-D, IC10	LM2877 (5 off)
IC9	74LS123

Miscellaneous

Printed circuit board	
S1-S10-SPST 10 bank DIL switch	
TV5 heatsink	
8 pin i.c. socket (4 off)	
14 pin i.c. socket	
16 pin i.c. socket (6 off)	
20 pin i.c. socket (4 off)	
24 pin i.c. socket	

ROBOT

Capacitors

C101, C102, C105A-D, } C106A-D, C107, C108 }	47n ceramic (12 off)
C103, C104	4700µ/16V horizontal electrolytic (2 off)

Diodes

REC1	6A rectifier block
------	--------------------

Transformer

T1	0-120V, 0-120V primary 6-0-6V at 4A secondary
----	--

Potentiometers

VR101A-D	1k linear
----------	-----------

Miscellaneous

Motors, mechanical parts, fixings etc.
A kit of parts is available from—

**Powertran Cybernetics,
Portway Industrial Estate,
Andover,**

Hants, SP10 3NN £125—Robot plus 15% VAT
£48.50—Interface plus 15% VAT.

to 255. Because of the redundancy in address selection 65480, 65488, 65496, 65504, 65512, 65520 and 65528 would be equally effective addresses.

The decoder enables IC4 which is an eight bit wide data latch which holds the data indefinitely after the writing-in process is completed. The data is converted into a d.c. level in the range 0V to 1V by IC6 which is a digital-to-analog converter and IC7a converts the current output of the DAC into a voltage, the feedback resistor R18 giving it a gain of 1 volt/ma. IC7a is also used to add in an offset voltage to balance out the residual voltage from VR101 when the axis is at its zero code position i.e. lowest or furthest left position. The position of the axis is sensed by VR101 to which is applied about 2V derived from the 5V rail via R11, R12. 1V corresponds to the position in the centre of the travel of that axis. VR2 is used in setting the range of movement and IC7b is a unity gain buffer enabling the low (1k) input impedance of the power amplifier stage to be driven without loading VR101 significantly.

IC8 performs two functions simultaneously. It compares the measured position of the axis with the programmed-in desired position and serves as a bridge output power amplifier to drive the motor either backwards or forwards with a voltage dependent on how far away from the desired position the axis has reached. To see how the circuit operates,



Micrograsp with computer interface board, RAM pack and adaptor

first we consider the half with pins 7, 8, 10. The desired position voltage (DPV) is applied to pin 8, feedback via R22 makes pin 7 a virtual earth point elevated above ground by the voltage on pin 8. The measured position voltage (MPV) forces a current into this point via R21 resulting a voltage at pin 10 which is $R22(DPV-MPV)/R21$ i.e. pin 10 will go positive when MPV is less than DPV.

The other half of the i.c. behaves similarly except that pin 2 will go negative when MPV is less than DPV. As the circuit is symmetrical the voltage applied to the motor is therefore twice $R22(DPV-MPV)/R21$. The components selected resulting in a servo action which is close to critically damped.

R23 + C10 and R24 + C11 are the Zobel networks used almost universally to stop power amplifiers becoming power oscillators in the MHz region.

Capacitors C12, C13 are for local decoupling to also assist in ensuring stability and C105, C106 are suppression capacitors fitted as close as possible to the motor. Without these the interference from the motor brushes is sufficient to make the computer abort its program. Only four of the five axes are servo controlled as the gripper needs only to be either holding or releasing.

The gripper is activated by a motor turning a lead screw which then pulls together the jaws. To hold an object IC9a is triggered in a manner similar to the enabling of the data

latches. This monostable then provides a signal for about 2 seconds, as determined by R25, C14, which causes IC10 to apply a voltage to the motor to pull in the jaws. When an object is seized the motor will stall but the amplifier is fully protected and as the stall period is less than 2 seconds no overheating occurs. On triggering IC9b the motor is driven the opposite way until it stalls at the jaws fully open position. Gripper operating commands could be POKE 65477,0 to hold and POKE 65478,0 to release, though this data as indicated by 0 is quite irrelevant and anything between 0 and 255 could be written. If the address allocated to axis 0 (servo circuit A) is A then axis 1 is A + 1, axis 2 is A + 2, axis 3 is A + 3, hold is A + 5 and release is A + 6.

The rotation shoulder and elbow motors take up to about 1A each and the other two motors up to about 0.5A each. The reference voltage for the DAC and the position sensing potentiometers comes from IC1 which provides excellent stability. The amplifiers requirements however are non-critical and an unbalanced supply is entirely adequate. The circuit shown (Fig. 7) provides $\pm$ approximately 9V. The supply is sited in the robot base where, as well as providing useful ballast at the rear of the base the mains connections are fully enclosed. The interface board is therefore free of mains and is safely operated whilst unenclosed and closely connected to the computer.

Next Month: Assembly, testing and calibration

FREE! READERS' ADVERTISEMENT SERVICE

PE BAZAAR

RULES Maximum of 16 words plus address and/or phone no. Private advertisers only (trade or business ads. can be placed in our classified columns). Items related to electronics only. No computer software. PE cannot accept responsibility for the accuracy of ads. or for any transaction arising between readers as a result of a free ad. We reserve the right to refuse advertisements. Each ad. must be accompanied by a cut out valid 'date corner'. Ads. will not appear (or be returned) if these rules are broken.

VALVES, unused assortment. Details Oxford (0865) 779855. Mr. G. Dean, 66 Fern Hill Road, Oxford.

ZX81 16K, Micro Gen. Joysticks, two books and software. Best offer taken. Tel: 01-556 5994. Michel Nair, 114 Richmond Road, Leytonstone, London E11.

2 x 61 NOTE keyboards or the whole PV valued organ as is. W.H.Y. acceptable. A. Johnson, 1 Babbacombe Road, St. Yvechale, Coventry CV3 5PE.

WANTED: BF900, BF494, Chokes: 4.7mH (TOKO), 47mH. M. Ekbatani, 95 Nursery Road, Cheshire Hulme, Cheshire. Tel: 061 485 4493.

RADIO telephone Cambridge Boot Cambridge Dash Mount £25 each Vanguard No control unit £10. Edwards, 2 Beach Road, Burton Bradstock, Bridport, Dorset DT6 4RF. Tel: 0308 89625.

POCKET computer—Sharp PC1211 with cassette interface and printer only £50. Phone: 01-876 6661.

COMMUNICATIONS Receiver, 2–20MHz, Ex R.A.P., calibrator, variable selectivity, 3kHz readout, mains p.s.u., R1475, working well, £48.

Tel: Cambridge 860150.

MULTIMETER with metal case £15 incl. postage. Tel: 01-554 2913 Evenings.

UK101 Mon 2. 8K, Marrick sound generator, software. Swap for PE string ensemble or similar. Tel: Newcastle 582449.

ZX80 Computer with leads transformer manual etc. £60 ono. Tel: Glyndwr 310 after 6p.m. Terry J. Bluck, 2 Maes Owain, Glyndyfrdwy, Nr. Corwen, Clwyd.

CB TRANSCEIVER, Commtron Nato CXX. £40 plus small straight forty rig or £85. Tel: 061 998 9109.

TANDBERG 3541X, Mint, unused, £90, SME FD200 Damper £12. Pair monitor audio 7.5m cable £12. Unopened. Tel: (07605) 402.

110V 1kW mains transformer with voltmeters/fully enclosed with sockets and carrying handle. Buyer collects. Offers. C. H. Kaufman, "Spring Grove", Sledgate Drive, Wickersley, S. Yorks S66 0AW. Tel: (0709) 548564.

CLEF Bandbox, fully complete working £265 o.n.o. Phone: 0233 812406. C. Maxwell, "Red Tiles", Brook, Ashford, Kent, TN25 5PG.

WANTED back issues Practical Electronics from June 1979—till July 81 any price paid. I. V. Olver, 11 Clarks Close, Deal, Kent CT14 9JE. Tel: 03045-64445.

VOLTAGE tester probe £5. Transistor checker £12. Signal injector £6. Tel: 01554 2913 Evenings.

2708 EPROM's, little used, erased, still some left at £1.50 each. First come first served! Newnham, 21 Welbeck Avenue, Ilkeston, Derbyshire, DE7 4NL. Tel: Ilkeston (0602) 304339.

32K DYNAMIC RAM board, suitable for PET, UK101 etc. £40. Also PE/Technomatic interface boards £40. S. Riddle, St. Marshalswick Lane, St. Albans, Herts AL1 4UT.

SELENIUM bridges, One 25A, One 12A, fifty ½A, sell or swap for any working oscilloscope tube. Mark Daniels. Tel: Leicester 823249 (After 5p.m.)

CRT-lin GEC E4103/B/4 + Data £5; Morse-key £2; two Army hand-telephones No. 2 £6; Variac non-working £2. D. L. Buckley, 142A Lynton Road, West Acton, London W3. Tel: 01-993 3123.

Please publish the following small ad. FREE in the next available issue. I am not a dealer in electronics or associated equipment. I have read the rules. I enclose a cut-out valid date corner.

Signature Date

Please read the **RULES** then write your advertisement here—one word to each box. Add your name, address and/or phone no.

COUPON VALID FOR POSTING BEFORE 10 DEC. 1982. (One month later for overseas readers.)

SEND TO: PE BAZAAR, PRACTICAL ELECTRONICS, WESTOVER HOUSE, WEST QUAY ROAD, POOLE, DORSET BH15 1JG.

BLOCK CAPITALS PLEASE

Name & Address:			

For readers who don't want to damage the issue send a photostat or a copy of the coupon (filled in of course) with a cut-out valid "date corner"

Ultimum Computer Interface

Part 2

THE ULTIMUM is a motherboard organised universal interface system, the bus of which is broad based enough to allow it to interface with almost any microcomputer. It can also evolve to become a computer in its own right.

THE 16/64K RAM CARD

The first card available for the ULTIMUM is a dynamic RAM card. It may be configured as a 16 or 64Kbyte card, dependent on the RAM i.c.s used.

Fig. 2.1 shows the circuit diagram. This is a rather unconventional design as it has to cater for both Z80 and 68/65xx busses which have very different timing requirements.

The dynamic RAMs have to be refreshed to preserve their contents, and this is done when the microprocessor is not reading or writing to the memory. This kind of refresh is called transparent as it does not affect the processor.

65/68 series microprocessors never address memory when their clock output is low (the Q1 cycle) so this time slot is used for refresh. The Z80 on the other hand, provides a refresh timing signal to indicate that the memory is not being accessed. The Z80 also provides other refresh signals but these are not used in this design.

The refresh involves sequencing through a series of consecutive addresses on the RAM address lines. IC13 has a built in counter which is incremented on each memory refresh cycle.

Because dynamic RAMs are in 16 pin packages, there are not enough lines to fully address them. Consequently some of the pins have to have addresses multiplexed into them. IC13 will do this for 16K memories, but additional circuitry is needed for the 64K RAMs and this is provided by IC16 and IC17.

ULTIMUM is the missing link between your computer and the outside world! Just take a look at the interface board line-up.

WE01 RAM

A 16/64K Byte dynamic RAM card (detailed in this article).

WE02 BRR

A ROM/Battery back-up RAM card for use with 2516/2716/2732 EPROMS and 6116 static memory chips. There are two sockets available for 6116 RAMS with battery back-up allowing up to 4K per card of RAM to be stored permanently when the system is switched off.

WE03 PRG

An EPROM programmer designed for use in conjunction with the EPROM card above. This has hardware timers and EEPROM facilities.

WE04 FDC

This is perhaps the most complex of the daughter cards. It is a very comprehensive floppy disc controller for up to 5 disc drives per card. It has *its own* processor which performs all the standard disc read/write routines and communicates to the ultimum bus via a pia chip. This makes software patching for different computers possible. The card includes an operating system ROM programmed for each host computer.

WE05 PRT

A part card with RS232c, parallel and Centronics interfaces, and a real time clock.

WE06 ADC

An analogue card with 12-bit precision A>D and D>A capability. A fast conversion 8-bit A>D is also included.

WE07 SBD

A sound board using a brand new chip to give up to nine oscillators with programmable frequency, waveform, ADSR envelope shaping and band filtering.

WE08 SPK

A phoneme speech card which is software programmable from RAM or ROM.

WE09 RES

A terminal card which provides 80 column video output and a keyboard interface to allow for connection of up to eight keyboards. It has optional character sets including teletext and block graphics.

WE10 CPU

A second processor card based on the very powerful 6809 c.p.u. This card can share the other system cards with the host computer and can be used to control the terminal card for multitasking operations.

WE11 PRO

The system breadboarding card—an invaluable card for anybody wishing to experiment with their own daughter cards.

WE12 EMU

This card has facilities to emulate up to 4K of ROM. RAM is memory mapped into host computer, then software switched into emulation.



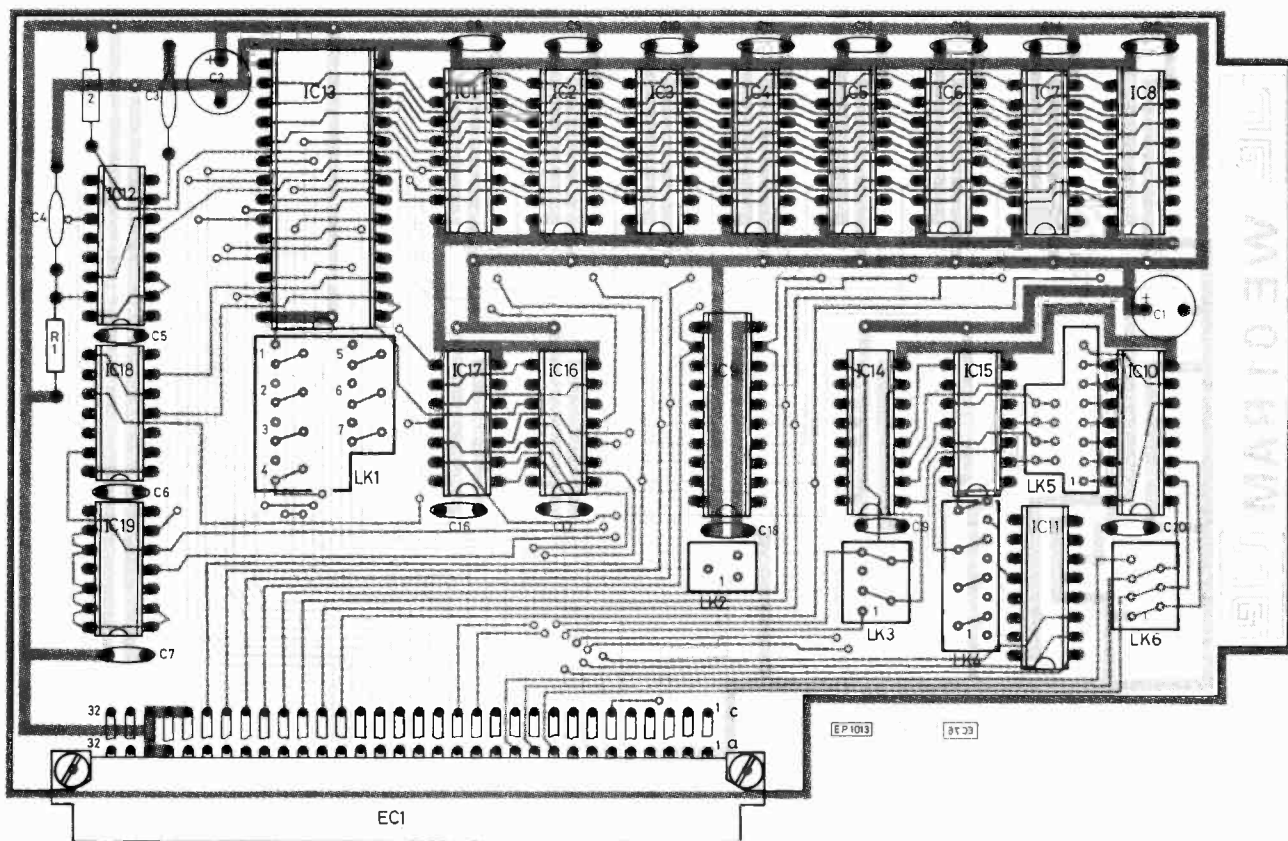


Fig. 2.2. Component layout of the RAM board

IC12 is used to provide the multiplex timing. The rest of the circuitry is decoding and buffering to allow paging and connection to the mother board.

ASSEMBLY

The component layout is shown in Fig. 2.2. As with the ULTIMUM, start with the sockets, then the capacitors and finally insert the i.c.s. taking special care with the static-sensitive memories.


THE LINKS

There are several links to be set up. To make life a little easier, many are initially configured for 64K RAMs, as most people will opt for this capacity.

Link 2 is set to the Rfsh position for Z80 based systems and Q2 for 65/68xx computers.

To give the user a wide range of decoding options there are several links used for setting up the address space. The function of these links is given in Table 2.1. The paging facility can be used to allow the 64K RAM to be mapped in pages of 16K, and 4K blocks for the 16K. Many other configurations are possible. The paging may be omitted if not required.

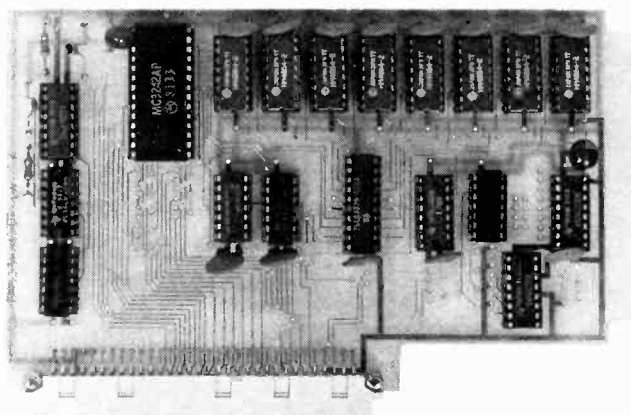If you are using 16K memories, link sets 1 and 3 require cutting and switching over. Cutting the set-up tracks is best done with a sharp blade. Applying a hot soldering iron will then remove the tracks between the cuts.



ULTIMUM is a motherboard configured universal interface system designed to work with most microcomputers

COMPONENTS . . .

16K/64K DYNAMIC RAM CARD

Resistors

R1, R2 5k1 $\frac{1}{4}$ W 5% (2 off)

Capacitors

C1, C2 100 μ /6V3 tant. (2 off)
C3, C4 10p disc ceramic (2 off)
C5-C20 100n disc ceramic (16 off)

Integrated Circuits

IC1-IC8 4816/4864* (8 off)
IC9 74LS373
IC10, IC11 74LS138 (2 off)
IC12 74LS123
IC13 MC3242
IC14 74LS148
C16, IC19 74LS08 (2 off)
IC15, IC17 74LS32 (2 off)
IC18 74LS04

Miscellaneous

14 pin d.i.l. socket (5 off)
16 " " " (12 off)
20 " " " "
28 " " " "
Printed circuit board WE01
PL1 2 x 32 'A+C' DIN Euro Plug (right-angled pins)

Option*

- a) For 16K RAM IC1-8=4816 (16384 x 1 bit i.c.)
- b) For 64K RAM IC1-8=4164/4864 (65536 x 1 bit i.c.)

TABLE 2.1. Links for the RAM board. Some links are in sets

Link set 1 (7 links near IC13)

These links set for 64K RAM. Cut and change over for 16K option. Their function is to set up IC13 address multiplexer for 64K or 16K operation.

Link set 2 (one link)

Set to RFSH position for Z80 systems, to Q2 position for 68/65x systems.

This all-important link tells the refresh circuitry when it may perform the refresh. It also gives the timing for read and write.

Link set 3 (2 links near IC14)

These links set for 64K RAM. Cut and change over for 16K operation.

These links determine whether the RAM is to be decoded in 8K or 16K blocks.

Link set 4 (4 links near IC11)

These links set for permanent (not paged) memory mapping. Cut one or more links and connect to Q0, Q1, Q2 or Q3 to allow AS lines (from 8255 port on mother board) to map in/out memory.

Link set 5 (four double links near IC10)

These are the main decoding links. Y0 to Y7 of IC10 allow you to map the RAM in blocks of 16K (in the case of 64K RAM) to any 16K boundary. If 16K RAM is fitted and link set 6 set up (see below), the memory may be mapped to any 8K boundary, in 2 blocks of 8K each.

Link set 6 (three links near IC10)

These are set up for 64K RAM. Cut and link the other way for 16K RAMs.

These links set the decoder up to decode in 8K or 16K blocks. If left in their default position, these only Y0, Y1, Y2, Y3 are available from IC10. Linked the other way, all outputs are enabled each representing an 8K boundary.

ROM AND BATTERY BACK-UP RAM CARD

This card provides five sockets each of which may be configured to accept a 4K EPROM, a 2K EPROM or a 2K x 8 RAM. Two of the sockets have back-up power from a rechargeable battery, giving up to 4K of non-volatile RAM. All the necessary address decoding and selection is provided on the card.

OPERATION

This is a nice simple card. IC6 provides address decoding to 4K boundaries which is sufficient for 2732 EPROMS. The provision of the inverter on the A11 line and ICs 8 and 9 allows decoding to 2K boundaries for 2716/2516 PROMS and 6116 RAMs. Fig. 2.4 shows the link layout for setting up the addressing. The As lines allow for the overlaying in sophisticated systems of up to three 4K slots per Battery RAM/ROM card, accessible under software control by writing the appropriate data to the Motherboard 8255 AO acts as an enable. A1 as a disable. Care should be taken not to enable more than one chip into the same part of memory space at a time.

Sockets 4 and 5 are provided with the option of a battery back-up power supply of 3V. This is sufficient for low power 6116 RAMs to hold information for about a year—even if the card is unplugged. The power for normal-mode use and for the battery trickle charge is derived from the twelve volt rail by a Zener shunt regulator (R1 D2). Switching between

main and back-up power is effected by diodes D3 and D1. The transistor circuitry on the CS lines ensures that they stay up with the back-up power line when the main power disappears, keeping the RAMs deselected and thus in low power mode. Links 6 and 7 provide for not using the battery back-up if this option is not required. Links 1 to 5 configure respectively sockets 1 to 5 for 2732s, 2716/2516s or 6116s. Fig. 2.4 shows the required layout of these links. Finally IC10 tells the motherboard when the data bus buffers must be activated.

CONSTRUCTION AND TESTING

Construction is straightforward. Links should be inserted and soldered in place first, discrete components next, and then the integrated circuits. The battery should be fitted last.

Testing the card requires an operational Motherboard and host computer. To test for EPROM you will require (a) an EPROM with known contents, and (b) a program to read it. If you have access to a PROM programmer and an eraser then life is made easy for you; simply copy your operating system or language system ROM into a spare EPROM drop this into the socket to be tested and write a little program to check the copy against the original. Mere mortals will have to make do with viewing their language ROMs first few bytes using operating system facilities, noting them down on a scrap of paper, moving the ROM in question to the socket under test and viewing them again in their new position in

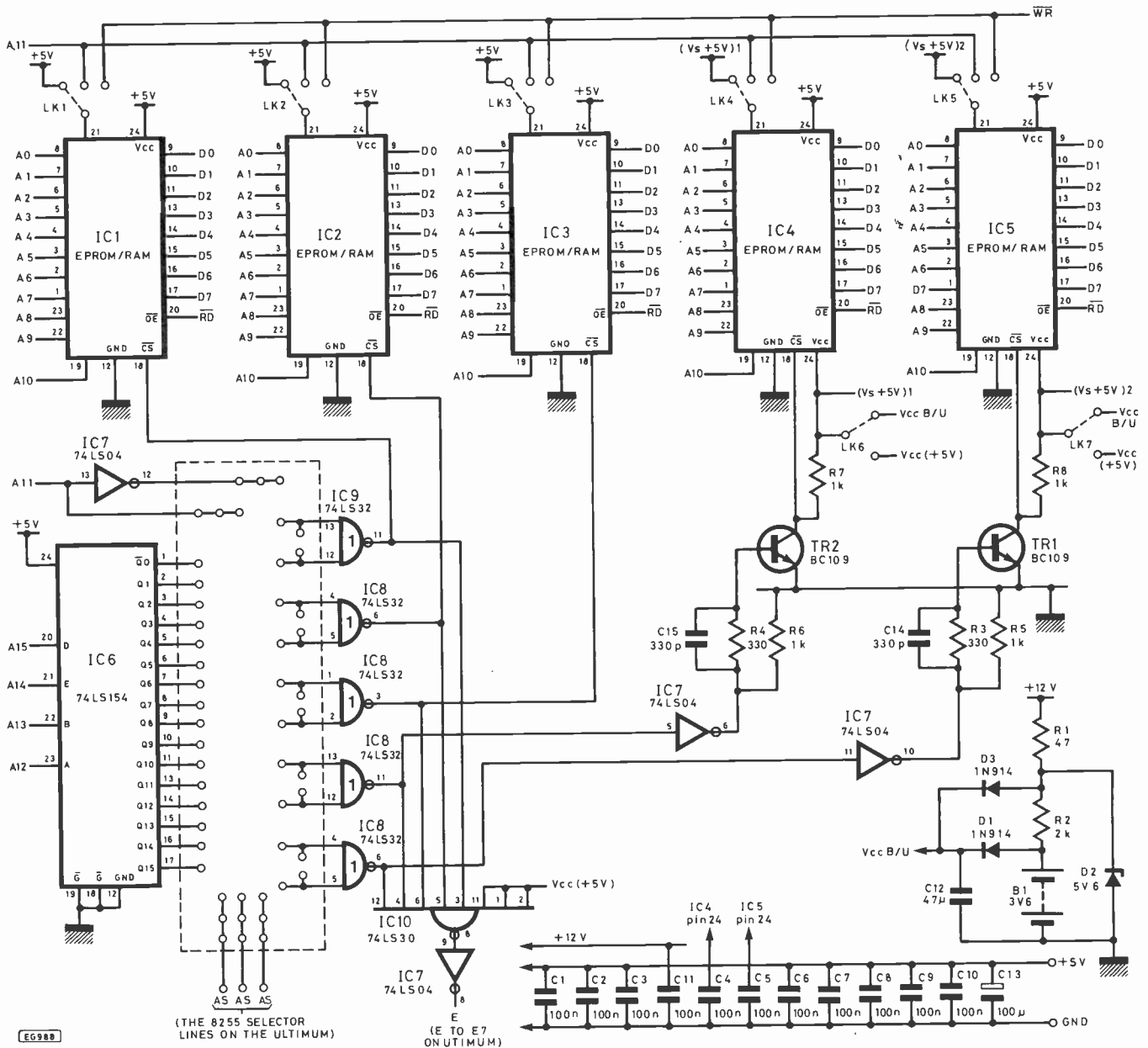


Fig. 2.3. Circuit diagram of ROM/Battery Back-up RAM board

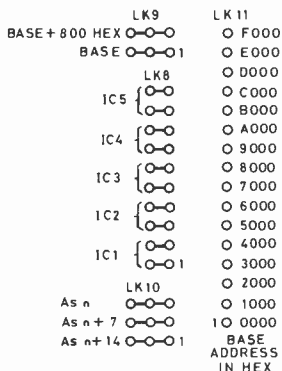


Fig. 2.4a. Addressing links on the Battery Back-up board. Link one of the pad pairs for each i.c. in L8 to the appropriate one in L11 to set the 4K base address. If the i.c. is only 2K, link the other pair to either of the L9 triplets to set the 2K boundary. Otherwise, link the two pad pairs together (unless you want to be clever and bring in an As line with L10! N is the number of the Euroconnector into which the card is plugged. The relationship between the As line numbers and the 8255 port bits was shown last month on the Mother-board circuit diagram)



Fig. 2.4b. Power links

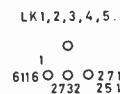


Fig. 2.4c. Configuration links

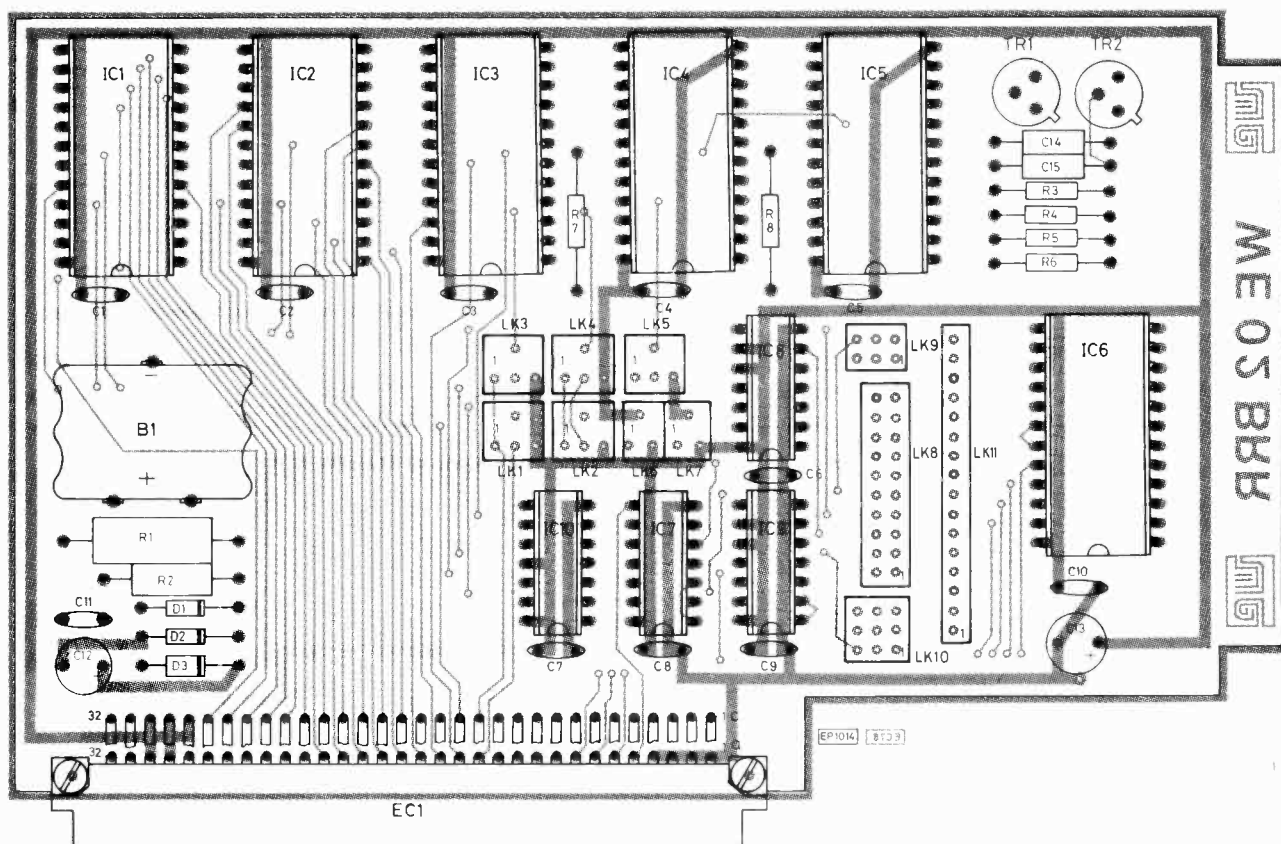


Fig. 2.5. Battery back-up board component layout

memory. If your system is such that you cannot move a ROM without losing your operating system then you have real problems!

Testing RAM is more simple; all that is required is to write

a known pattern into a location (e.g. all zeroes or all ones), read it back to check it, and go on to the next one. Keep a count of the errors; it should be zero over several cycles through the RAM.

COMPONENTS . . .

BATTERY BACK-UP BOARD

Resistors

R1	47 1W
R2	2k $\frac{1}{2}$ W
R3, R4	330 (2 off)
R5-R8	1k (4 off)

All resistors $\frac{1}{4}$ W 5% unless otherwise stated

Capacitors

C1-C11	100n disc. cer. (11 off)
C12	47 μ /6V3 tant.
C13	100 μ /6V3 tant.
C14, C15	330p polystyrene (2 off)

Semiconductors

TR1, TR2	BC109 (2 off)
D1, D3	1N914 (2 off)
D2	5V6/1W3 Zener

Integrated Circuits


IC1/IC5	EPROM/RAM see text (5 off)
IC6	74LS154
IC7	74LS04
IC8, IC9	74LS32 (2 off)
IC10	74LS30

Miscellaneous

14 pin low profile d.i.l. socket	(4 off)
24 pin low profile d.i.l. socket	(6 off)
P.c.b. mounting battery	3V6
P.c.b. WE02 BRR	
2 x 32 A+C DIN Euro-Angle plug	

Constructors Note

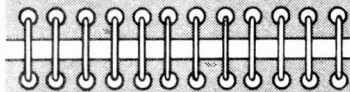All kits for the Ultimium system are to be available from **Watford Electronics** (See advertisers' Index). Send SAE for price list of boards now available.



INDUSTRY NOTEBOOK

By Nexus



Genesis

Overwhelmed by the profusion of electronics in daily life all the way from children's toys to giant computers, we tend to forget that in the beginning all we had was wireless telegraphy as distinct from telegraphy by wire. The 'wireless' in its then embryonic state had only one application where it could obviously score and that was in maritime communication where, quite clearly, it was impractical to link ships at sea by wires. Up to the advent of what we now call radio communications a ship's position could be reported only when visually sighted and identified by a watcher on shore. Similarly, ships at sea could only communicate when in visual or hailing range of each other.

When Marconi formed the Wireless Telegraph and Signal Company Ltd on 20th July 1897 it was the maritime world which quickly saw new possibilities. The Italian navy was first off the mark in adopting the Marconi system but within months Lloyds of London, the great shipping insurance syndicate, also became interested. The impetus thus originated with both naval and mercantile shipping interests becoming enthusiastic supporters of a remarkable invention which was to blossom years later into the huge and exciting industry which we now call electronics.

Marine radio and electronics nowadays doesn't get much of a press. We take it for granted as 'old hat'—a remote and hazy background to more exciting and immediate developments such as the laser or optical fibres or the popular crazes for personal computers and video.

Although in the background, marine electronics remains big business and highly competitive. I was reminded of this as further details of maritime operations in the Falklands conflict came to light. A total of 51 warships and 52 merchant ships were employed together with 171 aircraft of the

Fleet Air Arm. Eighteen thousand sailors and marines were at sea and at any one time during the operation the supply 'pipeline' of 8,000 miles length was carrying half a million tons of fuel and stores to sustain the armada.

One may imagine the organisation required and the level of efficiency of communications necessary to ensure smoothness, particularly as the sharp end was in perpetual flux of battle. And, as this was in every sense a war (albeit undeclared by either side as is today's custom) there would have been the additional complications of encryption to preserve secrecy and periods of radio silence to conceal ship movements.

The whole electromagnetic spectrum from VLF (for submerged submarines) to microwave (satellite communication to the operations centre near London) was employed. VHF and UHF to aircraft and between ships at short range. The bulk of naval ship-to-ship traffic, however, was on HF through the Marconi Integrated Communications System Mk 3 (ICS3), standard in the Royal Navy and adopted by other NATO and non-NATO navies. ICS3 is flexible both in frequency and power management and enables commanders to access the transmitter, receiver and antenna systems best suited to his communications requirement at any time with a number of different users working into the system simultaneously on different frequencies using voice, telegraphy or data.

ICS3 is also adaptable to new technology. It already has frequency agility from extensive use of broad-band techniques and auto-tuning enabling rapid change of frequency. Although unlikely to have been used in the South Atlantic it is also adaptable to frequency hopping.

In the merchant navy, too, we have come a long way from early spark transmission. Minimum radio requirements for vessels over 1,600 grt were established at the 1974 Safety of Life at Sea Convention (SOLAS 74). They include main and reserve MF telegraphy transmitters and receivers, automatic keyers, radiotelephone transmitter and receiver on the distress frequency with auto-alarm, VHF radiotelephone and portable lifeboat transceiver.

Most large vessels have far more than the minimum equipment with additional high-powered HF transmitter and telex and facsimile facilities, radio direction finders, and other radio navigation equipment which may include Loran C, Decca Navigator, Omega (a world-wide VLF positioning system), and Satellite Navigation. If we include radar (often a dual installation) and echo sounders, the total electronic package can approach £100,000.

Although world shipbuilding, including the UK, is in recession, ships are being built and the race is on to supply equipment. Marconi International Marine, who supply radio and electronic sea-going officers if required as well as hardware, have recently won orders for complete installations in ten new buildings under construction in India, Japan and Korea. Apart from proven quality

of equipment, Marconi export successes in merchant shipping are due to the worldwide servicing network with a Marconi presence in every major port.

The slack caused by decline in the number of ships at sea has been taken up by large installations on oil rigs which, in addition to SOLAS requirements, have continuous need for commercial transmission and extra housekeeping requirements such as UHF/VHF radio paging and aero-nautical beacons for helicopter guidance.

Balance

Overseas sales of marine electronics equipment is just one area of industry that contributed to a record £6 billion surplus on current account balance of payments last year and helped repay £1.6 billion on foreign currency borrowing. Compare this performance with the rising total of virtually bankrupt countries unable to service interest charges let alone repay capital borrowed.

Surprise

There were plenty of raised eyebrows when Racal announced entry into the Pay-TV business. This was a company which had always shunned the entertainment sector of electronics. When Racal acquired Decca they couldn't get rid of Decca's domestic TV interests fast enough, eventually selling it off to a Far Eastern entrepreneur. Had Sir Ernest Harrison gone off his rocker doing a U-turn? Closer examination showed that he hadn't lost his touch or his sense of direction.

In fact Racal stays in the capital goods sector of the industry as an extension of traditional communications business and expect to generate billions of pounds in the next decade in cable and subscription TV. To get in on the act Racal has teamed itself on a 50/50 basis with Oak Industries of San Diego, California, who are already established with not only the technology but also operating experience with five Oak-owned STV systems and 610,000 paying subscribers. Old-timers in the industry will remember Oak switches which were the first products.

Oak moved into Pay-TV in 1977 and is now in all modes, cable, STV and direct broadcast by satellite (DBS). All use encryption technology to ensure that programmes can be received only by subscribers who have appropriate decoding apparatus. Racal have great experience in signal encryption and will no doubt contribute to the technology in the years ahead.

Immediately, however, Oak need to expand into international markets and the new joint company, Racal-Oak Communications Ltd, although based in the UK will cover the whole of Europe. The two equal partners are clearly delighted with their marriage which was blessed at the inauguration ceremony by none other than Mr Kenneth Baker, Minister for Information Technology, who hinted ever so slightly that he, himself, might have been the marriage broker following a meeting with Oak's chairman last June.

PE micro-file

FILESHEET 2

R.W.Coles

6800 • 6802

APPEARING hot on the heels of the Intel 8080A in 1974, the 8 bit NMOS Motorola 6800 soon established a significant following of designers who liked it for its single 5 volt supply operation and its elegant instruction set which had been modelled after the PDP11 minicomputer. By the end of the decade Motorola was building on its success and introducing several new devices, all described as "6800 family members" and all bearing a close resemblance to their parent. The 6802 was one of these, and was intended to directly replace the 6800 in new applications where its on-chip clock and RAM array would make it easier to use than the basic 6800 which was itself becoming obsolete.

The powerful 6801 is intended as a 6800 system-on-a-chip, with RAM, ROM, Clock, Multiplier, Serial and Parallel I/O all available in a single package. The 6803 is a ROM-less version of the 6801 but the 6805 goes the other way with a "sawn-off" version of the 6800 architecture for smaller single chip applications and low cost. The shortened registers and reduced memory addressing range of the 6805 allow it to fit into a 28 pin package complete with ROM RAM and parallel I/O. A CMOS version, the MC 146805 and an EPROM version, the 68705, are also available. Perhaps the thing to note about the 6801 and the 6805 is that they share, to a large extent, the instruction set and features of their ancestor.

Also in the 6800 family is the 6809 which represents an attempt to capture a slice of the data processing market for the Motorola family which until the 6809, could not compete well in this field with the 8080A or more particularly with the Z80. The 6809 is a very nice chip with most of the problems of the 6800 put right and with lots of new features and facilities, but unfortunately for Motorola, it turned up too late, when most of the data processing sockets had already been gobbled up by the 6502 made by MOS Technology. The 6502 is to the 6800 what the Z80 is to the 8080A, a successful attempt by outsiders to improve on the basic chip and to steal a march on the originators.

The 6800 and 6802, then, can be considered to be at the centre of a large and expanding family of devices which have a big following, and a large part of this success must be attributed to the original designers of the 6800 who came up with a simple but capable architecture and an elegant instruction set. The popularity of these devices should ensure their availability for many years to come.

REGISTERS

With so much going for it, you may be wondering why the 6800 lost out to the 8080 and its "messy" instruction set in many applications. Although there are many secondary reasons, the primary reason must surely be the 6800's lack of CPU registers. In some respects the 6800 register set is good. There are two general purpose accumulators, compared with the one on the 8080A, and there is a 16 bit index register where the 8080 has none, but that is as far as it goes. Where the 8080A has six general purpose 8 bit registers the 6800 has none, with the result that temporary data storage and counters usually have to reside in main memory. To be sure, the use of main memory for this purpose is well supported with extra instructions to allow register like operations to be performed there, and it could be argued that access is made available to a virtually unlimited register set by this method, but the net result is a reduction in flexibility and in speed of access to the temporary data and the counters.

Even more of a problem, according to some, is the provision of only one index register, since most programs need two. Although

the 8080 has no true index registers, it is quite possible to use the DE and HL pairs as pseudo index registers at the cost of a few extra instructions. Achieving the same result with the 6800 would be a more difficult and time consuming job.

As can be seen from the file sheet, the 6800 and the 6802 share the same register set, which has two 8 bit registers ACCA and ACCB, and three special purpose 16 bit registers IX (Index register) SP (Stack Pointer) and PC (Program Counter). In addition there are 5 single bit flags which are for some operations grouped together as the 8 bit CCR (Condition Code Register).

The two accumulators are identical and are used as the focus of many of the instructions, particularly those which use the ALU (Arithmetic and Logic Unit). The accumulators may be added or compared with one another and either can be used to hold the result of arithmetic, logic, data test, and data handling instructions.

The Index Register is intended for use as a memory pointer and is used to implement register indirect addressing of data tables which are created in RAM by the programmer. Since only the Index Register is available as an indirect address pointer, this addressing mode is actually termed Indexed Addressing. The Index Register pointer can be moved through the full address range of 64K bytes by increment and decrement instructions, but the real advantage of this 6800 feature lies in the ability to add an offset value which is specified in the instruction. In effect, the Index Register may be used to hold the base address of a table with access to individual table entries being gained by specifying a 0-255 offset value to be added to the Index Register value. The contents of the Index Register itself are not modified when this addressing mode is invoked. For example, the two byte instruction: ADDA 00H,X adds the content of the memory location pointed to by the Index Register to the accumulator, while: ADDA 08H,X adds the content of the memory location pointed to by the Index Register value plus 8, to the accumulator, leaving the Index Register itself unmodified. It is this offset capability which makes Indexed addressing so efficient; the 8080A programmer would have to use extra register arithmetic instructions to achieve the same result and would end up with a modified pointer value into the bargain.

The Stack Pointer register in the 6800 and 6802 works in exactly the same manner as the 8080A version, and is used to control access to a Last-In-First-Out (LIFO) stack in RAM memory. In comparison with the 8080A however, the 6800 stack instructions are more limited, the 6800 is restricted to pushing or pulling a single byte from one of the two accumulators. The stack concept is also important for automatically storing subroutine return addresses and processor status following an interrupt, and the 6800 comes out well here since on interrupt it saves *all* the CPU registers on the stack automatically whereas the 8080A saves only the Program Counter, leaving the programmer to save the rest using PUSH instructions.

The Program Counter holds no surprises and is virtually identical to the 8080A in terms of its addressing range and its operation.

The 6800 and 6802 flags are somewhat different to those of the 8080A. There is no Parity flag, and this is sometimes a drawback, but there are two extras, namely Overflow, which is set if arithmetic overflow occurs as the result of an ALU operation, and Interrupt, which indicates whether interrupts have been enabled or disabled.

INSTRUCTIONS

The 6800/6802 instruction set is regular and elegant, and this makes these processors easy to program and ideal for use in tutorial systems.

6800/6802 REFERENCE FILE SHEET

GENERAL

Although appearing shortly after the 8080A the 6800 never really caught on quite as well. This is mainly due to the more powerful architecture of the former but it is a pity because the 6800 has a more elegant instruction set and hardware which makes it a good device for beginners and a better device than the 8080A when it is capable of doing the job. The 6802 is a simple upgrade of the 6800 which has an on-chip clock generator and 128 bytes of RAM. The 6802 is recommended for all new designs.

REGISTERS The 6800/6802 have two 8 bit general purpose data registers (ACC A & ACC B) and three specialised 16 bit memory pointers.


ACCUM A	8	ACC A
ACCUM B	8	ACC B
INDEX REG	16	IX
STACK POINTER	16	SP
PROGRAM CNTR.	16	PC

FLAGS:-


D7	D6	D5	D4	D3	D2	D1	D0
		AUX CARRY	INT	SIGN	ZERO	OVERFLOW	CARRY

INSTRUCTION SET AND SOFTWARE

The 6800 and 6802 share a common instruction set which has been modelled after the PDP11 minicomputer as far as possible. The instruction set is more elegant and less messy than the competing 8080A/8085A but is hindered by a scarcity of CPU registers which is overcome to some extent by the "Direct" addressing mode which allows fast access to page zero (256 bytes) of memory. Reset causes branch to address which must be stored in address/location's FFFF & FFFF. One, two and three byte instructions are used and "Direct, Extended, Immediate, Relative, Indexed and Implied" addressing modes are available. Chips are well supported in software including Tiny Basic.

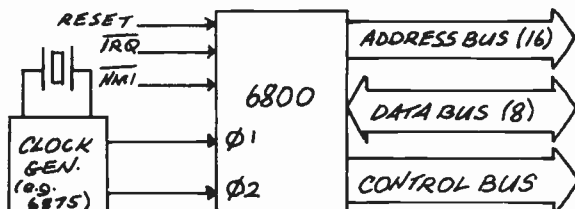

BASIC TWO CHIP 6800 CPU COT

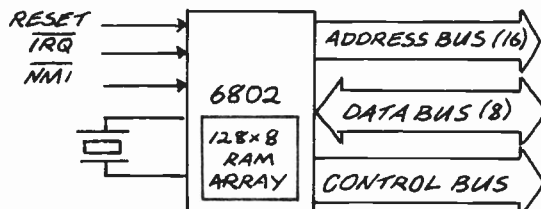

BASIC SINGLE CHIP 6802 EQUIVALENT

PERFORMANCE DATA

	6800	6802
MEMORY ADDRESS RANGE:-	64K	64K
I/O ADDRESS RANGE:-	(MEMORY MAPPED)	
CLOCK FREQUENCY*:-	1MHz	1MHz
POWER SUPPLIES:-	5V	5V
INTERRUPTS:-	IRQ	IRQ
	NMI	NMI

*NOTE: 1.5 MHz & 2.0 MHz SELECTIONS OF BOTH CHIPS ARE ALSO AVAILABLE.

BENCHMARKS

	6800	6802
ADD REGISTER TO ACCUM	2μS	2μS
O/P ACCUM TO PORT ①	5μS	5μS
MOVE FROM MEMORY TO MEMORY	9μS	9μS
① EXTENDED ADDRESSING MODE		

VSS	1	40	RESET	VSS	1	40	RESET
HALT	2	39	TSC	HALT	2	39	XTAL
phi1	3	38	N.C.	MR	3	38	EXTAL
IRQ	4	37	phi2	IRQ	4	37	E
VMA	5	36	DBE	VMA	5	36	RE
NMI	6	35	N.C.	NMI	6	35	VCC(STBY)
BA	7	34	R/W	BA	7	34	R/W
VCC	8	33	D0	VCC	8	33	D0
A0	9	32	D1	A0	9	32	D1
A1	10	31	D2	A1	10	31	D2
A2	11	30	D3	A2	11	30	D3
A3	12	29	D4	A3	12	29	D4
A4	13	28	D5	A4	13	28	D5
A5	14	27	D6	A5	14	27	D6
A6	15	26	D7	A6	15	26	D7
A7	16	25	A15	A7	16	25	A15
A8	17	24	A14	A8	17	24	A14
A9	18	23	A13	A9	18	23	A13
A10	19	22	A12	A10	19	22	A12
A11	20	21	VSS	A11	20	21	VSS

PIN DIAGRAMS

MANUFACTURERS

ORIGINATOR :- MOTOROLA
 6800 2ND. SOURCES:- A.M.I, HITACHI, FAIRCHILD
 SESCOSEM
 6802 2ND. SOURCES :- A.M.I, HITACHI, FAIRCHILD
 SESCOSEM + MITEL
 PLESSEY, MEDL (IN CMOS)

SUPPORT CHIPS

6800 needs an external 2φ clock generator such as 6871 or 6875 and has a family of support devices including:- 6821 (parallel I/O) 6828 (interrupt controller) 6840 (timer-counter) 6844 (DMA) 6850 (UART) 6802 has ROM/timer/I/O combo chip (6846) In addition to above 6800 parts

INDEX REGISTER AND STACK POINTER INSTRUCTIONS

OPERATIONS	MNEMONIC	ADDRESSING MODES				COND. CODE REG.			
		IMMED	DIRECT	INDEX	EXTND	H	I	N	Z
Compare Index Reg	CPX	BC 3	3	9C 4	2	AC 6	2	BC 5	1
Decrement Index Reg	DES								
Increment Index Reg	INX								
Load Index Reg	LDS	CE 3	3	DE 4	2	EE 6	2	FE 5	3
Store Index Reg	STS	DF 3	3	9E 4	2	AE 6	2	BE 5	3
Stack Pointer - Index Reg	TSX	9F 3	3	AF 4	2	BF 6	2	CF 5	3

- ① (Bit N) Test Sign bit of most significant (MS) byte of result = 1?
 ② (Bit V) Test: 2's complement overflow from subtraction of ms bytes?
 ③ (Bit N) Test Result less than zero? (Bit 15 = 1)

JUMP AND BRANCH INSTRUCTIONS

OPERATIONS	MNEMONIC	ADDRESSING MODES				COND. CODE REG.			
		IMMED	DIRECT	INDEX	EXTND	H	I	N	Z
Branch Always	BRA	20 4	2						
Branch If Carry Clear	BCC	24 4	2						
Branch If Carry Set	BES	25 4	2						
Branch If Equal	BED	27 4	2						
Branch If Greater Than Zero	BGT	2E 4	2						
Branch If Higher	BHI	22 4	2						
Branch If Less Than Zero	BLE	2F 4	2						
Branch If Lower Or Same	BLS	23 4	2						
Branch If Minus	BNE	26 4	2						
Branch If Not Equal Zero	BVC	28 4	2						
Branch If Overflow Clear	BVS	29 4	2						
Branch If Overflow Set	BPL	2A 4	2						
Branch If Plus	BSR	8D 8	2						
Jump	JMP								
Jump To Subroutine	JSR								
No Operation	NOP								
Return From Interrupt	RTI								
Return From Subroutine	RTS								
Software Interrupt	SWI								
Wait for Interrupt*	WAI								

- ① (All) Load Condition Code Register from Stack. (See Special Operations)
 ② (Bit 1) Set when interrupt occurs. If previously set, a Non Maskable Interrupt is required to exit the wait state.

CONDITION CODE REGISTER INSTRUCTIONS

OPERATIONS	MNEMONIC	ADDRESSING MODES				COND. CODE REG.			
		IMMED	DIRECT	INDEX	EXTND	H	I	N	Z
Clear Carry	CLC	0C 2	1						
Clear Interrupt Mask	CLI	0E 2	1						
Clear Overflow	CLV	DA 2	1						
Set Carry	SEC	0D 2	1						
Set Interrupt Mask	SEI	0F 2	1						
Set Overflow	SEV	0B 2	1						
Accumulator A ← CCR	TAP	06 2	1						
CCR ← Accumulator A	TPA	07 2	1						

- R = Reset
 S = Set
 * = Not affected
 ① (ALL) Set according to the contents of Accumulator A

OPERATIONS	MNEMONIC	ADDRESSING MODES				COND. CODE REG.			
		IMMED	DIRECT	INDEX	EXTND	H	I	N	Z
Add	ADD	38 2	2	98 3	2	AB 5	2	BB 4	3
Add Accumulator	ADDB	C8 2	2	DB 3	2	EB 5	2	FB 4	3
Add with Carry	ABA	89 2	2	99 3	2	AB 5	2	BB 4	3
And	ADC	C3 2	2	DB 3	2	EB 5	2	FB 4	3
And	ANDB	84 2	2	94 3	2	AB 5	2	BB 4	3
Bit Test	BITA	85 2	2	95 3	2	AB 5	2	BB 4	3
Clear	CLR	C5 2	2	DB 3	2	EB 5	2	FB 4	3
Compare	CLRB	81 2	2	91 3	2	AB 5	2	BB 4	3
Compare Accumulator	CMPS	C1 2	2	DB 3	2	EB 5	2	FB 4	3
Complement 1's	COM	63 7	2	73 6	3				
Complement 2's (Negate)	NEG	60 7	2	70 6	3				
Decimal Adjust, A	DAA	19 2	1						
Decrement	DEC	6A 7	2	7A 6	3				
Exclusive OR	EXOR	88 2	2	98 3	2	AB 5	2	BB 4	3
Increment	INC	C8 2	2	DB 3	2	EB 5	2	FB 4	3
Load Accumulator	LDA	86 2	2	96 3	2	AB 5	2	BB 4	3
Or, Include	ORA	C8 2	2	DB 3	2	EB 5	2	FB 4	3
Push Data	PSHB	CA 2	2	DA 3	2	EA 5	2	FA 4	3
Pop Data	PULB	69 7	2	79 6	3				
Rotate Left	ROL	59 2	1						
Rotate Right	ROR	58 2	1						
Shift Left, Arithmetic	ASL	48 2	1						
Shift Right, Arithmetic	ASR	58 2	1						
Shift Right, Logic	LSR	54 2	1						
Store Accumulator	STAB	93 4	2	A7 5	2	AB 5	2	BB 4	3
Subtract	SUBB	80 2	2	90 3	2	AB 5	2	BB 4	3
Subtract Accumulator	SBCA	82 2	2	92 3	2	AB 5	2	BB 4	3
Subtract with Carry	SBCB	C2 2	2	DB 3	2	EB 5	2	FB 4	3
Transfer Accumulator	TAB	17 2	1						
Test, Zero or Minus	TST	60 7	2	70 6	3				
Test, Zero or Minus	TSTB	40 2	1						

- LEGEND:
 DP Operation Code (Hexadecimal)
 # Number of MPU Cycles
 + Number of Program Bytes
 - Arithmetic Plus
 * Arithmetic Minus
 MGP Contents of memory location pointed to by Stack Pointer
 R Register
 S Set
 * Not Affected
 ① Bit = Zero
 00 Byte = Zero

Note - Accumulator addressing mode instructions are included in the column for IMPLIED addressing

6800-6802
INSTRUCTION SET

There are 72 basic instructions in the set, but the availability of more than one addressing mode for many of them results in a total set of 197 different instructions. Instructions may be one, two or three bytes in length, where the first (or only) byte contains sufficient information to identify the instruction and its addressing mode, and the other byte or bytes contain ancillary information such as a memory address. Instructions are provided for binary and BCD 8 bit arithmetic, logic operations, shifts and rotates, data load, data store, conditional or unconditional branch, and interrupt and stack manipulation.

Two instructions of particular note are SWI and WAI. SWI stands for SoftWare Interrupt and is rather similar in operation to the 8080A Restart (RST) instruction with the exceptions that there is only one (as opposed to 8 RSTs) and SWI causes all registers to be stacked, not just the PC. The SWI vector is also in high memory (FFFAH and FFFBH) as opposed to low memory for the 8080A RSTs. WAI stands for Wait for Interrupt, and has no direct equivalent in the 8080A. It causes all CPU registers to be stacked and the processor to be halted while awaiting an interrupt. This provides a fast interrupt response but also nullifies some of the advantages to be had from asynchronous interrupts. A comprehensive set of addressing modes are available as follows:— Direct; in which a single byte page zero address is specified as part of the instruction; Extended; in which a two byte address is specified (like 8080A Direct!), Immediate; in which the instruction contains the data to be used, not an address reference, Inherent; (the same as 8080A Implied), Relative; which allows branching forwards or backwards in memory relative to the program counter value, and Indexed which uses the Index Register and an offset supplied by the instruction as already described. Both the Relative and the Indexed mode have no direct equivalent in the 8080A instruction set. The Relative addressing range is from -125 to +129 locations relative to the first byte of the two byte relative branch instruction, this mode reduces the size and the execution time of a program.

SOFTWARE

Like the 8080A family, the 6800 family has extensive software support because of its popularity and its long existence. It does, however, lack a universally accepted disc operating system such as the 8080A's CP/M. Perhaps the best known 6800 software is the Motorola MIKBUG monitor which was supplied with their evaluation board, the MEK68D2, but there are also a number of other software tools including Editors, Assemblers, Compilers (notably for FORTRAN) and Interpreters, including a TINY BASIC.

INTERFACING

The 6800/6802 have no need of the IO/M line of the 8080A family since there is no separate I/O address space. Also, instead of the separate $\overline{RD}$ and $\overline{WR}$ lines of that family the 6800/6802 have a single RD/ $\overline{WR}$ line and a separate VMA (Valid Memory Access) line. By use of appropriate gating it is possible to convert the 6800 scheme to the 8080A version and vice-versa, and this is important if you ever wish to use peripheral chips such as UARTs from a different family to that of the processor itself.

The 6800 requires an external two phase clock generator, and two approaches to this are possible. The first approach to appear was a rather unconventional hybrid device, the MC6871, which included not only the clock generator electronics but also an appropriate crystal *inside* the package. Later on, the more conventional MC6875 appeared in a 16 pin DIL. This device provides some extra facilities but needs an external crystal.

The 6802 does not need an external clock generator, only a crystal, and has the added bonus of a 128 byte RAM array on the chip. The first 32 bytes of this array may be retained in a low power standby mode by using the additional supply pin, VCC Standby. These differences mean that the 6802 is not completely pin compatible with the 6800. The DBE (Data Bus Enable) and TSC (Three State Control) pins of the 6800 are not available on the 6802, and neither are the $\phi 1$ and $\phi 2$ clock inputs for obvious reasons. Since the $\phi 2$ clock signal is used for systems control, an equivalent output is provided on the 6802 by E (Enable). Two other new 6802 pins (in addition to the crystal pins) are MR (Memory Ready) which when driven low causes the memory cycle to be extended to allow interface to slow memory or peripherals, and RE (RAM Enable) which is used to select the internal RAM array when required.

The interrupt schemes used by the 6800 and 6802 are identical and fairly simple. One advantage of the 6800/6802 over the 8080A is that the former have a Non-Maskable Interrupt (NMI) in addition to the standard maskable input available on all three. The NMI can never be disabled and is therefore useful in some systems to warn of power failure or other not-to-be-ignored happenings. Intel at first said that there was no need for an NMI, and then introduced one on their 8085A!

On the occurrence of an NMI, the processor stores the CPU registers on the stack and then loads the PC with the address stored in memory locations FFFCH and FFFDH. The maskable IRQ interrupt has the same general effect except that the vector is fetched from FFF8H and FFF9H. Note that only a single vector is normally available for each source and without an external interrupt controller chip, multiple interrupt sources have to be polled by software. The 8080A is difficult to compare directly, since it always needs at least some external gating to accept vectors, but thanks to the single byte RST instructions it is a comparatively simple matter to build a scheme to cater for up to 8 separate sources without polling. The 8085A has additional direct interrupt lines of course.

PERIPHERAL CHIPS

The 6800 series is blessed with an extensive family of peripheral devices capable of performing most of the commonly required functions and some of the rather more exotic ones.

Apart from the clock generators mentioned earlier, perhaps the most often specified peripheral device is the Peripheral Interface Adaptor or PIA for short. This function is performed by the 6821 device which has two 8 bit parallel ports useful for communicating with the full range of possible input and output devices such as switches, lamps, and line printers.

Communication with the CPU takes place over the bidirectional CPU data bus using standard 6800 or 6802 control signals, and two interrupt outputs (one for each port) are available for connection to an interrupt controller chip like the 6828 or to be Wire-OR'ed to the IRQ input of the processor. Each of the four possible sources of interrupt can be separately enabled or disabled by the processor if required. After the 6821 in popularity comes the 6850 Asynchronous Communications Interface Adaptor (ACIA) which most (Non-Motorola!) people call a UART. The 6850 is a simpler device than the Intel 8251 USART because while the 8251 provides asynchronous or synchronous serial communication, the 6850 is asynchronous only, with an additional part, the 6852, available if a synchronous link is required.

Other devices available include the 6840 triple 16 bit timer, the 6844 Direct Memory Access (DMA) controller, and the 6860 Modem. The 6802 also has its own special "Combo" peripheral device, the 6846, which provides 2K bytes of ROM, 10 parallel I/O lines and a timer. Since this device uses masked ROM it is not usually suitable for home projects.


APPLICATIONS

As with the 8080A/8085 there would appear to be little point in using the 6800 in new applications now that the 6802 is available at a reasonable price. An added incentive to use the 6802 is the fact that CMOS versions are available from other manufacturers making it possible to build a low power consumption system when necessary for battery powered applications.

Both processors are ideal for learning about both the hardware and software aspects of microprocessors and the 6800 is widely used in tutorial systems for this reason. Neither chip can be recommended for data processing applications, however; if this is your requirement and you like the style of the 6800, then choose the 6502 or better still the 6809.

The 6800 and 6802 come into their own as controllers for small systems and are mostly used for this purpose. Their simple low-cost hardware approach and their elegant easy to use instruction set suit them ideally for jobs such as appliance control, vending machines, car computers, and PROM programmers. In the author's opinion, if a 6802 is powerful enough to perform a particular control task then it is probably wise to choose it in preference to the 8085A because the resulting system will probably be simpler, cheaper, and easier to program. All in all the 6800 or the 6802 are not a bad choice for the hobbyist because it will later be easy to move on to more powerful chips like the 6502 or the 6809.

SPECIAL OFFER

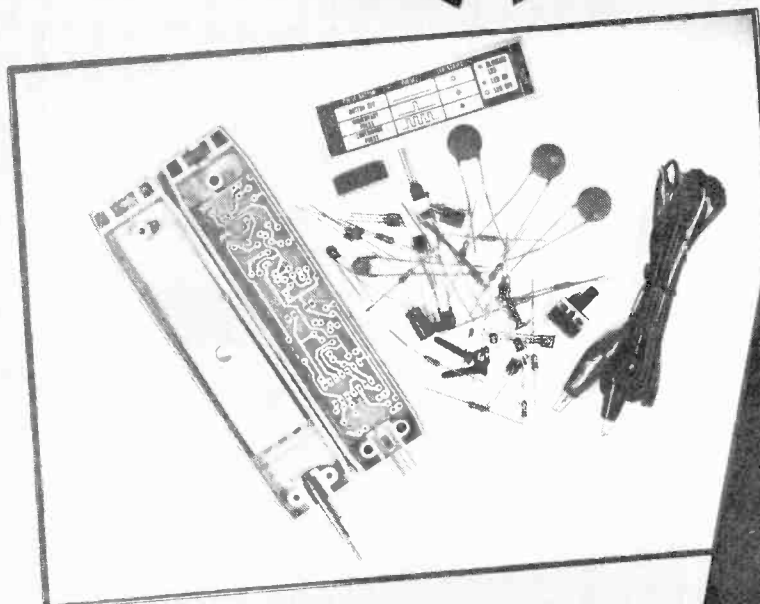

DIGITAL PULSER KIT

£17.45

INCLUDING V.A.T. POSTAGE AND PACKING

Back in October '81 Tom Gaskell presented the *PE Pulser* design as part of the *Digital Design Techniques* series. The ingenious design has been taken up by GSC and the kit shown above is the result. We are pleased to have been able to arrange this special offer price for PE readers.

SPECIFICATION

Supply voltage 5 to 18V

Pulse width TTL and 5V CMOS outputs, approx. 1-5µs
15V CMOS outputs, approx. 3µs

Pulse repetition rate 100Hz (at $V_{CC} = 5V$ d.c.)

Supply current (no load), less than 20µA

(into a short circuit), less than 10mA

Protected from reverse supply connection and probe short circuit.

To: GSC Shire Hill Industrial Estate, Saffron Walden,
Essex CB11 3AQ. Tel. 0799 21682

Please complete both parts of the coupon in BLOCK CAPITALS

Please send me

Kit/s

One Pulser kit costs £17.45 including VAT and p.&p.

I enclose PO/Cheque No. Value

Name

Address

Please allow 28 days for delivery

OFFER CLOSES FRIDAY DECEMBER 31 1982

Name

Address

SEMI-PROFESSIONAL MIXING DESK

Part Three



THE p.c.b. design for the power supply unit is shown in Fig. 1 with the component layout shown in Fig. 2. Before the components are soldered, the 'L' shaped heatsink should first be fitted to the p.c.b.

All the components should then be soldered into position with mica washers being used on the two i.c.s. Carefully check the orientation of the semiconductors and the electrolytic capacitors.

The case components should be mounted as shown in Fig. 3 and all the mains wiring covered with rubber sleeving. The two output rails should be tested before the power supply is connected to the mixing desk.

PA MIXING—LIVE CONCERTS

Mixing the sound for a live music show differs considerably from mixing in a recording studio. Firstly everyone plays at the same time which means that there are many more mixer channels to be balanced and equalised etc. Secondly the high sound level on stage makes it difficult for the players to hear each other with any degree of sound balance. Fig. 4 shows how all the instrument amplifiers, drums and singers are set-up and fed to the mixer which is normally positioned in the audience where the sound engineer can hear clearly the sound of the PA system. It also shows how a separate sound system is provided for the players on stage, so that they can all hear what each person is playing. This other mix is derived from an auxiliary mixer output which is independent from the main stereo PA mix.

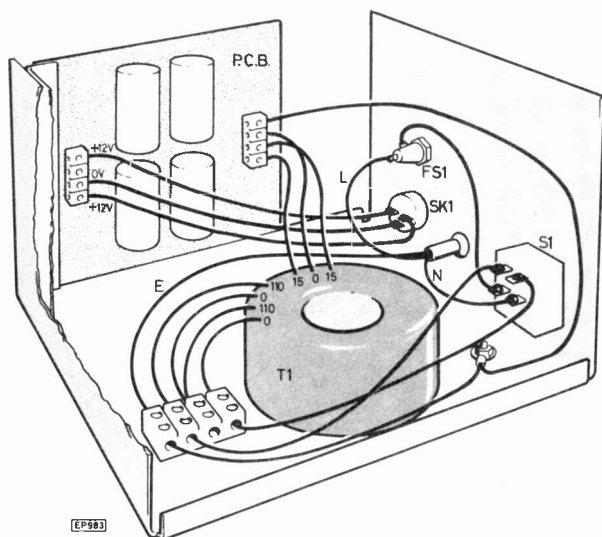


Fig. 3. Wiring diagram for the p.s.u.

The mixer also adds effects to the overall sound, such as reverb and echo, using the other auxiliary outputs as well as taping the stereo mix for the inevitable post-mortem of the concert. Live sound mixing is certainly more liable to problems than studio recording, the most common one being feedback or howl-round between the microphones and the on-stage monitoring systems which are placed close to the players. Highly directional microphones are favoured for this reason. Also, because there is never any second chance with live sound it is essential to set up the system and balance the sound before the audience arrives, so that everything is ready when the players walk on to give their performance.

USING THE MIXING CONSOLE

The mixing desk is a modular system built up from sets of 6 input channel modules, individual output channels and the Auxiliary PFL/Headphone output channel. Its main applications lie in the small four-track recording studio where cassette systems are now available for around £600, and live music mixing with PA systems. However, it is flexible enough to be considered for almost any sound mixing requirement. A simplified description follows to illustrate how the mixer is used in the multitrack studio for recording and mixing down as well as in the live concert situation.

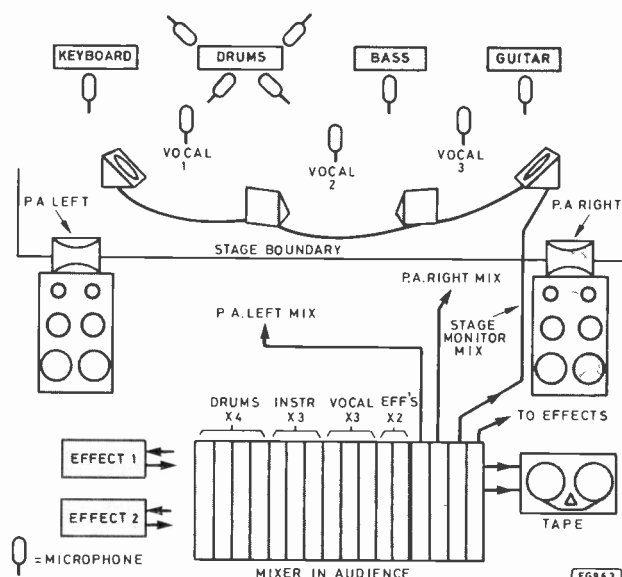


Fig. 4. Live concert mixing

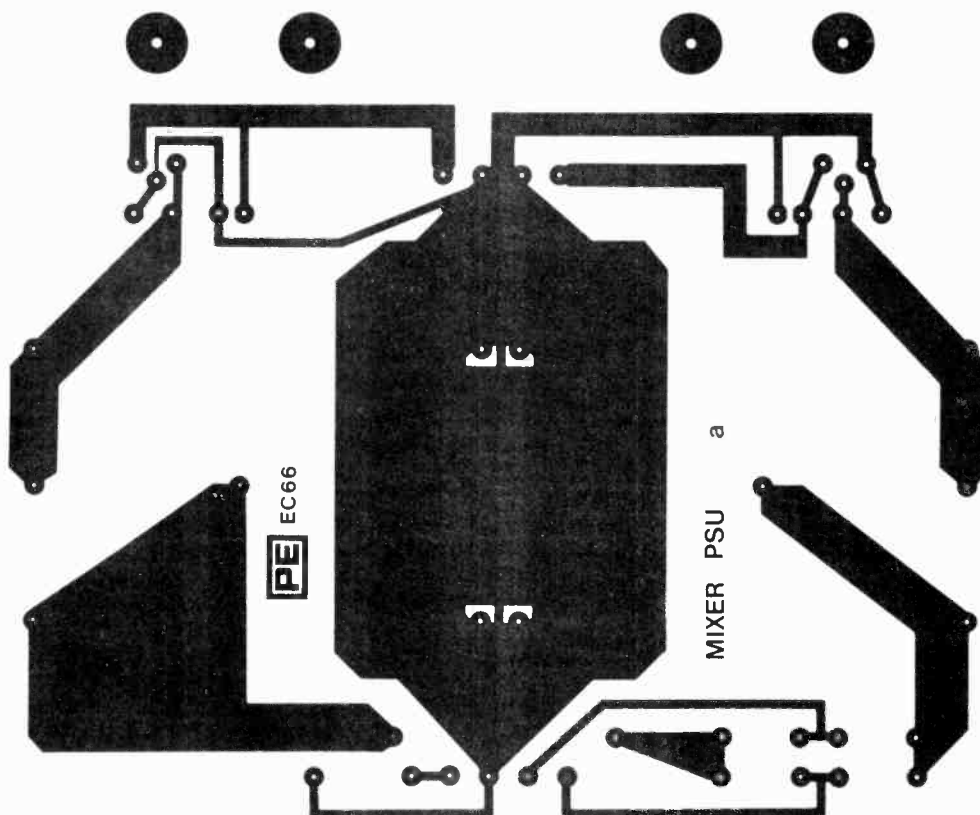


Fig. 1. P.c.b. design for the p.s.u.

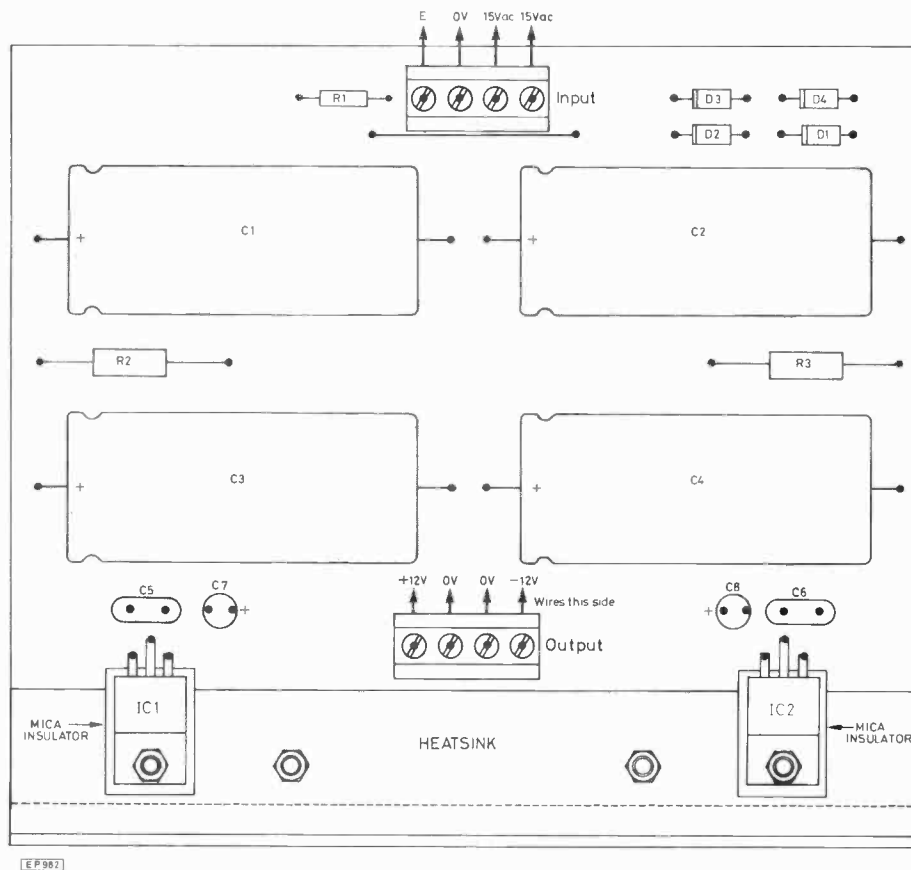


Fig. 2. Component layout

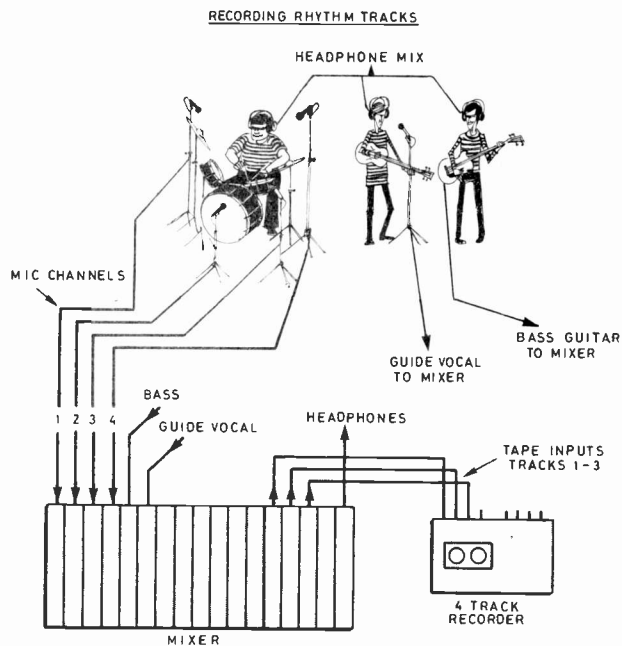


Fig. 5. Recording rhythm tracks

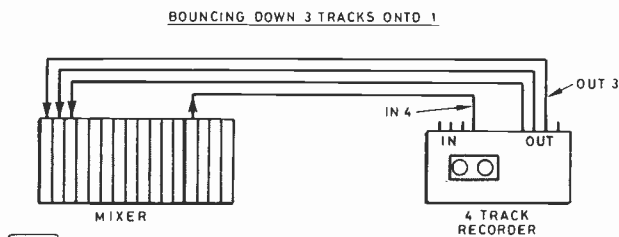


Fig. 6. Bouncing down 3 tracks onto 1

THE MULTITRACK STUDIO

Recording

The first stage of most music recording involves laying down on tape the basic rhythm structure. This usually means drums and bass guitar, along with a rough 'guide' track of vocals to help the rhythm players through the song's arrangement. Fig. 5 shows 4 microphones set up around the drum kit, the bass guitar and the vocal microphone which have all been connected to the mixer input channels. Listening on headphones the recording engineer uses the Pre Fade Listen (PFL) function to examine the sound coming in on

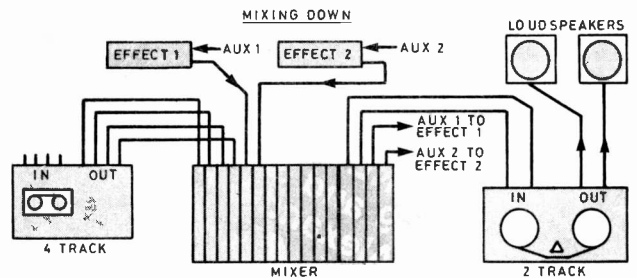


Fig. 7. Mixing down

each mixer channel, to check that all is well and to add equalisation to any sounds that need it. The drum microphones are all routed to one mixer output and recorded onto one tape track, while the bass and vocals are separately recorded on two other tracks. During this process the players listen to each other using headphones, driven from one of the auxiliary outputs of the mixer which allows them a balanced mix of what is being recorded onto tape. Next comes the addition of the other instrument sounds like guitars, keyboards and vocals, but because of the limited number of tracks available on tape a process known as 'bouncing-down' is used to conserve tape track space. Fig. 6 shows how the mixer may be used to mix three tracks together onto the one remaining track, which then makes room for three new tracks. In this way the recording is built up layer by layer until all the necessary ingredients of the sound are on tape and ready for the final 'mix-down'.

Mixing Down

In this final stage of the recording process the four tracks of sound are reduced to a two-channel stereo format which necessitates the use of a second tape recorder. Fig. 7 shows how the mixer is used to transfer the sound across from one recorder to the other, and in doing so it allows a number of useful enhancements to be made for the final result. Firstly there is the question of attaining the right balance between the four tracks and the positioning of each track within the stereo sound image. This is known as panning. Final alterations are also made to the equalisation of each track to highlight the overall tone quality, and there is a further opportunity to add special effects such as reverberation, echo, chorus and phasing etc. The auxiliary mixer outputs are used to send any mixture of the sounds to these effects, whose outputs are then brought back on the remaining mixer input channels. Finally the end result is reached with a stereo tape that may be played on any domestic sound system. Improvements in technique come with practice, and care is taken to ensure that maximum level goes onto tape wherever possible. ★

BAZAAR

100 T1L220, 5 ULN2003A, 50 BC108, 50 BC 308, 20 BC170, 50 1N4004. Plus more. £25. Send cheque made payable to A. Hodgson to: G. Hodgson, 2 Marlborough Avenue, High Harrington, Wokingham, Cumbria CA14 4NW.

WANTED circuit diagrams of valve instrument pre-amplifiers and power amplifiers (30 watts upwards). J. Gillbanks, 28 Allderidge Avenue, Hull, N. Humberside HU5 4EQ.

UK101 8K with Cegmon, fan cooled, 300/600 Baud, RS232. Hex keyboard, books, tapes etc. £120 o.n.o. P. G. Wagstaff, 5 Grove Farm Close, Leeds. Tel: 611271.

OLIVETTI TE300 10 CPS terminal with stand. £35 o.n.o. Tel: Wokingham 782461.

WANTED Rockwell/Aim 65 £50, KIM 1 or SYM 1. Also interested in MK14 or Acorn SYS 1. R. Billingham, 35 Morland Road, Croydon, Surrey CR0 6HA. Tel: 01-654 6822.

PE MINISONIC MK2 perfect £125. Transcendant 2000 immaculate £150. Verner professional DFM £15 wanted small television. Hugh Bridge, 175 Crofton Road, Orpington, Kent BR6 8JB. Tel: Farnborough, Kent (0689) 57055.

SEM Sentinel fet 160m converter, 9V, IF 14MHz £15 inc. i/p. Mr. A. E. Dowdeswell, Silver First, 7a Leatherhead Road, Ashted, Surrey KT21 2TW. Tel: Ashted 72515.

SPARKRITE Voyager car drive computer unused £40. D. V. Potter. Tel: 021 749 3367. Evening or weekend.

TWO MAPLIN synths, one with PA1A Computer, other with large sequencer, £450 each o.n.o. must sell. Ken Hitchmough, 106 Church Street, Littleborough, Lancs. Tel: 0706 79081.

RADIO TV servicing Vol. 1-6 £10 Collected, Post £3. L. Marks, 14 Avenue Rd., Kingston, Surrey.

ATOM 24K VIA PI. Acorn built, £200. Hoddesdon 68414. Also Acetronic MPU 1000 game for sale. Daniel Jarman, 21 Hawthorn Rd., Hoddesdon, Herts EN11 0PJ.

ACORN Atom 12K ROM, 12K RAM, all leads p.s.u. and manual included. Excellent condition £190. David Houghton, 2 Western Villas, Church Road, Kennington, Ashford, Kent TN24 9DG. (0233) 23077.

STRING ensemble fully working, cased, keyboard etc. £200. Also Minisonic II not working, cased, keyboard, offers. Mr. M. Smalley, 28 Oakfield Avenue, Knebworth, Herts. Tel: (0438) 736531 (Work).

MULTIMETER, Kaise SK-6200 3½ digit I.c.d. Auto-range and zero-adjust. £30 o.n.o. Phone Alan 01-866 4579.



See us at the NEW Electronic Hobby Fair
on stands 259 and 302, 18-21 November,
at Alexandra Pavilion.

Now any reason with IC's

With the new LM2A logic monitor from GSC, you can see just what's going on in an integrated circuit for only £75.*


The LM2A's sixteen LED indicators show the static and dynamic logic states of all the pins on 14 or 16-pin IC packages, and GSC's unique Proto-Clip provides rapid, reliable contact with the circuit.

You can use the LM2A with different logic families, too. A front-panel switch lets you select TTL or C-MOS, and a variable threshold control covers any voltage from +1V to +9V for other logic levels. It's small and light enough to hold in the hand, and operation is simplicity itself.

Take the logical course of action — fill in the coupon now.

* Price excluding P&P and 15% VAT.

GLOBAL SPECIALTIES CORPORATION

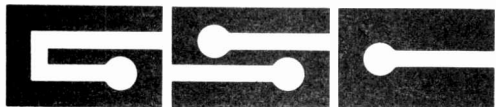

G.S.C. (UK) Limited, Dept 5L,
Unit 1, Shire Hill Industrial Estate,
Saffron Walden, Essex CB11 3AQ.
Telephone: Saffron Walden (0799) 21682.
Telex: 817477.

G.S.C. (UK) Ltd., Dept 5L, Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ

Model LM2A	LOGIC MONITOR	Unit price inc. P & P 15% VAT £88.55	Qty. Req.
------------	---------------	--------------------------------------	-----------

Name _____
Address _____

I enclose cheque/P.O. for £ _____ or debit by Barclaycard/Access/
American Express card no. _____ exp. date _____

FOR IMMEDIATE ACTION — The G.S.C. 24 hour, 5 day a week service.
Telephone (0799) 21682 and give us your Barclaycard, Access, American
Express number and your order will be in the post immediately.

For FREE
catalogue
tick box ☐

BAZAAR

MONOPHONIC Synthesiser 2 x v.c.o. Four octave keyboard interface facilities stereo outputs, sequencer effects voltage controlled panning £300. Mr. P. Redpath, 47 Corbett Road, Waterloo, Hants. Tel: Waterloo 53595.

MICROTAN 65 with Tanbug £40. Prog. graphics gen 256 x 256 £40. Documentation. M. Goonewardane, 241 Norbury Crescent, London SW16 4LF. Tel: 01-764 0839.

TELEQUIPMENT DB Scope Type D43 handbook, working £60 o.n.o. Wanted XTAL filter KIG XF51A for FT75 also golfball motor needed. Horndean (0705) 596058. J. McDonald, Mews Cottage, Pond Lane, Clanfield, Portsmouth PO8 0RG.

FRG 7000 £200. WW2 RAF 1132A £10. AVO valve tester £5, Taylor ditto 45A £5, plus carr. Edwards, 2 Beach Road, Burton Bradstock, Bridport, Dorset. 0308 89625.

REEL TO REEL tape recorders. Sony 250 stereo £40. Sony TC106 Mono £20, V.G.C. Derby 764373. Mr. J. F. Ashfield.

FOR COMPUTIK; AY-3-8910 sound board £20. Tool kit EPROM £10. BASIC 5 EPROM £12. 5V 3A supply £10. Mr. N. Odell, 31 Humphrey Road, Greenhill, Sheffield S8 7SE. Phone (0742) 745027.

ZX81 Unfinished 16K RAM. Full set chips worth £12 plus data for £6. Phone (0223) 832308. A. Fowke.

VALVE millivoltmeter, Marcink TF 899, £5.00. Holdway, Flat 9, Back No. 10, Westwood Road, Portsmouth, Southampton.

MINISONIC Mk. 11. Synth. Eaton Audio p.c.b.'s complete i.c. sockets unused £55 p.&p. Seon Smyth—0436 71181.

10 LM3900 quad. Op-amp new unused, £4, or 45p each. Please send s.a.e. T. Walters, 18 Herondale, Birch Hill, Bracknell, Berks RG12 42T.

UK101 10K metal case 48 x 32 screen sound joystick program graphics Cegmon 8K extra utility roms. £140 o.n.o. A. Smith—Poole (0202) 671659.

9V 100mA mains p.s.u. £3.50 o.n.o. Eight 4118 1K byte static RAM will separate. Offers. Mr. R. A. Boyce, 11 Jevington, Birch Hill, Bracknell, Berkshire RG12 4ZD. Tel: Bracknell 57903.

SINCLAIR ZX81, 16K RAM, 9 months old, complete, excellent condition, £80. Tel: Lyminge 862604. D. P. Harmer, Whitehall Cottage, Rhodes Minnis, Canterbury, Kent CT4 6YA.

TELEQUIPMENT D83 + D1016 for sale also DMM and components send s.a.e. for details. Wanted ZX81/ZX Spectrum. B. K. Jain, 17 Taylors Lane, London NW10 9JH.

NEW, used valves. Numerous types, instrument Crt's 6 inch, 5 inch, 2 1/2 inch dia. Large s.a.e. for details. A. D. Jones, Penwood, The Avenue, Ross-on-Wye, Herefordshire HR9 5AW.

WANTED Oscilloscope, ZX81, IBM typewriter. Send information and price to Petter Enge, Feltspatv, 3B, 3220 Haukeid, Norway.

HONEYWELL 520 X-Y recorder 30cm x 40cm bed. Working but needs pen arm. F.O.C. buyer collects. Tel: 01-577 3171.

AUDIOGENERATOR. Belco AG761. Sine/square waves, 19Hz—220KHz £30. Tel: 051 734 3908 (Liverpool).

ZX81 16K with p.s.u. plus 6 games cassettes. Galaxian, chess, 3D Maze, etc. £100 o.n.o. M. D. Smith, 52 Vesper Road, Leeds, Yorkshire LS5 3NX. Tel: 0532 757303 7p.m.

SMALL oscilloscope, working but needs attention £30 o.n.o. Also home built audio signal generator £15 o.n.o. D. Daniel, Flat 1, 78A Harehills Avenue, Leeds LS7 4EU.

P.E. JOANNA circuit boards and power supply £17. Five octave keyboard £25 Phone 0427 5848. (North Lincs).

32K DYNAMIC RAM pack with p.s.u. Suitable most 6502 systems, £75. 32 2114 L2 static rams (16K). £40. C. Dunne, 87 Ram Gorse, Harlow, Essex CM20 1PZ Tel: (0279) 415335.

WANTED lightweight pair headphones, good quality 4-track R-T-O-R tape recorder. Good quality Echo/Reverb unit, Synthesizer. Keith Edmunds, Orissor College, Corwen, Clwyd LL21 0DR. Tel: 0490 2791.

TELEQUIPMENT scope D67A 25MHz as new tv-field + line. 100% wkg £425.—Gould-Advance—J3A Audiogen. As new 100% wkg £125. G. Finke, Reading 23335 (Evenings).

ATARI Games system plus eleven cartridges including: adventure, invaders, soccer, chess. Worth over £300 only £230. Mr. M. Ward, 9 St Andrews Avenue, Crewe, Cheshire CW2 6JJ.

EXCHANGE double beam scope 10MHz Philips. Mint condition for ZX81 16K with peripherals or sell £130. Roy Lowe, 43 Poplar Way, Leeds 13. Phone: Leeds 638678.

HEATHKIT SW717 shortwave receiver £85.00. Data Dynamics 390RO printer £85.00. West Hyde jubilee v.d.u. cabinet, keyboard £45.00. Mr. R. W. Hearn, 10 Speedwell Close, Pakefield, Lowestoft, Suffolk NR33 7DU. Tel: Lowestoft 66026.

UK101, cased, 8K RAM, 300/600 Baud, new mon, EASICOMP sound £120 Also Radofin teletext adaptor £100. Tel: 01-455 7544.

T.V. GAME electronics and case including 18 switches £8. D. Choi, 13 Highfield Drive, Davyhulme, Manchester M31 2AF.

COMPUTER CASE. Black Microtype model 3. Pre-cut UK101 keyboard. Space for fan, numeric keypad, add-ons. Unused, £20. Mr. D. Hunt, 1 Love St., Kilwinning, Ayrshire KA13 7LQ. Tel: 0294 52250.

MIDWICH COMPUTER COMPANY LIMITED

FAST EX-STOCK DELIVERY OF MICROCOMPUTER COMPONENTS AT UNBEATABLE PRICES

MIDWICH NOW APPOINTED OFFICIAL ACORN BBC MICRO DEALER

ACORN ATOM UPGRADES

Description	Price
* Atom disc pack (AAH06)	299.00**
* Atom colour card (AAH07)	39.25**
* 4K Atom DOS (AAS41)	60.00**
* 4K FP ROM (AAS22)	20.00
* BBC ROM Set (X000X)	49.95**

BBC Microcomputer Upgrades

* Memory Upgrade (BBC1)	21.50
* Printer & User I/O kit (BBC2)	7.60
* F Disc interface inc DOS (BBC3)	99.95
* Analogue input kit (BBC4)	7.60
* Serial I/O & RGB kit (BBC5)	10.25
* Expansion bus & tube kit (BBC6)	5.95
* Printer cable inc Amphenol plug (not assembled) (BBC21)	13.00
* User port connector & cable (BBC22)	2.00
* Analogue input plug & cover (BBC44)	2.25
* 5 pin DIN plug for serial (BBC111)	0.60
* 6 pin DIN plug for RGB int. (BBC109)	0.60
* 7 pin DIN plug for cassette (BBC141)	0.60
* Connector for bus & cable (BBC066)	3.50
* Single disc drive (I00K) (BBC31)	225.00**
* Dual disc drives (BBC32)	375.00**
* Teletext Receiver (200K) (BBC71)	144.34**
* Prestel receiver (BBC72)	90.00**
* Games Paddles (per pair) (BBC45)	11.00

** Prices on these items are likely to change please contact sales office before ordering.
As some items are on extended delivery from Acorn please check availability before ordering items marked **

ACORN SOFT FOR THE ATOM

Word pack ROM inc manual (AC100)	26.00
Atom Forth (AC101)	6.00
Forth Theory & Practice (AC102)	6.00
Forth Utilities (AC103)	10.00
Atom Synthesiser (AC104)	10.00
Atom Database inc manual (AC105)	10.00
Utility pack 1 (Disassembler Fast cos)	10.00
Reverb (AC106)	10.00
Games pack 1 (Asteroids, Sub-hunt, Breakout) (AC107)	10.00
Games pack 2 (Droptight, Zombi, Mastermind) (AC108)	10.00
Games pack 3 (Rat Trap, Lunar Lander, Black Box) (AC109)	10.00
Games pack 4 (Star Trek, Four Rws, Space Attack) (AC110)	10.00
Games pack 5 (Invaders, Reversi, Wumpus) (AC111)	10.00
Games pack 6 (Dodgems, Simon, Amoeba) (AC112)	10.00
Games pack 7 (Life Forms, Ballistics, Snake) (AC113)	10.00
Games pack 8 (StarGate, Go Miku, Robots) (AC114)	10.00
Games pack 9 (Snapper, Baines, Minotaur) (AC115)	10.00
Games pack 11 (Missile base, Snooker, Dominoes) (AC116)	10.00
Atom Adventures (Dungeon, Intergalactic House) (AC117)	10.00
Atom Chess (AC118)	10.00
Atom Calc (AC119)	34.00
Atom Lisp (AC120)	15.00
Lisp Theory & Practice (AC121)	6.00

ACORN SOFT FOR THE BBC MICROCOMPUTER

Graphs & charts on the BBC Micro (AC122)	7.50
Graphs & Charts Cassette (AC123)	7.50
Algebraic manipulation pk (AC124)	8.65
Forth on BBC Micro (AC125)	7.50
Lisp on BBC Micro (AC126)	14.65
Lisp on BBC Micro (AC127)	7.50
Lisp on BBC Micro (AC128)	14.65
Games-Philosophers quest (AC129)	8.65
Games-Defender (AC130)	8.65
Games-Monster (AC131)	8.65
Games-Snapper (AC132)	8.65

NEW EPROM PROGRAMMER FOR BBC MICROCOMPUTER

* Programs 2516 2716 2532 2732 Industry Standard EPROMS	
* No external power supply required	
* Plugs straight into expansion socket	
* Easy to use	
* Includes all Software required	
EPROM Programmer (Kit)	49.95
EPROM PROGRAMMER (Assembled)	57.95

ACORN & BBC MICRO COMPONENTS	Price
2114 Low Power	
200ns	0.80
4516/4816 100ns	2.69
6522	3.19
74LS244	0.69
74LS245	0.69
81LS97	0.90
OP8304	4.50
DS3691N	4.50
DS88LS120N	4.50
20 way Right Angle	
IDC Header	2.46
26 way Right Angle	
IDC Header	3.24
34 way Right Angle	
IDC Header	3.80
15 way Right Angle	
D SKT	3.50

NEW CATALOGUE NOW AVAILABLE

Please send 0.25 + SAE

SPECIAL OFFERS

200ACPU	3.45
6821	0.74
6522	3.18
UPD7002	4.35
DP8304	4.50

Device	Price
Z80 FAMILY	
Z80CPU	2.95
Z80ACPU	3.45
Z80CTC	2.64
Z80ACTC	2.95
Z80ADART	5.70
Z80ADMA	11.95
Z80PIO	2.75
Z80API0	2.95
Z80ASIO-0	11.99
Z80ASIO-1	11.99
Z80ASIO-2	11.99
MK3886	11.00
MK3886-4	14.47

6800 FAMILY	
6800	2.99
6802	3.49
6803C	12.10
6809	8.45
6810	1.12
6821	1.20
6840	3.95
6845	6.75
6850	1.40
6880	1.07
6887	0.80
68488	9.11
6875	5.62
6843	13.99
68800	6.30
68802	19.11
68821	2.29
68810	2.00
68840	4.70
68850	2.86

6500 FAMILY	
6502	3.45
6520	2.99
6522	3.19
6532	5.95
6080 FAMILY	
6085A	4.40
8212	1.55
8216	0.60
8251A	3.19
8255A	2.95

BUFFERS	
81LS95	0.90
81LS97	0.90
81LS98	0.90
8126A	1.20
8128A	1.20
8195	1.35
8197A	1.35
8198	1.45

DATA CONVERTERS	
ZN425	3.45
ZN426	3.00
ZN427	5.99
ZN428	4.75
ZN429	2.10
ZN432	13.00
ZN433	25.90
ZN435	4.40
UPD7002	4.35
ZN447	72.9
ZN448	5.45
ZN449	2.56
ZN440	56.63

FLOPPY DISC CONTROLLERS	
ED1771	17.12
WD1391 KIT	45.50
WD1393 KIT	45.50
WD1395 KIT	45.50
WD1397 KIT	45.50
(KITS INCLUDE)	
FD179X + WD2143	
+ WD1691	

MISC SUPPORT CHIPS	
AY3-1015	2.99
AY3-1270	7.95
AY3-8910	5.99
AY5-1013	2.99
AY5-3600	7.95
DP8304	4.50
MC1488	0.55
MC1489	0.55
MC3446	2.95

MEMORIES

2114 Low Power	
200ns	0.80
2708 450ns	2.79
2716 450ns	
2716 350ns	2.10
2716 350ns (+SV)	3.59
2716 450ns 3 Rail	5.95
2732 350ns	4.40
2732 450ns	3.75
2532 450ns	3.60
2564 450ns	9.99
2764 450ns	9.99

VOLTAGE REFERENCES

ZN404 2.45V	0.49
ZN423 1.25V	1.00
ZN4588 2.45V	1.08
ZN Ref 0.25 2.49V	1.60
ZN Ref 0.40 1.10V	1.60
ZN Ref 0.62 1.17V	1.60
ZN Ref 1.00 1.96V	2.56

OVM CHIPS

ZN450E	7.61
ZN450 KIT	17.35
LINEARS	
LM301AN	0.25
LM308N	0.89
LM311N	0.69
LM319N	2.14
LM324N	0.30
LM348N	0.59
LM553N	0.16
LM556CN	0.45
LM741 (8 PIN)	0.14
LM747CN	0.64
LM748 (6 PIN)	0.34
LM725CN	3.20

REGULATORS

7805	0.39
7812	0.39
7815	0.39
7815	0.29
7812	0.29
7815	0.29
7905	0.55
7912	0.55
7915	0.55
LM309K	0.99
LM317K	3.20
LM323K	4.95
LM338K	POA
4522	1.24
4526	0.69
4527	0.64
4528	0.59
4532	0.69
4541	0.99
4543	0.79
4553	2.44
4555	0.50
4556	0.50
4585	0.78

UHF MODULATORS

6MH2(UM1111)	3.70
8MH2(UM1233)	4.40

CRYSTALS

1MHz	2.90
1008MHz	2.90
18432MHz	2.20
24576MHz	2.45
36864MHz	2.95
4MHz	1.45
6MHz	1.45
8MHz	1.70
96604MHz	1.95

CMOS 4000 'B' SERIES

4001	0.10
4002	0.12
4006	0.65
4007	0.15
4008	0.60
4009	0.39
4010	0.39
4011	0.11
4012	0.15
4013	0.24
4014	0.74
4015	0.49
4016	0.19
4017	0.37
4018	0.67
4019	0.41
4020	0.49
4021	0.69
4022	0.65
4023	0.15
4024	0.31
4025	0.16
4026	1.29
4027	0.23
4028	0.49

MEMORIES

4116 150ns	1.10
4116 200ns	0.70
4118 150ns	3.38
4164 200ns TI	4.65
4164 200ns NEC	4.95
4516/4816 100ns	
5516 250ns	2.69
6116 P3 150ns	9.38
6116 LP3 150ns	3.85
	5.75

SPECIAL LOW PRICES FOR QUANTITIES

Device	Price
4031	1.69
4033	1.69
4034	1.90
4035	0.94
4040	0.49
4041	0.77
4042	0.44
4043	0.69
4044	0.64
4045	1.69
4046	0.64
4047	0.49
4048	0.54
4049	0.24
4050	1.24
4051	0.44
4052	0.59
4053	0.77
4054	0.84
4055	0.84
4056	0.59
4057	0.98
4058	0.29
4059	0.21
4060	0.12
4061	0.15
4062	0.12
4063	0.12
4064	0.12
4150	0.12

NEW JOYSTICKS AND CONTROLLER FOR ZX81 AND SPECTRUM

* Controls 1 or 2 Joysticks	
* Fire Button Facility (1 or 2)	
* Easy to use	
* Plugs straight into Expansion Slot	
* Edge Connector provided for RAM Pack Discs etc	
Joystick Controller (Kit)	19.95 ea
Joystick Controller (Assem)	24.95ea

SEMICONDUCTOR UPDATE

R.W.Coles

FEATURING MC1468705G2 D60T OP-22

ONE CHIP WONDER

I have always considered one chip microprocessors (that is to say those devices that cram CPU, RAM, ROM and I/O onto a single silicon chip), to be ideal for hobby projects. I say this because these devices are relatively simple to program and understand, and because they do not require any of the complex interconnections which would be necessary to support a multi-chip system based on, say, a Z80. All the budding designer has to worry about is interfacing to the outside world and program design, what could be easier?

Unfortunately there are some snags: The first one-chippers, such as the Intel 8048, had *masked* ROM which meant you had to buy them by the truck-load. These were soon followed by EPROM versions, such as the 8748, which improved things a lot, but even with these you still had to have a suitable PROM programmer. They also had the limitation of being made in NMOS only, so small battery powered systems were out because of the current drain. There has in fact always been at least *one* good excuse for not using them in the latest pet project!

Well the excuses have now run out, and as far as I can see there is absolutely no valid reason for not planning to build that pseudo-random, microprocessor controlled lawn sprinkler you have always promised yourself, thanks entirely to Motorola and their brand new MC1468705G2. (By the way, if you find that long part number off-putting, look at it this way: The MC14 bit just means its Motorola and CMOS, the 7 means that it has EPROM rather than masked ROM, and the G2 means that it is better than a G1(?) Take that lot away and you're left with a Motorola 6805, which my "Boys Wonder Book of Micros" tells me is just a sawn-off 6800 with added RAM, ROM and I/O).

The MC1468705G2 has 2106 bytes of U.V. erasable EPROM, 112 bytes of RAM, 4 eight bit I/O ports and a timer, all squeezed inside a 40 pin d.i.p. Enough to implement a pretty nifty sprinkler system! Even better, the chip has a 128 byte chunk of masked ROM pre-programmed with an EPROM programming algorithm so you don't even have to buy one of those. This means that you can make up a simple circuit board with a socket for the MC1468705G2 and a few external components which, given appropriate input data and a -13 volt programming supply, will act as your very own EPROM programmer.

Best of all though, the new chip is made in low power CMOS and has two additional instructions which also help to reduce supply current. The operating power consumption is typically 10 milliwatts, but execute a

WAIT instruction and this drops to 4 milliwatts even though data is retained and the clock and timer continues to run. Execute a STOP instruction and everything does just that, causing the power consumption to plummet to just 10 microwatts *without* destroying memory or register data. After issuing a STOP you can get the whole thing running again by generating an external interrupt or using the RESET input.

Anyone who knows the 6800 will get on fine with the MC1468705G2, although there are some differences. The new device only has a 13 bit address width to cover RAM, ROM and I/O, but this is more than enough for the on-chip resources and even allows for the addition of external EPROM if ports can be sacrificed as busses.

WHOPPER

In these days of glamorous microprocessors and ever more complex integrated circuits, it is easy to forget the humble transistors and diodes which were of course the start of it all. But these simple components are still essential at the "business-end" of most systems, and the development of newer and better devices continues despite the fact that the lions share of research funding has been diverted towards producing the ultimate microprocessor or memory chip.

The designers at Westinghouse have certainly not neglected semiconductor development it seems, because their latest device, the D60T, has pushed the frontiers of power transistor technology further out than ever before by providing the capability to switch 40 amps and 650 volts at 20kHz! There is nothing simple about the D60T either. Its semi-conductor chip is nearly 1 inch in diameter for example, bigger by far than most microprocessor chips, and the manufacture involves a triple diffusion process. Even the package is bigger and better, because that massive chip is mounted in a hex-nut housing which measures over 1.5 inches across the points and stands nearly 2 inches above the heat sink surface. (Yes, you *definitely* need a heat sink if you want to get anywhere near the D60T's maximum 885W dissipation at 25 degrees C!)

But mere physical details do not do justice to the mighty D60T, and the real story can only be revealed by examining the electrical specs. Would you believe a maximum collector current of 100 amps? or a maximum *base* current of 20 amps? Well then, how about a sustained collector-to-emitter voltage (V_{CE0}) of 800 volts, or even 1200 volts if you reverse bias the base? Yes folks, the D60T can do all this and more!

Probably the most important feature of the D60T though, is not all those noughts after the amps and volts numbers, but the speed at which it operates. Switching at 20kHz may not sound fast to all you logic fans who are used to Shottky TTL switching in a nanosecond or two, but at 40 amps and 600 volts its *very* fast

There are two problems with D60T, and the first is what on earth can you use it for. The manufacturers intend people to use it in place of Thyristors for motor speed controllers hooked up to 30 horsepower induction motors, but maybe you could use it in a 25 kilowatt class D disco amplifier, or to control your arc welder or... or... or something.

The second problem is that a single D60T could set you back around £50. Makes microprocessors look like child's play, doesn't it!

TIDDLER

Well if microprocessors make your head spin and the hairy-chested D60T makes you worry about your electricity bill, why not try an OP-22 from Precision Monolithics Inc?

PMI are famous, as their name suggests, for high grade analogue integrated circuits and especially op-amps. Their usual ploy is to take a standard design and to produce from it a higher performance version which they can sell to those who need that little bit extra and are prepared to pay a bit more for it. The OP-22 has been introduced as a high specification version of micropower op-amps like the National LM4250, with which it is pin compatible.

"Micropower" generally means supply currents of a few tens of micro-amps for battery supply applications, and the new PMI device brings precision operation to these areas for the first time. The supply current of the OP-22 can be set externally with a single resistor anywhere between 1 and 400 microamps, but as you may expect, bandwidth is also affected, so to get 10kHz you would need at least 300 microamps and even PMI cannot overcome that constraint.


Where PMI can deliver the goods however, is in the areas of open loop gain, input offset voltage, and common-mode rejection. The OP-22 has a gain of more than a million, a guaranteed offset voltage of 300 microvolts or less, and it can realise a common-mode rejection ratio of over 100dB for voltages to within 1.5 volts of the supply rails. Supplies of from 3 to 30 volts, single or split, can be used, and the OP-22 is available in either an 8 pin mini-d.i.p. or a TO99 metal can.

MICRO CONTROLLER

MICHAEL TOOLEY B.A.

DAVID WHITFIELD M.A. M.Sc.

PART TWO

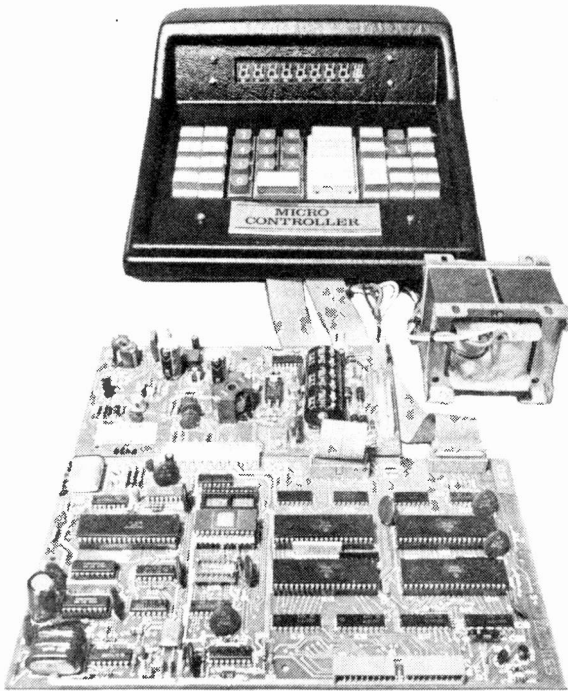

THIS month we describe in detail how to use the DISBUG monitor facilities. The instruction set for the 6800 is listed in full in Micro-file and there is a description given here of the full range of addressing modes. A step-by-step example of how to enter and run a program on the Microcontroller is included. Finally, the circuit and operation of the power supply module is described.

DISBUG MONITOR FACILITIES

The DISBUG monitor provides the user with facilities to allow the entry of programs into the user RAM area, the examination and change of memory locations (including PIA registers), the debugging of prototype routines, and the control of execution of developed programs. The user communicates with DISBUG via the keyboard, and the monitor uses the display to respond with prompts and information.

The Microcontroller contains 1024 bytes of read/write memory (addresses 0000 to 03FF inclusive). Some of this memory is required to allow DISBUG to operate, but the remainder (0000 to 03A0) is available for user applications. Fig. 2.1 shows the allocation of address space in the RAM area.

The DISBUG monitor facilities are grouped into editor modes (memory, register, preset and breakpoint) and command functions (go, proceed and restart). Each mode or function is invoked separately, and they are each described in detail below.

DISBUG DISPLAYS

The displays output by DISBUG follow a standard format. The normal prompt used when DISBUG is awaiting a command from the keyboard is "... dIS ...". When an editor key (MEMORY, REGISTER, PRESET or BREAKPOINT) is pressed, the display will change to the form "p-aaaa-dd". The "p" field will contain a prompt character to remind the user what input is expected next (e.g. "A" for address), the "aaaa" field will hold the address value, and the "d" field will hold the data value. Initially the second and third fields will often be empty. e.g. when the preset editor is invoked, the

display will show "L- -", indicating that the lower address value is expected. The data field will sometimes be used to display advisory information, rather than a strict data value. Such information (e.g. the breakpoint number) will not use standard numeric representation, to avoid confusion.

The numbers which are mentioned in the descriptions which follow, and those which appear in the DISBUG displays, are all in hexadecimal notation. All addresses must comprise of four hex digits (e.g. 008F), and all data values must comprise of two hex digits (e.g. 07); leading zeroes *must* be used where necessary to fill the fields to the appropriate lengths.

THE MEMORY EDITOR

The contents of any memory location may be examined and (optionally) changed using the memory editor. The memory editor is also used for entering programs into the user RAM area (0000 to 03A0). Remembering that the 6800 treats PIA registers as memory locations, the memory editor may even be used directly to control the operation of the Microcontroller's PIAs; modifications to the programming of the keyboard and display PIAs, however, may interfere with the normal operation of DISBUG. Writing new values to

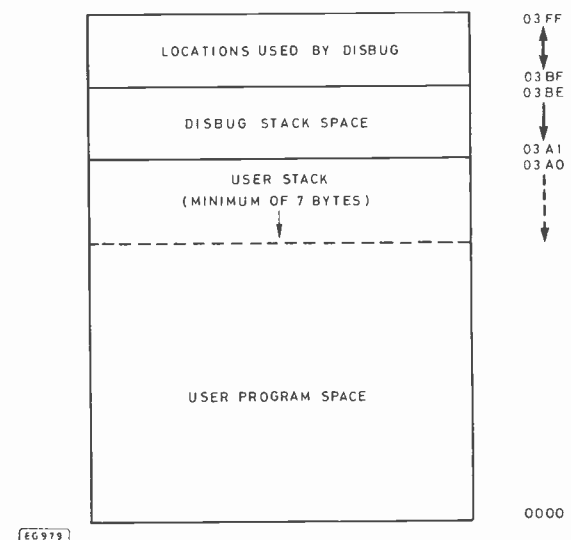


Fig. 2.1. Microcontroller RAM address allocations

EPROM addresses and unused addresses in the address map will have no effect, but beware of address images.

The memory editor may be invoked whenever the "... dIS ..." prompt is displayed by pressing the MEMORY key. The display will then change to "A- ", indicating that the memory editor is expecting the address of the memory location to be examined to be input. The numeric keys 0 to F are then used to specify the appropriate 4-digit address. After the fourth digit has been struck, the prompt character will change from "A" to "d", and the current contents of the specified location will be displayed in the data field of the display. The "d" prompt indicates that, if the user wishes to change the contents of this location, a new 2-digit value may now be input. When the first digit of the new value is entered, the data field will be cleared, and the new digit displayed, e.g. the display might show "d-01Fb- 7". No change is necessary, however, and by default the contents of the location will remain as currently displayed.

After any new value, if any, has been entered, the location may be closed with the ENTER key. This will cause the "A- " prompt to re-appear, ready to examine another location. If the NEXT key is used in place of the ENTER key, the next sequential location will automatically be opened and displayed. The PRIOR key will cause the previous location to be opened and displayed.


The CANCEL key may be used at any time to abandon an uncompleted memory change and return to the "... dIS ..." prompt. To exit from the memory editor when the "A- " prompt appears, either the ENTER or CANCEL keys may be used.

To gain familiarity with the operation of the memory editor, readers are encouraged to step through the DISBUG EPROM (addresses F800 to FFFF), safe in the knowledge that the contents of these locations are permanently programmed.

THE REGISTER EDITOR

After a breakpoint has been encountered in a program under development, the contents of the CPU registers may be examined/changed using the register editor. The REGISTER key may be pressed to invoke the register editor whenever the "... dIS ..." prompt is displayed. The register values with which the program will 'proceed' may then be examined, and optionally changed. Users should note that changing the address held in the program counter will affect the address from which the program will proceed.

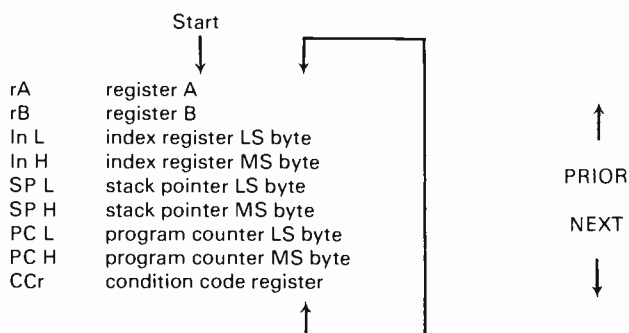The display of register contents used by DISBUG is cyclic in nature, and shows only one 8-bit (2 hex digit) value at a time. The sequence is as follows:



The initial display will show the current contents of the A register. Typically the display would be "d- rA -32", indicating that the current contents of register A is 32, and that this may be changed by entering a new 2-digit data

value (hence the "d" prompt character). The ENTER key will cause the currently displayed value to be saved and the register editor to be exited. The NEXT key will cause the current value to be saved, and the contents of the next register (B in this case) to be displayed. The PRIOR key will cause the displayed value to be saved and the contents of the previous register (the condition code register in this case) to be displayed. The previous value of any register will remain unchanged if no new value has been specified.


The CANCEL key may be used at any time to exit from the register editor, and this will abandon any change which has not yet been completed.

THE BREAKPOINT EDITOR

Temporary halts or breakpoints are often useful as an aid to debugging a program. They allow the programmer to split programs into convenient blocks so that each block may be tested separately. In practice, breakpoints are implemented by using the monitor program to replace instruction codes at the specified point(s) with software interrupt codes (3F's on the 6800). The replaced instruction codes, and their addresses, are remembered by the monitor so that the breakpoints may be removed when required. The software interrupt allows the contents of the CPU registers to be examined at the breakpoint because these are pushed onto the stack; users should remember to allow 7 bytes of stack to be used by the breakpoint editor.

Breakpoints are set and reset by pressing the BREAKPOINT key to enter the breakpoint editor. This may be done whenever the "... dIS ..." prompt is displayed. DISBUG allows the user to insert up to four breakpoints in a program; these breakpoints are numbered from 0 to 3, and are identified in the displays as b0 to b3, respectively. It is important to note that, for 2-byte and 3-byte instructions, the breakpoint must be set at the FIRST byte of the instruction, i.e. at the op code byte.

When the breakpoint editor is entered it displays the address at which the first breakpoint (b0) has been set. A typical display of "A-01E5-b0" would indicate that breakpoint 0 has been set at address 01E5. If no breakpoint has been set, the address shown will be FFFF; this address is within the DISBUG EPROM, and is therefore not a possible breakpoint address. The address of the breakpoint may be changed by entering a new 4-digit address (hence the A prompt character), followed by ENTER, NEXT or PRIOR. These keys will respectively: change the current breakpoint address to any new value specified and then exit from the breakpoint editor; change the current breakpoint address to any new value specified and then display the next breakpoint; or change the breakpoint address to any new value specified and then display the previous breakpoint. A breakpoint is reset by specifying an address of 'FFFF'. No change to a breakpoint is required, however, and unless a new 4-digit address is specified, the breakpoint address remains unchanged. The CANCEL key may be used at any time to exit from the breakpoint editor; any uncompleted breakpoint change will be abandoned.

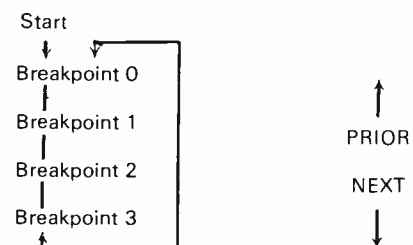

The display of breakpoints is cyclic, i.e. the next breakpoint from 3 (the last one) is breakpoint 0, and the prior breakpoint from 0 (the first one) is breakpoint 3.

THE PRESET EDITOR

Areas of read/write memory may be preset to the user-defined values using the preset editor. This is particularly useful for initialising RAM to known values, e.g. all zeroes, filled with NOP instruction codes (01's), etc.

The area of memory to be preset is specified by entering the lower and upper addresses for the block. If the two addresses are equal, only the specified address will be preset with the data value; in effect the same as using the memory editor, but much slower. If the lower address is specified as greater than the upper address, all memory locations *except* those between the two limits, but including the limits, will be preset. This will also have the effect of causing DISBUG to crash if the memory over-written includes the DISBUG RAM!

The preset editor may be entered whenever the normal DISBUG prompt is displayed. Pressing the PRESET key will cause the display to change from ". . . dIS . . ." to "L- -". This indicates that the lower (start) address of the block of memory to be over-written should be entered. After the appropriate four digits have been entered, the ENTER key should be pressed to record the address. The display will then change to "U- -", indicating that the upper (end) memory address should be entered. After the appropriate four digits have been entered, the ENTER key should again be used to record this address. DISBUG will then output a display of "d- -" to indicate that the data value to be written to memory should be entered. When the appropriate two digits have been entered, the ENTER key should be pressed. This will cause the data value to be recorded, and the block of memory identified to be over-written with the specified data value. Over-writing DISBUG EPROM addresses and "unused" addresses in the address map will have no effect. After the preset operation has been completed, DISBUG will return to its usual ". . . dIS . . ." prompt.

A preset operation may be abandoned at any stage by using the CANCEL key; no change to any address specified occurs until the ENTER following the data value is pressed.

THE GO FUNCTION

A user program is started using the GO function key. After GO has been pressed, DISBUG will prompt for the program start address by displaying "A- -". The user should then enter the 4-digit address from which execution of the program should commence. After entering the four address digits, the program may be started by pressing the ENTER key. Alternatively, using the CANCEL key will abandon the start request.

When DISBUG starts a program the 6800's registers are set up to the following initial values:—

rA = 00
rB = 00
In = 0000
SP = 03A0 (Start of the user stack)
PC = The requested start address
CCr = 00 (Interrupts enabled and all status bits clear)

Before the user program is actually started, DISBUG inserts any breakpoints which may have been set. A breakpoint which has been set at the program start address will be ignored, but it will be remembered for a future occasion (e.g. for starting at a different address or proceeding from a breakpoint). DISBUG then starts the program from the address now held in the PC, with all of its other registers in the states specified above.

THE PROCEED FUNCTION

The proceed function allows the user to continue with the execution of a program after a breakpoint has been encountered. Alternatively, proceed can be used to start a program from a defined point, but with the CPU registers in user-defined states. This is achieved by first using the register editor to set up the required register values, with the start address in PC, and then using proceed to start the program. The proceed function may be called whenever the ". . . dIS . . ." prompt is displayed.

After the PROCEED key has been pressed, DISBUG will respond by producing a display of the form "E-aaaa-Pr". The "E" prompt indicates that the next input expected is the ENTER key. The "aaaa" value will show the address from which the program will resume execution. The "Pr" reminds the user that a proceed has been requested. Pressing the ENTER key will cause the program to proceed (after a brief delay). The display will go blank unless the user program writes to the display PIA. The CANCEL key in place of ENTER will abandon the proceed request and return to the ". . . dIS . . ." prompt.

If the user has changed any register contents since the last breakpoint, the program will resume with these new values; any change to the program counter will change the address from which execution restarts. Before DISBUG passes control back to the user program, any breakpoints which have been set (with the exception of any set at the restart address) will be re-installed.

When an executing program encounters a breakpoint (or other software interrupt instruction), it will cause control to return to DISBUG. The monitor will then remove all of the breakpoints which have been set, and replace the original op codes. Any SWI instructions inserted directly will remain. DISBUG will then output a display of the form "E-aaaa-Br", where "aaaa" specifies the address of the breakpoint, and "E" indicates that the ENTER key will cause the ". . . dIS . . ." prompt to re-appear. The address of the breakpoint (or other SWI) encountered may always be re-inspected by examining the PC contents with the register editor. A command key may be used in place of ENTER to enter an editor or function directly instead of via the prompt.

THE RESTART FUNCTION

The restart function is provided to allow the user to re-initialise the DISBUG monitor program. A restart will have the same effect as entering the monitor from switch-on, but without the need to interrupt the mains supply. The RAM area used by DISBUG (03A1 to 03FF) is reset to its start-up values, and the display and keyboard PIAs are correctly configured; the user RAM area is totally unaffected. Restarts are thus a convenient way of ensuring that user programs have not corrupted the DISBUG RAM or PIAs.

A restart may be requested whenever the normal ". . . dIS . . ." prompt is displayed. Pressing the RESTART key will result in the display of the restart prompt, "rEstArt". The restart may then be activated by pressing the ENTER key, or abandoned by pressing CANCEL. ENTER causes the welcome message "dISr1.0" to be displayed for approximately 2 seconds, followed by the normal DISBUG prompt of ". . . dIS . . .".

THE 6800 INSTRUCTION SET

The 6800 instruction set contains 197 different instructions which fall into four major categories:

- (a) accumulator and memory
- (b) index register and stack
- (c) jump and branch
- (d) condition code register

The full instruction set is shown in Micro-file. This table also summarises the op codes, number of bytes, number of machine cycles required for execution, and the effect of the instruction on the registers and memory. Each instruction is also represented by a mnemonic code (e.g. CLR for clear), which is of no significance to the 6800, but which provides a useful standard notation for writing programs.

In many cases, more than one instruction op code is associated with each mnemonic (e.g. LDA A can have op codes of 86, 96, A6 or B6). The actual op code selected will depend on the addressing mode required; in the case of LDA A the modes available are immediate, direct, indexed and extended, respectively. When an assembler is used to translate from mnemonic codes to hex op codes, and there is a choice of addressing modes, some means must be provided to indicate the mode required. This is usually specific to the assembler being used, but for example # is often used to indicate the immediate mode. In manual translation, the programmer selects the appropriate op code from the table, but such a notation is still useful when writing the program in mnemonics.

The following sections describe the features of the six addressing modes which are available. When translating from mnemonic codes to op codes, the programmer should select the most appropriate mode, bearing in mind the length and flexibility of the resulting instruction. No attempt is made to provide a full description of the operation of each instruction; users are referred to a 6800 programming manual for further details. It should be remembered that the 6800 treats the peripheral registers in the PIAs as memory locations and the same instructions are used for manipulating their contents, e.g. B7 18 02 writes the contents of register A to the A control register in the display PIA.

INHERENT ADDRESSING MODE

Some instructions do not require additional address information for them to be completely meaningful since the required data is already present in the microprocessor's own internal registers. The following are examples of the inherent addressing mode:

CLRA	sets register A to zero (i.e. it clears the register).
PSHA	pushes data onto the stack. The contents of register A is stored on the stack at the address specified by the stack pointer and the stack pointer is then decremented by one.
INX	increments the index register by one.
SEI	sets the interrupt mask in the condition code register. The processor is then inhibited from servicing an interrupt emanating from a peripheral device, and will continue to ignore interrupts and execute the program instructions until interrupts are re-enabled by means of a clear interrupt mask instruction (CLI).
NOP	causes the program counter to be incremented without affecting any of the other registers. It is useful during program development as a "stand-in" for some other instruction that is to be determined during debug, and also for equalising execution time through alternate paths in a control program.

IMMEDIATE ADDRESSING MODE

In this addressing mode the operand immediately follows the op code, and may consist of one or two bytes. Two byte operands are only used for instructions relating to the index

register and stack pointer (CPX, LDX, LDS). In all other cases a single byte follows the op code. Examples of immediate addressing are:

LDA A FF	this instruction loads register A with the value FF (the instruction would be coded as 86 FF).
LDX 0300	this instruction loads the index register with the value 0300 (the instruction would be coded as CE 03 00).

DIRECT ADDRESSING MODE

Using this mode of addressing the operand of the two-byte instruction is stored in a memory location with an address which has a most significant byte equal to 00, and the least significant byte equal to the second byte of the instruction. With direct addressing, the valid memory address range is 0000 to 00FF, and consequently only a restricted range of memory is accessible. This addressing range falls within the user RAM area of the Microcontroller.

Examples of the use of direct addressing are:

LDA A 43	this instruction loads the contents of location 0043 into register A (the instruction op code would be 96 43).
CMP B BC	this instruction compares the contents of register B with the contents of memory location 00BC, and sets the condition code register bits as appropriate (the instruction op code would be 91 BC).

EXTENDED ADDRESSING MODE

In this mode the memory address of the operand is specified by the second and third bytes of the instruction. The most significant byte of the memory address is specified by the second byte of the instruction, and the least significant byte of the memory address is specified by the third byte. Instructions using the extended addressing mode are able to access the full 64K bytes of the 6800's address range, i.e. 0000 to FFFF. Examples of instructions using the extended addressing mode are:

LDA B 00BC	this instruction loads register B with the contents of memory location 00BC (the instruction op code would be F6 00 BC). Note that this instruction would use only 2 bytes if it used direct addressing, but is a valid instruction, nevertheless.
INC 03B7	this instruction increments by one the contents of memory location 03B7 (the instruction op code be 7C 03 B7).
LDX 01A5	this instruction loads the most significant byte of the index register with the contents of location 01A5, and the least significant byte with the contents of location 01A6 (the instruction op code would be FE 01 A5). Note that the index register, like the stack pointer, is a 16-bit register and requires 2 bytes of memory to specify its contents.

RELATIVE ADDRESSING MODE

The relative addressing mode in the 6800 is used solely for branch instructions. These instructions allow the normal sequence of "one instruction following another" to be

changed, and enable the implementation of decision making in programs. The instructions used for branching are two-byte instructions. The first byte contains the opcode which specifies the branch condition (e.g. BCS is used to branch if the carry bit is set), and the second byte contains the offset.

The offset is a 2's complement 8-bit number which is used to specify where the program will branch to if the branch condition is satisfied; in the example the branch will only occur if the carry bit is set when the instruction is encountered. The range of destination addresses is restricted to $-7D$ to $+81$ relative to the branch instruction (hence the name). This range results from the fact that, when the branch instruction is executed, the program counter will be pointing to the next instruction, which will be two bytes on from the branch code. If A is the address of the branch instruction in memory, then the destination address, D, will be in the range:

$$[(A + 2) + 7F] \geq D \geq [(A + 2) - 80]$$

Two examples are given in Fig. 2.2 which illustrate how to calculate the two hex-digit offset value, J, which must be coded as the second byte of the branch instruction. With practice the values may rapidly be worked out by mental arithmetic!

INDEXED ADDRESSING MODE

Indexed addressing involves 2-byte instructions, and makes use of the contents of the 16-bit index register, in addition to op code, to specify the address of the source/destination of the instruction operand.

The address is calculated by taking the contents of the in-

dex register and adding the offset value contained in the second byte of the instruction. For example, if the current contents of the index register are 0300, an instruction of STA A 27,X (coded as A7 27) would result in the contents of register A being stored in memory location 0327. The offset in the second byte of the instruction may take any value in the range 00 to FF, and is assumed to be positive. The index register is unaffected by indexed instructions; thus STA A 27,X followed by STA B 28,X would result in registers A and B being stored in locations 0327 and 0328, respectively.

Special instructions are provided for loading, manipulating and storing the contents of the index register, as used by the indexed addressing modes of instructions. Typical instructions relating to the index register are LDX, INX, DEX, and STX. The use of indexed addressing is particularly useful for manipulating tables, and for jumping to addresses picked up from tables/memory locations (JMP nn,X and JSR nn,X); this is a technique much used internally by DISBUG.

THE STACK

The 6800 uses part of its read/write memory to implement a stack. This stack is used for:

- (a) storing subroutine return addresses
- (b) temporary program data storage
- (c) storage of CPU status (register contents) while responding to interrupts.

The stack works on a last-in first-out (LIFO) principle and a stack pointer (16 bits) is provided in the CPU to indicate the address of the next free stack location. When data (e.g. a return address) is "pushed" onto the stack, the stack pointer is *decremented* by the number of bytes pushed (e.g. two for a return address). When data is "pulled" from the stack, the stack pointer is correspondingly *incremented*.

The stack pointer must be initialised (via the LDS instruction) to the start (top) of the stack area. The amount of RAM allocated for stack operations must allow two bytes for each nested subroutine call, and seven bytes for each category of concurrent interrupt (NMI, IRQ, SWI). Additional allowance must be made if the stack is to be used for temporary variable storage (via PSHA and PSBH). Every stack push must have a corresponding stack pull if the stack is not to extend indefinitely! Once initialised, maintenance of the stack pointer is performed automatically by the CPU.

GETTING STARTED

A practical demonstration of programming the Micro-controller concludes the second part of this series. The program which is presented is used as a means of demonstrating the operation of DISBUG. However, it is not expected that readers will fully understand the detailed operation of the program since it uses a number of sub-routines which are contained within DISBUG itself. In the next issue further examples of programs will be presented to illustrate how control programs may be constructed. Once the user has become familiar with the way in which programs are entered and controlled, it is but a short step to write a PIA control program. The sample program is:—

Address	Instruction	Mnemonic	Op Code
0000	LDA A	# 15	86 15
0002	JSR	F9BD	BD F9 BD
0005	CLR	03FA	7F 03 FA
0008	LDX	# 03FB	CE 03 FB
000B	LDA A	03E3	B6 03 E3
000E	JSR	F8F7	BD F8 F7
0011	LDA A	03E2	B6 03 E2
0014	JSR	F8F7	BD F8 F7
0017	JSR	F814	BD F8 14
001A	BRA	E4	20 E4

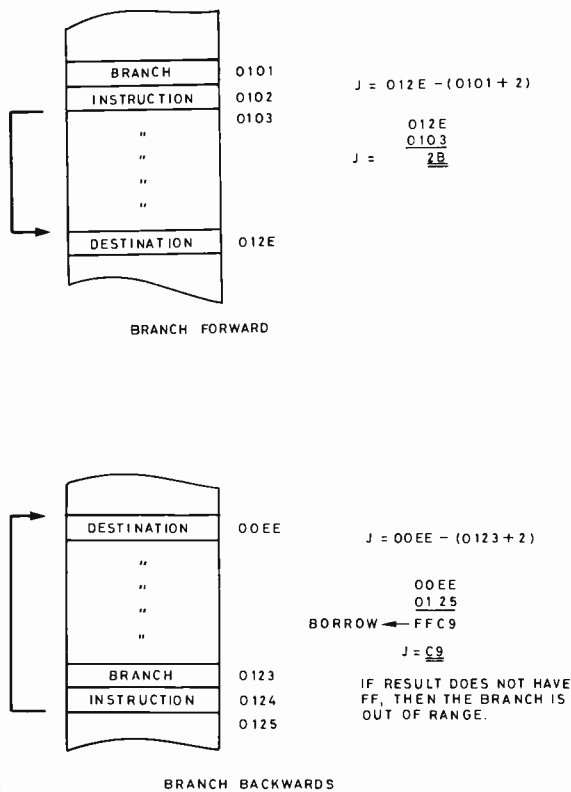


Fig. 2.2. Calculation of branch offset values

When the Microcontroller is switched on, DISBUG outputs a display of "dis r1.0" for approximately 2 seconds. After this time, the display changes to the normal prompt of "...dis..." to indicate that DISBUG is awaiting a user command from the keyboard. The memory editor is used to enter programs into the user RAM area of memory. The sequence of keystrokes required to enter the demonstration program is as follows:

KEYSTROKE(S)	DISPLAY
	...dis...
MEMORY	A- -
0 0 0	A- 000-
0 8	d-0000- 8
6	d-0000- 86
NEXT 1 5	d-0001- 15
NEXT B D	d-0002- bd
NEXT F 9	d-0003- F9
"	"
"	"
repeat for remaining codes	"
"	"
NEXT E 4	d-001b-E4
ENTER	A- -
ENTER	...dis...

EG985

The program is now stored in RAM. To demonstrate the use of the breakpoint editor, a breakpoint will now be placed at the end of the loop at location 001A. This is done as follows:

KEYSTROKE(S)	DISPLAY
	...dis...
BREAKPOINT	A-FFFF-b0
0 0	A- 00-b0
1 A	A-001A-b0
ENTER	...dis

EG982

The program is now run from the start address (0000) as follows:

	...dis...
GO	A- -
0 0 0 0	A-0000-
ENTER	


EG983

The display will now go blank, flash briefly, and then return with a display of "E-001A-bP" to indicate that it has found the breakpoint at location 001A. Pressing the ENTER key will cause "...dis..." to reappear. The PROCEED key is then struck to request that the program continue from the breakpoint:


	...dis...
PROCEED	E-001A-Pr
ENTER	

EG984

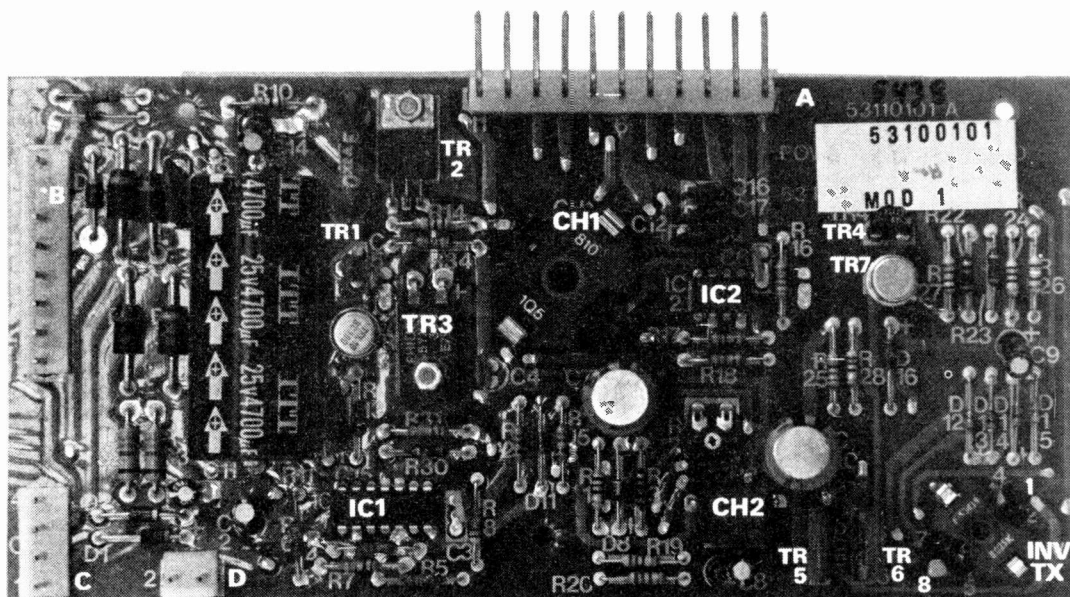The program will then restart from location 001A. The display will go blank for a short period, and then a four-digit running seconds count will appear in the centre of the display. The program, which uses the 1 second real time clock interrupt, must be stopped by interrupting the power.



P.s.u. board

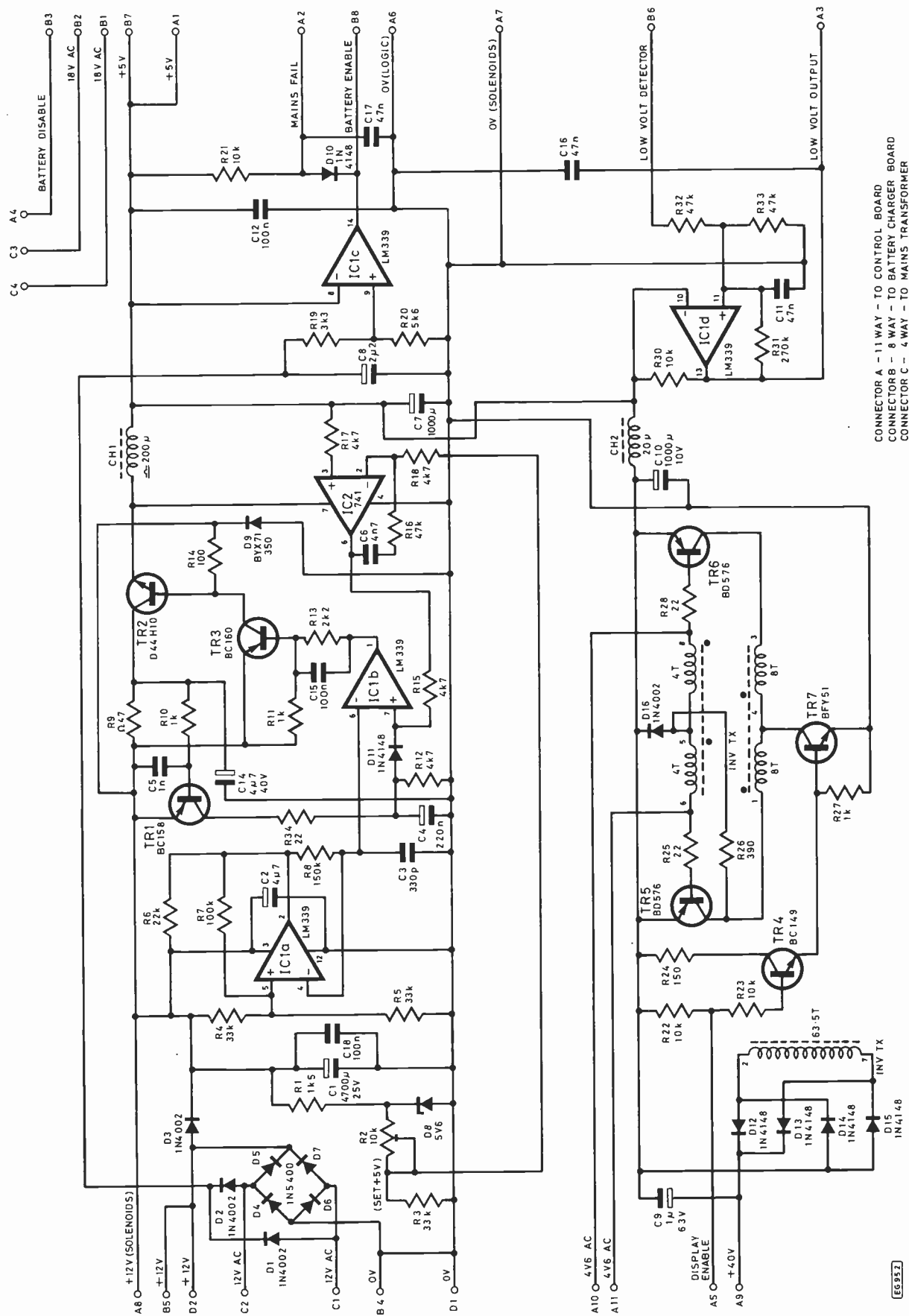

CONNECTOR A - 11 WAY - TO CONTROL BOARD
 CONNECTOR B - 8 WAY - TO BATTERY CHARGER BOARD
 CONNECTOR C - 4 WAY - TO MAINS TRANSFORMER

Fig. 2.3. Circuit diagram for the p.s.u.

POWER SUPPLY

The power supply provides the following outputs which are required for the Microcontroller:

- (a) +12V high current supply (unregulated) for the four output interface buffers. Unloaded output is approximately 17V.
- (b) +5V regulated supply for the CPU, RAM, ROM system clock, and control logic
- (c) +40V supply for the gas discharge display
- (d) 4-6V a.c. for the display filament.

In addition to the above supply rails, logic control signals are provided for detecting the presence of low-voltage or mains failure conditions.

The mains transformer has two series-connected 110V primary windings and two separate secondary windings. One of these provides 12V at approximately 2A for the bridge rectifier arrangement formed by D4, D5, D6 and D7. The other secondary winding provides approximately 17V at 0.5A and is not used in the basic Microcontroller system. It may, however, be used in conjunction with ancillary equipment or for system expansion.

The complete circuit diagram of the Microcontroller power supply is shown in Fig. 2.3. The unregulated d.c. output from the bridge rectifier is developed across reservoir capacitor, C1, and additional high frequency decoupling is provided by C18. The regulator operates on the switched mode principle with series-pass transistor, TR2. IC1a is connected as an oscillator which produces a square wave output at approximately 33kHz. The output of this oscillator is inverted by means of the comparator formed by IC1b. Over-current protection is provided by means of TR1 which effec-

tively turns off the comparator stage. The output current is sampled by means of the voltage drop developed across R9 and trip operates at a load current of approximately 1.5A.

The voltage reference for the supply regulator is provided by D8 and associated components. Potentiometer, R2, provides accurate adjustment of the reference voltage to 5V. The reference voltage is compared with the output voltage of the supply using the comparator arrangement formed by IC2. Feedback components, C6 and R16, improve the stability of this stage.

Failure of the supply mains is detected by a further comparator arrangement formed by IC1a. Low voltage detection is similarly provided by IC1d. Both the mains failure and low-voltage control signals are used in the Microcontroller RAM control logic.

A simple inverter arrangement is used to provide the +40V rail. TR5 and TR6 are connected as an astable oscillator which operates at 12kHz and is gated by means of TR7. The secondary of the inverter transformer feeds the bridge rectifier, D12, D13, D14 and D15. Positive feedback to the bases of TR5 and TR6 is by means of two further secondary windings and these are also used to provide the 4-6V a.c. filament supply. The display is enabled by a logic 'high' which turns TR4 and TR7 'on'. Note that R22 acts as a pull-up which ensures that the inverter supply operates when the power supply is disconnected from the Microcontroller.

NEXT MONTH: *Programming the PIA's, writing control programs, controlling peripheral hardware and sample applications.*

PE SPECIAL CASSETTES OFFER

V.H.S. VIDEO

V.H.S. E180 VIDEO (3 HOURS)

£7.65 each (minimum of 5); **£7.50 each** (min. 10); **£7.44 each** (min. 15); **£7.40 each** (min. 20) including VAT and postage.

Over the last couple of years PE offers arranged with Videotone have proved highly successful and we have now been able to arrange special prices (only available to PE readers) on these high quality tapes.

We believe these tapes are excellent value and we are pleased to offer them to readers. They are covered by a money back guarantee (return within 21 days for refund). Not only are the tapes of high quality but the cassettes are of screw together construction and the case labels have space for notes on the recordings.

Send valid coupon to:

Videotone Ltd., 98 Crofton Park Road, Crofton Park, London SE4.

C90 AUDIO

C90LH CASSETTES

56p each (minimum of 5); **53p each** (minimum of 25).
Prices include VAT and postage.

Easy to build projects for everyone

Everyday ELECTRONICS

Our Sister Publication

Everyday Electronics

features the following projects in the **December** issue. On Sale 19 Nov:

Security Vari-Light

Add-On Memory for ZX81

Ultrasonic Velocity Measurer

PLUS . . .

Information Technology
Part 2

1983 Schools Design
Competition details (Over
£2,000 in Prizes)

Introducing Electronics Part 3
(Practical Experiments for
Beginners)

Special Multimeter Offer

BLOCK CAPITALS PLEASE

Please send me V.H.S. 3-hour Video tapes at £ each. (£7.65 for 5 to 9, £7.50 for 10 to 14, £7.44 for 15 to 19, £7.40 for 20 or more; including VAT & postage.)

Please send me C90LH Audio tapes at p each. (56p for 5 to 24, 53p for 25 or more; including VAT & postage.)

I enclose cheque/PO for £ No.

Name

Address

Coupon valid for posting before 10th December '82
(or one month later for overseas readers).

Tandy®



**DON'T BE
CAUGHT OUT
THIS WINTER!**

Versatile 40 Channel 4 Watt Emergency CB UNIT

£79.95

Stuck in a snow drift, run out of petrol, broken down in the middle of nowhere...! It can happen anytime and probably will in the worst of weathers. With the prospect of another bad winter approaching, here is a device that could save a lot of worry, money and lives.


It's an incredibly easy to use 40 channel 4 watt emergency CB Unit that can be stored under your seat or in the boot in its protective case ready for that day of crisis, or be used for long periods as a normal unit with all "big rig" features.

21-9113 £79.95



Includes Protective
Storage Case

**Tandy For Total CB
Communications**

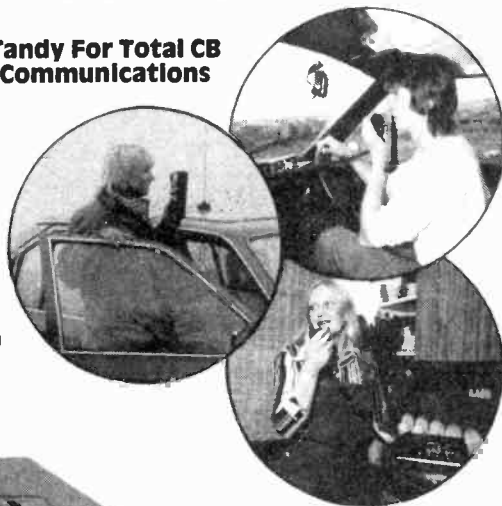

Navaho 40 Channel 4 Watt CB Base Station

£129.95



Realistic TRC-3000. With a mobile set in the car and a base station in the home or office you can keep in touch! The PLL gives precise frequency control, RF output and signal strength meter, LED modulation indicator. Full 40 channels and 4 watts output. Speaker jack and headphone jack. Includes microphone.

Base Station Desk Mike.
21-9031 £21.95

Base Station Antenna.
21-9022 £39.95

21-9115 £129.95

OVER 290 STORES AND DEALERSHIPS NATIONWIDE
Check your phone book for the **Tandy** Store or Dealer nearest you



Known as Radio Shack in the USA
Prices may vary at individual stores.
Offers subject to availability.

Patents Review

Copies of Patents can be obtained from:
the Patents Office Sales, St. Mary Cray, Orpington, Kent. Price £1.60 each.

PIN BULLETINS

At last something useful for nothing! Although surprisingly few people realise it, patents are often a wonderful source of first hand information on technology. A patent effectively freezes the inventor's original thoughts in print because, once filed and published, a patent can't be re-written, like the second edition of a book. Also patents remain perpetually in print. Even if all the printed copies have been sold you can still buy a photo-copy from the Patent Office. The problem of course is in finding the information you want from the literally millions of patents on file. A search by name (i.e. the name of the inventor, or the firm which filed the application for the inventor) is relatively easy, but still tedious because you have to search through annual alphabetical lists. And some firms file hundreds of patents a year. A subject matter search (i.e. all patents in a particular field of technology) is much more difficult and time-consuming. You first have to establish the classification mark for the technology that interests you, and then look up every patent that carries that mark. As often as not most of them are irrelevant, because it's only occasionally that your field of interest exactly coincides with a particular classification mark. Random searches, relying on pure serendipity, are like the football pools.

Now, the British Library is publishing a series of newsletters, called PIN Bulletins, which deal with interesting and important patents in popular and topical subject areas. These bulletins can be a very valuable short cut. Bulletin No. 2, for instance, discusses the patents on the Sinclair flat screen television research. Bulletin No. 3 looks at the patent coverage on Prestel-Viewdata, the war-time Enigma coding machines and satellite data communications. You can get copies of the PIN Bulletins free, from any of the libraries in the Patents Information Network. In practice this means any large library which keeps copies of published patents.

THE CRANFIELD PATENT

There's an interesting story behind British Patent 1 394 291. It was applied for in February 1972, by the Cranfield Institute of Technology, with Jack Dinsdale named as inventor. Dinsdale is a lecturer at Cranfield and hi-fi enthusiast, who had invented a clever bearing for a gramophone turntable. The patented bearing is like a fairly loose fitting piston and cylinder arrangement, but with helical grooves cut in the mating cylin-

drical surfaces. The bearing is filled with oil and when the central piston part (which carries the gramophone turntable) is rotated, the helical grooves create a hydrodynamic thrust which pumps the oil downwards. So the rotating parts float on oil. If the spindle is turned in the opposite direction the oil is pumped upwards and the bearing locks like a brake.

The patent application was accepted and published by the British Patent Office in May 1975 and in December that year Cranfield sold the patent rights to Plessey, then the parent company of hi-fi manufacturer Garrard. The sale price was said to be £5,000. At that time hi-fi sales were still reasonably strong and Garrard was a major name in British hi-fi. Garrard planned to incorporate the Cranfield bearings in a new, top range turntable. But hi-fi sales slumped and so did Garrard's fortunes. No turntable with the Cranfield bearing ever appeared. But even after Plessey shed loss-making Garrard, the Ilford company kept on paying the annual renewal fees necessary to keep the Cranfield patent in force. This has prevented other manufacturers from using the idea.

The Rock turntable made by Elite Townshend of Walton-on-Thames incorporates other Cranfield technology, such as artificial granite material for damping and a viscous fluid damped pickup arm. But Cranfield could not license Elite Townshend to use the patented bearing and had to design another, which relies on a cup of PTFE. It's unclear why Plessey kept the patent in force, because after the Garrard experience Plessey showed no further interest in hi-fi. Perhaps the patent was automatically renewed because no one thought to decide otherwise.

In April, 1982, however, Plessey sold the patent rights back to Garrard, for a nominal £1. So it is now up to Garrard to keep the patent in force and this will entail paying over £100 a year in renewal fees. After being sold off by Plessey, Garrard was bought by the Brazilian company Gradiente Electronics, but the future of Garrard is again in doubt. The company pulled out of the 1982 Harrogate International Festival of Sound and Video at the last minute, leaving the official exhibition catalogue with a glossy advert for Garrard on the front page, but no Garrard products on display. The next renewal fee for the Cranfield patent falls due for payment on February 2nd, 1983. Although there is a period of grace available for late payment it's likely that several hi-fi manufacturers will be checking with the Patent Office in February to establish

whether or not Garrard is still keeping the Cranfield patent alive.

LOUDSPEAKERS

The Hohyu Rubber Company Ltd of Osaka, Japan has filed a British patent application for a new type of loudspeaker diaphragm. (2 087 688). Although patents for new speakers and new diaphragm materials, all supposedly offering perfect sound reproduction, are two a penny, this Japanese proposal is worth noting because of its radical thinking. This is probably due to the fact that the applicants are primarily involved in rubber technology, rather than loudspeaker design.

Traditionally a loudspeaker diaphragm is built as light and rigid as possible, so that it moves as a piston without isolated vibrations which cause cone breakup. The Japanese here suggest that this approach should be abandoned. Instead the diaphragm should be made of cured rubber with a very low rigidity so that it can vibrate freely, and not as a piston. The inventors liken their new cured rubber diaphragm to "artificial vocal cords".

Various rubber materials are listed, all highly flexible and formed by moulding and heat-curing under pressure. According to the patent the conventional diaphragms were stripped out of a three-way hi-fi speaker system and replaced by samples of the new floppy rubber units. Signals were then fed in from a hi-fi system (Sansui amplifier, Denon turntable and Shure V-15 type III cartridge) while a panel of "four trained listeners" made notes. Whereas the original system sounded only "ordinary" the system modified according to the invention sounded consistently "excellent".

European Patent Application 0 054 945 from the Nissan Motor Company offers a high level of sound in a motor car from a small loudspeaker drive unit. Most in-car systems, especially budget units factory-fitted prior to sale, rely on small loudspeaker drive units mounted in the door panels. These easily overload when the system is played loud, for instance on a motorway. They are also prone to irritating cavity resonances at specific frequencies in the high bass range. Nissan suggests the answer is to join the resonance problem rather than fight it. Instead of using a conventional loudspeaker, with drive coil and diaphragm, the Nissan unit has a driver which is coupled directly to a panel of the vehicle. So the vehicle panel acts as a diaphragm. Obviously the system is usable only at fairly low frequencies.

YOUR GUIDE TO THE WORLD OF MICROPROCESSORS MICRO-PROFESSOR

*A low cost tool for learning,
teaching & prototyping.*

Micro-Professor is a low-cost Z80 based microcomputer which provides you with an interesting and inexpensive way to understand the world of microprocessors.

Micro-Professor is a complete hardware and software system whose extensive teaching manual gives you detailed schematics and examples of programme code. A superb learning tool for students, hobbyists and microprocessor enthusiasts, as well as an excellent teaching aid for instructors of electrical engineering and computer science courses.

The **Micro-Professor** is much more than a teaching device. Use it for bread boarding and prototyping, designing your own custom hardware and software applications with Z80, 8080 and 8085 compatible code.

The standard 2K bytes of RAM is expandable to 4K, and the standard 2K bytes of ROM can be increased to 8K.

All this plus built-in speaker, a cassette interface, and sockets to accept optional CTC/PIO. Bus is extendable.

As well as being an exciting learning tool, the **Micro-Professor** is a great low-cost board for OEM's.



Micro-Professor
£79.95

**EPB-MPF EPROM
Programming Board**
£84.95 + p&p


For all + 5V 1KP/2KB/4KB
EPROMS Read/Copy/List/
Verify Capability.

**SSB-MPF Speech
Synthesizer Board**
£69.95 + p&p


A vocabulary of up to 400
words based on the TMS
5200 chip.

**PRT-MPF Printer
Board £74.75 + p&p**

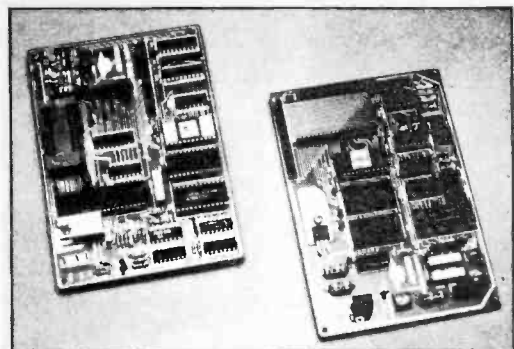Memory dump
BASIC program listing
Z80 disassembler



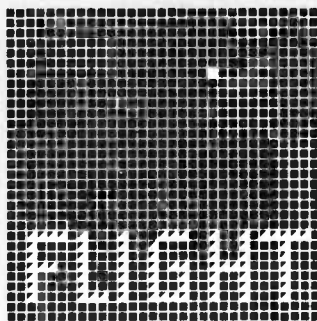Micro-Professor is a trade mark of Multitech Industrial Corporation.
Z80 is a trade mark of Ziilog Inc.



Flight Electronics Ltd.

Complete the coupon today! Please allow 28 days for delivery.

Please send me	Price	Qty	p&p
Micro-Professor	£79.95		£2.95
SSB-MPF board	£69.95		£2.95
EPB-MPF board	£84.95		£2.95
PRT-MPF board	£74.75		£2.95

Name

Address

Total

I enclose cheque/P.O. for £

Mail order only • Trade enquiries welcome • Bulk order discounts • Prices include VAT

Flight House, Quayside Rd, Southampton, Hants SO2 4AD
Tel: (0703) 34003/27721. Telex: 477793



(by phone or post)

Ingenuity Unlimited

A selection of readers' original circuit ideas. Why not submit *your* idea? Any idea published will be awarded payment according to its merits. Each idea submitted must be accompanied by a declaration to the effect that it has been tried and tested, is the original work of the undersigned, and that it has not been offered or accepted for publication elsewhere. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought. Articles submitted for publication should conform to the usual practices of this journal, e.g. with regard to abbreviations and circuit symbols. Diagrams should be on separate sheets, not in the text.

UNIVERSAL PROBE


THIS unit consists of a square wave generator with a 27 kilohm output resistance. The frequency of oscillation is about 1 kHz.

Tracing is done through an operational amplifier with a gain of about 2.2. Further gain is obtained by use of TR2 which drives an earphone. This should be mounted on the circuit board, inside the unit, to avoid too many umbilical cords. The sound tube on the earphone should be removed. If low level signals, with a d.c. component, are to be traced, C4 and S3 provide decoupling of the input probe. This may load some high impedance circuits but is not likely to prevent testing for most applications.

S4 allows the unit to be switched from an analogue function to a digital function. It should be noted that for most digital uses, S3 should remain open.

The input voltage is fed to the inverting input of the 741, so that the output is normally high. As the input voltage of the amplifier rises, so the output voltage falls; as decided by the amplifier gain R_{11}/R_8 . The high to low transition of the gates in IC3, was found to be approx. 3.6V; but if this varies, R11 can be set accordingly. When the output of the 741 falls below 3.6V the flip flop of IC3 changes state, and a logical high is indicated. Variations exist at the construction stage—precise voltage level change may be obtained by using a Schmitt device in place of IC3. The input voltage that causes a logical '1' to be indicated can be altered by changing R11. If R11 is reduced, the gain of the amplifier is reduced, and so the input voltage level which is necessary to cause a low to high change will rise. The object of the universal instrument is to use a voltage level suited to both TTL and CMOS.

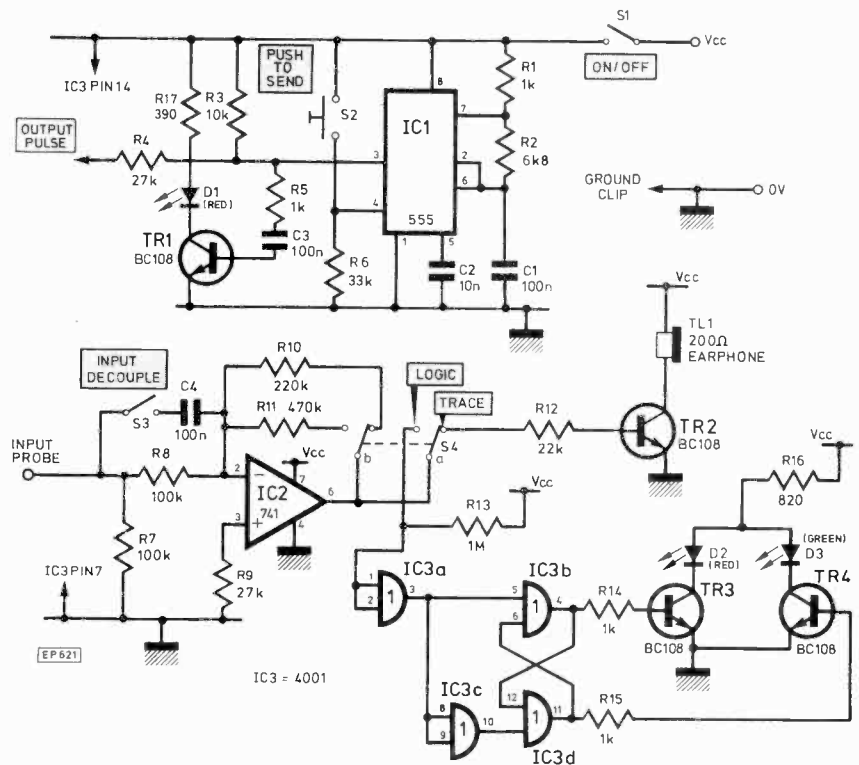As mentioned previously in the article, the Universal Probe may be used for other—more diverse applications. When S2 is open, the output lead, through R3 and R4, is at a logical '1' and so if used in conjunction with the input probe (Set to 'Logic' mode), continuity tests on high resistance circuits can be made; e.g. the instrument indicates logical '1' if the circuit is continuous.



If the output lead were connected to one side of a good capacitor and the input probe to the other side, the logical '1' indicator may flash momentarily but logical '0' should prevail. If now the 'Push to Send' button is pressed, an alternating current will pass through the capacitor and the logic l.e.d.s will indicate pulses. This test could be done with the unit set to 'Trace' and an audible indication of capacitor operation will follow. The square wave contains some high frequency harmonics so most capacitors can be tested in this way. High value electrolytic capacitors may take some time to charge through R3 and R4 before a logical '0' is shown. This fact could be used to estimate the value of an electrolytic capacitor. The

unit should be calibrated with certain known values. Charging time to 1.5V can be counted since it will take 10s of seconds and differences will be noticed between capacitors of different sizes.

Semiconductor components may also be tested using the logical high at the output lead, and the input probe. Diodes will conduct and show a logical '1' when the output lead is connected to the anode and input probe to the cathode. Where reverse connection is made a logical '0' will result. Transistors may be tested in a similar way—testing base-emitter, base-collector junctions.

J. L. Gordon,
St. Helens,
Merseyside.


THE circuit shown is a Disco Lights Sequencer with four channels rated at whatever wattage the user chooses. The unit, as well as having the standard "1 bulb on, 3 bulbs off" operating mode has, in addition, two other operating modes, which makes it considerably more versatile and yet cheaper than the expensive units that are bought commercially.

The two new modes are:

- An invert mode where instead of "1 on, 3 off" there is the converse mode of "3 bulbs on, 1 bulb off" which gives a higher ambient light level.
- A pulse/chain mode which gives a pronounced effect of the bulbs being pulsed rather than the usual effect of switching instantaneously from one bulb to the next and results in a very convincing stroboscopic effect being obtained. This strobe effect is greatly enhanced if different coloured bulbs are used and an exciting strobe lighting display occurs when fast, lively disco music is being played.

From the technical viewpoint the circuit features some distinct advantages over some commercial units. It has zero voltage switching so essential if r.f.i. is to be avoided and has the unique feature of powering the bulbs on both the positive and negative swings of the mains supply which means that the bulbs have full power and give full illumination in contrast with many commercial units that supply only half-wave to the bulbs. In addition,

DISCO LIGHTS SEQUENCER

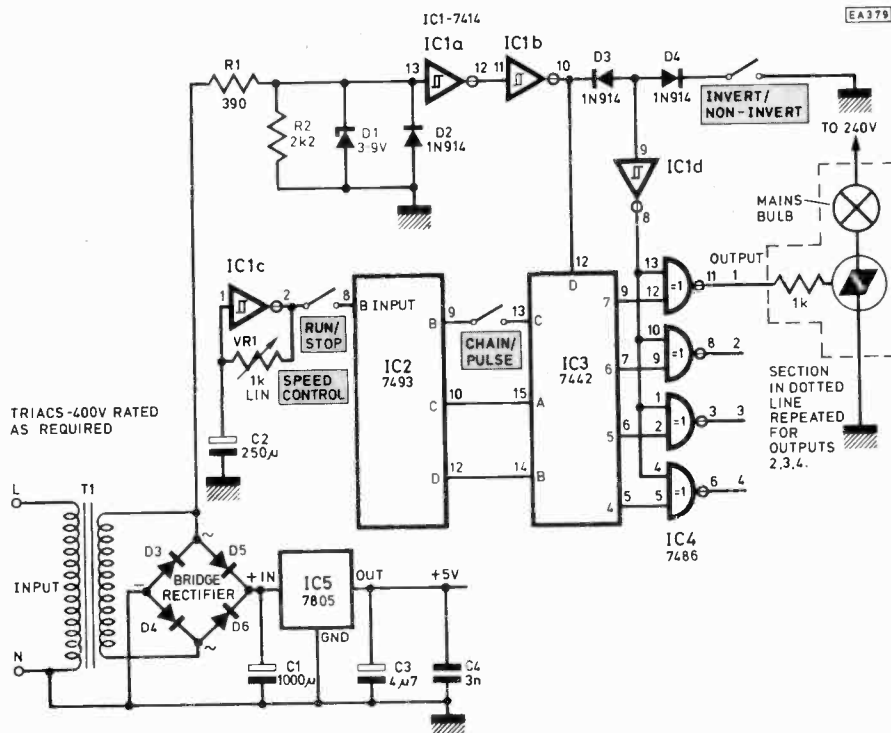

there is the all important safety aspect, because many commercial units require their circuitry to be live and so are inherently dangerous; however, the design given here has its circuitry tied to the neutral rail

and so the circuitry is harmless if accidentally touched.

P. McChesney,
Wirral,
Merseyside.

BAZAAR

SONY TC377 open reel stereo recorder, mixing, s.o.s. echo £120. Swap UK101 plus/or expansion, printer etc. Mr. M. A. Saunders, 7 Drumcliff Road, Thurnby Lodge, Leicester LE5 2LH.

ORGAN keyboards, plastic keys, metal frame complete with contacts £13 plus postage. Rhythm unit £20 o.n.o. Mr. R. I. Tait, 114 Crabtree Lane, Bromsgrove, Worcs. Tel: Bromsgrove 71862.

FOR SALE Acorn Atom + extras. Engineering magazines 1978-80, for details write or see page 62 P.E. Sept. Pete Stephens, 49 King's Court, Bishops Stortford, Herts CM23 2AB. (0279) 52719 after 9p.m. and weekend.

WANTED information on a project on a Disco Desk with built in light effects built in front. £2. For information, J. R. Worton, 1 St. Giles Crescent, Willingham Road, W/ton.

BACK numbers PE, Television, May 1980, August 1982. All good condition. Reasonable offers. A. Craig, 27 Dan's Road, Ballymena, Northern Ireland. Tel: Ballymena 42949.

VIDEO Recorder (Philips) CCTV camera, lens, modulator, tapes, etc. Ideal experimenters monochrome system. (Working) £90 o.n.o. David Palmer, 110 Ramsden Square, Cambridge, Cambs. CB4 2BL.

COMPUKIT 8K, Cegmon £140. Ohio 610 Board 24K RAM £150. Single disk unit £230.

Premier screen kit £45 + extras. R. W. Alderton, 77 Wilkinson St., Sheffield 10. Tel: 20571.

UK101 8K, excellent 9 inch National monitor, cassette recorder, software, 7 books, magazines, bargain £185 o.n.o. 70 Electronic magazines HE, EE. 01-856 2797. Mr. Rivander Bahra, 218 Shootershill Road, Blackheath, London.

WANTED IC's FDY7022P and FDY7023P used in Gross Desk Calculator 2131. Tel: 0495 245825 (after 6p.m.). J. Edwards.

MAPLIN 4600 Synthesiser offered around £450. Falkon R/C helicopter complete, offers around £185. Mr. R. Bailey, 52 Princess Street, Case Terrace, Nr. Walsall, Staffs WS7 8JN. Tel: 0543 77016.

WANTED. Charger and instruction manual for Tandy TRS 80 Printer cassette interface. Mr. K. Wenman, 2 Hythe Road, Sittingbourne, Kent.

MAGAZINES for sale, 4 bound volumes P.E. '64-'66, P.E. '66-'68 plus 100 P.E., P.W., E.E., P.T.V. Dec. 1945 to 1980. £30. J. Jones, 10 West Harbour Road, Charlestown, Fife, Scotland. Tel: Limekilns 872118.

AVO 73 (Not digital) £45 o.n.o. Phone Wickford 62943 after 4p.m. Mr. A. Ding, 71 Ethelred Gardens, Wickford, Essex.

UK101 8K rough case Mono 1 and WEMON. All RS232 components fitted. £150. S. Morgan, 17 Willenhall Road, Bilston, West Midlands WV14 6NW. Tel: Bilston 403416.

WANTED e.h.t. output transformer for a Teleton Anex 12" b/w portable television model TA-12. N. Kay, 4 Harland Close, Cosby, Leicester. Tel: Leic. 865037.

WANTED buy, loan, service manual or circuit diagram Civic radio XR5930 Hungarian Rhapsody. Will pay postage. D. Jackson, 77 Andover Road, Winchester SO29 6AU.

NAD 3020 stereo amplifier perfect condition and working order, little used. £65 o.n.o. Rustington 5615. Mr. S. Busbridge.

ELECTRONIC continuity checker. New, audible tone, safe around semiconductors, sounds over 150kΩ valuable test piece £5-00. Paul Wilson, 2 Ramage Road, Carluke, Strathclyde, Scotland. Tel: 50374.

MAGAZINES for sale, P.E., P.W., E.E., Jan. 65-July 75. Details on request. Tel: 061 764 9684. Iain Kent.

12LBS electronic components inc. soldering iron. Also 13lbs. inc. ready made p.c.b.'s with batteries, £12-50 each. Ian Wilson, 10 Lowgate, Gosberton, Spalding, Lincs. Spalding 840256.

MAPLIN MES 53 Organ, MES 55 Rhythm, Touch Sensitive piano + cabinet. Give away at £400. Tel: (06076) 67069. A. Laurent.

WANTED any non-working or part built Microcomputer. Jain, 17 Taylors Lane, London NW10.

PE RANGER, hand held C.B. complete, aerial microphone. Ideal Christmas present. £35 o.n.o. 01-551 3914. Jonathan Roberts.

STUDENT leaving soon. Lots of articles for sale. Good value, s.a.e. for list. K. Y. Chang, 70 Ashley St., Glasgow G3 6HW.

LAB GEAR pattern generator E 5180E £40-00. V. Phillpott, 85 Prince Charles Road, St. Peters, Broadstairs, Kent. Thanet 61824.

Who but the people who made the micro possible
could help you understand it?

The Texas Instruments Electronic Library.

An in-depth series in understanding today's world of electronics.

The Understanding Electronics Series was specially developed and written to give you an in-depth knowledge of this world.

Each book is comprehensive, yet easy to understand. As informative for the electronics buff as for someone who's simply interested in what's going on today.

Together the library will give you the most complete range of titles available. Take advantage of our introductory offer and choose the book, or books you want from the titles below. You'll find whole new worlds of advanced technology unfolding before you.

Everything you've always wanted to know about:

1. Understanding Electronic Control of Energy Systems.

1st edition. Ref. LCB 6642. Covers motor, generator, power distribution, heating, air conditioning, internal combustion engine, solar and nuclear systems. Softbound 272 pages. £3.95.

2. Understanding Electronic Security Systems.

1st edition. Ref. LCB 7201. A complete guide covering the basics of hard wired, photosensitive, infrared, ultrasonic and microwave systems and their use in different applications. Softbound 128 pages. £3.95.

3. Understanding Solid State Electronics.

3rd edition. Ref. LCC 3361. The principles of solid state theory. It explains electrical movement, with intermediate tuition on the applications of solid state devices. Softbound 282 pages. £3.95.

4. Understanding Digital Electronics. 1st edition. Ref. LCB 3311. Describes digital electronics in easy-to-follow stages. It covers the main families of digital integrated circuits and data processing systems. Softbound 260 pages. £3.95.

5. Understanding Microprocessors. 1st edition. Ref. LCB 4023. An in-depth look at the magic of the solid state chip. What they are, what they do. Applications of 8-bit and 16-bit microprocessors; and design from idea to hardware. Softbound 288 pages. £3.95.

6. Understanding Computer Science.

1st edition. Ref. LCB 5471. This book tells you in everyday English how today's computer has been developed, what goes on inside it, and how you tell it what to do. Softbound 278 pages. £3.95.

7. Understanding Communications Systems.

1st edition. Ref. LCB 4521. An overview of all types of electronic communications systems. Softbound 282 pages. £3.95.

8. Understanding Calculator Maths.

1st edition. Ref. LCB 3321. Brings together the basic information—formulae, facts, and mathematical tools—you need to "unlock" the real power of the hand-held calculator. Softbound 230 pages. £3.95.

9. Understanding Optonics.

1st edition. Ref. LCB 5472. Optonics is the application of light and electronics to perform a wide range of useful tasks. From car headlights to missile guidance systems. Softbound 270 pages. £3.95.

10. Understanding Automotive Electronics.

1st edition. Ref. LCB 5771. Learn how electronics is being applied to automobiles. How the basic mechanical, electrical and electronic functions and the new microprocessors and microcomputers are being applied in innovative ways for vehicle drive train control, motion control and instrumentation. Softbound 288 pages. £3.95.

How to order

Fill in the coupon below or if someone else has already used it, simply:

1. List reference numbers and quantities required.
 2. Calculate total order value. Add £1.50 for postage and packing.
 3. Send the list, plus your cheque payable to Texas Instruments Ltd, PO Box 50, Market Harborough, Leicestershire.
- Allow 30 days for delivery.

**TEXAS
INSTRUMENTS**



ENERGY CONVERSION

2

WATER RESERVOIR
(POTENTIAL ENERGY)

DAM

WATERFALL

ELECTRIC
GENERATOR

OUTLET WATER FLOW
(WASTE KINETIC ENERGY)

TURBINE
PROPELLER
BLADES

MECHANICAL ROTATION
(KINETIC ENERGY)

Potential Energy of Elevated Water
Kinetic Energy

INTRODUCTORY OFFER
Order three books and get
any one of the
"Understanding" series
FREE

2

ENERGY CONVERSION

To: Texas Instruments Limited, PO Box 50, Market Harborough, Leics.
Please send me the following publications:

REFERENCE NO	QTY	REFERENCE NO	QTY
1		7	
2		8	
3		9	
4		10	
5			
6			

Free title choice: Understanding _____

Enclose a cheque for £ _____

Name: _____

Company (if any): _____

Address: _____

Registered office: Texas Instruments Ltd, Manton Lane, Bedford MK41 7PA.
Registered number: 57102 England.

PE1

INDEX

JANUARY 1982 TO DECEMBER 1982

VOLUME 18

CONSTRUCTIONAL PROJECTS

- Active Speaker System by *J. Macaulay* July 16
 Alarm System, Comprehensive Home Aug. 14
 Alarm, Versatile Car July 62
 Amplifier, Combo Aug. 26, Sept. 56, Oct. 66
 Analyser, Signature May 42
 Audio Debug Probe by *Chris Lare* Sept. 31
 Audio Test Set by *M. Tooley B.A. and D. Whitfield M.A., M.Sc.* July 26, Aug. 48
 Audio Sweep Oscillator by *C. J. Jordan* Oct. 40
 Auto Flash Slave by *R. A. Penfold* June 32
 Automatic Diamond Crossing Control by *Andrew Parr* July 47
 Automatic Photographer by *M. J. A. Turner* Aug. 42
 Automatic Signal Switching by *Andrew Parr* July 42
- Bandbox, PE Jan. 37, Feb. 62
 Base Station, PE Ranger Jan. 32, Feb. 48, March 44
 Bench PSU Feb. 26
 Breadboard, experiments June 38
 Burglar Deterrent by *R. A. Penfold* July 68
- Camera, TV Jan. 26, Feb. 42, March 62
 Car Alarm, Versatile July 62
 Car Computer, PE Jan. 58
 Cassette Deck, Stereo April 18, May 57
 CB Scanner by *C. F. Shorto and M. Ward* Sept. 36
 CB Synthesiser Nov. 47
 Chorus Unit, Mini Oct. 60
 Combo Amplifier by *Fred Judd and E. A. Rule* Aug. 26, Sept. 56, Oct. 66
- Comprehensive Home Alarm System by *Gilbert Davies* Aug. 14
 Computer, PE Car Jan. 58
 Controller, d.c. Power June 46
 Controller, Security Oct. 52
 Cost Monitor, Telectric Electricity March 22, April 58
 Crossing Control, Automatic Diamond July 47
- D.c. Power Controller by *M. Tooley B.A.* June 46
 Deterrent, Burglar July 68
 Digi-Dice, Dual Jan. 53
 Digitiser, Waveform Sept. 46
 Digital Stopwatch by *T. J. Johnson* Oct. 22
 DMM by *Martin Kent* Nov. 42
 Dual Digi-Dice by *Tom Gaskell B.A.* Jan. 53
- Eliminator, Indecision Jan. 22
 Emergency Light by *Stephen Ibbs* March 28
 Enlarger Timer by *Tom Gaskell B.A.* April 32
 Experimenters Breadboard by *J. Slack* June 38
- Flash Slave, Auto June 32
 Frequency Meter and Prescaler by *Stephen Ibbs* May 24
 Function Generator by *Andy Flind* May 50
- Generator, Function May 50
 Graphics, Medium Resolution April 41
- Ignition, Miniature Scorpio Car Feb. 20
 Indecision Eliminator by *W. C. Dickson* Jan. 22
 Infra-Red Remote Control by *Bart Trepak* Feb. 32, March 40
 Infra-Red Tape Control by *Chris Lare* July 56
 Instrument Tuner by *Stephen Ibbs* July 32
 Interface, Ultimium Nov. 30, Dec. 36
- Light, Emergency March 28
- Medium Resolution Graphics by *N. A. Climpson* April 41
 Meter, MPG June 26
 Microcontroller Nov. 20, Dec. 50
 Micrograsp by *Richard Becker* Dec. 30
 Microsynth by *A. R. Bradford M.Sc.* June 18, July 36, Aug. 36
- Miniature Scorpio Car Ignition by *Mike Rees* Feb. 20
 Mini Chorus Unit by *R. A. Penfold* Oct. 60
 Mixing Desk, Semi-Professional Oct. 30, Nov. 58, Dec. 44
 MPG Meter by *Lionel Taylor* June 26
- Organ, Stylochord Dec. 22
 Oscillator, Audio Sweep Oct. 40
- PE Bandbox by *Alan Boothman B.Sc.* Jan. 37, Feb. 62
 PE Car Computer by *P. MacFarlane* Jan. 58
 PE Ranger Base Station by *M. Tooley B.A. and D. Whitfield M.A., M.Sc.* Jan. 32, Feb. 48, March 44
 PE Robots by *R. Becker, T. Orr and R. Monkhouse* Jan. 64, Feb. 52, March 56, April 46
 Photographer, Automatic Aug. 42
 Probe, Audio Debug Sept. 31
 Programmable Timer/Controller by *T. J. Johnson* May 32, June 52
- PSU, Bench Feb. 26
- Ranger Base Station, PE Jan. 32, Feb. 48, March 44
 Reminder, Seat Belt Sept. 22
 Remote Control, Infra-Red Feb. 32, March 40
 Robot, Micrograsp Dec. 30
 Robots, PE Jan. 64, Feb. 52, March 56, April 46
- Scanner, CB Sept. 36
 Scorpio Car Ignition, Miniature Feb. 20
 Seat Belt Reminder by *David Shortland* Sept. 22
 Security Controller by *John G. Leith* Oct. 52
 Semi-Professional Mixing Desk by *Tim Orr* Oct. 30, Nov. 58, Dec. 44
- Signal Switching, Automatic July 42
 Signature Analyser by *A. Trebar* May 42
 Speaker System, Active July 16

Stereo Cassette Deck April 18, May 57
 Stopwatch, Digital Oct. 22
 Stylochorde by S. Ibbs Dec. 22
 Tape Control, Infra-Red July 56
 Telecric Electricity Cost Monitor
 by Stephen Day B.Sc., C.Eng.M.I.E.E. March 22, April 58
 Test Set, Audio July 32, Aug. 48
 Timer/Controller, Programmable May 32, June 52
 Timer, Enlarger April 32
 Transistor Projects March 32, April 40
 Tuner, Instrument July 32

TV Camera by Philip Gaffney Jan. 26, Feb. 42,
 March 62
 Ultimium Nov. 30, Dec. 36
 Ultrasonic Vision System by J. Brentham and
 F. Brentham April 24, May 66
 Versatile Car Alarm by M. Tooley B.A. July 62
 Vision System, Ultrasonic April 24, May 66
 Waveform Digitiser by Lindsay Robinson
 B.A.Hons Sept. 46

GENERAL FEATURES

Digital Design Techniques by Tom Gaskell B.A. Jan. 48,
 Feb. 36, March 48

E/Monitor Reworked by Roger Derry June 43
 Electrolube Review Oct. 38

INGENUITY UNLIMITED April 61, May 68, June 58,
 July 54, Aug. 62, Oct. 56, Dec. 61

Alarm Clock June 59

Bandpass Filter May 70
 Button Selector April 62

CB "Roger Bleep" Aug. 62
 Car Alarm July 55
 Car Battery Discharge Indicator June 60
 "Challenge" Oct. 56
 CMOS Touch Switch Oct. 57
 Courtesy Light Delay Aug. 62

Disco Lights Sequencer Dec. 62

Electronic Multimeter May 69

Instant Diode Tester Oct. 58
 Invaders 127 July 54

Loudspeaker De-Thump Aug. 63

Mic Operated Sound-to-Light June 58
 Micro Output Controller June 61
 Morse Tone Detector May 70

Octave Bank for VCOs April 63
 Overload Cutout for Thyristor Speed Control April 61

Percussion Synth Oct. 57

Quality Mic Amplifier April 64

Sound-to-Light Converter April 63
 Static Detector June 61
 Stereo Width Control Oct. 58
 Switch De-Bounce April 62

Temperature Alarm June 59
 Trailer Lamp Monitor June 60

Universal Probe Dec. 61

9V Power Supply April 64

12W FET PA May 68

Menta Review by David Whitfield M.A., M.Sc. Sept. 16
 MICROBUS by D.J.D. Jan. 72, March 60, May 62,
 July 50, Sept. 42

Micro-Professor Review by Michael Tooley B.A. Aug. 32
 Micro Prompt Feb. 60, April 54, June 42, Aug. 56,
 Oct. 70

Searchwater by Frank W. Hyde Sept. 28
 SEMICONDUCTOR UPDATE ... Jan. 25, Feb. 25, March 66,
 April 39, May 49, June 37, July 24,
 Aug. 47, Sept. 34, Oct. 28, Nov. 57, Dec. 49

RCA 1804, Weitek Corporation WTV008 Jan. 25

Western Digital WD2123, Precision Monolithics
 Incorporated OP-27 Feb. 25

National LM1035, Texas Instruments 99000
 Series, Signetics 8X60 March 66

Motorola MC146818, Triangle TDS 934,
 Commodore International 6600 April 39

National LM363, Texas Instruments TL783
 RCA 74HC Series May 49

Mostek MK3824/3821, Raytheon RC4191,
 Intel 27128 June 37

National MF10, RCA CA3300D,
 ITT SA6000 July 24

Cybernetic CY360, Texas Instruments TL068,
 Siemens SAB8256A Aug. 47

DEC MICRO/T-11, SGS-Ates TDA2009,
 TDA2320A, RCA CDP1871 Sept. 34

Analog Devices AD549, Intel iAPX 186,
 Teledyne TSC9403 Oct. 28

INMOS IMS26000, Xicor X2816A, X2804A,
 AMI Microsystems S3610, S3620 Nov. 57

Motorola MC1468705 G2, Westinghouse D60T,
 Precision Monolithics OP-22 Dec. 49

Strictly Instrumental by K. Lenton-Smith April 52,
 Aug. 54

NEWS AND COMMENT

BAZAAR	April 45, May 29, 47, 54, June 25, 36, 56, July 21, 46, 52, 61, 71, Aug. 41, 52, 55, Sept. 30, 44, 61, 62, Oct. 51, 55, Nov. 46, 64, 65, Dec. 35, 46, 47, 62
COUNTDOWN	Jan. 18, Feb. 16, March 18, April 14, June 14, July 12, Aug. 12, Sept. 12, Oct. 18, Nov. 18, Dec. 20
EDITORIAL	Jan. 17, Feb. 10, March 17, April 13, May 17, June 13, July 11, Aug. 11, Sept. 11, Oct. 17, Nov. 15, Dec. 17
INDUSTRY NOTEBOOK by <i>Nexus</i>	Jan. 21, Feb. 19, March 21, April 30, May 23, June 35, July 23, Aug. 25, Sept. 15, Oct. 21, Nov. 29, Dec. 42
NEWS AND MARKET PLACE	Jan. 18, Feb. 16, March 18, April 14, May 18, June 14, July 12, Aug. 12, Sept. 12, Oct. 18, Nov. 16, Dec. 18

Macrochip	April 28
Microprocessor competition	Oct. 39
PATENTS REVIEW	Jan. 63, Feb. 66, March 64, April 68, May 72, June 62, July 72, Aug. 64, Sept. 20, Oct. 50, Dec. 59
POINTS ARISING	Jan. 18, Feb. 51, April 14, June 14, July 12, Aug. 12, Sept. 12, Oct. 18, Nov. 16, Dec. 20
READOUT	April 53, June 36
SPACEWATCH by <i>F. W. Hyde</i>	Jan. 29, Feb. 41, March 68, April 66, May 55, June 51, July 35, Aug. 61, Sept. 26, Oct. 68, Nov. 40, Dec. 29

SPECIAL SUPPLEMENTS AND OFFERS

Automatic Test Equipment by <i>D. Mandelzweig</i>	between pages 40 & 41 May
Cassettes	April 51, May 46, June 49, July 53, Aug. 45, Sept. 27, Oct. 49, Nov. 56, Dec. 57
Loudspeakers	April 31, May 65, Sept. 45
Micro-file by <i>R. W. Coles</i>	between pages 40 & 41 Nov. 42 & 43 Dec.
PCB Drill	Jan. 35
Quasar Cassette	Oct. 65

Sound Synthesis by <i>A. R. Bradford M.Sc.</i>	between pages 36 & 37 June
Speechtime Clock Kit	May 41
Special digital pulser offer	Nov. 43
Using the IC Insertion Tool	Oct. 27
Using your free cable ties	Nov. 41
What CB?	Jan. 39

all in your
JANUARY 1983
issue!

FROST WARNING

This warning system can be programmed to provide both audible and visual indications of under or over temperature conditions.


DIGITAL TACHOMETER

Variable brilliance digital l.e.d. display of engine rev's for 4, 6 or 8 cylinder vehicles.


Also...
**DATA PULL-OUT
PE MICROFILE**

AUDIO BOOSTER

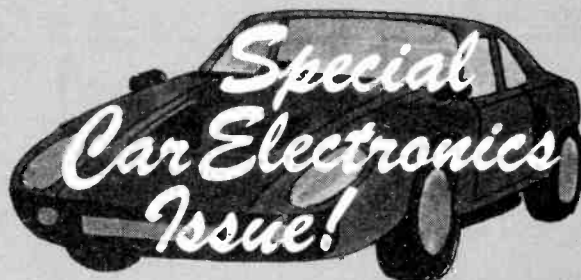Provides a four-fold increase in the audio output power of most car radios and cassette players.



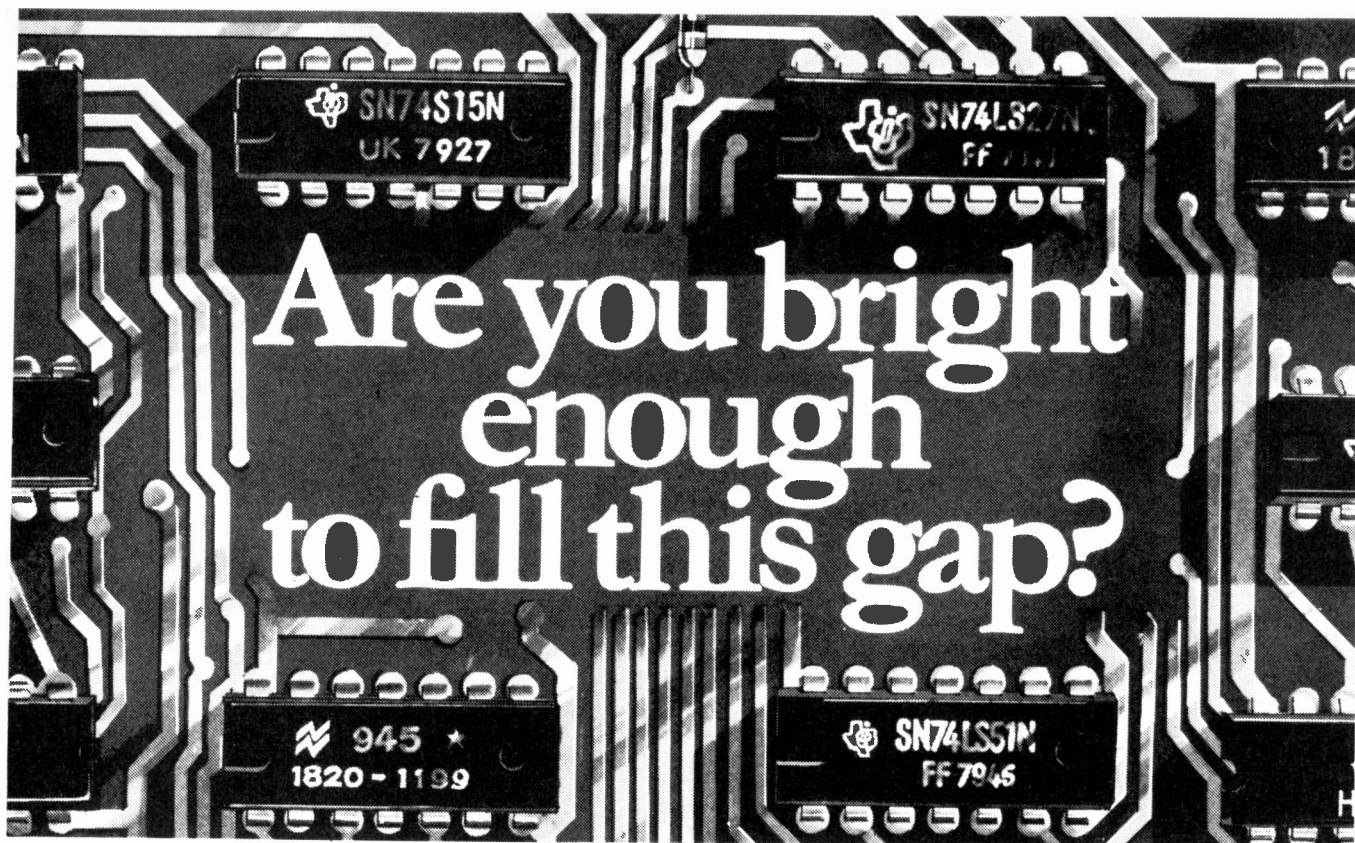**PRACTICAL
ELECTRONICS**
ON SALE FRIDAY, DECEMBER 10, 1982



Without fast and efficient communications, all the Army's modern technology and hardware would be useless.

Rather like rush-hour traffic in dense fog.

But with potentially much more disastrous consequences.

For this reason we're asking a lot from our Apprentice Technicians in the Royal Signals these days.

Right now we have a limited number of Technician Apprenticeships in Military Telecommunications.

You've got to have four 'O' levels, at grade C or better, including Maths, English and a Science subject before we'll be interested in you. We'll want to be sure that you're the right type, both physically and mentally, for such a crucial and exacting job.

And we'll want to be convinced that you've a real interest in Electronics.

Naturally, since we're asking this much of you, you'll expect quite a lot from us.

And you'll get it. If accepted, you'll go for two and a half years training at the Army Apprentices College in Harrogate, starting on January 6th next year.

There you'll receive a technical education in electronics equal to the best in the country, leading to a minimum of TEC Certificate.

And at the same time an academic and military training that will leave you in peak mental and physical form, ready for early promotion.

If you think you can handle this kind of challenge, and you'll be aged between 16 and 17½ in January, just fill in the coupon or call in at your nearest Army Careers Information Office, ideally before the end of the month.

You'll find our address in the 'phone book under "Army."

To: Major Martin Allington, M.O.D. DAR 2
(Dept PE1) Lansdowne House, Berkeley Square,
London W1X 6AA.

Name _____

Address _____

Date of birth: _____

Junior Army 
Apprentice Technician. Royal Signals

Sinclair ZX Spectr

**16K or 48K RAM...
full-size moving-
key keyboard...
colour and sound...
high-resolution
graphics...**

**From only
£125!**

First, there was the world-beating Sinclair ZX80. The first personal computer for under £100.

Then, the ZX81. With up to 16K RAM available, and the ZX Printer. Giving more power and more flexibility. Together, they've sold over 500,000 so far, to make Sinclair world leaders in personal computing. And the ZX81 remains the ideal low-cost introduction to computing.

Now there's the ZX Spectrum! With up to 48K of RAM. A full-size moving-key keyboard. Vivid colour and sound. High-resolution graphics. And a low price that's unrivalled.

Professional power— personal computer price!

The ZX Spectrum incorporates all the proven features of the ZX81. But its new 16K BASIC ROM dramatically increases your computing power.

You have access to a range of 8 colours for foreground, background and border, together with a sound generator and high-resolution graphics.

You have the facility to support separate data files.

You have a choice of storage capacities (governed by the amount of RAM). 16K of RAM (which you can upgrade later to 48K of RAM) or a massive 48K of RAM.

Yet the price of the Spectrum 16K is an amazing £125! Even the popular 48K version costs only £175!

You may decide to begin with the 16K version. If so, you can still return it later for an upgrade. The cost? Around £60.



Ready to use today, easy to expand tomorrow

Your ZX Spectrum comes with a mains adaptor and all the necessary leads to connect to most cassette recorders and TVs (colour or black and white).

Employing Sinclair BASIC (now used in over 500,000 computers worldwide) the ZX Spectrum comes complete with two manuals which together represent a detailed course in BASIC programming. Whether you're a beginner or a competent programmer, you'll find them both of immense help. Depending on your computer experience, you'll quickly be moving into the colourful world of ZX Spectrum professional-level computing.


There's no need to stop there. The ZX Printer—available now—is fully compatible with the ZX Spectrum. And later this year there will be Microdrives for massive amounts of extra on-line storage, plus an RS232 / network interface board.



Key features of the Sinclair ZX Spectrum

- Full colour—8 colours each for foreground, background and border, plus flashing and brightness-intensity control.
- Sound—BEEP command with variable pitch and duration.
- Massive RAM—16K or 48K.
- Full-size moving-key keyboard—all keys at normal typewriter pitch, with repeat facility on each key.
- High-resolution—256 dots horizontally x 192 vertically, each individually addressable for true high-resolution graphics.
- ASCII character set—with upper- and lower-case characters.
- Teletext-compatible—user software can generate 40 characters per line or other settings.
- High speed LOAD & SAVE—16K in 100 seconds via cassette, with VERIFY & MERGE for programs and separate data files.
- Sinclair 16K extended BASIC—incorporating unique 'one-touch' keyword entry, syntax check, and report codes.

um

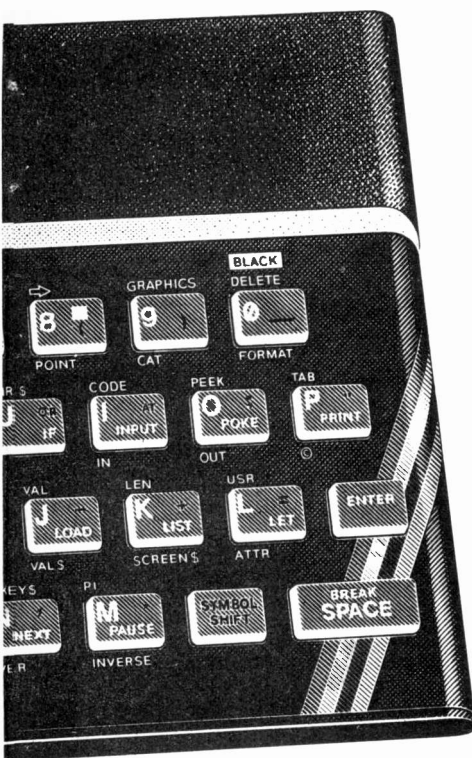

The ZX Printer – available now

Designed exclusively for use with the Sinclair ZX range of computers, the printer offers ZX Spectrum owners the full ASCII character set – including lower-case characters and high-resolution graphics.

A special feature is COPY which prints out exactly what is on the whole TV screen without the need for further instructions. Printing speed is 50 characters per second, with 32 characters per line and 9 lines per vertical inch.

The ZX Printer connects to the rear of your ZX Spectrum. A roll of paper (65ft long and 4in wide) is supplied, along with full instructions. Further supplies of paper are available in packs of five rolls.



The ZX Microdrive – coming soon

The new Microdrives, designed especially for the ZX Spectrum, are set to change the face of personal computing.

Each Microdrive is capable of holding up to 100K bytes using a single interchangeable microfloppy.

The transfer rate is 16K bytes per second, with average access time of 3.5 seconds. And you'll be able to connect up to 8 ZX Microdrives to your ZX Spectrum.

All the BASIC commands required for the Microdrives are included on the Spectrum.

A remarkable breakthrough at a remarkable price. The Microdrives are available later this year, for around £50.



RS232/network interface board

This interface, available later this year, will enable you to connect your ZX Spectrum to a whole host of printers, terminals and other computers.

The potential is enormous. And the astonishingly low price of only £20 is possible only because the operating systems are already designed into the ROM.

How to order your ZX Spectrum

BY PHONE – Access, Barclaycard or Trustcard holders can call 01-200 0200 for personal attention 24 hours a day, every day. BY FREEPOST – use the no-stamp needed coupon below. You can pay by cheque, postal order, Access,

Barclaycard or Trustcard.

EITHER WAY – please allow up to 28 days for delivery. And there's a 14-day money-back option, of course. We want you to be satisfied beyond doubt – and we have no doubt that you will be.

ZX Spectrum

Available only
by mail order
and only from

sinclair

Sinclair Research Ltd,
Stanhope Road, Camberley,
Surrey, GU15 3PS
Tel: Camberley (0276) 685311.

To: Sinclair Research, FREEPOST, Camberley, Surrey, GU15 3BR.

Order

Qty	Item	Code	Item Price £	Total £
	Sinclair ZX Spectrum – 16K RAM version	100	125.00	
	Sinclair ZX Spectrum – 48K RAM version	101	175.00	
	Sinclair ZX Printer	27	59.95	
	Printer paper (pack of 5 rolls)	16	11.95	
	Postage and packing: orders under £100	28	2.95	
	orders over £100	29	4.95	
			Total £	

Please tick if you require a VAT receipt ☐

*I enclose a cheque/postal order payable to Sinclair Research Ltd for £ _____

*Please charge to my Access/Barclaycard/Trustcard account no. _____

*Please delete/complete as applicable _____

Signature _____

PLEASE PRINT

Name: Mr/Mrs/Miss _____

Address _____

FREEPOST – no stamp needed. Prices apply to UK only. Export prices on application.

BAKER 50 WATT AMPLIFIER

£69
Post £2



Superior quality ideal for Hi-Fi/PA systems. Discos and Groups. Two inputs with Mixer Volume Controls. Master Bass, Treble and Gain Controls. 50 watts RMS. Three loudspeaker outlets 4, 8, 16 ohm. AC 240V (120V available).

BAKER 150 Watt AMPLIFIER 4 Inputs £89

Mono Slave 150W £75. post £2 Stereo Slave £125. post £2

DRILL SPEED CONTROLLER LIGHT DIMMER KIT. Easy to build kit. Controls up to 480 watts AC mains. £3

DELUXE MODEL Ready Built. 800 watts. £5

STEREO PRE-AMP KIT. All parts to build this pre-amp. 3 inputs for high, medium or low gain per channel, with volume control and P.C. Board. Can be ganged to make multi-way stereo mixers. £2.95

SOUND TO LIGHT CONTROL KIT MK II

Complete kit of parts, printed circuit. Mains transformer. 3 channels. Up to 1,000 watts each. Will operate from 200MV to 100 watts signal source. Suitable for home Hi-Fi £15 and all Disco Amplifiers. Cabinet extra £4.50. Post 95p

OR COMPLETE READY BUILT IN CABINET £27

200 Watt Rear Reflecting White Light Bulbs. Ideal for Disco Lights. Edison Screw 75p each or 6 for £4 or 12 for £7.50.

TINTED PLASTIC EQUIPMENT COVERS

Sizes: 14½ x 12½ x 3in. £5. 16½ x 15 x 4in. £5.

14 x 13 x 3in. £5. 18 x 12½ x 3in. £5. 16½ x 13 x 4in. £5.

17½ x 13½ x 4in. £5. 21½ x 14½ x 2in. £5. POST £1.50.

R.C.S. LOW VOLTAGE STABILISED POWER PACK KITS

£3.95. Post 65p.

All parts and instructions with Zener diode printed circuit, mains transformer 240V a.c. Output 6 or 7.5 or 9.1V d.c. up to 100mA or less. Please state voltage required.

PP BATTERY ELIMINATOR BRITISH

£4.50

Mains stabilized power-pack 9 volt. 400mA D.C. with overload cut out. Size 5 x 3½ x 2½in. Post 50p. DELUXE MODEL

Switched 3, 6, 7.5, 9 volt. 400mA D.C. Stabilized. £7.50. Post £1

240V MAINS TRANSFORMERS

250-0-250 80mA 6.3V, 3.5A, 6.3V 1A £5.00 £2

350-0-350 250mA 6.3V 6 amp. £12.00 £2

220V 25mA, 6.3V 1A £2.50 £1

220V 45mA, 6.3V 2A £3. 250V 60mA, 6.3V 2A £3.50 £1

GENERAL PURPOSE LOW VOLTAGE

2A, 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30V £6.00 £2

1A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £6.00 £2

2A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £10.50 £2

3A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £12.50 £2

5A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £18.00 £2

6V 3 amps £2.00 £1 15-0-15V 2 amps £3.75 £1

6-0-6V, 100mA £1.50 £1 16V 2 amps £3.00 £1

9V 250mA £1.50 80p 20V 1 amp £3.00 £1

9V 3 amp £3.50 £1 20-0-20V 1 amp £3.50 £1

9-0-9V 50mA £1.50 80p 20-40-20V 1 amp £4.00 £2

10-30-40V 2 amps £3.50 £1 30V 1½ amp £3.50 £1

12V 3 amps £3.50 £1 30V 5 amps and £4.50 £2

6-0-6V 1½A £3.50 £1 17-0-17V 2A £4.50 £2




£6.50 post 65p MINI-MULTITESTER

Deluxe pocket size precision moving coil instrument. Impedance + Capacity - 4000 ohms. Battery included. 11 instant ranges measure: DC volts 5, 25, 250, 500. AC volts 10, 50, 500, 1000. DC amps 0-250µA, 0-250mA. Continuity and resistance 0 to 600K ohms.

De-Luxe Range Doubler Model, 50,000 ohms. £18.50. 7 x 5 x 2in. Post £1

NEW PANEL METERS £4.50

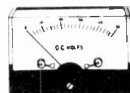50µA, 100µA, 500µA, 1mA, 5mA, 50mA, 100mA, 25 volt, VU Meter. 500mA, 1 amp, 2 amp. Facia 2½ x 2 x 1½in. Post 65p.



BLANK ALUMINIUM CHASSIS. 6 x 4in. £1.45; 8 x 6in. £1.80; 10 x 7in. £2.30; 12 x 8in. £2.60; 14 x 9in. £3.00;

16 x 10in. £2.90; 16 x 10in. £3.20. All 2½in. deep. 18 swg.

ALUMINIUM PANELS. 18 swg. 6 x 4in. 45p; 8 x 6in. 75p;

14 x 3in. 75p; 10 x 7in. 95p; 12 x 8in. £1.10; 12 x 5in. 75p; 16 x 6in. £1.10; 14 x 9in. £1.45; 12 x 12in. £1.50; 16 x 10in.

£1.75. ANGLE ALI. 6 x 2 x 3in. 18 swg. 25p.

ALUMINIUM BOXES. 4 x 4 x 1½in. £1. 4 x 2½ x 2in. £1.

3 x 2 x 1in. £1. 6 x 4 x 2in. £1.60. 7 x 5 x 3in. £2.40.

8 x 6 x 3in. £2.50. 10 x 7 x 3in. £3. 12 x 5 x 3in. £2.75.

12 x 8 x 3in. £3.60. All 18 swg with lids.

HIGH VOLTAGE ELECTROLYTICS

2/350V 35p 8+8/450V 75p 80+40/500V £2

4/350V 35p 8+16/450V 75p 50+50/300V 50p

8/450V 45p 16+16/450V 85p 100+100/275V 65p

32/350V 50p 32+32/450V £1.20 150+200/275V 70p

32/500V 75p 32+32/500V 75p 220/450V 95p

50/450V 95p 32+32/500V £1.80 32+32+32/325V 90p

HEATING ELEMENTS, WAFER THIN Semi-flexible.

11 x 9 x .in. Operating voltage 240V, 250W approx. Suitable for Heating Pads, Food Warmers, Convector Heaters, Propagation, etc. Must be clamped between two sheets of metal, etc.

ONLY 60p EACH (FOUR FOR £2) ALL POST PAID.

THE "INSTANT" BULK TAPE ERASER

Suitable for cassettes and all sizes of tape reels. A.C. mains 200/240V. £9.50 Post 95p

Ideal all Computer, Tapes, Discs, Cassettes.

HEAD DEMAGNETISER PROBE £5.00.



A.C. ELECTRIC MOTORS POST 75p.

2 Pole, 240V, 0.2 Amp. Spindle -

1-43 x 0.212in. £1.75. 2 Pole,

240V, 0.15 Amp Double spindle -

1-75 x 0.16in. Each £1. 2 Pole,

120V, .5 Amp Spindle - 0.75 x

0.2in. Two in series - 240V, 50p


each. Brush Motor. From a Food

Mixer 240V, .3 Amp High Speed

and Powerful Spindle - 0.5 x

0.25in. £2.95. Good Selection.

B.S.R. Motors £4. Garrard Motors £5.

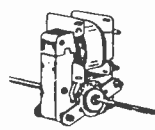

BAKER LOUDSPEAKERS

Model	Ohms	Inch	Watts	Type	Price	Post
Major	4, 8, 16	12	30	Hi-Fi	£14	£2
Superb	8, 16	12	30	Hi-Fi	£24	£2
Auditorium	8, 16	12	45	Hi-Fi	£22	£2
Auditorium	8, 16	15	60	Woofer	£34	£2
Group 45	4, 8, 16	12	45	PA	£14	£2
Group 75	4, 8, 16	12	75	PA	£18	£2
Group 100	8, 16	12	100	Guitar	£24	£2
Disc 100	8, 16	12	100	Disc	£24	£2
Group 100	8, 16	15	100	Guitar	£32	£2
Disc 100	8, 16	15	100	Disc	£32	£2

CROSSOVERS. 2-WAY 3000 c/s 30 watt 8 or 15 ohm £3.

3-way 950 cps/3000 cps. 40 watt rating. £4. 3-way 60 watts £6.

LOUDSPEAKER BARGAINS

3 ohm, 5in, 7x4in, £2.50; 6in, 8x5in, £3; 8in, £3.50; 10in, £5.

8 ohm, 2½in, 3in, £2; 5in, £2.50; 6in, £3; 8in, £4.50; 10in, £5.

12in, £6. 15 ohm, 3½in, 5x3in, 6x4in, £2.50.

25 ohm, 3in, £2; 5x3in, 7x4in, £2.50. 120 ohm, 3½in dia. £1.

DISCO MIXER. 240V, 4 stereo channels, 2 magnetic, 2

ceramic/tape, 1 mono mic channel, twin v.u. meters, headphone

monitor outlet, slider controls, panel or desk mounting, grained

aluminium fascia. £40. Post £2.

DELUXE STEREO DISCO MIXER/EQUALISER as above

plus L.E.D. V.U. displays 5 band graphic equaliser, left/right fader,

switchable inputs for phono/line, mike/line.

Headphone Monitor, Mike Talkover Switch £95. PP £2.

BOOKSHELF HI-FI ENCLOSURES TEAK £30 pair.

18 x 11 x 6in, 10 watts, 8 or 4 ohm, 2 way system. Post £2.

METAL PLINTH cut for Garrard or BSR

Size: 16 x 14 x 3in £4.00. Silver or Black finish. Post £2.

B.S.R. P204 SINGLE PLAYERS POST £2 each

SPECIAL OFFERS

Two speed 33/45 rpm Hi-Fi Decks with Stereo Cartridges,

cueing device and snake arm.

Ceramic Cartridge - 240V AC £15 or 9V DC £18.

Magnetic Cartridge - 240V AC £20 or 12V DC £24.

B.S.R. SINGLE PLAYER P170 RIM DRIVE £20.00

3-speeds 11in. turntable, "Slim" arm, cueing device, stereo

ceramic cartridge. 240V AC. Post £2.

B.S.R. DE-LUXE AUTOCHANGER £18

Stereo cartridge, plays all records. 3-speed. 240V AC. Post £2.

DECCA B.S.R. TEAK PLINTH 18½ x 14½ x 4in.

Space for small amplifier. BSR Board £5 post £1.50.

With Garrard Board £3 post £1.50. PVC covers £5 extra.

RADIO COMPONENT SPECIALISTS

Dept. 3, 337, WHITEHORSE ROAD, CROYDON,


SURREY, U.K. TEL: 01-684 1665

Post 50p Minimum. Callers Welcome.

Closed Wed. Same day despatch.

Access-Barclay-Visa. Lists 31p.

PE CAR COMPUTER

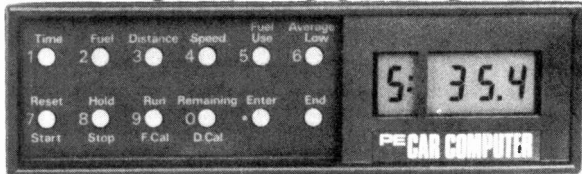

"One of the neatest, most comprehensive and most useful of these car computers that we have yet come across..."

Practical Motorist

- ★ Economy - save petrol by improving your driving technique and improving the tuning of your car.
- ★ Performance - dynamic checks on timing to improve performance and economy.
- ★ Security - protect your car by disabling the ignition. Enter a personalised combination to restart.
- ★ Attractive, easy to fit, easy to operate - comes complete with all parts needed. Full instructions provided.
- ★ Imperial or metric read outs.

The PE car computer has been specifically designed as an integral part of your car dashboard. Using highly accurate speed and petrol flow sensors it allows you to improve the fuel efficiency of your car by providing information on fuel consumption and tuning. In all over 30 functions including instant and average miles per gallon (or litres per 100 kilometres), estimated time to arrival, fuel needed to complete a journey, speed needed to meet an arrival time, acceleration tests, standing quarter miles and many more.

PE car computer: £88.50
Complete kit of parts: £78.50
Ignition cut-out £7.75

All prices include VAT. Allow £1 post & package. Goods by return. Send S.A.E. for list of separately available parts.



PIMAC SYSTEMS LTD

20 Bloomfield Road, Moseley, Birmingham B13 9BY.

Tel: 021-449 0384


OPEN FRAME MONITORS AVAILABLE FOR OEM'S

The 'PRINCE' of Monitors

offers better Monitoring.

24MHz Bandwidth - ensures a clear crisp display.

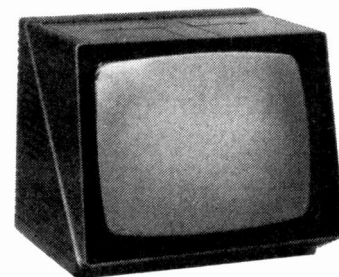Available with P4 White P31 Green AND L1 ORANGE



Scan 625 lines/50Hz. Deflection 110°. Active raster. 240x172mm. Bandwidth (3dB): 10 Hz-24 MHz (at 3dB points). Character display: 80 characters x 24 lines. Horizontal frequency: 15625 Hz ± 0.5 KHz. Vertical frequency: 50 Hz. Horizontal linearity: ± 3%. Vertical linearity: ± 2%. Geometric distortion: ± 1.5%. EHT (at zero beam current): 13kV ± 0.5kV. Power drain: 30 Watt approx. Voltage supply: 110V A.C. 50 Hz/220V A.C. - 50 Hz/240V A.C., 50Hz/ ± 10% upon request. Video input: 2 x BNC - or CINCH - or PL 259, (composite video) negative sync, input 0.5-4V p.p. across 75 Ohms. X Ray radiation: conforms to I.E.C. Spec. No. 65. Overall dimensions: 320 x 270 x 265 mm. Weight: 7 Kg. approx. Ambient temperature: 0-45°C.

OTHER CROFTON PRODUCTS INCLUDE: Computer peripheral equipment. Frame grabber, Floppy disk drives, Floppy disks, Computer power supplies, C.C.T.V. monitors, Uncensored monitors, Monitor P.C.B.s., Cathode ray tubes, VHF/UHF modulators, Video switchers, Video distribution amplifiers, Camera housings, Pan and tilt units, Camera lens, Camera tubes, Printed circuit board service.

CROFTON ELECTRONICS LTD

35, Grosvenor Road, Twickenham, Middx, TW1 4AD.
Telephone: 01-891 1923/1513 Telex: 295093 CROFTN G

Cheap Imitations?



Microdoctor

is an alternative to AUTOMATIC TEST EQUIPMENT which can be very expensive. MICRODOCTOR is perfectly adequate for diagnosing faults in microprocessor boards or computers in the REPAIR SHOP or on the PRODUCTION LINE. Reports are PRINTED on the integral thermal printer. Tests supported are CHECKSUM, RAMTEST, WAIT, READ, WRITE, I/O READ, I/O WRITE, DUMP IN HEX, DUMP IN ASCII, TEST DATA LINES (for shorts between data, address and rails), SEARCH (for two specified bytes), MAP (print a memory map of ROM, RAM, I/O and EMPTY SPACE). Supports both multiplexed and non-multiplexed address/data. Standard software will also DISASSEMBLE in Z80 mnemonics - other disassemblers cost extra. Programs for board-testing can be written in MINUTES - and retained for MONTHS even if the power is switched off (CMOS RAM is backed-up with rechargeable battery). Capacity is 15 different programs of 12 tests each. Included are two PROBE CONFIGURATION CARDS (One Z80, other uncommitted), PROBE with 24 inch cable and 40-pin DIL plug - and POWER SUPPLY. Extras available are 6502 disassembler retrofit ... £35. Clip-over PROBE (only needed if μ P is soldered-in) ... £35.

£295
+VAT



The Menta Z80 Development System

uses the MOST POWERFUL LANGUAGE OF ALL - direct ASSEMBLER MNEMONICS. MENTA has VISUAL AIDS to program development which the big systems lack: a TV display of PROGRAM, REGISTERS and STACK; single-step operation (watch the cursor move from instruction to instruction, see the register-contents change, observe stack operations, etc.) BUGS can be fixed immediately without reassembling. Full speed operation is supported too - with or without BREAKPOINTS. Designed originally for the Schools' Council to teach microprocessing, MENTA is a complex CONTROLLER in its own right, like any other Z80 system, with practical, commercial applications in ROBOTICS. Features include CASSETTE INTERFACE, ASSEMBLER/EDITOR, serial DISASSEMBLER (now included as standard), 24 bits of I/O - also TV FLYLEAD. POWER SUPPLY and COMPREHENSIVE MANUAL with SOURCE-CODE LISTING.

£99
+VAT

Goodies from Dataman

Olivetti Typewriter Interfaces

for ET121 and ET221 machines which permit the typewriter to be used as a DAISY WHEEL PRINTER for computers implementing the RS232, IEEE 488 (PET) or CENTRONICS PARALLEL busses: almost all computers in fact. Great for word processing and letter-writing! Same price, fitting free if requested (you pay carriage on typewriter if we fit).

£195.00

Thandar Logic Analyser Enhancements

The THANDAR TA2080 LOGIC-ANALYSER was NOT designed by DATAMAN - but we like this instrument and use it for product development. When writing software we use SOFTY for ROM-EMULATION, following the program-flow on the TA2080 screen. We modified our TA2080 to make it more useful; adding an RS232 OUTPUT TO PRINTER - also Z80 and 6502 DISASSEMBLERS. Now we can follow program operation in MNEMONICS on-screen and print TIMING or STATE DIAGRAMS and DISASSEMBLED CODE. Cost of this RETROFIT kit (12K of program ROM, socket for RS232, interface board, instruction sheet) is, if fitted by us and purchased with a TA2080

£195.00

Softy 1 with PSU

Yes, we still have a few old faithful 3 rail EPROM PROGRAMMERS around, as seen in Kensington Science Museum, if you are still using 2708's get yourself this fine old classic at a bargain price

£95.00

Ultra-Violet Eprom Erasers from

£33.00



Softy Eprom Programmer/Emulator

SOFTY has functions equal, at least, to equipment which sells for over £500. SOFTY EMULATES AND PROGRAMS 2716, 2516, 2732, 2532 EPROMS. (The type is selected by a personality switch. SOFTY will copy any of these EPROMS to any other). SOFTY has a HEX KEYPAD, a fast CASSETTE INTERFACE, a MEMORY MAP TV DISPLAY with powerful editing - such as INSERT, DELETE, SHIFT-BLOCK and many other facilities - too many to list here. RS232 SERIAL and CENTRONICS PARALLEL routines for INPUT and OUTPUT are standard. The price includes TV FLYLEAD, POWER SUPPLY and ROM EMULATOR CABLE WITH 24 PIN DIL PLUG. SOFTY is used as a DEVELOPMENT SYSTEM for new products or just as a STAND-ALONE EPROM PROGRAMMER.

£169
+VAT

Dataman Designs

LOMBARD HOUSE,
CORNWALL ROAD,
DORCHESTER, DORSET DT1 1RX.
Telephone: Dorchester (0305) 68066
Telex 418442 DATAMAN

Prepaid orders normally shipped by return.
Prices include first-class recorded post in UK.
Securitor, Red Star, etc. at extra cost.
VAT should be added at current rates.

All our own work!
Dataman

ELECTRONICS IS A FINE HOBBY

VELLEMAN-KIT



Velleman electronic kits are designed using the latest technologies, they are well packaged, include diagrams and instructions for assembly and application, and are graded by difficulty.

The kits listed below are some of the more popular ones and the prices include VAT and post and packing.

K1823	1 amp power supply	£6.99	K2577	Motor speed control	£7.59
K1874	Running light	£12.56	K2557	Digital Thermometer	£26.57
K2543	Transistor ignition	£9.97	K1682	Microprocessor timer	£48.37
K2565	Tape/Slide synchroniser	£9.66	K1771	FM Oscillator	£5.45
K2569	Three tone chime	£6.56	K611	7 Watt amplifier	£5.14
K2575	Microprocessor doorbell	£15.53	K2580	Powerswitch dimmer	£9.34

Our free illustrated catalogue is available on request from:

Velleman (U.K.) Limited,
P.O. Box 30,
St. Leonards on Sea,
East Sussex TN37 7NL.
Tel: 0424 753246.



Stocking distributors:

Baxol Tele Exports: Ballinaclesh, Rathdrum, Co. Wicklow, Rep. of Ireland.
S & R Brewster Ltd: Union Street, Plymouth, Devon.
Marshall's Electronics: 85 West Regent Street, Glasgow.



Revolution in circuit
board maker kits from
leading manufacturer

CM100
CIRCUIT MAKER

The CM100 Circuit Maker provides everything necessary to produce positive photographic film masters from same-size published circuit layouts and to make either single or double-sided boards from these or other positive film masters.

Features

- Economic and simple to use.
- No expensive equipment required e.g. darkroom, UV box, cameras etc.
- Photographic experience not needed.
- Simple etching process.
- Universal exposure and assembly frame custom-designed, professional quality.
- Ergonomically designed storage pack which includes free-standing shelf for chemicals.
- Step-by-step instruction manual, workbench and trouble-shooting charts provided.
- Special clearing process ensures excellent clear positive film masters.
- Photoresist available in non-aerosol form to eliminate 'spotting' when applied to the board.

Mercia Electronics, Coronet House, Upper Well St., Coventry CV1 4DF.

Send for full illustrated brochure
and price details, post to:

Name

Address

Signature

mercia
ELECTRONICS

Coronet House,
Upper Well Street
Coventry CV1 4AF
Tel: (0203) 58541

CAN WE SELL YOU SOME FRESH AIR?

ZEPHION
NEGATIVE ION GENERATORS



Dr J.B. Smith writes:- "Did you know that the air you breathe is made up of billions of tiny molecules, many of which may be either positively or negatively charged? ... The negatively charged molecules (called ions) are particularly interesting. For example, they attach themselves to dirt, smoke and pollen particles in the air making them heavier so that they fall to the ground, leaving behind purer air for you to breathe!"

The ZEPHION negative ion generator produces millions of these negatively charged molecules every second, flooding your home or office with invigorating mountain-fresh air.

Many users of these ion generators claim greatly increased alertness, loss of lethargy (particularly in stuffy, smoky offices) and relief from hay fever, asthma and many breathing problems."

BUILD IT YOURSELF!

clip the coupon

TO:- Dataplus Developments
81, Cholmeley road
Reading, Berks.
RG1 3LY TEL:- 0734 67027

NAME:-
ADDRESS:-

PLEASE SEND :-

☐ ZEPHION KITS @ £21.50p
(Kits include all parts)

☐ ZEPHION AIR TONERS
BUILT AND TESTED. @ £29.80p

Money immediately refunded if
items returned in good condition.

Prices include VAT & postage; allow 14 days for delivery.

DATAPLUS PE

SERVICE TRADING CO

WHY PAY MORE?

MULTI RANGE METER. Type MF15A a.c. d.c. voltmeter 10, 50, 250, 500, 1000. Ma 0-5, 0-10, 0-100. Sensitivity 2000V/24 range, diameter 133 by 93 by 46mm including test leads. Price £17.00 plus 75p P. & P. (£18.91 incl. VAT & P).

METERS (New) - 90 mm DIAMETER

A.C. Amp., 0-1A, 0-5A, 10A.
A.C. Volt, 0-300V.
A.C. Amp., 0-1A, 0-5A, 10A, 0-50A, 0-100A.
D.C. Volt, 15V, 30V.
All types £3.60 ea. + P. & P. 75p (£5.00 incl. VAT), except 0-50A, 0-100A, D.C. price £6.00 - 75p P. & P. (£7.76 incl. VAT).

HEAVY DUTY SOLENOID, m.f. by Magnetic Devices, 240V, A.C. Intermittent operation. Approx. 20 lb. pull at 1.25 in. ex-equip. Tested. Price: £5.95 P. & P. £1.50. (£8.57 incl. VAT). R.&T.

240V A.C. SOLENOID. Approx. 10lb pull. 10% rnf. Size 80x33x26mm. Price £1.75 + P. & P. 54p (£2.63 incl. VAT & P).

12V D.C. SOLENOID. Price: £1.50 + P. & P. 40p. (£2.18 incl. VAT). N.M.S.

WESTCOOL SERIES D6 Model A3 24V. D.C. Price £1.50 + 50p p. & P. (Total incl. VAT £2.30).

WESTCOOL SERIES D4 Model A. 24V. D.C. Price £1.00 + 30p p. & P. (Total incl. VAT £1.50). N.M.S.

AG/GT 24V. D.C. 70 ohm Coil Solenoid. Push or Pull. Adjustable travel to 3/16 in. Fitted with mounting brackets and spark suppressor. Size: 100 x 65 x 25 mm. Price: 3 for £2.85 P. & P. 50p. (min 3 off.) (£3.85 incl. VAT). N.M.S.

MINIATURE SOLENOID FLUID VALVE

12V D.C. 15 ohm coil normally closed. Stainless steel body with variable flow adjuster 1/2" B.S.T. inlet and outlet.
Size: 58x27x25mm. Weight: 130 gr.
Price: £2.60 + 35p P. & P. (Total incl. VAT £3.39).

230V A.C. SOLENOID OPERATED FLUID VALVE. Media: Air, Gas, 7 psi. Water 5 psi. 3/8" inlet/outlet. Forged brass body. Normally closed. Manufactured by Durance Asco. Price: £5.50 + £1.00 p. & P. (Total incl. VAT - £7.48).

SOLID STATE EHT UNIT

Input 230V a.c. Fully isolated output 10mm spark. Approx. 15kV. Built in 10 sec. Timer. Easily modified for 20 sec, 30 sec, to a continuous operation.
Designed for boiler ignition. Dozens of uses in the field of physics and electronics, eg. supplying neon or argon tubes etc.
Size: Length 155mm, width 85mm, height 50mm. Weight 530 grammes. Price £5.00 + 75 pence post & packing. Total incl. VAT £6.61. N.M.S.

A.E.G. CONTACTOR

Type L56/L11. Coil 240V 50 Hz. Contacts - 3 make: 600V. 20amp. 1 break. 600V. 20amp. Price: £5.75 P. & P. 75p (£7.47 incl. VAT). N.M.S.

AMF CONTACTOR

230V AC coil 2 c/o 25amp contacts £5.50 P. & P. 75p total £7.19.

ARROW-HART MAINS CONTACTOR

Cat. No. 130A30. Coil 250V or 500V. AC Contacts 3 make 50 amp up to 600V. AC 20 hp at 440V. 3 phase. 50 Hz. Price: £7.75 + p&p £1.00 (total incl. VAT £10.06).

SMITH BLOWER

Type FFB. 1706. Small, quiet, smooth running. 240V, A.C. operation. Output aperture 45x40mm. Overall size 135x165mm. Flange mounting. Price: £4.75 P. & P. £1.00. (£6.61 incl. VAT). Other types available. S.A.E. for details. N.M.S.

MICRO SWITCHES

Sub. Min. Honeywell Lever m/s type 3115m 906ft. 10 for £3.50 post paid (£4.03 incl. VAT). These V3 types.

Button type 10 for £3.00 (£3.45 incl. VAT).

Short Lever type 15amp. rating (Crouzet) 10 for £4.00 (£4.60 incl. VAT).

Long Lever 10 amp C/O. 10 for £4.50 (£5.18 incl. VAT).

Cherry E51 Rotary action low torque microswitch 5 amp contact £3.50. (£4.03 incl. VAT). N.M.S.

D.P. C/O lever m/s switch mfg. by Cherry Co. USA. Precious metal low resistance contacts. 10 for £3.00 P. & P. 50p. (£4.02 incl. VAT). (min. order 10). N.M.S.

A.C. Wkg. TUBULAR CAPACITORS.

Fraction of makers price. Motor start etc.		
1.5 mfd. 440V.A.C.	60p	5 mfd. 400V.A.C. £1.25
2 mfd. 250V.A.C.	60p	5.3 mfd. 180V.A.C. 60p
2 mfd. 450V.A.C.	75p	5.4 mfd. 280V.A.C. 75p
2.2 mfd. 440V.A.C.	75p	7.5 mfd. 200V.A.C. £1.00
3 mfd. 440V.A.C.	£1.00	15 mfd. 440V.A.C. £2.50
4.1 mfd. 440V.A.C.	£1.06	

P. & P. up to 2.5 mfd. 25p. 3 mfd. to 20 mfd. 50p. All plus VAT.

SPECIAL DISCOUNT FOR BULK ORDERS. N.M.S.

24 volt. D.C. BLOWER UNIT

Precision 24 volt. D.C. 0.8 amp Blower that works well on 12V 0.4 amp D.C. Producing 30 cu. ft. min at normal air pressure. £4.50 P. & P. 75p. (Incl. VAT £6.04). N.M.S.

INSULATION TESTERS NEW!

Test to I.E.E. Spec. Rugged metal construction suitable for bench or field work. Constant speed clutch Size L Bin W 4in H 6in weight 6lb. 500V. 500mohm. £49.00 + £2.00 p&p (total incl. VAT £58.65). 1000V. 1000mohm. £55 P. & P. £2.00. (£65.55 incl. VAT). S.A.E. for leaflet.

Yet another outstanding offer.

IMFD 600V Dubilier wire ended capacitors, 10 for £1.50 P. & P. 50p. (£2.30 incl. VAT). (Min. 10) N.M.S.

VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/240V a.c. 50/60 OUTPUT 0-260V

200 watt (1 amp inc. a.c. voltmeter)	£15.00
0.5 KVA (2 1/2 amp MAX)	£19.00
1 KVA (5 amp MAX)	£25.00
2 KVA (10 amp MAX)	£41.00
3 KVA (15 amp MAX)	£49.00
5 KVA (25 amp MAX)	£79.00
10 KVA (50 amp MAX)	£174.00
15 KVA (75 amp MAX)	£270.00

3-PHASE VARIABLE VOLTAGE TRANSFORMERS

Dual Input 200-240V, or 380-415V. Star connected.
3KVA 5 amp per phase max. £118.00 Carriage, packing & VAT extra.
6KVA 10 amp per phase max. £162.00
10KVA 16 amp per phase max. £329.00

LT TRANSFORMERS

Phone for enquiries or send s.a.e. for leaflet.

SNIPS OF THE MONTH

National R. Relay 12V. D.C. high speed 1 c/o. 1 amp contacts. Magnetically shielded. 1 pitch. Price: £1.25 post paid (£1.44 incl. VAT).

Omron Type M. 24V. A.C. 4 c/o. h.d. Price: 80p post paid (92p incl. VAT). Base 20p post paid (£1.12 incl. VAT).

220/240V. Primary secondary 24V & 4A. LT. Transformer, fully shrouded. Price: £4.50 + £1 p. & p. (£6.38 incl. VAT).

INDUSTRIAL STROBE KIT

Suitable for both Industrial and Educational purposes. Kit when assembled produces a variable speed 1 to approx. 70 flash per second. Light output approx. 0.5 joules. Price, less case. £27.00 + £2.00 P. & P. (total incl. VAT £33.36).

Super Hy-Light Strobe suitable disco, theatrical use etc. (approx. 16 joules). Price £40.

P. & P. £2.00 (£42.31 incl. VAT).

Suitable cases for either type £11.00 P. & P. £2.00 (£14.95 incl. VAT). Super Hy Light Strobe Kit, details on receipt of foolscap s.a.e.

XENON FLASHGUN TUBES

Range available from stock. S.A.E. for details.

ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES

4ft. 40 Watt £8.70 incl. VAT £10.00 (callers only).

2ft. 20 Watt £6.20 P. & P. £1.25 (£8.57 incl. VAT).

(For use in stan bi-pin fittings).

12in. 8 Watt £3.00 P. & P. 45p (£3.97 incl. VAT).

9in. 6 Watt £2.50 P. & P. 45p (£3.39 incl. VAT).

6in. 4 Watt £2.50 P. & P. 45p (£3.39 incl. VAT).

Complete ballast unit for either 9" or 12" tube 230V AC or £5.50 P. & P. 55p (£6.96 incl. VAT). Also available for 12V DC or £5.50 P. & P. 55p (£6.96 incl. VAT).

BLACK LIGHT BULBS

Self-ballasted Mercury U.V. 175W Bulbs, available for either B-8 c/o. or E.S. fitting. Price incl. p&p & VAT £11.50.

400W U.V. lamp and ballast complete. Price £38.00 + £3.50 p&p (total incl. VAT £47.73).

400 Watt U.V. lamp only, price £14.00 - £2.00 p&p (total incl. VAT £18.40).

Black Light U.V. Tubes from 6in to 4ft from stock. Foolscap s.a.e. for details.

***** EPROM ERASER! *****

Why waste money? Build your own EPROM ERASER for the fraction of the price of a made-up Unit.

Complete Kit of parts less case to include 12" 8 watt 2537 Angst Tube, Ballast Unit, pair of bi-pin leads.

Neon Indicator, Safety Microswitch, on/off Switch, and Circuit, LESS CASE. Price: £13.60 + 75p P&P (Total incl. VAT £16.50).

WARNING: Tube used in this circuit is highly dangerous to the eyes. Unit MUST be fitted in suitable case.

***** SUPERIOR Quality Precision Made *****

NEW POWER RHEOSTATS

New ceramic construction, embedded winding heavy duty brush assembly, continuously rated.

25 WATT 5/10/25/50/100/250/500/1kΩ 1.5kΩ £3.10 P. & P. 30p (£3.91 incl. VAT).

50 WATT 250Ω £5.50 P. & P. 50p (£6.90 incl. VAT).

100 WATT 1/5/10/25/50/100/250/500/1kΩ/1.5kΩ/2.5kΩ/3.5kΩ £7.25 P. & P. 75p (£9.14 incl. VAT).

Black, Silver, Skirted knob calibrated in Nos. 1-9 1/2 in. dia. brass bush. Ideal for above Rheostats 24p each + VAT.

RELAYS

Wide range of AC and DC relays available from stock. Phone or write in your enquiries.

230/240V A.C. 3 c/o. 11 pin base. Sealed 5 amp contacts £1.35 plus P. & P. 30p (£1.90 incl. VAT).

KMKI Relay. 230V. A.C. 1 c/o open type 10 amp contact, m.f. by 'Keyswitch'. 80p P. & P. 25p (£1.21 incl. VAT). 5 for £3.75 postpaid (£4.32 incl. VAT).

24V A.C. Sealed 3 c/o. 10a. 11-pin. £1.50 + 25p P. & P. (£2.01 incl. VAT).

24V D.C. Sealed 3 c/o. 7a. 11-pin. £1.35 + 30p P. & P. (£1.90 incl. VAT).

24V D.C. 2 c/o. 7 amp contacts. Sealed, octal base. £1.30 P. & P. 30p (£1.84 incl. VAT).

VERY SPECIAL OFFER - 12V DC. 2 make contacts. NEW. 3 for £1.75 - 25p P. & P. (£2.30 incl. VAT).

D.C. Relays: Sealed 12V 1 c/o 7 amp octal base £1.00 P. & P. 30p (£1.50 incl. VAT). Sealed 12V 3 c/o 7 amp 11-pin £1.35 P. & P. 30p (£1.90 incl. VAT). 24V. Sealed 3 c/o 7 amp 11-pin £1.35 P. & P. 30p (£1.90 incl. VAT).

GEARED MOTORS

5rpm 240V A.C. Mf. by Carter. £5.50 + £1.00 P. & P. (£7.48 incl. VAT).

7 1/2 rpm Motor approx. 30 lb. in. 110V A.C. complete with Transformer for 240V A.C. £9.25 + £1.50 P. & P. (total incl. VAT £12.94).

71rpm WYNSCALE motor approx. 20lb inch. A.C. supplied with auto transformer 240V. A.C. operation. £9.75 P. & P. £1.50 (£12.94 incl. VAT). N.M.S.

30 rpm. 230/240V. a.c. 50lb in. mf. PARVALUX. Price £15.50 P. & P. £2.00 (£20.13 incl. VAT). N.M.S.

42 R.P.M. 110 A.C. 50Hz. 100lb incl. reversible will operate on 230 A.C. Speed remains at 42 R.P.M. but torque reduces by 50%. Price £16.50 P. & P. £2.50 (£21.28 incl. VAT). N.M.S.

Transformer for 240 Volt A.C. op. £13.80 incl. VAT.

38.3 rpm GEARED MOTOR, torque 35 lb. in. reversible. 115V A.C. inc. start capacitor. Price: £10.50 + £2.00 p&p (total incl. VAT £14.38).

Suitable Transformer 230V A.C. operation. Price: £6.50 + 50p p&p (total incl. VAT £8.05). N.M.S.

N.E.C. GEARED MOTOR. 152 rpm 200 lb. in. 230V A.C. 50 Hz. Ratio 9.2 to 1. Non reverse. Incl. capacitors. Fraction of maker's price: £37.50 + Carr. & VAT. N.M.S.

200 rpm. 35lbs. in. 115V. 50KHz. Price: £16.50 P. & P. £2.00 (£21.28 incl. VAT). N.M.S.

Suitable Transformer for 230/240V. a.c. Price: £6.00 P. & P. £1.50 (£8.62 incl. VAT). N.M.S.

230/240V A.C. SYNCHRONOUS GEARED MOTORS

1rpm, 2rpm, 6rpm, 12rpm. 6 revs. per day. 12 revs. per day. Any type. Price: £3.90 + 40p p. & p. (£4.94 incl. VAT).

GEARED MOTOR. 120 rpm 1/10 hp approx. 15 lb. in. 230V. A.C. Cont. Rating. Non-reversible. Size 150mm x 90mm x 85mm spindle 8mm dia. - 30mm long. Complete with capacitor and relay for max. load starting. Offered at mere fraction of mfrs. price - £11.50 incl. of p. & p. & VAT.

Brand new CASSETTE TYPE MOTORS

3 types - BV. 7 1/2V. Price: 3 for £2.00 + 50p p. & p. (Total incl. VAT - £2.88).

230V a.c. FAN ASSEMBLY

Powerful continuously rated a.c. motor complete with 5 blade 6 1/2 in. Price £4.50 P. & P. 75p (£6.04 incl. VAT).

24V. D.C. GEARED MOTOR

24V. D.C. 200 rpm 10lbs/ins. continuously rated geared Motor mfg. by either Parvalux or Carter. Easily removed from chassis containing 9x24V. D.C. Solenoids, microswitches, friction clutch, precision gearing etc. etc. Ex-equipment London Transport Ticket Printer. Price: £8.00 P. & P. £2.00 (£11.50 incl. VAT).

SUB-MINIATURE PRECISION BUILT GEARED MOTOR

3-9v. D.C. operation, speed 2-6 RPM. Current consumption incredibly only

2-5 M.A. Ratio 1670:1. Torque approx 2lbs inch plus Motor - German Gearbox Swiss.

Size: L. 48 mm. Dia. 16 mm.

Shaft L. 5 mm. Shaft Dia. 2 mm.

Price £8.50 inc. P. & P. (Total incl. VAT £9.78).

THOMAS SINGLE DIAPHRAGM COMPRESSOR

Max. 20 psi 1 1/2 C.F.M. approx. 100 volts A.C. Price £16 - £2 p&p. Total £20.70 incl. VAT or Total £26.45 to include transformer for 230/240 volt A.C.

BLOWER/VACUUM PUMP. 3 phase A.C. Motor. 220/250V or 380/440V. 1.425rpm. 1/4 h.p. cont. Direct coupled to William Allday Alcosa carbon vane blower/vacuum pump. 0.9 cfm B hg. Price: £22.00 + £4.00 p&p (total incl. VAT £29.90).

VEEDER-ROOT PRE-SET COUNTER

Type MG1636. 3 fig. countdown any number from 999 to 001. 230V A.C. 2 Wheel setting. Changeover Microswitch to inform external circuitry on completion of countdown. Size: Width 85mm. Ht. 65mm. Dpth. 70mm. Price £4.00 - 75p P. & P. (Total incl. VAT £5.46).

SANGAMO WESTON TIME SWITCH

Type S251 200/250V. a.c. 2 on/2 off every 24 hours. 20 amps contacts with override switch dia 4 x 3 price £9.50 P. & P. £1.50 (£12.65 incl. VAT). Also available with Solarial R. & T.

Type S288 1 on, or 1 timed c/o every 24 hours, day omitting device. Price: £11.00 - £1.00 p. & p. (£13.80 incl. VAT). N.M.S.

Type S388. As above, plus 36-hours spring reserve. Less persp cover. Price: £13.00 - £1.00 p. & p. (£16.10 incl. VAT). N.M.S.

VENNER TIME SWITCH

ERD Time switch 200/250V a.c. 30 amp contact 2 on/2 off every 24 hrs. at any manually pre-set time. 36 hour Spring Reserve and day omitting device. Built to highest Electrician Board specification. Price £11.50 P. & P. £1.50 (£14.95 incl. VAT). R.&T.

A.E.G. TIME SWITCH

80amp. 2-on/off Spring Reserve Timeswitch, Price £15.50 P. & P. £1.50 (£19.55 incl. VAT).

Please allow 28 days for delivery

N.M.S. New Manufacturers Surplus R. & T. Reconditioned and Tested.

Personal callers only - Open Saturdays

9 Little Newport Street, London WC2H 7JJ

Phone 01-437 0576

SERVICE TRADING CO

57 BRIDGMAN ROAD, CHISWICK, LONDON W4 5BB 01-995 1560

ACCOUNT CUSTOMERS MIN. ORDER £10.00

All Mail Orders Callers
Ample Parking Space
Showroom open Mon-Fri.

PHONOSONICS SUPER SONIC DIY KITS

NEW MUSIC SUPER-KIT SERIES!

Basic functions plus a bit more! Self-contained but may be intercoupled. More are coming to ultimately achieve a modular sound synthesis & modification systems. All are mono, for stereo use 2. Will run from 9V to 15V DC supplies. Batteries not incl. Prices incl. UK P&P & 15% VAT. Sets incl. PCBs electronic parts, instructions. Most also incl. knobs, skts, sw's, wire, solder, box. For more info send S.A.E. (9 x 4 or bigger) for catalogue. Prices correct at press. E. & O.E. Despatch usually 7 days on most items. Payment: CWO mail order or collection by appointment. TEL 01-302 6184 Mon-Fri. Access, Barclay, Am Express accepted. Exports: Sterling payment please. Export catalogue £1.

SUPER-BOOST

Boost those outside octaves! Each unit has depth & range controls.

Super-Boost Bass SET-138-B £8.87
Super-Boost Treble SET-138-T £8.46

SUPER-CLEAN

Is hiss a problem? This could clean it up nicely.

SET-145 P.O.A.

SUPER-FREEKI

Gen-purpose freq-generator with Sine, Sq, Tri, Ramp, Pulse & variations. Switchable 0.4Hz-470KHz plus fine tune.

SET-128 £18.44

SUPER FUZZ

Spiky fuzz with fringing effect. 3 controls. Fringing Balance. Output.

SET-135 £12.99
Also, auto-control for deeper fringing from above.

SUPER-HUM-CUT

Humming badly? This steep notch filter really cuts live or recorded hum. Tunable for 25-100Hz.

SET-141 £11.43

SUPER-MIC-UP

Mic or guitar pre-amp with gain control & Bass & Treble cut sw's.

SET-144 £8.92
Ditto less tone sw's SET-147 £8.13

SUPER-MIX

2-chan mixer with variable input level & gain. No tone controls. Use Super-Tone if reqd. For more chans add several units.

SET-149 P.O.A.

SUPER-NOME

Variable metronome with audio-visual accented beat marker.

SET-143 £13.52

SUPER-PASS

Variable band-pass filter with gain & centre freq control.

SET-142 £9.69

SUPER-TONE

Tone control for Bass & Treble cut, gain, & range.

SET-139 £13.62

SUPER-TREM

A powerful tremolo with depth and rate controls.

SET-136 £10.71

SUPER-VIBE

Vibrato with extra Phasing & Reverb controls, plus rate & depth. An amazing unit!

SET-137 £23.99

SUPER-WAH

Wah-wah with auto & manual controls.

SET-140 £17.31

P.O.A. Price on Application - details in list.

VERY POPULAR - STILL AVAILABLE

GUITAR EFFECTS: 8 mode filter & envelope shaper for most instruments SET-42 £15.92

GUITAR FREQUENCY DOUBLER: Orig & doubled signals can be mixed SET-98 £11.75

GUITAR OVERDRIVE: Sophisticated Fuzz with filter & shape controls SET-56 £21.17

GUITAR SUSTAIN: Retains natural attack whilst extending note duration SET-75 £11.77

PHASER: 6-stage automatic unit with variable speed control SET-88 £21.08

LOTS OF OTHER STILL POPULAR KITS OF VARIOUS TYPES BIG & SMALL ARE IN OUR CATALOGUE.

PHONOSONICS

DEPT PE2D, 22 HIGH STREET, SIDCUP, KENT, DA14 6EH.
FOUNDED 1972. A DECADE OF DESIGN AND DELIVERY!

C.B.

C.B.

These are suitable for CB or standard audio use depending on socket type chosen (2 reqd for most - see below). For kit contents & order details see top left cols.

C.B. COMPRESSOR

Really helps avoid blasting your mods and adjacent channels! Preset it for the maximum that your rig will like and your signal strength won't top it.

SET-133-LS £12.37

FUNKY-WOBULO!

Add a wobble to your warble! A voice tremulant with depth & filtering modulation. 1 skt reqd.

SET-149 £11.49

FUNNY TALKER MK2

Modified ring modulator for fascinating metallic and modulated quality to your voice. Includes new high-gain pre-amp, voltage stabiliser, and output level control. SET-99-MK2-LS £19.06
Add-on kit for MK1 users to convert to the MK2 (box not required): SET-99ADN £3.39

MAD-RO!

Space invaders, machine gun, police cars, sounds like these & more from this 4-control unit. 1 skt reqd.

SET-146 £9.99

MULTIPLEXER

Are you using several front-end add-ons? This unit splits the microphone signal in up to 6 directions for feeding various extras, and also contains a six-input mixer for recombining the add-on signals onto one line. An extra two skts reqd for each to-from direction.

SET-132-LS £11.60

MUSICAL CALL SIGN

Programme your own individual 8-note call sign. Push button operated for use when you want.

SET-121-LS £14.23

ROGER TWO-GONG

Two-tone gong-like sound automatically activated at the end of transmission.

SET-126-LS £14.72

SIGNAL COMPARATOR

Uses special three-colour LEDs to give a visual indication of speech level. Also compares microphone level with levels from other units such as Roger Bleeps, etc. Helps avoid overmodulation and cross channel break-through.

SET-129-LS £16.70

SIMPLE REVERB

Enhances the spacious quality of your transmission, and at full control can produce that 'Monster-from-the-Deep' effect. With control over balance, echo and duration. The response from listeners is astonishing!

SET-122-LS £20.39

SINGLE ROGER

Gives a single bleep of a preset duration and pitch when the microphone switch is released at the end of transmission. SET-127-LS £10.07

SPEECH PROCESSOR

Dramatically improves the intelligibility of speech signals. We are making many sales on this directly because people have heard it on the air!

SET-110-LS £11.77

VOICE FILTER

For limiting the frequency band-width that reaches the rig from the microphone, helping to reduce background noise. Six selectable ranges plus by-pass.

SET-131-LS £12.97

VOICE OPERATED SWITCH

Release your hands for other things, let your voice do the switching for you!

SET-123-LS £13.80

CB POWER SUPPLY

From the mid-range of 13.8 volts, can be set anywhere between about 10V and 16V at approx. 300mA. Ideal for driving all these various CB add-ons! (Mic skts not required).

SET-130-LS £13.85

CONNECTORS AVAILABLE

4-pin chassis-socket SKT-SC4 46p plus P&P

4-pin line-socket SKT-LS4 P.O.A.

4-pin chassis-plug PLG-SP4 46p plus P&P

4-pin line-plug PLG-LP4 62p plus P&P

5-pin 180° DIN chassis-socket SKT-KS 16p plus P&P

5-pin 180° DIN line-plug PLG-KP 34p plus P&P

Std mono plus chassis-socket SKT-US 20p plus P&P

Std mono plus line-plug PLG-UP 18p plus P&P

If connectors ordered with kits in this ad, no P&P charge, else add 60p to total cost.

COMING SOON!

HISSING SID

JABBER-VOX

WHEEBY-JEEBY

and others!

watch our ads & lists.



Bigger and Better for 1982
the colourful Wilmslow Audio brochure
- the definitive loudspeaker catalogue!

Everything for the speaker constructor - kits, drive units, components for HiFi and PA.

50 DIY HiFi speaker designs including the exciting new dB Total Concept speaker kits, the Kef Constructor range, Wharfedale Speakercraft, etc.

Flatpack cabinet kits for Kef, Wharfedale and many others.

- ★ Lowest prices — Largest stocks ★
- ★ Expert staff — Sound advice ★
- ★ Choose your DIY HiFi Speakers in the comfort of our ★
two listening lounges
(Customer operated demonstration facilities)
- ★ Ample parking ★

Send £1.50 for catalogue
(cheque, M.O. or stamps - or phone with your credit card number)

- ★ Access - Visa - American Express accepted ★
also HiFi Markets Budget Card.



0625 529599

35/39 Church Street, Wilmslow, Cheshire SK9 1AS



Lightning service on telephoned credit card orders!
Please allow 7 days for delivery



TERRIFIC VALUE!!!

We have a big store to clear. 100 tons of stock must go. 10 kilo parcel of unused parts. Minimum 1,000 items includes panel meters, timers, thermal trips, relays, switches, motors, drills, taps and dies, tools, thermostats, coils, condensers, resistors, etc. etc. Individually would cost you a fortune!

YOURS FOR ONLY £11.50 plus £3.00 post.

IONISER KIT

Refresh your home, office, shop, work room, etc. with a negative ION generator. Makes you feel better and work harder - complete mains operated kit, case included £11.95 plus £2.00 postage.

CAR STARTER/CHARGER KIT

This kit has no doubt saved many motorists from embarrassment in an emergency you can start car off mains or bring your battery up to full charge in a couple of hours. The kit comprises: 250w mains transformer, two 10 amp bridge rectifiers, start/charge switch and full instructions. You can assemble this in an evening, box it up or leave it on a shelf in the garage, whichever suits you best.

Price: ONLY £12.50 + £3.00 post.

3 - 30V VARIABLE VOLTAGE

POWER SUPPLY UNIT

With 1 amp DC output, for use on the bench, students, inventors, service engineers, etc. Automatic short circuit and overload protection. In case with a volt meter on the front panel. Complete kit £13.80.

ZX81 OWNERS

Make yourself a full size keyboard! Key switches complete with plain caps. 6 for £1.15.

COMPUTER PRINTER FOR ONLY £4.95

Japanese made Epson 310 - has a self starting, brilliant drive motor. Complete with electronics - uses plain paper. Brand new with data. ONLY £4.95 plus £1.25 Post.

Cash, P.O. or cheque with order. Orders under £10.00, add 60p. Access & B/card orders by phone to Haywards Heath (0444) 454563. Delivery by return.

REVERSIBLE MOTOR WITH CONTROL GEAR

Made by the famous Franco Company this is a very robust motor, size approximately 7 1/2" long, 3 1/2" dia. 3/8" shaft. Tremendously powerful motor, almost impossible to stop. Ideal for operating stage curtains, sliding doors, ventilators, etc., even garage doors if adequately counter-balanced. We offer the motor complete with control gear as follows:

- 1 Franco motor with gear box. • 1 manual reversing and on/off switch. • 1 push to start switch. • 1 x 100w auto transformer. • 2 limit stop switches. • 1 circuit diagram of connections. £19.50 plus postage £2.50.

SPLIT MOTORS



Powerful mains operated induction motors with gear box attached. The final shaft is a 1/2" rod with square hole, so you have alternative coupling methods - final speed is approx. 5 revs/min. PRICE £5.50. Similar motors with final speeds of 80, 100, 160 & 200 r.p.m. same price.

8 POWERFUL BATTERY MOTORS (all different)

Suitable for models, meccanos, drills, remote control planes, boats, etc. £2.95.
12 VOLT MOTOR BY SMITHS
Made for use in cars, these are series wound and they become more powerful as load increases. Size 3 1/2" long by 3" dia. These have a good length of 1/2" spindle - price £3.45. Ditto, but double ended £4.25.

EXTRA POWERFUL 12 VOLT MOTOR

Made to work battery lawnmower, this probably develops up to 1/2 h.p., so it could be used to power a go-kart or to drive a compressor, etc. etc. £8.90 + £1.50 post. (This is easily reversible with our reversible switch - Price £1.15).

J. BULL (Electrical) Ltd. Established 30 YEARS
(Dept PE), 34 - 36 AMERICA LANE, HAYWARDS HEATH, SUSSEX RH16 3QU.

BEST SELLER



A quality digital multimeter for the price of an analogue.

The Beckman 3½ digit T100 multimeter offers:

- * numerous functions and ranges (200mV to 1000Vdc or 750V ac; 200µA to 10A ac or dc; 200 Ω to 20M Ω)
- * good accuracy (0.5% on Vdc)
- * numerous extras (like dedicated diode test range, high or low power ohms, numerous accessories)
- * easy operation and excellent protection

Also available is the T110 model, with 0.25% accuracy and buzzer for continuity testing, at £68.50 (inc. VAT, p&p).

BECKMAN

Beckman Instruments Ltd
Electronic Components UK Sales and Marketing Organisation
Mylen House, 11 Wagon Lane, Sheldon, Birmingham B26 3DU
Tel: 021-742 7921 Telex: 336659

Please send me:

() T100 meters at £57 (inc. VAT, p&p)

() T110 meters at £68.50 (inc. VAT, p&p)

I enclose a cheque or P.O.


(payable to Beckman Instruments Ltd) for: £

Name:

Address:

Please allow 14 days for delivery.

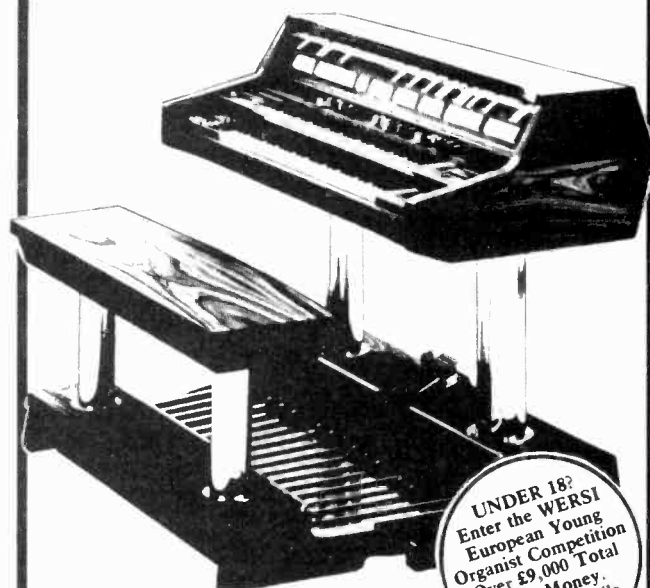With WERSI...
YOURSELF...
and just a little patience
THIS...



WERSI presents their range of electronic organs and accessories to YOU, the do-it-yourselfer. Now, you can build your own customised organ in a style to suit your own home, be it spinet or console, contemporary or traditional styling. For less than half the cost of a ready assembled model you can own a WERSI — superb organs that are the choice of leading professionals like Klaus Wunderlich and Franz Lambert. It's easy — many thousands have been built and there is a price range to suit every pocket. With the minimum of tools, revolutionary simplified electronics and step-by-step instructions — anyone who can read can build a WERSI. WERSI's unique up-dating service and accessory systems mean the organ will not easily become outdated — Build WERSI and you create a lifetime investment.

Want to know more about WERSI? We have successfully marketed these organs in the UK for many years. Our technical support service is second to none. There's a friendly welcome and free demonstration for you at any WERSI showroom. Alternatively fill in the coupon and we'll rush you all you want to know about the wonderful world of WERSI, with the address of your nearest showroom.

WERSI
ORGANS & PIANOS

WERSI ORGANS & PIANOS LTD
14-15 Royal Oak Centre, Brighton Road,
Purley, Surrey. Tel: 01-668 9733.

PLEASE SEND ME FURTHER DETAILS OF THE WERSI RANGE

NAME

ADDRESS

Send to WERSI ORGANS & PIANOS LTD,
14-15 Royal Oak Centre, Brighton Road, Purley, Surrey

PE

TRANSFORMERS

+VAT 15%

Delivery 7 days

30 V RANGE (2x15V tapped secs)
Sec Volt 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24,
30V or 12V-0-12V or 15V-0-15V.

Ref	30V	15V	Price	P&P
112	0.5	1	£3.19	£1.20
79	1	2	£4.32	£1.40
3	2	4	£6.99	£1.60
20	3	6	£8.10	£1.85
21	4	8	£9.67	£1.90
51	5	10	£11.95	£2.00
117	6	12	£13.52	£2.26
88	8	16	£18.10	£2.24
89	10	20	£20.88	£2.24
90	12	24	£23.20	£2.40
91	15	30	£26.60	£3.00
92	20	40	£35.64	£4.83

50 VOLT RANGE (Split Sec) Pri 120/240V (2x25V tapped secs) Voltages available 5, 7, 8, 10, 13, 15, 17, 20, 33, 40 or 20V-0-20V or 25-0-25V

Ref	50V	25V	Price	P&P
102	0.5	1	£4.13	£1.40
103	1	2	£5.03	£1.40
104	2	4	£8.69	£1.84
105	3	6	£10.36	£1.90
106	4	8	£14.10	£2.12
107	6	12	£18.01	£2.34
118	8	16	£24.52	£2.70
119	10	20	£30.23	O.A.
109	12	24	£36.18	O.A.

MAINS ISOLATORS

Pri 0-120; 0-100-120V (120, 220, 240V) Sec 0-CT-120V twice.

Ref	VA	Price	P&P
*07	20	£5.30	£1.50
149	60	£8.63	£1.60
150	100	£10.06	£1.84
151	200	£13.69	£2.12
152	250	£16.31	£2.64
154	500	£25.02	£2.90
155	750	£35.91	O.A.
156	1000	£45.89	O.A.
157	1500	£60.02	O.A.
158	2000	£72.43	O.A.
159	3000	£101.12	O.A.
160	6000	£207.92	O.A.

*Pri 0-240V Sec 115 or 240V only. State sec volts required.

CASED AUTO TRANSFORMERS

240V cable in 115V USA flat pin outlets.

VA	Price	P&P	Ref
20	£7.21	£1.25	56W
75	£9.35	£1.50	64W
150	£12.10	£1.84	4W
250	£14.73	£1.60	69W
500	£22.14	£2.24	67W
1000	£33.74	£2.80	84W
2000	£60.47	O.A.	95W

AUTO TRANSFORMERS

Volts out: 105, 115, 190, 200, 210, 220, 230, 240, for step up or step down.

Ref	VA	Price	P&P
113*	15	£2.39	£1.20
64	80	£4.85	£1.40
4	150	£6.48	£1.60
67	500	£13.30	£2.24
84	1000	£22.70	£2.80
493	1500	£28.17	O.A.
95	2000	£42.14	O.A.
73	3000	£71.64	O.A.
480	4000	£93.01	O.A.
57	5000	£108.30	O.A.

*0, 115, 220, 240.

96/48/36V RANGE

Pri 0-120/240V

Sec 2 windings 0-36-48V to give 36-0-36V or 48-0-48V or 96V.

Amps	Ref	Price	P&P
72v/96v	36v/48v		
1	2	431	£8.93
2	4	432	£14.69
3	6	433	£17.79
4	8	434	£22.24
5	10	435	£32.23
6	12	436	£40.36
8	16	437	£44.03

AVO METERS + VAT 15%

AVO 8 MK5. Latest Model.....£122.10	AVO 71 LCD.....£49.30	AVO 73 LCD: PORTABLES.....£68.90	AVO MMS Minor.....£43.60	DAI 17 Auto Range LCD.....£157.00	AVO DA116 LC9D Digital.....£131.50	AVO DA211 LCD Digital.....£58.50	AVO DA212 LCD Digital.....£81.90	Battery MEGGER BM7/500V.....£71.60	WEE MEGGER hand crank.....£101.50
-------------------------------------	-----------------------	----------------------------------	--------------------------	-----------------------------------	------------------------------------	----------------------------------	----------------------------------	------------------------------------	-----------------------------------

METAL OXIDE RESISTORS (1 per 100 (Electrosil) TR4 5% + VAT.

47Ω/75Ω/180Ω/360Ω/390Ω/430Ω/470Ω/510Ω/560Ω/820Ω/1K/1K1/1K2/1K3/1K6/1K8/2K/2K4/3K/16K/20K/22K/24K/47K/82K/100K/110K/120K/130K/180K/220K/270K/300K.	P&P 50p + VAT.
---	----------------

Telephones: Desk Type. Model 746 £11.50 + £1.20 P&P. Wall phones £18.20 + P&P. + VAT. Push button Trim phone £28.00 + P&P. + VAT.

Barrie Electronics Ltd.

3, THE MINORIES, LONDON EC3N 1BJ

TELEPHONE: 01-488 3316/7/8

NEAREST TUBE STATIONS: ALDgate & LIVERPOOL ST.

UK Postages. Overseas extra.

Voltages stated are on full load

Continuous Ratings

60V RANGE (2x25V tapped secs)

Pri 120/240V. Voltages available 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 or 24V-0-24V or 30V-0-30V.

Ref	60V	30V	Price	P&P
124	0.5	1	£4.70	£1.50
126	1	2	£7.15	£1.50
127	2	4	£9.20	£1.90
125	3	6	£13.31	£2.02
123	4	8	£15.15	£2.26
40	5	10	£19.16	£2.24
120	6	12	£21.86	£2.64
121	8	16	£30.72	O.A.
122	10	20	£35.76	O.A.
189	12	24	£41.22	O.A.

12 OR 24V OR 12-0-12V Pri 220-240

Ref	12V	24V	Price	P&P
242	300	15	£2.19	£0.70
213	1.0	0.5	£3.19	£1.20
71	2	1	£4.25	£1.20
18	4	2	£4.91	£1.60
85	5	2.5	£6.78	£1.50
70	6	3	£7.69	£1.40
108	8	4	£8.98	£1.64
72	10	5	£9.82	£1.80
116	16	8	£10.89	£1.90
115	20	10	£17.46	£2.44
187	30	15	£21.69	£2.64
226	60	30	£44.45	O.A.

SCREENED MINIATURES

Ref	mA	Volts	£	P&P
238	200	3-0-3	£1.10	0.90
212	1A, 1A	0-6, 0-6	£3.45	1.20
13	100	9-0-9	£2.59	0.80
235	330, 330	0-9, 0-9	£2.41	0.60
207	500, 500	0-8-9, 0-8-9	£3.36	1.20
208	1A, 1A	0-8-9, 0-8-9	£4.27	1.40
236	200, 200	0-15, 0-15	£2.41	0.90
214	300, 300	0-20, 0-20	£3.39	1.20
221	700(DC)	20-12-0-12-20	£4.13	1.20
206	1A, 1A	0-15-20 (x2)	£5.60	1.60
203	500, 500	0-15-27 (x2)	£4.83	1.50
204	1A, 1A	0-15-27 (x2)	£7.30	1.60
239	50	12-0-12	£3.11	0.90
234	500	6-0-6	£2.41	0.90

Constant Voltage Transformers

Clean mains to computers/peripherals

250 VA £137.36 + £6.50 VAT; 500 VA

£159.43 + £8.50 VAT; 1kVA £239.12

£11.00

250VA 500VA 1kVA. Tap-changing

types cased 400VA for mains fluctuations

INVERTERS

100VA cased (150VA tool rating) 12V

DC to 240V A.C. outlet socket. For

emergency lights, central heating boiler

pumps etc. £45. P&P + VAT 15%.

15V CT Range (7.5V-0-7.5V)

Ref Price P&P

171 500mA £2.53 £0.90

172 1A £3.59 £1.20

173 2A £4.35 £1.20

174 3A £4.54 £1.20

175 4A* £6.93 £1.40

TOROIDAL'S now stocked 30 to 530VA

PANEL METERS

43mm x 43mm 82mm x 78mm

0.50µA £6.70 0.50µA £7.37

0.500µA £6.70 0.500µA £7.37

0.1mA £6.70 0.1mA £7.37

0.30V £6.70 0.30V £7.37

Antex Irons 15/25W £4.50 12V £5.30

P&P .40 + VAT.

25W iron to B.S. spec 240V £1.95 +

.30 + VAT. De-solder pump, small

£5.17, large £5.86 + .40 + VAT.

400/440 to 240V

ISOLATORS

+ P&P + VAT

VA Price

60 £8.11

250 £16.07

350 £19.88

500 £24.77

1000 £50.53

2000 £74.79

3000 £104.86

6000 £207.92

BRIDGES

+ P&P + VAT

100V 25A £1.80

100V 35A £2.00

100V 2A £0.52

200V 4A £0.75

400V 1A £0.25

400V 4A £0.98

400V 6A £1.44

+ P&P 20p + VAT 15%

FREE!

WITH THIS
MAGAZINE

Our catalogue of **CASIO** products
The world's most versatile watch?



Over 30 of
the very latest
Casio watches



Portable
Computers

The future has arrived

Casiotone – the world's fastest selling keyboards?

Calculators – Electronic games –
Musical instruments

SPECIAL MONEY SAVING OFFER

Further copies available on request from:

TEMPUS

38 BURLEIGH STREET
CAMBRIDGE CB1 1DG
Telephone (0223) 312866

ZX SPEED AND CONTROL

DCP SPEECH PACK

£49.95 inc.

- Clips onto back of computer – Just plug it in and have a chat!
- Easy to use: one line POKE or OUT commands.
- Includes Word Pack 1 which has A-Z, 0 to million+ words (expandable).
- Complete with built in speaker and uses computer power supply.
- Neatly cased to match ZX Styling and profile.
- Uses no computer RAM-speech contained in internal ROM.
- You can add your RAM Pack, Printer, DCP Pack, etc onto back.
- SPECTRUM or ZX81 versions available – please state which.

As seen on
BBCTV

DCP INTERSPEC PACK

£39.95 inc.

- 8 BIT, 8 Channel Analogue to Digital Converter for joysticks, sensors, etc.
- 8 BIT Input Port and 8 BIT Output Port for Logic and Interfacing.
- 4 channel high current relay switches (1A @ 12v) for control.
- 4 Buffered Switch Inputs for control.
- "DCP BUS" Connector for easy system expansion.
- Comprehensive manual containing software and hardware examples.
- All these facilities in one compact cased unit at such a low price!
- Specially designed for the ZX Spectrum.

NEW!

All prices include VAT and Postage & Packing and units are fully assembled and guaranteed. Delivery normally by return or will be advised immediately.

DCP MICRODEVELOPMENTS LTD.
2 STATION CLOSE, LINGWOOD,
NORWICH NR13 4AX

DCP
microdevelopments

You should see Ambit's new Autumn Catalogue...

IT SPEAKS FOR ITSELF

Another milestone in component supply...

If you've been wondering just what's been going on at Ambit lately, we are now taking the wraps off the most advanced and imaginative concept in component, tool, and information distribution since we launched WR&E last year.

We have included new items and information to plug a few gaps, and we are just starting to implement a new interactive computerised system of service and information that simply cannot be overlooked by anyone interested in the communications, electronics, video and computing business.

- ★ Price on the page
- ★ 24 Hour response
- Guaranteed
- ★ Low prices
- ★ High quality
- ★ Export a speciality

No. 4. Autumn 1982

AMBIT INTERNATIONAL'S

WORLD of RADIO & ELECTRONICS

CONCISE PARTS CATALOGUE

128 PAGES

70 p

Some of the new items from this issue...

Weller/Cooper: Soldering Irons & Tools

You never expect buying the best

- ★ TCP series
- ★ Tips & spares
- ★ Cutters/pliers
- ★ Toolkits

Motorola RF Power: Transistors for transmitting

- ★ 1W/50MHz to
- ★ 80W/150MHz
- ★ ...& beyond

Test equipment

A rapidly expanding range

- ★ Auto DMMs
- ★ Scopes
- ★ Bananas (?)
- ★ Sig gens

TOKO inductors

RM assemblies

Intelligent LCDs

Uni Crystal Filters

Coaxial relays

Micros & memories

Linears

Keyswitches

Panelware

Hardware

WR&E

LOWEST PRICE FULL CEE MCADS 3 x £1 vouchers inside

128 Pages of the broadest component range in the business

24 HOURS A DAY, 7 DAYS A WEEK

AUTUMN '82 WR&E 70p

AT YOUR NEWSAGENT - OR DIRECT FROM

AMBIT INTERNATIONAL BRENTWOOD ESSEX CM14 4SG

Telephone (0277)230909, telex 995194 AMBITG, data RS232/300 baud (0277)230959*

*Dial (0277)230959, hook in your low cost modem and terminal (most personal computers can be configured to access REWTEL, details are being published in R&EW over the next few months) and REWTEL will give you access to up to 5000 pages of background to the WR&E catalogue, equivalents, news, updates, hot off-the-press product news, information, jobs being advertised in the industry. It's computing at its most versatile and worthwhile: why be satisfied with a 64K MCU, when you can gain free access to the 70MByte+ of the REWTEL computer ??

METERS

Large range of types in stock; also probes, leads, accessories etc

PANEL MOUNTING in 50, 100, 500µA, 1, 5, 10, 50, 100, 500mA, 1A either model

T Range 60 x 45mm £5.95

MU Range 50 x 45mm £2.68

MULTIMETERS N565A

YN 360TR

OMM D0601

New - 20KΩ/V AC/DC/R in 23 ranges 130 x 85 x 37mm £11.20N

20KΩ/V AC/DC/R in 21 ranges 145 x 95 x 45mm £16.45N

LCD 3½ digit (1999) Push button 26 ranges 170 x 80 x 38mm £32.00N

SOLDERING IRONS

Also large stocks of bits, desoldering devices, accessories etc

ANTEX C 240V £4.60N; K25-240V £5.30N; CSBP £5.45N; XSBP £5.55N; S14 Stand £1.70N

DRYX 50 watt temp. controlled £13.75N; Stand £4.00N

SOLDOER 500gm/18 SWG £7.80; Desolder braid 1.5m 54p

SWITCHES - Wavechange

Type CK - 1P/12 watt, 2P/6 W, 3P/4 W, 4P/3 W 48p; Min. Toggle - S7101, SPOT 57p; S7201 DPOT 87p; S7301 3POT £1.64; S7401 4POT £2.75; S7211 1P3W £1.40; Centre off S7103 SPOT 71p; S7203 DPOT 96p; Push Button min R531 make/R533 break 82p; R225 DPOT £1.34

DUAL IN LINE ERG colour coded 0.3" x 0.1" format, On/OH single throw 2P 54p; 4P SDA 95p; 6P SDB 138p; 8P SDB £1.87; 10P SDB £2.10

Low cost D-I-L 4P DSDA 85p; 8P DSDB £1.00

KEYBOARD

For use with ZX81 £31.30N

NICAD CHARGERS

For PP3-NC75 £4.95N; For AAC or D-NC1230 £8.20N

BOXES

High quality Black ABS plastic or diecast plain or stove grey

L	W	D	ABS	PLAIN	STOVE GREY
50	50	25	2002	98p	5002P 117p
100	60	25	2002	98p	5002P 117p
113	63	31	2002	105p	5003P 143p
121	66	40	2004	115p	5004P 182p
152	82	50	2005	134p	5005P 218p
192	113	61	2006	235p	5006P 314p

VERO RANGE Plastic Boxes

L	W	D	Price
72	47	25	21024 50p
120	50	35	21030 78p
180	110	55	21391 145p

'G' RANGE Professional Instrument Cases

L	W	D	Price
134	90	44	21089 £7.28N
224	140	64	21090 £11.02N
302	170	84	21091 £14.96N

ELECTROVALUE

FOR SERVICE YOU CAN TRUST

VEROBOX CASES

ABS, light grey top, dark grey bottom + 2 alt. panels

L	D	H	TYPE	PRICE
205	140	40	21034	£4.52
205	140	75	21035	£5.02
205	140	110	21036	£5.54
180	120	30	21037	£4.11
180	120	65	21038	£4.40
180	120	90	21039	£4.69
155	85	39	21040	£3.31
155	85	60	21041	£3.81
155	85	80	21042	£4.30
125	65	30	21047	£2.35
125	65	39	21048	£2.99
125	65	50	21049	£3.37

SIEMENS S566B Touch Dimmer I.C. £2.14

Order 30p or FREE ordered with I.C.

CAPACITORS

POLYSTYRENE SIEMENS

5% Tolerance 180V

5, 7, 10, 12, 15, 18, 22, 27, 33, 39pF 15p; 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820pF, 1n, 1n2, 1n5, 1n8, 2n2, 2n7, 3n3, 3n9, 4n7 10p; 5n6, 6n8, 8n2, 10n 13p

CERAMIC Very small 1.8, 2.2, 2.7 etc. up to 1n 5p each; 1n5, 2n2, 3n3, 4n7 6n8 5p; 10n, 22n, 6p, 33n, 47n 7p; 100n 8p

POLYESTER SIEMENS LAYER TYPE 7.5mm lead spacing 100V

1n, 1n5, 2n2, 3n3 6p; 4n7, 6n8, 8n2, 10n, 12n, 15n, 18n, 22n, 27n, 33n, 39n, 47n 7p; 56n, 68n 7p; 82n, 100n 9p; 120n, 150n 11p; 180n, 220n 12p; 270n, 330n, 390n, 470n 15p; 560n, 680n 24p; 10mm spacing 1µF 25p; 15mm spacing 2µF 35p; 22.5mm spacing 1µF 40V 54p; 3.3µF 100V 69p; 1n depth stocks

ELECTROLYTICS

NON-polar (for LS X-overs) 50V peak 2µF 28p, 4µF 28p; 6, 8, 10, 16µF 32p; 25µF 37p; 40, 60µF 59p; 100µF 69p

POLARISED SIEMENS or MULLARD FOR QUALITY (µF/V) 1/63, 2/2/63, 4/7/63, 5/8/40, 10/25, 22/10, 10p; 10/40, 22/25, 47/10, 11p; 47/25, 12p; 100/10, 13p; 100/25, 100/40, 15p; 220/10, 220/16, 16p; 220/25, 18p; 220/40, 20p; 470/10, 470/16, 470/25, 1000/10, 1000/16, 1000/16, 27p; 1000/25, 36p; 1000/40, 2200/16, 44p; 1000/63, 78p; 2200/40, 4700/16, 73p

Pluggable SIEMENS single ended

1/63, 2/2/63, 4/7/63, 10p; 10/63, 22/63, 8p; 22/40, 47/16, 10p; 47/40, 10p; 47/63, 10p; 100/16, 100/25, 10p; 100/40, 10p; 100/63, 20p; 220/10, 220/16, 220/25, 13p; 470/3, 15p; 470/10, 15p; 470/16, 15p; 470/25, 16p; 470/40, 26p; 1000/10, 23p; 1000/16, 24p; 1000/25, 40p

Large Caps - SIEMENS

2200/63 £1.77; 4700/40 £1.78; 4700/63 £2.98; 4700/100 £5.54; 10000/16 £1.93; 10000/25 £2.78; 22000/16 £3.20; 22000/25 £4.73

TANTALUM

0.1/35, 0.22/35, 0.47/35, 1/35, 2/2/16, 10p; 13p; 2/2/35, 4/7/16, 10/63, 16p; 4/7/35, 10/16, 22/63, 10/25, 16p; 22/16, 22/25, 33/10, 47/63, 100/3, 30p

LOW LEAKAGE All single ended

0.1/50, 0.22/50, 0.47/50, 4/7/35, 11p; 1/50, 2/2/50, 4/7/50, 10p; 10/16, 22/16, 11p; 10/35, 22/10, 22/16, 22/35, 4/7/6, 47/10, 12p; 47/16, 100/16, 12p

● NORMAL DESPATCHES WITHIN 24 HOURS

SIEMENS

LEO Bar Driver UAA 180 £1.65

RESISTORS

1, 1/2, 2 watt - all 2p each, 10 of one value 15p

2% Mullard metal film 5.1 ohms - 300K 5p each, 10 of one value 40p

5% wire wound 3W or 7W, most £12 values 1.2 ohms to 8K2 3p ea, 10 for 70pN

POTENTIOMETERS

Carbon rotary (P20) 100 ohms-4M7 lin, 220 ohms-2M2 log, 32p, w. switch 87p

Dual gang (JP20) 4K7 1M2 lin or log 95p, w. switch £1.50

SLIDERS

58mm, low cost 10K-1M log only 29p; Std 58mm mono 4K7-1M lin or log 74p; stereo matched £1.25; Graduated bezels 3p

PRESET

Min 10mm dia Horiz. or vert. 100 ohms-1M 13p

Preset Cermet rectilinear type 89P, 100Ω-1M, 10p

Preset Cermet 10mm dia Horiz. or vert. 100Ω-1M 29p

Plessey MPWT moulded carbon 47 ohms-2M2 5p

All orders brand new & guaranteed to spec.

CMOS SUPER SAVERS!

(Prices Net, and shown in pence)

4000	10	4015	40	4027	20	4069	14
4001	10	4016	20	4028	39	4070	14
4002	12	4017	35	4029	45	4071	14
4006	50	4018	45	4030	16	4072	14
4007	14	4019	25	4041	14	4081	14
4008	40	4020	42	4042	40	4082	14
4009	24	4021	40	4043	40	4083	20
4010	24	4022	35	4044	40	4510	48
4011	12	4023	14	4046	46	4511	48
4012	15	4024	32	4049	23	4516	53
4013	20	4025	14	4050	23	4518	40
4014	46	4026	80	4060	45	4520	80

BARCLAYCARD

Credit card orders can be accepted via mail order or telephone

Giro A/c no 38/671/4002

V.A.T.

additional at 15% on total value of all U.K. orders

FREE POSTAGE

and packing on U.K. C.W.D. orders value £5.75 (inc. VAT) and upwards. Under £5.75 please add 40p (inc. VAT)

DISCOUNTS

on C.W.D. orders over £23.00 - 5%

on C.W.D. orders over £57.50 - 10%

Discounts do not apply to 'Net' items (shown by N after the price) or to orders paid by credit card

Please mention this Journal when ordering or writing, etc.

MAIL ORDERS TO HEAD OFFICE & SHOP -

ELECTROVALUE LTD.

28c St Jude's Rd, Englefield Green, Egham, Surrey TW20 0HB

Telephone Egham (STD 0784, London 87) 33603; Telex: 264475

Northern Branch (Personal shoppers only) 680 Burnage Lane, Burnage, Manchester M19 1NA. Telephone 061 432 4945.

Computing Shop: 700 Burnage Lane, Manchester. Tel: 061 431 4866

Shop hours (all addresses) Mon-Fri 9am-5.30pm; Sat 9am-1.0pm

POWER DIMMER MODULES

CONTACT OUR SALES AND SAVE A FURTHER 20% NOW!

A range of electronic modular dimmers designed to suit your custom channel and facility requirement

- Considerable saving over commercial equipment
- All the commercial facilities and more
- Compatible special effects
- Preset/remote/master
- Easily installed and wired

SPC - Simple but effective 1000W controller £15.70

SPU - Used in conjunction with RS units for Remote desks in 1000 and 2000W versions £23.90 (2K)

MC - Master dimmer for SPC/RS units £7.90

RS - Remote controller for SPU/SPC Units £9.40

SUP/REF - Supply/signals for up to 50 modules £20.00

Discounts on above only (order £100 to £199 15% £200 to £299 20% £300 25%)

EFFECTS ACCESSORIES

MXSL - Four channel sound to light £36.90

MXLS - Four Channel Sequencer £23.70


MXLC-S Four channel sound chaser £26.70

PSU - Supply for MX £7.20

3 CHANNEL SOUND/LIGHT CHASER

£35.70

LB31000SLC

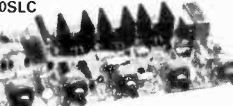

A high performance sound to light providing bass, mid and treble separation, employing active filters. Automatic switching to chase in the absence of a music signal 1000W/chan.

3 CHANNEL SOUND/LIGHT

£22.70

LB31000SL



All the advantages of the SLC without chase. Controls: bass/mid/treble/master sensitivity.

STEREO DISCO MIXER/PREAMP

Main supply £7.20
PFL supply £1.00

LBPA3 M - Magnetic C - Ceramic

£36.70

Magnetic or ceramic deck versions - please state

All the requirements of a stereo disco preamp on one board, left and right deck mixers/tone controls/misc. mixer/tones/mic. auto fade over decks/and P.F.L. The unit can be used with virtually any power amp.

AND MORE!

- * 4 CHAN S/L AUTO CHASER
- * 4 CHAN MULTI SOUND CHASER
- * 4 CHAN SEQUENCER
- * 4 CHAN SOUND CHASER
- * FASCIA PANELS

Don't forget our 3-way active cross-overs (300Hz-3KHz points) still £17.90 (supply £7.20).

Don't hesitate to write or phone for immediate information All prices include VAT. Please include 75p post except power dimmer (£1.75). Cheques/PO/C.O.D./Access all welcome. Goods by return (stocks allowing).

Tel: 01-640 6053 (Mon to Fri) 10 to 5)

L&B ELECTRONIC, 34 OAKWOOD PLACE, MITCHAM, SURREY CR2 1AQ.

ENFIELD ELECTRONICS

BARGAINS OF THE MONTH FOR ALL P.E. READERS!



For up to the minute prices please ring 01-366 1873. Please add 15% VAT @ 21.00 p & p per item ordered.

A superb stereo headphone

Specifications:

- 1) Sensitivity 1100B at 1.000Hz with 1mw
- 2) Frequency response: 20-19,000Hz
- 3) UNIT impedance 8 ohms
- 4) Matching impedance 16 ohms
- 5) Maximum input 0.5 watts per channel
- 6) Individual slide volume control (stereo/mono switch)
- 7) 10 foot coiled cord with stereo phone plug
- 8) Leatherette soft ear pads and head cushion

Price £5.95 - VAT - £1 p&p
Order No. LE 76VS



Universal NICAD battery charger. All plastic case with lift up lid. Charge/Test switch. LED indicators at each of the five charging points.

Charges: PP3 (9V), U12 (1.5V penlite), U11 (1.5V C), U2 (1.5V D), Power: 220-240V AC. Dims: 210 x 100 x 30mm. Super Special Offer at only £6.00 - VAT - £1 p&p
Order No. MW338

PLEASE ALLOW 10 DAYS FOR DELIVERY. OPEN 9am-6pm MONDAY TO SATURDAY.

208 Baker Street, Enfield, Middlesex. 01-366 1873.

TIME WRONG?

MSF CLOCK is ALWAYS CORRECT - never gains or loses, SELF SETTING at switch-on, 8 digits show Date, Hours, Minutes and Seconds, auto GMT/BST and leap year, also parallel BCD output, receives Rugby 60KHz atomic time signals, built-in antenna, 1000Km range, TIME RIGHT, £69.60.

60KHz RUGBY RECEIVER, as in MSF Clock, serial data output for computer etc, decoding details and ZX81 listings for LOCAL, GMT and SIDERAL time, £22.20.

SIGNAL GENERATOR, 10Hz-200KHz, sine, square, £19.70.

V.L.F.7 EXPLORE 10-150KHz, Receiver £19.40

PROGRAMMABLE CHIME, makes up your own tunes, £46.40.

Each fun-to-build kit includes all parts, printed circuit, case, postage etc, instructions, money back assurance so GET yours NOW.

CAMBRIDGE KITS

45 (FM) Old School Lane, Milton, Cambridge.

SINCLAIR COMPUTERS

We are the leading world-wide Sinclair export specialist including Norway, Sweden, Finland and Denmark. Write for our surprisingly low prices.

PRINTERS

Buy any of the below and get a free interface kit and word processor program for UK101 or Superboard. Seikosha GP100A £199. OKI Microline 83A £446. OKI Microline 84A £799. OKI Microline 80 £235. OKI Microline 82A £333. Epson MX70T £259. Epson MX80T/3 £319. Epson MX80F/T3 £349. Epson MX100/3 £429.



VIC 20 COMPUTER

Two special offers—If it is bought with the Vic20 we can supply the cassette recorder for £30.43. Alternatively, we will supply a free kit with each Vic20 to allow the use of an ordinary cassette recorder. Vic20 £130. Ordinary cassette conversion kit £6. Vic20 cassette recorder £36.50. High resolution cartridge £27.95. Machine code monitor £27.95. Vic printer £175.

Ram cartridges—3K £24, 8K £35, 16K £57. Game cartridges—Sargon II £19, all others £15 each. Joystick £6.32. Intro to Basic Part I £13. New lost cost memory board, no need for a mother-board, comes with 3K ram on board + socket for a rom + sockets for another 24K of low current Nmos ram (just plug in chips to expand memory) £49. 27K version £109. Extra memory chips £6 per 2K.




UK101 AND SUPERBOARD

32 x 48 display expansion kits UK101 £9, Series I Superboard £14. Guard band kit for Superboard only £10. The below accessories suit both the UK101 and Superboard—Extra ram £2.10 per K. 32K memory expansion board £60. Cegmon £22.50. Wemon £14.95. Word processor program £10. Centronics interface kit £10. 610 expansion board £179. Cased minifloppy disc drives with DOS single £275, dual £415. Stand alone floppy disc controller £85.

GENIE COMPUTERS

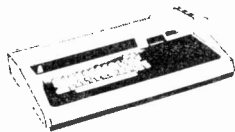New colour Genie 16K and accessories—phone for prices. Genie I 16K £279, 48K £330. EG3014 expander box 16K £179, 32K £189. Minifloppy disc drives single £199, dual £369. Double density convertor £72. Parallel printer interface £36. High resolution graphics unit £82. 12" monitor £40.



5V POWER KITS

Fully stabilised 5V computer and TTL power kits. Short circuit and over-voltage protection 1.5A £7.83, 3A £12.17, 6A £20.87.

SHARP COMPUTERS

We can supply any Epson MX80 printer to run direct from the MZ80K (i/o box not needed) for £39 plus printer price. We also specialize in interfacing printers to the MZ80K, MZ80A and MZ80B both with and without the i/o box.

TV GAMES*

AY-3-8550 + kit £9.26.

BI-PAK AUDIO MODULES*

PS12 £1.75. TS38 £2.90. AL60 £5.62. BMT80 £6.36. Stereo 30 £15. AL80 £8.56.

SWANLEY ELECTRONICS,

Dept PE, 32 Golds Rd.,
Swanley, Kent BR8 8EZ.
Tel. Swanley (0322) 64851.
Please allow 7 days for delivery.

Postage £3.50 on computers, £4.50 on printers and 50p on other orders. Please add VAT to all prices except those sections marked with a * Overseas and official credit orders welcome.

Technical Training in Radio, Television and Electronics

ICS have helped thousands of ambitious people to move up into higher paid, more secure jobs in the field of electronics—now it can be your turn. Whether you are a newcomer to the field or already working in the industry, ICS can provide you with the specialised training so essential to success.

Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed".

CITY AND GUILDS CERTIFICATES

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

Basic Electronic Engineering (C&G/ICS)
Radio Amateurs

CERTIFICATE COURSES

TV & Audio Servicing
TV, Radio and Audio Engineering
Radio & Amplifier Construction
Electronic Engineering*
Computer Electronics*
Industrial Electronics*
Radio Frequency Electronics*
Introduction to Microprocessing*
Electrical Contracting & Installation

*Quality for IET Associate Membership



Approved by CACC



Div. National Corporation
Education



Member of ABCC

POST OR PHONE TODAY FOR FREE BOOKLET

Please send me your FREE School of Electronics Prospectus

Subject of Interest _____

Name _____

Address _____

Post to: Dept B273
ICS School of Electronics
160 Stewarts Road
London SW8 4UJ



01 622 9911
(All Hours)

Technicians in Communications

GCHQ We are the Government Communications Headquarters, based at Cheltenham. Our interest is R & D in all types of modern radio communications—HF to satellite—and their security.

THE JOB All aspects of technician support to an unparalleled range of communications equipment, much of it at the forefront of current technology.

LOCATION Sites at Cheltenham in the very attractive Cotswolds and elsewhere in the UK; opportunities for service abroad.

PAY Competitive rates, reviewed regularly. Relevant experience may count towards increased starting pay. Promotion prospects.

TRAINING We encourage you to acquire new skills and experience.

QUALIFICATIONS You should have a TEC Certificate in Telecommunications, or acceptable equivalent, plus at least 2 years experience.

TRAINEE RADIO TECHNICIANS Persons suitably qualified and under 22 but with no practical experience may apply for our training scheme.

HOW TO APPLY For full details on this and information on our special scheme for those lacking practical experience, write now to

Recruitment Office
GCHQ, Oakley, Priors Road, Cheltenham
Glos. GL52 5AJ
or ring
0242 21491
ext 2269
(1530)





SELLING OR BUYING

A classified advertisement could solve your problem at very little cost.

RING LINDA
01-261 5846

RECEIVERS AND COMPONENTS

MIXED METAL FILM RESISTORS 100:80p, 1000:£5. Cermet potentiometers 10 mixed £1. Low profile sockets 24 pin 15p. P&P 40p. S.A.E. for lists T. Milner, 203 Goodman Park, Slough, Berkshire.

BOURNEMOUTH/BOSCOMBE. Electronic components specialists for 33 years. Foresters (National Radio Supplies), Late Holdenhurst Road. Now at 36, Ashley Road, Boscombe. Tel. 302204. Closed Weds.

BIG BARGAIN BOX

Our Big Bargain Box contains over a thousand components - resistors, capacitors, pots, switches, diodes, transistors, panels, bits and pieces, odds and ends. All useful stuff - would cost many times the price we are asking if bought separately. Approx. weight 4lbs. **ONLY £5.00** inc. post - you're bound to come back for another!!!

ESP, 174c FOUNDRY LANE, SOUTHAMPTON, SO1 3LS

Lots of surplus bargains on our latest list - send an SAE for your copy now.

ELECTRONICS COMPONENTS SHOP in Maidstone, Kent. Thyronics Control Systems, 8, Sandling Road, Maidstone. Maidstone 675354.

TURN YOUR SURPLUS capacitors, transistors, etc. into cash. Contact **COLES HARDING & CO.** 103 SOUTH BRINK, WISBECH, CAMBS. TEL: 0945 584188. Immediate settlement.

2m TRANSMITTER £20.00. Audio Compressor £9.00. Portable VLF receiver £12.00. Window Breaker £10.50. Pyramid Game £15.00 and many others. Complete kits. Only tools required are soldering iron and a screwdriver. Full money back assurance. Send SAE for details to: N. J. Edwards, 17 Palace Street, Norwich.

TELETRIC

THE ELECTRICITY COST MONITOR
FEATURED IN PE MARCH & APRIL '82
AS SEEN ON NATIONAL TELEVISION

Teletric Assembly Kit £59.50 + VAT
Teletric Unit Built & Tested £98.00 + VAT

P&P per kit or unit £3.00 + VAT

SAE for full details, Component List & Order Form

Cheque or Purchase Order to:

Response Company

Froxfield, Petersfield, Hants GU32 1DX.

ACCESS Tel: Petersfield (0730) 3063

SMALL ADS

The prepaid rate for classified advertisements is 34 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £11.20 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Electronics and crossed "Lloyds Banks Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Dept., Practical Electronics, Room 2612, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

BRAND NEW COMPONENTS BY RETURN

Electrolytic Capacitors 16V, 25V, 50V.
0.47, 1.0, 2.2, 4.7 & 10 Mfds. — 5p.
22 & 47—6p 100—7p. (50V—8p). 220—8p.
(50V—10p). 470—11p. (40V—16p). 1000/15V—15p.
1000/25V—25p. 1000/40V—35p.

Subminiature bead Tantalum electrolytics.
0.1, 0.22, 0.47, 1.0, 35V, 4.7 & 6.3V — 14p
2.2/35V, 4.7/25V—15p. 10/25V, 15/16V—20p.
22/16V, 33/10V, 47/6V, 68/3V & 100/3V—30p
15/25V, 22/25V, 47/10V—35p. 47/16V—80p.

Subminiature Ceramic Caps. E12 Series 100V.

2% 10 pf. to 47 pf.—3p. 56 pf. to 330 pf.—4p.

10% 390 pf. to 4700 pf.—4p.

Vertical Mounting Ceramic Plate Caps. 50V

E12 22 pf. to 1000 pf. £8 1500 pf. to 47000 pf.—2p

Polystyrene E12 Series 63V. Horizontal Mntg.

10 pf. to 820 pf.—3p. 1000 pf. to 10,000 pf.—4p.

Miniature Polyester 250V Vert. Mtg. E6 Series.

0.1, 0.068—4p. 1—5p. 15, 22—6p. 33, 47—10p.

68—12p. 100—15p. 150—22p. 220—24p.

Mylar (Polyester) Film 100V. Vertical Mounting.

.001, .0022, .0047—3p. .01, .022—4p. .04, .05, 0.1—5p.

High Stability Miniature Film Resistors 5%

1/4W E24 Series 0.51R—10MΩ. (Except 7M5)—1p.

1/4W E12 Series 1R to 10MΩ.—1p.

1/4W metal film E12 Series 10R—1MΩ. 5%—2p. 1%—3p.

1N4148—7p. 1N4002—4p. 1N4006—8p. 1N4007—7p.

BC107/8/9—12p. BC147/8/9 BC157/8/9 BF195—7p.

8 Pin i.c.s. 741 Op. amp.—18p. 555 Timer—24p.

Dil. Holders 8 pin—9p. 14 pin—12p. 16 pin—14p.

LED's. 3 & 5mm. Red—10p. Green & Yellow—14p.

Grommets for 3mm.—1p. Grommets for 5mm.—2p.

20mm. Q.B. Fuses .15, .25, 5, 1, 2, 3 & 5A—5p.

20mm. Anti Surge 100mA to 5.0A—8p.

20mm. Fuseholders P.C. or Chassis Mtg—8p.

Battery Snaps (pairs) PP3—8p. PP9—12p.

400mW Zener diodes E24 series 2V7 to 33V—8p.

Prices VAT inclusive Post 15p. (Free over £5.00).

THE C. R. SUPPLY CO.

127, Chesterfield Rd., Sheffield S80RN.

SILLY SEMICONDUCTOR SALE

ITT BC183 transistors. 4p each. 10 for 30p.

ITT IN4002 diodes. 3p each. 10 for 25p.

OPTRON Type OP160 infra red diode. High peer out-

put. Spectrally and mechanically matched to the

OP500 and OP500SL series photo transistors. Price

40p each. 3 for £1.

Data sheet if required 10p extra.

AIRLITE HEADSETS with Boom Mike. Must have cost

a fortune. Our price £4.50 per pair. p.p. £1. 2 pairs for

£9 post free. Less Boom Mike £4 per pair. p.p. £1. 2

pairs £3 post free. **AMPLIVOX HEADSETS** with

Boom Mike £4.50 per pair. Postage £1. 2 pairs £9

post free. Less Boom Mike £4 per pair. 2 pairs £8

post free. All headphones fitted with ex-Ministry

plug. Standard jack plugs available 25p each. 2 for

40p. Headphone extension sockets available at 25p

each. 2 for 40p. Impedance of first 2 Headphones

600 ohms. All headphones in good condition.

GENUINE AFV TANK HEADSETS and **MIKE £3.50**

each. p.p. £1. 2 pairs for £8 post free.

RIDICULOUS RESISTOR SALE

1 watt carbon film resistors. 5% tol. High quality resis-

tors made under exacting conditions by automatic

machines. E12 range 1R to 10MΩ. Lot A, 1000 (25

per value) £8. Lot B, 500 (25 per value) £4.25. Lot C,

100 (25 per value) 90p. Orders over £5 post free.

Otherwise postage 15p in (Phil).

BRIDGE RECTIFIERS. (Philips) 400 PIV. at 4 amp.

Well made. Should be over £2 each. Our price 90p

p.p. 20p.

HAVE YOU SEEN THE GREEN CAT? 1000s of new

components, electronic, radio, audio, at unbelievably

low prices. Send 50p and receive catalogue and FREE

RECORD SPEED INDICATOR. Try a JUMBO PACK.

Contains transistors, resistors, caps, petal switches,

radio and electronic devices. Over (£50 worth) for

£11. Carr. and packing £2.50. **MINI JUMBO PACK**

(£20 worth) for £5 p.p. £1.50.

PLEASE ADD 15% VAT to all orders including car-

riage and p.p.

MYERS ELECTRONICS

Dept P.E., 12-14 Harper Street, Leeds LS2 7EA.

Tel. Leeds 452045

New retail premises at above address (opposite

Corals). Callers welcome 9 to 5 Mon. to Sat. Sunday

10 till 3 pm.

NOTICE TO READERS

Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser to check both prices and availability of goods before ordering from non-current issues of the magazine.

T & J ELECTRONIC COMPONENTS - Quality components, competitive prices. Illustrated catalogue 45p. 98 Burrow Road, Chigwell, Essex.

300 SMALL COMPONENTS, transistors, diodes £1.70. 7lbs assorted components £4.25. 10lbs £5.75. Forty 74 series ICs on panel £1.70. 500 capacitors £3.20. List 20p refundable. Post 60p. Optional insurance 20p. JWB Radio, 2, Barnfield Crescent, Sale, Cheshire M33 1NL.

TRADE ONLY. Surplus/liquidators components etc. Silly prices. Lists: Bardwell Ltd., 288 Abbeydale Road, Sheffield S7 1FL.

BRYSTEP ELECTRONICS

10 Camphill Industrial Estate,
West Byfleet, Surrey KT14 6EW.
Tel. Byfleet (09323) 41547

CMOS			Part of our ex surplus/liquidator stock:	
4001	£0.10	4069	£0.15	
4007	£0.15	4070	£0.15	
4008	£0.47	4078	£0.18	4008 £0.21
4011	£0.11	4081	£0.14	4015 £0.28
4012	£0.16	4093	£0.28	4016 £0.12
4013	£0.22	4503	£0.39	4022 £0.25
4015	£0.50	4508	£1.44	4023 £0.10
4016	£0.19	4510	£0.48	4175 £0.50
4017	£0.38	4511	£0.45	4419 £1.50
4018	£0.45	4512	£0.50	4507 £0.18
4021	£0.40	4514	£1.19	4514 £0.60
4022	£0.48	4515	£1.20	4516 £0.38
4023	£0.16	4516	£0.59	4519 £0.15
4024	£0.32	4518	£0.35	4556 £0.24
4025	£0.16	4520	£0.59	8251 £2.00
4028	£0.48	4528	£0.64	2708 £1.25
4040	£0.48	4529	£0.70	2716 (3 Rail) £2.15
4042	£0.48	4531	£0.65	LM323K £2.00
4047	£0.58	4534	£3.98	SE9300 £0.25
4049	£0.22	4541	£0.98	5x7 Dot Matrix Displays 0.35" £2.00
4050	£0.22	4585	£0.90	
4066	£0.29			

Many, many other items held in stock.

S.A.E. for full stock and price list. Also, separate list of items which are ex: Surplus/Liquidator stock, at bargain prices. We fully guarantee your money back in FULL if any item fails, whether old or new, provided it is returned within 28 days of receipt. We have never had to return money yet.

SERVICE SHEETS

BELL'S TELEVISION SERVICES for Service Sheets on Radio, TV, etc £1.25 plus S.A.E. Colour TV Service manuals on request. S.A.E. with enquiries to B.T.S. 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 55885.

BOOKS AND PUBLICATIONS

ANY PUBLISHED, full-size service sheet by return £2 + L.s.a.e. CTV/Music Centres £3. Repair data with all circuits, layouts etc. Your named TV or video £8.50. Free 50p mag. all orders, queries. TIS (PE), 76 Churches, Larkhall, Lanarkshire.

AERIALS

AERIAL BOOSTERS trebles incoming signal, price £7.00. SAE leaflets. Velco Electronics, Ramsbottom, Lancashire BL0 9AG.

EDUCATIONAL

CAREERS IN MARINE ELECTRONICS. Courses commencing September and January. Further details, The Nautical College, Fleetwood FY7 8JZ. Tel. 03917 79123.

FOR SALE

SUPERB PHILIPS OSCILLOSCOPE, versatile, and with every facility. Only £120. Phone Colchester (0206) 866123.

ACORN ATOM Floating Point Eprom £15.00. Utility Eprom £18.00. Bargain price £30.00 pair. Davidson, 109 Highgate Lane, Farnborough, Hants.

PACK OF TWO BNC 75OHM plugs £1.20, 27vdc 4 pole (main 'Continental' type). Change over relay £1.20. Coax change over relay 9vdc £4. All prices include V.A.T. & postage. Send SAE for list. AFR Electronics, School Lane, Moulton, Northampton.

PSU's 5V5A £25.99, 1-2V 27V 1-2A with voltmeter £24.99 (with toroidal transformers). Fully fused and protected. Top brand VHS video cassettes; E120 £7.65, E180 £8.10. Prices include P&P. Edwards Electrics (J.C.) Unit 3, Mill Lane, Church Street, Bridgewater, Somerset.

FORTH FOR UK-101 ... may be modified for Superboard. Learn on 8K machine. Includes incremental compiler, documentation and sample programmes e.g. 6502 Assembler. £12. W. A. Powell, 16 Vantorts Road, Sawbridgeworth, Herts CM21 9NB.

COURSES

CONQUER THE CHIP... Master modern electronics the PRACTICAL way by SEEING and DOING in your own home. Write for your free colour brochure now to British National Radio & Electronics School, Dept. C2, Reading, Berks. RG1 1BR.

BECOME A WATCH AND CLOCK SERVICE TECHNICIAN

EARN TOP MONEY PART OR FULL TIME

- ★ Become your own Boss!
- ★ Run your business from home!
- ★ Earn up to £27.00 per hour!

Opportunities exist for practical and mechanically minded people to train to become Watch & Clock Service Technicians. No previous experience necessary. Unique 5 week Training Course, including one week residential training in one of U.K.'s busiest workshops. Send 12½p stamp for FREE information package.

**WATCH & CLOCK
TECHNICIANS TRAINING CENTRE.**
Dept. 16, Queens Parade Place, Bath, BA1 1NN.

MISCELLANEOUS

PARAPHYSICAL JOURNAL (Russian Translations): Psychotronic Generators, Kirlianography, Gravity Lasers, Telekinesis. Details: SAE 4x9", PARALAB, Downton, Wilts.

ULTRASONIC TRANSDUCERS, MINIATURE, 40KHz. £2.85 per pair + 25p P & P. Dataplus Developments, 81 Cholmeley Road, Reading, Berks.

PRACTICAL ELECTRONICS P.C.B.'s

JULY 82	Audiotest EG901	£6.44
AUG 82	Auto Photographer EP905	£1.56
	Combo amp EG908	£3.34
SEP 82	Combo amp EP931	£3.07
	Waveform digitiser EP935	£7.89
OCT 82	Mini Chorus EP950	£2.97

For full list and current pcb's send SAE. CWO Please. Postage + add 35p postage and packing to complete order. Europe 70p.

PROTO DESIGN

14 Downham Road, Ramsden Heath, Billericay, Essex CM11 1PU. Telephone 0268-710722

CLEARING LABORATORY: scopes, generators, P.S.U.'s, bridges, analysers, meters, recorders, etc. 0403 76236.

BURGLAR ALARM EQUIPMENT. Ring Bradford (0274) 308920 for our catalogue or call at our large showrooms opposite Odsal Stadium.

CABINET FITTINGS

Fretcloths, Coverings, Handles, Castors, Flight Case Locks & Parts, Jacks, XLRs, Bulgins, Reverb Trays, P & N mic Stands, ASS Glassfibre Horns, CELESTION POWER Speakers.

ADAM HALL SUPPLIES LTD.
Send 30p cheque/ P.O. for illustrated catalogue: Adam Hall (PE Supplies), Unit G, Carlton Court, Grainger Road, Southend-on-Sea.

MAKE YOUR OWN PRINTED CIRCUITS

Etch Resist Transfers - Starter pack (5 sheets, lines, pads, I.C. pads) £2.10. Large range of single sheets in stock at 45p per sheet.

Master Positive Transparencies from P.C. layouts in magazines by simple photographic process. 2 sheets negative paper, 2 sheets positive film (A4) £2.25. **Photo-resist spray** (200 ml) £3.90 (p + p 65p). **Drafting Film (A4) 25p.** **Precision Grids (A4) 65p.** 22p stamp for lists and information. P&P 50p per order except where indicated.

P.K.G. ELECTRONICS
OAK LODGE, TANSLEY, DERBYSHIRE.

THE SCIENTIFIC WIRE COMPANY PO Box 30, London, E.4. 01-531 1568.

ENAMELLED COPPER WIRE

SWG	1lb	8oz	4oz	2oz
8 to 34	3.30	1.90	1.00	0.80
35 to 39	3.52	2.10	1.15	0.85
40 to 43	4.87	2.65	2.05	1.46
44 to 47	8.37	5.32	3.19	2.50
48 to 49	15.96	9.58	6.38	3.69

SILVER PLATED COPPER WIRE

14 to 30	6.63	3.86	2.28	1.50
----------	------	------	------	------

TINNED COPPER WIRE

14 to 30	3.97	2.41	1.39	0.94
----------	------	------	------	------

10 x 10 Mtr reels 3 amp PVC cable mixed colours £5.00.
Prices include P&P, VAT. Orders under £2 add 20p. SAE for list of copper and resistance wire. Dealer enquiries welcome.

CENTURION ALARMS

We manufacture, you save £££'s

Send s.a.e. or phone for our Free list of professional D.I.Y. Burglar Alarm Equipment and accessories. Discount up to 20% off list prices, e.g. Control Equipment from £15.98, Decoy Bell Boxes from £5.95 inc.

TRADE ENQUIRIES WELCOME

0484-21000

or 0484 35527 (24 hr. ans.)

CENTURION ALARMS (PE)
265 Wakefield Road, Huddersfield HD5 9BE, W. Yorkshire
Access & Visa Orders Welcomed

When replying to Classified Advertisements please ensure:

- That you have clearly stated your requirements.
- That you have enclosed the right remittance.
- That your name and address is written in block capitals, and
- That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Practical Electronics for.....
insertions. I enclose Cheque/P.O. for £

(Cheques and Postal Orders should be crossed Lloyds Bank PLC, and made payable to Practical Electronics)

NAME

ADDRESS

Company registered in England. Registered No. 53626. Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS.

Send to: Classified Advertisement Department

PRACTICAL ELECTRONICS

Classified Advertisement Dept., Room 2612,
King's Reach Tower, Stamford Street,
London SE1 9LS. Telephone 01-261 5846

Rate:

34p per word, minimum 12 words. Box No. 60p extra.

CLEF ELECTRONIC MUSIC



ELECTRONIC PIANOS

SPECIALISTS SINCE 1972

Clef Pianos adopt the most advanced form of Touch Sensitive action which simulates piano Key inertia using a patented electronic technique.

7 1/4 OCTAVE DOMESTIC MODEL COMPONENT KIT £266 COMPLETE KIT £442

MANUFACTURED £695

Two Domestic Models are available including the 88-note full-size version. Four intermixable Voice Controls may be used to obtain a wide variation of Piano tone, including Harpsichord. Both Soft and Sustain Pedals are incorporated in the Design and internal Effects are provided in the form of Tremolo, Honky Chorus, and Phase/Flanger.

A power amplifier integrates into the Piano top which may be removed from the base for easy transportation.

SIX OCTAVE DOMESTIC MODEL COMPONENT KIT £234 COMPLETE KIT £398 MAN. £620

Component Kits include Keyboard, Key switch hardware, and all electronic components and may be purchased in four stages at no extra cost.

Complete Kits further contain Cabinets, wiring harness, Pedals and in the case of Domestic Models both Power Amplifier and Speaker.

The Six Octave Stage Piano has the same range of Voices and Effects and is designed for use with an External Amplifier and Speaker.

SIX OCTAVE STAGE MODEL COMPONENT KIT £234 MANUFACTURED £580

Please allow 7 days for normal despatch

MICROSYNTH THE COMPACT MUSIC SYNTHESIZER

Design — Allan Bradford
Published in P.E.



COMPLETE KIT * SWITCH ROUTING * 2 1/2 OCTAVES * 2 OSCILLATORS * THUMBWHEEL * 2 SUB-OCTAVES

£129.00

STRING ENSEMBLE

(As Published in conjunction with 'Practical Electronics')

A very popular Keyboard Synthesizer Kit, for Group or Home use, with a four octave compass and split Keyboard facility.

COMPONENT KIT £197.50

Comprehensive two speed organ rotor simulator plus a three phase chorus generator.

COMPONENT KIT £98.00

KEYBOARDS

Our Square Front Keyboards

88 NOTE (A-C) £62.67

73 NOTE (F-F) £51.75

FIVE OCTAVE £41.97

FOUR OCTAVE £31.62

Since 1972 Clef Products have consistently produced leading designs in the field of Electronic Musical Instruments, many of which have been published in technical magazines. With musical quality of paramount importance, new techniques have been evolved and the latest musically valid technology has been incorporated into projects which have been successfully completed by constructors over a wide range of technical capability. Back up TELEPHONE advice is available to all our customers. All instruments are on show.

PRICES INCLUDE VAT, UK CARRIAGE & INSURANCE (CARRIAGE EXTRA ON MFD PIANOS). Please send S.A.E. for our complete lists, or use our telephone VISA/ACCESS service. Competitive quotations can be given for EXPORT orders — in Australia please contact JAYCAR in Sydney. VISIT OUR SHOWROOM.

CLEF PRODUCTS (ELECTRONICS) LIMITED

(Dept. P.E.) 44A Bramhall Lane South, Bramhall, Stockport, Cheshire SK7 1AH 061-439-3297

"THE COMPUTER BAND-BOX" COMPLETE KIT £235

£235

£320 MANFD.



MASTER RHYTHM ALSO REQUIRED

A revolution in the field of Computer Music Generation!

A MUSICIANS INSTRUMENT FOR: SOLOISTS — SINGERS — RECORDING — PRACTICE LIVE PERFORMANCE — COMPOSITION

The BAND-BOX provides an Electronic Backing Trio consisting of Drums, Bass, and a Chord Instrument (one of 6 Waveform/Envelope combinations), with the capacity to store over 3,000 User Programmable Chord Changes on more than 120 different Chords. Using advanced Microprocessor technology, Playback of 50-100 Scores can be executed in any Key and at chosen Tempo. Complete Music Pad is electronically Indexed and stored on secondary battery back-up. Facility exists for composition of Intro, Repeat Chorus, and Coda sections including Multiple Score Sequences. Sockets are provided for Volume Pedal and Footswitch plus separate and mixed instrument Outputs. Total size 19" x 11" x 4 1/2" incorporating Master Rhythm.

THE Programmable DRUM MACHINE

(As Published in conjunction with 'Practical Electronics')

EIGHT TRACK PROGRAMMING / TWENTY FOUR PATTERNS / TWELVE INSTRUMENTS SEQUENCE OPERATION. COMPLETE KIT £79.00 MANFD. £119.00



The Clef Master Rhythm is capable of storing 24 selectable rhythmic drum patterns, invented, modified, and entered by the Operator on to Eight Instrumentation tracks. A three position Instrumentation control expands the number of instruments available to twelve, grouped into sounds typical of playing with Drumsticks, Brushes, or Latin American Bongos and Claves. Sequence operation allows two rhythm sections to be coupled with the second (B) section appearing at four, eight or sixteen Bar repetition. All drums can be adjusted for level and resonance on internal controls to suit individual taste, thus producing good musical sounds in a battery driven unit 8 1/2" x 5" x 2 1/4".

ALARMS

FREE CATALOGUE!

OUR GREAT NEW ILLUSTRATED CATALOGUE IS PACKED WITH INFORMATION ON SUPERB QUALITY, PROFESSIONAL BURGLAR ALARM EQUIPMENT

AT UNBEATABLE PRICES!

SEND SAE OR PHONE NOW FOR YOUR COPY



THIEFTEST BURGLAR ALARM D-I-Y SYSTEM



MAIN DISTRIBUTOR

A.D. ELECTRONICS
DEPT. PE
217 WARBECK MOOR
AINTREE LIVERPOOL
L9 0HU/051 523 8440

PARNDON ELECTRONICS LTD.

Dept No. 21 44 Paddock Mead, Harlow, Essex. CM18 7RR Tel: 0279 32700

RESISTORS: 1/4 Watt Carbon Film E24 range $\pm 5\%$ tolerance. High quality resistors made under strictly controlled conditions by automatic machines. Banded over and colour coded.

£1.00 per hundred mixed (Min 10 per value)

£8.50 per thousand mixed (Min 50 per value)

Special stock pack. 60 values. 10 off each £5.50

DIODES: IN4148 3p each. Min order quantity — 15 items
£1.60 per hundred

DIL SWITCHES: Gold plated contact in fully sealed base — solve those programming problems
4 Way 86p each. 6 Way £1.00 each. 8 Way £1.20 each

DIL SOCKETS: High quality, low profile sockets.
8 pin — 10p. 14 pin — 11p. 16 pin — 12p. 18 pin — 19p. 20 pin — 21p.
22 pin — 23p. 24 pin — 25p. 28 pin — 27p. 40 pin — 42p.

ALL PRICES INCLUDE V.A.T. & POST & PACKING — NO EXTRAS
MIN ORDER — UK £1.00 OVERSEAS £5 CASH WITH ORDER PLEASE
Same Day Despatch


LOW COST PROFESSIONAL TEST INSTRUMENTS



Belemic

Hand Held
Analogue and
Digital
Multimeters

16 Models
from £18.75

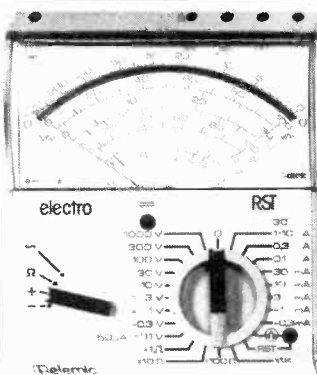

- ★ FREQUENCY METERS
- ★ ANALOGUE MULTIMETERS
- ★ DIGITAL MULTIMETERS
- ★ FUNCTION GENERATOR
- ★ OSCILLOSCOPES
- ★ POWER SUPPLIES
- ★ LOGIC PROBE
- ★ SCOPE PROBES

Write or phone for illustrated test instrument catalogue and price list

Black Star Ltd.
9A, Crown Street
St. Ives, Huntingdon
Cambs. PE17 4EB
Tel: (0480) 62440 Telex 32339



INDEX TO ADVERTISERS

A.D. Electronics	82
Ambit	77
Army	67
Aura	12, 75
Barrie	76
Beckman Instruments	75
Bi-Pak	6, 7
Blackstar	82
Brystep Electronics	80
British National Radio & Electronics School	13
Bull, J.	74
Cambridge Kits	78
Centurion Alarms	81
Clef Products	82
Cricklewood	10, 11
Crofton	70
C.R. Supply Co.	80
Dataman Design	71
Dataplus	72
DCP Developments	76
Electrovalue	78
Emos	83
Enfield	78
Flight Electronics	60
Government Communications Headquarters	79
G.S.C.	12, 47
Hall, Adam	81
ICS Intertext	79
ILP Electronics	4, 5, 84
Jupiter Cantab	21
L&B Electronics	78
Maplin Electronics	Cover 4
Mercia Electronics	72
Midwich Computers	48
Modern Book Co.	10
Myers, Gerald	80
Parndon Electronics	82
Phonosonics	74
Pimac Systems	70
Powertran	28, Cover 2
Proto Design	81
Radio Component Specialists	70
Radio & T.V. Components	9
Rapid Electronics	15
Response Co.	80
Riscomp	14
Service Trading	73
Sinclair Research	68, 69
Swanley Electronics	79
Tandy	58
Technomatic	84, Cover 3
Tempus	76
Texas Instruments	63
T.K. Electronics	8
Velleman U.K.	72
Videotone	14
Watch & Clock Technicians Training Centre	81
Watford Electronics	2, 3
Wilmslow Audio	74

ANNOUNCING THE NEW MAIL ORDER DIVISION OF THE GRENSON GROUP. VAST STOCKS AND COMPUTER CONTROLLED OPERATION HAVE ASSURED VERY COMPETITIVE PRICES. SEE FOR YOURSELF!

BENCH POWER SUPPLIES.

As featured in Feb 82 'Practical Electronics'.

Unit (BPU1)	KIT	BUILT
P + P	£35	£59
V.A.T.	£ 3.35	£ 3.35
	£ 5.75	£ 9.35

Triple output unit (1 ± 15V and +5V) available shortly.

The Grenson Group have over twenty years experience designing power supplies. Contact us now and we will try to solve your problem.

LARGE ELECTROLYTICS.

Sprague/General Electric made - computer grade - ideal for power supplies -

ONLY £2.50 EACH!

185,000 @ 15V. 300,000 @ 7V. 120,000 @ 15V. 100,000 @ 30V.
71,000 @ 40V. 60,000 @ 40V. 9,000 @ 50V.

SMALL ALUMINIUM ELECTROLYTICS.

Axial Leads			Radial Leads		
uF	V	Price	uF	V	Price
1000	6.3	15p	470	16	15p
22	10	05p	4.7	25	05p
100	10	05p	330	25	15p
22	16	05p	680	25	25p
			470	40	25p
			220	63	20p

OLD TIMERS SECTION.

OC44	70p	OC45	37p	OC71	34p	OC70	36p	OC42	70p
OC35	90p	OC25	75p	OC16	200p	OC170	44p	OC22	150p
2S024	200p	OC139	70p	OC140	75p	2S307	85p	2ST01	80p
OC84	25p	OC41	60p	2S301	80p	OC76	40p	OC73	40p
OC83	40p	OA5	10p	OA7	15p	OA10	15p	OA47	10p

MIXED BAGS.

Capacitors - 30 assorted values only £1.00!

Transistors - 20 small signal plastic - 1/2 n.p.n. - 1/2 p.n.p. only £1.50.

Lists available on request.

RESISTORS.

We have, amongst others, the following resistors in stock:-

Over 1 1/2 million 1/2 watt carbon film.

Over 1/2 million 1/2 watt metal oxide.

Over 1/2 million wirewound.

Further stock listed in our free catalogue.

Typical Prices

	1-9	10-99	100+
1/2 watt carbon	2p	1 1/2p	1p
1/2 watt metal oxide	6p	4p	3p
6 watt wirewound	25p	15p	12p

SERIES 74 I.C.'s.

Comprehensive stocks, competitively priced. Simple gates from only 10p.

See our free catalogue for details.

I.C. SOCKETS.

14 way - 10p. 46 way - could be broken to make smaller strips - 25p. 16 way - gold pins - 20p.

TRANSISTORS.

AC107	30p	BC149	7p	BC212L	9p	BC337	13p	BF198	13p
AC126	30p	BC159	12p	BC213L	12p	BC558	14p	BF199	15p
AC188	27p	BC171	10p	BC237	12p	BF115,	29p	BFR40	20p
ACV17	66p	BC173	10p	BC308	13p	BF194	13p	BFX29	25p
ACY19	65p	BC212	9p	BC327	18p	BF197	13p	BFY90	60p

2N706	15p	2N2222A	20p	2N3705	10p	2N4061	10p
2N1131	20p	2N2369A	15p	2N3711	10p	2N5172	15p
2N1132	20p	2N3702	10p	2N3904	15p	2N5179	30p

VOLTAGE REGULATORS AND P.S.U. COMPONENTS.

+ 5V 1A T0220	50p	+12V 0.5A T0220	50p	+15V 1A T0220	50p
+ 5V 1.5A T03	1.50p	+12V 0.5A T03	90p	+15V 0.5A T03	90p
- 5V 1A T0220	50p	+12V 1.5A T03	1.50p	-15V 1A T0220	50p
- 5V 1.5A T03	2.00p	-12V 1A T0220	50p	-18V 1A T0220	50p
+ 6V 0.5A T0220	50p	-12V 1.5A T03	2.00p	-24V 1A T0220	80p

2N3055 35p, 2N4347 (120V) 1.50p, 2N6258 (250W) 1.80p, 400mW Zeners 5p, 723 30p.

★ SPECIAL OFFER ★ ★ SPECIAL OFFER ★ ★ SPECIAL OFFER ★

For every order received in December 1982 of a value greater than £10.00, a free bag of assorted components worth at least £2.00 will be sent with the order.

Please allow 21 days for delivery.

Dept. A1, High March, Daventry, Northants NN11 4HQ.
Tel: 03272 5523 Telex: 311245 GRENEL G.

Please add 50p per order postage and packing plus 15% VAT on total. No VAT on overseas orders, postage at cost. Cheques and postal orders made payable to Emos Limited. Send large SAE for comprehensive catalogue.

EMOS

TOROIDALS



The toroidal transformer is now accepted as the standard in industry, overtaking the obsolete laminated type. Industry has been quick to recognise the advantages toroidals offer in size, weight, lower radiated field and, thanks to I.L.P., PRICE.

Our large standard range is complemented by our **SPECIAL DESIGN** section which can offer a prototype service within 7 DAYS together with a short lead time on quantity orders which can be programmed to your requirements with no price penalty.

TYPE	SERIES	SECONDARY	RMS	PRICE
	No	Volts	Current	
30 VA 70 x 30mm 0.45 Kg Regulation 18%	1x010	6+6	2.50	£5.12 +p/p £1.04 +VAT £0.92 TOTAL £7.08
	1x011	9+9	1.66	
	1x012	12+12	1.25	
	1x013	15+15	1.00	
	1x014	18+18	0.83	
	1x015	22+22	0.68	
	1x016	25+25	0.60	
50 VA 80 x 30mm 0.9 Kg Regulation 13%	2x010	6+6	4.16	£5.70 +p/p £1.30 +VAT £1.05 TOTAL £8.05
	2x011	9+9	2.77	
	2x012	12+12	2.08	
	2x013	15+15	1.66	
	2x014	18+18	1.38	
	2x015	22+22	1.13	
	2x016	25+25	1.00	
80 VA 90 x 30mm 1 Kg Regulation 12%	3x010	6+6	6.64	£6.08 +p/p £1.67 +VAT £1.16 TOTAL £8.91
	3x011	9+9	4.44	
	3x012	12+12	3.33	
	3x013	15+15	2.66	
	3x014	18+18	2.22	
	3x015	22+22	1.81	
	3x016	25+25	1.60	
120 VA 90 x 40mm 1.2 Kg Regulation 11%	3x020	110	0.72	£6.90 +p/p £1.87 +VAT £1.79 TOTAL £9.56
	3x029	220	0.36	
	3x030	240	0.33	
	4x010	6+6	10.00	
	4x011	9+9	6.66	
	4x012	12+12	5.00	
	4x013	15+15	4.00	
160 VA 110 x 40mm 1.8 Kg Regulation 8%	4x014	18+18	3.33	£7.91 +p/p £2.17 +VAT £2.14 TOTAL £12.22
	4x015	22+22	2.72	
	4x016	25+25	2.40	
	4x017	30+30	2.00	
	4x018	35+35	1.71	
	4x020	110	0.54	
	4x030	240	0.50	

- ★ 294 TYPES TO CHOOSE FROM!
- ★ ORDERS DESPATCHED WITHIN 7 DAYS OF RECEIPT FOR SINGLE OR SMALL QUANTITY ORDERS
- ★ 5 YEAR NO QUIBBLE GUARANTEE

TYPE	SERIES	SECONDARY	RMS	PRICE
	No	Volts	Current	
225 VA 110 x 45mm 2.2 Kg Regulation 7%	6x012	12+12	9.38	£9.20 +p/p £2.00 +VAT £1.88 TOTAL £13.08
	6x013	15+15	7.50	
	6x014	18+18	6.25	
	6x015	22+22	5.11	
	6x016	25+25	4.50	
	6x017	30+30	3.75	
	6x018	35+35	3.21	
300 VA 110 x 50mm 2.6 Kg Regulation 6%	6x026	40+40	2.81	£10.17 +p/p £2.00 +VAT £1.83 TOTAL £14.00
	6x025	45+45	2.50	
	6x033	50+50	2.25	
	6x028	110	2.04	
	6x029	220	1.02	
	6x030	240	0.93	
	7x013	15+15	10.00	
300 VA 110 x 50mm 2.6 Kg Regulation 6%	7x014	18+18	8.33	£10.17 +p/p £2.00 +VAT £1.83 TOTAL £14.00
	7x015	22+22	6.82	
	7x016	25+25	6.00	
	7x017	30+30	5.00	
	7x018	35+35	4.28	
	7x026	40+40	3.75	
	7x025	45+45	3.33	
500 VA 140 x 60mm 4 Kg Regulation 4%	8x033	50+50	5.00	£13.53 +p/p £2.35 +VAT £2.18 TOTAL £18.06
	8x042	55+55	4.54	
	8x028	110	4.54	
	8x029	220	2.27	
	8x030	240	2.08	
	9x017	30+30	10.41	
	9x018	35+35	8.92	
625 VA 140 x 75mm 5 Kg Regulation 4%	9x026	40+40	7.81	£16.13 +p/p £2.50 +VAT £2.19 TOTAL £21.42
	9x025	45+45	6.94	
	9x033	50+50	6.25	
	9x042	55+55	5.68	
	9x028	110	5.68	
	9x029	220	2.84	
	9x030	240	2.60	

IMPORTANT: Regulation—All voltages quoted are FULL LOAD. Please add regulation figure to secondary voltage to obtain off load voltage.

The benefits of ILP toroidal transformers

ILP toroidal transformers are only half the weight and height of their laminated equivalents, and are available with 110V, 220V or 240V primaries coded as follows:

For 110V primary insert "0" in place of "X" in type number.

For 220V primary (Europe) insert "1" in place of "X" in type number.

For 240V primary (UK) insert "2" in place of "X" in type number.

How to order Freepost:

Use this coupon, or a separate sheet of paper, to order these products, or any products from other ILP Electronics advertisements. No stamp is needed if you address to Freepost. Cheques and postal orders must be crossed and payable to ILP Electronics Ltd. Access and Barclaycard welcome. All UK orders sent within 7 days of receipt of order for single and small quantity orders.

Also available at Electrovalue, Maplin and Technomatic.

ILP Electronics, Graham Bell House, Roper Close, Canterbury, Kent, CT2 7EP.

Please send

Total purchase price

I enclose Cheque ☐ Postal Orders ☐ Int. Money Order ☐

Debit my Access/Barclaycard No

Name

Address

Signature

Post to: ILP Electronics Ltd, Freepost, 2 Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent, England

Telephone Sales (0227) 54778. Technical (0227) 64723. Telex 965780



CONNECTOR SYSTEMS

I.D. CONNECTORS (Speedblock Type)				D-CONNECTORS				DIL HEADER PLUGS		RIBBON CABLE	
No. of ways	Header	Recept.	Edge Conn.	9 way	15 way	25 way	37 way	RS 232 Connectors Available From Stock	10 way (Grey)	10 way (Grey)	
10	80p	90p	200p	MALE	130p	160p	250p	4 pin type IDC	14 way 60p	14 way 60p	
20	145p	125p	240p	Angled 160p	230p	265p	425p	6 pin type IDC	16 way 90p	16 way 90p	
26	175p	150p	300p	FEMALE				8 pin type IDC	20 way 105p	20 way 105p	
34	200p	160p	380p	Solder 110p	160p	210p	350p	10 pin type IDC	26 way 140p	26 way 140p	
40	220p	190p	550p	Angled 175p	240p	310p	500p	12 pin type IDC	34 way 220p	34 way 220p	
50	235p	200p	600p	Hood 95p	95p	95p	125p	16 pin type IDC	40 way 265p	40 way 265p	
				38 way Centronix Type Conn. £5.50				24 pin type IDC	50 way 330p	50 way 330p	
				25 way IEEE Type Conn. £5.50				40 pin type IDC	64 way 370p	64 way 370p	

JUMPER LEADS		EURO CONNECTORS (Indirect Edge Conn.)		EDGE CONNECTORS	
24" Ribbon Cable with headers		DIN STD	Plug	Skt	0.1" 0.156"
14 pin	16 pin	24 pin	40 pin	2x18 way	140p
1 end 145p	165p	240p	380p	2x22 way	200p
2 ends 210p	230p	345p	540p	2x23 way	210p
24" Ribbon Cable with sockets		Angled 2x32 way	250p	2x25 way	225p
20 pin	26 pin	34 pin	40 pin	1x43 way	260p
1 end 160p	210p	270p	300p	2x43 way	395p
2 ends 290p	385p	490p	540p	2x50 way	—
24" Ribbon Cable with D Conn.		2x32 way IDC a-c	—	1x77 way	700p
25 way Male 500p	Female 550p.	(for 2x32 way specify a+b or a+c)		S100 Conn	600p

★ SPECIAL OFFER ★

1-24	25-99	1-24	25-99
2114L-450	90p	2732	375p
4164-2	450p	4116-200	90p
2716 (+5V)	250p	6116-150	410p
2532	375p	6522	310p

OFFICIAL BBC DEALER

BBC Model 'A' £299 (inc. VAT) Model 'B' £399 (inc. VAT)
(Carr. £8/unit)

MEMORY PACK
8 x 4816 AP-3 100ns £21.60

ACORN DISC DRIVES
SINGLE DRIVE (100K)
£235 + £4 carr.
DUAL DRIVE (180K)
£799 + £6 carr.

DISC INTERFACE £70
PRINTER & USER PORTS
ICS 69, 70, 71, PL 9, 10 £9.50
PRINTER LEAD COMPLETE £13.50

ANALOGUE PORT
IC72, PL6 £7.30

RS423 & VDU PORTS
IC74, 75 SK 3 & 4 £10.80

ALL MATING CONNECTORS & CABLES AVAILABLE SEND FOR OUR BBC LIST

PRINTERS

NEC PC 8023 BE

80 col. 100 cps dot matrix printer. Bi-directional, Logic Seeking, Forward & Reverse Line Feed. Hi Res & Block Graphics, Proportional Spacing, International and Greek character sets. Auto underline, Friction/tractorselectable. £340 + £8 carr.

EPSON MX80 FT/3 and EPSON MX100 FT/3

Dot matrix printers. Bi-directional, Logic Seeking, Auto Underline, Bit Image Printing, Super & Sub-scripts, 80 col. 8 cps £325 + £8 carr. 136 col. 100 cps £430 + £10 carr.

SEIKOSHA GP100A

80 col. 30 cps dot matrix printer. High Res Graphics - Std & double width characters. £175 + £6 carr.

MONITORS

SANYO 12" Green screen monitor £99 + £6 carr.
BMC 14" Colour monitor £240 + £8 carr.
MICROVITEC 14" Colour monitor £269 + £8 carr.
SANYO COMPUTER GRADE CASSETTE RECORDER
£24.50 + £1.50 carr.

5V PSU

3A 5V Regulated Power Supply Fully Complete with mains fuse. £26 + £2 p. & p.

SOFTY II EPROM PROGRAMMER

The complete microprocessor development system for both Engineers and Hobbyists. You can develop programs, debug, verify and commit them to EPROMs. Will accept most + 5V EPROMs. Can also be used as a ROMULATOR. Full review in September 81 PE. Built unit complete with PSU and TV lead £169.

MICROTIMER

6502
BASED PROGRAMMER
CLOCK TIMER
PRICE FOR KIT £57.00

★ 224 switching times/week cycle ★ 24 hour 7 day timer ★ 4 independent switch outputs directly interfacing to thyristor/triacs ★ 6 digit 7 seg. display to indicate real time, ON/OFF and Reset times ★ Output to drive day of week switch and status LEDs. Full details on request.

RUGBY ATOMIC CLOCK

This Z-80 micro controlled clock/calendar receives coded time data from NPL Rugby. The clock never needs to be reset. The facilities include 8 independent alarms and for each alarm there is a choice of melody or alternatively these can be used for electrical switching. A separate timer allows recording of up to 240 lap times without interrupting the count. Expansion facilities provided. See July/August ETI for details. Complete kit £120 + £2 p.&p.

PLEASE ADD 40p p&p & 15% VAT
(Export no VAT p&p at Cost)

Orders from Government Depts. & Colleges etc. welcome.
BARCLAYCARD & ACCESS CARDS ACCEPTED

Detailed Price List on request.

Stock items are normally by return of post.

TTLs		74293	80p	74LS364	140p	4012	16p	LINEAR I.C.s		M51513L	230p
7400	11p	74298	100p	74LS365A	30p	4013	20p	AN103	200p	M51516L	500p
7401	11p	74365A	30p	74LS367A	30p	4014	48p	AY1-0212	600p	M83712	200p
7402	11p	74366A	30p	74LS368A	30p	4015	40p	AY1-1313	650p	MC1310P	150p
7403	12p	74367A	30p	74LS373	55p	4016	20p	AY1-1320	225p	MC1413	100p
7404	12p	74368A	30p	74LS374	55p	4017	32p	AY1-5050	80p	MC1458	36p
7405	15p	74390	75p	74LS375	45p	4018	45p	AY3-8910	380p	MC1495L	350p
7406	18p	74393	90p	74LS377	70p	4019	25p	AY3-8912	625p	MC1496	70p
7407	18p	74490	95p	74LS378	70p	4020	45p	AY5-1350	500p	MC3340P	120p
7408	14p	74LS SERIES		74LS38	70p	4021	20p	AY5-4007D	520p	MC3401	50p
7409	14p	74LS00	11p	74LS383	45p	4022	45p	CA3028A	80p	MC3402	50p
7410	14p	74LS01	11p	74LS384	45p	4023	13p	CA3019	80p	MC5093B	635p
7411	16p	74LS02	11p	74LS385	160p	4024	32p	CA3046	70p	ML920	800p
7412	14p	74LS03	12p	74LS386	100p	4025	13p	CA3048	220p	MM57160	620p
7413	16p	74LS04	12p	74LS387	100p	4026	80p	CA3059	285p	NE531	140p
7414	18p	74LS05	12p	74LS388	100p	4027	40p	CA3080E	70p	NE555	16p
7415	18p	74LS08	12p	74LS389	100p	4028	40p	CA3089E	200p	NE564	420p
7416	18p	74LS10	12p	74LS390	100p	4029	40p	CA3090A	375p	NE565	120p
7417	18p	74LS11	12p	74LS391	100p	4030	125p	CA3130E	90p	NE566	155p
7418	18p	74LS12	12p	74LS392	100p	4031	80p	CA3140E	100p	NE567	140p
7419	20p	74LS13	13p	74LS393	100p	4032	125p	CA3160E	100p	NE570	410p
7420	20p	74LS14	13p	74LS394	100p	4033	140p	CA3161E	100p	NE571	410p
7421	20p	74LS15	13p	74LS395	100p	4034	45p	CA3162E	450p	NE5534A	125p
7422	20p	74LS16	13p	74LS396	100p	4035	275p	CA3189E	300p	PL02A	500p
7423	20p	74LS17	13p	74LS397	100p	4036	110p	CA3240E	110p	RC4136	200p
7424	20p	74LS18	13p	74LS398	100p	4037	40p	CA3280G	200p	RC4151	200p
7425	20p	74LS19	13p	74LS399	100p	4038	40p	DAC1408B	80p	RC4558	225p
7426	20p	74LS20	13p	74LS400	100p	4039	40p	HA1366	195p	SC566	225p
7427	20p	74LS21	13p	74LS401	100p	4040	40p	HA1368	195p	SA01024A	80p
7428	20p	74LS22	13p	74LS402	100p	4041	40p	ICL7100	700p	SF96364	80p
7429	20p	74LS23	13p	74LS403	100p	4042	105p	ICL7100	700p	SL490	350p
7430	20p	74LS24	13p	74LS404	100p	4043	50p	ICL7100	700p	SN76477	450p
7431	20p	74LS25	13p	74LS405	100p	4044	45p	ICL7100	700p	SN76488	450p
7432	20p	74LS26	13p	74LS406	100p	4045	45p	ICL7100	700p	SR815	750p
7433	20p	74LS27	13p	74LS407	100p	4046	45p	ICL7100	700p	TA7120	150p
7434	20p	74LS28	13p	74LS408	100p	4047	45p	ICL7100	700p	TA7204	150p
7435	20p	74LS29	13p	74LS409	100p	4048	45p	ICL7100	700p	TA7205	150p
7436	20p	74LS30	13p	74LS410	100p	4049	45p	ICL7100	700p	TA7222	150p
7437	20p	74LS31	13p	74LS411	100p	4050	45p	ICL7100	700p	TA7310	150p
7438	20p	74LS32	13p	74LS412	100p	4051	45p	ICL7100	700p	TA7311	150p
7439	20p	74LS33	13p	74LS413	100p	4052	45p	ICL7100	700p	TA7312	150p
7440	20p	74LS34	13p	74LS414	100p	4053	45p	ICL7100	700p	TA7313	150p
7441	20p	74LS35	13p	74LS415	100p	4054	45p	ICL7100	700p	TA7314	150p
7442	20p	74LS36	13p	74LS416	100p	4055	45p	ICL7100	700p	TA7315	150p
7443	20p	74LS37	13p	74LS417	100p	4056	45p	ICL7100	700p	TA7316	150p
7444	20p	74LS38	13p	74LS418	100p	4057	45p	ICL7100	700p	TA7317	150p
7445	20p	74LS39	13p	74LS419	100p	4058	45p	ICL7100	700p	TA7318	150p
7446	20p	74LS40	13p	74LS420	100p	4059	45p	ICL7100	700p	TA7319	150p
7447	20p	74LS41	13p	74LS421	100p	4060	45p	ICL7100	700p	TA7320	150p
7448	20p	74LS42	13p	74LS422	100p	4061	45p	ICL7100	700p	TA7321	150p
7449	20p	74LS43	13p	74LS423	100p	4062	45p	ICL7100	700p	TA7322	150p
7450	20p	74LS44	13p	74LS424	100p	4063	45p	ICL7100	700p	TA7323	150p
7451	20p	74LS45	13p	74LS425	100p	4064	45p	ICL7100	700p	TA7324	150p
7452	20p	74LS46	13p	74LS426	100p	4065	45p	ICL7100	700p	TA7325	150p
7453	20p	74LS47	13p	74LS427	100p	4066	45p	ICL7100	700p	TA7326	150p
7454	20p	74LS48	13p	74LS428	100p	4067	45p	ICL7100	700p	TA7327	150p
7455	20p	74LS49	13p	74LS429	100p	4068	45p	ICL7100	700p	TA7328	150p
7456	20p	74LS50	13p	74LS430	100p	4069	45p	ICL7100	700p	TA7329	150p
7457	20p	74LS51	13p	74LS431	100p	4070	45p	ICL7100	700p	TA7330	150p
7458	20p	74LS52	13p	74LS432	100p	4071	45p	ICL7100	700p	TA7331	150p
7459	20p	74LS53	13p	74LS433	100p	4072	45p	ICL7100	700p	TA7332	150p
7460	20p	74LS54	13p	74LS434	100p	4073	45p	ICL7100	700p	TA7333	150p
7461	20p	74LS55	13p	74LS435	100p	4074	45p	ICL7100	700p	TA7334	150p
7462	20p	74LS56	13p	74LS436	100p	4075	45p	ICL7100	700p	TA7335	150p
7463	20p	74LS57	13p	74LS437	100p	4076	45p	ICL7100	700p	TA7336	150p
7464	20p	74LS58	13p	74LS438	100p	4077	45p	ICL7100	700p	TA7337	150p
7465	20p	74LS59	13p	74LS439	100p	4078	45p	ICL7100	700p	TA7338	150p
7466	20p	74LS60	13p	74LS440	100p	4079	45p	ICL7100	700p	TA7339	150p
7467	20p	74LS61	13p	74LS441	100p	4080	45p	ICL7100	700p	TA7340	150p
7468	20p	74LS62	13p	74LS442	100p	4081	45p	ICL7100	700p	TA7341	150p
7469	20p	74LS63	13p	74LS443	100p	4082	45p	ICL7100	700p	TA7342	150p
7470	20p	74LS64	13p	74LS444	100p	4083	45p	ICL7100	700p	TA7343	150p
7471	20p	74LS65	13p	74LS445	100p	4084	45p	ICL7100	700p	TA7344	150p
7472	20p	74LS66	13p	74LS446	100p	4085	45p	ICL7100	700p	TA7345	150p
7473	20p	74LS67	13p	74LS447	100p	4086	45p	ICL7100	700p	TA7346	150p
7474	20p	74LS68	13p	74LS448	100p	4087	45p	ICL7100	700p	TA7347	150p
7475	20p	74LS69	13p	74LS449	100p	4088	45p	ICL7100	700p	TA7348	150p
7476	20p	74LS70	13p	74LS450	100p	4089	45p	ICL7100	700p	TA7349	150p
7477	20p	74LS71	13p	74LS451	100p	4090	45p	ICL7100	700p	TA7350	150p
7478	20p	74LS72	13p	74LS452	100p	4091	45p	ICL7100	700p	TA7351	150p
7479	20p	74LS73	13p	74LS453	100p	4092	45p	ICL7100	700p	TA7352	150p
7480	20p	74LS74	13p	74LS454	100p	4093	45p	ICL7100	700p	TA7353	150p
7481	20p	74LS75	13p	74LS455	100p	4094	45p	ICL7100	700p	TA7354	150p
7482	20p	74LS76	13p	74LS456	100p	4095	45p	ICL7100	700p	TA7355	150p
7483	20p	74LS77	13p	74LS457	100p	4096	45p	ICL7100	700p	TA7356	150p
7484	20p	74LS78	13p	74LS458	100p	4097	45p	ICL7100	700p	TA7357	150p
7485	20p	74LS79	13p	74LS459	100p	4098	45p	ICL7100	700p	TA7358	150p
7486	20p	74LS80	13p	74LS460	100p	4099	45p	ICL7100	700p	TA7359	150p
7487	20p	74LS81	13p	74LS461	100p	4100	45p	ICL7100	700p	TA7360	150p
7488	20p	74LS82	13p	74LS462	100p	4101	45p	ICL7100	700p	TA7361	150p
7489	20p	74LS83	13p	74LS463	100p	4102	45p	ICL7100	700p	TA7362	150p
7490	20p	74LS84	13p	74LS464	100p	4103	45p	ICL7100	700p	TA7363	150p
7491	20p	74LS85	13p	74LS465	100p	4104	45p	ICL7100	700p	TA7364	150p
7492	20p	74LS86	13p	74LS466	100p	4105	45p	ICL7100	700p	TA7365	150p
7493	20p	74LS87	13p	74LS467	100p	4106	45p	ICL7100	700p	TA7366	150p
7494	20p	74LS88	13p	74LS468	100p	4107	45p	ICL7100	700p	TA7367	150p
7495	20p	74LS89	13p	74LS469	100p	4108	45p	ICL7100	700p	TA7368	150p
7496	20p	74LS90	13p	74LS470	100p	4109	45p	ICL7100	700p	TA7369	150p
7497	20p	74LS91	13p	74LS471	100p	4110	45p	ICL7100	700p	TA7370	150p
7498	20p	74LS92	13p	74LS472	100p	4111	45p	ICL7100	700p	TA7371	150p
7499	20p	74LS93	13p	74LS473	100p	4112	45p	ICL7100	700p	TA7372	150p
7500	20p	74LS94	13p	74LS474	100p	4113	45p	ICL7100	700p	TA7373	150p

COMPUTER COMPONENTS

GPUs		EF9365 £48		INTERFACE ICs & CRYSTALS	
1802CE	650p	MC6801	£65p	AD588CJ	75p
8008	£12	MC6802	£65p	AD588J	£20
8080	350p	MC6804	£65p	AM25510	350p
6502A	500p	SFF96364	£8	AM25512	£2
6800	225p	TMS9918	£60	AM26LS31	125p
6802	225p	TMS9917	£60	AM26LS32	125p
6809	650p	TMS9928	£38	COM8116	80p
6809E	£12	ZIF SOKETS		DAC80	£28
6809B	£12	(TEXT TOOL)		DM8131	275p
8035	350p	24 pin	£6	DP8304	250p
8039	£3	28 pin	£8	DS8830	140p
8085	450p	40 pin	£10	DS8831	140p
INS8060	£11	MEMORIES		DS8832	225p
TMS9980	£20	2101A	400p	DS8833	225p
Z8	£24	2102 L	120p	DS8836	150p
Z80	290p	2107B	500p	DS8838	225p
Z80A	320p	2111A	300p	FL13201	450p
Z80B	370p	2112-A	300p	MC1488	55p
8088	£18	2114-2L	100p	MC1489	55p
SUPPORT DEVICES		2147	450p	MC3418	950p
3242	800p	4027-3	300p	MC3446	300p
3245	2520p	4116-15	120p	MC3480	850p
6522	310p	4116-20	120p	MC3486	500p
6522A	550p	4118-3	500p	MC3487	300p
6532	550p	4118-4	450p	MC4044	250p
6551	800p	4164-2	500p	MC4411	675p
6821	100p	4816A-P-3	210p	MC4412	750p
6840	375p	5101	210p	ULN2003A	75p
6840A	650p	5516	800p	75107	90p
6850	110p	6116P-3	550p	7511012	90p
68850	220p	6514	120p	75114/15	160p
6852	250p	7489	180p	75121-22	140p
6857	375p	745189	325p	75150P	120p
6875	500p	745201	350p	75154	140p
8155	350p	745289	325p	75182	90p
8156	350p	93415	600p	7532-4	375p
8205	225p	93425	600p	75361	150p
8212	110p	ROMs/PROMs		75363	150p
8224	110p	745188	150p	75365	150p
8226	110p	745287	225p	75451-2	72p
8228	110p	745288	150p	75453/4	160p
8243	280p	745387	350p	8726	120p
8250	250p	74541	150p	8728	120p
8251	250p	74543/4	650p	8795/96	90p
8253	250p	745474	400p	8797/98	90p
8255	255p	745570	650p	81LS95	80p
8256	£36	745571	650p	81LS96	80p
8257	£4	745573	650p	81LS97	90p
8259	£4	745573	650p	9602	220p
8279	440p	EPROMs		9637AP	160p
8284	350p	2516 (-5V)	250p	ZN425E-8	350p
8288	100p	2532	375p	ZN426E-8	350p
Z80PIU	250p	2564	£12	ZN427E-8	650p
Z80CCT	250p	2708	250p	ZN428E-8	500p
Z80ACTC	250p	2716 (+5V)	250p	DISC CONTROL ICs	
Z80ADART	£7	2732	450p	FD1771	£20
Z80ADMA	£10	2716 (350ns)	500p	FD1791	£22
Z80SIO-0/1/2	£9	2732 (300ns)	500p	FD1793	£23
CRT CONTROLLER		TMS2716	750p	WD1795	£28
CRT6545	900p	UARTs		WD1797	£29
CRT5027	£18	AY-3 1015P	300p	WD1691	£15
CRT5037	£18	AY-5 1013P	300p	WD2143	550p
WIRE WRAP SOCKETS BY TEXAS		COM8017	300p	8271	£38
8 pin	25p	IM6402	450p	CHARACTER GENERATORS	
14 pin	35p	TR1602	300p	SN-3 2513ICP	750p
16 pin	40p	LOW PROFILE DIL SOCKETS BY TEXAS		SN742562AN	£1
8 pin	25p	40 pin	70p	MCM66760	750p
14 pin	35p	60 pin	80p	REAL TIME CLOCK	
16 pin	40p	80 pin	90p	MM58174	800p
20 pin	50p	100 pin	100p	MCM66760	750p
24 pin	55p	120 pin	110p	TRANSISTORS	
28 pin	60p	140 pin	120p	BRY39	40p
30 pin	65p	160 pin	130p	BSX19/20	24p
32 pin	70p	180 pin	140p	BU104	225p
36 pin	75p	200 pin	150p	BU108	150p
40 pin	80p	220 pin	160p	BU109	225p
44 pin	85p	240 pin	170p	BU125	150p
48 pin	90p	260 pin	180p	BU180A	120p
52 pin	95p	280 pin	190p	BU205	55p
56 pin	100p	300 pin	200p	BU208	55p
60 pin	105p	320 pin	210p	BU406	145p
64 pin	110p	340 pin	220p	XTX108	10p
68 pin	115p	360 pin	230p	XTX300	13p
72 pin	120p	380 pin	240p	XTX500	13p
76 pin	125p	400 pin	250p	XTX502	15p
80 pin	130p	420 pin	260p	XTX505	15p
84 pin	135p	440 pin	270p	XTX508	15p
88 pin	140p	460 pin	280p	XTX510	15p
92 pin	145p	480 pin	290p	XTX512	15p
96 pin	150p	500 pin	300p	XTX514	15p
100 pin	155p	520 pin	310p	XTX516	15p
104 pin	160p	540 pin	320p	XTX518	15p
108 pin	165p	560 pin	330p	XTX520	15p
112 pin	170p	580 pin	340p	XTX522	15p
116 pin	175p	600 pin	350p	XTX524	15p
120 pin	180p	620 pin	360p	XTX526	15p
124 pin	185p	640 pin	370p	XTX528	15p
128 pin	190p	660 pin	380p	XTX530	15p
132 pin	195p	680 pin	390p	XTX532	15p
136 pin	200p	700 pin	400p	XTX534	15p
140 pin	205p	720 pin	410p	XTX536	15p
144 pin	210p	740 pin	420p	XTX538	15p
148 pin	215p	760 pin	430p	XTX540	15p
152 pin	220p	780 pin	440p	XTX542	15p
156 pin	225p	800 pin	450p	XTX544	15p
160 pin	230p	820 pin	460p	XTX546	15p
164 pin	235p	840 pin	470p	XTX548	15p
168 pin	240p	860 pin	480p	XTX550	15p
172 pin	245p	880 pin	490p	XTX552	15p
176 pin	250p	900 pin	500p	XTX554	15p
180 pin	255p	920 pin	510p	XTX556	15p
184 pin	260p	940 pin	520p	XTX558	15p
188 pin	265p	960 pin	530p	XTX560	15p
192 pin	270p	980 pin	540p	XTX562	15p
196 pin	275p	1000 pin	550p	XTX564	15p
200 pin	280p	1020 pin	560p	XTX566	15p
204 pin	285p	1040 pin	570p	XTX568	15p
208 pin	290p	1060 pin	580p	XTX570	15p
212 pin	295p	1080 pin	590p	XTX572	15p
216 pin	300p	1100 pin	600p	XTX574	15p
220 pin	305p	1120 pin	610p	XTX576	15p
224 pin	310p	1140 pin	620p	XTX578	15p
228 pin	315p	1160 pin	630p	XTX580	15p
232 pin	320p	1180 pin	640p	XTX582	15p
236 pin	325p	1200 pin	650p	XTX584	15p
240 pin	330p	1220 pin	660p	XTX586	15p
244 pin	335p	1240 pin	670p	XTX588	15p
248 pin	340p	1260 pin	680p	XTX590	15p
252 pin	345p	1280 pin	690p	XTX592	15p
256 pin	350p	1300 pin	700p	XTX594	15p
260 pin	355p	1320 pin	710p	XTX596	15p
264 pin	360p	1340 pin	720p	XTX598	15p
268 pin	365p	1360 pin	730p	XTX600	15p
272 pin	370p	1380 pin	740p	XTX602	15p
276 pin	375p	1400 pin	750p	XTX604	15p
280 pin	380p	1420 pin	760p	XTX606	15p
284 pin	385p	1440 pin	770p	XTX608	15p
288 pin	390p	1460 pin	780p	XTX610	15p
292 pin	395p	1480 pin	790p	XTX612	15p
296 pin	400p	1500 pin	800p	XTX614	15p
300 pin	405p	1520 pin	810p	XTX616	15p
304 pin	410p	1540 pin	820p	XTX618	15p
308 pin	415p	1560 pin	830p	XTX620	15p
312 pin	420p	1580 pin	840p	XTX622	15p
316 pin	425p	1600 pin	850p	XTX624	15p
320 pin	430p	1620 pin	860p	XTX626	15p
324 pin	435p	1640 pin	870p	XTX628	15p
328 pin	440p	1660 pin	880p	XTX630	15p
332 pin	445p	1680 pin	890p	XTX632	15p
336 pin	450p	1700 pin	900p	XTX634	15p
340 pin	455p	1720 pin	910p	XTX636	15p
344 pin	460p	1740 pin	920p	XTX638	15p
348 pin	465p	1760 pin	930p	XTX640	15p
352 pin	470p	1780 pin	940p	XTX642	15p
356 pin	475p	1800 pin	950p	XTX644	15p
360 pin	480p	1820 pin	960p	XTX646	15p
364 pin	485p	1840 pin	970p	XTX648	15p
368 pin	490p	1860 pin	980p	XTX650	15p
372 pin	495p	1880 pin	990p	XTX652	15p
376 pin	500p	1900 pin	1000p	XTX654	15p
380 pin	505p	1920 pin	1010p	XTX656	15p
384 pin	510p	1940 pin	1020p	XTX658	15p
388 pin	515p	1960 pin	1030p	XTX660	15p
392 pin	520p	1980 pin	1040p	XTX662	15p
396 pin	525p	2000 pin	1050p	XTX664	15p
400 pin	530p	2020 pin	1060p	XTX666	15p
404 pin	535p	2040 pin	1070p	XTX668	15p
408 pin	540p	2060 pin	1080p	XTX670	15p
412 pin	545p	2080 pin	1090p	XTX672	15p
416 pin	550p	2100 pin	1100p	XTX674	15p
420 pin	555p	2120 pin	1110p	XTX676	15p
424 pin	560p	2140 pin	1120p	XTX678	15p
428 pin	565p	2160 pin	1130p	XTX680	15p
432 pin	570p	2180 pin	1140p	XTX682	15p
436 pin	575p	2200 pin	1150p	XTX684	15p
440 pin	580p	2220 pin	1160p	XTX686	15p
444 pin	585p	2240 pin	1170p	XTX688	15p
448 pin	590p	2260 pin	1180p	XTX690	15p
452 pin	595p	2280 pin	1190p	XTX692	15p
456 pin	600p	2300 pin	1200p	XTX694	15p
460 pin	605p	2320 pin	1210p	XTX696	15p
464 pin	610p	2340 pin	1220p	XTX698	15p
468 pin	615p	2360 pin	1230p	XTX700	15p
472 pin	620p	2380 pin	1240p	XTX702	15p
476 pin	625p	2400 pin	1250p	XTX704	15p
480 pin	630p	2420 pin	1260p	XTX706	15p
484 pin	635p	2440 pin	1270p	XTX708	15p
488 pin	640p	2460 pin	1280p	XTX710	15p
492 pin	645p	2480 pin	1290p	XTX712	15p
496 pin	650p	2500 pin	1300p	XTX714	15p
500 pin	655p	2520 pin	1310p	XTX716	15p
504 pin	660p	2540 pin	1320p	XTX718	15p
508 pin	665p	2560 pin	1330p	XTX720	15p
512 pin	670p	2580 pin	1340p	XTX722	15p
516 pin	675p	2600 pin	1350p	XTX724	15p
520 pin	680p	2620 pin	1360p	XTX726	15p
524 pin	685p	2640 pin	1370p	XTX728	15p
528 pin	690p	2660 pin	1380p	XTX730	15p
532 pin	695p	2680 pin	1390p	XTX732	15p
536 pin	700p	2700 pin	1400p	XTX734	15p
540 pin	705p	2720 pin	1410p	XTX736	15p
544 pin	710p	2740 pin	1420p	XTX738	15p
548 pin	715p	2760 pin	1430p	XTX740	15p
552 pin	720p	2780 pin	1440p	XTX742	15p
556 pin	725p	2800 pin	1450p	XTX744	15p
560 pin	730p	2820 pin	1460p	XTX746	15p
564 pin	735p	2840 pin	1470p	XTX748	15p
568 pin	740p	2860 pin	1480p	XTX750	15p
572 pin	745p	2880 pin	1490p	XTX752	15p
576 pin	750p	2900 pin	1500p	XTX754	



THE NEW MAPLIN CATALOGUE FOR 1983

BRINGS YOU
RIGHT UP-
TO-DATE IN
ELECTRONICS
& COMPUTING

Nearly 400 pages of all the most useful components and a whole big new section devoted to home computers and personal software. As always the catalogue keeps you up-to-date with the latest technology — even our ordinary miniature resistors are now superb quality 1% tolerance metal film, yet they're still only 2p each. As well as our usual quality products at low prices, now we're offering quantity discounts too. So pick up a copy of our catalogue now — it's the biggest *and* the best!

ON SALE IN ALL
BRANCHES OF WHSMITH
FROM 18th NOVEMBER 1982
PRICE £1.25

See us at the UK's new electronics exhibition — The Electronic Hobbies Fair — at the Alexandra Pavilion from 18th to 21st November. (Special bus from Alexandra Palace BR station and FREE car park in Alexandra Palace park!). The exhibition covers electronics, computing, amateur radio, CB, practical hi-fi and radio control modelling.

Post this coupon now for your copy of our 1983 catalogue, price £1.25 + 25p p&p. If you live outside the UK send £1.90 or 10 International Reply Coupons. I enclose £1.50.

Name

Address

Allow 14 days for delivery.

PE 11/82

MAPLIN
ELECTRONIC SUPPLIES LTD

P.O. Box 3, Rayleigh, Essex SS6 8LR.

Telephone: Southend (0702) 552911/554155

Shops at:

159-161 King Street, Hammersmith, London W6 Tel: (01) 748 0926

Lynton Square, Perry Barr, Birmingham. Telephone: (021) 356 7292

284 London Road, Westcliff-on-Sea, Essex. Tel: (0702) 554000

All shops closed Mondays