


PRACTICAL

Australia \$1.50 New Zealand \$1.60 Malaysia \$4.95 IR £1.23 (inc. VAT)


# ELECTRONICS

AUGUST 1983

85p

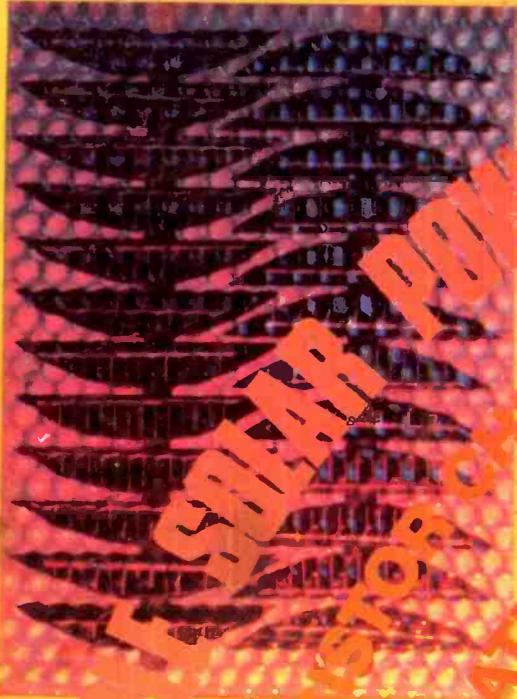

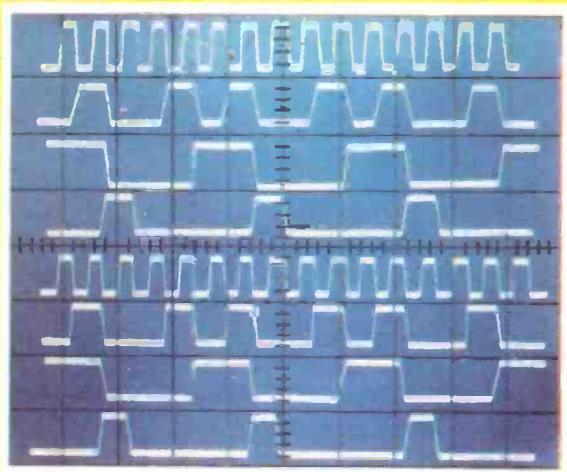**SIMPLY SOLAR POWERED PROJECTS....**  
**TRANSISTOR CHECKER: THERMOMETER**  
**SOIL MOISTURE DETECTOR: RADIO**  
**CONTINUITY TESTER**



**COMPUTER  
DIAGNOSIS  
LOGIC  
ANALYSER**  
Part One


**ROBOT VISION**

**Plus! Used Computer & Equipment Bargains**
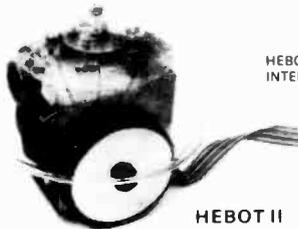
# Get moving with these new developments in UK Robotics

— advanced electrohydraulic designs for education, industry and now available to the home constructor.

Hebot II is a turtle-type robot which takes programming out of the two dimensional world of the VDU into the real three dimensional world. Given a DC supply of 9-15V it can perform a bewildering number of moves under computer control — forwards backwards left and right — with each wheel independently controlled. It has blinking eyes bleeps with a choice of two tones and has a solenoid operated pen to chart its progress. Touch sensors coupled to its shell return data about its environment to the computer for it to calculate evasive or exploratory action. Hebot II connects directly to an I/O port or alternatively with the universal interface board to the expansion bus of a ZX81 or other computer.



HEBOT KIT  
INTERFACE BOARD KIT  
£85.00  
£10.00

HEBOT II

Up to the nano-second hard, firm and software developments embodied in a complete system. 12 Mega Hertz 16 bit CPU; 64K upwardly compatible DRAM; separate 16K video DRAM and 24K T1 Power Basic with overwrite. Supports up to four Disc drives of mixed type with 16 serial I/O ports. Programmable Baud rate and comprehensive E Bus interface designed to support real world applications.

Very high resolution graphics gives 3D simulation in 16 colours on 36 prioritised planes of user definable characters. Software FORTH coming includes this trendy language along with NOS C/PM.

Hardware components available separately with details in Nov, Dec, and Jan issues of ETI. Software features include: Real time clock, full renumber command, buffered I/O to free machine whilst



£145.00  
£48.50  
£2.50  
£3.00

MICROGRASP, INTERFACE BOARD AND ZX81

printing, call to machine code routines, hexadecimal support and user-friendly textual error trapping messages.

If computers interest you then the Cortex will expand your understanding infinitely more than off the shelf machines. Use it in business, education, research or just play with the incredible graphics capability. At Powertran we are using these machines in conventional roles, in product control and R & D. We shall co-ordinate the Cortex user group and distribute software for the TMS 9995 CPU. Complete 16 bit 64K computer kit **£295.00 + VAT**. Complete 16 bit 64K computer ready built **£395.00 + VAT**



Top of the range is the Genesis P102 which has dual speed control, continuous servo operation and double acting cylinders for increased torque on the wrist and arm rotation joints. The microprocessor based control system has additional memory, position interrogation via the RS232C interface increasing the versatility of computer control and inputs are provided for machine tool interfacing.

6 axis system READY BUILT

£1950.00

#### Example prices and specifications

**Genesis S101**  
Base: 19.5" x 11" x 7.5"  
Lifting capacity: 1500gm  
Arm lift: 6.6"  
Weight: 29Kg

4 axis model in kit form £425  
5 axis model in kit form £475

**Genesis P101**  
Base: 19.5" x 11" x 7.5"  
Lifting capacity: 2000gm  
Arm lengths between axes: 14.0"  
Weight: 34Kg

6 axis model in kit form £675

Complete Systems as shown in Photograph on right


**Genesis S101**  
4 axis system in kit form £681.50  
5 axis system in kit form £737.50  
5 axis system Ready Built £1450

**Genesis P101**  
6 axis system in kit form £945.00  
6 axis system Ready Built £1650


All prices exclusive of VAT



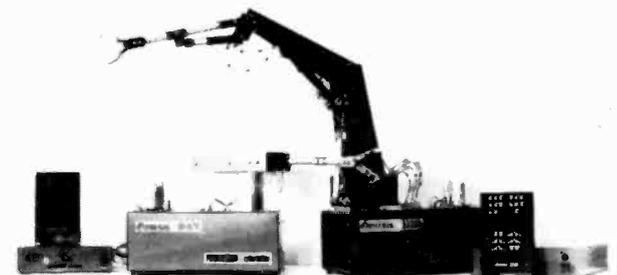GENESIS P102 PROCESSOR BOX AND HAND HELD CONTROLLER



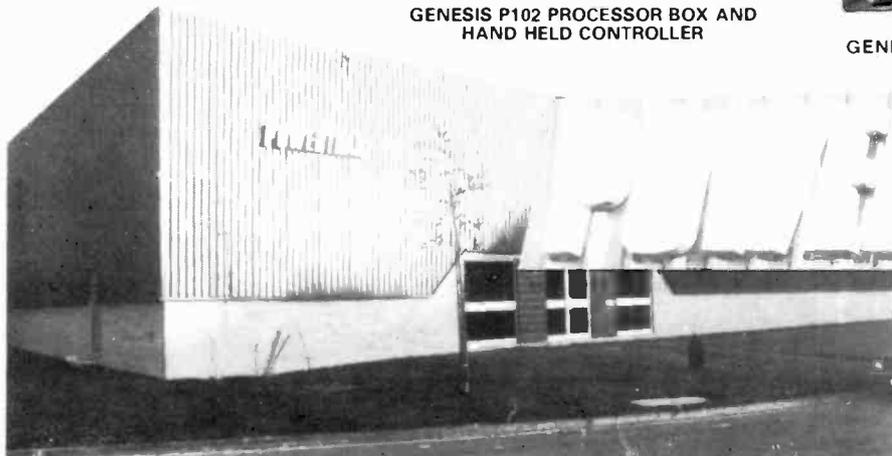GENESIS S101 AND GENESIS P101 WITH PROCESSOR BOXES AND HAND-HELD CONTROLLERS



WORLD LEADERS IN ELECTRONIC KIT DESIGN AND SUPPLY

(CYBERNETIC DIVISION)  
PORTWAY INDUSTRIAL ESTATE  
ANDOVER HANTS SP10 3WN  
Phone Enquiries (0264) 64455

Export enquiries to:-  
Powertran International, Hollom Down Farm,  
Lopcombe, Salisbury, Wilts. SP3 1BP.  
Tel: 0264 781545 Telex: 477407 ZENMON

# PRACTICAL ELECTRONICS

VOLUME 19

No. 8

AUGUST 1983

## CONSTRUCTIONAL PROJECTS

<b>SOLAR POWERED PROJECTS</b> by R. A. Penfold	22
M/W Radio	22
Soil Moisture Meter	25
Thermometer	26
Inebriation Detector	27
Continuity Tester	29
Transistor Checker	30
<b>LOGIC ANALYSER</b> by D. Mandelzweig	46
Stores 1K or 8-bit words at up to 5MHz	

## GENERAL FEATURES

<b>ROBOT VISION</b> by Geoff Mortimer and Liz Newbury	34
The latest systems explained	
<b>VERNON TRENT AT LARGE</b>	38
<b>SEMICONDUCTOR CIRCUITS</b> by Tom Gaskell BA (Hons)	40
Voltage converter (ICL 7660)	
<b>DEGLITCHING TECHNIQUES</b> by L. N. Owen	58
Defining and overcoming unwelcome transients	
<b>MICROPROMPT</b>	60
Hardware and software ideas for PE computer projects	

## NEWS AND COMMENT

<b>EDITORIAL</b>	15
<b>NEWS AND MARKET PLACE</b>	16
Including Countdown	
<b>SPECIAL OFFER-CASSETTES</b>	32
<b>SPACEWATCH</b> by Frank W. Hyde	33
Extra-terrestrial activities chronicled	
<b>BAZAAR</b>	42, 72
Free readers' advertisements	
<b>INDUSTRY NOTEBOOK</b> by Nexus	45
News and views on the electronics industry	
<b>PATENTS REVIEW</b>	57
Infra-red link—Stereo TV	
<b>STRICTLY INSTRUMENTAL</b> by K. Lenton-Smith	65
Yamaha pianos	
<b>READOUT</b>	66
<b>INGENUITY UNLIMITED</b>	67
Transistor analyser—Electronic die—Car lights on reminder—Micro multiplexed display	
Roger 'bleep bleep'—Steam whistle—Ni-Cad battery charger—High Z input for voltmeters	
<b>OVERSEAS SUBSCRIPTION AGENTS</b>	72

## SPECIAL SUPPLEMENT

<b>MICRO-FILE</b> by R. W. Coles	between pages 38 and 39
Filesheet 9 68000	

OUR SEPTEMBER ISSUE WILL BE ON SALE FRIDAY, AUGUST 5th, 1983  
(for details of contents see page 39)

© IPC Magazines Limited 1983. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

# WATFORD ELECTRONICS

33, CARDIFF ROAD, WATFORD, HERTS WD1 8ED, ENGLAND  
Tel. Watford (0923) 40588. Telex: 8956095 WAELEC

ALL DEVICES BRAND NEW FULL SPEC. AND FULLY GUARANTEED. SEND CASH P.O.'s OR CHEQUE WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS OFFICIAL ORDERS ACCEPTED (ACCESS ORDERS BY TEL. PHONE 0923-50234). TRADE AND EXPORT INQUIRY WELCOME. P & P ADD 50p TO ALL CASH ORDERS. OVERSEAS POSTAGE AT COST.

**VAT** Export orders no VAT. U.K. customers please add 15% VAT to total cost incl. p.p. We stock thousands more items. It pays to visit us. We are situated behind Watford Football Ground. Open Monday to Saturday, 9.00am to 6.00pm. Amped FREE Car parking.

**ALYXIN CAPACITORS:** (Axial Lead) 400V: 1nF, 1.5n, 2n2, 3n3, 4n7, 6n8 11p; 10n, 15n, 18n, 22n; 27n, 33n, 47n, 68n 16p; 100n, 150n 20p; 220n 30p; 330n 42p; 470n 52p; 680n 60p; 1µF 68p; 2µF, 4µF 75p. 1000V: 1nF 17p; 10nF 30p; 15n 40p; 22n 36p; 33n 42p; 47n, 100n 50p.

**POLYESTER RADIAL LEAD CAPACITORS:** 250V: 10n, 20n, 15n, 22n, 27n 6p; 33n, 47n, 68n, 100n 7p; 150n, 220n 10p; 330n, 470n 13p; 680n 19p; 1µ 23p; 1.5µ 40p; 2µ 46p.

**ELECTROLYTIC CAPACITORS** (Values in µF). 500V: 10µF 52p; 47 78p; 63V: 0.47, 1.0, 1.5, 2.2, 3.3, 8p; 4.7 9p; 10 10p; 15 12 22p; 33 15p; 47 12p; 68 16p; 100 19p; 220 26p; 1000 70p; 2200 99p; 50V: 68 20p; 100 17p; 220 24p; 400 68 15p; 22p; 33p; 330, 470 32p; 1000 48p; 2200 90p; 25V: 50p; 3000 76p; 4700 92p; 16V: 2.5, 4.0 8p; 47, 68, 100 9p; 125 12p; 220 13p; 330 16p; 470 20p; 680 34p; 1000 27p; 1500 31p; 2200 36p; 4700 79p.

**TAG-END TYPE:** 64V: 4700 246p; 3300 198p; 2700 139p; 50V: 3300 154p; 2200 110p; 40V: 4700 160p; 25V: 4700 98p; 10,000 320p; 15,000 345p.

**TANTALUM BEAD CAPACITORS:** 35V: 0.1µ, 0.22, 0.33 15p; 0.47, 0.68, 1.0, 1.5 16p; 2.2, 3.3 18p; 4.7, 6.8 22p; 10 28p; 16V: 2.2, 3.3 16p; 47, 6.8, 10 18p; 15 16p; 33p; 2.2 30p; 3.3, 47 40p; 100 75p; 220 88p; 10V: 1.5, 2.2 26p; 3.3, 47 35p; 100 55p.

**SILVER MICA (pf)** 2, 3.3, 4.7, 6.8, 8.2, 10, 12, 18, 22, 27, 33, 39, 47, 50, 56, 68, 75, 82, 85, 100, 120, 150, 180 15p each 220, 250, 270, 300, 360, 390, 470, 600, 800 & 820pf 21p each 1000, 1200, 1800 30p each 3000, 4700 60p each

**SIEMENS** multilayer miniature capacitors. 250V: 1nF, 1.5n, 2n2, 3n3, 4n7, 6n8, 8n2, 10n, 15n, 22n 7p; 18n, 27n, 33n, 47n 8p; 39n, 56n, 68n 9p. 100V: 100n, 120n, 10p; 150n 11p; 220n 13p; 330n 18p; 470n 23p; 680n 30p; 1µF 34p; 2µF 50p.

**CERAMIC Capacitors: 50V** Range 1nF to 6800pF 4p; 10nF, 15n, 10pF to 1nF 8p 33n, 47n 5p; 100n/30V 5p. **POLYSTYRENE Caps:** 1n5 to 1nF 10p

**RESISTORS S.I.L. Package:** 7 Commedon, 1000, 680K, 1K, 2K, 4K, 10K, 27K, 100K 24p 8 Commedon; (9 pins) 1501, 1801, 2701, 3301, 1K, 2K, 4K, 6K, 10K, 22K, 47K, 100K 26p.

**RESISTORS RANGE** Val 1-99 100+ 0.25W 202 4.7M E24 3p 1p 0.5W 202 4.7M E24 3p 1p 1W 202-10M E12 6p 4p 1µ Metal Film 5111-1M 8p 6p

**POTENTIOMETERS:** Carbon Track, 0.25W Log & Linear Values. 5001, 1K & 2K (LIN ONLY) Single 30p 5K1-2M1 Single gang D/P switch 78p 5K1-2M1 dual gang stereo 88p

**SLIDER POTENTIOMETERS** 0.25W Log and linear values 60mm track 5K1-500K Single gang 70p

**PRESET POTENTIOMETERS** 0.1W 501-2.2M Mini Vert. & Horiz. 7p 0.25W 100K-3.3M larger 10p 0.25W 250K-4.7M Vert. 10p

**RESISTORS** Hi-stab, Miniature, 5%, Carbon. 202 4.7M E24 3p 1p 0.5W 202 4.7M E24 3p 1p 1W 202-10M E12 6p 4p 1µ Metal Film 5111-1M 8p 6p

## TRANSISTORS

AC125/6	35	BC307/8	14	BFY64	35	TIP34C	88	2N1613	30	2SC1061	250
AC127/8	35	BC308B	15	BYV12	110	TIP35C	110	2N1718	110	2SC1066	85
AC147/2	35	BC309	15	BYV90	80	TIP36C	128	2N1760	295	2SC1162	30
AC176	28	BC337/8	15	BRX39	40	TIP36A	130	2N219A/20A	140	2SC1172	125
AC187/8	32	BC441	34	BSX20	20	TIP36C	140	21A/22A	25	2SC1173	125
AD142	120	BC461	34	BSX29	34	TIP41A	50	2N2369A	18	2SC1306	100
AD149	79	BC477/8	40	BU105	170	TIP41B	50	2N2646	48	2SC1307	150
AD161/2	42	BC516/7	40	BU107	190	TIP42A	55	2N2846	80	2SC1449	85
AF118	35	BC547/8	12	BU208	200	TIP42B	200	2N2934/05A	140	2SC1679	190
AF139	40	BC550	15	BU208	200	TIP42A	70	06A/07A	26	2SC1678	140
AF239	55	BC556/7	15	BU208	200	TIP21	73	2N2926G	10	2SC1923	50
BC107/8	10	BC558/9	15	MJ2955	70	TIP141	105	2N3053	26	2SC1945	225
BC107B	12	BCV70	16	MJ340	50	TIP142	105	2N3054	58	2SC1953	90
BC108B	12	BCV71/2	20	MJF102	70	TIP147	120	2N3095	48	2SC1957	90
BC108C	12	BD124	115	MJF103/4	30	TIS91/93	32	2N3098/9	10	2SC2314	85
BC109	12	BD131/2	48	MJF106	40	WV1010	80	2N3170	10	2SC2465	165
BC109B	12	BD133	60	MPSA05	25	VN101M	55	2N3771	179	2SC2574	35
BC109C	12	BD135/7	40	MPSA06	25	VN646F	78	2N3772	195	2SC2530	75
BC117/8	20	BD138/9	40	MPSA12	32	VN866F	94	2N3819	22	2SC2885	225
BC140/42	30	BD140	40	MPSA15	30	VN894F	96	2N3820	38	2SC2885	225
BC147/8	10	BD142	45	MPSA16	30	ZTX107/8	11	2N3866	90	2SC3128	110
BC147B	10	BD145	45	MPSA20	58	ZTX109	12	2N3866	90	2SC3128	110
BC148	10	BD148	45	MPSU05	55	ZTX121	28	2N3903/4	15	3N1410	112
BC149	9	BD159A	125	MPSU06	55	ZTX300	13	2N3906/5	15	40097	122
BC149C	12	BD695A	125	MPSU05	55	ZTX301/2	16	2N4069	45	40101	215
BC153/4	27	BD696A	125	MPSU55	60	ZTX303	25	2N4427	80	40100	130
BC157/8	10	BF180	38	MPSU56	60	ZTX304	17	2N4429	75	40100	95
BC159	11	BF194/5	12	MPS26	30	OC23	170	ZTX30/26	30	2N4871	55
BC167A	78	BF195/8	12	MPS28	36	BF224	25	OC23	170	2N4871	55
BC168C	10	BF200	20	MPS29	36	OC44	75	ZTX500/1	14	2N5179	45
BC169C	10	BF224	25	MPS30	36	OC44	75	ZTX502/3	18	2N5179	45
BC170	15	BF244A	28	MPS31	36	OC70	40	ZTX500/1	14	2N5179	45
BC171/2	11	BF244B	28	MPS32	36	OC70	40	ZTX500/2	18	2N5179	45
BC173	11	BF256B	35	MPS33	36	OC70	40	ZTX500/3	18	2N5179	45
BC177/8	16	BF257/8	35	MPS34	36	OC70	40	ZTX500/4	18	2N5179	45
BC179/81	20	BF259	35	MPS35	36	OC70	40	ZTX500/5	18	2N5179	45
BC182/3	10	BF336	40	MPS36	36	OC70	40	ZTX500/6	18	2N5179	45
BC183L	10	BF349/40	23	MPS37	36	OC70	40	ZTX500/7	18	2N5179	45
BC184L	10	BF380/81	25	MPS38	36	OC70	40	ZTX500/8	18	2N5179	45
BC191/2	10	BF400	28	MPS39	36	OC70	40	ZTX500/9	18	2N5179	45
BC212/3	10	BF429/28A	28	MPS40	36	OC70	40	ZTX500/10	18	2N5179	45
BC212L	10	BF485/86	28	MPS41	36	OC70	40	ZTX500/11	18	2N5179	45
BC213L	10	BF487/88	28	MPS42	36	OC70	40	ZTX500/12	18	2N5179	45
BC214	10	BF505/51	23	MPS43	36	OC70	40	ZTX500/13	18	2N5179	45
BC214L	10	BF552	23	MPS44	36	OC70	40	ZTX500/14	18	2N5179	45
BC237/8	14	BFV56	32	MPS45	36	OC70	40	ZTX500/15	18	2N5179	45

## LINEAR IC's

LM311	55	SAB3271	495	8251A	250	Z80DART	435	74142	175	LS191	36	4013	20	4440	999
LM318	150	SA8209	595	8252A	450	Z80ADART	850	74143	210	LS192	36	4014	46	4450	350
LM319	195	SG3402	295	8253	300	Z80ADMA	850	74144	210	LS193	37	4015	40	4451	350
LM324	30	SL490	350	8254	590	Z80ADMA	675	74145	50	LS194	33	4016	20	4490	350
LM334Z	90	SL6270	150	8256A	430	Z80AP10	275	74147	75	LS195	33	4017	32	4500	675
LM339	128	SN76013N	350	8257	325	Z80AP10	275	74148	80	LS196	45	4018	45	4510	28
LM339	47	SN76023N	350	8258	200	Z80AP10	275	74149	80	LS197	21	4019	25	4502	60
LM348	60	SN76033	350	8259	865	Z80AS10	90	74151	40	LS201	55	4020	42	4503	35
LM349	115	SN76477	420	8260	450	Z80AS10	90	74152	40	LS202	55	4021	40	4504	75
LM358	80	SN76488	480	8261	8283	Z80AS10	90	74153	40	LS203	55	4022	40	4505	185
LM358	175	SN76488	480	8262	450	Z80AS10	90	74154	40	LS204	55	4023	13	4506	35
LM358	175	SN76488	480	8263	450	Z80AS10	90	74155	40	LS205	55	4024	13	4507	35
LM358	175	SN76488	480	8264	450	Z80AS10	90	74156	40	LS206	55	4025	13	4508	35
LM358	175	SN76488	480	8265	450	Z80AS10	90	74157	40	LS207	55	4026	13	4509	35
LM358	175	SN76488	480	8266	450	Z80AS10	90	74158	40	LS208	55	4027	13	4510	35
LM358	175	SN76488	480	8267	450	Z80AS10	90	74159	40	LS209	55	4028	13	4511	35
LM358	175	SN76488	480	8268	450	Z80AS10	90	74160	40	LS210	55	4029	13	4512	35
LM358	175	SN76488	480	8269	450	Z80AS10	90	74161	40	LS211	55	4030	13	4513	35
LM358	175	SN76488	480	8270	450	Z80AS10	90	74162	40	LS212	55	4031	13	4514	35
LM358	175	SN76488	480	8271	450	Z80AS10	90	74163	40	LS213	55	4032	13	4515	35
LM358	175	SN76488	480	8272	450	Z80AS10	90	74164	40	LS214	55	4033	13	4516	35
LM358	175	SN76488	480	8273	450	Z80AS10	90	74165	40	LS215	55	4034	13	4517	35
LM358	175	SN76488	480	8274	450	Z80AS10	90	74166	40	LS216	55	4035	13	4518	35
LM358	175	SN76488	480	8275	450	Z80AS10	90	74167	40	LS217	55	4036	13	4519	35
LM358	175	SN76488	480	8276	450	Z80AS10	90	74168	40	LS218	55	4037	13	4520	35
LM358	175	SN76488	480	8277	450	Z80AS10	90	74169	40	LS219	55	4038	13	4521	35
LM358	175	SN76488	480	8278	450	Z80AS10	90	74170	40	LS220	55	4039	13	4522	35
LM358	175	SN76488	480	8279	450	Z80AS10	90	74171	40	LS221	55	4040	13	4523	35
LM358	175	SN76488	480	8280	450	Z80AS10	90	74172	40	LS222	55	4041	13	4524	35</



# FREE CAREER BOOKLET

**Train for success in Electronics Engineering, T.V. Servicing, Electrical Engineering—or running your own business!**

ICS have helped thousands of ambitious people to move up into higher paid, more secure jobs in the fields of electronics, T.V., electrical engineering—now it can be your turn. Whether you are a newcomer to the field or already working in these industries, ICS can provide you with the specialised training so essential to success.

### Personal Tuition and 80 Years of Success

The expert and personal guidance by fully qualified tutors, backed by the long ICS record of success, is the key to our outstanding performance in the technical field. You study at the time and pace that suits you best and in your own home.

You study the subjects you enjoy, receive a formal Diploma, and you're ready for that better job, better pay.

**TICK THE FREE BOOKLET YOU WANT AND POST TODAY**

#### ELECTRONICS ENGINEERING

A Diploma Course, recognised by the Institute of Engineers & Technicians as meeting all academic standards for application as an Associate.

#### T.V. & AUDIO SERVICING

A Diploma Course, training you in all aspects of installing, maintaining and repairing T.V. and Audio equipment, domestic and industrial.

#### ELECTRICAL ENGINEERING

A further Diploma Course recognised by the Institute of Engineers & Technicians, also covering business aspects of electrical contracting.

#### RUNNING YOUR OWN BUSINESS

If running your own electronics, T.V. servicing or electrical business appeals, then this Diploma Course trains you in the vital business knowledge and techniques you'll need.

Name .....

Address .....

**ICS**

ICS  
Dept K627  
160 Stewarts Road,  
London SW8 4UJ



01-622 9911  
(all hours)

## JUST OUT!

### OUR GREAT NEW CATALOGUE

Presented with a Professional Approach and Appeal to ALL who require Quality Electronic Components, Semiconductors and other Accessories ALL at realistic prices.

There are no wasted pages of useless information so often included in Catalogues published nowadays. Just solid facts i.e. price, description and individual features of what we have available. But remember, BI-PAK's policy has always been to sell quality components at competitive prices and THAT WE STILL DO.



We hold vast Stocks "in stock" for fast immediate delivery, all items in our Catalogue are available ex stock.

The Catalogue is designed for use with our 24 hours "ansaphone" service and the Visa/Access credit cards, which we accept over the telephone.

To receive your NEW 1983 BI-PAK Catalogue, send 75p PLUS 25p p&p to:-

**BI-PAK**

Dept PE8  
(Catalogues) PO Box 6  
WARE, Herts. SG12 9AD



Access & VISA accepted  
Ring 0920 3182 for  
immediate despatch

## MAIL ORDER ADVERTISING

### British Code of Advertising Practice

Advertisements in this publication are required to conform to the British Code of Advertising Practice. In respect of mail order advertisements where money is paid in advance, the code requires advertisers to fulfil orders within 28 days, unless a longer delivery period is stated. Where goods are returned undamaged within seven days, the purchaser's money must be refunded. Please retain proof of postage/despatch, as this may be needed.

### Mail Order Protection Scheme

If you order goods from Mail Order advertisements in this magazine and pay by post in advance of delivery, PRACTICAL ELECTRONICS will consider you for compensation if the Advertiser should become insolvent or bankrupt, provided:


- (1) You have not received the goods or had your money returned; and
- (2) You write to the Publisher of PRACTICAL ELECTRONICS summarising the situation not earlier than 28 days from the day you sent your order and not later than two months from that day.

Please do not wait until the last moment to inform us. When you write, we will tell you how to make your claim and what evidence of payment is required.

We guarantee to meet claims from readers made in accordance with the above procedure as soon as possible after the Advertiser has been declared bankrupt or insolvent.

This guarantee covers only advance payment sent in direct response to an advertisement in this magazine not, for example payment made in response to catalogues etc, received as a result of answering such advertisements. Classified advertisements are excluded.

## WHAT USE A MICRO WITHOUT A PRINTER?

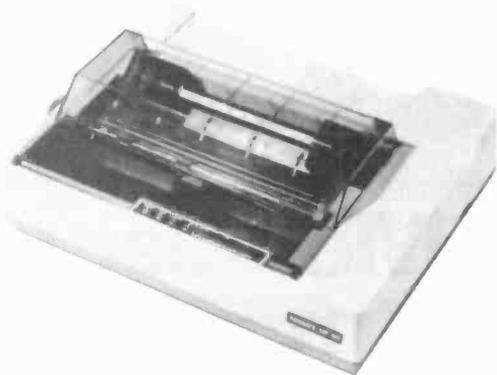

NEW A.D.M. 80 COL. DOT MATRIX WITH TRACTOR FEED. BACKED BY ONE OF BRITAIN'S LARGEST MANUFACTURERS, IT IS NOW STOCKED BY US.

### SPECIAL LAUNCH PRICE

£311.00 + VAT. Carriage £7.50 or collect from our warehouse.

## CROFTON ELECTRONICS LTD.

35 GROSVENOR ROAD, TWICKENHAM, MIDDX 01-891 1923/1513 Telex 295093

### ORIC AND SINCLAIR COMPUTERS



Oric 1 48K computer £147 (£150). Oric 1 16K n/a (n/a). Sinclair Spectrum 48K £113 (£133). Spectrum 16K £84.91 (£107). 32K memory upgrade kit for 16K Spectrum (Issue 2 only) £26.99 (£28). Fuller master unit for the Spectrum including speech synthesizer, sound synthesizer, amplifier and joystick ports £47.78 (£56). ZX microdrive n/a (n/a). ZX rs232 n/a (n/a). Keyboards with space bars for the ZX81 and the Spectrum £36 (£41). ZX printer £34.74 (£50). 5 printer rolls £10.43 (£16). ZX81 £43.43 (£52). ZX81 16K ram packs £26.04 (£28). New luxury spectrum computers 48K with full sized typewriter keyboards complete with normal space bar enclosed in a larger plastic case which also houses the power supply and the computer pcb £138.20 (£174).


### COMMODORE COMPUTERS

Commodore 64 £299 (£309). Vic 20 £130 (£140). Special offer package: Vic 20 + cassette recorder + basic course + 4 games £139 (£149). Converter to allow the use of most ordinary mono cassette recorders with the Vic 20 and the Commodore 64 built £8 (£9), kit £6 (£7). Commodore cassette recorder £36.50 (£44). We stock most accessories.

### OTHER COMPUTERS

Colour Genie £168 (£178). BBC Model B £424 (£440). Texas T199/4A £139 (£169). Atari 800 £347 (£380). Atari 400 16K with basic £173 (£215).

### PRINTERS

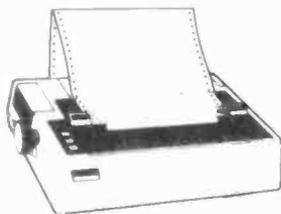

The Epson MX80FT/3 has been replaced by the almost identical CTI CP80 £262 (£282) and the very similar Star DPS10 £262 (£282). Epson FX80 £378 (£408). Epson MX100/3 £425 (£465). New Star DP515 15" carriage printer £374 (£414). Seikosa GP100A £199 (£219). Oku Microline 80 £287 (£227). Oku Microline 82A £360 (£408). Oku Microline 84 £730. Oku Microline 92 £470. The Bytewriter, the latest miracle, a combined daisy wheel printer and electric typewriter for only £418 (£448). We can supply interfaces to run any of the above printers from Sharp computers.

### SWANLEY ELECTRONICS

Dept PE, 32 Goldsiel Rd., Swanley, Kent BR8 8EZ, England.

Please allow 7 days for delivery.

UK prices are shown first. UK customers must add postage (£1 on Sinclair products, £3.50 on other computers and disc drives and £4.50 on other printers) and the 15% VAT. The bracketed prices are European export prices and include insured airmail postage to all the countries of Europe including Norway, Sweden, Finland, Denmark, Spain and Italy. No VAT should be added to export prices. We are the leading computer export specialist. Official UK credit orders welcome from government laboratories and educational establishments.

hi? performance hi? competitive hi?

MORE <sup>people are buying</sup> TRIO

\*\*\* FOR \*\*\*

## MORE DISPLAY

nearly 50% more with the NEW LARGE 6 inch rectangular CRT with illuminated inner face graticule, 6KV accelerator voltage for a brighter, higher resolution display with guaranteed accuracy.

\*\*\*


## MORE SENSITIVITY

1 milli Volt per cm in the vertical axis, valuable for observing complex low level waveforms especially with 20 nano sec per cm Sweep Speed.

\*\*\*
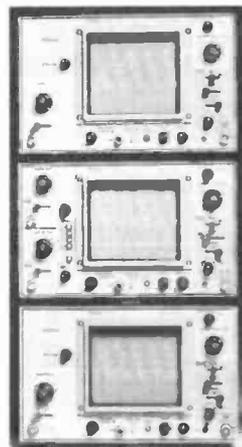
## MORE FACILITIES

like push-button MODES inc. Add, Sub, Alt and Chop - V mode trigger SOURCE - NEW super video sync - Front panel control of Astig, Trace rotation, Scale illum and X-Y - Chan I O/P, Int. Mod etc, etc.



NEW

20 MHz 1mV/cm  
CS 1022 Dual Trace  
CS 1020 Single Trace

NEW

10 MHz 1mV/cm  
CS 1012 Dual Trace  
CS 1010 Single Trace



AT REAL VALUE FOR MONEY PRICES

\*\*\*

Fully Guaranteed for 2 years inc.

Free 'pick up' and 'return'



In a hurry? Then ring (0799) 24922

House of Instruments, Clifton Chambers, 62 High Street, Saffron Walden, Essex CB10 1EE. Telephone: (0799) 24922 Telex: B18750

Ask for FREE DATA


# TRIO

hi? competitive hi?

# hi!


House of Instruments Ltd.

# GET BIG POWER

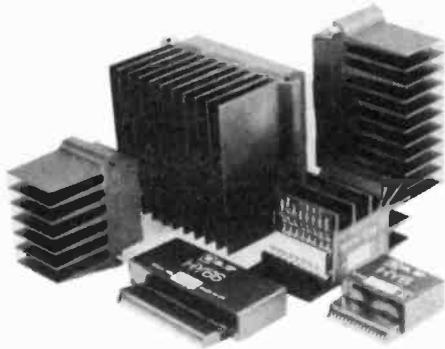
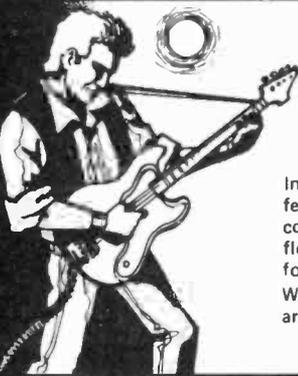
## Modular Amplifiers the third generation

Due to continuous improvements in components and design ILP now launch the largest and most advanced generation of modules ever.



## WE'RE INSTRUMENTAL IN MAKING A LOT OF POWER

In keeping with ILP's tradition of entirely self-contained modules featuring, integral heatsinks, no external components and only 5 connections required, the range has been optimized for efficiency, flexibility, reliability, easy usage, outstanding performance, value for money.

With over 10 years experience in audio amplifier technology ILP are recognised as world leaders.



### BIPOLAR MODULES

Module Number	Output Power Watts rms	Load Impedance $\Omega$	DISTORTION		Supply Voltage Typ	Size mm	WT gms	Price inc. VAT
			T.H.D. Typ at 1KHz	I.M.D. 60Hz/7KHz 4:1				
HY30	15	4-8	0.015%	<0.006%	$\pm 18$	76 x 68 x 40	240	£8.40
HY60	30	4-8	0.015%	<0.006%	$\pm 25$	76 x 68 x 40	240	£9.55
HY6060	30 + 30	4-8	0.015%	<0.006%	$\pm 25$	120 x 78 x 40	420	£18.89
HY124	60	4	0.01%	<0.006%	$\pm 26$	120 x 78 x 40	410	£20.75
HY128	60	8	0.01%	<0.006%	$\pm 35$	120 x 78 x 40	410	£20.75
HY244	120	4	0.01%	<0.006%	$\pm 35$	120 x 78 x 50	520	£25.47
HY248	120	8	0.01%	<0.006%	$\pm 50$	120 x 78 x 50	520	£25.47
HY364	180	4	0.01%	<0.006%	$\pm 45$	120 x 78 x 100	1030	£38.41
HY368	180	8	0.01%	<0.006%	$\pm 60$	120 x 78 x 100	1030	£38.41

Protection: Full load line. Slew Rate: 15v/ $\mu$ s. Rise time: 5 $\mu$ s. S/N ratio: 100db. Frequency response (-3dB) 15Hz - 50KHz. Input sensitivity: 500mV rms. Input Impedance: 100K  $\Omega$ . Damping factor: 100Hz >400.

### PRE-AMP SYSTEMS

Module Number	Module	Functions	Current Required	Price inc. VAT
HY6	Mono pre-amp	Mic/Mag. Cartridge/Tuner/Tape/Aux + Vol/Bass/Treble	10mA	£7.60
HY66	Stereo pre-amp	Mic/Mag. Cartridge/Tuner/Tape/Aux + Vol/Bass/Treble/Balance	20mA	£14.32
HY73	Guitar pre-amp	Two Guitar (Bass Lead) and Mic + separate Volume/Bass/Treble + Mix	20mA	£15.36
HY78	Stereo pre-amp	As HY66 less tone controls	20mA	£14.20

Most pre-amp modules can be driven by the PSU driving the main power amp. A separate PSU 30 is available purely for pre-amp modules if required for £5.47 (inc. VAT). Pre-amp and mixing modules in 18 different variations. Please send for details.

### Mounting Boards

For ease of construction we recommend the B6 for modules HY6-HY13 £1.05 (inc. VAT) and the B66 for modules HY66-HY78 £1.29 (inc. VAT).

### POWER SUPPLY UNITS (Incorporating our own toroidal transformers)

Model Number	For Use With	Price inc. VAT	Model Number	For Use With	Price inc. VAT
PSU 21X	1 or 2 HY30	£11.93	PSU 52X	2 x HY124	£17.07
PSU 41X	1 or 2 HY60, 1 x HY6060, 1 x HY124	£13.83	PSU 53X	2 x MOS128	£17.86
PSU 42X	1 x HY128	£15.90	PSU 54X	1 x HY248	£17.86
PSU 43X	1 x MOS128	£16.70	PSU 55X	1 x MOS248	£19.52
PSU 51X	2 x HY128, 1 x HY244	£17.07	PSU 71X	2 x HY244	£21.75

Please note: X in part no. indicates primary voltage. Please insert "0" in place of X for 110V, "1" in place of X for 220V, and "2" in place of X for 240V.

### MOSFET MODULES

Module Number	Output Power Watts rms	Load Impedance $\Omega$	DISTORTION		Supply Voltage Typ	Size mm	WT gms	Price inc. VAT
			T.H.D. Typ at 1KHz	I.M.D. 60Hz/7KHz 4:1				
MOS 128	60	4-8	<0.005%	<0.006%	$\pm 45$	120 x 78 x 40	420	£10.21
MOS 248	120	4-8	<0.005%	<0.006%	$\pm 55$	120 x 78 x 80	850	£19.86
MOS 364	180	4	<0.005%	<0.006%	$\pm 55$	120 x 78 x 100	1025	£45.54

Protection: Able to cope with complex loads without the need for very special protection circuitry (fuses will suffice).

Slew rate: 20v/ $\mu$ s. Rise time: 3 $\mu$ s. S/N ratio: 100db

Frequency response (-3dB): 15Hz - 100KHz. Input sensitivity: 500mV rms

Input impedance: 100K  $\Omega$ . Damping factor: 100Hz >400.

### 'NEW to ILP' In Car Entertainments

#### C15

Mono Power Booster Amplifier: to increase the output of your existing car radio or cassette player to a nominal 15 watts rms.

Very easy to use.

Robust construction.

£9.14 (inc. VAT)

Mounts anywhere in car.

Automatic switch on.

Output power: maximum 22w peak into 4 $\Omega$ .

Frequency response (-3dB) 15Hz to 30KHz. T.H.D. 0.1% at 10w 1KHz

S/N ratio (DIN AUDIO) 50dB. Load Impedance 3 $\Omega$ .

Input Sensitivity and impedance: (see table) 700mV rms into 15K  $\Omega$ . 3V rms into 8  $\Omega$ .

Size 95 x 48 x 50mm. Weight 256 gms.

#### C1515

Stereo version of C15.

£17.19 (inc. VAT)

Size 95 x 40 x 80. Weight 410 gms.

Model Number	For Use With	Price inc. VAT
PSU 72X	2 x HY248	£22.54
PSU 73X	1 x HY364	£22.54
PSU 74X	1 x HY368	£24.20
PSU 75X	2 x MOS248, 1 x MOS368	£24.20

# WITH A LOT OF HELP FROM





## PROFESSIONAL HI-FI THAT EVERY ENTHUSIAST CAN HANDLE...

### Unicase

Over the years ILP has been aware of the need for a complete packaging system for its products, it has now developed a unique system which meets all the requirements for ease of assembly, adaptability, ruggedness, modern styling and above all price.

Each Unicase kit contains all the hardware required down to the last nut and bolt to build a complete unit without the need for any special tools.

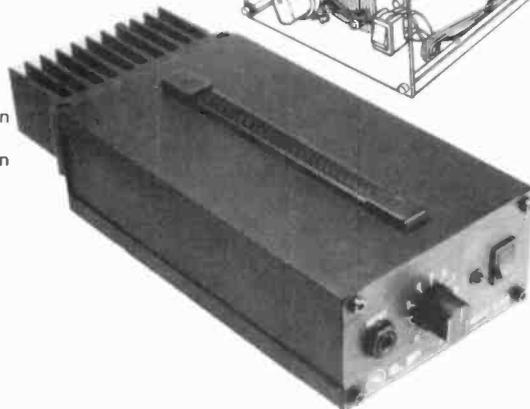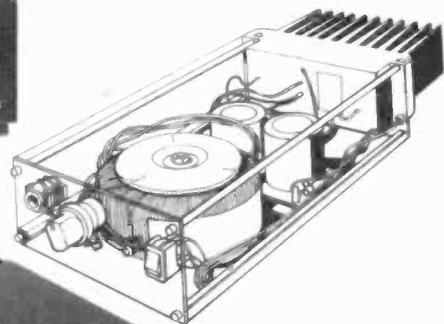Because of ILP's modular approach, "open plan" construction is used and final assembly of the unit parts forms a compact aesthetic unit. By this method construction can be achieved in under two hours with little experience of electronic wiring and mechanical assembly.



### Hi Fi Separates

**UC1 PRE AMP UNIT:** Incorporates the HY78 to provide a "no frills", low distortion, (<0.01%), stereo control unit, providing inputs for magnetic cartridge, tuner, and tape/monitor facilities. This unit provides the heart of the hi fi system and can be used in conjunction with any of the UP Unicase series of power amps. For ultimate hum rejection the UC1 draws its power from the power amp unit.

**POWER AMPS:** The UP series feature a clean line front panel incorporating on/off switch and concealed indicator. They are designed to compliment the style of the UC1 pre-amp. Performance for each unit which includes the appropriate power supply, is as specified on the facing page.



### Power Slaves

Our power slaves, which have numerous uses i.e. instrument, discotheque, sound reinforcement, feature in addition to the hi fi series, front panel input jack, level control, and a carrying handle. Providing the smallest, lowest cost, slave on the market in this format.

#### UNICASES

HiFi Separates					Price Inc. VAT
UC1	Preamp				£29.95
UP1X	30 + 30W/4-8Ω	Bipolar	Stereo	HiFi	£54.95
UP2X	60W/4Ω	Bipolar	Mono	HiFi	£54.95
UP3X	60W/8Ω	Bipolar	Mono	HiFi	£54.95
UP4X	120W/4Ω	Bipolar	Mono	HiFi	£74.95
UP5X	120W/8Ω	Bipolar	Mono	HiFi	£74.95
UP6X	60W/4-8Ω	MOS	Mono	HiFi	£64.95
UP7X	120W/4-8Ω	MOS	Mono	HiFi	£84.95
Power Slaves					
US1X	60W/4Ω	Bipolar	Power	Slave	£59.95
US2X	120W/4Ω	Bipolar	Power	Slave	£79.95
US3X	60W/4-8Ω	MOS	Power	Slave	£69.95
US4X	120W/4-8Ω	MOS	Power	Slave	£89.95

Please note X in part number denotes mains voltage. Please insert '0' in place of X for 110V, '1' in place of X for 220V (Europe), and '2' in place of X for 240V (U.K.) All units except UC1 incorporate our own toroidal transformers.

#### TO ORDER USING OUR FREEPOST FACILITY

Fill in the coupon as shown, or write details on a separate sheet of paper, quoting the name and date of this journal. By sending your order to our address as shown at the bottom of the page opposite, with FREEPOST clearly shown on the envelope, you need not stamp it. We pay postage for you. Cheques and money orders must be crossed and made payable to ILP Electronics Ltd. if sending cash, it must be by registered post. To pay C.O.D. please add £1 to TOTAL value of order.

**PAYMENT MAY BE MADE BY ACCESS OR BARCLAYCARD IF REQUIRED. Allow 28 days for delivery.**



Post to: ILP Electronics Ltd, Freepost 2, Graham Bell House, Roper Close, Canterbury, CT2 7EP, Kent, England. Telephone (0227) 54778. Technical (0227) 64723. Telex 965780.

Please send me the following \_\_\_\_\_

Total purchase price \_\_\_\_\_

I enclose Cheque  Postal Orders  Int. Money Order

Please debit my Access/Barclaycard No. \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

Signature \_\_\_\_\_

CALL IN AND SEE FOR YOURSELF

# AUDIO ELECTRONICS

ALL PRICES INCLUDE VAT

TEST EQUIPMENT CENTRES ALL MODELS ON DISPLAY OPEN SIX DAYS A WEEK

RETAIL • MAIL ORDER • EXPORT • INDUSTRIAL • EDUCATIONAL

## DIGITAL MULTIMETERS (UK C/P Free)



ALL MODELS 3 1/2 DIGIT UNLESS STATED



<b>HAND HELD</b>	With free carry case	Beckman T110 As T100 plus Cont. test. etc.	£67.85
KD25C=13 range 0.2A DC 2 meg ohm	£24.95	Sifam 2200B 21 range 2A AC/DC 20 meg ohm	£39.95
KD30S=16 range 10A DC 2 meg ohm	£29.95		
KD30C=26 range 1A AC/DC 20 meg ohm	£34.95		
KD55C=28 range 10A AC/DC 20 meg ohm	£39.95		
601D+ As 601D but 0.1% basic	£34.40		
703D+ As 601D but 0.1% basic	£41.30		
KD615ml6 range 10A DC 2 meg plus Hfe tester	£39.95		
189M 30 range 10A AC/DC 20 meg plus Hfe tester	£69.95		
HD30 16 range 0.2A AC/DC 2 meg ohm	£41.95		
HD30/B As above plus cont. buzzer	£44.50		
HD31 22 range 10 AC/DC 2 meg ohms plus cont. buzzer	£58.95		
DM2350 = 21 range 10A AC/DC 20 meg ohm miniature hand held auto range	£49.95		
Beckman T100 34 range 10A AC/DC 20 meg ohm	£56.35		

## FREQUENCY COUNTERS



<b>PFM200A</b> MHz hand held pocket 8 digit LED	£77.60
8110A 8 digit LED bench 2 ranges 100 MHz	£77.00
8610B 9 digit LED bench 2 ranges 600 MHz	£113.85
8000B 9 digit LED 3 ranges 1 GHz	£178.00
TF40 = 8 digit LCD 40 MHz	£126.50
TF200 = 8 digit LCD 200 MHz	£166.75
Optional carry case £6.84	
Prescalers - Extended range of most counters	
TP600 600 MHz	£43.00
TP1000 1 GHz	£74.00

## SIGNAL GENERATORS (220/240V AC)

<b>FUNCTION</b> : All sine/square/triangle/TTL etc	TG 100 1 MHz - 100 KHz	£90.00
	TG 102 0.2 Hz - 2 MHz	£166.75
<b>PULSE</b>		
	TG 105 Various facilities 5 Hz - 5 MHz	£97.75
<b>AUDIO</b> : Multiband Sine/Square		
	LAG27 10 Hz to 1 MHz	£90.85
	AG202A 20 Hz to 200 KHz (List £94.50)	£83.50
<b>RF</b>		
	SG402 100 KHz to 30 MHz (List £79.50)	£69.50
	LSG17 100 KHz to 150 MHz	£79.35

## ELECTRONIC INSULATION TESTER

YF 501 500 V/0-100M with carry case	£63.00
-------------------------------------	--------

## MULTIMETERS (UK C/P 65p)

HM102 220K/V 10A DC 22 range & cont. buzzer	£13.50
HM102Z 20 K/V 22 range & cont buzzer	£14.95
ETC5000/5001 21 ranges 50K/V Range doubler 10A DC	£18.95
TMK500 23 ranges 30K/V 12A DC plus cont. buzzer	£24.75
NM56R 20K/V 22 range pocket	£10.95
ETU 102 14 range 2K/V pocket	£6.50
830A 26 range 30K/V 10A AC/DC overload protection, etc.	£23.95
360TR 23 range 100K/V Large scale 10A AC/DC plus Hfe	£39.95
AT 1020 18 range 20K/V Deluxe plus Hfe tester	£18.95
YM 360TR 19 range 20K/V plus Hfe tester	£15.95
Matrix Professional multimeters In stock 3 models from	£74.75

## VARIABLE POWER SUPPLIES (UK C/P £1.00)

PP24V 0/12/24V 0/1A	£35.00
PP243 3 amp version	£59.95
PS 1307S 8/15V 7 amp twin meter	£24.95

## DIGITAL THERMOMETER

TM301 LCD -50°C to +75°C with thermocouple	£68.43
--	--------

## AC CLAMP METER

ST300 0/300A 0/600 VAC 0/1 Kohm 9 ranges With carry case (UK C/P 65p)	£28.50
---	--------

## LOGIC PROBES

LP10 10 MHz	£28.50
DLPS0 50 MHz with carry case and accessories	£52.33

## OSCILLOSCOPES



Full specification any model on request. SAE by post.

**'HM' Series HAMEG: 'SC' THANOR:**  
**CS' TRIO: '3' CROTECH 'DT' Salgan**

**SINGLE TRACE (UK C/P £3.00)**

3030 15 MHz 5mV 95mm tube plus component tester C/P £3.00	£177.10
SC110A Miniature 10 MHz battery portable	£171.00
Post free	
HM103 15 MHz 2mV 6 x 7 display plus component tester C/P £3.00	£181.70
Optional carry case £6.84 AC adaptor £6.69	
Nicads £12.50	
<b>DUAL TRACE (UK C/P £4.00)</b>	
DT 520 Dual 20 MHz	£241.50
NM203/4 Dual 20 MHz plus component tester	£287.50
CS1562A Dual 10 MHz (List £321.00)	£269.50
3131 Dual 15 MHz + component tester	£276.00
CS1566A Dual 20 MHz All facilities (List £401.35)	£349.50
HM204 Dual 20 MHz plus component tester sweep delay	£419.75
CS1820 Dual 20 MHz with extra facilities (List £508.30)	£485.00
OX710 Matrix dual 15 MHz + component tester	£304.75

**OPTIONAL PROBE KITS**

X1 £7.95 X1 - X10 £10.50 X10 £9.45 X100 £16.95	
--	--

## HIGH VOLTAGE METER

Direct reading 0/40 KV 20K/Volt (UK C/P 65p)	£23.00
--	--------

## DIGITAL CAPACITANCE METER

0.1 pF to 2000 mfd LCD 8 ranges DM6013 £52.75 (Carry case £2.95)	
--	--

## TRANSISTOR TESTER

Direct reading PNP, NPN, etc. TC1 (UK C/P 65p)	£21.95
--	--------

# AUDIO ELECTRONICS

Cubegate Limited  
 301 EDGWARE ROAD, LONDON W2 1BN. TEL: 01-724 3564  
 ALSO AT HENRY'S RADIO,  
 404/406 EDGWARE ROAD, LONDON, W2. TEL: 01-724 0323  
 HENRY'S COMPONENT SHOP. TEL: 01-723 1008

FREE CATALOGUE! SEND LARGE SAE (UK 20p)

ALL PRICES INCLUDE VAT

Order by Post with CHEQUE/ACCESS/ VISA or you can telephone your orders. All orders despatched within 5 days unless advised.

# CLEF ELECTRONIC MUSIC

## MICROSYNTH

2) Octave Music Synthesizer with two Oscillators, two Sub-Octs, Switched Routing and Thumbwheel. A comprehensive instrument offering the full range of Synth. Music & effects.  
 FULL KIT £137 Also available in 3 parts.



## PERCUSSION MICROSYNTH

Two Channel touch Sensitive unit plus variable angle L.F.O., phaser, internal and external triggering.

(Published in P.E.)

## BAND-BOX PROGRAMMABLE BACKING TRIO

THREE PIECE BACKING BAND  
 Generates the sounds of three instrumentalists to back Soloists

DRUMS + BASS + KEYBOARDS  
 Over 3,000 chord changes (60 scores) on 132 different chords - extendable to 200 scores. Master Rhythm also required.

FULL KIT £235 EXTENSION £82

(Published in P.E.)



## 88/72 NOTE PIANOS SPECIALISTS SINCE 1972

Using Patented electronic technique to give advanced simulation of Piano Key Inertia.



### COMPONENT KITS

including Keyboard	
88 NOTE	£266
72 NOTE	£234

The above may also be purchased in four parts.

### DOMESTIC KITS

inc. Cabinet, P.A., & Spkr.	
88 NOTE	£442
72 NOTE	£398

### STAGE MODEL

inc. Cabinet & Stand	
72 NOTE	£383



## MASTER RHYTHM PROGRAMMABLE DRUMS

Twenty-Four Rhythm programmable Drum Machine with twelve instruments. Eight sections are extended to 24/32 measures for two bar programming. Sequence operation and instrument tone adjust.

COMPLETE KIT	£79
STRING ENSEMBLE	£198.50
ROTOR-CHORUS	£98.00
SQUARE FRONT KEYBOARDS	
88 NOTE	£60
73 NOTE	£50
49 NOTE	£29
30 NOTE	£19

KEYSWITCH ITEMS ALSO AVAILABLE

CLEF PRODUCTS (ELECTRONICS) LIMITED  
 (Dept PE)  
 44A BRAMHALL LANE, SOUTH BRAMHALL, STOCKPORT, CHESHIRE SK7 1AH  
 TEL 061 439 3237

# ELECTROVALUE

Understandably Britain's most popular and relied-upon suppliers of SEMI-CONDUCTORS I.C.s COMPUTING EQUIPMENT TOOLS, BOXES, CONNECTORS and much, much more


**OUR SUMMER PRICE LIST TELLS ALL**  
 Send for your FREE copy by return  
**BETTER PRICES, BETTER CHOICE, BETTER SERVICE**  
 Don't forget to mention PRACTICAL ELECTRONICS with your request.

**ELECTROVALUE LTD.**  
 Head Office, Mail Order Dept and Shop  
 28d St. Judes Road, Englefield Green, Egham, Surrey TW20 0HB  
 Telephone Egham (STD 0784; London 87) 33603; Telex 264475  
 Also in Manchester for personal shoppers at:  
 680 Burnage Lane, Burnage, Manchester M19 1NA. Telephone 061-432 4945  
 Computing Shop -  
 700 Burnage Lane, Manchester. Telephone 061-431 4866

Step-by-step fully illustrated assembly and fitting instructions are included together with circuit descriptions. Highest quality components are used throughout.

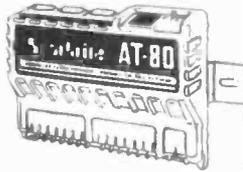
# Sparkrite

BRANDLEADING ELECTRONICS  
NOW AVAILABLE IN KIT FORM



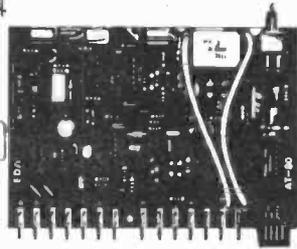
## AT-80 Electronic Car Security System

- Arms doors, boot, bonnet and has security loop to protect fog/spot lamps, radio/tape, CB equipment
- Programmable personal code entry system
- Armed and disarmed from outside vehicle using a special magnetic key fob against a windscreen sensor pad adhered to the inside of the screen
- Fits all 12V neg earth vehicles
- Over 250 components to assemble


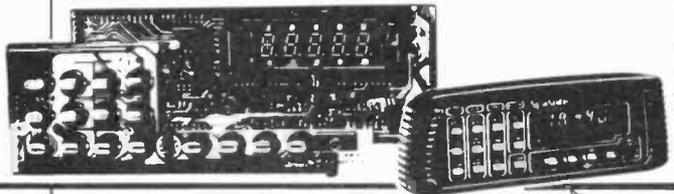
## VOYAGER Car Drive Computer

- A most sophisticated accessory
- Utilises a single chip mask programmed microprocessor incorporating a unique programme designed by EDA Sparkrite Ltd
- Affords 12 functions centred on Fuel, Speed, Distance and Time
- Visual and Audible alarms warning of Excess Speed, Frost/Ice, Lights-left-on
- Facility to operate LOG and TRIP functions independently or synchronously
- Large 10mm high 400ft-L fluorescent display with auto intensity
- Unique speed and fuel transducers giving a programmed accuracy of + or - 1%
- Large LOG & TRIP memories, 2,000 miles, 180 gallons, 100 hours
- Full Imperial and Metric calibrations
- Over 300 components to assemble
- A real challenge for the electronics enthusiast!




## SX1000 Electronic Ignition

- Inductive Discharge
- Extended coil energy storage circuit
- Contact breaker driven
- Three position changeover switch
- Over 65 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles




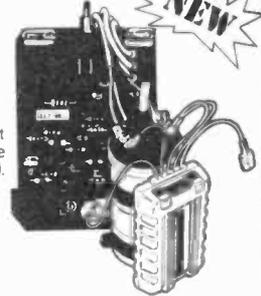
## TX1002 Electronic Ignition

- Contactless or contact triggered
- Extended coil energy storage circuit
- Inductive Discharge
- Three position changeover switch
- Distributor triggerhead adaptors included
- Die cast weatherproof case
- Clip-to-coil or remote mounting facility
- Fits majority of 4 & 6 cyl. 12V. neg. earth vehicles
- Over 145 components to assemble.


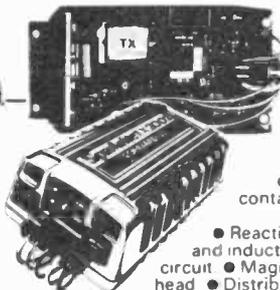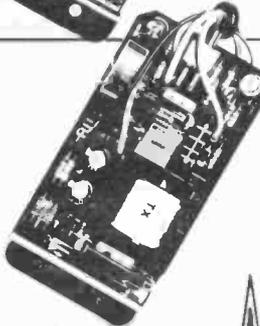
## SX2000 Electronic Ignition

- The brandleading system on the market today
- Unique Reactive Discharge
- Combined Inductive and Capacitive Discharge
- Contact breaker driven
- Three position changeover switch
- Over 130 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles




## TX2002 Electronic Ignition

- The ultimate system
- Switchable contactless
- Three position switch with Auxiliary back-up inductive circuit
- Reactive Discharge. Combined capacitive and inductive
- Extended coil energy storage circuit
- Magnetic contactless distributor triggerhead
- Distributor triggerhead adaptors included
- Can also be triggered by existing contact breakers
- Die cast waterproof case with clip-to-coil fitting
- Fits majority of 4 and 6 cylinder 12v neg. earth vehicles
- Over 150 components to assemble

All SPARKRITE products and designs are fully covered by one or more World Patents
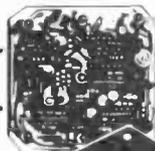
## SPECIAL OFFER

"FREE" MAGIDICE KIT WITH ALL ORDERS OVER £45.00



## MAGIDICE Electronic Dice

- Not an auto item but great fun for the family
- Total random selection
- Triggered by waving of hand over dice
- Bleeps and flashes during a 4 second tumble sequence
- Throw displayed for 10 seconds
- Auto display of last throw, 1 second in 5
- Muting and Off switch on base
- Hours of continuous use from PP7 battery
- Over 100 components to assemble

SPARKRITE, 82 Bath St., Walsall, W. Midlands WS1 3DE

SPARKRITE 82 Bath Street, Walsall, West Midlands, WS1 3DE England.

tel (0922) 614791 Allow 28 days for delivery

	SELF ASSEMBLY KIT
SX 1000	£12.95
SX 2000	£19.95
TX 1002	£22.95
TX 2002	£32.95
AT 80	£32.95
VOYAGER	£64.95
MAGIDICE	£9.95

PRICES INC. VAT, POSTAGE & PACKING

NAME \_\_\_\_\_ PE.8.83

ADDRESS \_\_\_\_\_

I ENCLOSE CHEQUE(S)/POSTAL ORDERS FOR

£ \_\_\_\_\_ KIT REF \_\_\_\_\_

CHEQUE NO \_\_\_\_\_

PHONE YOUR ORDER WITH   
SEND ONLY SAE IF BROCHURE IS REQUIRED

BRANDLEADING BRITISH ELECTRONICS  
CUT OUT THE COUPON NOW!

From  
**HAMEG...**

**NEW**



**S...STOP PRESS..STOP PRESS**  
...2 year warranty on all oscilloscopes..  
83.....as from 5 May 1983..... as from 5

**HM 103**

**£158**

*UK List  
ex V.A.T.*

**the original  
oscilloscope with built-  
in component tester**



Capacitor 33uF    Transistor E-C    Transistor B-E    B-E 1uF + 68 ohms

**NOW WITH IMPROVED SPECIFICATIONS**

**Y Deflection**

Bandwidth: DC-10 MHz (-3dB)  
Overshoot: Less than 1%  
Sensitivity: 2mV-20 V/cm  
Input Imp: 1M ohm//25pf  
Variable Control

**X Deflection**

Timebase: 0.2s - 0.2us/cm  
Triggering: 2Hz - 30MHz(3mm)  
Auto + level control  
Bandwidth: 2Hz - 1MHz  
Variable Control

**GENERAL INFORMATION**



Component Tester	For single components and in circuit
Calibrator	0.2V ± 1% for probe alignment
Power Supplies	Regulated including high voltage
A.C. Input	110, 120, 220, 240, V.A.C. 50-60 Hz
Weight	8½ Lbs.
Size	4½"(H) X 8 3/8"(W) X 10 7/16"(D)
CRT	Rectangular internal graticule
Accuracy	3% in vertical amplifier
Filter	T.V. trigger filter
Trace rotation	via front panel

*For more information on HAMEG's full range of top performance oscilloscopes contact:*

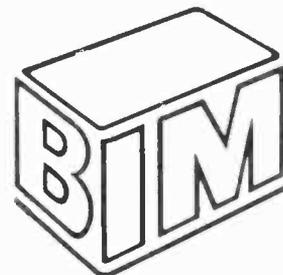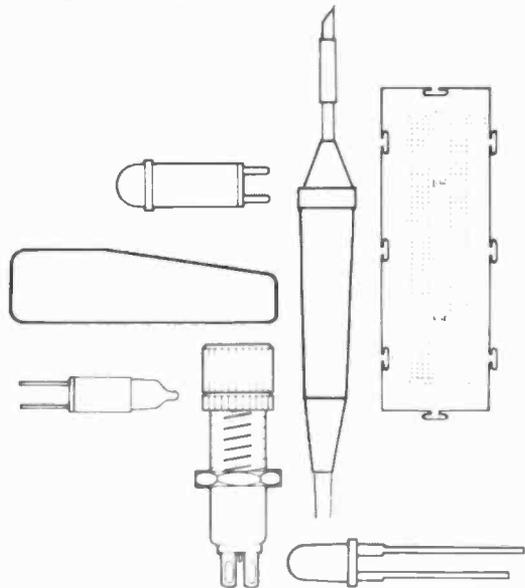**HAMEG LTD.**

74 - 78 Collingdon Street, Luton, Beds. LU1 1RX  
Tel: (0582) 413174

**ENCLOSURES  
INDICATORS  
BREADBOARDS  
ANCILLARY TOOLS**



**WRITE OR PHONE FOR OUR  
LATEST CATALOGUE**

**BOSS INDUSTRIAL MOULDINGS LIMITED**

James Carter Road, Mildenhall, Suffolk IP28 7DE  
Telephone: Mildenhall (0638) 716101  
Telex: 818758 Answer Back 'LITZEN G'



All devices guaranteed Brand New and to full spec. Items ex stock despatched same day. Prices are EXCLUSIVE of VAT. Please add 60p to order to cover P&P BEFORE calculating VAT. Payment by cheque, Postal Order, Bankers Draft or Cash (PLEASE register) with order. Official orders from Govt. Depts and Educational Institutes Welcome. Trade Accounts opened subject to satisfactory status - send for details. We are pleased to receive overseas orders please allow adequate postage - surplus refunded) which, unless accompanied by Bankers Draft in UK Currency may be subject to Bankers Commission and slight delay in despatch. Overseas trade enquiries welcome - send for full details. VAT not applicable to export orders. Price List detailing full range of components available - 30p refundable with first order - Please send SAE.

# COMM QUIP Ltd.

HAMILTON HOUSE, 11 WALKERN ROAD,  
STEVENAGE, HERTS. SG1 3QD.  
Telephone (0438) 729771 Telex 825378 G

LINEAR	LM3900	45	ZN428E	395	CMOS	4518	39	LS04	12
556CMDS	80	LM3909	70	ZN459	285	4000	11	LS05	12
556CMOS	140	LM3211	120	ZN1034E	200	4001	11	LS08	12
709	25	LM3914	175		4002	11	LS09	12	
741	14	LM3915	195	LOGIC ICs	4007	14	LS12	12	
748	35	LM13600	105	AYS-2376	590	4008	34	LS11	12
9400CJ	345	MC1496	68	MC1488	55	4009	24	LS12	12
AY-3-1270	710	MC3340	120	MC1489	55	4011	11	LS12	12
AY-3-8910	370	MC10CN	350	MM5303	625	4012	14	LS12	12
AY-3-8912	540	ML924	195	MM5307	1250	4013	20	LS14	22
CA3046	60	NE529	225	MM58174	700	4015	39	LS15	22
CA3080	65	NE531	135	MS6011	365	4016	20	LS20	12
CA3089	190	NE544	180	ULN2003	75	4017	32	LS21	12
CA3090A	370	NE555	16	8726	99	4020	42	LS22	12
CA3130E	85	NE556	45	8728	120	4021	39	LS27	12
CA3140C	35	NE565	110	8795	90	4021	39	LS28	12
CA3161E	100	NE566	140	8797	90	4022	39	LS28	12
CA3189	200	NE567	100	8797	90	4023	12	LS33	14
CA3240E	110	NE570	370	81LS95	80	4024	32	LS33	14
ICL7106	680	NE571	370	81LS96	80	4025	12	LS37	14
ICL7611	95	RC4136	55	81LS97	80	4027	20	LS38	14
ICL7621	180	RC4558	45	81LS98	85	4028	37	LS40	12
ICL7622	180	SL490	250	6532	310	4029	43	LS42	28
ICL8038	290	SL76477	380	6532	310	4029	43	LS47	35
ICL8211A	150	SP8629	250	6532	310	4029	43	LS48	40
ICM7224	775	TBA120S	70	6532	310	4029	43	LS49	50
ICM7255	80	TBA800	75	6532	310	4029	43	LS51	14
LF353	85	TBA810	95	6532	310	4029	43	LS54	14
LF356	90	TBA820	70	6532	310	4029	43	LS55	14
LM10	325	TBA950	220	6532	310	4029	43	LS55	14
LM301A	24	TDA1008	310	6532	310	4029	43	LS54	14
LM311	70	TDA1022	480	6532	310	4029	43	LS54	14
LM318	120	TDA1024	115	6532	310	4029	43	LS55	14
LM324	30	TLO61	40	6532	310	4029	43	LS55	14
LM334Z	90	TLO62	60	6532	310	4029	43	LS55	14
LM335Z	120	TLO64	95	6532	310	4029	43	LS55	14
LM339	45	TLO71	25	6532	310	4029	43	LS55	14
LM348	60	TLO72	45	6532	310	4029	43	LS55	14
LM358	55	TLO74	95	6532	310	4029	43	LS55	14
LM377	165	TLO81	24	6532	310	4029	43	LS55	14
LM380	65	TLO82	45	6532	310	4029	43	LS55	14
LM381	120	TLO84	90	6532	310	4029	43	LS55	14
LM384	110	TL170	49	6532	310	4029	43	LS55	14
LM384	130	UAZ240	115	6532	310	4029	43	LS55	14
LM386	65	ULN2003	75	6532	310	4029	43	LS55	14
LM387	120	ULN2004	75	6532	310	4029	43	LS55	14
LM393	95	XR2006	285	Z80ACTC	250	4502	50	LS55	14
LM711	60	ZN414	79	Z80ADART	775	4508	110	LS55	14
LM725	325	ZN423	130	Z80ADAMA	975	4510	45	LS55	14
LM733	69	ZN424	130	Z80AP10	270	4511	45	LS55	14
LM747	60	ZN425E	340	ZN425EB	320	4512	42	LS55	14
LM1458	40	ZN426E	290	ZN426EB	320	4514	110	LS55	14
LM2917	185	ZN427E	575	ZN427EB	575	4515	110	LS55	14
				ZN428EB	395	4516	50	LS56	33

COMPUTER ICs	MEMORIES	74LS
1802	2101	LS00
2650A	2114 (200ns)	LS01
6502	2532	LS02
6800	2564	LS03
6802	2995	
6809	1000	
8035	225	
8060	210	
8080A	750	
8085A	80	
8085A	4118-3	
780A	4164	
	420	
	150	
	725	
	5101 (450ns)	
	6116 (150ns)	
	6514	
	6810	
	395	
	85	
	295	
	1000	
	225	
	210	
	750	
	80	
	4118-3	
	4164	
	420	
	150	
	725	
	5101 (450ns)	
	6116 (150ns)	
	6514	
	6810	
	395	
	85	
	295	
	1000	
	225	
	210	
	750	
	80	
	4118-3	
	4164	
	420	
	150	
	725	
	5101 (450ns)	
	6116 (150ns)	
	6514	
	6810	
	395	
	85	
	295	
	1000	
	225	
	210	
	750	
	80	
	4118-3	
	4164	
	420	
	150	
	725	
	5101 (450ns)	
	6116 (150ns)	
	6514	
	6810	
	395	
	85	
	295	
	1000	
	225	
	210	
	750	
	80	
	4118-3	
	4164	
	420	
	150	
	725	
	5101 (450ns)	
	6116 (150ns)	
	6514	
	6810	
	395	

# The Big Event for '83

Sponsored by Practical Electronics, Practical Wireless and Everyday Electronics

The first Electronic Hobbies Fair in 1982 immediately established itself as the foremost consumer electronics exhibition-the biggest attendance and the largest number of exhibitors.


The 1983 Fair will build on the success and the experience of the first year. It will be 1983's largest and most influential

shop window for the whole range of electronic equipment and components for the electronics hobby enthusiast-constructural projects, home computers, amateur radio, video games, musical instruments and peripheral equipment-whether for the beginner, the specialist or the all-round enthusiast.


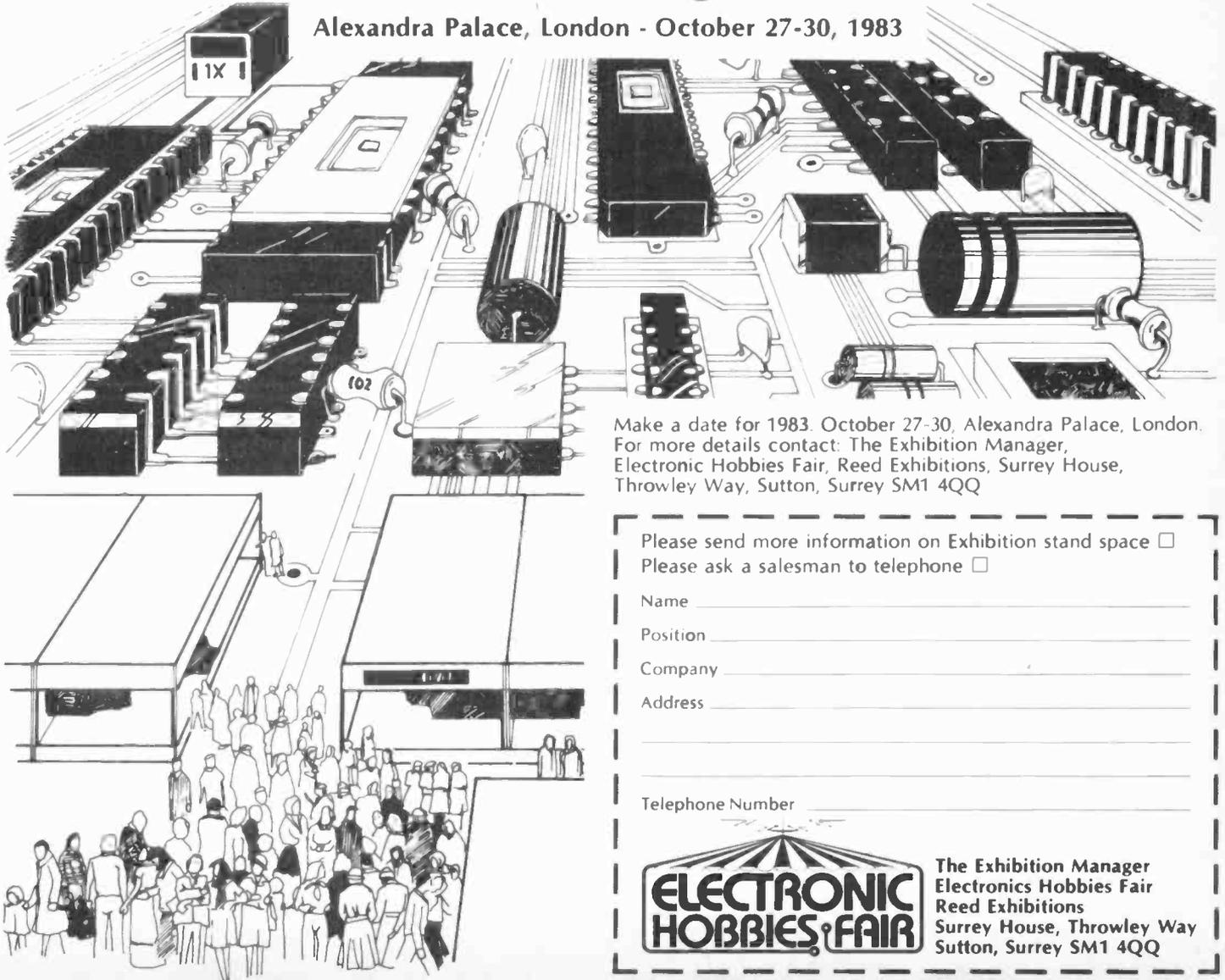
## ELECTRONIC HOBBIES FAIR

Alexandra Palace, London - October 27-30, 1983



Make a date for 1983. October 27-30, Alexandra Palace, London. For more details contact: The Exhibition Manager, Electronic Hobbies Fair, Reed Exhibitions, Surrey House, Throwley Way, Sutton, Surrey SM1 4QQ

Please send more information on Exhibition stand space   
Please ask a salesman to telephone

Name

Position

Company

Address

Telephone Number




**ELECTRONIC HOBBIES FAIR**

The Exhibition Manager  
Electronics Hobbies Fair  
Reed Exhibitions  
Surrey House, Throwley Way  
Sutton, Surrey SM1 4QQ
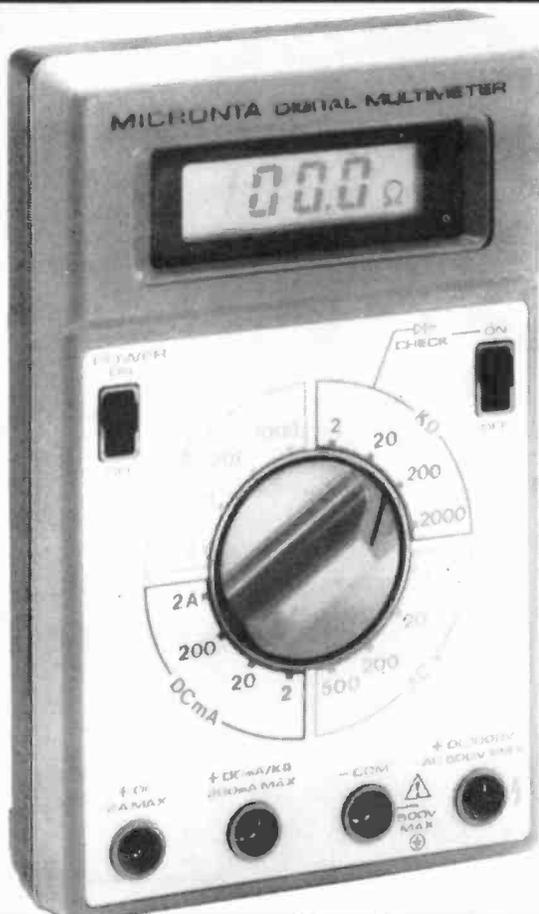
# Tandy®

The Largest Electronics Retailer In The World



## Compact 3 1/2-Digit 16-Range Multimeter

# NEW!

# £34.95

- Fused and Overload Protected
- Diode Check Function For Testing Semiconductors
- 10 Megohm Input

Digital accuracy at a practical price. Features easy-to-read display. Single-IC design assures extremely low battery drain and high accuracy. Single-knob switch, full auto-polarity operation. Low-battery and overrange indicators. Diode check on/off switch. **DC volts:** 2-20-200-2000V (max. 1000V), **AC volts:** 2-20-200-2000V (max. 500V), accurate from 45 Hz to 10 kHz. **DC Current:** 2-20-200mA-2A. **Resistance:** 2-20-200-2000k Ohms. 5<sup>3/16</sup> x 3<sup>1/4</sup> x 1<sup>7/16</sup>". Includes spare fuse, test leads. Requires 2 "AA" batteries. 22-189

### Regulated Power Supply



• Ideal as a Test Bench Supply  
**£19.95**  
 • Use With Mobile CB's and Ham Rigs - Converts 240 AC House Current to 13.8 Volts DC

Regulated 13.8v DC supply, operates most 12 to 14 volt DC devices. 2.5 amps continuous load, five amp surge - 240v AC, 50 Hz. Rugged metal cabinet. 22-7000

### Dynamic Transistor Checker



**£9.95**

- Makes Go/No-Go Tests on Small Signal and Power Types

Indicates relative current gain, "opens", "shorts". Socket plus hook clip leads for in-circuit tests. Output jacks for external meter or scope. 2<sup>3/4</sup> x 4<sup>3/8</sup> x 3<sup>1/16</sup>". Requires "AA" battery. 22-025

### Micronta™ Clamp Meter



**£27.95**

- Overload Protected
- Pointer Lock Switch

Measure AC current without disconnecting or breaking the line being checked. Large range selector is positioned for one-hand operation. Incorporates a pointer lock switch (for reading later). **AC current:** 0-6-15-60-150-300 amperes. **Accuracy:** ± 3%. 22-160

### 21 Ranges - 30,000 Ohms/Volt



**£39.95**

"Beep" continuity. **DC Volts:** 0-1000. **AC volts:** 0-1000. **DC Current:** 0-10 amps. **Resistance:** 0-1-10K-1-10 megs. (centre scale 10) dB: -20 to -62 dB. 5 ranges. **Accuracy:** ± 3% DC, ± 4% AC. 22-210

**OVER 340 STORES AND DEALERSHIPS NATIONWIDE** Check your phone book for the Tandy Store or Dealer nearest you

Known as Radio Shack In the USA  
 Prices may vary at dealers  
 Offers subject to availability

Prior to this advertisement, all quoted regular prices have been charged during the last six months at the Tandy Store, Tameway Tower, Bridge Street, Walsall, West Midlands. WS1 1LA

## CABLE—A BREAKTHROUGH?

WITH the recent news of a cable service for most UK homes and the exciting possibilities that have been dreamed up by the media it is sobering to read what follows, written more than eleven years ago by Fred Bennett who was then editor of PE.

"With commendable boldness and confidence in the future growth of telecommunications for domestic purposes, the Post Office is currently involved in the installation of a 'communication main' system in the new city of Milton Keynes, now arising in Buckinghamshire. Every house in the new city will be linked to this communication system. The cables will, so far as possible, be laid in a communal trench, with the other essential services, water, gas, electricity, and drainage.

"A standard telephone pair forms part of this 'main'. This cable is accompanied throughout, right up to every front door, by a high performance

coaxial cable. Besides being capable of carrying radio and television signals, this wideband coaxial cable provides for the transmission of two-way signals such as could be employed to operate viewphones and computer data terminals, and permits the carrying out of other useful functions, like the remote reading of gas and electricity supply meters.

"What happens in Milton Keynes may become the pattern for the future throughout the country. At any rate, this pioneer installation is worth noting and musing upon. It could herald another technological explosion making direct impact upon the domestic or 'consumer' section. We don't doubt that fertile minds will seize eagerly the opportunity it promises for further imaginative and useful exploitation of electronics."

Obviously with the increase in consumers resulting from wide scale cabling the cost of suitable equipment will fall. However, we cannot help wonder-

ing if it will all be worthwhile when the use of Viewdata is still so limited. The wonders of Information Technology will not be forced on a community that sees little advantage in the system. The availability of a vast range of cheaply hired video cassettes already reduces the chance of any "film channel" being successful.

As Vernon Trent indicates this month, technology can move as fast as it likes, the consumers are setting their own pace.

## PRICE INCREASE

Unfortunately rising costs have forced us to make a cover price increase. From next month PE will cost an extra five pence; this is slightly less than a six per cent increase. The last increase was a year ago.



**EDITOR** Mike Kenward  
**Gordon Godbold** ASSISTANT EDITOR  
**David Shortland** ASSISTANT EDITOR/PRODUCTION  
**Mike Abbott** TECHNICAL EDITOR  
**Brian Butler** TECHNICAL SUB EDITOR

**Jack Pountney** ART EDITOR  
**Keith Woodruff** ASSISTANT ART EDITOR  
**John Pickering** SEN. TECH. ILLUSTRATOR  
**Isabelle Greenaway** TECH. ILLUSTRATOR  
**Jenny Tremaine** SECRETARY

*Technical and Editorial queries and letters (see note below) to:*

Practical Electronics Editorial,  
Westover House,  
West Quay Road, Poole,  
Dorset BH15 1JG

**Phone: Editorial Poole 671191**

**We regret that lengthy technical enquiries cannot be answered over the telephone**

*Queries and letters concerning*

**advertisements to:**  
Practical Electronics Advertisements,  
King's Reach Tower,  
King's Reach, Stamford Street, SE1 9LS  
Telex: 915748 MAGDIV-G

**ADVERTISEMENT MANAGER** D. W. B. Tilleard } 01-261 6676  
SECRETARY **Christine Pocknell** }  
AD. SALES EXEC. **Alfred Tonge** 01-261 6819  
CLASSIFIED SUPERVISOR **Barbara Blake** 01-261 5897  
AD. MAKE-UP/COPY **Brian Lamb** 01-261 6601

## Letters and Queries

We are unable to offer any advice on the use or purchase of commercial equipment or the incorporation or modification of designs published in PE. All letters requiring a reply should be accompanied by a stamped, self addressed envelope, or addressed envelope and international reply coupons, and each letter should relate to one published project only.

Components and p.c.b.s are usually available from advertisers; where we anticipate difficulties a source will be suggested.

## Back Numbers

Copies of most of our recent issues are available from: Post Sales Department (Practical Electronics), IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF, at £1 each including Inland/Overseas p&p. Please state month and year of issue required.

## Binders

Binders for PE are available from the same address as back numbers at £5.50 each to UK or overseas addresses, including

postage and packing, and VAT where appropriate. State year and volume required.

## Subscriptions

Copies of PE are available by post, inland or overseas, for £13.00 per 12 issues, from: Practical Electronics, Subscription Department, Oakfield House, Perrymount Road, Haywards Heath, West Sussex RH16 3DH. Cheques, postal orders and international money orders should be made payable to IPC Magazines Limited. Payment can also be made using any credit card and orders placed via Teledata Tel. 01-200 0200.

Items mentioned are available through normal retail outlets, unless otherwise specified. Prices correct at time of going to press.

# NEWS &

## Farewell Analogue TV

It was hardly likely that the humble domestic television receiver would remain outside the swelling compass of digital technology for much longer. The bell tolls, and ITT is the campanologer with its "Digivision" system.

Until now, digital electronics has been applied only to two sections of the television set, these being the infra-red remote control and the local oscillator of the tuner. The situation has changed dramatically. In what is claimed to be the biggest revolution in television since the introduction of colour 30 years ago, ITT's Digivision offers an entirely new system which changes fundamentally almost every section of the receiver. Although Digivision is designed to receive conventional TV broadcast signals, it is almost 100 per cent digital in operation, and it is already on the commercial horizon. Receivers based on the Digivision chip set will be on sale in West Germany, the country of origin, in late 1983. They will become available in the UK in early 1984. ITT expects that in the future 50 per cent of all television sets sold throughout the world will incorporate Digivision. An understandable anticipation, it being the culmination of a 10 year, £20m investment project.

The benefits of a micro' based receiver, to both the user and the service engineer, are manifold. The end-user gets a television which makes an "intelligent" effort to op-


timise reception under all conditions (including ageing) by comparing performance characteristics with factory preset values stored in memory, and, naturally, making all necessary adjustments automatically. Sound quality is also improved with digital processing right to the loudspeaker (mono or stereo) using pulse-width modulation.

The service engineer will benefit from a tool that ITT calls an "electronic screwdriver". This diagnostics computer runs tests and makes adjustments to the receiver's EAROM data by way of an umbilical cable. The chassis has only one preset potentiometer. The engineer will be able to carry out most adjustments from the front of the set, following prompts on the screen.

Some amazing possibilities accompany the digital television era. Line and field storage is envisaged, which will allow display scanning standards to be defined and varied locally. For example, a 625 line, 50 fields/sec interlaced picture could be displayed at 1250 line, 150 fields/sec non-interlaced, yielding improvements in subjective definition and stability. Picture data

storage will also make possible selective "zoom" and "freeze" of any broadcast picture. Noise, interference and flicker will be eliminated, and ghost images will be "exorcised". The intriguing prospect of pictures from other channels being inset into one corner of the channel being watched, is with us.

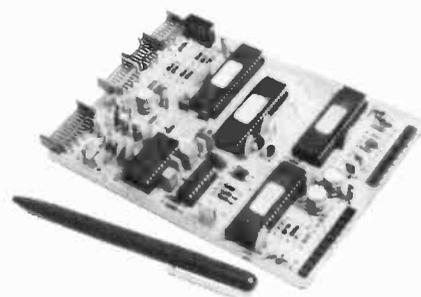These features by no means represent the extent of exciting possibilities that



The Digivision component board

should become reality between 1983 and 1986. Digivision will be able to accept signals directly from Prestel or a home computer, or from a video cassette recorder or video disc player operating on any television standard (PAL, SECAM, NTSC).

ITT's first production designs would comprise up to 300 components if they were analogue, but will instead comprise just seven VLSI chips.

## Piezoelectric Plastic

The electronics hobbyist of yore, enthused by experimentation with an OC71 transistor, a piece of paxolin and a tobacco tin, would have scoffed at the idea of discovering electronics, or physics using pre-designed circuits conveniently packed into little plastic bricks, no matter how many leads emerge from them. But he wouldn't have scoffed at the opportunities afforded by a new product from Metal Box's R&D lab's at Wantage, which opens up a whole new can of worms (as they say) for the experimentalist.


Think what could be done with a sheet of piezoelectric plastic which can be cut to any shape or size, to make a custom transducer. The idea is not new; the Japanese (of course) have been making a similar material for some time, but it has never been widely available. Metal Box make theirs from polyvinylidene fluoride (PVDF) which is metallised, and undergoes rather special treatment to give it the potential to be used in microphones, loudspeakers, impact detectors and push buttons, and who knows what else?

When acting as an audio transducer the material can be its own diaphragm, opening up amazing possibilities, which include large area microphones, flat loudspeakers, vibrating surfaces or platforms and ultrasonics. Other applications spring to mind: How about a flexometer (if there is such a thing)? Or an optical deflector, or perhaps an acoustically controlled LF oscillator? Or even a liquid atomiser?

The pure experimentalist's odyssey is assured with this film, because it is also pyroelectric, enabling it to be used for thermal im-

aging, heat sensing, fire detection, temperature measurement, and doubtless other applications as yet to be conjured. The plastic film is readily formed into complex shapes. The film is available in thicknesses of 10 and 22 micrometre, and is already proving valuable in medical applications.

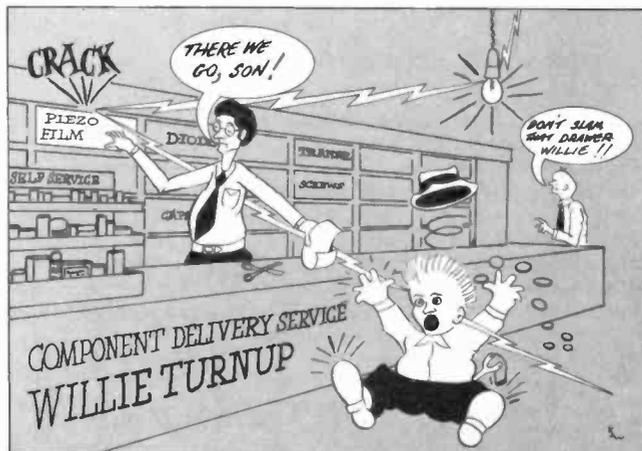
Sadly, at £20 for 200 sq. cm. (minimum qty.) Metal Box's piezoelectric film is at the moment a little expensive for dabbling with, but the manufacturer sees the price coming down as its use increases. Perhaps in the meantime, hobbyist suppliers will bulk buy and make the film available in less costly amounts.



# MARKET PLACE

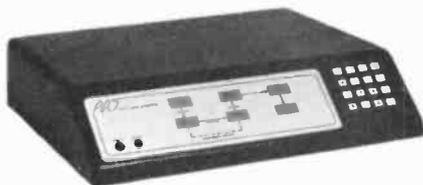
## Viewdata Bargain

The PAT Viewdata adaptor shown here is available for £55 (including VAT, plus postage) but before you reach for your cheque book there is just one point we should mention! Although they are in the manufacturer's packing and are new and unused they can only be purchased from J. Bull (Electrical) Ltd., untested and without guarantee. However, the components alone



are worth more than the cost and "if all else fails" the GI chips could be used for your own design system. The unit shown in the photo is now providing Prestel in the PE office, following installation of a jack (£15) by British Telecom. The equipment is beautifully made and at the price is obviously too good to miss, provided you are prepared to take a chance. But make up your mind quickly as the quantity is limited.

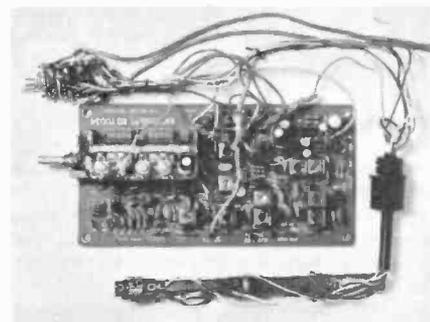Also from J. Bull is an excellent Amstrad a.m./f.m. tuner head. F.M. coverage is 87.5—108MHz at 2.5µV for 30dB signal to noise and a.m. coverage is: m.w. 525-1650kHz; l.w. 155-270kHz at 320µV/M.



Connections for a tuning meter, stereo beacon and a.f.c. switch are provided. With the addition of a 12V supply and simple stereo amp this would make a high quality portable radio or it could form the heart of a hi-fi system, as it was originally intended to do in the EX222 receiver. The tuners are new and the price is £6, including VAT plus postage.

J. Bull (Electrical) Ltd. (Dept PE), 34-36 America Lane, Haywards Heath, Sussex RH16 3QU. Tel: 0444 454563.

## Amorphous Solar Cells

Mitsubishi Electric Corporation of Japan has managed the successful manufacture of an experimental 100cm<sup>2</sup> solar cell with an energy conversion efficiency of 8.25%. Although this may not sound like a very exciting event, this level of efficiency is claimed to be the world's highest for such a large element size.

The high performance solar cell, which comprises one amorphous germanium and two amorphous silicon layers, has an open-circuit output of 2.24V. It is low cost, using less than 1% of semiconductor materials as compared with a single crystal solar cell, and furthermore large element sizes are possible. Exposure to the sun gradually changes the characteristics of conventional cells, but does so far less with Mitsubishi's cells. Production costs are also lower, since the amorphous cell can use a cheap and comparatively unsmooth steel plate as its substrate.

As part of the solar cell research venture called the "Sunshine Project" Mitsubishi is in charge of amorphous cell development. The project, started in 1980 by the

Japanese Agency of Industrial Science and Technology, had targeted the objective of a 10x10cm element with an efficiency greater than 8% by the close of 1982. This it achieved, and now Mitsubishi is working towards the production item.



Amorphous solar cell panels of Mitsubishi Electric

## Silicon News Corner

Bulletins announcing new semiconductor devices arrive at PE daily, so it is possible only to describe them briefly. Details of how to obtain further information are included, however.

**United Components** ♦ Two new enhancement mode, 400MHz power f.e.t.s, UMP1 & UMP2. Operating from 25-30V, UMP1 gives 5W at 110dB gain, and UMP2 gives 10W at 7dB. Almost infinite VSWR mismatch tol.

♦ New stackable rectangular (2 x 5mm) l.e.d. series. The high efficiency MV5X123 is available in red and yellow and high brightness green.

♦ Optically isolated gate, triac driver i.c. (6-pin) called MCP30XX series. 120 & 240V versions can drive up to 24VA loads. Pin replacements for MOC3000 series.

♦ Data Books: GI Opto £2.50. Plessey High Speed Data Processing £1.20, High Speed Dividers £1.50, Consumer Devices (inc. remote control) £1.50, Telecoms £1.50, & Linear (inc. power control) £1.50. **Siliconix** FET Design cat. £1.75, Analogue Switch £2.50, MOSpower Design cat. £2.50. United Components, Unit 5, Wye Industrial Estate, London Road, High Wycombe, Bucks HP11 1LH.

**Rastra** ♦ The CH1812 module provides Direct Connect Protective Hybrid (DCPH) interface to telephone line, conforming to regulations. Measures 0.66 x 2.1 x 1.1 in.

♦ DAC 9331-16 series comprises 16-bit latched D to A in monolithic technology. Features 0.0008% linearity, 2-chip construction, I/P registers, low power, HI-REL 24-pin d.i.p., 2 & 4 quadrant multiplication, single +15V supply. Cheap, ultra-robust commercial device. Rastra Electronics, 275 King Street, Hammersmith, London W6 9NF.

**Ferranti** ♦ TO92 style radio receiver, designated ZN414Z is the widely available TRF circuit, now in alternative package.

♦ Motor speed controller i.c. called ZN411E provides precise speed control for electric power drills. On-chip shunt regulator, soft-start and reverse capability. Hall effect compatible "Tacho" I/P, and current limit. Ferranti Electronics, Fields New Road, Chaderton, Oldham, Lancs OL9 8NP.

**Siliconix** ♦ Six new additions to the VN series power f.e.t.s offer 250W ratings, BV<sub>dss</sub> from 60-500V at 20A. These TO-3 packaged devices have on-resistance of 0.035-0.3. Siliconix Ltd., Morriston, Swansea SA6 6NE.

**Motorola** ♦ The marriage of the DIAC and the TRIAC results in a bilateral switch called the SIDAC, which conducts up to 1A when the voltage across it exceeds 115V for the MKIV-115, and 135V for the MKIV-135. Housed in "surmetic" 50 axial lead package, it is intended for pulse applications and fluorescent lamp starters. Motorola Ltd., York House, Empire Way, Wembley, Middlesex.

## 'Quiteron' Plasma Display Breakthrough

In the quest for the superconducting switch one early attempt (called the Cryotron) achieved a switching action by way of the transition from superconductor to normal metal—an action that was too slow for practical application. Another attempt, a three-terminal device invented at Argonne National Laboratory, did show small-signal current gain; but the most widely known breakthrough, called the Josephson Tunnel-Junction switch, functions with promisingly high speed and low power.


However, IBM's Thomas J. Watson research centre in Yorktown Heights, New York, has come up with a superconducting "transistor." The patented device is called the "quiteron" by its inventor, Sadeg M. Faris (shown in the photograph, holding a wafer of experimental samples).



The quiteron has yet to be optimised, but it is the first three-terminal superconducting device that can both amplify and switch, consequently having potential applications in analogue and digital circuitry. Like the familiar Josephson Junction, the quiteron is a cryogenic device that employs superconductivity, a phenomenon occurring near absolute zero (0 deg. K, or -273 deg. C) at which temperature certain metals lose all resistance to electrical current flow. The two devices are, nevertheless, based on entirely different principles.

The quiteron consists of two tunnel junctions formed by three thin films of superconducting materials separated from one another by two, even thinner, films of insulating material. Structures of this nature have been studied before, but the quiteron is the first to make use of the "non-equilibrium" superconductivity phenomenon known as the "heavy-QUasiparticle-Injection Tunnelling Effect" (pardon?). The name qu-i-t-e-ron was derived from this.

The secret of Siemens' success, where others have failed, in combining the flatness of the plasma display with the high intensity/resolution and colour potential of the c.r.t., is in the fact that its plasma is *not* used as a source of light, but as a source of *electrons*. The electrons are then guided by a specially developed grid to a conventional phosphor screen. The flat display developed by Siemens of Munich, West Germany, can illuminate up to  $10^6$  pixels without compromising other parameters—as in the past. The 14 inch plasma-discharge panel shown in the photograph is only six centimetres thick.

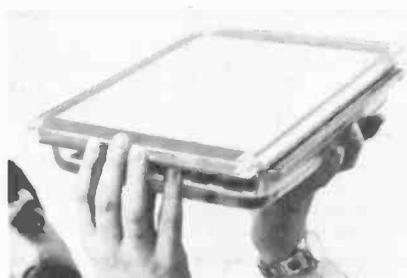

Because plasma acts as an electron source, as opposed to the hot cathode in a conventional c.r.t., this display requires a mere 4kV for its acceleration electrode (c.r.t. requires 20kV), and so it produces virtually no X-rays. This is a nice feature since the display will first begin to appear in VDU applications; and

with a resolution of 3.1 dots/mm horizontally, and 2.5 dots/mm vertically, arbitrary graphical images are possible. Power drain for the entire panel is 20W, and flicker is eliminated by a refresh frequency of 80Hz.

The display surface is perfectly flat, which allows a good focus right into its extreme corners. Also the electron flight-path is much shorter than in a c.r.t., being one millimetre between the control plate and the phosphor, so that the natural divergence of the beam electrons due to mutual electrostatic repulsion is minimised. This improves the focal sharpness still further.



As a VDU, the display may be driven entirely digitally, each pixel being addressable on a row-and-column basis. Pulse durations determine illumination levels, thereby allowing a full greyscale. But there is nothing grey about the future of this development, which is quite capable of invading the television market in due course.

## Trains and Boats and Planes

**"What is this life if, full of care,  
We have no time to stand and  
stare?"—William Henry Davies.**

And what better place to stand and stare than the South Kensington Science Museum's new gallery called "Telecommunications — A Technology For Change," which is heavily sponsored for its first year of life by STC to mark the company's Centenary.

The public may enjoy the story of telecommunications by way of two adjoining galleries. The first describes the subject's chronology, whilst the second demonstrates the technologies that make distant communication possible.

Life size mock-ups include the telegraph office at Tonbridge railway station in 1850, a ship's radio cabin of 1910 and the radio operator's position

in a World War II Lancaster bomber.


Tape recorded reminiscences of life in the service of cable companies throughout the period 1920-1950 add to the atmosphere, and working demonstrations and computer graphics displays illustrate aspects of modern telecommunications techniques. Packet switching and pulse code modulation principles are illustrated in this way, and a simulation of the System X digital exchange increases the visitor's understanding of services we all take for granted. A purpose-built cinema shows films produced by STC, but for those with an itch to twiddle knobs there is the remote controlled camera and monitor which may be operated by visitors. This installation oversees the museum's entrance, from a vantage point on the neighbouring Victoria and Albert Museum.

# MARKET PLACE
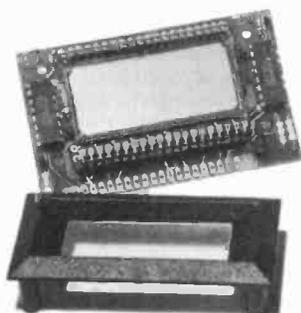
## PANEL METERS

A recently formed company called Martel has been set up to manufacture and market low cost, high quality instruments, control modules and counter timers.

Two particularly interesting items, from their range, are the MCM 3554/1 voltmeter and the MCF 4544/1 frequency meter. Both of these versatile digital panel mounting instruments have been designed



by Martin Kent the author of many projects published in PE.

The two instruments which are fully assembled and calibrated have many applications including uses in multimeter, thermometer and pH meter designs.

The voltmeter, based around the 7126 chip, has a  $\pm 200\text{mV}$  full scale and  $3\frac{1}{2}$  digits (0.5in high). The frequency meter, based


around the 7224 chip, has three ranges (2MHz, 200kHz and 20kHz) and  $4\frac{1}{2}$  digits.

Both meters are available to PE readers at a special offer price (valid to 31.8.83) of £9.95 plus VAT for the voltmeter and £19.95 plus VAT for the frequency meter. Data sheets are supplied with both devices.

Martel Instruments Limited, Knight House, Foxhill Road, Southminster, Essex.

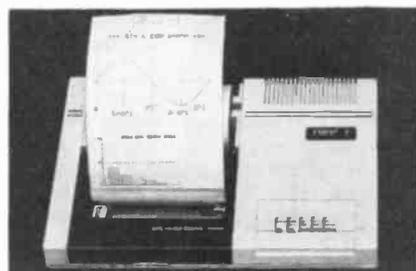
## PRINTERS

Two new printers have just been launched by Oric Products and Crofton Electronics. The Oric unit which is the first peripheral for the Oric 1 is a colour system with an inter-



nal power supply and a standard Centronics interface. The printer is priced at £169.95.

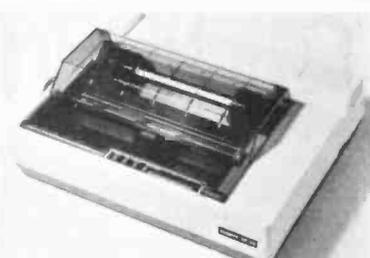The second unit is the AMD printer which is similar to the Epson having the Graftrax plus facility and is a 80 column, tractor feed machine with a parallel Cen-



tronics port. Crofton are offering the machine at a special launch price of £311.00 plus VAT and £7.50 carriage.

Crofton Electronics Ltd., 35 Grosvenor Road, Twickenham, Middlesex.

## and Finally...

The recently formed Irish Amateur Computer Club is seeking to add to its throng of 70+ members, with a particular desire to enrol more "hardware specialists". The IACC currently meets at least once a month in the Power's Hotel, Dublin (second Sunday of each month 10am to 2pm). Members receive regular bulletins and newsletters, and enjoy a good range of benefits and events. Sub-groups are envisaged, concentrating on specific tasks, topics and brands of computer.

For further details contact: Nigel Carey, 166 McKee Avenue, Finglas East, Dublin 11.

## Countdown . . .

Please check dates before setting out, as we cannot guarantee the accuracy of the information presented below. Note: some exhibitions may be trade only. If you are organising any electrical/electronics, radio or scientific event, big or small, we shall be glad to include it here. Address details to Mike Abbott.

**IBM User Show** July 12-14. Wembley. O  
**Internoise** (noise control conf.) July 13-15. A7  
**BAEC Amateur Electronics** July 16-24. Shelter, Esplanade, Penarth, S. Glamorgan. B9  
**Laboratory Edinburgh** July 18-20. University. E  
**Star '83 Aerospace** July 21-24. RAF Greenham Common. Z1  
**Acorn Exhibition** Aug. 25-28. Cunard Int. Hotel, Hammersmith, London. J3  
**BARTAG Rally** (radio teleprinter) Aug. 29. Sandown Park, Esher, Surrey. E2  
**Light Aviation Show** Sept. 1-3. Cranfield Institute, Bedfordshire. Z1  
**Electro West** Sept. 6-8. Bristol Exhibition Centre. Q  
**CAST** (Cable And Satellite Television) Sept. 11-14. NEC. F5  
**Weldex** Sept. 12-16. NEC B/ham. I  
**Testmex** Sept. 13-15. Grosvenor House, Park Lane, London. E  
**Home Entertainment Spectacular** Sept. 17-25. Olympia. I2  
**Peterborough R & ES Mobile Rally** Sept. 18. Werrina Stadium, Bishops Rd., Peterborough. L2  
**Personal Computer World Show** Sept. 28-Oct. 2. London. M  
**Laboratory London** Oct. 12-14. Barbican Centre. E

**Drives/Motors/Controls** Oct. 12-14. Leeds University. E  
**Computer Graphics** Oct. 18-20. Wembley. O  
**PARC** (computers in architecture, conf.) Oct. 18-20. Wembley. O  
**International Business Show** Oct. 18-26. NEC. T  
**Business Efficiency Exhibition** Oct. 22-26. Earls Court, London. Z  
**Electronics Hobbies Fair** Oct. 27-30. Alex Pavilion, London. Z1  
**Electronic Displays** Nov. 1-3. Kensington Ex. Centre, London. D4  
**Brainwave** (computing/video) Nov. 4-6. NEC Birmingham. G2  
**Compec** Nov. 15-18. Olympia, London. Z1  
**Northern Computer Fair** Nov. 24-26. Belle Vue, Manchester. Z1  
**Intron** Nov. 22-24. RDS Hall, Dublin. V  
**Automatic Testing/Test/Instruments**. Dec. 13-15. Metropole, Brighton. D4

A7 Institute of Acoustics ☎ 031-225 2143  
 B9 Cyril Bogod, British Am. Elect. Club ☎ 0222 707813  
 D4 Network ☎ 02802 5226  
 E Evan Steadman ☎ 0799 22612  
 E2 BARTG 89 Linden Gdns., Enfield, Middx.  
 F5 Cable & Satellite ☎ 01-487 4937  
 G2 Clapp & Poliak ☎ 01-747 3131  
 I Industrial Trade Fairs ☎ 021 705 6707  
 I2 Alan Taylor ☎ 01-486 1951  
 J3 Computer Marketplace ☎ 01-930 1612  
 L2 D. T. Wilson, 4 Conway Ave., Peterborough  
 M Montbuild ☎ 01-486 1951  
 O Online ☎ 09274 28211  
 Q Exhibitions for Industry ☎ 08833 4371  
 T Trident ☎ 0822 4671  
 V SDL Exhibitions ☎ Dublin 763 871  
 Z BETA Exhibitions ☎ 01-405 6233  
 Z1 IPC Exhibitions ☎ 01-643 8040

## COMPACT DISC SYSTEMS

This year's Spring Trade Shows saw the arrival of the audio compact disc (CD), the revolution in recorded sound. Since its launch back in March of this year every major record company has announced that it will enthusiastically support the CD format.

It is estimated that over 1000 titles will be available by the end of the year and most of these will be made in Hanover, West Germany by PolyGram but plans are already underway by two UK manufacturing companies to establish CD pressing plants in this country.



The Fisher AD800

The real breakthrough with CD has been that both the hardware and software producers worldwide have accepted the format originally developed jointly by Sony and Philips as the world standard with over 30 manufacturers now licensed.

Although at around £500 the systems are expensive many retailers believe the sales of CD units will be followed by an increase in speaker and amplifier sales because many people will prefer to buy their new systems from scratch.

For this reason Philips have produced a "flat membrane" range of speakers which they have designed for use with CD. The company say the new speakers reduce distortion and improve the overall sound quality when compared to normal speakers on both CD and conventional systems.

Another manufacturer following this line of thought is Pioneer who have updated their HPM series of speakers with power capabilities ranging from 90W to 240W.

Included in the wide range of models on show were the Fisher AD800, the Marantz CD-73 and the Hitachi DA100.

The Fisher AD800 model is fitted with a detachable storage unit which can hold up




The Marantz CD-73

to five discs and enables the AD800 to fit a 19in. rack system. Once the disc is placed in the holder it is automatically taken into the unit and the front loading door closed. The AD800 allows easy selection search of 16 tracks in any sequence and touch controls include fast forward, reverse/play/pause and stop. Priced at £479.95 inc. VAT the AD800 comes complete with the ADP105 CD storage unit.

The Marantz CD-73 system is a drawer loading unit which can be programmed to play track selections in any order, to skip specific tracks or to repeat them. The CD-73 is priced at £559.90 including VAT.

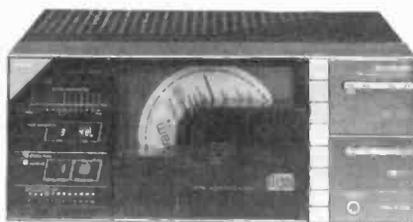The Hitachi DA100 also has random programming and skip features and includes a disc scan facility which when used will give a brief sample of the current disc program and then advances to a point 30 seconds ahead on the disc and plays another brief sample. The DA100 is priced at around £500.



The Hitachi DA100

## SORD GAMES

The home computer market abounds with versatile machines competing for our custom and the M5 is no exception. Manufactured by Sord of Japan and marketed in the UK by Computer Games Ltd its graphic capabilities will undoubtedly be the main selling point. With sixteen colours available the user will be able to create impressive animations from scratch or by using a pre-programmed cassette. With a BASIC 1 manual, p.s.u., connecting leads and two game cassette the M5 will retail at around £190 inc VAT.

Interestingly, 'joypads' will also be available—the joy 'stick' being replaced by a rather large button which when pressed at the relevant point on its circumference will transfer that directional information.

Also from CGL are a range of chess computer games including the Pocket Micro with a folding board. Players will be able to interrupt a game at any stage, pack it away and re-start at a later date. This feature will make the game unique, it will retail at around £32.




## MINI-MINDER

With the ever-increasing popularity of home intruder detection systems comes the inevitable jockeying for market position by the manufacturers.

Songuard are offering a system which incorporates an ultrasonic device that can be placed where protection is needed without actually running any wires. Known as the Songuard Bug it will act as a miniature detector and can be attached to doors, win-

dows, cupboards or even the jewellery box. What's the catch? Well the only non-wiring is between the device and its receiver, but it is indeed a very handy contrivance. The freestanding detector and alarm unit will retail at around £169.

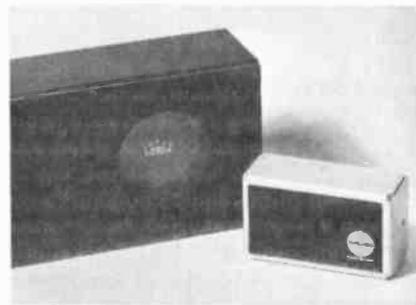The Songuard system is modular and also includes personal attack buttons, entry/exit keyswitch units and internal/external siren units. All auxiliary paraphernalia is also available from Songuard, Sales and Service, Mill Mead, Staines, Middlesex (0784 62016).



# TRADE SHOWS

## WATER BABY

Remember when the Walkman units first encouraged us to whistle while we worked, or jog with Jimmy Young? Well if you so desire you can now sing in the surf with a completely water-proof and sand-resistant model. The Sony Sports Walkman WMF5 has a disc drive system designed to reduce distortion. It incorporates an FM tuner and belt-clamp.

The Walkman will soon be available from retailers at around £111.

On the other side of the micro-electronic fence comes a new range of calculators from Sharp. A series of packs is the latest idea and besides the usual scientific types we now have one for the shopper, motorist, student, handyman, salesman and lady. There is also of course the inevitable school-pack which includes the ever-popular ruler, protractor and compasses etc. Function permutations are immense and it seems to make good sense to keep calculators simple and direct the resultant machines at a particular market requirement, hence the new range.



## HOME PHONE SYSTEMS

The telephone which seems to have been forgotten by everyone as a consumer product has recently been enjoying a revival of interest due to two new designs from Fidelity Radio.



The Wanderer

The first is the Fidelity Wanderer a completely cordless handset which can be used up to 200 metres from its base unit. The base unit itself is plugged into the normal BT socket and is also connected to the mains. The cordless handset incorporates a push-button dialling system and operates on frequencies of 47.46/47.54 MHz from the handset to the base and 1.642/1.782



The CRP 100

MHz from the base to the handset. The unit also features a unique digital coding system to prevent unauthorised dialling from other handsets in the same locality, a single push-button redial facility, a memory which stores a number entered whilst the phone is in use (ideal for Directory Enquiries), a call button on the base unit to page the handset user and an automatic recharging system for the Ni-Cad batteries. The Wanderer will retail at around £170.



The TAS-1G

The second design is the clock radio phone, the CRP 100, which incorporates the three facilities of a radio, alarm clock and telephone in one unit. It operates in precisely the same way as a conventional clock radio but has an automatic cut off when the telephone receiver is lifted. The radio operates an LW, MW and FM with selector switches for the radio, alarm radio, alarm buzz and off. A snooze touch sensor is provided and the readout is from a red l.e.d. display.

The TAS-1G from Sanyo is a basic telephone answering system which has several interesting features particularly its ability to detect the pay-tone from call-boxes. The machine accepts the call but automatically pauses until the pay-tone has finished before giving its recorded message. This avoids the caller losing part or possibly all of the message whilst the coins are being inserted. It will retail at around £148.

## NO CHARGE

Rechargeable batteries are becoming increasingly popular and Sanyo, the largest manufacturer of Ni-Cads, have experienced a doubling of demand over the last year for batteries and chargers in the UK.

To maintain their market position Sanyo have updated their Cadnica range of batteries, improving their sealing so they remain leakproof longer and enhancing the

overcharge and overdischarge (forced discharge) resistance. A typical forced discharge occurs when batteries with different levels of charge are not fully recharged and therefore balanced before being used in one piece of equipment.

Sanyo have also introduced a new universal multicharger, the NC1239, which is capable of charging every battery in their range, whilst the NC-AM1 charger for HP7 batteries is a solar powered system which is driven by a high power solar panel developed by Sanyo.





# *Simple* **SOLAR POWERED PROJECTS**

**R.A. PENFOLD**

**O**N the face of it there is no point in having designs for solar powered projects since any electronic project could be powered from a suitable array of solar cells. While this is indeed true, it does not take into account the fact that most solar cells are only capable of providing quite small currents, and all solar cells provide a modest output voltage of only about 500 millivolts. Most electronic projects would, therefore, require a large array of medium or high current cells in order to produce sufficient power, even under good operating conditions.

Although the difference in cost between solar cells and ordinary batteries has tended to reduce over the years, for most purposes a large array of solar cells is not a practical proposition. Of course, all these projects can be battery operated if so desired.

## **M/W RADIO**

**T**HE MW radio, like the other five projects in this set, has been designed to operate at low levels of supply voltage and current. In fact, this receiver will operate quite well at a supply voltage of 1 volt with a current consumption of under 1 milliamp. In other words it requires an input power of under 1 milliwatt for satisfactory results! Under reasonably bright conditions this enables the set to operate from just two small solar cells.

### **THE CIRCUIT**

The receiver is a simple MW Band type which has a ferrite rod aerial and an output which is intended to drive a crystal earphone (and which is unlikely to be suitable for any other type of earphone or headphones). Circuits using a couple of silicon transistors were tried, but the final design gave significantly superior results using a ZN414 plus a single transistor audio stage, and the full circuit of the set is shown in Fig. 1.

The ZN414 is ideal for this type of application as it gives a level of performance which is superior to that provided by most discrete T.R.F. designs, and it requires a nominal supply potential of only about 1.2 volts at a supply current of approximately 1 milliamp. It provides r.f. amplification, a.m. demodulation, and a simple automatic gain control (A.G.C.) action.

The ZN414 has a high input impedance so that it can be fed direct from the tuned winding of the ferrite aerial and the low impedance coupling winding is left unused. R1 is used to bias IC1 via the aerial winding (so that this resistor does not shunt the input impedance of IC1), and C1 couples one end of the ferrite aerial to the negative supply rail. R2 is the load resistor for IC1 and C2 is the r.f. filter capacitor for the detector stage of IC1. Note that IC1 obtains its positive supply only via R2 and there is no direct connection from IC1 to the positive supply rail.

The audio output level from IC1 is up to about 30

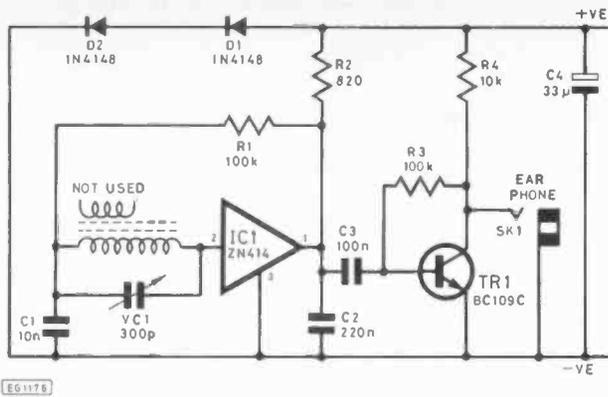


Fig. 1. Circuit diagram of the MW Radio

millivolts r.m.s., and this is just about sufficient to drive a crystal earphone at reasonable volume. However, better results are obtained using a small amount of audio amplification, especially when receiving weaker stations or when the supply voltage has fallen to a barely adequate level.

A simple common emitter audio amplifier based on TR1 is therefore used to boost the output from IC1. An amplifier of this type would normally be expected to have a voltage gain of about 40dB (one hundred times) or more, but in this case the voltage gain obtained is only about 20dB (ten times) or

response time of solar cells, and C4 should give adequate smoothing when necessary.

### CONSTRUCTION

With the only exceptions being the earphone socket (SK1) and solar cells the components are mounted on the printed circuit board. Details of the printed circuit are shown in Fig. 2 with the component layout shown in Fig. 3.

The specified tuning capacitor requires a single 10mm diameter mounting hole, and the mounting bush and nut of this component can be used to effectively bolt the completed board inside the case. Note that the case must be made from a non-metallic substance, otherwise it will screen the ferrite aerial and prevent any signal pick-up. With a little ingenuity it should be possible to use any variable capacitor having a maximum value of about 250p to 350p in the VC1 position.

The ferrite aerial used in the prototype is an Ambit MWC2 aerial coil fitted on a 140mm x 9.5mm ferrite rod which is in turn mounted on the printed circuit board using a pair of plastic mounting clips. These are bolted to the board using short 6BA bolts and fixing nuts. The set also works well using a Denco MW5FR ferrite aerial (which comes complete with a 140mm long ferrite rod), and this can be mounted on the board using a couple of large "P" type cable grips. The unit should, in fact, work perfectly well using any normal

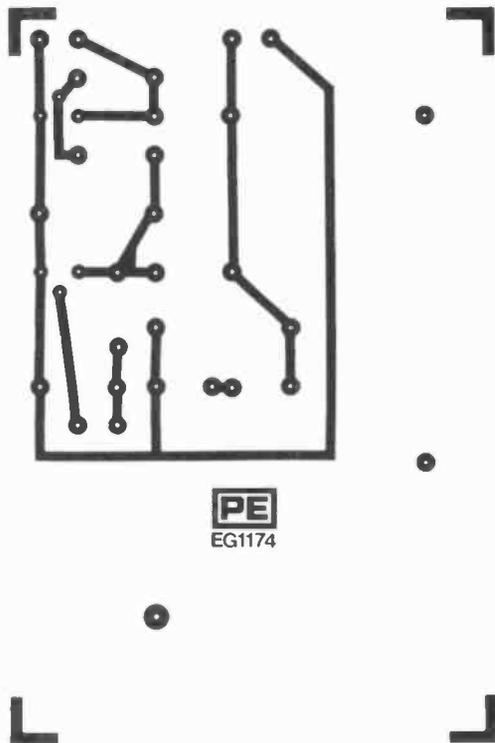


Fig. 2. P.c.b. design

so due to the very low levels of collector current and voltage that are used.

D1 and D2 are used to prevent the supply voltage from exceeding a suitable level, and C1 is a supply decoupling and smoothing capacitor. The output from the solar cells can contain a certain amount of noise, including mains hum if an artificial light source is used to power the circuit. Noise is not too much of a problem, though, mainly due to the very slow

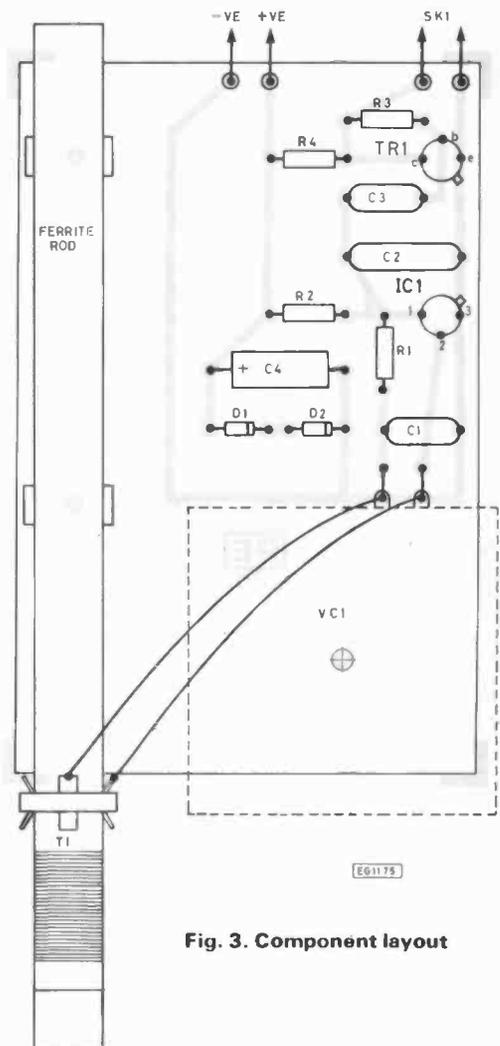


Fig. 3. Component layout

medium-wave ferrite aerial. Whatever aerial is used, only the larger winding is used and the small coupling winding is either removed or just ignored.

It is possible to use a shorter ferrite rod if a 140mm type will be too long to fit in the selected case. It is also possible to break a piece from a ferrite rod to shorten it, but sawing through the rod is practically impossible as ferrite is an extremely hard material. The rod can usually be persuaded to break at the desired point by filing or cutting a groove around the rod at this point, but great care must be taken when breaking the rod. It can easily take three whole rods to make one half if due care is not taken. Do not use a ferrite rod of less than about 75mm in length.


Obviously the solar cells must be mounted on the exterior of the case with the sensitive surface facing outwards. The set will operate from a couple of MS4A solar cells in direct sunlight, even if this is of the weak winter variety. However, three cells give better results and enables the set to work even in bright overcast conditions. The solar cells are connected in series, and with the MS4A type the sensitive surface is the dark side of the component. It is the negative leadout wire which connects to this side of the cell and the positive leadout which connects to the underside of the device.

As the circuit has such a low current requirement it should be possible to use any other solar cells as a power source, although very high current types would not be a very practical choice. Medium current types do not really have any advantage over low current types in applications where only a low current is required. The output voltage from a solar cell remains virtually constant as the load current is increased until a certain threshold level is reached, and the output voltage then falls sharply with the output current remaining virtually constant. If the light level received by the cell is reduced this gives a reduction in the output voltage, and the voltage obtained will be virtually the same whether a low or high current cell is used.

For operation in relatively low light levels it is therefore necessary to use several cells in series rather than just using two or three high current cells. Using a dozen or more cells in series is not an economically attractive proposition, but inexpensive 6, 9 and 12 volt solar panels are available and represent a more practical alternative. Using a 9 volt panel it was found to be possible to operate the set even on a dull winter day, or from artificial light (which provides a similar light level).
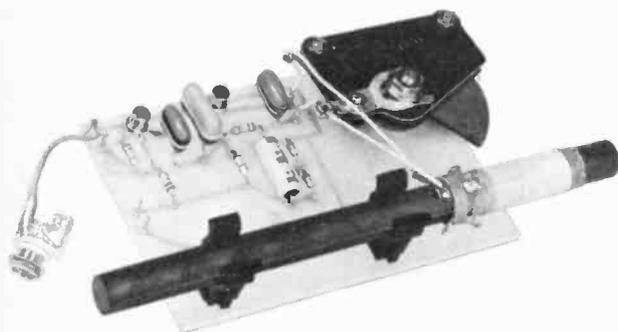
#### IN USE

The position of the coil on the ferrite rod controls the frequency coverage of the receiver to some extent, and the coil must be placed in a position that permits full coverage of the band. VC1 gives slightly more than complete coverage of the



## COMPONENTS . . .

### Resistors

R1, R3	100k (2 off)
R2	820
R4	10k
All resistors $\frac{1}{4}$ W 5% carbon	

### Capacitors

C1	10n polyester
C2	220n polyester
C3	100n polyester
C4	33 $\mu$ 16V axial elect

### Semiconductors

D1, D2	1N4148 (2 off)
TR1	BC109C
IC1	ZN414

### Miscellaneous

	Medium wave ferrite aerial with mounting clips
VC1	300p solid dielectric (Jackson Dilecon)
SK1	3.5mm jack socket
	Printed circuit board
	Control knobs
	Three MS4A solar cells or solar panel (RK23A)
	Wire, solder, etc.

### Constructor's Note

The solar power cells MS4A and panels are available from **Maplin Electronic Supplies Ltd., P.O. Box 3, Rayleigh, Essex.**

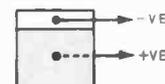
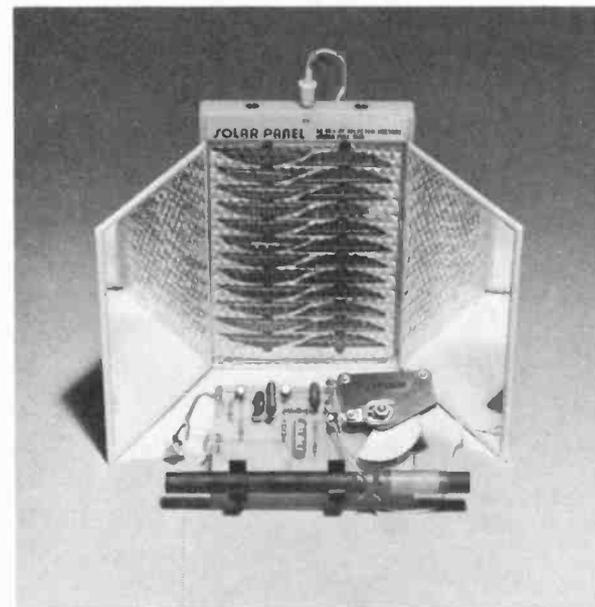


Fig. 4. Connection diagram for the MS4A solar cell

EG1203

MW Band, and this slight excess of coverage prevents the positioning of the coil from being too critical.

Despite the simple A.G.C. action of the ZN414 the set can be overloaded in strong reception areas, but if necessary the directivity of the ferrite aerial can be used to reduce the strength of received signals. ★

# SOIL MOISTURE METER

A SOIL moisture meter is really just a form of resistance indicator, and units of this type rely on the fact that the resistance through dry soil is very much higher than the resistance through a comparable sample of moist soil. Soil moisture meters are used primarily with potted plants where the surface of the soil can be very dry even though the soil only a little deeper may be quite wet. This can lead to over-watering and possibly the demise of the plant. The probes of a soil moisture meter avoid this by penetrating about 25 to 50mm below the surface of the soil so that the moisture reading obtained does not just indicate the moisture content of the surface soil, and can be used as a reliable guide.

Circuits of this kind indicate the soil moisture content in a variety of ways such as producing an audio tone that rises in pitch with increasing moisture content, or having a l.e.d. indicator which flashes at a rate that depends on the water content of the soil. A number of systems were tried, and the one finally adopted was to simply use a low cost moving coil meter to provide the moisture indication. This may seem less imaginative than the alternative methods, but it gives a clear and unambiguous indication of the soil's moisture content, and it enables a low voltage low current circuit to be used.

## THE CIRCUIT

The very simple circuit of the Soil Moisture Meter appears in Fig. 1. Using a circuit consisting merely of the probes and the meter connected in series across a low voltage supply was found to give a slightly inadequate level of sensitivity. The final circuit, therefore, uses an emitter follower buffer stage to drive the meter, and R2 is used to shunt the input of this stage so that the sensitivity of the unit can be adjusted and set at a level that makes it easy to interpret meter readings.

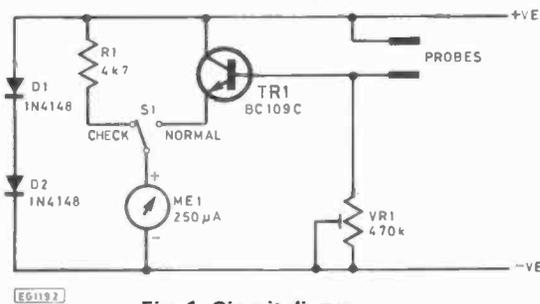


Fig. 1. Circuit diagram

D1 and D2 stabilise the supply voltage at about 1.3 volts so that consistent results are obtained. S1 can be used to switch ME1 across the supply lines (via series resistor R1) so that a check to ensure that an adequate supply voltage is present can be made.

Under direct sunlight two solar cells in series are sufficient to power the circuit, but it would probably be better to use three cells in series as the unit would then operate on any reasonably bright day. Using a solar panel as the power source, the unit would operate under comparatively dim conditions, and the actual power level taken by the circuit is only about 0.5mW or less.

## CONSTRUCTION

Fig. 2 shows the printed circuit design for the Soil Moisture Meter. If the specified meter is used the completed board can be soldered onto the tags of the meter, and the tags can be bent through 90 degrees so that the board fits

vertically behind the meter. It should be possible to use any meter having a full scale deflection sensitivity of about 1mA or less.

The probes can be made from a pair of inexpensive test prods of the type sold as replacements for multimeters. The two prods must be fixed together so that they are a constant distance apart when measurements are made and consistent results are obtained. There should be no problem in gluing or taping the two prods firmly together. Of course, any similar arrangement which provides a couple of thin metal prods about 25 to 50mm long should work equally well.

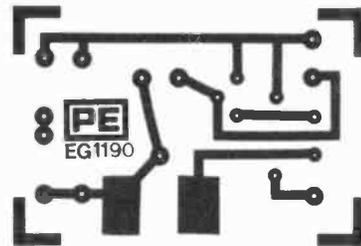


Fig. 2: P.c.b. design

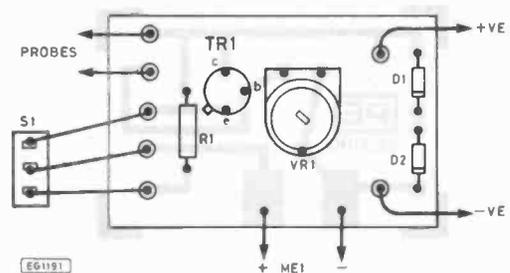


Fig. 3. Component layout

## ADJUSTMENT

It is important to carefully adjust VR2 to give the unit a suitable level of sensitivity if the unit is to give useful and helpful results. The most reliable way of setting VR2 is to first set up a few samples of soil having various moisture levels. VR2 should be given a setting that only gives a large deflection of the meter with the probes pushed into moist soil

## COMPONENTS . . .

### Resistors

R1	4k7 1/4W 5% carbon
VR1	470k 0.1W hor. preset

### Semiconductors

D1, D2	1N4148 (2 off)
TR1	BC109C

### Miscellaneous


ME1	250µA moving coil meter (Maplin, see text)
S1	Toggle, push-button or slider type switch s.p.d.t.

Pair of test prods and leads

Printed circuit board

Three MS4A solar cells or solar panel (Maplin)

Wire, solder, etc.

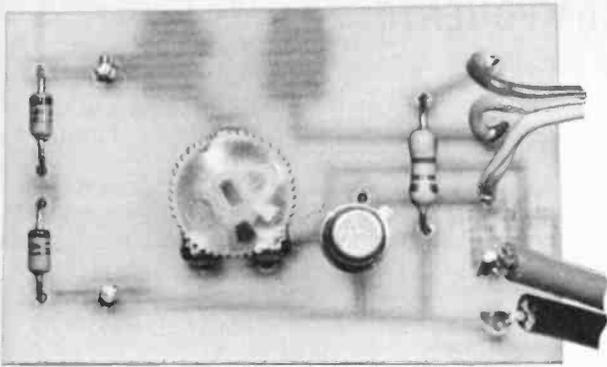

samples. The purpose of the unit is really to indicate whether or not the soil is excessively dry rather than how wet it is,

## THERMOMETER

THIS thermometer covers a range of zero to one hundred degrees centigrade, and despite the simplicity of the circuit it provides accurate results that are primarily limited by the accuracy with which the meter can be read. The sensor is a silicon diode which can be located remotely if desired, and connected to the rest of the circuit by a twin lead.

The circuit is designed to be powered from a solar panel, but a supply potential of only about 1.2 volts at a current of approximately 1.2 milliamps is required and the unit could be powered from three small solar cells under reasonably strong light.

### THE CIRCUIT

A simple bridge circuit is used, and the circuit diagram of the thermometer appears in Fig. 1. One side of the bridge circuit is formed by R4 and sensor diode D2. The latter is forward biased and a potential of about 0.6 volts is therefore produced across this component, but the precise voltage produced will vary slightly from one component to another, and more importantly, it varies with temperature. A reasonably linear relationship between temperature change and voltage change is obtained, with increased temperature giving a reduction in voltage. However, the voltage change is not very great, and is likely to be only about 2 millivolts or so per degree centigrade. With a thermometer that covers a range of one hundred degrees centigrade this gives a voltage swing of about two hundred to two hundred and fifty millivolts over the full temperature span, and this is sufficient to drive a moving coil meter without the need for any amplification.


The second section of the bridge circuit is formed by R1,

and with the unit adjusted in this way a low reading on the meter will indicate that watering is needed. Always make sure that the probes are pushed right down into the soil and are making good contact with it.

With the solar cells subjected to a strong light level, set S1 to the "check" position and make a note of the reading on the meter (this should be about 80 or 90% of full scale deflection). On any future occasions when the unit is used, if there are any doubts about the adequacy of the light level the battery check facility can be used to check the supply voltage, and the reading obtained should not be substantially lower than that obtained when making this initial trial. Note that the value of R1 will need to be altered if a meter having a full scale sensitivity other than  $250\mu\text{A}$  is used, and the change in value is inversely proportional to the change in meter sensitivity (e.g. R1 should be about 1k $\Omega$  using a 1mA meter. ★



R2 and VR1 is adjusted so that the bridge is balanced and the meter reads zero with D2 at zero degrees centigrade. If the sensor is then raised in temperature the voltage at the negative terminal of ME1 reduces, and a forward deflection of the meter is produced. VR2 is adjusted to give the circuit the correct sensitivity so that (say) a fifty degree rise in temperature would give a reading of fifty microamps on ME1. The existing zero to one hundred scale of the meter can therefore be retained.

It is essential for the supply fed to the bridge circuit to be extremely stable indeed as a change in supply voltage of just a few tens of millivolts would give a significant change in the reading on ME1 and hopeless accuracy. Using a simple shunt regulator circuit with a couple of forward biased silicon diodes in series would not be adequate in this case, and it is necessary to use a precision, temperature compensated, voltage reference. D1 is a precision 1.2 volt shunt stabiliser, and R5 is its load resistor. D3 ensures that the input potential cannot rise to a level that would produce an excessive current through D1 and a consequent loss of regulation efficiency.

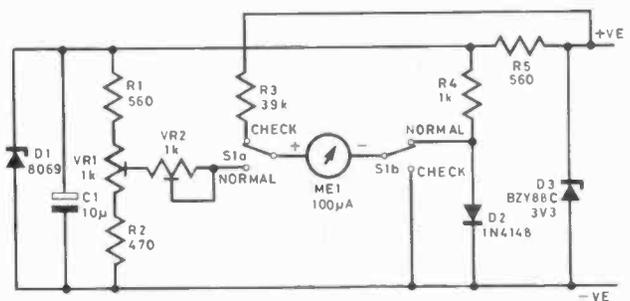

EG1179

Fig. 1. Circuit diagram

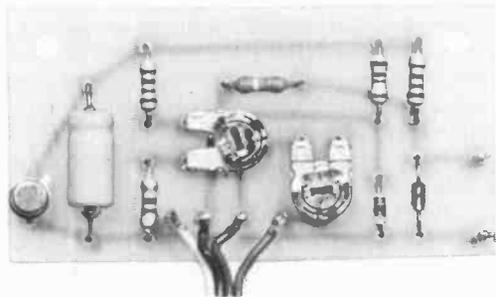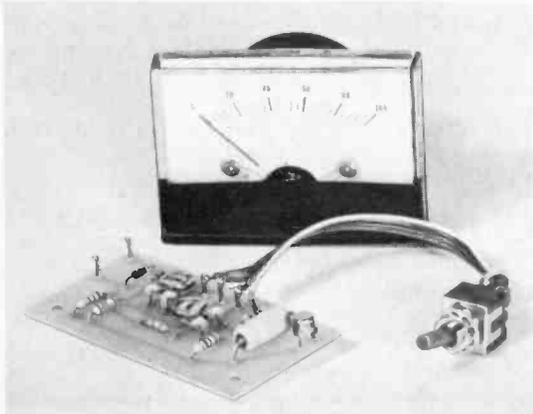

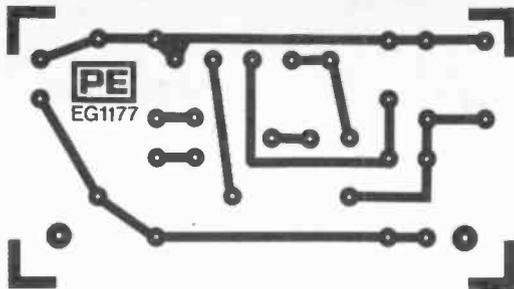


Fig. 2. P.c.b. design

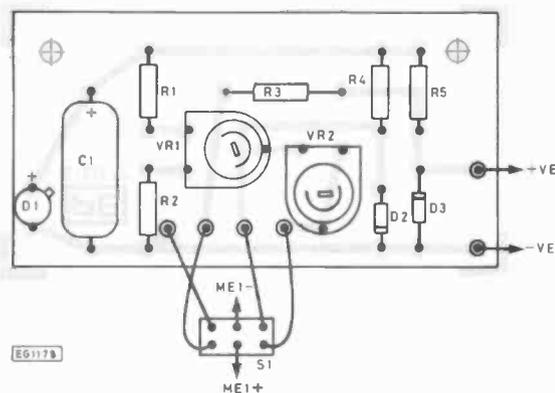


Fig. 3. Component layout

If the circuit is operated from three small solar cells in series (such as MS4As) D3 can be omitted since the available supply current would be inadequate to overdrive D1. R5 should be reduced to about 56 ohms in value as well.

S1 can be used to connect ME1 across the input from the solar cells, and series resistor R3 gives ME1 a full scale sensitivity of about 4 volts. This enables a check to be made to ensure that an adequate input voltage is present.

### CONSTRUCTION

The printed circuit design and wiring are shown in Figs. 2 and 3. Sensor diode D2 is shown as being mounted on the printed circuit board, but as mentioned earlier, it can be remotely located and connected to the main unit via a twin cable if desired. Even if it will eventually be mounted on the board it is a good idea to initially connect it to the board by way of a twin lead about half a metre or so in length as this

## COMPONENTS ...

### Resistors

R1, R5	560 (2 off)
R2	470
R3	39k
R4	1k
VR1, VR2	1k 0-1W hor. preset (2 off)
All resistors $\frac{1}{4}$ W 5% carbon	

### Capacitor

C1	10 $\mu$ 25V axial elect
----	--------------------------

### Semiconductors

D1	8069 precision 1.2 volt reference
D2	1N4148
D3	BZY88C3V3 3.3 volt 400mW Zener

### Miscellaneous

ME1	100 $\mu$ A moving coil panel meter
S1	Miniature toggle type d.p.d.t.
Solar cells or solar panel (Maplin)	
Printed circuit board	
Wire, solder, etc.	

will make it easier to set-up the unit ready for use.

Initially VR1 should be set with the wiper at about the middle of its track, and VR2 should be adjusted for maximum resistance (set fully anticlockwise). With D2 placed in ice cubes or iced water to reduce its temperature to zero centigrade and S1 set to the "normal" position, with power connected to the circuit VR1 should be adjusted immediately to zero the meter. D2 is then placed in warm water to increase its temperature to anything from about 50 to 100 degrees centigrade, but a thermometer must be used to measure the temperature of the water so that VR2 can be adjusted to give the appropriate reading on ME1. This procedure should then be repeated a few times to make sure VR1 and VR2 are set accurately.

With S1 placed in the "check" position ME1 should read at least half full scale deflection, and there is inadequate voltage from the solar cells if it does not. If the unit is powered from three small solar cells a slightly lower reading of about 30% of full scale deflection is acceptable. If this method of powering the unit is adopted it is a good idea to check the reading obtained with the cells in direct and fairly strong sunlight. If a significantly lower reading is obtained at some later occasion the supply potential is inadequate. ★

# INEBRIATION DETECTOR

THIS inebriation detector is really a simple reaction testing game using a row of eight light emitting diodes to give a relative indication of the operator's reaction speed. The unit is very simple to use, and about ten seconds after switch-on the first l.e.d. in the display switches on, and a push button switch must then be operated as quickly as possible. Soon after the first l.e.d. has switched on it cuts off again and the second l.e.d. lights instead, then this l.e.d. cuts off and the third l.e.d. lights up, and so on with the light appearing to move along the display. Operating the push button halts the display, and the quicker the button is operated the less far the light will have progressed along the display. Thus any degradation in reaction speed due to the consumption of alcohol can be detected.

To start a new sequence the push button is released, the

circuit is reset by switching off, and a new cycle commences when the unit is switched on again. The push button must be held down until the score has been read from the display as the display will continue to operate when the button is released.

This circuit requires somewhat more power than the other five solar powered projects, but it still only requires about 4 to 9 volts at a few milliamps in order to operate reliably. It can therefore be powered from a 6 or 9 volt solar panel in reasonably strong light.

### THE CIRCUIT

The circuit is comprised of two main stages: a clock oscillator and the display driver. Fig. 1 shows the full circuit diagram of the Inebriation Detector.

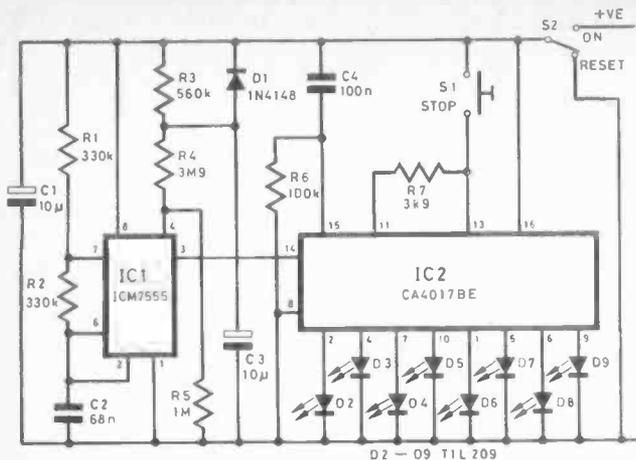


Fig. 1. Circuit diagram

The clock oscillator uses an ICM7555 (IC1) and this also provides the delay between switch-on and the display starting to count. IC1 is used in what is virtually the standard 555 astable configuration, and the values used for timing components R1, R2 and C2, give an operating frequency of about 20 hertz. With an eight i.e.d. display and human reaction times normally between about 200 and 400 milliseconds, this clock frequency should be suitable, but if necessary the clock can be made to run a little faster by reducing C2 to 47n, or a little slower by increasing it to 100n.

The clock oscillator is given a switch-on delay by providing a suitable control voltage to pin 4 of the device using a simple C-R timing circuit. Operation of IC1 is blocked if pin 4 is taken to less than about 0.5 volts, and at switch-on R5 takes this terminal to the negative supply

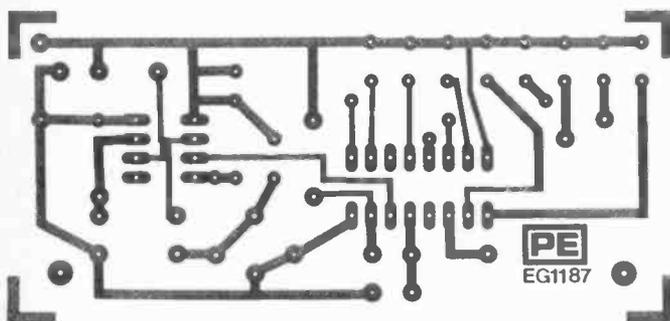


Fig. 2. P.c.b. design


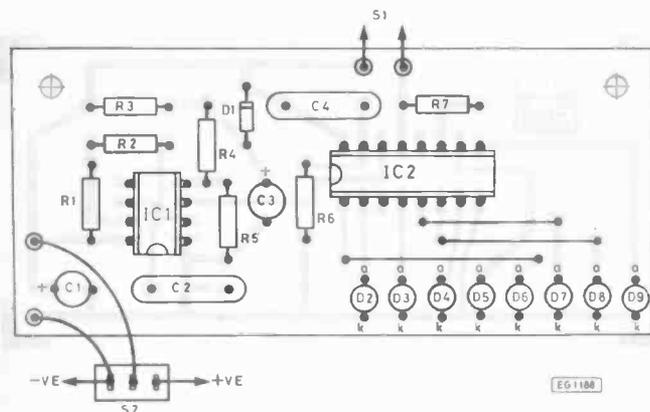


Fig. 3. Component layout

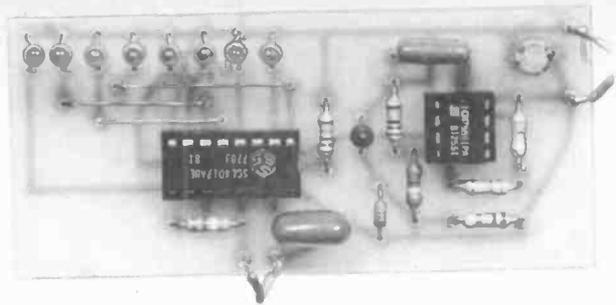

potential so that oscillation is blocked. However, as C3 charges via R3 part of the potential across C3 is fed to pin 4 of IC1 by the potential divider formed by R4 and R5. After approximately ten seconds the potential at pin 4 becomes sufficient to activate IC1 and the clock signal is produced at pin 3 of the device.

It is impossible to specify the switch-on delay time with any degree of accuracy since it varies considerably with fluctuations in the supply voltage. However, this is not really a disadvantage since it makes it impossible to predict the time when the display will start to operate and prevents contestants from obtaining low scores by having good anticipation rather than good reactions.

A CMOS 4017BE is used as the display driver, and at switch-on this is reset by the positive pulse generated by C4 and R6. Output "0" of the device then goes high while the other nine outputs are low. There is no i.e.d. connected to this output of the device (pin 3) and all eight display i.e.d.s are therefore switched off at this stage.

When the clock oscillator starts to operate, the 4017 is incremented by each clock pulse. Thus the first clock pulse causes output "1" to go high and D2 is switched on, the next clock pulse sends output "2" high and D3 switches on in place of D2, then output "3" goes high and D4 switches on, and so on. This continues until S1 is operated so that the

## COMPONENTS . . .

### Resistors

R1, R2	330k (2 off)
R3	560k
R4	3M9
R5	1M
R6	100k
R7	3k9
All resistors 1/4W 5% carbon	

### Capacitors

C1	10µ 16V radial elect
C2	68n polyester
C3	10µ 16V tantalum
C4	100n polyester

### Semiconductors

D1	1N4148
D2 to D9	TIL209 3mm red i.e.d.s (8 off)
IC1	ICM7555
IC2	4017BE

### Miscellaneous

S1	Push to make, release to break type
S2	Miniature toggle switch s.p.d.t.
	Printed circuit board
	Solar panel (Maplin)
	Wire, solder, etc.

clock inhibit terminal of IC2 is taken high and the counting action is halted. The display then stops, and whatever I.e.d. happened to be switched on at the instant S1 was operated remains switched on so that the player's score is shown on the display.

If S1 is operated too slowly, output "9" of IC2 (pin 11) goes high, and due to the coupling through R7 it takes the clock inhibit terminal high so that the count is halted and the display does not continuously cycle through "0" to "9". This prevents a score from being obtained if S1 is operated too slowly.

When S2 is set to the "reset" position a short circuit is placed on the supply lines so that C1 and C4 discharge fairly rapidly, and the unit operates properly when S2 is set back to the "on" position. D1 is included so that C3 is also discharged and a new switch-on delay is produced when the unit is switched on again.

### CONSTRUCTION

Construction of the unit is quite straight forward using the printed circuit design shown in Fig. 2. Note that there are three link wires on the board (Fig. 3) just above the display I.e.d.s. IC2 is a CMOS device and the usual MOS handling precautions should therefore be implemented, and IC2

should be fitted in a 16 pin d.i.l. socket. IC1 is also a CMOS component, but it has internal protection circuitry which renders MOS handling precautions unnecessary. As the ICM7555 is not the cheapest of i.c.s it is still probably worthwhile using a socket for this device.

As mentioned earlier, a solar panel is probably the best power source for this project since it would be uneconomic to buy a sufficiently large number of single cells (at least eight would be needed). The solar panel could be mounted on the case of the unit, but in use it would probably be more convenient to leave the inebriation detector and solar panel as separate units. The panels are provided complete with about one metre of twin cable, and this can be terminated in a 3.5mm jack plug with a matching power socket being mounted on the case of the inebriation detector.

If the output from the panel falls to an inadequate level either no operation at all will be obtained, or the first I.e.d. in the display might light up after the switch-on delay, but loading of the supply will produce a large voltage drop which will result in the display progressing no further. Adding a capacitor of about 680µ in value across the solar panel helps to give proper results in marginal lighting conditions, but obviously this can be of no help if the light level is totally inadequate. ★

# CONTINUITY TESTER

THIS very simple continuity tester produces an audio tone when a suitably low resistance is present across the test probes, and unlike some continuity tester designs it will not indicate continuity if a forward biased silicon junction is placed across the test prods. This helps to avoid confusing results when checking complex circuit boards where there can be a large number of semiconductor junctions and continuity would otherwise be indicated between virtually any two points in the circuit!

In order to keep the voltage and current requirements of the circuit to a minimum, it is based on the LM3909N low power oscillator i.c. This gives a very high level of efficiency and the unit will produce an audio tone of moderate volume from an input of only about 1.3 volts at a supply current of around 3 milliamps.

Fig. 1 shows the LM3909N in block diagram form, and as can be seen from this, the device is little more than an electronic switch. The LM3909N can be used in a variety of configurations to suit particular applications, but it is always used in what is really a simple relaxation oscillator circuit.

### THE CIRCUIT

The full circuit diagram of the Continuity Tester is shown in Fig. 2. In this circuit the LM3909N is used in its most simple configuration, and although this does not give quite the efficiency of some of the alternative configurations, it gives good results and excellent reliability at very low supply voltages. All that happens using this arrangement is that C2 charges via LS1 and R1 until the control voltage for the electronic switch falls below the trigger threshold, and the switch then closes so that LS1 is effectively connected across the supply rails and therefore passes a high current. It is not necessary for the solar cells to be able to provide the full current required by LS1 since it is only a short pulse of current that flows, and supply decoupling capacitor C1 can provide some of this current. During the periods when the electronic switch is in the off state the current consumption of the circuit is quite low and C1 can then recharge so that it is ready to supply another current pulse when the switch closes again. The circuit will oscillate with C1 removed, but the volume obtained is reduced drastically.

The electronic switch does not hold in the on state because once it has closed C2 discharges through R1 and

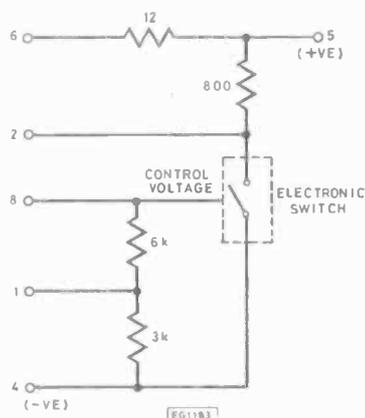


Fig. 1. Basic circuit

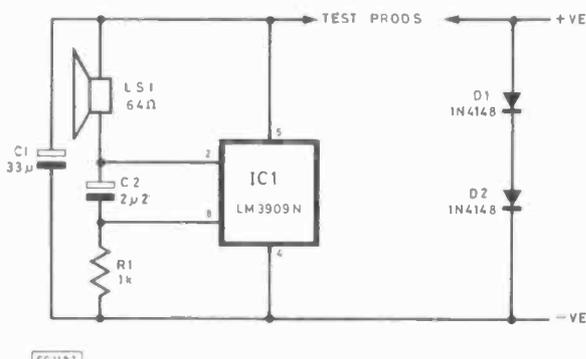


Fig. 2. Full circuit

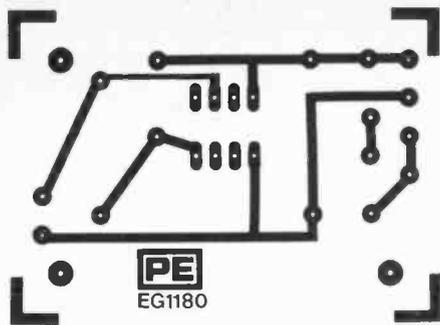


Fig. 3. P.c.b. design


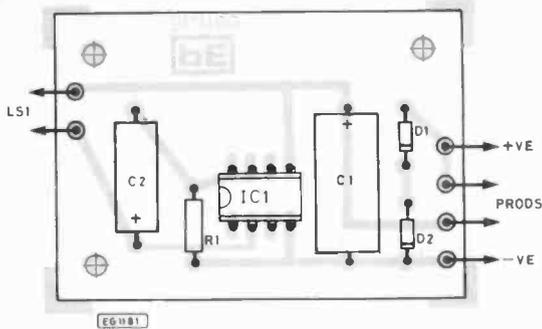


Fig. 4. Component layout

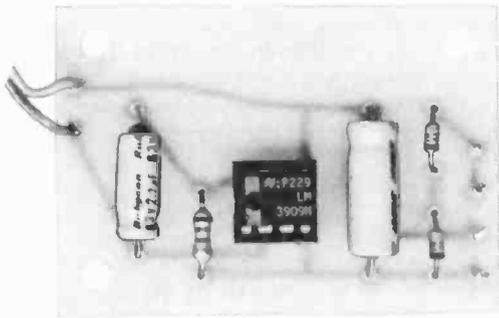

## COMPONENTS ...

### Resistor

R1 1k ¼W 5% carbon

### Capacitors

C1 33µ 16V axial elect  
C2 2µ2 63V axial elect

### Semiconductors

D1, D2 1N4148 (2 off)  
IC1 LM3909N

### Miscellaneous

LS1 64 ohm impedance miniature loudspeaker  
Test prods  
Printed circuit board  
Three solar cells type MS4A or solar panel (Maplin)  
Wire, solder, etc.

the switch until the control voltage goes above the switch-off threshold voltage. C2 then starts to charge via LS1 and R1 again, and continuous oscillation is produced.

D1 and D2 are used to limit the supply voltage to no more than about 1.4 volts. This is essential since the circuit will cease to operate if the supply voltage goes substantially above this figure.

## CONSTRUCTION

Details of the Continuity Tester printed circuit board are given in Fig. 3, and construction of the unit is perfectly straightforward (Fig. 4). The unit will work using an 8 ohm impedance loudspeaker for LS1, but this would increase the current consumption of the circuit and it is better to use a component having an impedance of 40 ohms or more.

In direct sunlight two small solar cells are sufficient to power the circuit, but three cells in series or a solar panel would be a more realistic power source.

The maximum voltage across the test prods is only about 1.4 volts and the maximum current flow between them is only about four milliamps or so. Both figures are sufficiently low to give no real risk of damaging delicate components when using the unit. ★

# TRANSISTOR CHECKER

SOLAR POWER has an obvious appeal for items of equipment that will receive only brief and intermittent use, and where the use of ordinary batteries would result in them running flat largely due to ageing rather than use. Solar cells are more expensive initially, but will go on operating year after year and have a certain novelty appeal as well.


A Transistor Checker is a good example of a piece of equipment in the category mentioned above. It is not a piece of test gear that is likely to be used every day, but on occasions a transistor checker of some kind is an essential piece of equipment. This simple design is a go/no go checker which can be used to test low, high, or medium gain devices, and an l.e.d. indicator light flashes on and off if the test device is serviceable. If the l.e.d. lights continuously the device under test has gone closed circuit, and if the l.e.d. fails to light the test device is open circuit.

The circuit requires a supply potential of 2 volts at a current of a few milliamps, and it could therefore be run from

four MS4A or similar solar cells under bright conditions. However, a 6 or 9 volt solar panel would permit operation under lower light levels and would be less expensive.

## THE CIRCUIT

Fig. 1 shows the circuit diagram of the Transistor Checker. The circuit is little more than an oscillator which pulses the base of the transistor under investigation with a small current, plus an l.e.d. indicator connected in the collector circuit of the transistor so that it lights up when the device is pulsed into conduction. The oscillator is based on an ICM7555 (IC1) and this has a couple of advantages over the standard 555 device in this application. One is simply that it requires a much lower supply current and will operate at a supply current of only about 50 to 100 microamps rather than the 5 to 10 milliamps required by the standard 555. Of greater importance though, the ICM7555 will operate from a supply potential of only about 2 volts which compares with

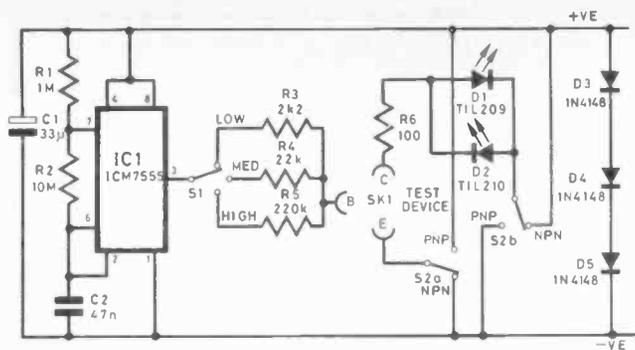

EG1186

Fig. 1. Circuit diagram

a minimum figure of about 5 volts for the 555.

IC1 is used in the standard 555 astable configuration, and timing resistors R1 and R2 have been given fairly high values in order to keep the supply current drawn by this part of the circuit down to a reasonable level. Timing capacitor C2 has a value which gives an operating frequency of nearly 2 hertz. R2 has been made fairly high in value when compared to R1 so that an almost squarewave signal is produced at the output of IC1. This signal has a peak to peak value that is virtually equal to the supply voltage, and it therefore switches the test device fully on and fully off so that unreliable and ambiguous results are avoided.

The output of IC1 is connected to the base of the device under test via whichever of the three resistors (R3 to R5) is selected using S1. With R3 in circuit the test device is fed with a base current of about 0.6 milliamps or so, and a current gain of only about 5 times or more through the test transistor is sufficient to give a collector current of a few milliamps and cause the i.e.d. indicator to light up.

With R4 switched into circuit the base current is reduced by a factor of ten, and the device under test then requires a current gain of about 50 or more in order to operate the i.e.d. indicator. With R5 switched into circuit the base current is reduced by a further factor of ten, and a current gain of about 500 times or more through the test device is needed in order to operate the indicator i.e.d. This gives only a very rough assessment of the current gain provided by the device being checked, but it does avoid the situation which can occur with some simple checkers where only a single base current is used, and a high gain device seems to be fully operational, whereas it actually has a very low level of current gain.

S2 is the npn/pnp mode switch, and one pole of this connects the emitter terminal of test socket SK1 to either the positive supply rail or the negative one, as appropriate. The other pole of S2 provides complementary switching in the collector circuit of the test device. In order to enable simple npn/pnp switching to be used, two i.e.d. indicators are incorporated in the circuit. D2 is connected with the correct polarity when the unit is used in the npn mode while D1 becomes operational in the pnp mode. These i.e.d.s are different colours so that they indicate the mode in use and help to prevent the unit from being used with the mode switch


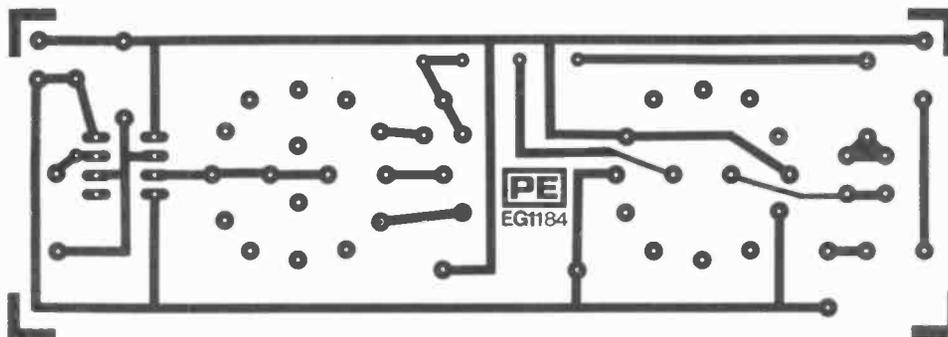
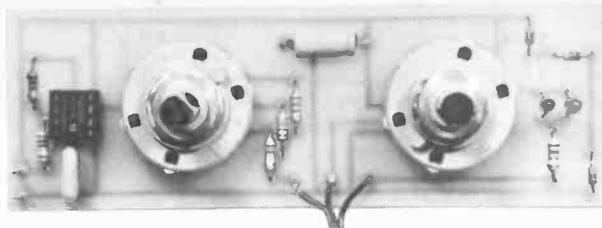


Fig. 2. P.c.b. design

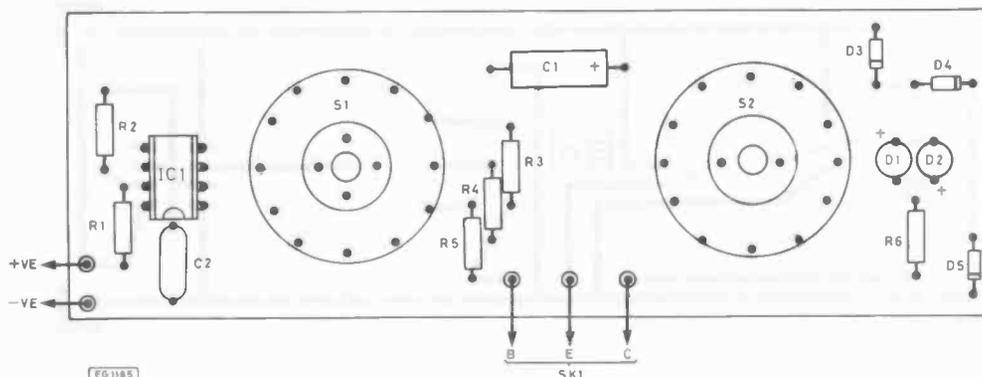

EG1185

Fig. 3. Component layout

inadvertently left in the wrong position. R6 is simply a current limiting resistor.

D3 to D5 are used to stabilise the supply voltage at about 2 volts so that a reasonably consistent base current is produced by the unit, even if a solar panel (which would otherwise give a very unstable supply voltage) is used as the power source.

### CONSTRUCTION

The printed circuit board for the Transistor Checker is shown in Fig. 2. This takes all the components apart from the solar cells and test socket SK1. The latter is a three way DIN type and most transistors can be plugged direct into one of these. A set of crocodile clip test leads must be made up so that other types can be connected to the unit.

If the two rotary switches used for S1 and S2 have printed circuit tags, they will fit onto the board without difficulty, but most component suppliers sell the type which has ordinary tags. It is possible to use this type of switch, but the ends of the tags must be cut off to leave what are effectively printed circuit pins, but do not remove any more of the tags than is absolutely essential. Push the switches right down onto the board before soldering them in place. The printed circuit board is mounted securely in the case when S1 and S2 are fitted onto the front panel, and no additional mounting of any kind is required.

The finished unit is very easy to use, but always make quite sure that S1 is set to a suitable position for the device being checked, and that S2 is set to the correct mode. Also make sure that the device under test is connected properly if D1 or D2 fail to flash on and off and the device appears to be faulty.

A simple way to check that the supply voltage is adequate is to simply place a short circuit across the emitter and

## COMPONENTS . . .

### Resistors

R1	1M
R2	10M
R3	2k2
R4	22k
R5	220k
R6	100

All resistors  $\frac{1}{4}$ W 5% carbon

### Capacitors

C1	33 $\mu$ 16V axial elect
C2	47n polyester

### Semiconductors

IC1	ICM7555
D1	TIL209 3mm red l.e.d.
D2	TIL210 3mm green l.e.d.
D3, D4, D5	1N4148 (3 off)

### Miscellaneous

S1	3 way 4 pole rotary switch
S2	6 way 2 pole rotary switch with adjustable end-stop
SK1	3 way DIN socket
	Printed circuit board
	Control knobs
	Solar panel (Maplin)
	Wire, solder, etc.

collector terminals of SK1. D1 or D2 (depending on the setting of S2) should light up if the supply voltage is adequate. ★

## PE SPECIAL CASSETTES OFFER

### CHROME C60 & C90

#### CR02 C60 CASSETTES

90p each (minimum of 5); 80p each (minimum of 25)

#### CR02 C90 CASSETTES

115p each (minimum of 5); 105p each (minimum of 25)

### FERRIC C90 AUDIO

#### C90LH CASSETTES

56p each (minimum of 5); 53p each (minimum of 25).

PRICES INCLUDE VAT AND POSTAGE.

These European-made tapes are excellent value and we are pleased to offer them to readers. They are covered by a money back guarantee (return within 21 days for refund). Not only are the tapes of high quality but the cassettes are of screw together construction and the case labels have space for notes on the recordings.

Send coupon to: Videotone Ltd., 98 Crofton Park Road, Crofton Park, London SE4.

Please send me ..... CR02 C60 Audio cassettes at ..... p each (90p for 5 to 24, 80p for 25 or more; including VAT and postage).

Please send me ..... CR02 C90 Audio cassettes at ..... p each (115p for 5 to 24, 105p for 25 or more; including VAT and postage).

Please send me ..... C90LH Audio tapes at ..... p each. (56p for 5 to 24, 53p for 25 or more; including VAT & postage.)

I enclose cheque/PO for £ ..... No. ....

Name .....

Address .....

BLOCK CAPITALS PLEASE

Coupon valid for posting before 5 Aug '83 (or one month later for overseas readers).

## EVERYDAY ELECTRONICS and computer PROJECTS

### ★ 1kW POWER CONTROLLER

Designed especially for dimming large filament lamps of the kind used for stage lighting

### ★ STORAGE 'SCOPE INTERFACE FOR BBC MICRO

Will be found useful when experimenting with musical sound effects, synthesiser and other sound generator circuits

### Plus

★ HOME SYSTEMS MONITOR

★ CAR INTRUDER ALARM

★ CIRCUIT EXCHANGE—

Readers' circuit ideas

AUGUST ISSUE ON SALE  
JULY 15

Place a regular order with your  
NEWSAGENT—Now!

# Space Watch...

## SHUTTLE 6 RE-ENTRY

The precisely guided re-entry of Challenger-6 into touchdown at the Edwards Air Force Base, California, at precisely 10.53 am, was a triumph for the team of Astronauts. They were Paul J. Weitz, USAF Col. Karol J. Bodko, Donald H. Peterson and Dr. Story Musgrave. This flight has increased the confidence in the procedures for the next Shuttle at Kennedy Space Centre, Florida.

Hypersonic and Supersonic manoeuvres carried out by the Shuttle were entirely satisfactory. They were carried out on re-entry before touchdown at Edwards Field. Confidence in the procedures for re-entry in the way of Lateral control, Stability and Reaction control were satisfactory, and so were the manoeuvres designed to check system capability and Rudder Authority.

There were three main questions to be answered about flight characteristics. These were designed to involve some thirty firings of jet-energy during descent. They were commanded instructions but were monitored by the astronauts for safety. The three hypersonic S-turns were made as is usual with re-entry. However, this time there were eight other sets of instructions to be accomplished.

The re-entry was made first at an angle of 40° as usual. The initial flight testing was made at 24,000 ft/s at an altitude of 261,000 ft. The test involved an aileron pulse followed by right-hand jet input as well as right-hand yaw jet pulse input. The crew then fired the orbital system engines for the vehicle to leave its orbit and commence its descent south of the Mauritius Islands of the Indian Ocean. The spacecraft then had a 27 second burn which brought it to 292,000 ft/s and a height of 400,000 ft, an interface required to bring it 4043 miles to Edwards Field. When the spacecraft reached a speed of 230,000 ft/s and sensed it was at 0.76 g, the first command to roll 80–85° was made. It was held at this speed until it had reached the crossrange of 377 n. miles from touchdown. At this point the attitude was corrected and Challenger's nose was pointed in Azimuth 10° to the north of the landing site.

The next test was made at 240,000 ft, and when the speed was 23,000 ft/s. This test involved yaw thrusters and was designed to check the behaviour of the ailerons and other surfaces which experience very thin air when reaching thin atmosphere. Another test was made at a height of 205,000 ft and at speeds of 18 and 15.6 mach to check the effec-

tiveness of the ailerons and their resistance to the pressure put on them at this time. Aileron stability is very necessary when carrying heavy loads such as will be encountered with Space-lab. This successful trip surely means that the re-usable vehicle is here to stay.

Many photographs were taken during this trip and some of these will be described, they are important. One of these pictures showed the astronauts climbing around the shuttle, and it was clear that they were making rather heavy weather of it. They did have some training in a water tank but it seems that this had not been sufficient. This may of course be lack of training, but this seems a little unusual. If this part of the de-briefing is released there might be some better understanding. There seems to have been trouble with the tethering lines. These did not work according to plan, though they had appeared satisfactory in the water tank. It is a little difficult for those on Earth to realise that as far as the astronauts are concerned they are free to move in any direction, it is not just a matter of up and down and side to side. It has already been decided that in the next trip a non-tethered extra-vehicular exercise would take place.

One of the pictures also showed the Earth and its clouds against the background of Space while the astronauts were working in the payload bay. All the pictures were taken with a 35 mm camera attached to the space-suit. Another thing was noticed by the monitoring devices: the heartbeat of Musgrave was still at 60 beats per minute whilst Peterson's had jumped to between 130 and 140; readers will remember that this happened with a previous crew. Challenger-6 was at that time in darkness and all lights were on as the 35 ft long Tracking and Data Relay satellite was raised to 59°. After the satellite had been launched the upper stage could be seen attached and inert to the disappointment of all concerned. At the moment it is not yet decided what its future fate might be.

## THE RED SHIFT AS A MEASURE

At last there seems to be a real attack on the question of the Red Shift. It has been more than a decade since Chris Arp of the California Institute of Technology was displaying photographs and models of objects which have thrown doubt on the idea that Doppler shift and Red shift are always the same. Several teams have sought to refute his views and even suggested that the connecting filaments which he saw were a figment of his imagination. It so happens that Jack Sulentic of the University of Alabama has recently confirmed Chris Arp's and his team's results. This was done using some hitherto unpublished photographic plates of the galaxy NGC 4319 and the object Markarion 205. When it is confirmed it will show that at least part of the Red shift in the light from astronomical objects is not produced simply by their receding from us in the expanding Universe.

Arguments have been made before about the Red shift with regard to some very important bodies and not all astronomers demand that the Doppler effect of sound is exactly the same as Red shift. That it applies to ordinary galaxies is true—this can easily be checked by measuring the speed in different ways simultaneously or by using different methods

and comparing measurements. However, there have been protagonists on both sides. It is therefore now becoming more and more important that some solution be found. As time passes, new discoveries are made and more sophisticated techniques devised so it is now imperative that what we believe to be true, is proved to be true. It is significant that recently a small group of people who were interested in this subject because very long baseline interferometry (VLBI) had revealed 'faster than light' speeds in Quasars. VLBI had shown that the quasar 3C279 showed an expansion rate which, when converted by the Hubble law, gave a figure 10 times the speed of light. The astronomers at Jodrell Bank, a small group set up to look into this matter and to provide at least some ideas about the future procedure, set out to discuss it.

There are now seven known radio sources that show these superluminal characteristics. These range up to at least 10 times the speed of light in their motions. These are 3C120, BL Lac, 3C273, 3C279, 3C345, 3C179 and NRAO 140. These were revealed because of the increased technique reliability. This was due to the many VLBI arrays and the routine production of milli-arc-second-scale maps. Some indirect measurements show that the variable velocities in some cases may be due to several components. The theoreticians do not believe the results, they do not believe that real faster-than-light motions exist. This breaks Einstein's light speed limit, therefore it must be an illusion. It is true that initially it had been admitted that, seen from a certain angle, it appeared that the law was violated; indeed the law itself was disputed. This was a very serious discussion and the matter was thrashed out thoroughly. No answers were found, though many suggestions were made.

The conclusion was that during the past 12 years more questions had been raised than had been answered. What now then, stalemate? Surely not. Are mathematics confounded or has something been missed? Are matters, then, to be left to others more adventurous? If one reporter is to be believed, the matter is to be left there and hope that during the next 12 years some solution will emerge. Is it then a return to the past, must Einstein be preserved right or wrong? Who mentioned Darwin . . . ?

## TAILPIECE

It is rare for this column to be concerned with such mundane matters as insurance, yet this is the second time that it has arisen, since it directly involves the recent failure of the Tracking and Data Relay satellite which failed to be sent to its planned orbit. There has been some criticism lately about insuring against this sort of thing. It seems that the constant failure of Ariane has already led to some re-thinking in London and New York. The average cost of a rocket is high and the composite of satellite and launch runs on average at three-quarters of a million pounds. The normal premium now seems to be about 10%, but only about 5% for a shuttle launch. It is easy to see that those looking for the biggest profit will prefer the shuttle.

# Frank W. Hyde



# ROBOT VISION

GEOFF MORTIMER  
& LIZ NEWBURY

**B**EFORE we can start discussing any particular aspect of robotics it is only sensible to ask the question, 'What exactly is a robot?' The word was coined in 1921 by Czech playwright Karel Capek and is derived from a Czech word meaning 'worker'. Capek's play, entitled 'RUR' (Rossum's Universal Robots), tells how a brilliant scientist named Rossum manufactures an army of mechanical 'robot' slaves to free mankind from the drudgery of work. However, after an irresponsible scientist in Rossum's laboratory gives the robots feelings, they grow to resent their lot and rebel against their creators, finally annihilating the human race.

Clearly Rossum's robots were far more sophisticated compared with those that current technology is capable of producing. The modern industrial robot is a cumbersome beast by comparison, needing many thousands of instructions to perform even a simple task, and certainly lacking both initiative and ability to oil its own springs. So what distinguishes a robot from just another piece of computer-controlled machinery? There are those who would say there is no difference, in Japan for example, any NC (numerically controlled) machine is considered for statistical purposes to be a robot. Since this is obviously not a very useful definition, we must draw a line somewhere.

Consider the difference between a digital alarm clock chip and a microprocessor. The former will undoubtedly be programmable (since the alarm would be of little use if the manufacturer had pre-set it to say, 7a.m!) but even the most ingenious electronics engineer would have difficulty adapting that chip to control his washing machine. Although a microprocessor can easily be programmed to perform the same function as the digital alarm clock chip, everyone knows that this is by no means the limit of its capabilities.

We can usefully think of the robot then, as the 'microprocessor' of the machinery world. As with the micro, the robot's hallmark is versatility, so there is no need for its designer to try and foresee its every possible use. A robot arm for instance, given an adequate reach, speed and lift capability, should be able to turn its hand (or gripper perhaps) to anything.

## WHY SENSORS?

Imagine a human brain completely divorced from its senses, unable to touch, hear, smell or see anything of its surroundings, and unaware of the positions of the limbs in its body. It is most unlikely that the brain would develop at all under these circumstances, and it is arguable that intelligence as we understand it depends entirely on the brain's ability to acquire sensory information. A computer without sensors would likewise be unprogrammable, since it would be impossible to input any code.

A robot cannot be 'intelligent' if it cannot directly acquire information about itself or its surroundings. Thus when you give a robot the ability to 'perceive' and so acquire information, you reap the immediate benefits of an artificial intelligence. These benefits are considerable: Firstly, programming can be simplified, and carried out at a higher level, and be more readily understood by the user. Secondly, the machine is able to learn about its environment during operation; and thirdly, obstacles can be avoided automatically without the need for specific programmed commands.

If a visual perception system is implemented, a robot can distinguish patterns and objects, and then act on the information. In manufacturing, for instance, it can identify and automatically reject broken or damaged parts on a production line. Another example might be a robot which picks up chocolates and automatically deposits them in the correct compartments of a box. Besides performing regular activities like these a seeing robot may intervene in abnormal situations, such as tools accidentally being dropped on to a conveyor belt, where the outcome is potentially dangerous or costly. Evidently, sensors in general and visual ones in particular are going to play a very important role in the advancement of robotics engineering.

## HOW CAN ROBOTS SEE?

In human beings the seeing process is essentially a dual one: Visual information is acquired by the eye, then processed or 'understood' by the brain. Neither the eye nor

the brain can 'see' on its own—both are necessary if the visual perception system is to function. So in order for a robot to see, it must be equipped with mechanisms for acquiring and for processing images. In the area of vision, as in many fields of robotics, engineers have attempted to simulate human systems as far as possible. Visual data is normally acquired by some form of camera which transmits the visual signal to a computer for processing. Camera technology is generally agreed to be adequate for most current requirements but, as has been the case in other fields, the computer technology itself is still lagging behind.

Ideally a computer should 'understand' an image by describing it in terms similar to those a human being might employ, then use the 'knowledge' so gained in future problem-solving situations. The way to achieving this lies in the development of more powerful computers, and more importantly, the improvement of software techniques. In many industrial situations, potential robot applications have needed some form of visual feedback, and recent developments have provided solutions to a number of such problems. It is also true that many situations exist which do not demand an ideal vision system, and with which current technology can cope quite adequately. Let us now consider some of the techniques in use today.

### VISION SENSORS


The simplest form of optical sensor is the photo-electric cell, the original 'electric eye'. A single photo-cell, however, is able to convey only one piece of information at a time. A robot (or computer) vision system usually requires a large amount of picture information to be supplied relatively quickly, and the solution lies in the use of some form of camera. Until quite recently the best sensor available was the TV camera tube, unfortunately rather a fragile device. Now, however, solid state 'retinas' employing charge

coupled device (CCD) technology have been developed. These units are far more robust than their glass counterparts, so are more suitable for use in industrial environments. They also have the advantage that they are much easier to interface to computers.
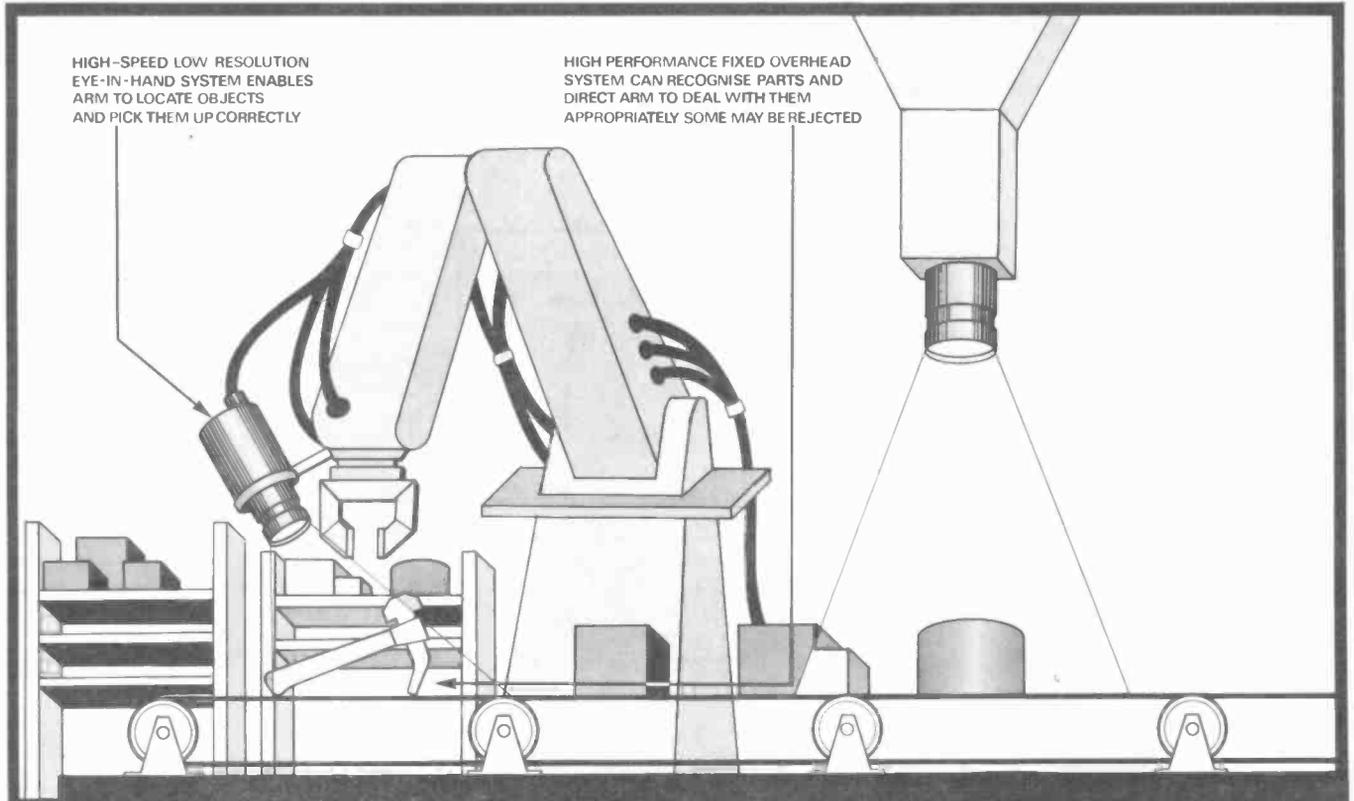
### VISION BASICS

Although computer vision systems may vary considerably in sophistication, a number of techniques are common to all of them. Before an image from a camera can be usefully processed, it has to be converted to a form which can be understood by the computer. This conversion process, known as digitisation, involves the division of the image into a grid of squares (or pixels), each of which is then stored in memory as a number (or pixel value). In a 'grey-scale' system the pixel value is called the grey-level, and is proportional to the brightness of that portion of the image represented by the pixel. In binary systems, the pixel value is either 1 or 0, corresponding to a brightness greater or less than a predetermined threshold, the stored image being basically a silhouette.

The resolution of a system is a measure of the number of pixels into which the image is digitised. Thus the higher the resolution, the more precise and detailed the stored image. However, if a very large amount of information is stored, the computing power required to process it becomes prohibitively large: a 256 x 256 pixel image contains 65536 pixels, a number equal to the total addressable memory capacity of most of today's microcomputers! A technique known as run-length encoding is often used to overcome the space problem, in which a string of numbers called a run code is set up, instead of storing every pixel. Each number corresponds to a number of adjacent pixels with the same value, together with the value itself. This allows a considerable reduction of the memory required, especially when



A typical example of the use of visual feedback: A two vision system enabling a robot arm to pick up different objects from a conveyor belt and place them in appropriate containers.

high resolution binary images are being processed. Let us look in detail at two vision systems representative of existing techniques.

### HIGH RESOLUTION GREY-SCALE SYSTEMS

The most sophisticated vision systems in use today attempt to extract and process the maximum possible information from an image. The resolution of such a system is typically 100,000 or more pixels, and perhaps 256 or more grey levels are distinguished.

Comprehensive signal processing and feature extraction algorithms are used to determine the shape, size, position and orientation of an object (or a number of objects) in view. Powerful mainframe or mini-computers are used in the processing of the image, often needing several processors to achieve sufficient computing power. By storing information about an object such as the relative positions of features like corners and holes, complex networks of tubes and pipes or contoured metal castings can be consistently recognised. Powerful contrast enhancement techniques enable information invisible to the human eye, such as hairline cracks in printed circuit board tracks, to be detected.

Using systems such as these in conjunction with robots it is possible to automate processes in which the type and orientation of parts to be manipulated is outside the control of the programmer. Here the robot uses its 'eye' to direct it in its task. However, even high-resolution systems have their limitations. Three-dimensional and mobile vision technology is still in its infancy, and it is not normally possible to compensate for the effects of variable lighting conditions. The high level of performance indicated above is generally attainable only in clear environments, using a fixed camera position and carefully controlled lighting. The advantages of high resolution systems lie in their increased information—handling capacity. These are offset though, by drawbacks such as considerable bulk, slow operation and high cost (typically over £20,000).


### LOW RESOLUTION BINARY SYSTEMS

An alternative approach is gaining favour in some areas of robotics applications. This minimises processing overheads, cost and complexity by using very low resolution (VLR) binary (i.e. silhouette) vision systems. These use typically only one or two thousand pixels of digitisation, and a limited number of feature extraction functions. They are able to process visual information at speeds comparable to that at which an efficient robot arm might move. In other words, direct real-time visual feedback loops can be established. The recognition-ability of such systems is usually limited to a small set of criteria. These might include area, perimeter, the number of 'holes' in an image, and so on. Nonetheless, since the camera is compact enough to be mounted on the end of the robot arm itself, areas of interest can be magnified simply by moving it nearer to the object. Calculating the position of the centre of gravity, provides a basis for location and orientation algorithms which are often fast and precise enough for the arm to follow a moving object. Unimation Ltd recently demonstrated this ability using a PUMA robot arm fitted with a 32 x 32 pixel camera. The robot followed a plastic toy building brick as it was moved across a surface, picking it up correctly when it remained stationary for longer than about four seconds.

VLR systems are of greatest use in situations where the identity of an object has been pre-determined, and where high-speed operation is important. Because VLR systems are simple and relatively inexpensive (typically under £1,000), they are popular among hobbyists and educational establishments. Though less sophisticated than their high-resolution counterparts, they employ many of the same techniques.
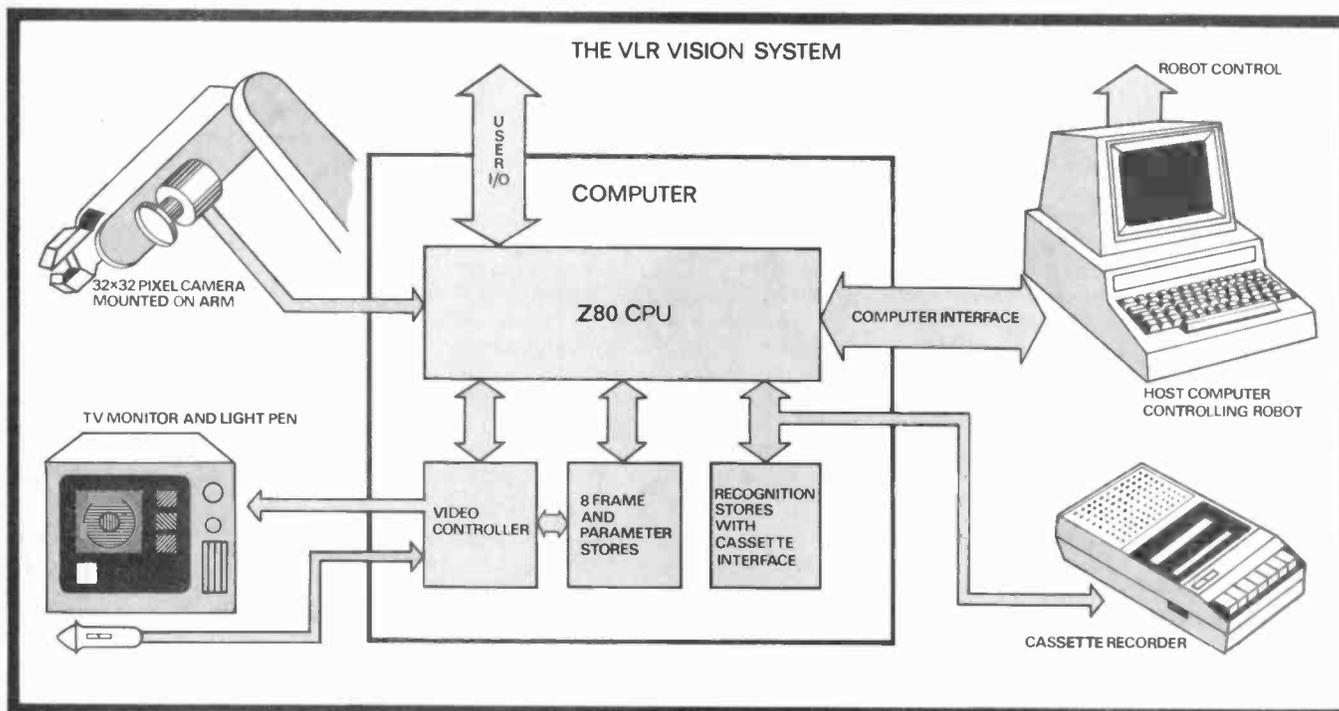
### THE COLVIS VLR VISION SYSTEM

An example of VLR technology is the COLVIS vision system, manufactured in the UK by Colne Robotics Co Ltd. This system employs a 32 x 32 pixel, binary solid-state camera using a dedicated Z80-based micro-



A typical configuration of the COLVIS high-speed system: Commands may be entered either with the light pen or via the user I/O channel. The host computer interrogates the system for visual information which it then uses to control the robot

computer. It can be used either on its own, or under the control of any micro or mini-computer fitted with an 8-bit bi-directional port. In stand-alone mode the system can perform simple vision-based control functions, and is programmed via a TV monitor and light pen. When under computer control, the system can be interrogated for either raw or processed vision data which is then transmitted back to the 'host' computer. In this way, a computer controlling a robot arm can be supplied with vision information on demand, and at no cost to its own processing time.

The system is supplied with software enabling it to determine the position, orientation and identity of objects in its field of view. The commands available to the user are in three groups:

- (i) Data acquisition
- (ii) Image processing (including feature extraction)
- (iii) Learning/recognition

Eight picture stores are provided, and the camera image can be read into any one of these, one at a time. Each picture store has an associated area of memory in which any of the following parameters can be updated on command:

PARAMETER	FUNCTION
Centre of gravity:	Position, orientation
Direction of longest dia:	Orientation
Direction of shortest dia:	Orientation
Area:	Recognition
Perimeter:	Recognition
Number of holes:	Recognition
Perimeter <sup>2</sup> /Area (compactness):	Recognition
Longest diameter:	Recognition
Shortest diameter:	Recognition

Measures are taken to ensure that the system always operates at its fastest possible speed. A comprehensive range of learning functions has been implemented, enabling the system to be taught to identify objects on the basis of some or all of the recognition parameters listed above. A 'Learn' command is given, together with a name for the object to be learnt. The system then calculates, and records the required recognition parameters in a data structure which incorporates a set of tolerances associated with each parameter. These tolerances are automatically initialised to a useful set of values, but for each learnt object the user can adjust them individually, in both the positive and negative axis. Learnt objects can be deleted or re-learnt; they can be saved on cassette tape or loaded from it. When the 'Recognise' command is given, the list of learnt objects is scanned, and those parameters in use are compared with ones calculated from the camera image. If the new parameters all fall within the specified tolerance for a learnt object, the system notifies the user (or host computer) that it has recognised that particular object. Up to 64 different kind of objects can be learnt at any one time. In normal use an operator would teach the system a new object, adjusting tolerances and changing the criteria (i.e. parameters used) for recognition, until optimum performance was achieved, before handing back control to the host computer.

Additional commands enable the system to pre-process picture information before parameters are calculated. These include picture inversion, exposure control, choice of light or dark background and several noise-reducing functions which strip or fill-in isolated pixels. A macro construction facility enables strings of commands to be stored in memory and executed as single instructions. The contents of any two frame stores may be displayed simultaneously on the

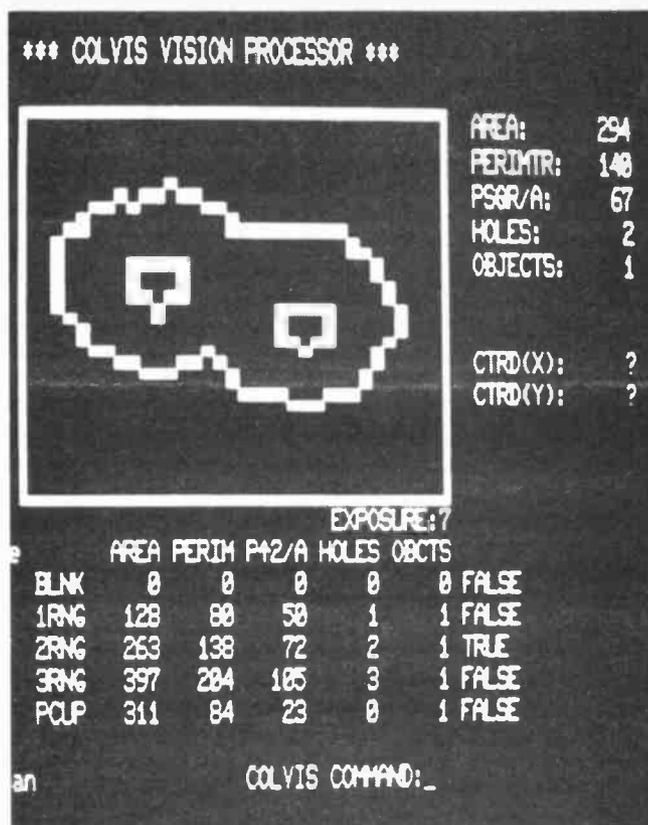


Fig. 1. VDU showing object identification

monitor screen, together with their associated parameter lists. When under computer control, all parameter, learning and frame store information can be transmitted on request to the master system.

In Fig. 1, the VDU shows an object (coded BLNK) which the system has learnt and identified: In the top right of the screen the parameter requirements are shown and are represented by the picture in the square. The list of parameters closest to those learnt, is shown in the lower part of the display, and has been identified as TRUE; the other possibilities being rejected as FALSE.

The COLVIS system is simple to use and fast-operating, making it ideal for educational purposes, though undoubtedly it will find its way into a number of industrial situations as well. An important aspect, particularly for educational establishments, is the low cost of this system; around £400.

#### LOOKING AT THE FUTURE

There is considerable scope at present for improving visual perception techniques. The vision system of the future will be able to process picture information far more efficiently than its relatively primitive predecessors, using extremely sophisticated high-level programming languages developed solely for such a purpose. We can expect computers themselves to be hundreds, perhaps thousands of times faster and more powerful. If technology within this field continues to advance at its present rate, some seemingly far-fetched predictions will rapidly become probabilities rather than remote fantasies. We can foresee vision systems installed overlooking large and complicated scenes—factory floors or perhaps crowded city centres. There, they will survey the area for abnormal events, capable of detecting fires, accidents and maybe even crimes! We must remain alert to the value and importance of robot vision, a field whose enormous potential is still to be explored and exploited. ★

# VERNON at TRENT Large!

*V.T.'s views and opinions are entirely his own and not necessarily those of PE*

YOU must have heard of the House of Floggit, to my mind one of the most interesting department stores in South London. Family-owned, it first opened its doors towards the end of the 19th century and, until recently, remained an undying echo of the Victorian era of retail trading when the customer was king.

Floggit's merchandise was, and still is, of superb quality. Its standards of service impeccable. The lady assistants wore modest frocks that suppressed any gender-indicating undulations. The gentlemen were dressed in formal suits, the jackets of which were never discarded, even on the most sweltering day. And such frivolities as the use of forenames and remarks of a jokey nature were OUT.

Accounting and stock control systems were equally traditional. Cash was handled with genteel disdain. The customer's payment—he wasn't up to much if he didn't have an account—would be placed in a kind of torpedo tube and shot off to the counting house by an overhead railway. If change was involved, it would be returned by the same means. All this gave the impression that so far as the management was concerned, the handing over of the money was no more than a slightly indecent incidental.

In those pre-VDU days a basement-based covey of brown-coated retainers, all with unnaturally-tapered index fingers, carried out a digital stock count at the end of each day, recording their findings in copperplate handwriting on a series of lists. The store was open six days a week and no matter how late the hour, no one was allowed to leave their post so long as there was a customer about.

This respectable, dependable and thoroughly stuffy and unprogressive profile began to change after Arnold Floggit took over the helm a few months ago. He succeeded his uncle Horace, the former chairman, who died without notice from a fit of the vapours on discovering Miss Playful (Toys and Games) up to no good in the stockroom with Mr. Stiff (Hardware).

Arnold, a very much younger man than his predecessor, was well and truly into electronics and—having once been stuck with Kenneth Baker at a cocktail party—had developed a special interest in information technology. And he was therefore aghast at the archaic and non-technical way in which the outfit was being run. There had to be fundamental changes.

His first tycoonish ploy was to set up an in-depth survey. This is, of course, standard procedure for anyone who can spell Harvard and consists of hiring hordes of expensive young analysts who dash around asking irrelevant questions and getting equally irrelevant answers. This leads to the production of a report, sometimes bound in limp leather and always costing a fortune.

On the basis of the report which eventually landed on his desk, Arnold decided to sink an odd million or so quid in a computer-based system which would do away with that absurd overhead railway, pep up accounting and stock-control and provide a constant flow of management information.

One day a team of young experts wearing Imperial College ties arrived to set up the computer. The staff didn't take much notice at first. All they knew was that a load of layabouts were mucking about in the basement.

But the course of events was soon brought home to them when one day one of the layabouts marched into Perfumery and dumped an electronic cash register on the counter. Miss Sniff, the buyer, 30 years with the firm, ignored it completely to begin with and continued to have fun with her overhead railway. The next sinister happening was a summons from above for all senior buyers. It was there that Arnold unveiled his grand plan and then handed the group over to Mr. Teachem, the training officer, for an intensive course of instruction in the modern miracle which was to transform their lives.

It was a frightening contraption so far as the conservative senior staff was concerned. It had more buttons than a cardinal's cassock and a habit of bleeping and popping whenever anyone laid a finger on it.

That first training session is not a happy occasion to record. Miss Silk of Haberdashery announced her intention to seek early retirement. Miss Swish of Ladies Fashions went all hysterical and had to be sedated with a swig of mint tea from the canteen. Mr. Spark (Major Domestic Appliances) eased his feelings by giving the thing a sly kick.

One cannot blame any of those present for their attitude when you consider the circumstances. Here they were, loyal servants who had grown grey in service, brought up in a world of dignified and calm, if stick-in-the-mud, working methods, being asked to become user-friendly with something which, in their opinion, belonged to another planet.

Arnold Floggit had not done things by halves and had gone all-out for sophistication. The cash register—which was not a cash register at all, but a thing called a terminal—was a multi-function beast. It could record both cash and credit transactions, log the date and time of each sale, with the identity number of the assistant concerned, and provide accurate, highly-detailed and easily-accessible data on stock movements. "I bet," said Mr. Crepe (Footwear) with dry cynicism, "it would boil an egg if you asked it nicely."

The day that the new system came into active public service had, for the younger members of the staff, a touch of carnival. Weaned on digital watches, up-market calculators and even home computers, they found little dif-

ficulty in adapting themselves to the revolution. Indeed, some of them regarded the occasion as the start of an era of liberation from the outmoded and sometimes despotic Floggit regime. Hopes were expressed by a few, including fashion-conscious little Wendy Penn (Stationery), that they could soon start turning up for work in flashy tops instead of bust-flattening blouses. Young Tom Channel (Radio and TV) prophesied that soon he'd be wearing cords and bomber jacket.

The over-40s were not so happy. The complicated procedures needed a strong mental digestion. An ordinary cash transaction, for example, involved the pressing of some 15 buttons, all in the correct order without, alas, a comforting cancel facility for the correction of cock-ups. Credit sales were even more complex. Barclaycard and Access, popular and convenient as they are, brought fresh terrors, as did the handling of cheques. And when some clever dick decided he wanted a refund, the effect on the hard-pressed salesperson was frightful to behold.

It will come as no surprise to you that all this sophisticated technology had adverse repercussions on customer-relations. The chap who'd just popped in for a set of batteries for his tranny on the way to the betting shop instinctively resented having to stand for 15 minutes witnessing a dazzling display of terminal trickery instead of merely slapping his money on the counter and pushing off.

In those departments where the older generation presided long queues were the order of the day. There was much muttering of "things aren't like this at Comet". The carriage trade, accustomed for generations to sedate service, switched to Harrods where they could hope for service almost as efficient as that accorded to the Queen. Turnover dipped, morale sagged and the star called Floggit began to dim in the retail firmament.

Arnold Floggit, dedicated technologist as he was, began to wonder whether or not he hadn't dropped one. A realistic fellow, he reasoned that by equipping his goose with a golden facility he may well have retarded her ability to lay golden eggs. And it was with a sigh of resignation and a fondly wave to his not inconsiderable investment that he did a swift turnabout. One could not help salute him.


Out went the computer and its attendant terminals. Back went the overhead railway and the brown-coated stock counters. All hopes of dress reform faded into the middle distance. The older generation had their happiness restored.

There is an obvious moral to this story. You will recall that in a previous issue of PE I enjoined the Church to adopt electronics techniques in the name of greater efficiency.

Perhaps at the same time I should have pondered on the problems of such retail houses as the House of Floggit and exhorted leaders like whiz-kid Arnold to pause before hurling themselves headlong into the electronics age.

Mind you, it's only a matter of time before Floggits, like other concerns, will have to succumb. In the meantime I shall take a middle-aged satisfaction in guessing at the mysteries of the formal frock, watching my money whizzing between counting house and counter by overhead railway and sympathising with youngsters in their heavy serge.

all in your  
**SEPTEMBER**  
issue!

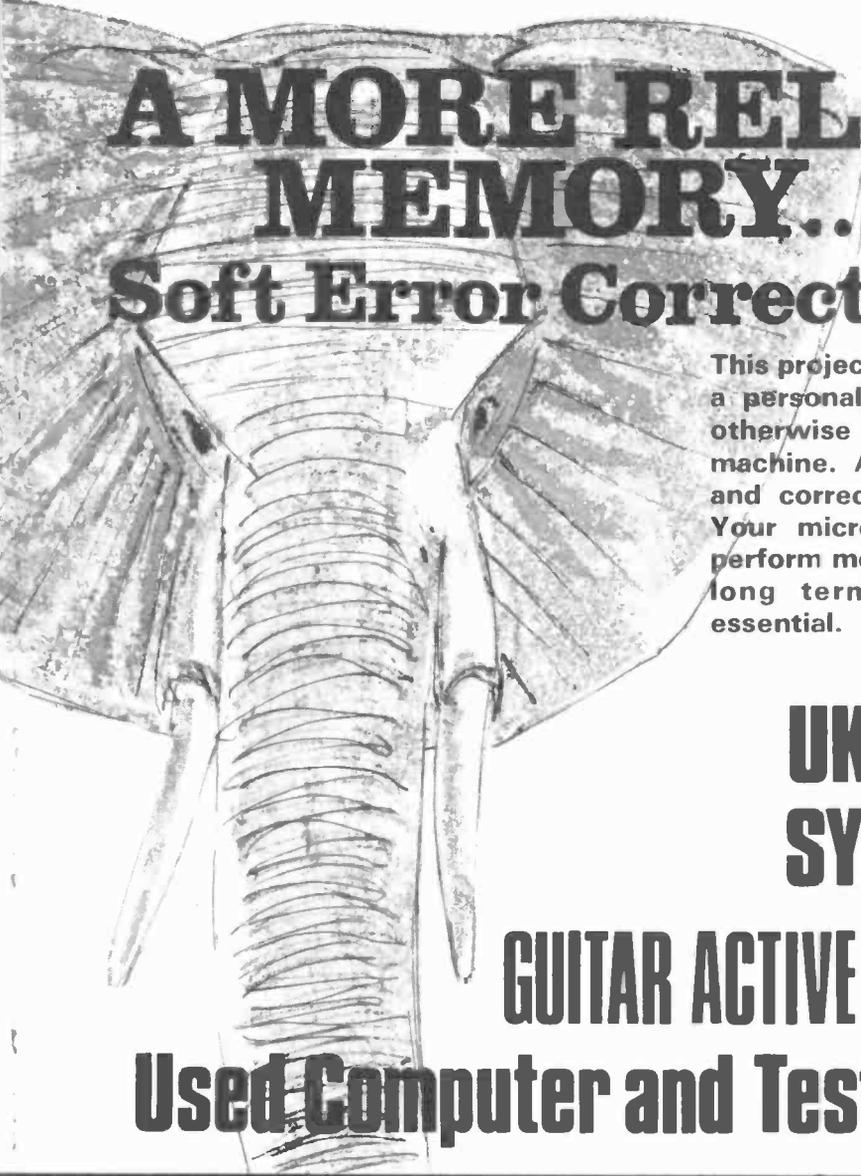

**A MORE RELIABLE  
MEMORY... Computer  
Soft Error Correction Board**

This project will improve the reliability of a personal computer to a degree only otherwise available on a professional machine. An ingenious error detection and correction technique is employed. Your micro can thus be improved to perform more sophisticated tasks where long term error free operation is essential.

**UK SATELLITE TV  
SYSTEM Explained**

**GUITAR ACTIVE TONE CONTROLS...**

**Used Computer and Test Gear Bargains!!**

**PRACTICAL**

**ELECTRONICS**

SEPTEMBER ISSUE ON SALE FRIDAY, AUGUST 5

# SEMICONDUCTOR CIRCUITS

TOM GASKELL B.A. (Hons)

## VOLTAGE CONVERTER (ICL 7660)

**M**OST modern logic and microprocessor circuitry take power from a single supply rail; either +5V for TTL and microprocessor-based systems, or higher voltages for some CMOS circuitry. The incorporation of any other supply rails within such a system can be a considerable nuisance, adding complexity, size, and cost to the final project. A frequent requirement is for a low current negative supply, used to provide power to a small amount of analogue circuitry within the logic system. Digital to analogue, and analogue to digital converters are examples of circuitry which sometimes requires this negative rail; likewise many op-amp circuits, and certain memory i.c.s. (especially dynamic RAMs). In all cases the power requirements are so small that it seems to be an 'overkill' to have to provide a complete negative supply system, whether derived from the mains supply or from extra batteries. The ICL 7660 is designed to help solve this problem. It is an 8 pin CMOS i.c. which converts a positive supply into a negative supply voltage. Hence, any nominal supply of +1.5V to +10V is converted to a negative supply of -1.5V to -10V, with sufficient drive current for most applications (typically up to 40mA for a +5V input).

### BASIC CIRCUIT

Fig. 2 shows the circuit design principle on which the ICL 7660 is based. Under the control of an internal 10kHz oscillator and switch control logic, four MOS power switches are used to charge up, and transfer charge between, C1 and C2. These capacitors are external to the i.c., since they must be relatively large; 10  $\mu$ F is typical. The sequence is as follows: S1 and S2 turn on, while S3 and S4 remain off. As a result, C1 is charged up to the positive supply voltage. Then, S1 and S2 turn off, while S3 and S4 turn on. The positive end of C1 is now taken from the positive supply down to 0V. The negative end of C1, which was previously at 0V, then becomes forced negative; for a positive supply of +5V, the negative end of C1 is taken to -5V. The charge on C1 transfers to C2, the reservoir capacitor, which then supplies current into the

load. S3 and S4 turn off, S1 and S2 turn on, C1 charges up again, and the whole cycle repeats continuously.

### USING THE CHIP

The pin-out of the ICL 7660 is shown in Fig. 1, complete with its specifications. There are several important points to note about the

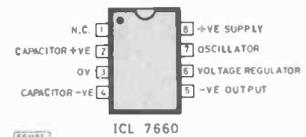


Fig. 1 Voltage converter integrated circuit pin-out with its specification below


Characteristic	Notes	Min. Value	Typically	Max. Value	Units
Supply voltage	All spec's measured at +5V supply	1.5	5	10.5	V
Quiescent current	No load on negative output		170	500	$\mu$ A
Temperature range		-20		+70	$^{\circ}$ C
Power dissipation				300	mW
Oscillator frequency			10		kHz
Output resistance	20mA load current		55	100	$\Omega$
Output resistance	Positive supply = 2V, 3mA load current		150	300	$\Omega$
Output voltage (as percentage of positive supply)	No load on negative output	-97	-99.9		%
Output ripple, pk/pk	5mA load current		0.1		V
Output ripple, pk/pk	20mA load current		0.2		V

specifications, and about the way that the i.c. is used in practical circuits. The absolute maximum supply voltage is +10.5V, so do not try to use it with supplies of over 10V; 15V CMOS is definitely not on! As with most CMOS i.c.s, connecting any pin to voltages outside its supply rails will cause damage, so ensure that no external signals are applied to the i.c. before its own supply is turned on. An internal voltage regulator is provided to prevent latching up (and potential damage) when supply voltages higher than +3.5V are used. This can adversely affect low voltage performance, so for voltages below +3.5V connect pin 6 to 0 volts, disabling this regulator. However, when voltages of +3.5V or more are used, this pin *must* be left floating, i.e. unconnected.

Finally, for supplies of +6.5V or more, or

use at high temperatures, a diode *must* be added in series with the output. Fig. 3 shows the basic voltage converter circuit, and D1 is the extra series diode if required. For the lowest forward voltage drop a germanium diode is the best choice; an OA47 is specified, but any similar diode will do. A 1N4148 or similar will work satisfactorily, but will drop slightly more voltage. Take care with the polarity of D1; the feed from pin 5 of the i.c. is a negative, not a positive one!

Because the negative supply is generated by the charging up and discharging of capacitors, it is far from being a perfect voltage source. As would be expected, the output voltage becomes less (i.e. nearer to 0V) as more current is drawn. In practice, the relationship between the output voltage and the current drawn is linear; the effect is the same as

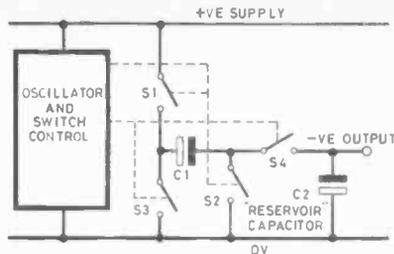


**Fig. 2 Principle of i.c. operation**

putting a resistor in series with a perfect voltage source. The value of this effective output resistance is dependent on the supply voltage, with 55 ohms being typical for a 5V supply, and 150 ohms for a 2V supply.

The graph of output voltage versus output current for a +5V supply is shown in Fig. 4. For most op-amps, A-D converters, D-A converters, etc., the current drawn is small, and the slight variations in negative supply voltage have no significant effect, but this characteristic of the i.c. should be borne in mind when designing appropriate circuitry.


Similarly, the relatively high level of ripple (typically up to a few hundred millivolts) should be noted, although again this should not normally cause any problems.

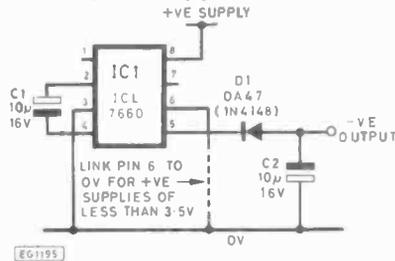


**Fig. 3 Basic voltage converter circuit. D1 is not necessary for supplies >6.5V. Include it if high temperatures are anticipated**

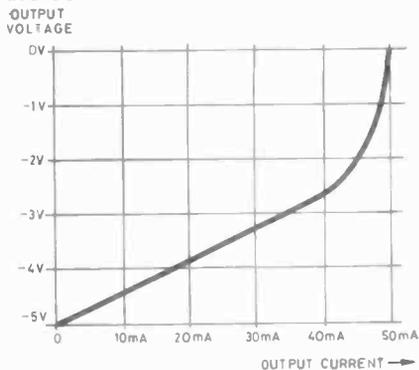**IMPROVING PERFORMANCE**

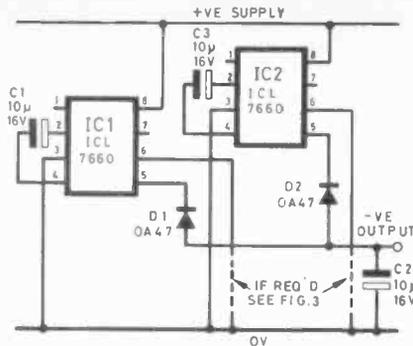Figs. 5, 6 and 7 show ways of improving the output characteristics of the ICL 7660. In Fig. 5 two devices are connected in parallel to give a lower effective output resistance to the negative supply. The reservoir capacitor C2 can be shared between the i.c.s. Any number of devices can be connected in parallel, the overall output resistance being the individual i.c. output resistance divided by the number of i.c.s used. For best performance, the output diodes, D1, D2, should be used at all voltages above 3.5V.

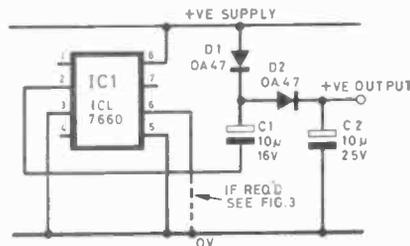


**Fig. 4 Graph of output voltage versus output current for positive supply**



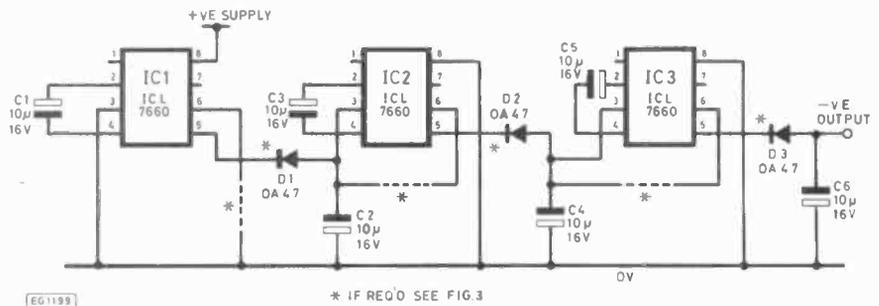
**Fig. 5 Parallel connection of i.c.s**

Fig. 6 shows a way of using the i.c. to provide a positive to positive voltage conversion! In this circuit the output voltage is twice the input voltage, less the two forward diode drops. This can provide up to approximately

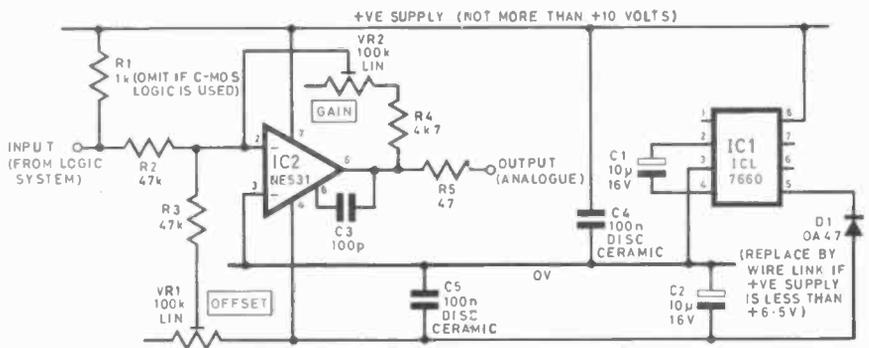


**Fig. 6 Positive voltage converter circuit**

19V, since the voltage doubling is performed only by C1, C2, D1 and D2. The +10.5 voltage limit on the i.c. is not exceeded, since D2 prevents the high voltage ever feeding back into the i.c. Note that C2 can't be a 16V type for all supply voltages, so use a 25V type instead.



**EG1199**




**Fig. 8 Logic level to analogue converter circuit**

Fig. 7 shows three devices connected in series to provide a larger negative supply voltage. Up to ten i.c.s can be connected in this manner, within the limits of a maximum negative voltage of -10V. However, in this configuration, the output resistances sum.

**EXTERNAL CLOCK**

Finally, the oscillator frequency of the ICL 7660 can be changed, if required, by feeding an external clock into pin 7. When fed from CMOS logic, a 1k series resistor should be provided, while for TTL a 4k7 pull-up resistor to the positive supply is needed. If an external clock is to be used, note that the conversion frequency is half the applied clock frequency, due to an internal divide-by-two circuit. The internal oscillator can be lowered in frequency by adding a capacitor (typically 33 to 330pF) between pin 7 and the positive supply. If the frequency is lowered, C1 and C2 should be increased proportionally to maintain the performance.

**Veroboard application of Fig. 8**

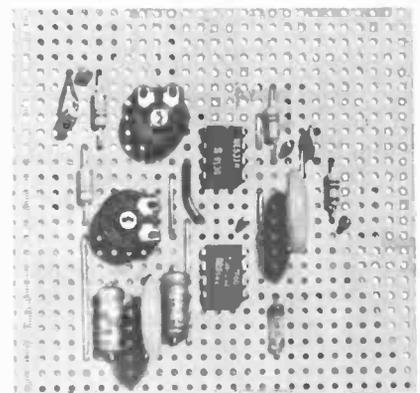

## APPLICATIONS CIRCUIT

Fig. 8 shows a simple application of this i.c. The circuit provides a logic system with a d.c. coupled analogue output, which is variable in level and symmetrical about 0V, rather than between 0V and the positive supply voltage. IC1 is the voltage converter used in a standard configuration to provide the negative supply to IC2, a high slew rate (i.e. high speed) op-amp. It is all powered from the logic system's own power rails, which are unlikely to be below 3-5V, so pin 6 of IC1 should be left open circuit. D1 can be replaced by a wire link for supplies of less than 6-5V. IC2 is used as an inverting amplifier, so precede this circuit with an inverting logic gate if polarity is important. The gain is variable between  $\times 0.1$  and  $\times 2$ , and is adjusted via VR2. VR1 provides an offset control, which provides biasing from the negative supply to the inverting input of IC2. This ensures that the output can be corrected to be exactly symmetrical about 0V, although it does put a small amount of high frequency ripple on the output, of course. Typically, a few tens of millivolts.

An NE 531 op-amp has been used to provide a very fast edge on the square wave output, but if this is not critical it can be replaced by a 741. If this is done, omit C3, the compensation capacitor, as 741s have internal compensation. Finally, C4 and C5 are extra supply decoupling capacitors, and C1 and C2

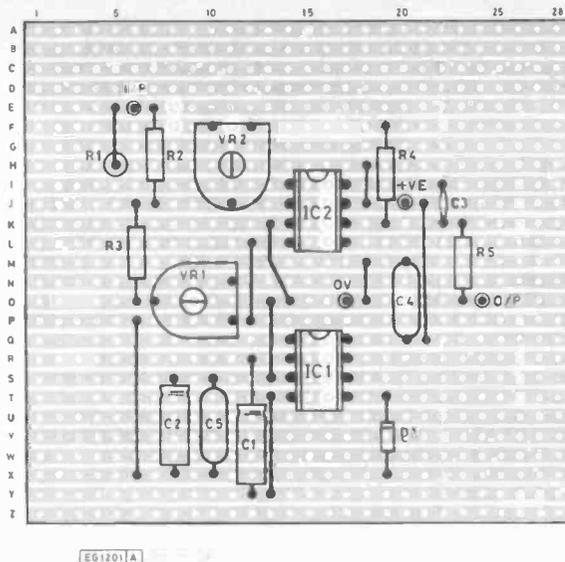


Fig. 9 Logic system with a d.c. coupled analogue output. Omit R1 if input is CMOS logic

can be 16V types or higher; 25V is quite acceptable.

This circuit is a fairly simple, but hopefully effective, demonstration of the way in which voltage conversion can provide a low power alternative supply rail in a larger system. Bear in mind the intrinsic limitations of the device,

and it can prove to be an extremely useful circuit element. The ICL 7660 is readily available from a number of suppliers, such as Technomatic, Maplin, and Watford Electronics.

Note: in Semiconductor Circuits (June 1983): In Fig. 1 pin 8 should be positive supply.

## FREE! READERS' ADVERTISEMENT SERVICE

# PE BAZAAR

**WEMON** for UK101 £8: Wanted January and March 1981 articles on OS65D published in Compute! Chris (0252) 546739 Farnborough, Hampshire.

**FLOPPY** disc controller 32K DRAM Romdos Link 6 and Vortex for UK101 only £150 possibly will deliver. Mr. M. Andrews, 'Conifers', Lyne Lane, Chertsey, Surrey. Tel: Ottershaw 3327.

**BUSH** AB23 EMI Pye Philips G6 chassis and spares cheap to clear + working panels. Mr. A. Bouskill, 129 Lyminster Road, Sheffield S6 1HY. Tel: 0742/311191 after 4p.m.

**DATA-DYNAMICS** 390 workshop manual wanted. Help—how can it be changed to RS232 from 90-0-90V? M. Foreman, 5 Manor Place, Frenchay, Bristol BS16 1PS. Tel: 566479.

**NAD 6040** cassette deck—with sendust head and Dolby HX. 20 months old £60. Tel: So'ton 332586 evenings. R. Dudley, 64 Hartington Road, Newtown, Southampton SO2 0EU.

**SCOPEX** 4D25 25MHz 'scope, exc. condition £250. Suggden SI453 audio Gen. £40. AVO d.m.m. DA116 £60. J. P. Evans, 90 Cedar Ave., Kidsgrove, Stoke-on-Trent ST7 1JZ. Tel: 0782 615351 Ext. 29.

**TEXAS** Instruments 58 Programmable calculator + master library book and programming book + mains adaptor £25. Mr. Toni Wales, 1 Sandringham Close, Thurlstone, Nr. Penistone, Sheffield S30 6RW.

**TEKTRONIX** oscilloscopes 545 A/B, 581 549 storage, loads plug-ins sampler, four channel, differential, all working, sensible offers. Mel Purcell, 3 Carrick Gardens, Carnbroe Estate, Bellshill ML4 1NU Scotland. Tel: (0698) 749317.

**MICRONTA** dynamic transistor tester, Tests transistors in or out of circuit. New with battery. £7.50. Call Chang 041 332 7695 9p.m. K. Y. Chang, 70 1-up, Ashley Street, Glasgow G3 6HW.

**FOR SALE** Rampacks (ZX81) 16K £20 64K £40 both perfect. Mr. K. Jenkins, 1 Sandal Road, New Malden, Surrey. Tel: 01 942 8352.

**PRINTER** dot matrix. Tractor feed, RS232. Switchable Baud/Parity. Suit UK101/Superboard £100. P. J. Cooper, Queensmere Lodge, Maldon Road, Bradwell-on-Sea, Essex. Tel: Maldon (0621) 76320.

**SCOPE** Probe, X1/X10 switch, BNC plug. As new with case. £10 inc. post. Dean—Tel: (0865) 779855.

**TRANSCENDENT** 2000 Synthesiser. Professionally built and improved. Home use only. Quick sale £139. Tel: Stevenage (0438) 50471. Mr. P. R. Williams, 10 Hadwell Close, Stevenage, Herts SG2 9DR.

**ICL7184** v.d.u. Service information wanted. Beg, borrow or buy. R. L. Savage, 95 Haven Baulk Lane, Littleover, Derby DE3 7AD. Tel: Derby 511459.

**RULES** Maximum of 16 words plus address and/or phone no. Private advertisers only (trade or business ads. can be placed in our classified columns). Items related to electronics only. No computer software. PE cannot accept responsibility for the accuracy of ads. or for any transaction arising between readers as a result of a free ad. We reserve the right to refuse advertisements. Each ad. must be accompanied by a **cut-out valid** "date corner". Ads. will not appear (or be returned) if these rules are broken.

Please publish the following small ad. FREE in the next available issue. I am not a dealer in electronics or associated equipment. I have read the rules. I enclose a **cut-out valid** date corner.

Signature ..... Date .....

Please read the **RULES** then write your advertisement here— one word to each box. Add your name, address and/or phone no.

**COUPON VALID FOR POSTING BEFORE 5 AUGUST 1983**

(One month later for overseas readers.)

SEND TO: PE BAZAAR, PRACTICAL ELECTRONICS, WESTOVER HOUSE, WEST QUAY ROAD, POOLE, DORSET BH15 1JG.

BLOCK CAPITALS PLEASE

Name & Address:			

For readers who don't want to damage the issue send a photostat or a copy of the coupon (filled in of course) with a **cut-out valid** "date corner"

PE BAZAAR  
AUGUST '83

# Midwich

COMPUTER COMPANY LIMITED



choice for microcomputer components

### BBC COMPUTERS

Model B	346.95
Model B + Disc Interface (Carriage 6.50 by Securicor)	441.95
Please phone to check delivery	
<b>BBC MICRO DISC DRIVES</b>	
BBC 31 Single 100K Drive Expandable to 2x100K	199.00
BBC 32 Dual 100K Drives	330.00
BBC 33 100K Upgrade for BBC 31	140.00
BBC 34 Dual 400K Drives	575.00
BBC 35 Utilities Disc	25.00

(supplied only with BBC 31, 32, 34)  
All Disc Drives (except BBC 33) are complete with Manual, Utilities Disc, and Connecting Cables

<b>BBC MICRO UPGRADE KITS</b>	
BBC A2/B Complete A to B Upgrade	44.75
BBC 1 16K Memory	18.00
BBC 2 Printer/User I/O Kit	7.50
BBC 3 Disc Interface Kit	95.00
only supplied with Disc Drives.	
BBC 4 Analogue Input Kit	6.70
BBC 5 Serial I/O & RGB Kit	7.30
BBC 6 BUS Expansion Kit	6.45
All Kits are supplied with full fitting instructions	

<b>PRINTERS</b>	
NEC 8023 Printer (Carriage 10.00)	320.00
<b>BBC CONNECTORS</b>	
BBC 21 Printer Cable and Amphenol Plug (not assembled)	13.00
BBC 22 User Port Connector and Cable 36"	2.46
BBC 23 Cassette Lead	3.50
BBC 24 7 Pin DIN Plug	0.60
BBC 25 6 Pin DIN Plug	0.60
BBC 26 5 Pin DIN Plug	0.60
BBC 25 Disc I/O Cable 34W IDC to 2x34 way card edge	12.00
BBC 36 Disc Power Cable	6.00
BBC 44 Analogue Input Plug and Cover	2.25
BBC 66 IM Bus Connector + 36" Cable	3.50

<b>BBC ACCESSORIES</b>	
BBC 45 Joysticks (per pair)	11.30
BBC 67 Erom Programme (assembled)	57.95
BBC 71 Teletext Receiver	225.00
BBC 72 Second Processor (6502)	170.00
BBC 73 Second Processor (280)	170.00

<b>ACORN SOFTWARE FOR THE BBC</b>	
SBE03 Business Games	8.65
SBE04 Tree of Knowledge	8.65
SBE02 Peeko Computer Inc Manual	8.65
SBE01 Algebraic Manipulation Pk	8.65
SBX01 Creative Graphics Cassette	8.65
SBX02 Graphics and Charts Cassette	8.65
SB801 Desk Diary Inc Manual	8.65
SB101 LISP Cassette	14.65
SB102 FORTH Cassette	14.65
SBG01 Philosophers Quest	8.65
SBG07 Sphinx Adventure	8.65
SBG03 Monsters	8.65
SBG08 Snapper	8.65
SBG15 Planteoid	8.65
SBG06 Arcade Action	10.35
SBG05 Rocket Raid	8.65
SBG13 Meteors	8.65
SBG14 Arcadians	8.65
SBG10 Chess	8.65

<b>ACORN SOFTWARE BOOKS FOR THE BBC MICRO</b>	
SB001 Creative Graphics	7.50
SB002 Graphs and Charts	7.50
SB004 LISP	7.50
SB003 FORTH	7.50
Please ring for current delivery on Acornsoft Products before ordering.	

<b>BBC MICRO COMPONENTS</b>			
4516 100ns	2.25	8271	36.00
6522	3.19	20 Way Header	1.46
74LS244	0.59	26 Way Header	1.76
74LS245	0.69	34 Way Header	2.06
74LS163	0.34	40 Way Header	2.32
DS3691N	4.50	15 Way D Skt	2.15
DS88LS120N	4.50	6 Way DIN Skt	0.90
UPD7002	4.50	5 Way DIN Skt	0.90

### BBC SOFTWARE IN EPROM

Wordprocessor "View"	52.00	TL014	0.36	4010	0.24	04
1.2 MOS	10.00	TL021	0.34	4011	0.10	05
<b>SPECIAL OFFER</b>						
Spectrum 32K Upgrade Kit	24.95	TL061	0.29	4012	0.16	08
DATA SHEETS are available on items marked D						
D1	0.75	D5	2.50	TL062	0.49	4013
D2	1.00	D6	3.00	TL064	0.98	4014
D3	1.25	D7	4.00	TL065	0.29	4015
D4	2.00			TL066	0.32	4016
				TL071	0.29	4017
				TL072	0.47	4018
				TL074	1.00	4019
				TL081	0.26	4020
				TL082	0.46	4021
				TL084	1.58	4022
				TL091	0.40	4023
				TL092	0.58	4024
				TL094	1.34	4025
				TL487	0.62	4026
				TL489	0.62	4027
				TL494	1.63	4028
				TL496	0.60	4031
				TL507	1.50	4033
				725	0.34	4034
				741	0.14	4035
				747	0.48	4040
				748	0.36	49
				748	0.34	51
				748	0.36	54
				748	0.36	55
				748	0.36	56
				748	0.36	57
				748	0.36	58
				748	0.36	59
				748	0.36	60
				748	0.36	61
				748	0.36	62
				748	0.36	63
				748	0.36	64
				748	0.36	65
				748	0.36	66
				748	0.36	67
				748	0.36	68
				748	0.36	69
				748	0.36	70
				748	0.36	71
				748	0.36	72
				748	0.36	73
				748	0.36	74
				748	0.36	75
				748	0.36	76
				748	0.36	77
				748	0.36	78
				748	0.36	79
				748	0.36	80
				748	0.36	81
				748	0.36	82
				748	0.36	83
				748	0.36	84
				748	0.36	85
				748	0.36	86
				748	0.36	87
				748	0.36	88
				748	0.36	89
				748	0.36	90
				748	0.36	91
				748	0.36	92
				748	0.36	93
				748	0.36	94
				748	0.36	95
				748	0.36	96
				748	0.36	97
				748	0.36	98
				748	0.36	99
				748	0.36	100

<b>MEMORIES</b>			
2114L 200ns	D1 0.80	FD1795	D6 28.00
2706 450ns	D2 2.95	FD1797	D6 28.00
2716 450ns	D1 2.45	WD1691	D2 12.00
2716 350ns	D1 4.95	WD2143-01	D2 6.99
2716 3 rail	D1 7.25		
2532 450ns	D2 3.45		
2732 450ns	D1 3.45		
2732 350ns	D1 5.45		
2764 300ns	D1 5.99		
4116 150ns	D2 0.85		
4116 200ns	D2 0.80		
4118 150ns	D1 3.25		
5516 200ns	D2 9.45		
6116 150ns	D1 3.30		
6116 Low Power			
150ns	D2 4.95		
4164 150ns TI	D3 4.45		
4164 200ns TI	D3 3.95		
4164 150ns			
4516 4816 100ns D3	4.45		
4532 200ns	D2 2.95		

<b>INTERFACE DEVICES</b>			
6402	3.80		
75107	0.47		
75110	0.56		
75150	0.64		
75154	0.77		
75160	2.80		
75161	2.56		
75162	3.95		
75172	1.95		
75173	1.44		
75174	1.95		
75175	1.44		
75182	0.50		
75183	0.50		
75188	0.37		
75189	0.37		
75451	0.22		
75452	0.22		
75453	0.22		
75454	0.22		
75468	0.88		
75491	0.33		
75492	0.47		
AY31015	D2 3.00		
AY31270	D1 6.40		
AY38910	D6 4.40		
AY36000	D2 6.70		
DP8304	D1 2.50		
MC1488	D1 0.37		
MC1489	D1 0.37		
MC3242A	D1 6.30		
MC3446	D1 2.50		
MC3448A	D1 3.75		
MC3480	D5 3.00		
MC3487	D1 2.00		
MC14411	D1 7.65		
MC14412	D1 9.45		
RD32513L	D1 6.50		
RD32513U	D1 6.50		

<b>6800 FAMILY</b>			
6800	D7 2.25		
6802	D5 2.50		
6809	D6 6.30		
6810	D1 1.15		
6821	D3 1.00		
6840	D4 3.75		
6845	D5 6.50		
6850	D2 1.10		
68498	D2 1.30		
68B00	D7 5.25		
68B09	D6 12.00		
68B10	D1 2.26		
68B21	D3 2.20		
68B40	D4 6.00		
68B50	D2 2.20		

<b>Z80 FAMILY</b>			
Z80ACPU	D2 2.99		
Z80BCPU	D2 9.00		
Z80ACTC	D1 2.80		
Z80BCTC	D1 9.00		
Z80ADART	D1 5.50		
Z80ADMA	D2 6.95		
Z80AP10	D1 2.75		
Z80BP10	D1 9.00		
Z80AS10	D4 9.00		

<b>UMF MODULATORS</b>			
UM1111 6MHz	D1 2.60		
UM1233 8MHz	D1 3.90		

<b>UMF MODULATORS</b>			
UM1111 6MHz	D1 2.60		
UM1233 8MHz	D1 3.90		

<b>8080 FAMILY</b>			
8085A	D4 3.50		
8212	1.10		
8216	1.10		
8224	2.10		
8228	3.27		
8251A	D5 2.50		
8253	4.00		
8255A	D5 2.25		

TL014	0.36	4010	0.24	04
TL021	0.34	4011	0.10	05
TL061	0.29	4012	0.16	08
TL062	0.49	4013	0.20	09
TL064	0.98	4014	0.40	10
TL065	0.29	4015	0.36	11
TL066	0.32	4016	0.20	12
TL071	0.29	4017	0.12	13
TL072	0.47	4018	0.36	14
TL074	1.00	4019	0.86	15
TL081	0.26	4020	0.36	20
TL082	0.46	4021	0.40	21
TL084	1.58	4022	0.80	22
TL091	0.40	4023	0.13	26

# T.V. SOUND TUNER

## BUILT AND TESTED

In the cut-throat world of consumer electronics, one of the questions designers apparently ponder over is "Will anyone notice if we save money by chopping this out?" In the domestic TV set, one of the first casualties seems to be the sound quality. Small speakers and no tone controls are common and all this is really quite sad, as the TV companies do their best to transmit the highest quality sound. Given this background a compact and independent TV tuner that connects direct to your Hi-Fi is a must for quality reproduction. The unit is mains-operated.

This TV SOUND TUNER offers full UHF coverage with 5 pre-selected tuning controls. It can also be used in conjunction with your video recorder. Dimensions: 11 1/4" x 8 1/2" x 3 1/4". E.T.I. kit version of above without chassis, case and hardware. £12.95 plus £1.50 p&p.



£24.95 + £2.00p&p.

## PRACTICAL ELECTRONICS STEREO CASSETTE RECORDER KIT

COMPLETE WITH CASE

ONLY £31.00 plus £2.75 p&p.

- NOISE REDUCTION SYSTEM. • AUTO STOP. • TAPE COUNTER. • SWITCHABLE E.O. • INDEPENDENT LEVEL CONTROLS. • TWIN V.U. METER. • WOW & FLUTTER 0.1%. • RECORD/PLAYBACK I.C. WITH ELECTRONIC SWITCHING. • FULLY VARIABLE RECORDING BIAS FOR ACCURATE MATCHING OF ALL TYPES.

Kit includes tape transport mechanism, ready punched and back printed quality circuit board and all electronic parts, i.e. semiconductors, resistors, capacitors, hardware, top cover, printed scale and mains transformer. You only supply solder & hook-up wire. Featured in April P.E. reprint 50p. Free with kit.



SPECIAL OFFER!

## STEREO TUNER KIT

This easy to build 3 band stereo AM/FM tuner kit is designed in conjunction with P.E. (July '81). For ease of construction and alignment it incorporates three Mullard modules and an I.C. IF System.

**FEATURES:** VHF, MW, LW Bands, interstation muting and AFC on VHF. Tuning meter. Two back printed PCB's. Ready made chassis and scale. Aerial: AM-ferrite rod, FM-75 or 300 ohms. Stabilised power supply with 'C' core mains transformer. All components supplied are to P.E. strict specification. Front scale size 10 1/2" x 2 1/2" approx. Complete with diagram and instructions.

**SPECIAL OFFER! £13.95 +£2.50p&p.** Self assembly simulated wood cabinet sleeve to suit tuner only. Finish size: 11 1/4" x 8 1/2" x 3 1/4". £3.50 Plus £1.50 p&p.




## STEREO CASSETTE DECK

Stereo cassette tape deck transport with electronics. Manufacturer's surplus - brand new and operational - sold without warranty.

£11.95 plus £2.50 p&p.

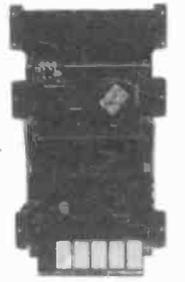Just requires mains transformer and input/output sockets and a volume control to complete. Supplied with full connection details.



## 125W HIGH POWER AMP MODULES

The power amp kit is a module for high power applications - disco units, guitar amplifiers, public address systems and even high power domestic systems. The unit is protected against short circuiting of the load and is safe in an open circuit condition. A large safety margin exists by use of generously rated components, resulting in a high powered rugged unit. The PCB board is back printed, etched and ready to drill for ease of construction and the aluminium chassis is preformed and ready to use. Supplied with all parts, circuit diagrams and instructions.

**ACCESSORIES:** Stereo/mono mains power supply kit with transformer: £10.50 plus £2.00 p&p.



**SPECIFICATIONS:** Max. output power (RMS): 125 W. Operating voltage (DC): 50 - 80 max. Loads: 4 - 16 ohm. Frequency response measured @ 100 watts: 25Hz - 20KHz. Sensitivity for 100w: 400mV @ 47K. Typical T.H.D. @ 50 watts, 4 ohms: 0.1%. Dimensions: 205x90 and 190x36mm.

**KIT £10.50 +£1.15 p&p**      **BUILT £14.25 +£1.15 p&p.**

## AUDAX 8"

**HIGH QUALITY 40 WATTS RMS BASS/MIDRANGE** Ideal for either Hi-Fi or Disco use this speaker features an aluminium voice coil a heavy 70mm diameter magnet. £5.95 +£2.20 P&P.

**AUDAX 40W Ferro-Fluid Hi-Fi Tweeter** X/over on 5kHz - 22kHz. 60mm square. 8 ohm. £5.50 +60p p&p.



## SPEAKER BARGAINS

**2 WAY 10 WATT SPEAKER KIT** B" bass/mid range and 3 1/2" tweeter. Complete with screws, wire, crossover components and cabinet. All wood pre-cut - no cutting required. Finish - chipboard covered wood simulate. size 14 1/2" x 8 1/2" x 4". PAIR for ONLY £12.50 plus £1.75 p&p.



**ALL CALLERS TO: 323 EDGWARE ROAD, LONDON W2. Telephone: 01-723 8432.** (5 minutes walk from Edgware Road Tube Station) Now open 6 days a week 9 - 6. Prices include VAT.



# SUPERKITS!

## NOW WITH NEW CHOICE OF CASES

BOXES SUPPLIED WITH STANDARD UNITS ARE PLAIN ALUMINIUM WITH A LIPPED LID. THE 'BLK' UNITS HAVE ALUMINIUM BOXES WITH STEEL TOP COVERED IN STYLISH BLACK STELVITITE LAMINATE. UNITS MARKED WITH '\*': DO NOT INCLUDE BOXES (FURTHER DETAILS IN LIST).

SETS INCL PCBs, ELECTRONIC PARTS, INSTRUCTIONS. MOST ALSO INCL KNOBS, SKTS, WIRE, SOLDER, BATTERIES NOT INCL BUT MOST WILL RUN FROM 9V TO 15V DC SUPPLIES. FOR FULLER DETAILS SEE CATALOGUE (SEE BELOW).


	STD UNIT	BLK UNIT
AUTOWAH: Guitar-triggered wah-wah	SET 58	£14.01 £16.41
BASS BOOST: Increases volume of lower octaves	SET 138-B	£9.40 £11.80
CALL SIGN: Programmable 8-note musical call sign	SET 121	£14.23 £16.23
CHORUS UNIT: A solo voice or instr. sounds like more!	SET 162	£31.59 £34.49
COMPARATOR: LED level indicator for 2 channels	SET 129	£16.73 £18.73
COMPRESSOR: Limits & levels maximum signal strength	SET 133	£12.37 £14.77
ECHO UNIT: With double tracking	SET 168	£44.82 £47.72
FREQUENCY DOUBLER: Raises guitar frequency by 1 octave	SET 98	£11.75 £13.75
FREQUENCY-GENERATOR: Multiple waveform test osc	SET 128	£19.15 £22.05
FUNNY-WOBULO: Novelty voice modulator for funny effects	SET 149	£12.78 £14.78
FLANGER: Fascinating delayed-feed-back effects plus phasing	SET 153	£22.54 £25.44
FUZZ: Smooth distortion whilst keeping natural attack & decay	SET 91	£11.68 £14.08
GUITAR EFFECTS: Multiple variation of level & filter modulation	SET 42	£16.58 £18.38
GUITAR OVERDRIVE: Fuzz plus variable filter quality	SET 56	£21.17 £24.07
GUITAR SUSTAIN: Extends effective note duration	SET 75	£11.77 £14.17
HARMONOLA: Versatile 3 octave organ*	SET 125-T	£166.97 —
HUM CUT: Tunable filter for reducing low frequency noise	SET 141	£12.02 £14.42
JABBERVOX: Voice disguiser with reverb & tremolo	SET 150	£23.64 £25.44
MAD-ROJ: Variable sirens, incl. police, galaxy machine-guns etc	SET 146	£10.47 £12.47
METRONOME: With audible & visual beat & down-beat marking	SET 143	£13.98 £15.98
MICROPHONE PRE-AMP: with switchable bass & treble response	SET 144	£9.12 £11.52
MINISONIC (PE) MK2: 3-octave very versatile music synthesiser*	SET 38	£181.92 —
MIXERS: Several - details in catalogue (see below)		
NOISE LIMITER: reduces tape & system hiss	SET 145	£10.59 £12.99
PHASER: with automatic & manual rate & depth controls	SET 164	£21.20 £24.10
REVERB: Analogue unit with variable delay & depth controls	SET 122	£20.39 £22.19
RHYTHM GENERATOR: 15 switchable rhythms (NEW UNIT)	SET 170	£38.27 £41.17
RING MODULATOR: for intermodulating 2 separate sine freqs.	SET 87	£13.62 £15.42
ROBO BOX: Versatile Robot type voice modifier	SET 165	£21.89 £24.79
ROGER 2-GONG: 2 gongs sounded at end of transmission	SET 126-LS	£12.55 £14.55
ROGER BLEEP: Single bleep sounded at end of transmission	SET 127-LS	£10.07 £12.47
SCRAMBLER: Codes & decodes transmissions authorised chans	SET 117	£21.81 £23.61
SEQUENCERS: 128-note keyboard controlled (keyboard incl.)	SET 76	£110.99 £114.59
16 note (up to 64-bit pattern) panel controlled	SET 86	£53.15 £56.95
SPEECH PROCESSOR: for clearer transmission	SET 110	£12.10 £14.50
STORM EFFECTS: Automatic & manual wind, rain & surf	SET 154	£16.72 £19.62
SWEEP GENERATOR: Audio test unit	SET 169	£16.42 £18.22
SYNTHESISER INTERFACE: allows instrument to trigger synth	SET 81	£9.59 £11.99
TREMOLO: Deep tremolo with depth & rate controls	SET 136	£10.71 £13.11
TREBLE BOOST: Increases volume of upper octaves	SET 138-T	£9.24 £11.64
TONE CONTROL: bass & treble cut, gain & range (6 controls)	SET 139	£13.82 £16.72
VIBRATO: variable rate & depth plus additional phasing	SET 137	£23.99 £26.79
VOCODAVOX: Modular Vocoder	SET 152	£68.96 £72.76
VODALEK: Robot type voice modulator with depth & rate controls	SET 155	£12.75 £14.75
VOICE FILTER: tunable for selected freq bandwidth & gain	SET 142	£10.21 £12.61
VOICE-OP-FADER: for reduction of music level during talk-over	SET 30	£10.02 £12.42
VOICE-OP-SWITCH: with variable sensitivity & delay	SET 123-LS	£13.80 £15.80
WAH-WAH: with auto-trigger, manual & oscillator control	SET 140	£17.31 £20.21
WHEEBY—JEEBY: 2 intercoupled oscillators produce variable sirens	SET 151	£13.78 £15.58
WIND & RAIN: manual control of these two effects	SET 28	£11.39 £13.79
WOBBLE-WAH: Oscillator controlled wah-wah	SET 161	£13.40 £15.40

**KIMBER ALLEN KEYBOARDS (surely the best?):** 3-Oct £32.43, 4-Oct £40.68, 5-Oct £48.52  
**KEYBOARD CONTACTS GJ (SPCO):** 3-Oct £20.29, 4-Oct £26.50, 5-Oct £32.71  
**KEYBOARD CONTACTS GB (DPST):** 3-Oct £23.27, 4-Oct £30.45, 5-Oct £37.62
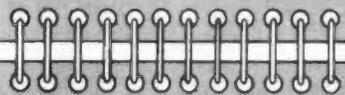
# PHONOSONICS

PHONOSONICS MAIL ORDER, DEPT P38, 22 HIGH STREET, SIUCCP, KENT DA14 6EH. 01-302 6184

Please use full address. Payment CWO, CHQ, PO, Access, Barclay, or pre-arranged collection. Prices incl UK P&P & 15% VAT. E&OE. Despatch usually 10-14 days on most items. For comprehensive catalogue send S.A.E. (if you live overseas send £1.00 or equiv.). MORE KITS ARE IN CATALOGUE.



# INDUSTRY NOTEBOOK

By Nexus



## Go-Ahead

The recommendations of the Alvey Committee that some £300 million should be invested in a cooperative research programme on advanced information technology have been endorsed by the Government. The taxpayers' contribution via the Department of Education and Science, the Ministry of Defence and the Department of Industry will cover half the cost with the remainder coming from industry. Hard-cash involvement by industry should ensure that research will be down-to-earth with marketable end-products both in software and hardware.

The Department of Industry will run the programme through a five-member directorate under Brian Oakley, seconded from his post as head of the Science and Engineering Research Council, and the directorate will report to a supervisory board of industrialists headed by Sir Robert Telford who is chairman of Marconi.

The Cabling of Britain programme has also got the go-ahead with the publication of the Government White Paper. It will be recalled that when first mooted the idea was universally applauded. Since that early flush of enthusiasm potential investors and manufacturers have had second thoughts. The flop of TV-am and generally reduced viewing figures suggest that a possible 30 channels of cable TV will not be a licence to print money. Those days are gone. Nonetheless, if cabling goes ahead as it inevitably will there will be a steady living as a reward for success.

Predictably the Opposition wanted monopoly powers granted to British Telecom and complained that the whole idea was divisive in that some poor people may not be able to afford the service. But, of course, there is nothing to prevent BT competing in the market and BT's chairman, Sir George Jefferson, positively welcomed the go-ahead and appointed Donald Wray as supremo of BT's spearhead thrust into the whole area of broadband local networks including interactive services. The argument on divisiveness is

plainly silly. Few of us can afford to motor in a Rolls-Royce but that is no reason why luxury cars shouldn't be built for those who can. The provisional indication of a £5 per week subscription is hardly likely to deter keen viewers.

Industry will benefit almost immediately. Racal-Oak have announced a £3 million initial contract from British Telecom for the supply of decoding equipment which ensures that viewers can access only those programmes and services to which they have subscribed.

## Inmos

Since my last comment on Inmos the company has revealed at a press conference the latest state of play. For newcomers, Inmos was born in 1978 during Labour's last administration using as midwife the National Enterprise Board who were to finance the company with £50 million in two instalments of £25 million. The objective was to build up an all-British VLSI chip capability while at the same time creating 4,000 new jobs in the UK. The business target was set at £150 million of profitable turnover by 1984.

Inmos started trading in 1981 and in that year (to December 31) achieved £2.1 million turnover with a trading loss of £13 million. Last year sales accelerated to £13.7 million and the loss rose to £20.4 million. This year turnover is running at some £20 million, whether profitably or not is as yet unclear.

Total new jobs created in the UK are 275, expected to increase to 575 during the coming year. Current forecast is that no more than 1,000 jobs will be available at the Newport, Gwent, factory and a second factory, scheduled in the original plans, is not shelved but certainly far in the future.

All is not gloom. The Transputer, described as a single-chip micro-computer, should hit the market at the end of next year although not contributing profit until 1985. Meantime the memory products can reasonably expect to be generating profits as the capacity for high volume production at Newport is steadily increased.

## Back-Up

No manufacturer can succeed without adequate after-sales service. But good engineers are in short supply, transport costs are high and hotels and meals don't get any cheaper. But even more important than cost is speed and quality of service on which the whole reputation of a company may well depend.

Engineering for reliability, testability and maintainability has made great advances in electronics manufacturing and overall reliability has greatly improved through LSI and other modern techniques. Against this there is the ever-increasing complexity of equipment and systems. At the end of the day things can and do go wrong and service engineers continue to be needed.

With high costs and a shortage of skilled people is there a better way of organising service visits, particularly those occasioned by panic? Digital Equipment has found an

answer not by putting more men on the road but taking their most skilled engineers off the road completely.

Not for them the tedium of traffic jams or living out of a suitcase. Instead, 16 of the best are housed in air-conditioned comfort at the company's Basingstoke customer service centre, offering a 24hr service.

The key to successful service is diagnosis and it is in this key role that the Basingstoke experts excel. Once the fault has been pin-pointed to component or, at worst, p.c.b. level, rectification is a simple matter and can be completed by a less skilled travelling engineer.

The operation depends on a data communications network over which the Basingstoke diagnosticians can access the faulty DEC minicomputer and, backed up by a large mainframe computer, perform powerful test routines even though the remote faulty mini may be hundreds of miles away. The European network is continually extended as every new DEC mini delivered is supplied with the necessary modem and auto-dialler to complete the remote testing link.

So now the experts, instead of making one or at most two service calls a day, can service many more just by staying put.

## Upturn

It is now clear that the current upturn in activity started last year with an increase in consumer spending. It is heartening to report that consumer electronics is back in business after so long in the doldrums. TV sales were a record last year and this year looks even better. Home computers are a brisk and expanding market and it is a pity that of over two million VTRs sold in the UK none were manufactured here.

Capital equipment sales remain buoyant with the defence sector aided by the replacement programme following the Falklands campaign. The Electronic Engineering Association reported an eight percent increase in output during the past year at £2,125 million. Direct exports totalled £740 million but is probably about £1,000 million after taking account of equipment fitted in, for example, aircraft or other systems sold as a complete package.

Some sectors have fared better than others. Marine electronics has slipped back as a direct reflection of the world slump in shipping. The UK market for military tactical radio has slackened now that the British army has been re-equipped but exports are still doing well. Avionics remains in the superstar class and won Marconi Avionics two Queen's Awards this year, one each in technology and exports. Latest Marconi scoop is a £25 million order from the Royal Australian Air Force for airborne anti-submarine systems. The company has also teamed with Honeywell in military application of ring laser gyroscopes for inertial navigation.

The EEA reports a drop in employment in the capital goods sector of three percent to 98,000, the result of modernisation in manufacturing and assembly techniques. A chief constraint to rapid expansion is the shortage of engineers, a perennial problem.

# LOGIC ANALYSER

Part One  
D. MANDELZWEIG

IT IS evident by looking at recent projects in this magazine, that digital electronics in general, and microprocessors in particular, are playing an ever-increasing role in amateur projects. Many hobbyists are designing their own, building from kits, or just using home computers. There comes a time when it is necessary to test new designs, debug built projects, or fault-find digital circuitry. The most useful piece of test equipment for this is a logic analyser. However, due to the price of commercially available equipment, such a luxury is normally out of reach of the amateur.

The logic analyser to be described was designed to overcome this problem. The unit is used with an oscilloscope (when the 'scope display option is fitted), a piece of test equipment more easily affordable to the hobbyist. With a guaranteed maximum working frequency of 5MHz (the prototype worked to 7.9MHz), the analyser can cope with nearly all microprocessor systems found in the home today. Even systems working at a faster clock frequency can be tested by running the system (while testing) at a lower clock frequency. Comparison of the logic analyser's specifications (see Table 1.1) with those of commercially available units shows that the facilities offered compare favourably, for a much smaller outlay.

The analyser was designed to be as modular as possible. This allows the power of the analyser to be increased as and when it is needed, and is affordable. Five options can be fitted to the basic unit. Only one option is required to have a useful instrument. All the options are plug-in, and therefore have retrofit capability, and can be fitted in virtually any order.


Since the majority of microprocessors run with a clock frequency less than 5MHz, and it was a design requirement to be able to test 5MHz systems, the use of a  $\mu$ P was ruled out. However, even using Schottky TTL, some clever use had to be made of available i.c.s, in order to achieve the design requirement. For this reason, it may still be of interest to readers who do not intend building the unit to read the paragraphs on the circuit operation description.

## WHAT IS A LOGIC ANALYSER?

An oscilloscope can display two (four on expensive models) traces of real-time information. When testing digital circuits, it is useful to be able to see the timing relationship between various signals, or alternatively, if looking for example at a data bus, to be able to look at the sequential data being put out on the bus. A logic analyser enables one to do this. Synchronously with the clock of the system under test, it captures and stores a number (depending on the memory size) of bytes, each byte being 8, 16 or 32 bits wide, depending on the design. The analyser then subsequently displays the timing diagram of the captured data on a CRT

display. In order to make the analyser more useful, a number of facilities are usually incorporated. As mentioned, the analyser can be driven synchronously with an external clock. When using the external clock, the negative or positive edge can be selected, and clock qualifiers are provided. These can be switch-selected such that a logical 1, 0 or X (don't care) makes the input valid, so that external signals can control when the analyser stores information. There are usually three methods of triggering an analyser to start (or stop) storing data. A word recogniser can be used to compare the incoming data with a previously set up bank of switches (one switch for each input, allowing a 1, 0 or X to be selected) when the data is equal to the present word, the analyser is triggered. An external input, with the rising or falling edge selectable, is also provided for triggering, or manual trigger is possible with a switch. To further enhance the triggering capability, the user can select how the analyser must store the data with respect to the trigger. The trigger can be used to stop storing data (for a 1K byte memory, the analyser will store 1024 bytes *before* the trigger occurs), called post trigger, start storing data on the trigger (store 1024 bytes *after* the trigger), called pre trigger, or store 512 bytes *before* and 512 bytes *after* the trigger, called centre trigger. A more detailed explanation of the uses and working of these facilities will be given below. Since it is normally impossible to display all the bytes of data stored simultaneously (the display would be unreadable) only a portion of the memory is displayed, and the user can scan up and down the memory. Expand facilities can also be provided, so that although less bytes are displayed, more display resolution is achieved. The more expensive analysers provide cursors which can be moved across the display. Some also provide the capability to store two sets of data in two separate memories, and then compare the memories for differences.

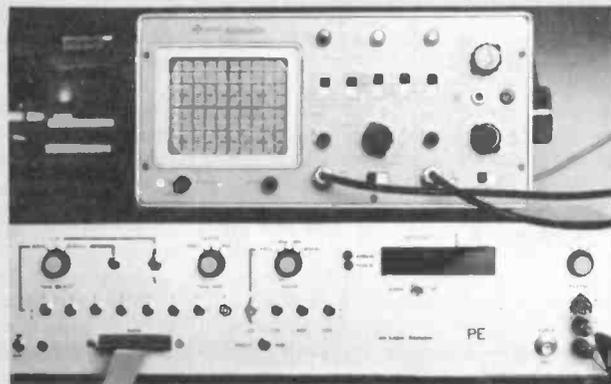This logic analyser includes most of these facilities. Eight input lines and a 1K x 8 memory allow 1K bytes of 8 bit



# SPECIFICATION

**TABLE 1.1. Specifications, modes and facilities**

DATA IN:	NO. OF INPUT LINES : 8 INPUT LOAD : 1 LSTTL LOAD EACH DATA MUST BE VALID AT THE RISING (FALLING) EDGE OF THE INPUT CLOCK DATA HOLD TIME : 60ns (ie DATA must be valid for at least 60ns after the rising (falling) edge of the clock occurs) STORAGE DEPTH : 1024 BYTES OPTIONAL : CMOS HI-Z INPUTS						
CLOCK:	<table border="0" style="width: 100%;"> <tr> <td style="width: 30%; vertical-align: top;">           EXT IN (Synchronous)         </td> <td style="vertical-align: top;">           : MAX 5MHz            RISING (FALLING) EDGE SELECTABLE CLOCK MUST BE HIGH (LOW) FOR 50ns MIN            INPUT LOAD : 1 LSTTL            MIN MARK OR SPACE : 60ns            : (OPTIONAL)         </td> </tr> <tr> <td style="vertical-align: top;">           INTERNAL (Asynchronous)         </td> <td style="vertical-align: top;">           5MHz CRYSTAL CONTROLLED            5MHz, 1MHz, 100kHz SELECTABLE FOR ASYNCHRONOUS OPERATION         </td> </tr> </table> <p style="margin-top: 10px;">When SYNCH clock is selected, 5MHz is available for synchronisation or as a clock drive at CLOCK OUT. When either 5MHz, 1MHz, or 100kHz asynchronous clock is selected, then the selected frequency is available at CLOCK OUT.</p>	EXT IN (Synchronous)	: MAX 5MHz RISING (FALLING) EDGE SELECTABLE CLOCK MUST BE HIGH (LOW) FOR 50ns MIN INPUT LOAD : 1 LSTTL MIN MARK OR SPACE : 60ns : (OPTIONAL)	INTERNAL (Asynchronous)	5MHz CRYSTAL CONTROLLED 5MHz, 1MHz, 100kHz SELECTABLE FOR ASYNCHRONOUS OPERATION		
EXT IN (Synchronous)	: MAX 5MHz RISING (FALLING) EDGE SELECTABLE CLOCK MUST BE HIGH (LOW) FOR 50ns MIN INPUT LOAD : 1 LSTTL MIN MARK OR SPACE : 60ns : (OPTIONAL)						
INTERNAL (Asynchronous)	5MHz CRYSTAL CONTROLLED 5MHz, 1MHz, 100kHz SELECTABLE FOR ASYNCHRONOUS OPERATION						
CLOCK OUT:	SEE OPTIONAL INTERNAL CLOCK ABOVE						
CLOCK QUALIFIERS:	NUMBER: 3 POS OR NEG LEVEL SENSITIVE Any or all may be chosen as negative, positive or don't care.  LEVELS MUST BE VALID A MINIMUM OF 2 <sub>fs</sub> BEFORE THE CLOCK EDGE.  NOTE: The qualifiers are level sensitive, and must be valid for the duration of the sample.						
ARMING:	THE UNIT IS MANUALLY ARMED, AND CAN BE RESET AT ANY TIME.  NOTE: To ensure that all old data is overwritten by the new data when POST or CENTRE trigger is selected, the unit must be armed at least $\frac{1024}{f_{in}}$ secs before the trigger occurs.						
TRIGGERING:	<table border="0" style="width: 100%;"> <tr> <td style="width: 30%;">WORD RECOGNISER</td> <td>: SELECT INPUT WORD ON SWITCHES, INCLUDING DON'T CARES.</td> </tr> <tr> <td>EXT TRIG</td> <td>: RISING OR FALLING EDGE SELECTABLE TRIGGER IS EDGE SENSITIVE TRIGGER MUST OCCUR WITHIN 70ns OF THE RISING (FALLING) EDGE OF THE CLOCK</td> </tr> <tr> <td>MANUAL TRIGGER TRIGGER SELECT</td> <td>: MANUAL SWITCH : PRE TRIGGER, POST TRIGGER OR CENTRE TRIGGER SELECTABLE.</td> </tr> </table>	WORD RECOGNISER	: SELECT INPUT WORD ON SWITCHES, INCLUDING DON'T CARES.	EXT TRIG	: RISING OR FALLING EDGE SELECTABLE TRIGGER IS EDGE SENSITIVE TRIGGER MUST OCCUR WITHIN 70ns OF THE RISING (FALLING) EDGE OF THE CLOCK	MANUAL TRIGGER TRIGGER SELECT	: MANUAL SWITCH : PRE TRIGGER, POST TRIGGER OR CENTRE TRIGGER SELECTABLE.
WORD RECOGNISER	: SELECT INPUT WORD ON SWITCHES, INCLUDING DON'T CARES.						
EXT TRIG	: RISING OR FALLING EDGE SELECTABLE TRIGGER IS EDGE SENSITIVE TRIGGER MUST OCCUR WITHIN 70ns OF THE RISING (FALLING) EDGE OF THE CLOCK						
MANUAL TRIGGER TRIGGER SELECT	: MANUAL SWITCH : PRE TRIGGER, POST TRIGGER OR CENTRE TRIGGER SELECTABLE.						
DISPLAY MODES:	<table border="0" style="width: 100%;"> <tr> <td style="width: 30%;">HEX DATA DISPLAY</td> <td>(OPTION 2) 2 DIGIT HEX DISPLAY OF DATA BYTE. ANY DATA BYTE WITH RESPECT TO THE TRIGGER WORD CAN BE DISPLAYED BY THE UP/DOWN SWITCH. THERE IS A DECIMAL DISPLAY OF THE ADDRESS OF THE DATA WORD BEING DISPLAYED</td> </tr> <tr> <td>SCOPE DISPLAY</td> <td>(OPTION 1) DISPLAYS 8 BITS BY 32 or 16 BYTES. THE START BYTE IS SELECTED BY THE UP/DOWN SWITCH, AND THE DECIMAL DISPLAY SHOWS THE ADDRESS OF THE START BYTE. BOTH OPTIONS MAY BE FITTED SIMULTANEOUSLY. IF THE SCOPE OPTION IS USED, A FURTHER OPTION MAY BE ADDED. THIS OPTION HIGHLIGHTS THE TRIGGER WORD WHEN IT IS DISPLAYED ON THE SCOPE.</td> </tr> </table>	HEX DATA DISPLAY	(OPTION 2) 2 DIGIT HEX DISPLAY OF DATA BYTE. ANY DATA BYTE WITH RESPECT TO THE TRIGGER WORD CAN BE DISPLAYED BY THE UP/DOWN SWITCH. THERE IS A DECIMAL DISPLAY OF THE ADDRESS OF THE DATA WORD BEING DISPLAYED	SCOPE DISPLAY	(OPTION 1) DISPLAYS 8 BITS BY 32 or 16 BYTES. THE START BYTE IS SELECTED BY THE UP/DOWN SWITCH, AND THE DECIMAL DISPLAY SHOWS THE ADDRESS OF THE START BYTE. BOTH OPTIONS MAY BE FITTED SIMULTANEOUSLY. IF THE SCOPE OPTION IS USED, A FURTHER OPTION MAY BE ADDED. THIS OPTION HIGHLIGHTS THE TRIGGER WORD WHEN IT IS DISPLAYED ON THE SCOPE.		
HEX DATA DISPLAY	(OPTION 2) 2 DIGIT HEX DISPLAY OF DATA BYTE. ANY DATA BYTE WITH RESPECT TO THE TRIGGER WORD CAN BE DISPLAYED BY THE UP/DOWN SWITCH. THERE IS A DECIMAL DISPLAY OF THE ADDRESS OF THE DATA WORD BEING DISPLAYED						
SCOPE DISPLAY	(OPTION 1) DISPLAYS 8 BITS BY 32 or 16 BYTES. THE START BYTE IS SELECTED BY THE UP/DOWN SWITCH, AND THE DECIMAL DISPLAY SHOWS THE ADDRESS OF THE START BYTE. BOTH OPTIONS MAY BE FITTED SIMULTANEOUSLY. IF THE SCOPE OPTION IS USED, A FURTHER OPTION MAY BE ADDED. THIS OPTION HIGHLIGHTS THE TRIGGER WORD WHEN IT IS DISPLAYED ON THE SCOPE.						

data words to be stored. The analyser has an external clock input (up to 5MHz), with the clock edge switch selectable. Three clock qualifiers are provided, and each can be selected for a 1, 0 or X. With the clock option fitted, the analyser can also run asynchronously at three selectable frequencies—5MHz, 1MHz and 100kHz. The selected clock frequency is buffered and is brought out to the front panel, so that the circuit under test can be driven by the analyser's clock. The three modes of triggering discussed above are provided: external (edge selectable), manual, and word recogniser. A bank of 8 switches is provided for this, and each input line can individually be set for a 1, 0 or X. The analyser allows the selection of pre, centre and post triggering as defined above. Two data display options are possible, one of which must be fitted to make the unit useful, although both can be fitted if desired. The one option displays 64 bytes by 8 bits (8 traces) of timing diagrams on a normal oscilloscope display (the oscilloscope must be a dual trace one with X-Y capability). The display can be expanded so that only 32 or 16 bytes are displayed. The display can also be scanned up and down the memory. The other option allows the Hex value of the data to be displayed on two 7-segment displays. For both options, a 4-digit display indicates the address of the data byte with respect to the trigger point for either the data being displayed in Hex for the Hex display option, or the first data byte of the set of 16, 32 or 64 bytes being displayed by the scope option. When both options are installed, the Hex data corresponds to the first (left-most) byte being displayed on the scope. A further option available which can only be used in conjunction with the scope display option, uses the Z-MOD input of the oscilloscope to brighten up the

trigger byte (the byte at which the analyser was triggered) when that byte is being displayed on the oscilloscope. Finally, the basic analyser accepts TTL compatible inputs, however the last option available will allow the testing of CMOS or other circuitry, at user defined supply rails.

## SPECIFICATIONS

A complete list of specifications is given in Table 1.1, and these are self-explanatory. Perhaps the only extra explanation required is that of ARMing. Normally the analyser is in the display mode, displaying previously captured data. To get the analyser ready to capture new data, the unit must be ARMed. This is done manually with a switch, and when it occurs, the ARM l.e.d. lights, the data being displayed becomes invalid, and the analyser awaits the trigger. During this time, the analyser is storing data, so that when a trigger comes, and POST triggering, for example, has been selected, the analyser can stop storing data immediately. If the trigger arrives too soon after the analyser is armed, then in this case (POST triggering) the memory will not be completely overwritten, and some old data will remain. This is the reason for the note given in the specifications. In any event, when the trigger arrives, the TRIG l.e.d. lights, and both remain on until the data has been stored. At this point, the l.e.d.s extinguish, and the analyser automatically reverts to displaying the new data. At any stage, the ARM/RESET switch can be used to reset the analyser from the ARMed state to the display state.

## CIRCUIT DESCRIPTION

Before considering how the circuit works, it is necessary to keep two factors in mind. The first is that with a 5MHz clock, only 200ns is available to do the following: increment the RAM address, check for a valid trigger, generate the Write pulse to the RAM, and then be ready to repeat the sequence. A look at the circuit diagram shows that signals

Fig. 1.1. Analyser timing diagram

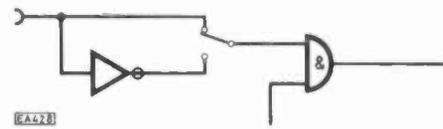
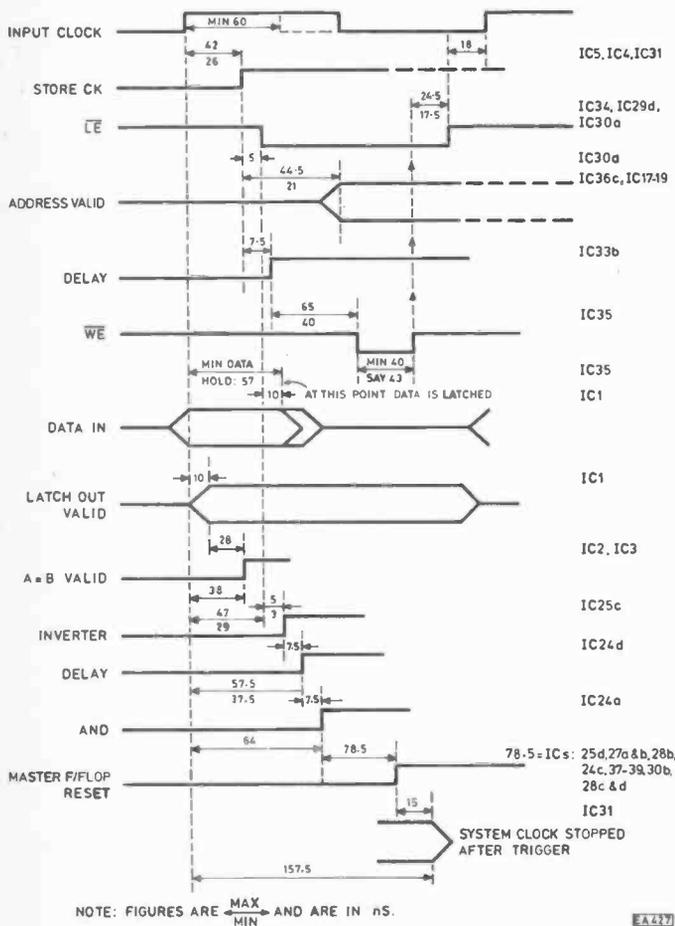


Fig. 1.2. Simple positive/negative selection

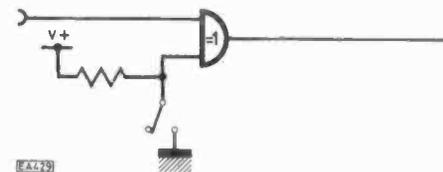


Fig. 1.3. Improved positive/negative selection

have to pass through quite a few i.c.s, and the propagation delays through each begin to add up. For this reason, one has to firstly be careful that the total worst case time to complete a cycle does not exceed 200ns, and secondly that the Enable, Latch, Data, and Clock pulses are generated in the correct time slots and sequence, to ensure reliable operation. With the aid of the timing diagram shown in Fig. 1.1, we will be looking at how correct timing was achieved.

The second factor concerns data skew. For example, consider the EXT. TRIG. input where either positive or negative edge triggering is possible. A simple way to achieve selection is shown in Fig. 1.2. The problem with this circuit is that:

1. When negative edge is selected, the input sees only one gate input, and when positive edge triggered, the input sees two gates.
2. Because of the extra inverter, the propagation delay for negative edge triggering is longer than that for positive edge triggering.

To overcome this, the circuit of Fig. 1.3 is used. This circuit has one further advantage, that the input signal itself is not physically switched—the switching is done by a d.c. level applied to the EX-OR gate. This second factor also applies to the clock and qualifiers' inputs, as well as to the word recogniser. In these two cases a different method was used to overcome the problem.

Refer to Figs. 1.4, 1.5 and 1.6 for the block diagram, front panel circuitry, and main board circuitry respectively. Assume that the unit is on, and has been reset. We now want to store data, so we must ARM the analyser using switch S16. This sets the master flip-flop consisting of IC28c & d L (low) on STORE, and H (high) on STORE become valid, with the following effect: IC1's outputs become valid (no longer in Tri-State). IC15 gates data from the data bus to the RAM, the RAM is put in the WRITE mode, IC27b and IC31 are enabled. Depending on the setting of S14, IC31 selects either the SYNC CLOCK, or one of the three asynchronous clock frequencies from the CLOCK OPTION, if it is fitted. Since the inputs to the i.c. are paralleled to both halves of the i.c., the same selected clock appears at both outputs (except in the case of SYNC CLOCK

selection, where the internal 5MHz clock appears at output 2Y). Thus the internal clock frequencies are buffered and made available at SK7 on the front panel. The output of 1Y is called the STORE CK. Normal gates were considered for the selection of STORE CK, but calculations of propagation delays proved that using IC31 would be faster, with the advantage of a smaller total chip count. Assume now that the SYNCH CLOCK has been selected. However, before continuing with the STORE CK, let us see how the SYNCH CLOCK was derived. Since the clock qualifiers must act on the input clock, some sort of gating must be incorporated. We also want to be able to select positive or negative clock edge, and the qualifier level. At the same time we must be careful of data skew. To solve the problem, all four inputs are buffered with a single LS TTL gate (IC5) each. This allows the lowest possible load to be applied to the circuit under test. The clock and qualifier inputs are fed to one set of inputs of a 4-bit magnitude comparator, IC4. The i.c. gives an output on pin 6 only when all the bits in one set of inputs correspond to the bits in the second set of inputs. Consider selecting positive edge for the CLOCK, positive level for CQ1, negative level for CQ2, and don't care for CQ3. For CQ1 positive, B2 input is low, and thus S2a is switched such that A2 is low. Similarly, for CQ2, B3 will be high, and with S3a in the position shown, R20 will hold A3 high. In the don't care case, S4 is switched such that R25 and R21 pull B4 and A4 high respectively. So when the correct inputs are applied to the qualifiers, the respective B inputs will be equal to the A inputs. For positive clock edge S1a wiper is at 0V, i.e. A1 is low, when the clock goes high, B1 will become low (due to the inverter) and because these inputs as well as the qualifier inputs are now equal, IC4 pin 6 goes high. When the clock falls, A1 is not equal to B1, so pin 6 goes low, and

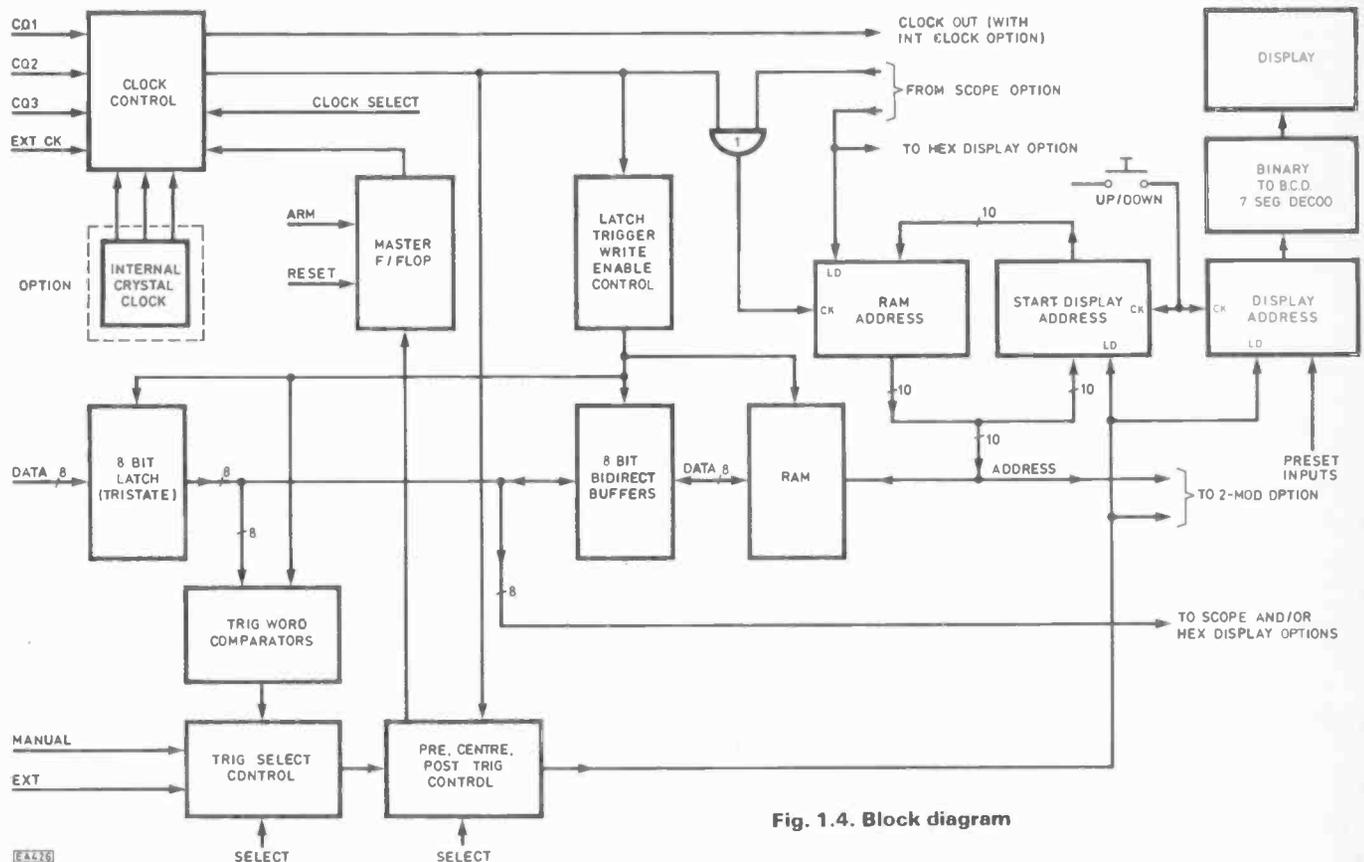


Fig. 1.4. Block diagram

thus follows the input clock. If a qualifier became invalid, the clock would stop, and that if negative clock edge is selected, the output at pin 6 would be an inverted version of the input clock. By the use of only one i.c., all the clock functions have been implemented, propagation delay has been kept to a minimum, and data skew has been avoided, as all inputs to the i.c. have similar propagation delays through the i.c.

Now to come back to the STORE CK. IC24b has been disabled by L on STORE, and its output is high. The STORE CK passes through IC36c, and is applied to the RAM address counters' clocks (ICs 17–19). Pin 1 of IC23a is low, and therefore pin 3 is high, with the result that the LD inputs of the RAM counters are high. Therefore the counters are being clocked, and the RAM is being addressed in time with the input clock. Now every time IC31 pin 7 (STORE CK) goes high, the output of IC30a ( $\overline{LE}$ ) goes low, latching the data into IC1. There are two further requirements of the STORE CK. Firstly a WRITE pulse with a minimum width of 40ns must be generated to store the data in the RAM, but only when the address and the data are valid. Secondly, the input latch, IC1, must remain latched for just long enough so that the memory stores valid data. The circuit works like this. When the analyser is ARMED, H on STORE goes high, and this sets the Q1 and Q2 outputs of IC34 (via the CLR inputs) to low. The output of IC29d is thus low, and because pin 12 of IC31 is still low,  $\overline{LE}$  is high. When the STORE CK goes high,  $\overline{LE}$  goes low, and the input data is latched. One cannot rely on the STORE CK to hold  $\overline{LE}$  low, because for a 1:1 mark-space ratio 5MHz clock, the high level is only valid for 100ns which, as we will see, is too short. So what happens is that the STORE CK clocks the first D-TYPE, and Q1 goes high. IC29d output thus goes high, and now regardless of whether the STORE CK falls away or not,  $\overline{LE}$  remains low. Q1 of IC35 goes low after the propagation delays of IC33b and IC35, and remains low for approximately 43ns, which is long enough to write the data into RAM. On the rising edge of Q1 (IC35), Q2 of IC34 is clocked high, IC29d goes low, and if the STORE CK has become low,  $\overline{LE}$  once again becomes high. If STORE CK is not yet low,  $\overline{LE}$  will remain low until this occurs. When the next STORE CK comes, the sequence is repeated. With this little bit of circuitry then, input data is latched, held long enough to be stored, the store pulse ( $\overline{WE}$ ) is produced, and the latch is disabled once again.

At this stage we have the input clock clocking the RAM, and input data being stored in the RAM. The counters IC17 to IC19 are cycling through a count of 1023. Now we must consider the trigger circuitry. The type of trigger is selected by S19, and IC25a, b & d. Manual trigger is simple: IC26 produces a pulse, IC25b goes low, IC27a goes high and IC27b goes low. EXT works similarly, with IC29c and S18 allowing the rising or falling edge to be selected. For this case S19 enables IC25a.

## WORD RECOGNISER

The word recogniser works in a similar fashion to the clock and its qualifiers, in that the incoming data is compared to data set up on switches S6 to S13. ICs 2 and 3 do the comparison, and produce a high level output when the data sets are equal. This output is gated via IC24a through IC25d to IC27a, if the word recogniser trigger has been selected. The requirement for gating the output is that a false trigger may occur while the latch outputs are settling, or input data is changing. To avoid this,  $\overline{LE}$ , suitably inverted (by IC25c) and delayed (IC24d) to allow for latch settling time, only enables IC24a when the data at the output of IC1 is valid.

Now when IC27b goes low, the flip-flop consisting of

IC28a & b sets. The flip-flop is capacitively coupled, and this allows pin 5 to go high even if IC27b stays low so that the flip-flop can be reset when necessary (this ensures that triggering is only edge sensitive for all the triggering modes). IC28a goes low, lighting the TRIG l.e.d. The flip-flop consisting of IC30c & d is set by IC28b via C7, which again allows the second flip-flop to reset before the first one does. The flip-flop triggers the monostable IC32, which provides a positive and negative pulse. The positive pulse is used to reset the second flip-flop, and also for the Z-MOD option, to be described in a future part. The reason for the second flip-flop being necessary, as will shortly be explained, is that the first flip-flop can be reset immediately after being set. Thus the time for which the flip-flop is set is virtually that of the propagation delays of two STTL gates, being approximately 10ns. Since a 74121 requires a minimum input pulse of 50ns, this lengthened pulse is provided by the second flip-flop. The negative pulse produced by IC32 (ADL) firstly loads the address that was on the address bus into ICs 20–22, so that the address at which the analyser was triggered, is stored. ADL also loads the preset binary number 0, 511 or 1023, depending on S5 into the counters ICs 7–9. IC10 and IC11, two EPROMS, decode the binary number into BCD, and the number is displayed on displays 1–4. Thus the display is preset with a number depending on which TRIG POSITION is selected—0 for POST, 511 for CENTRE, or 1023 for PRE trigger. With IC28b output low, counters IC37–39 are preset to zero, and when POST goes high, the counters and IC24c are enabled. This allows STORE CK to clock ICs 37–39. Again, depending on position of S5, either POST, or QA or QB is switched to IC30b. If PRE trigger is selected, QB is connected, allowing the counter to count to 1023 before a pulse is produced which resets the main flip-flop. The count of 1023 allows the memory to be filled with 1K of data from when the trigger occurs. In other words, the analyser was triggered to start storing data, and this is thus called PRE-trigger. If CENTRE trigger is selected, the counters count to 511 before resetting the main flip-flop. Here the memory is only filled with 512 bytes of data after the trigger and thus contains 512 bytes of stored data before the trigger occurred. Hence the name centre trigger.

## POST TRIGGER

Finally for POST trigger, it is required that the analyser stops storing immediately, so POST signal is connected directly to the reset. As can now be seen, when POST is selected, IC28b causes itself to be reset via the switch and IC30b, and for this reason IC30c & d are required as explained above. Once the main flip-flop and IC28a & b have been reset, the ARM and TRIG l.e.d.s extinguish, IC1 becomes Tristate, IC15 gates RAM data to the data bus, the RAM goes into its read mode, IC31 (and thus the STORE CK) is disabled, and ICs 17–19 have their LD input taken low by IC23a, so that the trigger address loaded into ICs 20–22 now passes through ICs 17–19. This means that the data stored when the analyser was triggered is on the data bus, and the data corresponds to the trigger position being displayed on the address display. If POST trigger had been selected, 0 would be displayed, showing that the data byte on the bus is the first data byte stored, i.e. the trigger data byte. For CENTRE trigger, 511 would be displayed, implying that the trigger data byte is in the middle of the RAM, and similarly, for PRE trigger, 1023 will be displayed, indicating that the trigger byte was the last byte stored. Before discussing briefly how the data is displayed (the display options will be described in Part 3), let us now look at the timing diagram, Fig. 1.1.

## SYSTEM TIMING

We will take the rising edge of the input clock as reference. Using maximum and minimum propagation delays as given in the Texas Instruments TTL Data Book, STORE CK will go high a maximum of 42ns later and a minimum of 25ns, due to the delays through IC5, IC4 and IC31. Taking into account the delay through IC30a,  $\overline{LE}$  goes low 5ns later. Also, 44.5ns after STORE CK goes high, the address on the data bus becomes valid (delays are due to IC36c and the counters IC17-19). Now if IC33b is not in circuit, and the minimum propagation time across IC35 is assumed, it is possible that  $\overline{WE}$  will become valid 2.5ns before the address is valid. Thus the delay through IC33b is included to ensure that this cannot happen. Now since it takes (worst case) 47ns for  $\overline{LE}$  to go low, and then 10ns for  $\overline{LE}$  to latch the data, the input data must remain valid for 57ns, hence the 60ns data hold time specified. Also, to ensure that  $\overline{LE}$  remains low for fast clocks, the input clock must remain high for at least 62ns, to allow the clock propagated through IC34 and IC29d to hold  $\overline{LE}$  low. After a worst case delay of 65ns across IC35, the  $\overline{WE}$  becomes valid for 43ns

and then 24.5ns later (due to IC34, IC29d and IC30a)  $\overline{LE}$  goes high again (assuming of course that the STORE CK is already low). This would then be a worst case total of 182ns after the input clock edge, which allows 18ns spare before the next clock edge arrives. As is specified, the data input must be valid at the rising edge of the input clock, and becomes valid at the output of IC1 10ns later due to the delay through IC1. The comparators take 28ns for the compare, and including the delay of IC1, the A = B output is valid 38ns after the rising clock edge. Now including the delay of IC25c,  $\overline{LE}$  applied to IC24a (without IC24d) would take a minimum of  $29 + 3 = 32$ ns, which would mean that IC24a could be enabled 6ns too early. Thus the delay of IC24d is included to ensure that the A = B signal is valid before IC24a is enabled. IC24a adds 7.5ns and then the trigger path adds a further 78.5ns before the master flip-flop is reset. This means that the time taken between the rising edge of the input clock and the point at which a word recogniser trigger stops the STORE CK, is 157.5ns. This last calculation ensures that the analyser is reset within 200ns, i.e. before the next clock edge arrives.

## COMPONENTS . . .

### Resistors

R1-R25, R34, R35, R40,	
R68, R70	10k (30 off)
R26-R29, R36-R39, R63-R67,	
R72-R75, R77-R88	1k (29 off)
R30, R32, R69	100k (3 off)
R31, R33	27k (2 off)
R42-R62	470 (21 off)
R41	270
R71	220
R76	2k 1% $\frac{1}{4}$ W

All resistors are 5%  $\frac{1}{4}$ W unless otherwise stated

### Capacitors

C1, C2	2 $\mu$ 2/16V tant. (2 off)
C3, C4, C9-C26	100n/16V tant. (18 off)
C5	4 $\mu$ 7/16V tant.
C6, C7	150p ceramic (2 off)
C8	30p ceramic
C28, C30, C32	1 $\mu$ /35V tant. (3 off)
C27, C29, C31	10 $\mu$ /35V tant. (3 off)
C33	4700 $\mu$ /25V elect.
C34, C35	2200 $\mu$ /25V elect.

### Transistors & Diodes

TR1	BC108
REC1	100V p.i.v. 5A
REC2	100V p.i.v. 1A
D1, D2, D3	3mm red l.e.d. (3 off)

### Integrated Circuits

IC1	74LS373
IC2, IC3, IC4	74S85 (3 off)
IC5	74LS04
IC6	ICM7556
IC7-9, IC20-22	74LS193 (6 off)
IC10, IC11	2716 (2 off)
IC12-14	74LS47 (3 off)
IC15	74LS245
IC16	MK4801A-55
IC17-19, IC37-39	74LS191 (6 off)
IC23	74LS00
IC24, IC33	74S08 (2 off)

IC25, IC28	74S00 (2 off)
IC26, IC32, IC35	74121 (3 off)
IC27	74S20
IC29	74S86
IC30	74S02
IC31	74S153
IC34	74S74
IC36	74S32
IC40	7912CT
IC41	7812CT
IC42	LM323K

### Switches

S1, S18, S21	DPDT min. toggle (3 off)
S2-4, S6-13	DPDT (with centre off) min. toggle (11 off)
S5, S19, S20*	4P3W rotary (3 off)
S14	3P4W rotary
S15	DPDT momentary action
S16, S17	DPDT momentary action (with centre off) (2 off)

### Miscellaneous

T1	Transformer 9V @ 3A
T2	15-0-15 @ 150mA
SK101*	Red banana socket
SK102*	Black banana socket
SK103*	Green banana socket
SK7	BNC female chassis mount
SK4, SK5	16 pin i.c. socket (2 off)
SK3	14 pin i.c. socket
SK1, SK2, SK6, SK8	Double-sided wire-wrap p.c.b. edge connector. See text (4 off)

14 pin wire-wrap sockets for displays (6 off)

Sockets for i.c.s: See text

Heatsink, nuts & bolts, stand-off pillars.

Case: 440mm x 110mm x 200mm deep.

Soldercon i.c. socket strips (see text)

16-way ribbon cable

Ribbon cable headers to fit 16-pin i.c. sockets (4 off)


Fuse and fuseholder (chassis mount 500mA)

Coloured "Easy-Hooks"

X1-X4 0.3" i.e.d. 7-seg. display (Maplin common anode type)

X5-X6 0.3" i.e.d. 7-seg. display (FND357)

\*These items are used with the display options. Since they are relatively cheap, it is recommended that they are fitted to ease retro-fitting of these options. Refer to text.

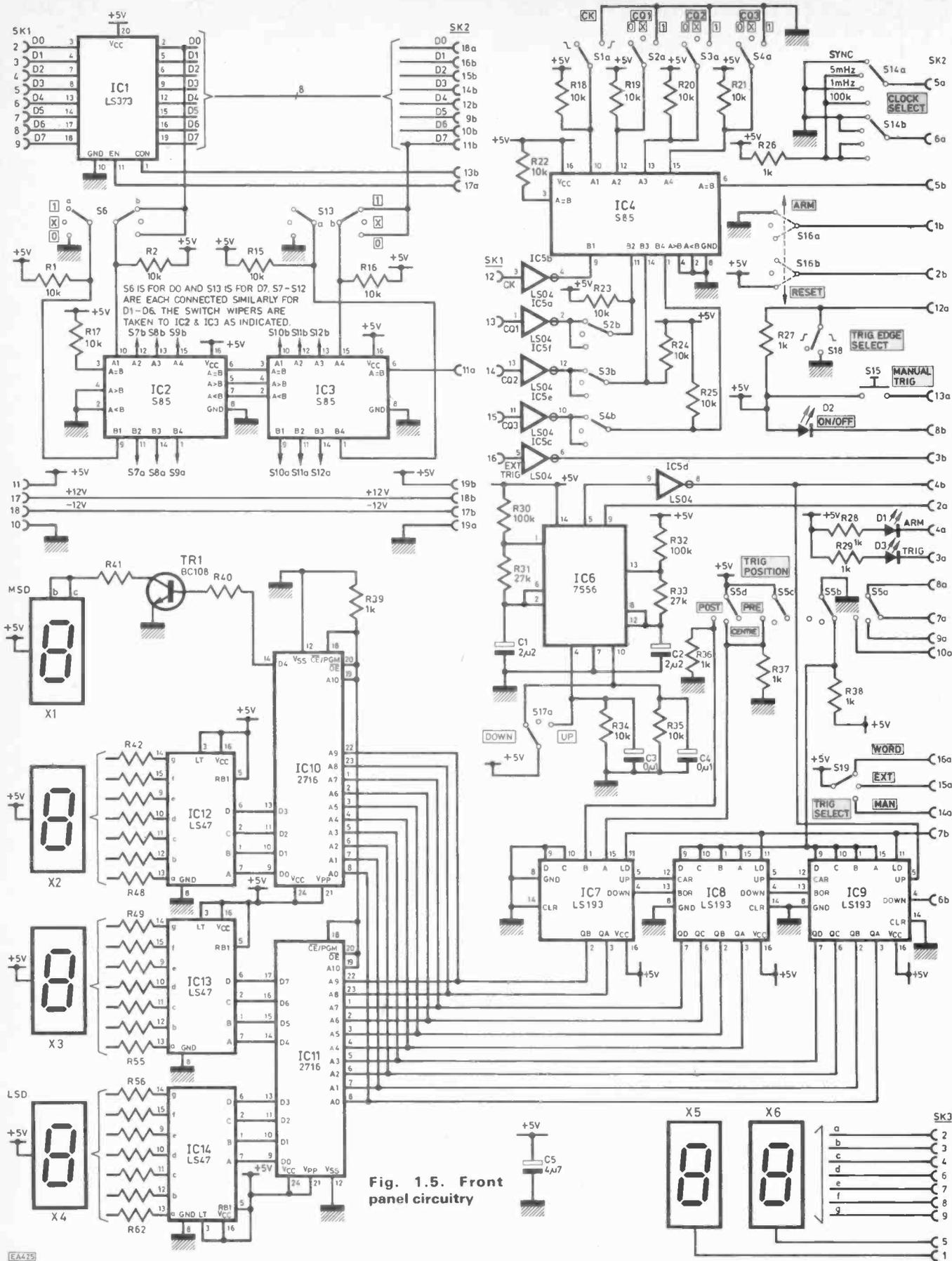

EA425


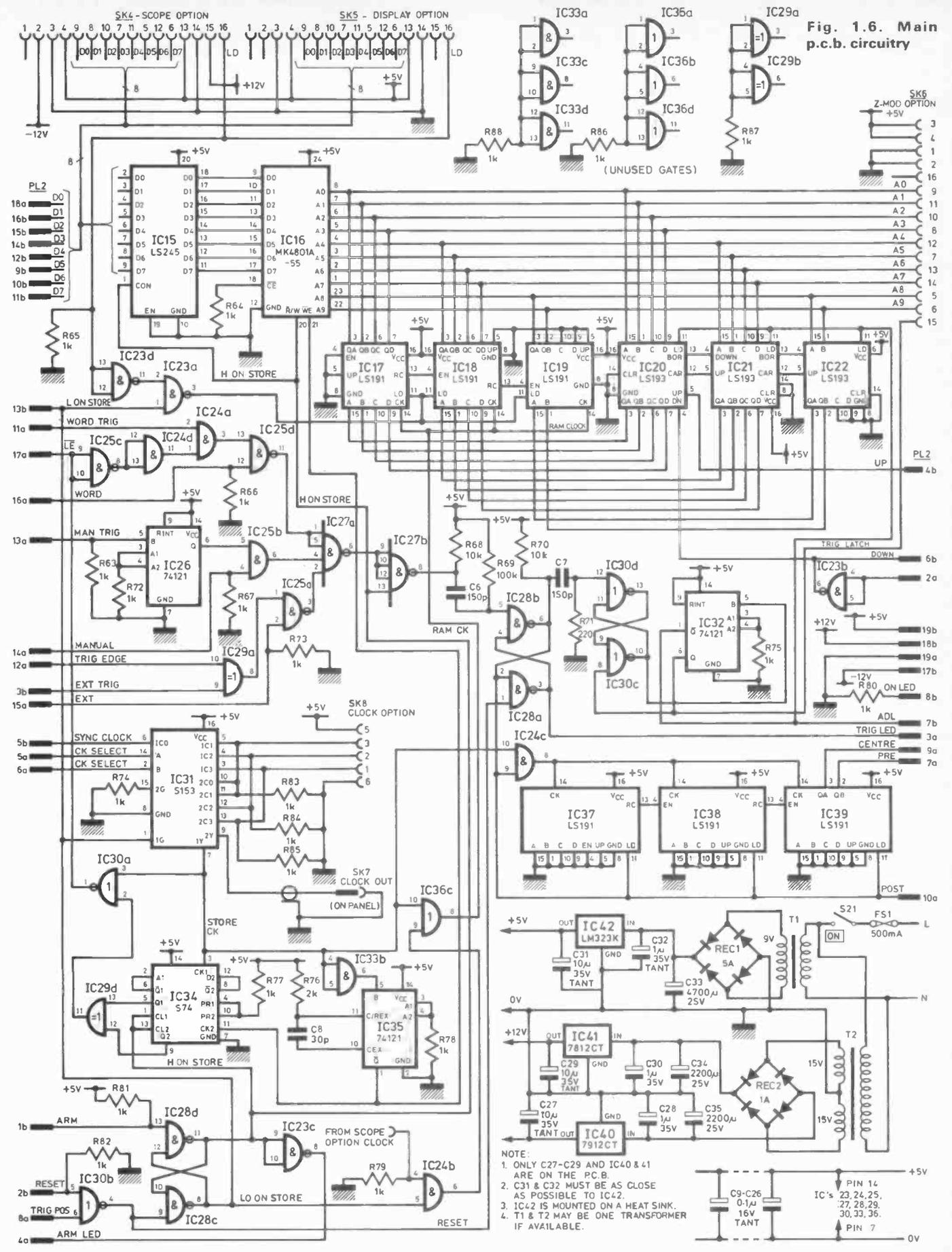


Fig. 1.6. Main p.c.b. circuitry

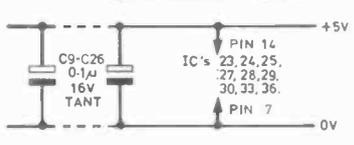- NOTE:
1. ONLY C27-C29 AND IC40 & 41 ARE ON THE P.C.B.
  2. C31 & C32 MUST BE AS CLOSE AS POSSIBLE TO IC42.
  3. IC42 IS MOUNTED ON A HEAT SINK.
  4. T1 & T2 MAY BE ONE TRANSFORMER IF AVAILABLE.



The clock modifiers *must* be valid before the trigger word appears, to get the analyser triggered. Once triggered, the modifiers can then be used to select data to be stored, i.e. to start and stop storage as required. The reason for this requirement is that the trigger pulse is gated through by IC24a, which is enabled by LE, which is in turn derived from the STORE CK. So if the modifiers are invalid there is no SYNC CLOCK, which means no STORE CK. Hence the trigger word will never get through. Once IC28b and IC28a have been set, it does not matter if no more pulses come through, therefore the modifiers can be used.

All unused inputs of the probe (including unused modifiers and EXT input) should be tied high or low, especially when operating at higher frequencies. Floating gate inputs can affect other inputs of the same i.c., and although no problems were experienced with the prototype, this is good practice.

#### DATA DISPLAY

Assuming no scope option, the input to IC23d (LD) is low, and the output of IC23a is therefore low. As already explained, the address on the outputs of ICs 20-22 are therefore passed through ICs 17-19, and the data corresponding to that address is on the data bus. Because LD is low, the latch on the Hex display option is disabled (not latched) and the data on the data bus is displayed. If S17 is now activated, one of the halves of IC6 oscillates, and the counters ICs 7-9 and ICs 20-22 increment or decrement in unison. ICs 7-9 keep track of the address of the data byte being displayed, while the RAM address is being set by ICs 20-22. If now the scope option is fitted, the option applies a 64kHz, 32kHz or 16kHz clock (depending on the option's expand switch) to IC24b, which at this time is enabled. This clocks ICs 17-19. LD is also being held high, so the LD in-

puts of ICs 17-19 are invalid. However, every 64, 32 or 16 clock pulses, LD is pulsed low, reloading ICs 17-19 with the base address stored in ICs 20-22. Also, the Hex display option gets the pulse, so the latch on the option latches in the data only when the base address (from ICs 20-22) is valid. Now similarly, when S17 is operated, the base address in ICs 20-22 change, and so the starting point from which the scope displays its 64, 32 or 16 bytes is changed. In this way, the whole memory can be scanned up and down in segments of 64, 32 or 16 bytes.

#### POWER SUPPLY

The power supply is conventional, using 3-terminal regulators. Although the  $\pm 12V$  has not yet been made use of, it is used for the CMOS input option, and the scope display option. The transformer supplying the +5V must have a rating of at least 2A, as the total current consumption of the complete unit exceeds 1A.

#### COMPONENTS

Full constructional details of the basic unit will be given in the next issue; however, a comment on the components is necessary. The Schottky TTL must not be replaced by LS TTL, otherwise the 5MHz specification will not be achieved. Double-sided p.c.b.s have had to be used, but do not have to be through-hole plated. Since it is not wise to solder i.c.s direct to the p.c.b., it is recommended that Soldercon i.c. socket strips are used. These allow soldering on both sides of the p.c.b. and are cost effective. The alternative is to use wire-wrap sockets, to allow the sockets to stand proud of the p.c.b., so that the pins can be soldered both sides where necessary. The prototype was built using Soldercon strips, and these worked well, while providing a neat solution.

# IT PAYS TO HAVE THE BEST CONNECTIONS

especially to PRACTICAL ELECTRONICS—the magazine for connecting hobbyists. The latest technology in a monthly selection of useful constructional projects for your home...for your car—in fact, there are hundreds of ways PRACTICAL ELECTRONICS can help you.

The biggest problem is avoiding breakdowns, like missing important issues—but now it's made easy with the PRACTICAL ELECTRONICS subscription service.

Just fill in the coupon below and have PRACTICAL ELECTRONICS delivered direct to your door every month. Avoid disconnection send off the coupon today.

Alternatively ring our special Teledata Hotline. And why not order a subscription for a friend too!

## PRACTICAL ELECTRONICS SUBSCRIPTION ORDER FORM

Annual Subscription Rates	
U.K.	£13.00
U.S.A. CANADA	\$28.60
Other Overseas Surface Mail	£13.00
(Students: Deduct £1.00 (\$2.20) and quote Student number.)	

Complete this form and post it, with payment or Credit Card authorisation to:  
IPC Magazines Ltd.,  
Room 2816, King's Reach  
Tower, Stamford Street,  
London SE1 9LS.  
You can use this form to order a gift subscription too. Hotline. Phone TELEDATA 01-200 0200 with your Credit Card No. Allow 4 weeks for order processing.



**HOTLINE**  
PHONE  
TELEDATA

01 200 0 200

Post copies to:

NAME: \_\_\_\_\_

ADDRESS: \_\_\_\_\_

Post Code: \_\_\_\_\_

If a Gift Subscription enter your own name and address here.

NAME: \_\_\_\_\_

ADDRESS: \_\_\_\_\_


Post Code: \_\_\_\_\_

I enclose my cheque/P.O. payable to IPC Magazines Ltd. for £ \_\_\_\_\_  
Charge my Credit Card A/C at quoted rate.

\_\_\_\_\_

Card Valid from: \_\_\_\_\_ to \_\_\_\_\_

Signature \_\_\_\_\_

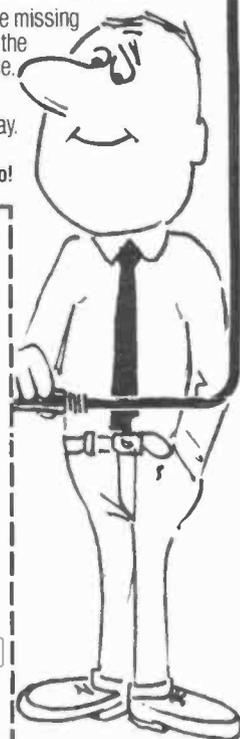

# From the world's largest manufacturer of scientific instruments



**B**eckman instruments are used worldwide in medicine and science, in industry and environmental technology, where precision and reliability are vital: from the Beckman photo-spectrometer in a space probe scanning for signs of life to a Beckman clinical electrolyte analyser.

## World's widest range of hand-held multimeters

This same perfection in design and manufacture goes into Beckman digital multimeters, themselves widely used in testing, measurement, research and engineering because of their accuracy and their intelligent features.

Now the electronics enthusiast has access to the same standard of reliability in the T90, T100 and T110 models.

## Digital performance at analogue cost

All models undergo 100% factory testing. Their accuracy is guaranteed to be held over a long period and reliability is outstanding, thanks to fewer components and interconnections. All components are of the highest quality and include a CMOS integrated circuit and gold inlaid switch contacts.

The digital display can be read at a glance, and all functions are selected with a single rotary switch, rather than with confusing rows of push buttons.

Battery life is exceptional - 200 hours at continuous operation.

The T90 gives an accuracy of 0.8% Vac and is remarkable value for money at £43.45 (+VAT).

The T100 is a full range function meter with 0.5% accuracy at £49.00 (+VAT), while the T110 offers even greater accuracy of 0.25% plus an audible continuity indicator at £59.00 (+VAT).

To feel like a professional you can order your Beckman straight off the coupon, or send for full technical data.

## **BECKMAN** World leaders in multimeters

Beckman Instruments Ltd  
Electronic Components UK Sales and Marketing Organisation  
Mylen House, 11 Wagon Lane, Sheldon, Birmingham B26 3DU.  
Tel: 021-742 7921 Telex: 336659

## **I want to go digital!**

### Please send me:

- \_\_\_\_\_ T90 meters at £50.60 (inc. VAT, p&p) \_\_\_\_\_  
\_\_\_\_\_ T100 meters at £57.00 (inc. VAT, p&p) \_\_\_\_\_  
\_\_\_\_\_ T110 meters at £68.50 (inc. VAT, p&p) \_\_\_\_\_

I enclose a cheque/P.O. payable to:  
Beckman Instruments Ltd for £ \_\_\_\_\_

Please send me full data on the Beckman enthusiast's multimeter range.  (Tick box if required)

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

Please allow 14 days for delivery

## LOW COST/HIGH QUALITY INSTRUMENTS

Designed by Martin Kent, author of digital instrument projects published previously in Practical Electronics. Versatile digital panel mounting instruments, fully assembled and calibrated, at special prices to enable you to complete a range of projects this summer. LCD displays and CMOS LSI result in ultra-low power consumption for portable applications. Top-grade components and p.t.h. p.c. boards used throughout. Applications ideas included for making multimeter, thermometer, pH meter, h.f. dfm, etc

### VOLTMETER (MCM3554/1)

- ★ 7126 based
- ★ ± 200mV full scale
- ★ 3½ digits, 0.5in height
- ★ High accuracy
- ★ Provision for attenuators/current shunts
- ★ £12.00 inc. p&p and VAT

£9.95\*  
+ VAT



\*Special P.E. reader prices valid to 31/8/83. Cheque/P.O. with order. Same day despatch for goods in stock.

£19.95\*  
+ VAT



### FREQUENCY METER (MCF4544/1)

- ★ 7224 based
- ★ Ranges 2MHz, 200KHz, 20KHz
- ★ 4½ digits, 0.4in height
- ★ High stability crystal timebase
- ★ Event Counter/Stopwatch Timer operation
- ★ £25.00 inc p&p and VAT

## MARTEL INSTRUMENTS LIMITED

Knight House, Foxhall Road, Southminster Essex CM0 7LB  
Tel: Maldon (0621) 772151 Telex: 995722 (Martel G.)

# TOROIDALS


The toroidal transformer is now accepted as the standard in industry, overtaking the obsolete laminated type. Industry has been quick to recognise the advantages toroidals offer in size, weight, lower radiated field and, thanks to I.L.P., PRICE.

Our large standard range is complemented by our SPECIAL DESIGN section which can offer a prototype service within 7 DAYS together with a short lead time on quantity orders which can be programmed to your requirements with no price penalty.

\*Gold service available.  
21 days manufacture for urgent deliveries.

\*Orders despatched within 7 days of receipt for single or small quantity orders.

\*5 year no quibble guarantee.

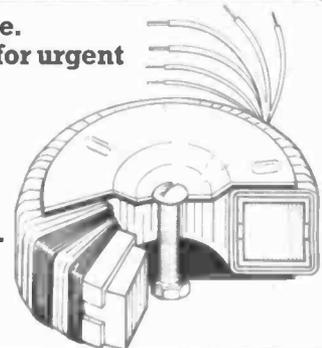

TYPE	SERIES No	SECONDARY Volts	RMS Current	PRICE	TYPE	SERIES No	SECONDARY Volts	RMS Current	PRICE	TYPE	SERIES No	SECONDARY Volts	RMS Current	PRICE
<b>NEW!</b>	<b>NEW!</b>	<b>NEW!</b>												
15 VA	0x010	6+6	1.25	<b>£5.12</b> + p & p £0.78 + VAT £0.89 TOTAL £6.79	120 VA	4x010	6+6	10.00	<b>£7.42</b> + p & p £1.72 + VAT £1.37 TOTAL £10.51	300 VA	7x013	15+15	10.00	<b>£10.88</b> + p & p £2.05 + VAT £1.94 TOTAL £14.87
62 x 34mm	0x011	9+9	0.83		90 x 40mm	4x011	9+9	6.66		110 x 50mm	7x014	18+18	8.33	
0.35Kg	0x012	12+12	0.63		1.2Kg	4x012	12+12	5.00		2.6Kg	7x015	22+22	6.82	
Regulation	0x013	15+15	0.50		Regulation	4x013	15+15	4.00		Regulation	7x016	25+25	6.00	
19%	0x014	18+18	0.42		11%	4x014	18+18	3.33		6%	7x017	30+30	5.00	
	0x015	22+22	0.34		4x015	22+22	2.72			7x018	35+35	4.28		
	0x016	25+25	0.30		4x016	25+25	2.40			7x026	40+40	3.75		
	0x017	30+30	0.25		4x017	30+30	2.00			7x025	45+45	3.33		
				4x018	35+35	1.71		7x033		50+50	3.00			
				4x028	110	1.09		7x028		110	2.72			
				4x029	220	0.54		7x029		220	1.36			
				4x030	240	0.50		7x030		240	1.25			
30 VA	1x010	6+6	2.50	160 VA	5x011	9+9	8.89	500 VA	8x016	25+25	10.00	<b>£14.38</b> + p & p £2.40 + VAT £2.52 TOTAL £19.30		
70 x 30mm	1x011	9+9	1.66	110 x 40mm	5x012	12+12	6.66	140 x 60mm	8x017	30+30	8.33			
0.45Kg	1x012	12+12	1.25	1.8Kg	5x013	15+15	5.33	4Kg	8x018	35+35	7.14			
Regulation	1x013	15+15	1.00	Regulation	5x014	18+18	4.44	Regulation	8x026	40+40	6.25			
18%	1x014	18+18	0.83	8%	5x015	22+22	3.63	4%	8x025	45+45	5.55			
	1x015	22+22	0.68	5x016	25+25	3.20		8x033	50+50	5.00				
	1x016	25+25	0.60	5x017	30+30	2.66		8x042	55+55	4.54				
	1x017	30+30	0.50	5x018	35+35	2.28		8x028	110	4.54				
				5x028	110	1.45		8x029	220	2.27				
				5x029	220	0.72		8x030	240	2.08				
				5x030	240	0.66								
50 VA	2x010	6+6	4.16	225 VA	6x012	12+12	9.38	625 VA	9x017	30+30	10.41		<b>£17.12</b> + p & p £2.55 + VAT £2.95 TOTAL £22.62	
80 x 35mm	2x011	9+9	2.77	110 x 45mm	6x013	15+15	7.50	140 x 75mm	9x018	35+35	8.92			
0.9Kg	2x012	12+12	2.08	2.2Kg	6x014	18+18	6.25	5Kg	9x026	40+40	7.81			
Regulation	2x013	15+15	1.66	Regulation	6x015	22+22	5.11	Regulation	9x025	45+45	6.94			
13%	2x014	18+18	1.38	6x016	25+25	4.50	4%	9x033	50+50	6.25				
	2x015	22+22	1.13	6x017	30+30	3.75		9x042	55+55	5.68				
	2x016	25+25	1.00	6x018	35+35	3.21		9x028	110	5.68				
	2x017	30+30	0.83	6x026	40+40	2.81		9x029	220	2.84				
	2x028	110	0.45	6x025	45+45	2.50		9x030	240	2.60				
	2x029	220	0.22	6x033	50+50	2.25								
	2x030	240	0.20	6x028	110	2.04								
				6x029	220	1.02								
				6x030	240	0.93								
80 VA	3x010	6+6	6.64											
90 x 30mm	3x011	9+9	4.44											
1Kg	3x012	12+12	3.33											
Regulation	3x013	15+15	2.66											
12%	3x014	18+18	2.22											
	3x015	22+22	1.81											
	3x016	25+25	1.60											
	3x017	30+30	1.33											
	3x028	110	0.72											
	3x029	220	0.36											
	3x030	240	0.33											

#### The benefits of ILP toroidal transformers

ILP toroidal transformers are only half the weight and height of their laminated equivalents, and are available with 110V, 220V or 240V primaries coded as follows.

IMPORTANT: Regulation — All voltages quoted are FULL LOAD. Please add regulation figure to secondary voltage to obtain off load voltage.

For 110V primary insert "0" in place of "X" in type number.

For 220V primary (Europe) insert "1" in place of "X" in type number

For 240V primary (UK) insert "2" in place of "X" in type number.

Also available at Electrovalue, Maplin, Technomatic and Barrie Electronics.

For mail order please make your crossed cheques or postal orders payable to ILP Electronics Ltd. Barclaycard/Access welcome. Trade orders standard terms.

Post to: ILP Electronics Ltd, Graham Bell House, Roper Close  
Canterbury CT2 7EP, Kent, England  
Telephone (0227) 54778 Telex 965780



**ILP**  
TRANSFORMERS  
(a division of  
ILP Electronics Ltd)

# Patents Review

Copies of Patents can be obtained from:  
the Patents Office Sales, St. Mary Cray, Orpington, Kent. Price £1.60 each.

## INFRA-RED HELMET LINK

Motor cyclists and their pillion passengers have a problem with communication, largely because British law (very reasonably) compels them to wear crash helmets. The obvious solution is a radio link. But if the legal CB wavelengths are used the link is likely to be useless, especially in city areas, because these frequencies are now so cluttered and blitzed by illegal high-powered transmitters, that normal use is impractical.

David Thompson of London W8 and Nicholas Hobson of SW3 have filed a British patent application (2 103 043) on an alternative approach. They suggest using an infra-red transmitter and receiver system built into the crash helmets. This seems a sensible approach, because the distance between rider and passenger is small, and their front-back positioning is fixed. The system can be modified, however, for sideways use with a side car.

Fig. 1 shows two helmets, each with microphone 3 and headphones 4 inside. L.e.d. 5 serves as an infra-red emitter and photo diode 6 as a receiver, on the front, rear and/or side of the helmet as necessary.

Inside each helmet there is an infra-red transceiver, shown schematically in Fig. 2. Speech picked up by microphone 14 is amplified at 15 and split into two paths. One path triggers threshold switch 16 and the other controls AGC circuit 17. The controlled signal is limited at 18 and band-pass filtered at 19 to around 300-330Hz. The processed signal is then fed to one input of Pulse Width Modulator 20, while the other input receives a triangle carrier generated by oscillator 21 at around 20kHz. The pulse width modulated output is converted to Pulse Position Modulation by circuit 22. The inventors say PPM allows average transmitted power to be greatly reduced.


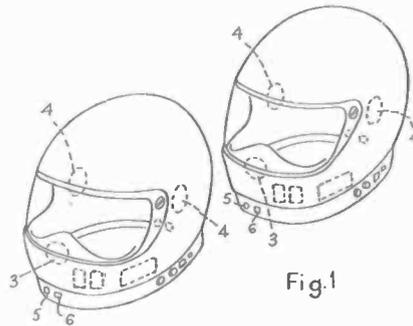


Fig.1

The pulse train is applied via amplifier 23 to l.e.d. 24, operated on a 940nm wavelength (eg Siemens type LD 241).

In the receiver photo diode 26 (type

BPW 34, for instance) outputs to LC filter 27, so that d.c. and low frequency components are shunted to earth. The wanted HF signal is amplified at 28 and band limited at 29 to optimize signal-to-noise ratio at the input of amplifier 30. This outputs a pulse train similar to that produced at converter 22 in the transmitter. Demodulator 32 uses the pulse train to sample a triangle wave locally generated by oscillator 33, phase locked to the transmitter oscillator. Both the positive and negative slopes of the triangle are sampled. The difference between the samples corresponds to the phase error between the two oscillators and is used to control the oscillator 33 to close the phase locked loop. The sum voltage of the samples is the audio signal which is band-pass filtered at 35, amplified at 38 and fed to earphone loudspeaker 39.

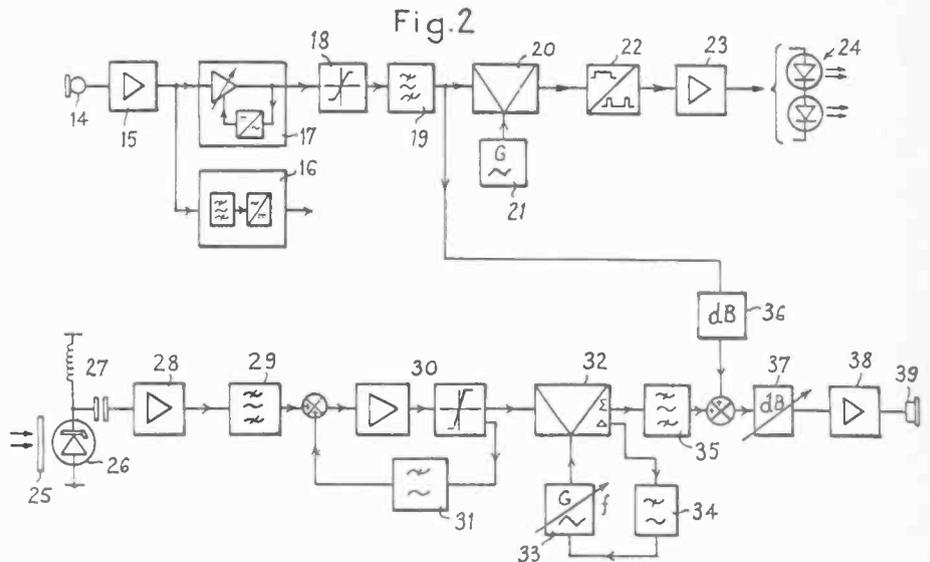

## DOUBLE-CARRIER STEREO TV

There is currently a move in Germany to protect the native TV manufacturers from foreign competition, by the use of a patented stereo sound system. For the last sixteen years Europe has been able to limit the number and type of colour sets made by Far Eastern firms, both in the Far East and in Europe, by clever use of the Telefunken patents on the PAL signal coding system. But now the PAL patents are running out and in Germany IGR (Interessengemeinschaft fur Rundfunkschutzrechte GmbH) is hoping to

do the same with a folio of patents on the double-carrier system now being used to transmit stereo sound with some TV programmes in West Germany. This is one very good reason why the Germans adopted a very different approach to that used in Japan.

In that country the two channels of sound are multiplexed on a single carrier, whereas in Germany they are transmitted on two separate carriers. Unfortunately the German patents on stereo TV sound are likely to prove far weaker than the PAL patents, for the simple reason that there is nothing new in twin carrier transmission.

IGR's only hope is to patent details of the system.

European patent application 0 069 864 is an example of what looks increasingly like a doomed attempt at fending off foreign competition. The patent application, in the name of IGR, has been filed in all the major European countries, including Britain. This is an expensive tactic but the application covers only a trivial circuit detail.

Even if IGR can persuade the European Patent Office that such a simple idea is new, and worthy of a patent, it is hard to see how it can be used to ward off the Japanese competition.

# Deglitching Techniques

L.N. Owen B.Sc.

TO most hobbyists the function or even existence of a Deglitcher is somewhat obscure. However, with the increasing interest generated in these pages over recent years concerning microprocessor interfacing, particularly in digital to analogue conversion, a number of experimenters may well have been 'glitched' without being fully aware of their situation, the results being curious logic spikes and consequently distortion of the desired output.

## THE GLITCH DEFINED

A glitch is a transient spike which occurs at the output of any DAC (digital to analogue converter) when the input code is changed. All DACs suffer from glitching. The transients are due to the finite, variable times taken for digital signals to drive analogue switches. These variations are caused by small imperfections introduced to the integrated circuit during fabrication, hence stored charge, or gate to drain capacity, is inconsistent. The resultant effect is that both digital and analogue switches turn on and off at different rates at different times. Consequently a series of states is experienced when the input, and hence the output, is changed.

This behaviour is most pronounced when small changes occur about the most significant bit (MSB). To illustrate this point consider the incrementing of data from  $127_{10}$  to  $128_{10}$ ; in binary form this corresponds to a transfer of  $01111111_2$  to  $10000000_2$ ; in other words a complete change of state is

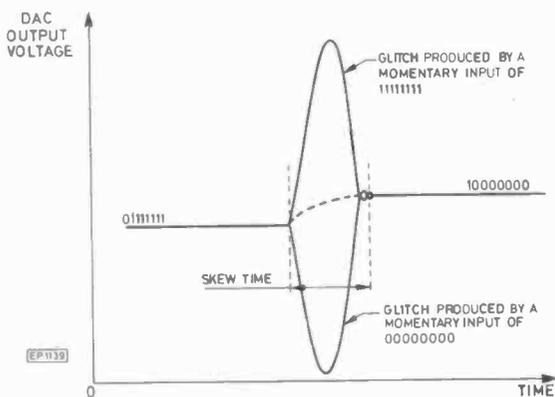


Fig. 1. Glitch effects

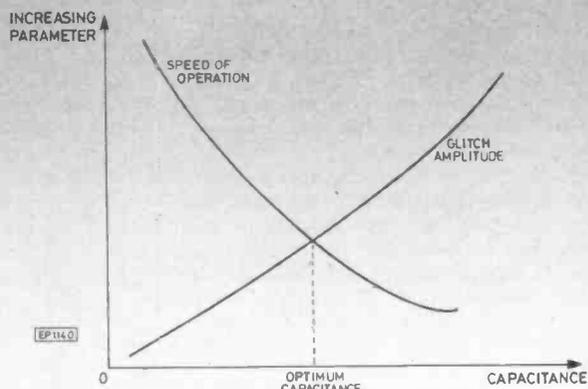


Fig. 2. Effect of damping


required for each logic input. If this is analysed further the DAC must switch the MSB on and switch off the other lesser seven bits in order to synthesise the corresponding analogue voltage. However these switches of logic level do not occur simultaneously and thus for a small space of time there are many possible input values. The two worst cases are  $11111111_2$  (the MSB switches on while the lesser bits are still on) and  $00000000_2$  (the lesser bits turn off prior to the MSB turning on). Both of these cases are shown in Fig. 1.

## DEGLITCHING

The immediate concern is the various methods of glitch elimination. The first point to make is that complete deglitching is only possible by over-damping the system. In most cases this is possible but wholly undesirable due to the sluggish response. However the principle of damping is a useful one and is commonplace in comparatively slower systems.

In its simplest form a capacitor strapped across the DAC's output acts as a reservoir for smoothing purposes. The choice of capacitance depends on a compromise between response time and glitch amplitude. Unfortunately these two parameters work against each other and hence alternative methods are necessary for higher speeds (Fig. 2).

One such method is to load all the logic bits into a storage register before updating the DAC. In this way the skew time of the digital drive circuitry is reduced simply by ensuring

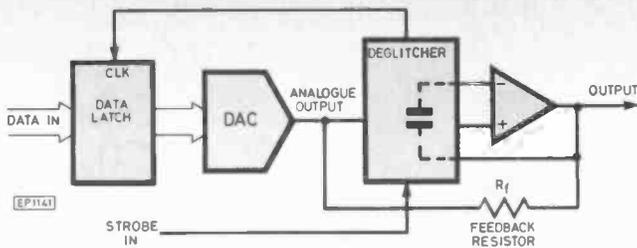

**Fig. 3. Switched feedback Deglitcher**



that all the data bits are input at the same time. However the output stages are still prone to fabrication problems as mentioned earlier. Another problem with the storage register system is that significant propagation delay times are added to the signal processing and this hinders fast operation.

This leads to the third, and most efficient, method of reducing glitches: a Deglitcher. In making this statement it must be noted that glitches cannot be eliminated, only reduced. A Deglitcher is a switched feedback element, and as such a device it must be included in the feedback loop of an operational amplifier used at the output stage of the DAC. They are essentially analogue devices with some clock functions, closely related to sample and hold amplifiers. The principle of a Deglitcher circuit is to isolate a DAC glitch and substitute its own small glitch. This latter glitch comes from charge dumping on the Deglitcher hold capacitor during transitions from sample to hold and hold to sample. Since this is independent of the DAC, changes in the digital input codes will have no bearing on the glitch size. Therefore the glitch is small and constant.

Implementation of a Deglitcher is shown in the block diagram of a DAC system in Fig. 3. The timing of the circuit is given in Fig. 4. Here, when the external storage registers are full a pulse, 'Strobe In', is applied to the Deglitcher. The rising edge of this pulse places the Deglitcher into its hold mode and then triggers an internal mode control gate pulse. At a small but specified time after the 'Strobe In' pulse has been received, a 'Strobe Out' pulse is generated. This allows data to be transmitted from the storage registers to update the DAC. After the DAC has assumed its new data level the falling edge of the Deglitcher mode control switches the mode from hold to sample and hence reconnects the DAC output to the amplifier, which quickly assumes its new value. Obviously a sufficiently fast op-amp must be used.

Minimising glitches in this manner results in an essentially linear analogue representation of a digital input. This is extremely important in applications such as cathode ray tube display driving where large high speed transients are integrated over a number of microseconds thus affecting accuracy, lengthening system settling time and creating distortion.

**Fig. 4. Timing diagram**

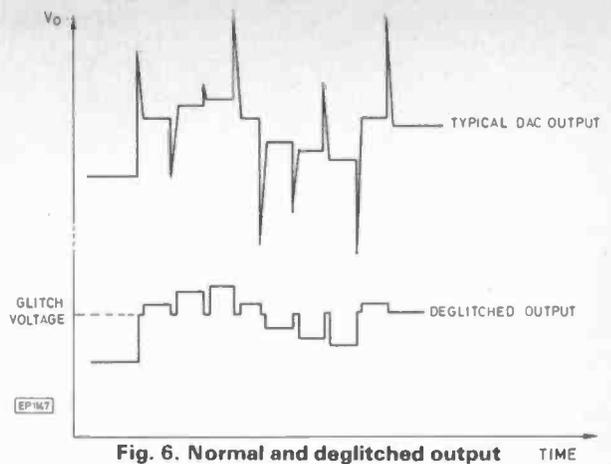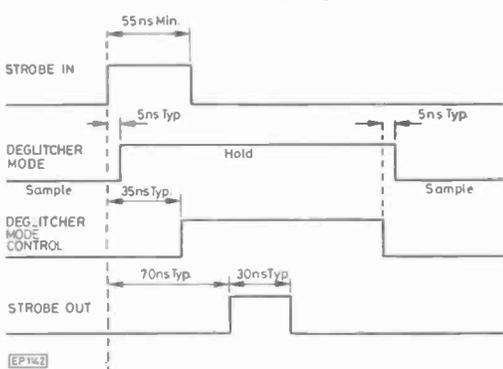


**Fig. 6. Normal and deglitched output**

**PRACTICAL SYSTEM**

Such a system is realised in Fig. 5. In this particular example the DAC is an 8 bit device, but it could be of any resolution. The particular Deglitcher is the Teledyne Philbrick 4902 which is a high reliability hybrid module. This device requires an f.e.t. op-amp and hence an LF 351 is used. The Deglitcher has three externally controllable variables. The 'Jump Trim' determines the voltage of the hold signal, and the 'EOS Trim' is the offset voltage compensation for the device.

Other features of the circuit are the clamped output of the DAC using two Schottky diodes, the debounce of the strobe input and the feedback resistor  $R_f$ . The diodes prevent damage due to over voltage, and glitches, by supplying a low resistance path to ground. The debounce network consists of low value components in order to attain a reasonably fast, clean edge for the Deglitcher to trigger from; situations such as these always call for a compromise between speed and effectiveness. The feedback resistor  $R_f$  is one of the major components in the circuit. During the sample mode the constant glitch is generated. The amplitude of the glitch is a function of the DAC output current and the feedback resistor. Hence, during the sample mode  $V_o = -I_o R_f$ . The output becomes that of Fig. 6. Pin 11 is the strobe o/p which enables the data latches to update their registers.

Typical applications where this sort of circuit is employed are CRT display systems, fast process controllers, camp generators, automatic test equipment and symbol recognition devices. ★

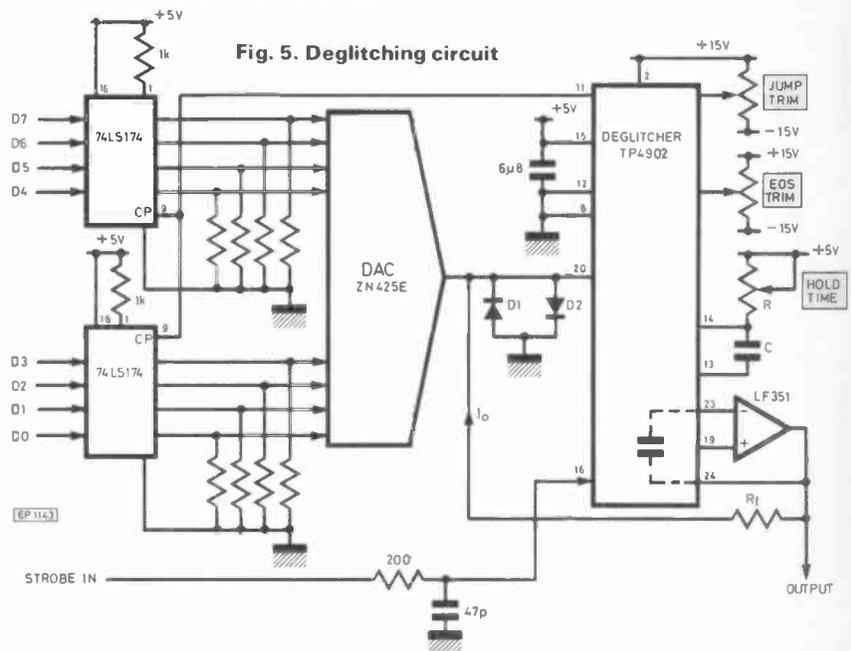

**Fig. 5. Deglitching circuit**

# MICRO PROMPT.

The hardware and software exchange point for PE computer projects

## Increasing RAM to 3K

Sir—The available user-RAM on the PE Microcontroller is 1K bytes. More complex control programs become restricted due to lack of user-RAM. The circuit described increases this memory by 2K bytes whilst retaining:

- a) battery backup facility
- b) "DISBUG" monitor facilities with the minimum of p.c.b. modifications, and at very low cost.

- 8) IC27 pin 3 to IC7 pin 1 (i.c. pin only)
- 9) IC26 pin 24 to VRAM
- 10) Connect 3k3 resistor from IC7 pin 1 to +Vcc

IC6 (address decoder) output Y1 is enabled for a valid memory address between 0000 and 03FF, generating a chip select for the 1K RAM (IC8, 9). The additional 2K RAM is located at addresses 0400 to 0BFF, utilising the outputs Y2 and

Y3 of IC6. If either of these outputs is true, IC27 pin 11 goes high. This enables IC27 pin 1, which is phased with BUS 02 clock, to generate chip select to IC26, provided the +5 volt power supply rail is held.

The Microcontroller uses a clock stretching input to IC1 (clock generator) whenever any address in RAM is assessed. For compatibility of software timing this is used in the modified circuit. IC27 gates provide a preset to IC24 (dual D type flip-flop) whenever any of IC6 outputs Y1, Y2 or Y3 are true. This enables the clock and D inputs to generate: i) memory ready to IC1 pin 6; ii) enable to the other flip-flop (IC24).

This second flip-flop (IC24) generating the "write enable" signal to IC25 pin 5, enabling this gate to provide a read or write signal to all of the RAMs.


Memory standby/supply power is taken from the supply (VRAM) and Use of the HM 6116 LP RAM device ensures low power consumption. This device has a standby power of 20 microwatts (typical), ensuring the Microcontroller will still retain memory data for many months, when not used—a prime requirement.

The memory map shows the user locations of RAM. It must be remembered to avoid the area of DISBUG RAM when combining the existing 1K RAM and the additional 2K RAM in any software routine.

Before making any modifications to the Microcontroller p.c.b. it is essential the wiring of IC25 is examined. The gates used within this package may differ from the circuit diagram supplied with the Microcontroller. Modification details refer to IC25 pin/gates as on my Microcontroller p.c.b. Use a low-profile 24-pin d.i.l. socket for IC26.

S. Marke,  
Towcester.

Fig. 1. Circuit diagram (with added 2K memory and Chip Select and Write Enable)

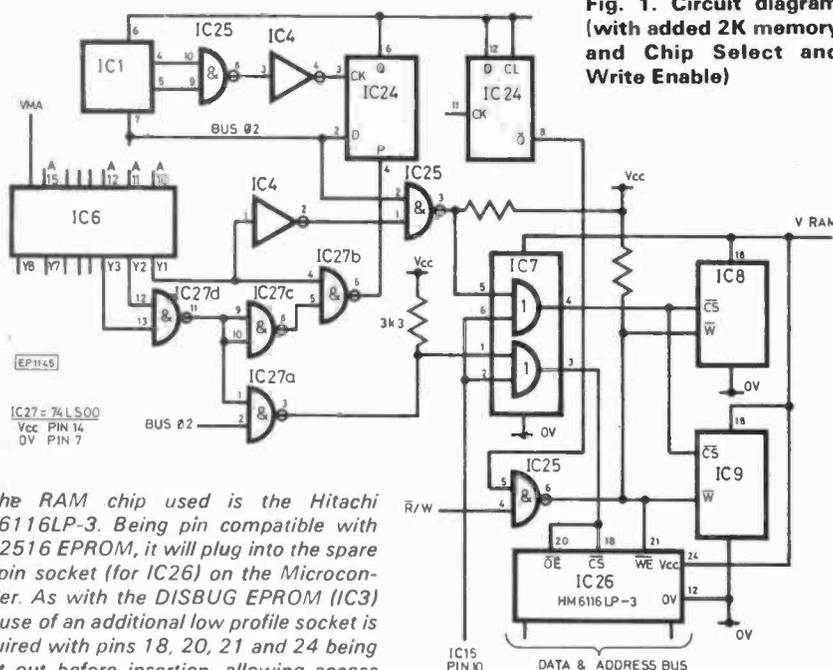

The RAM chip used is the Hitachi HM6116LP-3. Being pin compatible with the 2516 EPROM, it will plug into the spare 24-pin socket (for IC26) on the Microcontroller. As with the DISBUG EPROM (IC3) the use of an additional low profile socket is required with pins 18, 20, 21 and 24 being bent out before insertion, allowing access for modifications. The p.c.b. wiring of address and data lines are compatible. Modifications are however required for the control signals—p.c.b. modifications being:

- 1) cut track between IC24 pin 4 and IC25 pin 1
- 2) cut track to IC7 pin 3 (near IC7) and join the now isolated track to IC7 pin 4
- 3) carefully lift IC7 pin 1 (to allow access to this pin only, for wiring)

Additional wiring required is as shown on the circuit diagram. The 74LS00 chip (IC27) can be sited above IC10 (spare socket) on the Microcontroller or on adjacent Veroboard. All wiring connections can be made on top of the p.c.b. wire as follows (6116 chip removed):

- 1) 74LS00 interconnections, power supply, ground
- 2) IC25 pin 6 to IC26 pin 21
- 3) Join IC26 pins 18 and 20, wire to IC7 pin 3
- 4) IC27 pins 12, 13 to IC6 pins 13, 14 respectively
- 5) IC27 pin 2 to BUS 02
- 6) IC27 pin 4 to IC6 pin 15
- 7) IC27 pin 6 to IC24 pin 4

Table 1. Memory map

DISBUG MONITOR	FFFF
	F800
KEYBOARD P.I.A.	IC00 → IC03
DISPLAY P.I.A.	1800 → 1803
USER P.I.A.	1400 → 1403
USER P.I.A.	1000 → 1003
ADDITIONAL 2K RAM (USER)	0BFF (OBFF)
	07FF
DISBUG RAM (USER STACK)	0400
RAM (USER)	0000



48	PHA	85 F9	STA Z5	A5 F0	B9A	LDA X0	85 FD	STA Z3
A5 FA	LDA Y1	85 FA	STA Z6	18		CLC	A5 F0	LDA X0
85 F1	STA Y0	A9 01	LDA #S01	65 FE		ADC Z4	18	CLC
68	PLA	85 FE	STA Z4	85 F0		STA X0	65 FA	ADC Z6
85 FA	STA Y1	85 FF	STA Z7	A5 FD		LDA Z3	85 F0	STA X0
20 B1 1E	B1A JSR POINT	A5 FB	LDA Z1	18		CLC	A5 EF	LDA FLAG
A5 F9	LDA X1	C5 FC	CMP Z2	65 FC		ADC Z2	C9 01	CMP #S01
38	SEC	B0 1A	BCS B4A	85 FD		STA Z3	90 09	BCC B8A
E5 F0	SBC X0	48	PHA	A5 EF		LDA FLAG	A5 F1	LDA Y0
85 FB	STA Z1	A5 FC	LDA Z2	C9 03		CMP #S03	38	SEC
A5 FA	LDA Y1	85 FB	STA Z1	B0 09		BCS B5A	E5 FF	SBC Z7
C5 F1	CMP Y0	68	PLA	A5 F1		LDA Y0	85 F1	STA Y0
B0 0D	BCS B2A	85 FC	STA Z2	18		CLC	B0 07	BCS B7A
A9 01	LDA #S01	A5 FE	LDA Z4	65 F9		ADC Z5	A5 F1	B8A LDA Y0
85 EF	STA FLAG	85 FA	STA Z6	85 F1		STA Y0	18	CLC
A5 F1	LDA Y0	A5 FF	LDA Z7	90 07		BCC B6A	65 FF	ADC Z7
38	SEC	85 F9	STA Z5	A5 F1	B5A	LDA Y0	85 F1	STA Y0
E5 FA	SBC Y1	E6 EF	INC FLAG	38		SEC	8A	B7A TXA
85 FC	STA Z2	E6 EF	INC FLAG	E5 F9		SBC Z5	48	PHA
B0 09	BCS B3A	A9 00	LDA #S00	85 F1		STA Y0	20 B1 1E	JSR POINT
38	B2A SEC	85 FE	STA Z4	A5 FB	B6A	LDA Z1	68	PLA
E5 F1	SBC Y0	85 FF	STA Z7	C5 FD		CMP Z3	AA	TAX
85 FC	STA Z2	A5 FB	B4A LDA Z1	B0 24		BCS B7A	E8	INX
A9 00	LDA #S00	85 FD	STA Z3	A5 FD		LDA Z3	E4 FB	CPX Z1
85 EF	STA FLAG	46 FD	LSR Z3	38		SEC	90 A6	BCC B9A
A9 00	B3A LDA #S00	A2 00	LDA #S00	E5 FB		SBC Z1	60	RTS

### MICROCONTROLLER CLOCK

Many people have noticed that the Microcontroller clock is not accurate and typically loses 10 to 20 secs every 24 hours. David Whitfield, a co-author of the project, has investigated this problem and encountered difficulty in tracing a missing second every 5 to 10 minutes. In the end he used a BBC micro programmed as a rather crude logic analyser to monitor the 1 Hz clock and compare it with the internal clock on the BBC machine. This, in conjunction with the test program published in the December copy of PE, showed the following:

- 1 The 1Hz clock does not "swallow" whole seconds due to the circuitry associated with IC2. This would have been a convenient solution.
- 2 The accuracy of the Microcontroller's 1Hz clock is better than that of the BBC micro's system clock over a long period. This is probably due to the higher interrupt load on the BBC's CPU and its dependence on the CPU clock for timing.
- 3 The internal DISBUG clock *does* lose count at a long term rate of around 1 in 400. The loss is in the form of a random "missed" second, which seems to occur at random intervals.

These observations confirm the behaviour of the unit can be repeated, and is therefore probably shown by all units. To try and ex-

Address (Hex)	Label	Instruction	Mnemonic	Op Code			
0000	START:	LDX #ALTINT	CE 00	32			
0003		STX IRQSRA	FF 03	DC			
0006		LDX #S0000	CE 00	00			
0009		STX TICK	FF 03	E2			
000C		STX TOCK	FF 03	C1			
000F		LDA #S15	86 15				
0011		JSR PROMPT	BD F9	BD			
0014	AGAIN:	LDX #ADDIS	CE 03	FB			
0017		LDA A(TICK + 1)	B6 03	E3			
001A		JSR TWODIG	BD F8	F7			
001D		LDA A TICK	B6 03	E2			
0020		JSR TWODIG	BD F8	F7			
0023		LDX #DATADIS	CE 03	F8			

Table 2. Real time clock test program

amine the problem further, David ran the program listed. This sets up an alternative count to TICK (which he called TOCK!) at RAM location 03C1. TOCK is driven by the IRQ interrupt handler which already manages the 1Hz count in TICK; the modification to the interrupt handler starts at address 0032, and is added by the first two instructions (see the data sheet in May PE). The TOCK count uses a spare space in DISBUG RAM to set up the clock.

The main difference between TICK and TOCK is that TICK only updates the count when an interrupt has occurred AND the B-side of PIA IC12 shows that it was caused by the 1Hz clock. TOCK, however, is updated whenever an interrupt occurs. Since there is only one interrupt set up by DISBUG (the 1Hz clock), the results from TICK and TOCK should be the same. If anything, TOCK might be expected to gain on TICK due to the effects of spurious noise-induced interrupts; TICK does a check on the PIA status to avoid this problem. The test program, when run from 0000, and compared with a "real" clock, allows the two counts to be displayed simultaneously. The full TICK count is shown in the address area of the display, while only the two least significant digits of TOCK are shown in the data area. After a few hours of running, watching and comparing, it is evident that TICK loses counts, but that TOCK does not appear to gain any.

Further tests show that the problem is that the 1Hz interrupt is sometimes not reflected in



the control register of PIA IC12. As to why this might be so, David is still investigating. In the meantime he has developed a short "fix" to allow TOCK to be used in place of TICK; just use 03C1/2 in place of 03E2/3. The "fix" should be included in the initialisation code of any program (remembering to set the address shown accordingly), just before the main loop. DISBUG will initialise TOCK in the same way as TICK, setting it to 0000 at power-up or restart.

Table 1. Software fix for the real time clock: setting up 'TOCK'. Include this code at the start of a user program which wants to use TOCK, which is located at 03C1/2, instead of TICK (which is located at 03E2/3)


LDX #ALTINT	CE	Put address where code below starts (e.g. 03 80) in these two bytes
STX IRQSRA	FF 03	DC
Include this code IN ADDITION to that above at any convenient position in RAM which is unused (suggestion is to locate it at location 0380)		
ALTINT: LDX	TOCK	FE 03 C1
	INX	08
	STX	TOCK FF 03 C1
	RTI	3B

If an addition to the IRQ interrupt handler is already made by the program, omit the first patch (since the program must already contain an equivalent), and add the first 3 instructions only of the last patch to the new interrupt handler. The reason is that only one additional handler may be defined.

	LDA	A(TOCK + 1)	B6 03	C2
	JSR	TWODIG	BD F8	F7
	JSR	DISPLAY	BD F8	14
	JMP	AGAIN	7E 00	14
ALTINT: LDX	TOCK	FE 03	C1	
	INX	08		
	STX	TOCK	FF 03	C1
	RTI		3B	



# LOW COST PROFESSIONAL TEST INSTRUMENTS

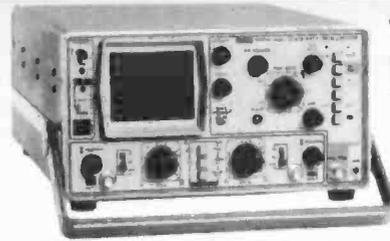

Write or phone  
for illustrated  
Test Instrument  
catalogue and  
price list.

- ★ FREQUENCY COUNTERS
- ★ ANALOGUE METERS
- ★ DIGITAL METERS
- ★ FUNCTION GEN
- ★ OSCILLOSCOPES
- ★ POWER SUPPLIES
- ★ LOGIC PROBE
- ★ SCOPE PROBES

**BLACK STAR LTD.**  
9A, Crown Street, St. Ives,  
Huntingdon, Cambs. PE17 4EB.  
Tel: (0480) 62440 Telex: 32339



## PARNDON ELECTRONICS LTD.

Dept PE1, 44 Paddock Mead, Harlow, Essex. CM18 7RR Tel: (0279) 32700

**RESISTORS:** 1/4 Watt Carbon Film E24 range  $\pm 5\%$  tolerance. High quality resistors made under strictly controlled conditions by automatic machines. Banded and colour coded.  
£1.00 per hundred mixed (Min 10 per value)  
£8.50 per thousand mixed (Min 50 per value)  
Special stock pack 60 values. 10 of each £5.50

VOLUME  
DISCOUNTS  
AVAILABLE

### 4MHz MICRO-CHIPS AT MICRO PRICES

Z80A-CPU	£3.25		£2.83	
Z80A-CTC	£3.10	Inc.	£2.695	
Z80A-PIO	£3.10	VAT	£2.695	Exc.
Z80A-DMA	£12.00	P&P	£10.435	VAT
Z80A-SIO0	£9.95		£8.655	
Z80A-SIO2	£9.95		£8.655	

Full List Available - Send SAE

ALL PRICES INCLUDE V.A.T. & POST & PACKING - NO EXTRAS  
MIN ORDER - UK £1.00 OVERSEAS £5 CASH WITH ORDER PLEASE  
Same Day Despatch

# ALARMS

## FREE CATALOGUE!

OUR GREAT NEW ILLUSTRATED CATALOGUE IS  
PACKED WITH INFORMATION ON SUPERB QUALITY,  
PROFESSIONAL BURGLAR ALARM EQUIPMENT

**AT UNBEATABLE PRICES!**

SEND SAE OR PHONE NOW FOR YOUR COPY

A.D. ELECTRONICS  
DEPT. PE  
217 WARBECK MOOR  
AINTREE LIVERPOOL  
L9 0HU/051 523 8440



THIEFCHECK BURGLAR  
ALARM D-I-Y SYSTEM



MAIN  
DISTRIBUTOR

# MASTER ELECTRONICS NOW!

## The PRACTICAL way!


This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to start or further a career in electronics or as a self-employed servicing engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write personally at any time, for advice or help during your work. A Certificate is given at the end of every course.

You will do the following:

- Build a modern oscilloscope
- Recognise and handle current electronic components
- Read, draw and understand circuit diagrams
- Carry out 40 experiments on basic electronic circuits used in modern equipment
- Build and use digital electronic circuits and current solid state 'chips'
- Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-Fi and microprocessor/computer equipment.

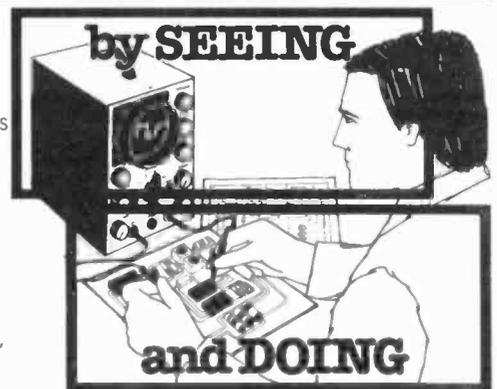

## New Job? New Career? New Hobby? Get into Electronics Now!

**FREE!**  
COLOUR BROCHURE

Please send your brochure without any obligation to

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

I am interested in:

- COURSE IN ELECTRONICS as described above
- RADIO AMATEUR LICENCE
- MICROPROCESSORS
- LOGIC COURSE
- OTHER SUBJECTS \_\_\_\_\_

POST NOW TO:

BLOCK CAPS PLEASE

PE/8/821

**British National Radio & Electronics School** Reading, Berks. RG1 1BR

# Strictly

by K. Lenton-Smith

## GLENN MILLER

Students of light music will be familiar with the problem that faced Glenn Miller 45 years ago. He was searching for a particular sound that would set his band apart from others—and inadvertently found his answer through a mishap to his lead trumpet. The player concerned had split his lip and the trumpet part had to be taken by the clarinet (both instruments being pitched in B $\flat$ , the same music could be used).

In fact, Miller re-arranged his parts to suit this event and the resulting blend of *solis* saxes and clarinet produced a sound unmistakable today.

I feel sure that modern combo groups have that same problem—how to sound different from the rest. In the Miller era, pure musicianship was the only method: if the mains supply failed, only the announcer's microphone was affected. Today, complete failure of the electronics would bring most music to an abrupt halt, and render vocalists inaudible!

Electronic effects, especially those used in recording studios, are limitless in popular music today, and it is a moot point whether the standard of musicianship has fallen as a direct result. Combo groups look carefully at the equipment they buy and how to make the most of it. In this article we will look at what the world's largest manufacturer, Yamaha, has to offer.

## COMBO

As the electric guitar is the mainstay of the group, it ought to be dealt with before other instruments. Yamaha has introduced new instruments recently, many of them featuring 'through-neck' design: in this case the neck extends right through the body of the instrument to its heel, giving more uniform transmission of string vibration to the pick-up. The SG series and SF series have solid bodies with humbucking coils. The SC series use a single coil. SA series guitars are semi-acoustic with single coil/humbucking and have exceptional tonal ability. AE series are acoustic and provide that warm and intimate sound for contemporary jazz. Among these, the hard-rock musician would probably choose the SF series for its extensive distortion control and powerful Alnico-5 pick up magnets.

The new BB series of electric basses has been developed with the aid of leading performers. They offer full, balanced response with plenty of punch and definition.

A range of effectors that can be fitted in-line include phasing, chorus, flanger,

octaver, distortion, tone booster, compressor, parametric EQ, limiter, noise gate and noise selector. When the inbuilt guitar controls are also taken into account, performers have ample scope for modifying waveforms from the pickup.

## KEYBOARDS

Among Yamaha's pianos, one of the most interesting is Digital Keyboard GS1. This 88-key model looks like a small baby grand and features touch-response: up to 16 notes may be played simultaneously, 16 voices are available and it will read magnetic cards for voicing, vibrato may be applied and piano-type pedals control this, damper and tremolo are also featured. GS2 is a smaller, 73-key version with a similar specification.

Models CP-80 and CP-70B are 88 and 73-key acoustic pianos with amplification, the latter model being portable despite the metal frame carrying the strings. Both instruments allow the player to control timbre over three distinct parts of the keyboard compass, with variable tremolo depth and speed.

CP35 and CP25 are 73 and 61-key digital pianos with 16 note capacity in two pitches, decay, tremolo, flanger, filter and equaliser controls. The CP25 keyboard may be split, when each section then allows 8-note capacity.

A useful keyboard to use at home is the CP11. This is also digital (10 note polyphonic) but the keyboard can be split and 6 notes are then reserved for the chord section. Eight rhythm patterns are provided and these control the auto-accompaniment. The available tones are Piano 1, Piano 2 and Harpsichord. Sustain operates normally but the EG control allows decay only after the playing key has been released—producing organ-like tones. Tremolo is fitted and the instrument has an internal 5W speaker.

Yamaha's Symphonic Ensembles are best described as very comprehensive portable organs: they have one/two manuals with organ tone, solo synth, poly synth and string chorus etc. Optional 13 note pedalboards may be attached. This SK series is ideally suited to a skilled keyboard player in a group.

Synthesisers from Yamaha range from CS70M—a polyphonic programmable instrument with 61 keys and 12 VCOs—to the CS-5, a 3-octave monophonic keyboard with a single VCO.

## PRODUCER SERIES

This idea from Yamaha should be very welcome to any neighbour of a practising pop enthusiast! The sound capabilities of stage and recording equipment have been compressed into a small and affordable system that can be used without disturbance to others. It is based on three units—MA10, MM10 and CS01.

MA10 is a headphone amplifier which will drive two sets of MH10 stereo phones and has a Monitor Out facility to feed other MA10s or a power amplifier. The input jack accepts signals from guitar or keyboard and input connections can also be made through Monitor In and Aux.

MM10 is a stereo Mic/Line mixer, each of the four channels having individual pan pots and level controls. CS01 is a 2½-octave monophonic synthesiser with VCO, VCF, VCA and EG (Envelope Generator): a Breath Controller allows alteration of the VCO and VCF characteristics, leaving both hands free to use the keyboard and sliders. All three units run from mains adaptors providing 9–12 v.d.c. (Type PA-1).

By interconnecting these units, a group of instrumentalist/vocalists can hear the combined stereo output through headphones with total realism and clarity. Interconnections require some thought, though Yamaha can offer suggestions in this respect. The Producer Series should be a boon to practising musicians and neighbours alike as one word that appears to be synonymous with combo music is decibels!

## AMPLIFIERS

These are comprehensive and fall into three categories. The JX series cover outputs from 20W to 50W into 8... at 3% THD and have integral controls. G and B Mk II series handle from 50W to 100W into 8... at 10% THD. Alternatively, stackable amplifiers can be supplied using G100II amplifier head or B100II head with one of the S Series speaker enclosures in conjunction: outputs up to 240W are available by this method. Different amplifiers are used for guitar and bass (indicated by codes G and B) because of the differences in tonal spectrum. New preamplifiers PG1 and PB1 (for bass) have recently been introduced.

Mixing consoles from Yamaha will accept up to 32 inputs, depending on the model concerned, with faders, equaliser, echo panpots and talkback. Analogue Delay Units E1010 and E1005, Graphic Equaliser Q1027, frequency Dividing Networks F1040 and F1030 are other items to interest groups. General speaker systems, individual drivers and horns are supplied for those that prefer to assemble to their own specification.

## PERCUSSION

The company is well known for its orchestral instruments, including its System Drums. The YD-9000RA system includes two bass drums, snare drum, seven mounted toms, hi-hat and seven mounted cymbals of various sizes—surely enough for any

drummer to be in his element? Certainly, Peter Erskine, Cozy Powell, Al Foster and Jim Keltner appear to be, as users of Yamaha percussion.

Individual drum units in any of 14 colour finishes are available. Shell and hardware sets, cymbal stands, snare drum stands, single and double tom stands, foot pedals, thrones, mutes and other hardware can be purchased singly to build up a user-defined system.

## ORGANS

While looking at Yamaha's products, their highly reliable organs must be included, especially as the musical back-up—through the Yamaha Music School—is excellent: it is the world's largest teaching organisation. How it came into being and has helped 6 million people with a

systematic approach to music is a long story, obtainable from Kemble (Organ Sales) Milton Keynes, the UK end of Nippon Gakki. I am sure that Len Rawle, Musical Director and a well-known organist, will be prepared to help.

The whole of the Yamaha organ family is based on the 'block-builder' principle where each time you move up the range you find all the previous features plus extra ones. All are based on PASS (Pulse Analogue Synthesis System), which produces a range of instrument sounds unobtainable until recently.

A and B series organs have two 37 or 44-note manuals, 13 pedals, presets and 12 auto rhythms. From B-55N upwards, organs are fitted with an arpeggiator and Variable Tone Levers. C series instruments have a roll-top fallboard to exclude dust (and small children's intrusion) when not in

use. A doppler speaker is fitted from C55-N onwards.

Programmable Rhythm comes with the D series, also polyphonic synthesiser voices and multi-channel sound. Model DB5 has an extra 37 note manual with 12 synthesiser presets and can be coupled to upper or pedal.

Serious musicians will choose the E series for its full 5-octave manuals and 25-note pedalboard. Preset pistons allow instant change from baroque to cinema or entertainment organ.

Flagship of the organ range is the EX models, which are space age designs both in terms of the console (column mounted) and the electronics. PASS technology has been taken to its limits to produce a vast number of instrumental voices and sound effects. But you will need £50,000 to purchase the GX1!

# Readout...

## INMOS

Sir—Re the little note about INMOS in the April Industry Notebook.

Some of the things that Nexus says about INMOS may very well be true but don't forget that the company was messed around by the present government for political reasons. They were forced to set-up their factory in a place they didn't want and their second investment payment of some £50 million was delayed for several months whilst the government tried to wriggle out of the original contract.

In fact the original INMOS investment was made by the NEB and any loss to the taxpayer must be taken from the NEB books and not INMOS. Your view—sorry the view of Nexus that if a product is worthwhile then private capital will automatically be attracted to it is naive. How does he explain the problem Ferranti had when they wanted money for their ULA project. Not one merchant bank would look at them. In the end they went to the NEB and asked Tony Benn for £7 million. Obviously the NEB could smell success better than the banks. Later Thatcher sold those Ferranti shares on the open market for £54 million to the very people who refused the original investment. Could we possibly offset the losses that INMOS are making with the profits made on the Ferranti deal? Nexus should be criticising the government for killing off the NEB when it was doing a good job helping small business men (and large), creating jobs and making a profit as well. Does Nexus imagine that the Japanese stand back and let private enterprise do everything—their government hands out plenty of money for their banks to invest in industrial research and development—and where would the American electronics industry be without those big defence contracts?

And anyway what is £100 million? It represents just 4 or 5 weeks subsidy to the EEC agricultural fund for food that could be bought cheaper on the world market and is either

destroyed or sold off cheaply to the Russians. Or it represents 3 months for the defence of those barren rocks in the South Atlantic, and that after an initial investment of some £2000 million.

The remarks about C&W were equally silly. C&W were making handsome profits during the whole time they were owned by the taxpayer. Selling them off was a political not economic decision.

Please keep us informed about what is happening in the industrial world with a more balanced view of the political and economic problems that have to be faced by governments and industries.

If any of the statements I have made in this letter are inaccurate then it is partly your fault for not keeping me better informed. I do not wish to offend but if I need puerile political views then I would subscribe to the Telegraph or the Mail—they do it so much better than your magazine.

John Hunt  
UNDP  
Rangoon  
Burma.

### Nexus comments:-

*Inmos cannot be compared directly with Ferranti. The respective investments were different in kind, in quantity, in time and made for quite different reasons. It remains true that a worthwhile product or service attracts private capital. Indeed, as Mr Hunt points out, Ferranti had no difficulty in attracting £54 million once it became worthwhile. Similarly, Cable & Wireless, modestly profitable, was heavily oversubscribed when brought to the market. C&W's performance and profit can only now be fairly described as 'handsome'. The problem, as I am sure Mr Hunt would agree, is spotting the winners and although he may think £100 million is peanuts, by ordinary investment standards it is a large gamble on an outsider only just beginning, after four years, to show any form. The NEB's betting record has been no better than the average punter.*

## POSITIVE FEEDBACK

Sir—In response to your recent encouragement to readers to provide some feedback I am putting pen to paper.

I have subscribed regularly to your magazine for many years, am aged 32 and my interest in electronics is through hobby only. I often buy the odd issue of your competitors' magazines to see what's available and find I prefer your magazine for the following reasons:

The projects are presented clearly, are detailed and complete.

The content on the whole is what I want.

The style avoids the chatty slightly flip-pant style evident in at least one competitor.

Now some criticisms:-

Why terminate "Semiconductor Update", I certainly appreciated the feature.

I'm afraid this new feature 'Vernon Trent' just leaves me cold. I buy your magazine for information, not the sort of article common in the daily press.

My PE Micro-controller does not keep good time. The internal clock in the monitor loses approximately 1 second every 300 seconds or so. Is the crystal at fault or is there a bug in the monitor? I know I can allow for this in my own software but I may be short of space for this. I enclose s.a.e. Colin A. Kerr  
Edinburgh.

*Thank you for all your comments; we are always pleased to receive them. The only other comments we have had regarding VT have been in favour—more views welcome! Regarding Semiconductor Update this was replaced by Semiconductor Circuits, which not only introduces a new chip each month but provides data plus a working circuit and layout. We have also added Silicon News Corner to News and Market Place, thus providing information on a range of new chips as they are announced. Our intention was to cover this area more fully and show how to use the chips that are now available.*

*Your query on the Micro-controller is answered in Microprompt.*

# Ingenuity Unlimited

A selection of readers' original circuit ideas. Why not submit *your* idea? Any idea published will be awarded payment according to its merits.

Each idea submitted must be accompanied by a declaration to the effect that it has been tried and tested, is the original work of the undersigned, and that it has not been offered or accepted for publication elsewhere. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought.

Articles submitted for publication should conform to the usual practices of this journal, e.g. with regard to abbreviations and circuit symbols. Diagrams should be on separate sheets, not in the text.

## TRANSISTOR ANALYSER


THIS unit was designed and built to help with the sorting out of large bags of untested transistors. It indicates whether the transistor under test is:

- 1) Functional/non-functional
- 2) npn/npn
- 3) Germanium/silicon.

IC1 and associated components forms a conventional astable multivibrator, the output of which drives the collector and base (through R4) of TR1, the transistor under test, alternately positive and negative with respect to ground. If the transistor is of the pnp type, negative pulses will drive it into conduction so lighting indicator D1; if it is npn D2 will be lit (a faulty transistor will either light both lights or neither).

Simultaneously, the base voltage of the transistor (which will be varying between ground and  $V_{be}$ ) is fed to window detector IC2/3 and associated components, which gives a high output in the range  $\pm 4V$ . A high output will light D8 indicating a germanium transistor whilst a low output will light D7 indicating a silicon transistor. D3-D6 can be any medium power diodes which come to hand, whilst the output is more legible if different colour diodes are used for D1 and D2, and for D3 and D4.

S. D. Draper,  
Sudbrooke,  
Lincoln.

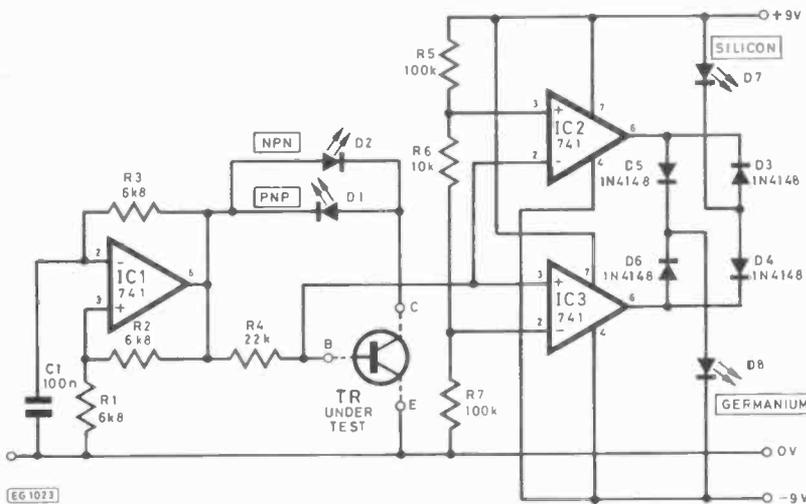


EG1023

THIS circuit is for an electronic die. When the 'spin' button (S1) is pressed then released the i.e.d. display shows a random number between 1 and 6, arranged in the standard die format.

The 555 (IC1) is in the astable mode running at 1kHz. When S1 is pressed pulses are fed into the 4017 (IC2) decade counter, this sends a pulse out of each of the nine outputs in turn. The sixth pin is connected to the reset pin (15) so that it counts up to 6 then resets. When S1 is released the counter will stop at one output and current will flow through the OR gates of the 4075 (IC3) and light up the i.e.d.s at a number between 1 and 6. While S1 is depressed all the i.e.d.s will appear to light up at once as the unit flashes through its cycle.

Stephen Ives,  
Burnham-on-Crouch,  
Essex.

## ELECTRONIC DIE

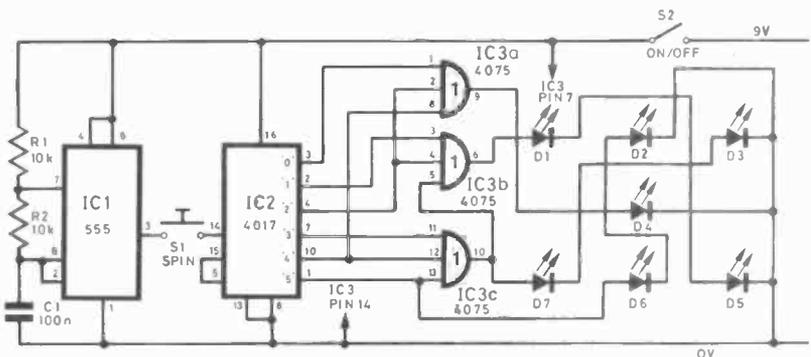

EG1113

# CAR LIGHTS-ON WARNING

The circuit in Fig. 1 has been fitted to the author's car for over a year and works well. It is an audible alarm which sounds when the door is opened with the lights on. An extra feature of this simple design is a time limit so that the alarm does not continue to sound if the door is left open with the lights on. This could be the case at a petrol station or when dropping off a passenger.

The alarm needs only two connections to the car electrics (Fig. 2). The first is to the feed for the panel lights and the second is to the wire which runs from the door courtesy-light switch to the light itself. The whole circuit, including the speaker, was mounted on Veroboard behind the dashboard.

The key to the design is D1. This detects the closure of the necessary switches and feeds current to the alarm. The alarm itself is an NE555 timer i.c. connected as an astable oscillator, running at audio frequency. The output from this component is sufficient to directly drive the speaker.

The time limit is provided by the combination of C1 and R4, connected to the

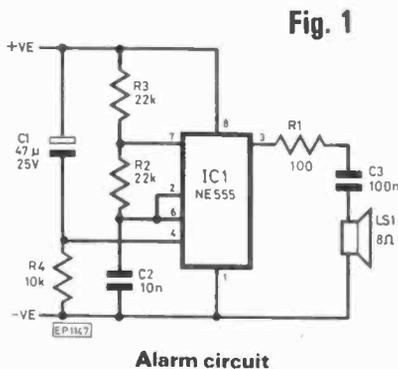


Fig. 1

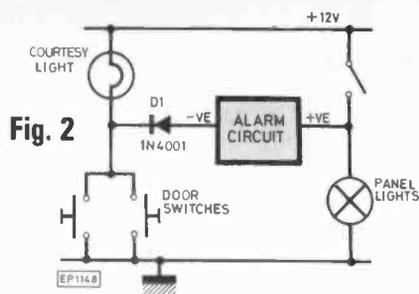


Fig. 2

Connections to car electrics

reset pin of the timer. When the alarm initially sounds, C1 is discharged and gates the timer into oscillation. As C1 charges, the voltage at pin 4 becomes more negative and eventually turns off the sound. In fact, the result is not an abruptly ending tone, owing to a feature of the internal design of the NE555. The pitch of the oscillation is low for about three seconds, then quite high for three seconds—before it stops.

D. J. Greaves,  
Cambridge.

# MICRO MULTIPLEXED DISPLAY

THE circuit shown (Fig. 1) is driven from a 6802 evaluation unit and can operate up to eighteen displays although only six are used in this application.


**HARDWARE:** The hex display requires four data lines, therefore the 8 bits on the PIA output lines (PB0–PB7) can supply data to two displays at any instance.

The PIA CB2 port is programmed to produce a strobe pulse on each 'write' operation and this is used via the 7493 and 7442 to generate three 'blanking' signals in sequence which multiplex two displays per occasion.

Decimal 3 output from the 7442 is used to reset the 7493 following generation of the blanking pulses.

Before transmitting data to the display, it is necessary to ensure that the 7493 is in the 'ready' position. This is achieved by means of the 74LS132 (IC9). When the reset switch (S1) is depressed then the oscillator formed by IC9 is enabled via TR2 and the 7493 is clocked until output 3 (Pin 4) on the 7442 is low. The reset circuit 'locks up' at this point and the 'ready' i.e.d. is energised via TR1. The display is now ready to accept data from the 6802.

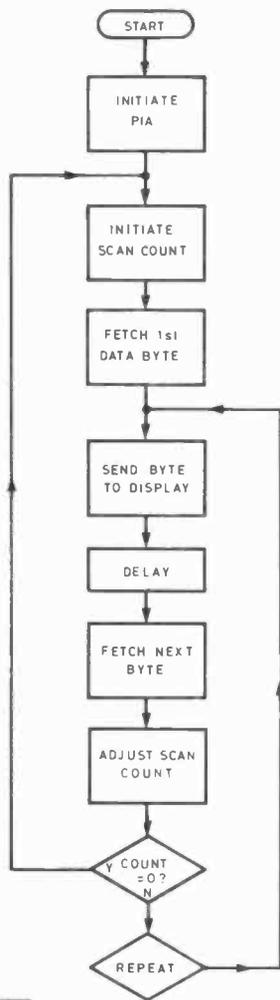**SOFTWARE:** The 6821 PIA is initiated with 'B' side as outputs and CB2 producing a strobe pulse on each write operation. Address 0030 is used as a scan counter and is loaded with 04 (pin ). The first data byte is obtained from address 0040 and after sending to the display, the



Flow chart

Add	Code	Mnemonics	Comments
0000	7F 4003	CLR PIA CRB	Set all PIA
0003	86 FF	LDAA# FF	'B' I/O lines
0005	B7 4001	STAA PIA DRB	as outputs
0008	86 2C	LDAA# 2C	and select
000A	B7 4003	STAA PIA CRB	CB2 to
			produce o/p
			strobe pulse.
000D	C6 04	LDAB# 04	Set up scan
000F	07 30	STAB \$ 30	count at
			addr 0030
0011	CE 0040	LDX# 0040	Fetch 1st
0014	A6 00	LDAA#00	data byte
			from addr
			0040
0016	B7 4001	STAA PIA DRB	Send byte to
			display
0019	01	NOP	External
001A	01	NOP	data bus
			'settling'
			time delay
001B	08	INX	Fetch next
			byte
001C	7A 0030	DEC \$0030	Adjust scan
			count
001F	27 EC	BEQ	Start new
			scan
0021	20 F1	BRA	Send next
			byte to
			display

Notes:


- 1 Scan Count is located at addr 0030.
- 2 PIA CBR is located at addr 4003.
- 3 PIA DRB is located at addr 4001.
- 4 Display data located at addr's 0040, 41 and 42.

Software table

next byte is read from 004 etc. When three bytes have been transmitted to the display the programme jumps back to re-load the scan counter, and thus the cycle is repeated. As mentioned earlier, it is possible to expand the system to cater for 18



## STEAM WHISTLE

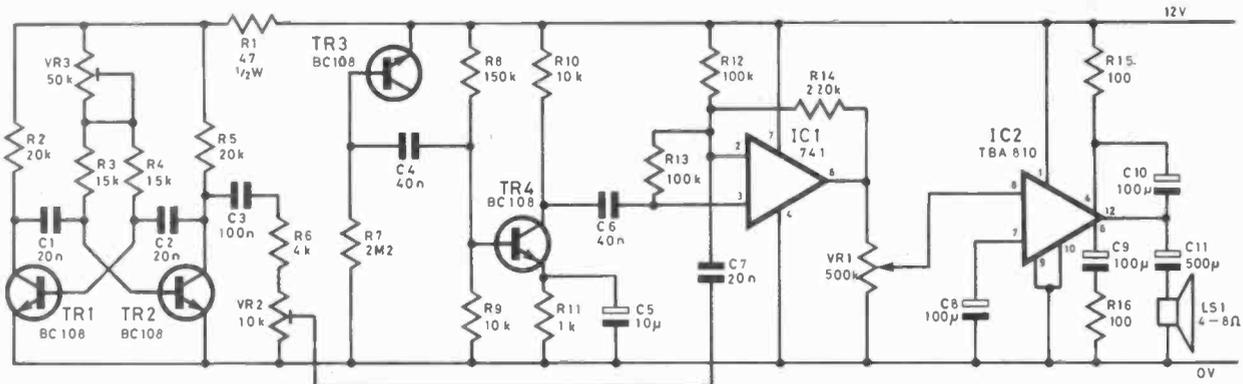

EG995


**T**HIS circuit produces a sound similar to that of a steam locomotive whistle. TR1 and TR2 form a multi-vibrator, the frequency of which is set by VR3. This is the "toot" part of the whistle. TR4 amplifies white noise generated

across the reverse biased transistor TR3. White noise and "toot" are mixed by IC1, the ratio of each being set by VR2. The output from IC1 is fed to a simple amplifier based around the TBA 810 device.

The positive 12V could be fed to the

circuit by a push switch near the controller or by the model train itself by means of reeds or microswitch devices.

David John,  
Alvaston,  
Derby.

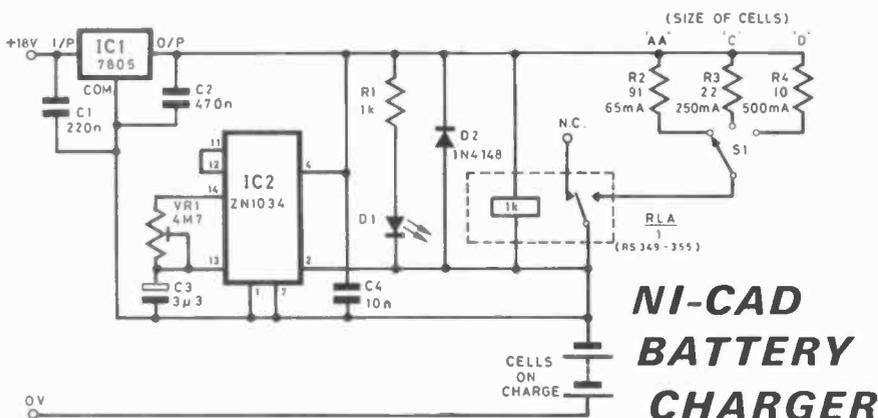

## NI-CAD BATTERY CHARGER


EG1014

**T**HE circuit shown is for a constant current Ni-Cad battery charger. It features a timed charge rate followed by a trickle charge for an indefinite period.

At switch on the output of the ZN1034 timer goes low bringing on the relay. This in turn passes a constant current from a 7805 voltage regulator to charge the batteries. After a delay of up to 12 hours, as set by the potentiometer, the output goes high switching off the relay. The cells now pass only the quiescent current of the circuit which is approximately 12 mA.

Up to six cells may be charged in series and an l.e.d. is included to indicate when the batteries are on full charge.

P. Thompson,  
Glasgow.

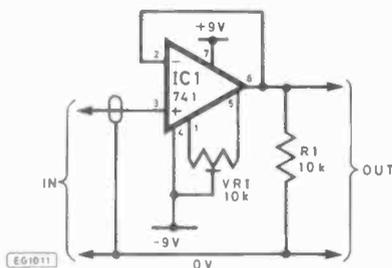

EG1011

**F**OR measuring voltages in circuits where currents are very small and resistances large, an ordinary multimeter is unsuitable because it draws an appreciable current from the circuit and therefore gives erroneous readings. It may also upset the operation of the circuit. This very simple impedance converter makes it possible to get true readings with even the most ordinary meter.

## HIGH Z INPUT FOR VOLTMETER

The op amp is connected as a unity-gain voltage follower. The voltage to be measured is applied between the non-inverting terminal and 0V. In this mode the input impedance can be very high—many tens of megohms maybe—but the output of the op amp is of very low impedance and will easily drive an ordinary meter. The voltage at the output will follow exactly that at the input, and the use of the offset nulling facility in a 741 ensures precise tracking between input and output. The nulling preset should be adjusted so that, with the input shorted, there is exactly nil voltage between output and the 0V line, as measured with the most sensitive range of a meter. The current drawn

from the supply is minimal, and if two little 9V batteries are used, voltages up to about 8V may be measured. If only one battery is used, the junction between two 1k resistors across the supply will provide the 0V point, allowing measurement of voltages up to about 4.5V. To avoid any interference or hum pick-up, the input must be screened to 0V, and the whole ought to be in a metal case grounded to 0V.

Make input and output connections before switching power on; if pin 3 is left floating pin 6 will quickly drift into saturation and perhaps damage the sensitive range of a good meter.

S. A. R. Guest,  
Truro.

# Computer Hobbyists... £50 for your program!

PE is interested in buying software written by hobbyists for popular microcomputers. If you have a game, biorhythm, mortgage, bank, filing, calendar or other general purpose program you have written yourself we would like to see it—even if you are new to software writing.

We will offer £50 for each accepted program, so send it in, you have nothing to lose.

Program tapes carrying your name and address and, if possible, a listing should be sent to Practical Electronics Software, IPC Magazines Ltd., Westover House, West Quay Road, Poole, Dorset. Each program should be accompanied by the following signed declaration:

The enclosed program entitled ..... is my own work and has not been offered to any other company. The program is for a ..... machine (state type of computer it will run on). It requires ...K of memory.

If you are under 16 years please get your parent or guardian to countersign the declaration.

All tapes will be returned.

# Grab a Banana

Pantec's revolutionary hand held multimeter introduces a new concept in low cost, high sensitivity meters. Banana's full range of functions make it a must for the electronics hobbyist.

- It's shock-proof
- It's totally protected up to 250v AC/DC
- It's got audible bleeper for continuity checks and battery test
- It's got permanently connected probes (no socket selection)
- You can operate it with one hand
- It's only **£25.99**

incl. VAT and UK P/P



#### SPECIFICATIONS

- Sensitivity: 20k $\Omega$ /V DC and 10k $\Omega$ /V AC
- DC Volts: 0.5-5-25-100-500V
- AC Volts: 50-250-1000V (max 750V)
- DC Current: 50 $\mu$ A-50mA-500mA-2.5A
- Resistance: Up to 2M $\Omega$  in 3 ranges
- Accuracy: 2% DC - 4% AC
- Dimensions: 173 x 86 x 29 mm
- Weight: 200g
- Supplied with soft carrying case and spare fuse

Write or phone for details

## The Banana Multimeter

**PANTEC**

Carlo Gavazzi (UK) Ltd.,  
162/164 Upper Richmond Road,  
London SW15 2SL  
Tel: 01-785 9022 Telex: 8952493

# BAZAAR

**WIRELESS** World 1953 to 1963. Electronic Eng. bound volumes 1960 to 1963 offers. B. M. Fuller, 25 Manor Road, Barnet, Herts.

**SPECTRUM** wanted. Please state price, postage and eventual faults (if any, detailed). Andre Bakken, Wergelandsvegen 26, 8500 Narvik, Norway.

**WANTED** heads for Truvox R94 tape recorder or R94 series recorder deck. B. T. Hughes, 25 The Drive, Arden Park, Bredbury, Cheshire SK6 2ED. Tel: 061 430 5068.

**KEYBOARD** Carter 75 COMF ASCII professional metal frame type. Brand new unused £30 plus p&p. N. F. Harris, 4 Field Rise, Burton on Trent. Tel: 0283 42558.

**GRAND** clearout of my surplus components. Both new and used. Many bargains s.a.e. for list. J. H. Rudge, 20 Blackthorne Close, Sollihull, West Midlands B91 1PF.

**BARGAIN:** PE Microsynth without case, needs slight attention. Constructed kit. £85 o.n.o. K. P. Holloway, 63 Highlands Road, Andover, Hants SP10 2PZ. Tel: 0264 62438 after 6pm.

**WANTED** circuit diagram for Kenwood trio tuner amp KR 3200. Loan, sale, all replies acknowledged. Mr. A. Jeremiah, 77 Gwendoline Street, Treherbert, Rhondda, Mid. Glam. CF41 5BP.

**PRACTICAL** Electronics Jan. 1978 to May 1983 in good condition £15. o.n.o. Buyer collects. Tel: Ringwood 6730. F. Crane, 'Homeland', 20 School Lane, St. Ives, Ringwood, Hants. BH24 2PF.

**UK101** 8K cased Cegmon, new BASIC 4 and sound including programs and books. D. Callender—Tel: Banbury 0295 53475.

**WANTED** borrow, buy operating instructions and or circuit for "Eagle International" Proa 120 power amp. A. Ross, 109 Balnagask Road, Aberdeen AB1 3HP.

**NEW:** Thandar TG100 Func/Gen, logic probe LP-1, TRS-80 pocket computer printer. Tel: Newcastle 674196 after 6p.m. Mr. P. A. Jackson, 38 Alverston Close, Lemington Rise, Newcastle NE15 8TB.

**CHIPS** 8085 £2—8755 4 off £4 each, TMS 4030 40 off 75 pence each. G. Heath, 103 Pollards Oak Road, Oxted, Surrey. Tel: Oxted 4503.

**URGENTLY** wanted, Practical Wireless December 1975. NAD 3020 stereo amplifier for sale. Perfect. Ring 090 62 5615. S. Busbridge, 29 Clarence Drive, East Preston, Littlehampton, Sussex BN16 1EJ.

**WANTED** circuit diagram for Tequipment oscilloscope, type D43 also manual. Mr. A. Cockerill, 23 Cortina Ave, High Barnes, Sunderland SR4 8NE. Tel: 284962.

**UK101** 32 x 48 12K BASIC, 16K RAM, Motherboard, EPROMS + programmer, sound, 1/2 MHz 3/600B + software £200 o.n.o. Tel: 01-868 9524. N. Brooks, 103 Drake Rd, Harrow, Middlesex HA2 9DZ.

**WANTED** (ideal for beginner) a walkie talkie and telephone amplifier. Circuit diagram and construction details. Francis Anthony, Apt. Blk 34, Whampoa West, 12-87, Singapore 1233, Republic of Singapore.

**VARIOUS** University laboratory instruments for sale. Scales, counters, stabilised e.h.t. high voltage generators. S.a.e. for details. Mr. J. Gardner, 84 Old Lansdowne Rd, West Didsbury, Manchester M20.

**ROLAND** Rhythm 77 £50. Harvard 40 channel hand-held C.B. £25 or swap both for synthesiser. John Hill, 28 South Rd, Watchet, Somerset (any time).

**PAIR** 16 ohm 12W peak ITT speakers in teak cabinets £10 or near. J. H. Bailey, 10 Henley Lodge, Yatton, Bristol. Tel: 0934 832025.

**MICROTAN** 65 cased with p/supply, Tanex, XBug, graphics, keyboard, leads & manuals. £110-00 or Exchange good SC110 scope. Mr. E. Read, 23 Ditchbury, Lymington, Hants. Tel: Lymington 77473.

**WANTED** Hamlin type 3920-313-050, 6 digit l.c.d. to complete project. G. M. Kenny, 5 Harcourt Ave, Wallasey, Merseyside. Tel: 051 639 8956.

**WANTED** blown up ZX81 or similar RAM pack etc. up to £10 paid. Mr. C. Cox, 8 Levana Close, London SW19 6HP. Tel: 01-789 8754.

**YAMAHA** CS01 mono synth, as new. Only £120. M. Read, The Old Punch Bowl & Grapes, Adstock, Buckingham, Bucks. Tel: Winslow 2757.

**WELLER** soldering gun, case, spare tips £16; Benkson personal stereo cassette, headphones, case, batteries £30 o.n.o. Mr. D. Evans, 27 Summerhill Rd, Onchan, Isle of Man. Tel: 0624 3634.

**HAMEG** HM312 scope, one year old, pristine, £170 inc. delivery. Mr. C. Bowden, 7 Parc Eglos, Helston, Cornwall TR13 8UP.

**BINATONE** 5-star 40-channel 4 watt FM-CB mobile transceiver. Full controls. New. £30. Call Chang 041 332 7695 after 9p.m. K. Y. Chang, 70, 1-up, Ashley St., Glasgow G3 6HW.

**O.S.I.** C2 16K, Cegmon, software, user group mags. £175 o.n.o. Tel: Redditch (0527) 44952. W. J. Partridge, 31 Duxford Cl, Redditch, Worcs. B97 5BS.

**300** plus electronic mags, for sale. All popular publications from 1972 £40 buyer collects. J. Parsons, 31 Ball Rd, Llancumney, Cardiff CF3 9BW. Tel: 0222 793169.

**WANTED** service manual/parts list for Olivetti TE300/329 teletype. R. Caradine, Naworth Castle, Brampton, Cumbria. Tel: (06977) 3408.

**PW** Dec. 68 to May 83, good condition, offers. C. Wooff, 38 Wigan Road, Ashton-in-Makerfield, Wigan, Lancs WN4 9BJ. Tel: 724207.

**UK101:** 40K, Cegmon, 20-screens, hi-rb board, tool kit, twin-disks, 2 x DOS + much more, write/phone for details. C. Hellen, Vine Cott., Main Road, Alresford, Colchester, Essex CO7 8DD. Tel: Wivenhoe (020622) 5671.

**ACORN** System 1 c.p.u. board wanted. Working or faulty. Tel: Bob Brookes, 0905 51303 daytime.

**AVO** 8 MKV as new £45. Tel: Newport, Gwent 0633 63241 after 6p.m.

**AVO** multimeter 240V supply 40,000 ohms/volt usual functions plus capacitance-power £15. Tel: Rochdale (0706) 76590. D. R. Halsall, 6 Lincoln Drive, Smithybridge, Littleborough, Lancs.

**WANTED** information or circuit cards from the Metropolitan Vickers 950 computer. Mr. Andrew Wylie, 18 Rue De Lausanne, 1201 Geneva, Switzerland.

**YAMAHA** PS-10 automatic bass chord portable full-size keyboard. 3½ octave. Auto-Rhythm. New. £165. Call Chang 041 332 7695 after 9p.m. K. Y. Chang, 70, 1-up Ashley Street, Glasgow G3 6HW.

**COMPONENTS** surplus BC207, 0.15 µF/250V, 0.22µF/400V, 4.7nF polystyrene, 2.2µF/40V elec, 2µF/10V elec. All £3 per 100 + p&p. D. G. Robins, 21 Mountfield Rd, Bramhall, Stockport, Cheshire. Tel: 061 439 3648.

**WANTED** JVC Turntable as supplied by BK Electronics approx. 18 months ago. Tel: Alan 01-866 4579.

**LARGE** box of new electronic components. Value over £80.00. Accept £10.00. Mr. G. Nicholson, 95 Priory Estate, South Elmsall, Pontefract WF9 2ST.

## OVERSEAS AGENTS

Subscriptions to PE are available direct from us — see notice on page 54 — however, there are also a number of overseas agents around the world who can accept your subscription order. These agents are listed below for your information and assistance.

### BELGIUM

Agence et Messageries De La Press SA  
1 Rue de la Petite-Ille  
B-1070 Brussels

Industrial & Business Pubs.  
200 Avenue de Messidor  
BTE 4  
1180 Brussels

Office International De Librairie S.P.R.L.  
30 Avenue Marnix  
1050 Brussels 5

Scientific & Technical Book Centre  
Rue de Neutchatel 12  
1060 Brussels

W. H. Smith & Son (Belgium) S.A.N.V.  
Boulevard A Max Lean 71-79  
B-1000 Brussels

### DENMARK

Arnold Busck Boghandel  
Kjobmagergade 49  
Copenhagen K DK 1150

Dansk Centralagentur D C A /Inc Tidskrift Service/  
Slusholmen 6-8  
DK-2450 Copenhagen SV

Dansk Bladdistribution v/Mogens Schroder  
Rosenberggade 54  
P.O. Box 2125  
DK-1015 Copenhagen K

DBK Subscription Service  
Siljengade 6  
DK-2300 Copenhagen 5

Jul Gjallerups Boghandel  
Solvgade 87  
DK-1307 Copenhagen K

N J Haaseg Bogimport A/S  
Loevstraede 8  
1132 Copenhagen K

Munksgaard Int.  
Book & Pubs Ltd.  
35 Norre Sogade  
DK-1370 Copenhagen K

Rhodos International  
Subscription Agency  
Strandgade 36  
Copenhagen DK-1401

### SCIENTIA

International Sub Agency Aps  
Loevstraede 4A  
DK-1152 Copenhagen K

### FINLAND

Akateeminen Kirjakauppa Oy  
P.O. Box 128  
S F 00101 Helsinki 10

Lehtimarket Oy  
P.O. Box 16  
SF-00311  
Helsinki 51

Lehtitoimisto Kankainen  
P 119  
SF-2B101 Pori 10

Suomalainen Kirjakauppa Oy  
C/o Rautakirja Oy  
Subscription Department  
P.O. Box 2  
01641 Vantaa 64

### FRANCE

B E D I  
8 Place de la Republique  
75011 Paris

### S. Brentano

Subscription Department  
37 Avenue de L'Opera  
75002 Paris

Dawson-France SA  
B P 40  
F-91121 Palaiseau

Europelodiques SA  
31 Avenue de Versailles  
78170 La Celle St. Cloud

France Publications  
108 Rue Reaumur  
Paris 75002

Lavoisier Abonnements  
Technique et Documentation  
11 Rue Lavoisier  
F-75384 Cedex 08

Mons. R. Martin  
Boite Postale 22  
92420 Vaucresson

Office International de  
Documentation et Librairie  
48 Rue Gay-Lussac  
75240 Paris Cedex 05

W. H. Smith & Son SA  
248 Rue de Rivoli  
75001 Paris  
Attn: Miss M. Nolot  
Subscription Department

**W. GERMANY**

Ex Libris Buchhandelsges.  
Ferdinand-Dirichs-Weg 28  
6 Frankfurt-AM-Main

Philip Korte & Co.  
Mode-Vertrieb  
P.O. Box 1536  
D-6800 Mannheim 1

Kunst & Wissen-Erich Bleber  
Postfach 46  
Wilhelmstrasse 4  
7000 Stuttgart 1

W. E. Saarbach GmbH  
Postfach 10 16 10  
Follerstrasse 2  
5 Cologne 1

H. G. Schaderbrodt  
St. Andre Strasse 26A  
6105 Ober-Ramstadt

Buchhdig Konrad Wittwer  
Koenigstr 30  
Postfach 147  
7 Stuttgart

**D.D.R.**

Buchexport Volkseigener  
Aussenhandelsbetrieb Der  
D.D.R.  
701 Leipzig Postfach 160  
Leninstrasse 16

**ITALY**

Anglo American Book Co. SRL  
Via Della Vite 57  
00187 Roma

Bozzi F. Illi S.A.S.  
Piazza Della Meridiana 2  
16124 Genova

Centre Edizloni Technische  
Internazionali SRL  
Via Pordonone 17  
20132 Milan  
Attn: Mr. A. Vais

Goerlich & Co.  
Via San Sentatore 6/2  
Casella Postale 1712  
Milan 20100

Ulricho Hoepfli  
Casa Editrice Libraria  
Via U Hoepfli 5  
20121 Milan  
Intersciantia  
Via Mazze 28  
10149

Nuova Stampamerica Subs  
Agency SAS  
Via P. Micca 3  
10121 Torino

Sperling & Kupfer  
Piazza San Babila 1  
20122 Milan

Lib. Internazionale Di Stefano  
Via C. Roccatagliata Ceccardi  
16121 Genova

**NETHERLANDS**

Bookimpex B.V.  
Vaenkade 26/27  
The Hague 2513 EG

D & N-Faxon B.V.  
Subscription Service  
P.O. Box 197 1000 AD  
Amsterdam

International Journals Group  
P.O. Box 2192  
1000 CD Amsterdam  
For the attention of: Ms. W.  
Boenker

Kniphorst's Boekhandel  
Postbus 67  
6700 VB Wageningen

De Muiderkring N V  
Nijverheidswerf 17-21  
1400 AA Bussum

Martinus Nijhoffs Boekhandel  
P.O. Box 269  
250 AX The Hague

Swets Subscription Service  
P.O. Box 830  
2160 SZ Lisse

**NORWAY**

A/S Narvesens  
Litteraturtjenste  
Box 6125 Etterstad  
Oslo 6

Tidsskriften Sentralen Tanum-  
A/S  
P.O. Box 1177 Sentrum  
Oslo 1

**SPAIN**

Commercial Atheneum S.A.  
Apartado De Correos 1148 de  
Barcelona  
E-Barcelona

Diaz De Santos  
Wholesale Subscription Agency  
Lagasca 95  
Madrid 6

Distribuidora Internacional-  
Dinter  
Apartado 9156  
Duque de Sesto 38  
Madrid 9

Libreria Mundi-Prensa  
Apartado 1223  
Castello 37  
Madrid 1

**SWEDEN**

Esselte Tidsskrifts Centralen  
Subscription Agency  
P.O. Box 62  
Gamla Brogatan 26  
S-101 20 Stockholm  
Attn: Mr. D. Schuttz-Subs  
Manager

Lundgrens Bokhandel  
Soderkatan 3  
S-211 34 Malmo

SCI-TECH Publications AB  
Box 73  
122 21 Enskede 1

Utlandsk Facklitteratur  
Tage Nilsson  
Transkvarnsgatan 6 C  
S-573 00 Tranas  
Wennergren Williams AB  
Fack  
S-104 25 Stockholm 30

**SWITZERLAND**

J. de Croze International  
Establishment  
81 Avenue Louis Casai  
P.O. Box 44-1216  
Geneva

Hans Huber Booksellers  
Langgasstrasse 76  
CH 3000 Bern 9

Naville and CIE  
5-7 Rue Levrier  
Case Postale 887  
CH 1211 Geneva 1

Kurt Staheli & Co.  
Bahnhofstrasse 70  
CH-8021 Zurich

**U.S.S.R.**

Mezhdundarodnaja Kniga  
G-200  
Moscow

**AUSTRALIA**

Collins Booksellers Pty Ltd  
115 Elizabeth Street  
Melbourne  
Victoria 3000  
Attn: Subscription Dept. 2nd  
Floor

Engineering Publications (Aust)  
P.O. Box 319  
Split Junction  
N.S.W. 2088

Globe Subscription Agency Pty  
Ltd  
P.O. Box 471  
Double Bay  
N.S.W. 2028

Gordon & Gotch Limited  
P.O. Box 29  
Burwood 3125  
Victoria

John Hinton Pty Ltd  
P.O. Box 311  
Chatswood  
N.S.W. 2067

International Subscription  
Agencies Pty Ltd  
P.O. Box 709  
Toowong Qld 4066

McGills Authorised  
Newsagency Pty Ltd  
187-193 Elizabeth Street  
Melbourne  
Victoria 3000

Robinson Manton Pty Ltd  
190 Bourke Street  
Melbourne  
Victoria 3000

Standard Book Suppliers Pty  
Ltd  
Subs Department  
136 Rundle Street  
Adelaide 5000

Tait Book Shop  
415 Bourke Street  
Melbourne C1

Mrs. Camille Sandham  
The Technical Book & Magazine  
Co.  
289-299 Swanston Street  
GPO Box 2192 T  
Melbourne  
Victoria 3000

Thoroughbred & Classic  
Agencies  
321 Warrigal Road  
Chellenham  
Victoria 3192

University Co-operative  
Bookshop  
76-84 Bay St  
Broadway  
N.S.W. 2007

**ARGENTINA**

Carlos A. Traboulsi (Bookstore)  
Casilla de Correo 4574  
1000 Buenos Aires

**BRAZIL**

P.T.I. Ltda  
Subscription Agents  
Caixa Postale 1703  
01000 Sao Paulo SP

**CHINA**

China National Pubs Import  
CDR  
P.O. Box 88  
Peking

**INDIA**

Allied Publishers Ltd  
Post Box 155  
13/14 Asaf Ali Road  
New Delhi 110002

Allied Publishers Subscription  
Agency  
15 J.N. Heredia Marg.  
Ballard Estate  
Bombay 400038

Allied Publishers Subscription  
Agency  
750 Mount Road  
Madras 600002

Central News Agency  
23/90 Connaught Circus  
New Delhi 110001

Creative Books & Periodicals  
Pvt Ltd  
7 Nanabhai Lane  
Bombay 400-023

Higginbothams Private Ltd  
165 Anna Salai  
(Post Box 311)  
Madras 600002

Global Publishers Service Pte  
Ltd  
Block A31 3rd Floor  
Shai Ram Industrial Estate  
GD Ambekar Road, POB No.  
7121  
Bombay 400 031

International Book House Pte  
Ltd  
Indian Mercantile Mansion Extn  
Madame Cama Road  
Bombay 400 039

L. B. Publishers & Distributors  
(Private) Ltd  
90-91 Mahatma Gandhi Road  
Bangalore 560 001

Macmillan India Limited  
Subscription Department  
21 Patullo Road  
Madras 600 002  
Tamil Nadu

Mahajan Brothers  
Super Market-Basement  
Ashram Road  
Ahmedabad-9 (GS)

Strand Book Stall  
Dhannur  
Sir P M Road  
Bombay 1

Subscribers Subscription  
Services India  
21 Raghunath Dadaji Street  
2nd Floor  
Bombay 400 001

Universal Subscription Agency  
Pvt Ltd  
117/H-1/294-8 Model Town  
Pandu Nagar  
Kanpur 208005

**ISRAEL**

Hakhen Agencies Ltd  
44 Derekh Patah Tikva  
Rooms 410-412  
P.O. Box 36125  
Tel Aviv

ABC Bookstore  
71 Allenby Road  
P.O. Box 1283  
Tel Aviv

Sifriat Poalim Limited  
Supply Department  
73 Allenby Street  
Post Box 526  
Tel Aviv

**JAPAN**

Asahiya Shoten Ltd  
Foreign Books Dept  
Central POB 398  
Osaka 530-91

Hokuto Trading Co. Ltd  
4-5 Aizumi-Cho  
Shinjuku-Ku  
Tokyo 160

Kinokuniya Company Ltd  
Attn: Teruzo Kubota  
General Manager, Journal Dept  
Odakyu West-Shinjuku Bldg  
47-1, 1 Chome, Hatsudai  
Shibuya-Ku  
Tokyo 151

Japan Pub Trading Co. Ltd  
P.O. Box 5030  
Tokyo International  
Tokyo 100-31

Kaigai Publications Ltd  
P.O. Box 5020  
Tokyo International  
100-31 Tokyo

Kitao Publications Trading Co.  
Ltd  
New Asaki Bldg  
3-18 Nakanoshima 2-chome  
Kita-ku C P O Box 936  
Osaka 530-91

Kokusai Shobo Ltd  
5 Ogawamachi 3-chome  
Kanda  
Chiyoda-ku  
Tokyo 101

Koyo Shoji Co. Ltd  
Nitto Bldg  
4-10 Nihonbashi Hongoku-Cho  
Chuo-Ku  
Tokyo 103

Maruzen Co. Ltd  
P.O. Box 5050  
Tokyo International  
100-31

Oriental Book Service Co. Ltd  
C/o Roppongi Building  
11-4 Roppongi 4-chome  
Minato-Ku  
Tokyo 106

O.T.O. Research Corporation  
Takeuchi Bldg.  
1-34-12 Takatanobaba  
Shinjuku-Ku  
Tokyo 160

Pacific Book Inc  
Morikawa Building  
7-41 Idabashi 1-Chome  
Chiyoda-Ku  
Tokyo 102

Sanyo Shuppan Boeki Co. Inc  
Chief Foreign Dept  
P.O. Box 5037  
Tokyo International 100-31

Shimada & Co. Inc  
9-29 Minami-Aoyama 5-Chome  
Minato-Ku  
Tokyo 107

Tokyo Publications Service Ltd  
P.O. Box 5085  
Tokyo International  
Tokyo 100-31

U.S. Asiatic Co. Ltd  
Tsutsumi Building  
13-12 1-Chome Shimbashi  
Minato-Ku  
Tokyo

**MALAYSIA**

S S T Trading Sdn Bhd  
385 Jln 5/59 P.O. Box 227  
Petaling Jaya  
Selangor

**NEW ZEALAND**

Gordon & Gotch (NZ) Ltd  
P.O. Box 3207  
Auckland

R. Hill & Son Ltd  
Ideal House  
Eden Street  
Newmarket, Auckland 1

Peryer Educational Books (S.I.)  
Ltd  
8 Yaldhurst Road, Upper  
Ricceton  
Christchurch 4  
P.O. Box 6034  
Technical Books Ltd  
P.O. Box 5174  
1st Floor, McKenzies Bldg.  
(Opp. Kirkcaldies)  
222 Lambton Quay  
Wellington

**SOUTH AFRICA**

American & Overseas  
Publications (Pty) Ltd  
Box 42476 Fordsburg  
Johannesburg Tvl 2033

Argo Publications  
Post Box 1475  
Johannesburg 2000

Messrs. M & L Ettin  
International Journals  
P.O. Box 66321, Broadway  
Johannesburg 2020

Mr. Harold C. Leon  
P.O. Box 61141  
Marshalltown 2107  
Transvaal

Technical Books (Pty) Ltd  
P.O. Box 2866  
Capetown 8000

Trelaw Subscription Agency  
P.O. Box 8255  
Johannesburg

Universitas Books (Pty) Ltd  
P.O. Box 775  
Pretoria 0001



When replying to Classified Advertisements please ensure:

- That your have clearly stated your requirements.
- That you have enclosed the right remittance.
- That your name and address is written in block capitals, and
- That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

## RECEIVERS AND COMPONENTS

### FANTASTIC ELECTRONIC BARGAINS

#### VERSATILE BENCH POWER SUPPLY UNITS

Contains high quality transformer made to exacting specifications giving one 20v output and one 20-0-20v. output. All outputs 3amps. D.C. input 110/250v. 50 c/s. Bridge Rectification. Contained on metal chassis with robust compact case size 7" x 5 1/2" x 4 1/2", easily modified to give 40v, or 60v output. Makes an ideal variable power supply. Normally cost around £60.00. OUR PRICE AS NEW with circuits £8.50. Carr. £3. 2 units for £20 carr. free.

**AMPLIVOX ULTRA LIGHTWEIGHT TRANSDUCER EAR-PHONES.** Impedance 300 ohms. Made to fit inside protective and crash helmets, or can be used as pillow earphones. As new £8 per pair. P & P £1.00. 2 pairs £8 post free. 4 pairs £15 post free.

New release of **MODERN DYNAMIC MOVING COIL MICRO-PHONES.** 200 ohms impedance. Switch incorporated. With lead and DIN plug. Used but nice condition. 3 designs of case housing. Price one mike our choice £2 plus 50p p.p. Bargain offer all 3 mikes £4.50 p.p. £1.

**FOOT SWITCH.** (Mains operation). Contains two micro switches and lead. Metal case. Good condition. £3.50 each. Postage 50p. 2 for £7.50 post free.

**HAVE YOU SEEN THE GREEN CAT.** 1000x of new components, radio, electronic, audio at unbelievably low prices. Send 50p for catalogue (refundable on purchase).

Try a **JUMBO PACK.** Contains transistors, resistors, caps, pots, switches, radio and electronic devices. OVER £50 worth for £11.00. Carriage and packing £2.50.

**MINI JUMBO PACK** (£20 worth) for £5. P & P £1.50. Please add 15% VAT to all orders including carriage and P.P.

**Myers Electronic Devices**

Dept PE3, 12/14 Harper Street, Leeds LS2 7EA. Leeds 452045. New retail premises at above address (opposite Corals). Callers welcome 9 to 5 Mon. to Sat. Sunday 10 to 1 by appointment. **GOVT. SURPLUS ITEMS ALWAYS IN STOCK.**

# SMALL ADS

The prepaid rate for classified advertisements is 34 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £11.20 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Electronics and crossed "Lloyds Banks Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Dept., Practical Electronics, Room 2612, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

**PE CAR STEREO AUDIO BOOSTER** (Jan '83) 20w RMS/channel 0.2% thd: Full stereo kit of semiconductors (inc 2 x TDA2004 power IC's), resistors & capacitors, Only £12.45 inc VAT & P&P. Also new improved PE Miniature Scorpio CD electronic ignition: Full kit, down to last nut & bolt, inc drilled metalwork, wound transformer, unbeatable price/performance, Only £13.50 inc VAT & P&P. MICROSTATE LTD, 5 Northfield Close, Fernhill Heath, Worcester, WR3 7XB.

**ELECTRONICS COMPONENTS, MERSEYSIDE.** Myca Electronics, 2 Victoria Place, Seacombe Ferry, Wallasey, L44 6NR, Mail Order send 50p. For price list refundable off first order. Tel. 051-638-8647.

**PE PCB'S** EP965 £0.72, EG1138 £1.03, EA421 £0.48, EC90 £1.48, EA398 £0.99, EC84 £0.95, EG1076 £0.80, EG1074 £0.84, EG1000 £2.25, EA1060 £0.54, EA400 £2.16. Kits also available, 10% discount 2+ boards. Tel. (0865) 60741 for latest prices. **BRADLEY PRINTED CIRCUITS** (G. D. Cowan), 9 Harcourt Terrace, Headington, Oxford, OX3 7QF.

### BRAND NEW COMPONENTS BY RETURN

**Electrolytic Capacitors 16V, 25V, 50V.**  
0.47, 1.0, 2.2, 4.7 & 10 Mfd. — 5p.  
22 & 47 — 6p, 100 — 7p, (50V — 8p), 220 — 8p.  
(50V — 10p), 470 — 11p, (40V — 16p), 1000/15V — 15p.  
1000/25V — 25p, 1000/40V — 35p.

**Subminiature bead Tantalum electrolytics.**  
0.1, 0.22, 0.47, 1.0 & 35V, 4.7 & 6.3V — 14p.  
2-2/35V, 4.7/25V — 15p, 10/25V, 15/16V — 20p.  
22/16V, 33/10V, 47/8V, 68/3V & 100/3V — 20p.  
15/25V, 22/25V, 47/10V — 35p, 47/16V — 80p.

**Subminiature Ceramic Caps. E12 Series 100V.**  
2% 10 pf. to 47 pf. — 3p, 56 pf. to 330 pf. — 4p.  
10% 390 pf. to 10,000 pf. — 4p.

**Vertical Mounting Ceramic Plate Caps. 50V.**  
E12 22 pf. to 1000 pf. £6 1500 pf. to 47000 pf. — 2p.

**Polystyrene E12 Series 63V. Horizontal Mntg.**  
10 pf. to 820 pf. — 3p, 1000 pf. to 10,000 pf. — 4p.

**Miniature Polyester 250V Vert. Mtg. E6 Series.**  
0.1 to 0.68 — 4p, 1 — 5p, 15, 22 — 6p, 33, 47 — 10p.  
68 — 12p, 1.0 — 15p, 1.5 — 22p, 2.2 — 24p.

**Mylar (Polyester) Film 100V. Vertical Mounting.**  
0.01, 0.022, 0.047 — 3p, 0.1, 0.22 — 4p, 0.4, 0.5, 0.1 — 5p.

**High Stability Miniature Film Resistors 5%.**  
1W E24 Series 0.51R — 10M. (Except 7M5) — 1p.  
1/2W E12 Series 1R0 to 10M. — 1p.  
1/4W E12 Series 10R to 10M. — 5p.

1W metal film E12 Series 10R-1M. 5% — 2p, 1% — 3p.  
1N4148 — 2p, 1N4002 — 4p, 1N4006 — 8p, 1N4007 — 7p.  
8C107/8/9 — 12p, 8C147/8/9, 8C157/8/9, BF195 & 7 — 10p.

8 Pin i.c.s. 741 Op. amp — 18p, 555 Timer — 24p.  
DIL Holders 8 pin — 3p, 14 pin — 12p, 18 pin — 14p.

LED's. 3 & 5mm. Red — 10p, Green & Yellow — 14p.  
Grommets for 3mm. — 1p, Grommets for 5mm — 2p.

20mm. Q.B. Fuses .15, .25, .5, 1, 2, 3 & 5A — 6p.  
20mm. Anti Surge 100mA to 5.0A — 8p.

20mm. Fuseholders P.C. or Chassis Mtg. — 8p.  
Battery Snaps (pairs) PP3 — 6p, PP9 — 12p.

400mW Zener diodes E24 series 2V7 to 33V — 6p.

Prices VAT Inclusive Post 15p. (Free over £5.00).

**THE C. R. SUPPLY CO.**

127, Chesterfield Rd., Sheffield S8 0RN.

## NOTICE TO READERS

Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser to check both prices and availability of goods before ordering from non-current issues of the magazine.

**TURN YOUR SURPLUS** capacitors, transistors, etc. into cash. Contact **COLES HARDING & CO.** 103 SOUTH BRINK, WISBECH, CAMBS. TEL: 0945 584188. Immediate settlement.

**BOURNEMOUTH/BOSCOMBE.** Electronic components specialists for 33 years. Forresters (National Radio Supplies), Late Holdenhurst Road. Now at 36, Ashley Road, Boscombe. Tel. 302204. Closed Weds.

**300 SMALL COMPONENTS**, including transistors, diodes £2.20. 71bs assorted components £6.00. Fifty 74 series I.C.s on panel £2.20 post paid. List 25p refundable. **J.W.B. RADIO**, 2 Barnfield Crescent, Sale, Cheshire, M33 1NL.

**NOW OPEN IN NEWCASTLE** For the best in Electronic Components. Test Equipment and Accessories.

**MARLBOROUGH ELECTRONIC COMPONENTS**  
15 Waterloo Street, Newcastle NE1 4DE  
Tel. 618377

Open 9am-6pm Mon-Sat - Easy Parking  
Stockists of:  
Transistors, Resistors, Capacitors, I.C. Diodes,  
Electronic Books, Etc.

## SOFTWARE

**CONVERT ZX81** to EPROM programmer with ZP4000 unit. S.A.E. details. **ENTERPRISE TECHNOLOGY LTD.** P.O. Box 140, Wigan, WN3 6LF, Lancs.

## AERIALS

### AERIAL BOOSTERS

Next to the set fitting

**B45H/G-UHF TV**, gain about 20db. Tunable over the complete UHF TV band. PRICE £8.78.

**BH-VHF/FM RADIO**, gain about 14db, when on the off position connects the aerial direct to the radio. £7.70.

All Boosters we make work off a PP3/006p/6F22 type battery or 8v to 18v DC. P&P 30p PER ORDER.

**ELECTRONIC MAILORDER LTD**, 62 Bridge St, Ramsbottom, Lancs BL0 9AG. Tel (070682) 3036

Access/Visa Cards Welcome SAE Leaflets

## BOOKS AND PUBLICATIONS

**COMPLETE FULL-SIZE SETS** any published service sheets, £2 + LSAE except CTVs/Music Centres from £3 + LSAE. Manuals from 1930 to latest. Quotations, free 50p magazine, price lists unique technical publications for LSAE. Repair data/circs almost any named TV/VCR £8.50 by return. **TIS PE**, 76 Church Street, Larkhall, Lanarks, ML9 1HE. Phone (0698-883334).

### ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Practical Electronics for .....

insertions. I enclose Cheque/P.O. for £.....

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Practical Electronics)


NAME.....

ADDRESS.....

Company registered in England. Registered No. 53626. Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS.

Send to: Classified Department,

**PRACTICAL ELECTRONICS**

Classified Advertisement Dept., Room 2612,

King's Reach Tower, Stamford Street,

London SE1 9LS. Telephone 01-261 5846

Rate:

34p per word, minimum 12 words. Box No. 60p extra.

**MISCELLANEOUS**

**IONIZER.** Feel alert, invigorated and healthier with the amazing ZEPHION negative ion generator. Kit: £21.50p. Built: £29.80p or S.a.e. brings leaflets. Dataplus Developments, 81 Cholmeley Road, Reading, Berks, RG1 3LY. Tel. 0734 67027.

**ELECTRONIC ORGAN KEYBOARDS** and other parts being cleared out as special offer. Elvins Electronic Musical Instruments, 40A Dalston Lane, London E8. Tel: 01-986 8455.

**PRACTICAL ELECTRONICS P.C.B.'s**

May 83	Personal Stereo Amp EC90	£3.47
June 83	Program Conditioner EP965	£1.95
	Automobile Tester EG1138	£3.23
July 83	Counter EG1157	£2.47
	Counter EG1154-62	per set £4.78
	Counter EG1168-72	per set £7.10

For full list and current pcb's send SAE CWO Please. Postage: add 35p postage and packing to complete order. Europe 70p.

**PHOTO DESIGN**  
14 Downham Road, Hamsden Heath, Billericay, Essex CM11 1PU. Telephone 0268-710722

**BURGLAR ALARM EQUIPMENT.** Ring Bradford (0274) 308920 for our Catalogue or call at our large showrooms opposite Odsal Stadium.

**CLEARING LABORATORY:** scopes, generators, P.S.U's, bridges, analysers, meters, recorders, etc. 0403-76236.

**THE SCIENTIFIC WIRE COMPANY**  
811 Forest Road, London E17. Telephone 01-531 0574

**ENAMELLED COPPER WIRE**

SWG	1 lb	8 oz	4 oz	2 oz
8 to 34	3.63	2.09	1.10	0.88
35 to 39	3.82	2.31	1.27	0.93
40 to 43	6.00	3.20	2.25	1.61
44 to 47	8.67	5.80	3.49	2.75
48	15.96	9.58	6.38	3.69

**SILVER PLATED COPPER WIRE**

14 to 30	9.09	5.20	2.93	1.97
----------	------	------	------	------

**TINNED COPPER WIRE**

14 to 30	3.97	2.41	1.39	0.94
----------	------	------	------	------

Fluxcore Solder

	5.90	3.25	1.82	0.94
--	------	------	------	------

Prices include P&P VAT. Orders under £2 add 20p. SAE for list of copper and resistance wire. Dealer enquiries welcome.

**CABINET FITTINGS**

Fretcloths, Coverings, Handles, Castors, Flight Case Locks & Parts, Jacks, XLRs, Bulgins, Reverb Trays, P & N mic Stands, ASS Glassfibre Horns, CELESTION POWER Speakers.

**ADAM HALL SUPPLIES LTD.**

Send 30p cheque/ P.O. for illustrated catalogue: Adam Hall (PE Supplies), Unit G, Carlton Court, Grainger Road, Southend-on-Sea.

**CENTURION ALARMS**

We manufacture, you save £££'s Send s.a.e. or phone for our Free list of professional D.I.Y. Burglar Alarm Equipment and accessories. Discount up to 20% off list prices, e.g. Control Equipment from £15.98, Decoy Bell Boxes from £5.95 inc.

**TRADE ENQUIRIES WELCOME**  
☎ 0484-21000  
or 0484 35527 (24 hr. ans.)  
**CENTURION ALARMS (PE)**  
265 Wakefield Road, Huddersfield HD5 9BE, W. Yorkshire  
Access & Visa Orders Welcomed

**BUSINESS OPPORTUNITIES**

**BORED? FRUSTRATED? ANGRY? AMBITIOUS?** Then read THE ENTREPRENEUR, probably the world's most exciting monthly publication for self-reliant men and women wishing to create/develop/survive in their own business. Free introductory offer: S.a.e. THE ENTREPRENEUR, Dept. B38A, Aiston, Cumbria CA9 3RP.

**EDUCATIONAL**

**CAREERS IN MARINE ELECTRONICS.** Courses commencing September and January. Further details, The Nautical College, Fleetwood FY7 8JZ. Tel: 03917 79123.

**COURSES**

**CONQUER THE CHIP ...** Master modern electronics the PRACTICAL way by SEEING and DOING in your own home. Write for your free colour brochure now to British National Radio & Electronic School, Dept C2, Reading, Berks RG1 1BR.

**SERVICE SHEETS**

**BELL'S TELEVISION SERVICES** for service sheets on radio, TV, etc. £1.25 plus SAE. Service Manuals on Colour TV and Video Recorders, prices on request. SAE with enquiries to B.T.S., 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 55885.

**FOR SALE**

**SHEETMETAL FOLDERS.** 18" x 18G steel, 16G Aluminium, Bench or Vice held. £38. Carriage £4. Leaflet 01-890 7838.

**KITS & PCB's FOR P.E. PROJECTS**

Full Kits including PCB's, Hardware and Cases (unless listed separately), I.C. Sockets, Veropins, Wire, Nuts & Bolts all included. Reprints 45p extra.

Program Conditioner June 83	£16.98	Battery Tester April 83	£12.55
Automobile Test Set May 83	£32.56	Viper Delay April 83 (Less Relay)	£7.44
Mains Watchdog May 83	£14.47	Car Audio Booster (Stereo) Jan 83 (Less Case)	£18.98
Personal Stereo Amplifier May 83 (less case and transformer)	£26.96	Diecast Case extra	£4.75
Switched Capacitance Phaser April 82	£20.48	Frost/Overheating Warning Jan 83	£6.20

**PCB's** Top quality printed Circuit Boards made from P.E. masters glass fibre board, roller tinned & drilled.

2 Digit Down Counter July 83	£2.27	Digital Stopwatch Oct. 82	£2.23
4 Digit LCD Up Counter July 83 (2)	£4.88	Audio Sweep Osc. Oct. 82	£5.52
4 Digit LED Down Counter July 83 (3)	£8.83	Mini Chorus Unit Oct. 82	£2.85
4 Digit LCD Down Counter July 83 (3)	£7.68	Audio Debug Probe Sept. 82	£1.58
Program Conditioner June 83	£1.89	Waveform Digitiser Sept. 82	£12.60
Automobile Test Set June 83	£3.47	Combo Amp (Main) Aug. 82	£3.45
Mains Watchdog May 83	£2.07	Combo Amp (Preamp) Aug. 82	£3.62
Personal Stereo Amp May 83	£4.54	Audio Test Set July 82	£6.38
Battery Tester April 83	£1.95	Instrument Tuner July 82 (2)	£3.61
Viper Delay April 83	£2.08	Versatile Car Alarm July 82 (2)	£3.65
Switched Capacitor Phaser April 83	£2.26	Burglar Deterrent July 82	£2.74
Digital Frequency Meter	£3.73	Auto Flash Slave June 82	£1.34
Car Accessory P.S.U. March 83	£1.53	Prescaler + Freq. Meter May 82 (3)	£2.80
Car Radio Booster Feb. 83	£1.74	Prog. Timer/Controller May 82 (3)	£9.08
Digital Tacho Jan. 83 (3)	£4.80	Battery Backup June 82	£2.34
Car Audio Booster Jan. 83	£3.25	Function Generator May 82	£3.58
Stylochord Dec. 82 (3)	£7.49		

**MORE KITS AND COMPONENTS IN OUR LISTS**  
FREE PRICE LIST  
Price list included with orders or send s.a.e (9 x 4)  
CONTAINS LOTS MORE KITS, PCB's & COMPONENTS

**ELECTRONICS CATALOGUE**  
Illustrations, product descriptions, circuits all included. Up-to-date price list enclosed. All products are stock lines for fast delivery. Send 80p in stamps or add 80p to order. Free to Schools/Colleges requested on official letterhead.

**MAGENTA ELECTRONICS LTD**  
MAGENTA ELECTRONICS LTD.  
PC12, 135 HUNTER ST., BURTON-ON-TRENT, STAFFS. DE14 2ST  
MAIL ORDER ONLY  
0283 65435. MON-FRI 9-5.  
ACCESS/BARCLAYCARD (VISA) BY PHONE OR POST.

ADD 45p P&P TO ALL ORDERS  
PRICES INCLUDE VAT.  
SAE ALL ENQUIRIES  
OFFICIAL SCHOOL ORDERS WELCOME OVERSEAS. Payment must be in sterling. IRISH REPUBLIC and BFPO - UK PRICES. EUROPE - UK PRICES + 10% ELSEWHERE - Write for Quote.

**OVERSEAS ORDERS**

Overseas readers are reminded that unless otherwise stated, postage and packing charges published in advertisements apply to the United Kingdom only.

Readers wishing to import goods from the United Kingdom are advised to first obtain from the advertiser(s) concerned an exact quotation of the cost of supplying their requirements carriage paid home.

**TALK TO THE WHOLE WORLD**

Study now for the **RADIO AMATEUR'S EXAMINATION**  
We have had 40 years successful experience in training men and women for the G.P.O. Transmitting licence.



FREE R.A.E. brochure without obligation from:-

**British National Radio & Electronics School**  
READING, BERKS. RG1 1BR

Name .....

Address .....

PE/8/817  
BLOCK CAPS PLEASE

# INDEX TO ADVERTISERS

A. D. Electronics .....	64
Audio Electronics .....	8
Beckmann .....	55
Bi-Pak .....	4
Blackstar Limited .....	65
Boss Industrial Mouldings .....	10
British National Radio & Electronics School .....	64 & 75
Centurion Alarms .....	75
Clef Products .....	8
Commquip .....	12
Cricklewood Electronics .....	11
Crofton .....	5
The C.R. Supply Co. ....	74
Electronic Mail Order .....	75
Electrovalue .....	8
G.C.H.Q. ....	12
Adam Hall Supplies Ltd .....	75
Hameg .....	10
House of Instruments .....	5
ICS Intertext .....	4
I.L.P. Electronics .....	6 & 7, 56
Magenta .....	75
Maplin Electronics .....	Cover IV
Marlborough Electronics .....	74
Martel .....	56
Micro State .....	74
Midwich .....	43
Modern Book Co. ....	12
Myers Electronics .....	74
Pantec (Carlo Gavazzi) .....	71
Parndon Electronics .....	64
Phonosonics .....	44
Powertran .....	Cover II
Proto Design .....	74
Radio & T.V. Components .....	44
Scientific Wire Co. ....	75
Sparkrite .....	9
Swanley .....	5
Tandy .....	14
Technomatic Ltd. ....	76 & Cover III
T.K. Electronics .....	63
Watford Electronics .....	2 & 3

# TECHNOMATIC LTD

## 01-452 1500 01-450 6597

### CONNECTOR SYSTEMS

I.D. CONNECTORS (Speedblock Type)			D-CONNECTORS 9 way 15 way 25 way 37 way				DIL HEADER PLUGS		RIBBON CABLE (Grey)	
No. of ways	Header Plug	Receptacle Conn	Solder	80p	105p	160p	250p	RS 232 Connectors Available from Stock	10 way	40p
10	90p	85p	Angled	150p	210p	250p	365p	Solder IDC type	14 way	60p
20	145p	125p	Solder	105p	160p	200p	335p	14 pin	16 way	60p
26	175p	150p	Angled	165p	215p	290p	440p	16 pin	20 way	85p
34	200p	160p	Hood	90p	85p	90p	100p	24 pin	26 way	120p
40	220p	190p	36 way	Centronix Type Conn. £5.50				24 pin	34 way	160p
50	235p	200p	25 way	1EEE Type Conn. £5.50				40 pin	40 way	180p
									50 way	200p
									64 way	280p

RS 232 JUMPERS (25 way D)			EURO CONNECTORS (Indirect Edge Conn.)			EDGE CONNECTORS	
24" Single end Male	£5.00		DIN STD	Plug	Skt	2x18 way	0.1" 0.156"
24" Single end Female	£5.25		41617 21 way	160p	165p	2x22 way	190p
24" Female-Female	£10.00		41617 31 way	170p	170p	2x23 way	175p
24" Male-Male	£9.50		41612 2x32 way	220p	275p	2x25 way	225p
24" Female-Male	£9.50		Angled 2x32 way	275p	320p	2x28 way	190p
			41612 3x32 way	260p	300p	1x43 way	260p
			Angled 3x32 way	375p	350p	2x43 way	395p
			2x32 way IDC a+c		525p	2x50 way	—
4 way 70p	8 way 90p	10 way 140p	(for 2x32 way specify a+b or a+c)			1x77 way	600p
6 way 85p						S100 Conn	— 600p

### ★ SPECIAL OFFER ★

1-24	25-99	1-24	25-99
2114L-450	80p	75p	2732
4164-2	450p	430p	4116-200
2716(+5V)	250p	225p	6116-150
2532	350p	335p	6522
		350p	335p
		80p	75p
		375p	350p
		310p	300p

### OFFICIAL BBC DEALER

BBC Model B £399 including VAT. (Carr. £8)

Model A to B upgrade kit £49.50

Installation charge £15

Individual upgrades and all mating connectors available.

### BBC DISC DRIVES

Disc Interface Kit £95 Installation £20  
BBC Single Drive 100K £235. BBC Dual Drive £799

### BBC COMPATIBLE DRIVES

Single 100K £180 200K £250 400K £330  
Dual 200K £350 400K £475 800K £590

Cable for Single Drive £8. Dual Drive £12.

(Carr. Single Drive £6, Dual Drive £8)

Disc Manual & Formatting Diskette £17.50

Diskettes: 40 track SS £15, 80 track SS £24. 80 track DS £32.

(Price for 10 carr. £2)

VIEW 16K WORD PROCESSOR ROM £52

TELETEXT RECEIVER £195.65 + £2 p&p

TORCH Z80 DISC PACK £780.00 + £2 p&p

WORDWISE 8K ROM £39 + £2 p&p

BUSINESS, EDUCATION AND FUN SOFTWARE IN STOCK

Please phone to confirm delivery details.

BOOKS (No VAT £1 p&p)

BASIC PROGRAMMING ON BBC £5.95

LET YOUR BBC TEACH YOU TO PROGRAM £6.95

BBC MICRO REVEALED £7.95

BBC MICRO AN EXPERT GUIDE £6.95

BBC COMPUTERS PLAY £6.95

ASSY LONG PROGRAM ON BBC £8.95

NEW FOR BBC

### PRINTERS

#### NEC PC 8023 BE

80 col 100 cps dot matrix printer. Bi-directional. Logic seeking, 2K buffer. Forward and Reverse line feed. Hi Res & Block Graphics, Proportional Spacing, International and Greek character sets, Auto underline, Friction/tractor selectable. £345 + £8 carr.

#### EPSON RX80 and EPSON FX80

RX80 100CPS 80 col Tractor Feed. FX80 160CPS 80 col F & T Feed. Logic seeking, Bi-directional, Bit Image Printing, 9 x 9 Matrix, Auto Underline. RX80 £298. FX80 £389

MX100 F/T3 £425

Carr. £8/Unit

#### SEIKOSHA GP100A & 250A

80 col. 30 cps dot matrix printer. High Res Graphics - Std & double with characters. £180 + £5 carr. GP250A £235 + £8 carr.

7400 11p	7401 11p	7402 11p	7403 12p	7404 12p	7405 15p	7406 15p	7407 15p	7408 14p	7409 14p	7410 14p	7411 14p	7412 14p	7413 16p	7414 18p	7415 18p	7416 18p	7417 18p	7418 18p	7419 18p	7420 14p	7421 18p	7422 18p	7423 18p	7424 18p	7425 18p	7426 18p	7427 18p	7428 18p	7429 18p	7430 18p	7431 18p	7432 18p	7433 22p	7434 22p	7435 22p	7436 22p	7437 22p	7438 22p	7439 22p	7440 15p	7441 55p	7442A 30p	7443 50p	7444A 50p	7445A 36p	7446 36p	7447 36p	7448 36p	7449 36p	7450 36p	7451 36p	7452 36p	7453 15p	7454 15p	7455 15p	7456 15p	7457 15p	7458 15p	7459 15p	7460 15p	7461 15p	7462 25p	7463 25p	7464 25p	7465 25p	7466 25p	7467 25p	7468 25p	7469 25p	7470 25p	7471 25p	7472 25p	7473 25p	7474 18p	7475 22p	7476 22p	7477 22p	7478 22p	7479 22p	7480 22p	7481 22p	7482 22p	7483 22p	7484 22p	7485 22p	7486 18p	7487 170p	7488 170p	7489 170p	7490A 20p	7491 35p	7492A 25p	7493A 36p	7494 35p	7495A 35p	7496 35p	7497 90p	7498 90p	7499 90p	7999 90p	8000 90p
----------	----------	----------	----------	-----------	----------	-----------	-----------	----------	----------	----------	----------	-----------	-----------	-----------	-----------	----------	-----------	-----------	----------	-----------	----------	----------	----------	----------	----------


# COMPUTER COMPONENTS

8002CE	850p	CR15027	£18	INTERFACE ICs	775p	CRYSTALS	100p
2650A	£12	CR15037	£18	AD588CJ	£20	32 768KHz	100p
6502	350p	CR15047	£18	AD589C	£20	100KHz	250p
6502A	150p	CR15057	£18	AM25510	350p	200KHz	250p
6800	225p	CR15067	£18	AM25L5251	£25	1.0MHz	250p
6802	225p	CR15077	£18	AM26L531	125p	3.27MHz	250p
6805	225p	CR15087	£18	AM26L532	125p	1.8432MHz	210p
6809E	£12	CR15097	£18	AM26L533	125p	2.0MHz	225p
6809E	£12	CR15107	£18	AM26L534	125p	2.4576MHz	210p
6809E	£12	CR15117	£18	AM26L535	125p	2.5MHz	250p
6809E	£12	CR15127	£18	AM26L536	125p	2.662MHz	250p
6809E	£12	CR15137	£18	AM26L537	125p	2.822MHz	250p
6809E	£12	CR15147	£18	AM26L538	125p	3.5795MHz	100p
6809E	£12	CR15157	£18	AM26L539	125p	3.686MHz	300p
6809E	£12	CR15167	£18	AM26L540	125p	4.00MHz	300p
6809E	£12	CR15177	£18	AM26L541	125p	4.194MHz	200p
6809E	£12	CR15187	£18	AM26L542	125p	4.43MHz	110p
6809E	£12	CR15197	£18	AM26L543	125p	4.608MHz	250p
6809E	£12	CR15207	£18	AM26L544	125p	5.00MHz	175p
6809E	£12	CR15217	£18	AM26L545	125p	6.00MHz	150p
6809E	£12	CR15227	£18	AM26L546	125p	6.144MHz	150p
6809E	£12	CR15237	£18	AM26L547	125p	7.00MHz	150p
6809E	£12	CR15247	£18	AM26L548	125p	7.168MHz	175p
6809E	£12	CR15257	£18	AM26L549	125p	8.00MHz	175p
6809E	£12	CR15267	£18	AM26L550	125p	8.268MHz	175p
6809E	£12	CR15277	£18	AM26L551	125p	10.00MHz	175p
6809E	£12	CR15287	£18	AM26L552	125p	10.50MHz	150p
6809E	£12	CR15297	£18	AM26L553	125p	12.00MHz	175p
6809E	£12	CR15307	£18	AM26L554	125p	14.318MHz	150p
6809E	£12	CR15317	£18	AM26L555	125p	14.756MHz	250p
6809E	£12	CR15327	£18	AM26L556	125p	20.00MHz	200p
6809E	£12	CR15337	£18	AM26L557	125p	16.00MHz	200p
6809E	£12	CR15347	£18	AM26L558	125p	17.7MHz	200p
6809E	£12	CR15357	£18	AM26L559	125p	18.00MHz	200p
6809E	£12	CR15367	£18	AM26L560	125p	19.832MHz	150p
6809E	£12	CR15377	£18	AM26L561	125p	19.968MHz	150p
6809E	£12	CR15387	£18	AM26L562	125p	20.00MHz	200p
6809E	£12	CR15397	£18	AM26L563	125p	27.145MHz	150p
6809E	£12	CR15407	£18	AM26L564	125p	36.667MHz	175p
6809E	£12	CR15417	£18	AM26L565	125p	48.0MHz	175p
6809E	£12	CR15427	£18	AM26L566	125p	55.5MHz	400p
6809E	£12	CR15437	£				

Send now for an application form — then buy it with MAPCARD.

MAPCARD gives you real spending power — up to 24 times your monthly payments — instantly!

# Maplin News

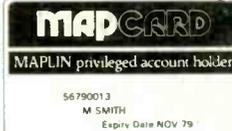

## Sole UK Agents for Heathkit

NOW THE world-famous Heathkit range of superb electronic kits is available from Maplin — the newly appointed exclusive UK distributor. Kits range from a simple clock for beginners to a unique Robot (see pic) with which you can learn about robotics.

There is a range of training courses covering electronics and computing topics, many containing constructional projects. For full details, pick up a copy of the latest Maplin magazine or write for a free copy of our Heathkit catalogue. Order As XH62S.



## GREAT PROJECTS FROM E&MM



OUR NEW book "Best of E&MM Projects Vol. 1" brings together 21 fascinating and novel projects from E&MM's first year.

Projects include Harmony Generator, Guitar Tuner, Hexadrum, Syntom, Auto Swell, Partylite, Car Aerial Booster, MOS-FET Amp and other musical, hi-fi and car projects. ORDER AS XH61R. PRICE £1.

## Computer Shopping Arrives

AS FROM June 1st you can place orders directly with our computer from your personal computer. The computer shopping revolution has arrived! To communicate, you'll need a modem (our RS232 compatible modem kit is LW99H price £39.95) and an interface (our ZX81 interface LK08J price £24.95 is available already with many more for most popular micros coming soon).

Just dial us up on 0702 552941 and you'll be able to interrogate our stock file then place your order, type in your credit card number and a few minutes after you hang up your order will print out in our warehouse ready for packing. And all without saying a word.

Try out the future way of shopping now! You'll see immediately what stock we've got available and you'll discover how easy it is to ensure your order is exactly right. And you'll see precisely what the current price is for each item and what total amount will be charged to your credit card. It all helps to make buying easier. So give us a ring now!

## Maplin's Fantastic Projects

FULL DETAILS in our project books. Price 70p each.

In Book 1 (XA01B) 120W rms MOSFET Combo-Amplifier • Universal Timer with 18 program times and 4 outputs • Temperature Gauge • Six Vero Projects.

In Book 2 (XA02C) Home Security System • Train Controller for 14 trains on one circuit • Stopwatch with multiple modes • Miles-per-Gallon Meter.

In Book 3 (XA03D) ZX81 Keyboard with electronics • Stereo 25W MOSFET Amplifier • Doppler Radar Intruder Detector • Remote Control for Train Controller.

In Book 4 (XA04E) Telephone Exchange for 16 extensions • Frequency Counter 10Hz to



600MHz • Ultrasonic Intruder Detector • I/O Port for ZX81 • Car Burglar Alarm • Remote Control for 25W Stereo Amp.

In Book 5 (XA05F) Modem to European standard • 100W 240V AC Inverter • Sounds Generator for ZX81 • Central Heating

Controller • Panic Button for Home Security System • Model Train Projects • Timer for External Sounder.

In Book 6 (XA06G) Speech Synthesiser for ZX81 & VIC 20 • Module to Bridge two of our MOSFET Amps to make a 350W Amp • ZX81 Sound on your TV • Scratch Filter • Damp Meter • Four Simple Projects.

In Book 7 (XA07H) Modem Interface for ZX81/VIC20 • Digital Enlarger Timer/Controller • DXers Audio Processor • Sweep Oscillator • CMOS Crystal Calibrator.

## 25W Stereo MOSFET Amplifier



- Over 26W/channel into 8Ω at 1kHz both channels driven.
- Frequency response 20Hz to 40kHz ± 1dB.
- Low distortion, low noise and high reliability power MOSFET output stage.
- Extremely easy to build. Almost everything fits on main pcb, cutting interwiring to just 7

wires (plus toroidal transformer and mains lead terminations). • Complete kit contains everything you need including pre-drilled and printed chassis and wooden cabinet.

Full details in Projects Book 3. Price 70p (XA03D). Complete kit only £55.20 incl. VAT and carriage (LW71N).

## MATINEE ORGAN

EASY-TO-BUILD, superb specification. Comparable with organs selling for up to £1000.

Full construction details in our book (XH55K). Price £2.50. Complete kits available. Electronics (XY91Y) £299.95\*. Cabinet (XY93B) £99.50\*. Demo cassette (XX43W) £1.99. \*Carriage extra



## Maplin's New 1983 Catalogue

Over 390 pages packed with data and pictures and all completely revised and including over 1000 new items.

On sale in all branches of WH SMITH. Price £1.25.



### POST THIS COUPON NOW!

Please send me a copy of your 1983 catalogue. I enclose £1.50 (inc. P&P). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the UK send £1.90 or 10 International Reply Coupons. Despatch by return of post where goods available.

Name .....

Address .....

Post Code .....

PE 883

MAPLIN ELECTRONIC SUPPLIES LIMITED, P.O. Box 3, Rayleigh, Essex SS6 8LR. Telephone: Sales (0702) 552911 General (0702) 554155.

Shops at: 159 King St., Hammersmith, London W6. Tel: 01-748 0926. 284 London Rd., Westcliff-on-Sea, Essex. Tel: (0702) 554000. Lynton Square, Perry Barr, Birmingham. Tel: (021) 356 7292.

Shops closed Mondays. All prices include VAT & carriage. Please add 50p handling charge to orders under £5 total value.

809