

**PRACTICAL**

**OCTOBER 1984 · 90p**

# ELECTRONICS

**ROBOTICS · MICROS · ELECTRONICS · INTERFACING**

*New Series...*

## SEQUENTIAL LOGIC TECHNIQUES

**COUNTERS, TIMERS  
AND MEMORIES**



**RADAR SECURITY ALARM**

**FILTER SHIFT PHASER**

**Disc Drive Buyer's Guide**

## SOLDER

Recommended for general purpose, fine work and pcb's, a top quality flux-coated 60% tin, 40% lead solder. 22swg. **ONLY 82p for 10 metres (FR21X)**

MAPLIN PRICE RIGHT!  
**82p**



MAPLIN PRICE RIGHT!  
**£9.95**

MAPLIN PRICE RIGHT!  
**£1.95**



## DATA CASSETTES & FLOPPY DISKS

Pack of 5 good quality C12 cassettes. **ONLY £1.95 (BK95D)**


Pack of 10 top quality 5¼in floppy disks single-sided, single or dual density. **ONLY £17.95 (YJ00A)**



MAPLIN PRICE RIGHT!  
**£17.95**
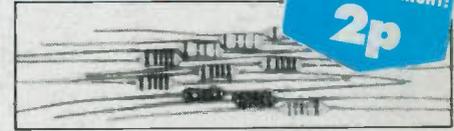
## VIDEO COPYING KIT

Copy video tapes to and from virtually any VHS or Beta machine. Kit makes six different video and six different audio leads. **ONLY £9.95 (RK71N)**



MAPLIN PRICE RIGHT!  
**2p**

## RELAYS

Sub-miniature 12V relays will switch up to 10A at 240V AC.

	Coil voltage	Coil resistance	Contact ratings DC current	Contact ratings AC Current (resistive)	Size (mm)
Single-pole changeover	8.4 to 15.6V	400Ω	up to 10A at 30V	up to 10A at 240V	21×16×14
Double-pole changeover	8.4 to 13.2V	270Ω	up to 5A at 30V	up to 5A at 240V	29×20×13

Relays are fully enclosed and direct pcb mounting.

**INCREDIBLY LOW PRICE £1.65 each**

(SINGLE-POLE YX97F)

(DOUBLE-POLE YX98G)



MAPLIN PRICE RIGHT!  
**£1.65**

## RESISTORS

Far superior to carbon film, these superb quality, very high stability, exceptionally low noise resistors have a ±1% tolerance and are rated 0.4W at 70°C yet are only 6.5mm long and 2.5mm diameter nominal. E24 range 10Ω to 1M. **EXCEPTIONALLY LOW PRICE 2p each (M+VALUE)**

# COMPARE OUR PRICES... then choose MAPLIN for Quality and Service as well!

Well over £1½ million worth of top quality electronic components always in stock

## D-CONNECTORS

Gold over nickel plated contacts and solder terminations. Thermoplastic cover allows side or top entry and includes cable clamp.

## SUPERB QUALITY AND AMAZINGLY LOW PRICES

	Plug	Socket	Cover
9-way	<b>68p</b> (RK60Q)	<b>95p</b> (RK61R)	<b>£1.14</b> (RK62S)
15-way	<b>95p</b> (BK58N)	<b>£1.43</b> (BK59P)	<b>99p</b> (BK60Q)
25-way	<b>£1.39</b> (YQ48C)	<b>£2.19</b> (YQ49D)	<b>£1.14</b> (YQ50E)

## COMPARING OUR PRICES

When you compare our prices, remember that many of our competitors quote VAT exclusive prices. This hidden extra makes a big difference to their seemingly low prices.

On an order as little as £6.67, the VAT is a whole £1 extra!

## TELEPHONE CONNECTORS

Three examples from our range of telephone fittings. All are BT approved and sockets are shuttered.

Flush fitting jack socket for main telephone. **ONLY £3.99 (FJ27E)**

Flush fitting jack socket for extension telephones. **ONLY £2.65 (FT34N)**

Line cord, 3m long, spade terminals to phone plug. **ONLY £1.95 (FG29G)**



MAPLIN PRICE RIGHT!  
from **68p**



MAPLIN PRICE RIGHT!  
from **£2.65**

MAPLIN PRICE RIGHT!  
**£1.95**



## SHOPS ONLY

PRESENT THIS COUPON IN ONE OF OUR SHOPS AND WE'LL KNOCK 5% OFF ANY ONE COMPLETE ORDER VALID UNTIL 29th SEPTEMBER 1984

## SHOPS ONLY

PE10

N.B. All our prices INCLUDE VAT and Carriage. A 50p handling charge must be added if your total order is less than £5 on mail-order.

## MAPLIN ELECTRONIC SUPPLIES LTD.

Mail Order: P.O. Box 3, Rayleigh, Essex SS6 8LR. Tel: Southend (0702) 552911. SHOPS

- BIRMINGHAM Lynton Square, Perry Barr, Tel: 021-356-7292.
  - LONDON 159-161 King Street, Hammersmith, W6. Tel: 01-748-0926.
  - MANCHESTER 8 Oxford Road, Tel: 061-236-0281.
  - SOUTHAMPTON 46-48 Bevois Valley Road, Tel: 0703 25831.
  - SOUTHEND 282-284 London Road, Westcliff-on-sea, Essex. Tel: 0702 554000.
- Shops closed all day Monday. Despatch by return of post where goods available.



# neptune



## for low-cost training in real-life robotics

The advanced design of the Neptune 2 makes it the lowest cost real-life industrial robot.

It is electro-hydraulically powered, using a revolutionary water based system (no messy hydraulic oil!)


It performs 7 servo-controlled axis movements (6 on Neptune 1) – more than any other robot under £10,000.

Its program length is limited only by the memory of your computer. Think what that can do for your BASIC programming skills!

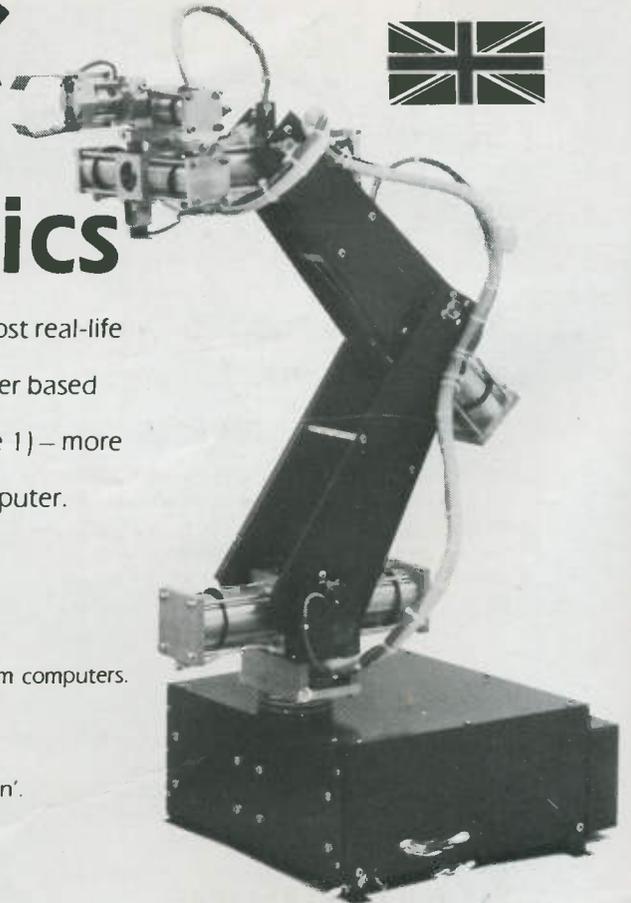**And it's British designed, British made.**

Other features include:

- Leakproof, frictionless rolling diaphragm seals.
- Buffered and latched versatile interface for BBC VIC 20 and Spectrum computers.
- 12 bit control system (8 on Neptune 1).
- Special circuitry for initial compensation.
- Rack and pinion cylinder couplings for wide angular movements.
- Automatic triple speed control on Neptune 2 for accurate 'homing in'.
- Easy access for servicing and viewing of working parts.
- Powerful – lifts 2.5 kg. with ease.
- Hand held simulator for processing (requires ADC option).



Neptune robots are sold in kit form as follows:

Neptune 1 robot kit (inc. power supply)	£1250.00	ADC option (components fit to main control board)	£95.00
Neptune 1 control electronics (ready built)	£295.00	Hydraulic power pack (ready assembled)	£435.00
Neptune 1 simulator	£45.00	Gripper sensor	£37.50
		Optional extra three fingered gripper	£75.00
Neptune 2 robot kit (inc. power supply)	£1725.00	BBC connector lead	£12.50
Neptune 2 control electronics (ready built)	£475.00	Commodore VIC 20 connector lead and plug-in board	£14.50
Neptune 2 simulator	£52.00	Sinclair ZX Spectrum connector lead	£15.00

**All prices exclusive of VAT and valid until the end of 1984.**


## mentor desk-top robot

This compact, electrically powered training robot has 6 axes of movement, simultaneously servo-controlled. It gives smooth operation, and its rugged construction makes it ideal for use in educational establishments. Other features include long-life bronze and nylon bearings, integral control electronics and power supply, special circuitry for inertial compensation, optional on-board ADC, and hand-held simulator as the teaching pendant. Like Neptune, Mentor's program length is limited only by your computer's memory. Programming is in BASIC.

Mentor is all-British in design and manufacture and comes in kit form at an astonishingly low price:

Mentor robot kit (inc. power supply)	£345.00
Mentor Control electronics (ready built)	£135.00
Mentor Simulator (requires ADC option)	£42.00
ADC option (Components fit to control electronics board)	£19.50
BBC connector lead	£12.50
Commodore VIC 20 connector lead and plug-in board	£14.50
Sinclair ZX Spectrum connector lead	£15.00

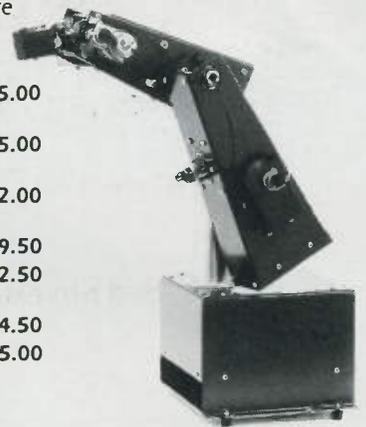**All prices exclusive of VAT and valid until the end of 1984.**



## CYBERNETIC APPLICATIONS LIMITED

PORTWAY TRADING ESTATE, ANDOVER, HANTS SP10 3PR  
TEL: (0264) 50093 Telex: 477019

# PRACTICAL ELECTRONICS

VOLUME 20

No. 10

OCTOBER 1984

## CONSTRUCTIONAL PROJECTS

<b>FILTER SHIFT PHASER</b> by John M. H. Becker .. .. .	10
Add a new phase to your music	
<b>RADAR SECURITY ALARM</b> by Powertran Cybernetics .. .. .	30
Four-channel doppler radar security alarm	
<b>NEPTUNE ROBOTS</b> by Richard Becker and Tim Orr .. .. .	38
Part Two: Central electronics and computer interfacing	
<b>PULSE DIRECTION LOGIC PROBE</b> by S. A. Withey .. .. .	52
Detects input/output logic levels plus high-speed pulse direction	
<b>OPTO-LOCK</b> by Tom Gaskell BA (Hons) CEng MIEE .. .. .	56
Security lock using infra-red	

## GENERAL FEATURES

<b>SEQUENTIAL LOGIC TECHNIQUES</b> .. .. .	16
Part One: Introduction and counters	
<b>DISC DRIVES EXPLAINED</b> by M. Tooley BA and D. Whitfield MA MSc CEng MIEE .. .. .	20
Part Two: What to look for and a Buyer's Guide	
<b>MICRO-BUS</b> .. .. .	29
Focus on micro's for the home constructor	
<b>VERNON TRENT AT LARGE</b> .. .. .	51
<b>SEMICONDUCTOR CIRCUITS</b> by Tom Gaskell BA(Hons) CEng MIEE .. .. .	54
Encoder/decoder (MM53200N)	
<b>INGENUITY UNLIMITED</b> .. .. .	58
Readers' circuit ideas	

## NEWS AND COMMENT

<b>EDITORIAL</b> .. .. .	7
<b>NEWS AND MARKET PLACE</b> .. .. .	8
Including Countdown and Points Arising	
<b>INDUSTRY NOTEBOOK</b> by Nexus .. .. .	36
News and views on the electronics industry	
<b>READOUT</b> .. .. .	46
Readers express their opinions	
<b>SPACEWATCH</b> by Dr. Patrick Moore O.B.E. .. .. .	49
Other Solar Systems?; Invisible Bodies; Search for ET; Sky This Month	
<b>BAZAAR</b> .. .. .	50
Free readers' advertisements	

OUR NOVEMBER ISSUE WILL BE ON SALE FRIDAY, OCTOBER 5th, 1984  
(for details of contents see page 37)

© IPC Magazines Limited 1984. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.



<b>SPEAKERS</b> 811, 0.3W, 2", 2.25", 2.5" 3" 0.3W, 2.5" 401i, 641i or 801i		<b>OPTO</b> LEDs price includes Clips TIL208 Red 3mm 10 TIL211 Green 3mm 14 TIL212 Yellow 14 TIL220 2" Red 12 0.2" Vcl, Gm, Amber Rectangular LEDs with two part dip. R, G & Y 45 Rectangl. Stackable LEDs 18 Triangular LEDs R&G 18 0.2" Flashing LED Red 56 0.2" Bi colour LEDs Red/Green 100 Green/Yellow 80 0.2" Tri colour LEDs Red/Green/Yellow 85 Pin diode High Bright Green or Yellow 59 LD771 Infra Red (emit) 46 TIL32 Infra Red (emit) 52 SFH205 (detector) 118 TIL78 (detector) 55 TIL38 50 TIL81 82; TIL100 90		<b>0.5" LCD DISPLAYS</b> 13 digit 495 14 digit 530 16 digit 620 18 digit 725 20 digit 825 24 digit 925 100mA T092 Plastic Casing 5V 7805 50p 7905 50p 12V 7812 45p 7912 50p 15V 7815 45p 7915 50p 24V 7824 45p 7918 50p 100mA T092 Plastic Casing 5V 7805 30p 7905 50p 6V 7812 30p 7912 50p 8V 7818 30p 7918 50p 12V 7824 30p 7924 50p 15V 7830 30p 7930 50p		<b>VOLTAGE REGULATORS</b> 1A T0220 Plastic Casing +ve -ve 5V 7805 50p 7905 50p 12V 7812 45p 7912 50p 15V 7815 45p 7915 50p 24V 7824 45p 7918 50p 100mA T092 Plastic Casing 5V 7805 30p 7905 50p 6V 7812 30p 7912 50p 8V 7818 30p 7918 50p 12V 7824 30p 7924 50p 15V 7830 30p 7930 50p		<b>DIL SOCKETS</b> Low profile Wire wrap 8 pin 8p 25p 14 pin 14p 35p 16 pin 16p 42p 18 pin 18p 52p 20 pin 20p 60p 22 pin 22p 65p 24 pin 24p 70p 28 pin 28p 80p 40 pin 38p 99p		<b>SPECTRUM 32K UPGRADE</b> Upgrade your 16K Spectrum to full 48K with our RAM Upgrade Kit. Very simple to fit. Fitting instructions supplied. <b>ONLY £20</b>			
<b>DIODES</b> AA119 15 AA129 20 AA330 15 BA100 15 BAX13 20 BY126 24 BY127 24 CRO33 250 OA9 40 OA70 12 OA79 15 OA81 20 OA85 15 OA90 8 OA91 8 OA95 8 OA200 8 OA202 8 IN914 8 IN916 5 IN4001/2 5 IN4003 6 IN4004/5 6 IN4006/7 7 IN4148 4 IN5401 15 IN5404 16 IN5406 17 IN5408 19 IS44 9 IS921 9 6A/100V 40 6A/400V 50 6A/800V 65		<b>BRIDGE RECTIFIERS</b> (plastic case) 1A/50V 18 1A/100V 20 2A/50V 25 2A/100V 34 2A/200V 39 2A/400V 46 2A/600V 55 6A/100V 65 6A/200V 85 6A/400V 125 10A/200V 215 10A/300V 298 25A/200V 240 25A/300V 395 VM164 56 BY118 50		<b>OPTO SWITCH</b> Reflective TIL139 225 Slotted similar 188 7 Segment Displays TIL321 5" C An 140 TIL322 5" C Ch 140 DL704 3" C Ch 125 DL707 3" C An 125 FND357 or 500 130 3" Red C.A. 140 +1 3" Red or Green Bargraph 10 seg Red Bargraph NSM3914 500		<b>ALUM. BOXES</b> 4x2x2" 103 4x2x2 1/2" 103 4x4x2 1/2" 105 5x4x2 1/2" 120 5x2x1 1/2" 90 5x2x1 1/2" 90 5x4x1 1/2" 99 6x4x1 1/2" 120 6x4x3 1/2" 150 7x5x3 1/2" 180 8x6x3 1/2" 210 10x4x3 1/2" 240 12x5x3 1/2" 260 12x8x3 1/2" 295		<b>SLIDE SWITCH</b> 1A DPDT 15 1A DPDT C/OFF 14 1A DP on/on/on 40 TOGGLE 2A 250V 35 1A DPDT 48 1A DPDT C/OFF 48 1A DP on/on/on 54		<b>DIL PLUGS (Headers)</b> Pins Solder IDC 14 38p 95p 16 42p 100p 24 88p 138p 28 185p 290p 40 195p 218p		<b>IDC CONNECTORS</b> (Speed block type) PCB Male with latch 2 rows Strt Pins Angle 10 way 90p 95p 85p 120p 16 way 130p 150p 110p 195p 20 way 145p 166p 125p 240p 26 way 175p 200p 150p 320p 34 way 205p 236p 189p 340p 40 way 220p 250p 200p 420p 50 way 235p 270p 200p 470p	
<b>ZENERS</b> Range 2V7 to 39V 400mW 8p each Range 3V3 to 33V 1.3W 15p each		<b>VARICAPS</b> MVAM2 165 BA102 30 BB105B 40 BB106 40		<b>FERRIC CHLORIDE</b> Crystals 1lb 195p + 50p p&p		<b>DALE ETCH RESIST</b> Pen plus spare tip 100p		<b>ROTARY: (Adjustable Stop Type)</b> 1 pole/2 to 12 way, 2p/2 to 6 way, 3 pole/2 to 4 way, 4 pole/2 to 3 way 48p		<b>'D' CONNECTORS:</b> Pins 9 15 25 37 way way way way		<b>TRANSFORMERS</b> (mains Prim. 220-240V) 3-0-3V, 6-0-6V 100mA; 9-0-9V 75mA; 12-0-12V 75mA, 15-0-15V 75mA; 6VA; 2x6V-5A; 2x9V-4A; 2x12V-0.3A; 2x15V-25A 250p 12VA; 2x4V5-1.3A; 2x6V-1.2A; 2x12V-0.5A; 2x15V-0.4A 345p (35p p&p) 24VA; 6V-1.5A 6V-1.5A; 9V-1.2A 9V-1.2A; 12V-1A 12V-1A; 15-8A 15-8A; 20V-6A 20V-6A 385p (60p p&p) 50VA; 2x6V-4A; 2x9V-2.5A; 2x12V-2A; 2x15V-1.5A; 2x20V-1.2A; 2x25V-2A; 2x30V-0.8A 520p (60p p&p) 100VA; 2x12V-4A; 2x15V-3A; 2x20V-2.5A; 2x30V-1.5A; 2x40V-1.25A; 2x50V-1A 965p (60p p&p)	
<b>TRIACS</b> 3A/100V 48 3A/400V 56 3A/800V 85 6A/100V 60 6A/400V 69 8A/300V 115 12A/100V 78 12A/400V 82 12A/800V 95 16A/100V 103 16A/400V 105 16A/800V 220 25A/400V 185 25A/800V 295 35A/100V 480 30A/400V 525 T2800D 125		<b>COPPER CLAD BOARDS</b> Fibre Single Double Glass sided sided 6" x 6" 100p 110p 6" x 12" 175p 225p		<b>PUSH BUTTON</b> Spring loaded Latching or Momentary 6A SPDT c/over 150 DPDT c/over 200 SP changeover 64 SPST on off 55 SPST c/off 85 SPDT Biased 105 DPDT 6 tags 80 DPDT C/OFF 98		<b>ROTARY:</b> 1 pole/2 to 12 way, 2p/2 to 6 way, 3 pole/2 to 4 way, 4 pole/2 to 3 way 48p		<b>MALE</b> Solder 80p 110p 160p 240p Angle 150p 210p 250p 350p Strait 170p 160p 220p 310p		<b>EDGE CONNECTORS</b> 1" 20 pin 40 pin 2x18 way 210p 2x22 way 215p 2x23 way 175p 2x25 way 285p 2x28 way 190p 2x30 way 310p 2x36 way 360p 2x40 way 380p 2x43 way 450p 2x75 way 650p			
<b>SCR's</b> Thyristors 0.8A-100V 32 5A/300V 38 5A/400V 40 5A/600V 48 8A/300V 60 8A/600V 95 12A/100V 78 12A/400V 82 12A/800V 95 16A/100V 103 16A/400V 105 16A/800V 220 25A/400V 185 25A/800V 295 35A/100V 480 30A/400V 525 T2800D 125		<b>VEROBOARDS</b> 0-1" Clad Plain VCI Board 2 1/2 x 3 1/2 95 - DIP Board 180 2 1/2 x 5 1/2 110 - Vero Strip 144 3 1/2 x 3 1/2 110 - 395 3 1/2 x 5 1/2 125 95p 3 1/2 x 7 1/2 420 275p 4 1/2 x 11 1/2 590 - S-Dec 480 Pkt. of 100 pins 55p Spot Face Cutter 150p Pin Insertion Tool 185p Eurobreadboard 395 Bimboard 1 695 Superstrip SS2 113		<b>ROTARY:</b> 1 pole/2 to 12 way, 2p/2 to 6 way, 3 pole/2 to 4 way, 4 pole/2 to 3 way 48p		<b>FEMALE</b> Solder 105p 160p 200p 338p Angle 165p 215p 290p 400p Strait 175p 200p 300p 420p		<b>JUMPER LEADS</b> Ribbon Cable Assembly DIL Plug (Headers) Single Ended Lead 24" long Length 14pin 16pin 24pin 40pin 24" 145p 165p 240p 325p Double Ended Leads 6" 185p 205p 300p 465p 12" 198p 215p 315p 490p 24" 210p 235p 345p 540p 36" 230p 250p 375p 595p					
<b>DIAC</b> ST2 25 100 75p 500 370p		<b>SOLDERCON PINS</b> Spare Wire (Spool) 75p; Wire Wrapping Stakes 100		<b>VERO WIRING PEN and Spool</b> Spare Wire (Spool) 75p; Wire Wrapping Stakes 100		<b>AMPHENOL CONNECTORS</b> 36 way IEEE 475p 470p 24 way Centronix 525p 475p 24 way Female 490p 450p		<b>COVERS</b> 80p 75p 75p 90p IDC 25 way Plg. 385p, Skt. 450p		<b>SIL SOCKETS</b> 0.1" 20 pin 40 pin 2x18 way 210p 2x22 way 215p 2x23 way 175p 2x25 way 285p 2x28 way 190p 2x30 way 310p 2x36 way 360p 2x40 way 380p 2x43 way 450p 2x75 way 650p			

### COMPUTER CORNER

- **SEIKOSHA GP100A** - Unihammer Printer, normal & double width characters, dot resolution graphics 10" Tractor feed, parallel interface standard. **£138**
- **SEIKOSHA GP 250X** Printer **£175**
- **EPSON FX80 PRINTER** 160 CPS, 11x9 matrix, proportional spacing, superscript, subscript, dot addressable graphics, Normal, Italic & Elite characters. Up to 256 user definable characters. Down loadable character set. Condensed and double width printing. 4 user defined margin positions. Tractor and Friction feed. 10" maximum width, Bi-directional, logic seeking. Centronix Interface standard. **£319**
- **EPSON RX80 PRINTER** **£229**
- **EPSON RX80 FT PRINTER** **£245**
- **KAGA - RGB** 12 inch medium resolution colour monitors **£174**
- **ZENITH 12" Hi-RES**, Green Monitor 40/80 column select switch, value for money. **£75**
- **MICROVITEC 14"** colour monitor. RGB input. Lead incl. **£173**
- **MICROVITEC 1451** Hi-res 14" Monitor incl. Lead **£295**
- **TEX EPROM ERASER**. Erases up to 32 ICs in 15-30 min. **£30**
- **Spare 'UV lamp bulbs** **£9**
- **C12 COMPUTER Grade BASF Cassettes** in Library Cases **36p**
- **8 1/2" or 9 1/2" Fan fold paper** (1000 sheets) **£7 (150p)**
- **Teleprinter Roll** (ho VAT) **£3.50**

MANY MORE PRINTERS, MONITORS, INTERFACES, AVAILABLE. CALL IN AT OUR SHOP FOR DEMONSTRATION OR WRITE IN FOR OUR DESCRIPTIVE LEAFLET.

### BROTHER HR-15 DAISY-WHEEL PRINTER

An exceptionally high quality Daisy Wheel printer at the price of a standard Dot matrix printer. 18CPS; bi-directional; 3K Buffer; proportional spacing; underlining; bold print; prints in black & red; superscript & subscript; facility to vary pressure for carbon copies; Centronics & RS232 interfaces as standard. Optional extras: Single sheet feeder; sophisticated electronic typewriter keyboard; beige colour.

**Only £349 (Carr. £7)**

### SPECTRUM CENTRONICS/RS232 PRINTER INTERFACE

★ It was the first!  
It is still the best!

★ Centronics and BI-DIRECTIONAL RS-232 with full hand-shaking.

★ Obeyes SPECTRUM LLIST and LPRINT.

★ Split-Speed Operation for RS-232. (Use it to communicate with the BBC MICRO or OTHER PERIPHERALS).

★ Interface 1, Interface 2 & Microdrive compatible.

★ Configuration program creates customised M/C driver to suit your printer.

★ HI-RES screen dumps in 2 sizes on EPSON, SEIKOSHA, STAR, SHINWA, MANNESMAN TALLY, NEC, RITEMAN, KAGA, etc. This is a STANDARD FEATURE! Not an extra.

★ Compatible with TASWORD 2.0 and most professional programs.

Price: **£29.95 (Carr. £1)**  
Centronics Cable £7

### CRYSTALS

32.768KHz	100
100KHz	545
200KHz	370
455KHz	275
1MHz	275
1.008M	370
1.28MHz	450
1.5MHz	420
1.6MHz	395
1.8MHz	545
1.8432M	250
2.0MHz	225
2.4576M	225
2.5MHz	225
2.56250M	225
3.2768M	150
3.57954M	150
3.6864M	300
4.0MHz	150
4.032MHz	250
4.194304M	100
4.194304M	100
4.43519M	200
4.608MHz	200
4.80MHz	160
5.0MHz	200
5.185MHz	300
5.24288M	300
6.0MHz	140
6.144MHz	150
6.5536MHz	200
7.0MHz	150
7.168MHz	150
7.68MHz	200
8.0MHz	150
8.0833M	395
8.867237M	200
9.00MHz	200
9.375MHz	360
10.0MHz	175
10.5MHz	150
10.7MHz	200
10.24MHz	200
12.0MHz	175
12.528MHz	300
14.31818M	175
14.7456M	170
14.765MHz	250
15.0MHz	240
16.0MHz	220
18.0MHz	180
18.432M	150
19.968MHz	200
20.0MHz	150
24.0MHz	170
24.930MHz	325
29.695MHz	150
26.670MHz	325
27.125MHz	295
27.145MHz	190
27.648MHz	300
38.86667M	240
48.0MHz	240
55.5MHz	400
100MHz	295
116.0MHz	300
145.8MHz	225

### BBC MICROCOMPUTER

Model B **£326**. Price includes FREE Data Recorder and 5 Games software worth **£80**. We stock the full range of BBC Micro peripherals, Hardware & Software like, Disc Drives (Top quality Cumana & Mitsubishi), Diskettes, Printers, Printer Paper, Interface Cable, Dust Covers, Cassette Recorder & Cassettes, Monitors, Connectors (Ready made Cables, Plugs & Sockets), Plotter (Graphic Tablet) EPROM Programmer, Lightpen Kit, Joysticks, Sideways ROM Board, EPROM Eraser, Machinecode ROM. The highly sophisticated Watford's 16K BEEB DFS, WORDWISE, BEEBCALC, Software (Educational Application & Games), BOOKS, etc. etc. Please send SAE for our descriptive leaflet.

### DISC DRIVES FOR BBC MICRO

- **CS100 - TEAC** Cased with own Power Supply, S/S, 40 track, 5 1/4", 100K **£129**
- **CD200 - TEAC** Twin Cased with own PSU, S/S, 40 track, 5 1/4", 200K **£255**
- **CS200 - TEAC** Single Cased with own PSU, S/S, 80 track, 5 1/4", 200K **£175**
- **CD400 - TEAC** Twin Cased with own PSU, S/S, 80 track, 5 1/4", 400K **£365**
- **MITSUBISHI 5 1/4"** Slim line Disc Drives double sided, double density, track density 96 TPI, track to track access time 3msec.
- **SINGLE MITSUBISHI** Slim line - Cased with own PSU, DS/DD, 1 Megabytes (400K with BBC) **£199**
- **TWIN MITSUBISHI** Slim line - Cased with own PSU, DS/DD, 2 Megabytes (800K with BBC) **£395**
- Single Drive Cable for BBC Micro **£7**
- Twin Drive Cable for BBC Micro **£10**

**Many more types available.**  
Please send SAE for our detailed leaflet.  
N.B. Carriage is extra on drives.

## WATFORD ELECTRONICS

Tel. (0923) 40588 Telex. 8956095

# FREE CAREER BOOKLET

**Train for success in Electronics Engineering, T.V. Servicing, Electrical Engineering—or running your own business!**

ICS have helped thousands of ambitious people to move up into higher paid, more secure jobs in the fields of electronics, T.V., electrical engineering—now it can be your turn. Whether you are a newcomer to the field or already working in these industries, ICS can provide you with the specialised training so essential to success.

## Personal Tuition and 80 Years of Success

The expert and personal guidance by fully qualified tutors, backed by the long ICS record of success, is the key to our outstanding performance in the technical field. You study at the time and pace that suits you best and in your own home.

You study the subjects you enjoy, receive a formal Diploma, and you're ready for that better job, better pay.

**TICK THE FREE BOOKLET YOU WANT AND POST TODAY**

### ELECTRONICS ENGINEERING

A Diploma Course, recognised by the Institute of Engineers & Technicians as meeting all academic standards for application as an Associate.

### T.V. & AUDIO SERVICING

A Diploma Course, training you in all aspects of installing, maintaining and repairing T.V. and Audio equipment, domestic and industrial.

### ELECTRICAL ENGINEERING

A further Diploma Course recognised by the Institute of Engineers & Technicians, also covering business aspects of electrical contracting.

### RUNNING YOUR OWN BUSINESS

If running your own electronics, T.V. servicing or electrical business appeals, then this Diploma Course trains you in the vital business knowledge and techniques you'll need.

Name .....

Address .....

**ICS**

ICS  
Dept EDSA4  
160 Stewarts Road,  
London SW8 4UJ.



01 622 9911  
(all hours)

### ORIC AND SINCLAIR COMPUTERS



Oric 1 computer 48K £95 (£92) £102.  
Oric Atmos computer 48K £171 (£158)  
£168. Oric Colour Printer £134 (£123)  
£140. New Sinclair QL Computer £495  
(£455) £475. Sinclair Spectrum 48K  
£131 (£131) £143. Spectrum 16K £101  
(£105) £117. Interface 2 £20.45 (£20)  
£24. Microdrive £51 (£50) £60. RS232  
interface £51 (£50) £60. Blank micro-  
drive cartridges £8 (£8) £9. 32K memory  
upgrade kit for 16K Spectrum (Issue 2  
and 3 only) £31 (£28) £30. Fuller Master  
Unit for the spectrum including speech  
synthesizer, sound synthesizer, amplifier  
and joystick port £56 (£56) £62. Fuller  
FDS full sized keyboard for the spec-  
trum with proper space bar £52 (£52)  
£62. Spectrum printer interfaces with  
cables:- Centronics £51 (£47) £52.  
RS232 £35 (£33) £38. ZX printer has  
been replaced by the Alphacom 32 £71  
(£67) £77. 5 printer rolls £13 (£16) £21.  
ZX81 computer £45 (£44) £54. ZX81  
16K ram packs £28 (£25) £30.


### COMMODORE COMPUTERS

Commodore 64 £204 (£184) £204. Vic  
20 £104 (£97) £117. Vic 20 starter pack  
£150 (£143) £173. Converter to allow  
most ordinary mono cassette recorders  
to be used with the Vic 20 and the  
Commodore 64: £9.78 (£9) £11. Bargain  
package:- cassette convertor + com-  
patible cassette recorder £37 (£38) £44.  
Commodore cassette recorder £43  
(£44) £50. Centronics printer interfaces  
for Vic 20 and the Commodore 64 £45  
(£41) £46. RS232 printer interface for  
Commodore 64 £45 (£41) £46. Disc  
drive £233 (£209) £234. 1525 Printer/  
Plotter £165 (£149) £159. 1525 Printer  
£235 (£220) £245. 1526 Printer £350  
(£330) £360.

### ACORN COMPUTERS

Electron £203 (£209) £229. BBC Model  
B £404 (£357) £387. 14" Colour monitor  
£228 (£299) £319. Kenda double density  
disk interface system £139 (£125) £135.  
Disc drives 5.25" 40 track:- single £200  
(£184) £204, dual £356 (£325) £355.

### PRINTERS

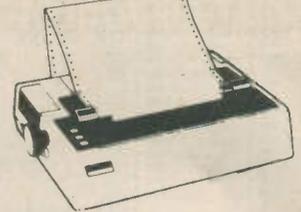

Brother HR5 £185 (£171) £190. Shinwa  
CTI CP80 £225 (£218) £248. Cannon  
PW1080A £332 (£299) £329. Epson  
RX80 £277 (£251) £282. Epson RX80F/T  
£314 (£286) £316. Epson FX80 £399  
(£358) £388. Combined matrix printers  
and electric typewriters: Brother EP22  
£173 (£166) £186. Brother EP44 £258  
(£235) £260. Smith Corona TP1 Daisy  
wheel printer £252 (£225) £255. MCP40  
Oric colour printer/plotter £134 (£123)  
£140. Interfaces to run the above print-  
ers from Vic and the Commodore 64  
£45 (£41) £46. We can supply interfaces  
to run the above printers from Sharp  
computers £58 (£52) £55.

### UK101, SUPERBOARD AND VIDEOGENIE COMPUTERS

We still support these gorgeous  
machines. Please write for our free  
price list.

### SWANLEY ELECTRONICS

The Computer Export Specialists  
Dept PE, 32 Goldsel Rd., Swanley, Kent BR8 8EZ, England.

Please allow 7 days for delivery.

Tel: Swanley (0322) 64851. UK prices are shown first and include post and VAT. The second price in brackets is for export customers in Europe and includes insured air mail postage. The third price is for export customers outside Europe (including Australia etc) and includes insured airmail postage.

**KITS FROM £7  
... TO £60**

# Sparkrite

Buy Sparkrite Brand Leading Auto Electronics  
in self-assembly kit form – And save pounds!!

- Electronic Ignition systems – contact triggered and contactless
- Electronic Car Security Systems—including a new ultrasonic unit
- Car Drive Computer – with 12 functions

**SEND FOR FREE LITERATURE PACK – TODAY!**

**8 SOPHISTICATED  
KITS TO CHOOSE  
FROM.**



To:

SPARKRITE (A Division of Stadium Ltd.), Queensway, Enfield, EN3 4SD.  
Telephone: 01-804 4343

NAME .....

ADDRESS .....

PE

# BI-PAK BARGAINS

## MINIATURE TOOLS FOR HOBBYISTS

-  Miniature round nose side cutters - insulated handles 4 1/2 inch length. Order No. Y043
  -  Miniature long nose pliers - insulated handles 5 1/2 inch length. Order No. Y044
  -  Miniature bend nose pliers - insulated handles 5 1/2 inch length. Order No. Y045
  -  Miniature end nippers - insulated handles 4 1/2 inch length. Order No. Y046
- Miniature snipe nose pliers with side cutter and serrated jaws - insulated handles 5 1/2 inch length. Order No. Y042

### FLEXEY DRIVER

A flexible shaft screwdriver for those awkward to get at screws. Overall length 8 1/2 inch. Order No. FS-1 Flat blade 4mm FS-2 Cross point no. 1 **£1.75 each.**




### GRIP-DRIVER

8 1/2 inch screwdriver with spring loaded grip on end to hold screws in position while reaching into those difficult places. Order No. SD-1 Flat blade 4mm SD-2 Cross point no.0. **£95p each.**

ALL AT **£1.25 each**

## 13 PIECE TOOL KIT AND CASE

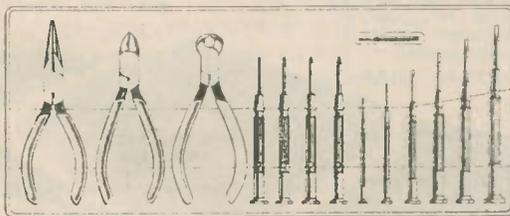

13-piece tool set housed in attractive moulded plastic case with clear sliding cover

- 1 off 5" snipe nose "radio" pliers with side cutters
- 1 off 4 1/2" side cutters
- 1 off 4 1/2" end cutters
- 2 off hex "Allen" key drivers 2mm and 2.5mm,
- 2 off cross-point "Phillips" drivers No. 0 and No. 1 (with tommy bar)
- 6 off precision screwdrivers. Sizes from 1mm to 3.5mm

**ONLY £7.50** ORDER No. VP102

## PRECISION JEWELLERS' TOOLS

Rustproof Tempered Handles and Blades. Chrome Plated Handles. Swivel Heads for use on Precision Work.

### 5T21 SCREWDRIVER SET

6 precision screwdrivers in hinged plastic case. Sizes - 0.8, 1.4, 2, 2.4, 2.9 and 3.8mm **£1.75**

### 5T31 NUT DRIVER SET

5 precision nut drivers in hinged plastic case. With turning rod. Sizes - 3, 3.5, 4, 4.5 and 5mm **£1.75**

### 5T41 TOOL SET

5 precision instruments in hinged plastic case. Crosspoint (Phillips) screwdrivers - H0 and H1 Hex key wrenches. Sizes - 1.5, 2 and 2.5mm **£1.75**

### 5T51 WRENCH SET

5 precision wrenches in hinged plastic case. Sizes - 4, 4.5, 5, 5.5 and 6mm **£1.75**

## MULTITESTER

1,000 opv including test leads & Battery

AC volts - 0-15-150-500-1,000

DC volts - 0-15-150-500-1,000

DC currents - 0-1ma-150ma

Resistance - 0-25 K ohms 100 K ohms

ohms

Dims - 90 x 61 x 30mm.

O/No. 1322 OUR PRICE **£6.50 ONLY**

## SPEAKER PROTECTOR

Limits voltage to speaker or to the permissible max., by automatically introducing a resistor in series with speakers. When excessive voltage is reduced the unit resets itself. Electronic voltage-sensing relay circuit. Spring terminals. Cut-off level adjustable from 10W-120W. Full instructions included. Dims: 85 x 74 x 25mm. O/No. VP 118 **£9.95**



## HIGH PASS FILTER/SUPPRESSOR

CB/TV. High pass filter. Reduces unwanted signals picked up by antenna. Dims: 45 x 25 x 17mm. O/No. VP 115 **45p**

Designed to reduce harmonics on the VHS and TV band. Cut-off frequency: 30MHz. V.S.W.R.: Less than 1.2 to 1. Insertion loss: -0.2dB @ 27MHz. Impedance: 50 ohms. Dims: 80 x 55 x 40mm. O/No. VP116 **£2.75**

## LOW PASS FILTER



## DC-DC POWER SUPPLY

DC to DC adaptor. Plugs into car cigar lighter aperture. Output 3, 4.5, 6, 7.5, 9, 12V @ 800mA. Has universal output spider plug, also 9V battery snap and polarity reversing facility. O/No. VP 119 **£2.45**

## SIGNAL INJECTOR

Simple push button operation. Oscillates at 700 - 1K Hz with harmonics to 30MHz. 1.4V p/p output. Impedance 10kΩ. Ideal for trouble shooting with audio equipment. One "AA" penlight battery supplied. O/No VP96 **£2.50**

## LOGIC PROBE

Automatic levelling. White LED indication. Minimum width of measuring pulse 30 milliseconds. Maximum input frequency 10M Hz. Input impedance: 100kΩ. Power consumption: 40mA maximum. Power supply: 4.5 - 18 V d.c. ORDER No. VP97 **£10.50**

## CURRENT/POL CHECKER

Heavy duty test prods with built-in indicators for testing polarity. Indicates whether a.c. or d.c. 3.5V to 400V. O/No. VP98 **£2.50**

## TESTER

Universal tester with ceramic buzzer. Tests diodes, transistors, resistors, capacitors and continuity. One "AA" penlight battery included. Test current: Max 2µA. Test voltage: 12V. Response range: 100MΩ. Max voltage: 500V. Internal resistance: 390kΩ. Length: 135mm. O/No. VP99 **£5.00**

## CIRCUIT TESTER

D.C. continuity tester for circuit checking on all low voltage equipment and components. Diode checking also possible. Takes two AA batteries. 90cm lead has crocodile clip. Body length 145mm. O/No. VP100 **75p**

## ELECTRONIC SIREN 12v DC

Red plastic case with adjustable fixing bracket. Emits high-pitched wailing note of varying pitch - 100 cycles per minute. Dims - 90mm (dia.) 60mm (depth). Power - 12v DC. D/P 90dBA 1m type. Our Price: **£5.50** O/No. VP79

## TAPE RECORDER SWITCH

Unit to control motor of tape recorder. 1.8m cord and 2.5mm plug attached. On/Off switch. Dims: 55 x 20 x 20mm. O/No. VP 127 **£1.00**

## POWER SUPPLY OUR PRICE £4.25

Power supply fits directly into 13 amp socket. Fused for safety. Polarity reversing socket. Voltage switch. Lead with multi plug. Input - 240V AC 50Hz. Output - 3, 4, 5, 6, 7.5, 9 & 12V DC Rating - 300 ma VP109.

## RATCHET SCREWDRIVER KIT

Comprises 2 standard screwdriver blades 5 & 7mm size 2 cross point size 4 & 6 1 Ratchet handle. 5-in-1 Kit. £1.45 each. O/No 3298

## ELECT & PIEZO BUZZERS

**PIEZO**  
Miniature round piezo-electronic buzzer. White plastic. Low consumption. Frequency: 4kHz approx. Output: 70dB (A) @ 1 typ. Power: 12Vd.c. 4mA. Dims: 22 (dia.) x 11.5mm. Fixing Centres: 26.5mm. O/No. VP 107 **95p**

**PIEZO**  
Piezo buzzer. White plastic. 90mm leads. For use on a.c. mains. Frequency: 3.5kHz approx. Output: 80dB (A) @ 1m typ. Power: 240V a.c. 5mA. Dims: 32 (dia.) x 14mm. Fixing centres: 38mm. O/No. VP 108 **£1.15**

**ELECTRONIC**  
Miniature electronic buzzers. Solid state. Ivory plastic. 150 leads. Frequency: 500 Hz approx. Dims: 22 x 16 x 15mm. Output: 82dB (A) @ 1m typ. Fixing centres: 26mm. 3V 25mA. O/No. VP 82. 6V 25mA. VP 83. 9V 25mA. O/No. VP 84. 12V 25mA. VP 85. **80p each**

## SUB-BOX

A neat swivelling disc provides close tolerance substitution resistors of 36 preferred values from 50ohms to 1Kohm. Simply fix clips into circuit and swivel until optimum result is achieved. O/No. VP 112 **£4.75**

## MINIATURE VICE

Miniature plastic and metal vice with strong suction base for portability. Single action to secure or release suction. Plastic jaws with rubber pads. 20mm wide, open out to 40mm. Dims: 85 x 65 x 60mm approx. **FANTASTIC VALUE** O/No. VP 95 **ONLY £1.60**

## LEARN A LINGO! PILLOW SPEAKER

Slim under pillow unit. 8ohms 2" speaker. 1.5m lead with 3.5mm mono jack plug. Black. Dims: 65 (dia.) x 17mm. O/No. VP 88 **£1.25**

## METRIC & BRITISH MEASURES

Steel tapes in sturdy ABS plastic case. Silk wrist strap. These yellow coated convex tapes have inch and metric graduations. Automatic push-button return. 2m long - 13mm wide. O/No. VP 89 **£1.00**  
3m long - 13mm wide. O/No. VP 90 **£1.50**  
5m long - 16mm wide. O/No. VP 91 **£2.00**

## BATTERY TESTER

Tests all types of battery including standard, NICAQ, Alkaline etc. Takes all standard sizes including 6V lantern batteries and watch/hearing aids cells. Also tests fuses and lamps by means of internal 9V (PP3) battery. Can also be used to recharge NICAQ batteries by means of external 3-12V d.c. power supply (not included). Full instructions provided. Dims: 185 x 103 x 30mm (approx.) O/No. VP 101 **£7.00**

## FM MONITOR

FM monitor for 2 metre band. All metal. Attached earphone. PL259/S0239 connectors. 144MHz. 10W maximum. Dims (Body) 55 x 30 x 23mm. O/No. VP 120 **£4.20**

## DUMMY LOAD

50 ohms 30W. UHF co-axial plug fitting (PL259). O/No. VP 121 **£5.20**

## PICK-UP COIL

Large telephone pick-up coil for high sensitivity. Suction pad to stick to telephone. 90cm lead to 3.5 jack plug. Connects direct to cassette recorder. Dims: 32 (dia.) x 17mm (body) 36mm (dia.) sucker. O/No. VP 87 **£1.00**

# BI-PAK

Send your orders to Dept PE10 BI-PAK PO BOX 6 WARE, HERTS  
SHOP AT 3 BALDOCK ST. WARE, HERTS  
TERMS CASH WITH ORDER. SAME DAY DESPATCH. ACCESS  
BARCLAYCARD ALSO ACCEPTED. TEL (0920) 3182. GIRO 388 7006  
ADD 15% VAT AND 75p PER ORDER-POSTAGE AND PACKING



Use your credit card. King us on Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail. Remember you must add VAT at 15% to your total order. Postage add 75p per Total order.

# TOP QUALITY KITS AT LOW-BUDGET PRICES



## MPA 200 100w Mixer/Amplifier

A rugged mixer amp designed for adaptability, stability and easy assembly. The MPA 200 has four inputs (sensitivities can be easily changed), 3 separate tone controls and a master volume control. Steel cabinet to suit 19" rack systems.

Complete kit **£79.50 + VAT**



## SP2 200 2-Channel 100 watt Amplifier

An ingeniously designed power amp. The SP2 200 can deliver over 100w rms into 8 ohms on each channel. Separate volume control and a sensitivity of 0.775 mV (0dBm) make this unit suitable for virtually all pre amps or mixers. Construction is very simple, with minimal wiring and the steel cabinet is suitable for 19" rack mounting.

Complete kit **£99.50 + VAT**



## Chromatheque 5000 5 Channel Lighting Effects System

Versatility is the key aspect of the Chromatheque. Musical input can perform switching or modulation of the light output. 5 banks of lamps of up to 500w each can be controlled in either analogue or digital mode. Variable light level controls provide scope for "mood" lighting. The kit's single-board concept makes for straightforward assembly.

Complete kit **£79.50 + VAT**



## Digital Delay Line

Digital quality at an Analogue price! With this unit you can have Phasing, Flanging, ADT, Chorus, Echo and Vibrato at the touch of a button. In a steel cabinet suitable for 19" rack mounting.

Complete kit (400ms delay) **£179.00 + VAT**

Parts for Extra 400ms delay (up to 3 can be added)

**£19.50 + VAT**




## Cortex II 16-bit 16-colour Computer

The new slimline Cortex offers constructors the speed and power of 16-bit computing for the same price as an 8-bit games machine. The standard kit has TV, cassette and RS232C interfaces - others are available as optional extras. Add disc drives, printer and monitor for a fully-fledged business system.

Complete kit **£299.00 + VAT**

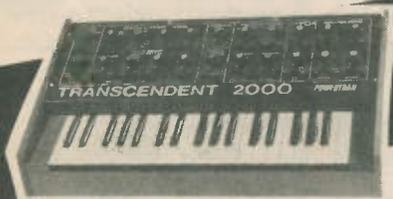Optional extras Phone for illustrated brochure



## Transcendent 2000

This professional quality, single board 3-octave synth is transposable 2 octaves up or down giving an effective 7-octave range. There is portamento, pitch bending, VCD with shape and pitch modulation, VCF with high and low pass outputs and separate dynamic sweep control; noise generator and an ADSR envelope generator.

Complete kit **£150.00 + VAT**




## Hebot II Robot Turtle

At a price that makes even a TV look expensive, Hebot provides an exciting introduction to computer control. Independent drive of the two wheels, flashing "eyes", two-tone horn and a retractable pen are directed by your microcomputer while four collision detectors relay information about the robot's environment.

Complete kit **£95.00 + VAT**

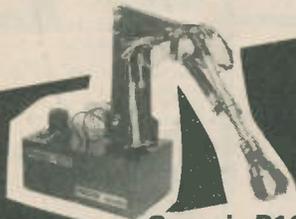Universal computer interface board kit **£11.00 + VAT**



## Genesis P101 Hydraulic Robot Arm

With its own dedicated microprocessor or under the control of an external computer, the Genesis P101 simulates the operation of industrial robots at a mere fraction of their cost. With this robot, practical robotics experience is available without tying up valuable capital.

\*6-axis robot system kit **£1050.00 + VAT**  
6 axis robot kit **£750 + VAT**



## MicroGrasp Electric Robot Arm

A real programmable robot arm at an affordable price. Five motors - four with servo control - are mounted directly on the axes they drive (no fiddly strings and pulleys!). The robot can be controlled by any microcomputer with an expansion bus.

Robot kit with power supply **£215.00 + VAT**  
Universal computer interface board kit **£57.00 + VAT**



## Genesis P102 Hydraulic Robot Arm

A sophisticated robot system with microprocessor control, two speed, double acting hydraulic operation and the option of external computer control.

The P102 offers "hands-on" experience for robotics training, at a fraction of the cost of an industrial robot.

\*6-axis robot system kit **£1476.00 + VAT**

\*System includes Robot, Processor Box and Teach Pendant



# DOPPLER RADAR INTRUDER ALARM

Featured in this Issue

All kits are complete down to the last nut and bolt and are supplied with an easy-to-follow assembly handbook.

Write or phone for further details, stating which product(s) interest you.

Access/Visa cardholders may order by telephone to avoid delays.

Prices apply to UK only and are correct at time of going to press. Overseas customers - please contact our Export Department for the name and address of your local dealer. Allow 21 days for delivery. Offers subject to availability.

# POWERTRAN cybernetics Ltd.



PORTWAY INDUSTRIAL ESTATE, ANDOVER,  
HANTS SP10 3PE. TEL (0264) 64455

## LICENSING

THE Government has just published a consultative paper on the relaxation of licensing requirements for low power radio devices in the UK. The proposals cover such items as aids for the disabled, garage door openers, radio microphones and radio doppler alarm systems.

Licensing restrictions on metal locators and model control equipment were changed some time ago and this new move will allow further freedom to buy and use equipment working on approved frequencies and below specified power levels—providing of course the proposals are passed.

At the present time however you will need a licence to use the *Doppler Radar Alarm* published in this issue. We will keep you informed if the situation changes.

This alarm system with up to four transmitter/receiver units can be easily

set up to protect your home and could well be a very worthwhile investment.

## MORE ROBOTICS


Maybe one or two readers are a little tired of reading about robots and robotics on this page but I make no apology for including some more on the subject. Much of the future of industry is tied up with robotics and it is now becoming a significant subject in education and of course for hobbyists with an eye on the future and possibly a career.

Next month we take an in-depth look at small robots with two articles from Tom Ivall and a buyers' guide to products available from around twenty UK companies. These items will form a Free 16-page Robotics Supplement which will also be carried by our sister publication *Everyday Electronics*.

PE is the leading publication in the area of serious use of small robots with

designs for six units now published. Back in October 1981 we published an article by Professor Wilfred Heginbotham OBE, D.Sc. Director General of PERA (Production Engineering Research Association) which set the scene on industrial robots and the future. Readers bred on our designs may have a significant part to play in that future. PE intends to also play a part in the development of robotics and we are actively pursuing new designs and ideas in the small robot area which will continue to break new ground.

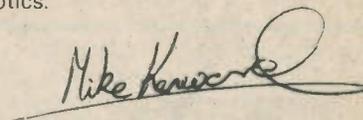*Everyday Electronics* will also publish some interesting low cost educational robotics projects starting with *Alfred* next month and moving on to other new educational ideas in robotics.



**Editor** Mike Kenward

**Secretary** Pauline Mitchell

### Assistant Editors

Dave Barrington (Production)

David Shortland (Technical)

### Technical Editor

Mike Abbott

### Projects Editor

David Brunskill

### Technical Sub-Editors

Richard Barron

Brian Butler

### Art Editor

Jack Pountney

### Assistant Art Editor

Keith Woodruff

### Senior Tech. Illustrator

John Pickering

### Tech. Illustrator

Isabelle Greenaway

*Technical and editorial queries and letters (see note below) to:*

Practical Electronics Editorial,  
Westover House,  
West Quay Road, Poole,  
Dorset BH15 1JG

**Phone: Editorial Poole 671191**

**We regret that lengthy technical enquiries cannot be answered over the telephone**

*Queries and letters concerning advertisements to:*

Practical Electronics Advertisements,  
King's Reach Tower,  
Stamford Street, London SE1 9LS  
Telex: 915748 MAGDIV-G

**Advertisement Manager** David Tilleard 01-261 6676

**Secretary** Christine Pocknell 01-261 6676

### Advertisement Sales Executives

Alfred Tonge 01-261 6819

Richard Willett 01-261 6865

**Classified Supervisor** Barbara Blake 01-261 5897

**Ad. Make-up/Copy** Brian Lamb 01-261 6601

## Letters and Queries

We are unable to offer any advice on the use or purchase of commercial equipment or the incorporation or modification of designs published in PE. All letters requiring a reply should be accompanied by a stamped, self addressed envelope, or addressed envelope and international reply coupons, and each letter should relate to **one published project only**.

Components and p.c.b.s are usually available from advertisers; where we anticipate difficulties a source will be suggested.

## Back Numbers and Binders

Copies of most of our recent issues are available from: Post Sales Department (Practical Electronics), IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF, at £1 each including Inland/Overseas p&p. Please state month and year of issue required.

Binders for PE are available from the same address as back numbers at £5.50 each to UK or overseas addresses, including postage, packing and VAT where appropriate. State year and volume required.

## Subscriptions

Copies of Practical Electronics are available by post, inland for £13, overseas for £14 per 12 issues, from: Practical Electronics, Subscription Department, IPC Magazines Ltd., Room 2816, King's Reach Tower, Stamford Street, London SE1 9LS. Cheques, postal orders and international money orders should be made payable to IPC Magazines Limited. Payment for subscriptions can also be made using a credit card.

Items mentioned are available through normal retail outlets, unless otherwise specified. Prices correct at time of going to press.

## Pirates caught RED handed

Piracy of software has reached such staggering proportions in the UK that (according to the Guild of Software Houses) for every one legitimate manufacturers' copy sold there are ten counterfeit copies sold. It is further estimated that this contraband market is depriving software houses of around £100 million per annum in lost revenue.

Many software producers are funding and/or working on systems to ensure that illegal copies cannot be made, in order to keep original programs 'original'.

One such company is Rising Edge Data Ltd., who have developed a patented protection system to prevent mass copying of computer software. The system is known as RED and can be adopted by any computer company or programmer and while preventing mass copying will still allow the originator to make back-up copies,


The secret of RED is in the digitised security card which is the same size and shape as a credit card and the reader unit which plugs into the computer. The reader unit will prevent a program being run until the unit is activated by the insertion of the magnetically encoded card. The code on the 'key' card is identical to a program code written into the software, only when the two codes match will the computer allow the program to be run. This means that without the 'key' card a user cannot run the program; RED can be used with most of the popular micros.

The system as yet is being considered by software houses and independent writers

and if adopted would mean that home users would have to buy a RED reader unit in order to run protected software. Tapes could then be sold along with their 'key' cards.

RED's success will depend on the willingness of software originators to accept the concept and of course the users' willingness to buy a reader unit. Although no price has been set for a reader unit, the manufacturers accept that it will have to be very low.

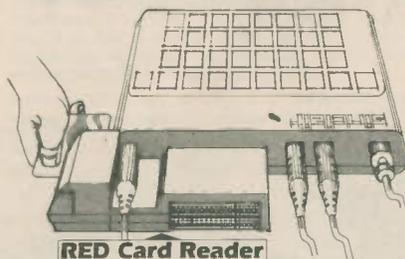Rising Edge Data is a subsidiary of Abacus Programs, Swansea. For further information contact Active Marketing, 113 Walter Road, Swansea SA1 5QQ. (0792 472927).



RED Card Reader

## BBC WIND TESTS

An Acorn BBC Microcomputer is being used in wind tunnel tests at Southampton University to improve the performance of aircraft, racing cars and other motor vehicles.

The wind tunnel enables engineers to measure the aerodynamic forces operating on the racing car. To simulate normal race circuit air conditions a 200 horse power fan blows air over a detailed one-third scale model of the car, while a moving belt under the wheels simulates the ground effects of travelling at speed.



The computer, a BBC Model B Micro, scales up the data gained from the model car in the tunnel tests to direct loads that the real car would encounter. This allows the racing team to study the effect of modifications to the basic design under controlled and economical conditions.

A further program on the machine works out how these modifications will affect lap times. The software 'models' the Silverstone circuit and calculates lap times after the model car has undergone changes in aerofoil settings and body design. These are then adapted to the real car for 'live' testing.

## BEWA MULTIMETERS



An impressive range of 3½ digit hand-held multimeters have been introduced into the UK by House of Instruments.

The range of 9 models in colour coded format (i.e. the Multimeter body) are in three model ranges of accuracy 0.1%; 0.25% and 0.5% each model in the 0.5% and 0.25% range offering a.c./d.c. current facilities of 2A, 10A and 20A, the 20 Amp being a new facility not hitherto available in this price range.

The BEWA multimeters conform to DIN & VDE specifications and are ruggedly conceived with side push-button selection. Ample protection is offered and prices start as low as £43.41 inc VAT and P & P for the 6010GS (pictured). From House of Instruments, Clifton Chambers, 62 High Street, Saffron Walden, Essex CB10 1EE. (0799 24922).

## Quadriennium

The BBC has extended the agreement with Acorn Computers for the manufacture and distribution of the BBC Microcomputer for a further four year period from 1 September 1984.

The BBC Computer Literacy Project is now in its third successful year. There is a growing demand for computer education, and the BBC plans to make new computer series and produce new books and software, as well as repeating existing series.

More than 350,000 BBC Microcomputers have been sold to date. Over half the micros used in education in Britain are BBC machines, and during the last year, three quarters of the computers bought by schools were BBC micros. It is against this background that the BBC has decided to renew the contract with Acorn.

# MARKET PLACE


## Helping hand NEON DRIVER OPTION

Few DIY jobs are more frustrating than the one that needs "three hands"—two to hold the work and a third to apply solder or adhesive. The smaller the component, the more difficult it is to position it accurately and firmly.

Gripmate, produced by an innovative Sussex company, is a tiny clamp that provides not just one extra "hand" but four, able to grip small electronic components and similar items in an infinite number of positions.

A base block clamped to any bench or table top carries four semi-rigid wires, each fitted with a crocodile clip to hold the work. Alternatively, any of the wires can be replaced with one holding either a magnifying glass for close-up work, or perhaps a magnet.

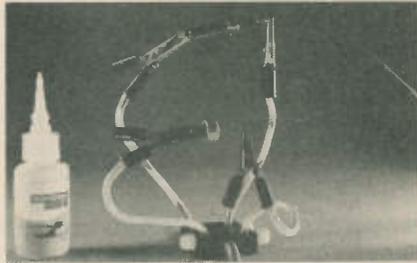The four-handed model costs £4.85 (a basic type with two arms sells for £1.00 less), and the magnifier and magnet come for £2.50 and £1.50 respectively, prices include VAT and p & p, from Kemplant Ltd, Durfold Wood, Plaistow, Billingshurst, W. Sussex RH14 0PN. (048 649344).



An electronic single-pole voltage tester, designed as an effective alternative to the conventional neon voltage testers, is announced by Steinel (UK) Ltd. The Mono Check will give a bright, easily visible indication in virtually any circumstances, when voltage is detected. A special electronic sensing circuit overcomes the problems of neon types which can often be very difficult to see when the user presents a very high insulation to earth.

DIY enthusiasts will appreciate the tough, high quality construction of the

Mono Check and the safety aspects of the design. The voltage testing range is from 80V to 240V a.c. and there is a very generous overvoltage range of six times normal maximum (1500V). The Mono Check can be used in all situations in temperatures from -20 to +80 degrees C and in humidities up to 95 per cent. The battery lasts for around one year. The price of £3.99 includes the 12V battery, VAT and P & P. From J. E. M. Marketing, 180 Princess Avenue, Palmers Green, London N13 6HL. (01-889 1415).



## Briefly...

*Job hunters who take TOPS computer training courses stand a 10 per cent better chance of finding employment this year than last. So far this year 59 per cent of leavers found a job within three months of completing their courses. Improved prospects in trade and industry along with curriculum changes are believed to be the main factors in this encouraging trend.*

The Rt. Hon. Kenneth Baker, MP, Minister for Information Technology, announced recently that Britain will be a major participant in the European Space Agency's ERS-1 programme to develop a remote sensing satellite. The data provided will be of value to a range of users for forecasting winds, waves, sea-ice and weather; users will be able to receive information within three hours. Britain is one of the first countries to sign-up and will take a 14 per cent share in the £325 million project. ERS-1 is due to be launched in 1989.

## Countdown ...

Please check dates before setting out, as we cannot guarantee the accuracy of the information presented below. Note: some exhibitions may be trade only. If you are organising any electrical/electronics, radio or scientific event, big or small, we shall be glad to include it here. Address details to Mike Abbott.

**Computer Roadshow** (Architects/surveyors) Sept. 11-13. B/ham. U2  
**Testmex** Sept. 11-13. Grosvenor Ho. Pk. Lane, London. E  
**Leeds Energy Manager** Sept. 12-13. W3  
**What Peripherals** Sept. 13-16. Barbican. J3  
**Computer Roadshow** (Healthcare) Sept. 14-16. Birmingham. U2  
**Personal Computer World Show** Sept. 19-23. Olympia 2, London. M  
**Computer Roadshow** (Healthcare) Sept. 22-24. Manchester. U2  
**Semiconductor International** Sept. 25-27. NEC. T1  
**Computer Trade Forum** Sept. 25-28. NEC, Birmingham. T1  
**Pemec** (British Robot Assn.) Sept. 25-28. NEC. G2  
**Building & Home Improvement** Sept. 25-30. Earls Court, London. M  
**Computer Fair** Sept. 29. Prestatyn High School. See the I.T. mobile exhibition, armed forces and Microelectronics Education Programme Centre. Competition, clubs, hardware/software. Z9  
**Computer Roadshow** (Healthcare) Sept. 29-Oct. 1. Edinburgh. U2  
**Computer Graphics** Oct. 9-11. Wembley Conf. Cntr., London. O  
**Machine Intelligence** Oct. 9-11. Cunard Int. Hotel, London. I  
**Software Expo** Oct. 16-18. Wembley Conf. Cntr., London. O

**Internecon** Oct. 16-18. Metropole, Brighton. T1  
**Scottish Energy Manager** Oct. 23-24. Slean Dhu Hotel, Glasgow. W3  
**Business Equipment Show** Oct. 23-26. Olympia, London. Z  
**Drives, Motors & Controls** Oct. 24-26. Harrogate Exhibition Cntr. E  
**Electron & BBC Micro User** Oct. 25-28. Alexandra Palace, London. L  
**International Test & Measurement** Oct. 30-Nov. 1. Olympia. D4  
**Leisuretronics** Nov. 8-11. Royal Horticultural Hall, London. T  
**P.c.b. Manufacture & UV Box Construction** (meeting) Nov. 17. Electronic Organ Constructors Society. Y4  
**Computers In The City** Nov. 20-22. Barbican, London. O  
**Data Security** Nov. 20-22. Barbican, London. O

D4 Network ☎ 0280 815226  
E Evan Steadman ☎ 0799 26699  
G2 ☎ 01-747 3131  
I ITF ☎ 021-705 6707  
J3 Computer Marketplace ☎ 01-930 1612  
L Database ☎ 061-456 8383  
M Montbuild ☎ 01-486 1951  
O Online ☎ 01-868 4466  
T Trident Exhibitions ☎ 0822 4671  
T1 Cahners ☎ 0483 38085  
U2 Macro Exhibitions Ltd. ☎ 0992 469556  
W3 MCM ☎ 01-231 1481  
Y4 Percy Vickery ☎ 0202 423863  
Z Beta Exhibitions ☎ 01-405 6233  
Z9 Mr. Carson ☎ 0244 535606

# FILTER SHIFT PHASER



**JOHN  
M.H. BECKER**

**A**N ENHANCED phasing effect is produced in this unit by passing a music signal through modulated voltage controlled filter and delay line stages, then mixing this processed signal with the original at the output. The rate and depth of modulation, the v.c.f. response and mixing balance are panel controlled. The v.c.f., phase and by-pass modes are selected via electronic gates for quiet switching. It may be used with most electronic musical instruments or pre-recorded sources. A block diagram is given in Fig. 1.

## GATE AND STATIC FILTER

The electronic changeover gates IC3a and IC3b are connected to allow either the original or v.c.f. processed signal to pass through, and are activated by S1. R22 maintains a small d.c. current on the output of the gates to minimise switch over noise. The output from the gates is then fed to the first static filter stage around IC4d in which C11 and C12 limit the maximum frequency to about 5kHz at unity gain. This limit is imposed to reduce harmonic distortion in the delay stage where the maximum signal frequency preferred is approximately one third of its controlling clock signal.

## DELAY STAGE

IC8 is a 512-stage bucket brigade delay line chip that passes the audio signal through at a rate determined by the frequency of the controlling clock. The delay increases as the clock frequency reduces. Waveform distortion through the chip is kept to a minimum by applying an optimum bias voltage on its input via VR1. The twin outputs are summed at VR2, to produce a slightly attenuated delayed signal that inherently includes a trace of the clocking signal. This is partially balanced out by adjusting VR2. The remainder is filtered out by the second static filter stage around IC1d, where unity gain is maintained for the low pass signal as set by C17 and C18.

## MIXER AND OUTPUT

From IC1d the signal may be switched through the electronic gate IC3c activated by S2. VR3 then allows the desired level to be mixed with the original signal at IC1c. Here a gain of two is given to the processed signal to allow for attenuation in the delay stage. The original signal passes through at unity gain with little insertion loss. The phasing effect is produced when the phase relationship between the two signals changes. Note that the maximum level of the

## INPUT SPLITTING

The signal to be processed is brought into the unity gain buffer stage IC1a and fed simultaneously to the final output stage IC1c, the voltage controlled filter around IC1b and IC2, and the selector gates IC3a and IC3b.

## VOLTAGE CONTROLLED FILTER

The purpose of the filter is to give enhancement to a frequency bandwidth that is being constantly shifted up and down depending on the modulating control voltage applied. On its own the modified output gives a marked change to the quality of the audio signal, and when combined with phase shifting of the delay stage further interesting changes result. At a slow rate of modulation the filter effect on its own is similar to phase shifting with harmonic overtones. At a fast rate, a bubbly *wah* effect results. VR7 controls the frequency bandwidth emphasised, but should not be regarded as a level control, though at its lower end it behaves in a similar fashion as the bandwidth is moved out of the audio range. The circuit for the v.c.f. consists of a mixer stage IC1b, two transconductance op. amps IC2a and IC2c, and two high impedance stages IC2b and IC2d. The workings are too complex to be described here, but essentially the bandpass range as seen at pin 8 of IC2b is determined by the current flowing into C5 and C6, as set by the control voltage on R21 via VR7, with a gain factor determined by the value of R7.

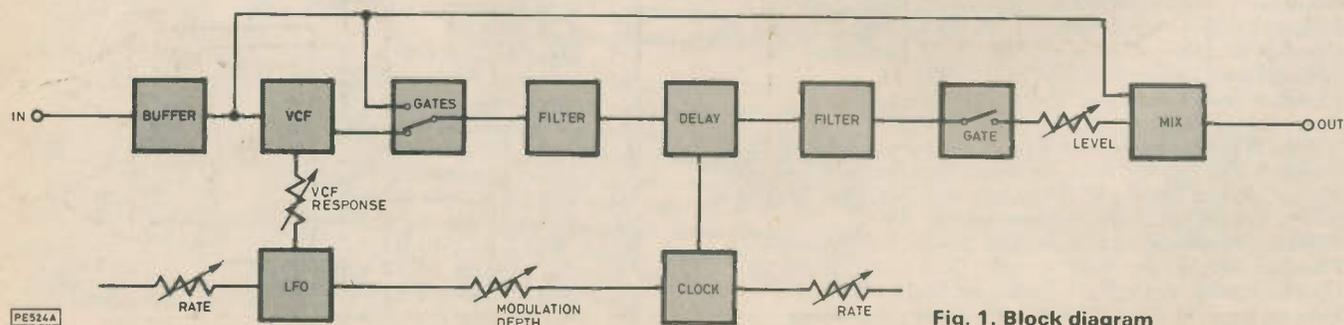


Fig. 1. Block diagram

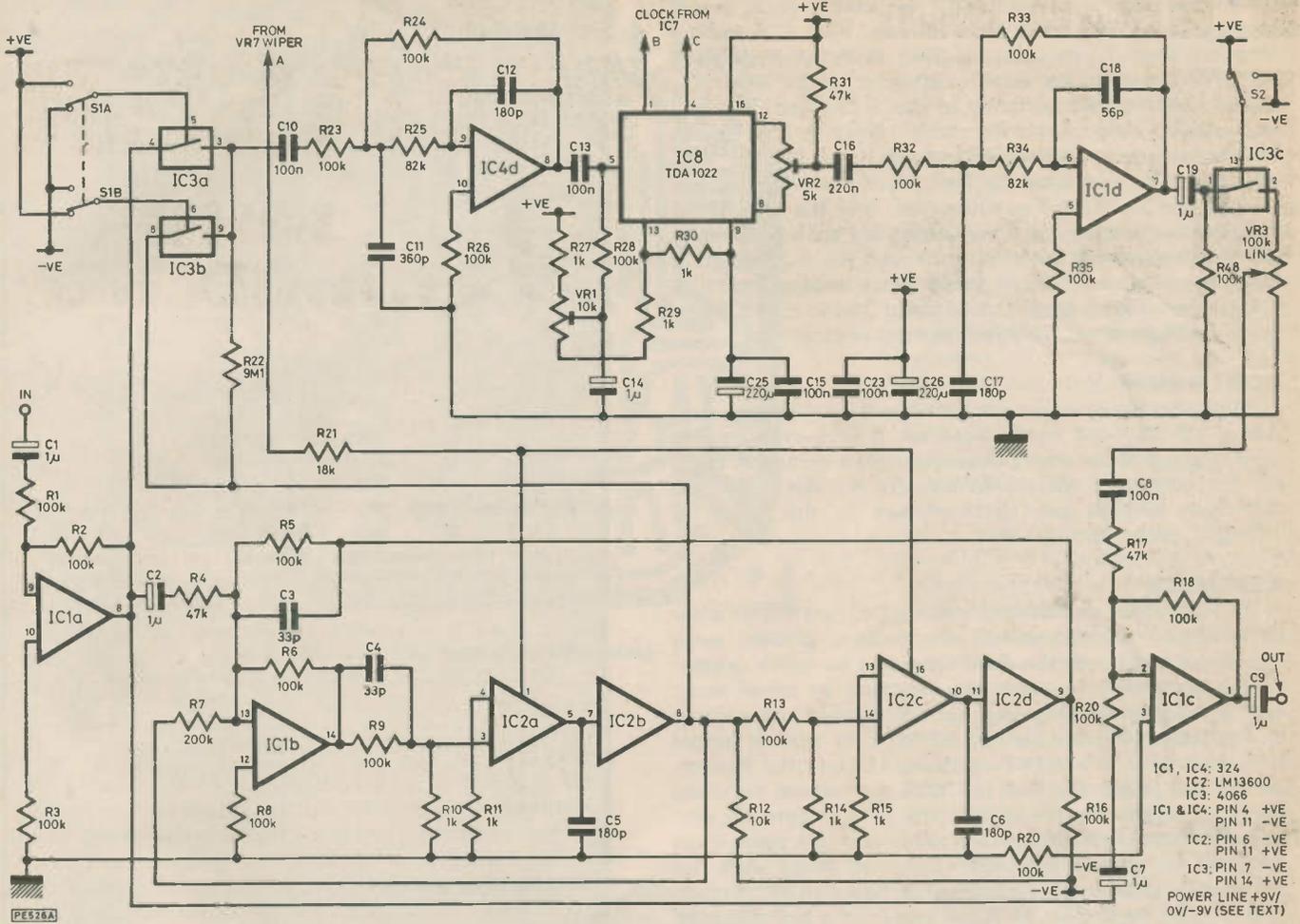


Fig. 2. Circuit diagram

combined signal can be up to twice that of the original depending on the relationship. From IC1c the combined signal can be fed to the normal amplifier system.

### MODULATING OSCILLATOR

The modulation voltage needed to vary the phase and v.c.f. changes is derived from the circuit around IC4a/b. The

frequency range is determined by C20 which varies its charge at a rate set by VR4. Each time the threshold trigger point of the comparator IC4b is passed, the direction of charge is reversed resulting in a triangular waveform at pin 7 of IC4a, variable by VR4 between about 7 and 2 cycles per minute. This can modulate the v.c.f. via VR7, and the delay clock generator stage via VR5, with IC4c optimising the voltage swing. C24 slightly smooths the peaks of the modulating waveform.

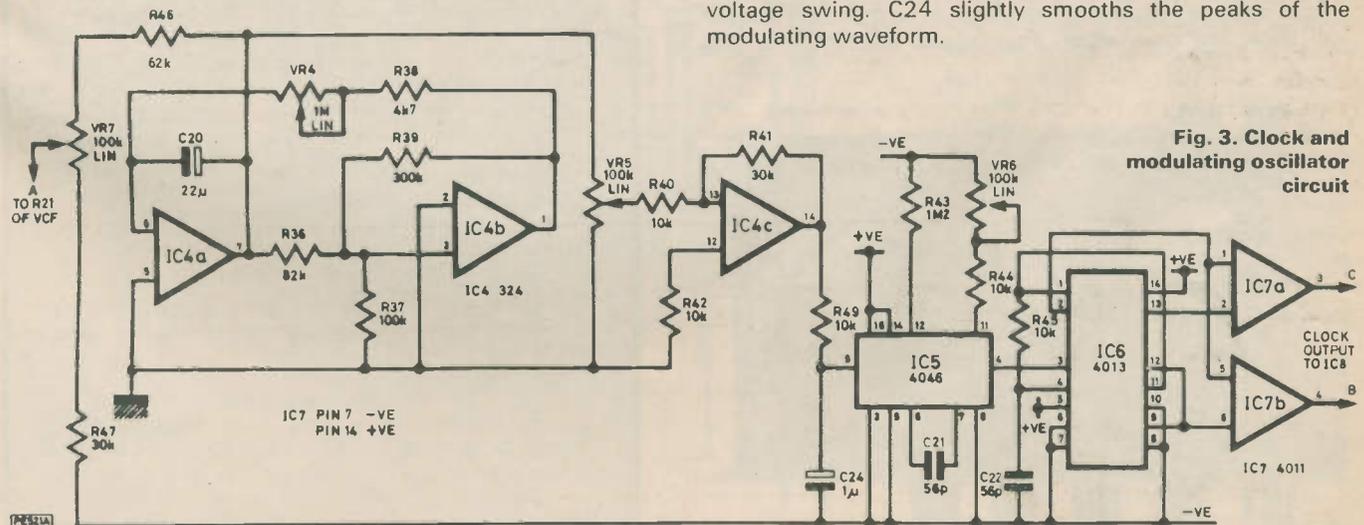


Fig. 3. Clock and modulating oscillator circuit

## CLOCK GENERATOR

IC4 is a linear voltage controlled oscillator where the output frequency is determined by the relationship of the power supply voltage, R43, the total of R44 and VR6, C21 and the voltage present on its input via IC4c. With the modulation off, VR6 can vary the clock range from about 46kHz to 430kHz. With a voltage swing of about 13V from IC4c the clock sweep range becomes about 15kHz to 83kHz with VR6 at maximum resistance, and 86kHz to 840kHz with VR6 at minimum resistance. The output from IC5 is taken through the twin flip flop stage IC6, and the twin gates IC7a/b. Here the output is two antiphase square waves at half the frequency of the input clock, and without overlap to their edges thus achieving a quieter clock residual from IC8. The full signal delay range is thus about 3ms to 17ms. These calculated figures may vary with component tolerances.

## POWER SUPPLY


The unit is designed for use with two 9 volt batteries supplying +9V/0V/-9V at about 10mA. If a power supply is used in place of batteries this should not be exceeded, but it can be reduced to about +5V/0V/-5V without significant detriment, though the optimum lies in the range of +6V/0V/-6V to +9V/0V/-9V.

## ASSEMBLY

Be methodical and assemble the p.c.b. carefully in order of resistors, small capacitors, i.c. sockets, presets, large capacitors and finally the short link wires for which resistor off-cut leads may be used. Ritually check all solder joints with a magnifying glass, even for experienced constructors this still pays off in trouble-free testing. Only after all control wiring has been finished should the i.c.s be inserted, remembering that i.c.s 3 and 5-8 are MOS and require the usual handling precautions. Note that the jack sockets are also wired as battery on-off switches and mono jack plugs must be used for correct operation. Screened leads were not found to be necessary with the battery operated unit, though they may be needed for the signal leads to the jack sockets if a mains power supply is used in the same box. Ensure that the box is grounded. For the battery unit a link wire from a pot body to the 0V line is adequate. Upon completion the box may be painted and control legends applied with letreset or similar, covering them with a clear varnish or plastic film.
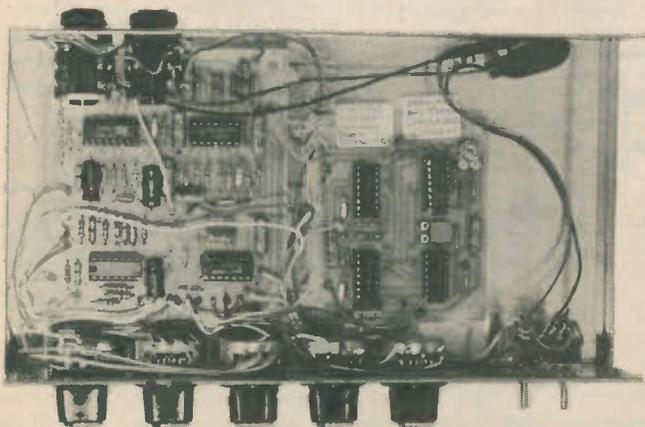
## SETTING UP

VR1 and 2 midway, VR3-VR7 minimum, S1 and 2 off. Apply a music signal to the input, at this time a pre-recorded source such as a cassette music track of an orchestral nature will show the best effect. Plug output into amplifier and



## COMPONENTS . . .

### Resistors

R1-3, R5, R6, R8, R9, R13,	
R16, R18-20, R23, R24, R26,	
R28, R32, R33, R35, R37, R48	100k (21 off)
R4, R17, R31	47k (3 off)
R7	200k
R10, R11, R14, R15, R27, R29,	
R30	1k (7 off)
R12, R40, R42, R44, R45, R49	10k (6 off)
R21	18k
R22	9M1
R25, R34, R36	82k (3 off)
R38	4k7
R39	300k
R41, R47	30k (2 off)
R43	1M2
R46	62k

### Potentiometers

VR1	10k skel.
VR2	5k skel.
VR3, VR5-7	100k lin. mono rota (4 off)
VR4	1M lin. mono rota

### Capacitors

C1, C2, C7, C9, C14, C19, C24	1µF/24V elect (7 off)
C3, C4	33p polystyrene (2 off)
C5, C6, C12, C17	180p polystyrene (4 off)
C8, C10, C13, C15, C23	100n (5 off)
C11	360p polystyrene
C16	220n
C18, C21, C22	56p (3 off)
C20, C25, C26	22µF/10V elect (3 off)

### Integrated Circuits

IC1, IC4	324 (2 off)
IC2	LM13600
IC3	4066*
IC5	4046*
IC6	4013*
IC7	4011*
IC8	TDA1022*

### Miscellaneous

PP3 battery clip (2 off)
P.c.b. clip (8 off)
Round knobs (5 off)
Main Control p.c.b.
Clock p.c.b.
14-pin i.c. sockets (5 off)
16-pin i.c. sockets (3 off)
Stereo jack socket (2 off)
S1 DPDT switch
S2 SPDT switch
Case—Phonosonics type BK3
Rubber stick-on feet (4 off)
Connecting wire

**\*CAUTION**—MOS devices are liable to sudden death from static electricity and are subject to special handling precautions.

### Constructors' Note

Complete kit of parts available from: **Phonosonics**, 8 Finucane Drive, Orpington, Kent BR5 4ED. Price £46.00 inc. UK p&p and VAT.

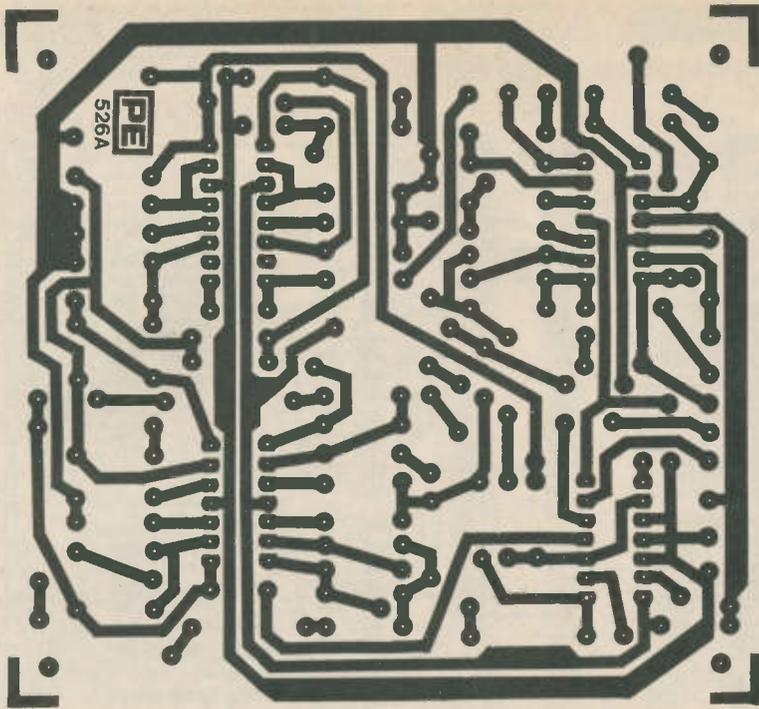


Fig. 4. Main board p.c.b. layout (actual size)

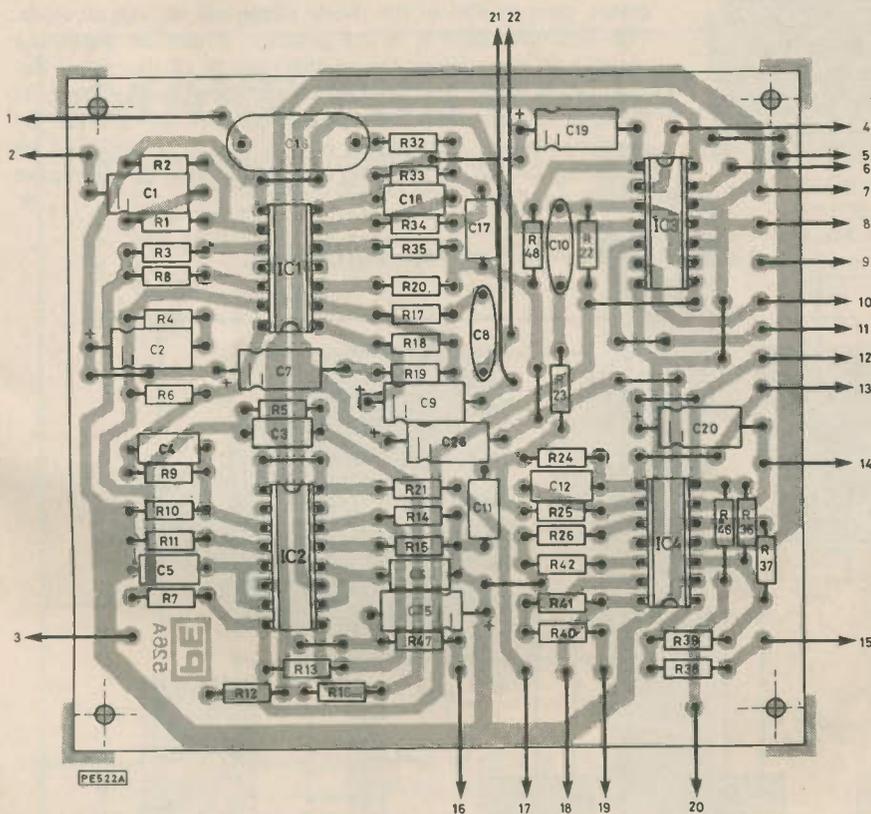


Fig. 5. Main board component layout

check that the signal passes through at a normal level. Switch on S2, bring up VR3 fully and a change in signal level and quality should be apparent as the delayed and original signals are mixed without modulation. Vary VR6 and the phase shifting effect should be heard. Adjust VR1 around its midway point until minimum distortion is apparent on higher volume signals. Remove music source, return VR6 to min (slowest clock), increase amplifier volume until background hiss from the delay stage is heard, then adjust VR2 around its midway point until this minimises, at which point the twin outputs of IC8 are balanced. If no significant change is observed with the variation of VR1 and VR2, leave them midway and ignore. If an oscilloscope is used the balance points will be obvious. Return amplifier to normal volume, reapply music, maximise VR6, bring up VR4 and VR5 to about three-quarters and automatic phasing at a moderate rate should be evident. Adjusting VR6 will change the quality, VR4 the rate, and VR5 the depth. Taking VR4 and VR5 beyond the three-quarters position will introduce extreme results best reserved for producing unusual effects. Turn down VR5 so removing the automatic phasing. Switch the v.c.f. into circuit with S1 and by bringing up VR7 the filter shifting effect will come in. This affects the higher frequencies first, and as VR7 is progressively increased lower frequencies will be modified. Adjusting VR4 will vary the rate of shifting. Switching on S1 will now introduce phase shifting as well as filter shifting.

#### USE

For the best signal to noise characteristics the input level should preferably be close to, but not greater than, 2.5V r.m.s. The final output of course must not exceed the amplifier requirements. The inherent noise output of the TDA 1022 is typically 0.2mV r.m.s. at a clock frequency of 100kHz. The quality of the phasing effect can be introduced for most music inputs, though it will be most apparent with those having higher harmonic contents or harsher waveforms in the mid to upper octave ranges. The filter shifting effect will be apparent with practically any input music signal and will give further emphasis to the phasing effect when the filter characteristics are set for a low to mid frequency pass range. For normal use three-quarters settings of VR4-7 will usually be best, with VR3 from three-quarters upwards. With the latter much less than about half, the

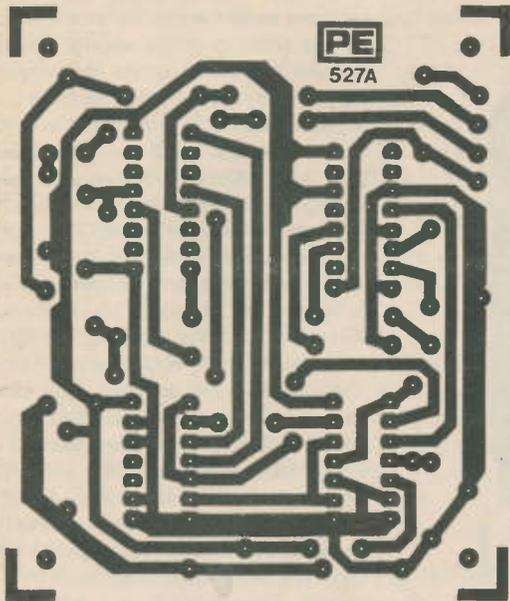


Fig. 6. Delay board p.c.b. (actual size)



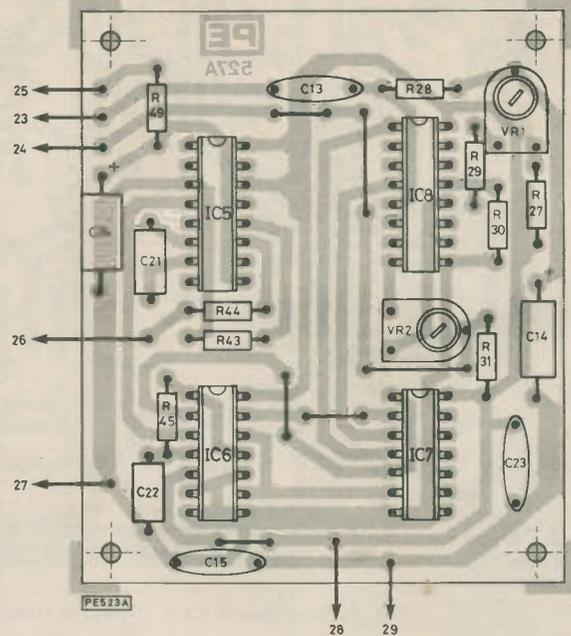


Fig. 7. Delay board component layout

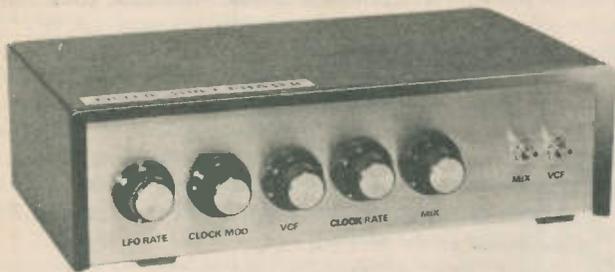

phase cancellation at the mixer stage will be less obvious. The optimum setting is the position where an antiphase signal can completely cancel the original of the same frequency at some point during the shifting cycle. The best position can be determined experimentally and marked on the front panel. By-passing of the effects is achieved by switching off S2, so allowing only the original signal to pass to the amplifier. ★

Fig. 8. Wiring diagram of the Filter Shift Phaser

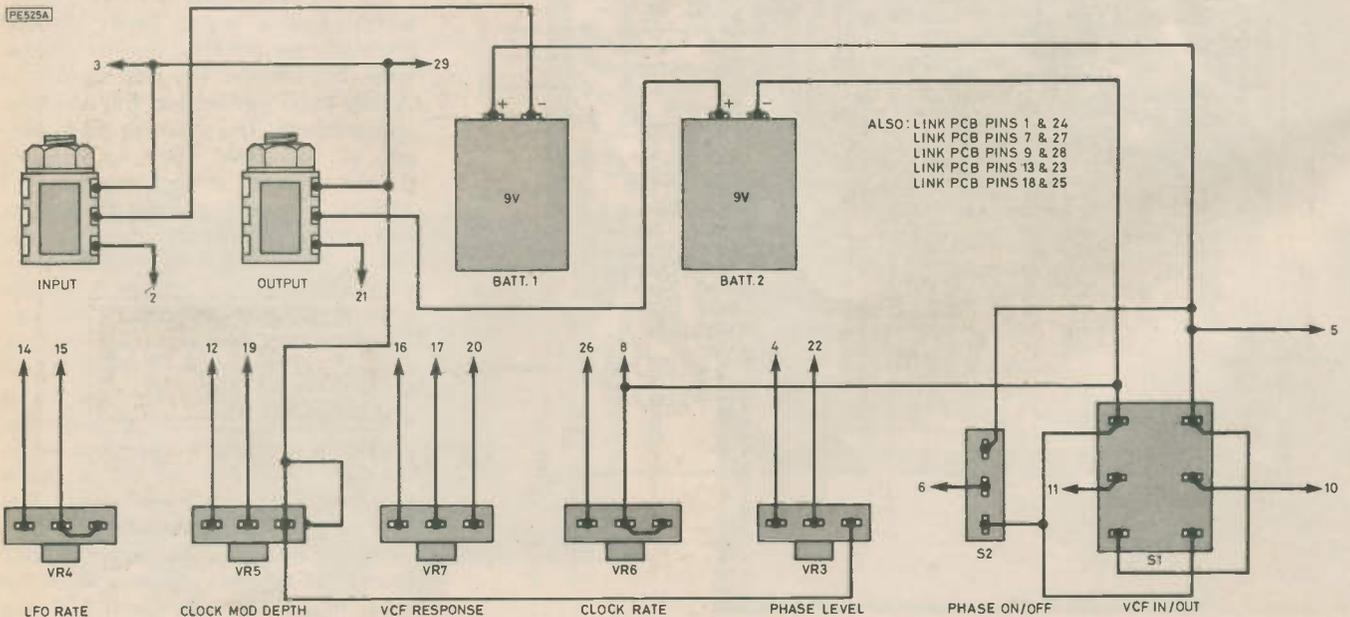



P.E. MONO-STEREO ECHO-REVERB (SEP84) 200ms echo, lengthy reverb, multi-tracking kit as published - BLK box: SET 218 £55.66

## P.E. ECHO AND P.E. PHASER AND OTHER SUPERKITS! FOR BETTER MUSIC AND EFFECTS



P.E. FILTER-SHIFT PHASER (OCT84). Enhanced Phasing with modulated filter shifting. Kit as published - BLK box: SET 226 £39.13

### PANEL CONTROLLED SUPERKITS

	CODE	STD BOX	BLK BOX
BASS BOOST: Increases volume of lower octaves	SET 138B	£8.46	£11.46
BLOW BOX: Voice operated VCF & VCA for fascinating effects	SET 214	£24.33	£28.33
CHORUS UNIT: A solo voice or instrument sounds like more!	SET 162	£31.40	£34.90
COMPRESSOR: Limits & levels maximum signal strength	SET 133	£10.86	£13.86
DIGITAL TO ANALOGUE: 8-bit binary to Lin & Log voltage	SET 176	£23.96	£26.96
ENVELOPE SHAPER: Note triggered ADSR unit with VCA	SET 174	£17.15	£20.85
EQUALISER: Variable combinations of Low, Mid, Top & Notch	SET 217	£22.33	£25.83
EQUALISER: 10 Channels fully variable	SET 134	£37.83	£41.83
FADER: Voice operated with 5 response controls	SET 167	£14.21	£17.21
FILTER: For voice bandwidth enhancement over background	SET 142	£9.23	£12.23
FLANGER: Fascinating music effects, plus phasing	SET 153	£22.74	£26.24
FREQUENCY CHANGER: Tunable note & waveform modifier	SET 172	£34.46	£37.96
FREQUENCY DOUBLER: Guitar octave raiser & tone changer	SET 128	£19.04	£22.54
FREQUENCY GENERATOR: Multisawtooth, 0.4Hz-470KHz	SET 149	£12.40	£15.40
FUNNY-WOBBLE: Modulates a singing voice	SET 91	£10.57	£13.57
FUZZ: Smooth distortion, retains attack & decay	SET 56	£19.73	£22.73
GUITAR OVERDRIVE: Heavy fuzz with selectable qualities	SET 222	£22.81	£25.81
GUITAR SUSTAIN: Extends note decay time, with noise gate	SET 173	£32.87	£36.37
GUITAR TO SYNTH INTERFACE: With voltage & trig outputs	SET 197	£22.69	£25.69
HAND CLAPPER: Auto & manual variable clap effects	SET 156M	£12.03	£15.53
HEADPHONE AMP: 2 watts into phones or speaker, variable	SET 141	£11.26	£14.26
HUM CUT: Tunable mains hum cut filter	SET 150	£23.84	£27.34
JABBERVOX: Voice disguiser with reverb & tremolo	SET 143	£13.81	£16.81
METRONOME: With audio output & visual beat & downbeat	SET 147	£7.13	£10.13
MIC PRE-AMP: Variable gain & switched tone response			
MIXERS: Several in catalogue	SET 213	£19.87	£23.37
MOCK STEREO: Splits mono signal into stereo simulation	SET 189	£57.14	£61.14
MULTIPROCESSOR: Ring, Rub, Fz, Fuzz, Wah, Trem, Vib	SET 177	£16.96	£20.46
MULTIWAVEFORM VCO: Log voltage to frequency, switchable	SET 196	£18.79	£21.79
MUSIC MODULO: 8 variable tremolo & wah guitar effects	SET 121	£12.91	£16.41
MUSICAL CALL SIGN: Programmed call sign generator	SET 145	£9.37	£12.37
NOISE GATE: Reduces tape & system noise	SET 164	£18.40	£21.90
PHASER (SIMPLE): Auto & manual rate & depth controls	SET 203	£25.54	£29.54
REVERB: (SIMPLE) Mono/stereo, variable depth & delay	SET 185	£30.64	£34.64
RHYTHM GENERATOR: Computer driven, 9 drum effects	SET 170	£35.64	£39.14
RHYTHM GENERATOR: 15 pre-programmed rhythms, 9 effects			

BLK BOX - steel & all, black plastic finish. STD BOX - plain aluminium, flipped lid.  
DC BOX - robust diecast. SET codes include PCBs, parts, instructions, boxes, wire, solder.  
More details & kits in catalogue - send S.A.E. (Overseas £1 or 5 IRC's).

RING MODULATOR: Enhances music harmonic modulation	SET 179	£15.76	£19.26
ROBOVOX: Versatile robot type voice modifier	SET 165	£21.03	£24.53
ROGER CALL SIGN: Twin gongs, auto triggered	SET 126	£11.38	£14.38
ROGER CALL SIGN: Single tone auto triggered	SET 127	£3.04	£12.04
SIRENS: Auto triggered by sound or pulse	SET 199	£19.33	£23.43
SIRENS: Manually controlled, constantly varying	SET 151	£13.19	£16.89
SIRENS: Manually variable, incl gun & space type	SET 146	£9.96	£12.96
SPEECH PROCESSOR: Clearer speech and level control	SET 110	£9.60	£12.60
STORMS EFFECTS: Auto & manual wind, rain & surf effects	SET 154	£15.86	£19.36
SWEEP GENERATOR: Auto sine wave 20Hz-15KHz, variable	SET 169	£16.41	£19.91
SYNTHESISER: 2-oct push sw, variable ES, Freq, Shape, Span	SET 182	£39.76	---
TOM-TOM SYNTH: Sound triggered, multivariable	SET 190	£15.05	£18.05
TONE CONTROL: Bass, mid, treble, gain & cut	SET 139	£13.17	£16.67
TREBLE BOOST: Increases volume of upper octaves	SET 138T	£8.13	£11.13
TREMOLO: Mono variable rate & depth modulation	SET 136	£9.71	£12.71
TUNING FORK: 96 note audio/visual tuning aid	SET 46L	£29.38	£32.88
VOLTAGE CONTROLLED FILTER: 12dB, variable modes	SET 178	£17.02	£20.52
VIBRATO: Variable rate & depth of freq shift	SET 137	£23.94	£27.44
VOCODER: Modular vocoder, 7 chans, extendable	SET 152	£34.31	£38.31
VOCODER: Robot type voice modulator	SET 155	£12.44	£15.44
VOICE OP SWITCH: Variable sensitivity & delay	SET 123L	£13.41	£16.41
WAH-WAH: Auto, manual & note triggered	SET 140	£17.26	£20.76
WIND & RAIN: Manually variable effects	SET 28	£9.03	£12.03
WOBBLE-WAH: Oscillator controlled wah-wah, variable	SET 161	£12.60	£15.60

### MATCHED LINKING FOOT SWITCHED STAGE USE KITS

			DC BOX
LINKAFEX CHORUS: Variable rate, depth, intensity, feedback	SET 204		£42.96
LINKAFEX DELAY: Delay 10ms-450ms, plus repeat, feedback	SET 206		£42.09
LINKAFEX DISTORTION: Variable level & tone, v. smooth	SET 209		£23.24
LINKAFEX EQUALISER: Low, mid, top, notch, width, 12dB	SET 216		£25.43
LINKAFEX FLANGE: Variable rate, depth, intensity, feedback	SET 207		£34.92
LINKAFEX MODULO: 8 tremolo & wah effects	SET 211		£24.41
LINKAFEX OVERDRIVE: 4 switchable heavy fuzz effects	SET 215		£25.13
LINKAFEX SUSTAIN: Extends note decay, plus noise gate	SET 223		£26.47
LINKAFEX TONE CONTROL: Bass cut, gain, treble cut, gain	SET 208		£24.09
LINKAFEX PHASER: Variable rate, depth, intensity, feedback	SET 205		£34.33
LINKAFEX NOISE GATE: Auto quiescent noise damper	SET 225		£22.80

Add 15% VAT & £1 P&P to all orders (overseas details in cat).  
Payment CWO, CHQ, PO, ACCESS, VISA, or pre-arranged collection.  
Details correct at press. E&OE. Despatch usually 10-14 days.


**PHONOSONICS, DEPT PE50, 8 FINUCANE DRIVE, ORPINGTON, KENT, BR5 4ED.**  
**Tel: Orpington 37821 (STD 0689, London 66), Mon-Fri 10-7.**

# MAKE THE RIGHT CONNECTIONS !

We have the answer whether you need:

- 0.1" or 0.156" edge connectors
- Two part Euro connectors
- Miniature 'D' connectors
- Ribbon cable connectors (including headers and sockets)

Plus many more

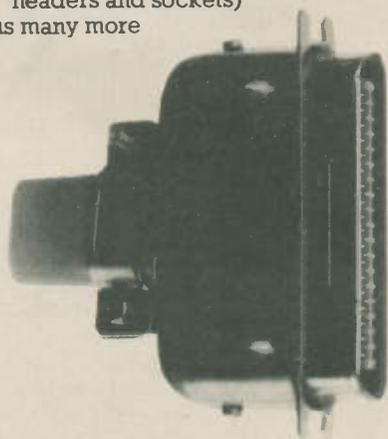

The NEW Delta connector to IEEE 488 specification is now available for either ribbon or round cable connection in both 24 and 36 ways. Metal covers are also available.

For further information on these products and local availability, plus a copy of the 'Hobby Herald', containing the full product range, telephone Chandlers Ford (04215) 62829 or write to:



**BICC-VERO ELECTRONICS LIMITED**

Retail Dept.,  
Industrial Estate,  
Chandlers Ford,  
Hampshire SO5 3ZR.



# SEQUENTIAL LOGIC

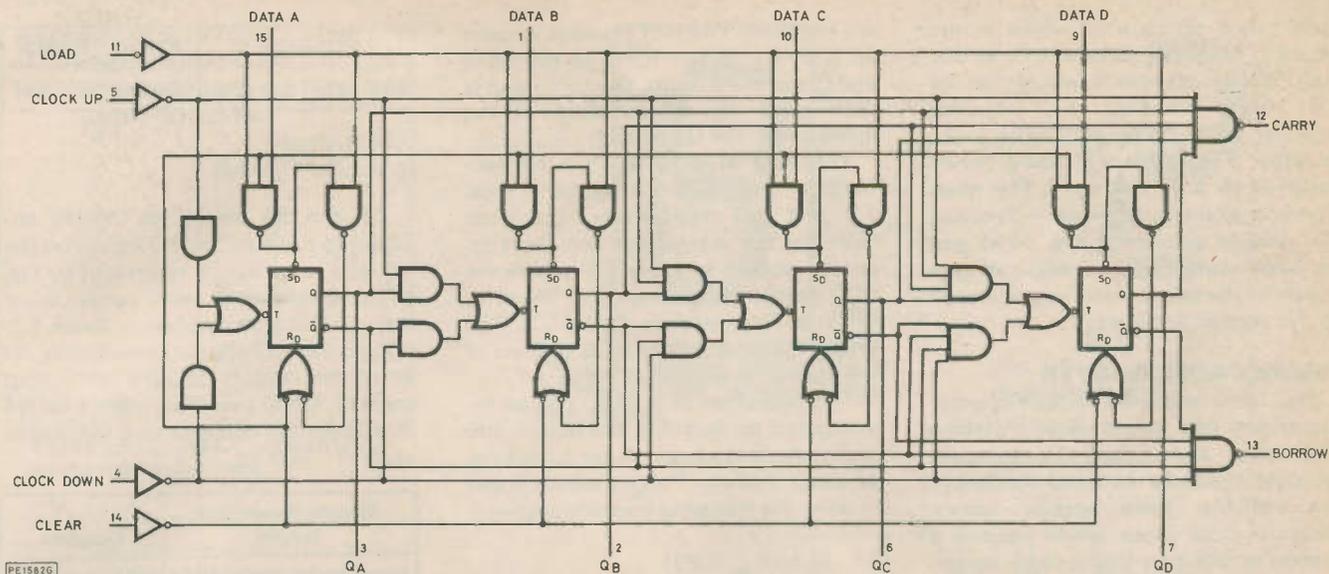


Fig. 1.2. Internal logic of the 74193

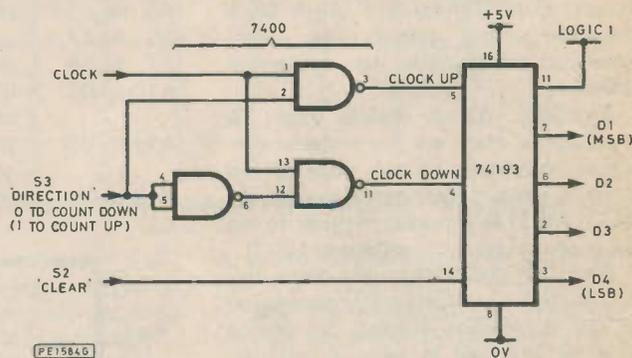
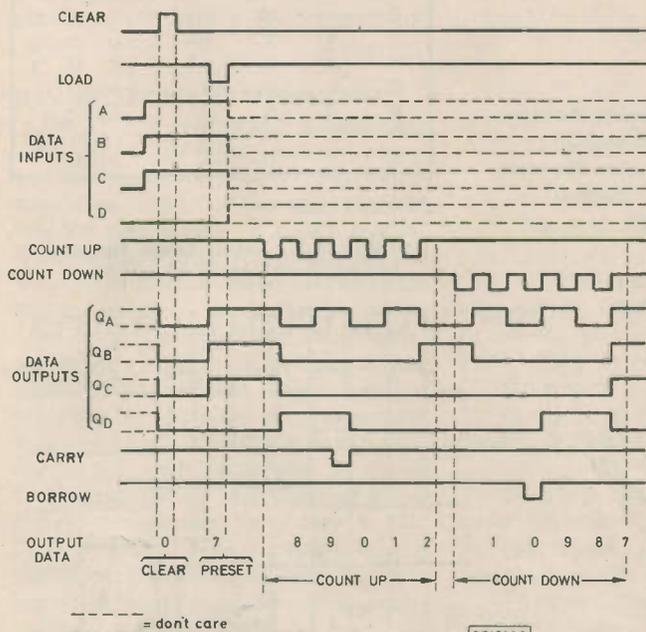


Fig. 1.3 (left). Typical timing diagram for the 74193

Fig. 1.4 (above). Up/down counter using a 74193

The 74193 and 7400 devices should be inserted into sockets C and F respectively. As usual, care should be taken to ensure the correct orientation with pin-1 of each device aligned with pin-1 of the relevant socket. The following links should be made on the Logic Tutor:—

- C2 to D3 (D3 indicates QB)
- C3 to D4 (D4 indicates QA)
- C4 to F13 (clock down)
- C5 to F3 (clock up)
- C6 to D2 (D2 indicates QC)
- C7 to D1 (D1 indicates QD)
- C8 to 0V (common)
- C11 to logic 1 (active-low load input)
- C14 to S2 (S2 clears the counter)

- C16 to +5V (supply)
- F1 to clock
- F2 to S3 (direction control)
- F4 to F5
- F5 to F2
- F6 to F14
- F7 to 0V (common)
- F15 to F1
- F16 to +5V (supply)

With S3 set to give a logic 1 (count up), depress S2 to reset the counter (D1 to D4 will all become immediately extinguished indicating a count of '0000'). After releasing S2, a normal 4-bit binary count will be produced with D1 indicating the most significant bit (MSB) and D4 the least significant bit

(LSB). Readers should confirm that all changes of state take place on the falling edge of the clock input.

On the second counting sequence, allow the count to proceed to, say, '1000' and then depress S3 to generate a logic 0 on the direction input. On the next falling clock pulse, the count should be decremented (to '0111') and should then continue to count down. It should also be noted that, at any time, the output can be cleared by means of S2.

## DECADE COUNTERS

Counters which have ten states in their counting sequence are particularly useful in a number of applica-

# SEQUENTIAL LOGIC

tions, most obvious of which is the counting of digital pulses prior to display. Whilst decade counters can be built using standard J-K bistables together with some additional logic, several TTL devices have been designed to fulfil this need. The most common example of an asynchronous TTL decade counter is the 7490 and we shall continue by investigating a variety of decade counter stages based on this particular device.

## 7490 DECADE COUNTER

The 7490 is a 4-bit decade counter comprising four master-slave bistables internally connected to provide separate divide-by-two and divide-by-five sections. Each section has a separate clock input which causes a change of state on falling clock transitions. Due to internal ripple delays, state changes of the Q outputs do not occur simultaneously and thus decoded output signals are unfortunately susceptible to unwanted spikes.

An AND gated master reset is provided to clear all the bistable elements regardless of the state of the clock. A similar AND gated master set (MS1, MS2) is provided in order to set the output state to nine (binary 1001).

Since the output from the divide-by-two section is not internally connected to the succeeding stages, the device may be operated in various counting modes. In a BCD (8421) counter, the  $\overline{CP1}$  input must be externally connected to the Q0 output. The  $\overline{CP0}$  input receives the incoming count producing a BCD count sequence. In a symmetrical bi-quinary divide-by-ten counter, the Q3 output must be connected externally to the  $\overline{CP0}$  input. The input count is then applied to the  $\overline{CP1}$  input and a divide-by-ten square wave is obtained at output Q0. To operate as a divide-by-two and a divide-by-five counter, no external interconnections

are required. The first bistable is used as a binary divider ( $\overline{CP0}$  as the input and Q0 as the output). The  $\overline{CP1}$  input is then used to obtain divide-by-five operation at the Q3 output.

The internal logic and pin connections for the 7490 are shown in Figs. 1.5 and 1.6 respectively. The truth table for the master set and reset inputs is shown in Table 1.1 whilst the BCD counting sequence (Q0 linked to  $\overline{CP1}$ ) is illustrated in Table 1.2. The timing diagram for the BCD outputs of the counter is illustrated in Fig. 1.7.

The operation of a 7490 can be investigated by inserting the device into socket A of the Logic Tutor (checking, as usual, that pin-1 aligns with A1) and making the following connections:—

- A1 to A14 (CP1)
- A2 to A3
- A3 to S3 (reset)
- A5 to +5V (supply)
- A6 to A7
- A7 to S4 (set)
- A10 to D2 (D2 indicates the state of the Q2 output)
- A11 to D3 (D3 indicates the state of the Q1 output)
- A12 to 0V (common)

- A13 to D1 (D1 indicates the state of the Q3 output)
- A14 to D4 (D4 indicates the state of the Q0 output)

A16 to clock  
(A total of 12 links)

S4 and S3 should be initially adjusted to produce logic 0 inputs on the set and reset inputs respectively. The count should now cycle continuously through the states shown in Table 1.2. A logic 1 on S3 should immediately set all of the outputs to zero (an output state of '0000') whilst a logic 1 on S4 should set the count to nine (an output state of '1001').

Master Reset/Set Inputs				Outputs			
MR1	MR2	MS1	MS2	Q3	Q2	Q1	Q0
1	1	0	X	0	0	0	0
1	1	X	0	0	0	0	0
X	X	1	1	1	0	0	1
0	X	0	1				count
X	0	X	0				count
0	X	X	0				count
X	0	0	X				count

(X=don't care)

Table 1.1. Truth table for the set and reset inputs of a 7490

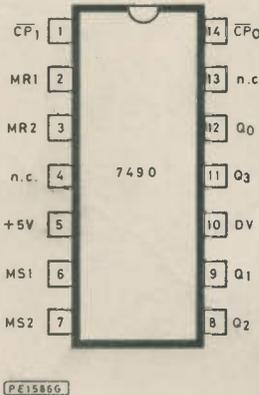


Fig. 1.6. Pin connections for the 7490

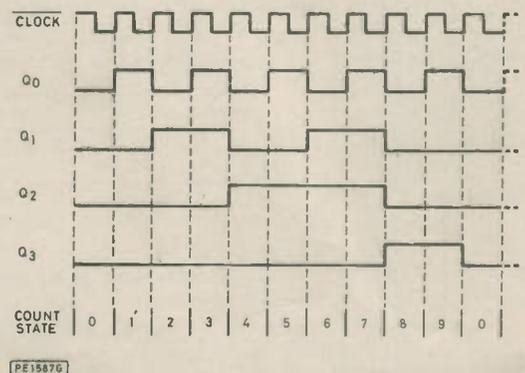


Fig. 1.7. Timing diagram for the BCD outputs of a 7490

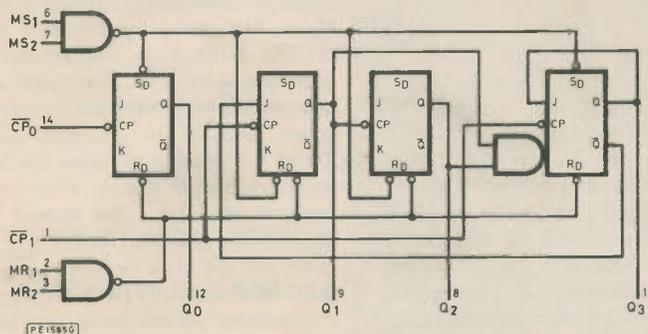


Fig. 1.5. Internal logic of the 7490

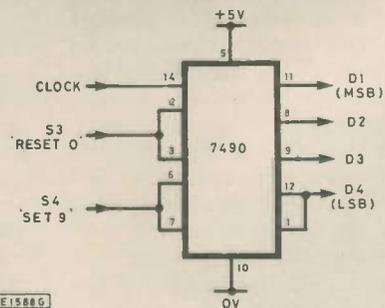


Fig. 1.8. Simple BCD counter using a 7490

COUNT STATE	OUTPUTS			
(I/P clock pulse)	Q3	Q2	Q1	Q0
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1

(Q0 connected to CP1)

**Table 1.2. BCD counting sequence for the 7490**

An obvious disadvantage of this simple decade counter is that the output stage is displayed in binary form, hence we shall now turn our attention to producing a display in conventional denary form.


### SEVEN SEGMENT DISPLAYS

The normal format and pin connections for a common anode seven-segment display is shown in Fig. 1.9. It should be noted that the segments are labelled a to g and that, with a common anode display, it is necessary for these inputs to be taken low in order that the display is illuminated.


In order to illuminate a particular segment, a current of typically 20mA needs to be supplied. This is usually achieved by taking the common anode to the +5V rail, whilst the seven segments are each connected in series with a resistor of 150 ohms or so. A typical arrangement is shown in Fig. 1.10. A logic 1 (high) applied to any particular segment line will not forward bias the i.e.d. concerned into conduction. A logic 0 (low), on the other hand, causes current to flow, the value of current being dependent on the forward characteristic of the i.e.d. and the value of series connected resistance.

Before proceeding further, readers may like to confirm that the seven-segment display is functional by 'hard-wiring' it to produce various patterns. The display used MUST be of the common anode variety (common cathode displays are also available) and should be inserted into the d.i.l. socket marked C on the Logic Tutor. The device should be oriented so that pin-1 aligns with C1 and segment a is uppermost. (Note that pins C8 and C9 are unused).


Rather than use seven individual series connected resistors, a 14-pin

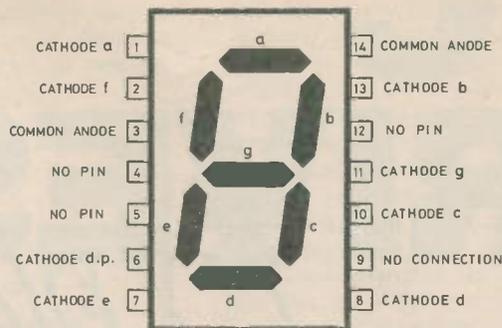

**Fig. 1.9. Normal format for a common anode seven-segment i.e.d. display**

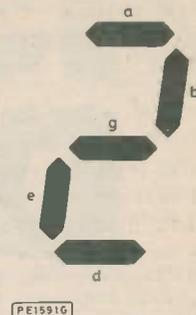

**Fig. 1.11. Typical seven-segment display output**

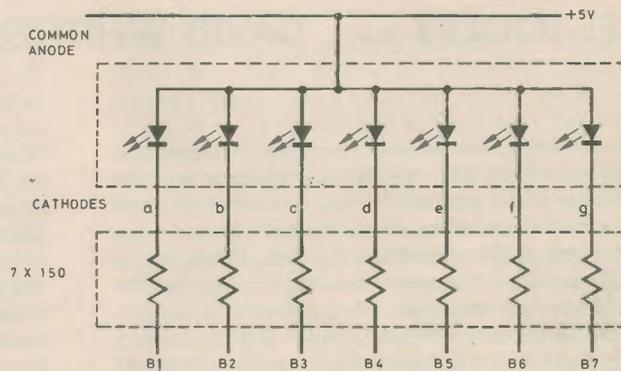

**Fig. 1.10. Typical arrangement for driving a seven-segment i.e.d. display**

d.i.l. 150 ohm resistor network may be employed to limit the segment currents. This should be inserted into d.i.l. socket B, again ensuring that pin-1 aligns with B1. Where readers have difficulty in obtaining such a network, seven 0.25W 150 ohm resistors may be connected from B1 to B16, B2 to B15, B3 to B14, and so on, ending with B7 to B10.

The following links should be made on the Logic Tutor:—

- B16 to C1 (cathode a)
  - B15 to C15 (cathode b)
  - B14 to C12 (cathode c)
  - B13 to C10 (cathode d)
  - B12 to C7 (cathode e)
  - B11 to C2 (cathode f)
  - B10 to C13 (cathode g)
  - C16 to +5V (common anode)
  - C3 to +5V
- (A total of 9 links)

The arrangement now conforms to the circuit shown in Fig. 1.10 in which each segment has its own 150 ohm series resistor terminated at B1 to B7 for segments a to g respectively. Now connect a link from 0V to B1 and check that segment a becomes illuminated, then repeat for each of the other segments in turn.

Having checked that each individual segment of the display is operational, it

is worth demonstrating that we can use the 'hard-wiring' technique to provide any particular indication that we may require. If, for example, a '2' is required, we should arrange for segments a, b, d, e, and g to be illuminated. This is achieved by linking B1, B2, B4, B5 and B7 to 0V. The resulting display should be similar to that shown in Fig. 1.11.

Hard-wiring of displays is fine if the indication is never to be changed. In most practical applications this is not, of course, the case. Usually the display is used to indicate the state of a count and we thus need some arrangement which can accept a binary coded decimal (BCD) input and provide the required decoding logic to illuminate the appropriate i.e.d. segments. Fortunately, several TTI devices are available which are designed to fulfil this particular need.

#### Constructor's Note

Logic Tutor Board p.c.b's, components and constructional details are available from Howard Associates, 59 Oatlands Avenue, Weybridge, Surrey KT13 9SU (0932 42376).

**NEXT MONTH: Decade counters.**

# DISC DRIVES

## *Explained!*

MICHAEL TOOLEY BA

DAVID WHITFIELD MA MSc CEng MIEE

PART 2

LAST month we looked at the basic features of floppy disc drives. This month we continue by looking at some of the options which are often available to buyers. Most of these are not so much a feature of the drives themselves, but more of the way in which they are packaged for sale. If this seems a rather mundane point, it is worth bearing in mind that the difference in price between two 'bare' drives and a twin-drive package can easily exceed £100! Before buying, therefore, it is a good idea to be sure that you are getting all that you need, but not paying for what you neither want nor need.

The 5.25" floppy disc drive packages available today usually (but not always) contain drive units of Japanese origin. High reliability and excellent value for money result from high volume production since this allows the very latest in floppy disc and manufacturing technology to be applied. Indeed, the floppy disc drive market is now so competitive that this must be done in order for the manufacturers to remain in business. Typical drive units currently on the market come from TEC, TEAC, Mitsubishi, Hitachi, Tandon, Canon and Shugart, to name but a few of the more popular makes.

When we are looking for a floppy disc unit to connect to our computer system, we usually want a little more than just the bare drives. We will begin, therefore, by looking at the additional features which may be appropriate for us to consider.

### POWER SUPPLIES

Floppy disc drives are invariably designed to be operated from an external power supply, rather than directly from the mains. Modern drives typically require d.c. power at +5 volts and at +12 volts. The +12 volt supply is normally used to drive the rotational motor, the stepping motor and part of the read/write circuitry. The +5 volt supply, on the other hand, powers the remainder of the read/write circuitry and the logic circuits. Power requirements are now fairly modest; the M4853 half-height Mitsubishi drive, for example, requires 0.5 to 0.7 amps at +5 volts, and 0.5 to 1.0 amps at +12 volts. Supply current requirements, however, continue to fall with the use of more advanced technology. The latest TEAC FD-55 drives, for example, require only 4.9W when operating, and only 1.6W in standby mode.


Some computers have power supplies which are capable

of powering one or two floppy disc drives. The BBC Micro, for example, is capable of supplying external equipment with up to 1.25 amps at +5 volts and 1.25 amps at +12 volts. Thus, we can often use the internal power supply when using discs with the BBC Micro. However, even where the computer is able to supply power for the disc drives, a separate supply is often still preferred. This is because a separate supply keeps the load on the computer's power supply to a minimum, allowing it to run cooler and leaving the spare supply capacity free for other uses. Another advantage of a separate power supply is that it gives the system the greatest flexibility, since the disc unit is then self-contained. Many computers, however, do not offer the option of using the internal power supply, and then we are left to provide an external power supply. The additional cost of a disc power supply will usually be around £30-£40.

Although it is possible to build your own disc drive power supply, it is usually much easier to buy one which has been specially designed for disc drive applications. Power supply units of this type now commonly employ switched-mode designs. These are compact, efficient and light-weight, are usually installed in the case of the disc drive(s), and are almost always capable of powering two 5.25" drives. A point to check in a packaged unit is that the supply is fully wired, complete with a mains switch, fuse and 3-core lead.

If you are putting together your own disc drive package, however, it will be necessary to obtain a suitable power supply. This should preferably be a fully-shrouded unit, but an open-chassis supply may be used provided that all points at mains potential are safely protected to avoid electric shock risk. In addition to the power supply, a two-pole mains switch, warning neon and mains fuse will also be required. The mains lead should be 3-core, and secured to the case with a cable clamp (not knotted!), and protected with a grommet. You will also need to provide d.c. power leads between the power supply and the drive(s). These leads should be suitably rated for the expected maximum supply current, and it will be necessary to obtain the appropriate power connectors to suit the drive(s) being used. Typically the power connector is a 4-pin type, but unfortunately there is little or no standardisation at present. Fig. 1 shows a typical power connector as found on Mitsubishi M4852 and M4853 drives. In addition to the power leads, a further lead is required to securely bond the chassis of each drive to a com-

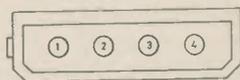mon mains earth terminal; a suitable bonding point is usually provided on the drive's chassis for this purpose. Where a metal case is being used, this should also be bonded securely to the common earth terminal.



- 1: +12V.d.c.
- 2: 0V (+12V RETURN)
- 3: 0V (+5V RETURN)
- 4: +5V.d.c.


**Fig. 1. Mitsubishi disc drive power connector**

## CASES

As we have mentioned, the disc drives produced by the drive manufacturers are bare drives and nothing more. They are produced with a front panel which is usually styled and suitable for mounting in an equipment cabinet or in a case of their own. The basic drive, however, is usually of an open chassis construction, with the electrical connections (disc interface bus and power) at the rear. To prevent the intrusion of foreign bodies (biscuit crumbs, dust, electronic components, children's fingers, etc.) into the delicate workings of the drive mechanics, therefore, a case becomes an essential addition. Any power supply can then also be mounted safely out of harm's way inside the same case.

With the market now increasingly dominated by half-height drives, we usually consider twin-drive arrangements when thinking of cases. This is usually true even if funds dictate that our initial purchase is of one rather than two drives. Adding a second drive to a case bought with this upgrade in mind will usually be neater, easier and cheaper in the long term. Thus we can start with a twin case which is fitted with a single drive (and possibly a power supply), and upgrade to a second drive at a later date.

There is usually a choice of mechanical arrangements for two half-height drives; side-by-side or vertically stacked, as shown in Fig. 2. One arrangement may be more convenient than the other, but either way, the drives themselves are usually mounted horizontally. The side-by-side arrangement can be very convenient if bench space is at a premium; the computer may be situated below a 'perch' which supports the drives, with the monitor/TV on top of the disc unit. This can have the added advantage of raising the monitor/TV to a more comfortable height. Alternatively, the computer may rest on the drives, with the monitor/TV above.

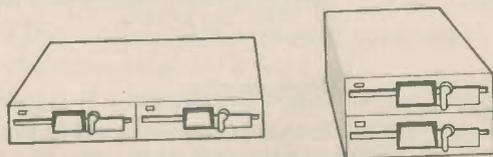

**Fig. 2. Twin drive configurations**

If making your own case, it is important to make sure that adequate ventilation is provided. The amount necessary will depend on the efficiency of the power supply (usually quite high with switched-mode designs, and hence there is little waste heat generated), and the power consumed by the disc drives themselves. Ventilation slots should be carefully positioned to minimise the possibility of unwanted objects falling into them, and they should be small enough to keep out even the smallest of probing fingers. One approach to the problem is to provide slots on the base of the case, with


exit slots on the sides near the top of the case. Provided that the case is then mounted on suitable feet, this arrangement is usually more than adequate. With the very low power drives, it may be possible to dispense with ventilation slots altogether, provided that a metal case is used; waste heat is then removed by conduction. Any case should provide substantial and secure mountings for the drives and power supply. On vertically stacked units, it is usually necessary to provide a heavy gauge spacer bracket to separate the two drives to allow free air circulation.

In conclusion, the disc unit's case should be considered as the first line of defence against the attentions of dirt and the hardships of the computer workplace. It may also affect how easy the drives are to use, and consequently careful consideration should be given to the design of the disc case.

## CABLES

Connecting the newly acquired disc drives to the computer can be an unexpectedly expensive and/or confusing business. If we buy a package tailored for a particular computer, then all this should already have been sorted out by the supplier, but watch out for an additional charge for the cables. Typically a twin-disc cable may cost around £10 to £15, mostly as a result of the cost of the connectors. As for the complete cables themselves, there is often quite some confusion regarding how they should be connected.

The signals on the standard disc interface bus were shown in Table 2 last month. Each of these signals is driven either from the drive to the computer, or from the computer to the drive. The disc interface bus uses open-collector gates for driving these signals, and the general arrangement for each signal is as shown in Fig. 3. The open-collector signals must each be terminated by a resistor at the receiving end (as shown in Fig. 3). If this is not done, the signal on the line swings only a few mV when changing state between logic 0 and logic 1. The bus should, however, only be terminated at one of the drives; the disc manual should indicate how to select whether a particular drive terminates the bus or not.

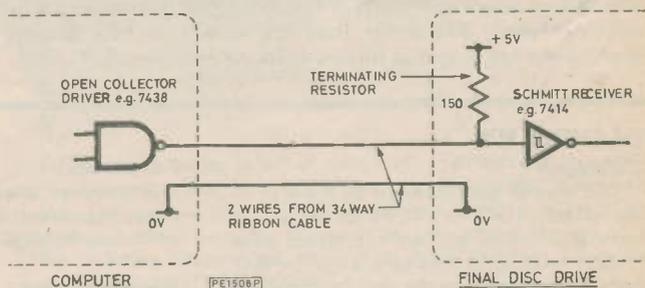

**Fig. 3. Disc interface signal driving**

Each signal in the bus goes to all of the drives connected to the bus, using the so-called 'daisy-chain' arrangement, as shown in Fig. 4. The normal arrangement is to use a flat 34-way ribbon cable, with the appropriate number of drive connectors (usually of the insulation displacement type) fitted at suitable intervals along the cable. The connectors then fit onto the data connectors at the rear of each drive. As already mentioned, the bus should only be terminated once, and this should be done at the drive which is furthest away from the computer, i.e. last on the lead. If buying only a single drive initially, it is worth buying a twin-drive cable, since this will be required eventually and will work just as well with only one drive connected, provided this uses the last connector on the cable.

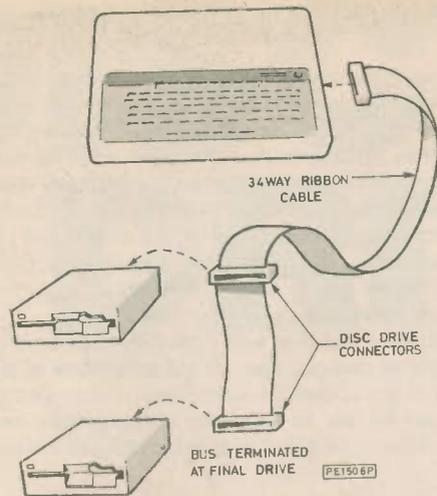


Fig. 4. Daisy-chain disc cable arrangement

At any given instant, only the drive identified by the drive select signals (pins 6/10/12/14) takes any notice of the signals on the bus. The drives must thus each be able to identify themselves. This is normally achieved by setting up links in each drive; a procedure which should be fully described in the drive manual. Needless to say, we can expect that setting two drives to the same identity will cause all manner of problems! Drives are typically numbered starting from zero, and a twin drive unit will thus usually have its two drives set up as 0 and 1. The numbering of the drives does not need to bear any relationship to their physical order of connection on the cable, and can be done purely for our own convenience. It is a good idea, however, to label the drives after set-up, otherwise confusion may well result!

#### OTHER EXTRAS

There are a few remaining points which mustn't be overlooked when completing the shopping list for the disc unit 'package'. Assuming that the computer has already been upgraded, some of the other items needed are:

Blank discs  
Manual  
Formatter

When buying blank discs, it is well worth buying only good quality types. There is nothing worse than losing valuable software due to unreliable discs; learning the lesson of false economy the hard way is no fun! Do not be tempted to use single-sided discs for double-sided applications; although they will usually work satisfactorily, the second side (the top) is not guaranteed to be reliable. A good start is to buy a box of ten double-sided double-density 80-track discs; this will encourage the keeping of backup copies, initially at least, and the discs will be suitable for all future applications. In addition to the discs themselves, it is also a good idea to invest in a suitable disc storage case to protect the discs when not in use.

A manual is essential for getting the maximum benefit out of your floppy disc drives. In addition, it will usually be necessary to refer to the DFS software documentation when setting up for the first time. It is always worth checking that adequate documentation is provided with the drive unit before taking delivery. There is nothing worse than having to make a second trip to collect the missing data, particularly if there is an additional charge involved.

The final item on the list is actually a piece of software; the formatting program. This is often supplied on a disc, itself already formatted, and it must be suitable for your particular computer system. In many cases, the formatter is supplied with the DFS software, but this is not always the case.

#### FINALLY

So, the great day has finally arrived and the floppy disc drives have come to the top of the shopping list. The discussion above and last month's article should allow you to put together a list of points to consider when choosing a drive unit for your system. It is often easier to buy a complete package, but you may prefer to build up your own, at least in part. In either case, make sure you know what you need, and then shop around for the best value. The buyer's guide should help you by providing a selection from the currently available models. The glossary summarises the meaning of some of the terms involved. Next month we shall be reviewing some of the drives mentioned in the buyer's guide.

## GLOSSARY

### Catalogue

The area of the disc used by the disc filing system (DFS or DOS) to record the names, locations and various status information relating to files stored on the disc. Sometimes known as the disc directory.

### Disc interface

The hardware in the computer which provides the interface between the computer's CPU and the disc drives themselves.

### Double density

A method of recording data which uses a higher data rate and the MFM recording technique to double the disc's data storage capacity when compared to single density recording.

### FDC

The Floppy Disc Controller Chip (FDC) is the LSI integrated circuit which is usually at the heart of the disc interface in the computer. The FDC provides most of the detailed control functions in the interface.

### Formatter

A program used to lay down the basic track, sector and catalogue structure on a previously blank disc.

### Head load time

The time taken for the read/write head(s) to be brought into contact and settle on the disc surface. Typically around 50msec.

### Motor start time

The time taken for the rotational motor to run up to full speed (300 r.p.m.) after commanded to do so by the computer. Typically around 250msec.

### Sector

The basic unit of data which is read from or written to a floppy disc is a sector. All data transfers to/from a disc involve one or more complete sectors. A sector, sometimes known as a block, is usually 256 bytes.

### Settling time

The time which must be allowed after a read/write head movement before data may be read or written. Typically around 15msec.

### Single density

The basic method of recording data on the disc surface using FM encoding. This usually provides 2560 bytes on each track.

### Step time

The time taken for the read/write head(s) to move from the current track position to an adjacent track position. Typically a figure in the range 3 to 25msec. Also known as the track-to-track seek time.

### Track

A circular magnetic track laid down on the recording surface of a floppy disc, and used for the storage of data. Typically there are 40 or 80 tracks on one side of a disc.

# DISC DRIVES BUYER'S GUIDE

**T**HIS Buyer's Guide has been designed to show the wide range of disc drive units currently available. The important points to look for when considering which particular drive to purchase are difficult to list in order of importance because they will depend greatly upon your own personal requirements, i.e. in certain cases the physical size may be more important than the actual weight or an integral p.s.u. may be more important than whether the drive is 40 or 80 track.

However, no matter what your own personal requirements are, all the following points should be borne in mind when considering any disc drive to ensure you understand exactly what you are buying:

- 1) *The size of the discs to be used in the drive, i.e. 8in., 5.25in., 3.5in. or 3in.*
- 2) *Whether the drive is a single or dual unit.*
- 3) *If the drives are dual, are they mounted side by side or one above the other?*
- 4) *Is a p.s.u. included or housed separately?*
- 5) *Can your computer's p.s.u. support the drives if a p.s.u. is not supplied?*
- 6) *Is the drive unit cased or not?*
- 7) *Is the drive half or full height?*
- 8) *Is a manual supplied with the drive?*
- 9) *Are the cables and formatter disc supplied and are they compatible with your computer?*
- 10) *Is the drive 40 or 80 track?*
- 11) *What is the capacity of the drive?*
- 12) *What is the physical size and weight and, finally, what is the PRICE?*


Although we cannot cover all these points in our guide we have given as much information as possible, together with addresses and phone numbers where a full specification on the drives mentioned can be obtained. (Prices include VAT).

The Hitachi HFD range from Datafax have unformatted capacities of 500K, 1M and 1.6Mbytes with the HFD510 being a 5.25in. double-sided, half-height, with 80 tracks and a 1Mbyte capacity, priced at £210. The Datafax range also includes the 3.5in. drives from Epson and the 3in. range from Hitachi. Full details from: **Datafax Systems Ltd.**, Datafax House, Bounty Road, Basingstoke, Hants RG21 3BZ. (0256 64187)




The Teac FD55F from Viglen is one of five models in the FD55 series. They are all 5.25in. half-height drives with capacities which vary from 125K to 1.6Mbytes. The 55F is a 40/80 track switchable, double-sided, single drive unit with a 400K capacity and is priced at £225. **Viglen Computer Supplies**, Unit 7, Trumplers Way, London W7 2QA. (01-843 9903)

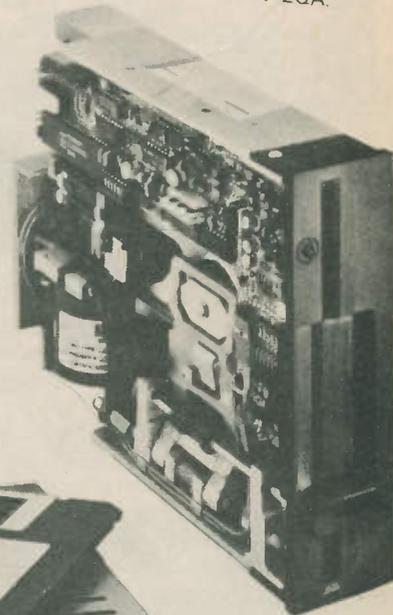The CDC 9428 and 9429 5.25in. half-height disc drives provide 500K or 1Mbytes of storage respectively. The 9428 is a 40 track, double-sided drive (price on application), whilst the 9429 is an 80 track, double-sided, double-density drive (price on application). **Control Data Ltd.**, 179/199 Shaftesbury Avenue, London WC2 8AR. (01-240 3400)



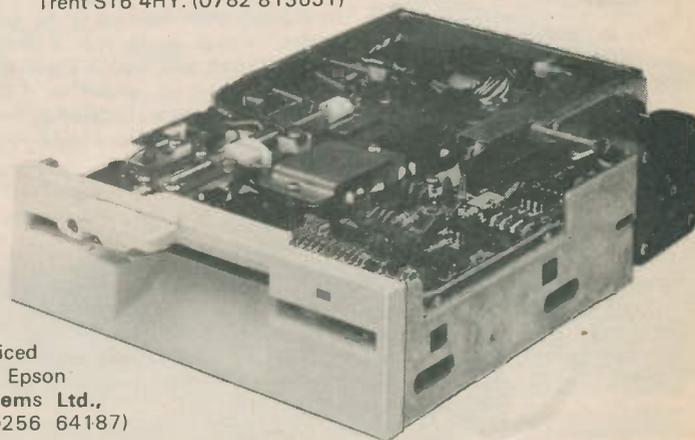The Teac FD35 series of 3.5in. drives from Tekdata are a condensed version of the FD55 series and are fully compatible. There are 8 models in the range offering capacities from 250K to 1Mbyte. The FD35B is a 500K capacity 80 track, double-sided drive, priced at £159. **Tekdata Electronics**, Federation Road, Burslem, Stoke-on-Trent ST6 4HY. (0782 813631)




# DISC DRIVES BUYER'S GUIDE


The Watford Electronics disc drive range includes the CLS 100 which is a cased, single-sided, 40 track, 100K, 5.25in. drive, without a p.s.u.; the CLS 400, a double-sided, 80 track, 400K drive and the CLS 400/S a 40/80 track switchable 400K unit. All three of these units are also available as dual drives and all six units can be supplied with integral p.s.u.'s. Cables are also supplied suitable for use with the BBC micro with all drives.

The prices of the range vary from £115 for the CLS 100 to £395 for the CDB00 which is a cased, dual drive with 800K storage, double-sided, 80 track unit.

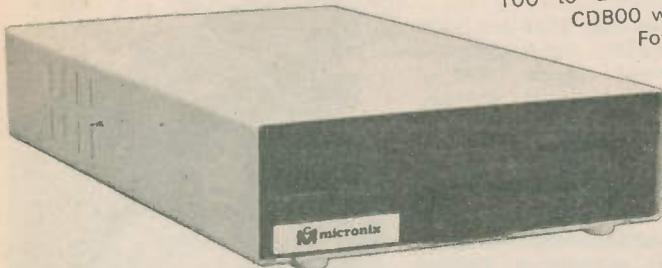
For further details: **Watford Electronics**, Dept PE, Cardiff Road, Watford, Herts. (0923 37774)



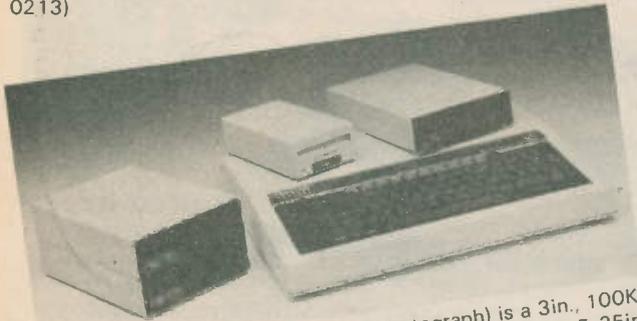
The Micronix range of 5.25in. drives are supplied complete with a DFS manual, formatter disc and disc drive cable. The MX150 is a 100K, 40 track, single-sided drive (£170.20), and the MX151 is a 200K, 40 track, double-sided drive (£216.20); the MX152 is a 400K, 80 track, double-sided drive (£238). **Micronix Computers Ltd.**, Suite 2, 26 Charing Cross Road, London WC2. (01-240 0213)



The Teac FD30A (shown centre in photograph) is a 3in., 100K, single-sided drive, and is fully compatible with Teac's 5.25in. drives. The actual floppy disc used in the 30A is stored in a hard case, not the soft sleeve used by other floppy discs. This makes loading more positive and reduces the disc's susceptibility to damage by handling. The FD30A is priced at £159 and is available from **Viglen Computer Supplies**, Unit 7, Trumpers Way, London W7 2QA. (01-843 9903)

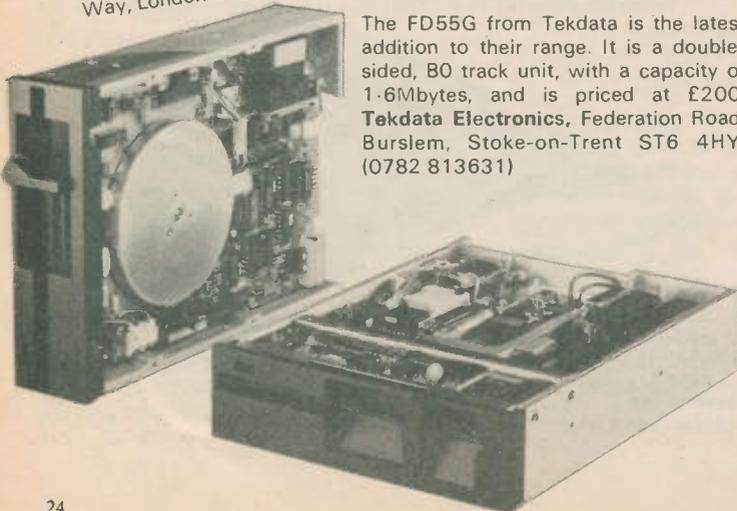

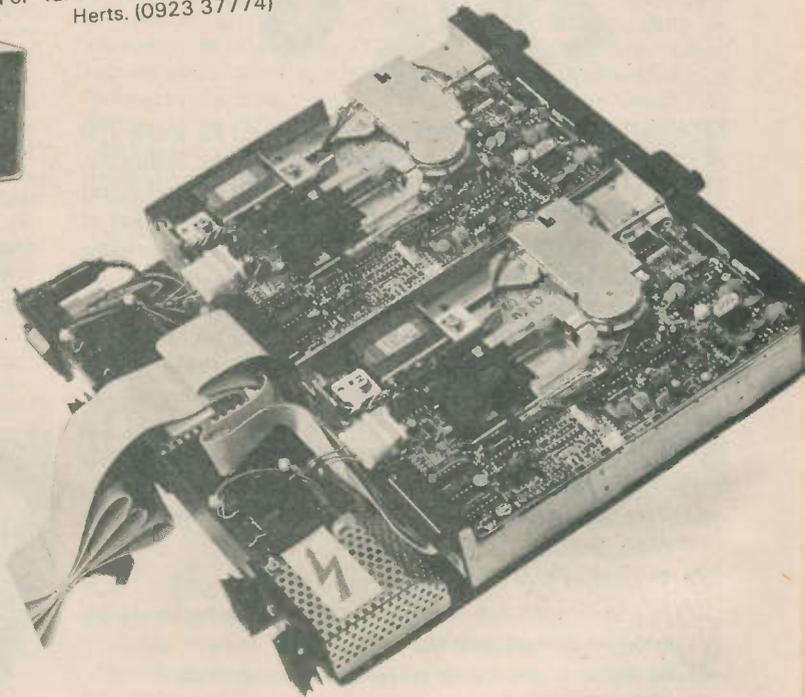The FD55G from Tekdata is the latest addition to their range. It is a double-sided, 80 track unit, with a capacity of 1.6Mbytes, and is priced at £200. **Tekdata Electronics**, Federation Road, Burslem, Stoke-on-Trent ST6 4HY. (0782 813631)



An internal view of the CD400K drive unit from Cumana



The Cumana range of disc drives include the CD200K: a 40 track, single-sided drive with 200K of memory. The CD400K: an 80 track, single-sided drive with 400K of memory. The CD400/S: a 40/80 track, single-sided drive. The CD800/S: a double-sided version of the 400/S; and the CD400/D, a 40 track, double-sided drive with 400K of memory. Prices for the drives vary from £350 to £575. **Cumana Ltd.**, Unit 1, The Pines Industrial Estate, Broad Street, Guildford GU3 3BH. (0483 503121)

MAIL ORDER MICROS

# SALES DRIVE!

Check these crazy deep-cut VAT-INCLUSIVE prices and see how much you save

Make no mistake, these are the very latest half-height drives from TEAC — world leaders in high performance, high reliability 5¼ inch\* floppy disk technology. They come complete with Formatting Disk, User Manual, Case, and Cables for direct connection to the Model 'B' with DFS disk interface and with a FULL TWELVE MONTH GUARANTEE.


If you've got a BBC Model 'B' with DFS disk interface, you'll never get another chance like this to add disk storage. But ACT NOW, this unrepeatable offer is only available while stocks last.

\*3 inch versions also available; please ring for details.
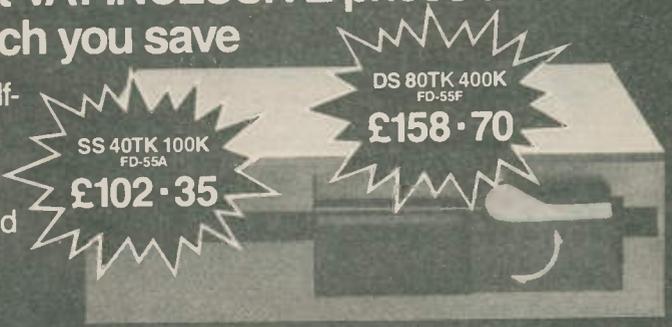
## HOW TO ORDER

Fill in the coupon below; enclose your cheque, made payable to Mail Order Micros, or complete the Access/Barclaycard details if you wish to pay by credit card; and post to: MAIL ORDER MICROS, 2a GREEN STREET, SANDBACH, CHESHIRE, CW11 9AX. Telephone 0782 811711.

Enquiries from Dealers and Educational Authorities welcomed.



SAVE £66.70 TO £81.65 ON SINGLE DRIVES



SAVE £118.45 TO £181.70 ON DUAL DRIVES

SINGLE DRIVES		Our previous price (VAT Inclusive)	NOW (VAT Inclusive)	QTY	TOTAL
FD-55A	SS 40TK 100K	(£169.05)	£102.35		
FD-55B	DS 40TK 200K	(£205.85)	£124.20		
FD-55E*	SS 80TK 200K	(£198.95)	£129.95		
FD-55F*	DS 80TK 400K	(£240.35)	£158.70		
DUAL DRIVES					
FD-55A	SS 40TK 200K	(£319.70)	£201.25		
FD-55B	DS 40TK 400K	(£389.85)	£241.50		
FD-55E*	SS 80TK 400K	(£374.90)	£241.50		
FD-55F*	DS 80TK 800K	(£458.85)	£297.85		
DUAL DRIVES (with integral power supply)					
FD-55A	SS 40TK 200K	(£428.95)	£289.80		
FD-55B	DS 40TK 400K	(£499.10)	£331.20		
FD-55E*	SS 80TK 400K	(£486.45)	£332.35		
FD-55F*	DS 80TK 800K	(£569.25)	£387.55		
Post and packing (first unit)			£ 5.75		£ 5.75
Post and packing (each additional unit)			£ 2.50		
			<b>TOTAL £</b>		

Post to: MAIL ORDER MICROS, 2a GREEN STREET, SANDBACH, CHESHIRE, CW11 9AX.

I enclose cheque for \_\_\_\_\_

Please debit my ACCESS/BARCLAYCARD (delete whichever not applicable)

Card number \_\_\_\_\_

Signature \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

\_\_\_\_\_

Credit card orders must be signed by the card holder; address above must be the same as the card holder.

\*Price includes 80/40 Track Switch

2a Green Street Sandbach Cheshire CW11 9AX



MAIL ORDER MICROS

Telephone 0782 811711

# SECURITY

Assemble and install your own system and save pounds

# SECURITY

## A COMPLETE SECURITY SYSTEM FOR ONLY £39.95 + V.A.T.



contains:  
Control Unit  
Enclosure & mechanical fixings  
Key Switch & 2 keys  
LED's  
5 1/2" Horn Speaker  
4 High quality surface mounting Magnetic Switches

CA 1250  
HW 1250  
KS 3901  
LED1  
HS 588  
MS 1025

With only a few hours of your time it is possible to assemble and install an effective security system to protect your family and property, at the amazingly low cost of £39.95 + V.A.T. No compromises have been made and no corners have been cut. The outstanding value results from volume production and direct supply. Assembly is straight forward with the detailed instructions provided. When installed you can enjoy the peace of mind that results from a secure home. Should you wish to increase the level of security, the system may be extended at any time with additional magnetic switches, pressure pads or ultrasonic sensors. Don't wait until it's too late - order today. Order code: CS 1370

## EXTENDED SYSTEM CS 1480 Price £62.50 + V.A.T.

This system contains, in addition to the CS 1370, an ultrasonic detector type US 5063 + its enclosure, an additional horn speaker and a further 2 magnetic switches. This system represents outstanding value for money for the high level of security provided. Order Code: CS 1480

## SELF-CONTAINED ULTRASONIC ALARM UNIT CK 5063 only £37.00 + V.A.T.



Requires no installation. Easily assembled using our professionally built and tested modules.

- Adjustable range up to 25ft.
- Built-in entrance and exit delay
- Built-in timed alarm
- Key operated switch - Off, Test and Operate
- Provision for an extension speaker
- Fully self-contained
- Uses US 5063, PSL 1865, Key Switch 3901, 3" Speaker 3515

Now you can assemble a really effective intruder alarm at this low price using tried and tested Riscomp modules. Supplied with full instructions, the kit contains everything necessary to provide an effective warning system for your house or flat. With a built-in LED indicator and test position the unit is easily set-up requiring no installation. It may simply be placed on a cupboard or desk. Movement within its range will then cause the built-in siren to produce a penetrating 90db's of sound, or even 110db's with an additional speaker. All parts included and supplied with full instructions for ease of assembly. Size 200 x 180 x 70mm. Order as CK 5063

## ALARM CONTROL UNIT CA 1250



Price £19.95 + V.A.T.

The heart of any alarm system is the control unit. The CA 1250 offers every possible feature that is likely to be required when constructing a system whether a highly sophisticated installation or simply controlling a single magnetic switch on the front door.

- Built-in electronic siren drives 2 loud speakers
- Provides exit and entrance delays together with fixed alarm time
- Battery back-up with trickle charge facility
- Operates with magnetic switches, pressure pads, ultrasonic or I.R. units
- Anti-tamper and panic facility
- Stabilised output voltage
- 2 operating modes full alarm/van't tamper and panic facility
- Screw connections for ease of installation
- Separate relay contacts for external loads
- Test loop facility

## HARDWARE KIT HW 1250



only £9.50 + V.A.T.

This attractive case is designed to house the control unit CA 1250, together with the appropriate LED indicators and key switch. Supplied with the necessary mounting pillars and punched front panel, the unit is given a professional appearance by an adhesive silk screened label. Size 200 by 180 by 70mm

Add 15% VAT to all prices  
Add 70p post and packing to all orders  
Units on demonstration  
Shop hours 9.00 to 5.30 p.m.  
Closed Wednesday  
Saturday 9.00 to 1.00 p.m.  
SAE with all enquiries  
Order by telephone or post using your credit card

## SIREN & POWER SUPPLY MODULE PSL 1865



only £9.95 + V.A.T.

A complete siren and power supply module which is capable of providing sound levels of 110db's at 2 metres when used with a horn speaker. In addition, the unit provides a stabilised 12V output up to 100mA. A switching relay is also included so that the unit may be used in conjunction with the US 5063 to form a complete alarm.

## POWER SUPPLY & RELAY UNIT PS 4012 Price £4.95 + V.A.T.

Provides stabilised 12V output at 85mA and contains a relay with 3 amp contacts. The unit is designed to operate with up to 2 ultrasonic units or 1 infra-red unit IR 1470.

## SIREN MODULE SL 157

Produces a loud penetrating sliding tone which, when coupled to a suitable horn speaker, produces SPL's of 110db's at 2 metres. Operating from 9-15V. Price £2.95 + V.A.T.

## 5 1/2" HORN SPEAKER HS 588

This weather-proof horn speaker produces extremely high sound pressure levels (110db's at 2 metres) when used with the CA 1250, PS 1865 or SL 157. Price £4.95 + V.A.T.

## 3-POS. KEY SWITCH 3901

Single pole, 3-key switch intended to use with the CA 1250. Price £3.43 + V.A.T.

## MAGNETIC SWITCH MS 1025

Surface mounting superior quality. Price £1.17 + V.A.T.

## US 4012 ULTRASONIC MODULE

Basic low cost ultrasonic detector suitable for wide range of movement detection applications featuring 2 LED indicators and having adjustable range 5-25ft. Price £10.95 + V.A.T.

## DIGITAL ULTRASONIC DETECTOR US 5063



only £13.95 + V.A.T.

- 3 levels of discrimination against false alarms
- Crystal control for greater stability
- Adjustable range up to 25ft
- Built-in delays
- 12V operation

This advanced module uses digital signal processing to provide the highest level of sensitivity whilst discriminating against potential false alarm conditions.

## ULTRASONIC MODULE ENCLOSURE

only £2.95 + V.A.T.

Suitable metal enclosure for housing an individual ultrasonic module type US 5063 or US 4012. Supplied with the necessary mounting pillars and screws etc. For US 5063 order SC 5063; for US 4012 order SC 4012.

## INFRA-RED SYSTEM IR 1470 only £25.61 + V.A.T.



Consisting of separate transmitter and receiver both of which are housed in attractive moulded cases, the system provides an invisible modulated beam over distances of up to 50ft. operating a relay when the beam is broken. Intended for use in security systems, but also ideal for photographic and measurement applications. Size 80 by 50 by 35mm.

## RISCOMP LIMITED

Dept PE22  
21 Duke Street,  
Princes Risborough,  
Bucks. HP17 0AT.  
Princes Risborough (084 44) 6326

# WINCHESTER'S, FLOPPIE'S ????

## 8", 5 1/4" OR SUB 5 1/4" - 3 1/2" OR 3"

WHATEVER YOU REQUIRE IN THE DISC DRIVE LINE - RING US. WE PROBABLY MANUFACTURE AND DISTRIBUTE THE WIDEST RANGE OF DISC DRIVES IN THE COUNTRY. SEND FOR A FULL BROCHURE NOW, WHICH INCLUDES A RANGE OF OVER 40 O.E.M. DRIVES. ALSO 5 1/4" & 3" DRIVES FOR THE BBC, DRAGON, TANDY TRS 80 AND SPECTRUM (WITH OUR NEW INTERFACE FOR THE SPECTRUM HOME COMPUTER)

5 1/4" 1-5 Evaluation Prices  
1MB £149.00  
500k £119.00  
250k £95.00

TOSHIBA & CHINON DRIVES Also available EPSON, TEAC etc



3 1/2" 1-5 Evaluation Prices  
1MB £175.00  
500k £145.00  
250k £125.00

EPSON or CHINON



UK'S BEST QUANTITY PRICING AVAILABLE ON REQUEST

WE CAN SUPPLY ALL TYPES OF CABLES & CONNECTORS FOR DISK DRIVES. RING NOW!

ALL TYPES OF MEDIA AVAILABLE 8", 5 1/4", 3 1/2" & 3"


WE POSSIBLY MANUFACTURE AND DISTRIBUTE THE WIDEST RANGE OF DRIVES IN THE COUNTRY. RING FOR BROCHURE NOW!

SOME OF OUR RANGE OF DRIVES


EPSON, 5 1/4", 3 1/2"  
TOSHIBA, 8", 5 1/4"  
HITACHI, 5 1/4", 3"  
CHINON, 5 1/4", 3 1/2", 3"  
NEC, 8"

**datafax**  
**systems ltd**

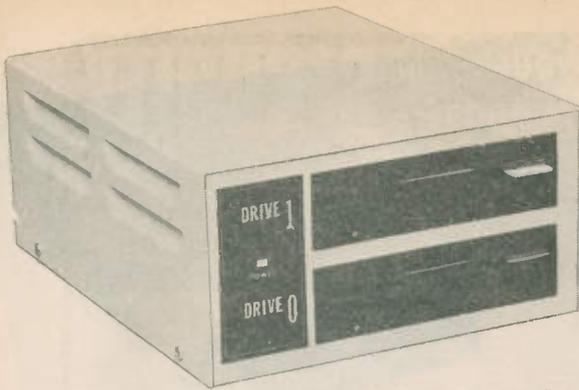
(0256) 64187 DATAFAX HOUSE,  
BOUNTY ROAD, BASINGSTOKE,  
HANTS RG21 3BZ. Telex 268048



The CD55FS from Technomatic is a 5.25in. dual drive disc unit with a maximum 800K storage (2 x 400K switchable drives), incorporating double-sided discs. Each drive is separately switchable between 40 track and 80 track via a hardware switch. This unit has a built-in p.s.u. with mains switch and is supplied with a manual, formatter disc, connector cables and a 13A mains plug. Price £483; **Technomatic Ltd.**, 305 Edgware Road, London NW10. (01-723 0233)

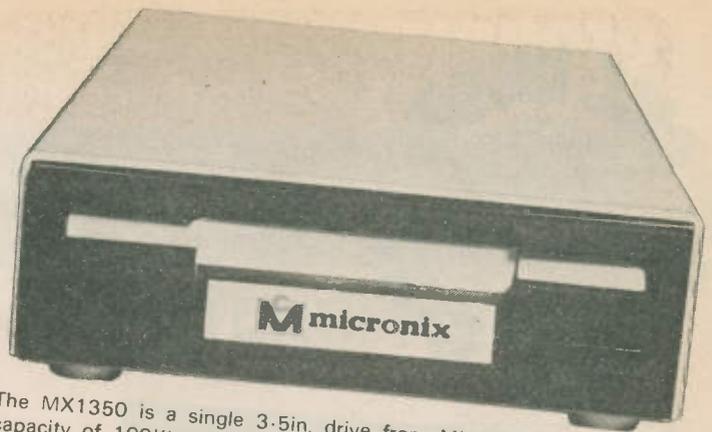


The MX1350 is a single 3.5in. drive from Micronix, it will provide a capacity of 100Kbytes of storage; a dual unit, the (MX2350) is also available with a 200Kbyte storage capability. Both these units are 40 track and are single-sided, and are boxed in metal housings, supplied complete with power cable, disc drive cable, formatter disc and DFS manual. Prices respectively are £181.70 and £353.05. **Micronix Computers Ltd.**, Suite 2, 26 Charing Cross Road, London WC2. (01-240 0213/0217)

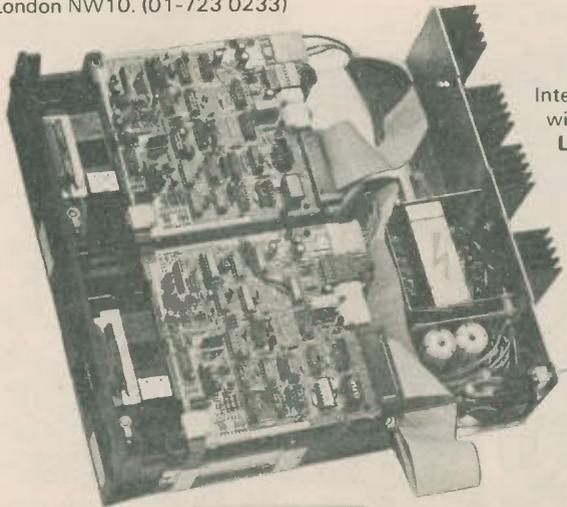

Internal photograph of the Cumana full-height unit with integral power supply. **Cumana Ltd.**, Unit 1, The Pines Trading Estate, Broad Street, Guildford, Surrey GU3 3BH. (0483 50312)




The TRK1 from Tech OP Ltd is a dual 5.25in. drive unit offering 800Kbytes storage on 80 track, single-sided discs. The TRK2 will provide 1600Kbytes of storage using 80 track, double-sided discs. These half-size units are supplied with full documentation, all connectors and a formatting and utilities disc for BBC B micros. Prices respectively are £275 and £349. **Tech OP Ltd.**, 19 Rodney Road, Cheltenham. (0242 570999)

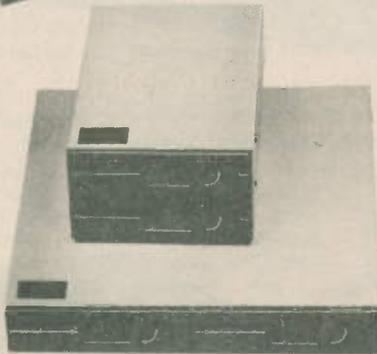


Mail Order Micros supply a range of twelve disc drives for use with the BBC micro. The units are available with integral p.s.u.'s in dual stacked or dual flat versions or, without a p.s.u. in a dual stacked version. All versions are supplied with formatting/utility disc and manual. Disc capacities are from 200K, 40 track, single-sided drives to 800K, 80 track, double-sided units. **Mail Order Micros**, 2a Green Street, Sandbach, Cheshire CW11 9AX. (0782 811711)

The HFD 305's from Datafax have been designed for use with the new 3in. compact floppy disc by Maxell; two units are available in this range—the 305(S) a single drive and the 305(D) a dual drive. Storage capacity is from 125Kbytes (single density—single drive) to 500Kbytes (double density—dual drive). Supplied with formatter disc, cables and manual, these units are respectively priced at £155 and £180. **Datafax Systems Ltd.**, Datafax House, Bounty Road, Basingstoke, Hants RG21 3BZ. (0256 64187)

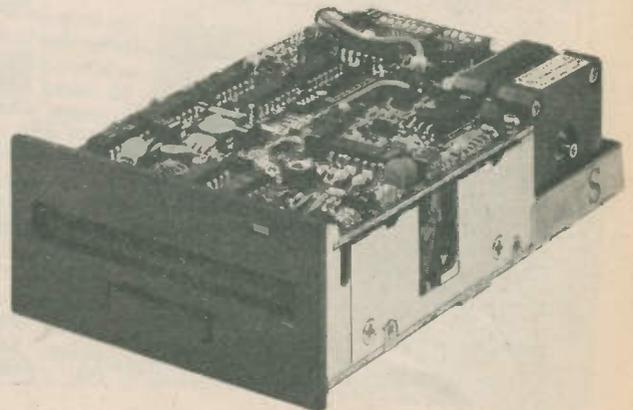

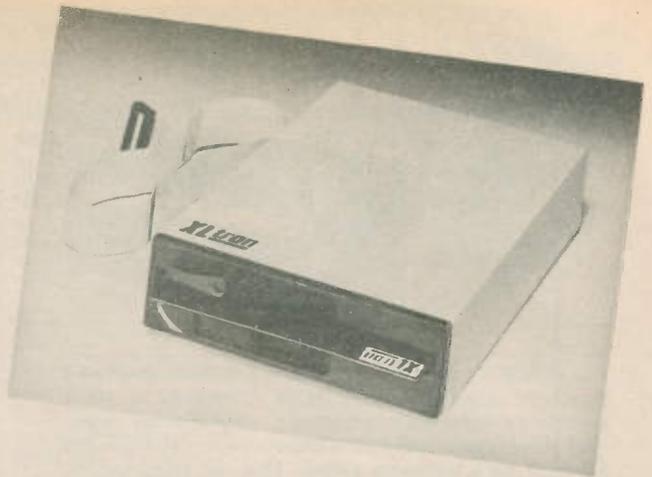
# DISC DRIVES BUYER'S GUIDE


The XLtron drive is a BBC compatible, half-height, single or double-sided drive complete with an interconnecting cable and manual. The single drive is priced at £150, and the double-sided drive at £166. Disco Technology Ltd., 20 Orange Street, London WC2H 7ED. (01-930 1612)



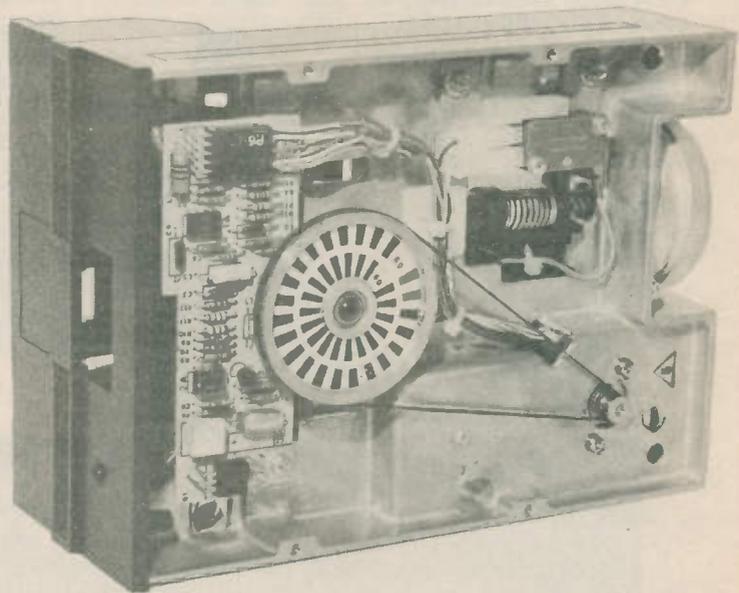
The 3in. drives from Mail Order Micros are available in single or dual units. They are supplied with leads and connectors, formatting/utility disc and a manual. The drives can be powered from the p.s.u. of the BBC micro. The single drive has 80 tracks and a 200Kbytes capacity, whilst the dual drive has a 400Kbytes capacity. Mail Order Micros. (Address below.)



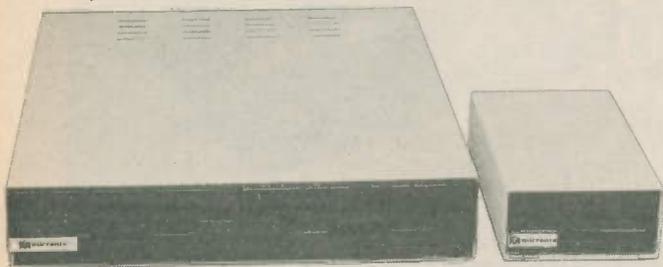
An internal view of a standard height disc drive showing the drive belt arrangement. (Courtesy of Cumana Ltd.)



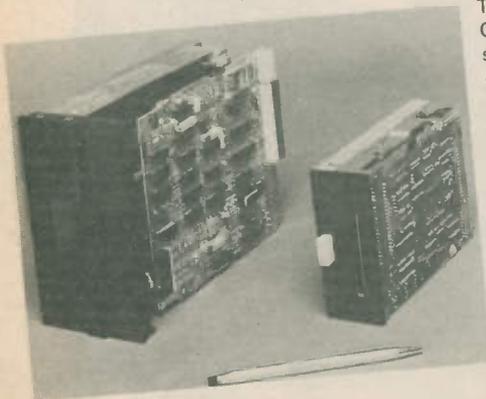The MX252 from Micronix is an 800K dual, 5.25in., 80 track, double-sided drive, priced at £492. It is shown alongside the MX-130 which is a 100K 3in. single-sided, 40 track unit, priced at £181.70. Both units are supplied complete with drive cables, formatter and DFS manual. Micronix Computers Ltd., Suite 2, Charing Cross Road, London WC2. (01-240 0213)



The Shugart SA300 from Mail Order Micros is 3.5in., single-sided microfloppy drive with 40 tracks and 500K memory capacity. The drive is compatible with 5.25in. units and is available in either a single or dual drive configuration. A formatter, instruction manual and connecting cables are supplied. The single drive is priced at £102.35, and the dual unit at £201.28. Mail Order Micros, 2a Green Street, Sandbach, Cheshire CW11 9AX. (0782 811711)

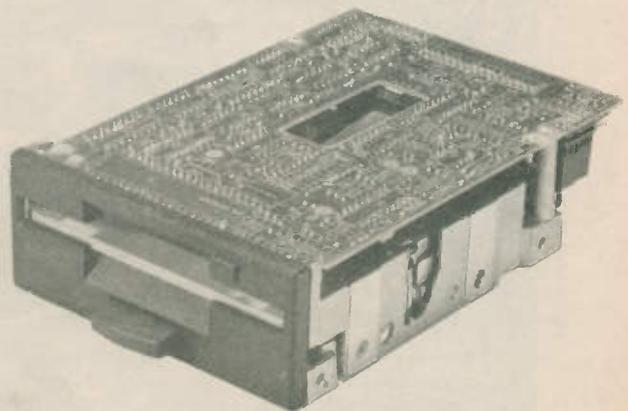

The 350 1Mbyte floppy disc drive from Shugart is a 3.5in., double-density, single drive unit with 80 tracks. The drive is supplied complete with a formatter disc, manual and interconnecting leads. Mail Order Micros. (Address left.)

# MICRO-BUS

## and MICROPROMPT

Appearing every month, Micro-Bus now presents ideas, applications and programs for the most popular micro-computers and all micro-related projects so far published in PE. Ideas must be original, and payment will be made for any contribution featured.

### SPECTRUM "CLOUSEAU"

Sir—"Clouseau" is a cheap, reliable, extremely sensitive, acoustic burglar alarm system for the ZX Spectrum. Clouseau requires no soldering, and, in the case of the BASIC system, no knowledge of electronics. Clouseau works by taking the input from the EAR socket, and checking to see if there is any noise indicating, perhaps, a burglar.

Clouseau can also be used as a baby minding device, indicating when the baby, being monitored, makes any noise.

Clouseau is extremely sensitive, and networks of microphones can be set up, allowing more than one room to be monitored at a time.

The IN command on the Spectrum is used for reading the values at the Spectrum's I/O ports. These are not merely for the connections on the back edge-connector of the computer, but also for reading data from the keyboard, and EAR connector.

The value from the EAR socket is read with the line:

```
LET A = IN 65022
```

The value at the EAR socket is determined by what the computer can hear at the socket. When there is no noise at the connection, a value of 255 is returned. However, if there is any noise at all, the value read will be different.

It is, by connecting a system of leads, amplifier, tape recorder, and microphones to this connector, that a simple, but very sensitive Burglar Alarm/Child Minder experiment can be constructed.

For the basic system of one monitoring station, you will need:

The set-up shown in Fig. 1, and run the program with the tape recorder in RECORD mode. To do this, without a tape in, you will need to manually press down the erase protection detector tab at the rear left hand corner of the cassette receptacle.

More microphones can be added in series or parallel, but Ohm's law must be followed. If the original resistance is 8 ohms, then the final resistance of the microphone network must be 8 ohms.

A suitable sound amplifier can be purchased from many high street outlets, or

the hi-fi system may be used.

The microphone with your cassette recorder will do. Most are compatible, but, just in case, check in your cassette recorder manual. The extra lead can be bought from specialist electronic shops or by mail order. The amplifier is required to make the Spectrum's BEEP loud enough to be used as an alarm.

The program gives an e.c.g. type print-out of the trace from the EAR socket, on the T.V. screen. The alarm sounds when any noise is heard. A time delay is included so that you can set the alarm, and leave the room before the system activates. The sensitivity depends upon the volume setting of the cassette recorder.

David Harrison,  
Burgess Hill,  
West Sussex.

```
10 REM _____
20 REM _____
30 REM _____ CLOUSEAU _____
40 REM _____
50 REM _____
60 REM _____ Intruder Alarm V 1.0 _____
70 REM _____
```

```
80 REM _____
90 REM © David Harrison 1983 _____
100 REM _____
```

```
110 BORDER 0: PAPER 0: INK 7: 8
RIGHT 1: FLASH 0: CLS
120 GO SUB 280
130 LET A=100
140 PLOT 0,A
150 FOR N=0 TO 252 STEP 2
160 LET EAR=(IN 65022)/2
170 DRAW 2, A-EAR
180 IF EAR <> 255/2 THEN GO SUB 2
20
190 LET A=EAR
200 NEXT N
210 CLS : GO TO 130
220 REM HEARD A NOISE
230 FLASH 1: INK 2: BORDER 2:
PAPER 2: INK 7: CLS
240 PRINT AT 8, 0; "
INTRUDER"
250 PRINT AT 12,0; "ALERT"
260 BEEP 1.5, 45
270 GO TO 260
280 REM TIME DELAY
290 INPUT "Time Delay in Seconds"; TD
300 PAUSE TO*50
310 RETURN
```

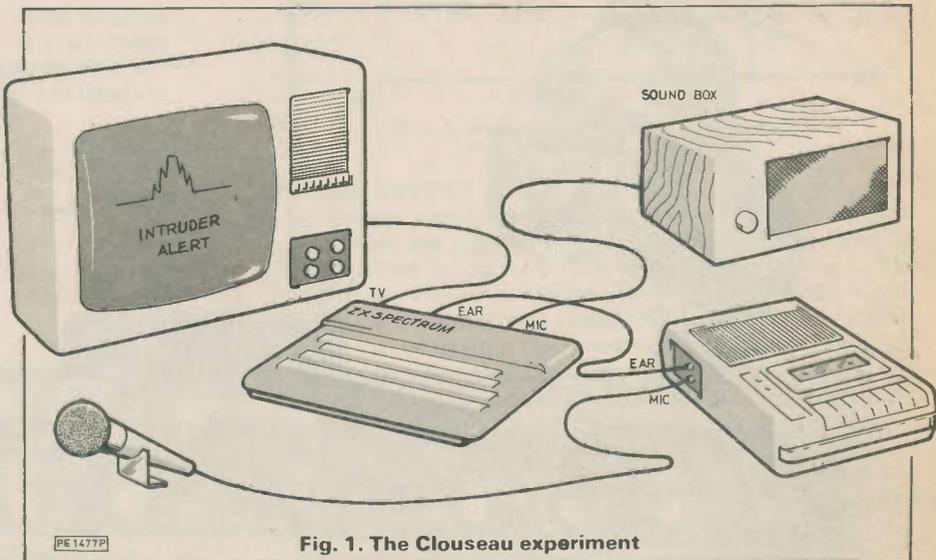


Fig. 1. The Clouseau experiment

# Radar Security Alarm

## Part One

A DESIGN BY POWERTRAN CYBERNETICS

INTRUDER alarm systems fall into several distinct categories as far as the actual detection is concerned. These can be summarised generally as follows:

### a) HARD WIRED

Hard wired systems where doors, windows and other entry points are wired to a central control unit. Magnetic switches and magnets, either surface mounting or flush mounting types, are positioned so that the contacts break as the door or window is opened. Pressure mats may also be placed at strategic points on stairs or landings. These are normally open contact devices where the pressure of a person's foot will make the contact.

### b) ULTRASONIC

These sensors are usually self contained in one small box which can be conveniently mounted high on a wall covering the area to be protected. Ultrasonic sound waves are generated in one head and a similar head 'listens' to the sound pattern generated within the protected area. If the pattern remains constant no output appears from the receiver head and associated electronics. If a disturbance occurs in the protected area the received signal changes and the change is amplified and used to trigger the alarm circuit. The ultrasonic system is very sensitive and is affected by draughts or anything causing air movement.

### c) INFRA-RED

#### i) Active Infra-Red

An infra-red emitter is arranged within a housing for its energy to be collimated by a lens to provide a narrow beam. An infra-red detector in a similar housing is positioned to intercept the transmitter beam, thus providing a signal all the while the beam remains unbroken. The system can be made very robust and is suitable for inside or outside use. The beam is invisible and unaffected by sunlight or other outside influences and responds instantly to passage of an object through the beam. The transmitter and receiver can be mounted in the same housing with energy transfer accomplished using an optical reflector of the multi face type similar to a cycle reflector.

#### ii) Passive Infra-Red

The Passive infra-red detector uses a pyro-electric element of doped ceramic, sensitive to infra-red (heat) radiation. This produces an electrical output when there is a change in the amount of infra-red radiation striking the sensitive area. Physically, the detector, in its wall-mounted housing, 'looks' at the area of coverage through an infra-red filter and an infra-red opaque grid which has the effect of allowing infra-red radiation from objects within 'windows' to fall on the detector. If an infra-red source (intruder) passes across these windows the detector plays 'now you see me, now you don't' with the result that the intruder causes several sudden changes in the level of radiation reaching the detector any of which are used to trigger the alarm system.

### d) RADIO DETECTION

This usually takes the form of a module emitting radio energy in the 10 Giga Hertz region. The active element is a Gunn diode in a self-oscillating circuit which is tuned by the cavity in which it is located. The energy is directed to the area to be protected by the antenna and an adjacent cavity contains the detector diode. This, in a similar manner to the ultrasonic unit, reacts to movement within the protected area by producing an output from the detector at the Doppler fre-



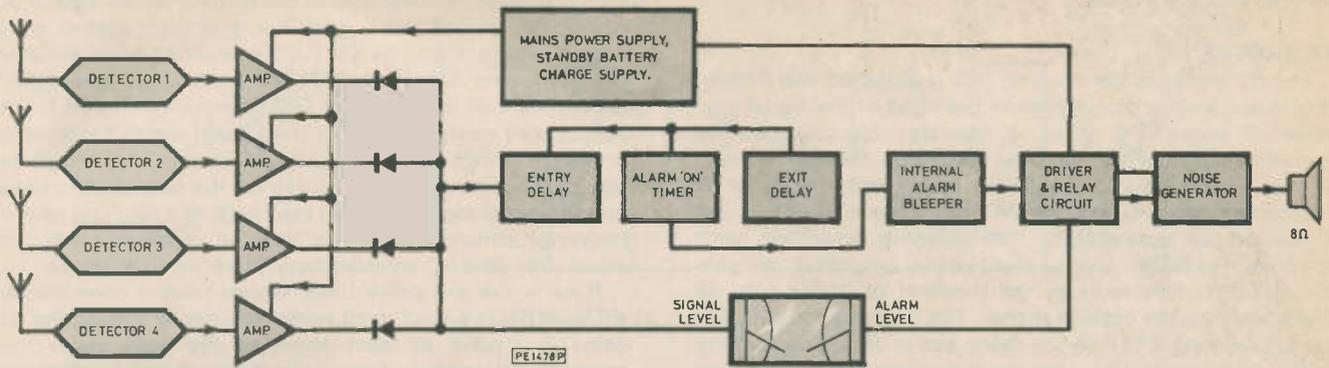


Fig. 1. Schematic diagram of the complete unit

quency caused by the movement of the intruder.

The system described here is a Doppler Radar Alarm which can be made by the home constructor from readily available components.

### HOW IT WORKS

The oscillator frequency is generated on the oscillator (lower) printed circuit board and radio frequency energy is transferred to the detector (upper) board by the proximity of the two loops. One end of the upper loop is connected to the system ground (0 volts) and the other end is connected directly to the antenna. The mid point of the antenna loop is connected via the detector and diode D101, to C104. If the transmitted energy is represented by  $P_t$  and energy reflected from nearby objects back to the antenna is represented by  $P_r$  then the signal presented to the detector is the vector sum of  $P_t + P_r$  where the frequencies are the same but the relative phases are different, hence a steady d.c. level appears across C104. If a moving target enters the area an additional component within  $P_r$  appears at the detector due to the Doppler frequency shift. It is this shift which causes the d.c. level on C104 to vary at a frequency equal to the difference between the transmitted signal and the reflected signal—which for a man size target moving at 1 m.p.h. (1.5 feet per second) is about 1 cycle per second. Hence under steady state conditions the detected d.c. level will not pass through the a.c. coupled signal amplifier but the 1 Hz Doppler signal will.

### UHF OSCILLATOR

The critical frequency determining components of the

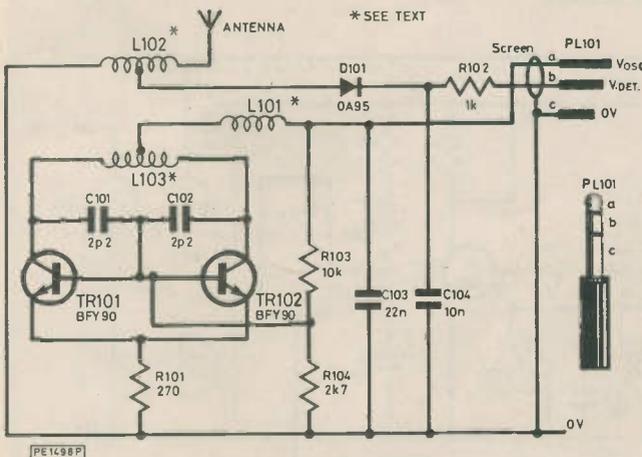


Fig. 2. Oscillator/Detector circuit

UHF oscillator are formed by the printed circuit wiring. The dimensions of the main centre tapped loop form the tuned circuit for the oscillator. The transistors are BFY90 devices which oscillate satisfactorily at the working frequency. The remaining components are feedback and decoupling capacitors and biasing resistors.

The antenna pick-off coil is positioned on a second p.c.b. mounted parallel to the oscillator board and spaced by nuts on the mounting screws. A tapping on the antenna loop is fed to the detector and filter circuit. The complete oscillator/detector unit is coupled to the control box using miniature 2 core screened cable. Up to four detectors can be accommodated by the control box and each detector has its own amplifier and hence the sensitivity of the system is individually controlled on the front panel of the control unit.

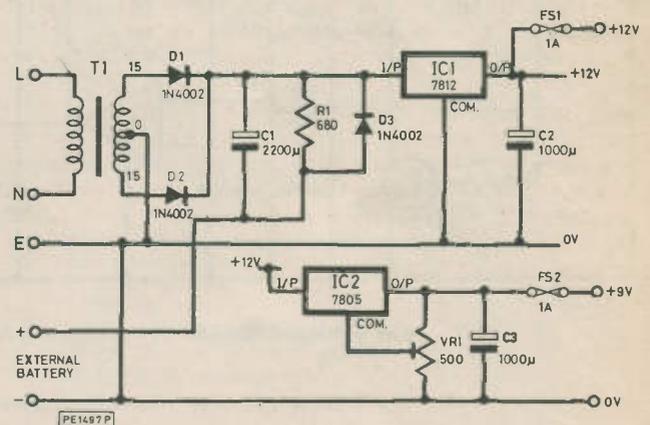


Fig. 3. Power Supply circuit diagram

### POWER SUPPLY

A toroidal transformer is used to derive the low voltage supply from the mains. The mains plug should be fused at 3 amps. This is the only fuse in the primary side of the transformer. The centre tapped secondary is full wave rectified by D1 and D2 and smoothed by C1. R1 is a trickle charge resistor to keep the external back up battery charged. In the event of mains failure the battery will supply the circuits via D3. IC1 provides 12 volts and IC2 provides 9 volts (adjustable by VR1). The 9 volt (nominal) powers the signal amplifiers and the oscillator detector units.

The oscillators are powered via R105 (R205 etc.) and VR1 is adjusted to give a voltage at the junction of R105 and D107 of 8 volts. At this voltage level, D107 will not conduct and D108 in the collector of TR103 will be off.

Should the 2 core cable to the detector be broken the voltage on D107 will rise above 8.2 volts and TR103 conducts to indicate a break.

### RF SIGNAL

The RF signal in the antenna coil is detected and filtered to give a standing d.c. voltage at the input of the signal amplifier of about 1.5 volts. A moving object within the operating range of the detector will cause this d.c. level to change at the Doppler frequency which is of the order of 1 cycle per second. The two 741 operational amplifiers are connected as conventional non-inverting amplifiers with selective feedback giving appreciable reduction of gain above 20Hz. This reduces the problem of mains pick up whilst keeping the circuits simple. The output from IC102 is a.c. coupled via C110 to the diode pump circuit comprising D103, D104 and C111. Low leakage capacitors are required throughout the signal amplifier and tantalum bead types are satisfactory. A moving target within the range of a detector produces a low frequency signal and continued movement 'pumps up' the voltage of C111, this voltage in turn causes the Darlington pair TR104, TR105 to conduct and D109 lights, indicating a moving target. As TR105 collector goes low the signal level is indicated on the VU meter, ME1a.

The earthy side of the VU meter is the signal summing line from all the detectors and if any one goes low IC3a timer is triggered. This is the entry delay timer and the length of delay is controlled by VR2.

When the entry timer IC3a is triggered, pin 5 goes high. The positive going edge is differentiated by C5 and D4 with no net change in the status of pin 8 IC3b. At the end of the entry delay period pin 5 goes low and the negative going edge is differentiated by C5, R3 the resulting pulse initiating the alarm time 'ON' timer IC3b. When this is triggered pin 9 IC3b goes high and turns on TR3 energising relay RL1. One pair of relay contacts connect the 12 volt supply to the noise generator circuit comprising IC5a, IC5b and TR4. A separate pair of relay contacts is available on the rear of the control unit for switching an external load such as a latching relay or contactor controlling a flood light or an electric bell. The alarm 'ON' time is controlled by VR3 on the front panel.

IC4a is the exit delay timer whose time is controlled by VR2b (VR2 is a dual gang potentiometer to ensure the exit delay is always at least equal to the entry delay thus preventing triggering of the alarm during the exit period).

The only switch on the front panel is the ALARM ON-OFF switch. When the alarm is switched to the 'OFF' position, pin 6 is grounded causing the output pin 5 to be high. This causes TR2 to conduct with the collector low. The collector is connected to the RESET pins 4 and 10 of IC3a and b thus keeping the entry timer and alarm timer inhibited during the exit period. The alarm signal from pin 9 IC3b also drives TR1 emitter follower. The emitter of TR1 is connected to pin 10 of IC4b. This is connected as an astable timer whose output drives the internal piezo electric bleeper, to give an audible indication that the alarm has been triggered.


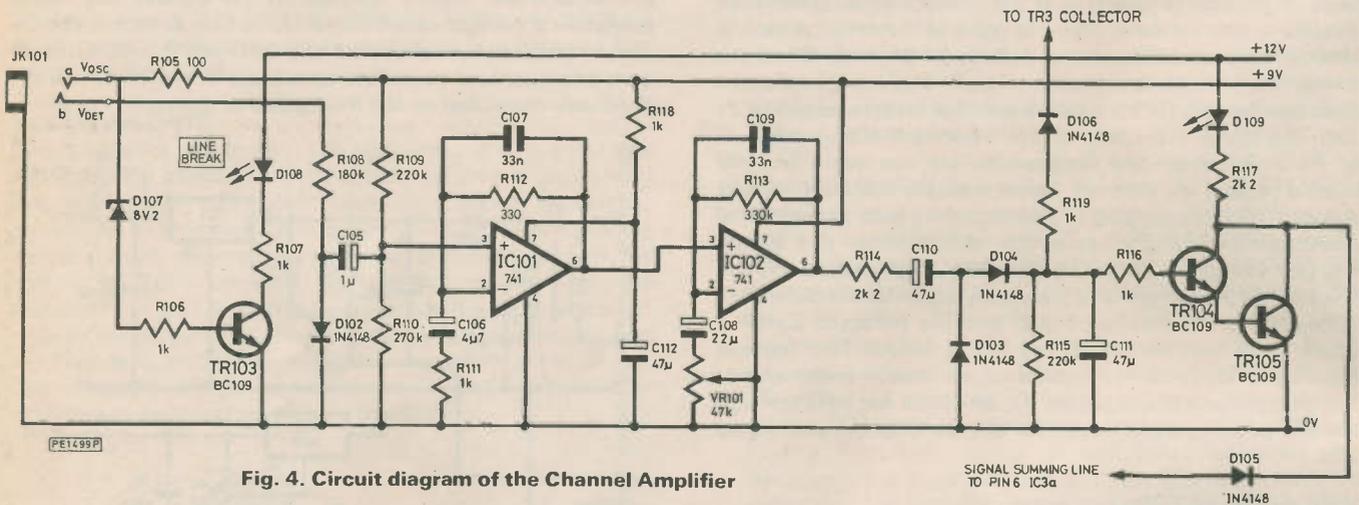


Fig. 4. Circuit diagram of the Channel Amplifier

Fig. 5. Circuit diagram of the Timing and Delay circuits

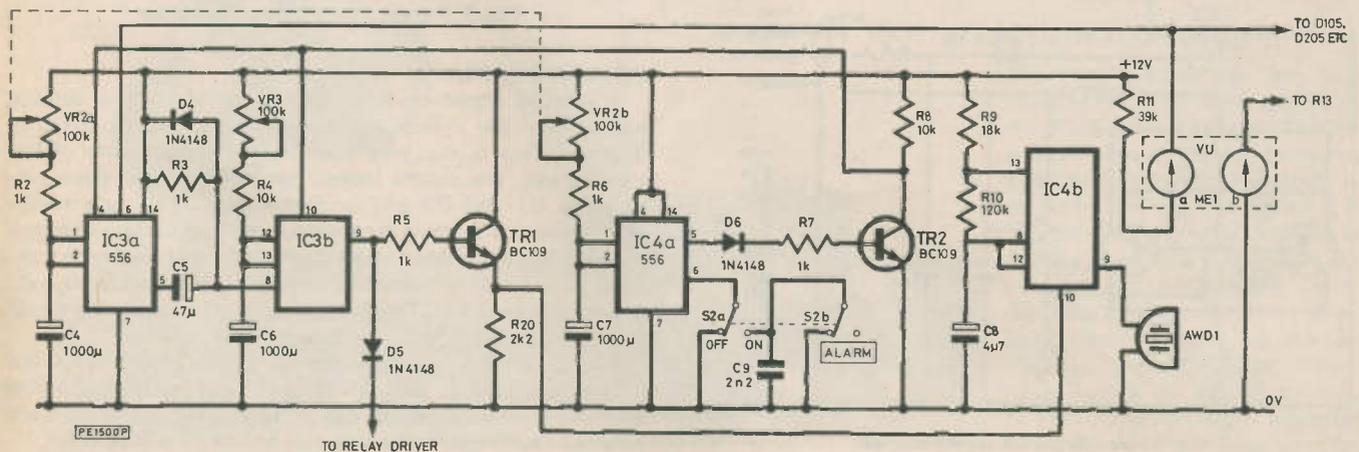

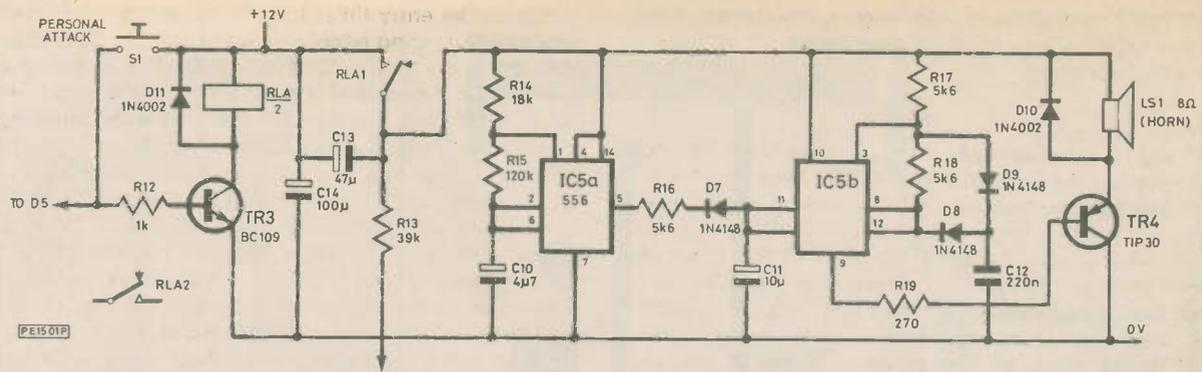


Fig. 6. The Noise Generator circuit diagram

## NOISE GENERATOR

The Noise Generator uses a dual timer i.c. which produces a wailing high level sound in an 8Ω re-entrant horn loud-speaker. The output from pin 9 drives a *pn-p* power transistor with the loudspeaker forming the emitter load. The main printed board has an area of copper strips at one end. This is provided to allow extra components to be added if required such as a thyristor and associated components to switch an external load.

The junction of D5 and R12 to +12V is a suitable point to insert personal attack buttons. As the system is powered all the time mains is connected, the PA button will activate the siren as soon as it is operated. If the base connection of TR3 is brought out to the rear panel, this, together with the BATT-VE terminal, forms a useful point for remotely disarming the alarm simply by shorting the base to ground via a

suitable keyswitch. It is important to use the base of TR3 rather than the PA connection on the left hand side of R12 because, if the PA button is pressed while the alarm is switched off at the remote key switch position, a short circuit will appear across the supply.

The only part of the system on the outside of the building is the siren and its enclosure. A high degree of security is obtained if the cable supplying the horn enters the enclosure through the rear of the box straight through the wall so that no cable is exposed. Further protection is afforded if 4 core cable is used with a reed switch/magnet assembly between the lid of the enclosure and the fixed part. The reed switch should be arranged to make contact if the lid containing the magnet is removed. The resulting contact pair is arranged to parallel the PA wiring as described earlier.

## COMPONENTS . . .

### OSCILLATOR/DETECTOR UNIT

Oscillator/Detector unit and signal amplifier.

**NOTE** The 4 oscillator/detector units and the 4 signal amplifiers are all identical. The electronic components have a prefix of 100, 200, 300, 400. Only the components of channel 1 are listed.

#### Resistors

R101	270
R102, R106, R107, R111, R116,	
R118	1k (6 off)
R103	10k
R104	2k7
R105	100
R108	180k
R109, R115	220k (2 off)
R110	270k
R112, R113	330k (2 off)
R114, R117	2k2 (2 off)

All resistors  $\frac{1}{4}$ W 5%

#### Potentiometer

VR101	47k lin (panel mtg)
-------	---------------------

#### Capacitors

C101, C102	2p2 ceramic (2 off)
C103	22n
C104	10n
C105	1µ 35V tant
C106	4µ7 10V tant
C107, C109	33n 400V polycarb (2 off)

C108	22µ 16V tant
C110, C111	47µ 6.3V tant (2 off)
C112	47µ 10V elect

#### Semiconductors

D101	OA95
D102-106	1N4148 (4 off)
D107 8V2 Zener	BZX61
D108 green i.e.d.	TIL 220
D109 red i.e.d.	TIL 220
TR101, TR102 transistor	BFY90 (2 off)
TR103, TR104, TR105 transistor	BC109 (3 off)
IC101, IC102 op.amp.	741 (2 off)

#### Miscellaneous

Oscillator P.c.b.  
 Detector P.c.b.  
 Base Plate cover assy.  
 Telescopic Antenna  
 Grommet  
 Insulator  
 Antenna Fixing Screw M3 PH 30mm  
 P.c.b. mounting screws M3 CSK 20mm (3 off)  
 P.c.b. antenna fixing nuts M3 (17 off)  
 Cable min 2 core + screen 10 metres  
 0.25 in. Jack plug 3 Pole  
 Antenna adaptor  
 M3 15mm PH  
 TIL Grommet and clip (8 off)

Fig. 7 (right). The P.c.b. assembly and component layout of the Detector board

Photographs showing the internal and external view of the Oscillator / Detector unit


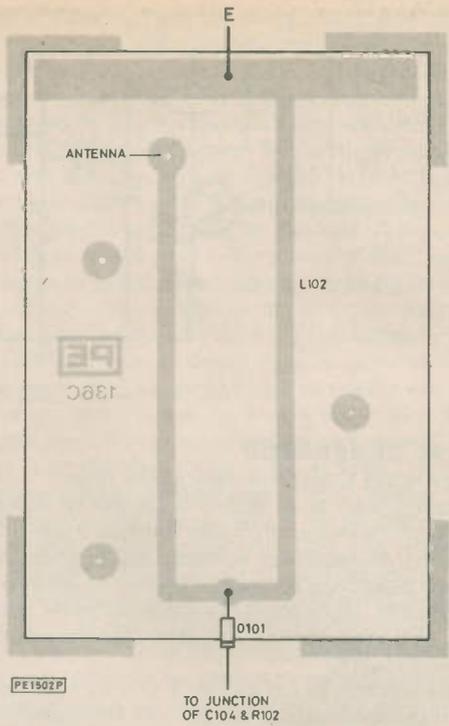
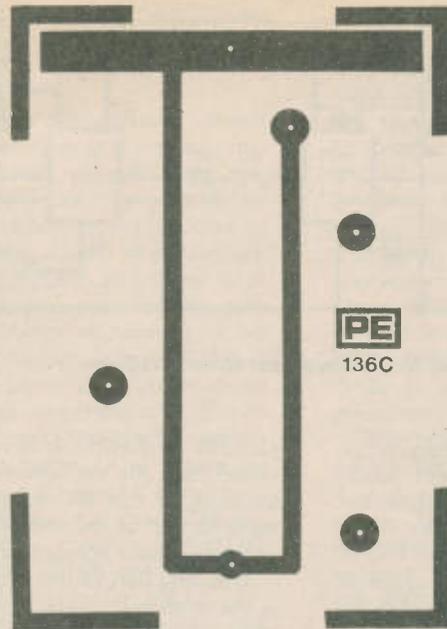
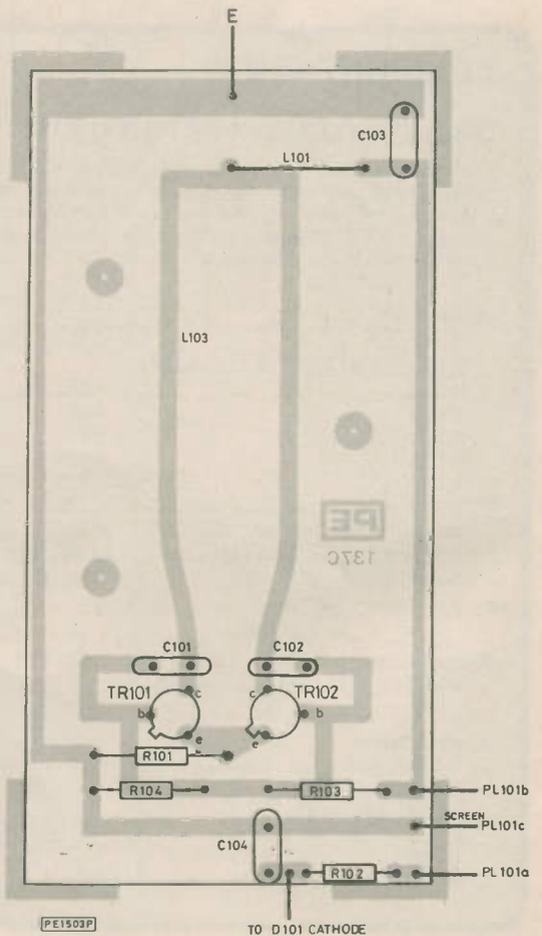


Fig. 8 (below). The P.c.b. and component layout of the Oscillator board

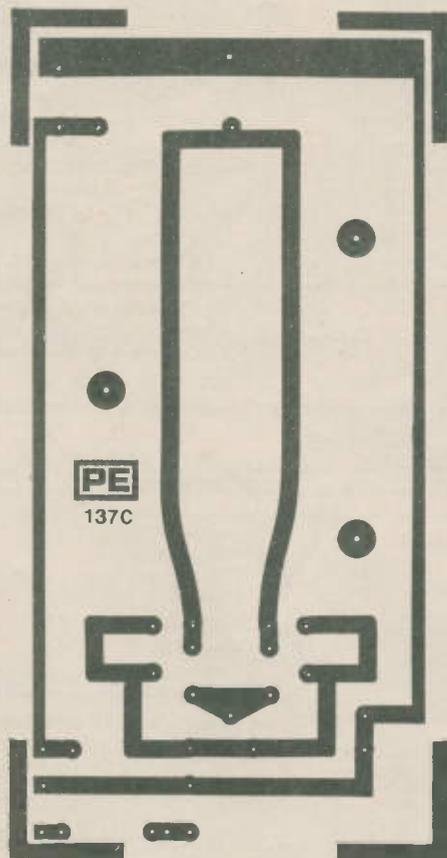

# COMPONENTS . . .

## MAIN PC BOARD

### Timing Circuits

#### Resistors

R1	680 $\frac{1}{2}$ W
R2, R3, R5, R6, R7, R12	1k (6 off)
R4, R8	10k (2 off)
R9, R14	18k (2 off)
R10, R15	120k (2 off)
R11, R13	39k (2 off)
R16, R17, R18	5k6 (3 off)
R19	270
VR1 P.c.b. Trim Pot	500R
VR2a,b	100k dual gang pot
VR3	100k pot
All resistors $\frac{1}{4}$ W 5%	

#### Capacitors

C1	2200 $\mu$ 25V
C2, C3	1000 $\mu$ 16V (2 off)
C4, C6, C7	1000 $\mu$ 16V elect (3 off)
C5, C13	47 $\mu$ 16V elect
C8, C10	4 $\mu$ 7 25V elect (2 off)
C9	2n2 polycarb (2 off)
C11	10 $\mu$ 16V elect
C12	220n 400V polycarb
C14	100 $\mu$ 25V

#### Semiconductors

D1,2,3	IN4002 (3 off)
D4-9 diode	IN4148 (6 off)
D10,11 diode	IN4002 (2 off)
IC1 Voltage regulator	7812
IC2 Voltage regulator	7805
IC3,4,5 timer	556 (3 off)
TR1,2,3 transistor	BC109 (3 off)
TR4 power transistor	TIP30

#### Miscellaneous

Speaker 8 $\Omega$  re-entrant horn speaker  
Piezo bleeper  
VU meter  
Cabinet  
Relay DPCO 12V 110 $\Omega$   
Chassis assy  
P.c.b.  
3 Pole jack socket (4 off)  
2 Pole jack socket  
Knobs (2 off)  
DPCO Min rocker switch  
Terminal block 5A 6-way  
Grommet  
M3 6mm PH (7 off)  
M3 8mm CSK (4 off)  
10mm M3 T spacer (4 off)  
Heatsink TV5 (3 off)  
M3 16mm PH (2 off)

#### Chassis Assy Nuts & Bolts

M3 8mm CSK (4 off)  
M3 washers (11 off)  
M3 nuts (8 off)  
M3 6mm PH (2 off)  
M3 6mm CSK (2 off)  
M4 Taptite x 10mm PH (2 off)  
4BA PH x  $\frac{5}{16}$

#### Power Supply

3 core 3 amp mains cable 3 metre  
PCB Fuse holder (2 off)  
Fuse 1A (2 off)  
Toroidal transformer prim. 240V, sec. 15-0-15  
6 way 5A terminal block  
4BA solder tag

#### Constructors' Note

A complete kit of parts is available from:

**Powertran Cybernetics Ltd.,**  
**West Portway,**  
**Andover, Hants.**  
**SP10 3WN.**  
**Tel: (0264) 64455.**

Standard kit inc. 2 Transmitters £129.00  
Pair of extra Transmitters £39.00  
Special Offer: Extended kit inc. 4 Transmitters £149.50

## CONSTRUCTION

When assembling the oscillator and detector boards, the components should be kept as close to the board as possible. The case connection of the BFY90's (TR101/TR102) should be snipped off as close to the body as possible and when mounting TR101 it should be noted that the base connection will pass through the collector and emitter legs. All the component legs should be long enough to enable the components to be bent over to lie on the board.

## OSCILLATOR/DETECTOR UNITS

After all the components have been mounted and soldered the assembly should continue as follows:

- 1) Insert the three 20mm CSK screws through the base plate and secure with nuts, then add extra nuts to support the oscillator board, copper side up. Ensure that the board is spaced to prevent components touching.
- 2) Add three more screws and insert the antenna fixing screws through the detector board, and secure with a nut on


the copper side making sure there is a good contact between the nut and the copper.

3) Place the detector board on the assembly and adjust the nuts until the boards are about 6mm apart. Connect points E on the two boards and connect the mid point of the detector loop with the cathode of the D101 to the junction of R102 and C104.

4) Strip the two core screened cable and after passing through the grommet connect the red and blue wires to the circuit board as shown, with the screen soldered to the copper earth strip.

5) Place the cover over the boards with the grommet in place and secure the assembly with a nut, after insulating the antenna screw. The antenna should then be screwed on and the jack plug soldered to the cable. This may have to be removed after testing in order to route the cable. The connections to the jack plug are shown in Fig. 2.

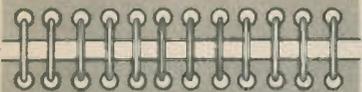**NEXT MONTH: Assembly, Testing and Calibration.**



# INDUSTRY NOTEBOOK

By Nexus

## Tale of Two Thorns

Speculation on the future ownership of Inmos was finally quashed with Thorn-EMI buying out the government holding for £95 million. The Inmos board was pleased. Uncertainty had disappeared and confidence restored.

Government was pleased to pass on a responsibility no longer welcome and to recover the taxpayers' investment. Opposition from the Labour left was routinely ideological but there was consolation at least in control remaining nominally in British hands.

Lofty sentiments on protecting national technological heritage are just plain silly when targeted at an electronics industry which since its earliest days has been international through cross-licensing of designs. Inmos is no exception with most of its production development having taken place in the United States and its "most secret" dynamic RAM technology being made available under licence to NMB/Minibea of Japan. As part of the agreement Inmos will purchase a significant portion of the output of NMB.

Another gigantic "leak" of Inmos technology is the agreement for Racal-Redac to market worldwide the complete Inmos hardware/software package for designing advanced VLSI circuits including the transputer.

Of course, you don't give the information away for nothing. In both cases Inmos gains a down payment plus continuing royalties.

The other Thorn in the news is Waldo Thorn who had much to do with the early build-up of International Rectifier in its Italian and British plants. He then turned his attention to component distribution as MD of Celdis and is now MD Northern Europe for the Italian semiconductor manufacturer SGS. The company was well in the red until gripped by the throat by ex-Motorola executive Pasquale Pistorio whose shake-up resulted in turning huge losses into a small profit.

Waldo has boosted sales by 83 percent on his patch and has been setting up a

£1.5 million CAD centre at his Aylesbury HQ.

## Long Life

Technology advances so rapidly that this year's exciting new product can be obsolescent in a couple of years' time and obsolete in five. But Mullard's Hazel Grove factory has recently ended a 14-year long production run of SOD 38 rectifiers used mainly in TV sets and domestic appliances.

Over the period 87 million had been produced which placed end-to-end would extend to 1,370 miles, nearly as far by air from London to Moscow. But this enormous throughput generated only £12 million of revenue, peanuts by today's standards but a wonderful example of how cheaply we get our components by well-managed mass production.

## Big Spenders

Well beyond the peanut bracket is the proposed £800 million investment in Britain by STC and ITT over the next five years. The development plan is interesting in that the two companies, nominally separate, made virtually a joint announcement.

The ITT investment of £196 million was announced by Daniel Weadock, president of ITT Europe, the STC investment of £600 million by STC chairman Sir Kenneth Corfield. Forecast is the creation of 5,000 new jobs, 3,000 in STC the rest in ITT although in ITT's case most will be in that company's hotel and insurance businesses.

Although the two companies were "divorced" in 1982 when ITT sold £500 million worth of its majority shareholding in STC, there is still a family connection. In fact ITT still holds about 35 percent of STC's equity and STC chairman Sir Kenneth Corfield is senior officer of ITT, UK.

On a smaller scale is the new £6 million factory for BICC-Vero at Chandler's Ford near Southampton. Vero products are well known and enthusiastically used by electronic hobbyists as well as the professionals.

Another £2 million is being spent on equipping the factory with the most up-to-date design and production equipment in order, in the words of MD John Grillo, to beat the Japanese and Germans at their own game. The existing workforce will be reinforced with 150 new jobs.

## Vive le Sport

Love it or hate it—it's been a great year for sport. Detractors are right to point out the blemishes, too commercialised, too political, too little decency and courtesy, general lack of purity in the old traditional sense of playing the game. There's no denying, however, that as an industry it is a vigorous growth area in both cash throughput and employment.

What's in it for the industry? Let's look at the football World Cup to be staged in Mexico in 1986 at a dozen separate stadia. I am pleased to report that the new equipment needed is to be supplied by Pye TVT of

Cambridge under a contract valued at £30 million and won against strong international competition, an industrial sporting event in its own right.

They are to supply more than 100 main and 60 portable cameras coupled into nine completely equipped OB vehicles with all the modern ancillaries such as caption generators and video effects. The overall distribution system includes hundreds of TV monitors, headsets and microphones for a thousand commentary positions. Each match will have seven fixed and three portable cameras, the latter for tunnel and touch-line shots and for on-the spot interviews.

The electronics doesn't stop at TV. Every venue of sporting importance has a powerful PA system, electronic scoreboards, electronic timekeeping. Then there are walkie-talkies for security people and medical electronics to check on personal fitness and possible drug abuse. Computers are in there for instant recall of past performances and advance bookings.

It is impossible to estimate the overall fall-out to industry one way and another. All one can say is that it's huge, so perhaps we should not grumble too much about the inflated earnings of the superstars.

## Antique Yet Modern

This year is the 116th since the Anglo-Mediterranean Telegraph Company was founded under the chairmanship of Lord William Hay. We know it today as Cable & Wireless.

It is still strong in tradition. The outdated "wireless" which came into the title 50 years ago has been retained, as indeed the court of directors rather than a humdrum board, now chaired by recently knighted Sir Eric Sharp, again following a procession of peers and knights.

There is, however, nothing old-fashioned in the conduct of C & W's world wide communications activities today. Privatized in 1981, the company used its new-found liberty to go for growth. Turnover has risen from £403 million to £650 million with a rise in pre-tax profit of 21 percent.

In the UK, formerly prohibited territory to preserve the old GPO (now BT) monopoly, the main business is still Mercury Communications in which the first international links were established via satellite in August. But now an agreement with Western Union has resulted in setting up Easylink, a flexible electronic mail service which, in the United States, is attracting 10,000 new subscribers a month. C & W is investing £5 million in UK's Easylink and has a 75 percent stake with Western Union holding the remainder.

C & W's involvement in the Far East was emphasised earlier this year by the first ever overseas meeting of the court of directors at the Hong Kong HQ. They visited the People's Republic of China where C & W is involved in joint ventures and also Macau to attend the opening of C & W's new satellite earth station. In all, the company expects to invest £1 billion in the Far East over the next decade.

all in your

# NOVEMBER

issue!

## SPECIAL 16 PAGE PULL OUT ROBOTICS SUPPLEMENT

In this special supplement we look at the world of Robotics from their historical development to their present day role.

Mechanics, programming, control and sensing systems are covered together with a comprehensive buyer's guide packed with all the latest information on all the most up-to-date robots.

**READ!!**



## NICKEL CADMIUM BATTERIES

This series of articles explain the advantages, disadvantages, characteristics and typical applications of Ni-Cad batteries. The series concludes with a constructional project of an automatic Ni-Cad charger.



## RING MODULATOR

Remember Sparky the magic piano? The mashed potato Martians? The Daleks? Interface your voice to this (using a microphone), and bring them all back to life. Give your voice the *freezing shivers* or a *metallic twang*. A sound lab in a box!

PRACTICAL

# ELECTRONICS

ROBOTICS · MICROS · ELECTRONICS · INTERFACING


NOVEMBER ISSUE ON SALE FRIDAY, OCTOBER 5

# neptune ROBOTS

RICHARD B. H. BECKER —

SYSTEM DESIGN AND MECHANICAL ENGINEERING.

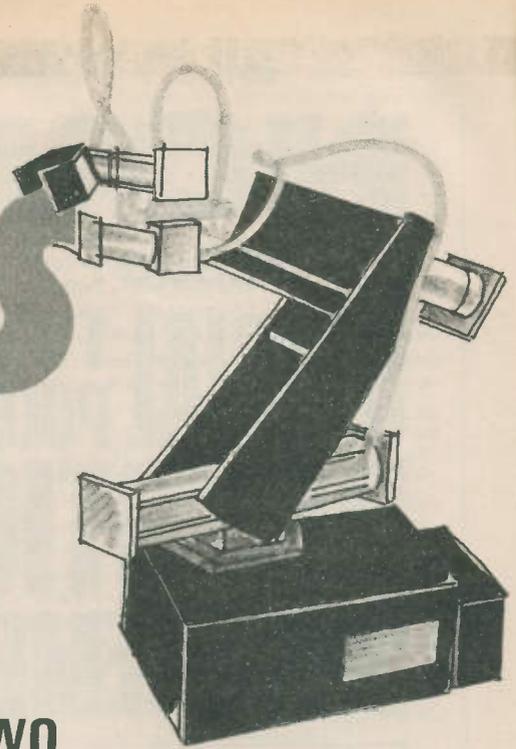TIM ORR — COMPUTER INTERFACE AND CONTROL ELECTRONICS.



THE ROBOTS are directly controlled by a BBC, VIC-20, or Spectrum computer, and the way that control is achieved is explained here. It involves digital-to-analog conversion, multiplexing to each of the axes; and then conversion of the position data back from analog into digital form, to be fed back to the computer for display on the TV.

## THE CONTROL SYSTEM

The robot arm behaves in a very simple manner. It goes to where it is told to go! Once it has been given its instructions it is left to its own devices to proceed to the next set of position co-ordinates. This makes interfacing it with a remote computer extremely easy. All that the computer has to do is WRITE the 7 axis position co-ordinates into some memory locations. These memory locations are in fact the robot's internal latches.

The position co-ordinates are 12 bits long, and so the computer sends the information in two stages, first an 8-bit byte and second a 4-bit nibble. These 12-bit words are held in the robot's internal latches, with one pair of latches per axis. Each latch has a different address in memory: the computer can alter the data

## PART TWO

in any one or all of the latches, merely by writing to the appropriate addresses. The data held in each pair of latches then represents the intended axis position. The data is converted into a d.c. voltage by a 12-bit digital-to-analog converter (DAC) and then it is fed into individual axis servo units. 12-bit DACs are rather expensive, and so the cost of having one per axis would be prohibitive. To avoid this expense a single DAC together with a multiplexer is used to distribute the position voltage to each axis.

Great care has to be used when multiplexing a 12-bit signal because extraneous events in the multiplexing process could destroy the accuracy of the system. The position voltages are sent to the axes' servo units. These units compare this voltage with the position feedback voltages from the axles of the arm and wrist. The servo units open and close hydraulic valves so

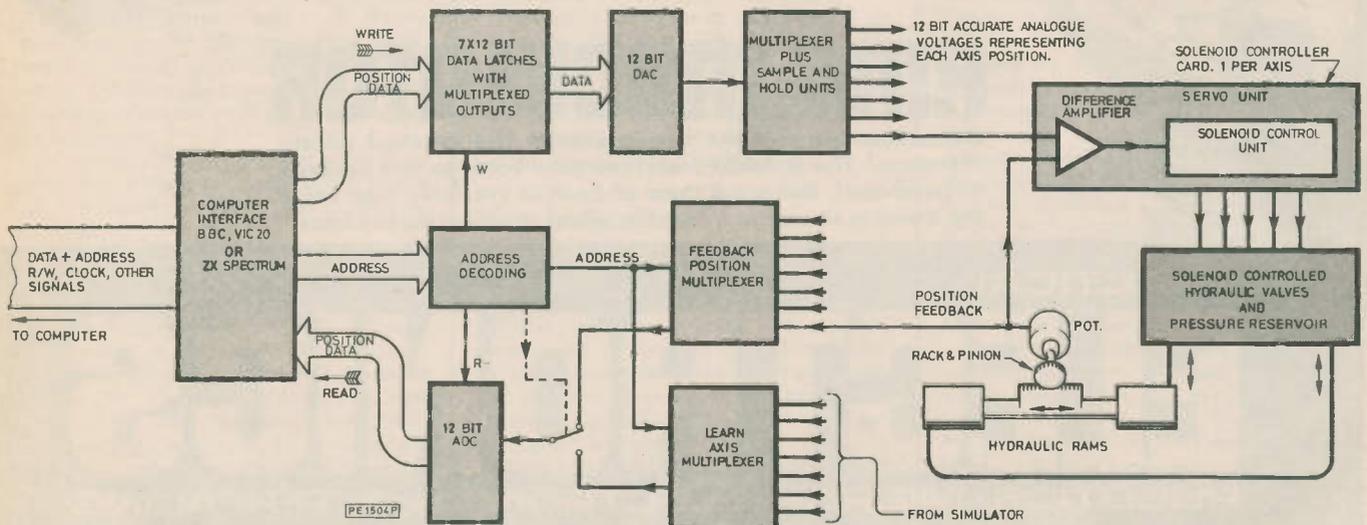


Fig. 2.1. Block diagram of the NEPTUNE Robot system

# ROBOTICS PROJECT

that the arm moves to a position of balance where all the feedback voltages equal the computer-generated position voltages. When this occurs, the arm has reached the position that it is told to go to.

The host computer can also measure the time-varying position of the arm: a multiplexed analog-to-digital converter (ADC) looks at the position feedback voltages. Multiplexing is used here too as 12-bit ADC's are even more expensive than 12-bit DAC's, at about 4 times their price. By performing a READ from two address locations, the axis position can be measured with 12-bit accuracy, but before performing a READ the multiplexer must be addressed to the required axis. This is done by writing a control byte into the multiplexer's latch. Also, the ADC must be told to Start Converting, which means toggling a data bit (part of the control byte) from a 1 to a 0 to a 1. This entails two more WRITE instructions, but can be over within microseconds. The ADC generates an answer in about 35 microseconds from the "Start Conversion" command. At that rate you could READ all 7 axes in about 0.5 milli-seconds.

The system also incorporates a "learn" axis input to which the simulator teaching pendant connects. This input is essentially the same as the position feedback multiplexing unit; by changing one bit in the control byte the ADC will measure d.c. voltages from the simulator. The simulator is a small mechanical model of the arm which can be manipulated by hand. By continuously READING these voltages and then WRITING to the arm, the arm will follow the movements of the simulator. All this information passes through the computer and so it is possible to record it either as a function of time or as a sequence of points in space.

The general system is shown in Fig. 2.1. Most of the hardware lives on the main p.c.b., and the external computers plug directly into this board via ribbon cable connector leads.



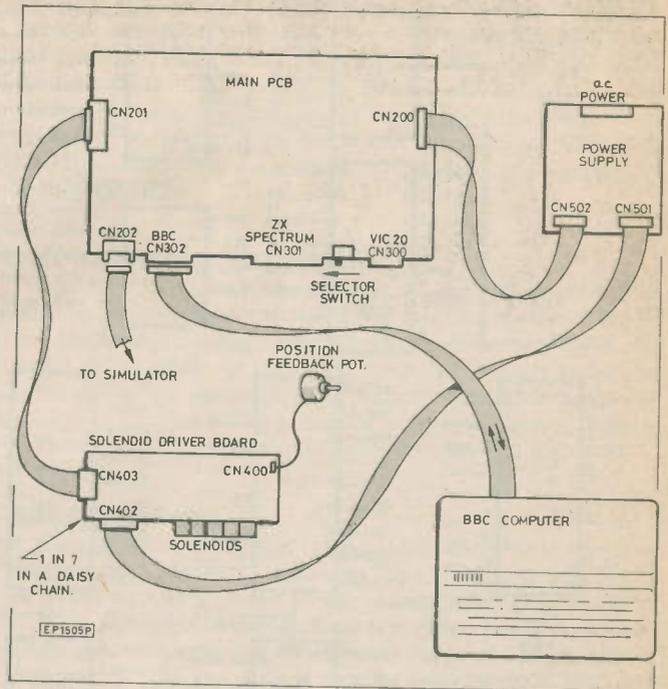


Fig. 2.2. The system interconnected with ribbon cable

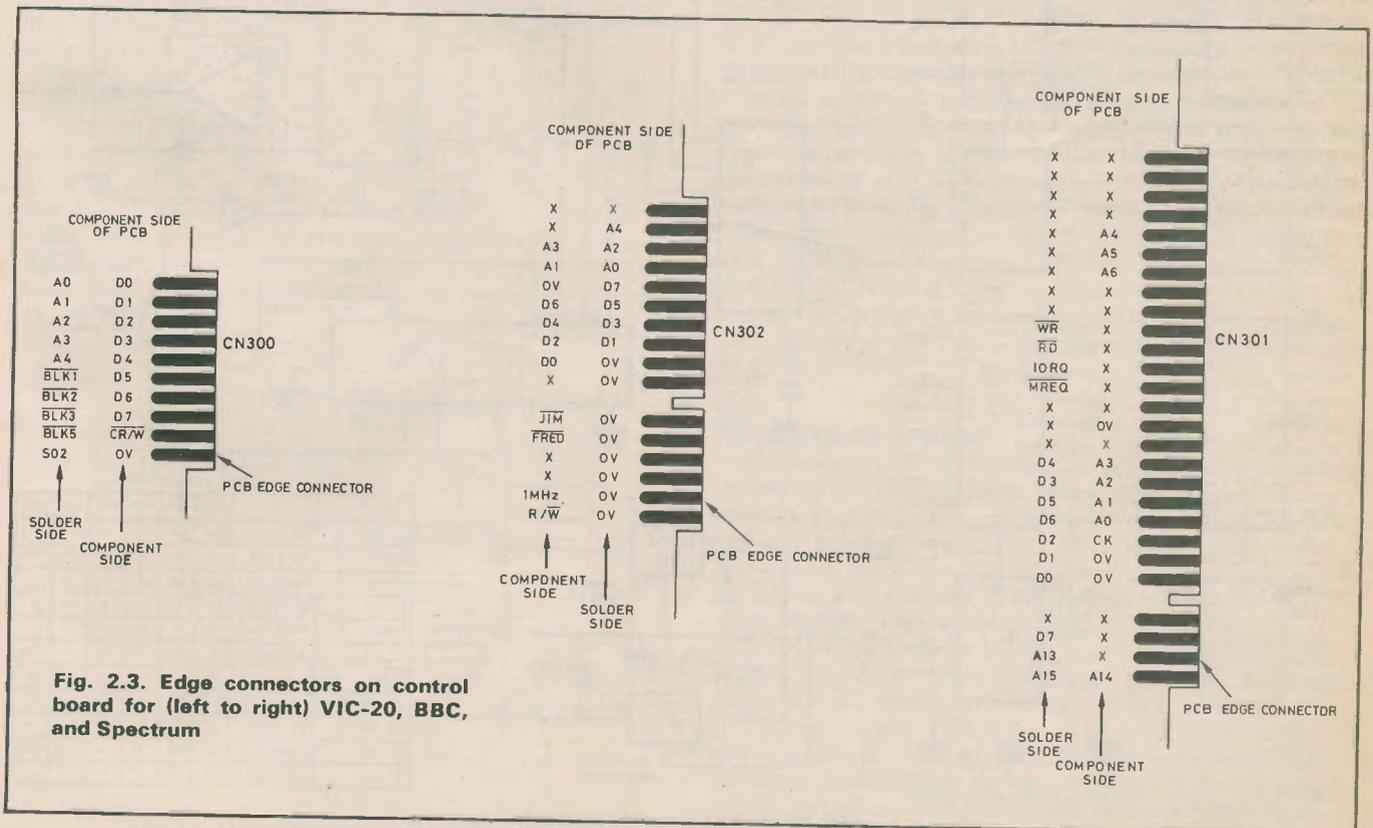The servo units (7 off) are directly connected to the solenoid valves which are in turn directly connected to the manifold. The power supply is on a separate p.c.b. All interconnections are made with pre-assembled ribbon cable IDC two-part connectors (Fig. 2.2).



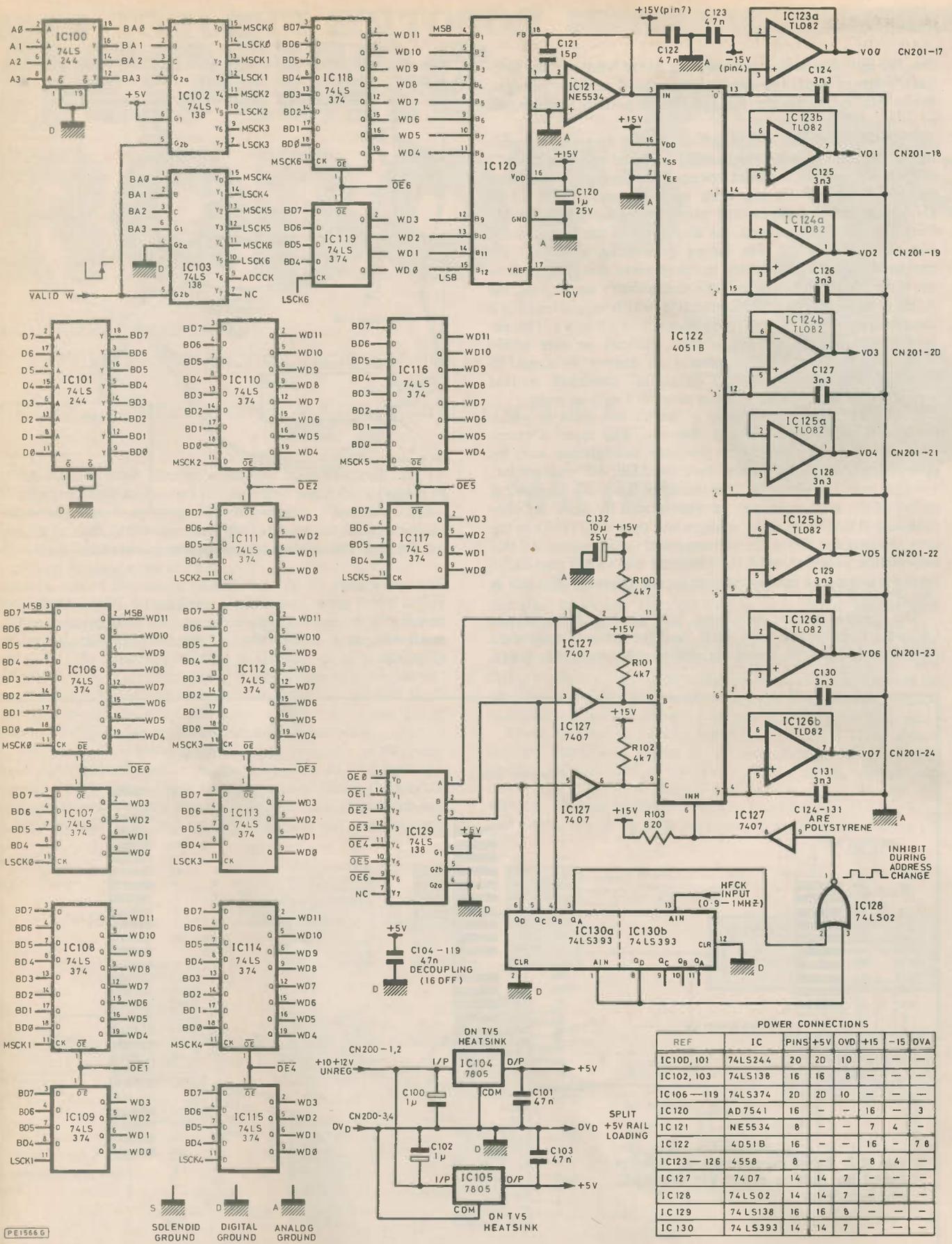

**POWER CONNECTIONS**

REF	IC	PINS	+5V	OVD	+15	-15	DVA
IC100, 101	74LS244	20	20	10	-	-	-
IC102, 103	74LS138	16	16	8	-	-	-
IC106-119	74LS374	20	20	10	-	-	-
IC120	AD7541	16	-	-	16	-	3
IC121	NE5534	8	-	-	7	4	-
IC122	4051B	16	-	-	16	-	7 8
IC123-126	4558	8	-	-	8	4	-
IC127	7407	14	14	7	-	-	-
IC128	74LS02	14	14	7	-	-	-
IC129	74LS138	16	16	8	-	-	-
IC130	74LS393	14	14	7	-	-	-

**Fig. 2.4. Robot control electronics**

## INTERFACES

The NEPTUNES can be driven by any one of three popular micro computers: the BBC, the Commodore VIC-20 and the Sinclair ZX Spectrum. Most micros have user-accessible interfaces and with small changes others could also be used. The NEPTUNE's requirements are a parallel data bus (8 bits), the lower address lines, the clock signal from the micro and the READ and WRITE signals. By using these basic signals it is possible to write 12-bit data words (a byte and a nibble) to the 7 axes of the robot. Also, using this simple interface, the axis position can be read (again with 12-bit resolution) by the host computer.

This enables the real time motion of the arm to be monitored and recorded. The learn axis information is first read by the computer and then written into the arm, enabling direct control of the position of the arm without writing-in software and position control data. The signal pinout for all three computers on the main NEPTUNE board is shown in Fig. 2.3. All three edge-connectors are directly accessible to the user. Other signals from the computer are available, but are not used.

## THE HARDWARE

The hardware shown in Fig. 2.4 is used to store the position co-ordinates and convert them into d.c. voltages for the servo units. IC101 is used to buffer the computer data bus. If the robot electronics were directly connected to the host computer's data bus the loading of it and the spurious signals picked up by it, would almost definitely crash the system. The same is true for the address bus, hence the buffer IC101. IC102 and IC103 decode the bottom 4 address lines, providing 16 available address locations to WRITE into.

A VALID WRITE signal is also required to activate the address decoders. This is obtained from the computer interface circuits. When one of the outputs of IC102 or 103 goes low and then high, it clocks the latch to which it is connected (IC106 to 119). Any data on the data bus at this time is then stored in the latch. This is a WRITE cycle. As the system uses 12-bit words, the writing has to be done twice. First an 8-bit byte is stored and then a 4-bit nibble at the next address location.

The data is extracted from these latches by enabling their outputs in sequence. This data is wired into the 12-bit DAC (IC120) which generates the d.c. position voltages. IC122 is used to demultiplex the DAC output voltage, the voltages being stored on sample and hold devices, IC123 to 126. A binary counter (IC130), which is clocked by the host computer's system clock, is used to generate the multiplexer addresses and output enable decodes. Great care has to be taken over the demultiplexer design, as it is very easy to corrupt the output voltages.

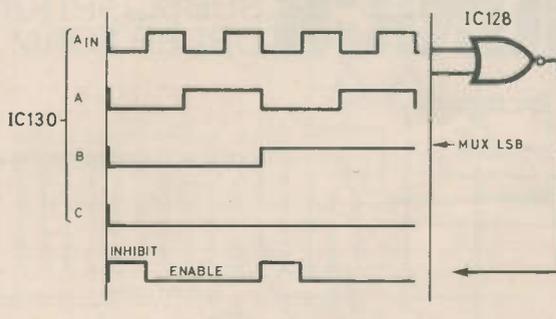


Fig. 2.5. Demultiplexer inhibit timing

The 4051 (IC122) suffers from momentary internal short circuits when the address changes on its inputs and this can seriously damage your sampled and held output voltage which would then become corrupted. An overlapped inhibit signal prevents this (Fig. 2.5). Also, when is a capacitor not a capacitor? Answer, when it is used in a sample and hold circuit. A parameter called dielectric absorption can make the voltage on a capacitor go soggy. Fortunately not all dielectric materials behave similarly and the cure is to use a capacitor constructed from polystyrene.

## THE COMPUTER INTERFACE

The NEPTUNE robots were designed to interface with three popular micro-computers, the BBC, the Commodore VIC-20 and the Sinclair ZX Spectrum. All computers perform reads and writes to the robot. As far as the computers are concerned, the robot arm is just another area of memory. The three computers have significantly different internal electronics and so require different interface circuits at the robot end. See Fig. 2.6.

## BBC INTERFACE

Connection to the BBC is via the 1MHz bus. This is a parallel interface with the lower 8 address lines, 1MHz system clock, R/W and an address block decode called FRED (Hex FC00 to FCFF). The BBC computer internally buffers the data and address lines, which makes the interfacing very easy indeed. Simple decoding (IC300 and 301) is used to generate valid read and write pulses.

## VIC-20 INTERFACE

The VIC-20 is similar to the BBC in that both computers use a 6502A microprocessor. The VIC provides four 8K block decodes, one of which is to be selected by the user with link 12, that is the first position selects block 1 (Hex 2000-3FFF). Valid read and write signals are generated by IC303 and 304.

## SINCLAIR ZX SPECTRUM INTERFACE

Every signal is available at the back of the Spectrum, but there are many possible problem areas and so great care was needed in the design of this interface. The Spectrum uses a Z80 processor and so some dissimilarities between this computer interface and the other two are inevitable. Also the use of the memory map varies and reading presents a few problems. In a 48K Spectrum, a PEEK read anywhere in the memory map would cause a read of either the Spectrum's ROM or the RAM and this would clash with data from the robot interface connected to the bus. An IN read is therefore used treating the robot as an I/O device instead of part of memory.

## ADDRESS DECODING

Unfortunately the address lines are not decoded and are used directly for keyboard scanning and peripheral control. There are however a couple of non-conflicting addresses (hex 3F and 5F) and these are decoded by IC305-309. Writing requires more addresses than are available as I/O, however no conflict is caused by writing with a POKE to the address space 0000 to 1FFF where the Spectrum ROM is resident.

Only one computer at a time must be connected to NEPTUNE. All the data buses and address buses are directly connected to all interfaces, and so if two computers were simultaneously connected, a bus clash would occur. A selector switch is used to route the valid read and write signals and the computer clock signal to the relevant places in the control electronics. A l.e.d. near each connector indicates which computer interface has been selected.

**SUPER HY-LIGHT STROBE KIT**

Designed for Disco, Theatrical uses, etc.

Approx. 16 joules. Adjustable speed. Price £45 + £2 p&p (Total inc. VAT £54.05. Case and reflector price £15 + £2 p&p (total incl. VAT £19.55); Footscap SAE for further details including Hy-Light and Industrial Strobe Kits.

**ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES**

4ft 40 watt £10.44 (£12.00 inc. VAT)  
 2ft 20 watt £7.44 + £1.25 p&p (£9.99 inc. VAT)  
 18in 15 watt £5.00 + 75p p&p (£6.61 inc. VAT)  
 13in 10 watt £4.00 + 75p p&p (£5.46 inc. VAT)  
 12in 8 watt £3.60 + 50p p&p (£4.71 inc. VAT)  
 9in 6 watt £3.00 + 50p p&p (£4.02 inc. VAT)  
 6in 4 watt £3.00 + 50p p&p (£4.02 inc. VAT)



230V AC Ballast Kit for either 6in, 9in or 12in tubes £5.50 p&p 55p (£6.96 inc. VAT)  
 For 13in & 18in Tubes £6 p&p 75p (£7.76 inc. VAT)  
 For 12V DC op. 12in & 13in tubes only £5.50 p&p 75p (£7.18 inc. VAT)

175 WATT SELF-BALLASTED MERCURY BULBS Available for either B.C. or E.S. fitting, price £10.80 + p&p £1.25 (total incl. VAT £13.65).  
 400W UV LAMP only £16.80 post £2 (£21.62 inc. VAT & p&p).  
**L.T. TRANSFORMERS**  
 \*Special Offer 0-6.3 V-0, 6.3 V at 10 Amp (12 V 0 10 Amp or 6 V at 20 Amp) Price £9.00, p&p £2.00 — inclusive of VAT £11.50 N.M.S.

**ROBOT ENTHUSIASTS**

The following two Motors are ideally suited for experimenters in this field:

1. ESCAP precision Swiss-made ironless rotor, 6V DC geared Motor with 70:1 gearbox 6V DC - 16 r.p.m. 3V - 8 r.p.m. amazing power; no load current, only 10 ma. approx. Size 4 x 2 1/2 cm. Ex-equipment, tested and guaranteed. ONLY £4.50 + 50p p&p (total incl. VAT £5.75)
2. 12/24V D.C. reversible Precision built motor manufactured by Escap — will operate from 24-V down to 2-V DC — Current consumption negligible. A range of speeds between 2 to 36 RPM obtainable: 6 Volt DC — 9 r.p.m. N/L 6 MA, 12 Volt DC — 18 r.p.m. N/L 10 MA, 24 Volt DC — 36 r.p.m. N/L 18 MA. Total length of motor and gear box 90 M/M. Max. Dia 42 M/M. Shaft Length 15 M/M. Shaft Dia 6 M/M. Approx. Half manufacturers price: £15.00, p&p £2.00 — total inclusive of VAT £19.55.

**VORTEX BLOWER & SUCTION UNIT**

Powerful multi-stage dynamically balanced, totally enclosed 9" dia. Rotators, 3,500 rpm, 1 1/2" I.D. inlet and outlet, 110V A.C. Price £30. Suitable transformer for 240V A.C. £10 + £4.50 p&p (total incl. VAT £51.18) N.M.S.

**COOLING or EXTRACTOR FAN** Quiet smooth running Size 4 3/4 x 4 3/4 x 1 1/2 Supplied for 240V a.c. operation Price £4.75 £1 p&p (total incl. VAT £6.62) N.M.S.



**240V A.C. SOLENOID VALVE**

Designed for Air/Gas at 0.7 Water 5 psi Inlet/outlet 3/8" Forged brass body. Manuf. Dewraswitch Asco Price £5.50 £1 p&p (£7.48 inc. VAT) N.M.S.

**VARIABLE VOLTAGE TRANSFORMERS**

INPUT 230, 240V a.c. 50/60 OUTPUT 0-260V	
230V 1A Max.	£15.00
0.5KVA 2A Max.	£19.00
1KVA 5A Max.	£27.00
2KVA 10A Max.	£41.00
3KVA 15A Max.	£54.00
5KVA 25A Max.	£95.00
10KVA 50A Max.	£181.00
15KVA 75A Max.	£275.00



**3-PHASE VARIABLE VOLTAGE TRANSFORMERS**

Dual input 200-240V or 380-415V, Star connected  
 3KVA 5amp per phase max £113.40  
 6KVA 10amp per phase max £170.10  
 10KVA 16amp per phase max £345.45

All V.V.Ts plus carriage and VAT

Comprehensive range of TRANSFORMERS L.T. ISOLATION & AUTO (110-240V) Either cased with American socket and mains lead or open frame type available for immediate delivery. Leaflet on request.

**12V D.C. BILGE PUMPS**

400 G.P.H. 15ft. head, 3amp, £8.00 + £1.00 p&p (£10.35 inc. VAT)  
 700 G.P.H. 10ft. head, 3.5amp, £11.50 + £1.50 p&p (£14.95 inc. VAT)  
 1750 G.P.H. 15ft. head, 9amp, £15.00 + £1.75 p&p (£19.26 inc. VAT)



**SINGLE DIAPHRAGM COMPRESSOR NMS**

Max 20 PSI. One CFM approx. 240 volts A.C. £18 - £2 p&p (£23 inc. VAT).

**EPROM ERASURE KIT**

Why waste money? Build your own EPROM ERASURE for a fraction of the price of a made-up unit. Complete kit of parts less case to include 12, 8 watt 2537 Angst Tube. Ballast unit, pair of bi-pin leads. Neon indicator, safety microswitch, on/off switch and circuit.  
**LESS CASE** Price £13.60 75p p&p (Total incl. VAT £16.50)  
**Warning:** Tube used in this circuit is highly dangerous to the eyes. Unit must be fitted in suitable case.

**FROM STOCK AT PRICES THAT DEFY COMPETITION!**

- |                        |                    |
|------------------------|--------------------|
| AC GEARED MOTORS       | C.F. BLOWERS       |
| DC MOTORS              | AC CAPACITORS      |
| MICROSWITCHES          | STROBE KITS        |
| RELAYS                 | FLASH TUBES        |
| REED SWITCHES          | CONTACTORS         |
| SOLENOIDS A.C. or O.C. | SYNCHRONOUS MOTORS |

Phone in your enquiries

**Superior Quality Precision Made NEW POWER RHEOSTATS**



New ceramic construction, heavy duty brush assembly, continuously rated.  
 25 WATT 5/10/25/50/100/150/250/300/500/1KΩ  
 1.5kΩ £3.80 + 30p p&p (£4.71 inc. VAT).  
 50 WATT 250Ω £5.50 + 50p p&p (£6.90 inc. VAT).  
 100 WATT 1/5/10/25/50/100/250/500/1kΩ/1.5kΩ/2.5kΩ/3.5kΩ £9.50 + 75p p&p (£11.78 inc. VAT).  
 Black Silver Skirted Knob calibrated in Nos 1.9, 1.1in. dia. brass bush. Ideal for above Rheostats 30p ea. + VAT.

**INSULATED TESTERS NEW!**

Test to I.E.E. Spec. Rugged metal construction suitable for bench or field work constant speed clutch. Size L Bin. W 4in, H 6in, weight 6lb. 500V, 300 megohms, £49, p&p £2 (£58.65 incl. VAT) 1000V 1000MΩ £55 p&p £2 (£65.55 incl. VAT) SAE for leaflet



**SPECIAL OFFER!**

AUTO TRANSFORMER tapped 90-260V, 3.5 KVA 1 phase totally enclosed in metal case, mf. Woden. Price: £60.00 + carriage at cost + VAT. N.M.S.

**GEARED MOTORS**

5 rpm 240V AC Mf. by Carter, £6.05 £1 p&p (£8.11 inc. VAT) N.M.S.  
 28 rpm torque 20lb.in. reversible 1/80th h.p. 110V AC. Price: £9.50 + p&p £1.80 total incl. VAT £12.99).  
 Suitable TRANSFORMER for 230-240V AC operation. Price: £5.20 + p&p £1.40 (total incl. VAT £7.59). N.M.S.  
 38.3 rpm GEARED MOTOR, Torque 35lb in reversible 115V AC inc. start capacity. Price £11.55 + p&p (total incl. VAT £15.58). N.M.S.  
 Suitable TRANSFORMER 230V AC operation. Price £4.50 + 50p p&p (total incl. VAT £5.75).  
 CROWN 37 rpm 2000lb.in. approx. 110V AC, reversible geared motor. Price £35 p&p £4.50 (£45.42 incl. VAT) N.M.S.  
 Suitable TRANSFORMER for above £10 p&p £1.50 (£13.22 incl. VAT).  
 71 rpm torque 10lb.in. reversible 1/70th h.p. 110V AC motor. Price: £9.50 + £1.80 p&p (total incl. VAT £12.99).  
 Suitable TRANSFORMER for 230-240V AC operation Price: £5.20 + p&p £1.40 (total incl. VAT £7.59). N.M.S.  
 57 RPM 240V 1/22 h.p. continuously rated REVERSIBLE 50 lb.in. manuf. by Wynstruments. New. Ideal for garage doors, curtains etc. ONLY £12.00 + £2.00 p&p (incl. VAT £16.10), inclusive capacitor.

**CHECK METER**

200-240V A.C. 50amp fully reconditioned. £7.50 + £1.75 p&p (total incl. VAT £10.64)

**SANGAMO WESTON TIME SWITCH**

Type S251 200/250 A.C. 2 on/2 off every 24 hours, 20 amps contacts with over-ride switch Diameter 4 x 3 price £9.50 + £1.50 p&p (£12.65 inc. VAT & p&p) Also available with solar dia R&T Other types available from stock.

N.M.S. New Manufacturers' Surplus R&T Reconditioned and tested Good normally despatched within 7 days.

Ample parking space  
 Showroom open  
 Monday-Friday



**SERVICE TRADING CO**

57 BRIDGMAN ROAD, CHISWICK, LONDON W4 5BB. 01-995 1560  
 ACCOUNT CUSTOMERS MIN. ORDER £10

Personal callers only. Open Saturdays

9 Little Newport Street  
 London WC2H 7JJ  
 Tel: 01-437 0576

**DON'T MISS A VITAL COPY!**

Ever been in the middle of a project only to find the next issue sold out? An annual subscription to **PRACTICAL ELECTRONICS** solves the problem.

Wherever you live you'll receive every copy regularly each month. It's the quick, practical way to solve delivery problems.

**SUBSCRIPTION RATES**

U.K. £13.00  
 Overseas £14.00

**COMPLETE AND POST THIS ORDER FORM TODAY!**

**PRACTICAL**

**ELECTRONICS**

**SUBSCRIPTION ORDER FORM**

Annual Subscription Rates  
 U.K. £13.00  
 Overseas £14.00  
 (Students: deduct £1 and quote Student number)

POST COPIES TO


NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

POST CODE \_\_\_\_\_

Complete this form and post it, with payment or credit card authorisation to:  
**Practical Electronics**  
 Subscription Dept.  
 Oakfield House,  
 35 Perrymount Road,  
 Haywards Heath,  
 West Sussex RH16 3DH

 I enclose my cheque/P.O. payable to IPC Magazines Ltd. for £ \_\_\_\_\_  
 Charge my credit card A/C at quoted rate



Card valid from: \_\_\_\_\_ to \_\_\_\_\_

Signature \_\_\_\_\_

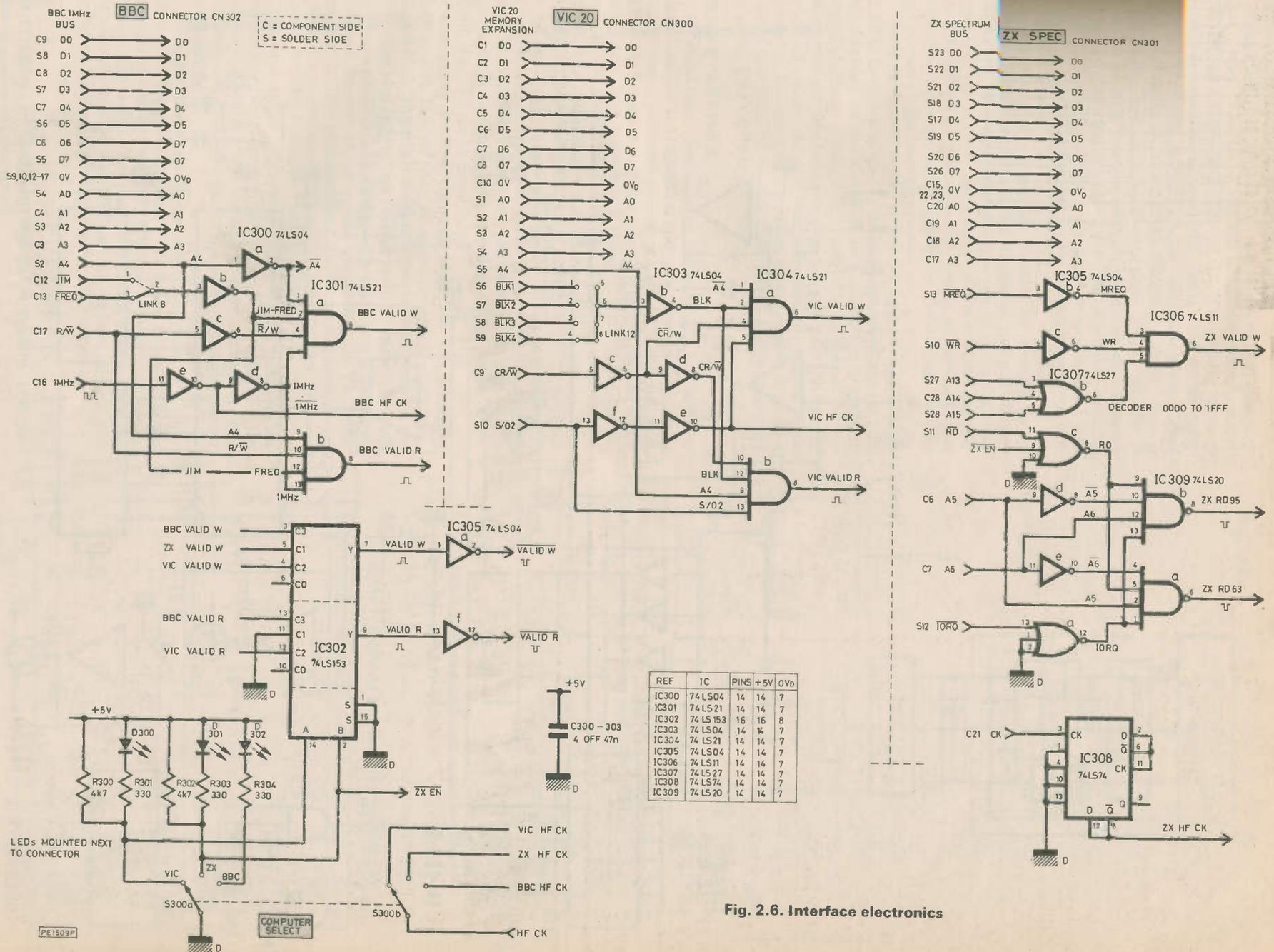


Fig. 2.6. Interface electronics

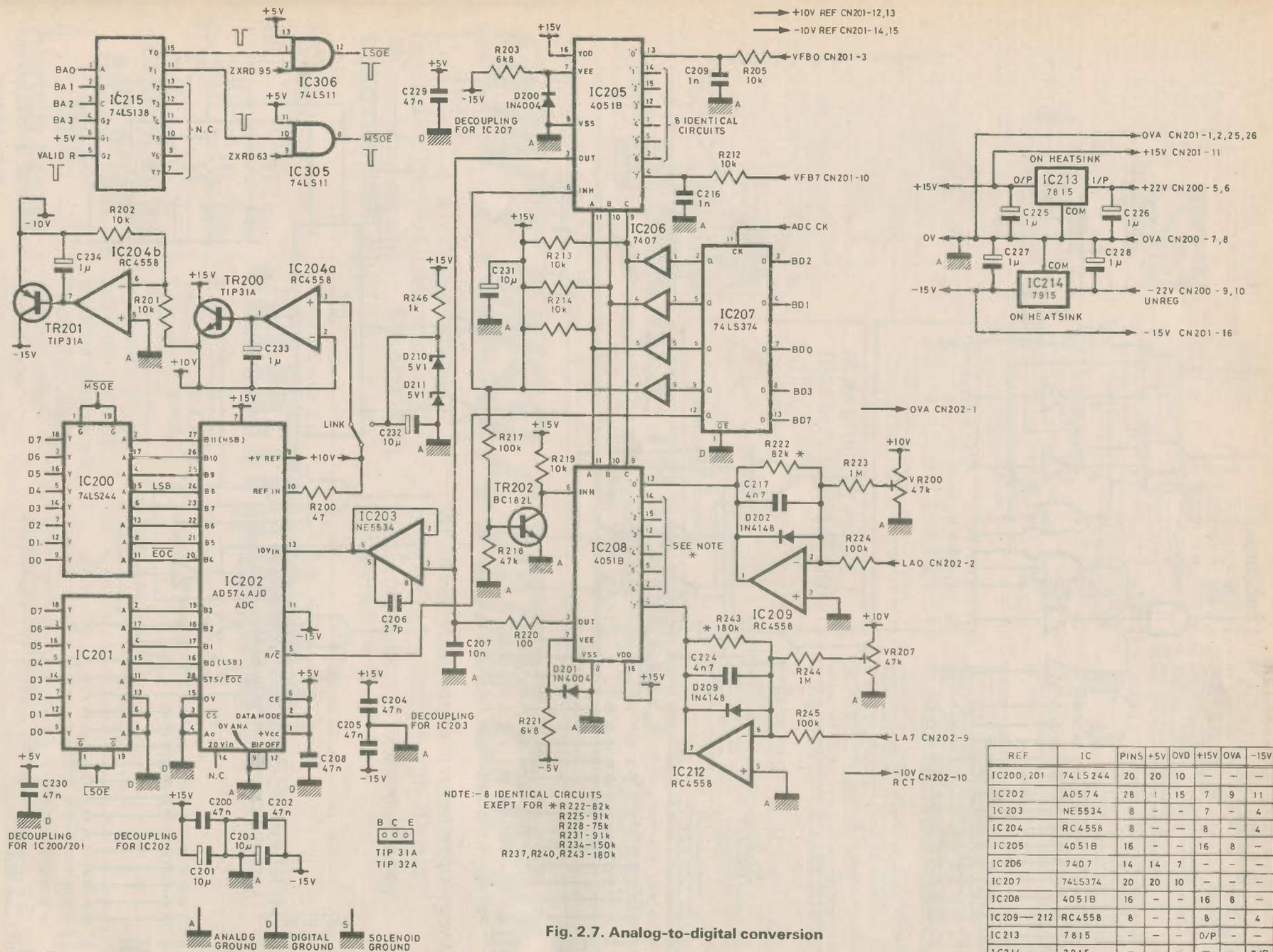


Fig. 2.7. Analog-to-digital conversion

REF	IC	PINS	+5V	OVd	+15V	OVA	-15V
IC200, 201	74LS244	20	20	10	-	-	-
IC202	AD574	28	1	15	7	9	11
IC203	NE5534	8	-	-	7	-	4
IC204	RC4558	8	-	-	8	-	4
IC205	4051B	16	-	-	16	8	-
IC206	7407	14	14	7	-	-	-
IC207	74LS374	20	20	10	-	-	-
IC208	4051B	16	-	-	16	8	-
IC209-212	RC4558	8	-	-	8	-	4
IC213	7815	-	-	-	O/P	-	-
IC214	7915	-	-	-	-	O/P	-
IC215	74LS138	16	16	8	-	-	-

## ANALOG TO DIGITAL CONVERTER

NEPTUNE has the ability to read in, via an ADC, the position of each of its arm joints and to transfer this information back to the host computer. See Fig. 2.7. The position feedback voltage is converted into a 12-bit binary code by the ADC IC202. This device performs a single conversion in about 25 $\mu$ s, which is fast enough for real time monitoring of all the 7 axes. A read of all 7 axes can be achieved in under 200 $\mu$ s. The ADC is an AD754 which uses an internal, successive approximation register to perform a fast conversion. The only signal needed to operate the ADC is a high-to-low Start Conversion signal, R/ $\bar{C}$  on pin 5. The ADC then performs the conversion and 25 $\mu$ s later the result is ready.

Two sources of voltages are available for selection by the system. When multiplexer IC205 is selected, feedback voltages (VFB0 to VFB7) from the robot axes can be read by the host computer. This is a very useful feature in that it enables the computer to observe the dynamics of the system and optimise future trajectories based upon past experiences. The computer can also plot out these trajectories on a printer.

When multiplexer IC208 is selected the learn axis voltages (LA0 to LA7) can be read by the computer. VFB7 and LA7 are not necessary for the control of the robot but are provided to enable additional sensors to be connected to the system. The LA parameters are then fed back to the axis controllers so that the robot arm copies the real time motions and positions of the simulator. The computer memorises the movements either on a regular time basis, for example every 100ms, or when instructed by pressing the COPY key.

### READ OPERATION

A typical read operation is as follows (Fig. 2.8). The multiplexer selection and multiplexer address is set up in control latch IC207. This is performed by writing a control byte to this latch (Table 1). The selected analog voltage is then connected to the ADC input. Start conversion is initiated by taking BD7 on the latch IC207 from a high to a low. This is another write to IC207. The conversion is now underway. It is best to delay resetting BD7 until after the end of conversion ( $\bar{E}OC$ ) so as not to risk disturbing the analog voltage. A test can be performed to see if the ADC is finished, as pin 28 of the ADC is a status bit (also called  $\bar{E}nd\ Of\ Conversion$ ), and when this bit goes low the conversion is complete. By performing a read on bus buffer IC201, the  $\bar{E}OC$  can be tested.


Alternatively the host computer could just wait a suitable length of time. This will occur automatically with programs written in BASIC. Reading is then performed in two steps. First the most significant byte is read (MSOE IC200) and then the least significant nibble (LSOE IC201). The conversion is now complete and the next analog voltage can be selected. The ADC provides the 10V reference signal for use on the servo potentiometers and simulator. If the ADC is not fitted then the zener diode (D210, 211) reference is used.

The axes operate independently; the voltage representing the required axis position is sent to the solenoid driver board of the appropriate axis, together with the position feedback voltage. For seven axes of movement, therefore, there are seven solenoid driver boards.

The system utilised is a closed loop servo system. When it is desired to change an axis position, the analog equivalent of the data operates the hydraulic valves, via the solenoid driver board, and the axis moves. The position feedback voltage from the potentiometer is then compared with the required position, and movement continues until the two voltages are the same.

**NEXT MONTH: Details of the servo system, and the power supply requirements.**

### READ CYCLE

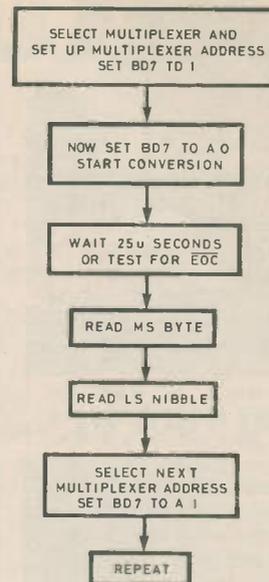

### TIMING DIAGRAM

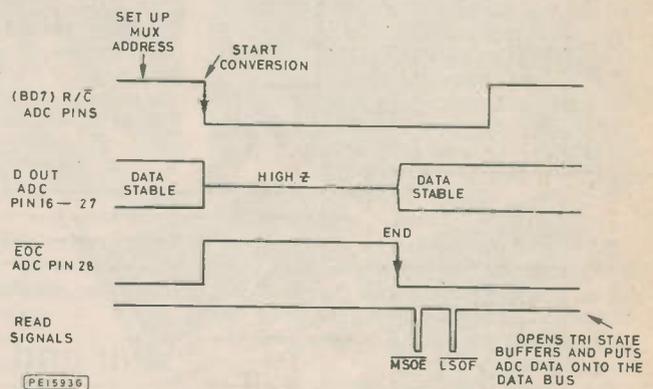


Fig. 2.8. Sequence for read and conversion

Table 1. Neptune axis selector, latch IC207

BD7	BD6	BD5	BD4	BD3	BD2	BD1	BD0	HEX	Signal
/	x	x	x	0	0	0	0	x0	VFB0
/	x	x	x	0	0	0	1	x1	VFB1
/	x	x	x	0	0	1	0	x2	VFB2
/	x	x	x	0	0	1	1	x3	VFB3
/	x	x	x	0	1	0	0	x4	VFB4
/	x	x	x	0	1	0	1	x5	VFB5
/	x	x	x	0	1	1	0	x6	VFB6
/	x	x	x	0	1	1	1	x7	VFB7
/	x	x	x	1	0	0	0	x8	LA0
/	x	x	x	1	0	0	1	x9	LA1
/	x	x	x	1	0	1	0	xA	LA2
/	x	x	x	1	0	1	1	xB	LA3
/	x	x	x	1	1	0	0	xC	LA4
/	x	x	x	1	1	0	1	xD	LA5
/	x	x	x	1	1	1	0	xE	LA6
...	x	x	x	1	1	1	1	xF	LA7

x = don't care. / = start conversion bit. 1 $\rightarrow$ 0 = start conversion.

# Readout...

## Forward Looking

Sir—I read with interest and some amusement your comments on the IEE in *Vernon Trent at Large* in the August issue of P.E.

You accuse the Institution of living in the past. May I suggest it must be some time since you yourself visited the Institution. The statue of Faraday which you regard as 'off-putting' has now been put off and no longer dominates the entrance hall. Some of us thought that 'all that marble' really was a bit much and proposed that the floor should be carpeted. Our members would have none of it and we are now hard at work re-laying the marble floor (at some considerable expense). You say we do not hold meetings, debates and conferences but only seminars or conversazioni. Again have you seen our programme? I cannot recall when last we held a conversazione and only a limited number of seminars which are essentially tutorial are held.

One of the interesting aspects these days is the large number of younger members who have joined the Institution. The vigour with which they promote their views and their effectiveness in influencing the affairs of the Institution is most encouraging.

We believe we are a forward-looking Institution; why not come and see where we are going rather than dwell on the past.

Howard Losty (Sec),  
IEE, London.

*It is about two years since I was last in direct contact with the IEE and at that time I did not detect any appreciable change in the atmosphere and outlook of the preceding 18 years. It seems times are a'changing with the speed of light.*

*The removal of the giant Faraday is a real step forward. But what has happened to this awesome example of the sculptor's art? I do hope he's not being kept on ice in the basement in case some future generation of the IEE management has a change of heart.*

*It's a shame about the marble. But I can't help feeling that the spirited objection of your members to its removal only goes to prove my argument that reluctance to change is still deep-seated. Of course, you could have saved a lot of money if you had broken up Faraday and used the pieces in your relaying operation.*

*No, I haven't seen any of your latest programmes, I'm afraid. That's remiss of me. But in fairness, I was cheered to read, sometime after my article was written, that you had taken over the Dominion Theatre for the Faraday Lecture. This is really reaching out, staging such an august event in a building to which in earlier months people were flocking to see Mary Poppins.*

*I stand duly rebuked over the seminars and conversazioni.*

*Your statement that younger people are joining the Institution in large numbers is clearly at variance with the official report on which my observations were based. But obviously I must accept what you say so far as*

*the IEE is concerned. I only hope that the 'vigour with which they promote their views and their effectiveness in influencing the affairs of the Institution' will continue to bring that breath of fresh air, which from my viewpoint seemed to be lacking.—VT.*

## Interfacing VIC

Sir—With reference to your *Commodore 64 RS 232C Interface* by R.A. Penfold in the August issue of Practical Electronics. Could you please inform me whether the described interface is also appropriate to the VIC 20?

I have recently wished to couple a Tandy CGP115 printer/plotter to the VIC 20 and, of course, came up against the very problem that your article solves for the '64.

R.A. Prince,  
Welwyn Garden City,  
Herts.

*I have tried the CBM64 RS232C Interface with a VIC-20, and without any software or hardware modifications it does seem to work. However, there is a slight problem in that as the electrolytics in the power supply section of the unit charge up the 20mm 1A quick-blow fuse in the VIC does occasionally blow. This does not seem to affect the CBM64 which has a slower acting 1.25 inch fuse. The problem with the VIC can be overcome by replacing the quick-blow fuse with an anti-surge type, or adding current limiting resistors of about 10R in series with each 9V output of the user port would probably eliminate the problem.—R.P.*

## War and Peace

Sir—Isn't it enough that we have to put up with political views being pressed on us by national newspapers and TV, without our hobby magazine attempting to do the same?

I refer to *Industry Notebook* by Nexus. He's at it again (August); airing his views about Unions—one of his hobby horses—and giving his blessing to military electronics. Miners, lorry drivers etc.—Nexus is there to give us his opinion and to lecture us. Just what 'industry' are you reporting on, Nexus?

There's no mistaking his allegiance, I'll give him that, but I don't think he should use his page to stir up this sort of stuff. To clarify (I hope), I mean that I am not interested in his opinions or views, only his reporting, and even that ought to be relevant to the magazine's title.

Of all the developments and news about industry there is no need for him to scrape the bottom of the barrel. News of rival Standards, processes, who's first with what system etc., is what I like to read.

I haven't expressed that very well, but I can give you an example of interesting reporting on the Electronics Industry—the newspaper "Electronics Times," should give a good idea. Of course, there will be large

amounts on military electronics in it, and an occasional mention of Unions (especially in relation to Telecoms)—but not in that irritating 'take it from me, sonny' style, which Nexus seems to have.

Give it a rest, Nexus, and stop using *Industry Notebook* as a platform for your political views.

D. Field,  
Poole, Dorset.

## Bigoted Outlook

As your publication provides no forum for political answers to the highly prejudiced statements of your contributor 'Nexus' I am writing to you in order to express my opposition to some of his/her more outrageous sentiments over the past few months.

I have in mind *Industry Notebook* in the August issue. Having criticised the GCHQ Union for a "prolonged and noisy protest" the writer (wrongly) states: "with GCHQ employees surrendering their membership for immediate financial advantage" (Paragraph 2).

This is not the case—the workforce at GCHQ were faced with three alternatives—1) Drop out of the Union with a cash sweetener. 2) Be transferred (under a cloud) to regions unknown. 3) Be sacked. Equally vain is this writer's claim that it was "a lost cause"—vis-a-vis the recent High Court finding.

I am not an ex-employee of GCHQ nor have I been a member of a Civil Service T.U.

After a vicious attack, culled from the right-wing press, which contained all the heavy old clichés about ballots, violence, obscenities, provocation, civil war and union "bosses", the writer dissolved the working class in eight lines of nonsense and in the next paragraph brought in the questions of "sweetheart agreements, peaceful negotiation, creation of wealth".

Where have you been keeping this character? Can he/she inform us how you create wealth in a closed coal mine after you have been sacked?

I am aware that this letter deals with political issues but nonetheless I consider that a technical journal should confine itself to technical matters. General interest items should of course be included but please, not a column devoted to the bigoted outlook of one contributor.

I feel so strongly about this issue that it puts a severe strain on my loyalty to 'P.E.' I am certain that there are other electronics journals who do not inflict one-sided-no right of reply-articles on their readers.

W.L. Thomas,  
Lydney, Glos.

*Nexus replies:*

*Nobody has been 'attacked' by me. I did comment that the GCHQ and Miners' causes were just. The remainder of which Mr Thomas complains was fact, not opinion. The GCHQ picket was prolonged and noisy and the NUM remains split and picketing was as described. There is a movement, led by the EETPU in the new industries, to eliminate strikes as being outdated, destructive and benefiting nobody. The initiative is from the EETPU, not from me, and deserves to be put on record. Build-up rather than smash-up seems reasonable. Why not give it a chance!—Nexus.*


in the field...



in the lab...



in the boardroom...

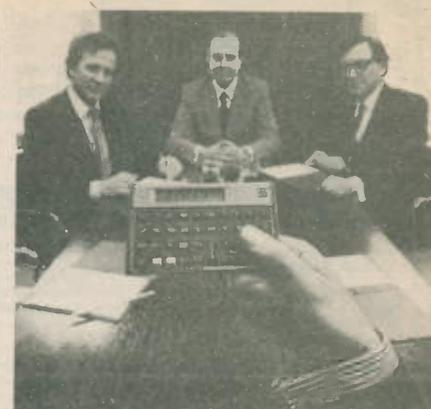

on the site...



in the computer room... in your pocket...



With a professional calculator from Hewlett-Packard, you always have the answers at your fingertips, wherever you go.

Like a computer you can program them to handle the most demanding tasks. But each one has also been pre-programmed to solve the problems of a particular area, AUTOMATICALLY.

Specialised programs make your work easier

There is a professional calculator for



A complete manual of instructions and programs has been written for each member of the HP professional calculator range.

scientists and engineers, for software and computer specialists, for higher mathematics activities, and for the

business user. Each one has the functions you need to make your work easier. Functions like statistics for engineers, binary bit manipulation for software users—depreciation, yields and returns and a calendar for the business world. Each has a constant memory—you can store data with the power off!

And that is not all. Each has a specially written program manual to help you make your calculator solve the most demanding problems your way. From the moment you switch on, you have all the facts you need at your fingertips.

You can see the Hewlett-Packard professional calculators at your dealer, complete and send the coupon below, and we will give you full details of the Hewlett-Packard professional calculator range and how it can help you.



HP 11C is for scientists and engineers. Pre-programmed maths, trig, log and stat functions.

HP 12C for business. Pre-programmed discounting and depreciation, interest and business statistics.

HP 15C for mathematicians. 448 bytes of program capacity, complex numbers facility, root finding, integration and ten matrix operations.

HP 16C for software activities. Four number bases, versatile bit manipulation and up to 64 bits in binary.

# Hewlett-Packard Calculators for Professionals.

All the calculating power you will ever need.

SEND TO: FREEPOST, Enquiry Section, Hewlett-Packard Ltd, Eskdale Road, Winnersh, Wokingham, Berkshire, RG11 1BR. Please send me details of the Hewlett-Packard professional calculator range (together with details of my local stockists). I am particularly interested in:

- Science and engineering applications
- Software and computer applications
- Higher mathematics applications
- Business applications

Name \_\_\_\_\_  
Position \_\_\_\_\_  
Company \_\_\_\_\_  
Address \_\_\_\_\_  
Postcode \_\_\_\_\_  
Tel No: \_\_\_\_\_ PREL 01  
**hp HEWLETT PACKARD**

# TOP QUALITY... TOP SERVICE BOTTOM PRICES!

For FREE CATALOGUE send 9" x 6" SAE — contains full list of stock range all at very competitive prices. Cash with order (except account customers). Access or Barclaycard telephone orders welcome. Add 65p p&p + 15% VAT to all UK orders. Overseas customers add £2.50 p&p Europe, £6.00 elsewhere. Giro No. 529314002. Goods by return subject to availability. Shop open 9am—5pm (Mon-Fri), 10am—4pm (Sat). ALL PRICES EXCLUDE VAT



COMPUTER SHOWROOM  
TOP HARDWARE, LATEST  
SOFTWARE, PERIPHERALS,  
ACCESSORIES AND MUCH,  
MUCH MORE!  
Export Enquires welcome

## INFRA-RED REMOTE CONTROL KITS



These kits are designed to enable infra-red remote control to be incorporated into virtually any application from switching car locks or alarms to controlling Hi-Fi or TV. The application will determine the interface circuitry between the receiver and the controlled device. General instructions and applications are supplied. The kits are coded and provide a high degree of security and noise immunity.

**MK 18 Transmitter Kit** — for use with MK11/MK12 receivers. Requires PP3 battery. Size: 8 x 2 x 13cms. Range approx. 60 ft. **£6.80**

**Keyboards for MK18**  
MK9 4-way for use with MK12 **£1.90**  
MK10 16-way for use with MK12 **£5.40**  
MK13 11-way for use with MK11 **£4.35**  
MK11 Receiver Kit — mains powered. Provides 10 latched plus 3 analogue outputs ideal for controlling audio amplifiers, TV or lighting where control of light brightness is required. **£13.50**

**MK14 AC Power Controller Kit** — (phase) controlling AC loads from MK11 analogue outputs, eg lamp dimming. **£5.20**

**MK19 Stereo Amplifier Controller Kit** — for remote control of bass, treble and volume (or balance) by MK11. Includes a one of 10 decoder remote channel or input selection. May be connected between the pre-amp and power amp of almost any audio system. **£10.70**

**MK12 Receiver Kit** — mains powered with 16 latched or momentary outputs. Latched version is for applications requiring one output on at a time, eg TV channel selection. Momentary type gives an output only during transmission. Lines may be latched as required. Size: 9 x 4 x 2cms. **£13.50**

**MK15 Dual Latched Solid State Relay** — for switching mains loads such as lamps, TVs, etc. from the outputs of the MK12 (momentary). 15 items may be switched independently using 8 MK15s. Triacs (not supplied) switch at mains zero to reduce interference. **£4.50**



Protect your home and property and save by building your own burglar alarm system.



**Stair Mat 23 x 7 in (950 120) £1.70**  
**Floor Mat 29 x 16 in (950 125) £2.60**  
**Tamper-proof connecting block (950 110) £0.30**  
**Door/Window Contacts. Flush mounting, 4 wire, Magnet/switch Per Pair. (950 140) £0.95**  
**Window Tape 0.5' wide, 50m (950 145) £2.50**  
**Window Tape Terminations Per pair. (950 150) £0.36**  
**Key-operated Switch. 1.5A/250V**

## PANTEC KITS

**PN2 FM Micro Transmitter £6.95**  
**PN3 Stabilised Power Supply £12.60**  
**PN5 2 x 10w Stereo Amplifier £13.00**  
**PN6 2 x 40w Stereo Amplifier £23.00**  
**PN7 Pushbutton Stereo Preamp £11.80**  
**PN8 Tone & Volume Control £12.80**  
**PN11 3w FM Transmitter £10.90**  
**PN13 Single Channel FM Transmitter £8.95**  
**PN14 Receiver for above £14.50**

## BT STYLE PHONE CONNECTORS



**Line Jack Units** — Master Unit (first line unit) has bell capacitor and surge arrester.

Flush or surface mounting. Screw connectors.

**Master (flush) (960 110) £3.00**  
**Master (surface) (960 112) £3.00**  
**Master (mini surface) (960 113) £3.00**  
**Secondary (flush) (960 114) £2.65**  
**Secondary (surface) (960 116) £2.65**  
**Secondary (mini surf) (960 117) £3.00**  
**Dual outlet adaptor (960 118) £4.20**  
**4-way line cord — with plug to spade terminals (960 120) £2.00**  
**4-way line cord (960 130) £0.20 per m**

## OTHER KITS

**CT1000K Clock/Timer £14.90**  
**CT1000K8\* Clock/Timer + Box £17.40**  
**KK101 Electronic Lock £11.50**  
**KK102\* 3-Note Door Chime £5.50**  
**KK113 MW Radio £5.50**  
**KK126 DVM/Thermometer £15.50**  
**DL1000K 4-Channel Light Chaser with Dimmer £15.95**  
**DL21000K 4-Channel Chaser £8.95**  
**DL3000K 3-Channel Sound-to-Light £12.95**  
**TD300K+ 300W Touchdimmer £7.75**  
**TS300K+ 300W Touchswitch £7.75**  
**LD300K+ 300W Lightdimmer £3.95**  
**TDR300K+ IR Remote Controlled Lightdimmer £14.95**  
**MK6\* IR Transmitter for TDR300K £4.50**  
**TDE/K+ Touchdimmer extension £2.50**  
**TSA300K+ Time Delay Touch Switch (300W) £5.00**  
**MK1 Thermostat £4.60**  
**MK2 Solid State Relay £2.60**  
**MK4 Proportional Temperature Controller £6.50**  
**MK5 Mains Timer (1KW) £4.50**

\* includes box. + includes front panel  
All kits include PCBs, components and assembly instructions.  
For further details send S.A.E.

## REMOTE CONTROL ICs

**ML922 10-Channel Decoder £4.10**  
**ML924 Programmable Decoder £2.10**  
**ML926/7/8/9 16-Channel Decoders £1.70**  
**SL486 Infra-Red Preamp £2.20**  
**SL490 32 Command Transmitter £2.80**

## TRIACS

**400V Plastic Q4006LT 6A with Trigger £0.85**  
**TXAL2288 8A isolated Tab £0.65**  
**TIC206D 3A £0.49**  
**TIC226D 8A £0.58**  
**TIC246D 16A £0.95**  
**TIC263D 25A £2.10**

## LCD DIGITAL MULTIMETERS

**LOW COST! 10M ohm. 3 1/2 digit 0.4 in display. Auto zero and polarity, low batt. indication, overload protection. Includes test leads, battery, spare fuse, manual, carrying case. £23.95**

AC Volts: 0—200—500.  
DC Volts: 0.2-20-200-1000.  
DC Current: 0.20m-200mA.  
Resistance: 0.2k-20k-200k-2M.  
Size: 138 x 86 x 36mm. (405 202)

**Professional — 10M, 0.5 in, 3 1/2 digit. Overrange and low battery indication. Overload protection. Includes leads, spare fuse, battery, manual and case. Transistor Checker. Size: 175 x 93 x 42mm. £32.00**

AC Volts: 0-200-750.  
DC Volts: 0.200m-2.20-200-1000.  
DC Current: 0.20u-2m-20m-200mA-0.10A.  
Ohms: 0.200-2k-20k-200k-2M. 0-20M. (405 204)



**Auto Ranging. 3 1/2 digit 10mm display. Continuity buzzer, low battery, overload and range indication. 10A internal shunt for AC/DC current measurement. Carrying case supplied. £44.85**

AC Volts: 0-2-20-200-600.  
DC Volts: 0.2-2-20-200-1000.  
AC Current: 0.200mA-0.10A.  
DC Current: 0.200mA/0.10A.  
Resistance: 0.200-2k-20k-200k-0.2M.  
Size: 160 x 85 x 29mm. (405 206)

**High Sensitivity Temperature Probe. For use with a multimeter to measure temperatures from -50°C to +250°C. Accuracy: 1.5°C@25°C, 2°C@100°C. Response time (in water), 5 seconds. Includes case, calibrated scale and instructions. (405 220) £7.95**

## IR GARAGE DOOR CONTROLLER KIT

For controlling motorised garage doors and switching garage and drive lights on/off up to a range of 40 ft.



Lots of applications like controlling lights and TVs, etc. in the home. Ideal for aged or disabled persons, this coded kit comprises of a mains-powered infra-red receiver with a normally open relay output plus two latched transistor outputs, battery-powered transmitter and opto-isolated solid state mains switch.

**XX103 £25.00**  
**XX106 Extra transmitters £10.00**

## HOME LIGHTING KITS

These kits are designed to replace a standard wall switch to control up to 300w of lighting.



**TDR300K Remote Controlled Light Dimmer £14.95**  
**MK6 Transmitter for above £4.50**  
**TD300K Touch Dimmer £7.75**  
**TS300K Touch Switch £7.75**  
**TDE/K 2-way extension for above kits £2.50**  
**LD300K Rotary controlled Light Dimmer £3.95**

## MICROPROCESSOR TIMER KIT

Designed to control 4 outputs independently switching on and off at preset times over a 7-day cycle. LED display of time and day, easily programmed via 20-way keyboard. Ideal for central heating control (including different switching times for weekends). Battery back-up circuit. Includes box. 18 time settings.



**CT6000K £39.00**  
**XX114. Relay Kit for CT6000 includes PCB, connectors and one relay. Will accept up to 4 relays. 3A/240V c/o contacts £3.90**  
**701 115 Additional Relays £1.65**

## ELECTRONIC LOCK KIT

With hundreds of uses indoors, garages, car anti-theft devices, electronic equipment, etc. Only the correct easily changed four-digit code will open it! Requires a 5-15V DC supply. Output 750mA. Fits into standard electrical wall box. Complete kit (except front panel) **£11.50**  
**XX101 Electric Lock Mechanism for use with existing door locks and the above kit. (Requires relay.) 12V AC/DC coil (701 150) £14.95**

# ELECTRONICS

11-13 Boston Road  
London W7 3SJ

ORDERS  
01-567 8910

ENQUIRIES  
01-579 9794

01-579 2842 TECHNICAL AFTER 3pm

CLOCK TOWER

EALING & NORTH  
CIRCULAR RD.

UXBRIDGE ROAD

CAR PARK

To A4 and BOSTON MANOR (P/CADILLAC LINE)

BOSTON RD

HANWELL LT GARAGE  
TK



## OTHER SOLAR SYSTEMS?

The Infra-Red Astronomical Satellite (IRAS) was launched on 25 January 1983, as a joint Anglo-American-Dutch venture. Its orbit carried it round the Earth in a period of 103 minutes, and it stayed in sunlight for most of the time, because its path took it above the poles; its mean altitude was 560 miles.

Almost immediately after launch, the first important results started to come in, and during its active career, which lasted through most of 1983, IRAS sent back a stream of fascinating information. Several new comets were discovered (including one which became briefly visible with the naked eye) and one known periodical comet, Tempel 2, was found to have a dust-tail twenty million miles long. There were also "dust rings" in the Solar System itself, and IRAS detected a strange asteroid whose orbit carries it within 9,000,000 miles of the Sun.

Yet the main work concerned the infra-red sources far beyond the Sun's realm. IRAS surveyed the whole sky, and detected thousands of new sources. All in all, it was possibly the most successful astronomical satellite to date.

The information was collected at the Rutherford-Appleton Laboratory at Chilton, in Oxfordshire, where the preliminary analyses were carried out. Two of the American scientists there were Dr. Hartmut Aumann of the Jet Propulsion Laboratory in California, and Dr. Fred Gillett of the Kitt Peak Observatory in Arizona.

They were using various stars as sources for calibrating the infra-red telescope on board IRAS when they made a startling discovery. Dr. Gillett was examining some of the records when he said, suddenly: "Hey! Alpha Lyrae has a huge infra-red excess." Alpha Lyrae is, of course, the brilliant blue Vega, 26 light-years away and over 50 times as luminous as the Sun.

What did it mean? At first Aumann and Gillett wondered whether there could be some mistake, so they examined other bright stars, such as Altair, which is of the same type as Vega though it is less powerful. Nothing unusual was found.

There really was material associated with Vega, and the two scientists wondered whether it could be "mass flowing out" from the star, but this idea was soon abandoned. Further studies showed that the material took the form of a cloud of particles, larger than the "dust" particles found in interstellar space.

The infra-red radiation came from a region extending out to more than 7,000,000 miles from Vega. This is eight times the distance between the Sun and the Earth, so there had to be a considerable quantity of material. In fact, it was estimated that the total mass was about

the same as that of all the planets in our Solar System put together.

Could it be a cloud of the same kind as the "solar nebula" from which the Earth and the other planets in the Sun's family were formed, more than 4,500 million years ago? Aumann and Gillett came to the conclusion that this was a possibility, but very small particles would have been drawn back into Vega; this would leave intermediate and larger-scale debris in orbit, and this could have condensed into planets, or at least started to do so.

Moreover, there was the question of temperature. The material was found to be about -300 degrees Fahrenheit, about the same as that of the particles making up the rings of Saturn.

All this was exciting. Surveys were continued, and one more star—Fomalhaut—was found to have a similar infra-red excess, for the same reason. There could be no doubt about it; the material was there, and planets were a real possibility. But could they be of the same type as the Earth, and could they support our kind of life?

To answer this, we must look more closely at the two stars concerned. Vega, as we have seen, is more than 50 times as powerful as the Sun; Fomalhaut, at a distance of 22 light-years, is the equal of 13 Suns. Both are much hotter than the Sun, and both are more massive. This means that they run through their life-cycles much more quickly.

Nothing much will happen to the Sun for the next 5000 million years or so, which is fortunate for us; but Vega will not last for more than a few hundreds of millions of years before it uses up the available nuclear "fuel" which keeps it shining steadily. It will then have to change its whole structure, and there will be a period during which it will send out

## THE SKY THIS MONTH

For the next fortnight or so you have a good opportunity to see the elusive little planet Mercury—provided that you get up early! It is emerging from the morning twilight, and reaches its greatest elongation (apparent distance from the Sun) on 14 September, when it will appear telescopically as a tiny half-moon. Rather surprisingly, it is then brighter than any star visible from Britain except Sirius, but this is not obvious, because Mercury is always seen against a light background.

Most of our knowledge of it comes from one space-probe, Mariner 10, which made three active passes of the planet and sent back pictures showing a rough, crater-scarred surface very like that of the Moon. Mercury is smaller than the Earth (its diameter is 3000 miles) and has practically no atmosphere, so that life there is out of the question.

Look for Mercury with binoculars by all means—but only when the Sun is still below the horizon. Never sweep around with binoculars after sunrise; there is always the danger of looking straight at the Sun by mistake, with tragic results for your eyesight.

The other inner planet, Venus, is visible after sunset, low in the west; it is over 90 per cent illuminated. Mars and Saturn are being lost in the evening twilight, though Jupiter is still brilliant in the south-west during evenings. The Moon is full on 10 September, and will be new on the 25th.

Now that the nights are lengthening, the stars can be seen to better advantage. The "Summer Triangle" of

Vega, Altair and Deneb is still very much in evidence. The Plough or Great Bear is at its lowest, in the north, though over Britain it always remains well above the horizon. Arcturus is setting in the north-west, Capella rising in the north-east.

Also in the east, during late evening, look for the lovely star-cluster of the Pleiades or Seven Sisters, in Taurus (the Bull). The Pleiades have been recorded since very ancient times, and there are many legends about them; according to one tale they were seven beautiful girls who were chased by the hunter Orion, and were saved from a fate worse than death by being transformed into stars and placed in the sky! I always think that the first sign of the Pleiades in the evening is an indication that winter, with its fogs and snows, lies ahead.

The main autumn constellation is Pegasus. In mythology, Pegasus was a flying horse. In the sky he is marked by four reasonably bright stars forming a "Square". At present the Square is high in the south during evenings, and is not hard to locate, even though many people looking at maps imagine it to be smaller and brighter than it really is.

Follow down the line of the two western (right-hand) stars of the Square, almost to the horizon, and you will come to the bright star Fomalhaut, which is always very low down as seen from Britain—from North Scotland it is unlikely to be seen at all. It is one of two stars (Vega is the other) being studied by IRAS, the Infra-Red Astronomical Satellite, and found to be associated with material which may be planet-forming.

much more energy than it does now, with disastrous results for any life-bearing planets. The same is true of Fomalhaut, though here the time-scale may be rather longer.

Therefore, it seems that Vega's system (and also Fomalhaut's) will never evolve into a Solar System like ours, because it will not have sufficient time before conditions become hopelessly hostile. We cannot expect Earth-type life, and probably no life of any kind. For this, we must look to more sedate stars which more closely resemble the Sun.

### INVISIBLE BODIES

In spite of this, the IRAS revelations are immensely significant. It had already been suspected that some dim, relatively nearby stars are attended by planets, because they show slight "wobblings" in their slow motion across the background of more distant stars, and these "wobblings" may be produced by invisible bodies of planetary type.

Now, with the news from Vega and Fomalhaut, the presence of other Solar Systems becomes even more plausible. And after all, why not? Our Sun is an ordinary star—one of 100,000 million in our Galaxy alone, and modern telescopes can record at least a thousand million galaxies. It would be absurd to suggest that in all this host, the Sun is unique in having a family of planets.

IRAS has come to the end of its active career. It will be succeeded by new infra-red satellites, which will examine other stars and will almost certainly detect material around some of them.

There is also the forthcoming space telescope (the Hubble Telescope), due to be launched within the next few years; it will have a 94-inch mirror, and will operate from above the atmosphere in free flight round the Earth, controlled from the ground. Its main investigations will be in the visible and near infra-red parts of the electromagnetic spectrum, and it

will be far more effective than any telescope at ground level could hope to be.

### SEARCH FOR ET

If planetary systems are common (as now seems more likely than ever), we must ask ourselves about the chances of extra-terrestrial life. Here, too, we would surely be conceited in claiming that we are unique, but as yet we have no positive information to guide us, and contact with other civilisations will be a very difficult matter—even assuming that they exist within reasonable range of us.

Meanwhile, the new findings have caused something of a change in outlook, and we may hope for more striking developments in the near future. So if you go outdoors on the next clear night and locate Vega and Fomalhaut, you will be able to realise that there is something very significant about them—even though to us they appear as nothing more than tiny points of light.

## FREE! READERS' ADVERTISEMENT SERVICE

# PE BAZAAR

**RULES** Maximum of 16 words plus address and/or phone no. Private advertisers only (trade or business ads. can be placed in our classified columns). Items related to electronics only. No computer, software. PE cannot accept responsibility for the accuracy of ads. or for any transaction arising between readers as a result of a free ad. We reserve the right to refuse advertisements. Each ad. must be accompanied by a **cut-out valid "date corner"**. Ads. will not appear (or be returned) if these rules are broken.

**WANTED** reasonably priced S.S.B. adaptor for Grundig Satellit 2000. Mr. Alagheband, 93 Philbeach Gardens, London SW5 9EU.

**FOR** sale ex. equipment computer i.c.'s 8156, 8085, 8255 all £5 each, £9 for two. Phil Burden, 273 Dilworth Court, Stockport SK2 5PJ. Tel: 061-456 4620 after 6 p.m.

**5 BU208's**, 1 BU108, 2 BU105's £1.60 each or £12.00 the lot. Heatsinks to fit 30p. Mr. J. Armitage, 99 Marten Drive, Netherton, Huddersfield, W. Yorks. Tel: (0484) 662233 after 6.30 p.m.

**STORAGE** cabinets (three) for small electronic components. Steel frame, sixty transparent drawers. Hardly used. £10 each. P. Lee, 62 Naylor Road, London N20 0HN. Tel: 01-445 8224.

**EVERSHEDS** Duster low resistance ohm meter minimum reading 10 microhms (one scale division). Offers around £75. J. Nolan, 16 The Warren, Cromer, Norfolk. Tel: 512108.

**BIDIRECTIONAL** dot matrix printer 80 car memory had little use. Manual and circuit diagram £125. R. H. Pearce, 8 Holly Oak Road, Coxford, Southampton. Tel: Southampton 788278.

**BBC B MICRO** 1-2 O/S perfect condition £250. Mr. P. Batchelor, 34 North Avenue, Abingdon, Oxon. OX14 1QW. Tel: 0235 20760.

**PINBALL** machines. Bally 'Magic Circle'. Some repair needed, £45. Gottlieb 'Eye of the Tiger' 1978, £145. Matthew-Benton. Tel Bristol (0272) 48627.

**WANTED** Commodore PR 100 programmable calculator. Any condition or i.c.'s for experiment. T. Northover, 17 Cedarcroft Road, Chessington, Surrey KT9 1RS.

**BI-PAK** audio modules: AL60 £3.50 each or £6 for both: PA100 £12. All working perfectly. Mr. S. Ince, 15 Heathfield, Eight Ash Green, Colchester, Essex CO6 3QP. Tel: Colchester 579713.

**PRACTICAL** Electronics 1965 to 1974 inclusive. A few missing. Offers please. Mr. K. Chorley, 7 Foxfield, Everton, Lymington, Hants SO4 0LR. Tel: Lymington 45231.

**HAMEG** scope HM307 built-in component tester as new with probes £85. Tel: Milton Keynes 564737.

**WANTED** circuit diagram for 'Intellivision' speech module. Write to: Mr. P. Blomley, 6 Penning Drive, Milnrow, Lancs. OL16 3DT. Tel: Rochdale 32863.

**WANTED** JVC GNC 80 Genlock/Sync coupler for JVC video cameras type G71 or S100 (or circuit). Mr. J. Henderson, 27 Poplar Avenue, Great Harwood, Blackburn, Lancs. Tel: (0254) 885129.

**WANTED** Signalite (general instrument) gas discharge display type SL 700-4 (or direct equivalent). Brian C. O'Donnell, 15 Glenmoy Terrace, Forfar, Angus DD8 1NL, Scotland. Tel: (0307) 64239.

**OSCILLOSCOPE** USSR S Beam £30. Collins TX/RX TCS-12 £25. Practical Electronics/Wireless 1966-1979 offers—buyers collect. Mr. J. B. Carlile, 10 Cedric Avenue, Marshalls Park, Romford RM1 4JL. Tel: Romford 67627.

**WANTED** large sheets glass fibre PCB DS & SS. PCB drill with optics. High class R.F. test gear. Mr. S. J. Branson, 111 Park Road, Peterborough PE1 2TR. Tel: (0733) 67604 (weekends).

**HELP.** Wanted any information on oscilloscope made by A.C. Cossor model 1052. To buy or borrow. Mr. R. Parkes, 102 Abbotts Street, Bloxwich, Walsall, West Midlands WS3 3BP. Tel: Bloxwich 78144.

Please publish the following small ad. FREE in the next available issue. I am not a dealer in electronics or associated equipment. I have read the rules. I enclose a **cut-out valid** date corner.

Signature ..... Date .....

Please read the **RULES** then write your advertisement here—one word to each box. Add your name, address and/or phone no.

**COUPON VALID FOR POSTING BEFORE 5 OCTOBER 1984** (One month later for overseas readers.)

**SEND TO: PE BAZAAR, PRACTICAL ELECTRONICS, WESTOVER HOUSE, WEST QUAY ROAD, POOLE, DORSET BH15 1JG.**

BLOCK CAPITALS PLEASE

Name & Address:			

For readers who don't want to damage the issue send a photostat or a copy of the coupon (filled in of course) with a **cut-out valid "date corner"**

PE BAZAAR  
OCTOBER '84

# VERNON at TRENT Large!

V.T.'s views and opinions are entirely his own and not necessarily those of PE

OVER the past few months I've been looking (sometimes, as you've probably noticed, with a jaundiced eye) at the continuing impact that electronics is making on the way we live, play and work.

I've wandered into industry, agriculture, retail trading, the domestic scene, the Church, medicine, help for the blind and so on. I've even been able, in our April issue, to lift the veil on certain hush-hush developments in the United States that can only be described as revolutionary. And if you believed that report, you will—as the Duke of Wellington said to someone who asked him if his name was Simpkins—believe anything.

Until last week, however, I hadn't got around to the subject of sport, with which the visual and audio media confidently thinks every man-jack of us is besotted. It was then that I ran into an old buddy, Jerry Monk, group publicity manager of the Greyhound Racing Association. He came up with a lot of interesting facts, including the shameful revelation that his particular sport seems, by and large, to be getting along, thanks very much, with no more than a modicum of electronic intervention.

As a sporting attraction, Jerry told me, greyhound racing ranks second only to football in the UK, drawing about eight million fans through the turnstiles every year. The animal itself has a noble history. King Solomon described it as "one of the four things that are comely in going" (he didn't say what the other three were—I'm longing to find out).

Greyhound kennels existed in Anglo-Saxon times and Canute—probably still smarting under the disobedience of the waves—petulantly decreed that only those of royal descent should be allowed to keep greyhounds. The regal touch was revived in 1968 when the Duke of Edinburgh's *Camira Flash* won the Greyhound Derby at White City.

Originally greyhound coursing involved a live hare. Then in 1876 there came a startling innovation at Hendon in North London. For the first time the prey was an artificial hare which ran on a live rail embedded in the turf of a 400-yard straight course.

The forerunner of modern greyhound racing came into being in Tucson, Arizona, in 1909, with dogs competing on a circular course. Belle Vue, Manchester, saw the first British meeting within this concept in July 1926.

★ ★ ★

On-course betting on greyhound races is handled by the totalisator. Mindful that PE readers have in many cases led sheltered lives, let me explain that this is an electro-

mechanical system in which the aggregate stake, less admin charges and tax, is paid out to winners in proportion to their stakes. It is, in essence, a jumbo-size calculator with a jumbo-size read-out.

"Many of these machines," said Jerry, "have been in use for more than 30 years and are approaching the end of their useful lives. We can't replace them because they aren't being made anymore.

"So, bowing to the march of technological time, we are just embarking on a heavy capital investment to provide the 10 stadia we own throughout the UK with fully-computerised totes based on microprocessors. Already they have been installed at Wimbledon in SW London, Slough and Portsmouth.

"They will have the great advantage of faster operation and will make possible a much wider variety of betting combinations. And eventually the giant visual boards which have been with us for so long will be replaced by monitors set up in strategic positions round a course and giving much more information than hitherto.

"It's an expensive operation, as I say, but we believe that it will eventually more than pay its way."

Another project in hand, though it cannot accurately be described as one involving electronics, is to run the hare on a linear motor. The dividend here is vastly simplified maintenance.

"But while we naturally want to keep up with the times so as to give our patrons the advantages of modern developments," said Jerry, "you have to remember that basically our business is based on animals. Greyhounds are motivated by instinct and training, not by what electronic research and development offers.

"People often ask whether the hare is really necessary to a successful race. On the face of it, it isn't. Generally speaking, greyhounds will run because they are trained that way, whether or not they have a prey to follow.

"We've proved that by experiment. But the hare still has to be there. Should one nervous dog cotton on to its absence and falter, the rest of the field will falter too."

★ ★ ★

Greyhound racing has had a somewhat chequered career in Britain. Originally it was regarded as a cloth-cap type of sport. Indeed, at one point the totalisator was outlawed because it was thought it encouraged the working classes to fritter their money away.

Then by the early 1950s it had achieved a greater respectability. Track managements

went out of their way to build up an "have-an-evening-out-with-the-wife" image. Catering facilities were improved out of all recognition.

Industry was wooed to provide sponsorship—many of the big classic races are now backed by household names. A night at the dogs became as much a feature of company-customer entertaining as a box at Goodwood.

Nevertheless, the sport has been hard-hit by the cold wind of recession and by the emergence of the betting shops which have enabled punters to back their fancies without turning out on a cold night. But the tide is turning again and attendances are on the upturn.

---

**"... only those of royal descent should be allowed to keep greyhounds."**

---

But however one may advocate the adoption of chip and other modern technology as a means of cutting costs, improving profits and increasing efficiency in other fields, one stark fact remains. Greyhound racing, while still hovering on the electronics periphery, manages to achieve a staggering betting turnover of more than £600 million a year.

Maybe there's some sort of moral here.

★ ★ ★

My friends at the Sutton (Surrey) "Talking Newspaper for the Blind" (see the March issue of PE) have been looking at a new type of reading machine, developed in the USA and available in this country at the bargain price of £25,000!

This is how it works: The material to be read is placed face downwards on a scanner, similar to a photo-copier. A remote hand-held control panel is then activated which causes the machine to automatically locate the first line of text and begin scanning the page. Within seconds an electronic voice reproduces the material.

The machine is designed to read any printed material in book or magazine form. It will also handle documents, office memoranda or typewritten correspondence. It can speed up or slow down, repeat previous lines or spell out difficult words. And while many other facilities can be achieved via its 32 controls, it cannot, alas, cope with handwriting.

While the cost of this machine could not possibly be borne by any individual charitable organisation, efforts are being made in the USA to provide its benefits at major public libraries.

Ways and means are now being sought in Sutton for bringing this benefit to its 500 sightless persons.

Here's a thought. The cost of a reading machine is probably around the equivalent of the annual salaries of three Deputy Assistant Administrators (Class III), or whatever, while away their time in the Civic Offices.

## PULSE DIRECTION

# LOGIC PROBE

S.A. WITHEY

In modern electronic circuits it is necessary to be able to detect high speed clock pulses and their direction, in addition to the d.c. logic levels of inputs and outputs. This is possible if a very expensive oscilloscope is available which can hold and stretch very short duration pulses. Many logic probe designs either omit the pulse function, or include it in association with the alternate switching of the logic level l.e.d.s. In the design presented here, a logic "0" is indicated by a green l.e.d. and a logic "1" by a red l.e.d. High speed pulses are indicated by a yellow l.e.d. in conjunction with a double pole, single throw switch, which indicates whether the pulse is positive or negative. This is not a fussy circuit. Apart from the 7404 Hex inverter and the miniature switch, the components used are values normally found in the workshop. TR1 can be any general purpose npn transistor and D1 and D2 any silicon switching diodes of 4148 or 914 type. Resistors R4 to R6 can be any value between 47 and 150 ohms, according to the brightness of the l.e.d.s available, 100 ohms being suitable for a normal quality l.e.d. and 47 ohms if using cheap pack l.e.d.s. C1 stretches a detected pulse sufficiently to illuminate the yellow l.e.d. The value and type is not critical, a 4 $\mu$ 7 electrolytic being chosen because it is of small physical size when laid on its side, but having sufficient capacity to hold a slow frequency pulse.

### CIRCUIT DESCRIPTION

The circuit shown in Fig. 1 is powered by the host circuit which is being tested. This must be a +5V supply. With the probe in its quiescent state, i.e. not in contact with any active circuit, the input to IC1a (inverter 1) is floating—it is neither at logic "0", nor logic "1". Its output, which is connected to the input of IC1b is at logic "0". Therefore the output of IC1b is at logic "1" and unable to turn D3 on. TR1 is turned off leaving a logic "0" at the input to IC1c and logic "1" at its output disabling D4. At the same time, the input to IC1d is floating and its output is at logic "0". The input to IC1e is also at logic "0" and its output, being at logic "1", disables D5.

With a logic "0" at the tip of the probe and the input to IC1a the junction of IC1a output and IC1b input is at logic "1". The resulting logic "0" at the output of IC1b pulls the cathode of D3 to ground potential, turning it on and indicating a logic "0" at the tip of the probe. Meanwhile, TR1 remains turned off. If S1 is in the "0" position, touching a logic "0" with the tip of the probe produces a pulse at D5. Whilst there is a logic "0" at the cathode of D3 the input of IC1d which has been floating, is pulled down to logic "0" through D1. Its output goes to logic "1", charging C1, which acts as an a.c. coupling capacitor to the input of IC1e placing a logic "1" at its input and a logic "0" at its output. This pulls

the cathode of D5 down, causing it to turn on. A series of high frequency pulses prevents C1 from discharging, holding D5 on.

With a logic "1" at the tip of the probe, TR1 is turned on, bringing the input to IC1c to logic "1" and its output to logic "0". This brings the cathode of D4 low and turns it on. At the same time the input of IC1a being at logic "1" disables indicator D3. If switch 1 has been changed to the "1" position, any pulses appearing at the probe tip will be indicated by D5 turning on, as previously described.

TR1 and its associated resistors have the effect of stabilizing the inputs from the probe tip. Without it the inputs would float, causing either D3 or D4 to turn on. Similarly D2 prevents the input to IC1d from floating. R3 ties the input of IC1e to ground until pulled up by the output from IC1d.

### CONSTRUCTION AND TESTING

The circuit is constructed on a p.c.b. 35 x 60mm. The circuit design is shown in Fig. 2 and the component layout in Fig. 3.

The circuit is simple and could be a suitable introduction to drawing with etch resist pen. This is carried out by first taping a photocopy or tracing of the p.c.b. design over the copper side of the board and drilling the holes. Holes should



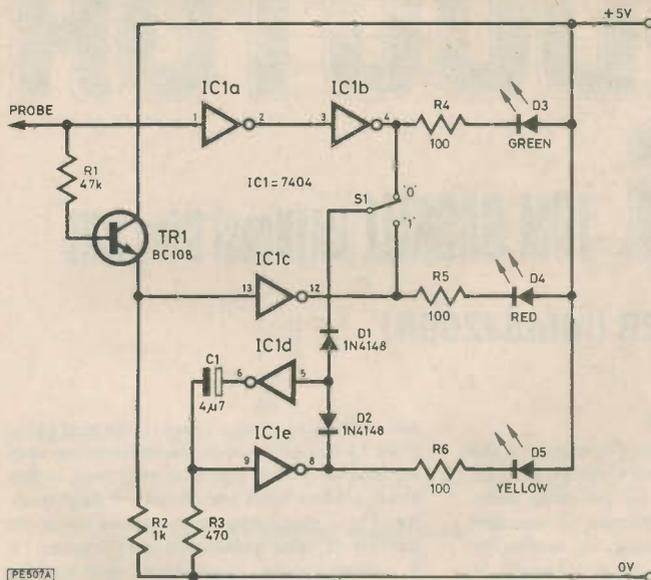


Fig. 1. Circuit diagram

be 0.8mm for IC1, the transistor, the diodes and capacitor and 1mm for the resistors, i.e.d.s and leads. After drilling, the board should be cleaned to remove any burrs. When drawing with the etch resist pen, first draw pads around the holes and use these as a guide for drawing the lines. Since the inverter at pins 11 and 10 of the i.c. are not used, there is no need to draw these pads, allowing a line to pass between them. Etch in a solution of ferric chloride. Clean off the etch-resist when etching is complete.

Mount resistors, followed by diodes, i.c., with or without socket, transistor, capacitor and last of all the i.e.d.s. The i.e.d.s should stand-off from the surface of the p.c.b. so that they will locate in the holes in the case. Care should be taken with the polarisation of the diodes, the cathode being indicated by a broad band; the i.e.d.s, where the cathode is indicated by a flattened side and the capacitor, usually indicated by a + or - sign. The transistor emitter is indicated by a small lug on the metal case. S1 is a miniature d.p.s.t. type with 0.15" space between connectors; it is soldered directly onto the edges of the p.c.b. Stranded red and black wires with miniature croc leads are used for the power leads.

After completion of the board, a probe tip made from a suitable conductive rod is first of all bent at the p.c.b. end before it is inserted, from the component side, through the 2mm hole provided and soldered to the large pad on the copper side. The probe was designed to fit into a small plastic case of the type shown. The p.c.b. basically 'clips' into position once the holes for the switch (S1), the probe and the croc leads have been made; non-conductive foam could be used to hold the board more firmly if necessary. It was found that a small piece of plastic had to be cut away from one of the securing pillars in order to seat the p.c.b. properly so that the other edge rested on the ledge on the inside of the case.

## TESTING

Connect the probe to a suitable +5V source, then touch the probe tip to each of the positive and negative terminals. The i.e.d.s will then respond to the relevant logic levels. ★

## COMPONENTS...

### Resistors

R1	47k
R2	1k
R3	470
R4-R6	100* (3 off)

### Capacitors

C1	4µ7* elect. 16V
----	-----------------

### Semiconductors

D1-D2	1N4148 (2 off)
D3	Green i.e.d.
D4	Red i.e.d.
D5	Yellow i.e.d.
TR1	BC108 or general purpose npn
IC1	7404

### Miscellaneous

D.p.s.t. miniature slide switch (0.15") pitch; Case type 21026 (Electrovalue); 2mm dia. conductive rod (probe tip); Croc clips (2 off).

\*See Text

### Constructor's note

Case available from, Electrovalue, 28 St Judes Road, Englefield Green, Egham, Surrey. TW20 0HB. (0784 33603).


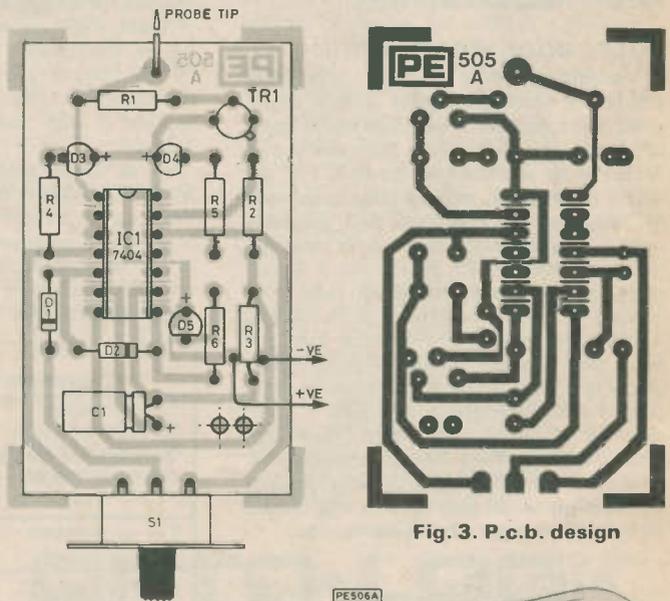


Fig. 3. P.c.b. design

Fig. 2. Component layout

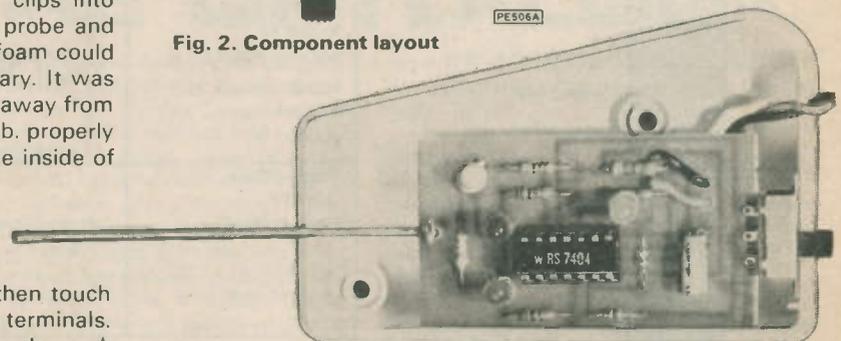

# SEMICONDUCTOR CIRCUITS

TOM GASKELL BA(Hons) CEng MICE

## ENCODER/DECODER (MM53200N)

THE encoding and decoding of information is a very complex business, and is done for many different reasons. One of the most common of these is in control applications where one unit must control a number of others independently of each other, or where any given unit should respond only to instructions from one other specific unit. Under these circumstances there must be some means by which units can uniquely identify and recognise each other. This can prove difficult to implement, especially when a high degree of immunity against error is called for; for example, in security systems. This month we look at the MM53200N, a novel i.c. from National Semiconductor which provides an interesting solution to some of these problems.

### PULSE CODE MODULATION

The MM53200N is an 18 pin digital MOS LSI device which can behave as both an encoder and a decoder. It works on the principle of pulse code modulation, as illustrated in Fig. 2. The basic waveform is shown in Fig. 2a, and is a continuous series of pulse codes each of which is 11.52ms long. (All durations quoted assume the nominal 100kHz clock frequency.) Between each pulse code is a reset pulse, also 11.52ms long. Each pulse code consists of 12 individual bits; Fig. 2b and Fig. 2c show the arrangement of these. For each bit, a short negative duration of pulse corresponds to a logic 0, and a long negative duration of pulse corresponds to a logic 1. Since there are 12 bits in each code it follows that there are 2<sup>12</sup>, or 4096, different combinations. When used as a decoder the i.c. only responds to one of these, so each encoder can control up to 4096 decoders without interaction.

### BASIC OPERATION

The two different modes of operation of the i.c. are shown in Figs. 3 and 4. All the connections are identical except for the mode selector, pin 15 (high level = encode, i.e. transmit the signal, low level = decode, i.e. receive the signal), the receive input, pin 16 (connect to 0V for transmit), and pin 17 which is the transmit output or the negative pulse to indicate that a valid sequence of codes has been received, as appropriate.

The bit select inputs have internal pull-up resistors to the positive supply, so a switch being open corresponds to a logic 1, and closed to a logic 0. In the transmit mode, these 'bit select inputs' are scanned sequentially to produce the waveforms shown in Fig. 2.


There is no transmit enable facility as such, so the transmission of codes will continue for as long as power is applied, although the mode select pin (pin 15) could effectively be used to stop transmission of codes if required.

In the receive mode the incoming signal is fed into a Schmitt trigger circuit to help to 'clean up' the waveform, and is then compared to the locally programmed code at switches S1 to S12 in a sequential manner. If there is an error in the incoming code compared with the locally programmed code the system is reset

and comparison starts again on the next pulse. If all 12 bits of the code are received correctly an internal 'valid' signal is generated, which clears a 64ms timer and clocks a 3 stage counter. The 3 stage counter is used to count the number of 'valid' pulses, and after 4 pulses, i.e. 4 correct codes, have been received, the receive output goes to a low level, i.e. logic 0. Four valid codes must be received within the 64ms time window or else the system is reset without the receive output ever being allowed to go to a low level. The process must then start all over again. After the receive output goes low (signalling the correct receipt of four valid codes) the next valid code must be received within 128ms. Hence, at least 1 code in 6 received must be valid to maintain the receive output at a low level.
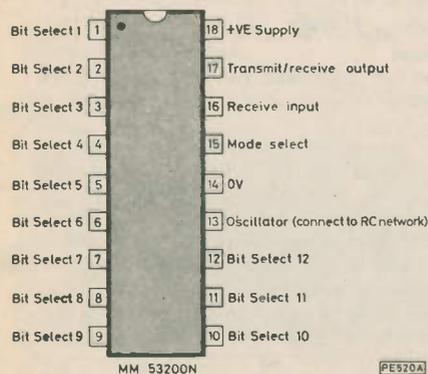
### USING THE I.C.

The specification and pinout of the MM53200N are given in Fig. 1. Note that the supply range is only +7 to +11V, limiting its use in some applications but making it ideal for use with 9V batteries. The internal oscillator uses an external 100k resistor and 180pF capacitor, as shown in Figs. 3 and 4. Oscillator stability is non-critical, so ±5% tolerance components can be used. As with most MOS logic families the output is much



Characteristic	Notes	Minimum value	Typically	Maximum value	Units
Supply voltage	All spec's measured over the full supply range	7	9	11	V
Quiescent current				12	mA
Temperature range		-25		+70	°C
Oscillator frequency	For 100k resistor & 180pF capacitor ( <i>exact</i> values)	87	100	115	kHz
Pull-up resistors	Pins 1 to 12, internally connected to pin 18	200k		1.2M	Ω
Input voltage to pin 16 (receive input)	For logic 1 level	4.0		(+ve supply)	V
Input voltage to pins 1 to 12 & pin 15	For logic 0 level	0		2.0	V
	For logic 1 level	(+ve supply)		(+ve supply)	V
	For logic 0 level	-0.5		0.5	V
		0			V
Output voltage at pin 17:					
Logic 1 level	Output (source) current = 5μA	(+ve supply)		(+ve supply)	V
Logic 0 level	Output (sink) current = 2mA	-0.5			V
		0		1.0	V

Fig. 1. Pinout and specification

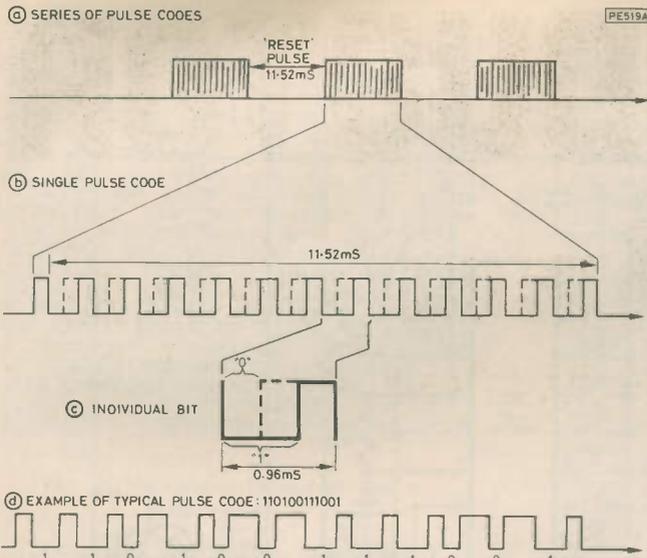


Fig. 2. Pulse code waveforms

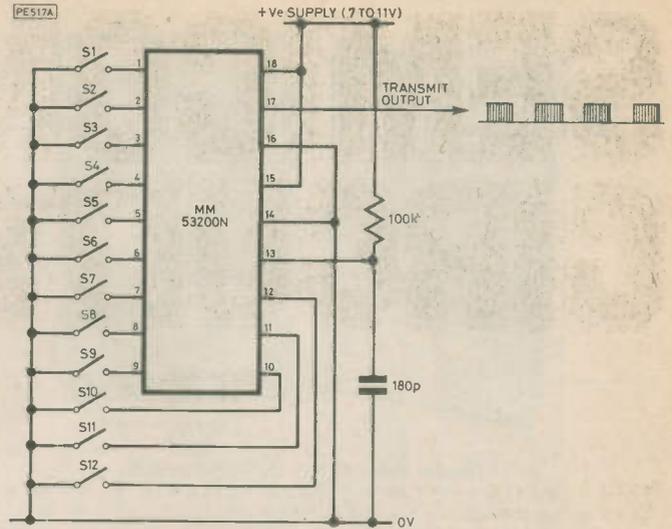


Fig. 3. I.c. in transmit mode

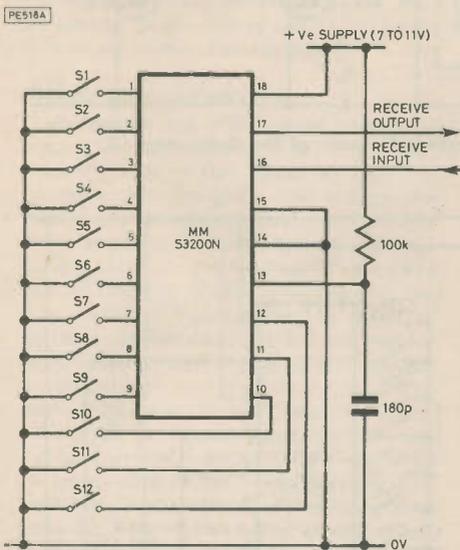


Fig. 4a. I.c. in receive mode

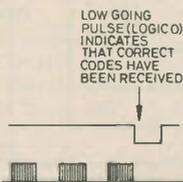


Fig. 4b. Output/input receive waveforms

better at sinking current to 0V than it is at sourcing current from the supply. No maximum current specifications are available from the manufacturer, so to be safe the transmit/receive output should be used either to feed directly into a CMOS input, or to sink current only, at up to 2mA.

The i.c. is almost completely immune to false triggering, largely due to the internal timing which requires valid codes to be received within very definite time windows. Cross interference of devices, even those in very close proximity, is eliminated under almost all conceivable circumstances. However . . . there is

a penalty to be paid! The MM53200N is very critical of incoming waveforms, which must have no 'jitter' on any of the pulse edges and must have a very accurate pulse width or mark/space ratio. The low frequency component of 11.52ms in the waveform, combined with the high frequency demands of accurate pulse width, mean that a fairly wide bandwidth is necessary when communicating between i.c.s. If this communication is via lengths of wire all is well, but when resorting to more esoteric transmission media there can be potential problems! (Many of these can be overcome, of course.) Certainly other types of encoder and decoder i.c.s are more tolerant of serious waveform distortion than the MM53200N, although they cannot usually offer the same high security, high numbers of combinations, or simplicity of use.

### TYPICAL APPLICATIONS

One of the main applications of this i.c. is in security based systems, acting as an electronic lock and key. This is the basis of the applications circuit this month, which also incorporates an infra-red optical link designed to overcome waveform pulse width difficulties over short transmission ranges. Although the i.c. is designed to work at 100kHz, this can easily be varied over a considerable range (assuming that both send and receive circuits

are modified in the same way). No manufacturer's data is available about the limits of frequency variation; however, several different operating frequencies (spaced apart by much more than 30% to prevent the i.c.s locking to the wrong frequency) could give even more effective combinations of codes.

Consider also the use of the i.c.s in a burglar alarm system; they could pass codes over two out of the four cores used in the interwiring of sensors, and could raise the alarm if the cable was cut, shorted, or otherwise interfered with. The i.c.s could also be used as part of a simple remote control system, with up to 4096 devices actuated by one controller. This would be a fairly expensive exercise, however, since the i.c.s cost several pounds each! The bit select inputs, pins 1 to 12, need not be switch controlled, of course; they could be controlled by a logic system, enabling automatic changing of codes or even 'searching' for a specific incoming code. The i.c. could also be used as a 'transponder', reacting to the receipt of one valid code with the transmission of another.


The MM53200N is an i.c. which offers a simple solution to a number of encoding and decoding problems, although care must be taken with the quality of code transmission. It is available from Macro Marketing, Burnham Lane, Slough, Bucks SL1 6LN.

## THE OPTO-LOCK

THIS is an applications project using the MM53200N as a 'security device'. It consists of two parts: a portable 'key' and a fixed 'lock' which is used to interface with a house burglar alarm, car alarm, electrical garage doors, solenoid operated mechanical lock, or whatever else needs turning on or off. It is an optically based design, using infra-red light to carry the coded signal from the key to the lock. The range was designed to be fairly low, from a few centimetres to a metre or so, dependent on ambient light conditions. This is ideal for locking and unlocking an alarm via a

window or windscreen, making the lock and the alarm less vulnerable to being tampered with.

The circuit diagram of the opto-key is shown in Fig. 5. IC1 is used in the transmit mode as already described. TR1, R2, and R3 are arranged so that the output of IC1, pin 17, only sinks current as advised in the specifications. The infra-red emitters, D2 and D3, are driven by the high gain Darlington pair TR3 and TR4. TR2 provides an inverting function between TR1 and TR3 so that the i.e.d.s are turned off when the output of IC1 is at a low

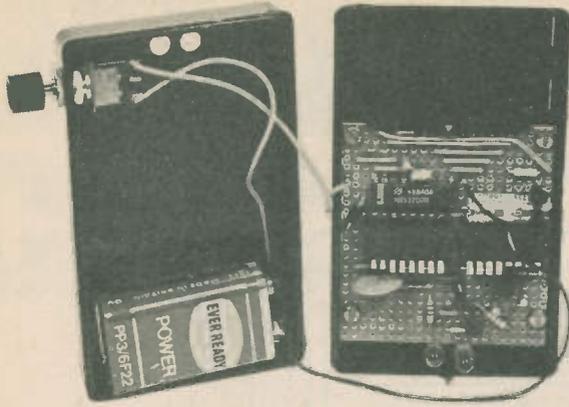

Internal view of the Opto-Key case

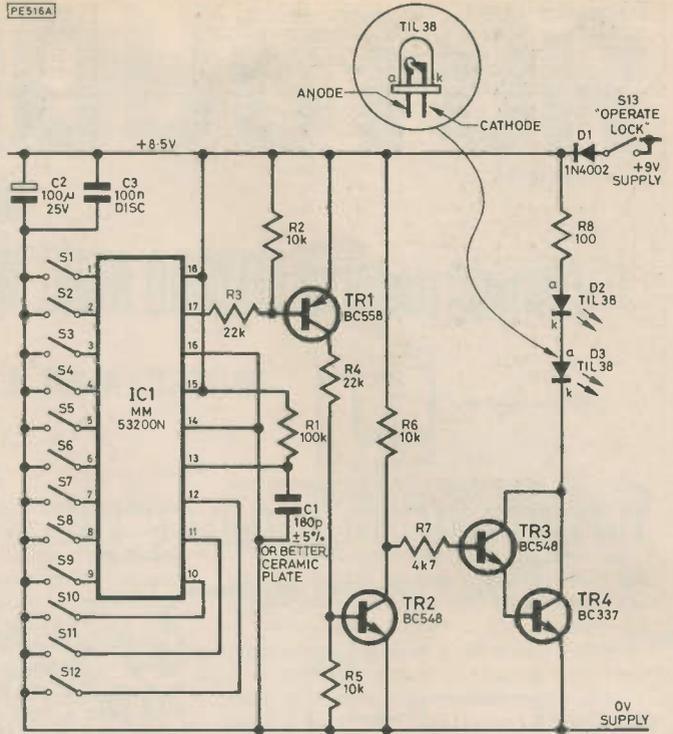
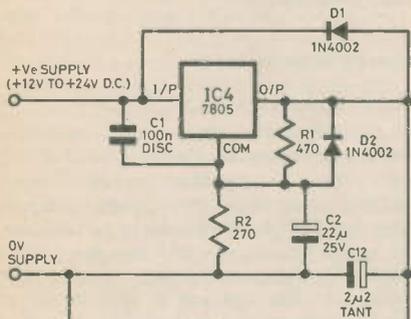


Fig. 5. Circuit diagram of the Opto-Key


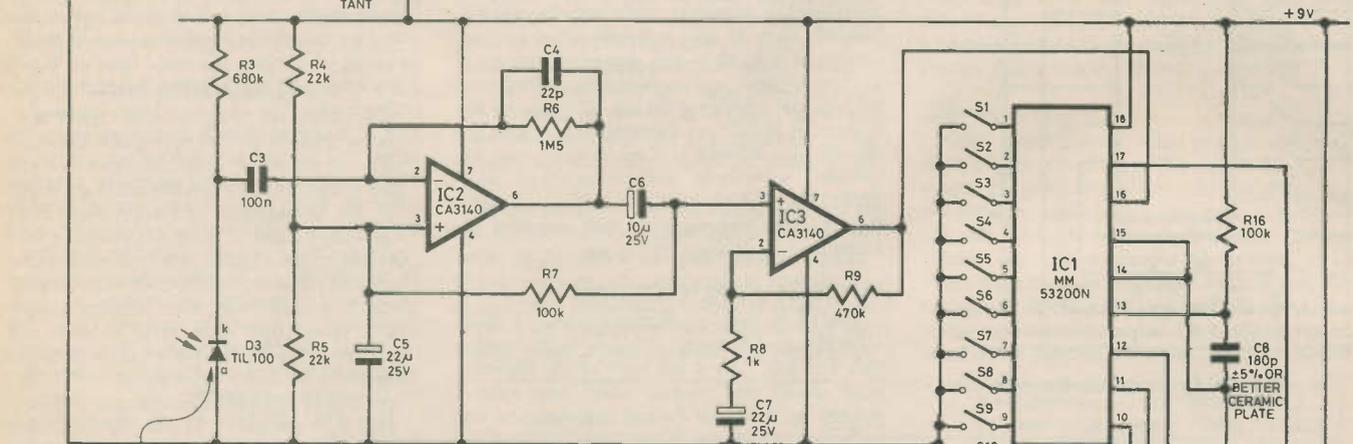
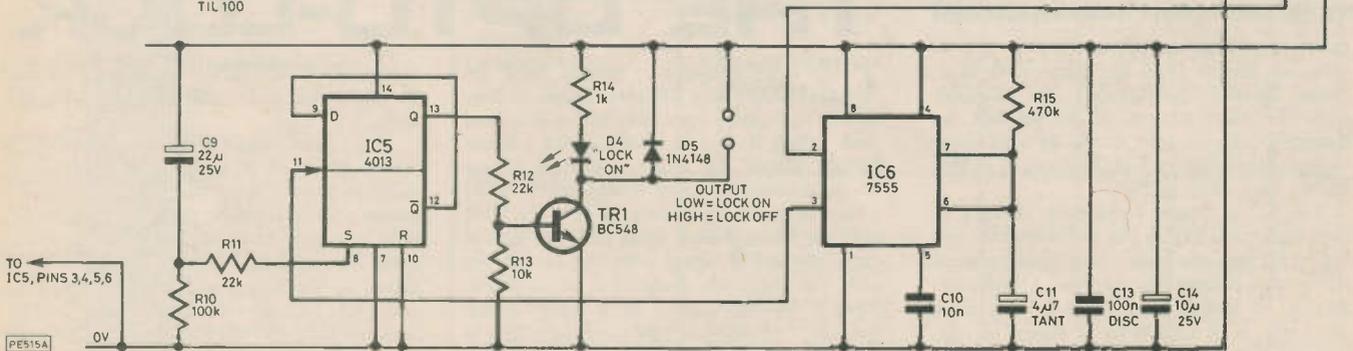


Fig. 6. Circuit diagram of the Opto-Lock

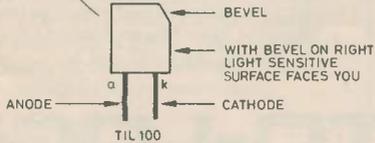

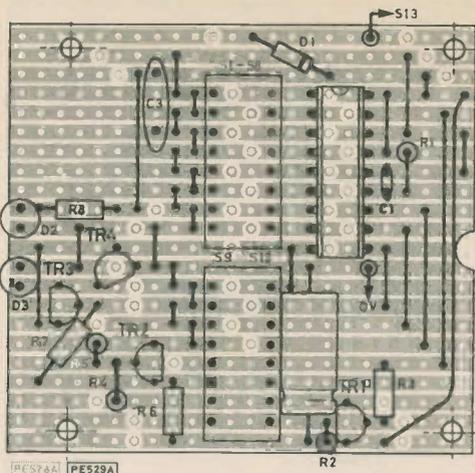


Fig. 7. Veroboard layout of the Opto-Key

level, and on when the output of IC1 is high. This ensures that the emitters are turned on for as little time as possible, minimising power consumption. D1 protects against mis-connection of the battery, and C2 and C3 provide smoothing of the supply.

### RECEIVE CIRCUITRY

The receive side of the system is shown in Fig. 6, the 'opto-lock'. D3 is an infra-red detector diode reverse biased by R3. The leakage current through the diode is dependent on the infra-red radiation falling on it. A f.e.t. input amplifier, IC2, amplifies this leakage current variation. R4, R5, and C5 provide a half rail reference voltage at the non-inverting input, which necessitates the use of C3 to decouple the inverting input. R6 sets the gain of this amplifier and C4 rolls off the frequency response to optimise the waveform shape. The output of IC2 feeds into IC3, which is connected in a non-inverting configuration. R7 biases the non-inverting input to the half rail reference voltage, and C7 decouples the feedback loop. R8 and R9 determine the gain of this stage (471x), the output of which is of sufficient amplitude (normally clipping the rails) that it can be fed directly into the receive input of IC1, which is an MM53200N connected in the receive mode.

The receive output of IC1 triggers a 7555 CMOS timer to give an output duration of a minimum of several seconds when the lock is operated. This output pulse triggers IC5, a D-type flip flop connected as a divide-by-two counter. The first operation of the key will unlock the system, the next will lock it again, the next will unlock it, etc. The inclusion of IC6 ensures that a wait of several seconds must occur between each operation of the lock, reducing the chances of an unauthorised person quickly checking all 4096 possible combinations!

The output of IC5 turns on TR1, which illuminates the 'lock on' l.e.d. and provides an open collector for turning on a low power relay or operating other circuitry. For solenoid or higher power relay switching, extra buffer circuitry should be provided as required. C9, R10, and R11 provide a power-on reset action to ensure that the lock is always turned on when power is first applied, as a failsafe

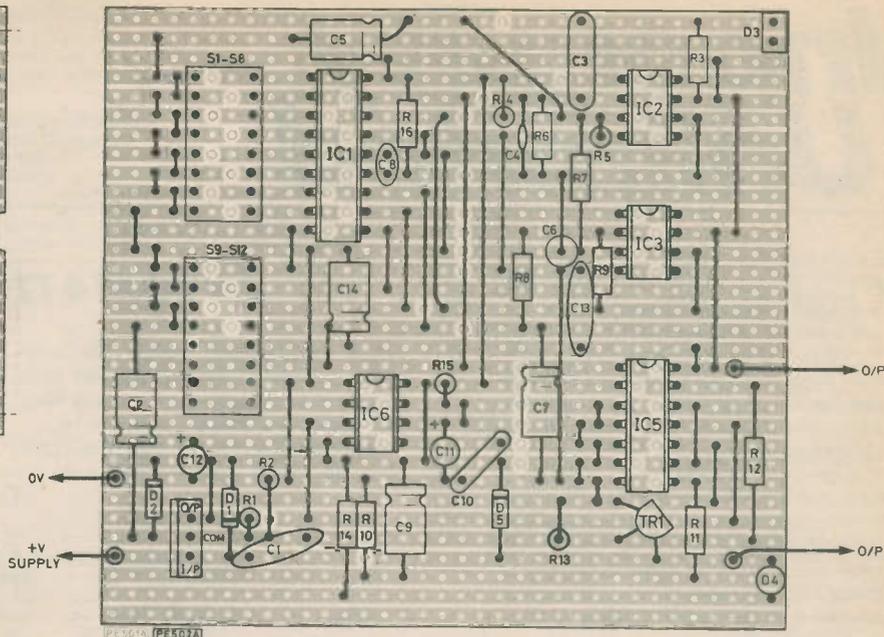


Fig. 8. Veroboard layout of the Opto-Lock

measure. To do the reverse, and turn the lock off when power is first applied, interchange pins 8 and 10, i.e. pin 10 should go to R11, and pin 8 to 0V. Finally, because of the specific supply voltage limits of IC1, a +9V regulator circuit has been provided, using IC4 and associated components. IC4 is actually a 5V device, but the resistive divider in the common lead forces it up to a 9V output. The input to this i.c. can be from +12 to +24V d.c., and a heatsink should not normally be necessary unless a relay or other circuitry also have to be driven from the regulated supply.

### CONSTRUCTION

The circuits are laid out on Veroboard as shown in Figs. 7 and 8. The opto-key has been specifically designed to fit into a plastic West Hyde 'Tinos' case, type TIN600D. This has internal p.c.b. mounting pillars, a battery compartment with a battery clip provided, and a pocket clip. A momentary action switch S13 is mounted at the side on the top half of the case, and a space is allowed for its body on the Veroboard. (See the photograph). Holes should be drilled in the top of the case to allow the infra-red emitters to poke through. These should be left standing well clear of the Veroboard surface so that they do protrude when the case is screwed together. When testing the circuit, be aware that these emitters do not show any visible light; if necessary, temporarily replace them with ordinary l.e.d.s, which should glow with a slight flicker when S13 is operated.

8-way (octal) s.p.s.t. p.c.b. switches have been used to program IC1 in both key and lock circuits to allow for flexible code setting. If preferred, of course, these can be replaced with wire links where appropriate. Since only 12 switches, not 16, are used, the last 4 switches in one bank of 8 are unused. Note that the Veroboard tracks beneath these unused 4 switches are left uncut. Needless to say, the switch settings of lock and key should be

exactly the same! The opto-lock is shown uncased since it will usually be fitted in other equipment. Note carefully the orientation of infra-red sensor D3. The sensor tends to be susceptible to visible light as well as infra-red, and although the circuitry will work quite well without optical filters, the addition of a piece of infra-red transmitting filter in front of D3 will enhance performance considerably; use Kodak type 87 or 87c, or their equivalents, available from many photographic suppliers. A simple lens arrangement will also help to collect the available infra-red radiation most efficiently. D3 and D4 have been arranged at the edge of the board to make it easy to fit the unit into an enclosure while leaving these devices board mounted. If D3 must be taken off the Veroboard, use screened cable to connect it, of as short a length as possible. C4 may have to be changed in value to optimise the waveform shape if this is done.

The circuits are designed to work at a range of several centimetres to a metre or so. Under high ambient light conditions, especially artificial light, the range decreases. At very close proximity of key and lock amplifier IC2 saturates badly, distorting the waveform and preventing detection by IC1. If used in this way, reduce the value of R6 or place several thicknesses of paper directly in front of D3 (both on the lock board) to attenuate the signal.

For ranges greater than one metre, try adding extra stages of amplification and possibly pulse shaping. Extra infra-red emitters can be added to the opto-key, with their own driving stages. Ideally, for optimum range, a high frequency carrier should be used. Indeed, in the prototype system a 200kHz carrier was tried, with a wideband receive amplifier and a phased-locked loop i.c. to extract the modulating envelope and feed it to IC1. The range extended to many metres, but jitter on the capture time of the PLL was sufficient to cause IC1 to fail to read the input reliably.

# Ingenuity Unlimited

A selection of readers' original circuit ideas. Why not submit *your* idea? Any idea published will be awarded payment according to its merits. Each idea submitted must be accompanied by a declaration to the effect that it has been tried and tested, is the original work of the undersigned, and that it has not been offered or accepted for publication elsewhere. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought.

## AUTOMATIC BILGE PUMP

ONE of the chores associated with small boats is the need to bail out rain water etc., often at inconvenient times. Providing a 12V supply is available a small bilge pump will take care of the pumping and the following circuit will ensure the water level is kept to a minimum without constant attention.

A probe is connected to IC1a which is biased so that its output is low, similarly IC1b is connected to a shorter probe and biased in the same way. Both outputs are gated via IC1c whose output is inverted to make TR1 normally off. A third probe is connected to the negative supply to complete the circuit.

As the water level in the bilge rises and touches probe 1 the output from IC1a goes high but has no effect. If the water level rises further so as to touch probe 2 then TR1 will switch on and activate the pump via RLA1. As the water level drops the pump will remain on as the bias for IC1b remains low due to the volt drop at the collector of TR1. As the water level falls further the output of IC1a goes low and the circuit returns to the normal state with the pump turned off.


Obviously the circuit had to be waterproof so it was fitted into a plastic tube. The probes were connected to the circuit board via insulated mains cable. It was found that stainless steel wire (ex fishing

tackle) made suitable probes. The relay should be totally encapsulated and after fitting inside the tube, the tube was filled with potting compound.

It is best to mount the unit close to the centre line of the boat to minimise the ef-

fects of movement. The standby current is only a few microamps, probably less than the normal loss of charge of the battery.

G. W. Coles,  
Polruan,  
Cornwall.

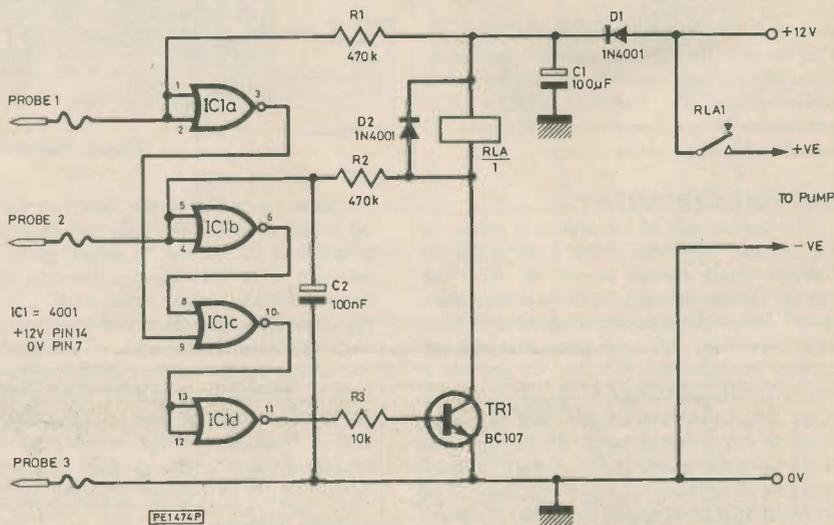

## MICROPOWER REGULATOR

THE voltage regulator described here was designed to power a CMOS microprocessor data logger which had to run for several days from Ni-Cad cells without recharging. An ordinary low power regulator such as a 78L05 con-

sumes several milliamps and thus in a circuit with a very low quiescent current, would contribute quite significantly to the current drain of the batteries. The regulator shown here requires approximately 100µA, and thus gives a considerable saving in battery current. The common or garden low power regulator also requires an input voltage which is about 2 volts above the output voltage, whereas the design given here will work with an input only 0.5 volts above the output voltage, so fewer cells can be used to power the circuit.

The 9491 is a bandgap voltage reference which gives a very stable 1.2V and can operate from a current as low as 50µA. This reference voltage is fed to the inverting input of a CMOS op-amp where it is compared with a fraction of the output voltage. The output of the op-amp drives the base of the BC477 and this transistor increases the output current of the op-amp.

If the output voltage  $V_{out}$  starts to decrease due to increasing load, then the fraction of  $V_{out}$  at the non-inverting input of the op-amp decreases and this causes


the output voltage of the op-amp to fall, and thus turn the transistor on more and so compensate for the increased load.

Pin 8 of the op-amp sets the quiescent current of the op-amp to one of three values. If it is connected to  $V+$  then the quiescent current is 10µA, if connected to  $V-$  then the quiescent current is 1mA, and if connected to a voltage between  $V-$  and  $+0.8V$  or  $V+$  and  $-0.8V$ , then the quiescent current is 100µA. Therefore connecting pin 8 to the reference voltage gives a quiescent current of 100µA. The capacitor across the output prevents any oscillation of the circuit.

Using the component values given, the circuit performs as follows.

$V_{out}$  5.06V with 10mA load  $V_{in}$  minimum = 5.27V  
with 40mA load  $V_{in}$  minimum = 5.57V  
No load current = 112µA


B. Hunter,  
Monifieth,  
Dundee.

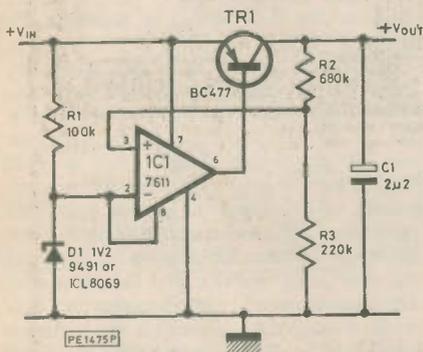
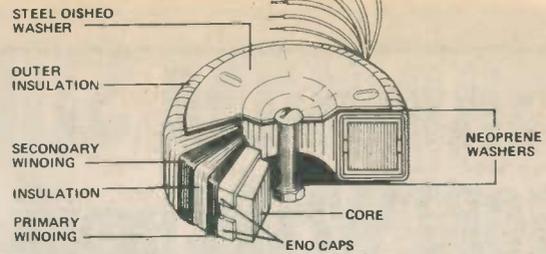
# TOROIDALS

The toroidal transformer is now accepted as the standard in industry, overtaking the obsolete laminated type. Industry has been quick to recognise the advantages toroidals offer in size, weight, lower radiated field and, thanks to I.L.P., PRICE.

Our large standard range is complemented by our **SPECIAL DESIGN** section which can offer a prototype service within 14 DAYS together with a short lead time on quantity orders which can be programmed to your requirements with no price penalty.



15 VA 62 x 34mm 0.35Kg Regulation 19%			50 VA 80 x 35mm 0.9Kg Regulation 13%			120 VA 90 x 40mm 1.2Kg Regulation 11%			225 VA 110 x 45mm 2.2Kg Regulation 7%			500 VA 140 x 60mm 4Kg Regulation 4%		
<b>SERIES</b>	<b>SECONDARY</b>	<b>RMS</b>	2x010	6+6	4.16	4x010	6+6	10.00	6x012	12+12	9.38	8x016	25+25	10.00
<b>No</b>	<b>Volts</b>	<b>Current</b>	4x011	9+9	2.77	4x011	9+9	6.66	6x013	15+15	7.50	8x017	30+30	8.33
0x010	6+6	1.25	2x012	12+12	2.08	4x012	12+12	5.00	6x014	18+18	6.25	8x018	35+35	7.14
0x011	9+9	0.83	2x013	15+15	1.66	4x013	15+15	4.00	6x015	22+22	5.11	8x026	40+40	6.25
0x012	12+12	0.63	2x014	18+18	1.38	4x014	18+18	3.33	6x016	25+25	4.50	8x025	45+45	5.55
0x013	15+15	0.50	2x015	22+22	1.13	4x015	22+22	2.72	6x017	30+30	3.75	8x033	50+50	5.00
0x014	18+18	0.42	2x016	25+25	1.00	4x016	25+25	2.40	6x018	35+35	3.21	8x042	55+55	4.54
0x015	22+22	0.34	2x017	30+30	0.83	4x017	30+30	2.00	6x026	40+40	2.81	8x028	110	4.54
0x016	25+25	0.30	2x028	110	0.45	4x018	35+35	1.71	6x025	45+45	2.50	8x029	220	2.27
0x017	30+30	0.25	2x029	220	0.22	4x025	110	1.09	6x033	50+50	2.25	8x030	240	2.08
(encased in ABS plastic)			2x030	240	0.20	4x025	220	0.54	6x028	110	2.04	625 VA 140 x 75mm 5Kg Regulation 4%		
			80 VA 90 x 30mm 1Kg Regulation 12%			160 VA 110 x 40mm 1.8Kg Regulation 8%			300 VA 110 x 50mm 2.6Kg Regulation 6%			9x017	30+30	10.41
			3x010	6+6	6.64	5x011	9+9	8.89	7x013	15+15	10.00	9x018	35+35	8.92
			3x011	9+9	4.44	5x012	12+12	6.66	7x014	18+18	8.33	9x026	40+40	7.81
			3x012	12+12	3.33	5x013	15+15	5.33	7x015	22+22	6.82	9x025	45+45	6.94
			3x013	15+15	2.66	5x014	18+18	4.44	7x016	25+25	6.00	9x033	50+50	6.25
			3x014	18+18	2.22	5x015	22+22	3.63	7x017	30+30	5.00	9x042	55+55	5.68
			3x015	22+22	1.81	5x016	25+25	3.20	7x018	35+35	4.28	9x028	110	5.88
			3x016	25+25	1.60	5x017	30+30	2.66	7x026	40+40	3.75	9x029	220	2.84
			3x017	30+30	1.33	5x018	35+35	2.28	7x025	45+45	3.33	9x030	240	2.60
			3x028	110	0.72	5x026	40+40	2.00	7x033	50+50	3.00			
			3x029	220	0.36	5x028	110	1.45	7x028	110	2.72			
			3x030	240	0.33	5x029	220	0.72	7x029	220	1.36			
						5x030	240	0.66	7x030	240	1.25			

**Why a Toroid?**

- \* Smaller size & weight to meet modern 'slimline' requirements.
- \* Low electrically induced noise demanded by compact equipment.
- \* High efficiency enabling conservative rating whilst maintaining size advantages.
- \* Lower operating temperature.

**Why ILP?**

- \* Ex-stock delivery for small quantities.
- \* Gold service available. 21 days manufacture for urgent deliveries.
- \* 5 year no quibble guarantee.
- \* Realistic delivery for volume orders.
- \* No price penalty for call off orders.

Price including P&P and VAT

VA	Size	£	VA	Size	£
15	0	5.47	160	5	8.76
30	1	5.84	225	6	11.18
50	2	6.50	300	7	13.04
80	3	7.03	500	8	18.74
120	4	7.79	625	9	23.40

Mail Order — Please make your crossed cheques or postal orders payable to ILP Electronics Ltd.

Trade — We will open your credit account immediately upon receipt of your first order.

Post to: ILP Electronics Ltd., Dept. 6  
Graham Bell House, Roper Close,  
Canterbury, Kent. CT2 7EP  
Tel: (0227) 54778 Telex: 965780



**ILP ELECTRONICS LTD.**

## MASTER ELECTRONICS NOW! The PRACTICAL way!

YOUR CAREER..YOUR FUTURE..YOUR OWN BUSINESS..YOUR HOBBY  
**THIS IS THE AGE OF ELECTRONICS!**  
the world's fastest growth industry...

Our new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn by the practical way in easy steps, mastering all the essentials of your hobby or to start, or further, a career in electronics or as a self-employed servicing engineer. All the training can be carried out in the comfort of your own home and at your own pace.

A tutor is available to whom you can write personally at any time, for advice or help during your work. A Certificate is given at the end of every course.

- You will do the following:
- Build a modern oscilloscope
  - Recognise and handle current electronic components
  - Read, draw and understand circuit diagrams
  - Carry out 40 experiments on basic electronic circuits used in modern equipment using the oscilloscope
  - Build and use digital electronic circuits and current solid state 'chips'
  - Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-Fi, VCR and microprocessor/computer equipment.



**British National Radio & Electronics School Reading, Berks. RG1 1BR**

**FREE!**  
COLOUR  
BROCHURE

Please send your brochure without any obligation to

I am interested in:

- COURSE IN ELECTRONICS as described above
- RADIO AMATEUR LICENCE
- MICROPROCESSORS
- OTHER SUBJECTS please state below

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_

Post now to:

PE/10/842

BLOCK CAPS PLEASE

**British National Radio & Electronics School Reading, Berks. RG1 1BR**



OR TELEPHONE US  
0734 51515 OR  
TELEX 22758  
(24.HR SERVICE)



## Affordable Accuracy - Low Cost Multimeters from Armon

### SPECIFICATION MODELS

#### HC-6010 & HC-7030 DIGITAL

- \* 10 amp AC/DC
- \* Battery: Single 9V drycell. Life 200 hrs.
- \* Dimensions: 170 x 89 x 38mm
- \* Weight: 400g inc. battery
- \* Mode Select: Push Button
- \* AC DC Current: 200µA to 10A
- \* AC Voltage: 200mV to 750V
- \* DC Voltage: 200mV to 1000V
- \* Resistance: 200Ω to 20MΩ
- \* Input Impedance: 10MΩ
- \* Display: 3 1/2 Digit 13mm LCD
- \* O/Load Protection: All ranges

**28 RANGES, EACH WITH FULL OVERLOAD PROTECTION**

HC-7030  
0.1% Accuracy  
£35.95



HC-6010  
0.5% Accuracy  
£29.95



HC-102BZ  
£13.00

### SPECIFICATION

#### HM 102R ANALOGUE

- \* DC Voltage: 0.25, 2.5, 10, 50, 250, 500, 1000 volts, 20,000 ohms/volt.
- \* AC Voltage: 2.5, 10, 50, 250, 500, 1000 volts, 8,000 ohms/volt.
- \* Decibels: -20 to +62dB.
- \* DC Current: 0-50, 500µA, 0-5, 50, 500mA.
- \* Ohmmeter: 0-10 Megohms in 4 ranges, 50 ohms Centre Scale.
- \* Power Supply: One 1.5 V Size 'AA' battery (incl).
- \* Size & Weight: 135 x 91 x 39mm, 280gr.

#### HC 102BZ WITH BUZZER, BATTERY SCALE & 10A DC RANGE

HC 102R  
£11.00

### ARMON ELECTRONICS LTD.

Dept L, Heron House, 109 Wembley Hill Road, Wembley, Middlesex HA9 8AG

Telephone 01-902 4321 (3 lines) Telex No. 923985

Please add 15% to your order for VAT. P&P free of charge. Payment by cheque with order.

Offer applicable to mainland UK only.


Please allow 15 days for delivery.


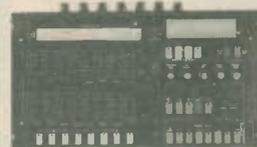
### P.E. HYPERCHASER

4 Channel Pseudo Intelligent Light Unit.  
Kit of Parts **£78.50**

Kit includes PCB, Case, Facia, all you need - Post & Packing inc.



### P.E. STARDESK

8 & 4 Channel light mixer. A full set of parts for this exciting project inc VAT & Carr. **£209**

Telephone your order now on (01) 684 8007

### BENSHAM RECORDING LTD

327 Whitehorse Road, Croydon, Surrey CR0 2HS  
9 am-5 pm, Mon-Sat.

Please allow 14 days for delivery



# ELECTROVALUE



for **CAPACITORS** of all preferred types

**POLYESTER LAYER** (Siemens) B.32509 5mm PCM 10% tolerance 63V. In 13 values from 0.0047 to 0.47µF  
B.32510 7.5mm PCM 10% tolerance 100V min. In 7 values from 0.0047 to 0.47µF  
B.32512 15mm PCM 10% tolerance 100V 1µF, 2.2µF  
B.32560 7.5mm PCM 26 types 10% tolerance 400V 0.001 to 0.0068µF  
9% tolerance from 0.0082 to 0.68µF in 400, 250 & 100V

**CERAMIC PLATE**  
Above 1000pF, in E6 values to 4700pF  
C.333 100Vdc 1.8-4700pF - 10 types  
B.37448 63Vdc 2.5mm PCM 0.01-0.68pF - 5 types  
B.37449 63Vdc 5mm PCM 0.047, 0.68, 0.1µF  
**CERAMIC DISC**  
1nF-10nF, 300Vac  
**ELECTROLYTIC**  
Axial in 48 values from 1 to 10000µF, 10 to 63Vdc  
Canned in 9 values from 2000 to 220000µF, voltages to 350

Reversible from 2 to 100µF  
Low Leak, Almm. 0.1-100µF, 17 values, 6-50Vdc  
Radial 15 values 1-1000µF, 16-63Vdc  
**TANTALUM BEADS**  
in 18 values from 0.1-100µF, 6.3-35Vdc  
**POLYSTYRENE (Siemens)**  
39 values 5pF to 18nF, 160Vdc.  
The above ranges should meet the majority of current requirements. Mention P.E. when sending for our very latest free 40-page A-Z list showing thousands of items of all types.

**BRITAIN'S LEADING QUALITY COMPONENT SUPPLIERS - SEND FOR FREE 40 PAGE A-Z LIST**

ATTRACTIVE DISCOUNTS - FREE POSTAGE - GOOD SERVICE & DELIVERY

### ELECTROVALUE LTD

28 St. Jude's Rd, Englefield Green, Egham, Surrey TW20 0HB.

(0784) 33603 Telex 264475. North: 680 Burnage Lane M/c (061-432 4945)  
EV Computing Shop, 700 Burnage Lane, Manchester M19 1NA (061-431 4866).

ACCESS AND BARCLAYCARD Phoned Orders Welcome

## OVERSEAS ORDERS

Overseas readers are reminded that unless otherwise stated, postage and packing charges published in advertisements apply to the United Kingdom only.

Readers wishing to import goods from the United Kingdom are advised to first obtain from the advertiser(s) concerned an exact quotation of the cost of supplying their requirements carriage paid home.

## CLEF ELECTRONIC MUSIC

### THE NEW CLEF CMS

The FULLY programmable digital synthesiser that you can AFFORD

THE NEW CLEF COMPUTER MUSIC SYSTEM is so user programmable that you need a BBC Micro to run it! 32 harmonically programmable oscillators. 32 programmable envelopes: 5 octave touch sensitive keyboard, up to 4 OSC/ENVS per note. Real time sequencing. Massive potential for future software. Complete system (without BBC Micro) £475 built. Phone or write for details. Modular systems also available.

### MASTER RHYTHM PROGRAMMABLE DRUMS



As Published in P.E.

Twenty-Four Rhythm programmable Drum Machine with twelve instruments. Eight sections are extended to 24/32 measures for two bar programming. Sequence operation and instrument tone adjust. COMPLETE KIT **£79**  
STRING ENSEMBLE **£198.50**  
ROTOR-CHORUS **£98.00**

SQUARE FRONT KEYBOARDS  
88 NOTE £60 49 NOTE £29  
73 NOTE £50 30 NOTE £19  
KEYSWITCH ITEMS ALSO AVAILABLE

### 88/72 NOTE PIANOS SPECIALISTS SINCE 1972

Using Patented electronic technique to give advanced simulation of Piano Key Inertia.

COMPONENT KITS including Keyboard  
88 NOTE **£266**  
72 NOTE **£234**  
The above may also be purchased in four parts.  
DOMESTIC KITS inc. Cabinet, P.A., & Spkr.  
88 NOTE **£442**  
72 NOTE **£398**  
STAGE MODEL inc. Cabinet & Stand  
72 NOTE **£383**



ALL PRICES INC. VAT. CARR & TELEPHONE ADVICE. S.A.E. for full Specs & MANF. PRICES. VISA-ACCESS-AMERICAN EXPRESS. Competitive quotes can be given for export. Allow 3-14 days for normal despatch.

CLEF PRODUCTS (ELECTRONICS) LIMITED  
(Dept P.E.) 44A BRAMHALL LANE SOUTH BRAMHALL  
STOCKPORT CHESHIRE SK7 1AH

As Published in P.E.

### BAND-BOX PROGRAMMABLE BACKING TRIO



THREE PIECE BACKING BAND Generates the sounds of three instrumentalists to back Soloists  
DRUMS + BASS + KEYBOARDS Over 3,000 chord changes (60 scores) on 132 different chords - 16 chord sounds. Master Rhythm also required.  
FULL KIT **£235**

TEL 061-439 3297



When replying to Classified Advertisements please ensure:

- (A) That you have clearly stated your requirements.
- (B) That you have enclosed the right remittance.
- (C) That your name and address is written in block capitals, and
- (D) That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

### RECEIVERS AND COMPONENTS

**TURN YOUR SURPLUS** capacitors, transistors, etc into cash. Contact **COLES HARDING & CO.**, 103 South Brink, Wisbech, Cambs. Tel. 0945 584188. Immediate settlement.

**BOURNEMOUTH/BOSCOMBE.** Electronic components specialists for 33 years. **FORRESTERS (NATIONAL RADIO SUPPLIES)**, Late Holdenhurst Road. Now at 36, Ashley Road, Boscombe. Tel. 302204. Closed Weds.

**FIFTY 74 SERIES ICs** on panel £2.20. Assorted components £5.00/£6.50 7lbs or 10lbs post paid. J. W. BLANSHARD, 2 Barnfield Crescent, Sale, Cheshire M33 1NL.

**TRANSISTORS, RESISTORS, CAPACITORS** and more. Eg. 14 pin di socket 9p. Write or phone for VAT inclusive price list. **HUNT ELECTRONICS**, PO Box 57, Derby, DE6 6SN. Tel. (0283) 703071.

#### RESISTOR PACKS FOR ALL PROJECTS

1/2 watt carbon film resistors 5% 1 ohm to 10M E24 series. Packs of 10 each value (1690 resistors) **£10.00**. Your choice of quantities/values 125 for **£1.00**. VAT and Post Free.

**GORDON HALLETT**  
20 Bull Lane, Malden Newton,  
Dorchester, Dorset DT2 0BQ.

## SMALL ADS

The prepaid rate for classified advertisements is 36 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £12.00 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Electronics and crossed "Lloyds Banks Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Dept., Practical Electronics, Room 2612, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

#### BRAND NEW COMPONENTS BY RETURN

**Electrolytic Capacitors 16V, 25V, 50V.**  
0.47, 1.0, 2.2, 4.7 & 10 Mfds. — 5p.  
22 & 47—6p. 100—7p. (50V—8p) 220—8p. (50V—10p).  
470—11p. (40V—18p). 1000/15V—15p. 1000/25V—25p.  
1000/40V—35p. 4700V/25V—70p.

**Subminiature bead tantalum electrolytics.**  
0.1, 0.22, 0.47, 1.0 @ 35V, 4.7 @ 63V — 14p.  
2.2/35V, 4.7/25V—15p. 10/25V, 15/16V—20p.  
22/16V, 33/10V, 47/6V, 68/3V & 100/3V—32p.  
15/25V, 22/25V, 47/10V—35p. 47/16V—80p.

**Subminiature Ceramic Caps. E12 Series 100V.**  
2% 10 pf. to 47 pf.—3p. 56 pf. to 330 pf.—4p.  
10% 390 pf. to 4700 pf.—4p.

**Vertical Mounting Ceramic Plate Caps. 50V.**  
E12 22 pf. to 1000 pf. E6 1500 pf. to 47000 pf.—2p.

**Polystyrene E12 Series 63V. Horizontal Mtng.**  
10 pf. to 820 pf.—3p. 1000 pf. to 10,000 pf.—4p.

**Miniature Polyester 250V Vert. Mtg. E6 Series.**  
0.1 to 0.68—4p. 1—5p. 15, 22—6p. 33, 47—10p.  
68 — 12p. 1.0 — 15p. 1.5 — 22p. 2.2 — 24p.

**Mylar (Polyester) Film 100V. Vertical Mounting.**  
0.01, 0.022, 0.047—3p. 0.1, 0.22—4p. 0.4, 0.5, 0.1—5p.

**High Stability Miniature Film Resistors 5%.**  
1W E24 Series 0.51R—10MΩ. — 1p.  
1W E12 Series 1R0 to 10MΩ. — 11p.  
1W E12 Series 10R to 10MΩ. — 5p.

**1W metal film E12 Series 10R-1MΩ. 5% — 2p. 1% E24 — 3p.**  
1N4148—2p. 1N4002—4p. 1N4005—6p. 1N4007—7p.  
BC107/8/9—12p. BC147/8/9, BC157/8/9, BF195 & 7—10p.  
8 Pin i.c.'s. 741 Op. amp—18p. 555 Timer—24p.

**DI Holders 8 pin—9p. 14 pin—12p. 16 pin—14p.**  
**LED's. 3 & 5mm. Red—10p. Green & Yellow—14p.**

**Grommets for 3mm—11p. Grommets for 5mm—2p.**  
**20mm. Q.B. Fuses 15, 25, 5, 1, 2, 3 & 5A—5p.**  
**20mm. Anti Surge 100mA to 50A—8p.**  
**20mm. Fuseholders P.C. or Chassis Mtg—8p.**

**Battery Snaps (pairs) PP3—6p. PP9—12p.**  
**400mW Zener diodes 24 series 2W to 33V—8p.**  
Prices VAT inclusive Post 20p. (Free over £5.00).

#### THE C.R. SUPPLY CO.

127, Chesterfield Rd., Sheffield S8 0RN.

### SOFTWARE

#### 6809 CPU CARD

Powerful Add-on to Your Home Computer

Quality, plated through PCB with full assembly instructions. Full RS232 Serial Interface (up to 19,200 Baud). Data storage to cassette (via external CUTS interface). Versatile Parallel Interface for control applications, or keyboard and printer. Operation at 1MHz or 2MHz. 2K/8K Static Ram with 2K/8K EPROM, or alternatively, 4K/16K EPROM (2 sockets). Communication via serial link to your home computer. Software available: Monitor, Disassembler, Editor/Assembler. Coming soon: FORTH Programming Language, Floppy Disk Interface, EPROM Programmer, and others.

Prices: PCB only £29.95; with Monitor £39.95; Monitor + Disassembler £14.95; Upgrade £5; Mon + Dis + Editor/Assembler £34.95; Upgrade £20.

**SOLASCAN MICRO-SYSTEMS LIMITED**  
91 Bryanston Road,  
Bitterne, Southampton SO2 7AL.

### NOTICE TO READERS

Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser to check both prices and availability of goods before ordering from non-current issues of the magazine.

### HOME SECURITY

## SECURITY Alarm Systems

FREE COMPREHENSIVE CATALOGUE!

- LOWEST DISCOUNT PRICES
- HIGHEST QUALITY EQUIPMENT
- FREE DIY DESIGN GUIDE
- FULLY ILLUSTRATED
- MICROCHIP CIRCUITRY
- QUICK DESPATCH SERVICE
- FULL INSTRUCTIONS

SEND SAE DR PHONE

**C-TEC SECURITY, Dept PW**  
60 Market St, Wigan WN1 1HX  
Telephone (0942) 42444



**WHO CAN PUT A PRICE ON A PEACE OF MIND**  
PROFESSIONAL EQUIPMENT AT LOW! LOW! PRICES.  
**HOME SECURITY IS NOW AVAILABLE AT TRADE PRICES**  
ADVANCED SECURITY PRODUCTS LTD  
2 Ealing Road, Aintree,  
Liverpool L9 0HU, Merseyside.  
Tel: 051-525 3440  
FREE CATALOGUE PHONE OR S.A.E.

### ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Practical Electronics for.....

insertions. I enclose Cheque/P.O. for £.....

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Practical Electronics)


NAME .....

ADDRESS .....

Company registered in England. Registered No. 53626. Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS.

Send to: Classified Department,

**PRACTICAL ELECTRONICS**  
Classified Advertisement Dept, Room 2612,  
King's Reach Tower, Stamford Street,  
London SE1 9LS. Telephone 01-261 5846

Rate:  
36p per word, minimum 12 words. Box No. 60p extra.

10/84

# F.I.Diag.E

Formed in 1981 in recognition of the special knowledge and skills required by persons involved in fault diagnosis, plant management and maintenance engineering.

At the present admission is based solely on competence and capability without regard to age or academic attainments.

To obtain further particulars send a fully stamped and addressed envelope to:

**INSTITUTION OF DIAGNOSTIC ENGINEERS**  
3 Wycliffe Street, Leicester LE1 5LR61, England

## EDUCATIONAL/TUITION

### IMPROVE YOUR PROSPECTS

with skills all employers want. Train the easy way with modern home study courses from Ideal Schools.

#### MODERN ELECTRONICS

Takes you from the beginning, right up to C & G level 2 and BTEC national level.

#### COMPUTER PROGRAMMING

Learn BASIC with a Spectrum included if you wish.

For free booklet, write today to:



**IDEAL SCHOOLS**  
(Ref. PE1) Freepost,  
Woking,  
Surrey GU21 4BR.

## SERVICE SHEETS

**BELL'S TELEVISION SERVICES** for service sheets on Radio, TV, etc. £1.50 plus SAE. Colour TV Service Manuals on request. SAE with enquiries to B.T.S., 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 55885.

## FOR SALE

**PRACTICAL ELECTRONICS** November 1964 to December 1976. Clean, in binders. Details: (0332) 703996.

**SHEET METAL FOLDERS** 18" x 18G, bench or vice held £38. Leaflet, 01-890 7838. 90 Granville Avenue, Feltham, Middx. TW13 4JN.

## BOOKS AND PUBLICATIONS

**FULL SIZE SERVICE SHEETS** £2 + L.S.A.E.; CTV/MusC £3 + L.S.A.E. Repair/circs almost any named TV/VCR £9.50. L.S.A.E. free quotations for manuals, sheets - free mag inc. service sheets. T.I.S.P.E., 76 Church Street, Larkhall, Lanarks. Phone 0698 883334.

## SERVICES

### INVENTORS

Think of something new?  
Write it down!—

American industry offers potential royalties for your innovations and new products. We offer free confidential disclosure registration and initial consultation in London regarding your idea's potential value. Write without delay for your free information package.

**American Inventors Corporation**  
82, Broad Street, Dept PT  
Westfield, Massachusetts 01086  
United States of America.

A fee based marketing company.

## MISCELLANEOUS

**SUPERB INSTRUMENT CASES** by Bazelli. manufactured from PVC faced steel. Vast range. Competitive prices start at a low £1.50. Punching facilities at very competitive prices. — **BAZELLI** (Dept 23), St Wilfreds, Foundry Lane, Halton, Lancaster LA2 6LT.

**ELECTRONIC ORGAN KEYBOARDS** and other parts being cleared out as special offer. **ELVINS ELECTRONIC MUSICAL INSTRUMENTS**, 40a Dalston Lane, London E8. Tel. 01-986 8455.

THE SCIENTIFIC WIRE COMPANY				
811 Forest Road, London E17. Telephone 01-531 1568				
ENAMELLED COPPER WIRE				
SWG	1 lb	8 oz	4 oz	2 oz
8 to 34	3.63	2.09	1.10	0.88
35 to 39	3.82	2.31	1.27	0.93
40 to 43	6.00	3.20	2.25	1.61
44 to 47	8.67	5.80	3.49	2.75
48	15.96	9.58	6.38	3.69
SILVER PLATED COPPER WIRE				
14 to 30	9.09	5.20	2.93	1.97
TINNED COPPER WIRE				
14 to 30	3.97	2.41	1.39	0.94
Fluxcore	5.90	3.25	1.82	0.94
Solder				

Prices include P&P VAT. Orders under £2 add 20p. SAE for list of copper and resistance wire. Dealer enquiries welcome.

**BATTERIES.** Button cells AG10 12mm x 4mm. £3 for 10. **STANKIEWICZ**, 5 Marine Drive, Rottingdean, Brighton BN2 7HJ.

**BURGLAR ALARM EQUIPMENT.** Ring Bradford (0274) 308920 for our Catalogue or call at our large showrooms opposite Odsal Stadium.

**CLEARING LABORATORY:** scopes, generators, P.S.U.'s, bridges, analysers, meters, recorders, etc. 0403-76236.

**TEKTRONIX OSCILLOSCOPES**, all types, lowest prices. Telequipment S51E £80 delivered. Details: **SINCLARE** 01-316 1779.

**HEATHKIT.** U.K. spares and service centre. **CEDAR ELECTRONICS**, Unit 12, Station Drive, Bredon, Tewkesbury, Glos. Tel. (0684) 73127.

## CABINET FITTINGS

Fretcloths, Coverings, Handles, Castors, Flight Case Locks & Parts, Jacks, XLRs, Bulgins, Reverb Trays, P & N mic Stands, ASS Glassfibre Horns, CELESTION POWER Speakers.

**ADAM HALL SUPPLIES LTD.**

Send  
30p cheque/  
P.O. for illustrated  
catalogue. Adam Hall (PE Supplies),  
Unit G, Carlton Court, Grainger Road,  
Southend-on-Sea.

# Leader of the Packs

## AC/DC COMPONENT PACKS

Pack No	Qty	Description	Price
TF 11	12	RED 5mm LED	£1.00
TF 12	30	500mz ZENERS 5%	£1.00
TF 15	50	1 amp Rect. Diodes in 4000 series	£1.00
TF 16	6	1 amp Bridge Rect.	£1.00
TF 17	100	Transistor pads	£1.00
TF 18	20	A/S Fuses 20mm	£1.00
TF 19	10	3A Rect. Diodes	£1.00
TF 110	2	ORP 12	£1.00
TF 111	5	BR 100 DIAC	£1.00
TF 112	10	BC109B	£1.00
TF 113	10	LC's all different	£1.00
TF 114	50	BFR 86	£1.00
TF 115	12	8 pin DIL sockets	£1.00
TF 116	20	10mm Horiz. Pre set (10 values)	£1.00
TF 117	10	Slide Pots - 3K all the same	£1.00
TF 118	10	Mixed Pots	£1.00
TF 119	10	Feed throughs	£1.00
TF 120	25	Electrolytic Caps	£1.00
TF 121	50	Polyester Caps	£1.00
TF 122	100	Mixed Resistors - Incl. Wire Wound	£1.00
TF 123	100	Mixed Transistor Hardware	£1.00
TF 124	25	5mm LED clips and rings	£1.00
TF 125	10	BC 107	£1.00
TF 126	10	BC 108	£1.00
TF 127	6	Green 5mm LED	£1.00
TF 128	6	Yellow 5mm LED	£1.00
TF 129	150 approx.	Mixed nuts/bolts/washers/self tapper	£1.00
TF 130	25	Mixed Electrolytics Axial	£1.00
TF 131	25	Mixed Electrolytics Radial	£1.00
TF 132	50	Mixed Polyester Axial	£1.00
TF 133	50	Mixed Polyester Radial	£1.00
TF 134	15	BC 337	£1.00
TF 135	20	500MA A/S 20mm Fuse	£1.00
TF 136	50	Mixed Ceramic Discs	£1.00
TF 137	50	Mixed Ceramic Plates	£1.00
TF 21	200	47 pf 160V Polystone Cap	£2.00
TF 22	10	LM 3900 N	£2.00
TF 23	10	Mixed DTL	£2.00
TF 24	5	4700 mf 25V Tag Elect 2" x 1"	£2.00
TF 25	10	1000 mf 63V Ax Elect	£2.00
TF 26	50	.022 mf 400V RAD POLY	£2.00
TF 27	10	100 mf 250V Ax	£2.00
TF 28	10	2.2 mf 160V Polyester RAD	£2.00
TF 29	10	VDR's	£2.00
TF 210	10	Mixed TTL (74 series)	£2.00
TF 211	4	2N 3055 H(RCA)	£2.00
TF 213	200	IN 4151 Diodes	£2.00
TF 214	200	IN 4148 Diodes	£2.00
TF 51	100	White/Red 5mm LED	£5.00
TF 52	50	BC 108C	£5.00
TF 53	2	10,000 mf 63V Comp. grade	£5.00
TF 54	½KG	Reel 22g ersin multicore	£5.00
TF 55	10	2N3055 H(RCA)	£5.00
TF 56	5	OC71	£5.00
TF 57	3	10,000 mf 40V Comp. grade elect	£5.00
TF 58	720	½W Carbon film 1Ω-10MΩ ten values	£5.00

ALL PRICES INCLUDE VAT - ALL GOODS BRAND NEW & NORMALLY DESPATCHED BY RETURN POST.  
TERMS: Cash with order. POST & PACKING: Please add 75p to total order.

**AC/DC ELECTRONICS COMPONENTS**  
DEPT P.E., 45 CHURCH STREET,  
ENFIELD, MIDDLESEX.

# ★ BAKER ★

## GROUP P.A. DISCO AMPLIFIERS post £2

150 watt Output, 4 input Mixer pre-amp Illustrated	£99
150 watt Output, Slave 500 mv. Input 3 Speaker Outputs	£80
150+150 watt Stereo, 300 watt Mono Slave 500 mv. Inputs	£125
150 watt P.A. Vocal, 8 inputs, High/Low Mixer Echo Socket	£129
100 watt Valve Model, 4 inputs, 5 Outputs, Heavy duty	£125
60 watt Valve Model, 4 inputs, Low Imp and 100V line output	£69
60 watt Mobile 240V AC and 12V DC. 4-8-16 ohm 4-100V line	£69

## BAKER LOUDSPEAKERS

Type	Model	Size	Watts	Ohms	Price
P.A./Disco/Group	DG50/10	10	50	8/16	£18.00
Midrange	Mid 100/10	10	100	8	£25.00
Hi-Fi	Major	12in	30	4/8/16	£16.00
Hi-Fi	Superb	12in	30	8/16	£26.00
P.A./Disco/Group	DG45	12in	45	4/8/16	£16.00
Hi-Fi	Wooler	12in	90	8	£25.00
Hi-Fi	Auditorium	15in	60	8/16	£37.00
P.A./Disco/Group	DG75	12in	75	4/8/16	£20.00
P.A./Disco/Group	DG100	12in	100	8/16	£26.00
P.A./Disco/Group	DG100/15	15in	100	8/16	£35.00

DISCO CONSOLE Twin Decks, mixer pre amp £105. Carr £12.  
COMPLETE DISCO 150 watt £330; 300 watt £390. Carr £30.

DISCO MIXER. 240V, 4 stereo channels, 2 magnetic, 2 ceramic/ tape, 1 mono mic channel, twin v.u. meters, headphone monitor outlet, slider controls, panel or desk mounting, grained aluminium fascia. VU output facility. £49. Post £1.

DELUXE STEREO DISCO MIXER/EQUALISER as above plus L.E.D. V.U. displays 5 band graphic equaliser, left/right fader, switchable inputs for phone/line, mike/line. Headphone Monitor, Mike Talkover Switch As above with 7 Band Graphic £128. **£118 PP £2**

P.A. CABINETS (empty) Single 12 £30; Double 12 £36. Carr £10.  
WITH SPEAKERS 60W £27; 75W £52; 90W £71; 150W £80.  
HORNBOXES 200 Watt £30, 300 Watt £35. Post £4.

WATERPROOF HORNS 8 ohms, 25 watt £20, 30 watt £23, 40 watt £29, 20V plus 100 volt line £38. Post £2.  
MOTOROLA PI220 ELECTRONIC 40RM TWEETER, 3in square £5  
100 watts. No crossover required. 4-8-16 ohm, 7 1/2 x 3in. £10

CROSSOVERS. TWO-WAY 3000 cps 40 watt rating, £4, 80 watt £6, 100 watt £10.  
3 way 950 cps/3000 cps 40 watt rating, £4, 80 watt £6, 100 watt £10.  
LOUDSPEAKER BARGAINS Please enquire, many others in stock  
4 ohm, 5in, 7x4in £2.50; 6in, 8x5in £3.8in, £3.50, 6in, 20W £7.50.  
8 ohm, 2in, 3in £2; 5x3in, 6x4in, 7x4in, 5in £2.50; 6in, 20W £7.50; 8 x 5in £3; 8in £4.50; 10in £5; 12in £6, 8in, 25W £8.50.  
15 ohm, 2in, 3in, 5x3in, 6x4in, 7x4in, 5in 10W £5, 8in, £4, 10in, £7, 25 ohm, 3in, £2; 5x3in, 6x4in, 7x4in, £2.50, 120 ohm, 3in dia, £1.

Make	Model	Size	Watts	Ohms	Price
AUDAX	WOODFER	5in	25	8	£10.50 £1
GOODMANS	HIFAX	7 1/2 x 4in	100	8	£30 £2
GOODMANS	HB WOODFER	8in	60	8	£13.50 £1
WHARFEDALE	WOODFER	8in	30	8	£9.50 £2
CELESTION	DISCO/Group	10in	50	8/16	£21 £2
GOODMANS	HPO/Group	12in	120	8/15	£29.50 £2
GOODMANS	HPO/DISCO	12in	120	8/15	£29.50 £2
GOODMANS	HP/BASS	15in	250	8	£72 £4
GOODMANS	HPO/BASS	18in	230	8	£84 £4

## RCS SOUND TO LIGHT CONTROLLER KIT

Printed circuit. Cabinet, 3 channels, 1,000 watts each. Will operate from Hi-Fi or Disco. £19. Post £1.  
Ready Built Deluxe 4 Channel 4,000 watt with chaser + speed + programme controls £69. Post £2.

## MAINS TRANSFORMERS

Model	Price Post
250-0-250V 80mA, 6.3V 3.5A 6.3V 1A	£7.00 £2
350-0-350V 250mA, 6.3V 6A CT £12.00 Shrouded	£14.00 £2
250V 60mA, 6.3V 2A	£4.75 £1
220V 25mA, 6V 1 Amp £3.00 220V 45mA, 6V 2 Amp	£4.00 £1
Low voltage tapped outputs available	
1 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£6.00 £2
ditto 2 amp £10.50 3 amp £12.50 5 amp £16.00 £2	

LOW VOLTAGE MAINS TRANSFORMERS £5.50 each post paid 9V, 3V, 2A; 12V, 3A; 16V, 2A; 20V, 1A; 30V, 1A; 30V, 5A-17-0-17V, 2A; 35V, 2A; 20-0-20V, 1A; 12-0-12V, 2A; 20-0-20V, 1A; 25-0-25V, 2A.

## £8.50 post 50p MINI-MULTI TESTER

Deluxe pocket size precision moving coil impedance + Capacity 4000 ohms. Battery included. 11 instant ranges measure: DC volts 5, 25, 250, 500, AC volts 10, 50, 500, 1000, DC amps 0-250µA; 0-250mA. Resistance 0 to 600K ohms.

De-Luxe Range Doubler Meter, 50,000 o.p.v. 7 x 5 x 2in. Resistance 0/20 meg in 5 ranges. Current 50µA to 10A. Volts 25/1000V DC, 10V/1000V AC. £21.00 post £1.

## PANEL METERS

£5.50 post 50p  
50µA, 100µA, 500µA, 1mA, 5mA, 100mA, 500mA, 1 amp, 2 amp, 5 amp, 25 volt, VU 2 1/2 x 1 1/2 Stereo VU 3 1/2 x 1 1/2.

ALUMINIUM CHASSIS 18 s.w.g. 4 sides, riveted corners: 6 x 4 x 2 1/2in. £1.75; 8 x 6 x 2 1/2in. £2.20; 14 x 9 x 2 1/2in. £3.60; 12 x 3 x 2 1/2in. £1.80; 12 x 8 x 2 1/2in. £3.20.

ALL ANGLE BRACKET 6 x 3 x 1/2in. 30p.  
ALUMINIUM PANELS 18 s.w.g. 12 x 12in. £1.80; 14 x 9in. £1.75; 6 x 4in. 55p; 12 x 8in. £1.30; 10 x 7in. 96p; 8 x 6in. 90p; 14 x 3in. 72p; 12 x 5in. 90p; 16 x 10in. £2.10; 16 x 6in. £1.30.

ALUMINIUM BOXES. MANY OTHER SIZES IN STOCK.  
4 x 2 x 2in. £1.20; 3 x 2 x 2in. £1; 6 x 4 x 2in. £1.90; 8 x 6 x 3in. £3.00; 12 x 5 x 3in. £3.60; 6 x 4 x 3in. £2.20; 10 x 7 x 3in. £3.60; 7 x 5 x 3in. £2.90; 12 x 8 x 3in. £4.30.

HIGH VOLTAGE ELECTROLYTICS 32+32+32/450V £1.50  
20/500V 75p 8+8/500V £1 125/500V £2  
32/350V 45p 8+16/450V 75p 220/400V £2  
32/500V 95p 16+16/350V 75p 16+32+32/500V £2

## SINGLE PLAY DECKS Post £2

Make	Model	Cartridge	Price
BSR	P170	Ceramic	£20
GARRARD	6200	Ceramic	£22
BSR	PIB2	Ceramic	£26
BSR	P232	Magnetic	£28
BSR	P200	Magnetic	£34
AUTOCHANGER	BSR	Ceramic	£20

DECCA TEAK VENEERED PLINTH Superior finish with space and panel for small amplifier. Board cut for BSR or Garrard 18 1/2in. x 14 1/2in. x 4in. Black/chrome fascia trim. Tinted plastic cover £5 Post £1

TINTED PLASTIC COVERS for Decks, Music Centres, etc. Post £1  
17 x 12 1/2 x 3 1/2in. £5 16 1/2 x 13 x 4in. £5  
22 1/2 x 13 1/2 x 3 1/2in. £5 17 1/2 x 13 1/2 x 2 1/2in. £5  
21 1/2 x 14 1/2 x 2 1/2in. £5 17 1/2 x 13 1/2 x 4 1/2in. £5  
14 1/2 x 13 x 3 1/2in. £5 21 x 13 1/2 x 4 1/2in. £5  
18 1/2 x 12 1/2 x 3 1/2in. £5 30 1/2 x 13 1/2 x 3 1/2in. £5  
14 1/2 x 12 1/2 x 2 1/2in. £5

## RADIO COMPONENT SPECIALISTS

Dept 3, 337, WHITEHORSE ROAD, CROYDON SURREY, U.K. Tel: 01-684 1665  
Post 5p Minimum Callers Welcome. Lists 32p Same day despatch Closed Wed.



# ADVANCED TELECOMMUNICATIONS

## Careers with extensive scope at Cheltenham

Join the Government Communications Headquarters, one of the world's foremost centres for R & D and production in voice/data communications ranging from HF to satellite - and their security. Some of GCHQ's facilities are unique and there is substantial emphasis on creative solutions for solving complex communications problems using state-of-the-art techniques including computer/microprocessor applications. Current opportunities are for:

### Telecommunication Technical Officers

Two levels of entry providing two salary scales: £6262 - £8580 & £8420 - £9522

Minimum qualifications are TEC/SCOTEC in Electronics/Telecommunications or a similar discipline or C & G Part II Telecommunications Technicians Certificate or Part I plus Maths B, Telecommunication Principles B and either Radio Line Transmission B or Computers B or equivalent: ONC in Electrical, Electronics or Telecommunications Engineering or a CIE Part I Pass, or formal approved Service technical training. Additionally, at least 4 years' (lower level) or seven years' (higher level) appropriate experience is essential in either radio communications or radar, data, computer or similar electronic systems.

At the lower entry level first line technical/supervisory control of technicians involves "hands-on" participation and may involve individual work of a highly technical nature. The higher level involves application of technical knowledge and experience to work planning including implementation of medium to large scale projects.

### Radio Technicians - £5485 - £7818

To provide all aspects of technical support. Promotion prospects are good and linked with active encouragement to acquire further skills and experience. Minimum qualifications are a TEC Certificate in Telecommunications or equivalent plus 2 or more years' practical experience.

Cheltenham, a handsome Regency town, is finely-endowed with cultural, sports and other facilities which are equally available in nearby Gloucester. Close to some of Britain's most magnificent countryside, the area also offers reasonably-priced housing. Relocation assistance may be available.

For further information and your application form, please telephone: Cheltenham (0242) 32912/3 or write to:



Recruitment Office, Government Communications Headquarters, Oakley, Priors Road, Cheltenham, Gloucestershire, GL52 5AJ.

# INDEX TO ADVERTISERS

AC/DC Electronics	63
Advance Security Products Ltd	62
American Inventors Corporation	63
Armon Electronics	61
Bensham Recordings	61
Bicc Vero	15
Bi-Pak	5
British National Radio & Electronics School	59
Clef Products	61
C.R. Supply Co.	62
Cricklewood	Cover III
C-Tec Security	62
Cybernetic Applications	Cover II
Data Fax	26
Electrovalue	61
G.C.H.Q.	64
Hallet Gordon	62
Hall Supplies, Adam	63
Hewlett Packard	47
ICS Intertext	4
Ideal Scores	63
ILP Electronics	59
Institute of Diagnostic Engineers	63
Mail Order Micro	25
Maplin Supplies	Cover IV
Modern Book Co.	64
Phonosonics	15
Powertran	6
Radio Component Specialists	64
Riscomp	26
Scientific Wire Co.	63
Service Trading	42
Solarscan Ltd.	62
Sparkrite	4
Swanley Electronics	4
T.K. Electronics	48
Watford Electronics	23

# FAULT DIAGNOSIS OF DIGITAL SYSTEMS

by Cannon, D. (Texas Ins.) Price: £9.50

A GUIDE TO PRINTED CIRCUIT BOARD DESIGN by C. Hamilton Price: £8.00

PRINCIPLES OF TRANSISTOR CIRCUITS by S.W. Amos Price: £8.20

CIRCUITS & SYSTEMS A MODERN APPROACH by A. Papoulis Price: £11.00

DIGITAL ELECTRONICS PRACTICE USING INTEGRATED CIRCUITS by R.P. Jain Price: £8.00

SCR MANUAL INCL. TRIACS & OTHER THYRISTORS by G.E.C. USA Price: £15.00

THE ART OF ELECTRONICS by Horowitz/Hill Price: £18.00

A PRACTICAL INTRODUCTION TO ELECTRONIC CIRCUITS by M.H. Jones Price: £8.20

DOMESTIC VIDEOCASSETTE RECORDERS A SERVICING GUIDE by S. Beeching Price: £15.50

1984 THE RADIO AMATEUR'S HANDBOOK by A.R.R.L. Price: £12.00

☆ PRICES INCLUDE POSTAGE & PACKING ☆

# THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST of British and American Technical Books

19-21 PRAED STREET LONDON W2 1NP

Phone 01-402 9176

Closed Saturday 1 p.m.

Please allow 14 days for reply or delivery.