TELEVISION

PLQ ! JPE ! ! !

!!! **cl** PLQ

AND HOME ELECTRONICS REPAIROCTOBER 2001 £3.00POINT SOME (f point f po



Hard-disk video recording DVD players revealed Servicing the NEI CE25/28 Satellite, PC, Monitor, TV, VCR and DVD faults

Not everything is as tempting as it first appears...

Video heads for example. Are you tempted to turn away VCR repairs due to the high cost of manufacturers replacement video heads? Or perhaps your tempted to use any head you can get your hands on just as long as its cheap and hope that it works OK. There is an alternative.

'The Classic video head.'

Classic video heads are manufactured by Futek one of the worlds leaders in head technology and suppliers of 100,000s of video heads every year to VCR manufacturers.

Designed by experts from drum to tip each head is performance matched to the original. The quality of the Classic video head is confirmed by its use in some of the worlds largest video copying houses where performance and life are the critical characteristics required.

The Classic video head provides the ideal solution where ease of fitting, performance, life and cost control are important to you and the range of video heads stocked covers most manufacturers and models

For more information on the entire Classic range and details of a distributor near you, call 01635 278678, visit us on the web; www.classic-electronics.co.uk or email us at sales@classic-electronics.co.uk



Technical helpline 01635 278678



CONTENTS October 2001 Vol. 51, No. 12

707 Seeds of the future

708 Teletopics

DVD developments. Networked home trial. New video equipment. Manufacturing moves.

714 Panasonic's plasma displays

The display produced by a plasma panel has perfect colour purity, perfect convergence and perfect focusing across the whole screen. The panel can have a viewing angle of 160°, and you can hang it on the wall. Brian Storm investigates Panasonic's PDP technology. A number of interesting technical features contribute to the excellent pictures provided.

720 Hard-disk video systems

The various videotape and optical-disc recording formats have now been joined by hard-disk recording systems such as TiVo and Sky+. George Cole describes the technologies and products available in the UK and elsewhere.



726 Servicing the NEI CE25/CE28 series chassis

These chassis, made in Spain or Turkey, were used in a number of different models. In this initial instalment Alan Dent provides a detailed guide to fault-finding in the power supply, timebase and RGB output sections of the chassis.

730 Audio faults

Hints and tips on repairing professional and consumer equipment.

732 What a life

The joys of tench fishing. An early start then a mixed bag of TV faults – also a camcorder problem. Donald Bullock's servicing commentary.



734 DVD player servicing In this second part of his current series K.F. Ibrahim

In this second part of his current series K.F. Ibrahim starts an account of how DVD players work. The basic block diagram description is followed by an investigation of the laser unit then the derivation of error signals and the operation of the servo system.

738 DX and satellite reception

Terrestrial DX and satellite TV reception reports. News on broadcast TV and satellite band changes. An international DTT update. Aerials for Band I reception. Roger Bunney reports.

742 TV fault finding

746 Monitors

Guidance on repairing computer and other monitors.

748 VCR clinic

749 Help wanted

750 Jack's workshop

Snowy pictures, a Grundig digibox problem and a replacement capacitor kit for the Amstrad DRX100 digibox.

751 Test case 466

752 Satellite notebook

BBC satellite radio. Digital TV channel update. A dead Amstrad digibox.

754 Web service

Useful web sites for TV professionals, technicians and enthusiasts.

758 Letters

TV health hazards. Goodmans TV repairs. CRT testing. Mouse operating tip.

760 Next month in Television

Next issue, dated November, on sale October 17th.



Cover photography Mark Swallow

Editor Martin Eccles

Consultant Editor John A. Reddihough

Group Advertisement Sales Executive Pat Bunce 0208 722 6028 Fax 0208 772 6098

Editorial Office 01782 870684 Fax 01782 878233

Note that we are unable to answer technical queries over the telephone and cannot provide information on spares other than that given in our Spares Guide.



TA-903B CRT Rejuvenator

Seeds of the future

t's interesting how research always seems to continue despite adverse economic conditions. There is much concern at present about the recessionary conditions throughout the world. Yet we are, fortunately, experiencing nothing remotely akin to the worldwide economic slump of the Thirties. It was during those years however that TV as we know it was developed. Progress was taking place in many other fields as well, in particular electrical engineering, the chemical industry and transport. By 1933 RCA had demonstrated a fully-electronic TV system, with 240-line scanning and transmission at VHF from atop the newly-built Empire State Building. RCA had increased the resolution to 343 lines interlaced by mid 1936. Other US firms were active in TV development, but the severity of the depression was such that regular broadcasting did not start until the early Forties.

In the UK EMI had, during the early Thirties, developed the fullyelectronic TV system that became the basis of the BBC's TV service from late 1936 onwards. Much work was being done elsewhere, in Germany and France for example. Some suggest that the German 180line system could claim to have been the first to be brought into service, with its start in 1935. There were transmissions from the Berlin Radio Tower, but these were to 'public viewing rooms'. Hitler was not prepared to allow TV broadcasting to develop freely – in fact it was placed under the jurisdiction of the Ministry of Air just prior to the opening of the 1935 Berlin Radio Show. Initially at least, video origin was by mechanical scanning from film, a technique Baird was by then using. But it seems that an electronic camera had come into use by the time of the Olympic Games in 1936.

Despite the economic problems of the era, research continued and considerable progress was made. Our current economic woes are quite benign in comparison, though certain industries are suffering to an extent to which they are unaccustomed. The electronics industry and, in particular, the semiconductor section is going through a very difficult period. During the last few weeks there have been announcements of huge job losses – 16,400 at Fujitsu, 18,800 at Toshiba and 14,700 at Hitachi, to quote the largest. Clearly this is no ordinary downturn.

August 12th saw the twentieth anniversary of the launch of the IBM PC, which was the start of the process that led to a PC on virtually every business desk. Some 500m PCs are estimated to have been in use worldwide by the end of the year 2000. But the first fall in global PC sales for fifteen years occurred during the second quarter of this year. The fall was to some extent the consequence of the massive purchasing of PCs, and allied equipment, because of the Y2K scare. However that might be, the

PC market has become a mature one which is unlikely to boom again. The second quarter of this year also saw the first year-on-year fall in mobile phone sales. It had to happen eventually, and this too is probably now a mature market. The telecoms companies expected the market to continue to expand as second- and third-generation phones came along. But that third generation has failed to get going: there are limits to what it is convenient to do with a mobile phone.

These two industries account for most of the increased demand for semiconductor devices in recent years. Their reduced sales have clobbered the semiconductor industry, which is not only suffering from reduced demand but also because of excessive investment in production capacity to meet anticipated sales. Semiconductor manufacturers are used to cyclic fluctuations in demand, but have nevertheless experienced a compound annual growth rate of 15-17 per cent. Revenues have now collapsed. From a peak reached last year, revenues have been falling by 25-75 per cent a quarter. Hence those horrendous job losses.

As in the sombre decade of the Thirties however, research continues apace. It has no doubt been reigned back somewhat, but firms that intend to remain in the forefront can't afford to neglect research. In fact interesting results are being produced. For example IBM has just announced a major breakthrough in semiconductor technology. It has long been clear that there are limits to what can be achieved with conventional silicon technology. The next step has to be circuitry at the molecular level. The single-atom gate has been anticipated for some time, and has been demonstrated in laboratories. What IBM has now come up with is a voltage-inverter based on the semiconductor properties of a single carbon nanotube molecule. IBM, and others who have been working on nanotube technology, expect that minute chips using it will eventually replace silicon. The advantages include much higher operating speeds and much lower power consumption.

Data storage is another area that's receiving a lot of research attention. There are limits to the magnetic storage of bits. Below a certain physical size, a bit's magnetic characteristics become unstable. To progress in this field, a new approach to storage technology is required. Organisations that are active in this field include IBM, Hewlett-Packard and Carnegie Mellon University. All three are using new storage surfaces that store bits as a few thousand atoms. The complexities lie in writing and reading such bits: various nanotechnology probes are being studied. Hewlett-Packard has recently been awarded a patent covering molecular technology that could replace conventional semiconductor memory arrangements. As throughout the electronic age, research continues to produce the

seeds of the future – whatever the economic conditions.

COPYRIGHT

© Cumulus Business Media. All rights reserved. No part of this publication may be reproduced, stored or transmitted in any form or by any means without the written permission of the publishers.

All reasonable precautions are taken by *Television* to ensure that the advice and data published are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it.

CORRESPONDENCE

All correspondence regarding advertisements should be addressed to the Advertisement Manager, Television, Cumulus Business Media, Anne Boleyn House, 9-13 Ewell Road, Cheam, Surrey, SM3 8BZ. Editorial correspondence should be addressed to Television, Editorial Department, Cumulus Business Media, Anne Boleyn House, 9-13 Ewell Road, Cheam, Surrey, SM3 8BZ.

INDEXES AND BINDERS

Indexes for Vols. 38 to 48 are available at £3.50 each from SoftCopy Ltd., who can also supply an eleven-year consolidated index on computer disc. For further details see page 760.

Binders that hold twelve issues of *Television* are available for £6.50 each from Television Binders, 78 Whalley Road, Wilpshire, Blackburn BB1 9LF. Make cheques payable to "Television Binders".

BACK NUMBERS

Some back issues are available at £3.00 each.

SUBSCRIPTION ENQUIRIES

Telephone:01444 445 566Fax:01444 445 447Credit card orders:01622 778 000Address: Television, Subscriptions Dept, PO Box 302,Haywards Heath, West Sussex RH16 3YY, UK.Make cheques payable to:TelevisionSubscription rates:UK£32.00 per yearAirmail Fire£36.00 per year

Airmaii	EILA	L30.00 per year
Airmail	Europe	£46.00 per year
Airmail	Rest of World	£59.00 per year

NEWSTRADE ENQUIRIES

Distributed by COMAG Telephone:

ISSN 0032-647X

01895 444055



TELETOPICS

DVD developments

The Recordable DVD Council, a 66member body that consists of leading DVD technology developers and users, including Hitachi, JVC, Matsushita (Panasonic), Samsung and Toshiba, has launched a worldwide programme to promote recordable DVD products that comply with the recording standards approved by the DVD Forum, i.e. DVD-RAM, DVD-R and DVD-RW. But the first DVD recorder to appear in the UK, the Philips DVD1000, uses the slightly different DVD+RW format. It's now on sale, at about £1,500, with the rewritable discs at £20 each.

Columbia Tristar and Sony Pictures Entertainment have developed Superbit DVD-Video and are releasing titles that use this technique. It provides higher picture quality than a standard DVD by using a special high bit rate during the encoding process. Superbit titles make use of space that's normally allocated to extra material such as deleted scenes. They are compatible with standard DVD-Video players.

Manufacturing moves

Philips, Europe's largest consumer electronics group, is to contract out manufacture of many of its products. As a first step manufacture of its VCRs is to be subcontracted to Funai Electric of Japan, the world's largest VCR manufacturer. Funai will produce Philips machines at its plants in Shanghai and elsewhere. The Philips VCR plant in

Panasonic has launched a portable DVD player, Model DVD-LA95, which has a 9in. LCD display screen, the industry's largest for a portable DVD player. It's the first portable DVD player that can read DVD-RAM discs. Weight is less than 1kg, including a built-in rechargeable battery and a TV tuner. The display can handle the 4:3 and 16:9 formats. Up to two and a half hours of DVD playback is provided by the battery pack, while use of an optional rechargeable battery pack, to be sold separately, gives up to eight hours of DVD movies or thirteen hours of TV programming. The DVD-LA95 plays DVD-Video, DVD-Audio, DVD-RAM, DVD-R (recorded on Panasonic's DVD video recorder, to be released shortly), CDs, CD-R and CD-RW discs. Panasonic's parent company Matsushita says that portable players currently make up about 15 per cent of the DVD player market in Japan. The DVD-LA95 was launched in Japan on September 1st, at an 'open' price, with

Austria will close, with the loss of some 1,000 jobs. In future Philips' in-house production will be focused on newer lines such as flat-screen TV sets and DVD recorders. The company has been making a loss in recent months.

Hitachi plans to close its TV assembly plant at Hirwaun, South Wales, by the end of the year, with the loss of 174 jobs. This

This high-quality dual-board camera module, Model CB60H, has been added to the Pecan range of CCTV camera products. Based on a Sony 1/3in. CCD image sensor, the module provides a horizontal picture resolution of 450 lines with quality images at light levels as low as 3 lux. It's supplied with an integral varifocal lens with a DC-controlled auto-iris as standard, but is compatible with other lens types. The composite and S-video outputs are compatible with PAL or NTSC equipment. There's also a YC output and an RS232 interface.

Operation is at either 24V AC or 12V DC. If AC is used, the unit automatically synchronises to power line zero crossing to ensure roll-free vertical switching and recording. An external vertical phase-delay adjustment provides camera sync with multiphase power installations.

The CB60H can also be supplied in an application-ready form, such as a vandalresistant or covert housing. For further details apply to Stortech Electronics Ltd., Unit 2, Spire Green Centre, Pinnacles West, Harlow, Essex CM19 5TS. The phone number is 01279 419 913, fax 01279 419 925.

shipment to overseas markets scheduled for later this year.

US company Zeros & Ones has developed a new compression system that enables up to five full-length movies to be stored on a single DVD, and has produced a demonstration disc. The compression technology, code-named MC10, uses more than a hundred processes ranging from high-definition image quality enhancements at the sub-pixel level during pre-compression to pixel-by-pixel motion tracking and processing during the compression stages. MC10 is claimed to achieve three to ten times greater compression than MPEG-2, with equivalent or superior image quality. Zeros & Ones intends to develop commercial versions of the technology and license it. The company says that MC10 could be used in DVD players and PVRs (hard-disk personal video recorders), and for videoconferencing systems and broadband applications.

will be the end of a long period of set manufacture that started when Sobell moved production there in the mid-Forties.

Matsushita is to close its transformer plant at East Kilbride in November, with the loss of 100 jobs. The plant, built in 1992, manufactured Panasonic-branded LOPTs for TV sets and monitors.

VOD

A report from Frost and Sullivan on video on demand (VOD) in Europe forecasts a substantial growth in the market. It notes that the European roll-out of VOD lags that in the US. Video Networks launched VOD commercially in the UK during the last quarter of 2000, but audiences remain limited. Frost and Sullivan suggest that as the prices of STBs and bandwidth technology falls, network operators will be encouraged to launch viable VOD business models because the services will be affordable to average mass-market consumers. The company forecasts that by 2006 VOD will attract more than 8.5 million subscribers across Europe.

CPC telephone numbers

There are new telephone numbers for component distributor CPC of Preston. The sales office can be reached on 08701 202 530, fax 08701 202 531.



New video equipment

Panasonic has now launched in the UK its 50in. plasma panel display, Model TH-50PHD, which can be used with various TV, video and PC signal sources. For an account of some of the technology employed, see the article later in this issue (page 714). The panel can provide normal video displays at 720 pixels per line resolution and all monitor resolutions up to UXGA (1,600 x 1,200 pixels). Price is about £9,800 plus VAT. Panasonic is also due to launch 15 and 22in TV sets with LCD screens and new 42 and 47in. projection TV models.

Samsung has developed a 40in. LCD panel for use with widescreen TV sets: the resolution is 1,280 × 768 pixels.

Sharp has released two new digital video (DV) camcorders, Models VL-WD250H and VL-WD450H, that incorporate the industry's largest optical zoom at 26x. The range of picture enhancement facilities with the VL-WD250H includes Cat's Eye, which enables recordings to be made at light levels as low as 1 lux, digital gamma correction for improved detail in darker areas of the scene, digital image stabilisation and picture-in-picture effects. Sound performance can be enhanced with an optional zoom microphone which works in conjunction with the built-in microphone to provide a lifelike mix of wide-angle and narrow-band sound that varies with the amount of lens zoom employed. The VL-WD450H (pictured) has additional features: a Super Cat's Eye circuit that provides monochrome recording in complete darkness (0 lux); the ability to record still images and indexing information on a SmartMedia card; and software for downloading images to a PC.

Philex has introduced the AV Hub Plus selector, which makes viewing from different signal sources easier and adds to the versatility of home or office AV equipment. It provides automatic or remote control of up to four different pieces of AV equipment, simplifying cable arrangements with no need for connection/ disconnection and thus reduced wear and tear on both the equipment and connections. Viewing programmes from or recording with two different VCRs at the same time is possible, also four-way recording. There are facilities for an additional satellite decoder, a lock function to protect recordings from accidental interruption, and front AV



inputs for camcorders and games consoles. For further details apply to Philex Electronic Ltd. – phone 020 8202 1919 or e-mail sales@philex.com

MHP extension

Interactive TV software developer Open TV has completed joint development, with Matsushita, of an extension to the advanced digital interactive TV system MHP (Multimedia Home Platform). The latter was accepted by the DVB (Digital Video Broadcasting) project group as a standard API (Application Programming Interface) for use with services such as games, enhanced TV, shopping and banking – before the MHP standard was set, such applications could have required adaptations to operate with different broadcasting networks and set-top box designs. The MHP standard enables digital interactive content and services to be developed and used by all compatible TV settop boxes, IDTV sets and multimedia PCs. The new MHP 1.0.1 extension will be available for certification as soon as the DVB releases its MHP Test Suite later this year.

Open TV also says that its interactive

Networked home trial

EA Technology has invited manufacturers of white and brown goods to join a consortium which will, in 2002, run the world's first large-scale field trial of multiple service provision to networked homes. The trial is backed by the International Energy Agency (IEA), which is part of the Organisation for Economic Co-operation and Development (OECD). Projects are also running in Australia, Canada, Finland and the Netherlands.

A key item in the UK trial will be a gateway unit developed EA Technology, called FlexGate, which provides communication between any domestic appliance or system and any external system, regardless of the protocols involved or the communications channel (phone line, cable TV, wireless, fibre etc.). EA Technology's commercial manager Robert Davis says "the unit is totally platform-independent and extremely flexible. It's a simple, lowcost black box that will be available from a growing number of manufacturers and is equally suitable for existing and new homes."

Networked home applications will include: remote monitoring of energy and water use, meter readings and faults; the ability to control heating and cooking remotely and shop for the best energy spot prices; monitoring emergency situations; TV software will run with the new IBM STB03xxx series of PowerPC-based set-top box chips. These combine a PowerPC processor, an MPEG-2 audio/video decoder, a memory interface subsystem and a range of peripheral interfaces on a single silicon substrate. The chips provide highspeed operation, at 162MHz, and have a 16kbyte instruction cache and an 8kbyte data cache to provide the performance required for a range of new services.

and remote diagnosis of faults in domestic appliances with in-built intelligence and some maintenance.

EA Technology is based at Capenhurst near Chester and was formerly the research arm of the electricity industry. It became independent following a buy-out in October 1997.

For further information on the trial, EA Technology can be contacted on 0151 347 2460 – or check at the website www.eatechnology.com *A prototype FlexGate unit.*



Grandata Ltd distributor of electronic components

CD Pick Ups and Assemblies

PART NO PRICE	PART NO PRICE	PART NO PRICE
2001600001£28.00	KSS213E£13.75	5 RAE0150Z£28.00
6142205006£47.00	KSS213F£12.00	RAE1052Z£20.00
6450067983£18.00	KSS320B£22.75	5 RAE150Z Mechanism£35.00
6450253089 £25.00	KSS330A £28.00	RCTRH8112£14.00
482269110487 £45.00	KSS331A	RCTRH8136
A4672541A (Mini Disc) £54.00	KSS331C(RP)2 £38.00	RCTRH8147 Mechanism
CDM12.1 Mech£16.00	KSS360A	(Suitable for Denon & Sharp) .£10.00
CDM12 3BLC £45.00	K\$\$363A£22.00	RCTRH8151£16.00
CDM12.4	KSS480A£20.00	RCTRH8153£36.00
CDM9/44£21.00	KSS540A£17.00	RCTRH8173 (Mini Disc) .£20.00
CDM9/44 Mech£24.00	KSS542A£23.50	RCTRH8175 (Mini Disc) .£60.00
DAX11A£26.00	KSS543A£22.00	SF90£20.00
H8112AF£16.00	KSS580A£23.00	SF91£16.00
HOPM3£21.50	KSS880£24.00	SF91 Carriage£20.00
HPC1MX£20.00	KSS240A Original£ 30.00	SFC93£17.00
KCP1H£17.50	NKS240A	SFP1£12.00
KSL2101ABM Mech£18.00	(Replacement for KSS240A)£20.00	0 SFP100£16.00
KSM213CCM Mech£15.00	OPTIMA5S£11.50	SFP101 (5 & 8 PIN PLUG) £15.00
KSM620AAA Mechanism	OPTIMA6S£11.50	SFP101 with amp IC£15.00
(Suitable for Pioneer)£26.75	OPTIMA7 (Mini Disc)£12.00	SFP101 without amp IC .£21.00
KSS210A Original£14.00	OPTIMA710A£19.00	0 SFP101N15£14.00
KSS210A Replace£11.00	OPTIMA720A£14.7	5 SFP101N16£14.00
KSS210B£15.00	PEA1030£44.00	SOAD70A£52.00
KSS212A£16.00	PEA1179£45.00	SOH90T4N£17.00
KSS212B£11.50	PEA1291£45.00	SOHA1£19.50
KSS213B£11.50	PWY1009£48.00	SOHAP£18.00
KSS213C£11.50	PWY1010£45.00	0 X49460541 (Mini Disc)£90.00
KSS213D£16.00	RAE0113Z£30.00	0 X49482601 (Mini Disc)£65.00
	RAE0140Z£45.00	
	CD Spindle Motor	'S
22.5 mm Shaft	Order Code : CDMOT1	Price : £ 2.00 + vat
8mm Shaft	Order Code : CDMOT2	Price : £ 2.00 + vat

Fault Finding & Reference Books

New VCR Fault Finding Guide (Issue 6 - 2001) Over 400 A5 pages of information Approximately 25% additional information

Over 8000 different faults listed Seperate section for VCR/TV combinations This book has been revised and uodated with approximately 25% addditional information and conatins over 8000 fault entries for a range of VCRs and TV/VCR combination units. As in previous issues the new information has been merged with existing data to give a comprehensive listing which has been arranged in order by brand and model and fault symptons to provide a quick reference to numerous fault conditions on a range of models.

Order Code : BOOK01 Price : £ 17.50 (No VAT - Postage £ 2.00 + vat)

Jaeger SMD Decoder Book

Over 10,000 SMD Codes listed Over 200 pages listing each device by : Markings , Manufacturer , Device Type Correction Type Designation , Base Number , Case Size

Order Code : BOOK08 Price : £ 7.50 (No VAT)

Jaeger 2001 Semiconductor Comparison Book

This A5 book contains vital reference information on 36,800 type on semiconductors , together with alternatives , descriptions and base connections

Order Code : BOOK04 Price : £ 20.00 + vat (plus £ 2.00 +vat Postage)

K.P. House , Unit 15 , Pop In Commercial Centre , Southway , Wembley , Middlesex . HA9 0HB England Tel : (020) 8900 2329 Email : grandata.ltd@btinternet.com Fax : (020) 8903 6126 Website : http://www.grandata.co.uk

Grandata Ltd distributor of electronic components

105° c Radial Electrolytic Capacitors

VALUE CODE PRICE PER	VALUE CODE PRICE PER	VALUE CODE PRICE PER	VALUE CODE PRICE PER	VALUE CODE PRICE PER
PACK	PACK	PACK	PACK	PACK
10 Volts	10 Volts continued	50 Volts continued	100 Volts	350 Volts
100uF	1500uF .CAP47 . £3.905	33uFCAP141 £0.8510	0.47uF .CAP91 .£0.505	1uF10
470uFCAP29£1.2010	2200uF .CAP48£2.00	47uF .CAP65£0.8510	1uFCAP92 .£0.85 . 10	3.3uFCAP157£1.5010
1000uF .CAP119 .£1.5010	3300uF .CAP49 .£2 202	68uFCAP142 £0.90 . 10	1 5uFCAP93£0.705	10uFCAP158£2.2510
2200uF .CAP120 £2 10 10	4700uF .CAP50 £3.65 2	100uFCAP66 .£0.8510	2 2uFCAP94£0.505	22uFCAP159£3.4010
	6800uF .CAP51 .£3.90	220uF CAP67£1 75 10	3 3uFCAP95£0.505	
16 Volts		330uFCAP68 . £2.4510	4.7uFCAP96£0.505	400 Volts
22uF CAP121 £0.35 . 10	35 Volts	470uFCAP69£4.35 10	10uFCAP97£0.9510	1uF CAP107£2.155
33uFCAP122 .£0.3510	1uFCAP130 .£0.4010	680uF .CAP70 . £4.90 . 5	22uF CAP98£1.05 10	2.2uFCAP108£2.255
47uFCAP123 £0.35 10	3.3uFCAP131 .£0.4010	1000uF .CAP71 .£5.25 10	33uFCAP99£1.555	4.7uFCAP109£3.155
100uF CAP124 .£0.60 10	4.7uF CAP132 £0.45 10	1500uF .CAP143 .£4.505	47uFCAP100£1.7510	10uFCAP110£4.005
220uFCAP125 .£0.8010	10uFCAP52 £0.5010	2200uF .CAP72 .£3.252	100uFCAP101£2.1010	22uFCAP111£2.502
330uFCAP30£1.7510	22uFCAP53 £0.4510	3300uF CAP144 .£3.252	220uF CAP102 £6.005	470FCAP112£3.502
470uF CAP31£1.75 . 10	33uF . CAP54£0.505		470uFCAP103£6 005	1000F
680uFCAP32£2.10	47uFCAP55£0.8510	63 Volts		2200FCAP161 .£7.002
1000uF CAP33 £2.10 . 10	68uF CAP133 .£0.5510	0 22uF .CAP145 £0.4510	160 VOIIS	450 1/-14-
2200uF .CAP34 . £5.25 10	100uFCAP56£0.8510	0.47uF .CAP73£0.3510	2 2UF CAP146 . £0 45 10	450 VOILS
3300uF .CAP35 . £5.00 5	150uFCAP57£0.955	TUFCAP74E0.3510	100FCAP147_£1.4010	10F . CAP113 .£2.00
4700uF .CAP36 . £6.10 . 10	2200FCAP58 .£1.45	2.20F .CAP75 . £0.35 .10	22UF. CAP148	4.7.1E CAD115 64.05 5
	3300F	3.30F .CAP76 £0.50 .10	1000E CAR150 52.25 5	10.5 CAP116 65.50 5
25 Volts	4700FCAP135 10	14.70FCAP77£0.3510	1000F. CAP 130,23.25	2211E CAP117 54 15 2
100FCAP37£0.45	1000-F CAP59	100FCAP78 .20.50 10	200 Volts	2201
220FCAP36 . £0.4510	10000F .CAP60	22UE CAPPO E0.75 10	1000E CAP151 \$3.25 5	2 - 2 - 2
1330P CAP120 £0.40	3300UE CAP62 \$10.00 5	33UE CAP81 £0.85 10	10001 ·OAF 13123.23	
69.4F CAD127 50.55 10	4700 UE CAP136 53.50 2	47uE CAP82 £0.95 10	250 Volts	100
1000E CAP40 60.70 10	470001 .CAF 130 23 30	68uE CAP83 £1.30 5	1 JUE CAP152 £0.60 10	
120UE CAD128 50.85 10	50 Volts	100µE CAP84 £1.20 10	3 3UE CAP104 £1.75 10	10000
1500F CAP41 50.95 5	10E CAP137 F0.35 10	150uF CAP85 £2.80 5	10uF CAP105 £2.60 10	1000
220UE CAP42 £1.20 10	2 20E CAP138 £0.35 10	220uF CAP86 £2.80 10	22uFCAP153£2.3010	
330uE CAP43 £1.40 5	3.3uF CAP139 £0.3510	330uF CAP87 £4.00 10	47uF CAP106	
470uF CAP44 £1.90 10	4.7uFCAP140 .£0.35 10	470uF CAP88 £5.25 . 10	100uFCAP154£4.50	
680uF	10uF CAP63 £0.5010	680uF CAP89 £5.0010	220uF CAP155. £2.00	
1000uF CAP46	22uFCAP64 £0.7010	1000uF .CAP90 .£5.40 .5		

Fuses

20mm Gl	lass	Wickman Fuses				
TIME LAG QUICK BLOW		FAST BLOW	SLOW BLOW			
CURRENT RATING ORDER CODE PRICE CU R (CURRENT RATING CODE 100mA FUSE36 .75p 100 160mA FUSE01 .75p 166 250mA FUSE02 .75p 315 400mA FUSE04 .75p 30 500mA FUSE05 .75p 50 630mA FUSE06 .75p 63 800mA FUSE08 .60p 14 1.25A FUSE09 .60p 1.25A 1.6A .FUSE10 .60p 1.60p 2.5A .FUSE13 .55p 3.15A 3.15A .FUSE13 .55p 3.44 A .FUSE14 .55p 4A 5A .FUSE15 .60p 6.33	URRENT RATING ORDER CODE PRICE 00mA FUSE37 .60p 60mA FUSE17 .60p 50mA FUSE17 .60p 15mA FUSE18 .60p 00mA FUSE19 .60p 00mA FUSE20 .60p 00mA FUSE21 .60p 00mA FUSE23 .60p 00mA FUSE23 .60p 00mA FUSE23 .60p 20mA FUSE25 .60p 25A FUSE26 .60p 25A FUSE26 .60p 25A FUSE27 .60p 25A FUSE29 .50p 15A FUSE20 .50p 3A FUSE31 .50p	CURRENT RATING ORDER CODE PRICE 0.04A .FUSE53 60p 0.05A .FUSE54 .35p 0.063A .FUSE55 .35p 0.063A .FUSE55 .35p 0.1A .FUSE55 .35p 0.1A .FUSE56 .35p 0.125A .FUSE58 .30p 0.16A .FUSE58 .30p 0.2A .FUSE61 .30p 0.315A .FUSE61 .30p 0.4A .FUSE63 .30p 0.5A .FUSE64 .30p 0.5A .FUSE63 .30p 0.63A .FUSE65 .30p 0.63A .FUSE65 .30p 0.63A .FUSE65 .30p 0.63A .FUSE65 .30p 1A .FUSE66 .30p 1A .FUSE65 .30p 1A .FUSE66 .30p 1A .FUSE68 .30p 1A .FUSE69 .30p	CURRENT ORDER PRICE RATING CODE 65p 0.05A .FUSE74 65p 0.06A .FUSE75 .5p 0.08A .FUSE76 .65p 0.1A .FUSE76 .5p 0.16A .FUSE77 .5p 0.16A .FUSE78 .35p 0.25A .FUSE80 .30p 0.25A .FUSE81 .30p 0.315A .FUSE83 .30p 0.5A .FUSE84 .30p 0.6A .FUSE86 .30p 0.6A .FUSE84 .30p 0.5A .FUSE84 .30p 0.6A .FUSE84 .30p 0.6A .FUSE84 .30p 0.6A .FUSE86 .30p 1.25A .FUSE88 .30p 1.6A .FUSE89 .30p 1.6A .FUSE89 .30p 2.5A .FUSE91 .30p 2.5A .FUSE93 .30p			
All above Fuse prices are for a pack of 10 All above Wickman Fuse prices are for single units						
CERAMIC PLUG TOP (MAINS) FUSESRATING CODE PRICERATING CODE PRICE3AFUSE33 £1.005AFUSE34 £1.0013AFUSE35 £1.00						

	Soldering Irons and Solder								
1	Antex Soldering	Irons		1	Solder				
h	Description	Order Code	Price	f 1	Solder Gauge & Weight	<u>Code</u>	<u>Price</u>		
I	25 watt 240 VAC Iron	SI01	£12.50 + vat		18 SWG 500 grammes	SI10	£ 5.00		
ł	25 watt Spare Element	SI03	£6.00 + vat	2	20 SWG 500 grammes	SI11	£ 6.50		
l.	15 watt 240 VAC Iron	SI02	£12.50 + vat	- A		0140	0 7 0(
	15 watt Spare Element	SI04	£6.00 + vat	100	22 SWG 500 grammes	5112	£ 7.00		

5.00 6.50 7.00

Grandata Ltd distributor of electronic components

Transistors / Linear IC's

TRANSIST	TORS	BU 2527AF	400p	TIP 30C	250	LM 393	450	STK4221 II	1200n	ISTK5486	4500	STR 453	500n	TDA 2003	650
1.0.1.0.0		BU 2527AX	250p	TIP 31A	22p	LM 723	40p	STK4231 II	1050p	STK5488	480p	STR 454	1300p	TDA 2004	150p
2N 2218A	24p	BU 2532AL	325p	TIP 31C	27p	LM 741DIL	18p	STK4231 V	1400p	STK5490	450p	STR 455	550p	TDA 2005	150p
2N 2222	23p	BU 2722AF	330p	TIP 32A	21p	LM 747	55p	STK4272	500p	STK561	400p	STR 456	470p	TDA 2006	70p
2N 2309	15p	BUF 405A	200p	TIP 320	28p	MB 3730	250p	STK4273	700p	STK5632	415p	STR 457	300p	TDA 2007	1200
2N 2646	40p	BUH 1215	450p	TIP 33C	60p	NE 5532P	1400	STK4301	500p	STK5720	4000	STR 50020	3500	TDA 2009	160p
2N 2904	20p	BUH 315	200p	TIP 34	65p	NE 555	20p	STK4311	650p	STK5725	350p	STR 50103A	260p	TDA 2010	150p
2N 2905	20p	BUH 315D	175p	TIP 34C	60p	NE 556	40p	STK433	400p	STK5730	300p	STR 50112A	650p	TDA 2020	120p
2N 2906	18p	BUH 515	200p	TIP 35C	65p	SAA 1293	850p	STK4332	365p	STK583	400p	STR 50113	500p	TDA 2030	80p
2N 2907	18p 28p	BUH 5150	250p	TIP 41A	20p	SAA 3004	400p	STK435	37 SP	STK6324B	300p	STR 50115	500p	TDA 2030H	2000
2N 3053	180	BUH 517D	1750	TIP 41C	220	SAA 5010	2200	STK436	4300	STK6327	1200p	STR 50330	4750	TDA 2050V	4500
2N 3054	40p	BUH 715	425p	TIP 42A	20p	SAA 5012	400p	STK4362	450p	STK6328A	400p	STR 51424	700p	TDA 2052V	525p
2N 3055	38p	BUL 310	125p	TIP 42C	22p	SAA 5020	350p	STK437	600p	STK6431	600p	STR 53041	400p	TDA 2530	300p
2N 3055H	50p	BUT 11A	30p	VOLTAG		SAA 5030	440p	STK4372	490p	STK6607	400p	STR 54041	320p	TDA 2532	100p
2N 3440	1750	BUT 11AX	50p	REGULAT	ORS	ISAA 5231	1700	STK4392	500p	STK6732	10000	STR 55041	450p	TDA 2578A	2100
2N 3442	85p	BUT 12A	80p			SAA 7000	550p	STK441	680p	STK6822	750p	STR 56041	550p	TDA 2581	100p
2N 3771	85p	BUT 12AF	90p	7805	18p	STK 0049	510p	STK4412	450p	STK6875	650p	STR 58041	250p	TDA 2593	80p
2N 3772	90p	BUT 18A	80p	7806	18p	STK 0050	1200p	STK4432	600p	STK6922	1500p	STR 59041	300p	TDA 2595	200p
2N 3819	290	BUT 56A	65p	7809	25p	STK0080	1000p	STK459	560p	STK6962	2750	STR 6020	270p	TDA 2003A	450p
ACY 18	48p	BUZ 77B	250p	7812	18p	STK015	900P	STK460	660p	STK6972	300p	STR 61001	475p	TDA 3560	600p
ACY 19	48p	BUZ 80	135p	7815	25p	STK025	650p	STK461	600p	STK6981B	500p	STR 80145	475p	TDA 3561	300p
AD 149	60p	BUZ 80AF	200p	7818	25p	STK084	600p	STK463	950p	STK6982	600p	STR 81145	375p	TDA 3562A	260p
AF 127	100p	BUZ 90A	180p	7824	25p	STK1039	460p	STK465	900p	STK6982H	600p	STR 83145	500p	TDA 3651	2000
BCY 33	2000	BUZ 91A	260p	7912	300	STK1049	7000	STK4803	13000	STK7217	2500	STR 9005	4000	TDA 3652TX10	8000
BCY 70	16p	IRF 510	70p	7915	30p	STK1060	700p	STK4813	800p	STK7225	500p	STR 9012	300p	TDA 3653B	80p
BCY 71	16pi	IRF 520	75p	7918	30p	STK2025	620p	STK4833	850p	STK7226	1700p	STRD 1706	360p	TDA 3654	800
BCY 72	16p	IRF 530	75p	7924	30p	STK2030	1000p	STK4873	1100p	STK730-060	650p	STRD 1806	360p	TDA 3654Q	85p
BD 131	25p	IRF 540	80p	LM 309K	100p	STK2101	1050p	STK501	475p	STK730-080	700p	STRD 1816	350p	TDA 4500	300p
BD 133	50p	IRF 620	100p	LINISTIT	1000	STK2230	1300p	STK5315	500p	STK7309	4000	STRD 6108	450p	TDA 4505	2000
BD 135	20p	IRF 630	75p	LINEAR	C's	STK2240	1800p	STK5323	600p	STK7310	320p	STRD 6202	400p	TDA 460011	160p
BD 136	20p	IRF 640	150p	1115454	000	STK2250	1600p	STK5324	300p	STK73405 II	550p	STRD 6601	650p	TDA 4601	120p
BD 137	20p	IRE 720	85n	AN 5265	200p	STK3044	500p	STK5325	750p	STK73410	350p	STRU 6801	500p	TDA 46010	1900
BD 139	20p	IRF 730	125p	AN 5512	100p	STK3152 II	9000	STK5330	850p	STK7348	400p	STRM 6559	850p	TDA 4610	3700
BD 140	20p	IRF 740	90p	AN 5515	160p	STK3156	500p	STK5331	300p	STK7356	425p	STRS 6707	1000p	TDA 4950	100p
BD 244	50p	IRF 820	90p	BA 5402	180p	STK4017	400p	STK5332	180p	STK7358	440p	STRS 6708	575p	TDA 6101Q	120p
BEQ 162	100p	IRF 830	85p	BA 5406	180p	STK4019	480p	STK5333	350p	STK73908	550p	STV 21028	800p	TDA 6103Q	1250
BFQ 232	750	IRF 9620	85p	HA 13150A	1150p	STK4024 II	550p	STK5336	3500	STK7404	600p	STV 2110B	800p	TDA 6107Q	3000
BFQ 235A	750	IRF 9630	130p	HA 13151	875p	STK4025	530p	STK5337	500p	STK7406	650p	STV 2116A	750p	TDA 8138A	130p
BFQ 252A	60p	IRFBC 30	120p	HA 13152	800p	STK4026	480p	STK5338	295p	STK7408	675p	STV 2118B	1000p	TDA 8139	200p
BFQ 255A BFQ 262A	75p	IRFBC 40	210p	HA 13153A	900p	STK40261	480p	STK5339	400p	STK7410	1500p	STV 9379	400p	TDA 8170	170p
BFX 84	150	IRFP 240	300p	HA 13158	800p	STK4036	800p	STK5342	245p	STK7563	800p	TA 8200AH	325p	TDA 8172	2000
BFX 85	20p	IRFPC 40	300p	KIA 6210AH	400p	STK4038	680p	STK5343	380p	STK7573	300p	TA 8207K	175p	TDA 8179S	750p
BFX 87	15p	IRFPC 50	450p	L 200	200p	STK4042 II	800p	STK5352	500p	STK760	500p	TA 8210	260p	TDA 8350Q	275p
BEX 89	400	MJ 11015	250p	L 272	200p	STK4044	950p	STK5353	400p	STK7707	400p	TA 8211AH	200p	TDA 8362AN3	200p
BFY 50	14p	MJ 11016	300p	LA 4445	200p	STK4050 II	1600p	STK5362	400p	STK780	480p	TA 8215H	300p	TDA 8702	2750
BFY 51	14p	MJ 15003	250p	LA 4446	170p	STK405-050A	1200p	STK5364	250p	STK78603	750p	TA 8216H	300p	TDA 8703	500p
BFY 52	140	MJ 15004	300p	LA 4450	330p	STK4060	510p	STK5371	350p	STK795	325p	TA 8217P	120p	TDA 9102C	250p
BU 1508AX	1300	MJ 15016	250p 350p	LA 4451	1200	STK4101	500p	STK5372	200p	STK8260	1200p	TA 8218AH	425p	TEA 1039	1500
BU 1508DX	105p	MJ 15022	400p	LA 4461	120p	STK4111	400p	STK5383	300p	STK8280	1850p	TA 8221AH	600p	TEA 2017	1000p
BU 180	100p	MJ 15023	400p	LA 4705	400p	STK4112	500p	STK5391	375p	STR 10006	450p	TA 8227	250p	TEA 2018A	80p
BU 204	65p	MJ 15024	400p	LA 7830	90p	STK4121	480p	STK5392	500p	STR 11006	325p	TA 8251AH	700p	TEA 2019	600p
BU 206	1000	MJF 16206	450p	LA 7837	1500	STK4130 II	700p	STK5434	5700	STR 17006	500p	TA 8256H	450p	TEA 2037A	1750
BU 207	150p	MJF 18004	175p	LA 7838	200p	STK4131	480p	STK5436	500p	STR 20015	400p	TA 8427K	200p	TEA 2164	160p
BU 208A	75p	MJF 18006	200p	LA 7840	175p	STK4132 II	600p	STK5441	350p	STR 2005	400p	TA 8659AN	900p	TEA 2260	225p
BU 208AT	200p	MJF 18008	1/5p 350p	LA 7850	225p	STK4133 II STK4140 II	750p	S1K5443	575p	STR 2012	350p	TA 8659CN	800p	TEA 2261	185p
BU 2506DF	90p	OC 28	350p	LM 2405T	6250	STK4141 II	420p	STK5451	390p	STR 30115	2750	TA 8701AN	2750	TEA 5101A	300p
BU 2506DX	100p	S 2000A3	175p	LM 2406T	400p	STK4141 V	480p	STK5461	500p	STR 3135	250p	TBA 120S	40p	TEA 5101B	175p
BU 2508A	100p	S 2000AF	90p	LM 2416T	650p	STK4142	530p	STK5462	350p	STR 370	300p	TBA 520	120p	TEA 5170	200p
BU 2508AF	110p	S 2000N	150p	LM 2419T	800p	STK4150 H	1200p	STK5464	300p	STR 371	400p	TBA 530	100p	UC 3842AN	80p
BU 2508D	1300	S 2055AF	1750	LM 324	300	STK4152	650p	STK5467	400p	STR 381	390p	TBA 560	90p	UC 3842N	80p
BU 2508DF	120p	S 2055N	150p	LM 339	35p	STK4161	650p	STK5468	300p	STR 383	410p	TBA 810AS	40p	UC 3843AN	80p
BU 2508DX	150p	TIP 121	35p	LM 380	80p	STK4162	550p	STK5471	900p	STR 384	350p	TBA 820M	35p	UC 3844	70p
BU 2520AF	170p	TIP 122	30p	LM 381	150p	STK4171	900p	STK5472	375p	STR 40090	350p	TDA 1170N	85p	UC 3844AN	80p
BU 2520DF	2250	TIP 126	40p	LM 386	60p	STK41/211	680p	STK5473	480p	STR 40115	650p	TDA 1170S	85p	UPC 1488H	80p
BU 2520DX	200p	TIP 127	35p	LM 387	100p	STK4182 II	750p	STK5476	350p	STR 4211	315p	TDA 1524A	200p	0.0.00	. 1001
BU 2522AX	150p	TIP 145	50p	LM 389N	105p	STK4191	900p	STK5477	700p	STR 440	800p	TDA 1541A	400p		
BU 2525A	325p	TIP 147	80p	LM 3900	40p	STK4192	700p	STK5478	250p	STR 4411547	5p 4125	TDA 1557Q	300p		
BU 2525AX	1900	TIP 29A	220	LM 3914	160p	STK4197 II	10500	STK5479	470p	STR 450A	800n	TDA 1675A	200p		
BU 2525D	240p	TIP 29C	25p	LM 3915	160p	STK4204 II	1050p	STK5482	285p	STR 45111	550p	TDA 16846	200p		
BU 2525DX	175p	TIP 3055	50p	LM 3916	270p	STK4211 V	800p	STK5483	440p	STR 452	475p	TDA 2002	50p		

 Please note that this a very small selection of the transistors and IC's that we stock.
 We stock a full range of Japanese Transistors 2SA,2SB, 2SC,2SD,2SJ,2SK series , Diodes , CMOS , TTL Logic ICs , Computer ICs , Zenor Diodes...etc
 Please call us for any items that are not listed on 020 8900 2329



We also stock the following :

Video Heads, Pinch Rollers, Belt KIts, Idlers, Service Kits, Video Motors, Cassette Housings, Audio Control Heads, Mode Switches, Video Lamps, Satellite Spares, LNB's, Back Up Batteries, Servicing Tools and Aids, Digital Multimeters TV Switches, Line Output Transformers, Japanese Transistors, Linear IC's, Computer IC's, CMOS and 74 Series and

much much more !!!.....All at competitive prices

Please contact us if you cannot find the part you are looking for.

* Please add £1 p+p and VAT to all orders
 * All components are brand new
 * We accept payment by Access , Switch , Visa , Cheque and Postal Order
 * All prices quoted are subject to availability and may be changed without prior notice

E & OE

K.P. House, Unit 15, Pop In Commercial Centre, Southway, Wembley, Middlesex. HA9 0HB England Tel : (020) 8900 2329 Email : grandata.ltd@btinternet.com Fax : (020) 8903 6126 Website : http://www.grandata.co.uk



Panasonic's Plasma Display TVs How would you like a TV set that has perfect colour purity, perfect

recently had to evaluate a Panasonic GP2D chassis plasma display panel, as used in TV Model TC37PD1, for technical training purposes. The most striking feature initially is the weight difference between the 37in. plasma display panel and say the Panasonic Model TX36PF10, which has a 36in. CRT. I could manoeuvre the panel with no difficulty at all, lifting and carrying it to a suitable bench with ease. In comparison, movement of a TX36PF10 set requires at least four fit people or the use of a fork-lift truck.

Panel configuration

Panasonic plasma display panels (PDPs) consist of a plasma cell matrix with 480 rows of 2,556 RGB cells, i.e. 1.226,880 cells in total. They are currently produced in 37 and 42in. sizes, with a 50in. version in prospect. As the cells are alternately red, green and blue, the display resolution is 852 × 480 pixels. The RGB cells are arranged so that they form vertical stripes – in this one respect the display is similar to a CRT screen. But with Panasonic PDPs the RGB cells/stripes have different widths, to improve colour rendering and brightness. This is referred to as an asymmetrical cell arrangement, see Fig. 1.

Each cell has a phosphor lining and is filled with a weak mixture of neon and xenon gas, which is activated in a similar way to a fluorescent tube – by applying a specific trigger voltage. Once activated, the gas produces a burst of wideband electromagnetic radiation (ultra-violet). This energises the phosphor to produce light. The ultra-violet radiation is the main cause of phosphor energisation and thus illumination. Brightness is determined by the gas energisation (discharge) time. Control of this is known as sub-field drive, see below.

Fig. 2 shows the basic arrangement of a plasma display cell. Fig. 3 provides greater detail. There are three electrodes, a vertical data electrode at the rear and, at the front, horizontal scan and sustain electrodes. The cell contains two thirds

convergence and perfect focusing across the whole screen? Would you like it to have a viewing angle of 160°, and be able to mount it on the wall? These are the inherent advantages of using a plasma display panel to present the TV picture. Brian Storm investigates the Panasonic approach to PDP technology, in the form of the GP2D chassis

of an atmosphere that consists of a mixture of xenon and neon gas, and is coated on its sides and rear with coloured phosphor. 1.226.880 of these cells are precisely arranged between glass sheets. As mentioned above, the cells are arranged to provide vertical stripes, 2,556 across the panel.

In addition to the front glass sheet there's a front protective screen to help filter out the wideband electromagnetic radiation generated by the activated cells. A supporting cast aluminium sheet at the rear gives strength and support.

What is plasma?

The term plasma is used for the type of display device described above. But what actually is plasma? It consists of positive free ions and negative free electrons and has properties that are fundamentally different from those of solids, liquids and gases. Because of this, plasma is considered to be a fourth state of matter.

Plasma is rare in the terrestrial environment, occurring naturally in lightning and flames. Elsewhere in the universe however plasma is the predominant state of matter – in fact 99 per cent of the known universe seems to consist of plasma. The stars consist of dense, high-temperature plasma, and very low-density plasma is present as tenuous gas clouds in the vast voids between them. It is only on temperate planetary bodies that matter exists in its more familiar physical states.

Plasma technology has for many years been used in fluorescent lighting. The principle here is that a low-density inert gas is triggered to a plasma state. When in its plasma state the gas generates ultraviolet light, which activates the phosphor coating on the inner surface of the sealed glass tube to provide light. This is precisely the principle employed by plasma panels, but there is of course the considerable additional complexity involved in controlling the instantaneous brightness of each cell.

The scanning system

Specially-generated scan and sustain waveforms, and a data-drive system to select, sequentially, the cells that require selection and sustaining, are needed to drive a plasma panel.

Fig. 4 shows the waveforms that are present at a cell's scan and sustain electrodes respectively. The highamplitude, two-level pulses in the scandrive waveform are initialisation pulses. They are applied to the cell, between the scan and sustain electrodes, to neutralise any charge that may remain from previous activation and prepare the cell for its next operation. The initialisation process basically ensures that each cell has a consistent light output each time it is selected. Following initialisation, a large positive write pulse is applied to the cell's data electrode. The action of this combines with a negative pulse applied to the scan electrode to activate the cell. A series of opposite-polarity sustain pulses is then applied between the scan and sustain electrodes, to keep the cell lit for a certain length of time: the longer the cell is lit, the brighter its output.

This process of cell initialisation, write and sustain is the basic principle of plasma panel operation. It's known as the sub-field drive system. See Fig. 5.

Panasonic plasma panels use a complex multiple split sub-field drive system known as Plasma AI drive. Traditionally, an eight sub-field drive system based on the power of 2 has been used to drive plasma panel cells, see Fig. 6. Each TV field period is divided into eight sub-field periods. The first sub-field has one sustain cycle, the second has two, the third has four and so on. Thus we have 1, 2, 4, 8, 16, 32, 64 and 128. which provide 256 different brightness levels from a cell. This is done by selecting any or all of the possible sustain periods. Thus the 1 and 2 sustain periods, i.e. three sustain cycles, may be used in a very low-brightness area of the display. In a high-brightness area the 16, 32, 64







Fig. 2: Basic plasma cell construction.









and 128 sustain cycles, a total of 240, might be used.

The problem with this system is timing. We are not increasing the actual cell brightness but the time during which the cell is illuminated. The main problem occurs between 127 and 128 sustain cycles. For 127 1 + 2 + 4 + 8 + 16 + 32 +64 + 0 = 127 are used, while for 128 0 +0 + 0 + 0 + 0 + 0 + 0 + 128 are used. This timing difference produces edge artefacts, especially with lateral movement. Typically, an object moving to the right develops a black edge at the left, with vertical red lines within the object. An object moving to the left develops a white edge at the right, with vertical green lines within the object. In these days of high-quality display panels such motion artefacts clearly need to be reduced or eliminated. Hence the Panasonic Plasma AI drive system.

Panasonic Plasma At drive

Al stands for adaptive intensification, and is used with many Panasonic TV sets to maintain good black and white levels with a wide range between, thus making blacks blacker and whites whiter. Plasma AI redefines the traditional eight-bit subfield drive system by using a linearcoded 10, 11 or 12 sub-field drive system. A high-brightness scene uses 12 sub-field drive to improve the dynamic range. A low-brightness scene uses 10 sub-field drive, as this improves the lighter part of the scene. Anywhere in between uses 11 sub-field drive. Because this is a linear coded system (1, 2, 4, 7, 11, 16, 24, 31, 42, 52, 66 etc.) there are no immense timing errors, as in the eight-bit system, and motion artefacts are greatly reduced.

Even within this linear system there are certain sustain values that could produce motion artefacts. This is overcome by programming the software to avoid certain combinations of numbers. The result is that this Plasma AI system can produce moving pictures of excellent quality, without any of the problems that were associated with previous plasma displays.

Line scanning

There's another problem that has to be solved, panel brightness. As a plasma cell emits only a fairly feeble glow, normal successive pixel scanning as used with a CRT would produce a weak picture. To overcome this problem, complete lines of cells are illuminated.



Lower data drive

Video/RGB processing, interlace-toprogressive scan conversion, scaling and sub-field drive

Fig. 8: Panel layout, rear view.

Line one is illuminated completely, then line two completely and so on. This process is known as line-sequential scanning and provides a good light output level.

Panasonic takes this a step further by employing a dual-scan system to double the light output. The plasma panel in effect consists of two horizontal panels joined together in the middle, see Fig. 7. The two panels are scanned simultaneously. What we have is two separate displays of 240 x 852 pixels giving, together, 480 x 852 pixels.

The combination of this dual-scan system with Plasma AI produces a display that rivals the CRT in brightness and contrast. This is clearly important with a display that has to compete at the top end of the domestic TV market.

Real black level

One of the deficiencies of plasma displays is the lack of a black level. Black is never truly black, as the initialisation of each cell before write and sustain results in a very low background illumination. In a newer panel Panasonic has increased the display blackness by initialising only once during a complete sub-field cycle, i.e. once in 10, 11 or 12 depending on the Plasma AI analysis. This increases the black-to-white ratio from about 250:1 to about 3,000:1, which is far in excess of a standard CRT.

It's possible that visual artefacts could arise because of the less frequent initialisation process, but the subjective increase in picture quality seems worth the risk.

Energy recovery

A major problem with plasma display panels is their capacitance. There's a tiny capacitance between the electrodes of each cell: multiply this by 1,226,880 and you have a large capacitance. The drive waveforms therefore require considerable power to overcome the initial charging of each cell.

To compensate for this, Panasonic uses a power-factor controller in the main feed to the switch-mode power supplies and an energy-recovery circuit that works alongside the scan-drive system.

Use of the power-factor controller results in greater than 90 per cent efficient regulation of the high-voltage supplies. As a result, a great deal less heat is generated throughout the regulation processes.

The energy-recovery circuitry recovers some of the capacitive charge energy from the panel. This can be used to assist the scan-drive circuit.

These techniques reduce the power consumed by the panel and, as a result, the heat generated by the panel-drive circuits and power supplies. The reason for all this additional processing is to



Fig. 9: Board layout at the rear of the panel. Board functions are listed in Table 1.

remove the need for internal cooling fans and reduce the energy demand on the mains supply.

Panel layout

Fig. 8 shows the layout at the rear of the Panasonic plasma panel. Fig. 9 illustrates the board layout. Table 1 lists board functions.

Input connections

A plasma display panel is not itself a TV set: it's a display device. It has no builtin tuner unit, or scart inputs. Panasonic does however have a tuner box with three scart sockets at the back and RCA audio/video inputs at the front. The plasma panel itself has three difference input sections, see Fig. 10. The AV section has BNC composite video and 4-pin S-video (separate luminance and chrominance) inputs. The centre section has component-video

inputs as used in broadcast-quality applications. The third section is for PC use.

In Japan, a tuner/games console can be connected to the large port in the PC



Fig. 10: Input connections to the panel, European version.

Table 1: Board functions (see Fig. 9).

Board	Function	Board	Function
C1 C2 C3 C4	Data drive (upper left) Data drive (upper right) Data drive (lower right) Data drive (lower left)	P6 P7 P8 S1	Primary voltage control Sustain voltage protection Processing voltage protection Power switch and remote-cor trol receiver
D DS F H2 H4 HG P1	Digital processing/control Input converter Line filter PC input terminal Speaker terminal Interface Power supply	S2 SC SD SS SS2 SS3 SU	Factory use Scan drive Scan output (lower) Sustain drive Sustain connection (upper) Sustain connection (lower) Scan output (upper)
P3 P5	Sustain voltage control Processing voltage control	∨1	Front switch

section, but this is software-disabled for Europe. The European tuner's output is connected to the BNC inputs. Be careful when making this connection. If the 'out' BNC video connector is used there will be an over-white, crushed-video effect.

Each section has its own audio inputs: RCA for the AV and component-video sections and stereo jack for the PC section.

Handling precautions

The internal pressure within a plasma panel is at two thirds of an atmosphere. At above 3,000m the internal pressure will exceed the external pressure and there will be loss of cell integrity at the centre of the screen (a bulge), with the gas from a number of cells being released and combining. The panel is ruined of course. A replacement panel is typically half the cost of the entire unit – about £4,000.

Another way of damaging the cell integrity of a plasma display panel is to transport it on its face or back, because a bump or jolt may flex the panel, again releasing and combining cell gases. Panels should be transported and stored as you would watch them, i.e. vertically upright. I have transported many panels without problems simply by placing them upright on the back seat of my car and securing them with the seat belts.

Video processing

The video/RGB/drive processing carried out in a plasma panel is extremely complex. The following is a brief summary of what's involved.

Video decoding and digitisation: Any large-screen display must use a highquality digital comb filter to separate perfectly and clean up the luminance and chrominance components of the signal while maintaining their full bandwidth. Plasma panels are no exception. A highquality comb filter is incorporated in the digital decoder chip. It provides Y, U and V outputs for the component interface sections that produce digitised Y, U and V signals.

Interlaced-to-progressive converter:

The first complex processing stage converts the interlaced video or RGB signals to progressive-scan signals. This complex processing uses complete frame memories to store successive fields of information. The processing must also analyse picture movement for the adaptive motion processing, by considering past, present and estimated future lines of information. This section also provides picture noise reduction and auto/manual aspect ratio control.

Format converter or scaler: The plasma panel has a 480×852 cell address system or, more correctly because of the dual-scan system, a $240 \times 852 \times 2$ format. All incoming formats must be converted accurately to this one. The processing is again complex, and requires memories for storing and converting picture information while being careful not to affect natural motion in the picture.

Plasma AI: This section analyses the overall picture information and selects the 10, 11 or 12 sub-field drive system depending on picture content. The complex analysis works through millions of convoluted calculations a second.

Sub-field drive generator: This section generates the sub-field drive information and the scan/sustain timing and data drive signals, depending on the information provided by the Plasma AI section.

Display panel defects

It's not unusual to find that a plasma display panel has one or two dead cells. As three coloured cells contribute to each pixel, this may not be obvious until a single red, green or blue raster is displayed. These single-colour rasters are built into the normal service menus to enable a panel to be checked for defects. During manufacture single cells that flicker annoyingly may be produced. These are burnt out with a laser, as a dead cell is far less noticeable than a flickering one.

A customer may query the number of dead cells allowed with any one panel. Panasonic publishes a specification chart at its technical internet site

www.panasonic.co.uk/dealer

This specification allows three dead red cells and three dead blue cells within the central viewing area of the display and six each dead red, green and blue cells in the outer viewing area. The mathematically astute will realise that a good panel may have 24 dead cells. But, as production has improved over the last two years, I've seen panels that are almost perfect. Very rarely will you find more than a couple of dead cells in a modern panel. The pre-production sample I used when preparing this article had five dead cells, three red and two green.

Image burn

One problem that plasma panels can suffer from is after-image burn. It would obviously be the result of leaving a bright, stationary image on screen for some time. The Panasonic panel has a built-in burn removal system that can be accessed from the service menu. Basically, a thick white bar (scroll bar) repeatedly moves across the screen, helping to bring the affected cells back to normal emission.

Image burn can be caused by two things. First, activated or energised gas. This effect can take half an hour to occur. After considerably longer times there may be phosphor damage. Activated gas can be cured by using the scroll bar, but phosphor damage creates a permanent burn.

Telephone Sales:	01630 69 2604	Univer	201	Fax Sales:	01630 69 2612
Inventory	Management	Univer	Sal	Stock So	olutions
EUROPES	LARGEST	TRADER	OF	CUSTOMER	RETURNS
EUROPES	LARGEST	TRADER	OF	REFURBISH	ED STOCK
EUROPES	LARGEST	TRADER	OF	CLEARANCE	STOCK
	ARE YO	U READY	ТО	PROFIT?	
CALL OR FAX UNIVERSA	L NOW AND CHANGE YOUR F	ORTUNE Ω s		TEL 44 (0)1630 69 2604 /	FAX 44 (0)1630 69 2612
Amstrad, Olivetti, Toshiba, Epso Sainsbury's Stores, Akura, Com Samsung, Computer 2000, IDS,	n, United Marine, PST, Fidelity, Thom let, Orpro Company, Profilo Telra, Fun Terim, Electrolux, Morphy Richards a	son, Tesco Stores, Ferguson, Ph al, Hon eywe ll, Goblin, Sony, ind many more	ilips, CIM Inte	ORLDWIDE STOCK	SOLUTIONS
Iniversal House Tern Valley Bu	isiness Park Market Dravton St	ronshire England TE9 3SC			

October 2001 TELEVISION

Available Now...



The NEW Seme Trade Catalogue of General Spares & Accessories including the NEW SAU * 8 CD Catalogue

The most powerful combination of parts information ever produced for the service industry. If you would like our Trade Catalogue including the latest **STI** * CD please contact sales and add **CAT2002** to your next order. * Free carriage on all **STI** orders of £12 or more.



Tel: 01664 484000 Fax: 01664 563976 *email: sales@seme.co.uk*







Have you got problems with a particular repair? Place your questions on the pinboard and you should soon receive tips/or diagrams from either EURAS International or fellow technicians worldwide.

For trial details call us now on 0117 9860900, e-mail at sales@euras.com

The various videotape and optical-disc recording formats have now been joined by hard-disk recording systems such as TiVo and Sky+. George Cole describes the technologies and products available in the UK and elsewhere

Video systems



Intil recently all domestic video recording formats used magnetic tape as the storage medium. It's easy to appreciate why: videotape is cheap, reusable and provides high-density recording. With VHS you can get up to four or five hours' recording time from a single cassette in the standard-play mode, even longer in the long- and extended-play modes. The data-VHS format uses compression technology to extend the recording time to up to 21 hours with an E-240 cassette. VHS uses ferric-oxide tape, while camcorder formats like Hi-8, Digital-8 and MiniDV use metal-particle or metalevaporated tape that gives even higher storage density.

Despite its benefits videotape can be a frustrating medium to use, especially when it comes to searching for a particular scene or recording. Developments like turbo-drive decks, which provide fast tape winding, and the VHS Index Search System have helped. But because tape is a linear format it can never provide fast random access like a disk or disk-based format.

This year will see the launch of the first domestic DVD recorders in the UK. They record video on a 4.7Gbyte optical disc and provide random access and other features that are beyond the capability of VHS. But even this format will struggle to match the functionality of the new generation of video recording systems that reached the UK market last year: hard-disk video recorders.

These devices use hard-disk technology as the storage medium, and bring new features and functionality. So far, three hard-disk products have been introduced in the UK: the TiVo and Sky+ set-top boxes, and JVC's HM-HDS1, an S-VHS-ET VCR combined with a 40Gbyte hard-disk drive. Many more hard-disk products will arrive during the next year or two. Datamonitor, a market-research company, forecasts that by the year 2005 48 per cent of the set-top boxes in Europe will incorporate some form of hard-disk technology.

Hard-disk basics

What follows is a very basic description of a hard disk, which is best-known as a storage device that resides somewhere inside every PC. The advantages of hard-disk technology are high storage capacity, relatively low cost and the fact that, unlike RAM memory, data continues to be stored when the power is

Check out the new look TELEVISION AND HOME ELECTRONICS REPAIR

Tips, guides and reports for people repairing televisions and electronics equipment



Subscribe now...

AND HOME ELECTRONICS REPAIR SUBSCRIBE

World-wide (please tick one of the following):

UK	Europe	Rest of World
3 years (36 issues) 🗆 £64	🗆 £92	□ £119 1 year FREE!
1 years (12 issues) 🗆 £32	£ 46	59 Saving 10%

IN EVERY ISSUE

- News, equipment reviews, components, servicing solutions, business-building ideas.
- Television, VCR, satellite, CDs, PCs, consumer electronics.
- State of the art reports on digital TV and other developments.

FULL MONEY-BACK GUARANTEE

If you are not completely satisfied with TELEVISION within the first 60 days, we'll refund your money in full - no questions asked.

Please allow 28 days for delivery of your first issue.

EUSINESS MEDIA Cumulus Business Media Limited Anne Boleyn House, 9-13 Ewell Rood, Cham, Simy, SMAT MBZ, UK (Registered No. 4189911) Cumulus Business Media Limited may use this information far direct marketing purposes, from ourselves or other companies. If you do not wish to receive direct marketing please write to us at Cumulus Business Media Limited, Perrymount Road, Haywards Heath, West Sussex, RH 16 3DH.

THREE WAYS TO PAY

TELEVISION	que for £	made payable to
2. Please charge m	ny: Visa A Switch D	MEX Mastercard
Account number		(Switch/Delta o
Expiry date	(Switch/Delta/applica Valid from	ble for certain credit cards) Issue number
Signature		Date
3. Please invoice m	ne/my company	
 Please invoice n Purchase order n Name: 	ne/my company	
 Please invoice n Purchase order n Name: Company name: 	ne/my company umber:	
3. Please invoice n Purchase order n Name: Company name: Address:	ne/my company	
3. Please invoice n Purchase order n Name: Company name: Address: Postcode: So that we can keep you	umber:	lated information, please supply your
3. Please invoice n Purchase order n Name: Company name: Address: Postcode: So that we can keep you email address in the spo Email address in the spo	umber:	lated information, please supply your
3. Please invoice n Purchase order n Name: Company name: Address: Postcode: So that we can keep you email address in the space Email address : If you do not wish to receive relevant	umber:	lated information, please supply your

RETURN TO: 'TELEVISION' SUBSCRIPTIONS, PERRYMOUNT ROAD, HAYWARDS HEATH, UK, RH16 3DH . OR CALL: +44(0)1444 445566 (QUOTING CODE 139). FAX: +44(0)1444 445447. switched off. Over the years computers have used a variety of data-storage media, including punch cards, magnetic tape and floppy discs, but the hard disk is at the heart of today's PCs.

IBM invented the hard disk in the Fifties, as a replacement for punch cards. The first hard disks had a diameter of about 20 inches and stored only a few Mbytes of data. But this was equivalent to tens of thousands of punch cards, while data could be accessed very quickly in comparison with the older medium. These hard disks were very, very expensive however. Storage cost was about £7,000 per Mbyte! In the Seventies IBM developed a new type of hard disk, code-named Winchester. These new disks were smaller yet offered higher storage capacity. Storage cost was down to about £70 per Mbyte. These disks are the basis of the modern type. Today some hard disks are the size of a ten-pence piece and can store tens of Gbytes of data.

Hard disks have a magnetic recording layer similar to that used by audiocassette tape. But whereas audio tape uses a plastic base film, with a hard disc the layer is formed on a glass or aluminium disk called a platter. To increase storage capacity, most hard disks have several platters that are stacked on top of each other, with spaces in between for the read/write heads – these are mounted on actuator arms.

Data is stored on the surface of a platter as a series of tracks and sectors, the latter being pie-shaped sections of the platter. Hard disks rotate at high speed, typically 3,600 or 7,000 r.p.m., the data being read or written by record/playback heads that skim over the surface of a platter – if a head touches a platter, the disk suffers a crash.

Hard discs are stored inside an airtight aluminium case to protect them from dust and vibration. A PCB contains the electronics for interfacing with other devices, such as the motor that spins the platter.

Home PCs have for many years been able to store text, data, games and audio on a hard disk, but video has been more of a problem. This is because video files are very large and, even when compressed, can require Gbytes of storage capacity for high-quality video. In the Eighties and early Nineties most domestic PCs had a hard disk whose storage capacity was measured in Mbytes. Over the past few years however the capacity of hard drives has increased and they have become cheaper. Today, most home PCs have a hard disk with a capacity of 10Gbytes or more.

It now costs less than 1p to store



A PVR developed by Pace, with hard-disk drive for data storage.

1Mbyte of data on a hard disk, and a typical hard-disk drive costs about £70. According to NDS, the capacity of hard drives will double by next year, while by 2005 it will be possible to store 1,000 hours of video on a hard disk.

DVRs, PVRs and PTRs

Incorporating a hard disk in a consumer electronics product like a digital set-top box presents many challenges. These include coping with the heat generated, the noise from the motor and fan, and vibration. But the latest hard-disk drives, sometimes called 'whisper drives', are no noisier than a VCR. One issue is reliability, and whether a hard drive is likely to crash. In fact most hard-disk 'crashes' are caused by a software problem: they often involve a breakdown in the PC's operating system, insufficient RAM, or a software conflict. Many hard-disk video products use the Linux operating system, which is more stable than Windows, and according to Pace the mean time before failure (MTBF) with a modern hard disk is typically more than 500,000 hours.

The inside of an integrated harddisk/set-top box is similar to that of a conventional STB. The main differences are the presence of the hard drive, an interface card, an additional tuner, a cooling fan, some additional circuitry and the need for a power supply with greater power-handling capability. These are all fairly standard items. Perhaps the greatest challenge is to ensure that the software operates in the required manner.

But why use a hard disk to store video when there's cheap and cheerful VHS tape? The answer is that hard-disk recording provides new features that are impossible with VHS and that even the new DVD recorders will struggle to match.

The most obvious benefit of disk over tape is the fast access provided by the former: you can find a specific recording quickly and easily without having to wind through metres of tape. Hard-drive read/write heads also make it possible to pause a live TV broadcast while the remainder of the programme is being recorded. So, if the phone rings while you are watching your favourite TV programme, you can pause until the interruption ends then continue watching where you left off. The rest of the programme will have been recorded on the disk. It's even possible to record two different programmes at the same time, then watch them on the screen together - so far however this feature is available with only one hard-disk video system.

There are two basic hard-disk recording devices. A digital video recorder (DVR) simply records video on a hard disk. Over the next few years we are likely to see many TV sets with a built-in DVR. The personal video recorder (PVR) or personal television recorder (PTR) is a smarter version of the DVR: it combines a hard-disk video recorder with smart software. Products in this latter category include TiVo and Sky+.



Internal view of a Pace PVR with harddisk drive.

TiVo

The first PVR, TiVo, was launched in the US in 1999 by the company of the same name. It came to the UK in October last year, and was marketed initially by BSkyB. Sony and Philips, which have invested in the TiVo company, manufacture the US version. TiVo is also built into some DirecTV digital satellite receivers in the US.

The TiVo PVR looks like a large VCR. It's designed to work with most TV systems, terrestrial, cable and satellite, and with both analogue and digital signals. There are one or two exceptions however, see below. TiVo uses MPEG-2



The Sky+ remote control unit.

video compression and a Power PC processor that runs Linux.

US consumers can choose TiVo products that provide up to 20, 30 or 60 hours of storage capacity. Prices start from the US equivalent of about £150.

The UK version of TiVo is made by Thomson. It has a 40Gbyte hard drive that can store about 40 hours of video. Picture quality in this mode is quite poor however. So many viewers prefer to use a lower compression ratio. TiVo offers four settings: best, which gives up to fourteen hours' recording time and close to DVD picture quality; high, which gives up to 22 hours' recording time at a lower picture quality; medium, which gives up to 28 hours' recording time; and basic which provides a recording time of 40 hours plus.

TiVo works with most analogue and digital TV systems, the exceptions being analogue satellite and digital cable. TiVo plans to make its PVR compatible with the latter later this year.

The TiVo PVR can be connected to a TV set, set-top box, VCR and telephone line. There are connection sockets for RF in/out; three scart sockets for TV, VCR (with RGB loop-through) and set-top boxes (auxiliary); twin phono audio sockets; and a serial data port jack. There's also an IR blaster, for controlling an STB, and an internal V90 (56kbits/sec) modem. The telephone connection is used for downloading programme data, which TiVo needs to be able to operate, and software updates.

In the UK TiVo currently costs about £400. In addition there is either a £10 monthly subscription, or a £199 lifetime subscription, for downloads that provide software updates and channel information. TiVo uses the latter for various features, such as being able to record all the episodes of a favourite series. It can also 'learn' which programmes the viewer likes to watch and automatically record them. TiVo has struck deals with Channel 4 and UKTV, which will download programme trailers on to a TiVo hard drive. These trailers can be used to ensure that a TiVo unit records the programmes as they are broadcast. TiVo lacks some useful features however, such as PDC which automatically adjusts the timer recording switch-on should a programme's published start time alter, for example when the previous programme overruns. A planned software update will enable viewers to extend the recording by fiveminute increments.

In May TiVo reported that in the three years since its US launch the number of subscribers worldwide had reached 200,000. This does not sound a lot but, as TiVo points out, the figure exceeds the number of VCRs sold during the first three years after launch – some 120,000 worldwide.



The TiVo PVR box with remote-control unit.

Since the launch of Sky+, some have questioned the long-term viability of TiVo in the UK. TiVo costs £100 more than Sky+, but the price gap narrows when you take into consideration the £50 (or £100) installation charge for Sky+ – TiVo has a self-installation system. And while TiVo is compatible with a range of TV systems, Sky+ is a dedicated digital satellite system. In the long term TiVo looks more likely to become a feature found in set-top boxes, VCRs and TV sets rather than a standalone format.

Sky+

BSkyB unveiled its Sky+ PTR in July, and it should now be on sale. The product is aimed at SkyDigital viewers and, unlike the digibox, is unsubsidised. It can be used with free and pay-TV services.

The Sky+ PTR uses a blend of technologies developed by Pace, NDS, OpenTV and NEC. Pace provides the hard-disk technology, NDS the XTV (Xtended TV) technology (see below), OpenTV the middleware and NEC the chipset. The Sky+ box contains a 40Gbyte hard drive, an MPEG-2 decoder, a V90 modem, and a twin satellite tuner/demodulator. It has two RF outputs, an S-video output, phono audio outputs, an optical digital audio output that provides Dolby Digital sound, a high-speed data interface and two smart card slots - one for a Sky viewing card and the other for an interactive card. The hard drive can store up to 40 hours of video, but in practice BSkyB quotes about 20-22 hours. This is because, unlike the TiVo unit, Sky+ stores, records and displays a TV programme at the same data rate at which it's being transmitted. Sky often uses statistical multiplexing to improve bandwidth efficiency: as a result, the bit rate may vary with programme content.

The Sky+ box works with a new quad LNB that has to be installed professionally. It provides many features, such as live pause; one-touch recording; the ability to record one digital TV broadcast while watching another; the ability to record one programme while watching a prerecorded programme; recording and playback of subtitles; full VCR-type functionality; automatic recording of favourite programmes; and an extended version of the Sky Guide EPG. BSkyB says that its EPG interface is to digital TV viewers what the Windows interface is to a PC user, i.e. very familiar.

Sky+ doesn't use PDC, but its timer recording system is linked to the Sky EPG. If the broadcaster shifts the programme time and this data is sent to the Sky EPG, Sky+ boxes automatically adjust the recording time.

A novel feature is the ability to record a

programme by name rather than by time and channel number. An A-Z feature displays all the programmes being broadcast during the next 24 hours. Programmes can also be searched by type, such as drama, comedy, thriller and romance. By simply scrolling down the programme list and clicking on any of interest, the user programs Sky+ to record these.

Other useful features of the Sky+ boxinclude the ability to 'lock' programmes so that they cannot be overwritten accidentally, and a horizontal bar display that tells the user how much hard disk space remains available. Users can also bookmark scenes, and a disk management system automatically carries out housekeeping tasks such as disk defragmentation. The latter means rearranging programme material that has been stored by the disc in different sectors, so that the material is in one place and is thus more readily accessed.

The Sky+ box has an impressive list of features, but earlier reports on the capabilities of XTV had led many industry observers to believe that it would provide new and advanced features, such as software wizards which could, for example, automatically find and record all programmes featuring your favourite actor. XTV can provide personalised TV by 'learning' what a viewer likes to watch. This information could be used to 'target' programmes and advertisements for individual viewers so that material selected by the PVR is available for them on the hard disc. But many of these features rely on new broadcasting standards being set.

NDS is a member of the TV Anytime Forum, which is at present developing standards for PVRs and other devices. The Forum is working on a standard for metadata – data that can be added to enable programme material to be identified by type, and could thus be used by a PVR to provide services such as those mentioned above. Once metadata standards have been agreed, broadcasters could start using them to tag their programmes.

Features like personalised TV raise the question of privacy – a broadcaster could know what you watch and when. BSkyB can already interrogate a Sky+ hard-disk directory and collect personal information, but says it has no plans to do this. The Data Protection Act should prevent this happening without a viewer's permission.

The price of the Sky+ box surprised many observers, who had expected it to retail at about £400-500. In fact the price is £300, which Sky says is unsubsidised. The answer to this puzzle lies in the installation charge (£50 for existing BSkyB subscribers, £100 to nonsubscribers) and a £10 monthly



The TiVo Lifestyle image.

subscription fee. BSkyB says that the fee pays for programme data and software updates, but admits that this was the only way of getting the hardware price below $\pounds 300$.

VCR archiving

Suggestions that PVRs and PTRs will make the VCR redundant are unfounded. Neither TiVo nor BSkyB expects its units to make the VCR obsolete. While a hard-disk is ideal for watch-and-wipe recording, once the hard disk has been filled up something has to be overwritten – or transferred elsewhere.

Both units are designed to be connected to a VCR for the transfer and storage of recordings The Sky+ box has a batch recording system that enables the user to preselect the recordings he wants to be transferred to tape. The box transfers them to a VCR automatically – provided a VCR with a blank tape has been connected of course.

ReplayTV

ReplayTV is another PVR system that's available in the US. The ReplayTV company originally marketed hardware PVR products but subsequently became a software and services provider. At present the only manufacturer that supplies ReplayTV products for the US market is Panasonic, which has a stake in the company.

ReplayTV offers similar features to TiVo, but there's no monthly subscription fee. Panasonic has launched several ReplayTV PVRs in its Showstopper range. Model PV-HS2000 provides up to 30 hours' recording. Model PV-HS3000, with a 61-4Gbyte disc, can record up to 61 hours of video in its extended mode, 30.5 hours of video in its medium mode and 20.5 hours in its high mode. Panasonic has also launched a TV set with a built-in ReplayTV PVR, Model PV-SS2710. It has a 27in. screen and can record up to 30 hours of video.

Ultimate TV

Microsoft bought the WebTV service, which offers viewers enhanced TV, interactive TV and internet services, in 1997. One version of WebTV, known as Ultimate TV, has a PVR that can store up to 35 hours of video. It can also record two different programmes simultaneously, and has a picture-inpicture facility for watching two programmes together on a single screen, and in addition 300x picture search.

Ultimate TV is currently available only with the DirectTV service. Sony and RCA have launched combined DirecTV receiver/Ultimate TV digital set-top boxes.

Dish PVR

US digital satellite broadcaster EchoStar offers new subscribers the Dish PVR 501. The PVR can record up to 35 hours of programming and has a skip forward feature that advances playback by thirty seconds to bypass advertisements.

Pace

Pace has developed hard-disk products that extend the scope of the digital settop box. One product is the Games Gateway, which uses technology derived from Sega's Dreamcast 128-bit games console. It has a 40Gbyte hard disk that can store up to 60 games, and will



The Pace Games Gateway, which uses technology derived from Sega's Dreamcast games console.

include graphics and sound cards or chips to provide enhanced performance. Pace believes that the STB/PVR will evolve into a domestic gateway. a networking device that links the TV to lots of appliances around the home and services outside it.

Nokia Media Terminal

Nokia has developed what it calls the Media Terminal, a network box that includes a PVR with a 40Gbyte hard drive. Other features include an Intel Celeron processor running Linux and 64Mbytes of RAM. The Media Terminal is expected to be launched in Sweden later this year.

Games consoles

Microsoft's Xbox games console, which is due for release in Europe next year, has an internal 8Gbyte hard drive for storing games. Sony has developed a 40Gbyte external hard drive for the PlayStation 2 console. It's currently available in Japan.

PC video recorders

We've now come full circle, with home PCs turning into PVRs and digital video recorders thanks to large-capacity hard disks. compact TV tuners and video editing software. MGI (formerly called Diva) markets software that turns a standard PC into a PVR. It requires a PC system with a minimum specification that includes a 500MHz Pentium III processor, Windows 98. 128Mbytes of RAM and 8Gbytes of available hard-disk space. Packard Bell's Dre@am Machine PC has a 40Gbyte hard drive and a DVD-R recorder. The product is designed so that the user can edit video footage on the hard disk then transfer it to a DVD-R disc.

Apple's latest G4 computer has a built-in DVD-R drive, while Hewlett-Packard and Dell plan to launch PCs with built-in DVD+RW drives. These machines may offer similar features to the Packard Bell product.

Hard-disk combi products

Hard disks are being combined with other video equipment. The JVC HM-HDS1 for example is a combined S-VHS-ET recorder and 40Gbyte harddisk drive. Its HD drive offers several recording modes from SP to SEP. SP operates at 6-4Mbits/sec to provide about 14 hours of DVD-quality recording. SEP operates at 2-2Mbits/sec to provide a recording capacity of about 40 hours. The hard disk can be used as a PVR or for non-linear and randomassemble editing, with the results transferred to S-VHS or VHS tape.

Toshiba has produced the RD-2000, a DVD-RAM recorder combined with a 30Gbyte hard drive that can store up to 33-5 hours of video.

		\$1			
REFURB D	GIBOX	KES			
PACE 2200 GRUNDIG 200 AMSTRAD 100/200	1 off £150 5 off £125 1 10 off £100	ALL PRICES INCLUDE VAT + DELIVERY			
PACE 2500 GRUNDIG 300	1 off £199 10 off £150	ALL PRICES INCLUDE VAT + DELIVERY			
PACE 2500 S3 GRUNDIG 310 PANASONIC DSB3 ALL UNITS IN BOXES W	1 off £250 5 off £225 0 10 off £199 ITH NEW REMOT	MLL PRICES INCLUDE VAT + DELIVERY			
AND LEADS ETC PLUS 12 MONTHS WARRANTY LARGE SELECTION OF ECHOSTAR SPARES					
TRADE REPAIR CENTRE ALL TYPES OF DIGITAL RECEIVERS REPAIRED. CALL US – LARGE QUANTITY DISCOUNTS					
SATELLITE AND DIGITAL SERVICES Unit 4/5 Caddsdown Industrial Park Bideford, Devon EX39 3DX 01237 470333/01271 325777/888					



The best in CRT Screen Polishing

Registered Office:

'Fairlands', Beckney Avenue, Hockley, Essex SS5 5NR

> Tel: Southend on Sea (01702) 201108

C.R.T.'S REPROCESSED TO ORIGINAL MANUFACTURER'S SPECIFICATION.

PHILIPS, SONY, HITACHI, etc. POLISHING SERVICE AVAILABLE

The wis headend that says YES to

- Quality
- Ease of use
- Agility
- Each module an . almost total entity
- Superb value

WISI's Topline headend system is very competitively priced yet is of superior design and build. It is easy-to-use with high quality channel processing that allows the user to retain quality of vision and sound for both analogue and digital signal sources. There are processors far satellite TV, terrestrial TV and radio.Each individual module incorporates its own control system enabling quick and easy set up. These channel processors come together in an 'all-in-one' base unit which contains all necessary accessories for ease of ordering no additional items required.

U.K. STOCKIST J.W. Hardy Communications



- CHECK THESE FEATURES
- Frequency agile freely selectable in the VHF of UHF range.
- Adjacent channel capable
- TV standards 64 QAM B/G, D/K, I, L, M. Modular system for headend stations in SMATV and CATV systems
- Modules for Analogue and Digital
- Satellite TV & Radio Analogue & Digital Terrestrial TV & Radio Analogue & Digital Tearestrial TV & Radio Analogue & Digital Terrestrial TV Carverters: Analogue & Digital compatible Terrestrial TV Carverters: Analogue & Digital compatible
- TV Modulators Analogue & Digital Individually programmable modules
- High output level

- . Wall mounting or 19" rack mount with lockable cabinet door
 - May we send you full details?



J.W. HARDY COMMUNICATIONS, 231 Station Road, Birmingham B33 8BB Telephone 0121 784 8478 Fax: 0121 789 7931

ONLINE SHOPPING CHEAPER AND EASIER www.elclondon.co.uk

TV. VIDEO SPARES AND ELECTRICAL ITEMS



ELC EAST LONDON COMPONENTS 63 PLASHET GROVE, LONDON E6 1AD. TWO MINUTES WALK FROM UPTON PARK TUBE STATION TEL: 020 8472 4871 FAX: 020 8503 5926 E-mail: sales@elclondon.co.uk

SPECIAL OFFERS	MARCONI 2019A	GOULD OS 300 OSCILLOS	COPE	RADIO COMMUNICATIONS TEST SETS
Thet AIA .	Tableton Contained Manager	DUAL TRA 20MHz TE	STED	MARCONI 2955/2955A from £1500 SCHLUMBERGER 4040 £900
	T- J	MANUAL	£95	SPECTRUM ANALYSERS
	AM/FM synthesised signal	MARCONI 2022E Synthesised AM/FM Sig Gen 10KHz-1 01GHz LCO Display etc	£525-£750	ADVANTEST R4131B 109kHz-3 5GHz£3500 H P 8591E 1MHz-1 8GHz, 75 Ohm £4500
ONLY	generator 80kHz-1040MHz	H P 8657A Synthesised 100kHz-1040MHz Sig Gen H P 86568 Synthesised 100kHz-990MHz Sig Gen	£2000 £1350	H P 85588 with Main frame 100kHz-1500MHz £150
CTRONIX 2445A 4Ch) MHz Delay Cursors etc . pplied with 2 Tektronix probes	NOW ONLY £400	H P 8656A Syntheseed 100kHz-990MHz Sig Gen H P 8640A AM/FM 500kHz-1024MHz Sig Gen H P 8640A AM/FM 500kHz-512MHz Sig Gen	£995 £400 £250	H P 853A (Dig Frame) wrth 8559A 100kHz-21GHz E2250 H P 3580A Audio Analyser 5Hz-50kHz As new \$1000 B & K 2033B Signal Analyser
TRONIX 2232 Digital Storage Scope, Dual Trace,	MARCONI 893C AF Power Meter Sinad Measurement	PHILIPS PM5328 100kHz-180MHz with 200MHz Sig Gen	Freq Counter	H P 182 with 8557 10kHz-350MHz £50
MHz, 100m/s with probes £525	Used £60	IEEE RACAL 9081 Swith AM/EM Sig Gen 5-520MHz	£550 £250	MARCONI 2370 30Hz-110MHz from £500
3312A Function Gen 0 1Hz-13MHz AM/FM	MARCONI 893B - No Sinad £30	H P 3325A Synth Function Gen 21MHz	2600	HP141 Systems 8553 1kHz-110MHz from
eep/Tri/Gate/Burst etc E300	MARCONI 2610 True RMS Voltmeter Autorangin 5Hz-	MARCONI 6500 Amplitude Analyser	£1500	from £100
0 Oisplay £180	GOULD J3B Sine/Sq Osc 10Hz-100KHz Low distortion	H P 8903A Distortion Analyser	£1000	H P 5372A Frequency and Time Interval Analyser . £2250
RUS CRL254 Sound Level Meter with Calibrator.	£75-£125	WAYNE KERR 3245 Inductance Analyser	£2000	
12008, LEU E150 DYSTONE 1002 Receiver 150kHz-30MHz + Broadcast	AVD 8Mk6 in Ever Heady Case with leads etc £80 Others Avos from 550	PLP 8112A Pulse Generator Sowerz DATRON AutoCal Multimeter 5%76 doit: 1065/1061A. 10711	1250 rom £300-£600	OSCILLOSCOPES
Unused £125	GODOWILL GFC8010G Freq Counter 1Hz-120MHz	MARCONI 2440 Frequency Counter 20GHz	£1000	TEKTRONIX TDS380 Dual Trace, 400MHz, 2G/S £2000
INELL AMM255 Automatic Mod Meter 1 5MHz- 17 Unused 5300	Unused £75	H P 53508 Frequency Counter 20GHz H P 52424 10Hz 18CHz Engrander Counter	£2000	TEKTRONIX TDS350 Dual Trace, 200MHz, 1G/S, unused £1500
1. 0.0004	GDDDWILL GVT427 Dual Ch AC Millivoltmeter 10My-in 12 Ranges Fren 10Hz-1MHz C100-C125	B&K Accelerometer type 4366	£300	TEKTRONIX TDS320 Dual trace, 100MHz, 500M/S, £1200 TEKTRONIX TDS310 Dual Trace, 50MHz, 200M/S \$956
3310A Function Gen 0 005Hz–5MHz, S125	SOLARTRON 7150 OMM 64 digit True RMS - IEEE	H P 11692D Dual Directional Coupler 2MHz-18GHz	£1600	LECROY 9400A Dual Trace, 175MHz, 5G/S . £1500
ELL FLM4 Sine/Sq Oscillator 10Hz-1MHz, low	£95-£150	TEKTRONIX P6109B Probe 100MHz Readout, Unused	11250	TEKTRONIX TAS485 4 Ch 200MHz etc. unused
rtion, TTL output, Amplitude Meter £125	SOLARTRON 7150 Plus £200	TEKTRONIX P6106A Probe 250MHz Readout. Unused	£85	TEKTRONIX THS720A Dual Trace LCD 100MHz 500M/S
545A Logic Probe with 546A Logic Pulser 547A Current Tracer £90	9300 5Hz-20MHz usable to 60MHz, 10V-316V £95	H P 16508 Logic Analyser 80 Channel MARCONI 2305 Mod meter, 500kHs 2GHz	£1000 £750	HITACHI VC6523 Dual Trace 20MHz 20M/S Delay Cursors etc
E 77 Multimeter 37, digit Handheld £60	9300B Version £150		2100	unused £600
E 1000 LCO Clamp Meter 0–1000A In	9301/9302 RE Version to 1 5GHz from £200-£300 HIGH DUALITY BACAL COUNTERS	ROHDE & SCHWARZ APN 62		PHILIPS PM3092 2+2 Ch 200MHz Delay etc £800 As new £950 PMILIPS PM3092 2+2 Ch 200MHz Delay etc £800 As new £950
ring Case £60	9904 Universal Timer Counter 50MHz £50	SIGNAL GENERATOR. BALANCED/	425	TEK TAS465 Dual Trace 100MHz Delay etc. 2700 AS new 200
ACAL 9008	9916 Counter 10Hz-520MHz 2 575	UN-BALANCED OUTPUT. LCD DISPLAY		TEK 24658 4 Ch 400MHz. Delay Curs £1500
UTOMATIC	9918 Counter, 10Hz-560MHz, 9-digit E50	H P 6012B DC PSU 0-60V, 0-50A 1000W	£1000	TEK 2465 4 Ch 300MHz Delay Curs £900
ODULATION	SOLARTRON 7045 BENCH	FARNELL AP60/50 1kW Autoranging	£1000	TEK 466 Analogue Storage Dual TOUWITZ Detay £430 TEK 466 Analogue Storage Dual 100MHz £250
ETER AM/FM	MULTIMETER	FARNELL H60/50 0-60V 0-50A	£750 £400	TEK 485 Dual Trace 350MHz Delay E550
5MHz-2GHz ONLY	4½ digit BRIGHT	Power Supply HPS3010 0-30V, 0-10A	£120	TEK 475 Dual Trace 200 MHz Delay £400
	LED WITH LEADS	FARNELL L30-2 0-30V, 0-2A FARNELL L30-1 0-30V, 0-14	083 063	PHILIPS PM3217 Dual Trace 50MHz Delay £200-£250
8494A Attenuator DC-4GHz 0-11dB N/SMA£250 8492A Attenuator DC-18GHz 0-6dB APC7 £95	ONLY (30)	Many other Power Supplies available	100	GOULD OS1100 Dual Trace 30MHz Delay . £200
Y OTHER ATTENUATORS, LOADS, COUPLERS		Isolating Transformer 240V In/Dut 500VA	£40	HAMEG HM303 4 Dual Trace 30MHz £32
etc AVAILABLE	HUNTRON TRACKER Model 1000 . £125	PORTABLE APPLIANCE TE	STER	HAMEG HM303 Dual Trace 30MMZ \$250 HAMEG HM203 7 Dual Trace 20MMz \$250
DATRON 1061 HIGH QUALITY 5½	FLUKE 8050A OMM 4/ digit 2A True RMS £75	MEGGER PAT2 Only	180	FARNELL DTV20 Dual Trace 20MHz
DIGIT BENCH MULTIMETER	FLUKE 8010A OMM 37 digit 10A £50	MEddeliff Are only		MANY OTHER OSCILLOSCOPES AVAILABLE
True RMS/4 wire Res/Current	MARCONI TF2015 AM/FM sig gen 10-520MHz £175 EARNELL LE1 Size So Operatives 10Hz 1MHz 575	TIME 1051 Low Ohm Res Box		
Canvertor/IEEE (159)	RACAL/AIM 9343M LCR Databridge, Digital Auto £200	0.01ohm to 1M Ohm in	£100	RACAL RECEIVER RA1772
CTEWADT -		0.01ohm steps. Unused		BASICALLY WORKING
SIEWARI O				
110 WYKEHAM ROAD, REA	INDING, BERKS RG6 1PL	USED EQUIPME	NT - GUAI	RANTEED. Manuals supplied
Callers welcome Sam 5 30pm Monday M	Friday (other times by arrangement)	This is VERY SMALL SAMPLE OF ST	OCK, SAE 0	r telephone for lists. Please check availability before
Callers welcome sam-stophil Monday to	rinuay (unier times by attangement)	Druening GARMIAGE all Uni	15 £10, VAI	to be added to total of goods and carriage.

TED	SCHLUMBERGER 4040
£95	SPECTRUM ANALYSERS
E525-£750 £2000 £1350 £965 £400 £250 £550 £550 £560 £1500 £1500 £1000	ADVANTEST R41318 109kHz-3 5GHz £3500 H P 8591E 1MHz.1 8GHz, 75 0hm £4500 E ATONAILTECH 757 001-22GHz £150 H P 85588 with Main frame 100kHz-1500MHz £1250 H P 8538 with Main frame 100kHz-1500MHz £1250 H P 8538 (Dip Frame) with 8559 A100kHz-21GHz £2250 H P 8330, Audio Analyser 5Hz-50kHz As new £1000 B & K 2033R Signal Analyser £750 H P 182 with 8557 10kHz-350MHz £500 M ARCONI 2370 3042-110MHz £500 H P 182 with 8557 10kHz-350MHz £500 H P 182 with 8553 1kHz-110MHz £500 H P141 Systems 8553 1kHz-110MHz from £500 B 545 4500Hz / 1220MHz from £750, 8555 10MHz-16GHz £500 H P 5372A Frequency and Time Interval Analyser £2260
£2000 £1250 £1000 £2000 £2000 £300 £1600 £1600 £1250 £85 £1000 £750	OSCILLOSCOPES TEKTRONIX TDS380 Dual Trace, 400MHz, 2G/S
425 £1000 £755 £400 £120 £80 £66 £400 £120 £80 £66 £400 £120 £80 £1000 £120 £80 £1000 £1000 £1000 £1000 £755 £400 £1000 £1000 £755 £400 £1000 £120 £80 £1000 £120 £80 £1000 £120 £80 £1000 £120 £80 £1000 £120 £80 £400 £120 £80 £400 £120 £80 £400 £120 £80 £400 £120 £80 £400 £120 £80 £400 £120 £80 £400 £120 £80 £400 £120 £120 £80 £400 £120 £100 £	unused
100	RACAL RECEIVER RA1772 50KHz -30MHz LED DISPLAY BASICALLY WORKING



TELEVISION October 2001

Servicing the NEI CE25/CE28 series chassis

These chassis, made in Spain or Turkey, were used in a number of different models. Alan Dent provides a detailed guide to fault conditions you could encounter

here were three main versions of this chassis. The first was manufactured by Clarivox in Spain. It's easy to identify: the single-sided board is made of biscuit-coloured material. Version two was made by Vestel in Turkey. The board has double-sided copper and is made of greencoloured material. Version three was introduced in early 1994. It's similar to the basic Vestel version but the audio output stages use a different IC with associated alterations to the layout. It has facilities for adaptation to include a satellite receiver, scart sockets and mono audio. Models fitted with these chassis include the NEI 2571, 2591, 2871, 2891, C25F1TFXZ and C28F1TFXZ, and the Nikkai TLG2501, TLG2801, 5959 and 6666

The power supply

The chassis use a conventional chopper power supply, though the control chip IC100 (type TDA8380) is an uncommon device. Fig. 1 shows the primary side of the power supply circuit, Fig. 2 the secondary side. Regulation feedback from the secondary side is via optocoupler IC101. Fusible resistor R102 (0.22Ω , 2%), which provides current limiting, is a key item.

No output because R102 has failed or is out of tolerance can result in base-collector breakdown in the chopper transistor TR100. The following components will probably have to be replaced: TR100, R102, IC100, IC101, R109, C107, C108 and D104.

If C109 is $2 \cdot 2\mu$ F, change it to $3 \cdot 3\mu$ F. D104 should be a BZX85 series $1 \cdot 3W$ zener diode. If a 300mW zener diode is fitted, uprate it.

Multi-component failure can also be caused by components in the snubber network: check whether C105 is dryjointed or leaky or R328 is open-circuit.

If there's no output because of failure of TR100 and a replacement fails

immediately, R107 or C122 could be low in value or R112 high in value. If TR100 gets very hot (100°C) before it fails, L100 could be dry-jointed or open-circuit. The normal heatsink temperature for TR100, measured at its case, is approximately 50-60°C.

If there's no output with no major failures, check whether R101, R103, R112, R115, R116, C110, C111, C122, D104 or D106 is open-circuit, C112 is short-circuit or IC101 is short-circuit between pins 3 and 4.

If there's no output and the power supply is tripping, the line output transistor TR128 could be short-circuit. Also check the values of R109 and R111, and that D104 is a BZX85 type. The earth track to pin 4 of IC100 could be open-circuit, especially after a power supply blow up. Here's a summary of other power supply faults I've come across:

Low HT (64V nominal): The ripple voltage at pin 5 of IC100 must be in millivolts. If the ripple is higher, C110 is probably open-circuit.

Low HT (139V) and no raster, with the power supply chassis line at 7V relative to the signals chassis: You will also find that the I²C bus appears to fail, i.e. the set seems to be OK in standby but there is no control after coming out of standby. Earth link LK172, top to bottom, is open-circuit. It's under C130.

High HT (180V with no control): IC101 could be faulty or there could be no feedback to IC101 or IC100. Check TR102/3/4 and the associated components, R124/5 which could be open-circuit and C125 which could be short-circuit. If C114's voltage rating (160V) has been exceeded, replace it.

HT is **OK** in standby but drops at power up: The voltage fall may be from 154V to 120V depending on power requirement. R112 is open-circuit.

Set will not switch to standby: TR130 is probably short-circuit. The symptoms are that there's a raster and audio but the standby LED is on.

Noisy chopper transformer (highpitched squealing): R117 or C113 is open-circuit.

In normal operation the power consumption should be as follows:

HT supply 300mA nominal, 400mA at maximum beam current. 26V supply 70mA quiescent, 1·13A at maximum volume. 12V supply 40mA quiescent, 400mA typical.

Line driver and output stages

The line drive signal is generated by a TDA4504B IF/timebase generator chip, IC001, which is mounted on the jungle subpanel. Its line drive output at pin 29 is AC-coupled by C151 (0.1μ F) to a two-transistor driver stage (TR106 JC501P and TR105 BC337), with DC restoration by D123 (1N4148). Fig. 3 shows the circuit. The output is transformer-coupled

(TX101) to the base of the BU508AF line output transistor TR128.

The line output stage is conventional, with a diode modulator (D116, D117) for EW correction. The line output transformer, TX102, generates the tube's EHT, focus, first anode and heater voltages, a 200V HT supply for the RGB output stages, a 28V supply for the field output and EW chips, and a 5V supply for teletext and other functions. The 5V supply is stabilised by IC103 (7805).

A short-circuit line output transistor will cause power supply tripping. Before fitting a replacement check the tuning capacitor C134 (1.2nF, 1.6kV) which could be opencircuit, the result being excessive flyback pulse voltage. In this event the TDA8145 EW correction chip IC107 may be damaged. Other causes of failure of TR123 are shorted turns in the LOPT (TX102) or a drive fault. In the latter case check the value of R174 (6.8 Ω fusible) which feeds the line driver stage, and R123 (1 Ω , 1W) which is in series with the base of TR128 – also see note below on TR128 failure after five minutes.

If a replacement line output transistor goes short-circuit immediately, check the components in the EW modulator circuit: D116 (BY228) or D117 (BY299) might be short-circuit or C131 (9·1nF, 1·6kV, 5%) or C132 (27nF, 400V) could be opencircuit.

If a replacement output transistor goes short-circuit after about five minutes the line drive voltage could be low, not turning TR128 off fast enough. The usual cause is that TR105 (BC337) in the drive stage is open-circuit, though TR106 (JC105P) could be faulty. It might be that the track from pin 1 of the LOPT to the junction of R121/C312/R122 is broken – this will remove the feedback pulses to IC001. Another possibility is that R371 (1 Ω fusible) in the scan current path is opencircuit - this is a side-effect of no EW correction. The line drive could be low or of the wrong frequency because the earth for the module that houses IC001 is broken: this usually occurred with the early Clarivox PCB.

Some causes of no raster because of loss of line drive are: R174 (see above) opencircuit, the DC restorer diode D123 shortcircuit or connected the wrong way round, and the IC001 module earths open-circuit.

Line collapse with possibly arcing or a squealing noise occurs when L116 in the line scan current path shorts to D121.





Replace D121 (BA157) and C140 (10μ F, 250V) – these two components form the rectifier circuit for the 200V RGB HT supply.

Here are some other possible line scan faults:

Excessive width: D117 (BY299) in the EW modulator open-circuit or low EHT because the tuning capacitor C134 ($1\cdot 2nF$, $1\cdot 6kV$) is faulty. See also the EW modulator section.

Non-linear scanning: If the temperature of TR128 is OK, the linearity coil L104 is fitted the wrong way round. If TR128 is getting hot (it may be destroyed) TR105 (BC337) is open-circuit.

Picture breathing: The symptoms are width variation with beam-current changes, also non-linear line scanning. Check C132 (27nF, 400V) in the EW diode modulator. It's likely to be opencircuit.

Picture disturbances: For striations/line ringing check the line linearity coil damping resistor R135 (1k Ω , 1W fusible), C610 (10nF) on the CRT base panel, and the damping network on the Nokia deflection yoke. Any of these items could be open-circuit. For ragged/wavy verticals refer to the jungle chip (IC001) section. Picture disturbances of these sorts can be caused by the earth link LK174, which is adjacent to C130, when it's high-resistance or dry-jointed.

EW modulator

The EW diode modulator is in the line output stage: various faults have been referred to in the section above. It's driven by the TDA8145 chip IC107. Note that the width control affects the parabolic waveform to some extent. Here's a summary of some possible EW fault conditions.

Excessive width: If the controls have no effect, check the supply (about 27V) at pin 6 of IC107. If this is missing the fusible resistor R154 (27 Ω) could be open-circuit. If there's no voltage at pin 7, check whether C160 (22nF) is short-circuit or R153 (220k Ω) is open-circuit. There should be about 7.5V at pin 8: check C159 (3.3nF) if this voltage is low. IC107 could be faulty. If R368 (2.2 Ω fusible) is open-circuit there will be no EW modulator drive.

If the width control works but not fully, check whether the fusible resistor R371 (1 Ω) is open-circuit. In this situation TR128 overheats and fails. If there is no control and R371 is open-circuit check D117 (BY299) which is probably shortcircuit.

Underscanning: If there's no foldover and the controls have some effect, check whether D109 (1N4148) is short-circuit. There will be excessive voltage at pin 8 of IC107. If there's foldover and no effect from the controls, R181 ($10k\Omega$) or D116 (BY228) could be open-circuit. In the latter case R154 and IC107 could fail.

Bottom half bowing: If the bottom half of the raster is bowed out, the top half is OK and the controls work partially, IC107 is faulty.

Controls have partial effect, with ringing on verticals: C134 (1.2nF, 1.6kV) in the line output stage is faulty.

Pincushion control acts as a width control with the width control working normally: Check that there's a field ramp waveform at pin 1 of IC107. If missing, the link from PL102 or the track is opencircuit.

The jungle module

The TDA4504B IF/timebase generator (jungle) chip IC001 is mounted on a separate subpanel, which also houses the TDA2545A sound IF chip IC002. So various IF and timebase faults can have their origin here. The following is a summary of various faults l've encountered.

It might be thought that a picture shifted 10cm to the left has its cause in this area. In fact the component that causes the fault is D734 (1N4148) in the RGB shift circuit on the text panel: it produces this symptom when it goes short-circuit.

Ragged verticals: Can be caused by a poor soldered connection to the jungle module. R022 $(3.3k\Omega)$ or C017 $(2.2\mu F)$ could be open-circuit. These two components are connected to pin 27 of IC001 and act as the APC filter in the line timebase generator circuit.

Top pulling with video playback: Change R022 to $1.5k\Omega$, R023 to $82k\Omega$, C017 to 4.7μ F and C021 to 68nF.

Line frequency drift: Check whether C022 (2.7nF) is leaky

No horizontal shift: R016 ($36k\Omega$), which is connected to pin 31 of IC001, is opencircuit. This removes the feed from the horizontal shift control RV003. There is also an anti-breathing feed to this pin.

Field roll/picture cogging: $C009 (10\mu F)$ is open-circuit. This affects the AGC action.

Field roll: With signals from a local relay station, or TV games, increase the value of R013 from $1k\Omega$ to $1.5k\Omega$. There could be a weak input to the sync separator (IC001 pin 28) from IC110 in the teletext circuit because R211 ($1.2k\Omega$) has gone high in value.

Field cramping: The exact symptom is bottom half OK, top half severely cramped but with no foldover. Check R018 ($15k\Omega$) and R019 ($43k\Omega$) which can go high in value. R019 can rise to about $80k\Omega$. The junction of these resistors is connected to pin 5 (field feedback) of IC001.

Height jitter: Check R027 $(1.3M\Omega)$ and C013 (220nF) in the field ramp circuit connected to pin 3 of IC001.

Patterning on video: C012 (2·2nF) is open-circuit. It decouples the field feedback at pin 5 of IC001. The symptom appears as instability.

Weak picture: This symptom occurs when R010 $(2 \cdot 2k\Omega)$ is open-circuit.

Video muted by IC117: IC001 is faulty. IC117 is the microcontroller chip. It receives an ident input from IC001 (pin 14) at pin 29.

No picture, no OSD, raster if first anode voltage increased: This occurred with early (Clarivox) chassis when the earth



connections to the jungle module were poor. These connections are rather fragile with a single-sided PCB. Repair using tinned-copper wire to strengthen the joints.

Negative picture: If there is excessive video (2V p-p) at pin 6 of the module, the preset contrast control RV004 $(1k\Omega)$ is high in value or open-circuit. If the video level is OK, check whether link LK107 on the main panel is open-circuit.

Field timebase

The field generator circuit is in IC001 on the jungle subpanel. Its field drive output at pin 4 is fed to pins 1 and 2 of the TDA3654 field output chip IC106 on the main board. There is feedback between the two ICs. See relevant fault notes above.

Field collapse: IC106's supply pin 9 is fed with 28V via fusible resistor R140 (1 Ω), which may be open-circuit. If so IC106 could be short-circuit. Check the components in the field scan current path: R147 (0·33 Ω), C146 (3,300 μ F) and R141 (0·68 Ω). Field collapse can be caused by a short-circuit in IC107 (TDA8145) – the field output at pin 5 of IC106 is fed to pin 2 of IC107. This can cause failure of IC106. If so, replace IC106 but disconnect the link to IC107. If the field scanning is OK, IC107 is faulty.

Near full field collapse: Check the 33V zener diode D124.

Line pairing at top of screen: Instability caused by R148 (0.5W), which is connected in parallel with the field scan coils, being open-circuit. It's value depends on CRT type, 120Ω with a Nokia tube, 390Ω with a Philips tube or 220Ω with a Videocolour tube.

CRT base panel

IC601 (TEA5101A) on the CRT base panel contains the RGB output stages. It also incorporates auto grey-scale circuitry. Preset resistors are, unusually, added to balance the RGB drives, which come from the TDA8391 chip IC111 on the main board. It is important that the correct series heater resistor (R614) is fitted should the CRT be replaced. The value of R614 is 3.9Ω with a Nokia or Philips tube, 1.6Ω with a Videocolour tube. R614 is fusible.

Fault conditions associated with this panel are as follows.

Uncontrollable brightness: There is no HT supply to IC601. Check the fusible resistors R625 (100Ω) and R137 (10Ω) – the latter is on the main board. Another possibility is D121 (BA157) which is also on the main board.

No raster: The 12V supply at pin 2 of IC601 is missing. Check fusible resistor R612 (10Ω). This assumes that the tube's supplies are present, in which case a raster will appear when the setting of the first anode control is advanced.

One primary colour missing: IC601 could be faulty. The cause could be the relevant feedback resistor being opencircuit – this upsets the dark-current signal and cuts off the drive. The feedback resistors are R604 (blue), R605 (red) and R617 (green). They are $47k\Omega$, IW.

Coloured tint – any primary colour: IC601 is faulty.

Coloured flashing lines: IC601 is faulty.

Washed out pictures/slow to warm up: This is usually after the tube has been replaced or in an early production set, where the value of R614 is incorrect (see above).

Striations: Check C610 (10nF) which decouples the tube's first anode supply.

Next month

In part 2 we will cover faults that can arise in the audio circuitry, the signal processing and switching circuitry, the tuner, the microcontroller system, and the teletext section.



AUDIO FAULTS

Reports from Robin Beaumont Geoff Darby and Russell J. Fletcher

We welcome fault reports from readers – payment is made for each fault published. See page 746 for details of where and how to send reports.

Technics SLHD51E CD player

This player is part of a four-unit system, all linked together by ribbon cables. The customer's complaint was that after several hours the controls would lock up – neither the front-panel nor the remote-control buttons had any effect, but if the CD unit was unplugged the rest of the system worked normally. I tested the system for a week. As the fault didn't show up, the equipment was returned to the customer.

Shortly afterwards another identical system came in with the same symptoms, but this time permanent. I confirmed that disconnecting the CD player would solve the problem, also that the eject button on the player always worked, and that taking off the CD player's front control panel enabled the tuner and tape deck to work normally.

The CD player's front control panel uses a resistive-ladder arrangement. The switches short different resistors in the chain to chassis, the resistance change being detected by the control circuit. The control line should read open-circuit when no buttons are pressed, but my meter detected a resistance of a few $k\Omega$. Further investigation ceased when the fault disappeared!

I inspected the panel for liquid or other contamination, but found nothing. This meant that either one of the switches or the 1,000pF capacitor must have an intermittent leak. As these items are inexpensive, I replaced all nine switches and the capacitor. This provided a permanent cure.

The CD eject button is the switch that shorts the control line to chassis, so it was always detected correctly. **R.B.**

Sony TC-TX333 cassette deck

This was one of those increasingly rare faults that tests your ability to read a circuit diagram, understand it and reach a rapid and correct diagnosis. The front-panel keys FF, Rew, Rec, CD Sync and Eject did nothing, while all the other keys just turned the unit on and off. The first-mentioned set of keys are all connected to the microcontroller chip's key-0 line, while the others are connected to the key-1 line. The chip uses a clever technique to interpret the effect of so many keys linked via just two lines. Key-0 and key-1 are in fact inputs to DA converters in the chip. A network of resistors is connected around the key switches, and as a result different voltages appear on the key lines with different key presses. The chip compares these voltages with an internal look-up table to determine what's required.

In this case the key-0 line had only 0.5V on it with no keys pressed. As a result the

chip thought that the on/off key had been used when any key connected to this line was pressed and, because it looked as if a key was permanently in use, the key-1 line was locked out, rendering all the keys connected to this line inactive.

A new microcontroller chip got the unit working normally. **G.D.**

Sony CD turntables

Many Sony hi-fi models, for example those in the HCD-XBxx series, have a mainly metal CD turntable with a soft plastic coating on the disc-contact surface. Over a period of time this coating tends to pick up debris from discs. This can have two effects. First, if particles much larger than dust are picked up the disc may not sit flat, and thus wobble as it rotates. The result is poor 'playability' in general, with the symptoms generally worse on later tracks. Secondly, the grip between the turntable and the disc can be reduced significantly. You can hear the disc sort of skid to a halt after the TOC reading, rather than coming to the more normal controlled stop.

The cure is to clean the turntable with a cotton bud soaked in isopropyl alcohol. **G.D.**

Musical Fidelity A1, A100, A120 and MA60

We've had several of these class A hi-fi amplifiers in for attention recently. They have either failed or have come in for general service – usually because the function switch is noisy - and seem to be on the point of failure. The unreliable function switch is a Lorlin type with silverplated contacts. The other problems are associated with components that appear to be underrated. Look out for component and PCB discoloration. Replace faulty 400mW zener diodes with 1W devices. Faulty zener diode load and output stage bias resistors should also be suitably uprated. Some electrolytics fail because they are mounted close to hot-running components. Uprate any that have to be replaced. R.J.F.

Trio KT5550 tuner

The owner of this tuner said there was no output from the left channel. With no service information and very little else to go by for this elderly unit I decided to replace the LA3350 stereo decoder IC. Lucky guess! **R.J.F.**

Sony CDP-M20 and similar models

We get lots of these CD players in with the complaint that the tray opens immediately after the close instruction. The cause is no more complex than a faulty loading belt. **R.J.F.**

Servicing Audio and Hi-Fi Equipment

'Its readers will benefit from its wealth of easily assimilated information, and repairs hitherto thought impossible will speedily become routine. And the first may well cover its purchase price. Congratulations on a comprehensive, well-written and lucid work' *Electronics Informer*.

'Interesting, entertaining and useful for both practitioners and teachers. All round a satisfying book which deserves to be considered as a tool rather than an ornament collecting dust on the shelf.' *Skillset Newsletter*

Service engineers and technicians have come to regard this book as essential to their work. As a bench-side companion and guide it has no equal. Its purpose is to ease and speed up the processes of fault diagnosis, repair and testing of all classes of home audio equipment: receivers, amplifiers, recorders and playback machines. The mechanics and electronics of domestic audio are examined by Nick Beer in a down-to-earth and practical way, concentrating on what goes wrong, how to track down problems, and how to solve them.

A symptom index and comprehensive manufacturer and supplier guide allow quick access to specific advice and suggestions.

The third edition is bang up to date with the latest technology - DVD, CD Recordable, PC audio systems. There is also new material on PA equipment.

* Essential bench companion for all service engineers.

* New technology such as DVD and expanded material on MiniDisk will ensure another successful launch to this new edition



Nick Beer

Please supply the following title: **Servicing Audio and Hi-fi Equipment** Total_____ Name Address

Postcode

Telephone

Method of payment (please circle)

Mastercard/Visa/Cheque/PO Cheques should be made payable to Cumulus Business Media

Credit card no_

Card expiry date

Signed

Price includes delivery and packing

UK Price: £32.00 Europe £34.00 ROW £36.50

Return to Jackie Lowe, Cumulus Business Media Anne Boleyn House, 9-13 Ewell Road, Cheam, Surrey, SM3 8BZ



The joys of tench fishing. An early start then a mixed bag of TV faults – and a camcorder problem. Donald Bullock's servicing commentary

suppose I brought it on myself. There's no fishing like tench fishing, and I've sung its praises so often to Paul and Steven that they are now hooked on it. That's why I sometimes have to open and look after the shop on my own. At times it can be a bit much for one person.

Arrival

Three people were waiting outside when I arrived the other morning. I knew them all. There was Quiet Norman Glutton, who was sitting on a huge Ferguson TV set eating a pasty. The others were a regular oriental customer, Mr Bakwa Ng, and the domineering Mrs Runner with her son Clarence. If they hadn't all seen me drawing up I think I'd have fled past and hammered on the door of the Red Lion to ask for a large brandy.

"Hi Don" said Quiet Norman as I got out of the car. "Take the old girl's set in, will you? While I pop along to Crubbs Foodstore to see what they've got to eat. I'm famished."

The telephone rang as we entered the shop. "Joo do calls the same day" a voice said.

"We do our best" I replied, "where are you?"

"Baker's Way" the voice continued.

"Sorry" I said, "where's that?"

"First left at New Zealand, just past Australia" said the voice. There was frenzied laughter, then he hung up.

I looked at the phone, then hung up too. "Good morning, Donald, I am being glad to see you" said Mr Ng with a smile.

"There's a loose wire in my set. It's giving me only a line."

He presented me with a Goodmans Compact 110, and I wrote 'field collapse' on the card as he departed. I looked at Mrs Runner.

"Tell Mr Bullock about our telly,

Clarence" she ordered.

Clarence looked up and made to speak. "It's gone wonky, ain't it Clarence?" she cut in, "Tell Mr Bullock what was on 'im

when 'e went".

Clarence opened his mouth but wasn't quick enough.

"It was that fat woman, that Whimpey Opera, wasn't it, Clarence? Now tell Mr Bullock."

Clarence made another attempt.

"Cat's got 'is tongue I think" she continued. "it's our Bush, Mr Bullock. Dead. Now Clarence, shut up and get the set outa the car for Mr Bullock."

Norman's Fergie

As they left Quiet Norman returned, paring at a pie with his pen-knife.

"Ain't bad pies" he announced. "The Fergie belongs to my new girlfriend. Dopey and loaded, 'er is. I likes 'em that way."

"What's wrong with it?" I asked him, "Nuthin', 'er's all right" he replied. I leaned forward. "The set, Norman. the set "

"Aw. Silly picture."

I wrote 'silly picture' on a job card as he departed, still busy with his pie.

The set was a Ferguson D68N, which means the ICC9 chassis. When I got it on the bench and switched it on I found that the sides of the picture were bowed. I've had EW trouble before with these sets, and it didn't take me long to home in on the BD675 EW diode modulator driver transistor TL40. It was warm – and shortcircuit.

Starting the day with an easy repair is always cheering. I fitted a replacement transistor and switched on again. But what's this? Still a silly picture!

I applied a fingertip to the new transistor, which was warm. It was also short-circuit. What had blown it? My gaze settled on CL42 (4.7μ F, 160V), which generates the collector supply for TL40. When I removed and tested it I found it was dead short. Once a new capacitor and transistor had been installed there was a sensible picture.

No zoom

As I struggled to get the Fergie TV off the bench, ready for collection. the lovely Cassandra Grant came in with her Panasonic camcorder and W.D., her dim boyfriend.

"It won't zoom, Mr Bullock" she purred. "It was all right until W.D. used it, wasn't it, dear?"

"Huh?" said W.D.

"What did you do to it?" I asked, turning to W.D.

"Nuthin', I dunno, just nuthin'." The camcorder was a Panasonic NVG2. Its lens had zoomed in but was reluctant to zoom out. As Cassandra and her boyfriend had ambled off, I began dismantling the camcorder to get to its lens assembly. The zoom motor has an attached reduction gearbox, to give a slow and smooth zoom action. This had seized up, and I couldn't free it. SEME supply the motor and gearbox as a single unit, part no. VEM0408. I ordered one and put the camcorder aside.

Only a line

I decided to tackle Mr Ng's little set next. Field collapse, eh? When I tried the set the fault was nothing of the sort. It was line collapse. So I followed the line scan coil wires from the yoke and came to the coupling capacitor CH01 (4.7μ F). It was a bit of a gooey mess, and proved to be opencircuit when I removed and tested it.

I cleaned around the area and fitted a replacement. This did the trick, restoring the line scan action.

Then the phone rang. I answered it. "Is that the television shop?" an anxious voice asked. "Here, the top of your roof's ablaze. I've just driven past in my car."

I dropped the phone, ran out and looked up a the roof. No sign of any fire. I ran back in and picked up the phone. Frenzied laughter.

"Who's that?" I yelled, but the line was dead.

The last time I'd had some silly phone calls it had been Ribby Ellis, the self-styled practical joker. Was he back in town I wondered?

The dead Bush

Ah well, time to have a go at Mrs Runner's set. It was a Bush 2169, and was indeed dead. I took the back off and checked for DC voltages. Nothing. So I moved back to the chopper circuit. No voltage anywhere, not even AC.

I then saw that the mains fuse had died a violent death. The P3NA990 chopper transistor Q1 could well have been the cause, and a check showed that it was dead short. Did it just die or was there a cause? I peered about in the area and saw some pappy high-value resistors. I don't trust high-value resistors, so I unsoldered and checked the ones here. Sure enough, two had gone high in value. R5 had risen from $680k\Omega$ to $830k\Omega$, while R4, which should have been $270k\Omega$, was virtually open-circuit.

I replaced the P3NA990 and the two resistors, gritted my teeth and switched the set on. To my relief an excellent picture appeared.

Once I'd boxed the set up and got it on to the floor I peered out of the window. It was a gentle, sunny day. just right for tench fishing. I looked at my watch. Time the boys were back. Why should I be slaving here while they were lolling about the banks? Then their car drew up and in they came.

"Had a nice time?" asked Steven.

"Not one bit" I replied, "and I think I'm



going mental. I've had over thirty idiots in and four crazy telephone calls. How many tench did you get?"

"Didn't get one bite" came the reply.

A huge Sony

Just then Mr Macquater came in. He doesn't see straight. He looked at Paul with one eye and Steve with the other.

"Hello Don" he said, "it's a big 'un, I'm telling you."

"Never mind" I replied, "let's take a look at it."

Steven and Paul went out to his car and returned with a huge 29in. Sony set, Model KV29F1. It's fitted with the BE3D chassis.

"Picture's all right at first" said Macquater, "then goes like this." He pulled himself into an arc.

Steven took the set on. "It'll probably be dry-joints" he commented, looking around the line output section. He found some around the 2SC4793 EW modulator driver transistor Q801. Once they had been resoldered the set was OK.

Church Hall set

An enormous old car bounced to a stop outside. The rotund Reverend Goode eased himself out at one side while his curate, Deacon Blande, alighted from the other. They came in.

"Ah Donald" sang the Reverend, "I trust you are well. Now then, I have this massive television set in the boot. It's from the Church Hall. Been frightening the old folks it has. Ticking, or something, they say."

We all went outside to get the TV, which was a 29in. Daewoo GB2898ST (CP775 chassis). The reverend gentlemen then went on their way as we struggled to get the set in and on to the bench. "The Reverend Goode" he said. "Very upset. Seems his curate tried to phone us to see if they'd left their remote control unit. Got a wrong number and suffered terrible abuse. He fainted. Whoever would have done such a thing?

It was tripping. Paul took the back off and started to look around inside. A check on the 2SD1880 line output transistor Q401 revealed that it was short-circuit. So was the BY228 diode D403 in the EW modulator circuit. After replacing them, Paul switched the set on again. A picture came up, but there was severe EW distortion.

He decided that D403's demise could well have damaged the 2SB546 EW driver transistor Q403, and was right. He also checked the associated 6.8μ F, 50V bipolar electrolytic C302, which was also shortcircuit. But replacements failed to cure the fault.

Q403, a pnp transistor, had no voltage at its emitter. What else was there around here? A series resistor, R406 (4.7Ω , 0.5Wfusible). But where was it? After some searching it was discovered in a hideaway position, behind a heatsink close to C302. It was open-circuit, presumably the result of Q403's failure. Replacement of this item completed the repair. The set then produced a picture with normal scanning – and excellent quality.

A Roberts Radio

Our next visitor was old Stan, who was

carrying an ancient Roberts portable. Steven gave him a smile.

"This wireless o'mine's stopped working" he croaked. "I reckon there's someone in there."

"Shouldn't think so" Steven said, "but I'll take a look for you."

It was the battery of course. Once a replacement had been fitted the set sprang to life.

"Wonderful" said old Stan, "only I thought there was someone in there."

Confusion

Steven slipped next door for some cigarettes. Then the telephone rang. I answered it, expecting more jokery.

"Nyahhy wah, nyn wouh trol" said the earpiece. Just what I'd been waiting for. I'd give him a piece of my mind.

"Just get off the phone and stay off it" I said calmly. "A Godless oaf whose idea is to mess busy people about needs his mind seeing to. To hell with you, and that's final." Then I slammed the phone down and sauntered out the back to put the kettle on.

"I sure told him" I said to Paul. The phone rang again as Steven returned with his cigarettes. He answered it.

"Why, hello Reverend. What? Good gracious, how terrible. Yes, I agree, too awful. Yes, it is here. It was left on the counter. See you later, Reverend."

As he hung up he had a puzzled expression. "The Reverend Goode" he said. "Very upset. Seems his curate tried to phone us to see if they'd left their remote control unit. Got a wrong number and suffered terrible abuse. He fainted. Whoever would have done such a thing? And I wonder what he said."





player servicing

In this second part of his new series K.F. Ibrahim starts an account of how DVD players work. The basic block diagram description is followed by an investigation of the laser unit then the derivation of error signals and the operation of the servo system ast month's instalment dealt with the characteristics of DVD discs and the way in which the recorded video and audio signals are first digitised, encoded and then stored on the disc as channel data. This time we'll concentrate on how a DVD player functions.

Basic player block diagram

A simplified, basic DVD player block diagram is shown in Fig. 9. The optical unit (OPU) generates the laser beam that scans the disc, and also detects the reflected beam, thus reading the data pattern (pits and lands) recorded on the disc. Its output consists of a varying RF signal, which is produced by the pits and lands, and error signals for servo control (focusing and tracking). The next block amplifies the RF signal to a level suitable for feeding to the RF processor, and processes the error signals which are passed to the servo control section.

The functions of the RF processor are as follows: RF signal conditioning; clock signal extraction; 16/8 demodulation (EFM+); frame/sector sync detection; and error correction. Its output is the programme data stream, which consists of the video, audio and other PES data, and a disc speed control signal. The associated DRAM stores recorded data sectors as they arrive, enabling the processor to rearrange them as the original blocks for error correction. Demultiplexing separates the video and audio PES data for feeding to the A/V decoder block. This operates with a DRAM that stores picture information so that inter-frame decoding can be carried out, and also serves as a one-second audio delay for lip sync.

The function of the video buffer is to store video frames to ensure a seamless video display when the OPU is re-reading or searching for a disc sector. This is followed by an NTSC/PAL encoder which incorporates a digital-to-analogue decoder. It produces an NTSC or PAL encoded output suitable for feeding to the TV monitor in use.

How these blocks are integrated in IC form depends on the chip set used. There has already been some increased integration to reduce the chip count. Philips for example has introduced a system-on-chip (SoC) IC that integrates the functions of system control and AV decoding, while Sanyo has developed a chip that integrates the functions of RF processing, demultiplexing and AV decoding.

Note that the RF signal produced by the OPU is an analogue signal that has to be converted to digital form by the RF processor. It's an irregular waveform that can be properly observed only by using a digital storage oscilloscope. If an analogue oscilloscope is used, a pattern known as the eye – because of its shape – can be observed. The minimum analogue oscilloscope bandwidth for this purpose is 40MHz (20MHz for CD playback use). The amplitude of the eye pattern represents the laser strength and is specified by the manufacturer.



The OPU

This is probably the most critical part of a DVD player. It generates the laser beam, reads the recorded data which is fed out as an RF signal, and produces outputs to ensure that the beam is focused and tracks correctly.

The OPU is mounted on an arm that positions it physically with respect to the disc, moving the unit in and out to follow the spiral track or read different sectors of the track. The OPU must be able to read SL and DL DVD discs and also conventional audio CDs. This means that it must be able to generate laser beams at different wavelengths, 650 or 635nm (red laser) for DVDs and 780nm (blue laser) for CDs. It must also be able to focus at different depths (to cater for dual-layer discs). This can be achieved in three different ways: by using a single-lens holographic arrangement, with an aspherical lens to focus at different depths; by using a twin-lens arrangement with two different lenses; or by using a twin-laser arrangement which has two separate laser and lens assemblies.

Fig. 10 shows the main components of a laser optical pickup unit. The laser beam is generated by a low-power aluminium-gallium-arsenic (AlGaAe) semiconductor diode. The collimator lens adjusts the beam so that it follows a parallel path on its way to the optical grating lens, which bends the laser beam so that there are then two beams, a main beam for reading the data stream and a side beam for tracking purposes. This is followed by the beam splitter. Before it reaches the disc, the beam is focused by the objective lens.

The laser beam penetrates the disc surface and is reflected back towards the objective lens by the record layer. Provided the beam is precisely focused, the reflected beam returns along the same path as the incident beam, towards the beam splitter. This turns the reflected beam through 90° , directing it towards the photodiode detector assembly via the detector lens.

Focal depth and numerical aperture

Since the track pitch is only $0.74\mu m$ with a DVD and the minimum pit length is only $0.4\mu m$ (see Table 4 for a comparison with CD track characteristics), the size of the spot that reaches the disc's information layer has to be very small – so that it can distinguish the pits and avoid reading adjacent tracks. For DVD reading the laser spot diameter is set at $0.54\mu m$ (the figure for a CD is $0.87\mu m$).



Fig. 10: The main components of a laser optical pickup unit.

Spot diameter is directly proportional to the wavelength of the laser beam and inversely proportional to the numerical aperture (NA) of the objective lens. Mathematically, this is expressed as W =

Table 4: Comparison between CD and DVD parameters.

Parameter	CD	DVD	
Track pitch Min. pit length	1.6µm 0.84µm	0·74μm SL 0·40μm DL 0·44μm	
Linear velocity Channel bit rate Objective lens Numerical aperture Wavelength Spot diameter	1·21m/s 4·3218Mbits/s plastic 0·45 0·78µm (red) 0·87µm	3.49m/s 26.16Mbits/s glass 0.6 0.65µm (blue) 0.54µm	



(b)

(c)

 $k/(2 \times NA)$, where W is the spot diameter and k is the wavelength. The numerical aperture works out at 0.6 (compared with 0.45 with a CD).

The effect of this larger NA is to reduce the focal depth, which in turn means that the readout is more sensitive to disc thickness and other irregularities. The first problem is overcome by making the thickness of the disc substrate 0.6mm, the latter by increasing the disc's stiffness through gluing two substrates together (see Fig. 1 last month). The optical head is still sensitive to disc warping however - this tilts the disc. As the optical head moves across the disc during playback a changing tilt angle produces what's known as a skew error, which affects the reading of the data. For this reason a tilt or skew sensor is mounted on the surface of the optical unit. It produces a skew error signal, which is used to ensure that the optical head moves in parallel with the surface of the disc.

The photodiode detector assembly

An array of four photodiodes is used to detect the strength of the reflected beam. Fig. 11 shows the arrangement: the outputs from the photodiodes (A, B, C and D) are added together to provide the RF output signal. Since the pits and land reflect the beam at a different strength, the output represents the recorded ones and zeros.

Obtaining a focus error signal

When the laser beam is correctly focused its reflection forms a circular pattern at the centre of the four photodiodes, as shown at (a) in Fig. 12. To obtain a focus-error signal (FE) for servo control, the photodiode outputs are also fed to the inverting and non-inverting inputs of an operational amplifier. With correct focusing A + C = B + D and the output from the op-amp is zero, as shown at (a). If the beam is incorrectly focused it takes on an elliptical shape at the diodes, as shown at (b) and (c).

When the distance between the OPU and the disc is too great, output A + C is greater than output B + D. As a result a positive-going output signal is obtained from the operational amplifier, see Fig. 12 (b). The opposite situation, when the OPU and the disc are too close, produces a negative-going output from the op-amp as shown at (c).

Tracking error signal

In addition to the main beam, which is used to generate the RF and FE signals, the grating lens produces two side beams. After reflection these are directed to two separate photodiodes, E and F, at the

(a)

sides of the main photodiode block, see Fig. 13 (a). When the tracking is correct, as shown at (b), the outputs from photodiodes E and F are equal. They are fed to the inputs of an op-amp which thus produces zero output. If there's mistracking, i.e. the main beam is slightly to the right or left of track centre, the output from E will greater than F or vice versa. As a result the tracking op-amp will produce an output (E - F = TE) which is either positive- or negativegoing depending on whether the mistracking is to the right or left. This is illustrated at (c).

The two-axis tracking and focus actuator

The objective lens is mounted between two separate coils (focus and tracking) which are at right-angles to each other and are within the magnetic field produced by a permanent magnet, see Fig. 14. This assembly can move the lens in the horizontal and vertical directions to provide tracking and focusing correction respectively.

Current through the tracking coil A moves the lens horizontally while current through the focus coil B moves the lens vertically.

Because of the smaller pit size and closer tracks, the two-axis actuator used with DVDs is smaller than that used with CDs.

Servo control

Fig. 15 shows the basics of a DVD player servo control system in block diagram form. The RF amplifier receives the OPU's RF output signal, which it passes to the RF processor via a low-pass filter. It also receives separate signals from the various photodiodes, including skew sensor diodes G and H. These are processed to produce four error signals: focus error (FE), tracking error (TE), pull-in (PI) and tilt (or skew) error.

The servo DSP (digital signal processor) receives these signals and also a spindle control signal from the RF processor. This spindle control signal depends on the data flow rate and thus the speed of the disc. The outputs from the DSP are fed to drivers which, in turn, control the relevant actuators and motors. The servo DSP is fully programmed and controlled by the syscon microprocessor chip.

Start up

When the tray is closed or when play is selected a servo start-up routine is initiated. It carries out the following operations: disc diameter identification; disc type identification (DVD or CD and SL or DL for DVDs); and auto adjustments. The following action will thus be observed: the spindle motor rotates the disc at a relatively high speed; the sled motor moves the OPU across the disc, from the centre to the circumference and back again, to determine its diameter; the two-axis actuator moves the objective lens up an down, a process known as focus search; simultaneously the objective lens is moved sideways to establish accurate tracking.

If the tracking error voltage is low, i.e. 0.4V or less, the inserted disc is a DVD. A CD, with its wider track pitch, will produce a higher TE voltage of around



Fig. 14: Operating principle of a twoaxis tracking and focus actuator.



Fig. 15: Block diagram of a DVD servo-control system.

2V. This distinction provides CD/DVD detection

The difference between a single- and a dual-layer DVD is indicated by the intensity of the reflected beam. The pullin (PI) signal supplies this information. It's obtained during the focus search process. A high PI signal of about 1V indicates that the data layer is highly reflective, i.e. it's a single-layer disc. A low PI of about 0.5V means that the disc is of the dual-layer type.

Tracking control

Accurate tracking is ensured by the twoaxis device's horizontal actuator for small adjustments and the sled motor for larger adjustments. The sled motor keeps the OPU moving along the spiral track and, where necessary, introduces a jump when a different sector of the track is to be read.

The sled error (SE) is calculated within the servo DSP, which monitors the tracking error (TE) signal. The lowfrequency component of the TE signal, the result of the gradual spiralling of the track towards the outer circumference of the disc, is used to control the sled motor. The high-frequency component, caused by the jerky track itself, is used to control the tracking actuator.

Tilt/skew control

The skew sensor uses two photodiodes (G and H). one at each side of the disc, to detect disk tilt or skew. If the disc is not parallel with the OPU, the reflected light at each photodiode will be unequal. The tilt motor is then activated to make a correction. This correction is made once only, at the beginning of disc playback.

Next month

Next month's instalment will complete our examination of the DVD player. Subjects covered will include system control, the user interface, the AV decoder and DVD audio processing.

K.F. Ibrahim is Senior Lecturer at the College of North West London and is author of several books, including *Digital Television* and *Television Receivers*.



Terrestrial DX and satellite TV reception reports. News on broadcast TV and satellite band changes. International DTT update. Aerials for Band I reception. Roger Bunney reports

DX and Satellite Reception

Terrestrial DX-TV reception varied a lot during July. Early in the month things were really humming then, towards the middle of July, Sporadic E propagation died away. Finally there was a lift at the end of the month, with a welcome flourish across Bands I and II.

Dramatic VHF action in the radio amateur bands has been reported. First there were transatlantic 50MHz (6 metre) multiple-hop SpE openings on May 25th and 31st, with communications between the UK and both the US and Canada. Unusually, both openings occurred during day-time hours, from approximately 1200-1600. And on May 26th there was, during the evening to about midnight, two-way tropospheric communication at 144MHz (2 metres) between the UK and the Canary Is, a distance of some 3,000km.

During a multiple-hop SpE opening a few days earlier, on May 18th, there was two-way amateur radio communication between the UK and stations in Jordan, Israel and Egypt. Amateur callsign VQ9IO was heard during this opening and several contacts have been confirmed between VQ9IO and amateur radio stations in the southern UK. Station VO9IO is on the Chagos Archipelago in the Indian Ocean, about 1,500km south west of Sri Lanka. This is an amazing distance, about twice that of the main UK-Jordan/Egypt propagation skip. My thanks to the RSGB bulletin Radcom for this information.



Shot from an outside broadcast report on talks at Smithsburg, Maryland, relayed via the NSS K Reuters Atlantic lease.

My own experiences of transatlantic SpE TV reception have always occurred between about 1900 through to late evening, as the MUF has risen to ch. A5 (77.25MHz video), with many cochannel signals present on the lower channels and less interference on the higher ones. N. American SpE TV can occur between late July and mid-August. A good indication is to check for ch E3 reception from RUV (Iceland) first.

Here's the collated SpE TV log for July:

- 2/7/01 TVE (Spain) chs. E2-4; RAI (Italy) chs. IA, B; TVA (Italy) ch. E3-; TeleA (Italy) ch. E2-; Canal + (France) ch. L3; RTL Klub (Hungary) ch. R2; RTP (Portugal) ch. E3.
- 3/7/01 RAI IA, B; RTP E3, 4; TVE E2-4; RTL R2; TVA E3-; TeleA E2-; ORT (Russia) R2.
- 4/7/01 RAI IA, B; TVA E3-; TeleA E2-; TVE E3; RTP E3; ORT R1, 2; NRK (Norway) E2-4; SVT (Sweden) E2, 3; TVR (Romania) R3; ETV (Estonia) R2
- 5/7/01
- RTL R2; RAI IA; TVA E3-; TVE E2; RTP E3. NRK E3, 4; LTV(Latvia) R2; RTL R2; RTP E3;TVE E2-6/7/01 4; RAI IA; TVA E3-; HRT (Croatia)E4.
- 7/7/01 TVE E2, 4; C+ L4; RAI IA; RTP E3.
- 9/7/01 TVE E3.
- 10/7/01 TVE E2; RTP E2-4 (see note below).
- 11/7/01 RTL R2; TVE E2, 3; RTP E3; RAI IA, B; TVA E3-; C+ L3
- 12/7/01 NRK E4; RAI IA; RTL R2.
- 14/7/01 RAI IA
- 17/7/01 TVA E3-; RAI IA.
- 19/7/01 TVE E3.
- 21/7/01 RTP E3; SVT E2.
- 22/7/01 RAI IA; RTL R2; LRT (Latvia) R2; UT (Ukraine) R2.
- 26/7/01 NRK E3; SVT E2.
- 28/7/01 LRT R2; NRK E2, 3,

29/7/01 RAI IA, B; TVA E3-; TeleA E2-; TVE E2-4; RTP E3; RTL R2; TVR R2.

30/7/01 RAI IA, B; TeleA E2-; TVA E3-; C+ L3, 4; TVE E2.

RTP ch. E4 received on the 10th by Peter Schubert, Rainham is either a mainland 50W relay or a 180W transmitter in the Azores.

The 2001 Sporadic E season was reasonably active though short-lived. Propagation was mainly on a north-south axis, bringing Scandinavian and Iberian signals to the UK. The Italian shopping channels TVA (53MHz video) and TeleA (47.9MHz video) were received quite often: reception of the main RAI transmitters was less frequent - strange.

Satellite sightings

Though most satellite TV signals are now digital, analogue ones are still present. They are confined to main-line programming, and are often duplicated in digital form somewhere. The Albanian TVSH channel continues to provide a strong analogue PAL signal across the UK. It comes up during the evenings via Eutelsat II F3 at 21.5°E. Check at 11.556GHz horizontal – the audio is at 6.5MHz. On July 18th the channel carried live OB football from 1900 hours.

At the same time, just up the tuning scale, horse-racing was being uplinked by SISLink. This was a digital feed at 11.686GHz H (SR 5,632, FEC 3/4), with the identification "8MHz basic". Afternoon and evening horse racing can often be seen at the top end of II F3's Ku-band coverage. Various sports events are at present being carried. Late on Sunday morning, the 22nd, a locked-off shot appeared via SISO2 UKI-27. It appeared to be an almost deserted circular running track and was interspersed with colour bars. This was at 11.663GHz H (SR 5,632, FEC 3/4).

July 22nd was during the course of the G8 summit talks at Genoa, with the attendant demonstrations. That morning Jonathon Hunt of Sky News transmitted a live report from Italy, using 'SIS26 coder 1 UKI-257 Genoa Sky News'. This was at 11.041GHz H (5,632 + 3/4). Unlike other uplinkers, SISLink tends to use different frequencies. For example the SISLink-13 UKI-147 truck that covered the riots in Bradford on the 9th for Sky News used 11.692GHz H. On the 26th it covered premier Blair leaving a field in Cumbria via helicopter, this time at 11.047GHz H.

Eutelsat II F3 resembles a busy railway station, with activity constantly changing over the course of a day. If I scan down from 11.750GHz at say 1700 hours it will be worth doing a second scan twenty minutes later. Various transmissions pop up, do their bit, then cut and run.

The Americans took a great interest in the Tour de France this year, with a daily edited report of the day's cycling for the US networks. This was carried by Channel 1 in the Globecast multiplex at 11.590GHz V (SR 20,145, FEC 3/4) via NSS K (21.5°W). On the 24th a teleport Stateside switching error occurred. The Outdoor Life Network caption appeared inlaid over colour bars via the Reuters 11.462GHz V lease. The transmission was suddenly cut, reappearing a few minutes later within the Globecast channel package at 11.590GHz V. The transmission originated from Stamford, CT.

The Digichat web site (see satellite news) had said that the Tamil TV Network is carried in the clear via Hot Bird (13°E). Following the Tamil Tigers raid on the Sri Lankan airport on July 24th I checked at 12·245GHz H (SR 27,000, FEC 3/4) and found about eight channels, including the Tamil TV Network (TTN), but unfortunately encryption had arrived. A mass of international programming is now available at 13°E.

A couple of reports have drawn attention to the fact that the BBC is using Telecom 2A (8°W) and Telecom 2B/D (5°W) for regional feeds. Edmund Spicer (Littlehampton) and Roy Carman (Dorking) have both found that BBC OBs are active between 11.569GHz V and 11.690GHz H. Edmond noted that UKI-16 was using an SR of 6,111, while Roy saw another UKI-16 feed that used the more common 5,632 SR. A few BBC uplink trucks now use an SR of 4,898 and FEC 7/8. One of the feeds to London was encrypted.

Roy found an Italian channel, Tell you your fortune, via Telecom 2A at 12.702GHz V, with SR 2,500 and FEC 2/3. He describes it as doubly appalling. The male presenter defies description, and the OB is rebroadcasting an analogue feed with heavy hum on both the video and audio.

Several sat-zappers noted test transmissions in mid-July from the newly launched Astra 2C, then at 32.5°E. This was prior to its move to 19.2°E to provide back-up for the ancient Astra 1A.

Following a couple of reports in *TeleSatellite* magazine I have, over the past few weeks, been intermittently checking the 245-270MHz band for reception of Asian and American studio-to-



Shot from an ORT (Russia) PTP channel programme.

transmitter links (STLs) that use the 300MHz band (i.e. 50MHz higher). The 300MHz signals travel out into space and are received by US military satellites which provide 50MHz down-conversion and 'inadvertent downlinking'. It's these downlinks that provide reception of the STL signals. Basic equipment and a scanner does work – signals are present. More on this next time!



Broadcast news

Isle of Man: A local station, Manx TV, is to open in early 2003, based in Douglas. It will provide local entertainment, news and sport. As part of the *Your TV* local TV group it will operate around the clock, like the Isle of Wight RSL station TV 12. At



Crossed wideband Band I dipoles with, above, a discone aerial, chimney-mounted at Roger's home.



Roger has been experimenting with this double-discone wideband aerial, Model DD1300, which is mounted on a temporary mast in the garden.

present Manx TV is establishing a channel in conjunction with NTL.

All UK-TV RSL details, both on-air stations and planned allocations, are listed at

http://www.itc.org.uk/divisions/eng-div/trans/r-s-l.htm New Zealand: A Maori-language TV channel is being considered as part of the TV4 network. About a million households can at present receive the commercial terrestrial TV service TV4, out of a total household count of 1.2m.

China: The Beijing-based CCTV national TV service has opened two new channels, CCTV-10 which is broadly educational and CCTV-11 which provides classical music, dance and opera. These analogue channels will be available in the Beijing area initially then extended to other population centres.

International DTT update

RTE (Ireland) is to open four DTT channels by the end of 2003: a 24-hour news channel should be on air by the end of 2002. The first Portuguese DTT services should already be on air, run by the Plataforma de Televisao group. They will include the RTP and SIC networks. The Czech Republic intends to open DTT services in late spring 2003, aiming for 90 per cent coverage within three years and an analogue switch-off in 2012: public service broadcaster CST and the commercial channels Prima and Nova are guaranteed coverage. Sweden is encouraging rapid take-up of DTT by the public, with a proposed analogue switch off in 2003, though this short timetable is thought to be impractical. There's already a rapid expansion of DTT programming and more services are signing up for the available multiplexes.

Australian DTT is expanding, with services in Darwin, regional Queensland, Victoria and Tasmania due to be in operation by March 2003. All main areas are to have dual analogue and digital services by early 2004.

DTT is to start in the three main Japanese cities by the end of the year, with nationwide coverage expected by 2006 and an analogue switch-off in July 2011. Vietnam has just started DVB-T test transmissions, using the COFDM modulation technique.

Aerials for Band I reception

The Band I aerial system I've been using recently is quite modest compared with previous years, consisting of two horizontal wideband dipoles mounted at 90° to give either north-south or east-west reception. An external Nevada Communications VHF relay unit is used to select the output from one dipole or the other, feeding it to a single downlead. On the same mast, though not too clearly visible in the accompanying photograph, there's a D160 wideband discone aerial. It's a standard discone with an inductively-loaded vertical whip to enhance low-VHF performance. A discone provides wideband coverage with low gain. Out of interest, I used the discone aerial one torrid evening to check a TeleA signal. Remarkably, reception was stronger with the discone aerial than with either of the wideband dipoles. The results I obtained during several SpE openings encouraged me to experiment further.

Nevada Communications also supplies a double-discone aerial, Model DD1300, which has a second, upper array of longer cone elements. This suggested improved VHF performance and, as the offer price was very reasonable at just under £40, I decided to buy one. I mounted it at about 14ft (aerial centre) on a temporary mast in the garden. In this position there's clear signal pick-up from the south but the aerial is otherwise screened by nearby buildings. This situation provides an unfair and demanding test for comparison with reception via the Band I dipoles, which are at 30ft and clear to the horizon all round. The output from the DD1300 is taken indoors via a coaxial tieline (CT125), with a switcher for selection of the output from either the DD1300 or one of the dipoles.

The results I've obtained with the DD1300 are startling. In many cases the DD1300's signal output is far higher than that from either of the wideband dipoles. A TeleA signal often provides a visible picture when no signal is apparent from the dipoles. The situation is similar with TVE signals from Spain. The improvement is greatest with shorter-skip signals, which suffer from polarisation shift. It seems that a horizontallypolarised (when transmitted) signal twists along the propagation path to become vertically polarised. With longer-skip signals, say 800 miles plus, the tendency is for the original horizontal polarisation to be retained. Certainly a long-hop horizontallypolarised signal remains in the same plane at the reception site.

I anticipate that reception via the vertically-polarised DD1300 aerial would be improved by raising it to a similar height to the Band I dipoles, thus clearing obstructions.

Incidentally the temporary mast on which the DD1300 aerial is mounted consists of a modified Hills rotary washing line, upside down, with a 6ft by lin. standard alloy mast sleeved and inserted inside to increase the height.

Satellite news

There are problems with Gorizont 31 at 40.5°E. As a result some Russian analogue TV services are not at present available in western Russia and eastern Europe. Cable systems that have previously taken the services are now using other downlinks, such as Express 2A (80°E) and Gorizont 26 (11°W). The difficulty with this is incorrect time zoning.

The EBU has leased capacity until the end of 2002 aboard PAS-9 over the North Atlantic for the carriage of sporting events. Both the 2002 Winter Olympics at Salt Lake City and the Edmonton World Athletics Championships have been booked and there are options on other sports action.

There are rumours that London may be used as the base for production facilities by another Iraqi opposition group operating a satellite channel. The group hopes to be transmitting programmes to the Middle East during the autumn, using a Lockheed Martin satellite.

A remarkable-looking satellite, Thuraya, is now in operation at 44°E with coverage of Europe, the Middle East, Africa and Central Asia. It provides voice, fax, data and GPC connection via a handmobile that's similar to the standard mobile GSM phone but costs \$US995, with calls at 55c a minute. Subscribers can "roam" the area covered, accessing fixed and mobile units in the L band. The transmit/receive aerial includes a 40 x 52ft mesh "saucer". For further information and pictures, refer to

http://www.hsc.com/factsheets/geomobile/thuraya/thuraya.html – or just THURAYA.

Eutelsat is now operating as a limited reliability company called Eutelsat S.A., based in Paris. The change should mean greater commercial freedom to develop new products and services and "greater flexibility for striking strategic alliances and joint ventures".

There's a new digital satellite web site, in English, with news on latest channel changes, technical information, letters etc. It's called Digichat, and I found it while scrolling down for RSD Communications. The internet address is

http://homel.stofanet.dk/kjoge/index1.html

If anyone requires a new, cheap analogue satellite system for 13 or 19.2°E, check with the grocery chain Lidl. In late July the company had on offer an 80cm dish with LNB, 20m of coaxial cable, plugs and a receiver with 999 memory locations, three scart sockets and DiSEqC 1.0 for £39.99, with installation instructions. It's badged Welltech. A wall bracket set was available at £1.99. The receiver's IF tunes across 900-2,150MHz, with audio tuning over 5-9.5MHz.



WATCH SLIDES ON TV MAKE VIDEOS OF YOUR SLIDES DIGITISE YOUR SLIDES (using a video capture card)



"Liesgang diatv" automatic slide viewer with built in high quality colour TV camera. It has a composite video output to a phono plug (SCART & BNC adaptors are available). They are in very good condition with few signs of use. For further details see www.diatv.co.uk .£91.91+ val = £108.00

Board cameras all with 512x582 pixels 8.5mm 1/3 inch sensor and composite video out. All need to be housed in your own enclosure and have fragile exposed surface mount parts. They all require a power supply of between 10 and 12v DC 150mA.

47MIR size 60x36x27mm with 6 intra red LEDs (gives the same illumination as a small			
torch but is not visible to the human eye)£37.00 + vat = £43.48			
30MP size 32x32x14mm spy camera with a fixed focus pin hole lens for hiding behind a			
very small hole£35.00 + vat = £41.13			
40MC size 39x38x27mm camera for 'C' mount lens these give a much sharper image			
than with the smaller lenses			
Economy C mount lenses all fixed focus & fixed iris			
VSL1220F 12mm F1.6 12x15 degrees viewing angle£15.97 + vat = £18.76			
VSL4022F 4mm F1.22 63x47 degrees viewing angle£17.65 + vat = £20.74			
VSL6022F 6mm F1.22 42x32 degrees viewing angle£19.05 + vat = £22.38			
VSL8020F 8mm F1.22 32x24 degrees viewing angle£19.90 + vat = £23.38			
Better quality C Mount lenses			
VSL1614F 16mm F1.6 30x24 degrees viewing angle£26.43 + vat = £31.06			
VWL813M 8mm F1.3 with iris 56x42 degrees viewing angle£77.45 + vat = £91.00			
1206 surface mount resistors E12 values 10 ohm to 1M ohm 100 of 1 value £1.00 + vat			
1000 of 1 value £5.00 + vat			



Please add 1.66 + vat = £1.95 postage & packing per orde

JPG ELECTRONICS Shaws Row, Old Road, Chesterfield S40 2RB. Tel 01246 211202 Fax 01246 550959 Mastercard/VIsa/Switch Callers welcome 9:30 a.m. to 5:30 p.m. Monday to Saturday



Reports from Michael Dranfield Eric Oliver Graham Richards Gary Laidler Eugene Trundle Mike Leach and Roger Burchett

TV FAULT FINDING

We welcome fault reports from readers – payment for each fault is made shortly after publication. See page 746 for details of where and how to send reports.

Matsui 2092T

I have come across two different versions of this set. Although the model number is the same, they are fitted with different microcontroller chips and have different line output transformers. In addition a different remote-control unit is required. The grey Philips LOPT fitted in one version goes short-circuit between the primary winding and chassis. The black LOPT is more reliable, but this version suffers from dry-joints at the line driver transformer. As a result, the 2SD1555 line output transistor fails. Circuit protector SOC2000, which is next to the chopper transformer, sometimes goes open-circuit when the line output transistor dies. M.D.

Sharp 59CS03H

There were no teletext or on-screen displays. As the text and on-screen display signals come from the same chip, IC401 (SDA5273C26), I carried out scope checks here. The clock crystal was operating correctly at 20.48MHz, video entered the chip at pin 10, there were field and line sync pulse inputs at pins 4 and 5 respectively, and the power supplies were OK - 3V at pin 23 and 5V at pins 11, 12, 16, 21 and 25. There were blanking pulses at pin 64, but there was no RGB information at pins 61, 62 and 63. In view of this I decided that the chip must be faulty and ordered a replacement. Good job it cost only £7, because the fault was still present when it had been installed.

I then studied the electrical adjustment

manual and discovered that there are two NVM adjustments, one relating to the OSD contrast and the other the teletext contrast. But the problem was how to navigate through the service menu without an onscreen display – only a black box was present on the screen when a button was pressed. Fortunately the service manual lists the adjustments in the order in which they come up on the screen, so I was able to step through to the OSD contrast adjustment. Bingo, up came the OSD. I was now able to see the service screen. Moving on to the text contrast, I found that this was also set at zero.

New values couldn't be stored however. When I moved on to the next adjustment the text and OSD contrast settings were reset to zero. I was beginning to wish I'd changed the NVM in the first place. Then I noticed, in the electrical adjustment manual, that the OSD and text contrast are set by the user menu. Using the instruction book, I managed to scroll down to the text and OSD and turned them up. The personal settings could then be stored.

To complete the repair I cleaned around the anode cap, in case an EHT flashover had been responsible for the problem. An odd thing I discovered is that with the Megatext chip removed the set fires up then trips out with a two-second cycle. **M.D.**

Bush BTV170T

This 14in. TV/VCR combi unit had no TV sound, though there was sound when a tape was played. The customer also mentioned that teletext had stopped working some time back. I had to buy the service manual to reprogram the EEPROM. Don't buy the EEPROM, as it comes blank and you will still need the service manual.

The sound fault was cured by changing the data at address 0D to B3. For teletext, address 08 needs to be 44 and address 09 needs to be 61. For the **Tatung-badged** version of this set without teletext, address 08 needs to be 40 and 09 needs to be 60. Apart from this the other NVM data is the same. This information will help if you have the wrong manual for the job. **M.D.**

Samsung CI5373T

This set had a dead power supply. I found the cause in the snubber network, where C803 (2.2nF, 800V) was short-circuit. The two series-connected resistors R802 and R803 were open-circuit: both are 100Ω safety resistors, though my manual shows the value as 10Ω . Unfortunately IC801, HC801 and DZ801 had also been destroyed. **M.D.**

Tatung 190 Chassis

The picture was rippling when this set was switched on from cold. Checks on the power supply lines showed that everything was OK, but a scope connected to pin 26, line drive output, of the TDA4505 IF/timebase generator chip IC101 revealed all. The mark-space ratio of the drive waveform was wrong. The fault cleared as the set warmed up. A new TDA4505 chip restored normal operation. **M.D.**

Sharp 59CS03H

This set was dead. The cause, as so often, was failure of the TDA8375A IF/video processor/timebase generator chip IC201. There was a low resistance between pin 56, the line drive output, and chassis. A replacement brought the set back to life.

I mentioned this problem to an electronics engineer who designs recording studios. He came up with a novel solution. The output at pin 56 of the TDA8375A is open-collector, with two Schottky protection diodes, one connected to the internal supply rail (cathode to the rail) and the other to the internal earth (anode to earth). As a Schottky diode has an 0.5V forward voltage drop, he suggested applying a 2V battery to forward bias the shorted diode and blow it open-circuit! I haven't tried this, but he assures me that it will work as has done it in the past. M.D.

Ferguson ICC7/8 Chassis

There have been problems with the supply of field output chips for use as replacements in these chassis. If you fit a Phoenix Modkit 8F and find that there is cramping at the bottom of the screen, fit a 2.7V zener diode instead of the 2V zener diode supplied in the kit. It's connected from pin 7 to chassis, with its anode to chassis.

If you fit the new type of TDA8178FS chip made by S.T. Sing and find that there is still no field scanning, fit a $3.9k\Omega$ resistor between pins 2 and 7 and a 2.7V zener diode from pin 7 to chassis, anode to chassis. **E.O.**

Goodmans 286NS/05 (Philips L6.3 chassis)

The problem with this set was lack of

width, with the EW adjustments having no effect. These sets have separate line scan coupling and EW coupling capacitors (instead of using a single capacitor to do both jobs). C2915 provides the line scan coupling and C2913 the EW coupling. They are both 390nF, 250V capacitors. The cause of the problem was that C2915 had gone open-circuit.

The set had been in a week or so previously because it was dead with the line output transistor faulty. Now we know why the transistor had failed! A new capacitor plus adjustment of the width etc. controls restored normal scanning. **G.R.**

JVC MX and MX II chassis

If the HT starts to come up and then shuts down, don't overlook D521 (BY228) in the rather complicated EW diode modulator circuit. It's partly hidden by a large pulse capacitor behind the line output transformer.

Models fitted with these chassis include the AV25/AV28GS1EK and AV25/AV28S1EK. G.R.

Bang and Olufsen 7730

This set's problem was no sync and weak video. My problem was that I didn't have a circuit diagram! But scope checks brought me to TR1 (BC547C) on the AV/scart board. There was plenty of video at its base, but nothing at its emitter. When I removed it for test I found that it was leaky collector-to-emitter. A replacement restored this old set's performance to new. **G.R.**

Ferguson C51F (ICC6 chassis)

This set tripped nine times then there was nothing (the LED didn't always blink). I carried out checks around the microcontroller chip IR01 and found that the conditions at the line and field sync pulse input pins 26 and 27 were incorrect. Further investigation brought me to TL90 (BC848B) which monitors the beam current. It's closely connected to TF01 (another BC848B), which I also replaced. The originals read OK when checked out of circuit, but replacements cured the fault. **G.R.**

Akai CT2137UKT

There was no audio, just hiss. The sound was OK via the scart connector. Not thinking about set-up menus etc., I replaced the 6MHz filter 30F2 next to the TDA8362A jungle chip. This made no difference. There was an empty place for another filter, 30F1, so I fitted a 6MHz resonator here. This produced perfect sound. **G.R.**

Goodmans GD2880A (Ferguson ICC9 chassis)

The job card listed three faults. No remotecontrol operation was cured by replacing the IR detector on the front PCB. The second fault was "intermittently dead". Checks in the supply/reset circuitry for the microcontroller chip IR01 revealed incorrect voltages around TR85 (BC848B) and TR87 (BC858B). Two new transistors sorted this problem out. The final fault, a blank raster but video via the scart connector OK, was cleared by replacing TX16 (BC858B) in the scart processing section of the receiver. G.R.

Bush 2863NTX/A (11AK19 chassis)

This set came in with the line output transistor short-circuit. When I fitted a replacement and switched on again the bottom two inches of the picture were badly cogged and the new transistor was running hot. The capacitors in the line output stage all seemed to be OK, so I carried out a close inspection with a magnifier. This revealed an almost invisible dry-joint at wire link J613, which is connected to the emitter of the line output transistor. Once this had been attended to, a long soak tested proved that the set was now OK.

I've since had two more of these sets with the same fault. G.L.

Sanyo CBP2180A (A5 chassis)

If the picture is shifted towards the righthand side of the screen, replace the horizontal centring potentiometer VR411 ($50k\Omega$). The fault is sometimes intermittent. Don't try to clean VR411, as the set will nearly always pay you a return visit. **G.L.**

Ferguson C51F (ICC6 chassis)

This set's picture was affected by what can only be described as line twitch. It got worse as the set warmed up, but use of freezer failed to locate the culprit. After much checking with an oscilloscope I found that TV71 (BC858B) was the guilty party. It's in the line pulse feedback path to pin 13 of the STV2110 colour decoder/ video processor/timebase generator chip IV01. When it was checked with a meter it produced perfect readings, but a replacement cured the fault. G.L.

Bush 2868NTX (11AK19 chassis)

This set was brought in because it was dead. But there were no short-circuits or signs of distress. In view of the number of these sets I've repaired recently, I really ought to get a circuit diagram! Checks in the power supply revealed that R825 (2.2M Ω) was open-circuit. So I fitted a replacement and, in hope, switched on. Nothing – the set was still dead. After a lot more checks I found that R806 (22k Ω) was open-circuit. Its replacement finally restored normal operation. Has anyone got an 11AK19 circuit diagram going cheap?! G.L.

Daewoo DMQ2159 (CP315 chassis)

For the first thirty minutes or so after

switching this set on the picture was excessively bright with low contrast and field flyback lines visible. The cause was C426 ($3\cdot3\mu$ F, 250V), which is the reservoir capacitor for the 190V supply to the RGB output stages. It's at the rear of the main PCB. E.T.

Bang and Olufsen MX3000

Many of these sets are still going strong after more than a decade. At this stage in their lives a common problem is dry-joints. When these are at thyristor DL21 the result is intermittent field collapse; when they are in the tube heater circuit on the main PCB the picture disappears; and when they are around the line output transformer the result may, for example, be spasmodic line underscanning. Always scrape, flux and tin the affected pins or leads before resoldering. E.T.

Hitachi C28300TN (A5 chassis)

If the picture takes a long time to appear and/or has heavy white bands across it from cold, replace C954 (1,000 μ F, 35V). It's the reservoir capacitor for the 12.6V supply, on the secondary side of the chopper transformer. You'll find it on the power/deflection panel. M.L.

Nokia 6361 (D-E FST chassis)

After carrying out resoldering in the line output and power supply sections to cure the usual intermittent problems I found that the picture was quite badly shaded, dark at one side and light at the other. The culprit was C525 (10μ F, 50V), which smooths the output from the 12V regulator. M.L.

Matsui 1455

This set was stuck in standby. My first checks were on the transistors in the HT switching circuit, Q605 and Q606, as they have given a lot of trouble in the past. Not this time however. The cause was R624 (100k Ω), which links the on command to the base of Q605. M.L.

Samsung CI5061 (P68SA chassis)

The customer said that the brightness varied. But on the first two occasions when this set came in the fault didn't appear. On the third occasion the picture was very dark at switch on, but the brightness returned after about a minute. The set didn't repeat this performance.

I pondered and decided that the line output transformer was probably the cause, with a dodgy first anode potentiometer. But, to my embarrassment, the set came back a fourth time. On this final occasion the fault was almost permanent. The brightness was actually fluctuating very fast. It did this in all modes, including text and AV. The cause was eventually traced to the 2SA539-Y transistor Q905 on the tube base panel. It's a pnp transistor that's connected in series with the emitters of the three RGB output transistors. M.L.

Sony KVX2182U (BE3B chassis)

Sets that are stuck in standby can be a problem. There are often so many possible causes, with all sorts of protection circuits which can operate, that it can be difficult to know where to start. If you should get one of these Sony sets with the problem however the first suspect is the memory chip IC002. It's a small, surface-mounted device which is on board A. There's an 80 per cent chance that a replacement will cure the problem, with no other faults evident. The part no. is 8-759-334-20. You will need to set up the width etc. afterwards. M.L.

Hitachi G8Q Chassis

We all know what happens when C933 (2,200 μ F, 25V) in this chassis dries up, don't we? Line tearing, leading to no picture with the sound OK. Then finally nothing, as if the set is dead. The 12V line is in trouble of course, because C933 is the reservoir capacitor for the supply to the 12V regulator. While you are replacing C933, do yourself a favour and change C932 (470 μ F,16V) as well. It's the reservoir capacitor for the 8V supply. You'll be glad you did, as the following story shows.

The set, a **CPT2578**, had for some years lived in a flat within walking distance. I had replaced C933 about twice. The owner then moved to a converted farmhouse miles away, and the set was installed two floors up. That meant two sets of narrow stairs. Guess what happened next?

The aerial rigger had retuned the set for the different transmitter. Then strange teletext faults appeared, the most obvious being the need to switch the set off at the mains, then on again, to return to TV from text. Two days later the set came on with a blank screen, the sound being OK. Could I call and investigate?

I made the call with a feeling of foreboding. A check on the memory program showed that it was wrong. After setting the bits correctly the text faults seemed to have been cured, but I still had a blank screen. When I turned up the A1 control flyback lines appeared. My first thought was sandcastle pulse problems, but I wasn't convinced about this. The owner lugged the set down the stairs, and back to the workshop it came.

Initial checks showed that the sandcastle pulses were indeed wrong, but I could smell something getting hot. That something was the L932/R931 combination in the 8V supply, which feeds the 5V regulator on the text panel. The regulator was getting hot. Things cooled down when I removed the text board and fitted a link to reconnect the video. A scope check then revealed that there was a large ripple on the 8V line. C932 was the culprit.

The sandcastle trouble was caused by the TDA2579A timebase generator chip IC701, which also produces the sandcastle pulses. It takes its supply from the 12V rail. Once a replacement had been fitted there was a good picture.

There was a clean 8V supply when C932, L932 and R931 had been replaced. But it was loaded down when I refitted the text panel, and there was a repeat of the overheating. It was difficult to assess how much silicon was faulty on the text board. Both RAM chips were damaged at least. Fortunately I had another text board, of unknown condition. It proved to be a working board.

The moral is to replace both C933 and C932. My notes suggest that when C932 starts to dry up diagonal bands of interference can be seen, particularly in the text mode. But the owner saw nothing amiss until it was too late. **R.B.**

Phoenix CTV2105R

This set is fitted with the **Fidelity ZX4000** series chassis, or a version of it. But the component reference numbers are not the same. For example C80 (100μ F, 25V), which causes low start-up voltage at pin 9 of the TDA4600 chopper control chip when it fails, is C94 in this version.

The fault this time came to light when the owner's son used the mains switch, for the first time in many months, to turn the set off - it normally stayed in standby. The set refused to come on straight away and when it did finally start up, after many frantic thumps on the mains switch, it couldn't be turned off.

The mains switch, which was the original one, had succumbed and was now welded on permanently. The cause of the very slow start up was the chopper transistor's base drive coupling capacitor C95 (100 μ F, 25V). Its value had fallen to 60 μ F. Incidentally this item is C78 in the ZX4000 series chassis. Fortunately the chopper had survived and, after resoldering some suspect joints, the set was declared to be healthy again. **R.B.**

Goodmans 2032

This Comet model is similar to the **Nikkai NT20**. Top foldover is a common fault with these sets. The item to check is C313 ($2\cdot 2\mu F$, 200V) which goes open-circuit. **R.B.**

Valve Radio and Audio Repair

* A practical manual for collectors, owners, dealers and service engineers * Essential information for all radio and audio enthusiasts *

This book is not only an essential read for every professional working with antique radio and gramophone equipment, but also dealers, collectors and valve technology enthusiasts the world over. The emphasis is firmly on the practicalities of repairing and restoring, so technical content is kept to a minimum, and always explained in a way that can be followed by readers with no background in electronics. Those who have a good



E27.00 ** Price includes delivery and packing **

grounding in electronics, but wish to learn more about the practical aspects, will benefit from the emphasis given to hands-on repair work, covering mechanical as well as electrical aspects of servicing. Repair techniques are also illustrated throughout.

This book is an expanded and updated version of Chas Miller's classic Practical Handbook of Valve Radio Repair. Full coverage of valve amplifiers will add to its appeal to all audio enthusiasts who appreciate the sound quality of valve equipment.

Post to Jackie Lowe, Cumulus Business Media, Anne Boleyn House, 9-13 Ewell Road, Cheam, Surrey, SM3 8BZ

How to pay (Valve Radio and Audio Repair Handbook) paperback		
I enclose a cheque/bank draft for £ (payable to Cumulus Business Media)		
Please charge my credit/charge card Mastercard American Express Visa Diners Club		
Credit Card No: Expiry Date:		
Signature of Cardholder		
Cardholder's statement address: (please use capitals)		
Name		
Address		
3		
Post CodeTel:		



PIEZO ELECTRIC SOUNDER, also operates efficiently as a microphone. Approximately 30mm diameter, easily mountable, 2 for £1. Order Ref: 1084. LIQUID CRYSTAL DISPLAY on p.c.b. with i.c.s. etc. to drive it to give 2 rows of 8 figures or letters with data.

Order Ref: 1985. 30A PANEL MOUNTING TOGGLE SWITCH, Doublepole, Order Ref: 166

SUB MIN TOGGLE SWITCHES. Pack of 3. Order Ref: 214

HIGH POWER 3in SPEAKER 11W 8ohm). Order Ref: 246

MEDIUM WAVE PERMEABILITY TUNER. It's almost a complete radio with circuit. Order Ref: 247

HEATING ELEMENT. mains voltage 100W, brass encased. Order Ref: 8.

MAINS MOTOR with gearbox giving 1 rev per 24 hours. Order Ref: 89.

ROUND POINTER KNOBS for flatted ¼in, spindles, Pack of 19. Order Ref: 295.

CERAMIC WAVE-CHANGE SWITCH. 12-pole, 3-way with ¼in, spindle, Order Ref; 303.

REVERSING SWITCH. 20A double-pole or 40A single pole. Order Ref: 343.

LUMINOUS PUSH-ON PUSH-OFF SWITCHES. Pack of 3. Order Ref: 373.

SLIDE SWITCHES. Single pole changeover. Pack of 10. Order Bef: 1053.

PAXOLIN PANEL. Approximately 12in. x 12in. Order Ref: 1033.

CLOCKWORK MOTOR. Suitable for up to 6 hours. Order Ref: 1038

TRANSISTOR DRIVER TRANSFORMER. Maker's ref. no LT44, impedance ratio 20k ohm to 1k ohm; centre tapped, 50p. Order Ref: 1/23R4.

HIGH CURRENT RELAY, 12V d.c. or 24V a.c., operates changeover contacts. Order Ref: 1026.

3-CONTACT MICROSWITCHES, operated with slightest touch, pack of 2. Order Ref: 861

HIVAC NUMICATOR TUBE, Hivac ref XV3. Order Ref: 865 or XN11 Order Ref: 866

2IN. ROUND LOUDSPEAKERS. 50Ω coil. Pack of 2. Order Ref: 908.

5K POT, standard size with DP switch, good length %in. spindle, pack of 2. Order Ref: 11R24

13A PLUG, fully legal with insulated legs, pack of 3. Order Ref: GR19.

OPTO-SWITCH on p.c.b., size 2in. x 1in., pack of 2. Order Ref: GR21

COMPONENT MOUNTING PANEL, heavy paxolin 10in. x 2in., 32 pairs of brass pillars for soldering binding components. Order Ref: 7RC26.

HIGH AMP THYRISTOR, normal 2 contacts from top, heavy threaded fixing underneath, think amperage to be at least 25A, pack of 2. Order Ref: 7FC43.

BRIDGE RECTIFIER, ideal for 12V to 24V charger at 5A, pack of 2. Order Ref: 1070

TEST PRODS FOR MULTIMETER with 4mm sockets. Good length flexible lead. Order Ref: D86.

LUMINOUS ROCKER SWITCH, approximately 30mm square, pack of 2. Order Ref: D64.

MES LAMPHOLDERS slide on to %in. tag, pack of 10. Order Ref: 1054.

HALL EFFECT DEVICES, mounted on small heatsink, pack of 2. Order Ref: 1022.

12V POLARISED RELAY, 2 changeover contacts. Order Ref: 1032.

PROJECT CASE, 95mm x 66mm x 23mm with removable lid held by 4 screws, pack of 2. Order Ref: 876.

LARGE MICROSWITCHES, 20mm x 6mm x 10mm, changeover contacts, pack of 2. Order Ref: 826.

MAINS RELAY with 15A changeover contacts. Order Ref: 965.

COPPER CLAD PANELS, size 7in. x 4in., pack of 2. Order Ref: 973

100M COIL OF CONNECTING WIRE. Order Ref: 685. WHITE PROJECT BOX, 78mm x 115mm x 35mm Order Ref: 106

MIC ROSWITCHES, LEVER-OPERATED faulty would be

equipment, batch tested, any fa replaced, pack of 10. Order Ref: 755, MAINS TRANSFORMER, 12V-0V-12V, 6W. Order Ref:

811

THIS MONTH'S SPECIAL

IT IS A DIGITAL

MULTITESTER, complete with backrest to stand it and handsfree test pro holder. This tester measures d.c volts up to 1,000 and a.c. volts up to 750; d.c. current up to 10A and resistance up to 2 megs. Also tests transistors and diodes

and has an internal buzzer for continuity tests. Comes complete with test prods, battery and instructions. Price £6.99. Order Ref⁻ 7P29

front engraved 0-100. Price £1.50 each. Order Ref: 1/1600

VERY THIN DRILLS, 12 assorted sizes vary between 0.6mm and 1.6mm. Price £1. Order Ref: 128

EVEN THINNER DRILLS. 12 that vary between 0.1mm and 0.5mm. Price £1. Order Ref: 129. BT PLUG WITH TWIN SOCKET. Enables you to plug

2 telephones into the one socket for plugs, Price £1,50, Order Ref; 1,5P50, for all normal BT

D.C. MOTOR WITH GEARBOX. Size 60mm long, 30mm diameter. Very powerful, operates off any voltage between 6V and 24V D.C. Speed at 6V is 200 rpm, speed controller available. Special price £3 each. Order Ref: 3P108

FLASHING BEACON. Ideal for putting on a van, a tractor or any vehicle that should always be seen. Uses a Xenon tube and has an amber coloured dome Separate fixing base is included so unit can be put away if desirable, Price £5, Order Bef: 5P267

MOST USEFUL POWER SUPPLY. Rated at 9V 1A this plus into a 13A socket, is really nicely boxed. £2. Order Ref: 2P733.

MOTOR SPEED CONTROLLER. These are suitable for D.C. motors for voltages up to 12V and any power up to 1/6h.p. They reduce the speed by intermittent full voltage pulses so there should be no loss of power. In kit form these are £12. Order Ref: 12P34. Or made up and tested, £20. Order Ref: 20P39.

BT TELEPHONE EXTENSION WIRE. This is proper heavy duty cable for running around the skirting board when you want to make a permanent extension. cores properly colour coded, 25m length. Only £1. Order Ref: 1067

LARGE TYPE MICROSWITCH with 2in. lever. changeover contracts rated at 15A at 250V, 2 for £1 1/2R7

BALANCE ASSEMBLY KITS, Japanese made, when assembled ideal for chemical experiments, complete with tweezers and 6 weights 0.5 to 5 grams. Price £2 Order Ref: 2P44

CYCLE LAMP BARGAIN, You can have 100 6V 0-5A MES bulbs for just £2.50 or 1,000 for £20. They are beautifully made, slightly larger than the standard 6.3V pilot bulb so they would be ideal for making displays for night lights and similar applications. DOORBELL PSU. This has AC voltage output so is

ideal for operating most doorbells. The unit is totally enclosed so perfectly safe and it plugs into a 13A socket. Price only £1. Order Ref: 1/30R1. INSULATION TESTER WITH MULTIMETER. Internally generates voltages which enable you to

internally generates voltages which enable you to read insulation directly in megohms. The multi-meter has four ranges, AC/DC volts, 3 ranges DC milliamps, 3 ranges resistance and 5 amp range. These instruments are ex-British Telecom but in very good condition, tested and guaranteed OK, probably cost at least £50 each, yours for only £7.50 with leads, carrying case £2 extra. Order Ref: 7.5P4. **REPAIRABLE METERS.** We have some of the above

testers but slightly faulty, not working on all ranges should be repairable, we supply diagram, £3. Order Ref: 3P176.

TWO MORE POST OFFICE INSTRUMENTS Both instruments contain lots of useful parts, including submin toggle switch sold by many at £1 each. They are with battery extremely nice cases, both in compartment and flexible carrying handles, so if you don't need the instruments themselves, the case may

be just right for a project you have in mind. The first is Oscillator 87F. This has an output, continuous or interrupted, of 1kHz. It is in a plastic box Price only £1. Order Ref: 7R1.

The other is Amplifier Ref. No. 109G. This is in a case size 80mm wide, 130mm high and 35mm deep. Price £1. Order Ref: 7R2.

HEAVY DUTY POT. Rated at 25W, this is 20 ohm resistance so it could be just right for speed controlling a d.c. motor or device or to control the output of a high current amplifier. Price £1. Order Ref: 1/221 1

STEPPER MOTOR. Made by Philips as specified for the wind-up torch in the Oct '00 Practical Electronics is still available, price £2. Order Ref: 2P457.

SOLDERING IRON, super mains powered with longlife ceramic element, heavy duty 40W for the extra special job, complete with plated wire stand and 245mm lead, £3. Order Ref: 3P221.



various sorts in stock, so if you need anything special give us a ring. A few new ones that have just. arrived are special in that they are plug-in and come complete with a special base which enables you to check voltages of connections of it without have to go underneath. We

RELAYS



have 6 different types with varying coil voltages and contact arrangements. All contacts are rated at 10A 250V AC.

Coil Voltage	Contacts	Price	Order Ref:
12V DC	4-pole changeover	£2.00	FR10
24V DC	2-pole changeover	£1.50	FR12
24V DC	4-pole changeover	£2.00	F R 13
240V AC	1-pole changeover	£1.50	FR14
240V AC	4-pole changeover	£2.00	FR15
Prices include	hase		

MINI POWER RELAYS. For p.c.b. mounting, size 28mm x 25mm x 12mm, all have 16A changeover contacts for up to 250V. Four versions available.

they all look the same but have different coils: 6V Order Ref: FR17 12V Order Ref: FR18 24V Order Ref: FR19 48V Order Ref: FR20

Price £1 each less 10% if ordered in quantities of 10, same or mixed values.



RECHARGEABLE NICAD BATTERIES, AA size, 250 each, which is a real bargain considering many firms charge as much as £2 each. These are in packs of 10, coupled together with an output lead so are a 12V unit but easily dividable into 2 x 6V or 10 x 1.2V. £2.50 per pack. 10 packs for £25 including carriage. Order Ref: 2.5P34. FOR OUICK HOOK-UPS. You can't beat leads with a croc

clip each end. You can have a set of 10 leads, 2 each of 5 assorted colours with insulated crocodile clips on each end. Lead length 36cm, £2 per set, Order Ref: 2P459.



11

BIG 12V TRANSFORMER. It is 55VA so that is over 4A which is normal working, intermittently it would be a much higher amperage. Beautiful transformer, well made and very well insulated, terminals are in a plastic frame so can't be accidentally touched. Price £3.50. Order Ref: 3.5P20.

BUY ONE GET ONE FREE

ULTRASONIC MOVEMENT DETECTOR. Nicely cased, free standing has internal alarm which can be silenced. Also has connections for external speaker or light. Price £10. Order Ref: 10P154.

CASED POWER SUPPLIES which, with a few small extra components and a bit of modifying, would give 12V at 10A. Originally £9.50 each, now 2 for £9.50. Order Ref: 9.5P4.

3-OCTAVE KEYBOARDS with plano size keys, brand new, previous price £9.50, now 2 for the price of one. Order Ref: 9.5P5

1.5V-6.V MOTOR WITH GEARBOX. Motor is mounted on the gearbox which has inter-changeable gears giving a range of speeds and motor torques. Comes with full instructions for changing gears

Ref: 7P26. MINI BLOWER HEATER. 1kW, ideal for under desk or airing cupboard, etc., needs only a simple mounting frame, price £5. Order Ref: 5P23.

and calculating speeds, £7. Order



TERMS







MONITORS

Fault reports from Ian Field Geoff Butcher and Gerry Mumford

We welcome fault reports from readers – payment for each fault is made after publication.

Reports can be sent by post to:

Television, Fault Reports, Anne Boleyn House, 9-13 Ewell Road, Cheam, Surrey SM3 8BZ

or e-mailed to: tessa2@btinternet.com

CTX 1565D

These monitors can be a bit puzzling when dead, since a short almost anywhere on the secondary side of the power supply can activate the safety shutdown transistor, which shorts out the supply to pin 7 of the UC3842 choppercontrol chip. The second transistor in this part of the circuit assists the start-up resistor, by disconnecting it once the power supply has started up. So the cause of this fault is unlikely to be an opencircuit start-up resistor.

Possibly the most common causes of this type of shutdown are failure of the B+ chopper MOSFET Q401 or any of the rectifiers on the secondary side of the circuit. On this occasion however the 2SC4924 line output transistor was the cause. Line drive is coupled to this transistor's base by C701 (100μ F, 50V), which was so bad that it failed to produce any deflection at all on my home-brew ESR bridge. I upgraded the replacement to an HF-SMPSU type and added an 0.33μ F Mylar capacitor in parallel to further reduce self-heating.

One of the rectifiers on the secondary side of the circuit was a bit wobbly. Despite being soldered to a heat fin, it had cooked the bonding between its tracks and the PCB. Some stout link wire was used to eliminate the risk of cracks developing in the lifted track foil. I applied a layer of black ink from a jumbo marker pen to the heat fin to improve its ability to radiate heat. This reduced its operating temperature significantly. **I.F.**

ICL PD0110

These Acer produced chassis are well constructed. I had a batch of them that had come from a local school which had undertaken an upgrade. They are SVGA but only just, as they provide only 800 × 600 in addition to the basic VGA modes. Nevertheless they were worth checking out as they were quickly snapped up by customers as temporary/spare monitors.

They were all working, requiring only small adjustments such as grey-scale set up and, in a couple of cases, attention to the heater supply components.

The focus isn't too good. This is partly because of the poor HF performance of the video amplifiers and quite possibly coarse shadowmask pitch. The video outputs are DC coupled, so there are no coupling electrolytic capacitors to deteriorate and therefore no improvement to be had. The biggest single cause seems to be that the design uses the LM1203 chip's built-in cathode bias controls instead of separate presets to superimpose a clamp level on the video outputs. This way of using the LM1203 always seems to produce inferior video resolution. In one case I tried replacing every single electrolytic capacitor on the CRT's base PCB. This produced a just-noticeable improvement, but was certainly not worth the effort.

These monitors were all fitted with the Hitachi tube type M34JMA30X72(J). I've found that Hitachi tubes do sometimes give poorer focus performance than you might expect. But 'flashing' the focus electrode produced no improvement, suggesting that the CRT may not have been what was limiting the picture resolution. In the end I sold off the monitors cheap: no one who bought them has come back to complain!

One had something rattling about inside when it arrived. This turned out to be the screw from the top-steady bracket on the line output transformer. **I.F.**

Intertan VCM100S

The customer said that this monitor worked all right but the picture was too narrow. When I took the back off I saw that the monitor had been badly affected by cigarette smoke. Even TV sets were never tar-coated to this extent! In addition the soldering had deteriorated with age. Unfortunately the monitor has to be completely dismantled to get at the print side. I wondered whether the heavy deposits were loading anything down – this has been known with heavilycontaminated TV sets.

So, while it was apart, I cleaned everything with a mild solvent. This made no difference. The sub-width control VR440 was next tried. Even at maximum it failed to produce the required width. It's in series with the front panel width control and, as maximum resistance produces maximum width, when set at maximum it also reduces the range of the user width control.

There's no adjustable width inductor, so the only option left was to try to optimise the flyback tuning. As the existing tuning capacitor C952 ($6\cdot8nF$, $1\cdot6kV$) was in good condition, I varied the value by adding 1nF in increments. The width peaked at a value of $10\cdot5nF$, so I fitted $9\cdot5nF + 1nF$. With the preset backed off to minimum, the user control had maximum adjustment range. The width was just right with the user control centred. **I.F.**

Multiscan L7031LD

This 17in. monitor was tripping. On investigation I found that Q710 (Mitsubishi FS10UM5) in the B+ PWM circuit was short-circuit. Despite its rather unusual-looking type number, this device is a fairly normal MOSFET. The PWM circuit is different from that found in smaller monitors. It's a flyback converter instead of the usual buck regulator. A flyback regulator is safer, because a buck regulator carries out voltage step-down unless the series switch MOSFET goes short-circuit, when the full unregulated input voltage is applied to the line output stage. When the MOSFET in the flyback converter type of circuit fails, it shorts the B+ input, activating the power supply excess-current trip.

I removed the faulty MOSFET and lifted one end of the inductor to break the circuit, then inserted a 60W bulb to configure the circuit for step-down and limit the current. It didn't supply enough current for the line output stage to get going, so power resistors were added in parallel until some light appeared on the screen. This proved that the line output stage was operational. At this stage the combined resistance value was very low, and most of the 46V input was reaching the line output stage.

The next step was to find a suitable replacement for Q710. I settled for a 2SK1221, which has the ratings Id = 10A and Vds = 250V. It worked without any sign of distress, and the regulated B+ rail settled at 66.5V. **I.F.**

Bluepoint DC1464

The power supply was tripping silently. I found that someone else had replaced D111, which is on a heat fin, back-tofront! The original diode had been cut out, leaving enough lead attached to the heat fin to twist together with the replacement diode's lead. It was probably fortunate that the previous 'repairer' had dropped a large blob of solder on the track side of the PCB, as this shut the power supply down. Otherwise, the monitor would probably have been a loud and expensive write-off!

Not knowing the correct diode type (the replacement had been a BYW95B), I checked the voltage rating of its reservoir capacitor C120. It was 63V, so I decided that a UF5404 would be suitable. The repaired power supply then worked, but Q415 (2SC5326) was short-circuit. This had probably been the original and only fault. Once a replacement had been fitted the monitor was as good as new.

During the repair I found a number of marginal dry-joints in the line output stage. These could have been the cause of Q415's failure. **I.F.**

CTX 1565D

The first thing I noticed after removing the back was that all four screws which secure the CRT to the front moulding were about half unscrewed. The CRT was free to flop about! This usually means that the monitor has been dropped, stripping or cracking the screw bases. But these had been unscrewed!

After checking for any other forms of tampering, I powered the unit and found that there was a tilted display. It was possible to correct this by slackening the yoke-clamp Allen screw and easing the deflection assembly into the correct position. The convergence errors that this introduced were very slight, and were easily corrected with the wire-wound preset Yv and inductor Xv on the scan assembly. I didn't have to disturb the ring magnets.

While working on the deflection assembly it became apparent that the red output was intermittent. The CRT's red cathode pin had all but let go, and the soldering to all the three RGB output transistors was very poor. I.F.

AOC 7Gir

"There was a flash and it went off" the customer said. On investigation I found that the chopper FET had blown apart and the 47Ω resistor which is in series with its gate had burnt out. There were signs that the transistor had been running hot for some time before its final demise.

I replaced the transistor, the resistor and the UC3842 control/driver chip, and checked the associated components. The monitor then powered up and worked normally, but the new transistor heated to a higher temperature than seemed right after about ten minutes the heatsink temperature was at over 50°C. I then noticed that there was space on the PCB for two diodes, D907 and D931, in the chopper drive circuit. They had never been fitted. As an experiment I fitted them, using a 1N4148 in position D907 and a BYX85C15 zener diode in position D931. The result was a good 5°C reduction in the temperature of the heatsink.

After a good burn-in period the chopper heatsink remained at a lower temperature than the heatsink in the line output stage. I considered this to be satisfactory. **G.B.**

CTX 1765D

There was almost total line collapse, with only about 3cm of scan remaining. I found that the 2SC4924 line output transistor Q314 was leaky, and in addition R380 (1Ω , 0.25W) was opencircuit. There were also masses of dryjoints in this area – at R390, Q318, Q336, D317, T303 and T401. These had probably been the cause of the trouble. **G.M.**

Dell D825TM (Sony chassis)

This monitor powered up but there was no screen display. A check on the heater voltage showed that it was low -2.8Vinstead of 6.3V. The cause was the associated reservoir capacitor C632 (470µF, 16V). The heater supply is derived from the chopper circuit. **G.M.**

Philips 15B (CM2300 chassis)

There was excessive width with EW bowing, and the OSD adjustments had little effect. The cause of the trouble turned out to be a non-polar electrolytic capacitor, C2614 ($3\cdot 3\mu F$, 63V), in the EW driver stage. It was bulging. G.M.

Eizo F353, Model MA1767

The power supply was working but there was no display. On investigation I found that the 2SC5244 line output transistor Q501, the 2SD1889 EW driver transistor Q512 and the associated 30V, 500mW zener diode ZD502 were all short-circuit. As a result the 2SK1547 regulator FET Q930 on the secondary side of the power supply had been damaged and fuse F901 (800mA, wire-ended) had blown. Note that this item is on the track side of the PCB, between the positive connection to C908 and T901, with the track underneath it cut, i.e. it's a late addition/modification. **G.M.**

Tatung TM3401 (Y2 chassis)

The problem with this old-timer was partial frame collapse, with the top third of its shrunken raster compressed and over bright while the rest was expanded and dim. A check showed that the 21V supply to the TDA1675 frame timebase chip was low at only 14V. It follows a rather complicated path, via a sub-board that's bolted to the line output transistor's heatsink. A power FET on this sub-board switches the supply. Most of the voltage loss was across this FET, which was quite hot. It's drive is obtained from a 74LS123N logic-gate chip, IC701. The cause of the trouble was this chip, which wasn't turning the FET on hard enough.

Note that this chassis is also used in the Apricot XJ52178B and Viglen MT1428E monitors. G.M.

Acer JD156N

This monitor was dead and tripping. As usual with these monitors, there was a large dry-joint at pin 3 of the line output transformer – this is the B+ (HT) feed for the line output stage. The other pins were all, as usual, OK. But unfortunately pin 3 had this time arced over, destroying the FS10KM B+ regulator FET Q810 along with the associated voltage-doubler inductor L805 (part no. 2371131800). In addition EW modulator diode D421 (FSF05A60) was leaky. Replacement of these items restored the display. G.M.



VCR CLINIC

Reports from Eugene Trundle John Coombes Martyn Davis Roger F. White Ronnie Boag Geoff Butcher and Nick Beer

We welcome fault reports from readers – payment for each fault is made after publication. See page 746 for details of where and how to send reports.

Toshiba V312B

The front panel didn't light up and there was no action or response – except that the head drum was whizzing around faster than normal! Checks showed that there was lowfrequency ripple on the outputs from the power supply. The culprit turned out to be DP15, a 3.9V zener diode that's wired across RP33 on the primary side of the power supply. It was short-circuit. This item is not shown in the circuit diagram, and was not fitted in all production batches. E.T.

LG KE14U43

This TV/VCR combi unit had a nasty buzz on sound, but only with tape playback. Consultation with LG revealed that replacement of three capacitors helps with early production units like this one. Change the value of C358 on the video panel from 0.022μ F to 0.033μ F. It's connected to pin 65 of IC300. On the TV board, change the value of C607 to 100μ F and C603 to 56nF. With this particular machine there was also cyclic variation of the off-tape sound volume. It was cured by giving the ACE head assembly a little more 'lean-forward' into the tape. **E.T.**

Aiwa VX-T1450K

Access is good with this TV/VCR combi unit, and the deck can be got going for test while it's out of the cabinet. There was little sign of life with this one until fuse F90 had been replaced. The capstan motor rotation was then intermittent, the result being shutdown, chewed tapes etc. The motor itself was responsible. It's available from CPC under part number AWS6-003-030-600 at a little over £40 net. E.T.

Hitachi VTF450

Noisy playback, rewind and fast forward can be caused by the cassette housing's failure to drop the cassette low enough for correct drive. In this case however the cause proved to be a faulty tooth-type drive belt, which stretches and knocks on the chassis. To prevent stretching of the new belt, replace the take-up pulley as well. J.C.

Mitsubishi HS721 etc

The mode operation diodes can fail, causing a number of symptoms. In this case the machine cut out in playback after a few seconds because D5A9 and D5A1 were faulty. Other symptoms caused by faulty mode operation diodes include failure to accept a tape in the standby mode, no taperemaining indication, and no tape autoplay only without its tab (in this case tape ejection may not work).

There is a modification kit which consists of all these diodes. It applies to the HS600 mono series and the HS700 mono and hi-fi series. J.C.

Toshiba V404B

No results because of a power supply problem can be caused by CP007 and/or

CP008. Check them by replacement. J.C.

Mitsubishi HS621

The customer complained that this machine was either dead or ran erratically. There was no trouble once the following electrolytic capacitors had been replaced: C910 (4.7μ F, 5V), C915 (2.2μ F, 50V) and C9A3 ($1,000\mu$ F, 10V). M.D.

Sharp VCM301

This machine was brought in because there was no deck operation. Curiously, the power supply was OK. After much hunting around I discovered a dry-joint at Q9903, on the secondary side of the power supply. M.D.

Mitsubishi HS750V

This machine came in with the complaint "dead – won't accept tapes". Checks showed that the power supply was working and that all the main voltages on the secondary side were apparently correct. But the 6.5V that should be present at D9AZ was low at only about 1V. Once C9A3 (1,000 μ F, 10V) had been replaced this voltage was correct and the machine ran normally. M.D.

GoldStar PW9041, T1631

If the fluorescent display is dim, replace C25 (100μ F, 10V) in the power supply. M.D.

Sharp VCH81H

There was no capstan rotation. After checking the supplies to the motor I took a closer look at the motor itself and found that a 10 μ F, 25V capacitor had leaked on to the motor's PCB. As a result the print was open-circuit. A fairly neat repair was possible, and after fitting a replacement capacitor everything was OK. **R.F.W.**

Lloyds L444

The display had just two zeros, with occasional flicker, and there were no functions. It was the first time I'd ever seen a Lloyds VCR, but the Sharp deck was familiar. The fault was in the power supply however, where a $3,300\mu$ F, 25V radial electrolytic capacitor had a slight bulge in its top. When I unsoldered it one leg fell off. A replacement restored normal operation. **R.F.W.**

JVC HRJ665

This machine went dead intermittently. The cause was dry-joints at DS207. **R.B.**

Sanyo VHR789

This machine wouldn't accept tapes. A check showed that there was no voltage across the loading motor, which was short-circuit. **R.B.**

Akai VSJ717

There was no playback or E-E sound. Replacement of the TDA9605 chip IC801 cured the fault. **R.B.**

Matsui VP9505

This machine would sometimes eject a cassette immediately after insertion. At other times it would thread up and work normally. A new mode switch made no difference.

Some cassettes seemed to be more troublesome than others. Having found one that never seemed to work, I discovered that the left-hand end of the lift didn't go home fully. As a result, the cassette-down switch didn't operate and the machine ejected the tape.

I found that a new lift assembly, part no. HOUS471, is available from SEME at a surprisingly low cost, so it wasn't worth messing about with the original one. Once the new lift assembly had been installed the machine worked correctly at all times. **G.B.**

Panasonic NVA3B

A colleague was having problems with this VHS-C Slimcorder. When power was applied the chopper circuit started up but was pulsing. A raster appeared in the EVF then disappeared, and there was no video at the AV outputs. He had disconnected the camera head to eliminate the effect of a fault in this area – we occasionally get jammed iris motors for example – but this had made no difference to the symptoms. There didn't seem to be any shorts across the outputs from the power supply, and hot checks were inconclusive because of the speed of the pulsing.

I was able to establish that when the power supply started up its three main outputs appeared. Not all three feedbacks were present however. The camera 18V and -8V supplies provided via T1001 came up momentarily, like the others, but feedback at pin 22 of IC1001 was nil. I then found, by carrying out DC checks, that the $22k\Omega$ surface-mounted resistor R1008 was open-circuit. When I inserted a temporary replacement, from a scrap PCB, the unit seemed to be working properly but the camera section was still disconnected. When it was plugged in the fault returned!

Disconnecting the camera section cleared the pulsing. So there had been two faults. It's relatively easy to establish the nature of a fault in the camera head as there are only two connectors, one for the lens motors and sensors and the other for the imager. In fact the imager was the cause of the problem. No shorts could be detected, and none of the few surfacemounted components on the flexiprint was the cause. A new imager restored order – and sanity.

Note that the imager's part number changed during production. The part number in the manual, VEK7146, applies to earlier models with a shorter FPC. The later part number, VEK7375, applies with the longer FPC. **N.B.**

The help wanted column is intended to assist readers who require a part, circuit etc. that's not generally available. Requests are published at the discretion of the editor. Send them to the editorial department – do not write to or phone the advertisement department about this feature.

Wanted: Amstrad UF20 VCR for breaking. Require head and drum assembly plus guide unit. Condition of head unimportant. Also, could anyone help identify the maker or importer of a colour portable badged "Univercell" (exact spelling on remote-control unit)? It has a separate power supply panel on the left-hand side looking in from the rear, and may be of Nokia origin, perhaps 1996 vintage. Better, could anyone supply a circuit diagram, in particular of the power supply?

Phone John Martin on 020 8337 3366 or e-mail

john-martin@FreeNet.co

Wanted: JVC GR-45E camcorder, working or non-working but with working viewfinder. Accessories not important. Phone Andrew Duggan at ATD Electricals – tel/fax 01248 602 584 (Gwynedd).

Wanted: Single LCD display (one of three) for the Sony VPL-V500QM data projection unit. The LCD may have been produced only as part of a complete assembly, in which case a dud assembly with say one dud LCD would do. John Stockley, 27 Campden Road, Croydon CR2 7ER. Phone 020 8688 3089 any time.

For sale: Practical Television magazines from 1959-1979. Twelve full years, eight part sets. Also 19 Radio and Television Servicing books covering models before 1955 up to 1975-76, circuit diagrams for the Sanyo VCR Model VTC9300P and portable stereo music system Model G2711, service manuals for the Thorn 850, 950, 8000 and 9600 chassis, and a Breeze Electrical System. Offers please on 01233 663 835. Wanted: Sentercel K8/50 EHT rectifier plus 0.05μ F, 2kV EHT smoothing capacitor for the Telequipment oscilloscope Model D43. Geoff Davies, 13 Bowen Road, Rugby CV22 5LF. Phone 01788 574 774. Wanted: BUZ77 transistor for the NEI

11AK08 chassis. Allan Watson, 2 Masefield Avenue, Padiham, Lancs BB12 8SY. Phone 01282 774 114.

Wanted: Remote control unit for the Orion satellite receiver Model JRD2001. F. Nedza, 40 Brynhyfryd, Glynneath, Neath, West Glamorgan SA11 5BA. Phone 01639 720 429.

Wanted: CRT (6in.) for the Decca marine radar Model 060, or information of a possible source of supply. The tube fitted is a Brimar F15-100LD 910/FV. Maybe there's an equivalent? No burns. Phone Dennis Shakeshaft on 01287 637 681 (Cleveland). Wanted: Help with the Ferguson Model T59N (TX92 chassis?). The problem is locking up with no response to the remotecontrol unit. Jim Lesurf, 110 Hunters Square, Dagenham, Essex RM10 8BG. Phone 07974 611 402.

Wanted: Sony SLF1UB portable Betamax VCR. Must be in mint condition and in full

working order. Will pay good money for the right unit. A.C. Griffin, 89 The Ridgeway, Sedgley, West Midlands DY3 3UN. Phone 01902 880 063.

Wanted/for sale: Cash paid for working Goodmans Model 149TT TV set, with or without cabinet. Have for sale a Gardner inverter, Model 107A: input 11-15V DC, output 220-240VAC nominal, square waveform. Price £50 ono. R.S. Rosier, 3 Downs View Road, Maidstone, Kent ME14 2JB. Phone 01622 761 391.

Wanted: SC84202 IC or tuning board 29504 003 02 for the Grundig A6410/2/3/4 (CUC220 chassis). This is required to repair a set that's otherwise in very good condition, for an elderly lady in poor health. All expenses paid. Reg Stroud, 2A Linden Road, Gloucester GL1 5HD. Phone 01452 503 581.

Wanted: A reel-to-reel audio tape recorder, also help in getting a Heathkit AFM2 tuner and AA22U amplifier going. Manuals or any information would be welcome. David Holdsworth, 11 Star Farm Close, Bradwell, Norfolk NR31 8UZ. Phone 01493 668 867. Wanted: Information on replacing the 5532 dual analogue op-amp in the Nad 524 CD player with a Burr Brown OPA2604 FET op-amp. A circuit showing this modification and component values would be a great help. The op-amps are a direct swap pin-forpin, but I understand that there are different



JACK'S WORKSHOP Jack Armstrong

ike most people in the trade, I like to close my door in the evening and forget about work. Sometimes, unfortunately, this isn't possible. When the doorbell sounded at 9pm I knew it was another of these occasions.

"The pictures are all snowy, so will you mend our zapper again?" asked Mrs Wattle.

I was a little taken aback by this, but the two elderly ladies who live just across the road and like to call themselves "sisters" are quite inoffensive. So I agreed to do whatever was necessary to cure the "snowy pictures"

As I entered the house Miss Dorb handed me the remote-control unit. I

reflected on how unlike they were for "sisters", one plump with a button nose, the other very thin with a roman nose. "Pictures snowy. Must be that battery wire again" she said.

I pointed the device at the TV set and pressed a button at random. It had to be that way – the numbers had long ago worn off. A very grainy BBCI picture appeared, and the sound faded in and out of the background hiss.

"Well, the handset's OK but, oops." I had just dropped the thing on the floor and the 9V battery went spinning across the room, with its clips still attached.

"I'll just go and solder the wires back

on" I said sheepishly.

"Told you it was the battery wires" a know-it-all voice behind me said.

While I was in the workshop I also made up a coaxial lead from CT100 cable, with a male TV plug at each end. I had just bought some new screw-connection plugs and was quite keen to try them out and compare them with the cheap ones whose plastic insert melts when you try to solder the end of the centre pin (the trick is to file off the nickel plating to expose the brass). The new plugs were fine, though a little fiddly for someone with eyesight like mine!

When I returned to the Wattle and Dorb house I tried the remote-control unit. It was just fine. Then I pulled out the old, brown cable that connected the TV set to the wall socket and replaced it with my pristine white one. The pictures were perfect.

"Lovely" said Miss Dorb, "better than we've seen for ten years. How much do we owe you for the battery thing?"

The pair seemed to think that £2 was a little expensive for "fixing the zapper", but I pointed to the nice white cable and mentioned that the picture was, as Miss Dorb had said, "better than we've seen for ten years." They acquiesced, but I didn't get a tip. Must remember to charge a lot more next time. Maybe they won't ask again. I could recommend Wossname up Church Street, then they'd know the meaning of "dear".

A Grundig digibox

Talk of the devil! Who should wander in this morning than Wossname.

"Hello there. Not seen you for months. Been on holiday? Looking rather thin.'

"Yes, well, I've been away, you see."

"Good grief! Not in prison?" The light suddenly dawned on me. "What you been up to, you old rogue? Stealing chickens again?

"Not exactly. You know those bl**dy two dee mac cards?"

"D2Mac, yes."

"That's the fella."

"The ones you tried to sell me?" He looked sheepish, so I knew I was right. 'Got caught, did you?'

'Sort of. The guy in the pub - tall guy,



A Grundig GDS200 modem board – there are two versions, which are interchangeable.

you said 'hello' to him. Thought he must be OK if you knew him."

"Ah, you mean Bob the policeman. Went to school with him. Nice bloke, but funny ideas about right and wrong. You didn't sell him a card, did you? Wouldn't trust him with my grandmother."

"Sold him the lot. Next thing I know, I'm arrested. Shop's been closed for four months while I've been away. They took all the stock as evidence.'

"You won't see that again!"

"Too true. Anyway, I didn't come in to talk about me 'olidays. Could you take a look at this? Been struck by lightning she says."

I removed the screws and levered the top cover off the GDS200, cutting my finger in the process. I seem to manage to do that each time! Everything inside looked perfect.

"No lightning in here" I smiled.

"Course not. But it won't turn on. Try it."

I plugged it in and it didn't light up. Not even the little green LED inside. I replaced the power supply with a good one that I keep for testing, but it made no difference. On a hunch I removed the modem board, then reconnected the power lead. This time the digibox lit up its red and green LEDs and sequenced them off and on, which is normal when the modem is removed. When I fitted a spare modem board the digibox worked perfectly.

Since spares are available only to authorised agents, I contacted Gordon at Kesh Electrics to ask if he could fix the

modem board. He thought he might be able to, as he'd already repaired several of them. So this wasn't a new fault.

As it turned out, every chip on the modem board had apparently been damaged. Gordon was fortunately able to send me one that had come from an unrepairable GDS200. The price was very reasonable, and Wossname subsequently accepted my inflated estimate. He always manages to extort cash from his customers somehow!

Kesh Electrics can be contacted on 01365 631 449 and can carry out various digibox repairs.

The accompanying photograph shows a GDS200 modem board: two versions, which are interchangeable, have been fitted.

Amstrad DRX100

Last month I mentioned, foolishly, that I had never had capacitor failure with the DRX100 digibox's power supply. It has now happened to me, and I find that I'm not alone - lots of engineers have had this sort of trouble. The parts which fail are listed in the accompanying table.

Table 1: Relkit 34 components list.

C₃ C7, C22, C24, C25 C8, C10, C12 C11, C13-C18 C19, C20 D12

82µF,400∨ 33µF, 50∨ 1,000µF, 10∨ 330µF, 25∨ 220µF, 50∨ 1N4937

Thanks to some work done by Robert Philpot and other engineers from the TV email group, SatCure is now able to supply a capacitor kit for this model, Relkit 34. The items included are shown in Table 1 - the capacitors are all low-ESR types rated at 105°C. The kit costs £6.95 plus £2.50 postage and VAT at 17.5%. You can order from the SatCure website at http://www.satcure.co.uk

If you have any questions about Apple Macs you can e-mail Jack from the internet web site at: http://www.ukstay.com/jack

You can also contact Mac Users and ask questions at the Yorkshire Mac User Group web site (YMUG):

http://www.ymug.york.co.uk

Information about Sky Digital Satellite receivers can be found at:

http://www.satcure.co.uk

You can order Apple Mac cables, connectors, batteries and other accessories from the SatCure web site at: http://www.satcure.com

Test Case 466

Nora Wilkins was in a fix. On impulse, she had bought a £40 small-screen black-and-white TV set for use in her kitchen. She spends a lot of time there, cooking and baking for her dos in aid of local charities. When she got the set back she plugged it in, extended the aerial and wound the tuning knob from one end to the other. But all she obtained was a flickering, snowy, barely-recognisable shadow, at just one point. She returned it and had been given another one, but the results were no better - until she took it to her friend Gwen's house on the other side of town. There, it produced much better, though rather ghosty, images on all the local channels.

Now Nora, a widow, is not rich, and thought that her local dealer might be unable to help anyway. But didn't she live opposite that nice young man Cathode Ray, and didn't Ray owe her a favour, having almost run over her cat the other day with that big white van of his? She went to see Ray and invited him in for a cup of tea, and to "just tune in" her little TV set

The cat, knowing that Ray doesn't like him, abandoned the kitchen as soon as he arrived. The area is not a good one for TV reception, and Ray was not surprised that virtually no signals could be obtained from the built-in telescopic aerial. But what was this? A coaxial cable was coiled up in the corner of the window sill, and there was a coaxial to mini-jack adaptor

in the TV box. They were very soon assembled, after which Ray confidently switched on the little TV and wound its tuning knob - only to find that things were little better than before. There was virtually no signal! He was told that reception was OK in Nora's living room, so they took the little set there and hooked it up. It now produced reasonable pictures and sound, though its RF gain seemed to be less than that of the main set and its tuning knob was very fiddly. A check in the bedroom, where another aerial cable came through a hole in the ceiling, showed that here too the signals were failing to get through.

The aerial cable in the lounge was looped through a mains power unit that looked very ancient. It must have been providing the 18-24V its yellowing case boasted, or there would have been no signals at all, Ray reasoned. So suspicion fell on the three-way UHF distribution amplifier that was taped half-way up the aerial mast. It would have to be replaced and, after acquainting Nora with the £27-odd cost, Ray ordered a threeway outdoor type from the Whizzo Electronics catalogue in the workshop. It arrived very quickly, and Ray didn't have too much trouble fitting it. The short chimney stack and mast were accessible from the garage roof: step-ladder stuff!

Back indoors, Ray switched the power to the mains unit on then turned on the living-room set to admire the result of his handiwork. All he got was a screenful of snow on all channels. The kitchen and bedroom outlets were likewise dead! What was the cause? There was nothing wrong with Ray's wiring, and the Whizzo unit was perfectly OK. For the solution, turn to page 760.



SATELLITE NOTEBOOK

Reports from Christopher Holland and Tony Cattell

BBC satellite radio

In his column in the August issue Donald Bullock mentioned that his digibox often goes into standby after a power cut. When this happens during the night he doesn't get the BBC radio service of his choice, to which the receiver was left tuned the night before, when he wakes up. He didn't have this problem with his previous analogue receiver.

One way around this problem is to use the single-receiver version of the Kesh Electrics Digimemo unit I reviewed in the December 2000 issue of *Television*. You enter the station you require as the 'favourite channel' and the unit returns the digibox to this after a power supply interruption. Details of the unit can be obtained from the Kesh Electrics web site (www. pacelink.co.uk).

As the BBC Radio stations, except for Radio 5 which is encrypted, are all transmitted in clear digital form, a good solution to the problem is to buy a simple digital receiver that isn't capable of receiving encrypted channels. A good thing about such receivers is that they usually return to the station being received prior to a power cut, though it's as well to confirm that this is so before you make the purchase. The new receiver can be connected to the same dish, pointing at $28 \cdot 2^{\circ}$ E, via a twin LNB. An advantage of this arrangement is that the radio stations continue to be available when someone is watching the telly.

A fairly well-kept secret is that the BBC is still transmitting its radio services, with the exception once again of Radio 5, in analogue form from 19·2°E. Tune to the CNBC transponder at about 10·728GHz (vertical polarisation) and you will find Radio 3 at 7·56MHz, Radio 4 at 7·74MHz and the World Service at 7·38MHz. Tune up the band to 11·243GHz (horizontal polarisation), the German RTL Shop transponder, and you will find Radio 1 at 7·74MHz and Radio 2 at 7·92MHz. These transmissions are all in mono. For how long they will continue to be available remains to be seen.



Photo 1: Test card J, seen recently at 12-129GHz V.

Don't despair too much about TV in the morning, Donald. Look what I found recently on the BBC Parliament channel (at 12·129GHz V, transponder 22), see Photo 1. A real live test card! Unfortunately it was accompanied by a test tone, not the test card music of the Fifties and Sixties. Surely, with all the digital space the BBC has available at its three 28·2°E digital transponders, there should be room for a permanent test card! C.H.

Digital TV update

There have been quite a few changes since our last complete listing (February, pages 236/7) of the transponder allocations at $28 \cdot 2^{\circ}$ E. Table 1 shows the situation at mid-August, when this issue of *Television* was being prepared for publication. Note however that channels can alter quickly. The transponder number is in brackets after the frequency and the EPG number in brackets after the channel name. It seems quite likely that Astra 2D's three ITV transponder allocations will become active during the next few months.

Transponder 4 is the digibox default frequency. Add 700 to the Box Office numbers. Some channels are listed at more than one frequency: only one will be the 'active' channel in the EPG at any one time, though Sky can change this round rapidly.

Cards with a Welsh address place S4C at EPG 104, Channel 4 at 184. The correct BBC1 and 2 regions for the viewing card's address are at EPG 101 and 102. Out-ofarea BBC2 regions are available at 964/5/6. Out-of-area BBC1 regions are not available at present though there seem to be plans to make them available at 967/8/9 – these numbers are mentioned in the spoken audio "channel line up" on 996.

The correct Channel 4 region is brought in at 104 by the viewing card (184 in Wales), but out-of-area regions can be stored as 'extra channels'.

Viewing cards in the Republic of Ireland bring in Sky 1 Eire at 106 and BBC 1 and 2 Northern Ireland at 214 and 215. Other BBC channels are not available there, nor are the UK Channels 4 and 5. Sky News Eire is allocated to ch. 501. With the exception of World Service, BBC radio stations are not listed in the Irish EPG, but can be stored as 'extra channels'. Radio 5 is not available.

The Irish channel Tara TV (EPG 178), which is aimed at UK-based viewers, has recently been blocked to Irish viewing cards. C.H.

Amstrad DRX100

This digibox was dead. Yes, an Amstrad that didn't need the tuner replaced for a change! The cause of the fault turned out to be Q1, which is type 1L0380R. It's not the easiest device to obtain from the usual spares suppliers but can be obtained from SatCure, whose e-mail address can be found at the company's web site www. satcure.co.uk **T.C.**

Table 1: Digital transponder listing.				
5	0.4			
Frequency	Sat/	Pol	Channels and EPG numbers	
[012]	Deani			
10.862 (51)	2D/UK	н	Disney (613), Disney Plus (614), Toon Disney (615), Playhouse Disney (616), Playiam Interactive	
10-876 (52)	2D/UK	V	Box Office (5, 10, 15, 19, 20, 25, 30, 40, 46, 54)	
10-921 (55)	2D/UK	н	Sky Travel (145), Tara (178), Hallmark (190), Kerrang (457), Starplus (672), Box Office (36-39)	
10-936 (56)	2D/UK	V	Sky Sports Extra (404)	
11.508 (D3S)	EB	н	Discovery Home & Leisure +1 (134), Smash Hits (451), Animal Planet +1 (571)	
11.585 (D7S)	EB	Н	Fashion (220)*, Best Direct (644)*, MBI (698), AI Jazeera *†	
11.680 (D12S)	EB	V	Extreme Sports (422)*, Go Barking Mad (425)*, Digital Classics (464), Euronews (528)*, God (650)*, TBN (652)*	
11.720 (1)	2A/S	н	BBC1 England/N. Ireland (101), BBC2 England (102), BBC Choice (160), BBC News 24 (507), BBC Knowledge (573).	
11.739 (2)	2A/S	V	Living (112), Challenge (121), Bravo (124), Trouble (607), Travel Shop (632)*	
1 <mark>1</mark> .758 (3)	2 A /N	н	Channel 5 (105), Sky Sports 1, 2, 3 (401/2/3), Premiership Plus (433), God Revival (651)	
11.778 (4)	2 A /N	V	EPG background audio, Box Office 18†, 47, 48, 59, Box Office Widescreen 1, 2, No 5, Sky Enquiries Interactive	
11.798 (5)	2A/S	н	BBC1 Wales/Scotland (101), BBC2 Wales/Scotland/N. Ireland (102), all BBC Radio stations	
11.817 (6)	2A/S	V	UK Gold 1 (109), UK Gold 2 (110), UK Style (148), UK Drama (151), Play UK (217), UK Horizons (564), UK Horizons +1 (565)	
<mark>1</mark> 1⋅836 (7)	2 A /N	Н	Sky 1 (106), Premier 1 (301), Premier Widescreen (305), MovieMax (308), Box Office 1-4	
<mark>11.85</mark> 6 (8)	2 A /N	V	Premier 2 (302), MovieMax 2 (309), Sky Sports News (413), Nat Geographical (558), Box Office 6, 7	
1 <mark>1.</mark> 876 (9)	2A/S	Н	Discovery (551), Discovery +1 (552), Adventure (553), Civilisation (554), Sci Trek (555), Wings (556), Discovery Kids (618)	
11.895 (10)	2A/S	V	Paramount (127), all MTV/ VH1 channels (440, 441, 443, 444, 446, 447, 448), Nick Junior (605)	
11.914 (11)	2 A /N	Н	Premier 3 (303), MovieMax 3 (310), Sports 3 (403), Box Office 11-14	
11.934 (12)	2 A /N	V	Premier 4 (304), MovieMax 4 (311), Sky Sports 1, 2, 3 in pubs‡, Box Office 16-18, Playboy/Adult (974), Retail Info (997)‡	
11.954 (13)	2A/S	Н	Travel Shop 2 (633)*, Screenshop (640)*, Dating (656)*, TVX (977), Red Hot (989-991)	
11.973 (14)	2B/S	V	Sony TV Asia (670), Zee Cinema (678), Bangla (679), Pakistani (680), Asia 1 (682)*	
11.992 (15)	2B/N	Н	Open Shopping	
12.012 (16)	2 A /N	V	Open Shopping	
12.032 (17)	2B/S	Н	ITN News (525)*, QVC (630)*, Ideal World (638)*, Bid up (647)*, Jobshop (654)*, B4U Music (668)*, Lashkara (691), ITN Radio News (878)*, <i>QVC Interactive</i>	
<mark>12.05</mark> 1 (18)	2A/S	V	Travel (181)*, TCM (327)*, CNN (513)*, Cartoon channel (601), Boomerang (603)*, Shop (634)*, CNN Radio*.	
12.070 (19)	2B/N	Н	Sky 1 Ireland (106), Sky Cinema (315), Sky Sports Extra (404), Cartoon Network +1 (602), Box Office 21-4	
12.090 (20)	2 B /N	V	Sky Cinema (315), Sky Cinema 2 (316), Rapture (458), Disney Channel (613), Box Office 26-29	
12.110 (21)	2B/S	Н	Channel Health (193)*, Shop America (641)*, UCB Europe (875)*, UCB Cross Rhythms (876)*, UCB Inspirational (886)*, Bible (890), UCB Talk (891)*	
<mark>12·</mark> 129 (22)	2A/S	V	S4C (104, 184), BBC Parliament (508)*, S4C 2 (519)*, Einstein (576)*, Simply Shopping (643)*, B4U Movies (667), Zee (676), Simply Shopping Interactive	
12·148 (23)	2 A /N	н	Granada (118), Sky Sports News (413), Bloomberg (504), Nick (604), Box Office 31-5	
12·168 (24)	2 A /N	V	Channel 4, 6 UK regions, (104), E4 (205), Film 4 (323-6), E4 Ineractive	
12·188 (25)	2B/S	Н	Music Choice (480/1), History (561), Biography (563), Sky Latest Ireland (999)	
12.207 (26)	2B/S	V	Sky News (501)*, History +1 (562), Channel line up (996)*, Sky Welcome (998)	
12.226 (27)	2A/N	Н	Breeze (136), Men & Motors (139), Racing channel (416), History channel (561), Box Office 41-5	
12.246 (28)	2B/N	V	Upen Shopping MarijaMari 5 (2011), Kias (450), Fari Kida alia 1 (2011), Davi Offica (2050, Divisio Divisio (2000), Datailija fa	
12.200 (23)	20/5	п	Ireland (997)‡	
12.285 (30)	2B/S	V	Game Network (223)*, Energis promo	
12-303 (31)	2B/N	H	Open Shopping Mollhaine (2011) CNRC (510) Manage (510)* Advanture Open (500) Minnie (257)* Telly Sport (259)	
12.324 (32)	28/19	v	Capital Gold (863)*, XFM (864)*, Youth FM (871)*, Premier (873), Heart FM (874)*, One Word (877), Storm Live (881)*, Primetime (882), Sunrise (833)*, Talk Gospel (884), The Storm (887), TWR (888)*, Real Radio (896)*, Costcutter*, Sky News Radio*	
12-344 (33)	2B/S	н	Liberty (202)*, Magazine Showcase (208), Pin (636)*, Gurjari (692), CEE I (693), Anjuman (694), Classic FM (856)*, Classic Gold (859)*, Planet Rock (861)*, Core (862)*, WRN (872)*, Solar Radio (879)*, Punjab (880)*, Total Rock (885)*, LBH (889)*, RTE Radio (892)*, Asian Air (893)*, Club Asia Radio*†, EWTN*†, SSR Radio*†	
12 <mark>·36</mark> 3 (34)	2B/S	V	Nat Geographic +1 (559), Nick replay (605), Star News (671), Box Office 18†, 1-4, Sky Business/Pub Channel‡	
12-382 (35)	2B/N	Н	Eurosport (419), The Box (449), Q Music (455), Community ch (655)*, Sky Movies Active	
12.402 (36)	2B/N	V	Where it's at (461), SBN Radio*†	
12.422 (37)	2B/S	H	Prime TV (685), Teletext Holidays	
12.441 (38)	2B/S	V	BBC Sport Interactive	
12.460 (39)	2B/N	H	Sky Sports Extra (404)	
12.480 (40)	28/N	V	Artsworid (199), IVIU I V (410), Uneisea I V (427), Maydoy (981), Spice (982)	
2A = Astra 2A, 2B =	= Astra 2B, 2	D = Astra 2D	, EB = Eurobird, UK = UK footprint, N = North footprint, S = South footprint.	

Interactive services shown in italics. * Unencrypted. † No EPG no. allocated. ‡ Channel not available with a normal domestic viewing card.



site space contact Pat Bunce 020 8770 201 -MAILS p.bunce@cumulusmedia.co. Fax: fo reserve your web fel: 020 8722 6028

AcquiVision

http://www.acquivision.com

Acquivision solutions, including XY-Plotting, Oscilloscope (with FFT), Data Logging and Custom Software, have been getting the most from computers since 1994, Download software. Telephone (01903) 830502

Alltrade

http://www.alltrade.co.uk



Phone 01273 413798 Fax 01273 425700

Full e-commerce site with over 1500 products with in-stock quantities!! We supply everything associated with Digital/Analogue Terrestrial & DTH/Motorised Satellite reception. All Antennas. All Brackets. All Cables. All Connectors. All Amplifiers. We provide a free MATV/SMATV planning service as well.

A.R.D. Electronics Plc

http://www.ardelectronics.com



A.R.D.'s Website details all the information you need to know about this new and exciting electronic component distributor. It shows how to: open an account (credit or cash), obtain a trade catalogue and place orders (both online and direct)

Baird 30 Line Recordings

http://www.dfm.dircon.co.uk

For history buffs and the curious here's a tascinating site containing early TV recordings and their background.

BBC

http://www.bbc.co.uk/enginfo If you need any help with your reception go to this site – both of the addresses point here. There's special advice for people with loft installations, and caravaners and boating enthusiasts.

Doknet Service manuals

http://www.doknet.com

This Dutch site says it has 350,000 service manuals and 1 million service parts. You interogate the data base by filling out an order form, with the "request" box ticked, and then wait for an email to arrive back on your computer. However, an on-line index would be useful and maybe on-line downloading of the manuals.

Dönberg Electronics

http://www.donberg.ie



As the leading distributor for the TV, Video and Audio trade in Ireland, we supply over 2000 shops & service dept with Audio-Video and TV spares, Semiconductors, Test Equipment, Service Manuals, Remote Controls etc. At present we stock over 30,000 different lines

EURAS International Ltd

http://www.euras.com/english

"The definitive fault index... based on feedback from manufacturers, technicians and workshops throughout Europe" IER Magazine. Available on CD-ROM including ECA vrt-disk 2000. Subscription includes free Internet access for update downloading, access to pin board, discussion forums and classified ad section. Monitor database also available.





Goot Products

http://www.kieagoot.co.uk

Kiea Trading Company is the sole agent of Goot products, We specialise in supplying the soldering and desoldering product range manfactured by Goot Japan for the UK market. Goot uses advanced production technology to manufacture high quality soldering iron products for industrial, prfessional and general purpose use.

Matrix Multimedia Ltd

http://www.matrixmultimedia.co.uk



Matrix Multimedia publishes a number of highly interactive CD ROMs for learning electronics including: Complete electronics course, Analogue filter design, and PICmicro(R) microcontroller programming (C and assembly).

M.C.E.S.

http://www.mces.co,uk

The MCES site gives details of our range of service including Tuners, Video Heads, RF & IF Modules plus latest prices and special offers.

NTL

http://www.ntl.co.uk

Go to this site for information on NTL's Broadcast, Interactive and Telecom services, including packages for home area by area. There's also a useful transmitter site map and database, giving locations and information. The site also contains useful documents,



which describe digital TV, interactive TV and digital Radio. There's also a useful contacts list.

Mauritron Technical Services

http://www.mauritron.co.uk

The UK's leading independent supplier of Service Manuals and Operating Guides from valve to video. Also available on CD Rom or download direct from the internet.

PC Universe

http://www.pc-universe.net



PC Universe supplies core computer components at "WORLD-beating" prices. Our range of reliable brand name products is available to order online 24-7.

Nationwide delivery. Free Tech support at all levels. Call LO Call 0845 4585817

Sky digital repairs

http://www.horizonsatellites.co.uk

The Horizon site gives details of our range of products and services including Sky Digital Receiver Repairs.

Servicing Advice

http://www.repairfaq.org/REPAIR/ F_Repair.html

Here are some frequently asked questions about servicing consumer electronic equipment, with a US bias. But there's some good material on monitors and CD players and CD-ROM drives. (thanks to David Edwards for this information)



Switch-it-on

http://www.switch-it-on.co.uk

We sell multiregion dvd players to trade and public, also tv, videos, hifi and playstation 2. We design our own upgrades on dvd and we sell all spare parts. All makes and most models stocked.

Service Engineers Forum

http://www.E-repair.co.uk

The forum is now visited by Thousands of engineers every week, over 3000 pages of content including new repair tips, servicing articles, circuits, help, for sale, wanted & industry news sections, open access to the site is free to all engineers.

Our product mailing list is also available free of charge for engineers without net access, ring Mike on 0151 522 0053 with your address details.

Televes

http://www.televes.com/ingles/ ingles.htm

Televes website was launched as an easier way to keep in contact with our World-wide Network of Subsidiaries and Clients. This site is constantly updated with useful information/news plus you can download info on our range: TV Aerials & accessories, Domestic and Distribution amplifiers, Systems Equipment for DTT and Analogue TV, Meters and much more.



The Service Engineers Forum

http://www.E-repair.co.uk.

A brand new site dedicated to the needs of service engineers containing detailed servicing articles, circuits & repair tips. The site also includes for sale, wanted & special offer sections, industry news & much more. An impressive site well worth visiting.

For customers without net access, servicing product details are also available by ringing Mike on 0151 522 0053

UK Electrical Direct

http://www.uked.com

For a comprehensive on-line directory, buyers guide and resource locator for the UK Electrical Industry look at this site. Many of the companies listed have links to their own web sites, making this a one-stop shop for a huge amount of information.

UK Mailing List Group

http://www.egroups.com/list/uktvr epair

Following on from the newsgroup discussion last month there is a UK Email group for TV technicians where you can



Put your web address in front of 21 000 electronics enthusiasts and experts. *Television* acknowledges your company's need to promote its web site, which is why we are how dedicating pages in every issue to announce your

WEB ADDRESS.

This gives other readers the opportunity to look up your company's name, to find your web address and to browse the magazine page to find new sites. send an Email to everyone in the group. There's just over 30 people in the group at present. For more details and how to register look at the egroup home page. Just a general comment though - you do have to be careful who you give your Email address to so that you can avoid "spamming" - that is getting lots of unwanted Email about dubious Russian site (amongst others).

PSA

http://www.psaparts.com



This web site gives details of various specialist parts for repairers, from rare semiconductors to compute batteries and printer parts. The vast majority of items are in stock, and can be purchased online via this site's shopping facility.

Repairworld

http://www.repairworld.com

Repairworld is a US based fault report database which is updated bi-weekly. It operates on a subscription basis and describes itself as an "affordable solution for all technicians". There is apparently no minimum number of months for which you have to subscribe.

We understand that cost is an important factor, as web sites are an added drain on budgets. But we are sure you will agree that the following rates make all the difference:

FOR 12 ISSUES:

Lineage only will cost £150 for a full year, just £12.50 per month. This includes your company's name, web address and a 25-word description. Lineage with colour screen shot costs £350 for You can see some samples of the material for free, monitors, VCR, DVD and Camcorders being of particular relevance to UK users. The site provides a "chat room" where you can talk via your keyboard to others "in the room".

Vintage Wireless Co London

http://www.vintagewirelesslondon. co.uk

Phone 0207 2583448 Fax 0207 2583449



Supplies of vintage hi-fi, wireless, sales & service, spare parts, valves, components, transformers, knobs, ceramic cartridges, stylus and more. Vintage hi-fi litreture, magazines, circuits. Wanted tannoys & early hi-fi audio valves for cash.

To reserve your web site space contact Pat Bunce Tel: 020 8722 6028 Fax: 020 8770 2016

a full year, which equates to just $\pounds 29.17$ per month.

This price includes the above mentioned information, plus a 3cm screen shot of your site, which we can produce if required.

To take up this offer or for more information ring:

Company name	Web address	Web address	

Special Offer Sale - 20 Remote Controls £20.00 (mixed all well known brands)

	N ICC	7 HAND SET	£3.00
FERGU	SON	VIDEO	
FV90 LV H	AND S	ET	£3.00
FV80 LV H	AND S	ET	£3.00
FERGUSO	N		
BATTERY	CONV	ERTER TA606	£15.00
24V DC/24	JV AC		£15.00
D JOY 14	TWERS	WETERS	JE
0-30 V 37	r- 1 AA 11	P/P FS 00	en 650.00
BRIDGE R	ECTIFI	ERS 10	FOR £1.00
BURGLAR	ALAR	M KIT full descrip	tion £7.00
CAMCORE	ER-UI	VIVERSAL BATT	ERY 9.6V -
1400MA	FOR J	VC-PANASONIC-	PHILIPS
CUNCORE			£5.00
CAPACITO	DC.	POD SHOULDER	POD \$3.00
IIN/2KV	2N7/2	KV 4N7/4KV	EACH 15n
5N6/2KV	6N2/2	KV. 9N1/2KV	EACH 15p
35V-22U	F, 50V-	4 7UF, 50V-100UF	
			EACH 25p
AA BATTE	RIES I	.5 VOLT	
STC ALKA	LINE	D	10p
DIGITAL		P TANCE METER (£2.00
200PF-20	MF	TANCE METER .	£28.00
FILTERS -	455 &	480	EACH 10p
GAS SOLD	ER IRC	ON-PORTASOL H	OBBY
			£10.00
INFRA REI	D DETI	ECTOR	
WIDE/SH	IORT /	NGLE WITH RE	LAY £5.00
INFRA REI	D KECI	EIVER-MAISUM	61.00
MILLI VOL	TMET	ER-ELECTRONIC	LEADER
LMV-181	A 40V	A/C IN-IMV F/S	
		£5	P&P £5.00
IMV-300	VCAL	IBRATED ~	_
		COST £225	.00 £5 P&P
COLOUR I	V BAI	TERY	LOUT
CONVER	(IEK I	N 24VDC TO 2401	£14.00
MODULAT	OR-TI	INABLE SATELL	TE TH
MODULAI			£1.00
PANEL-IK2	-FM22	III STEREO	£1.00 £5.00
PANEL-IK2 PANEL-CV	-FM22 C80-PC	TH STEREO	£1.00 £5.00 £5.00
PANEL-IK2 PANEL-CV POSITOR I	-FM22 C80-PC 8 2 PD	TH STEREO DWER	£1.00 £5.00 £5.00 20p
PANEL-IK2 PANEL-CV POSITOR I POSITOR-2 POWTER SU	-FM22 C80-PC 8 2 PD 322 66	111 STEREO DWER 1 2 98012	£1.00 £5.00 £5.00 20p 50p
PANEL-IK2 PANEL-CV POSITOR 1 POSITOR-2 POWER SU 12V DC 6	2-FM22 C80-PC 8 2 PD 322 66 PPLY	III STEREO DWER 2 98012 	£1.00 £5.00 £5.00 20p 50p
PANEL-IK2 PANEL-CV POSITOR I POSITOR-2 POWER SU 12V DC & POWER SU	2-FM22 C80-PC 8 2 PD 322 66 PPLY & 24V PPLY-	11 STEREO DWER 2 98012 - DC-REGULATED 3-12	£1.00 £5.00 £5.00 20p 50p £2.00 2V 500MA
PANEL-IK2 PANEL-IK2 POSITOR I POSITOR-2 POWER SU 12V DC & POWER SU	-FM22 C80-PC 8 2 PD 322 66 PPLY & 24V PPLY-	11 STEREO DWER 2 98012 - DC-REGULATED REGULATED 3-12	£1.00 £5.00 £5.00 20p 50p £2.00 2V 500MA £5.00
PANEL-IK2 PANEL-CV POSITOR I POSITOR-2 POWER SU 12V DC & POWER SU PSU AC 12'	-FM22 C80-PC 8 2 PD 322 66 (PPLY & 24V (PPLY- V 500M	11 STEREO OWER 2 98012 - DC-REGULATED REGULATED 3-1:	£1.00 £5.00 £5.00 20p 50p £2.00 2V 500MA £5.09 £1.50
PANEL-IK2 PANEL-CV POSITOR I POSITOR-2 POWER SU 12V DC & POWER SU PSU AC 12' PSU AC 12' PSU AC 9V	2-FM22 C80-PC 8 2 PD 322 66 PPLY & 24V PPLY- V 500M IA	2 98012 	£1.00 £5.00 £5.00 20p 50p £2.00 2V 500MA £5.08 £1.50 £1.50
PANEL-IK2 PANEL-CV POSITOR 1 POSITOR-2 POWER SU 12V DC 4 POWER SU PSU AC 12' PSU AC 12' PSU AC 9V QUARTZ 1H	2-FM22 C80-P(8 2 PIN 322 66 (PPLY & 24V (PPLY- V 500N IA ALOG OV FOI	2 11 STEREO DWER 2 298012 	112-1 V £1.00 £5.00 £5.00 20p 50p £2.00 2V 500MA £5.09 £1.50 £1.50 £1.50
PANEL-IK2 PANEL-CV POSITOR 1 POSITOR-2 POWER SU 12V DC 4 POWER SU PSU AC 12' PSU AC 12' PSU AC 9V QUARTZ 11 500W 200	2-FM22 C80-P(8 2 PI) 322 66 PPLY 24V PPLY- 24V PPLY- 1A ALOG 0V FOI BLOC	2 98012 - C.REGULATED REGULATED 3-1: 1A EN R OUTDOOR LAN	112-1V £1.00 £5.00 20p 50p £2.00 2V 500MA £5.00 £1.50 £1.50 £1.00 £5.00
PANEL-IK2 PANEL-CV POSITOR 1 POSITOR 2 POWER SU 12V DC 4 POWER SU 12V DC 4 POWER SU PSU AC 12' PSU	-FM22 C80-PC 8 2 PD 322 66 PPLY & 24V PPLY- V 500M IA ALOG OV FOI BLOC UB MII	II STEREO DWER 2 98012 - DC-REGULATED REGULATED 3-1: 1A EN R OUTDOOR LAN	112-1V £1.00 £5.00 £5.00 20p 50p £2.00 2V 500MA £1.50 £1.50 £1.50 £5.00 25p
PANEL-IK2 PANEL-CV POSITOR I POSITOR-2 POWER SU 12V DC 6 POWER SU PSU AC 12' PSU AC 9V QUARTZ IH 500W 200 R.S. SAFE I RELAYS-ST SATELLJT-	-FM22 C80-PC 8 2 PD 322 66 PPLY & 24V PPLY- V 500M IA ALOG 0V FOI BLOC UB MID TUNI	II STEREO DWER 2 98012 - DC-REGULATED REGULATED 3-1: 1A EN R OUTDOOR LAN NIATURE SR UNIT - 242761	£1.00 £5.00 £5.00 £5.00 20p 50p £2.00 2V 500MA £5.00 £1.50 £1.50 £1.50 £1.50 £1.50
PANEL-IK2 PANEL-CV POSITOR-1 POSITOR-2 POWER SU 12V DC / POWER SU PSU AC 12' PSU AC 9V QUARTZ H \$500W 200 R.S. SAFE J RELAYS-SI SATELIJT	P-FM22 C80-PC 8 2 PD 322 66 PPLY 24V PPLY- V 500N IA ALOG 0V FOI BLOC UB MII 5 TUNI E BAN	II STEREO DWER 2 98012 - DC-REGULATED REGULATED 3-1: 1A EN R OUTDOOR LAN NIATURE ER UNIT - 242761 D/VIDEO OUT	£1.00 £5.00 £5.00 £5.00 20p 50p £2.00 2V 500MA £5.09 £1.50 £1.50 £1.50 £1.50 £1.50 £1.50 £1.00 £5.00
PANEL-IK2 PANEL-CV POSITOR 1 POSITOR 2 POWER SU 12V DC 4 POWER SU PSU AC 12' PSU AC 12' PSU AC 22' QUARTZ H 500W 200 R.S. SAFE 1 SATELIJTI BAS SCART TO	P-FM22 C80-PC 8 2 PD 322 66 PPLY 24V PPLY- V 500N IA ALOG DV FOI BLOC UB MII 5 TUNI E BAN 4 PHO	ILI STEREO DWER 2 98012 	112-1V £1.00 £5.00 £5.00 £5.00 £0p 50p £2.00 2V 500MA £5.00 £1.50 £1.50 £1.50 £1.50 £3.00 £3.00 £3.00 £3.00
PANEL-IK2 PANEL-CV POSITOR 1 POSITOR 2 POSITOR 2 POWER SU I2V DC 4 POWER SU PSU AC 12' PSU AC 12' PSU AC 12' PSU AC 12' PSU AC 12' PSU AC 12' PSU AC 12' SU QUARTZ H SOW 200 R.S. SAFE 1 BASS SCART TO SCART TO	2-FM22 C80-PC 8 2 PD 322 66 PPLY 2 24V PPLY- V 500M IA ALOG DV FOI BLOC UB MII 5 TUNI E BAN 4 PHO 6 PHO 6 PHO	ILI STEREO DWER 2 98012 	112-1V £1.00 £5.00 £5.00 £5.00 £5.00 £0p 50p £2.00 2V 500MA £5.00 £1.50 £1.50 £1.50 £1.50 £3.00 £3.00 £3.00 £3.00
PANEL-IK2 PANEL-CV POSITOR 1 POSITOR 2 POWER SU 12V DC 4 POWER SU PSU AC 12' PSU AC 12' PSU AC 12' PSU AC 12' PSU AC 12' PSU AC 12' PSU AC 12' SATELIJTI BSU AC 9V QUARTZ H SOW 200 R.S. SAFE 1 SATELIJTI BAS SCART TO SCART TO SCART TO	2-FM22 C80-PC 8 2 PIP 322 66 7 PIPLY 2 24V PIPLY- V 500M 1 A ALOG 0V FOI BLOC UB MII 5 TUNI E BAN 4 PHO 6 PHO "D" PI SCAR	ALL STEREO DWER 2 98012 	112-1V £1.00 £5.00 £5.00 £5.00 £5.00 £0p 50p £2.00 £2.00 £2.00 £2.00 £2.00 £2.00 £1.50 £1.50 £1.50 £5.00 25p 1 £3.00 £3.00 £1.00
PANEL-IK2 PANEL-CV POSITOR 1 POSITOR 2 POWER SU 12V DC 2 POWER SU PSU AC 12' PSU AC 9V QUARTZ 14 SOCKT TO SCART TO SCART TO SCART TO SCART TO	I-FM22 C80-PC 8 2 PDL 322 66 PPLY 322 67 PPLY 4 2 24V V 500M I A ALOG OV FOI BBLOC UB MII 5 TUNI E BAN 4 PHO 6 PHO 6 PHO 5 CAR' S CON	11 STEREO DWER 2 298012 	112-17 £1.00 £5.00 £5.00 20p 50p £2.00 £2.00 £1.50 £1.50 £1.50 £1.00 £5.00 25p 1 £3.00 £3.00 £3.00 £3.00 £3.00 £1.00
PANEL-IK2 PANEL-CV POSITOR 1 POSITOR 2 POWER SU 12V DC 2 POWER SU 12V DC 2 POWER SU PSU AC 12' PSU	I-FM22 C80-PC 8 2 PDL 322 66 PPLY 322 67 PPLY 4 232 60 PPLY 4 PPLY- PLY- PLY- PLY- PLY- PLY- PLY- PLY	ILI STEREO DWER V 2 98012 	112-17 £1.00 £5.00 £5.00 20p 50p £2.00 £1.50 £1.50 £1.50 £1.50 £1.00 £5.00 25p 1 £3.00 £3.00 £3.00 £3.00 £1.00
PANEL-IK2 PANEL-IK2 POSITOR 1 POSITOR 2 POWER SU 12V DC 4 POWER SU 12V DC 4 POWER SU 12V DC 4 POWER SU 12V DC 4 POWER SU PSU AC 9V PSU AC 9V QUART2 H SOUW 20 SCART TO SCART TO SCART TO SCART TO SCART TO SCART TO SCART TO SCART TO	-FM22 C80-PP 8 2 PP 332 66 PPLY- 322 67 700 PPLY- 500 V V 500 V V V V	ILI STEREO DWER V 2 98012 	F1.00 £1.00 £5.00 £5.00 £5.00 £5.00 £0p 50p \$0p £00 \$0p £00 \$0p £00 \$0p £00 £1.50 £1.50 £1.50 £1.50 £3.00 £3.00 £3.00 £3.00 £3.00 £1.00 £3.00 £1.00 £1.00 £3.00 £1.00 £3.00 £1.00 £3.00
PANEL-IK2 PANEL-CV POSITOR-2 POSITOR-2 POSITOR-2 POWER SU I2V DC 4 POWER SU PSU AC 12' PSU AC 12' P	2-FM22 C80-PP 8 2 PP 332 66 PPLY- 322 67 72 24V PPLY- 72 24V 70 24V 7000000000000000000000000000000000000	ILI STEREO DWER V 2 98012 	112-1V £1.00 £5.00 £5.00 £5.00 £5.00 £0p 50p £2.00 2V 500MA £5.09 £1.50 £1.50 £1.50 £3.00 £3.00 £3.00 £3.00 £3.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00
PANEL-IK2 PANEL-IK2 POSITOR-1 POSITOR-2 POSITOR-2 POWER SU 12V DC 4 POWER SU PSU AC 12' PSU AC 12'	-FM22 C80-PK 8 2 PDF 8 2 PDF 9 2 24V PPLY- V 500M 1A ALOGO BLOC UB MII 5 TUNN E BAN BLOC UB MII 5 TUNN E BAN BLOC UB MII 5 TUNN E BAN MHZ N MHZ N MHZ N RMER-	A STATE OF	F1.00 £1.00 £5.00 £5.00 £5.00 £5.00 £0p 50p £2.00 2V 500MA £5.00 £1.50 £1.50 £1.50 £3.00 £3.00 £3.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £2.00 £1.00 £1.00 £2.00 £1.00 £1.00
PANEL-IK2 PANEL-IK2 POSITOR-1 POSITOR-2 POSITOR-2 POWER SU 12V DC <i>i</i> POWER SU PSU AC 12' PSU AC 12' PSU AC 12' PSU AC 22' PSU AC 9' PSU AC	-FM22 C80-PC 8 2 PD 8 2 PD 9 2 24V PPLY- V 500M 1 A ALOGO BLOC UB MII 5 TUNI E BAN BLOC UB MII 5 TUNI E BAN BLOC UB MII 5 TUNI E BAN MHZ N MHZ N MHZ N MHZ N MHZ N MHZ N	ILI STEREO DWER V 2 98012 	F1.00 £1.00 £5.00 £5.00 £5.00 £5.00 £0p 50p £2.00 20p 2V 500MA £5.00 £1.50 £1.50 £1.50 £1.50 £3.00 £3.00 £3.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00
PANEL-IK2 PANEL-IK2 POSITOR 1 POSITOR 2 POSITOR 2 POWER SU 12V DC 2 POWER SU PSU AC 12' PSU AC 12' SOWER SU SOWER SU SOWER SU SOWER SU SOWER SU SOURD S.5 SOUND 5.5 SOUND 5.5 SOUND 5.0 SOUND 5.5 SOUND 5.0 SOUND 5.1 SOUND	-FM22 C80-Pc(82 Pt) 322 66 PPLY- 322 67 PPLY- 70 PPLY- 70 PPLY- 7	ILI STEREO DWER 2 98012 	F1.00 £1.00 £5.00 £5.00 £5.00 £5.00 £0p 50p £2.00 £2.00 £2.00 £2.00 £1.50 £1.50 £1.50 £1.50 £3.00 £3.00 £1.00
PANEL-IK2 PANEL-IK2 POSITOR 1 POSITOR 2 POSITOR 2 POWER SU 12V DC 2 POWER SU 12V DC 2 POWER SU PSU AC 12' PSU AC 9' SATELLIT BSU AC 9' SCART TO SCART TO SCART TO SCART TO ALL PIN' SOUND 5.5 SOUND 6.0 TRANSFO D 12' PLOE TA 12' PSU AC 12' PSU AC 9' PSU AC 9	-FM22 C80-PtC 82 PtD 322 66 PPLY & 24V PPLY- PPLY- V 500N IA ALOG 0V F01 BLOC UB MII E BAN 4 PHO 6 PHO 6 PHO 9 F0 BLOC UB MII E BAN 4 PHO 6 PHO 8 CON 8 CON	ILI STEREO DWER 2 98012 	F1.00 £1.00 £5.00 £5.00 £5.00 £5.00 £0p 50p £2.00 £2.00 £2.00 £2.00 £2.00 £2.00 £1.50 £1.50 £1.50 £3.00 £3.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £2.00 £1.00
PANEL-IK2 PANEL-IK2 POSITOR 1 POSITOR 2 POSITOR 2 POWER SU 12V DC 4 POWER SU 12V DC 4 POWER SU PSU AC 12' PSU AC 9' QUARTZ 14 SOURD 5.5 SOUND 5.5	2-FM222 C80-PcC 82 PtD 322 66 PPPLY- 322 67 22 67 22 67 22 67 22 67 22 67 22 67 22 67 22 67 22 67 20 77 20 7	A STEREO DWER V 2 98012 	ETRES £2.00 £5.00 £5.00 £5.00 £00 £2.00 £2.00 £2.00 £1.50 £1.50 £1.50 £1.50 £1.00 £3.00 £3.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £3.00 £3.00 £3.00 £1.00 £3.0
PANEL-IK2 PANEL-IK2 POSITOR 1 POSITOR 2 POWER SU 12V DC 6 POWER SU 12V DC 6 POWER SU 12V DC 6 POWER SU 12V DC 6 POWER SU PSU AC 12' PSU AC 12'	-FM222 C80-PcX 8 2 PtD 322 66 PPPLY- 322 67 PPLY- 8 24V V 500M IA AALOG 0V FOI BLOC UB MII E BAN UB MII E BAN 4 PHO 6 PHO "D" PL 8 CAR K PPLY- 1A AALOG 0V FOI BLOC UB MII E BAN 4 PHO 1A AALOG 0'' FOI BLOC C V 500M 1A AALOG 0'' FOI BLOC C V FOI SCAR S C R SCAR SCAR	A STEREO DWER V 2 98012 	F1.00 £1.00 £5.00 £5.00 £5.00 £5.00 £0p 50p £2.00 2V 500MA £5.00 £1.50 £1.50 £1.50 £1.50 £3.00 £3.00 £3.00 £3.00 £3.00 £3.00 £1.00 £1.00 £1.00 £2.00 £1.00 £2.00 £1.00 £2.00 £1.00 £2.00 £1.00 £2.00 £1.00 £2.00 £1.00 £3.00 £3.00 £1.00 £4.00 £5.00
PANEL-IK2 PANEL-IK2 PANEL-CV POSITOR-2 POSITOR-2 POSITOR-2 POWER SU I2V DC 4 POWER SU PSU AC 12' PSU AC 12' PS	2-FM222 C80-PxC 82 PtD 322 66 PPLY- 322 67 PPLY- 322 66 PPLY- 322 66 PPLY- 132 67 PTC 424 V 500N 14 A ALOG 0V FOI BLOC V FOI PLI V TOI V FOI SCAR' SCAR' S SCAR'	ILI STEREO DWER V 2 98012 	ETRES £1.00 £5.00 £5.00 £5.00 £5.00 £2.00 20p 50p £2.00 £1.50 £1.50 £1.50 £1.50 £3.00 £3.00 £3.00 £1.00 £1.00 £1.00 £1.00 £2.00 £2.00 £2.00 £5.00 £1.00 £5.00 £1.00 £5.00 £1.00 £5.00 £1.00 £5.00 £1.00 £5.00 £1.00 £5.00 £1.00 £5.00 £1.00 £5.00 £1.00 £5.00 £1.00 £5.00 £1.00 £5.00 £1.00 £5.00 £1.00 £5.00 £1.00 £5.00 £1.00 £5.00 £1.00 £5.00 £1.00 £5.00 £1.00 £5.00
PANEL-IK2 PANEL-IK2 PANEL-CV POSITOR-1 POSITOR-2 POWER SU 12V DC 4 POWER SU 12V DC 4 POWER SU PSU AC 12' PSU A	-FM222 C80-PxC 82 PtD 322 66 PPLY- 322 67 PPLY- 322 66 PPLY- 322 66 PPLY- 132 66 PPLY- 132 66 PPLY- 14 SCAR'	ILI STEREO DWER 2 98012 	ETRES £2.00 £5.00 £5.00 £5.00 £5.00 £2.00 2V 500MA £5.00 £1.50 £1.50 £1.50 £1.50 £1.50 £1.00 £3.00 £1.00 £1.00 £1.00 £1.00 £1.00 £2.00 £2.00 £2.00 £2.00 £3.00 £1.00 £2.00 £2.00 £2.00 £2.00 £2.00 £3.00 £2.00 £2.00 £2.00 £2.00 £3.00
PANEL-IK2 PANEL-IK2 POSITOR-1 POSITOR-2 POSITOR-2 POWER SU 12V DC 4 POWER SU 12V DC 4 POWER SU PSU AC 12' PSU	-FM222 C80-PcC 82 PtD 322 66 PPDLY- 322 66 PPDLY- 322 66 PPDLY- 132 26 PPDLY- 132 26 PDLY- 132 26 PDLY- 132 26 PDLY- 132 60 PDLY- 10 PDL 10 PDLY- 10 PDLY- 10 PDLY- 1	ILI STEREO DWER 2 98012 	ETRES £2.00 £3.00 £5.00 £5.00 £5.00 £2.00 20p £2.00 £1.50 £1.50 £1.50 £1.50 £1.50 £1.50 £1.00 £3.00 £3.00 £1.00 £1.00 £1.00 £1.00 £2.00 £2.00 £2.00 £3.00 £3.00 £3.00 £3.00 £1.00 £2.00 £2.00 £2.00 £3.0
PANEL-IK2 PANEL-IK2 POSITOR-1 POSITOR-2 POSITOR-2 POWER SU 12V DC <i>i</i> POWER SU PSU AC 12' PSU AC 9V QUARTZ H SOWER SU SOWER SU SOWER SU SOWER SU SOWER SU SOWER SU SOWER SU SOWER SU SOWER SU SOWER SU SOUND 5.5 SOUND 6.0 TRANSFOI MAINS O-120V-0 TRIPLER K TRIPLER - FERGUS ADAPTOR AC MAIN	-FM222 C80-PtC 82 PtD 322 66 PPDLY- 322 67 PPDLY- 322 60 PPDLY- 132 60 PPDLY- 142 60 PPDLY- 16 8 CON 16 PDLY- 16 8 CON 17 9 CON 17 17 17 17 17 17 17 17 17 17 17 17 17	ILI STEREO DWER 2 98012 	ETRES £1.00 £5.00 £5.00 £5.00 £00 200 200 200 200 200 200 2
PANEL-IK2 PANEL-IK2 PANEL-CV POSITOR-1 POSITOR-2 POWER SU 12V DC / POWER SU 12V DC / POWER SU PSU AC 12' PSU AC 12' PSU AC 12' PSU AC 12' PSU AC 12' PSU AC 12' PSU AC 9V QUARTZ H 500W 20 AC 9V AC 80 AC 9V AC 80 AC 9V QUARTZ H 500W 20 AC 9V AC 80 AC 9V AC 80 AC 9V QUARTZ H 500W 20 AC 9V AC 80 AC 9V AC 80 AC 9V QUARTZ H 500W 20 AC 9V AC 80 AC 9V AC	2009 2009	ALL STEREO DWER V 2 98012 	ETRES £1.00 £5.00 £5.00 £5.00 20p 50p £2.00 £2.00 £1.50 £1.50 £1.50 £1.50 £1.50 £1.50 £1.50 £1.00 £3.00 £3.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £2.00 £2.00 £2.00 £3.00
PANEL-IK2 PANEL-IK2 PANEL-CV POSITOR-1 POSITOR-2 POWER SU I2V DC / POWER SU I2V DC / POWER SU PSU AC 12' PSU AC 9' QUARTZ H SOW DC 5.5 SOUND 6.0 TRANSFO D 12' PSU AC 12' PSU AC 12' PSU AC 9' PSU	2-FM222 C80-PcX 82 PtD 322 66 PPPLY- 322 68 PPPLY- 322 66 PPPLY- 8 2 PtD 4 S 24V V 500N IA ALOG 6 PHO 6 PHO 70° PLY- 1 S CAR' S CON MHZ D SON SON 200 200 200 200 200 200 200 200 200 20	11 STEREO DWER V 2 98012 DC-REGULATED REGULATED 3-1: IA EN ROUTDOOR LAN NIATURE ER UNIT - 242761 ID/VIDEO OUT NO LEADS 1.5M NO LEADS 1.5M NO LEADS 1.5M NECTED - 1.5 MI MPM 1000T RS ENCAPSULAT PRI 0-9V-0-9V SE 0 ERSAL - TEXT - VA354 ATTERY-VA365 SD143 SD157 SD157 SD157	ETRES £1.00 £5.00 £5.00 £5.00 20p 50p £2.00 £2.00 £1.50 £1.50 £1.50 £1.50 £1.50 £1.50 £1.00 £3.00 £3.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £3.00 £1.00 £1.00 £1.00 £3.00 £1.00 £1.00 £1.00 £3.00 £1.00
PANEL-IK2 PANEL-IK2 PANEL-CV POSITOR 1 POSITOR 1 POSITOR 2 POWER SU 12V DC 4 POWER SU PSU AC 9V 20WER SU 20WER SU 20WERS	2-FM222 C80-PcX 82 PTD 322 66 PPPLY- 322 68 PPPLY- 322 66 PPPLY- 82 24V V 500N IA ALOG 0V FOI DUB MIL E BANN 4 PHO 6 PHO "D" PJ PLY- S CON MH2 N MH2 N M M M M M M M M M M M M M M M M M M M	11 STEREO DWER 2 98012 - 2 98012 - C-REGULATED 3-1: 1A EQUATED 3-1: IA COUTDOOR LAN NIATURE ER UNIT - 242761 ID/VIDEO OUT NO LEADS 1.5M NO LEADS 1.5M NO LEADS - NECTED - 1.5 MI MPM 1000T MPM 1040 RS ENCAPSULAT PRI 0-9V-0-9V SE 0 ERSAL - TEXT - VA354 ATTERY-VA365 SD143 SD143 SD157 SD157 SD157 SD157 SD157	ETRES £1.00 £5.00 £5.00 £5.00 £5.00 £00 £2.00 200 £2.00 £1.50 £1.50 £1.50 £1.50 £1.50 £1.50 £1.50 £1.50 £1.00 £3.00 £3.00 £1.00 £3.00 £1.00 £3.00 £1.00 £3.00 £1.00 £3.00 £1.00 £3.00 £1.00 £3.00 £1.00 £3.00 £1.50 £1.50 £1.50 £1.50 £1.50 £1.50 £1.50 £3.00 £1.50 £3.00 £3.00 £3.00 £1.50 £3.00 £3.00 £3.00 £1.50 £1.50 £1.50 £3.00 £3.00 £3.00 £1.50 £1.50 £1.50 £3.00 £3.00 £1.50 £1.50 £1.50 £1.50 £1.50 £1.50 £1.50 £1.50 £1.50 £1.50 £1.50 £1.50 £1.50 £1.50 £1.50 £1.50 £1.50 £1.00 £3.00 £1.00

15p £1,00 40p £1,00 30p £1,00 50p £1,00 £1,00 £1,00 £1,00

SD141 SD141 SD142

BI TO BI Ph BUTO BUTO BUTA BUTA BUTA BUTAD

£1.00 £1.00 20p 50p 20p 20p 15p £1 80p £1.00 50p 65p

£1.00 £1.00 \$0p £1.00 \$0p £1.00 \$0p £1.00 \$0p £1.00 £2.00 £2.00 £1.00

81 81 81

CAMCORDER BATTERY, HIGH CAPACITY 9 6V 1800MA-VA310 £3.00 CAMCORDER BATTERY CHARGER 9 6 VOLTS VAZ65 EACH £6.00 CAMCORDER LENS 20 FF- TELE-CONVERSION LENS x1.4 & A0.7 £1.00 CARDIOLD CAMERA MICROPHONE-VA SUPER 218 TELESCOPIC BOOM & STAND 500 CARDIOL CAMERA MICROPHONE-VA 500 CHASSIS-TX80-NEW-NO TUNER PP £5.00 EACH 115.00 CHASSIS-TX80-NEW-NO TUNER PP £5.00 DEACH 115.00 CHASSIS-TX80-NEW-NO TUNER PP £5.00 DEACH 415.00 CHASSIS-TX80-NEW-NO TUNER PP £5.00 DEACH 415.00 FV70B, FV71LV, FV72LV, FV74LVX FV61LV, FV62LV, FV67LV, FV74LVX FV61LV, FV62LV, FV72LV, FV74LVX FV71HV £30.00 FV71B, EXTIL 62.00 PAVEL-TU228B TEXT FOR TX89, TX99, TX100 £6.00 PANEL-T1228B TEXT FOR TX89, TX99, TX99, TX100 £6.00 PANEL-T1228B TEXT FOR TX89, TX98, TX99, TX100 £6.00 PANEL-T1228B TEXT FOR TX89, TX98, TX98, TX99, 55.00 PANEL-TUDE BASE-CS £5.00 PANEL-TUBE BASE-CS £5.00 PANEL-TUBE BASE-CS £5.00 PANEL-TUBE BASE-CS £5.00 PANEL-TUBE BASE-TX89, TX98, TX99 £5.00 PANEL-TUBE BASE-TX89, TX98, TX99, 55.00 PANEL-TUBE-BASE-TX89, TX98, TX99 £5.00 PANEL-TUBE-BASE-TX89, TX98, TX99, 55.00 PANEL-TUBE-BASE-TX89, TX98, TX99, 55.00 TX100 £5.00 TX100 £5.00 PANEL-TEXT PC315-11 - ISSUE 7 £15.00 PANEL-TELETEXT PC315-11 - ISSUE 7 £15.00 PANEL-TELETEXT PC315-11 - ISSUE 7 £15.00 PANEL-TELETEXT PC315-11 - ISSUE 7 £100 PANEL-TELETEXT PC315-11 - ISSUE 7 £100 PANEL-TUBE-SISWITCH MODE STR 4211	N N	emote		JIIITO	IS T	4
9 6V 1800MA-VA310 £3.00 CAMCORDER BATTERY CHARGER 9 6 VOLTS VAZ65 EACH £6.00 CAMCORDER LENS 2 OFF- TELE-CONVERSION LENS x1.4 & A0.7 £1.00 CARDIOLD CAMERA MICROPHONE-VA SUPER 218 TELESCOPIC BOOM & STAND \$25.00 CHASSIS-TX80-NEW-NO TUNER PP £5.00 EACH £15.00 CHASSIS-TX80-NEW-NO TUNER PP £5.00 CHASSIS-TX80-NEW-NO TUNER PP £5.00 CHASSIS-TX80-NEW-NO TUNER PP £5.00 DECK AND CAPSTAN MOTOR: FV61LV, FV62LV, FV67LV, FV68LV EACH £30.00 FV70B, FV71LV, FV72LV, FV74LVX EACH £30.00 FV31R £12.00 PANEL-T228B TEXT FOR TX89, TX99, TX90, TX100 £5.00 PANEL-T228B TEXT FOR TX89, TX99, TX99, TX100 £5.00 PANEL-T20 THORN FRONT - - 8 BUTTONS 01M4-515-002 £5.00 PANEL-TUDE BASE-TX89, TX89, TX99 £5.00 PANEL-TUDE BASE-TX89, TX89, TX99 £5.00 PANEL-TUDE BASE-TX89, TX89, TX99 £5.00 PANEL-TUDE BASE-TX89, TX80, TX99 £5.00 PANEL-TELETEXT PC332A5 - ISSUE 4 £15.00 PANEL-TELETEXT PC332A5 - ISSUE 4 £15.00 PANEL-TELETEXT PC332A5 - ISSUE 4 £15.00 PANEL-TELETEXT PC335A1 £5.00 SOULLATOR No 5587881 £5.00 SOUER SUPPLY VIDEO SWITCH MODE STR 4211 ISSUE 10 £8.00 POWER SUPPLY VIDEO SWITCH MODE STR 4211 ISSUE 10 £8.00 POWER SUPPLY VIDEO SWITCH MODE STR 4211 ISSUE 10 £8.00 POWER SUPPLY VIDEO SWITCH MODE SUP 421 IDED CHASSIS WITH TUNER-IR £5.00 POST £4.00 POST £	САМСС	ORDER BATT	ERY, H	IGH CAPAC	TTY	Γ
CAMCORDER BATTERY CHARGER 9 6 VOLTS VAZ65 EACH £6.00 CAMCORDER CAR ADAPTOR CHARGER- AND BATTERY-VA308 £5.00 CAMCORDER LENS 2 OFF- TELE-CONVERSION LENS x1.4 & a.0.7 £1.00 CARDIOLD CAMERA MICROPHONE-VA SUPER 218 TELESCOPIC BOOM & STAND £5.00 CHASSIS-TX80-NEW-NO TUNER PP £5.00 EACH £15.00 CHASSIS-TX80-NEW-NO TUNER PP £5.00 DECK AND CAPSTAN MOTOR: FV61LV, FV62LV, FV67LV, FV68LV EACH £30.00 FV70B, FV71LV, FV72LV, FV74LVX EACH £30.00 PANEL-T228B TEXT FOR TX89, TX99, TX100 £5.00 PANEL-TU28B BASE-TCCS £5.00 PANEL-TU28B BASE-TCS £5.00 PANEL-TUDE BASE-TX89, TX98, TX99 EACH £4.00 PANEL-TUBE BASE-TX89, TX98, TX99 EACH £4.00 PANEL-TUBE BASE-TX89, TX88, TX99 EACH £4.00 PANEL-TUBE BASE-TX89, TX88, TX99 EACH £4.00 PANEL-TUNING 1509G-TX9, TX10 £5.00 PANEL-TUNING 1509G-TX9, TX10 £5.00 PANEL-TUNING 1509G-TX9, TX10 £5.00 PANEL-TELETEXT PC232A5 - ISSUE 4 £15.00 PANEL-TELETEXT PC332A5 - ISSUE 4 £15.00 PANEL-TELETEXT PC315-11 - ISSUE 7 £15.00 PANEL-TELETEXT PC315-11 - ISSUE 7 £16.00 POWER SUPPLY VIDEO SWTTCH MODE STR 4211 ISSUE 10 STR 4211 ISSUE	96V	1800MA-VA3	10		£3.00	
CAMCORDER CAR ADAPTOR CHARGER - AND BATTERY-VA308 £5.00 CAMCORDER LENS 2 OFF - TELE-CONVERSION LENS x1.4 & x0.7 £1.00 CARDIOID CAMERA MICROPHONE-VA SUPER 218 TELESCOPIC BOOM & STAND £5.00 CHASSIS-TX80-NEW-NO TUNER PP £5.00 EACH £15.00 CHASSIS-TX80-NEW-NO TUNER PP £5.00 EACH £15.00 CHROME BOARD-ICCS I/Cs U4647TKF OR HA11498 £6.00 DECK AND CAPSTAN MOTOR:- FV61LV, FV62LV, FV67LV, FV68LV EACH £30.00 FV70B. FV71LV, FV72LV, FV74LVX EACH £30.00 FV70B. FV71LV, FV72LV, FV74LVX EACH £30.00 FV71HV £3.00 FV31R £12.00 HEAD AND DRUM MODULATOR-SATELLITE-TI040-SRD3/4 MODULATOR-SATELLITE-TI040-SRD3/4 £2.00 PANEL-T228B TEXT FOR TX89, TX99, TX99, TX10 £6.00 PANEL-T028B TEXT FOR TX89, TX99, TX10 £6.00 PANEL-T00NS 01/M-515-002 £5.00 PANEL-TUBE BASE-TCS £5.00 PANEL-TUBE BASE-TX89, TX98, TX99, 55.00 PANEL-TUBE BASE-TX89, TX98, TX99, 56.00 PANEL-TUBE BASE-SWITCH MODE- TX33, TX86, TX89 EACH £4.00 TX100 £5.00 POWER SUPPLY 12V-3A <td< td=""><td>CAMCO 9.6 V</td><td>ORDER BATT</td><td>ERY C</td><td>HARGER</td><td>1 66 00</td><td></td></td<>	CAMCO 9.6 V	ORDER BATT	ERY C	HARGER	1 66 00	
AND BATTERY-VA308 £5.00 CAMCORDER LENS 2 OFF - TELE-CONVERSION LENS x1.4 & x0.7 £1.00 CARDIOID CAMERA MICROPHONE-VA SUPER 218 TELESCOPIC BOOM & STAND £5.00 CHASSIS-TX80-NEW-NO TUNER PP £5.00 EACH £15.00 CHASSIS-TX80-NEW-NO TUNER PP £5.00 EACH £15.00 CHROME BOARD-ICCS I/Cs U4647TKF OR HAI1498 £6.00 DECK AND CAPSTAN MOTOR:- FV61LV, FV62LV, FV67LV, FV68LV EACH £30.00 FV70B. FV71LV, FV72LV, FV74LVX EACH £30.00 FV70B. FV71LV, FV72LV, FV74LVX EACH £30.00 FV71HV £30.00 FV71BV £2.00 PANEL-T1228B TEXT FOR TX89, TX99, TX100 £6.00 PANEL-T228B TEXT FOR TX89, TX99, TX10 £6.00 PANEL-T1228B TEXT FOR TX89, TX99, TX10 £5.00 PANEL-T1228B TEXT FOR TX89, TX99, TX10 £6.00 PANEL-T1228B TEXT FOR TX89, TX99, TX10 £6.00 PANEL-T128B TEXT FOR TX89, TX98, TX99, TX10 £6.00 PANEL-T128B TEXT FOR VIDEOSTAR CAMERA PP3 £4.00 TX100 £5.00 FANSFORMERS-SWITCH MODE: TX35, TX86, TX89 £5.00 <td>CAMCO</td> <td>ORDER CAR</td> <td>ADAPI</td> <td>OR CHARG</td> <td>ER -</td> <td></td>	CAMCO	ORDER CAR	ADAPI	OR CHARG	ER -	
CAMOURDER LENS 2 DEP - TELE-CONVERSION LENS X.1.4 & x0.7 E1.00 CARDIOLD CAMERA MICROPHONE-VA SUPER 218 TELESCOPIC BOOM & STAND E5.00 CHASSIS-TX80-NEW-NO TUNER P/P £5.00 EACH £15.00 CHROME BOARD-ICCS J/CG U4647TKF OR HA11498 £6.00 DECK AND CAPSTAN MOTOR:- FV61LV, FV62LV, FV67LV, FV74LVX EACH £30.00 FV70B, FV71LV, FV72LV, FV74LVX EACH £30.00 FV70B, FV71LV, FV72LV, FV74LVX EACH £30.00 FV77HV £30.00 FV71RV £30.00 FV71RV £30.00 FV71RV £30.00 PANEL-TS90 THORN FRONT - - - 8 BUTTONS £5.00 PANEL-TUBE BASE-TCS £5.00 PANEL-TUBE SASEWITCH MODE TX85.00 RANSFORMERS-SWITCH MODE <t< td=""><td>AND</td><td>BATTERY-VA</td><td>308</td><td></td><td>£5.00</td><td></td></t<>	AND	BATTERY-VA	308		£5.00	
£1.00 CARDIOLID CAMERA MICROPHONE-VA SUPER 218 TELESCOPIC BOOM & STAND £5.00 CHASSIS-TX80-NEW-NO TUNER P/P £5.00 EACH £15.00 CHROME BOARD-ICCS I/CS U4647TKF OR HAI1498 £6.00 DECK AND CAPSTAN MOTOR:- FV61LV, FV62LV, FV67LV, FV74LVX EACH £30.00 FV70B, FV71LV, FV72LV, FV74LVX EACH £30.00 FV70B, FV71LV, FV72LV, FV74LVX EACH £30.00 FV70B, FV71LV, FV72LV, FV74LVX EACH £30.00 FV71W £30.00 FV31R £12.00 HEAD AND DRUM MODULATOR-SATELLITE-T1040-SRD3/4 £2.00 PANEL-TI228B TEXT FOR TX89, TX99, TX90 £5.00 PANEL-TUDE BASE-TCS £5.00 PANEL-TUBE BASE-TCS £5.00 PANEL-TUDES STAR CAMERA PRJ £4.00 PUNER SUPPLY 12V-3A FOR VIDEOSTAR CAMERA PRJ £4.00 TX100 £5.00 PANEL-TUBE BASE-TX89, TX86, TX86, T880 £5.00 PANEL-TUBE BASE-TX89, TX86, T880 £5.00 PANEL-TUBE BASE-TX89, TS86, T5.00 £5.00 PANEL-TUBE BASE-TX89, TS86, T5.00 £5.00 PANEL-TUBE BASE-TX89, TS95, 50.00 £4.00 TX100 £5.00 POWER SUPPLY 12V-3A £5.00 POWER SUPLY VINCH MODE	TELE	-CONVERSI	2 OPP	- VS x1.4 & x0).7	
CARDIOID CAMERA MICROPHONE-VA SUPER 218 TELESCOPIC BOOM & STAND E5.00 CHASSIS-TX80-NEW-NO TUNER P/P £5.00 EACH £15.00 CHASSIS-TX80-NEW-NO TUNER P/P £5.00 EACH £15.00 CHROME BOARD-ICCS U/CS U4647TKF OR HA11498 EACH £30.00 FV70B, FV71LV, FV72LV, FV74LVX EACH £30.00 FV70B, FV71LV, FV72LV, FV74LVX EACH £30.00 FV70B, FV71LV, FV72LV, FV74LVX EACH £30.00 FV77HV £30.00 FV77HV £20.00 PANEL-REMOTE TX 100 £5.00 PANEL-TR288 TEXT FOR TX89, TX98, TX99, TX100 £6.00 PANEL-TUBE BASE TX89, TX98, TX99 £5.00 PANEL-TUBE BASE-ICCS £5.00 PANEL-TUBE BASE-ICCS £5.00 PANEL-TUBE BASE-TX89, TX98, TX99 £6.00 PANEL-TUBE BASE-TX89, TX98, TX99 £6.00 PANEL-TUBE BASE-TX89, TX98, TX99 £6.00 PANEL-TUNING 1509G-TX9, TX10 £5.00 POWER SUPPLY 12V-3A FOR VIDEOSTAR CAMERA PP3 £4.00 PUSH BUTTON UNIT-TX85, TX86- 8 BUTTONS £5.00 TX160 £5.00 TX160 £5.00 TX100 £5.00 FOR VIDEOSTAR CAMERA PP3 £4.00 TX160 £5.00					£1.00	
SUPER 218 TREESCOPIC BOOM & STARD ES.00 CHASSIS-TX80-NEW-NO TUNER P/P £5.00 EACH £15.00 CHROME BOARD-ICCS UCS U4647TKF OR HA11498 EACH £30.00 FV70B. FV71LV, FV72LV, FV74LVX EACH £30.00 FV70FV £30.00 FV70FV £30.00 FV70FV £20.00 PANEL-TWS0 THORN FRONT- - -8 BUTTONS 01M4.515-002 £5.00 PANEL-TUBE BASE-TX89, TX98, TX99 £5.00 PANEL-TUBE BASE-TX89, TX98, TX99 £4.00 PUSH BUTTON UNIT-TX85, TX86- \$ BUTTONS FV80 TUTON UNIT-TX85, TX86- \$ BUTTONS FV80 TUTON UNIT-TX85, TX86- \$ BUTTON UNIT-TX85, TX86-	CARDI	DID CAMERA	MICR	OPHONE-V	A	
CHASSIS-TX80-NEW-NO TUNER P/P £5.00 EACH £15.00 CHROME BOARD-ICCS U/CS U4647TKF OR HA11498 £6.00 DECK AND CAPSTAN MOTOR:- FV61LV, FV62LV, FV67LV, FV68LV EACH £30.00 FV70B, FV71LV, FV72LV, FV74LVX EACH £30.00 FV70B, FV71LV, FV72LV, FV74LVX EACH £30.00 FV77HV £30.00 FV77HV £30.00 FV77HV £30.00 PANEL-REMOTE TX100S £5.00 PANEL-T1228B TEXT FOR TX89, TX98, TX99, TX100 £6.00 PANEL-TUBE BASE-TX89, TX98, TX99 £5.00 PANEL-TUBE BASE-TX89, TX88, TX99 £5.00 PANEL-TUBE-BASE-TX89, TX98, TX99 £5.00 PANEL-TUBE-BASE-TX89, TX98, TX99 £5.00 PANEL-TUBE-BASE-TX89, TX98, TX93 £5.00 PANEL-TUBE-BASE-TX89, TX98, TX95 £5.00 PANEL-TUBE-BASE-TX89, TX98, TX95 £5.00 PANEL-TUBE-BASE-TX89, TX98, TX96 £5.00 POWER SUPPLY 12-3A FOR VIDEOSTAR CAMERA PP3 £4.00 PUSH BUTTON UNIT-TX85, TX86- £5.00 RUTTONS 01MA-515-002 £5.00 TX100 £5.00 TX100 £5.00 TX8100 EACH £4.00 TX100 £5.00 OSCILLOSCOPE 20MHZ DOUBLE BEAM - </td <td>3011</td> <td>R 210 ILL</td> <td>COLIC</td> <td>BOOMACS</td> <td>£5.00</td> <td></td>	3011	R 210 ILL	COLIC	BOOMACS	£5.00	
EACH £15.00 CHROME BOARD-ICCS I/Cs U4647TKF OR HA11498 £6.00 DECK AND CAPSTAN MOTOR:- FV61LV, FV62LV, FV67LV, FV68LV EACH £30.00 FV70B, FV71LV, FV72LV, FV74LVX EACH £30.00 FV70B, FV71LV, FV72LV, FV74LVX EACH £30.00 FV77HV £30.00 FV77HV £30.00 FV77HV £30.00 FV77HV £30.00 PAREL-REMOTE TX100s £5.00 PANEL-T1228B TEXT FOR TX89, TX98, TX99, TX100 £6.00 PANEL-TUBE BASE-TX89, TX98, TX99 £5.00 PANEL-TUBE-BASE-TX89, TX98, TX99 £5.00 PANEL-TUBE-BASE-TX89, TX98, TX93 £5.00 PANEL-TUBE-BASE-TX89, TX98, TX95 £5.00 PANEL-TUBE-BASE-TX89, TX98, TX93 £5.00 POWER SUPPLY 12V-3A FOR VIDEOSTAR CAMERA PP3 £4.00 PUSH BUTTON UNIT-TX85, TX86- B BUTTONS £5.00 TX NSFORMERS-SWITCH MODE:- TX85, TX86, TX89 EACH £4.00 TX100 £5.00 MODULATOR No, 5587881 £5.00 OSCILLOSCOPE 20MHZ DOUBLE BEAM - V212 £15.00 MAINS SWITCH WITH STAND-BY £5.00 OSCILLOSCOPE 20MHZ DOUBLE BEAM - V212 £18.00 <th< td=""><td>CHASS</td><td>IS-TX80-NEW</td><td>-NO T</td><td>UNER P/P</td><td>25.00</td><td></td></th<>	CHASS	IS-TX80-NEW	-NO T	UNER P/P	25.00	
UCS U4447TKF OR HA11498 £6.00 DECK AND CAPSTAN MOTOR:- FV61LV, FV62LV, FV67LV, FV68LV EACH £30.00 FV70B, FV71LV, FV72LV, FV74LVX EACH £30.00 FV77HV £30.00 FV77HV £30.00 FV71HV £30.00 FV71BV £30.00 PANEL-REMOTE TX.100 £5.00 PANEL-TU228B TEXT FOR TX89, TX98, TX99, TX100 £6.00 PANEL-TUBE-BASE-TX89, TX98, TX99, E5.00 PANEL-TUBE-BASE-TX89, TX88, TX95 £5.00 PANEL-TUBE-BASE-TX89, TX88, TX95 £4.00 TX100 £5.00 POWER SUPPLY 12-3A FOR VIDEOSTAR CAMERA PP3 £4.00 TX85, TX86, TX89 EACH £4.00 TX100 £5.00 TX100 £5.00 ICC5 3112-338 326842 £4.00 TX18, SWTCH WITH STAND-BY £5.00	CHRON	E BOARD-IC	YC S	EACH	£15.00	
DECK AND CAPSTAN MOTOR:- FV61LV, FV62LV, FV67LV, FV68LV EACH £30,00 FV70B, FV71LV, FV72LV, FV74LVX EACH £30,00 FV77HV £30,00 FV77HV £30,00 FV71R £12,00 HEAD AND DRUM MODULATOR-SATELLITE-T1040-SRD3/4 £2,00 PANEL-T1228B TEXT FOR TX89, TX99, TX99, TX100 £6,00 PANEL-T1228B TEXT FOR TX89, TX99, TX90, T5100 FOR TX89, TX99, TX90, TS100 £5,00 PANEL-TUBE BASE-TCCS £5,00 PANEL-TUBE BASE-TCCS £5,00 PANEL-TUBE BASE-TCS £5,00 PANEL-TUBE BASE-TCS £5,00 PANEL-TUBE BASE-TX89, TX98, TX99 £6,00 PUSH BUTTON UNIT-TX85, TX86 - 8 BUTTONS £5,00 TX160 £5,00 TX185, TX86, TX89 EACH £4,00 TX100 £5,00 TX160 £5,00 TX160 £10,00 TX85, TX86, TX89 EACH £4,00 TX160 £10,00 MAINS SWITCH WITH STAND-BY £500 MODULATOR NO 5587881	I/Cs L	4647TKF OR	HAII	198	£6.00	
EACH £30.00 FV70E, FV71LV, FV72LV, FV74LVX EACH £30.00 FV70B, FV71LV, FV72LV, FV74LVX EACH £30.00 FV70B, FV71LV, FV72LV, FV74LVX EACH £30.00 FV70B, FV71LV, FV72LV, FV74LVX EACH £30.00 FV70H VR £30.00 FV77HV £30.00 FV71HV £30.00 FV71HV £30.00 FV71HV £30.00 PANEL-TUB2B BASE-TCCS £5.00 PANEL-TUBE BASE-TCCS £5.00 PANEL-TUNING 15090	DECH	AND CAPS	TAN M	OTOR:-		
FV70B, FV71LV, FV72LV, FV74LVX EACH £30.00 FV77HV £30.00 FV31R £12.00 HEAD AND DRUM 22.00 PANEL-REMOTE TX100s £5.00 PANEL-TI228B TEXT FOR TX89, TX99, TX100 £6.00 PANEL-TI208 TEXT FOR TX89, TX99, TX100 £6.00 PANEL-TUBE BASE-TCC £5.00 PANEL-TUBE BASE-TCS £5.00 POWER SUPPLY 12V-3A FOR VIDEOSTAR CAMERA PP3 £4.00 PUSH BUTTON UNIT-TX85, TX86- 8 BUTTONS £5.00 TX180 £5.00 15.00 473190-00, 40153060 EACH £4.00 TX100 £5.00 152.00 152.00 152.00 HTACHI DECODER-TELETEXT PC232A5 - ISSUE 4 £15.00 DECODER-TELETEXT PC232A5 - ISSUE 4 £15.00 PANEL-TUELTY TOSISTA CAMERA P3 £0.00 SCILLOSCOPE 20MHZ DOUBLE BEA	1 401	LV, I VO2LV, I	VUILV	EACH	£30,00	
EACH £30.00 FV77HV £30.00 FV31R £12.00 HEAD AND DRUM MODULATOR-SATELLITE-T1040-SRD3/4 £2.00 FAREL-REMOTE TX100s £5.00 PANEL-T1228B TEXT FOR TX89, TX98, TX99, TX100 £6.00 PANEL-T1208 TEXT FOR TX89, TX98, TX99, TX100 £6.00 PANEL-T10BE-BASE-TX89, TX98, TX99 £5.00 PANEL-TUBE-BASE-TX89, TX98, TX99 £5.00 PANEL-TUBE-BASE-TX89, TX98, TX99 £6.00 PANEL-TUBE-BASE-TX89, TX80, TX99, 55.00 PANEL-TUBE-BASE-TX89, TX86, TX86- PANEL-TUBE-BASE-TX89, TX86, TX86- 8 BUTTON UNIT-TX85, TX86- 8 BUTTON UNIT-TX85, TX86- 16 BUTA DECODER-TELETEXT PC232A5 - ISSUE 4 £15.00 IXC5 3112-338 326842 £4.00 MODULATOR NO 5587881 £5.00 POULATOR NO 5	FV70	B. FV71LV, F	V72LV,	FV74LVX		
FV31R £12.00 HEAD AND DRUM MODULATOR-SATELLITE-T1040-SRD3/4 £2.00 PANEL-REMOTE TX 100s £5.00 PANEL-T1228B TEXT FOR TX89, TX98, TX99, TX100 £6.00 PANEL-T1208 TEXT FOR TX89, TX98, TX99, TX100 £6.00 PANEL-T1328B TEXT FOR TX89, TX98, TX99, TX100 £5.00 PANEL-TUBE BASE-ICCS £5.00 PANEL-TUBE-BASE-TX89, TX98, TX99 £5.00 PANEL-TUBE-BASE-TX89, TX98, TX99 £4.00 PUSH BUTTON UNIT-TX85, TX86- 8 BUTTONS £5.00 POWER SUPPLY 12V-3A FOR VIDEOSTAR CAMERA PP3 £4.00 TX100 £5.00 TX160 £5.00 TCC5 3112-338 326842 £4.00 TX100 £5.00 ICC5 3112-338 326842 £4.00 TX100 £5.00 HEAD AND DRUM - 620E £12.00 MAINS SWITCH WITH STAND-BY £50p MODULATOR NO 5587881 £5.00 SCILLOSCOPE 20MHZ DOUBLE BEAM - V212 £188.00 PANEL-TELETEXT PC315-11 - ISSUE 7 £15.00 FNC1145752 £20.00 POWER SUPPLY VIS WITCH MODE \$8.00	FV77	HV		EACH	£30.00 £30.00	
HEAD AND DRUM £2.00 MODULATOR-SATELLITE-T1040-SRD3/4 £2.00 PANEL-REMOTE TX 100s £5.00 PANEL-T1228B TEXT FOR TX89, TX98, TX99, TX100 £6.00 PANEL-TX90 THORN FRONT -	FV31	R			£12.00	
SIDDUCATOR-SATELLITE- F1080-SR0394 £2.00 PANEL-REMOTE TX 100s £5.00 PANEL-TI228B TEXT FOR TX89, TX98, TX99, TX100 £6.00 PANEL-TI228B TEXT FOR TX89, TX98, TX99, TX100 £6.00 PANEL-TUBE-BASE-TX89, TX98, TX99 £5.00 PANEL-TUBE-BASE-TX89, TX98, TX99 £5.00 PANEL-TUBE-BASE-TX89, TX98, TX99 £6.00 PANEL-TUBE-BASE-TX89, TX98, TX99 £6.00 PANEL-TUBE-BASE-TX89, TX98, TX99 £6.00 PANEL-TUBE-BASE-TX89, TX98, TX99 £6.00 POWER SUPPLY 12V-3A FOR VIDEOSTAR CAMERA PP3 £4.00 PUSH BUTTON UNIT-TX85, TX86- 8 BUTTONS £5.00 TX100 £5.00 ICC5 3112-338 326842 £4.00 TX100 £5.00 ICC5 3112-338 326842 £4.00 HITACHI DECODER-TELETEXT PC232A5 - ISSUE 4 £15.00 PANEL-TELETEXT PC315-11 - ISSUE 7 £15.00 S0 MODULATOR NO 5587881 £5.00 S0 OSCILLOSCOPE 20MHZ DOUBLE BEAM - V212 £188.00 PANEL-TELETEXT PC315-11 - ISSUE 7 £15.00 PANEL-TELETEXT PC315-11 - ISSUE 7 £15.00	HEADA	ND DRUM	I PTTC		3/4	
PANEL-REMOTE TX 100s £5.00 PANEL-T1228B TEXT FOR TX89, TX98, TX99, TX100 £6.00 PANEL-T1208 TEXT FOR TX89, TX98, TX99, TX100 £6.00 PANEL-TUSO THORN FRONT -	MODUL	AIOK-SALE	LLIIE-	11040-3KD.	£2.00	
PANEL-112288 TEX1 FOR TX89, TX98, TX99, TX100 £6.00 PANEL-TX90 THORN FRONT - -8 BUTTONS 01M4-515-002 £5.00 PANEL-TUBE BASE-ICCS £5.00 PANEL-TUBE-BASE-TX89, TX98, TX99 £5.00 PANEL-TUBE-BASE-TX89, TX98, TX99 £6.00 PANEL-TUBE-BASE-TX89, TX98, TX99 £6.00 PANEL-TUBE-BASE-TX89, TX98, TX99 £6.00 POWER SUPPLY 12V-3A FOR VIDEOSTAR CAMERA PP3 £4.00 PUSH BUTTON UNIT-TX85, TX86- 8 BUTTONS £5.00 TRANSFORMERS-SWITCH MODE:- TX85, TX86, TX89 EACH £4.00 TX100 £100 £5.00 ICC5 3112-338 326842 £4.00 HITACHI DECODER-TELETEXT PC232A5 - ISSUE 4 £15.00 ICC5 3112-338 326842 £4.00 MAINS SWITCH WITH STAND-BY £50p MODULATOR NG 5587881 £5.00 OSCILLOSCOPE 20MHZ DOUBLE BEAM - V212 ØPANEL-TELETEXT CG3P - ISSUE 6 £10.00 PANEL-TELETEXT PC315-11 - ISSUE 7 £15.00 POWER SUPPLY VIDEO SWITCH MODE \$8.00 POWER SUPPLY VIDEO SWITCH MODE ¥1.00 STR 4211 ISSUE 10 \$8.00 </td <td>PANEL-</td> <td>REMOTE TX</td> <td>100s</td> <td></td> <td>£5.00</td> <td></td>	PANEL-	REMOTE TX	100s		£5.00	
PANEL-TX90 THORN FRONT - -8 BUTTONS OIM-4-515-002 £5.00 PANEL-TUBE BASE-ICCS £5.00 PANEL-TUBE-BASE-TX89, TX98, TX99 £5.00 PANEL-TUBE-BASE-TX89, TX98, TX99 £5.00 PANEL-TUBE-BASE-TX89, TX98, TX99 £5.00 POWER SUPPLY 12V-3A FOR VIDEOSTAR CAMERA PP3 £4.00 PUSH BUTTON UNIT-TX85, TX86- 8 BUTTONS £5.00 TRANSFORMERS-SWITCH MODE:- TX85, TX86, TX89 EACH £4.00 TX100 £5.00 473190-00, 40153000 EACH £5.00 ICC5 3112-338 326842 £4.00 £12.00 MAINS SWITCH WITH STAND-BY £50p MODULATOR NO 5587881 £5.00 OSCILLOSCOPE 20MHZ DOUBLE BEAM - V212 C188.00 PANEL-TELETEXT C38P - ISSUE 6 £10.00 PANEL-TELETEXT G8P - ISSUE 6 £10.00 PANEL-TELETEXT C38P - ISSUE 6 £10.00 PANEL-TELETEXT V7753E £20.00 POWER SUPPLY VIDEO SWITCH MODE \$8.00 STR 4211 ISSUE 10 £8.00 POWER SUPPLY VIDEO SWITCH MODE ¥10.00 THCK, FILM-HM9204A £3.50	FOR	T1228B TEXT	X99 T	X100	£6.00	
-8 BUTTONS 01M4-515-002 £5.00 PANEL-TUBE-BASE-ICCS £5.00 PANEL-TUBE-BASE-TX89, TX98, TX99 £5.00 PANEL-TUBE-BASE-TX89, TX10 £5.00 POWER SUPPLY 12V-3A FOR VIDEOSTAR CAMERA PP3 £4.00 PUSH BUTTON UNIT-TX85, TX86- 8 BUTTONS £5.00 TRANSFORMERS-SWITCH MODE:- TX85, TX86, TX89 EACH £4.00 TX100 £5.00 473190-00, 40153000 EACH £5.00 ICC5 3112-338 326842 £4.00 15.00 HITACHI DECODER-TELETEXT PC232A5 - ISSUE 4 £15.00 MAINS SWITCH WITH STAND-BY £50p MODULATOR No. 5587881 £5.00 OSCILLOSCOPE 20MHZ DOUBLE BEAM - V212 C188.00 PANEL-TELETEXT C38P - ISSUE 6 £10.00 PANEL-TELETEXT C38P - ISSUE 6 £10.00 PANEL-TELETEXT C38P - ISSUE 6 £10.00 PANEL-TELETEXT V753E £20.00 POWER SUPPLY VIDEO SWITCH MODE \$8.00 STR 4211 ISSUE 10 £8.00 POWER SUPPLY VIDEO SWITCH MODE ¥1.00 STR 4211 ISUE 10 for £1.00 <t< td=""><td>PANEL-</td><td>TX90 THORN</td><td>FRON</td><td>IT -</td><td>40100</td><td></td></t<>	PANEL-	TX90 THORN	FRON	IT -	40100	
PANEL-10BE BASE-TX89, TX98, TX99 £5.00 PANEL-TUNING 1509G-TX9, TX10 £5.00 POWER SUPPLY 12V-3A FOR VIDEOSTAR CAMERA PP3 £4.00 PUSH BUTTON UNIT-TX85, TX86- 8 BUTTONS £5.00 TRANSFORMERS-SWITCH MODE:- TX85, TX86, TX89 EACH £4.00 TX100 £5.00 44.00 TX85, TX86, TX89 EACH £4.00 15.00 473190-00, 40153000 EACH £5.00 ICC5 3112-338 326842 £4.00 HITACHI DECODER-TELETEXT PC232A5 - ISSUE 4 £15.00 HEAD AND DRUM - 620E £12.00 MAINS SWITCH WITH STAND-BY £50p MODULATOR No. 5587881 £5.00 OSCILLOSCOPE 20MHZ DOUBLE BEAM - V212 £188.00 PANEL-TELETEXT GSP - ISSUE 6 £10.00 PANEL-TELETEXT GSP - ISSUE 6 £10.00 PANEL-TELETEXT V7753E £20.00 POWER SUPPLY VIDEO SWITCH MODE \$8.00 STR 4211 ISUE 10 £8.00 POWER SUPPLY VIDEO SWITCH MODE ¥10.00 THCK, FILM-HM9204A £3.50 FMODULES: \$827-51 EACH £3.00	- 8 BI	JTTONS 01M	4-515-0	002	£5.00	
PANEL-TUNING 1509G-TX9, TX10 £5.00 POWER SUPPLY 12V-3A FOR VIDEOSTAR CAMERA PP3 £4.00 PUSH BUTTON UNIT-TX85, TX86- 8 BUTTONS £5.00 TRANSFORMERS-SWITCH MODE:- TX85, TX86 8 BUTTONS £5.00 TX85, TX86, TX89 EACH £4.00 £5.00 TX100 £5.00 473190-00, 40153000 EACH £5.00 ICC5 3112-338 326842 £4.00 HITACHI DECODER-TELETEXT PC232A5 - ISSUE 4 £15.00 HEAD AND DRUM - 620E £12.00 MAINS SWITCH WITH STAND-BY £50p MODULATOR NG 5587881 £5.00 OSCILLOSCOPE 20MHZ DOUBLE BEAM - V212 £188.00 PANEL-TELETEXT G8P - ISSUE 6 £10.00 PANEL-TELETEXT C3P - ISSUE 6 £10.00 PANEL-TELETEXT VC352E £20.00 POWER SUPPLY VIS WITCH MODE \$8.00 STR 4211 ISSUE 10 £8.00 POWER SUPPLY VIDEO SWITCH MODE VTM312ELM VTM312ELM £10.00 THICK, FILM-HM9204A £3.50 FOODULES: 5827-01-51, 5827-51 S824-04-10,	PANEL-	TUBE-BASE-	TX89.	TX98, TX99	£5.00	
POWER SUPPLY 12V-3A FOR VIDEOSTAR CAMERA PP3 £4.00 PUSH BUTTON UNIT-TX85, TX86- 8 BUTTONS £5.00 TRANSFORMERS-SWITCH MODE:- TX85, TX86, TX89 EACH £4.00 TX85, TX86, TX89 EACH £4.00 £5.00 473190-00, 40153000 EACH £5.00 ICC5 3112.338 326842 £4.00 HITACHI DECODER-TELETEXT PC232A5 - ISSUE 4 £15.00 HEAD AND DRUM - 620E £12.00 MAINS SWITCH WITH STAND-BY £50p MODULATOR No, 5587881 £5.00 OSCILLOSCOPE 20MHZ DOUBLE BEAM - V212 C188.00 PANEL-TELETEXT G8P - ISSUE 6 £10.00 PANEL-TELETEXT G8P - ISSUE 6 £10.00 PANEL-TELETEXT V753E £20.00 POWER SUPPLY VIS WITCH MODE S8.00 STR 4211 ISUE 10 £8.00 POWER SUPPLY VIDEO SWITCH MODE VTM312ELM £10.00 THICK, FILM-HM9204A £3.50 HOSIDEN TUBE BASE - MIXED 10 for £1.00 AA Bateries made by STC Group of Companies 10p each ITT IF MODULES: 5827-51 EAC	PANEL-	TUNING 150	G-TX	9. TX10	£5.00	
PUSH BUTTON UNIT: TX85, TX86- 8 BUTTONS £5.00 TRANSFORMERS-SWITCH MODE: TX85, TX86, TX89 EACH £4.00 TX85, TX86, TX89 EACH £4.00 £5.00 473190-00, 40153060 EACH £5.00 ICC5 3112.338 326842 £4.00 HITACHI DECODER. TELETEXT PC232A5 - ISSUE 4 £15.00 HEAD AND DRUM - 620E £12.00 MAINS SWITCH WITH STAND-BY £50p MODULATOR NO. 5587881 £5.00 OSCILLOSCOPE 20MHZ DOUBLE BEAM - V212 £188.00 PANEL-TELETEXT G8P - ISSUE 6 £10.00 PANEL-TELETEXT G8P - ISSUE 6 £10.00 PANEL-TELETEXT V7753E £20.00 POWER SUPPLY VISEO SWITCH MODE STR 4211 ISSUE 10 STR 4211 ISSUE 10 £8.00 POWER SUPPLY VIDEO SWITCH MODE VTM312ELM £10.00 THICK, FILM-HM9204A £3.50 HOSIDEN 10p each 10p each TUBE BASE - MIXED 10 for £1.00 AB atteries made by STC Group of Companies 10p each ITT IF MODULES: 5827-01-51, 5827-51 EACH £3.00	POWER	SUPPLY 12V	-3A Tamfi	A PP3	£4.00	
8 BUTTONS £5.00 TRANSFORMERS-SWITCH MODE: TX85, TX86, TX89 EACH £4.00 TX100 £5.00 473190-00, 401530800 EACH £5.00 ICC5 3112-338 326842 £4.00 HITACHI DECODER-TELETEXT PC232A5 - ISSUE 4 £15.00 HEAD AND DRUM - 620E £12.00 MAINS SWITCH WITH STAND-BY £50p MODULATOR NO 5587881 £5.00 OSCILLOSCOPE 20MHZ DOUBLE BEAM - V212 £188.00 PANEL-TELETEXT G8P - ISSUE 6 £10.00 PANEL-TELETEXT C3P - ISSUE 6 £10.00 PANEL-TELETEXT V7753E £20.00 POWER SUPPLY VISENTCH MODE STR 4211 ISSUE 10 STR 4211 ISSUE 10 £8.00 POWER SUPPLY VIDEO SWITCH MODE VTM312ELM VTM312ELM £10.00 THICK, FILM-HM9204A £3.50 HOSIDEN 10p each TUBE BASE - MIXED 10 for £1.00 SABateries made by STC Group of Companies 10p each ITT IF MODULES: 5827-01-51, 5827-51 EACH £3.00 S28-04-10, 5829-02-58 EACH £3.00	PUSH B	UTTON UNIT	-TX85	TX86 -	1,4.00	
TX85.7X86.7X89 EACH 54.00 TX85.7X86.7X89 EACH 55.00 ICC5 3112.338 326842 £4.00 HITACHI ECODER.TELETEXT PC232A5 - ISSUE 4 DECODER.TELETEXT PC232A5 - ISSUE 4 £15.00 HEAD AND DRUM - 620E £12.00 MAINS SWITCH WITH STAND-BY £50p MODULATOR No. 5587881 £5.00 OSCILLOSCOPE 20MHZ DOUBLE BEAM - V212 CR88.00 PANEL-TELETEXT G8P - ISSUE 6 £10.00 PANEL-TELETEXT G8P - ISSUE 6 £10.00 PANEL-TELETEXT C3P - ISSUE 6 £10.00 PANEL-TELETEXT V7753E £20.00 POWER SUPPLY VISEO SWITCH MODE STR 4211 ISSUE 10 STR 4211 ISSUE 10 £8.00 POWER SUPPLY VIDEO SWITCH MODE VTM312ELM VTM312ELM £10.00 THICK, FILM-HM9204A £3.50 HOSIDEN 10p each TUBE BASE - MIXED 10 for £1.00 SABateries made by STC Group of Companies 10p each ITT IF MODULES: 5827-01-51, 5827-51 EACH £3.00 5828-04-10, 5829-02-58 EACH £3.00 5828-04-10, 5829-02-58 EACH £3.00 5929-03-41 E	8 BUT	TTONS	UTCU	MODE.	£5.00	
TX 100 £5.00 473190-00, 40153000 EACH £5.00 ICC5 3112-338 326842 £4.00 HITACHI ECODER-TELETEXT PC232A5 - ISSUE 4 DECODER-TELETEXT PC232A5 - ISSUE 4 £15.00 HEAD AND DRUM - 620E £12.00 MAINS SWITCH WITH STAND-BY £50p MODULATOR NO 5587881 £5.00 OSCILLOSCOPE 20MHZ DOUBLE BEAM - V212 £188.00 PANEL-TELETEXT G8P - ISSUE 6 £10.00 PANEL-TELETEXT G8P - ISSUE 6 £10.00 PANEL-TELETEXT V7753E £20.00 POWER SUPPLY VISEO SWITCH MODE STR 4211 ISSUE 10 £8.00 POWER SUPPLY VIDEO SWITCH MODE VTM312ELM £10.00 THICK, FILM-HM9204A £3.50 HOSIDEN £10.00 TILETEXT CONVERSION KIT TUBE BASE - MIXED 10 for £1.00 ABatteries made by STC Group of Companies 10p each ITT IF MODULES: 5827-01-51, 5827-51 EACH £3.00 5828-04-10, 5829-02-58 EACH £3.00 5828-04-10, 5829-02-58 EACH £3.00 5929-03-41 EACH £3.00 5929-03-41	TX85	TX86. TX89	AUCH	EACH	£4.00	
473190-00, 40153000 EACH £5.00 ICC5 3112-338 326842 £4.00 HITACHI ECODER-TELETEXT PC232A5 - ISSUE 4 DECODER-TELETEXT PC232A5 - ISSUE 4 £15.00 HEAD AND DRUM - 620E £12.00 MAINS SWITCH WITH STAND-BY £50p MODULATOR NO 5587881 £5.00 OSCILLOSCOPE 20MHZ DOUBLE BEAM - V212 COSCILLOSCOPE 20MHZ DOUBLE BEAM - V212 PANEL-TELETEXT G8P - ISSUE 6 £10.00 PANEL-TELETEXT C3P - ISSUE 6 £10.00 PANEL-TELETEXT V7753E £20.00 POWER SUPPLY VISEO SWITCH MODE STR 4211 ISSUE 10 £8.00 POWER SUPPLY VIDEO SWITCH MODE VTM312ELM £10.00 THCK, FILM-HM9204A £3.50 HOSIDEN TUBE BASE - MIXED 10 for £1.00 AA Batteries made by STC Group of Companies 10p each ITT IF MODULES: 5827-01-51, 5827-51 EACH £3.00 5828-04-10, 5829-02-58 EACH £3.00 5828-04-10, 5829-02-58 EACH £3.00 5929-03-41 EACH £3.00 5929-03-41 EACH £3.00 5929-03-41 EACH £3.00 109 600 POST £4.00 POST £4.00	TX10	0			£5.00	
Intervention Status HITACHI DECODER-TELETEXT PC232A5 - ISSUE 4 £15.00 HEAD AND DRUM - 620E MAINS SWITCH WITH STAND-BY £500 MODULATOR NO 5587881 £500 OSCILLOSCOPE 20MHZ DOUBLE BEAM - V212 £188.00 PANEL-TELETEXT G8P - ISSUE 6 £10.00 PANEL-TELETEXT G8P - ISSUE 6 £10.00 PANEL-TELETEXT G8P - ISSUE 6 £10.00 PANEL-TELETEXT V7753E £20.00 POWER SUPPLY VISEO SWITCH MODE STR 4211 ISSUE 10 STR 4211 ISSUE 10 £8.00 POWER SUPPLY VIDEO SWITCH MODE VTM312ELM VTM312ELM £10.00 THICK, FILM-HM9204A £3.50 HOSIDEN TUBE BASE - MIXED 10 for £1.00 AA Batteries made by STC Group of Companics 10p each ITT IF MODULES: 5827-01-51, 5827-51 EACH £3.00 5828-04-10, 5829-02-58 EACH £3.00 5828-04-10, 5829-02-58 EACH £3.00 S929-03-41 EACH £3.00 5929-03-41 EACH £3.00 5929-03-41<	47319	0-00, 4015300	10 247	EACH	£5.00	
HITACHI DECODER-TELETEXT PC232A5 - ISSUE 4 £15.00 HEAD AND DRUM - 620E £12.00 MAINS SWITCH WITH STAND-BY £50p MODULATOR No 5587881 £5.00 OSCILLOSCOPE 20MHZ DOUBLE BEAM - V212 V212 £188.00 PANEL-TELETEXT OSP - ISSUE 6 £10.00 PANEL-TELETEXT PC315-11 - ISSUE 7 £15.00 PANEL-TELETEXT V7753E £20.00 POWER SUPPLY VISEO SWITCH MODE STR 4211 ISSUE 10 £8.00 POWER SUPPLY VIDEO SWITCH MODE VTM312ELM £10.00 THICK, FILM-HM9204A £3.50 HOSIDEN £10.00 TUBE BASE - MIXED 10 for £1.00 ABatteries made by STC Group of Companics 10p each ITT IF MODULES: 5827-51 EACH £3.00 5828-04-10, 5829-02-58 EACH £3.00 5828-04-10, 5829-02-58 EACH £3.00 5828-04-10, 5829-02-58 EACH £3.00 5929-03-41 EACH £3.00		5112 500 520		-		
DECODER-TELETEXT PC.22AS - ISSUE 4 £15.00 HEAD AND DRUM - 620E £12.00 MAINS SWITCH WITH STAND-BY £50p MODULATOR No.5587881 £5.00 OSCILLOSCOPE 20MHZ DOUBLE BEAM - V212 V212 £188.00 PANEL-TELETEXT G8P - ISSUE 6 £10.00 PANEL-TELETEXT PC315-11 - ISSUE 7 £15.00 PANEL-TELETEXT PC315-11 - ISSUE 7 £15.00 PANEL-TELETEXT VT753E £20.00 POWER SUPPLY VIV SWITCH MODE STR 421 ISSUE 10 STR 421 ISSUE 10 £8.00 POWER SUPPLY VIDEO SWITCH MODE VTM312ELM VTM312ELM £10.00 THICK, FILM-HM9204A £3.50 HOSIDEN TUBE BASE - MIXED 10 for £1.00 AA Batteries made by STC Group of Companies 10p each ITT IF MODULES: 5827-01-51, 5827-51 EACH £3.00 5828-04-10, 5829-02-58 EACH £3.00 5828-04-10, 5829-02-58 EACH £3.00 S929-03-41 EACH £3.00 5929-03-41 EACH £3.00 5929-03-41 EACH £3.00 1D906/7 MATSUI 10p <td>HITA</td> <td>CHI</td> <td></td> <td>10.10</td> <td></td> <td></td>	HITA	CHI		10.10		
HEAD AND DRUM - 620E £12.00 MAINS SWITCH WITH STAND-BY £50p MODULATOR No. 5587881 £5.00 OSCILLOSCOPE 20MHZ DOUBLE BEAM - V212 V212 £188.00 PANEL-TELETEXT G8P - ISSUE 6 £10.00 PANEL-TELETEXT PC315-11 - ISSUE 7 £15.00 PANEL-TELETEXT PC315-11 - ISSUE 7 £15.00 PANEL-TELETEXT VT753E £20.00 POWER SUPPLY VTV SWITCH MODE STR 421 ISSUE 10 £8.00 POWER SUPPLY VIDEO SWITCH MODE VTM312ELM £10.00 THICK, FILM-HM9204A £3.50 HOSIDEN TUBE BASE - MIXED 10 for £1.00 ABatteries made by STC Group of Companics 10p each ITT IF MODULES: 5827-01-51, 5827-51 EACH £3.00 5828-04-10, 5829-02-58 EACH £3.00 5828-04-10, 5829-02-58 EACH £3.00 S929-03-41 EACH £3.00 5929-03-41 EACH £3.00 TELETEXT CONVERSION KIT £3.00 POST £4.00 POST £4.00 %0p BUTTAF 50p BUWA 10p %0p BUWA <t< td=""><td>DECOD</td><td>CK-IELEIEA</td><td>I PC2</td><td>32A3 - 1330</td><td>£ 4 £15.00</td><td></td></t<>	DECOD	CK-IELEIEA	I PC2	32A3 - 1330	£ 4 £15.00	
MAINS SWITCH WITH STAND-BY £50p MODULATOR No.5587881 £5.00 OSCILLOSCOPE 20MHZ DOUBLE BEAM - V212 V212 £188.00 PANEL-TELETEXT G8P - ISSUE 6 £10.00 PANEL-TELETEXT PC315-11 - ISSUE 7 £15.00 PANEL-TELETEXT PC315-11 - ISSUE 7 £15.00 PANEL-TELETEXT PC315-11 - ISSUE 7 £15.00 PANEL-TEXT-VT753E £20.00 POWER SUPPLY TV SWITCH MODE STR 421 ISSUE 10 £8.00 POWER SUPPLY VIDEO SWITCH MODE VTM312ELM £10.00 THICK, FILM-HM9204A £3.50 HOSIDEN TUBE BASE - MIXED 10 for £1.00 AA Batteries made by STC Group of Companies IOp each ITT IF MODULES: 5827-01-51, 5827-51 EACH £3.00 S529-03-41 EACH £3.00 5828-04-10, 5829-02-58 EACH £3.00 5929-03-41 TELETEXT CONVERSION KIT £3.00 POST £4.00 POST £4.00 Øp BUTTAF \$0p BUWAT \$0p Øp BUTTAF \$0p BUWAT \$0p Øp B	HEAD A	ND DRUM -	620E		£12.00	
MODULATION JOINT 22.00 OSCILLOSCOPE 20MHZ DOUBLE BEAM - V212 V212 €188.00 PANEL-TELETEXT G8P - ISSUE 6 £10.00 PANEL-TELETEXT PC315-11 - ISSUE 7 £15.00 PANEL-TELETEXT PC315-11 - ISSUE 7 £15.00 PANEL-TELETEXT PC315-11 - ISSUE 7 £15.00 PANEL-TEXT-VT753E £20.00 POWER SUPPLY TV SWITCH MODE STR 421 ISSUE 10 £8.00 POWER SUPPLY VIDEO SWITCH MODE VTM312ELM £10.00 THICK, FILM-HM9204A £3.50 HOSIDEN TUBE BASE - MIXED 10 for £1.00 AA Batteries made by STC Group of Companies 10p each ITT IF MODULES: 5827-01-51, 5827-51 EACH £3.00 5828-04-10, 5829-02-58 EACH £3.00 5828-04-10, 5829-02-58 EACH £3.00 S929-03-41 EACH £3.00 5929-03-41 EACH £3.00 TELETEXT CONVERSION KIT £3.00 POST £4.00 POST £4.00 %0p BUTTAF 50p BUTTAF 10p %0p BUTTAF 50p BUTTAF 10p	MAINS	ATOR No 55	H STA	ND-BY	£50p	
V212 €188.00 PANEL-TELETEXT G8P - ISSUE 6 £10.00 PANEL-TELETEXT PC315-11 - ISSUE 7 £15.00 PANEL-TEXT-VT753E £20.00 POWER SUPPLY TV SWITCH MODE STR 4211 ISSUE 10 £8.00 POWER SUPPLY VIDEO SWITCH MODE VTM312ELM £10.00 THTAI ISSUE 10 £8.00 POWER SUPPLY VIDEO SWITCH MODE VTM312ELM £10.00 THKEXT.FILM-HM9204A £3.50 HOSIDEN TUBE BASE - MIXED 10 for £1.00 AA Batteries made by STC Group of Companics 10p each ITT IF MODULES: 5827-01-51, 5827-51 EACH £3.00 5828-04-10, 5829-02-58 EACH £3.00 5828-04-10, 5829-02-58 EACH £3.00 CORE 2 90° ITT TEXT PANEL £3.00 CORE 2 90° ITT TEXT PANEL £3.00 I996/7 MATSUI VIDEO CHASSIS WITH TUNER-IR £5.00 POST £4.00 ⁶⁰ 0 BUTIAF 500 BUTIAF 500 ^{61.00} 10 BUTIAF 500 BUTIAF 100 ^{61.00} 80 BUTIAF 500 BUTIAF 100	OSCILL	OSCOPE 20N	HZ DO	UBLE BEA	M	
PANEL-TELETEXT PC315-11 - ISSUE 0 £10.00 PANEL-TELETEXT PC315-11 - ISSUE 7 £15.00 PANEL-TEXT-VT753E £20.00 POWER SUPPLY TV SWITCH MODE STR 4211 ISSUE 10 £8.00 POWER SUPPLY VIDEO SWITCH MODE STR 4211 ISSUE 10 £8.00 POWER SUPPLY VIDEO SWITCH MODE VTM312ELM £10.00 THICK, FILM-HM9204A £3.50 HOSIDEN TUBE BASE - MIXED 10 for £1.00 AA Batteries made by STC Group of Companies 10p each ITT IF MODULES: 5827-01-51, 5827-51 EACH £3.00 S929-03-41 EACH £3.00 5929-03-41 EACH £3.00 CORE 2 90° ITT TEXT PANEL £3.00 CORE 2 90° ITT TEXT PANEL £3.00 1996/7 MATSUI VIDEO CHASSIS WITH TUNER-IR £5.00 POST £4.00 ⁶⁰⁰ BUTHAF 500 BWWST 100 100 ⁶¹⁰⁰ BUTHAF 500 BWWST 100 100 ⁶¹⁰⁰ BUTHAF 500 BWWST 100 100 ⁶¹⁰⁰ BUTHAF 500 BWWST 100 100	V212 PANEL	TELETEVT	9D 19	E SLIE 6	188.00	
£15.00 PANEL-TEXT-VT753E £20.00 POWER SUPPLY TV SWITCH MODE STR 4211 ISSUE 10 £8.00 POWER SUPPLY TV SWITCH MODE STR 4211 ISSUE 10 £8.00 POWER SUPPLY VIDEO SWITCH MODE VTM312ELM £10.00 THICK, FILM-HM9204A £3.50 HOSIDEN TUBE BASE - MIXED 10 for £1.00 AA Batteries made by STC Group of Companies 10p each ITT IF MODULES: 5827-01-51, 5827-51 EACH £3.00 5828-04-10, 5829-02-58 EACH £3.00 5929-03-41 TELETEXT CONVERSION KIT £3.00 CORE 2 90" ITT TEXT PANEL £3.00 1996/7 MATSUI VIDEO CHASSIS WITH TUNER-IR £5.00 POST £4.00 *0p BUTTAF 50p BUTTAF 10p *109 BUTTAF 50p BUTTAF 10p *109 BUTTAF 50p BUTTAF 10p *40p BUTTAF 50p BUTTAF 10p *40p BUTTAF 50p BUTTAF 10p *40p BUTTAF 50	PANEL-	TELETEXT P	C315-1	I - ISSUE 7	10.00	
PANEL-TEXT-VT753E £20.00 POWER SUPPLY TV SWITCH MODE STR 4211 ISSUE 10 £8.00 POWER SUPPLY VIDEO SWITCH MODE VTM312ELM £10.00 VTM312ELM £10.00 THICK, FILM-HM9204A £3.50 HOSIDEN TUBE BASE - MIXED 10 for £1.00 AA Batteries made by STC Group of Companies 10p each ITT IF MODULES: 5827-01-51, 5827-51 EACH £3.00 5828-04-10, 5829-02-58 EACH £3.00 5828-04-10, 5829-02-58 EACH £3.00 TELETEXT CONVERSION KIT £3.00 CORE 2 90° ITT TEXT PANEL £3.00 I996/7 MATSUI VIDEO CHASSIS WITH TUNER-IR £5.00 POST £4.00 ⁶⁰⁰ BUTTAF 500 BUTTAF 100 ⁶¹⁴⁰ BUTTAF 500 BUTTAF 100 ⁶¹⁴⁰ BUTTAF 500 BUTTAF 100 ⁶⁴⁰ BUTTAF 500 BUTTAF 100 ⁶⁴⁰ BUTTAF 500 BUWES 100 ⁶⁴⁰ BUTTAF 500 BUWES 100 </td <td></td> <td></td> <td>_</td> <td></td> <td>£15.00</td> <td></td>			_		£15.00	
STR 4211 ISSUE 10 £8.00 POWER SUPPLY VIDEO SWITCH MODE VTM312ELM £10.00 VTM312ELM £10.00 THICK, FILM-HM9204A £3.50 HOSIDEN TUBE BASE - MIXED 10 for £1.00 AA Batteries made by STC Group of Companies 10p each ITT IF MODULES: 5827-01-51, 5827-51 EACH £3.00 5828-04-10, 5829-02-58 EACH £3.00 5828-04-10, 5829-02-58 EACH £3.00 TELETEXT CONVERSION KIT £3.00 CORE 2 90° ITT TEXT PANEL £3.00 1996/7 MATSUI VIDEO CHASSIS WITH TUNER-IR £5.00 POST £4.00 ***** \$************************************	PANEL-	SUPPLY TV	E Switc	HMODE	\$20.00	
POWER SUPPLY VIDEO SWITCH MODE VTM312ELM £10.00 THICK, FILM-HM9204A £3.50 HOSIDEN TUBE BASE - MIXED 10 for £1.00 TUBE BASE - MIXED 10 for £1.00 AA Batteries made by STC Group of Companies 10p each ITT IF MODULES: 5827-01-51, 5827-51 EACH £3.00 5828-04-10, 5829-02-58 EACH £3.00 5929-03-41 EACH £3.00 TELETEXT CONVERSION KIT £3.00 CORE 2 90° ITT TEXT PANEL £3.00 1996/7 MATSUI VIDEO CHASSIS WITH TUNER-IR £5.00 POST £4.00 ************************************	STR 4	211 ISSUE 10			£8.00	
HOD ZEEN 210.00 HICK, FILM-HM9204A £3.50 HOSIDEN TUBE BASE - MIXED 10 for £1.00 AA Batteries made by STC Group of Companies 10p each IFT IF MODULES: 5827-01-51, 5827-51 EACH £3.00 5828-04-10, 5829-02-58 EACH £3.00 5828-04-10, 5829-02-58 EACH £3.00 TELETEXT CONVERSION KIT £3.00 CORE 2 90° ITT TEXT PANEL £3.00 I996/7 MATSUI VIDEO CHASSIS WITH TUNER-IR £5.00 POST £4.00 90p BUTH AF £1.00 BWWSC 10p 140 BUTH AF £1.00 BWWSC 10p 150 BUTH AF \$20p BWWSC 10p 160 BUTH AF \$20p BYUE \$20p 160 BUWSC 10p BYUE \$20p \$20p 160 BUWSC 10p BYUE \$20p \$20p	POWER	SUPPLY VID	EO SW	TTCH MOD	E 00	
HOSIDEN TUBE BASE - MIXED 10 for £1.00 AA Batteries made by STC Group of Companies 10p each ITT ITT FMODULES: 5827-01-51, 5827-51 EACH £3.00 5827-01-51, 5827-51 EACH £3.00 S827-01-51, 5827-51 EACH £3.00 S829-02-58 EACH £3.00 CORE 2 90° ITT TEXT PANEL £3.00 CORE 2 90° ITT TEXT PANEL £3.00 POST £4.00 POST £4.00 POST £4.00 BYWER 100	THICK.	FILM-HM920	4A		£3.50	
ACOSIDILET Signature AROSIDILET AROSIDILET AROSIDILET INTER BASE – MIXED 10 for £1.00 AA Batteries made by STC Group of Companies 10p each 10p each ITT IF MODULES: 5827-01-51, 5827-51 EACH £3.00 5828-04-10, 5829-02-58 EACH £3.00 5929-03-41 EACH £3.00 5929-03-41 EACH £3.00 CORE 2 90° ITT TEXT PANEL £3.00 CORE 2 90° ITT TEXT PANEL £3.00 CORE 2 90° ITT TEXT PANEL £3.00 1996/7 MATSUI VIDEO CHASSIS WITH TUNER-IR £5.00 POST £4.00 60p BUTH AF £1.00 BY WHS 10p £1.00 BUTH AF £1.00 BY WHS 10p	HOST	DEN	-	_		
AA Batteries made by STC Group of Companies 10p each IDP each ITT IF MODULES: 5827-01-51, 5827-51 EACH £3.00 5828-04-10, 5829-02-58 EACH £3.00 5929-03-41 EACH £3.00 TELETEXT CONVERSION KJT £3.00 CORE 2 90° ITT TEXT PANEL £3.00 1996/7 MATSUI VIDEO CHASSIS WITH TUNER-IR £5.00 POST £4.00 POST £4.00 BYWST 10p £1.00 BYWST 10p BYWST 10p £1.00 BUTTLAF 50p BYWST 10p £1.00 BYWST 10p BYXT 10p £1.00 BYWST 10p BYXT 10p £1.00 BYXT 10p Sop £1.00 BYXT 10p Sop £1.00 BYXT 10p Sop £1.00 BYXT 10p Sop	TUBE B	ASE - MIXEI	0 10 for		£1.00	
10p each ITT IF MODULES: 5827-01-51, 5827-51 EACH £3.00 5828-04-10, 5829-02-58 EACH £3.00 5929-03-41 EACH £3.00 5929-03-41 EACH £3.00 TELETEXT CONVERSION KJT £3.00 CORE 2 90° ITT TEXT PANEL £3.00 1996/7 MATSUI VIDEO CHASSIS WITH TUNER-IR £5.00 POST £4.00 POST £4.00 BYWST 10p 10p £1.00 BITTI AF £1.00 BYWST 10p 12p £1.00 BUTTI AF £1.00 BYWST 10p 13p £1.00 £1.00 BUTTI AF £1.00 BYWST 10p 13p £1.00 BYWST 10p £1.00 BUTT AF £1.00 BYWST 10p 13p £1.00 BYWST 10p £1.00 BUTT AF £1.00 BYWST 10p 13p £1.00 BYWST 10p £1.00 BUTT AF £1.00 BYTT 10p 25p BYTT 10p 25p BYTT 10p 20p 40p BYTT 10p 20p 40p BYTT 10p<	AA Batt	eries made by	STC G	eup of Com	panies	
ITT IF MODULES: 5827-01-51,5827-51 EACH £3.00 5827-01-51,5827-51 EACH £3.00 5828-02-02-58 EACH £3.00 5929-03-41 EACH £3.00 CORE 2 90° ITT TEXT PANEL 1996/7 MATSUI VIDEO CHASSIS WITH TUNER-IR F100 POST £4.00 POST £4.00 BUTH 4- £1.00		-		10	p each	
IF MODULES: 5827-01-51,5827-51 EACH £3.00 5828-04-10,5829-02-58 EACH £3.00 5929-03-41 EACH £3.00 TELETEXT CONVERSION KIT £3.00 CORE 2 90° ITT TEXT PANEL £3.00 CORE 2 90° ITT TEXT PANEL £3.00 I996/7 MATSUI VIDEO CHASSIS WITH TUNER-IR £5.00 POST £4.00 000 113 £1.00 800 800 800 807 800 807 800 807 807	ITT					
3827-01-31,3827-31 EACH 83.00 5828-04-10,5829-02-58 EACH 83.00 5929-03-41 EACH 83.00 TELETEXT CONVERSION KIT £3.00 CORE 2 90° ITT TEXT PANEL £3.00 1996/7 MATSUI VIDEO CHASSIS WITH TUNER-IR £5.00 POST £4.00 POST £4.00 60p BUTH AF £1.00 BUTH AF £1.00 BYWST 159 BUTH AF £1.00 FL00 BUTH AF £1.00 BUTH AF 60p BYWST ALEW SP 60p BUTH AF 60p 80p BUTH AF 50p 60p BUTH AF 60p 80p BUTH AF 50p 80p BUTH AF 60p 60p BUTH AF 50p 60p BUTH AF 60p 60p	IF MOD	ULES:-		FIC		
5929-03-41 EACH £3.00 TELETEXT CONVERSION KIT £3.00 CORE 2 90° ITT TEXT PANEL £3.00 1996/7 MATSUI £3.00 VIDEO CHASSIS WITH TUNER-IR £5.00 POST £4.00 POST £4.00 60p BUTH AF £1.00 BUTH AF £1.00 BWWST 10p £1.00 BUTH AF £1.00 BVWST 10p £1.00 BUTH AF £1.00 BVWST 10p £1.00 BUTH AF £1.00 BVWST 10p £1.01 BUTH AF £5.00 BUTH AF 20p F1.02 BUTH AF 600 BVWST 10p £1.01 BUTH AF 50p B1X100 10p £1.61 BUTH AF 50p B1X100 10p £1.62 BUTH AF \$0p B1X100 10p £1.61 BUTH AF \$0p B1X100 10p £1.62 BUTH AF \$0p B1X100 10p £1.62	5828-	01-51, 5827-51	2-58	EACH	£3.00	
TELETEXT CONVERSION KIT £3.00 CORE 2 90° ITT TEXT PANEL £3.00 1996/7 MATSUI \$3.00 VIDEO CHASSIS WITH TUNER-IR £5.00 POST £4.00 POST £4.00 60p BUTHAF \$100 1111 \$20p WW 5 \$10p 1113 £1.00 BWWSC \$10p 1113 \$100 BYWSC \$10p 1113 \$100 BYWSC \$10p 1140 BUTHAF \$10p \$10p \$10p 1140 BUNKAF \$10p \$10p \$10p 1140 BUNKAF \$10p \$10p \$10p 1140 BUNKAF \$10p	5929-	03-41		EACH	£3.00	
1996/7 MATSUI VIDEO CHASSIS WITH TUNER-IR £5.00 POST £4.00 POST £4.00 60p BUTHA 20p BYWS* 15p 75p BUTHA 20p BYWS* 10p 60p BUTHA 20p BYWS* 10p 61.00 BUTHA 600 BYWS* 10p 640p BUTHA+ 61.00 BYX* 25p 640p BUTHA+ 61.00 BYX* 10p 640p BUTHA+ 61.00 BYX* 10p 640p BUTHA+ 54p BYX* 10p	TELETE CORE 2	ST CONVER	SION I	KJT EL	£3.00 £3.00	
1996/7 MATSUI VIDEO CHASSIS WITH TUNER-IR \$5.00 POST £4.00 POST £4.00 *00p BUTHA 20p 75p BUTHA 20p 75p BUTHA 20p 800p BUTHA 10p 61.00 BUTHA 100 80p BUTHA 100 80p BUTHA 10p 61.50 BUWHA 60p 80p BUTHA+ 61.00 90p BUTHA+ 61.00 90p BUWHA 60p 91.00 BUWHA 10p 61.60 BUWHA 60p 90p BUWHA 60p 90p BUWHA 50p 90p BUWHA 10p 60p BUWHA 10p 60p <t< td=""><td></td><td></td><td></td><td></td><td></td><td></td></t<>						
VIDEO CHASSIS WITH TUNER-IR 45.00 POST £4.00 POST £4.00 60p BUTHAF 50p 75p BUTHAF 20p 800 FWMS 10p 11.00 BUTHAF 61.00 80p BUTHAF 61.00 80p BUTHAF 61.00 90p BUTHAF 60p 90p BUTHAF 60p 90p BUTHAF 60p 90p BUTHAF 6	1996/7	MATSUI				
Opp BL TILLAF S0p BY Winter 15p 75p BL TILLA S0p BY Winter 10p EL00 BUTTLAF EL00 BY Winter 10p EL00 BUTTLAF S0p BY Winter 10p EL00 BUTTLAF S0p BY Winter 10p EL00 BUTTLAF S0p BY Winter 10p 40p BUX91 S0p BY Winter 10p 40p BUT91 S0p BY Winter 10p	VIDEO	CHASSIS WI	IN TUP	POST	£4.00	
00p BUTHAF 50p BYWS 15p 75p BUTHAF 20p FYWK 10p EL00 BUTHAF EL00 BYWS 10p EL00 BUTHAF EL00 BYWS 10p FL00 BUTHAF EL00 BYWS 10p FL00 BUTHAF EL00 BYWS 25p 90p BUTHAF EL00 BYWS 10p FL50 BUWA 40p BYL 10p 90p BUWA 60p BYL 10p FL60 BUWA 50p BYL 10p 60p BUSA 50p BYL 10p 60p BUSA 50p BYL 10p 90p BUSA 50p BYL 10p 90p BUSA 50p BYL 50p 90p BUSA 20p BUSA 50p 90p BUSA 20p BYL 50p						F
Line Division Division Lips Lips <thlips< th=""> <thlips< th=""> <thlips< th=""></thlips<></thlips<></thlips<>	60p 75p	BUTHAF	50p 20p	BYW S BYW S	15p 10p	
E1.50 B1.W.1 Jop B1.X.1 Jop B1.X.1 Jop 90p B1.W.1 60p B1.X.1 Jop	£1.00 £1.00	BUTI AF	£1.00	BYWSS A LC	0V 8p 10n	
£1,00 BUX £1,00 BYX 10p £1,00 BUX 50p BYX 20p 40p BUX 50p BYX 10p 90p BUX 50p BYX 10p 90p BUX 20p BZW 10p 90p BUX 20p BZW 10p	£1.50 90p	BUW11 BUW4	40p 60p	BY	25p 10p	
90p BLAN AT 50p BIZING 10p 90p BLAN 20p BZWC10 5p	£1.00	BUX	£1.00 50p	BYX mill BYX 21 mill BYX 21 mill	10p 20p	
allow pitor op proving op 1	40p 90p £1.00	BL 1 14 BY187	20p 5p	BZW13 C	3p	

MATSUI - ORION	COMPLETE REPAIR
DECKS WITH HEADS -	PINCH ROLLER, ID
D1096 VXA110 VP 9401 £16.00	
HEAD-VSR1500 = ORION D2096 £5.00	T
PANEL-MAIN-VSR 1500 P/P £5.00ea £3.00	IF TERC8-022A TBJ
OWER SUPPLY-VSR 1500 15.00	SATELLITE SXT230
TYPE STK \$343.VP9501 68.00	SATELLITE
OWER SUPPLY-SWITCH MODE-1500 £3.50	WITH BASE BAN
	SMALL UNF/VHF
AMSUNG TECU5983 VA24A	4944
/HF-Tuner with Aerial Socket	U321, U341, U342, U
Fit most new TV's £5	U344, U411, U412, U
FERGUSON NICAM MODULE III	U743, 7744
Art No 989 591-E00 £5	AMSTRAD
	UE33-BO1
VIDEO DECVE	MRF7-7E33
VIDEO DECKS	MAISULORION VIL
AIWA 1500	FERGUSUN
AATSULVAA TIUU	MTP2011_AP00
RION D1094 £5 £9 POST	UHF - ICC5
DRION D1096	VHF - ICC5
DRION D2096 ETC	TX85, TX86, TX89, 1
CAPSTAIN MOTOR FOR ABOVE DECKS	TX98, T99, TX100
£8.00	ORION
0 HIGH VOLTAGE CAPS 1500V - 2000V	1500 - UE33 BO9
MIXED \$1.00	PANASONIC
AL IV ADAPTOR - ROB EV OPH OUT \$5.00	SMALL UHF/VHF
	DOUBLE SIDE NIC
HANDSETS	ICC5 NICAM SINGL
MSTRAD	SHARP
680 £3.00	TUNER AND IF 1810
700 £5.00	TATUNG
000 £15.00	UNIVERSAL 205 OF
800 £4.00	WITH AERIAL SU
INIVERSAL £3,00	M
DECCA	HITACHI
TERCHICON	CAPSTAN 150E
EKGUSUN CI KA	MATSUI
V41R/3V59	CAPSTAN I/C NO. N
V41R/FV42 - FV51-52	2 TYPES 1995 TO 19
CC5 £7.00	VIDEO
K2000, 1K7000 EACH £4.00	AND HEAD
RD2, SRD3 SRD4 EACH £1.00	MITSUMI
780 £2.00	MOD MRF7-UF32
VISAILELINE WIINIPSI 25.00	MOD TMUG3-103A
TT2158 (NO REDIACEMENT) 55 00	MITSUBISHI
IDEO RM933E VIDEO PLUS £30.00	CAPSTAN-HSE41-I/
ATSUI	(D. 11 + D.
500 £5.00	Treble A Ba
/SR 1500 £4.00	
7X3080 £3.00	12v t
000/ORION - TV AND VIDEO £2.00	TV MODULATOR
C = PACE 900, FERGUSON, SONY,	AUDIO IV 10K
	HV100
M35 - VIDEO 55.00	
IOKIA	TV AERIALA
£4.00	1 WAY 20dB
7P9401	2 WAY 18dB
01(196	4 WAY 10dB
VIDEO PLUS	S WAY 40B
RION	
V AND VIDEO £2.00	COMPUTER 3
IDEO WITH LCD - 1992/93 MODELS \$5.00	LEADS
AMSUNG	2% METRES LONG
ANDSETS, TV & VIDEO - 12 TYPES EACH	2 METRES LONG -
£3.00	
ANYO	SCART TO SCART
INIVERSAL VIDEO £3.00	
No accounts	
	Z COMPONE
	ICNITON OUR
Gall A Sop 63 BISHOPSTI	CONTON, SHOE
-	SSET SSTRAF

KIT. CLUTCH AND LER D2906 £7.00 **JNERS** ZA-00ZA-ALPS £3.00 2180968 £3.00 D MIN SXT2302234 £4.00 £3.50 112A £4.00 343 944 EACH £2 £3.00 DEO TUNER IF £5.00 £5.00 £5.00 £5.00 £5.00 X90 EACH \$4.00 EACH £4.00 £4.00 £3.00 M £10 E BOARD ICC5 £10 587 PA1 UK £3.00 EQUIVALENT CKET £3.00 DTORS £3.00 156730 ASP £15.00 97 MODELS MATSUI PSTAN MOTOR P/P £5.00 £20.00 £5.00 £5.00 C M51782ASP £2.00 tteries 12 for £1 o 15 D.C. WITH LEADS £5 EACH MPS VHF /UHF EACH £5 EACH £5 EACH £5 EACH £5 PIN MAINS

BLACK EACH £1 - ALL PINS - 1 METRE EACH 60p No Credit Cards NTS BURYNESS,

EACH £1.50

- GREY

Tel: 01702 338894 Fax: 01702 338805 Specific P/P charges are PER ITEM • For UK addresses add P/P to order then 17.5% VAT to total. This applies to EC unless VAT No. is given • Exports - P/P at cost • Postal Order/Cheque with order. Unless otherwise specified add £1.70 P/P to SMALL ORDERS + Additional P/P for HEAVIER GOODS. Technical information by telephone only . Government/School Orders on official headings Callers to shop - 212 London Road, Southend-on-Sea Open Saturday Only 10-12noon - 2-5pm.

PLEASE ADD 17.5% VAT TO BOTH THE GOODS TOTAL AND P/P CHARGE

M3 M5 S1352 SAA1 SAA3 SAA5 SAA5

20p £5.09 4p £1.00 £1.00 £1.50 £1.50 £2.00 £2.00

15p 6p 5p 15p 15p 15p 15p 15p 15p 10p 12p 10p £1.00

H 11 0 HA11 5 HA11 5 HA11 HA11 1 HA11 51NT HA11 51NT HA11 51NT HA11 51 HA11 51

5p 10p £4,00 £1.00 £1.50 £1.50 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00 £1.00

£2.00



LETTERS

Send letters to "Television", Cumulus Business Media, Anne Boleyn House, 9-13 Ewell Road, Cheam, Surrey SM3 8BZ

or e-mail tessa2@btinternet.com using the subject heading 'Television Letters'.

Please send plain text messages. Do NOT send attachments. Type your full name, address, postcode, telephone number and e-mail address (if any).

Your address and telephone number will not be published unless requested, but your e-mail address will unless you state otherwise. Please send ONLY text intended for the letters page. Correspondence relating to subscriptions and other matters must be sent to the office address given above.

Health hazards

Following the letter headed ozone in the August issue, I'd like to clear up a couple of misconceptions. First, ozone isn't electrified air. The air we breathe contains about twenty per cent oxygen which, like most common gases, normally exists in the form of molecules that each contain two atoms. Oxygen can however take another form, with three atoms in the molecule. This is ozone. Pure ozone is a pale blue gas with a pungent smell. It's a powerful oxidising agent which is highly destructive to all forms of organic material and causes severe irritation to the respiratory system. It is very unstable, and rapidly breaks down to form normal diatomic oxygen. Ozone occurs when oxygen is subjected to electrical stress or exposed to short-wave ultraviolet radiation (UV-C) - the latter is the mechanism that maintains the stratospheric ozone layer.

A corona discharge forms small quantities of ozone and nitrogen oxides, all of which contribute to the characteristic smell. The quantities produced depend on the voltage and the current density. It's very unlikely that corona discharge in a domestic TV set could produce enough ozone to present any significant health hazard – the ozone will be rapidly breaking down, and natural room ventilation will dilute what's left. The air in even an apparently unventilated room is replaced completely every few hours via airbricks and diffusion through the walls.

Asthmatics are particularly sensitive to the respiratory irritation caused by ozone yet, speaking as an asthma sufferer myself, I cannot recall the smell from any TV corona ever causing me any distress – even as a teenager in the Sixties, when I was forever tinkering with old valve TV sets which were notorious for corona around their wired-in EHT rectifiers. The danger occurs when the 'cold' corona progresses to form an arc. Incidentally, air ionisers run at about -7.5kV, as corona discharge at this voltage forms copious quantities of ions with minimal ozone and nitrogen oxide production.

The plastic materials used in modern TV sets can produce very poisonous fumes when they burn. Take for example an arcing line output transformer. The potting compound will more than likely be polyurethane resin. This is not particularly flammable but will break down to produce, among other things, deadly hydrogen cyanide gas when it is subjected to the high temperature of an arc. Burning PVC insulation releases hydrogen chloride: when this is inhaled it is dissolved by the moisture in the lungs, producing hydrochloric acid. The toxic fumes from an established TV fire certainly do represent a serious health risk in the workshop as well as in the home.

I'm not sure how ionised air could be

made to explode. The only difference between ionised and neutral air is that some of the atoms in the former may have one more or one less electron in their outer (valence) shell - depending on whether the ionisation is negative or positive respectively. All natural air is slightly ionised, and heavily ionised air rapidly loses its 'charge'. There is no explosive mechanism involved otherwise thunderclouds would explode and no one would dare have an ioniser in their home. The polarity of any ionisation is important from a health point of view. Negative ions cause brain chemistry changes that lead to a feeling of wellbeing. Positive ionisation produced by corona discharge in a TV set has the opposite effect.

A line output transformer fault may produce internal heating without rupture of the casing. In this situation the heated plastics cannot burn, as there is no oxygen present. They break down instead. forming volatile hydrocarbons of which some are gaseous. The internal pressure builds up, and eventually the outer casing of the transformer bursts. If an arc is present, the vapours released may ignite. This, together with the noise of the transformer's case bursting. may give a passable impression of an explosion! *Pete Roberts, Runcorn, Cheshire.*

Goodmans TVs

Have you tried to repair a Goodmans TV set or VCR bought from Comet recently? We have just been told by Comet's head office that the company will no longer supply circuit information or spare parts to independent service engineers. Thus when any product sold by Comet develops a fault after the guarantee period the customer has to either return it to Comet for repair or buy something new. Is Comet advising customers at the point of sale that they will be tied to the company for service?

Is this going to be another nail in the coffin for independent service engineers? As a small company we can have little influence with the big boys in the trade. If we could get together with other independents and large spares suppliers however, maybe our voice would be heard.

Is there any help or hope out there? N.D. Bottrill and D.K. Veitch, NDC Electronics, 290 Prince of Wales Road, Sheffield S2 1FF. e-mail ndcelectronics@aol.com

CRT testing

Here's a quick way of assessing the condition of a colour CRT if you don't have a tester to hand. Check the voltages across the flashover protection resistors that are connected in series with the three cathodes. The voltage across a resistor is proportional to the current through it, in this case the beam current, which in turn depends on the cathode emission.

If, when checking these voltages, you notice that one differs markedly from the others, you can be pretty sure that the relevant cathode's emission is low. This would mean that the CRT is the cause when the symptom is a poor or missing primary colour.

The cathode voltage with respect to chassis is the check for the operation of an output stage of course. *Miodrag Krajcinovic*, *Belgrade, Yugoslavia*.

The 11AK08 and 11AK10 chassis

In the February 2000 issue of *Television* Alan Dent wrote about servicing the Vestel-manufactured 11AK08 and 11AK10 chassis. The model numbers he listed are no longer useful however as they relate to NEI and Nikkai sets. They will get you nowhere nowadays when ordering spares. The 11AK08 chassis was used in the Alba Model CTV3459 and the 11AK10 in the Alba Model CTV4889.

The chopper transformer is notorious for going short-circuit on the primary side. It can be obtained from CPC, the part no. being AB42003900 for the 11AK08 chassis and AB4040504910 for the 11AK10 chassis. The special version of the TDA8362A jungle chip (IC401) used in these sets has been mentioned on a couple of occasions. It's available, but is expensive. Some sets were fitted with the TDA8361A. I have found that the TDA8361AN3, which is available for about £6.50 from A.R.D. Electronics (01282 683 000), will work all right as a replacement for either of these chips. John Hepworth.

Peterlee, Co. Durham.

Dodgy mouse operation

Because I smoke, I tend to suffer from computer mouse reliability problems. The tobacco tar deposits that accumulate on the mouse mat get picked up by the ball and are transferred to the rollers. This occurs with other airborne pollutants of course, but it's worse when you smoke. Cleaning the rollers will usually revive a mouse, but take care to avoid scratching or roughening their surfaces as this will help the next accumulation of gunge to stick to them.

Here's a tip if you find that you need to clean the rollers frequently. Apply a very light, even smear of white heatsink compound to the ball. If the coating is thick enough to be sticky it will increase the amount of debris collected. But if it's a very thin coating the silicon grease will prevent dirt sticking to both the ball and the rollers. In addition, the magnesiumoxide filler acts as an incredibly fine polishing abrasive. In normal use it polishes out the minute scratches on the rollers to which the dirt adheres. I also use it to polish the plastic lens on the EverReady swivel torch that gets rattled about in my toolbox.

Because I use a Microsoft Inport mouse card to free a serial port (unless the computer has a built-in PS/2 port), my choice of mouse is limited. I normally avoid the electrical-contact type of position-sensor design, as this is affected by smoke and pollution. It wasn't until the Microsoft own-brand mouse I had been using became very troublesome and I had to look for a replacement that I realised the enclosed sensors at the ends of the rollers were contact types instead of slotted-disc opto-interrupter encoders. Although the contacts had survived, the greater operating torque required was making it difficult to maintain reliable operation. The replacement I eventually found is a Mouse Systems type with slotted-disc opto-position encoding and nylon instead of steel rollers. This type has virtually zero operating torque on the rollers and the nylon, although still vulnerable to abrasion and dirt accumulation, responds better to the 'polish'. Ian Field,

Letchworth, Herts.

ITV Digital's woes

As the UK's digital terrestrial TV service descends into ever deeper crisis, I feel we should ask who's in the driving seat? For the last few years Mr Brown and his chums at the Treasury seem to have been anxious to get their hands on the TV UHF spectrum space and sell it off. To this end pressure has been put on the public to accept that, like it or not, they are soon going to have to go digital. This is in stark contrast to the original plan for a gradual, 405-style run down. But if ITV believes it's the driving force, it needs to ask what it has that Sky hasn't got? If the only answer is itself, its position needs serious consideration. For one thing, unless it is being supported by someone else, no company can continue haemorrhaging as ITV Digital is for long.

The public hasn't taken to the idea of digital TV in the way the government wanted or hoped. Most people simply don't understand what's meant by "digital", associating the term with computers. The majority of people I speak to certainly don't understand that all their children's analogue portables will simply cease to work, but that's another matter.

In comparison Sky has been extremely astute in its approach to digital TV. It obviously has some very clever marketing people who are well in touch with the public. When Sky first appeared in 1988 I was sceptical as to whether people could be persuaded to take up the new technology and also pay for the programmes provided – with, in addition, the programmes put together in packages so that people have to pay for some they don't want! Sky became a success in a relatively short space of time however, by concentrating in particular on sports coverage. But the really clever bit is how Sky has managed the introduction of its digital services. Initial advertising got people interested then, when they went to dealers to see for themselves, a fully-operational system was up and running with a huge selection of programming and stunningly good pictures on the major channels. The EPG was a surprise that captured the imagination.

Having got people interested, and with a huge word-of-mouth publicity machine in operation, Sky then announced that in a very short time it would simply switch off its analogue services, so you'd better move to the digital ones instead. The response that might have been expected from the great British public would be outrage, after spending all that money on analogue equipment. But free digiboxes were made available, and people said fair enough. They took out bigger and better packages - even stumped up another £40 or more to get the equipment installed! Now that's marketing at its cleverest and best. Unless ITV Digital feels that it can compete on a similar footing, it might as well give up now.

What would ITV via satellite involve? For a start, everyone would be able to receive it. Channel 5 too. No more messing about with multiplex allocations and transmitter power levels to try to ensure that you get digital as well as analogue TV via an existing aerial. The only downside I can see is that a certain amount of regionalisation would be lost. But this has already happened – there are no longer many ITV companies that join together and operate as a network only for major drama and entertainment programmes.

The obvious loss would be local news. But the geographical areas now covered by 'local' news are quite large, and a bit larger would hardly be noticed.

The ITV Digital situation is complex, with probably many subtleties and political angles. But from the outset it appeared to me to be doomed. Sky Television had already achieved huge success, there were potential interference problems and those associated with inadequate signal levels. The future of digital TV does seem to lie with satellite and cable.

Geoff R. Darby, Northampton.

CORRECTION

Because of a server computer font fault at the editorial office there were errors in the first letter on page 502 of the June issue. All signal levels should have been specified as dB μ V. Unfortunately the computer deleted the μ s. This happened at the last moment, after page checking. Our apologies. That's technology for you.

Answer to Test Case 466

- page 751 -

Nora's cat was in attendance as this little disaster unfolded, and gave Ray a look of contempt as it stalked off to the kitchen. Cats can judge people, Nora says

Ray was correct in his suspicion that the old masthead distribution amplifier was faulty. It had certainly been there for many, many years, and was maybe older than Ray himself! That it required an 18-24V supply stood witness to its longevity, and this turned out to be the key to the problem. Ray hadn't replaced the power supply, even though the Whizzo amplifier came complete with a new one that provided an output rated at 12V. The output from the old power unit, with the light current load presented by the modern amplifier, had risen to a very generous level – higher in fact than its rated maximum of 24V. This had been too much for the UHF booster amplifier up aloft. It had succumbed, and subsequent inspection showed that some of its internal bits had got very hot.

Nora's little kitchen set now produces almost snowfree pictures while she makes her quiches and sausage rolls, and the big set in the living room gives better pictures than before. All thanks to the lower noise figure of the (second!) new amplifier now clamped to her aerial pole and the new power unit. It's not to be revealed here how the matter of the electrocuted amplifier was resolved, nor where its body lies. Nora doesn't know, Ray does. And maybe, just maybe, the cat does. Look out for the big white van, tabby!

NEXT MONTH IN TELEVISION

Servicing the Philips VR258

John Coombes provides a detailed guide to faultfinding with this Turbo deck VCR.

The Berlin Radio Show

The International Funkausstellung (Berlin Radio Show) is the world's largest consumer electronics exhibition. It's where every new development gets an initial public showing. George Cole reports on this year's main developments, which included the first TV sets to feature DVB Multimedia Home Platform interactive technology, DVD recorders, Bluetooth camcorders and hard-disk recorders.

Motor home installation work

There's lots that can be added to a motor home and money to be made from the installation work. Tom Baker resumes his series: this time, how to fit an electric step.

NiCad pulse-charger circuit

Ian Field presents a simple NiCad battery pulse charger circuit based on the use of a conventional iron-cored transformer. It can be built from scratch at little cost.

TELEVISION INDEX & DIRECTORY 2001 Plus hard-copy index and reprints service

Here's the essential repair information you need! The **Television Index & Directory 2001**, in CD-ROM form, contains the text of over 13,000 high quality fault reports on TVs, VCRs, Camcorders, Monitors, Satellite TV units, Audio equipment and CD players, searchable by make and model, plus the text of 156 Test Cases and 165 major servicing articles, from thirteen years of Television magazine. It also contains a full thirteen year index of Television, a Spares Guide, a directory of Trade and Professional Organisations, an International TV Standards guide, a satellite TV Channel Finder, a TV transmitter list and a compendium of internet resources for service engineers. The software is quick and easy to use, and runs on any PC with Windows 95, 98, ME or NT. The CD-ROM also contains a free index, worth £20, to Electronics World magazine.

Television Index & Directory 2001 CD-ROM, £199

Television Index & Directory 2001 CD-ROM upgrade, £46 (to qualify for this upgrade you need to have purchased a previous version of the Television Index on floppy disk or on CD-ROM)

Television Index only, £36

Television Index only upgrade from previous versions, £16

Hard-copy indexes of Television magazine are available for Volumes 38 (1988) to 50 (2000) at £3.50 per volume.

Reprints of articles from Television back to 1988 are also available, at the flat rate of £3.50 per article – you can order through our web site, or write to the address below.

The above prices all include UK postage and VAT where applicable. Add an extra £1 postage for non-UK EC orders, or £5 for non-EC overseas orders, although Channel Island residents do not need to add any extra postage. Cheques should be made payable to SoftCopy Ltd. Access, Visa or MasterCard Credit Cards are accepted. Allow up to 28 days for delivery (UK).

SoftCopy Limited, 1 Vineries Close, Cheltenham, GL53 ONU, UK

Telephone 01242 241 455 Fax 01242 241 468 e-mail: sales@softcopy.co.uk web site: http://www.softcopy.co.uk

Published on the third Wednesday of each month by **Cumulus Business Media**. Anne Boleyn House, 9-13 Ewell Road, Cheam, Surrey SM3 8BZ. **Cumulus Business Media** is a division of **Highbury Communications PLC Filmsetting** by JJ Typographics Limited, Unit 4, Baron Court, Chandlers Way, Temple Farm Industrial Estate, Southend-on-Sea, Essex SS2 5SE. **Printed** in England by Polestar (Colchester) Ltd., Newcomen Way. Severalls Industrial Park, Colchester, Essex CO4 4TG. **Distributed** by Comag, Tavistock Road, West Drayton, Middlesex UB7 7GE (tel. 01895 444 055). **Sole Agents** for Australia and New Zealand, Gordon and Gotch (Asia) Ltd.; South Africa, Central News Agency Ltd. *Television* is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed by way of Trade at more than the recommended selling price is subject to currency exchange fluctuations and VAT, and that it shall not be lent, resold, hired or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

FRUSTRATED

Looking for ICs TRANSISTORS? A phone call to us could get a result. We offer an extensive range and with a World-wide database at our fingertips, we are able to source even more. We specialise in devices with the following prefix (to name but a few).

2N 2SA 2SB 2SC 2SD 2P 2SJ 2SK 3N 3SK 4N 6N 17 40 AD ADC AN AM AY BA BC BD BDT BDV BDW BDX BF BFR BFS BFT BFW BFX BFY BLY BLX BS BR BRX BRY BS BSS BSV BSW BSX BT BTA BTB BRW BU BUK BUT BUV BUW BUX BUY BUZ CA CD DX CXA DAC DG DM DS DTA DTC GL GM HA HCF HD HEF ICL ICM IRF J KA KIA L LA LB LC LD LF LM M M5M MA MAB MAX MB MC MDA J MJE MJF MM MN MPS MPSA MPSH MPSU MRF NJM NE OM OP PA PAL PIC PN RC 5 SAA SAB SAD SAJ SAS SDA SG SI SL SN SO STA STK STR STRD STRM STRS SV1 T TA TAA TAG TBA TC TCA TDA TDB TEA TIC TIP TIPL TEA TL TLC TMP TMS TPU U UA UAA UC UDN ULN UM UPA UPC UPD VN X XR Z ZN ZTX + many others ZTX + many others

We can also offer equivalents (at customers' risk). We also stock a full range of other electronic components. Mail, phone, Fax, Credit Card orders & callers welcome.





ww.telepart.co.uk catalogue out NOW cameras, monitors, switches quads, multiplexers, the lot

Video Surveillance

	• C-Mos B/W Camera
21	15mm x 15mm£29
	• C-Mos Colour Camera
-	15mm x 15mm£65
-	• PCB B/W Camera 32mm x 32mm£24
	PCB Colour Camera w/Audio
-	32mm x 32mm£65
_ 🦿	• 23cm (1.3Ghz) Video/Audio
A COLORADO	Transmitter£35
	• 13cm (2.4Ghz) Video/Audio
	Transmitter£35
	• 1.2 Watt 2.4Ghz Video/Audio
	Transmitter£120
	• 4" TFT Boxed Colour Monitor
A STATE	w/Audio£110
	• Video to VGA Converter£65
	• VGA to Video Converter£90
	• External USB Video Capture Box£55
	All prices exclude VAT
ا /۸//۸//۸	Many more products on our website:
vv vv vv .	
	Tel: 01753 522 902

Setbacks



Televés UK Ltd Tel. 01633 875821 Fax 01633 866311 televes.uk@televes.com www.televes.com









website: www.centralwd.co.uk

TELEVISION October 2001

FAX :020 8884 1314

CC Trade Ltd

Lady Smith House, Easy Road, Leeds, West Yorkshire LS9 8QS

SPECIAL OFFERS

5,000 customer returned Morphy Richards and Goblin Vacuums £6.00 10,000 Toasters, 4 slice cool wall, customer returns £1.75 Also a full range of other Morphy Richards products, too many to mention. We also do a full range of A grade Morphy Richards Products at guaranteed unbeatable prices. Steam irons from £5. Vacuums from £12, just a few examples of our fantastic deals. We also carry a full range of TV, Video and Hi-fi, etc.

For all enquiries please telephone 0113 2480512 or fax 01132 496990

A guaranteed deal you will not beat!



TUBES

WIDESCREEN at a price worth fitting

28"	Panasonic	W66EHK
28"	LG	W66QBD
28"	Videocolour	W66EHU
28"	Videocolour	W66EJU
28"	Videocolour	W66EGV
32"	Videocolour	W76EDX
	Ring Irene	for prices

EXPRESS TV The Mill, Mill Lane, Rugeley, Staffs WS15 2JW Tel: 01889 577600 Fax: 01889 575600

NEWTECH.

Unbeatable opening offers!! All Top Brand TV'S DVD'S VCR'S Hi-fi'S

Sharp Viewcam, without accessories working	£75.00
Camcorders, without accessories working (Sony, Panase	onic, JVC, Hitachi)£55.00
New 'B' Grade 32" Widescreen, with r/control, f/text, Nica	m stereo£150.000
New 'B' Grade 33" TV, with r/control, f/text, Nicam stereo.	£150.000
New 'B' Grade 28" Widescreen, with r/control, f/text, Nica	m stereo£100.000
New 'B' Grade 28" TV, with r/control, f/text, Nicam stereo.	£75.000
New 'B' Grade 21", f/text£50.00	Top quality items exclusive
New 'B' Grade 21", with r/control£40.00	
New 'B' Grade, portable TVs£30.00	IO NEWTESH

★ Special opening offer ★ selected top brand 28" Widescreen TV's£150.00
 Sony, Panasonic, Toshiba, Philips, Hitachi and JVC
 VCR's LP.....£30.00
 Video+.....£35.00
 Nicam.....£40.00
 Untested DVD players from.....£30.00

Untested Top Brand DVD's (Sony, Panasonic, Toshiba and Philips)......£40.00

Tel: 0121 665-6336

Unit 10, Fazeley Street Industrial Estate, Fazeley Street, Digbeth, Birmingham Open: Monday-Saturday 9.00am - 6.00pm

All major credit cards accepted



TELEVISION October 2001

Service Link

No other consumer magazine in the country can reach so effectively those readers who are wholly engaged in the television and affiliated electronics industries. They have a need to know of your products and services.

PHONE 020-8722 6028

FAX 020-8770 2016

The prepaid rate for semi-display setting is £15.00 per single column centimetre (minimum 4 cm). Classified advertisements £2.00 per word (minimum 20 words), box number £22.00 extra. All prices plus 171/2% VAT. All cheques, postal orders etc., to be made payable to Cumulus Business Media, Ann Boleyn House, 9-13 Ewell Road, Cheam, Surrey SM3 8BZ

SERVICE DATA

SERVICE SHEE	IS AND MANUALS	THE JOULE A400 RADI	O DECODING SYSTEM
For most makes and models of TV - Video - SAT - CD - Audio Complete Service S/Man Sheet CTV - 10.00 4.00 VCR - 15.00 6.00 Service sheets include circuits and essential electrical/VCR mechanical set-up information. All other items - price on application. Add P/P of 1.50 to order total. No VAT. Payment by cheque or P.O. only please. D-TEC PO BOX 1171, FERNDOWN, DORSET BH22 9YG Tel: 01202 870656		 The highly acclaimed A-400 car radio decoding system has just got even better – and so has the price! Latest version 9.4 software now covers an even broader range of radios including:- Philips, Ford, Grundig, Blaupunkt, Kenwood, Becker, Clarion, Pioneer, Panasonic, J. V.C. Volvo and Hitachi. There is also a new Misc. section covering a variety of 'odd ball' radios. The latest addition to our decoding system is the X3000 – a stand alone device for decoding the new Ford Traffic 3000 and 4000 models – even if they are displaying 'Lock 13' Contact us now for further information and prices on 01325 310278 or visit our web site at www.elecsys.com where you can download a brochure and demo software or purchase a decoding system on-line. Joule Electronics, Hilton Road, Aycliffe Industrial Park, Newton Aycliffe, Co. Durham DL5 6EN 	
Fryerns	FAX BACK		
Tree FFS Circuit	OPEN SERVICE	NEED HELP NOW?	WWW.PCPARTS4U.CO.UK
	AVAILABLE	Then ring the	32MB DIMM £3!!
V's, VCR's SATELLITE AUDIO & HI-FI	TEL/FAX A.T.V. on	HELPLINE ★ Genuine help available to all repairers	DVD-ROMs £25!!
Most Models Covered rices are from £4.75 + £2.75 P/P	0114 285 4254	of T.V V.C.R SAT - AUDIO (Inc Valves)	CD WRITERS CASH
1 item - total £7.50 inc 2 items - total £12.25 inc	SAT/CTV Circuits £5.00 VCR Circuits £7.00	- MICROWAVE - MONITOR AND MOST ELECTRONIC EQUIP	CO WAITERS ESSI
3 items – total £16.50 inc etc e: some items priced individually Payment by credit and PO	CTV Manuals £10.50	Over 30 years experience and vast data base	AMD K6-2 500 £20!!
or cheque Tel/Fax: 01206 211570	VCR Manuals £14.50 (P/P add £2.50 to each order)	Calls cost 60p per minute	CHEAP! CHEAP!
il: colin@fryems.fsbusiness.co.uk 2 The Lodge	419 LANGSETT ROAD,	Hours of Business Mon to Fri 9.00 am-12.30 pm : 2.15 pm-5.30 pm	OUFOK OUT OUD WEDDITE FOD
Easthorpe Green Marks Tey, Colchester	SHEFFIELD S6 2LL	Sat Morn 9 am-12 noon ELECTRON G.T. 9 CHAPEL ST. DONISTHORPE	MORE LOW PRICES
COOTRA	VISA	SWADLINCDTE, DERBYSHIRE DE12 7PS	
WANTED	REPAIRS	SERV	ICES
EST CASH	accént	TIMELAPSE VI	DEO SUPPLIES
For ALL valves		Video Heads and	ranair narts for
especially KT88,			a magandana
PX4 and other	CAMCORDER REPAIRS		eu recuraers
audio types	Collection and delivery	Hitachi VTL 1000	heads only £34.50

anywhere in the UK.

All makes, fast service.

Phone free for details.

Fax: 01905 796385

(0800) 281009

Tel: 01403 784961 Minimum UK order £50+VAT+ Freight

Service Informate TV's

Prices

3 it note: so Pay

e-mail: c

BE PR

> es P

Billington Export Ltd Sussex RH14 9EZ Fax 01403 783519 Email: sales@bel-tubes.co.uk Visitors by appointment

LASSIFIED TEL:020 8722 602

MISCELLANEOUS

Toshiba K V6200 heads only £27.00 Sony 2N4P-SQ heads only £49.00 JVC SRS970 heads only £49.00

Tel: 01642 895488 Fax: 01642 351634

FOR SALE	
1043 Leeds Road BRADFORD BD3 7DB Tel: 01274 665670/660196 ELECTRICS LIMITED Fax: 01274 665246	PI ex cle
E-Mail: tradesales@instorelec.fsnet.co.uk	

EVERYTHING FULLY GUARANTE	ED
COMBI TVCB from	
14" PORTABLES SCART	£59
WIDESCREEN TV from	.£185
ON DIGITAL WIDESCREEN	.£375
SVHS VCR	. £195
MICROWAVE DVENS	£34
DVD MULTI REGION	E120
Reading + Digital + CDIR + Continues + First +	ALC: NOT

CREDIT CARDS WELCOME • 48 HR DELIVER



application form write, phone or fax:

HARVEY ELECTRONICS 43 Loop Road, Beachley, Chepstow, Mons, NP16 7HE Tel: 01291 623086 Fax: 01291 628786

Visa: Mastercard accepted

LINEAGE

RIVATE RETAILER has excellent part change colour televisions and videos to ear. Tel: 01494 814317.

RECRUITMENT

Family Business Requires Bench/ **Field Engineer**

Experienced in repairs to TV/Video/Audio Must be physically fit will suit

25-40 year old. Salary negotiable dependina on experience.

Contact Mr. B. Farbon **Brooke Domestic Services** Unit 4. Woodward House. Cambridge Street, Bietchley, Milton Keynes MK2 2TH Tel: 01908 640221

For further details on advertising please contact Pat Bunce

020 8722 6028

Experienced Bench and Field Technicians. **Domestic Appliance** Engineers and **Technical Installers** required by SERVICESPEED (SLOUGH) TEL: 01753 524848

Top Class Fully Qualified, Analogue, Digital Audio, Video Engineer required for expanding

Sony Regional Authorised **Service Centre**

Are you seeking the rewards you deserve?

Then call Simon Thomas. 0121 707 5700 or Email: BSS.ASC@TALK21.COM

PSL

Professional AV rental company

Require

Service Engineers

An exciting opportunity to repair Professional audio and video equipment. Excellent package for the right candidate.

> Please write enclosing your career details To Mike Noake PSL. Unit 2, 41 Humber Road. London NW2 6EN Or e-mail: workshop psl@aol.com www.presservgroup.com

ADVERTISERS' INDEX

	Aerial Techniques	739
	Alban Electronics	706
	Bitz Technology	761
	Campion Wholesale	766
	Canvey Colour	724
	CC Trade TV	765
	Central TV	764
	Charles Hyde	IBC
	Coastal	
	Colour Trade	763
	Cricklewood	
ŀ	East London Comp	725
	Economic Devices	761
	Electronic World TV	764
	Eptsoft	OBC
	Euras	719
	Express TV	765
Í	Grandata	710-713

J & N Factors	745
JPG Electronics	741
J. W. Hardy	.725
LA Electronics	763
MCES	.741
New Tech	766
Satellite and Digital	
Services	724
Seme	719
Sendz	757
Stewart of Reading	72 <mark>5</mark>
Teletest	719
Televés	.761
TW Electronics	. IFC
Universal	718
Vision Tech	765
Web Service754, 755.	, 756
Wiltsgrove	762

LASSIFIED TEL:020 8722 6028

Charles Hyde & Son

is the Distributor in the UK and Ireland for (

remote controls

(manufactured by Ruwido GMBH - the best in Europe).

CHOICE I

The Original Manufacturers Remote

ā.

I for I technology

CHOICE 2

The COM I: I copy remote.

NB The same the same as always, only the colour of the pack has charged.

I for I technology

CHOICE 3

The COM Universal copy remote

multi-brand technology

Great choice from one source!

Charles Hyde & Son Ltd, Prospect House, Barmby Road, Pocklington, York, YO42 2DP.







www.charleshyde.co.uk

'Electronics and Computing '95, '98, NT or 2000 **Principles V7**

Looking for a change of direction and need a quick refresher or skills update, then this is the software for you



Visit www.eptsoft.com or telephone for full details, including a description by **Robert Penfold. Electronics:-**

Atomic Structures, DC Current flow, Basic Electronics, Simple DC Circuits, Types of Switching, Variable Voltages, Ohm's Law, DC Volt∉ge, DC Current, Series/Parallel Resistors, AC Measurements, AC Voltag∋ and Current, AC Theory, RCL Series/Parallel Circuits, Capacitance, Capacitors, Inductance, Inductors, Impedance, Communication System, Signals, Attenuators, Passive/Active Filters, Tuned Circuits, Coupling and Selectivity, Oscillators, Circuit Theorems, Diode Theory, Diode

Applications, Transistor Theory, Bipolar Transistor, Torona Configurations, Transistor Circuits, Field Effect Trans-sors, Opera Amplifier Theory and Applications, Sum and Difference Amplifiers. **Electrical:-**

and AC Power, SCR, Power Supplies, Voltage Regulators, gnetism, Motors/Generators, Transformers, Three Phase Systems. **Digital Techniques:-**

Logic Gates, Flip Flops, Combinational Logic, Counters, Counting, Shift Registers, Logic Interfacing, Timers, Boolean Algebra and DeMorgan s

Microprocessors and PIC Microcontrollers:-

Hence Computer, Busses, A.L.U, Clock and Reset, Instructions and Hence Cells, ROM and RAM, Memory Addressing, Market Cells, ROM and RAM, Memory Addressing, Market Cells, ROM and RAM, Memory Addressing, Hence Cells, Hence

Personal user £99 95 +VAT Education* £299.95 + VAT (*Includes unlimited multi-user site licence.)

Measurement and Component Testing:-

Analogue multi-meter, Measurement, Component Testing. Mathematics:-

Simple Numbers, Number Types, Roots, Triangle Ratic's, Triangle Angles, Area, Surface Area and Symmetry, Volume, Percentages Ratio's, Fractions, Vectors, Circle Angles, Laws, Algebra Rule Powers, Simplifying, Equations, Graphing, Slope and Trans Angles, Complex Numbers, Statistics, Lottery Number P Science

Computing:-

Hardware Devices, Data Structures, Data Files, Binan Number, Bina Arithmetic.

Toolbox:-

DC Calculations, AC Calculations, Numbers, Applicatio

eptsoft limited. Pump House, Lockram Lane, Witham, Essex. UK. CM8 2BJ. Tel: +44 (0)1376 514008. Fax: +44 (0)870 0509660. Email: info@eptsoft.com. Switch, Delta, Visa and MasterCard accepted. No additional postage or airmail charges.