Tips, guides and reports for people repairing televisions and electronic equipment

TELEVISION PLQ ! JPE ! ! !

AND HOME

'AIR

NOVEMBER 2003 £3.20

Report from the IFA Berlin Show









TV interference from TETRA
A flexible CCTV security system

Satellite, Audio, Monitor, TV, VCR and DVD faults



With most of Europe's leading TV manufacturers including Alba, Beko, Daewoo, Philips, Samsung and Toshiba, to name but a few, choosing Eldor as their supplier of Line Output Transformers and Classic, as Eldor's sole European distributor, finding the transformer you need is as easy as 1, 2, 3...

- 1... Locate the label on the original transformer.
- 2... Make a note of the Eldor part number shown on the label.
- 3... Locate this number on your Eldor look-up card and order the Classic part number listed from your usual Classic distributor.

If you don't yet have a copy of the Eldor look-up card phone your Classic distributor with the Eldor part number and tell them you want an original Eldor part.

For more information on the entire Classic range or details of a distributor near you, call 01635 278678, visit us on the web; www.classic-electronics.co.uk or email us at sales@classic-electronics.co.uk





CONTENTS

November 2003

Vol. 54, No. 01

3 Comment

Companies that wax and wane.

4 Teletopics

The European HDTV system. Flat TV update. Business news. Flat CRTs from LG.Philips. Video recording devices. DAB update. Sharp's 'wireless TV'

6 A flexible CCTV system Simple inexpensive off-the-shelf CCTV kits are readily available but lack individual expansion capabilities and flexibility. Ian Rees has devised a system that should fulfil the needs of small-tomedium sized installations, with some added innovations found only in dedicated PC or professional

12 At the Internationale **Funkausstellung**



The 2003 IFA exhibition featured the latest developments in digital TV, flat-screen technology, DVD players and recorders, camcorders with various storage systems and domestic networking. George Cole was there to report for us.

16 The TETRA problem

TETRA is an international standard for digital mobile communications. The police and other emergency services in the UK are gradually adopting TETRA systems. They are high-powered, and can cause UHF TV interference problems. Bill Wright describes the situation and the remedies that can be used.

25 Servicing the Sharp DA100 (50Hz) and DA50W chassis

Part 3 of this series, by Alex Towers, deals with the dynamic focus, EW correction and field output stage circuitry and outlines line and field timebase fault-finding procedures.

32 Letters

DTT redundant? Fire hazard. Reliability. Polarity protection. Vintage radio repairs.

33 Help wanted

34 DX and Satellite Reception

Terrestrial DX and satellite TV reception reports. Broadcasting news. LNB-dish matching. Interference from PLT. Roger Bunney reports.

38 Audio faults

Hints and tips on repairing professional and consumer equipment.

40 Monitors

Guidance on repairing monitors and related equipment

44 VCR clinic

45 Test Case 491

46 TV fault finding

50 Web service

Useful websites for TV professionals, technicians and enthusiasts.

54 Satellite notebook

High-definition TV tests. Digital channel update. BBC1 regional oddities. Update at 34.5°W. Unusual test cards. Digibox fault reports.



57 Next month in Television

58 What a life!

TV and VCR faults. Band III converters. Warm sets. Donald Bullock's servicing commentary.

Editor

John A. Reddihough

Deputy Editor

Tessa Winford

Advertisement Sales

Reuben Gurunlian 01322 611 292 Fax 01322 616 376

Publishing Director Tony Greville

Note that we are unable to answer technical queries over the telephone and cannot provide information on spares other than that given in our Spares Guide.

Disclaimer

We work hard to ensure that the information presented in Television is accurate. However, Television's publisher - Highbury Business Communications - will not take responsibility for any injury or loss of earnings that may result from applying information presented in the magazine. It is your responsibility to familiarise yourself with the laws relating to dealing with your customers and suppliers, and with safety practices relating to working with electrical/electranic circuitry particularly as regards electric shock, fire hazards and explosions.

Next issue, dated December, on sale November 19

WILTSGROVE LTD

35/38 River Street, Digbeth, Birmingham B5 5SB

TEL: 0121 772 2733 - FAX: 0121 766 6100

ONLINE CATALOGUE!

http://www.wiltsgrove.co.uk

Make/Model, Product Category, Manufacturers part number, Key Word search or Our Order Code e-mail: sales@wiltsgrove.co.uk http://www.wiitsgrove.co.uk

Opening Times: 9:00am - 6:00pm (Monday to Saturday)

VALID UNTIL THE END OF NOVEMBER 2003

14" BLACK & WHITE MONITOR

SPECIFICATION:

Proceedings.	E HE I SHE III JULY / BIN
Power Consumption	35 Watts
Decid States	B.E. Z.Phia Democate Village, Sain, Rep.
Input Impedance	BNC Connector, 750hm / High Switchable
C	The second
Resolution	1000 TV Lines
Charles .	Demonic IIIs No.
	Vertical 10% Max
CET	16
Operating Temperature	-10°C to +60°C
Design (Northeat	200 4 346 4 395
Weight	10 20Kgs



£72.50

Order code: AV-1051

4 WAY CAMERA SWITCHER

SPECIFICATION:

Prod Wilde	
	ACTION HILLOWS IN PROPERTY 2 9
Video Inputs	1 0 Vp-p / 75 ohms - 4 inputs
Value Out us	CLEVES TEACHER SHOWING THE
Video Gain	From Attenuation to amplifier, 0.8 to 1.4 Vpp
V 1 3 8 m l	Contract to the contract to th
Max Video Input	2 0 Vpp
C Inp	Retail Top-GOS
Switch Internal	Approx 1 to 15 sec
nr '	Person I fell (recent
Power Consumption	3W Max
HAR Owners	160
Position & Power Lamp	Long Life LED
Andrew Temperature	THE REPORT OF THE PERSON NAMED IN COLUMN 1
Construction	Steel, with gray enamel finish
	250440
Weight	Approx 0.82Kgs

£39.95

Order code: AV-1071

4 CH COLOUR DUPLEX MULTIPLEXER

SPECIFICATION:

VIDEU SIGNAL	Digital Married Vision Property Vision Property Vision Colombia	Timber 11 Inches
ELECTRICAL	Power Supply Power Consumption	100~240V, 50/ Approx, 10W
VIDEO FEATURES	Crartes Format Assumed a Desir Engineer States	TAXABLE PARTY
CONNECTOR	Video Input Video Output Monitor Output VCR Input VCR Output	4 BNCs 4 BNCs 2 BNCs 1 BNC & 1Y/C





1 BNC & 1Y/C 25 Pin D-Sub DC Jack Alarm In/Out Power Jack MECHNICAL ALARM FEATURE

Alarm Inputs
Alarm Outputs Multiple Alarm Display Alarm Duration Video Loss Indicate

4 Inputs (NO/NC selectable) 1 Relay Output (3A max) Sequence 1 ~ 60 sec Alarm with Blue Screen

NVIRONMENTAL

FEATURES:

- High Quality Digital Processing • 4 Channel Camera Input
- Duplex Operation Recording &
- Freeze Ficture onplayback mode
- or live made
- Fully compatible with Time Lapse VCR / S-VHS & other VCR
- Digital Motion Detect
- Display Mode (1h / 4CH)

£229.00

Order code: AV-6022

1/4" COLOUR WEATHER-PROOF BULLET CAMERA

SPECIFICATION:		-
PULLVO	1 Sections to the Property Co.	and the same of
Picture Elements	NTSC/EIA 510 (H) x 492 (V) PAL/CCIR 500 (H) x 582 (V)	
De transfer	- Service	
Honzontal Resolution	330 TV Lines	
and March	Test of the second	
Auto White Balance	2500°K ~ 9500°K	3 V
ACC	701	
Gamma Charactenstics	0.45	
1 n l lutt	THE RESIDENCE OF SHIP	and .
Power Source	DC 12V ± 10%	
6 Jr (1	* Sport No.	
S/N Ratio	More than 48dB	
Vesigliand.	Company to have 100 kins	CCA
Minimum Illumination	0.5 LUX / 75 ohms	£64
Charles Townson or 1	THE PERSON NAMED IN COLUMN TWO IS NOT THE PERSON NAMED IN COLUMN TWO IS NAMED IN COLUMN TW	



1.95

Order code: AV-1420

14" HIGH RES COLOUR MONITOR

SPECIFICATION:

Planer Table	16 Depre
Scanning Frequency	NTSC H 15 734 KHz V 60 Hz PAL H 15 625 KHz V 50Hz
Syntheresister	Desired printed the second street speed
Video Signal Input	1 0Vp-p / 75 Ohms
FOR Impediation	TLOURS I Right Switchurfer
Honzontal Resolution	NTSC 450 TV Lines PAL 500 TV Lines
See	Bullion parlation agreement
Sound Input	400mV 1k ohm
Speaker Impedance	8 Ohms
Plant Server	ACCUSED THE REAL PROPERTY.
	PAL AC 220-230V / 50 Hz
C I	204
Dimensions (WxHxD)mm	356 x 335 375
The grade of the g	Apro Milita



£129.95

Order code: AV-1056

BLACK & WHITE BULLET CAMERA

SPECIFICATION:

House Fire Of Course	NY WWW. Torrison Dogs.
Scanning System	2 1 Interlace (NTSC Standard) / 2 1 Interlace (PAL Standard)
	525 Lines/60 Fields/30 Frames / 625 Lines/50 Fields/25 Frames
School Security	PETROPORE RESIDENCE TO THE CONTROL OF T
Effective Pix Is	768(H) x 494(V) / NTSC 752(H) x 582(V) PAL
PROFESSOR STATE	A. Emmilia A. Addison (V)
Video Output	1.0Vp-p NTSC Comp / 1.0Vp-p PAL Comp
Contract of the last of the la	Name and Address of the Owner, where the Party of the Par
Sync System	INT Only
Paradolis .	There then bed Victoria
Gamma	r=0 45
API TIME	THE PODGET
Power Source	DC 12V 200mA 4.5W
Par .	ATTO BUT OF
Minimum Illumination	0 Lux
0	STATE OF THE PARTY
Lens Type	Regular Lens



FEATURES:

- Built-in 6 LEDs to observe the
- security area under dark of 0 Lux

 Can be used under water of 30m
- Extremely low power

£39.95

Order code: AV-1540

DVR STAND ALONE 4 CHANNEL

SPECIFICATION:

Desiration Made:	Prost Farms Critical Control of C
Resolution	720 x 480
D No.	HOUSE STOCKBOOK AND
Recording Speed	720 x 240 1-10 Frames/sec (adjustable) 360 x 240 1-15 Frames/sec (adjustable)
Restriction of the Alexander	1 -
Compression	MJPEG
Sim Sim Mail	140
Camera Input	4 CH BNC (NTSC/PAL)
Value 1 of the last	Company Value (INC) + 2
Playback Function	Playback - forward reverse Fast Forward F - I Reverse Toward one frame Zoom in
HOD	MODE STATE OF THE
Search Mode	Date, Time, Camera
Comment	1044
Power Supply	AC100V ~ 240V, 50/60Hz DC 12V/4A
Plant Constability	
Dimension (WxDxH)mm	313 x 255 x 44
Greek .	714.7

FEATURES:

- Up to 30 frames per second
- video display

 Simultaneously recording live view display
- Automatically detects NTSC/PAL
 Tapeless recording replaces conventional time-lapse recorder
- Four set input and one set output alarm connection Automatically recording, after being triggered
 • Highly stable non-PC based
- proprietary system
- Automatically returns the onginal operation when power recovery from failure

£429.00

Order code: AV-6070

BOTH ITEMS REQUIRED FOR COMPLETE SET

BRACKET for CAMERA HOUSING

CAMERA HOUSING - OUTDOOR





Order code: AV-1365 £29.75

TRADE ONLY

* PRICES SUBJECT TO AVAILABILITY, VAT & CARRIAGE. * PRICES MAYBE CHANGED WITHOUT PRIOR NOTICE.

Freefax Orderline: 0500 55 05 05

Companies that wax and wane

When I was young large companies seemed to me to be pretty permanent fixtures - despite the depression and war years. After all, they owned giant mills, steel plants, Atlantic liners, coal mines or what have you: not the sorts of things one might expect to come into and out of use over a relatively short period of time. Yet the mills have closed, UK steelmaking has declined dramatically, the liners have long since given way to aircraft, and the pits are no longer active. The fields of electrical and electronic manufacturing are similarly affected by change. Who, back in the Seventies, would have thought that the mighty Thom Electrical Industries would fade away? Once Sir Jules departed it seemed to do just that. Interestingly, Philips has proved its survival capability to date, though the going has been tough at times. More recently we have had the extraordinary business of the internet company bubble. Some of these companies shot up to a huge size on paper only to shrivel away within months

Boards, when they are not busy fiddling the books, can have a very difficult time. Companies have to evolve to maintain a role in the everchanging economy. Sometimes they succeed brilliantly, sometimes they make disastrous mistakes - Marconi springs to mind as an example of the latter.

Recent reports suggest that several well-known companies may be faltering. Nokia, the world's largest mobile phone maker, has announced a restructuring. The company has an unusual background - it started off in the forestry industry, then evolved into electronics. Forestry has long since gone, and since 1992, when the mobile phone boom started, the company has concentrated on this area. But mobile phones have become cheap, commodity items, and sales have been flagging. The industry is now placing increased emphasis on data services. So Nokia is to be reorganised, with three divisions: mobile phones and networks, multimedia and 'enterprise solutions'. The latter will target business customers. Multimedia will concentrate on imaging, gaming and entertainment services, including camera-phones - the company is about to launch the N-gage portable gaming unit, which has wireless connectivity (bluetooth) built in so that interactive games can be played. Nokia's mobile phone-PC combination comes under enterprise solutions. This may provide some sort of indication as to the way in which things are going.

Motorola's problems appear to be more serious - its chairman and chief executive Chris Galvin has just resigned. So have other major company officers. Motorola was founded in 1928 by Chris Galvin's grandfather Paul, and was for many years famed for its car radios. In the early days of ICs it became a major manufacturer of chips for consumer electronics. It is still heavily involved in the semiconductor field, but this part of the business has been lossmaking for some time. More recently it has concentrated on mobile phones, but has found

it hard to compete with Nokia - its market share has dropped from 26 to under 15 per cent. Other, more successful divisions include wireless services and products. There have been delays in introducing new mobile phones and phone-cameras, some with colour screens, including the V810 clam-shell phone-camera that's intended as a leading new product, marking a shift of emphasis from engineering to design. There have been suggestions that the company might be broken up. It has cut 56,000 jobs, about a third of the workforce, in recent years.

Eastman Kodak, for long synonymous with photographic film, aims to reinvent itself as a giant in the digital imaging field - after making a rather belated start. The example of Polaroid, inventor of instant prints, is not helpful: it became bankrupt in 2001. Kodak will have its work cut out to succeed in fields that are dominated by the likes of Canon, Sony, Olympia, Nikon, Xerox, Hewlett-Packard and Epsom. But it has launched several initiatives. including digital cameras, the Ofoto internet site, and a joint flat-panel display venture with Sanyo.

Intel has already had one narrow escape when, in the eighties, it moved from D-RAM to microprocessor chip manufacture, a field it has come to dominate. Since the early nineties it has grown in size by a factor of ten. But the semiconductor industry has been through huge upheavals during the last decade and Intel's chief

Cover: Our cover photographs this month show some of the highlights of IFA 2003 (see page 12), including Pansonic's DMR-E100H combined DVD-RAM recorder with 80GB hard disk and an SD Memory Card slot, one of Sony's DVD-RW/R camcorders and a Philips LCD TV Model 42PF9965

executive, Craig Barrett, feels that the coming decade will bring "major, major dislocation", with Asia as the centre of this convulsion. Intel is responding by moving much of its R&D work overseas. As Craig Barrett has put it, "essentially all PC and handheld design work is now done in Taipei (Taiwan), so I put my engineers where the action is"

Is nothing sacred? How about Microsoft and IBM? The latter has had its problems in recent times, while Microsoft is facing increased competition from the likes of Linux. Its proneness to email viruses has not done it any favours. But we shall see. One thing is certain: free markets are fearsome taskmasters

COPYRIGHT

C Highbury Business Communications, 2003. All rights reserved. No part of this publication may be reproduced, stored or transmitted in any form or by any means without the written permission of the publishers.

All reasonable precautions are taken by Television to ensure that the advice and data published are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it.

CORRESPONDENCE

All correspondence regarding advertisements should be addressed to the Advertisement Manager, Television, Highbury Business Communications, Nexus House, Azalea Drive, Swanley, Kent, BR8 8HU. Editorial correspondence should be addressed to Television, Editorial Department, Highbury Business Communications, Nexus House, Azalea Drive, Swanley, Kent, BR8 8HU.

INDEXES AND BINDERS

Indexes for Vols. 38 to 52 are available at £3.50 each from SoftCopy Ltd., who can also supply an fifteen-year consolidated index on computer disc. For further details see page 697.

Binders that hold twelve issues of Television are available for £6.50 each from Modern Bookbinders, Pringle Street, Blackburn, BB1 1SA. Telephone: 01254 59 371 Make cheques payable to "Television Binders".

Newstrade Enquires Distributed by COMAG

Telephone: 01895 444055

ISSN 0032-647X

SUBSCRIPTIONS

Highbury Subscription Services, Link House, 8 Bartholomew's Walk, Ely, Cambridge CB7 4ZD. Telephone 01353 654 431 Fax 01353 654 400 Email hbc.subs@highbury-wyvern.co.uk Please notify change of address.

Subscription rates:

UK 1 year £33.80, 2 years £54.00, 3 years £71.00. Republic of Ireland 1 year £38.95, 2 years £62.00, 3 years £81.85. Mainland Europe 1 year £49.00, 2 years £78.40, 3 years £102.90. Rest of World 1 year £63.50, 2 years £101.00, 3 years £133.00. Cheques should be made payable to Television.

BACK NUMBERS

If available issues are £4.00 each.



TELETOPICS

The European HDTV system

An official statement on 13 September announced that Europe's first high-definition service, Euro 1080, will start broadcasting on 1 January 2004. Transmission will be via satellite, to households and theatres. Programming will include the European and the World Soccer Championships and the Olympic Summer or Winter Games. The first programme, scheduled to start at 11 a.m., will be the New Year's Concert from Vienna.

Some 2.5m HDTV sets are expected to have been sold in the US during 2003. Japan is ever farther ahead, with more than 6m households being able to watch HD television. Many broadcasters throughout the world are currently transmitting HDTV, including NBC, Channel 7 Australia, NHK Japan, Korean BS, China CTV and TV Globo Brazil. Europe lags behind in sticking with standard-definition TV,

despite having developed the HD-MAC system back in the Eighties.

Euro 1080 will launch with two channels, the Main Channel and the Event Channel. The former will broadcast free-toair via satellite to households and small venues (sports bars, hotel chains, airports etc.) a four-hour rolling programme consisting of live and delayed live content, the footprint extending from Norway to Portugal and Greece, covering more than thirty countries. The latter will distribute event programmes to 'Event Cinemas', i.e. theatres equipped with an electronic projection system and a 5.1 surround sound system. Content will range from big events to specific regional programming. Euro 1080 will co-produce HD content with public broadcasters, production houses and record companies, and also exchange

LG.Philips has introduced two new TV picture tubes, the Cybertube+ SuperSlim range. Depth has been reduced significantly to make them competitive with flat-panel displays.

The 32in. tube is the world's first real-flat widescreen, slim-line CRT, measuring just 35cm from front to back (see above). This has been achieved by increasing the deflection angle to 125°. The photo shows the significantly shallower

profile of the glass envelope over much of its rear surface area. The tube will enable manufacturers to produce sets with the cost and performance advantages of CRT technology while being little deeper than a plasma model. Only minor chassis modifications are required to cater for the new tube.

The other tube in the range is a 21in., 110° real-flat 4:3 screen type that uses a hybrid coil. The 38cm depth knocks 13cm off that of a conventional 21in. tube

The company has also demonstrated a 36in. real-flat widescreen high-definition picture tube that uses its unique HF rectangular deflection yoke and an improved high-resolution gun.

programmes with HDTV services worldwide. It also plans to acquire rights from owners of major events.

Anyone with a 60cm dish pointed at the satellite will be able to receive the Euro 1080 signal. Viewers will also have to purchase an HDTV set-top box and display in order to see the pictures at their best. There have so far been no announcements of prices or manufacturers of such equipment. Connections will involve linking the new STB to the dish with the existing satellite receiver linked to an IF loop output. The HDTV STB will provide component, composite and S video outputs.

It will also be possible to distribute the HDTV signals via a coaxial cable network, with the cable service operator being able to include the digital HDTV stream with any existing data stream. Cable operators who have upgraded their networks to carry DVB TV can multiplex the HDTV transport stream with other channels.

The HDTV multiplexed signal occupies a 7MHz channel bandwidth and uses QAM 256 modulation with a bit rate of 40Mbits/sec. The display parameters are 1.920 pixels × 1,080 lines, with 50Hz interlaced frames.

Central play-out and post-production for the service will be located at Hove, Belgium. Euro 1080 is using Panasonic D5 HD and DVCPRO-HD as tape formats for production, post-production and content recording. Other equipment such as cameras, vision mixers and video servers is being supplied by Thomson. Sound will be available in Dolby Digital form.

Test transmissions are already taking place and can be viewed, as Hugh Cocks reports in Satellite Notebook (see page 54).

Flat TV update

Sony has announced that it will boost its flatpanel TV range substantially and is aiming for a 30 per cent share of the market. The company is reorganising its Japanese manufacturing facilities and plans to increase its flat-panel range from seven models last year to 27 in time for the Christmas sales season. Sony has held talks with Samsung about a joint venture to produce LCD panels — at present Sony relies on Hitachi and LG.Philips for its supplies. Sony does not have its own LCD production technology.

Samsung forecasts that global sales of flatscreen PC monitors will exceed those of CRT models for the first time next year, while sales of flat-screen TV sets could outnumber those of CRT sets within five years. "Explosive" growth is expected next year as prices fall: the price of a 32in. Samsung LCD set is forecast to fall from about \$4,000 by the end of this year to something like \$3,000 next year as increased production leads to economies of scale. At present the price of an LCD TV set is on average about five times that of a CRT set.

Sharp, the world's leading LCD TV manufacturer with a market share of about 60 per cent, forecasts that demand will double from 1.4m sets last year to 3m this year and 8m in 2005, when the company is to cease producing CRT sets. It forecasts that in 2007 fifty per cent of the TV market will consist of flat-panel sets, with 37 per cent LCD. The company is rapidly converting its European TV centre at Barcelona from CRT to LCD

TV production and has plans for a second European plant.

Taiwan's largest LCD manufacturer, AU Optronics, is to invest US\$2:35bn in a sixth-generation manufacturing complex, the first phase in an expansion plan that will involve over US\$5bn. AUO will be producing 32, 37 and 42in. TV-suitable LCD panels in the new plant, which is scheduled to come on-line late next year.

DisplaySearch Taiwan forecasts that the LCD TV market will take off strongly in the second half of next year, doubling from 4·2m units this year to 8·4m in 2004. Another market report suggests that sales will reach 30·7m units by 2007. There has already been a warning of future over-supply and price wars.

Dell has announced that it might enter the TV market with LCD sets.

Business news

Last month we reported that electrical/electronics retailer PowerHouse had been placed in administrative receivership. As we went to press it was announced by the administrators that the chain has been sold to a New Zealand retailer, Pacific Retail Group, which will buy the 142 PowerHouse stores, infrastructure and brand, saving over 2,000 jobs. PRG has a 33 per cent share of the NZ market and has branched out into lingerie retailing.

Parts of BoxClever, the TV rental group, have been placed in administrative receivership, including Endeva which provides servicing and logistics back-up, including call-centre support. Endeva employs most of BoxClever's 4,000 staff and runs its 160 outlets. The aim seems to be to restructure the loss-making units and sell them on.

Annual results from Dixons were better than expected, with turnover up from £4-888bn to £5-761bn for the year to May 3 and pre-tax profit only marginally down at £279m compared to £282m. The company reports strong sales of laptop PCs and digital cameras and camcorders during the 18 weeks to September 6. Sales of extended warranties have stabilised after a big fall last year, the result of bad publicity arising from the Competition Commission probe.

Margins on extended warranty sales are higher than on actual product, and Dixons is the market leader in this field.

Amstrad returned to profit (£3·8m) during the year to June 30 as a result of increased sales of digiboxes to BSkyB. The Em@iler business (Amserve) continued to make a loss but is expected to break even this fiscal year. following a halving of the price of the unit last Christmas. Over 255,000 Em@ilers have now been sold: the bigger the user base the greater the possibility of generating significant revenue, which comes from phone and on-line charges and advertising.

Audio developments

Warner Music, in conjunction with Sony, intends to launch combined CD and DVD music-video discs early next year. They will have a music album on the CD side and DVD music-video material on the other side. The technology is being supported by Universal Music, EMI and BMG.

Toshiba has developed the Gigabeat G20, a compact audio player based on a 1.8in., 20GB hard disk that can store over 300 hours of music recorded at 128kbits/sec equivalent to 5,000 four-minute pieces of music or 500 CDs. The unit weighs just 138g. A small lithium-ion battery provides more than eleven hours of continuous playback between charges. The player is compatible with two types of software: Windows Media Audio 9, which is now preinstalled in new Windows PCs; and Toshiba Audio Application, which comes with the player. WMA, MP3 and WVA format audio can be stored and played. A CD compressed to 60MB can be downloaded in approximately 30 seconds via the USB2 connector.



NEC has developed a working prototype mobile phone that can receive terrestrial digital TV transmissions. It uses a portable aerial and incorporates a UHF tuner and an OFDM decoder chip that was developed for wideband CDMA mobile phones. Its disadvantage at present is battery life while in the TV mode. This is about an hour. NEC considers that a life of one hour talk-time and one hour TV time will be required for the product to be a viable commercial proposition. The company is working on improvements that include better receivers, lower power consumption and the development of digital TV/mobile internet applications. The prototype was demonstrated at Telecom 2003, which was held in Geneva during October.

Sharp's wireless TV

Sharp has launched the world's first 'wireless TV'. The Aquos Mobile Model LC15L1E is a 15in. LCD set that can operate completely free of cables and leads. It uses a 2·4GHz spread-spectrum video/audio transmission system with a range of 30cm as a link between the screen and other equipment, to source DVD, VCR and broadcast TV material, and has a battery that provides over two hours' operation. It also has two scart sockets and an aerial socket. The price is about £1,200.

Sharp Microelectronics Europe has launched a megapixel CCD sensor module that can be used to add a camera feature to a slimline mobile phone. The LZOP3721 is claimed to be the smallest and slimmest of its type, measuring just 13.5 x 11 x 9.7mm.

Video recording

Samsung has launched a range of camcorders, Models IT Cam 5, 7 and 9, that use a 1.5GB hard disc as the storage device. Use of MPEG-4 compression enables several hours of video to be recorded on the disc. Top of the range Model IT Cam 9 has an LCD screen for monitoring and playback, a Memory Stick slot and a USB2.0 connector for fast downloads to a PC. Prices range from £500-£700 depending on specification.

Thomson has launched a hand-held video recorder, Model RD2780, that can record video material, MP3 music or JPEG

files on a 20GB hard disc and has a 3·5in. colour screen. It can record directly from a TV set. Use of MPEG-4 compression enables up to 80 hours of video to be stored on the disc. Price is about £500.


Kane Wireless has launched the Vision Station, which consists of a TV tuner for installation in a PC and software that enables programmes to be recorded on memory cards that can be played back via a PDA such as an iPaq or XDA. Use of compression technology from Essential Viewing enables programmes to be stored on the PC's hard disc in a very small space. The system is on sale at Argos and Carphone Warehouse for about £300.

DAB update

The world's first 5.1-channel surround-sound broadcasting system is being tested in a six-month trial in the central London area. Capitol Radio is using Microsoft's Windows Media Audio 9 format, which can compress 5.1 audio into a 128kbits/sec internet protocol stream. NTL Broadcast is providing the trial multiplex, in the L band (1.4GHz). Reception involves use of a PC. RadioScape and Imagination Technologies (Pure) are providing receiving equipment. The RadioScape receiver consists of two PCI-bus cards, while the Pure Model DRX-702ES can feed 5.1 sound to the PC via its USB socket.

Earlier this year RadioScape, NTL and Microsoft demonstrated video via DAB. UK digital radio company Perstel has demonstrated a prototype receiver with a 7in. colour LCD screen. There is so far no broadcaster commitment to DAB video in the UK, but German broadcasters have expressed interest in transmitting the 2006 Football World Cup in this format.

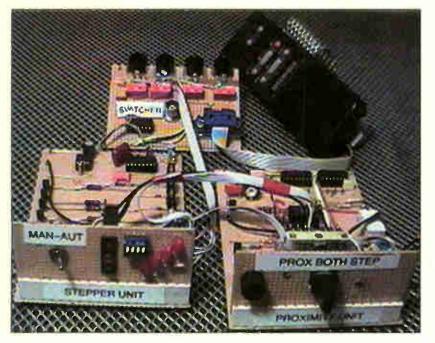Sony has announced that it will launch portable DAB radio receivers early next year.



Simple inexpensive off-theshelf CCTV kits are readily available but lack individual expansion capabilities and flexibility. Ian Rees has devised a system that should fulfil the needs of small-tomedium sized installations, with some added innovations found only in dedicated PC or professional systems

A flexible CCTV system

imple, inexpensive off-theshelf CCTV kits are widely available from DIY stores. The cheapest domestic systems consist of a small CCD camera, 20m of multicore cable, a power supply and a scart plug for connection to a TV set or VCR. Multicamera switching systems with a monitor can be purchased for use with larger domestic or small commercial premises. Some systems

include a PIR detector that can trigger a domestic VCR. The main disadvantages of these kits are their lack of individual expansion capability and flexibility.

This article describes a flexible CCTV system that should fulfil the needs of most small-to-medium sized installations, with some added innovations found only with dedicated PC-based or professional systems. It features a complete integrated control system, but individual circuit sections can be made to operate alone. In its basic form it can accept inputs from two-thirty cameras for splitting and viewing with one-three independent video monitors.

Basic block diagram and operating modes


Fig. 1 shows the complete system in block diagram form. It's built using inexpensive and readily available parts. No rocket science is involved, so the system is simple to understand and readily adaptable. For simplicity, only four cameras and proximity detectors are shown in Fig. 1. There are three possible modes of operation: automatic stepping, proximity control and manual switching.

The stepper controls the switcher unit so that the camera outputs are fed in sequence to the monitor and VCR. The automatic stepping sequence has variable dwell times for each camera. If required, indi-

vidual cameras can be deselected from the sequence. The proximity unit allows better site monitoring by using proximity detectors that are mounted in the field of view of the cameras. Proximity detectors 1-4 can be pressure mats, active/passive infra-red, VOX or gate switches etc. A short audio warning alarm is sounded when the VCR records an event under the control of the proximity unit. In the automatic mode sequential and proximity camera switching can be done independently or together. When done together the sequence switching continues until a proximity sensor is activated. The associated camera is then selected, triggering the alarm and VCR. After a preset time the VCR is turned off and the sequenced switching continues.

The ability of the proximity unit to follow activity from camera to camera can be a considerable advantage in comparison with sequence-only systems. The proximity unit can be used with a domestic VCR. Because only the event is recorded, not the periods in between, a domestic VCR can record large amounts of action in the long-play mode. The short beep tone produced by the audio alarm when an event is detected is very useful. The alarm sound relieves an observer from the need to watch the monitor(s) continually. It can be used even if no recordings are required, to draw attention to activity on the site.

Fig. 1: Basic block diagram of the flexible CCTV security system.

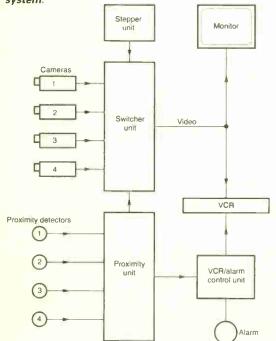

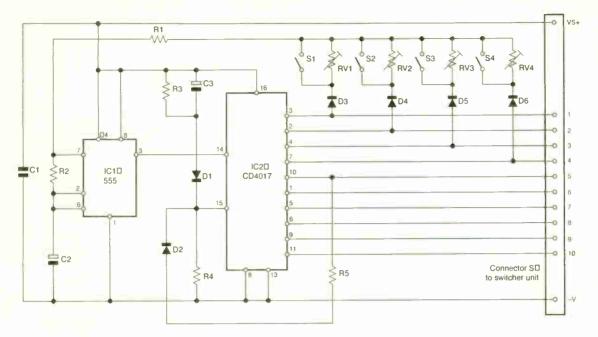


Fig. 2: The stepper unit circuit.

The stepper unit

Fig. 2 shows the stepper unit circuit. It generates a sequence of outputs that's used by the switcher unit to select the cameras. The 555 timer chip IC1 and CD4017 decade-counter chip IC2 produce timed switching pulses that are continuously adjustable up to 250 seconds at each step by presets RV1-4.


When closed, switches S1-4 bypass the relevant timing step: they are used to move quickly across an installed camera that may not be required at the time.

When the supply (VS+) is connected to the circuit C3 charges and IC2 is reset, as pin 15 is taken high. Pin 3, the first in the count chain, provides an output at pin 1 of connector S to a relay driver transistor

in the switcher unit. All the other outputs, at pins 2-10 of connector S, are low. The timing cycle is set by RV1 and the associated components.

The first clock pulse from pin 3 of IC1 moves the counter along one. Pin 2 of IC2 is then high, providing a drive output to the relay driver transistor connected to pin 2 of connector S. Pin 3 and all the other out-

Fig. 3: The proximity unit circuit.

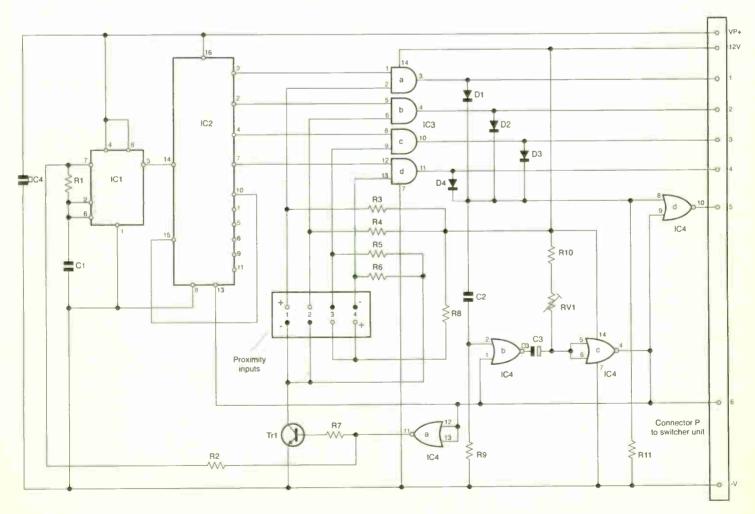

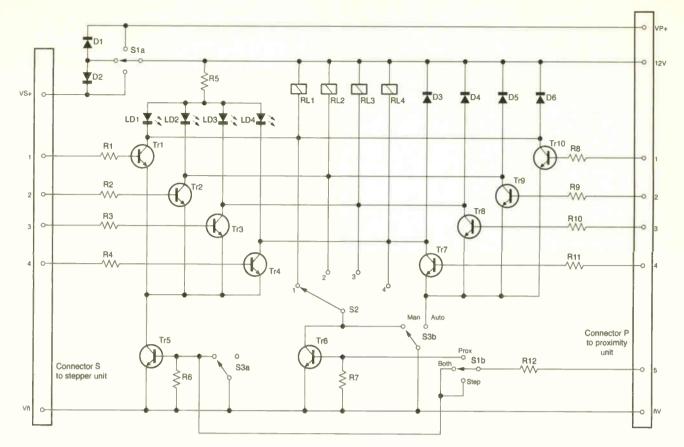


Fig. 4: The switcher unit circuit.

put pins of IC2 are now low. RV2 now provides the adjustable dwelltiming period and thus the relevant camera output on time.

Up to ten sequential outputs can be obtained from the CD4017 decade-counter chip, after which it will automatically recycle. In the four-camera version shown, a reset is forced at the unused fifth step by connecting pin 10 of IC2 via R5 and D2 to pin 15. A 2-9 drive sequence can be set up by using this forced-reset method.

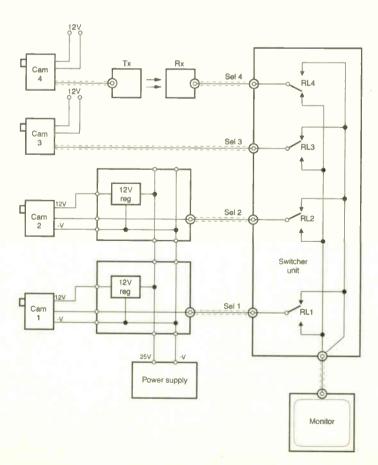


Fig. 5: Video switching with a four-camera system.

The proximity unit

The proximity unit circuitry, shown in Fig. 3, can also control up to ten inputs. But to simplify matters only four inputs are shown. The clock chip IC1 and counter IC2 use a similar circuit arrangement to that in Fig. 2. The 555 chip runs at about 500Hz. It drives pin 14 of the counter chip whose outputs are used, in conjunction with the and gates in IC3, to scan the proximity detector inputs.

As shown, proximity inputs 1 and 2 are configured for normally-closed detectors such as infra-red beambreak or PIR units. Pressure mats and gate/door switches can be used with the normally-open inputs 3 and 4. A check with Table 1 shows that a high output is obtained only when both inputs of an and gate in IC3 are high. When the cycling output from IC2 coincides with a high from the proximity input, the output from the relevant and gate goes high. The rising edge of the high is passed via D1, D2, D3 or D4 and C2 to trigger the monostable timer formed by IC4b/c. The timer turns off Tr1 and freezes the scan of IC1, IC2, holding a high output to the switcher unit from IC3 via connector P. The relevant relay driver in the switcher unit then selects the camera associated with the proximity input. The dwelltime is adjustable between 10-60 seconds by RV1. With Tr1 turned off, the normally-earthed ends of the proximity inputs go high for the duration of the timed period. This

ensures that IC3 continues to provide an output after the proximity

input stops.

Nor gate IC4d produces a low during this period. It's used either to turn off the stepper unit or default camera of the proximity unit depending on the position of switch Sla/b in Fig. 4. Audio alarm and VCR switching are controlled by IC4's complimentary outputs at pins 5 and 6 of connector P. At the end of the timing period IC4b/c revert to their original state, returning control to the stepper unit or proximity default. Only one camera is selected at a time, and any new proximity inputs received during the freeze period are ignored. The same process occurs whichever proximity input is triggered.


Take care when wiring the proximity inputs, and note that the '-' terminals are above chassis earth potential (-V) when Trl turns off. If the '-' terminal is accidentally shorted to -V earth none of the proximity inputs will select and hold. Simultaneous proximity triggers that might cause more than one camera to be selected are automatically sorted by the scanning action to provide a single output.


The switcher unit

I always feel that I should use solidstate devices in my circuits, but make no apologies for using relays in this part of the system. Miniature relays are simple, robust and reliable. They have not got the extended service life of solid-state devices, but fitting them in sockets can ameliorate this. I have in fact never had to replace any electromagnetic relays in long-standing systems where they have been employed.

Fig. 4 shows the switcher unit circuitry, which receives inputs from the stepper and proximity units. Two sets of driver transistors control the four relays. This may seem a bit unnecessary, but the arrangement works very well and makes function switching simple.

The three-position function switch S1 enables the cameras to be controlled by the stepper or proximity unit or both together. When proximity is used alone and not triggered a default camera needs to be selected, otherwise the monitor screens will be blank. Selection is done by Tr6, which works in conjunction with the manual switch S2. When Tr6 is turned on at the end of a proximity freeze cycle (S1a/b in the prox position) S2 selects the default camera. With S1 set at its centre (both) position the stepper and proximity units run together. As long as there are no

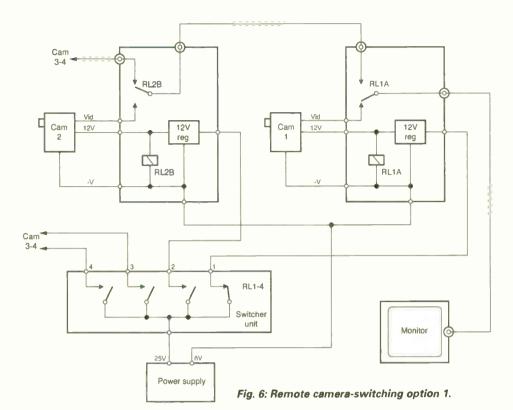


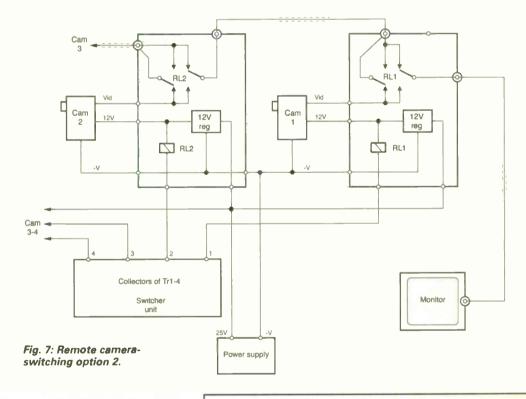

proximity inputs the cameras will be controlled by the stepper unit. If a proximity input is received, the proximity unit takes over, interrupting the stepper cycle by turning off Tr5 (through the gate action of IC4d in Fig. 3) and switching on the required camera as described above. The stepper action continues once the proximity unit's freeze period has been completed.

LED indicators L1-4 show which

Table 1: Truth tables for IC3 and IC4 (Fig. 3).					
And	d gate IC	03	Nor	gate IC4	
Inp	uts	Output	Inpu	uts	Output
a	b		а	b	
L H H	L H L	L L H	L H H	L H L H	H L L

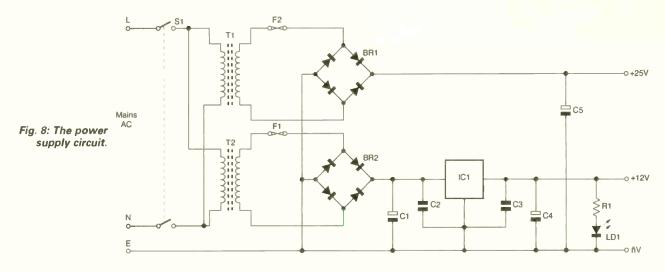

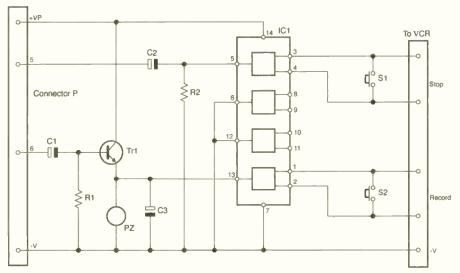


Fig. 9: The VCR control and audio alarm circuit.

camera is activated. With the auto/manual switch S3 set to manual, cameras can be selected directly using switch S2. Note that if the relays have suppression diodes built-in, D3-6 will not be required.

Signal switching

The supply of power to the cameras and sending images to the monitor(s) and VCR(s) can be carried out in a variety of ways. Fig. 5 shows how a four-camera system using a variety of camera types can be selected for video signal only.

A 25V DC line from the power supply feeds cameras 1 and 2. Assuming that the CCD cameras are 12V DC types, local L7812 12V IC regulators reduce the supply for these cameras. This method compensates for the voltage drop along the DC supply cables. Camera 3 is shown using its own 12V power supply derived from the mains. Where a location is difficult to cable, a 2GHz RF link can be used, as shown for camera 4. Composite video outputs are selected by relay contacts RL1-4. Unselected video inputs are muted to prevent crosstalk between cameras. Reed relays are best, but sub-miniature

mechanical types have proved to be satisfactory.

The disadvantage of this cabling arrangement is the large number of coaxial lines that have to be run individually and terminated at the switcher. If they are many in number they can be difficult to conceal. The position of the security room or office is never at a convenient location, so a considerable amount of time and energy may be required to expand or modify the system later.

A good way of simplifying the problem is to use remote switching, as shown in Figs. 6 and 7. Remote switching uses one video feed daisy-chained via the cameras in the system. One additional multicore telephone-type cable can supply both power and control to the cameras.

In Fig. 6 switcher unit relays RL1-4 now supply the switched 25V DC feed to the selected camera. Each camera has a local routeing relay (RL1A, RL2B etc.) connected to the output from its L7812 12V stabiliser. When one of these relays is selected, its contacts connect the camera's video output to the coaxial line. All cameras on the feed line other than the one selected are then isolated. The line down to the moni-

tor(s) is maintained via the normally-closed contacts in the de-energised relays in the video line. As only one camera at a time is switched on, minimum power is drawn by the system and crosstalk is eliminated.

An irritating problem with simple systems is the time taken for the monitor's field scanning to roll into lock when cameras are liveswitched. Careful adjustment of the monitor's field hold can minimise but not eliminate the problem. Methods usually employed with better cameras and systems are not always available with cheaper CCD units. Some systems use signal blanking at changeover, increasing the time available for the monitor's field timebase to lock. The short time required for a camera to produce a picture when first switched as in Fig. 6 can give a similar if inferior effect, masking the fieldsync problem by turning a shortcoming into an advantage. Ensure that any cameras used in this way are able to produce a viewable and locked image quickly at cold switch-on.

If supply switching is not practical because of the cameras used, the arrangement shown in Fig. 7 can be used with the cameras powered all the time. The switcher unit relays RL1-4 are now located at or near the camera. Each relay coil is connected directly to the switcher unit via the control cable. The relay contacts connect the signal from the selected camera to the coaxial feed and mute signals from the unselected cameras. Miniature double-pole relays are used, the second pole muting unselected signals farther along the chain. Depending on line transmission, mismatching and other losses, muting may or may not be required.

In practice a mixture of remote and local camera control can be used for optimum flexibility.

Power supply

The power supply requirements are simple, see Fig. 8. It is best to use separate supplies for the cameras and control electronics. Transformer T1 and fuse F2 are selected to match the current requirements of the cameras in the system. One of my early installations that used a single power supply started to malfunction when an extra camera was fitted – the increased current drain reduced the voltage just enough to upset the stepper-unit timing. Fortunately it was possible to power the camera locally from the mains. which corrected the problem.

It is important to include capacitors C2 and C3 in Fig. 8. They must be soldered as close as possible to the input and output pins of the regulator IC1, to prevent instability. Instability in IC1 will usually result in low output when the stabiliser is on load. It's best to solder the capacitors carefully to the legs of the IC. Although not shown in Figs. 5, 6 and 7, similar capacitors should be fitted to the stabilisers here.

The upper input voltage limit of the stabiliser specified is 30V DC. A heatsink may be required if it runs hot. Overheating will make it shut down. The lower input voltage level should not be less than 15V if stabilisation is to be efficient. The L7812 is rated at 1A. If more current is required (up to 2A) an L78S12 should be used.

VCR control and alarm

Slow-scan VCRs are currently still expensive at about £400 while domestic ones are available at less than £50. This system's ability to record short bursts of event action triggered by proximity detectors makes the use of a domestic VCR very attractive. With a standard three-hour VHS tape used in the long-play mode and the proximity dwell timing set to 60 seconds, 360 event recordings can be made before tape rewind $(60 \times 60 \times 6 = 21,600)$ seconds/60 = 360 events). Even allowing for false triggering, this is still a considerable recording period. A four-hour tape would increase the recording time, but these are prone to damage and tangling in cheap VCRs.

The employment of staff to watch one or more video monitors continuously is not practical with a small installation. Use of the proximity unit to trigger an audio alarm immediately draws attention to the monitor(s) when an event has been detected.

Fig. 9 shows the circuit of the control/alarm unit. IC1 is a CD4066

quad bilateral switch chip that's used to control the VCR record and stop. The rising edge of the trigger output from the proximity unit charges C1 and briefly biases Tr1 on. This transistor then supplies voltage to the piezo-sounder PZ and pin 13 of IC1. With a positive voltage at pin 13 of IC1, the impedance between pins 1 and 2 changes from high to low. This change is used to operate the VCR's record function. A hardwire connection can be made across the record-button switch on the VCR or the remote-control unit. When the timed-record period ends, pin 5 of connector P goes high charging C2. Pin 5 of IC1 then briefly lowers the impedance between pins 3 and 4 and the VCR stop function operates, in the same way as for record. Press-button switches \$1 and \$2 are included to check the VCR link and provide a convenient means of checking or

setting the record and stop func-

Hardwiring directly to a VCR is usually simple, but connection to a remote-control unit can be tricky and requires care. If you don't want to modify the remote-control unit supplied with the VCR, a cheap universal type could be bought. The only solderable connection points likely to be found will be at the control IC. Trace the print back from the record and stop button pads to the IC. A good light, optical magnification and a fine-pointed soldering iron are required for this task. A four-way flat ribbon cable is best for the link. Leave the remote-control unit powered by its own battery.

Next month

In Part 2 next month we'll consider cameras, proximity detectors, system expansion, construction and installation.

Components list

Stepper unit

470Ω
1kΩ
470kΩ
2.2kΩ
1MΩ linear presets
0.1µF 100V ceramic
100µF 25V electrolytic
1µF 25V electrolytic
555 timer
CD4017
1N4148
1-pole 1-way switches

(4-way DIP switch OK)

Proximity unit

R1	1kΩ
R2, R10	100kΩ
R3-6	10kΩ
R7	18kΩ
R8	6.8kΩ
R9	15kΩ
All 0.25W 5%	
RV1	1MΩ linear preset
C1, C2	47nF 100V Mylar
C3	100µF 25V electrolytic
C4	0.1μF 100V ceramic
IC1	555 timer
IC2	CD4017
IC3	CD4081
IC4	CD4001
D1-4	1N4148
Tr1	BC547B

Switcher unit

R1-4	18kΩ
R5	1kΩ
R6, R7	2.2kΩ

R8-12	18kΩ
All 0.25W 5%	
D1, D2	BY133
D3-6	1N4148 (see text)
Tr1-10	BC547B
LD1-4	5mm red LEDs
RL1-4	12V 700Ω relays (see text
S1	2P 3W switch
S2	1P 4W switch (see text)
S3	2P 2W switch

Power supply

R1	1kΩ 0·25W 5%
C1	1,000µF 40V electrolytic
C2, C3	0.1µF 100V ceramic
C4	47µF 16V electrolytic
C5	2,200µF 40V electrolytic
IC1	L7812 (see text)
BR1, BR2	3A bridge rectifiers
LD1	0.5mm LED
T1	240V/16V mains TX (see text
T2	240V/16V 1A mains TX
F1	500mA 20mm fuse
F2	See text
S1	DP mains on/off switch

VCR control and audio alarm unit

R1 R2 Both 0-25W 5%	3·3kΩ 22kΩ
C1 C2 C3 IC1	33µF 25V electrolytic 22µF 16V electrolytic 1µF 16V electrolytic CD4066
PZ	12V piezo buzzer 2.7kHz 10mA
\$1, \$ 2	Normally-open momentarily- close push-button switches



at the Internationale Funkausstelung

The 2003 IFA featured the latest developments in digital TV, flat screen technology, DVD players and recorders, camcorders with various storage systems and domestic networking. George Cole was there to report for us

he Internationale Funkausstelung (IFA) is held in Berlin every two years and has become the world's largest consumer electronics show. Unlike most other electronic shows it's open to the public. So the exhibition halls are full of people interested in the latest developments in consumer electronics. At this year's show there were 1,007 exhibitors spread over 160,000 square metres of floor space. Major attractions included flat-screen TV sets, DVD recorders and networked products.

Digital TV

On August 4 Berlin and Brandenburg became the world's first DTT-only region

when the analogue TV transmitters were switched off for the last time. The digital switchover took place just six years after Germany's first DTT tests were carried out and eighteen months after a Memorandum of Understanding was signed between public and commercial broadcasters and the Media Institution of Berlin and Brandenburg, which co-ordinated the switchover. The German government aims to end all analogue TV transmissions in 2010.

The Panasonic TX32DTX30C is the company's first IDTV set released in Germany for free-to-air (FTA) transmissions. Its features include a 32in. Quintrix 16:9 CRT, 100Hz scanning, a 500-page teletext memory and three scart sockets. Pioneer unveiled an FTA digital set-top box, Model DBR-TF100GB, and plans to launch an IDTV set for Continental markets. The DBR-TF100GB has two scart sockets, an RF loopthrough/modulator module and a newly designed user interface that Pioneer plans to adopt across its entire range. Nokia's MediaMaster Models 260S and 260T are digital STBs for satellite and terrestrial reception respectively. They include an 80GB hard drive on which up to 40 hours of TV programming can be recorded: it's also possible to transfer to it more than 3,000 images from camera-phones using a

The Panasonic TX32DTX30C is the company's first IDTV set released in Germany for free-to-air (FTA) transmissions.





The Pioneer DV565A is a versatile player that can also handle DVD-Audio and SACD discs and JPEG images stored on a CD.

wired or a wireless Bluetooth connection. Pace's digital STB offerings included Models DC210 and DS201. They use Pace's new common hardware system that enables a cable, satellite or terrestrial frontend to be added as required. The Puma is an integrated dual-decoder and twin-tuner satellite STB with an optional 20GB hard drive that enables it to be used as a personal video recorder (PVR). The Samsung SPVR-7400CI is a digital PVR with 80GB hard drive and two common interface (CI) slots. Humax showed the PVR8000, a PVR with a smart removable hard drive, making it easy for owners to upgrade to a larger-capacity drive.

The German market is also a target for Multimedia Home Platform (MHP) products. MHP is a specification developed by the Digital Video Broadcasting (DVB) project to add features such as interactivity and internet links to digital TV broadcasts. Sony had a large display of MHP sets, all with CRTs, including Model DVP-NS430S which includes a slot for a Memory Stick card. The Humax CI8140 in an MHP-compliant STB that also includes a Dolby Digital optical output socket. Samsung and Nokia also showed MHP set-top boxes.

TV sets

On some stands, for example Philips, it was hard to find a CRT model. Philips will have launched thirteen non-CRT TV models by the end of the current year, with ten screen sizes. They include five models (50PF9965, 42PF9965, 37PF9965, 32PF9965 and 30PF9965 - the first two digits indicating the screen size) that incorporate the company's Pixel Plus technology. Model 30PF9965 has an LCD screen, the other models having plasma screens. Pixel Plus is a digital processing technology that provides enhanced resolution. Philips held an interesting demonstration that compared Pixel Plus with rival digital-enhancement technologies developed by Sharp, Sony, Panasonic and Samsung. Both LCD and plasma products were compared and certainly, on the evidence, Pixel Plus provided the best pictures from a subjective point of view. But the demonstration also highlighted how difficult it can be to make definitive comparisons, as the sets may have different display rates, e.g. 75Hz or 100Hz and interlaced or progressive scanning. Philips

also showed two small-screen LCD sets and three portable LCD models, with screen sizes from 13 to 20in.

Sony's offerings included for LCD Wega models, KLV-15SR2, KLV-21SR2, KLV-17HR2 and KLV-23HR2 – the latter has a Memory Stick card slot. The SR2 models provide XGA (1,024 x 768) resolution while the HR2 models feature WXGA (wide XGA, i.e. 1,280 x 720) resolution. All models include a composite/component video processor that converts an analogue signal to digital form then processes it to reduce noise. A digital comb filter improves Y/C separation while Sony's Digital Reality Creation (DRC) technology provides enhanced resolution.

Panasonic displayed a number of LCD TV sets including the TX-22LT3F, a 16:9 model with integrated tuner. It uses Panasonic's Real Mach panel technology that provides a contrast ratio of 400:1. Sharp's massive stand was heavily populated with LCD sets. One of the highlights was Model LC15L1E (Aquos Mobile), a TV set that operates without a TV aerial or a power socket. The 15in. LCD set uses a lithium-ion battery for power and an AV transmission system to pick up and deliver sound and pictures. Samsung had on show a 54in, LCD TV with a contrast ratio of 800:1: the TFT-LCD module is only 2in. thick.

JVC's LCD TV sets included Models LT32C31, LT26C31, LT23E31 and LT17E31, which all incorporate the company's DIST (Digital Image Scaling Technology). Grundig was showing its Tharus range of LCD and plasma sets. The company also offers the Megalogic system, a TV guide and teletext function to the 2.5 specification, and Teleweb that enables teletext pages to be surfed as if one is using the internet instead of the conventional approach of entering combinations of page numbers.

There were also lots of plasma screens around, including the Pioneer Models PDP-504HDE and PDP-434HDE (the first two digits indicate the screen size in inches) that incorporate the company's Pure Digital image-processing technology. The images I saw certainly looked clean and sharp. Both models incorporate a multimedia viewer that can read JPEG images stored on a memory card. Thomson showed a 50in, plasma set, Model 50WB03, which uses the company's Hipix technology to multiply the number of pixels per line by 1.5 to create a sharper picture. Panasonic's plasma Models TH42PA20E and TH37PA20E feature the company's Real Mach technology. Model PD42V31 from JVC includes DIST technology and a 3D sound system.

Samsung showed a 70in. plasma display panel with 2.07 million pixels (1.920 x 1.080 scanning), twice the resolution of today's panels. It expects this to be used for public display systems rather than the living room. The LG stand displayed 71 and 60in. plasma displays and a 52in. TCD TV set.

Other TV products of interest included the Thomson Model TW610S, a 61in. projection set with a built-in DVD player, and a TV recorder from the German company Metz. The latter has a 160GB hard drive that can store up to 200 hours of programming and functions such as live pause. In addition by subscribing to a special service users can set the TV's timer via the internet.

Philips gave a glimpse of the future with a PolyLED display. The company's research stand showed a 2 x 3in. full-colour prototype with a resolution of 176 x 220 pixels. Unlike a TFT display, PolyLED doesn't require a backlight and thus consumes less power. Construction basically consists of two glass plates that sandwich the PolyLEDs. Philips envisages



Philips DVDR 70

that the technology will be used initially in portable products such as mobile phones but also has plans for in-car systems. The two biggest problems at present are scaling up production and increasing the lifetime, which is currently a few thousand hours the target is 8,000 hours by 2005. Philips also showed its Mirror TV. This combines a 17-30in. LCD screen with polarising technology that enables almost 100 per cent of the light to be passed through a reflective surface. The screen can therefore be flipped between a TV display and a mirror. Philips sees considerable potential in the hotel market, and the demonstration room was set up like a hotel living room and bathroom. You could shave while watching the morning news in a corner of the mirror. A domestic version is expected possibly in 2005.

DVD

It was hard to spot a VCR on any of the stands: DVD is fast becoming the format of choice for watching video material at home, with more than half of European homes (53 per cent) now having a DVD layer. This has been helped by the falling cost of DVD players. In a keynote speech Gerard Kleisterlee, president of Philips, pointed out that in 2001 DVD players were at the cutting edge of technology and commanded a fair price premium but, since then, the price has fallen by a factor of ten. In some cases DVD players are given away free with other products, such as large-screen TV sets. The good news is that manufacturers are still developing DVD products with added features.

The Pioneer DV565A is a versatile player that can also handle DVD-Audio and SACD discs and JPEG images stored on a CD. It reads CD Audio, Video CD and Super VCD discs, and DVD-R and DVD-RW discs recorded in the Video Mode.

The Samsung Model DVD-HD935 is claimed to be the world's first HDTV-compliant DVD player. It uses scaling-up technology to increase the video resolution to 720 x 1,080 (lines). Faroudja's DCDi de-interlacing picture technology improves movement within the picture and sharpens outlines.

Star Media showed an interesting player, Model DivX5000. DivX is a form of video compression that's widely used on the internet. It's based on MPEG-4 technology and enables up to two hours of video to be stored on a CD-R disc. DivX picture quality is surprisingly good. The system is also used by some digital cameras and camcorders to record video clips that can be sent over the internet. Star Media emphasised that the DivX5000 can play DVD discs from all regions. The company also showed DVD players with progressive-scan PAL outputs.

The Thomson Model DTH7500 is a combined DVD player and 80GB hard drive that can store up to 80 hours of video. Other features include live pause, a front USB connection, a generic memory-card reader and JPEG reader: digital photos or MP3 music files can be transferred from a PC to the DTH7500's hard drive.

The LG Latrion is a combined 29in. TV set, DVD player and VCR.

There was a stand devoted to DVD-Audio, with a selection of players and discs. The format seems to have a higher profile in Germany than in the UK. I came across a number of DVD-Audio (and SACD for that matter) discs in record shops. According to the DVD-Audio Council, whose members include JVC, Panasonic, Sharp and Toshiba, there are not more than 500 DVD-Audio titles available worldwide.

DVD recorders

If IFA is anything to go by, it looks as if consumers, retailers and service engineers will have to learn to live with several recordable DVD formats. There is little sign of the market consolidating, and there were giant stands devoted to all the major recordable formats and their respective associations. Many companies that support one format are also members of a rival DVD association however. So it's no surprise that there is much consumer confusion over recordable DVD.

The DVD+RW Alliance, which has more than sixty members including Philips, Sony, Thomson, Dell, HP and TDK says that 80 per cent of the consumer DVD records sold in Europe are +RW machines. A new x8 recording speed was announced for +R discs.

Sony announced two new dual-format DVD recorders, Models RGR-GX7 and

RGR-GX3, which record on both DVD+RW and DVD-RW discs. Sony has also developed two DVD-RW camcorders – apparently because the -RW specifications were finalised first.

Philips launched five new DVD recorders, the DVDR70, 75, 77 and 80 separates and the LX9000R, a DVD recorder and home-entertainment system it includes a 5.1-channel speaker system with Dolby Digital, DTS and MPEG multichannel sound. Model DVDR77 provides an 8-hour recording time on a single disc and has a memory-card feature that can read almost all the types of memory cards used by digital cameras, enabling JPEG images to be transferred to DVD discs. Another feature converts JPEG images into DVD-compatible slide shows that can be played by almost all DVD players and PC DVD drives. The DVDR80 includes the Guide Plus+ on-screen guide, which enables users to make a timed recording simply by selecting the programme from an on-screen menu and pressing a button.

Yamaha's Model DRX2 plays all types of DVD discs except DVD-RAM, and also plays CD-R/RW discs. It offers six recording modes that provide recording times between 1-6 hours, including linear PCM audio in the two-hour mode.

Benq, a company with manufacturing operations in the Far Easy including Malaysia and Taiwan, had on show what is claimed to be the world's slimmest DVD recorder, Model JH300, which is just 5.9cm high. It's a DVD+RW machine that includes a progressive-scan output. It will be launched in NTSC markets first.

The Humax Model DRP560, a sleek silver box with an orange trim, is a DVD+RW recorder that can also play back DVD-R and DVD-RW discs (the latter in the video mode). It has six recording modes.

The RW Products Promotion Initiative (RWPPI) represents the DVD-RW and DVD-R formats. It has 58 member companies, including Prioneer, Samsung, Sony, LG and NEC. Pioneer is the main driver behind the -RW format, so it was no surprise that the company's press event had a lot to say about the format. Evidence that DVD-RW has better compatibility with standard DVD-Video players was quoted. The DVD+RW Alliance had made



The JVC DR-M1 DVD-RAM recorder is also compatible with DVD-R and DVD-RW discs

the same claim for its format less than half an hour previously!

Pioneer's flagship product is Model DVR-5100H-S, a DVD recorder with an 80GB hard drive that can store up to 102 hours of video programming. It has four modes, Fine (17 hours), SP (34 hours), LP (68 hours) and EP (10-2 hours). The company's previous recorder, Model DVR-77H, used eleven LSI chips. These have been replaced with a single LSI chip that has four million gates. A high-speed copying system can transfer EP recordings on to a blank disc at x24 speed. Once a DVD-R/RW disc has been formatted in Video Mode, the DVR-5100H-S creates a menu of thumbnail images that show what has been recorded on the disc. Pioneer was asked why it had launched a DVD burner that can also record on DVD+RW discs. A company spokesman explained that Pioneer makes a lot of drives for OEM manufacturers, who have demanded that the DVD drives are compatible with a variety of recordable DVD formats. He stressed that the company has no intention of launching a consumer product with DVD+RW operation.

The Sharp Models DV-HR350S and DV-HR300S are combined DVD-RW and hard disk recorders

The Recordable DVD Council (RDVDC) is an association of more than ninety companies, including Panasonic, Toshiba, Hitachi and Samsung, that support the DVD-RAM format. To add to the confusion there's yet another group, the RAM Promotion Group (RAMPG), whose members include Hitachi, Panasonic, Toshiba and JVC. Using the slogan 'Real DVD', the RDVDC had much to say about the compatibility of DVD-RAM products with other types of DVD discs. But this compatibility is essentially one-way, as almost all DVD-Video players can't play DVD-RAM discs, even ones without a protective caddy. This is because DVD-RAM uses a different recording format, land-and-groove with zoned constant linear velocity (ZCLV). While this enables DVD-RAM to provide hard-disk type features such as random access, the price paid is lack of compatibility.

Panasonic released a brochure listing all the European DVD products that are compatible with DVD-RAM discs, but only five are consumer DVD-Video players – four from Panasonic and one from JVC. The Panasonic DMR-E100H is a combined DVD-RAM recorder with an 80GB hard drive. It also has an SD Memory Cared slot. The Panasonic SC-HT1000 is a DVD-RAM home-theatre system with 5.1-channel sound and DVD-Audio compatibility.

The JVC DR-M1 DVD-RAM recorder is also compatible with DVD-R and DVD-RW discs. It incorporates a block noise reduction circuit and Hadamard noise reduction for reducing 'mosquito noise'. Other features include a progressive-scan PAL output, a timebase corrector and on-



Panasonic has developed a range of camcorders that record on an SD Memory Card. The D-snap range consists of Models SV-AV100.

disc timer programming. The latter writes timer data on disc, enabling the timer to be set simply by inserting a programmed disc. The DR-M1 is also part of JVC's QP-ES9AL home-theatre system.

Blu-ray

I found a number of Blu-ray recorders at the show. This format could be the next step after recordable DVD, using a blue laser and 27GB discs that can store up to two hours of high-definition video. Philips and JVC had prototype Blue-ray recorders on their stands while Sony and LG showed production recorders, Models BDZ-S77 and BD-VDR respectively.

Camcorders

A number of tapeless camcorders were shown at IFA. The Hitachi Models DZ-MV350E and DZ-MV380E, also the Panasonic Model VDR-M30, use 8cm DVD-RAM and DVD-R discs. The Sony Models DCR-DVD100 and DCR-DVD200 use 1.4GB DVD-RW and DVD-R discs that can store up to 60 minutes of video. They also have a x10 zoom and a high-speed USB 2.0 connection for transferring images to a PC.

One product that turned a lot of heads was the Samsung ITCAM7, which incorporates a 1.5GB hard drive to store moving video, still images, music and data files. It can thus be used as a camcorder, digital camera, portable MP3 player or even as a portable hard drive. Video is compressed in MPEG-4 form and can be played back at 25 frames/second with VGA (640 x 480) resolution. You can connect it to a TV set, VCR or PC.

Panasonic has developed a range of camcorders that record on an SD Memory

Card. The D-snap range consists of Models SV-AV100, SV-AS10 and SV-AV20. They record both MPEG-2 and MPEG-4 video and can store up to 20 minutes of MPEG-2 video on a 512MB card. The following recording modes are available with the D-snap range: MPEG-2 fine mode at 6Mbits/sec and standard mode at 3Mbits/sec; and MPEG-4 super fine (320 x 240) at 1Mbits/sec, normal (176 x 144) at 30kbits/sec, or economy (176 x 144) at 100kbits/sec. The SD Memory Card has a maximum data transfer rate of 10Mbits/sec – 1GB cards are under development.

As the D-snap range uses an SD card instead of tape or a disc, the camcorders are extremely small. Model SV-AV100 measures 3·32 x 8·89 x 6·49cm (credit-card size) and weighs 156g. Model SC-AS10 weighs just 56g, making it lighter than a pack of cards. How do you go about servicing such a tiny device? When a D-snap camcorder is placed in a base station images can be transmitted to a TV set or sent via a USB link to a PC.

Home networks

Home networking and system convergence were major themes at this year's IFA. Many companies showed systems that are designed to link various domestic entertainment devices to each other and/or the internet.

LG's home network involved a living room, kitchen and study, with a wall-mounted plasma screen as the main display. Philips has extended its Connected Home concept. This involves a broadband internet connection to a 'Connected Planet' which uses WiFi wireless technology to distribute digital content such as music and video around the home. Users thus have access to information and entertainment anywhere and anytime via various devices.

Philips' new products included the Streamium MX6000I, a DVD home entertainment system with WiFi access to content stored on a PC or on-line. In fact there were quite a few WiFi hotspots dotted around the IFA, and people were using laptop PCs to log on to the internet from a variety of places. Philips' Portable Blue is a tiny optical disc about the size of a 10p piece: it can store up to 1GB of data, using blue-laser technology.

Thomson's Oz server stores music, video and images and distributes them around the home using 5GHz RF technology. JVC also demonstrated a 5GHz home-

distribution system.

The Broadband Box, a Swedish company, demonstrated a product with the same name. It's a combined PC, DVD recorder, digital TV recorder, audio library, radio, photo album and internet terminal, all contained in a large silver and maroon box, with a broadband connection for downloading digital content from the internet. It's an impressive product. But whether consumers will want to put all their digital eggs in one basket remains to be seen.

The TETRA problem

TETRA is an international standard for digital mobile communications. The police and other emergency services in the UK are gradually adopting TETRA systems. They are high-powered, and can cause UHF TV interference problems. Bill Wright describes the problem and the remedies that can be used



Photo 1: TETRA 'tyre marks' on a TV screen. Reception was with a verticallypolarised logperiodic aerial and a singlestage UHF/VHF masthead amplifier, 3km from the TETRA mast which was 15° off-axis from the TV transmitter. The **TETRA field** strength was 15dB stronger than that of the analogue TV channels.

ETRA stands for TErrestrial Truncked RAdio. It's an international standard for digital mobile communications and, in the UK, the police and other emergency services are gradually adopting TETRA systems. TETRA bears some resemblance to the digital mobile phone networks, but the cells are generally larger and the transmission powers higher.

The introduction of any new transmission system is likely to cause some degree of interference to existing services. But the problems that TETRA is causing to TV reception seem to be much more widespread than anyone anticipated. There are deep political issues involved with the implementation of TETRA and, in many districts where a TETRA mast has appeared. there is local feeling that the Home Office, having committed billions to the scheme, is riding roughshod over responsibility for TV interference problems. This is not the place to go into that, so I will simply describe the technical problem and suggest remedies.

The frequencies allocated for police and fire service TETRA use in the UK are 380-385MHz (mobile) and 390-395MHz (fixed). The company that operates TETRA, O2 Airwave, is building a network using these frequencies – the process should be more or less complete by the end of the year.

TETRA and TVI

There is nothing particularly pernicious about these transmissions. TETRA interference has become noteworthy simply because the transmitters are new, quite high-powered, and are often in residential areas. Most of the normal TVI (TV interference) remedies apply when dealing with TETRA interference. But, as the interfering signals are digital, some familiar TVI symptoms such as audio breakthrough will not be

present. And as the base stations transmit continuously the interference does not stop and start like, for example, TVI from a taxi base station. Apart from these points, my comments here about TETRA interference apply equally to any strong interfering transmissions, especially to those between 300-450MHz.

TETRA interference problems are most likely to arise when one of more of the following conditions apply:

- (1) The TETRA mast is within a few km.
- (2) The TV aerial is vertically polarised.
- (3) The TV aerial is of the group A (chs. 21-35) or wideband type.
- (4) A masthead amplifier, particularly a two-stage one, is in use.
- (5) The TV field strength is poor.

Since TETRA transmitter aerials are flat panels that are designed to radiate most power towards the target area, the field strength in areas very close to the mast might be rather less than expected. But areas on high ground 2-3km from a mast, on the other side of a valley for example, can be pretty well swamped with signal.

Interference problems are uncommon when the TETRA field strength is relatively low, unless a masthead or distribution amplifier is in use. At locations where the field strength is very high however interference is quite common, even where the TV field strength is good and the aerial is connected to the TV set directly, with no signal amplification.

If the interfering field strength is very high, the unwanted signal can enter either via the aerial or directly into the TV set or VCR. This is really an EMC (electromagnetic compatibility) shortcoming with the TV set or VCR. The symptoms can be very peculiar. and may not look like TVI. More or less anything is possible, though a common symptom is faint patterning even when the TV set is working with a scart input. I'm generalising from experience with only a small sample, but the very cheap 'supermarket special' TV sets seem to be more susceptible to the problem than others. If you come across a set that works perfectly on your bench but persistently misbehaves in the customer's home, have a good look around the immediate neighbourhood for a transmission mast. Since TETRA often shares a site with cellphone and other transmissions, the mast will probably not be new. Look for new panel arrays. These will often be mounted below the cellphone panels, on arms that position them away from the mast. Some TETRA transmission sites are atop blocks of flats, so TV sets on the higher floors

of adjacent high-rise blocks may be in a very strong interfering field (the occupiers will be as well – there are contentious health concerns about this).

TETRA transmissions are properly engineered of course, and the out-of-band radiation should be minute. Nevertheless the second harmonic coincides with UHF TV ch. 60. So, if you encounter strange problems with this channel, TETRA could be the culprit.

Masthead amplifiers

Normally it's the fundamental frequency that causes the trouble, because 400MHz is well within the passband of most aerial amplifiers. Thus the vast majority of problems arise when some sort of aerial amplifier is in use. If you think about it, use of a masthead amplifier means that the TV signals are likely to be on the low side, so a fairly-close TETRA transmitter could produce a field strength 30-40dB higher than that of the TV signals. Even allowing for the fact that the aerial is pointing at the TV transmitter rather than the TETRA mast, and isn't designed for 400MHz reception, it is quite likely that the masthead amplifier will be presented with enough input signal to cause overloading. In its resulting non-linear condition, the amplifier will add interference to TV channels that have no obvious relationship to the interfering frequency.

The effects vary. DTT (Digital Terrestrial Television) often withstands this interference surprisingly well, and remains unaffected when the analogue channels are quite badly affected. But reception will be impossible beyond the point where the DTT carrier-to-noise ratio falls off the edge of the 'digital cliff'.

Because the TETRA signal is digital, the familiar telltale signs of breakthrough are not present with analogue TV reception. The word 'breakthrough' implies that the interfering carrier's modulation is visible or audible in recognisable form at the TV set, and this doesn't happen with TETRA. There are no disembodied voices whispering "you go round the back while I watch the front" or suchlike police chat coming from the customer's TV set. Interference to analogue reception can be mistaken for that caused by an oscillating masthead amplifier, but a closer examination of the screen will often suggest the real cause of the trouble.

The appearance of the patterning varies a great deal, depending on the relative strength of the interference, but Photo 1 is fairly typical. The distinctive white horizontal bars, each made up of diagonal stripes, have given rise to the description 'tyre marks'. This effect is presumably the result of the pulsed nature of the TETRA signal. There may well be cross-modulation, with one TV channel appearing faintly behind another.

In a really severe case TETRA can wipe out the TV signal completely. But the first time I encountered TETRA interference the symptoms were much less dramatic. There was slight cross-modulation, and some rather vague patterning on the screen. At first I wondered whether the masthead amplifier had some weird fault. When I connected the aerial lead to the spectrum analyser I saw, as expected, a huge spike some way below the UHF TV band. Thinking that the amplifier was oscillating, I disconnected its power supply as a check. This should kill any such oscillation of course. But to my surprise the spike, though greatly reduced, was still present. When a small screwdriver was used as the aerial the spike was very tall. I climbed on to the roof and soon found that the signal, at 392MHz, came from the direction of an innocuous-

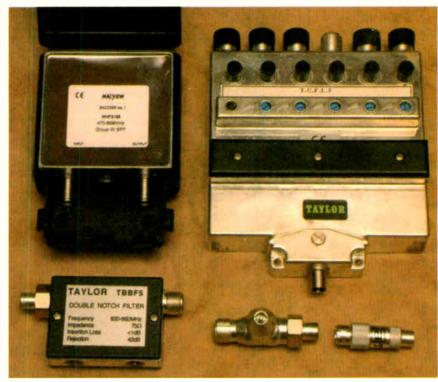


Photo 2: Various types of filter. Clockwise from the top left bandpass, channel-pass/leveller, high-pass, single-notch and double-notch.

looking callphone mast about 3km away.

A two-stage masthead amplifier is much more likely to be affected than a single-stage one. Two-stage amplifiers have a gain of about 25dB, single-stage ones about 14dB. Quite often the extra gain provided by a two-stage amplifier is unnecessary, and the only thing you need to do to get rid of the interference is to fit a single-stage one instead. The rule-of-thumb I use for assessing whether a two-stage masthead amplifier is required is simple. Assuming that the downlead losses are less than 3dB, I would consider the use of a two-stage amplifier only when the weakest analogue channels are below -8dBmV ($52dB\mu V$) at the aerial terminals.

If TETRA or other signals below the UHF TV spectrum are causing problems, it's best to use a UHF-only masthead amplifier. These incorporate a high-pass filter that can provide a good degree of protection against interference at 400MHz.

It's also important to use a fully-screened masthead amplifier. Most if not all the major manufacturers now have fully-screened products available. Some of the more 'vintage' masthead amplifiers are poor performers by modern standards, and are very susceptible to strong out-of-band or in-band interference. Maximum output levels are often rather low, which means that the cross-modulation threshold is easily exceeded by unwanted transmissions.

Filters

Having sorted out the masthead amplifier, if there is one, the next thing you have to consider when faced with strong out-of-band interference is the use of filters. Fortunately lots of these are available. Four basic types are relevant: bandpass, channel-pass/leveller, notch (single or double) and high-pass – see Photo 2.

A bandpass filter passes only the specified frequency range. A high-pass filter rejects everything blow its cut-off frequency. A notch filter rejects a spot frequency. A channel-pass filter passes only the channels specified. There are pros and cons with each type, but whichever type is used it must normally be inserted before the first amplifier in the system. All filters lose a little bit of the wanted signal as well, and with the filter in front of the masthead amplifier the carrier-to-noise ratio will inevitably be degraded, if only slightly. This is unavoidable, but in a marginal reception area it's a good reason for not fitting a filter if this can be avoided. In a difficult case where it's felt that the slight loss before amplification introduced by the filter is unacceptable, it might be possible to use a low-gain amplifier before the filter. Further amplification to overcome cable or distribution losses can follow the filter.

In many cases a bandpass filter will do the trick, with no further complications. They are also known as 'group-pass filters'. Since the filter will normally be before the masthead amplifier it will usually be outdoors, so it must be built into a weatherproof housing. Fringe and Maxview amongst others have such filters. The Maxview MHF range is fully-screened and has F connectors. It includes types for channels 21-37, 21-42, 21-68, 35-53, 35-68 and 48-68. To reject TETRA at 400MHz, use the filter designed for the highest possible group of channels. Through loss with the wanted channels is less than 1dB while the rejection at 400MHz is better than 25dB.

High-pass filters are most familiar to us as in-line CB filters. Examples are the Antiference TVI and TVI-U. These filters' cut-off frequency is generally not high enough to reject TETRA signals.

Notch filters come into their own when a distribution system carries VHF-FM and DAB radio as well as TV. A notch filter tuned to the exact TETRA frequency should be fitted in-line with each aerial feed prior to the amplifiers. Aerials for DAB can receive a lot of TETRA signal, but fortunately a double-notch filter can provide very high rejection – as much as 40dB is possible. Accurate tuning is difficult without a spectrum analyser.

Taylor Bros (Oldham) can supply notch filters for any frequency. Alternatively bandpass filters are available from Taylor Bros for VHF-FM (type TBP2) and DAB (type TBP3). These are indoor units which are intended to be fitted just in front of the distribution amplifier. In the unlikely event that a masthead amplifier is used for VHF-FM or DAB, the filter can be fitted into a standard ABS electrical junction box. A 120 x 180 x 50mm box with a rubber seal on the lid is ideal.

It is unlikely that you would need to resort to channelpass filters with a simple domestic installation. On the other hand the majority of distribution systems would benefit from having such a filter at the aerial input, even when out-of-band interference isn't a problem. But if the aerial receives TETRA or any other unwanted signal at significant strength a channel-pass filter/leveller is a must. By 'significant strength' I mean about 6dB lower than the digital TV multiplexes. Since TETRA often appears at the aerial terminals at higher strength than even the analogue TV channels, it is very likely in areas with TETRA coverage that a distribution system will need a channel-pass filter/leveller. We now take this for granted, the only exceptions being small systems with twenty or fewer outlets in places where the TV signals are very strong, at about 20dBmV or more. Filters for five analogue channels and six digital multiplexes can cost as much as £150. Believe me, we wouldn't use them if there was a cheaper alternative that works as well.

Aerial work

Don't start adding filters and changing masthead

amplifiers without giving the aerial a cursory glance at the very least. A bit of aerial work can pay dividends both technically and financially, the latter because customers seem to see more value in shiny things on the chimney than in boxes in the loft or your time.

The fundamental requirement is to improve the ratio between the wanted and unwanted transmissions as much as possible. First I'll state the obvious: the aerial should be pointed at the TV transmitter accurately, and should be sited as advantageously as possible. If raising the aerial or moving it to another chimney gives better line-of-site to the transmitter without improving the view towards the TETRA mast, it's worth doing the work. Apart from alleviating the TETRA problem, there will be a general improvement in reception. Don't waste your time putting the aerial off-beam from the transmitter in the hope of 'nulling out' the interference: it doesn't work.

TV aerials designed to work right down to the bottom of the UHF TV spectrum (470MHz) seem to function surprising well at 400MHz, even exhibiting directional properties and gain! If possible, avoid the use of wideband aerials. These are often installed unnecessarily nowadays, thanks largely to a widespread misconception that they are always needed for DTT reception. If all the analogue and digital TV signals required are in group B or C/D, the low-frequency response of a wideband aerial merely contributes to troublesome interference such as that from TETRA. The inferior performance of a wideband in comparison with a grouped aerial can also make a difference.

As a desperate last resort, it might be possible improve the signal-to-interference ratio by relocating the TV aerial to a spot that's screened from the TETRA mast. Unfortunately 400MHz signals aren't attenuated by buildings and trees as much as UHF TV ones, so this might not be all that effective.

Most VHF-FM aerials have to be installed horizontally, which helps avoid TETRA interference. Unfortunately DAB aerials have to be installed vertically.

In conclusion

The electromagnetic spectrum has become ever more crowded over the years. During my time as an aerial installer I have seen all sorts of innovations that have caused UHF TV reception problems. In the late Seventies and early Eighties there was the CB craze. Then we had the illegal high-powered cordless phones. Meanwhile many of the CB fanatics migrated to amateur radio and started to transmit lots of watts at 144MHz and 432MHz, usually in the middle of crowded housing estates. Next illegal video senders became popular – I could write a book about the trouble they caused. Low-powered RSL radio stations have sprung up all over in recent years, cellphone masts adorn every bit of high ground, and we now have five analogue channels and six digital multiplexes competing for space in the UHF TV spectrum, with the old channel-spacing rules thrown to the winds. No wonder we have interference problems!

We must remember though that the majority of these problems are not caused by the interfering transmitter but are the result of poor EMC (electromagnetic compatibility) at the receiving end. Poor amplifier design, the wrong type of amplifier, cheap coaxial cable, poor TV set design and an inadequate aerial installation can all open the door to interference.

Ensuring good EMC performance has become an important part of installers' work over the years. TETRA is just the latest challenge. I'm sure it won't be the last!

distributor of electronic components

Specials Offers and New Arrivals!!

High Quality Fully Shielded Foil Wrapped Scart Lead

Length: 1.5m Width: 12mm

Box of 25

Price: £ 30.00 + vat

Box of 50

Price: £ 50.00 + vat

Order Code: PLG26

Fully Shielded 21 Pin Connected Scart Lead

Length: 1.5m Width: 8mm

Box of 50

Price: £ 30.00 + vat

Box of 100

Price: £ 55.00 + vat

Order Code: PLG23

2 Phono to 2 Phono Cable

Length: 1.2m

Box of 25

Price: £ 12.50 + vat

Box of 50

Price: £ 20.00 + vat

Coax Fly Lead Plug to Socket

Length: 2m

Box of 50

Price : £ 15.00 + vat

Box of 100

Price: £ 25.00 + vat

Order Code: COXCABLE

Scart Plug to Scart Sockets 5 way splitter

Length: 0.4m

Box of 10

Price: £ 20.00 + vat

Order Code: PLG44

Order Code: PLG33 Switched Scart to

3 Phono and S-Video Sockets

Box of 10

Price: £ 10.00 + vat

Box of 20

Price: £ 17.00 + vat

Order Code: PLG85

New Arrival!!

Jaeger 2003 / 2004 Semiconductor Comparison Book

This A5 sized book contains vital information on 41,400 types of components.

Transistors , Diodes , Thyristors , IC's all covered with details of :

Design

Brief data / description Construction type...etc

Order Code: BOOK04
Price: £ 23.00 - No VAT
(plus £ 2.00 + vat for Postage)

Aerial Installation Accessories

SLx Aerial Amplifiers

Now with built in Digital ByPass Operates with Sky™ DigiEye

Class leading noise figure of 4dB or less

6dB signal amplification on all models

		-
Description	Order Code	Price
2 Way - No Bypass	SLX2	£ 8.00 + vat
2 Way - With Bypass	SLX2B	£ 9.25 + vat
4 Way - No Bypass	SLX4	£ 13.00 + vat
4 Way - With Bypass	SLX4B	£ 14.00 + vat
6 Way - No Bypass	SLX6	£ 18.00 + vat
6 Way - With Bypass	SLX6B	£ 19.00 + vat
8 Way - No Bypass	SLX8	£ 18.50 + vat
8 Way - With Bypass	SLX8B	£ 20.00 + vat

SLx Masthead Amplifiers UHF TV antenna pre amplifier designed for the professional aerial installer

15dB gain masthead amplifier ideal for majority of domestic installations

26dB gain masthead amplifier for longer cable runs (loss of more than 3dB) or if

Requires 12V DC power supply via downlead either via dedicated power supply unit or from a distribution amplifier with line powering

connected to passive splitters

15dB Amp Order Code: 27830R Price: £ 4.30 + vat

26dB Amp Order Code: 27831R Price: £ 4.50 + vat

> SLx Masthead Amp PSU Order Code: 27832R Price: £ 5.00 + vat

Postage for 2+ £ 5.00 + vat

Coax Plug Aluminium



Order Code : PLG51 Bag of 10 Price : £ 1.25 + vat

Price: £ 1.25 + vat Bag of 100 Price: £ 9.00 + vat

Screw Type Coax Plugs



Order Code: PLG62 Bag of 10 Price: £ 1.60 + vat

Bag of 100 Price : £ 12.50 + vat

Twist On F Connectors



Order Code: PLG101

Bag of 10

Price: £ 1.00 + vat

Bag of 100 Price : £ 6.00 + vat

Coax Coupler Socket to Socket



Order Code PLG54

Bag of 10 Price: £1.50 + vat Coax Coupler
Plug to Plug



Order Code PLG55

Bag of 10 Price: £1.50 + vat Y Splitter Inductive 3 way



Order Code YSPLITTER Price: 40p + vat

Bag of 10 Price: £ 3.00 + vat

K.P. House , Unit 15 , Pop In Commercial Centre , Southway , Wembley , Middlesex . HA9 0HB England

Tel: (020) 8900 2329

Fax: (020) 8903 6126

Email: sales@grandata.co.uk

distributor of electronic components

Digital Satelitte Accessories

Sky™ Digital

Remote Controls

Sky™Digital Remote & TV Link Eye Combination



Order Code: SKYPACK1

Price: £ 16.00 + vat each

5 +

£ 14.50 + vat each

Order Code: RCSKY

£ 7.95 + vat

£ 7.45 + vat each

each 10 +

£ 6.95 + vat each

Sky™Digital Remote & SLx Link Eye Combination





Order Code: SKYPACK2

Price: £ 13.00 + vat each

5 +

£ 11.50 + vat each

SLx Link Eye
Allows control of Sky™ Digibox via the signal feed for second TV

Order Code: 27833R

1 - 9 £ 6.50 + vat each

10 - 24 £ 5.50 + vat each

Sky™ Digital TV Link Eye

Order Code: TVLINKEYE

Price

£ 10.75 + vat

5 + £ 7.99 + vat each

£ 6.99 + vat each

SLx Amp By Pass Kit

For use with aerial amplifiers and Sky™ Digibox

Allows for operation of Link Eye in conjunction with a distribution amplifier



Order Code: 27829R Price: £ 5.00 + vat

Satellite Repair / Mod Kits

Amstrad DRX100

Tuner Repair Kit

Order Code

SATKIT35

Price £ 1.40 + vat

Power Supply Reliabilty Kit

Order Code SATKIT36

Price £ 12.00 + vat

Amstrad DRX100 Amstrad DRX100

Power Supply Repair Kit

Order Code SATKIT37

Price £ 13.50 + vat

Grundig GDS200

Digital Satellite Receiver Repair Kit

Early psu MODEL : DS0 - 0385 REV C

Price: £ 10.00 + vat

Grundig GDS200/300

Digital Satellite Receiver Repair Kit

> LATER psu TYPE REV 03 DSO - 0375 REV A DSO - 0385 REV 5

Order Code: SATKIT34A Order Code: SATKIT34B Price: £ 10.00 + vat

Digital Satellite Receivers Fan Kit

Suitable for

Amstrad DRX100, DRX200 Grundig GDR200, GDS200 Pace Digibox

plus many more analogue makes and models

Order Code: FANKIT1 Price: £ 10.00 + vat

Panasonic Digital Satellie Receiver Fan Kit

Suitable for Panasonic TU-DSB20/30, TU-DSB31/35

Order Code: FANKIT2 Price: £ 15.00 + vat



Grundig Digital Satelitte ReceiversReliability Kit

These kits contain capactiors that are generally of higher specification than those fiited by the manufacturers.

New **Arrivals**!!

GDS200

Early PSU DSO0385 Rev C

Kit Contains 9 capactitors

Code: RELKIT34A Price: £ 4.00 + vat

GDS200 / GDS300

Later PSU DSO0375 Rev A DSO0385 Rev F Kit Contains 11 capactitors

Code: RELKIT34B Price: £ 4.00 + vat

GDS200 / GDS300

Later PSU Rev₀₃

Kit Contains 13 capactitors

Code: RELKIT34C Price: £ 4.00 + vat

GDS200 / GDS300

Samsung PSU PSSH370601B

Kit Contains 12 capactitors

Code: RELKIT34D Price: £ 4.00 + vat

GDS300

Samsung PSU PSSH370603B

Kit Contains 13 capactitors

Code: RELKIT34E Price: £ 4.00 + vat

Grandata

distributor of electronic components

Television Re its

	KIT TYPE	C	ODE	
& MODEL				& MOD
	ALBA			G
1452T	PSU	ON\	WAKIT	2029T
1427T	PSU	ON\	VAKIT	2029TA
1402	PSU	ON\	NAKIT	F16 CH/
	PSU			F16 CH/
	PSU			F16
	PSU			F16
	PSU			
	STANDBY			
	PSU			CUC 73
	PSU			CUC 730
	PSU			(BUZ90)
2152T	PSU	ON\	WAKIT	CUC 730
	STANDBY			(MJF180
	STANDBY			
	PSU			
	PSU			HIT14RO
	PSU			
	PSU			
CTV485	PSU	ON\	WAKIT	AV29SX
				AV29SX
	AKAI			AV29SX
	PSU			AV29SX
	PSU			AV29TS
	PSU			C14E1E
CT2863UNT	PSU	ON\	WAKIT	C14T1E
				C21ET1
DE	CCA/TAT	UNG		CS21M3
TVC563	STANDBY	MOD	KIT37	
	GOLDSTA	R		1455
	FRAME		KIT36	1498
	FRAME			2086
	FRAME			2098
	FRAME			21V1N (
	FRAME			21V1T(N
	FRAME			TVR180
				1
	OODMAI			
	PSU			AV1 SEF
	PSU			CT1M5B
	PSU			CT21M5
	PSU			CT25M5
	PSU			CT21A2
	PSU			CT21AX
	PSU			CT21A3
2019R	PSU	. ON		
ORDER	CODE PRI	CE	ORD	ER COL
CRUMPIC	KIT1£ 10	0.60	MITS	KIT3
		181		KIT35
	KIT2£ 10			KIT36
				KIT37
GRUNDIG	KIT3£ 10			

10101		JII IXE
MAKE	CIT TYPE	CODE
& MODEL		
GOODS	ZANC	Continued
2029T		
2029TA		
F16 CHASSIS		
F16 CHASSIS		
F16		
F16		
	RUND	
CUC 7350		GRUNDIGKIT1
CUC 7301/3 (BUZ90)		
(BUZ90)	PSU	GRUNDIGKIT2
CUC 7301/3		
(MJF18004)	PSU	GRUNDIGKIT3
	<u>HINAR</u>	
HIT14RC	PSU	ONWAKIT
	JVC	
AV29SX1EK		JVCKIT1
AV29SX1EN		JVCKIT1
AV29SX1EN1I		JVCKIT1
AV29SX*PF		JVCKIT1
AV29TSIE1I C14E1EK		JVCKIT1
C14E1EK		
C21ET1EK		
CS21M3EK		
0021110211111111		
	MATSL	JI
1455		
1498		
2086	PSU	ONWAKIT
2098	PSU	ONWAKIT
21V1N (BUZ90)		
21V1T(MJF18004)		
TVR180R/T/2080	STANDBY	MODKIT37
		0111
	<u>rsubi</u>	
AV1 SERIES		
CT1M5B CT21M5BT		
CT25M5BT		
CT21A2STX1		
CT21AX1B		
CT21A3STX1		

	Mod	
MAKE & MODEL	KIT TYPE	CODE
MITS	UBISHIc	ontinued
	PSU	
CT25A2STX .	TDA 8178S	MITSKIT1
	TDA 8178S	
	TDA 8178S	
	TDA 8178S	
	PSU	
CT28AV1BDS	PSU	MITSKIT3
CT29AS1	TDA 8178S	MITSKIT2
	TDA 8178S	
	TDA 8178S	
CT29B2	KIT TYPE	MITSKIT2
& MODEL	W	0022
	TDA 8178S	
	TDA 8178S	
	TDA 8178S PSU	
MS SERIES	PSU	MITSKIT3
II .	EI/NIKK	A I
	SPSU	
	PSU	
	PSU	
P	ANASON	C
	TDA 8175	
TX25XD60	VERT OUTPUT	PANKIT2
		PANKIT2
		PANKIT2
		PANKIT2
TX-W26D3	.VERT OUTPUT	PANKIT2
	PHILIPS	
310.10708		PHILKIT3

PANKIT2 PANKIT2 PANKIT2 PANKIT2 PANKIT2	59DS03H
PHILKIT3 PHILKIT10 PHILKIT10 PHILKIT6 PHILKIT5 PHILKIT4 PHILKIT9 PHILKIT7	35065920

MAKE & MODEL

310.32262

310.62264

ANUBIS A

CP110 CHASSIS

G90A CHASSIS

G90B CHASSIS

G110 CHASSIS

GR2.1 CHASSIS

GR2.2 CHASSIS

D-16 CHASSIS

HSM VIDEO

JSM VIDEO

KSM VIDEO

LSM VIDEO

CI5944

CI6844

VIK310

VIK320

VIK350

VI375.

VI395.

WINNER 1

51CS03H

51CS05H

59CS05H

59CSD8H

ORDER CODE PRICE
GRUNDIGKIT1 £ 10.50 GRUNDIGKIT2 £ 10.50 GRUNDIGKIT3 £ 10.50 GOODKIT1 £ 11.00 JVCKIT1 £ 11.00 MITSKIT1 £ 3.00 MITSKIT2 £ 15.00

ORDER CODE	PRICE
MITSKIT3	£ 6.00 £ 9.50 £ 5.00 £ 6.50 £ 12.00
PANKIT1	£ 15.00

ORDER ÇODE	PRICE
PANKIT2 PHILKIT1 PHILKIT10 PHILKIT2 PHILKIT3	£ 9.00 £ 7.60 £ 8.50 £ 2.50
PHILKIT4	£ 4,25
PHILKIT5	£ 5.75

310.20491

310.20496

310.31994

310.32252

310.32253

310.32254

310.32255

ORDER CODE	PRICE
PHILKIT6	c 5 50
PHILKIT7	
PHILKIT8	
PHILKIT9	£ 7.50
SAMKIT2	£ 8.00
SAMSUNGKIT	£ 16.00
SHARPKIT1	£ 11.00

ORDER CODE	PRICE
SHARPKIT2	£ 11.00
SHARPKIT3	£ 9.00
THOMKIT1	£ 7.00
THOMKIT2	£ 12.00
THOMKIT3	£ 9.00
THOMKIT4	£ 4.00
THORNKIT1	£ 12.75

CODE

PHILKIT8

PHILKIT1

.PHILKIT2

PHILKITS

PHILKIT10

PHILKIT10

PHILKIT3

.PHILKIT1

.PHILKIT1

PHILKIT6

PHILKIT5

PHILKIT4

PHILKIT9

PHILKIT7

SAMKIT2

SAMKIT2

SAMSUNGKIT

SAMSLINGKIT

.SAMSUNGKIT

.SAMSUNGKIT

SAMSUNGKIT

SAMSUNGKIT

SHARPKIT1

SHARPKIT1 SHARPKIT2

SHARPKIT2

SHARPKIT2

SHARPKIT3

SHARPKIT2

SHARPKIT2

SHARPKIT2

.THOMKIT2 THORNKIT1 .THORNKIT1

..THOMKIT1

.THOMKIT3 THOMKIT1

THOMKIT3

.THOMKIT4

THOMKIT2 THOMKIT2

THOMKIT4

PHILIPS...Continued

SOPS

SOPS

SOPS

SOPS

SOPS

SOPS.

SOPS.

SOPS

SOPS

SOPS

SOPS

FRAME

PSU

PSU

PSU

.PSU

.PSU

SHARP

.PSU

.PSU

.PSU

SAMSUNG

Repair Kits - New Arrivals!!

Matsui

1496R/T and 2096R/T Repair Kit for Power Supply using a BUZ90

Order Code MODKIT43

Price £ 7.00 + vat

Matsui

1496R/T and 2096R/T Repair Kit for Power Supply using a H3N90

Order Code MODKIT44

Price £ 7.00 + vat

Sharp

56FW53H,66FW53H, 66FW54H.76FW53H. 76FW54H PSU & Dolby Upgrade

Order Code MODKIT45

Price £ 4.00 + vat

Sony VCR

SLV715HB SLV777UB Repair Kit for Power Supply

Order Code MODKIT40 Price

£ 6.00 + vat

Thomson

ICC17 Power Supply Repair Kit

Order Code MODKIT41 **Price** £ 6.00 + vat

distributor of electronic components



Konig Remote Controls



The color	ELECTRON	AIC			KOIII	9 1	CHIOL			0			ELECT	IONIC
Company	Part No.	Code	Part No.	Code	Part No.	Code	Part No.	Code	Part No.	Code	Part No.	Code	Part No.	Code
Company		-			HITACHI conti	nued		-						
Column									RC9020					1R9953
March Marc	CT2885	IR9700	A14R	IR9259	C2546	IR9677	C1	IR9161	RC9050	IR9556	RRMCG0777PESA	IR9487	1480TBT	IR9953
AMSTON BOOK 1.0000 CONTROL MATER 1.0000 CONTROL MAT	IR16	IR9700	B51F	IR9639	C2547TN	IR9677		IR9161	RC9060	IR9556	RRMCG0898CESA	IR9487	1480TBY	IR9953
March Marc										IR9434				IR995
Section Process Proc	NG65		B59N	IR9639	C2567TN	IR9983	D1	IR9161	1	1K97 10	RRMCG1031BM5A	IR9788	1510RDT	IR9962
Section Color Co	SRD550	189386							SAMSUNG CX5312W	IR9432	RRMCG1036BM5A			IR996
March 10 1964 1965 1966 196	SRX510	IR9386	B68NX	IR9639	C2659H	IR9142	E2	IR9161	CX5325W	IR9432	RRMCG1048BM5A	IR9788	155R9BT	IR9962
BALO SEAD	AE6001	IR9352						IR9700						IR996
MAND 1958	B&O		D51ND	IR9639	C2846TN	IR9677	FS10	IR9573	RM104	IR9432	SV2044G	IR9487	156R9	IR9962
SECON 1982	Beolink 100	IR9843	D59F						RM109	IR9546				IR996
March Marc			D68N	IR9639	C2866TN	IR9677	FS4/2	IR9573	SANYO		SV2145S	IR9487	156R9BW	IR9962
Red	RC51331													IR996
MATERIAL	RC61331	IR9398		IR9639							SV2877S			IR985
1922 1920		- 1	RCU1742	IR9584	CBP1646R	IR9142	RC1	IR9157	JXFF	IR9457	100	111(9407	2100RBG	IR9962
1925 - 1. 1925 1925												ID0074		IR996
March Marc	1570-46	IR9516	RH880	IR9594	CBP222	IR9142	IRS1	IR9535	JXGT	IR9460	RM607	IR9974	2102RBZ	IR996
March Marc				IR9325		IR9142								IR9962
1866	1555-46	IR9516	RHT10	IR9639	CL2156TAN	IR9983	RCN610	IR9752	JXLB	IR9460	RM620	IR9511	2140RB	IR9852
Color														tR985
MACH	IC16	IR9504	T49N	IR9639	CL2586TAN	IR9983	SM1	IR9491	RC254	IR9974	RM631	IR9511	2145DB	IR985
MOST MOST STORE MOST							SM2	IR9491						
Michael Mich	IM32	IR9503	T59F	IR9639	CL28W1TAN	IR9983			RC307	IR9457	RM634	IR9511	2152DB	IR995
MITO 16						IR9983								IR995
1.016 1.056.0 1.056.						IR9602	EUR50100	IR9826		IR9457				IR995
1872 1870	IQ16	IR9504		IR9584	CLE874A	IR9602	EUR51921	IR9835		IR9457	RM650	IR9336	216R9B	IR995
TOTAL MEANS MEAN						IR9602		IR9826						IR996
Telescope Tele		IR9248	176UPL	1K9039	CLE876C	IR9477		IR9834						IR995
1500 1500			GOLDSTAR	100403										IR985
Carrier Carr	TC190	IR9529	105209B	IR9862	CLE902A	IR9677	TC1785DRS	IR9826	RC700	IR9139	RM658	IR9321	219R	IR996
CROWN R5839 155-224V R5854 CLE 274 R5856 R5857 R5856 R5857 R5856 R5857 R5856 R5857 R5856 R5857 R5856 R5857 R5856 R5856 R5857 R5856 R5856 R5857 R5856 R5856 R5857 R5856														
R65131 R9390 10520A R9880 CLECA R9862 TC2181C R9865 R9440 R9			105-224V	.IR9854	CLE921A	IR9983	TC2185DRS	IR9826	RC711	IR9460	RM671	IR9123	2522DB	IR9953
ROS 105-200	RC51331	IR9398												IR9950
Case	RC61331	IR9398	105-230C		CLE922B	IR9982	TC21R1U	fR9826	S03		RM677	IR9448	2535DB	IR9852
DMC1414 R3937 C874902 R39403 C7294FTA R3967 TNOSECU2 R3968 S1AM12S R3968 R3944 Z55076 R3940 R39401		1K9397	CB20E40X	IR95 ,4	CP2146TA	IR9677	TCC23PFR	IR9826		- 9	RM682	IR9442	2537DD	IR9852
DMC DMC DMC DMC DMC DMC DMC DMC	DAEWOO	IP0307												IR9852
DMZ2915 IR9840 VS668K	DMQ14A 1	IR9840	CBT4902E	IR9403	CP2556TAN	IR9983	TNQ8E0422	IR9826	51AT15S	IR9788	RM685	IR9442	2550TB	IR9953
DMC2955 IR9840 PR9540 CRUMDIG CRUMDIG CP286TAM R9693 TNOSE0432 IR9860 S4C50SSN IR9711 Nav697C IR9469 IR9441 25550B IR9460 CP286TAM IR9693 TNOSE0432 IR9660 IR9442 R9467 Nav6960 IR9441 CP280TAM IR9693 CP286TAM IR9693 TNOSE0434 IR9460 IR9442 R9467 Nav6960 IR9442 S550B IR9460														IR9950
PROPRIES CLCS20	DMQ2595	IR9840			CP2856TAN	IR9983	TNQ8E0432	IR9826	54CS05SN	IR9711	RM687C	IR9448	2555	IR9953
2015 R8954 CUC\$301 R9526 CPT1557 R8576 TX158TT R9584 R9576 TX158TT R9584 R9586 TX158TT R9586 TX158TT R9586 R9586 TX158TT R9586 TX158TT R9586 TX158TT R9586 TX158TT R9586 TX158TT R9586 TX158TT R95	DMQ2895	1K9840	CUC503		CP28WD2TAN	IR9983	TNQ8E0436	IR9836	5V2145	IR9487	RM694			IR995:
2285		IR9594				IR9983								IR995
2415 R8584 R6212 R8614 CPT1561 R8676 TZ4STT R8634 C2021 R8467 R8467 R8640 Z5708 I R8467 R8670 R8	2285	.IR9584	CUC5302	IR9529	CPT1557	IR9576	TX14S1T	IR9834	72CS05SN	IR9711	RM719	. IR9448	2563DD	IR9953
2422 R8954 RC300								IR9834						IR995
2433 Ri9584 TP550VT Ri9590 CP72555 Ri9575 TZ5A2C Ri936 CV3709 Ri9467 Ri9482 Ri9452 2850B II 2453 Ri9584 TP560VT Ri9509 CP72556 Ri9575 TZ5A2C Ri9436 CV3709 Ri9467 Ri9487 Ri9431 Ri9434 28370D II 2453 Ri9584 TP560 Ri9599 CP72556 Ri9575 TZ5A2C Ri9436 CV3709 Ri9467 Ri9431 Ri9443 28370D II 2463 Ri9584 TP560 Ri9599 CP7275 Ri9575 TZ5A2C Ri9436 CV3708 Ri9467 Ri9431 Ri9443 28370D II 2475 Ri9594 TP560 Ri9599 CP72770 Ri9575 TZ5A2C Ri94836 CV3708 Ri9467 Ri9483 Ri9484 Ze5570B II 2512 Ri9594 TP560 Ri9596 CS71430 Ri9576 TZ5A2C Ri9586 CV3709 Ri9467 Ri9487 Ri9433 Ri9484 Ze5570B II 2413 Ri9594 TP560 Ri9696 CS71430 Ri9576 TZ5A2C Ri9836 CV3709 Ri9467 Ri9487 Ri9483 Ri9484 Ze5570B II 2414 Ri9594 TP560 Ri9696 CS71430 Ri9576 TZ5A2C Ri9836 CV3709 Ri9487 Ri9487	2422	IR9584	RC300	IR9614	CPT2155	IR9575	TX21S1TC	IR9834	CV2121	1R9487	RM820	IR9452	2579DB	IR9953
2452 R19584 TP610						IR9575	TX2111C							IR9953
2453 IR-9564 TF-921 IR-9299 CPT2669 IR-9575 TYZ5WZC IR-9365 DV1416SN IR-9467 RM322 IR-943 Z6550D II							TX25A2CI	IR9836		IR9487		IR9443		IR9852
2475 R8554 TP650 R8509 CP7270 R8575 TX28A210 R8936 DV7106SN R9447 R8451 R8452 25570D II 29132 R8564 TP661 TOP R8615 CS71430 R8576 TX28A2C R8936 DV2108TS R8711 R8451 R8576 R8451 R8576 TX28A2C R8936 DV2108TS R8711 R8451 R8576 R8451 R8576 TX28A2C R8936 DV2108TS R8451 R8451 R8561 R8576 TX28A2C R8936 DV2108TS R8451 R8451 R8561 R8562 R8562 TP711 R8552 CT2116 R8451 TV20W2C R8936 DV2507TS R8711 R8451 R8562 TP712 R8561 R8576 TV20W2C R8936 DV2507TS R8711 R8452 R8562 TP712 TR512 TR512	2453	IR9584	TP621	IR9299	CPT2669	IR9575	TX25W2C	IR9836	DV1416SN	IR9487	RM832	IR9443	2853DD	IR9953
29132 198564 TP661				IR9509										IR995
Sect	26H3	IR9594	TP661	IR9562	CST1430	IR9576	TX28A2C	IR9836	DV21081S	IR9711	RM836	IR9871	2857DD	IR995
1413 R9594 TP710 R9529 TP712 R9541 TP712 R9541 TP712 R9541 TP712 R9541 TP712 R9541 TP712 R9541 TP715 R9749 TP715					CST1435	IR9576								IR995
4414 R9584 TP712 R9614 R9574 TP715 R9749 R974 TP715 R9749 R9749 TP715 R9749 R9741 TP720 R9614 AV25TS1EN R9688 TP716 R9749 AV25TS1EN R9688 TP716 R9749 AV25WMEN R9688 TP717 R9749 AV25WMEN R9698 TP717 R9698 TP717 TP717 R9749 AV25WMEN R9698 TP717 TP717 R9698 TP717 TP	41H3	1R9594	TP710	IR9529	CT2116	IR9476	TX28W2C	IR9836	DV25073S	IR9711	RN 841	IR9452	2873DB	IR995:
4415	4414	IR9584	TP712	IR9614		IK9542	TX29AD1D	IR9835	DV25083S	IR9711	M883	IR9871	2879DB	IR995;
1433 R8584 TP770 R8614 M2ZSTSIEN R8689 TR33A2CI R8868 TP777 R8749 AZZWIEN R8689 TP777 R8749 AZZWIEN R8689 RC5020 R9510 DV3750S R87818 14GZ1D570 R8639 3357DB JF780 R8689 RC5020 R8610 DV3750S R8788 14GM55 R8639 R86590 R8749 AZZWIEN R8698 RC5020 R8610 DV3750S R8788 14GM55 R8639 R86590 R8749 AZZWIEN R8698 RC5020 R8610 DV3750S R8788 14GM55 R8639 R8659 R8660					AV21TS1EN	IBOSOS		IR9836	DV28037S	IR9711			3327DB	IR995
51A2 R9584 TP770 R9749 AV25VM1EN R9689 R5002 R9510 DV360S R9741 14G21570 R9639 33770B II 15A3 R9584 TP7800 R9749 AV295X1EN R9698 R5514 R9596	4433	.IR9584	TP760HIFI	IR9614	AV25TS1EN	IR9698	TX33A2CI		DV28081S	IR9711	THOMSON		3357DB	IR995:
51AA IR9584 TP800 IR9749 AV29SX1EN IR9698 RC5140 IR9510 DV3760S IR9788 14GM56 IR9639 3787DB J. 1		IR9584			AV25VM1EN		RC5002	.JR9510			14G21D570			IR9953
Formal F	51A3	IR9584	TP800	IR9749	AV29SX1EN	IR9698	RC5140	IR9510	DV3760S	IR9788	14GM56	IR9639	3787DB	IR995
1616 2 R9594 TRC2 R9715 R626072 R9696 R625260 R9510 DV54325 R9711 221MG51 R9696 48P16DG J.	61A5	IR9584	TRC1	IR9715		IR9698	RC5240	IR9510	DV5403S	IR9711				IR9953
Section Sect	51G2	IR9594			RC8072	IR9698	RC5250	IR9510	DV5432S	IR9711	21MG51	IR9639	48PJ6DG	IR995
14	51H3	IR9594	HITACHI		RMC530	IR9698	RC5300	IR9510	DV5470S	IR9711	RCT2000	IR9259	56PW8DB	IR995
18 18 18 18 18 18 18 18			2970491					IR9510	DV5935H	IR9711	RCT3000	IR9831	7037DD	IR985
1982 1985	51K3	. IR9594	C1405	IR9476	RMC7611E	IR9698	RC5420	IR9553	DV6303S	IR9711	RCT5020	IR9502	CT6869	IR995
1983 18984		.IR9584 IR9584									RCT5141S	IR9470		IR996
1995 1995 1996	59B3	IR9584	C2067	IR9142	RMC7711E	IR9698	RC5801	IR9553	DV6332S	IR9711	TOSHIBA	(Doors	CT9387	IR996
1992 189584 C2146TM 189677 1400RB 189542 C71414 175903 189584 C2147TM 189677 1400RB 189584 C2147TM 189677 1400RB 189584 C215TM 189681 189584 C215TM 189983 FB300 189618 180684 189465 DV70018 189711 1400RB 189962 C719432 189584 C2156TM 189983 FB300 189618 180684 189465 DV70018 189711 1400RB 189962 C719455 189484 189594 C2170TM 189983 1852 189514 180684 189484 DV70032 189711 1400RB 189962 C719475 189594 C2170TM 189983 1870 189514 1806804 189434 DV70032 189711 1400RB 189962 C719475 189594 C225TM 189184 189594 189	59B5	IR9584	C2114	IR9476			RC5901	IR9556	DV7001S	IR9711	1400R	.IR9962	CT9399	IR996
5962 189594 C2156TN			C2146TN	IR9677			RC5903	IR9556	DV7002S	IR9711	1400RB	IR9962	CT9414	IR9962
1963 18954 C2166TN 189677 6850 189514 180616 189465 DV7024S 189711 1400RBT 189622 C79475 18 18954 1895	59G2	IR9594	C2156TN	JR9983	FB300		RC6404	IR9465	DV7011S	IR9711	1400RBN	IR9962	CT9455	IR996
5915 189594 C216TN 18983 FB70 189514 RC6804 189434 DV7036S 189711 1400RDT 189622 C79480 189514 RC7187 189594 C2257H 189142 FB72 189514 RC7181 189465 RRMCG0351CESA 189487 1440RB 189524 C79526 189524 RC7181 189465 RRMCG0351CESA 189487 1440RB 189524 C79526 189524 RC7181 189465 RRMCG0351CESA 189487 1440RB 189524 RC7181 RC7181 RC7181 RRMCG0351CESA RS487 1440RB RS852 C79526 189524 RC7181 RC7181 RRMCG0370CESA RS487 RRMCG0370CESA RS487 RS		IR9594	C2166TN							IR9711		IR9962	CT9475	IR996
59IS2 IR9639 C2259H IR9142 FB90 IR9514 RC7141 IR9465 RRNCG0351CESB IR9467 1440RBT IR9526 I 1490RD I 1490RD I 1490RD I	59H5	IR9594	C2186TN	IR9983	FB70	IR9514	RC6804	IR9434	DV7036S	IR9711	1400RDT	IR9962	CT9480	IR996
6223 IR9584 C2261 IR9142 F891 IR9514 RC7500. IR9464 RRMCG0351CESD IR9467 1440RD IR9467 I440RD IR9585 I79784 IF9785	59LS2	IR9639	C2259H	IR9142		IR9514						IR9852 IR9852		IR996
66B2 IR9584 C2268H IR9142 MATSUI RC7512 IR9864 RRMCG0483PESA IR9487 1440TBT IR9582 C79859 IF 66B3 IR9584 C2273 IR9142 076L067240 IR9490 RC7535 IR9864 RRMCG0489CESB IR9467 1450RB IR9852 C79859 IF 66H3 IR9594 C2273H IR9142 076L067240 IR9490 RC8201 IR9430 RRMCG0588PESA IR9487 450RD IR9852 C79867 IF 66H4 IR9594 C22W1TN IR9983 2076R IR9490 RC8205 IR9710 RRMCG0617PESA IR9487 1480RD IR9852 C79867 IF 66H4 IR9594 C24W1TN IR9983 2076R IR9490 RC8205 IR9710 RRMCG0617PESA IR9487 1480RD IR9852 C79867 IF	6223	.IR9584	C2261	IR9142		IR9514	RC7500	IR9464	RRMCG0351CESD	IR9487	1440RD	IR9852	CT9784	IR995
6683 IR9584 C2273 IR9142 076G047240 IR9490 RC7535 IR9864 RRMCG0489CESB IR9467 1450RB IR9852 C79867 IF 66H3 IR9594 C2273H IR9142 076G067240 IR9490 RC8201 IR9434 RRMCG0588PESA IR9467 1450RB IR9852 C79868 IF 66H4 IR9594 C24W1TN IR9893 2076R IR9490 RC8205 IR9710 RRMCG0617PESA IR9467 1480RB IR9852 C79900 IF	66B2	IR9584	C2268H	IR9142	MATSU		RC7512	IR9864	RRMCG0483PESA	IR9487	1440TBT	IR9852		IR995
66H4					076G047240				RRMCG0489CESB	IR9487	1450RB	IR9852	CT9867	IR9953
10000 IR9494 CZ4W5111N IR9983 Z92T IR9490 RC9010 IR9434 RRMCG0618PFSA IR9487 1480RRT IR9491 CT00A0 II	66H4	IR9594	C24W1TN	IR9983	2076R	IR9490	RC8205	IR9710	RRMCG0617PESA	IR9487	1480RB	IR9953	CT9900	IR9953
013943	66H5	IR9594	C24W511TN	.IR9983	2092T	.IR9490	RC9010	IR9434	RRMCG0618PESA	. IR9487	1480RBT	IR9953	CT9949	IR9953

Price: £ 6.50 + vat each

This is just a selection of Konig Remote Controls that we stock.

distributor of electronic components

Transistors / Linear IC's

Part No.	Price	Part No.	Price	Part No.	Price	Part No.	Price	Part No.	Price	Part No.	Price	Part No.	Price	Part No.	Price	Part No.	Price
BU208A	10 75	IRF5450	£5 00	MJE350	£0.80	STK4191		STK5464	£3 00	STR371	£4 00		10.00	1DA4665	£2 50	TDA8138	£2.00
BU2506DF	£0 90	IRF5740	£3.00	MJF		STK4191 X	£14 00	STK5466	£5 00	STR380	£3,50	TDA2460-2	£0.70	TDA4670	£4 75	TDA8138A	£1.30
BU2506DX BU2508A	£1.00	IRF5840	£0 80	MJF16206	£4.50	STK419-130 STK419-140	£15 00	STK5467	£4 00	STR381	£3.90	TDA2501	£8.00	TDA4671	£5 00 £3 50	TDA8138B	£2.00
BU2508AF	£1.00	IRF611	£1 20	MJF18004	£2.00	STK4192	£16 00	STK5471	£9.00	STR384	£3 50	TDA2507	£4.50	TDA4681	£4 50	TDA8140	£2.00
BU2508AX	£1 30	IRF620	£1 00	MJF 18008	£1.75	STK4197 II	£9 50	STK5472	£3.75	STR40090	£3.50	TDA2510	£4.50	TDA4685	£2 75	TDA8143	£1 60
BU2508D	£1 30	IRF630	£0 75	MJF18204 STK0025	£2 50 £4 20	STK4199 II STK4199II	£10 50	STK5473	£4.80	STR40115 STR4090A	£6 00 £6 50	TDA2514A TDA2515	. £5 00 . £4 50	TDA4686	£5 00	TDA8145	£1.20
BU2508DX	£1 50	IRF640	£1 50	TK0039	£6 00	STK420	£4 00	STK5476	£3.50	STR41090	£3.30	TDA2520-1	£9 00	TDA4700A	£7 50	TDA8153	£10.00
BU2520AF	£1 70	IRF640F	£2 00	15TK086	£10.00	STK4204 II		STK5477	£4.50	STR4142	£4 50	TDA2521	. £8 00	TDA4710H	£7 00	TDA8170	£1 70
BU2520AX BU2520DF	£2 25	IRF630S	. £2.00	TK1040	£4 60	STK4204II	£10 50	STK5478	£2 50	STR4211	£3 15	TDA2522 TDA2523	£12 00	TDA4714C	£3 50	TDA8171	£2.00
BU2520DX	£2 00	IRF644	£2 00	5TK 1049	£7 00	STK4211 V	83	STK5481	£4.70	STR440	83	TDA2525	£4,50	TDA4720	£6 60	TDA8173	£1.75
BU2522AX BU2525A	£1.50	IRF650	£2 00	STK1050	£6 50 £7 00	STK4221 II		STK5482	£2 85	STR441	£9 50	TDA2530	. £3 00	TDA4725	£6.00	TDA8174	£2.00
BU2525AF	£2 20	IRF720	. £0 85	STK2025	£6 20	STK4231 V		STK5486	£4 50	STR442	£16 00	TDA2549	£3 00	TDA4800	£3 00	TDA8177	£3 00
BU2525AX	£1 90	IRF730	£1 25	STK2028	£5 00	STK4241		STK5487	£5 25	STR450A	£7 00	TDA2558	. £4 00	TDA4810	£5 00	TDA8177F	£3.50
BU2525D BU2525DF	£2 40	IRF740	£0 90 £3 00	STK2029	£6 00	STK4241 V STK4272		STK5488 STK5490	£4 80 £4 50	STR451	£8 00	TDA2560Q	£14 00	TDA4850 TDA4851	£4.75	TDA8179S	£12.50
BU2527AF	£4 00	IRF820	£0 90	STK2038	£7 00	STK4273	£5 50	STK561	£4 00	STR4512	£4 00	TDA2574V	£3 50	TDA4852	£3 25	TDA8205	£12.50
BU2527AX	£2 50	IRF830	£0 85	STK2048	£9 50	STK4274	£5 00	STK563	£4 15	STR452	£4 75	TDA2576A	£9.00 £2.00	TDA4854	£5 00	TDA8212 TDA8214B	£10.50
BU2527DF BU2527DX	£2 00	IRF840	£0.85	STK2058 IV	£16 00£10 50	STK430	£5 00	STK5632 STK5720	£3 00	STR454	.£13 00	TDA2578A	. £7 00	TDA4856	£5.00	TDA8215H	£10 00
BU2532AL	£3 25	IRF840F	£1 75	STK2110	£5 50	STK4301	£5 00	STK5725	£3.50	STR455	£5 50	TDA2579A	£2 10	TDA4858	£3.50	TDA8217	£2.25
BU2708AF	£2 00	IRF9140	£4.00	STK2139	£6 75	STK4311 STK433	£6 50	STK5730	£3.00	STR456	£4 70	TDA2579B	£3.25 £48 00	TDA4860	£2.00	TDA8303	£4.00
BU2708DF	£2 00	IRF9510	£1.50	STK2230	£4 70	STK4332	£3 65	STK6316	£3.00	STR470	£3 00	TDA2653A	. £4 50	TDA4866	£2.75	TDA8305	£5.00
BU2708DX	£2 00	IRF9511	£1 50	STK3102 II	£5 30	STK435	£3 75	STK6324B	£5 00	STR50020	£3 50	TDA2710-1	£4 00	TDA4880	£4.50	TDA8305A	£5.00
BU2720AX BU2720DF	£2 00 £2.00	IRF9520	£1 50	STK3106 STK3122 III	£25 00	STK4352	£5,00 £4 30	STK6327 STK6328A	£12 00	STR50092 STR50103A	£5 50	TDA2820M	£1 00	TDA4918A TDA4930	£17.00	TDA8310 TDA8350Q	£6.00
BU2720DX	.£2 00	IRF9531	£2 00	STK3152 II .	£9 00	STK4362	£4.50	STK6431	£6.00	STR50112A	£6 50	TDA3190	£2 00	TDA4935	83.00	TDA8351	£2.00
BU2722AF	£3.30	IRF9540	£1 75	STK3156	£5 00	STK437	£6.00 £4 90	STK6607	£4.00	STR50113 STR50115	£5 00	TDA3301B	£16 00	TDA4940	£2.00	TDA8354Q	£2.75
BU2725AF BU2725DF	£2.00	IRF9541	£0.95	STK350-030 STK392-040	£12 00	STK4372	£4 90	STK6712BIV STK6722	£6.50	STR50213	£4.00	TDA3501	£3.00	TDA4941	£2.00	TDA8360N3	£8.00
BU2725DF	£2.00	IRF9620	£0 85	STK401-050	83	STK4392	£5.00	STK6732	£10.00	STR50330	£4.75	TDA3502	£3 60	TDA4950	£1.00	TDA8361AN3	£8 00
BU2727AF BU2727A	£2.00	IRF9622	£2.00	STK401-080 STK401-120	£9 00	STK441	£6.80	STK6822 STK6875	£6 50	STR51041 STR51213	£5.00	TDA3504	£3.00 £4.50	TDA4951	£4.50 £3.00	TDA8361N3 TDA8362AN	£9.00
BU2727AF	£2.00	IRF9640	£2 30	STK401-140	£12 00	STK443	£7.00	STK6922	£10 00	STR51424	£7.00	TDA3521	. £7 50	TDA5400	£6.00	ITDA8362AN3	£7 50
BU506DF	£1 00	IRFBC20	£1 10	STK4017	£4 00	STK4432	£6.00	STK6932	£4.50	STR53041	£4.00	TDA3560	£6 00 £3 00	TDA5500	£4.50	TDA8362BN3	
BU508AF BU508APH	£0 60	IRFBC30	£1 20	STK4019 STK402-040 .	£4 80 £7 00	STK457	£4.70 £5.60	STK6962	£2 75	STR54041 STR5412	£3 20	TDA3561	£3 00	TDA5610-2	£4.50	TDA8362N4	£12.00
BU508AXI	£0.90	IRFBE30	£2 25	STK402-070	£7 00	STK460	£6.60	STK6981B	£5.00	STR55041	£4 50	TDA3562A	. £2.60	TDA5620	£4.50	TDA8362N5	£12.00
BU508D	£0 75	JRFD9120	£1 00	STK402-070 STK402-071	£7.00	STK461	£6.00 £9.50	STK6982	6 00 6 00	STR56041 STR58041	£5 50	TDA3563	. £3 50 . £4.00	TDA5702 TDA5830-2	£13.00	TDA8366N2 TDA8366N3	£15.00
BU508DR	£1 30	IRFD9220	£1.00	STK402-090	83	STK465	£9.00	STK7216	£4 20	STR59041	£3 00	TDA3564	£3 25	TDA6100Q	£1.50	TDA8370	£11.50
BUH1015	£4 25	IRFF120	£3.00	STK4021	£3 80	STK4773	£8.20	STK7217	£2 50	STR60001	£5 25	TDA3565	£2 20	TDA6101Q	£1.20	TDA8372A	£16.50
BUH1215 BUH515	£4.50	IRFIBC40G	£1.00	STK402-100 STK402-100	69 00	STK4793	£8 00 £10 00	STK7225	£5 00	STR6008X	£5 75	TDA3566	£2 80 £3.00	TDA6103Q	£2 25	TDA8374 TDA8375A	£10.00
BUH515D	£2 50	IRFP054	£4 00	STK402-120	£9 00	STK4813	£8 00	STK7233	£7 00	STR61001	£4 75	TDA3567	£3 50	TDA6107Q	£3.00	TDA8376	£15.00
BUH517	£2 75	IRFP064	£5.00	STK4024 H	£5 50	STK4833	£8 50 £7.20	STK7251	£5 00	STR7001	£6 00	TDA3569	£3.00 £3.75	TDA6108JF	£3.00	TDA8380	£4.00
BUH517D BUH715	£1 75	IRFP150	£2.50	STK4025	£5 30 £4 80	STK4843	£17.00	STK7253 STK730-060	£6 50	STR81145	£3 75	TDA3576B	£7 00	TDA6120Q	£5.50	TDA8425	£5.00
BUL310	£1 25	IRFP240	£3.00	STK4026II	£4 80	STK4863	£7 00	STK730-080	6 00	STR81159	£4.00	TDA3650	£6 75	TDA6160-2S	£4.75	TDA8432	£5.50
BUL381	£1 50	IRFP340	£2.80	STK4026V	£5 00	STK4873 STK488-010	£8 00	STK7308	£7 00	STR8124 STR83145	£10.00	TDA3651	£2 00 £3 50	TDA6160-2X TDA7052	£2.50	TDA8433	£6.00
BUT11A	£0.35	IRFP350	£3.25	STK4032 II	£5 10	STK488-050	£8 00	STK7310	£3 20	STR83159	£7 00	TDA3652	£5 00	TDA7056	£2 00	TDA8443	£3.50
BUT11AF	.£0.35	IRFP360	£8.00	STK4034 X	£9 25	STK4893	£10.00	STK73405 II	£5 50	TDA1420	00 83	TDA3652TX10.	£8 00	TDA7262	£3 25	TDA8451	£3.25
BUT11AX BUT12	£0.50	IRFP450	£2.70	STK4036	£4.70 £8 00	STK4913	£9.00 £5.50	STK73410 STK73410 II	£3 50 }	TDA1470	£12 00	TDA3653B TDA3653C	£0 80 £0 85	TDA7263	£3.50 £4.00	TDA8461	£9.50
BUT12A	£0,80	IRFP9140	£14.50	STK4038	£6 80	STK50322	£3.50	STK7348	£4 00	TDA1540	£4 20	TDA3654	£0 80	TDA7264	£5.00	TDA8501	£3.75
BUT12AF BUT18	£0.90	IRFP9240	£3.00	STK4040 II STK4042 II	£6 50 t	STK5314	£4.75 £5.00	STK7356	£4 25	TDA1541 TDA1541A	£5 00 £4 00	TDA3654Q TDA3724	£0 85 £3 00	TDA7265	£5.00 £5.00	TDA8560Q	£11 00
BUT18A	£0 80	IRFPC50	£4 50	STK404211	. £9 50	3TK5323	£6 00	STK7359	£4 25	TDA1546T	£10 50	TDA3725	£3 00	TDA7269	£5.00	TDA8561Q	£5.25
BUT18AF	£0 65	IRFPC60	6 00	STK4050 II	£16 0u	STK5324	£3.00	STK73605	£3.75	TDA1547	£10 00	TDA3730	£4 00	TDA7269A	£2.75	TDA8562Q	£5 00
BUT56AF	£0.65	IRFPE40	£5 50	STK405-030 . STK405-050A	£7 00	STK5325	£3 70 £7 50	STK73907 STK73908	£7 00	TDA1552Q TDA1553AQ	£3 50 £3.25	TDA3740 TDA3750	£4 (00)	TDA7293V	£5.50	TDA8563Q	£4.75
BUZ71	£0 75	IRFPF40	£5 50	STK405-070A	£8 00	STK5330	£8.50	STK73908	£5 50	TDA1553CQ	£3.00	TDA3770	£7 75	TDA7295	£4.00	TDA8566Q	£5 50
BUZ71AF BUZ72A	£1 00	IRFPF50	£4 50	STK4050V STK405-120	£15 00	STK5331	£3 00	STK7402	£6 00	TDA1554Q TDA1555Q	£3.00	TDA3771 TDA3803A	£4 60 £5 00	TDA7296	£5.00 £3.50	TDA8567Q	£7.00
BUZ72AF	£1 00	IRF\$740	£1 /5	TK405-120	£11 00	STK5332	£6 50	STK7404	£6 50	TDA1556Q	£3.25	TDA4400	£1 75	TDA7300	£5 50	TDA8569Q	83
BUZ73A	£1 50	IRFZ20	£0 65	5TK4065	£6 50	STK5335	£3 50	STK7406H	£7 50	TDA1557Q	£3 00	TDA4420	£1 20	TDA7302	£4 50	TDA8571J	£9.00
BUZ73AF BUZ76A	£0.60	IRFZ42	£2 75	5TK407-040	£7 00	STK5336	£3 50	STK7408	£6 75	TDA1558Q TDA1561Q	£3 00	TDA4421	£3 00 £2 00	TDA7310	£8.00	TDA8703	£5.00
BUZ77A	£2 00	IRFZ46N	£1 50	STK407-090	£8 50	STK5338	£2 95	STK7458	£12.50	TDA1562Q	£5 50	TDA4427	£3 (1)	TDA7313	£6.50	TDA8709	£7 00
BUZ77B BUZ80	£2.50	MJ10016	£2 75	STK4101	£4 00	STK5339	£4 00 £3 50	STK746	£3.00	TDA1580 TDA1599	£4 0u	TDA4429T	£20 00 £1.50	TDA7318	£5.50 £7.00	TDA8741	£5.50
BUZ80AF	£2 00	MJ11015	£2 50	STK4112	£5 00	STK5342	£2.45	STK7554	£4 80	TDA1602A	£4 00	TDA4474	£4 00	TDA7340	83	TDA8840	£10 00
BUZ83	£2.00	MJ11016	£3 00	STK411-230	£12.00	STK5343	£3.80	STK7561	£6 50	TDA16846	£2 00	TDA4480	£6 00	TDA7350	£3.00	TDA8841 TDA8842	£10 00
BUZ900 BUZ901	£10 00 £15 00	MJ11032	83 00 83	STK411-240E	£14 00 £4.80	STK5352	£5 00 £5.00	STK7561A	£10 00	TDA1670A TDA1675	£2.00	TDA4481 TDA4482	£11.00	TDA7359	£3.00	TDA8843	£15 00
BUZ905	£10.00	MJ15003	£2 50	STK412-150	£18.50	STK5353	£4.00	STK7563	00 83	TDA1675A	£2 00	TDA4500	£3 11)	TDA7362	£4.50	TDA8844	£14 00
BUZ906	£16.00	MJ15004 MJ15015	£3 00	STK4122 5TK4130 II	£5.60 £7.00	STK5361	£3.75	STK7563F	£6 50	TDA16833 TDA16846	£2 00	TDA4501	£2 80 £4 00	TDA7365 TDA7370V	£5.50	TDA9102C TDA9103	£2 50
BUZ90A	£1 80	MJ15016	£3 50	STK4130II	£7 00	STK5364	£2 50	STK7576	£15 00	TDA1701	£14 00	TDA4503	£3 25	TDA7372A	£4 50	TDA9105	£5 00
BUZ90AF	£2 80	MJ15022 MJ15023	£4 00	STK4131	£4 80	STK5364	£2 50	STK760	£5 00 £3 00	TDA1770	£7 50	TDA4504B TDA4505A	£8 00 £3 00	TDA7374V TDA7375V	£3.50	TDA9109	£10.00
BUZ91A BUZ93	£1.50	MJ15023 MJ15024	£3 00	STK4132 II	£6.00 £7.50	STK5371	£3 50 £3 50	STK770	£4 00	TDA1870A	£2.00	TDA4505E	£6 50	TDA7376B	£10.00	TDA9143	£4 00
IRF 120	. £2 25	MJ15025	£3 00	STK4140 II	83,	STK5372	£2 60	STK7707	£9 00	TDA1872A	£2.75	TDA4510	£2 00	TDA7377	. £4.50	TDA9144	£12.00
IRF130	£4 75 £5 50	MJE13004 MJE13005	£0.60	STK4141 II STK4141 V	£4 20 £6.00	STK5373	£3 75	STK780	£4 80 £7 50	TDA1908A	£2 50 £6 00	TDA4556	£3 70 £4 00	TDA7381	£11.00	TDA9151	£11 00
IRF230	£5 50	MJE13007	£1 00	STK4142	£5 30	STK5391	£3 75	STK78617	.£24 00	TDA1941	£3 00	TDA4560	£2 70	TDA7385	£10.00	TDA9162	£11 00
IRF240	£4 25	MJE13009	£1 00	STK4151	£6 80	STK5392	£5 00	STK795 STK8050	£3 25	TDA2003	£0 65	TDA4565	£1 50 £2 50	TDA7386	£11.00 £10.00	TDA9170 TDA9176	£7 00
IRF250	£3.75	MJE15028 MJE15029	£2 00	STK4152 STK4154V	£14 00	STK5422	£4 50	STK8250	£5 00	TDA2005	£1 50	TDA4568	£2 25	TDA7394	£6.00	TDA9177	00 8£
IRF330	£6 00	MJE15030	£2.5	STK4161	£6 50	STK5431	£5 50	STK8260	£12 00	TDA2006	£0 70	TDA4580	£10 00	TDA7396	£4.50 £7.00	TDA9210 TDA9302H	£4.50
IRF340	£3.25	MJE15031	£4 00	STK4161V	£8 50 £5.50	STK5434	£5 70 £5 00	STR10006	£18 50	TDA2009	£1.20	TDA4600	£2 00	TDA7439	£6 50	TDA9500	£7 5
IRF440	£5.50	MJE18004	£1.25	STK4164 II	£11 75	STK5441	£3 50	STR11006	£3.25	TDA2030	£0 80	TDA4601	£1 20	TDA749S	£4 25	TDA9503	£9.0
IRF450IRF510	£6.50	MJE18006 MJE18008	£1.20	STK4171 STK417-130	£15.00	STK5443	£5 75 £3 50	STR17006 STR20005	£5.00	TDA2030H	£6 00	TDA4601D	£0.65	TDA7560 TDA8000	£18 00	TDA9610H	£9 50
		MJE243	£0.60	STK4172 II	£6 80	STK5451	£3 90	STR20005	£2.75	TDA2050V	£2 00	TDA4610	£3.70	TDA8116	£3 50		
1RF520	£0.75	MUE243															
	£0.75 £1.00	MJE253 MJE340	£0 85 £0 25	STK4181 STK4182 II	£6 80 £9 00	STK5461 STK5462	£5 00	STR3315	£2 75	TDA2051V TDA2052V	£5 25	TDA4650 TDA4651	£3.00 £8.00	TDA8120B TDA8137	£4.00		

Please note that this a very small selection of the transistors and IC's that we stock.

We stock a full range of Japanese Transistors 2SA,2SB, 2SC,2SD,2SJ,2SK series, Diodes, CMOS, TTL Logic ICs,

Computer ICs, Zenor Diodes...etc

K.P. House , Unit 15 , Pop In Commercial Centre , Southway , Wembley , Middlesex . HA9 0HB England

Tel: (020) 8900 2329 Fax: (020) 8903 6126 Email: sales@grandata.co.uk

distributor of electronic components

Line Output Transformers

Part No Code Price	Part No Code Price	Part No Code Price	Part No Code Price	Par No Code Price
14.7				THE STATE OF THE S
ALBA	HITACHIcontinued	PANASONICcontinued	PHILIPScontinued	THOMSONcontinued
3714002LOT02£12.00	2433453LOT82£12.50	TLF 14568 FLOT40£15.00	AT 2079 / 21LOT395£12.00	10588080.P2LOT1505£19.00
043714002JLOT02£12.00	2433751LOT01£13.00	TLF 14584 FLOT41£17.00	AT 2079 / 24LOT392£15.00 AT 2079 / 40LOT73£11.50	151128140LOT1505£19.00 151281.4LOT1505£19.00
43700000LOT02£12.00	2433752 LOT01 £13.00	TLF 14586 FLOT42£17.00	AT 2079 / 99LOT276£11.50	15128140LOT1505£19.00
444077040	2433891LOT23£12.50	PHILIPS	AT 2079/30 01LOT106£12.50	153144.6LOT1505£19.00
AMSTRAD 1810951LOT55£14.00	2433893 LOT23 £12.50	3119 108 31260LOT90£12.50	AT 2079/30102LOT106£12.50	15314460LOT1505£19.00
3714002LOT02£12.00	2433952 LOT33£10.00	3119 108 31290LOT73£11.50	A1 207 3/00 102E01 100E12.00	1531447 ALOT1505£19.00
043714002JLOT02£12.00	2434002 LOT226 £14.50	3119 108 31440LOT433£16.00	SAISHO	1532873 ALOT1505£19.00
43700000LOT02£12.00	2434141LOT33£10.00	3119 108 31441LOT433£16.00	3714002LOT02£12.00	3233500 LOT244£14.50
AM152591 LOT55 £14.00	2434274 LOT44 £10.50	3119 108 31442LOT433£16.00	043714002JLOT02£12.00	3233900 LOT244£14.50
711102031	2434393 LOT405£22.50	3119 198 62930LOT57£11.00	43700000LOT02£12.00	40011200LOT244£14.50
FERGUSON	2434593LOT44£10.50	3122 108 10246LOT111£15.00	7140021LOT02£12.00	40148300 LOT244£14.50
00 D-3-508-002LOT381£15.50	2435006LOT401£17.00	3122 138 36070LOT111£15.00		
06 D-3-083-001LOT82£12.50	2435131LOT251£14.50	3122 138 36072LOT111£15.00	SHARP	TOSHIBA
06 D-3-083-002LOT82£12.50	2436201LOT90£12.50	3122 138 36920LOT57£11.00	RTRNF 1220 CEZZLOT39£18.50	1810951LOT55£14.00
06 D-3-084-001LOT23£12.50	23236465LOT392£15.00	3122 138 36922LOT57£11.00	RTRNF 2001 CEZZLOT338£17.50	2433751£13.00
06 D-3-087-001LOT23£12.50	2433891H£12.50	3122 138 36923LOT57£11.00	RTRNF 2006 CEZZLOT308£13.50	23236098LOT288£14.00
06 D-3-088-001LOT84£14.50	45150504LOT362£16.00	3122 138 37050LOT132£15.00	RTRNF 2023 CEZZLOT310£15.00	23236198LOT288£14.00
06 D-3-093-001LOT204£16.00		3122 138 37620LOT90£12.50		23236201LOT395£12.00
06 D-3-508-003LOT276£14.00	MATSUI	3122 138 37771LOT129£14.00	SONY	23236245LOT395£12.00
06 D-3-512-001LOT204£16.00	20070LOT438£16.00	3122 138 37992LOT1116£19.00	1-439-286-00LOT46£13.00	23236255 LOT289£15 00
29201-022-01LOT63£17.00	20071LOT438£16.00	6122 138 38040LOT73£11.50	-439-286-11LOT46£13.00	23236425LOT288£14.00
473197LOT304£15.50	20072LOT438£16.00	3122 138 38123LOT395£12.00	1-439-286-12LOT46£13.00	23236427 LOT395£12.00
D 059 / 37LOT200£14.00	20073£16.00	3128 138 20200LOT433£16.00	1-439-286-13LOT46£13.00	23236428LOT289£15 00
	20074 LOT438 £16.00	3128 138 20201LOT433£16.00	1-439-286-21LOT46£13.00 1-439-332-41LOT100£15.00	23236424LOT129£14.00 TFB 4090 ADLOT395£12.00
GOODMANS	20075 LOT438£16.00	3128 138 20202LOT433£16.00	1-439-332-41LOT100£15.00	TFB 4124 AELOT393£15.00
1142.5057LOT1164£15.00	3714002LOT02£12.00 3221008LOT438£16.00	3138 108 30100LOT106£12.50	1-439-332-42LOT101£14.50	TFB 4124 AFLOT392£15.00
1142.5077LOT1164£15.00	043714002JLOT02£12.00	3138 108 30101LOT106£12.50 3138 108 30103LOT106£12.50	1-439-363-11LOT268£14.00	110 7127 AFEO 1392215.00
1142,5079LOT1164£15.00	043221088PLOT438£16.00	3139 128 30400LOT90£12.50	1-439-363-21LOT268£14.00	Track and a dead of the other
1152-5016LOT1934£19.00	43700000LOT02£12.00	140348-08LOT1577£18.00	1-439-387-11LOT311£14.50	We are stockist of both
1179,0387LOT1147£16.00	7140021LOT02£12.00	40348A-08 LOT1577 £18.00	1-439-387-21LOT311£14.50	Konia
1192.0527LOT1147£16.00	17.0027	40348A-09LOT1577£18.00	1-439-416-11LOT255£16.00	Konig
1352.5008LOT1167£15.00	MITSUBISHI	4812 140 10246LOT111£15.00	1-439-416-12LOT255£16.00	3
1352.5008ELOT1167£16.00	731003£15.50	4812 140 10349LOT106£12.50	1-439-416-21LOT255£16.00	and
1352.5016LOR1934£19.00	334 P 18506LOT51£15.50	4812 140 10369LOT90£12.50	1-439-416-23LOT255£16.00	
1352.5027LOT1270£16.00		4812 140 10421LOT90£12.50	1-439-416-41LOT255£16.00	HR Diemen
1352.5033LOT1270£16.00	OREGA	4822 140 10246LOT111£15.00	1-439-41 6- 51LOT255£16.00	THE BIGHTON
	40153201LOT349£17.50	4822 140 10274LOT123£14.50		LOPT's
HINARI		#822 140 10306LOT57£11.00	THOMSON	EOI 13
3714002LOT02£12.00	ORION	4822 140 10349LOT106£12.50	105009.8LOT1505£19.00	This is just a selection
043714002JLOT02£12.00	3714002LOT02£12.00	4822 140 10381LOT128£13.00	10500980LOT1505£19.00	
43700000LOT02£12.00	043714002JLOT02£12.00	4822 140 10384LOT127£15.50	10500980.P1LOT1505£19.00	of the LOPT's that we
CF 124 BLOT67£14.50	43700000LOT02£12.00	4822 140 10406LOT73£11.50	10531460LOT1505£19.00	
CF 124 ELOT67£14.50	BANASONIC	4822 140 10544LOT433£16.00	105660060LOT1505£19.00	stockPlease call on
HITACHI	PANASONIC TLF 14512 FLOT39£18.50	4822 140 10566LOT433£16.00 AT 2076 / 10LOT57£11.00	10566060LOT1505£19.00	000 0000 0000 6
2424593 LOT44 £10.50	TLF 14512 FLOT40£15.00	AT 2077 / 81LOT121£15.00	0566060.P2LOT1505£19.00	020 8900 2329 for copy
2432461 LOT169£15.00	TLF 14521 FLOT39£18.50	AT 2077 / 81LOT395£13.00	105880.8LOT1505£19.00	of our LOPT catalogue
2432761 LOT169 £15.00	TLF 14567 FLOT39£18.50	AT 2079 / 15LOT129£14.00	10588080LOT1505£19 00	or our LOP1 catalogue
2302101201103213.00		7.1. 25.57 10		

CD Pick Ups and Mechanisms

Part No. Price	Part No Price	Part No Price
CDM12.1 Mechanism£14.00	KSS 213 B£8.75	OPTIMA 6 S£11.50
KHM220AAA		OPTIMA 5£11.50
DVD Laser £ 40.00	KSS 213 D£16.00	RCTRTH8151£20.00
KSS 210A Original£11.00	KSS 213 F £12.00	RCTRTH8112£14.00
KSS 210A Replacement .£9.50	KSS 240 A £30.00	RCTRH8147 Mech £ 10.00
KSS 210 B£15.00	NKS 240 A	
1	Replacment for KSS240A £20.00	

Check out our Online Catalogue at

www.grandata.co.uk

This advertisement is just a selection of our stock.

Please contact us if you cannot find the part you are looking for.

* Please add £1 p+p and VAT to all orders (Unless Otherwise stated) * All components are brand new

* We accept payment by Access , Switch , Visa , Cheque and Postal Order

* All prices quoted are subject to availabilty and may be changed without prior notice

E & OE

K.P. House, Unit 15, Pop In Commercial Centre, Southway, Wembley, Middlesex. HA9 0HB England

Tel: (020) 8900 2329 Email: sales@grandata.co.uk

Fax : (020) 8903 6126 Website : http://www.grandata.co.uk

Servicing the Sharp DA100 (50Hz) and DA50W chassis

Part 3 of this series, by Alex Towers, deals with the dynamic focus, EW correction and field output stage circuitry and outlines line and field timebase fault-finding procedures

e ended last month with the operation of the basic line drive and output stage circuitry. Before we start on fault-finding in this area we should take a look at the focus-modulation circuits used in larger-screen models, since these are linked to the line-scan current path.


Dynamic focusing

Because of their larger screen size, 66cm and 76cm models employ a focus-modulation circuit. It's driven by the line-scan current waveform. The function of the focus modulator is to ensure that the picture is kept in focus at the edges of the display. When the beams are deflected to the edges of the screen they become distorted, as the distance they travel is greater than at the centre of the screen.

Fig. 24 shows the circuit used in GF models. The primary winding of transformer T1602 is connected in series with the line-scan current path, prior to the chassis return via the scan-correction capacitor C613. The signal generated in the secondary winding is fed to the slider of the focus control potentiometer, and is thus superimposed on the DC focus voltage.

This basic arrangement is used in both FW and GF models. Because of the different type of screen with FW models however a rather more complex focus-modulation circuit is used, see Fig. 25. With FW models the screen is not truly flat, the curvature affecting the time taken by the beams to reach the screen to a greater extent than with a flat screen. Focus correction in both the horizontal and vertical directions is therefore required. Horizontal correction is carried out as with GF models, but vertical correction is added, see Fig. 25. The EW drive signal is fed via R1610 and C1605 to pin 2 of lC1601, whose output at pin 1 drives Q1602 and Q1601. The latter adjusts the waveform produced by T1602's secondary winding.

Fig. 26 shows the focus-modulator PCB in FW models.

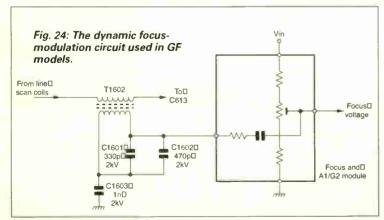

Line output stage faults

If the negative supply used to switch off the line output transistor Q601 is too low it won't turn off rapidly. A large voltage will be developed across its collector-emitter junctions during the switch-off period, while current is still being drawn. The power generated has to be dissipated by the transistor itself, which will get very hot and will eventually fail. The usual cause of this problem is C607, which can fall in value or become leaky. As a result, the negative switch-off supply falls. If this has not already been done, it's advisable to fit a 105°C capacitor in this position.

For intermittent failure of the line output transistor it's advisable to replace C607, D610 and D611. Dry-joints can also cause this problem. The areas most commonly affected are the line scan coils' chassis return circuit (C613, R613 and the associated components) and the scan coil connector itself. Sometimes C613 or R613 become open-circuit, the result being loss of line scanning with the possibility that the output transistor becomes short-circuit or leaky. C613 can fail under load, so it's best to check it by substitution. C528, C632 and C615 can also be responsible for intermittent failure of the line output transistor.


Note that the correct type of line output transistor must be used. An incorrect type will result in erratic operation or premature failure of the device. The Sharp part number for Q601 is RH-TX0144BMZZ.

You could find that the line drive is missing even though the main microcontroller chip IC1001 has gone through the boot-up sequence. The line drive signal comes from pin 50 of the video/deflection processor chip IC801. IC1001 produces a line mute output at pin 57—this is rather misleadingly referred to as HOUT. The mute can be released to enable the line output stage to start up by short-circuiting the base-emitter junction of Q607 (2SC2412) or temporarily disconnecting link wire JL2, see Fig. 27.

If D1601 on the focus-modulator PCB (66 and 76cm models only) becomes leaky or short-circuit, the result will be an over-large picture as the EHT drops to about 20kV.

EW correction

In addition to the normal EW correction required with a 4:3 aspect ratio, 110° deflection tube a widescreen set requires a change of correction for different scanning modes. There are generally three basic modes with widescreen sets, 4:3. 14:9 and 16:9, but in addition the latter can have three variants. full. panorama and cinema. The full mode is used to stretch a 4:3 format picture which contains fast-moving action, for example motor racing: so it doesn't matter greatly if the horizontal linearity is not constant across the screen. The panorama mode is similar but for slow-action or even stationary displays, for example news programmes, where any variation in linearity would be noticeable. To overcome this problem the linearity

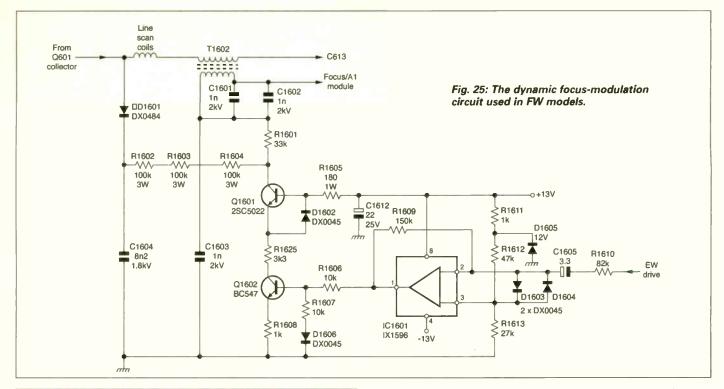

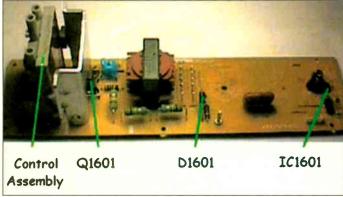


Fig. 26: Photo of the FW focus-modulator PCB.

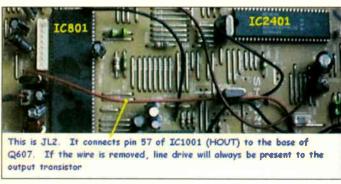


Fig. 27: Location of link wire JL2.

is kept constant at the centre of the screen, the sides of the picture being stretched to fill the screen. The cinema mode is for use with pictures that are in true 16:9 format. When setting the geometry, the set must be put in the 'full' mode.

Fig. 28 shows the basic EW correction and line scan circuitry used in these sets. It's centred on transistor Q506, which operates slightly differently from a conventional EW diode-modulator driver in that it is turned on to increase rather than reduce the width. This enables the circuit to work more efficiently, and as a result the transistor does not become overly hot in operation.

IC503 is a switching amplifier. Integrated line-frequency pulses from the line driver circuit are fed to the inverting input via Q501,

while a parabolic EW signal from pin 32 of the video/deflection processor chip IC801 is fed to the non-inverting input. The result is a pulse-width modulated output at line frequency, with the width of the pulses determined by the parabolic EW signal. This output is fed to Q506, which is biased for class D operation, is then low-pass filtered and is finally used to drive the diode modulator (D603/604 and C601/610). The low-pass filter consists of L603 and C610. In addition the output from the filter is fed via C611 to coil L604. The centre tap of this coil is connected to the line linearity circuit, while the other end is connected to chassis. Thus the line linearity can be adjusted by the parabolic EW signal.

Fig. 29 shows the print side of the EW circuit and Fig. 30 the component side.

Fault-finding in the EW correction circuit

It is important to establish in which part of the circuit the fault lies. Check the control output at pin 32 of IC801. There should be a parabolic waveform here, at a base frequency of 50Hz. It will change shape depending on the amount of correction applied. So it is important to enter the service mode (see later) and ensure that none of the adjustments are at minimum or maximum.

If this waveform is present and changes as adjustments are made, the cause of the fault will be in the drive or output circuitry. Faults that can be experienced in this area include:

(1) R519 (usually $100k\Omega$), which is connected to the 150V supply, can go high in value or open-circuit. It's mounted on the component side of the PCB. The part number is VRD-RA2HD104J. Note that the value is sometimes $150k\Omega$. Check the value before fitting a replacement, as incorrect value will result in poor EW geometry performance.

(2) Q506 (2SD2391), which is a surface-mounted device, can be leaky, short-circuit, open-circuit or can overheat. The part number is RH-TX0151BMZZ. If it has to be replaced, the following should also be changed: L603/4, D502-4, D516 and C528.

The resistance of L603 and L604 can fall – L603 is normally 8Ω . The part numbers are L603 RCLIP0286BMZZ and L604 RCLIP0284BMZZ. Clamp diodes D502-4, part number RH-DX0551BMZZ, can be intermittently faulty. Clamp diode D516, part number RH-EX0837BMZZ, can also be intermittently faulty – it's not shown in the GF circuit diagram but is fitted to the chassis. The reservoir capacitor C528 (10μ F, 63V) can become leaky. Its part number is VCEAGA1JW106M.

(3) The EW modulator diodes D603 and D604 can go open- or short-circuit. Part numbers are D603 RH-DX0299BMZZ and D604 RH-DX0302BMZZ.

(4) A dry-joint can be present at C601 and/or C610.

If the waveform at pin 32 of IC801 is not present, is severely distorted or the adjustment range is poor, the cause of the fault could be the EEPROM chip IC1003 or the video/deflection processor chip IC801. In this case it is recommended that IC1003 is first blanked (see later). If this does not cure the problem, IC801 is probably defective.

Sometimes it may not be possible to set the geometry correctly in all modes after blanking the EEPROM. In this case ensure that the EPROM (IC1002) is the correct type – see Part 1. When the correct EPROM has been fitted, the

EEPROM will have to be blanked to enable the correct data to be downloaded to it.


Replacement EPROMs have been produced to provide minimal geometry adjustments. If the picture geometry is still poor after carrying out this procedure, the fault will lie elsewhere in the EW circuitry.


The CRT PCB

Two types of CRT PCB are used, one for 66cm and 76cm sets and the other for the 56cm Model 56FW53H. The major difference is that there is no scan-velocity modulator or picture-rotation circuitry in the 56cm model, so the PCB is smaller. Note that the RGB output chip IC1801 can be one of three types, see Part 1. Fig. 31 shows the 66cm and 76cm PCB, Fig. 32 the 56FW53H PCB.

It's possible for the grey-scale to wander, the picture brightness ramping up or down. If the A1/G2 voltage is set correctly, check IC1801 by substitution.

Picture smearing will occur if the reference voltage at pin 2 of IC1801 (type TEA5101A or TDA6019JF) is about 10V instead of about 11·5V. This normally shows in the red display. If the voltage is below 9V the picture will blank. In both cases Q912 (TX0130) or its associated components can be the cause. This transistor can run hot (especially with GF modules, because the transistor draws more current). If you suspect that the transistor could fail because of this, a 68Ω , 0·5W resistor can be added between its collector and emitter. It is easiest to fit this resistor on the print side of the PCB.

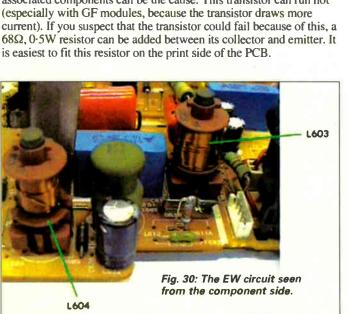

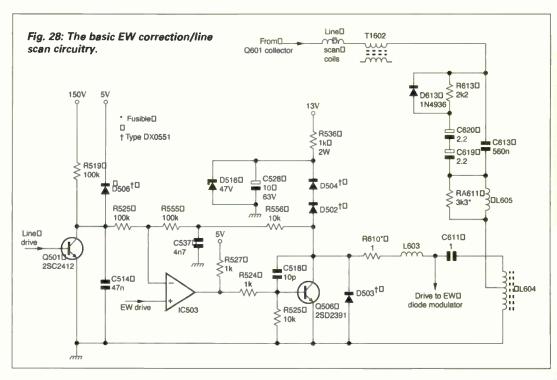


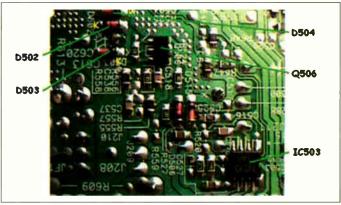


Fig. 29: The EW circuit seen from the print side.

Class D output stages

Sharp used discrete-component class D output stages for a number of years to minimise dissipation. Subsequently a specially-designed IC was introduced for the purpose. This device is ideal for TV audio and field output stages, where high efficiency (low energy use) is required. The TDA7480 IC is for use in audio and field output circuits, while the TDA7481 version is used to drive the sub-woofer in sets with Dolby Pro-Logic. Table 3 shows the pin details for the TDA7480, with voltages when used in the field output stage

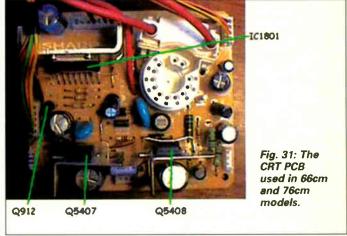

(IC501). The voltages differ slightly when the chip is used in the audio output stage.

Note that pins I-3 and I7-20 are all connected together by a large area of print on the bottom of the PCB. This area is used as a heatsink for the device, so it's very important that all these pins are soldered when fitting a replacement, otherwise premature failure of the device may occur. Note that when the IC is correctly

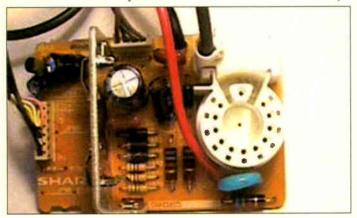


Fig. 32: The CRT PCB used in Model 56FW53H.

fitted it does not get hot during operation.


The external components fitted to pins 8 and 9 determine the base frequency of the PWM section of the IC. With an audio circuit the frequency will vary from the base frequency by at least the bandwidth of the audio signal (20kHz): this ensures that no beat signals that could interfere with the audio signal are produced.


The voltage at the standby/mute pin 12 determines the IC's operating state. At less that 0·8V the IC will switch to standby (no output). With a voltage between 1·8-2·5V the output will be attenuated by 60-80dB. For normal operation the voltage should be above 2·7V.

The field output stage

Fig. 33 shows the basic field output stage circuit. The TDA7480 chip IC501 is operated in a similar way to its use in the audio output stage, except that there's no mute circuit – though C511 prevents operation until the +13V supply is present.

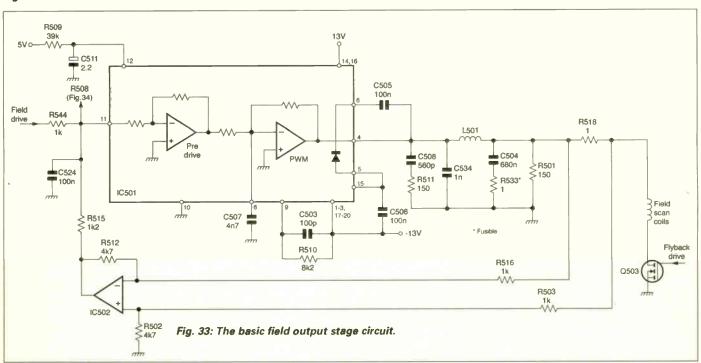The pulse-width modulated output at pin 4 is fed to a low-pass filter (L501, C504) that produces a ramp drive for the scan coils. The ramp is at +13V when the scan starts at the top of the screen, decreasing to -13V when the scan reaches the bottom of the screen. The scan coils are returned to chassis via Q503, which is switched on during the field scan period and off during the flyback. IC502



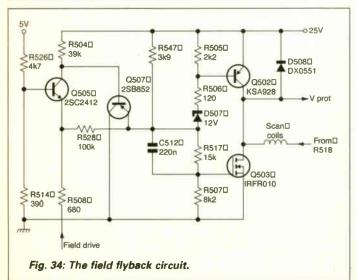


provides an error-signal output that's fed to pin 11 of IC501 for linearity and height correction.

Fig. 34 shows the circuit used to generate the field flyback. Q503 is switched off to start the flyback and Q502 is switched on, connecting the 'earthy' end of the scan coils to +25V. Since there is -13V at the other end of the scan coils at this time, there is effectively 38V across them. The beams are thus driven back the top of the screen.

The field drive signal from pin 31 of IC801 has a negative-going pulse in addition to the ramp waveform. This negative-going pulse initiates the flyback. It's fed via R508 to the emitter of Q505, whose base voltage is set by the potential-divider R526/R514 so that it switches on only when the negative-going pulse appears at its emitter. When Q505 switches on its collector voltage falls, switching Q507 on. Q507's emitter voltage then falls to chassis potential. This has two effects. First Q503 is switched off because its gate bias has been removed. Secondly D507 conducts, switching Q502 on.

The field flyback pulses generated at the collector of Q502 are fed to pin 11 of IC801 as the V prot signal, see Fig. 35. This provides an indication that the field output stage is working. If IC801 does not detect the negative edge of this pulse, it assumes that the field output

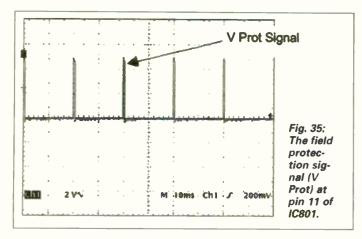

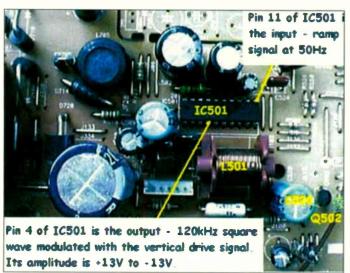


Fig. 36: The field output stage, component side of the PCB.

stage is not working and blanks its RGB outputs.


Fig. 36 shows the field output stage from the component side and Fig. 37 the layout on the print side of the PCB.

Field timebase faults

Most field-scan faults are caused by software corruption or output IC failure. If the EEPROM gets corrupted it can cause severe vertical distortion, no drive, or foldover at the top of the screen. An EEPROM problem can be solved by blanking it, using the blanking OTP (see later). As the audio and field output ICs are the same, a substitution check will prove whether the field output IC is faulty.

When a 56FW53H set is fitted with a Thomson tube, check that EEPROM location F7 on page 0C is 0D. This location controls the field blanking point and, if set incorrectly, can cause red, blue and green lines to flash intermittently at the top of the screen. The setting can be incremented to 0E, 0F or 10 if necessary. 10 is the maximum allowable value – any higher setting will result in an unstable blanking level. If the symptom persists with a setting of 10, there's a fault elsewhere in the chassis.

Field collapse produces the blank-screen symptom. To avoid a line being burnt on the screen in this event IC801 monitors, at pin 11, the field flyback pulses. It blanks the screen when these pulses are missing, by shutting down its RGB outputs. When the blank-screen symptom is present, check for 50Hz pulses at an amplitude of 5V at pin 11 of IC801. They may be missing or corrupted because of a fault in the flyback circuit. The

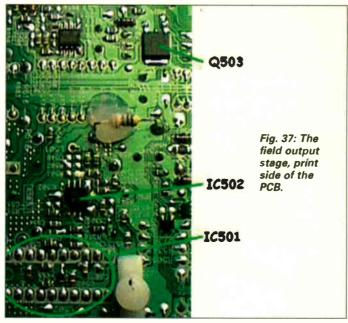

usual cause is that Q502 and/or Q503 is leaky or short-circuit. In this case the 25V supply will probably be low.

Red, green and blue lines may be seen at the top of the screen. This normally means that the automatic grey-scale correction lines generated during the field flyback period are not being blanked correctly. Adjustment of the A1/G2 setting on the line output transformer will normally cure this problem. It is possible for the fault to be caused by incorrect operation of the field flyback circuit however. First check that the +25V supply generated by D510/C520 is not low (below 18V) and that there is no excessive ripple here. If there is a problem in this area, the flyback circuit is unable to generate a high enough pulse to send the beams back to the top of the screen. It is not unusual to find that C520 or the feed resistor R530 (10 Ω , shown as R617 in Fig. 22) is faulty.

If there is severe vertical distortion or a very small picture, pin 12 (mute) of IC501 may not be at 5V. At any voltage less than 2.7V the IC's output will be attenuated by 70dB. The cause could be failure of C511 or R509.

Foldover at the bottom of the screen when the set has been operating for about fifteen minutes can be caused by failure of the 100nF surface-mounted capacitor C505. Replace it with a capacitor from Sharp, part no. VCKYTV1HF104Z.

Next month

Next month we'll continue with the operation of the audio circuitry and fault finding in this section of the receiver.

Table 3: TDA7480 pin details

Pin(s)	Nominal voltage	Function
1-3	-13·1V	Negative supply
4	OV	PWM output
5	-2.5V	Anode of internal bootstrap diode
5 6 7	9-9V	Connection to external bootstrap capacitor
7	0V	No connection
8	0V	Connection to external feedback integrating capacitor
9	-11-8	Connection to external frequency-setting resistor
10	0V	Signal earth
11	0V	Input
12	5V	Standby/mute control
13	0V	No connection
14	14·1V	Positive signal supply
15	-2.5V	Reference voltage
16	14-1V	Positive power section supply
17-20	-13·1V	Negative supply

Passive Component Analyser (Model LCR40)

fully inclusive UK price

Just clip on the test leads and press test. The Atlas LCR will automatically identify the type of component, apply the appropriate test level and frequency, display the component's value and more!

so you can use the optional SMD tweezers Probes are detachable too. for your tiny unmarked

passives - fantastic.

Inductance range: 1µH to 10H

Capacitance range: 1pF to 10,000µF

Resistance range: 1Ω to $2M\Omega$

Basic accuracy: 1% Test signals: 1V, 3mA max

"Astonishingly, this little unit seems to pack most of the punch of a large and very expensive automated LCR bridge into its tiny case."

Andy Flind - EPE Magazine March 2003

Automatic component identification (Inductor, Capacitor or Resistor)

- Component value measurement
- Auto frequency (DC, IkHz, 15kHz, 200kHz)
- Inductor DC resistance measurement
- Non-volatile probe compensation men ory
- Detachable probes allowing use of opt onal test prods. SMD tweezers, etc...
- Hands free mode with value hold



Supplied with mini-hook

grabbers as standard

Semiconductor Analyser

enclosure colours may vary

(Model DCA55)

fully inclusive UK price

Check and . identify your semi's

Automatic component identification

Pinout identification

Transistor gain measurement

MOSFET gate threshold measurement

- PN junction characteristics measurement
- Shorted Junction identification
- Transistor leakage measurement
- Just connect the part anyway round and press the button!

Auto power on/off

Bipolar transistors, Diode protected transistors, instrument that Resistor shunted transistors, Enhancement mode MOSFETs, Depletion mode MOSFETs. Junction FETs.

Low power triacs and thyristors, Diodes and diode networks. LEDs (+bicolours)

"It's the kind of should be on every

> engineers and enthusiasts bench."

EPE Magazine March 2000

NPN birolar Darlineton

Diode protection between C-E

Resistor shunt between B-E

Current sain Hfe=126

Enhancement mode N-Ch MOSFET

Date Threshold Ues=3.470

LCR40 and DCA55 Pack

Why not order both analysers at the same time and take advantage of our special offer, saving you £10!

Visit www.peakelec.co.uk to download the data sheets, user guides and copies of independent reviews. You can pay using a cheque, postal order, credit or debit card and even pay securely online. Please contact us for your volume requirements

Mble from Farnell, Maplin, Rapid and CPC (prices vary)



Atlas House, Kiln Lane Harpur Ind. Est., Buxton Derbyshire, SK179JL, UK

www.peakelec.co.uk sales@peakelec.co.uk Fax. 01298 70046 Tel. 01298 70012



NEED A CHEAP TUBE?

BRAND NEW PHILIPS W66ECK/ESF AT £145.00

Other types available.

NEW TUBES BOUGHT FOR CASH.

Visit www.dlec.co.uk

Tel: 01474 361276/327677 Fax 01474 335228

E-mail: sales@dlec.co.uk

D'Lec Components Ltd 3 Manor Court, Sole Street Cobham, Kent DA13 9BU

Nunar Electronic Calls & Orders

Following the success of the highly acclaimed F4 Service Management in the early 1990's the powerful software Nunar allows you to use your existing F4 customer records to create a new database for organising service calls and processing customer orders.

Nunar works independently from F4 and can also work in conjunction with any computerised system you are using. It provides five different search methods to instantly locate your customers. All details are then used to create a service call or customer order. Customers are located by either of the following fields:

Owner ID Postcode Address Name Telephone

The postcode and telephone searches for example locate and transfer all details from your customer database, this avoids duplicating details when booking in. A professional image is portrayed when customers are located from their telephone number. When using caller display this enables you to have customer information on screen before answering the telephone.

She boasts an infinite user entry when used on a network and is tailored to fit your exact requirements. Please contact us for more information.

Logik Business Solutions 17 Marsworth, Stafford Tel: 01785 222082 Mob: 07748 916526

ALDER OMPONENTS (HECKMONDWIKE) LIMITED

127A WESTGATE, HECKMONDWIKE WEST YORKSHIRE WF16 0EW TEL: (01924) 411089 FAX: (01924) 411104



Calder Components stock an extensive range of spares and components for the TV, aerial, satellite and video repair trade. We offer a friendly service usually with next day delivery and do not charge for postage and packing. We have a comprehensive range of parts in stock.

Our specialist areas are:

REMOTE CONTROLS

We stock a wide range of models including both originals and equivalents. BSkyB remotes a speciality with attractive prices for large orders.

PACE DIGIBOX SPARES

We hold a comprehensive stock of top selling spares including PSU kits, tuners, IC's, etc plus BSkyB remote controls. We also stock panels and covers for digiboxes and remotes. A full catalogue and price list is available on request,

LOPTX'S

We can provide a vast range of LOPTX's. Currently we have a special offer on the following:

Eldor 1192.1327 at £9.20 each
Eldor 1192.0797 at £9.50 each
Eldor 1142.1615 at £10.00 each
Orega 1034.2010 at £10.00 each
Orega 1036.9690 at £13.50 each

Volume discounts are available for large orders of the above.

All orders or enquiries are welcome by either telephone or fax on the above numbers.

REMOTES DIRECT

All makes and models Replacement and Originals remote controls available.

!!!!!!At a fraction of the cost!!!!!!

Please contact for instant quote

ROB or MARK

Tel: 01257 793527

E-mail: infrared@btconnect.com


Or check out our website and order on-line

Website:

www.remotesdirect.co.uk

Also available a wide range of satellite equipment

And various other electronics!!!!!!!

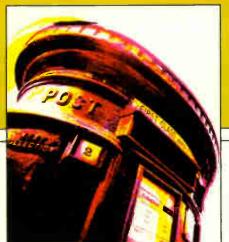

unless you state otherwise. and cheaply almost anywhere. We now

DTT redundant?

I had to laugh when I read the item headed 'Aerials for DTT' in Teletopics (September). After all the misleading publicity about how good DTT is. someone has finally admitted that "because the characteristics of DTT reception differ significantly from those of analogue TV reception, it's much more difficult to ensure that an aerial installation will be satisfactory". Those of us in the trade always knew this.

Where do Monkey and Johnny Vegas fit into this? According to them, when it was still ITV Digital, all you had to do for super digital pictures was to pick up a box from your local dealer and glue it to the end of your existing aerial. Over much of the country this simply didn't work. Since the reworking and renaming of the service. it has been improved technically and the signal is more robust. Yet the Digital TV Group still says that the aerial system is of paramount importance for the system to work - you can get problems because of co-channel interference, multipath reception, marginal signal strength and overloading. Perhaps my memory is becoming foggy, but weren't all these problems going to disappear as a result of DTT's marvellous error-correction systems and the extreme robustness of the digital signal?

We already have a perfectly good digital TV delivery system, via Astra. Once you've bought your DTT box then paid out anything up to £150 to get your aerials sorted out, you can receive a service that's of limited technical capability because of bandwidth limitations and can, for the same reason, never be expanded to include the premium channels. You might as well go for Astra.

Satellite broadcasting is superior: the signals can be received relatively easily

or e-mail t.winford@highburybiz.com using subject heading 'Television Letters'. Please send plain text messages. Do NOT send attachments. Be sure to type your full

Send letters to "Television", Highbury Business Communications,

Nexus House, Azalea Drive, Swanley, Kent, BR8 8HU

name, address, postcode, telephone and e-mail address (if any).

Your address and telephone number will not be published but your e-mail address will

Please send ONLY text intended for the letters page. Correspondence relating to subscriptions and other matters must be sent to the office address given above.

have a sorry mess of a broadcasting system. All that was needed was a little cooperation between all parties. Once again the politicians got it wrong. Geoff Darby,

Earls Barton, Northampton.

Fire hazard

When I took the back off a Bush Model WS6671 (Vestell 11AK19 chassis) recently I noticed, printed on the top righthand side of the PCB, the words 'risk of fire'. Too true! The fault was a dry-joint at C613 (12nF) in the EW diode-modulator circuit, and the associated fusible resistor R629 (2.7 Ω) had in turn been fried. This seems to be something of a design muck up. Had the genius who was responsible thought about it, a fusible resistor that's designed to go open-circuit in the event of an overload in the circuit it protects is likely to get hot and should therefore be mounted on long leads in mid air, not close to the PCB. As a result R629 burnt a hole in the board the size of the Grand Canyon. and carbonised some of the board as well.

All was not lost as I persevered, cleaning up the PCB with a fibre pen, and mounted the replacement fusible resistor in mid air. Otherwise the set would have been consigned to the skip. So yet another big waste was avoided.

The EW coil was also damaged, and it took some time to obtain a replacement. I was told that there is quite a demand for it. Ray Withey, Edinburgh.

Reliability

During the Seventies and Eighties I was a regular contributor to this magazine. I've long since left the trade, but still buy the magazine regularly. Recent reports on the demise of the service industry as we knew it, because of the greater reliability of modern sets and the 'throw-away approach that cheap new equipment has brought about, lead me to relate the following story.

Way back in 1979 a friend of mine bought two 'nearly new' Philips sets fitted with the G11 chassis. By nearly new I mean that they had been in use for about six months in a hotel. New owners and a change of regime meant that they were no longer required. So my friend snapped them up for his own use. I gave them the onceover at the time, and also carried out a little experiment that I'll come to shortly.

Twenty four years on the sets both remain in daily use and work perfectly. I had replaced the notorious HT reservoir electrolytic capacitor in both sets. In one set I'd had to replace the TDA2600 field timebase chip, the two EW modulator diodes, and attend to dry-joints all over the place. But both sets have their original CRTs and line output transformers, also the original line output transistors and power supply thyristor rectifiers. Even the troublesome beam-limiter transistors on the power panel are the same.

Why? Maybe because of the little experiment I mentioned earlier. At the time I decided to see how low the nominally 152V HT voltage could be set without materially affecting the performance of the sets. I found that it could be reduced to 142V with no noticeable effect on picture quality. There was a slight reduction in both the width and the height. This was only to be expected, and was easily corrected by slight adjustment of the appropriate timebase presets.

Although it has always been said that under-running a receiver is as detrimental as over-running it, I can only assume that the de-stressing effect of my adjustments was the reason for this remarkable longevity. Either that or an amazing coincidence - remember that we're talking about G11s!

I would be interested in any opinions readers may have about this. Steven Knowles. Enfield, Middx.

Polarity protection

With reference to Jim Littler's letter (October) concerning protection against reverse-polarity battery connection, a simpler solution is to add a bridge rectifier to the battery input of any device that's to be used with a car or truck battery. I have done this many times - and have watched

with amusement the expressions on people's faces when I have swapped the battery connections over and the piece of equipment still works!

Fig. 1 illustrates this.

David Mawtus,

Scarborough, North Yorkshire.


Vintage radio repairs

I was very interested to read Pete Roberts' article on the Bush Model VTR103 transistor radio in the October issue. More on vintage radio please!

You can always recognise the VTR103 with its red pip at the end of the telescopic FM aerial. I have one in my collection (cream coloured front and back with brown rexine sides). It works on all three bands but the VHF quality is not so good. I might replace the AF115 transistor in the VHF mixer/oscillator stage with an AF125, as Pete suggests, to see if this provides any improvement. I don't think anyone has interfered with the VHF alignment!

The large, circular Perspex tuning knob on the front of the VTR103, TR82 and the original MB60 valve mains/battery model was always difficult to remove. I usually

Fig. 1: Addition of a bridge rectifier between a battery and the equipment it powers. It doesn't matter which way round the battery is connected. In (a) diodes D1 and D2 provide the connection, in (b) diodes D3 and D4 do the job.

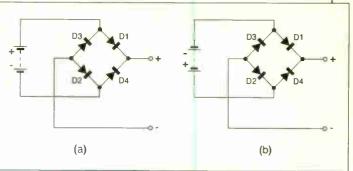

try to place an old cloth under and around the knob and try to get an even 'pull' on it. Don't bend the pointer in the process! If any damage to the knob does occur, a replacement can be found from a scrap DAC70 or VHF90C valve radio. It's a good idea to put some vaseline on the control shaft and on the inside of the control knob, where the shaft goes in, so that the knob can more easily be removed should the need arise. Like Pete, I've never had to replace those Hunts Mouldseal capacitors in these transistor radios. The only time that I replace them is in valve radios.

The backs of these transistor sets often suffer from damage. They are usually held by a coin-screw that gives access to the battery, but people try to lever the back off with a screwdriver. Hence pieces of missing plastic around the sides of the back. In addition some previous owners drill out holes in order to install various sockets, which never get used, in the back of these sets. The back looks very tatty in this condition. So I fill the spaces with epoxy resin and try to match the original colour.

Mike Horne, www.mikesradio.freeservers.com

HELP WANTED

The help wanted column is intended to assist readers who require a part, circuit etc. that's not generally available.
Requests are published at the discretion of the editor. Send them to the editorial department or email to t.winford@highburybiz.com

Wanted: Remote-control unit for the Manhattan 9000 stereo satellite receiver, also operating instructions. Willing to pay for these or does anyone know where I might purchase them? Phone Mike Commelford on 0771 525 8580 (Chesterfield).

Wanted: Line output transformers (oil-filled) for the Murphy Models V290C and V320A, which date from around 1956-58. I am also looking for a Murphy Model V410 or V430. Full costs paid. Phone Trevor Goodenough on 01563 540 444 or email trevor@goodenough.freeserve.co.uk

For disposal: A Commodore Vic 20 computer with cassette deck, manuals, tapes

and power supply. Believed to be working but needs good clean and some TLC. Free for collection (Bishops Stortford). If interested, please email David Martin at dandjmartin@ntlworld.com

Wanted: Service manual for the Technics SA-DV170 stack audio system incorporating a carousel DVD player. I have sorted out the power connection problem but one channel of the base unit, which also contains the power supply, is dead. Can anyone help? D. Housley, 30 Arncliffe Drive, Heelands, Milton Keynes, Bucks, MK13 7LH. Wanted: Old half-inch diameter ferrite

Willing to pay very good money for them.
Peter Tankard, 16A Birkendale Road,
Sheffield, S6 3NL. Phone 07931 463 823
(mobile) 9 a.m. to 10.30 p.m.

Wanted: A TMP47C834N R165 microcontroller IC for the Philips TV Model 14PT156A/05. G.T. Singleton. 59 Garstang Road, Catterall, Preston, Lancs, PR3 0HD. Phone 01995 606 864.

Wanted: Circuit diagram (photocopy OK) for the Schneider Model STV2801, or any information on the power supply and line output circuitry. The set is lifeless and I suspect a power fault. IC102 could be faulty but the number cannot be seen. Donald Bills, 46 Blewitt Street, Pensnett, Brierley Hill, Dudley, DY5 4AN.

Wanted: For spares. Quad 303 and 405 power amplifiers, 33 and 44 preamplifiers and FM2 and FM3 tuners. Working or nonworking. Phone Mike on 01758 613 790. Wanted: Can someone out there help or at least point me in the right direction? I have a DVD player that provides S-video and composite video outputs, but the TV input

I wish to use expects to see YUV or Y/Cr/Cb. The only converter I can find listed is a semi-professional multiple switched input device that also gives an RGB output but is far too expensive at almost £300. It will obviously do what I want, but has too many extra bits I would never use – I need simple S-video in to YUV out. I'm sure I can't be unique in requiring such a device! Phone Mike Harris on 0161 485 1621 (Cheshire) or (mobile) 07966 377 684, or email mike.harris@ukonline.co.uk

Wanted: Tigan loudspeaker cloth, large size. Phone Steve Beeching on 01636 626 895 or email

steve@grovefarm.force9.co.uk

Wanted: Manual (photocopy OK) for the Telequipment S54A oscilloscope. Your price paid! Phone Steve (M.D. Stevenson) on 01702 522 929.

Wanted: Working teletext PCB for the ITT Compact 80-R-DST chassis, a remotecontrol unit for the Sony Betamax VCR Model SL-C30UB, and a tuning tool for the Ferguson TX90 chassis (it operates the AFC). Phone Mark on 01268 414 654. Wanted: Remote-control IC type µPD550-25 for the Hitachi music centre Model SDT900. I know it's an oldie, but someone out there must have one. Please have a good look! Phone Stan (Stanley Swales) on 01924 829 653 (Wakefield. West Yorkshire). Wanted: Spare parts for the Bush MB60 valve mains/battery radio, and control knobs for the Pye Fenman II valve radio (they suffer from brittleness and don't come away from the set easily!). Please email Mike Horne at mike@jhorne62.freeserve.co.uk



DX and Satellite Reception

Terrestrial DX and satellite TV reception reports. Broadcasting news. LNB-dish matching. Interference from PLT.
Roger Bunney reports



People blocked the main routes out of New York during the power outage in NE America in early August. This shot, from WCBS, was received via NSS-7 (21.5°W).

uring August there was a remarkable spell of hot weather, broken by colder weather from the north with rain from the 28th. The very settled high-pressure system from the 4th produced the best tropospheric propagation for some years. A noteworthy feature was the first Band III DAB-DX!

Tropospheric conditions improved from about the 3rd, giving sustained reception from Scandinavia, Denmark, Germany. France and the Benelux countries in all TV bands. On several days Band III and the UHF bands were jammed with signals. Highlights were reception of SVT-1 Vannas (Sweden) ch. E2 and YLE Tervola (Finland) ch. E3 while, of particular interest, Cyril Willis (King's Lynn) achieved the first recorded Band III DAB-DX, with reception from many stations in the Benelux countries and UK regionals at up to about 200 miles. So we now know that terrestrial digital DX is possible. After two weeks of excellent reception, the opening began to falter on the 16th.

Sporadic E conditions were also very active. Here's the SpE log:

3/8/03 TVE (Spain) ch. E3; RTP (Portugal) chs. E2-4.

4/8/03 TVE E3.

5/8/03 TVE E2. 3; RTP E3; RAI (Italy) IA.

6/8/03 NRK (Norway) E2, 3; SVT (Sweden) E2-4.

7/8/03 RAI IA: Tele A (Italy) E2-; C+ (Canal Plus, France) L2.

8/803 MTV (Hungary) R1; RTP E3.

9/8/03 NRK E3: RAI IA: TVE E2.

10/8/03 RAI IA. B; HRT (Croatia) E4.

14/8/03 RAI IA, B; BT (Belarus) R1; RTP E3; RTL (RTL Klub, Hungary) R2.

15/8/03 UT (Ukraine) R2; MTV R1; RTP E2, 3; TVE E2-4.

16/8/03 MTV R1

17/8/03 NRK E4; RTL KL R2; MTV R1; RAI IA, B; TVE E2; TVE-IZ (Izana, Canary Is) E3; HRT E4; Dubai E2.

18/8/03 NRK E2-4; YLE (Finland) E4.

19/8/03 BT R1; C+ L2.

20/8/03 RTL KL R2; UT R2; RTP E2: TVE E2. 3.

During several late-evening spells of SpE reception from Spain the signals fell to a low but viewable level for some hours. On the 20th TVE ch. E2 produced late-evening signals that rose to very high levels with severe hum, almost like Auroral propagation. Odd.

All in all an excellent month.

Satellite sightings

During the late afternoon on August 4 there was the largest power outage in NE America for years. affecting an area from Ohio to New York and the Great Lakes to Pennsylvania. When I checked NSS-7 (21.5°W) for breaking news I found very fragmented reports via CNN Newsource at 11.563GHz H (SR 6.109, FEC 3/4). There were live helicopter-camera shots that showed a mass of home-going New Yorkers blocking the freeways, roads etc., and pictures from the WCBS and WNYW TV stations. These were interrupted several times for studio inserts to provide updating reports, I assume from the CNN NY bureau as there was an NY1 corner ident logo. Between these news inserts studio technicians and on-screen presenters attempted to gauge the power-loss area. with phoned-in reports from affiliated stations. When I rotated the dish to 12.5°W (Atlantic Bird-1) there was a total absence of signals - the outage had closed down the teleport. But later in the evening the GlobeCast downlinks returned. The CNN uplink teleport is at Atlanta, Georgia, which was outside the blackout region.

Less than an hour before the East Coast blackout President Bush was seen at the US Marine Corps Miramar Airbase, California, where he made a patriotic speech to marines recently returned from Iraq. The speech was carried by CNN Newsource.

The major bombing at the UN's Baghdad HQ on the 19th brought several satellite uplinks there into operation. APTN was running at both 10·961 and 10·964GHz V (4,167. 5/6) via Eutelsat W1 (10°E). Content concentrated on rescue work, with numerous

live reports back to networks in Europe and the US. ITN's Martin Giessler for example used the 10-964GHz channel. A couple of days earlier an American news package via Eutelsat W2 (16°E) at 12-533GHz H (5,632, 3/4) featured a large water main that had been damaged by an explosion, flooding the surrounding area. The same day an oil pipeline was blown up.

Eutelsat W1 is a major carrier of news and sports. Interesting that a rare N. Korean feed was seen on the 3rd. At the time the Israeli Satlink facility was present at 12·741GHz V (5,632, 3/4) with a threshold-level signal (1,425). At the end of a programme with Chinese-script captions a fluttering N. Korean flag (star in the middle) was seen, followed by colour bars then a blank screen. It seems to have been a relay of the main Pyongyang TV channel and, I suspect, was carried for the final Satlink network news broadcast. Satlink continued with a carrier, and later fed APTN footage from Jerusalem and Ramallah.

On the 9th it was the Mey Highland Games with Prince Charles and Camilla in attendance. Their appearance was the main reason for a sat truck to be present, since the sporting events were very parochial – tug of war, tossing the caber, and an odd game that required each contestant to hurl a large weight above his head while standing under a jumping-frame cross bar, then avoiding the weight crashing down on his head a few seconds later! There was a pleasant and happy crowd in that distant Caithness field. Seen via Eutelsat W1, the APTN UP4 feed, at 10-970GHz V (4,167, 5/6).

One evening in middle of the month I checked the Atlantic Bird-I GlobeCast transponder at 11·014GHz H (20,145, 3/4) and found that the Channel I circuit carried a 'GlobeCast Miami FI' ident. A check on the signal level with the RSD information menu showed a normal 70 per cent level, but the inlaid serial ident on the level bar alternated between the usual 'standard hop', 'hop 3', 'hop 4' and 'hop 8'. Very odd. Another oddity has been the transmission identified as 'Service I' from Europe*Star-I (45°E) at 12·678GHz V (6,109, 3/4). It carries the serial ident 'NDS Network', so it's obviously a TV feed. Although I've monitored the carrier on most days I've never seen video content.

HellasSat (39°E), which was launched to provide coverage of the 2004 Olympic Games in Greece, provides regular transmissions at 10·976GHz V (5,632, 3/4). Alan Richards (Nottingham) came across a Euro-political discussion here, with interpreters and four audio subcarriers for different languages. The transmission ended with a Greek-language documentary on the Olympics and a news update on construction progress at the venues for the various events. The service ident was unusual – 'Mountain 1'. Alan also found French-language content from Ethiopia, Mozambique, Cameroon and the Congo via the Atlantic Bird-2 (8°W) GlobeCast transponder at 11·501GHz H (6,111, 3/4) during each weekday evening in mid-July. All rare sightings.

The Montenegro downlink via Atlantic Bird-3 (5°W) has been affected by jamming. Check at 12.642GHz H (3,885, 7/8).

Edmund Spicer (Littlehampton) viewed a major NASA press conference via the Atlantic Bird-I GlobeCast channel I feeder following publication of the damning official report on the Columbia shuttle disaster. The NASA chief answered questions from its staff and interested parties. Clearly things will change.

News

The 2003 NAB convention revealed considerable broadcaster interest in the use of MPEG-4 video compression, which can be almost twice as efficient as MPEG-2. Recently developed bridging technology enables the two to be used together as deemed best, probably MPEG-2 for in-house purposes and MPEG-4 for transmission and broadband video applications.

Microsoft is increasing its presence in the broadcasting field with the Windows Media 9 system that was introduced last year, including the H264 and WM9 software packages. WM9 is already being used by Associated Press for rapid compilation and transmission of despatches to the newsroom from battle zones etc. via satellite phone. Panasonic is using WM9 for digital content manage-



Closedown of Pyongyang TV (N. Korea), seen via Eutelsat W1 (10°E).

ment in sports and archiving. Tandberg TV is exploiting it for encoding video and audio, achieving remarkable quality with bit rates less than half that required for the equivalent quality with MPEG-2.

There's clearly a move to the use of increased signal compression in the broadcasting world.

Peter Merrett of Sciteq Pty Ltd., Australia, reports in the NZ trade magazine SatFACTS on a digital satellite receiver fitted with a new low-threshold tuner developed by Sharp. It achieved a signal level of 50 per cent compared with 20 per cent, going into pixellation, with a standard tuner. Sharp produces an extremely wide range of satellite tuners for digital equipment.



FULLY COMPREHENSIVE 35 PAGE CATALOGUE AVAILABLE BY RETURN OF POST FOR £1.50

AERIAL TECHNIQUES LTD Tel: 01202-423555 Fax: 01202-425055

59 Watcombe Road, Southbourne, Bournemouth, Dorset BH6 3LX, UK E-mail: atech@dircon.co.uk www.aerial-techniques.com

Est 1979 Callers by Appointment please



Edmund Spicer took this photo of the BT TES-43 satellite truck at Littlehampton.

Radio Marti and TV Marti, the US government-backed broadcasters to Cuba via a balloon at some 10,000ft above Key West, Florida, are to start broadcasting via satellite in order to overcome jamming. Ku-band downlinking capacity has been leased aboard the Hispasat satellite at 30°W.

The Russian ORT TV channel is being made available to US cable operators by Ascent Media Network, via Intelsat. The channel is received in London, sent via transatlantic fibre-optic cable to the New York AMNS switching centre, then on to International Channel Networks, Colorado for distribution.

LNB-dish matching

Recently Roy Carmen mentioned that the performance, i.e. signal output level, of his 1m Triax dish seemed to be the same as that of his 1·2m Channel Master dish, though the claimed performance of the two LNBFs used is similar – an LNBF is an LNB with integrated feedhom. I am wondering whether the cause could be poor LNB-dish matching with the larger dish. I use a 1·2m Channel Master dish myself and am happy with it – apart from the fact that it becomes rather grubby and requires an annual clean off. My main concern in dish selection was a smooth polar response with minimal secondary lobes. Trying for example to receive low-level signals from Eutelsat 2F1 (21·5°E) with its inclined orbit (2·3° drift) is a challenge, being next to the Astra 1 powerhouse at 19·2°E. The polar response of the Channel Master dish seems to be excellent.

I've seen many glowing references to Triax equipment. Certainly the company's terrestrial aerials are first class, and its dishes are also said to be excellent. Roy has always tended to try the latest, lowest-noise LNBs as they appear on the market, to optimise performance with a smallish dish. Inevitably these are LNBFs. Most dishes used for reception from Hot Bird are up to 70-80cm in diameter, perhaps slightly larger in the far north. It occurs to me that LNBFs might be optimised for use with smaller rather than larger dishes. For optimum performance the feedhorn must 'see' the surface of the dish with minimal overlap, as overlap introduces noise. Conversely low-cost LNBFs may not see the whole surface of a larger dish, thus failing to produce maximum possible output. My own Channel Master dish uses a dedicated Channel Master feedhorn and flange assembly - the LNB is bolted on to the rear C120 flange of the feedhorn. This is referred to as an LNB+F. It ensures - I hope! - that the feed and dish match.

While Roy and I were considering the dish v. LNB(F) situation, an article on testing and evaluating LNBFs for digital signal reception appeared in *SatFACTS* (May 2003 issue). It included a small section on "lowering the noise wall". I quote from it: "In marginal

reception situations you have only two choices – to get more signal or reduce the noise wall." This means use a higher-gain (larger) dish or improve the noise performance with a lower-noise LNB. The article points out that many people, when using an offset dish, neglect to use an LNBF whose 'feed pattern' is designed to see the physical shape of the dish correctly. A shaped dish requires a 'shaped feed pattern'. In theory a dish and LNBF should be sold as a matched pair. Otherwise the LNBF used may have been designed for a dish with a different shape, thus reducing the performance and polar response. In the UK dishes and LNBFs tend to be sold separately, which could explain why the expected performance is not achieved.

Bill Wright (www.wrightsaerials.tv) has carried out a few tests with a cheap 0.6dB noise LNB and signal analyser and found that ground noise was on average 7dB higher than sky noise. The comparison was with the LNB pointing at the sky and then at the ground, buildings etc. Aiming it at a tree produced similar readings to ground noise. These measurements were made at night: solar radiation might increase the noise during the day.

An LNB that sees beyond the edge of a prime-focus dish will pick up ground noise. Ground noise is less with an offset dish, as the LNB is aimed upwards. But in either case a response with minimal side lobes is important. Offset feeds are usually flared to optimise pick-up efficiency. Bill also comments that commercial dishes have a non-reflective skirt around the rim, perhaps to minimise man-made and thermal noise.

Interference from PLT

The following is not relevant to DX-TV or satellite reception. But many readers are in the trade, while others DX on the MW and SW bands, and may thus experience the problem.

Perhaps 18-24 months ago I mentioned concern in amateur radio circles about a new form of communication, PLT (Power Line Telecommunications) – sending data to houses, offices etc. via power lines. The EMC column in the June 2003 issue of the RSGB journal *RadCom* discusses two types of PLT, Ascom and Mainnet. Ascom uses up to three carrier frequencies, 2·4, 4·8 and 8·4MHz, with a IMHz bandwidth. Mainnet uses a single carrier with a wider bandwidth, 4·25-6MHz. With both systems the sidebands tail off slowly, so the bandwidth is far in excess of the nominal one.

Dave Lauder, who has written the EMC column in *RadCom* for many years, has warned that PLT would cause serious disruption to amateur radio and SW transmissions if adopted. The government seems to be encouraging it. PLT trials have been carried out at Crieff in Scotland, and have been threatened for the Winchester, Hants area. Ominously, there was a mention of PLT tests recently in the business section of my local paper. It's now the end of August and I suspect that the Winchester tests have begun.

White noise and a sharp buzzing, with a rapid pulsing noise (several pulses per second), have become audible on the MW band from about 750kHz, increasing in level with frequency. By 1,400kHz the noise can be heard on weaker MW signals. At 1,600kHz a communications receiver measures S7 on the S meter scale. At 1,820kHz the reading rises to S9, and remains at this level up to 2,600kHz when it drops to S7. Tuning higher, I find that the noise falls to S6 but increases to S8-9 from 4,400kHz through to 6,200kHz, with white noise plus buzzing. It falls to S7 at 7,000kHz, then tails off into general SW noise from 7,300kHz.

Being involved in MW-DX I am aware of general MW conditions and know that this is a new and wideband form of interference. It clearly affects MW broadcasts, which is disturbing. The RSGB website that covers the Crieff PLT tests has sound clips of the Ascom system. These show a close resemblance to what I am hearing at my location. I have reported the problem to the RSGB and am making representations to the local electricity supply company. But big business interests are involved! I'll report further as things develop.

The following RSGB site contains the Crieff information: http://www.qsl.net/rsgb_emc/crieff

Export Enquiry Only

Genuine Returns


Tv's ,Vcr's ,Dvd's ,Audio, Small Appliances Iron's , Toasters Etc Container load Available!!

LARGE QUANTITY!!

Also Available for UK Market
Products from
SONY HITACHI TOSHIBA PANASONIC DAEWOO
BEKO SVA MORPHY RICHARDS PHILIPS KINGAVON
& TRADEX

Call- 07836 520036



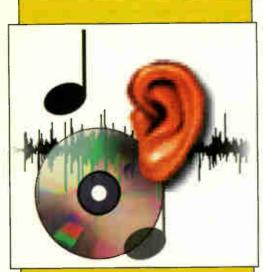

AUDIO FAULTS

Reports from
Geoff Darby Charles Coultas
and Chris Bowers

We welcome fault reports from readers – payment for each fault is made after publiation. See page 40 for details of where and how to send reports.

Yamaha CRXM5

If one of these comes in and you suspect the laser unit, be very careful how you quote for the job. I would suggest that you allow a good two hours for labour if the laser unit is type KSS580.

There are two reasons for this. First the laser unit is not very easy to get at. You will spend twenty minutes or so getting to the point where the changer is out and you can see the deck itself. Secondly and much more importantly, you have to change the laser unit to type KSS710A. Although this is physically similar to the KSS580 in general mechanical terms, its connections and electrical characteristics are entirely different. So it comes with a kit of parts and two large sheets of modification instructions and diagrams.

The modifications involve removal of links from the PCB, removal of a number of surface-mounted resistors, replacement of others with resistors of different value, print cuts, and the addition of standard carbon resistors and a lot of wires across the back of the board. All this is after you've actually removed the main board of course.

In all fairness the instructions are fairly comprehensive, though a little misleading in places. For success you must follow the numbered instructions completely blindly. Do not attempt to figure out what you are doing by referring to the modified circuit diagram, as this will mislead you. All the resistors you are told to remove in the first couple of steps are still in the circuit diagram, but are shown with new values, in red. This is not correct. They should just be removed, and left removed, as the instructions say.

When it comes to the print cuts and adding the wires and external resistors, refer to the print layout supplied for help with interpreting instructions like "short the No 10 pin of PN801 to the No 9 pin cut above (the +side of C823)". You'll need good eyes or a magnifier to see the modifications clearly on the print layout. But they are there, and are correct. The procedure is not helped by instructions like 'remove chip resistor R830 (silkscreened as R832)". Yes, R830 and R832 are marked incorrectly on the board but are shown correctly in the circuit diagram! One of them has to be removed and the value of the other has to be changed, so make sure you get them the right way round. Also one of the carbon resistors that has to be fitted has a value of 100Ω . The resistor supplied has this value, but its packet is incorrectly marked 100kΩ.

Finally there is a problem with the flexiprint connection tail from the replacement laser unit. It's upside down in comparison with the original, so it has to be twisted over before it can be inserted into the connector that joins it to the long white flexiprint which goes up to the main board. Be careful to do this close to the connector. Otherwise, even though the tail comes round a piece of plastic that should isolate the moving part from the fixed part, the twist can migrate up to the transition point and make the laser run stiff on its tracks.

Once I'd carried out these modifications a further twenty minutes were required to reassemble everything. I was then rewarded with a fully working unit. I dread to think what I would have done had it not worked. You certainly wouldn't want to put the original laser unit back, and such a situation would probably leave you seriously concerned as to whether your original diagnosis had been incorrect or you had made an error in fitting the modification kit. G.D.

Sony STR-DB940

This gigantic AV amplifier arrived on the bench with a note to say that it "makes a buzz from the sub". I soon discovered that the output to the sub had quite a high level of treble on it intermittently instead of being pure sub (bass). This odd behaviour could be instigated by slight movement of the flexiprint between the main PCB and the 'vol' sub-PCB.

No amount of cleaning of the connectors

or foil tails at the flexiprint's ends would correct the problem. I was loath to believe that the cable itself was faulty, as it was quite thick and had never been stressed with tight bends near its ends. Eventually however I decided to order a replacement. When this had been fitted the problem was no longer present. G.D.

Sony HCD-MD313

This CD/MD player/radio/amplifier was brought in because 'no disc' was displayed when a CD was inserted. Without thinking too much about it, I suspected the optical block and ordered a replacement. But when it was fitted the fault was still there. I then noticed, as I should have done before, that the CD wasn't rotating. So maybe the optics had been OK after all.

Investigation into why the motor was not rotating led nowhere. The motor worked all right when it was tested with a 1.5V battery, and the sled and focus seemed to be working normally. I replaced the motor/focus/sled drive IC, but this made no difference.

Much delving around with the scope didn't help, but I then found that focus search was missing. I sat back and thought about the problem. Perhaps the disc doesn't spin until some positive result is obtained from the focus search. When I scoped the output from the focus-coil drive IC it was cycling up and down but the lens wasn't. A little further investigation showed that the flexible, flat cable to the optical unit was damaged. I also realised that I had forgotten to remove the solder short that protects the laser when the optical unit is in transit! I probably damaged the flat cable with all the messing about I subjected the drive to.

A new flat cable and removal of the solder short put matters right. C.C.

Sony MZ-R90

There was no recording with this MiniDisc unit. A look inside revealed the cause: the overwrite head didn't come down because of a defect with the HC gear, reference 113. A new gear, part no. 4-222-215-01, restored normal operation. C.B.

Sony ICF-SW7500

This small LCD radio produced an IC-type cracking noise after five-six minutes with FM operation only. A look inside, on the B side of the main board, revealed that the small surface-mounted electrolytic capacitor C69 (220 μ F, 4V) had started to leak on to the board. A quick board clean up and replacement of the capacitor, part no. 1-126-246-11, restored normal FM sound. C.B.

Sony MZ-R900

This silver MiniDisc player had a broken LCD module. I've had this problem several times. You have to fit a replacement module, part no. 1-804-171-11. Units with serial numbers CED325801-326000 are prone to this fault. C.B.

Rocket science?

Buying spares doesn't have to be...

We purchase from many suppliers, both UK and abroad so that you don't have to.

- ✓ Run by T.V. engineers for T.V. Engineers.
- You speak to experienced engineers with in-depth knowledge of TV/Video trade.
- CLASSIC[®]
 distributors and
 trade counter.
 Cards, Switch
 and Accounts.

- We stock parts that engineers advise us to stock, with regular updates.
 - Free or low £1.00 p&p on orders means:

YOU CAN
EASILY
AFFORD TO
ORDER
MORE THAN
ONCE A DAY!!!







Engineers countrywide have already found our compact catalogue an invaluable aid...
to order your free copy today...


Ring Mike on 0114 273 9622

IrwinElectronics

"The television engineer's wholesaler"

Unit 200, JC Albyn Complex, Burton Rd., SHEFFIELD S3 8BX

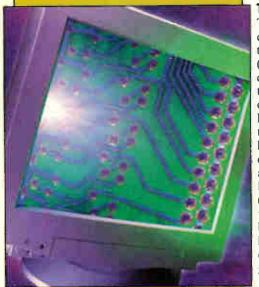Online you can place orders at www.IrwinElectronics.co.uk



MONITORS

Fault reports from Gerry Mumford and Ian Field

We welcome fault reports from readers – payment for each fault is made after publication.

Reports can be sent by post to:

Television Magazine Fault Reports, Highbury Business Communications Nexus House, Azalea Drive, Swanley, Kent BR8 8HU

or e-mailed to: t.winford@highburybiz.com

Taxan EV760TCO95

This dead monitor produced the usual clicking sound of the trip action. Checks in the line output stage revealed that D104 (BY329-1200) in the EW diode modulator circuit was leaky. When the monitor was tested after fitting a replacement it powered on very briefly, with a massive burst of EHT, then started to trip again. This time the line output transistor Q106 (2SC5048) had gone short-circuit. The massive burst of EHT before its demise gave the game away: the real cause of the fault was the line output stage tuning capacitor C105 (6.2nF. 2kV) which was open-circuit and, when removed, was seen to have a slightly bulged appearance. Once these two items had been replaced the EHT was down to its correct level and the monitor produced a good display. G.M.

Viewsonic M70 (Model VCDTS21503-1E)

This monitor powered up with light from the green LED but no display. There was no EHT and a quick visual inspection revealed that C556 (100μ F, 200V) on the secondary side of the power supply was leaking electrolyte. Replacement of this capacitor cured the fault.

Since the first occasion we've had many more of these monitors with this fault but, deceptively, the capacitor has always looked OK – especially in the Taxan variant that uses an almost identical chassis. G.M.

Viglen AX1595

This monitor was dead with a blown up power supply. The items one usually has to replace in this event are the 2SK2545 chopper FET Q301, the UC3842 controller chip IC301 and the 15V, 500mW zener diode ZD301. In this case we also had to replace the mains bridge rectifier diodes D301-4 (unmarked, use type 1N4007) and the current-sensing resistor, which consists of five 1Ω , 0.5W resistors connected in parallel (R306-R310). Once the replacements had been fitted we had a working unit with a good display. G.M.

Elonex/AST TE1438A

The complaint with this monitor was no blue. It had received previous attention which, to say the least, didn't help. Whoever had last removed the screening plate from the CRT base PCB hadn't bothered to unsolder the lugs! A vague attempt had been made to reattach the plate, but it fell off as I eased the CRT base connector off. I then noticed that the pads for Q205 in the green emitter-follower pair circuit had been pushed off the PCB. As I unsoldered the transistor the tracks fell off completely.

Once the missing tracks had been

replaced with stout wire, and the PCB had been cleaned for closer inspection, I found that the blue cathode pin on the CRT base receptacle had pushed its solder pad off the PCB. The heater pins' pads had also lifted, but not severed the tracks.

The damaged solder lands for the screening plate's lugs were repaired by binding tined-copper wire along the edge of each slot. The best way to describe this repair method is that it's like the 'blanket stitch' without the fancy loop! After cleaning off the green varnish, you anchor a length of tinned copper wire at one end of the slot and repeatedly thread the wire around the edge of and through the slot, pulling it tight, so that it runs along the edge like a 'layer-wound' coil. Solder the tail end down at the end, to secure the turns and restore the integrity of the earth track if this has been broken.

Depending on the thickness of the tinned-copper wire used, the legs of the screening plate might be a tight fit. They can usually be eased in if heat from a soldering iron is applied at the same time. I.F.

Apricot XJ52023

Sometimes a monitor comes in simply because a switch has been mis-set. This 17in. monitor spent some time making clicking noises before it started up and produced a distorted blank raster. So I decided to try the two slide-switches at the back: sync on/off and power saving on/off. When the sync on/off switch was moved from off to on the 'fault' completely disappeared.

The only difference the power-saving switch makes is that in the on position removal of either the H or V sync pulses shuts the monitor down, while in the off position removal of either the H or V sync pulses simply blanks the raster. The situation is no different whether the 15-pin sub-D or 5 x BNC input is used.

I am puzzled as to why a monitor would have a switch to cut off the sync input. As I don't have the manual I've no clue as to what purpose it might serve. To prevent a repeat performance I considered gluing the switch in the on position, but instead opted for a sort of compromise. I cut the sync switch lever flush with the screening plate and concealed it with tape. Thus it's not impossible to operate the switch should the need arise, but anyone intending to do so will fir t have to remove the tape.

I cut the power-management switch lever down to about half its length to reduce the chance of inadvertent operation. It's unlikely to stop the monitor working but could cause erratic operation while the PC is booting up and initialising the sync-ratio registers on its video output card. I.F.



- Possibility of 32 programs memorized per frequency band, Display (2 Lines of 16 characters).
- Range of measurement of signal strength from 20 to 120
- dBµV, manual or automatic attenuator. Battery life about 1 hour 20 minutes, weight 5,8 Kg.

- Display of full-band and 4 possible expanded spectrums.

 Channels and frequency plans of cable and TV standards memorized

 Frequency, signal strength in dBJV or bargraph, displayed on a digital display (2 lines of 16 characters).

 Voltage of remote power supply in 14v or 18v and 22 KHz in satellite + DISEQ C^{TV} v1.2 switching

The panoramic field strength meter MC30A combines in one instrument all the functions necessary for installing and checking TV or satellite roception, both analogue and digital. The visualization of the spectrum and the picture allows the carrying out of all the necessary adjustments with this one instrument. The high technology used in the MC30A allows a range of possibilities unheard of in a instrument in this price category.

NEW Lacuna Terrestrial Digital Meter Lacuna Digital Satellite Meter A custom designed, small lightweight ABS case, created with the Small, lightweight custom designed for terrestrial digital installations Identifies transmitter Measures signal strength, carner/noise and BER . UHF / VHF Analouge and digital measurement Removable 'F' connector 4 line LCD with backlight Weight including batteries 600g

- Signal strength and BER will be displayed together Indetifies the chosen satellite
- Signal strengths and BER settings calibrated facility for recalibration by distributor Removable 'F' connector
- Compatible with all satellite transmissions e Ku and C band, DVB and DSS

COASTAL AERIAL SUPPLIES

Unit X2, Rudford Industrial Estate, Ford, Arundel BN18 0BD Telephone: 0870 2641990 Fax: 0870 264 1991

Sole Import Distributors

. 12v line power facility

FRUSTRATED!

Looking for ICs TRANSISTORS?

A phone call to us could get a result. We offer an extensive range and with a World-wide database at our fingertips, we are able to source even more. We specialise in devices with the following prefix (to name but a few).

2N 2SA 2SB 2SC 2SD 2P 2SJ 2SK 3N 3SK 4N 6N 17 40 AD ADC AN AM AY BA BC BD BDT BDV BDW BDX BF BFR BFS BFT BFW BFX BFY BLY BLX BS BR BRX BRY BS BSS BSV BSW BSX BT BTA BTB BRW BU BUK BUT BUV BUW BUX BUY BUZ CA CD DX CXA DAC DG DM DS DTA DTC GL GM HA HCF HD HEF ICL ICM IRF J KA KIA L LA LB LC LD LF LM M M5M MA MAB MAX MB MC MDA J MJE MJF MM MN MPS MPSA MPSH MPSU MRF NJM NE OM OP PA PAL PIC PN RC S SAA SAB SAD SAJ SAS SDA SG SI SL SN SO STA STK STR STRD STRM STRS SVI T TA TAA TAG TBA TC TCA TDA TDB TEA TIC TIP TIPL TEA TL TLC TMF TMS TPU U UA UAA UC UDN ULN UM UPA UPC UPD VN X XR Z ZN ZTX + many others ZTX + many others

We can also offer equivalents (at customers' risk).
A LARGE RANGE OF ELECTRONIC COMPONENTS ON OUR CD ROM - LIST AVAILABLE ON REQUEST Mail, phone, Fax, Credit Card orders & callers welcome.











Cricklewood Electronics Ltd

40-42 Cricklewood Broadway. London NW2 3ET Tel: 020 8452 0161 Fax: 020 8208 1441 www.cricklewoodelectronics.co.uk E-mail: sales@cricklewoodelectronics.com

Sky Digital

Satellite **Tuner Repairs**

We also repair Power Supplies, Complete Set Top Box's **UHF Tuners and Modulators**

For more information and latest prices See our web site

www.mces.co.uk

15 Lostock Road Davyhulme Manchester M41 0ES

E-mail: sales@mces.co.uk

Phone: 0161 746 8037 Fax: 0161 746 8136

AUBBS

NEW LOWER PRICES:-

14" Philips/Orion	34 <mark>EAC, 34AGT, 34JLI</mark>	£30
24" Philips widescreen	W56ECK, W56ESF	£160
24" Thomson widescreen	W56EGV	£160
26" Panasonic standard	66ECF	£55
26" Philips standard	66EAK	£75
26" Thomson standard	66ECY, 66EDN, 66EH	J £55
28" Thomson widescreen	W66EGV, W66EJU	£85
28" LG widescreen	W66QBD	£85
28" Philips widescreen	W66ECK, W66ESF	£160
29" Philips standard	68ESF	£135
32" Thomson widescreen	W76EDX	£120
32" Philips widescreen	W76ESF	£245

All prices include carriage but are subject to VAT

We also de-scratch tubes

EXPRESS TV

The Mill, Mill Lane, Rugeley, Staffs WS15 2JW

Tel: 01889 577600 Fax: 01889 575600



20% discount for TV readers

digimess ® oscilloscopes from £109.00 inc vat & del



Vann

Draper

Electronics Ltd

The test & measurement specialists

www.vanndraper.co.uk

Test equipment from Grundig, digimess®

Vann Draper is offering over 20% discount to readers of Television magazine on their new range of digimess ® analogue oscilloscopes, prices shown below include discount.

The range consists of a 10MHz single channel as well as 20, 40 and 60MHz dual channel types. Triggering modes are Auto, Norm and TV, with the 40 and 60MHz versions also including PP Auto triggering. Z axis inputs & input delay lines are provided on the 20, 40 and 60MHz types and all models are supplied complete with mains lead, operating manual and a 1 year guarantee.

Model number	M010	M020	M040	M060
Price (inc vat & del)	£109.00	£289.00	£459.00	£649.00
B/W & no of CH's	10MHz single	20MHz dual	40MHz dual	60MHz dual
Accelerating voltage	1.3kV	2kV	14kV	14kV
Screen size 8 x 10	1 div = 6mm		1 div = 10mm	
Vertical (3%)	5mV - 5V/div		5mV - 5V/div	
Vertical mode	CH1	CH1, CH2, AL	T, ADD, CHOP,	INVERT CH2
Horizontal (3%)	0.1S - 0.1uS/div		0.5S - 0.2uS/d	l <mark>i</mark> v
Dims (cm) & wt	22x27x9, 3kg		32x42x13, 6.5	kg

To order, simply post the coupon to: Vann Draper Electronics Ltd, Stenson House, Stenson, Derby DE73 1HL. Or Tel 01283 704706 Fax 01283 704707 Email sales@vanndraper.co.uk Web www.vanndraper.co.uk

Use this coupon for your order

Please supply me:

.....(Price) (Qty) . . . (Model) (Qty) . . . (Model) (Price)

Address:

Tel No

Total C

Cheques payable to Vann Draper Electronics Ltd or debit my Visa, Mastercard or Switch card:

Card type:

Card No:

Switch iss No: Expiry date:

Signature:

Overseas readers can still obtain this discount but carriage charges vary according to country. Please telephone, fax, email or write to Vann Draper.



S.V.G.A II

NEW! SVGA II now has a slimline case, 9 display outputs at 640°480, 800°600 & 1824°768. Colourbars, crosshatch, dot, black, red, green, blue, white and flashing white patterns. Test and set-up computer monitors without a PC. 15 way D type output, runs on 8-12V DC adapter and be built in a couple of hours.

New lower kit price of only £29.5∅.

Can be supplied in PC Bone or Black case. Software upgrade available for original SVGA generator.



MULTIGEN VIDEO GENERATOR

From the Author of SVGA generator and Videogen comes a new all in one unit. Ten display outputs in PAL, NTSC & VGA of testcard, colourbars, grayscale, crosshatch, centering, red, green, blue, white and flashing white. PAL 625 lines 50Hz - NTSC 515 lines 60 Hz, Composite & S Video outputs - VGA 648°488 68 Hz, 15 way D - AUDIO 1 KHz Phono output. Unit can be powered via 8-12V DC adapter, 2 AA alkaline or rechargeable batteries

Full kit of parts to build the Multigen, £58 or £62 including 1.6A/hr NiMH Batteries.

Based on a 50 mips Ubicom Scenix micro running software routines to create fully interfaced test patterns. An Analogue devices AD722 chip persons the RGB conversion giving a IVolt signal into 75 chm termination. A DC DC converter power supply enables just 2 AA cells to power the Multigen. Audio tone output is a sine-wave generated by a wien bridge oscillator circuit with a buffered output. The kit comes with a high quality double sided PCB with ready programmed micro and AD72.2 chip ready soldered. All components including case, self adherive overlay, drill template and full construction details are supplied in the kit. Only soldering of components to PCB and drilling, filling of plastic end panels is required to construct Multigen.

The unit can be built in three to four hours. Visit our Website for circuit diagrams, layout details and actual screen shots of the different

patterns produced.

Note: Micro can be re-programmed onboard for future software upgrades. Now availlable in PC Bone or Black case, please state when ordering.



Please add £2 postage to all orders, £3 for overseas orders. Send cheque, Postal Orders or International Money Orders to J Harding, 43 Jonathan road, Trentham, Stoke-on-Trent, Staffs, ST4-8LP England. Comming soon, D-G/N a PAL 512*288 digital pattern generator with 3:4 / 16:9 Testcards & Scart RGB output.

that are recharged via adapter.

For more information on these two kits and future products, send S.A.E. or.

Visit our website "http://www.videocorner.co.uk" or Email us at "roy a videocorner.co.uk"

Repair SMDs on PCBs in seconds with the NEW Hot Jet'S'

Desoldering and soldering of SMDs by hot air and without contact is the fast and efficient way for the modern repair workshop. And now, Welwyn Tool can offer the complete package - a range of hot air tools, SMD Rework Stations, nozzles to suit all SMD requirements, free demonstrations and free colour instructional brochure ... all available from Distributors nation-wide.

For further information, please ask for Reference No. TMS

WELWYN TOOL CO.LTD.

4 SOUTH MUNDELLS, WELWYN GARDEN CITY HERTS AL7 1EH. TEL: (01707) 331111. FAX: (01707) 372175.

PUT HOT AIR TO WORK FOR YOU

ONLINE SHOPPING CHEAPER AND EASIER

www.elclondon.co.uk

TV, VIDEO SPARES AND ELECTRICAL ITEMS



ELC EAST LONDON COMPONENTS 63 PLASHET GROVE, LONDON E6 1AD.

TWO MINUTES WALK FROM UPTON PARK TUBE STATION TEL: 020 8472 4871 FAX: 020 8503 5926

E-mail: sales@elclondon.co.uk



lectronicworld

Our HUGE product range has HUNDREDS of models, most of which are NEARLY NEW.

You'll find EXCELLENT QUALITY with the very latest style in HOME ENTERTAINMENT and the ultimate range of PREMIUM BRANDS.

Our prices, we believe CAN'T BE BEATEN.





Electrical Goods at UNBEATABLE Prices...





See our new awesome web site. Just click on the wholesale link to view just a small sample of our stock.









All prices are Exclusive of VAT BIRMINGHAM

208 Bromford Lane. Erdington, Birmingham B24 8DL

Tel: 0121 327 3273 Fax: 0121 322 2011

LONDON

221 Kenton Road, Middlesex HA3 0HD Tel: 020 8907 9387

PRESTON


Unit 434 Ranglet Road, Walton Summit, Preston PR5 8AR

Tel: 01772 316066







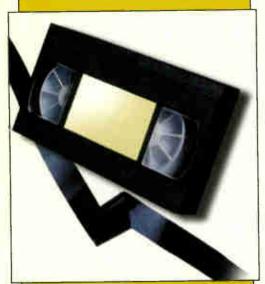

VCR CLINIC

Reports from
Bob Flynn
Graham Richards
Andrew Duggan
Gary Laidler
John Coombes
J.S. Ogilvie
M.J. Abbott
and
Mark Tyerman

We welcome fault reports from readers — payment for each fault is made after publication. See page 40 for details of where and how to send reports.

Ferguson FV62 (R2000 mechanism)

There was no wind or rewind, though sometimes these functions would start then stop. All other functions were OK. The cause was traced to wear on the main brake lever (item K156) – it was worn underneath, where it contacts the clutch unit. Replacement cured the fault. The Ferguson part no. is 70420433. B.F.

Sony SLV-SE700 (5 mechanism)

This VCR was dead with the input fuse blown. The cure was to replace the four 1N4005L bridge-rectifier diodes and the 2SK3047 chopper FET, which was very leaky. The TDA16846 chopper control IC was OK. B.F.

Hitachi VTM230E

The half-loading arm (item 256) was sticking on the cam gear underneath it. The reason for this was not obvious, but was found to be that the pinch roller was not secure on its shaft because the plastic sleeve had a split in it. **B.F.**

Toshiba V856B

The playback picture had spots in the background, the same as you get when the deck earthing is poor. Replacing CP051 (1μ F, 50V) in the power supply cured this fault and also improved the display brightness. While I had the power supply out I also replaced CP041 (220μ F, 10V) which causes dim displays, and CP007 (10μ F, 50V) and CP008 (100μ F, 25V) which cause no-power problems. **B.F.**

Saisho VR1200HQ/Matsui VX820

If the machine is dead with no clock display, though the standby LED lights briefly, go straight to the clock PCB and remove the five or six blobs of brownish glue, especially the one near the reset chip IC602. For no tuning check whether D2584 is open-circuit. **G.R.**

Sony SLV315

For full display illumination that's possibly intermittent, with maybe a whistling sound, remove the rewind/forward wind rotary-control assembly and dismantle it carefully. Clean the tracks and pins and reassemble. **G.R.**

GoldStar RC7031

This Nicam/VideoPlus VCR produced just a blue screen, with an occasional negative-looking picture appearing in the E-E mode. A check on the electrolytics C707 ($4\cdot7\mu$ F) and C727 (220μ F) proved that they were faulty. The repair was completed by replacing the video coupling capacitor C710

 $(47\mu\text{F})$ and the 12V supply decoupling capacitor C711 $(47\mu\text{F})$. G.R.

Sony SLV-SE70

There was no RF output/loop-through and no AV output. The cause was traced to Q607, which was dry-jointed. It's mounted on the print side of the PCB, near the power supply plug/socket CN600. G.R.

Ferguson FV81LV

The clock display could hardly be seen and dimmed even more when a function was selected. CP041 (220 μ F, 10V) in the display heater feed circuit was virtually opencircuit. While I had the power supply out I replaced the 10μ F and 100μ F electrolytics on the primary side as a precaution. G.R.

Akai VS66EK

The complaint was tape jammed with the loading motor running, also patterning in the E-E mode. After clearing the mechanism jam I scoped the 6V supply and found that there was lots of noise present. Replacement of the following electrolytic capacitors restored normal life to this machine: C1 (2,200 μ F, 35V), C6 (100 μ F, 25V), C15 (220 μ F, 35V), C24 and C25 (both 47 μ F, 25V). G.R.

Sanyo VHRH900E

This VCR was brought in with a tape partially loaded. When the tape had been removed the machine appeared to work normally. It was put on soak test, and after some time failed again. The tape was once more removed but this time, while the deck was finishing the loading cycle, it seemed to slow down. A new loading motor cured the problem. As a precaution, a new mode switch was also fitted. A.D.

Samsung SV209B

This machine chewed tapes and was very noisy in the FF/rewind modes. Removal of the gearing and idler assembly required some care. I then found that the centre gear was cracked.

This VCR uses the same deck as the **Toshiba V209UK** and other models. The centre gear is part no. BY730111. It's available from SEME. A.D.

Toshiba V703

This VCR's display was very dim. The customer wanted it fixed for sentimental reasons. Fortunately the state of C810/C813 gave the game away. They were leaking badly but hadn't damaged the print. G.L.

Hitachi VTM620

The complaint with this machine was that the E-E sound was missing at switch on.

The owner explained that it used to come on after a minute but now took ten minutes. So out with the hairdryer and freezer, which led me to the culprits – C407 and C411. G.L.

Philips Turbo deck

If tape playback is very jittery and the take-up spool is very jerky, fit service kit 1. It contains the changing gear, double gear and gear pulley. J.C.

Panasonic NVSD200 (K deck)

If one of these machines won't accept a tape, or intermittently won't do so, check the take-up sensor for dry-joints. J.C.

Samsung SV421

Tape chewing can be caused by a worn pinch roller of faulty mode switch. In this case however the idler assembly was tight. J.C.

Toshiba V631UK

A 'clicking noise' was the complaint with this machine. It seems to be quite a common problem with a number of Toshiba VCRs or, in some cases, the symptom may be a jammed mechanism that prevents loading. The cause of all this is a

guide post that breaks off – the symptom depends on where the post lands. Its part no. is AC61-00122A. J.C.

Panasonic NVHD625 (K deck)

If there are loading problems or no FF/rewind etc. check the main lever unit, part no. VXL2307. It has a habit of cracking at one end. While you have the machine apart, check the loading-motor coupler (part no. VDP1434 or SEME VDC7540) for any signs of cracking. If in doubt, replace it. Also clean the mode switch. This will sort the machine out. **J.S.O.**

Sharp VCM27HM

This machine produced a blue screen in the playback mode, but the picture was OK in the FF rewind search modes. On close inspection 1 could see that the top edge of the tape was being creased, as a result of which it rode up on the audio/control head. A replacement pinch roller put this machine back in working order. J.S.O.

Panasonic NVHD100

If there is no display check Q1701 (2SD973A-R) on the front display PCB. It tends to burn out. A BC337 can be

used as a replacement. J.S.O.

Sharp VCA63HM

If the power supply is squealing replace C913 (47 μ F). **J.S.O.**

Philips VR6547/05

The complaint with this VCR, which is fitted with a JVC deck, was tape chewing. The cause was a faulty clutch assembly. This can be obtained from CPC under order code VSID469. The Konig 1493 will fit, but the pulleys have to be swapped. M.J.A.

Toshiba V720UK

This machine wouldn't play tapes because there was no take-up. The boss on the gear centre assembly was cracked. Part no. is BY730111. M.J.A.

Goodmans TVC146

The fault with this TV/VCR combi unit was no power. I found that the power switch SW08 was dry-jointed, ready in fact to fall off the board. M.T.

Ferguson FV44

This VCR had a very dim display. Replacement of C28 cured the fault. M.T.

Test Case 491

Test Case Rentals does not claim to have the richest clientele in the world. The situation is quite the opposite in fact, and prepayment meters, bread-and-butter TV sets and a diminishing number of VCRs are the stock-in-trade: exotica such as plasma screens figure hardly at all in the inventory. There are a few score Sony SLV-SE720Gs amongst the VCRs rented out, and the common problem that arises with them, data corruption in the EEPROM, is well known to the workshop crew.

The effects of this fault, apparently brought on by incorrect marking and insertion of an electrolytic capacitor during production, are most often lack of any display on the front-panel indicator, incorrect functions when the on-board control keys are used, and various picture and sound problems during playback. The cure is to replace the now-faulty capacitor, C701, which is usually distressed and bulging as a result of its reverse-voltage ordeal, and to reduce the value of resistors R668 and R669 from $10k\Omega$ to $4.7k\Omega$. In some cases it is also necessary to replace IC701 on the motherboard, though we haven that to do this so far. Then, once the option bytes in the memory chip have been programmed correctly, all should be well. This has been our experience — until now!

Sage was not at all fazed then when a similar Model SLV-SE820G came in with the familiar symptoms described above. After replacing the capacitor and the two resistors he reassembled the machine, fired it up and pressed the record key, smartly followed by a five-second dwell on the zapper's menu key. The TV screen then produced the options display, in which the selected bytes appear highlighted. As is often the case, only two or three of them were shown in this way, and Sage set

about programming the numbers. Having had to use them a number of times before, he had them listed in his little benchside notebook: 3-14 inclusive, 19, 27, 33-35, 40, 41, 45, 47, 51, 60, 61, 63, 66, 69 and 72.

These were all banged in and then memorised with a stab on the zapper's menu key. The machine was next switched off and on again to reboot, after which the auto-setting of the head-switching point was invoked by keying 'test' (a concealed button behind the VCR's front panel) then SP/LP on the zapper – with an alignment tape playing. This setting is also stored in the EEP-ROM. All done then! Sage checked the picture and sound with his *Snow White* tape, made a quick test recording, then turned to the paperwork . . .

The machine went back to the customer next day, and no more was heard of it until after the weekend. Then Sage was summoned to the reception counter, to be confronted by the Sony machine's owner. He was brandishing the VCR in one hand and its instruction book in the other. Sage had mucked the VCR up, it was alleged. Since the machine had been returned, its dial-timer had not worked! Sage, muttering apologies, crept back to his bench with the machine, then consulted the instruction book to discover what the dial-timer was supposed to do. Set a timed recording, that's what. It did nothing at all when it was tried.

Sage was convinced that the cause was simply failure to reconnect the front-panel's ribbon cable during reassembly. Was this the case, or had the little jog-control mechanism been damaged perhaps? Sage delivered the machine in person later that day. What had ailed it? For the solution (think first!) turn to page 57.



Reports from Michael Dranfield Philip Salkeld Glyn Dickinson Les Mainstone **Andrew T. Duggan** Martin Cole Ian Turnbull **Jerry Fedorak Dave Husband** Martyn S. Davis and **Steve Hague**

We welcome fault reports from readers - payment for each fault is made after publiation. See page 40 for details of where and how to send reports.

TV FAULT FINDING

Grundig 28EKB-T70-1020A (Professional 2500 chassis)

This newish set was dead. When it was switched on from standby the green LED lit up but nothing else happened. Not having seen one of these sets before I was quite pleased to find a large, blackened dry-joint at the line scan coils socket. But the set remained dead after resoldering this joint, and the power supply was up and running. Scope checks around the line driver FET (TL1) showed that gate drive was present but there was nothing at the transistor's drain. Nor was there any voltage at the drain connection to the driver transformer. At this point I was stuck, not knowing the set. Fortunately the local Grundig dealer lent me a manual, and I then found that a surface-mounted BAV203 diode (DL2) between pin 3 of the driver transformer and chassis was shortcircuit. M.D.

Ferguson ICC5 chassis

As this old set used to provide such excellent pictures its owner gave the goahead for repair at up to £40. The picture was very ragged, as if there was a dried up electrolytic capacitor across the HT supply. But I found that tweaking the EW potentiometer cured the trouble. Unfortunately the picture then lacked width, so it was obviously not a power supply problem. Further investigation showed that CG01 (10µF, 50V), which is

connected to pin 6 of the TDA4950 EW chip IG01, had dried out.

A replacement capacitor cured the raggedness, but the EW control now did nothing. At this point I noticed that with the new 10µF capacitor fitted the TDA4950 chip was getting very hot. A replacement IC restored normal operation. M.D.

JVC AV28WFR1EKS

The problem with this set was field collapse. But there was a wavy instead of a straight line across the screen. The last time I'd seen this symptom was with a set fitted with the Thorn 9000 chassis! The cause had been a dry-joint at the earthy end of the field scan plug/socket: the field collapse was being modulated by the line scan coils.

But no dry-joints could be found this time, and a resistance check showed that the field scan coils were open-circuit. It seemed that a new tube would be needed but, with nothing to lose, I decided to heat up the solder joints on the yoke and flow some fresh solder on. This provided a complete cure. Also a good tip from the customer - a 24-can case of Stella lager who thought he was going to have to shell out for a new tube! M.D.

Thomson 32WX65US (ICC19 chassis)

There was no luminance though the OSD was OK. A scope check showed that the luminance signal was missing at pin 4 of IV001, so the cause of the problem was on the digital signal module, which is difficult to get at. The luminance signal passes through five ICs and a handful of surfacemounted transistors on this module. It's not easy to carry out scope checks on the module, but I eventually found that there was a luminance input at pin 26 of IV601 (TDA9143) but no output at pin 12. A replacement IC cured the fault. M.D.

Toshiba 28W93B (C8SS chassis)

This set was stuck in standby though 125V was present at the HT fuse F470 in the power supply. After finding nothing wrong in the line output stage I returned to the power supply to check the LT rails and found that there was no voltage at pin 21 of plug 813A. Tracing back from this I discovered that R430 (56Ω, 0.5W) was open-circuit and that there was a shortcircuit at the emitter of Q430. The cause of the trouble was the 0.01 µF disc ceramic capacitor from this point to chassis, C431. It was short-circuit. A new capacitor and resistor restored normal operation. P.S.

Goodmans 285NS

These sets always seem to come in dead because the line output transformer has

been arcing, as a result of which the output transistor blows. SEME can supply the transformer, under code no. HR7927. On this occasion however the set was still dead once these items had been replaced. There was HT at C805, the mains bridge rectifier's reservoir capacitor, and at pin 1 of the STR5707 chopper chip 1801, but there were no other supplies. I decided to carry out a resistance check between pins 2 and 4 of 1801, and discovered that they were short-circuit. A replacement restored normal working order. P.S.

Tatung T28NE51 (E chassis)

I was called out to this set, the complaint being no sound. When I tried the remote-control unit I found that the green cursor which shows the volume level remained at zero. The brightness, contrast etc. all varied. So the sound was locked. To release it you press vol+ on the set and at the same time press the mute button on the remote-control unit. After doing this the sound returned and could be adjusted normally. **P.S.**

Beko 16328NX

This oldish set had a vertical shift problem, i.e. a black line that was well up from the bottom of the screen. Use of freezer revealed the culprit, which was R725 (150k Ω , 0.5W). A long soak test after fitting a replacement confirmed that this resistor had been the cause of the fault. **P.S.**

Samsung Cl6844N

In most cases replacement of the TDA8350Q field and EW output IC will cure field faults in these sets. However you will sometimes find a side effect, flyback lines at the top of the picture. To clear this fault replace R307 (10Ω , 1W). P.S.

Beko NR28426NDS

If you come across a dead set and the cause is not the sand-filled fuse, go straight to the BU508D line output transistor T504. You will find that it's short-circuit. Don't replace it until you have fitted a new line output transformer (TR502), because this will have been arcing. As this set was in warranty the replacements had to be ordered direct from Beko, **P.S.**

Grundig ST82-774 (CUC7890 chassis)

This monster seemed to be dead apart from the fact that the front display was illuminated. Investigation showed that the HT and LT supplies were present. When I moved to the line output stage I found that there was no drive. These sets use a

TDA8140 line driver chip, IC526. Checks here showed that there was an input from the line generator at pin 7 (what a relief!) but no drive output at pin 1. A replacement IC restored normal operation. The next problem was to get the set off the bench. What a weight! P.S.

Philips Anubis AA-5 chassis

The report with this 21in. set said "crackling then dead". Seeing a dreaded triangle on the line output transformer's label I replaced it. The result was a tripping set, though all the supply voltages were correct. Line drive was present, but at very low amplitude – the TDA8361E jungle chip had been dealt a mortal blow. A replacement restored the EHT, and revealed field collapse! A new TDA3654 IC brought the picture back. I wonder how loud that "crackling" had been?

Note that this chassis differs from the Anubis A, which has a different jungle chip. G.D.

Grundig \$770-755/9 (CUC6460 chassis)

This set was dead though there was 330V at the mains bridge rectifier's reservoir capacitor C626 (220 μ F). This item is followed by a DC Wickman fuse, Si624 (1.6A), which was open-circuit. I also noticed that there was a bad dry-joint at C648 (470pF, 1.6kV), which is in parallel with the chopper transistor T644. I replaced the latter (IRFBC40) and IC631 (TDA4605/03), also C648 and, as a precaution, C633 (100 μ F, 25V) and C661 (1 μ F, 63V). A new fuse completed the repair and, at switch on, the set sprang to life, L.M.

Philips 29PT727B (GR2.4 AA chassis)

This set had a faulty line output transistor (BU2520AF) and transformer. I gave the customer an estimate, which was accepted. Fortunately it allowed some leeway for unforeseen eventualities. When the transistor and transformer arrived they were fitted and the EW modulator diodes D6546 (BY228) and D6547 (BYW95C) were replaced. After a quick check around the line output stage for anything else amiss I switched the set on. Result, a flashing front LED.

After the customary expletive, I isolated the line output stage and provided the power supply with a dummy load. It declared itself very happy. So attention was redirected to the line output stage, where I found that F1534 (315mA) was open-circuit. This led me back to the EW drive circuit, which is on the CRT base panel, and opened a can of worms.

Tr7533 (BD440) was short-circuit, so this and the two surface-mounted transistors Tr7530 and Tr7537 (both type BC848B) were replaced. I also replaced two diodes, D6560 (LL4148) and D6561 (BZX79-C68), which provide a feed to the protection circuit. The BZX79-C68 diode had tested OK with my equipment. After that the set was fired up, voltage checks were carried out and the set was boxed up. After five hours on the soak test bench it died again, with a thin squealing sound. At this stage I contemplated a plumbing course.

Off came the back and out came the chassis. This time I found that the bulky scan-correction capacitor C2550 (680nF, 250V) was the culprit, with a short-circuit reading. I assume that it had failed as a result of stress from the previous problems. L.M.

Samsung CI5337AN (US60A chassis)

This set, with its excellent, usually trouble-free chassis, arrived with a note to say that it did odd things at odd times, sometimes flashing and the text not working. Two of the diodes in the mains bridge rectifier circuit, D801 and D802 (type 1N4003), showed signs of overheating, so replacements were fitted. They are on the larger of the two PCBs. When the set was switched on it produced a blank raster, with no signs of any audio or video. I was suspicious of the two 12V regulators IC801 and IC802, but replacements made no difference. The culprit turned out to be the 5V regulator IC804 (MC7805). Once this had been replaced the set worked and, after retuning, behaved itself with normal text. L.M.

Grundig CUC2030 chassis

"Turns itself off when my back's turned" claimed the elderly lady customer. When I took the back off and removed the chassis I noticed a number of dry-joints on the secondary side of the power supply. These were repaired and the set was switched on. All the supply-line voltages were checked and found to be correct, so the chassis went back into the cabinet. When the set was switched on it was dead! Out came the chassis again and, after much twisting and tapping, a dry-joint was found at C53009. Dealing with this cured the erratic shut down. L.M.

Philips 25PT4494/05 (L6.3 AA chassis)

At switch on this set produced a raster but no sound. The front and remote controls produced no response, and there were no signs of any graphics. A check on the outputs at the secondary side of the power supply showed that the 5V rail was at only 0.2V. This led to a check on transistor Tr7505 (BC337-40) which was open-circuit. A replacement cured the fault. L.M.

Daewoo DVT1482P

This combi unit was dead with no illumination from the standby LED. After some attempts the LED did light, but when Power was pressed the unit just tripped and died. While making a few checks in the power supply I noticed that C811 ($100\mu F$, 16V) was almost touching the heatsink for the chopper transistor Q801. As a result it had dried up. A replacement solved the problem. A.T.D.

Bush 1433 (11AK20M chassis)

This set was dead with a short-circuit chopper transistor – Q801, type 2SK2750. Checks revealed that in addition the following were either blown or short-circuit: R851 (0·33 Ω), R801 (2·2 Ω , 5W), R819 (0·47 Ω), R812 (1k Ω , surface-mounted) and D808 (BA159). Just in case, I decided to replace the MC44603AP chopper control chip IC801 as well. After that the set ran perfectly. **A.T.D.**

Philips LO1.1E chassis

If you get a loud mechanical noise as soon as the set is switched on from the mains, the degaussing coil is vibrating/rattling on the CRT's rimband. To cure the fault all that's required is a spot of hot-melt glue to keep the coil away. M.C.

Hitachi C32WF523-311

This flat-screen set would switch to standby after a few seconds. Checks revealed the cause to be loss of the first anode supply, because of a fault within the CRT. The tube fitted was an LG type W76QDD259X. I.T.

Philips 25PT4521 (MD1.1 chassis)

There was no picture because of field scan failure. I found that the -15V supply, which is derived from the line output transformer, was missing with circuit protector CP1463 (800mA) open-circuit. The cause of this was transistor Tr7440 (BC327), which was short-circuit, and diode D6440 (1N4148), which was leaky. These two components are mounted on a small sub-panel. I.T.

LG KE14U73

Very intermittently this combi unit's picture would disappear with motorboating on sound. In the fault condition all the main supply voltages dropped significantly. The cause was a

dry-joint at R811 in the current-sensing part of the power supply. I.T.

Hitachi C2142N

The complaint with this set was loss of red, because of failure of the TDA6108 RGB output chip. A modified CRT base PCB is available from Hitachi to prevent repeated failure. The part no. is VS20089197. I.T.

Panasonic TX21GV1

The sound would sometimes disappear when a cassette was inserted in this combi unit. The cause was traced to dry-joints at C613 in the audio circuit on the VCR PCB. I.T.

Proline 28N1

This set was stuck in standby. When the remote-control unit was used to bring it out of standby the power supply would whistle then go back to standby. Cold checks in the power supply revealed that C25 was dry-jointed. Once it had been resoldered the set came back to life with good results. J.F.

Minato ST1411

This 14in. colour portable was dead. Checks in the power supply revealed that R502 ($100k\Omega$), one of the start-up resistors, was open-circuit. In addition there was a dry-joint at C506. Once these points had been attended to everything was OK. J.F.

Grundig W70-2030

This one-year old widescreen set was brought in because it was dead. The standby LED at the front would sometimes light up. Visual checks in the power supply area revealed the cause of the trouble, dry-joints with arcing at plug R629 to the transformer (mounted at the corner of the cabinet). Normal operation was restored by resoldering the plug. J.F.

Wharfedale 550S (PT92 chassis)

Two of these sets required attention on the same day. The first one produced a rustle of EHT at switch on then shut down. Checks in the line output stage revealed a diode that looked as if it had nipped outside and spent too long in the sunshine. Sure enough it read 22Ω . That was the easy one.

Set two seemed to have a blanking fault – the picture was cutting out about once a second, though the sound and teletext were OK. So I dusted off the scope and ordered a service manual. After much wasted time checking waveforms and voltages I decided to enter the service mode (press sub-page on the remotecontrol unit and volume down on the set)

to find out what was inside the micro. I discovered an item marked CL (cathode drive level), for which the manual suggested a setting of 4. It was actually at 8. To be on the safe side I set the level to 3. After that all was well.

Note that this chassis is used in the **Bush Model 2876T** amongst others. **D.H.**

Philips 25PT4523 (MD1.2E chassis)

This set was dead with its input fuses blown. It didn't take long to spot the cause. A small, blue high-voltage capacitor, C2540, had blown itself in half. This 220pF capacitor is connected in parallel with the chopper transistor. Its failure had taken out the big cement resistor and two of the mains bridge rectifier diodes.

For good measure I replaced the chopper FET, all four mains bridge rectifier diodes, all three HV capacitors and the large 1Ω anti-surge resistor. I was then rewarded with the satisfying sound of EHT rustling up and a working set. M.S.D.

Philips 32PW9544 (MD2.25E chassis)

There was a degree of urgency associated with the repair of this large, expensive dead set. When the customer arrived to report the fault she apparently became hysterical then abusive – to the extent that the police had to be called in. She then phoned our various managers to offer them her views, and followed this with a four-page letter to our MD. So it was a chance for me, the lowly engineer, to shine and retrieve the situation.

On investigation I found that the chopper FET was short-circuit and the control IC had a short-circuit diode and open-circuit resistor connected to pin 3, which drives the FET. The following items were replaced: Tr7541 (STW9NA60), IC7520 (MC44604), D6524 (BYV10-20), R3524 (10 Ω), R3546 and R3547 (both 0-39 Ω). Once this had been done there was the sound of EHT to confirm that the repair was successful. Phew! M.S.D.

Hitachi C2142 (11AK19 chassis)

I have not come across this model before – it didn't look like a Hitachi set. The reported fault was no sound. When I took the back off I was a little surprised to find a Vestel 11AK19 chassis. Not that I mind: it's relatively predictable, and easy to work on. A few quick checks revealed that pin 2 of the TDA2614 audio output chip was being held low. This is the mute pin, which is controlled by transistor Q100 (BC548B). When it was tested this transistor proved to be leaky. A replacement restored the sound. S.H.

SPARES & REPAIRS

SPECIALISTS IN ALL MAKES AND MODELS OF SATELLITE EQUIPMENT

ECHOSTAR / TECHNOMATE / HUMAX / MANHATTAN
GRUNDIG / PANASONIC / PACE / AMSTRAD

SAME DAY COLLECTION FROM MAINLAND
UK ADDRESSES - BOOK BEFORE 1PM

LARGE SELECTION OF REFURB BOXES COMPLETE
WITH 12 MONTHS WARRANTY AND
NEW ACCESSORIES

SPARE PARTS FOR DIGIBOXES - NEW AND USED - POWER SUPPLY UNITS, TUNERS, MODEMS, RF SOCKETS, BGA'S AND CHIPS

WE ALSO STOCK COSMETICS FOR ALL DIGIBOXES

TO SDS!



SILVER PACE 2200 DIGIBOXES

DISCOUNTS ON QUANTITIES



1 HOWARD AVENUE BARNSTAPLE DEVON EX32 8QA TEL: 01271 325888 FAX: 01271 329163 chrissds@hotmall.com



Campion Electronics Ltd.

SUPPLIERS OF QUALITY EX-RENTAL TV'S

and video equipment to independent retailers across the UK and EIRE.

FREE DELIVERY SERVICE

to most areas of UK

WORLDWIDE EXPORT SERVICE

Large stock of TVs suitable for export Experts in UHF/VHF conversion

Visit our large warehouse at:

Units 1 & 2 Tenat Works, Worcester Rd, Kidderminster, Worc, DY10 1JR

Tel: (01562) 746000 (2 Lines)

Just 20 miles from Birmingham City Centre



Largest selection of

MAJOR MANUFACTURERS NEW "B" GRADE PRODUCTS

T.V. VIDEO AUDIO MICROWAVE OVENS

Contact Paul Bean

BSMART (CRAWLEY) LTD. 10/11 LLOYDS COURT, MANOR ROYAL, CRAWLEY, SUSSEX RH10 2QX

> Tel: (01293) 618000 Fax: (01293) 400133

MEB SERVICE

To reserve your web site space telephone Tel: 01322 611292 Fax: 01322 616376 E-MAILS r.gurunlian@highburybiz.com



Alban Electronics

http://www.albanelectronics.co.uk

Alban stocks, supplies and provides technical support for a range of terrestrial/cable/satellite and analogue/ digital TV equipment. PROMAX (manufacturers electronic test equipment including signal level meters, spectrum analysers, BER/CSI/MER analysers for QPSK, QAM & COFDM, optical fibre light sources and power meters, 16:9 test pattern generators), ALCAD (manufacturers of R.F. wide band and adjacent channel amplifiers, aerials for MATV, SMATV & IRS systems) and ANTARES (cascadeable multi-switches) ALBAN has a complete after sales repair and calibration service that is fully supported by the manufacturers, in addition provides a free system design service using only reliable high quality components.

Alltrade Aerials & Satellite Ltd

http://www.alltrade.co.uk Leading distributor to the trade



Full e-commerce site with over 1500 products with in-stock quantities!! We supply everything associated with Digital/Analogue Terrestrial & DTH/Motorised Satellite reception. All Antennas. All Brackets. All Cables. All Connectors. All Amplifiers. We provide a free MATV/SMATV planning service as well.

Phone 0845 075 0751 Fax 01273 425700


Cricklewood Electronics

http://www.cricklewoodelectronics.co.uk


Cricklewood Electronics stock one of the widest ranges of components, especially semiconductors including ICs, transistors, capacitors, resistors. all at competitive prices.

Charles Hyde & Son Ltd

http://www.charleshyde.co.uk

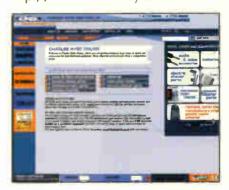

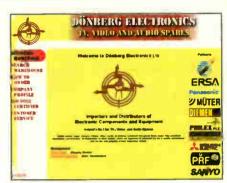Search for both original and copy spare parts in our extensive database covering Akai, Alba, Bush, Ferguson, Goldstar, Hitachi, LG, Matsui, Nokia, Saisho, Sanyo, Sony, Sharp, Thomson, Panasonic, Philips, Samsung, Tascam, Teac, Toshiba, Yamaha and many more. In addition huge ranges of Lasers, Lopts, Remote controls and Semiconductors may be accessed.



Dönberg Electronics

http://www.donberg.ie

http://www.donberg-electronics.com

http://www.electronic-spare-parts.com

As the leading distributor for the TV, Video and Audio trade in Ireland, we supply over 2000 shops & service dept with Audio-Video and TV spares, Semiconductors, Test Equipment, Service Manuals, Remote Controls etc. At present we stock over 35,000 different lines. We hold agencies for: Panasonic, Sharp, Mitsubishi, Sanyo, Beko, Ersa, Müter, Diemen HR, Philex, PRF, Königelectronics. We specialise in parts for all continental sets and obsolete semiconductors.

J W Hardy Communications

http://www.jwhardy.co.uk



R.F. Network Specialist. Shop online - for R.F.network components. We supply a full range of TV, radio reception equipment to receive analogue/digital signals from both

terrestrial and satellite sources. We provide a free planning service for your R.F. networks, MATV and SMATV etc

Irwin Electronics

http://www.irwinelectronics.co.uk

As Classic Distributors we complement our existing mail and trade counter business with our website. You can order parts on-line quickly and easily. We intend to explore alternative ways of assisting engineers to run their business successfully.

MMWafercards

http://www.mmwafercards.com



Smartcards and programmers for all access-controlled applications. Incorporating www.satstore.co.uk
The Enthusiasts Satellite Store.
Tel 01386 48731 Fax 01386 765875

M.C.E.S.

http://www.mces.co.uk

The MCES site gives details of our range of service including Tuners, Video Heads, RF & IF Modules plus latest prices offers.



Swires Research


http://www.swires.com

Swires Research produce high quality instruments for the television industry, including portable signal level meters and spectrum analysers for digital and analogue RF signal measurements.

Televes

http://www.televes.com

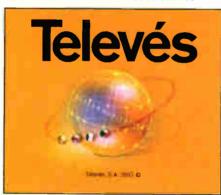Televes website was launched as an easier way to keep in contact with our World-wide Network of Subsidiaries



and Clients. This site is constantly updated with useful information/news plus you can download info on our range: TV Aerials & accessories, Domestic and Distribution amplifiers, Systems Equipment for DTT and Analogue TV, Meters and much more.

Wiltsgrove

http://www.wiltsgrove.co.uk



wiltsgrove LTD founded in 1984, is renowned as a leading supplier of Audio, Video, TV, Spare parts and Accessories.

We are now pleased to announce the launch of our ONLINE CATALOGUE:

http://www.wiltsgrove.co.uk

Our easy to use search engine will allow you to find the products you require via:

- Make / Model.
- Product Category.
- Key Word search.
- Manufacturers part number.
- Our Order Code.

All orders before 5pm will be dispatched the same day.

Tel: (0121) 772 2733 **Fax:** (0121) 766 6100 **Email:** sales@wiltsgrove.co.uk


Make sure of your copy of Television

It can be difficult finding a copy of *Television* at local newsagents. The number of magazines being published keeps increasing, which means that newsagents have less shelf space for the display of individual titles. Specialist magazines in particular get crowded out.

There's a solution to the problem. Most newsagents provide "shop-save" and/or home-delivery services. There's no charge for a shop save. You simply ask your newsagent to order a copy for you: it will be kept on one side each month ready for you to collect. Home-delivered copies are ordered in the same way, but generally incur a delivery charge.

A newsagent can order any magazine for you, whether or not the shop normally stocks it.

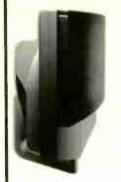If you buy your copies of *Television* from a newsagent and want to make sure you get every issue, just ask at the counter.



Installation Engineers Bang & Olufsen

wish to appoint a number of Installation Engineers to work with our exclusive stores throughout **Yorkshire*** and the **Midlands***

The position

As an Installation Engineer your primary role will be to:

- Professionally install Audio Visual products to the highest standards in our customers nomes
- Install multiple room BeoLink systems, distributing audio and video sources around the home
- Provide technical assistance to our Sales staff
- Extend the experience beyond the point of installation

Oualifications

We are looking for engineers with installation experience who understand and share the values of our brand. Above all we are seeking outgoing individuals who are focused on delivering excellence for our discerning customers

What we offer

An excellent salary package.

In addition to comprehensive product & installation training, we offer a challenging and rewarding role where you will have an opportunity to demonstrate the competences of the World's leading home electronics brand.

* Recruiting in SHEFFIELD - LEEDS - LEICESTER - PETERBOROUGH

Applications

If you feel you have the qualities & capabilities we are looking for to take up this exciting opportunity then please send your written application and CV to:

Mr Nick Hayes Bang & Olufsen Freepost NEA5589 LINCOLN LN5 7BR

www.bang-olufsen.com

BANG & OLUFSEN



POSSIBLY
LARGEST & DLDEST
EST. IN
THE UK EST FOR
3D YEARS

Wholesaler Distributors & Expert Agents of Domestic Electronics & Appliances

FULL RANGE OF FACTORY
GRADED TV'S DVD / VIDEOS
HI-FI SMALL & LARGE
DOMESTIC GOODS

TECHNICAL SUPPORT

Now Available

TV's, DVD's, VCR & AUDIO

Over 40 years of genuine experience

Experts on:-

Thomson • Sanyo • Beko • LG • Tatung • Ferguson

0907 076 70 80

Call cost 60p mi

MAIN DEALER

- **Thompson**
- Sanyo
- Beko







Tel: 0121 359 7020 Fax: 0121 359 6344

Phoenix House, 190 Bridge St. West, Newtown, Birmingham B19 2YT


Email: inquiries@colourtrade.com



Your connection to the digital future

MTD proudly announces the complete range of Fracarro products

Aerials

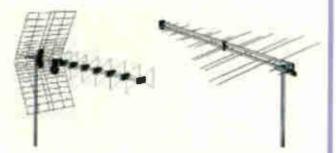

A wide range of aerials including the CAI benchmarked BLU420

RO.VE.R.




Test Equipment for digital and analogue

Dishes

A wide range of satellite dishes, including the Penta HQ range




Channelised Amplifiers

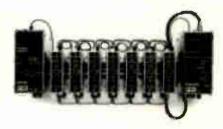


The leading K Series channelised amplifers for distribution of digital and analogue signals

Philips GII: The leading IRS Range



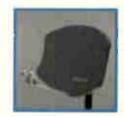

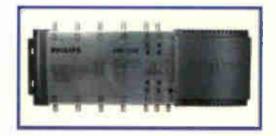

FRACARRO

Martin Turner Direct Ltd

Unit 16C, Severn Bridge Ind Est, Caldicot, Monmouthshire. NP26 5PT E-mail: enquiries@martinturnerdirect.co.uk Company registration No. 2885911

PHILIPS

Tel: 01291 421422

Fax: 01291 422701



view and make recordings of the transmissions (see Photos 1-3). Recordings of the signal on a hard disk gobble a massive 180MB a minute, which didn't give much viewing time when transferred to a standard 680MB CD! I found that playback of the CD was possible only with a fairly recent PC, using the Windows Mediaplayer or the Elecard software mentioned in the September issue article. Attempts at playing the disc with a PC that had less than a 2GHz processor resulted in picture and sound dropout. Definition with a computer monitor is very good, especially if the monitor is large and can



Photo 1: Euro 1080 HDTV test transmission.

SATELLITE

Reports from
Hugh Cocks
Christopher Holland
and
Michael Dranfield

High-definition TV tests

The European 1,080-line high-definition TV system is due to start a regular transmission schedule at the beginning of next year. More information can be found on the internet at www.euro1080.tv

There are 25 frames per second, with a horizontal definition of about 1,900 lines. Tests are currently being carried out via the Astra 1 slot (19·2°E), at 12,168GHz V (symbol rate 27,500, FEC 3/4). Conventional MPEG-2 satellite receivers will tune in the signal but because of the large amount of data transmitted to achieve this definition, about

NOTEBOOK

24.000Mbits/sec, they either crash under the data onslaught or show intermittent pixellated blocks on the screen. The best results I have obtained so far with a conventional receiver have been with an old Nokia 9600 box, which showed a zoomed-in top-left portion of the picture in 625-line format, though with intermittent picture and sound dropout.

PC-based satellite-receiver systems work much better. Using the TechiSat PC card system described in the September issue and a fast computer I was able to



Photo 2: Euro 1080 HDTV test transmission.



Photo 3: Euro 1080 HDTV test transmission.

Photo 4: White line dashes at the top lefthand corner of the screen with BBC1 regional transmissions, seen when these are displayed in the letterbox mode.



Photo 5: Nigerian NTA 2 caption received via Intelsat 903.



Photo 6: Nigerian NTA 2 news reader received via Intelsat 903.

be set to the highest-definition possible.

Some experimentation with the receiving software was necessary. The Prog DVB program mentioned in the previous article would record perfectly well but displayed some blocks with live pictures. DVB Viewer however gave the best-quality live pictures but wouldn't record properly! The programs sometimes had to be opened and closed once or twice for live pictures to be displayed, because an 'error' message appeared on the screen instead. The software was obviously not entirely happy about handling this amount of data.

At the time of writing this report the transmissions consist of an approximately one-hour long demonstration tape that shows clips of various live orchestral and operatic performances, with the Astra and Euro 1080 logos in the top right-hand corner. No doubt dedicated HDTV receivers will soon be available, if not already at a cost, and possibly fantastic picture quality will be achieved if the

Table 1: Latest digital channel changes at 28-2°E

Channel and EPG no.	Sat	TP	Frequency/pol
Arrow Radio (911)	2B	32	12-324GHz V
BBC1 Channel Is (958*)	2D	50	10-847GHz V
Factory Outlet (670)	2B	33	12-344GHz H
Paramount 2 (128)	2A	11	11-914GHz H
Pop Plus (620)	EΒ	C6	11-426GHz V
Vectone Urdu** (828)	EB	C10	11-644GHz H

TP = transponder. EB = Eurobird. 2A/B/D = Astra 2A/B/D.

- *BBC1 Channel Is will be on EPG 101 with viewing cards registered with in the region.
- ** Plus three Vectone test channels.

output is fed to say a large-screen plasma TV display. H.C.

Digital channel update

The latest channel additions at 28·2° are listed in Table 1. Where allocated, the EPG number is shown in brackets after the channel name.

ATN TV (EPG no. 827) via Eurobird transponder D12S has returned to the EPG after being off-air for several months.

RTE Radio I has been given EPG no. 910. This is the stereo version, which has been available for over a year via Astra 2D transponder 43 (10·744GHz H) using the digibox add-channels facility. The mono version of RTE Radio I (EPG no. 892) via Astra 2B transponder 32 (12·344GHz H) has been renamed RTE Europe, probably because of the much wider footprint of Astra 2B compared to Astra 2D. RTE Radio I has also recently started up via the good old-fashioned LW band, with a high-powered transmitter at 252kHz.

Ekushey TV (EPG no. 814) and Total Rock Radio (EPG no. 885) have ceased transmissions. C.H.

BBC1 regional oddities

I've noticed that the BBC! English regional variations all have a small time delay compared with BBC! London when transmitting national programmes. This is no doubt because the London output is sent to the regional studio and then returned.

When the digibox video output is set to 'letterbox' the regions all have a series of white line dashes at the top left-hand corner of the screen (see Photo 4). These seem to be the same whichever region is selected. The dashes are not present with BBC1 London. Scotland, Wales and Northern Ireland. I've also noticed that when a non-digibox receiver is used in the letterbox mode the dashes appear briefly after channel selection and are then suppressed. C.H.

Update at 34.5°W

The C-band channels available via Intelsat



Photo 7: Nigerian Minaj transmission via Intelsat 903.

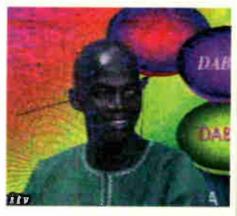


Photo 8: Nigerian MITV transmission via Intelsat 903.



Photo 9: Snell & Willcox widescreen test pattern with GTV 9 Melbourne identification received via Eutelsat W3.

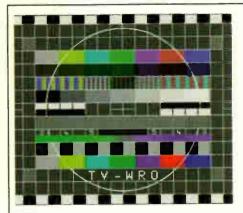


Photo 10: TVP (Poland) test pattern with Wroclaw identification received via Eutelsat W3.



Photo 11: British Telecom/NewSkies Satellites caption received via Eutelsat W3.

903 at 34.5°W were listed here about a year ago. Since then a Nigerian multiplex has become available at quite a reasonable signal strength. The frequency is 3.890GHz, with left-hand circular polarisation, a symbol rate of 16,300 and 3/4 FEC. TV channels are NTA 2 (see photos 5-6). MITV (see Photo 8) and Minaj (see Photo 7). Radio stations in the package are Cool FM, Ray FM, Rhythm FM and Star FM.

The MITV photo is of appalling quality. The signal appears to be picked up off-air at low strength complete with ghosts, the result being intermittent dropouts with the digital signal transmitted. It has been like this since I first started to take a look some weeks ago, with no attempt to improve the signal at the uplink site! H.C.

Unusual test cards

Continuing our series of unusual test cards and captions, Photo 9 is a very rare shot of a Snell & Willcox widescreen test pattern from the Australian TV station GTV 9 in Melbourne. It was transmitted prior to a Eurovision newsfeed via Eutelsat W3 (7°E).

Photo 10 is from state broadcaster TVP (Poland), again transmitted prior to a Eurovision newsfeed via W3, this time from the regional city of Wroclaw. I recall this Polish test card being transmitted via the terrestrial TVP network many years ago.

Photo 11 shows a British Telecom/NewSkies Satellites caption, again via W3.

The transmissions were at 11.043GHz, with vertical polarisation, a symbol rate of 6.665 and 7/8 FEC. H.C.

Pace 2200

This was a later version of the 2200 fitted with the ZIF tuner. It produced the 'no satellite signal received message'. The dealer who sent it to me said he had fitted a new tuner, but it looked more like a used than a new one. My first step was to check the installation menu, to confirm that the settings were all correct. I then removed the tuner and plugged it into my test rig. This confirmed that it was OK, so I refitted it and checked the tuning, 3·3V and 5V supplies, the serial clock and data lines, and the LNB supply. Everything seemed to be in order, but the digibox still didn't work.

I then realised that the 22kHz tone was missing from the LNB supply, though it was set to 'on' in the menu. The tone is generated by a pulse-width modulator within the ST20 housekeeping microcontroller chip U600, the tone output being at pin 142. It was present here. I continued scope checks through to C102 (470pF) and found that it was missing at the output side of this capacitor. But a replacement capacitor made no difference.

The tone is switched on and off by toggling pin 1 of U600. Time was wasted here. The tone is on when this pin is high (1.53V) and off when it's low (0V). But the change is not instantaneous: it takes place three seconds after you press 'select' with the remote-control unit. Very naughty!

Anyway U600 was OK, so it was back to the output side of C102. This is connected to the collector of the LNB switch-off transistor Q138 and the LM358M 22kHz tone amplifier chip U103. Clearly one or other of these items was deleting the tone. Replacing Q138 made no difference: replacing U103 made D101 (BAS16) go up in smoke. I also found that D107 (15V zener diode) and the 2SK2414 FET Q103 were leaky. Replacing all these items (U103, D101, D107 and Q103) finally restored normal operation. M.D.

Panasonic TU-DSB30

The picture produced by this digibox was covered in red and green blocks, which

indicates a failed SDRAM chip. There are two to chose from, IC302 and IC303. I decided to check their temperatures using a laser-sighted digital thermometer. This showed that IC302 was running 2°C hotter than the other chip. A replacement (KM416S1120DT-G8) SDRAM in the IC302 position cured the problem.

I first used this trick about ten years ago, to locate a faulty RAM chip in an Atari computer that had eight of them in parallel. M.D.

Amstrad DRX100

This digibox was stuck in standby with no LNB voltage present. Its owner said he had fitted a power-supply capacitor kit some eighteen months previously. Checks showed that the cause of the problem was with the 3·3V supply, where the voltage was low at 2·2V. The value of the $1.000\mu F$, 16V reservoir capacitor C12 had fallen to $12\mu F$, with an ESR of 12Ω . All the capacitors were green in colour and made by 'Nover'. The quality of the kit capacitors that had been fitted was in fact probably worse than that of the originals.

Replacement capacitor kits were originally produced by SatCure, but have been copied by other firms that have undercut prices by using poor-quality components. I recommend purchasing capacitor kits from SatCure, which supplies low-ESR capacitors rated for high ripple current. M.D.

Pace 2500S5

Unlike the 2500S3, this model has the ZIF front-end on the main board. The MAX2115 ZIF chip is unfortunately prone to failure. This particular digibox produced the 'no satellite signal received' message, and the cause was traced to the ZIF chip.

Replacement is far from easy. You have to use a soldering station to remove the screening can after removing the LNB socket. The replacement chip measures only 6mm square and has 48 solder pads underneath. Unlike BGA chips, which come with pre-attached solder balls, the MAX2115 has bare pads. An exact amount of solder has to be applied to the PCB, then the chip is sat on top and taken up to reflow. This requires great skill and care to get it right. It's not my favourite job. M.D.

Amstrad DRX100

This digibox had a familiar symptom – it produced the 'no satellite signal received' message – but this time the tuner's local oscillator was running and it was producing Q and I outputs. The OSD said a signal was being received, but with no quality.

The cure was to replace the BMC4200KEF QPSK channel decoder chip U100. M.D.

Solution to Test Case 491

- see page 45 -

Home electronic and also electrical equipment is increasingly processor-controlled and software-driven. Few problems arise when the codebook and command set are burnt into a rugged ROM chip of some sort. EEPROMs used for the purpose are not so reliable however – their grip on the contents seems to be less firm!

With the user, factory and installation settings stored in a memory chip and acted upon by a microcontroller chip, we have in effect a mini computer. It has software, an operating system and peripherals, e.g. a deck mechanism. PCs do the right thing only when they are programmed correctly, and this was the problem with the Sony SLV-SE820G VCR. Sage had entered the right codes, but for the wrong model – the less-sophisticated SLV-SE720G. Thus the machine in question was suffering from some sort of an identity crisis and, in its new role as an SLV-SE720G, wouldn't have anything to do with its jog-timer knob – you don't have one of these with the SE720G!

Sage got out the SE820G data and found that its code table is somewhat different. He soon had the correct bytes entered – 3-15 inclusive, 19, 23, 27, 29, 32-35, 40, 41, 45, 47-50, 60, 61, 63, 64, 66, 69 and 72. After that the machine's functions and features could all be used.

This sort of thing is becoming increasingly common with modern equipment, along with software updates, not all of which can be transmitted over the air. So be wary!

NEXT MONTH IN TELEVISION

Mobile phones and their repair

Mobile phones are part of everyday life for most people nowadays. Chris Archer outlines their history, how they operate, and then describes dismantling and repair procedures for some common models. The aim is to provide enough basic information to enable you to attempt repairs rather than consigning faulty phones to the bin.

Maintaining PA amplifiers

Here's a useful sideline, looking after the PA amplifiers used by local bands. Geoff Darby has been involved in this work for some time and explains the sort of problems you get and how to deal with them.

Tackling the Vestel 11AK33 chassis

This chassis is used in various recent Hitachi and Wharfedale models. Tripping is a common fault condition which must be dealt with the right way. Alan Dent tells you how to go about it and describes some other fault conditions you might encounter.

Putting the triac to work

The triac is a useful semiconductor device that's not as widely used as it deserves to be. J. LeJeune describes its origin, mode of operation and how to make use of it.

PLUS ALL THE REGULAR FEATURES

TELEVISION INDEX & DIRECTORY 2003

Plus hard-copy index and reprints service

Here's the essential repair information you need! The Television Index & Directory 2003, in CD-ROM form, contains the text of nearly 15,000 high quality fault reports on TVs, VCRs, Camcorders, DVD players, Monitors, Satellite TV units, Audio equipment and CD players, searchable by make and model, plus the text of 180 Test Cases and over 200 major servicing articles, from fifteen years of Television magazine. It also contains a full fifteen year index of Television, a Spares Guide, a directory of Trade and Professional Organisations, an International TV Standards guide, a satellite TV Channel Finder, a TV transmitter list and a compendium of internet resources for service engineers. The software is quick and easy to use, and runs on any PC with Windows 95, 98, ME, NT, XP or 2000.

Television Index & Directory 2003 CD-ROM, £199

Television Index & Directory 2003 CD-ROM upgrade, £46 (to qualify for this upgrade you need to have purchased a previous version of the Television Index on floppy disk or on CD-ROM)

A six-month update of the index and fault reports will be avail-able in May 2003. If you wish to take advantage of this, £10 should be added to your order.

Television Index only, 1988—2002, £36

Television Index only upgrade from previous versions, £16

Hard-copy indexes of Television magazine are available for Volumes 38 (1988) to 52 (2002) at £3.50 per volume.

Reprints of articles from Television back to 1988 are also available, at the flat rate of £3.50 per article — you can order through our web site, or write to the address below.

The above prices include UK postage and VAT where applicable. Add an extra £1 postage for non-UK EC orders, or £5 for non-EC overseas orders, although Channel Island residents do not need to add any extra postage. Cheques should be made payable to SoftCopy Ltd. Access, Visa or MasterCard Credit Cards are accepted. Allow up to 28 days for delivery (UK).

SoftCopy Limited, 1 Vineries Close, Cheltenham, GL53 ONU, UK

Telephone 01242 241 455, Fax 01242 241 468 e-mail: sales@softcopy.co.uk web site: http://www.softcopy.co.uk

Published on the third Wednesday of each month by Highbury Business Communications, Nexus House, Azalea Drive, Swanley, Kent, BR8 8HU. Highbury Business Communications is a division of Highbury Communications PLC. Filmsetting by Impress. Unit 2, Parkway, Southgate Way, Orton Southgate, Peterborough PE2 6YN. Printed in England by Polestar (Colchester) Ltd., Newcomen Way, Severalls Industrial Park, Colchester, Essex CO4 4TG. Distributed by Comag, Tavistock Road, West Drayton, Middlesex UB7 7GE (tel. 01895 444 055). Sole Agents for Australia and New Zealand. Gordon and Gotch (Asia) Ltd.; South Africa, Central News Agency Ltd. Television is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to currency exchange fluctuations and VAT, and that it shall not be lent, resold, hired or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.



WHAT A LIFE!

TV and VCR faults. Band III converters. Strange customers and warm sets. Donald Bullock's servicing commentary

le were due to return to Spain earlier in the month but, by way of getting their pound of flesh, Steven and Paul thought up a wheeze that would keep me in the workshop for a couple more days. They decided to go on an extended tench fishing exercise. It's my own fault I suppose. I became addicted to the sport at fourteen or so and I guess they are just taking after me. Of course they are nowhere near as good at it as I am!

Enter Shiner

I had scarcely taken my coat off when Shiner Albright danced in. He's a 'ten per center' – he will take this or fetch that for anybody, saying that he does it out of the goodness of his heart. So he might, and no one says a word against him. But he always insists on a ten per cent discount from the shop, and charges the customer ten per cent on the price he should have paid to the shopkeeper. A handy way of getting by. He's also a natural charmer, with a quiet and casual gift of the gab. People queue up to have him help them.

He brings us a lot of jobs, so we can't complain. This time he brought in a Sharp VCM29HM VCR and a Toshiba TV set, Model 2151TB.

"For two of my good friends, Donald" he said. Then he heard cups chinking, but didn't let on. It was Greeneyes making the tea. He's always full of compliments for the ladies, and Greeneyes falls for his charm. He dropped his voice and smiled at her.

"There wouldn't be a cup of that nectar for poor old Shiner, would there?" he asked.

There was of course.

The Toshiba TV

When he'd danced off I put the Toshiba set on the bench and plugged it in. After five seconds it clicked off. So I tried it again, and once more it tripped. I removed the back and looked around the chassis for dry-joints. There was a beauty at the mains bridge rectifier's reservoir capacitor. I felt good as I speedily dealt with it and tried again.

I didn't feel so good when the set tripped off once more. I had to do a bit of thinking. Then I reached for the meter to check the HT output from the power supply. It should have been about 115V, but the reading was way out at 145V. No wonder.

I decided to check the electrolytics on the primary side of the power supply and soon found that C817 (22µF, 100V) had fallen to about 2µF. It's the reservoir for the STR58041 chopper chip's –42V supply. The set worked perfectly once a replacement had been fitted.

The VCR

Then I got round to the Sharp VCR. Apparently it kept chewing tapes and seizing up. When I opened it I found that there was a large amount of tape debris, all saturated with oil. After cleaning out the debris and mopping up the oil I carefully degreased the deck. In so doing I noticed that the left-hand spool was stiff, because the back-tension band was sticking to it. A new one put that right.

When Shiner breezed back I'd prepared the bills, taking care to add the ten per cent that he would want subtracted. He paid up happily after deducting his ten per cent, as he always does.

"Er, Shiner" I commented, "you didn't accidentally drop a teeny spot of oil in the recorder's works by any chance, did you?"

"Well, in a manner of speaking, just the tiniest drop" he replied, "but I want to thank you for doing these two so quickly. One is my granny's, the other

belongs to my aunt Rosie. You've made them both happy, Donald. Now it just so happens that I have another couple of jobs for you."

More TVs

He ran out then returned with a giant Goodmans TV, Model GTV69W3BLU4. We know it, the chassis being the Vestel 11AK19PRO. From where I was the set seemed to run in on its own two legs.

"Dead as a dodo" he said as he put it down. "It belongs to my uncle Herbie." Then he danced out again and returned with a widescreen Sharp set, Model 66FW54H (DA100 chassis).

"Cracking and banging and all sorts" he announced. "Belongs to my late younger brother's wife." He winked at me, clicked his tongue then put on a devout face.

The Goodmans set had a short-circuit line output transistor, type BU2508AF. A replacement restored the picture, but the width was poor and there was severe EW distortion. It didn't take long to establish that the BUK444-200A EW driver FET was short-circuit. I fitted a PNQ20T in its place as this is more up to the job. But the bowing remained. After checking the various capacitors in the circuit, including the scan-corrector C630 that gives a lot of trouble, I turned my attention to the EW modulator diodes. The capacitors had both been OK, but D611 (BY299P) was opencircuit. A replacement completed the repair, and the picture was perfect.

Not bad I thought, now for the Sharp set. There was a lot wrong with this one, which was arcing badly. The HT reservoir capacitor C720 ($100\mu F$, 200V) had blown off its top, and the BUH515 line output transistor Q601 was short-circuit. R623 (1Ω , 2W safety type) in the HT feed to the line output stage had gone open-circuit, and I assume that there had been excessive HT.

The MOC8106 otpocoupler IC705 in the power supply is the prime suspect in this event, and turned out to be faulty. So were R765 and R766 (both 100Ω) in the feed to pin 1 of the optocoupler. They all live on the copper side of the board.

There were a number of faults on the CRT base PCB. The TEA5101A RGB output chip IC1801 had to be replaced, also Q5407 (2SA1837) and Q5408 (2SC4793) in the scan velocity-modulator output stage. R5425 (470Ω, 1W) in the supply to this stage was open-circuit.

It took some time to replace these various items. I then switched the set on, somewhat gingerly, and breathed a sigh of relief when it behaved perfectly. To prevent a recurrence of this sort of thing Sharp recommends adding a 170V avalanche diode in parallel with C720, with its cathode to the positive side. The part number is RH-EX0875BMZZ.

Band III converters

Last month I mentioned that Bill and Hilary Wright were looking for a picture of a Band III converter, the first type of set-top box, that used to sit on top of BBC-only sets in the Fifties, after the start of ITV transmissions. I was doubtful whether there would be much response - they soon became obsolete, as the setmakers devised their own Band I/III tuners for fitting inside their sets. And what a mixed bag of tuners they introduced! Some were quite good and tidy, others were good but clumsy, and some were an absolute headache. The worst, to my mind, were the Ultra 'trombone' ones. They remain etched in my memory!

To my surprise however there was a good response. It's clear that many readers have collections of vintage radio and TV sets and other brown goods items. I received photos from two readers, Bob Webb of Burton upon Trent and Dave Higgison of Doncaster. One was of a brand new, unused converter made by Champion! Dave mentions that it was potentially lethal, because it has a two-pin 5A mains connector into which the TV set could be plugged. Nothing wrong with that but, instead of fitting a shrouded socket, there's a two-pin unshrouded live plug! My thanks to Bob and Dave.

Emaile

I am also grateful to those who have sent me emails on various points. Keep it up! You can reach me at

donald@wheatleypress.com
Greeneyes is also very grateful to a
reader we recently met and is about to
settle in Spain. It wasn't long before
Television was mentioned and, when
this column came up, Greeneyes
confirmed that I was the guilty scribbler.

He stepped back, looked at me carefully, then said:



"Coo, but that picture at the top of the column is an old one of you, isn't it?"

In fact of course I'm much younger and more handsome than the picture makes out. I think someone else walked in front of the camera as it was clicked . . .

Strange types

Dave Smith of Leigh, Lancashire tells me about some of the strange types who have wandered into his TV and electronics shop. One was an old lady who came in and studied a large card display of control knobs. She declined assistance and eventually turned away, showing some upset. Dave approached her again and it transpired that she thought she was in an ironmongers and wanted a brass doorknob.

Another time a tall, intelligent-looking chap slapped his money on the counter and asked for a packet of rubber goods. Dave explained that they didn't sell them, and that he should try the chemists opposite.

"But," the chap persisted, "I naturally assumed that you would be the best place to try, this being an electronics shop. After all each one is electrically tested, isn't it?"

Then there was the chap who bought a radio kit and brought it back, saying it didn't work. It looked neat and tidy but when Dave investigated he found that a fine-nozzled tube of grey Bostick had been used instead of solder!

Darren Henwood of Romford, Essex mentions the oddball who came into his TV shop and plonked a pair of wellworn shoes down. "I'd like these soled and heeled please" he said.

Warm sets

Peter Nutkins of Charmouth, Dorset called at our place in Spain last year. He commented on the fact that customers often complain that their sets, after being repaired, get too warm. He

The first sort of set-top box, a Band III converter that dates from the mid Fifties.

recalled an incident in his early days in the trade when a customer with a Bush TV22 complained that it got too warm. Peter reassured him that he was mistaken, then placed the palm of his hand on the side of the Bakelite cabinet. It was red hot!

When he looked inside he soon found the reason for the heat. In an effort to suppress some slight mains-borne interference someone had added an RC circuit that consisted of a large wirewound resistor in series with an even larger paper capacitor. This had been fitted to the side of the cabinet, on a tag strip, and wired across the mains input. The capacitor had gone short-circuit and the resistor was indeed red hot.

Another case involved a Bush TV53. This model had a strip of gold-coloured metal trim along the bottom of the tube's implosion screen. The owner phoned repeatedly to complain that she got shocks from the trim while adjusting the controls. He explained that this wasn't possible, as there was no connection between the trim and anything live.

Eventually she threatened legal action and he called to discuss the matter. In fact she was right! While it was true that there was no physical connection of anything live to the metal trim, a fault condition made it fleetingly and painfully 'live'. The EY51 EHT rectifier was going short-circuit intermittently. As a result the EHT would momentarily collapse and induce a charge in the metal. Profuse apologies and a new EY51 restored good customer relations.

Peter did not mention it, but I wonder why the lady didn't notice the effects of spasmodic EHT collapse on her picture? Too busy getting shocks maybe.



582x628 Resolution 380 lines Automatic aperture lens Mirror function PAL Back Light Compensation MLR, 100x40x40mm. Ref FE2 £69

lens 12V d.c. 200mA

Colour CCTV camera, 8mm

Built-in Audio .15lux CCD camera 12V d.c. 200mA 480 lines s/n ratio >48db 1V P-P output 110mm x 60mm x 50mm. Bet FF1 699






Excellent quality purposeTV/TFT scre screen, works purposeTV/TFT screen, works as just a LCD colour monitor with any of our CCTV cameras or as a conventional TV. Ideal for use in boats and caravans 49.7MHz-91.75MHz VHF channels 1-5,168-25MHz-222.75MHz VHF channels 6-12, 471.25MHz-869.75MHz. 12, 471.25MHz-869-75MHz Cable channels 112-325MHz-166-75MHz Z1-Z7, Cable channels 224-25MHz-446-75MHz Z8-Z35 5" colour screen. Audio output 150mW. Connections. external aeral. Connections, external aerial, earphone jack, audio/video input, 12V d.c. or mains, Accessories supplied Power supply, Remote control, Cigar lead power supply, Headphone Stand/bracket. 5" model £139 Ref EE9, 6" model £149. Ref

construction High tec fibre glass limbs Automatic safety catch Supplied with three bolts Track style for greater accuracy. Adjustable rear sight 50lb drawweight 150ft sec velocity Break action 17 string 30m range £21.65 Ref PLCR002 Fully cased IR light source suitable for CCTV applications. The unit measures 10 x 10 x The unit measures 10 x 10 x 150m, is mains operated and contains 54 infra-red LEDs. Designed to mount on a standard CCTV camera bracket. The unit also contains a daylight sensor that will only activate the infra-red lamp when the light level drops below a preset level. The infra-red lamp is suitable for indoor or exterior use, typical useage would be to pro additional IR illumination for CCTV neras. £49. Ref EE11



Mains operated and designed to be used with any CCTV camera causing it to scan. The clips can be moved to adjust the span angle, the motor reversing when it detects a clip. With the clips removed the scanner will rotate constantly at appro 2-3rpm, 75 x 75 x 80mm £23. Ref EE12

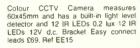Self-cocking pistol plcr002 crossbow with metal body. Self-cocking for precise string alignment Aluminium alloy construction High tec fibre






A high quality external colour CCTV camera with built-in infra-red LEDs measuring 60 x 60 x 60 mm Easy connect leads colour Waterproof PAL 1/4in. CCD 542 x 588 pixels 420 lines 0.05 lux 3-6mm F2 78 deg lens 12V d.c. 400mA Built-in light level sensor 599 Ref FE13 high quality external colour level sensor, £99, Ref EE13

Colour pinhole CCTV camera module with audio. Compact, just 20x20x20mm, built-in audio and easy connect leads PAL CMOS sensor 6-9V d.c. Effective Pixels 628x582 Illumination 2 lux Definition >240 Signal/noise >40db sumption 200mW £35. Ref EE21



sensitivity. Effective pixels 628 x 582 Power source 6-12V d.c. Power consumption 200mW £36.

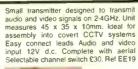Power con Ref EE16
Complete wireless CCTV sytem with video. Kit comprises pinhole colour camera with simple battery connection and a receiver with video output, 380 lines colour 2-4GHz 3 lux 6-12V d.c. manual tuning Available in two versions, pinhole and standard. C79 (pinhole) Ref EE17, £79 (standard). Ref EE18





audio and video 2.4GHz wireless receiver 190x140x30mm, metal case, 4 channe 12V d.c. Adjustable elay, 4s, 8s, 12s, 16s. £45. Ref EE20

The smallest PMR446 radios currently (54x87x37mm). These available (54x87x37mm). These tiny handheld PMR radios not only look great, but they are user friendly & packed with features including VOX, Scan & Dual Watch. Priced at £59.99 PER PAIR they are Priced at \$59,99 PEH PAIH they are excellent value for money. Our new favourite PMR radios! Standby. – 35 hours Includes: – 2 x Radios, 2 x Belt Clips & 2 x Carry Strap £59,95 Ref ALAN1 Or supplied with 2 sets of rechargeable batteries and two mains chargers £84,99. Ref Alan2





Beltronics BEL55O Euro radar and GATSO detector Claimed Detection Range: GATSO up to 400m. Radar & Laser guns up to 3 miles. Detects GATSO speed cameras at least 200 GATSO speed cameras at least 200 metres away, plenty of time to adjust your speed £319. Ref BEL550

TheTENS mini Micronrocessors offer six types of automatic programme for shoulder pain, back/neck pain, aching joints, Rheumatic pain, migraines headaches, sports injunes, period pain. In fact all over body treatment. Will not interfere with existing medication. Not suitable for anyone with a heart pacemaker. Batternes supplied. £19,95
Ref TEN327 Spare pack of electrodes £5.99. Ref TEN327X





Dummy CCTV cameras These motonsed cameras will work either on 2 AA battenes or cameras will work either on 2 AA battenes or with a standard DC adapter (not supplied). They have a built-in movement detector that will activate the camera if movement is detected causing the camera to pan' Good deterrent. Camera measures 20cm high, Supplied with fixing screws. Camera also has a flashing red I.e.d. built in. £9.95. Ref CAMERAB

INFRA-RED FILM 6" square piece of flexible infra-red film that will only allow IR light through. Perfect for converting ordinary torches, lights, headlights etc to infra-red output only using standard light bulbs Easily cut to shape. 6" square £15. Ref IRF2 or a 12" sq for £29 IRF2A



GASTON SEALED LEAD-ACID BATTERIES



1-3AH 12V @ £5 REF GT1213 3-4AH 12V @ £8 REF GT1234 7AH 12V @ £8 REG FT127 17AH 12V @ £18 REF GT1217

All new and boxed, bargain prices Good quality sealed lead-acid

SOLAR PANEL 10 watt silicon solai SOLAR PANEL 10 watt silicon solar panel, at least 10 year life, 365 x 26mm, waterproof, ideal for fixing to caravans, boat, motorhomes etc. Nicely made unit with fixing holes for secure fittings. Complete with leads and connectors. Anodised frame. Supplied with two leads, one 3M lead is used for the ofly with two croc clips, the other lead is used to connect extra panels. Panels do NOT require a blocking dode, they can be left connected at all diode, they can be left connected at all times without discharging the battery.

times without discharging the battery. £84.99. REF PAN 8A solar regulator 12V, 96 watt, 150mm x 100mm x 25mm £28. REF SOLREG2



High-power modules (80W+) using 125mm square High-power modules (80W+) using 125mm square multi-crystal silicon solar cells with bypass didoe. Anin-reflection coating and BSF structure to improve cell conversion efficiency: 14%. Using white tempered glass, EVA resin, and a weatherproof film along with an alumnium frame for extended outdoor use, system Lead wire with waterproof connector. Four sizes, 80W 12V dc. 1200 x 530 x 35mm, 5287. REF NE30. 123W 12V dc., 1499 x 662 x 46mm, 5439. REF NE30. 125W 24V, 1190 x 792 x 46mm, 5439. REF NEL5 and 155W 24V, 157 x 826 x 46mm, 5543. 165W 24V, 157 x 826 x 46mm, £593

BULL GROUP LTD

UNIT D, HENFIELD BUSINESS PARK, HENFIELD, SUSSEX BN5 9SL TERMS: CASH, PO, CHEQUE PRICES + VAT WITH ORDER PLUS £5.50 P&P (UK) PLUS VAT.

Tel: 0870 7707520 Fax 01273 491813

www.bullnet.co.uk

THE TIDE CLOCK, These clocks the state of the tide. Most areas in the world have two high tides and two low tides a day, so the tide clock has been specially designed to rotate twice each lunar day (every 12 hours and 25 lunar day (every 12 hours and 25 minutes) giving you a quick and easy indication of high and low water. The Quartz tide clock will always stay calibrated to the moon. £21 REFTIDEC





INEAR ACTUATORS 12-36V D.C. BUILT-IN ADJUSTABLE LIMIT SWITCHES. POWER COATED 18in. THROW UP TO 1,000lb. LINEAR ACTUATORS 12-36V D.C. BUILT-IN ADJUSTABLE LIMIT SWITCHES. POWER COATED 18in. THROW UP TO 1,000lb. THRUST (400lb. RECOMMENDED LOAD). SUPPLIED WITH MOUNTING BRACKETS DESIGNED FOR OUTDOOR USE. MOUNTING BHACKETS DESIGNED FOR COTIDORN USE. These brackets originally made for moving very large satellite dishes are possibly more suitable for closing gates, mechanical machinery, robot wars etc. Our first sale was to a company building solar panels that track the sun! Two sizes available, 12in, and 18in, throw. £29.95. REF ACT12, £34.95 REF ACT18.





POWERSAFE DEEP CYCLE BATTERIES 12V 51AH NOW ONLY £29.95 EACH YUASA 6V 100AH NOW ONLY £19 EACH



BRAND NEW MILITARY ISSUE DOSE METERS (radiation detectors). Current NATO issue. Standard emergency services unit.
Used by most of the world's
military personnel. New and boxed.
£69. REF SIEM69

NIGHT VISION SYSTEM.
Superb hunting rille sight to fit most rilles, grooved for a telescopic sight. Complete with infra-red illuminator. Magnification 2.7x. Complete with rubber eye shield and case. Opens up a whole new world! Bussian made Can be NIGHT VISION SYSTEM world! Russian made. Can be used as a hand held mounted on a rifle, £99, REF



Samarium These Samarium magnets measure 57mm x 20mm and have a threaded hole (5/16th UNF) in the centre and magnetic strength of 2-2 gauss. We have tested these on a steel beam running through the offices and found that they will take more than 170lb. (77kg) in weight before being pulled off. With keeper. £19.95. REF MAG77. These



Peltier Effect heat pump. Semiconductor thermo-electric device which works on the Petiter effect. When supplied with a suitable electric current, can either cool or heat. Also when subject to an externally applied temperature gradient can produce an electric can produce an electric current, ideal for cooling or

current. Ideal for cooling or controlling the temperature of sub assemblies. Each module is supplied with a comprehensive 18-page Peltier design manual featuring circuit designs, design information etc., etc. The Peltier manual is also available separately. Maximum watts 56-2 40 x 40mm Imax, 5-54 Vmax, 16-7 Tmax (c-dry N2), 72. 529-95 (inc. manual. REF PELT2.



New transmitter, receiver camera kit. £69. Kit contains channel switchable camera with builtchannel switchable camera with Dultiin audio, six IR I.e.d. s. and transmitter,
four channel switchable receiver, 2
power supplies, cables, connectors
and mounting bracket £69. Wireless
Transmitter, Black and white camera
(75 x 50 x 55mm), Bulti-in 4 channel
transmitter (switchable), Audio huiting transmitter (switchable). Audio built-in

6 IR i.e.d.s. Bracket/stand. Power supply 30m range Wireless
Receiver 4 channel (switchable), Audio/video leads and scart adapter. Power supply and manual, £69. REF COP24.

This miniature Stirling Cycle Engine measures 7in. x 41/4in. and comes complete with built-in alcohol burner. Red flywheels and chassis mounted on a green base, these all-metal beauties silently base, these all-metal beauties sitently running at speeds in excess of 1,000 r.p.m. attract attention and create awe wherever displayed. This model comes completely assembled and ready to run. £97. REF SOL!



SHOP ONLINE WWW.BULLNET.CO.UK





24 HOUR SERVICE £7.50 (UK) PLUS VAT. OVERSEAS ORDERS AT COST PLUS £3.50

Sales@bullnet.co.uk

P.J.HILL

TV. VCR. SPARES

FLYBACK TRANSFORMERS BY

ELDOR, OREGA, TERMAL, CLASSIC ALSO BUDGET RANGE.

Enquire by No's off old transformer & model No. For Akai, Akora, Alba, Aiwa, Bush, Beko, Daewoo. Ferguson, Formentii, Goodmans, Grundia, Hinari, ITT, JVC, Matsui, Net, Orion, Panasonic, Philips, Samsung, Sanyo, SEG, Sharp, Sony, Thomson, Tatung, Toshiba, etc.

REMOTE CONTROL BY CLASSIC

Video heads & spares, CD Lasers, belts, mains switches, semi conductors, valves, switch mode transformers (including Matsui 2196N) service kits, T/V, VCR & satellite resistors, capacitors, valves, tuners, triplers etc.

ASK ABOUT OUR SERVICE MANUAL LIBRARY FOR TN VIDEO & MICROWAVE & AUDIO.

MOST CREDIT & DEBIT CARDS



E7 NORTHWAY TRADING EST. NORTHWAY LANE, TEWKESBURY, GLOS, GL20 8JH, Tel: 01684 296902

Fax: 01684 294317



1394 894777 F a: 44 [0] 1384 895788

Data & Display Components

H.P. 6063B DC Electronic Load 3-240V/0-10A 250W

SPECIAL OFFERS



H P. 3312A Function Gen 0 1Hz-13MHz AM/FM £300 Sweep/Trt/Gate/Burst etc FARNELL AMM255 Automatic Mod Meter 1 5MHz-£300 2GHz Unused FARNELL DSG1 Low Frequency Syn to 99 99kHz, Low Distortion TTL/Square, Pulse Outputs etc. FLUKE 8060A Handheld True RMS DMM 41/2 H P 3310A Function Gen 0 005Hz-5MHz Sine/S distortion TTL Output Amp H.P. 545A Logic Probe and 547A Current Tracer FLUKE 77 Multimeter 3 FLUKE 77 SERIES II

BLACK STAR ORION PALITY THURLBY/THANDAR THURLBY THANDAR PSU Racal 9008 Automistic Mo 1 5MHzz-2GHz Modulation Mete

Datron 1061A digit Ben in Multimeter £225

500KHZ-512MHZ KENWODD CS4025 Dscilloscope Dual Trace 20MHZ LEADER LB0523 Oscilloscope Dual Trace 35MH. GOULD OS300 Dscilloscope Dual Trace 20MHZ

95
NATIONAL PANASONIC VP7705A Distortion Analysis KENWDOD VT176 Millivoltmeter 2Channel KENWOOD FL140 Wow & Flutter Meter KENWOOD FL180A Wow & Flutter Meter Used £75 Unused £125 MARCONI 893B - No Sinad MARCONI 2610 True RMS Voltmeter Autorangii GOULD J3B Sine/Sq Osc. 10Hz-100l AVO 8 Mk6 in Ever Ready Case FARNELL AP60/50 FARNELL H60-/50 0-60V 0-50A FARNELL H60/25 0-60V, 0-25A FARNELL Dual PSU XA35-2T 0-35V 0-2A Twice QMD LCD

JUST IN

H P 8640A SIGNAL GENERATOR AM/FM £250 FARNELL L30-1 0-30V, 0-1A
Many other Power Supplies available
Isolating Transformer 240V In Out 500

Farmell DTV 12-14 OSCILLOSCOPE Dual Trace 12 MHZ TV. Coupling..ONLY £75 FARNELL LFI Sine/Sq OSCILLATOR 10HZ-1MHZ ILLOSCOPES AVAILABLE £5000 sed AM/FM S.g Gen £525 - £750 RAS APNB2 Syn 1Hz - 260KHz Sig Gen
Balainced/Unbalanced Output LCD Display
PHILIPS MM5328 Sig Gen 100KHz - 180MHz
200MHz
Freg Counter IEEE
RACAL 9081 Syn AMIFM Sig Gen 5MHz - 520MHz
H P 33254 Syn Function Gen 21MHz
MARCON 6500 Amplitude Analyser - 1
H P 4192 Impedence Analyser - 1
H P 5498 Free Counter 20GHz

H P 1650B Logic Analyser 80 Channel ... MARCONI 2305 Mod Meter 500KHz - 2Ghz

H P. 66311B PSU Q - 15V/0-3A... H P. 66309D PSU Dual 0 - 15V 0-3A/0-12V 0-1.5A H.P 6632B PSU 0 - 20V/0-5A H.P 6623A PSU Triple Output ranging from €850 ent 34401A DMM 61/2 digit £400/£450 €400 15MHz 15MHz 5000 15MHz 15MHz 15MHz 15MHz 15MHz 15MHz 15MHz 15MHz 1600. BLACK STAR JUPITOR 2010 Function Gen 0.24z with Frequency Counter HP . 8116A Pulse Generator 1 mH-50MHz HP . 85578 Syn Signal Gen 0.1-2080MHz CD-AXIAL SWITCH 15GHz 1EEE CABLES SPECTRUM ANALYSERS HP 8504 50Hz - 0 50Hz HP 8504 50Hz - 2 9GHz Synthesised HP 8594E 9KHz - 2 9GHz - 1 HP 8594E 1 MHz - 1 8GHz 75 0 hm HP 8538 with 8559A 100KHz - 21GHz HP 8558B with Main Frame 100KHz - 1500MHz HP 3585A 20Hz - 40MHz HP 3580A 5Hz - 50KHz ADVANTEST R4131B 10KHz - 3.5GHz FATDWAIties 757 0.001 - 25GHz £750 .£600 EATDN/Ailtech 757 0 001 - 22GHz £750 MARCONI 2382 100Hz - 400MHz High Res MARCONI 2370 30Hz - 110MHz H P 182 with 8557 10KHz - 350MHz €500 HP 141T Systems 8553 1KHz - 110MHz 8554 50GKHz - 1250MHz 8555 10MHz - 18GHz.... 8555 10MHz - 18GHz.

H P 8443 Tracking Gen/Counter 110MHz.

H P 8444 Opt 059

B & K 2033R Signal Analyser

H P 875-4A Network Analyser 4MHz - 1300MHz.

H P 3577A Network Analyser 5Hz - 200MHz.

H P 53310A Modulation Domain Analyser £250 £750 £1250 001/003 ONO SOKKI Portable FFT Analyser £1500

RADIO COMMUNICATONS TEST SETS

MARCONI 2955/2955R
Rohde & Schwarz CMT 0.1 - 1000MHz
Schlumberger 4040

STEWART OF READING



HEME 1000 LCD Clar

110 WYKEHAM ROAD, READING, BERKS RG6 1PL Telephone: (0118) 9268041 Fax: (0118) 9351696 www.stewart-of-reading.co.uk Callers welcome 9am-5.30pm Monday to Friday (other times by arrangement)

£40

USED EQUIPMENT - GUARANTEED. Manuals supplied. This is a VERY SMALL SAMPLE OF STOCK. SAE or telephone for lists. Please check availability before ordering. CARRIAGE all units £16. VAT to be added to total of goods and carriage.

ADVERTISERS INDEX

Aerial Techniques35	Kudos Marketing63
Alban ElectronicsOBC	Logik Business Solutions31
Bang & Olufsen52	Martin Turner Direct53
B Smart	
Blundell Production EquipmentIBC	M.C.E.S41
Bull Electrical 60	Mulitigen42
Calder Components31	Peak Electronic Design30
Campion Electronics49	P.J Hill61
Coastal Aerial Supplies41	Remotes Direct31
Colourtrade52	Stewart of Reading61
Cricklewood Electronics Ltd41	
D'Lec Components31	Satellite & Digital Services49
East London Components43	TW Electronics IFC
Economic Devices49	Trade Electronix37
Electronic World T.V. & Video43	Urwin Electronics
Express TV41	Vann Draper Electronics Ltd42
Grandata Ltd19-24	
Horizon Global Electronics62	Video Display Europe Ltd61
Instore Electrics62	Welwyn Tools43
JPG Electronics62	Wiltsgrove2



What a **Lovely Pair!**



HORIZON DIGITAL TERRESTRIAL METER

HDTM

- Signal Strength and BER displayed together
- Pre and post BER displayed on sub menu
- 10 pre programmed transmitters (via website) or all channel step through
- · Audible tune-in, with back light
- 7 or 8 MHz channels
- 2K and 8K mode
- Automatic Transmission and constitution
- VHF (band3) and UHF bands
- RF input range 167-862 MHz
- Input dynamic range -72dBm~-20dBm
- Input connector BNC. Input imp75 ohms. Loop through
- External power for mast amplifiers, etc.
- Built in universal charger 80-250 V Ac. Intelligent charger (CE approved) with delta V delta T detection. Fast charge, then Trickle
- Run time with full charge: Minimum 5 hours from 2.5 Ah battery
- Figure of 8 mains input connector. 2.1 mm Female PSU plug for external charge via supplied car charger
- Computer interface: Serial port (Com 1-4) for upgradeable software on transmitters.

HORIZON DIGITAL SATELLITE METER

HDSMV2

- Signal Strength and BER displayed together
- · 32 Transponders or 16 satellites, horizontal & renual
- · Audible tune-in, with back light
- DVB, C&Ku band, Mpeg, V Sat compatible
- Input dynamic range -65dBm~-25dBm
- Input connector F-female. Input imp 75 ohms
- Symbol Frequency rate from 1 Msps 45Msps
- Universal charger 80 V ~ 250 V Ac. Int Illigant Charge (CE approved) with delta V delta T detection Fast charge, then Trickle
- Run time with full charge (single LNB): Minimum 3 hours from 2.4Ah battery
- Figure of 8 mains input connector. 2.1 mm Female PSU plug for external charge via car charger
- · LNB short circuit protection 500 mA automatic limiter
- RF input range 950- 2150 MHz
- Computer interface: Serial Port (COM 1,2,3 or 4) for upgradeable software on satellite settings.

www.horizonhge.com

Speed up your installations call NOW on +44 (0)20 8281 3777 or email sales@horizonhge.com for a reliable solution



WATCH SLIDES ON TV MAKE VIDEOS OF **YOUR SLIDES DIGITISE YOUR** SLIDES



(using a video capture card)

"Liesgang diaty" automatic slide viewer with built in high quality colour TV camera. It has a composite video output to a phono plug (SCART & BNC adaptors are available). They are in very good condition with few signs of use. For further details see www.diatv.co.uk ..£91.91+ vat = £108.00

Board cameras all with 512x582 pixels 8.5mm 1/3 inch sensor and composite video out. All need to be housed in your own enclosure and have fragile exposed surface mount parts. They all require a power supply of between 10 and 12v DC 150mA.

47MIR size 60x36x27mm with 6 infra red LEDs (gives the same illumination as a small torch but is not visible to the human eye). ... £37,00 + vat = £43,48

30MP size 32x32x14mm spy camera with a fixed focus pin hole lens for hiding behind a very small hole .£35.00 + vat = £41.13

40MC size 39x38x27mm camera for 'C' mount lens these give a much sharper image than with the smaller lenses......£32.00 + vat = £37.60

Economy C mount lenses all fixed focus & fixed iris VSL1220F 12mm F1.6 12x15 degrees viewing angle. £15.97 + vat = £18.76VSL4022F 4mm F1.22 63x47 degrees viewing angle... \$17.65 + vat = \$20.74 VSL6022F 6mm F1.22 42x32 degrees viewing angle.. £19 05 + vat = £22 38 VSL8020F 8mm F1.22 32x24 degrees viewing angle... £19.90 + vat = £23.38Better quality C Mount lenses VSL1614F 16mm F1.6 30x24 degrees viewing angle... .£26,43 + vat = £31,06

VWL813M 8mm F1.3 with iris 56x42 degrees viewing angle......£77,45 + vat = £91.00 1206 surface mount resistors E12 values 10 ohm to 1M ohm 100 of 1 value £1.00 + vat 1000 of 1 value £5.00 + vat

866 battery pack originally intended to be used with an orbitel mobile telephone it contains 10 1.6Ah sub C batteries (42x22dia the size usually used in cordless screwdrivers etc.) the pack is new and unused and can be broken open quite . £7.46+vat = £8.77



Please add 1.66 + vat = £1.95 postage & packing per order

JPG ELECTRONICS

Shaws Row, Old Road, Chesterfield, \$40 2RB Tel 01246 211202 Fax 01246 550959 Mastercard/Visa/Switch Callers welcome 9:30 a.m. to 5:30 p.m. Monday to Saturday



171 HAREHILLS LANE, LEEDS LS8 3QE Tel: 0113 240 1114. Tel/Fax: 0113 240 7275. Mobile: 07976 403134

Email: sales@instoreleeds.freeserve.co.uk

MANUFACTURES GRADED PRODUCTS **ALL PRICES PLUS VAT:** ALL PRODUCTS FULLY GUARANTEED

PHILIPS 32PW6506 32" WIDESCREEN REAL FLAT. FM RADIO, 50HZ £349.00

PHILIPS 32PW9527 32" WIDESCREEN REAL FLAT, DOLBY, 100HZ, PIXEL PLUS £549.00

PHILIPS LX3000 DVD PLAYER 5.1 SURROUND SOUND SYSTEM, 75W RMS £139.00

PHILIPS 14" TV/VCR COMBI FROM £84.00 PHILIPS 14" PORTABLES FROM £59.00

PHILIPS VCR'S FROM £39.00 PHILIPS AUDIO SYSTEMS FROM £44.00

FURTHER OFFERS AVAILABLE PLEASE CALL FOR A PRICE LIST **CREDIT CARDS WELCOME: NEXT DAY DELIVERY**



Panasonic

Willoughby Road, Bracknell, Berkshire, RG12 8FP

www.panasonic-spares-direct.co.uk

Panasonic CS UK

TELEVISION November 2003

Service Link

TELEPHONE 01322 611292 FAX 01322 616376

FOR SALE

FOR SALE

SERVICE DATA

SERVICE DATA

EX RENTAL TVs, VCRs, **PORTABLES**

Combi Washing Machines, Fridge Freezers etc.

For stock list call

Barry McDonald 01622 719313 or 07836 789528

CLOSED DOWN

SERVICE CENTRE Everything like large quantity of CTV. VCR, Camcorders, Audio and Hi-Fi service manuals for Sony, Panasonic, JVC, Toshiba etc. Books and lots more plus test equipment, meters etc.

Spare parts and cabinets, lots of made test leads.

New audio video leads accessories Please call Matt 07958 471033

STOP

LOPT'S. REMOTES **ALL TV COMPONENTS**

TIDMAN MAIL ORDER LTD 236 SANDYCOMBE RD KEW RICHMOND **SURREY TW9 2EQ** (1/2 MILE FROM KEW BRIDGE) PHONE: 020-8948-3702

PHOTOGRAPHIC SERVICES

BENCH ENGINEER REQUIRED

TO REPAIR ANALOG AND DIGITAL CAMCORDERS ETC

- Minimum experience 5 years
- Able to work to component level
- Location Kent
- Performance pay 20-35k + healthcare

Contact Trevor on Tel: 01732 761270 E-mail address: trev4dnh@aol.com

PROJECTOR SPARES

VIDIKRON

projector spare parts and service information.

> **PROJECTSPARES** Tel: 01444 831769 Fax: 01444 831580 E-mail:

projectspares@btinternet.com

ICC17 LOPTX Kit

Widescreen Special

Ferguson W7023U etc. Thomson 24WK23U etc Pt no. 10608670P1

ONLY £24.95!

IrwinElectronics

Telephone 0114 273 9622

SKY - DIGIBOXES

SALES - PERFECT COMPLETE SILVER PANASONICS £95 INCLUSIVE PRICES Other models £65 Faulty Boxes £20 Miniumum 3 boxes Plus carriage.

K.T.V. Warehouse, Tucking Mill, Camborne, Cornwall TR14 8NP. Tel: 01209 718043 11am-4pm

REPAIRS

Trade repairs to Sky digiboxes

Pace, Amstrad, Grundig, Panasonic, (including Fluid Ingress).

All makes repaired at a fair fixed price. Scan Digital Services

For details Give Alan a ring on Tel/Fax: 01633 25 40 50

E-Mail: alan@scansat.globalnet.co.uk

NEED HELP NOW?

Then ring the

★ ELECTRON TECHNICAL HELPLINE ★

Genuine help available to all repairers of

T.V. - V.C.R - SAT - AUDIO (Inc Valves)

Over 30 years experience and vast data base

0906 470 1706

Calls cost 60p per minute

Hours of Business Mon to Fri 9.00 am - 12.30pm : 2.15pm - 5.30pm





TEL A.T.V. on 0114 285 4254

CTV Circuits...... from £5.00 VCR Circuits from £7.00 CTV Manuals...... from £10.50 VCR Manualsfrom £14.50 User instructions also available (P/P add £2.50 to each order)

419 LANGSETT ROAD SHEFFIELD S6 2LL

MANUAL COLLECTIONS PURCHASED. (POST 1995)

SERVICE MANUALS

Have you ever turned away work for want of a Service Manual? Have you ever bought a Service Manual and never used it more than once?

Then why not join ...

THE MANUALS LIBRARY

For details and membership application form write. phone or fax:

HARVEY ELECTRONICS

43 Loop Road, Beachley, Chepstow, Mons, NP16 7HE

Tal: 01291 623086 Fax: 01291 628786

Visa: Mastercard accepted

Fryerns

Service Information



Circuit Diagrams

TV's, VCR's, SATELLITE CAMCORDERS, AUDIO & HI-FI's

Prices are from £5.50 + £2.75 P&P add a further £5.50 per item in the same order note: some items priced individually

we now supply universal tv/video remotes at competitive prices

Payment by credit card, PO or cheque Tel:Fax 01206 211570 e-mail: colin@fryerns.fsbusiness.co.uk



2 The Lodge Easthorpe Green Marks Tey, Colchester CO6 1HA

SERVICE INFO

TV - VIDEO - AUDIO

Prices- any make/model CTV s/man 10.00 15.00 **VCR** s/man CTV 5.00 circs VCR 7.00 circs

Other items POA

All prices include p/p. Do not add any VAT

AMTel

Huna, Caithness KW1 4YL 01955 611313 www.amtel.org.uk

WANTED

BEST CASH PRICES PAID

FOR VALVES KT88. PX4 AND MOST AUDIO/OTHER TYPES.

Tel: 01403 784961

Billington Export Ltd Sussex RH14 9EZ Fax 01403 783519 Email: sales@bel-tubes.co.uk Visitors by appointment

For a FREE consultation on how best to market your products/services to a professional audience contact REUBEN on 01322 611292

DOWNLOAD FREE SAMPLE CHAPTERS AT www.newnespress.com

DVD PLAYERS AND DRIVES

K. F. Ibrahim £24.99

- The engineer's guide to DVD technology
- ▼ Fully up-to-date coverage of video, PC and audio applications

This book is a comprehensive guide to the technology and its application, with a special focus on design issues and pitfalls, maintenance and repair. The

principles of DVD technology are introduced from the basics, and DVD applications are illustrated by genuine technical information in the form of block diagrams and circuit schematics. All current forms of DVD player and writer are introduced, including equipment types that are only just appearing on the market.

processing; Video encoding; Audio encoding; The DVD player; Microprocessors for DVD systems;




Signal processing; Servo control; Microprocessor control; The power supply and user interface; DVD writers: DVD drives

for Personal

Computers; Testing and fault diagnosis; Glossary; Appendices, including DVD specifications and standards: Index

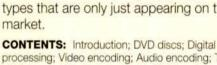August 2003 336pp 234 x 156mm 150 illustrations Paperback ISBN 0750657367




CLOSED CIRCUIT TELEVISION


CCTV Installation, Maintenance and Operation

Second Edition

Joe Cieszynski £24.99



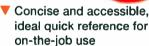

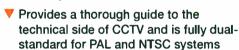

CCTV is an essential quide for professionals involved in the installation and maintenance of CCTV systems, system design, specification and purchasing and the management of CCTV systems. This book provides a thorough guide to the technical side of the subject from cameras and monitors, video recording, cabling and transmission through to installation and maintenance.

CONTENTS:The CCTV industry: Signal transmission and cabling; Light and lenses; Lighting technology; Television fundamentals; The camera; Monitors; Video recording; Switchers; Telemetry and integrated alarm systems; Motion detection; Commissioning and maintenance; Ancillary equipment; Glossary; Index

September 2003 320pp 156 x 234mm 150 illustrations Paperback ISBN 0750657286

VALVE AMPLIFIERS

Third Edition


Morgan Jones £29.99



Valve

Amplifiers

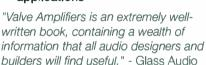The definitive modern guide to tube amplifiers for home and professional audio applications



Valve Amplifiers has been widely recognised as the most complete guide to valve amplifier design, modification, analysis, construction and maintenance written for over 30 years. Design principles and construction techniques are provided so readers can devise and build from scratch designs that actually work. Practical aspects, including safety, and other essentials of design are addressed throughout in the familiar context of current best practice in electronic design. using only currently available components.

CONTENTS: Preface; Circuit analysis; Basic building blocks; Distortion; Component technology; Power supplies; The power amplifier; The pre-amplifier; Appendix; Index

August 2003 640pp 156 x 234mm 300 illustrations Paperback ISBN 0750656948

NEWNES PC TROUBLESHOOTING POCKET BOOK


Third Edition

Howard Anderson Mike Tooley

£17.99



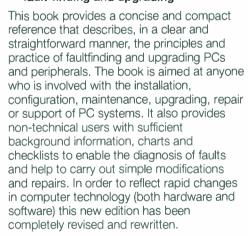▼ All the essential data for PC fault-finding and upgrading



CONTENTS: PC fundamentals; System architecture and construction; Processor types and families; Support devices; Semiconductor memory; The parallel printer interface; The serial communications ports; The PC expansion bus; Floppy disk drives; Hard disk drives; Viruses; Displays; DOS system configuration; Windows troubleshooting; Tools and test equipment; Reference section; Diagnostic software; Index

August 2003 256pp 110 x 190mm 60 illustrations Hardback ISBN 0750659882



NEWNES GUIDE TO TELEVISION AND VIDEO TECHNOLOGY

Third Edition

Eugene Trundle

£17.99

BESTSELLER

'A truly accessible guide to TV technology and the Digital revolution. Essential information for all servicing students and professionals.' - Electronic Servicing & Technology

'Newnes Guide to Television and Video Technology is essential reading for service engineers and electronic servicing students.' -Digital Broadcasting, 2001

The third edition of the Newnes Guide to Television & Video Technology is the definitive guide to analogue and digital TV technology. Eugene Trundle explores the fundamentals of Digital TV (satellite, cable and terrestrial) and Digital Video, as well as providing a thorough grounding in analogue systems.

CONTENTS: Basic television; The PAL system; Transmission and reception; Colour decoding; The TV receiver; Teletext; PAL-Plus, MAC and enhanced TV; Digital TV; Satellite TV; Cable TV; Development of video tape recording; Video tape; Signal processing; Signal processing; Servo systems and motor drive; System control for VCRs; The complete VCR; Tape formats compared; DVD players; Index

February 2001 464pp 138 x 216mm Paperback 291 illustrations ISBN 0750648104

NEWNES GUIDE TO DIGITAL TV

Second Edition

Richard Brice £24.99

 A uniquely concise and readable guide to the technology of digital television

Newnes Guide to Digital Television provides a down-to-earth guide to all aspects of digital TV, encompassing the electronics of the equipment, broadcast applications, installations and servicing, and the different transmission methods - terrestrial, satellite and cable. It provides an overview of digital TV for specialists in any one area as well as an introduction for those who want to gain a basic grasp of the technology. The second edition has been updated with all the key developments, and includes new and expanded sections on digital video interfaces, DSP, DVD, video servers, automation systems, HDTV, 8-VSB modulation and the ATSC system.

CONTENTS: Foundations of television; Digital video and audio coding; Digital signal processing; Video data compression; Audio data compression; Digital audio production; Digital video production; The MPEG multiplex; Broadcasting digital video; Consumer digital technology; The future; Index

October 2002 304pp 234 x 156mm 4 illustrations Paperback ISBN 0750657219

VIDEO DEMYSTIFIED

Third Edition

Keith Jack £50.00





Provides international coverage

'Video Demystified is a one-of-a-kind book. Anyone who designs multimedia or digital-video products will most certainly benefit from reading it.' - Electronics Handbook

This book contains expanded coverage of digital video processing technologies, video compression, digital video interfaces, and the MPEG1 and MPEG2 standards. Also Included within the book are two CDs, which provide video test files for MPEG1, MPEG2, H261, and H263 and an electronic version of the book. This is by far the most informative analogue and digital video reference available.


Included is a list of references at the end of each chapter, along with a 50-page glossary at the end of book.

CONTENTS: Introduction to video; Colour spaces: rgb, yuv, yiq, ycbcr, photoycc, his, hls, and hsv; chromaticity; non-rgb space considerations; Gamma correction; Video signals overview: Analog video interfaces: Digital video interfaces: Digital video processing: Sdtv-Hdtv Ntsc, Pal, and secam overview: Ntsc ntsc and pal digital encoding and decoding: Smpte 314m; Aaux; Vaux; IEEE digital television; Atsc; Dvb: Index

May 2001 784pp 180 x 234mm Paperback 2 CD ROMS ISBN 1878707566

DICTIONARY OF VIDEO AND TELEVISION TECHNOLOGY

Keith Jack Vladimir Tsatsoulin £29.99

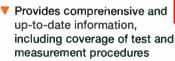

Electronic version of the book accompanies text





CD Rom

'It gives concise but thorough explanations of essential concepts and terms in video and television and is the most complete dictionary covering this fast-paces field.' -Electronic Engineering Times


This up-to-date reference contains virtually all the terminology commonly used in modern global video and television technology, with thorough definitions aimed at the engineering level. It covers all international video standards, digital and analogue video signals, data compression, video conferencing, encoding/decoding—indeed, every term associated with video/television technology.


CONTENTS: Contains thousands of terms and their definitions in alphabetical order

November 2002 322pp 178 x 228mm Paperback with CD-ROM ISBN 187870799X

SERVICING TV, SATELLITE AND VIDEO EQUIPMENT

Eugene Trundle £21.99

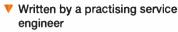

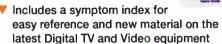

'A genuinely practical hands-on guide for service engineers, including a section on the latest digital equipment.' The Engineers Journal

Based on many years of practical bench and field experience, the book wastes little space on theoretical principles and circuit description where it is well covered elsewhere: here the emphasis is on the practical business of fault diagnosis and repair. Includes a symptom index for easy reference and new material on the latest Digital TV and Video equipment.

CONTENTS: Test and diagnostic equipment; Power supplies; Line timebase; Field timebase; Luminance and decoder; Tuners and vision receivers; Audio receiver section; TV control systems; Picture tubes; Teletext decoders; Video deck mechanics; System control in VCRs; Servos and motors; VCR luminance section; VCR chroma stages; VCR audio servicing; Camera section, clock; Display and timer circuits; Dealing with intermittent faults; Repair techniques; Safety; BEAB and BS415; Digital TV; Symptom index

November 2001 336pp 189 x 246mm Paperback ISBN 0750655070

VIDEO AND CAMCORDER SERVICING AND TECHNOLOGY

Fifth Edition

Steve Beeching £20.99

This book provides fully up-to-date coverage of the whole range of

current home video equipment, analogue and digital. It is the key to successful servicing of VCRs and camcorders and cover the new generation of video equipment: DVD and hard disk recording (MPEG2).

As well as traditional VCRs the scope of Video and Camcorder Servicing and Technology includes the full range of video cameras designed for home use and editing systems, and the latest DVD and hard-disk equipment.

'It furnishes readers with everything they need to know about troubleshooting and repairing traditional VCRs, video cameras designed for home use and editing systems, and the latest DVD equipment.' Poptronics

CONTENTS: Magnetism and magnetic recording; Azimuth tilt technique; Frequency modulated recording and playback; Motor control and servomechanisms; Colour recording and playback; Systems control; Long play; Hi fi audio; Still pictures and slow motion; Carncorders; Digital carncorders; MPEG and D-VHS; Editing; PDC and IEEE1394; Soldering and desoldering; Index

April 2001 320pp 189 x 246mm 150 illustrations Paperback ISBN 0750650397



NEWNES TV AND VIDEO ENGINEER'S POCKET BOOK

Third Edition

Eugene Trundle

£17.99

BESTSELLER



'A gem of a book... can be used by service engineers throughout the world.' Elektor Electronics

This well-known book is an essential tool for every service engineer, and an extremely useful reference source for a wide range of engineers, students, sales and installation staff. The third edition has been thoroughly updated to include digital and other new technologies, with new chapters on digital camcorders and VCRs, digital television, Dolby sound systems, and home cinema.


CONTENTS: Components and assemblies; Television and video waveforms and standards; Satellite TV; TV signal processing; Teletext and viewdata; Nicam stereo sound; Timebase circuits; Power supply systems; Video on magnetic tape; Video recorder signal processing; Servo systems; Video recorder deck control; Audio record and playback; Control systems; Test equipment and fault diagnosis; Digital TV; Digital Camcorders and VCRs; Dolby sound systems and home cinema; Reference data; Index


October 1999 503pp 105 x 190mm 1 illustration Hardback ISBN 0750641940

NEWNES SERVICE ENGINEER'S POCKET BOOK

Geoff Lewis lan Sinclair

£14.99

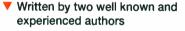

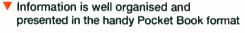

This Pocket Book aims to provide the service engineer with all the necessary information to carry out work on domestic electronics equipment. Packed full of data, tables of standard values, formulae and charts, this useful and portable little book will be both an essential reference for all those working in consumer electronics and a handy revision aid for students.

CONTENTS: General faultfinding; The workshop; Basic circuits; Power supplies; Aerials, feeders and propagation; Audio systems; Television and teletext receivers; Satellite television systems; Video recorders and cameras; Television distribution systems or Community Area Television (CATV); Index

April 1998 256pp 90 x 190mm 1 illustration Hardback ISBN 0750634480

FURTHER INFORMATION

All publication dates, prices and other details are correct at time of going to press but may be subject to change without further notice.

Enquiries about late publication dates should be addressed to:

lan Seager Newnes, Linacre House, Jordan Hill, Oxford OX2 8DP,UK

> Tel: +44 (0)1865 314464 Fax: +44 (0)1865 314572

PRACTICAL ELECTRONIC FAULT FINDING AND TROUBLESHOOTING

Robin Pain £21.99

'Robin Pain has put down in words (almost entirely free of maths) the experience of many years practical work on audio, radio, TV and computer equipment.' Electronics Education

It isn't enough to be able to design. It isn't even enough to be able to debug. To be a real faultfinder, you must be able to get a feel for what is going on in the circuit you are examining. In this book Robin Pain explains the basic techniques needed to be faultfinder.


CONTENTS: Voltage, current and resistance; Capacitance, inductance and impedance; Diodes, transistors, op amps and negative feedback; Analogue fault finding techniques; Audio frequency; Radio frequency; Digital fault finding techniques; Discrete logic; Serial interfaces; Parallel interfaces; Microprocessor systems; Memory; Addressing; Microprocessor action; I/O control; CPT control; Dynamic RAM; Microprocessor systems: Fault finding techniques; Fault finding; Memory problems; Appendices; Index

April 1996 240pp 156 x 234mm 1 illustration Paperback ISBN 0750624612

AUDIO AND HI-FI HANDBOOK

Revised Edition

lan Sinclair £31.99

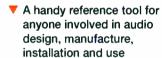

 A comprehensive - and comprehensible guide to audio electronics

Written by a team of experts and specialist contributors, this comprehensive guide has proved to be an invaluable resource for professional designers and service engineers. The third edition includes new chapters on servicing, Nicam stereo and digital satellite radio. For the first time in paperback, this revised edition features a completely new chapter on the most recent digital developments, CD-R/RW, HDCD, Internet audio, MP3 players and DAM-CD.

CONTENTS: Sound waves and acoustics; Studio acoustics; Microphones; Sound synthesis; Introduction to digital principles; Compact disc technology; Other digital systems (DAT, NICAM, DCC, MD); DVD audio standards; MP3 music on the internet; Nicam and satellite radio; Analogue tape recording; Noise reduction systems; The LP record; Disc reproduction; Tuners and radio receivers; Preamps and inputs voltage amplifiers/controls; Valve amplifiers; Loudspeakers; Loudspeaker enclosures; Headphones; Public address; In-car audio; Servicing; Interconnections; Index

October 2000 480pp 189 x 246mm Paperback ISBN 0750649755

NEWNES DICTIONARY OF ELECTRONICS

S W Amos R S Amos £12.99

Practical Electronic

Fault Finding and

Troubleshooting

AUDIO & HI-FI



 A concise glossary for electronics, TV, radio and computing

Includes a handy appendix of acronyms

The Newnes Dictionary of Electronics has become an essential item on the bookshelves of electronics engineers, managers, technicians, students and enthusiasts. The book is in a convenient compact format that makes it an ideal working dictionary. The definitions are clear and concise, supported by numerous illustrations and circuit diagrams.

'The Newnes Dictionary of Electronics has become an essential item on the bookshelves of electronics engineers, managers, technicians, students and enthusiasts. The definitions are clear and concise, supported by numerous illustrations and circuit diagrams.' EPN

CONTENTS: Listing of electronics terms

March 2002 389pp 138 x 216mm 300 illustrations Paperback ISBN 0750656425

PC SYSTEMS, INSTALLATION AND MAINTENANCE

Second Edition

R. P. Beales £19.99

in the field



Updated throughout to cover new technologies and latest developments

 Additional website resources feature colour figures to download, appendices and web links

Written in a straightforward, easy to read style, Rob Beales provides the knowledge and techniques needed to build, troubleshoot, and maintain persona: computer systems. Updated throughout in line with current technologies this is THE PC hardware handbook for students, IT support staff, small business users and home office users covering the set-up, running and maintenance of PC systems.

CONTENTS: PC hardware technology: The PC defined; The system-unit; Peripherals; Networks. assembling, Configuring and upgrading: Building a complete PC system. Systems support: Routine maintenance and troubleshooting; Health & safety: Glossary

September 2003 448pp Paperback 111 Illustrations ISBN 0750660740

For more information on these and other Newnes books please go to www.Newnespress.com

MULTIFUNCTION PERIPHERALS FOR PCS

Technology, Troubleshooting and Repair

Marvin Hobbs £25.99

This resource explains how multifunction peripherals work in theory and in practice, with lots of hands-on examples and important troubleshooting and repair tips. -Poptronics

Multifunction devices combine the essentials of a fax machine, printer, scanner, and copier into one peripheral for small and home offices. As the market for this equipment grows, the need for skilled repair and maintenance increases. Unfortunately the service documentation supplied by the manufacturers is completely inadequate making the repair jobs even harder and more expensive. Marvin Hobbs teaches you how multifunction peripherals work in theory and in practice with lots of hands-on examples and important troubleshooting and repair tips you don't want to miss.

CONTENTS: Diagnostics and maintenance; Ink jet Printers in MFD machines; Laser and LED printers in MFD machines; Thermal printers; Scanners; Fax function; PC software for printer control; Standards and protocol; Consumables; Glossary; Abbreviations; References

February 2000 232pp 178 x 254mm 234 illustrations Paperback ISBN 0750671254

ELECTRONIC CLASSICS

Collecting, Restoring and Repair

Andrew Emmerson £21.99

- A highly popular type of 'modern antique'
- Covers technical aspects of classic valve-based circuitry
- The most complete work for vintage audio and TV enthusiasts, dealers and repairers

"What an amazing collection of information!...This is a book which should be in every vintage radio enthusiast's reference library. Radiobygones

This highly readable book encompasses all aspects of buying, collecting, restoring, repairing, sourcing parts, professional services, clubs and societies, etc. Covering the technical side as well as collecting, this book offers the most comprehensive coverage available. The most complete work for vintage audio and TV enthusiasts, dealers and repairers.

CONTENTS: Repairing and restoring; First-line repairs; Electrical components; Cabinet and chassis; Finishing off a set; Buyer's guide - where to find parts; Service data - where to find it; Professional services directory; Clubs and societies; Recommended reading; Museums and other places to see professional restorations; Keeping track of your collection; What's it worth; Patronising dealers; Buying at auctions and antique fairs; Collector's luck; Safety; References; Index

August 1998 400pp 156 x 234mm 1 illustration Paperback ISBN 0750637889

TELEVISION IC DATA FILES

Second Edition

John Edwards £18.99

Over 30% new material

The second edition covers over 70 ICs not included previously, making this book an essential update for the many service engineers who have discovered that John Edwards books are a vital workshop tool. However, the purpose of the book remains to cover the devices most frequently found faulty in television sets in production since the late 1980s, so all the key ICs will still be found here.

CONTENTS: A collection of television ICs files presented in alphabetical/numerical order

January 2000 256pp 156 x 234mm Paperback ISBN 0750645814

VCR IC DATA FILES

John Edwards £20.99

Due to the increasing complexity of television and video equipment there is a growing need for service information that is current, accurate, affordable and readily available. The purpose of this book is to provide the workshop technician and the field engineer with a valuable and convenient method of fault finding without the need to consult workshop manuals which are often expensive or indeed out of stock.

CONTENTS: A collection of VCR ICs files presented in alphabetical/numerical order

July 1998 448pp 156 x 234mm 1 illustration Paperback ISBN 0750639938

TELEVISION MICROPROCESSOR IC DATA FILES

John Edwards £19.99

- ▼ Comprehensive cover of most commonly used ics
- Convenient reference for working engineer

Complementing the first volume in this series, Television IC Data Files, the most popular microprocessor ICs used in televisions are covered here. Each device is presented graphically with the relevant data information given against each pin to enable the engineer to quickly compare voltage measurements and signal in/out data on a faulty device, with those in the book. All the measurements and signal data in the book were taken under actual working conditions.

CONTENTS: A collection of television microprocessor ICs presented in alphabetical/numerical order

March 1997 240pp 156 x 234mm Paperback ISBN 0750633352

TELEVISION

TV FAULT FINDING GUIDE

Peter Marlow £20.99

▼ Real repair and troubleshooting info - not just cribs from manufacturers' data sheets



Peter Marlow's **TV Fault Finding Guide** is a distillation of the most used fault reports from 11 years of Television magazine. Arranged by make and model the information is extremely easy to access, and the book is a convenient size for the bench or to carry with you. Unlike other fault guides, this one is based on top quality information from leading authorities, and genuine repair case studies. This is real-life servicing information, not just a compilation of manufacturers' manuals.

CONTENTS: Introduction; A-Z of manufacturers and models

March 2000 400pp 156 x 234mm Paperback ISBN 0750646330

VCR FAULT FINDING GUIDE

Peter Marlow £20.99

▼ Approximately 2,000 reports on 193 models from 35 different manufacturers



 Instant on-the-spot diagnosis and repair advice


This book is an essential repair and troubleshooting tool from an experienced Television magazine author. Unlike other fault guides, this one is based on top quality information from leading authorities, and genuine repair case studies. This is real-life servicing information, not just a compilation of manufacturers' manuals. This will undoubtedly become one of the service engineer's most useful tools.

CONTENTS: Introduction; A-Z of manufacturers and models

March 2000 464pp 156 x 234mm Paperback ISBN 0750646349



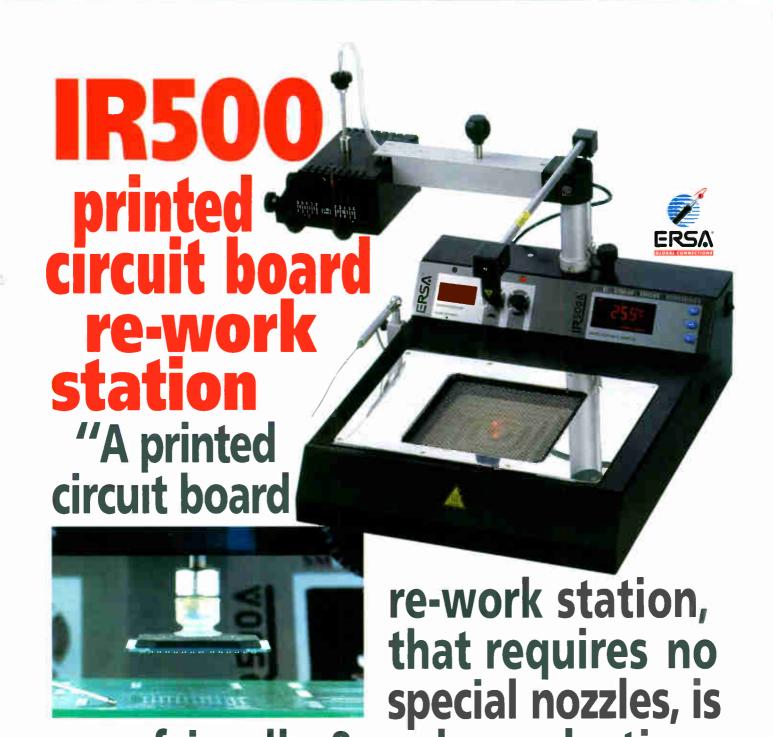Why not register to receive our monthly eNews. We will send you details on our latest publications, regular discounts, free sample chapters, relevant information and more. To subscribe either fill in the form overleaf and tick the box or alternatively go to www.newnespress.com



user friendly & makes selective

removal & replacement of all types of components easy, without damage"



PRODUCTION EQUIPMENT




tel: 024 7647 3003 www.blundell.co.uk sales@blundell.co.uk

203 Torrington Ave, Coventry West Midlands, CV4 9UT, UK


TELEVISION TEST PATTERN GENERATORS

The new GV 998 is a digital pattern generator offering more advanced features at again a realistic price. Those features include :

- ◆ MPEG-2 format Transport Stream generation
- Video and audio included in the TS
- Video and audio inputs
- Generation of a variable frequency sound carrier for decoding verification
- Multistandard and multisystem analogue TV signal generation
- Possibility to edit different fields of the TS database to present the name of the service provider
- Remote control via a personal computer
- Moving video patterns to check MPEG-2 decoders

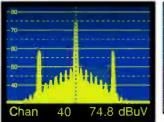



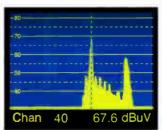

PROMAX



PROMAX GV SERIES

- Choice of 12 instruments
- NICAM and Teletext
- 4:3 and 16:9 Formats
- Full field and VITS
- Computer Controlled
- Front panel memories
- Own Company Logo
- Computer Monitor testers
- Hand Held Models
- Multi Standard, PAL, NTSC, SECAM
- High Quality Construction
- ◆ Attractive Price Levels ◆ Full After Sales Service
- Available from Stock















PROMAX

SELECTED ITEMS FROM THE PROMAX RANGE OF TEST EQUIPMENT



Analogue and Digital Satellite Detector.



PRODIG 1

Satellite Dish Installer's Meter Does more than just BSkyB




PRODIG 2

Analogue & Digital Aerial Meter Measures digital channel power and C/N



MC 377+

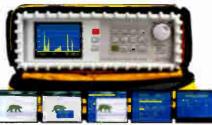Analogue & Digital, Satellite & Terrestrial Measures channel power and C/N



PROLINK 3 + 4 SERIES

Satellite & Terrestrial, Analogue & Digital, Spectrum Analyser with BER (optional on P3)

Alban

ALBAN ELECTRONICS LIMITED

THE PROMAX SERVICE CENTRE

6 Caxton Centre, Porters Wood, St. Albans, Hertfordshire, AL3 6XT.

TEL: 01727 832266 FAX: 01727 810546

WEB: www.albanelectronics.co.uk EMAIL: info@albanelectronics.co.uk

SALES + SERVICE + CALIBRATION



TELECOMMUNICATIONS TEST EQUIPMENT

AE 767 Spectrum Analyser



