

SERVICING TV RECEIVERS

Practical Television 16

APRIL 1960

AND TELEVISION TIMES



CONTENTS

CONSTRUCT YOUR OWN ABACS
CATHODE FOLLOWER VOLTMETER
THE SAFETY FACTOR IN MODIFICATIONS
TWO INTO ONE — 2
UNDERNEATH THE DIPOLE
ETC. ETC. ETC.

TELEVISION SPARES

All Makes All Models By return of post

**LINE OUTPUT TRANSFORMERS FRAME OUTPUT TRANSFORMERS
DEFLECTOR COILS**

LINE AND FRAME BLOCKING OSCILLATOR TRANSFORMERS

ALL POTENTIOMETER AND SLIDER CONTROLS

MAINS DROPPERS

METAL RECTIFIERS

GERMANIUM DIODES

FOCUS MAGNETS

ION TRAPS

E.H.T. CONDENSERS

Our Range of Spares is probably the most extensive in the country and includes all Spares for Tape Recorders, Radio and Record Player Units.

Technical Advice Free. Service Manuals supplied on loan.

Terms: C.W.O. or C.O.D. All Components are supplied at list prices, plus 2.6 p.p.

Please enclose S.A.E. with all enquiries.

NEWBURY RADIO

272, ROMFORD ROAD, FOREST GATE, LONDON, E.7.

MARyland 3100

ADCOLA

(Regd. Trade Mark)

SOLDERING EQUIPMENT

THE INSTRUMENTS CREATED
FOR THE DISCRIMINATING
USER.

British & Foreign Pats., Regd.
Designs, etc.

ILLUSTRATED
Protective Shield
(Cat. No. 68)
Instrument $\frac{1}{8}$ " Bit
(Cat. No. 70)

The ideal combina-
tion for transistor
and other intricate
work.



Apply direct for catalogues:—

ADCOLA PRODUCTS LTD.,

**GAUDEN RD.,
CLAPHAM HIGH ST.,
LONDON, S.W.4.**

Telephones
MACaulay 4272 and 3101

TELEVISION TUBES REBUILT

**A NEW GUN IN EVERY TUBE
BUY DIRECT FROM THE FACTORY!**

12 MONTHS' GUARANTEE

12" - - - - £5. 0.0

14" - - - - £5.10.0

17" - - - - £6.10.0

Immediate dispatch on receipt of Remittance

SPECIAL TERMS TO THE TRADE
Carriage and insurance 12/6 extra

MARSHALLS for TELEVISION LTD.


131 St. Ann's Road, Tottenham,
London, N.15. STAmford Hill 3267

A REVOLUTIONARY NEW BRITISH INVENTION!

- ★ Uses standard tapes
- ★ Plays at 7½" per. sec. or 3 other speeds
- ★ Records direct from radio or microphone
- ★ Erase and fast rewind

£13.12s

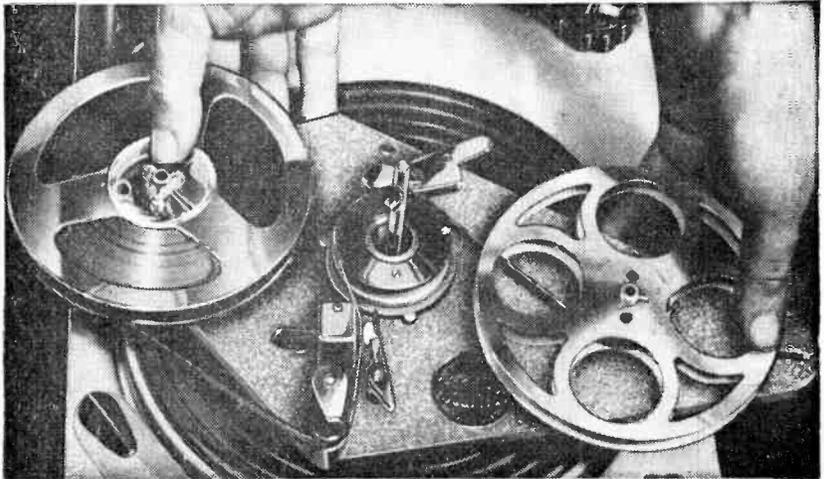Special moving-coil microphone and tape extra.
EASY TERMS



Instantly turns any gramophone into a first-class Tape-Recorder and back into a record-player in a moment!

Gramdeck is completely new . . . a revolutionary and ingenious invention that instantly turns your gramophone into a tape-recorder and back into a gramophone at will! Slip the Gramdeck on to your turntable and you have the finest tape-recorder you've ever heard! Lift it off . . . your gramophone is ready to play records again. There are no motors or valves to go wrong—and you get a quality that has to be heard to be believed! Everyone is praising the Gramdeck.

"The quality is at least equal to that obtained from a good microgroove disc." says a leading professional journal.

"Ingenious—simple . . . why on earth did no one think of it before!"—THE TAPE RECORDER. "Thoroughly recommended."—GRAMOPHONE RECORD REVIEW. "Quality of reproduction excellent . . . real hi-fi results . . . potential is tremendous . . . both designer and manufacturer should be congratulated."—BRITISH RADIO & T/V RETAILERS REVIEW.

"Better than many so-called hi-fi recorders . . . robust . . . carefully designed . . . excellent value."—AMATEUR CINE WORLD.

WORKS FROM ANY RECORD-PLAYER OR RADIOGRAM

Gramdeck records and reproduces with a wonderful depth and breadth of tone. Because it uses equipment that is already in your gramophone it only costs a fraction of the high-quality tape-recorder you would normally require. Full details, specifications, photographs, easy terms, etc., are given in the Gramdeck Book. Send for your FREE copy, today.

MADE BY THE FIRM THAT MAKES RADAR EQUIPMENT FOR VISCOUNTS & BRITANNIAS

FREE BOOK—POST NOW!

I would like to know how to turn my gramophone into a first-class tape-recorder . . . please send me the Gramdeck Book—FREE and without obligation.

((Write if you prefer not to cut page))

NAME _____

ADDRESS _____

Gramdeck (Dept. PT/807) 29 Wright's Lane
Kensington, London, W.8

Gramdeck
GRAMOPHONE TAPE RECORDER
HIGH QUALITY TAPE-RECORDING FOR EVERY HOME

GRAMDECK TURNS A TURNTABLE INTO A TAPE-RECORDER



BENTLEY ACOUSTIC CORPORATION LTD.

THE VALVE SPECIALISTS. 38 CHALCOT ROAD, LONDON, N.W.1. Telephone: PRIMROSE 9090

EXPRESS POSTAL SERVICE! ALL ORDERS DESPATCHED SAME DAY AS RECEIVED. FOR ONLY 2/6 EXTRA TELEPHONE FOR THAT URGENT ORDER TO BE DESPATCHED IMMEDIATELY BY OUR SPECIAL C.O.D. SERVICE.

ANY ORDER INSURED AGAINST DAMAGE IN TRANSIT FOR ONLY 6/6 EXTRA.

0A2	17/6	6C8	12/6	6X4	6/6	198G6G	7475	7/6	EABC80	9/6	EL41	9/6	LN152	10/6	QS150/15	10/6	UCH81	9/6	
0B2	17/6	6C9	12/6	6X5GT	6/6		9002	5/6	EAC91	7/6	EL42	13/11	LN309	11/6		10/6	UCL82	11/6	
OZ4	6/6	6C10	10/6	6/30L2	10/6	19H1	10/6	AC/PEN	EAF42	9/6	EL81	12/6	MH4(C)	7/6	R12	9/6	UCL83	19/3	
IA3	3/6	6CD6G	36/6	7A7	12/6	20D1	15/3	5-pin 23/3	EB34	2/6	EL84	8/6	MHL4	7/6	R18	14/6	UF41	9/6	
IA5	6/6	6CH6	12/6	7B6	21/3	20F2	26/6	7-pin 15/6	EB41	8/6	EL85	13/11	MHLD6	12/6	R19	19/11	UF42	12/6	
IA7	15/6	6D3	19/11	7B7	8/6	20I1	26/6	AC2PEN/	EB91	5/6	EL91	9/6	ML4	12/6	S130	15/6	UF80	10/6	
IC5	12/6	6D6	6/6	7C5	8/6	20P1	26/6	DD 26/6	EB33	23/3	EL95	10/6	MU14	9/6	SD6	12/6	UF85	10/6	
ID5	9/6	6E5	12/6	7C6	8/6	20P3	23/3	AC5PEN	EBC33	7/6	EM34	10/6	MX40	15/6	SP4(7)	15/6	UF86	17/11	
ID6	10/6	6F1	26/6	7D8	23/3	20P5	23/3		EB41	8/6	EM71	23/3	N37	19/11	SP41	3/6	UF89	9/6	
IHS5GT	11/6	6F6G	7/6	7H7	8/6	25A6G	11/6	AC6PEN 7/6	EBC81	8/6	EM80	9/6	N78	19/11	SP42	12/6	UL41	9/6	
IL4	6/6	6F6GTM	8/6	7R7	12/6	25L6GT	10/6	AC/SG 23/3	EBF80	10/6	EM81	9/6	N108	19/11	SP61	3/6	UL44	26/6	
ILD5	5/6	6F8	12/6	7S7	10/6	25U4	16/7	AC/TP 32/6	EBF83	13/11	EM84	10/6	N308	20/7	SU25	26/6	UL46	14/6	
ILN5	5/6	6F11	17/3	7V7	8/6	25Y5	10/6	AC/VPI 15/6	EBF89	9/6	EN31	37/6	N339	29/10	SU61	9/6	UL84	8/6	
INS5GT	11/6	6F12	5/6	7Y4	8/6	25Y5G	10/6	AC/VP2 23/3	EBL21	23/3	EY51	9/6	P61	3/6	T41	23/3	UM4	17/3	
IR5	7/6	6F13	11/6	7Z4	18/7	25Z4G	9/6	ATP4	5/6	EBL31	23/3	EY83	16/7	PABC80	TDD4	24/7	UM80	15/3	
IS4	9/6	6F14	26/6	8D2	3/6	25Z5	10/6	AZ1	18/7	EC52	5/6	EY84	14/6		13/11	TH48	15/6	URIC	9/6
IT5	7/6	6F15	15/3	8D3	5/6	25Z6GT	10/6	AZ31	10/6	EC54	6/6	EY86	10/6	PCC84	8/6	TH41	26/6	U06	19/11
IS6	6/6	6F16	9/6	9B5W6	15/3	25Z6GT	10/6	AZ41	13/11	EC70	12/6	EZ35	6/6	PCC85	9/6	TH233	33/2	U07	16/7
IU5	10/6	6F17	12/6	9D2	4/6			B36	24/7	EC92	12/6	EZ40	7/6	PCC88	23/3	TH231	20/6	U08	26/6
2A7	10/6	6F32	10/6	10C1	12/6	27S0	19/11	BL63	7/6	ECC32	10/6	EZ41	7/6	PCC89	14/6	TP22	15/6	U09	7/6
2P	26/6	6F33	7/6	10C2	26/6	28D7	7/6	CI	12/6	ECC33	8/6	EZ80	7/6	PCF80	8/6	TP25	15/6	UY1N	18/7
2X2	4/6	6G6	6/6	10D2	2/6	30C1	8/6	CIC	12/6	ECC34	24/7	EZ81	7/6	PCF82	11/6	TP2620	3/6	UY21	16/6
3A4	7/6	6H6GTG	3/6	10F1	10/6	30F5	7/6	CBL1	26/6	ECC35	8/6	FC2A	24/7	PCL82	12/6	TY86F	13/3	UY41	7/6
3A5	10/6	6H6GTM	3/6	10F9	10/6	30F11	10/6	CBL31	23/3	ECC40	23/3	FC4	15/6	PCL83	11/6	UI12	14	UY85	7/6
3B7	12/6	6H6G	8/6	10LD3	8/6	30L1	9/6	CCH35	23/3	ECC81	8/6	FC13	26/6	PEN44	12/6	UI6	12/6	VMS4B	23/3
3D6	5/6	6J5GTG	5/6	10LD11	3/6	30L5	14/6	CK506	6/6	ECC82	7/6	FC13C	26/6	PEN44	23/3	UI8/20	9/6	VP4(7)	12/6
3Q4	4/6	6J5GTG	5/6		15/11	30P12	8/6	CL33	19/3	ECC83	8/6	FW4/500	9/6	PEN44	26/6	U22	8/6	VP8	15/6
3Q5GT	9/6	6J6	5/6	10P13	15/6	30P16	8/6	CV63	10/6	ECC84	8/6			PEN4D	26/6	U25	29/10	VP2B	14/6
3S4	7/6	6J7G	6/6	10P14	19/3	30P11	11/6	CV271	10/6	ECC85	8/6	FW4/800	9/6	PEN25	26/6	U26	17/11	VP4B	23/3
3V4	7/6	6J7GT	10/6	10D3	24/7	31	7/6	CV428	30/6	ECC88	23/11			PEN25	19/11	U26	9/6	VP13C	7/6
5R4GY	17/6	6K6GT	8/6	12A6	6/6	33A/158M		CY1	18/7	ECC91	5/6	G230	10/6	PEN36	16/6	U31	10/6	VP23	6/6
5U4G	8/6	6K7G	5/6	12A6C	15/3		30/6	CY31	16/7	ECC90	11/6	G232	12/6		10/6	U33	26/6	VP41	6/6
5V4G	11/6	6K7GT	6/6	12AD6	17/3	35/51	12/6	D1	3/6	ECCF82	10/6	G234	14/6	PEN40DD		U35	26/6	VR105/30	
5Y3G	8/6	6K8G	8/6	12AE6	13/11	35A5	21/3	D15	10/6	ECH3	26/6	H30	5/6		25/6	U37	26/6		9/6
5Y3GT	7/6	6K8GTG	8/6	12AH7	8/6	35L6GT	9/6	D63	5/6	ECH21	23/3	H63	12/6	PEN44	26/6	U43	9/6	VR150/30	
5Z3	12/6		12/6	12AH8	12/6	35W4	7/6	D77	5/6	ECH35	9/6	HABC80		PEN45	19/6	U45	9/6		9/6
5Z4G	10/6	6K25	19/11	12AT6	7/6	35Z3	10/6	DAC32	11/6	ECH42	10/6		13/6	PEN45DD		U50	8/6	VT61A	5/6
5Z4GT	12/6	6L1	23/3	12AT7	8/6	35Z4	6/6	DAF91	7/6	ECH81	9/6	HL23	10/6		26/6	U52	8/6	VT501	5/6
6A7	26/6	6L6G	9/6	12AU6	23/3	35Z5GT	9/6	DAF96	9/6	ECH83	13/11	HL23DD		PEN46	7/6	U54	19/11	W61M	26/6
6A8	10/6	6L6M	12/6	12AU7	7/6	41M1TL	8/6	DD41	13/11	ECL80	10/6			PEN383	23/3	U76	6/6	W76	6/6
6AB7	8/6	6L7GT	12/6	12AV6	12/7	42	23/3	DF33	11/6	ECL82	10/6	HL41	12/6	PEN453DD		U78	6/6	W81M	6/6
6AB8	10/6	6L18	13/6	12AX7	8/6	43	12/6	DF66	15/6	ECL83	19/3	HL41DD			33/2	U107	16/7	W107	15/3
6AC7	6/6	6L19	23/3	12BA6	8/6	50C5	12/6	DF70	15/6	EF9	23/3		19/3	PEN/DD		U191	16/7	W729	18/7
6AG5	6/6	6LD3	8/6	12BE6	10/6	50CD6G		DF91	6/6	EF22	14/6	HL42DD		4020	33/2	U201	16/7	X24M	24/7
6AK5	8/6	6LD20	15/11	12BH7	21/3		36/6	DF96	9/6	EF36	6/6		19/3	PL33	19/3	U251	14/6	X31	26/6
6AL5	5/6	6N7	8/6	12E1	30/6	50L6GT	9/6	DF97	9/6	EF37A	8/6	HN309	24/7	PL36	14/6	U281	19/11	X41	15/6
6AM6	5/6	6P1	19/3	12J5GT	4/6	530G	19/11	DH30	15/6	EF39	5/6	HV92	20/7	PL38	26/6	U282	22/6	X6(C)	12/6
6AQ5	8/6	6P25	12/6	12J7GT	10/6	72	4/6	DH63	8/6	EF40	15/6	HV92A	6/6	PL81	12/6	U301	22/6	X61M	26/6
6AT6	8/6	6P28	26/6	12K5	17/11	75	24/7	DH63(Met)		EF41	9/6	KF35	8/6	PL82	8/6	U329	14/6	X63	10/6
6AU6	10/6	6Q7G	8/6	12K7GT	6/6	77	8/6		17/6	EF42	11/6	KK32	21/11	PL83	9/6	U339	16/7	X65	12/6
6AV6	12/6	6Q7GT	11/6	12K8GT	14/6	78	8/6	DH76	6/6	EF50(A)	7/6	KL35	8/6	PL84	12/6	U403	16/7	X66	12/6
6B7	10/6	6R7G	10/6	12Q7GT	6/6	80	9/6	DH77	8/6	EF50(E)	5/6	LL32	24/7	PL820	18/7	U404	8/6	X76M	14/6
6BBG	4/6	6SA7GT	8/6	12SA7	8/6	83	15/6	DH101	28/6	EF54	5/6	KT2	5/6	PM28	12/6	U401	29/10	X78	21/3
6BBGT	5/6	6S7	10/6	12S7	8/6	83V	12/6	DH107	13/11	EF73	10/6	KT33C	10/6	PM12	6/6	U4020	16/7	X79	21/3
6BA6	7/6	6S7GT	8/6	12SG7	8/6	85A2	15/6	DK32	15/6	EF80	7/6	KT36	29/10	PM12M	6/6	UABC80	9/6	X101	33/2
6BE6	7/6	6S7GT	8/6	12SH7	8/6	150B2	15/6	DK40	21/3	EF85	5/6	KT41	26/6	PM24M	21/3	UAF42	9/6	X109	17/3
6BG6G	23/3	6S7GT	8/6	12S7	8/6	185B7	33/2	DK91	7/6	EF86	12/6	KT44	15/6	PM4	10/6	UAF41	12/6	XD(1.5)	6/6
6BH6	9/6	6S7GT	8/6	12SK7	8/6	185BTA	33/2	DK92	10/6	EF89	9/6	KT61	12/6	PM25	59/8	UBC41	8/6	XFG1	18/6
6B16	7/6	6S7GT	8/6	12SQ7	12/6	304	10/6	DK96	9/6	EF9	5/6	KT63	7/6	PM31	16/7	UBC81	11/6	XYF12	9/6
6BQ7A	15/6	6SN7GT	6/6	12SR7	8/6	305	10/6	DL33	9/6	EF92	5/6	KT66	15/6	PM32	17/11	UBF80	9/6	XYF34	17/6
6BR7	23/3	6S7GT	9/6	12TA	10/6	402Pen/A		DL66	15/6	EF97	13/3	KT88	22/6	PM30	7/6	UBF89	9/6	XH(1.5)	6/6
6BW6	10/6	6G5GT	8/6	14B6	19/3		23/3	DL68	15/6	EF98	13/3	KTW61	8/6	PM81	9/6	UBF91	23/3	XSG(1.5)	6/6
6BW7	7/6	6U4GT	12/6	14H7	23/3	807	7/6	DL92	7/6	EC32	8/6	KTW62	8/6	PM82	9/6	UBC84	14/7		
6BX6	7/6	6U5G	7/6	14S7	27/10	956	3/6	DL94	7/6	EL32	5/6	KTW63	8/6	PM83	9/6	UBC85	9/6	Y63	6/6
6C4	7/6	6U7G	8/6	15D1	26/6	1821	16/7	DL96	9/6	EL33	12/6	KTZ41	8/6	PM30	19/11	UCF80	16/7	Z63	10/6
6C5G	6/6	6V6G	7/6	18	23/3	5763	12/6	DM70	7/6	EL34	15/6	KTZ63	10/6	OP21	7/6	UCH21	23/3	Z66	20/6
6C6	6/6	6V6GTG	8/6	19AQ5	10/6	7193	5/6	EAS0	2/6	EL38	26/6	L63	6/6	OP25	15/6	UCH42	9/6	Z77	5/6

BEST BRANDS ONLY. MAZDA, MARCONI, MULLARD, PHILIPS, TELEFUNKEN, AMERICAN, EUROPEAN, ETC. FREE! TRANSISTOR AND GERMANIUM DIODE DATA AND PRICE LIST. S.A.E. PLEASE.

NEW METAL RECTIFIERS—FULLY GUARANTEED

DRM-1B	15/4	RM-1	7/6	WX3	3/6	14A100	27/6	14RA 1-2-8-2	17/6	16RE 2-1-8-1	8/6
DRM-2B	16										

LOOK!!

A GENUINE UNREPEATABLE OFFER

Absolutely Brand New 12" and 14" CATHODE RAY TUBES

Made by one of England's leading manufacturers

Because of a very special bulk purchase we are able to offer the home constructor and the amateur repair mechanic absolutely brand new 12" and 14" TV Tubes at the fabulously low prices of:-

12" **£5.5.0** 12"

14" **£6.6.0** 14"

Carriage and Insurance paid

These tubes are not reconditioned, or "seconds," or export rejects, but
**BRAND NEW BOXED STOCK DIRECT FROM THE FACTORY AND MADE AVAILABLE BY A
 SPECIAL BULK PURCHASE WHICH IS UNREPEATABLE**

Direct Replacements for MW31-16, MW31-74, C12FM, 121K, 12XP4, etc., and MW36-24, MW36-44, C36-24, C14HM, 141K, 14LP4, 14KP4A, etc., respectively.

Unconditionally guaranteed for full twelve months from date of purchase if returned securely packed.

Take advantage of this special bargain now. Orders executed by return. Send cash, cheques, etc., with order to

St. James's General Trading and Investment Co. Ltd.

2 SERJEANT'S INN, LONDON, E.C.4

Please note that we are MAIL ORDER only. We regret that we cannot cater to callers.

STOP PRESS.—NEW 10" and 15" Tubes also available at give-away prices. Send your inquiries now.

D.C. OSCILLOSCOPE



A.C. MAINS 200-250 VOLTS
SIMPLIFIED SERVICING
PROBLEMS WHEN USING

THE 'TESTGEAR' SCOPE 3in. D.C. OSCILLOSCOPE


Engineered to precision standards, this high-grade instrument is made available at the lowest possible price, incorporating the essential features usually associated with luxury instruments.

This "SCOPE" will appeal particularly to Service Engineers and Amateurs. A high gain, extremely stable differential

Y-amplifier (30 mV/C.M.). Provides ample sensitivity with A.C. or D.C. inputs. Especially suitable for measurement of transients or operating conditions where maintenance of D.C. levels is of paramount importance. Push-pull X amplifier: Fly-back suppression; Internal Time-base Scan Waveform available for external use; pulse output available for checking T.V. Line 60/50 Transformers, etc.; Provision for external X 1/1 and 1/10. Brightness Modulation. Size 10in. high, 6in. wide, 9in. deep. Wgt. 11 lbs. £15.15.0. plus P. & P. 7/8, or 30/- deposit, plus P & P 7/6 and 12 monthly payments of 28/6.


FULL 12 MONTHS' GUARANTEE INCLUDING VALVES AND TUBE. ALIGNMENT ANALYSER TYPE MC12

A.C. mains 200/250V. Provides: "Wobulator" (Sweep Frequency) operation, for FM TV alignment linear frequency sweep up to 12 Mc/s. From 400 kc/s-40 Mc/s. Capacitance Measurement. Two ranges provided 0-60pF and 0-120pF. Special Facility enables true resonant frequency of any tuned circuit, transformer, etc., to be rapidly determined. Cash price £6.19.6. plus 5/- P. & P. H.P. terms 25/- deposit plus 5/- P. & P. and six monthly payments of 21/6

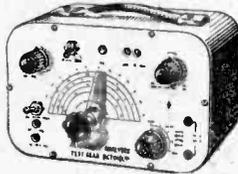

WOLSEY 3-ELEMENT FOLDED DIPOLE
I.T.V. Aerial less mounting bracket for External use, complete with 12 yds. of coaxial cable. 15/-; 4 element, 17/6; 5 element, 25/- P. & P. on above. 3/6.

LINE E.H.T. TRANSFORMER

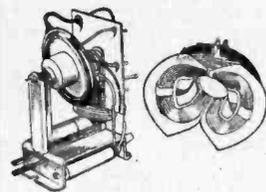

With built-in line and width control 14 KV. Scan coil, 90° deflection, on ferrite yoke. Frame C.P. transformer 18 KV. smoothing condenser. Can be used for 14in., 17in. or 21in. tubes. Complete with circuit diagram.

29/6 Plus 4/- P. & P.

Focus Magnet suitable for the above (state tube). 10/- Plus 2/6 P. & P.

F.M. TUNER UNIT

by famous German manufacturer. Coverage 88-100 Mc/s. Complete with ECC85, size 4in. x 2in. x 2in.

25/- P. & P. Circuit Diagram 1/-

FREE with Unit.

10.7Mc/s. I.F. and Discriminator Coil, 4/- pair.

MAINS TRANSFORMERS

All with tapped primaries. 200-250 volts, 0-160, 180, 200 v., 60 ma. 6.3 v. 2 amps. 10/6. 320-0-320 v. 75 ma., 6.3 v., 2.5 amp., 5 v., 2 amp., 19/6. 280-0-280, 80 ma. 6.3 v. 2 amp., 6.3 v. 1 amp., 10/6. Postage and packing on the above, 3/-.

AC/DC POCKET MULTI-METER KIT




Comprising 2in. moving coil meter scale calibrated in AC/DC volts, ohms and milliamperes. Voltage range AC/DC 0-50, 0-100, 0-250, 0-500. Milliamps 0-10, 0-100. Ohms range 0-10,000. Front panel, range switch, wire-wound pot. (for ohms zero setting), toggle switch, resistor and rectifier. In grey hammer finish case.

19/6 Plus Built and tested P. & P. 1/6 7/8 extra.

Point to point wiring diagram 1/-, free with kit.


SIGNAL GENERATORS

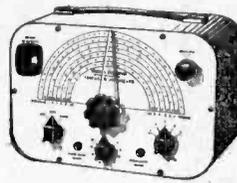

£6.19.6 or 25/- deposit and 6 monthly payments of 21/6. P. & P. 5/- extra. Coverage 100 Kc/s-100 Mc/s on fundamentals and 100 Mc/s to 200 Mc/s on harmonics. Metal case 10in. x 6in. x 5in., grey hammer finish. Incorporating three miniature valves and Metal Rectifier. A.C. Mains 200/250. Internal Modulation of 400 c.p.s. to a depth of 30%; modulated or unmodulated R.F. output continuously variable 100 milli-volts, C.W. and mod. switch, variable A.F. output. Incorporating magic-eye as output indicator. Accuracy plus or minus 2%

Cash £4.19.6 or 25/- deposit and 4 monthly payments of 21/6. Plus Postage and Packing, 5/-


Coverage 120 Kc/s-84 Mc/s. Metal case 10in. x 6in. x 4in. Size of scale, 6in. x 3in. 2 valves and rectifier. A.C. mains 230-250 v. Internal modulation of 400 c.p.s. to a depth of 30%. modulated or unmodulated R.F. output continuously variable. 100 milli-volts. C.W. and mod. switch variable A.D. output and moving coil output meter. Grey hammer finished case and white panel. Accuracy plus or minus 2%

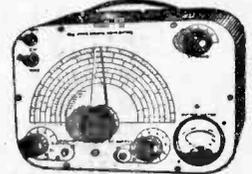

SIGNAL & PATTERN GENERATOR

£6.19.6. P. & P. 5/-.

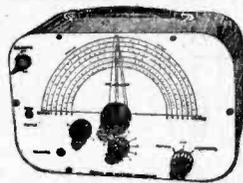
Or 25/- deposit, P. & P. 5/- and 6 monthly payments of 21/6. Coverage 76 Mc/s-210 Mc/s. in five bands, all on fundamentals, slow motion tuning, audio output, 8 vertical and horizontal bars, logging scale. In grey hammer finished case with carrying handle. Accuracy ± 1% A.C. mains 200-250 v.



CHANNEL TUNER

Will tune to all Band I and Band III stations. BRAND NEW by famous manufacturer. Complete with P.C.C. 84 and P.C.F. 80 valves (in series), I.F. 16-19 or 33-28. Also can be modified as an aerial converter (instructions supplied). Complete with knobs.

22/6 Plus 3/6 P. & P.

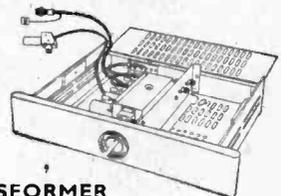


HEATER TRANSFORMER

To suit the above, 200-250 v., 6/- Plus 1/6 P. & P.

8-WATT PUSH-PULL AMPLIFIER

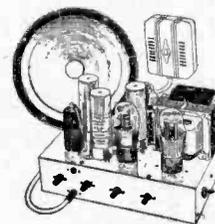COMPLETE WITH CRYSTAL MIKE AND 8in. LOUDSPEAKER



A.C. mains 200-250 v. Size 10in. x 6in. x 2in. Incorporating 6 valves, H.F. pen., 2 triodes, 2 output pens and rectifier. For use with all makes and type of pick-up and mike. Negative feedback. Two inputs, mike and gram., and controls for same. Separate controls for Bass and Treble lit. Response flat from 40 cycles to 15 Kcs..

±2 db : 4 db down to 20 Kcs. Output 8 watts at 5% total distortion. Noise level 40 db down all hum. Output transformer tapped for 3 and 15 ohm speech coils. For use with Std. or L.P. records, musical instruments such as Guitars, etc. £4.19.6 P. & P. 7/6.

Or 20/- deposit Plus P. & P. 7/6. and 4 monthly payments of 23/-.

RADIO & T.V. COMPONENTS (Acton) LTD.

23, HIGH STREET, ACTON, LONDON, W.3.

All enquiries S.A.E. GOODS NOT DESPATCHED OUTSIDE U.K.

You can't help earning more!

WITH NEWNES

Radio & Television Servicing



**OVER
2,300
POPULAR
MODELS**

MORE THAN
3,800

Circuit & Component
Layout Diagrams

OVER
3,750 Pages

**2 Years' Free
Postal Advisory
Service**

*Increases your earnings
FOR YEARS TO COME*

An investment
for every reader
of Practical Television

Ready for instant use are thousands of diagrams—TV receivers from single band sets to latest 13-channel 110°-tube models, including transportables, and combined TV/FM sets. Also radios, including Transistor and VHF/FM models, Radiograms, Portables, Transistor Personals, Tape Recorders, Car Radios, Record reproducers (including Stereo).

Practical Guidance on Modern Circuit Developments. Fault-finding and Alignment. Servicing Tape Recorders. Aerial Installation. Electrical and Car interference suppression. Servicing Transistor and VHF/FM Radios. Printed-wiring sets. Servicing Equipment. Salvaging Picture Tubes, etc.

**NEW 1960 Edition in 6 volumes
FREE FOR 7 DAYS**

This New Edition of Newnes Complete Library of Servicing Data is exactly suited to your needs. Here in six packed volumes are all the circuits, component and layout diagrams you must have for speedy, efficient repair work, tuning and general maintenance—over 2,300 models pre-1954 right up to 1960. All the famous makes below are included—everything you want for years to come. If you've never seen previous editions be sure to see this one!

TELEVISION, RADIO, RECORD REPRODUCERS, TAPE RECORDERS

All these popular makes—

Ace, Alba, Ambassador, Argosy, Armstrong, Baird, Banner, Beethoven, Berec, Brayhead, Bush, Capitol, Champion, Channel, Collaro, Corsor, Cyldon, Dansette, Decca, Defiant, Dynatron, E.A.R., Eddystone, Ekco, Elizabethan, E.M.I., Emerson, English Electric, Ever Ready, Ferguson, Ferranti, G.E.C., Grundig, H.M.V., Invicta, K-B., McCarthy, McMichael, Marconiphone, Masteradio, Motorola, Murphy, Pageant, Pam, Perdio, Peto Scott, Philco, Philips, Pilot, Portadyne, Pye, Pye Telecommunications, Radiomobile, Rainbow, Raymond, Regentone, R.G.D., Robert's Radio, Sobell, Spencer-West, Stella, Strad, Ultra, Valradio, Vidor, Walter, Webcor.



Important Reference Data on Valve and Picture Tube Bases and Equivalents. B.B.C. and European Broadcasting Stations. TV and VHF/FM Channels and Stations. Battery equivalents. Colour codes, etc.

POST NOW No Cost-No Obligation

GEORGE NEWNES, LTD., 15-17 Long Acre, London, W.C.99.

Send me Newnes RADIO AND TELEVISION SERVICING without obligation to purchase. I will return it in 8 days or send 11/- deposit 8 days after delivery, then twenty monthly subscriptions of 11/- paying £11 11s. 0d. in all. Cash price in 8 days is £11 0s. 0d.

Name _____

Address _____

Occupation _____

Your Signature _____
(Or Your Parent's Signature if under 21)

Tick (✓) where applicable

HouseOWNER	<input type="checkbox"/>
Householder	<input type="checkbox"/>
Living with Parents	<input type="checkbox"/>
Lodging Address	<input type="checkbox"/>

RV103

Transistor Set Parcel



Cabinet as illustrated—with handle and knobs—2 gang tuning condenser—printed circuit—tuning scale—full circuit

diagram showing other necessary parts—separate value £3—will all be sent for 29/6, plus 2/6 post and insurance.

Metal Rectifier Bargain


250/300 volt, 250 mA equivalent of R.M.5 will replace many expensive valve types and will last. Price 12/6, plus 1/- post.

Connecting Wire



P.V.C. covered in 100ft. coils—2/9 a coil or four coils different colours, 10/-, post free.

Now reduced to 9/6

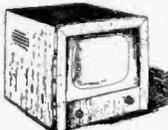

14in. TV cabinet of the latest styling—beautifully veneered and polished—limited quantity, sale price

9/6 each. Carriage and packing 3/6 extra. Masks 10/- extra.

This Month's Nip Super Transistor Kit



Makes ideal bedroom radio, uses one transistor and one crystal diode. Complete with case 19/6 Post 2/6

For Your Lab.


Resistance substitution boxes are great time savers and you really cannot have too many of them; here then, is an opportunity to acquire these at a very low rate. Our R.S. kit available for only 8/6, plus 1/6 postage, comprises one 50 W. precision variable resistor 0-100 K., six 2-3 watt fixed resistors, one 6-position switch, one pointer knob and one ordinary knob and instructions. This unit when made up will give an infinite variability over the range 100 ohm to 2 meg.

Exact Replacements

Live output transformers available from the following receivers, 59/6 each.
Argosy—T2, T3, CTV517.
Icarus—2014, 2017, 2114, 2117.
Cossor—930, 930T, 931, 933/4/5, 937, 938, 938A, 938F, 939, 939A, 939F, 943T, 946.
Decca—D14, D17, D17C.
DeLant—TR4537, TR1753.
Ferguson—308T, 308T1.
H.M.V.—1824, 1824A, 1825, 1825A, 1826, 1826A, 1827, 1827A, 1829, 1829A, 1865, 1869.
Marconi—VT63DA, VT68DA, VT69DA.
R.G.D.—9014T, 9017T, 7017C, C54.
Reverton—14T, 17C, 17 Comb., 17T.
Sobell—TS17, T346.

Most others available at short notice. ALSO exact replacement line blocking, frame blocking and frame output transformer—for most makes and types. Post inquiries please, enclose S.A.E.

TURRET TUNERS

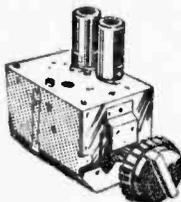

Ideal for converting an old or building into new TV. These are brand new stock, not surplus, supplied complete with valves and coils for local Band I and Band II, static free.
Model 1, I.F. Output 33/38 Mc's series heaters.
Model 2, I.F. Output 16/19 Mc's parallel heaters. With instructions and circuit diagram, 79/6, knobs 3/6 extra, postage and insurance 2/6.

Useful Aids for Your Workshop

E.H.T. Sealer. This is a highly insulated preparation which is applied by means of a hot soldering iron direct to E.H.T. terminals, solder tags, etc. It hardens immediately after being applied and acts as a permanent seal against corona discharge and surface leaks. 2/6 per stick.


Polythene Spacer Washers. These are 3in. diameter, perforated with 1in. hole in centre. Specially useful for the re-insulation of focus coil assemblies. 2/- per dozen.

Polythene Tape. 2in. wide, 10 thou. thick. Specially designed to replace and/or strengthen insulation of E.H.T. components up to 25kV. 5/- per roll.
Sponge Cushioning. This is a sponge rubber strip 1in. wide x 1/4in. thick. For the flexible mounting of C.R.T. tubes and masks. Also acts as a dust seal. 5/- per foot.

Rubber Cord. Sponge rubber 1/4in. diameter. For sealing around C.R.T. masks. 1/- per foot.
P.V.C. String. Strong, flexible, this P.V.C. string can be used for cable forming, binding of ends, marling of wires, etc. 25yd. roll 3/6.

Anti-static Screen Cleaner. Specially prepared for TV tubes and screens. Will clean both glass and perspex and its anti-static qualities will delay the collection of dust. 3/- per tube.

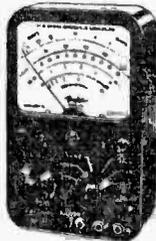Cellulose Cement. Specially prepared quick drying cement for the quick and efficient gluing of metal, glass, ceramic, wood, fabrics, etc. When dry it is a very good insulator and is impervious to heat and acid. 4/6 per tin.



The Taylor Meter Model 127A

A pocket size meter but with a big scale and a sensitivity of 20,000 Ohms per volt D.C., therefore an ideal unit for television servicing—robustly made and complete with leads and probes—20 ranges as follows:
D.C. current 50 micro-amps. to 1 amp.
D.C. voltage—0-1,000 volt in seven ranges (25 KV. with external probe, optional extra).
Volts A.C.—0-2,500 in six ranges.

Ohms—0-20 Ohm in three ranges (self-controlled).
Self-contained. 3in. movement. Price £10 or 20/- deposit and 21 fortnightly payments of 10/-. Non-callers add 5/- carriage and insurance.

Band III Convertors

Suitable Wales, London, Midlands, North, Scotland, etc. All the parts including two EF80 valves, coils, fine tuner, contrast control, condensers and resistors. (Metal case available as an extra.) Price only 19/6, plus 2/6 post and insurance. Data free with parts or available separately, 1/6.



Please send two more kits, the one you sent last week is performing magnificently. We receive this sort of letter every day of the week, so if you have hesitated because you thought our kits too cheap you need hesitate no longer.

Building A Scope?



3in. oscilloscope tube. American-made type No. 3FP7, octal base 6.3 v. 0.6 amp. heater, electrostatic deflection, brand new and guaranteed, with circuit diagram of scope. 15/- each, plus 1/6 post and ins.

A.C./D.C. Multimeter Kit

Ranges: D.C. volts 0-5, 0-50, 0-100, 0-500, 0-1,000. A.C. volts 0-5, 0-50, 0-100, 0-500, 0-1,000. D.C. milliamps 0-5 0-100, 0-500. Ohms 0-50,000, with internal batteries. 0-500,000 with external batteries. Measures A.C./D.C. volts, D.C. current and ohms. All the essential parts including metal case, 2in. moving coil metre, selected resistors, wire for shunts, range selector, switches, calibrated scale and full instructions, price 19/6, plus 2/6 post and insurance.



Yaxley Switches

1 Pole 3 way	1/6
1 Pole 5 way	2/-
2 Pole 2 way ceramic	2/6
2 Pole 4 way	2/-
2 Pole 6 way	2/6
2 Pole 8 way	3/6
2 Pole 11 way	3/6
2 Pole 12 way	4/6
3 Pole 3 way	1/6
3 Pole 6 way	3/6
4 Pole 4 way	3/-
6 Position shorting	2/-
6 Pole 3 way	2/6
6 Pole 3 way ceramic	3/6
8 Pole 2 way	2/-
9 Pole 3 way	2/6
12 Pole 2 way	2/-

Miniature Microphone

American made, Dynamic type, real bargain at 2/6, plus 6d. post.



ELECTRONIC PRECISION EQUIPMENT LTD.

66, GROVE ROAD, EASTBOURNE, SUSSEX

This is the correct address for post orders and for prompt attention please mark your envelope Dept. 5, also enough for postage. Personal shoppers should use one of the companies below.


Electronics (Croydon) Ltd.
266 London Road,
Croydon.
Phone: CRO 6558
Half day Wednesday.

Electronics (Finsbury Park) Ltd.
29 Stroud Green Rd.,
Finsbury Park, N.4.
Phone: ARCHWAY 1049.
Half day Thursday.

Electronics (Manor Park) Ltd.
520 High Street North,
Manor Park, E.12.
Phone: LIFORD 1011
Half day Thursday.

Electronics (Ruislip) Ltd.
42-46 Windmill Hill,
Ruislip, Middx.
Phone: RUISLIP 5780.
Half day Wednesday.

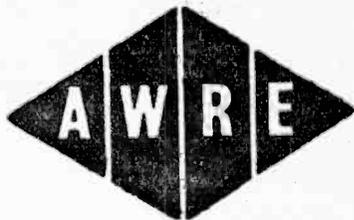U.K.A.E.A.
ATOMIC WEAPONS
RESEARCH
ESTABLISHMENT
ALDERMASTON



have vacancies for

ELECTRONIC MECHANICS —

engaged on the prototype construction of a very wide range of electronic equipment.

INSTRUMENT MECHANICS —

engaged on fault-finding, repair and maintenance of electronic and electro/mechanical instruments.

Skilled craftsmen who have had considerable industrial experience of electronics, or who have received equivalent training and experience in H.M. Forces are invited to apply.

HOUSING

Married applicants living beyond daily travelling distance will become eligible for a house within a reasonable period, and lodging allowance will be paid while waiting. Loans to assist house purchase may also be available.

VOCATIONAL TRAINING

Financial and other assistance may be given to craftsmen taking approved technical courses leading to City and Guilds or National Certificates.

Opportunities of promotion occur throughout the Authority for qualified men.


An Illustrated Brochure is available giving details of the above together with:

- ★ Rates of pay
- ★ Sick pay
- ★ Superannuation Scheme
- ★ Recreational Facilities

If you would like a copy send a postcard quoting Ref: PA471 to:

The Industrial Recruitment Officer,
Building F6.1, A.W.R.E.
Aldermaston, Berks.

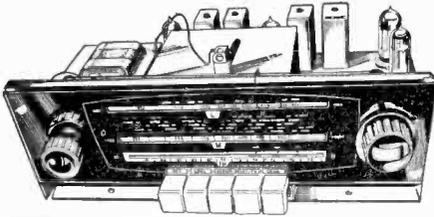BRAND NEW AM/FM (V.H.F.) CHASSIS AT £13.68. (P. & P. 10/-)




Why buy a F.M. Tuner at the same price? Tapped input 220-225 v. and 226-250 v. A.C. ONLY. Chassis size 15 x 6 1/2 x 5 1/2 in. high. New manufacture. Dial 1 1/4 x 4 in. in gold and black. Pick-up. Extension Speaker, A.E., E., and Dipole sockets. Five "piano" push buttons—OFF, L.W., M.W., F.M. and Gram. Aligned and tested. With all valves & O.P. Transformer. Tone-control fitted. Covers 1,000-1,900 M.; 200-500 M.; 88-99 Mc/s. Valves E200 rect., ECH81, EF89, EABC80, EL84, ECC85. Speaker & Cabinet to fit chassis. 47/6. 10 x 6 in. ELLIPTICAL SPEAKER, 20/-.

TERMS:—(Chassis) £4.16.8 down—10/- carr.—and 6 Monthly Payments of 30/-, or with Cabinet & Speaker £5.9.2 down and 7 Monthly Payments of 32/-.

We are specialists in ITA Converters. Our converters give direct switching ITA to BBC, metal rectifier, co-axial plug. Can be fitted in 5-10 mins., and need no alteration to your set. ALL AREAS. ALL SETS. ALL CHANNELS. 12 months' guarantee (3 months on valves).


"READY TO USE" ITA CONVERTER

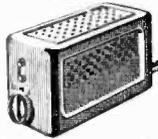Separate gain controls. Valves PCF80 and PCC84. Switch positions ITA (1)—ITA (2)—BBC. Bakelite moulded cabinet 8 1/4 x 4 x 6 in. £5.5.0. P. & P. 3/-.



3-VALVE AMPLIFIER (INCL. RECT.) Capable of giving 6 watts. Mains and output transformers. Valves ECC81, EL84 and Rect. 3 Controls. volume, bass and treble. On/Off switch. Fully guaranteed. Chassis size 8 1/2 x 3 1/2 in.; with 7 x 4 in. elliptical speaker or 6 1/2 in. round (Goodmans); state which.

Only 67/- (3/- P. & P.)

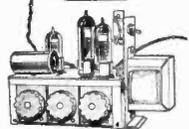

STUPENDOUS OFFER! 13-CHANNEL TUNER

I.F. 34-38 Mc/s complete with valves PCF80 and PCC84. Removed from chassis but in working order.



15/- (2/6 P. & P.) Knobs 2/6 extra. Some tuners less valves 7/6.

ITA TABLE TOP AERIAL


An ITA table top aerial with amazing performance. The Wolsey Hi-Q at 19/6 (2/6 post). Gives good reception up to 20 miles, and has cross-over unit in base with socket for BBC aerial. Same model but very slightly tarnished for ONLY 12/6 (2/6 post).




PERSPEX UNSCRATCHED. (Post 2/- each or 6 post free.) 12 1/2 x 9 1/2 x 1 1/2 in. clear, 4/6; 14 1/2 x 11 x 1 1/2 in. clear, 5/-; 15 x 12 x 1 1/2 in. tinted, 6/-; (Also 15 x 12 in. slightly scratched at 3/-).

AUTOMATIC RECORD CHANGERS. COLLARO CONQUEST with manual play also. Turnover crystal pick-up. 4-speed. A.C. mains 200-250 v., see illus.

£7.10.0 (5/- P. & P.)

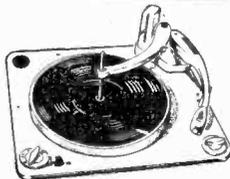


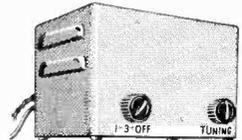For the last 50 ITA Converters of this (50th Brand New and Fully Guaranteed) we will accept the "Below Cost" figure of ONLY 60/- (3/- P. & P.) Reduced from £4.7.6. Two valves—ECC81—grey hammer finish—Switch positions OFF, ITA, BBC. Own Power supply. BUY IT NOW.



60/- (3/- P. & P.)

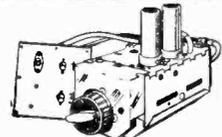THE BRAYHEAD TURFET TUNER £7.0 post free. Complete with booklet and fitting instructions. State set and model No. when ordering. Converts your 5-channel BBC only set to receive ITA as well.




ITA AERIALS clipping to existing mast 1-2 in. dia. 3-element, 10/-; 5-el., 25/-; 2-el., 47/6; Loft mounting, 3-el., 17/-; 5-el., 23/-; Combined single BBC and 5-el. ITA, 75/- with chimneys—lashings; Co-axial cable semi-air-spaced, 6d. yd. or 20 yds.. 9/- Aerial and cable prices carr. paid.

50 SILVERED MICA AND CERAMIC CONDENSERS, 10/-; 50 RESISTORS, 5/-; ALL NEW.

NEW WAXED TUBULARS. 350 v. or above, 3 of each. .001, .002, .005, .01, .02, .05, 1 mF. Total 21 for 4/6, post paid.

NEW ITA AND BBC TUNER. By well-known manufacturer for superhet TVs with 35-38 Mc/s I.F. For all areas; covers all 13 channels. Switch gives BBC and two ITA selections. Suits G.E.C. sets BT453, 454, 5146, 5147, 5543, 5642 and 6641. Mains and Output Transformers. Metal Rectifier, ECL82 Valve. Tone and Volume Controls. On/Off switch. Fully Guaranteed. Two Knobs supplied. Ready to play. Useful for Stereo.

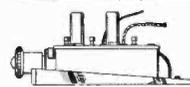

WITH VALVES PCF80 and PCC84, 22/6 (P. & P. 3/-). Some without valves at only 12/6 (P. & P. 3/-).

GRAMOPHONE AMPLIFIER with 5 in. SPEAKER. On Fabric-covered Baffle 12 1/2 x 8". Mains and Output Transformers. Metal Rectifier, ECL82 Valve. Tone and Volume Controls. On/Off switch. Fully Guaranteed. Two Knobs supplied. Ready to play. Useful for Stereo.



ONLY 57/-, post 3/-

BERIC "PIONEER" RADIO IN MAKER'S CARTON. Valves DK96, DF96, DAF96, DL96. Beric Ever-Ready Battery B103. 18/6 extra. Two Short Wavebands 2.5 to 7 Mc/s and 6.5 to 17 Mc/s. Cabinet, 12" x 7 1/2" x 6". ONLY £4.15.0 (2/6 p. & p.). In kit form with instructions and fully wired coil pack. Two Short Wavebands £4. One M.W. and S.W. £4.5.0. Plus 2/6 p. & p. Separate Items supplied.



Delivery by return. C.O.D. 2/- extra. Terms: Cash with order or one-third down and balance plus 7/8 (up to £7.10.0) in four equal monthly payments. Balance over £7.10.0 add 1/- in £1 and pay in not more than 6 monthly payments. See special terms for A.M.-F.M. chassis. All new goods unless stated. Send 6d. for 16-page catalogue.

GLADSTONE RADIO

58A HIGH STREET, CAMBERLEY, SURREY.


Tel. 22791

or callers to 3 Church Road, Bristol 5 Tel. 51207

(Camberley closed Sats.)



Practical Television

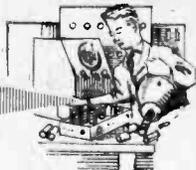

& TELEVISION TIMES

Vol. 10 No. 115

EVERY MONTH

APRIL, 1960

Editorial and Advertisement Offices:
PRACTICAL TELEVISION
George Newnes, Ltd., Tower House,
Southampton Street, Strand, W.C.2.
(C) George Newnes Ltd., 1960.

Phone: Temple Bar 4363
Telegrams: Newnes, Rand London.
Registered at the G.P.O. for trans-
mission by Canadian Magazine Post.

SUBSCRIPTION RATES

including postage for one year

Inland - - £1.2.0 per annum
Abroad - - £1.0.6 per annum
Canada - - 19s. per annum

CONTENTS:

	Page
Editorial	341
Versatile V Aerial	342
Servicing TV Receivers	343
London to Birmingham TV Link	347
Timebase Faults	349
Two into One—2	352
Safe Modifications	353
Interference Limiters	358
A Cathode Follower Voltmeter	360
Telenews	362
Make your own Abacs	364
Underneath the Dipole	371
Letters to the Editor	375
Your Problems Solved	376

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Television." Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for the manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed to: The Editor, "Practical Television," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

Owing to the rapid progress in the design of radio and television apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in "Practical Television" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

Sound Improvements

MOST of the modern developments in the design of TV receivers seem to be concentrated on improvements to the reproduced picture; the quality of the sound, far from being improved with the advent of new models, seems to be deteriorating. The increasing use of cathode ray tubes with deflection angles of 110deg has caused the depth of cabinets to be reduced, and smaller loudspeakers to be used.

Early TV receivers were bulky units and the designer was forced to employ large cabinets to accommodate the chassis. Whilst these receivers are ugly by modern standards, the cabinets were large and made of thick wood. In console models particularly, there was sufficient space to use 8in. or even 12in. diameter loudspeakers and the quality of the reproduced sound was excellent. Now, fashion dictates that TV receivers be as small as possible and large diameter loudspeakers are rarely used. In order to reduce the frontal area of the cabinet many designs position the loudspeaker at the side of the receiver. Whilst this procedure may occasionally permit the use of an 8in. diameter loudspeaker, the improvement in sound quality thereby obtained is offset by the way in which the highly directional top notes are absorbed by the furnishings of the room.

To summarise, the loudspeaker employed in a TV receiver should have as large a diameter as practicable and should be positioned to face the viewer. As we have shown, these two requirements conflict and there are, we think, two solutions to the problem, one for existing receivers, and the other for new models. If the sound reproduction of an existing receiver is poor, it may be improved by using a separate loudspeaker and enclosure. However, if such a course is adopted and the receiver is of the live chassis variety care must be taken to ensure that no dangers are created by the additional wiring.

The solution proposed for incorporation in new TV receiver designs would give little difficulty in execution and would involve little alteration to either appearance or basic design. As we have pointed out, the high notes emitted by a loudspeaker are directional and are lost if it is not facing the viewer but the bass notes suffer little or no deterioration. Thus, provided the high notes are directed towards the viewer, reproduction will generally be satisfactory and certainly improved. This principle can be realised by using a large diameter speaker in the wall of the cabinet, where there is generally a large space available. A small diameter, high efficiency, "tweeter" can be placed at the front of the cabinet in a central position.

It has been said that "A picture is worth a thousand words" but it is surely wrong to neglect the sound section of the TV receiver and concentrate only on improving the vision section.

Your next issue, dated May, will be published on April 22nd

A Versatile "V" Aerial

A SIMPLE INDOOR AERIAL

By C. A. Oldroyd

OUR TV set was due for retirement; it had given us years of faithful service. The family wanted something new, with a bigger screen. In due course the latest 17in. set arrived, and was installed. Its performance was superb and apart from the TV programmes it also provided the VHF radio broadcasts. The serviceman suggested fitting two additional rods to the existing outside aerial, and a new download; but I was thinking of fixing-up a special indoor aerial for the VHF transmissions. We are a long way from the transmitter, and although the built-in aerial brought in a signal, an external aerial was obviously needed.

Polarisation

In addition to the outside TV aerial a loft aerial had been installed. It was a modest "V" aerial consisting of two copper tubes, as shown in Fig. 1. The rods of an aerial for F.M. should lie in a horizontal plane, and since the rods of a "V"

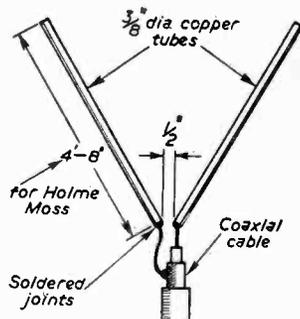



Fig. 1.—The construction.

total length of the reflector (before bending) can be determined from column "b" in the table in the January issue.

Apart from the dipole which has no directional effect, the "V" aerial is, perhaps, the most compact and versatile aerial for TV and VHF reception. It is surprising that its design has not been developed beyond the original, simple type. Gain could be increased by fitting a reflector, as suggested in Fig. 2. Even then the double "V" does not take up much room, and is compact enough to be erected in small lofts.

Construction

One point must be borne in mind when making up simple aeriels: one cannot afford to lose any energy, and the joints between aerial rods and downloads should be soldered; for this reason the elements were cut from copper tubing. The reflector can be bent from one piece of tube and Fig. 3 shows a suggested method of fixing the reflector to the wooden base. A is the copper tube, and B the baseboard. The clip C clamps the tube to the base B. To provide a good seating for the bend, a groove D is cut into the face of B with a half-round wood chisel. Bolts E are countersunk 3/16in. Whit. There is no need to mount aerial and reflector on a long baseboard: the two elements can be fixed to two smaller bases. This allows the spacing to be altered without having to remount the reflector. For greater selectivity, and increased gain, a director element in front of the aerial may be well worthwhile.

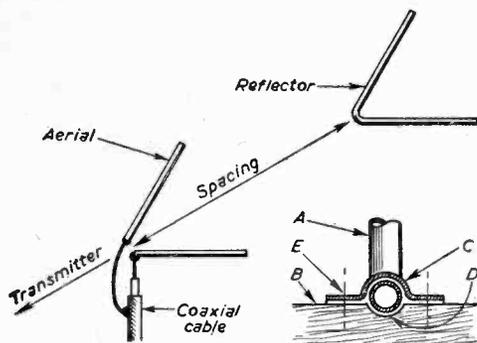

Figs. 2 and 3.—Adding a reflector, and the method of fixing the elements.


aerial slope outwards, and are neither vertical nor horizontal, it was hoped that it would bring in the VHF transmissions. A trial showed that it did so surprisingly well; a special VHF aerial could not have done better. Now neither a new VHF aerial nor a new feeder line was required; and if anything went wrong with the outside aerial, the "V" loft aerial could be used for the reception of the TV programmes. With the new set, the loft aerial worked quite as well as with the outside aerial, despite the fact that we are about sixty miles from Holme Moss.

Dimensions

It will be realised that for stations other than those operating on Channel 2, the length of the elements forming the dipole (see Fig. 1), will be different. An article on aerial design appeared in the January issue and in the table of dimensions on page 185, the figures in the column "a" may be divided by two and used as a basis for the length of the elements of the "V". The remaining dimensions given in Fig. 1 may still be used. The

DIMENSIONS OF THE ELEMENTS				
Channel	Length of dipole elements		Length of reflector (before bending)	
	ft.	in.	ft.	in.
1	5	3	10	11
2	4	8	9	8
3	4	2	8	9
4	3	10	8	1
5	3	6	7	5
8	1	2½	2	7
9	1	2½	2	6½
10	1	2	2	5½
11	1	1½	2	5

Servicing Television Receivers

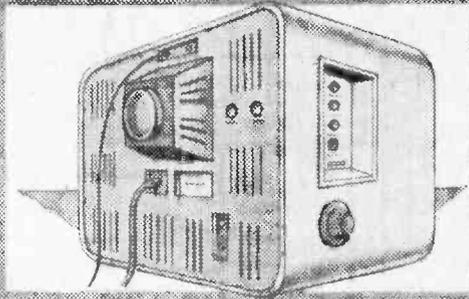

No. 54—THE PHILIPS 1115U, STELLA ST8314U, etc.

By L. Lawry-Johns

THERE is a very close resemblance between the above receivers and many others in the Phillips, Stella family. The basic design started with the Philips 1101U 12in. model (console version, the 1200U) and continued with the 1114U 14in. version, 1427U console, to the 1437U, 1726U (17in.), Stella 8314U. Fitted with turret tuners, the Philips 1446U, 1746U, Stella ST6414U and ST6417U followed.

All models use a double chassis system, the dual band versions having the tuner fitted in the centre. To avoid confusion, it is worth noting that the Philips 1748 and Stella ST8317U are completely different receivers using a much simplified circuit based on the earlier 12in. versions, the Philips 1100U—1236U—1238U—1229U and Stella 1500U.

Intermediate Frequencies

All these receivers use an 8.5Mc/s sound, 12Mc/s vision I.F. with a single 0.3A series heater chain. The Cyldon P10L, Brayhead 10s and similar tuners with PCC84 and PCF80 valves and a low I.F.

output are suitable for conversion. The usual method of fitting is by removing V1, the EF80 R.F. amplifier. Inserting the R.F. plug, removing the V2 EF80 mixer and inserting the mixer (I.F.) plug or adaptor. Various other methods suggest themselves, such as wiring all leads to the R.F. plug, altering the V1 and V2 bases so that V2 is retained and used as an extra I.F. amplifier, or wiring the leads to the valve bases instead of using the plugs.

Common Faults

Of the various "usual" complaints, the most common is undoubtedly weak line hold. This shows as persistent loss of hold where the picture repeatedly slips sideways necessitating frequent adjustment of the hold control. In fact, the "hold" circuit is rarely at fault and where it is, a replacement V15 (ECL80) or hold control (0.5M—500k) will most often put things right. In the majority of cases the line sync pulses are too weak to lock the oscillator owing to excessive clipping by the line sync clipper (triode section of V15). The

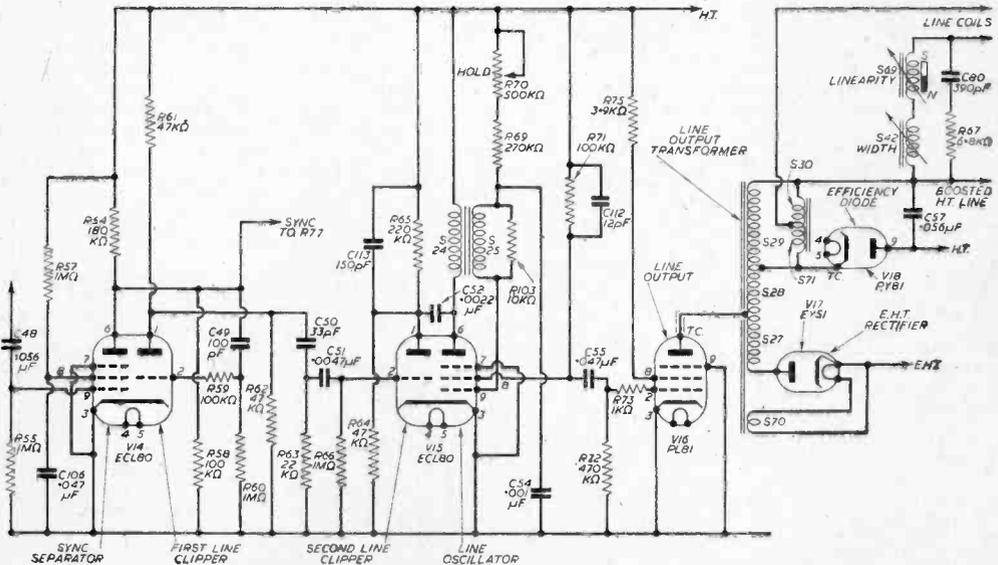


Fig. 1.—Sync separator and line timebase circuits.

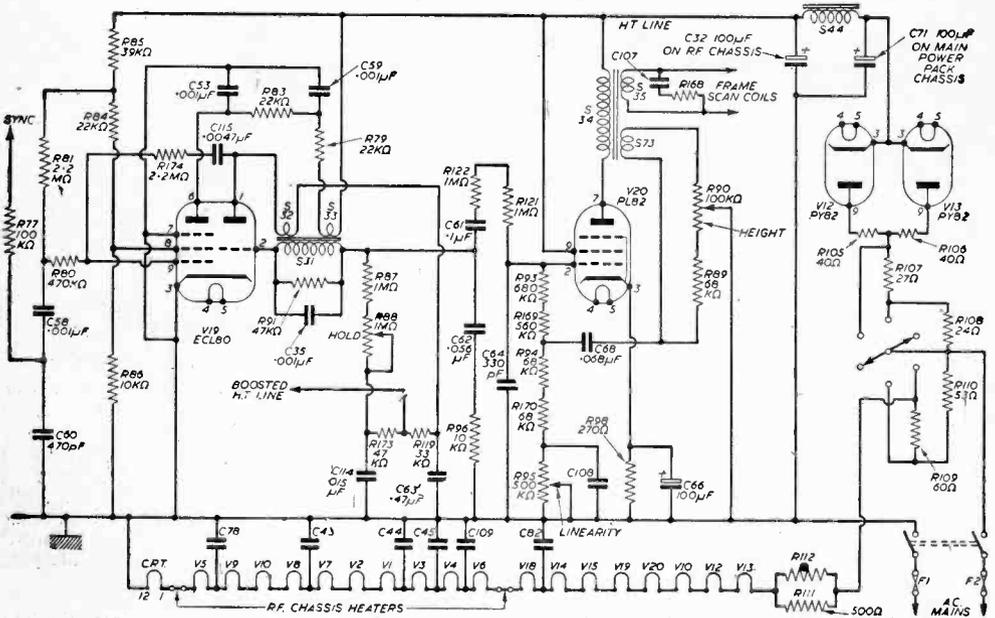


Fig. 2.—H.T. supply and frame timebase circuits.

anode load resistor is R65 (220k-red, red, yellow), this being the resistor wired to pin 1 of V15. This resistor often goes high in value and should be replaced. It will usually be found beneficial to reduce the value to 100k. This results in a much stronger locking pulse and the setting of the hold control becomes less critical. It is sometimes recommended that R64 (47k) be disconnected also but the writer has rarely found this necessary.

Horizontal White Line

Another very common fault is complete loss of height resulting in the appearance of a thin white line. When this fault appears, first check the PL82 (V20) and ECL80 (V19). If these are in order, check for H.T. at pin 1 of V19. If absent, check at the top tags of the frame blocking oscillator transformer (S32 tags). If H.T. is present at one of the upper front tags but not at the other the winding is open circuit. Sometimes the internal connections corrode resulting in a high resistance joint with varying height and intermittent collapse. In cases where doubt exists, sharply tapping the transformer will often confirm the diagnosis. This small transformer has six tags in all; two pairs at the top and one pair under the front. Tags S32—S31 form the oscillator windings and S33 is the frame sync coupling from the clipper stage which is the pentode section of V19.

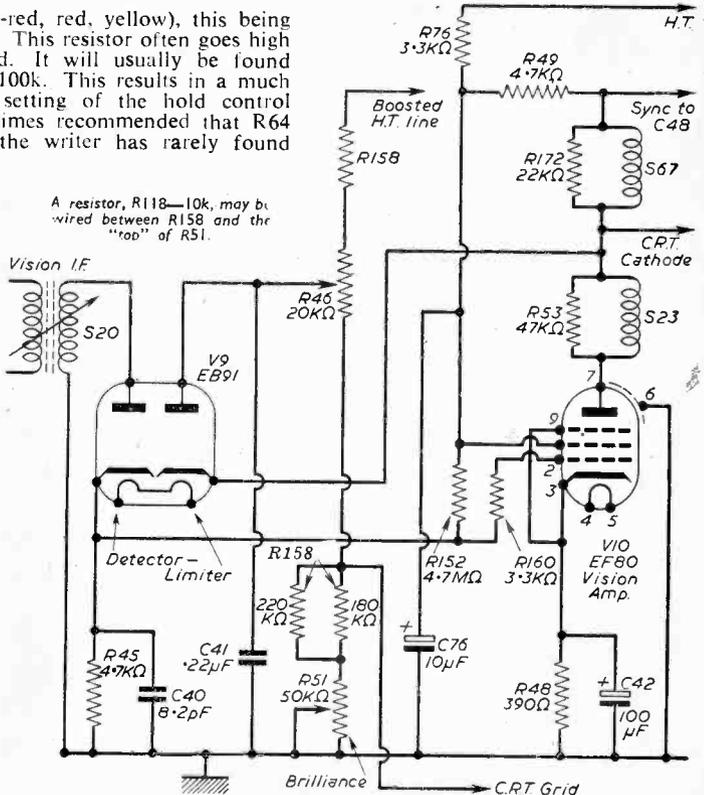


Fig. 3.—Video detector and amplifier stages.

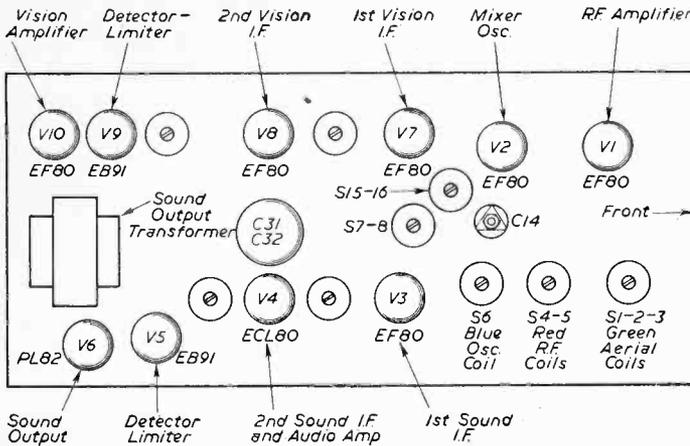


Fig. 4.—Chassis layout.


A Less Common Fault

On occasions, the height control (R90) becomes defective and this produces a rather startling effect, similar to that seen in "the hall of mirrors." The lower part of the screen is vastly elongated and the top compressed. These symptoms would normally lead one to suspect an open-circuited linearity capacitor but in most receivers in this range, a feedback winding is included in the frame output transformer and this feedback is divided and controlled to effect variations for height. When the circuit is working normally, quite a heavy feedback is applied. When a component, such as the height control becomes open-circuited, no feedback is applied and the above effects become obvious. When the bottom of the picture is compressed the PL82 may be fairly suspected but when the bottom is opened out the PL82 grid resistors R93 and R169 should be checked.

Sound on Vision and Vision on Sound

Sound on vision, showing as vibrations of the picture as the sound modulation varies, and vision

Fig. 5.—The input stages of the receiver.

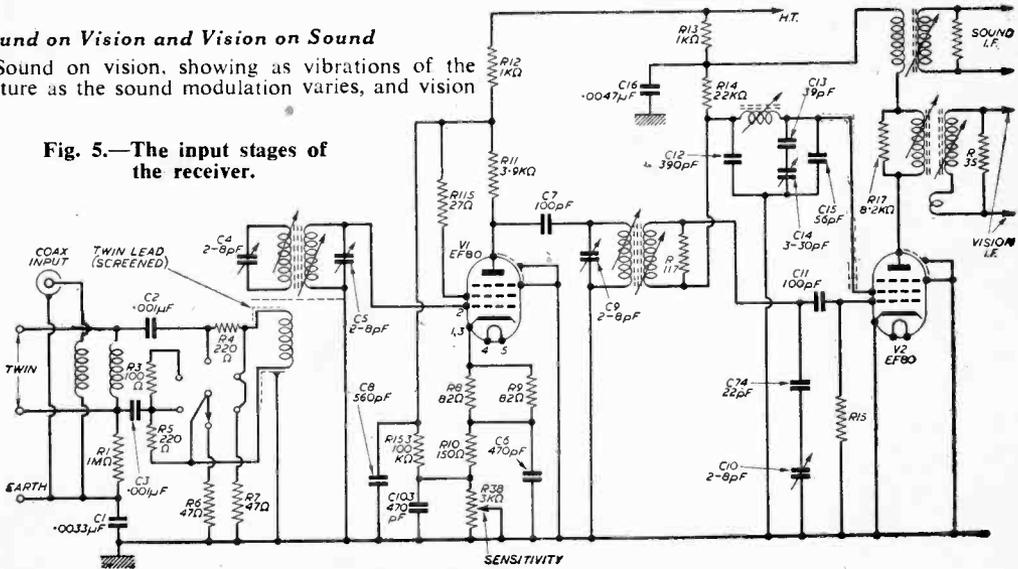

on sound showing as a buzz on the sound on white picture content, could be due to misalignment of C14. However it is often the case that C14 is correctly set and the above symptoms continue. This is normally caused by an open-circuited electrolytic capacitor and the C31—C32 can should be checked. A wire ended 32μF 350VW capacitor is useful to check these sections quickly. The negative side of the capacitor is touched to chassis, the positive end to each tag in turn and the effect noted. A correct replacement should be used (65 + 100μF).

Weak Frame Hold

The grid leak R81 (2.2M) is returned to a point of H.T. potential. When this resistor (red, red, green) goes high in value, the setting of the frame hold becomes critical the picture rolling upward or downward frequently. Weak sync and impaired definition often results as C76 (10μF electrolytic in the H.T. supply to the video amplifier) becomes open-circuited.

White Screen

When the screen is brilliantly illuminated with the brilliance fully down, it can be assumed that the cathode potential of the tube has fallen to a very low level. This D.C. voltage is derived from the video amplifier anode circuit. If the voltage at

Note—Ferrite beads are used in certain parts of the circuit and have been indicated by dotted lines. For an example see the screen grid lead of V2, below.

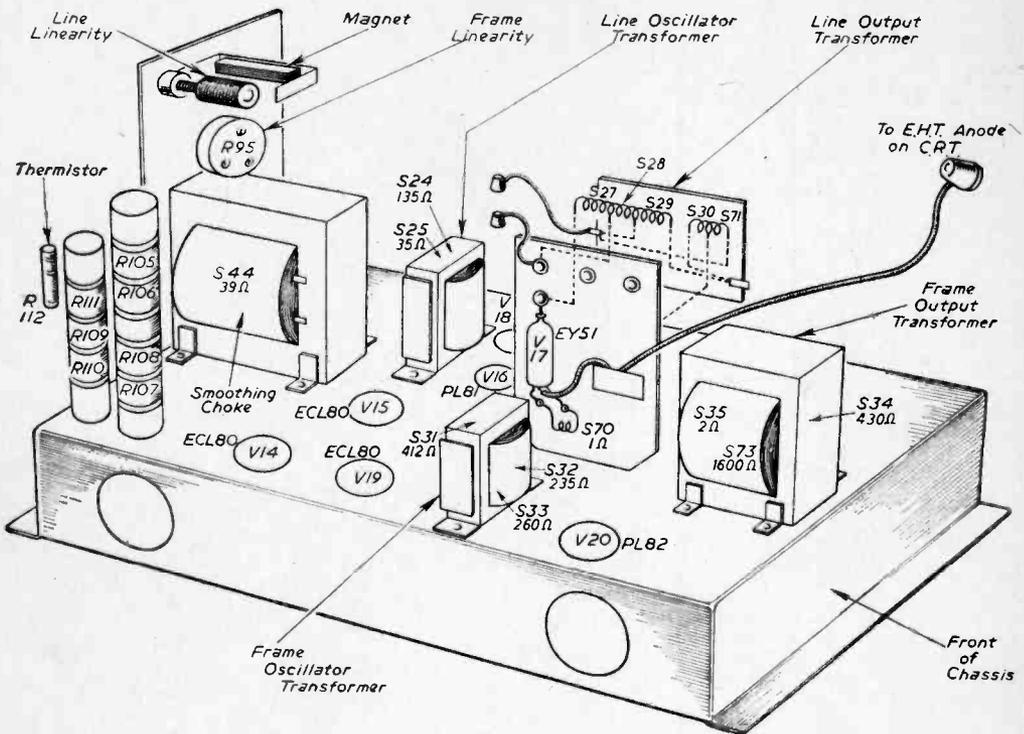


Fig. 6.—The chassis layout.

pin 11 of the CRT base is absent or very low, the most probable cause is a heater to cathode short in the tube itself. Pin 12 of the CRT base is connected to chassis and therefore a heater-to-cathode short results in the anode of the video amplifier being connected to chassis. This absence of cathode voltage on the tube results in a heavy flow of beam current with the brilliance at minimum. As the brilliance is advanced the beam current increases still further resulting in the EHT rectifier being overloaded and the screen darkens. Thus the brilliance control appears to work in reverse.

The cure is quite simple. A 6.3V isolating transformer (with mains primary) may be fitted under the tube neck. Pins 1 and 12 are the tube heater pins. The leads to these are removed, connected together and soldered to one of the primary tags of the transformer to form the chassis connection. The other primary tag is connected to the lower tag of the rear left side mains dropper to pick up the live side of the mains. The secondary tags are connected to pins 1 and 12 of the tube base.

Instability

The tube is not necessarily the cause of excessive brilliance however. Oscillation in the vision I.F. stages would result in the anode voltage at the video amplifier falling to a very low level. If this is suspected, short pin 2 of V10 to chassis.

If the brilliance returns to normal when advanced (there will be no picture, of course) and the anode voltage at pin 7 of the video amplifier

(or pin 11 of the CRT) rises to say 150 to 180, the decoupling capacitors (4,700pF) associated with pin 8 of each vision I.F. stage (V7 and V8) should be shunted with a capacitor of similar value (say 0.003 to 0.005 μ F) which is known to be "good".

Other Shorts

Reference to the video circuit diagram will show that the cathode circuit of V9 presents another possible source of a short circuit path from the video anode circuit. Here the symptoms are a little different, however, since a heater-to-cathode short will modulate the cathode very slightly with a low A.C. ripple which will show on the bright raster (with the brilliance at minimum) as light and dark bars with the heaters of V5 and the tube glowing brighter than normal. A very bright raster will also result if C76 should develop a short. In this case, R76 will overheat severely.

No Picture

If the sound is in order but there is no brilliance on advancing the brilliance control, check for EHT as outlined in previous issues of this journal, testing for a spark at either end of EY51, with and without the CRT clip connected. Then check PL81, PY81, ECL80, etc. The symptoms of a low EY51 (picture expands and fades as brilliance is advanced) have also been described so many times that a full description is hardly necessary. This also applies to the symptoms of a failing tube and other common faults.


(To be continued)

London to Birmingham TV Link

A NEW TRUNK CIRCUIT

THE first long-distance trunk TV circuit in Britain to be built, installed and maintained by private enterprise was formally handed over to Associated Television in London recently. The circuit carries high quality vision and sound from the Alpha Studios at Aston Road, Birmingham, to the ATV London Headquarters at Marble Arch. It will enable ATV's London management to monitor programmes originating in Birmingham and to watch rehearsals and dry runs. It will also enable advertisers in London to see programmes radiated from Birmingham without having to travel to Birmingham as at present.

The new microwave scheme which has been manufactured and installed by Pye Telecommunications Limited has many entirely novel features. Apart from being the first long-distance trunk circuit of its kind to be operated by free enterprise, it is also the first 7,000Mc/s microwave permanent trunk circuit in Great Britain. It makes use of passive reflectors, which eliminate the expensive waveguides normally required by such systems to carry the transmitter power to the aerials. The microwave link carries high quality TV sound in addition to the picture. Radiotelephone circuits for

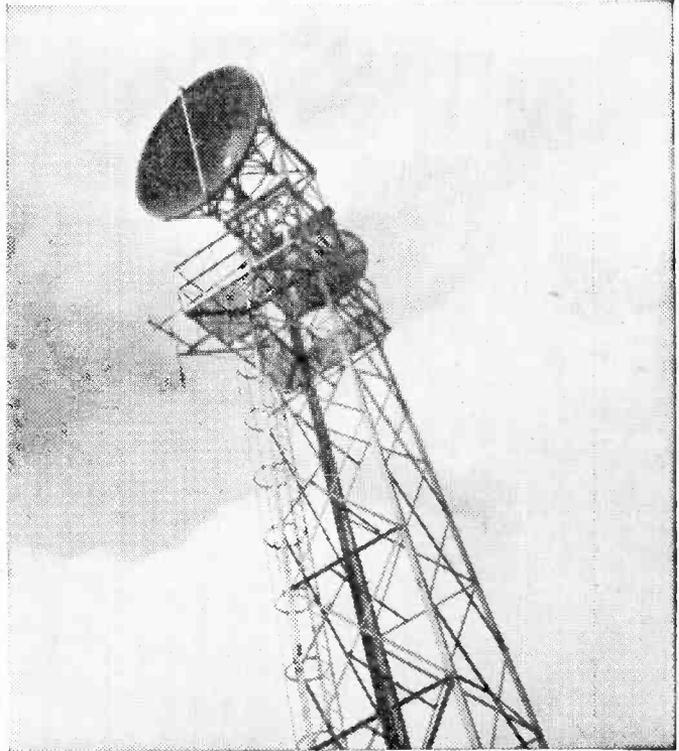

The microwave aerial system at Cold Ashby between Market Harborough and Rugby.

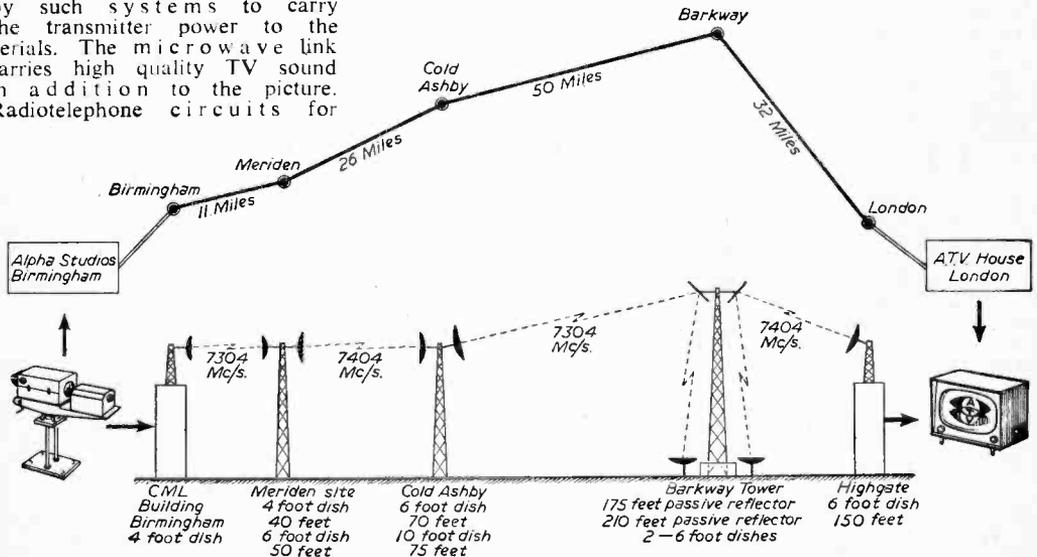


Fig. 1.—A diagram of the route taken by the new TV link.


engineering maintenance have been put on a separate 450Mc/s channel. One of its features has been very low cost—probably a fraction of links previously supplied for the purpose.

The passive reflectors are employed at the Barkway Tower and their method of operation is indicated in Fig. 1. At the frequencies used on the link, the radiation can be focused and beamed in much the same way as light waves. The signal is therefore led by waveguide to a dish aerial (as may be seen in the illustration on this page) and this aerial is directed towards a metal sheet at the top of the tower which acts as a mirror to reflect the signal beam in the required direction.

Faults

The circuit, which is routed via automatic radio repeater stations at Meriden, Cold Ashby, Barkway and Highgate, is 135 miles long. The repeater stations are fully automatic and unattended. Apparatus faults occurring at any station are automatically indicated on the London control board by telemetry circuits operating over the 450Mc/s control link.

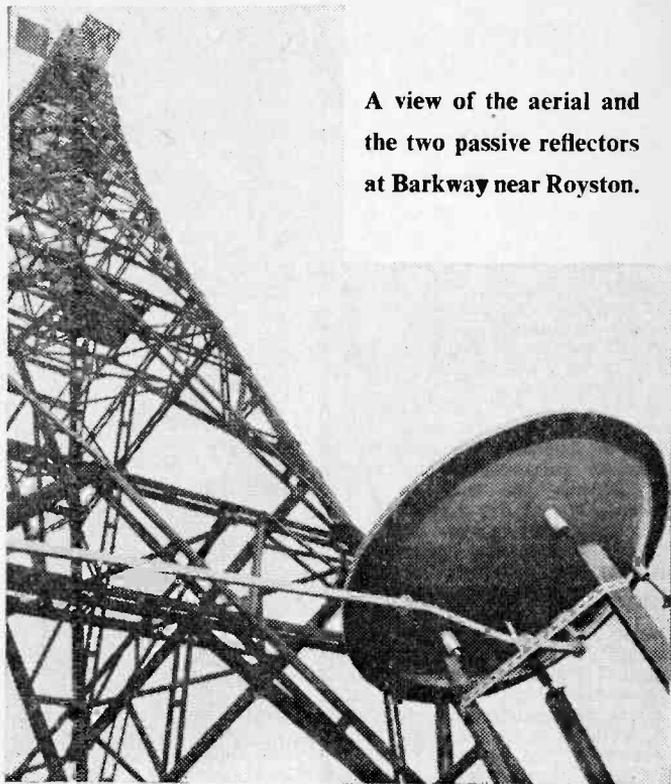Authority to install and operate the system was granted by the General Post Office, who have recently made a band of microwave frequencies available



A view of the aerial and the two passive reflectors at Barkway near Royston.

for operations of this kind. The Birmingham to London Link is thought to be the first of many such applications.

FULL POWER AT THRUMSTER

THE Thrumster television and VHF sound broadcasting station of the BBC was brought into full service on 1st March 1960. A temporary television service at reduced power has been in operation at this station since 15th December 1958; on 1st March this was brought into full-power operation and in addition a three-programme VHF sound broadcasting service was opened.

Test transmissions were radiated each weekday from 15th February—on television at full power from 10 a.m. to 1 p.m. and on VHF from 9 a.m. to approximately 11 p.m., and as in the case of other new transmitters, these test transmissions are for engineering purposes and to assist the radio trade in the installation and adjustment of receivers and aeri-als.

Site

The new BBC station shares the site of the G.P.O. communications station at Thrumster some 3½ miles south-south-west of Wick. The aeri-als for both the television and VHF sound services are mounted on a Post Office mast which is 325ft. high. The site is 236ft. above sea level.

Thrumster receives its television and VHF sound programmes direct from the BBC transmitting

station at Meldrum, Aberdeenshire and special aeri-als mounted on a separate 150ft. mast are provided for this purpose.

TV Service

Thrumster will radiate the BBC's television service on Channel 1 (vision 45Mc/s; sound 41.5Mc/s) using vertical polarisation. These conditions are the same as those which have been used for the temporary service. The transmitting aerial is directional giving an e.r.p. of 0.25 to 7kW according to direction. The new station will extend the BBC's television service to almost the whole of Caithness and in conjunction with the BBC's Orkney station the total population coverage will be some 43,000.

VHF Sound Service,

Thrumster transmits the Scottish Home Service on 94.5Mc/s, the Light Programme on 90.1Mc/s and the Third Programme with Network Three on 92.3Mc/s. Polarisation in this case is horizontal. The VHF aerial system, like that for the television service, is directional giving an e.r.p. of 0.1 to 10kW according to direction. The coverage will be almost identical with that of the television service.

Timebase Faults

CHECKING SYNC CIRCUITS

By G. J. King

SOMETIMES a leak develops from the element of a pre-set control associated with the frame timebase circuit to chassis. Such a leak does not always affect the performance of the generator generally. This point was revealed to the writer while investigating an early receiver for an unstable frame. The fault was finally established to be due to a leak between the frame linearity control and chassis—replacing the control cleared the symptom.

No Line Lock—Frame Hold Normal

It is general practice to supply the line generator with sync pulses derived from the anode of the sync separator valve via a series capacitor shunt resistor combination. Such a network is depicted by Fig. 1(a), and is often termed a differentiating circuit. Not only are the line sync pulses subjected to little attenuation by this form of coupling but the pulses also undergo a shaping process, essential for correct "firing" of the line generator. This is illustrated by the waveforms in Fig 1, which show at (b) a positive-going line sync pulse at the anode of the sync separator valve, and at (c) its modified shape developed across the resistor R.

The action of the circuit is such that the uncharged capacitor C offers little impedance to the leading edge of a pulse; the current in the resistor R and therefore the volts drop across it are at maximum. As time goes on, however, C charges exponentially and the potential across R falls. A virtual change of input in the negative direction is provoked by the trailing edge of the pulse, and the potential across R is thus changed instantly from a positive to a negative magnitude, which is again followed by an exponential return to zero. For optimum operation of this circuit the value of the time constant formed by RC must be appreciably smaller than the 10μs line pulse duration.

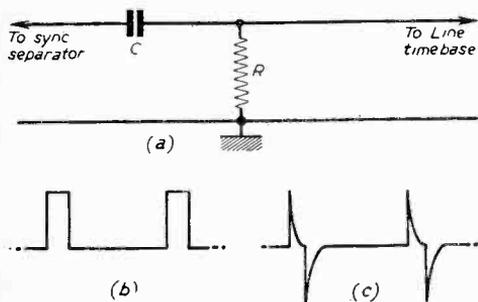


Fig. 1.—A basic differentiator circuit is shown at (a) and line sync pulses at (b), while (c) shows how the pulses are shaped due to the action of (a).

It is easy to see, therefore, that a change in value of any component associated with the line pulse coupling circuit might severely impair the efficiency of line lock. In receivers where a simple differentiating circuit is used, the symptom of no line lock can nearly always be traced to an open circuit differentiating capacitor.

In certain receivers the line generator demands the application of positive-going sync pulses for successful operation, and where a conventional pentode sync separator is employed, providing negative-going sync pulses at its anode, a form of phase reversing section must also be included in the line pulse feed circuit. A triode valve is often used to perform the phase reversing function. Fig. 2 shows the circuit details, and as will be seen the differentiating components, CR, go to make up the grid coupling circuit.

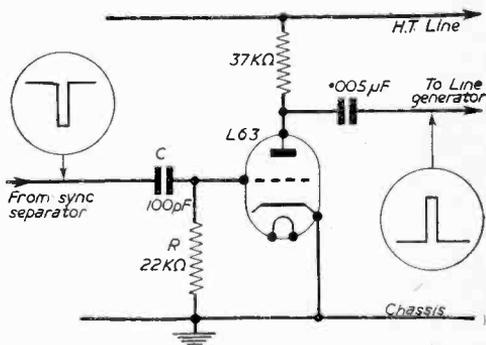


Fig. 2.—A typical line sync inverter circuit using a triode valve.

In a receiver of this type we have, therefore, another factor which could fail and cause a loss of line hold. The sudden occurrence of this symptom should immediately lead one to suspect the triode valve for low emission. On the other hand, an open-circuited anode load resistor would produce a similar effect by blocking the passage of line sync pulses.

Top of Picture Bent to the Right

The repetition frequency of a sawtooth generator in its "free-running" (unsynchronised) state is determined by the time constant in the circuit. For instance, the potential on the grid of the generator valve rises exponentially until it reaches a value which "fires" the valve (flyback). This effect we can illustrate as in Fig. 3 (a).

The repetition frequency of a synchronised generator is wholly controlled by correct injection of the appropriate sync pulses, the effect being that just before flyback would be initiated—should the generator be free-running—a sync pulse arrives and the valve is immediately "fired". We can clearly visualise from this, then, that the correct setting of hold control is such that in the free-running state the generator frequency should be very slightly lower than the sync pulse frequency. A line sync pulse exercising complete control on the repetition frequency of the generator during a normal line scan is shown by Fig. 3 (b).

During the framing pulse period, which generally comprises eight $40\mu\text{s}$ frame pulses radiated collectively, the line generator is held in synchronism by reason of the differentiated leading edge of every other frame pulse (see Fig. 4). A condition may arise, however, where the pulse—not necessary for line synchronising—which occurs in the middle of a line scan during the framing period fires the generator prematurely. How this undesirable condition may result is depicted at Fig. 3 (c).

Owing to such an occurrence the line generator is momentarily caused to operate at twice its normal frequency, and its output voltage is reduced to one-half of normal during this period. The line

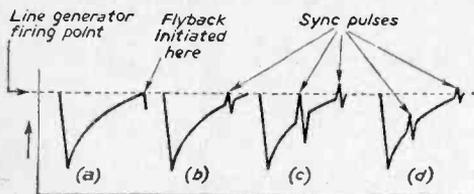


Fig. 3.—Firing points of line generator: (a) free-running, (b) normal synchronised line scan, (c) fired prematurely in the middle of a line scan during the framing period, (d) normal synchronised line scan during the framing period.

output valve drive, and thus its bias potential diminishes as a result, and the first few full amplitude lines at the top of the screen tend to be displaced to the right-hand side. The top section of the picture bends over to the right and is much more noticeable where excessive vertical picture content exists at the top of the screen. Sometimes the bending over is not stable, in which case the top of the picture appears to waver between the vertical and the bent positions.

It would follow, therefore, that since even the pulses which occur half-way through a line scan—remember these occur only during the framing period—possess sufficient amplitude to fire the generator prematurely, the overall amplitude of the line sync pulses generally must be far too large. This is the normal cause of this symptom, and it can be prevented without much trouble by taking steps to reduce the amplitude of the line sync pulses by the inclusion of a simple attenuator, generally in the form of a potential divider system. Fig. 3 (d) shows the normal relative amplitude of the sync pulses for correct "firing" of the line generator during the framing period.

Top of Picture Bent to the Left

Bending to the left is another common and troublesome fault in the line timebase and, as with the previous symptom, the top of the picture often wobbles in a most disconcerting manner. The bend in this case is caused by a change in the relative amplitude between the pure line sync pulses and those which are used for line synchronising during the framing period. This sometimes results in the line generator momentarily falling out of synchronism during the framing period and giving rise—during its unsynchronised state—to an increased output.

The difference in output voltage of the generator between its synchronised and unsynchronised states

is easily realised by considering, for instance, waveforms (a) and (b) of Fig. 3. In (a), the free-running state, the horizontal scan continues until the potential across the time constant capacitor reaches a value sufficient to initiate flyback. In (b), during synchronisation, the line scan is cut short, however, since the line sync pulse initiates flyback slightly before it would otherwise have occurred.

We can see, then, that the line generator falling out of sync during the framing period—at the top of the screen—will provoke an increase in the bias of the line output valve, and this has the effect of displacing to the left the first few lines of picture following the framing period.

The change in amplitude of the sync pulses during the framing period is often caused by a slight variation in main D.C. level of the composite sync pulse chain when it is conveyed to the line generator through the differentiating network. Although the leading edge of every other frame pulse is differentiated for application to the line generator, the duration of a pure line pulse is considerably less than the duration of a frame pulse.

A sudden occurrence of this symptom should lead one to suspect first of all an alteration in the value of a resistor or capacitor associated with the differentiating, or line sync feed network. A defect in the sync separator stage proper may also cause the symptom. It is, therefore, advisable, particularly in obstinate cases, to check the sync separator

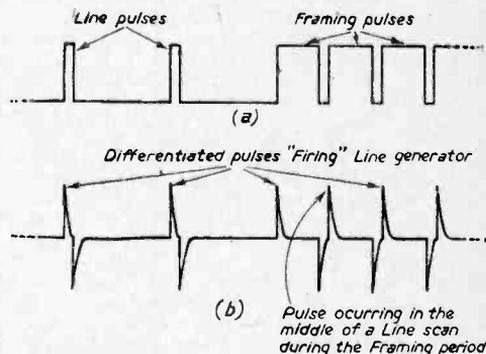


Fig. 4.—The differentiated pulses employed to hold the line generator in synchronisation during the framing period.

valve for emission and the associated components for value and it is important to pay special attention to the insulation property of the sync separator coupling capacitor.

Flywheel Synchronising

Flywheel synchronisation is now in common use in quite a number of the more sensitive—fringe area—receivers. In a large number of cases it represents—from the performance aspect anyway—a desirable inclusion, for as we have already discovered the trouble with most conventional sync separator stages is that the circuits are not able fully to differentiate between a line sync pulse and an interference pulse.

Such differentiation is rendered even more difficult in areas of poor signal strength owing to

the fact that insufficient signal is available at the input to the sync separator to produce a 100 per cent clipping action. Moreover, it often follows that in high interference and weak signal areas, the interference level might well exceed that of the signal, and this factor, coupled with valve and circuit noise, provokes premature line timebase triggering to give rise to the symptom we have already considered of "ragged verticals".

The relevant circuit details of a form of flywheel sync are depicted in Fig. 5, and though, perhaps, formidable in appearance its mode of operation is quite straightforward and easy to follow.

Operation

Valve V1 constitutes the sync separator valve, to the control grid of which the composite video signal is applied through C1. This section follows conventional design inasmuch as the positive going sync pulses drive the valve into grid current and the resulting charge across C1 is sufficient to place the video portion of the wave-form below cut-off. The line sync pulses thus appearing in the anode circuit are differentiated by C2 and R1, and phase inverted by the transformer T1 for direct application to the small metal rectifiers.

Leaving this section for a minute, let us now divert our attention to the ECL80, V2. This valve is primarily employed as the line scan voltage generator, and is wired in the form of a multi-vibrator using the triode section, and the control grid and screen grid of the pentode section as a second triode with common cathode coupling by R2 and anode to grid cross coupling by C3 and C4. The frequency of operation can be controlled manually by altering the time-constant C4 and R3, where the resistor forms the main line hold control, and the capacitor, also being variable, enables the correct line generator frequency to be adjusted so that it falls in the centre of the range of R3.

The sawtooth voltage appearing across C3 is fed through C5 to the control grid of the line amplifier. Apart from supplying scanning energy to the line deflector coils, the line output transformer also provides a small sampling pulse voltage for application to the metal rectifiers through C6 and C7, and because the winding concerned is centre-tapped, the sampling pulses are in two opposite phases which are balanced about earth potential.

Discriminator

Thus, the two metal rectifiers (discriminating rectifiers) are in receipt of two signals; the sync signal from the sync separator, and the line generator signal from the line output transformer.

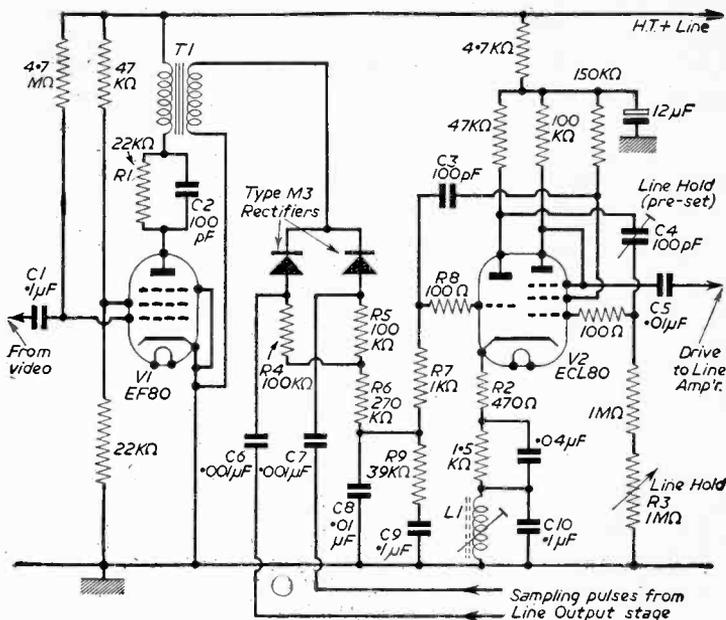


Fig. 5.—The "auto-sync" and associated circuits of a commercial television receiver.

The criterion for accurate line synchronising is, of course, to ensure that the two signal frequencies are matched, and this is where the discriminator takes over.

How this happens can be realised by assuming for the time being that only the sampling signal voltage is being applied to the rectifiers. Each rectifier is, therefore, receiving a voltage differing in phase by 180 degrees. Both rectifiers conduct equally and the currents in the load resistors R4 and R5 are of similar magnitudes. The resulting voltages are added in opposition, and resolve to provide zero potential at the junction R5, R6.

When both signal voltages are applied to the rectifiers the balance is maintained, but only so long as the phase of the two voltages corresponds. Should the generator frequency start wandering, for instance, the balance will be disturbed, and a control potential will exist at the junction R5, R6, the magnitude of this potential depending on the phase difference between the two frequencies. It is this potential which is utilised, by being fed through R6, R7 and R8, and filtered by C8, C9 and R9, to control the frequency of the multi-vibrator at the grid of the triode section.

Momentum

A momentum or flywheel effect is given to this system by the inclusion of a tuned circuit, L1 and C10, in the cathode of the generator valve. The tuned frequency is in the region of 8,500c/s, and its oscillatory effect tends to maintain line sync even for a brief period, should the sync pulses fail completely, or should they become distorted due to impulsive interference or other reasons.

Safe Modifications

THE SAFETY FACTOR IN SERVICING

By L. E. Higgs

THE Coroner's Court is a formidable place and I hope and trust none of us ever find ourself there—dead or alive as a result of modifications or alterations to television equipment in either a professional or amateur capacity.

Whether or not changing the design of a receiver is correct depends on the circumstances of each case, and in particular, to whom the set belongs. Some may retort that they may do as they like with their own property, in order to learn by experiment, save money on spares, save time by using substitute parts lying around at hand rather than wait the arrival of the exact items from elsewhere, and in any case the results are often better than the original.

Chances

This is true; nobody minds, nobody cares, nobody knows—unless that one in a thousand chance crops up when a person is accidentally hurt, or worse, killed (one in a million). Then the coroner, police, borough safety officer, several insurance companies, the injured party's solicitors, TV manufacturer (and newspaper men) swarm up and turn the spotlight on our right to do as we like with our own equipment.

Fortunately such happenings are rare but the safety aspect of alterations must always be kept in mind. Another point with our own receivers is the possibility of it evolving into a "Bitzer"—bits of this and bits of that—with no clear integrated design of section matching into section, an irregular circuit maze that other service men refuse to touch should it break down when the originator is temporarily absent. Finally, remember the loss of value when resale or part-exchange is attempted.

Nevertheless, we all like to have a dabble—"research" the large companies call their dabbings, and it is best to confine it to an old receiver that we intend running to a standstill. (This avoids the wrath of the rest of the family too.)

Policy

The other person's TV that we are called upon to service is quite a different matter from our own. He is entitled to expect a proper workman-like job for his money, executed with the correct parts, and indistinguishable from the original condition of the set. By doing this we ensure safety, reliability, and, above all, our good name. If the set later goes into the hands of another man there can be no report of bad work (right or wrong) because there will be no way of telling the job from the rest of the set.

There come many occasions, though, when the ideal cannot be realised owing to obsolescence, delivery delay, or the customer's poverty. On such problems we can use our skill of improvisation—with the customer's consent—as we have to with conversions (Band 11), tube boosts and requested attachments such as 'phones, tape sockets, and extension speakers.

Dangers

The discovery of an elderly lady, deaf, listening to TV sound with a pair of 'phones framed with bare metal, connected direct to chassis and output valve anode (Fig. 1), quite unaware as she watched her gangster films that she was wearing a similar rig to the condemned man in the electric chair,

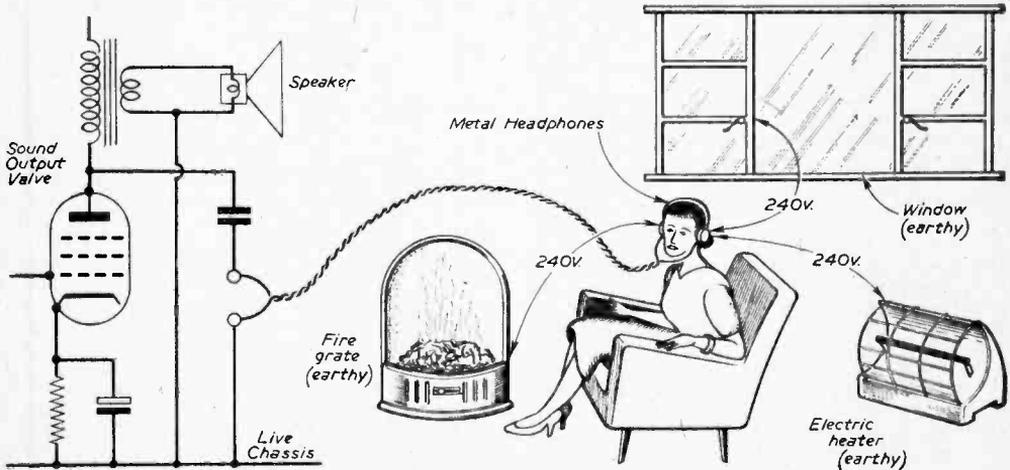


Fig. 1.—The dangers of connecting headphones direct to a live chassis.

first brought home to me the dangers of well meaning modifications by people unaware of the danger. It only needed a leak to 'phone frame by the frayed silk tinsel lead—not designed to withstand mains voltage—to place this lady's head 240V above earth when the mains plug is the

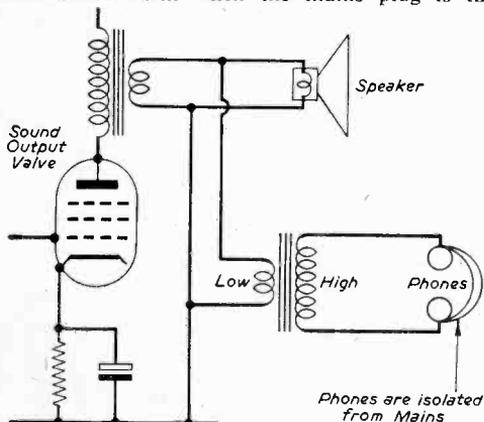


Fig. 2.—Headphones should be wired using an isolating transformer.

wrong way round. All well and good if she stays in her warm dry chair, feet on the carpet, but the moment she leans over to switch off the earthed metal electric heater, or opens the steel-framed windows, or just pokes the fire with the brass fire iron? "Killer TV Strikes Again" will probably be the headline.

All attachments from live-chassis equipment must be via a double wound transformer with insulation adequate to resist mains breakdown (Fig. 2). An extraordinary amount of damage can be produced when a tape recorder with an earthed chassis is fed from the speech coil of a speaker of a TV or radio with a live chassis, when, as often is the case, the coil is taken down to chassis. Recorder input, switch wafers, contacts, and speaker, manage to burn up before the fuses go. Its good policy to "megger" any attachments to the mains plug when finished, in particular the aerial socket on newly fitted ITV converters. Ensure that no bare metal parts can be reached by the customer's fingers. The authorities use a dummy finger (of a specified size) to test guards and shields to ensure protection, and insist on even the grub screws in control knobs being covered with wax.

Ventilation

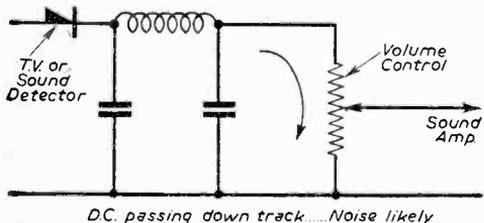


Fig. 3(a).—The usual method of wiring the volume control; D.C. passes through the control.

Another point of care when modifying is to see that any components that become hot are placed in well ventilated positions where no scorching, melting or blistering of cabinet or parts can take place. Wire-wound volts droppers and tube booster resistors are the main offenders. It is a problem to decide whether to replace a whole dropper or just to bridge the o/c section with a small wire-wound resistor. Rightly, replacement of the complete resistor is the best policy, and if more than one section has gone, the likelihood is that other original sections will follow. But where the first section goes and a long delay in obtaining a replacement is expected, it is tempting to wire in a 5W wire-wound and complete a quick, cheap, job. It is legitimate I think as long as the customer is informed.

Improvements

Modifications that result in improved performance are very gratifying, some being the result of using more up-to-date parts on obsolete sets. Contact-cooled rectifiers that prematurely cause reduced H.T. can with advantage be replaced with the earlier air-cooled types. Volume controls that become "noisy" owing to the to and fro on/off switching may be replaced by unswitched types, and a separate toggle switch for the mains provided in the side of the cabinet. This facility is appreciated by the older folk who dislike turning knobs, and like to control the set in one simple move. Persistently noisy controls are usually caused by D.C. passing through the track. Blocking off

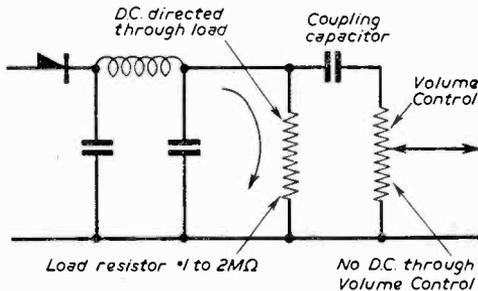


Fig. 3(b).—Fitting an isolating capacitor before the volume control.

the steady current with a capacitor and grid leak (Fig. 3) stops this recurring annoyance for good.

Some of the simpler alterations can be the most effective, especially to improve ease of service. My favourite with those sets which have solid bottoms, such as certain Pye models, is to cut out the slotted cabinet base with a padsaw, making a neat inspection cavity which can be covered with a perforated panel—safety again. The other cabinet improvement that saves much time where it can be applied is the conversion of the fixed viewing glass to a detachable one. Alternatively, after cleaning a tube which was difficult to replace, seal it off from the air with sponge rubber strip fixed with adhesive crêpe paper (as used in packing departments). The reason for this interest in time saving in my own case is that some of these instances are on rental contracts, and time saved on repeat calls is money saved. The fact that the

Every keen radio man must see it!

NOW COVERS RADIO-ASTRONOMY

FREE for 7 days

AND WITHOUT OBLIGATION

The long-awaited New Edition of this practical engineering and servicing work is now ready for you. If you are a Radio Engineer, Technician, Mechanic, Instructor, Student or Keen Amateur, this great wealth of data will prove invaluable. Newest developments and techniques are included—from latest transistors to low noise micro-wave devices; from advances in quality reception to radio-astronomy and space-probe communication. Be up to date by sending to-day for **FREE EXAMINATION**. Newnes Radio and TV Engineers' Reference Book is of absorbing interest to you—*post coupon below—now!*


PACKED WITH DATA FOR DAY-TO-DAY NEEDS—WRITTEN BY 50 SPECIALISTS

Formulae. Calculations. Communication Theory. Electron Optics. Colour, Projection and Industrial TV. Materials. Studio Equipment. Transmitter Power Plant. V.H.F. Transmitter-Receiver Equipment. Amateur Equipment. Waveguides. Receiver Design. Radio Links. Broad-band Systems. Radio Navigation & Radar. Radio Astronomy & Satellite Communication. Valves. Cathode-Ray Tubes. Transistors. Crystal diodes. Resistors. Capacitors. Inductors. Transformers. Microphones. Gramophone Mechanisms. Loudspeakers. Interference. Recording. Measuring Instruments. Installation & Servicing. Ionospheric Forecasting. Units & Symbols. Developments, etc.

SEE THESE PRACTICAL FEATURES

Latest types of Transistors and their use ● Single-Sideband Transmitters ● V.H.F. Scatter & Meteor Burst Communication Systems ● Travelling Wave Tubes ● Radio-Astronomy ● Modern Car Radio Receivers ● Stereophonic Reproduction and Recording Techniques ● TV. & Radio—latest Practice in Receiver Installation and Servicing ● New Air Navigation Aids.

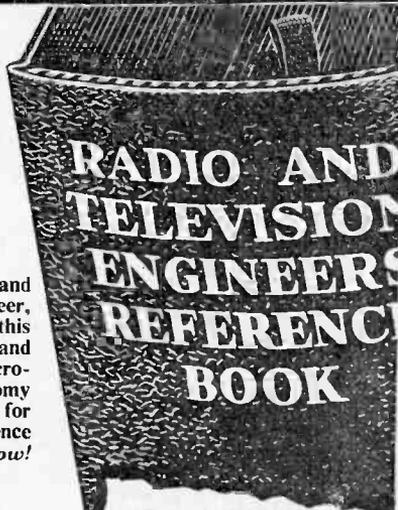Broadcasting • Communications • Navigation • Radar, etc.



New 3rd Edition

Over 1,800 Pages
47 Main Sections
2,000 DIAGRAMS,
TABLES, FORMULÆ &
CALCULATIONS

Many Exciting New Features

JUDGE FOR YOURSELF

Post Now
for 7-day
Free Test!

GEORGE NEWNES, LTD., 15-17, LONG ACRE, LONDON, W.C.99.
Please send me Newnes RADIO AND TELEVISION ENGINEERS' REFERENCE BOOK without obligation to purchase. I will either return the book within eight days or I will send the first payment of 5/- eight days after delivery, then ten monthly subscriptions of 10/-, until the sum of 105/- has been paid. Cash price within eight days is 100/-.

Name

Address

.....

Occupation

Your Signature
(Or your Parent signs if you are under 21)

Tick (✓) where applicable

HouseOWNER	<input type="checkbox"/>
Householder	<input type="checkbox"/>
Living with Parents	<input type="checkbox"/>
Lodging Address	<input type="checkbox"/>

RB39

Go buy Suffolk Tubes . . . they're better!

EVERYTHING IN C.R.T.'s

REBUILT
RESCREENED
RE-ALUMINIZED



SUFFOLK TUBES LTD

SUFFOLK HALL 1-3 UPPER RICHMOND ROAD PUTNEY S.W.15

Tel: VANDyke 5267 and 4304

GOVERNMENT SURPLUS AND MANUFACTURERS CLEARANCE

METERS. 500-0-500 Microamp. 3 1/2 in. dia. 37/6 ea. Dual Range 0-5 v. 0-100 v. FSD 1 ma. 20/- ea. ; 50-0-50 Microamp. 2 1/2 in. 30/-
TV AERIALS. Combined BBC/ITV. 3 element 32/6. 5 element 37/6. ITV 3 element 22/6. 5 element 27/6.
CO-AX CABLE 6d. 9d. AIR SPACED 9d. DIPLEXERS 12/-
GERMANIUM DIODES P.-. 10/- doz. TRANSISTORS from 6/-
VOLUME CONTROLS. Long Spindle Midget. 10K-2 meg. Less Switch. 3/- D.P. switch 4/6.
CONDENSERS. Twin Gang .0005 Standard 5/6. Midget 6/6.
V.H.F. CHASSIS. contains over 50 components, 5/6 ea.
FERRITE ROD AERIALS M. and L. Wave. Mfrs. Surplus 6/8 ea.
METAL BOXES. Well vent. p. packs, etc. 1 1/2 x 1 1/2 x 7/8. 8/6 ea.
SEL. RECS. 12 v. 1 amp. 5/- 2 amp. 11/6. 4 amp. 15/- 500 v. 1 amp. containing 30/35 mm. discs, 10/- ea.
ELECTROLYTICS. Canned. 20+20 mid. 450 v. 2/6 ea. 25/- doz.
V.A.K. SLIDERS. 10 ohm 30 w. for chargers, trains. 3/- 3ea.
CONNECTING WIRE. P.V.C. 100 ft. 2/6. various colours.
RELAYS. Large stocks, assorted sizes, from 2/6 ea.
PICK-UP ARM with turn-over cartridge 19/6.
VENNER SILVER-ZINC ACCUMULATORS. H.105. New. 15/-.

VALVES TESTED ON MULLARDS ELECTRONIC TESTER

1L4	5/-	6F1	7/6	8D2	4/6	EB41	7/6	PEN45	7/6
1T4	6/6	6F6	7/-	9D2	5/-	EB91	5/6	PEN46	7/-
1U4	6/-	6F13	7/6	10F1	7/6	ECH42	8/-	PL81	12/6
3A4	6/-	6J5	6/-	12AB	7/6	ECL90	9/-	PL83	9/-
5Z4	9/-	6J6	6/-	12AH8	8/-	EF96	5/-	SP41	4/-
4D1	4/-	6J7	5/-	12AT7	6/-	EF97	9/-	SP61	4/-
6AG5	5/-	6K7	4/6	12AU7	7/-	EF98	5/6	VR150/30	40/-
6AL5	5/-	6L6	4/6	12AX7	7/-	EF99	3/6	UL84	9/-
6AM5	5/-	6SA7	6/-	12BH7	10/-	EF99	8/-	VCR97	15/-
6AM6	6/-	6SC7	4/6	12SH7	5/-	EF99	8/-	VCR138A	25/-
6AQ5	6/-	6SJ7	5/-	12SJ7	6/6	EF91	6/-	VCR139A	25/-
6AU6	7/-	6SK7	5/-	12SK7	5/-	EF92	7/-		
6EA6	8/-	6SL7	7/-	15D2	6/-	EL32	5/6		
6BE6	5/6	6SN7	7/-	50C5	10/-	EL91	5/6		
6BH6	5/6	6U5	6/6	807	6/-	EY51	5/-		
6BW6	6/6	6V6	6/6	EA50	1/6	EY51	8/-		
6C4	5/-	6X1	7/-	EABC80	8/-	EY86	9/6		
6D2	6/-	6X5	7/-			P61	4/-		

SECONDHAND VALVES. YOUR CHOICE. £1.0.0 for EIGHT.
ECL90, 6C4, 6AM6, 6AG5, 6J6, EF90, 6BE6, 3A4, EF90, SP61, P61, 6J5, PY80, PY82, Z77, 6AL5, 6K7, 6SJ7, EL32, EF42, 6D2, 20P1, 6F13, SP41, EY51, EB91, EF91, EF39, PCL83, EF36, PEN45, PEN46.

ENQUIRIES—S.A.E. PLEASE

HUGGETT'S LIMITED
2-4 PAWSONS ROAD, WEST CROYDON



TOP QUALITY AT
UNAPPROACHABLE
PRICES

With 12 Months
Full Guarantee

NEW GUN TV TUBES

*This means Completely New Gun Assembly with New Button and Base. Rescreened and Realuminized. VIRTUALLY A NEW TUBE. All Mullard and Mazda and Hardglass Types.

12"-14"	-	-	£6.0.0
15"-17"	-	-	£6.10.0
21"	-	-	£9.0.0

Electro Statics 10/- extra.

All carriage and insurance now paid by us, to your address and on return of old tube all by passenger train, inclusive at £1.

All C.W.O. Old tubes must be returned to us, or an extra charge of 10/- will be made on 12 to 17in. tubes.

SABRINA C.R.T. COMPANY
"ELECTRON WORKS," NORTH BAR
BANBURY, Oxon. Phone 2390.

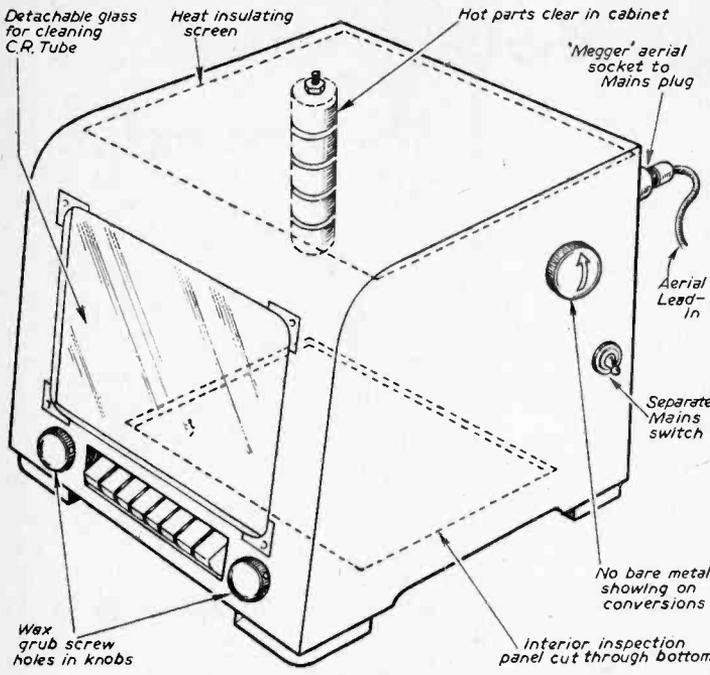


Fig. 4.—Various modifications to improve safety.

for tuning, etc., until the station is correctly set on its channel.

Common sensitivity controls are troublesome where Band I is strong and Band III weak, here if there can be found spare, unused, contacts on a switch wafer in the tuner, as there are in the Bush TV 43, the sensitivity control can be shorted out on the weak station, or a separate one switched in. Parts that experience and observation show are overloaded and prone to fail — solid carbon screen resistors in line timebases, decoupling resistors in H.T. lines—are worth changing for wire-wound types. To measure one of these over-run parts, hot and then cold, comparing it with the value it ought to be, is a revelation — three different readings.

Polish

Some modern cabinets are constructed of very thin single layer material with consequential cracking of the polish with the grain, flaking, and discoloration owing to the heat developed within the cabinet. The provision of a heat baffle by fitting a false roof of hard

property does not belong to the client has allowed circuit modification for simpler and more reliable working. A receiver with flywheel sync, notorious for wobbly verticals and line slip with every slight change in circuit condition or ignition interference has been given steady line hold permanently just by cutting out the flywheel section and providing plain sync. How this is executed depends on model and circuit; Fig. 5 shows a typical example. The point of interest with this modification is that when the sync is applied in antiphase the line will still hold, but the top of the raster just will not lock at any position, wavering about as the incorrect pulses force the line to start at any point except the right one.

board or similar fibre, inclined up to the rear of the cabinet to deflect out heat, leaving a small air pocket between the two to act as a heat insulator, will prevent this if done in time (Fig. 4).

Tuning

Difficulty in reaching tuning points in certain tuners in spaces of restricted access can be overcome by punching or drilling a small hole in the screening cover opposite the oscillator slug path and counting the number of clicks or channels to bring it into coincidence, where it is turned back a fraction, tested by switching back, the difference observed, repositioning

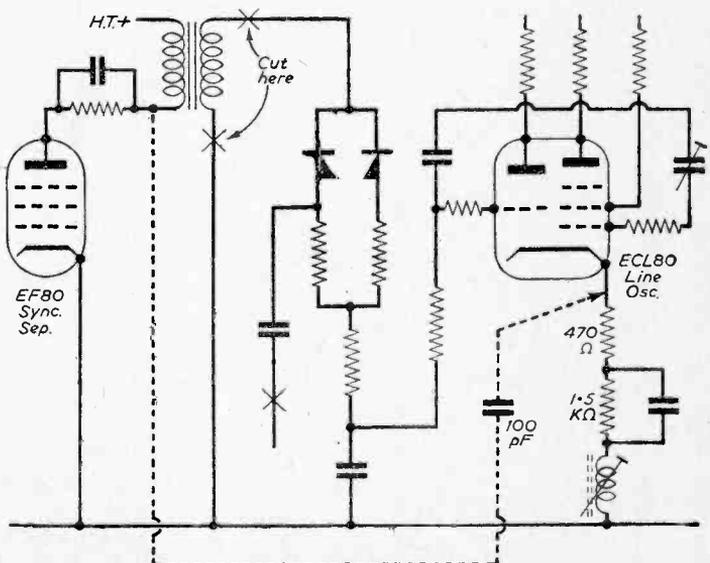


Fig. 5.—Conversion from "auto" to "plain" sync.


Vision Interference Limiters

SIMPLE "SPOTTER" CIRCUITS

EVEN with the widespread use of suppressors on all types of electrical equipment, interference is still a problem in many areas and any limiting circuit should be made as efficient as possible. This is particularly important when one is unfortunate enough to be situated near a main road as well as in an area of low signal strength.

In fact, the efficiency of the more advanced "Spotters"—to be described—is such that it is actually beneficial for the interference to be over a certain level with respect to the signal strength. This was borne out in practice, when careful siting of the aerial to reduce ignition interference from a main road resulted in an inferior picture, although the signal strength was—if anything—slightly greater.

Fig. 2.—Manually-operated interference limiter.

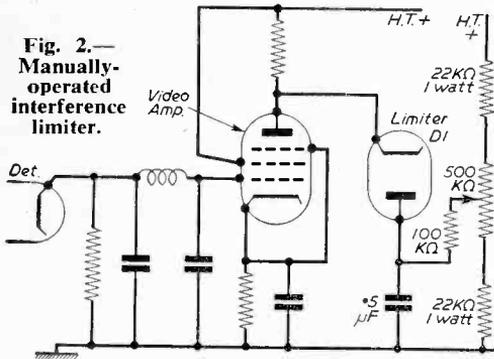

By far the most common "spotter" circuit both in commercial and home constructed television receivers is the so-called automatic limiter (Fig. 1). It is, of course, only automatic in the sense that no manual adjustment is necessary—bias for the diode being obtained by setting the time-constant of C and R so that C charges to a mean level approximating to peak-white. Pulses of interference exceeding peak-white level in amplitude cause the diode to conduct—thus shorting the video load and reducing the output, designers who employ this circuit work on the assumption that "what you never see you never miss", for it is virtually impossible to obtain reasonable spot suppression without severely clipping the picture highlights.

Highlights

To avoid losing highlights it is only necessary to provide means whereby the bias potential may be adjusted manually to suit the contrast level (Fig. 2). However, this circuit suffers from the disadvantage that limiting is accomplished by shunting the diode and condenser across the video load and, although the condenser can be made large, the internal resistance of the diode—even is small—is not zero.

Instead of using the interference pulse as a switch to short-circuit the video load, it can be used

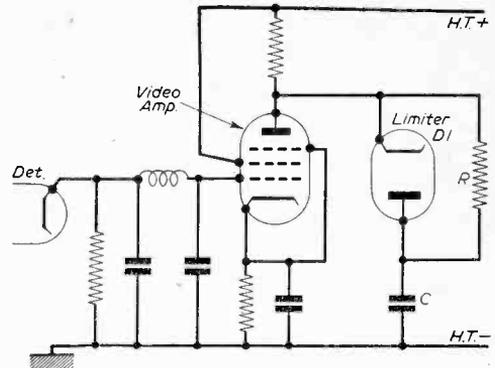


Fig. 1.—Simple automatic type of vision limiter.

(Di is a diode with as low an internal resistance as possible; R1 may have a value of 1—10M according to the level of highlight clipping which can be tolerated and C may have a value of 0.1μF).


in the form of negative feedback to the video grid circuit, and in this form the internal resistance of the diode is not so critical (Fig. 3).

A similar method is to feed the pulse to the grid of the tube (assuming cathode modulation is in use), but the limiting efficiency of the circuits shown in Figs. 3 and 4 is only slightly better than the previous methods.

Black-spotters

In America, where negative modulation of the vision carrier is used, with zero modulation corresponding to the white level, interference pulses appear on the screen as black spots, and because of this visitors who have seen American television often think that they have conquered interference problems. This is not really true, of course, but it is a fact that black spots are far less noticeable—at normal viewing distances—than white ones. This is partly due to the light intensity being lower, but also because the average picture is predominantly in shades of grey. If we take the circuit shown in Fig. 4, but

Fig. 3.—Negative pulse feedback type limiter.

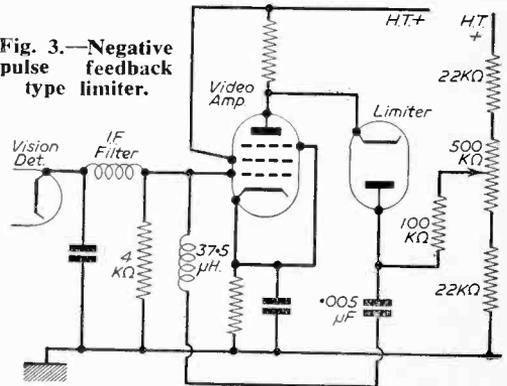

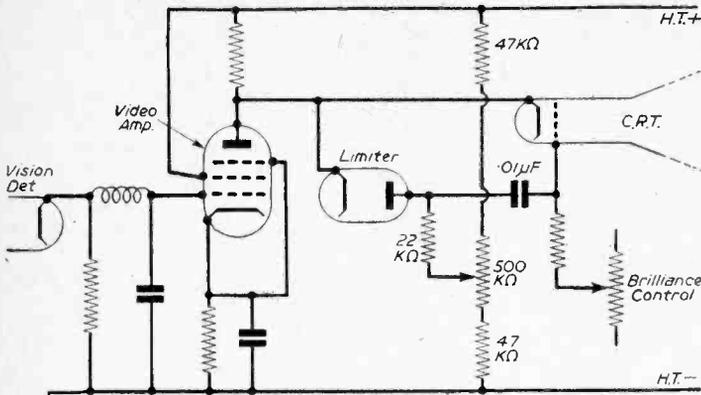


Fig. 4.—Spot inversion type interference limiter.

amplify the interference pulse before feeding it to the picture tube grid, its amplitude will be in excess of that on the cathode, and the effect will be to drive the tube to beam current cut-off and the visible effect on the screen will be a black spot instead of a white one (Fig. 5). Thus an interference pulse in excess of peak-white level is no longer limited to that (peak-white) light intensity, but can be reduced to zero (black level). Unfortunately interference pulses which do not exceed peak-white level do not operate the black-spotter circuit and this explains the statement in the opening

paragraphs that there is an optimum interference - to - signal ratio.

The "black-spotter" circuit is of no advantage where the prevailing interference level is below peak-white at the video anode, but, under certain conditions, principally in fringe areas, the reduction in visible interference spots cannot be stressed strongly enough. It is not always convenient, or practical, to add an extra stage to an existing receiver, but the circuit shown in Fig. 6 can be fitted to any receiver which already has some form of diode limiter.

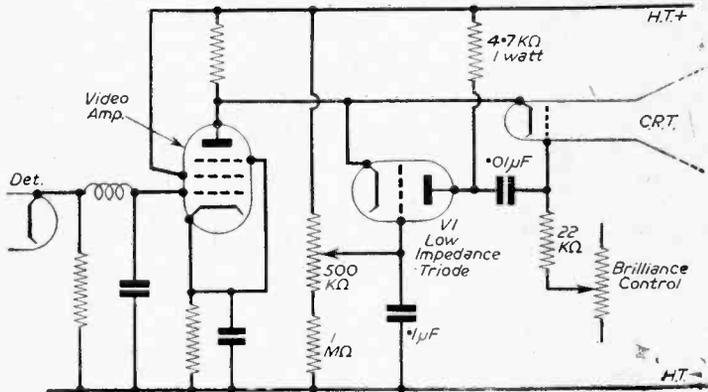


Fig. 5.—"Black spotter" limiter, using extra triode valve.

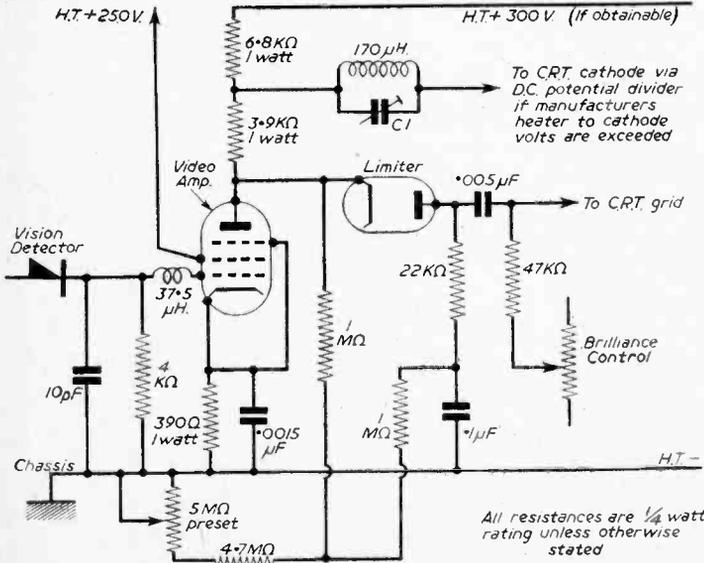


Fig. 6.—Circuit which can be added to any existing receiver.

The modifications are simple to carry out, and in an area where its inclusion is worthwhile, the slight falling off in response, caused by the higher video load, should not be apparent. If necessary a series correcting choke can be added and this will usually more than compensate for any high-frequency loss.

The extra amplification needed for the limiter circuit is obtained by using a tapped video load and it is an advantage to increase the H.T., if possible, to compensate for this additional resistance.

If the potential divider providing the bias for the diode is fed from the video anode, as shown, the circuit becomes semi-automatic in operation and small changes in contrast will not necessitate re-adjustment of the limiter-control.

All resistances are 1/4 watt rating unless otherwise stated

A Cathode Follower Voltmeter

A ONE VALVE CIRCUIT PERMITTING ACCURATE READINGS WITH METERS

WHEN using an ordinary voltmeter on television equipment, the readings are often very inaccurate owing to the comparatively large current drawn by the instrument. For example in Fig. 1, the presence of the meter will make the anode voltage about 16 per cent lower than normal. The cathode follower voltmeter will give a considerable improvement in this instance and in many others. This old dodge does not seem to be widely known nowadays among experimenters.

Basic Circuit

The basic circuit is shown in Fig. 2. The voltage under test is applied as an input to a cathode follower and the output of the cathode follower is

For lower ranges, where the circuit impedances will usually be lower (e.g. cathode voltages), the meter will often give most accurate results when connected directly.

Even in cases where the error of the cathode follower voltmeter is large compared with the voltage under test, it may still have advantages because of the small loading.

The error due to bias can be determined from curves or by a check using a low impedance supply. On the other hand, the change in voltage which occurs on connecting the meter directly may be difficult or even impossible to calculate.

While the basic circuit is adequate where a "hook up" is used for a few measurements, a leak from grid to earth is desirable if the circuit is made in permanent form to prevent possible meter overloading when the grid is left floating. This can be made very high so that the loading on the circuit under test is still very small (say 4.7M giving a load of $53\mu\text{A}$ at 250V).

A grid stopper (about 220k) is advisable to limit grid current if excessive voltage is applied.

Naturally the valve must not be worked with the grid positive with respect to the cathode for the loading would then be appreciable. The upper limit of voltage measurement is thus less than the H.T. supply by the drop across the valve at zero bias.

To cater for higher voltages the grid could be shifted to a tap at the mid-point of the grid leak by a ± 2 press button as shown in Fig. 4.

The heater-cathode insulation might be inadequate but for many valves, this insulation will withstand up to 250V so this point will often not arise. Battery operation of the heater is quite feasible for the short periods for which the instrument will be used or a separate small heater transformer could be used.

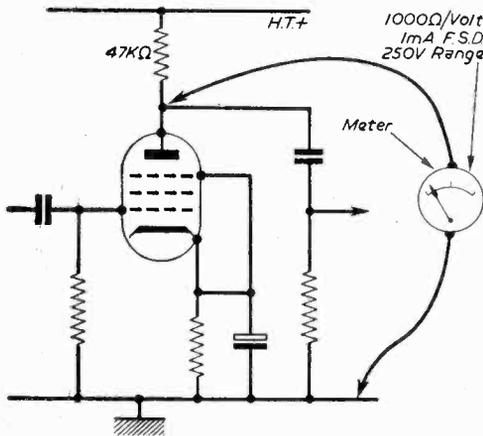


Fig. 1.—Using a conventional meter to read an anode voltage; errors may be introduced if the meter takes a large current.

applied directly across the meter (using the same range as would be used directly). The input resistance of the cathode follower is of course very high and so the load on the circuit under test is negligible. There will however be an error because grid bias is required and so the cathode voltage will exceed the grid voltage by this amount. This error will be much less than that caused by loading in a circuit such as in Fig. 1. The heater and H.T. supplies are simply tapped off those of the apparatus under test.

The errors due to bias have been found from the makers curves for $\frac{1}{2}$ 12AX7 assuming a meter having an f.s.d. of 1mA as this is probably the most usual meter in the amateur's den. These are plotted in Fig. 3 for two values of H.T. and, for comparison, two error curves for the meter connected directly as in Fig. 1 have been put on the same graph.

Advantages and Limitations

In the example taken, there is a decided gain in accuracy and this will hold for most measurements where the voltage is more than about 25.

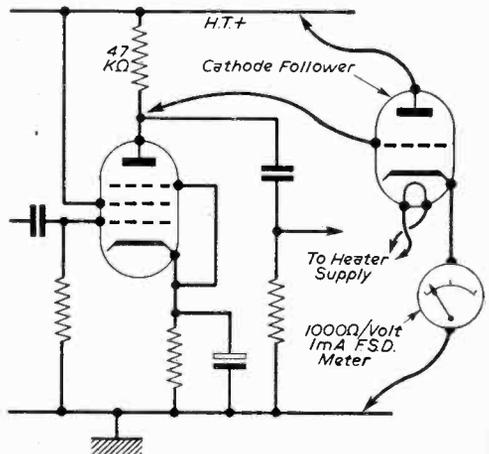


Fig. 2.—Using the cathode follower voltmeter for reading an anode voltage.

By J. COOPER

OF LOW SENSITIVITY

Circuits using valves of different heater ratings may require checking. Battery or separate transformer operation is again the answer.

Choice of Valve

If the valve curves are available, the performance of the circuit with any meter can be checked easily by the usual load line construction. If, however, only a fixed set of operating conditions are given, an approximation to the error curves can be drawn.

The formulae for this purpose are:—

Maximum Error = (V/μ) volts.

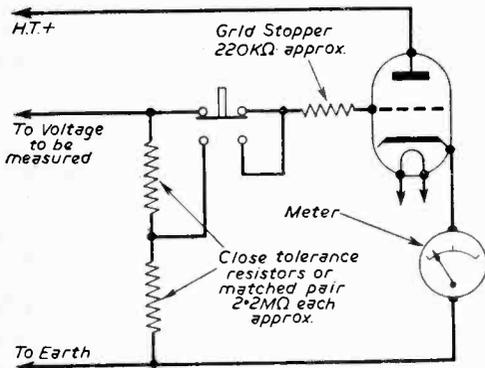


Fig. 4.—A suitable circuit for the cathode follower voltmeter.

$$\text{Maximum meter reading} = \frac{V}{(1 + ra/Rm)} \text{ Volts.}$$

Where V = H.T. supply voltage.
 μ = Amplification factor of valve
 a = Anode resistors of valve in ohms

(Quoted in operating conditions)
 Rm = Meter resistance in ohms.

To show the use of these formulae, it will be assumed that $\frac{1}{2}$ 12AT7 is being considered for use with a meter of $200\Omega/V$ (5mA f.s.d.) and an H.T. supply of 300V, the meter range being 250V. Firstly, two axes should be drawn on the graph paper as in Fig. 5. Now the maximum error should be worked out. In the case considered, a value of 55 is quoted for μ .

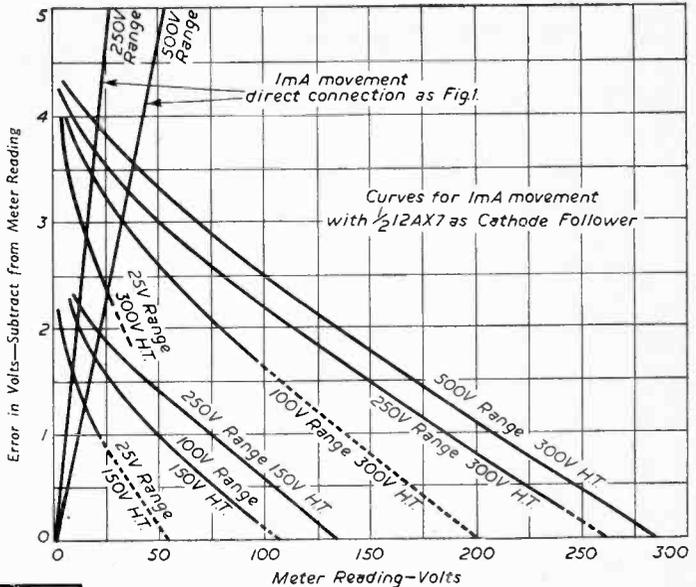


Fig. 3.—Error curves corresponding to the connections in Figs. 1 and 2.

\therefore Max. Error = $300/55 = 5.5V$.

This value of 5.5V should be marked on the error axis—point A in Fig. 5.

To find the maximum meter reading requires a value which is given as $10,000\Omega$ and Rm.

$$Rm = 250V \times 200\Omega/V = 50,000\Omega$$

Thus, max. meter reading =

$$\frac{300}{1 + (10,000/50,000)} = \frac{300}{1.2} = 250V.$$

A point should then be marked at 250V on the meter reading axis (point 'B' in Fig. 5). Then join these points by a straight line.

(Continued on page 380)

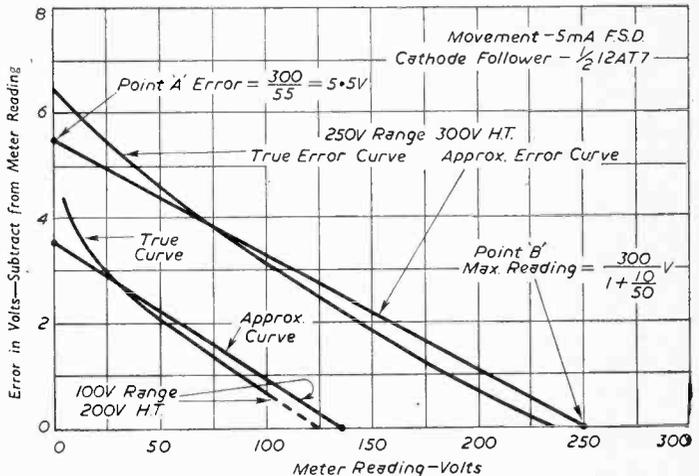


Fig. 5.—Comparison of approximate method and true error.

TELENEWS



Television Receiving Licences

THE following statement shows the approximate number of Television Receiving Licences in force at the end of January 1960 in respect of television receiving stations situated within the various Postal Regions of England, Wales, Scotland and Northern Ireland.

Region	Total
London Postal	1,773,249
Home Counties	1,370,459
Midland	1,557,496
North Eastern	1,672,193
North Western	1,368,563
South Western	856,602
Wales and Border Counties	612,711
Total England and Wales	9,211,173
Scotland	872,089
Northern Ireland	136,605
Grand Total	10,219,867

International Festival

THE Swiss television network has now given its full support to the world's first International Festival of Television Arts and Sciences. Announcement of this official backing was made by Mr. Edward Haas, Director of the Swiss Television Authority. He said the network would sponsor the International Festival to be held at Montreux during the second half of May next year, and disclosed that governmental and independent networks from Africa, Asia, Britain, the Commonwealth countries, Europe, the Middle East, Russia, Latin America and the United States have been asked to participate. The first British network to express its interest is ABC Television. Other Networks from Australia, Argentine, France, Germany, Holland, Mexico, Russia, Britain and America are now also in touch with Montreux. The idea of the Festival was first proposed by the Montreux City Council some months ago and was originally scheduled for May this year. Because of the tremendous

interest aroused, it has been postponed to permit maximum world participation.

Amateur TV Convention

THE fifth Amateur Television Convention, organised by the British Amateur Television Club, will be held on Saturday, 10th September 1960, in the Conway Hall, London, W.C.1.

Contract


MADAME S. EKE, Chief Engineer of the Turkish Broadcasting Administration, recently paid a visit to the Marconi Company's Chelmsford Works. Marconi's are currently engaged in fulfilling a £1,000,000 contract for the complete re-organisation of the long wave

broadcasting station at Ankara; this includes the doubling of the existing power output to 240kW and a considerable extension of the existing studio and control facilities.

ITA's Dover Station

THE Independent Television Authority's transmitting station at Dover, which came into full programme service on 31st January serves a population of approximately one million. The service area covers those parts of Kent and Sussex which are bounded by Folkestone, Dover, Margate, Chatham, Tunbridge Wells and Eastbourne.

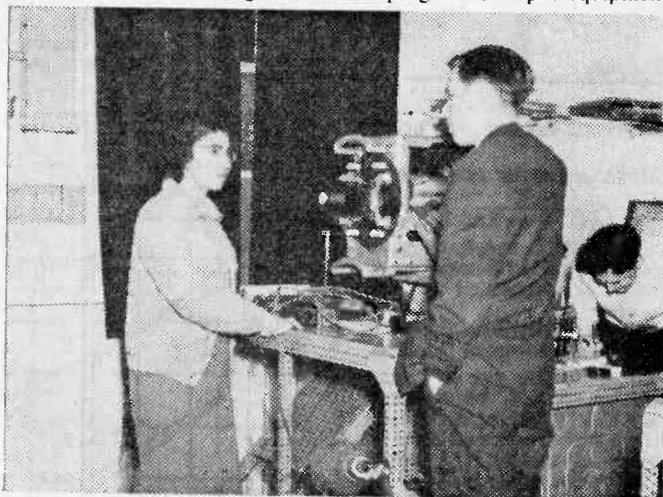Marconi's Wireless Telegraph Co. Ltd. have been responsible for the supply and installation of the transmitters, the combining units, the paralleling equipment, the programme input equipment,



Madam S. Eke, Chief Engineer of the Turkish Broadcasting Administration recently paid a visit to Marconi's Chelmsford Works. Here she is seen discussing the latest Marconi television camera, the Mark IV, with Mr. A. G. Husbury of Broadcasting Division.

the control desk, the flying spot caption scanner and test equipment.

The two Band III vision transmitters are each of 4kW peak output power whilst the two sound transmitters each have an output of 1kW. Provision has been made at the Dover station for parallel operation should this ever be required, but it is the present intention of the Authority to use one vision and one sound transmitter only for the programme service, with the other two as 'stand by'.

The transmission is vertically polarised, with an effective radiated (vision) power of 100kW in the direction of maximum propagation. The station operates in Channel 10, the vision signals being radiated on a frequency of 199.7135Mc/s and sound on 196.1985Mc/s.

New British Standard

Fixed ceramic-dielectric capacitors Grade 1 for use in telecommunication and allied electronic equipment (B.S. 2133A: 1960) Grade 1 General requirements and tests.

THIS new publication specifies general requirements and tests for fixed ceramic-dielectric capacitors, Grade 1, for use in telecommunication and allied electronic equipment.

The capacitors are suitable for use in tuned circuits or in any other application where low loss and stability of capacitance are essential. They are for radio-frequency currents not exceeding 1A or a reactive power not exceeding 200VA and having a nominal temperature co-efficient not exceeding 1500 parts per million. They are not intended for radio interference suppression nor for isolation purposes in telecommunication equipment. (Capacitors for these applications are dealt with in B.S. 613 and B.S. 415, respectively).

Part 1 includes a series of mechanical robustness and climatic and durability tests for the capacitors together with colour codes for indicating capacitance value, tolerance and temperature co-efficient.

Part 2 of B.S. 2133A, comprising a list of standard sizes, ratings, etc., for these capacitors, will be published in due course.


Copies of this Standard may be obtained from the British Standards Institution, Sales Branch, 2 Park Street, London W.1. Price 12s. 6d. (Postage will

be charged extra to non-subscribers.)

Rehearsal Rooms

GRANADA TV's new rehearsal rooms at the Oval, London, are now in use for the first time. The illustration below shows leading members of the cast of "Member of the Wedding"—which was transmitted on Tuesday, 16 February—rehearsing a scene under the direction of Julian Amves. They are (left to

Orthicon Cameras and a zoom lens. The cameras can be fitted with either 3in. or 4½in. Image Orthicon pick-up tubes. In this case, they will use 4½in. tubes, which can easily be replaced through the lens turret, without opening the side panels of the camera. Four video outputs and four sound outputs from the vehicle are provided to make it possible to distribute signals independently to four monitors.

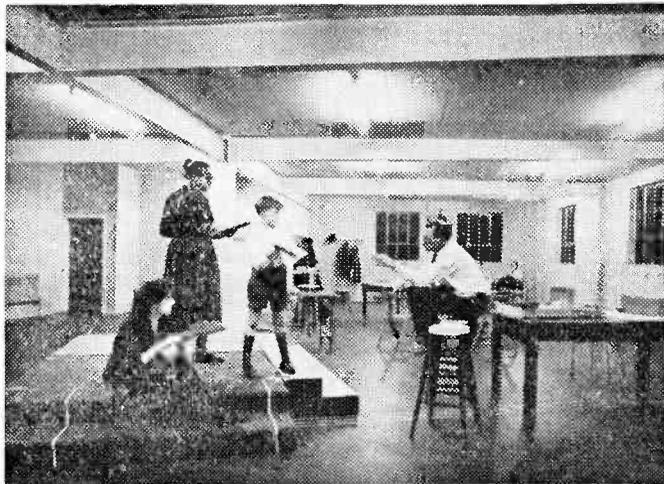

Granada TV's new rehearsal rooms at the Oval, London. This illustration shows leading members of the cast of the play "Member of the Wedding", rehearsing a scene under the direction of Julian Amves.

right) Frances Guka, Vinette Carroll and Dennis Waterman. Granada Group Ltd., has acquired the lease of a former factory building at the Oval. It has a total floor space of 2,000sq. ft. and is being converted and modernised at a cost of £25,000. The building is designed as a central depot for servicing more than fifty Granada theatres in London and the Home Counties. It will also provide additional facilities—including the rehearsal rooms for Granada's television operations.

TV Unit for Hungary

AN order has been received from Elektroimpex, Budapest, on behalf of the Hungarian Broadcasting Authority by E.M.I. Electronics Ltd., for one of the Company's latest Outside Broadcast Units. The vehicle, which will be used for televising outdoor events from all over Hungary, will be equipped with four of the latest E.M.I. Image

when the vehicle is used as the control room for a Television Studio.

Another interesting feature is the provision of a special position in the Unit for a "Production Chief Engineer". Besides inspecting the picture quality of all four camera channels, he can check the output of a microwave link, the picture received by the off-air monitoring receiver and one external video source.

BBC Appointment

THE BBC has announced the appointment of Mr. W. L. Nicoll, A.M.I.E.E., as Engineer-in-Charge of the Kirk o' Shotts Television and VHF sound broadcasting station in succession to the late Mr. J. Cleland. Mr. Nicoll joined the Corporation in 1937 as a maintenance engineer at the Burghhead transmitting station. He has held the post of Assistant Engineer-in-Charge of the Kirk o' Shotts station since it was opened in March 1952.

Make Your Own Abacs

SIMPLIFY RESISTOR CALCULATIONS

By T. Pickering

MOST amateur wireless enthusiasts use abacs at some time during their career, but how many of them are able to construct their own? Very few, probably, because abacs (or nomogram) theory is rather complicated and many amateurs have neither the time nor the inclination to master it. For this reason a simple, straight-forward method is given below for one commonly used type of abac.

Equations

The abac to be described will solve equations such as $y = k \cdot x_1^a \cdot x_2^b \dots$, x_n^c , where x_1, x_2 etc., are variables and k, a, b , etc., are constants. This may look rather formidable at first sight, but a familiar example is the expression of Ohm's Law i.e. voltage = current \times resistance or, $E = IR$. In this case, comparing the expression for Ohm's Law with the general equation given above, $y = E, x_1 = R, x_2 = I$ and k, a and b are all equal to one.

To illustrate the principle of construction, an abac will be made to solve Ohm's Law. This will be very handy when resistor values have to be calculated, as once constructed, it is there for good and tedious calculations are eliminated. The materials required in its construction are some tracing paper (or similar semi-transparent paper), a slide rule or semilog paper and a little patience.

Procedure

The procedure is as follows; first draw up a modulus chart as shown in Fig. 1, using the semilog paper or the centre portion of a five inch or ten inch slide rule to mark off on tracing paper a one-cycle log scale. Draw two lines like this spaced about six inches apart. Number from one to ten then join the numbers with horizontal lines as shown. Then, starting at 1 in the bottom left-hand corner, draw a line connecting 10 in the top right-hand corner, then 1 to 9, 1 to 8 and so on down to 2. The space between 1 and 2 should then be marked off as shown or, preferably, the whole thing re-drawn up to the horizontal lines and then each whole number space subdivided as illustrated in the space between 1 and 2. When the modulus chart (or charts) is completed, the abac can be commenced.

On a sheet of tracing paper draw two vertical lines a few inches apart. Using the modulus chart

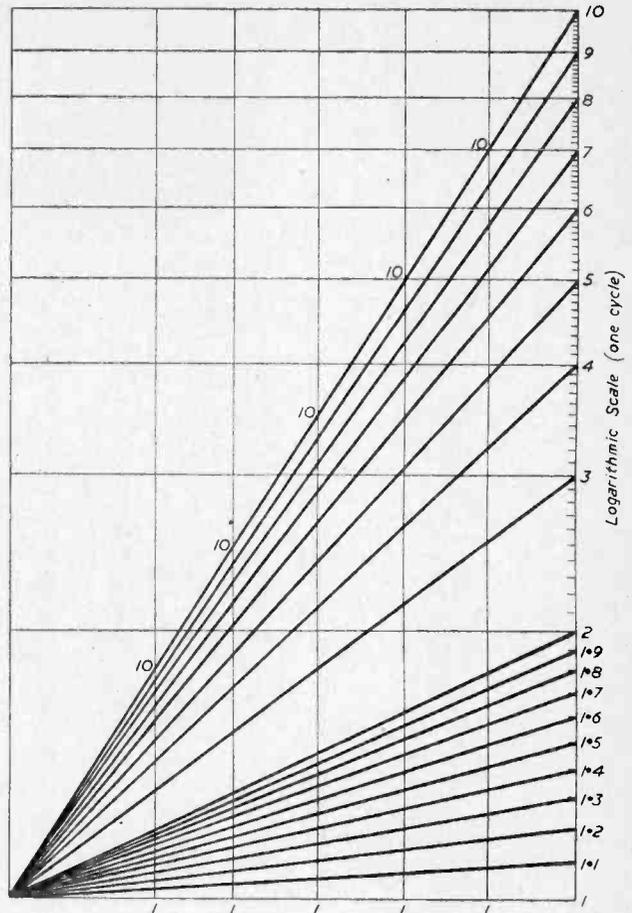



Fig. 1.—Drawing the modulus chart.

of Fig. 1, mark off suitable set of values on the left-hand vertical line as shown in Fig. 2 on the lines marked "milliamps". On the scale in Fig. 2, one and a half cycles has been used. This was done by using one of the smaller scales on the modulus chart and half repeating it. On the right-hand vertical line mark off a set of values for voltage as in Fig. 2. (Note that this is also a small cycle repeated three times *but in the reverse direction*.) The reason for this is that the equation being solved is another equivalent of Ohm's Law, $R = E/I$ or $R = E I^{-1}$, where I has a negative exponent so that one of the lines (it is immaterial which one) has to be marked off in the reverse direction.

Second Scale

The second modulus chart or the portion of Fig. 1 which has been subdivided (between 1 and 2) may now be used to subdivide the larger spaces on the current and voltage lines. This is most easily carried out by placing the abac over the modulus chart and moving it so that the ten-line

7-VALVE AM/FM RADIOGRAM CHASSIS

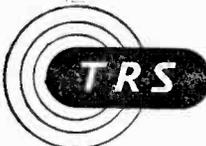

Valve Line up:
ECC85, ECH81,
EF89, EABC80,
EL84, EM81, EZ80.



3 waveband and switched gram positions. Med. 200 m.-500 m., Long 1,000 m.-2,000 m., VHF/FM 88-95 Mc/s.
4 Controls. Vol., On-off, Tone, Tuning. Wavechange. P.U., Ae. and E., and speaker sockets. Magic eye tuning. Philips continental tuning insert with permeability tuning on FM, and combined AM/FM IF transformers, 460 Kc/s and 10.7 Mc/s. Dust core tuning all coils. Latest circuitry, including AVC and Neg. Feedback. 3 watt output. Sensitivity and reproduction of a very high standard. Chassis size 13 1/2 in. x 6 1/2 in. Height 7 1/2 in. Edge illuminated glass dial 1 1/2 in. x 3 1/2 in. Vertical pointer, Horizontal station names, gold on brown background. A.C. 200/250 v. operation.

£13.10.0 Carr. and Ins. 5/-. Complete with 4 knobs walnut or ivory to choice

As previously announced fresh supplies are now being received, but we regret some slight delay may be experienced in fulfilling orders for this popular item.

RE-GUNNED TV TUBES

New Reduced Prices!

And now 12 months' Guarantee!

12in.	£6	17in.	£8.10.0
14in.	£7	21in.	£10.10.0
15in.	£7.10.0		

All tubes Rebuilt with new Heater Cathode and Gun Assembly—reconditioned virtually as new! Full 6 months' unconditional Guarantee. As used by our own Service Dept. Comprehensive stocks—quick delivery. 10/- part exchange allowance on your old tube.

RECORD PLAYER CABINETS

Contemporary styled, rexine covered cabinet in two-tone fawn and brown, or mottled red with white polka dot. Size 18 1/2 in. x 14 in. x 8 1/2 in., fitted with all accessories, including baffle board and anodised metal fret. Space available for all modern amplifiers and autochangers etc. Uncut record player mounting board 14 x 13in. supplied.

£33.3.0



2-valve AMPLIFIER Mk.2

Latest developed circuit giving a higher fidelity response and greater output (2-3 watts) using twin stage valve ECL82 and neg. feedback Tone Control. Complete with knobs, etc., wired and tested ready to fit in above cabinet.

ONLY £2.17.6. P. & P. 1/-.

6in. speaker and matching transformer, 22/- P. & P. 1/6.

SENTRELEC RECTIFIERS. E.H.T. Type Fly-back Voltages, K3/25 2 kV., 5/-; K3/40 3.2 kV., 6/9; K3/45 3.6 kV., 7/8; K3/50 4 kV., 7/9; K3/100 8 kV., 13/6. **MAINS TYPES**—RM1, 125 v., 60 mA., 4/8; RM2, 125 v., 100 mA., 5/6; RM3, 125 v., 120 mA., 7/8; RM4, 250v., 250 mA., 16/-; RM4B type 270 mA., 17/8; RM6, 250 v., 300 mA., 21/-.

SPEAKER FRET—Expanded Bronze anodised metal 8 x 8in., 2/3; 12 x 8in., 3/-; 12 x 12in., 4/6; 12 x 15in., 6/-; 24 x 12in., 9/-, etc. Listed above are only a few items from our very large stock. Send 3d. stamp today for Complete Bargain List.

FULLY GUARANTEED VALVES

NEW REDUCED PRICES	NEW REDUCED PRICES
1R5, 1T4 7/0 DAF96 9/- EF80 9/6 PCF82 10/6	185 7/6 DF96 9/- EF86 13/6 PCL83 12/6
384, 3V4 8/ JPK96 9/- EF91 8/6 PL41 12/6	324 9/6 DL96 9/- EL41 10/6 PLS2 9/6
6K7 5/6 EABC80 9/6 EL84 9/6 PLR3 11/6	6K8 8/6 EBC41 9/6 EM81 10/6 PY80 7/6
6Q7 8/6 ECC83 9/6 EY51 9/- PY81 9/6	6N7 8/6 ECC84 10/6 EY86 10/- PY82 7/6
6V6 7/6 ECF80 11/6 EZ80 7/6 PY83 10/6	6X4 7/6 ECF82 11/6 IZ81 7/8 UZ5 12/6
7C5 9/- ECH81 10/6 NU14 9/6 U191 12/6	7X4 8/6 ECL80 10/6 PCC84 10/6 UCH42 10/6
35L6 9/6 ECL82 11/6 PCF80 10/6 UY41 10/-	

Send for List of more Valve Bargains.

SPECIAL PRICE PER SET

1R5, 1T4, 185, 384 or 3V4	27/6
DK96, DP96, DAF96, DL96	35/-
6K8, 6K7, 6Q7, 6V6, 6Z4 or 6X5	38/-

COAX


80 OHM CABLE. Stand 4in. diam. Low Loss Seal-Air Spaced Aerialax. Top grade cable—not to be confused with inferior types
SPECIAL REDUCED PRICES
20 yds. 12/6. p. & p. 1/6; 60 yds. 32/8. p. & p. 3/-; 40 yds. 22/8. p. & p. 2/6; All other lengths 8d. per yard
Coax Plugs 1/-, Sockets 1/-, Couplers 1/3, Cable End Sockets 1/6, Outlet Boxes 4/8.

TRANSISTOR 'ONE-WATT' AMPLIFIER

6 v. Battery operated
Latest Push-Pull, 4 Transistor circuit giving full 1 watt Output into standard 3 ohm speaker. Good sensitivity and improved freq. response. Neg. feedback. Var. Tone and Volume Controls. Chassis Size 6 1/2 in. x 3 1/2 in. x 1 1/2 in. Current consumption 10 mA quiescent—250 mA at 1 watt. 2 matched GEC GET15 Transistors. 42/- pr. 2 GEC GET3 Transistors. 21/- pr. Driver Trans. (to 3 ohms). 10/8
Output Trans. (to 3 ohms). 10/8
Complete Kit of Parts incl. circuit etc. speaker.
ONLY 99/6 P. & P. 2/6.
Circuit and instruction booklet 1/6 post free.

VOLUME CONTROLS

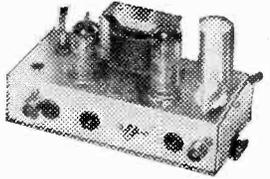10,000 ohms—2 Megohms. All long spindles. Morganite Midget Type. 1 1/2 in. diameter. Guar. 1 year. Log or Lin. Ratios. Less Sw. 3/-. D.P. Sw. 4/9. Twin Ganged controls. 1/2 meg. 3/4 meg., 1 meg., less Sw. 8/9 ea.



BAND 3 TV CONVERTER

All channels 7-13 (180-205 Mc/s). Mk. 2 Model. Latest cascade circuit using ECC84 and EF80 valves. 18db gain over standard circuits. Built-in Power Supply 200-250 v. A.C. Size 6 1/2 in. x 3 1/2 in. x 3 1/2 in. Simple to fit—only external plug-in connections. Wired and aligned ready to use. Only 79/6, P. & P. 2/6.
B1-B3 changeover Sw. and BBC Aerial Socket fitted and wired. 8/- extra.
Band 3 Aerials. Single Dipole with 4 yds. cable, 13/9. 3 Element Beam, 25/-, 5 Element, 32/6, etc. B1-B3 Crossover Units, 7/6.

RECORD PLAYER BARGAINS

NEW RELEASE BY E.M.I.—4-speed Single Player Unit fitted with latest stereo and monaural Xtal cartridge and dual cassette styli. Auto stop and start. A fidelity unit and bargain buy at only **£8.19.6.**
BSR—UAS Model.—4-speed autochanger with crystal turnover cartridge, etc., wired for stereo. Bargain **£8.19.6.**
Garrard—Latest RC121/D/Mk. 2—fitted with GCR Xtal cartridge, plug-in, modular head. Auto manual selector, etc. The connoisseur's choice for audio perfection. Bargain 10 gns.
Plug-in stereo head GCR/10 £2 extra.
All above are brand new, fully guaranteed models. Carr. and Ins. 4/6.
Comprehensive bargain range of Collaro, BSR and Garrard Units in stock. Send for comprehensive bargain lists.

G.R.T. Heater

Isolation Transformers
New improved types—mains prim. 200/250 v. tapped.

All Isolation Transformers now supplied with alternative *no boost plus 25%*, and *plus 50%* boost taps, at no extra charge.
2 v. 24 type 12/6 (P. & P. 1/6)
6.3 v. .6A 12/6 ..
10.5 v. .3A 12/6 ..
13 v. .3A 12/6 ..
Other voltages available at same prices.
Small size and tag terminated for easy fitting.

JASON FM TUNER UNITS

(87-105 Mc/s)
Designer-approved kits of parts for these quality and highly popular tuners available as follows.
STANDARD MODEL (FMT)—as previously extensively advertised. COMPLETE KIT, 5 gns. post free. Set of 4 spec. valves, 30/-, post free.
LATEST MODEL (FMT2)—attractively presented shelf mounting unit to enclosed Metal Cabinet with Built-in Power Supply. COMPLETE KIT, 57 p. & p. 3/6. Set of 5 spec. valves, 38/6.
NEW JASON COMPREHENSIVE F.M. HANDBOOK. 2/6 post free. 48 hr. Alignment Service, 7/6, p. & p. 3/6.

TYGAN FRET (Murphy pattern) 12 x 12in., 2/-; 12 x 18in., 3/-; 12 x 24in., 4/-, etc.
SPEAKERS P.M. 3 ohm 2 1/2 in. Elac, 16/6. 3 1/2 in. Goodmans, 18/6. 5in. R. & A., 17/8. 6in. Celestion 18/6. 7 x 4in. Goodmans, 18/6. 8in. Rois, 20/-, 8in. Special Cone G'mans, 21/8. 10in. R. & A., 25/-.

Terms: C.W.O. or C.O.D. Kindly make cheques, P.O.s etc., payable to T.R.S. Post/Packing up to 1/6. 7d. 11s. 1/1, 3/6, 1/6, 5/6, 2/-, 10/6, 2/9
Hours: 9 a.m.-6 p.m. 1 p.m. Wed. Open all day Saturday.



RADIO COMPONENT SPECIALISTS (Est. 1946)

70 BRIGSTOCK ROAD, THORNTON HEATH, SURREY (THO 2188)

50 yards Thornton Heath Station. Buses: 130A, 133, 159, 166 and 190

RST

MAIL ORDER DEPARTMENT
 211 Streatham Road, Mitcham, Surrey
ALL VALVES LISTED ARE NEW STOCK
 *Terms C.W.O. or C.O.D. Postage 3d. per valve.
MITCHAM 6201.

AZ31 10/6	EF92 5/-	PCF82	UY85 7/6	6K8G 7/6
B65 8/6	EL42 10/-	VP4B 17/6	6K8GT	
DAF81 7/6	EL84 7/-	W81M 5/9	6L1 12/6	
DAF86 9/6	EL90 8/6	W142 9/-	6L5G 7/6	
DF81 5/-	EM30 10/-	PCL83 11/6	6L18 12/6	
DH719 7/6	EM81 10/-	PEN12 12/-	6L19 21/-	
DK91 9/-	EY81 10/6	PEN4A 17/6	6N7G/GT 7/6	
EABC80	EY84 8/6	PEN4VA 17/6	6S17GT 6/6	
	EY86 9/6	PL36 15/-	6V6G 5/6	
EA4210	EY91 9/-	PL81 14/9	6S5GT 5/6	
EB81 5/-	EZ35 7/-	PL82 8/-	7S7 10/6	
EBC41 9/6	EZ40 7/6	PL83 10/6	7Y4 7/6	
EBF80 9/6	EZ41 7/6	PY80 8/6	8D3 5/6	
EBF89 9/-	EZ80 7/6	PY81 7/6	10LC11	
EC91 9/6	EZ81 7/6	PY82 8/-	12A8 15/-	
ECC33 8/-	FC2 21/-	PY83 8/6	12A8 9/-	
ECC81 8/-	FC4 17/6	R10 21/-	12A7 9/-	
ECC83 9/6	FC13 17/6	R19 19/6	12A7 9/6	
ECC84 9/6	CZ32 11/6	R19 19/6	12A6 9/-	
ECC85 9/6	H30 5/6	TDD4 17/6	12B6 9/6	
ECF80	HG3 9/6	TP22 17/6	12B6 9/6	
	HBC90 9/6	U142 8/-	12BH 15/-	
ECF82 12/6	HL92 6/6	U147 7/-	12J7G/GT 8/6	
ECH35 9/6	HL133D 10/-	U153 9/-	12K7GT 9/6	
ECH4210	KT33C 10/-	UABC80 8/-	12K8GT 9/6	
ECH81 9/-	KT66 17/6	UAF42 9/6	12K9GT 12/6	
ECL80 9/-	LZ319 12/6	UBC41 9/6	12Q7GT 8/6	
ECL82 12/6	MKT4(5) 17/6	UBF80 9/6	6B12 5/-	
EF37A 8/6	(or 7) 17/6	UCH42 9/-	6B13 17/6	
EF40 15/-	M14 9/6	UCH81 9/-	6D2 5/6	
EF41 9/6	MSP4 17/6	UCL83 23/6	6F1 15/6	
EF42 10/6	MU14 9/-	UF41 9/-	6F12 5/-	
EF50(A) 4/6	MX40 17/6	UF49 8/-	6F13 17/6	
EF90 7/-	N142 9/6	UP89 8/-	6G5C 7/6	
EF85 7/-	N153 11/6	UL41 9/6	6J7GT 9/6	
EF98 11/6	PCC84 9/6	UL84 9/6	6K7 4/6	
EF89 10/-	PCF80 10/6	UY41 7/6	6K7G 4/6	
EF91 5/-			6K7GT 10/6	

SEND FOR LISTS.

Quotations given for any types not listed. Obsolete and old types a speciality.

TELEVISION TUBES REBUILT

A NEW GUN IN EVERY TUBE
 Buy direct from the factory!
 12 months' guarantee

12 inch - £5-0-0
 14 inch - £5-10-0
 17 inch - £6-10-0

Special terms to the trade

Carriage and insurance 12/6 extra

ELECTRONIC MAINTENANCE SERVICES

131, St. Ann's Road, Tottenham, London, N.15 STAmford Hill 3267

FREE TO AMBITIOUS ENGINEERS

— THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

Have you sent for your copy?
ENGINEERING OPPORTUNITIES is a highly informative 156-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronics Courses, administered by our Specialist Electronics Training Division—the B.I.E.T. School of Electronics, explains the benefits of our Employment Dept. and shows you how to qualify for five years promotion in one year.

We definitely Guarantee
"NO PASS — NO FEE"

Whatever your age or experience, you cannot afford to miss reading this famous book. If you are earning less than £20 a week, send for your copy of "ENGINEERING OPPORTUNITIES" today—FREE.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY (Incorporating E.M.I. Institutes)
 (Dept. SE/20), 29 Wright's Lane, London, W.8

WHICH IS YOUR PET SUBJECT?

- Mechanical Eng.
- Electrical Eng.
- Civil Engineering.
- Radio Engineering.
- Automobile Eng.
- Aeronautical Eng.
- Production Eng.
- Building, Plastics, Draughtsmanship, Television, etc.

GET SOME LETTERS AFTER YOUR NAME!

- A.M.I.Mech.E.
- A.M.I.C.E.
- A.M.I.Prod.E.
- A.M.I.M.I.
- I.O.B.
- A.F.R.Ae.S.
- B.Sc.
- A.M.Brit.I.R.E.
- City & Guilds
- Gen. Cert. of Education
- etc., etc.

PRACTICAL EQUIPMENT

- Basic Practical and Theoretic Courses for beginners in Radio, T.V., Electronics, etc., A.M.Brit.I.R.E. City & Guilds Radio Amateurs' Exam. R.T.E.B. Certificate P.M.G. Certificate Practical Radio
- Radio & Television Servicing Practical Electronics Electronics Engineering Automation

INCLUDING TOOLS!

The specialist Electronics Division of B.I.E.T. (Incorporating E.M.I. Institutes) NOW offers you a real laboratory training at home with practical equipment. Ask for details.

B.I.E.T. SCHOOL OF ELECTRONICS

POST COUPON NOW

Please send me your FREE 156-page "ENGINEERING OPPORTUNITIES" (Write if you prefer not to cut page)

NAME _____

ADDRESS _____

SUBJECT OR EXAM THAT INTERESTS ME _____ (SE/20)



THE B.I.E.T. IS THE LEADING ORGANISATION OF ITS KIND IN THE WORLD

subdivision just fills one space on the current line, then mark off the subdivisions where they cross the current line. Do the same with each space on current and voltage lines until the spaces become too small to subdivide into ten, then mark off as a half-space (i.e., divide into two instead of ten).

Resistance Scale

When current and voltage spaces are completed, the position of the resistance scale must be determined this must lie between and parallel to the current and voltage scales. In order to do this it is best to use one fixed resistance (say 1k) and remembering that $1A = 1000mA$, then $100V/100mA = 1k$. Take a ruler and lay it across the current and voltages scales at 100mA and 100V (line 1, Fig. 2) and join the two points. The resistance scale must lie somewhere on this line. Since 50V divided by 50mA also equals 1k, another line (line 2, Fig. 2) drawn from 50mA to 50V will intersect the first line at a point through which the resistance scale passes. To make certain, 10V divided by 10mA equals 1k, so draw a further line between 10mA and 10V and this, again should intersect the first two lines (line 3, Fig. 2). At the intersection of these three lines, draw another line which is vertical and therefore parallel to the current and voltage lines, and this is the line on which resistances are to be marked off.

Having fixed the scale at 1k, the 100Ω mark may be fixed by joining 100mA and 10V (line 4, Fig. 2), since $10V \text{ divided by } 100mA = 100\Omega$. Further points may be fixed by lines 5, 6 and 7 (Fig. 2) as shown. It will be noticed that all these cycles are the same length, so all that is now necessary to complete the abac is to determine the points on one cycle, then trace them and mark off on the others. This may be done quite easily as $4V \text{ divided by } 200mA = 20\Omega$, $6V \text{ divided by } 200mA = 30\Omega$, and so on for a complete cycle.

Uses

The use of the abac, of course, should by now be fairly familiar, as it has been used to determine several points on the resistance scale. It may be used to calculate current, voltage or resistance, providing that any two of the three values are known, e.g., if the voltage drop across a resistance of 300Ω with a current of 90mA flowing is required, simply place a ruler or straight-edge on 90 on the milliamp scale and 300 on the resistance scale and read off the result on the voltage scale, i.e. 27V. Similarly, knowing that the P.D. across a 1½k resistor is 60V, the current passing may be obtained by placing a straight-edge

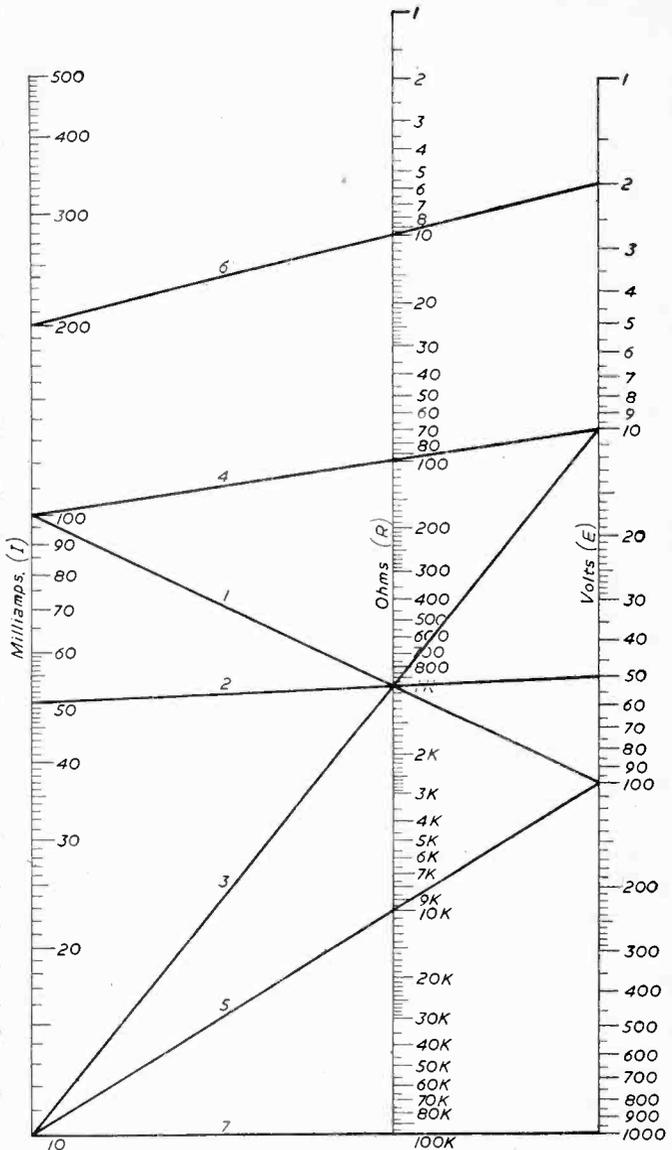


Fig. 2.—An abac for Ohm's Law.

at 60 on the voltage scale, 1.5 on the kilohm scale and reading the result (40mA) on the current scale.


It may be found convenient to mark off the current scale in milliamps on one side and amps on the other as can be seen in Fig. 3. This will save time and avoid errors in converting from one to the other. One further abac will be described employing exactly the same technique as before, since Watts = Volts × Amps, two of the scales have been used in the first abac and it is only necessary to trace them on to another sheet of paper. Notice, however, that this time neither scale is reversed.

Power Scale

To find the position of the power (i.e. Watts) scale, proceed as before by using a constant value of Watts, ten being convenient. Now $100V \times 100mA = 10W$, so draw a line (line 1, Fig. 3) from 100 on the voltage line to 100mA (0.10A) on the current scale and follow this with a line from 200mA to 50V, 250mA to 40V and the intersection of these lines (1, 2 and 3, Fig. 3) fixes the position of the wattage scale. Draw a vertical line through this and draw lines 4, 5 and 6 (Fig. 3) which intersect the scale at 1, 0.1 and 100W respectively. As in Fig. 2 it will be seen that the cycles are all of equal length, so that fixing the graduations of one automatically fixes them all. Thus $100mA \times 90V = 9W$, $100mA \times 80V = 8W$, $100mA \times 70V = 7W$, and so on. The lower (decimal) scale of watts may be marked off on the other side as its equivalents in milliwatts, which again will be found rather convenient.

The use of the abac is similar to the previous one: providing any two of the three variables are known, the unknown may be found. It may, for instance, be used for calculating resistor ratings, e.g., if a resistor has a P.D. of 80V across it and a current of 0.025A (25mA) is passing through it, what should the minimum rating of the resistor be? Lay a straight-edge across 80 on the voltage scale and 25 on the milliamp scale and read off the answer, 2W on the wattage scale.

Fig. 3.—An abac for power dissipation.

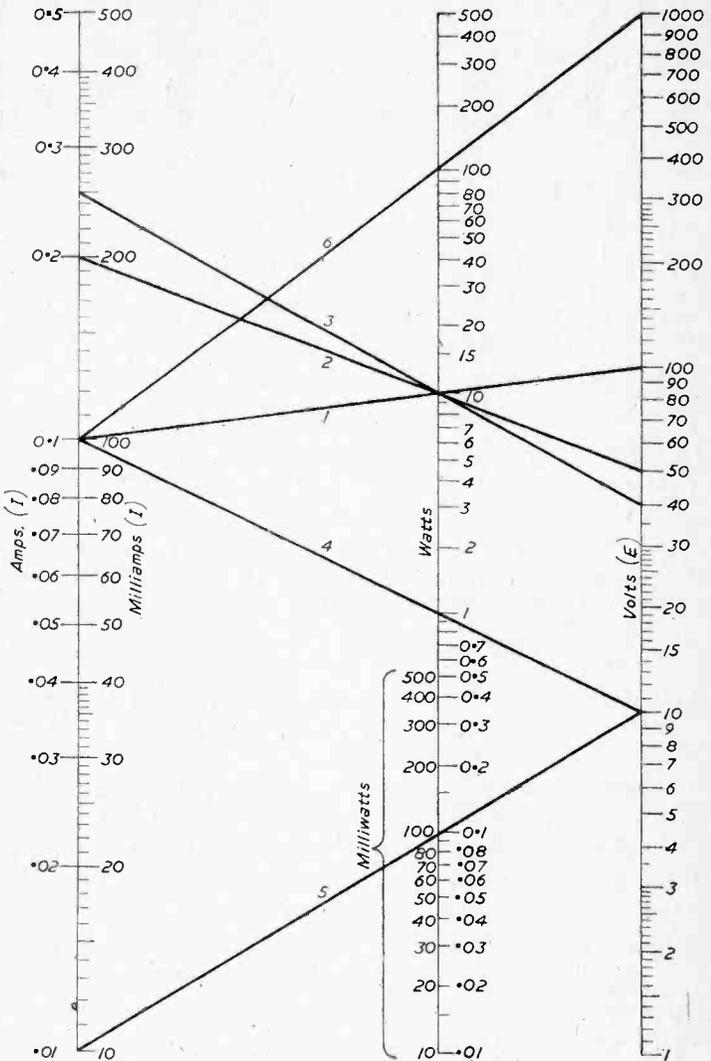

TWO INTO ONE—2

(Continued from page 352)

Further Procedure


It may happen that a fault not covered in this article may develop. All the faults that may occur could not possibly be covered and if you need advice, write in (observing the Query rules). May I advise, however, that it is much better for you to try and locate the fault yourself. By this means you will teach yourself more than many articles can tell you. In making application for assistance, please state as briefly as possible the stage you have reached, and the snag encountered. Do not forget to give the maker's name and the model number of the set.

Should you succeed in making one of these two sets work both on sound and vision, you can now

teach yourself quite a lot as regards faults and their symptoms. Try altering valves of resistors and also capacitors. Make a note of the effect on either vision or sound. Do not expect though, that a certain symptom is always the result of one certain fault. You will find after a short experience, that two or even three different faults will cause apparently the same symptom.

A Final Warning

Please remember the warnings given in Part 1 of this article about the danger of high voltages on a television receiver. Remember that if these receivers are A.C./D.C. the chassis may be alive to the mains voltage. If using screwdrivers, use only those with well insulated handles.

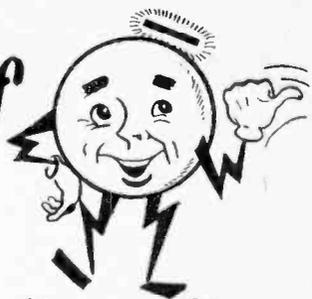LOTS & LOTS of 

TINKERS, TAILORS, *
SOLDIERS, SAILORS,
AIRMEN, APPRENTICES & Ordinary Chaps
like You and Me Are Learning
BASIC ELECTRICITY & BASIC ELECTRONICS
THIS NEW 'PICTURE BOOK' WAY
Why don't you too?

Now available to Civilian Readers, in eleven illustrated Manuals, is this NEW-STYLE Training Course, developed for the U.S. Navy by the New York firm of Management Consultants, VAN VALKENBURGH, NOOGER & NEVILLE, INC., and adapted to British usage by a special team investigating the most modern methods of teaching Electricity and Electronics at Training HQ of the Royal Electrical and Mechanical Engineers.

IT HAS ALREADY BEEN ADOPTED for Training by:—REME—Royal Signals—Technical Training Command, RAF—N.Z. and S. African Air Forces—Army of Pakistan—National Cash Register Co.—Richard Thomas & Baldwins—Uganda Electricity Board—Addressograph-Multigraph—Mullard.

* To be honest, we're not yet 100% sure of either the Tinkers or the Tailors. But there's no shadow of doubt that they all could learn Electricity and Electronics this wonderfully simple "PICTURE-BOOK WAY" if they wanted to!

COUPON - SEND NOW!

To THE TECHNICAL PRESS LTD.
 1 Justice Walk, Lawrence St., London, S.W.3.

Please send me your FREE prospectus, describing 'BASIC ELECTRICITY' and 'BASIC ELECTRONICS'

NAME

ADDRESS

.....

FROM YOUR POINT OF VIEW...

Midland "New Alumina" rebuilt C.R.T.'s, completely rescreened and aluminised offer you the finest value available today! The ever growing demand for these thoroughly reliable tubes is *your* assurance of satisfaction and service.

**Now POPULAR TUBES
at POPULAR PRICES . . .**

more Midland "rebuilt"—the tubes you can trust, at amazingly low cost

All types carry a 12-month guarantee and are available off the shelf NOW. Contact—



MIDLAND Tubes Ltd. 37, GEORGE STREET, MANCHESTER, I.


Telephone: CENTRAL 4568/9

NEW! DO-IT-YOURSELF TRAINING TECHNIQUE in RADIO & ELECTRONICS


You LEARN while you BUILD...

SIMPLE... PRACTICAL... FASCINATING... 1st stage receiver

ANNOUNCING—after many years of highly successful operation in the U.S.A. and in Europe—the latest system in home training in electronics is now introduced by an entirely new British training organisation. **AT LAST**—a comprehensive and simple way of learning —by practical means—the basic principles of radio and electronics, with a minimum of theory. **YOU LEARN BY BUILDING** actual equipment with the components and parts which we send you. You advance by simple steps using high quality equipment and performing a whole series of interesting and instructive experiments. No mathematics! **INSTRUCTION MANUALS** and our teaching staff employ the latest techniques for showing clearly how radio works in a practical and interesting manner. You really have fun whilst learning! And you end by possessing a first rate piece of home equipment with the full knowledge of how it operates and—very important—how to service and maintain it afterwards. A full library of magnificent illustrated textbooks are included with the Courses. **IN FACT** for the 'Do-it-Yourself' enthusiast, the hobbyist, or those wanting help with their radio career training, or to set up their own full or part-time servicing business—then this new and exciting instructional system is exactly what is needed and it can all be provided at very moderate cost. Easy payments available. Post the coupon now, for full details. There is no obligation.

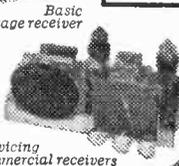

No Mathematics!

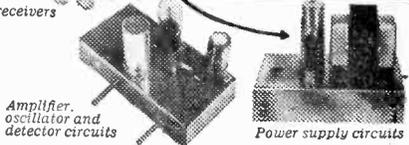

**BUILD YOUR OWN • RADIO EQUIPMENT • TEST GEAR
• HI-FI INSTALLATION—AND LEARN AS YOU DO IT**

RADIOSTRUCTOR

BRITAIN'S LEADING RADIO TRAINING ORGANISATION

**FREE—
POST TODAY**


To: **RADIOSTRUCTOR** (Dept. G40),
40 Russell Street, Reading, Berks.

Please send brochure, without obligation, to:

Name _____
Address _____

**BLOCK
CAPS.
PLEASE**

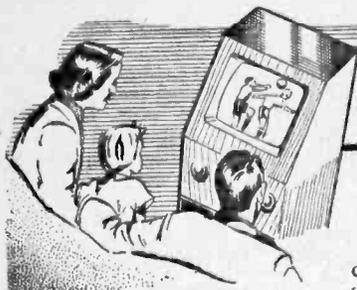(821) We do not employ representatives 4-60



UNDERNEATH THE DIPOLE

A MONTHLY COMMENTARY

By Iconos

"Down-beat" BBC TV?

WHAT has been happening lately to the dignified BBC television service? Why have its standards of good taste been lowered in so many programmes, particularly those of the "interview" type? Who has changed the policy of competition with ITV from a defensive one into an offensive one—in more senses than one? Why have the pleasant slightly pompous and smiling announcers become aggressive, and why have new recruits to the ranks of their interviewers included ill-mannered angry young men who provoke their victims in front of the TV camera and embarrass the viewers sitting in front of their sets? These are queries which have puzzled many viewers lately and have formed a topic of conversation on the 8.20 a.m. train to town. Even Granada's "Under Fire", notorious for the truculence of

chairman and audience, appears anaemic by comparison with the bad manners of the BBC's angry boys. Worse still is the growing "down-beat" flavour of some of the BBC documentary programmes, which seem to be always ready to give maximum prominence to the views and opinions of none-too-friendly nations. In fact, there have been occasions when I have felt that the great Corporation might well have added the prefix "Anti-" to its honoured title.


Sour Grapes

"Panorama" has always been considered to be a first-class piece of television journalism. It is still first-class, but it is no longer high-class. In an effort to become contemporary, provocative and lively, some of its items have become merely sour. Naturally, the lower journalistic standards may attract more viewers, even if it does not please them. There are various degrees of mud-slinging, third degrees and candid

interviews, but none of them are very elevating or constructive.

Ulster and Anglia

I HAVE visited several of the ITA's regional stations, the most recent visits being to the Belfast studios of Ulster Television and the Norwich television centre of Anglia. Belfast studios are a compact and very well devised conversion of factory buildings, with a small stage and an excellently laid out technical area and master control. Cameras in the studio are of the vidicon type, requiring more light than image orthicon cameras, but giving particularly pleasing results on close-ups. By contrast, the network vision pictures looked harsh and contrasty to me, after their long journey up the lines and microwave links from London. Local programmes are still on a modest scale, yet the small stage is very fully utilised and it can't be long before a second stage will be needed. By comparison, Anglia's Norwich studio seemed lavish, with an immense Master Control Room, four flying spot telecines, a three-camera O.B. truck and an elaborate tape operated programme switching and indicating equipment, known as "TOPSIE". Here, like Ulster, the technical equipment has been most efficiently laid out, though everything is naturally on a bigger scale to cope with a much larger local programme schedule. The conversion of the old Agricultural Hall premises into a television centre has been done very well indeed, and no attempt has been made to patch any modern embellishments on to the exterior of this eighty years old building of the Alexandra Palace type of architecture. The interior decor has a dignified modern appearance which blends surprisingly well with the elaborate decorative patterns of the original ironwork supporting the roof. Full marks for all concerned with

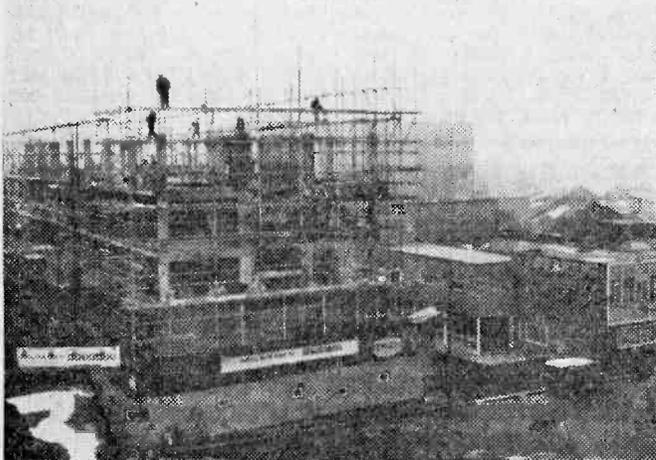

Phase IV of the Granada TV Centre in Manchester (a £460,000 ten-storey office building) is now being built. The new building, which will be linked with the existing television studios, control rooms, technical departments and offices, is expected to take 20 months to complete.

the planning and design of both Ulster and Anglia stations!

Image Orthicons Galore

While in East Anglia, I took the opportunity of visiting the great Marconi works at Chelmsford and was privileged to see some of the latest types of studio cameras and ancillary equipment being tested. Dozens of the new lightweight Mark IV image orthicon TV cameras were coming off the assembly line for delivery in all parts of the world. The English Electric 4½ in. image orthicon camera tube is used in these cameras, which have been found superior to the American 3 in. camera tube, even by the Americans themselves! I was able to see the prototype of a most ingenious automatic slide changing apparatus, part of the latest Marconi vidicon telecine equipment. The sound side of television had not been neglected. There was a most elaborate 18 channel sound mixer with quadrant faders—an ultra-modern version of the BBC's original dramatic control panel. Very great improvements have been made in the sound equipment, including provision of compressor amplifiers, so necessary in these days of "naturalistic" dialogue, throw-away lines and end syllables dropped by the actors. It was disillusioning to think of the degradation sound will subsequently receive on so many modern television receivers, with tiny little loud speakers fitted in the side or the back.

Spot Wobble

THE better the picture at the transmitting end, as seen on high-class monitors, the more conscious one is of the degradation it receives at the receiving end, by maladjustment or by poor design. Unfortunately, it is true to say that probably the most important selling point of a television receiver is the styling of the cabinet. Two or three years ago, one mass-production set manufacturer turned out a fine console set which included spot-wobble, to reduce the visibility of the lines on the picture. This device is no longer available on the same maker's current sets—and I haven't yet found the reason why. It is true that spot-wobble is not always successful in areas where aerials are grouped together on roofs, due to

interference effects. In such circumstances, the resultant picture becomes broken up by a tweedy kind of interference pattern, which disappears when the spot-wobble device is switched off. But where there is no such interference, spot-wobble improves the quality of a picture very considerably. I hope some enterprising makers will revive the use of this worthwhile refinement.

The Church on TV

THERE have been many fine live outside television broadcasts from cathedrals and churches during the last few years, particularly from the BBC. Probably the best and most moving outside broadcast of this type from an ITA contractor was made by Anglia, quite recently, when this regional station taped the solemn ceremony in Norwich Cathedral of the enthronement of Rt. Rev. William Scott Fleming as the 68th Bishop of Norwich. The impressive dignity of the ancient ritual, the wonderful sounds of the choir and the R.A.F. trumpeters and also the interpolated shots of the huge congregation, were skilfully picked up by the Anglia cameras. I saw a replay of the Ampex tape on closed circuit during my recent Norwich visit and was particularly impressed with the quite thrilling and delicate handling by the Anglia producer, Geoff Rimmer. Anglia are particularly well equipped with Ampex, two fixed equipments being set up in the very large master control room. Ampex taping is no longer regarded as an expensive luxury—it has become a "must" for all stations.

Japan has just produced its own video tape recorder, working on an entirely different system—not just the usual Japanese copy. But I have the feeling that the Ampex standards are now so firmly established that there is little likelihood of alternative methods being generally accepted.

Production Grammar

MANY years ago, in the days of the silent films, a primer on film production techniques was written by a film producer, L. C. McBean. Mr. McBean died some years ago. His films are forgotten. The silent film has become a talkie, with colour, cinemascope and all the gimmicks. But though techniques have progressed and changed, the McBean book is still a valuable reference work for all the elements of cinematography, especially of trick photographic work. The equivalent primer for television production has now appeared—"The Grammar of Television Production" by Desmond Davis, a front-rank television director who recently died. This work was sponsored by the Guild of Television Producers and Directors and is profusely illustrated with sketches and diagrams. Like McBean's primer, it is a reference book which should be studied by all producers, directors, lighting men and engineers connected with television. Certain parts of it should even be learnt off by heart, especially the fundamental principles of reaction shots and camera angles. Would-be script writers should keep it always at their bedside, for constant consultation.

PRACTICAL WIRELESS

Chief Contents of April Issue

Now on Sale, 1/6

A QUALITY OCTET
IMPROVING THE 19 SET
A REPETITIVE TIMER
RECORD PLAYER AND CABINET
TRANSISTORISED MORSE PRACTICE OSCILLATOR
TRANSISTORISED SUPER-REGENERATOR
FREQUENCY METER BC 221
MODEL CONTROL CIRCUITS
ETC. ETC. ETC.

TUBES

DIRECT FROM OUR FACTORY. New low prices. New top quality guns. ALL GUARANTEED

Carrriage and Insurance 12/6

CRM92, MW22-7, MW22-14, MW22-14c £2-10
 MW22-17, MW22-18

12KPA, 121K, C12B, CRM121, CRM121A, CRM121B, CRM122, CRM123, MW31-14k, MW31-16, MW31-18, MW31-74

141K, 7901A, C14FM, CRM141, CRM142, CRM143, MW36-24, MW36-44

17ASP4, 171K, AW36/21, C17FM, CRM171, CRM172, MW43-64, MW43-69

7401A, AW43-80, C17BM, C17BM, CRM173, CRM152A, CRM182B, CRM153, CRM178, MW43-80, MW41-1

AW53-80, CRM212, MW53-20, MW53-80

6 MONTHS REVACUUMED £2-10

12 MONTHS REGUNNED £4-10

12 MONTHS NEW TYPES £4-15

MW31/74

MW36/24

MW43/64

£2-15

£4-10

£3-5

£5-5

£3-15

£5-15

£4-5

£6-5

£5-10

£8

£8-10

NEW 108K (Eq. 116) TUBES SPECIAL OFFER: 59/-
 PLEASE NOTE: Many other types not listed available. S.A.E. enquiries

13 CHANNEL TV'S

TABLE MODELS. FAMOUS MAKERS. Complete with all valves and tubes. These sets are unequalled in value due to huge purchase direct from source. They are untested and are not guaranteed to be in working order. Carr. Free.

12" - £3.19.
14" - £7.10.
17" - £12.10.

12" 5 CHANNEL TV'S 55/-

Complete Table Models as Above. Carr. Free.

B.S.R. MONARDECK TAPE DECKS £9.10.0

12in. TV'S 5 channel table models including speaker, line trans., cabinet. Top makes requiring only valves and tube to complete, your choice if available **15/-** (carr. 4/-). Or £28 per dozen, carr. free.

14in. TV'S 5 channel as above **35/-** (carr. 4/-).

100 CONDENSERS 10/-

A must for your spare box. A well-balanced assortment of miniature silver mica and ceramic condensers. 5-10,000 P.P. List value over £5.

100 RESISTORS - assortment **7/6** (-2 watt, -1/2 watt).

W.A. FOCUS MAGNETS

Standard type, focus and centring controls, with mount insulator. 9/6. Dims. latest double magnet type, 12/6. ION TRAPS. 3/6.

CO-AX standard and low loss, 25 yds, 12/6. 50 yds, 22/6. 100 yds., 42/6. Co-ax. Plus 1/3. Wall outlet boxes, 3/6.

VALVES ALL GUARANTEED 3 MONTHS

PL81 SOILED AMAZING 4/6

EY51 SHORT 4/6 U25 SHORT 8/-

B.S.R. UAS AUTOCHANGERS, £8.15.0

TRANSISTORS: RED SPOT 4/6

I.F., L.F. and Output up to 800 kc/s. (48-dozen). WHITE SPOT. R.F. and I.F. 2.5 Mc/s. 6/6 (69/- per dozen). XA103, 15/- XA104, 17/6; XE104, 10/-; GET15, 25/-

DIODES - General purpose, famous make, 9d. 8/- doz. GEX44 type, 9/6.

RECTIFIERS: For Chargers, selenium, 12 volt 3-4 amps. 9/6. (Carr. 1/-) £5 per doz. 260 v. 60 ma. 5/-, RM1, 6/6; RM2, 9/-; RM3, 9/-; RM4, 15/6; RM5, 21/-; 14A86, 17/-; 14A97, 23/-; 14A100, 25/-; 16KX1-15-1, 7/6; 18A1A1, 16-1, 7/6; 18R12-2-3-1, 14/-; 14RA1-2-3-2, 17/-; 14RA1-2-3-3, 20/-.

TURRET TUNERS

3R Ma. I.F. Standard Famous Make with coils listed £7. Complete with PCF80 **45/-** and PC284 valves, boxed (carr. 3/-).

Ditto complete except for 1 oscillator coil, 35/-

EXTERNAL I.T.V. CONVERTERS WITH INTERNAL POWER PACK. Finished to hammered gold. Very compact. Trimming controls. Gain and Trimming controls. Listed £3/10/- at £7.10. Our Price, carr. 2/6. **£3/10/-**

COLLARD CONQUEST CHANGERS £7.10.0

PM SPEAKERS Standard 3 ohms, ex-equipment, top makes, performance guaranteed.

8in. **8/-** 6in. **11/-** 10in. **13/-**
 9 1/2in. 7X4 10X6

TV PROJECTION UNITS

Complete Standard Philips optical units with Mullard MW6-2 projection tube **£3/10/-** (untested) at a fraction of cost.

25 kv. LINE TRANSFORMERS in sealed cans including 3 EY15 valves, standard type for above units, **45/-**

CONNECTING WIRE

25 FT. P.V.C. Insul., excellent (5 coils, diff. colours, 4/6)

CRTS ECR30 (VCH139A), 15/-; 6FP7, 19/-; ECR35 (VCR135), 9/-; VCR97, 12/6.

B9A Ceramic super valveholders, (6/8 doz., 12/- doz.) **8d.**

BBC/ITA for high signal areas **9/6**

Plugs into set, var. attenuator, listed 2/6.

14in. Table cabinets, mask glass **12/6**

VALVES BY RETURN OF POST

10% DISCOUNT SPECIAL OFFER TO PURCHASERS of any SIX VALVES marked in black type (15% in dozen). Post: 1 valve, 6d; 2-11, 1/-.

NEW LOW PRICES GUARANTEED 3 MONTHS


FREE TRANSIT INSURANCE. All valves are new or of fully guaranteed ex-Government or ex-equipment origin. Satisfaction or Money Back Guarantee on goods if returned unused within 14 days.

OZ4	5/6	6AT6	7/-	6K6GT	6/6	7A7	10/6
1A5GT	6/-	6AU6	8/6	6K7	5/9	7B5	12/6
1A7GT	12/6	6B7	3/6	6K7G	2/3	7B6	12/6
1CG1T	11/6	6B9G	3/6	6K7GT	5/-	7B7	7/6
1D5	9/6	6B9A	6/-	6K8	6/-	7C5	7/6
1D6	9/6	6B9E	6/6	6K8GT	11/-	7C6	7/6
1E6GT	9/6	6B9GG	12/6	6K25	7/6	7E7	9/6
1L4	3/6	6B9H	6/6	6L1	13/6	7H7	7/6
1L5	3/6	6B9J	6/-	6L8	9/6	7K7	8/-
1LD5	4/6	6B9K	10/6	6L16G	7/6	7E7	7/6
1N5GT	9/6	6B9W	6/6	6L7	9/-	7S7	9/6
1R5	9/6	6B9W	8/6	6L15	9/-	7V7	9/6
1S4	9/6	6B9X	5/6	6L10	11/6	7X4	7/6
1S5	6/-	6C4	3/6	6L13	3/6	7Z4	7/6
1T4	4/6	6C5	5/6	6L12	7/6	8D3	3/6
2D2	4/6	6C6	4/3	6L12D	8/6	10C1	11/-
3A4	5/6	6C9	9/6	6N7	9/6	10C2	13/6
3A4	7/6	6C9D	18/6	6P1	14/-	10C14	9/-
3A4GT	8/6	6C9E	9/6	6P25	9/-	10C15	6/6
3S4	9/6	6D1	9/6	6P28	9/-	10C19	10/6
3V4	7/6	6D2	3/6	6Q7G	9/6	10L14	8/-
5B4G	11/-	6D3	11/6	6Q7GT	9/6	10L15	8/-
5U4G	5/6	6D6	4/6	6H7G	9/6	10L1D	8/-
5V4G	9/6	6F1	6/6	6SA7	5/9	10P13	9/6
5Y9G	6/6	6F15	5/6	6S7G	4/6	10P14	9/6
5Z4GT	6/6	6F1M	7/6	6SH7	4/6	10P18	8/-
5Y9G	5/6	6F2	3/6	6S7	9/-	12A6	5/3
5Z4GT	11/-	6F13	6/6	6SK7	5/3	12A17	9/6
6A7	11/-	6F14	9/6	6SL7GT	6/6	12A18	9/6
6A8G	9/6	6F15	5/6	6SN7GT	4/6	12B7	7/6
6A8GT	13/6	6F16	6/6	6SQ7	6/3	12A17	6/6
6A8B	8/3	6F13	6/6	6S7	6/6	12A17	6/6
6A7	4/3	6H6	2/-	6U4GT	10/6	12A17	10/6
6A05	4/3	6J3	4/3	6U6G	6/3	12B4	6/6
6A07	3/6	6J5G	2/6	6V3	5/6	12B26	6/6
6A5	6/6	6J5GT	3/6	6V6GT	6/6	12B17	6/6
6A15	3/6	6J6	4/-	6X2	9/-	12C8	6/6
6A16	4/6	6J7	7/6	6X4	4/-	12E1	12/6
6A15	3/6	6J7G	5/3	6X5G	5/6	12J5GT	3/6
6A05	6/-	6J7GT	7/6	6X5GT	6/6	12K7GT	6/6

10E	12K8GT12	50D08G16	DF91	4/6	EC022	6/6	EM34	8/6	EN108	18/-	T41	7/6	UCB91	9/6
12E	12Q7GT	6/-	50L07T	9/6	DF96	5/3	EC053	7/6	EM30	9/6	N3D2	16/6	UCB30C	12/6
12E	12R0GT	6/-	50L07	6/6	DF97	5/3	EC054	8/6	EM81	8/6	U11	8/6	UC183	13/6
7/6	12S17	5/6	54K4	4/6	DF178	6/-	EC055	8/6	EM94	9/6	P81	2/3	UF41	8/6
7/6	12S27	5/6	5818PT	11/-	DH77	7/-	EC080	10/3	EM95	10/6	PAB	2/3	UF42	7/6
7/6	12S7GT	6/6	75	8/-	DK32	12/6	EC082	9/6	EN31	16/-	PC084	7/6	UF80	9/6
9/6	13A74	9/6	77	6/6	DK91	9/6	EC021	14/-	EY11	9/6	PC085	5/6	UF85	9/6
7/6	13A75	14/9	78	7/6	DK92	8/6	EC035	7/6	EA11	9/-	PC088	19/-	UF86	12/-
6/6	13A76	7/6	80	6/6	DK96	8/3	EC042	9/6	EY35	9/6	PC089	13/6	UF89	7/6
8/6	13A77	8/6	83	9/6	DL33	8/6	EC081	8/3	EB96	8/6	PCF80	7/6	UF91	7/6
4/6	13A78	9/6	90AV	4/6	DL35	11/6	EC080	8/3	EZ40	7/6	PCF82	9/6	UL44	12/6
8/6	13A79	8/6	11727	10/6	DL82	9/6	EC082	10/-	EZ41	7/6	PC085	9/6	UL48	9/6
16/-	13A80	9/6	1852BT	16/-	DL93	8/6	EC083	14/6	EZ80	6/9	PC083	11/6	UL45	8/-
3/-	13A81	11/6	23A	3/-	DL92	8/6	EP82	12/-	EZ81	7/6	PC084	9/6	UL80	6/6
5/-	13A82	12/6	807A	5/-	DL94	7/6	EP86	3/3	GT1C	7/6	PC085	4/6	UL82	12/6
3/6	13A83	9/6	1307E	3/6	DL96	8/3	EP89	4/3	GZ22	8/6	PC085	7/6	UL84	12/6
15/-	EA50	9/6	EA50	15/-	EA50	9/6	EP40	13/6	GZ34	12/6	PC086	5/3	UL88	18/6
7/6	EA51	8/6	EA52	7/6	EA51	8/6	EP41	8/6	GZ35	10/6	PC083	9/6	UL91	11/-
10/-	EA53	10/6	EA54	10/-	EA53	10/6	EP42	7/6	HA0C0	9/6	PC086	12/6	UL92	11/6
10/-	EA54	10/6	EA55	10/-	EA54	10/6	EP43	8/6	HA0C1	9/6	PC086	12/6	UL93	11/6
10/-	EA55	10/6	EA56	10/-	EA55	10/6	EP44	8/6	HA0C2	9/6	PC086	12/6	UL94	11/6
10/-	EA56	10/6	EA57	10/-	EA56	10/6	EP45	8/6	HA0C3	9/6	PC086	12/6	UL95	11/6
10/-	EA57	10/6	EA58	10/-	EA57	10/6	EP46	8/6	HA0C4	9/6	PC086	12/6	UL96	11/6
10/-	EA58	10/6	EA59	10/-	EA58	10/6	EP47	8/6	HA0C5	9/6	PC086	12/6	UL97	11/6
10/-	EA59	10/6	EA60	10/-	EA59	10/6	EP48	8/6	HA0C6	9/6	PC086	12/6	UL98	11/6
10/-	EA60	10/6	EA61	10/-	EA60	10/6	EP49	8/6	HA0C7	9/6	PC086	12/6	UL99	11/6
10/-	EA61	10/6	EA62	10/-	EA61	10/6	EP50	8/6	HA0C8	9/6	PC086	12/6	UL100	11/6
10/-	EA62	10/6	EA63	10/-	EA62	10/6	EP51	8/6	HA0C9	9/6	PC086	12/6	UL101	11/6
10/-	EA63	10/6	EA64	10/-	EA63	10/6	EP52	8/6	HA0C10	9/6	PC086	12/6	UL102	11/6
10/-	EA64	10/6	EA65	10/-	EA64	10/6	EP53	8/6	HA0C11	9/6	PC086	12/6	UL103	11/6
10/-	EA65	10/6	EA66	10/-	EA65	10/6	EP54	8/6	HA0C12	9/6	PC086	12/6	UL104	11/6
10/-	EA66	10/6	EA67	10/-	EA66	10/6	EP55	8/6	HA0C13	9/6	PC086	12/6	UL105	11/6
10/-	EA67	10/6	EA68	10/-	EA67	10/6	EP56	8/6	HA0C14	9/6	PC086	12/6	UL106	11/6
10/-	EA68	10/6	EA69	10/-	EA68	10/6	EP57	8/6	HA0C15	9/6	PC086	12/6	UL107	11/6
10/-	EA69	10/6	EA70	10/-	EA69	10/6	EP58	8/6	HA0C16	9/6	PC086	12/6	UL108	11/6
10/-	EA70	10/6	EA71	10/-	EA70	10/6	EP59	8/6	HA0C17	9/6	PC086	12/6	UL109	11/6
10/-	EA71	10/6	EA72	10/-	EA71	10/6	EP60	8/6	HA0C18	9/6	PC086	12/6	UL110	11/6
10/-	EA72	10/6	EA73	10/-	EA72	10/6	EP61	8/6	HA0C19	9/6	PC086	12/6	UL111	11/6
10/-	EA73	10/6	EA74	10/-	EA73	10/6	EP62	8/6	HA0C20	9/6	PC086	12/6	UL112	11/6
10/-	EA74	10/6	EA75	10/-	EA74	10/6	EP63	8/6	HA0C21	9/6	PC086	12/6	UL113	11/6
10/-	EA75	10/6	EA76	10/-	EA75	10/6	EP64	8/6	HA0C22	9/6	PC086	12/6	UL114	11/6
10/-	EA76	10/												

Multi-Purpose VALVE FILAMENT TESTER

Model VT41

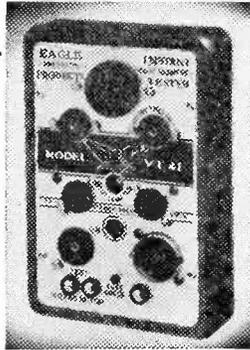

- Pocket size
- Battery operated

GIVES INSTANT CHECK OF:

- ★ All TV and Radio Valves and Fuses.
- ★ All pilot lamps.
- ★ Circuit Continuity.
- ★ Built-in 7 and 9 pin valve straighteners.
- ★ Built-in Battery Test.

Finished in black hammer case with gold front panel. Complete with internal batteries and ready for use.

With this revolutionary instrument you can test all current Valves, Fuses, Continuity and other radio parts. All components tested are shown "good" or "faulty" on panel indicator.

30/-


P. & P. 2/6.

From your local dealer or if in difficulty order direct:

EAGLE PRODUCTS (Dept. P.T.1)
EAGLE WORKS, COPTIC ST., LONDON, W.C.1.

TV TUBES

Completely Remanufactured as new

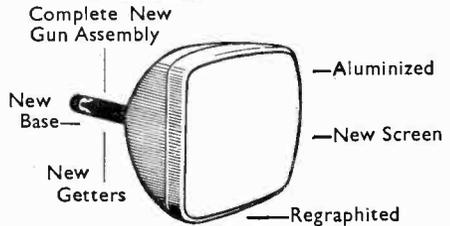

COMPLETELY NEW TUBES EXCEPT THE GLASS

ALL MAKES AND TYPES FROM STOCK
12" £5 19 0
14" £6 10 0
15"-17" £6 19 0

12 months NEW tube guarantee.
C.W.O. or C.O.D. Carr. & Ins. 10/- (passenger)
20/- refunded on your old tube when returned in our container.

The Finest Tubes. The Fastest Service

LAWSON TUBES
156 PICKERSLEIGH ROAD, MALVERN WORCS. MAL 3798

VALVES

SAME DAY SERVICE

NEW! TESTED! GUARANTEED!

SETS

1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DK92, DL92, DL94, any 4 for 23/6
DAF96, DF96, DK96, DL96
6K7G, 6K8G, 6Q7G, 6V6G, 6X5G, or 5Y3G 4 for 30/-
.. .. . 5 for 27/-

1A7GT 12/-	6L1 15/-	25Z4G 8/6	EBC41 8/6	EY86 8/3	P230 17/-
1D5 9/6	6L18 12/3	25Z6GT 8/6	EBP80 8/6	EZ40 6/9	SP61 3/6
1HSGT 10/-	6P25 9/-	30C1 8/6	EBP83 8/6	EZ41 7/6	T41 15/6
1N3GT 10/-	6Q7G 6/9	30L1 8/-	EBL21 20/6	EZ80 6/3	U25 15/6
1R5 6/9	6Q7GT 9/8	35L6GT 10/-	ECC92 11/-	EZ81 7/-	U26 12/-
1S4 9/-	6SL7GT 6/3	35Z4GT 6/-	ECC81 5/9	FW4/500 8/-	U50 7/6
1S5 5/9	6SN7GT 4/9	35Z5GT 8/6	ECC82 6/9	GZ32 8/-	U76 8/-
1T4 4/9	6U4GT 11/-	39 4/6	ECC83 7/-	KT33C 7/-	U78 6/-
1U5 6/6	6V6G 5/-	50CD6G 26/9	ECC84 8/9	KT41 14/6	UAPC80 7/9
3A5 10/6	6V6GT 6/6	50L6GT 8/6	ECC85 8/3	KT61 10/-	UAF42 9/6
3Q4 8/6	6X4 5/-	AZ31 9/6	ECP80 10/-	KT63 6/6	UBC41 7/9
3S4 9/9	6X5GT 5/6	B36 8/6	ECP82 10/-	KT71 8/6	UBF80 9/6
3V4 7/6	7B7 7/6	CL33 13/-	ECH21 20/6	MH4 6/-	UBF89 8/6
5U4G 5/3	7C5 7/6	DAC30 10/-	ECH35 6/9	MU14 8/-	UBL21 20/6
5V4G 9/6	7C6 7/6	DAF91 5/9	ECH42 6/9	MX40 12/6	UCC34 12/9
5Y3GT 6/9	7H7 7/6	DAF96 8/3	ECH81 8/6	N18 8/6	UCB5 8/-
5K9G 9/6	7S7 9/9	DCC90 10/8	ECL80 8/6	PCC94 8/-	UCF80 14/-
6AL5 3/9	7Y4 7/-	DF93 10/-	ECL82 10/6	PC99 12/6	UCH21 20/6
6AM5 5/-	10C1 14/6	DF91 4/9	EP39 4/6	PCF80 8/-	UCH22 9/-
6AM6 3/6	10C2 17/6	DF96 8/3	EP41 8/9	PCF82 9/3	UCH81 8/6
6AQ3 6/-	10F1 15/6	DH76 6/6	EP42 11/6	PCL82 9/3	UCL82 11/6
6AT8 7/3	12A8H 10/6	DH77 7/3	EP80 6/6	PCL83 11/9	UCL83 13/-
6BA6 6/6	12AT7 5/9	DK32 12/-	EP85 6/9	PCL84 8/-	UP41 8/6
6BE6 6/-	12AU6 7/6	DK40 14/-	EP86 10/6	PENA4 11/-	UP42 8/6
6BH6 5/9	12AU7 6/6	DK91 6/9	EP89 8/6	PEN36C 9/6	UP48 7/6
6B36 5/9	12AX7 7/6	DK92 8/6	EP91 3/6	PEN45 8/-	UL41 8/-
6BR7 10/-	12BA6 9/-	DK96 8/3	EP92 4/6	PEN46 5/6	UL84 8/-
6BW6 10/-	12K7GT 5/6	DL33 9/-	ECL82 10/6	PL36 11/9	UP41 8/-
6BW7 6/6	12K8GT 11/6	DL35 10/6	ECL82 10/6	PL38 11/9	UY21 14/-
6CD6G 22/6	12Q7GT 5/6	DL37 6/9	EL41 9/-	PL81 9/6	UY41 6/6
6F1 14/8	12Z3 7/6	DL94 7/6	EL42 10/6	PL82 7/6	UY45 6/9
6FG 6/6	14S7 16/9	DI36 8/3	EL84 7/-	PL83 8/-	VP48 9/6
6F13 12/6	18AQ5 7/-	EACB90 7/-	EM34 6/6	PY32 12/-	VP41 6/-
6F14 17/6	20F2 17/6	EAC91 4/6	EM80 9/-	PY80 7/6	W76 6/6
6K7G 3/9	20L1 17/6	EAF42 8/6	EM81 9/-	PY81 6/9	W77 4/6
6KTGT 6/-	25A8G 11/-	EB91 3/9	EM84 10/4	PY82 7/-	X76M 11/6
6K8G 6/9	25L6GT 9/-	EBC33 5/9	EY81 9/-	PY83 7/9	Z77 3/6

JUST PUBLISHED

USING AN OSCILLOSCOPE

By D. W. Easterling

- 6/6 Postage 6d.
- TELEVISION SERVICING Vol. 4. (Practical Servicing and Fault Finding.) By G. N. Patchett. 7/6. Postage 6d.
- TELEVISION ENGINEERS' POCKET BOOK. By J. P. Hawker. 12/6. Postage 8d.
- SHORT WAVE RECEIVERS FOR THE BEGINNER. A Data Pub 6/-, Postage 6d.
- MODEL RADIO-CONTROL. By E. L. Safford. 21/-, Postage 1/-.
- A BEGINNER'S GUIDE TO TELEVISION. By F. J. Camm. 7/6. Postage 6d.
- THE HOME ELECTRICIAN. By F. J. Camm. 12/6. Postage 8d.
- GUIDE TO BROADCASTING STATIONS. Compiled by "WWV". 3/6. Postage 6d.
- BRIMAR VALVE AND TELETYPE MANUAL. No. 8. 6/-, Postage 1/-.
- RADIO VALVE DATA. Compiled by "WWV". 6th Ed. 5/-. Postage 9d.
- NEW 1960 CATALOGUE. 1/-.

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS of British and American Technical Books
19-23 PRAED STREET, LONDON, W.2.
Phone: PADdington 4185.
Open 6 days 9-6 p.m.

READERS RADIO

24, COLBERG PLACE, STAMFORD HILL, LONDON, N.16. STA. 4587

Post 6d. per valve extra.
Any Parcel Insured Against Damage in Transit 6d. extra.
Any C.O.D. Parcel 2/6 extra.

Letters to the Editor

The Editor does not necessarily agree with the opinions expressed by his correspondents.

SPECIAL NOTE: Will readers please note that we are unable to supply Service Sheets or Circuits of ex-Government apparatus, or of proprietary makes of commercial receivers. We regret that we are also unable to publish letters from readers seeking a source of supply of such apparatus.

TRENDS IN TV DESIGN

SIR.—There is one point I should like to make about a recent article and a letter in reply published in the December issue. Whilst it is true that the controls may be dispensed with—a fact which would probably lead to better reception and fewer trips to the serviceman—certain items are essential for ideal reception. Granted that if these are provided the customer will try and find a better setting, but why not fit them underneath the chassis, say, mounted on brackets or a strip of insulating material. All such variables should, in my opinion, be so placed, and then the serviceman could find the best setting, by using a proper television servicing instrument, and the customer could not get at them without taking the chassis out of the case, and I think this would be a suitable deterrent.—H. R. MALIN (S.E.1).

625 LINE DEFINITION

SIR.—I am fully sympathetic with Mr. Jenkins in his problem set out in the January issue. I, too, want to experiment and try and find an arrangement which I can adopt when (and if) the new definition starts up. Unfortunately, there are no transmissions on which one can experiment. I believe Band IV and V transmissions have taken place, which gave some an opportunity of trying out tuners, but why cannot the BBC or ITV give us some high definition pictures on the vacant Saturday morning period? I think that if the BBC can spare the transmitter for stereo experiments, they must surely be able to spare it for high definition transmissions which I think are very much more important, as stereo may come eventually but will not use two transmitters.—F. L. KERRISON (Ramsgate).

SYNC SEPARATION

SIR.—I recently had a fault which caused much comment and hours of fault finding, but which eventually turned out to be a simple matter to cure. I would like to pass on the hint in case other readers may be similarly placed. The trouble was poor frame hold. Line seemed to lock perfectly, but the frame would periodically slip, sometimes locking with a bar across the centre of the picture. The power supply was provided with improved smoothing, and everything was checked, even to the extent of replacing the valves and components in the clipper and oscillator stages, but still the trouble persisted. One night, whilst adjusting the

signal strength I noted that a reduction of signal caused the slip, but at the strongest position, the hold was best. This made me think that the sync separator might be at fault, and this was checked. To cut a long story short, it was finally found that the grid leak from the sync separator to earth was open-circuited. The wire end was detached inside the moulded component and could be pulled without coming adrift, but enabled the resistor to be rotated about the wire. Replacement of this cured the trouble.—R. MURRAY (Belfast).

CRITICAL LINE LOCK

SIR.—In "Your Problems Solved" in the February issue a reader described the fault of critical line hold with a shift to the right in a Cossor 946. Having cured this fault in a set recently I am in a position to give advice. If, after replacing the 12AU7, and the 6AB8, there is no cure I suggest the replacement of C47 which has a value of 0.002 μ F. This is a cathode bypass capacitor of the 12AU7 line multivibrator. In my particular set this capacitor varied with the temperature and caused lateral picture shift.—S. WITTON (Buckingham).

AN ACORN VALVE TV BOOSTER


SIR.—In your January issue you gave a constructional article on the above and in the list of parts there is a small slip. There are three condensers used in this and they are all 0.01 μ F, but not 25VW as given. They should, of course, be 250VW.—F. TREEBY (Eastbourne).

LENGTHENING TUBE LIFE

SIR.—I was recently given, in all good faith, a "tip" which may eventually reach other viewers. I was told that by turning round my tube at monthly intervals, the scanning would come at a different place on the screen, and thereby give prolonged life to the tube. Surely, this is a fallacy. It might prevent a residual spot from appearing always in the same place and thus prevent a burn, but with modern tubes provided with an ion trap, I fail to see how rotation of the tube can have any effects whatsoever. It will, of course necessitate readjusting the scanning coil unit, and any magnets fitted to the tube.—K. L. PEARSON (Tiverton).

TV SCOPE

SIR.—I believe I have read somewhere that it is possible to use a television receiver as an oscilloscope. The idea is that the timebases are altered slightly and the modulation of the signal is removed, with the result that one can obtain a series of waveforms on the tube, not only of the signal with and without sync but also of the response curves of the tuned circuits. If this is practicable, I wonder if any reader can provide the necessary data.—E. W. GIRLING (Portsmouth).

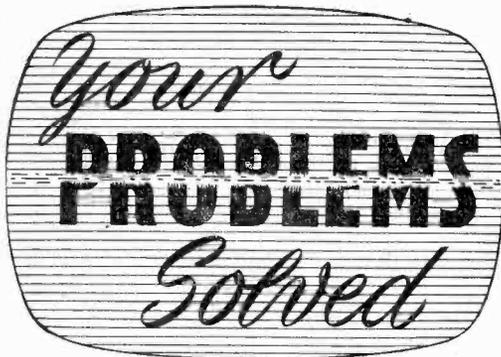

Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying surplus equipment. We cannot supply alternative details for constructional articles which appear in these pages. WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE. The coupon from p. 380 must be attached to all queries, and if a postal reply is required a stamped and addressed envelope must be enclosed.

FERGUSON 992

This set has been converted to ITA with the makers' own converter type "A". The EBC is perfect but I cannot get sound or vision on ITA. When a probe is placed on L2 of the converter heavy 'mush' results on sound and vision. There is no response whatever when tuning pedals are pressed. All valves have been checked by substitution. The gain control is in order but valve voltages are not stated on the service sheet. Is it possible that the oscillator is not working? When the switch on the converter is turned, usual loud clicks and flashes on the screen are evident.—F. Johnson (London S.W.6).

It would appear that the oscillator stage is not working although a defective aerial or aerial plug could give rise to similar symptoms. We mention this since the probe at L2 does promote "mush." The suspects are the 8.2k triode anode feed receiver, its 800pF decoupling capacitor and the grid components. Upon inspection it may be found that the 8.2k resistor is overheating owing to the capacitor having developed a short circuit.

PHILLIPS MODEL 1115U:15

I cannot receive either vision or sound. Could you please tell me where to look? The tube shows a raster.—E. Mitchell (Ripon).

The fault will be located on the front of the right side R.F. chassis. Check first the two EF80 valves on the front left side of this chassis and the components associated with them. See that the coil cans are properly fitted.

ENGLISH ELECTRIC TV63 3360M

I get a fairly good picture on this receiver, but only about three-quarter size. If I try to get it larger it goes out of focus. I have renewed the SU25 and the 185 BTA in the cage. I am unable to get a service sheet to help me to check H.T. voltages. If you can suggest the parts most likely at fault will you please state their positions in the set. Another thing that may have some bearing

on the fault is I get a light flick on the screen about 6in. from the top every few seconds—something like car interference, but much too slow for that.—W. Ayre (Kettering).

You should replace the metal rectifier situated in the centre of the lower pack chassis. Check the 185BT frame output valve on the front left side.

MURPHY V216C

There are striations on the left hand side of the picture; line output valve (20P4) appears to be glowing blue and the cathode is glowing red. I would be grateful if you could tell me if the CRM153 tube has an equivalent or if it could be replaced by any other make. If so, what modifications would be necessary.—S. Bryant (Weybridge, Surrey).

Although the striations are often due to a faulty 20P4 they may also be caused by a faulty 4.7k resistor which is wired across one half of the width control and is located on the adjacent tagstrip. There is no direct equivalent for the CRM153.

ULTRA VT917

The trouble began with a short between chassis and voltage adjustment. It blew the fuses and I have not been able to obtain EHT since. I have replaced U25, and all valves light up except U25. Sound is OK. Could you tell me the damage and what extent has been caused, and how to put this right.—G. K. Southwick (Brierley Hill, Staffs).

There is no reason why a short from the voltage adjustment to chassis should cause a loss of EHT. You must assume that this is a separate fault. First check the H.T. from the U801. If low, check U801 and its surge resistors, 100 ohms each. If the H.T. is in order check 20P4 and U329 valves on right side and all associated components. Check voltages: 20P4—pin 4, 125V, pin 8 10V, boosted H.T. 450V.

DEFIANT TR1252:TA

The tube is soft, and I am going to replace it with a new one, but could you tell me if it will take a larger tube? Will it take a turret tuner, or will it need one that runs off the mains, for converting to ITA Channel 8 and BBC Channel 5?—R. E. Perrett (Peterlee).

Although the CRM152a 15in. is strictly speaking a wide-angle tube, the deflection angle is only 67 deg., and the existing scanning circuits should be able to fill it. A duodecal base is required. A turret tuner can be used and the Cyldon U10L or Brayhead 10s (with "U" series valves) is recommended.

FERRANTI 14T3

The first problem is serious overheating of the line output valve PL81, which becomes almost red hot after a few minutes. When I remove anode cap of either PL81 or PY81 it cools immediately to normal. The EHT transformer had short to heater winding of EY51, but otherwise no faults, but I have ordered a new one.

Could you give me wiring details for transformer, also which one of two leads on the transformer tag board should go to PL81 and PY81? There is also a frame fault, causing fold-over at bottom and loss of height; height control is at limit.—G. Callin (Stirlingshire, Scotland).

NEW! TAYLORMETER Model 127A

20,000 o.p.v. POCKET SIZE!

Performance equal to a high priced instrument
OUTSTANDING FEATURES:

- ★ Sensitivity 20,000 o.p.v. D.C. 1,000 o.p.v. A.C.
- ★ 20 Ranges.
- ★ D.C. Current 50 μ A, to 1 Amp.
- ★ D.C. Volts 0.3 v. to 1,000 v. (25 kV by probe).
- ★ A.C. Volts 10 v. to 1,000 v.
- ★ 3 Resistance Ranges from 0-20 megohms (self-contained).
- ★ Meter 40 μ A 3 $\frac{1}{2}$ " arc.
- ★ Accuracy D.C. 3%, A.C. 4%.
- ★ Dimensions 5 $\frac{3}{4}$ " x 3 $\frac{3}{4}$ " x 1 $\frac{1}{4}$ ".

Price: £10.0.0


Credit Sale Terms available
 9 monthly instalments of
 £1.4.4d.

Complete with Instruction Manual
 and interchangeable test
 prods and clips.
 High quality leather case, if required,
 H.V. Probe for 25 kV £4.15.0.

Write for full details
 and catalogue.

**TAYLOR ELECTRICAL
 INSTRUMENTS LIMITED**

MONTROSE AVENUE, SLOUGH, BUCKS.

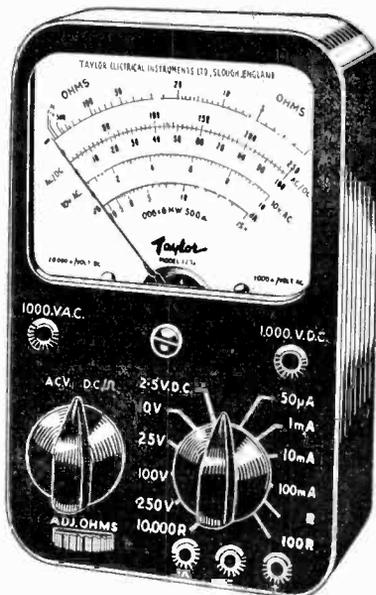

Telephone: Slough 21381

Cables: Taylins, Slough.



Unrepeatable Offer

**COSSOR 10" TUBE
 108K — BRAND NEW**

EQUIVALENT H.M.V. 3/16

Twelve months guarantee

NOT A RE-GUN

— we have a few only

2!/- each


Plus 12/6 Post, Packing & Insurance

**HARVERSON SURPLUS
 LIMITED**

48 Beddington Lane
CROYDON, SURREY

THOrnton Heath 2577

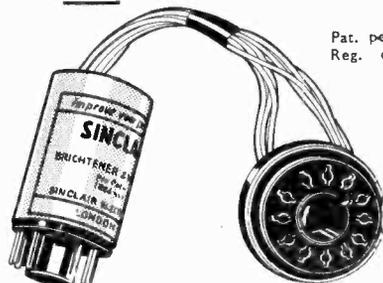**Is YOUR TV TUBE DIMMING?
 YOU CAN EXTEND THE LIFE OF THAT
 TUBE AND IMPROVE THE PICTURE**



Pat. pending.
 Reg. design.

PRICE **30!/-**

Package & Postage 2/6
 (Postal Orders.
 C.W.O. C.O.D.)

- NO SOLDERING
- NO WIRING
- JUST PLUG IN
- IT'S AUTOMATIC
- IT'S GUARANTEED!

One of the most common TV Tube faults is low emission, resulting in loss of brightness, contrast, definition and focus. The Sinclair Unit restores the cathode emission and corrects the above faults for a very low cost. Applicable to all sets operating off A.C. mains.
IMPORTANT. State make and model No. of set and tube in block capitals, please. If not satisfied money refunded if returned within 7 days.

SINCLAIR ELECTRONICS
 33 BERWICK STREET, LONDON, W.1.

Phone: REGent 5520

New TV Tubes

RESCREENED NEW GUN C.R.T.S.
EXACT PLUG-IN REPLACEMENTS
CATHODES TRIPLE COATED
LATEST SILVER SCREEN FOR
BRILLIANCE

LARGE GETTERS FOR HIGH VACUUM
FULLY GUARANTEED 12 MONTHS

We can supply replacements for—

Mullard, Mazda, Cathodeon, G.E.C., English
Electric, Emiseone, Emitron.

12", 14"—£6/15/0

15", 16", 17"—£7

21", 24"—Extra

Carriage Free,

Trade Discount, 20 Weeks' Credit available,

Express Electronics

281 PARLIAMENTARY RD., GLASGOW, C.4

Telephone: BEL 4569 BRI 7296

VIDIO 'REBUILDS' COST LESS—BECAUSE THEY'RE BETTER!

TOP QUALITY
and **NEW GUN UNITS**

'NEW ALUMINIA'— a special service

Right up to Vidio-high standards,
all types of re-screened and
aluminised tubes are available now—
immediate free delivery.

ALL TUBES
GUARANTEED FOR ONE YEAR

Get full details NOW from

VIDIO

Replacements Ltd.

HALES STREET
DEPTFORD HIGH STREET
LONDON, S.E.8

Tel.: TID 4506



FIRST-CLASS TELEVISION and RADIO COURSES . . .

GET A CERTIFICATE!

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure your professional qualification or learn Servicing and Theory. Let us show you how!

FREE GUIDE

The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success compelling qualifications as A.M.Brit.I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs' Exams, Gen. Cert. of Educ., London, B.Sc. (Eng.), A. M. I. P. E., A. M. I. Mech. E., Draughtsmanship (all branches), etc., together with particulars of our remarkable Guarantee of SUCCESS OR NO FEE


Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER
150,000 SUCCESSSES

NATIONAL INSTITUTE OF
ENGINEERING
(Dept. 462), 148, HOLBORN,
LONDON, E.C.1.

S. Africa: P.O. Box 8417, Jo'burg.
Australia: P.O. Box 4570, Melbourne.

54 Gns. — '17'

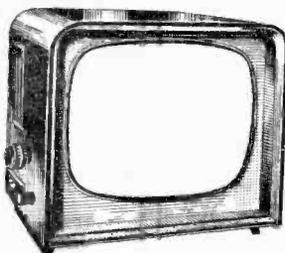

A full specification 17in. Television Receiver to Spencer-West standards now available at your Dealers. Remarkable performance and priced at 54 Gns. only, complete.

For Leaflet apply to:—

SPENCER-WEST LTD.
Quay Works, Great Yarmouth
Norfolk

Phone: Great Yarmouth 4908/9
Grams: Spencer-West, Great Yarmouth

NEW VALVES!

Guaranteed Set Tested
24 HOUR SERVICE

1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91,
DK92, DL92, DL94, SET of 4, 21/6
DAF96, DF96, DK96, DL96, SET of 4, 27/6

1D5	8/-	DL33	8/6	PCL82	8/9
1R5	6/3	DL35	10/6	PCL83	11/6
1S6	4/9	DL92	6/3	PEN41	11/-
1T4	4/-	DL94	7/3	PEN36C	8/6
3S4	6/3	DL96	6/11	PL38	11/6
3V4	7/3	EBC41	7/11	PL38	14/6
5U4G	5/3	EBF90	8/-	PL81	9/-
5Y3GT	6/-	ECC81	5/6	PL82	7/6
SZ4G	9/6	ECC82	6/-	PL83	7/6
6K7G	2/-	ECC83	6/6	PY32	11/-
6K8G	5/6	ECC84	8/3	PY80	7/-
6Q7G	6/3	ECC85	8/-	PY81	6/8
6SL7GT	8/-	ECP80	9/9	PY82	6/8
6EN7GT	4/6	ECH35	8/6	PY83	7/3
6V6G	5/-	ECH42	8/6	U25	11/-
6V6GT	6/6	ECL80	7/9	U26	11/8
6X6GT	5/-	EF41	8/6	U52	5/3
12X7GT	5/6	EF60	8/-	UABC30	7/6
12R8GT	11/6	EF85	9/6	UAF42	9/-
12Q7GT	5/6	EF86	10/3	UBC41	7/9
35L6GT	9/-	EF89	7/6	UBF80	8/6
35Z4GT	5/6	EL41	7/3	UCC84	12/9
AZ31	8/9	EL84	6/9	UC85	7/-
B36	8/8	EY61	8/6	UCF80	14/-
CL33	12/8	EY86	8/-	UCH42	7/9
DAC32	9/9	EZ40	6/9	UCH81	8/-
DAF91	5/6	EZ41	7/6	UCL82	10/6
DAF96	6/11	EZ89	6/3	UCL83	12/6
DF33	9/9	EZ81	7/-	UF41	8/3
DF91	4/6	EZ82	9/-	UF42	7/6
DF96	6/11	KT63	8/6	UF89	7/-
DH77	6/8	MU14	7/9	UL41	7/6
DK32	12/-	PC84	7/6	UL84	7/8
DK91	6/3	PCC89	11/6	UY21	12/6
DK92	8/-	PCF80	7/6	UY85	6/9
DK96	8/11	PCF82	8/6	VP4B	9/6

Postage 6d. per valve extra. Any Parcel Insured Against Damage in Transit 6d. extra. Any C.O.D. Parcel 2/6 extra. Office address, no callers.

GERALD BERNARD
90 CARR MANOR AVENUE,
LEEDS 17

Check 1.8k Ω resistor to pin 8 of the PL81. The heater winding of the EY51 could be hand wound with well-insulated wire, such as coaxial inner.

The L.O.T. should be numbered as follows: 6 to PL81 anode top cap; 5 to PY81 cathode top cap; 3 to scan coils, 0.5 μ F capacitor, 4.7M Ω resistor (to pin 10 of CRT), 15k Ω to 33k Ω (height circuit); 2 to resistors to horizontal holds; 1 to 22k Ω resistor to 4.7k Ω and P181 control grid.

K.B. CONSOLE KF40:F

I bought this TV with an o/c filament in C.R. tube. I had it rebuilt and fitted it myself but picture is very dim. I improved it by altering all the slugs in the coils and managed to get a fairly good picture, but if I turn up the brightness to get a good picture, it expands and the screen goes blank. Also when set for a good picture and a brighter scene is set on screen, the screen goes blank and I have to turn the brightness down again to get a picture. I have to keep on doing this during a programme, and also the focus is not very good.—E. Brookes (Castle Cary, Som).

You should replace the R12 (EHT rectifier) valve which is wired on the top of the line output transformer, which is situated inside the left side screened section.

The R12 (EY51) is soldered into position, and this soldering must be carefully done. No sharp ends or edges of solder must be left and the connecting wires must be kept short and direct.

H.M.V. 1807A

The fault is as follows, most of the time the picture is perfect, but suddenly the picture will go, leaving a blank screen but for a small amount of fluorescent light around the edge of the screen. This light is fluctuating as though it was rolling downwards. If I turn the brightness up, all signs of life leave the screen, and on turning brightness down as far as it will go, bright bands appear which roll downwards. They are quite bright.—J. Redmond (Blackheath, S.E.3).

The fault could be due to a heater-cathode short in the tube or perhaps in the video amplifier 277. It is always, however, good practice to replace the B36 valve, which often gives rise to misleading symptoms.

PHILLIPS PROJECTION TG 1800A:15

The picture has collapsed to a thin line across the screen. I cannot get height by adjusting the height or frame hold controls. What valve or component do you advise checking or replacing in the frame section? I have no service sheet for this receiver.—L. Blackburn (Oldham).

The first component we would advise you to check is the frame blocking oscillator transformer. This is a small black component with four tags, secured by two screws under the rear centre of the chassis. Check the continuity of each pair of tags: normally, one winding will be found open circuited. The thin line should not be observed on the screen unless the protection circuit is inoperative or the frame scanning coils are disconnected or defective. We presume, therefore, you have observed the line on the face of the actual tube.

MARCONIPHONE VT53DA

There are two distinct pictures with a black band down the middle.—F. Ellis (Criccieth, N. Wales).

You should change the B36 valve and check the 330k resistor situated on the small tag panel near the KT36 valve base. This resistor is connected to the horizontal hold control at one end, to the line blocking oscillator transformer at the other. Colours—orange, orange, yellow. You may find a 390k fitted (orange, white, yellow).

MURPHY 12 in. V118

The picture on the above set is good but when switching on with full volume the sound is very faint. After about 10 minutes it gradually becomes louder, it reaches maximum volume, which is quite loud, and then remains. One way to obtain full volume when switching on is to adjust what must be the oscillator screw, which stands proud through the frame on the right hand side of the set when viewed from the back. This unfortunately has the opposite effect because while getting full volume at the start it gradually gets fainter, until after about ten minutes again it is necessary to readjust the oscillator to obtain audible sound.—K. E. Frost (Walton-on-Thames).

Your fault is frequency drift in the local oscillator and we suggest you first try replacing the local oscillator valve, which is the 6F12 nearest to the oscillator tuner, and if not successful proceed to check by substitution the condensers and resistors in the associated circuit.

FERRANTI 17K3

When the picture is set, as I think, correctly there are about 12 vertical white bars through which the picture can be seen down the left-hand side. If I move the width control I can remove these, but then the picture is mis-shapen. Another fault is the top 3in. of the screen are elongated, giving an egg-like appearance to circular objects. I have replaced ECL80, PL81, PY81, but can see no visible improvement in either the height or width faults.—G. Metcalf (Mixenden, Halifax).

You should check the 6.8k resistor across the linearity coil and the 2.7k associated with the width coil. Check the setting of the vertical linearity control, the value of the 2.2M grid leak resistor of the ECL80, and the resistors associated with the linearity control.

PYE V4

For the last two years I have been feeding the heater of the tube, which was weak, or appeared so, with a 6V transformer. There is a fair picture but it is grey or blue, and if I advance the brilliance up too far the picture goes negative. Also if I increase the heater voltage to eight, after ten minutes the picture gradually shows only the whiteness till finally it disappears altogether, but on first giving it 8V it is a fairly good picture. I have to hand a Brimar tube type C14BM. Can I use this instead of the MW36-24? The only difference I can see myself is that the 36-24 is a tetrode and the C14BM a triode, in which case the screen pin would not be in use.—R. A. Demin (Ramsgate).

Two other difficulties that we can foresee are focussing and the ion trap. A triode tube needs a greater focusing field, but since the V4 magnet

is nearly always set at its minimum it should be able to cope. The ion trap will probably end up in the bakelite tube base, where its function will be that of coarse picture positioning.

KB MV100

This set is approximately 3½ years old and has just started to give me trouble. The picture broke up, giving poor linearity. The set now shows a ¼ in. white line across the centre of the screen. I have replaced valves 6BW6 and 12AU7 with no effect, and checked PCCP4 and PFC82, which have been reported OK. The only exception being that the emission on PFC82 is down a bit. — G. Mason (Chesterfield).

You will have to check the 6BW6 valve base voltages, ensuring that H.T. is present at the anode and screen (if absent at anode only, suspect frame output transformer). Check the voltage at the cathode. The H.T. should be about 200V or more, cathode about 15V. Then check 6SN7GT as the blocking oscillator transformer may be o.c., resulting in no voltage being present at the triode anode.

FERGUSON 988T

The above set is for five channels. London, Holme Moss, Kirk O' Shotts, Wenvoe, and Sutton Coldfield. It is in perfect order and I am thinking of using it in the N.E. of England (Pontop Pike). Would I have any difficulty in tuning in the set to that station?—W. T. Elwell (Sutton Coldfield).

There are only three adjustments to make. First unscrew the rotary capacitor in the rear right side square can (only a little), using a plastic tool, until Channel 5 sound is heard. Then adjust the two brass threads on the rear edge for optimum vision and sound. Retrim the oscillator capacitor for optimum sound and freedom from sound and vision. Make no other adjustments.

STRAD 12in. TA1414

I would like some help regarding foldover on my TV set which has a cathode ray tube 14KP4A. The picture is about 2in. in depth with foldover at the top. There is a continuous plopping sound from inside the tube. The valves have been tested and found to be satisfactory. I have changed the height control. The line whistle is audible.—T. Porter (Southport, Lancs).

We would suggest that you check the 6AB8 (ECL80) frame output valve and the capacitors associated with it, including the 100µF 12V cathode decoupler. If the noise described from "inside the tube" could be more accurately described as coming from the scanning coils, the frame coils may well be at fault.

PORTADYNE T237

Can you please oblige me with details on how to set up the above set for service?—A. Moxey (London E.3).

Setting up is quite simple and a rough outline is as follows: Switch on and allow 4-5 minutes to warm up. Advance brilliance with aerial plug removed to show a blank raster. Reduce brilliance just enough to fade this out. Replace aerial plug, set to desired channel and advance volume and set

fine tuner for maximum sound. Advance contrast half-way. Advance sensitivity to show modulation on the screen. Lock with frame hold and line hold. Adjust height and width as required.

ULTRA Y84NF

When switching on the set all I get is a horizontal line across the tube face about ¼ in. wide. The sound is still very good. Please can you help me to locate the trouble.—W. Burrell (King's Lynn, Norfolk).

Check the 6K25 and UL46 on the front right side of the chassis. If these valves are in order, check the wire-wound anode resistor of the UL46. This has a resistance of 3K and no H.T. will reach the anode pin of the UL46 if it is open circuit.

DECCA DM14

After switching on the set a bright, defocused raster appears, unaffected by the brilliance control. After about 10 minutes a normal picture appears. Sometimes after switching on there is a very, very faint picture, but low brilliance. The picture will jump back to normal itself, or by switching the set off and on again. I have replaced the PL81 and H.T. smoothing condenser with no results. When fault is on H.T. is 180 volts, when picture is normal H.T. is 205 volts. The sound is OK all the time. Am I right in thinking C.R. tube is faulty?—R. G. Dunn (Sutton Coldfield).

You describe two distinct faults. One, a bright defocused raster indicates a tube fault, probably a heater-cathode short, which occurs intermittently. The faint picture could be due to a partially shorted heater in the tube, but the fact that the H.T. falls to 180V at the same time seems to point to a different cause, such as variation in the mains supply voltage. Both effects could be due to a defective on-off brilliance control and we would suggest you replace this item first (250KΩ with D.P. switch).

CATHODE FOLLOWER VOLTMETER

(Continued from page 361)

The same process has been carried out for another set of conditions and together with true error curves has been plotted in Fig. 5. The true and approximate curves agree within about ¼V over the effective range on the meter.

These results show incidentally that, providing the H.T. can supply 5mA, this high consumption meter can be used for serious work in conjunction with a cathode follower whereas it would be almost useless when used directly.

When sufficient heater power is available, two in parallel will be advantageous as the effective value of r_a is then halved (but μ is unchanged).

QUERIES COUPON

This coupon is available until APRIL 22nd, 1960, and must accompany all Queries sent in accord with the notice on page 376.

PRACTICAL TELEVISION, APRIL 1960.

LASKY'S RADIO

RECORD VALUE! 12-channel TURRET TUNER

MAKER'S SURPLUS COMPONENT BARGAINS


WIDE ANGLE 38 mm.

Line E.H.T. Trans. Ferroxcube core, 9-18 kv.	19/6
Scanning Coils, Low imp. line and frame.....	19/6
Ferroxcube cored Scanning Coils and Line Output Trans., 10-15 kv., EY51 winding Line Trans. with width and linearity controls, circuit dia., pair...	50/-
Frame Output Transformer	6/6
Frame or line block osc. Transformer	4/6
Focus Magnets Ferroxcube P.M. Focus Magnets, iron Cored	19/6
Duomag Focallisers	22/6
300 m/a Smoothing Chokes	10/6

STANDARD 35 mm.

Line Output Transformers 3.9 kv. E.H.T. and 6.3 v. winding, Ferroxcube.....	17/6
Scanning Coils, Low imp. line and frame.....	7/6
Frame or line blocking oscillator Transformer...	4/6
Frame Output Transformer Focus Magnets :	7/6
Without Vernier	12/6
With Vernier	17/6
200 m/a Smoothing Chokes	7/6

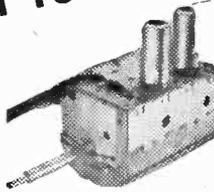Complete with PCC84 and PCF80 valves, I.F. 33-38 Mc/s. Complete with coils for five Band I channels and channels 8, 9, 10, Band III. New and unused.



TO-DAY'S VALUE OVER 47
LASKY'S PRICE 39/6
Post Free

SEND FOR OUR NEW COMPONENTS CATALOGUE

OVER 100 ILLUSTRATED PAGES, SIZE 8 x 5 1/2 in..
Never before has such a comprehensive and useful components catalogue been made available to the home constructor, and our prices will save you pounds!
Price 2/- post 6d.

Our latest 12 page BARGAIN BULLETIN free with every copy, or separately price 6d. post free.

CO-AXIAL CABLE, 80 Ohms Impedance, 9d. per yard. 12 yards or more, 7d. per yard. Post extra.
20,000 VALVES in stock including new and manufacturers' surplus, also imported Valves. Send for our new list and save money. Large stocks of TRANSISTORS.

LASKY'S (HARROW ROAD) LTD.

Open All Day Saturday, Early Closing, Thurs. Mail Orders to Dept. P.T., Edgware Road, 42, TOTENHAM COURT ROAD, W.1. 207, EDGWARE ROAD, LONDON, W.2.
Telephone: MUSUm 2895. PADDington 3271/2.



C.R. TUBES NEW, UNUSED & GUARANTEED

16in. Metal Cone, famous make, Type T901/B. 6 volt, .3 amp. heater, ion trap, 12-14 kv. E.H.T., wide angle, standard 38 mm. neck. LIST £16.
LASKY'S PRICE £6.9.6.
Carr. & Insur. 21/-.
Masks, Anti-Corona, Bases and Ion Traps available.

FERRANTI 9in., T9/3, 4 v. heater, triode, octal base, standard deflection. LIST £9.
LASKY'S PRICE 50/-

FERRANTI 12in., T12/44 and T12/54. LIST £12.
LASKY'S PRICE 84/-
Carr. & Insur. 12/6.

FERRANTI 17in. type TR17/10, 6.3 v., .3 amp. heater.
LASKY'S PRICE £7.19.6
Carr. & Insur. 12/6.

REGUNNED C.R. TUBES	
14 in. £6.10.0	... Carr. 12/6.
17 in. £6.19.6	... Carr. 21/-.
21 in. £7.18.6	... Carr. 25/-.

REGUNNED TV TUBES

Supplied from stock and despatched by British Railways, same day. COMPLETE NEW MULLARD or SUPERIOR ELECTRON GUNS fitted in every tube, and fully guaranteed for 12 MONTHS FROM DATE OF INSTALLATION.

Mullard AW AND MW types available.

	Mullard	Mazda
12 in.	£5.0.0	£5.0.0
14 in.	£5.0.0	£5.0.0
15 in.	—	£6.0.0
17 in.	£6.0.0	£6.0.0
21 in.	£8.0.0	£8.0.0

Carriage 5/- extra.

Other types available; Brimar, E.E., G.E.C. etc.
C.W.O. to:—

CLARKSONS (Tube Distributors)

120 Commercial Road, LEEDS 5
Phone: Leeds 56916

Under the ELECTROVAC process at our fully equipped factory of over 6,000 sq. ft., all tubes are opened, ALL expendable parts removed, a Brand New Electron Gun fitted and a vacuum produced to give a performance and life AS NEW. Progressive picture and vacuum tests over five days ensure the utmost reliability in service. Each tube carries an unconditional **Twelve Months' Guarantee**. The following are prices for the most widely used types, ex stock:

12"	Mullard, Mazda, Ferranti, Emitron Cathodeon, G.E.C., Cossor Types	£6.6.0
14"	" " " " " "	£6.6.0
17"	" " " " " "	£7.7.0
21"	Mullard, Mazda, Ferranti, Cossor and Emitron types	£9.9.0

Plus carriage, packing and insurance 10/-, refundable in full on receipt of old tube in our carton supplied.

Cash with order. Regret no C.O.D.

ELECTROVAC MANUFACTURING CO. LTD
(Dept. P.T.14) Chapel Works, Sunnyside Road, Chesham Bur

HOLIDAY ACCOMMODATION

LOOKING for a lazy holiday? Try RECVLVER LODGE (PT), Bellinge, Kent.

SETS & COMPONENTS

H.M.V. 151N. English Electric 15in., Ultra, etc., Televisions not working, originally £175 each. **£5/10/-**. **TOMLINS.** 127, Brockley Rise, Forest Hill, S.E.23.

TV TUBES. Factory rebuilt. Top quality with brand new gun assembly. 12 months' guarantee. 12 inch. **£5/17/6**; 14, 15, 16, 17 inch. **£6/10/0**. Carriage 12/6. **R. HAINSWORTH** (Dept. C2), 31 Alredale College Mount, Undercliffe, Bradford 3, Yorks.

AERIALS AT TRADE PRICES
For Example **DOUBLE FIVE ARRAY COSTS ONLY 60/-**.
Band III Self-contained Pre-Amplifiers Only **£3.15.0**. Band III Converters, 100/-.
Turret Tuners, 99/-. Complete Rebuilt T.V. Tubes from 25/- Revacuumed ones, All Sizes. **£2.10.0**. All Tubes are Guaranteed.
Super Low-loss Coaxial Cable, 1/1 yd. Standard, 6d., v.l. Splitters, 8/8 each.
S.A.E. FOR FULL LISTS.
G. A. STRANGE, Broadfield, North Wrexall, Nr. Chippenham, Wilts.
Tel.: Marshfield 236.

SELLING UP. Must clear, 17 inch TVs, Test Gear and S. Sheets, Chassis, Cabinets, Components, Valves, Tuners, etc. Your Price Bargains. **A. PHILLIPS,** 8 Fettes House, N.W.8. **PRI 7085.** Evenings, Sundays.

MULLARD TUBES, reclaimed, 6 months' guarantee. 9in., 30/-. 12-14in.. 59/6. 17in.. 79/6. All picture tested. **FITTED FREE.** Picture shown to callers. Other makes, types, cheap. Salvaged spares for modern and obsolete sets. Prices from: **LOT 17/6, LOT 7/6, Occ. Tr. 6/5.** Mains Tr. 10/-. Valves: 1,000 types in stock. **EF91, EB91, 6J5, 2/6, EF80, 10P1, UP42, 3/6.** Save money. Send a S.A.E. with enquiries or for free list. "ST. JOHN'S RADIO," 156 St. John's Hill, S.W.11. (BAT9838).

17 INCH tubes £5. new guns. all sizes available, guaranteed. **STAR TUBES,** Brief Street, Bolton.

RECLAIMED VALVES, tested and perfect. Huge stocks. Any type, price 5/-, plus 6d. postage each; delivery by return. **LEWIS,** 57, Chalford Walk, Woodford Green, Essex.

RENFREW ELECTRONICS
ANDERSON DR., RENFREW
REN 2642

YOUR GUARANTEE TO CHEAPER VIEWING

17" Mazda Tube with new American Gun-mount... **£7/15/-**
14" Mazda Tube with new American Gun-mount... **£6/10/-**
17" Mullard Tube with new American Gun-mount... **£7/15/-**
14" Mullard Tube with new American Gun-mount... **£6/10/-**
One Year's Guarantee. Cash with Order. 7s. 6d. allowed on old tube returned in carton supplied.
Dealers' Inquiries Invited.
Less than 1 per cent. returns.

RATES: 4/- per line or part thereof, average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Television," Tower House, Southampton St., Strand, London, W.C.2.

NEW TUBES

	2 Years' Guarantee	1 Year Guarantee
14 in. Type M.W. ...	£10.10.0	£8. 0.0
17 in. Type M.W. ...	£12. 0.0	£9. 0.0
17 in. Type C.R.M. ...	£13.10.0	£10.0.0
and Equivs. Carriage 5s.		
12 in. NEW 1 year Guarantee tubes ONLY	£5.19.6	

LINE OUTPUT TRANSFORMERS

Direct Replacements for 500 sets. Compare these prices (add 2s. 6d. post):

Pye. LV30, 16T, CS17, etc. ...	50/-
18T, V4, etc., LV21, Luxury 17 ...	60/-
Cossor. 930, 931, 933, 934, etc. ...	60/-
Baird. T29, T163 ...	53/-
T164, T167, T172, 2014, 1712 ...	60/-
Ferguson. 990T to 997T; 103T to 145T, 203T to 246T ...	66/6
Ekco. TS46; TS113-114; T161, 164; T222, 231; TSC311, etc., etc. ...	55/-
Invicta. T108 to T110 ...	52/-
T101 to T104; T114 to T126; T133 to T142 ...	60/-
Bush. TV IIA, B; 12A, B; TVF 12A, TUG 12A, B; TRG12A, B ...	45/-
TV12AM; TV22, 24; TRG24, TUG24 ...	60/-
G.E.C. and H.M.V. mostly 55/- to 60/-	

WESTWAY RADIO

5 Westward Way, Harrow, Middlesex.

TELEVISION TUBES

NEW TV TUBES. TWELVE Months' Guarantee

	£.s.d.
12" MW 31-74 ...	6. 0.0
14" MW 36-24 ...	7. 0.0
17" MW 43-64 ...	8. 0.0
17" MW 43-69 ...	8. 0.0
Carriage ...	10/-

FULLY Rebuilt TV Tubes TWELVE Months' Guarantee

	£.s.d.
12" MW 31-74 CRM 123 ...	5. 0.0
14" MW 36-24 CRM 141 ...	5.10.0
14" AW 36-21 CRM 142 ...	5.15.0
17" MW 43-64 CRM 171 ...	6.10.0
17" MW 43-69 CRM 172 ...	6.15.0
17" MW 43-80 CRM 173 ...	6.15.0
21" MW 53-20 CRM 211 ...	8.15.0
21" MW 53-80 CRM 212 ...	8.15.0
15" CRM 152 CRM 153 ...	6.10.0
Carriage paid	

CATHODE RAY TUBE SERVICE

35 Bromwood Road, St. Paul's Cray, Orpington 21285
Battersea 6859

SETS & COMPONENTS (continued)

TV TUBES

New: M.W. 36-24 **£7/17/6**.
M.W. 43-64 **£8/17/6**.
Re-gunned and re-screened:
14in. Mullard **£6/5/-**.
17in. Mullard **£6/15/-**.
All tubes guaranteed for one year. Carriage and insurance 10/-. Orders despatched by Passenger train.
KIRKGADE RADIO
82 Kirkgate, Huddersfield. Tel.: 9601.

CALLING 9in. Television owners. Brand new, factory fresh, 9in. Ferranti Tubes, originally **£14/10/-**, will replace Mazda, Brimar, G.E.C. etc. **£4/10/-** each, 6 months' guarantee. **TOMLINS.** 127, Brockley Rise, Forest Hill, S.E.23.

VALVES from 1/6. All guaranteed. Radio T/V Components. Lists 3d. **HAMILTON RADIO (T).** 237, Sedlescombe Rd. N., Hastings.

12 INCH TVs, £2/10/-; 9in., £2/5/-, complete. Carr. Paid. **COOPER'S,** 53 Church Road, Birmingham 13.

TV TUBES from stock. 17in. new gun. **£4/15/-**, new gun and rescreened. **£5/15/-**. 12 months' guarantee. **TV ELECTRIC & CYCLE CO.,** 1 High Street, Chalvey, Slough, Bucks. Tel.: Slough 21860.

REBUILT TV TUBES

FULLY GUARANTEED 12 MONTHS
ALL MAKES — 12" to 21"
BLANE & MARTIN ELECTRONICS
SANDOWN LANE
LIVERPOOL

Details on request. Tel. SEF. 3428

BRAYHEAD TURRET TUNERS for any area. Will convert over 600 models. Complete with booklet and fitting instructions. State set and model No. when ordering. Carriage paid. 10 m/c models 95/-, 16 m/c and 35 m/c. 120/-, C.W.O. or C.O.D. **DURHAM SUPPLIES,** 175 Durham Road, Bradford 8, Yorkshire.

TELEVISION TUBES! Rebuilt, new guns, 12 months' guarantee. 12, 14 in., 70/-, 17in., 79/6. Quantity discounts. 3 Park Avenue, New Barnet. **BAR3185.**

T/V SPARES
LARGEST RANGE OF NEW AND USED SPARES

Line Outputs our Speciality. Used from £1. New from 45/-. Also breaking hundreds of TVs for Spares. All Coils, Transformers, Chassis, Valves, etc. No Lists. Send S.A.E. and State Requirements for Immediate Quote.

VALVE KITS. A complete Kit for YOUR set (one of each type) from 50/-. Quote Model Number for exact price.

TV BARGAINS. Reconditioned All-channel Models at New Low Prices. 14inch from 22 gns., 17inch from 29 gns. Fully guaranteed. Terms available.


T.G.S. LTD., 112 Gamberwell Road, S.E.5. Phone **RODney 7917**

SETS & COMPONENTS (continued)

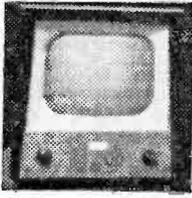C. EDWARDS

1070 HARROW ROAD
LONDON, N.W.10.
LADBROKE 1734

Offers
S/H TV in
First-class
Condition.
12in. £5. 0.0.
14in. £7.10.0.
17in. £15. 0.0.
(all 5 channel)
+15/- carriage.
Guaranteed
tubes, all sizes,
12" 30/6, 14" £3,
17" £4.



in stock: **PYE, FERGUSON, EKCO**
CASH ONLY. 15/- Carriage.
Trade Enquiries Welcome.

AERIAL "GEN" in the January Issue. We have the "pukka" materials. Band III folded dipole, fitted insulator 8/-; elements 1/8 each. post 1/6. Stacked array element kits, July issue, still available, 30/-. S.A.E. price list. **AERIAL SUPPLY**, 165 Beoley Road, Redditch, Worcs.

SALVAGED VALVES

All at 2/6 each

BF91	U31	10F1
DH77	6F1	E36
Z77	6F13	KT330
EB91	6P25	EF50
	6P28	& Many Others

Minimum Order £1. S.A.E. for List. All Valves Tested on Mullard High Speed Valve Tester. C.W.O. to—

ARION TELEVISION, 4 Maxted Rd., S.E.15

T.V. TUBES, factory rebuilt (re-gunned), fully guaranteed, 14in. £4, 17in. £5. p. and p. 10/-. 24, Bristol Rd., Brighton.

LONDON TELEVISION

OFFER THE FOLLOWING BARAINS. RIGIDLY TESTED EX-EQUIPMENT TELEVISION VALVES. Individually Boxed. 3/- to 7/6 each.

WIDE ANGLE SCANNING TELEVISION CHASSIS, Complete less valves. 30/- each. Most makes in stock.

TELEVISION COMPONENTS at Bargain prices. Please write for your individual requirements. Carriage extra.

The undermentioned Televisions for Personal Callers Only.

14in. TELEVISIONS. Working. £40.0 to £8.0.0. 17in. TELEVISIONS. £9.0.0 to £14.0.0. Trade enquiries invited.

4, HENDERSON RD., EASTNEY, PORTSMOUTH.

FOR SALE

VALVE CARTONS at keen prices. Send 1/- for sample and list. J. & A. BOXMAKERS, 75a, Godwin St., Bradford, 1.

SATISFACTION ASSURED. — 12in. Televisions, £9/10/-; 14in. £16; 17in. £19/10/-. Write for quotation, stating requirements. We guarantee satisfaction. TOMLINS, 127, Brockley Rise, Forest Hill, S.E.23.

FOR SALE (continued)

ASTOUNDING VALUE.—9in. Televisions. 45/-; 12in. Televisions. 70/-; 14in. £9/10/-; 15in. £5/10/-; 17in. £14. Complete but not guaranteed working; as received in part exchange. TOMLINS, 127, Brockley Rise, Forest Hill, London, S.E.23. All famous makes available; carriage 7/6.

SERVICE SHEETS; also Current and Obsolete Valves for sale. JOHN GILBERT RADIO, 20, Extension, Shepherds Bush Market, London, W.12. (Phone: SHE 3052.)

MAKING YOUR OWN TELESCOPES. Enlargers, Projectors, Viewers, Microscopes, Episcopes, etc., then our booklets "How to Use Ex-Gov. Lenses and Prisms." Nos. 1 and 2. 2/6 ea. will show you easily and quickly how to achieve the finest possible results at lowest possible cost. The most comprehensive lists of optical and scientific equipment in the British Isles is free for s.a.e. H. W. ENGLISH, Rayleigh Rd., Hutton, Brentwood, Essex.

1,000 TELEVISIONS, all makes, from £3 working, 10/- not. Callers only. 9 till 6, including Sats. 39, Whitehorse Lane, Stepney, London.

100 BAYS of brand new adjustable steel Shelving, 72in. high x 34in. wide x 12in. deep. stove enamelled dark green; sent unassembled, 6-shelf bay, £3/15/-; sample delivery free; quantity discounts. N. C. BROWN LTD., Eagle Steelworks, Heywood, Lancs. (Tel.: 69018.)

TELEVISIONS. 12in., 14in., 17in. and Projections. Require attention, from £3. In working order—12in. BBC from £7. 14in. BBC/ITA with reganned CRT from £18. 17in. from £25. Send for Lists. Carriage Paid.

CADMAN'S

Service Department, Bryan St., Hanley, Stoke-on-Trent.

WANTED

NEW VALVES WANTED. — EY51, ECL80, PCC84, PCF80, PCL83, PL81, PCL82, PY81, R19, U801, 30P4, etc. Best cash prices by return. DURHAM SUPPLIES, 175, Durham Rd., Bradford 8, Yorkshire.

WANTED—VALVES. Modern TV and radio types. Large or small quantities. Box No. 22.

WANTED. Service Sheets and Manuals. No quantity too large or too small; highest prices paid. SULTAN RADIO, 2 Stanley Road, Tunbridge Wells, Kent.

NEW TV VALVES WANTED. Send valves, cash by return for: P. J. P. ANDREWS, 61-63, Rosemary Rd., London, S.E.15.

A PROMPT CASH OFFER for your surplus Brand New Valves, Speakers, Components, Test Instruments, etc. R.H.S., 155, Swan Arcade, Bradford, 1.

MISCELLANEOUS

LOUDSPEAKERS, Electric Clocks and Shavers repaired promptly. **MODEL LOUDSPEAKER SERVICE.** Shipton on Cherwell, Oxford.

PROTECT YOUR CAR AT NIGHT
"LITON"

PHOTOELECTRIC PARKING LIGHT SWITCH

will switch your lights on at dusk—off at dawn, automatically, while you are at work, in bed, or away from home. Controlled by light. Transistorised. Avoid accidents, fines. Save your battery.

KIT OF PARTS. 52/6
BUILT AND TESTED. 57/6
Pat. Pending. Send 6d. stamp for pamphlet. "St. John's Radio," 156, St. John's Hill, S.W.11. BATTERSEA 9838

EDUCATIONAL

INCORPORATED Practical Radio Engineers home study courses of Radio and TV engineering are recognised by the trade as outstanding and authoritative. Moderate fees to a limited number of students only. Syllabus of Instructional Text free. "The Practical Radio Engineer" Journal, sample copy 2/-, 6/00 Alignment Peaks for Superhets 5/90 Membership and Entry Conditions booklet 1/-, all post free from the SECRETARY, I.P.R.E., 20, Fairfield Road, London, N.8.

"**HOW AND WHY**" of Radio and Electronics made easy by a new, non-maths, practical way. Postal instructions based on hosts of experiments and equipment building carried out at home. New Courses bring enjoyment as well as knowledge of this fascinating subject. Free brochure from: Dept. 12 P.T., RADIO-STRUCTOR, 40, Russell St., Reading, Berks.

STUDY RADIO, TELEVISION AND ELECTRONICS with the world's largest home study organisation—I.C.S. Courses for the enthusiast and for those seeking examination qualification. Brit.I.R.E. City and Guilds, R.T.E.B., etc. Build your own equipment with Practical Radio Course. Write to-day for free book. INTERNATIONAL CORRESPONDENCE SCHOOLS, Intertext House, Parkgate Road (Dept. 516), London, S.W.11.

*** LEARN ***

RADIO & T/V SERVICING

for your OWN BUSINESS/HOBBY

by a new exciting no-maths system, using practical equipment, recently introduced to this country.

FREE Brochure from:—

RADIOSTRUCTOR
DEPT. G78, 46, MARKET PLACE
READING, BERKS. 1/60

AERIALS

MAKE YOUR OWN AERIALS

SAVE £££s
TV aerial manufacturer offers "do-it-yourself" kits. 50 components include castings, pressings, mouldings, tubes, brackets, can be utilized to make 100 different models. TV, V.H.F., amateur. Brochure gives full illustrations, element dimensions and prices. Discounts for quantities.

THE RICHARD MAURICE EQUIPMENT CO.
Portsmouth Road, Cobham, Surrey.
COBHAM 3239.

SERVICE SHEETS

FAULTFINDER FILES (TV) showing common faults that each receiver is prone to and other useful servicing information, 2/- ea. List 9d. plus postage. S.P. DISTRIBUTORS, 11, Old Bond St., London, W.1.

SERVICE SHEETS. TV 4/- ea. Radio 3/- ea. List 1/-. All orders dispatched on day received. C.O.D. if required. Also manuals for sale and hire. Mail Orders Only. **SULTAN RADIO**, 29 Church Road, Tunbridge Wells, Kent.

SERVICE SHEETS (continued)

SERVICE SHEETS for sale, all types, from 1/-. Free Fault Finding Guide with all service sheets. 100 T/V Service Sheets covering 330 popular models, 18/6. Radio, T/V, Electronic, Books, S.A.E. lists / enquiries. **HAMILTON RADIO (T)**, 237, Sedlescombe Rd. N., Hastings.

SERVICE SHEETS. Radio, T.V., 5,000 models. Lists 1/-, S.A.E. enquiries. **TELRAY**, 11, Maudland Bk., Preston.

SERVICE SHEETS. — We have the largest stock of Radio and TV Sheets in the country for sale at 4/-ea. Why tolerate delay in obtaining your supplies when we will dispatch by return? 1960 Radio and Television Service Sheet List Now Ready. 1/- Also Manuals for sale and hire. List 9d. S.A.E. please. Mail Order Only. S.P. DISTRIBUTORS, 11 Old Bond Street, London W.1.

SERVICE SHEETS.—Huge stock at 4/- ea. List 1/-. Immediate delivery. **GLOBE SUPPLIES**, 33 Fairfield Close, Sidcup, Kent.

APPOINTMENTS

WANTED 677 Trainee Engineers

The Electricity Supply Industry has vacancies this year for 677 recruits to its engineering training schemes. They are required both by the Central Electricity Generating Board and by the 12 Area Electricity Boards.

83 university graduates are needed as graduate trainees. They should possess a degree in electrical or mechanical engineering of a British university.

73 technical college graduates are required as engineering trainees. They should possess a Diploma in Technology, a College Diploma, a Higher National Diploma or a Higher National Certificate in electrical or mechanical engineering.

521 school-leavers are needed as student apprentices. There are two levels of entry: for those who possess a good Ordinary level G.C.E., including passes in maths and science, and for those who have taken G.C.E. at "O" level and have also obtained passes in maths and physics at Advanced level.

Training for university and technical college graduates is by means of a planned two-year course of practical experience,

satisfying the requirements of the professional institutions.

Training for school-leavers is by means of a five-year apprenticeship, including day-release or a Sandwich Course, leading to a professional engineering qualification.

On satisfactory completion of training, all trainees are guaranteed employment in this essential, expanding industry. A wide range of careers is available in many types of engineering — generation, transmission, distribution, commercial and research. Because the demand for electricity doubles every ten years, the prospects of promotion are good.

For further information write to:

**The Education and Training Officer,
The Electricity Council,
154 Winsley Street,
London, W.1**

EDDY'S (Nottm.) LTD.

116-118 ALFRETON ROAD, NOTTINGHAM

**HUGE PURCHASE!
TRANSISTORS**

RED SPOT 4/9 each. Doz. Lots 4/3 each
WHITE SPOT 7/- each. Doz. Lots 6/6 ea.
Postage and Packing 6d.

LUXEMBOURG EXPANDING AERIALS. Compact and easy to fit. No technical knowledge required. Greatly improves reception. 3/11. Post 6d.

ACOS MIKES. 40-1. 25/6. Post 1/6.

NIFE ACCUMULATORS. Size 3 x 2 1/2 x 1/2 in. 7 amp 1.25 v. Weight 13ozs. 1/11. Post and Packing 1/6 one only, add 9d. cell.

SPECIAL OFFER!

CAR RADIO KITS. Seven Transistors. Long and Medium Waves 2 watts output. R.F. stage and automatic gain control. Complete kit with cabinet 10 1/2 gns. Speaker extra 17/11. Post and Packing 5/-. Please state voltage.

JACK PLUGS. Standard 1/11. Post 6d.
2000mfd. CONDENSERS. 6 volt working 1/6. Post 6d.

DIMMER SWITCHES. Ideal for train speed regulators. 1/11. Post 9d.

GERMANIUM DIODES. 1/- each, 9/6 Dozen. Post 4d.

HEADPHONE CORDS. High Quality 6ft. lengths. 1/11 Pair. Post 6d.

SPEAKER GOLD GRILL. 6 1/2 x 4in. 1/- each. Post 6d.

VIBRATORS. 12v. 4 pin. 4/11. Post 1/-.

CO-AXIAL CABLE. Air spaced suitable for TV fringe area V.H.F. etc. 7 1/2d. per yard. Cut to any length. Post 1/3 Doz. yards.

ACOS CRYSTAL PICK-UPS. Turnover Head (2 sapphire styli). 29/11. Post 2/6.

THROAT MIKES. 1/- Post 6d. Could be used for electrifying musical instrument.

RECTIFIER/STABILISER for 1.4v. valves Midget. 3/- Post 6d.

10mfd. PAPER CONDENSERS. Block. Ideal for cross over networks. 3/11. Post and Packing 1/-.

ALL ABOVE ARE NEW AND GUARANTEED

Surplus New and Guaranteed Valves

1A7GT	12/6	6K8G	6/6	B36	8/6
1C5GT	10/6	6Q7G	7/6	DAF96	8/3
1D5	9/6	6SA7M	6/-	DK96	8/6
1H5GT	9/9	6S24G	5/-	DL96	8/3
1L4	3/9	6SN7GT	4/9	DM70	7/6
1N5GT	9/9	6V6G	5/9	EB41	7/-
1R5	6/6	6V6GT	6/6	ECC81	6/-
1S5	6/6	6X5GT	6/6	ECC82	7/-
1T4	4/9	10F9	7/6	ECC83	7/6
3Q5GT	8/9	12A6	5/6	ECC84	8/9
5U4G	5/9	12AT6	8/6	ECC85	8/6
5Z4G	9/-	EB91	4/-	ECF80	10/6
6AM6	4/-	20D1	9/6	ECF82	10/6
6BBG	2/11	25A6G	8/-	ECH42	8/9
6BA6	6/6	25L6GT	9/-	ECL80	9/6
6BE6	6/6	25Z4G	7/6	ECL82	10/6
6C4	3/6	35L6GT	9/6	EF41	8/6
EL84	8/3	35V4	6/9	EF42	7/6
6C6	4/3	35Z4G	7/6	EF50	1/9
6CH6	9/3	807(B)	3/9	EF80	6/6
6F1	6/6	95A	1/6	EF85	7/6
6J5GT	3/6	95S	3/11	EF86	11/-
6L5M	4/3	956	2/11	EF89	8/-
6K7G	2/3	AZ1	12/6	EL41	9/3

Any parcel insured against damage in transit for only 6d. extra per order. All uninsured parcels at customers' risk. Postage and packing 6d. per valve extra. Over £3 Free C.O.D. or C.W.O. only. C.O.D. charge 3/- extra.

S.A.E. with all enquiries.

**RECORD
PLAYER
CABINET**



RP2

4/1
DEPOSIT

Balance at 2/11 per week for 19 weeks. A beautifully styled cabinet. Made by a famous manufacturer. In polka dot cloth with clipped lid and carrying handle. Size 16 x 14½ x 8½ in. deep. Will take a B.S.R. Monarch 4-speed Autochanger and 7 x 4 in. elliptical speaker and most of the modern portable amplifiers. Carr. & Ins. 4/6. Cash price **59/6**

**EXTENSION
SPEAKERS**

19/9



Polished oak cabinet of attractive appearance. Fitted with Bin. P.M. speaker W.B. or Goodmans of the highest quality. Standard matching to any receiver (2-5ohms) switch and flex included. Ins. & Carr. 3/9. Bin. P.M. Speaker 8/9. Std. 2-5 ohms. With O.P. Trans., 10/-, P. & P. 2/6. Elliptical Speaker 7 x 4 in. 19/6. Elliptical Speaker 9½ x 4½ in. 22/6.

**STEREO RECORD
PLAYER CABINET**

with extension speaker cabinet



at the
amazing
offer of
99/6

Portable 1960 show model in two tone colours. Extension speaker cabinet secured in lid. Size 18 x 14 x 18½ in. high. This stereophonic player rests at 35gns. in the shops today. A must for teenagers, and an essential for the enthusiast. Carr. & Ins. 5/6 with order. OR 6/1 initial payment and balance at 4/11 for 19 weeks.

Many other types and sizes of beautifully designed cabinets in stock at prices from **29/6 to 79/6**

- U.A.B. B.S.R. MONARCH 4-SPEED AUTO-CHANGER
8/1 initial payment and 19 weekly payments of 6/11
(Cash Price £6.19.6.)
- T.U.9 B.S.R. 4-SPEED SINGLE PLAYER 89/6 Carr. & Ins. 5/6
- COLLARO CONQUEST 4-SPEED AUTOCHANGER
3/1 payment and 19 weekly payments of 6/11
(Cash Price £6.19.6.)
- PORTABLE AMPLIFIER MK DJ 59/6 P & P 3/6

NO DEPOSIT—INTEREST FREE—20 OR 36 WEEKS TO PAY
DUKE & CO. (Dept. E.4), 621/3 Romford Road, Manor Park, E.12
Tel.: ILF 600/3

**RECORD
PLAYER
CABINET**



RP3

4/7
DEPOSIT

Balance at 3/5 per week for 19 weeks. A delightful looking cabinet. Size 14½ x 17½ x 8½ in. in two-tone leatherette. Will take a B.S.R. Monarch 4-speed auto-changer and 6 in. round speaker. Carr. & Ins. 4/6. Cash price **69/9**

MODERN 17" TV CHASSIS
Complete and working **22 gns.**

A chassis including 17 in. tube, permanent magnet speaker, 13 channel Turret Tuner (any two selected channels fitted). Other channels supplied on request at 7/6 each. 13 valves. Chassis and valves guaranteed for three months. CRT, 12 months' full guarantee. Sound I.F. 19.5 Mc/s Vision 16 Mc/s. A.C. only. Ready and working to fit into your own cabinet. Carr. & Ins. 25/-. As above with 14 in. tube, complete and working £19.19.0.

"AS-NU"

**Regunned
TV Tubes**

Supplied from stock, and despatched by British Railways same day.

COMPLETE NEW GUNS

fitted in every tube and fully guaranteed for TWELVE MONTHS.

		Mullard	Mazda
12 in. ...	£4.15.0	£5.0.0	
14 in. ...	£5.0.0	£5.10.0	
15 in. ...	—	£6.5.0	
16 in. ...	£6.10.0	—	
17 in. ...	£6.0.0	£6.5.0	
21 in. ...	£8.10.0	£8.10.0	

Plus 10/- Carr. & Ins.

Other types available. Please contact:

J. P. WRIGHT

1c Shotton Street, Doncaster
Sole Distribution Agent
Phone: DON 2636 or 66252

**BRAND NEW
GUARANTEED VALVES**

**CHECK THESE PRICES AND
SEE HOW WE CATER FOR THE
CITIZEN'S POCKET**

DAF96 8/-	EF86 11/-	PY82 6/9
DF96 8/-	EL41 9/-	PY83 7/9
DK92 8/3	EL84 8/-	UAF42 9/-
DK96 8/3	EY51 9/6	UBF89 9/-
DL94 7/3	EY86 8/9	UCC85 7/9
DL96 8/-	PCC84 7/6	UCH42 9/-
EBC41 8/3	PCC85 11/-	UCH81 8/9
ECC81 5/9	PCF80 7/3	UF41 8/6
ECC82 6/3	PCF82 9/-	UF89 7/3
ECC83 6/9	PCL82 9/-	UL41 8/6
ECC84 8/6	PL36 14/-	U25 11/3
ECC85 8/6	PL81 9/9	IR5 6/9
ECC86 10/10	PL82 8/-	IS5 6/-
ECL80 8/3	PL83 7/9	IT4 5/-
EF80 6/3	PY81 6/6	354 6/6

Postage 6d. valve extra.

May we quote for obsolete and transmitting types? (S.A.E. please.)

CITIZENS' VALVE SERVICE
(REGD.)

Office Address—No Callers :
**103, GANTSHILL CRESCENT,
ILFORD, ESSEX.**

**A SUPER SPECIAL
TV TUBE OFFER**

Why buy rebuilt or reconditioned tubes when we can supply you with a brand new 17 in. tube to replace the MW 48-64, 48-69, 171K, 172K, 17 ASP4, 17 AXP4, C17-1, C17-A, CR17-22, C17-FM, MW 48-60. Made by world-famous manufacturers complete with 12 months' maker's guarantee. Our Unbeatable Price £8.10.0. Also available brand new 14 in. to replace 36-24, 36-44, TR14-21, TR14-22, 11 KP4A, 14-LP4, 141K, C36-24 or for AW 36-20, 36-21 12 in. brand new 81 MW 31-74, all at £7 each. Also Cossor 65K 15 in. 4 volt filament equivalent to TA15 or 85K by fitting 6 volt filament transformer 10 gns. Cossor 108K 10 in. equivalent to EM1 816 £8.10.0. Ferranti 9 in. T9/5 4 volt filament 50/-, Post, packing & insurance 10/- extra.

**NEW MAX
ELECTRONICS**

for London's Finest Bargains in electronic and radio equipment. Also Largest Selection of Tape Recorders in the U.K. Also in stock 500 shop soiled and H.P. reprocessed TV sets in all sizes. All Guaranteed.

220, Edgware Road, London, W.2.
Tel. PAD 5607

TRANSFORMERS

Suppliers to B.B.C., I.T.A. and leading radio manufacturers, single or long runs, prompt delivery, home and export.

Rewinds to all makes.
H.W.FORREST(Transformers)Ltd.
Shirley, Solihull, Warwickshire
Tel.: SHirley 2483

R.S.C. (BRADFORD, LEEDS) (and MANCHESTER)

(Leeds) Ltd.

54-56 MORLEY ST. (Nr. Alhambra) BRADFORD.
5/7 COUNTY ARCADE, BRIGGATE, LEEDS, 1.
8/10 BROWN ST. (Market St.), MANCHESTER.
Mail orders to Dept. N., 29-31 Moorfield Rd., Leeds, 12.

Post Terms C.W.O. or C.O.D. No C.O.D. under £1. Postage 1/9 extra under £2. 2/9 under 25. Open to callers 9 a.m. to 6 p.m. Wednesdays until 1 p.m. S.A.E. with enquiries, please. Trade supplied.

R.S.C. TRANSFORMERS

Fully Guaranteed

Interleaved and Impregnated

Primaries 200-230-250 v 50 c/s screened
TOP SHROUDED DROP THROUGH
250-0-250 v 70 ma, 6.3 v 2 a, 5 v 2 a ... 17/9
350-0-350 v 80 ma, 6.3 v 2 a, 5 v 2 a ... 18/9
250-0-250 v 100 ma, 6.3 v 4 a 5 v 3 a ... 23/9
300-0-300 v 100 ma, 6.3 v 4 a, 5 v 3 a ... 23/9
350-0-350 v 100 ma, 6.3 v 4 a, 5 v 3 a ... 23/9
350-0-350 v 150 ma, 6.3 v 4 a, 5 v 3 a ... 29/9

FULLY SHROUDED UPRIGHT
250-0-250 v 60 ma, 6.3 v 2 a, 5 v 2 a ... 17/9
Midjet type 2-3 1/2 in. ... 25/9
250-0-250 v 100 ma, 6.3 v 4 a, 5 v 3 a ... 27/9
300-0-300 v 100 ma, 6.3 v 4 a, 5 v 3 a ... 27/9
350-0-350 v 100 ma, 6.3 v 4 a, 5 v 3 a ... 27/9
350-0-350 v 150 ma, 6.3 v 4 a, 5 v 3 a ... 35/9
425-0-425 v 200 ma, 6.3 v 4 a, C.T. ... 49/9
6.3 v 4 a C.T. 5 v 3 a ... 49/9

FILAMENT TRANSFORMERS
All with 200-250 v 50 c/s Primaries: 6.3 v. 1.5 a, 6/9; 6.3 v 2 a, 7/6; 0-4-6.3 v 2 a, 7/9; 12 v 1 a, 7/11; 6.3 v 3 a, 8/11; 6.3 v 6 a, 17/8.

CHARGER TRANSFORMERS
200-250 v 0-9-15 v 1 a, 12/9; 0-9-15 v 3 a, 16/9; 0-9-15 v 5 a, 19/9; 0-9-15 v 6 a, 23/9.

OUTPUT TRANSFORMERS
Midjet Battery Pentode 66:1 ... 3/9
Standard Pentode 5,000 to 3 ohms ... 3/8
Small Pentode 5,000 to 3 ohms ... 5/8
Standard Pentode 7,8,000 to 3 ohms ... 5/8
Push-Pull EL84 to 3 or 15 ohms ... 18/9
Push-Pull 10-12 watts 6V6 to 3 or 15 ohms ... 18/9
Push-Pull 10-12 watts 6V6 to 3, 5, 8 or 15 ohms ... 19/9

SMOOTHING CHOKES
100 ma 10 h 250 ohms ... 8/9
80 ma 10 h 350 ohms ... 5/6
60 ma 10 h 400 ohms ... 4/11

SELENIUM METAL RECTIFIERS

Special quotes for quantities of 50 to 5,000.
H.T. (H.W.) F.W. (Bridge)

250 v 50 ma .. 3/11	6/12 v 1 a .. 3/11
250 v 80 ma .. 5/11	6/12 v 2 a .. 6/11
250 v 100 ma .. 6/11	6/12 v 3 a .. 9/9
Contact Cooled	6/12 v 4 a .. 12/3
250 v 80 ma .. 6/11	6/12 v 5 a .. 14/6
250 v 75 ma	6/12 v 6 a .. 15/6
F.W. (Bridge) 8/11	6/12 v 10 a .. 25/9
	6/12 v 15 a .. 27/9

CO-AXIAL CABLE 1/2 in. .. 8d. yd.
75 ohms 14/36 11d. yd.
Twin-screened Feeder 11d. yd.

BATTERY SET CONVERTER KIT
All parts for converting any normal type of Battery Receiver to A.C. mains 200-250v 50 c/s. Supplies 120 v, 90 v or 60 v at 40 ma. Fully smoothed and fully shielded L.T. of 2 v at 0.4 to 1 a. Price including circuit. 49/9. Or ready for use, 9/9 extra.

ALL DRY RECEIVER BATTERY ELIMINATOR KIT—All parts for the construction of a unit (metal-case 6-4-2in.) to supply Battery Portable receivers requiring 90 v and 1.5 v. Fully smoothed. From 200-250 v 50 c/s mains. Price, inc. point-to-point wiring diagrams. 39/9. Or ready for use, 46/9.

D.C. SUPPLY KIT—Suitable for Electric Trains. Consists of mains trans. 200-250 v 50 c.p.s., A.C. 12 v 1 a Selenium F.W. Bridge Rectifier, 2 Fuseholders, 2 Fuses, Change Direction Switch, Variable Speed Regulator. Partially drilled Steel Case, and Circuit. **33/9**

TELEVISION RECTIFIERS
250 v 200 ma. Size 3 x 1 1/8 in. Brand New, 6/9.

EX-GOVT. MAINS TRANSFORMERS

All 200-250 v 50 c/s input.
Removed from New ex-Govt. units, **22/9**
270-0-275 v 100 ma, 6.3 v 7 a, 5 v 3 a
300-0-300 v 60 ma, 6.3 v 2 a .. 11/9
255-0-265 v 150 ma, 6.3 v 11 a, 5 v 3 a, 5 v 3 a
350-0-350 v 100 ma, 6.3 v 2 a, 5 v 2 a .. 18/9
0-10-25 v 24 a, 79/6, carr. 15/-.

AUTO 0-110/120-220/240 v, 50 watts .. 8/11

EX-GOVT. SMOOTHING CHOKES—
60 ma 5-10 h 250 ohms .. 2/11
80 ma 10 h 150 ohms .. 2/9
100 ma 5 h 100 ohms Tropicalised .. 3/11
100 ma 8-10 h 100 ohms Parmeko .. 6/9
120 ma 12 h 100 ohms .. 8/9
150 ma 10 h 150 ohms .. 9/9
200 ma 3-5 h 100 ohms Parmeko .. 7/8

EX-GOVT. CASES. Well ventilated, black crackle finished, un drilled cover. Size 14 x 10 x 8 1/2 in. high. IDEAL FOR BATTERY CHARGER OR INSTRUMENT CASE. OR COVER COULD BE USED FOR AMPLIFIER. Only 9/9, plus 2/9 postage.

BATTERY CHARGERS
For 200/250 v 50 c/s A.C. mains. 12 months guarantee. Attractive, well ventilated hammer finished cases, 6 or 12 v 4 amp, with meter and variable charge rate selector, as illustrated **69/9**
Or Deposit 13/3 and 5 monthly payments of 13/3. 6 v or 12 v 1 amp type. Also suitable for electric train power supply. Only 29/9 post 2/9.



INRAXIA LTD.

The Name for High Grade
REBUILT TUBES

ALL TYPES OF

12" to 17"

only £7/15/0

CARRIAGE FREE

£1 allowed for old Tube

12 MONTHS' GUARANTEE

INRAXIA LTD.,
65/66 Coleshill Street,
BIRMINGHAM, 4.

'Phone: ASTON CROSS 4815

CHALMERS & JOY

TELEVISION ENGINEERS
79 HILLTOWN, DUNDEE

Telephone No. 6298

Terms: C.W.O. or C.O.D. Callers welcome
NEW VALVES! BOXED! 12 MONTHS, GUARANTEE!

6X4 8/2	EY51 10/-	PL81 12/6
6V6 13/6	EY86 10/-	PL82 9/6
EB91 7/6	EZ40 7/9	PL83 12/6
EBG90 10/-	PCC84 12/-	PL84 9/6
ECC84 12/-	PCF80 13/-	FY81 9/11
ECP80 12/6	PCL82 13/6	FY82 7/4
ECL80 10/6	PCL84 13/-	UL41 10/6
EF91 14/-		

P. & P. 1/6, any quantity.

NEW TUBES! 12 MONTHS GUARANTEE

MW 43-69 £9.0.0

P. & P. 12/6, incl. insurance.

SEMI AIR-SPACED COAXIAL CABLE
7d. per yard, P. & P. 1/- per 20 yards.
Boost Transformers for Tubes, 2 v., 6.3 v. or 13 v., prim. 200-250 v. A.C.
14-Sound Output Transformers (multi ratio) 10/-
Transistor Transformer (Driver OC71 into OC72's) 10/6
Transistor Transformer (Output OC72's into 3 ohms) 10/-

P. & P. 2/- per order.
Midjet Volume Controls, D.P. Switch 5/-
less Switch 3/6
10k, 25k, 50k, 100k, 250k, 500k, 1M, 2M.
P. & P. 1/6.

REBUILT TV TUBES

FULLY GUARANTEED 12 months

Complete New Gun fitted in every Tube

12 in.	£5.0.0
14 in., 15 in.	£5.10.0
17 in.	£6.10.0
21 in.	£9.0.0

Immediate Delivery

Carriage & Insurance 10/- extra

NU-GUN TELETUBES Limited

3 The Mews, Duckett Rd.,
Harringay, London, N.4.

Telephone: MOUNTVIEW 2903

The book for every practical model maker . . .

RADIO-CONTROLLED MODELS

by F. J. CAMM

This practical book is the result of numerous experiments and long research on the subject and includes information already published in the nationally read "Practical Mechanics" plus additional material. Contents include steering control gear; receivers; transmitters; control box; tuned reeds; model actuators; tuning transmitting aerials; details for model battleship and aircraft, etc. Fully illustrated with circuit details, diagrams and photographs, etc.

12s. 6d. FROM ALL BOOKSELLERS

... or in case of difficulty 13s. 6d. by post from G. ARTHUR PEARSON LIMITED, Tower House, Southampton Street, London W.C.2.



Safety first every time with these patented spring-loaded AVO Prodclips.

Cleverly designed for use as insulated prods, they are invaluable for reaching and holding test points which are difficult of access.

Suitable for use with AvoMeter, Multiminator and Avo Electronic Test Meter Leads. Post Free 15/- per pair.

AVO LTD · AVOCET HOUSE, 92-96 VAUXHALL BRIDGE ROAD, LONDON, S.W.1. VICTORIA 3404 (12 lines) A MEMBER OF THE METAL INDUSTRIES GROUP OF COMPANIES.

STOP! Don't waste time and MONEY looking any further.

SENSATIONAL offer direct from the factory to you the public.

REBUILT TELEVISION TUBES


12" 14" 16" 17" **£5.0.0**
 21" **£6.0.0**

Carriage and Insurance 12/6 extra
 FULL 12 MONTHS' GUARANTEE. C.W.O.

S.A.E. will bring you full data on the "BROMLEY" tape recorder which is hand built for the Connoisseur at only 49gns.

EASY H.P. TERMS
 IMMEDIATE ATTENTION ASSURED

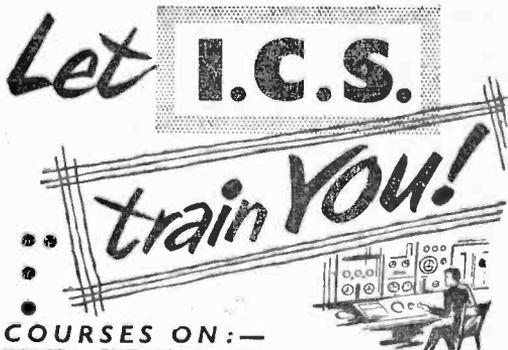MAYDAY ELECTRONICS (MAIL ORDER)
 9, MAYDAY ROAD, THORNTON HEATH, SURREY
 Tel.: THO 7805



COURSES ON:—

- RADIO and TELEVISION
- SERVICING · ELECTRONICS

EXAMINATION COURSES FOR:—

- C. & G. Radio Servicing Certificate (R.T.E.B.)
- C. & G. Radio Amateurs' Exam. (Amateurs' Transmitting Licence)
- British Institution of Radio Engrs., etc.

Whether you plan to have your own business, to become an electronics engineer or to take up a career in industry, an I.C.S. Course will help you to success. You learn at home in your own time, under expert tuition. Moderate fees include all books.

LEARN-AS-YOU-BUILD

Practical Radio Course

- A basic course in radio, electronic and electrical theory backed by thorough practical training. You build a 4-valve T.R.F. and a 5-valve superhet radio receiver, signal generator and multi-tester.
- Other Learn-as-you-Build radio courses are available

MULTI-TESTER (Sensitivity 1,000 ohms per volt)

5-VALVE SUPERHET RECEIVER

RF/AF SIGNAL GENERATOR

Post this Coupon TODAY! for FREE book on careers in Radio, etc., and full details of I.C.S. Courses.

International Correspondence Schools
 (Dept. 164B), Intertext House, Parkgate Road, London, S.W.11.

Please send book on

Name and Address Age

Occupation 4.80

INTERNATIONAL CORRESPONDENCE SCHOOLS

REGUNDED

Television Tubes, 12 months' guarantee. 12" to 14" £5.10.0. 15" to 17" £6. Carriage and insurance 10s. extra.

SCOTCH RECORDING TAPE

1200 Reels—Standard 23/-
1800 Reels—Extra Play 37/6.

DUBBLER TYPE "C" CONTROL S500K.
8/6 each.

CO-AXIAL CABLE, semi-airspaced, 75 ohms, 6d. yard.

RECTIFIERS

RMI 5/3, RM2 6/9, RM3 7/6, RM4 13/6, RM5 19/6, 14A86 19/6, 14A97 19/6, 14A100 19/6, LW7 17/6, 18RA.1-1-16-1 6/-. FC31 (14RA 1-2-8-3) 22/6, RC10L (14RA 1-2-8-2) 18/6.

METERS Panel Mounting (Round)

Moving Coil	F.S.D.	Res.	Scale	Size	Price
Weston (U.S.A.)—	1 mA	150 ohms	0-100	3 1/2"	27/6
Weston (U.K.)—	1 mA	75 ohms	0-100	3 1/2"	22/6
W.D. (U.K.)—	5 mA	0.0037 ohms	0-20	2"	9/-
W.D. (U.S.A.)—	500 microA	—	0-600	2 1/2"	15/6

COSSOR BATTERY ELIMINATORS

Two separate units identical in size to the B126 and AD35 batteries, 1.5 v. L.T., 90 v. H.T. Suitable for the latest low consumption valves, fully stabilised. New in original cartons. Listed at 63/-. Price 37/6. Post 1/6.

OSMOR JIFFY PUNCH

Type 1	Hole size 1/4"	7/-
Type 2	8/-
Type 3	9/3

ALPHA RADIO TERMS.—Cash with order or C.O.D. Postage and Packing charges extra, as follows: Order value 10/- add 1/3; 20/- add 1/9; 40/- add 2/6; £5 add 3/6. Minimum C.O.D. Fee and Postage 3/-. For full terms of business see inside cover of our catalogue. Personal Shoppers 9 a.m. to 5 p.m. Monday to Friday. Saturday 10 a.m. to 1 p.m.

103 LEEDS TERRACE, WINTOWN STREET, LEEDS, 7.

ALPHA RADIO SUPPLY CO.

VALVES GUARANTEED ALL TESTED BEFORE DESPATCH

AZ1	10/-	GZ32	12/-	354	7/8
AZ31	10/-	PCC84	9/-	3V4	8/8
DAF96	8/9	PCC85	9/6	5X3G	8/-
DF96	8/9	PCF80	9/6	5Z4G	9/8
DK96	8/9	PCL82	12/-	6AL5	4/-
DL96	8/9	PCL83	14/6	6F1	14/-
EAF42	10/6	PL33	14/6	6F15	14/-
EBC33	8/9	PL38	26/6	6J7G	6/8
EBC41	9/6	PL81	12/6	6K7G	3/8
ECC81	8/-	PL82	8/6	6K8G	6/8
ECC82	7/6	PL83	11/6	6K25	19/11
ECC83	9/-	PY32	17/6	6L6M	9/8
ECC84	10/-	PY81	8/6	6AM6	4/6
ECC80	12/-	PY82	7/-	6Q7G	7/6
ECC82	13/-	PZ30	19/11	6V6G	6/-
ECH42	9/6	TP25	10/-	6V8GT	7/6
ECH41	9/-	U5	11/-	6X5GT	7/-
ECL80	10/-	U26	12/6	7B6	10/9
EF39	5/9	U37	26/6	7H7	9/-
EF41	9/9	U281	19/11	7S7	9/8
EF80	8/-	U80	29/10	7Y4	8/-
EF86	13/-	UAF42	9/6	8A1	15/-
EL33	14/-	UBC41	8/-	10P13	15/-
EL41	10/6	UCH42	10/6	12A17	7/6
EL42	10/6	UF41	9/-	12AX7	8/-
EL84	9/-	UL41	10/-	12A07	8/-
EM34	9/6	UUS	26/6	20P1	26/6
EM80	10/-	UY1N	12/6	20A6G	10/8
EY51	10/-	UY41	7/6	25Z4G	9/6
EY86	10/-	1R5	7/6	27S2	19/11
EZ40	7/6	1S5	6/6	35L8GT	10/-
EZ81	7/6	1T4	8/-	35Z4GT	8/-

OSMOR CHASSIS CUTTERS

Type 1	Hole size 1/4" x 1/4"	19/9
Type 2	21/6
Type 3	24/9

CONVERT YOUR RADIOGRAM with one of these Modern Automatic Record Changer Units

Monarch UA8 4-speed automatic record changers with Ful-Fi turnover crystal cartridge, £8.19.6. Carriage 3/6.
Collaro Conquest 4-speed fully mixing changer complete with Studio "O" crystal cartridge, £7.19.6. Carriage 3/6.
Garrard RC120/D Mark II, 4-speed unit manual control to enable records to be played singly £8.19.6. Carriage 3/6.
Garrard RC121, the latest 4-speed automatic record changer, £10.19.6. Carriage 3/6.

REPANCO TRANSISTOR AMPLIFIER and FEDER UNIT CIRCUITS. Envelope 1/6. Post 4d.

WIRELESS WORLD, Guide to Broadcasting Stations. Twelfth Edition, 3/6. Post 4d.

HIGH RESISTANCE HEADPHONES 400 ohms. 13/8 pair.
LOW RESISTANCE HEADPHONES, 120 ohms. 7/6 pair.

RESISTORS, Assorted, 100 for 12/6.

HEATER TRANSFORMERS
All 240 v. input. 4 v. 3 amp. 10/-, 6.3 v. 1 1/2 amp. 6/8, 6.3 v. 3 amp. 10/-, 12.6 v. 1 amp. 5/9, 5 v. 2 amp. 10/-, 2 v. 3 amp. 8/3.

CATALOGUE

Our 1960 catalogue is now available. Please send 1/- in stamps for your copy.

SPECIAL VALVE OFFER

For Limited Period

EB91	4/-	UF42	8/6	6L1	8/-
ECL32	8/6	UL41	7/-	6L18	9/-
ECL32	9/-	UL44	7/6	6P25	6/8
EP81	5/-	UL45	7/6	6S20	7/6
EP91	4/-	UBC41	7/6	6SN7GT	5/6
EL33	10/6	UCH42	7/6	7Q7	6/-
EY83	7/8	U35	8/6	10F1	6/-
GZ32	8/-	SP61	2/6	10P13	8/6
KT33C	6/6	3D6	2/8	10P14	8/6
KT36	8/6	8AT3	6/6	12AT7	6/-
PL33	8/-	6CH6	7/-	20D1	7/8
PL82	7/8	6BG6G	10/6	20F2	8/6
PL83	7/8	6F1	6/-	20L1	8/6
PY80	7/-	6F13	8/-	20P1	9/6
PY82	7/-	6F14	6/-	807	6/-
PZ30	11/-	6F15	6/-	185BT	12/6
UAF42	8/8	6J5GT	5/-	1625	8/-

Postage 4d. per valve.

Air-Spaced Coaxial Cable, 75 ohms, 8d. yd. Ion Traps, 5/-; Midget 2 Gangs, 6/8; 24in. Flush Meters, 0-100 mA and 0-500 mA. 17/5.

TV AERIALS: We carry large stocks; send S.A.E. with your requirements and we shall reply and send leaflets by return.

MAIL ORDER ONLY — NO CALLERS

Terms: C.W.O. or C.O.D., minimum C.O.D. 3/-; post age packing other than valves, under £2, 1/6; under £5, 2/-; aerials 2/6.

ELECTRO SERVICES & CO.

221 BATTERSEA PARK RD., S.W.11

Mac. 6833/4

B.B.C. - I.T.V. - F.M. AERIALS



B.B.C. (HAND D) Tele-scopic loft, 19/8. External, S/D, 26/3.

I.T.V. (BAND 3), 3 Element, loft array, 24/-, 5 Element, 32/6. Wall mounting, 3 Element, 33/9, 5 Element, 41/3.

COMBINED B.B.C. + I.T.V. Loft 1+3 Element, 41/3, 1+5 Element, 48/9. Wall mounting, 1+3 Element, 56/3, 1+5 Element 82/9. Chimney and mast mounting units also available.

F.M. (BAND 2), Loft "H", 28/-, 3 Element, loft, 52/6. S/D loft, 12/6. External S/D, 26/3. State channel when ordering. C.W.O. or C.O.D. P.P. 2/6. Coaxial cable, 8d. yd. Coaxial plugs, 1/3. Send 8d. stamps for illustrated lists.

K.V.A. ELECTRONICS (Dept. T.P.)
3B, Godstone Road, Kenley, Surrey

A 3d. stamp will bring you a copy of our latest

RADIO & TELEVISION COMPONENT Catalogue
JAMES H. MARTIN & CO.
FINSTHWAITE, NEWBY BRIDGE, ULVERSTON, LANCs.

RES/CAP. BRIDGE 37/-

p. & p. 2/-
Checks all types of resistors, condensers 6 RANGES

Built in 1 hour. Direct reading
READY CALIBRATED
Stamp for details of this and other kits.

RADIO MAIL (Dept. Vx)
Raleigh Mews, Raleigh Street, Nottingham

Still available — a comprehensive, practical "basic" course in TV transmission and reception..

A BEGINNER'S GUIDE TO TELEVISION

by F. J. CAMM. Covers:—


Persistence of Vision and Scanning · Cathode-ray Tube · The Timebase · Receiving and Transmitting Systems · The Aerial · Tracing the signals through the Receiver · Video Section · The Television Camera · The tuning Signal, Test Card C, and tracing faults · Colour · The N.T.S.C. System—Tricolour Tubes explained · Telecine—Video Tape Recording · Stereoscopic Television · Technical Terms · Index.

With 61 illustrations

ONLY 7s. 6d. FROM ALL BOOKSELLERS

... or in case of difficulty send 8s. 6d. to **GEORGE NEWNES LTD., Tower House, Southampton St., London, W.C.2.**

Build your own Aerials...

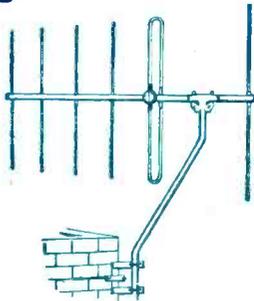

AT HOME

AERIAL FITTINGS FOR BAND III, BAND I & RADIO F/M.
 Useful formulae and hints for constructing your own aerial quickly and cheaply. Catalogue illustrating our increased range of Diecast Alloy Fittings, including Band III to Band I Mast Couplers, Reflector and Director Rod Holders, Insulators (both "Inline" and "H" types), Masthead Fittings, Masts and Elements, Chimney Brackets, etc. Send 1/- in stamps for the above, to:—

Fringevision Ltd.

MARLBOROUGH, WILTS. Phone: 657/8

AS ADVERTISED ON TELEVISION

Save £££

12 Months' Guarantee

FACTORY REBUILT...

TELEVISION TUBES

ALL TYPES AND SIZES—Immediate Delivery
 FITTED WITH COMPLETE NEW GUN

Price

12" £5.12.6 14" £5.17.6 15" £6.5.0 17" £7.0.0
 21" £9.10.0

TERMS TO
 THE TRADE

Plus 10/- carriage and insurance.
 Cash with order or C.O.D.

RE-VIEW (LONDON) LTD.

10 High Street

Colliers Wood, S.W.19

Telephone: Liberty 3272

C.R.T. ISOLATION TRANSFORMERS
TYPE A. OPTIONAL 25% and 50% BOOST.
2 V. OR 4 V. OR 6.3 V. OR 10.8 V. OR
13.3 V. 12/6. TAPPED MAINS INPUT.
TYPE A.2. HIGH QUALITY, LOW CAPACITANCE,
10/15 pF. OPTIONAL BOOST 25%, 50%, 75%, 16/6. TAPPED MAINS INPUT.
TYPE B. MAINS INPUT, MULTI OUTPUT 2,
4, 6.3, 7.3, 10 AND 13 VOLTS. BOOST 25%
AND 50%. LOW CAPACITY. 21/-

TRIMMERS, Ceramic. 30, 50 70 pF. 9d. 100 pF. 150 pF. 1/3. 250 pF. 1/6. 500 pF. 2/0 1/9.
 RESISTORS. Preferred values. 10 ohms to 10 meg. 1 w. 4d. 1 w. 4d. 1 w. 6d. 1 w. 8d. 2 w. 1/1.
HIGH STABILITY. 1 w. 1/1. 2 w. Preferred values
 100Ω to 10 10 meg. Ditto, 5 w. 100Ω to 5 meg. Ω. 9d. 5 watt. **WIRE-WOUND RESISTORS** { 1 3
 10 watt. 25 ohms-10000 ohms { 1 6
 15 watt. 25 ohms-10000 ohms { 1 6
 15,000 ohms-50,000 ohms, 5 w. 1/9; 10 w. 2/3.

PLASTIC RECORDING TAPE
 Long Play 7in. Plastic reel. 1,700ft. ... 35/-
 Long Play 5in. Plastic reel. 1,200ft. ... 28/-
 Long Play 5in. Plastic reel. 8,500ft. ... 21/-
 Long Play 5in. Plastic reel. 2,200ft. ... 7/8
 Standard 7in. Plastic reel. 1,300ft. ... 24/-
 Standard 5in. Plastic reel. 600ft. ... 15/-
 "Instant" Bulk Tape Eraser and Head Defluxer, 200/250 v. A.C., 27/6. Leaflet, S.A.E.

O.P. TRANSFORMERS. Heavy Duty 50 mA, 4/6. Multiratio, push-pull, 7/8. Miniature, 384, etc., 4/6.
L.F. CHOKES 15/10 H. 60/65 mA, 5/-; 10 H. 85 mA, 10/6; 10 H. 150 mA, 14/-.

MAINS TRANSFORMERS 200/250 v. A.C. STANDARD. 250-0-250, 80 mA. 6.3 v. 3.5 a. tapped 4 v. 4 a. Rectifier 6.3 v. 1 a. 5 v. 2 a. or 4 v. 2 a. ditto, 350-0-350 ... 22/6
MINIATURE 200 v. 20 mA. 6.3 v. 1 a. ... 10/6
MIDGET 220 v. 45 mA. 6.3 v. 3 a. ... 15/6
SMALL 250-0-250, 80 mA. 6.3 v. 3.5 a. 19/8
STD. 250-0-250, 65 mA. 6.3 v. 3.5 a. ... 17/8
HEATER TRANS. 6.3 v. 14 amp. ... 7/6
 Ditto, tapped sec. 2, 4, 6.3 v., 14 amp. ... 8/6
 Ditto, sec. 6.3 v. 3 amp. ... 10/6

ALADDIN FORMERS and core, 1in. 8d., 2in. 10d. 0.3in. FORMERS 5087/8 and Cans TV12. 2in. sq. x 2in. and 4in. sq. x 1 1/2in., 2/- ea., with core.
TYANA - Midget Soldering Iron, 230 v. 40 w. 10/9.
REMPLOY Instrument Iron, 230 v. 25 w. 17/8.
MAINS DROPPERS. 3in. x 1 1/2in. Adl. Sliders. 0.5 amp. 1,000 ohms. 4/2. 0.2 amp. 1,000 ohms. 4/3.
LINECORD. 0.3 amp., 60 ohms per ft., 0.2 amp., 100 ohms per ft., 2-way, 6d. per ft. 3-way, 7d. per ft.
LOUDSPEAKER P.M. 3 OHM. 5in. Rola, 17/6. 8in. Plessey, 19/8. 6in. x 4in. Rola, 18/-.
 4in. Rola, 18/6. 10 x 6in. 27/6. 10in. Rola, 30/-.
 4in. Hi-Fi Tweeter, 8/-; 12in. S.A., 30/-.
 14 x 5in. 45/-; 12in. 15 ohm. 10 v. Plessey, 45/-.
STENTORIAN HF 1012 10 in. 3 to 15 ohm, 10 v. 95/-
 12in. Baker 15 watt 3 ohms, or 15 ohms, 105/-.
CRYSTAL DIODE G.E.C. 2/-; GEX34, 4/-.
HIGH RESISTANCE PHONES. 4,000 ohms, 16/8
MIKE TRANSF. 50. 1. 3/8 ea.; 100:1. Potted, 10/6.
SWITCH CLEANER. Fluid squirt sprout. 4/3
TWIN GANG TUNING CONDENSERS. 365 pF miniature 1in. x 1 1/2in. x 1 1/2in., 10/-; 0.0005 Standard with trimmer, 9/5; less trimmer, 8/-; midget, 7/8.
SINGLE. 50 pF, 2/8; 75 pF, 100 pF, 160 pF, 7/-; solid dielectric 100, 300, 500 pF, 3/8.
SPEAKER FRET GOLD CLOTH. 17in. x 2 1/2in. 5/-; 25in. x 3 1/2in. 10/-; Tycan dt. 6in. wide, 10/-; 11. 20 3in. wide, 5/- ft. Samples S.A.E.

New and Boxed VALVES 80-day Guarantee.

1R5	7/6	6K80	7/8	6AHC80	8/8	6AHC80	8/8
1S5	7/6	6L6G	10/8	6R91	6/8		10/8
1T4	6/-	6N7M	6/8	6RC33	8/8	6YR2A	6/8
2X2	3/6	6Q7G	7/6	6RC41	8/8	6M1U4	9/8
2X4	7/6	6SA7	6/8	6RF80	10/8	6P41	3/8
6Y4	7/8	6BJ7M	6/8	6YCS4	9/8	6YCS4	9/8
5U4	7/6	6SN7	6/8	6C180	9/8	6PCF80	9/8
5Y3	7/6	6V6G	7/8	6CH42	10/8	6CL82	11/8
5Z4	9/6	6X4	7/8	6CL82	10/8	6EN25	6/8
6AM6	6/-	6X5	6/8	6PF39	5/8	6P82	10/6
6B8	5/6	6ZAT7	8/-	6PF41	9/8	6P82	7/8
6BE6	7/8	6ZAT7	8/-	6PF50	5/8	6Y82	7/8
6BH6	10/6	6ZAT7	8/-	6PF52	7/8	6Y82	7/8
6BW6	10/6	6ZB16	10/8	6PF91	5/8	6Y81	3/8
6D6	6/-	6ZK7	8/6	6PF92	5/8	6Y81	10/11
6E0G	7/6	6ZQ7	8/6	6PF92	5/8	6Y81	10/11
6H6	3/6	6ZL6	6/8	6PL32	5/8	6Y81	10/11
6H7	5/6	6ZL6	6/8	6PL84	8/8	6Y81	9/8
6J6	5/6	80	10/6	6PML	9/8	6Y81	8/5
6J7G	6/8	807	5/8	6L240	7/8	6Y82	8/8
6K6T	6/6	95A4	1/6	6Z80	7/8	6Y81	10/5
6K7G	5/6	9E450	1/6	6E1145	7/8	6Y81	10/6

TELEVISION REPLACEMENT LINE OUTPUT TRANSFORMERS

70/- ea. from stock.
 For Makes and Models

Argosy: T2, CTV517. **Decca:** D17 & C. **Defiant:** TR1753. **RGD:** 6017T, 7017C, C54. **Regentone:** 17C, 17T, 17 Comb.

Argosy: T3. **Decca:** D14. **Defiant:** TR1453T. **Regentone:** 14T. **RGD:** 6014T.

Marconi: VT63DA. **Baird:** 2014, 2017, 2114, 2117. **Cossor:** 930 & T, 931, 933-4-5, 937, 938 & A. & F. 939 & A & F, 943T, 946.

H.M.V. 1824 & A, 1825 & A, 1826 & A, 1827 & A, 1829 & A, 1865, 1869.

Marconi: VT68DA, VT69DA. **Sobell:** TS17, T.346.

Ferguson: 306T, 308T. Other makes available (7 days). S.A.E. with enquiries.

LINE BLOCKING TRANSFORMERS, 10/- to 16/6.

FRAME BLOCKING TRANSFORMERS, 13/6 to 21/-

FRAME OUTPUT TRANSFORMERS, 27/6 to 39/-

Most makes available (7 days). S.A.E. with all enquiries.

TV and RADIO SERVICE SHEETS, 1,500 models. Send 2/6, your Model No. and S.A.E.

HIGH GAIN TV PRE-AMP KITS BAND I BBC
 Tunable channels 1 to 5. Gain 18dB. EOC84 valve. Kit price 29/6 or 49/8 with power pack. Details 6d. (PCCSA valves if preferred).

BAND III ITA—Same prices.
 Tunable channels 8 to 13. Gain 17dB. EOC84 valve.

CRYSTAL MIKE INSERT by Acos, precision engineered. Size only 2in. x 3/16in. 6/6.

ALUMINIUM CHASSIS. 18 s.w.g. modified. With 4 sides, riveted corners and lattice fixing holes. 2 1/2in. sides, 7 x 4in. 4/6. 3 x 7in., 5/9. 11 x 7in., 6/9. 13 x 9in., 8/6. 14 x 1 1/2in., 10/6. 15 x 1 1/2in., 12/6. 18 x 1 1/2 x 3in., 16/6.

TELETRON "TRANSIDYNE" MIDGET SUPERHET PORTABLE 6" x 4" x 1 1/2" 6 transistors, printed circuit, Ferrite aerial. All parts and cabinet, 21/19.6. We include Edwards Transistors for maximum performance. Details 9/-.

BBC TRANSISTOR RADIO. Med. and Long Wave. Complete kit, 32/6, phones 7/8 extra. Deaf Aid Earpiece with special Lead 15/-; Details 6d.

GARRARD TA MK II SINGLE PLAYER

AUDIO PERFORMANCE

Designed to play 16, 33, 45, 78 r.p.m. Records 7in., 10in., 12in. Lightweight Xtal pick-up. GC8 plug-in head. Auto stop. Stereo-wired. **OUR PRICE £8.10.0** each. Post Free (Stereo Heads £2 extra).

Model 4HF. TRANSMISSION QUALITY. With Plug-in Normal Heads, £18.0.0. (Stereo Heads £2 extra).

Volume Controls 80 ohm COAX Long spindles. Guaranteed Post 1st. per yard extra. 1 year. Midget Semi-air, spaced. 5k ohms to 2 Meg. Air. Losses cut 6d. per No Sw. D.P. 50%. 3/9. 4/9. Fringe Quality 1/- yd. Linear or Log Tracks. Air Spaced. 1/- yd.

COAK PLUGS 1/- LEAD SOCKET 2/- **FIL SOCKET** 1/- **OUTLET BOXES** 4/6 **BALANCED TWIN FEED** 7d. 500 ohms. **DITTO SCREENED** per 1/6. 80 ohms only. **WIRE-WOUND POTS.** 3 WATT. Pre-set Min. TV Type. All value 25 ohms to 25 K., 3/- ea. 30 K., 2/8. 4/-; (Carbon 30 K., 2 to 2 meg. 3/-) **WIRE-WOUND 4 WATT.** Pots. Long Spindle Values. 100 ohms to 50 K., 6/8; 100 K., 7/6. **CONDENSERS.** New Stock. 0.001 mfd. 7 kv. T.C.C. 5/6; 0.010, 20 kv., 9/6; 0.1 mfd., 7 kv., 9/6; 0.100, 500 v. 0.001 to 0.05 mfd., 9d.; 0.1, 1/-; 0.25, 1/6; 0.5, 500 v., 1/9; 0.1, 1/350 v., 9d.; 0.12, 0.00 v. 0.11, 500 v., 1/9; 0.1 mfd., 2,000 volts, 3/8. **CERAMIC COND.** 500 v., 0.3 pF to 0.01 mfd., 9d. **SILVER MICA CONDENSERS.** 10%, 5 pF to 500 pF, 1/-; 600 pF to 3,000 pF, 1/3. Close tolerance 1 pF 1.5 pF to 47 pF, 1/8. Ditto 1% 50 pF to 815 pF, 1/8; 1,000 pF to 5,000 pF, 2/-.

I.F. TRANSFORMERS 7/6 pair 485 Kcs./Sec. Tuning Instrument Can. 2in. x 1in. x 1in. High Q and good bandwidth. By Pte Radio. Data sheet supplied. Wearite M800 I.F. 485 Kcs, 12/6 per pair. Wearite 550 I.F. 485 Kcs, 12/6 per pair.

NEW ELECTROLYTICS. FAMOUS MAKES TUBULAR TUBULAR CAN TYPES
 1/350v. 2/- 50/350v. 5/6 8/500v. 3/-
 2/450v. 2/3 100/25v. 2/16 500v. 4/-
 4/450v. 2/3 250/25v. 2/8 32/350v. 5/8
 8/450v. 2/3 500/12v. 3/10 100/270. 5/8
 8/500v. 2/9 8/450v. 4/8 2,500/3v. 4/-
 16/450v. 3/6 8/500v. 5/- 5,000/3v. 5/-
 16/500v. 4/- 8/450v. 5/6 4/- 32/350v. 4/8
 25/250v. 5/8 8/450v. 5/6 50/350v. 7/-
 25/250v. 1/9 16/450v. 5/6 64/120/275v. 7/6
 50/250v. 2/- 16/450v. 6/- 64/120/350v. 11/6
 50/250v. 2/- 32/32/350v. 4 6 100/200/275v. 12/6

LATEST EMI. 4-SPEED SINGLE RECORD PLAYER. Acos 73 hi-hi stereo and normal crystal pick-up. 8in. motor, heavy turntable. Special Offer, £8.19.6. Post 3/6.

MAINS TYPE SELENUM 300 v. 85 mA, 7/6. **CONTACT COOLED** 250 v. 50 mA, 7/6. 60 mA, 8/6; 85 mA, 9/6; 300 mA, 21/6; 300 v. 27/6. **COILS** Wearite "P" type, 3/- each. Osmor Midget "U" type adj. dust cover, 4/- All ranges. **TELETRON.** L & Med. T.R.P., with reaction, 3/8. **FERRITE ROD AERIALS.** M.W., 8/8; M. & L., 12/6. **T.R.F. COILS A.I.P.** 7/- pair. H.F. CHOKES, 2/6. **FERRITE ROD.** 7in. x 3in., dia. 2/6.

JASON F.M. TUNER COIL SET. 26/-, H.F. 3 coil, aerial coil, Oscillator coil, two I.F. trans. 107 Mc/s. Ratio Detector and heater choke. Circuit book using four 6AM6, 2/6. **COMPLETE JASON F.M. KIT WITH VALVES.** £6.5.0 Model FEMT.

FULL WAVE BRIDGE SELENUM RECTIFIER: 2, 4 or 12 v. 14 amp., 8/8; 3 a. 11/3; 4 a. 17/6; 5 a. 21/6; 6 a. 24/6. **TRANSFORMERS.** Tapped input 200/350 v. for charging at 2, 6 or 12 v., 14 amps., 15/6. 2 amps., 17/6; 4 amps., 22/6. Circuit included. **VALVE and TV TUBE** equivalent books, 6/-.

TOGGLE SWITCHES. S.P. 2/-, D.P. 3/6, D.P.D.T. 4/- **WAVECHANGE SWITCHES**
 3 D. 4-way 2 water long spindle ... 8/6
 2 P. 2-way, or 3 P. 2-way short spindle ... 2/6
 2 P. 6-way, 3 P. 2-way, 4 P. 3-way long spindle ... 3/6
 3 P. 4-way, or 1 P. 12-way long spindle ... 3/8

VALVEHOLDERS. Pax Int. Oct. 4d. EF50, EA50, 6H, 11Z4, 6X4, 12T. Eng. and Amer. 4.5, 6 and 7 pins. 1/- **MOULDED MAZDA** and Int. Oct., 6d. **6Y8.** 88A, 88C, 89A, 9d. 87G with oct. can. 1/6. **89A** with can. 1/9. **CERAMIC EF50, 87G, BA.** Int. Oct. 1/-; S.CANS 87G, 89A, 1/- ea.

RADIO COMPONENT SPECIALISTS

OUR ONLY ADDRESS
337 WHITEHORSE RD., WEST CROYDON
 Post and Packing 1/-, over £2 free. (Export post Extra.) C.O.D. 1/6. (Wed. 1 p.m.) THO 1665. Buses 133 or 68