


DECEMBER 1983

Australia \$1.80: New Zealand \$2.10: Malaysia \$5.50: I.R. £1.98 (inc. VAT)

90p

TELEVISION

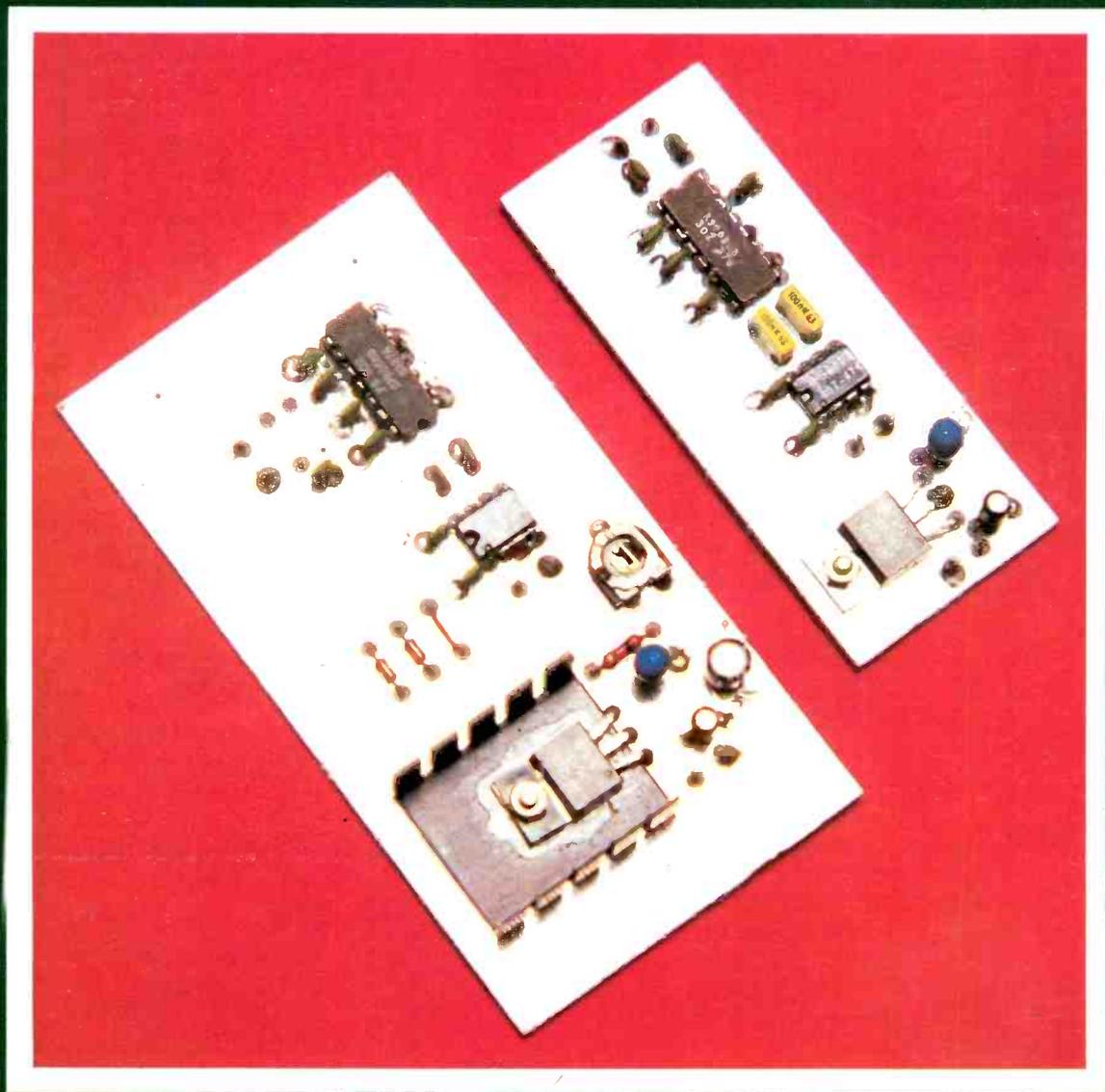SERVICING-VIDEO-CONSTRUCTION-DEVELOPMENTS



PRACTICAL PRESCALER MODULES
SERVICING THE THORN 1600 CHASSIS
UNDERWATER TV • VCR CLINIC
ADDING CONTINENTAL SOUND
AN UNUSUAL CHOPPER CIRCUIT

Interested in Television Servicing?

Try a ZED Pack. Effect Repairs at Minimum Cost.

Z1	300 mixed $\frac{1}{2}$ and $\frac{1}{4}$ watt and miniature resistors	£1.95	Z20	10 Assorted switches including: Pushbutton, Slide, Multipole, Miniature etc. Fantastic Value	£1.20	Z44	TO3 Mounting kits (BU208)	8 for 60p
Z2	150 mixed 1 and 2 watt resistors	£1.95	Z21	100 Assorted Silver Mica caps	£2.20	Z45	TO220 Mounting kits (TIP33)	10 for 60p
Z3	300 mixed capacitors, most types amazing value	£3.95	Z22	10 Mixed TV convergence Pots	£1.00	Z46	TO126 Mounting kits (BD131)	12 for 60p
Z4	100 mixed electrolytics	£2.20	Z23	20 Assorted TV Knobs including: Push Button, Aluminium and Control types	£1.20	Z47	Pack of each Mounting kit. All include insulators and washers	£1.50
Z5	100 mixed Polystyrene Capacitors	£2.20	Z24	10 Assorted Valve bases B9A, EHT, etc.	£1.00	Z48	3a 1000v Diodes (IN5408 type)	8 for £1.00
Z6	300 mixed Printed Circuit Components	£1.95	Z25	10 Spark Gaps	£1.00	Z49	Brushed Aluminium Push Button Knobs, 15mm long x 11mm Diam. Fit standard $3\frac{1}{2}$ mm square shafts	10 for £1.00
Z7	300 mixed Printed Circuit resistors	£1.45	Z26	20 Assorted Sync Diode Blocks	£1.00	Z50	Chrome finish 10mm x 10mm Diam as above	10 for £1.00
Z8	100 mixed High Wattage Resistors, wirewounds etc.	£2.95	Z27	12 Assorted IC Sockets	£1.00	Z51	Aluminium Finish, Standard Fitting Slider Knobs, (Decca)	10 for £1.00
Z9	100 mixed Miniature Ceramic and Plate caps	£1.50	Z28	20 General Purpose Germanium Diodes	£1.00	Z52	Decca "Bradford" Control Knobs Black and Chrome, $\frac{1}{4}$ " Shaft	8 for £1.00
Z10	25 Assorted Potentiometers	£1.50	Z29	20 Assorted Miniature Tantalum Capacitors, Superb Buy at	£1.20	Z53	Tuner P/B Knobs, Black and Chrome. Fit most small Diam Shafts, ITT, THORN, GEC etc.	8 for £1.00
Z11	25 Assorted Presets, Skeleton etc.	£1.00	Z30	40 Miniature Terry clips, ideal for small Tools etc.	£1.00	Z54	Spun Aluminium Control Knobs (ITT) $\frac{1}{4}$ " Shaft, suitable for most sets with recessed spindles	8 for £1.00
Z12	20 Assorted VDR's and Thermistors	£1.20	Z31	5 CTV Tube Bases	£1.00	Z55	14 Pin DIL I.C. Sockets	12 for £1.00
Z13	1 lb Mixed Hardware, Nuts, Bolts, Selftappers, "P" clips etc.	£1.20	Z32	10 EY87/DY87 EHT bases	£1.00	Z56	16 Pin Quil I.C. Sockets	12 for £1.00
Z14	100 mixed New and marked transistors, all full spec, includes: PBC108, BC148, BC154, BF274, BC212L, BC238, BC184L and/or Lots of similar types	ONLY £4.95	Z33	20 PP3 Battery Connectors	£1.00	Z57	16 Pin DIL TOQUIL I.C. Sockets	10 for £1.00
(Z14A)	200 Transistors as above but including power types like BD131, 2N3055, AC128, BFY50 etc.	£9.95	Z34	6 Miniature "Press to Make" Switches, Red Knob	£1.00	Z58	22 Pin DIL I.C. Sockets	10 for £1.00
Z15	100 Mixed Diodes including: Zener, Power, Bridge, Signal, Germanium, Silicon etc. All full spec.	£4.95	Z35	12 Sub Min S.P.C.O. Slide Switches	£1.00	Z59	B9A Valve Bases P.C. Type	20 for £1.00
Z16	20 1N4148 Gen Purpose Diodes	£1.00	Z36	12 Min D.P.C.O. Slide Switches	£1.00	Z60	0.47 Ω $\frac{1}{2}$ Watt Emitter Resistors	40 for £1.00
Z17	20 1N4003 10D2	£1.00	Z37	8 Standard 2 Pole 3 Pos Switches	£1.00			
Z18	20 Assorted Zeners, 1 watt and 400 mw	£1.50	Z38	4 HP11 Batt Holders (2 - 2 Flat type)	4 for £1.00			
			Z39	3.5mm Jack Sockets, switched, enclosed Type	8 for £1.00			
			Z40	100 Miniature Reed Switches	£2.30			
			Z41	100 Subminiature Reed Switches	£4.20			
			Z42	20 Miniature Reed Switches	£1.00			
			Z43	12 Subminiature Reed Switches	£1.00			

High quality COAX PLUGS, silver plated pin, grub screw fixing, 5 for £1
COAX COUPLERS 5 for £1
COAX FLYING SOCKET 3 for £1

ELECTROLYTIC

1 μ f 63v	20 for £1.00
1 μ f 350v	10 for £1.00
2.2 μ f 63v	20 for £1.00
4 μ f 350v*	10 for £1.00
10 μ f 25v	20 for £1.00
22 μ f 16v	20 for £1.00
100 μ f 25v	20 for £1.20
160 μ f 25v*	20 for £1.50
330 μ f 25v	10 for £1.00
400 μ f 40v*	8 for £1.00
470 μ f 25v	10 for £1.00
470 μ f 35v	8 for £1.00
1000 μ f 35v	6 for £1.00
1000 μ f 40v*	5 for £1

*Axial. All others are Radial.

CAN TYPES

22 μ f 375v (3 pin)	50p
50 μ f 250v (3 pin)	50p
100 μ f 350v	80p
2000 μ f 100v	£1.00
1000 μ f 100v	60p
2,200 μ f 40v	60p
2,200 μ f 63v	70p
3,500 μ f 35v	50p
220 μ f 400v ITT/RBM	£1.00
6,800 μ f 70v	£1.00
10,000 μ f 40v	£1.00

R.B.M. USERS LOOK!
 No more messy soldering. 24 pin I.C. sockets for SL901 etc.
SPECIAL OFFER: 5 for £1.00
 100 for £12.50.

SPECIAL OFFERS

100 Assorted Polyester Capacitors, Mullard C296's and others
 160v 400v only £2.00
 100 Assorted Mullard C280's
 Cosmetic imperfections etc. £2.00
 200 Mullard Miniature Electrolytics
 Cosmetic imperfections etc. £2.00
PACK OFF EACH £5.00

12V BULBS on leads, Suitable for most VIDEO RECORDERS.
70p each 4 for £2

CAR RADIO SUPPRESSOR KIT
 Comprises: in line aerial suppressor, power lead suppressor and clock/accessory suppressor. With leaflet.
£1.95 each, 10 for £1.20
 Further Discount on large quantities

ZENER DIODES

0v7, 2v7, 4v3, 4v7, 5v6, 6v2, 6v8, 7v5, 27v, 30v, ALL 400mw.	
10 of one value	80p
10 of each	£6.60
1.3 watt, 12v, 13v, 18v, 47v	
10 of one value	£1.00
10 of each	£3.00

DIODES

25 - 1N4002	£1.00
100 for £2.50	
20 - 1N4003	£1.00
100 for £3.00	
20 - 1N4005	£1.50
100 for £5.00	
20 - 1N4148	£1.00
100 for £2.50	
10 - SKE4F2 06 (600v 2a fast switching)	£1.00
12 - BY127	£1.00
8 x BY255 (3A 1,300V)	£1.00
10 - BA158 (600v 400ma)	£1.00
IN5402 3a 200v	8 for £1.00
6A, 100V, Bridge Rectifier, Very small.	80p ea. 3 for £2.00

I.C.'s

CA270AE	£1.00	6 for £5.00
MC1327P	£1.00	6 for £5.00
TBA120SB	50p each	5 for £2.00
TBA820	£1 each	6 for £5.00
TBA810P	£1.00	6 for £5.00
555 Timer	30p	4 for £1.00
TAA661B	£1.00	6 for £5.00
SN76660N	50p	5 for £2.00

THORN SPARES

"3500" Transductor	£1.20, 3 for £3.00
"3500" Focus Assembly with VDR	£1.50
"8500" Focus Assembly, Rotary type	£1.50, 3 for £4.00
"8500".0022 2000v Line Capacitor	10 for £1.00
"1590 91" Portable metal boost Diode (W11)	5 for £1.00
"1500" Bias Caps 160 μ f 25v	20 for £1.50
"1500" Jelly pot, L.O.P.T. Pinksot	£3.50
"900 950" 3 stick triplers	£1.00, 3 for £2.50
"950" Can. 100 - 300 - 100 - 16 μ f	£1.00

THYRISTOR CONVERGENCE POTS

SS106 (BT106)	75p each
3 for £2.00, 10 for £5.50	
511, 1011, 2011, 3011, 5011, 10011, 20011, 1K, 8 of one type	£1.00, 8 of each type £6.00.

V.C.R. BATTERY PACKS.
HITACHI PORTABLE V.C.R. Nicad pack. Type VTBP60E £20 each. Brand New and Boxed 3 for £50
THORN "VIDEOSTAR" 3V25/26 Nicad pack. Type VA214. Also suitable for J.V.C. etc. Brand new and boxed. £20 each, 3 for £50.
THORN "VIDEOSTAR" Nicad packs. Same as above but secondhand, untested. Contain 10 "C" size Nicads (HP11) which can be replaced if necessary. £10 each, 3 for £25.

MISCELLANEOUS

BG100 tripler for CVC45 etc. only £3.50
 Line output transformer for RBM823A £4.25 each, 3 for £10.00
 ITT VC200 4P/B Transistor Tuner. Suitable for some Pye and Philips sets, 3 hole fixing £2.75 each
 Decca Bradford Tuner. 5 button type £4.00 each, 4 for £12.00
 UHF Modulator UHF out Video in. Ch. 36. 2 $\frac{1}{2}$ " x 2 $\frac{1}{2}$ " x $\frac{1}{2}$ " complete with 9 foot coaxial lead and plug. With connection data £3.00 each, 2 for £5.00
 GEC Hybrid 2040 series Focus Assembly with lead and VDR rod £2.00 each, 3 for £5.00
 Convergence Panel for above. Brand new leads and plug. £3.00 each
 GEC 2010 Transistor Rotary Tuner with AE, SKT, and leads £1.95 each, 3 for £5.00
 Bush CTV 25 Quadrupler type Q25B equivalent to ITT TU25 30K £3.00 each, 2 for £5.00
 Focus VDR Rods 2 $\frac{1}{2}$ " x $\frac{1}{2}$ ". Suitable for GEC. 75p each, 3 for £2.00
 Decca etc. £12.50 each, 3 for £30.00
 Grundig UHF/VHF Varicap Tuner for 1500GB, 3010GB. £12.50 each, 3 for £30.00
 EHT Lead with Anode cap (CTV) suitable for split Diodes sets 1m long 60p each, 3 for £1.50
 EHT Cable 30p per metre, 10 metres £2.50
 4.433 Mhz CTV Crystals 70p each, 3 for £2
 75 Ω 21 Loudspeaker 60p each, 4 for £2
 6 Mhz sound filters, ceramic 3 pin "TAIYO" type 50p each, 3 for £1.00
 PYE CT200 Control Knobs 8 for £1.00
 Degaus VDRs, 1 $\frac{1}{2}$ " diam, for RBM etc. 5 for £1.00
 Mains Neons 10 for £1.00
 2k2 Screened Resistors.
 White ceramic, 9 watt, with fusible link. 8 for £1.00
 E.H.T. Discharge probe, with heavily insulated handle, with lead and chassis connector. 60p each, 3 for £1.50

UNIVERSAL TEST LEAD KIT

Comprises: Red and black meter leads with 14 interchangeable probes, clips, points, plugs etc with screw threads. ONLY £2.50

I.C. EXTRACTING TOOLS

Small	90p	Large	£1.20
-------	-----	-------	-------


SMART ALUMINIUM FINISHED

$\frac{1}{4}$ " SHAFT KNOBS
 $\frac{1}{2}$ " diam. Ideal for TV or Hi-Fi.
 10 for £1 100 for £8

GEMINI ELECTRONIC COMPONENTS

Dept. TV, The Warehouse, Speedwell Street, London S.E.8.

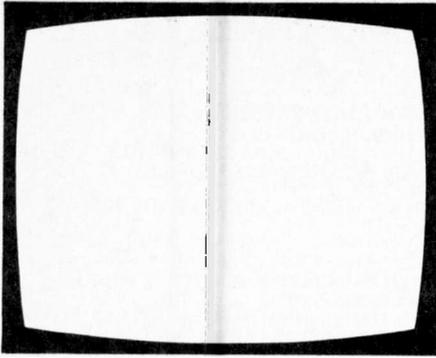Please quote ZED code where shown. Send cheque* or Postal Order. Add 60p P&P and 15% VAT.
 *Schools etc. SEND OFFICIAL ORDER. Allow up to 28 days for delivery. Most orders despatched same day.
 ZED PACKS now available for CALLERS at 50 Deptford Broadway, London, S.E.8.
 Send large S.A.E. for list of Quantity, Prices and Clearance Lines etc.



TELEVISION

December
1983

Vol. 34, No. 2
Issue 398

COPYRIGHT

©IPC Magazines Limited, 1983, Copyright in all drawings, photographs and articles published in *Television* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Television* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

CORRESPONDENCE

All correspondence regarding advertisements should be addressed to the Advertisement Manager, "Television", King's Reach Tower, Stamford Street, London SE1 9LS. Editorial correspondence should be addressed to "Television", IPC Magazines Ltd., King's Reach Tower, Stamford Street, London SE1 9LS.

SUBSCRIPTIONS

An annual subscription costs £11 in the UK, £12 overseas (by surface mail). Send orders with payment to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex, RH16 3DH.

BINDERS AND INDEXES

Binders (£4.50) and Indexes (45p) can be supplied by the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. Prices include postage and VAT. In the case of overseas orders, add 60p.

BACK NUMBERS

Some back issues are available from the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF at £1.10p inclusive of postage and packing.

QUERIES

We regret that we cannot answer technical queries over the telephone nor supply service sheets. We will endeavour to assist readers who have queries relating to articles published in *Television*, but we cannot offer advice on modifications to our published designs nor comment on alternative ways of using them. All correspondents expecting a reply should enclose a stamped addressed envelope.

Requests for advice on dealing with servicing problems should be directed to our Queries Service. For details see our regular feature "Service Bureau". Send to the address given above (see "correspondence").

this month


- 65 Leader**
- 66 Practical Prescaler Modules** *C. Toms*
Two economical prescaler designs capable of handling signals in the ranges 150MHz-2GHz and 150-650MHz. The prescalers are available in kit form or ready built and tested.
- 68 Letters**
- 68 Readers' PCB Service**
- 71 TV Fault Finding**
Reports on TV faults from Mick Dutton, Peter H. Dolman, H. Davies and John Coombes.
- 72 Teletopics**
News, comment and developments.
- 74 VCR Clinic**
A modification devised by Richard Roscoe to cure tape slack in the JVC HR7300/Ferguson 3V30 range of machines plus fault reports from B. Atkinson, G3TEP, Les Harris and John Coombes.
- 76 An Unusual Chopper Circuit**
The chopper power supply used in the latest ITT large-screen chassis (CVC1200 series) provides mains isolation and uses a rather unusual circuit. A brief account of its mode of operation.
- 77 Underwater TV** *Peter Graves*
Getting TV pictures from beneath the sea presents many problems. An account of current practice in this field.
- 80 Adding Continental Sound** *William Falkland*
A simple method of providing a switched 5.5/6MHz intercarrier sound channel for UK or system B/G sound reception.
- 82 Quick Checks Q and A, Part 3** *S. Simon*
How to tackle common fault conditions in the Thorn 3000/3500 series chassis.
- 83 Christmas Story** *Bryon Pascoe*
What happened last time round. A story with a moral about VCRs.
- 84 Satellite TVRO System, Part 3** *Nick Harrold*
This time the sound section of the receiver, including an expander circuit for correct reception from the Gorizont satellite.
- 86 Servicing the Thorn 1600 Chassis** *John Coombes*
A fault-finding guide on this popular 17in. monochrome transportable chassis.
- 88 Long-distance Television** *Roger Bunney*
Reports on DX reception and conditions and news from abroad.
- 91 The Betamax Video system, Part 5** *Eugene Trundle*
The sound section in Betamax machines and a survey of the main models using this format, with notes on some of their quirks.
- 94 Who's Cognizant?** *Les Lawry-Johns*
More admissions on how to do simple jobs the difficult way.
- 95 Next Month in Television**
- 96 Service Bureau**
- 97 Test Case 252**

OUR NEXT ISSUE DATED JANUARY WILL
BE PUBLISHED ON DECEMBER 14

MANOR SUPPLIES

NEW MKV CHEQUERBOARD & PAL COLOUR TEST GENERATOR FOR TV & VCR.

TEST DEMONSTRATIONS AT 172 WEST END LANE

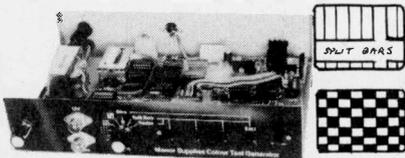


- ★ 40 different patterns and variations.
- ★ Broadcast transmission accuracy (fully interlaced sync pulses with correct picture blanking).
- ★ EBU colour bars, BBC colour bars, whole rasters & split bars (specially useful for VCR service), white, yellow, cyan, green, magenta, red, blue and black.
- ★ Chequerboard.
- ★ Mono outputs with border castellations, cross hatch, grey scale, vertical lines, horizontal lines and dots. UHF modulator output plugs straight into receiver aerial socket.
- ★ Additional video output for CCTV & VCR.
- ★ Facilities for sound output.
- ★ Easy to build kit. Only 2 adjustments. No special test equipment required.
- ★ Mains operated with stabilised power supply.
- ★ All kits fully guaranteed with back-up service.
- ★ Also available with VHF Modulator.

Price of Kit **£80.50**
 Standard Case (10½"×6½"×2½") **£5.50**
 De Luxe Case (10"×6"×2¼") **£8.50**
 Optional Sound Module (6MHz or 5.5MHz) **£4.50**
 Built & Tested in De Luxe Case including Sound Module **£120.75**

SPECIAL TEST REPORT TELEVISION DEC. 1982
 Post/Packing £2.50
 All above prices include VAT 15%

PAL COLOUR BAR GENERATOR (Mk4)

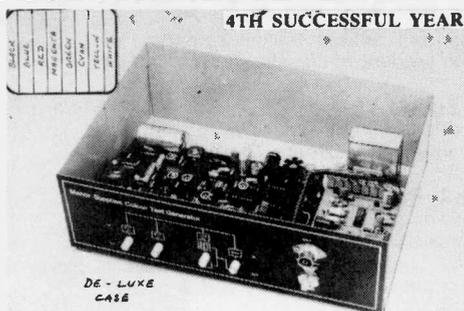

- ★ Output at UHF, applied to receiver aerial socket.
 - ★ In addition to colour bars R-Y, B-Y etc.
 - ★ Cross-hatch, grey scale, peak white and black level.
 - ★ Push button controls, battery or mains operated.
 - ★ Simple design, only five i.c.s on colour bar P.C.B.
- PRICE OF MK 4 COLOUR BAR GENERATOR KIT £34.50. DELUXE CASE £8.50. BATT HOLDERS £3.20 OR MAINS SUPPLY KIT £4.80 (Combined P&P £1.80).**

MK 4 DE LUXE (BATTERY) BUILT & TESTED **£66.70 + £1.80 P & P.**
 MK 4 DE LUXE (MAINS) BUILT & TESTED **£78.20 + £1.80 P & P.**
 VHF MODULATOR (CHI to 4) FOR OVERSEAS **£6.60.**
 EASILY ADAPTED FOR VIDEO OUTPUT & C.C.T.V.
 (ALL PRICES INCLUDE 15% VAT)

MANOR SUPPLIES TELETEXT ADAPTOR KITS

MK 1 (Texas XMII) Cable remote control **£158.70** p.p. £2.80.
 MK 2 (Philips/Mullard) Infra-red remote control **£198.40** p.p. £2.80.
 Further details on request.

Goods available if in stock immediately over shop counter (Mail order between 3 days and 1 week from receipt of order).

TV SERVICE SPARES

BACKED BY TWENTY YEARS EXPERIENCE & STAFF OF TECHNICAL EXPERTS

TELEVISION MAGAZINE PROJECT PARTS

NEW COLOUR PORTABLE TV
 MONO PORTABLE TV, SMALL SCREEN MONITOR
 LISTS AVAILABLE, PANEL TEST SERVICE

PHILIPS UHF MODULATOR (AUDIO & VIDEO INPUT) **£17.25** p.p. £1.00.
 MULLARD TELETEXT DECODER + INTERFACE suitable for TX9, TX10 **£69.00** p.p. £1.80. (Decoder only **£57.50** p.p. £1.80).
 SAW FILTER IF AMPLIFIER PLUS TUNER COMPLETE AND TESTED for T.V. SOUND & VISION **£32.80** p.p. £1.20.
 THORN TX9, TX10 SAW FILTER IF PANEL **£9.80** p.p. 80p.
 PAL DECODER KIT FOR RGB MONITORS **£31.00** p.p. £1.00.
SPECIAL OFFER TEXAS XMII TELETEXT DECODER NEW & TESTED, AT REDUCED PRICE £46.00 p.p. £1.60.
 PHILIPS-PYE G11 TYPE TELETEXT DECODERS **£28.75** p.p. £1.60.
 TELETEXT 23 BUTTON DE-LUXE HANDSET WITH 5 YDS. CABLE **£7.80** p.p. £1.20. XMII STAB. POWER SUPPLY **£4.40** p.p. £1.20.
 CROSS HATCH UNIT KIT, AERIAL INPUT TYPE, INCL. T.V. SYNC AND UHF MODULATOR. BATTERY OPERATED. ALSO GIVES PEAK WHITE & BLACK LEVELS. CAN BE USED FOR ANY SET **£12.65** p.p. 60p. (ALUM CASE **£2.90** DE LUXE CASE **£5.50** p.p. £1.20.)
 ADDITIONAL GREY SCALE KIT **£3.35** p.p. 45p.
 UHF SIGNAL STRENGTH METER KIT **£21.60** (VHF version also available). ALUM CASE **£2.90** DE LUXE CASE **£8.50** p.p. £1.80.
 CRT TESTER & REACTIVATOR PROJECT KIT FOR COLOUR & MONO **£29.40** p.p. £2.00.
 BUSH A823 POWER BASIC PCB. IN FIBREGLASS **£6.40** p.p. £1.00.
 BUSH Z718 BC6100 SERIES IF PANEL **£5.75** p.p. 90p.
 BUSH A816 IF PANEL (SURPLUS) **£1.90** p.p. 90p.
 DECCA 80, SERIES, IF FRAME T.B. **£5.75** each p.p. £1.40.
 DECCA 80, 100 LINE SCAN UNIT salvaged **£11.50** each p.p. £2.00.
 GEC 2040 Convergence panels, Decoder panels **£2.88** each p.p. £1.80.
 GEC 2040 IF PANELS **£3.22** p.p. £1.60.
 THORN TX9 PANELS ex factory for small spares. Includes I.C.s & Semiconductors etc. **£5.75** p.p. £2.00.
 THORN TX9 PANELS salvaged ex factory for spares incl. LOPT & mains transformers **£11.50** p.p. £2.80.
 THORN TX9 PANELS ex factory salvaged complete cond **£23.00** p.p. £2.80.
 THORN TX10 T.B. PANELS salvaged ex factory **£17.25** p.p. £3.00.
 THORN TX10 SIGNAL BOARDS salvaged ex factory **£17.25** p.p. £2.00.
 TX10 type Remote & tuning control panel **£8.50** p.p. £1.50.
 THORN 3000 LINE T.B., POWER PCB **£5.75** each p.p. £1.30.
 THORN 8000/8500 IF/DECODER PANELS salvaged **£3.70** p.p. £1.80.
 THORN 8000/8500 FRAME T.B. PANELS salvaged/spares **£2.88** p.p. £1.40.
 THORN 9000 SERIES TOUCH TUNE REMOTE CONTROL UNIT PLUS ULTRASONIC TRANSMITTER HANDSET **£19.32** p.p. £1.84.
 THORN 9000 IF/DECODER PANELS Salvaged **£5.75** p.p. £1.60.
 PHILIPS G8/G9 IF/DECODER Panels for small spares **£1.75** p.p. £1.40.
 G8 Decoder panels salvaged **£4.25**. Panels for spares **£2.00** p.p. £1.40.
 G9 Scan Panel. Basic PCB in fibreglass **£16.68** p.p. £1.80.
 GRUNDIG 8630 Series Varicap Tuners **£7.82** p.p. £1.00.
 VARICAP, U321, U322, ELC 1043/06 ELC 1043/05 **£7.82** p.p. 80p; G.I. type (equiv. 1043/05) **£4.00** p.p. 60p. MAKERS VARICAP CONTROLS Pye CT200 4PSN **£8.60**, A823 4PSN **£5.50**, Decca 6PSN **£6.70** p.p. 80p etc.
SPECIAL OFFER ELEVEN POSITION VARICAP CONTROL UNIT UHF/VHF £2.10 p.p. £1.00.
 BUSH "Touch Tune" Varicap Control Z179, Z718 types **£4.40** p.p. 95p.
 VARICAP UHF-VHF ELC 2000S **£9.80**. BUSH TYPE **£7.82** p.p. 85p.
 VARICAP VHF MULLARD ELC 1042 **£7.95** p.p. 80p.
 UHF/625 Tuners, many different types in stock. DECCA Bradford 5 position **£2.88** p.p. £1.80 etc.
 LOPT TESTER Service Dept approved **£17.82** p.p. £1.20.
 LOPTS NEW & GUAR. P/P Mono **£1.35p**, Colour **£1.45p**, Bobbins 80p.

BUSH 161 to 186 (twin panel).....	£6.80	R.B.M. A823	£5.60
BUSH, MURPHY 774 series	£9.80	R.B.M. Z179	£11.30
BUSH, MURPHY A816 series	£9.80	R.B.M. T20, T22	£11.30
FERG., HMV, MARCONI, ULTRA		R.B.M. T20, T22 Bobbin	£6.44
950, 1400, 1500, 1580, 1590, 1591	£6.80	DECCA Bradford (state Mod No)	£10.15
THORN 1600, 1615, 1690, 1691	£10.50	DECCA 80, 100	£10.15
GEC 2000 to 2038 series	£7.80	GEC 2028, 2040, 2100	£6.70
GEC series 1 & 2	£9.20	GEC 2110 Series	£12.20
INDESIT 20/24EGB	£8.80	ITT CVC 5 to 9, CVC20	£11.30
ITT/KB VC 200, 300	£8.80	ITT CVC25, CVC30 series	£10.15
MURPHY 1910 to 2414 (twin panel)	£6.80	PYE 691-697	£11.50
PHILIPS 170, 210, 300 SERIES	£8.80	PYE 713, 715	£7.85
PYE, INVICTA, EKCO, FERR. 368, 169, 569, 769 series	£8.80	PYE 725 (90°) 731 to 741	£10.60
		PHILIPS G8	£10.15
		PHILIPS G9	£11.30
		PHILIPS 570, 571	£7.85
		THORN 3000/3500 SCAN, EHT	£7.85
		THORN 8000/8500/8800	£14.80
		THORN 9000 to 9600	£10.15
		THORN 9800	£21.90


OTHERS AVAILABLE, PRICES ON REQUEST. ALSO F.O.P.T.S. TRIPLERS Full range available. Mono & Colour.

Special Offer: Thorn 1400 5 stick EHT Tray **£1.72** p.p. 65p.
 TRANSDUCTORS suitable for G8, A823, Bradford etc. **£1.72** p.p. 60p.
 6-3V CRT Boost Transformers **£5.80**, Auto Type **£3.20**, p.p. £1.20.
 THORN 3000 Mains TX **£5.75**. 8000 Mains choke **£5.60** p.p. £1.80.
 CALLERS WELCOME AT SHOP PREMISES Telephone 01-794 8751/7346
 THOUSANDS OF ADDITIONAL ITEMS INVITED, ENQUIRIES
 LARGE SELECTION TESTED COLOUR PANELS POPULAR MODELS

MANOR SUPPLIES

172 WEST END LANE, LONDON, N.W.6.

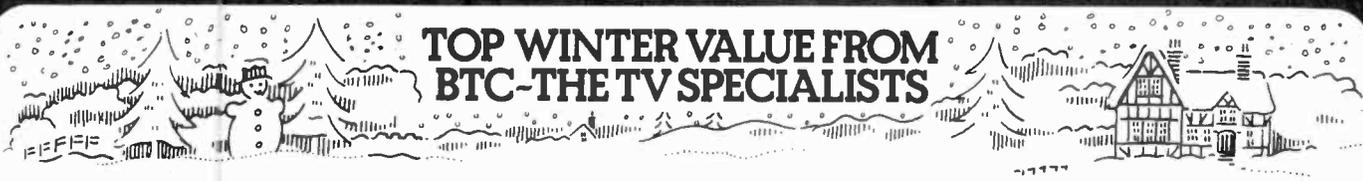NEAR: W. Hampstead Tube Stn. (Jubilee) Buses 28, 158, C11 pass door
 W. Hampstead British Rail Stns. (Richmond, Broad St.) (St. Pancras, Bedford)
 W. Hampstead (Brit. Rail) access from all over Greater London.
 Mail Order: 64 GOLDERS MANOR DRIVE, LONDON N.W.11.
 ALL PRICES INCLUDE VAT AT 15%



**TOP WINTER VALUE FROM
BTC-THE TV SPECIALISTS**

You won't better these BTC bargains!

Top quality sets to set you up for the winter televiewing boom.
Brighten your winter profits with better sets from BTC.

COLOUR

DECCA BFD 30
TELPRO
KORTING
PYE 697, GEC 2040

HYBRIDS

UNTESTED		WORKING	
ONE TO TEN	£15.00	ONE TO TEN	£25.00
ONE TO TEN	£15.00	ONE TO TEN	£25.00
OVER TEN	£12.00	OVER TEN	£21.00

COLOUR

PHILIPS G8's
2-CHIP BUSH/MURPHY
GEC 2110, 8500
3500 VARICAPS
P/BUTTON HITACHI's
18" PHILIPS

SOLID STATES

UNTESTED		WORKING	
ONE TO TEN	£25.00	ONE TO TEN	£40.00
ONE TO TEN	£25.00	ONE TO TEN	£40.00
OVER TEN	£23.00	OVER TEN	£35.00
OVER TEN	£23.00	OVER TEN	£35.00
ONE TO TEN	£23.00	OVER TEN	£35.00

COLOUR

1-CHIP BUSH/MURPHY
THORN 3000, THORN 8000
18" PYE's
ROTARY JAPS

UNTESTED		WORKING	
ONE TO TEN	£20.00	ONE TO TEN	£35.00
ONE TO TEN	£20.00	ONE TO TEN	£35.00
OVER TENS	£18.00	OVER TENS	£30.00

COLOUR

LATER SETS
ie. THORN 9000
TOUCH TUNE SETS
etc.

UNTESTED		WORKING	
ONE TO TEN	£45.00	ONE TO TEN	£55.00
ONE TO TEN	£45.00	ONE TO TEN	£55.00
OVER TENS	£38.00	OVER TENS	£50.00

MONO

SINGLE STANDARD MONO TV's
IN BATCHES OF 20 @£4.00 EACH

SPARES PANELS, TUNERS, LOPTS, TUBES, STANDS, INDOOR AERIALS.
ALWAYS IN STOCK — NEW OR S/HAND ABOVE SPARES INCLUDE BRITISH & CONTINENTAL TV's.
PLEASE RING OR WRITE FOR QUOTES.



**PLEASE
NOTE -15%
VAT ON ALL
PRICES**

0274~306018

CASH & CARRY SPECIAL SERVICE
TO THE TRADE OR ASK ABOUT
SPECIAL DELIVERIES ON LARGE QUANTITIES.

OPENING TIMES MON-FRI
9.00-12.00/1.00-5.45
(CLOSE 4.30 SAT)

BRIARWOOD TRADING COMPANY

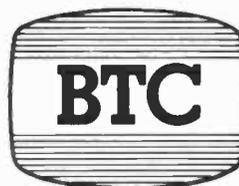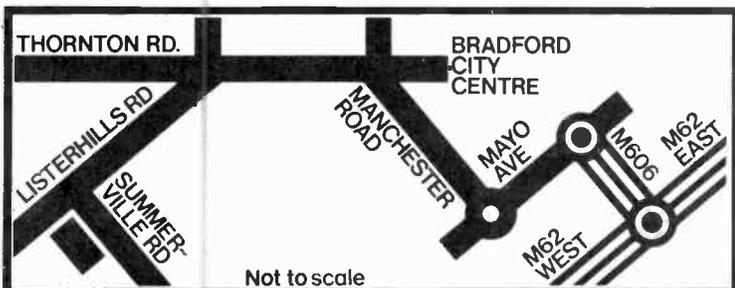

BRIARWOOD TRADING COMPANY
LEGRAMS MILL, SUMMERVILLE ROAD,
BRADFORD BD7 1NH

Switch to the biggest wholesaler of quality late model used TV's

- Thousands of Quality Sets always in stock
- Colour/Mono/VCR's and Audios available
- Murphy/Pye/Philips/Sony/National Panasonic and other big names
- We are big – we buy in bulk – we offer you the keenest prices
- Cash and Carry or we will deliver
- New and used stands always in stock

VISIT OUR NEW SHOWROOM TODAY OR RING US ON 0562 743735



CAMPION THOMPSON
ELECTRICAL WHOLESALERS

Incorporating



Campion House, Franchise Street, Kidderminster, Worcestershire DY11 6RE.

TEL-X

BLACKBURN & SCOTLAND

For The Very Best in Ex-Rental TV's

You've tried the rest, now try us and see for yourselves that we mean the very best in TV's.

PRICES ON REQUEST

Too numerous to list Working and Non-Working.

PHONE US NOW

TEL-X BLACKBURN

Roe Lee Industrial Estate,
Whalley New Road, Blackburn, Lancs.

(0254) 679984

TEL-X SCOTLAND

Pickerings Corner,
Netherton Road, Wishaw, Motherwell.

(0698) 350611

FREE CAREER BOOKLET

Train for success in Electronics Engineering, T.V. Servicing, Electrical Engineering—or running your own business!

ICS have helped thousands of ambitious people to move up into higher paid, more secure jobs in the fields of electronics, T.V., electrical engineering—now it can be your turn. Whether you are a newcomer to the field or already working in these industries, ICS can provide you with the specialised training so essential to success.

Personal Tuition and 80 Years of Success

The expert and personal guidance by fully qualified tutors, backed by the long ICS record of success, is the key to our outstanding performance in the technical field. You study at the time and pace that suits you best and in your own home.

You study the subjects you enjoy, receive a formal Diploma, and you're ready for that better job, better pay.

TICK THE FREE BOOKLET YOU WANT AND POST TODAY

ELECTRONICS ENGINEERING

A Diploma Course, recognised by the Institute of Engineers & Technicians as meeting all academic standards for application as an Associate.

T.V. & AUDIO SERVICING

A Diploma Course, training you in all aspects of installing, maintaining and repairing T.V. and Audio equipment, domestic and industrial.

ELECTRICAL ENGINEERING

A further Diploma Course recognised by the Institute of Engineers & Technicians, also covering business aspects of electrical contracting.

RUNNING YOUR OWN BUSINESS

If running your own electronics, T.V. servicing or electrical business appeals, then this Diploma Course trains you in the vital business knowledge and techniques you'll need.


Name

Address

ICS
ICS
Dept P285,
160 Stewarts Road,
London SW8 4UJ.



01-622 9911
(all hours)

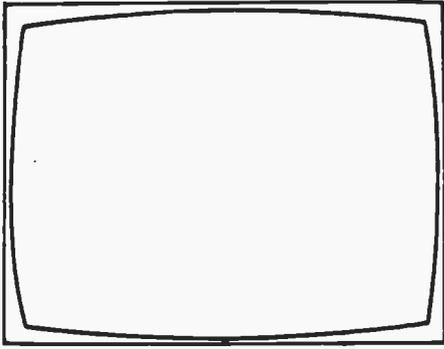

TELEVISION

The World of Instant Piffle

One can't help wondering why the world becomes a worse shambles day by day when we have available this wonderful tool, our much vaunted information technology, that should have brought about an era of sweet reason. Time was when access to more information in itself seemed to be a good thing that would lead to a better world. After all, most bad decisions stem from inadequate knowledge. Increase the amount of information available and we should all be able to make wiser decisions. But there's a difference between knowledge and information. Raw information by itself means little. It has to be put into context and assessed before it can contribute to our understanding. And that takes time.

We seem to have a growing problem here. Information is available to those who need it in vast quantities, while communications have become instantaneous world wide. The two sometimes seem to be making matters worse rather than better however. Instantaneous communications have led people to expect instantaneous answers and decisions. They are getting them - because the communications/information technology available to decision makers seems to impose upon them the need to react immediately. What's the point of having a hot line if you can't make a hot decision? But time is required to arrive at considered decisions. Your computers and satellites don't understand this, and the technology they represent doesn't allow for it. Computers crunch numbers and satellites crunch communications time. The human brain still has a trick or two, but there seems to be the feeling that having created all this technology we should be able to act within the same microsecond time scale. The ultimate daftness now seems to have arrived: obviously ill considered decisions are made by those in authority, and before they or anyone else can think the matter through the decision makers are on TV screens all over the world explaining that there's no alternative.

Sooner or later someone must yell "wait!" We don't want to go back to the situation where it took several weeks to communicate with a distant part of the globe and get a reply. But the technology we increasingly rely upon must be put in its place. At the moment it often seems that the information technology tail is wagging the dog. The result is an increasingly muddled world and increasing difficulty in getting considered policies adopted and put into effect.

There is also, I've noticed, a growing lack of clarity as the amount of information that rains down upon us increases. A statement can be made, retracted, altered, commented upon, reformulated, made non-operative and so on at such a rate that no one can be all that sure what's going on. Sometimes it seems that this is a deliberate ploy to confuse the issue. Then there's a tendency to sort of manhandle information. First it's leaked ("figures to be released later today show that . . ."), after which it suddenly becomes old hat ("yesterday's announcement has led to comment that . . ."). It's going to be damn difficult for future historians to figure out just what was going on towards the end of the twentieth century despite the mountains of data they'll doubtless have at their disposal.

It's difficult to know what can be done about all this. The ultimate horror of course consists of those stories of possible nuclear hostilities due to information being misunderstood, misused or just mistook. It seems urgently necessary for us to put this monster we've created in its place, to make sure that we control the communications system rather than the other way round. I often breathe a sigh of relief nowadays when I hear someone say "no comment".

Within the domestic context information technology has to some extent come to mean the personal computer. The UK has more personal computers per head of the population than any other country. I must be one of a decreasing minority who wonder just what people do with them. The question was put in an interesting article in *The Guardian* recently, and the reply seemed to be not much. You can perhaps regard the personal computer as a cross between a calculator, a glorified typewriter with memory and a video games console. Calculators are cheaper and simpler however, and laboriously typing into a computer's memory information that can be jotted down on a scrap of paper doesn't help all that much. But games are better on a computer than a games console. It seems people do just that, play games with the thing - video games and computer games. This is harmless enough of course, but has one or two interesting implications.

For many people computers have replaced live electronics as a hobby interest. This brings to mind the arguments that once raged in the world of amateur radio. Were you a true ham if you bought your equipment and chose the role of an operator, rather than concentrating on building your equipment, experimenting with it and seeing what it could achieve? A swing away from an interest in live electronics to computers will inevitably go hand in hand with an increasing tendency to regard electronics in black box terms, whether the box is a computer or whatever. Possibly this is inevitable - a consequence of silicon chip technology. So much modern equipment would be totally uneconomic to consider in terms of construction bit by bit. When, one wonders, did the last hi-fi enthusiast solder together his kit amplifier? Inevitable or not, the consequence must be a diminution in the general appreciation of what electronics is all about.

Where all this will eventually lead remains to be seen. For the moment the urgent need is to teach those who use communications technology to do so wisely. It would be nice to see an end to the dominance of instant comment and instant piffle. It would also be nice to think that something could be done about the information clutter in which we now seem to live. But I fear I'm shouting into the wind.

EDITOR

John A. Reddihough

ASSISTANT EDITOR

Luke Theodossiou

ART EDITOR

Roy Palmer

ADVERTISEMENT MANAGER

Roy Smith

01-261 6671

CLASSIFIED ADVERTISEMENTS

Barbara Blake

01-261 5897

PLEASE NOTE

Our next issue dated January will appear well before Christmas, on December 14th, so that you can get your copy before the usual chaotic conditions in the retail trade at this time of the year. Our best wishes to TV/video men everywhere.

HELD OVER

Part 24 of our VCR Servicing series will appear next month.

Practical Prescaler Modules

C. Toms

Two prescaler modules are presented in the present article. Both stem from the frequency counter-timer project featured in the April-June 1983 issues of the magazine.

A prescaler capable of handling inputs in the range 150MHz-2GHz was promised in the previous series of articles - prescaler no. 2. The main reason for the delay in providing details of this has been the difficulty in obtaining supplies of the Plessey SP8668B ECL divider chip. The cost of this i.c. is appreciable - exceeding £40 trade. As a result, it was decided to present an alternative, prescaler 3, which is cheaper to build but has an upper frequency range of 575MHz guaranteed, 650MHz typical. It should be noted that the typical upper figure of 2GHz given for prescaler 2 is assessed, not that specified by Plessey. The SP8668B is guaranteed to work at up to 1.5GHz. The prototype unit exceeded an upper range of 2GHz however. Obviously to achieve an upper range of 2GHz the associated 8629 divider i.c. must be capable of achieving the specified typical operating limit of 200MHz.

Prescaler 2 covers typically 150MHz-2GHz and costs around £55 to build. Prescaler-3 covers typically 150MHz-650MHz and costs approximately £22 to build.

The circuit of prescaler 2 is shown in Fig. 1. The input signal is a.c. coupled to IC1 (SP8668B) via C2. IC1 divides by ten and drives IC2 (SP8629) which divides by 100 (this i.c. was used in prescaler 1). In this way the

required division by 1,000 is obtained, with a capability well in excess of 1.5GHz. Pin diodes D1-2 (input protection) are optional.

The circuit of prescaler 3 is shown in Fig. 2. An SP8680B (IC1) gives division by ten and again operates with an SP8629 to give a total division of a thousand, this time with an upper limit of typically 650MHz. D1-2 are optional.

Figs. 3-6 show the print patterns for the two prescalers and Figs. 7-8 the component layout details. Both prescalers use a "ground-plane" PCB. Care should be taken not to omit any top side connections and to avoid using excessive heat on the i.c.s. The voltage regulator circuit (IC3 and associated components in both circuits) should be assembled and tested *before* the divider i.c.s are soldered in. In the case of prescaler 2, check that VR1 gives a range of 5V to approximately 7.5V, then set back to 5V (VR1 fully anticlockwise). After completing the board assembly by soldering in IC1 and IC2, slowly increase the supply voltage to 6.8V, adjusting VR1 whilst checking that the supply voltage to pins 1 and 8 of IC2 does not exceed 5.5V.

Both prescalers were found to operate perfectly when installed on the main frequency counter-timer board (mounted vertically, to the rear in front of the battery) without extra screening. Prescaler 2 was originally designed to be mounted inside a 60 x 110 x 25mm deep diecast box however. Some readers may wish to take advantage of this extra screening precaution: in this case, don't forget to earth the box. The connections to the main board for both units are as shown in Fig. 11, June 1983 (page 428), with the chassis connections made to the nearest 0V pin on the main board.

WKF Electronics can supply full kits for the prescalers as follows: prescaler 2 £53, prescaler 3 £21. Alternatively the prescalers can be supplied built and tested at £59 for prescaler 2 and £26 for prescaler 3. These prices do not include VAT. The boards for prescalers 2 and 3 are available from Readers' PCB Services Ltd. at £4.50 and £3.50 respectively, inclusive of VAT, post and packing. The address in both cases is Fleet House, Whitwell, Worksop, Notts S80 4TW.

Components list - Fig. 1

C1-9	.01 ceramic	D3-4	1N4148
C10	100µF tantalum	IC1	SP8668B
C11	1µF electrolytic	IC2	SP8629B
C12	47µF electrolytic	IC3	LM2931 T5-0
D1-2	BA379	R1	1k
VR1 470Ω subminiature horizontal preset			

Components list - Fig. 2

C1-8	.01 ceramic	D1-2	BA379
C9-10	0.1 polyester	IC1	SP8680B
C11	100µF tantalum	IC2	SP8629B
C12	1µF electrolytic	IC3	LM2931 T5-0

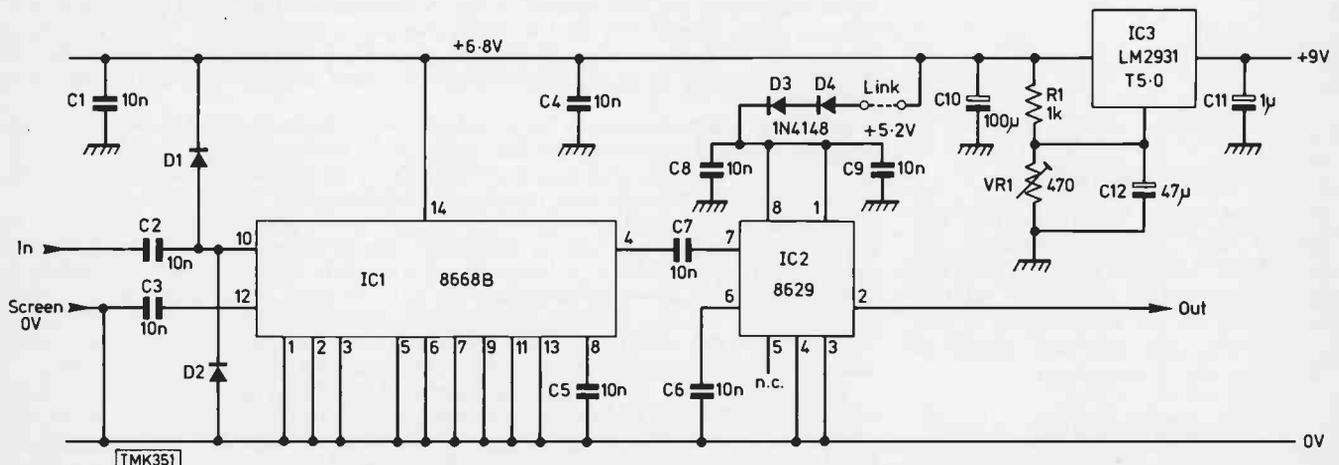


Fig. 1: Circuit diagram, prescaler 2.

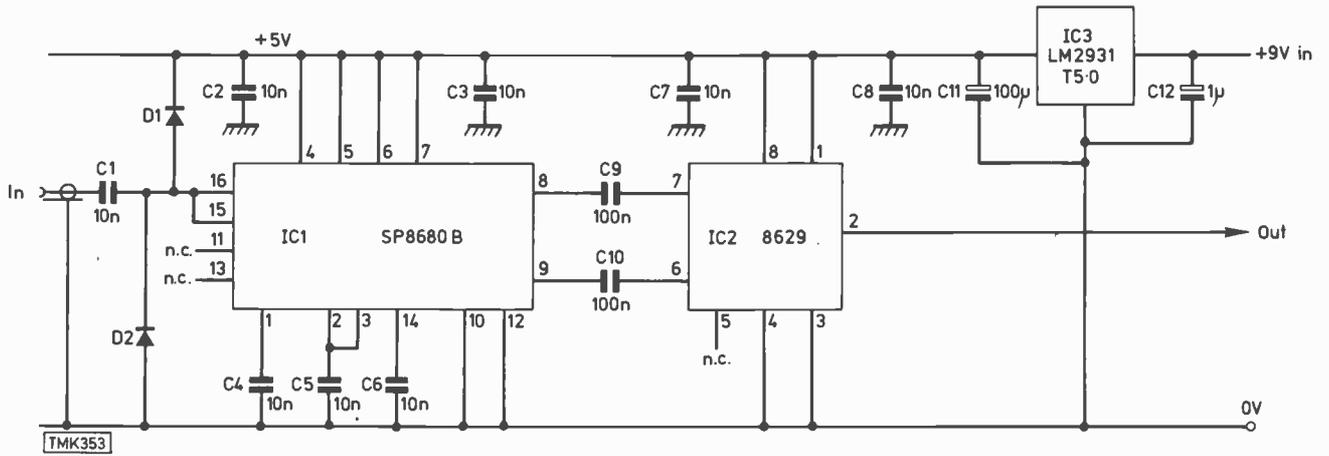


Fig. 2: Circuit diagram, prescaler 3.

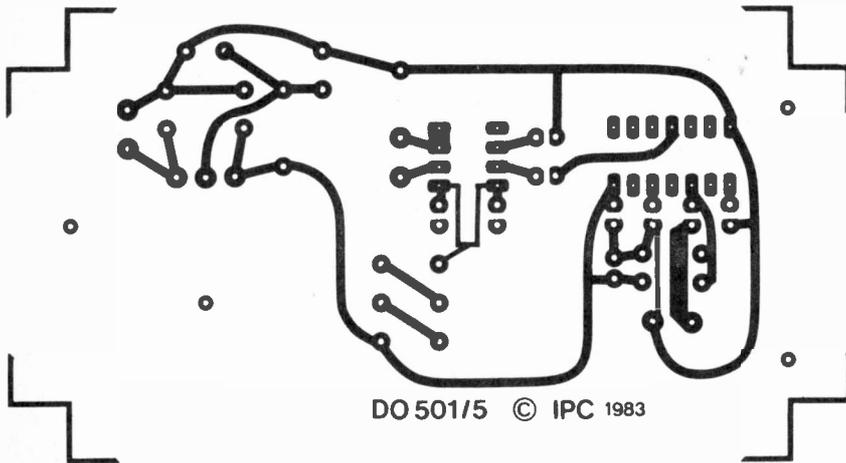


Fig. 3 (above): Prescaler 2 board track pattern (scale 1:1).

Fig. 4 (right): Prescaler 2 board pattern, component side.

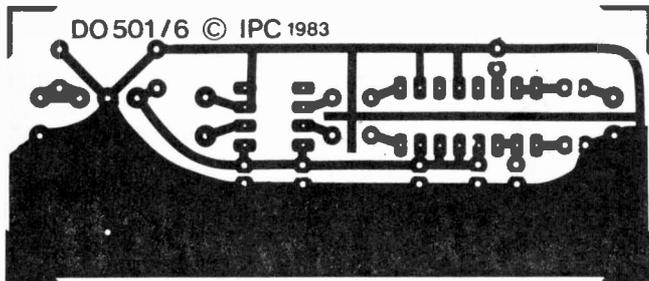
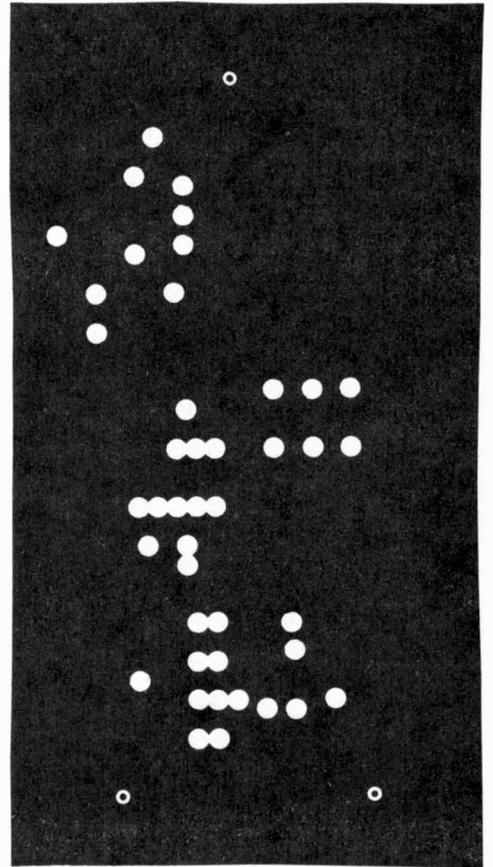


Fig. 5: Prescaler 3 board track pattern (scale 1:1).

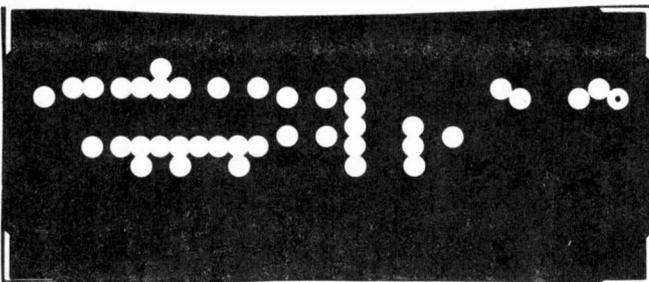


Fig. 6: Prescaler 3 board pattern, component side.

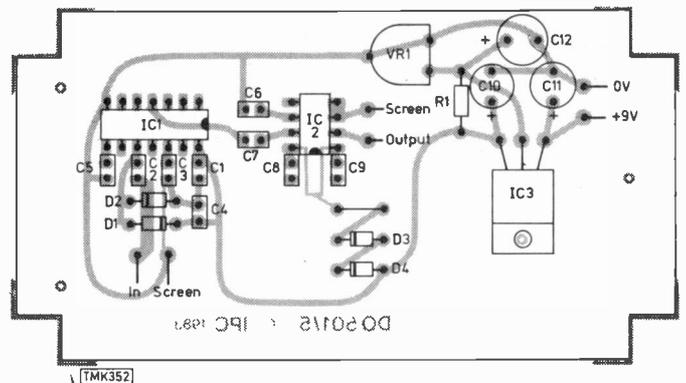


Fig. 7: Component layout, prescaler 2.

Finally a list of corrections and modifications to the original frequency counter-timer project. IC9 on the main panel is type LM2931 T5-0 – shown incorrectly in the components list. R14 and C12 are not shown in the

component layout, Fig. 7. R14 should be fitted in the position shown as a wire link to the right of S7/8. C12's negative lead should be fitted in the vacant hole beside the thick track to the right of S6 – the positive lead goes to the

Letters

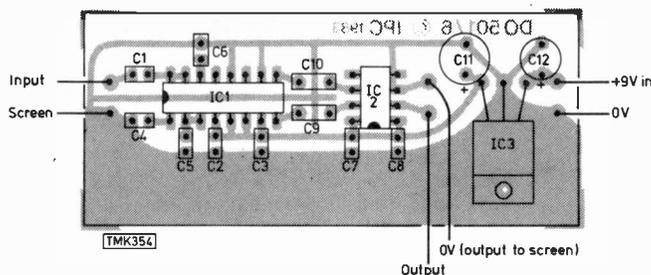


Fig. 8: Component layout, prescaler 3.

5V rail. S1-4 are one interlocking bank; S5-8 are also interlocking but independent of S1-4. S9 is push on, push off. S10 is push to make (momentary). In the main logic circuit (Fig. 6) pins 1 and 2 of IC4b are shown reversed. There are two errors in IC2's pin numbers. The pin to the left of the chassis pin 36 is pin 31, that to the right pin 30. The regulator is shown as IC8 instead of IC9. Also, pin 5 of IC4b connects to pin 10 (number omitted) of IC4a.

IC2 (prescaler 1) should have been shown as type LM2931 Z5-0 in the components list and in Fig. 5. It's shown reversed in Fig. 10, i.e. the flat should face the edge of the board. No socket need be used for IC1.

The regulator output decoupling capacitors C2 (Fig. 6) and C8 (Fig. 5) should be increased in value from 1µF to 100µF (tantalum). Otherwise the regulators can take off at around 15MHz and block the prescalers.

The measurement (113mm) shown at the top of the front panel cutout diagram (Fig. 8) should read 103mm. If the recommended enclosure is used, the front panel slots can be made by scoring with a sharp knife or scalpel. Don't fit the adhesive fascia until all the holes have been made in the plastic panel. Once the adhesive fascia has been fitted, the hole and slot sections can be removed by making diagonal cuts through the aluminium, bending back the unwanted sections, then cutting off with a fine file abraded along the hole and slot edges. The rear edges of the plastic front panel must also be chamfered to allow for the thickness of the fascia within the panel guides.

CLOCK CONVERSION

In the December issue last year Derek Snelling wrote an article on twelve-hour VCR clock conversions. I've recently modified a Sharp VC8300H in this way. The details may be of interest to other readers as they are not given in the manual and Sharp won't even admit to the possibility of doing this.

To convert the clock unit fitted to this machine, which uses an in-house clock-timer microcomputer i.c. type MP2794S, proceed as follows. Remove the top cover (release three screws) and the front of the VCR, then unclip the clock panel and lay it forward without unplugging it. Locate the common print connection to D5009, D5010 (not fitted in this model) and D5011, then cut the print between D5010 and D5011 or remove D5009, whichever is more convenient. Finally reassemble. The clock will now operate in the twelve-hour mode, with a.m. or p.m. illuminated as appropriate.

C. T. Marden,
Ecton, Northants.

LIVE CHASSIS

At last it seems that engineers are ignoring the "half-mains" labels and warnings on sets fitted with mains bridge rectifiers and are treating the chassis in such sets with the respect they deserve. A letter of mine on the hazards associated with these receivers appeared in the November 1977 issue of the magazine. Many manufacturers and technical authors have continued to put about the half-mains 120V story however, some opting for terms like "floating chassis" – hardly floating as the set is clearly tied to the mains supply whichever way it's connected. Thanks then to Keith Cummins for making the danger so clear in his letter in the October issue.

T. I. Birnie, Tech.(C.E.I.).
Lancaster.

TELEVISION READERS PCB SERVICE

All boards are epoxy glassfibre and are supplied ready drilled and roller-tinned.

Any correspondence concerning this service must be addressed to READERS' PCB SERVICES LTD, and not to the Editorial offices.

Issue	Project	Ref. no.	Price
Sept/Oct 1980	New CTV Signals Panel	D077	£9.50
May 1981	Switch-mode Power Supply	D089	£6.75
June 1981	Simplified Signals Board	D088	£10.00
August 1981	Timebase Board	D091	£9.00
August 1981	CRT Base Board	D087	£2.00
September 1981	Remote Control Preamplifier	D085	£1.00
September 1981	Remote Control Interface	D090	£7.00
September 1981	Channel Display Module	D095	£1.00
October 1981	Remote Control Transmitter	D084	£4.00
October 1981	TV Pattern Generator	D094	£6.50
December 1981	Clock-timer Display Board	D092	£6.50
December 1981	Clock-timer Main Board	D093	£10.00
March 1982	TV Sound Tuner	D098	£6.00
May 1982	LOPT Tester	D099	£2.50
May 1983	Frequency Counter Main Board	D0501/1	£15.00
May 1983	Frequency Counter Display Board	D0501/2	£1.00
June 1983	Frequency Counter Prescaler - 1	D0501/3	£1.00
June 1983	Frequency Counter Preamplifier	D0501/4	£1.00
June 1983	In-Situ Transistor Tester	—	£1.00

Send orders to:
Readers' PCB Services Ltd.
(TV),

**Fleet House,
Welbeck Street,
Whitwell,
Workshop,
Notts.**

Prices include VAT, post and packing. Cash with order.

AC128	39p	BD386	68p	MJE182	47p
AC131	40p	BD592	1.20	MJE340	50p
AC138	40p	BD589	1.20	MJE520	65p
AC141K	39p	BD677G	1.35	MJE2955	1.50
AC142K	38p	BF137	20p	MJE3055	1.50
AD161	32p	BF153	20p	NK1241	8p
AD162	32p	BF154	25p	NK1276	20p
AD263	1.05	BF167	24p	NK1453	1.65
AF139	38p	BF173	29p	PN107	7p
AF239	41p	BF181	30p	RI038	80p
AU113	2.10	BF194	16p	RI039	80p
BC107	15p	BF197	15p	R2008B	1.80
BC108	15p	BF198	15p	R2010B	1.10
BC109	15p	BF199	15p	R2010	70p
BC115	15p	BF223	18p	R2255	1.30
BC117	21p	BF238	20p	R2305	80p
BC125	26p	BF240	9p	R2322	50p
BC142	30p	BF241	21p	R2323	50p
BC143	31p	BF255	10p	R2443	25p
BC147	12p	BF256S	20p	RCA16446	30p
BC148	12p	BF257	28p	RCA16599	1.25
BC153	16p	BF259	28p	RCA16600	1.40
BC154	16p	BF271	25p	RCA16799	1.13
BC157	12p	BF274	11p	RCA16800	1.42
BC158	12p	BF337	29p	RCA16802	1.38
BC159	15p	BF362	50p	SI299	2.25
BC171	9p	BF391	21p	2N800D	1.25
BC174B	23p	BF412	16p	56800A/B	3.50
BC182LB	12p	BF422	47p	25A473	1.30
BC184LC	12p	BF450	49p	T6052V	1.30
BC208	9p	BF459	40p	T6053V	1.30
BC213L	12p	BF461	59p	T9039V	1.25
BC237	12p	BF596	15p	T9010V	1.45
BC238	8p	BF694	16p	T9053V	1.30
BC250A	15p	BF881	29p	T9054V	1.00
BC251	8p	BF887	25p	T9039V	1.10
BC307	10p	BF742	30p	TIP31	35p
BC308	8p	BF743	30p	TIP41A	45p
BC309	14p	BFX38	40p	ZTX550	30p
BC347	17p	BFY51	34p	2N3810	10p
BC394	8p	BFY52	34p	2N3904	24p
BC454	8p	BRC1883	1.43	25A473	1.30
BC455	8p	BU105	1.00	25A564	1.0p
BC456	10p	BU126	1.10	25B187	48p
BC460-6	40p	BU207	1.05	25C109A	19p
BC463	22p	BU208	1.15	25C388A	20p
BC546	8p	BU208A	1.15	25C460	37p
BC549	8p	BU326A	1.30	25C394A	18p
BC559	8p	C1172B	9p	25C495F	63p
BC595	8p	C1129	9p	25C734	48p
BCX33	22p	E5386	14p	25C784	51p
BCX34	11p	E9005	25p	25C785R	12p
BD131	30p	ME0404	8p	25C1162	48p
BD222	48p	ME0412	8p	25C1957	79p
BD232	50p	ME0602	8p	25C2570	27p
BD244	85p				

300 Mixed Resistors	1.50
300 Mixed Capacitors	1.50
150 Mixed Electrolytics	2.00
100 W/W Resistors	1.00
20 Mixed Conv Pots	1.00
40 Mixed Pots	1.50
20 Mixed Sliders	1.00
40 Mixed Presets	60p
20 Mixed VDR & Thermistors	1.00
20 Mixed Ferrite Cores	50p
100 Mixed Ceramic Discs	1.00
20 Mixed Valve Bases	1.00

AERIAL SOCKETS	
AE Socket & Lead, Pye, ITT, Thorn	25p
AE Socket & Lead GEC	25p
AE Socket & Lead. (long) GEC	25p
AE Socket & Lead. Pye 691/693	25p
AE Socket & Lead. Philips KT3	25p
AE Socket & Lead. Thorn coil portable	25p
AE Socket & Lead. (long) Pye 725/731	25p
AE Socket & Lead. ITT CVC32, etc	25p
UHF TV Aerial for portable	50p
Indoor Aerial Parabolic Type Reflector to Help Combat Ghosting Problems	2.50
Line Connectors	38p
Coax Plugs	10 for 1.65
Band Change Switch Assy. Pye 725	40p
Flush Mounting TV/FM Diplexer	1.00
Switched Flush Fitting Aerial Outlet	1.00

FUSES	
50MA 20mm 10 for 70p	250MA 10 for 65p
315MA A/S 10 for 50p	750MA 10 for 65p
500MA 10 for 50p	7A 10 for 50p
1A 10 for 50p	10A 10 for 50p
2.5A 10 for 1.00	20A 10 for 50p
3.15A 10 for 1.00	50A 10 for 50p

THICK FILM RESISTOR UNITS	
3500 Thorn (5 Pin Connection) video	1.70
4000 Thorn (4 Pin Connection)	1.90

Thorn 8/8K5 ex equip panels	
untested	
PSU	2.88
FTB	3.75
Decoder	4.00
Thorn 9K ex equip panels	
untested	
PSU	12.00
Decoder	5.00
Thorn 9K6 ex equip panel	
untested	
Decoder	5.75
Thorn TX9 main panel	
Complete (no tuner) ex-factory	11.00

CAN TYPES	
0.2MF 250V	50p
2MF 250V	50p
22MF 275V	50p
50MF 275V	50p
100MF 150V	65p
100MF 250V	70p
100MF 450V	75p
220MF 400V Thorn 9K	95p
220MF 450V Thorn 4K	250MF 35V 65p
400MF 350V Thorn 8K	300MF 40V 65p
800MF 250V Print type	80p
800MF 250V	70p

CAPACITORS	
3.3PF	350V 3000PF 2KV
6.8PF	63V 3300PF 250V
8.2PF	350V 4700PF 400V
10PF	350V 0.047MF 500V
12PF	1000V 0.075MF 2KV
22PF	63V 0.1MF 250V
30PF	63V 0.1MF 600V
47PF	350V 0.15MF 400V
182PF	63V 0.2MF 200V
250PF	2000V 0.2MF 250V
330PF	63V 0.22MF 250V
330PF	160V 0.47MF 400V
330PF	8KV 1MF 250V
470PF	250V 1MF 600V
560PF	63V 22MF 400V
1000PF	250V 33MF 250V
1500PF	250V 39MF 250V
1800PF	160V 47MF 250V
2700PF	63V

Any 10 @ £1.00

10 Spark Gaps	1.00
10-16 pin Quil IC Socket	90p
20 Assorted TV Knobs	1.00
10-16 pin Quil to Dil IC Socket	90p
100 Mixed Diodes	1.00
50 Mixed Mica Washers	65p
300 Mixed Resistors & Capacitors	1.50
10-16 pin Dil to Dil IC Socket	1.00
50 Electrolytics & 50 Capacitors	1.00
50 Mixed Poly Capacitors	1.00
30 Mixed Neons & Bulbs	1.00

Thorn Mains TX 3000/3500	7.50
Thorn Mains TX 8000/8500	10.00
Thorn S.O.P.T 8000/8500	3.50
Thorn Scan TX 3000/3500	6.00
Thorn EHT TX 3000/3500	6.00
Thorn LOPT 960	12.00
Thorn LOPT 1615	7.25
Thorn LOPT 1590/91	7.25
Thorn LOPT 1690/91	7.25
Thorn LOPT 1690/91	9.80
Thorn LOPT 8500	9.80
Thorn LOPT TX9	9.85
Thorn LOPT 9800	17.00
Pye LOPT 713	10.00
Pye LOPT 725	9.85
Pye LOPT 169	9.70
GEC LOPT 3113	14.75
Diode Split LOPT AT2076/35	7.45
Sanyo LOPT AM-WM-21	6.75
Sanyo LOPT AM-WM-4	7.30
Philips LOPT G8	7.80
Sanyo LOPT (CV21) 4-2751-44700	9.60
ITT LOPT CVC5-9	5.00
ITT LOPT CVC45	9.75
Baird 8750	10.25
Baird 8752	10.25
Korting AZ9100	10.25
Korting B92-170	10.25
Korting AZ2101	10.25
Korting AZ2103	10.25
Korting ZTR1001	10.25
Siemens V1155	11.75
Siemens V1823	11.75
Zanussi BS2222	10.25
Zanussi BS2223	10.25
Salora F9057	10.25
Salora F9029	10.25
Hitachi CNP160	9.85

INTEGRATED CIRCUITS	
BRC1330	1.40
BRC3064	1.00
BRC/M/200	1.00
BRC/M/300	1.00
CA3060	1.58
LM1303P	1.48
MD231B	2.20
MD237B	2.00
MC1239B	2.86
MC1327AP	1.25
MC1358P	1.30
MC1455P	18p
MC14516BSCP	60p
SAA1025	7.20
SAA1124	4.50
SAA5010	1.80
SL432A	1.80
SL1430	2.50
SN15846N	60p
SN74123N	65p
SN74154N	1.40
SN76001N	1.40
SN76110N	1.14
SN76013ND	1.80
SN76023N	1.80
SN76033N	2.00
SN76115N	2.00
SN76131N	1.58
SN76229N	1.25
SN76271N	1.00
SN76530P	1.30
SN76545	1.40
SN76622N	1.00
SN76660N	80p
SN76666N	75p
SN76744	1.92
TA7117P	1.00
TA7109AP	2.80
TA7100A	1.40
TBA120B	1.20
TBA1205	1.20
TBA120U	1.00
TBA395	1.00
TBA480Q	1.40
TBA500	2.65
TBA510	2.50
TBA510A	2.66
TBA510B	1.30
TBA510C	1.25
TBA510D	1.40
TBA510E	1.75
TBA510F	1.40
TBA510G	1.40
TBA510H	1.40
TBA510I	1.40
TBA510J	1.40
TBA510K	1.40
TBA510L	1.40
TBA510M	1.40
TBA510N	1.40
TBA510O	1.40
TBA510P	1.40
TBA510Q	1.40
TBA510R	1.40
TBA510S	1.40
TBA510T	1.40
TBA510U	1.40
TBA510V	1.40
TBA510W	1.40
TBA510X	1.40
TBA510Y	1.40
TBA510Z	1.40

DIODES	
AA112	8p
AA119	8p
AA143	8p
BA1115	14p
BA154	8p
BB103	8p
BF303	46p
BT106	1.50
BT116	1.00
BY127	12p
BY204	26p
BY298	22p
BYX22/400	30p
IN60	8p
IN620	8p
IN4001	4p
IN4002	4p
IN4003	4p
IN4004	5p
IN4005	5p
IN4006	5p

EHT TRAYS	
Thorn 3000	5.50
Thorn 8000	3.50
Thorn 8500	6.00
Thorn 9000	5.00
Thorn 9600	6.00
Thorn 900/950	1.50
Thorn 1500 3 stick	1.80
Pye 3R5+15+45 (713)	63p
Pye 713 4 lead	5.83
Pye 713 5 lead	5.97
Pye 725	6.35
Decca Bradford	5.00
Baird 8750	7.10
Korting AZ9100	7.10
Philips G8 (520)	6.50
Philips G8 (550)	6.50

SWITCHES ETC	
AM-LS-200 Mono Scancoils Sanyo	1.00
M-LS 145 Mono Scancoils Sanyo	1.00
4-2761-44570 Scancoils Sanyo	1.00
Thorn 4000 Coil L401	1.00
Thorn 4000 Coil L701/2/3	12p
Pye 713 Coil L831/832	65p
Philips G8 Coil L482 Late Type	90p
Philips G9 Luma Delay Line	90p
Pye 713 Luma Delay Line	90p
Convergence Yoke Assy AT1023/05	5.90
Rank A823 4 P/B Assy	5.80
ITT CVC8 On/Off Switch	65p
Thorn 3500 6 P/B Assy + Leads	1.75
ITT CVC9 On/Off Switch + Relay	90p
Philips G8 On/Off Switch	65p
Thorn 3/3500 A1 Switch	50p
Thorn 4000 A1 Switch	50p
Korting Shift Pot 50Ω	65p
2.5A Push to make on/off switch	15p

Thorn 10Ω 20W (3500) R751 Safety Resistor	75p
Pye 713 Speaker 5" x 3" 70Ω	1.00
Pye 713 Complete Tube Base Panel with Focus Slider & Leads	2.75
Pye 713 Control Knobs	4 for 50p
Tube Base Socket ITT CVC32	45p
Tube Base Socket Thorn 3000/8000 etc	50p
IC Insertter 16 Pin	50p
Large IC Extractor	50p
Crystal 4.43MHz	65p
EHT Lead & Cap for Split Diode Lopt	90p
Anode Cap	47p
Sanyo Anode Cap Assy + Lead. 12TCD-CT-1G65p	
Degauss Thermistors. PT37P. ITT/GEC	35p
Degauss VDR E2990/HP230 3000/8000	25p
Casters Set of 4	1.90
Double Fuse Holder on Small Pax Board 20mm type	10p
Single Fuse Holder on Small Pax Board 20mm type	5p
Direct Panel Mounting 20mm Fuse Clips (pair)	15p
Single Fuse Holder on Small Pax Board. As per early 3000 mains input	6p
EHT Cable	Metre 25p
13A Plugs	12 for 4.80
TX9 Tube Base and Panel	65p
3K PSU PL22 edge connector. + Lum to PSU (New)	40p
9K5 Complete Lum with all Plugs (New)	2.00
LM340 T12 on Heatsink	25p
T9051V on Heatsink	60p
BF259 with Heatsink	14p
TIP110 with Heatsink	40p
L129/130/131 Coil	10p
6MHz Ceramic Filter	25p
DL700 (Philips) Chroma Delay Line	1.00
DL50 Chroma Delay Line	1.00
T9006A Lum Delay Line	1.00
9K5/9K Lum. Delay Line	65p
Plastic Cover for 3K5 SP8385	15p
TX9 Back Ground Control 10K	15p
TX9 Gain Control 100K	15p
1500 Metal Chassis Supports Pair	2.40
Thorn 8K5 Focus Pot	2.75
Thorn 4000 Focus Pot	2.75
Thorn 18Ω 9W (3K5) R752	30p

SERVICE AIDS	
Ambersil MS4 Silicone Grease	12oz 2.15
Ambersil Freezer	12oz 1.99
Ambersil Amberlube	6oz 1.89
Ambersil Ambertron	16oz 1.95
Ambersil Anti-Static Screen Cleaner	7oz 1.95
Ambersil 40 + Protective Lubricant	14.1oz 2.15
Ambersil Amberclens Foaming Cleaner 13oz	

ELECTRONIC EQUIPMENT SERVICING

(TELEVISION/VIDEO full-time College courses)

- Technician Education Council awards ●

TRAINING INVOLVES A HIGH PERCENTAGE OF WORKSHOP FAULT DIAGNOSIS ON TELEVISION & VIDEO CASSETTE RECORDERS

- **15 MONTHS COURSE** for beginners to include Electronic Fundamentals
(Next course commences on January 9th)
- **6 MONTHS COURSE** for BSc, HND, CGLI, TEC and similar applicants
(Next course commences on January 9th)
- **3 WEEKS INTENSIVE VCR COURSE** for applicants with Colour TV background
(Next course commences Jan. 9th)

Also courses in Computers/Microprocessors, and Robotics leading to TEC awards.

LONDON ELECTRONICS COLLEGE (Dept T3/4)

Prospectus from: **20 Penywern Road,
Earls Court, London SW5 9SU
Tel: 01-373 8721**

NORTHERN T.V. DISTRIBUTORS TRADE WAREHOUSE NOW OPEN!! GOOD QUALITY SETS AT GOOD PRICES

I.E.	OFF THE PILE	WORKING
Pye Chelsea 18"	£22.00	£28.00
Pye Solid State	£25.00	£35.00
Philips G8 550	£23.00	£30.00
Philips G8 520	£14.00	£22.00
Decca Bradford	£13.00	£20.00
ITT Hi Brid	£18.00	£28.00
ITT Solid State	£40.00	£60.00
G.E.C. Solid State	£25.00	£35.00
Jap. sets from	£25.00	£35.00
I.E.: Hitachi & Mitsi. etc		
26" sets from	£10.00	
Mono sets from	£2.00	

Some Inline sets also available

I.E. ITT, C.V.C. 25 & 30
Bush T20 & T22, Thorn 9000 etc.

All prices subject to availability of stock

Quality discount available. Hundreds of sets to choose from.

Number One source of second hand T.V.'s in the North.

All prices subject to 15% VAT.

**UNIT 2, PERTH COURT, 11th AVENUE
TEAM VALLY IND. ESTATE
GATESHEAD, TYNE & WEAR
Tel: Newcastle 875389**

Sets also available at our Birmingham Branch:

**811 WASHWOOD HEATH ROAD,
WARD END
BIRMINGHAM B8 2NP
Tel: 021-784 2561**

TUNERS + TUNERS

- ★ If you repair sets regularly – phone us today and we will dispatch immediately – no need to send cash 'up front'.
- ★ All tuners dispatched by first class post for receipt by you the next day.
- ★ All popular tuners/tuner repairs supplied 'off the shelf'.
- ★ Unusual types repaired same day as received (subject to spares availability).

TELEPART

13 Worcester Street,
Wolverhampton, WV2 4CJ.
Phone: (0902) 773122.

NO!

If you see an advertisement in the press, in print, on posters or a cinema commercial which you find unacceptable, write to us at the address below. (TV and radio commercials are dealt with by the I.B.A.)

The Advertising Standards Authority.
If an advertisement is wrong, we're here to put it right.

ASA Ltd, Brook House, Torrington Place, London WC1E 7HN.

TV Fault Finding

Reports from Mick Dutton,
Peter H. Dolman,
H. Davies and John Coombes

Philips KT3 Chassis

The fault on a set fitted with the Philips KT3 chassis was no results. The output from the mains bridge rectifier was correct and was present at the collector of the chopper transistor T1463, so we checked the voltages around the TDA2581Q chopper control i.c. The only incorrect voltage was at pin 12, to which T7336 is connected. This transistor had developed a collector-emitter leak, a replacement clearing the fault.

Another of these sets suffered from very intermittent loss of sound. This was eventually traced to a dry-joint on the 6MHz input ceramic filter on the sound panel. **M.D.**

Decca 130 Chassis

When we unpacked this set there was only a very faint picture with normal sound – the contrast and brightness controls had some effect. We measured the voltages in the RGB output stages, which are of the cascode type, and found the readings at the collectors of the upper transistors in each pair (Q203, Q208 and Q211) high while those at the bases of the lower transistors were 0.5V instead of approximately 2V. After a good deal of head scratching and a comparison between our faulty set and a working one we discovered that capacitors had been fitted instead of 100k Ω resistors in the feedback networks (R226/244/251). This upset the biasing no end! Fitting the correct resistors provided a lovely picture. Subsequently we encountered a set with a capacitor in place of the feedback resistor in the red output stage. **M.D.**

Thorn TX9 Chassis

The problem with this set (Thorn TX9 chassis with remote control) was that the tuning kept drifting while it was not possible to get channels at the bottom of the band. The 33V tuning rail was correctly stabilised, but in the fault condition the output from the tuning controls would vary very slightly. Also it was not possible to tune these controls down to get zero volts at the tuner. We found that the fault could be made to come and go by moving the main chassis, and after a lot of searching a crack was discovered in the earth track beneath where the line output transistor's heatsink is mounted. As a result, the lower ends of the tuning controls were floating. **M.D.**

Fidelity CTV14R

We encountered a rather elusive intermittent fault in a new Fidelity Model CTV14R recently. The owner complained that the sound and vision disappeared after about a quarter of an hour, "as if the aerial had been disconnected". There was loss of channel indication at the same time. A soak test confirmed this description, but in addition we noticed that just prior to failure the channel selected would spontaneously step to a new position (there are six in these sets).

Sequential channel change is effected by applying a negative-going pulse to pin 6 of the ML232 channel selector i.c. These pulses are supplied from the collector of the step driver transistor TR2, and an oscilloscope check

revealed that the cause of the problem was the occasional presence of positive-going pulses at the base of this transistor, though these didn't originate in the remote receiver/decoder section. The source of the trouble was finally traced to current leakage on the print side of the panel from the 77V line via the lacquer coating on the copper track connected to the base of TR2! The problem is due to the 4W resistor R121 (5.6k Ω) which provides the supply to the TAA550 voltage stabiliser – its broad mounting legs straddle the adjacent print area, and in this case the lower leg pressed tightly on the lacquered print. Easing R121 away from the board cured the problem. Presumably as R121 heated its leg penetrated the lacquer, bringing 77V to within a hair's breadth of TR2's sensitive base circuit. It would seem that if TR2 is held on for long enough all channel selection positions are cancelled, causing the eventual no signals effect. On earlier circuits R121 is shown as being a $\frac{1}{2}$ W device, which could explain the problem. **P.H.D.**

Remote Control Trouble

A fault we had with a Pye 1062 teletext receiver (Philips K30 chassis) turned out to be rather embarrassing. The customer's complaint was that the remote control didn't function, neither would the set change channels using the manual controls. We naturally assumed that the set rather than the remote control transmitter was at fault and took it back to the workshop. Another engineer looked at the set and found that it worked all right with our own remote control handset. He said he'd done some soldering to eliminate the possibility of an intermittent dry-joint.

On returning the set to its owners however the problem was exactly as before. The remote side of the set was as dead as ever, stuck on channel one, and it wouldn't change manually. This time I took the remote control back as well. When we tried this on another identical set which was known to be working correctly the symptoms appeared. What was the handset doing to these sets? It seems that the faulty remote control unit was constantly transmitting, the freak signal locking the whole remote control side solid, with no control by either remote or manual operation. **H.D.**

Rank T20 Chassis

Random tripping with poor e.h.t. regulation is usually due to the e.h.t. tripler. If the problem persists after replacing this, check whether 5R13 (330 Ω) is open-circuit – the resistor links one of the tripler's connections to chassis.

Intermittent picture flickering and jumping is usually caused by the coupling capacitor 4C9 (1 μ F) in the field amplifier circuit playing up. If there's also a very slight hum however the 12V regulator transistor 4VT7 (2N5296) is suspect. You may find that its emitter voltage is varying slightly, but this is not always the case. **J.C.**

Hitachi CBP260

In the event of lack of width in this model (NP9A chassis), check whether R756 (30 Ω , 1W) is open-circuit. This will remove the drive to the EW diode modulator. **J.C.**

Teletopics

VIDEO MOVES

It seems that portable video enthusiasts will soon have plenty of hardware to choose between. We already have the VHS-C and CVC systems, and now the Sony Betamovie cam-corder, which uses a standard Betamax cassette, is available in the UK. It won't stop there! Looming ahead is JVC's competitor to Betamovie, the Victor Movie, shown so far only in prototype form in Japan. It's lighter than Betamovie (1.9kg compared to 2.48kg, without batteries) and has playback facilities, though it's likely to be a bit more expensive. Meanwhile Philips intend to introduce an 8mm format cam-corder in the second half of 1984, provisionally designated Model VKR850. It uses a half-inch Newvicon tube, has an electronic viewfinder that enables the tape to be played back, and a six times power zoom lens. Philips have yet to make a decision on the suggested price.

Announcements from both Philips and Grundig that they are to produce VHS machines have led to a certain amount of speculation about the future of the V2000 system, to which both companies remain committed. Philips point out that they sell VHS machines in the American and other markets, and that it's logical for Philips to manufacture the machines themselves. Grundig were apparently approached to produce VHS machines for sale in a non-European market. One suggestion is that the V2000 system could become a full-specification format for the European market, with VHS machines being introduced as bread-and-butter lines. We shall have to see. The latest defector from the V2000 camp is Bang and Olufsen, who have recently announced an Hitachi-sourced VHS machine.

BOOMING TRADE

The TV/video boom continued during the first half of the year, with deliveries of large-screen colour sets up 18 per cent, small-screen colour sets up 56 per cent, and VCRs up 46 per cent compared to the same period in 1982. Deliveries to the trade are not the same as sales of course, and there's a suggestion that VCR stock levels are at present high. The small-screen colour set market seems to be very lively at present however. This is something that can't be said about sales of teletext equipped sets – deliveries have been only marginally up on last year.

ORIENTAL MOVES

A colour TV chassis developed by a government-assisted research body has been adopted by ten leading Taiwan setmakers. Most of the circuitry is incorporated in two chips, reducing the component count by some twenty per cent whilst increasing the reliability factor. It seems that production runs in Taiwan – there are over twenty setmakers – are relatively small in comparison to those common in Japan and South Korea.

The lengthy process of establishing dumping charges against Taiwan and South Korean setmakers in the USA has moved a stage further. Allegations were first made last May, and the US Commerce Department has now reached a preliminary finding that dumping in violation of

the Anti-dumping Act has taken place – the finding is that South Korean sets have been entering the USA at prices over 9.5 per cent below fair market value while sets from Taiwan have been exported at over 30 per cent down. It seems that further processes have to be gone through before dumping duties can be levied.

ITV DBS

The Bill to enable the IBA to set up a DBS TV service is expected to be introduced before Christmas and to be enacted by the late spring or early summer of 1984. The IBA will then be able to advertise DBS contracts. These will indicate the range of options open to potential applicants, lay down technical standards, indicate the means of funding that will be possible and the types of programming that could be considered. Companies or consortia of companies applying can but need not be those with current ITV contracts. The IBA hope to start preliminary discussions with those interested in providing such services at an early date. Existing ITV companies are pressing for an extension to their franchises, which are due to end in 1989, on the basis that this time scale makes it difficult to take the investment decisions that would be required for DBS. Under the arrangements at present envisaged, the IBA will control the uplink but the programme contractor will be responsible for the provision of the satellite. It's stressed that the financial risks for programme contractors will be considerable.

DIGITAL TV ICs

Three new i.c.s have been added to the ITT Digivision range of i.c.s for processing signals in TV sets digitally (see *Television*, November 1981). Two are for chrominance and luminance signal enhancement in NTSC receivers, the third providing a low-cost teletext decoder.

Several firms, including Philips and Sony, are working on TV receiver i.c. memories that store a complete TV field, the idea being to double the number of lines by reading the information out of the memory at 100Hz. The Philips memory uses seven chips and is designed in such a way that it's cheaper than the equivalent RAM. The use of a memory increases the apparent definition, reduces noise and luminance/chrominance crosstalk and enables special effects such as freeze frame to be incorporated.

VINTAGE WIRELESS CO.

After trading for twelve years at Staple Hill, Bristol, The Vintage Wireless Company has moved to larger premises at Tudor House, Cossham Street, Mangotsfield, Bristol BS17 3EN (telephone 0272 565472). The staff is being increased and the aim is to improve service to collectors and all users of valve based equipment. A trade counter with vintage items on display will be opened on November 30th, but the firm operates primarily on a mail order basis.

NEW VCRs

ITT's latest introduction is a mid-range VHS machine, Model VR3975. It supersedes the TR3942 and features stereo sound with Dolby B, full-function infra-red remote control, and an eight-event, two-week timer. Suggested price is around £525. Sanyo's Betamax Model VTC6500 has an eight-event, two-week timer with daily and weekly repeat, infra-red remote control and forward colour

picture search. Suggested price is £480. Bang and Olufsen's Model 4462 is a VHS machine with infra-red remote control, a five-event, two-week timer with daily and weekly repeat and a suggested price of £625. The Sharp Model VC387H features concealed controls, infra-red remote control and a height of just 3.7in. Suggested price £680. There's Dolby sound, a five-event two-week timer and other top range features.

RTEEB LEN BRIGGS AWARD

The third Len Briggs Award for the most outstanding candidate in the Radio, Television and Electronics Examination Board's "Certificate of Competence in Colour Television Servicing", for 1983, was awarded to Gordon J. Roberts at a luncheon of the Council of Management on October 18th. Mr. Roberts studied at South London College and is Service Director of Forbes Rentals Ltd., Croydon.

FILM-TO-VIDEO TRANSFER SERVICE


A service which Rediffusion call "Video Album" is now available at some 250 of their branches throughout the country. The service enables customers with Super-8 or 8mm films, and 126 or 35mm slides, to have these transferred to VHS or Betamax video cassettes no matter what the condition or how old the film material. For an extra charge, titles and music can be added. The charge for the basic processing ranges from £30 for a fifteen minute (200ft) movie or up to 80 slides, to £100 for a two-hour film or up to 700 slides. The original material is first professionally cleaned and then colour-graded for best results - John Reay, Rediffusion's sales director, comments that old films can actually be improved.

4GHz SATELLITE RECEIVER

Hugh Cocks (Cripps Corner, Robertsbridge, E. Sussex TN32 5RY) is now able to supply 4GHz satellite receivers, type KB1. The head unit has a helical feed and consists of a four-stage gallium arsenide f.e.t. LNA with a minimum gain of 43dB and a noise figure of 1.25dB, followed by a down-converter tunable over 3.65-4.2GHz with 46dB of i.f. amplification at 750MHz (nominal - adjustable at the receiver). The indoor unit incorporates second conversion to 40MHz, quadrature vision detection, CCIR de-emphasis, video amplification and clamping, two-position audio demodulation and expansion. The basic receiver costs £385 plus carriage - this does not include the dish or connection cable. The head unit alone is available at £230 and the indoor unit at £155, plus carriage in both cases.

SURFACE MOUNTING TECHNOLOGY

Mullard have initiated a major campaign to increase awareness of the advantages of surface mounting component technology in the UK's electronics industry. Advantages include: increased component packing density (board sizes reduced by 35-50 per cent, with a packing density of six surface mounted devices per square cm instead of three components in conventional encapsulations); assembly costs reduced by as much as 50 per cent; much better h.f. performance; and much improved reliability (abolition of radial/axial leads eliminates failures caused by breaking or cracking when bending or cropping). In addition to a wide range of active and passive

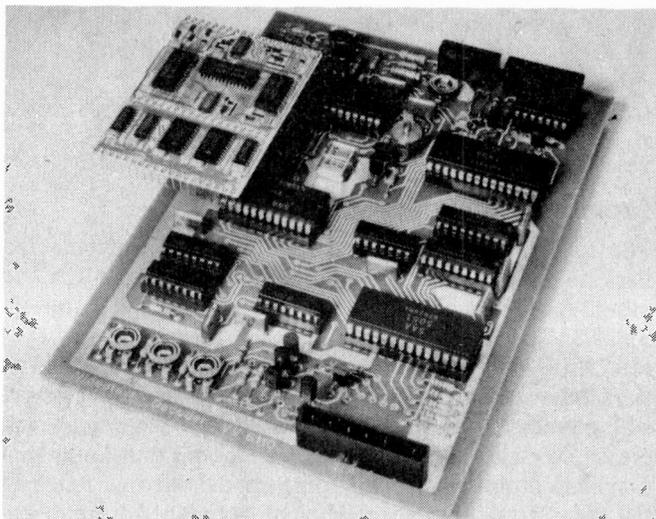

Comparison between a teletext decoder using conventional through-panel component mounting and the equivalent using surface mounting technology.

components for surface mounting, Mullard are offering the Philips Elcoma range of automatic placement machines - their first ever commercial foray into the production equipment market.

At present the cost of components in surface mounting packs is higher than those with conventional leads - prices are expected to equalise when production levels become similar. There are however savings in board material, factory space and so on. When it comes to a complex assembly such as a TV chassis, severe design constraints are imposed by the use of surface mounting due to the limited number of different items the placement equipment can handle. As a result, surface mounting in TV sets is likely to be encountered first in sub-assemblies such as teletext decoders, then possibly in hybrid surface mounting/component insertion panels.

Mullard believe that the future lies very much with surface mounting, and express concern that its growing use in Japan and the USA could leave the UK's electronics industry at a considerable disadvantage unless substantial investment in the new technology starts now.

TV SETS

Some interesting new sets have been released recently. The Network 20in. Model NWC2044R colour receiver for example incorporates a switch-off system that operates five minutes after the end of a transmission. This could operate from the a.g.c. line, with gating and a delay circuit, though we've no details at present. The set is of Italian manufacture and features synthesised tuning with full infra-red remote control. Sony's latest 14in. colour set, Model KV1430, supersedes the KV1400 and features a front connection for video games or a computer: the screen is raised a few inches so that the game console/computer can be placed in front without obscuring the display. Fidelity's Model CM14 14in. colour monitor will accept RGB, RGBY or a composite video input, plus audio, via a 21-pin scart socket and can be used with almost any games console or computer. The price is under £200 and the set is fitted with a high-definition, 90° high-brightness tube. The video bandwidth is quoted as being over 12MHz. A detachable, anti-glare tinted glass front is provided. A new range of large-screen colour sets has been introduced by Philips. They are fitted with the K35 chassis, an uprated version of the K30.

VCR Clinic

Reports from Richard Roscoe, B. Atkinson, Les Harris and John Coombes

Tape Slack Modification

The following modification was devised to prevent tape slack on the JVC Models HR7200EK and HR7300EK and other VCRs that use the same chassis, e.g. the Ferguson 3V29/3V30. The problem initially arose with a JVC HR7300EK. It would occasionally stop after rewind with slack tape sticking out beyond the flap. When the cassette was extracted this slack tape would of course snag and crease. We also handle Hitachi VCRs, and thus know that a similar problem plagued some models in this range in the past. To overcome it, Hitachi introduced a modification in the form of a small additional circuit board which produces a short pulse (800msec duration) at the end of the rewind cycle. The pulse is used to kick the mechanism so that any slack is taken up. For further details see VCR Clinic, November 1982. We've fitted this board in the past and thus know that it does indeed solve the problem.

The HR7300EK is completely microcomputer controlled however, and already has a pulse for the purpose. It's called "short REW" and lasts for 240msec. As a result we decided to turn our attention to the mechanical components initially. We made sure that the brake drums and pads were o.k., checked the various springs and bearings and made sure that the mechanism was as responsive as possible. This improved matters, but the fault persisted. We then contacted the JVC service department who said they'd not come across the problem. So all we could do was to check the action of the control circuitry as closely as possible.

After putting the machine through innumerable operating cycles the conclusion we came to was as follows. The circuitry was operating correctly, but sometimes the mechanism simply didn't have enough time to respond to the 240msec short REW pulse. Since Hitachi had opted for an 800msec pulse, we wondered whether stretching the JVC machine's short REW pulse to 800msec would provide a cure? So we did it and tried it and for anyone with the same problem we can recommend this modification as a complete cure.

The pulse stretcher circuit is shown in Fig. 1. It uses three CMOS 4011 quad two-input NAND gates which are supplied from the 10V line used to power the microcomputer i.c.s. No additional decoupling was found to be necessary. The circuit was built on a small piece of Veroboard which was held in place by the wiring loom between the mechacon and the servo panels. Since the pulses are relatively slow, radiation or crosstalk is no problem. The connections between the pulse stretcher circuit and the control circuitry are shown in Fig. 3.

The four outputs from port G of microcomputer IC2 (pins 22-25) control the direction of the reel motor. Its speed is controlled by various outputs depending on the mode the machine is in. The output we are concerned with comes from pin 10 of IC4 - the reel motor unloading/idler power control. As the timing diagram (Fig. 4) shows, this line carries other pulses besides the short REW pulse: one of the jobs of the logic circuitry in the modification is to detect which is which. To this end one of the outputs from port G (IC2, pin 23) is fed to gate 1a. This line is low except when the reel motor is performing a rewind function, when it goes high. So gate 1a is blocked except

during a rewind operation. Its output will be high, gate 1b's output low and gate 1d's output high. This opens gates 2c, 2d, 3d and 3c to respond to whatever is on their other inputs. Thus during a non-rewind operation, the pulses fed to R54 follow exactly those at pin 10 of IC4, via gates 2a and 2c. Similarly the control lines to the reel motor via pins 3 and 4 of IC8 follow the outputs from port G (pins 23 and 22 respectively). In addition, the control line to the brake solenoid, from pin 18 of IC2, is fed out undisturbed to pin 5 of IC9. This bit hasn't been mentioned before, but clearly if the motor is to rewind for 800msec instead of 240msec the brakes must be held off for 800msec as well. Thus any function other than a reel motor rewind one is unaffected by the modification.

Inspection of the timing diagram will show that there are three situations where a pulse is present on the unloading/idler line during a rewind operation, i.e. when pin 23 of IC2 is high. First, during unloading. Secondly, when the 1.5sec slow rewind pulse leading into fast rewind is present. And finally when the 240msec short rewind pulse appears. Gates 1b and 1c form a monostable multivibrator with a time-constant of about 800msec, set

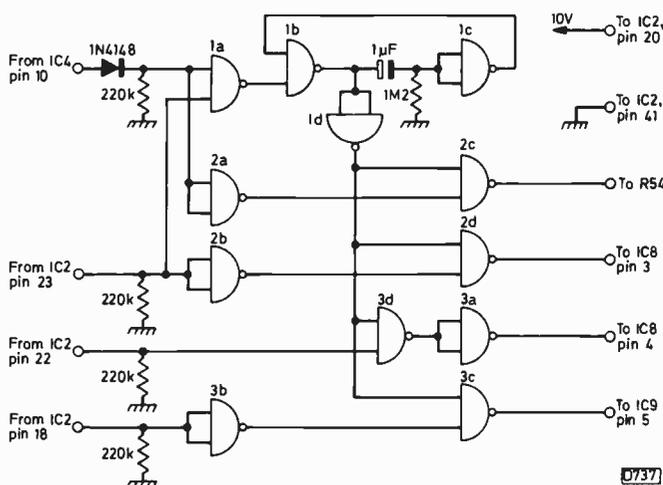


Fig. 1: Pulse stretcher circuit for the JVC HR7300EK.

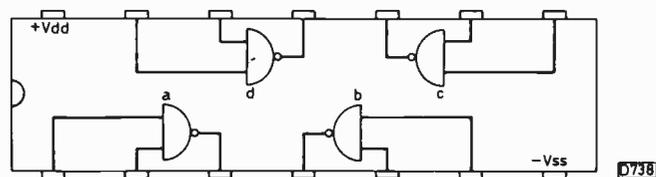


Fig. 2: Pin connections for the 4011 gate i.c.

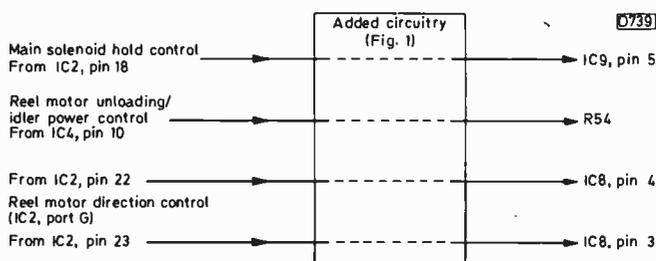


Fig. 3: Connections to the pulse stretcher circuit.

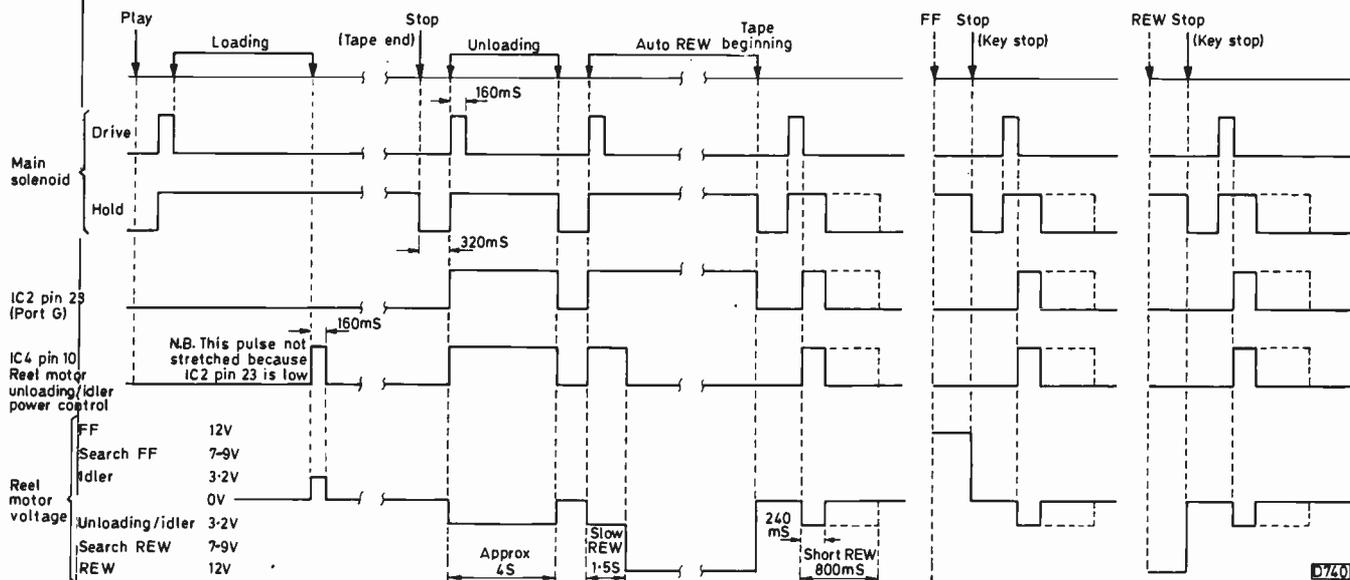


Fig. 4: Timing diagram for various control functions.

by the values of the $1\mu\text{F}$ capacitor and the $1.2\text{M}\Omega$ resistor. It's triggered by the pulses on the control line to gate 1b (since gate 1a will be open). The pulse output from gate 1b has the nice property of being 800msec long if the trigger pulse is shorter than this or as long as the trigger pulse if it's longer than 800msec. This is just what we want, since the unloading and slow rewind functions will be unaffected but the short REW pulse will be stretched to 800msec. This stretched pulse is fed to the other control lines so that the motor rewinds and the brakes are held off for 800msec.

Connecting the board to the existing circuitry involves breaking the print between the relevant pins of IC2, IC8 and IC9, lifting one end of R54 (or mounting it bodily on the Veroboard), and soldering the ten connections to the relevant points on the mechacon panel. Since this panel is quite densely packed, thin wire is best - preferably colour coded for future reference. Care is obviously required, but as long as a sharp knife and a clean, fine-tipped soldering iron are available no real difficulty should arise.

One final point. If any mistakes that have the effect of turning the reel motor driver chip IC12 hard on are made in the wiring up, the chip protection device CP2 will blow. So if the motor fails to turn, check CP2. If it has blown, check your wiring before replacing it and trying again. **R.R.**

A Click Tip

No, not a Japanese video engineer but a reminder that could save a service call. If the complaint is mechanical clicks while the tape is moving, the "fault" is probably the tape counter sticking on a particular number and clicking as it tries to jump to the next. A press on the reset button is usually all that's required. This doesn't apply to later machines with electronic counters of course - but they have problems of their own! **R.R.**

Sharp VC8300

The customer's description of the fault was that the VCR worked all right for the first or second playing of a prerecorded tape or one recorded on the machine, but after this the picture would get noisy and eventually disappear.

We recorded a colour-bar signal and played it back.

Sure enough the picture was perfect at first, but after the second replay it started to get noisy while after the fourth playback it had disappeared into the noise. When we played the tape on a new machine we found that it had been erased. We then checked the erase oscillator and found that it was producing the correct output on record and also a very low output on playback. This led us to the record/playback i.c. (I601). The low playback output should be 0.5V but in fact was 1V. This was just enough to start the erase oscillator, though not to produce a full-amplitude output. It seemed that the low-amplitude output was too little to erase the tape in one pass, taking three or four plays for the purpose. Rather expensive with prerecorded tapes! A replacement chip restored normal operation. **B.A.**

Hitachi VT5500

This VCR had been to another company who seemed to have done it more harm than good. First there were no functions due to a short, as a result of which there was no regulated 12V supply. After we'd dealt with that we found there was no clock display. There was still no display after replacing the clock i.c. (IC101), but flicking the on-off switch lit up the display and enabled it to be set. On pressing a channel select button the display went out again! The channel select i.c. (IC701) was found to be running hot, a replacement finally clearing the fault. **L.H.**

Hitachi VT8000 Series

In the event of intermittent colour, check IC203 (HT4209) on the luminance/chrominance panel by replacement. For colour drop-out/no colour, if the top of the picture is affected but the bottom is correct, check Q225 (2SC2021) by replacement. We've had several cases of intermittent fast forward or rewind operation due to the reel motor. **J.C.**

Mitsubishi HS310

In the event of no colour on prerecorded tapes, remove the bottom cover and resolder the joints around crystal X6F1. **J.C.**

An Unusual Chopper Circuit

A feature of the latest large-screen ITT chassis (CVC1200 series) is its rather unusual switch-mode power supply. This employs discrete component circuitry and provides mains isolation, but the precise mode of operation is not easy to see when you first glance at the circuit in the manual. The chopper transistor itself can be spotted readily enough of course, but the control circuitry contains quite a number of transistors and diodes whose functions are not so clear. We are indebted to Arthur Thomas of ITT for his assistance in the preparation of the following brief description of the circuit (see Fig. 1).

In normal operation the chopper circuit is driven at line frequency by a pulse-width modulator on the mains isolated part of the switch-mode power supply panel. The isolating transformer Tr712 couples the drive to the mains connected chopper circuit.

T713 is the chopper transistor, T721 the pulse-width modulator and T711 the chopper driver. T731 varies the d.c. conditions at the base of T721 to provide regulation against mains voltage variations. This action takes place as follows. The negative voltage swing at tag k on the chopper transformer Tr711 is mains dependent. This excursion is rectified by D731/C725 and used to set T731's base voltage, in turn influencing T721's base voltage. The latter also depends on the setting of the set h.t. control R726 and the loading on the h.t. line, since this supplies R726 via R734 and R736. The d.c. conditions at the base of T721 thus depend on the h.t. load and the mains input voltage.

T721 is switched on by a sawtooth voltage produced by integrating the line flyback pulse appearing at tag 1 of the

line output transformer. D723/722 clip the pulse, R725/C724 providing the integration. The point at which T721 switches on during the sawtooth ramp depends on the d.c. conditions which, as we've seen, depend on the h.t. and mains voltages. The output from T721 is thus a variable mark-space ratio squarewave which is coupled to the base of T711 via Tr712 and D701. During the chopper transistor's "on" period, T711 provides T713 with drive current via R713 and D711. T712 is then reverse biased. When T711 switches off, T712 switches on, being forward biased via R714. As a result, the base of T713 is returned to the negative rail provided by D713/C713 and it rapidly switches off.

Something has to be done to get this lot going at switch on. C703 charges from the 300V rail via R716, producing a sawtooth which is coupled to the base of T703 via C728. T703 thus switches on, connecting the lower end of R708 to chassis. As a result T711 is brought into conduction, driving T713 on with drive current supplied by C728.

Since the chopper transformer Tr711 provides T713 with an inductive load, the current through T713 rises linearly, producing a sawtooth voltage across R721 in its emitter circuit. This sawtooth is negative-going with respect to chassis, so T702's emitter is driven negatively with respect to its base. T702 thus switches on, in turn switching T701 on. T711's emitter and base are thus shorted together and T711/T713 both switch off. Circuit operation is then sustained by feedback action. In addition to playing a part in the start-up action, T702/T701 act as a trip under excess current conditions.

In the absence of drive via the line output stage the

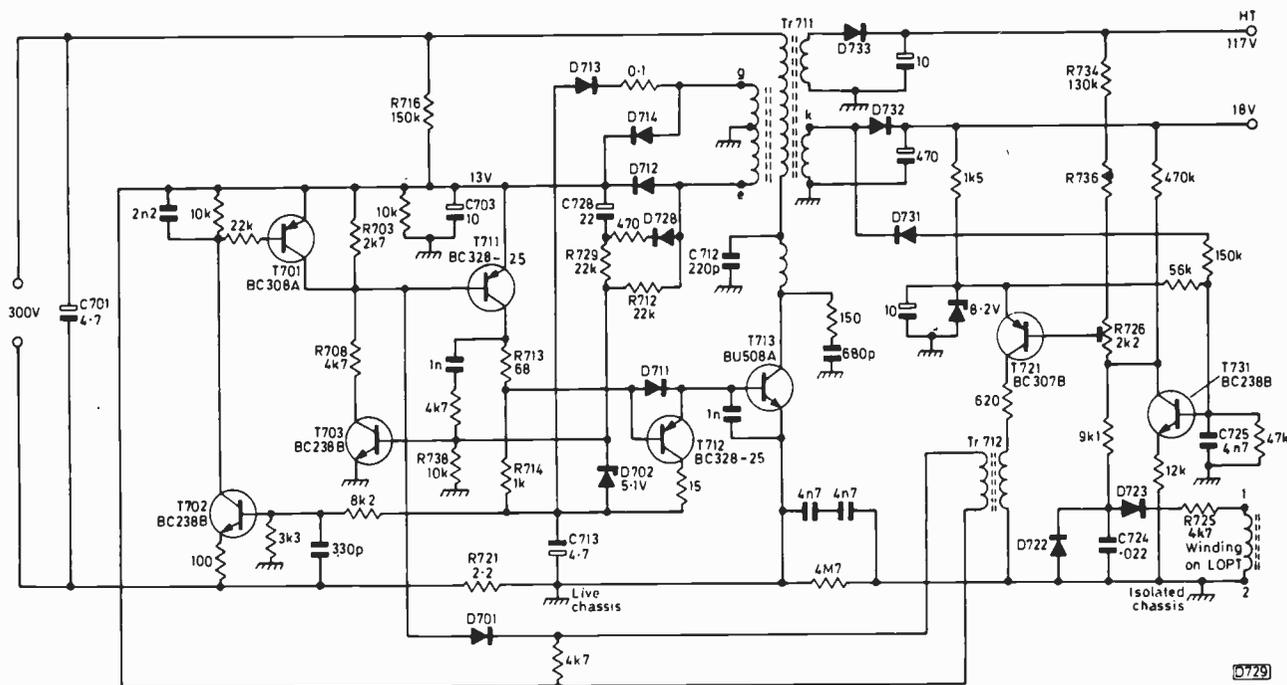


Fig. 1: Simplified circuit of the switch-mode power supply used in the ITT CVC1200 series chassis. The h.t. is 117V in the 90° 20in. version, 145V in the 110° 22/26in. version, the l.t. rails being 18V and 24V respectively. The values of the flyback tuning capacitor C712 and the resistors (R734/R736) feeding the set h.t. control R726 differ in the two versions of the chassis: the values shown above apply to the 90° version.

chopper circuit free runs at approximately 20kHz, with feedback from tags g and e on the transformer. D714 conducts when T713 switches on, providing a start voltage (D714 functions only in the absence of drive from the line output stage). T703 is driven from tag e via R712. Since there's no regulation in the free-running condition, the output voltages must be limited. This feature is provided by zener diode D702 in T703's base circuit. In the free-running condition the 18V and 117V rails will both be below normal. If D702 is short-circuit the switch-mode power supply will not start; if it's open-circuit, the output voltages will rise above limits.

Under normal conditions C728 remains discharged,

both plates being returned to tag e on the chopper transformer via D712 and D728 respectively. If the load on the chopper outputs is reduced, the pulse amplitudes at tags e and g vary and C728 charges, shutting the power supply down. The set must be switched off for at least 17 seconds before the switch-mode power supply will restart.

In some early sets there were differences in T703's base drive circuit – in particular R738 was connected between the junction of R729/C728 and chassis. If the chopper transistor fails, ensure that R738 is fitted between the base of T703 and chassis.

An isolation transformer rated at 500VA, 240V must be used when working on the switch-mode power supply.

Underwater TV

Peter Graves

Few manufacturers other than the makers of underwater equipment expect their products to work reliably after being thrown into dirty water and then pulled down to crushing depths by unskilled operators! There's a greater pressure change between the surface of the sea and a point forty feet below it than between the surface and the outer edge of the atmosphere. At quite modest depths the pressure on an underwater camera housing is measured in hundreds of pounds per square inch, and a camera lowered too far will quite literally be crushed flat.

Most cameras for underwater use are based on the use of a circular tube for strength and have a thick glass or Perspex front plate sealed with neoprene O-rings. The back plate is made of metal and carries the camera's cable connector. Connectors can be fitted for lights and diver-communications. Both the connectors and the back plate are sealed with O-rings. The finest camera housings are made from titanium, which is light, strong and corrosion resistant. It's also expensive and difficult to machine. For general use the choice lies between stainless steel and aluminium alloy.

Underwater cameras are similar to their surface counterparts electronically, with the controls made automatic or remotely operated. The tube and scan coils are mounted along the central axis of the housing, with circuit boards arranged around or behind them. For some applications separate-head cameras are used, with the lens, camera tube, scan coils and head amplifier in one unit which is connected to the rest of the electronics by a multicore cable. Since most of the electronics are at the surface, the business end can be made very compact for intricate inspection jobs such as checking the insides of pipes. General purpose underwater cameras are self-contained, with the complete camera inside the underwater housing. Power is supplied down the cable, usually as low-voltage d.c. for safety and to avoid hum pickup on the video via the long cable run. The composite video signal returns to the surface via a separate cable, further cores carrying the remote controls such as focus.

For diver hand-held use the camera is fitted with a pistol grip and a bar for carrying a light. Viewfinders are rarely used because of the extra bulk, complication and handling difficulties they cause. Operations are directed from the surface by verbal commands down the diver communications circuits – the communications cables can be separate,

going down with the diver's air lines, or form part of the camera cable, coming out to a small underwater connector on the camera's rear bulkhead.

With a rigid diving helmet the communication leads go to a microphone and a miniature loudspeaker mounted in the air space inside. A diver with a closely fitting soft helmet uses a bone conductor – a small encapsulated microphone/loudspeaker that fits tightly under the helmet and presses against the mastoid bone beneath the ear. The thin film of water trapped between the bone conductor and the skin provides good acoustic coupling, allowing two-way conversations through the vibrations in the diver's skull bones.

Cables

Underwater cables operate in a harsh environment – continually wet, crushed by pressure and being dragged over the sides of boats and the sea bed. A thick outer sheath of polyurethane or neoprene seals the cable and provides resistance to abrasion. Load bearing cables have an additional sheath of steel armouring wires or, for less strenuous applications, a central core of braided strands of Kevlar, an immensely strong polyamide plastic.

If there's the slightest cut in the cable's outer sheath at depth, water under pressure will be forced up inside the cable, ruining the affected section which has to be cut off and the dry part reterminated. Some cables have a waxy or rubbery filling between the cores inside to prevent water ingress, a technique known as water blocking.

Most underwater connectors are moulded on to the cable to give a good mechanical joint that's also watertight. The disadvantage of this type of connector is that repair in the field is difficult. Some kinds of connector can be stripped and remade without moulding. They are prone to leakage and mechanical damage however. The choice of connector can thus be a difficult one.

The video signal usually travels to the surface via a high-grade 75Ω coaxial cable. Some systems use a twisted pair cable, with a balanced line driver circuit in the camera and a balanced-to-unbalanced circuit in the surface equipment. Twisted pairs are less prone to electrical interference (when used as a balanced system) and mechanical damage, but the send and receive circuits are more complicated. With very long cables, say over a few thousand feet, the video signal can be modulated on to a low-frequency carrier (typically 10MHz) and sent via a screened twisted pair to a demodulator at the surface. Although cable attenuation is greater at higher frequencies, the losses across the band are reduced and compensation is easier.

Cable handling in the field must be carefully supervised.

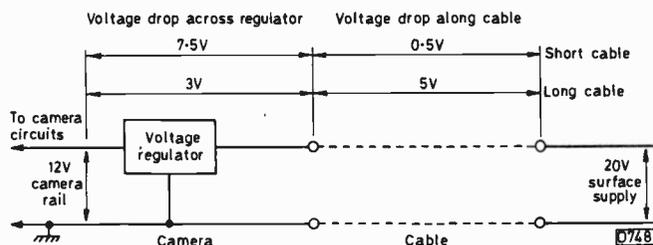


Fig. 1: Constant-voltage supply arrangement.

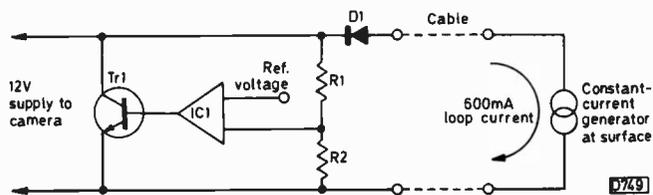


Fig. 2: Constant-current system with shunt regulator.

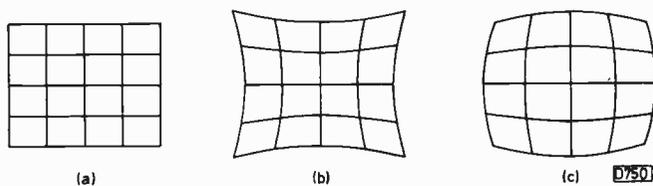


Fig. 3: Image distortion. (a) Object; (b) pincushion distortion; (c) barrel distortion.

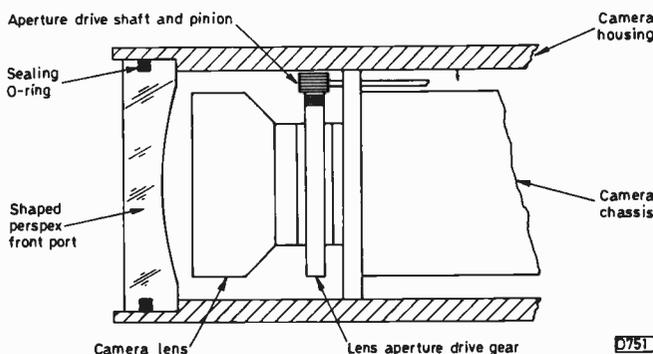


Fig. 4: Underwater camera port and optical arrangements.

Too little cable played out will hold back a diver or an underwater remote-controlled vehicle while too much will form loops that add to the cable drag and are likely to get caught on underwater obstructions or sucked into the ship's thrusters – the thrusters always win and have been known to chew up entire underwater vehicles. Unskilled helpers regard the cable as a sort of rope that can be knotted to a convenient railing or left in a tangle on the deck when it's been hauled in. Cable on the deck has a fatal fascination for the handlers of heavy machinery and welding torches however: more damage can occur to a cable out of the water than in it.

Voltage Regulation

With a long cable run the voltage drop along the supply cores becomes significant. Thus some form of compensation is required to keep the camera's rail voltages constant. The simplest system consists of a variable power supply at the surface. It's adjusted with the cable connected until the camera rail voltage is correct. If the cable length is changed and the supply is not readjusted the camera voltage can go disastrously high or uselessly low. So some form of automatic cable voltage drop compensation is

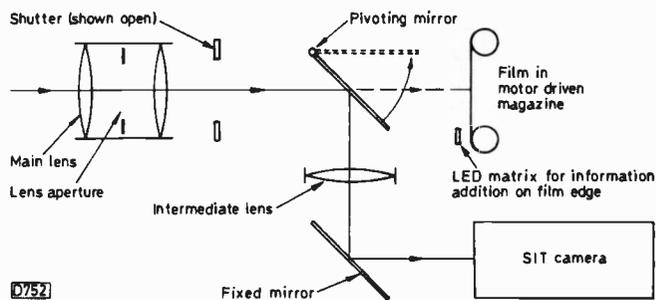


Fig. 5: Simplified diagram of a combined stills and TV camera.

generally required. The two most common systems are loosely described as "constant-voltage" and "constant-current" arrangements.

The constant-voltage system employs a series voltage regulator in the camera and a voltage supply at the surface. In a typical set up, shown simplified in Fig. 1, the camera rail voltage is 12V and the surface supply 20V. The difference between the two voltages is taken up partly by the voltage drop along the cable and partly by the voltage drop across the regulator. Changing the cable length alters the proportions of the voltage drops between the cable and the regulator. With a short cable the voltage drop along the cable will be negligible and the whole voltage difference between the surface supply and the camera rail will appear across the regulator. Sufficient heatsinking must be provided. Provided the sum of the voltage drop along the cable, the minimum voltage drop across the regulator (so that it's just working), and the camera rail voltage does not exceed the supply voltage on the longest cable used, compensation will be automatic for all cable lengths up to the maximum.

In a constant-current system (Fig. 2) the camera and cable form part of a constant-current loop, typically 600 or 800mA. The camera incorporates a shunt regulator that keeps the camera rail voltage constant. This voltage is nominally 12V. A portion is tapped off by the potential divider R1, R2 and compared with a fixed reference voltage from a zener diode by voltage comparator IC1. The comparator's output drives the shunt transistor Tr1 in the appropriate manner to compensate for voltage changes on the rail. If the rail voltage increases, the transistor is driven harder into conduction to shunt current from the rail and restore the voltage to the nominal value. Diode D1 protects the camera from reversed supply voltages. As long as the sum of the voltage drop across the shunt regulator (rail voltage plus diode D1 drop, about 13V) and the voltage drop along the cable does not exceed the open-circuit voltage of the constant-current generator at the surface, the camera rail voltage will not change with different cable lengths.

Optics

Water is optically very thick compared to air, and light rays travelling from the water are refracted (bent) as they cross the front port and enter the air inside the camera. With a parallel sided front port the image appears to have pincushion distortion (Fig. 3) and also appears to be closer to the camera than it actually is. To correct for this distortion, the inside surface of the port is shaped and polished to form a plano-concave lens that distorts the image in the opposite direction (barrel distortion). By careful choice of the curvature of the port and the focal length of the camera lens the pincushion and barrel

distortion will cancel. Fig. 4 shows how the port is shaped and how it's sealed into the camera housing.

An alternative to the shaped port is the domed port formed from Perspex. Light rays cross both boundaries of the port at right angles to the surface and refraction is zero. There are one or two alternative lens systems for underwater work, but they are rarely encountered in TV practice. Narrow-angle lenses (about 12mm or over) with parallel sided front ports can for example be used. With the narrow field of view, the light rays forming the image enter the camera at a small angle to the central axis of the lens. The refraction is thus small and distortion minimal.

Water is a light attenuator and this limits the maximum range of a camera. It's a filter that progressively absorbs the longer wavelengths (i.e. red first, which is why underwater scenes look blue). If this was not enough, most naturally occurring bodies of water contain particles of mineral and organic matter that scatter the light rays, further reducing image contrast and camera operating range. Conditions vary greatly, and it's often difficult to convince a customer unused to underwater TV images that the poor pictures are due to the environment rather than the camera. Broadcast television studio shots taken in brightly lit studios with everything in focus lead some people to think that all TV pictures should be like this!

Almost all underwater jobs require some form of additional lighting. The suspended particles in the water make its provision something of an art rather than a science. There are two main types of lighting in use: gas-discharge and incandescent lamps.

Thallium iodide (predominantly green) and mercury vapour (blue) are the commonest gas-discharge types, though others have been tried. The spectral output of a gas-discharge tube consists of a few sharply defined frequencies, making them unsuitable for use with colour cameras. Discharge lamps are very efficient in turning electrical energy into light energy but they are expensive, cannot easily be dimmed, and need high voltages and special control circuitry.

Incandescent lamps – usually tungsten-halogen bulbs – are cheap, can be dimmed easily and have a spectral output that's continuous over the visible spectrum. They are inefficient however, so that more power has to be supplied for the same light output as an equivalent discharge lamp. The excess is dissipated as heat. Fortunately, in operation underwater lamps are surrounded by an excellent heatsink! The higher wattage lamps can be operated in air for only a few minutes before they overheat. Lamp sizes range from about 10W, used for close-up inspection with a sensitive camera, to several kilowatts for long range colour viewing.

Whatever kind of lighting is used, the suspended particles in the water scatter light back into the camera, reducing the image contrast. The equivalent situation on land is that of driving in fog. Increasing the amount of light thrown forward from the car by turning on the headlights doesn't improve the visibility – all you see is a solid wall of white, caused by the light scattered back to the eye by the water droplets suspended in the air. Better visibility is obtained if additional light is kept to a minimum.

There are several underwater solutions to the problem. The first is the car driver's – use less light and a more sensitive camera, minimising the blinding effect of back-scattered light. Alternatively, the lighting unit can be arranged to be at one side of and angled towards the central axis of the camera, so that the majority of the

scattered light is scattered off towards the other side of the camera and doesn't enter the lens. This method requires some experimentation for best results, and it's often difficult to get enough separation between the light and the camera. Divers object to long arms dangling off the side of the camera – they get snagged and broken off.

If a short focal length lens is fitted (between about 4.5 and 8mm) the field of view of the camera is very wide and the camera can be taken very close to the object being examined while still seeing a useful amount of it. The closer you get the less the number of scattering particles between the object and the camera, so the clearer the picture.

In really murky water a clear water cone is used. Its simplest form is a transparent plastic bag filled with clean water and sealed. The bag is pressed between the object and the camera so that all dirty water is removed. More elaborate versions use a Perspex cone fitted to the front of the camera. The flat face of the cone that goes against the object can have a measuring scale engraved on it, a useful facility as it's difficult to estimate lengths underwater with no points of reference. Crude estimates are made by asking the diver to put his hand or knife in the field of view.

Tubes

Most types of camera tube have been tried in underwater cameras. The current trend is away from the more easily damaged vidicon towards Newvicons, Chalnicons and silicon-diode array tubes in the 1in. and 3/4in. versions. There's no best tube – all have advantages and disadvantages.

The more sensitive the tube, the less extra light needed. This reduces back-scatter problems. Because of this, cameras using the silicon intensifier target tube have become popular for many underwater applications, despite cost, size and complexity – the tube alone costs between £700 and £1,000. It consists of a conventional silicon-diode array tube (tough enough to withstand electron bombardment) with an electron image intensifier mounted at the front. The combination gives an enormous increase of gain over the unassisted tube – the SIT tube is roughly two thousand times as sensitive as a vidicon tube.

Colour cameras are useful where the fault conditions being looked for are differentiated by colour rather than brightness, e.g. rust patches amongst green weeds. Underwater colour cameras are usually standard surface units stripped of nonessentials such as viewfinders and shoe-horned into an underwater housing with the controls made remote at the surface. They tend to be bulky, less sensitive and have a poorer resolution than equivalent monochrome cameras. Solid-state image pickup cameras are still in their infancy in the underwater world, where the emphasis is on rugged reliability rather than state-of-the-art development.

Photographic Stills

The high-sensitivity, continuous pictures from a TV camera can be combined with the high resolution and accurate colour rendering of a stills photographic camera by using a SIT camera as the viewfinder of a single-lens reflex camera. The system used in the Osprey type OE2300A TVP camera is shown in simplified form in Fig. 5 in its normal, TV active, position.

The pivoting mirror reflects the image from the lens on

to the fixed mirror and then on to the faceplate of the SIT tube. The shutter is open. The lens aperture is under the control of the TV camera's aperture servo circuit to compensate automatically for changes in scene illumination. The lens focus is controlled from the surface, and the optical path is arranged so that focusing the TV camera also focuses the image on the film plane. Using the TV picture, the whole unit is lined up on the object to be photographed, the stills camera trigger is pressed, the shutter closes completely, the pivoted mirror swings out of the way, and the TV aperture control circuits lose control of the aperture which is set by a remote f-stop control to suit the film speed. The shutter opens and closes to make the exposure on the film and the film is wound on by a motor drive. Provision exists for firing an external flash gun. During film wind-on data such as time, frame number and other identifying data can be exposed on to the film edge by an LED matrix. The pivoted mirror swings back into place, preventing stray light entering the film magazine, the shutter opens and the TV camera regains control of the lens aperture.

In Conclusion

Some of the problems associated with underwater television have been described – there are still many to be solved and a considerable amount of development work is going on. The use of 3-D systems, the transmission of slow-scan television pictures through the water by acoustic pulses, and techniques for improved pictures in poor

visibility conditions are some of the more interesting.

The problems are psychological as well as technical. The human perception system does not work well with images of strange objects in unusual surroundings. Watching a monitor for long periods leads to operator fatigue. An example is the inspection of oil and gas pipelines on the sea bed. The surface operator must move a remotely controlled vehicle just above the pipe for extended periods, looking for defects in a pipe which is boringly the same for mile after mile. Big problems like an anchor caught round the pipe are easily seen, but equally important small cracks in the concrete pipe coating may be missed due to wandering attention. Another example is the exterior of a concrete oil platform that has to be inspected in its entirety and consists of literally acres of featureless concrete.

The rising cost of diving and the increasingly complex regulations affecting every part of this work are leading to greater use of remotely controlled vehicles underwater. These range from simple powered camera platforms to multirole vehicles with multiple cameras and a range of remotely operated tools. Unlike divers they can stay down indefinitely. The combination of diver and a hand-held camera remains a powerful one however. A diver can be directed from the surface to cover an area in a way that no underwater vehicle can. There's an additional safety factor in having a camera supervising a group of working divers, while the fact that the client can watch the job in progress from the surface can be highly motivating!

Adding Continental Sound

William Falkland

You don't have to be a DX-TV enthusiast to want your set to be able to handle 5.5MHz sound. In the southern and eastern parts of the UK, especially near the coast, signals of entertainment quality can often be received from the continent for hours at a time – given favourable weather conditions and a well-sited wideband aerial. Programmes from Holland in particular include a great many that have English-language speech. The ordinary UK set will reproduce the picture all right but the only thing to be heard on the sound channel will be a loud hiss, due to the subcarrier being at 5.5MHz instead of 6MHz.

Input Filter Switching

Fortunately most modern sets can be adapted to receive 5.5MHz sound fairly simply – reception of French signals is another matter altogether. Sound selectivity is usually provided by a miniature ceramic filter, so conversion may involve little more than the addition of switching to select a 6MHz filter for the UK system I or a 5.5MHz filter for the continental systems B/G.

The switching can be done by an electronic switch such as the CD4066 i.c. (see Fig. 1). This chip includes four single-pole switch sections and each can be individually controlled by applying CMOS logic levels to the relevant control pin (low for off, high for on). A pair of switches is used for each ceramic filter to ensure good isolation of the unwanted filter. Fig. 2 shows the switching for a typical

intercarrier sound channel.

It may be possible to dispense with the two input switches if the video detector is capable of driving both filters at once. In this case an additional matching resistor should be provided to ensure that the signal fed to the extra filter has the correct source impedance, and to avoid interaction between the filters.

Detector Circuit Switching

Further switching is required in the demodulator stage. One of the most commonly used intercarrier sound i.c.s is the TBA120 series, which is generally operated with an LC tank circuit. To retune this to 5.5MHz, some extra parallel capacitance can be switched into circuit. A single-pole switch is required, but it's important to use one with a low resistance in the on state to ensure that the tuning remains sharp. A small relay would do the job, but a semiconductor device will probably be easier to fit in the space available. The VN10LM MOSFET shown in Fig. 2 acts as a voltage-controlled switch: it's turned on by applying to the gate a voltage between about 2V and 10V with respect to the source. In the on condition the source-drain resistance is a few ohms.

In some sets, including those that use the TBA120T intercarrier sound i.c., a ceramic filter is used in the demodulator circuit. There are two types, and both are different from the input selectivity type – it's important to

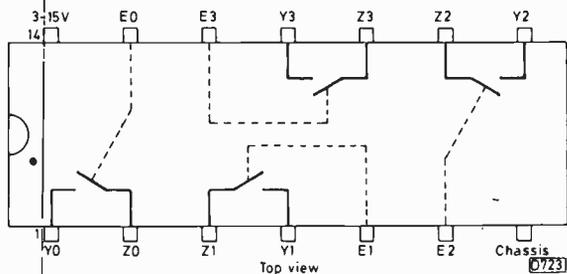


Fig. 1: Pin connections for the 4066 switch i.c. Pins E0-E3 are the control terminals for the four switches.

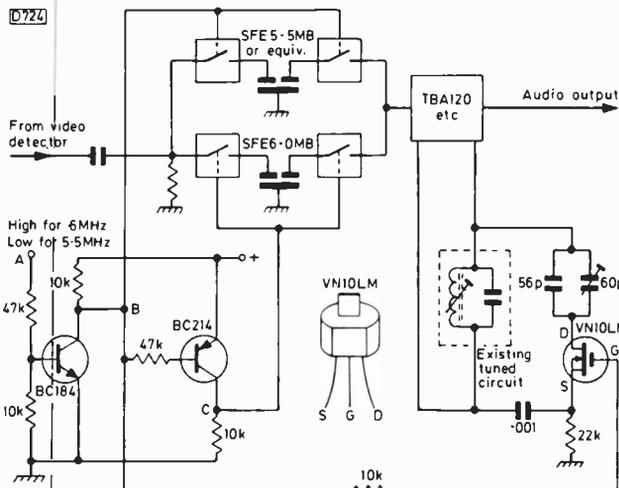


Fig. 2: 5.5/6MHz switched sound circuit with a 4066 selecting one or other ceramic input filter and a small power MOSFET switching in or out extra capacitance in the detector tuned circuit – the exact value of the added capacitance will depend on the existing detector circuit.

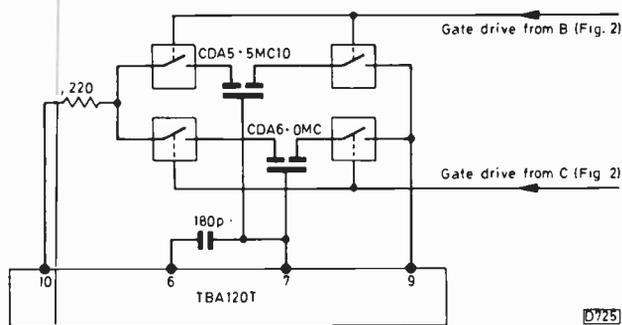


Fig. 3: Use of a second 4066 when ceramic filters are used in the detector circuit.

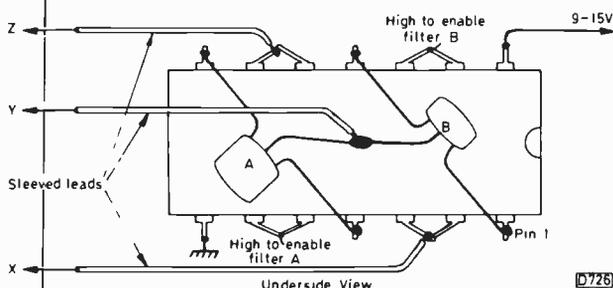


Fig. 4: Solder the filters directly to the pins of the 4066, on its underside. Wires X, Y and Z can then be inserted in the holes used by the original filter – their stiffness will support the assembly above the board. Keep the connecting wires as short as possible.

use the correct one. A further 4066 chip can be used to provide switching (see Fig. 3).

Practical Details

By wiring the switches Christmas tree fashion, with the filters and the connecting wires soldered directly to the i.c. pins, a very compact assembly which should fit comfortably into whatever space is available is achieved (see Fig. 4). The filters are symmetrical about the centre pin and can be fitted either way round. Keep the connecting wires short to avoid r.f. instability, especially if the intercarrier chip's output circuitry is close to the input. The current drawn by a 4066 is negligible – its supply can be taken from that of the intercarrier sound chip. Standard 4000 series devices require a supply of between 3-15V.

It's important for the health of a 4066 i.c. that the voltages applied to the switches lie somewhere between those at the supply terminals. If the potential applied to a switch is close to one or other of the supply rails the switch's linearity may be degraded, but since the signal is frequency modulated this will have no adverse effect. Drawing current through the switches should be avoided. The resistance of a CMOS switch in the on condition is typically about 50Ω, low enough to make little difference to the level of the intercarrier sound signal or to the matching of the filters. Control voltages to turn the switches on and off can be provided by a couple of bipolar transistors as shown in Fig. 2.

The remote-controlled Grundig set (CUC220 chassis) for which the modification was originally devised has a button on the keypad intended for selecting the sound circuitry for transmissions using the German stereo/bilingual system. This button, which produces a level change at terminal 12 of the frequency synthesizer board, provides a convenient way of switching between the 5.5/6MHz sound standards. A connection was made between terminal 12 and point A in Fig. 2. The two bipolar transistors were fitted inside the tuner/i.f. can near the filters, with a wire lead to them fed through a slot in the can. This set makes an excellent receiver for DX use incidentally: the multiband electronic tuning allows rapid band scanning and the digital channel number display makes station identification very simple.

With sets that use a TBA120T, no alignment is required when adding the extra filters. Where an LC tuned circuit is used in the demodulator stage, make sure that the extra wiring and components have not detuned the circuit too much. Tune to a UK station, set the switch to 6MHz, and adjust the coil slug *very slightly* to find the position giving clearest sound. Then switch to 5.5MHz and adjust the trimmer for the loudest hiss – or, if a continental station is available, for clearest sound.

The 4066 is sold under various guises such as the CD4066, MC14066 or simply the 4066 by most constructor component dealers. A suffix beginning with B means that the device will work on supplies up to 18V. The VN10LM power MOSFET, a Siliconix device, is available via RS Components Ltd. The VN10KM, which differs in incorporating protection diodes, is available through Tandy stores. Suitable 5.5MHz input filters are available from Sendz Components. For i.c.s such as the TBA120T, TA7146P, μPC1391H and μPC1382C the correct detector filter is type CDA5.5MC10. With i.c.s such as the CA3065, TA7176P and AN241 use detector filter type CDA5.5MD3. The difference is between quadrature and differential peak detection.

Quick Checks Q and A

Part 3

S. Simon

The Thorn 3000/3500 Series

The problem is "no results" with the tube heaters out. What's the first thing to check?

The red button cutout. If there's an a.c. supply at one tag but nothing at the other it's obviously open-circuit. Did it die or was it killed? Before subjecting it to another possible strain, check the rectifier diodes W601-4 at the front of the power supply panel for shorts. If these read correctly, press the red button and see if it holds. If the set now functions correctly it's likely that the cutout itself is beginning to feel old and is in need of replacement, or that there's an intermittent short which has yet to show up.

If the tube heaters are alight but there are no other obvious signs of life, what initial checks should be made?

First ensure that the full d.c. supply is present at the body of the R2010 chopper transistor at the front left of the power supply panel. If it's not reaching the transistor, the surge limiting resistor R609 near the h.t. fuse (F603) could be open-circuit. If the full d.c. is reaching the chopper transistor, its drive circuit is probably not working. The key check point is the 100Ω section (R607) of the "dropper" resistor assembly at the rear of the panel – the right-hand section. The tag at the right side end should read about 12V, the next one in about 45V. If the latter figure is more like 30V, suspect the 45V supply reservoir capacitor C607, 1000μF 63V – it's likely to be open-circuit. This is a frequent cause of non-operation.

If however the tag is at some 45V and the end tag registers much the same voltage instead of 12V, the chances are that the 30V supply fuse F602 (500mA) on the underside of the panel or, if this is intact, the chopper driver transistor VT605 (E1222) is open-circuit. VT605 is underneath, on the left-hand side, with a heatsink on it. If the voltage at the right-side dropper tag is a lot less than 12V and the dropper itself is hot, VT605 could be short-circuit or is perhaps being turned on too hard.

Diode W610, which is in series between the emitter of VT605 and chassis, should not be overlooked. If it's open-circuit, this could be the reason for the voltage at the end tag being high. If it's short-circuit, VT605 will be turned on too hard (low voltage at the end tag).

There are many other possibilities of course, including the front right 30V zener diode W605 which, if defective, will stop the chopper working.

The picture is very distorted, in an hour-glass fashion (amongst other things), and there's a hum on the sound. What are the main suspects and where are they?

The 1000μF electrolytic previously mentioned (C607) and the main h.t. electrolytics under the front left side (C602/3/6) are the main suspects. A small mirror can be used to view the condition of C602/3/6 without removing the power supply panel. Severe corrosion may be seen. This check should be made as a matter of routine, since the unit often leaks without other signs of distress, spilling corrosive fluid on to the lower panel. This upsets the working conditions of the offset pulse generator with the result that the picture goes dark etc.

The effects of this leakage can be hard to clear – a

replacement panel as well as a new electrolytic unit may be required. In addition to using the mirror, a torch or bench light should be used to examine the condition of the components at the front left of the video panel – look for the presence of dampness, which can often be cleared before damage is done.

The complaint is that the picture got darker and darker. Which key component in the set could be responsible?

The key component is the 1.5Ω wirewound resistor R907 on the small beam limiter panel at the top. The reason for the dark picture is that the voltage across this resistor, which is in series with the line output stage, has brought the beam limiter circuit into operation. The voltage should be 1.3V under no-load conditions. If it's higher, R907 is likely to have increased in value.

R907 is a key check since no voltage across this resistor (with the resistor intact) shows that the line output transistor is not being switched on whilst excessive voltage (with the value of R907 correct) indicates the presence of an overload in the line output stage.

There's a sudden drop-out of one primary colour. For example green may be lost, leaving red and blue to give a magenta picture. What and where are the first checks to make?

Voltage checks should be made at the tube base socket. If green is lost, check at pins 5 (green first anode) and 6 (green cathode). Pin 7 is the green grid pin, which is connected to the other two grid pins. Compare the readings at pins 5 and 6 with those at the equivalent red and blue gun pins. In all probability, the voltage at pin 5 will be much lower than the 400-900V specified. If so, check the convergence panel to ensure that all three beam switches are on. Leakage through these switches is extremely common and is the main cause for one of the primary colours being absent. If a replacement switch is not to hand, remove the faulty one and join the centre to the top contacts or divorce the lower contacts from chassis. The associated decoupling capacitors can go short-circuit – if necessary check after disconnecting one end. These are the ones on the convergence panel – those on the tube base (spark gaps) are also not above suspicion.

If the first anode voltages are all above 400V, what else is likely to cause the loss of one primary colour? We are talking about sudden loss, not a gradual loss that could throw suspicion on the tube.

Since the first anode voltages are correct it's likely that one of the cathode voltages is incorrect. One is probably much higher than the other two. Note that the three RGB output transistors are on the left-side video panel, at the rear with heatsinks.

First check the relevant collector voltage to ensure that the supply is actually reaching the collector. Then switch off and check the suspect output transistor with an ohmmeter to ensure that it's not open-circuit base-to-collector or base-to-emitter. This is the most likely situation. If the transistor is all right, check back from the emitter to the preceding pnp driver transistor and if

necessary to the npn transistor prior to this.

What are the weak links in the design of the RGB output stages?

The weak links are where the heat is. Apart from the output transistors themselves, the thick-film unit used as the load and biasing resistors in later models is a source of trouble. Earlier models had three separate wirewound load resistors which were much more reliable. The thick film unit is similar to (but not the same as) that used in the Pye 725 etc. chassis. They all tend to deteriorate, giving intermittent results depending on which section is affected. Change the unit if there's the slightest doubt.

The picture is marred by regular vertical rippling, accompanied by a high-pitched twittering noise. This can be caused by an open-circuit electrolytic on the power supply panel, but what should be checked first?

It's quite common for the core of L502 to fall out and drop on to the decoder panel. L502 is in the 60V supply line to the line output stage, and is located under the left side of the swing-up panel. If the coil former is empty, look below. Provided the set has not been disturbed, the core will be found. Refit and lock it in firmly.

The complaint is of smoke and a smell of burning. Inspection shows that some of the resistors on the convergence panel are burnt. What's the cause?

There are two large wirewound resistors (R707/8) on the panel. In the 3000 chassis both are 10Ω but in the 3500 chassis one is 18Ω. When one of these resistors goes open-circuit, current is diverted through small components which are unable to bear the load. Hence the burn up. The first move should be to identify the large, open-circuit resistor and replace it, after which the burnt components can be checked and replaced as necessary.

Christmas Story

Bryon Pascoe

As Christmas approaches I recall last year's events.

Mike phoned the day before Christmas Eve to say he thought the tube in his Siemens colour set (FC211) had gone. The set's been a decidedly awkward customer and the news of its failure so close to Christmas gave rise to a sinking feeling in the stomach. A quick nip of the Christmas booze, whilst the lady of the house wasn't looking, turbo charged the system however and off I went. Mike's wife came to the door and bustled me in out of the cold, and the usual conversation that always goes with a TV breakdown followed. During this she said that Mike had finally given in to pressure and agreed that they could have a video for Christmas – provided the tube in the telly hadn't gone. A challenge indeed.

So, with fingers crossed we set about the monster. The fault turned out to be an open-circuit line flyback tuning capacitor (0.01μF, 1.5kV) that had knocked out the BU208. Mind you I went through three BU208s before finding the cause. No wonder they sell them in tens nowadays. Then smiles all round.

"I'll bring a video along tomorrow, about 7 p.m." I said, bearing in mind all the other promises I'd made for Christmas Eve. Topped up with four hours' semi-conscious slumber, I woke up to find the temperatures outside below freezing. So on with the thermal underwear. Along with all the other gear loaded into the estate car went two VHS machines – I'd a full day's calls ahead.

"It'll be after seven" I said to Mike's wife over the phone. "That's all right, he won't be back till 8.30" said she. "By the way the telly's o.k. except when it goes very bright and red." That gut feeling again, with thoughts that it may well be the tube this time.

I arrived at 8.45 and was again bustled inside out of the cold. Deposited one video in its sealed carton on the floor. "You'd better check the set first. Shouldn't think it's very much." What confidence!

"No problem" I said as I pushed the loose tube base connector back into place. What an engineer! More chat as I slit the carton open.

"Easy to work?" asked Mike.

"Piece of cake! Here we go" I said, touching the play button. There was this ghastly whining noise as something inside the machine attacked the tape. "Faulty tape" said I quickly as I managed to get the machine to present me with the cassette and a long length of mangled tape. "It's that common is it?" asked Mike.

"Not really, but I've known it before." I inserted my own cassette containing a recording of a film I'd not yet seen. That noise again! Touching the stop button didn't seem to have any effect.

"Machine's got a fault. No problem, I've another one in the waggon." Out into the cold again, quick dive into the muddle, extract recorder number two and dash back into the warm. Unpack again, more chat, unwrap new cassette, insert, touch play. Once again that noise as yet another tape got done in. Gut feeling as I caught sight of Mike's expression. Beginning to run out of chat. "Got to be something silly." "Sure has" said Mike.

Sweating now, and not all due to Mike's central heating. Look at instruction book. Print going out of focus. Keep calm. Then it dawned. "I know what the problem is – it's the dew. You know, condensation" I explained to a bewildered Mike.

Half an hour later after a drink and an uncomfortable wait, I loaded another cassette. Touch play. That welcome, silky sound greeted my ears. Smiles all round and an exchange of Christmas greetings, then off to the homestead. Got back just before Christmas Day began.

A week later I pulled into Geoff's garage. Whilst filling up we exchanged Christmas business stories. Told him about the video demonstration at Mike's and he laughed like a drain.

A couple of days afterwards Geoff brought his video in for attention. It had a recording fault. Fixed it within an hour and kept it for the night to watch that film on my tape, since repaired with a large chunk missing. Down to the garage the following morning, another cold one. No Geoff, so I left the recorder in his office for him to take back that evening. Phone rang just after eight. It was Geoff.

"This recorder you were supposed to fix. It's just knackered my best tape" he bawled.

Immediate recall by me. "Remember what I told you about the demonstration at Mike's? Well, it's just happened to you!"

"Oh no, the bloody dew" came the faint reply. Laughed like a drain I did.

Satellite TVRO System

Part 3

Nick Harrold

This next part in the series deals with one way of handling the audio signal. There are many 4GHz satellite signals that can be received on even a small terminal such as this. Unfortunately however there's no single sound standard. Some transmissions carry the audio on a subcarrier, some use a different transponder entirely, whilst some use sound in sync. The circuit to be described caters for the multitude of different audio subcarriers in use, being tunable over the range 5.5-8MHz.

By far the strongest signal receivable in the UK at the moment comes from the Russian Gorizont satellite, which is in orbit at 14°W (London coordinates 30° elevation, 198° true azimuth). The 3.675GHz spot beam can even be received without a dish by just pointing the open end of the waveguide at the satellite. This spot beam carries two sound channels, the TV sound on a 7MHz subcarrier and a radio channel on a 7.5MHz subcarrier. To achieve a good signal-to-noise ratio, these two channels are both compressed at the uplink and must therefore be expanded again in the receiver if the correct dynamic range is to be obtained.

The Sound Board

A block diagram of the tunable sound i.f. board is shown in Fig. 7. It consists of two parts, a tunable phase-locked loop to demodulate the signal and a pilot-tone gain-controlled amplifier. An NE564 i.c. is used in the PLL while the amplifier is built around an NE571 i.c.

Fig. 8 shows the PLL circuit. The sound subcarrier is

Components list – Figs. 8 and 9

Resistors:	R30	95k4±	C20	100µF, 16V	
R1	5k6	R31	56k	C21	470µF, 16V
R2	1k2	R32	10k	C22	330µF, 12V
R3	47Ω	RV1	1k	C23	10µF, 12V
R4	470Ω	RV2	5k	C24	.001
R5	1k2	RV3	10M	C25	.001
R6	1k	*13k+1k		C26	.002
R7	1k	†6k8+200Ω		C27	10µF, 12V
R8	18k	‡100k/2M2		C28	0.1
R9	2k2			C29	0.22
R10	15k	Capacitors:	C30	100µF, 16V	
R11	15k	C1	2p	C31	.01
R12	10k	C2	100p	C32	10µF, 16V
R13	5k6	C3	.01	C33	.01
R14	1k2	C4	100p	C34	150p
R15	1k	C5	.01	C35	150p
R16	2k2	C6	100p	C36	.01
R17	10k	C7	.01		
R18	2k2	C8	.001	Coil:	
R19	5k6	C9	.01	L1	3.9µH
R20	14k*	C10	.001	Semiconductor	
R21	14k*	C11	.001	devices:	
R22	7k†	C12	.001	IC1	NE564
R23	1k	C13	47p	IC2	NE571
R24	6k2	C14	.001	IC3-5	747
R25	3k3	C15	1µF, 12V	Tr1-2	BC109
R26	100k	C16	1µF, 16V	D1	BB109
R27	95k4±	C17	10µF, 16V	D2	6.2V
R28	100k	C18	10µF, 16V	VR1	7805
R29	100k	C19	100µF, 16V		

taken from the output of the wideband f.m. demodulator described in Part 1 – from the emitter of Tr3, Fig. 3. This point is prior to any de-emphasis or filtering, which would attenuate the subcarrier. The signal is first amplified by Tr1 and then fed via the drive level control RV1 to the NE564's input at pin 6.

As with the NE564 video demodulator described last month (IC1, Fig. 5) the drive level is adjustable for optimum quality output. The oscillator frequency is set by varicap diode D1 in conjunction with C13 – RV2 applies a variable d.c. bias to D1 for tuning over the required frequency range. The audio output at pin 14 is fed to Tr2 for further amplification, up to a level of about 100mV, before being fed to the expander circuitry.

Expander Circuit

The expander circuit is shown in Fig. 9. The audio input is fed to pin 2 of the operational amplifier IC3a. The output at pin 12 follows two paths.

The first path consists of a high-Q 11kHz tuned amplifier whose active sections are IC3b, IC4a and IC4b. The amplified 11kHz pilot-tone signal output at pin 10 of IC4 is at a suitable level to drive the rectifier circuitry in IC2 (input at pin 2).

Path two feeds the signal to the variable-gain section of IC2 via the notch filter comprising IC5 and the associated components. This notch filter is tuned to 11kHz and is included to remove the annoying whistle that would otherwise be present on the final audio output.

The processed audio output appears at pin 7 of IC2 and is then passed to the de-emphasis network C31/R32. The resultant audio is suitable for feeding to a good quality amplifier.

RV3 sets the pilot-tone level. Simple switching is all that's necessary to enable the expander to be taken out of circuit with a non-companded signal.

Construction

The PPL and expander circuitry were built on a double-sided printed panel, with the tracks on one side and the other completely covered with copper. The components were all mounted on the copper-clad side. There's no reason why Veroboard should not be used, provided care is taken.

All the supply rails should be adequately decoupled, and the connections around the PPL in particular need to

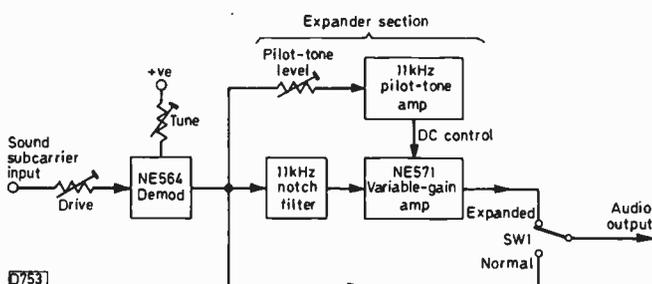


Fig. 7: Block diagram of the sound board.

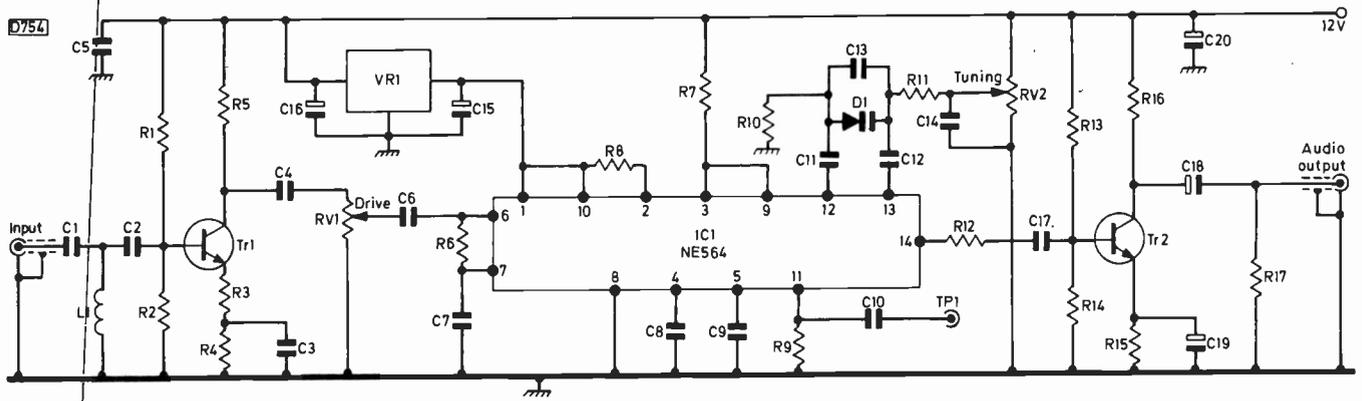


Fig. 8: The PLL sound detector circuit.

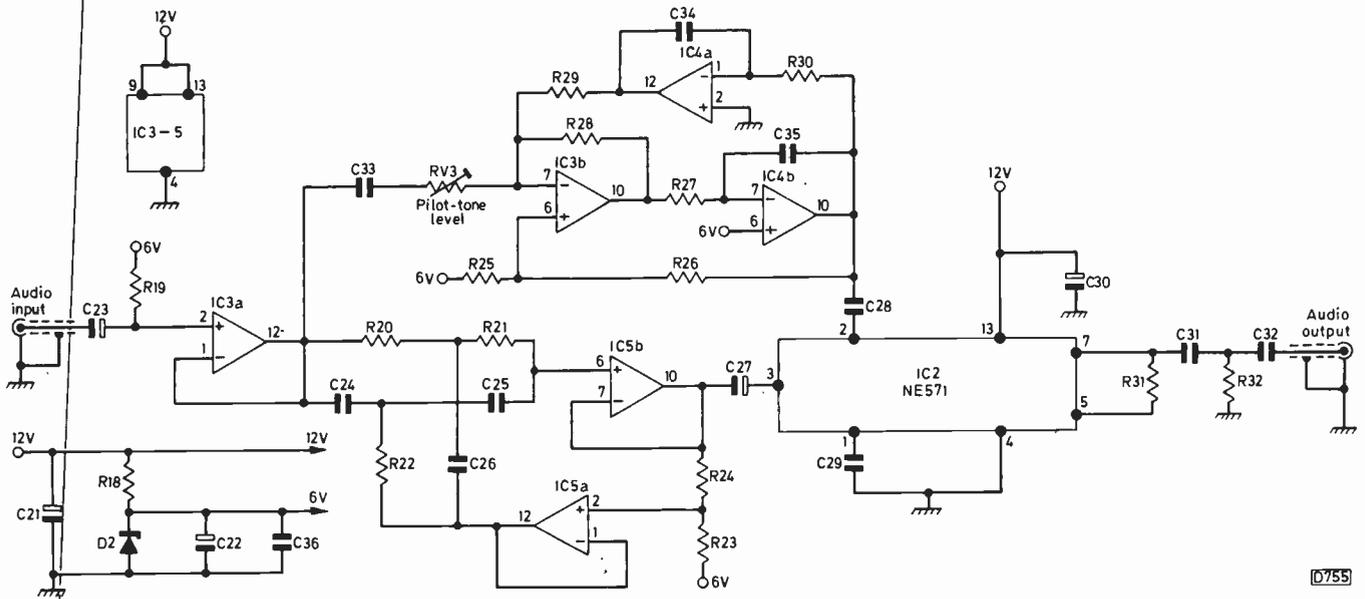


Fig. 9: Audio expander circuit.

be kept as short as possible. RV1 and RV2 are both front panel mounted controls. Use screened cable for the input and output connections to and from the board.

Any varicap diode with a nominal capacitance of 30pF can be used in position D1. The type of varicap diode used in colour decoder crystal oscillator circuits has been found to work well. Types HC7007 and MV2108 are suitable alternatives.

Construction of the expander circuit is less critical and no problems should be experienced provided the leads are kept short.

Testing and Setting up

Assuming that a 12V supply is present, check that pin 10 of IC1 is at 5V. Connect a frequency counter to TP1. When RV2 is rotated, the oscillator frequency should vary over the range 5.5-8MHz. If this range cannot be obtained, try altering the value of C13 slightly.

To check that this part of the sound board is operating, connect a short length of wire to the input capacitor C1. With RV1 set at maximum, shortwave broadcasting stations should be heard as RV2 is rotated. Alternatively, coupling the input close to the video detector stage of a conventional TV set should enable the 6MHz intercarrier sound signal to be resolved.

Moving on to the expander circuit, check that the voltage at the cathode of zener diode D2 is approximately 6V. Connect the output from an audio signal generator to

input capacitor C23 and, with an oscilloscope connected to pin 3 of IC2, tune the generator through the range 0-12kHz. A sharp notch should occur at 11kHz. Depending on component tolerances, slight adjustment might be required to the values of R20/21/22 and C24/25/26 to achieve this.

Connect the oscilloscope to pin 2 of IC2 and again tune the generator through the range 0-12kHz. This time a sharp peak should occur at exactly 11kHz. Slight changes in the values of R30, R27, C34 and C35 can be tried, but be careful not to increase the bandwidth too much. This part of the circuit has a Q of 100 and a bandwidth of 110Hz: these characteristics must be preserved if the circuit is to function correctly. Too great a bandwidth will result in spurious operation of the expander caused by high-frequency speech sibilants etc.

Next couple the output from the PLL to the expander's input. Assuming that you are receiving the Horizont satellite, tune the PLL to 7MHz. With the expander switched out, adjust RV1 for best sounding audio consistent with minimum video buzz. Switch the expander into circuit and adjust the amplitude of the pilot-tone signal (RV3) so that the NE571 i.c. operates over the linear portion of its gain range. A dramatic change in the signal's dynamic range should be noted when the expander is switched into circuit.

A correction should be noted to Part 1, where the 38V supply reservoir capacitor was shown in Fig. 4 with a voltage rating of 35V instead of 64V.

Servicing the Thorn 1600 Chassis

John Coombes

This solid-state monochrome chassis was used in three 17in. transportable sets — the Ferguson 3831, Marconiphone 4831 and the Ultra 6831. They date from the mid-seventies. It's a somewhat unusual chassis with a simple half-wave mains rectifier, a "dropper resistor" assembly and a shunt regulator which is in series with the line output stage (see Figs. 1-2).

Field Collapse

The most common fault is field collapse. The field output stage was modified twice, so that any of three circuits may be encountered (see Figs. 3-5). Failure of the amplifier/output i.c. is the usual cause and for replacement purposes Thorn supply the small module used in final production. Whenever the chip has failed it's worth checking that the supply is correct at 28V. This voltage can rise if the shunt regulator is inoperative due to R157,

which is part of the dropper assembly, being open-circuit.

If necessary check R108, C99, R109 and the scan coils for being open-circuit, and C88, C101 and C102 for being short-circuit. The height control R95 can also go open-circuit, sometimes causing intermittent field collapse.

If the field hold control is set at one end of its track, check the field oscillator transistors VT7 and VT8 (both BC147) and the value of R88 (470k Ω) which is in series with the hold control.

No Results

No sound or raster can be due to several things of course. First check the mains input fuse F1. If it's open-circuit, check the mains filter capacitor C97 and the h.t. rectifier W24 for shorts. If the fuse is o.k. but there's no h.t., check sections R112, R114 and R120 of the dropper assembly. If R112 (fusible) is open-circuit, check the h.t. reservoir capacitor C104 which could be short-circuit.

Alternatively the trouble could be in the line timebase. The first check is to ensure that the shunt regulator is working, i.e. that there's 30V at the junction of R146/R156. No voltage here could mean that the line output stage is inoperative. Check the e.h.t. stick rectifier by removing the e.h.t. connector — beware of possible shocks. If the sound then comes up, the e.h.t. stick (Thorn recommended replacement type TS20-11HAC) could be faulty or the line output transformer could have shorted.

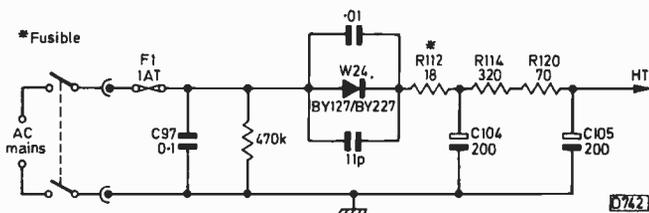


Fig. 1: Mains input/h.t. rectifier circuit.

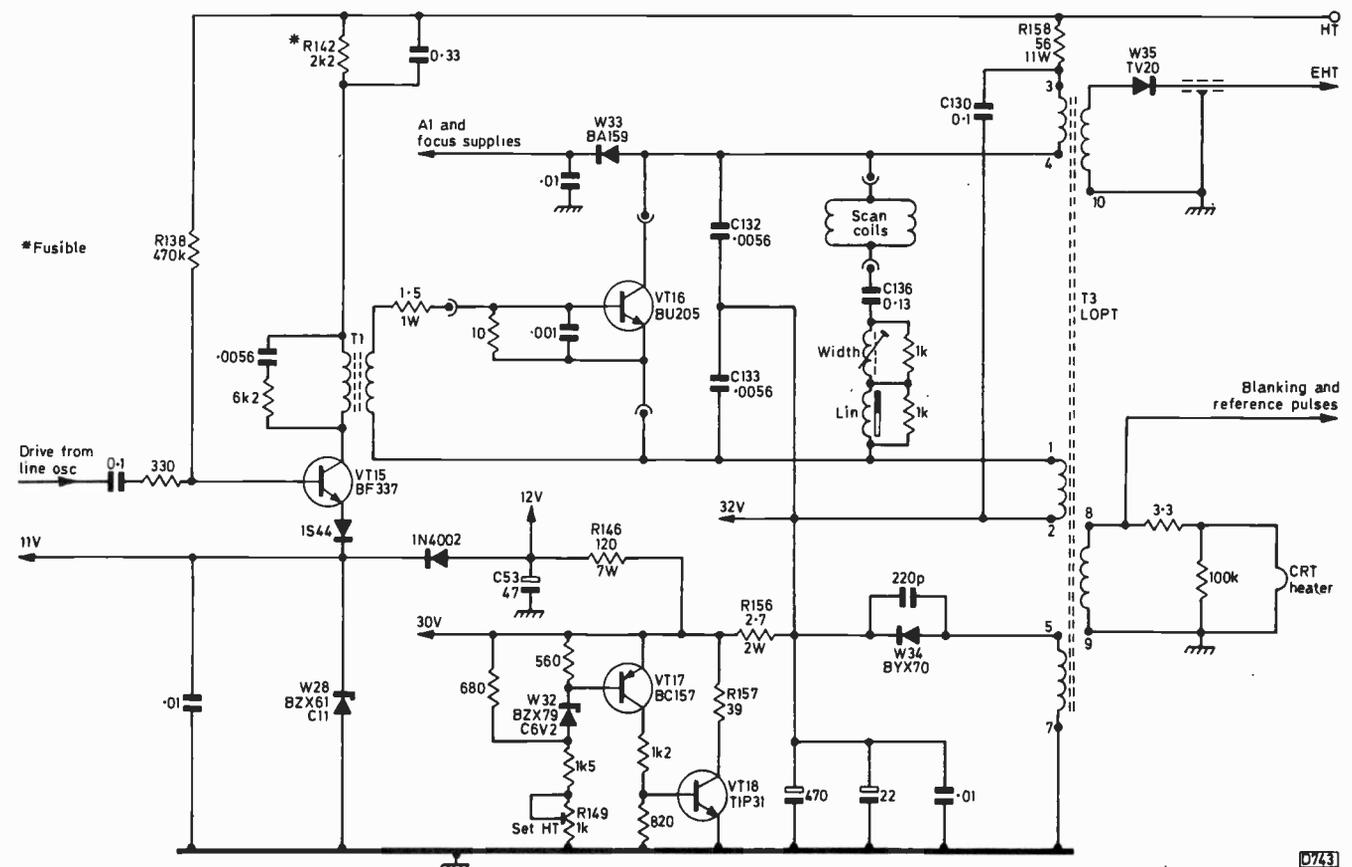


Fig. 2: The line driver and output stage circuits, with shunt regulator VT17/VT18 and associated components.

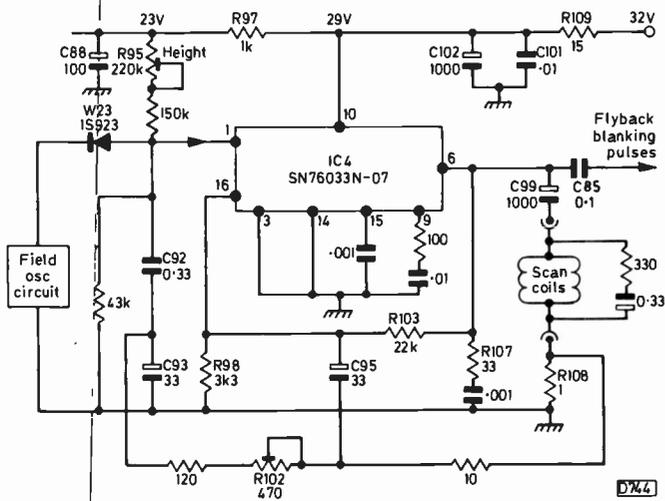


Fig. 3: Field amplifier/output circuit used in early sets.

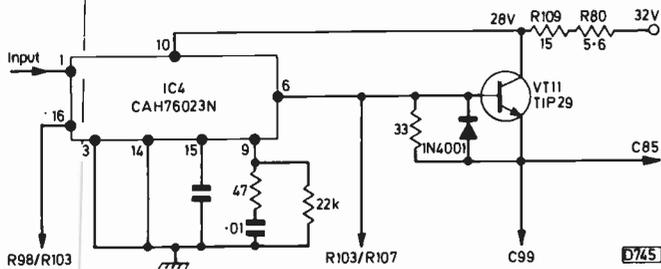


Fig. 4: Modified field output circuit with VT11 added.

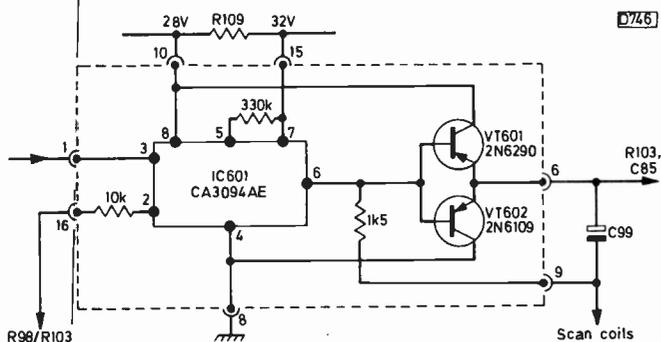


Fig. 5: Final field amplifier/output circuit using module.

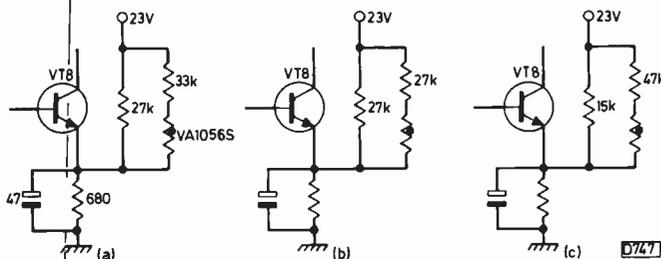


Fig. 6: Field oscillator bias circuit modifications. (a) Early. (b) With circuit shown in Fig. 4. (c) With Fig. 5.

bias resistor R138 (470k Ω) going very high in value. The result can be a dead line output transistor or a very hot one with the line output stage working at a very low level of efficiency.

Set HT Control Inoperative

If there's a normal picture but the set h.t. control R149 has no effect, check whether R157 is open-circuit. As previously mentioned, this can contribute to failure of the field timebase chip. The correct procedure for adjusting R149 is to connect a meter (20k Ω /V) switched to the 250V range between the junction of R158/C130 and the cathode of W34 and then, with the brightness, volume and contrast controls at minimum, set R149 for a reading of 140V.

No Sync

In the event of no sync, first check the sync separator transistor VT9 (BF197). If necessary check C111 (270pF) for leakage and C103 (0.22 μ F)/ R115 (3.3M Ω) for being open-circuit.

Tuning Troubles

Tuning troubles are not unusual. There's a varicap tuner (ELC1043/05 or Thorn SC4) and a TAA550 tuning voltage stabiliser. If R5 (24k Ω) which feeds the stabiliser goes high in value the result can be no signals at all. In the event of tuning drift the first suspect is the TAA550 (IC5) — check whether the voltage at the junction of IC5/R5 is varying. Beware however — this can be due to faulty pushbuttons, and may affect one channel or several. The other possibility for drift is of course the tuner.

Sound, No Raster

The most likely cause of sound but no raster is that the BF337 video output transistor VT5 is open-circuit. The recommended replacement is type BF258. Other things to check if necessary are the video driver VT4 (BC147) and the TCA270SQ detector/a.g.c. chip (IC1). Check the voltages around the i.c. carefully: if incorrect, replace the i.c. The chip can be responsible for sound with a blank raster.

Weak Signals

In the event of a snowy picture with noisy sound, check the i.f. transistors VT1, VT2 (both BF196) and VT3 (BF197), the tuner supply resistor R13 (10 Ω) and the tuner.

Sound Faults

For no sound, first check whether the 27V supply is present at pin 10 of the SN76013ND-07 audio output chip (IC3). If not, check R74 (56 Ω fusible) for being open-circuit and W19 (BZX61-C27) and C82 (470 μ F) for being short-circuit. Next check whether the TBA120AS intercarrier sound chip (IC2) is being supplied at pin 11 (13.5V). If not, check the feed resistor R46 (1k Ω) and the decoupler C58 (100 μ F). If necessary check whether the loudspeaker (35 Ω) or the output coupling capacitor C84 (220 μ F) is open-circuit. Either chip can be responsible for no sound or distorted sound. The inter-chip coupling capacitor C72 (0.22 μ F) and a displaced speaker cone are other causes of sound distortion we've encountered.

turns (this can be intermittent, the set working for an hour or so before loss of sound and raster). If there are still no results, check the line output transistor for being short-circuit and the driver transistor's feed resistor R142 (fusible) for being open-circuit. The driver transistor VT15 (recommended replacement type BF259) could be short-circuit. Other possibilities are an open-circuit primary winding on the driver transformer T1 or shorted turns on the line scan coils L25/26.

A point to watch out for is the driver transistor's base

Long-distance Television

Roger Bunney

The early autumn traditionally produces enhanced tropospheric activity. Certainly tradition ran true to form in 1983. Prevailing high pressure towards the end of the month gave excellent reception at v.h.f. and u.h.f. from the 22nd to the 30th, though the ATV contest during the weekend 10-11th unfortunately occurred during a wet and depressing couple of days. Sporadic E propagation has waned and was concentrated in the first part of the month. SpE loggings are as follows:

- 6/9/83 TSS (USSR) ch. R1; RTVE (Spain) E2.
- 9/9/83 TVP (Poland) R1; MTV (Hungary) R1; ORF (Austria) E2a; ARD (W. Germany) E2.
- 10/9/83 RTVE E3.
- 11/9/83 TSS R2.
- 12/9/83 RTVE E3; ARD E2.
- 13/9/83 RTP (Portugal) E2; RUV (Iceland) E3.
- 18/9/83 Unidentified ch. E2 programme material (1710 BST).
- 23/9/83 Many short periods of unidentified programmes throughout the band. CST (Czechoslovakia) R1; ARD E2.
- 24/9/83 Auroral activity throughout Band I. Programmes and test cards, mainly unidentified.
- 26/9/83 As 24th.

The enhanced tropospheric propagation during the last ten days of September gave excellent results for many enthusiasts throughout the UK, with a high incidence of tropospheric ducting in many parts. Here at Romsey for example ORF ch. E9 Bruck (20kW e.r.p.) was logged on the 26th at 0850 though other ORF stations were absent – Bruck is close to the Hungarian border, a distance of some 830 miles. Later that same hour Switzerland ch. E35 (TSI) was seen, though the other high-power outlets were not present. The various u.h.f. French channels (TDF) spread into southern Scotland (over land paths), W./E. German stations as usual swamped the eastern UK, and farther to the north east many NRK (Norway) and SR (Sweden) Band III/u.h.f. signals were logged. Arthur Milliken (Wigan) noted strong Swiss signals from Saentis (TSI) on the 29th for example. Band III was very active at

Romsey, with W./E. German stations. The Belgian TV services were seen in full colour in S. Devon, Presteigne (Wales) and on the east coast, and NRK ch. E2 was observed at several locations (rather an unusual logging).

The high-pressure system was drifting away by the 29th, with rain spreading from the west. Thus ended what had been a very rewarding period. Though good, the opening can't be classified as memorable or intense. U.H.F. reception from W. Germany was too selective – at my distance it was necessary to seek out the signals. The increasing problem now of course is the many UK u.h.f. channels used for early morning TV programmes.

ATV reception at 435MHz proved exciting, with the Belgian station ON5VW providing P4 level pictures at Romsey on the 27th, along with another co-frequency picture. Several UK stations, including G8LES (see later), were also received. There were several reports of W. German/Dutch ATV signals being received in E. Anglia.

There have been widespread reports of RTL (Luxembourg) using the 5534 pattern (5544 with a clock inlay) on ch. E7, with their new system B transmissions from a newly replaced mast. Paris has been seen testing scrambled transmissions on ch. 5, in preparation for the Canal Plus service. The 315m TV mast at Wavre, Belgium, carrying v.h.f. and u.h.f. aerials, has collapsed. Fortunately the earlier mast was not dismantled, enabling the v.h.f. services to be continued.

My thanks to Arthur Milliken (Wigan), Iain Manziens (Aberdeen), Simon Hamer (Powys), Brian Renforth (Torquay), Nick Harrold (Southend) and David Moller (Eastbourne) for sending in logs of their reception.

Chain Letter


A chain letter suggesting that if the recipient continues the chain he will receive in short time over 1,000 picture postcards is circulating in DX circles. My personal view is that such activities should not be encouraged – I returned the letter sent to me to the last name on the list.

News Items


Taiwan: The Chinese Television Service (CTS) in Taipei recently opened its first u.h.f. transmitter on an experimental basis, with some two hours' programmes daily. The intention is to provide an educational service on this outlet.

Australia: It seems that the cultural TV services at present being transmitted in Melbourne and Sydney on ch. 0 are to close on January 1st, 1985, leaving just the u.h.f. outlets in operation.

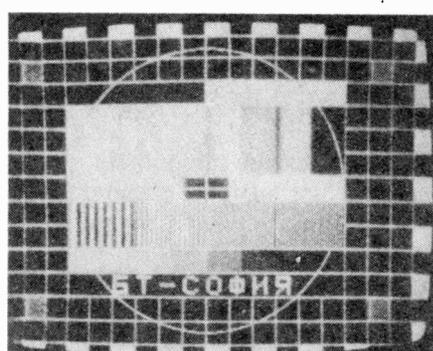Falkland Islands: There are rumours of a possible Falklands TV service following the installation of a grade



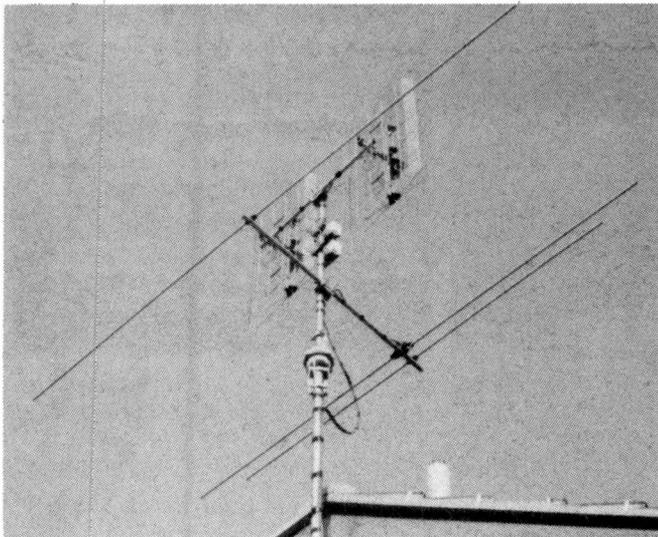Left: The Basque (N. Spain) ch. E33 Bilbao transmitter's station identification slide – the transmitter was logged in the UK (south coast) during the recent enhanced tropospheric conditions. Centre: Saudi Arabian ch. E7 test pattern. Right: Standard test pattern used by Bulgarian TV – courtesy BDXC.



A. Palfreyman's aerial system at Sheffield.

B. Intelsat ground station on the islands. The only TV available at present is via cassettes.

E. Germany: The last Band I transmitter, Cottbus ch. E4, is to close during 1985 when the DFF-2 service moves to u.h.f.

Satellite TV

From the various US satellite/electronics magazines we receive it's evident that prices of satellite receiving equipment across the Atlantic are falling fast. Most quality systems now come within the \$1,400-\$1,700 bracket, though a complete system comprising 6ft dish, mount/support and the electronics has been seen for just \$760! A trade catalogue lists a 100° LNA with spun dish and electronics at just \$1,295. Reports show that 90 per cent of home satellite receiver users live in rural areas.


On the commercial front, Hugh Cocks (Bre Cottage, Cripps Corner, Staplecross, Robertsbridge, East Sussex TN32 5RY) is now offering a 4GHz receiver package (electronics) for under £400 complete in the UK. The receiver consists of a four-stage LNA and a double-conversion converter with video and audio outputs, a.f.c. to defeat the Gorizont 1 dispersal signal and an optional audio expander. Further details of the KB1 unit are available from Hugh (send SAE please).

Spectrum Changes

Gosta van der Linden reports that the re-engineered French Band I service will have three channels instead of four. These will be as follows: ch. 1 55.75MHz vision carrier, ch. 2 60.5MHz vision, ch. 3 63.75MHz vision, with the sound carrier spaced 6.5MHz below the vision carrier in each case. The Band III channels previously referred to as chs. 1-6 are now known as chs. 4-9.

As mentioned last month, there are to be changes in UK Band III spectrum use, taking effect from January 1st, 1985. These will present profound problems as far as UK DX-TV operation is concerned. Considerable information, including the frequencies for private mobile radio use, is contained in a news release sent in by Robin Crossley - it's intended for PMR manufacturers. The services will be restricted to mainland UK, i.e. excluding Northern Ireland. They will give users "high quality circuits" based on 50 per cent location and 90 per cent time. Potential users are to be specified shortly by the DTI

SOUTH WEST AERIALS

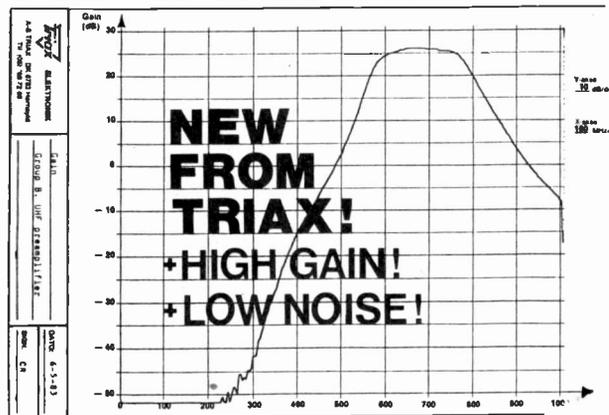

NEW FROM TRIAX - the 2000 range of low noise masthead UHF group amplifiers, high gain (26dB) with low noise (2.2dB typ) within the prescribed groups (A,B,C/D) and sharp cut-off in adjacent groups - ideal for fringe area use and 'non-local' group amplification. The lowest noise UK group amplifier now on the UK market with the high quality expected from Triax equipment.

NEW FROM TRIAX - Mast mounting UHF group filters - the 7000/F3 diplexers Group A (21-34) with B,C/D (39-68) into a single downfeeder; 7000/F4 combines chs.21-51 with chs.55-68. Typical throughout loss 0.8dB, spur isolation typ. 30dB. Provides a DC pass on both inputs. Both 2000 and 7000 series units are housed in weatherproof, condensation-free high impact grey plastic housings.

For all that's best in aerial technology, contact South West Aerials - the reception (and DXing!) specialists.

Triax 2000 series low noise, high gain m/head amplifier (26dBg@2.2dB nf)	£22.25
<small>(state group respd. A,B,C/D)</small>	
Triax 45013 wideband m/head amplifier, separate VHF and UHF	£16.75
<small>i/p, 1 common o/p, 22dB gain</small>	
<small>(suitable Triax power unit 60160A £11.20)</small>	
Triax 7000 series mast mounting filters; 7000/F3, 7000/F4	£9.45
<small>(spec. above) each @</small>	
Wolsey HG36 High gain multiple director yagi (18dBd),	£32.80
<small>state group A,B,C/D</small>	

The above prices include VAT, packing, postage/Securicor delivery. Customer consultancy available - please include SAE with ALL enquiries. Access/Barclay-card welcome. Send 54p for our 1983 catalogue.

South West Aerials, 11 Kent Road, Parkstone, Poole, Dorset BH12 2EH. Tel 0202 738232.
Allow 10-14 days for delivery of stock items.


TV LINE OUTPUT TRANSFORMERS

ADD 15% VAT to ALL prices.

Delivery by return of post

If the Transformer you require is not listed please phone.

RANK BUSH MURPHY		DECCA	
Z146 A640 dual std mono	8.51	MS1700 2001 2020 2401 mono	8.00
Bush A792, A793 single std mono	8.51	MS2404 2420 2424 mono	8.00
A774 single std mono	8.50	1210 1211 1511 portable	11.50
A816 solid state mono	9.00	GYPSY portable	11.50
Z712 T16a T16b mono portable	9.00	CS1730 1733 colour	8.00
A823 A823b A823av colour	10.00	CS1830 1835 colour	8.00
Z179 Z722 series colour	10.00	'30' series BRADFORD colour	8.00
T20a T22 series colour	10.00	80 series colour	8.00
		100 series colour	8.00
WINDING		PHILIPS	
T20A T22	5.51	210 300 series mono	8.00
		320 series solid state mono	8.50
G.E.C.		G8 series colour	8.00
2047 to 2105 3112 to 3135	8.00	G9 series colour	8.50
"GAIETY" FINELINE	8.00	G11 series colour	14.98
2114 portable mono	8.00	KT2 Lopt	9.00
3133 3135 M1501H portable mono	8.00	KT3 Lopt	10.60
DUAL STD hybrid colour	11.00	KB-ITT	
SINGLE STD hybrid colour	10.00	VC200 VC205 VC207 mono	8.00
SINGLE STD solid state 90°	8.50	VC300 VC301 VC302 portable	8.00
or 110°		CVC1 CVC2 colour	9.00
		CVC5 CVC7 CVC8 CVC9 colour	9.00
FERGUSON HMV MARCONI		CVC20 series colour	9.00
1590 1591 1592 1593 mono	8.00	CVC30 CVC32 series colour	8.00
1612 1613 1712 mono	8.00	CVC40 series	14.56
1690 1691 mono	8.50	L.O.P.T TESTER	
1600 1615 series mono	9.74	Total Price Including VAT.	£16.79
3000 3500 EHT or SCAN	8.58		
8000 8500 8800	11.70	Tidman Mail Order Ltd.,	
9000 9200 9300	11.52	236 Sandycombe Road,	
9500 9600 9650	9.56	Richmond, Surrey.	
9800 TX9 TX10	P.O.A.	Approx. 1 mile from Kew Bridge.	
INDESIT, GRUNDIG, TANDBURG,		Phone: 01-948 3702	
TELEFUNKEN, FIDELITY,		Mon-Fri 9 am to 12.30 pm.	
KORTING, TYNE, B+O.		1.30 to 4.30 pm.	
Price on application.		Sat 10 am to 12 pm.	

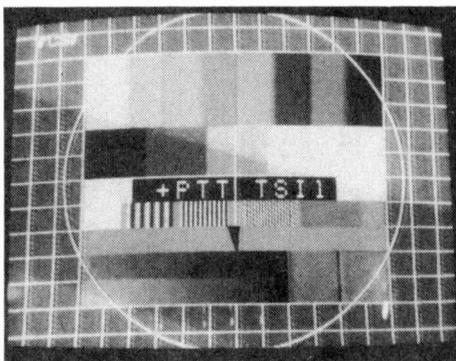

Left: Caen FR3, ch. E28, received by John Tellick during the August enhanced tropospheric conditions. Centre: FuBK test pattern in use by TSI, Switzerland. Courtesy Alexander Wiese. Right: UK Satellite TV caption received on cable in Helsinki via the OTS-2 satellite. Courtesy Petri Pöppönen.

and it's expected that they will include those displaced from Band II, which is to be emptied for further domestic broadcasting, i.e. police, fire, ambulance etc. Other operators will be large concerns with multi-channel needs for message handling or "common base stations providing a service to users generally". The frequencies listed last month are suggested as a guide and have not been finalised (there was also an error – sub-band 3 mobile starts at 216.5MHz). The transmit/receive spacing will be 8MHz with a 1MHz guardband between transmit/receive. The frequency allocations will be chosen to minimise interference to continental services.

We are present awaiting further information on the future of Band I – indications are that the future use of this spectrum will be delayed.

Cordless Phones

The use of the 49MHz cordless phone (which is not approved by BT) is being closely monitored by the authorities in certain areas. In a recent case a company advertising 50 mile range cordless phones was visited by BT and the entire stock seized, including information identifying the importer. A vigilant DXer actually heard the transmission at 49MHz by the owner, telling his staff to "hide everything as there are a couple of BT blokes at the door"! The authorities seem to be taking a firmer line now that the 47MHz cordless phone band is in use.

From our Correspondents . . .

A. Palfreyman has just started DXing in Sheffield, using a twin-Triax u.h.f. grid system and a wideband Band I array at the end of his house and a Grundig 6400 v.h.f./u.h.f. colour receiver. Between the end of July and the present time he has received a large number of signals including TVR (Rumania). The u.h.f. aerials were installed just in time for the August tropospheric openings which gave excellent noise-free colour from NOS (Dutch TV) on various channels, also ARD (W. Germany) chs. 39 and 56.

A DX contact at present resident in Jordan within a few miles of the ch. E3/6 transmitter mast has sent us a local paper showing typical programme timings, as follows: the Koran at 1730 local time then programmes with Arabic news at 2000 and 2300 and close down at 2400. That applies to the main (E3) JTV service. The "Foreign" channel (E6) comes on air at 1800 (French) with 1900-2030 Hebrew, 2030-2300 English and Arabic news 2300-2330.

Kevin Jackson (see October column) reports that during "lift" conditions very good quality signals have been received from Denmark and W./E. Germany using just a

Band III folded dipole at his ninth floor flat in Sheffield. All channels through to E11 are resolved with ease. The August Perseids gave him RAI (Italy) ch. D and SR (Sweden) ch. E5!

Gosta van der Linden (Holland) reports that the AFN-TV service at Soesterberg will be on ch. A80, which is just above the European u.h.f. band at 867.25MHz (vision carrier). The idea apparently is to prevent the local populace viewing the programmes. He's seen Rumania using the PM5544 pattern with "TVR-BUCURESTI" identification in the lower black section, also the electronic pattern favoured by DFF (E. Germany) though without identification insert.

Amateur Television

I've received a long letter from Mike Sanders (G8LES) providing information on his ATV activities. If any reader receives vision with his call sign the signal will have come from his home at Thames Ditton, Surrey. He operates at 10kW e.r.p. peak directional in the 435MHz band, using a rotatable MBM88 (70cm) aerial, and at up to 1kW e.r.p. peak in the 1240-1290MHz band (24cm) with a quad stack of 23-element Yagis. The signals are fed via 1in. diameter coaxial cable with, at 430MHz, a twin Mutek gallium-arsenide f.e.t. preamplifier providing a gain of 26dB with a maximum noise figure of 1.5dB.

144.75MHz is normally used for ATV communication – the Daiwa SR9 receiver with appropriate crystal is the cheapest means of getting this frequency – with visual response via a camera. The 435MHz band is shared with certain PMR users, and as a result ATV pictures sometimes suffer from interference. There are plans to establish 24cm repeaters, some a.m. and others f.m. – the eventual aim is for all 24cm video to be f.m. From Thames Ditton video exchanges are possible with stations in the Midlands and along the south coast, with signal enhancement via aircraft reflection!

Mike also transmits ATV from his car, with a range of typically six miles at 435MHz. Flutter is particularly troublesome and 24cm is to be investigated to see if f.m. mobile working is better.

Any readers seeking further information on ATV, e.g. BATC addresses etc., should drop a line with SAE.

Some days after receiving Mike's letter I heard G4HMG at Iver discussing TV on 750 with a station in Somerset. I called G4HMG who suggested that a "one way" video link would be possible, and in due course grade P1½ pictures were received from Iver over a most difficult path. The local home counties' ATV club is G6HCT – write with SAE to Phil Miller, 33 Switchback Road North, Maidenhead, Berks. Visitors are welcome.

The Betamax Video System

Part 5

Eugene Trundle

The low linear tape speed used in the Betamax system is not conducive to good sound reproduction. An audio frequency response of 50Hz to 8 or 10kHz, with 40dB signal-to-noise ratio and 4 per cent distortion, is typical. Whilst this is no worse than with many machines of other formats, it's unlikely to send a hi-fi enthusiast wild. Even to the non-critical user, the shortcomings of VCR sound are obvious on certain types of programme material. The advent of stereo sound, with narrower sound tracks, tended to degrade the signal-to-noise ratio further. Beta Noise Reduction (BNR) was introduced to bring about an improvement.

Beta Noise Reduction

BNR is in principle similar to the Dolby noise reduction system. During record, h.f. enhancement is given to the audio signal, the higher frequencies being boosted prior to recording on the tape. The degree of h.f. boost is proportional to signal amplitude in a manner that may be familiar to video men as the non-linear pre-emphasis used for the luminance signal in current VCRs. The playback audio amplifier has a non-linear, i.e. amplitude-dependent, gain characteristic, with a falling h.f. response – the characteristic is complementary to that of the recording amplifier. Hence hiss, whose energy is largely in the h.f. part of the spectrum, is minimised during playback – an improvement in signal-to-noise ratio of up to 12dB is achieved.

A degree of "companding" (compression of the dynamic range on record, with a corresponding expansion during replay) is inherent in the BNR system. This can have the effect of slightly raising the background noise during quiet parts of the sound track, the subjective result depending much on the programme material. There's been some adverse comment about this in some quarters, particularly where critical appraisal of BNR sound is made by a listener used to audio hi-fi equipment. Longitudinally recorded video sound will never be as good as conventional hi-fi sound, but BNR certainly gives a worthwhile improvement over the original Betamax sound system.

Beta Hi Fi

While BNR improves the signal-to-noise ratio and with it the dynamic range of the sound signal, it will do nothing for the other parameters of the sound system such as bandwidth, distortion and wow and flutter. Further improvement can be achieved by a system called Beta Hi Fi. This has been pioneered by Sony for use in the USA but has not appeared in European machines. It's quite revolutionary in its operation, though something along similar lines has been announced recently by Matsushita for VHS system use.

The key to high-quality sound with a helical VCR system is to record the sound helically as well in order to get the benefit of the much higher read/write speed. It can't be done at audio base band – whilst the octave range would be adequate and the h.f. response fantastic, with 33 micron tracks the signal-to-noise ratio and other important characteristics would be very poor. As for video, a

modulation system is necessary: the sound signal (mono or stereo) is frequency modulated on to a carrier in the region of 1MHz, so that it sits in the sort of no-man's land between the outer sidebands of the f.m. luminance and the colour-under signals. During playback the fairly narrow-band sound signal is selected by a sharp cut-off bandpass filter before demodulation.

The system appears to work well, and the performance figures quoted are very good – signal-to-noise ratio 80dB, frequency response 20Hz to 20kHz and distortion 0.3 per cent. To retain compatibility with existing machines, the sound signal is also recorded conventionally on longitudinal tracks. The crunch is that the system is at present limited to US machines working to the NTSC standard, because the NTSC luminance and chrominance signals occupy less bandwidth (and tape spectrum space) than European signals. The reasons are tied up with the narrow I and Q (chrominance) signal bandwidths and the 60Hz field frequency. In PAL standard machines the tape spectrum is chock-full of video information, and on playback the presence of sound carriers could cause unacceptable beat and interference effects with the sidebands of the luminance and chrominance signals. Perhaps this gives some clue to the Matsushita "depth multiplex" system, which is understood to be suitable for European use.

Picture Channel Audio Recording

The PC (picture channel) audio idea is nothing to do with recording TV sound but is available for use with VCRs. For vision recording, a wide bandwidth and high information packing density are required. Why not use these desirable characteristics for sound? An adaptor such as the Sony PCMF1 can be used to convert the incoming audio signal to pulse code modulation for recording on the tape helically. The adaptor samples the audio input at about 44kHz (above Nyquist frequency for the specified 20Hz–20kHz input) and produces a digital 14 or 16 bit word signal chopped at TV line and field rate so that it's recognised and accepted by a conventional VCR. The digital signal is fed into the VCR's video input and helically recorded in the same way as a video signal – it occupies virtually the same bandwidth. During replay the VCR's output is fed back to the adaptor (now acting in the decode mode) and converted to base band audio. The performance is impeccable, with 90dB dynamic range and parameters such as distortion and wow and flutter being virtually non-measurable.

The system doesn't like VCRs, such as the Sony SL8000 and Sanyo VTC9300, without a capstan servo. In these machines the capstan speed during playback is tied to the mains frequency and its stability is not good enough to prevent distortion and dropouts on replayed audio. The dropout compensator, so important for TV applications, is not required in the audio PCM mode. In fact it degrades the results, which is why later Sony VCRs have a PCM switch to disable the DOC circuit. VCRs without this facility will work with PCM audio but the performance may be degraded, though not usually to the extent that it

becomes noticeable. In all cases a high quality video tape is recommended, of preferably no longer than two hours' playing time, i.e. the L500. The PCMF1 adaptor works perfectly well with VHS machines – with the above constraints. The longitudinal audio track is left free for cue, identification and announcement use.

Why the choice of two PCM modes, 14 and 16 bit? This depends on the specification and performance of the VCR. The 16-bit mode offers best dynamic range and lowest distortion, and is suitable for machines such as the Sony F1 and C9. For use with three-hour tapes or in machines without a PCM button the 14-bit mode is preferred, as it gives higher data redundancy and error protection, at the expense of slightly reduced performance.

As with any system, an audio chain is only as good as its weakest link. While PCM won't degrade an audio signal, it won't improve it either! Why use it? The advantages seem

to be that off-air timed stereo radio recordings can be made, unattended, for up to three hours, using the VCR's timer; as a transcribing machine for audio use there will be virtually no quality degradation, even on multi-generation copies; while in the professional audio field performance better than that of a conventional quarter-inch tape audio machine is provided. The cost of the PCMF1 is around the four figure mark however, so we won't be coming across many of them in domestic environments. To realise and justify a 90dB signal-to-noise ratio with an audio signal you would need to be in a sealed cave under a mountain at night, having killed off all insects and cut off your blood circulation... How ridiculous to buy stereo equipment with low distortion and high signal-to-noise ratio for use in a car, which is moving most of the time – ambient conditions will in these circumstances offer a signal-to-noise ratio of maybe 20dB, but I digress.

SURVEY OF BETAMAX VCRs TO DATE

To round off this series, there follows a brief run down on the main Betamax VCRs that have been sold in the UK. There are three main manufacturers, Sony, Sanyo and Toshiba. There's not been much "badge engineering", the main exception being the Bush Model BV6900 which is basically the Toshiba V5470B.

Sanyo

VTC9300P and -PN: Large, piano-key operated single-motor machines. Notable as being amongst the first domestic consumer products to use a microcomputer i.e. – it operates in the clock/counter circuit. Three-day, one-event plus serial timer and simple colour picture-pause facility (see Fig. 7). A wired remote pause control is provided, but the VCR/aerial switch is inconvenient. These machines commonly sold at under £300, and in doing so did much to increase the Betamax system's share of the market.

These models have a well-known tendency to shut down due to failure of the 12V regulator transistor Q702 (on panel W3). A reliable substitute is the TIP41.

VTC5600P: An attractive looking machine with sloping front and touch controls. Full infra-red remote control and a one-week five-event timer. Simple pause in colour and a slow-motion facility (25 per cent of normal play speed) are provided. A comb-filter circuit for luminance crosstalk cancellation is fitted.

These machines have proved reliable in service, and such faults as have occurred seem quite random in nature.

VTC5300P: A light and relatively slim machine for its time, with direct drive motors and light touch control including the eject function, performed by a solenoid. One-week one-event and serial timer. The tape counter is mechanical, in contrast to earlier models. Simple picture-pause facility with colour. Luminance comb filter circuit.

Apart from an occasional aversion to worn tapes, few troubles have been encountered and reliability is reasonably good.

VTC5000P: A touch-control replacement for the early VTC9300 series, aimed at the same economy end of the market. All secondary mechanical functions on the deck are performed by the loading motor via a threading ring. Light and small with very low board and component count. Eight-day one-event timer with serial facility. Monochrome pictures during simple still frame and pic-

ture-search modes. Fluorescent tape counter/clock display, as on early models. Luminance comb filter circuit.

At the time of writing these machines are too new to be able to assess their reliability. It promises to be good, though I've had one or two instances of random blowing of the mains fuse and the odd failure of infra-red spool rotation detectors.

Sony

SL8000UB: The first Sony VCR on the UK market. Piano-key operated and fairly bulky single-motor machine. Three-day one-event timer. Simple picture-pause with colour. Wired remote pause control. TV-video switch.

Like the early Sanyo VCRs this machine was built to last! There are few common faults that routine maintenance will not cure. A tendency to shed drive belts is sometimes apparent now these machines are a few years old – a set of new belts will cure this. An occasional fault encountered is sudden stopping of the machine during forward, fast forward or rewind: while this can be due to the CX141 syscon chip, or even to the tape-end sensor coils, more often the joints and connections to the end sensors or the associated presets RV701/2 are responsible. Another potentiometer that's prone to intermittency is RV14 on the Y/C panel: this causes spasmodic colour-lock trouble on replay. The luminance and audio signals are mechanically switched between record and replay: the slide switches can be a source of trouble, causing intermittent audio and picture break-up or dropout. Cleaning of these switches is difficult, so replacement is recommended.

SL8080UB: As for the 8000UB, but with cue and review. The picture and sound are disabled in these modes, which serve to avoid the need to disturb the play and stop keys. A simple form of automatic tape search was also incorporated in this machine – a cue signal is recorded at each operation of the record key. In the fast forward or rewind mode, selecting automatic picture search will initiate stop at the first cue signal.

SL3000UB: Piano-key portable with direct drive head drum and an early form of clean assembly edit facility. Gives good results when used with HVC2000P camera. Not a very common machine, at least in my part of the world!

SLC7UB: Fairly large touch-controlled machine with sophisticated electronics. Two-week four-event timer. Full infra-red remote control of all deck functions and broadcast channel selection. Self-seek u.h.f. tuning with twelve preset stations. Picture search (cue and review), triple speed, still, slow motion and frame-by-frame advance – all in colour, but noise bars visible in search mode (in the other trick modes the noise bars are shunted to the top and bottom of the picture by the capstan servo). Automatic tape programme search, as described for the SL8080, Luminance comb filter circuit. Clean assembly edit facility. Autorewind at tape end.

The C7 has a switch-mode power supply to provide the main 12V power lines within the machine – the first application of this principle to a domestic VCR so far as I am aware. In spite of this it's not a light machine.

Considering its sophistication and high component count, the reliability of the C7 is good. I've had a few cases of micro-madness in the syscon circuit. Diagnosis is not easy, and in one or two cases I had to return the machine to Sony for servicing. The one weak spot mechanically is the friction drive system for fast transport (fast forward and rewind). The symptom is that the spools will slow down and maybe even stop in these modes. Cleaning the appropriate friction surfaces and idlers will effect a temporary cure, but the permanent solution is to fit the modified idler kit supplied by Sony. It's not expensive or difficult to fit – for machines up to serial no. 355300 the part no. is A6706-348-A; for serial nos. above 355300 it's X3653-315-0.

SLC5UB: Similar in appearance to the C7 but aimed at the middle sector of the market – its more modest price tag reflects the absence of some of the features incorporated in the C7. Touch button controlled. Remote control by optional wired handset RM75T. One-week one-event timer. Monochrome simple still picture and monochrome visual search (cue/review). Clean assembly edit facility.

Reliability is good, but rewind modification kit remarks above are also applicable to this machine. All C5s will take kit A6706-348-A.

SLC6UB: Sony's first UK front-loading machine. A middle-of-the-market model with pleasing appearance – the front styling is more conventional than Sony's earlier touch-control VCRs described above. One-week one-event timer. Two options for remote control: simple wired RM72 handset offering picture search and pause, or "bolt-on" infra-red receiver kit RM-C6K which passes the same simple commands via an infra-red link. Picture search and simple still frame in colour. Luminance crosstalk comb filter circuit.

The C6 has not been around long enough to establish any nasty habits, but the part no. for the rewind kit is A-6706-391-A. A few cases of failure to eject have been reported – this is caused by failure of switch S7103 on TT-2 panel.

SLF1UB: A small, high-technology portable VCR with low power consumption. There's a wide range of accessories for location work. It's a dual-purpose machine in that the styled-to-match tuner-timer TTF1UB completes the ensemble to make up a full-specification "static" system. Where applicable, the following remarks apply to the combination F1 system. Light-touch controls. LCD tape time elapsed counter. Two-week nine-event timer. Full-function remote control. Clean edit facility. Picture search. Simple still, slow motion, frame-by-frame, double speed, normal and slow-backwards playback modes, all in colour.

Go-to-zero facility.

SLC9UB: Magic! The current top-of-the-range domestic machine. A slim and well styled front loader. Stereo sound and BNR. Full-function remote control. Light touch controls. Two-week nine-event timer. Eleven times normal speed picture search in colour, with only wire-thin mistracking bars. Very good still frame. Colour replay in continuous forward or reverse at double speed, normal speed, one fifth normal or one tenth normal, plus slow motion and frame-by-frame advance. Programmed APS with up to nine cue points. Tape time elapsed counter. Go-to-zero facility. Auto back-space clean editing. Tape remaining indicator. Self-seek u.h.f. tuning with automatic sequential programming of station memory bank. Luminance comb filter. Switch-mode power supply. Seven microcomputers and extensive use of LSI.

The C9 uses a lot of advanced technology, both mechanical and electronic, to achieve the highest specification to date for a domestic VCR – its performance is very good indeed, and every review I have read is full of praise.

Toshiba

V5250B: This is identical to the Sony Model SL8000UB.

V5470B: Piano-key operated with TV-video switch. A little smaller than its Sanyo and Sony contemporaries, and unusual for its vintage and type in having three motors, one for direct drive of the head drum. Several other features not usually associated with piano-key machines are also incorporated. One-week three-event timer. Soft-touch station tuning. Still frame in colour with the noise bars shunted out of the picture. Colour picture search. Trick speed replay in colour, continuously variable from still to double speed. Digital capstan and head servos. "Programme quick select" facility, similar to the automatic tape search system used in the Sony SL8080UB.

The capstan motor can be a weak spot in this machine, the usual symptom being wow or flutter on sound – bad cases will also give rise to lateral picture instability. Before condemning the motor it's worth checking the mechanical alignment of the tape path and the condition of the play idler. Intermittent shutdown during a timed recording can occur: to cure this, change R619 (servo logic panel) to 330k Ω . Intermittent shutdown of the deck functions may be due to IC501 or the stop microswitch – the latter can cause full stop regardless of which keys are pressed! The record/playback switch S101 can cause intermittent noise and picture breakup if it's dirty, maladjusted or worn.

V8600B: Fairly bulky touch-controlled VCR with four video heads. One-week three-event timer. BNR sound system. TV/video switch. Programme quick select feature. Comprehensive wired remote control. Picture search at seven times normal speed. Excellent colour pictures in the still and slow-motion modes due to the four-head system. Double-speed playback. Auto rewind at tape end.

Reliability is good, and stock faults are mainly confined to solenoid trouble and the failure of Q661 (servo/logic panel). The latter fault removes the u.h.f. output on replay.

V9600B: Toshiba's first front loader, with radically restyled presentation. Aimed at the lower-price end of the market. This machine has something of a VHS look about it! Three-day one-event timer. Mechanical mode switching by loading ring, similar to the Sanyo VTC5000. Provision for wired remote pause control (optional extra). Simple still frame, slow motion and picture search, all in colour. Touch-button sequential channel selection.

Who's Cognizant?

Les Lawry-Johns

I used to be, but it seems I no longer am. This makes even the most simple job long and tedious.

For example I spent a lot of time trying to find the cause of horizontal black lines appearing intermittently across the picture of a Bush set fitted with the T20 chassis. At last I gave up and sent the chap off to Geoff for a second opinion. Within an hour Geoff phoned to ask me if I was all there as he'd put it right in minutes. It was the tube base arcing at the focus pin of course. We all know that one - I keep a dozen tube bases in stock for just this reason, and often lend one out to the simple souls who omit to do so. But I didn't recognise the symptoms myself (cries of "retire, retire!").

No Sound

Then look at last Sunday morning. We are around for only an hour or so while we make up (cook says Mr. Lord) the books and clear up the mess left over from the Saturday madness, before we make ourselves presentable to go and collect the sea food and play our Sunday card game. Just as Honeybunch and I were playing an innocent game of truth or dare however this chap came in with a Thorn 1590 portable (Ferguson Model 3816). He said it had no sound or picture.

Without further ado I whipped off the cover shell and checked the l.t. fuse. It was o.k. So I checked the mains input fuse, which was also o.k. Next I plugged in and switched on. The tube lit up and so did the screen. With an aerial connected it produced a good picture.

"Fancy that" said the chap, but I was already on the track of the no sound condition. Check the speaker and headphone socket. Check the voltages in the audio output stage, then in the bias, driver and audio amplifier stages. I injected an audio signal at the base of the audio amplifier transistor. Loud and clear... So I began to think dark thoughts about the preceding chip. Before going further I injected the signal at the centre tag of the volume control. No sound. Turn up the volume control and the sound is loud and clear. "Had to make sure" I explained, "why don't you take it to an expert next time instead of a moron like me?"

The G11

Now everyone knows their G11s. I mean everyone. A lady phoned to say that her Philips CTV had broken down with a white line across the screen and that she couldn't bring it in because it was too heavy. So I arrived with a complete case of G8 and G11 spares. It was a 26in. G11. Now any fool knows that field collapse is due to the TDA2600 i.c., with perhaps the 800mA fuse gone as well, and that the 470 μ F h.t. reservoir capacitor is possibly responsible for the chip and maybe the BU208A failing.

I whipped open the spares box and rummaged around for a TDA2600. Looked here and there until she picked one up and asked "is this what you're looking for?" Oh dear, but I took it from her gratefully. Next unsolder the heatsink and remove the faulty chip. The solder hadn't

been disturbed, so I presumed it was the original one. I was surprised to find one pin folded upon itself: it had obviously made contact, so I fitted the new chip and checked the fuse which was intact. The 470 μ F reservoir capacitor was a red one and had been sparking at the rivet. In went a new one. "This would have caused you trouble later" said I, "so it's better out than in." "Of course" she agreed. As all seemed to be in order I switched on. The raster came up with incomplete field scan and collapsed, tried to build up again and collapsed. I checked the voltages: the 40V supply was smooth, but the voltages around the chip rose and fell together. Tried this and that to no avail. "I'll pop it back to the shop where I can check it more thoroughly" said I.

Off came the frame and I lugged the set out to the car, trying not to huff and blow. Back on the bench I checked the associated components, having fitted another TDA2600 just in case. Everything checked out o.k., though the voltages were all over the place of course. The new chip then went short-circuit and blew the fuse. I checked the voltages with no chip in: all were as expected and steady. Another chip was fitted and the comedy continued. The evening shadows fell, my spirits with them. At last I gave up.

In a dream I saw someone holding a TDA2600 with one leg folded up, and wondered what this foretold. Next morning I paid a visit to my friends Don and Raymondo. I told them how upset I was and why. "It's the holder" said Don. "It's the holder" said Ray. What wise boys they are. Of course it was the quil to dil chip holder. The folded up leg on the old chip had opened up the clip so that a new, unfolded leg couldn't make proper contact. All was well when a new holder and a new chip were fitted.

I rushed the set back to its owner. She saw me puffing up the path with it and opened the front door. There she stood, making it difficult to enter. I tried to get past but the set, and she, got sort of jammed in such a way that I felt embarrassed. "Awfully sorry" I gasped. "Don't worry about me, just push through." If it had been a bloke I'd have told him to . . . off out of the way, but I didn't like to as she was a lady. So I pushed back on her to make way for the set. It was now obvious to me that she was a lady, but I didn't linger long. In went the set, pulling me with it, while she still stood against the door jamb as though nailed there. I think the edge of the frame just ran down her backbone and she was frightened to move in case she broke in half.

So ended another right muck up. Anyone else would have thought about that folded up pin, but all I could do was to dream about it.

A Right Pair

Then look what happened when I went to fix a set that wouldn't tune properly. I got it tuned all right, but when I came to leave she asked me (another lady, who's a friend of ours) how much. Didn't want to charge her at all, but I didn't want to offend her either. So I said a pound. She gave me this, commenting that it was obviously not enough for the call, and went out to the kitchen to get something else for me.

She came back with two large pears and suggested I put them in my box. There wasn't room for a peanut, so I put one in each trouser pocket. I felt a bit uncomfortable whilst driving back, but soldiered on. When I got back and went into the shop both legs were soaking wet and my trousers had changed colour. Ever helpful, Honeybunch

said "couldn't you wait?" "Margaret sent us some pears" I tried to explain, showing her what was left.

Birds

In came this pretty young girl with a radio cassette. So I thought I'd show off a bit and do it whilst she waited. It was used on mains only, so I checked across the plug pins and found that the transformer's primary circuit was intact. Off came the back to check the fuses. Both the mains and the l.t. fuses were intact, so I plugged in to see what we had or didn't have.

There was a.c. from the transformer to the bridge rectifier. There was about 10V d.c. across the reservoir capacitor. A lead went from this point to the mains socket for switching purposes, and there was no output from the switch. "Simple" said I, "got it now." Since battery operation was never used, and indeed there was no sign of a negative lead from the battery compartment, I shorted the switch contacts across, expecting the set to burst into life. It gave a grunt and the 10V reading dropped to zero. "There's probably a short and it's probably blown the fuse" I said, with a sickly smile. The fuse was intact. I removed the screwdriver from the switch contacts and the 10V reappeared across the reservoir. I removed the mains plug and prepared to look for shorts. There were no shorts and the 10V remained across the reservoir. Since the voltage was still present I thought that the bridge had charged the reservoir and that all was well in this department. I again shorted the switch contacts and the 10V fell to zero. "I'll leave it with you then" said the girl, "and call back later. Perhaps you'll have got someone else to see to it in the meantime."

I stared at the set and called it a nasty name, like I call the bird when it goes to bite me. Once again I plugged it in and the 10V appeared at the reservoir. It remained there until I shorted the switch, this time with a permanent soldered connection. There was no voltage at the reservoir capacitor but there was at the output from the bridge rectifier, half a millimetre away. I applied the iron to the seemingly perfect joint and the radio burst into life. How the bridge had charged the reservoir capacitor across a high-resistance gap had once more fooled me.

I mentioned a bird just now. It's taught me the meaning of the term "bird brain" you see. A while ago one of Honeybunch's relatives was posted to Northern Ireland - he's in the army. Anyway, he thought the bird wouldn't be safe, so he gave it to HB who he knew would be crackers about it (true). It's not very old, about six months, so HB says we've got to be patient with it. It's a very handsome cockatiel. HB calls it Crystal and I call in Grumpy, and because of our cat we have to keep him upstairs. So for the best part of the day he's on his own though he gets plenty of attention from six o'clock onwards. HB talks to him continually. "Who's a clever boy then?", "there's a pretty boy" and all that sort of thing. He's yellow and white with orange patches on his cheeks. I add my terms of endearment - "who's a made up ponce then?"

In spite of all this loving attention he remains wary, suspicious and downright spiteful. He pecks through his millet at a great rate then squawks for more. When HB tries to give him more he attempts to bite her. I've told her to put him on iron rations for a week to teach him to be grateful but she'll have none of it.

All right, so he's mentally disturbed. Something nasty must have happened to him when he was younger. Yes. He was hatched.

next month in

TELEVISION

● THE LUXOR SX9 CHASSIS

The main idea behind the new Luxor SX9 is to provide as flexible a chassis as possible. It will drive 20, 22 and 26in. c.r.t.s, features frequency synthesized tuning with 99-channel access and 29-channel storage, offers teletext as an option, has a scart socket fitted as standard, and with the addition of an extra module is suitable for direct satellite reception. Amongst the circuit features are parallel sound and a Motorola single-chip (type TDA3301) decoder with automatic black level control. Some rather interesting techniques are used in the digital side of the set, and we'll be concentrating mainly on these.

● SERVICING THE SONY SLC7UB

The Sony SLC7UB is one of the most complex VCRs to have appeared on the market and can produce some puzzling faults. David Botto provides a guide to various fault conditions, concentrating on the electronic side.

● TEST CARDS FOR CHRISTMAS

The festive spirit takes over with the BBC's captions and test cards at Christmas. Keith Hamer and Garry Smith provide an illustrated account of some of the unusual test patterns seen in recent years.

● SERVICING FEATURES

We've many hints and tips to pass on in the regular VCR Clinic and TV Fault Finding features. S. Simon deals with the Thorn 8000 and 9000 chassis in his Q and A guide.

● AUTO CHANNEL SCANNER

When you've several channels to choose from it's an advantage to be able to monitor them sequentially. For this purpose James Dilworth devised an auto channel scanner system that selects one channel for about ten seconds then changes to the next and so on, each channel being monitored at least once a minute. If an interesting programme is seen, a switch is thrown and the set resorts to normal channel select operation.

PLUS ALL THE REGULAR FEATURES

ORDER YOUR COPY ON THE FORM BELOW:

TO
(Name of Newsagent)

Please reserve/deliver the January issue of TELEVISION (90p), on sale December 14th, and continue every month until further notice.

NAME

ADDRESS

.....
.....

Service Bureau

Requests for advice in dealing with servicing problems must be accompanied by a £1.00 postal order (made out to IPC Magazines Ltd.), the query coupon on page 97 and a stamped addressed envelope. We can deal with only one query at a time. We regret that we cannot supply service sheets nor answer queries over the telephone.

SONY KV1820

The fault is no sound or raster. On initial investigation the chopper transistor and its driver, also the surge limiting resistor R602, were found to be faulty and were replaced. This restored the h.t. supply, but at only 45V instead of 135V. The start-up diode D612 then went open-circuit. The h.t. rose to 135V after this, but kick-starting the line oscillator with an 18V battery reduces it to 45V again.

Since the power supply seems to be able to produce 135V off load, it's likely that the fault is in the line output stage. On occasions we've found that the trouble was due to a defective efficiency diode (D806). The best course would be to supply the set via a variac, measuring the h.t. current as the mains input is increased. With the h.t. at 60V there should be a small picture and the current, monitored at pin 1 of connector CNF3, should be around 200mA. If it's more, check the line output stage by disconnecting items in turn, starting with the tripler and yoke. If the current is much less than 200mA, concentrate on the power supply unit, if necessary disconnecting the over-voltage and excess-current circuits while monitoring the h.t. current as before.

PHILIPS N1501

This VCR produced sharp, steady pictures on my 19 and 12in. Bush monochrome sets until recently. Now there's a flickering effect – on the 19in. screen the whole picture fluctuates sideways by some quarter of an inch, affecting all verticals. The tape path has been checked and cleaned.

There seems to be a variation in either the head or the tape speed. If the fault is present in still frame, check for wear in the head lower bearing and lubricate this. If the movement of the picture is regular, the head servo ripple preset R214 on the servo panel needs adjustment – a scope is required for this. If the fault is not present in still frame, check whether the movement corresponds with the pinch wheel revolutions; if so, replace it. The tape servo ripple preset R252 may need adjustment. Failing this, check that both the head and capstan motors are absolutely free – the bottom bearings tend to become tight.

THORN 8000 CHASSIS

A brilliant white line appears about three quarters of an inch below the top of the screen – it's some 7/8in. deep. Adjusting the height control reduces the brightness of the line and moves it to near the top, where it appears as foldover. The set operates correctly in every other way.

This sort of problem is usually caused by trouble in the top half of the field output stage. Check the 2N6178 output transistor VT401, diode W413 in series with its

base, and the flyback clamp diode W414. If necessary, check the bootstrap capacitor C438 (10 μ F) and the bias diodes W411/2.

KÖRTING HYBRID COLOUR CHASSIS

The problem is lack of width – the picture is only five inches wide. The resistors in the width circuit are all o.k. and the line timebase valves and the electrolytics in this area have been replaced. The line output stage derived voltages are all low, and the PL509's screen grid voltage is only 140V instead of 225V.

The low screen grid voltage suggests that either the feed resistor R424 (2.7k Ω) has gone high in value or the decoupling electrolytic C422 (25 μ F), which is mounted off the board, is leaky. In this case the PL509 will be running cool. If the valve is running hot, the drive waveform could be incorrect. Check C419 (220pF) in the shaping network for open-circuit and the line oscillator's anode circuit resistors R416 (47k Ω) and R417 (8.2k Ω) for changed value.

DECCA 80 CHASSIS

The line shift control VR403 won't move the picture left. Despite the control being at one end of its range, there's a quarter inch gap down the left-hand side of the screen. I've tried replacing the control and the two diodes which produce the shift voltage.

The shift control should provide correction in either direction and despite your problem is probably working correctly. First check the purity, then set up the line hold control VR321. This is done by shorting the test pins adjacent to R306, then adjusting VR321 for vertical bars. Remove the link and the problem should be resolved, with adjustment of VR403 as necessary.

GEC HYBRID COLOUR CHASSIS

The picture is sharp and the geometry good, but there's smearing and streaking across the screen, the effect varying with picture content. Reducing the setting of the contrast control removes the smearing but leaves a green tint over the whole screen. When the contrast control is turned up there are usually two faint, broad blue bands which vary with picture content.

This sort of thing is usually due to clamping problems at the c.r.t. grids, and is aggravated by grid current in a soft, gassy tube. Try three new PCL84 colour-difference output/clamp valves, and check the three 8.2M Ω triode clamp anode load resistors. If there's no improvement, reactivating the tube may well make a big difference. If the tube is past it, the only viable solution is to fit a regunned replacement.

SONY KV2000

I initially found that the chopper transistor Q607 was short-circuit. After replacing this there was a quick rush of e.h.t. and sound (e.h.t. top cap disconnected), then the protection circuit came into operation. Overriding the excess current trip by temporarily shorting out C610 produces an h.t. of 100V instead of 135V – this cannot be controlled by the preset. With no load the power supply trips about once a second. All the semiconductor devices in the power supply and the line output stage appear to be o.k., checked with a meter out of circuit. It's difficult to know whether the power supply is faulty or overloaded.

Check the current flowing on load at pin 1 of power supply connector F3. If it's in excess of 400mA, the line timebase is in trouble. Unload the line output transformer

gradually — start by disconnecting plug E to isolate the e.h.t. transformer. If the current consumption is less than 400mA, concentrate on the power supply. We've known thermistor Th602 and zener diode D605 in the error amplifier circuit, and the chopper transistor's emitter resistor R628 (1Ω, 1W), cause trouble in this department.

THORN 9800 CHASSIS

There's an intermittent fault on this set. At switch on the picture is normal, but after a time that varies between three quarters of an hour to an hour and a half the height reduces to about three inches. Sometimes the fault doesn't appear for two or three days. If the set is left switched on the fault goes after a time that also varies. Switching the set off and allowing it to cool makes no difference.

We've seen the fault on this and other chassis — it's usually due to dry-joints around the pincushion correction transducer. Carefully check the connections to T501 and the phase coil L505.

TEST CASE

252

Each month we provide an interesting case of television servicing to exercise your ingenuity. These are not trick questions but are based on actual practical faults.

There are many traps for the unwary in television servicing, as most of our readers will know! What appears to be something obvious can turn out to be obscure, while conversely sometimes the most difficult looking faults can be caused by something simple. In much modern domestic electronic equipment several diverse faults can produce the same symptom as far as the user is concerned — examples include the “no deck functions” condition with a VCR and the “dead set” condition with a TV set.

As an illustration, we were recently confronted by a Bang and Olufsen set fitted with the 5000 chassis. The symptom was a pumping effect, the power supply switching on and off at about one second intervals. When this sort of thing happens, it's important to observe all the symptoms carefully so that the fault area can be narrowed down as far as possible. The technician dealing with the set noted that once the picture tube had warmed up a contracting raster was visible on each pump cycle, and that a corresponding burst of sound was present each time the h.t. line perked up. This suggested that the receiver and timebase sections of the set were in working order, and that the problem lay in the power supply itself.

It was known that the power supply incorporates over-current and over-voltage protection, designed to pulse the

h.t. supply in the presence of abnormal conditions. If the e.h.t. or l.t. line voltages rise significantly, tripping will occur: a likely cause is excessive h.t. voltage. An AVO 8 was accordingly hooked on to the main 172V h.t. line as a check. The meter needle peaked at just 94V at each pump cycle, so the possibility of excessive h.t. voltage was discounted and other avenues were explored. No abnormal current was flowing through the sensing resistor 6R27, and shorting it out experimentally had no effect on the symptom.

Pursuing the possibility of a protection circuit fault, the technician next warily turned off 6TR6 by linking its base and emitter leadouts, whereupon the pumping action at once stopped. This confirmed that the tripping action was being initiated by this transistor, and now that a stable picture was present it could be seen to be considerably overscanned in both the horizontal and vertical directions. Suddenly everything fell into place in the technician's mind and a diagnosis was made with little more ado. What fundamental error had been committed during the investigation, and what was the true cause of the fault?

ANSWER TO TEST CASE 251 — page 41 last month —

Last month's “confessions from a workshop” described an elusive and spasmodic line whistle coming from within a new Hitachi Model CPT2028, and the heroic attempts to track it down by component substitution. The whistle was still present after replacing the chopper, line drive and line output transformers, leaving us at something of a loss.

The culprit was finally traced by resorting to something very similar to a feather with which, believe it or not, we gently brushed relevant areas of the chassis. Full marks to the feather, for it discovered that the offending whistle was coming from FB701, a ferrite bead on the cathode lead of the 12V rectifier D703. Its factory-applied blob of sealment had missed the target, and the bead was actually vibrating on the diode's leadout wire. A blob of silicone rubber compound silenced it forever!

We were a little wide of the mark last month in saying that this Hitachi set doesn't have a line linearity coil. In fact L704 performs this function. It's a fixed and sealed device however, with no means of adjustment and, so far as we can see, not propensity to whistle.

QUERY COUPON

*Available until 14th December 1983.
One coupon, plus a £1.00 (inc. VAT)
postal order, must accompany EACH
PROBLEM sent in accordance with the
notice on page 96.*

TELEVISION DECEMBER 1983

Published on approximately the 22nd of each month by IPC Magazines Limited, King's Reach Tower, Stamford Street, London SE1 9LS. Filmsetting by Trutape Setting Systems, 220-228 Northdown Road, Margate, Kent. Printed in England by The Riverside Press Ltd., Thanet Way, Whitstable, Kent. Distributed by IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. Sole Agents for Australia and New Zealand — Gordon and Gotch (A/sia) Ltd.; South Africa — Central News Agency Ltd. Subscriptions: Inland £11, overseas (surface mail) £12 per annum, payable to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex RH16 3DH. “Television” is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to currency exchange fluctuations and VAT, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

TV TRADE SALES LTD

		WORKERS			NON-WORKERS		
		£			£		
BUSH	20" & 22" CTVS	20.00	+	VAT	12.00	+	VAT
THORN	8000/8500 17" CTVS	30.00	+	"	15.00	+	"
DECCA	18" - 22" CTVS	30.00	+	"	20.00	+	"
GEC	Hybrid	20.00	+	"	12.00	+	"
GEC	Plastic Cab C2111	25.00	+	"	20.00	+	"
PHILIPS		35.00	+	"	20.00	+	"
THORN	3000/3500	30.00	+	"	20.00	+	"
NORDMENDE	26" CTVS	35.00	+	"	20.00	+	"
MONOS		6.00	+	"	2.00	+	"

DISCOUNT ON BULK ORDERS

COLOUR PANELS FOR ALL LISTED MAKES FROM: £3.50 + VAT

VALVES

TRIPLERS

LINE OUTPUT TRANSFORMERS

TUNERS (PUSH BUTTON)

MAINS DROPPERS

SMALL NUMBER OF REGUNNED TUBES AVAILABLE FROM: £20.00 + VAT

TRADE DAY: WEDNESDAY

TV TRADE SALES LTD

CORNFORD ROAD, MARTON, BLACKPOOL

TEL: 0253 696266

G.G.L. COMPONENTS
108 SCOTLAND ROAD, CARLISLE, CUMBRIA CA3 9EY
PHONE (0228) 20358/39693

ACCESS NOW AVAILABLE



(STOP PRESS)

Hitachi and Sony tubes
now rebuilt.

INTEGRATED CIRCUITS				TRANSISTORS				LINE O/P TR.		NEW VALVES							
TYPE	PRICE (£)	TYPE	PRICE (£)	TYPE	PRICE	TYPE	PRICE	TYPE	PRICE	TYPE	PRICE						
LC7120	4.30	TBA480Q	1.40	TDA2591	2.70	AC127	22	BC184L	11	BF115	30	BU205	1.42	RBM T20/22A	12.20	DY802	72
LC7130	4.50	TBA510	2.30	TDA2593	2.30	AC128	22	BC208	12	BF167	26	BU206	1.35	PHILIPS G8	22.95	PCF802	86
MC1327A	1.00	TBA520Q	1.30	TDA2600	5.30	AC128K	30	BC212L	10	BF184	28	BU208A	1.40	PHILIPS G9	7.90	PCL82	78
MC1358P	1.60	TBA530Q	1.00	TDA2611A	1.50	AC141K	30	BC213L	10	BF185	29	BU208/021.70		PHILIPS G11	8.75	PCL84	81
MC1330P	0.90	TBA540Q	1.27	TDA2640	1.80	AC142K	30	BC214L	10	BF194/394	12	BU326A	1.48	THORN 1590/1	13.50	PCL805	90
ML231B	1.95	TBA550Q	1.40	TDA3560	5.10	AC176	28	BC237B	11	BF195	13	BU407	1.12	THORN 1690/1	8.68	PCL86	81
ML232B	1.70	TBA560Q	1.60	UPC1156H	2.95	AC176K	30	BC300	25	BF196	11	BU500	1.80	THORN 1615	9.68	PFL200	1.35
MR475	2.00	TBA750Q	2.45			AC187K	30	BC303	26	BF197	11	BU526	2.00	THORN TX10	12.50	PL504	1.50
SAS560S	1.83	TBA800	0.80			AC188K	33	BC337	11	BF198	14	BUW81A	3.20	PYE 731/713(110)	10.20	PL508	2.90
SAS570S	1.90	TBA810AS	1.15			AD149	70	BC338	10	BF241	15	MJE340	0.40	PYE 725(90)	10.20	PY88	69
SAS580	2.40	TBA820	1.40			AD162	42	BC547	10	BF256LC	25	MJE3000	1.50	ITT CVC 1-9	9.60	PY500A	1.90
SAS590	2.40	TBA890	2.95	BA102	15	AD162	42	BC548	10	BF258	25	R2008B	1.45	DECCA 2230	8.30	PY81/800	69
SL901B	4.80	TBA920Q	1.50	BA115	14	AF126	38	BC557	10	BF259	28	R2010B	1.45	DECCA 80	8.58		
SL917B	6.95	TBA950/2X	2.65	BA154	07	AF127	36	BC558	10	BF337	28	R2540	2.35	DECCA 100	8.58		
SL1327Q	1.30	TBA990	1.55	BB105B	25	AU110	2.10	BD124P	55	BF338	30	TIP29C	45	GEC 2110	9.45		
SN76003N	2.05	TCA270SQ	1.30	BB105G	25	AU113	2.20	BD131	33	BF355	32	TIP30C	45	ITT CVC 20	7.75		
SN76013N	1.80	TCA800	1.95	BY127	10	BC107B	14	BD132	33	BF362	38	TIP31C	46	ITT CVC 25/30/32	8.00		
SN76023N	1.80	TCA940	1.55	BY133	15	BC108B	14	BD201	80	BF458	30	TIP32C	47				
SN76110N	0.90	TDA1002A	1.50	BY139	15	BC109B	14	BD202	70	BF459	36	TIP33B	80				
SN76226DN	1.45	TDA1003A	2.80	BY164	40	BC139	24	BD203	70	BF490	1.60	TIP41C	48	RBM T20/22A	7.35		
SN76227N	1.00	TDA1004A	2.70	BY179	60	BC140	26	BD204	83	BF472	30	TIP42C	48	RBM A823	7.20		
SN76660N	0.65	TDA1035	3.20	BY210/800	30	BC141	26	BD222	50	BF473	30	TIP2955	70	PHILIPS G8-550	6.90		
SN76666N	0.83	TDA1044	3.10	BY223	86	BC142	23	BD232	50	BFX85	30	TIP3055	55	PHILIPS G9	6.45		
TN7120P	2.05	TDA1170	1.80	BY227M	23	BC143	25	BD233	37	BFY51	22	TV106/02 1.60		THORN 950 MK2	4.35		
TA7130P	2.00	TDA1412	0.90	BYX10	20	BC148	09	BD234	40	BR100	18	2N3054	55	THORN1500-3S	4.25		
TA7193P	4.20	TDA2190	3.20	BYX55/600	26	BC157	10	BD236	43	BR103	55	2N3073	12	THORN1500-5S	4.55		
TA7205AP	2.80	TDA2020	2.95	BYX71/600	78	BC158	11	BD237	40	BT106	1.15	2N5496	50	THORN3000/3500	7.75		
TAA550	0.28	TDA2522	1.80	OA90	07	BC159	11	BD238	39	BT116	1.30	2SC1172Y		THORN8000	4.00		
TBA120AS	0.62	TDA2523	2.25	1N4001-7	07	BC160	22	BD410	50	BT106/2	1.58		1.85	THORN8500/8800	5.90		
TBA120AS	0.70	TDA2530	2.10	1N5401-8	12	BC172	10	BD434	50	BT119	2.30	2SC2029	2.00	THORN9000	8.40		
TBA120SB	0.90	TDA2540	1.95	Y969	85	BC177	22	BD437	70	BT120	2.30	2SC2078	2.00	PYE 731	6.55		
TBA120U	1.00	TDA2560	1.80	BZX61-range	18	BC182	10	BD438	78	BU105/021.44	25C2091	1.10		DECCA 2230	6.30		
TBA395	1.25	TDA2581	1.70	BZY88-range	11	BC182LB	11	BD707	1.05	BU126	1.78	2SC2078	2.20	DECCA 80	6.30		
TBA396	0.85	TDA2590	2.25			BC183LB	11	BDX32	1.65	BU204	1.50	2SC1969	2.45	DECCA 100	6.76		
														GEC 2001H	6.95		
														ITT CVC 20/30	6.85		
														Universal	5.90		

WE WILL ONLY SUPPLY TOP QUALITY, BRANDED COMPONENTS. REPUTATION COUNTS WITH US

REBUILT TUBES

Full range of tubes available. Range includes Deltas, PCL, 20AX/30AX inc. Hitachi and Sony tubes also. Prices and delivery on application.

Quantity discounts available on request.

TV ELECTROLYTICS

DECCA 30(400/400)350V	2.55
DECCA 80/100(400)350V	2.90
PHILIPS G8(600)300V	2.00
PHILIPS G9(220)63V	1.15
PHILIPS G11(470)250V	2.20
PYE 691/7(200-300)350V	2.10
RBM A823(2500/2500)30V	1.10
THORN1400(150/100/100/100/150)320V	2.40
THORN3500(175/100/100/400)350V	2.25
THORN3500(1000)70V	0.85
THORN9000(400)400V	2.75

PUSH BUTTONS/TUNERS


DECCA/ITT 4W	6.45
DECCA/ITT 6W	7.40
PYE201 6W	15.80
PHILIPS G8S/L	13.90
PHILIPS G8S/O	12.00
HITACHI 4W	8.50
ITT CVCS 7W	9.40
ITT CVCS/9	12.80
PHILIPS G11 (TIP SW.)	23.80
1043/05TFK	8.20
U321 TFK	7.95
U322 TFK	7.40

* ADDITIONS TO RANGE *

TYPE PRICE (£)	TYPE PRICE (£)
AN240 3.00	LA4422 2.75
AN7140 2.40	LC7137 4.80
AN7150 3.30	TA7222 2.10
HA1322 2.10	TA7227 4.50
HA1366 2.30	UPC575 1.80
HA1339 2.80	UPC1025H 3.20
HA1377 3.80	UPC1181 2.30
HA1388 4.20	UPC1182 2.20
LA4102 2.70	UPC1185 3.50
LA4400 2.80	UPC2002 2.90

THIS IS ONLY A VERY SMALL PART OF OUR RANGE. WE WILL BE DELIGHTED TO SEND DETAILS OF OUR WHOLE RANGE

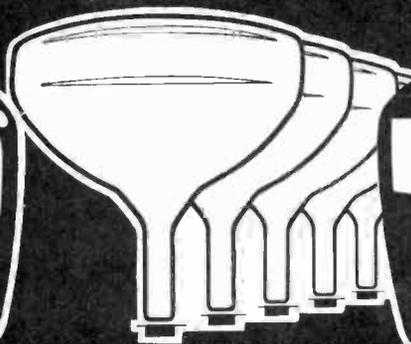ORDERING
Please Add 50p For P/P U.K. Add 15% VAT To This Total.
Export Orders - Cost.
DELIVERY BY RETURN ON ALL STOCK ITEMS.



QUALITY REBUILT CRTs

ALL

**SONY
CRTs**

Southern England
DOUBLE D. DISTRIBUTORS
27 Florence Rd., Parkstone, Poole, Dorset.
Tel. (0202) 742347



ALL

**HITACHI
CRTs**

Midlands and North Wales
FAIRHURST SUPPLIES
Tel. 061-480 8247
Answering service outside normal hours

London and Home Counties
ALPHA TUBES
53 Lowther Rd, Dunstable, Beds.
Tel. 0582-68934

S. Wales and S. W. England
ASTEN MEAD (Electronics Ltd)
Component Distributors, Dorset.
Tel. (0258) 72823, Telex 46246

Northern England
GEORGE LAWSON ELECTRONICS
108 Scotland Rd, Carlisle, Cumbria.
Tel. (0228) 20358/39693

Scotland
SOUTER WHOLESALERS
Colour Tube Specialists.
Tel. Selkirk 20255

A SELECTION OF CRT's REBUILT BY TSR:-

All Monitor CRT's, All Sony CRT's, including projection systems S.D. 102 R/G/B - 510ABZB22, 510ACAB22, etc.

HITACHI QPF	MATSUSHITA	370DLB22	510HWB22	560ZB22
510SWB22	470ESB22	370FHB22	510JEB22	670XB22
510VLB22	470FGB22	370GYB22	510JGB22	A37-544x
510VSB22	470GMB22	370HVB22	510JKB22	A37-565x
560CSB22	510GJB22	370ZB22	510LDB22	A42-556x
560DZB22	510GLB22	420DKB22	510MXB22	A42-570x
560EGB22 etc.	510HSB22	420ERB22	510RJB22	A51-580x
	560BCB22 etc.	420GFB22	510UFB22	A51-590x
		470CTB22	560AKB22	A56-540x
		470ELB22	560ATB22	A66-540x
MITSUBISHI QPF		470ERB22	560AWB22	A56-611
510TSB22		470ESB22	560DTB22	A56-612
510TVB22	OTHER IN-LINES	470ETB22	560DYB22	A56-613 etc.
510TWB22	320ARB22	470FTB22	560ETB22	AXT37-001
560DEB22	370AUB22	490DVB22	560EUB22	AXT51-001
560DRB22	370BDB22	510CJB22	560HB22	AXT56-001
560DSB22 etc.	370BRB22			

N.B. We can deal with all your CRT requirements from Delta's to Sony's.

If your CRT is not above, please contact us and our Gun Department will make a gun for your CRT. Our many customers, including some of the National Rental Groups, have proved our quality.



T.S.R. VACUONICS LTD.,
Tom Stewart Lane,
St. Andrews, Fife,
Scotland.
Tel: (0334) 74035

Information on all other CRTs available on request

MANTEL

Manchester's No. 1 in Ex-Rental TVs
Over 2,000 TVs in stock
Special Offer on Working Colour TV's

★ All sets are Serviced with repolished cabinets ready for sale

★ Philips G8 550s 22/26 £45
 ★ Philips 18" £40
 ★ Philips G8 520s 22/26 £35
 ★ GEC S/State from £35
 ★ Thorn 17" 8000 £30
 ★ Decca 30 18/20/22/26 £30
 ★ Japanese from £30
 ★ Many other makes available from £25

Discount on quantity

Ex Equipment Panels & Tubes Available

Deliveries may be arranged to the North and Scotland.

Ring for quote. Callers welcome.

Some Examples of UNTESTED TVs available

Thorn 10 for £125
 Philips 6 for £90
 Bush 6 for £80
 GEC 6 for £60
 Decca 6 for £60
 Mono TVs avail. s/s £4 each
 New TV trolley stands.
 All sizes £4.95
 All Prices subject to V.A.T.

419 Barlowmoor Road, Chorlton, Manchester 21 2ER.
Tel: 061 861 8501

MICRO-TOUCH PROGRAMME SELECTOR


REPLACEMENT FOR 7 PIANO-KEY TYPE: DECCA, TELEFUNKEN etc.

- DIRECT REPLACEMENT
- CUSTOM MOULDING FOR PROFESSIONAL FINISH
- 7 BUTTONS ALIGN WITH EXISTING LEGEND
- L.E.D CHANNEL INDICATORS
- USED BY MAJOR MANUFACTURER

VERMILLION ELECTRONICS LTD.

UNIT 14, HALESFIELD 18.
 TELFORD. TF7 4QT
 SHROPSHIRE.
 TEL. (0952) 506771

PRICE: £16:00 POST FREE U.K +15% V.A.T

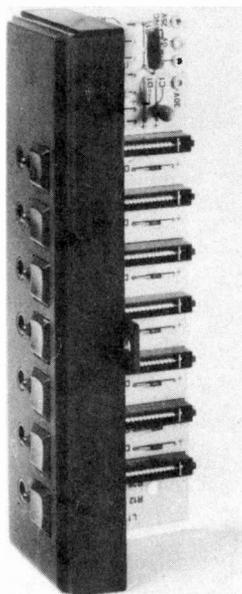

TELETRADERS

Forde Road, Brunel Industrial Estate,
 Newton Abbot, Devon
 Telephone: (0626) 60154

The Best Quality Sets Available
 Anywhere

3500 Electronic 22" £30
 Bush Electronic £15
 GEC & Pye Hybrid £5
 Grundig Solid State £30
 Decca Bradford £10
 ITT CVC 5,8,9 £25

Also Philips G9, G11, ITT CVC 35, 45, 50,
 Thorn 9000, 9600, 9800, Bush T20.

All sets complete with excellent cabinets
 Full spares back-up of tubes and panels –
 send for list
 Bulk terms to other wholesalers



THE NO. 1 WHOLESALER IN THE SOUTH

COLOUR TELEVISION & MUSIC CENTRE

**35 Stafford Road, Weston Super Mare,
Avon**

(NOTE NEW ADDRESS) (15 MINS PAST BRISTOL SOUTHWARD ON M5)

SOLID STATE COLOUR TELEVISIONS

**ALL SETS IN PERFECT
RUNNING ORDER**

HITACHI 213s 217s 20 INCH

REMOTE CONTROL, LIKE NEW (VHF - UHF)

NATIONAL PANASONICS

WITH MAGIC LINE, VERY CLEAN

PYE CHELSEA

18", 6 Button, Sliding Controls,

Brilliant Condition. Good sellers as computer monitors

£39.50

THE ABOVE ARE WORKS MODIFIED FOR MOST
PARTS OF THE WORLD VHF - UHF

PYE 721 & 731 THORN 8800

22"-26", could be mistaken for new **All £49.00 each**

PYE 725

20" unmarked cabinet

£59 each

Also Thorn 9000, 9200, 9400, 9600 Remote Control 20" - 22"

Minimum 5 sets

Prices subject to V.A.T.

BIG REDUCTIONS FOR EXPORT ORDERS OVER 100 SETS

WE HAVE!! WHAT WE SAY WE HAVE

SO **RING NOW: Weston Super Mare 413537**

OPENING HOURS 9 - 6 MONDAY TO SATURDAY, 9 - 1 SUNDAYS

N. J. ELECTRONICS

UNITS 82/83/84 STORFORTH LANE TDG. EST., HASLAND, CHESTERFIELD, DERBYSHIRE S41 0SN
Tel. CHESTERFIELD 209079

PUSH BUTTONS

DECCA 30 4 way	680p
DECCA 30/80/100 6 way	780p
THORN 3500/8500	275p
THORN 8800/9000	275p
GEC 2110 series	1100p
GEC 2112 series	1295p
GEC 2136/7 series	850p
2112 Conversion	1300p
HITACHI 190 4 way	895p
CVC 5 series 7 way	1000p
CVC 8/9 replacement	1285p
CVC 20/30/32 6 way	780p
CVC 25 6 way	850p
PHILIPS G8 520	1100p
G8 550	1355p
G11 tip switch	2250p
PYE 713 4 way	875p
PYE 715 6 way	1350p
PYE 725 UHF/VHF	1350p
RR1 A823 4 way	875p
RR1 A823 6 way	950p
RR1 T20A 6 way	1050p
RR1 Z718 6 way	950p
TELPRO 561 4 way	850p
THORN 1615 b/w 4 way	870p

LINE OUTPUT TRANSFORMERS

AUTOVOX 90°	975p	PHILIPS G8	890p
AUTOVOX 110°	975p	PHILIPS G9	850p
DECCA 1700 mono	980p	PHILIPS G11	1295p
DECCA 1830/1730	980p	PHILIPS K30	1495p
DECCA 2230/2630	830p	KT 3	795p
DECCA 80	770p	PHILIPS 570	950p
DECCA 100	790p	PHILIPS 210 mono	990p
GEC 2110	950p	PYE 725	895p
GEC diode split	1200p	PYE 731	895p
GRUNDIG 1500 mono	1370p	RR1 A640/793	1175p
GRUNDIG 6011/5010	1150p	RR1 Z774 comp.	1290p
ITT CVC 5/8	1025p	RR1 T20	1290p
ITT CVC 20	1075p	THORN 1590/1	1050p
ITT CVC 30/32	875p	THORN 1615	1000p
ITT CVC 40	1300p	THORN 1690/1	875p
ITT CVC 45	975p	THORN 1500 20"	700p
INDESIT mono	1075p	THORN 1500 24"	700p
KORTING 90°	1075p	THORN 9600	1000p
KORTING 110°	1250p	THORN 9800	2300p
SABA	1250p	SKANTIC colour	1250p

EHT TRAYS

DECCA 1830	590p	DECCA 100	625p
DECCA 2230	625p	THORN 9000	780p
DECCA 80	625p	SIEMENS Universal	550p

INTEGRATED CIRCUITS


TA 7072P	290p	TDA 2611A	115p	UPC 1188H	360p
TA 7108P	244p	TDA 2640	180p	UPC 1190C	200p
TA 7117P	320p	TDA 2653	210p	UPC 1191V	170p
TA 7129AP	320p	TDA 2680	210p	UPC 1197C	170p
TA 7130P	138p	TDA 2690	220p	UPC 1198H	141p
TA 7139P	275p	TDA 3560	510p	UPC 1200V	197p
TA 7157P	320p	TDA 3561	650p	UPC 1204C	163p
TA 7171P	330p	TDA 3950	240p	UPC 1208C	200p
TA 7172P	330p	TDA 4600	210p	UPC 1211C	400p
TA 7176AP	300p	TDA 9400	280p	UPC 1212C	134p
TA 7193P	520p	UA 783P3C	90p	UPC 1215V	270p
TA 7202P	330p	UPC 41C	350p	UPC 1216V	199p
TA 7203P	330p	UPC 554C	134p	UPC 1217G	359p
TA 7204P	216p	UPC 555H	80p	UPC 1218H	300p
TA 7205P	140p	UPC 566H3	350p	UPC 1222	200p
TA 7208P	270p	UPC 574J	55p	UPC 1223	370p
TA 7210P	560p	UPC 575C2	149p	UPC 1225	300p
TA 7222P	170p	UPC 577H	350p	UPC 1226	249p
TA 7223P	350p	UPC 585C	149p	UPC 1227	200p
TA 7227P	510p	UPC 1009H	241p	UPC 1228H	90p
TA 7310P	170p	UPC 1017G	250p	UPC 1230H	360p
TA 7313P	280p	UPC 1018C	119p	UPC 1238V	190p
TA 7609P	400p	UPC 1024H	63p	UPC 1245	220p
TA 7611AP	290p	UPC 1025H	370p	UPC 1250	240p
TA 75902P	203p	UPC 1026C	160p	UPC 1350C	450p
TDA 1003	200p	UPC 1028H	240p	UPC 1353C	280p
TDA 1004A	200p	UPC 1031HZ	240p	UPC 1356CZ	300p
TDA 1044	150p	UPC 1032H	98p	UPC 1358H	300p
TDA 1170	280p	UPC 1035C	250p	UPC 1363C	350p
TDA 1180	210p	UPC 1037	162p	UPC 1365C	500p
TDA 1190	200p	UPC 1042C	280p	UPC 1366C	300p
TDA 1327	170p	UPC 1043C	260p	UPC 1367C	300p
TDA 1412	100p	UPC 1156H	240p	UPC 1368H	400p
TDA 2020	190p	UPC 1158H	78p	UPC 1370CZ	400p
TDA 2010	180p	UPC 1161C3	158p	UPC 1373H	111p
TDA 2522	240p	UPC 1163H	98p	UPC 1377C	450p
TDA 2523	220p	UPC 1168C	275p	UPC 1378H	400p
TDA 2530	220p	UPC 1170C	175p	UPC 1382C	197p
TDA 2532	270p	UPC 1171C	162p	UPC 1384C	570p
TDA 2540	220p	UPC 1176C	242p	UPC 1447H	98p
TDA 1365	575p	UPC 1177H	260p	UPC 2002V	280p
TDA 2541	230p	UPC 1178C	214p	THIS IS ONLY A FRACTION OF OUR STOCK. PLEASE SEND 50p FOR OUR NEW CATALOGUE WHICH WILL BE REFUNDED ON ORDERS OVER £5.	
TDA 2580	205p	UPC 1180C	300p		
TDA 2571A	210p	UPC 1182H	270p		
TDA 2581	130p	UPC 1183H	230p		
TDA 2582	180p	UPC 1185H	350p		
TDA 2583	270p	UPC 1186H	98p		
TOA 2800	500p	UPC 1187V	170p		

Add 65 pence Postage + 15% VAT to all orders.
All goods despatched by post same day as order received. All goods should be delivered within 4 working days.

UNIVERSAL PROGRAMME SELECTOR FOR VARICAP TUNING

UK Regd. Design No. 1006611

6 way interlocked d.p. switch 100 K tuning potentiometers
Top quality through hole plated pcb
Dimensions: 5" by 2½" by 1"
Ideal for replacement when original parts are obsolete or unobtainable
Template guide supplied for drilling of your own fascia design
Range of pre-cut and drilled fascia/mounting kits for selected TV chassis enabling our unit to be fitted without further cutting drilling or modification
All orders despatched same day

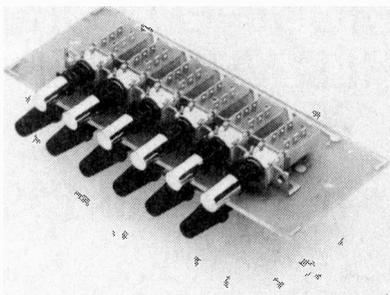

DIRECT REPLACEMENT FASCIA/MOUNTING KITS

- Type 30-80 Replaces 7 piano-key unit as fitted to Decca/Telefunken 30 and 80 chassis
- Type 30-C Replaces 7 piano-key unit as fitted to Decca console using long perspex illuminated control panel
- Type 100 Replaces 8 position touch tune selector (AEG SAS 660 SAS 670) as used in Decca/Telefunken 100 chassis
- Type CVC8-9 Replaces 5 rectangular push button plus thumbwheel as used in ITT

SELECTOR **£11** + VAT

FASCIA/MOUNTING KITS (each) **£2** + VAT

All orders despatched on day of receipt.

ALDERSON-JAMES LTD

160 KINGS ROAD ● HARROGATE ● N. YORKS
TEL: HARROGATE (0423) 60058 HG1 5JG

VIDEO HEADS

MONOLITH
electronic products

HIGH QUALITY UNIVERSAL VIDEO HEAD REPLACEMENTS FOR ALL VHS AND BETAMAX VCR MACHINES

- VHS Part No. 3HSS (5mm Centre Hole) **£29.95** PRICE
- VHS Part No. 4HSS (15mm Centre Hole) **£29.95** EACH
- BETAMAX Part No. PS3B **£38.95** EX.
- REPLACEMENT KIT (14 Pieces Boxed) **£ 8.25** V.A.T.
- PLEASE ADD 15% V.A.T. PLUS P. & P. £1.50 PER ORDER
- OUR FULL CATALOGUE AVAILABLE ON REQUEST.
- Please allow between 14 and 28 days for delivery.

AUDIO + VIDEO HEADS - MOTORS - PARTS
Suppliers to most U.K. Distributor/Service Organizations

THE MONOLITH ELECTRONICS CO. LTD

5-7 Church Street, Crewkerne, Somerset TA18 7HR, England
Telephone Crewkerne (0450) 74321 Telex 46306 MONLTH G

"NORTH LONDON WHOLESALE'S"

TV SALES

COLOUR TELEVISIONS
Most makes and sizes available,
WORKING OR UNTESTED.

Re-gunned tubes available. 5 mins. M.1.
Evening appointments possible.

Please telephone us for details on:—

WATFORD 45590

AA117 0.090	BC157 0.055	BD222 0.310	BU108 1.000	OC72 0.500	TIP29C 0.250	3N128 0.550	2SA473 0.370	28 pin 0.200	PCL82 0.630	LM723 0.320	LED 5mm
AA119 0.090	BC159 0.055	BD225 0.310	BU110 1.100	OC200 1.800	TIP30 0.160	3N143 0.650	2SB54 0.250	40 pin 0.250	PCL84 0.500	LM741 0.150	YELLOW 0.100
AA132 0.050	BC182 0.060	BD232 0.310	BU111 1.400	OC207 1.000	TIP31A 0.240		2SB77 0.320		PCL85 0.550	LM741	LED 5mm
AC107 0.280	BC182L 0.060	BD237 0.210	BU126 0.700	ORP12 1.000	TIP32 0.240	IN.914 0.020	2SB337 1.200	VALVES	PCL86 0.550	Met	0.450
AC126 0.170	BC183 0.060	BD238 0.240	BU204 0.750	ORP60 1.000	TIP32A 0.240	IN.400 0.040	2SB405 0.220	DY87 0.530	PCL805 0.550	LM3900 0.250	BRIDGE
AC127 0.150	BC183L 0.060	BD433 0.280	BU205 0.750	ORP61 1.000	TIP33 0.500	IN.4002 0.040	2SC460 0.210	DY802 0.450	PLP200 0.850	NE555 0.150	RECTIFIERS
AC128 0.150	BC184 0.060	BD437 0.280	BU208 0.750	R2008B 0.800	TIP34 0.500	IN.4003 0.040	2SC495 0.600	ECC82 0.400	PL36 0.800	NE556 0.400	1A/50V 0.160
AC128K 0.230	BC184L 0.060	BD535 0.380	BU208A 1.200	R2010B 0.800	TIP41A 0.220	IN.4004 0.040	2SC495 0.600	ECC83 0.430	PL504 0.950	NE556 0.400	1A/100V 0.180
AC141K 0.230	BC212 0.060	BD536 0.380	BU208D 0.800		TIP41C 0.250	IN.4005 0.040	2SC733 0.400	ECC84 0.400	PL508 1.900	350	0.300
AC142K 0.230	BC212L 0.060	BD537 0.400	BU326 0.850	SAS560 1.100	TIP42A 0.220	IN.4006 0.040	2SC733 0.400	ECC85 0.400	PY81 0.700	BYX55/	1A/200V 0.190
AC153K 0.230	BC213 0.060	BD538 0.400	BU406 0.850	SAS570 1.100	TIP42C 0.250	IN.4007 0.050	2SC1161 1.100	ECC86 0.400	PY88 0.480	600	0.300
AC176 0.180	BC213L 0.060	BDX32 1.000	BU407 0.750	SN76003N1.400	TIP47 0.400	IN.4148 0.020	2SC1279 0.240	ECH81 0.490	PY500A 1.600	BYX55/	1A/400V 0.210
AC176K 0.200	BC214 0.060	BDX65 0.800	BU408 1.000	SN76013N1.400	TIP48 0.400	IN.5400 0.090	2SC1306 1.000	ECH84 0.520		600	0.300
AC187 0.150	BC214L 0.060	BF180 0.160	BU500 1.100	SN76023N1.400	TIP49 0.400	IN.5401 0.100	2SC1307 1.000	ECH84 0.520		600	0.300
AC187K 0.200	BC237 0.070	BF181 0.180	BU526 0.800	SN76033N1.500	TIP110 0.470	IN.5402 0.110	2SC1520 0.250	ECL82 0.590		600	0.300
AC188 0.170	BC238 0.070	BF183 0.200	BU526 0.800	SN76110N0.700	TIP112 0.540	IN.5403 0.110	2SC1969 1.300	ECL84 0.570		600	0.300
AC188K 0.230	BC300 0.180	BF184 0.200	BU527 0.800	SN76115 0.700	TIP115 0.540	IN.5404 0.120	2SC2029 1.200	ECL85 0.570		600	0.300
AC188 0.170	BC300 0.180	BF185 0.200	BU527 0.800	SN76226 0.900	TIP117 0.560	IN.5405 0.130	2SC2078 1.200	ECL86 0.490		600	0.300
AC188K 0.230	BC302 0.180	BF194 0.050	BU527 0.800	SN76227 0.800	TIP122 0.460	IN.5407 0.130	2SC2122A 2.000	EFL80 0.310		600	0.300
AC188 0.170	BC302 0.180	BF195 0.050	BU527 0.800	T2800D 0.520	TIP125 0.470	IN.5408 0.130	2SC2952 0.270	EFL85 0.340		600	0.300
AC188K 0.230	BC303 0.180	BF196 0.050	BU527 0.800	TAG06-60 0.420	TIP126 0.560	VOLTAGE REGULATORS	2SD2952 0.270	EFL89 0.340		600	0.300
AC188 0.170	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7805 0.350	2SK135 4.000	EFL89 0.340		600	0.300
AC188K 0.230	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7812 0.350	2SK135 4.000	EFL89 0.340		600	0.300
AC188 0.170	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7815 0.350	2SK135 4.000	EFL89 0.340		600	0.300
AC188K 0.230	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7818 0.350	2SK135 4.000	EFL89 0.340		600	0.300
AC188 0.170	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7824 0.350	2SK135 4.000	EFL89 0.340		600	0.300
AC188K 0.230	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7905 0.350	2SK135 4.000	EFL89 0.340		600	0.300
AC188 0.170	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7912 0.400	2SK135 4.000	EFL89 0.340		600	0.300
AC188K 0.230	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7918 0.400	2SK135 4.000	EFL89 0.340		600	0.300
AC188 0.170	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7924 0.400	2SK135 4.000	EFL89 0.340		600	0.300
AC188K 0.230	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7924 0.400	2SK135 4.000	EFL89 0.340		600	0.300
AC188 0.170	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7924 0.400	2SK135 4.000	EFL89 0.340		600	0.300
AC188K 0.230	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7924 0.400	2SK135 4.000	EFL89 0.340		600	0.300
AC188 0.170	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7924 0.400	2SK135 4.000	EFL89 0.340		600	0.300
AC188K 0.230	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7924 0.400	2SK135 4.000	EFL89 0.340		600	0.300
AC188 0.170	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7924 0.400	2SK135 4.000	EFL89 0.340		600	0.300
AC188K 0.230	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7924 0.400	2SK135 4.000	EFL89 0.340		600	0.300
AC188 0.170	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7924 0.400	2SK135 4.000	EFL89 0.340		600	0.300
AC188K 0.230	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7924 0.400	2SK135 4.000	EFL89 0.340		600	0.300
AC188 0.170	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7924 0.400	2SK135 4.000	EFL89 0.340		600	0.300
AC188K 0.230	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7924 0.400	2SK135 4.000	EFL89 0.340		600	0.300
AC188 0.170	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7924 0.400	2SK135 4.000	EFL89 0.340		600	0.300
AC188K 0.230	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7924 0.400	2SK135 4.000	EFL89 0.340		600	0.300
AC188 0.170	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7924 0.400	2SK135 4.000	EFL89 0.340		600	0.300
AC188K 0.230	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7924 0.400	2SK135 4.000	EFL89 0.340		600	0.300
AC188 0.170	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7924 0.400	2SK135 4.000	EFL89 0.340		600	0.300
AC188K 0.230	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7924 0.400	2SK135 4.000	EFL89 0.340		600	0.300
AC188 0.170	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7924 0.400	2SK135 4.000	EFL89 0.340		600	0.300
AC188K 0.230	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7924 0.400	2SK135 4.000	EFL89 0.340		600	0.300
AC188 0.170	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7924 0.400	2SK135 4.000	EFL89 0.340		600	0.300
AC188K 0.230	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7924 0.400	2SK135 4.000	EFL89 0.340		600	0.300
AC188 0.170	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7924 0.400	2SK135 4.000	EFL89 0.340		600	0.300
AC188K 0.230	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7924 0.400	2SK135 4.000	EFL89 0.340		600	0.300
AC188 0.170	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7924 0.400	2SK135 4.000	EFL89 0.340		600	0.300
AC188K 0.230	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7924 0.400	2SK135 4.000	EFL89 0.340		600	0.300
AC188 0.170	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7924 0.400	2SK135 4.000	EFL89 0.340		600	0.300
AC188K 0.230	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7924 0.400	2SK135 4.000	EFL89 0.340		600	0.300
AC188 0.170	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7924 0.400	2SK135 4.000	EFL89 0.340		600	0.300
AC188K 0.230	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7924 0.400	2SK135 4.000	EFL89 0.340		600	0.300
AC188 0.170	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7924 0.400	2SK135 4.000	EFL89 0.340		600	0.300
AC188K 0.230	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7924 0.400	2SK135 4.000	EFL89 0.340		600	0.300
AC188 0.170	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7924 0.400	2SK135 4.000	EFL89 0.340		600	0.300
AC188K 0.230	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7924 0.400	2SK135 4.000	EFL89 0.340		600	0.300
AC188 0.170	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7924 0.400	2SK135 4.000	EFL89 0.340		600	0.300
AC188K 0.230	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7924 0.400	2SK135 4.000	EFL89 0.340		600	0.300
AC188 0.170	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7924 0.400	2SK135 4.000	EFL89 0.340		600	0.300
AC188K 0.230	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7924 0.400	2SK135 4.000	EFL89 0.340		600	0.300
AC188 0.170	BC303 0.180	BF196 0.050	BU527 0.800	TAG521-200 0.720	TIP127 0.560	7924 0.400					

HUSSAIN CENTRAL TV

Best quality sets available in the Midlands

Clearance sale to all traders

G11, Teletext, ITT, CVC40 Remote control,
TX10, Panasonic, Sony, Hitachi, Tandberg.
All latest stock plus 5000 ex-rental T.V.'s.

Available at very low, low prices

Ring **021-622 1023** or **021-622 1517**
48 Pershore St., City Centre, Birmingham 5.

**ELECTRONICS
ENTHUSIASTS...
LOOK NO FURTHER!**

For regular, comprehensive designs for easy-to-build projects for both leisure and business use, EE is the one to watch out for. This month...

ENVIRONMENTAL DATA RECORDER

Stores data for subsequent readout via computer VDU. Portable and weatherproof, the unit is of particular value for field work. PLUS—ideas for Christmas.

CLUCKING EGG TIMER · CHILDRENS' DISCO LIGHTS · MAGIC CANDLE

PLUS...the latest instalment of the popular series **Microcomputer Interfacing Techniques and Teach-In '84.**

All in the December issue...

EVERYDAY
ELECTRONICS
and computer PROJECTS

NOW ON SALE 90p

PRECISION VISION LTD.

67 LONDON ROAD, HEADINGTON, OXFORD

SPECIAL OFFER THIS MONTH:-

- ☆ Large quantity of 18" Decca PIL Tube 80 Series, all in good working order.
- ☆ Limited quantity of Toshiba Colour Portables.
- ☆ Used VHS, Beta, 2000 System Videos in excellent working order.
- ☆ Good selection of modern colour TV's.

**PLEASE PHONE FOR CURRENT STOCK POSITION
(0865) Oxford 750212**

20AX APOLLO 30AX

HIGH TEMPERATURE PUMPED COLOUR TUBES

*Fast Mail Order service to any part G.B. Delivery 2-3 days.
Just phone for a quotation. Delivery Manchester area free same day.
Two year guarantee. Fitting while you wait or in your home £20.*

18"	A47 - 342 x343	470 BEB22 (£45.00)	£37.00
19"	A49 - 120 x/192 x		£37.00
20"	A51 - 220 x/110 x/161 - 510JKB22	(£45.00)	£38.00
22"	A56 - 120 x/123 x/140 x/410		£38.00
25"	A63 - 120 x		£39.00
26 x	A66 - 120 xA67 - 120 x/140 x/150/200		£39.00
20AX	56-510		£48.00
30AX	56/66-540		£48.50

20" - 22" SOLID STATE COLOUR TVs FULLY SERVICED & SOAK TESTED. VERY RELIABLE WITH GOOD TUBE £61.00, WITH NEW TUBE £83.00 inc DELIVERY

061 799 0854 24 hour answering service.

**43 Clarke Cres, Little Hulton,
Nr. Manchester M28 6XM.**

SETS & COMPONENTS

★ TELEBEST ★

We specialise in working sets.

BUSH · DECCA · G.E.C.
GRUNDIG · PYE · PHILIPS
THORN Etc.

From £25 plus VAT.

Non workers available
Mono £2.00 plus VAT

Call Ronnie on:

01-514 1333

for stock availability

841 Romford Road,

Manor Park, London E12.

TELEVISION

Trade & Retail supplies of
s/h colour & mono TVs.
Most makes available,
workers or non-workers

SOUTHPARK DISTRIBUTORS

Unit 4 Rubastic Road,
Brentpark Industrial Estate,
Southall, Middx. UB2 5LL.
01-574 4631, Ext 28

AT LAST A REGUNNER IN THE SOUTH

WETSTED TUBES

- * ALL DELTA CRT's £30.00 + VAT
- * ALL P.I.L. CRT's £45.00 + VAT
- * MOST SIZES FROM STOCK
- * 1 YEAR GUARANTEE, OPTIONAL 4 YEAR
- * FREE DELIVERY WITH 5 CRT's OR OVER OTHERWISE ADD £3.00 PER ORDER WITHIN 20 MILE RADIUS OF MAIDSTONE.

PHONE NOW

EAST PECKHAM 872400

REBUILT COLOUR TUBES DELTA TYPES

Example Prices

All sizes up to 22" — £28.00
All sizes up to 26" — £32.00

All In Line P.I.L. Mono
Gaming Machine C.R.T.s

Fast U.K. Delivery

Call or Phone:

RE-LIFE T.V. TUBES

PLANE STREET,
OLDHAM, LANCS.
061-665 2668

Big reductions on Contract Orders
Home or Overseas.
Wholesalers Required
in certain parts of the U.K.

TELEVISION

No other consumer magazine in the country can reach so effectively those readers who are wholly engaged in the television and affiliated electronic industries. They have a need to know of your products and services.

The prepaid rate for semi display setting £6.00 per single column centimetre (minimum 2.5 cms). Classified advertisements 35p per word

COLOUR TV PANELS Fully Tested & Working

	IF	CDA	Decoder	LTB	Line Board	Frame Board	Power
GEC 2040	3.50	3.50	4.00	5.00	—	—	—
DECCA 13/30	3.00	—	5.00	5.00	—	—	4.00
BUSH 'A'	2.00	—	5.00	5.00	2.50	—	2.00
THORN 8-8½"	—	—	10.00	5	—	—	5.00
PYE 205	3.00	3.50	5.00	8.00	—	2.00	—
THORN 3+3½K	3.00	—	5.00	8.00	—	—	10.00
G8	6.00	—	8.00	5.00	15.00	—	5.00
BUSH twin chip decoder	10.00	—	—	—	—	—	—

Post & packing: 1 panel £1.50; 2 panels £2.25; 3 panels £3.00 etc.
Hybrid panels do not include valves.

Terms cash with order.

26" CRT's fully tested £10

fitted with
brand new
transformer

LAVITE LTD.,

Golcar C of E School, Church St., Golcar, Huddersfield. Tel.: 0484-643273
Callers by appointment only.

RANK BUSH MURPHY TV PANELS

Repair, exchange, sales service, prompt efficient service. All chassis covered. New PCB available to replace burnt T20 line Panel. We charge only £16 to repair switch mode power supply. Ring Monday to Saturday and ask for Mr. Kheili.

T. K. Panels Service,

31 Bronte Paths, Stevenage, SG2 0PG.
Tel. (0438) 61567.

SCRATCHED TELEVISION TUBES, Don't despair, send for repair, 20 years experience. Phone 0507 85300.

CAMPBELL ELECTRONICS LTD. COLOUR T.V. PANEL EXCHANGE/ REPAIR SERVICE

THORN, RANK, PHILIPS, GEC,
DECCA, TELPRO, GRUNDIG etc.

90 Day Guarantee on all repairs — same day postal service.

Telephone Telford (0952) 502422
for catalogue and price list.

CAMPBELL ELECTRONICS LTD.,

Unit 5, Heath Hill Estate,
Dawley, Telford, Shropshire.

TEST EQUIPMENT

- UHF T.V. Pattern Generators
- Crosshatch & 4 patterns £17.25
- As above but with Greyscale £18.50

Prices include P&P and VAT.

Also available:

- PAL COLOUR BAR GENERATOR
- CAPACITANCE METER
- TRANSISTOR TESTER

S.A.E. for prices and full details.
The above items are not kits.

C.M.J. ELECTRONICS

Unit 8, 16 Union Mill, St., Horseley Fields,
Wolverhampton, WV1 3DW. Tel. (0902) 871563.

REYSTRONICS: SCHRADER Tunable UHF Amplifier RB45 A.S. MV30DB gain. 1-6dB noise. Ch. 17-65. £39.50, p&p £1.50. Telephone 01-979 7380.

TRADE COLOUR TV'S ALWAYS 200 IN STOCK

Phillips G8 from £10
Bush Twin Chip from £8
Pye Chelsea from £15

Colour TV's in good working order from £35.

E.G. Phillips G8's 22" £35.

Avo repairs prompt service scopes etc.
Ring us for spares and type availability
anytime.

(0934) 514047/512792/27560

P&R SUPPLIES, Unit 5,

Worle Industrial Estate,
Weston-Super-Mare. Exit 21 M5.

COLOUR TV'S FROM £15.50 + VAT

GUARANTEE COMPLETE GOOD CABINETS
SPARES AVAILABLE

PYE CT205/CT200. BUSH A823 TH3500/8500 Phil G8.
DECCA. BRAD. ITT. CVC5. JAP. GRUNDIG

SMITHS ELECTRONICS

43 PARK PARADE
LONDON NW10

01-965 1230
01-961 3997

When replying to Television Classified Advertisements please ensure:

- (A) That you have clearly stated your requirements.
- (B) That you have enclosed the right remittance.
- (C) That your name and address is written in block capitals, and
- (D) That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

SERVICE PAGES

(minimum 12 words), box number 70p extra. All cheques, postal orders etc., to be made payable to Television, and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Dept., Television Room 2612, IPC Magazines Limited, Kings Reach Tower, Stamford Street, London SE1 9LS. (Telephone 01-261 5846).

GRUNDIG Panel exchange. Working sets. Circuits. Wanted - remote control units. Ochre Mill 0785 814643 anytime.

BARRY TV SERVICES (EAST ANGLIA)

Your friendly wholesalers. We cater for the smaller dealer who requires regular small supplies of quality used colour TV's. From £25 + VAT. Fully working with good tubes and cabinets, straight from our retail shelves, ready to sell or rent.

Delivery available

Contact John, Dave or Steve on
Ely 61462
or Cambridge 69215

NOW OPEN IN NEWCASTLE

FOR THE BEST IN ELECTRONIC COMPONENTS
TEST EQUIPMENT AND ACCESSORIES

Marlborough Electronic Components
15 Waterloo Street, Newcastle NE1 4DE
Tel: 618377

Open 9am-6pm Mon-Sat. Easy Parking
STOCKISTS OF TRANSISTORS, RESISTORS,
CAPACITORS, I.C., DIODES, ELECTRONIC BOOKS ETC.
CENTRAL STATION



RANK BUSH MURPHY TRANSFORMERS

LINE OUTPUT TRANSFORMERS

Z718 (T703A, T706A)

(1) New (Complete) £20.50

(3) Less Focus Module and Rectifier £10.50

Z718 SPARES (T703A, T706A)

Pri. - £5.50, Sec. - £6.00,

Rectifier - £3.00, Lead - £2.50

T20, T22 (T705A)

£9.00

T26 (T705B)

£9.50

Switch-mode Transformers

T114 A/B £8.00

Genuine RBM Units

Prompt Postal Service.

Add 15% V.A.T. to all Prices.

DISCOUNT For QUANTITIES

**WOODSDALE COMPONENTS
MR SKEHAN**

34 Field End Road, Eastcote,
Pinner, Middlesex HA5 2QT.
01-868 5580

Agents Office, callers by appointment only.

JAPANESE COLOUR TV's, Hitachi, Sony, Panasonic, Mitsubishi, Toshiba, Sharp. COLOURLAND TV. Trade Only. 0484 863489.

TURN YOUR SURPLUS capacitors, transistors etc., into cash. Contact COLES-HARDING & CO., 103 South Brink, Wisbech, Cambs. 0945 584188. Immediate settlement.

TELEVISION

Trade Supplies of Good Quality Colour & Mono TV's. Most Makes available, suitable for Sale or Re-Rent.

**GENERAL
FACTORS**

UNION STREET,
DONCASTER
(0302) 49583-68416

GOOD MOTORWAY ACCESS

TUBES £29
INCLUSIVE

**REGUNS
TWO YEAR GUARANTEE**

A56-120 A51-110
A49-191 A47-342 or 3
A44-270 A67-120

A66-120 or 140 (26" add £5)

Add £5 per tube for quick insured delivery. No need to spend £5 returning old glass if you buy from us (except in-line).

U-VIEW TUBES

29, WARMSWORTH ROAD, DONCASTER
YORKS. DN4 0RP. TEL 0302 855017.

Callers ring first. Open every day, including Sunday. These prices apply to 1983.

INLINE TUBES

51 161
56 500
PLUS MANY
MORE SONY
HITACHI ETC.

£49

U-VIEW
INCLUSIVE
AND
DELIVERY

TUBES £19.50

Inclusive and delivered. Slightly used with a six month guarantee. Sizes available as above U-VIEW (TUBES) 26" add £5.

N.W. ELECTRONICS

Sale of the Year!

Open 6 days
Mon-Sat until 5.30

2,000 Colour T.v.'s to Choose from

BUSH 1 CHIP £10 BUSH 2 CHIP £15

(Excellent Cab condition. Change over sets - high percentage workers)

GEC 2010 PLASTIC AND WOOD CAB..... £25

PHILIPS G8 £15

PYE 223 £35

BUSH 718 TIL TUBE..... £35

BUSH T22 P.O.A. (dependent on quantity required)

Other makes in stock include G11, HITACHI, SANYO ETC.

White Goods

FRIDGES, FRIDGE/FREEZERS, HOOVER TWINS, HOTPOINT TWINS,
AUTOS etc.

SPECIAL OFFER - We need the room

100 HOOVERMATICS MIXED 3174, 3334, 3301L


£500 - DELIVERY ARRANGED.

LARGE QUANTITY FRIDGES, FRIDGE/FREEZERS FROM **£10**

HOOVER AUTO'S FROM **£14**

Don't forget we are open all day Saturday 9-5.30

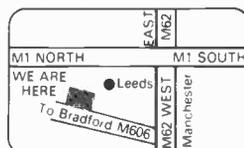CASH ONLY - WORKING TV'S FROM **£29** - ASK FOR DETAILS.



**UNIT 1, WHARFEDALE ROAD,
M606, EUROWAY ESTATE,
BRADFORD. [0274] 688458**

OPEN MON - SAT 9 - 5.30

**T.V. SPARES, PANELS
AND MANUALS
PHILIPS · GRUNDIG**

**TELEVIEW 01-994 5537
194, Acton Lane, London W.4.**

EX EQUIPMENT PANELS. Thorn 3500. Complete untested. Power and time base £4.00. Others £2.00. Power and time base tested working £8.00. Postage £1.75. Eastwood, T.V. Shop, 65 Burnley Road, Todmorden, Lancs. 070681 7197.

**! YOU HAVE TRIED THE REST
NOW TRY THE BEST !**

**Quality 6 Button TVs
on Offer**

Ultra 6725 22"	GEC S/S
Furg. 3738 22" T/T	ITT CK505
Furg. 3749 22"	Philips 550 22"
Furg. 3722 22"	Bush T20

Also 17" 8000 various models + many more to choose from.

SCARBOROUGH TV TRADERS CO LTD
85 Columbus Ravine, Scarborough,
N. Yorks. 0723 68087.
1 hour from A64/A1 junction

SATELLITE TV RECEIVER

Receives 3.65-4.2GHz band. Ideal for demonstration terminal in UK. 100 degree KELVIN LNA. £385 + Carriage.

SAE DATA, TVDX lists,

H. Cocks,
Cripps Corner, Robertsbridge,
Sussex. Tel: 058083 317.

**TELEVISION TUNER
REPAIRS
ALL TYPES**

**BRITISH, EUROPEAN
JAPANESE ETC.**

MEN-TU ELECTRONICS LTD.
SALTERNS LANE,
FAREHAM, HANTS.
Tel: 0329-235116

COLOUR TV's FROM £10

**IN
NORTH HERTS.**

- ★ Weekly Stock
- ★ Working Sets to Order
- ★ Bulk Discounts Available
- ★ Mountains of Spares
- ★ Friendly Service
- ★ Phone Call Preferred

SCREENPLAY
REAR OF 28 SUN STREET,
HITCHIN,
HERTS.

Phone: Hitchin 31644

TELEVISION

IRISH T.V. DEALERS

(No. 1 for s/hand T.V.s)

We are your number one source for good quality reconditioned colour televisions, most with re-gunned tubes. (We now have our own re-gunning plant.)

700 sets to choose from all with VHF/UHF tuners. Most leading makes supplied. Fresh stocks weekly.

Prices from off the pile £50.

Working sets from £73.

Sets with re-gunned CRTs from £99.

Prices subject to V.A.T. Re-gunned CRTs guaranteed for one year.

We also stock Philips Videos, Televverters, Mono TVs, VHF Aerials and of course our own re-gunned tubes.

**Phone for delivery or visit our new spacious warehouse:*

**TELE SPARES LTD. Unit 113, Elm Road,
Western Ind. Estate, Dublin 12.
Tel: 01 521211/521756.**

**WIZARD DISTRIBUTORS
MANCHESTER**

SPECIALIST DISTRIBUTORS TO THE TRADE
OF T.V. & VIDEO SPARES.

WE STOCK A FULL RANGE OF PARTS &
COMPONENTS INCLUDING C.R.T.'s

RANK - THORN - PHILIPS - ITT -
DECCA - GEC ETC.

THANDER & LEADER STOCKIST

TRADE COUNTER OPEN: 9-4.30

CATALOGUE ON REQUEST.

Mail Order Enquiries Welcomed

EMPRESS STREET WORKS,

EMPRESS STREET,

MANCHESTER M16 9EN.

TEL: 061-848 0060.

**NORTHERN IRELAND
DEALERS**

Thorn 3500/8000, Philips 550, Decca
100/80/302

Most other makes available

Prices: Non-workers from £20

Guaranteed workers from £40

Mono sets from £3

*Delivery anywhere in N. Ireland for
bulk orders*

S. M. Electronics

Tel: Cookstown (NI) 06487/64277

Thorn 3000/3500
Thorn 9000
UNIVERSAL
1 year guarantee

**TRIPLERS
£4.50 inc.**

The UNIVERSAL TRIPLER can be used in most
G.E.C., I.T.T., Pye, Rank, Decca & Continental
sets.

WING ELECTRONICS

15 Waylands, off Tudor Rd, Hayes End, Middlesex



- * Britains most reliable source of quality TVs.
- * Hundreds of working polished TVs.
- * New adjustable TV stands.
- * Pye 18" Chelsea's working & polished £35.00 in quantity.

Krystal Marketing Ltd,
8 Breedon Cross Storage,
Date Road, Selly Oak,
Birmingham B29 6AQ.

Phone 021-471 3023
Telex 335540-G
Ask for Les

GRUNDIG MILLIVOLTMETERS 100UV/300 V.
Working order £15 + £5 P&P. Also P.S.Vs isolating
transformers etc. S.A.E. Lists. S.H.E., 5 St Joseph's
Park, Ballycruttell, Downpatrick BT30 7EN.

SECOND HAND Colour TV spares and tubes. Most
makes. Telephone Southport (0704) 74411. Anytime.

JABCO LOPT TESTER

This instrument is now used in hundreds of
Service Workshops and Manufacturers with
household names all round the world. Saving
countless hours in checking Line O.P. stages
and the unnecessary fitting of new LOPTS.
Mains operated. Straight forward indication of
good or bad by Red & Green Leds. No controls
to set up.

Instruction booklet on testing many common
Lopts in situ including jelypots.

£16.50 inclusive. C.W.O. delivery 3 days. £18
overseas post by sea. £21 airmail.

J. BAKER & CO.

1, Old Shoreham Rd., Southwick,
Sussex BN4 4RD.
Tel: Brighton 593315.

TORBAY (TRADE) T.V.

For Good Quality Used Colour & Mono
T.V.'s, Popular Makes, Quantity Discounts,
Trade Workers from £22.50 + VAT.
(Non Workers available)

**6, CASTLE CHAMBERS
HIGHER UNION STREET,
TORQUAY, DEVON
Tel: (0803) 22767.**

GLOBETEL

Tel: 807 6992

Les & Phil - Ex. S.T.S. Colindale
Rear of Globestone Ltd.,
1-7 CHURCH ST., EDMONTON.

We have now opened our own
warehouse for used T.V.'s at
very fair prices.

All popular makes in stock, eg:
Philips, Pye, Grundig,
Jap. sets, etc.

Look forward to seeing both old
and new cust.

We also stock & buy used videos
- VHS only.

SERVICE PAGES

SUFFOLK T.V. TUBES

PLEASE NOTE THAT AS FROM 1ST OCTOBER 1983 OUR PURLEY WAY FACTORY WILL BE CLOSED. WE WILL BE PLEASED TO SUPPLY CUSTOMERS OLD AND NEW FROM OUR PREMISES AT:

**1 PARK ROAD,
HACKBRIDGE, SURREY SM6 7ER.
Tel: 669 7825/7826**

Suppliers of Mono and Colour Tubes to major rental companies. All colour tubes hot pumped at 385°C and rebanded to British Standard 415 1972 Clause 18-2. 19" and 22" Tubes approved. Other types pending.

**BRITAINS LARGEST INDEPENDENT MANUFACTURER.
REBUILDERS SINCE 1958.**

TV VALVES

COLOUR VALVES PY500/A-65p, PL509/519-£1.50.
MONO VALVES ECC82, EF85, EF183, EF184, DY87,
DY802, PCF80, PCF802, PCL82, PCL83, PCL84, PCL85/
805, PCL86, PCC84, PCC89, PC92, PC97, PC86, PC88,
PFL200, PL36, PL504, PY800, PY88 ETC.
MONOCHROME VALVES ALL 35p EACH.
ALL VALVES EX-EQUIPMENT & TESTED.
P&P 50p Per order, Access/Visa Cards welcome.
ELECTRONIC MAILORDER LTD, 62 Bridge St.,
Ramsbottom, Lancs, BL0 9AG. Tel. (070682) 3036.

CAPITAL REGUN TUBES

19 Goulton Road,
London E5

Your North East London
C.R.T. Dealer

- Very competitive prices
- Extended Guarantees
- Discount to Callers
- Delta and In-Line Supplied
- Suppliers to Large Rental Outlets

Phone ANGUS COLGAN
on 01-986 0702.

PERSONAL

SERVICE ENGINEER available for contract work in Berkshire. Own (w/shop) equipment spares VCR Audio TV. Telephone 0628 26520.

AERIALS

AERIAL BOOSTERS

Next to the set fitting
845H/G-UHF TV, gain about 20dbs, Tunable over the complete UHF TV band. Price £8.70.
BII-VHF/FM RADIO, gain about 14dbs, when on the off position connects the aerial direct to the radio. Price £7.70.
All boosters we make work off a PP3/006p/6F22 type battery or 8V-18V DC. P&P 30p per order.
ELECTRONIC MAIL ORDER LTD, 62 Bridge St, Ramsbottom, Lancs BL0 9AG. Tel (070682) 3036
Access/Visa Cards Welcome SAE Leaflets

2 METRE PARABOLIC DISHES

Glassfibre Construction.
Suitable for 4 And 12 GHz £290
Polar Mounts And Feed Supports Available.
Send S.A.E. for Details
SP ANTENNA SYSTEMS,
3 Woolpack Corner, Biddenden,
Ashford, Kent TN27 8BU
Tel: 0580 291090

AERIALS AND ACCESSORIES

North Londons Specialist Aerial Supplier
Wholesale and Mail Order.
VHF/UHF antennas, masts, brackets, cable, amplification and distribution equipment etc. All types of aerial hardware and software supplied. Single and multipoint systems planned and installed.
Send 50p for our new 1983 catalogue and price list.
S.C.S. AERIALS
(Aerial Distributors)
26-28 Port Vale, Hertford, Herts. SG14 3AB.
Tel: 0992 50478.

BOOKS AND PUBLICATIONS

"RADIO AND TELEVISION SERVICING" books, new editions for the last 6 years always in stock. Prices on request. BELLS TELEVISION SERVICES, 190 Kings Road, Harrogate, N. Yorkshire. Tel. 0423 55885.

COMPLETE FULL-SIZE SETS any published service sheets £2 + LSAE except CTVs/Music Centres from £3 + LSAE. Manuals from 1930 to latest. Quotations, free 50p magazine, price lists, unique technical publications for sale. Repair data/circs almost any named TV/VCR £8.50 by return. TIST, 76 Church Street, Larkhall, Lanarks ML9 1HE. Phone (0698 883334).

SITS VACANT

ELECTRONIC ENGINEERS

Honeywell need dynamic, experienced Electronic Engineers to join their highly skilled team responsible for troubleshooting high-technology video-graphic systems. Our benefits package is most attractive, including company car and 5 weeks holiday. For further details contact:

**Richard Gould,
Honeywell Control Systems Ltd,
Honeywell House,
Charles Square,
Bracknell, Berks RG12 1EB.
PLEASE QUOTE REF. T/79/H.**

SERVICE SHEETS

SANDHURST PUBLICATIONS

Television Service Sheet Specialists
Workshop Manuals, large selection of Japanese and European TV Sheets. Callers 5.30-7.00 pm. Upper Floor. Send S.A.E. for Catalogue and Enquiries:
49C Yorktown Road,
Sandhurst, Camberley, Surrey GU17 7AG.

BELL'S TELEVISION SERVICES for service sheets on Radio, TV, etc. £1.50 plus S.A.E. Service manuals on colour TV and Video Recorders, prices on request. S.A.E. with enquiries to B.T.S., 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 55885.

TECHNICAL INFO SERVICES

76 Church St - Larkhall - Lanarks

Giant TV & VCR DIAGRAM MANUALS

Brit CTVs	3 vols	£45
Vol. 1 Decca G.E.C. ITT		£17
Vol. 2 Philips Pye Redif.		£17
Vol. 3 Rank Bush Thorn		£17
Foreign CTVs	2 vols	£32
Mono (Stand + Port)	2 vols	£32
Early VCR (VHS/Philips)		£17
VCR later models + Betamax		£17

New T.V. Rep. Manuals £6.90 each
1983 Brit. CTV or Foreign CTV 4
Complete set of 15 for £95

Comprehensive practical T.V. Repair course in manual £8.50

Large SAE brings FREE 50p magazine inc. service sheet/details of unique T.V. publications. Any quotation plus price lists, etc.

Full size service sheets £2 + I.s.a.e.
CTVs/Mus. C. £3 + I.s.a.e.

Worlds largest collection of service manuals 1930 to date. From £4.50 to £35 each.
e.g. Autovox/G8/A823 £7.50 each

**FOR FAST QUOTES
RING 0698 883334**

Order form

Please insert the enclosed advertisement in the next available issue of Television

Heading

Signature

Date

No. of irs..... Chq/PO

Classified Advertisement
Department,
Room 2612,
King's Reach Tower,
Stamford Street,
SE1 9LS.

12/83

NAME AND ADDRESS

30,000 SERVICE SHEETS IN STOCK. COLOUR MANUALS ALSO AVAILABLE

TV Monos, Radios, £3.00. Tuners £3.00. Tape Recorders, Record Players £3.00. Transistors £3.00. Car Radios £3.00 + SAE. Stereograms & Music Centres £3.00. Radiograms £3.00. Also Colour available. State if circuit will do if sheets are not in stock. Circuits £3 - colour. All TV Sheets are full length 24 x 12 not in Bits and Pieces. All other Data full lengths. All Sheets £3 except colour. SAE please. Old Valve Radios £3 + SAE 9 x 3.

C. CARANNA, 71 BEAUFORT PARK, LONDON NW11 6BX. (MAIL ORDER)

WANTED

MITSUBISHI 470CNB22 C.R.T. required. MILNE, 20 Graham Road, Wimbledon SW19. Collect locally.

WANTED. We will clear any amount of colour sets from small Rental Companies, Hotels, etc. Please phone P & R Domestic Electrical Clearance Supplies, Weston Super Mare (0934) 514047.

WANTED. INSTRUCTION MANUAL for Sharp VC 6300 VCR. Purchase or loan. 01-890 0727.

WANTED FOR CASH any videos, TV's, televistas, test equipment or tube plants. Ring SCOTT on 01-299 1234.

WANTED URGENTLY. Video recorders, R/C CTV's, portables. Cash available. Ewan, 0892-45938.

COURSES

CONQUER THE CHIP... Master modern electronics the PRACTICAL way by SEEING and DOING in your own home. Write for your free colour brochure now to British National Radio & Electronics School, Dept. C4, Reading, Berks RG1 1BR.

TO RENT

TV SERVICE DEPARTMENTS with bench and outside aerial; also suitable for TV storage. £25.00 per week. No premium. Price includes rates and electricity. Located in centre of London. Telephone now TELEMANN 01-739 3123/2707.

PROPERTY FOR SALE

T.V. SALES & SERVICES, Brighton. Showroom, workshop, office and living accommodation above. Outside forecourt and display area. Stock, fixtures and fittings negotiable. Rent £1,000 p.a. Price for long lease £14,000. Tel. Brighton (0273) 692743 or 737944 anytime.

MISCELLANEOUS

WHITE GOODS WHOLESALE. Hotpoint AVTO's, Hoovers, Fridges, Twin Tubs. Phone 0542 4700 for prices. Hurry stock limited.

SATELLITE D.I.Y. KITS

See live TV from other countries from outer space.

Write for details and prices.

Full instructions on installation.

Example price: 2 meter DIY dish £189.

Secam Sets/LNA/Down Convertors etc.

ANNIS & SON

42 Oxford Street, Whitstable, Kent.

BURGLAR ALARM EQUIPMENT. Latest discount catalogue out now. Phone C.W.A.S. ALARM 0274 682674.

FOR SALE

SONY VP2030 tri standard video player, V-matic. Sony CVM 2030 monitor (100 volt). Original cost £1,900, offers. Phone Steyning, Sussex 814021 after 6pm.

500 OLD RADIO/TV CCT'S for sale. Offers. Tel. 0803 525613. Mostly 50's & 60's.

T.V. PANELS

SPECIAL CLEARANCE

T.V. PANELS

Makes	Power Supply	Line Panel	T/Base Panel	Decoder	Video	Tripler	IF	Convergence
Thorn 3500	£8.00	£8.00	£5.00	£4.00	£5.00	£3.00	£2.00	£5.00
Thorn 8500	£5.00	-	£5.00	£11.00	-	£3.00	-	£4.00
Philips G8	£10.00	£12.00	£5.00	£8.00	-	£3.00	£8.00	£5.00
GEC 515	£8.00	£12.00	£5.00	£8.00	-	£3.00	£10.00 with sound panel	£5.00
Bush	£6.00	£9.00	£6.00	£11.00	-	£3.00	£5.00	£4.00

COMPLETE NON-WORKING PANELS AT HALF PRICE OR LESS FOR QUANTITY

★ Parts also available for other makes. ★ All panels are fully tested and working. ★ Add 15% VAT on all above prices. ★ Postage and packing: 1 panel £1.50; 2 panels £2.00; 3 panels; £2.50 etc.

TOP QUALITY TELEVISIONS

★ Wide range of CTV's in good working order from £25. Mono £2.50. ★ Eg. Thorn 3500; 8500; Philips G8; Bush etc. ★ Plenty of working/non working (complete) sets at competitive prices. ★ Ready to sell or to rent. ★ Please refer back to June & July issue of Television magazine.

M S ELECTRONICS, Unit 1, Warwick Street, Earlsdon, Coventry. Tel: (0203) 714213, or
M S VISION, 72 Robertson Street, Glasgow. Tel: (041) 221-2146

CALLERS WELCOME

For a good selection of used TV sets in good cabinets...

* Large stock of working sets. * U.K. Delivery Service.



UNIT 40, HARTLEBURY TRADING ESTATE, NR. KIDDERMINSTER, WORCS. DY10 4JB Tel. Hartlebury (0299) 250161

SELLING OR BUYING

A classified advertisement could solve your problem at very little cost

RING MANDI

01-261 5846

1983 PRICE LIST

DISPLAY ELECTRONICS

GOLD LABEL COLOUR TUBES

2 YEAR GUARANTEE

90° up to 19".....£33
90° up to 22".....£36
90° up to 26".....£39

The above prices are for standard 38mm Delta Gun Types.

Add £5 Gun surcharge for 20AX Types. Other in-line & P.I.L. Types, prices on application.

GOLD LABEL MONO TUBES

2 YEAR GUARANTEE

19"/20".....£12
23"/24".....£14

GREEN LABEL COLOUR TUBES

12 MONTHS GUARANTEE

90° up to 19".....£28
90° up to 22".....£31
90° up to 26".....£34

Green Label Prices apply only to standard 38mm Delta Gun Types. They will be of particular interest to customers refurbishing ex-rental sets.

BUDGET CORNER

Buy any 5 mixed types take 20% discount.

Buy any 3 mixed types take 10% discount.

Budget prices apply only to colour tubes. The mix can include Gold & Green Label Types if required.

CALLERS WELCOME

Late night Thursdays until 8 p.m.
Saturdays until Midday

N.B. Customers intending to collect orders are requested to telephone in advance:- even popular types may be out of stock for short periods.

UNIT 1
SWAN WHARF
WATERLOO ROAD
UXBRIDGE
MIDDLESEX

Telephone: UXBRIDGE 55800

VISIONTEL

**BEST QUALITY EX-RENTAL
SETS FROM £10 HERE IN
CENTRAL LONDON!**

**100's OF SETS
ALWAYS IN STOCK –
COMPETITIVE PRICES**

VIDEO RECORDERS

(SUBJECT TO AVAILABILITY)

We also have PYE – DECCA –
GEC – ITT – GRUNDIG – JVC –
PHILIPS G9 – THORN 9000 and
MANY – MANY – MORE!

**FOR CURRENT STOCK DETAILS
TELEPHONE 01 328 3787
OR VISIT US AT
55 KILBURN HIGH ROAD NW6**

TELEVISION TUBE SHOP LTD

BRAND NEW TUBES AT CUT PRICES

A31-19W/20W	19.95	230DB4CT468.....	31.00
A31-120W/300W	17.95	240DB4/240AB4A	22.00
A31-410/510W	17.95	CT507 equiv	21.95
A34-100W/510W	18.50	310DGB4/DMB4.....	23.00
A34-514W	24.25	310EUB4	19.95
A38-160W/170W	17.50	310EUB4A	18.50
A44-120W/R	25.00	310EYB4	18.75
A50-120W/R	19.00	310FXB4	17.50
A61-120W/R	21.00	310GNB4A.....	31.00
9AGP4	£21.82	310HCB4	31.00
190AB4/C4	23.00	340AB4	22.50
		340AYB4	30.00
		340AXB4	30.00
		340RB4/CB4.....	26.00
		340AHB4	26.00
		RIGONDA 6".....	14.00

**Some Rebuilt Japanese
& European Types
Available from
£14.00 +VAT £2.10**

COLOUR TUBES

(NEW & MULLARD/THORN COLOREX)*

12VARP22	£62.50	A56-120X	£54.00
330AB22	73.50	A56-410X	64.00
A44-271X	60.00	A56-500X/510X	63.00
A47-342X	61.00	A63-120X	63.00
A47-343X	61.00	A66-120X	65.00
A49-191X	53.00	A66-140X/410X	70.50
A51-161X	70.00	A66-500X/510X	65.00
A51-220X	55.00	A67-120X	65.00
A51-500X/510X	64.50	A67-140X/200X	69.50
A51-570X	73.00	A67-150X	75.00

Old Bulb Required for 110° Colorex
ADD 15% VAT TO ALL THE ABOVE PRICES.

Please allow 7 days for delivery

ALL TUBES TESTED BEFORE SALE & FULLY GUARANTEED
TELEVISION TUBE SHOP LTD
52 BATTERSEA BRIDGE RD., LONDON, SW11.
Tel. 228 6859/223 5088 CARRIAGE: Mono £3, Colour £10.

**EMCO – EUROSONIC – GRUNDIG – TELETON + ALL BRITISH MAKES
ETC., ETC. ● ALL SPARES READILY AVAILABLE ●**

IMMEDIATE CREDIT AVAILABLE – TRADE ONLY

If you are a trader simply phone for the part you require and we will send it – no quibble – no hold up for status check. Satisfy us over the phone that you are a trader and we will supply almost any TV component by return "off the shelf". e.g. LOPTX – EHT trays – droppers – OSC coils – switches – cans – smoothers – I.C.'s, etc. etc.

**YOU CAN BE 95% SURE WE CAN SUPPLY ANY
TV COMPONENT BY RETURN
IF YOU NEED SPARES FAST – RING NOW!**

ACCESS AND BARCLAYCARD ACCEPTED.

Applies to U.K. only.

TELEPART (W'TON)

THE TELECENTRE, WORCESTER ST.,
WOLVERHAMPTON (0902) 773122

COLOUR TV SETS

Philips G8, Pye 222, Decca 30 series, ITT,
Pye Chelsea, Thorn 3500/8000, GEC,
many others including JAP.

Working hybrids from £15.
Working solid state from £25.
Non-working sets from £5.
Working panels and tubes available.

REBUILT TUBES

Delta – In Line – PIL.
SOUTHBRIDGE TV CENTRE
120, Selhurst Rd., London, S.E.25.
Tel: 01-771 3535.

A.B.C. TRADE SALES

COLOUR T.V.'s

Philips G8, Pye, Decca 30's,
Thorn's 3000's, 3500's, 8000's
Prices start from £12 - Working sets from £20
Hundreds of Mono T.V.'s from £2.00
Jap. sets from £30.00

Special prices for quantity
9,000 sq. feet Warehouse
**83 SHOWELL ROAD, BUSHBURY,
WOLVERHAMPTON, STAFFS.**
Tel. Wolverhampton 722637

DIODES			Voltage Regulators		
OA 47	8p	BZX 83c20	10p	MJ 2253	60p
OA 90	8p	BZX 83c27	10p	MJ 3040	60p
OA 91	8p	BZX 83c33	10p	MV 2209	25p
IN 60	5p	BZX 84c6v8x10	30p	SP 8385	25p
IN 541	5p	BZY 88c0v7	10p		
IN 914	3p	BZY 88c3v9	10p		
IN 2069a	10p	BZY 88c4v3	10p		
IN 2070	10p	BZY 88 6v2	10p		
IN 4001	3p	BZY 88c12	10p		
IN 4002	3p	CV 8617	10p		
IN 4004	4p	Y 716	10p		
IN 4005	4p	Y 730	10p		
IN 4006	4p	Y 827	30p		
IN 4007	5p	Y 860	30p		
IN 4148	3p	Y 933	5p		
IN 4448	3p	Y 969	5p		
IN 4742	10p	Y 997	30p		
IN 4722	10p				
IN 4751	10p				
IN 5235	10p				
IN 5254	10p				
IN 5392	10p				
IN 5393	10p				
IN 5928B	10p				
IAY 30	10p				
IM 72Z55	10p				
IR 106a	20p				
IR 3051	10p				
IS 164	10p				
IS 921	10p				
IS 3011a	10p				
IS 3072a	10p				
IS 5024a	50p				
IS 5030	50p				
ITT 921	10p				
ITT 923	10p				
ITT 1075	10p				
ITT 2001	10p				
ITT 2002	10p				
ITT 4150	10p				
ZE 1.5	10p				
ZF 3.0	10p				
ZF 3.3	10p				
ZF 10	10p				
ZF 11	10p				
ZF 12	10p				
ZF 15	10p				
ZF 33	10p				
ZF 43	10p				
ZF 47	10p				
ZF 82	10p				
ZPD 3.9	10p				
ZPD 4.7	10p				
ZPD 5.6	10p				
ZPD 10	10p				
ZPD 47	10p				
ZPY 8v2	10p				
ZPY 12	10p				
ZPY 16	10p				
ZPY 24	10p				
ZPY 43	10p				
ZPY 47	10p				
ZPY 56	10p				
ZTE 2	10p				
ZTK 22	10p				
ZTK 33	10p				
ZTK 33a	10p				
ZTX 102c	10p				
ZTX 107	10p				
ZTX 108c	10p				
ZTX 109k	5p				
ZTX 213	10p				
ZTX 341	10p				
ZTX 342	10p				
ZTX 384	10p				
ZTX 451	10p				
ZTX 550	10p				
ZW 13	12p				
ZW 27	10p				
ZW 4-3	10p				
ZW 310	10p				
ZX 68	50p				
ZY 47	10p				
ZY 72	10p				
AA 112	10p				
AA 113	10p				
AA 119	8p				
AA 143	10p				
AA 144	10p				
BA 102c	10p				
BA 157	8p				
BA 159	8p				
BA 173	8p				
BA 182	8p				
BA 201	8p				
BA 202	8p				
BA 243	8p				
BA 248	8p				
BA 316	8p				
BAV 10	10p				
BAV 21	10p				
BAW 21	10p				
BB 103	10p				
BB 105A	10p				
BB 105B	10p				
BB 105G	10p				
BB 121a	10p				
BZX 46c22	15p				
BZX 61c110	6p				
BZX 61c15	6p				
BZX 61c20	10p				
BZX 61c30	10p				
BZX 61c220	10p				
BZX 70c6v2	8p				
BZX 70c33	8p				
BZX 79c3v9, 4v7,					
5v1, 5v6, 6v2, 6v8,					
7v5, 11, 12, 30,					
47	10p each				
BZX 83c4v3	10p				
BZX 83c5v6	10p				
BZX 83c8v2	10p				
BZX 83b12	10p				
BRC 83c13	10p				
R 1038	50p				
R 1039	50p				
R 2008b	£1				
R 2009	£1				
R 2010b	£1				
R 2029	50p				
R 2210	60p				
R 2257	60p				
R 2265	50p				
R 2305	50p				
R 2306	50p				
R 2322/2323	pair 80p				
R 2323	15p				
R 2396	50p				
R 2461	£1				
R 2030	£1				
R 2443=BD124	40p				
R2737=TIP31A	40p				
R2738=TIP41	30p				
R2775=TIP41c	40p				
R3129=TIP47	40p				
BU 105/04	80p				
BU 108	£1				
BU 124	50p				
BU 126	80p				
BU 180a	65p				
BU 204	70p				
BU 205	£1				
BU 206	£1				
BU 207	£1				
BU 208	60p				
BU 208A	£1.20				
BU 208D	£1.30				
BU 222	£1				
BU 326	£1				
BU 407	60p				
BU 426V	60p				
BU 500	£1				
BU 526	75p				
BUX 84	50p				
BUW 84	30p				
BUY 71	£1				
E 1579	25p				
E 1580	25p				
E 1611	25p				
E 5359	10p				
E 5444	10p				
E 5577	10p				
E 9004	10p				
E 9005	10p				
TIC 106a	30p				
TIC 116n/Y 1003	35p				
TIC 126N	40p				
TIC 206m	30p				
TIC 226m	30p				
TIC 236E	30p				
TICV 106D					
(T092 case					
2A/400V)					
TIP 29	10p				
TIP 29C	25p				
TIP 30C	40p				
TIP 30A	35p				
TIP 31	30p				
TIP 31B	40p				
TIP 32	25p				
TIP 33B	50p				
TIP 34C	50p				
TIP 35C	50p				
TIP 36	50p				
TIP 41C	40p				
TIP 41B	40p				
TIP 42/BRC 6109	30p				
TIP 42B	40p				
TIP 47	40p				
TIP 48	40p				
TIP 49	30p				
TIP 100	30p				
TIP 112	30p				
TIP 115	50p				
TIP 117	50p				
TIP 120	35p				
TIP 125	35p				
TIP 130	30p				
TIP 131	30p				
TIP 136	30p				
TIP 640	75p				
TIP 2955	35p				
T 6032	30p				
T 6036	40p				
T 6040	40p				
T 6047	40p				
T 6049	40p				
T 6051	40p				
T 6052	40p				
T 9004	40p				
T 9005	40p				

PHILIPS DIY HOME SECURITY ALARMS KITS
Send for details. Prices £54 to £112.
BRITISH MADE APACHE OFF ROAD KIT
WITH BATTERY £50
2 CHANNEL RADIO CONTROL £40

Various Tools and Accessories

Mains timer, 13 amp — up to 2 hours: easy to use, plugs into socket	£3
Sellotape PVC Electric Insulation	
25mm x 20M	50p
50mm x 20M	70p
Telescopic aerials (radio)	£1
UHF Radio Aerial	50p
Xcelite pliers	£3.90
Xcelite snips	£5
Xcelite cutters	£3.90
GKN Supascrew kits	£2.50
VU meter	45p
Pull up large aerial	75p
Soldering iron 6v/23w	£2.50
Portable TV aerial	75p
Neon screwdriver	50p
Phillips snips	£2
2 way baby alarm/intercom with long leads	£5
Phillips universal battery tester/charger, fuse/bulb tester	£5
Volt/ohm test meters 1000 ohm/volt	£5
Eisenmann NICAD CHARGER 5.5V/150 ma	£2
12V Nicad pack, "AA"	£2.50
"AA"/1.25V Nicad	£1
"C" Nicad	£2
Duracell PP3	60p
1/2" x 1/2" microphone/speaker	50p
Continental 2 pin plug with 5ft mains lead (black & blue)	5 for £1
7" Ferrite rod with LW/MW coils	50p
Xcokute 5" bent nose plier	£3.50
De-solder pump + 2 nozzels	£5.20
Plastic box for i.c.s with anti-static pad 6"x3"x1/2"	75p
Can of handy oil	40p
Flat Red LED	12p

Quantity Reductions		BF 470	20 for £2
BY204/4	25 for £1.00	Metal BD 124	10 for £8
BY206	25 for £1.00	20 Slider Knobs	70p
BD132/676a	20 for £2	6 Mixed UHF Aerial Isolating Sockets, some with long leads	£1.00
W005 bridge	20 for £2		
G11 touch button red	6 for £1		
6Meg filter	10 for £2.60		
BY210/600	25 for £1.00		
BY298 3 amp/fast/R	20 for £1.50		
BD239	20 for £2.00		
MR856	25 for £1.50		
BU126	10 for £6.00		
BU208	10 for £5.00		
BU205	10 for £8.00		
BU105	10 for £6.00		
2SC2122A	10 for £8.00		
BF458	10 for £1.00		
BD136	10 for £1.25		
BF224	20 for £1.40		
OA90	40 for £1.00		
IN4148	40 for £1.00		
IN4448	40 for £1.00		
BYX10	100 for £4.00		
KT3 multcaps	10 for £7.50		
50 High voltage ceramic condensers	£1.50		
Mixed Mounting Kit for Power Transistors	50p		
300 Condensers	£1.50		
300 Resistors	£1.50		
150 Electrolytics	£2.00		
15 Bulbs	40p		
100 Diodes	£1.50		
100 Fuses	£2.00		
100 W/W Res.	£1.50		
BF 199	20 for £1		
BC 547	100 for £4		
10 x 20 Turn 100k pots. Rank	£2		
Thorn 9 volt power supply regulated	£3.00		

Mixed Packs

15 Panel mount rocker switch	£1.50
250V/10A	£1.00
Pack of mixed coloured wire	£1.00
25 LED red/yellow/green	£1.50
20/C Holders	£1.20
20 Large LED Red	£1.00
20 Small LED Red	£1.00
10x20 Turn 100K Pots	£1.00
100 Mixed Transistor	£2.50
20 Convergence Pots	80p
100 Mixed Sticks	£1.00
10 Thermistors	50p
20 Slider Pots	£1.00
30 Presets	50p
15 VDR + thermistors, degaussing, HT, etc.	£1.00
40 glass reed switch	£1
10 press to make switch	£1
40 Pots	£1.50
10 Gun Switches	50p
5 Tube Bases	£1.00
1,000 Diodes, Condensers, Resistors on Bandolier	£3.00
Lucky Dip 600 gram	£1.00
25 mixed High voltage pulse condenser	£1.00
Jungle Bag 5Kg	£5.00
20 Knobs	£1.00

SENDZ COMPONENTS
63 Bishopsteignton,
Shoeburyness, ESSEX SS3 8AF
SAME DAY SERVICE
All items subject to availability.
No Accounts : No Credit Cards
Postal Order/Cheque with order
Add 15% VAT, then £1 P+P
Add Postage for overseas
Callers: To shop at 212 London Rd.,
Southend. Tel. 0702-332992

SENDZ COMPONENTS

63 Bishopsteignton,
Shoeburyness, ESSEX SS3 8AF

SAME DAY SERVICE

All items subject to availability.

No Accounts : No Credit Cards

Postal Order/Cheque with order

Add 15% VAT, then £1 P+P

Add Postage for overseas

Callers: To shop at 212 London Rd.,
Southend. Tel. 0702-332992

3 Way regulated adaptor 240V 6V/7.5/9V/300mA £3.50	GEC 2040 £5.00	GEC 2110 £7.00	Pye mono £3.00	Rank mono T704A £3.50	CVC32 ITT £7.50	EHT Split Diode Leads £1.00	GEC portable chassis + LOPT £6	Thorn 1613/1713 chassis £9.75	Full remote G11 hand set, repaired £12 exchange	Hills 520 multimeter + case. 20,000Ω/volt, fuse diode protected + logic test facility. 10meg/1200 volt £19.50	Hand-set Thorn 9000 ultrasonic sound & channel change £3.50	60.CP2605 Philips infra red hand set. Full remote 9 C.H. £6.00	12 C.H. £12.00	12/300 10p	600/300V £1.50	4.7M/350v 10p	16/350 25p	50/350 10p	220/350 30p	300/350 40p	700/350 50p	22/375 15p	330/385 CVC 820HT 60p	0.1/400 15p	.56K/400v 20p	8/400 15p	33/400 20p	320/400 50p	400/400 40p	2k 10,000P/400 in box 40p	394K/400V 20p	23/450 15p	220/450 40p	0.1/600 15p	.047/600 15p	0.1/800 15p	0.047/1000 10p	0.01/1000 10p	0.1/1000 10p	.15/1000 20p	.47/250V A.C. 10p	.47/1000 50p	.001K/1250 10p	0.0047/1500 10p	.005/1500 10p	.0105/1500 10p	1n8/1500 15p	2n2/1500 15p	G11.11000/1500 15p	G11.8200/2KV 15p	0.1/2KV 20p	10n/2KV 15p	3n9/2KV 15p	210/8KV 10p	0.0015/2KV 10p	5n2/2KV 10p	6n2/2KV 15p	7500p/2KV 10p	4n7/2KV 15p	8n2/2KV 15p	0.0082/2500 15p	150/3500 10p	1800/4KV 5p	4.7n/5KV 10p	170/8KV 10p	180/8KV 10p	210/8KV 10p	270/8KV 10p	1000/10KV 10p	210/12KV 10p	1000/12KV 10p	1200/12KV 10p	Multi-Caps																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																															
THORN 4000 ultra sonic hand set insert with 7 buttons (no case) £5	Universal £6.00	11 TEZ Rank £3.00	9000 Thorn £5.00	KT3 £4.00	G9 Philips £4.00	GEC 2110 £4.00	9500 Thorn £4.50	2040 GEC £3.50	GEC TVM25 Tripler £2.00	G8 Philips £4.50	Decca 80 100 £4.50	LP1194 Pye 731 £3.50	Grundig TVK 52 £2.50	11TBG £3.00	11THY £4.00	D22 for Pye 18" colour portable £4.00	LP 1193/63 £4.00	BG 100/41 £3.25	BG 100/61 £3.25	New Philips Infra Red Transmitter 9ch & Vol. & brightness change £7.00	GEC Portable Line Trans. £3.00	THORN 9000 tube base & panel £1.50	9000 front panel £5.00	9000 front panel (remote) £8.00	THORN 8800/9000 Remote Unit U705 £6.00	THORN 9000 Frame Panel £8.00	G8 Convergence Panel £12.00	T/text ultrasonic rec'r panel £14.00	Philips Handset (2 button unit) £8.00	THORN 9000 Syclops panel £1.50	THORN 8000/8500 timebase panel £8.00	THORN 8000/8500/8800 chroma panel £15.00	THORN 8500 convergence panel £6.00	Philips Infra-Red (full remote transmitter) Philips KT3 16C928/20C934 Pye KT3 7228/7324 K12 26C £12	G11 handset, Full remote top £12.00	Video cassette lamps on lead. 12-14V. 50p or 3 for £1.00	GEC 8 touch unit assy complete with all I.C.'s + pots £6.00	9000 Frame Panel £7.00	Transmitter Decca RC11 £14	Transmitter Decca RC12 £14	G11 E.W. coils £1.00	G11 Tuner Unit/U321 £6.00	G11 6 Button Key Switch £2.00	G11 Transient Suppressors 245V 10 for £1.00	G11 Scan Coils £5.00	KT3 AE Sockets 25p	4000 Thorn Frame Panel £5.00	4000 Thorn Power Supply £3.00	4000 Thorn Line OP Panel £20.00	NPN PNP 80V 6 Amp TO66 O.P. Trans. pair 25p	GEC IC CBF16848. SN16861. SN1682 each 50p	Thorn Tuner Panel 6-100K Pots & Components NEW No Tuner £2.00	6 button 100K pots + cursors on panel for varicap tuning £1.50	THORN 1600 mains lead: switch: 3 slider assy. £2.00	5 button touch tuner BBC1/2 ITV1/2 video with ic SAS 560T/570T £7.00	Control panel 5 sliders + mains lead £1.50	Thorn 8800 remote receiver unit U705 £6	G11 8 touch button unit replaces old 6 P.B.U. £20	International Rectifier EHT Diodes 6A/600V Stud Diodes 20p	6A/1000V Stud Diodes 20p	G770/HV34 6KV 3 for 8p	EHT Rectifier wire ends 16Kv 10p	25A473 PNP C/P 10p	Tube Base + base-unit for 820 Euro chassis £4.00	GEC Line O/P Trans. & Rec Stk for Portable £3.00	CVC 20/25/30/35/40 decoder panel £10	CVC 20/25/30/35/40 decoder panel (untested) £5	CVC 40/45 1F panel £5	Thorn 3500 6 push button unit & cable form £1.50	470/16 6p	1500/16 20p	3300/16 20p	10000/16 25p	15000/16 25p	3300/18 20p	470/25 5p	680/25 5p	1000/25 Radial 10p	1250/25 10p	1500/25 10p	2200/25 10p	3300/25 20p	4700/25 25p	5000/25 25p	10000/25 25p	1500/30 20p	3300/30 30p	1500/35 10p	2200/35 25p	50/40 5p	220/40 5p	400/40 20p	680/40 20p	1250/40 20p	1500/40 20p	2000/40 25p	2000/40 25p	2200/40 25p	2500/40 25p	3300/40 25p	6800/40 35p	750/50 10p	1000/50 20p	1250/50 25p	2000/50 20p	3000/50 25p	15/63 5p	Z743 RANK IF Panel Export 5.5MHz 3 I.C.'s 47/63 Bipolar 15p	TBA750+SC9504P+SC9503P £1.50	Tuner Unit VHF Sylvania GTR Videon MTS900 BIP VHF £7.50	G11 dynamic correction panel £6	CVC 20 Front panel with sliders + mains input panel £4	THORN 3500 Tuner panel (ELC 1043/05 + pots) £7	CVC 40 PUSH BUTTON ASSY with sliders: complete with lamp assy + pots £14	CVC 5 Mains on/off + 5 pots £2	GEC Convergence panel TO CLEAR £1	Universal Focus. Fits Pye, Thorn and Decca Units. £1.75	Large Type 75p	Decca Small 75p	KT3 Focus Unit 75p	ITT Small for use with Split Diode 50p	8/350 8p	Thorn 3500 Focus Unit £1.50	Remo TV12SP 50p	TV11 50p	TV13 50p	TV14 50p	TV18 60p	TV20 £1.00	TV45 50p	16 Button Key Pad 1 to 0 + * + # + 4 blank £3.00	Condensers	470/16 6p	1500/16 20p	3300/16 20p	10000/16 25p	15000/16 25p	3300/18 20p	470/25 5p	680/25 5p	1000/25 Radial 10p	1250/25 10p	1500/25 10p	2200/25 10p	3300/25 20p	4700/25 25p	5000/25 25p	10000/25 25p	1500/30 20p	3300/30 30p	1500/35 10p	2200/35 25p	50/40 5p	220/40 5p	400/40 20p	680/40 20p	1250/40 20p	1500/40 20p	2000/40 25p	2000/40 25p	2200/40 25p	2500/40 25p	3300/40 25p	6800/40 35p	750/50 10p	1000/50 20p	1250/50 25p	2000/50 20p	3000/50 25p	15/63 5p	Z743 RANK IF Panel Export 5.5MHz 3 I.C.'s 47/63 Bipolar 15p	TBA750+SC9504P+SC9503P £1.50	Tuner Unit VHF Sylvania GTR Videon MTS900 BIP VHF £7.50	G11 dynamic correction panel £6	CVC 20 Front panel with sliders + mains input panel £4	THORN 3500 Tuner panel (ELC 1043/05 + pots) £7	CVC 40 PUSH BUTTON ASSY with sliders: complete with lamp assy + pots £14	CVC 5 Mains on/off + 5 pots £2	GEC Convergence panel TO CLEAR £1	Universal Focus. Fits Pye, Thorn and Decca Units. £1.75	Large Type 75p	Decca Small 75p	KT3 Focus Unit 75p	ITT Small for use with Split Diode 50p	8/350 8p	Thorn 3500 Focus Unit £1.50	Remo TV12SP 50p	TV11 50p	TV13 50p	TV14 50p	TV18 60p	TV20 £1.00	TV45 50p	16 Button Key Pad 1 to 0 + * + # + 4 blank £3.00	Condensers	470/16 6p	1500/16 20p	3300/16 20p	10000/16 25p	15000/16 25p	3300/18 20p	470/25 5p	680/25 5p	1000/25 Radial 10p	1250/25 10p	1500/25 10p	2200/25 10p	3300/25 20p	4700/25 25p	5000/25 25p	10000/25 25p	1500/30 20p	3300/30 30p	1500/35 10p	2200/35 25p	50/40 5p	220/40 5p	400/40 20p	680/40 20p	1250/40 20p	1500/40 20p	2000/40 25p	2000/40 25p	2200/40 25p	2500/40 25p	3300/40 25p	6800/40 35p	750/50 10p	1000/50 20p	1250/50 25p	2000/50 20p	3000/50 25p	15/63 5p	Z743 RANK IF Panel Export 5.5MHz 3 I.C.'s 47/63 Bipolar 15p	TBA750+SC9504P+SC9503P £1.50	Tuner Unit VHF Sylvania GTR Videon MTS900 BIP VHF £7.50	G11 dynamic correction panel £6	CVC 20 Front panel with sliders + mains input panel £4	THORN 3500 Tuner panel (ELC 1043/05 + pots) £7	CVC 40 PUSH BUTTON ASSY with sliders: complete with lamp assy + pots £14	CVC 5 Mains on/off + 5 pots £2	GEC Convergence panel TO CLEAR £1	Universal Focus. Fits Pye, Thorn and Decca Units. £1.75	Large Type 75p	Decca Small 75p	KT3 Focus Unit 75p	ITT Small for use with Split Diode 50p	8/350 8p	Thorn 3500 Focus Unit £1.50	Remo TV12SP 50p	TV11 50p	TV13 50p	TV14 50p	TV18 60p	TV20 £1.00	TV45 50p	16 Button Key Pad 1 to 0 + * + # + 4 blank £3.00	Condensers	470/16 6p	1500/16 20p	3300/16 20p	10000/16 25p	15000/16 25p	3300/18 20p	470/25 5p	680/25 5p	1000/25 Radial 10p	1250/25 10p	1500/25 10p	2200/25 10p	3300/25 20p	4700/25 25p	5000/25 25p	10000/25 25p	1500/30 20p	3300/30 30p	1500/35 10p	2200/35 25p	50/40 5p	220/40 5p	400/40 20p	680/40 20p	1250/40 20p	1500/40 20p	2000/40 25p	2000/40 25p	2200/40 25p	2500/40 25p	3300/40 25p	6800/40 35p	750/50 10p	1000/50 20p	1250/50 25p	2000/50 20p	3000/50 25p	15/63 5p	Z743 RANK IF Panel Export 5.5MHz 3 I.C.'s 47/63 Bipolar 15p	TBA750+SC9504P+SC9503P £1.50	Tuner Unit VHF Sylvania GTR Videon MTS900 BIP VHF £7.50	G11 dynamic correction panel £6	CVC 20 Front panel with sliders + mains input panel £4	THORN 3500 Tuner panel (ELC 1043/05 + pots) £7	CVC 40 PUSH BUTTON ASSY with sliders: complete with lamp assy + pots £14	CVC 5 Mains on/off + 5 pots £2	GEC Convergence panel TO CLEAR £1	Universal Focus. Fits Pye, Thorn and Decca Units. £1.75	Large Type 75p	Decca Small 75p	KT3 Focus Unit 75p	ITT Small for use with Split Diode 50p	8/350 8p	Thorn 3500 Focus Unit £1.50	Remo TV12SP 50p	TV11 50p	TV13 50p	TV14 50p	TV18 60p	TV20 £1.00	TV45 50p	16 Button Key Pad 1 to 0 + * + # + 4 blank £3.00	Condensers	470/16 6p	1500/16 20p	3300/16 20p	10000/16 25p	15000/16 25p	3300/18 20p	470/25 5p	680/25 5p	1000/25 Radial 10p	1250/25 10p	1500/25 10p	2200/25 10p	3300/25 20p	4700/25 25p	5000/25 25p	10000/25 25p	1500/30 20p	3300/30 30p	1500/35 10p	2200/35 25p	50/40 5p	220/40 5p	400/40 20p	680/40 20p	1250/40 20p	1500/40 20p	2000/40 25p	2000/40 25p	2200/40 25p	2500/40 25p	3300/40 25p	6800/40 35p	750/50 10p	1000/50 20p	1250/50 25p	2000/50 20p	3000/50 25p	15/63 5p	Z743 RANK IF Panel Export 5.5MHz 3 I.C.'s 47/63 Bipolar 15p	TBA750+SC9504P+SC9503P £1.50	Tuner Unit VHF Sylvania GTR Videon MTS900 BIP VHF £7.50	G11 dynamic correction panel £6	CVC 20 Front panel with sliders + mains input panel £4	THORN 3500 Tuner panel (ELC 1043/05 + pots) £7	CVC 40 PUSH BUTTON ASSY with sliders: complete with lamp assy + pots £14	CVC 5 Mains on/off + 5 pots £2	GEC Convergence panel TO CLEAR £1	Universal Focus. Fits Pye, Thorn and Decca Units. £1.75	Large Type 75p	Decca Small 75p	KT3 Focus Unit 75p	ITT Small for use with Split Diode 50p	8/350 8p	Thorn 3500 Focus Unit £1.50	Remo TV12SP 50p	TV11 50p	TV13 50p	TV14 50p	TV18 60p	TV20 £1.00	TV45 50p	16 Button Key Pad 1 to 0 + * + # + 4 blank £3.00	Condensers	470/16 6p	1500/16 20p	3300/16 20p	10000/16 25p	15000/16 25p	3300/18 20p	470/25 5p	680/25 5p	1000/25 Radial 10p	1250/25 10p	1500/25 10p	2200/25 10p	3300/25 20p	4700/25 25p	5000/25 25p	10000/25 25p	1500/30 20p	3300/30 30p	1500/35 10p	2200/35 25p	50/40 5p	220/40 5p	400/40 20p	680/40 20p	1250/40 20p	1500/40 20p	2000/40 25p	2000/40 25p	2200/40 25p	2500/40 25p	3300/40 25p	6800/40 35p	750/50 10p	1000/50 20p	1250/50 25p	2000/50 20p	3000/50 25p	15/63 5p	Z743 RANK IF Panel Export 5.5MHz 3 I.C.'s 47/63 Bipolar 15p	TBA750+SC9504P+SC9503P £1.50	Tuner Unit VHF Sylvania GTR Videon MTS900 BIP VHF £7.50	G11 dynamic correction panel £6	CVC 20 Front panel with sliders + mains input panel £4	THORN 3500 Tuner panel (ELC 1043/05 + pots) £7	CVC 40 PUSH BUTTON ASSY with sliders: complete with lamp assy + pots £14	CVC 5 Mains on/off + 5 pots £2	GEC Convergence panel TO CLEAR £1	Universal Focus. Fits Pye, Thorn and Decca Units. £1.75	Large Type 75p	Decca Small 75p	KT3 Focus Unit 75p	ITT Small for use with Split Diode 50p	8/350 8p	Thorn 3500 Focus Unit £1.50	Remo TV12SP 50p	TV11 50p	TV13 50p	TV14 50p	TV18 60p	TV20 £1.00	TV45 50p	16 Button Key Pad 1 to 0 + * + # + 4 blank £3.00	Condensers	470/16 6p	1500/16 20p	3300/16 20p	10000/16 25p	15000/16 25p	3300/18 20p	470/25 5p	680/25 5p	1000/25 Radial 10p	1250/25 10p	1500/25 10p	2200/25 10p	3300/25 20p	4700/25 25p	5000/25 25p	10000/25 25p	1500/30 20p	3300/30 30p	1500/35 10p	2200/35 25p	50/40 5p	220/40 5p	400/40 20p	680/40 20p	1250/40 20p	1500/40 20p	2000/40 25p	2000/40 25p	2200/40 25p	2500/40 25p	3300/40 25p	6800/40 35p	750/50 10p	1000/50 20p	1250/50 25p	2000/50 20p	3000/50 25p	15/63 5p	Z743 RANK IF Panel Export 5.5MHz 3 I.C.'s 47/63 Bipolar 15p	TBA750+SC9504P+SC9503P £1.50	Tuner Unit VHF Sylvania GTR Videon MTS900 BIP VHF £7.50	G11 dynamic correction panel £6	CVC 20 Front panel with sliders + mains input panel £4	THORN 3500 Tuner panel (ELC 1043/05 + pots) £7	CVC 40 PUSH BUTTON ASSY with sliders: complete with lamp assy + pots £14	CVC 5 Mains on/off + 5 pots £2	GEC Convergence panel TO CLEAR £1	Universal Focus. Fits Pye, Thorn and Decca Units. £1.75	Large Type 75p	Decca Small 75p	KT3 Focus Unit 75p	ITT Small for use with Split Diode 50p	8/350 8p	Thorn 3500 Focus Unit £1.50	Remo TV12SP 50p	TV11 50p	TV13 50p	TV14 50p	TV18 60p	TV20 £1.00	TV45 50p	16 Button Key Pad 1 to 0 + * + # + 4 blank £3.00	Condensers	470/16 6p	1500/16 20p	3300/16 20p	10000/16 25p	15000/16 25p	3300/18 20p	470/25 5p	680/25 5p	1000/25 Radial 10p	1250/25 10p	1500/25 10p	2200/25 10p	3300/25 20p	4700/25 25p	5000/25 25p	10000/25 25p	1500/30 20p	3300/30 30p	1500/35 10p	2200/35 25p	50/40 5p	220/40 5p	400/40 20p	680/40 20p	1250/40 20p	1500/40 20p	2000/40 25p	2000/40 25p	2200/40 25p	2500/40 25p	3300/40 25p	6800/40 35p	750/50 10p	1000/50 20p	1250/50 25p	2000/50 20p	3000/50 25p	15/63 5p	Z743 RANK IF Panel Export 5.5MHz 3 I.C.'s 47/63 Bipolar 15p	TBA750+SC9504P+SC9503P £1.50	Tuner Unit VHF Sylvania GTR Videon MTS900 BIP VHF £7.50	G11 dynamic correction panel £6	CVC 20 Front panel with sliders + mains input panel £4	THORN 3500 Tuner panel (ELC 1043/05 + pots) £7	CVC 40 PUSH BUTTON ASSY with sliders: complete with lamp assy + pots £14	CVC 5 Mains on/off + 5 pots £2	GEC Convergence panel TO CLEAR £1	Universal Focus. Fits Pye, Thorn and Decca Units. £1.75	Large Type 75p	Decca Small 75p	KT3 Focus Unit 75p	ITT Small for use with Split Diode 50p	8/350 8p	Thorn 3500 Focus Unit £1.50	Remo TV12SP 50p	TV11 50p	TV13 50p	TV14 50p	TV18 60p	TV20 £1.00	TV45 50p	16 Button Key Pad 1 to 0 + * + # + 4 blank £3.00	Condensers	470/16 6p	1500/16 20p	3300/16 20p	10000/16 25p	15000/16 25p	3300/18 20p	470/25 5p	680/25 5p	1000/25 Radial 10p	1250/25 10p	15

Tuner Units	
ELC1043/05 Mullard	£6.00
ELC1043 (Ex Panel)	£3.75
ELC1042	£5.00
ELC2000	£7.00
ELC2004	£10.00
EL2006	£10.00
EL2060	£7.00
ELC2060 on panel NEW	£5.00
Mullard 1043/05 on panel	£5.00
U321 (UHF) Mullard	£7.00
U322 (UHF)	£4.00
V314 (VHF)	£5.00
U341 UHF	£7.00
ELC1043/05 Thom	£5.90
Small V/Cap Mitsumi	
UHF	£4.00
VHF	£3.00
Portable & rotary Tuners Sanyo & Mitsumi UHF	£5.00
NSF-UHF-VHF	£8.00
Mullard	£10.00

Video Modulator. Application, video tape recorders, TV cameras, video games, closed circuit TV.

C.C.T.R. system. Data supplied.

Berec Battery SB1142 2 amp discharge current 8.4 volts with magnet switch made for emergency lighting. Nickel cadmium battery £4.00

Sylvania UHF VHF F6013 (Fits Rank)	£6.00
Sylvania UHF F4720B	£6.00
Sylvania VHF 900	£6.00
Decca Bradford Tuner 5	
Button	£4.00
Small Tuner DX 175-220MHz	
Auto Changeover	£5.00
9000 Thom Tuner on Panel	£7.00
D.P.D.T. switch Black knob:	
Chassis or PCB mount	4p
each or 40 for £1.00	

THORN 1400 4P.B. Mech. Tuner
 THORN 1500 4P.B. Mech. Tuner
 THORN 1590 4P.B. Mech. Tuner
 THORN 3500 4P.B. Mech. Tuner
 THORN 8000 4P.B. Mech. Tuner
 THORN 8500 4P.B. Mech. Tuner
 All new & boxed £4 each + £1 postage each

Diodes	
1 Amp 1600v	7p
3 Amp 100v	7p
3 Amp 1200v	10p
7 Seg Display, Led Red Delay Lines	50p

BFT43	10p	2SC2122A	£1.00
BFT84	8p	2SC2229	15p
BFW11	20p	2SC7350	15p
BFX29	30p	2SD180 TO3 80v/	
BFX84	25p	6A	15p
BFY50	15p	2SD200	£2.00
BFY52	20p	2SK30A	10p
BFY90	25p	2SN30A	8p
BRC116	40p	BC107	10p
BRX43	15p	BC108	10p
BRX48X	10p	BC109/2N930	5p
BSY95a	10p	BC113	10p
BTY80	10p	BC114	10p
BSX19	17p	BC115	10p
BSX20	17p	BC116	10p
FT3055	30p	BC117	20p
TCE82	30p	BC125	10p
2N930	5p	BC139	10p
2N2221	8p	BC141	25p
2N2222	8p	BC142	25p
2N3055	40p	BC143	25p
2N3702	10p	BC147	10p
2N3703	10p	BC148	10p
2N3705	10p	BC149	10p
2N3711	10p	BC153	10p
2N3583	10p	BC154	10p
2N3904	15p	BC157a	10p
2N3906	15p	BC159	10p
2N4355	10p	BC160	25p
2N4442	£1.00	BC171	10p
2N4444	£1.00	BC172	10p
2N5296	40p	BC173	10p
2N5496	50p	BC174	10p
2N5983	30p	BC182L	10p
2N6099	40p	BC183	10p
2N6109	40p	BC184	10p
2N6130	50p	BC187	10p
2N6133	20p	BC204	10p
2N6348	20p	BC207	10p
2N6399A	20p	BC212	10p
2X 2N6099 on heat sink	50p	BC213	10p
2SB407 Sanyo TO3	10p	BC214	10p
2SB474	10p	BC237	10p
2SB566	10p	BC238	8p
2SC381	10p	BC239	10p
2SC458	50p	BC250	8p
2SC515	10p	BC251	10p
2SC732	10p	BC252	10p
2SC733	10p	BC262	10p
2SC828	10p	BC263b	20p
2SC1030	£1.00	BC294	10p
2SC1172A	10p	BC298	10p
2SC1173	10p	BC300	30p
2SC1311	20p	BC301	30p
2SC1419	20p	BC303	30p
2SC1546	20p	BC307	7p
2SC1617	£1.00	BC308	7p
2SC1684	20p	BC309	10p
2SC1725	20p	BC327	10p
2SC2068	20p	BC328	10p
2SC2073	8p	BC328/338 pair	15p
		BC337	10p
		BC338	10p

SENDZ COMPONENTS

63 Bishopsteignton, Shoeburyness, ESSEX SS3 8AF

SAME DAY SERVICE

All items subject to availability.
 No Accounts - No Credit Cards
 Postal Order/Cheque with order
 Add 15% VAT, then £1 P + P
 Add Postage for overseas

Callers: To shop at 212 London Rd., Southend. Tel. 0702-332992

TAU80	£1.00	CA3146	£1.00
DL11	50p	CA920AE	£1.00
DL20A	80p	CA1310	50p
DL70	£1.00	CD4510	30p
DL600	£1.00	CBF16848	50p
DL700	£1.00	DM7492	50p
UDL11	30p	HEF4001	10p
KT 3 Luminescence	75p	HF4011AF	10p
Luminescence Delay Line		HEF4016	15p
MDL-CBL Min.	50p	HEF4053B	30p
3.15 Fuses	4p	M913	£2.00
Co-Ax Joint	12p	M1024	£2.00
Co-Ax Belling Lee Plug	12p	M1025	£2.00
Co-Ax Splitter	£1.00	MC476p	£1.00
UHF Modulator CCIR	£3.00	MC1307	75p
Infra Red Emitting Diode	20p	MC1327	£1.25
NE286H Small Neon Lamps		MC1330	75p
GEC	5p	MC1349	50p
Mullard 5 Watt Amps. LP1162		MC1352	£1.00
New	75p	MC1358	£1.00
		MC14001	10p
		MC14002	15p
		MC14013	25p
		MC14016	25p
		MC14066BCP	30p
		MC14069	15p
		MC14514	50p
		MC1748	80p
		MCM2114	£1.00
		NES11NE	£1.00
		MEM4956PT	£1.00
		MM5387	£1.00
		MM5611	£1.00
		MM5840	50p
		ME6100	£1.00
		ME545B (Dolby)	75p
		NES55P	60p
		NES55S	60p
		NES55	60p
		IL1	30p
		OPT600	30p
		OPT601	30p
		SAA611	£1.00
		SAA661	£1.75
		SAA1020	£4.00
		SAA1021	£4.00
		SAA1024	£2.50
		SAA1025	£2.50
		SAA1073	£3.00
		SAA1074	£3.00
		SAA1075	£3.00
		SAA1124	£2.00
		SAA1130	£2.50
		SAA1174	£3.00
		SAA1176	£3.00
		SAA1250	£3.00
		SAA1272	£3.00
		SAA1276	£3.00
		SAAS000	£1.50
		SAAS000A	£1.50
		SAAS010	£3.50
		SAAS012	£3.50
		SAAS012A	£4.00
		SAAS020	£3.50
		SAAS030	£5.00
		SAAS040	£3.50
		SAAS040A	£4.40
		SAAS050	£3.50
		SAF1039	£2.00
		SAS560	£1.00
		SAS570	£1.00
		SAS560	£1.00
		SAS670	£1.00
		SL901B	£4.40
		SL918	£6.00
		SL917 MOD	£6.00
		TAA320A	50p
		TAA470	£1.50
		TAA550	25p
		TAA570	75p

BC347	10p	OPT600	30p
BC349b	10p	OPT601	30p
BC350	20p	SAA611	£1.00
BC365	10p	SAA661	£1.75
BC384	10p	SAA1020	£4.00
BC394	10p	SAA1021	£4.00
BC413	10p	SAA1024	£2.50
BC414	10p	SAA1025	£2.50
BC416	10p	SAA1073	£3.00
BC440	30p	SAA1074	£3.00
BC454	10p	SAA1075	£3.00
BC455	10p	SAA1124	£2.00
BC456	10p	SAA1130	£2.50
BC460	25p	SAA1174	£3.00
BC462	10p	SAA1176	£3.00
BC463	10p	SAA1250	£3.00
BC478	10p	SAA1272	£3.00
BC527	10p	SAA1276	£3.00
BC532	10p	SAAS000	£1.50
BC546	25p	SAAS000A	£1.50
BC547	10p	SAAS010	£3.50
BC548	10p	SAAS012	£3.50
BC556	10p	SAAS012A	£4.00
BC557	10p	SAAS020	£3.50
BC558	10p	SAAS030	£5.00
BC559	10p	SAAS040	£3.50
BC635	10p	SAAS040A	£4.40
BCX31	25p	SAAS050	£3.50
BCX32/36 pair	50p	SAF1039	£2.00
BD116	25p	SAS560	£1.00
BD124	50p	SAS570	£1.00
BD124 (metal)	60p	SAS560	£1.00
BD130Y	25p	SAS670	£1.00
BD131	30p	SL901B	£4.40
BD132/676a	30p	SL918	£6.00
BD135	25p	SL917 MOD	£6.00
BD136	30p	TAA320A	50p
BD176	25p	TAA470	£1.50
BD182	£1.00	TAA550	25p
BD202	60p	TAA570	75p
BD203/204 pair	£1.25		
BD204	60p		
BD207	30p		
BD221	20p		
BD222	20p		
BD226	20p		
BD233	30p		
BD235	30p		
BD238	30p		
BD239	15p		
BD243a	30p		
BD250a	30p		
BD252	20p		
BD253B	50p		
BD331	20p		
BD332	7p		
BD416	25p		
BD433	25p		
BD437	25p		

Filters	Thyristors	Thermistors
5.5MHz	BT119	VA110A
6MHz	BT120	ITTP7266312
BFU455K	BRC4443	PTH451 AOR
	G11 Thyristor	PT37P Fits Pye & Bush
	Decca 80-100	PT34
		Degausing Thermistor (fits most sets)
		GEC Double Thermistor

TAA611	£1.50	TAA621	£2.00
TAA661	£1.75	TAA641	£1.50
TA7117	50p	TA7117	50p
TA7315AP	50p	TA7607AP	50p
TBA120A	50p	TBA120A	50p
TBA120SA	50p	TBA120B	40p
TBA120SB	40p	TBA120SQ	£1.00
TBA120U	50p	TBA120C	40p
TBA1441	£1.00	TBA231	75p
TBA395Q	50p	TBA396Q	£1.00
TBA396	75p	TBA440C	£1.00
TBA480Q	£1.00	TBA510	£1.00
TBA510Q	£1.00	TBA520	£1.00
TBA530	£1.00	TBA540	£1.00
TBA540Q	£1.00	TBA560CQ	£1.00
TBA560C	£1.00	TBA570	£1.00
TBA625	£5.00	TBA625	£5.00
TBA641BX1	£2.00	TBA651	£2.00
TBA673	£1.00	TBA720A	£1.00
TBA750Q	£1.20	TBA750Q	£1.20
TBA800	40p	TBA810S	70p
TBA820	70p	TBA890	£1.00
TBA900	£1.20	TBA920	£1.50
TBA920Q	£1.50	TBA950	£1.00
TBA960Q	£1.00	TBA990Q	£1.00
TBA1440	£1.00	TMS1000NL	£4.00
TMS1943NL	£2.00	TMS9890	£4.00
TMS9901	£2.00	TMS2716	£2.00
TMS3529	£2.00	TMS4014	£1.50
TMS4014	£1.50	TX012	£5.00
TMS9902	£3.00	UPD2114C 4K	75p
RAM	SN74133	SN74133	50p
SN74133	50p	SN16861	50p
SN16861	50p	SN16862AN	£1.00
SN16862AN	£1.00	SN16964AN	50p
SN29764	£1.00	SN29728N	50p
SN29728N	50p	RGP30G	10p
MPSA43	10p	MJ13005	30p
MJ13005	30p	MJE117	25p
MJE117	25p	MJE340	28p
MJE340	28p	MJE660	25p
MJE660	25p	MJE661	25p
MJE3055	£1.00	MJE2801	30p
MJE2801	30p	MJE2955	30p
MJE2955	30p	MJE13005	30p
MJE13005	30p	Sanikron Diode	10p
Sanikron Diode	10p	SKE2G2/04	30p

3 Pin Blue Thermistor (h/s most sets)	Crystal T/V
BLY49	T/V 4.433-619KHz
I.C. Heat Sink	6 MHz Crystal
20xTO5 Heat Sink	8.8867-238KHz Min
T4040 Clock Display	Mminiature ITT 6meg
CVC 9 power supply board	
CVC 20/2 mains panel	
FED4/1220/4 3 pin ITT	
MFD 4 Amp Mains Filters	
ITT Mains Filter 1/250v/	
CVC 20 to 45 chassis	
Pots 10 k with Switch	
Pots 47 k with Switch	
Mullard Surface Wave Filter	
RW 153P Colour TV Filter	
Mullard Surface Wave Filter	
RW 154 Colour TV Filter	
G11 Line Scan P.C.B.	
ELC 1042 P.C.B.	

BTT6018-ML237B	£1.50	AC188	15p
ML237B	£1.00	AC188K	15p
BT18124	£1.00	ACY18</	