

SEPTEMBER 1984

Australia \$1.80, New Zealand \$2.20, Malaysia \$5.50

£1.00

TELEVISION

SERVICING·PROJECTS·VIDEO·DEVELOPMENTS

VCR Servo Systems



Servicing the Grundig GSC100

The Salora Ipsalo-2 Circuit

CCTV Commentary ● VCR Clinic

TV Fault Finding ● DX-TV

MANOR SUPPLIES

NEW MKV PAL COLOUR TEST GENERATOR FOR TV & VCR.

TEST DEMONSTRATIONS AT 172 WEST END LANE



- ★ 40 different patterns and variations.
- ★ Broadcast transmission accuracy (fully interlaced sync pulses with correct picture blanking).
- ★ EBU colour bars, BBC colour bars, whole rasters & split bars (specially useful for VCR service), white, yellow, cyan, green, magenta, red, blue and black.
- ★ Chequerboard.
- ★ Mono outputs with border castellations, cross hatch, grey scale, vertical lines, horizontal lines and dots. UHF modulator output plugs straight into receiver aerial socket.
- ★ Additional video output for CCTV & VCR.
- ★ Facilities for sound output.
- ★ Easy to build kit, standard parts. Only 2 adjustments. No special test equipment required.
- ★ Mains operated with stabilised power supply.
- ★ All kits fully guaranteed with back-up service.
- ★ Also available with VHF Modulator.


Price of Kit **£70.00**
 De Luxe Case (10"×6"×2½") **£7.40**
 Optional Sound Module (6MHz or 5.5MHz) **£3.90**
 Built & Tested in De Luxe Case including Sound Module **£105.00**

SPECIAL TEST REPORT 'TELEVISION' DEC. 1982

Post/Packing £2.50
 Add VAT 15% TO ALL PRICES

PAL COLOUR BAR GENERATOR (Mk4)

4TH SUCCESSFUL YEAR

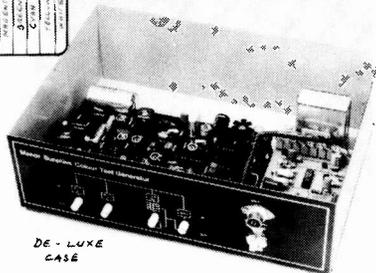

- ★ Output at UHF, applied to receiver aerial socket.
- ★ In addition to colour bars R-Y, B-Y etc.
- ★ Cross-hatch, grey scale, peak white and black level.
- ★ Push button controls, battery or mains operated.
- ★ Simple design, only five i.c.s on colour bar P.C.B.

PRICE OF MK 4 COLOUR BAR GENERATOR KIT **£30.00**. DELUXE CASE **£7.40**. BATT HOLDERS **£2.80**. MAINS SUPPLY KIT **£4.20** (Combined P&P **£2.20**).

MK 4 DE LUXE (BATTERY) BUILT & TESTED **£58.00** + **£2.20** P & P.
 MK 4 DE LUXE (MAINS) BUILT & TESTED **£68.00** + **£2.20** P & P.
 VHF MODULATOR (CH 1 to 4) FOR OVERSEAS **£5.75**.
 EASILY ADAPTED FOR VIDEO OUTPUT & C.C.T.V.
 (ADD VAT 15% TO ALL PRICES)

MANOR SUPPLIES TELETEXT ADAPTOR KITS (LESS CASE)

MK 1 (Texas XMII) remote control **£120.00** p.p. **£3.00**.
 MK 2 (Mullard) infra red remote control **£150.00** p.p. **£3.00**.
 Further details on request. Tel 01-794 8751/7346

Goods available if in stock immediately over shop counter (Mail order between 3 days and 1 week from receipt of order).

TV SERVICE SPARES

BACKED BY TWENTY YEARS EXPERIENCE & STAFF OF TECHNICAL EXPERTS

TELEVISION MAGAZINE PROJECT PARTS

COLOUR PORTABLE TV
 MONO PORTABLE TV, SMALL SCREEN MONITOR ETC.

- THORN TX10 type Remote & Tuning Control Panel **£9.40** p.p. **£1.50**
 PHILIPS UHF Modulator (Audio & Video Input) **£15.00** p.p. **£1.50**
 SAW FILTER IF AMPLIFIER PLUS TUNER complete and tested for T.V. Sound & Vision. **£28.50** p.p. **£1.20**.
 THORN TX9, TX10 Saw Filter IF Panel. **£8.50** p.p. **80p**.
 PAL DECODER KIT for RGB Monitors **£27.00** p.p. **£1.00**.
 SPECIAL OFFER TEXAS XM11 Teletext Decoder New & Tested at reduced price. **£40.00** p.p. **£1.60**.
 TELETEXT 23 Button De-Luxe Handset with 5 yds Cable. **£6.80** p.p. **£1.20**.
 XM11 Stab. Power Supply. **£3.80** p.p. **£1.20**.
 CROSS HATCH UNIT KIT, Aerial Input type, incl. T.V. sync. and UHF Modulator, Battery Operated, also gives Peak White & Black Levels, can be used for any set. **£12.00** p.p. **80p**. (Alum. Case **£2.55**, De Luxe Case **£6.80** p.p. **£1.40**.)
 ADDITIONAL GREY SCALE Kit **£2.90** p.p. **45p**.
 UHF SIGNAL STRENGTH METER KIT **£20.00** (VHF version also available). Alum. Case **£2.55**. De Luxe Case **£7.40** p.p. **£1.80**.
 CRT TESTER & REACTIVATOR PROJECT KIT For Colour & Mono **£28.00** p.p. **£2.80**.
 BUSH Z718 BC6100 series IF Panel **£5.00** p.p. **90p**.
 BUSH A816 IF Panel (Surplus) **£1.65** p.p. **90p**.
 DECCA 80 Series IF, Frame, T.B. **£5.00** p.p. **£1.40**.
 GEC 2040 Convergence Panels, Decoder Panels, **£2.50** p.p. **£1.80**.
 GEC 2040 IF Panels **£2.80** p.p. **£1.60**.
 GEC 2110 Convergence Panels **£5.00** p.p. **£1.80**.
 GEC "20AX" Series Switch Mode Power Supply **£5.00** p.p. **£1.80**.
 PYE 691-7 CDA Panels. Makers tested stock. **£6.00** p.p. **£1.45**.
 PYE 725 T.B. Unit. Makers tested stock. **£20.00** p.p. **£2.80**.
 THORN TX9 Panels ex factory for small spares. Includes I.Cs & Semiconductors etc. **£5.00** p.p. **£2.00**.
 THORN TX9 Panels salvaged ex factory for spares incl. LOPT & Mains Transformers. **£10.00** p.p. **£2.80**.
 THORN TX9 Panels ex factory salvaged complete cond. **£20.00** p.p. **£2.80**.
 THORN TX10 T.B. Panels salvaged ex factory. **£15.00** p.p. **£3.00**.
 THORN TX10 IF/Decoder Panels salvaged ex factory. **£15.00** p.p. **£2.00**.
 THORN 3000 Line T.B. PCB, Power PCB **£5.00** each p.p. **£1.30**.
 THORN 8000/8500 IF/Decoder Panels salvaged **£3.20** p.p. **£1.80**.
 THORN 8000/8500 Frame T.B. Panels salvaged/spares **£2.50** p.p. **£1.40**.
 THORN 9000 Series Control & Receiver Unit **£6.80** p.p. **£1.80**.
 THORN 9000 IF/Decoder Panels Salvaged. **£5.00** p.p. **£1.60**.
 PHILIPS G8/G9 IF/Decoder Panels for small spares **£1.50** p.p. **£1.40**.
 G8 Decoder Panels salvaged **£3.80**. Panels for spares **£1.75** p.p. **£1.40**.
 G9 Scan Panel. Basic PCB in Fibreglass **£14.50** p.p. **£1.80**.
 G11 Frame Panels, IF Panels **£18.00** each p.p. **£2.00**.
 GRUNDIG 8630 Series Varicap Tuners **£5.00** p.p. **£1.00**.
 VARICAP. U321, U322, ELC1043/06, ELC1043/5 **£6.80** p.p. **80p**. G.I. type (equiv. 1043/05) **£3.50** p.p. **80p**. Makers Varicap Controls PYE CT200 4PSN **£7.50**, BUSH 4PSN **£4.80**, DECCA 4PSN **£5.80** p.p. **80p**.
 SPECIAL OFFER ELEVEN POSITION Varicap Control Unit UHF/VHF **£1.80** p.p. **£1.00**.
 BUSH "TOUCH TUNE" Varicap Control Z179, Z718 types **£3.80** p.p. **95p**.
 VARICAP UHF-VHF ELC2000S, ELC2060 **£9.80**, BUSH **£7.80** p.p. **90p**.
 VARICAP VHF MULLARD ELC 1042, PHILIPS, **£6.90** p.p. **80p**.
 UHF/625 TUNERS, many different types in stock. DECCA Bradford 5 position, MULLARD 4 position **£2.50**, JAP Rotary **£4.80** p.p. **£1.80**.
 TV SOUND IF Panels **£6.80** p.p. **£1.00**.
 LOPT TESTER, Service Dept approved **£15.50** p.p. **£1.20**.
 LOPTS New and guar. P/P Mono **£1.35**, Colour **£1.50**, Bobbins **80p**.
- | | | | |
|------------------------------------|-------|-------------------------------------|--------|
| BUSH 161 to 186 (twin panel)..... | £5.90 | R.B.M. A823 | £4.90 |
| BUSH, MURPHY 774 series | £8.50 | R.B.M. Z179 | £9.80 |
| BUSH, MURPHY A816 series | £8.50 | R.B.M. T20, T22 | £9.80 |
| FERG., HMV, MARCONI, ULTRA | | R.B.M. T20, T22 Bobbin | £5.60 |
| 950, 1400, 1500, 1580, 1590, 1591 | £5.90 | DECCA Bradford (state Mod No) | £8.80 |
| THORN 1600, 1615, 1690, 1691 | £9.15 | DECCA 80, 100 | £8.80 |
| GEC 2000 to 2038 series | £6.80 | GEC 2028, 2040, 2100 | £5.80 |
| GEC series 1 & 2 | £8.00 | GEC 2110 series | £10.60 |
| INDEST 20/24EGB | £7.65 | ITT CVC 5 to 9, CVC20 | £9.80 |
| ITT/KB VC200, 300 | £7.65 | ITT CVC25, CVC30 series | £8.80 |
| MURPHY 1910 to 2414 (twin panel) | £5.90 | PYE 691-697 | £10.00 |
| PHILIPS 170, 210, 300 series | £7.65 | PYE 713, 715 | £6.80 |
| PYE, INVICTA, EKCO, FERR. | | PYE 725 (90°) 731 to 741 | £9.20 |
| 368, 169, 569, 769 series | £7.65 | PHILIPS G8 | £8.80 |
| SPECIAL OFFER | | PHILIPS G9 | £10.20 |
| DECCA 20/24, 1700, 2000, 2401 ... | £3.80 | PHILIPS 570, 571 | £6.80 |
| GEC 2114J/Junior Fineline | £2.80 | THORN 3000/3500 SCAN, EHT ... | £6.90 |
| PYE 40, 67 | £1.75 | THORN 8000/8500/8800 | £12.90 |
| KB VC ELEVEN (003) | £1.75 | THORN 9000 to 9600 | £12.90 |
| KB VCI | £2.80 | THORN 9800 | £19.05 |

OTHERS AVAILABLE, PRICES ON REQUEST. ALSO LOPTS.
 TRIPLERS Full range available. Mono & Colour.
 Special Offer: Thorn 8000 (2 lead) EHT Tray **£2.80** p.p. **80p**.
 TRANSDUCTORS suitable for G8, A823, Bradford etc. **£1.50** p.p. **60p**.
 6.3V CRT Boost Transformers for Colour & Mono **£5.00** p.p. **£1.20**.
 CALLERS WELCOME AT SHOP PREMISES
 THOUSANDS OF ADDITIONAL ITEMS, ENQUIRIES INVITED
 LARGE SELECTION TESTED COLOUR PANELS POPULAR MODELS
 Telephone 01-794 8751, 794 7346


MANOR SUPPLIES

172 WEST END LANE, LONDON, N.W.6.

NEAR: W. Hampstead Tube Stn. (Jubilee) Buses 28, 159, C11 pass door
 W. Hampstead British Rail Stns. (Richmond, Broad St.) (St. Pancras, Bedford)
 W. Hampstead (Brit. Rail) access from all over Greater London.

Mail Order: 64 GOLDERS MANOR DRIVE, LONDON N.W.11.

PLEASE ADD VAT 15% TO ALL PRICES

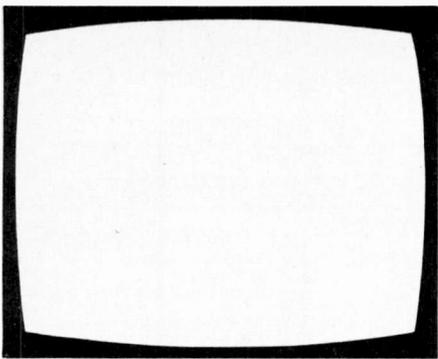

TELEVISION

September
1984

Vol. 34, No. 11
Issue 407

COPYRIGHT

©IPC Magazines Limited, 1984. Copyright in all drawings, photographs and articles published in *Television* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Television* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

CORRESPONDENCE

All correspondence regarding advertisements should be addressed to the Advertisement Manager, "Television", King's Reach Tower, Stamford Street, London SE1 9LS. Editorial correspondence should be addressed to "Television", IPC Magazines Ltd., King's Reach Tower, Stamford Street, London SE1 9LS.

SUBSCRIPTIONS

An annual subscription costs £11 in the UK, £12 overseas (by surface mail). Send orders with payment to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex, RH16 3DH.

BINDERS AND INDEXES

Binders (£4.50) and Indexes (45p) can be supplied by the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. Prices include postage and VAT. In the case of overseas orders, add 60p.

BACK NUMBERS

Some back issues are available from the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF at £1.20p inclusive of postage and packing.

QUERIES

We regret that we cannot answer technical queries over the telephone nor supply service sheets. We will endeavour to assist readers who have queries relating to articles published in *Television*, but we cannot offer advice on modifications to our published designs nor comment on alternative ways of using them. All correspondents expecting a reply should enclose a stamped addressed envelope. Requests for advice on dealing with servicing problems should be directed to our Queries Service. For details see our regular feature "Service Bureau". Send to the address given above (see "correspondence").

this month

- 585 Leader**
- 586 The Salora Ipsalo-2 Circuit**
Salora's second Ipsalo (integrated power supply and line output) circuit makes use of a pair of transistors to perform the chopper action.
- 587 CCTV Commentary** *Andy Denham*
Notes on Frowds' cameras and faults experienced with Hitachi monochrome monitors.
- 588 Tiny Tim's Dilemma** *Les Lawry-Johns*
Thirty years of writing for *Television*, and a little longer than that dealing with errant TVs, and what has Tim to show? Piles of bills and not much in the bank.
- 591 TV Fault Finding**
Notes on TV faults from Mick Dutton, Jim Rainey, Tony Thompson, Robin D. Smith and Malcolm Burrell.
- 592 Servicing the Grundig 2 x 4 Super, Part 2** *Mike Phelan*
Operation of the DTF and servo circuits and how to tackle faults in this part of the machine.
- 596 Cable 84** *Harold Peters*
A visit to Cable 84, the second annual conference and exhibition for the cable and satellite TV industry.
- 596 Teletopics**
News, comment and developments.
- 598 VCR Servo Systems, Part 1** *Eugene Trundle*
A surprisingly wide variety of servo arrangements have been used in domestic VCRs. The purpose of this article is to consider the approaches adopted by different designers and see how they achieve the required results.
- 602 TV Test Pattern Generator, Part 4** *Tony Jenkins, G8TBF*
This concluding instalment covers modifications, setting up and constructional notes.
- 606 VCR Clinic**
Notes on video faults from Mike Phelan, Steve Beeching, T.Eng. (C.E.I.), Peter Dolman, Tony Thompson, Malcolm George, Ian Hutton, Les Grogan, Hugh Allison, John Coombes and Peter Blundell, Tech. (C.E.I.).
- 608 Servicing the Grundig GSC100 Chassis** *Denis G. Mott*
A detailed run-down on faults experienced with this second-generation thyristor line timebase chassis.
- 611 Letters**
- 612 Servicing the Sony KV2000UB, Part 2** *David Botto*
The timebase panel and the signals circuits.
- 613 Next Month in Television**
- 614 Long-distance Television** *Roger Bunney*
Reports on DX conditions and reception. Also interference problems and details of a 12GHz satellite receiver developed by Chris Wilson.
- 617 Service Bureau**
- 618 Test Case 261**

OUR NEXT ISSUE DATED OCTOBER WILL
BE PUBLISHED ON SEPTEMBER 19

P. V. TUBES

HAVE MOVED

Just phone your order through, we do the rest.



Telephone: Accrington (0254) 36521
Accrington (0254) 32611
Telex: 635562 Griffin G (For P.V.)

SUPPLIERS OF TELEVISION COMPONENTS

104 ABBEY STREET, ACCRINGTON, LANCBS BB5 1EE.
TRADE COUNTER OPEN MON-FRI 9 a.m.-5 p.m. SAT 9.30 a.m.-5 p.m. TRADE COUNTER CLOSED WEDNESDAY p.m.

| VARICAP TUNERS | | SWITCHES & ACCESS. | | DID YOU KNOW WE'VE GOT | | PHILIPS KT3 SPECIFICS | | SPECIFIC COMPONENTS | |
|---|--------------|-------------------------------------|-------|-----------------------------------|--------|--------------------------------|-------|--|------------|
| ELC1043-05 | 8.40 | On/off gen. purpose 4A | 75 | LOTS OF NEW THINGS! | | KT3 postistor | 1.80 | Philips G8 knobs sm/lg | 50 |
| ELC1043-06 | 8.40 | G8 on/off | 1.38 | Decca speaker 16R | 4.50 | Mains electrolytic 225/25 380V | 2.90 | 90° transistor | 2.50 |
| ELC2003 | 18.80 | G11 on/off | 1.58 | 8R | 3.75 | Selector unit Mod. 933 | 13.42 | Thorn 1591 speakers sm | 4.10 |
| Philips G8/G9 | 10.50 | G11 on/off remote | 1.58 | B+K tube bases Dynascan | | On/off switch Mod. 933 | 3.20 | lg | 4.50 |
| Philips G11 (U321) | 8.50 | Gen. purpose rotary | 66 | No. 3 | 9.50 | Tripler | 10.85 | Thorn 1500 controls | 59 |
| U322 | 7.20 | Thorn Tx 9/10 | 1.06 | No. 6 | 11.08 | Luminance chroma panel | 24.00 | 390K frame 470K line contrast 1K5 | each |
| U341 | 9.50 | GEC 2040 | 98 | No. 8 | 10.08 | 2023 IF module | 14.98 | Focus control Thorn/GEC | 1.83 |
| Thorn 1691 | 17.90 | Thorn 1501 push | 2.90 | 5 1/2" floppy disc s/s s/d | | U321 IF module | 13.80 | Thorn 9000 focus unit | 6.95 |
| Rank T20 | 13.00 | Rank tuner buttons | | 15R fused res. G9 | | R.G.B. panel | 10.30 | Thorn 8500 focus unit | 4.75 |
| PUSH BUTTON ASS. | | 1 1/2" x 1/2", 2" x 1/2", 2" x 3/4" | 38 | G11 line lin coil | 2.95 | Sound panel | 8.50 | Thorn Tx10 focus cont. | 9.00 |
| Decca 4 way | 6.88 | Rank drive cams | 15 | G11 pot G2 R.G.B. | 5.30 | Power panel | 10.50 | Decca bridge trans. | 1.97 |
| 6 way | 7.50 | GEC 2110 tuner neons | 14 | C18 computer cass. | | Mains input panel | 14.30 | Decca 30 width cont. | 50 |
| GEC 2110 6 way | 7.98 | Thorn 3500 A1 beam | 70 | C12 computer cass. | | Line sync panel | 10.20 | Decca 2M2 HT cont. | 50 |
| GEC Slim 6 way | 6.50 | GEC 2110 A1 cont. R/B/G | 58 | 5 1/2" floppy disc s/s s/d | 1.61 | Mark II chroma panel | 16.50 | Rank T20 focus cont. | 2.20 |
| GEC/ITT/PYE 7 way | 14.50 | ITT CVC5 on/off | 1.24 | G11 line lin coil | 2.95 | Sound module | 6.50 | Pye 731 HF choke | 6.50 |
| Pye 4 way (713/15) | 9.00 | EAGLE MULTIMETERS | | G11 line sync panel | 54.00 | LOPT | 3.50 | Delay lines DL20, OL60, DL700 | 2.20 |
| Pye 6 way (207/715) | 16.00 | KEW 7N | 5.25 | G11 pot G2 R.G.B. | 5.30 | Focus unit | 3.50 | CRT tube base | 7.20 |
| Pye 697 repair kit | 9.00 | KEW 14 | 7.95 | G11 line sync panel | 54.00 | K30 LOPT | 17.60 | EHT final anode cap | 5.30 |
| Pye 725-735 | 11.00 | KEW 20 | 14.80 | G11 power panel | 37.50 | K30 focus unit | 2.90 | 6.3V CRT boost trans. | 6.80 |
| Philips G8 (early) | 13.50 | EM5 | 11.95 | G11 timebase panel | 37.50 | K30 EHT lead | 5.90 | Focus rod | 1.25 |
| Philips G8 (late) | 13.90 | EM20A | 15.95 | G11 bridge trans. | 97 | Selector unit 1002 (early) | 11.20 | Focus holder | 2.00 |
| Rank A823 | 10.75 | EM10 | 13.95 | G11 EW correc. coil | 1.95 | TMS 1000 panel 1234 | 13.00 | AFC unit G8 | 8.82 |
| Rank T20A | 9.75 | EM50 | 17.95 | G11 final anode lead | 1.50 | Euro decoder panel 1234 | 46.00 | IF gain module | 9.00 |
| Hitachi 4 way | 10.75 | MM50 | 27.95 | G11 focus unit | 5.80 | Power supply 1234 | 23.50 | C.D.A. panel | 20.00 |
| Philips G11 unit | 23.00 | MM100 | 39.95 | G11 39R 3W resistor | 60 | A1 gun switches | 7.00 | G8 rear conv. panel | 23.00 |
| Philips KT3 | 14.50 | MM100 | 39.95 | G11 RGB 10G diodes | 50 | On/off switch | 2.60 | SPARK GAPS | |
| Philips KT30 | 10.30 | MM100 | 39.95 | Labgear CM7091 UHF/VHF colour bar | 116.00 | Selector unit 1002 (late) | 9.90 | Decca 100 | 52 |
| ITT CVC 8/9 (mod) | 12.00 | MM150 | 74.95 | Televerta up converta | 37.20 | Hand set 1201 | 14.50 | 0.75 pf | 1.50 |
| ITT 6 way with VCR | 8.90 | T1206 | 6.95 | | | Hand set 1234 | 14.50 | 0.01 pf | 32 |
| Thorn 8800 6 way round | 7.50 | MMC100 | 17.95 | | | Diode ZTX 33B | 2.20 | | |
| Thorn 9000 unit | 10.50 | | | | | DL 20 delay line | 2.20 | | |
| Thorn 9000 switchback | 2.90 | | | | | | | | |
| SERVICE AIDS | | ANTEX SOLDERING EQUIPMENT | | SUNDAY EQUIPMENT | | Solder Mop Stnd. | | Specific Video Leads (please state models) | |
| SERVISOL Freeze-It | 1.02 | C15W Iron 240V | 4.41 | Test Lead Set | 4.20 | Sidecutters sm. | 1.20 | 74 | 4.25 |
| SUPER SERVISOL | 82 | C240 Element | 1.80 | Degaussing Coil Stick | 17.00 | Long Nose Pliers | 1.20 | Universal Video Lead Kit | 6.00 |
| SERVISOL Foam Cleanser | 89 | Bits 102 | 90 | Signal Injector | 4.00 | SM Torch | 42 | EHT Cable | per mtr 25 |
| SERVISOL Plastics Seal | 1.00 | 106 | 90 | Elect. Circuit Tester | 1.50 | Quick Set Adhesive | 75 | | |
| SERVISOL Silicone Grease | 1.08 | 821 | 90 | 5A Choc Bloc (12) | 40 | Sm. Neon Screwdriver | 40 | PLUGS | |
| SERVISOL Tubes Silicone Grease | 1.84 | CS17W Iron 240V | 4.41 | Fuse Wire 5A, 15A, 30A | 05 | Lg. Neon Screwdriver | 65 | 15 | 12 |
| SERVISOL Aero Klene | 84 | CS240 Element | 2.25 | 4-way 13A Mains Conn. | 5.00 | Min. Screwdrivers | 15 | 75 | 22 |
| SERVISOL Aero Duster | 1.10 | Bits 1100 | 90 | Safe Block (mains) | 7.00 | Artistic Foam (12" sheet) | 1.18 | 75 | 22 |
| SERVISOL Excel Polish | 88 | Bits 1101 | 90 | 13A Plug Top (box 10) | 4.80 | I.C. Inserters | 1.18 | 180° | 4 pin |
| SERVISOL Video Head Cleanser | 82 | 1106 | 90 | Portable Oscilloscope | 155.00 | | | 180° | 5 pin |
| Super 40 | 1.50 | XS25W Iron 240V | 4.59 | Probes (x10) | 10.90 | | | std | 5 pin |
| Fire Extinguisher 640G | 2.50 | XS240 Element | 2.25 | Probes (x1) | 10.90 | | | Car Aerial Plug | 18 |
| Heat Sink Compound 25G | 1.08 | Bits 50 | 90 | KHP30 Meas. Probe 30kV | 172.00 | | | 2.5mm Jack Plug | 14 |
| Silicone Rubber Tube 110G | 2.98 | 51 | 90 | Bell Wire (100m) | 32.00 | | | 3.5mm Jack Plug | 14 |
| Solda Mop standard reel | 74 | Temp. Controlled | 10.50 | Mains Cable (circular 100m) | 10.75 | | | Stand Jack Plug | 20 |
| ELECTROLUBE PRODUCTS | | 30W Iron CSTC | 10.50 | (2 core) | 13.25 | | | STEREO Jack Plug | 36 |
| Electrolube Adhesive | 82 | 40W Iron XSTC | 10.50 | (3 core) | 99.00 | | | Coax Plugs | each 1.80 |
| Electro-Mech lubricant | 1.48 | Unit for above TCSU1 | 32.64 | Factory recon. Avo meters | 13.25 | | | PL259 | 40 |
| Elect. cleaning solvent | 1.82 | Stand | 2.00 | Avo Batteries | 2.20 | | | Reducers for PL259 | 16 |
| Freezer | 1.49 | MLXS Auto Repair Kit | 6.30 | Vero Board | 2.59 | | | Line Connectors | 16 |
| Foam cleanser | 1.12 | WELLER | | Isolating trans. 500VA 240V | 20.40 | | | | |
| Heat transfer compound | 1.14 | Heat gun | 12.00 | Solder 500g | 7.00 | | | | |
| Silicone compound | 1.94 | Heat gun tips (pair) | 57 | D.I.Y. Solder | 6.50 | | | | |
| Special contact fluid (Snorkell) | 3.20 | 3/16" Iron tips 25W (MT5) | 57 | Solder Sucker | 81 | | | | |
| Permagard | 1.52 | | | Nozzles | | | | | |
| Elec. mech. lubricant pen | 74 | | | | | | | | |
| VIDEO | | | | | | | | | |
| Video care kits | 3.50 | | | | | | | | |
| VHS E30 video tape | 3.06 | | | | | | | | |
| VHS E60 video tape | 4.00 | | | | | | | | |
| Scotch E120 video tape | 5.00 | | | | | | | | |
| E180 video tape | 4.50 | | | | | | | | |
| Beta L500 video tape | 4.90 | | | | | | | | |
| Beta L750 video tape | 5.80 | | | | | | | | |
| Philips VCC 240 | 6.20 | | | | | | | | |
| Philips VCC 360 | 8.30 | | | | | | | | |
| Philips VCC 480 | 10.21 | | | | | | | | |
| Philips LVC 1700 | 15.10 | | | | | | | | |
| VIDEO HEADS | | | | | | | | | |
| 3HSS VHS | 32.50 | | | | | | | | |
| 4HSS VHS | 32.80 | | | | | | | | |
| PS3B Beta/Sony | 42.00 | | | | | | | | |
| VIDEO RECORDER HEADS | | | | | | | | | |
| Philips V2000 | 55.00 | | | | | | | | |
| Philips 1700 | 55.00 | | | | | | | | |
| Video lamps | 1.30 | | | | | | | | |
| Video lamp holders | 3.30 | | | | | | | | |
| VCR DRIVE BELTS | | | | | | | | | |
| 22.5 mm | 80 | | | | | | | | |
| 50.5 mm | 82 | | | | | | | | |
| 52.5 mm | 84 | | | | | | | | |
| 71 mm | 86 | | | | | | | | |
| 80 mm | 88 | | | | | | | | |
| 100 mm | 1.54 | | | | | | | | |
| 109 mm | 1.56 | | | | | | | | |
| 127 mm | 1.60 | | | | | | | | |
| 147 mm | 2.10 | | | | | | | | |
| 161.5 mm | 2.14 | | | | | | | | |
| Video head cleaner | 90 | | | | | | | | |
| AUDIO HEADS AND MOTORS | | | | | | | | | |
| Mono record/playback | 4.32 | | | | | | | | |
| Stereo playback | 4.79 | | | | | | | | |
| Stereo record/playback | 4.99 | | | | | | | | |
| Stereo record/playback (Dolby) | 6.90 | | | | | | | | |
| Stereo record/playback (glass face) | 10.95 | | | | | | | | |
| Mono/stereo erase | 2.25 | | | | | | | | |
| ELECTRONIC/rotation clockwise motors | | | | | | | | | |
| 6V MD6515 | 4.95 | | | | | | | | |
| 9V MD9516 | 4.95 | | | | | | | | |
| 12V MD12517 | 4.95 | | | | | | | | |
| STATIONERY | | | | | | | | | |
| Service Call Pad (100) | 1.20 | | | | | | | | |
| Repair Ticket (100) | 3.90 | | | | | | | | |
| Job Card (100) | 2.50 | | | | | | | | |
| Rental Payment Card (50) | 3.50 | | | | | | | | |
| Rental Agreements (100) | 3.50 | | | | | | | | |
| H.P. Agreements (100) | 3.50 | | | | | | | | |
| Maintenance Agreement (100) | 3.50 | | | | | | | | |
| LABGEAR | | | | | | | | | |
| CM7061 Power Unit 12V | 10.70 | | | | | | | | |
| CM7062 Reg. Power Unit 12V | 11.67 | | | | | | | | |
| CM7060 MHA 10db 12V W/B | 9.39 | | | | | | | | |
| CM7065 VHF/UHF MHA W/B 12V 13.66 | | | | | | | | | |
| CM7067 UHF 12V MHA (Specify A-B or C/D) | 10.21 | | | | | | | | |
| CM7068 UHF 12V MHA High Gain (Specify A-B or C/D) | 15.19 | | | | | | | | |
| CM7053 Behind Set UHF Amp. (Mains) | 12.13 | | | | | | | | |
| CM7054 Behind Set UHF Amp. (Battery e.g. Caravans) | 9.92 | | | | | | | | |
| CM7043 Second Set Amp. UHF | 11.54 | | | | | | | | |
| CM7093 Behind Set UHF Amp. 3 Sets | 14.54 | | | | | | | | |
| CM7063 Dist. Amp. VHF/UHF 17db/output 12V | 20.10 | | | | | | | | |
| CM7108 VHF/UHF 8+1 Dist. Amp. | 41.20 | | | | | | | | |
| CM9700 27mhz CB Suppress. | 3.86 | | | | | | | | |
| CM6011 Outdoor Splitter (2 way) W/B | 7.46 | | | | | | | | |
| CM9003 Flush Single Outlet | 1.40 | | | | | | | | |
| CM9010 Flush Twin Outlet | 1.86 | | | | | | | | |
| CM9034 UHF Group Filters with DC Through Pass (state A/B/CD) | 6.97 | | | | | | | | |
| CM6006 6 Way Passive Splitter | 10.97 | | | | | | | | |
| CM7042 TV Games Combin. | 2.68 | | | | | | | | |
| CM9009 Flush TV/FM Outlet | 2.90 | | | | | | | | |
| CM7091 Col. Bar Gen. | 116.00 | | | | | | | | |
| OFFICIAL ORDERS ACCEPTED FROM SCHOOLS, LOCAL AUTHORITIES ETC. | | | | | | | | | |
| WE HAVE A FULL RANGE OF AERIALS AND ACCESSORIES FROM TRADE COUNTER AERIAL EQUIPMENT | | | | | | | | | |
| Plastic Tape | 50 | | | | | | | | |
| F.M. Plugs | 25 | | | | | | | | |
| Set Top Aerial | 2.30 | | | | | | | | |
| Loop Aerial | 1.00 | | | | | | | | |
| Master Amp/Power Unit WB | 18.00 | | | | | | | | |
| Aerial Isolator Kit | 2.08 | | | | | | | | |
| Attenuator 6db, 12db, 18db | 1.80 | | | | | | | | |
| 27MHz Filter 50db | 2.10 | | | | | | | | |
| Cable Clips 7mm | per 100 1.18 | | | | | | | | |
| Single Outlets | 80 | | | | | | | | |
| Surface Splitter | 1.70 | | | | | | | | |
| A Splitter | 15.00 | | | | | | | | |
| ICOM Coax | 7.00 | | | | | | | | |
| Coax Plugs | per 10 1.80 | | | | | | | | |
| 1" U Bolts | 30 | | | | | | | | |

T.T.L. 74LS SERIES

| | | | | | | | | | | | |
|--------|----|---------|----|---------|------|---------|------|---------|------|-------|----|
| 74LS00 | 58 | 74LS37 | 35 | 74LS92 | 65 | 74LS160 | 90 | 74LS251 | 65 | 7805 | 78 |
| 74LS02 | 58 | 74LS38 | 35 | 74LS93 | 60 | 74LS161 | 85 | 74LS253 | 95 | 7806 | 78 |
| 74LS03 | 58 | 74LS40 | 35 | 74LS107 | 60 | 74LS162 | 4.04 | 74LS257 | 1.20 | 7807 | 78 |
| 74LS04 | 58 | 74LS42 | 60 | 74LS109 | 58 | 74LS163 | 85 | 74LS258 | 95 | 7808 | 78 |
| 74LS05 | 58 | 74LS47 | 85 | 74LS112 | 50 | 74LS184 | 85 | 74LS259 | 1.70 | 7812 | 78 |
| 74LS08 | 58 | 74LS48 | 63 | 74LS113 | 44 | 74LS185 | 1.50 | 74LS273 | 1.90 | 7815 | 78 |
| 74LS09 | 58 | 74LS49 | 33 | 74LS114 | 70 | 74LS174 | 85 | 74LS283 | 1.30 | 7818 | 78 |
| 74LS10 | 58 | 74LS51 | 33 | 74LS123 | 80 | 74LS175 | 85 | 74LS293 | 1.20 | 7824 | 78 |
| 74LS11 | 58 | 74LS54 | 43 | 74LS125 | 85 | 74LS191 | 1.82 | 74LS352 | 1.40 | 78L05 | 68 |
| 74LS13 | 37 | 74LS55 | 60 | 74LS126 | 60 | 74LS192 | 1.30 | 74LS353 | 1.40 | 78L08 | 68 |
| 74LS14 | 48 | 74LS73 | 60 | 74LS132 | 83 | 74LS193 | 1.30 | 74LS365 | 75 | 78L12 | 68 |
| 74LS15 | 33 | 74LS74 | 65 | 74LS138 | 83 | 74LS194 | 75 | 74LS366 | 82 | 7905 | 98 |
| 74LS20 | 36 | 74LS75 | 65 | 74LS139 | 85 | 74LS197 | 95 | 74LS367 | 1.85 | 7906 | 98 |
| 74LS21 | 36 | 74LS76 | 65 | 74LS151 | 85 | 74LS240 | 2.20 | 74LS368 | 85 | 7908 | 98 |
| 74LS22 | 36 | 74LS78 | 65 | 74LS153 | 85 | 74LS241 | 2.20 | 74LS373 | 1.40 | 7912 | 98 |
| 74LS26 | 44 | 74LS93A | 89 | 74LS155 | 85 | 74LS242 | 2.20 | 74LS374 | 1.55 | 7915 | 98 |
| 74LS27 | 35 | 74LS96 | 98 | 74LS156 | 1.02 | 74LS243 | 2.20 | 74LS393 | 1.20 | 7918 | 98 |
| 74LS30 | 35 | 74LS95 | 98 | 74LS157 | 78 | 74LS244 | 2.20 | 74LS670 | 1.78 | 7924 | 98 |
| 74LS32 | 35 | 74LS90 | 60 | 74LS158 | 85 | 74LS245 | 2.30 | | | 79L05 | 72 |

VOLTAGE REG.

P. V. TUBES TEL: 0254 36521/32611
104 ABBEY STREET, ACCRINGTON

MAINS DROPPERS

| | | | | | | | | | | | |
|--------------------------------|------|-------|------|--------|-------|--------|------|----------|------|----------|------|
| DECCA 20 | 2.48 | 30FL2 | 1.70 | EF183 | 99 | PCF800 | 1.38 | PL508 | 2.90 | MISTERS | |
| DECCA 27R/47R | 1.40 | DY802 | 98 | EF184 | 1.09 | PCF801 | 1.13 | PL509/19 | | VA1104 | 75 |
| DECCA 56R/68R | 1.40 | DY867 | 86 | EH90 | 1.82 | PCF802 | 1.12 | | 5.30 | VA1040 | 75 |
| R.B.M. A823 56R/68R | 9.40 | ECC81 | 1.08 | EL34 | 3.50 | PCF805 | 1.80 | PV88 | 81 | VA8650 | 55 |
| R.B.M. 161 | 82 | ECC82 | 98 | EL84 | 1.05 | PCF806 | 1.30 | PV500A | 2.30 | VA1039 | 35 |
| GEC 2000/2018 | 70 | ECC83 | 1.07 | EY86/7 | 68 | PCF808 | 1.83 | PV800/1 | 69 | GEC Dual | |
| GEC 27840 | 64 | ECC84 | 80 | EY500A | 1.50 | PCH200 | 1.45 | UCH81 | 2.25 | Posistor | 1.68 |
| PYE 713/15 3R5/15/45R | 1.80 | ECC85 | 98 | EZ80/1 | 56 | PCL82 | 1.20 | UCL83 | 1.82 | GEC | Dual |
| PYE 725/31 3R0/56R/27R | 1.84 | ECC88 | 1.35 | GY501 | 1.45 | PCL84 | 1.20 | UY65 | 1.35 | 2040 | |
| PYE 725 56R/27R | 1.04 | ECC80 | 80 | GZ34 | 3.50 | PCF86 | 92 | PL802T | 4.00 | (CK1) | 1.98 |
| PHILIPS 210/5050 30R/125R/2K85 | 1.75 | ECC82 | 86 | KT66 | 8.50 | PCL805 | 1.09 | 40K06 | 5.30 | | |
| | | ECH81 | 1.60 | KT88 | 12.00 | PD500 | 2.93 | 21L08 | 3.00 | | |
| | | ECH84 | 1.66 | PC92 | 3.00 | PFL200 | 1.86 | 17DW4A | 1.60 | | |
| | | ECL80 | 84 | PC97 | 1.85 | PL36 | 1.87 | 3AT2B | 5.90 | | |
| | | ECL82 | 1.30 | PC85 | 85 | PL81 | 94 | 12B7A | 3.75 | | |
| | | ECL86 | 1.99 | PC805 | 1.40 | PL83 | 1.43 | 12HG7 | 3.20 | | |
| | | EF86 | 1.96 | PCF200 | 1.35 | PL504 | 84 | | | | |

'4000 B' SERIES CMOS

| | | | | | | | | | | | |
|-------|----|-------|----|-------|----|-------|------|-------|------|--------------|----|
| 4001B | 21 | 4032B | 39 | 4069B | 22 | 4511B | 76 | 4539B | 77 | 79L24 | 72 |
| 4002B | 21 | 4033B | 64 | 4070B | 22 | 4512B | 72 | 4541B | 96 | I.C. SOCKETS | |
| 4003B | 21 | 4034B | 80 | 4071B | 22 | 4513B | 1.68 | 4543B | 1.12 | OIL to OIL | |
| 4004B | 72 | 4035B | 98 | 4072B | 22 | 4514B | 1.88 | 4545B | 1.96 | 8 way | 22 |
| 4005B | 72 | 4036B | 98 | 4073B | 22 | 4515B | 1.88 | 4547B | 2.40 | 14 way | 29 |
| 4006B | 72 | 4037B | 98 | 4074B | 22 | 4516B | 1.76 | 4549B | 1.20 | 16 way | 32 |
| 4007B | 72 | 4038B | 98 | 4075B | 22 | 4517B | 1.76 | 4551B | 1.20 | 18 way | 32 |
| 4008B | 72 | 4039B | 98 | 4076B | 22 | 4518B | 1.76 | 4553B | 1.20 | 20 way | 32 |
| 4009B | 72 | 4040B | 98 | 4077B | 22 | 4519B | 1.76 | 4555B | 1.20 | 22 way | 32 |
| 4010B | 72 | 4041B | 98 | 4078B | 22 | 4520B | 1.76 | 4557B | 1.20 | 24 way | 34 |
| 4011B | 72 | 4042B | 98 | 4079B | 22 | 4521B | 1.88 | 4559B | 3.60 | 38 way | 45 |
| 4012B | 72 | 4043B | 98 | 4080B | 22 | 4522B | 1.88 | 4561B | 1.84 | 40 way | 84 |
| 4013B | 72 | 4044B | 98 | 4081B | 22 | 4523B | 1.88 | 4563B | 1.84 | | |
| 4014B | 74 | 4045B | 96 | 4082B | 22 | 4524B | 1.88 | 4565B | 1.84 | | |
| 4015B | 76 | 4046B | 96 | 4083B | 22 | 4525B | 1.88 | 4567B | 1.84 | | |
| 4016B | 76 | 4047B | 96 | 4084B | 22 | 4526B | 1.88 | 4569B | 1.84 | | |
| 4017B | 66 | 4048B | 96 | 4085B | 22 | 4527B | 1.88 | 4571B | 1.84 | | |
| 4018B | 66 | 4049B | 96 | 4086B | 22 | 4528B | 1.88 | 4573B | 1.84 | | |
| 4019B | 66 | 4050B | 96 | 4087B | 22 | 4529B | 1.88 | 4575B | 1.84 | | |
| 4020B | 66 | 4051B | 96 | 4088B | 22 | 4530B | 1.88 | 4577B | 1.84 | | |
| 4021B | 66 | 4052B | 96 | 4089B | 22 | 4531B | 1.88 | 4579B | 1.84 | | |
| 4022B | 66 | 4053B | 96 | 4090B | 22 | 4532B | 1.88 | 4581B | 1.84 | | |
| 4023B | 66 | 4054B | 96 | 4091B | 22 | 4533B | 1.88 | 4583B | 1.84 | | |
| 4024B | 66 | 4055B | 96 | 4092B | 22 | 4534B | 1.88 | 4585B | 1.84 | | |
| 4025B | 66 | 4056B | 96 | 4093B | 22 | 4535B | 1.88 | 4587B | 1.84 | | |
| 4026B | 66 | 4057B | 96 | 4094B | 22 | 4536B | 1.88 | 4589B | 1.84 | | |
| 4027B | 66 | 4058B | 96 | 4095B | 22 | 4537B | 1.88 | 4591B | 1.84 | | |
| 4028B | 66 | 4059B | 96 | 4096B | 22 | 4538B | 1.88 | 4593B | 1.84 | | |
| 4029B | 66 | 4060B | 96 | 4097B | 22 | 4539B | 1.88 | 4595B | 1.84 | | |
| 4030B | 66 | 4061B | 96 | 4098B | 22 | 4540B | 1.88 | 4597B | 1.84 | | |

LINE OUTPUT TRANS.

| | | | |
|----------------------|--------|-----------------------------------|-------|
| R.B.M. T20A | 13.95 | THORN 950 Mk II | 4.25 |
| R.B.M. A774 Mono | 11.74 | THORN 1400 3 Stack | 5.20 |
| R.B.M. Z179 | 15.00 | THORN 1500 3 Stack | 5.20 |
| R.B.M. Z718 22" | 19.50 | THORN 1500 5 Stack | 5.29 |
| PHILIPS 320 | 8.70 | THORN 1600 | 4.95 |
| PHILIPS 210/300 Mono | 10.00 | THORN 3000/3500 | 7.98 |
| PHILIPS G8 | 8.75 | THORN 8000 | 5.28 |
| PHILIPS G9 | 7.75 | THORN 8500/8800 | 7.15 |
| PHILIPS G11 | 13.50 | THORN 9000 | 7.93 |
| PYE 697 (Printed) | 14.50 | DECCA 1730/1830 | 4.48 |
| PYE 713/731 | 10.00 | DECCA 30 | 6.76 |
| PYE 725 90" | 10.50 | DECCA 80 | 8.60 |
| PYE 169 | 10.00 | DECCA 100 | 7.50 |
| DECCA 80/100 | 8.58 | UNIVERSAL ITT or REMO | 8.00 |
| DECCA 1700 | 9.00 | GEC 2100 | 7.40 |
| DECCA 1730 | 8.58 | GEC 2200 (20AX) | 6.50 |
| DECCA 2230 | 8.58 | GEC 2040/2028 | 8.00 |
| GEC 2110 | 9.45 | GEC 2110 Pre Jan '77 | 7.00 |
| GEC 2040 | 9.50 | GEC 2110 Post Jan '77 | 7.00 |
| GEC 2200 | 6.65 | PHILIPS G8 Short Focus Lead | 6.75 |
| ITT CVC 1-9 | 10.85 | PHILIPS G8 Long Focus 550 | 6.75 |
| ITT CVC 25/30/32 | 8.65 | PHILIPS G9 | 6.37 |
| ITT CVC 20 | 8.60 | Pye/Philips K3 Tripler | 10.85 |
| THORN 3000 EHT | 9.95 | PYE 691/3 | 6.58 |
| THORN 3000 SCAN | 7.95 | PYE 713/4 Lead | 8.79 |
| THORN 8000 | 11.33 | PYE 713 Doubler 5 Lead | 8.79 |
| THORN 8500 | 11.33 | PHILIPS/Pye KT3 | 6.67 |
| THORN 9000 | 10.65 | PYE 731/725 | 7.60 |
| THORN 3000/3500 | 10.00 | R.B.M. A823 (plug in) AV | 7.60 |
| Mains | | KORTING (similar to Siemens TVK1) | 7.32 |
| THORN 1591 | 8.68 | ITT KB CVC5/9 | 6.90 |
| THORN 1681 | 9.88 | ITT KB CVC20/25/30 (Mullard) | 5.95 |
| THORN TX10 | 12.50 | RR1 T20 | 6.80 |
| THORN 1615 | 9.75 | | |
| PHILIPS KT3 | 7.70 | | |
| RANK BUSHRANGER | £10.00 | | |
| PYE 741 | 8.20 | | |
| THORN 9800 | 23.00 | | |
| B+ D (2000, 3000) | 12.70 | | |
| B+ O (3000 EHT) | 18.90 | | |

RECTIFIER TRAYS

| | |
|-----------------------------------|-------|
| THORN 1400 3 Stack | 5.20 |
| THORN 1500 3 Stack | 5.20 |
| THORN 1500 5 Stack | 5.29 |
| THORN 1600 | 4.95 |
| THORN 3000/3500 | 7.98 |
| THORN 8000 | 5.28 |
| THORN 8500/8800 | 7.15 |
| THORN 9000 | 7.93 |
| DECCA 1730/1830 | 4.48 |
| DECCA 30 | 6.76 |
| DECCA 80 | 8.60 |
| DECCA 100 | 7.50 |
| UNIVERSAL ITT or REMO | 8.00 |
| GEC 2100 | 7.40 |
| GEC 2200 (20AX) | 6.50 |
| GEC 2040/2028 | 8.00 |
| GEC 2110 Pre Jan '77 | 7.00 |
| GEC 2110 Post Jan '77 | 7.00 |
| PHILIPS G8 Short Focus Lead | 6.75 |
| PHILIPS G8 Long Focus 550 | 6.75 |
| PHILIPS G9 | 6.37 |
| Pye/Philips K3 Tripler | 10.85 |
| PYE 691/3 | 6.58 |
| PYE 713/4 Lead | 8.79 |
| PYE 713 Doubler 5 Lead | 8.79 |
| PHILIPS/Pye KT3 | 6.67 |
| PYE 731/725 | 7.60 |
| R.B.M. A823 (plug in) AV | 7.60 |
| KORTING (similar to Siemens TVK1) | 7.32 |
| ITT KB CVC5/9 | 6.90 |
| ITT KB CVC20/25/30 (Mullard) | 5.95 |
| RR1 T20 | 6.80 |

REPLACEMENT ELECTROLYTICS

| | |
|---------------------------------------|------|
| PYE 169 (200/200/100/32) | 3.40 |
| PHILIPS 320 (400/400/200V) | 2.74 |
| DECCA 30 (400/400/350V) | 3.40 |
| DECCA 80 (400/350V) | 5.29 |
| DECCA 100 (800/250V) | 3.97 |
| DECCA 1700 (200/200/400/350V) | 4.83 |
| PHILIPS G8 (600/300V) | 2.30 |
| PHILIPS G9 (600/300V) | 2.21 |
| PHILIPS G11 (470/250V) | 2.90 |
| PYE 691/7 (200/300/350V) | 2.70 |
| PYE 731 (600/300V) | 2.31 |
| RBM A823 (2500/2500/30V) | 1.66 |
| RBM A823 (800/300V) | 2.83 |
| RBM Z146 (300/300/350V) | 3.55 |
| RR1 T20A (220/400V) | 2.00 |
| ITT CVC5/9 (200/200/75/25) | 2.98 |
| ITT CVC 20 (220/400V) | 2.90 |
| GEC 2110 (600/250V) | 1.94 |
| GEC 2040 (1000/2000/35V) | 1.19 |
| GEC 2040 (300/300/150/100/50) | 4.10 |
| THORN 3500 (400/40V) | 30 |
| THORN 950 (100/300/100/16/275V) | 1.83 |
| THORN 1400 (150/100/100/100/150/320V) | 2.79 |
| THORN 1500 (150/150/100/300V) | 2.20 |
| THORN 1500 (12/300V) | 31 |
| THORN 3500 (175/100/100/400/350V) | 2.78 |
| THORN 3500 (1000/63V) | 86 |
| THORN 3500 (1000/70V) | 86 |
| THORN 8000/8500 (2500/2500/63V) | 3.38 |
| THORN 8000/8500 (700/250V) | 2.31 |
| THORN 8000/8500 (400/350V) | 2.56 |
| THORN 9000 (400/400V) | 3.28 |
| GEC (200/200/150/50) | 2.64 |
| PHILIPS 69 2200/63V | 1.25 |
| THORN 4700 P/C 25V | 1.20 |
| THORN 1591/1691 4700/25V | 1.20 |

CRYSTALS & FILTERS

| | |
|-----------|------|
| 6MHz | 74 |
| 5.5MHz | 74 |
| 4.3MHz | 1.30 |
| 8.8MHz | 1.30 |
| 9.9MHz | 6.00 |
| 10.692MHz | 6.00 |

MULTITURN POTS

| | |
|-------------|----|
| GEC TCE | 55 |
| PHILIPS G8 | 55 |
| DECCA, RANK | 55 |

P. V. TUBES

PLEASE NOTE OUR NEW ADDRESS - COME AND SEE US
 104 ABBEY STREET, ACCRINGTON, LANCBS BB5 1EE.
 Tel: 0254 36521/32611 Telex: 635562 Griffin G (For P.V.)

HOW TO ORDER
 ADD 65p per order P+P (U.K.). Heavier parcels e.g. cable, service aids, degaus. coils please allow £1.20 P+P (U.K.). Export orders charged at cost. First Class Mail is used whenever possible. Add 15% VAT to total except where it states zero rate.

Goods are despatched on the day we receive your order. If for any reason we are out of stock we will try to inform you as quickly as possible. We try our best to give a speedy, fair and efficient service. As our regular customers know, orders telephoned in before 4 p.m. will be despatched the same day. V.A.T. invoice on request. Give us a ring - we'll give you service. Please ask if what you need is not listed - we will try to help. Prices are subject to change without notice.

| SEMICONDUCTORS | | | | INTEGRATED CIRCUITS | | | | DIODES | | | | | | | |
|----------------|------|-----------|------|---------------------|------|------------|-------|-----------------------|-------|----------|------|---------------|------|--------------|------|
| AC107 | 35 | BC557 | 8 | R2008B | 1.90 | AN2140 | 3.91 | SN76003N | 2.49 | TBA990 | 1.90 | UPC1168C | 1.28 | AA119 | 9 |
| AC126 | 30 | BC558 | 9 | R2010B | 1.92 | AN240 | 3.84 | =SN76013N | | TBA14406 | 2.44 | UPC1176C | 1.46 | BA102 | 17 |
| AC127 | 32 | BCY72 | 13 | R2265 | 1.50 | AN318 | 3.98 | SN76023N | 2.00 | TCA160 | 1.20 | UPC1177H | 1.56 | BA115 | 13 |
| AC128 | 32 | BD115 | 45 | R2322 | 62 | AN262 | 2.45 | SN76110N | 1.15 | TCA760 | 2.30 | UPC1178C | 1.28 | BA145 | 17 |
| AC128K | 40 | BD116A | 65 | R2323 | 67 | AN301 | 5.15 | SN76115N | 2.27 | TCA270SQ | 2.50 | UPC1180C | 1.84 | BA148 | 17 |
| AC141K | 39 | BD124P | 79 | R2461 | 1.50 | AN7150 | 3.97 | SN76131N | 2.00 | TCA800 | 3.10 | UPC1181H | 1.62 | BA154 | 4 |
| AC142K | 38 | BD131 | 50 | R2540 | 2.80 | AN6340 | 7.85 | SN76226DN | 2.00 | TCA830 | 2.44 | UPC1182H | 2.95 | BA155 | 16 |
| AC176 | 35 | BD132 | 49 | RCA16334 | 99 | AN6341 | 4.45 | SN76227N | 1.18 | TCA830S | 1.75 | UPC1183H | 1.38 | BA156 | 15 |
| AC176K | 35 | BD133 | 60 | RCA16029 | 90 | AN6341N | 5.10 | SN76532N | 1.50 | TCA900 | 2.20 | UPC1185H | 3.66 | BA317 | 26 |
| AC186 | 41 | BD135 | 38 | RCA16039 | 99 | AN6344 | 7.85 | SN76533N | 1.70 | TCA910 | 2.20 | UPC1188H | 2.20 | BAX13 | 4 |
| AC187 | 38 | BD136 | 38 | RCA16091 | 2.95 | BA521 | 3.00 | SN76033N | 2.49 | TCA940 | 1.95 | UPC1190G | 1.20 | BAX16 | 8 |
| AC187K | 38 | BD137 | 38 | RCA16040 | 99 | BA521 | 2.00 | SN76544N | 2.35 | TDA440 | 2.20 | UPC1197C | 1.06 | BB1058 | 30 |
| AC188 | 35 | BD138 | 35 | RCA16041 | 96 | BA536 | 3.00 | SN76650N | 1.05 | TDA1002 | 1.95 | UPC1198C | 84 | BB1056G | 30 |
| AC188K | 39 | BD139 | 35 | RCA16334 | 84 | CA555 | 46 | SN76660N | 1.05 | TDA1003A | 5.50 | UPC1200V | 1.18 | BY126 | 12 |
| AD143 | 82 | BD140 | 44 | RCA16335 | 86 | CA556 | 80 | SN76666N | 80 | TDA1004A | 3.35 | UPC1211V | 2.10 | BY127 | 11 |
| AD161 | 54 | BD144 | 1.70 | RCA16799 | 86 | CA741 | 25 | SN76693A | 1.47 | TDA1006A | 2.50 | UPC1212V | 1.34 | BY133 | 15 |
| AD162 | 54 | BD150 | 60 | RCA16957 | 2.88 | CA748 | 45 | STK015 | 6.25 | TDA1005 | 3.60 | UPC1215V | 1.66 | BY164 | 45 |
| AD161/62 MP | 1.15 | BD159 | 65 | TC45 | 10 | CA9065 | 1.80 | STK032 | 13.25 | TDA1010 | 1.54 | UPC1216V | 1.20 | BY176 | 65 |
| AF106 | 49 | BD166 | 52 | TC46 | 54 | HAI1124 | 1.65 | STK043 | 11.05 | TDA1035 | 4.70 | UPC1217G | 1.13 | BY179 | 83 |
| AF114 | 89 | BD179 | 70 | TIC46 | 60 | HAI1151 | 1.65 | STK433 | 5.65 | TDA1037 | 2.95 | UPC1218H | 1.80 | BY182 | 87 |
| AF118 | 1.20 | BD182 | 1.20 | TIC46 | 65 | HAI1322 | 2.65 | STK435 | 5.06 | TDA1044 | 4.37 | UPC1223C | 2.20 | BY184 | 55 |
| AF121 | 75 | BD183 | 75 | TIL78 | 46 | HAI1342 | 2.49 | STK436 | 9.50 | TDA1060A | 4.44 | UPC1225H | 1.50 | BY199 | 28 |
| AF124 | 48 | BD201 | 85 | TIP29C | 43 | HAI306N | 2.60 | STK437 | 7.85 | TDA1062 | 1.56 | UPC1226C | 1.50 | BY206 | 14 |
| AF125 | 46 | BD202 | 80 | TIP30A | 47 | HAI366WR | 4.3 | STK459 | 8.20 | TDA1083 | 1.68 | UPC1227V | 1.20 | BY210/600 | 28 |
| AF126 | 46 | BD203 | 80 | TIP30C | 43 | HAI392 | 3.95 | STK441 | 8.10 | TDA1170S | 3.00 | UPC1228H | 54 | BY210/800 | 33 |
| AF127 | 38 | BD204 | 99 | TIP31C | 55 | HAI1219 | 2.49 | STK461=465 | 9.60 | TDA1190 | 3.50 | UPC1230H | 3.95 | BY223 | 90 |
| AF139 | 58 | BD222 | 46 | TIP32C | 42 | LA4031P | 3.21 | STK463 | 14.30 | TDA1180 | 2.91 | UPC1238V | 1.16 | BY229 | 22 |
| AF178 | 1.54 | BD223 | 56 | TIP34B | 60 | LA4032P | 2.90 | SW153 | 2.74 | TDA1200 | 2.95 | UPC1245V | 1.35 | BY299 | 22 |
| AF239 | 60 | BD225 | 47 | TIP34B | 60 | LA4102 | 3.37 | TA7050P | 95 | TDA1220A | 2.12 | UPC1353C | 1.92 | BYX10 | 20 |
| AL102 | 2.00 | BD232 | 68 | TIP41C | 47 | LA4250 | 3.57 | TA7051P | 95 | TDA1270 | 3.95 | UPC1353C | 6.38 | BYX36/10 | 30 |
| AU106 | 2.50 | BD233 | 60 | TIP42C | 50 | LA4400 | 3.05 | TA7063P | 2.20 | TDA1327 | 1.70 | UPC1356C2 | 2.08 | BYX36/600 | 35 |
| AU107 | 2.00 | BD234 | 63 | TIP47 | 70 | LA4422 | 3.28 | TA7074P | 1.00 | TDA1352B | 1.60 | UPC1363C | 2.08 | BYX55/600 | 30 |
| AU113 | 2.00 | BD235 | 60 | TIP120 | 65 | LCT130 | 5.93 | TA7108P | 3.43 | TDA1412 | 1.20 | UPC1378H | 1.80 | BYX71/600 | 90 |
| BC107 | 20 | BD236 | 65 | TIP2955 | 90 | LCT120 | 5.87 | TA7120P | 2.43 | TDA1415 | 1.40 | UPC1358H | 2.77 | OA47 | 9 |
| BC108 | 20 | BD237 | 65 | TIP3055 | 63 | LCT137 | 5.50 | TA7129AP | 3.76 | TDA1470 | 4.67 | UPC1360C | 2.20 | OA91 | 10 |
| BC109 | 20 | BD238 | 65 | TIS91 | 1.80 | LM1011 | 3.25 | TA7130P | 1.93 | TDA1770 | 4.80 | UPC1363C | 2.16 | OA91 | 10 |
| BC114 | 12 | BD243 | 85 | TU106/02 | 1.50 | LM1340T | 75 | TA7141P | 95 | TDA2002 | 2.80 | UPC1366C | 1.84 | OA95 | 5 |
| BC115 | 17 | BD244 | 85 | 2N696 | 21 | LM1303N | 2.63 | TA7146P | 4.67 | TDA2003 | 1.20 | UPC1368H2 | 2.15 | OA202 | 11 |
| BC116A | 16 | BD410 | 79 | 2N918 | 82 | MC3712 | 1.95 | TA7193P | 1.67 | TDA2004 | 2.52 | UPC1370C2 | 2.58 | IN514 | 4 |
| BC117 | 30 | BD434 | 74 | 2N2904 | 51 | MC3107 | 1.99 | TA7171P | 1.85 | TDA2006 | 1.78 | UPC1382C | 1.08 | IN4001 | 4 |
| BC118 | 24 | BD437 | 86 | 2N2905 | 28 | MC3130P | 1.60 | TA7172P | 1.85 | TDA2010 | 2.00 | UPC1384A | 3.78 | IN4002 | 4 |
| BC119 | 36 | BD438 | 84 | 2N3054 | 60 | MC31327 | 1.70 | TA7173P | 1.85 | TDA2140 | 5.95 | UPC1447H | 58 | IN4003 | 4 |
| BC139 | 28 | BD507 | 52 | 2N3055 | 60 | MC31351P | 2.93 | TA7176P | 2.50 | TDA2150 | 2.22 | UPC41C | 2.80 | IN4004 | 5 |
| BC140 | 32 | BD508 | 55 | 2N3702 | 11 | MC1330P | 90 | TA7202P | 4.27 | TDA2190 | 4.70 | UPC5743 | 38 | IN4005 | 5 |
| BC141 | 26 | BD509 | 56 | 2N3703 | 10 | MC1349 | 1.99 | TA7204P | 3.77 | TDA2020 | 4.66 | UPC577H | 2.46 | IN4006 | 5 |
| BC142 | 30 | BD510 | 60 | 2N3705 | 10 | MC1350 | 1.50 | TA7205AP | 3.72 | TDA2030 | 2.80 | UPC585C | 1.28 | IN4007 | 6 |
| BC143 | 31 | BD278A | 61 | 2N3706 | 10 | MC1352 | 1.75 | TA7208P | 3.40 | TDA2521 | 4.17 | TDA 1011 | 4.00 | IN4418 | 2 |
| BC147 | 13 | BD517 | 80 | 2N3708 | 17 | MC1358P | 1.50 | TA7210P | 6.60 | TDA2522 | 2.40 | 11A 4112 | 75 | IN4448 | 10 |
| BC148 | 9 | BD520 | 75 | 2N5294 | 48 | MC1495L | 3.00 | TA7222P | 2.42 | TDA2523 | 3.40 | IC/Transistor | | IN5401 | 12 |
| BC149 | 12 | BD526 | 62 | 2N5296 | 48 | MC13002 | 3.90 | TA7223P | 3.74 | TDA2524 | 2.25 | equivalent | | IN5402 | 14 |
| BC157 | 16 | BD535 | 82 | 2N5298 | 1.69 | MC14011BCP | 66 | TA7227P | 5.98 | TDA2525 | 3.64 | leaflet £2.25 | | IN5403 | 12 |
| BC158 | 16 | BD536 | 91 | 2N5496 | 53 | MC14049UB | 43 | TA7228P | 5.98 | TDA2530 | 2.70 | | | IN5404 | 12 |
| BC159 | 15 | BD636A | 1.49 | 2N6107 | 75 | MC7742 | 1.35 | TA7310P | 2.78 | TDA2532 | 2.56 | | | IN5405 | 13 |
| BC160 | 25 | BD697 | 1.24 | 2N6109 | 81 | MC7812 | 1.35 | TA7609P | 4.39 | TDA2540 | 3.84 | | | IN5406 | 16 |
| BC161 | 28 | BD698 | 1.39 | 2N6119 | 1.21 | ML231 | 2.20 | TA7611AP | 2.92 | TDA2541 | 3.84 | | | IN5407 | 16 |
| BC170B | 15 | BD698 | 1.50 | 2SA715 | 0.98 | ETTR6016 | 2.20 | TAA300 | 58 | TDA2560 | 3.50 | | | IN5408 | 20 |
| BC171 | 15 | BD707 | 95 | 2SC495 | 1.10 | ML232 | 2.20 | TAA310 | 2.83 | TDA2571 | 2.56 | IT44 | 4 | IN5409 | 4 |
| BC172 | 15 | BDX32 | 2.10 | 2SC496 | 1.31 | ML236 | 2.20 | TAA320 | 2.00 | TDA2576 | 3.75 | ITT2002 | 11 | Y969 - Disc. | |
| BC173 | 12 | BF115 | 38 | 2SC643A | 1.50 | ML237 | 2.50 | TAA550 | 55 | TDA2576A | 3.75 | REP BZX85 30V | | BZY15-24R | 1.18 |
| BC174 | 10 | BF117 | 36 | 2SC1096 | 1.72 | ML238 | 6.00 | TAA630 | 3.90 | TDA2577 | 3.25 | | | BZY15-12R | 1.18 |
| BC177 | 27 | BF125 | 26 | 2SC1172Y | 2.20 | ML239 | 2.50 | TAA8400S1 | 1.96 | TDA2581 | 3.30 | | | | |
| BC178 | 26 | BF127 | 47 | 2SC1173Y | 1.69 | ML920 | 4.12 | TAA661B | 1.20 | TDA2582 | 2.60 | | | | |
| BC162L | 9 | BF154 | 23 | 2SC1306 | 2.73 | ML922 | 3.29 | TBA120A | 80 | TDA2590 | 3.25 | | | | |
| BC183L | 12 | BF158 | 18 | 2SC1307 | 3.00 | ML926 | 2.18 | (A), (S), (AS), (SA), | | TDA2591 | 2.95 | | | | |
| BC184L | 14 | BF160 | 27 | 2SC1449 | 1.67 | ML928 | 2.18 | TBA120B | 1.30 | TDA2593 | 2.95 | | | | |
| BC186 | 18 | BF167 | 24 | 2SC1520 | 0.68 | MM5387ANN | 4.15 | TBA120SB | 1.37 | TDA2600 | 5.30 | | | | |
| BC187 | 18 | BF173 | 22 | 2SC1678 | 2.67 | MM5402N | 6.65 | TBA120T | 95 | TDA2610 | 3.20 | | | | |
| BC204 | 10 | BF177 | 52 | 2SC1909 | 2.90 | MRF475 | 2.50 | TBA120U | 1.10 | TDA2611A | 1.95 | | | | |
| BC206 | 13 | BF178 | 46 | 2SC1953 | 1.44 | MRF477 | 10.00 | TBA395 | 1.20 | TDA2640 | 2.92 | | | | |
| BC209 | 10 | BF179 | 28 | 2SC2028 | 1.82 | MSNS807 | 7.87 | TBA396 | 80 | TDA2652 | 3.96 | | | | |
| BC212L | 9 | BF180 | 39 | 2SC2029 | 2.60 | MS1513L | 2.80 | TBA440N | 2.75 | TDA2680 | 3.40 | | | | |
| BC212L | 13 | BF181 | 39 | 2SC2078 | 2.90 | MS15153L | 3.28 | (TBA1441) | | TDA2690 | 1.35 | | | | |
| BC213 | 13 | BF182 | 36 | 2SC2091 | 1.34 | SAA1025 | 4.40 | TBA440P | 2.50 | TDA3190 | 2.00 | | | | |
| BC214 | 10 | BF183 | 29 | 2SC2166 | 2.73 | SAA1124 | 2.50 | TBA4800 | 1.50 | TDA3500 | 6.90 | | | | |
| BC237 | 14 | BF184 | 36 | DEC1 | 2.20 | SAA1250 | 3.94 | TBA510 | 3.00 | TDA3560 | 6.00 | | | | |
| BC238 | 14 | BF185 | 36 | DEC2 | 2.20 | SAA1251 | 4.90 | TBA520(O) | 1.68 | TDA3561 | 6.50 | | | | |
| BC251A | 18 | BF185 | 36 | THY15/80 | 2.20 | SAA5000 | 4.39 | TBA530(O) | 1.38 | TDA3571 | 3.75 | | | | |
| BC252 | 12 | BF194/39A | 16 | THY15/85 | 2.20 | SAA5010 | 6.30 | TBA540 | 1.68 | TDA3950 | 3.15 | | | | |
| BC261 | 18 | BF195 | 16 | BU208B | 2.20 | SAA5020 | 6.50 | TBA550(O)</ | | | | | | | |

HOCKLEY DISCOUNT TELEVISIONS

MIDLANDS NEWEST WHOLESALERS

FRESH STOCK WEEKLY

SEPTEMBER SALE PRICES

| | |
|--------------------------|--------|
| Bush from | £6.00 |
| G8 520 from | £5.00 |
| G8 550 from | £10.00 |
| G.E.C. Solid State | £20.00 |
| Pye Solid State | £18.00 |
| Pye Chelsea | £20.00 |
| I.T.T. Hybrid | £18.00 |
| Decca Hybrid | £12.00 |
| Japanese Models | £22.00 |

Also latest stock G11, B.R.C. 9000, Decca 80 & 100 Series I.T.T. CVC30, 45 etc.

WORKING SETS FROM £18.00
SPECIAL OFFER ON WORKING SETS.
MINIMUM 6 SETS

RING US NOW

021-551-2233

**94 Soho Hill,
 Hockley,
 Birmingham B19 1AE.**

Opening hours 9 - 7 Monday - Saturday
 Sundays by appointment.

CUSTOMER CAN'T PAY? DONT LOSE HIM FIT A TV METER



COINAGE
 AVAILABLE
 10p
 50p
 £1

COMPLETELY VARIABLE TIMINGS



MANUFACTURERS OF TV COIN OPERATED METERS CONTACT (0202) 674272
**87-89 Sterte Avenue,
 Poole, Dorset. BH15 2AW.
 Telex: 418253 LUMIC G**

FREE CAREER BOOKLET

Train for success in Electronics Engineering, T.V. Servicing, Electrical Engineering—or running your own business!

ICS have helped thousands of ambitious people to move up into higher paid, more secure jobs in the fields of electronics, T.V., electrical engineering—now it can be your turn. Whether you are a newcomer to the field or already working in these industries, ICS can provide you with the specialised training so essential to success.

Personal Tuition and 80 Years of Success

The expert and personal guidance by fully qualified tutors, backed by the long ICS record of success, is the key to our outstanding performance in the technical field. You study at the time and pace that suits you best and in your own home.

You study the subjects you enjoy, receive a formal Diploma, and you're ready for that better job, better pay.

TICK THE FREE BOOKLET YOU WANT AND POST TODAY

ELECTRONICS ENGINEERING

A Diploma Course, recognised by the Institute of Engineers & Technicians as meeting all academic standards for application as an Associate.

T.V. & AUDIO SERVICING

A Diploma Course, training you in all aspects of installing, maintaining and repairing T.V. and Audio equipment, domestic and industrial.

ELECTRICAL ENGINEERING

A further Diploma Course recognised by the Institute of Engineers & Technicians, also covering business aspects of electrical contracting.

RUNNING YOUR OWN BUSINESS

If running your own electronics, T.V. servicing or electrical business appeals, then this Diploma Course trains you in the vital business knowledge and techniques you'll need.

Name

Address

ICS ICS Dept. EGS94
 160 Stewarts Road,
 London SW8 4UJ.



01-622 9911
 (all hours)

| WE WILL ONLY SUPPLY TOP QUALITY, BRANDED COMPONENTS. REPUTATION COUNTS WITH US | | | | G.G.L. COMPONENTS 108 SCOTLAND ROAD, CARLISLE, CUMBRIA CA3 9EY PHONE (0228) 20358/139693 | | | | BUY WITH  | | E.H.T. TRAYS | |
|--|-----------------------|-----------------------|-----------------------|---|-----------------------|------------------------------|------------------------------|--|-----------------------------|--------------------------|--------------------------|
| INTEGRATED CIRCUITS | | | | TRANSISTORS | | | | LINE O/P TR. | | DIODES | |
| TYPE PRICE (£) | TYPE PRICE (£) | TYPE PRICE (£) | TYPE PRICE (£) | TYPE PRICE (£) | TYPE PRICE (£) | TYPE PRICE (£) | TYPE PRICE (£) | TYPE PRICE (£) | TYPE PRICE (£) | TYPE PRICE (£) | TYPE PRICE (£) |
| LA3122 2.10 | TBA520 1.30 | STK0050 7.50 | UPC1185H2 3.30 | BC548 10 | BR100 18 | RBM T20/22A 12.20 | RBM T20/22A 12.20 | PHILIPS G8 7.90 | PHILIPS G8 7.90 | BY127 10 | BY133 15 |
| LA3301 1.97 | TBA530 1.00 | STK011 7.35 | UPC1188H 3.30 | BC567 10 | BR101 32 | RBM Z18 18/20/22 22.95 | RBM Z18 18/20/22 22.95 | PHILIPS G9 8.75 | PHILIPS G9 8.75 | BY164 40 | BY179 30 |
| LA4031 1.66 | TBA550 1.40 | STK015 7.15 | UPC1198H 1.30 | AC127 22 | BC568 10 | BR103 55 | BR103 55 | PHILIPS G11 13.50 | PHILIPS G11 13.50 | BY210/800 60 | BY227M 26 |
| LA4031P 2.45 | TBA560Q 1.60 | STK016 7.45 | UPC1200V 1.90 | AC128 22 | BD124P 55 | BT106 1.15 | BT106 1.15 | PHILIPS G11 13.50 | PHILIPS G11 13.50 | BY27M 26 | BYX10 20 |
| LA4032 2.34 | TBA750Q 2.45 | STK020 9.05 | UPC1208C 1.85 | AC128K 30 | BD132 33 | BU126 1.70 | BU126 1.70 | THORN 1590/1 8.68 | THORN 1590/1 8.68 | BYX55/600 26 | BYX71/600 78 |
| LA4051 2.79 | TBA800 1.80 | STK032 11.32 | UPC1211C 4.05 | AC188K 33 | BD201 80 | BU204 1.50 | BU204 1.50 | THORN 1690/1 9.68 | THORN 1690/1 9.68 | IN4001-7 07 | IN5401-8 12 |
| LA4101 1.88 | TBA810AS 1.15 | STK035 12.67 | UPC1215V 2.50 | AD149 70 | BD202 70 | BU205 1.42 | BU205 1.42 | ITT CVC 20/30 6.85 | ITT CVC 20/30 6.85 | BZ188-range 11 | BZ188-range 11 |
| LA4102 1.97 | TBA820 1.40 | STK036 12.67 | UPC1216V 2.00 | AD161 42 | BD203 70 | BU206 1.35 | BU206 1.35 | THORN 1615 9.75 | THORN 1615 9.75 | PYE 1100/100 10.20 | PYE 1100/100 10.20 |
| LA4400 2.80 | TBA890 2.95 | STK043 11.33 | UPC1217G 3.35 | AD162 42 | BD204 83 | BU208A 1.40 | BU208A 1.40 | THORN TX10 12.50 | THORN TX10 12.50 | ITT CVC 1-9 9.60 | ITT CVC 1-9 9.60 |
| LA4420 1.94 | TBA920Q 1.50 | STK050 20.75 | UPC1218H 2.75 | AF127 36 | BD222 50 | BU208/02.170 1.70 | BU208/02.170 1.70 | PYE 725 (90) 10.20 | PYE 725 (90) 10.20 | OECCA 80 8.58 | OECCA 100 8.58 |
| LA4422 2.75 | TBA950/2X 2.65 | STK070 21.95 | UPC1222 2.05 | AU110 2.10 | BD232 50 | BU326A 1.48 | BU326A 1.48 | ITT CVC 25/30/32 8.00 | ITT CVC 25/30/32 8.00 | OECCA 100 8.58 | OECCA 100 8.58 |
| LA4430 1.93 | TBA990 1.55 | STK077 8.56 | UPC1223 3.40 | AU113 3.50 | BD233 37 | BU407 1.12 | BU407 1.12 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4460 2.95 | TCA270S 1.30 | STK078 8.45 | UPC1225 3.10 | BC107 14 | BD234 40 | BU500 1.80 | BU500 1.80 | OECCA 2230 8.30 | OECCA 2230 8.30 | OECCA 80 8.58 | OECCA 100 8.58 |
| LA4461 2.95 | TCA800 1.95 | STK082 9.75 | UPC1226 2.55 | BC108 14 | BD235 32 | BU526 2.00 | BU526 2.00 | OECCA 100 8.58 | OECCA 100 8.58 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4462 2.95 | TCA940 1.55 | STK086 12.89 | UPC1227 2.10 | BC109 14 | BD236 43 | BU826 3.20 | BU826 3.20 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4463 2.95 | TCA990 1.55 | STK087 9.75 | UPC1228 2.10 | BC110 14 | BD237 40 | R2008B 1.45 | R2008B 1.45 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4464 2.95 | TCA990 1.55 | STK088 9.75 | UPC1229 2.10 | BC111 14 | BD238 39 | R2010B 1.45 | R2010B 1.45 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4465 2.95 | TCA990 1.55 | STK089 9.75 | UPC1230H 3.45 | BC112 26 | BD239 39 | R2010B 1.45 | R2010B 1.45 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4466 2.95 | TCA990 1.55 | STK090 9.75 | UPC1231H 3.45 | BC113 26 | BD240 39 | R2010B 1.45 | R2010B 1.45 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4467 2.95 | TCA990 1.55 | STK091 9.75 | UPC1232H 3.45 | BC114 26 | BD241 39 | R2010B 1.45 | R2010B 1.45 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4468 2.95 | TCA990 1.55 | STK092 9.75 | UPC1233H 3.45 | BC115 26 | BD242 39 | R2010B 1.45 | R2010B 1.45 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4469 2.95 | TCA990 1.55 | STK093 9.75 | UPC1234H 3.45 | BC116 26 | BD243 39 | R2010B 1.45 | R2010B 1.45 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4470 2.95 | TCA990 1.55 | STK094 9.75 | UPC1235H 3.45 | BC117 26 | BD244 39 | R2010B 1.45 | R2010B 1.45 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4471 2.95 | TCA990 1.55 | STK095 9.75 | UPC1236H 3.45 | BC118 26 | BD245 39 | R2010B 1.45 | R2010B 1.45 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4472 2.95 | TCA990 1.55 | STK096 9.75 | UPC1237H 3.45 | BC119 26 | BD246 39 | R2010B 1.45 | R2010B 1.45 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4473 2.95 | TCA990 1.55 | STK097 9.75 | UPC1238H 3.45 | BC120 26 | BD247 39 | R2010B 1.45 | R2010B 1.45 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4474 2.95 | TCA990 1.55 | STK098 9.75 | UPC1239H 3.45 | BC121 26 | BD248 39 | R2010B 1.45 | R2010B 1.45 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4475 2.95 | TCA990 1.55 | STK099 9.75 | UPC1240H 3.45 | BC122 26 | BD249 39 | R2010B 1.45 | R2010B 1.45 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4476 2.95 | TCA990 1.55 | STK100 9.75 | UPC1241H 3.45 | BC123 26 | BD250 39 | R2010B 1.45 | R2010B 1.45 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4477 2.95 | TCA990 1.55 | STK101 9.75 | UPC1242H 3.45 | BC124 26 | BD251 39 | R2010B 1.45 | R2010B 1.45 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4478 2.95 | TCA990 1.55 | STK102 9.75 | UPC1243H 3.45 | BC125 26 | BD252 39 | R2010B 1.45 | R2010B 1.45 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4479 2.95 | TCA990 1.55 | STK103 9.75 | UPC1244H 3.45 | BC126 26 | BD253 39 | R2010B 1.45 | R2010B 1.45 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4480 2.95 | TCA990 1.55 | STK104 9.75 | UPC1245H 3.45 | BC127 26 | BD254 39 | R2010B 1.45 | R2010B 1.45 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4481 2.95 | TCA990 1.55 | STK105 9.75 | UPC1246H 3.45 | BC128 26 | BD255 39 | R2010B 1.45 | R2010B 1.45 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4482 2.95 | TCA990 1.55 | STK106 9.75 | UPC1247H 3.45 | BC129 26 | BD256 39 | R2010B 1.45 | R2010B 1.45 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4483 2.95 | TCA990 1.55 | STK107 9.75 | UPC1248H 3.45 | BC130 26 | BD257 39 | R2010B 1.45 | R2010B 1.45 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4484 2.95 | TCA990 1.55 | STK108 9.75 | UPC1249H 3.45 | BC131 26 | BD258 39 | R2010B 1.45 | R2010B 1.45 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4485 2.95 | TCA990 1.55 | STK109 9.75 | UPC1250H 3.45 | BC132 26 | BD259 39 | R2010B 1.45 | R2010B 1.45 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4486 2.95 | TCA990 1.55 | STK110 9.75 | UPC1251H 3.45 | BC133 26 | BD260 39 | R2010B 1.45 | R2010B 1.45 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4487 2.95 | TCA990 1.55 | STK111 9.75 | UPC1252H 3.45 | BC134 26 | BD261 39 | R2010B 1.45 | R2010B 1.45 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4488 2.95 | TCA990 1.55 | STK112 9.75 | UPC1253H 3.45 | BC135 26 | BD262 39 | R2010B 1.45 | R2010B 1.45 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4489 2.95 | TCA990 1.55 | STK113 9.75 | UPC1254H 3.45 | BC136 26 | BD263 39 | R2010B 1.45 | R2010B 1.45 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4490 2.95 | TCA990 1.55 | STK114 9.75 | UPC1255H 3.45 | BC137 26 | BD264 39 | R2010B 1.45 | R2010B 1.45 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4491 2.95 | TCA990 1.55 | STK115 9.75 | UPC1256H 3.45 | BC138 26 | BD265 39 | R2010B 1.45 | R2010B 1.45 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4492 2.95 | TCA990 1.55 | STK116 9.75 | UPC1257H 3.45 | BC139 26 | BD266 39 | R2010B 1.45 | R2010B 1.45 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4493 2.95 | TCA990 1.55 | STK117 9.75 | UPC1258H 3.45 | BC140 26 | BD267 39 | R2010B 1.45 | R2010B 1.45 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4494 2.95 | TCA990 1.55 | STK118 9.75 | UPC1259H 3.45 | BC141 26 | BD268 39 | R2010B 1.45 | R2010B 1.45 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4495 2.95 | TCA990 1.55 | STK119 9.75 | UPC1260H 3.45 | BC142 26 | BD269 39 | R2010B 1.45 | R2010B 1.45 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4496 2.95 | TCA990 1.55 | STK120 9.75 | UPC1261H 3.45 | BC143 26 | BD270 39 | R2010B 1.45 | R2010B 1.45 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4497 2.95 | TCA990 1.55 | STK121 9.75 | UPC1262H 3.45 | BC144 26 | BD271 39 | R2010B 1.45 | R2010B 1.45 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4498 2.95 | TCA990 1.55 | STK122 9.75 | UPC1263H 3.45 | BC145 26 | BD272 39 | R2010B 1.45 | R2010B 1.45 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4499 2.95 | TCA990 1.55 | STK123 9.75 | UPC1264H 3.45 | BC146 26 | BD273 39 | R2010B 1.45 | R2010B 1.45 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4500 2.95 | TCA990 1.55 | STK124 9.75 | UPC1265H 3.45 | BC147 26 | BD274 39 | R2010B 1.45 | R2010B 1.45 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4501 2.95 | TCA990 1.55 | STK125 9.75 | UPC1266H 3.45 | BC148 26 | BD275 39 | R2010B 1.45 | R2010B 1.45 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4502 2.95 | TCA990 1.55 | STK126 9.75 | UPC1267H 3.45 | BC149 26 | BD276 39 | R2010B 1.45 | R2010B 1.45 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4503 2.95 | TCA990 1.55 | STK127 9.75 | UPC1268H 3.45 | BC150 26 | BD277 39 | R2010B 1.45 | R2010B 1.45 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 | ITT CVC 20 7.75 |
| LA4504 2.95 | TCA990 1.55 | STK128 9.75 | UPC1269H 3.45 | BC151 26 | BD278 39 | R2010B 1.45 | R2010B 1.45 | ITT CVC | | | |

Z6000 Editing Systems With Version 2 Software

Even greater power and flexibility for post production operations . . .

9 Machine Capable

Interfaces to most 1" C, 1" B, 3/4" and High Speed 1/2" VTRs all assignable to the record side or a different source location, from the Z6000 keyboard.

250 Event Memory

Not just edit lines but total events.

Frame Accurate Edits

When using EBU/SMPTE code reference, the Z6000 'bumps' the servo-controlled capstans into the selected frame relationship.

Full List Management With Text Editing

Index; insert and delete event; move event; reduce and increase event duration; move, delete or insert blocks of events; 'ripple' to position all in and out points relative to the text edit.

Full A/B Roll And Sync Roll Capability

Videomedia provides full serial interface to most popular vision mixers.

True Pal Colour Framing

Recognises and handles 4 and 8 field sequences.

Transfer Register

A 'constant' register, which may require multi-use during an editing session.

Many More Features

Such as animation, auto-tag, selectable pre and post roll, full disk operating system, programme length counter, cruise control.

All these features are programmed for ease of operation to allow maximum creativity.

See us on Stand G36 at IBC '84 Brighton

Videomedia Europe
EUROPEAN LIAISON OFFICE
34 THE QUADRANT RICHMOND SURREY TW9 1DN
Telephone: 01-940 6188 Telex: 938853.

EAST CORNWALL COMPONENTS

| ZENER DIODES | |
|------------------------|------------------|
| 400mW Plastic 3V-75V | 8p each. 10/75p |
| 1.3W Plastic 3V-200V | 15p each. 10/75p |
| 1.5W Flange 4.75-47.5V | 4.00 |
| 2.5W Plastic 7.5-75V | £1.26 each |
| 20W Stud 7.5-75V | £7.31 each |

| INTEGRATED CIRCUITS (E) EACH | |
|------------------------------|--------------------------|
| AN240P | 3.42 SN76530P 1.40 |
| AN240 | 3.88 SN76533N 1.60 |
| AN7150 | 2.90 SN76650N 1.05 |
| CA3065 | 1.75 SN76660N 0.75 |
| CA4031P | 2.88 SN76666N 0.80 |
| CA4102 | 3.30 STK015 6.50 |
| CA4250 | 3.50 TA7108P 3.20 |
| CA4400 | 2.98 TA7120P 3.20 |
| CA4422 | 3.07 TA7129AP 3.65 |
| LC7120 | 5.33 TA7130P 1.55 |
| LC7130 | 5.26 TA7172 1.80 |
| LC7137 | 5.16 TA7193 5.50 |
| LM3800 | 0.80 TA7172P 1.80 |
| LM1303N | 2.52 TA7176 2.50 |
| HA1151P | 3.12 TA7202P 4.18 |
| MC1307P | 1.85 TA7204P 1.85 |
| MC1310P | 1.85 TA7205AP 1.50 |
| MC1312P | 2.25 TA7208P 3.27 |
| MC1327P | 1.25 TA7210P 6.50 |
| MC1330P | 0.83 TA7222P 1.88 |
| MC1349P | 1.85 TA7223P 3.68 |
| MC1350P | 1.20 TA7227P 1.56 |
| MC1351P | 2.50 TA7310P 1.80 |
| MC1352P | 1.50 TA7609P 4.28 |
| MC1357P | 2.88 TA7611AP 2.88 |
| MC1358P | 1.30 TAA263 2.46 |
| MC1456L | 1.15 TAA310A 2.68 |
| ML211B | 2.10 TAA550 3.38 |
| ML232B | 2.10 TAA570 1.99 |
| ML237B | 2.30 TAA611A12 3.50 |
| N555 | 0.25 TAA630S 3.30 |
| NE555 | 0.88 TAA661B 1.70 |
| NE555D | 0.80 TAA700 2.80 |
| SAA1024 | 1.20 TAA840 2.10 |
| SAA1025 | 0.40 TAD100 2.80 |
| SA5560A | 2.50 FM FILTER 1.20 |
| SA5560S | 1.85 TA120 AS 1.30 |
| SA5570S | 1.85 S, S, S, B 1.30 |
| SA5580 | 2.85 Q, T, U, L, UQ 0.52 |
| SA5590 | 2.32 TA120B 1.30 |
| SC9303P | 1.10 TA231 1.45 |
| SL432A | 4.00 TA281 2.65 |
| SL901B | 5.20 TA395 1.20 |
| SL917B | 7.25 TA480Q 1.50 |
| SL1327Q | 1.10 TA490 2.30 |
| SN7603N | 2.44 TA510 2.60 |
| SN76013N | 1.90 TA530/Q 2.60 |
| SN76023ND | 2.90 TA520/Q 1.80 |
| SN76033N | 2.45 TA530/Q 1.30 |
| SN78110N | 1.12 TA540/Q 1.40 |
| SN78115N | 1.65 TA550/Q 1.70 |
| SN78131N | 1.65 TA560C 1.70 |
| SN78262DN | 1.80 TA560CQ 1.60 |
| SN78272N | 1.10 TA570 1.50 |

| | |
|--------------|-------|
| UBA41BX1 | 4.50 |
| UBA700 | 2.85 |
| UBA750 | 2.80 |
| UBA800 | 1.60 |
| UBA810P | 1.10 |
| UBA810S | 1.20 |
| UBA820 | 1.40 |
| UBA890 | 3.88 |
| UBA920/Q | 3.00 |
| UBA950/2A | 3.05 |
| UBA950 | 4.05 |
| UBA960 | 1.88 |
| UBA960S | 3.90 |
| UBA970C | 4.00 |
| UBA980 | 4.02 |
| UBA990 | 3.10 |
| UBA1000 | 1.90 |
| UBA1000A | 3.80 |
| UBA1003A | 5.50 |
| UBA1005A | 5.50 |
| UBA1035S | 4.50 |
| UBA1044 | 4.30 |
| UBA1002 | 1.90 |
| UBA1003A | 5.50 |
| UBA1005A | 5.50 |
| UBA1035S | 4.50 |
| UBA1044 | 4.30 |
| UBA1170S | 3.00 |
| UBA1190 | 3.50 |
| UBA1200 | 2.98 |
| UBA1270Q | 3.70 |
| UBA1327A | 1.66 |
| UBA1352A/B | 1.56 |
| UBA1412 | 1.10 |
| UBA1412S | 0.95 |
| UBA1412S | 0.95 |
| Soldersucker | 4.50 |
| Nozzles | 0.65p |

| PLUGS & SOCKETS | |
|---------------------|------|
| Metal Coax Plug | 0.18 |
| Plastic Coax Plug | 0.10 |
| Metal Line Socket | 0.50 |
| Single Junc. Socket | 0.80 |
| Plastic Phone | 0.10 |
| F.M. Plugs | 0.20 |
| PC29 Plug | 0.38 |
| Reducer | 0.15 |

| SOLDERING SECTION | |
|---|-------|
| Watts Watt iron complete with steel and plug attached | 7.20 |
| CS 18W, as above | 1.56 |
| Antex 15W iron | 5.00 |
| Antex 18W iron | 5.50 |
| Antex 25W iron | 5.20 |
| Antex elements 2.0 | 2.00 |
| Antex bits | 0.95 |
| Antex stands | 1.90 |
| Soldersucker | 4.50 |
| Nozzles | 0.65p |

| MULTIMETER SPECIAL | |
|---|--|
| Russian type UA324 - (20,000 O.P.V.) | |
| DC Volts: 0.6, 1.2, 3, 12, 30, 60, 100, 1200. | |
| AC Volts: 3, 6, 15, 30, 60, 300, 600, 3000. | |
| DC Curr. M/A: 0.06, 0.6, 6, 60, 600, 3000. | |
| AC Curr. M/A: 0.3, 3, 30, 300, 3000. | |
| DC Resistance: 0.2, 5, 50, 500, 5000K. | |
| level dB: -10 to +12 | |
| Supplied with rechargeable batteries. | |
| Price £12.00 incl. of p/p & VAT. | |

| MULTISECTION ELECTROLYTICS | |
|----------------------------------|------|
| THORN 850 100+300+100+16/300V | 1.80 |
| 1400 150+100+100+100+150/320V270 | 0.17 |
| 1500 150+150+100/300V | 1.50 |
| 3000 220/63V | 1.20 |
| 3500 175/400V+100+100/350V | 1.70 |
| 8000/400/350V | 2.10 |
| 8000/750/250V/63V | 1.35 |
| 8000/750/250V | 0.40 |
| 9000 400/400V | 2.25 |
| Timer Amp 4700/25V | 0.70 |
| DECCA 90/30 400+400/350V | 2.45 |
| 1W 300+100+100+100/350V | 1.85 |
| GECC 2047 2048 2083 2084 2104 | 2.32 |
| 200+200+150+50/300V | 1.30 |
| 600/250V | 2.50 |
| ITT/KB 200+200+75+25/350V | 2.15 |
| 220/100V | 1.85 |
| PHILIPS GB 600/300V | 1.70 |
| GB 9 600/300V | 1.50 |
| G11 470/250V | 1.50 |
| G12 2200/63V | 1.25 |
| EKCO T148 125-200+100+32/275V | 2.15 |
| 691 Series 200+300/350V | 2.25 |
| 600/300V | 1.80 |
| RANK 300+300/300V | 2.05 |
| AB23 2500+2500/30V | 0.58 |
| 200/400V | 1.75 |
| 600/300V | 1.75 |

| VDRs, etc. | |
|-----------------|----------|
| E295Z | 0.28 |
| 01/ | 0.28 |
| E298CD | |
| /A258 | 0.25 |
| E298ED | |
| /A258 | 0.22 |
| /A260 | 0.22 |
| /A262 | 0.22 |
| /A265 | 0.22 |
| /P268 | 0.22 |
| E298Z2 | |
| /05 | 0.25 |
| /06 | 0.22 |
| E299DD/P116 | |
| P454 | all 0.23 |
| E299HD | |
| /P230 | 0.92 |
| VA1015 | 0.72 |
| VA1033/34/38 | |
| 39/40/53 | all 0.20 |
| VA1055/56/66/63 | |
| 67s | all 0.25 |
| VA1074 | 0.20 |
| VA1077 | 0.31 |
| VA1091 | 0.29 |
| VA1096/97/98 | all 0.20 |
| VA903 | 0.32 |
| VA1104 | 0.26 |
| VA1108/09/10 | all 0.64 |
| VA1112 | all 0.24 |
| VA6650 | all 1.20 |
| V2322 554 | |
| 02221 | 0.59 |

| MAINS POWER SUPPLY | |
|---|---------------------|
| Integral 13A 3-pin Plug terminating with 3.5mm Plug | 14 pin 0.10 0.70/10 |
| 240V, 12V 250mA PRICE £3.25 | 16 pin 0.11 1.00/10 |
| Each; £30.00/10 | 22 pin 0.21 1.95/10 |
| | 28 pin 0.30 2.75/10 |
| | 40 pin 3.10/10 |

| I.C. SOCKETS | |
|--------------|--------------|
| D11 to D11 | |
| 8 pin | 0.08 0.70/10 |
| 14 pin | 0.10 0.95/10 |
| 16 pin | 0.11 1.00/10 |
| 22 pin | 0.21 1.95/10 |
| 28 pin | 0.30 2.75/10 |
| 40 pin | 3.10/10 |

| TERMINAL BLOCKS | |
|-----------------|------|
| 2 amp 12 way | 0.19 |
| 5 amp 12 way | 0.20 |
| 10 amp 12 way | 0.46 |
| 15 amp 12 way | 0.46 |
| 32 amp 12 way | 0.46 |

| CO-AXIAL CABLE | |
|-----------------|---------------|
| 50ohm UR43 type | 34p per metre |
| 75ohm UR02 type | 22p per metre |

| PRESETS | |
|----------------------|--|
| 0.25V Time 100R-4M7 | |
| V & H 10p ea. 10/90P | |
| 0.1V Time 100R-1M | |
| V & H 7p ea. 10/65P | |

| MINIATURE MULTI-CORE | |
|----------------------|---------------|
| 4-core | 37p per metre |
| 9-core | 46p per metre |

| CHART RECORDER SPECIAL | |
|--|--|
| brand new 3 channel pen recorders complete with charts. Full spec. upon request once only price £40 + £10 p/p & VAT. | |

| FUSEHOLDERS | |
|-----------------------|------|
| 20mm Panel Mounting | 0.28 |
| 20mm Chassis Mounting | 0.06 |
| 1" Panel Mounting | 0.35 |
| 1" Chassis Mounting | 0.12 |
| Carline 1" holder | 0.10 |

| SERVICING AIDS | |
|------------------------------------|--|
| ALL SERVICING PRODUCTS | |
| Switch Cleaner 0.88 | |
| Circuit Freezer 0.88 | |
| Foam Cleanser 0.84 | |
| Aero Klene 0.78 | |
| Silicone Grease (Aerosol) 1.00 | |
| Antistatic Spray 0.82 | |
| Static Seal 0.88 | |
| Excel Polish 0.76 | |
| Fire Extinguisher 2.98 | |
| 640g 2.80 | |
| Video Head Cleaner 0.88 | |
| Silicone Grease (IC) 75g tube 1.00 | |
| Solder Mop (Std) 0.72 | |
| Solder Mop (L Gauge) 0.72 | |
| Additional P&P on above 30p | |

| REPLACEMENT TV MAINS DROPPERS | |
|---|------|
| GEC2010 8R + 15R + 17R + 70R + 63R + 188R | 0.95 |
| GEC 2018 10R + 15R + 19R + 70R + 188R | 1.15 |
| Philips GB 21R + 98 R | 1.18 |
| Philips 70 6R + 124R + 84R | 0.80 |
| Philips 300 118R + 148R (with link) | 0.85 |
| Philips 300 30R + 125R + 2.85K | 1.08 |
| RRI A640 250R + 14R + 156R 50W | 1.05 |
| RRI A816 302R + 70R + 6.2R | 0.78 |
| Thorn 1500 2.50R + 20.4R + 146R + 1.5K + 317R | 0.90 |
| Thorn 3000/3500 6R + 1R + 100R Fuse | 0.95 |
| Thorn 8000 56R + 1K + 47R + 12R | 0.95 |
| Thorn 8500 1K5 + 40R + 50R | 1.28 |

| VEROBORD | |
|-------------------------|------------------|
| 2" x 3" 0.1in. Clad | 1.83 |
| 2" x 5" 0.1in. Plain | 0.95 |
| 3" x 3" 1.05 DIP Board | 3.85 |
| 3" x 17" 3.25 HAND HELD | 1.15 |
| 4" x 17" 4.10 CONTROL | 1.75 |
| 4" x 17" 4.95 BOXES | 0.75 |
| Pkt. of 10 pins 50 | Vero Writing |
| Spot face cutter 1.48 | Pen + spool 3.50 |

| RESISTORS - CARBON FILM 5% | |
|----------------------------|------------------|
| 1W 1R0 to 10M (E12 Range) | 2p each. 15p/100 |
| 1W 2R2 to 10K (E24 Range) | 2p each. 15p/100 |
| 1W 10R to 2M2 (E12 Range) | 7p each. 85p/100 |
| 2W 10R to 2M2 (E6 Range) | 8p each. 70p/100 |

| RESISTOR KITS - each value individually packed | |
|--|-------|
| 1W pack 10 each value E12 - 10R to 1M 610 pieces | 5.00 |
| 1W pack 5 each value E12 - 10R to 1M 305 pieces | 3.00 |
| 1W pack 5 each value E12 - 2R2 to 2M2 365 pieces | 6.00 |
| 1W pack 5 each value E12 - 2R2 to 1M 353 pieces | 3.50 |
| 2W pack 5 each value E6 - 10R to 2M2 317 pieces | 18.00 |


| RESISTORS - WIREWOUND Generally 5% | |
|---|------|
| 2.5W - 0.22 to 270R - Available in preferred values | 0.20 |
| 1.5W - 1R to 10K - Available in preferred values | 0.21 |
| 0.3W - 0.47R to 22K - Available in preferred values | 0.25 |
| 11W - 1R to 22K - Available in preferred values | 0.29 |
| 17W - 1R to 22K - Available in preferred values | 0.37 |

| D CONNECTORS | |
|--------------------|----------------|
| 9 15 25 | |
| 55 way way way way | |
| Male | |
| Solder | 75 1.00 1.50 |
| Angle | |
| 1.40 2.00 2.40 | |
| Female | |
| Solder | 1.00 1.45 1.85 |
| Angle | |
| 1.50 2.00 2.40 | |
| Covers | |
| .80 .80 .80 | |

1984 CATALOGUE AVAILABLE - Many prices reduced - range increased - fully illustrated. Price 65p, per copy (free upon request with orders over £5) - includes 30p. Credit Note, special offer sheets, order form and pre-paid envelope. SEND NOW FOR YOUR COPY.

TRANSISTORS + DIODES

| Type | Price (£) | Type | Price (£) | Type | Price (£) | Type | Price (£) | Type | Price (£) | Type | Price (£) | Type | Price (£) | Type | Price (£) | | |
|----------|-----------|--------|-----------|-------|-----------|--------|-----------|--------|-----------|-------|-----------|-----------|-----------|-----------|-----------|--------|------|
| BY802 | 0.88 | AC127 | 0.30 | BC108 | 0.10 | BC302 | 0.32 | BD244A | 0.65 | BF258 | 0.30 | BT101/300 | 1.15 | BYX36/150 | 0.22 | TP32 | 0.40 |
| BY963/87 | 0.88 | A12 | 0.34 | BC109 | 0.10 | BC303 | 0.32 | BD3375 | 0.65 | BF259 | 0.32 | BT102/500 | 1.25 | BYX36/600 | 0.28 | TP32C | 0.60 |
| EC81 | 0.95 | AC128K | 0.34 | BC113 | 0.14 | BC307 | 0.10 | BD410 | 0.10 | BF262 | 0.30 | BT102/300 | 1.35 | BYX48/300 | 0.72 | TP33A | 0.63 |
| EC82 | 0.65 | AC132 | 0.55 | BC114 | 0.12 | BC308A | 0.10 | BD434 | 0.68 | BF263 | 0.30 | BT102/500 | 1.65 | BYX49/300 | 0.47 | TP34A | 0.72 |
| EC83 | 0.75 | AC141 | 0.26 | BC115 | 0.12 | BC323 | 0.99 | BD436 | 0.68 | BF270 | 0.30 | BT106 | 1.50 | BYX55/350 | 0.29 | TP41C | 0.46 |
| EC84 | 0.65 | AC141K | 0.40 | BC116 | 0.15 | BC327 | 0.14 | BD437 | 0.76 | BF271 | 0.26 | BT108 | 1.30 | BYX55/600 | 0.33 | TP42A | 0.52 |
| EC85 | 0.90 | AC127K | 0.26 | BC117 | 0.17 | BC328 | 0.14 | BD438 | 0.76 | BF272 | 0.18 | BT116 | 1.16 | BYX57/600 | 0.42 | TP47 | 0.60 |
| EC88 | 0.95 | AC128K | 0.18 | BC118 | 0.17 | BC337 | 0.12 | BD439 | 0.68 | BF274 | 0.32 | BT116 | 1.25 | BZ12 | 0.42 | TP110 | 0.88 |
| EC90 | 0.95 | AC151 | 0.45 | BC119 | 0.30 | BC338 | 0.12 | BD507 | 0.48 | BF323 | 0.92 | BT119 | 3.62 | C106D | 0.80 | TP195 | 0.88 |
| EC91 | 0.75 | AC152 | 0.45 | BC125 | 0.12 | BC350 | 0.14 | BD508 | 0.53 | BF336 | 0.26 | BT120 | 3.60 | E122 | 0.40 | TP295S | 0.60 |
| EC94 | 0.75 | AC176 | 0.28 | BC140 | 0.28 | BC440 | 0.30 | BD509 | 0.54 | BF337 | | | | | | | |

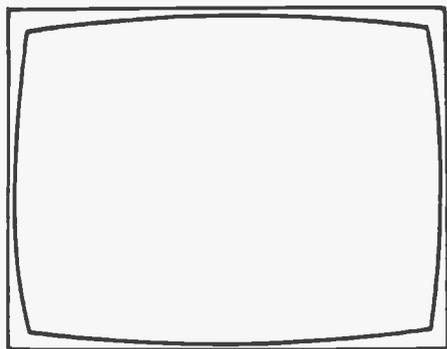

TELEVISION

Lessons from the Japanese

The effect that Japanese consumer manufacturing companies have had on standards of quality and reliability world wide is now appreciated by all. So much so that the question is why US and European companies lagged behind for so long? The fact seems to be that manufacturing, certainly in the consumer sector, had become something of a shambles in the west during the fifties and sixties. There was a happy go lucky approach and an understanding that when things went wrong the dealer would put them right. So we had stock faults, cars that were never right from new and so on. Inevitably there was a backlash and the consumer movement was born.

This dilatory approach to quality control didn't do for the Japanese at all. For their mass produced goods to be accepted world wide they had to work correctly from new and keep on working. Distance and the language problem made it difficult to rely on dealer networks to sort out the problems, but quite apart from this there was a different emphasis in Japanese manufacturing firms. The shop floor was seen as the centre of the operation and all attention was focused on it. The Japanese have an extraordinary aptitude for organising production. Not only efficient production lines but stock control, manning, quality control and everything else. Everyone concentrated on getting the product right, which meant producing it right. Contrast this with what tended to happen in the west. There, getting the product right meant market research, finding out the subconscious motives of prospective purchasers and so on. So emphasis was placed on the look of the product and its "sales features". The shop floor was left to take care of itself - you'd probably get trouble with the foreman or union if you interfered too much anyway. Salesmen, nay marketing men, concentrated on putting the firm's image across, accountants concentrated on making a profit, and production was supposed to come up with something or other in the required quantity at the appropriate time - the pre-Christmas rush, the spring sales boom and so on.

A vast mythology grew up over this - the supposed sex appeal of cars for example. The sales manager was assumed to know what he was about: his graphs showed when sales peaked, and production was organised to suit. Let's not belittle salesmanship however. It had become quite an art in the west and to some extent the engine of economic growth.

Because of cultural differences, this approach didn't suit the Japanese. Japanese women are regarded in a very Victorian light, so you don't devote time to getting the sex appeal of the latest car, stereo or whatever right. The emphasis in the highly ordered Japanese society is on the firm, and within the firm on production. It's interesting that the Japanese have been able to apply this technique wherever they've set up - and Japanese consumer goods manufacturers have now spread their operations around the globe. For geo-economic reasons, Japanese manufacturers had to be export orientated, but it was appreciated that you couldn't simply flood the west and destroy jobs there. That way the public wouldn't be able to buy the goods. So production lines were set up in the USA, the UK and elsewhere - the Japanese had learnt about the dangers of protectionism in the thirties. From being export orientated, Japanese manufacturers became multinational.

This fitted in rather neatly with the west's ability at salesmanship. Couple the latter with Japanese manufacturing ability and you've a sure formula for success. It's ironical that western sales organisations have contributed so much to the success of Japanese manufacturing concerns. But western countries would have been in difficulty had they come to rely on Japan as the consumer goods workshop of the world. Could Japanese manufacturing ability be exported? Could something so rooted in Japanese attitudes be successfully transplanted?

The answer as we know is yes. The story of Japanese success in this direction is an interesting one - with the same fundamental emphasis placed on the shop floor. The Japanese approach has not been rigidly applied elsewhere however - you don't start the day in Devon or California by singing the company song, and local management is left to get on with it subject to the overall requirements of quality control and efficient production.

It's interesting that the Japanese seem to have a different time scale to that usual in western countries. A fascinating report in the *Financial Times* recently chronicled Matsushita's approach to getting established in the USA. The story has parallels in the UK. Rather than start up in open competition on a green field site, the decision was taken to buy market share. By great good luck this suited Motorola, whose technical and manufacturing interests were moving in other directions. So in 1974 Matsushita took over Motorola's rundown TV plant in the suburbs of Chicago - and then spent some ten years getting it right!

Whilst being flexible, it seems that Japanese control has to be total. Hence Plymouth worked once Rank had left it to Toshiba but the joint GEC-Hitachi operation at Hirwaun failed to work successfully. It will be interesting to see how things develop now that GEC have pulled out.

Japanese concentration on the manufacturing process seems to be coupled with an element of benign neglect elsewhere. In another recent *Financial Times* piece Shizuo Takano, senior managing director of JVC, commented on the lack of auditing in Japanese companies. "We do have auditors but, to be honest, they don't do very much"! With that sort of management approach, it's not surprising that Japanese firms can adopt a longer time scale than is usual in the west!

EDITOR

John A. Reddihough

ADVERTISEMENT MANAGER

Roy Smith
01-261 6671

CLASSIFIED ADVERTISEMENTS

Barbara Blake
01-261 5897

CORRECTION - SONY KV2000UB

Under the heading "power supply fault finding" in Part 1 last month the advice was given to start off at about 150V a.c. from a variac. This should have read about 110V. It's important to start at 110V and then increase the input voltage gradually.

BUMPER ISSUE!

Watch out for our October issue which will contain extra pages and a data card listing AV in/out connections for the majority of VCRs that have been sold in the UK.

FRONT COVER

This month's cover photo shows an engineer carrying out VCR tests in the Thorn-EMI-Ferguson video laboratory. Our thanks to Ferguson for their assistance.

The Salora Ipsalo-2 Circuit

The Salora Ipsalo-1 circuit was described in the September 1980 issue of *Television* and was employed in versions of the Salora G chassis up to serial number 300,000 and versions of the H chassis up to serial number 200,000. To recap, Ipsalo stands for integrated power supply and line output, i.e. it's an ingenious circuit in which a single transformer is used as the switch-mode and line output transformer while also providing mains isolation. The aim is reduced power consumption. In the Ipsalo-1 circuit two thyristors were connected in series with the transformer's primary winding, one providing protection and a soft-start action while the other acted as the chopper device to provide regulation. Hence two separate driver transformers were required.

Now thyristors have tended to become unpopular for use as switching devices in TV sets. They're more difficult to control than transistors, and tend to produce interference. So transistors have come to predominate in power supplies and line output stages. The Ipsalo-2 circuit, which is used in later versions of the G and H chassis and the current J chassis, is an example of this tendency. The thyristors are out, replaced by a couple of switching transistors, while a single driver transformer (with separate secondaries) further simplifies matters.

A simplified circuit of Ipsalo-2 is shown in Fig. 1. At switch-on the mains bridge rectifier DB708-711 produces a 320V supply across the reservoir capacitor CB721. This is smoothed by RB713/CB722. Once the circuit comes into operation, the switching transistors TB700 and TB701 connect the primary winding of the transformer MB500 across this supply when they are switched on. As

with any switch-mode power supply, the energy delivered to the secondary windings on the transformer is controlled by the on/off times of the switching arrangement, in this case the two transistors TB700/1. By using a pulse-width modulator whose output mark-space ratio is controlled by feedback, regulation is achieved. Energy saving is provided by the diodes associated with the two switching transistors. When the transistors are switched off, the voltage across the transformer's primary winding will try to reverse. DB705 and DB704 will then conduct, returning the unused energy to the smoothing capacitor CB722. DB703 and DB706 conduct on the overshoot.

The line oscillator provides trigger pulses for both the chopper control and the line drive circuitry. The action of the line output stage charges CB513 to 142V.

Since the set's supplies are derived from the secondary windings on the transformer, a start-up system is required. A neat arrangement is used for this purpose. At switch-on CB715 will charge via RB734/716/715. When the voltage across it reaches some 35V the diac DB725 will fire, discharging CB715 (partially) and providing TB701 with base drive. TB700 is driven by transformer action. When the voltage across CB715 has fallen to 25V DB725 and the transistors switch off. As a result of this action a 10V p-p sawtooth drive waveform is developed across CB715. This mode of operation enables DB504 to produce a 28V supply across CB510. The 28V is fed to a simple emitter-follower regulator in the switch-mode control circuit (within the thick-film hybrid i.c.). This produces an 8.5V start-up supply for the control circuit and the line oscillator and driver stages. Once the line oscillator gets going,

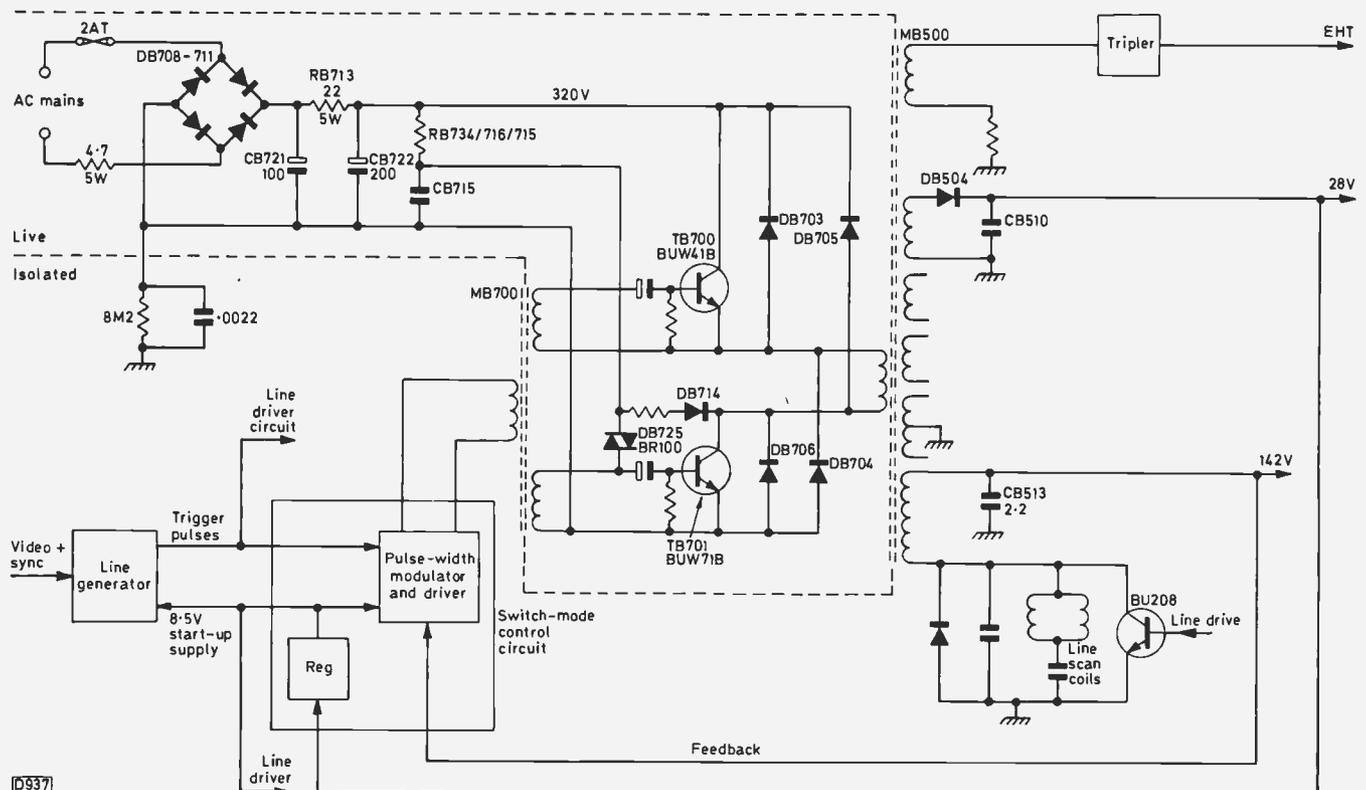


Fig. 1: Simplified circuit/block diagram of the Salora Ipsalo-2 system.

full operation commences. The start-up system is then disabled since DB714 switches on each time TB701 conducts, ensuring that the charge on CB715 doesn't reach the level at which DB725 fires. During normal operation the line oscillator, driver and switch-mode control circuit are powered by 15V/12V supplies derived from another secondary winding on the transformer.

The switch-mode control circuit consists of a bistable multivibrator (the pulse-width modulator) and a driver transistor for transformer MB700 plus extra bits for regulation etc. Regulation is achieved by using an RC charging circuit which is fed from the 142V h.t. rail, i.e. the supply to the RC network is proportional to the e.h.t. The 8 μ sec trigger pulses from the line oscillator are used to discharge the capacitor in this RC network. The capacitor then charges at a rate depending on the supply to the network. When the voltage across the capacitor has risen

sufficiently, the bistable is triggered. The width of the output pulse from the bistable is thus dependent on the e.h.t. This arrangement also provides the soft-start action, the h.t. voltage building up gradually after switch-on. In addition, overload protection is incorporated by bringing a zener diode into operation under overload conditions to disable the RC charging network.

The short (8 μ sec) trigger pulses provided by the line oscillator necessitate some complication in the line drive circuit. A monostable multivibrator is used to stretch the pulses before application to the line driver transistor, the width control being incorporated in the monostable's RC timing network. To obtain a standby condition, an inverter is powered and used to invert the input to the base of the line driver transistor. As a result, the switch-mode and line output sections of the circuit operate with the wrong phase relationship and the energy is drained from the line side.

CCTV Commentary

Andy Denham

When I heard that EMI had sold their camera interests to Frowds of Portsmouth, my first hope was that the new owners would introduce some improvements. Having almost always worked on the Surveyor II in pouring rain atop a 20ft pole, I've on many occasions cursed the lack of access. I eventually came to the conclusion that the only way to work on the beast was to take a spare panel to the site, fitted with some coaxial cable and mains flex, and take the camera down for removal to an on-site workshop. Most of our cameras are fitted with silicon diode tubes, so they usually have a motorised lens with remote lens control for zoom and focusing, and usually a remote iris servo amplifier. These extras demand a highly technical piece of equipment for testing – a PJ996 battery lantern. This completes the test equipment.

We were recently asked to update and add to an existing installation, using Surveyor IIs, so it was with some misgivings that I fitted three of them from Frowds. Access is still difficult, and the old complaint that the camera has to be dismantled for access to the interior still holds. Once inside, we had to fiddle with nuts and bolts to set up the camera with its large lens assembly. The modified video circuit seemed to give better results than the original version, and the internal iris servo is very good. All in all however this is still the familiar EMI camera.

The Surveyor VI

More recently still a Surveyor VI arrived from Frowds. I carefully unpacked all the boxes – sun shield, wiper unit, washer unit and, in the last box (of course), the camera itself. The first thing we noticed was the change to plugs and sockets at the rear of the housing – no more dicky edge connector. Perhaps the only minus point here is that pan head connections can no longer be made at the rear of the camera unless you are using the internal telemetry. Access is much improved: by simply removing four screws the innards slide out of the housing, complete with the lens assembly.

The only external control is still mechanical focusing, which positions the tube for the lens in use. Our camera

sported a massive 15-150mm 10:1 zoom lens, with motorised gearing fed from a socket at the rear of the camera.

A quick look through the technical specification showed some improvement on the earlier design. As usual, the sync can be by crystal, mains lock or external gen-lock. The standard is CCIR 625 lines 50Hz, or EIA 525 lines 60Hz, with 2:1 interlace in both cases. Internal protection is provided in the event of scan failure or excessive tube heater voltage, and the heater is soft-started to improve its life. The h.t. is not applied until the heater reaches its normal temperature, improving tube reliability. Links on the SPG board enable 900V to be selected for high-resolution tubes, e.g. vidicons and Newvicons, or 500V for silicon diode tubes.

The camera consumes only 14W, plus 4W for the window heater, and can be run off 200-250V 50/60Hz or 100-125V 50/60Hz a.c. supplies, or 24V a.c. (50/60Hz) or +12V/-12V d.c. supplies with slight modification (a single rail 12V version is to be made available later).

An internal telemetry panel that takes control commands via the coaxial cable is available as an optional extra.

In my opinion a much improved camera.

Hitachi Monochrome Monitors

Some servicing experiences with the Hitachi VM905-910 range of monitors are worth relating. The cause of cogging/line tear can often be traced to the boost reservoir capacitor or alternatively the line output stage supply filter capacitor. These are both electrolytics of 220/330 μ F. The usual cause of no line scan (line down the middle of the screen) is failure of the non-polarised electrolytic line scan coupling capacitor (3.3/4.7 μ F). No e.h.t. is often due to the U06C boost diode being dry-jointed. If you need to replace the boost diode, a BY298 is a suitable alternative. For no or weak sync, check the sync separator transistor's base coupling and emitter decoupling electrolytics. In the event of no or smeary video, poor contrast or shading on the left-hand side, check the video output transistor's h.t. supply decoupling capacitor. For no field scan/cramping, check the 1,000 μ F field scan coil coupling capacitor. In the 906/910 poor field linearity/lack of height can be caused by the 10 μ F coupling capacitor connected to the slider of the height control. In the 905/909, severe field foldover can be caused by the 100 μ F coupling capacitor to the base of the field output transistor. All these capacitors are electrolytics.

Tiny Tim's Dilemma

Les Lawry-Johns

Tiny Tim sat on his bench stool and looked at his little feet swinging beneath. He looked back at his desk, at what was causing him such acute pain. His bank statement said he'd a small amount in his current account. The income tax man said he owed a great deal more. The VAT was due and the wholesalers' statements completed the mess.

What was Tiny Tim to do? Go into the red? He already owed the bank a lot of money for something else, so he didn't feel inclined to throw himself on their mercy any more – even if they would play with him. He could throw himself off a cliff, but that might hurt. So Tiny sat and pondered. It was easier than working. After all, he'd worked his little fingers to the bone for more years than he could remember, not even having a day off, except Christmas Day that is. Even then old Fred had brought his set in at seven o'clock one Christmas night, which made Tim very angry though he didn't show it – good will to all men, except Fred. Now, after all that work, what had he to show for it? A nasty great tax demand for a start.

War Effort

Tim thought of the time years ago when he didn't have to work so hard. On D-day, when the soldiers were storming ashore amidst all that flack, Tiny Tim was in Gibraltar unpacking Blackburn Barracudas from their crates and helping to assemble them. He then helped to take them to bits again for crating and sending on to India. This procedure had puzzled Tim until he was told that they were originally unpacked and flown to India. As they needed a complete overhaul when they arrived it had been decided to ship them all the way instead. But no one had issued an order to stop the unpacking. So they were unpacked and built, then unbuilt and repacked and put on another boat. Thus Tim's war effort never received the acclaim it deserved. But the sun had shone and Tim had got his knees brown and had been repeatedly thrown out of the bars on Main Street – because he didn't like the pianist playing the White Cliffs of Dover and kept throwing a chair at him.

He'd done the same thing in Alexandria and got thrown out of the bars in Beer Street. This was the time when Subby Thomson was shooting down those Junker JU52s that dropped the cornettos over Benghazi. Oh dear how Tim's little mind rambles on. He was young then, and naughty of course. Tales have it that he should be blind, but instead he's just short-sighted. He got fed up last year, not being able to see properly through his glasses which he's repeatedly mended for the last twenty years or so. So he went off to see the man who makes you see better and ended up with an expensive pair of spectacles that enabled him to see a bumble bee about a mile away. He was so pleased, until he discovered that he couldn't see anything less than two feet away. So his nice new glasses remain in their case and he still has to wear his battered ones.

Tim sat and looked at his feet, or rather his shoes. His old shoes. He'd like some new ones, even if they did come from Italy. But he certainly couldn't afford to buy a pair with all this tax hanging over him – especially since Tinker

Bell had demanded a new gas cooker, and had got it of course. So he'd have to put up with the pebbles hurting his little feet as he walked his dog across the car park to where Peter Ripley parks his nice new car. Peter always laughs when he sees Tim, and Tim's glad he's so happy. Must be something to do with his wife being so pretty and all that.

Memories of FJC

Tim scolded himself for being so selfish. He mustn't want new things when he can make do with old ones. He remembered being scolded by F.J. Camm, the original editor of *Television*. F.J. had told him off for sending in too high an account for answering readers' queries. "Two and sixpence is too much, especially as they are mainly repetitive." So Tim had knocked ten per cent off each monthly account for a while. For a little while.

F.J. was a formidable man. Someone not to be trifled with. After all his brother Sidney Camm had designed those lovely Hawker aircraft, including the Hurricane which Subby Thomson used to shoot down the JU52s. Yes indeed, F.J. was a man to be reckoned with in the Practical days. Not at all like the present editor who is kindly and helpful, always ready to cut large tracts of nasty bits out of Tiny Tim's articles so as not to offend our readers, who are such sensitive souls. I bet they didn't get slung out of the bars in Alex during the war. Or in Gib.

Thirty Years Ago

Tim remembered the very first article he'd submitted to F.J., thirty years ago in 1954. On servicing the HMV 1807. Tim had suggested that this could form the start of a series on servicing TV receivers – practical hints on commercial models. "We shall require more than one to start a series" came the reply, "so we suggest you submit a further three or four." Tim struggled and came up with a further couple of hundred or so and blushes to think how serious he was, studiously writing them all with his little pen because he couldn't afford a typewriter. Tinker Bell bought him one for Christmas some years ago, so that he could earn more money to buy gas stoves and things like that.

So it was that in September 1954 we kicked off: "This series of articles is designed to help those who possess a commercial set of popular make, or who may be asked to help in the servicing of such a receiver. The whole point of these articles is that nearly every television set possesses its own peculiarities which, if known, make servicing much simpler. Time and again the same faults crop up with surprising regularity." There was a lot of "kitchen table" servicing back in the days when sets were cumbersome but amenable and service engineers were few and far between. We've come a long way together since then.

Back to Earth

After a sleepless (almost) night Tim came down to see what bills the postman had brought to upset him further. A nicely typed letter caught his eye. It was from his accountant. "Don't pay that tax demand Les (I mean Tim). It's a mistake and you've paid too much already. Wait until you hear from them to confirm our figures." Oh Glory be, Glory be – and a nice new pair of shoes. The little angel that used to sit on Tim's shoulder and look after him is still there after all. And Tim thought the bitch had gone.

POST A PART ELECTRONICS

236 FURTHERWICK ROAD,
CANVEY ISLAND, ESSEX
Telephone 0268 690868
Telex 99305 ROSSER G.



TRADE COUNTER NOW OPEN

ORDERS DESPATCHED SAME DAY
ADD 60p P&P, THEN 15% VAT.

ADD POSTAGE FOR OVERSEAS ORDERS.
ORDERS WITH AEROSOLS, PLEASE ADD 25p PER CAN.

| | |
|--|-------------|
| Thorn 100 20W (3500) R751 Safety Resistor | 75p |
| Pye 713 Speaker 5" x 3" 70Ω | 1.00 |
| Pye 713 Complete Tube Base Panel with Focus Slider & Leads | 2.75 |
| Pye 713 Control Knobs | 4 for 50p |
| Tube Base Socket ITT CVC32 | 45p |
| Tube Base Socket Thorn 3000/8000 etc | 50p |
| IC Inserter 16 Pin | 50p |
| Large IC Extractor | 50p |
| Crystal 4.43MHz | 65p |
| EHT Lead & Cap for Split Diode Lopt | 90p |
| Anode Cap | 47p |
| Sanyo Anode Cap Assy + Lead. 12TCD-CT-10 | 65p |
| Degauss Thermistors PT37P. ITT/GEC | 35p |
| Degauss VDR E2990/HP230 3000/8000 | 1.90 |
| Casters Set of 4 | 25p |
| Double Fuse Holder on Small Pax Board 20mm type | 10p |
| Single Fuse Holder on Small Pax Board 20mm type | 5p |
| Direct Panel Mounting 20mm Fuse Clips (pair) | 15p |
| Single Fuse Holder on Small Pax Board. As per early 3000 mains input | 6p |
| EHT Cable | Metre 25p |
| 13A Plugs | 12 for 4.80 |
| BF259 with Heatsink | 14p |
| TP110 with Heatsink | 10p |
| L129/130/131 Coil | 40p |
| 8MHz Ceramic Filter | 25p |
| DL700 (Philips) Chroma Delay Line | 1.00 |
| OL50 Chroma Delay Line | 1.00 |
| 1906GA Lum Delay Line | 1.00 |
| 8K5/9K Lum Delay Line | 65p |
| Plastic Cover for 3K5 SP3885 | 5p |
| TX9 Back Ground Control 10K | 15p |
| TX9 Gain Control 100R | 15p |
| 1500 Metal Chassis Supports Pair | 10p |
| Thorn 8K5 Focus Pot | 2.40 |
| Thorn 4000 Focus Pot | 2.75 |
| Thorn 18Ω 9W (3K5) R752 | 30p |

SERVICE AIDS

| | |
|-------------------------------------|-------------|
| Ambersil MSA Silicone Grease | 12oz 2.15 |
| Ambersil Freezer | 12oz 1.99 |
| Ambersil Ambrube | 6oz 1.89 |
| Ambersil Ambertron | 16oz 1.95 |
| Ambersil Anti-Static Screen Cleaner | 7oz 1.95 |
| Ambersil 40+ Protective Lubricant | 14.1oz 2.15 |
| Ambersil Ambrudens Foaming Cleaner | 13oz 1.26 |
| Ambersil Circuit Lacquer | 14oz 2.15 |

THICK FILM RESISTOR UNITS

| | |
|-------------------------------------|------|
| 3500 Thorn (5 Pin Connection) video | 1.70 |
| 4000 Thorn (4 Pin Connection) | 1.90 |
| 725/731 Pye (6 Pin Connection) | 2.20 |
| 713 Pye (6 Pin Connection) | 2.20 |

FUSES

| | | | |
|-----------|-------------|-------|------------|
| 50MA | 10 for 70p | 250MA | 10 for 65p |
| 315MA A/S | 10 for 50p | 750MA | 10 for 65p |
| 500MA | 10 for 50p | 7A | 10 for 50p |
| 1A | 10 for 50p | 10A | 10 for 50p |
| 2.5A | 10 for 1.00 | 20A | 10 for 50p |
| 3.15A | 10 for 1.00 | 50A | 10 for 50p |

| | |
|---------------------------------|-------|
| Thorn Mains TX 3000/3500 | 7.50 |
| Thorn Mains TX 8000/8500 | 10.00 |
| Thorn S.O.P.T. 8000/8500 | 3.50 |
| Thorn Scan TX 3000/3500 | 6.00 |
| Thorn EHT TX 3000/3500 | 6.00 |
| Thorn LDOPT 9600 | 12.00 |
| Thorn LDOPT 1615 | 7.25 |
| Thorn LDOPT 1590/91 | 7.25 |
| Thorn LDOPT 1690/91 | 7.25 |
| Thorn LDOPT 8000 | 9.80 |
| Thorn LDOPT 8500 | 9.80 |
| Thorn LDOPT TX9 | 9.85 |
| Pye LDOPT 713 | 10.00 |
| Pye LDOPT 725 | 9.85 |
| Pye LDOPT 731 | 10.18 |
| Philips LDOPT G9 | 8.90 |
| Philips LDOPT G11 | 13.75 |
| GEC LDOPT 3113 | 7.40 |
| Diode Split LOPT AT2076/35 | 14.75 |
| Sanyo LDOPT AM-WM-21 | 6.75 |
| Sanyo LDOPT AM-WM-4 | 7.30 |
| Philips LDOPT G8 | 7.80 |
| Sanyo LDOPT (CW21) 4-2751-44700 | 5.00 |
| ITT LOPT CVC5-9 | 9.50 |
| ITT LOPT CVC30 | 8.75 |
| ITT LOPT CVC45 | 9.75 |
| Baird 8752 | 10.25 |
| Korting A29100 | 10.25 |
| Korting B82-170 | 10.25 |
| Korting AZ2101 | 10.25 |
| Korting AZ2103 | 10.25 |
| Korting ZTR1001 | 10.25 |
| Siemens V1155 | 11.75 |
| Siemens V1823 | 11.75 |
| Zanussi BS2222 | 10.25 |
| Zanussi BS2223 | 10.25 |
| Salora FR0057 | 10.25 |
| Salora FR0029 | 10.25 |

| | |
|----------------------------|------|
| 300 Mixed Resistors | 1.50 |
| 300 Mixed Capacitors | 1.50 |
| 150 Mixed Electrolytics | 2.00 |
| 100 W/W Resistors | 1.00 |
| 20 Mixed Conv Pots | 1.00 |
| 40 Mixed Pots | 1.50 |
| 20 Mixed Sliders | 1.00 |
| 40 Mixed Presets | 60p |
| 20 Mixed VDR & Thermistors | 1.00 |
| 20 Mixed Ferrite Cores | 50p |
| 100 Mixed Ceramic Discs | 1.00 |
| 20 Mixed Valve Bases | 1.00 |

| | | | | | | | | | | | |
|---------|------|----------|----|--------|------|--------|----|---------|------|----------|------|
| AC128 | 39 | BC172 | 9 | BC559 | 8 | BF173 | 24 | BFR62 | 28 | NKT276 | 20 |
| AC131 | 40 | BC174B | 23 | BC595 | 8 | BF179 | 29 | BFR81 | 29 | NKT453 | 1.65 |
| AC138 | 40 | BC177 | 24 | BCX33 | 22 | BF181 | 33 | BFR87 | 25 | OT112 | 1.92 |
| AC141K | 39 | BC182L B | 12 | BCX34 | 11 | BF184 | 30 | BFR90 | 1.74 | OT121 | 2.08 |
| AC142K | 38 | BC183L | 12 | BD115 | 49 | BF185 | 30 | BFR91 | 2.08 | RT038 | 8.0 |
| AC153 | 39 | BC184L | 13 | BD131 | 30 | BF194 | 16 | BFX38 | 40 | RT109 | 9.40 |
| AC176 | 33 | BC187 | 24 | BD132 | 46 | BF196 | 16 | BFX50 | 40 | RT200 | 1.10 |
| AC176K/ | 33 | BC204 | 15 | BD133 | 59 | BF196 | 16 | BFY51 | 34 | RT205 | 1.30 |
| AC128K | 93 | BC208 | 9 | BD139 | 36 | BF197 | 15 | BFY52 | 34 | RT206 | 80 |
| AC188 | 38 | BC212L | 9 | BD140 | 38 | BF198 | 19 | BRC116 | 1.50 | RT222 | 50 |
| AD142 | 1.18 | BC213L | 12 | BD144 | 1.70 | BF199 | 15 | BRC1693 | 1.43 | RT243 | 25 |
| AD143 | 1.08 | BC237 | 12 | BD150 | 5.0 | BF223 | 18 | BU105 | 1.00 | RCA16446 | 30 |
| AD149 | 98 | BC238B | 8 | BD163 | 98 | BF224 | 19 | BU126 | 1.10 | RCA16599 | 1.25 |
| AD161 | 32 | BC238L | 8 | BD201 | 74 | BF238 | 20 | BU207 | 1.05 | RCA16600 | 1.40 |
| AD162 | 32 | BC250A | 15 | BD203 | 78 | BF240 | 9 | BU208 | 1.15 | RCA16799 | 1.13 |
| AD263 | 1.05 | BC251 | 8 | BD204 | 99 | BF241 | 21 | BU208A | 1.15 | RCA16800 | 1.42 |
| AF127 | 45 | BC252A | 20 | BD222 | 48 | BF255 | 10 | BU326A | 1.30 | RCA16802 | 1.38 |
| AF139 | 38 | BC294 | 37 | BD225 | 52 | BF256S | 20 | BU407 | 1.70 | S1299 | 2.25 |
| AF239 | 41 | BC301 | 32 | BD232 | 50 | BF257 | 28 | BU408 | 2.76 | S2800U | 1.25 |
| BC107 | 15 | BC303 | 31 | BD233 | 80 | BF259 | 28 | BU500 | 2.30 | S6980A/B | 3.50 |
| BC108 | 15 | BC307 | 10 | BD234 | 50 | BF271 | 25 | BU505 | 2.46 | S6990V | 1.30 |
| BC109 | 15 | BC308 | 8 | BD237 | 55 | BF274 | 11 | BU507 | 2.84 | T602V | 1.30 |
| BC115 | 16 | BC309 | 14 | BD238 | 65 | BF337 | 29 | BU129 | 9 | T9003V | 1.25 |
| BC117 | 21 | BC327 | 18 | BD241 | 59 | BF338 | 34 | CI172B | 9 | T9010V | 1.45 |
| BC125 | 26 | BC328 | 18 | BD244 | 85 | BF355 | 40 | E5386 | 54 | T9053V | 1.30 |
| BC126 | 23 | BC337 | 17 | BD278A | 81 | BF362 | 50 | E9003 | 28 | T9054V | 1.10 |
| BC139 | 27 | BC338 | 17 | BD386 | 68 | BF391 | 21 | E9005 | 25 | T9099V | 1.00 |
| BC141 | 34 | BC347 | 8 | BD433 | 71 | BF394 | 16 | ME0404 | 10 | TIC45X | 50 |
| BC142 | 30 | BC394 | 8 | BD437 | 83 | BF422 | 47 | ME0412 | 10 | TIC46 | 48 |
| BC143 | 31 | BC454 | 8 | BD592 | 1.20 | BF423 | 53 | ME6002 | 10 | TIC106C | 40 |
| BC147 | 12 | BC465 | 8 | BD589 | 1.20 | BF450 | 43 | MJ2501 | 2.36 | TIP29 | 42 |
| BC148 | 12 | BC466 | 10 | BD677G | 1.35 | BF453 | 53 | MJ3001 | 2.21 | TIP30 | 42 |
| BC149 | 12 | BC460 | 40 | BD707 | 95 | BF458 | 57 | MJE182 | 47 | TIP31 | 35 |
| BC153 | 16 | BC463 | 22 | BD708 | 95 | BF459 | 40 | MJE340 | 50 | TIP32 | 43 |
| BC1540R | 16 | BC546 | 8 | BDX10 | 93 | BF461 | 59 | MJE350 | 50 | TIP33 | 61 |
| BC154YL | 16 | BC547 | 12 | BDY20 | 1.09 | BF568B | 35 | MJE295 | 1.10 | TIP41 | 42 |
| BC157 | 12 | BC548 | 12 | BDY82 | 95 | BF586 | 15 | MJE3055 | 1.50 | TIP42 | 45 |
| BC158 | 12 | BC549 | 8 | BF137 | 20 | BF694 | 16 | NKT241W | 8 | TIP110 | 61 |
| BC159 | 15 | BC557 | 10 | BF153 | 20 | BF757 | 62 | NKT241G | 8 | TIS91 | 25 |
| BC171 | 9 | BC558 | 10 | BF154 | 25 | BF852 | 31 | NKT241Y | 8 | ZTX550 | 30 |

| | |
|----------------------------------|------|
| 10 Spark Gaps | 1.00 |
| 10-16 pin Quil IC Socket | 90p |
| 20 Assorted TV Knobs | 1.00 |
| 10-16 pin Quil to Dil IC Socket | 90p |
| 100 Mixed Diodes | 1.00 |
| 50 Mixed Mica Washers | 65p |
| 300 Mixed Resistors & Capacitors | 1.50 |
| 10-16 pin Dil to Dil IC Socket | 1.00 |
| 50 Electrolytics & 50 Capacitors | 1.00 |
| 50 Mixed Poly Capacitors | 1.00 |
| 30 Mixed Neons & Bulbs | 1.00 |

| | | | | | |
|--------|----|---------|------|----------|------|
| BF167 | 24 | BFR62 | 28 | NKT276 | 20 |
| BF173 | 29 | BFR81 | 29 | NKT453 | 1.65 |
| BF179 | 33 | BFR87 | 25 | OT112 | 1.92 |
| BF181 | 30 | BFR90 | 1.74 | OT121 | 2.08 |
| BF184 | 30 | BFR91 | 2.08 | RT038 | 8.0 |
| BF185 | 30 | BFT42 | 30 | RT109 | 9.40 |
| BF194 | 16 | BFT43 | 30 | RT200B | 1.10 |
| BF196 | 16 | BFX38 | 40 | RT210B | 1.10 |
| BF196 | 16 | BFY50 | 30 | RT230 | 1.30 |
| BF197 | 15 | BFY51 | 34 | RT235 | 1.30 |
| BF198 | 19 | BFY52 | 34 | RT206 | 80 |
| BF199 | 15 | BRC116 | 1.50 | RT222 | 50 |
| BF223 | 18 | BRC1693 | 1.43 | RT243 | 25 |
| BF224 | 19 | BU105 | 1.00 | RCA16446 | 30 |
| BF238 | 20 | BU126 | 1.10 | RCA16599 | 1.25 |
| BF240 | 9 | BU207 | 1.05 | RCA16600 | 1.40 |
| BF241 | 21 | BU208 | 1.15 | RCA16799 | 1.13 |
| BF255 | 10 | BU208A | 1.15 | RCA16800 | 1.42 |
| BF256S | 20 | BU326A | 1.30 | RCA16802 | 1.38 |
| BF257 | 28 | BU407 | 1.70 | S1299 | 2.25 |
| BF259 | 28 | BU408 | 2.76 | S2800U | 1.25 |
| BF271 | 25 | BU500 | 2.30 | S6980A/B | 3.50 |
| BF274 | 11 | BU505 | 2.46 | S6990V | 1.30 |
| BF337 | 29 | BU507 | 2.84 | T602V | 1.30 |
| BF338 | 34 | CI172B | 9 | T9003V | 1.25 |
| BF355 | 40 | E5386 | 54 | T9010V | 1.45 |
| BF362 | 50 | E9003 | 28 | T9053V | 1.30 |
| BF391 | 21 | E9005 | 25 | T9054V | 1.10 |
| BF394 | 16 | ME0404 | 10 | T9099V | 1.00 |
| BF422 | 47 | ME0412 | 10 | TIC45X | 50 |
| BF423 | 53 | ME6002 | 10 | TIC46 | 48 |
| BF450 | 43 | MJ2501 | 2.36 | TIC106C | 40 |
| BF453 | 53 | MJ3001 | 2.21 | TIP29 | 42 |
| BF458 | 57 | MJE182 | 47 | TIP30 | 42 |
| BF459 | 40 | MJE340 | 50 | TIP31 | 35 |
| BF461 | 59 | MJE350 | 50 | TIP32 | 43 |
| BF568B | 35 | MJE295 | 1.10 | TIP33 | 61 |
| BF586 | 15 | MJE3055 | 1.50 | TIP41 | 42 |
| BF694 | 16 | NKT241W | 8 | TIP42 | 45 |
| BF757 | 62 | NKT241G | 8 | TIP110 | 61 |
| BF852 | 31 | NKT241Y | 8 | TIS91 | 25 |
| | | ZTX550 | 30 | | |

INTEGRATED CIRCUITS

| | | | | | | | |
|------------|------|-----------|------|----------|------|----------|------|
| BRC1330 | 1.40 | SN78013ND | 1.80 | TBA530 | 1.26 | TDA2002 | 2.80 |
| BRC3064 | 1.00 | SN78023N | 1.80 | TBA540 | 1.20 | TDA2030 | 2.10 |
| BRC/M/200 | 1.00 | SN78033N | 2.00 | TBA550Q | 1.82 | TDA2522 | 2.10 |
| BRC/M/300 | 1.00 | SN78115 | 2.00 | TBA560C | 1.50 | TDA2530 | 2.81 |
| CA3060 | 1.58 | SN78131N | 1.58 | TBA611 | 2.05 | TDA2540 | 3.50 |
| LM1303P | 1.48 | SN78226N | 1.25 | TBA620A | 2.49 | TDA2580 | 3.50 |
| ML231B | 2.20 | SN78227N | 1.00 | TBA750 | 2.50 | TDA2591 | 3.50 |
| ML237B | 2.00 | SN78530P | 1.30 | TBA800 | 1.62 | TDA2611A | 1.95 |
| ML239B | 2.86 | SN78622N | 1.00 | TBA810S | 1.00 | TDA2640 | 2.90 |
| MC1327AP | 1.25 | SN78660N | 80p | TBA810AS | 1.00 | TDA2690A | 1.50 |
| MC1358P | 1.30 | SN78666N | 75p | TBA920 | 2.08 | TDA3560 | 6.00 |
| MC1455P | 18p | SN78744 | 1.92 | TBA950 | 1.95 | TDA9503 | 2.90 |
| MC14516BCP | 60p | TA7117P | 2.00 | TDA1440 | 1.92 | TCEP100 | 3.48 |
| SAA1025 | 7.20 | TA7109AP | 1.80 | TC2A70SA | 1.05 | TEA1008 | 1.95 |
| SAA1124 | 4.50 | TAA611 | 1.40 | TCA270C | 1.05 | MC14429P | 4.50 |
| SAA5010 | 6.00 | TBA120B | 1.20 | TCA270CQ | 1.05 | MC14514 | 5.00 |
| SL432A | 1.00 | TBA120C | 1.20 | TDA1004A | 4.00 | UA758PC | 2.50 |
| SL1430 | 2.50 | TBA120CQ | 70p | TDA1035T | 3.50 | UA1008A | 2.86 |
| SN15846N | 60p | TBA120S | 70p | TDA1037 | 2.72 | ULN2165 | 1.30 |

MANTEL

Manchester's No. 1 in Ex-Rental TVs
Over 2,000 TVs in stock
Special Offer on Working Colour TV's

All sets are Serviced with repolished cabinets ready for sale

| | | |
|-------------------------------------|-------------|-----|
| Philips G8 550s | 22/26 | £45 |
| Philips 18" | | £40 |
| Philips G8 520s | 22/26 | £35 |
| GEC S/State | from | £35 |
| Thorn 17" 8000 | | £30 |
| Decca 30 | 18/20/22/26 | £30 |
| Japanese | from | £30 |
| Many other makes available from £25 | | |

Discount on quantity

Ex Equipment Panels & Tubes Available

Deliveries may be arranged to the North and Scotland.

Ring for quote. Callers welcome.

419 Barlowmoor Road, Chorlton, Manchester 21 2ER.
Tel: 061 861 8501

Some Examples of UNTESTED TVs available

| | | |
|------------------------------|--------|---------|
| Thorn | 10 for | £125 |
| Philips | 6 for | £90 |
| Bush | 6 for | £80 |
| GEC | 6 for | £60 |
| Decca | 6 for | £60 |
| Mono TVs avail. s/s | | £4 each |
| New TV trolley stands. | | |
| All sizes | | £4.95 |
| All Prices subject to V.A.T. | | |

TELETRADERS

Forde Road, Brunel Industrial Estate,
 Newton Abbot, Devon
 Telephone: (0626) 60154

**The Best Quality Sets Available
 Anywhere**

All First Class working order and excellent cabinets.

| | |
|--------------------------------|-----|
| Philips G8 550 | £40 |
| Philips G11 | £85 |
| GEC Solid State | £35 |
| Thorn 3500 Electronic 22" | £35 |
| Thorn 9000 | £60 |
| Thorn 8800 | £45 |
| Thorn 9800 | £55 |
| Thorn 1500 Mono 20" very clean | £6 |

**Full spares back-up of tubes and panels –
 Bulk terms to other wholesalers**

☆ ☆ ☆

THE NO. 1 WHOLESALE IN THE SOUTH

SUMMER TV SALE!

ONLY UNTIL END AUGUST

| PHILIPS 520 | | PHILIPS 550 | |
|-------------|-----|-------------|-----|
| 22" Singles | £14 | 22" Singles | £20 |
| 6 for | £12 | 6 for | £16 |
| 20 for | £10 | 20 for | £12 |
| 26" Singles | £10 | 26" Singles | £16 |
| 6 for | £8 | 6 for | £12 |
| 20 for | £6 | 20 for | £8 |


Further discounts for van loads



Tel Mr Matt Kerr on 0698 282141
 Peacock Cross Industrial Estate
 Burnbank Road
 Hamilton
 Off M74 Motorway

TELEPART

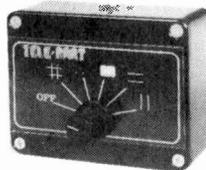13 WORCESTER ST.,
 WOLVERHAMPTON,
 WV2 4LJ
 Tel: (0902) 773122
 Telex: 336810



**Telepart
 Pattern Generator**

- * Exceptionally light and durable
- * Pocket size for outside service
- * PP3 battery power source
- * Five different test patterns for colour and mono TV
- * Cross hatch grid
- * Dot matrix
- * White raster
- * Horizontals
- * Vertices

A lightweight, extremely portable and versatile pattern generator for black/white and colour T.V. alignment and service at the customers home. At the turn of a switch, the generator can provide five essential test patterns for correct installation, fast checks and repairs. Pattern stability is first class and compares favourably with other more costly bulky generators only suitable for bench work. The generator is pocket size measuring 10x7.5x4 cm and weighs only 190 grams.

PRICE £14.95 (Subject to V.A.T.) POST & PACKING £1.45

TV Fault Finding

Reports from Mick Dutton, Jim Rainey,
Tony Thompson, Robin D. Smith and
Malcolm Burrell

Decca 140 Chassis

One or two problems have cropped up recently on this chassis. First, we had a batch of faulty line output transformers. The problem was with the built-in first anode control, which either drifted downhill making the picture dark or uphill causing excessive brightness with flyback lines. The power supply consists of the now familiar self-oscillating chopper with TDA4600 i.c.: we've had several BU426A chopper transistors fail after just a few hours' use, a replacement working perfectly. We've also had two cases of the mica washer behind this transistor breaking down – this is not obvious until the transistor is removed. In this case the symptom was recycling tripping.

One set suffered from very intermittent colour dropout, leaving a green and white display. This was due to the collector tabs of Q211 and Q203 on the tube base panel touching together – the wiring harness had been dressed too tightly, pulling on the components.

R423 (2.2M Ω), which is in series with the field hold control, tends to change value. The result is lack of height or more often field roll with a false lock position when the control is adjusted.

Very occasional failure to start was in one case traced to a crack in the print between D805 and R802 in the start-up circuit.

A set with remote control had a flickering LED display with occasionally no remote control. This was traced to a dry-joint where the lead is connected to the 5V line on the display panel. **M.D.**

Thorn TX9 Chassis

The problem with this 14in. portable (PC1001 main panel) was slight lack of height. Even with the height control at maximum the raster was about half an inch short at the top and bottom. A voltage check at the control showed that the cause was lack of voltage – due to the 3.3M Ω feed resistor R268 having gone high in value. **T.T.**

Fidelity CTV14R

The initial fault was reduced field scan (2½in.) with foldover. Whilst making voltage measurements around the TDA1170S field timebase i.c. the field collapsed then the set tripped and went dead. A replacement chip restored the original fault condition. The linearity control had little effect other than making matters worse, and gentle prodding around the area of the chip restored the picture to normal – though only momentarily. A dry-joint perhaps? I've had them before on this chassis. After running over the area with fresh solder we'd lots of shiny joints but the problem remained. Tap again, same result. No print cracks could be found so component prodding with a plastic knitting needle was resorted to. The culprit turned out to be C706 (10 μ F) in the feedback circuit. **T.T.**

Rank T22 Chassis

The symptom was low brightness, flickering to full brightness intermittently. At times the picture would disappear,

leaving almost total darkness apart from an odd line of colour here and there. It's seldom easy to make voltage checks with an intermittent fault, but the blacked out screen remained long enough for me to discover that the first anode voltages were low. 4R42 (150k Ω) in the first anode supply network was found to have a circular burn, a replacement restoring normal operation. **T.T.**

Philips G9 Chassis

The problem of tuning drift with one of these sets caused us a lot of trouble. Checks on the tuner and tuning control circuit failed to reveal anything of any significance – and the fault wouldn't show up in the workshop. The set went back and forth between us and the customer two or three times before we changed the tuner, which solved the problem. Our local channels are in group A, but the customer was linked to a communal system that uses group C/D channels. It appears that the tuner didn't like operating at the higher frequencies. **R.D.S.**

Rank T20 Chassis

The power supply was working correctly, providing the 200V h.t. line, but the line output stage was dead. A quick check revealed that 5R8, the 1 Ω resistor in series with the line output transistor's base, was open-circuit.

Another fault we had on one of these sets was bad EW bowing with excessive width. The EW loading coil 5L2 had shorted turns. **R.D.S.**

ITT Hybrid CTVs

We still get these sets in occasionally. An unusual fault we had recently was maximum colour saturation with the customer's colour control having no effect. The colour control circuit consists of a bridge arrangement with a tapped coil, a couple of varicap diodes, a capacitive trimmer and a resistive bias network. Various tests on the resistors and diodes were carried out before we decided to try the effect of adjusting the trimmer (C160). A quick turn cleared the fault and after setting it up (for no colour at the minimum setting of the colour control) correct saturation control was achieved. We can only assume that C160 was dirty/noisy.

The fault on another of these sets was intermittent low gain with slight tuner drift. Every day the set would suddenly go low gain (snowy picture). We looked for dry-joints on the i.f. strip and changed the tuner, but the fault persisted. In fact we spent quite a lot of time on it before we discovered that the i.f. preamplifier transistor T13d was faulty. **R.D.S.**

Philips G8 Chassis

The set was dead as a result of a lightning strike. Inspection showed that the earth part of the power supply printed circuit had blown away, and after bridging the print and switching on the h.t. was restored – but there was no e.h.t. Many checks were made to find out why the

– continued on page 594

Servicing the Grundig 2x4 Super

Part 3

Mike Phelan

This month we'll look at the machine's servo and DTF departments. As the V2000 system has been described in detail in these pages before, we'll give just a brief recap on the DTF system.

With DTF (dynamic track following) the video heads are mounted on piezoelectric arms which can be bent to move the heads in the vertical plane to centre them on the recorded tracks. On a basic machine this means that the customer's tracking control is eliminated; on a machine with trick playback facilities there will also be no noise bars on the picture at the various speeds.

The process is in two parts. In the record mode the servos work normally but no control track is laid down. Instead, a master oscillator produces five frequencies (f_1 - f_5) four of which are recorded in sequence field by field along with the luminance and colour signals. The frequencies lie below the lower chroma sideband and are chosen so that the harmonics cause no picture interference. The fifth frequency f_5 is recorded as a one and a half line burst following the field sync pulse. After this the machine goes into playback for one and a half lines: as there's a one and a half line offset between successive tracks, the burst from the previous track may be picked up. If this occurs the head is moved to give greater track

spacing before recording is resumed. Only one head is controlled in this way.

In the playback mode the four frequencies that were recorded in track by track sequence are filtered out. Any crosstalk between a previous or following line produces difference signals which are used to control the head positions. The order in which the frequencies are recorded on successive tracks is $f_1, 2, 4, 3$ (firing order!). The difference frequencies produced by crosstalk between tracks are approximately 15kHz and 46kHz (alternately and opposite from one head to the other) and are filtered out for control purposes. When one head is playing back, the presence of a 15kHz signal will bend it up while a 46kHz signal will bend it down; vice versa for the other head. The output stages that control the actuators (arms on which the heads are mounted) are operated from the $\pm 150V$ rails.

DTF Module

A block diagram of the DTF module is shown in Fig. 6. The microcomputer i.c. (IC2640) is reset every time threading occurs to reset the programme at the start of record or playback. The external clock IC2660 also clocks

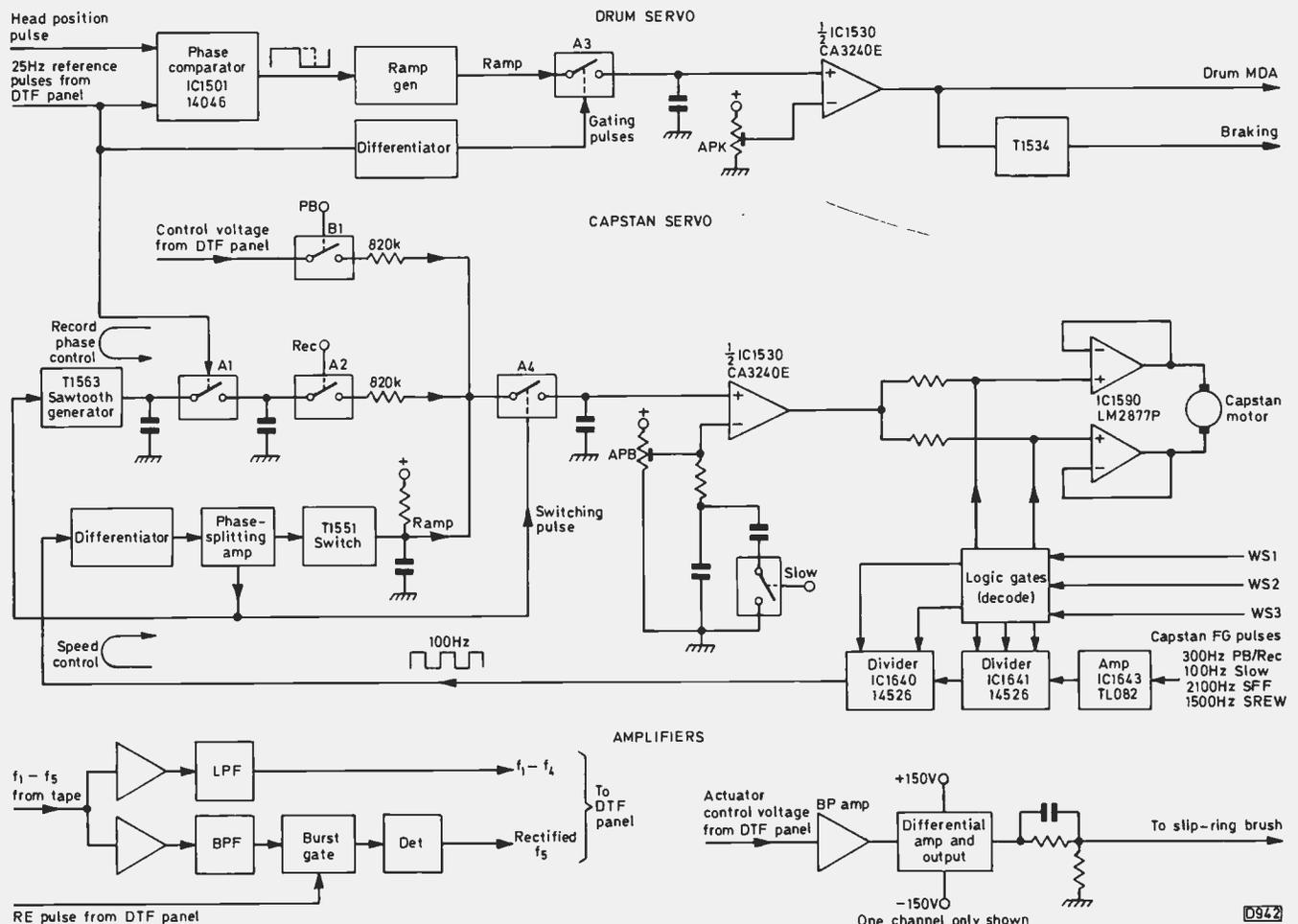


Fig. 5: Block diagram of the servo panel.

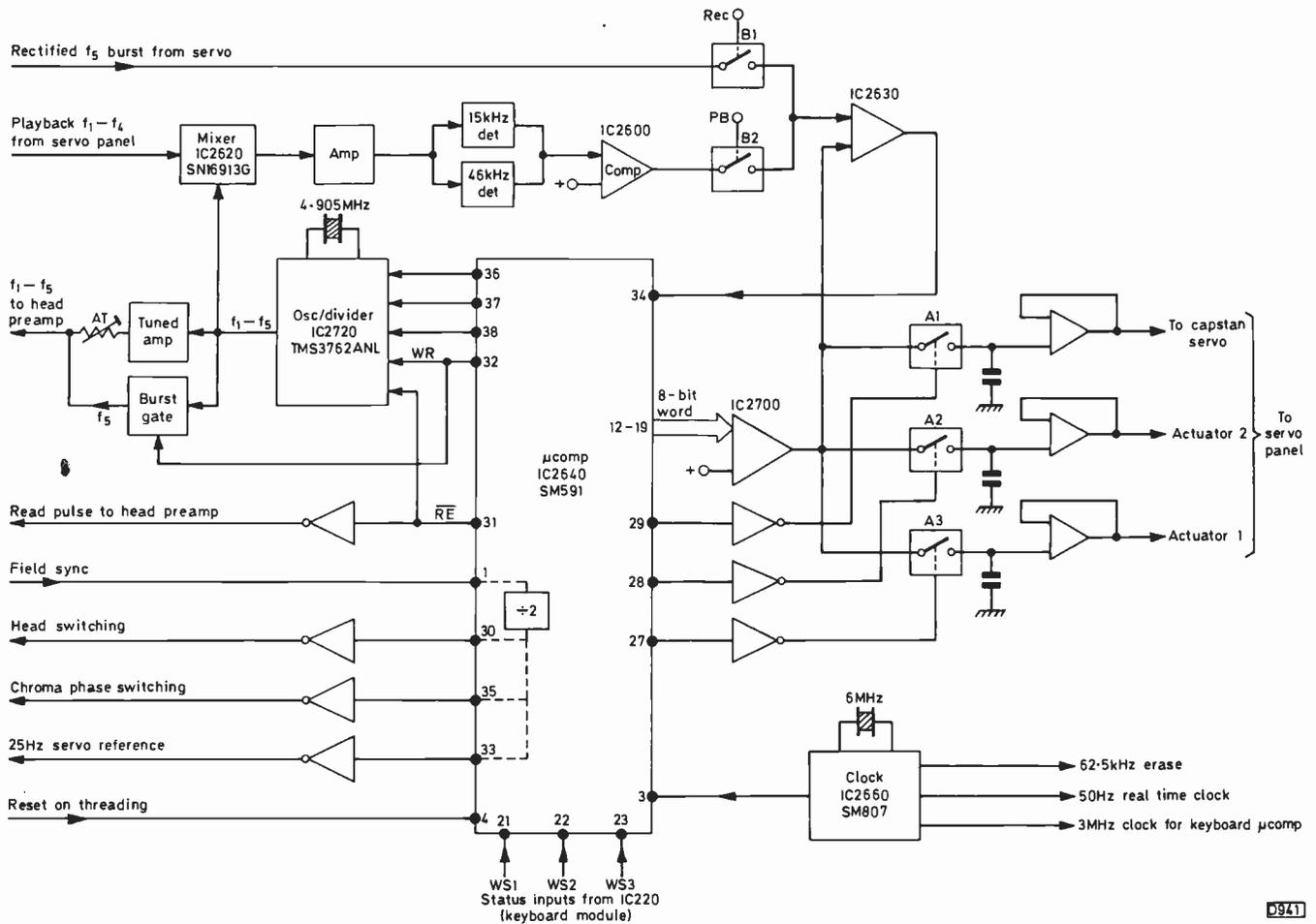


Fig. 6: Block diagram of the DTF panel.

the sequence control microcomputer on the keyboard and supplies the erase head and the real-time clock. A flip-flop divider within IC2640 provides outputs for head switching and chroma carrier phase shifting. This is also used as the servo reference, keeping the component count down.

Pins 36, 37 and 38 of IC2640 programme the divider in IC2720 to give the correct sequence of frequencies, while the WR pulse from pin 32 opens the gate for one and a half lines to record the f5 "burst". The RE pulse follows this to switch the head preamplifier to playback. The off-tape burst is rectified on the servo board and fed via switch B1 to the comparator IC2630 whose other input is fed with a d.c. level from IC2700. As the microcomputer i.c. is a digital device, IC2700 and a resistive network are used as a DAC to convert the 8-bit output to a voltage. This 8-bit word indicates the previous DTF burst's amplitude. So the machine knows how the track spacing is varying and corrects this by moving actuator 2. In the record mode A2 is closed while A1 and A3 are open.

During playback f1-f4 are filtered out by a broadband tuned amplifier and mixed in IC2620 with f1-f4 from IC2720. The output from IC2620 consists of a mixture of 15kHz and 46kHz which is then amplified and rectified. If the proportions of the two signals are unequal, the output from IC2600 goes high or low. This output is passed via switch B2 to comparator IC2630 whose output is fed back to the microcomputer i.c.

The DTF process is not continuous. Sixteen samples per field are looked at, the results being fed back to IC2700 in the form of an 8-bit data word. The outputs from IC2700 go to switches A1-3. A2 and A3 operate on alternate fields, sixteen times per field, the output capacitors hold-

ing the charge between each switch-on. A1 is switched on every 20msec during playback, feeding an output to the capstan servo. We'll return to this later.

Servo Module

A block diagram of the servo module is shown in Fig. 5. Table 1 shows the WS code table - you'll recall that this 3-bit code tells the servo and DTF which mode the machine is in.

The servo circuit is very simple and uses standard linear and logic i.c.s. We'll look at the head servo first. This is a phase control loop only but is slightly different from VHS ones. The two signals to be compared are applied to IC1501. One signal comes from an optodetector on the lower drum, the other from pin 33 of the DTF microcomputer i.c. This latter signal is derived from the field sync pulses on record and from the DTF clock on playback. As the servo operates in the same way in both modes no switching is involved - selection of the appropriate reference is done on the DTF board. IC1501 does away with the need for a speed control loop as its output is a squarewave whose mark-space ratio is determined by the phase difference between the two input signals - if there's a speed error the output will be predominantly high or low. The output is integrated to form a ramp which is sampled by gate A3, the gate being switched by the reference pulse after differentiation. The charge on the hold capacitor controls the head MDA. Should the motor tend to run excessively fast, T1534 turns on to operate the brake circuit. Simple but effective.

The capstan servo has a speed loop and, in record, a

Table 1: WS codes

| Mode | WS1 | WS2 | WS3 |
|----------|-----|-----|-----|
| Record | 0 | 1 | 0 |
| Playback | 0 | 1 | 1 |
| Still | 1 | 1 | 1 |
| Slow | 0 | 0 | 1 |
| SFF | 1 | 0 | 1 |
| SREW | 1 | 0 | 0 |

phase loop which compares the capstan FG with the reference. The phase loop is inoperative on playback, but the output from switch A1 on the DTF board is fed via B1 through a bleed resistor to the control line. We can now go into this.

If the tape speed is too high (within the confines of the speed loop) the DTF will bend both heads in the same direction. If the error is cumulative, control will periodically be lost. This won't do of course, so the DTF sample voltage is bled into the capstan servo to correct the tape speed – in effect altering the tracking as with a manual control.

The two 14526 programmable dividers IC1640-1 cater for the different capstan motor speeds (playback, slow motion, etc.). The division ratio is determined by whether pins 2, 5, 11 and 14 are low or high, the output being 100Hz irrespective of mode – the input frequencies are shown in Fig. 5. An array of logic gates decodes the WS signals to give the dividers the appropriate instructions and reverses the motor for SREW – there's no reel servo on this machine.

Some of you may be wondering how the head speed is altered in the trick modes to avoid loss of line sync – there doesn't seem to be anything in the head servo to do this. It's done by the DTF microcomputer altering the 25Hz reference frequency slightly.

Fault Finding

Now to faults. The first question must be: how does one distinguish between DTF and servo faults? You are presented with a picture covered in noise bars, but where does the fault lie? Totally incorrect head or capstan speed is fairly obvious. Failure of the head or capstan phase control loop in record will cause slowly moving noise bars on the machine's own recordings: if the head servo is at fault the noise will move even in still frame. Misadjustment of APB (capstan servo) produces severe wow during record. Failure of one or both DTF channels will give passable playback but several noise bars in fast search – don't forget the two 100Ω resistors in the power supply for this one.

A scope on the slipping brushes should show a sort of wobbly squarewave – only on one in record. Test point DTF-3 gives rows of dots and dashes – adjust APB to make them coincide, using a known good tape. If the dots are not fairly straight there's a tape path fault – look for bent guides, the cassette lift not square, dirt on the capstan, etc.

In fast search the rows of dashes become triangular but the rows of dots stay straight. Adjust VA1 and VA2 (DTF output gain controls) to make this so, on the machine's own recordings. The triangular ramp of dashes is because the heads have to be moved to cross several tracks. In the trick modes the microcomputer produces a ramp, leaving the DTF to apply only a small amount of correction.

We've had a few failures of IC1590 (LM2877) which gets very hot when faulty – the capstan motor runs very

slowly. If the capstan speed is incorrect, don't forget that the output from IC1640 will still be at 100Hz. The cause is sometimes a defective gate in the WS decoder. If one of the WS codes is stuck permanently high or low however the machine will go into the wrong mode but will be working correctly for that mode – not doing what it's told in other words.

We've had a few failures of passive components in the servos – sometimes difficult to locate. In one or two cases we've had to scope a good working machine and draw waveforms all over the manual to find the fault!

The DTF module is reliable. Up to now the only problems we've had have been failure of IC2620 and the 4.9MHz crystal – both giving no DTF. The DTF output transistors (on the servo board) can go short-circuit repeatedly, burning out the 100Ω resistors in the power supply. Slight noise bars during fast search, sometimes clearing, can in most cases be removed by carefully adjusting VA1 and VA2. The head servo adjustment APK moves the switching point: so this is the way to adjust it finely, using a good prerecorded tape and a monitor with the picture height reduced.

Next month a few words about the tape deck, the motor connection board, etc.

TV Fault Finding

– continued from page 591

line timebase wasn't working, and as the oscillator receives its supply from the output stage (after starting up) I decided to power it from an external 18V source. A scope check then revealed that the oscillator was working, but the rest of the timebase was still dead. I eventually found that part of the earth print on the i.f. strip had blown apart, and after bridging this the set came to life. Why this should prevent the oscillator from driving the rest of the line timebase is not clear, but it did!

R.D.S.

Thorn TX9 Chassis

The 1.6A mains fuse FS1 kept on blowing. The line timebase can be isolated from the power supply by disconnecting the fault-finding link (PC1040 main panel). This proved that the fault was in the power supply, and D66 (1N4007) which is in series with the h.t. rectifier thyristor turned out to be short-circuit. Odd that – it's not fitted in later production, though the thyristor type was changed.

R.D.S.

Waltham W190

The fault with this set was a plain raster with no modulation. Some quick checks revealed that the 13V supply was missing due to the 13V zener diode D608 (ZY13) having gone short-circuit. It's a 20in. monochrome set with some unusual circuitry – there's a common transformer for the chopper and line output circuits.

J.R.

Philips K30 Chassis

The set was dead with no h.t. at the collector of the line output transistor. There was 300V at the collector of the chopper transistor however so it seemed that this was without drive. It's always worthwhile removing the chopper drive panel and checking the semiconductor devices before condemning the TDA2581Q control i.c. The BSS58 driver transistor turned out to be short-circuit base-to-emitter.

M.B.

New Video Head Replacement Service

Substantial savings on video head replacement will be made possible by our new service which we are launching in September. New Japanese glass-filled heads to the latest specifications will be mounted and aligned on customers' existing upper cylinders, providing a rapid and profitable service to the trade. Manchester Colour Engineering Services is the first independent company to be permitted to install the same fully-automated, computer-controlled optico-electronic equipment as is used by the world's leading VCR manufacturers in Japan as part of their production lines. Our own staff in Manchester have been Japanese-trained to ensure the extremely high standards of precision involved – replacement heads have to be aligned to a tolerance of one-third of a micron.

Initially the service will be offered on 2-head VHS units only, for the following makes:

Akai, Ferguson, Hitachi, ITT, JVC, National Panasonic, Nordmende, Saba, Telefunken.

BETA system heads will be included at a later date – please contact us to discuss your BETA requirements.

SIX-MONTH GUARANTEE

Every repaired unit will be vacuum-packed for extended shelf-life. All units carry our six-month guarantee from the date of fitting.

HOW TO SEND

The cost of replacing both heads on customers' own upper cylinders is only £18.50 plus post/packing and VAT, total £21.75 per unit. Upper cylinders (which must be undamaged) must be packed in original makers' cartons, with an advice note detailing types and quantities enclosed.

Existing account customers will be invoiced in the normal way.

Non-account customers must send full remittance with order. A VAT invoice will be enclosed with the repaired units.

OUR TRACK RECORD


MCES are highly-experienced in the servicing of electronic components. Over the past decade we have realigned more than 500,000 UHF tuners of all types and makes. We also service a wide range of other items for the TV industry:

Video Modules
Aerial boosters
Modulators

Mullard Text Decoders
Eurodecoders
VM6101. VM6230 View Data
as used by Philips, Ferguson,
National, etc.

Philips Handsets
Simple & Full Remote
Teletext Remote
Full Stereo Remote

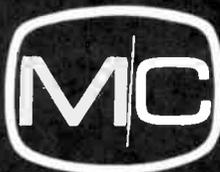Printed Board Assemblies
ITT CMR 800, ITT
CMR 803, Teletext,
View Data



COLOUR ENGINEERING SERVICES LTD

42-46 Moss Road, Stretford, Manchester M32 0AY

Telephone: 061-865 6021/2

Cable 84

Harold Peters

Cable 84, the second annual conference and exhibition for the cable and satellite industry, was held at Wembley over July 10-12th, only eight and a half hours after the Cable and Broadcasting Bill had finally passed through the Commons and about three weeks before it was due to receive the Royal Assent. Some 300 delegates attended the conference itself and were mainly concerned with the problems of getting cable networks started. At the exhibition greater interest was being shown in the stands displaying receiving and test equipment rather than cable machinery and electronics.

The show was much larger than Cable 83, and this time you could walk out on to the roof to inspect the "dish farm" that provided signals from ECS and Intelsat V to the stands below. Distribution of the signals was entrusted to Megasat Ltd. who were picking up all the transponders available, including Music Box which had started operations early to catch the show. Music Box shares the same transponder as Sky, offset and with different polarisation. The transmissions are unscrambled and the sound carrier

is at 6.6MHz with a pair of stereo coding signals at 7.1MHz. It was being received and demonstrated via a 1.2m dish on one stand – two exhibitors were offering complete 11GHz packages to pick up Music Box at around £1,200. Signals from the Russian satellite Gorizont were hardly to be seen, which was not surprising in view of what was on offer from ECS and Intelsat V.

GEC demonstrated Pal and MAC-C signals side-by-side, using the PM5544 test pattern, a severe test. The difference was about the same as between 405 and 625 lines when BBC-2 began in the sixties – impressive to the enthusiast, but not enough of a difference to sell the extra gear necessary from a general public point of view.

The slow and bumpy ride the Cable Bill had through parliament forced many of those involved in this field to consider other outlets, producing increased interest in smaller distribution systems, e.g. a modest dish atop a block of flats to provide extra channels to the communal system below. The logical progression towards DBS is only a matter of time, particularly now that the signals from ECS are coming in better than expected.

Some of the programmes are scrambled, but this seems to be something that programme contractors agree to only with reluctance – they'd like a simpler way of collecting their revenue.

Cable 85 next year will be held at Brighton on July 9-11th.

Teletopics

VIDEO DISCS

CBS, the US broadcast and entertainments group, are to cease production of CED videodiscs. The company has been producing the discs at their Carrollton, Georgia plant since 1982. CBS comment that the decision by RCA to end production of CED disc players led to a substantial fall in the demand for discs.

The future of the video disc appears to lie increasingly in specialised applications – for educational/training purposes where the interactive possibilities are an advantage, for juke box use (as previously mentioned in this column), and for use with microcomputers for video games and other purposes. It's interesting to note that JVC were showing an MSX microcomputer (the Japanese microcomputer standard adopted by a number of Japanese electronics firms) linked via an interface unit to a VHD player for video games purposes at the recent Chicago Consumer Electronics Show.

WHITHER 8mm?

As the year progresses, the likelihood of 8mm video equipment being introduced on the European market seems to be receding. Back in March we reported that the system "is to be introduced by a number of firms later this year". That was at the time of Kodak's announcement of the Matsushita-developed Kodavision 8mm video system. Shortly after this came the announcement that Polaroid would be introducing a Toshiba-developed 8mm system. It seems that the film companies saw 8mm as a way of getting into the video field in a big way. Video firms appear to have reservations however. Development of 8mm systems continues, but the VHS-C and Betamovie compact video

systems look set to dominate the portable video field for some time to come.

One problem with 8mm systems is the tape. Due to the higher recording density, the more recently developed types of video tape will have to be used, either metal powder or metal evaporated. The trouble with metal powder tape is that special heads are required. Metal evaporated tape can be used with standard head technology but is difficult and expensive to manufacture. Both types of tape are a lot more expensive than standard video tape. This presents something of a chicken-and-egg problem: the price of the tape won't come down until bulk production starts. In addition, it seems that PAL/SECAM operation with a drum speed of 1,500 r.p.m. (set by the European field frequency) is more difficult than NTSC operation with a drum speed of 1,800 r.p.m. (60Hz field frequency).

VIDEO HEAD REPLACEMENT SERVICE

A new service being launched by Manchester Colour Engineering Services Ltd. of 42-46 Moss Road, Stretford, Nr Manchester (telephone 061-865 6021/2) will enable substantial savings to be made when VCR video heads wear out. Instead of having to buy a complete upper drum when the heads are worn or damaged, service departments and VCR suppliers will be able to send the defective drum to MCES who will re-equip it with new glass-filled Japanese heads to the latest specifications. The cost of this is considerably less than that of a replacement drum.

MCES is an independent company and is the first to be permitted to install the same fully automated, computer-controlled optico-electronic equipment used by leading Japanese VCR manufacturers on their production lines. MCES staff have received training in Japan as part of the operation. The complex equipment used enables replacement heads to be aligned to an accuracy of some 0.3 microns.

The service is to start at the beginning of September and

will initially be restricted to two-head VHS drums used in Akai, Ferguson, Hitachi, ITT, JVC, Panasonic, Nord-Mende, Saba and Telefunken machines. A service for Beta units is to be offered later.

MCES has provided various services to the TV trade for over a decade, including u.h.f. tuner alignment and servicing of units such as Mullard text decoders, aerial boosters, Philips handsets, printed panels, etc.

TELETEXT-SPECTRUM ADAPTOR

O.E. Ltd. (North Point, Gilwilly Industrial Estate, Penrith, Cumbria CA11 9BN, telephone 0768 66748) have introduced an adaptor that enables a Sinclair Spectrum micro-computer (either 16K or 48K type) to be used as a teletext decoder. The TTX2000 adaptor, with interface cable and instructions, is available from the manufacturers at around £145 inclusive of VAT and postage/packing. It sits directly beneath the Spectrum to form a compact unit and will work with standard monochrome or colour receivers. There are four preset channel controls and the pages are called up by keying the appropriate number. The usual options such as hold and reveal are provided for. Teletext pages can be held on screen, stored on a microdrive for later recall, or printed out using a Spectrum or any compatible printer. O.E. Ltd. have also announced plans for a telesoftware programme to allow TTX2000 users to receive and download broadcast software for use with the ZX Spectrum. This downloader facility will be available as an upgrade ROM.

NEW COLOUR ENCODING IC


The New Motorola MC1377P l.s.i. encoder chip accepts RGB inputs and provides a composite output to either the NTSC or PAL standard. To simplify interfacing with a variety of sources, the RGB inputs are a.c. coupled: 1V peak-to-peak signals give full colour saturation. The only other input required is composite sync. The chroma and luminance signals are looped out of the chip to allow for bandwidth and delay tailoring. The device contains a subcarrier oscillator which can be used as a master oscillator or be driven from an external source, a voltage-controlled 90° phase shifter, two double-sideband modulators, RGB input matrixes and blanking level clamps.

mitsubishi's 40in. HIGH-DEFINITION TUBE

Mitsubishi have announced in Tokyo the development of the world's first 40in. (diagonal) high resolution tube for high-definition TV (1,125 lines) use. The aspect ratio is 5:3 and the phosphor dot pitch 0.45mm. Previous high-definition tubes had been limited to the 30/32in. sizes by the strength and weight of the glass required. Mitsubishi have also developed a wide-range, high-output video circuit with a flat response to 30MHz, and deflection circuits to ensure a high standard of linearity. In addition a digital convergence circuit achieves a precision of 0.1 per cent of screen width over the entire screen.

SINGLE-CHIP TELETEXT DECODER

The new ITT TPU2700 provides a single-chip teletext decoder with the capability of acquiring and storing eight pages simultaneously in conjunction with a 64K bit DRAM. It decodes the standard level-1 teletext transmissions and has been designed to interface with the Digivision 2000 series chips. The TPU2700's on-chip FIFO buffer enables it to be used with standard low-cost DRAM without speed problems.

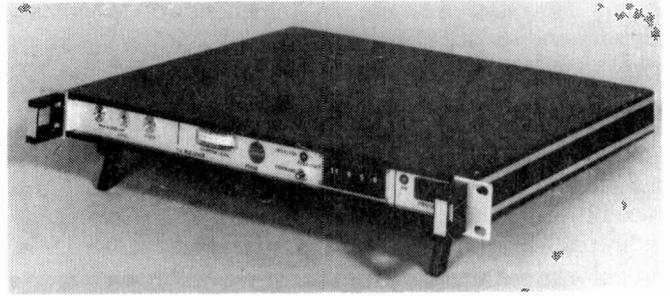

The new, compact Marconi Model P3400 satellite TV receiver is only 44.5mm thick. It's been designed for high quality, cost effective reception of the new European satellite TV transmissions from satellites such as ECS and the Intelsat series. The main users are likely to be cable system operators and telecommunications organisations requiring high quality vision and sound signals for distribution via terrestrial networks. The receiver is also intended for uses such as hotels and conference centres, language teaching institutes and for broadcasting organisations. The input at 900-1,700MHz comes from a low-noise downconverter mounted on the outdoor dish. For encrypted transmissions a further decoding unit is employed after the receiver to recover the vision and sound from the composite signal.

Compensation for ghost images with delays of up to 0.8µsec is automatically performed by the chip, which has underline capability and automatic character set selection – it will serve in receivers for eight different language teletext transmissions. The device comes in a 40-pin plastic DIP encapsulation, requires a single 5V supply and consumes typically 1.25W.

VCR SERVICING COURSES

The London Electronics College will from September be offering, in conjunction with the Manpower Services Commission, a full-time, six-week intensive training course in VCR servicing. The course includes a high percentage of practical work and instruction on state-of-the-art techniques such as digital and microcomputer technology as applied to VCRs. It's been developed in liaison with industry to help alleviate the present shortage of skilled video engineers and is intended for qualified TV technicians, or applicants with a similar background, who wish to extend their skills. The first two courses start on September 17th 1984 and January 7th 1985 and are open to both private fee paying and MSC sponsored applicants. Tuition fee for the full course is £600 plus VAT. For further details apply to the London Electronics College, 20 Penywern Road, London SW5 9SU (telephone 01-373 8721).

DIY HEAD MAINTENANCE KIT

The Monolith Electronics Co., Ltd. (5-7 Church Street, Crewkerne, Somerset, telephone 0460 74321) have introduced a new and more comprehensive video head replacement and maintenance kit for the home enthusiast. The VMC02 kit contains a novel head-concentricity gauge for aligning Betamax heads to an accuracy of better than three thousandths of a millimetre, a stroboscopic tachometer for verifying the head rotational speed with VHS machines, handling gloves, a cross-head screwdriver, an inspection mirror, a can of air-blast dust remover, an antistatic cloth, cleaning fluid, shaped spatulas, replacement service labels and a quality mains-operated soldering iron with solder – all for £19.95 including VAT plus £1.50 post and packing by mail order. A set of step-by-step instructions and a stock list of heads available from Monolith are provided. Cus-

tomers can make free use, by telephone, of Monolith's advisory and service department.

PORTABLE CCTV SURVEILLANCE SYSTEM

The Viguard portable CCTV surveillance kit, which is designed to provide temporary security, has been introduced by Pilkington Security Equipment Ltd. (Colomendy Industrial Estate, Rhyl Road, Denbigh, Clwyd, N.

Wales). It consists of a video camera, 7in. screen monitor, interfaces and a power supply, all contained in two lightweight suitcases, plus a separate fibre-optic cable reel to provide a video link of up to 1km. The fibre-optic cable allows the system to be used in an electronically noisy environment, cannot be bridged or tapped without detection, and provides good signal quality. Viguard can be powered from the mains or a 12V car battery via a cigarette lighter socket.

VCR Servo Systems

Part 1

Eugene Trundle

The circuits used in VCRs to process the luminance, colour and sound signals are fairly standardised and by now well understood. When it comes to system control and the servos however there's a wide diversity of techniques in use, varying between machines of different age and manufacture. It's also here that the major differences between basic "record and play" machines and those with added "trick" modes – still frame, slow motion and so on – are to be found. In the syscon department microcomputer techniques are now universally used – up to three of these complex i.c.s may be found lurking on the syscon panel. In the most advanced of current models microcomputer i.c.s are also finding their way into "trick-servo" circuits.

Many of us last made a study of servo circuits and techniques in the days of piano-key operated machines of one type or another. The simple arrangements used in these VCRs are not difficult to understand and service. Things have come a long way since then however, as a glance at the manual for a modern machine will show. The basic principles remain the same, and it's the purpose of this article to identify these and relate them to the various circuit arrangements that have been used over the years.

Basic Requirements

Let's start by setting down the bare essentials of servo operation in a domestic helical-scan machine. During record the capstan motor must rotate at an even speed to pull the tape past the heads at a rate appropriate to the format (N1500/N1700/VHS/Beta/V2000). This can be done without using a servo, but because variations in friction and load can effect the speed a simple servo system is generally provided to ensure steady passage of the tape.

The capstan speed is tied to a reference, usually a stable crystal oscillator though in some early machines (Philips and single-motor Beta models) the 50Hz mains supply was used. Hence the simple servo system shown in Fig. 1. Here we have a phase comparator that produces an error voltage proportional to the time difference between its two inputs, in this case the reference waveform and the

PG (pulse generator) feedback pulses. The error output voltage is used to modify the motor's speed and set it so that a steady relationship exists between the reference and the PG pulses. The shaft's position is thus phased to the reference. The PG pulses are produced by a couple of magnets mounted on the flywheel. Thus two PG pulses are produced per revolution of the flywheel.

When it comes to the head drum, the first point is that we have to record one 20msec TV field per head sweep. With two heads mounted diametrically opposite to each other in the drum, this implies 20msec per half revolution of the drum, 40msec per revolution and a precise speed of 1,500 r.p.m. This is unalterable where we have a 50 fields per second TV system: regardless of format, 1,500 r.p.m. is the required speed.

Having set the drum's speed, we have a second requirement. At some point during the field we have to switch from one recording head to the other. This will create a minor picture disturbance which must be kept out of sight. The field blanking period seems to be the ideal time to do this switching, but this period contains a series of critical timing pulses. Discontinuity here due to the head switchover could well cause vertical jitter on playback. The head switchover point is thus chosen to be about seven lines before the field sync pulse, and is "lost" off the bottom of the screen in the normally slightly overscanned raster. Now to keep the head switching point at this precise location we need a means of synchronising the drum's rotation to the incoming field sync pulses. A PG on the head drum provides a signal that indicates the head's position. We can compare the timing of this signal with that of the field sync pulses, using a servo like that shown in Fig. 1, to ensure that each head sweep starts just before the arrival of the field sync pulse in the TV signal being recorded.

So much for record. How about playback? Starting again with the capstan, we have the same requirement of a steady rotational speed, and some machines use the same arrangement as on record with no switching at all. The head drum must rotate at precisely 1,500 r.p.m., as during record, so that the heads pass over the tape at the correct angle. This will ensure that the head sweeps are parallel with the tracks recorded on the tape but will do nothing to ensure that they coincide, with the heads centred on the correct tracks – remember that due to the head azimuth offset, each head can read only its "own" tracks correctly.

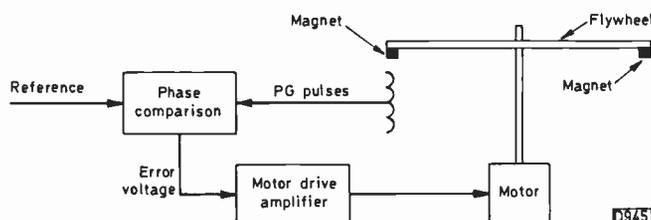


Fig. 1: Basic servo control loop.

Control Track

Unlike a conventional gramophone record groove which guides the stylus in addition to carrying the signal information, a magnetic tape track is not mechanically

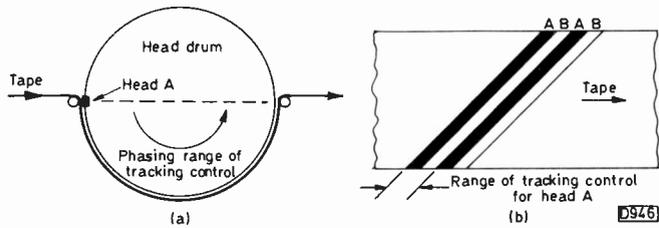


Fig. 2: Effect of the playback tracking control.

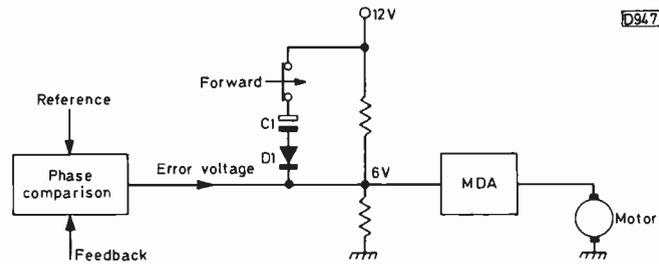


Fig. 3: Addition of a simple speed control arrangement.

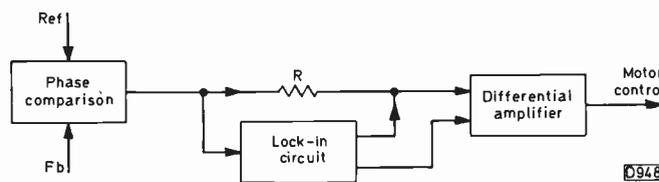


Fig. 4: Lock-in system used in Philips N1500 machines.

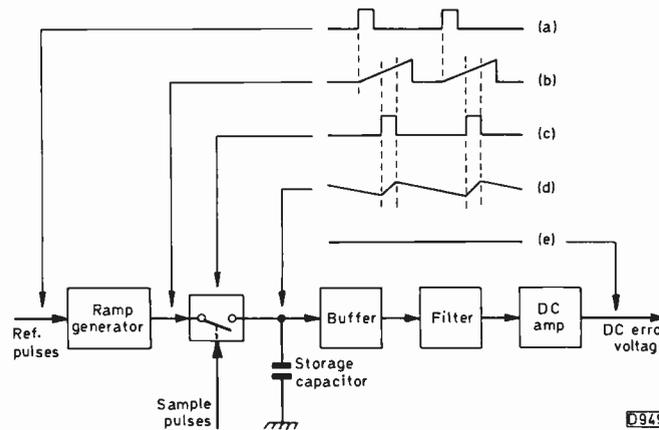


Fig. 5: Sample-and-hold principle.

locked to the reading head. In the V2000 system, specially recorded track identification signals enable the tracks to be identified and the heads kept in accurate alignment with them. The VHS and Beta systems rely on a separate marker system to indicate the position of each video track on the tape. This is the purpose of the control track, a narrow margin at the bottom edge of the tape, on which pulses are laid down during recording – one pulse for every two video tracks.

These control pulses can be used to phase the rotation of either the capstan or the head drum so that a fixed timing relationship is established between the tape tracks and the head sweeps. By phasing we mean getting the positions of the heads/tracks to coincide in addition to the speeds being correct. A potentiometer (tracking control) can be used to adjust the phasing process so that correct tracking is set and maintained, with each head following a path down the centre of its tracks to obtain minimum noise and inter-track crosstalk on playback.

Most machines are capstan controlled on playback, the control track pulses being used as a reference signal for

the capstan servo. Fig. 2 shows the effect of the tracking control. It normally has a range of about 180° of head rotation, thus embracing about two track widths. This ensures that correct tracking can be achieved with any tape under any conditions.

Speed and Phase

So far we've identified two distinct characteristics of the behaviour of a rotating shaft under servo control. These are its speed, which with a VCR is determined by the TV system and the format, and its phase, whose importance lies in the need to establish a specific head position/sync pulse relationship on record and head path/track position relationship on playback. The basic servo loop shown in Fig. 1 makes a poor job of speed control, so a separate means of establishing the correct speed quickly is required. In early machines this took two forms, see Figs. 3 and 4.

Fig. 3 shows a simple servo arrangement in which the error voltage output is mixed with a steady voltage from a potentiometer network connected across the supply rail. The potentiometer network provides a standing bias corresponding to the motor's normal running voltage, the overall arrangement providing a "window" of servo operation around the 6V point. The standing bias forms a crude speed control circuit: when "forward" is selected, the charging current of C1 via D1 increases the voltage applied to the motor so that it accelerates rapidly from standstill to a point within the lock-in range of the phase-controlling servo circuit.

The alternative approach shown in Fig. 4 was used in N1500 series Philips machines and takes the form of a lock-in or starting circuit. This governs the gain of the motor control amplifier according to the degree of ripple generated in the sample-and-hold phase comparator circuit – this ripple is proportional to the speed error. As the correct speed is approached, this ripple decreases and the effect of the circuit lessens. Once phase lock is achieved, it has no effect on the operation of the servo. As we shall see, later VCRs use a feedback loop for speed control in addition to that used for phase control, with an FG (frequency generator) on the controlled shaft to provide feedback pulses.

Sample-and-hold Technique

Let's briefly recap on the sample-and-hold principle. It's a very common arrangement and has only recently been succeeded by digitally-based systems. Fundamental to either technique is the requirement to produce an error voltage output proportional to the time lapse between two inputs – reference and sample. The reference will be some local timing source and the sample a tach pulse (PG) from the controlled shaft/flywheel.

The basic idea is illustrated in Fig. 5. The reference pulse (a) is used to start a ramp (trapezoid) generator which produces a linear ramp (b) whose amplitude at any subsequent instant will be proportional to the elapsed time. At some point during the ramp the sample pulse (c) arrives. This briefly closes a switch between the ramp source and a storage capacitor. As a result, the latter is charged to a voltage proportional to the elapsed time. Provided its discharge path is a high-impedance one, the capacitor holds its charge between sampling pulses. This charge forms the error voltage (d) and (e) which is used to control the motor. Note that some means must be pro-

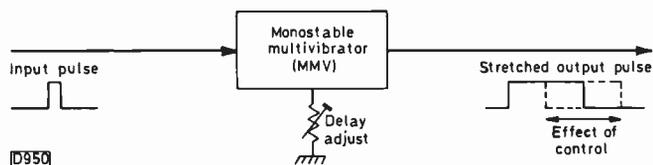


Fig. 6: Use of a monostable multivibrator (MMV) for pulse stretching, providing an adjustable delay.

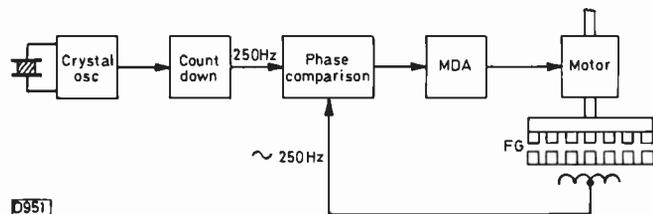


Fig. 7: Use of a frequency generator (FG). In the first FG circuits the "tone wheel" output was matched to a crystal oscillator in a phase-lock loop.

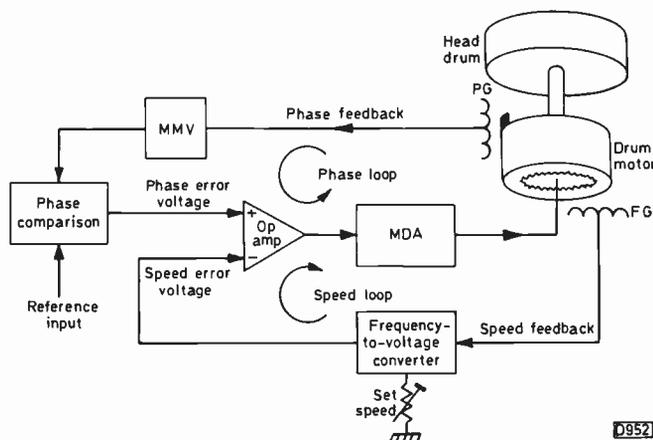


Fig. 8: Dual-loop servo system using an FG for speed feedback and a PG for phase control.

vided to discharge the storage capacitor between the sample pulses – otherwise it will charge to the peak voltage and stay there.

To obtain a symmetrical pull-in range, the ramp is normally sampled at about its mid-point. Since the error voltage output is proportional to the time lapse between the two input pulses, the circuit can be arranged so that either the reference or the sample feedback pulse triggers the ramp generator while the other does the sampling – both configurations are used in practice. The error voltage output along with the speed correction voltage is used to control the motor. A closed control-loop is thus established, and once conditions have settled down the motor's shaft will be phased to the reference source.

We've now got a phase-lock situation, but it's unlikely that the phase relationship established will be exactly correct. During record we may be recording the field sync pulses half way along the track. On playback the control pulses may be aligning the heads beside rather than in the centre of the tracks. In both cases we need to be able to adjust the servo's phasing in order to achieve the required result.

Phasing Adjustment

For record, presets labelled "head-switching point" are provided to adjust the head phasing and set the changeover point to just seven lines before the field sync pulse. During playback a similar control is provided on the

front panel to align the head sweeps with the tape tracks – the tracking control. The technique used in both cases is to delay either the reference or the feedback sample pulses in order to establish the exact phase relationship required.

This variable delay is simply achieved by using a monostable multivibrator (MMV for short) whose adjustable RC time-constant network provides the delay required. Once triggered, the multivibrator will provide a delay governed by the tracking control which is incorporated in its RC network. This delay or pulse-stretching feature is widely used – you'll find lots of MMVs in servo circuits. Fig. 6 illustrates the idea.

Speed Control

If a shaft is rotating in phase with a reference signal its speed must be spot on. After a disturbance however the correct speed must be re-established quickly. If we try to do this via the phase-control loop we will require a gently sloping ramp in order to cater for a wide range of speed variations – and this doesn't make for accurate phase control, because the small error voltage produced by a gently sloping ramp will have little effect on the servo action, leading to "soft" phase locking. A steep ramp gives tight and accurate phase locking because a large correction voltage is produced by small phase errors, but once a speed error is present the sampling pulses will appear at random on the ramp, confusing the sample-and-hold circuit and producing a jittery error voltage. As a result the motor will hunt, the instability playing havoc with the picture (and sound if it's the capstan motor that's being controlled).

Thus for close and accurate control it's best to have a dual servo loop, one to establish the correct speed and another to maintain the correct phase condition. This dual system is particularly important in portable VCRs where gyroscopic effects can occur, and in trick-speed and clever-edit machines where fast, precise control and quick speed recovery are necessary. All current and recent VCRs have dual loops for one or both servos.

For speed control we need a frequency feedback signal in the form of a tone whose frequency is proportional to r.p.m. Most motors nowadays are direct-drive types with the FG (frequency generator) built in. It takes the form of a multi-toothed wheel or a series of magnets that pass over a stationary coil system. Unusually, the Ferguson 3V01 (a piano-key portable) has a capacitive FG system for both the drum and the capstan: the toothed wheel spins within a toothed stator, the regular capacitance variation being sensed and amplified by a high-impedance f.e.t. stage.

For capstan speed control, the FG signal can be "paced" by a crystal oscillator, equilibrium being established when (say) one FG pulse occurs for every 9,800 crystal clock pulses – this is easy to arrange with i.c.-based counting circuits. This offers rigid speed lock with no necessity for a capstan tachogenerator, see Fig. 7. While an FG is used in this system, it's still basically a phase-locked loop, but with the advantage of closer control over the motor since there are more "beats to the bar". The system shown is a sort of half-way house between PG phase control and the true FG speed feedback control technique described below. A circuit like that shown in Fig. 7 must be supported by a resistive potential divider to establish the normal rotational speed initially.

The head drum's rotational speed cannot be locked to the likes of a crystal clock because phase locking to the incoming field sync pulses is required when recording –

TV Test Pattern Generator

Part 4

Tony Jenkins, G8TBF (JRW Developments)

Experience with the unit has resulted in some minor modifications.

It's been found that some batches of SN74LS04 i.c.s (IC1, logic board) are reluctant to oscillate at 20MHz though they are perfectly happy running at 10MHz. We therefore recommend the use of an SN74S04. The values of R1 and R2 have to be reduced to take into account the greater current taken by the S version of this i.c. – 330Ω has been found to be satisfactory in both positions. The idea is that both sections of the i.c. are biased for linear operation.

C2 is increased to 0.1μF for correct operation of the even/odd field detector. As the line ident output is not used it's been deleted from the board. A separate positive-going composite sync output has been added.

The following modifications have been made to the encoder/modulator board. The colour burst enable pulse at pin 15 of the TEA1002 was found to occur too early and to have insufficient duration. As a result the receiver's burst detector is likely to have an inadequate burst input, resulting in loss of colour. The first problem was overcome by introducing a delay in the sync pulse feed to pin 4 of the 4528. This consists of a 470Ω resistor in series with the pin and an 0.001μF capacitor to chassis. The modification has been incorporated in the board design. The duration of the enable pulse has been increased by changing the value of R4 to 8.2kΩ.

We also found that the action of the background control VR4 was too fierce in operation. The cure is to connect R1 to 5V instead of 12V. This is also taken care of in the board design.

Later batches of the TEA1002 appear to have a lower d.c. pedestal at the output, requiring D2 to be changed to the 1.5V type BZV46-1V5. If a 2V type is fitted, there can be sync crushing. We also recommend changing the value of R11 to 3.9kΩ to provide better biasing conditions for the UM1286.

If the sound facility is not to be used we suggest earthing pin 3 of the modulator to prevent spurious signals and general noise producing modulation. Most constructors will probably require some sort of sound facility and one of the simplest possible circuits that can be used is shown in Fig. 10. It consists of a CMOS type 4017 synchronous decade counter/divider. The i.c. is clocked by the 7.8kHz output pulses from IC5: its output is taken from the carryover pin and consists of 780Hz squarewaves with a 1:1 mark-space ratio. This signal is connected directly to pin 3 of the modulator. If an audio output is

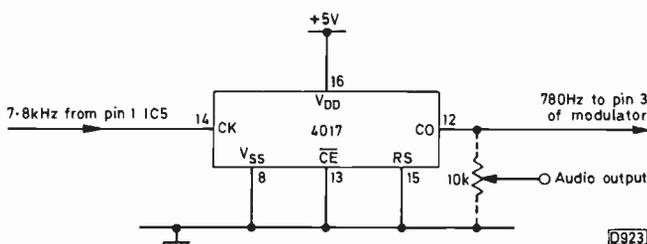


Fig. 10: Simple way of obtaining a 780Hz audio signal.

required, use a 10kΩ potentiometer and take the output from the slider. The circuit is so simple that it can be built on a small piece of Vero board or hard-wired on a 16-pin i.c. socket. A more sophisticated audio oscillator with a variable frequency sinewave output is planned for the near future.

Construction

The logic and encoder boards have been laid out to allow very simple interconnections when the two boards are stacked, i.e. one board is mounted atop the other. We suggest placing the encoder board on top as it has to be set up. A clearance of about 25mm between the boards is recommended – use spacers, threaded or unthreaded, plastic or metal. Once the boards have been stacked the connecting leads can be made, using either tinned copper wire (approximately 20 s.w.g.), individual insulated wire, or ribbon cable. If ribbon cable is used, leave a small loop to allow the top board to be hinged for access to the component side of the logic board. The power supply leads connect directly to the encoder board: the interconnecting leads include the 5V supply for the logic board.

Take the u.h.f. output from the modulator to a u.h.f. coaxial socket on the front panel via a phono plug and a short piece of 75Ω coaxial cable. The composite video output can be taken from the encoder board to a 75Ω BNC socket on the front panel via a short length of 75Ω coaxial cable. Note the extra earth pad on the encoder board for the coaxial cable braid. Composite sync and/or field sync can also be brought out if required, direct from the logic board. For the case we suggest the RS Components 508-655, but any plastic or metal enclosure of suitable size will do. Efficient decoupling throughout results in low radiation from the unit.

Assuming that there are no constructional errors, setting all the controls midway should produce a display, probably in colour. The first adjustment required is to the 8.8MHz oscillator. This is best done with a frequency counter connected to pin 14 of the TEA1002, but setting C1 midway or even using a fixed 12pF capacitor will probably be adequate. The grey-scale setting procedure is as follows.

- (1) Turn VR1, VR2 and VR3 full anticlockwise.
- (2) Adjust VR4 for a grey background to the crosshatch pattern.
- (3) Adjust VR3 until the left half of the grey-scale rectangle is at the same grey level as the background.
- (4) Adjust VR2 until the extreme left square is almost but not quite black.
- (5) Adjust VR1 until the extreme left square is black.

Some final tweaking may be necessary to ensure that there's a progressive black-to-white scale. If any control is advanced too far the d.c. level will drop below black level and cause sync disturbance – visible on the screen as pulling.

All key points on the logic board are labelled in the circuit diagram and probing a "dead" board with a scope

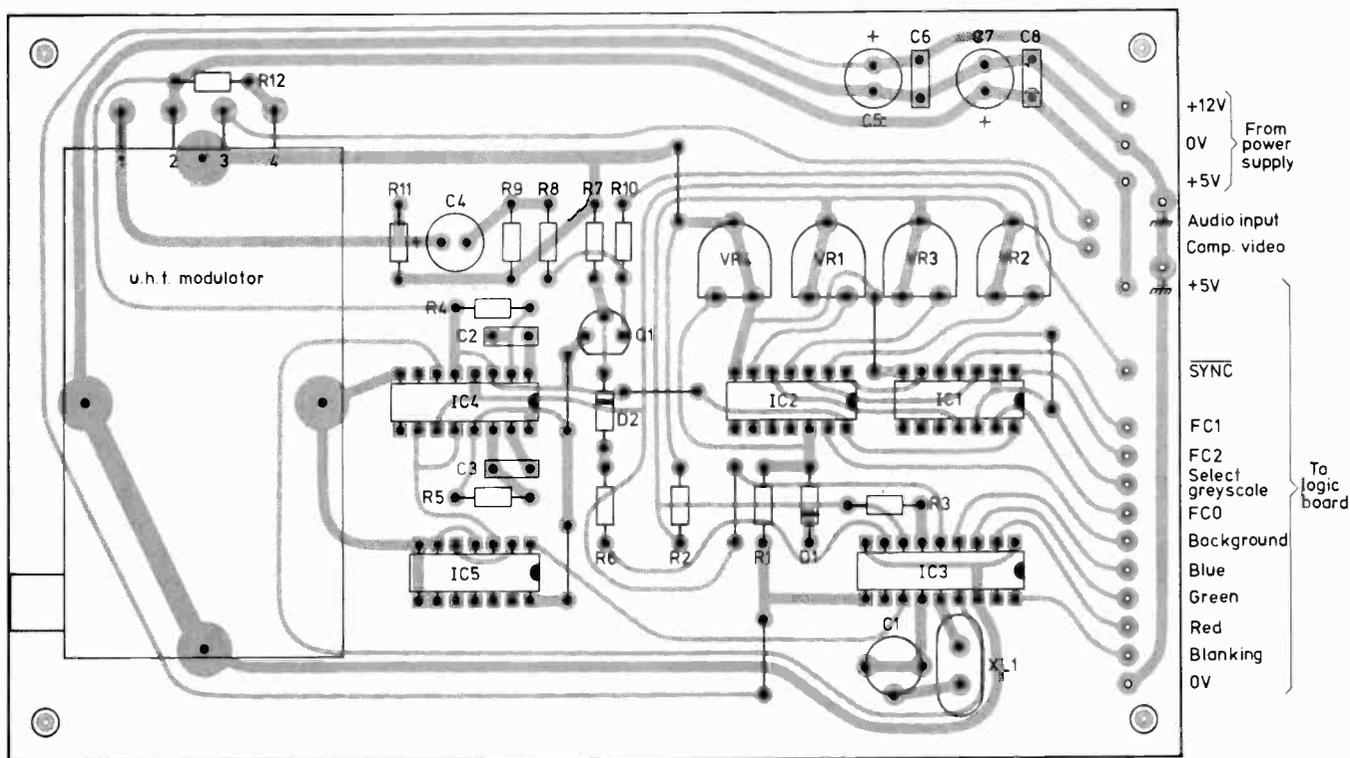


Fig. 11: Encoder/modulator board component layout.

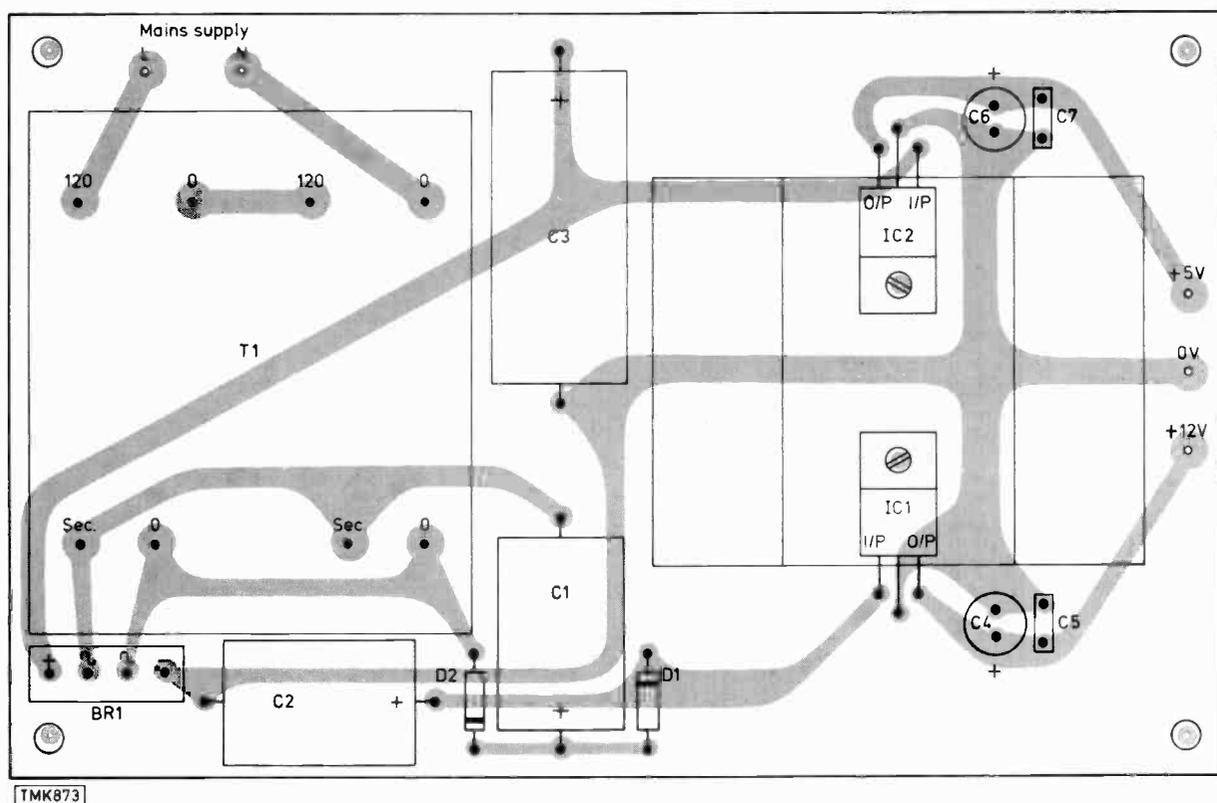


Fig. 12: Power supply panel component layout.

will quickly reveal the cause of the fault. The ZNA234E (IC8) does not normally run hot, but if you are concerned a small U-shaped heatsink can be bonded to the top using cyanoacrylate adhesive. The total current consumption of the unit is around 600mA from the 5V rail and 60mA from the 12V rail.

If an i.c. on the logic board develops a fault extraction can be a messy business. We suggest cutting the pins from the body then removing each pin separately, taking great care not to lift tracks from the top of the board. It's best to

use sockets for the i.c.s.

The bandwidth of the chroma signal is not limited. This leads to interference on colour transitions and some moiré effects. A bandpass filter would be required to reduce these effects. As this would delay the chroma signal, a compensating delay line would have to be added in the luminance circuit to ensure correct timing of the two signals. We decided that the extra complication was not justified since the interference is negligible with any use to which the generator is likely to be put.

ECONOMIC DEVICES, PO BOX 228, TELFORD TF2 8QP

| | | | | | | | | | | | | | | | | | |
|---------|------|-------------|------|-------------|------|--------------|-------|---------|------|--------|------|---------|------|------------|------|--------------|------|
| 16029 | 1.50 | ZSC1061 | 0.54 | 2SD898B | 2.67 | AN320 | 4.97 | BC171 | 0.10 | BD166 | 0.30 | BF137 | 0.11 | BLY49 | 2.00 | BY203/20 | 6.18 |
| 16181 | 1.13 | ZSC1096 | 1.05 | 40408 | 0.45 | AN322 | 4.36 | BC172 | 0.09 | BD168 | 0.06 | BF152 | 0.28 | BR100 | 0.20 | BY206 | 0.17 |
| 16182 | 1.13 | ZSC1104 | 2.00 | 40594 | 1.39 | AN331 | 2.99 | BC172B | 0.24 | BD175 | 0.39 | BF153 | 0.52 | BR101 | 0.37 | BY207 | 0.22 |
| 16334 | 0.06 | ZSC1106 | 4.12 | 40595 | 1.39 | AN337 | 3.99 | BC173 | 0.15 | BD177 | 0.39 | BF154 | 0.23 | BR103 | 0.45 | BY210-400 | 0.24 |
| 16335 | 0.72 | ZSC1114 | 5.61 | 40636 | 0.06 | AN340P | 1.06 | BC174B | 0.24 | BD179 | 0.44 | BF157 | 0.23 | BR88B | 0.58 | BY210-600 | 0.27 |
| 16446 | 0.09 | ZSC1124 | 1.10 | 40871 | 1.39 | AN355 | 3.36 | BC177 | 0.18 | BD181 | 0.90 | BF158 | 0.16 | BRC-M-300 | 1.58 | BY210-800 | 0.30 |
| 16600 | 1.25 | ZSC1151A | 4.29 | 40872 | 1.39 | AN362 | 1.47 | BC178 | 0.23 | BD182 | 0.90 | BF159 | 0.16 | BRC116 | 0.80 | BY223 | 0.85 |
| 16799 | 2.16 | ZSC1152 | 4.25 | 60857 | 1.16 | AN5111 | 2.34 | BC179 | 0.23 | BD183 | 0.90 | BF180 | 0.28 | BRC1330 | 1.00 | BY224-400 | 0.90 |
| 16801 | 0.00 | ZSC1157 | 4.12 | 74LS132 | 0.72 | AN5132 | 3.99 | BC182 | 0.08 | BD184 | 1.10 | BF167 | 0.30 | BRC300 | 1.82 | BY225-100 | 0.79 |
| 16802 | 1.03 | ZSC1182 | 0.95 | 74LS138 | 0.85 | AN5250 | 3.33 | BC182B | 0.23 | BD187 | 0.40 | BF173 | 0.34 | BRC4443 | 1.12 | BY226 | 0.28 |
| 16803 | 4.81 | ZSC1172 | 1.92 | 74LS157 | 0.79 | AN5435 | 2.80 | BC182L | 0.09 | BD189 | 0.35 | BF177 | 0.56 | BRC4444 | 1.12 | BY227 | 0.44 |
| 16905 | 1.35 | ZSC1195 | 2.63 | 74LS161AN | 1.18 | AN5610 | 6.75 | BC182LB | 0.12 | BD190 | 0.50 | BF178 | 0.30 | BRC5296 | 0.70 | BY228 | 0.54 |
| 17074 | 6.00 | ZSC1213 | 0.75 | 74LS196 | 1.25 | AN5613 | 3.72 | BC183 | 0.09 | BD201 | 0.54 | BF179 | 0.32 | BRC6109 | 0.75 | BY255 | 0.97 |
| 17127 | 3.91 | ZSC1226 | 1.32 | 74LS20 | 0.25 | AN5620X | 4.83 | BC183L | 0.09 | BD202 | 0.54 | BF180 | 0.32 | BRC82 | 0.90 | BY298 | 0.25 |
| 17376 | 1.43 | ZSC1306 | 0.85 | 74LS244 | 1.85 | AN6320N | 3.89 | BC183LB | 0.23 | BD203 | 0.54 | BF181 | 0.29 | BRC83 | 0.90 | BY299 | 0.25 |
| 1N4001 | 0.05 | ZSC1307 | 1.35 | 74LS30 | 0.29 | AN6342 | 1.36 | BC184 | 0.09 | BD204 | 0.54 | BF182 | 0.30 | BRC84 | 0.90 | BY476A | 0.76 |
| 1N4002 | 0.05 | ZSC1316 | 3.40 | 74LS367 | 1.85 | AN6344 | 4.80 | BC184L | 0.09 | BD207 | 1.00 | BF183 | 0.35 | BRX44 | 0.54 | BY456 | 0.30 |
| 1N4003 | 0.05 | ZSC1384 | 0.49 | 74LS373 | 1.55 | AN6383 | 10.20 | BC184LB | 0.23 | BD208 | 1.00 | BF184 | 0.39 | BRX49 | 0.45 | BYX10 | 0.26 |
| 1N4004 | 0.06 | ZSC1383 | 1.39 | 74LS47 | 1.85 | AN6551 | 0.56 | BC186 | 0.24 | BD222 | 0.44 | BF185 | 0.35 | BRX39 | 0.50 | BYX55-350 | 0.48 |
| 1N4005 | 0.07 | ZSC1398 | 0.51 | 74LS73 | 0.39 | AN6552 | 0.52 | BC187 | 0.18 | BD225 | 0.44 | BF194 | 0.15 | BRX55 | 0.60 | BYX55-600 | 0.25 |
| 1N4006 | 0.07 | ZSC1410 | 2.17 | 74LS74 | 0.39 | AN7145 | 2.84 | BC204 | 0.14 | BD228 | 0.57 | BF195 | 0.12 | BRX56 | 0.38 | BYX71-350 | 0.87 |
| 1N4007 | 0.07 | ZSC1413 | 3.00 | 74LS75 | 0.52 | AN7150 | 2.22 | BC207 | 0.12 | BD229 | 0.63 | BF196 | 0.15 | BSR59 | 1.17 | BYX71-600 | 0.85 |
| 1N4148 | 0.03 | ZSC1505 | 0.56 | 74LS86 | 0.49 | AN7151 | 2.05 | BC212 | 0.10 | BD231 | 0.45 | BF197 | 0.14 | BSS38 | 0.30 | BYX94 | 1.89 |
| 1N4448 | 0.12 | ZSC1578 | 6.67 | 74LS90 | 0.75 | AN7156 | 2.85 | BC212B | 0.23 | BD232 | 0.44 | BF198 | 0.15 | BSTBD1409 | 2.40 | BY556 | 0.18 |
| 1N5401 | 0.12 | ZSC1617 | 3.35 | 74LS92 | 0.75 | AN7158 | 2.34 | BC212L | 0.09 | BD234 | 0.30 | BF199 | 0.15 | BSTB01405 | 4.37 | BZV15-C12 | 0.72 |
| 1N5402 | 0.13 | ZSC1670 | 2.84 | 74LS93 | 0.75 | AN7218 | 1.49 | BC212LB | 0.23 | BD235 | 0.43 | BF200 | 0.33 | BSTC01406 | 2.25 | BZV15-C12R | 0.72 |
| 1N5403 | 0.14 | ZSC1678 | 1.25 | 74LS95B | 0.85 | AP58076 | 4.25 | BC213 | 0.09 | BD236 | 0.45 | BF216 | 0.32 | BSTC02233 | 2.25 | BZV15-C24 | 0.72 |
| 1N5404 | 0.15 | ZSC1810 | 1.40 | 7805 TO-220 | 0.63 | AS560S | 1.43 | BC213L | 0.09 | BD237 | 0.30 | BF218 | 0.30 | BSTC0246 | 4.51 | BZV15-C24R | 0.72 |
| 1N5408 | 0.18 | ZSC1815 | 0.41 | 7805 TO-3 | 1.85 | AU106 | 1.96 | BC213LB | 0.23 | BD238 | 0.29 | BF222 | 0.50 | BSTC1233 | 3.91 | BZV15-C30R | 0.72 |
| 1N514 | 0.05 | ZSC1829 | 2.01 | 7806 | 0.86 | AU110 | 1.96 | BC214 | 0.09 | BD239 | 0.44 | BF224 | 0.15 | BSTC1346 | 0.71 | BZK61 Range | 0.16 |
| 1S44 | 0.06 | ZSC1875 | 4.77 | 7808 | 0.54 | AU113 | 2.15 | BC214L | 0.12 | BD240 | 0.36 | BF237 | 0.59 | BSTC00143 | 2.79 | BZK70-C11 | 0.54 |
| 1S5012A | 0.73 | ZSC1891 | 3.35 | 7812 TO-3 | 0.54 | AY102 | 2.62 | BC214LB | 0.23 | BD243A | 0.47 | BF240 | 0.15 | BSTC0643 | 3.86 | BZK70-C12 | 0.54 |
| 1S921 | 0.09 | ZSC1929 | 2.25 | 7812 TO-220 | 1.05 | AY105K | 1.89 | BC225 | 0.24 | BD241 | 0.45 | BF241 | 0.15 | BSV57B | 2.86 | BZK70-C15 | 0.54 |
| 2582 | 1.94 | ZSC1942 | 5.70 | 7815 | 0.55 | AY106 | 1.98 | BC237 | 0.09 | BD242 | 0.45 | BF244 | 0.23 | BSW68 | 0.38 | BZK70-C30 | 0.54 |
| 2N1302 | 0.24 | ZSC1945 | 4.11 | 7818 | 0.55 | BA102 | 0.30 | BC238 | 0.09 | BD243 | 0.44 | BF245A | 0.33 | BSX19 | 0.38 | BZK70-C47 | 0.54 |
| 2N1303 | 0.34 | ZSC1953 | 1.75 | 7824 | 0.55 | BA1310 (IC) | 1.72 | BC238A | 0.11 | BD243A | 0.50 | BF255 | 0.18 | BSX20 | 0.30 | BZK79 Range | 0.89 |
| 2N2218 | 0.38 | ZSC1957 | 0.86 | AC107 | 0.86 | BA1320 (IC) | 1.22 | BC239B | 0.88 | BD244 | 0.44 | BF256 | 0.25 | BSX21 | 0.45 | BZ788 Range | 0.89 |
| 2N2219A | 0.29 | ZSC1959 | 0.36 | AC117 | 0.39 | BA1330 (IC) | 1.82 | BC251A | 0.15 | BD244A | 0.77 | BF256LC | 0.38 | BSY52 | 0.45 | BZ793-C12 | 0.99 |
| 2N2222 | 0.34 | ZSC1962 | 1.75 | AC123K | 0.39 | BA145 | 0.17 | BC252 | 0.12 | BD245C | 0.80 | BF257 | 0.30 | BSY79 | 0.46 | BZ793-C18 | 0.99 |
| 2N2846 | 0.75 | ZSC1989 | 2.92 | AC128 | 0.28 | BA154 | 0.08 | BC258 | 0.22 | BD246C | 0.74 | BF258 | 0.29 | BT100A | 1.46 | BZ793-C24 | 0.99 |
| 2N2904 | 0.32 | ZSC2027 | 2.67 | AC138 | 0.88 | BA155-01 | 0.12 | BC261A | 0.20 | BD253 | 0.95 | BF259 | 0.30 | BT106 | 1.20 | BZ793-C30R | 0.99 |
| 2N2905 | 0.39 | ZSC2028 | 1.91 | AC141 | 0.26 | BA156 | 0.12 | BC262 | 0.20 | BD278A | 0.60 | BF262 | 0.51 | BT108 | 1.31 | BZ793-C40 | 0.99 |
| 2N2906 | 0.34 | ZSC2029 | 1.49 | AC142K | 0.39 | BA157 | 0.17 | BC287 | 0.45 | BD317 | 1.96 | BF263 | 0.51 | BT109 | 1.31 | BZ793-C47 | 0.99 |
| 2N3053 | 0.24 | ZSC2057 | 1.07 | AC151 | 0.25 | BA159 | 0.12 | BC294 | 0.45 | BD318 | 2.00 | BF264 | 0.33 | BT112 | 2.25 | BZ793-C68 | 0.99 |
| 2N3054 | 0.90 | ZSC2073 | 1.40 | AC153 | 0.30 | BA182 | 0.17 | BC301 | 0.36 | BD375 | 0.38 | BF271 | 0.30 | BT113 | 2.25 | BZ793-C75 | 0.99 |
| 2N3055 | 0.55 | ZSC2078 | 1.25 | AC153K | 0.36 | BA222 (IC) | 1.26 | BC302 | 0.30 | BD377 | 0.69 | BF273 | 0.18 | BT116 | 1.52 | ZTK33 | 0.39 |
| 2N3055H | 0.77 | ZSC2091 | 0.59 | AC176 | 0.17 | BA284-2 | 0.15 | BC303 | 0.34 | BD379 | 0.89 | BF274 | 0.18 | BT119 | 1.80 | ZX18 | 2.47 |
| 2N3442 | 1.06 | ZSC2122A | 4.65 | AC176K | 0.40 | BA301 (IC) | 0.92 | BC307 | 0.89 | BD380 | 0.69 | BF324 | 0.16 | BT120 | 1.80 | XI060 | 0.46 |
| 2N3702 | 0.12 | ZSC2141 | 1.89 | AC179 | 0.25 | BA302 | 0.90 | BC307A | 0.14 | BD410 | 0.44 | BF336 | 0.27 | BT121 | 2.25 | C1129 | 0.52 |
| 2N3703 | 0.12 | ZSC2166 | 1.35 | AC183 | 0.85 | BA311 (IC) | 1.06 | BC308 | 0.12 | BD412 | 0.76 | BF337 | 0.36 | BT122 | 2.25 | CA1310E | 2.45 |
| 2N3704 | 0.12 | ZSC2216 | 0.62 | AC186 | 0.30 | BA312 (IC) | 0.98 | BC308A | 0.09 | BD418 | 0.76 | BF338 | 0.36 | BT123 | 1.80 | CA304A | 3.18 |
| 2N3705 | 0.12 | ZSC2233 | 2.20 | AC186K | 0.50 | BA313 (IC) | 1.28 | BC309 | 0.15 | BD433 | 0.33 | BF355 | 0.36 | BT125 | 2.25 | CA3046 | 2.23 |
| 2N3706 | 0.12 | ZSC2271 | 3.64 | AC187 | 0.35 | BA316 | 0.07 | BC317A | 0.11 | BD434 | 0.39 | BF362 | 0.54 | BT126 | 2.25 | CA3060 | 1.50 |
| 2N3707 | 0.14 | ZSC2278 | 1.03 | AC187-01 | 0.40 | BA317 | 0.07 | BC323 | 0.92 | BD435 | 0.42 | BF363 | 0.54 | BT128 | 2.25 | CA3065 | 1.17 |
| 2N3711 | 0.14 | ZSC2335-KIT | 7.81 | AC187K | 0.39 | BA318 | 0.08 | BC327 | 0.15 | BD436 | 0.42 | BF371 | 0.45 | BT128P | 2.79 | CA3089 | 3.30 |
| 2N3771 | 1.85 | ZSC2526 | 1.70 | AC188 | 0.33 | BA328 (IC) | 0.80 | BC328 | 0.10 | BD437 | 0.41 | BF391 | 0.36 | BT129 | 2.25 | CA3089E | 1.35 |
| 2N3772 | 1.55 | ZSC2551 | 0.95 | AC188-01 | 0.40 | BA333 (IC) | 1.24 | BC337 | 0.88 | BD438 | 0.44 | BF393 | 0.90 | BT151-800R | 1.47 | CA3090 | 2.00 |
| 2N3773 | 1.85 | ZSC2570 | 1.80 | AC188K | 0.39 | BA401 (IC) | 0.58 | BC338 | 0.10 | BD441 | 1.29 | BF417 | 1.20 | BT151 500R | 1.25 | CA3094 | 1.25 |
| 2N3819 | 0.28 | ZSC2570A | 0.95 | AC193K | 0.59 | BA511 (IC) | 1.98 | BC360 | 0.30 | BD442 | 0.56 | BF418 | 1.70 | BT16018 | 2.20 | CA3131EN | 2.83 |
| 2N3823 | 1.06 | ZSC284A | 4.38 | AC194K | 0.59 | BA521 (IC) | 1.81 | BC368 | 0.23 | BD507 | 0.54 | BF422 | 0.26 | BT16218 | 2.20 | CA3132EN | 2.83 |
| 2N3904 | 0.56 | ZSC2871 | 1.99 | AD140 | 0.96 | BA532 (IC) | 1.88 | BC440 | 0.99 | BD508 | 0.54 | BF423 | 0.26 | BT1802A | 4.82 | CBF78023N | 6.00 |
| 2N3908 | 0.56 | ZSC2728 | 0.95 | AD142 | 0.96 | BA536 (IC) | 2.72 | BC441 | 0.40 | BD509 | 1.29 | BF435 | 0.49 | BT18124 | 4.44 | CBF16848N-07 | 1.41 |
| 2N4101 | 1.10 | ZSC372 | 1.27 | AD143 | 0.96 | BA6304A (IC) | 2.85 | BC454 | 0.32 | BD510 | 0.45 | BF450 | 0.30 | BT18214 | 5.44 | CD4001 | 0.24 |
| 2N4240 | 3.00 | ZSC373 | 1.05 | AD145 | 1.45 | BA843 (IC) | 3.80 | BC455 | 0.32 | BD518 | 1.36 | BF451 | 0.26 | BT18224 | 2.70 | CD4002 | 0.24 |
| 2N4443 | 1.35 | ZSC383 | 1.20 | AD149 | 0.81 | BAV10 | 0.10 | BC460 | 0.38 | BD519 | 1.36 | BF457 | 0.37 | BU105 | 1.86 | CD4008 | 0.96 |
| 2N4444 | 1.12 | ZSC388 | 0.45 | AD161 | 0.10 | BAV18 | 0.10 | BC461 | 0.42 | BD529 | 0.38 | BF458 | 0.35 | BU106 | 2.25 | CD4011 | 0.24 |
| 2N4914 | 0.85 | ZSC41 | 1.99 | AD162 | 0.30 | BAV19 | 0.10 | BC462 | 0.27 | BD530 | 0.80 | BF459 | 0.35 | BU108 | 1.90 | CD4012 | 0.24 |
| 2N5064 | 0.84 | ZSC458 | 0.55 | AD282 | 0.95 | BAV20 | 0.10 | BC463 | 0.58 | BD533 | 0.80 | BF460 | 0.30 | BU109S | 1.90 | CD4013 | 0.37 |
| 2N5293 | 0.45 | ZSC485 | 0.83 | AF114 | 2.24 | BAV21 | 0.17 | BC464 | 0.58 | BD534 | 0.36 | BF469 | 0.27 | BU110 | 2.52 | CD4016 | 0.37 |
| 2N5294 | 0.45 | ZSC508 | 3.36 | AF115 | 0.79 | BAV12 | 0.10 | BC465 | 0.58 | BD535 | 0.44 | BF470 | 0.28 | BU111Y | 3.78 | CD4017 | 0.74 |
| 2N5296 | 0.40 | ZSC515A | 1.28 | AF116</ | | | | | | | | | | | | | |

ECONOMIC DEVICES, PO BOX 228, TELFORD TF2 8QP

| | | | | | | | | | | | | | | | | | |
|------------|-------|------------|-------|-----------|------|------------|-------|------------|------|-----------|------|-----------|------|-----------|------|-----------|-------|
| ESM532C | 4.18 | LM1303P/N | 1.50 | MPSU05 | 0.78 | SAA5010 | 4.98 | SN74190 | 1.81 | T8029V | 4.41 | TBA395 | 1.35 | TD41230 | 2.93 | TD49303 | 2.80 |
| ESM532C | 4.18 | LM1310P/N | 1.25 | MPSU10 | 0.78 | SAA5012 | 6.58 | SN7420N | 0.38 | T8032V | 0.89 | TBA395Q | 1.00 | TD41235 | 2.93 | TD49313 | 2.40 |
| ESM732C | 4.18 | LM3085N | 0.77 | MPSU55 | 0.90 | SAA5020 | 5.25 | SN7430 | 0.28 | T8033V | 0.73 | TBA396 | 1.00 | TD41270 | 2.84 | TE527 | 1.25 |
| ETT8016 | 2.05 | LM317CKC | 1.30 | MPSU56 | 0.30 | SAA5030 | 7.50 | SN7440N | 0.24 | T8035V | 0.86 | TBA400 | 2.17 | TD41327A | 1.85 | TE538 | 0.38 |
| ETTR8016 | 2.16 | LM339N | 0.88 | MPSU80 | 1.20 | SAA5040A | 14.75 | SN7473 | 0.56 | T8036 | 0.44 | TBA400P | 1.55 | TD41327B | 1.85 | TE626 | 1.35 |
| FND500 | 5.25 | LM3407 | 1.29 | MR510 | 0.30 | SAA5050 | 8.58 | SN7474N | 0.72 | T8037 | 1.91 | TBA400 | 1.42 | TD41330 | 1.85 | TEA1002 | 3.15 |
| FT3055 | 1.05 | LM3407S | 0.75 | MR812 | 0.80 | SAA661B | 1.88 | SN7490AN | 0.93 | T8041V | 0.86 | TBA400Q | 1.67 | TD41365 | 1.60 | TEA1009 | 0.94 |
| GF758 | 0.82 | LM3407T2 | 0.75 | MR914 | 0.46 | SAA700 | 3.80 | SN75110N | 0.25 | T8044V | 0.86 | TBA500PQ | 4.95 | TD41412 | 1.95 | TEA1020SP | 0.46 |
| GF759 | 1.02 | LM3407S | 0.75 | MSSD7002 | 0.85 | SAB1009B | 4.53 | SN78001ANQ | 0.75 | T8045 | 1.09 | TBA510 | 1.55 | TD41420 | 1.48 | TEA1087 | 0.48 |
| GF761 | 0.78 | LM342N | 0.56 | MVS240 | 0.52 | SAB1046P | 3.86 | SN78003N | 2.81 | T8049 | 1.10 | TBA510S | 6.39 | TD41470 | 2.83 | TIC108C | 0.55 |
| GH3F | 1.85 | LM3894N01 | 1.84 | MVS460 | 0.30 | SAB30011 | 7.34 | SN78013N | 3.43 | T8052V | 0.76 | TBA520 | 1.67 | TD41512 | 2.20 | TIC108M | 0.55 |
| HA11211 | 2.30 | LM567CN | 1.30 | MVS460-02 | 0.55 | SAB30012 | 5.34 | SN78013ND | 2.25 | T8058 | 0.46 | TBA520Q | 1.35 | TD41670 | 3.85 | TIC118D | 0.80 |
| HA11215 | 4.00 | LM748 | 1.65 | ME545B | 2.95 | SAB30013 | 3.28 | SN78013NDG | 8.87 | T8059 | 1.05 | TBA530 | 0.86 | TD41770 | 5.56 | TIC44 | 0.85 |
| HA11225 | 3.90 | LM8380 | 2.78 | ME545B | 3.00 | SAB30021 | 7.18 | SN78023N | 1.35 | T8001V | 1.09 | TBA530Q | 0.85 | TD41905 | 1.25 | TIC45 | 0.70 |
| HA11226 | 7.56 | LM8361 | 2.78 | ME5534N | 1.48 | SAB30022B | 12.34 | SN78023ND | 2.04 | T9003V | 0.88 | TBA540 | 0.98 | TD41908 | 2.95 | TIC47 | 0.70 |
| HA11229 | 2.51 | M1024 | 2.55 | ME555 | 0.34 | SAB30023B | 11.18 | SN78033N | 2.33 | T9005V | 2.16 | TBA540Q | 1.15 | TD41910 | 2.38 | TIP120 | 0.98 |
| HA11235 | 3.00 | M1025 | 4.70 | ME556 | 0.75 | SAB30024 | 4.77 | SN78039N | 2.36 | T9010V | 0.87 | TBA550 | 1.95 | TD41940 | 2.50 | TIP110 | 0.46 |
| HA1124 | 4.70 | M1124 | 2.54 | ME5560N | 3.16 | SAB3209 | 4.75 | SN78110N | 1.13 | T9011V | 1.27 | TBA550Q | 2.25 | TD41950 | 2.50 | TIP112 | 0.80 |
| HA11244 | 4.32 | M1130 | 4.86 | ME565N | 1.20 | SAB3210 | 2.93 | SN78115AN | 1.46 | T9013V | 5.81 | TBA560C | 0.86 | TD42002 | 1.24 | TIP117 | 0.86 |
| HA1125 | 3.90 | M191 | 5.74 | ME645B | 3.00 | SAB4209 | 12.75 | SN78131 | 1.74 | T9014V | 1.52 | TBA560CQ | 1.15 | TD42003 | 1.05 | TIP120 | 0.73 |
| HA11251 | 3.38 | M193 | 18.55 | ME646N | 3.00 | SAF1031 | 2.30 | SN782260N | 1.20 | T9016 | 0.92 | TBA570 | 1.55 | TD42004 | 2.82 | TIP121 | 1.08 |
| HA1137V | 2.57 | M51102L | 4.82 | ME650N | 3.94 | SAF1032 | 5.80 | SN78227N | 0.80 | T9022N | 0.39 | TBA570A | 1.55 | TD42006 | 1.25 | TIP126 | 0.96 |
| HA1138 | 3.56 | M5115P | 4.34 | ME645B | 3.00 | SAF1039 | 11.86 | SN78228N | 2.97 | T9034V | 1.25 | TBA570Q | 1.35 | TD42010 | 2.79 | TIP127 | 1.30 |
| HA11414 | 2.50 | M51231P | 2.79 | MP1106 | 4.80 | SAS5010 | 7.62 | SN78231 | 2.31 | T9035V | 1.26 | TBA625A | 1.97 | TD42020 | 2.75 | TIP295 | 0.78 |
| HA1144 | 6.38 | DA200 | 4.30 | DA200 | 0.10 | SAS560 | 1.88 | SN78242 | 4.75 | T9038V | 6.15 | TBA625B | 1.97 | TD42030 | 1.85 | TIP29A | 0.41 |
| HA1156 | 1.23 | M5134-3341 | 3.75 | DA202 | 0.10 | SAS560S | 2.97 | SN78243 | 4.75 | T9051 | 2.55 | TBA625C | 1.97 | TD42140 | 1.44 | TIP29C | 0.57 |
| HA11580 | 7.80 | M51394P | 6.25 | DA47 | 0.10 | SAS560T | 2.85 | SN78232 | 2.51 | T9053V | 1.03 | TBA641A12 | 3.75 | TD42150 | 5.63 | TIP29B | 0.40 |
| HA1160 | 3.45 | M5142P | 4.30 | DA90 | 0.87 | SAS570 | 1.61 | SN78360 | 1.97 | T9054V | 0.92 | TBA641BX1 | 2.07 | TD42151 | 1.75 | TIP305 | 0.65 |
| HA1166 | 3.08 | M5143P | 6.88 | DA91 | 0.88 | SAS570S | 0.80 | SN78390 | 2.80 | T9057V | 0.83 | TBA651 | 1.80 | TD42160 | 3.84 | TIP30A | 0.41 |
| HA1167 | 5.13 | M5144P | 3.42 | DA95 | 0.88 | SAS570T | 2.50 | SN78396 | 0.93 | T9063V | 2.94 | TBA673 | 2.35 | TD42161 | 1.88 | TIP30B | 0.63 |
| HA11711 | 16.13 | M51513L | 2.06 | OC28 | 0.96 | SAS580 | 4.41 | SN78510N | 2.85 | TA5814 | 1.35 | TBA700Q | 2.19 | TD42190 | 3.11 | TIP318 | 0.25 |
| HA11713 | 6.70 | M51515BL | 3.10 | OC29 | 1.95 | SAS5800 | 2.62 | SN78520P | 1.80 | TA7020P | 4.36 | TBA720 | 2.05 | TD42510 | 1.82 | TIP31C | 0.63 |
| HA11714 | 7.05 | M51516L | 3.40 | OC35 | 0.96 | SAS590 | 4.55 | SN78523N | 1.90 | TA7027 | 4.26 | TBA730 | 1.75 | TD42520 | 2.15 | TIP32B | 0.35 |
| HA11715 | 7.05 | M51517L | 2.90 | OC36 | 1.16 | SAS5900 | 2.32 | SN78533N | 1.56 | TA7050 | 1.58 | TBA750Q | 1.46 | TD42521 | 2.81 | TIP32C | 1.66 |
| HA11718 | 6.79 | M5152L | 1.00 | OC44 | 0.40 | SAS680 | 2.50 | SN78540N | 1.80 | TA7051 | 1.58 | TBA760 | 1.55 | TD42522 | 2.15 | TIP33C | 0.25 |
| HA11724 | 15.80 | M51522 | 4.90 | OC45 | 0.40 | SAS6800 | 1.20 | SN78544 | 1.60 | TA7060AP | 0.80 | TBA780 | 3.00 | TD42523 | 2.75 | TIP34 | 1.07 |
| HA11725 | 16.80 | M5191P | 4.49 | OC75 | 0.40 | SAS680S | 1.20 | SN78545 | 4.55 | TA7061AP | 0.78 | TBA800 | 0.80 | TD42524 | 4.50 | TIP41A | 0.39 |
| HA1180 | 4.88 | M5192 | 2.00 | DN188 | 1.70 | SAS6810 | 1.20 | SN78546 | 3.15 | TA7069 | 2.84 | TBA810AS | 1.46 | TD42525 | 2.96 | TIP41B | 0.48 |
| HA1203 | 1.56 | M53273P | 0.92 | ON236 | 2.90 | SAS670 | 2.50 | SN78546N | 3.15 | TA7070P | 1.52 | TBA810S | 1.46 | TD42530 | 2.19 | TIP41C | 0.24 |
| HA1306 | 1.74 | M53274P | 1.20 | OT112 | 0.98 | SAS6700 | 1.20 | SN78549 | 2.35 | TA7071 | 3.35 | TBA810T | 1.46 | TD42532 | 2.51 | TIP42A | 0.39 |
| HA1322 | 1.74 | MA06 | 0.97 | OT121 | 0.70 | SAS670S | 1.20 | SN78560 | 0.30 | TA7072P | 1.35 | TBA820 | 0.83 | TD42533 | 2.09 | TIP42B | 0.71 |
| HA1339 | 1.78 | MA8001 | 0.74 | PD144 | 2.83 | SAS6710 | 1.20 | SN78561 | 1.35 | TA7073P | 4.05 | TBA820M | 1.65 | TD42540 | 1.95 | TIP42C | 0.44 |
| HA1342 | 1.90 | MB3705 | 1.62 | PT1017 | 2.43 | SAS6800 | 2.30 | SN78570 | 2.80 | TA7074P | 1.95 | TBA890 | 1.85 | TD42541 | 1.95 | TIP47 | 0.65 |
| HA1350 | 2.87 | MB3712 | 2.65 | PT2014 | 2.76 | SAS6810 | 1.30 | SN78600 | 1.10 | TA7076P | 4.95 | TBA900 | 2.25 | TD42545Q | 3.17 | TIP48 | 0.68 |
| HA1365 | 3.85 | MB3713 | 1.30 | PT8042 | 1.82 | SBA550B | 1.95 | SN78611 | 2.85 | TA7089N | 1.41 | TBA920 | 1.50 | TD42560 | 1.96 | TIP49 | 3.23 |
| HA1366VVR | 1.82 | MB3730 | 2.94 | R1038 | 1.99 | SBA750 | 1.46 | SN78620 | 2.50 | TA7089P | 1.36 | TBA920Q | 2.10 | TD42571A | 2.81 | TIS43 | 1.21 |
| HA1367 | 3.29 | MC13002 | 4.86 | R1039 | 1.99 | SC948P | 1.90 | SN78622 | 1.35 | TA7092P | 3.85 | TBA940 | 1.70 | TD42575A | 2.95 | TIS90 | 0.22 |
| HA1368 | 1.80 | MC1303P | 1.96 | R2088B | 1.50 | SC9503 | 1.50 | SN78623 | 0.82 | TA7093P | 1.64 | TBA950 | 1.55 | TD42576A | 2.58 | TIS91 | 1.21 |
| HA1368R | 1.86 | MC1307P | 1.90 | R2089 | 1.20 | SC9504P | 1.46 | SN78630 | 3.81 | TA7093P | 1.58 | TBA950 | 1.55 | TD42576B | 2.58 | TIS91 | 1.21 |
| HA1370 | 2.97 | MC1310P | 1.25 | R2001B | 1.20 | SC9511P | 1.90 | SN78640 | 2.35 | TA7102P | 5.34 | TBA970 | 2.88 | TD42577A | 5.31 | TL071CP | 2.06 |
| HA1377 | 2.08 | MC1327P | 1.29 | R2029 | 1.20 | SC9557 | 1.20 | SN78650N | 1.24 | TA7108P | 1.40 | TBA970Q | 2.98 | TD42581 | 1.98 | TMS1000NL | 10.78 |
| HA1389 | 1.82 | MC1330P | 1.23 | R2030 | 1.20 | SG264A | 4.38 | SN78651 | 1.35 | TA7120P | 0.37 | TBA990 | 1.65 | TD42582 | 1.98 | TMS3748NS | 11.86 |
| HA1389R | 1.74 | MC1349P | 1.20 | R2257 | 2.16 | SG613 | 7.88 | SN78660N | 1.25 | TA7122B/P | 0.54 | TBAZ31 | 2.33 | TD42590 | 2.80 | TMS4116 | 1.87 |
| HA1392 | 2.88 | MC1350P | 1.10 | R2265 | 1.95 | SG629 | 6.28 | SN78665N | 1.35 | TA7124P | 2.00 | TCA001 | 1.29 | TD42591 | 2.80 | TV106 | 1.20 |
| HA1397 | 2.97 | MC1351P | 0.75 | R2305 | 1.07 | SG633 | 9.37 | SN78666N | 0.98 | TA7130P | 1.15 | TCA053BP | 3.94 | TD42593 | 2.80 | TV10810B | 2.70 |
| HA1398 | 2.88 | MC1352P | 1.01 | R2306 | 1.23 | SI-1020N | 4.76 | SN78670S | 3.98 | TA7136AP | 1.15 | TCA150 | 1.82 | TD42594 | 2.80 | U05G | 1.03 |
| HA1406 | 1.80 | MC1357P | 1.95 | R2322 | 1.26 | SI-1125HD | 10.70 | SN78705N | 3.99 | TA7137P | 0.85 | TCA160B | 1.82 | TD42600 | 5.50 | U143M | 2.80 |
| HA17723 | 5.40 | MC1358P | 1.55 | R2323 | 1.23 | SI-1130N | 6.30 | SN78707N | 3.99 | TA7141AP | 3.51 | TCA270Q | 1.55 | TD42610 | 2.53 | U3700 | 0.54 |
| HBF4030AF | 2.25 | MC14001 | 7.15 | R2348 | 1.82 | SKB2/04 | 0.70 | SN78709 | 4.85 | TA7146P | 8.84 | TCA270S | 1.95 | TD42611A | 1.25 | UA723CA | 4.02 |
| HD4480 | 15.80 | MC14011 | 0.23 | R2354A | 1.82 | SKB2F 1/04 | 1.26 | SN78709N | 4.95 | TA7146P | 1.51 | TCA270S | 1.65 | TD42611AQ | 2.55 | UA758PC | 3.06 |
| HD44801A05 | 15.90 | MC14013 | 0.37 | R2354B | 1.82 | SKB2G 2/04 | 0.95 | SN78730 | 4.23 | TA7149P | 2.10 | TCA290A | 2.05 | TD42612Q | 1.95 | UA763PC | 2.14 |
| HME6231 | 8.50 | MC14016CP | 0.37 | R2441 | 1.23 | SKB2G 3/04 | 0.95 | SN78810N | 0.82 | TA7153P | 4.53 | TCA420A | 1.90 | TD42620 | 4.26 | UAA170 | 1.87 |
| HME6232 | 7.71 | MC14025 | 0.54 | R2443 | 0.80 | SKE4F 1/02 | 1.26 | SN78920N | 2.83 | TA7161P | 5.86 | TCA440 | 1.85 | TD42630 | 2.34 | UAA180 | 1.35 |
| HME9102 | 2.92 | MC14049UBC | 0.52 | R2461 | 2.10 | SKE4F 1/06 | 0.66 | SN94041 | 4.25 | TA7162P | 4.25 | TCA4500A | 1.95 | TD42631 | 2.48 | UAA190 | 2.14 |
| HME9104 | 2.94 | MC1438R | 0.95 | R2477 | 0.92 | SKE4F 2/06 | 2.10 | SN94042 | 3.95 | TA7169 | 4.80 | TCA530 | 1.80 | TD42640 | 6.25 | ULN2204 | 1.95 |
| HT4207 | 15.80 | MC14433P | 2.56 | R2501 | 1.16 | SKE4F 2/08 | 0.80 | SP8385 | 0.50 | TA7171P | 2.53 | TCA640 | 2.83 | TD42643 | 2.93 | ULN2218F | 7.80 |
| IS689 | 1.87 | MC14510BAL | 3.15 | R2540 | 1.80 | SKE4G 2/02 | 0.87 | ST4441C | 3.27 | TA7172P | 1.28 | TCA650 | 1.85 | TD42643 | 2.95 | UPC1001H | 5.50 |
| IS751 | 1.87 | MC14556BCP | 3.15 | R2540X | 3.00 | SKE5F 3/10 | 1.45 | STK0029 | 2.42 | TA7176P | 2.25 | TCA660B | 2.63 | TD42652 | 7.85 | UPC1009C | 2.74 |
| ITT2003 | 0.20 | MC1712 | 3.52 | | | | | | | | | | | | | | |

VCR Clinic

Tony Thompson, Steve Beeching, T. Eng. (C.E.I.), Mike Phelan, Ian Hutton, Peter Dolman, Les Grogan, Malcolm George, Hugh Allison, John Coombes and Peter Blundell, Tech. (C.E.I.)

Panasonic NV333

A couple of faults on this otherwise quite reliable machine have come to light on a number of occasions. First, if the customer tends to use the wired remote control and the machine won't respond to on-board commands, working only with the remote control system, it's a good idea to change the minijack remote control input socket. This is a weak link and can go open.

Secondly, when a cassette has been loaded but the machine won't respond to any commands, even eject, don't get too involved before you've checked the cassette-down switch. This little devil lives under the main board and is a bit fiddly to get at due to the construction of the machine. It's a simple looking device with thin, long springy contacts. To check, bridge across it with wire: the machine should then respond to all function commands. It can be cleaned up but won't last. A replacement is necessary, though you can leave it bridged across as a temporary measure. **T.T.**

Grundig 2 x 4 Super

One of these machines would occasionally refuse to go into playback – it would move the loading ring slightly, then return to stop. Fast forward and rewind were o.k., but search fast forward and rewind did the same. We finally found that the autostop adjustment (BEA) was slightly out: the autostop worked, but in all modes except fast wind the too sensitive adjustment prompted the stop mode. **M.P.**

Hitachi VT9700

This machine had given us trouble for over a year. Every time it was brought in with the complaint that it ran slow it worked normally, much to our customer's embarrassment. Even bench testing with a scope tied to the servo failed to show anything amiss. Eventually, while on the bench for the umpteenth time, it stopped dead in its tracks. The capstan motor had seized solid, but by now it was some five months out of guarantee. Anyway I sent the motor to Hitachi with a covering letter describing the problem and asking whether they could see their way to supplying an under-guarantee replacement. Those nice people at Hitachi sent me one FOC and after fitting it the machine ran fine. For an hour or two anyway, then the original fault appeared, the first time we'd seen it.

After a certain amount of probing about we found that the output from the capstan servo sample and hold circuit was a squarewave, which also made the machine warble badly. The capstan trapezoid wasn't there and the charging capacitor C506 was found to be hanging on by only one leg. Refitting it restored normal operation. **S.B.**

JVC HRC3

It seems that all the world knew about it except me, and maybe some of you. It came to pass that a customer with a JVC HRC3 mini portable VCR had problems. These occurred when his recordings were placed in a cassette adaptor and then into an Hitachi VT19. At the beginning

of each new recording the VT19 would go into the LP mode for about five-ten seconds. Not a lot, but it seemed like ages before it reverted to normal speed. Well, I blamed the Hitachi VCR, which has suffered from certain problems (clock display keeps resetting; motorboating on one of the audio channels). Not so however – the same difficulty arose when a two-speed JVC HR7655 was tried. The problem lies within the HRC3's control track pulse recording level circuit. But don't try to do the modification yourselves – you'll only end in tears! **S.B.**

Odds and Ends

As if boards with double sided print aren't enough, the latest information on the new JVC camcorder (GRC1) to be launched this autumn has it that there will be "dedicated i.c.s, special four-layer boards and increased component density". Only a fool would try to repair one without specialised knowledge.

Did you hear about the stereo hi-fi VCR that records stereo audio on the helical tracks but has only a mono static head, thus making it non-compatible with current stereo VHS tapes? Panasonic did. So beware Sony – inside information from a long way away indicates that at least one Beta manufacturer has done the same thing. The audio switching is left, right and normal. Left and right are the new hi-fi channels and normal is a mono static head. Good authority has it that the forthcoming JVC HRD725 hi-fi will have a stereo static head. **S.B.**

Mitsubishi HS310

Playback was not possible because the head drum was running at the wrong speed. A recording was made and played back on another machine. This was successful, so whatever was wrong was something that acted on the drum servo on playback but not on record. On record the reference signal is obtained from the field sync. On playback the signal is divided down from the 4.433MHz crystal oscillator on the YC board – the oscillator and divider are both in IC6F3. Checks showed that both these signals were missing. Spraying the crystal (X6F2) with freezer restored normal operation and a replacement cleared the fault. **I.H.**

Ferguson 3V35

This machine came in with the head drum running at about 3,000 r.p.m.! Slowing it down by hand gave quite a good picture. We first checked the supply voltage to the HA13008 drum motor amplifier chip (IC407), having been caught out by this before. It was spot on at 13V. The HA13008 and quite a few other bits had been changed. We moved back to the preceding error amplifier chip and found that the drum phase error input (pin 12) was bouncing around all over the place while the drum speed input (pin 13) was low. As pin 13 goes low to increase the motor's speed, this meant that the fault was prior to this point – had it been high, this would have meant that the fault was between this point and the motor, and that the servo was making an attempt to correct the situation.

The FG feedback signal was o.k. in amplitude at pin 3 of the BA6328 drum speed discriminator chip IC404, where it enters for amplification, but the output at pin 4 was low and noisy. There's a feedback loop between these two pins and the culprit was in this network – C465 (100pF) was leaky. **M.P.**

Mitsubishi HS310

Several of these machines have been brought to us with vague complaints such as "sometimes stops in the timer mode, I think" and "just won't run satisfactorily". They've all worked faultlessly in the workshop however. Following much inaccurate speculation, the cause was eventually found to be a simple one – failure of the cassette lamp. The type used has a nasty habit of going open-circuit intermittently and momentarily, thus returning the machine to the stop mode. A defective lamp can usually be identified by watching for changes in its brightness while administering a deft flick with the thumb and forefinger. **P.D.**

Hitachi Disc Player

Sound o.k. but very weak video was the complaint with this disc player. We bypassed the r.f. modulator by feeding directly into the TV set's video input socket. The modulator is fed by an emitter-follower transistor (Q503) and we could find little when we made a scope check at its emitter (TP43). Furthermore Q503's collector voltage was only 5.4V instead of 10.8V. The 10.8V output from the power supply was correct (TP91) and the only thing between this and the collector of Q503 is the filter resistor R574 (2.2Ω, 0.25W). Replacing this cleared the fault. **L.G.**

Sony C7

The customer brought in a dusty looking C7 saying that it had stopped, a puff of smoke coming from just above the clock display. Checks in the power supply revealed that the chopper transistors Q101/2 were short-circuit while the resistor in series with them (R101) was open-circuit. Ah ha! I thought, I've read about this one (January 1984). So I sent off to Sony for the A6738-159A replacement kit. This was fitted and the power supply was run up under no load conditions, performing o.k. The rest of the C7 was powered from a 12V bench supply and produced talking pictures with colour, without taking too much current. So the power supply was confidently refitted and all plugs and sockets were connected. Guess what happened when I turned on? Another puff of smoke and Q101/Q102/R101 had again bit the dust. Further checks revealed that the two 4.7μF electrolytics associated with Q101/2 had fallen in value to something like 0.5μF. Sony replacements for all these items provided a final cure, but the next time it happened to me I decided that BU408s and 4μF, 350V electrolytics seem to provide a cheaper, reliable solution. **M.G.**

Akai VS5EK

While chatting up one of our lovely secretaries it transpired that she had to take her video cassettes round to a neighbour's house to rewind them since her machine would only play and record! When we checked the machine, attempting either fast forward or rewind created a furious "bleeping" and the ejected cassettes came out with a foot of tape hanging loose.

A look over the top mechanics revealed that the fast forward/rewind jockey wheel wasn't moving: careful examination underneath then revealed that the spring connecting the jockey wheel and the tape supply wheel brake had broken. This spring is well obscured by a lever, and is an experiment in self-control to replace. Since half the broken spring was missing, the unit was held "right way up" and gently shaken until the spring fell out – along with two hairgrips, a paper clip and a dead moth . . . **H.A.**

Ferguson 3V22

The problem was loss of line lock on playback. The drum pickup head was producing output pulses but the waveforms around the AN318 drum servo i.c. didn't seem to be of the correct shape. Replacing the chip cured the trouble. **J.C.**

Ferguson 3V30

When the machine was switched on the cassette's supply reel would rotate for approximately ten seconds then stop. After this no commands would be accepted. I at first suspected the end sensor of being leaky, but a replacement didn't provide a cure. It was then noticed that the same thing happened if no cassette was present. Checking the inputs to the control microcomputer i.c. showed that the unload switch wasn't making contact. **P.B.**

Sharp VC9700

This machine would work perfectly for about four hours. Hooking at the top of the picture would then start. Removing the covers cleared the fault of course, but no amount of board heating with a hairdryer would make it return. At this the covers were replaced and the machine was left to warm up. During a lull in the passing traffic we noticed a rubbing sound. This was finally traced to the head drum bearing – pricey . . . **P.B.**

Sharp VC8300

We've had quite a few of these machines that will load and eject a tape but do nothing else. If the bulb is o.k., the fault is usually a crack in the connector panel below the solenoids at the front of the deck. Amongst other things this panel connects the cassette-down switch with the system control microcomputer. It's necessary to remove the tape deck to repair the panel, but this isn't difficult. **M.P.**

Sanyo VTC5300

Intermittent failure to lace up or eject is generally caused by excessive resistance to travel of the loading ring. Clean the loading motor belt and sparingly lubricate the rollers that engage with the cam on the loading ring. If the fault persists, replace the reel/loading motor which probably has a dead spot. The reason for this is that it doesn't take kindly to being stalled: the commutator metal wears away, leaving exposed insulation – hence the dead spot. **M.P.**

Sanyo VTC5000

One of these machines came in with the complaint "intermittent lines on the picture on its own recordings". Sure enough the drum servo lost lock occasionally on

record – it varied with picture content. A scope connected to pin 10 of the BA848 servo i.c. showed that there were twice as many pulses here as there should have been – the rate was 50Hz. The input to the sync separator in this i.c. (pin 13) seemed to be o.k. but there was a very small pulse midway between the field sync pulses. This wasn't present

with a video input, the servo then working all right. While checking around the i.f. strip we noticed that the picture looked as though the a.f.c. was off tune. And that was it – not by enough to cause patterning, but enough to upset the sync separator action by emphasising h.f. transitions from peak white (on captions etc.). M.P.

Servicing the Grundig GSC100 Chassis

Denis G. Mott

During the past two-three years I've had to deal with a large number of these sets. This has enabled me to compile a faults list which I hope will be of help to other engineers. The chassis consists of a large, vertical main panel with a number of modules that take care of various circuit functions. The tubes are of the 90° in-line gun type while the line output stage is of the thyristor type. Unlike earlier Grundig colour chassis that employed a transducer for width/e.h.t. regulation, in this chassis a thyristor driven by a rather unusual circuit (more on this later) is used for the purpose. There are no less than six thyristors dotted around the chassis – e.h.t. regulator (Ty503), line scan and line flyback (Ty508 and Ty501), line generator start-up (Ty607), excess current trip (Ty615) and overvoltage trip (Ty2517).

Power Supply

We'll start with the power supply. Fig. 1 shows the basic power supply arrangement (in addition, 200V and 18.6V supplies, fused by Si629 and Si627 respectively, are derived from the line output stage). It's uncanny how many phone calls I get about this. As soon as people see a thyristor they throw up their hands in horror! In normal operation, a supply (+B13.5V) derived from the combi coil is used to power the line generator and e.h.t. control modules. So a start-up supply is required. This is provided by Ty607 whose anode is fed via the fusible resistor R607. The output is limited by the 10V zener diode Di607. Once the line timebase has come into operation, Di511 rectifies pulses developed across a secondary winding on the combi coil, feeding the Darlington series regulator transistor Tr635 via fuse Si511 and the fusible resistor R632. Assuming that there's no fault condition, the regulator circuit produces a 15V supply and Tr608 switches on, shorting the gate of Ty607 to chassis to disable the start-up system.

One of the most common conditions is no results due to R607 having sprung open. In this event, check the following: Ty607 short-circuit; Tr608 open-circuit or low gain; R608 high in value; R633 high or open-circuit; no 311V h.t. supply; no output from the line generator module; no drive to Ty503 from the e.h.t. control module; Si511 or Di511 open-circuit; Ty503 open-circuit; Di636 low voltage. This covers 90 per cent of faults causing R607 to ping. The cause of R621 in the h.t. supply being open-circuit is usually excess current trip operation due to a line output stage fault.

Excess Current Trip

The excess current trip module gives relatively few problems. If Ty615 has gone open-circuit there'll be no h.t. supply of course; if it's gone short-circuit there'll be no

protection until R621 pings. The operation of this circuit is as follows. If a fault condition causing an increase of 100 per cent in the h.t. current occurs, the voltage developed across R621 will increase from approximately 9V to 13V plus. As a result zener diode Di619 will conduct, turning on Tr618 to short Ty615's gate-cathode junction so that it switches off. The time-constant of C618/R618 is approximately 120msec, so that the trip "oscillates" until R621 pings. To check the operation of this module, connect a 10kΩ resistor from the junction of R619 and D619 to chassis: the module should now oscillate at the trip frequency.

EHT Control Module

The e.h.t. control module (see Fig. 2) may come as a surprise. TTL in a line timebase! Very useful actually. Here's how it works. IC2511 is a monostable multivibrator which is triggered at pin 5 by pulses from the line generator module. The multivibrator's on time is set by the time-constant network R2514/C2513. It's output at pin 1 is capacitively coupled to Tr2506 which provides a transformer coupled drive to the regulating thyristor Ty503. Pulses from the line output transformer enter the module at pin 9 and are rectified by Di2521/C2522. The resultant supply controls transistor Tr2516 which in turn controls the supply to the monostable's time-constant network, thus providing e.h.t./width regulation. The same line output transformer derived pulses enter the module at pin 8. Under excess voltage conditions Di2517 and in turn Ty2517 conduct, shutting the whole operation down.

The usual fault conditions are as follows. C2507 changes value, reducing the drive to Tr2506 which gets hot and dies due to the slower turn-off time. Ty2517 goes short-circuit, with the result that the monostable doesn't trigger. Zener diode Di2502 goes low which upsets things because TTL devices like a supply of 5V or thereabouts.

If you can't adjust the set e.h.t. control R2523, change the 9.1V zener diode Di2516. Then set the control midway, reinsert the module, monitor tag b on the line output transformer with an AVO 8 or 9 and adjust R2523 for 49V d.c. This will give correct e.h.t. and width. If you wind the control too far Di2516 will snuff it, so be careful.

Line Output Stage

Thyristor line output stages are not the easiest circuits for fault finding. The problem is that it either works or it doesn't, no half ways. A very useful tool is the transistor/thyristor tester featured in the June 1981 issue, since this enables you to check the power devices in situ before substitution. If you don't have a tester, the following checks and observations are worth making.

R621 and maybe R607 in the power supply will usually

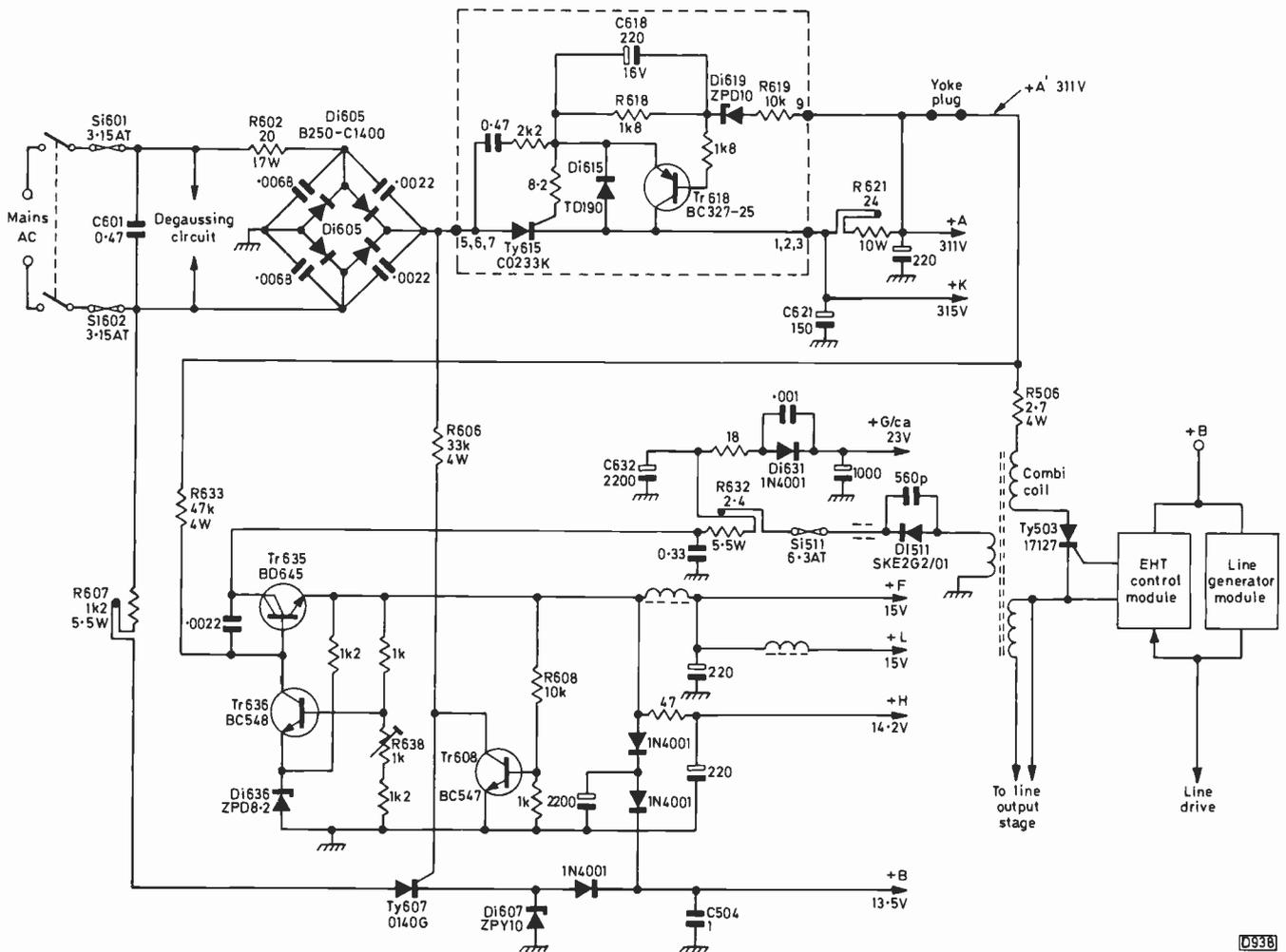


Fig. 1: Power supply arrangements used in the GSC100 chassis.

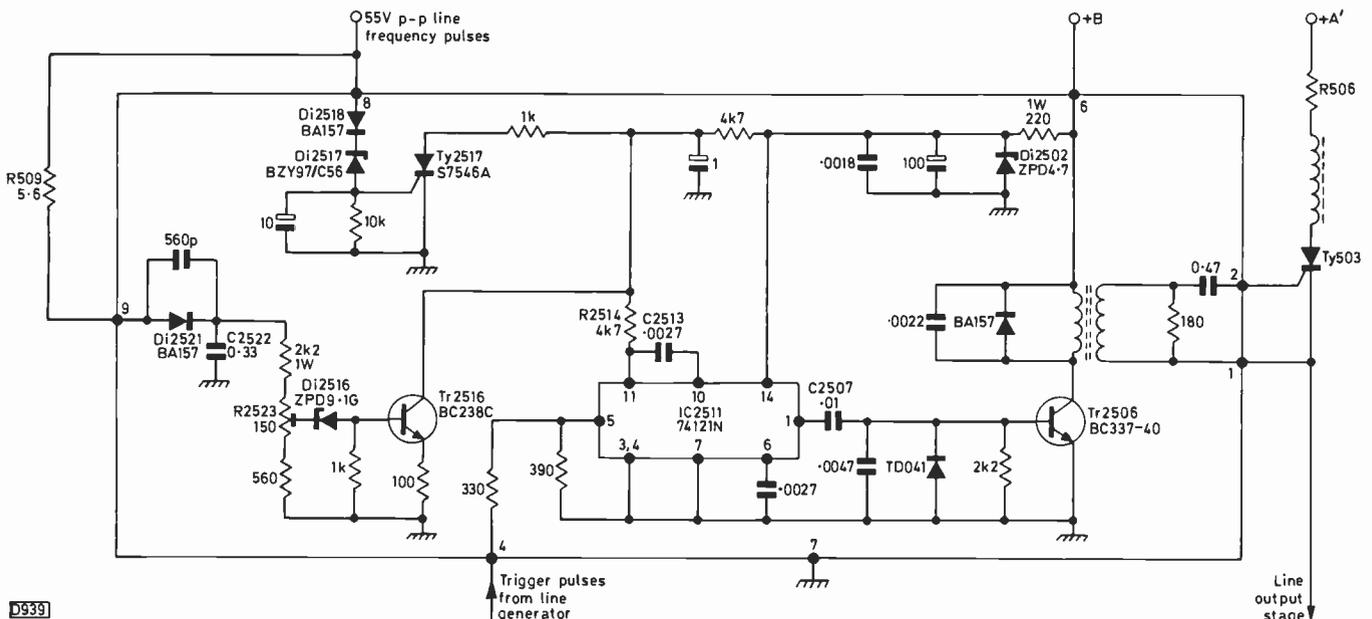


Fig. 2: E.H.T. control module circuit.

have pinged. When resoldered, the trip module will "plop" repeatedly, proving that excess current is flowing. If disconnecting the anode of the flyback thyristor Ty501 stops the tripping, it's probably short-circuit. If the set continues to trip, replace the scan thyristor Ty508 as it may be open-circuit. Also check the efficiency diode

Di508. Try disconnecting the tripler. Check the continuity of the scan coils, and the scan-correction capacitor C526 (2.3µF). It's also worth inspecting the solder around R502 (180Ω, 11W) in the scan thyristor's gate drive circuit – it gets a bit hot and tends to get dry-jointed.

I always replace devices in this area with exact Grundig

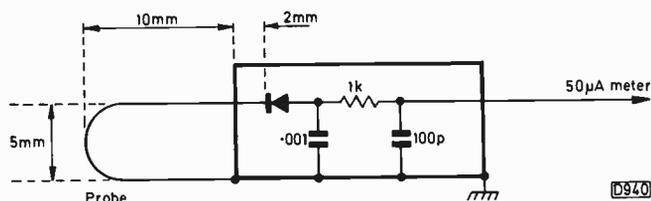


Fig. 3: Diode sniffer probe. Can be built on Veroboard.

replacements and not other types, though alternatives may be o.k. The line output transformer and combi coil don't readily fail, though I suppose some engineers will have found duff ones.

A useful tool, essential when running up a GSC100 line output stage, is a 2A variac. It saves on fuses and nerves.

Line Generator

The only problems we've had with the line generator module concern the TDA2591 chip. If the module fails to oscillate at start up the chip may be faulty – some are a bit funny about the voltage when cold.

The Field Timebase

The field timebase module employs a TDA1170 i.c. There've been some odd faults in this area. C441 (0.22µF) leaky causes poor field sync. Tr467 leaky causes funny field flyback blanking – sometimes almost anywhere during the field period. The field scan coupling capacitor C473 is on the main panel: when it's leaky or short-circuit the result is field collapse with the line shifting upwards to near the top of the screen.

Audio Module

There's little to report about the audio module apart from the TBA800 i.c. occasionally dying.

IF Module

The smoothing capacitor C2321 (10µF) on the i.f. module is a tantalum type and can go short-circuit, R607 eventually pinging. Don't forget that there are separate chroma and luminance outputs, with the chroma signal inverted. If you suspect that the SAWF is out of specification, the writer has access to a sweep generator especially designed for use with this module – contact is welcomed.

The Tuner

The tuner used by our company is of the v.h.f./u.h.f. type, part no. 29500. For many people, delving into tuners is taboo. If certain ground rules are observed however many common faults can be cleared.

Tuning drift or failure to tune is caused by one of the varicap diodes going leaky. These diodes normally have a very high impedance and any leakage at all will cause drift. The best method of tracing this fault is to connect a sensitive d.c. meter, switched to 50µA, in series with the varicap control line, disconnecting each of the diodes in turn until the current returns to zero. Replace these diodes with the exact type – no substitutes.

The r.f. amplifier transistor Tr118 tends to go sick after a thunderstorm. To confirm this, inject a signal via a loop into the output tuning area – some sort of signal should then be evident. To check that the mixer circuit is

operating, use the diode sniffer shown in Fig. 3. Insert the probe near the tuning elements and check for r.f. from ch. 21 to ch. 68. If any component has to be replaced, observe exactly how the original was fitted before removing it. Fit the replacement in the same way, otherwise severe mistuning may occur.

RGB Module

The RGB module can present difficulties due to the feedback paths. If a number of panels need repairing it's worth finding a good one and fitting a 24-pin i.c. socket so that the TDA2800 i.c. can be proved before making further investigations. Most faults occur in the RGB output stages however. Here are one or two odd faults: no luminance, C907 (22µF) or the delay line (on the main panel) open-circuit; no luminance and low brightness, C977 (2.2µF) leaky.

There are obviously many internal faults that could occur in the i.c., causing obscure symptoms. Some less common faults we've had on the module are as follows. R1919 open-circuit, no contrast control. Zener diode D1948 open-circuit or L1920 high-resistance, uncontrollable brightness. Other faults depend on which output stage is involved. For the red output stage, R1904 open-circuit causes a tint of that colour on the background and loss of h.f. response; C1912 or C1914 leaky causes no red; R1911 open-circuit results in full beam current, as does T1908 going leaky or short-circuit; T1901 going short-circuit causes no colour. The relevant components in the blue and green output stages give analogous faults.

Chroma Module

Many chroma module faults are due to the two i.c.s (TDA2510 and TDA2521). There seem to have been difficulties with the TDA2521 as at least three versions were made, the TDA2521/3 being the latest. If there's no colour, check the colour burst level at pin 7 of IC861. It should be 0.5V peak-to-peak. Under fault conditions it may rise to 2.5V p-p and not be controllable with R827. Check C833 which could be leaky, IC861, and C823/832 which could be open-circuit. If there's still no colour, check the reference oscillator and its tuning. As with the RGB module, if you've many panels to look after it's worth fitting i.c. sockets to a known good one for use as an i.c. test bed. If the R – Y or B – Y signals are missing, suspect IC861 and either L854 or L857 for being open-circuit. If R828 has burnt up, check whether C831 is short-circuit. Di881 (12V zener diode) leaky causes green flashing lines while C809 causes weak flashing colours.

As mentioned in a letter (June issue) C843 must be changed to 0.0047µF if you have a colour locking problem with the Sinclair Spectrum microcomputer.

In Conclusion

I hope this article has shed light on the problems that can be encountered with the GSC100 chassis. Most of the comments also apply to the GSC200 chassis which differs in only minor respects from the GSC100 (vision i.f. module, tuning system and the inclusion of a relay board). The author is Service Manager of Network Industries (Haycliffe Lane, Wisbey, Bradford). Finally the editor wishes to apologise for an error in last month's next month box: the width/e.h.t. control system is not of the current-dumping variety as was assumed from a quick glance at the circuit.

Letters

THE DECCA 100 CHASSIS

I've bought a lot of Decca 100s in the past and thought I knew all there was to know about them. Recently however I bought two of them, cheaply, with the same fault. I was told that every panel had been changed in both sets.

The fault was as follows. Both sets had been fitted with regunned tubes and after being switched on produced perfect BBC-1 pictures but severe picture judder on BBC-2, ITV and the Welsh channels. The only way to clear the fault was to lift the chassis upwards about six inches from its downwards position. On lowering the chassis the fault reappeared.

My first thought was that there might be some interaction between the line and field, so a good deal of time was spent moving wires, checking plugs, etc., all to no avail. But why was BBC-1 all right?

The TCA270 vision demodulator i.c. plugs in, so replacing this was simple. Still the same. Next try the MC1349 i.f. amplifier i.c. A little bit more difficult as the iron has to be used. Start to remove i.f. panel with the set still on, grabbing C110 to hold panel. Lo and behold, the fault clears! Replace C110 and all is well. Do same with second set and the result is two good sets ready to go out on rental. C110 (0.01 μ F) acts as a filter at the MC1349's a.g.c. input pin 5. I hope this warning about an obscure fault may help others.

Ted Lunt,

Great Sutton, South Wirral.

ECONOMICS OF SERVICING

A couple of recent items prompt me to write a few words on the economics of fault finding. The point that concerns me is how much time one should spend on a repair before starting to replace likely components, particularly with an intermittent fault. Take Malcolm Burrell's a.g.c. fault in the June issue. A very neat piece of detective work to arrive at C10 as the culprit, but the time spent setting up the biasing and connecting it to the various stages, also the equipment tied up, couldn't be justified in many firms where sets have to be turned around fairly quickly to avoid a backlog building up. There often comes a point where the fault is narrowed down to perhaps as many as a dozen or so components and the cost of replacing these en masse is less than the cost of the time that might be required to narrow down the cause of the fault further. You don't learn as much this way of course, so beginners in the trade should be encouraged to go the whole way – after all they're expected to take longer with repairs.

I freely admit that after a few quick checks, e.g. on supply lines and oscillators, and with signal faults a couple of scope waveform checks, I'll change a couple of likely items before making a more detailed study of the fault. I'm perhaps lucky in that we keep most spares in stock, including i.c.s, and that components don't seem to get damaged when removed, i.e. they can be replaced if the fault isn't cured. This may not be the most elegant way of doing repairs, but it gets results and in my experience achieves a higher repair turnover (with no more "bouncers" than with other methods). I think this must be particularly the case with intermittent faults. We

all know that they never happen when you want them to, and having to tie up the only scope and maybe half the meters whilst waiting for the fault to appear can delay other repairs. You may say use two scopes, but they're expensive – and what happens when you get two sets with intermittent faults that tie up scopes? Do you go out and buy a third?

There will always be the occasional set that doesn't yield to this approach, but then you also get the occasional fault that seems to defy logical analysis. Obviously the "proper" repair method shouldn't be given up entirely. Do the occasional one in slack moments to keep your hand in – also stick to the full routine until you're confident that you can narrow the fault down to a particular component if necessary.

*Derek Snelling,
Brownhills, Staffs.*

CLOCKS AND FUNNIES

In July's VCR Clinic Derek Snelling mentioned an ITV teletext clock time discrepancy. I've also seen this from time to time (sorry!). I suspect that it's due to the insertion of local magazines in the national Oracle broadcasts when they are used in the regions. The time is derived from a local source and not taken from London, so either could be "out" by a few seconds.

There are other funnies with Oracle. Headers containing clear-page bits are quite often repeated several times per frame, which can confuse some decoders. Also some data lines occasionally disappear for no apparent reason!

Laurence Cook,

Appleby-in-Westmorland, Cumbria.

ELECTRONIC CUTOUT

I think that Ged's cutout (July) is an excellent idea but wonder whether its cut off delay isn't perhaps rather long. Since the current detector is only half-wave, overloads that occur on the undetected half cycle are not passed on to the comparator until the next half cycle. The relay drive then works quickly but the relay itself will take 20msec to operate. So three or four half cycles of overload current pass uninterrupted. This must be much longer than a TX9's mains fuse takes to blow when the crowbar trips, and could invite more damage. Ged didn't say whether he still had the fuse in circuit, but I presume not as it would probably blow first in a crowbar set. I'm tempted to build a cutout but would prefer to use full-wave detection and triac power switching so that the first overload half cycle is also the last.

*G. M. Colebourn, Colebourn Electronics,
St Albans, Herts.*

Ged Whitney comments: I considered using a bridge rectifier instead of the half-wave circuit but to be honest the reason why this was not adopted was simply that the cutout seemed to work just fine without it, so I left it at that. The unit has been tried with a large number of sets since it was built some months ago and on only one occasion has the set's mains fuse blown – I think this was due to my inadvertently setting the trip too high.

In use I set the cutout so that it operates just a little way above the normal running current. For a set that consumes 80W, this will be approximately 0.33A, so a setting for 0.4A would normally be o.k. and assuming that a 1.6A semi-delay fuse is fitted there should be adequate time for the trip to operate. Information gleaned from a number of

sources reveals that a 1.6A semi-delay fuse takes about 60–80msec to rupture at ten times rating. As I don't have access to any transient recording equipment I accept Mr. Colebourn's estimate of a 20msec relay operating time.

A look at the TX9 circuit (PC1040 main panel version) shows that the crowbar thyristor CSR2 is connected in series with the mains fuse via the h.t. reservoir inductor L65, the regulator thyristor CSR1, the mains bridge rectifier and the mains filter coil L64, all of which should limit a surge current to some extent. If these components are damaged when the 1.6A mains fuse blows then the use of a crowbar arrangement appears to be dubious. Either way I think my unit would be preferable to say a thermal cutout wired across the fuseholder as suggested elsewhere in the July issue – as mentioned in my article, I tried this and it certainly didn't work for me!

I agree that a full-wave bridge rectifier would be an improvement. When I originally set down some thoughts on paper I roughed out a circuit with two operational amplifiers and a dual-gang potentiometer as the comparator, sensing the peak a.c. value directly without the use of rectifiers etc. The outputs from these operational ampli-

ers were to be summed and fed to a CMOS latch, then via an optocoupler to a triac. At the time this seemed to me to be too complex for what was being asked of it, so I settled for the transistor circuit. The relay was used because I wanted genuine isolation – and because it was convenient.

I'd be interested to see alternative designs. Any improvement on a basic idea is a good thing, and if we engineers can provide ourselves with better "mousetraps" our jobs will be that much easier.

GREAT PLUGTOP MYSTERY – CONT.

Some of the plugtops in use in my flat and the one in my workshop are never subjected to any kind of "wagging" (see letters July) yet their neutral pins still cook when cooking occurs. I've seen a vacuum cleaner wired up in the reverse polarity and although the negative lead enjoyed the mechanical isolation provided by the fuseholder it was still burnt. Perhaps Les's friend E.T. could point an enlightened finger for us? Ouch!

C. A. Burrows, *Burrows Service,
Thornton Heath, Croydon.*

Servicing the Sony KV2000UB

Part 2

David Botto

This month we'll deal with the rest of the timebase circuitry, the signals side and mention one or two odd faults.

Timebase Panel

As in other Sony TV sets, the field timebase circuitry is extremely reliable. But faults can occur! The 33V supply for the timebase is line output transformer derived – it leaves board E at pin 3 of connector E5 and arrives at pin 3 of connector D1. Absence of the 33V supply means no field timebase operation of course. The rectifier diode on panel E is D803 in earlier versions, D806 in later sets: the reservoir capacitor is C807/C812 (330 μ F, 50V).

We've never had to replace the CX157 field oscillator i.c. The field output transistors Q502 (2SC1663) and Q503 (2SA835) sometimes fail. In this event the driver transistor Q501 (2SC1670) should also be checked. There are several low-value resistors in this area. Check them all carefully, starting with the 1.2 Ω , 1W resistors in series with the emitters of the output transistors. Nasty field foldover at the top of the screen means that the bootstrap capacitor C508 (10 μ F, 50V) is losing capacitance or leaky. Replace it with a small 100V type.

If you've a picture that's curved in at the sides and the pincushion bias and amplitude controls have no effect, check the coupling capacitor C537 (10 μ F, 50V – C544 in later versions) first. Then check the two transistors Q512 (2SA733) and Q513 (2SC1124). These are Q508 (FRB829) and Q509 in later versions. The pincushion correction transformer T802 on board E can also fail.

Tuner

The tuner seems to lead a quiet life and seldom fails. If it does, the only reliable course is to replace it. There are two associated faults in earlier chassis: if the set drifts off tune, replace zener diode D111 (MZ12); if the set tunes

all right but switching on the a.f.c. detunes it, replace IC202 (M5134P).

Mk. I A Panel

Now to the signals panels, starting with the A panel in the Mark I chassis. All sorts of nasty things can happen on the displayed picture if the transistor leads become corroded, though it must in fairness be said that this only seems to happen when the set is used in a steamy atmosphere such as the kitchen or near a paraffin stove.

Examine the first two i.f. transistors Q201 and Q202 (both 2SC1129) – the slightest leakage in either of them will bring problems. A quick check on the video output from the panel can be made with an oscilloscope connected via a 10:1 probe to pin 2 of connector A1. Before leaving this panel, carefully examine all the small signal transistors and the small electrolytics for any signs of deterioration. We've never had to replace the CX095 intercarrier sound i.c.

Mk. I B Panel

There are no i.c.s on the B decoder board used in the Mk. I chassis – but there are 29 transistors. If you've colour problems, start by connecting your scope via its 10:1 probe to the junction of R438 (150 Ω) and VR301 (3.3k Ω). With a colour-bar signal you should see the colour bars. The passive subcarrier regenerator technique is used, i.e. the 4.43MHz crystal is driven by the bursts. With the scope connected to the junction of the driver transformer T303 and C316 (27pF) the burst should be seen. If it's missing or of less than 13V p-p, check the driver transistor Q303 (2SC403C). Its emitter decoupling capacitor C312 (4.7 μ F, 25V) can dry up and cause problems. The 4.43MHz reference signal can be checked at the collector of the following transistor Q304 (2SC403C). Adjustment of T303 is critical.

To override the colour-killer, connect the base of Q308 (2SC633A) to chassis. Check the bistable circuit by transferring the probe to the collector of Q312 (2SC633A) where a nice squarewave should be seen.

The luminance signal should be seen at pin 6 of connector B5 and the R - Y, G - Y and B - Y signals at pins 4, 3 and 2 respectively.

Strange green lines that vanish when the colour control is turned to minimum are due to failure of diodes D302/3 (1T40) - replace them both.

The main problem on this board is faulty transistors - but you'll find that the panel seldom gives trouble.

Mk. II A Panel

There's no B board in the Mark II chassis, the circuitry being included in the new A panel. Most of the signal handling here is done by i.c.s, making for even better reliability. IC201 is the vision i.f. i.c. Two different types have been used, CX100D and CX177. A scope at the junction of L301/R366 in the former case or L204/R314 in the latter should show the complete video waveform - chroma, luminance and sync pulses. At the junction of T301/R315 (earlier Mk IIs) or C311/R313 chroma alone should be seen. IC301 (CX108) contains the chroma and luminance amplifiers and the reference oscillator. Pins 4 and 8 are connected to the 4.43MHz coil which is linked to the 4.43MHz crystal via a 16pF capacitor (C325 or C317). With the scope probe at the collector of Q303 the 4.43MHz subcarrier should be seen at 1.2V p-p. IC302 (CX109) contains the chroma detectors, the G - Y matrix, the PAL switch, the a.c.c. and ident detectors plus one or two other bits and pieces. Two puzzling faults can be caused by this i.c.: wrong colour at the bottom one or two inches of the picture only, and sometimes an upright red bar on the left-hand side of the picture.

G - Y, B - Y and R - Y should be seen at pins 1, 2 and 3 respectively of connector A9 on this board, with Y at pin 4. To disable the colour-killer, unsolder pin 2 of IC302 and apply 4V to pin 2 of IC301 (you can use one of your PP9 batteries and a 5kΩ preset).

Miscellaneous Faults

Finally some odd faults. Nasty horizontal lines on the picture plus plenty of line whistle can be due to bad contact on power supply panel connector F3. This can also be caused by R640 (10kΩ - R639 in later Mk. II sets) or C628 (68pF, 500V - C623 in later Mk. II sets) going open-circuit.

There's a blanking circuit on board E. If the picture blanks out, the cause may be leakage in the transistors involved, Q802 (2SA677) and Q801 (2SC633A). Also test the two associated diodes D810 (1T40) and D809 (1T19-15B zener) and the values of R820 (22kΩ, 2W) and R821 (3.9kΩ, 1W). If R821 goes open-circuit you'll get ringing on the left of the picture. In later versions the resistors are R813 and R814 respectively, the zener diode is D811 (EQA01-16R), D810 is type 1TT600, Q801 type FRB829 and Q802 type FRB828B.

A disconcerting fault is the width varying in and out on odd occasions. While this can be due to the line output transformer, it's usually the scan coils playing up.

In conclusion, it's good to do two things to save yourself future headaches. Use only correct Sony replacement parts, including transistors, and spray a very thin coat of circuit varnish on any joints you've soldered.

next month in

TELEVISION

SPECIAL ISSUE!

The October issue of Television will contain **EXTRA PAGES** and a **DATA CARD**.

● VIDEO INFO CARD

Details of plug and socket types and connections for hundreds of VCRs to enable baseband links (audio and video) to be made. Tabulated for easy reference.

● A LOOK AT MONITORS

Once upon a time a monitor was simply a TV set with no tuner/i.f. section, used in closed-circuit applications where there was no need to modulate the video signal. Things are changing fast and monitors of various types are being increasingly used. Some are TV sets with extra circuitry for baseband links added. Others have varying degrees of resolution to provide displays for the growing number of video signal sources - games, computers and so on. Different line standards and wideband video give extremely high-quality displays for graphics and data. Next month Eugene Trundle takes a look at this expanding section of the TV scene.

● PANORAMIC SPECTRUM DISPLAY

It's useful to be able to display the TV bands on the screen of a scope - when looking for signals or aligning tuners for example. Denis G. Mott describes a simple way of going about it.

● N1700 VCR RENOVATION

Philips N1700 VCRs are now obsolete but can be picked up cheaply and are capable of giving very good results. Freddie Archer provides tips on renovating these machines.

● SYSTEM A MODULATOR

How to feed your 405-line sets once the transmissions have ceased! David Looser describes a vision and sound modulator that provides high-quality System A signals.

PLUS ALL THE REGULAR FEATURES

ORDER YOUR COPY ON THE FORM BELOW

TO
(Name of Newsagent)

Please reserve/deliver the October issue of TELEVISION (£1), on sale September 19th, and continue every month until further notice.

NAME

ADDRESS

Long-distance Television

Roger Bunney

Despite a few quiet days there was some dramatic reception during June. Tropospheric activity was high on the 8th and 9th, with reception from Denmark, Norway, W/E Germany and the nearer continental stations. There were two unusual events on the 8th: Cyril Willis (Cambridge) received Denmark chs. E3 and E4 and Ryn Muntjewerff (Holland) received the new Faroe Islands service on chs. E6 and E9. The signals from the Faroes, over a long sea path, were of fair strength and were present between 0915-1045BST. Congratulations to Ryn on this European "first" – the photograph shows the quality of the reception. On the 9th a large number of Swiss Band III/u.h.f. stations were received as far as the central Midlands: during the evening strong Luxembourg ch. E7 signals were present till closedown.




SpE also produced some dramatic reception. The following log collates reports from a number of UK DXers – unidentified signals have been omitted.

- 6/6/84 TVE (Spain) chs. E2, 3, 4.
- 7/6/84 TSS (USSR) R1, 2; RAI (Italy) IA; JTV (Jordan) E3 at 1710; EPT (Greece) E3; JRT (Yugoslavia) E3. An unidentified Arabic E2 station was logged at 1520-1635.
- 8/6/84 TSS R1, 2, 3, 4, 5, 6 (ch. R6 is in Band III); RTS (Albania) IC; RTVE (Spain) E2, 3, 4; ORF (Austria) E2a; +PTT (Switzerland) E2, 3; RAI IA, B; JRT E3; MTV (Hungary) R1, 2; DFF (East Germany) E4; Italian free station "Antenna Sicilia" (ch. not specified); CST (Czechoslovakia) R1, 2. An intense opening – also many unidentified signals!
- 9/6/84 TSS R1, 2; CST R1; TVP (Poland) R1, 2; MTV R1, 2; TVR (Rumania) R2; DFF E4; ARD (West Germany) E2; RAI IA; +PTT E2, 3; TVE E2, 3, 4; NRK (Norway) E2, 3; RUV (Iceland) E4.
- 10/6/84 JTV E3; JRT E3; RAI IA, B; TVE E3; TSS R1.
- 11/6/84 TVE E2, 3; RAI IA, B; ORF E2a; CST R1; SR (Sweden) E2.
- 12/6/84 TSS R1; SR E2; NRK E2; CST R1, 2; TVP R1, 2; JRT E4; RTP (Portugal) E2, 3; TVE E3, 4.
- 13/6/84 CST R1.
- 14/6/84 TVE E2; +PTT E2; TSS R1, 2.
- 15/6/84 TSS R1, 2, 3; TVP R1, 2; TVE E2; ZTV (Zimbabwe) E2 via TE.

- 16/6/84 CST R1; TVE E2.
- 17/6/84 RAI IA, B, C; JRT E3, 4; MTV R1, 2; ORF E2a, E3, E4; JTV Amman E3 (1305BST); ARD E2, 3; CST R1; NCT E3 (Italian free station – Udine).
- 18/6/84 TSS R1, 2; TVP R2; CST R1, 2; TVE E2, 3, 4; JRT E3; ORF E2a, E4; suspected Iran E2 FUBK test card with digital clock and white lettering at 1316BST; RAI IA, B, C; ARD E2, 4; ZTV E2 via TE.
- 19/6/84 TVE E2, 3, 4; TVP E3; RAI IA, B; JRT E3; MTV R1; ARD E2; ZTV E2 via TE; +PTT E2.
- 20/6/84 TVE E2, 3, 4; TSS R1, 2; TVP R1; RAI IA; RTP E2, 3.
- 21/6/84 NRK E2, 3, 4; SR E2, 3, 4; TSS R1, 2; ORF E2a; TVE E2, 3; RAI IA; TVP R1.
- 22/6/84 CST R1, 2; ORF E2a, 3, 4; RUV E4; TSS R1, 2; RAI IA; CBC Canada!
- 23/6/84 RTP E2, 3; TVE E3.
- 24/6/84 TSS R1, 2; NRK E2; SR E2.
- 25/6/84 TVP R1, 2; RAI IA; TSS R1; CST R1, 2; SR E2; EPT E3; unknown free Italian station "Studio 2 Italy".
- 26/6/84 TSS R1, 2; TVE E2 and TVE-2 E2; RAI IA.
- 27/6/84 RAI IA, B; TVE E3; +PTT E2; SR E2; TVP R2; Iran E2 at 0900, FUBK card with digital clock.
- 28/6/84 MTV R1; EPT E3; TVE E2.
- 29/6/84 RAI IA.
- 30/6/84 CST R1, 2; TSS R2; TVR R2; ORF E2a, 3; JRT E3, 4; EPT E3; RAI IA, B; TVE E2, 4; unidentified Arabic religious programme at 1100BST on chs. E2/4, possibly Egypt; CBC chs. A2/3 with weak video at 2120-2145, identified by programme sound.
- 4/7/84 RAI IA; EPT E3; TVE E3.
- 6/7/84 TVP R1; TSS R1, 2; TVE E2, 3, 4; RAI IA, B.

A remarkable log, with the once rare Greek ch. E3 (Akarnaika) becoming commonplace. This year certainly seems to be a good one for reception of Arabic stations: Iran was received in May and there've been a couple more possible sightings; Dhahran (Saudi Arabia) Aramco TV was logged by Ryn Muntjewerff on May 23rd – as a floater to JTV Amman between 1403-1550BST!

Perhaps the most dramatic reception was on June 22nd when system M, 525-line signals were received on chs. A2, 3, 4 between 1545-1605BST. Don Bassnett (Glasgow) received all three channels; Paul Barton (Harrogate) received ch. A3, which was undoubtedly the best signal – "Sesame Street" followed by the CBC news and at the end of the headlines the identification "this is CBHT Halifax". I've heard Paul's sound cassette and the quality is remarkable. A second Canadian signal is present but unidentifiable. The ch. A2 signal provided the identification caption "NTV" at 1600, but my WTFDA guide gives no clue as to its location. Can anyone help with this one? The ch. A4 signals were much weaker and couldn't be

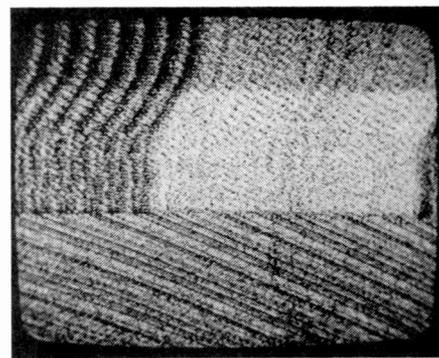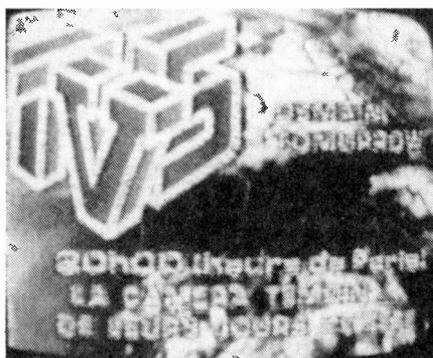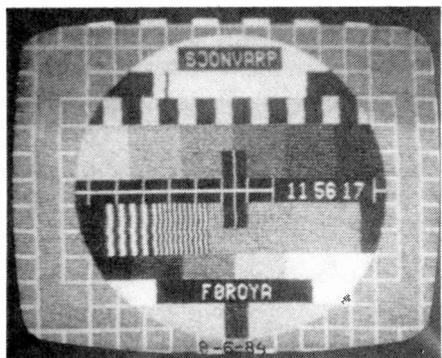

Left: Torshavn, Faroe Islands ch. E6 received by Ryn Muntjewerff (Holland) on June 8th via tropospheric propagation. Centre: Typical ECS/TV5 reception at 12GHz by Chris Wilson using the set-up shown in Fig. 1. Right: Appearance of home computer interference with programme, as radiated in Band I (photo from Robin Crossley).

identified. Don uses an Hitachi Model CMT2060 with PAL/SECAM/NTSC-system M switching; Paul uses a more conventional 625-line receiver and locked the video with reduced height. Congratulations to them both!

With Band III SpE on the 8th, the Faroe Islands via tropospheric propagation and Arabic signals in abundance, a very rewarding month! My thanks to the following for sending in reports of their reception. Graeme Wilson (Nunthorpe), Don Bassnett (Glasgow), Paul Barton (Harrogate), Cyril Willis (Cambridge), J. Bray (St. Neots), Simon Hamer (Powys), Bill Cotterill (Tipton), Tony Privett (Basingstoke), Iain Menzies (Aberdeen), Arthur Milliken (Wigan), Hugh Cocks (Sussex), Dave Shirley (Hastings).

News Items

South Africa: Bop-TV, the Bophuthatswana TV service, is now operating with reduced coverage. The authorities were displeased about enthusiastic reception in Soweto and Johannesburg – the programmes are uncensored and include American films and national/international news.

France: Three free TV stations are in operation in the Paris area – Canal 24, TIME and Antenne 1. The transmission times are irregular and the technical details unknown to us at present. French Canal Plus signals have been logged on ch. E29, thought to be from either Maubeuge (3.2kW e.r.p.) or Dunkirk (200kW e.r.p.) and causing co-channel interference with Goes, Holland. The identification “CDM BCH” on the French test pattern indicates origination from the main switching station at Butte Chaumont, Paris.

DX Publications: Mention of a booklet by Simon Hamer was made in the July column. This and the journal of the North England Radio Club International are no longer available.

Eire: New radio and TV transmitter lists are available on request from RTE, Reception Investigation Department, Dublin 4. The new Band III channel J (vision 223-25MHz, sound 229-25MHz) is at present being used by two low-power relays (Rosscarbery and Listowel) for RTE-2. It will also be used by the 100kW Kippure main transmitter which is undergoing tests and is expected to be brought into service by mid-1985.

EBU Listings

W. Germany: Neumuenster ch. E28 NDR-1 now 500kW e.r.p.


Belgium: Profondeville ch. E49 H RTBF-2 200kW e.r.p.; Brussels ch. E56 H RTBF 1kW e.r.p. – this station carries the TV5/ECS French language downlink signals.

From our Correspondents . . .

Robin Crossley (Dunstable) now works for a well-known UK satellite firm. Using a SAT-TEL receiver, he's successfully received all the available 12GHz downlink channels from ECS and Intelsat. This receiver is quite popular, its microcomputer control system being able to select the different bandwidths, audio subcarriers and pre-emphasis systems at present in use. Following a move, Robin has renewed his DX aerial system. This now consists of an Antiference XG14W with Schrader tunable head amplifier, an eight-element wideband Band III aerial and a three-element wideband Band I array. Like others, Robin is suffering from computer interference.

Nick Harrold (Rochford) is making good progress with

SOUTH WEST AERIALS

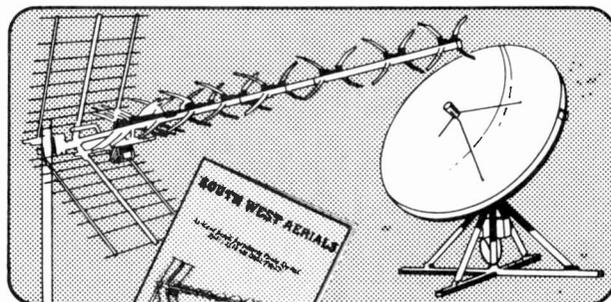

This catalogue is your key to solving a host of television and radio reception problems. We shall be delighted to forward your copy on receipt of 54p.

EQUIPMENT & PROFESSIONAL ADVICE

South West Aerials offer a unique blend of the best equipment and impartial professional advice.

Examples from our range:

| | |
|--|---------|
| WOLSEY HG36 'Quicksilver' High Gain (18dB) Grouped UHF Aerial (state group A,B or C/D) | £34.35 |
| LABGEAR CM7068 High Gain (27-29dB) Grouped UHF Masthead Amplifier (state group A,B or C/D) | £16.75 |
| LABGEAR CM7061 12 volt Matching Power Supply Unit for above Amplifier | £13.50 |
| JVC CX-610 6" Colour Television, Multi-Standard PAL/SECAM System B/G/I/D/K | £285.40 |
| VHF/UHF 5.5/6/6.5MHz Sound switching, 12/240 volt operation | £45.85 |
| HIRSCHMANN RO250 Rotator complete with Control Console (uses 3 core cable) | £45.85 |

We are THE DXing Specialists, advice on reception problems freely given, please include SAE with all enquiries.

All prices inclusive of VAT & Carriage

Delivery 7-10 days

SOUTH WEST AERIALS (T)

11, Kent Road, Parkstone,
Poole, Dorset, BH12 2EH.
Tel: 0202 738232



TV LINE OUTPUT TRANSFORMERS

PRICES INCLUDE VAT & CARRIAGE

Delivery by return of post.

| | |
|--|---|
| RANK BUSH MURPHY A774 with stick rectifier 9.78 A816, T16, T18, Z712, Z715 10.35 T20, T22, T26, Z179, A823 11.50 Z718 Basic unit 13.50 T24e, T24h split diode P.D.A. | ITT: VC200, VC205, VC207 9.20 VC300, 301, 302, 400, 401, 402 9.20 CVC1, CVC2 (FORGESTONE) 11.50 CVC5, CVC7, CVC8, CVC9 series 9.20 CVC20, CVC30, CVC32, CVC45 9.20 CVC40 split diode 16.74 FT110, FT111. P/no AT2063/02 11.50 |
| DECCA: 1210, 1211, 1511 11.50 1700, 2001, 2020, 2401, 2404 9.20 CS1730, 1733, 1830, 1835 9.20 30, 70, 80, 90, 100, 110, 130 Series 9.20 | PYE: 169, 173, 569, 368 series 9.20 CT200, CT200/1, CT213 series 10.35 725-731, 735, 737, 741 Series 9.78 |
| FERGUSON, THORN: 1590, 1591 9.20 1690, 1691. built in rect. 9.78 1600, 1615, 1700 series 11.78 1790 mono portable 9.20 3000, 3500, 8000, 8500, 8800 P.O.A. 9000, 9200, 9300 series 12.00 9500, 9600, 9650 series 10.99 9800, TX9, TX10 series P.O.A. MOVIESTAR 3781, 3787 12.00 | PHILIPS: 170, 210, 300 series 9.20 320 series 9.78 TX, T8 mono series P.O.A. KT2, KT3 series colour 9.20 G11 series split diode P.O.A. G8 and G9 Series £9.20 |
| FIDELITY: FTU12 mono 10.35 CTV14R, CTV14S colour 15.83 | BINATONE: 9909 mono 13.04 GRUNDIG: most models in stock NORDMENDE: FC125, Z206, Z306 11.50 SANYO: CTP5101, TJ series 11.50 SHARP: C1851H, C2051H 12.32 TELETON: TH14 mono 13.68 TOSHIBA: C800, C800B 19.45 TANDBURG: 190, CTV2-2, CTV3-3 P.O.A. TELEFUNKEN: most models in stock LINE OUTPUT TESTER 16.79 |
| G.E.C. 2047 to 3135 mono 7.50 1201H, 1501H, 2114, 3133, 3135 9.20 DUAL & SINGLE hybrid col. 10.00 SINGLE STD solid state 12.00 SINGLE STD split diode P.O.A. | Tidman Mail Order Ltd., 236 Sandycombe Road, Richmond, Surrey. Approx. 1 mile from Kew Bridge. Phone: 01-948 3702 Mon-Fri 9 am to 12.30 pm & 1.30-4.30 pm Sat 10 am to 12 noon. |
| INDESIT: 24EGB hybrid 9.50 12LGB, 12SGB mono portables 10.35 | |
| WINDINGS TYNE: main winding 6.80 RBM: T20, T22, T26, Z179 6.33 WALTHAM: W125 eht winding 2.37 KORTING: hybrid winding 6.90 | |

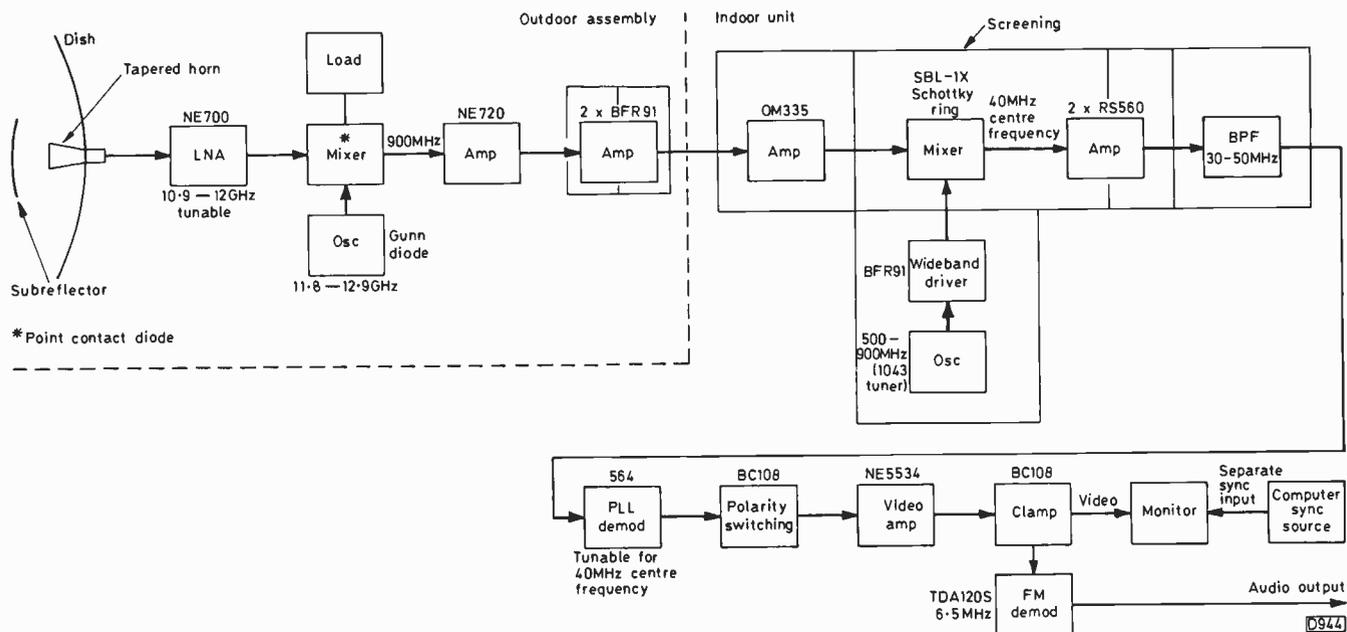


Fig. 1: Block diagram of Chris Wilson's present 12GHz satellite receiver system.

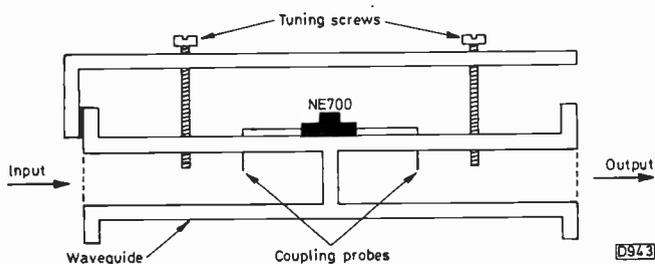


Fig. 2: Outline of the single-stage LNA.

his 12GHz receiver system, using a 10ft dish and no LNA. Six ECS transponders have been identified - Sky Channel, PK5, RAI, Teleclub, TV5 and ZDF.

Interference

Several enthusiasts have sent in reports indicating that interference from home computers is a growing problem. We are still awaiting replies from Sinclair and other firms/organisations approached. A local Spectrum here can be resolved, over a distance of 120ft via my aerials at 53ft, sufficiently well to be able to recognise and identify specific programmes being displayed and activity thereon - the video information is positive-going. The output is particularly high at 78.4MHz - try this if you wish to view information displayed on neighbouring Spectrums! I'd appreciate any further reports and observations on this problem.

Another problem that causes heartache in some areas is the 49MHz cordless phone. One version operates at 1.6/49MHz (1.6MHz base unit). The situation could become worse: apart from the DTI's proposal for a "low-power device band", the US FCC has approved a new type of cordless phone operating in the 46/49MHz band. The 1.6MHz type is to be withdrawn since the FCC intend to extend the medium-wave band to 1.705MHz. In the UK we could well find 1.6/49MHz units being dumped at cheap prices. The 46/49MHz equipment will have ten base frequency channels between 46.61-46.91MHz with a matching ten handset channels between 49.67-49.97MHz and a predicted range of "three blocks", though larger aerials would increase this. The new channels are to come

into operation on October 1st. Five of them correspond to the cheap walkie-talkie unit channels. New models are already appearing, one manufacturer claiming a 1,500ft range with indoor aerials extending to much greater distances with external ones.

David Moller (Eastbourne) has written in about another source of interference. The problem started with streaking on his ch. E37 pictures from Boulogne - regular bursts of streaking flashing on and off throughout the day and night. The source of the trouble was found to be radar pulses used for coastal surveillance. It can be largely eliminated by using a ch. E36 notch filter. Radar interference in the Southampton area originates from two sources, one at St. Boniface (high on the down above Ventnor, Isle of Wight) and the other at an airfield at Boscombe Down near Salisbury. The latter operates during daylight/flying times only.

12GHz Receiver System

Chris Wilson has sent in an impressive shot of TV5 reception via ECS and has provided details of his present receiver set-up (see Figs. 1 and 2). A 1.8m diameter fibreglass dish with focus at 70cm is used, with a subreflector and a five inch tapered feedhorn (this arrangement gives a 4dB gain compared to a "normal" system with the horn at the focal point of the dish). The dish is on a polar mount which can be swung from 60°E to about 35°W. The LNA and first converter are mounted at the rear of the dish. The LNA consists of a single stage using an NE700 gallium arsenide f.e.t. mounted on WG18 waveguide. The Gunn diode oscillator operates above the signal frequency, an arrangement that seems to be better when an LNA is used. The output from the head unit is at 900MHz.

The indoor section is fairly conventional except perhaps for the second conversion to 40MHz. The incoming sync is phased with a computer sync source to provide improved locking - a ZNA234 sync chip is awaited to replace the computer derived sync pulses. At the time of writing (late June) reception includes Sky, RAI, West Germany, Teleclub and PK5 (RAI and Teleclub with sound). The coverage is 10.9-12GHz.

Service Bureau

Requests for advice in dealing with servicing problems must be accompanied by a £1.00 postal order (made out to IPC Magazines Ltd.), the query coupon printed below and a stamped addressed envelope. We can deal with only one query at a time. We regret that we cannot supply service sheets nor answer queries over the telephone.

RANK T22 CHASSIS

There's severe EW distortion, the sides of the raster being bowed in. An earlier fault was no raster due to one of the EW modulator diodes 5D6 being short-circuit. The fault may have been present before this was replaced.

The area in which the fault lies can be determined by disconnecting 5L2 to remove the EW drive. If the fault remains, check the EW modulator diodes 5D6/7, ensuring that neither is leaky. If the width decreases, check the EW driver transistors 4V17/18 and if necessary find out why they are hard on.

MITSUBISHI CT200B

The fault consists of a line of increased brightness that moves slowly up or down the screen. Otherwise the set works well.

This sort of thing is normally caused by a 50Hz hum waveform getting into the signal stages. While there could be a fault in the power supply (smoothing etc.) it's more likely to be coming in on a high-impedance tuning line, i.e. via the a.f.c. or programme selector circuits. This can be proved by using a capacitor of say 0.1µF to decouple the tuner's tuning voltage pin. Hum can also be picked up by badly-dressed leads or cableforms.

BUSH A640 CHASSIS

This set is plagued by intermittent instability: every few minutes the vision signal is lost (raster o.k.) and the sound signal is severely reduced. This is accompanied by a whining noise that starts at a low frequency and rises over a second to a constant high pitched sound. Light tapping around the i.f. stages clears the fault for a while but won't instigate it.

Make sure that the earth bonding of the i.f. panel is good and that the mounting screws are tight. Clean the system switch contacts or solder them in the 625-line position. If necessary check the earth bonding of the i.f. lead from the tuner to P/S1 then check the decouplers associated with each i.f. stage - 2C18, 2C19 and 2C27.

G8/VCR COMPATIBILITY

The problem with this Philips G8/Ferguson 3V23 VCR combination is buzz on sound, with no effect on the picture, i.e. no sound on vision. It gets worse the longer one watches. The problem arises with prerecorded tapes or tapes recorded on the machine. Slight improvement can be obtained by fine tuning the VCR, but the colour drops out.

This is a common problem when a G8 is used with a VHS machine. If retuning the sound detector coil in the

set fails to provide a cure the VCR's modulation level will have to be reduced.

SONY SL8000UB

The original fault was failure of the keys to latch. This was cured by replacing a broken drive belt. The problems now are that the record key won't press down with play, the clock is stuck at 12.00 and the timer LED is flashing.

For the record fault, check that the safety tab activator is operational. If it's jammed, the machine will think the cassette has had the recording safety tab knocked out. The clock problem could be due to the timer control i.c. (IC3101, µPD552C-011) but is more likely to lie in the timing switch system, e.g. D3104 in the clock set line or a panel problem.

ITT CVC40 CHASSIS

The fault on this set is wavy verticals affecting only the top three inches of the screen. It's most noticeable with a lamp post, telegraph pole etc. which will have a kink at the top. Turning down the brightness, colour or contrast control setting straightens the lines but the brightness is affected. The lines also straighten on picture fade outs.

There seems to be something wrong with the e.h.t. regulation. The trouble could well lie in the earthing of the tube's Aquadag coating - this is done via the base panel. Alternatively check R39A (220kΩ) in the beam limiter circuit. If necessary check the value of the sync separator bias resistor R703 (2.2MΩ) on the sync/line oscillator module (CMS40).

GEC 2028

The fault with this hybrid, dual-standard colour set is foldover (a shadow) that extends about half-way across the screen from the left-hand side. It was intermittent to start with but is now permanent. The linearity does not seem to be affected.

Start by disconnecting the line shift coil L5. If this cures the problem it probably has short-circuit turns. If not, check the line oscillator supply smoothing electrolytic C68 then the shape of the line drive waveform. If these and the PL509 line output valve are o.k., the line output transformer could be faulty. Before condemning it, check the tuning capacitor C83 (200pF) and the damping components C82 (180pF) and R59 (1.5kΩ).

HITACHI NP8C CHASSIS

There's sound distortion, of an intermittent nature. Bass or loud passages are badly affected while some newsreaders, especially female, are at times barely intelligible.

Slight adjustment of the quadrature coil L402 might well clear the problem. If not, check whether the 11V zener diode ZD401 in the audio coupling network is

QUERY COUPON

*Available until 19th September 1984.
One coupon, plus a £1.00 (inc. VAT)
postal order, must accompany EACH
PROBLEM sent in accordance with the
notice printed above.*

TELEVISION SEPTEMBER 1984

leaky. Alternatively the audio output stage thermal fuse TF401 could have developed high internal resistance.

GRUNDIG 6011

The field scan is distorted, with bowing at the top and bottom – the top curvature is greater than that at the bottom.

A very common cause of this symptom is failure of C475 (0.27 μ F) in the NS correction circuit. If necessary check for dry-joints around the NS correction transducer PTC1 and its associated components.

TEST CASE

261

Each month we provide an interesting case of television servicing to exercise your ingenuity. These are not trick questions but are based on actual practical faults.

It's some years now since the TV setmaking division of the Rank Organisation shut its doors for the last time. Many of their products are still with us however, and it's interesting to speculate about what RRI would have been up to had they survived. Bush and Murphy TV sets are not difficult to service (we refer of course to the original Rank products) though some of our field technicians are none too familiar with them. Those we service are "adopted" as it were, since we never had a Bush or Murphy dealership. Hence this month's saga...

The cry for help came via the telephone, to the effect that a Bush Model BC6340 (T20A chassis with 22in. tube) had failed completely after several stop-and-start sessions over the previous week. After a hurried conflagration between the Resident Workshop Sage and the lucky field man assigned to the job, he was sent off with a circuit diagram, the means of making a 910 Ω resistor, some BYX71 diodes and a TBA950 chip. In the event, none of this was of any use whatsoever! On site he found 200V at one end of the h.t. fuse 5FS1 on the line output stage panel and nowt at the other.

His first move was to insert a meter switched to the 0-1A d.c. range across the fuseholder, disconnect the tripler and switch on – then off again quickly as the meter's pointer hit the right-hand stop! The performance was repeated after open-circuiting the line driver transistor's fusible collector feed resistor to remove the line drive. Again there was a high current reading. A resistance check across the BU208A line output transistor then revealed that it was virtually short-circuit. Thinking that his troubles were over, our technician replaced the fuse and the transistor and reconnected the link on the fusible resistor. Switching on with a flourish, he was mortified to hear a momentary "squegging" noise from

the line output stage followed by a resounding silence...

Meter checks showed that the fuse was this time intact, with normal voltage at the collector of the BU208A. The EW modulator diodes were removed and tested but proved to be o.k. The not-to-be-recommended stratagem of disconnecting the protection transistor 5VT2 made no difference to the symptom. A scope check at the collector of the line output transistor produced a trace of a decaying burst of line-rate waveform at the output transistor's collector at each switch on. It's at times like these that a man resorts to his radio-telephone (swank!) and consults his Resident Workshop Sage. Summoned to the reception office where the RT base station lives, RWS spoke thus: "Connect a 10W, 5.6k Ω resistor across the kick-start capacitor 4C19, then check the oscillator, driver and output stages with your scope – look out for fireworks if you leave the overvoltage protection disconnected."

There were no fireworks, but there was now some line drive. Pulses at the TBA950's output pin and pulses at the collector of the line driver transistor. No line output transformer activity though, and no current through the line output stage h.t. fuse. There was 200V at the collector of the line output transistor but not a bean at its emitter.

The diagnosis was made without any further reference to the RWS, but the technician had to return to the stores to obtain the necessary spare part. Not something you use every day, but something he should have taken along with him. What was it?

ANSWER TO TEST CASE 260 – page 561 last month –

The tale related last month is typical of many caravan TV installations we encounter during the holiday season. The set in question, a JVC CX500GB, is rated at 17W when operated from a 12V d.c. supply, representing a current drain of just under 1.5A. Between the car's battery and the TV set's 12V supply point there were three sets of plugs and sockets, two fuses and two sets of switch contacts. The caravan's internal wiring had been extended and adapted by somebody, using 2A mains flex. All these added up to a series resistance of perhaps 1.5-2 Ω , insignificant in most mains installations but crucial in a low-voltage circuit. Two ohms will produce a voltage drop of 3V at 1.5A, and this is quite enough to upset the operation of the voltage stabiliser within the set. Unusually for a colour set, the CX500GB's series regulator produces an output at 10.7V.

Meg's tap incorporated an electric pump to raise water from the floor-level tank, and this took a fair gulp of power via the same path as the TV set. This and the lighting system between them drew sufficient current virtually to stop the TV set from working.

The cure was to reduce the series resistance by rewiring the caravan properly with 60A cooker cable, and perhaps to provide separate leads for the various appliances. We also sold Andra one of those wideband TV aerials with a sucker mount and universal joint – the one he had on the pole was a group B type, rigidly vertical and quite useless for Heathfield or Walmington.

Published on approximately the 22nd of each month by IPC Magazines Limited, King's Reach Tower, Stamford Street, London SE1 9LS. Filmsetting by Trutape Setting Systems, 220-228 Northdown Road, Margate, Kent. Printed in England by The Riverside Press Ltd., Thanet Way, Whitstable, Kent. Distributed by IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. Sole Agents for Australia and New Zealand – Gordon and Gotch (A/sia) Ltd.; South Africa – Central News Agency Ltd. Subscriptions: Inland £11, overseas (surface mail) £12 per annum, payable to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex RH16 3DH. "Television" is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to currency exchange fluctuations and VAT, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever. ISSN 0032-647X.

CentreVision

0222-44754

SLOPER ROAD

LECKWITH

CARDIFF CF1 8AB

(WORKING SETS)

(WORKING SETS)

OPP CITY FOOTBALL GROUND
5 MINS FROM M4

TELEVISION/VIDEO (VHS + BETA)
TRADE WORKING ORDER WITH STAND

- ★ ITT CD752 REMOTE £115
- ★ GEC C2639H (PRESTEL/TELETEXT) £150
- ★ GEC STARLINE 22-20 REMOTE £45
- ★ PYE CHELSEA £38
- ★ GEC B/W PORTABLES £16
- ★ DECCA 22" BLACK FRONT VERICAP £30
- ★ RANK T20 REMOTE £75 + VAT
- ★ OFF THE PILE SETS FROM £8

PRICES SUBJECT TO VAT

OPENING HOURS 9 - 5.30 MONDAY - FRIDAY. SATURDAY 9 - 1pm

The World of . . .

"TELE PANELS"

52 Mount Pleasant Road, Chigwell, Essex.
Telephone 01-729 0506.



COMPARE OUR PRICES!

COMPARE OUR SERVICE!

| | IF | TUNER | DECODER | G8/G9 DECODER IF COMBINED | LINE OUTPUT | POWER | CONVERG | FRAME | VIDEO | 6 WAY TUNER SWITCH BANK |
|-----------------|-------|-------|---------|---------------------------------|----------------|-------|---------|--------------------------|-------|-------------------------------|
| PHILIPS G.8 | 5.00 | 4.50 | 7.00 | 15.00 | 14.00 | 8.00 | 5.00 | 5.00 | | 3.50 |
| THORN 3000/3500 | 2.00 | 5.75 | 4.00 | | 8.00 | 8.00 | 5.00 | 6.00 | 5.00 | 1.75 |
| GEC 2110 | 10.00 | | 5.00 | | 12.00 | 6.00 | 5.00 | 5.00 | 5.00 | 5.00 |
| PYE 731 | | | 10.00 | | 18.00 | 10.00 | 7.00 | 8.00 | | 4.50 |
| PUSH Z/718 | 7.50 | 6.50 | 14.00 | | 24.00 | 3.00 | 5.00 | 14.00 | | |
| BUSH T/20 | 7.50 | 6.50 | 14.00 | | 19.00 | 19.00 | 5.00 | 14.00 | | |
| DECCA BRADFORD | 3.00 | | 7.00 | | | 4.00 | | FRAME TIME BASE £4 | | |

TRIPLERS FOR ALL MODELS £3.00 SPEAKERS £1.50

P+P 1 PANEL £1.50 2 PANELS OR MORE £3.00

CASH WITH ORDER - PLEASE

POST OFF YOUR CHEQUE NOW! & YOUR PANELS SENT BY RETURN OF POST!!!

| | | | | | | |
|--|--|---|---|--|--|---|
| CAPACITORS 91 5 x .0047/1500 AB23 Chassis 1.50 92 10 x 220MFD 16V Elect. 0.50 93 10 x .047MFD 400V Mut Pol 0.50 94 5 x 4.7/100V C514 T3500 1.25 95 5 x 47/1000 Dubilier 3.00 97 10 x 0.1/2000V W/E 2.00 98 5 x 1/250 Supp ITT etc. 1.50 | 68 Grundig 3010/1500 3.00 89 Thorn 3500 7.50 70 Thorn 8500 5.40 71 Philips G8 6.30 72 Pye 731 4.50 89 10 x Anti Track EHT Cap 2.00 | 179 TDA2532 2.40 180 TDA2540 1.85 181 TDA2541 2.87 182 TDA2560 3.28 183 TDA2571 2.15 184 TDA2591 0.98 185 TDA2593 2.23 190 TDA2800 4.80 191 TDA2811 1.24 192 TDA2840 2.35 210 ETTR8016 2.28 211 ETT8016 2.28 212 BTT8018 2.28 220 SL901B Int Circuit 5.00 | 030 GEC 2100 Hybrid 4.00 032 Thorn T x 9 Chass. 14.50 033 Philips KT3 8.00 034 RRI T24 Chass. 14.00 036 Sanyo CTP5101 9.50 037 Split Diode EHT Lead 1.35 | SPECIFIC COMPONENTS 351 Thorn 1591 Speaker 2.00 352 Thorn 1600 Dropper 0.50 353 T x 10 Preset Drawer 3.00 354 T x 10 CRT Base Assy 4.00 355 3" Round BR Speaker 1.00 358 5 x Tho/3500 200 Conv. Pot. 1.00 359 5 x Tho/3500 50R Conv. Pot. 1.00 360 5 x TCE3500 A1 Rectifier 0.75 362 T9000 Rem. Receive Assy 5.00 363 T3500 Mains TX 5.00 364 T8500 Mains TX 7.50 365 T8500 (Plastic) Cut Dut 1.50 370 Pye 731 Thick Film Resis. 1.50 371 Pye 713/731 Vis. Gain Mod. 6.50 372 Pye 731 3R3 50W Metal cld. 1.29 373 100K x3 Drawer P'set Alt Pye 731 2.00 378 Grundig 5010/8010 Vid Mod. 4.00 384 5 x 10R Phil. G8 Conv. Pot. 2.40 385 5 x 15R Phil. G8 Conv. Pot. 2.40 386 5 x Phil. G8 2k x2 Lin. Bright. 2.50 387 5 x Phil. G8 10k Log. Colour 2.50 388 5 x Phil. G8 47k Log. Vol. 2.50 389 G8 Plastic Mains Switch 0.75 | 390 G8 Metal Mains Switch 1.23 391 G8 Line Stor/Eql. Coil 2.25 392 G8 R/G Symetry Coil 3.33 397 20 x 315A A/S 20mm Fuse 1.50 398 20 x 800MA A/S 20mm Fuse 1.50 399 20 x 2.5A A/S 20mm Fuse 1.40 400 20 x 2A A/S 20mm Fuse 1.40 401 20 x 1A A/S 20mm Fuse 1.40 402 20 x 1.25A A/S 20mm Fuse 1.40 403 5 x RRI T20 Tube Base 4.35 410 Phil. G11 E/W Load/ Coil 1.50 411 Phil. G11 Bridge TX 1.50 412 Phillips G11 Speaker 1.00 413 10 x TDA2800 IC Holder 1.50 415 PALKT3 Speaker 1.50 435 10 x Decca 30 10R Fusible 0.50 436 5 x Decca 30 3R9 Modulohm 1.75 437 Decca 30 47k Vol.+Switch 1.25 453 5 x 5R Universal Conv. Pot. 1.00 454 5 x 20R Universal Conv. Pot. 1.00 455 5 x 100R Universal Conv. Pot. 1.00 456 5 x 470R Universal Conv. Pot. 1.00 457 10 x 100k Tun/Pres TCE etc. 3.00 458 10 x 100k Tuner Preset G8 3.00 459 ELC1043/05 Tuner 6.00 | 460 ELC1043/06 Tuner 6.00 461 U321 New Tuner 7.95 462 U322 New Tuner 7.95 463 98003 Posister 0.99 464 98009 Posister 0.99 465 Mull.DL50 Delay Line 0.95 466 5 x VA1104 2.70 469 Cut Out Metal GEC 2100 1.00 470 5 x GEC2100 3 Lag Thermist. 1.00 479 5 x Gen. Purp. Ro- tary Switch. 3.80 480 5 x Gen. Purp.Push/ Switch. 3.75 481 20 x Neons GEC etc. 2.25 482 5 x Univ. Aerial Skt. Kit 5.50 483 10 x Metal Coax Plug 1.70 484 Focus Unit T20 Type 1.25 485 Foc/Unit Thorn 8500 Type 1.25 486 4.43Mhz Crystal 0.40 488 10 x Ring Type Spk/ Gap 1.50 489 TX10 Chass. Focus Unit 7.00 497 Oe-Soldering Pump 3.50 498 1 x 10 Trimming Tool 1.00 |
| EHT TRAYS 50 ITT CVC 5/9 3.00 51 Decca 1730/1830 5.00 52 Decca 80 Series 4.50 53 GEC 2040 Hybrid 3.00 54 T1500 5 Stick 3.50 55 Thorn 9000 7.00 56 Thorn 1400 2.00 57 Philips G9 3.50 58 Universal ITT Type 4.50 59 5 x TV11 EHT Rec for PTV's 1.00 60 3 x TV45 EHT Rec Z718 1.00 61 ITT CVC 45 4.00 63 RRI Z179 3.00 64 Pye 691/697 3.50 65 Pye CT200 4 Lead 3.50 66 Pye CT200 5 Lead 4.50 67 Korting 90 DGR Hyb 5.00 | INTEGRATED CIRCUITS 140 5 x TDA440 3.00 141 5 x TBA120AS 1.80 142 5 x TBA540 4.00 143 5 x TBA540Q 4.00 145 5 x TBA560 3.50 146 5 x TBA810S 3.00 147 5 x TBA920Q 4.50 148 5 x TBA990 3.25 149 5 x TBA520Q 4.00 150 5 x TBA530 4.25 151 5 x TBA950 4.50 154 10 x TCA270SQ 4.00 155 5 x MC1327Q 2.50 180 TDA1170 1.35 181 TDA1190 1.50 182 TDA1006A 1.45 184 TDA1035 1.83 185 TDA1044 2.23 186 TDA1190 1.50 187 TDA1412 0.90 172 TDA2002 1.80 173 TDA2020 2.50 174 TDA2030 2.15 178 TDA2523 2.35 | LINE OUTPUT TX 001 Philips G8 7.50 002 Decca 30 Series 7.00 003 Decca 100 Series 6.50 004 ITT CVC 25/30/32 7.00 005 Philips G9 7.50 006 RRI T20 9.92 007 RRI A823 7.00 008 RRI Z718 18" 18.95 009 RRI Z718 20/22/26" 18.95 010 RRI A774 Mono 10.87 011 Thorn 1890/91 7.00 012 Thorn 1615 6.50 013 ITT CVC 45 6.50 014 Phil TX Chass. 5.00 015 RRI Ranger 1/2 5.00 016 ITT CVC 5/9 8.50 017 Philips E2 Chass. 5.00 018 Thorn 9000 12.00 019 Thorn 9500/9800 8.50 020 Polish 161 Mono 6.00 021 Thorn 3500 Scant 4.50 022 Thorn 8500 11.00 023 Thorn 1590/91 8.50 024 Thorn 1500 15KV 4.00 025 GEC 2040/2100 Hybrid CTV 4.00 026 Bush 161 Mono 5.00 027 GEC Single Std Mono 5.00 028 Pye 691 (wired) 5.00 | PUSH BUTTON UNITS 110 Pye 713 4 Way 7.87 111 Pye 715 6 Way 11.95 112 Phil G8 Square 12.75 113 Phil G8 Sloping 14.50 114 Thorn 9000 2.50 115 Thorn 1615 4 Way 7.87 116 Decca 6 Way 6.95 117 Decca 4 Way 6.50 118 GEC 2110 6 Way 7.95 119 GEC 2136/7 Tapered 7.95 120 ITT CVC5 9.25 121 ITT CVC8 11.45 122 ITT 6 Way with V.C.R. 7.95 123 RRI A823 etc. 7.95 124 Hitachi 4 Way 7.95 125 RRI T20 6 Way 8.95 | SMOOTHING CAPACITORS 80 220/400 CVC32/ T20 1.20 81 200+300 Pye 691 2.00 82 600/300 Phil G8 1.90 83 175+100+100 T3500 1.50 84 2000/100 Volt 0.50 85 470 Mfd G11 1.50 86 400+400 Decca 30 2.50 87 200+200+75+25 ITT CVC5/9 1.50 88 400/400V Tho 9000 1.50 89 4700/25 Thorn 1590/ 91 0.80 | TRANSISTOR/DIODES 230 10 x AC128 1.50 235 50 x BC213L 2.50 250 10 x BD124 9.00 251 10 x BD131 1.80 270 10 x BU208A 8.50 271 10 x BU208 7.50 272 5 x BU326 10.00 273 5 x BU205 3.75 280 25 x 2N3055 (Texas) 7.50 281 10 x 2N2905 (Equiv. BC161/303) 0.50 290 10 x BT106 Thyristor 9.00 292 5 x BT119 4.50 293 5 x BT120 4.50 335 50 x BY127 Diodes 3.00 340 25 x TIP41A 6.50 341 25 x TIP41C 7.00 | |

All components are A1 quality from prime manufacturers, and are dispatched by post same day as order received together with any refund due. All goods should be delivered within 4 working days.
Please add 15% VAT and 90p P & P

QUICK SAVE T.V. SPARES

MUXTON HOUSE, MUXTON, TELFORD, SALOP.
REG. OFFICE ONLY. CALLERS STRICTLY BY APPOINTMENT. UK ONLY. PLEASE QUOTE STOCK NO.

TV LINE OUTPUT TRANSFORMERS

FAST RETURN OF POST SERVICE

RANK BUSH MURPHY
Z146 A640 dual std mono 7.00
Bush A792, A793
single std mono 7.00
A774 single std mono 7.00
A816 solid state mono 9.00

DECCA
MS1700 2001 2020 2401 mono 7.00
MS2404 2420 2424 mono 7.00
CS1730 1733 colour 8.00
CS1830 1835 colour 8.00
'30' series Bradford colour 8.00
80 series colour 8.00
100 series colour 8.00

FERGUSON HMV MARCONI
1600 8.00

G.E.C.
2047 to 2105 7.00
2000 to 2064 dual std mono 7.00
DUAL STD hybrid colour 8.00
SINGLE STD hybrid colour 8.00.00

Indesit 20EGB 24EGB mono 9.00

KB - ITT
VC200 VC205 VC207 mono 7.00
CVC5 CVC7 CVC8 CVC9 col. 8.00
CVC20 series colour 8.00
CVC30 CVC32 series colour 8.00
CVC45 8.00

PHILIPS
170 series dual std mono 7.00
210 300 series mono 7.00
G8 & G9 series colour 8.00
PYE 169-173-569-368 7.00
EKCO RV305-769-725-741 8.00
WALTHAM 125 9.00

REWIND SERVICE - available for most continental types, i.e. Kuba, Luxor, Korting, Tyne, Berry Skantic, K80 £15.00 inc pp, VAT. Old lopt required.

WINDINGS

SOVEREIGN 14" colour overwind 15.00
15.00

SONY 1320UB overwind 15.00
RANK BUSH MURPHY
T20a T22 Pry & Sec 6.00
Z718 series primary 6.00
Z718 series EHT overwind 7.00

ULTRA THORN
1690 1691 EHT overwind 7.00
1590 6.00

PYE
691 to 697 EHT overwind 4.00
691 to 697 primary 5.00

PRICES INCLUDE P.P. & 15% VAT

All lopts and windings are new and guaranteed

Open Mon.-Fri. 9 to 5.30 pm
Delivery normally by return.

PAPWORTH TRANSFORMERS

80 Merton High Street,
London SW19 1BE

S.A.E. all enquiries
Barclaycard and
Access welcome



For orders placed at the post office
Trans cash 506 4856

01-540 3955

ELECTRON GUNS TV TUBE COMPONENTS

If you are Rebuilding or Manufacturing TV tubes - We are the leading suppliers of Electron Guns and TV Tube Components to the TV Tube Industry. We specialise in all aspects of Electron Mount Technology.

Our product range includes more than 250 gun types for Colour, In Line, Mono and Display Tubes along with Mount Parts, Bases, Getters, Seal-offs, and all other associated items for TV Tube Production.

A Full Technical Back-up and Advisory Service is available to all customers World-wide.

Please request our current catalogues and Data Information.

GRIFTRONIC EMISSION LTD NEW ROAD, STUDLEY, WARWICKSHIRE B80 7LY ENGLAND.

Telephone: 052-785 2684 or 2639 Telex: 336924 Grifem G.

VIDEO HEADS MONOLITH electronic products

HIGH QUALITY UNIVERSAL VIDEO HEAD REPLACEMENTS FOR ALL VHS AND BETAMAX VCR MACHINES

VHS Part No. 3HSS (5mm Centre Hole) £29.95 PRICE

VHS Part No. 4HSS (15mm Centre Hole) £29.95 EACH

BETAMAX Part No. PS3B £38.95 EX.

REPLACEMENT KIT (14 Pieces Boxed) £ 8.25 V.A.T.

PLEASE ADD 15% V.A.T. PLUS P. & P. £1.50 PER ORDER
OUR FULL CATALOGUE AVAILABLE ON REQUEST.

Please allow between 14 and 28 days for delivery.

AUDIO + VIDEO HEADS - MOTORS - PARTS
Suppliers to most U.K. Distributor/Service Organizations

THE MONOLITH ELECTRONICS CO. LTD
5-7 Church Street, Crewkerne, Somerset TA18 7HR, England
Telephone Crewkerne (0460) 74321 Telex 46306 MONLTH G



CHROMOVAC

QUALITY REBUILDS

SPECIAL OFFERS
THIS MONTH ONLY

Get on the hot-line today!

SUPERIOR QUALITY TUBES **051 428 8777**

DELTA RE-BUILDS
most types of Inline Re-builds or new ex-stock
★ 2 YEAR WARRANTY
★ 4 YEAR OPTIONAL

Delta Rebuilds

Up to 19" £24
Up to 22" £28
Up to 26" £32
110° up to 22" £32
110° up to 26" £34
Low focus £30
A47 342 New £32

Delta only. Less 7½% 5+
Less 10% 10+ and over

Inline Rebuilds

Up to 22" £40
Up to 26" £45
Bonded Coil +£5

ALL SIZES OF NEW MONO TUBES AT COMPETITIVE PRICES

IN LINE TYPES EX-STOCK SELECTION NOT REBUILDS

370 HFB £45
370 HUB £45
420 CSB £45
420 EDB £45
420 EZB £45
420 ERB £45
510 UFB/A51-590 £55
A51-570 £55
A51-210 £55
510 VSB £60
AXT 51-001 £60
560 DYB £62
560 EGB £62
560 CGB £62

560 DMB £62
AXT 56-001 £62
560 ATB £65
660 AB £65
A67-701 £65
670 CZB £65
H6817 £65

CARRIAGE
£5 Singles, 2-3 £10, 4 £12
10 £15, 10+ Carriage paid
EXCLUSIVE OF V.A.T.
TERMS
Cash with order

QUANTITY DISCOUNT AVAILABLE
Ask for details

★ OUR TECHNICAL DEPT. WILL ADVISE YOU ON PROBLEMS. YOU MAY ENCOUNTER ON FITTING INLINE TUBES

DELIVERY: Ex stock items immediate dispatch on receipt of order. Others allow 14 days.

THE COMPANY WHO PUT HIGH STANDARDS FIRST

CHROMOVAC

CHROMOVAC LTD. UNIT 7, BEAR BRAND COMPLEX,
ALLERTON ROAD, WOOLTON; LIVERPOOL 25
Ask for MR. BUTTERWORTH ON: 051-428 8777

| | | | | | | | | | | | | | | | | | | | | | | | | |
|--------|------|--------|------|-------|------|------------|------|---------|------|---------|------|----------|------|---------|-----|---------|------|--------|------|------|------|-----------|------|--|
| AA117 | 9p | BC182L | 6p | BD225 | 31p | BU110 | 110p | TIP42A | 22p | 2N2484 | 20p | 2SC1969 | 130p | IN.4002 | 4p | LM323K | 420p | PCL85 | 55p | 4032 | 67p | 4506 | 110p | |
| AA119 | 9p | BC183 | 6p | BD232 | 31p | BU111 | 140p | TIP42C | 25p | 2N2646 | 38p | 2SC2029 | 120p | IN.4003 | 4p | LM723 | 32p | PCL86 | 55p | 4034 | 145p | 4507 | 45p | |
| AA132 | 9p | BC183L | 6p | BD234 | 32p | BU126 | 70p | TIP47 | 40p | | | 2SC2078 | 120p | IN.4004 | 4p | 78HGKC | 570p | PCL805 | 55p | 4035 | 70p | 4508 | 125p | |
| AC107 | 28p | BC184 | 6p | BD237 | 21p | BU204 | 75p | TIP48 | 40p | 2N2904 | 20p | 2SC2122A | 200p | IN.4005 | 4p | 78H05KC | 520p | PFL200 | 85p | 4038 | 71p | 4510 | 57p | |
| AC126 | 17p | BC184L | 6p | BD238 | 24p | BU205 | 70p | TIP110 | 47p | 2N2905 | 20p | 2SC2262 | 27p | IN.4006 | 4p | 78G11C | 190p | PL36 | 80p | 4040 | 57p | 4511 | 57p | |
| AC127 | 15p | BC212 | 6p | BD433 | 28p | BU208 | 75p | TIP112 | 54p | 2N2906 | 18p | 2SD23A | 37p | IN.4007 | 5p | 79G11C | 215p | PL504 | 95p | 4041 | 40p | 4512 | 57p | |
| AC128 | 15p | BC212L | 6p | BD437 | 28p | BU208A | 80p | TIP115 | 45p | 2N2907 | 18p | 2SK135 | 400p | IN.4148 | 2p | 79HGKC | 670p | PL508 | 190p | 4042 | 58p | 4513 | 120p | |
| AC129 | 15p | BC213 | 6p | BD535 | 38p | BU208D | 120p | TIP117 | 56p | 2N3019 | 28p | MB3712 | 150p | IN.5400 | 9p | | | PL519 | 450p | 4043 | 57p | 4514 | 110p | |
| AC141K | 23p | BC213L | 6p | BD536 | 38p | BU326 | 85p | TIP120 | 43p | 2N3053 | 18p | TA205 | 90p | IN.5401 | 10p | | | PY81 | 70p | 4044 | 56p | 4516 | 65p | |
| AC142K | 23p | BC214 | 6p | BD537 | 38p | BU406 | 85p | TIP121 | 46p | 2N3054 | 35p | UPC575 | 100p | IN.5402 | 10p | | | PY88 | 40p | 4047 | 65p | 4518 | 65p | |
| AC153K | 23p | BC214L | 6p | BD538 | 40p | BU407 | 75p | TIP122 | 47p | 2N3055 | 32p | | | IN.5403 | 11p | | | PY500A | 160p | 4048 | 49p | 4520 | 60p | |
| AC176 | 18p | BC237 | 7p | BDX32 | 100p | BU408 | 100p | TIP125 | 47p | 2N3055H | 38p | | | IN.5404 | 11p | | | | | 4049 | 40p | 4522 | 60p | |
| AC176K | 20p | BC238 | 7p | BDX65 | 80p | BU500 | 110p | TIP126 | 56p | 2N3440 | 58p | | | IN.5405 | 12p | | | | | 4050 | 40p | 4526 | 60p | |
| AC187 | 15p | BC300 | 16p | BF180 | 16p | BU526 | 80p | TIP127 | 56p | 2N3442 | 85p | | | IN.5406 | 13p | | | | | 4051 | 62p | 4527 | 60p | |
| AC187K | 20p | BC301 | 18p | BF181 | 18p | | | TIP147 | 100p | 2N3702 | 9p | | | IN.5407 | 13p | | | | | 4052 | 61p | 4528 | 65p | |
| AC188 | 17p | BC302 | 18p | BF183 | 20p | | | TIP2955 | 34p | 2N3703 | 9p | | | IN.5408 | 13p | | | | | 4053 | 61p | 74 SERIES | | |
| AC188K | 23p | BC303 | 18p | BF184 | 20p | | | TIP3054 | 38p | 2N3704 | 9p | | | | | | | | | 4054 | 61p | 7400 | 22p | |
| ACY18 | 40p | BC327 | 6p | BF185 | 20p | | | TIP3055 | 34p | 2N3705 | 9p | | | | | | | | | 4055 | 90p | 7401 | 16p | |
| ACY19 | 40p | BC328 | 6p | BF194 | 5p | | | TIS43 | 45p | 2N3706 | 9p | | | | | | | | | 4056 | 85p | 7402 | 18p | |
| AD142 | 40p | BC337 | 6p | BF195 | 5p | MJ2500 | 100p | TIS44 | 40p | 2N3707 | 9p | | | | | | | | | 4057 | 85p | 7403 | 22p | |
| AD149 | 45p | BC328 | 6p | BF196 | 6p | MJ2955 | 55p | TIS61 | 15p | 2N3708 | 9p | | | | | | | | | 4058 | 42p | 7404 | 18p | |
| AD161 | 22p | BC357 | 6p | BF199 | 6p | MJ3000 | 115p | TIS88A | 45p | 2N3771 | 85p | | | | | | | | | 4059 | 25p | 7405 | 10p | |
| AD162 | 22p | BCY32 | 150p | BF200 | 16p | MJ3001 | 115p | TIS90 | 15p | 2N3772 | 85p | | | | | | | | | 4060 | 27p | 7406 | 100p | |
| AF124 | 25p | BCY33 | 150p | BF240 | 16p | MJE29A | 30p | TIS91 | 18p | 2N3773 | 100p | | | | | | | | | 4061 | 27p | 7407 | 80p | |
| AF125 | 25p | BCY34 | 150p | BF241 | 16p | MJE30A | 30p | TIS93 | 20p | 2N3819 | 25p | | | | | | | | | 4062 | 27p | 7408 | 25p | |
| AF127 | 25p | BCY42 | 20p | BF255 | 12p | MJE320 | 30p | VK1010 | 80p | 2N3886 | 68p | | | | | | | | | 4063 | 27p | 7409 | 25p | |
| AF139 | 22p | BCY56 | 16p | BF256 | 18p | MJE350 | 80p | VN.10KM | 80p | 2N4031 | 25p | | | | | | | | | 4064 | 27p | 7413 | 35p | |
| AF239 | 22p | BCY70 | 16p | BF257 | 18p | MJE520 | 30p | VN.46AF | 80p | 2N4036 | 25p | | | | | | | | | 4065 | 27p | 7414 | 45p | |
| AL112 | 70p | BCY71 | 16p | BF258 | 18p | MJE520 | 30p | VN.86AF | 100p | 2N4037 | 25p | | | | | | | | | 4066 | 27p | 7417 | 32p | |
| AL13 | 80p | BCY72 | 16p | BF259 | 18p | MJE2955K | 90p | VN.86AF | 100p | 2N4443 | 76p | | | | | | | | | 4067 | 27p | 7420 | 22p | |
| AS215 | 100p | BD115 | 26p | BF336 | 20p | | | VN.89AF | 110p | 2N4444 | 76p | | | | | | | | | 4068 | 27p | 7421 | 25p | |
| ASZ17 | 100p | BD124P | 50p | BF337 | 20p | | | | | 2N5061 | 28p | | | | | | | | | 4069 | 27p | 7425 | 15p | |
| AU110 | 110p | BD124 | 110p | BF338 | 20p | OC28 | 100p | | | 2N5294 | 28p | | | | | | | | | 4070 | 27p | 7430 | 25p | |
| AY102 | 180p | BD128 | 35p | BF362 | 30p | OC29 | 80p | ZTX107 | 11p | 2N5296 | 30p | | | | | | | | | 4071 | 27p | 7437 | 28p | |
| AY106 | 180p | BD131 | 25p | BF422 | 21p | OC35 | 100p | ZTX108 | 11p | 2N5298 | 30p | | | | | | | | | 4072 | 27p | 7447 | 60p | |
| | | BD132 | 25p | BF458 | 19p | OC36 | 120p | ZTX109 | 12p | 2N6106 | 40p | | | | | | | | | 4073 | 27p | 7448 | 45p | |
| | | BD135 | 25p | BF459 | 19p | OC45 | 50p | ZTX112 | 27p | 2N6107 | 40p | | | | | | | | | 4074 | 27p | 7450 | 22p | |
| | | BD136 | 20p | BF459 | 19p | OC71 | 30p | ZTX300 | 13p | 2N6109 | 40p | | | | | | | | | 4075 | 27p | 7451 | 10p | |
| | | BD137 | 20p | BF459 | 19p | OC72 | 50p | ZTX301 | 16p | 3N.128 | 55p | | | | | | | | | 4076 | 27p | 7454 | 25p | |
| | | BD138 | 20p | BF459 | 19p | OC200 | 180p | ZTX302 | 16p | 3N.143 | 65p | | | | | | | | | 4077 | 27p | 7470 | 30p | |
| | | BD139 | 20p | BF459 | 19p | R2008B | 80p | ZTX303 | 16p | | | | | | | | | | | 4078 | 27p | 7473 | 30p | |
| | | BD140 | 20p | BF459 | 19p | R2010B | 80p | ZTX304 | 17p | | | | | | | | | | | 4079 | 27p | | | |
| | | BD144 | 90p | BFY50 | 14p | | | ZTX320 | 25p | | | | | | | | | | | 4080 | 27p | | | |
| | | BD150 | 30p | BFY51 | 14p | TAG06-60 | 42p | ZTX326 | 25p | | | | | | | | | | | 4081 | 27p | | | |
| | | BD157 | 38p | BFY56 | 25p | TAG521-200 | 72p | ZTX500 | 13p | 2SA73 | 30p | | | | | | | | | 4082 | 27p | | | |
| | | BD158 | 38p | BFY56 | 25p | TAG4443 | 76p | ZTX501 | 13p | 2SA104 | 32p | | | | | | | | | 4083 | 27p | | | |
| | | BD166 | 30p | BFY64 | 25p | TAG4444 | 76p | ZTX502 | 18p | 2SA198 | 22p | | | | | | | | | 4084 | 27p | | | |
| | | BD175 | 30p | BFY90 | 60p | TIP29 | 15p | ZTX503 | 18p | 2SA203 | 30p | | | | | | | | | 4085 | 27p | | | |
| | | BD177 | 30p | BR100 | 14p | TIF29A | 24p | ZTX504 | 25p | 2SB54 | 25p | | | | | | | | | 4086 | 27p | | | |
| | | BD179 | 32p | BSX20 | 15p | TIF29C | 25p | ZTX550 | 24p | 2SB77 | 32p | | | | | | | | | 4087 | 27p | | | |
| | | BD181 | 45p | BT106 | 90p | TIP30 | 16p | 2N1131 | 28p | 2SC480 | 21p | | | | | | | | | 4088 | 27p | | | |
| | | BD182 | 45p | BT109 | 90p | TIP31 | 16p | 2N1132 | 28p | 2SC495 | 60p | | | | | | | | | 4089 | 27p | | | |
| | | BD183 | 60p | BT116 | 80p | TIP31A | 24p | 2N1613 | 24p | 2SC733 | 40p | | | | | | | | | 4090 | 27p | | | |
| | | BD201 | 32p | BT119 | 100p | TIP32 | 24p | 2N1711 | 24p | 2SC1161 | 110p | | | | | | | | | 4091 | 27p | | | |
| | | BD202 | 32p | BT120 | 100p | TIP32A | 24p | 2N2218A | 24p | 2SC1279 | 150p | | | | | | | | | 4092 | 27p | | | |
| | | BD203 | 32p | BT120 | 100p | TIP33 | 24p | 2N2219 | 24p | 2SC1279 | 150p | | | | | | | | | 4093 | 27p | | | |
| | | BD203 | 32p | BU104 | 100p | TIP34 | 50p | 2N2221 | 23p | 2SC1306 | 100p | | | | | | | | | 4094 | 27p | | | |
| | | BD204 | 42p | BU105 | 80p | TIP41A | 22p | 2N2222 | 23p | 2SC1307 | 100p | | | | | | | | | 4095 | 27p | | | |
| | | BD222 | 31p | BU108 | 100p | TIP41C | 25p | 2N2389 | 15p | 2SC1520 | 25p | | | | | | | | | 4096 | 27p | | | |
| | | | | | | | | | | | | | | | | | | | | | 4097 | 27p | | |
| | | | | | | | | | | | | | | | | | | | | | 4098 | 27p | | |
| | | | | | | | | | | | | | | | | | | | | | 4099 | 27p | | |
| | | | | | | | | | | | | | | | | | | | | | 4100 | 27p | | |
| | | | | | | | | | | | | | | | | | | | | | 4101 | 27p | | |
| | | | | | | | | | | | | | | | | | | | | | 4102 | 27p | | |
| | | | | | | | | | | | | | | | | | | | | | 4103 | 27p | | |
| | | | | | | | | | | | | | | | | | | | | | 4104 | 27p | | |
| | | | | | | | | | | | | | | | | | | | | | 4105 | 27p | | |
| | | | | | | | | | | | | | | | | | | | | | 4106 | 27p | | |
| | | | | | | | | | | | | | | | | | | | | | 4107 | 27p | | |
| | | | | | | | | | | | | | | | | | | | | | 4108 | 27p | | |
| | | | | | | | | | | | | | | | | | | | | | 4109 | 27p | | |
| | | | | | | | | | | | | | | | | | | | | | 4110 | 27p | | |
| | | | | | | | | | | | | | | | | | | | | | 4111 | 27p | | |
| | | | | | | | | | | | | | | | | | | | | | 4112 | 27p | | |
| | | | | | | | | | | | | | | | | | | | | | | | | |

COLOUR TELEVISIONS

PYE CHELSEA – 6 button
PYE 723

PHILIPS G8 550 THORN 8000, 8800
THORN 9000, 9200, 9600 Remote Control

Working panels and tubes available.

REBUILT TUBES

Delta – In Line – PIL.

SOUTHBRIDGE TV CENTRE
120, Selhurst Rd., London, S.E.25.
Tel: 01-771 3535.

TEL-X BLACKBURN

FOR THE VERY BEST IN
TELEVISION DISPOSALS

Decca Philips Thorn ITT Pye GEC Bush + Remotes

☆ ☆ ☆ ☆ ☆ ☆ ☆ ☆

HUNDREDS TO CHOOSE FROM
WORKERS FROM **£25.00**
Off the Pile from **£ 8.00**

☆ ☆ ☆ ☆ ☆ ☆ ☆ ☆

DELIVERIES ARRANGED ON QUANTITY

TEL-X BLACKBURN

Unit P3, Roe Lee Industrial Estate,
Whalley New Road,
Blackburn, Lancs.

Tel: 0254 679984

COLOUR T.V.'S

FROM £20 LARGE SELECTION OF
WORKING COLOUR T.V.'s

BUY FROM OUR RETAIL SHOWROOMS
AT TRADE PRICES

ALL MAKES INC. ITT, PHILIPS, THORN, GEC, ETC.

DISCOUNT FOR SPEND OVER £100 LESS 5%
QUANTITY SPEND OVER £200 LESS 10%

VAN LOADS AVAILABLE DIRECT FROM SOURCE

WEST SIDE TV CENTRE
17 West Side Centre,
LUTON
Tel: 0582-24177

KENWOOD TV CENTRE
TRITEL HOUSE
Thornbury Roundabout,
Bradford,
Tel: Mr Kept 0274 665670

EMCO – EUROSONIC – GRUNDIG – TELETON + ALL BRITISH MAKES
ETC. ETC. ● ALL SPARES READILY AVAILABLE ●

IMMEDIATE CREDIT AVAILABLE – TRADE ONLY

If you are a trader simply phone for the part you require and we will send it – no quibble – no hold up for status check. Satisfy us over the phone that you are a trader and we will supply almost any TV component by return "off the shelf". e.g. LOPTX – EHT trays – droppers – OSC coils – switches – cans – smoothers – I.C.'s, etc. etc.

**YOU CAN BE 95% SURE WE CAN SUPPLY ANY
TV COMPONENT BY RETURN
IF YOU NEED SPARES FAST – RING NOW!**

ACCESS AND BARCLAYCARD ACCEPTED.

Applies to U.K. only.

TELE-PART (W'TON)

THE TELECENTRE, WORCESTER ST.,
WOLVERHAMPTON (0902) 773122

It's easy to complain about advertisements. But which ones?

Every week millions of advertisements appear in print, on posters or in the cinema. Most of them comply with the rules contained in the British Code of Advertising Practice.

But some of them break the rules and warrant your complaints.

If you're not sure about which ones they are, however, drop us a line and we'll send you an abridged copy of the Advertising Code. Then, if an advertisement bothers you, you'll be justified in bothering us.

The Advertising Standards Authority.

If an advertisement is wrong, we're here to put it right.

ASA Ltd, Dept 2 Brook House, Torrington Place, London WC1E 7HN

This space is donated in the interests of high standards of advertising.

LONDON'S LARGEST TELEVISION
WHOLESALER...
with over 4½ thousand sq. feet.

"TELEMANN"

8-10 RHODA STREET,
(Off Bethnal Green Road)
LONDON E.2. FREE CAR PARK
TEL: 01-739 2707

ALL MAKES IN STOCK AND GUARANTEED
COMPLETE

The only wholesaler with a
guaranteed single price. If the sets
work or not our price is the same!
Free delivery to the London area.

Telephone 01-739 2707 –
NOW!

Philips VCR 1700 with new boxed
1½ hour cassette and mains lead
£45. Single standard mono's £3.

PHILIPS 22" (Model 520) Parcel of ten £15
PHILIPS 22" (Piano Key 550) Parcel of ten £20
JAPANESE MODELS 18"-20" £30

FREE DELIVERY TO THE LONDON AREA!

SETS & COMPONENTS

GRUNDIG, WORKING FROM £40. Reconditioned panels from £4. Remote handsets wanted. Telequipment oscilloscopes. Ochre Mill 0785 814643.

JAPANESE COLOUR TVs. Panasonic, Hitachi, Mitsubishi, Toshiba, Sharp. Fully refurbished. Trade only. J.M. Pearson Television. 0484 863489.

NEED R.S. COMPONENTS for your project. No account?. We will supply you. For details phone 0376 519208.

SECOND HAND Colour TV spares and tubes. Most makes. Telephone Southport (0704) 74411. Anytime.

PANELS

**GOOD WORKING
POST PAID NO VAT**

| Make | Power Supply | Line Panel | T.Base Decoder | D | IF Tripler | Convergence |
|----------------|--------------|------------|----------------|--------|------------|-------------|
| Thorn 3500 | £12.00 | £9.50 | £6.50 | £5.00 | £3.00 | £4.00 |
| Thorn 8500 | £5.00 | - | £9.50 | £11.00 | - | £4.00 |
| GEC S/S | £6.50 | £11.00 | £6.50 | £9.50 | £11.00 | £4.00 |
| Bush Twin Chip | £6.50 | £6.50 | £6.50 | £11.00 | £6.50 | £4.00 |
| Decca | £6.50 | £6.50 | £6.50 | £9.50 | £6.50 | £4.00 |
| Bradford | £6.50 | £6.50 | £6.50 | £9.50 | £6.50 | £4.00 |

TUBES

£29.00

INCLUSIVE, REGUNS TWO YEAR GUARANTEE, QUANTITY DISCOUNTS

£14.50

SIX MONTH GUARANTEE SLIGHTLY USED

A56-120 A56-140 A51-110 A49-191 A47-342 or 343
A44-270-1 A66-120 A67-120 (All 26" add £5)

IN-LINE 51-161 From £35 plus 100's more

Delivery £5 per tube. British Isles.

No need to spend £5 returning old tube if you buy from us.

U-VIEW TUBES,

29 Warmsworth Road,

Doncaster, Yorkshire DN4 0RP.

Tel: 0302-855017.

Callers ring first: Open every day including Sunday

PORTABLE TV TUBES

£15 inclusive delivery with one year guarantee.

110" only - A31-101-120-300-410-510
A34-100-101-120-510

U-VIEW (TUBES)

29 Warmsworth Road, Doncaster DN4 0RP.
(0302) 855017.

Open 7 days. Callers ring first.

WETSTED TUBES

**PRESENTS AN
UNBEATABLE OFFER**

£26 ALL DELTAS ONE PRICE

£40 ALL P.I.L. ONE PRICE

* SPECIAL CRT POLISHING SERVICE
WHILE U WAIT **Only £5**

* ALL DELTA SIZES FROM STOCK
* DISCOUNT FOR ORDERS OF 5 CRTS OR OVER

* FREE DELIVERY WITHIN 20 MILE RADIUS OF MAIDSTONE

Ring Now

Maidstone 872400

or visit our factory.

Unit 32, Branbridges Ind Est.

East Peckham, Kent.

* Agents required in South

Prices do not include VAT

TELEVISION

No other consumer magazine in the country can reach so effectively those readers who are wholly engaged in the television and affiliated electronic industries. They have a need to know of your products and services.

The prepaid rate for semi display setting £6.00 per single column centimetre (minimum 2.5 cms). Classified advertisements 35p per word

GENERAL TELEVISION TRADE SALES

3-5 UNION ST.
DONCASTER

FACTORS

Telephone:
(0302) 68416

Regular weekly supplies of good quality TVs, all with excellent cabinets, we look after our sets, we don't knock them about, as you'll see if you call, suitable for re-sale or rent. Working or off the pile. We're always happy to see you, whether its for one TV or one hundred and one.

MONDAY TO SATURDAY 9 to 5.30

GOOD SETS
GOOD SERVICE
CALL & SEE US YOU
WON'T BE DISAPPOINTED
Special Prices on Philips G8's & Other Lines

STANDS, LEGS,
SLOTMETERS, PANELS,
TUBES ETC.



PHONE
NOW
(0302) 68416

RANK
SABA
KORTING
THORN
EKCO
ETC.

PHILIPS
PYE, JAPANESE
DECCA, GRUNDIG
GEC, ITT

**EXCELLENT MOTORWAY ACCESS FROM MOST PARTS
VIA M1 OR A1
WE'RE ONLY A SHORT DRIVE AWAY**

PROJECTION TVs, 60 inch screen. Also projection TV. D.I.Y. kits. For details phone 0376 519208.

SATELLITE TV RECEIVER

Receives 4GHz band. Ideal for demonstration terminal in U.K. 100 degree Kelvin LNA. £392 + VAT (+ Carr). LNA/down converter PCB's stocked for the constructor. SAE data.

HUGH COCKS TV SERVICES,
Cripps Corner, Robertsbridge,
Sussex TN32 5RY. Tel. 058083 317.

Thorn 3000/3500
Thorn 9000
UNIVERSAL
1 year guarantee

TRIPLERS
£4.50 inc. p&p

The UNIVERSAL TRIPLER can be used in most G.E.C., I.T.T., Pye, Rank, Decca & Continental sets.

WING ELECTRONICS

15 Waylands, off Tudor Rd, Hayes End, Middlesex

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact COLES-HARDING & CO, 103 South Brink, Wisbech, Cambs. 0945 584188. Immediate settlement.

NORTHERN IRELAND DEALERS

We have the best value in secondhand televisions. And our low, low prices are second to none. Philips 550, Decca 100/80/302, Pye 741 series and many other makes available.

Prices: Non workers (complete) from £20.

Guaranteed workers from £38.

We deliver bulk orders anywhere in Northern Ireland.

New loads arriving regularly so phone now for latest stocks.

SM ELECTRONICS

11 Sandholes Road, Cookstown N. Ireland.

Tel: Cookstown (NI) 06487/64277.

SERVICE PAGES

(minimum 12 words), box number 70p extra. All cheques, postal orders etc., to be made payable to Television, and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Dept., Television Room 2612, IPC Magazines Limited, Kings Reach Tower, Stamford Street, London SE1 9LS. (Telephone 01-261 5846).

SCREENPLAY *Bursting with Stock!*

Guaranteed - Complete Sets from £10.00
Trade Workers from £25.00
Panels By Post from £3.00
Mono's from £1.00
Stands - Aerials - Accessories Etc.


WORKING SETS

Phone us first for quantity, we can give an UNBEATABLE PRICE!!!

OPEN 5 DAYS -

Phone:

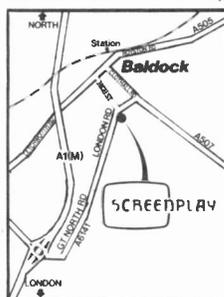Baldock 894905, Hitchin 31644
 SECTION THREE, UNIT FOUR, SERL COMPLEX,
 LONDON ROAD, BALDOCK, HERTS.



REBUILT COLOUR TUBES

EXAMPLE PRICES DELTA
 All sizes up to 22" — £28.00
 26" From — £32.00

All In Line P.I.L. Mono Gaming Machine
 C.R.T.s 560EGB22 56-611-510JKB22

20 AX £40.00
 30 AX £48.00

Fast U.K. Delivery

Call or Phone:

RE-LIFE T.V. TUBES
 PLANE STREET,
 OLDHAM, LANCS.
 061-665 2668

Wholesalers REG in North & South Wales
Competitive Prices

COLOUR TV's AT ROCK BOTTOM PRICES

SOME EXAMPLES ARE:

| | Untested | Working |
|-----------------|-------------|-------------|
| G8 520 | From £12.00 | From £20.00 |
| G8 550 | From £20.00 | From £30.00 |
| GEC Solid State | From £15.00 | From £25.00 |
| ITT Hybrids | From £12.00 | From £20.00 |
| JAP | From £25.00 | From £30.00 |

Many other makes always available

ALL SETS SOLD AS WORKING ARE PREPARED TO HIGH SPECIFICATIONS AND ARE READY FOR RETAIL OR RENTAL

REGUNNED TUBES:

| | | |
|----------------------|--------|----------------|
| Up to 22" Delta 90° | £27.00 | 2yr. guarantee |
| Up to 26" Delta 90° | £30.00 | 2yr. guarantee |
| Up to 22" Delta 110° | £28.00 | 2yr. guarantee |
| Up to 26" Delta 110° | £31.00 | 2yr. guarantee |
| PIL & In Line | £45.00 | 2yr. guarantee |

30AX (A56 410/A66 410) Add £5.00 for magnets.
 REGUNNED TO THE HIGHEST SPECIFICATIONS
 (OVER 15YRS. EXPERIENCE).

OURS ARE THE BEST BECAUSE WE WANT OUR CUSTOMERS TO COME BACK

INTEL TELEVISION SERVICES

Unit 27 Whessoe Road Darlington Co. Durham
 Telephone Darl. 486896

CANVEY COLOUR TUBES

Unit 3, Charfleets House, Charfleets Industrial Estate, Canvey Island, Essex.
 Tel: Canvey Island (0268) 690577

CURRENT PRICE LIST

DELTA TUBE TYPE FROM £27.50 to £31.50
 INLINE TUBE TYPE FROM £35.00
 MONO TYPES P.O.A.

ALL PRICES EXCLUSIVE OF VAT.

All Tubes Guaranteed for 2 YEARS and Reprocessed to Original Manufacturers Specifications.

A.B.D. TELEVISIONS

Suppliers of colour and mono televisions to the trade.

Workers and non-workers:

Pye Chelsea, Philips, Pye, GEC, Thorn 8500, 8800, 9000 and 9600, Bush T20 and TT22, ITT 600 series, Japanese, Hitachi, Nat. Pan J.V.C.

Many other modern sets by popular manufacturers.

For quotation and prompt service:

Ring Notts (0602) 864627
 UNIT 3+3A,
 Meadow Trading Est.
 Meadow Lane,
 Nottingham NG3 3HQ.

TO ADVERTISE IN THIS SPACE RING MANDI 01-261 5846

WOODSDALE COMPONENTS RANK BUSH MURPHY TRANSFORMERS

Line Output

| | |
|---------------------------------|--------|
| Z718 (T703A, T706A) | |
| New (Complete) | £20.50 |
| Less Focus Module and Rectifier | £10.50 |
| T20, T22 (T705A) | £10.00 |
| T26 (T705B) | £11.50 |
| Switch Mode T114A/B | £8.00 |

Genuine RBM Units.

AERIALS

| | |
|--|--------|
| UHF Aerials P & C Wideband 4 Bay Bowtie (12.5 dB) | £20.00 |
| Above with built-in Broadband amp. (27dB) plus stabilised power supply | £45.00 |

Prompt Postal Service.
 Add 15% VAT to all prices.
DISCOUNT for QUANTITIES.

34 Field End Road, Eastcote, Pinner, Middlesex. HA5-2QT.
 Tel: 01-868 5580.

N. Skehan

Agents Office. Callers by appointment only.

THE TV WAREHOUSE

Your local Trade and Retail suppliers of CTV's, Special clearance of older models.

THE TV WAREHOUSE

Watling Street (A5),
 Hockliffe, Beds.
 Tel. Leighton Buzzard 210686

N.W. ELECTRONICS

25 YEARS SUPPLYING THE TRADE

HUGE STOCKS OF COLOUR TV'S 2000 NOW IN STOCK

ROCK BOTTOM PRICES. ALL MAKES, ALL MODELS.

90% WORKERS (off the pile)

GENUINE REPOSSESSIONS AND EX RENT, NOW IN STOCK!

PYE KT 3, PHILIPS G11, G8, BUSH T20, 22, 718, GEC, 2010, 2201, 2002, 2659, HITACHI, SANYO, PYE 222 THORN 9000, 3500, 8800 ETC.

SPECIAL OFFERS

BUSH 2 chip 20"/22" Exc. CAB Cond. GENUINE CHANGE OVERS **£15 EACH**
(special quotes on bulk orders) . . . Single Chip **£10.**

| | | | |
|-------------------------------------|----------|-------------------|-----|
| PHILIPS 26" G8 EXC. COND. 550 model | £20 each | BUSH 718 PIL TUBE | £30 |
| BUSH 22" REMOTE 718 ONLY | £30 | BUSH T20 LIKE NEW | £65 |
| HITACHI 20" MODEL 190 EXC. CAB | £25 | in lots of 10 | £55 |
| THORN 9000 PIL TUBE | £40 | in lots of 50 | £50 |

VHS VIDEO

SHARP 7300, 8300, 9300. FERGUSON 3V28 3V22. SONY BETA.

MONO TV'S £2 EACH

BUSH, GEC, PYE, PHILIPS ETC. THORN 1500 **£6.** THORN 1600 **£15** (like new).

REFURBISHED TV'S TO ORDER

PHILIPS G11 **£85** BUSH T20/22 **£75** GEC 2010 **£38**

LATER MODELS PHONE FOR QUOTATION

WHITE GOODS

HOOVER TWINS FROM **£6.** HOTPOINT 1460 FROM **£10.**

AUTOS ALL MAKES FROM **£10**

SPARES! SPARES! TV PANELS

| | I.F. | DECODER | LINE D/P | POWER | CONVERG. | VIDEO | FRAME T3 |
|-------------|------------------|---------|----------|-------|----------|-------|----------|
| BUSH 2 CHIP | 3.00 | 8.00 | 6.00 | 3.00 | 3.00 | — | 5.00 |
| 3000/3500 | 2.00 | 4.00 | 8.00 | 8.00 | 5.00 | 5.00 | 6.00 |
| G8 | 5.00 | 7.00 | 14.00 | 8.00 | 5.00 | — | 5.00 |
| | with sound panel | | | | | | |
| GEC 2110 | 10.00 | 5.00 | 12.00 | 6.00 | 5.00 | 5.00 | 5.00 |
| BUSH 718 | 8.00 | 15.00 | 25.00 | 3.00 | 5.00 | — | 15.00 |
| BUSH T20 | 8.00 | 15.00 | 20.00 | 20.00 | 5.00 | — | 15.00 |

P&P 1 panel £1.50, 2 panels £2.00, 3 panels £2.50 etc. Quick Despatch - C.W.O. please
ALL PRICES PLUS VAT.

CASH ONLY - DELIVERY CAN BE ARRANGED

(0274) 688458 OPEN 6 DAYS A WEEK

**Unit 12, Wharfedale Road
M606 Euroway Estate
Bradford**

**OPEN MON-SAT 9-5.30
Don't forget! We are open
all day Saturday!**

EAST ANGLIA SUPPLIES

Fully working colour TVs from £25.00 plus VAT straight from our retail shelves. Most makes are available and small regular orders are welcome. Personal services guaranteed and if we can help you boost your rental or retail trade we would be delighted.

Free delivery available
(only petrol charged).

Contact John, Dave or Steve at
Barry T.V. Services
on Cambridge 69215
or Ely 61462

TELEVISION

Trade & Retail supplies of
s/h colour & mono TVs.
Most makes available,
workers or non-workers

SOUTHPARK DISTRIBUTORS

Unit 4 Rubastic Road,
Brentpark Industrial Estate,
Southall, Middx. UB2 5LL.
01-574 4631, Ext 28

ELECTRONIC SUPPLIES

Large superfluous stocks for disposal. 3000-3500 Power Packs Line Timebase Frame Chrominance Video I/F Etc. Complete but untested AUDIO Speaker Cabinets various types small to large, also various types complete RECORD DECKS Transcription Type BSR P128 P146R C173 GARRARD 620S SP25MK4 125SB RECORD CHANGERS BSR 123 C129-D1 C129-R2 2025TC 6300 5300. COMPONENTS Resistor Condensers Jack Plugs Sockets Transformers Switches Skeleton Pre-set EHT Trippers ETC.

Send 17p stamp for Catalogue to:
18 LEUCHA ROAD,
LONDON, WALTHAMSTOW E17 or
Phone 01-521 3912 after 6.30 evenings.
TRADE ENQUIRIES WELCOME

TELEVISION TUNER REPAIRS

BRITISH, EUROPEAN
JAPANESE ETC.

ELC 1043/05 TUNERS
AS NEW £4.60 inc.

MEN-TU ELECTRONICS LTD.
SALTERS LANE,
FAREHAM, HANTS.

Tel: 0329-235116

Trent Tubes

31 RADCLIFFE ROAD,
WEST BRIDGFORD, NOTTINGHAM

THE QUALITY REBUILDER

PHONE 0602 813329

ALL TUBES CARRY A 2 YEAR GUARANTEE

EXTENDABLE TO 4 YEARS

ALL SIZES OF STD DELTA's £26.50

A51-161, etc. £37.00

A56/66-510 (20AX) £40.00

A56/66-540 (30AX) £49.00

560 OZ B22 £41.00

JAPANESE TYPES OUR SPECIALITY

1000's MORE TYPES AVAILABLE

VDU MONO INDUSTRIAL TYPES PLEASE PHONE

☆ STOCKISTS ☆

PETERBOROUGH: H. DONNOR, 0733 71809

HENESFORD: Redivision Ltd., 054 38 77135

Thorn Colour TVs – Most models

Decca 1051/2 (100 series)

Philips 660 etc (G11) 550 (G8 Series 05)

ASSORTED GEC/BUSH/PHILIPS/JAP etc

Working or guaranteed untested basis

Competitive prices/good cabinets/top quality

If your standards are as high as ours, we want to deal with you – regularly!

REPOSSESSED TV CENTRES LTD 061-273 2854

335-341 Stockport Rd, Longsight, Manchester 13.

Sandwell T.V. Centre

1000's of T.V.'s at tremendously low prices.
mono's from £1-00.---colour from £7-00.
WORKING HYBRID £15-
Brunswick Park rd. Wednesbury off jct.9. M6.



- * Britains most reliable source of quality TVs.
- * Hundreds of working polished TVs.
- * New adjustable TV stands.
- * Pye 18" Chelsea's working & polished £35.00 in quantity.

Krystal Marketing Ltd,
Breedon Cross Storage,
Dale Road, Selly Oak,
Birmingham B29 6AQ.

Phone 021-471 3023
Telex 335540-G
Ask for Les

TRADE COLOUR TV's ALWAYS 200 IN STOCK

Colour from £5.00 Mono £2.00

BRAND NEW VIDEOS

V2022 and V2023

VHS and BETA

Just in

20" + 22" GEC

Boxed with stand £85.00

ALL STOCK CHANGES WEEKLY

(0934) 514047/512792/27560

P&R SUPPLIES, Unit 5,

Worle Industrial Estate,

Weston-Super-Mare. Exit 21 M5.

COLOUR TV PANELS Fully Tested & Working

| | IF | CDA/ Video | Decoder | LTB | Line Board | Power |
|-------------|-------|---------------|---------|-------|---------------|-------|
| GEC 2040 | 3.50 | 3.50 | 4.00 | 5.00 | - | - |
| DECCA 13/30 | 3.00 | - | 7.00 | 5.00 | - | 4.00 |
| BUSH A823 | 4.00* | - | 10.00* | 5.00* | 2.50 | 4.00 |
| THORN 8/8j | - | - | 10.00 | 5.00 | - | 5.00 |
| PYE 205 | 3.00 | 3.50 | 5.00 | 10.00 | - | - |
| THORN 3/3j | 5.00 | 5.00 | 5.00 | 8.00 | - | 10.00 |
| G8 | 6.00 | - | 8.00 | 7.00 | 15.00 | 5.00 |

*Please specify prefix A or Z.

Please add 15% VAT to above prices, then add post + packing.
Post + Packing: 1 panel £1.50; 2 panels £2.25; 3 panels £3.00 etc.

Hybrid panels do not include valves.

Terms cash with order.

Also a vast selection of modern working and non-working TVs at low prices. Please ring for current stock.

GOLCAR T.V. SERVICES (formerly LAVITE LTD.),

Old C of E School, Church Street, Golcar, Huddersfield. Tel.: 0484 643273

Callers by appointment only.

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of
Television for

insertions. I enclose Cheque/P.O. for £
(Cheques and Postal Orders should be crossed Lloyds Bank Ltd and made
payable to Television)

| | | | |
|--|--|--|--|
| | | | |
| | | | |
| | | | |

NAME

ADDRESS

Send to: Classified Advertisement Dept.

TELEVISION

Classified Advertisement Dept., Room 2612,
King's Reach Tower, Stamford Street,
London SE1 9LS. Telephone 01-261 5846.

Rate

35p per word, minimum 12 words. Box No. 70p extra.

Company registered in England. Registered No. 53626. Registered Office: King's Reach Tower, Stamford Street,
London SE1 9LS. 9/84

COLOUR T.V.s

THE BEST IN LONDON
200 + TVs WEEKLY

LOADS SMALL SCREEN
WORKING SETS TO
ORDER — ALL MAKES

WINDSOR WHOLESALE
TEL: 01-968 8771.

IRISH DEALERS

Most brand names of UHV — VHF
Colour & B/W working.

Clean sets at very keen prices.
Delivery arranged.

Quantity discount.

(SPECIALISTS IN EXPORT ORDERS)

TV TRADE SALES

E.D.I. House,
Kylemore Park West,
Dublin 10.
Tel. 01.264139 Ext 11.

WORKING CTV's

The Best & Cheapest in Lancashire

| | |
|------------------------|--------|
| I.E. Decca 18" to 26" | £24.00 |
| GEC 20" to 26" | £30.00 |
| Philips G8 22" to 26" | £25.00 |
| Bush 20" to 26" 2 chip | £18.50 |

All sets are tested & working

Many more makes & types available.
Working mono's only £3.50. Non work-
ers available.

Phone: John Powney
at Kirkham, near Preston
(0772) 683392.

TRADE-TEL TV DISPOSALS

G8550s from £8.00
Polished & Tested £30.00
UNIT B11A South West
Brunswick Dock
Liverpool L3
Merseyside

COLOUR BAR GENERATOR

Pal Colour Generator with 11 patterns plus sound. Grey
scale, Colour Bars, Red, Green & Blue Raster, Cross-
hatch, Dots, Chequer Board, Black Raster, White Raster,
Half Black & White £75.90.



| | |
|---|--------|
| Line Transformer Tester | £11.50 |
| B/W Generator, Crosshatch, Peak White, Dots, Half Black & White and Grey Scale | £18.50 |
| In Circuit Transistor Tester | £14.25 |
| Capacitance Meter measures 10pF to 1µF complete with moving coil meter | £14.75 |

S.A.E. for details. — Prices include P&P & VAT.

C.M.J. ELECTRONICS

Unit 8, 16 Union Mill Street, Horseley Fields,
Wolverhampton WV1 3DW.
Tel: (0902) 871563

TELEVISION

T.V. SPARES, PANELS AND MANUALS PHILIPS · GRUNDIG

TELEVIEW 01-994 5537
194, Acton Lane, London W.4.

IRISH T.V. DEALERS

English Tubes in Stock
Delta — In Line — Mono — Tubes Boxed — Bring
Glass — Try the Best. Tubes off Computerised
Assembly Line with Electronic Post-testing.
Hours 9 am-9 pm — Sunday 10 am-1 pm.

Phone: 029 50046
Kelleher Bros
T.V. Stores
Kanturk, Co. Cork.

BOOKS AND PUBLICATIONS

"RADIO AND TELEVISION SERVICING" books,
new editions for the last 6 years always in stock. Prices
on request. BELLS TELEVISION SERVICES, 190
Kings Road, Harrogate, N. Yorkshire. Tel. 0423 55885.
RADIO AND TELEVISION SERVICING BOOKS
76/77 — 77/78 — 78/79. 79/80 — 80/81 — 81/82 — 82/83
— (83/84 available August) £22.50 Free Delivery.
U-VIEW, 29 Warmworth Road, Doncaster. Tel.
0302 855017.

RADIO AND TELEVISION SERVICING MANUALS
1970 to 1976, mint condition. Also Television
Monthly 1977 to 1982. Offers. Tel. 061-865 6570.

COMPLETE FULL-SIZE SETS any published service
sheets £2 + LSAE except CTVs/Music Centres from
£3 + LSAE. Manuals from 1930 to latest. Quotations,
free 50p magazine, price lists, unique technical publica-
tions for sale. Repair data/circs almost any named TV/
VCR £8.50 by return. TIST, 76 Church Street, Lark-
hall, Lanarks ML9 1HE. Phone (0698 883334).

SERVICE SHEETS

TELEVISION SERVICE SHEET SPECIALISTS

Thousands of British, European, and Japanese models in stock.

Colour £2.00 Mono £1.50 (post free)

Manual prices on request.

Send stamped envelope for free catalogue and enquiries

SANDHURST TV SERVICES (MAIL ORDER)

49C Yorktown Road, Sandhurst, Camberley, Surrey GU17 7AG

30,000 SERVICE SHEETS IN STOCK ALSO COLOUR MANUALS AVAILABLE

TV Sheets, Black and White, also Radiograms, Record Players, Music Centres.
Japanese models in stock. Circuit diagrams only. Also Tape Recorders etc etc,
ALL AT £3. Please forward s.a.e. Send cheque or P.O.

C. CARANNA, 71 BEAUFORT PARK, LONDON NW11 6BX.

BELL'S TELEVISION SERVICES for service sheets
on Radio, TV, etc. £1.50 plus S.A.E. Service manuals
on colour TV and Video Recorders, prices on request.
S.A.E. with enquiries to B.T.S., 190 Kings Road,
Harrogate, N. Yorkshire. Tel. (0423) 55885.

TECHNICAL INFO SERVICES

76 Church St — Larkhall — Lanarks

Giant TV & VCR DIAGRAM MANUALS

| | | |
|---|--------|-----|
| Brit CTVs | 3 vols | £45 |
| Vol. 1 Decca G.E.C. ITT | | £17 |
| Vol. 2 Philips Pye Redif. | | £17 |
| Vol. 3 Rank Bush Thorn | | £17 |
| Foreign CTVs (now updated) | 2 vols | £32 |
| Mono (Stand + Port) | 2 vols | £32 |
| Early VCR (VHS/Philips) | | £17 |
| VCR later models inc. Betamax | | £17 |
| Domestic Equipment Exploded Diagrams in 2 huge binders for | | £32 |

New T.V. Rep. Manuals £7.50 each
1983 Brit. CTV or Foreign CTV 4
Complete set of 15 TV Rep Mans for £105

Unique T.V. Repair course £9.50
The only practical radio servicing and
repair course £9.50

Large SAE brings FREE 50p magazine
inc. service sheet/details of unique T.V.
publications. Any quotation plus price
lists, etc.

Full size service sheets £2 + I.s.a.e.
CTVs/Music Centres £3 + I.s.a.e.

Worlds largest collection of service man-
uals 1930 to date. From £4.50 to £35
each.

e.g. Autovox/G8/A823 £7.50 each
Integrated TV repair system £195.
Contains over £250 normal prices.

FOR FAST QUOTES
RING 0698 883334

EQUIPMENT FOR SALE

★ VIDEO FADER UNIT ★

- ★ SUITABLE FOR ALL VIDEO TAPE FORMATS
- ★ PRODUCE YOUR OWN HOME VIDEO
- ★ ALLOWS TAPE ASSEMBLY AT BLACK LEVEL
- ★ FULL COLOUR T.V. BANDWIDTH
- ★ MAINTAINS FULL SYNCHRONISM
- ★ OPERATES ON 12 VOLTS DC (P.S.U. AVAILABLE IF REQUIRED)
- ★ UNIQUE PRESENTATION
- ★ FULLY GUARANTEED
- ★ ONLY £59.95 INCLUDING P&P or send large S.A.E. for full spec
- ★ FIRST OF AN EXCITING RANGE OF NEW PRODUCTS AVAILABLE EXCLUSIVELY FROM:

LEAP PRODUCTS

5A London Road,
Loughton, Milton Keynes MK8 OAE
Please allow up to 28 days for delivery

When replying to Television Classified Advertisements please ensure:

- (A) That you have clearly stated your requirements.
- (B) That you have enclosed the right remittance.
- (C) That your name and address is written in block capitals, and
- (D) That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

SERVICE PAGES

MISCELLANEOUS

BURGLAR ALARM EQUIPMENT. Latest discount catalogue out now. Phone C.W.A.S. ALARM 0274 731532.

AERIALS

APEX ELECTRONICS & AERIALS CENTRE: TV - Stereo - CB aerials/accessories. 5 Park Road, Wellingborough - 73040.

CLEARVIEW AERIALS

Clearview have pleasure in announcing a full and comprehensive range of signal amplification equipment. For example: low noise electronically remote controlled masthead pre-amp 1.6db noise, CH, 17-69. Set side amplifiers, distribution amplifiers, notch filters 4 in 1 or 2 in 1 etc. Combiners for 2 UHF aerials 3db gain or 4 6db gain. Trade and retail.

Send large SAE for our comprehensive catalogue

CLEARVIEW AERIALS,
173 Kings Road,
Kingston Upon Thames, Surrey.

AERIAL BOOSTERS

B45H/G-UHF TV next to the set fitting, gain about 20db, PP3 battery or 8V to 14V/working. Price £8.70. P&P 30p.

UHF TV BOOSTER MODULE. PCB ready made up to cover the complete UHF TV band. Gain 10db, noise 1.9db. 8V to 14V/W. Price £2.50. P&P 30p.

AMPLIFIED SET TOP AERIALS. Trebles the gain, fully portable, price includes batteries. Price £9.70. P&P 50p.

CAPACITOR PACKS. Mixed C280 & Electrolytics, values from .01uf to 500uf. Price per pack of 150 capacitors £2.00. P&P 50p.

ELECTRONIC MAILORDER,
62 Bridge Street, Ramsbottom,
Lancashire, BL0 9AG.
Tel: Ramsbottom (070 682) 3036.

S.A.E. for leaflets. Access/Visa Welcome.

WANTED

'RADIO & TELEVISION SERVICING' books 1974-1984. Also T.V./video manuals. Stourbridge 0384 377209.

WANTED. We will clear any amount of colour sets from small Rental Companies, Hotels, etc. Please phone P & R Domestic Electrical Clearance Supplies, Weston Super Mare (0934) 514047.

BUSINESS/PROPERTY FOR SALE

FANTASTIC OPPORTUNITY

SHOP LEASE FOR SALE!
TV and Video repair/sales premises. Busy main road into London. Low rent/long lease. New shop front, grills and fully alarmed.

ONLY £7,950 for quick sale

TEL: 907 9232

FOR SALE

EX RENTAL VHS VIDEO'S. Trade only. Ring 0462 55960 for details.

CASSETTE MOTORS

6 volt D.C. with electronic speed control will fit Japanese decks.

New and unused £2.50 inc. p&p. C.W.O. please.

STEWART ELECTRONICS
4 Russell Street,
Ashton-U-Lyne, Lancs. OL6 9PX.
- CALLERS WELCOME -

FOR SALE

TANONTON ELECTRONICS SUPPLIES LIMITED

59 PALMERSTON ROAD, WALTHAMSTOW E.17

BARGAIN CORNER

New Service Manuals BU5005
Examples HMV Model No. 3470 BU208
Studio Six Audio Centre HMV Model No. 3497 BDX32
Stereo Tuner Amplifier HMV Model No. 3286 R2210
3286 R009
RAMO Cassette Recorder Ferguson T/V 3K5 4000 R008B
9000 Series. Pack or 10 mixed £5.00 R2029
Add £2 P&P R2781
2N3055 Unmarked 20 for £1.50 T9038
Mixed Bag IC's Reclaim Untested £1.00 T9013V
Small Spares £1.50 per box 2.5B425
Add £2 P&P (New) 2SC1030
Mixed Bag of Knobs (New) £1.00 2N6254
Mixed Bag Components New R.C. 2N3055
Transistors £2.00
Mixed Bag Transistors Approx. 50 Pieces 3K5 LTB Under Panel
Marked (New) £2.00
Full Spec £1.80 Add £1.50 P&P
Portable T/V Ring Special Offer 3K5
Aerials 50p Convergence Panels.
Tube Regunning Plant. SAE for details Blank & New £1.50 each
T/V Crystals 4433-691 50p Or 2 for £2.00

SEMI-CONDUCTORS

BU5005 £2.00 BTT8024 £1.50
BU208 £1.00 TOBF900 £1.50
BDX32 £2.00 TECP100 £3.30
R2210 60p TDA1327A £2.50
R009 £1.30 TD3F800 £1.50
R008B £1.50 TCA640 80p
R2029 80p TBA1205 £1.00
R2781 80p TBA395 £1.00
T9038 £1.00 TBA650 £1.50
T9013V £1.50 BTM8018 £1.25
2.5B425 £2.00 TM54034NL £1.25
2SC1030 £1.50 HBF4021AE £2.00
2N6254 80p MC1358P £1.00
2N3055 50p ML237B £1.80
3K5 LTB Under Panel (New) £2.00 BRC300 £1.00
Add £1.50 P&P CA270AE £1.00
Special Offer 3K5 ULN216D £1.00
Convergence Panels. SN76228N £1.80
Blank & New £1.50 each SN7417N £1.30
Or 2 for £2.00

IC'S 12 PIN

60p P&P Unless Otherwise Specified

ADD 15% VAT TO TOTAL, CHEQUE OR POSTAL ORDERS MADE PAYABLE TO:
TANONTON ELECTRONICS SUPPLIES LIMITED

PATTERN GENERATOR PROGRAM for Spectrum 16/48K. Colour bars, crosshatch, dots, chequer board, red, green, blue, black, white rasters. Send £3.50 for tape to: GW TVs, 1 Eachard Road, Cambridge CB3 0HZ.

VIDEO RECORDERS, Philips V2000 system. Working. £120.00. RETACH LTD. 01-845 2036 or Northwood (09274) 27019.

SATELLITE RECEPTION: 4 low noise 12 GHz Ga. As Fets type CFX13. £80. Tel: 0628 23641.

JAPANESE CTV CIRCUIT SHEETS 79 models from 11 brands. Send name and address to: ABDULLAH JUSOH, 1235, L/14, KG, Besut, Kemaman, Trengganu, Malaysia.

RADIO AND TELEVISION SERVICING 1972 to 1976. Very good condition. £12 each, £40 set. Telephone Polegate, Sussex 3667.

LABGEAR COLOURBAR GENERATORS £55.00 post paid. J. CAHILL, Beacon Television, 335A Cotmanhay Road, Ilkeston, Derbyshire.

TOP QUALITY TELEVISIONS SCOTTISH TRADERS

★ Wide range of CTV's in good working order from £25. E.g. Thorn 3500, 8500, 8800, Bush, Philips G8, GEC S/S CTV etc.

★ Plenty of working and complete non-working sets at competitive prices.

★ Ready sell or to rent.

For further particulars telephone:

SABA CO. LTD.
72 Robertson Street,
Glasgow.
Telephone: (041) 221-2146.

BEST VALUE IN SECONDHAND TV'S SETS CLEANED AND SOAK TESTED

MAKES
Philips G8, 5, 2 chip Bush/Murphy
Thorn 3000, 3500
Thorn 8800, 9000, 9600, touch tune sets etc.
Bush 720's, Philips G11, ITT CVC 35
Pye 18", 22"
GEC Solid State, all types
Japanese, Hitachi, National Panasonic
ITT CVC 5/8/9
Decca Broadford
GEC/Pye Hybrid

DISCOUNT FOR VAN LOAD DIRECT FROM SOURCES

| COMPLETE NON-WORKERS | WORKING |
|----------------------|---------|
| £14 | £25 |
| £13 | £22 |
| £25 | £40 |
| £50 | £70 |
| £16 | £26 |
| £16 | £28 |
| £15 | £28 |
| £14 | £28 |
| £10 | £20 |
| £5 | £10 |

Mono in batches of 20 at £200
SPECIAL OFFER!
Philips G8,5 26" £5
Thorn 3500 26" £5
Pye 205 26" £4

Other makes available on request. Discount for quantity.

★ Tubes tested all sizes at £8.00 each

★ Good quality stands at £2.00 each

| T.V. PANELS MAKES | T.V. PANELS | | | | T.V. PANELS | | | | T.V. PANELS | | | | | | |
|----------------------|-------------|------|------|-----|-------------|------|-------|------|-------------|------|---------|------|----|------|---------|
| | POWER | | LINE | | TIBASE | | VIDEO | | DECODER | | CONVERG | | IF | | TRIPLER |
| | W | N/W | W | N/W | W | N/W | W | N/W | W | N/W | W | N/W | W | N/W | WORKING |
| Thorn 3500 | 6 | 3 | 6 | 3 | 4 | 1.50 | 4 | 1.50 | 3 | 1.50 | 4 | 1.50 | 4 | 1.50 | 2.50 |
| Philips G8 | 6 | 2.50 | 12 | 6 | 6 | 3 | | | 6 | 3 | 6 | 4 | 4 | 2 | 2.50 |
| Pye S/S | 8 | 6 | 15 | 10 | 5 | 3 | | | 10 | 5 | 6 | 3 | 10 | 5 | 3.00 |
| GEC S/S | 6 | 4 | 11 | 8 | 5 | 3 | 5 | 3 | 5 | 3 | 4 | 3 | 10 | 8 | 3.00 |
| Decca (H) | 6 | 3 | | | 6 | 3 | | | 8 | 4 | 4 | 2 | 3 | 1 | 2.50 |
| Pye (H) | 8 | 4 | 8 | 4 | 4 | 2 | | | 6 | 3 | 4 | 2 | 3 | 1.50 | 2.50 |
| GEC (H) | 6 | 3 | | | 6 | 3 | | | 6 | 3 | 4 | 2 | 3 | 1 | 2.50 |

★ W - Working fully tested panel ★ Express delivery, subject to availability

★ N/W - Non-working panel ★ Add 15% VAT P&P 1 panel 1.50, 2 panels 2.00, 3 panels 2.50 etc.

ELASTIC
YARN

SABA CO LTD., Unit A, Derby Road, Sandiacre, Nottingham. Tel: (0602) 397555.

| All diodes at 10p or less in this list 20 of one type £1.00 | | Min 12 volt Relays 75p | ZTX 384 10p ZTX 451 10p ZTX 550 10p MJ 2253 60p MJE 3040 60p MJE 2209 10p SP 8385 50p | PHILIPS DIY HOME SECURITY ALARMS KITS Send for details. Prices £54 to £112. | | |
|---|--|------------------------|--|--|---|--|
| OA 47 8p OA 90 8p | Y 716 10p Y 729 30p Y 730 10p Y 827: 6A/1KV 20p Y 860 30p Y 933 5p Y 969 5p Y 997 30p | | Voltage Regulators +5V/LA78P05SC 30p -5V/LM79M05CP 25p -8V/79M08c 30p +6V/78M06c 30p +10v/78LA10 20p LM 337 30p LM 342/18 30p LM 340T 5.0 50p +12V/LM 340T12 50p +15V/78M15 15p +18V/MC78M18 20p +24V/78M24 30p MC 7724cp 40p MC 7824 40p TIS 90 10p TIS 91 20p TIS 92 20p TIS 93 20p | 10 Mixed TV & radio speakers £5 + £2 post | Philips GP422.4CH (£40 cost) £6 Stereo Dynamic Cartridge | 20AX GEC Split Diode lead £1.00 |
| IN 60 5p IN 541 5p IN 914 5p IN 2069a 10p IN 2070 10p IN 4001 3p IN 4002 3p IN 4003 4p IN 4004 4p IN 4005 4p IN 4006 4p IN 4007 5p IN 4148x40 10p IN 4448x40 10p IN 4722 10p IN 4751 10p IN 5235 10p IN 5254 10p IN 5349 10p IN 5392 10p IN 5928B 10p | R 1038 40p R 1039 40p R 2009 80p R 2010b 10p R 2029 50p R 2210 60p R 2257 60p R 2265 50p R 2305 50p R 2306 50p R 2322/2323 pair 80p R 2323 15p R 2326 50p R 2461 80p R 2030 50p R 2443=BD124 40p R2737 40p R2738=TIP41 30p R2775=TIP41c 40p R3129=TIP47 40p S 2008b 80p | | CB Radio transistor 16119 2A/40v.50Meg 5 for £1. | 8Ω 4" speakers £1 4700/10v x 10 50p 68/16 x 10 50p 150/16 x 10 50p 47/25 x 10 50p 220/25 x 10 50p 1/250 x 10 50p 8000/30v 50p 470/40v x 10 £1 22/100v x 10 £1 100/350v 70p 400/350v 70p 47/500v 25p 1/600v 25p .022/1kV 10p | 12 Volt Aerial Changer over Relays £1 | GEC Dynamic 20AX Convergence C2233H-R223GH £2.00 |
| IAV 30 10p | | | | 12 Volt Lorin Full Remote Relay Switch | Mullard Broadband R.F. power modules | |
| IM 72Z55 10p | | | | Mains timer. 13 amp — up to 2 hours: easy to use, plugs into socket | VHF. BGY33 £15 UHF. BGY22E £5 PT4236C £5 PT9783 | |
| IR 106a 20p IR 3051 10p | | | | Sellotape PVC Electric Insulation 25mm x 20M 50p | | |
| IS 164 10p IS 921 10p IS 3011a 10p IS 3072a 10p IS 5024a 50p IS 5030 50p | BU 105/04 80p BU 108 £1 BU 124 50p BU 126 80p BU 180a 65p BU 204 70p BU 205 £1 BU 206 £1 BU 207 £1 BU 208 80p BU 208 on heat sink 70p BU 208A £1.10 BU 208D 90p BU 222 £1 BU 326 £1 BU 407 60p BU 426V 60p BU 500 £1.10 BU 508A £1.20 BU 526 75p BU 807 £1 BUX 84 50p BUY 84 30p BUY 71 £1 | | | ITT CVC £8.25 50mm x 20M Chassis £40.00 | | |
| ITT 921 10p ITT 923 10p ITT 1075 10p ITT 2001 10p ITT 2002 10p ITT 4150 10p | | | | SPECIAL OFFERS UNTIL OCTOBER | | |
| ZE 1.5 10p | | | | 10 x G11 Cap 470/250 £15.00 | | |
| ZF 3, 3.3, 4.3, 10, 11, 12, 15, 33, 43, 47, 82 10p | | | | Soldering iron 6v/23w £2.50 | | |
| ZPD 3.9, 4.7, 5.6, 10, 47 10p | | | | Weller solder iron 15 watt/25 watt £5.00 | | |
| ZPY 8v2, 12, 16, 24, 43, 47, 56 10p | | | | 2 way baby alarm/intercom with long leads £5 | | |
| ZTK 22 10p ZTK 33 10p ZTK 33a 10p | TIC 106a 30p TIC 116m 40p TIC 116n/Y 1003 35p TIC 126N 40p TIC 206m 30p TIC 225S 40p TIC 226E 40p TIC 226m 30p TIC 236m 30p TICV 106D (T092 case 2A/400V) 10p TIP 29 20p TIP 30 35p TIP 30A 35p TIP 30B 40p TIP 30C 45p TIP 31 30p TIP 32 25p TIP 33B 50p TIP 33C 70p TIP 34A 50p TIP 34B 60p TIP 34C 70p TIP 35B 50p TIP 35C 70p TIP 35D 80p TIP 36 50p TIP 36C 70p TIP 41B 40p TIP 41D 70p TIP 42/BRC 6109 30p TIP 48 40p TIP 49 30p TIP 57 30p TIP 100 30p TIP 102 30p TIP 112 30p TIP 115 50p TIP 117 50p TIP 120 35p TIP 125 35p TIP 130 30p TIP 131 25p TIP 136 30p TIP 140 50p TIP 147 50p TIP 640 50p TIP 2955 30p T 6032 35p T 6036 40p T 6040 40p T 6047 40p T 6049 40p T 6051 40p T 6052 40p T 9004 40p | | | | Philips Neon Lamps for TV sets £1.00 | |
| ZW 13 12p ZW 27 10p ZW 4.3 10p ZW 310 10p | | | | Freeze £1.00 | | |
| ZX 68 30p | | | | Foam Cleaner £1.00 | | |
| ZY 47 10p ZY 72 10p | | | | Contact Cleaner £1.00 | | |
| AA 113 10p AA 119 8p AA 144 10p | | | | 12 Volt Lorin Full Remote Relay Switch £1.00 | | |
| BA 102c 10p BA 157 8p BA 159 8p BA 173 8p BA 182 8p BA 201 8p BA 202 8p BA 243 8p BA 248 8p BA 316 8p BA 318 5p | | | | Sellotape PVC Electric Insulation 25mm x 20M 50p | | |
| BAV 10 10p BAV 21 10p | | | | ITT CVC £8.25 50mm x 20M Chassis £40.00 | | |
| BAW 21 10p | | | | SPECIAL OFFERS UNTIL OCTOBER | | |
| BB 103 10p BB 105A x12 £1 BB 105B x12 £1 BB 105G x12 £1 BB 121a 10p | | | | 10 x G11 Cap 470/250 £15.00 | | |
| BRC 83c13 10p | | | | Soldering iron 6v/23w £2.50 | | |
| BZX 46c22 15p BZX 61 9-1 6p BZX 61c110 6p BZX 61c20 10p BZX 61c30 10p BZX 61c220 10p BZX 70c6v 8p BZX 70c12 20p BZX 70c33 8p BZX 79c3v9, 4v7, 5v1, 5v6, 6v2, 6v8, 7v5, 11, 12, 30, 47 10p each BZX 83c4v3, 5v6, 8v2, 12, 13, 24, 27, 33 10p each BZX 84c6v8 x10 30p BZX 85c8v2 10p BZX 88c0v7, 3v9, 4v3, 6v2, 8v2, 12 10p each | | | | Weller solder iron 15 watt/25 watt £5.00 | | |
| 1A/1600V 10p | | | | 2 way baby alarm/intercom with long leads £5 | | |
| CV 8617 10p | | | | Philips universal battery tester/charger, fuse/bulb tester To Clear £4 | | |
| | | | | Eisenmann NICAD CHARGER 5.5V/150 ma £2 | | |
| | | | | 12V Nicad pack. "AA" £2.50 | | |
| | | | | Hitachi 7.2v/1.8A Nicad pack £6.00 | | |
| | | | | Hitachi TP 007 Battery pack 7.2v/1.6A £7 | | |
| | | | | Hitachi Silver Oxide Battery G13 UCC357 IEC SR44 1.5V 60p | | |
| | | | | 70ML Silicone Sealer (clear) £1 | | |
| | | | | 100 Coax Plugs £10.00 | | |
| | | | | De-solder pump + 2 nozzels £5.20 | | |
| | | | | Plastic box for i.c.s with anti-static pad 6" x 3" x 1/4" 75p | | |
| | | | | Can of handy oil 'mobil' 40p | | |
| | | | | Flat Red LED 12p | | |
| | | | | 500gm 60/40 solder reel £7 | | |
| | | | | Clearweld glue pack 30p | | |
| | | | | Dual v/u meter -20 - +10db £1 | | |
| | | | | 3 x C90 Cassettes 70p | | |
| | | | | K30 thermistor 232266298009 75p | | |
| | | | | 75R/25 Watt 25p 18R/11 Watt 25p 120R/17 Watt 20p Front End Music Center. VHF/MW/LW 13"x3 1/2" £3 Output Stage for music center £5 | | |
| | | | | SONY 1400KV Chroma Panel £6 SONY 1400KV Tuner unit £3.50 SONY 1400KV Touch button unit £3.50 | | |
| | | | | Texas Viewdata Decoder VDP 12/80 Issue 3 with all IC's £10.00 | | |
| | | | | Quantity Reductions BY204/4 25 for £1.00 BY206 25 for £1.00 W005 bridge 20 for £2 G11 touch button red 6 for £1 BY298 3 amp/fast/R 20 for £1.50 BD239 20 for £2.00 MR856 25 for £1.50 BU126 10 for £6.00 BU205 10 for £6.00 BU105 10 for £6.00 2SC2122A 10 for £8.00 BF458 10 for £1.00 BD136 10 for £1.25 BF224 20 for £1.40 OA90 40 for £1.00 BYX10 100 for £4.00 KT3 multicaps 10 for £7.50 50 Ceramic Condensers £1.50 Mixed Mounting Kit for Power Transistors 50p 300 Condensers £1.50 300 Resistors £1.50 150 Electrolytics £2.00 15 Bulbs 40p Antistatic Discloth 5 for £1 100 Diodes £1.50 | | |
| | | | | 100 Fuses £2.00 100 W/W Res. £1.50 BF 199 20 for £1 10 x 20 Turn 100k pots. Rank £2 Thorn 9 volt power supply regulated £3.00 BF 470 20 for £2 20 Slider Knobs 70p 6 Mixed UHF Aerial Isolating Sockets, some with long leads. Fit ITT, GEC, Philips, Pye £1.00 | | |
| | | | | Mixed Packs TO66 12 Power Trans RCA 16182 NPN Replacement for BD124 and Mounting Kits £1.00 50 Mixed AC series Transistor £4.50 15 Panel mount rocker switch 250V/10A £1.50 25 Panel Mount Bulbs & Neons £1.50 10A £1.50 Mixed ribbon cables £1.00 25 LED red/yellow/green £1.20 20/C Holders £1.50 20 Large LED Red £1.00 20 Small LED Red £1.00 10x20 Turn 100K Pots £1.00 100 Transistor £2.50 20 Convergence Pots 80p 100 Sticks £1.00 10 Thermistors 50p 20 Slider Pots £1.00 30 Presets 50p 15 VDR + thermistors, degaussing, HT, etc. £1.00 40 glass reed switch £1 10 press to make switch 70p 40 Pots £1.50 10 Gun Switches 50p 5 Tube Bases £1.00 1,000 Diodes, Condensers, Resistors on Bandler £2.00 Lucky Dip 600 gram £1.00 Jungle Bag 5Kg £3.00 20 Knobs £1.00 40 Pots, 1" + 6mm spindles for audio/TV £3 20mm Fuse Holders £1.00 Chassis Mount 20 for £1 IN4001/6 100 mixed £2.50 EHT Diodes, small 20 for £1 | | |
| | | | | SPECIAL OFFER Decca-ITT etc. FEO4/1/250AC/4 Mains filters (grey type) x 4 £1 | | |
| | | | | BRIDGES SKB 2/08 L5A 30p KBL 005 30p KBL 02 30p KBP 04 30p W02 15p W004 15p W005 20p GEC remote panel. Main transformer 3/1c SAA 1025/5N 74141/TBA 231 £6 AT 2076/35 £7 AT 2076/55 GEC split diode transformer £10 AT 2048/11 LOPTI Mullard £2.50 | | |

SENDZ COMPONENTS

TO ORDER SEE BACK PAGE

| | | | |
|---|--------|--------------------------------------|-----|
| Thorn Spares | | BY 227 | 15p |
| 9000 Frame panel | £8 | BY 228 | 20p |
| 9000 Cyclops panel | £1.50 | BY 229/400 | 30p |
| 8000/8500 timebase panel | £8 | BY 237 | 5p |
| 8000/8500/9000 chroma panel | £15 | BY 238 | 5p |
| 8800 convergence panel | £6 | BY 254 | 10p |
| 8500 convergence panel | £6 | BY 255 | 30p |
| 4000 Frame panel | £5 | BY 298 | 10p |
| 4000 Chroma | £3 | BY 299 | 10p |
| 4000 Power supply | £20 | BY 406 | 10p |
| 1600 Mains lead, switch | £1 | BY 527 | 20p |
| 3500 6 push button + cable form | £1.50 | BY 407A | 10p |
| T605 1vNPN T066 80v/6A | 10p | BY 602 | 10p |
| 9000 Sound output panel | £1 | F 247 | 10p |
| 3500 Focus unit | £1.50 | XK 3102 | 50p |
| 3500 Mains Trans | £4 | XK 3123 | 50p |
| 3500 2amp thermal cutout | 75p | Hitachi 2A/1500V metal case wire end | 20p |
| 3500 IF panel | £2 | | |
| 3500 Frame panel | £2 | | |
| 3500 Line panel | £3 | | |
| 3500 A1 Diode | 20p | | |
| Export 3500 IF panel | £2 | | |
| IC board with set of SN74LS | £1 | | |
| 4000 Tube base | £4 | | |
| 3500 A1 pots | 50p | | |
| Beam limiter panel | £1.50 | | |
| 3500 Power panel with Y969 | £1 | | |
| 3 Way regulated adaptor 240V 6V/7.5V/9V/300mA | £3.50 | | |
| Rank/Toshiba preh unit 0354 | £9.50 | | |
| 2 banks of 3 PB unit. Pye 731 | £2 | | |
| 4 Push button unit preh | £1.00 | | |
| 6 Push button VHF/UHF for v.cap. GEC-Decca type | £7.00 | | |
| 7 Push button for CVCs ITT | £8.00 | | |
| KT3 12 Push button unit | £2.00 | | |
| KT3 (Export) 12 P.B.u | £2 | | |
| 6 Push button Unit Thorn | £1.00 | | |
| 6 Push button unit for GEC 2040 and ELC 1043/05 | £6.00 | | |
| Hearing aid unit | £3 | | |
| 6 Push button unit PYE 713 | £7.00 | | |
| 7 Lamps for P.B./Unit | 10p | | |
| Mains Droppers | | | |
| Pye 731 3+56+27R | 50p | | |
| Pye 3R5/15R/45R | 50p | | |
| Thorn 50/17/1K5 | £1.00 | | |
| 120/20/20/48/117 | £1.00 | | |
| 270/10/6 for Thorn 4000 | 50p | | |
| 18/320/70/39 | £1.10 | | |
| Thorn 50-40R-1K5 | 50p | | |
| Ae Socket & Lead | | | |
| GEC, ITT, Philips, Pye | 25p | | |
| 7x3/4 Thorn | £1 | | |
| Rank Toshiba Tube Bases | 30p | | |
| Speakers | | | |
| 6x4 G11 | 25 ohm | 70p | |
| 5x2x2 | 3 ohm | £1.00 | |
| 5x3 | 80 ohm | 70p | |
| 5x3 | 50 ohm | 50p | |
| 5x3 | 35 ohm | 70p | |
| 6x4 | 15 ohm | £1.00 | |
| 7x3 | 70 ohm | £1.00 | |
| 5x3 | 8 ohm | 70p | |
| 7x3 | 16 ohm | £1.00 | |
| 5" dia | 16 ohm | £1.00 | |
| 5" dia | 8 ohm | £1.50 | |
| 6 1/2" dia | 4 ohm | £1.50 | |
| 6 1/2" dia | 3 ohm | £1.50 | |
| 2 1/2" dia | 8 ohm | 75p | |
| 3" dia | 8 ohm | 75p | |
| 4 1/2" sq. | 15 ohm | 75p | |
| KT3 speaker | | 75p | |
| 3" dia | 15 ohm | 60p | |
| K30 | | | |
| OF-550 | 10p | | |
| OF-513 | 10p | | |
| Diodes | | | |
| BY 127 | 10p | | |
| BY 133 | 10p | | |
| BY 134 | 10p | | |
| BY 164 | 50p | | |
| BY 176 | 25p | | |
| BY 179 | 40p | | |
| BY 184 | 25p | | |
| BY 187 | 10p | | |
| BY 190 | 40p | | |
| BY 196 | 30p | | |
| BY 198 | 10p | | |
| BY 204/4 | 8p | | |
| BY 206 | 8p | | |
| BY 208/800 | 8p | | |
| BY 210/400 | 5p | | |
| BY 210/800 | 10p | | |
| BY 223 | 60p | | |
| BY 224/600: 4.8A/600v bridge | 50p | | |
| BY 226 | 15p | | |
| International Rectifier EHT Diodes | | | |
| 6A/600V Stud Diodes | 20p | | |
| 6A/1000V Stud Diodes | 20p | | |

| | | |
|--|--|----------------|
| NEW GEC 20AX Power Supply Switch Mode | | £12.00 |
| Complete new GEC portable chassis M1201H/M1501H with P.B.U./v.cap/LOPTI | | £10 |
| Field + Jungle panel for GEC 3133/3135 | | £1.50 |
| GEC 2110 line panel with transformer | | £7.00 |
| GEC 2110 tuner unit + IF Panel | | £12.00 |
| Pye/Chelsea Line on panel | | £12.00 |
| Pye 713 IF panel and tuner | | £7.00 |
| Pye 713 Chroma | | £10.00 |
| Pye/Chelsea Timebase panel with LOPTI | | £10.00 |
| Pye 731 Frame Panel | | £5.00 |
| Pye 731 Convergence Panel | | £5.00 |
| Pye 731 line O/P panel with transformer + tripler | | £12.00 |
| Pye 731 Chroma | | £10.00 |
| Pye 731 IF panel + tuner | | £10.00 |
| Pye 607/205 Line panel with transformer | | £10.00 |
| Pye CDA/205 panel | | £6.00 |
| GEC portable chassis + LOPTI 2114 New | | £4.00 |
| Thorn 1613/1713 chassis | | 9.75 |
| Hills 520 multimeter + case. 20,000Ω/volt, fuse diode protected + logic test facility. 10meg/1200 volt | | £19.50 |
| NEW MULLARD TELETEX | | £15.00 |
| Decoder Panel (VM6230) | | £15.00 |
| Panel 6101 | | £15.00 |
| Panel 6330 | | £15.00 |
| G8 Tuner Unit + Panel | | £6.00 |
| G8 Convergence Panel (late type) | | £12.00 |
| G8 Line O/P Panel | | £12.00 |
| G8 Power Supply | | £6.00 |
| G8 6 Sloping PBU | | £8.00 |
| G8 IF & Chroma | | £12.00 |
| G8 Chroma | | £6.00 |
| G11 IF Detector | | £3.00 |
| G11 Selector gain module | | £3 |
| Complete CVC 825 Chassis (both panels) | | £40.00 |
| AEC V/Cap Resistor Unit UHF with IC SAS660 SAS670 | | £3.00 |
| 2714 RANK IF Panels 6MHz 1 | | £3.00 |
| I.C. SL437F | | £3.00 |
| Z909B RANK IF Panels | | £2.50 |
| Export 5.5MHz 2 I.C.'s | | |
| TBA1205B TCA2705Q | | |
| Z743 RANK IF Panel | | |
| Export 5.5MHz 3 I.C.'s | | |
| TBA750+SC9504P+SC9503P | | £1.50 |
| Pye G11 Front panel with transducer, pots, tuner pots, 6 pb switch+lead | | £5.00 |
| GEC V/cap VHF/UHF tuner and IF+ sound O/P PC 706B3 | | £12.00 |
| Export GEC Line O/P PC 659B3 | | £6.00 |
| GEC Power Supply (Export) | | £10.00 |
| G11 dynamic correction panel | | £6 |
| CVC 20 Front panel with sliders + mains input panel | | £4 |
| CVC 40 PUSH BUTTON ASSY with sliders: complete with lamp assy + pots | | £14 |
| CVC 5 Mains on/off + 5 pots | | £2 |
| Universal Focus. Fits Pye, Thorn and Decca Units. | | |
| Large Type | | 75p |
| Decca Small | | 75p |
| KT3 Focus Unit | | 75p |
| K30 Focus Pot | | 40p |
| CVC 32 Focus Unit | | 10/375 |
| Focus Rod | | 25p |
| G11 focus | | £2.00 |
| ITT Small for use with Split Diode | | 50p |
| TV 11 | | 50p |
| Remo TV12SP | | 50p |
| TV13 | | 50p |
| TV14 | | 50p |
| TV18 | | 60p |
| TV20 | | £1.00 |
| TV45 | | 50p |
| Thorn 14/1500 rec stick | | 5p |
| 16 Button Key Pad 1 to 0 + * | | |
| # + 4 blank (Cherry) | | £3.00 |
| Condensers | | |
| 470/16 | | 6p |
| 1500/16 | | 20p |
| 3300/16 | | 20p |
| 10000/16 | | 25p |
| 15000/16 | | 50p |
| 3300/18 | | 20p |
| 47/25 | | 5p |
| 470/25 | | 5p |
| 680/25 | | 5p |
| 1000/25 Radial | | 10p |
| 1500/25 | | 10p |
| 3300/25 | | 10p |
| 4700/25 | | 25p |
| 5000/25 | | 25p |
| 3500/30 | | 25p |
| 470/35 | | 6p |
| 2200/35 | | 25p |
| 100/40 | | 5p |
| 220/40 | | 5p |
| 400/40 | | 20p |
| 1250/40 | | 20p |
| 1500/40 | | 20p |
| 2500/40 | | 20p |
| 1000/50 | | 20p |
| 1250/50 | | 25p |
| 2000/50 | | 25p |
| 3000/50 | | 25p |
| 3300/50 | | 25p |
| Infra Red and Ultrasonic G11 Teletext Decoder Panel | | £30 |
| RANK & ITT Mains Remote On-Off Switch (720R) | | £1.50 |
| RANK & ITT Mains Remote Switch 2865 ohm | | £1.50 |
| RANK & ITT Remote Switch 2800 ohm | | £1.50 |
| G11 Mains Switch | | 25p |
| 4 amp Mains Switch | | 30p |
| GEC Mains Switch 4 amp | | 30p |
| KT3 Mains Switch | | £1.00 |
| THORN Rotary Mains Switch | | 50p |
| G8 Mains Switch | | 75p |
| Thyristor 600/4 amp C106/2 | | 24p |
| G11 Preh Red LED P/Button for C.H. Change | | 20p |
| RANK TOSHIBA Transducers TPC-2011 | | 50p |
| CVC 5 Mains on/off +250K+100K+500K+500K Pot on Panel | | £2.00 |
| Thorn 12 or 24 volt battery converter for portable colour TV. | | £12.00 Post £1 |

| | | |
|---|------------|----------|
| 0.0082/2500 | 15p | |
| 150/3500 | 10p | |
| 1800/4KV | 5p | |
| 4.7nF/5KV | 10p | |
| 170/8KV | 10p | |
| 180/8KV | 10p | |
| 210/8KV | 10p | |
| 1000/10KV | 10p | |
| 210/12KV | 10p | |
| 1000/12KV | 10p | |
| 1200/12KV | 10p | |
| Mult-Caps | | |
| 470/250 G11 | 10 for £15 | |
| Thorn 3500 | | |
| 175/100/100/350v | £1.75 | |
| KT3/200/25/25/385v | £1.00 | |
| 300+300+150+100+50MFD | | |
| 350V | £2 | |
| 47/220/350v | 60p | |
| 150/150/100/100/100/320v | £2.00 | |
| 2500/2500/63v | 50p | |
| 470/470/250v | 50p | |
| 150/200/200/300v | 70p | |
| 400/400/200v | £1.70 | |
| 300/100/100/16/275v | £1.50 | |
| 100/200/325v | 40p | |
| 150/150/100/375v | £1.50 | |
| 300/300/100/32/32/300v | 2.00 | |
| 1500/2000/30v | 50p | |
| Jelly pot Thorn 00D4/013 | £3 | |
| 630/150/100/100/320v | £2.00 | |
| 2 digit LED 8.8 | 50p | |
| 2 digit LED +1.8 with panel + MCT4511 | £1.00 | |
| 4700/63 | £1.50 | |
| 250/64 | 10p | |
| 3300/70 | 50p | |
| 1/100 | 5p | |
| 1/100 x 10 | 30p | |
| 22/100 | 10p | |
| 4.7M/100 | 5p | |
| 470/100 | 70p | |
| 2000/100 | 75p | |
| 4700/100 | 70p | |
| 47/160 | 10p | |
| 800/160 | 50p | |
| 1/250 Pulse | 5p | |
| G11 0.47/250 | 10p | |
| 2.2 250v | 10p | |
| 33/250 A.C. | 10p | |
| 33/250V | 10p | |
| 39/250V | 15p | |
| 4n7/250 tested 5KV | 25p | |
| .91/250 | 35p | |
| .91/400 | 30p | |
| 22/250 | 15p | |
| 47/250 | 10p | |
| GEC Line O/P PC 659B3 | £1.75 | |
| G11 470/250V | £1.75 | |
| GEC600/250 | 60p | |
| 700/250 | 60p | |
| 800/250 | 60p | |
| CMD 40 | £5.00 | |
| CMD 40 | £5.00 | |
| CMD 41 | £5.00 | |
| CMF 25 | £2.00 | |
| CMF 26 | £2.00 | |
| CMF 40 | £2.00 | |
| CMH 10 | £1.50 | |
| CMH 31 | £1.00 | |
| CMK 12 (untested) | £4.00 | |
| CMK 30 (untested) | £4.00 | |
| CMN 20 | £1.50 | |
| CMN 21 | £1.50 | |
| CMN 40 | £1.00 | |
| CMN 45 | 25p | |
| CMP 10 | £2.00 | |
| CMP 11 | £4.00 | |
| CMP 40 | £2.00 | |
| CMS 11 | £2.00 | |
| CMS 40 | £2.00 | |
| CMU 12 | £10.00 | |
| CMU 14 | £8.00 | |
| CMU 30 | £7.00 | |
| CMU 45 | £7.00 | |
| CMZ 30 | £5.00 | |
| GMA 90 | £5.00 | |
| GMC 120 | £2.50 | |
| GMR 64 | £5.00 | |
| TMN 2 | £10.00 | |
| VCA 20 | £10 | |
| VCA 21 | £10.00 | |
| VMC 26 | £3.00 | |
| VMC 34 | £5.00 | |
| VMC 44 + 45 | £4.00 | |
| VMC 51 | £5.00 | |
| Hand Sets | | |
| Transducer Hand Set Insert, crystal, transducer, SAA 1124 & lead | | £3.50 |
| 8 C.H. Ultrasonic GEC Full Remote C2014H/C2219H | | £15.00 |
| New Replacement for G11 Ultrasonic Full Remote | | £15.00 |
| Thorn 4000 insert with 7 buttons | | £5.00 |
| Decca RC 11 | | £14.00 |
| Decca RC 12 | | £14.00 |
| G11 Infra-red full teletext | | £19.00 |
| C11 Ultrasonic full teletext for G26c | | £19.00 |
| 674/02 and G22c | | £16.00 |
| 66/02 | | £16.00 |
| Philips, 2 button | | £8.00 |
| Rank, Infra-red | | £10.00 |
| Dynatron-Full remote CTV 62, 63, 64 | | £19.00 |
| Hitachi infra red handset | | £18 |
| Philips full remote KT3, 16C928/20C934; 7228/7324; K12 26C 797/15T 66K 1826 | | £12.00 |
| G11, Full remote top button assy. | | £12.00 |
| G11, Full remote repair service (exchange unit) | | £12.00 |
| Philips infra red full remote 9 channel for 60 CP2605 | | £6.00 |
| Philips infra red full remote 12 channel for 60 CP2605 | | £12.00 |
| KT3-30 Push Button Kit | | £3.00 |
| KT3/K30 T/Text | | £15.00 |
| KT3/K30 Full remote | | £15.00 |
| KT3 Power supply | | £4.00 |
| Hitachi 8 button unit with resistor unit. Last year mod. | | £7.00 |
| GEC infra-red 2236-2026 | | £4.00 |
| GEC push pad hand set button blobs | | 10p each |

SENDZ COMPONENTS

63 Bishopsteignton,
Shoeburyness, ESSEX SS3 8AF
SAME DAY SERVICE

All items subject to availability.
No Accounts - No Credit Cards
Postal Order/Cheque with order
Add 15% VAT, then £1 Postage
Add Postage for overseas

Callers: To shop at 212 London Rd.,
Southend. Tel. 0702-332992

Open 9-1/2.30-6. G.V.M.T + school orders accepted on official
headings add 10% handling charge.

| | | | | | | | | | | | | | | | | | | | |
|---|--|---|--|---|--|--|--|--|--|---|--|--|--|--|--|---|--|---|--|
| Tuner Units GEC or Hitachi 6 push button unit 2110 Conversion £12 GEC 2110 V/Cap £6 ELC 1043/06 (AEG) £6 ELC1043/05 Mullard £6.00 ELC1043 (Ex Panel) £3.75 ELC1042 .. £5.00 ELC2000 .. £7.00 ELC2004 £10.00 ELC2006 £10.00 GEC Tuner V/Cap Hitachi After 1979 ET548, ET547 £10.00 U322 (UHF) .. £4.00 V314 (VHF) .. £5.00 U321 .. £6 U341 UHF £7.00 U411 UHF £7.00 U.V. 411 Tuner £10.00 ELC1043/05 Thorn £5.90 Small V/Cap Mitsumi £4.00 UHF .. £3.00 VHF .. £3.00 G8 Tuner £6.00 Portable & rotary Tuners Sanyo & Mitsumi UHF £5.00 6003 Bush V/Cap Tuner £10.00 NSF-UHF/VHF Varicap (old type) £8.00 Mosfit UHF/VHF (new type) £8.00 SONY 1400KV Tuner unit £3.50 Thorn Tuner PANEL with 6x100K pots + cursors NO TUNER £1.00 U321 on panel £6.00 Tuner unit VHS Sylvania GTR Videon MTS 900 £2.50 Mullard Video Modulator. Application, video tape recorders, TV cameras, video games, closed circuit T.V., C.C.I.R. system. Data supplied. £10.00 VT 100 Sound Tuner Kit. TV. Viosound. The latest design in low noise fitted with DNR, RF output and audio £30.00 Sylvania UHF VHF F6013 (Fits Rank) £6.00 Sylvania F6003 £6.00 Sylvania UHF F4720B £6.00 Sylvania VHF 900 £6.00 Decca Bradford Tuner 5 Button £4.00 Small Tuner DX 175-220MHz. Auto Changeover £5.00 9000 Thorn Tuner on Panel £7.00 D.P.D.T. switch Black knob. Chassis or PCB mount 4p each or 40 for £1.00. | | THORN 1400 4P.B. Mech. Tuner 15p THORN 1500 4P.B. Mech. Tuner 7p THORN 1590 4P.B. Mech. Tuner 15p THORN 3500 4P.B. Mech. Tuner 15p THORN 8000 4P.B. Mech. Tuner 10p THORN 8500 Mech. Tuner 10p £4.00 each | | Delay Lines DL120A 80p DL600 £1.00 G8 (Old Type) £1 DL700 £1.00 UDL11 30p KT 3 Luminance 75p Luminance Delay Line (CVC 45) 25p 10x630ma fuse 50p 10x2A fuse 25p 10x3.15 fuse 50p 10x500mA 80p 10x1 amp 80p 10x1.6 amp 80p 20 3.15 AS Fuses £1.70 Co-Ax Joint 15p Co-Ax Belling Lee Plug 12p Co-Ax Splitter £1.00 UHF Modulator CCIR £3.00 Infra Red Emitting Diode 20p NE286H Small Neon Lamps GEC & Philips 5p Mullard 5 Watt Amps. LP1162 New 75p | | T.V. Tubes 12" A31/300 Hitachi £10 15" A38/170W Hitachi £8 18" Hitachi P.I.L. tube with scan coils 470 KCB22-TC03 £25 | | Integrated Circuits AC76003 £1.50 AM25LS23PC 10p BAV40 40p | | SAA1272 £3.00 SAA1276 £3.00 SAA5000 £1.50 SAA5000A £1.50 SAA5012A £5.00 SAA5020 £3.50 SAA5030 £5.00 SAA5040 £3.50 SAA5040A £4.40 SAA5050 £3.50 SAF1032p £2.50 SAF1039 £2.00 SAS560 £2.00 SAS660 £1.00 SAS670 £1.00 SL901B £5.00 SL918 £6.20 TA7122 £1.15 TAA320A 50p TAA470 £1.50 TAA570 75p TAA611B £1.50 TAA621 £2.00 TAA661 £1.75 TAA641 £1.50 TA7117 50p TA7120P 50p TA7315AP 50p TA7607AP 40p TA7609P 50p TBA120A 50p TBA120AS 40p TBA120SA 40p TBA120B 40p TBA120SB 40p TBA120SQ £1.00 TBA120U 75p TBA120J 30p TBA120C 40p TBA1441 £1.00 TBA231 75p TBA395Q 50p TBA396Q £1.00 TBA396 75p TBA440P £1.00 TBA1440C £1.00 TBA480Q £1.00 TBA520 £2.00 TBA530 £2.00 TBA540 £1.00 TBA550Q £1.75 TBA560CQ £2.00 TBA570 £1.50 TBA625 50p TBA641 £2.00 TBA651 £2.00 TBA673 £1.00 TBA720A £1.50 TBA750Q £1.50 TBA780 £1.50 TBA800 50p TBA810AS 60p TBA810S 60p TBA820 60p TBA890 £1.00 TBA900 £1.50 TBA920 £1.50 TBA920Q £1.50 TBA950 £1.50 TBA990Q £1.00 TMS1000NL £4.00 TMS1943 £3.00 TMS3587 £1.00 TMS5611 £1.00 TMS5840 75p N64100 £1.00 TMS3529 75p TMS4014 70p TX-012 £1.00 TMS9902 £1.20 ULN2216 75p SN29848 50p SN29770BN £1.00 SN29771BN £1.00 SN29772BN £1.00 SN7402N £1 SN7472N £1 SN74107 £1.00 SN74167 70p SN7472N 20p SN75108AN £1.00 SN76001 £1.00 SN76003 £1.00 SN76013ND £1.00 SN76018 £1.00 SN76008 £1.00 SN76023N £1.50 | | SN76033 £1.50 SN76110N £1 SN76115AN 50p SN76131 50p SN76141N £1.00 SN76226 £1.00 SN76227N 60p SN76228N £1.00 SN76270 £1.00 SN76532N 50p SN76544N £2.00 SN76545 £3.50 SN76546 £1.00 SN76550 30p SN76552 30p SN76570 £1.00 SN76620 50p SN76650 50p SN76660N 40p SN76620AN 50p SN76666 £1.00 SN76705N £1 SN76707N 75p SN76708AN 75p SN76720 £1.50 UA783P3C 40p BT100A/02 40p BT138/10A 70p BT146 30p TBA540Q £1.50 TCA270 £1.00 TCA270Q £1.00 TCA640 £1.00 TCA660 £1.00 TCA270S £1.00 TCA270SQ £1.00 TCA740 £1.00 TCA800 £2.00 TCA830 £1.00 TCEP100 £2.25 TCE120CQ £1.00 TDA440Q £1.00 TDA1003A £1.00 TDA1010 £1.00 TDA1060A £1.50 TDA1072 £1 TDA1151 30p TDA1170 £1.00 TDA1190 £1.00 TDA1327A £1.00 TDA1412 50p TDA2003 80p TDA2004 £2 TDA2010 £1.00 TDA2140 £3.50 TDA2030 £2.00 TDA2525 £1.00 TDA2640 £2.00 TDA2522 £1.00 TDA2530 £1.50 TDA2532 £1.00 TDA2540 80p TDA2541 £1.00 TDA2571AQ £2.50 TDA2575A £1.00 TDA2581 £2.50 TDA2590 £1.00 TDA2593 £1.00 TDA2560 50p TDA2600 £5.00 TDA2611 £1.00 TDA2653 £1.00 TDA2002 £1.00 TDA2640 £2.00 TDA2680 £1.00 TDA2690 £1.00 TDA2593 £1.00 TDA3190 £1.00 TDA3560 £4.00 TDA3571Q £1.50 TDA9403 £3.00 TDA3651AQ £3 SN74LS125AN 30p SN74LS248 50p SN74516 50p SN16861NG 50p SN16862AN £1.00 SN16964AN 50p SN29764AN £1.00 UA721 40p UA7300 40p RGP30G 10p MPSA41 10p MPSA43 10p MJ13005 30p MJE51T 25p MJE340 28p MJE660 25p MJE661 25p MJE3055 £1.00 | | Transistors A1222 15p A1223 15p AC106 15p AC121 15p AC124 15p AC128 15p AC137 15p AC151 15p AC131 15p AC138 15p AC152 15p AC153K 15p AC152K 15p AC169 15p AC176 15p AC176K 15p AC178K 15p AC179 15p AC186 15p AC187K 15p AC188 15p AC188K 15p ACY21 25p AD143 50p AD149 50p AD161/162 pair 40p AF139 25p AF181 £1.00 AF239 25p AF367 25p AL102 £1.75 BC161 30p BD507 50p BD509 30p BD510 30p BD517 30p BD519 30p BD534 30p BD535 30p BD544D 30p BD562 30p BD610 30p BD646 50p BD676A 50p BD678 50p BD681 25p BD807 50p BD826 20p BD948 30p BDX75 30p BDX32 £1.25 BF115 20p BF121 20p BF127 20p BF137 20p BF157 20p BF160 20p BF161 20p BF164 60p BF179 30p BF180 20p BF181 20p BF182 20p BF184 20p BF194 10p BF195 10p BF196 10p BF197 12p BF198 10p BF199 10p BF200 10p BF222 10p BF224 15p BF238 15p BF240 10p BF244 10p BF245b 10p BF256 10p BF257 10p BF258 25p BF262 15p BF263p 15p BF264 15p BF271 10p BF272 10p BF273 10p BF274 10p BF324 25p BF337 50p BF355 50p BF362 50p BF363 15p BF367 15p BF391 15p BF394 10p BF419 30p BF423 15p BF448 30p BF450 20p BF458 30p BF459 30p BF468 30p BF469 30p BF470 20p BF480 50p BF594 10p BF597 10p | | TV Crystals 4MHz 4.433-619 8.867238 Large or small 50p each GEC Power Panel TV106 Thermistor PT34 New £1.00 | | I.C. Holders DIL - DIL 40 Pin x 4 £1.00 42 Pin x 5 £1.00 28 Pin x 4 80p 16 Pin x 10 50p 24 Pin x 5 75p 14 Pin x 10 70p 18 Pin x 10 80p DIL - QIL 16 Pin x 10 £1.00 18 Pin x 10 £1.00 28 Pin x 4 £1.00 8 Pin x 10 50p 16 Pin G11 each 10p | |
| BF694 10p BF758 30p BF760 30p BF734 15p BF743 10p BF784 8p BFW11 20p BFX29 30p BFX84 25p BFX50 15p BFX52 20p BFX90 25p BLY49 25p BPW41 25p BRCL116 25p BRX43 15p BRX48X 10p BRY56 30p BSS68 10p BSY79 10p BSY95a 10p BTY80 20p BSX19 17p BSX20 17p FT3055 30p TCER2 30p 2N930 30p 2N2221 8p 2N2222 8p 2N2906 10p 2N3055 40p 2N3566 10p 2N3702 10p 2N3711 10p 2N3583 50p 2N3904 15p 2N4355 10p 2N4442 £1.00 2N4444 £1.00 2N5296 40p 2N5983 30p 2N6099 40p 2N6109 40p 2N6130 50p 2N6133 50p 2N6348 20p 2N6399 20p 2X 2N6099 on heat sink 50p 2SA437 20p 2SB407 Sanyo TO3 20p 2SB474 30p 2SB566 10p 2SC381 10p 2SC458 50p 2SC515 10p 2SC732 10p 2SC733 10p 2SC1030 £1.00 2SC1172A 10p 2SC1173 10p 2SC1419 20p 2SC1546 20p 2SC1725 20p 2SC2068 20p 2SC2073 8p | | 2SC2122A £1.00 2SC2229 15p 2SC7350 15p 2SD180 TO3 80v/ 6A 15p 2SD200 £2.00 2SK30A 10p BC107 10p BC108 10p BC109 5p BC113 10p BC114 10p BC115 10p BC116 10p BC117 20p BC119 20p BC125 10p BC126 10p BC139 10p BC140 30p BC141 25p BC143 25p BC147 10p BC148 10p BC149 10p BC153 10p BC154 10p BC157a 10p BC158 10p BC159 10p BC160/16 25p BC171 10p BC172 10p BC173 10p BC174 10p BC183 10p BC184 10p BC204 10p BC207 10p BC212 10p BC213 10p BC214 10p BC237 10p BC238 8p BC239 10p BC250 8p BC251 10p BC252 10p BC262 10p BC263b 20p BC294 10p BC298 10p BC300 10p BC301 10p BC303 30p BC307 7p BC308 7p BC309 10p BC327 10p BC328 10p BC328/338 pair 15p BC337 10p BC338 10p BC347 10p BC349b 10p BC350 20p | | BC365 10p BC384 10p BC394 10p BC413 10p BC414 10p BC416 10p BC440 30p BC454 10p BC455 10p BC456 10p BC460 25p BC462 10p BC463 10p BC478 10p BC527 10p BC532 10p BC546 10p BC547 10p BC548 10p BC556 10p BC557 10p BC558 10p BC559 10p BC635 10p BCX31 25p BCX32/36 Pair 75p BCX32 25p BD116 25p BD124 50p BD124 (metal) 60p BD130Y 25p BD131 30p BD132/238 30p BD135 25p BD136 30p BD138 30p BD176 25p BD182 10p BD183 70p BD202 60p BD204 60p BD221 20p BD222 30p BD228 30p BD226 20p BD233 30p BD235 30p BD239 15p BD243c 30p BD244 50p BD250a 30p BD252 20p BD253B 50p BD331 20p BD332 20p BD373b 20p BD416 25p BD433 25p BD437 25p BD439 50p BD501 30p BF761 30p BF858 30p BF871 30p | | 5-5MHz Filters 15p 6MHz 30p BFU455K 5p Thyristors TD3F800 £1.50 BT106 Plastic 30p BT106 Metal £1.20 BT119 £1.00 BT120 £1.00 BRG4443 75p G11 Thyristor 60p Decca 80-100 60p 2N4444 £1.00 Thermistors VA1104 50p ITP7266312 15p PTH451 AOR 15p PT37P Fits Pye & PT34 most sets 20p GEC Double Thermistor 75p | | BLY49 50p I.C. Heat Sink 20 for £1 20xTOS Heat Sink £1.00 CVC 9 power supply board £1.50 CVC 20/2 mains £2.00 panel FIT Mains Filter 1/250v/ CVC 20 to 45 chassis 50p Pots 10 k with Switch 25p Pots 47 k with Switch 25p Mullard Surface Wave Filter RW 153P Colour TV Filter 40p Mullard Surface Wave Filter RW 154 Colour TV Filter 40p G11 Line Scan P.C.B. £1.00 G11 Power Supply P.C.B. £2.00 | | | | | | | | | | | |