

OCTOBER 1984

Australia \$1.80, New Zealand \$2.20, Malaysia \$5.50 **£1.00**

TELEVISION

SERVICING · PROJECTS · VIDEO · DEVELOPMENTS

EXTRA PAGES + DATA CARD



A Look at Monitors

Panoramic Spectrum Display

Vintage TV · N1700 Renovation

System A Modulator · DX-TV

VCR Clinic · TV Fault Finding

MANOR SUPPLIES

NEW MKV PAL COLOUR TEST GENERATOR FOR TV & VCR.

TEST
DEMONSTRATIONS
AT 172
WEST END LANE



- ★ 40 different patterns and variations.
- ★ Broadcast transmission accuracy (fully interlaced sync pulses with correct picture blanking).
- ★ EBU colour bars, BBC colour bars, whole rasters & split bars (specially useful for VCR service), white, yellow, cyan, green, magenta, red, blue and black.
- ★ Chequerboard.
- ★ Mono outputs with border castellations, cross hatch, grey scale, vertical lines, horizontal lines and dots. UHF modulator output plugs straight into receiver aerial socket.
- ★ Additional video output for CCTV & VCR.
- ★ Facilities for sound output.
- ★ Easy to build kit, standard parts. Only 2 adjustments. No special test equipment required.
- ★ Mains operated with stabilised power supply.
- ★ All kits fully guaranteed with back-up service.
- ★ Also available with VHF Modulator.

Price of Kit **£70.00**
De Luxe Case (10" x 6" x 2 1/2") **£7.40**
Optional Sound Module (6MHz or 5.5MHz) **£3.90**
Built & Tested in De Luxe Case including Sound Module **£105.00**


SPECIAL TEST
REPORT
'TELEVISION'
DEC. 1982

Post/Packing £2.50
Add VAT 15% TO ALL PRICES

PAL COLOUR BAR GENERATOR (Mk4)



4TH SUCCESSFUL YEAR

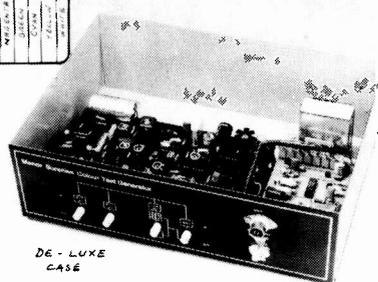

- ★ Output at UHF, applied to receiver aerial socket.
- ★ In addition to colour bars R-Y, B-Y etc.
- ★ Cross-hatch, grey scale, peak white and black level.
- ★ Push button controls, battery or mains operated.
- ★ Simple design, only five i.c.s on colour bar P.C.B.

PRICE OF MK 4 COLOUR BAR GENERATOR KIT
£30.00. DELUXE CASE £7.40. BATT HOLDERS £2.80.
MAINS SUPPLY KIT **£4.20 (Combined P&P £2.20).**

MK 4 DE LUXE (BATTERY) BUILT & TESTED **£58.00 + £2.20 P & P.**
MK 4 DE LUXE (MAINS) BUILT & TESTED **£68.00 + £2.20 P & P.**
VHF MODULATOR (CH 1 to 4) FOR OVERSEAS **£5.75.**
EASILY ADAPTED FOR VIDEO OUTPUT & C.C.T.V.
(ADD VAT 15% TO ALL PRICES)

MANOR SUPPLIES TELETEXT ADAPTOR KITS (LESS CASE)

MK 1 (Texas XMII) remote control **£120.00** p.p. £3.00.
MK 2 (Mullard) infra red remote control **£150.00** p.p. £3.00.
Further details on request. Tel 01-794 8751/7346

Goods available if in stock immediately over shop counter (Mail order between 3 days and 1 week from receipt of order).

TV SERVICE SPARES

BACKED BY TWENTY YEARS EXPERIENCE & STAFF OF
TECHNICAL EXPERTS

TELEVISION MAGAZINE PROJECT PARTS. COLOUR PORTABLE, MONO
PORTABLE, MONITOR, TEST GENERATORS, ETC.

THORN TX10 Teletext Interface Panels suitable for Mullard Decoders **£2.50** p.p. £1.00.
THORN TX10 Facia Control Panel incl. Remote Control receiver **£7.50** p.p. £1.50.
THORN TX10 type Remote & Tuning Control Panel **£9.40** p.p. £1.50.
THORN TX10 Series Facia Control Panel with 8 position Channel Selector **£5.00** p.p. £1.50.
PHILIPS UHF Modulator (Audio & Video Input) **£15.00** p.p. £1.00.
SAW FILTER IF AMPLIFIER PLUS TUNER complete and tested for T.V. Sound & Vision. **£28.50** p.p. £1.20.
THORN TX9, TX10 Saw Filter IF Panel. **£8.50** p.p. 80p.
PAL DECODER KIT for RGB Monitors **£27.00** p.p. £1.00.
SPECIAL OFFER TEXAS XM11 Teletext Decoder New & Tested at reduced price. **£40.00** p.p. £1.60.
TELETEXT 23 Button De-Luxe Handset with 5 yds Cable. **£6.80** p.p. £1.20.
XM11 Stab. Power Supply. **£3.80** p.p. £1.20.
CROSS HATCH UNIT KIT, Aerial Input type, incl. T.V. sync. and UHF Modulator, Battery Operated, also gives Peak White & Black Levels, can be used for any set. **£12.00** p.p. 80p. (Alum. Case **£2.55**, De Luxe Case **£6.80** p.p. £1.40). ADDITIONAL GREY SCALE Kit **£2.90** p.p. 45p.
UHF SIGNAL STRENGTH METER Kit **£20.00** (VHF version also available). Alum. Case **£2.55**. De Luxe Case **£7.40** p.p. £1.80.
CRT TESTER & REACTIVATOR PROJECT KIT For Colour & Mono **£28.00** p.p. £2.80.
BUSH Z718 BC6100 series IF Panel **£5.00** p.p. 90p.
BUSH A816 IF Panel (Surplus) **£1.65** p.p. 90p.
DECCA 80 Series IF, Frame, T.B. **£5.00** p.p. £1.40.
GEC 2040 Convergence Panels, Decoder Panels, **£2.50** p.p. £1.80.
GEC 2040 IF Panels **£2.80** p.p. £1.60.
GEC 2110 Convergence Panels **£5.00** p.p. £1.80.
GEC "20AX" Series Switch Mode Power Supply **£5.00** p.p. £1.80.
PYE 691-7 CDA Panels, Makers tested stock. **£6.00** p.p. £1.45.
PYE 725 T.B. Unit, Makers tested stock. **£20.00** p.p. £2.80.
THORN TX9 Panels ex factory for small spares. Includes I.C.s & Semiconductors etc. **£5.00** p.p. £2.00.
THORN TX9 Panels salvaged ex factory for spares incl. LOPT & Mains Transformers. **£10.00** p.p. £2.80.
THORN TX9 Panels ex factory salvaged complete cond. **£20.00** p.p. £2.80.
THORN TX10 T.B. Panels salvaged ex factory. **£15.00** p.p. £3.00.
THORN TX10 IF/Decoder Panels salvaged ex factory. **£15.00** p.p. £2.00.
THORN 3000/3500 Power supply unit. New cond. **£10.00** p.p. £2.80.
THORN 8000/8500 IF/Decoder Panels salvaged **£3.20** p.p. £1.80.
THORN 8000/8500 Frame T.B. Panels salvaged/spares **£2.50** p.p. £1.40.
THORN 9000 Series Control & Receiver Unit **£6.80** p.p. £1.80.
THORN 9000 IF/Decoder Panels Salvaged. **£5.00** p.p. £1.60.
THORN 9000 Series. Long panel facia unit incl. 6 Position Channel Selector & Loudspeaker **£6.00** p.p. £2.00.
PHILIPS G8/G9 IF/Decoder Panels for small spares **£1.50** p.p. £1.40.
G8 Decoder Panels salvaged **£3.80**. Panels for spares **£1.75** p.p. £1.40.
G9 Scan Panel. Basic PCB in Fibreglass **£14.50** p.p. £1.80.
G11 Frame Panels, IF Panels **£18.00** each p.p. £2.00.
GRUNDIG 8630 Series Varicap Tuners **£5.00** p.p. £1.00.
VARICAP. U321, U322, ELC1043/06, ELC1043/5 **£6.80** p.p. 80p. G.I. type (equiv. 1043/05) **£3.50** p.p. 80p. Makers Varicap Controls PYE CT200 4PSN **£7.50**, BUSH 4PSN **£4.80**, DECCA 4PSN **£5.80** p.p. 80p.
SPECIAL OFFER ELEVEN POSITION Varicap Control Unit UHF/VHF **£1.80** p.p. £1.00.
BUSH "TOUCH TUNE" Varicap Control Z179, Z718 types **£3.80** p.p. 95p.
VARICAP UHF-VHF ELC2000S, ELC2060 **£9.80**, BUSH **£7.80** p.p. 90p.
VARICAP VHF MULLARD ELC 1042, PHILIPS, **£6.90** p.p. 80p.
UHF/625 TUNERS, many different types in stock. DECCA Bradford 5 position, MULLARD 4 position **£2.50**, JAP Rotary **£4.80** p.p. £1.80.
TV SOUND IF Panels **£6.80** p.p. £1.00.
LOPT TESTER, Service Dept approved **£15.50** p.p. £1.20.
LOPTS New and guar. P/P Mono **£1.35**, Colour **£1.50**, Bobbins **80p.**

BUSH 161 to 186 (twin panel).....	£5.90	R.B.M. A823	£4.90
BUSH, MURPHY 774 series	£8.50	R.B.M. Z179	£9.80
BUSH, MURPHY A816 series	£8.50	R.B.M. T20, T22	£9.80
FERG., H.M.V., MARCONI, ULTRA		R.B.M. T20, T22 Bobbin	£5.60
950, 1400, 1500, 1580, 1590, 1591	£5.90	DECCA Bradford (state Mod No.)	£8.80
THORN 1600, 1615, 1690, 1691	£9.15	DECCA 80, 100	£8.80
GEC 2000 to 2038 series	£6.80	GEC 2028, 2040, 2100	£5.80
GEC series 1 & 2	£8.00	GEC 2110 series	£10.60
INDESIT 20/24EGB	£7.65	ITT CVC 5 to 9, CVC20	£9.80
ITT/KB VC200, 300	£7.65	ITT CVC25, CVC30 series	£8.80
MURPHY 1910 to 2414 (twin panel)	£5.90	PYE 691-697 (state model no.)	£10.00
PHILIPS 170, 210, 300 series	£7.65	PYE 713, 715	£6.80
PYE, INVICTA, EKCO, FERR.		PYE 725 (90°) 731 to 741	£9.20
368, 169, 569, 769 series	£7.65	PHILIPS G8	£8.80
SPECIAL OFFER		PHILIPS G9	£10.80
DECCA 20/24, 1700, 2000, 2401	£3.80	PHILIPS 570, 571	£6.80
GEC 2114/Junior Fineline	£2.80	THORN 3000/3500 SCAN, EHT	£6.90
PYE 40, 67	£1.75	THORN 8000/8500/8800	£12.90
KB VC ELEVEN (003)	£1.75	THORN 9000 to 9600	£12.90
KB VCI	£2.80	THORN 9800	£19.05

OTHERS AVAILABLE, PRICES ON REQUEST. ALSO LOPTS.

TRIPLERS Full range available. Mono & Colour.
Special Offer: Thorn 8000 (2 lead) EHT Tray **£2.80** p.p. 80p.
TRANSDUCTORS suitable for G8, A823, Bradford etc. **£1.50** p.p. 60p.
6-3V CRT Boost Transformers for Colour & Mono **£5.00** p.p. £1.20.


CALLERS WELCOME AT SHOP PREMISES
THOUSANDS OF ADDITIONAL ITEMS, ENQUIRIES INVITED
LARGE SELECTION TESTED COLOUR PANELS POPULAR MODELS
Telephone 01-794 8751, 794 7346

MANOR SUPPLIES

172 WEST END LANE, LONDON, N.W.6.

NEAR: W. Hampstead Tube Stn. (Jubilee) Buses 28, 159, C11 pass door
W. Hampstead British Rail Stns. (Richmond, Broad St.) (St. Pancras, Bedford)
W. Hampstead (Brit. Rail) access from all over Greater London.

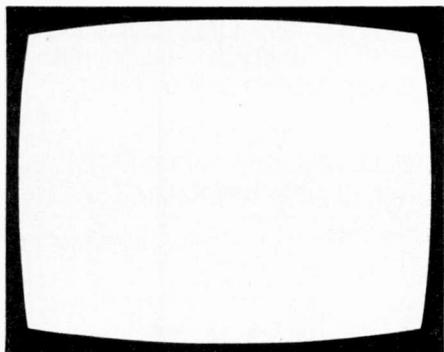Mail Order: 64 GOLDERS MANOR DRIVE, LONDON N.W.11.
PLEASE ADD VAT 15% TO ALL PRICES



TELEVISION

October
1984

Vol. 34, No. 12
Issue 408

COPYRIGHT

©IPC Magazines Limited, 1984, Copyright in all drawings, photographs and articles published in *Television* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Television* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

CORRESPONDENCE

All correspondence regarding advertisements should be addressed to the Advertisement Manager, "Television", King's Reach Tower, Stamford Street, London SE1 9LS. Editorial correspondence should be addressed to "Television", IPC Magazines Ltd., King's Reach Tower, Stamford Street, London SE1 9LS.

SUBSCRIPTIONS

An annual subscription costs £11 in the UK, £12 overseas (by surface mail). Send orders with payment to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex, RH16 3DH.

BINDERS AND INDEXES

Binders (£4.50) and Indexes (45p) can be supplied by the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. Prices include postage and VAT. In the case of overseas orders, add 60p.

BACK NUMBERS

Some back issues are available from the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF at £1.20p inclusive of postage and packing.

QUERIES

We regret that we cannot answer technical queries over the telephone nor supply service sheets. We will endeavour to assist readers who have queries relating to articles published in *Television*, but we cannot offer advice on modifications to our published designs nor comment on alternative ways of using them. All correspondents expecting a reply should enclose a stamped addressed envelope. Requests for advice on dealing with servicing problems should be directed to our Queries Service. For details see our regular feature "Service Bureau". Send to the address given above (see "correspondence").

this month

- 641 Leader**
- 642 System A Modulator** *David Looser*
A high-quality vision and sound modulator to provide Band I signals.
- 644 Renovating the Philips N1700** *Freddie Archer*
Notes on keeping these high-quality machines in operation.
- 647 A Look at Monitors, Part 1** *Eugene Trundle*
Monitors are playing a much larger role nowadays, with the need for various special displays. This part deals with basic performance requirements.
- 652 VCR Clinic**
Reports on VCR servicing from Derek Snelling, Steve Beeching, T. Eng. (C.E.I.), M. S. Barakat, Les Harris, Ian Hutton and John Coombes.
- 654 Letters**
- 655 On being fooled** *Les Lawry-Johns*
Even chassis you know well can come up with faults to try your patience. There's also Tinker Tim who does the same thing.
- 656 Teletopics**
- 658 Panoramic Spectrum Display** *Denis G. Mott*
Interfacing a tuner and scope to get a panoramic band display. Useful for band scanning and tuner alignment.
- 659 Pre-War Television** *Harold Peters*
What it was like during those three years when London had the world's first regular TV broadcasting service - the sets, the programmes and the development of the system.
- 661 Next Month in Television**
- 662 Servicing the Grundig 2 x 4 Super, Part 4** *Mike Phelan*
The motor connection board and the mechanics.
- 666 Long-distance Television** *Roger Bunney*
Reports on DX conditions and reception and news from abroad.
- 669 TV Fault Finding**
Notes on TV servicing problems from Mick Dutton, Graham Colebourn, B.Sc., Malcolm Burrell, P. J. Bradford, Nick Lyons, M. S. Barakat, John Coombes, Robin D. Smith and Philip Blundell, Eng. Tech.
- 672 VCR Servo Systems, Part 2** *Eugene Trundle*
The development of more complex techniques from dual-loops to four-loop systems, digital servos and trick-mode operation.
- 677 Book Notices**
- 678 Service Bureau**
- 679 Test Case 262**

OUR NEXT ISSUE DATED NOVEMBER WILL
BE PUBLISHED ON OCTOBER 17

T.T.L. 74LS SERIES

74LS00	58	74LS37	35	74LS92	65	74LS160	90	74LS251	65	78
74LS02	58	74LS38	35	74LS93	60	74LS161	85	74LS253	95	7805
74LS03	58	74LS40	35	74LS107	80	74LS162	4.04	74LS257	1.20	7806
74LS04	58	74LS42	80	74LS109	58	74LS163	85	74LS258	95	7808
74LS05	58	74LS47	85	74LS112	50	74LS164	85	74LS259	1.70	7812
74LS08	58	74LS48	83	74LS113	44	74LS165	1.50	74LS273	1.90	7815
74LS09	58	74LS49	33	74LS114	70	74LS174	85	74LS283	1.30	7818
74LS10	58	74LS51	33	74LS123	80	74LS175	85	74LS293	1.20	7824
74LS11	58	74LS54	43	74LS125	85	74LS191	1.02	74LS352	1.40	78L05
74LS13	37	74LS55	60	74LS126	60	74LS192	1.30	74LS353	1.40	78L08
74LS14	46	74LS73	60	74LS132	63	74LS193	1.30	74LS365	75	78L12
74LS15	33	74LS74	65	74LS138	83	74LS194A	75	74LS366	82	78L24
74LS20	35	74LS75	65	74LS139	65	74LS197	95	74LS367	1.65	7905
74LS21	35	74LS76	65	74LS151	85	74LS240	2.20	74LS368	65	7906
74LS22	35	74LS78	65	74LS153	85	74LS241	2.20	74LS373	1.40	7912
74LS26	44	74LS83A	89	74LS155	65	74LS242	2.20	74LS374	1.55	7912
74LS27	35	74LS86	39	74LS156	1.02	74LS243	2.20	74LS393	1.20	7915
74LS30	35	74LS85	98	74LS157	78	74LS244	2.20	74LS670	1.78	7918
74LS32	35	74LS90	60	74LS158	65	74LS245	2.30			7924
										79L05
										79L12
										79L15
										79L24

'4000 B' SERIES CMOS

4001B	21	4032B	1.04	4072B	22	4511B	76	4539B	77	79L24
4002B	21	4035B	80	4073B	22	4513B	1.68	4543B	96	I.C. SOCKETS
4008B	72	4038B	99	4075B	22	4515B	1.88	4551B	96	DIL to DIL
4011B	21	4040B	72	4076B	80	4518B	76	4554B	1.20	8 way
4012B	21	4042B	58	4077B	22	4519B	64	4560B	1.76	29
4013B	30	4043B	71	4078B	22	4520B	76	4561B	74	14 way
4014B	74	4044B	71	4081B	22	4521B	1.68	4566B	1.20	16 way
4015B	76	4046B	96	4093B	43	4522B	88	4580B	3.60	38 way
4016B	31	4047B	70	4094B	1.56	4526B	88	4581B	1.84	40 way
4017B	66	4049UB	32	4099B	1.20	4527B	1.20	4582B	80	DIL to QUIL
4018B	72	4050B	32	4160B	72	4528B	88	4583B	1.00	14 way
4020B	76	4051B	72	4161B	72	4529B	1.04	4584B	40	16 way
4021B	70	4052B	72	4162B	72	4530B	62	4585B	88	18 way
4022B	70	4053B	72	4163B	72	4531B	72	4597B	1.84	18 way
4023B	21	4060B	96	4502B	72	4532B	1.00	4598B	2.40	QUIL to QUIL
4024B	50	4066B	43	4505B	1.88	4536B	2.64	4599B	2.00	14 way
4025B	21	4068B	22	4510B	76	4538B	1.04		16 way	36

LINE OUTPUT TRANS.

R.B.M. T20A	13.95
R.B.M. A774 Mono	11.74
R.B.M. 2179	15.00
R.B.M. 2718 22"	19.50
PHILIPS 320	8.70
PHILIPS 210/300 Mono	10.00
PHILIPS G8	8.75
PHILIPS G9	7.75
PHILIPS G11	13.50
PYE 697 (Printed)	14.50
PYE 713/731	10.00
PYE 725 90"	10.50
PYE 169	10.00
DECCA 80/100	8.58
DECCA 1700	9.00
DECCA 1730	8.58
DECCA 2230	8.58
GEC 2110	9.45
GEC 2040	9.50
GEC 2200	6.65
ITT CVC 1-9	10.85
ITT CVC 25/30/32	8.65
ITT CVC 20	8.60
THORN 3000 EHT	9.95
THORN 3000 SCAN	7.95
THORN 8000	11.33
THORN 8500	11.33
THORN 9000	10.85
THORN 3000/3500	10.00
Mains	8.68
THORN 1591	9.68
THORN 1615	12.50
THORN 1615	9.75
PHILIPS KT3	7.70
RANK BUSHRANGER	£10.00
PYE 741	8.20
THORN 9800	23.00
B+O (2000, 3000)	12.70
B+O (3000 EHT)	18.90

RECTIFIER TRAYS

THORN 950 Mk II	4.25
THORN 1400 3 Stck	5.20
THORN 1500 3 Stck	5.20
THORN 1500 5 Stck	5.29
THORN 1600	4.95
THORN 3000/3500	7.98
THORN 8000	5.28
THORN 8500/8800	7.15
THORN 9000	7.93
DECCA 1730/1830	4.48
DECCA 30	6.76
DECCA 80	6.60
DECCA 100	7.50
UNIVERSAL ITT or REMO	6.00
GEC 2100	7.40
GEC 2200 (20AX)	6.50
GEC 2040/2028	6.60
GEC 2110 Pre Jan '77	7.00
GEC 2110 Post Jan '77	7.00
PHILIPS G8 Short Focus Lead	6.75
PHILIPS G8 Long Focus 550	6.75
PHILIPS G9	6.37
Pye/Philips K3 Tripler	10.65
PYE 691/3	6.58
PYE 713/4 Lead	8.79
PYE 713 Doubler 5 Lead	8.79
Philips/Pye KT3	6.67
PYE 731/725	7.60
R.B.M. A823 (plug in) AV	7.60
KORTING (similar to Siemens TVK1)	7.32
ITT KB CVC5/9	6.90
ITT KB CVC20/25/30 (Mullard)	5.95
RRI T20	6.80

REPLACEMENT ELECTROLYTICS

PYE 169 (200/200/100/32)	3.40
PHILIPS 320 (400/400/200V)	2.74
DECCA 30 (400/400/350V)	3.40
DECCA 80 (400/350V)	3.97
DECCA 100 (800/250V)	3.97
DECCA 1700 (200/200/400/350V)	4.83
PHILIPS G8 (600/300V)	2.30
PHILIPS G9 (600/300V)	2.21
PHILIPS G11 (470/250V)	2.90
PYE 691/7 (200/300/350V)	2.70
PYE 731 (600/300V)	2.31
RBM A823 (2500/2500/30V)	1.66
RBM A823 (600/300V)	2.83
RBM Z146 (300/300/350V)	3.55
RRI T20A (220/400V)	2.00
ITT CVC5/9 (200/200/75/25)	2.98
ITT CVC 20 (220/400V)	2.00
GEC 2110 (600/250V)	1.94
GEC 2040 (1000/2000/35V)	1.19
GEC 2040 (300/300/150/100/50)	4.10
THORN 3500 (400/40V)	1.83
THORN 950 (100/300/100/16/275V)	1.30
THORN 1400 (150/100/100/100/150/320V)	2.79
THORN 1500 (150/150/100/300V)	2.20
THORN 1500 (12/300V)	31
THORN 3500 (175/100/100/400/350V)	2.78
THORN 3500 (1000/63V)	86
THORN 3500 (1000/70V)	86
THORN 8000/8500 (2500/2500/63V)	3.38
THORN 8000/8500 (700/250V)	2.31
THORN 8000/8500 (400/350V)	2.56
THORN 9000 (450/400V)	3.28
GEC (200/200/150/50)	2.64
PHILIPS 69 2200/63V	1.25
THORN 4700 P/C 25V	1.20
THORN 1591/1691 4700/25V	1.20

RECTIFIER STICKS

TV11	74	TV18	90
TV13	79	TV20	1.20

FUSES

1 1/2" QUICK BLOW	Per Pack type of 10
100ma	73
250ma-500ma-750ma-1A	60
1.5A-2A-2.5A-3A-5A	60
1 1/2" ANTISURGE	
250ma, 500ma, 600ma, 630ma, 750ma, 850ma,	
1A, 1.25A, 1.5A, 2A	1.70
2.5A, 3A, 5A	2.70
20mm ANTISURGE	
80ma	4.80
100ma	2.50
160ma, 200ma	2.20
315ma, 500ma, 630ma, 800ma, 1A, 1.25A, 1.6A,	
2A	1.30
2.5A, 3.15A, 4A, 400ma	1.90
20mm QUICK BLOW	
100ma, 250ma, 500ma, 630ma, 800ma	90
1A, 1.25A, 1.6A, 2A, 2.5A, 3.15A, 5A	60
1" MAINS	
2A, 3A, 5A, 10A, 13A	1.00

NEW MONO TUBES

MULL. A31/510 110° 12"	18.50
MULL. A34/510 110° 14"	20.00
ASO/120WR 110° 20"	15.00
A61/120WR 110° 24"	17.50
VEGA 12" 90° (Jap Types)	15.00
CME1520 (15" Mono)	15.00
MULLARD COLOUREX*	
18" A47/343X	59.00
19" A49/120X	53.00
20" A51/110X	53.00
22" A56/120X	48.00
25" A63/200X	55.00
26" A66/120X	60.00
26" A67/120X	62.00
26" A66/140X (410X) 110°	36.00
26" A66/140X (410X) 110°	36.00
20" A51/161X	72.00
22" A56/510X	60.00
A51 570X	92.00
A56 510	60.00
A66 510	92.00
WHILE STOCKS LAST	
1 year warranty Option on 4 years.	
Quotes on delivery and glass charges	

REBUILD COLOUR TUBES

ALL AVAILABLE EX-STOCK ON GLASS FOR GLASS EXCHANGE FROM TRADE COUNTER. SOME TYPES AVAILABLE WITHOUT EXCHANGE FOR SMALL GLASS CHARGE

17" A44/271X	32.00
18" A47/342X (Low Focus)	32.00
18" A47/343X (Std Focus)	32.00
20" A51/110X	30.00
19" A49/120X	30.00
22" A56/120X	30.00
25" A63/200X	34.00
26" A66/120X	34.00
26" A67/120X	34.00
22" A56/140X (410X) 110°	36.00
26" A66/140X (410X) 110°	36.00
20" A51/161X	60.00
22" A56/510X	50.00
A56 510	89.00
A66 510X	75.00
A66 500X	64.00

SLIDER POTENTIOMETER

Lin or Log	
470R-1K-2K2-4K7	65
10K-47K-470K	

MIDGET CONTROLS

Insulated Spindle Length 44mm

Log or Lin Without Switch	
5K-10K-25K-50K-100K-250K-500K-1M	39p
With D.P.S.T. Switch	
Log: 5K-10K-25K-50K-100K	81p
250K, 500K, 1M, 2M	
Dual gang Controls	1.25
16mm Rotary Controls 10K, 22K, 100K, 1M, 10K	39p

WIREWOUND RESISTORS*

4W 1R-10K	24p
7W 1R-22K	26p
11W 1R-22K	29p
17W 1R22K	32p
(Preferred values)*	

THICK FILM RESISTOR NETWORK

Standard or miniature	
Horizontal or Vertical	
100R-2M2	16p
THORN 3500 (5 pin connection)	1.98
PYE 731 (6 pin connection)	2.20
THORN 9000 (Circuit Ref. R704/7)	1.98

CARBON RESISTORS*

1/4W 3R3-8M2	20
1/4W 3R3-8M2	20
1W 10R-10M	36
2W 10R-10M	62
Sold in packs of 10 per type i.e. per value	

EVER READY BATTERIES

HP2	26	PP6	82
HP7	12	PP7	82
HP11	24	PP9	84
HP16	13	R6PP	17
PP3	42	R14PP	26
PP3-C	53	1289	45

RECHARGEABLES EVER READY

RX6 (HP7)	1.10
RX14 (HP11)	1.95
RX20 (HP2)	2.15
RX22 (PP3)	3.75
Universal Charger	6.00

P. V. TUBES TEL: 0254 36521/32611
104 ABBEY STREET, ACCRINGTON

MAINS DROPPERS

DECCA 20	2.48
DECCA 27R/47R	1.40
DECCA 56R/68R	1.40
R.B.M. A823 56R/68R	94
R.B.M. 161	82
GEC 2000/2018	70
GEC 27840	64
PYE 713/15 3R5/15/45R	1.80
PYE 725/31 3R0/56R/27R	1.84
PYE 725 56R/27R	1.04
PHILIPS 210/5050 30R/125R/2K85	ECF82
	1.75
PHILIPS 210/5051 -/118R/148R	93
PHILIPS G8/5081 47R Section	50
PHILIPS G8/5083 2R2/68R	95
THORN 1400	1.20
THORN 1500</	

P. V. TUBES

PLEASE NOTE OUR NEW ADDRESS - COME AND SEE US

104 ABBEY STREET, ACCRINGTON, LANCS BB5 1EE.

Tel: 0254 36521/32611 Telex: 635562 Griffin G (For P.V.)

HOW TO ORDER
ADD 65p per order P+P (U.K.).
Heavier parcels e.g. cable, service aids, degaus. coils please allow £1.20 P+P (U.K.).
Export orders charged at cost. First Class Mail is used whenever possible. Add 15% VAT to total except where it states zero rate.

Goods are despatched on the day we receive your order. If for any reason we are out of stock we will try to inform you as quickly as possible. We try our best to give a speedy, fair and efficient service. As our regular customers know, orders telephoned in before 4 p.m. will be despatched the same day. V.A.T. invoice on request. Give us a ring - we'll give you service. Please ask if what you need is not listed - we will try to help. Prices are subject to change without notice.

SEMICONDUCTORS

AC107	35	BC557	8	BF337	41
AC128	30	BC558	9	BF338	41
AC127	32	BC772	13	BF355	56
AC128	32	BD115	45	BF362	68
AC128K	40	BD116A	85	BF363	72
AC141K	39	BD124P	79	BF371	70
AC142K	38	BD131	50	BF392	35
AC176	35	BD132	49	BF422	34
AC176K	35	BD133	60	BF423	46
AC186	41	BD135	38	BF435	35
AC187	38	BF136	38	BF457	35
AC187K	38	BD137	38	BF458	43
AC188	35	BF138	35	BF459	43
AC188K	39	BD139	35	BF460	86
AD143	82	BD140	44	BF462	86
AD161	54	BD144	1.70	BF469	46
AD162	54	BD150	60	BF470	56
AD161/62 MP	1.15	BD159	65	BF597	10
AF106	49	BD166	52	BF757	54
AF114	89	BD179	70	BF758	54
AF118	1.20	BD182	1.20	BFR39	27
AF121	75	BD183	75	BFR40	30
AF124	48	BD201	85	BFR79	85
AF125	46	BD202	91	BFR90	1.74
AF126	46	BD203	90	BF742	39
AF127	38	BD204	99	BF743	39
AF139	58	BD222	46	BFW10	60
AF178	1.54	BD223	56	BFX29	40
AF239	60	BD225	47	BFX84	42
AL102	2.00	BD232	68	BFX65	30
AU106	2.50	BD233	60	BFX86	30
AU107	2.00	BD234	63	BFX88	46
AU113	2.00	BD235	60	BFY50	30
BC107	20	BD236	65	BFY51	30
BC106	20	BD237	57	BFY52	24
BC109	20	BD238	65	BFY90	95
BC114	12	BD243	85	BR100	34
BC115	17	BD244	85	BR101	45
BC116A	16	BD410	79	BR103	83
BC117	30	BD434	74	BRC4443	94
BC118	24	BD437	86	BRC4444	98
BC119	36	BD438	94	BRX46	40
BC139	28	BD507	52	BRX39	56
BC140	32	BD508	55	BRX55	45
BC141	26	BD509	56	BRX56	57
BC142	30	BD510	60	BSV57B	89
BC143	31	BD278A	81	BSW67	68
BC147	13	BD517	60	BT100	1.65
BC148	9	BD520	75	BT101	1.20
BC149	12	BD526	62	BT102/500	1.20
BC157	16	BD535	82	BT106	1.60
BC158	16	BD536	91	BT107	1.69
BC159	15	BD696A	1.49	BT108	1.69
BC160	25	BD697	1.24	BT109	99
BC161	28	BD698	1.39	BT116	1.21
BC170B	15	BD698	1.90	BT119	3.66
BC171	15	BD707	95	BT120	3.66
BC172	15	BDX32	2.10	BT151/800	1.20
BC173	12	BF115	38	BU104	2.00
BC174	10	BF117	36	BU105	1.88
BC177	27	BF125	26	BU108	1.50
BC178	26	BF127	47	BU124	1.90
BC182L	9	BF154	23	BU126	1.75
BC183L	12	BF158	18	BU204	1.58
BC184L	14	BF160	27	BU205	1.42
BC186	18	BF167	24	BU206	1.80
BC187	18	BF173	22	BU208	1.60
BC204	10	BF177	52	BU208A	1.65
BC206	13	BF178	46	BU208/02	2.10
BC209	10	BF179	28	BU326A	1.75
BC212	9	BF180	39	BU407	1.70
BC212L	13	BF181	39	BU426	3.07
BC213	13	BF182	36	BU500	2.30
BC214	10	BF183	29	BU526	2.46
BC237	14	BF184	36	BU508	3.20
BC238	14	BF185	36	BU806	1.40
BC251A	18	BF194/394	16	BU807	2.94
BC252	12	BF195	16	BUW84	1.45
BC261	18	BF198	16	BUW91A	3.84
BC262	18	BF197	16	BUX84	1.50
BC300	50	BF198	18	I1222	40
BC301	53	BF199	21	MCR101	45
BC303	33	BF200	35	MCR220	1.50
BC307	20	BF224	25	ME0411	20
BC308	25	BF225	20	MJE340	68
BC323	99	BF241	25	MJE520	50
BC327	18	BF256	55	MJ3000	1.98
BC328	18	BF257	28	MPSA92	35
BC337	18	BF258	25	MR814	45
BC338	18	BF259	35	MR854	55
BC461	30	BF262	84	MR475	2.46
BC547	13	BF263	75	MR479	2.60
BC548	13	BF271	24	ON447	99
BCX32	30	BF273	24	ON448	99
BC549	8	BF274	24	OT112	91
BC550	7	BF336	36	OT121	1.91


INTEGRATED CIRCUITS

R2008B	1.90	AN214Q	3.91	SN76003N	2.49
R2010B	1.92	AN240	3.84	=SN76013N	
R2265	1.50	AN318	3.98	SN76023N	2.00
R2322	62	AN262	2.45	SN76110N	1.15
R2323	67	AN301	5.15	SN76115N	2.27
R2461	1.50	AN715Q	3.97	SN76131N	2.00
R2540	2.80	AN6340	7.85	SN76226DN	2.00
RCA16334	90	AN6341	4.45	SN76227N	1.18
RCA16029	99	AN6341N	5.10	SN76532N	1.50
RCA16091	2.95	AN6344	7.85	SN76533N	1.70
RCA16092	99	BA521	2.80	SN76033N	2.49
RCA16040	96	BA536	3.00	SN76544N	2.35
RCA16041	84	CA555	46	SN76650N	1.05
RCA16334	90	CA556	84	SN76660N	80
RCA16335	90	CA741	25	SN76666N	80
RCA16799	99	CA748	45	SN76530A	1.47
RCA16957	2.88	CA3065	1.80	STK015	6.25
TIC45	90	HA1124	1.65	STK032	13.25
TIC46	60	HA1151	3.89	STK043	11.05
TIC47	65	HA1322	2.65	STK433	5.65
TIL78	48	HA1342	2.49	STK435	9.06
TIP29C	43	HA1306N	2.60	STK436	5.50
TIP30A	47	HA1366VWR	2.80	STK459	8.20
TIP30C	43	HA1392	3.95	STK441	8.10
TIP31C	56	HA1219	2.49	STK461=465	9.60
TIP32C	42	LA4031P	3.21	STK463	14.30
TIP33B	75	LA4032P	2.90	SW153	2.74
TIP34B	1.06	LA4102	3.37	TA7050P	95
TIP41C	47	LA4250	3.57	TA7051P	95
TIP42C	50	LA4000	3.05	TA7063P	2.20
TIP47	70	LA4422	3.28	TA7074P	1.00
TIP120	65	LC7130	5.93	TA7078P	3.43
TIP2955	30	LC7120	5.87	TA7120P	2.43
TIP3055	63	LC7137	5.50	TA7129AP	3.76
TS191	21	LM1011	3.25	TA7130P	1.93
TU106/02	1.80	LM1340T	75	TA7141P	95
2N696	21	LM1303N	2.63	TA7146P	4.67
2N918	82	MB3712	1.95	TA7193P	5.67
2N2904	51	MC1307	1.99	TA7172P	1.85
2N2905	28	MC1310P	1.60	TA7172P	1.85
2N3054	60	MC1327	1.70	TA7173P	1.85
2N3055	60	MC1351P	2.93	TA7176P	2.50
2N3702	11	MC1330P	90	TA7202P	4.27
2N3703	10	MC1349	1.99	TA7204P	3.77
2N3705	10	MC1350	1.50	TA7205AP	3.72
2N3706	10	MC1352	1.75	TA7208P	3.40
2N3708	17	MC1358P	1.50	TA7210P	6.60
2N5294	48	MC1495L	3.00	TA7222	2.42
2N5296	48	MC13002	3.90	TA7223P	3.74
2N5298	69	MC14011BCP	66	TA7227P	5.98
2N5299	1.66	MC14049UB	43	TA7228P	5.98
2N5496	53	MC1742	1.35	TA7310P	2.78
2N6107	75	MC7812	1.35	TA7609P	4.39
2N6109	81	ML231	2.20	TA7611AP	2.92
2SA715	1.98	ETTR6016	2.20	TAA300	58
2SC495	1.10	ML232	2.20	TAA310	2.83
2SC496	1.31	ML236	5.35	TAA320	2.00
2SC643A	1.50	ML237	2.50	TAA550	55
2SC1096	1.72	ML238	6.00	TAA630	3.90
2SC1172Y	2.20	ML239	2.50	TAA8400S1	1.96
2SC1173Y	1.69	ML920	4.12	TAA661B	1.20
2SC1306	2.73	ML922	3.29	TBA120A	80
2SC1307	3.00	ML926	2.18	(A),(S),(AS),(SA)	
2SC1449	1.67	ML928	2.18	TBA120B	1.30
2SC1520	68	MM5387ANN	4.15	TBA120S	1.37
2SC1678	2.67	MM5402N	6.85	TBA120T	95
2SC1909	2.90	MRF475	2.50	TBA120U	1.10
2SC1953	1.44	MRF477	10.00	TBA395	1.20
2SC2028	1.82	MSN6807	7.87	TBA396	80
2SC2029	2.60	MS1513L	2.80	TBA440N	2.75
2SC2078	2.90	MS1515L	3.28	(TBA1441)	
2SC2091	1.34	SA1025	4.40	TBA440P	2.50
2SC2166	2.73	SA1124	2.50	TBA480Q	1.50
DEC1	2.20	SA1250	3.94	TBA510	3.00
DEC2	2.20	SA1251	4.90	TBA520(O)	1.68
THY15/80	2.20	SA1500	4.39	TBA530(O)	1.38
THY15/85	2.20	SA5010	6.30	TBA540	1.68
BU206B	2.20	SA5012	6.50	TBA550(O)	1.58
BUW81A	3.84	SA5020	5.90	TBA560Q	1.59
		SA5030	8.25	TBA570	1.79
		SA5050	8.50	TBA690	1.50
		SA3210	2.93	TBA641BX1	3.50
		SAS560S	1.89	TBA673	2.45
		SAS570S	1.89	TBA700	2.12
		SAS660	3.25	TBA720	2.64
		SAS670	3.25	TBA750	2.98
		SAS580	2.90	TBA800	1.62
		SAS590	2.90	TBA810AS	1.10
		SL901B	5.50	TBA820	1.70
		SL917B	6.50	TBA920M	1.25
		SL1310	1.80	TBA900	3.94
		SL1327Q	1.20	TBA920(O)	3.00
		SL1430	1.25	TBA950(2X)	3.05
		SL1432	3.36	TBA970	4.09
		SL76544	2.05	TBA990	1.90

We will try to supply the original part when we can. Under certain circumstances we may have to supply an equivalent.

DIODES

AA119	9	UPC1168C	1.28
BA102	17	UPC1176C	1.46
BA115	13	UPC1177H	1.56
BA145	17	UPC1178C	1.28
BA148	17	UPC1180C	1.84
BA154	6	UPC1181H	1.62
BA155	14	UPC1182H	2.95
BA156	15	UPC1183H	1.38
BA317	26	UPC1185H	3.86
BAX13	4	UPC1188H	2.20
BAX16	8	UPC1190G	1.20
BB1058	30	UPC1197C	1.06
BB1059	30	UPC1198C	84
BY126	12	UPC1200V	1.18
BY127	11	UPC1211V	2.70
BY133	15	UPC1212V	1.34
BY164	45	UPC1215V	1.68

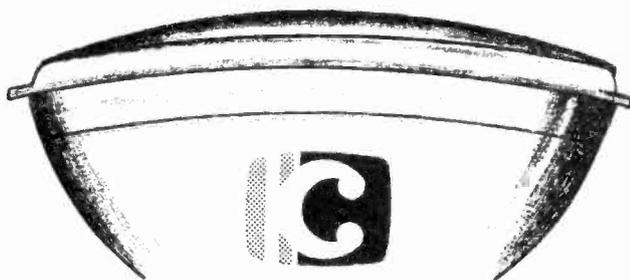

CHROMOVAC

**QUALITY
REBUILDS**

**SPECIAL
OFFERS**
THIS MONTH
ONLY



Get on the hot-line today!

SUPERIOR QUALITY TUBES

051

DELTA RE-BUILDS 428 8777

most types of Inline Re-builds or
new ex-stock

★ 2 YEAR WARRANTY
★ 4 YEAR OPTIONAL

Delta Rebuilds

Up to 19" £24
Up to 22" £28
Up to 26" £32
110° up to 22" £32
110° up to 26" £34
Low focus £30
A47 342 New £32
Delta only. Less 7½% 5+
Less 10% 10+ and over

Inline Rebuilds

Up to 22" £40
Up to 26" £45
Bonded Coil +£5

ALL SIZES OF
NEW MONO TUBES
AT COMPETITIVE
PRICES

IN LINE TYPES EX-STOCK SELECTION NOT REBUILDS

370 HFB £45
370 HUB £45
420 CSB £45
420 EDB £45
420 EZB £45
420 ERB £45
510 UFB/A51-590 £55
A51-570 £55
A51-210 £55
510 VSB £60
AXT 51-001 £60
560 DYB £62
560 EGB £62
560 CGB £62

560 DMB £62
AXT 56-001 £62
560 ATB £65
660 AB £65
A67-701 £65
670 CZB £65
H6817 £65

CARRIAGE
£5 Singles. 2-3 £10. 4 £12
10 £15. 10+ Carriage paid
EXCLUSIVE OF VAT
TERMS
Cash with order

QUANTITY
DISCOUNT
AVAILABLE
Ask for details

★ OUR TECHNICAL DEPT. WILL ADVISE YOU ON
PROBLEMS. YOU MAY ENCOUNTER ON FITTING
INLINE TUBES

DELIVERY: Ex stock items immediate dispatch on receipt of order.
Others allow 14 days.

THE COMPANY WHO PUT HIGH STANDARDS FIRST

CHROMOVAC

CHROMOVAC LTD. UNIT 7, BEAR BRAND COMPLEX,
ALLERTON ROAD, WOOLTON, LIVERPOOL 25
Ask for MR BUTTERWORTH ON: 051-428 8777

**FREE CAREER
BOOKLET**

Train for success in Electronics
Engineering, T.V. Servicing,
Electrical Engineering—or running
your own business!

ICS have helped thousands of ambitious people to
move up into higher paid, more secure jobs in the
fields of electronics, T.V., electrical engineering—now
it can be your turn. Whether you are a newcomer to
the field or already working in these industries, ICS
can provide you with the specialised training so
essential to success.

Personal Tuition and 80 Years of Success

The expert and personal guidance by fully qualified
tutors, backed by the long ICS record of success, is
the key to our outstanding performance in the
technical field. You study at the time and pace that
suits you best and in your own home.

You study the subjects you enjoy, receive a formal
Diploma, and you're ready for that better job, better
pay.

**TICK THE FREE BOOKLET YOU
WANT AND POST TODAY**

**ELECTRONICS
ENGINEERING**

A Diploma Course, recognised
by the Institute of Engineers
& Technicians as meeting all
academic standards for
application as an Associate.

**T.V. & AUDIO
SERVICING**

A Diploma Course, training
you in all aspects of installing,
maintaining and repairing T.V.
and Audio equipment,
domestic and industrial.

**ELECTRICAL
ENGINEERING**

A further Diploma Course
recognised by the Institute of
Engineers & Technicians, also
covering business aspects of
electrical contracting.

**RUNNING YOUR
OWN BUSINESS**

If running your own
electronics, T.V. servicing or
electrical business appeals,
then this Diploma Course
trains you in the vital business
knowledge and techniques
you'll need.

Name

Address

ICS ICS
Dept. EGSA4
160 Stewarts Road,
London SW8 4UJ.



01-622 9911
(all hours)

SEMICONDUCTORS

Part No.	£	Part No.	£	Part No.	£
16029		2SA699A		2SC1678	
16039	0.79	2SA715	0.98	2SC1758	1.08
16040	0.79	2SA72	0.76	2SC1829	0.46
16041	1.08	2SA73	0.47	2SC1871A	3.20
16334	1.02	2SB112	0.52	2SC1909	4.50
16335	0.64	2SB163	0.52	2SC1923	1.23
1N4001	0.79	2SB175	0.62	2SC1929	0.31
1N4002	0.05	2SB186	0.52	2SC1945	0.68
1N4003	0.05	2SB337	1.86	2SC1953	2.97
1N4004	0.05	2SB370	0.52	2SC1957	0.75
1N4005	0.06	2SB405	0.52	2SC1969	0.79
1N4006	0.06	2SB411	1.90	2SC1975	2.89
1N4007	0.07	2SB492	1.98	2SC2028	0.94
1N4148	0.07	2SB54	0.42	2SC2029	0.75
1N4448	0.03	2SB56	0.43	2SC2078	2.06
1N5401	0.08	2SB561	0.61	2SC2091	1.15
1N5402	0.12	2SB600	2.11	2SC2093	0.73
1N5404	0.13	2SB633T	2.47	2SC2122A	2.93
1N5406	0.15	2SB686	0.46	2SC2166	3.22
1N5408	0.18	2SB75	0.51	2SC2230	1.23
1N914	0.18	2SB77	2.02	2SC2314	1.23
1SV50	0.04	2SC1004A	1.86	2SC2355	1.23
2N3053	0.33	2SC1030	0.70	2SC2353	1.23
2N3054	0.33	2SC1096	0.96	2SC2353	1.23
2N3055	0.83	2SC1098	2.08	2SC2353	1.23
2N3703	0.69	2SC1152	1.98	2SC2353	1.23
2N3704	0.12	2SC1161	1.80	2SC2353	1.23
2N3705	0.15	2SC1172Y	0.91	2SC2353	1.23
2N3773	0.15	2SC1173Y	0.91	2SC2353	1.23
2N4444	3.04	2SC1222L	0.91	2SC2353	1.23
2N5296	1.10	2SC1237	0.91	2SC2353	1.23
2N5496	0.45	2SC1279	0.91	2SC2353	1.23
2SA102	0.57	2SC1337	0.91	2SC2353	1.23
2SA104	0.47	2SC1337	0.91	2SC2353	1.23
2SA1156	0.47	2SC1337	0.91	2SC2353	1.23
2A1232	0.74	2SC1337	0.91	2SC2353	1.23
1198	2.60	2SC1337	0.91	2SC2353	1.23
201	0.42	2SC1337	0.91	2SC2353	1.23
202	0.52	2SC1337	0.91	2SC2353	1.23
203	0.42	2SC1337	0.91	2SC2353	1.23
204	0.42	2SC1337	0.91	2SC2353	1.23


Phone (0945) 63281

For Issue 2 of our free Component Wallchart

Anglia

CONSUMER

Burdett Road,
Wisbech,
Cams. PE13 2PS

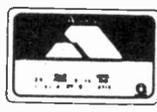

UPC1360C	3.15
UPC1363C	3.99
UPC1365C	3.61
UPC1366C	5.24
UPC1367C	3.06
UPC1368H2	3.45
UPC1370C2	4.49
UPC1373H	4.29
UPC1378H	1.11
UPC1382C	4.49
UPC1384C	1.97
UPC1447H	6.29
UPC2002V	0.98
	1.45

Don't forget to ask for your DRO

EAST CORNWALL COMPONENTS

ZENER DIODES	
400mV Plastic 3V-75V	8p each, 10/75p
1.3W Plastic 3V-200V	15p each, 10/15p
1.5W Flange 4.7-47V	£1.40
2.5W Plastic 7.5-75V	£1.26 each
20W Stud 7.5-75V	87p each

INTEGRATED CIRCUITS	
AN240P	3.42 SN76226D 1.80
AN214Q	3.88 SN76227N 1.10
AN715Q	2.90 SN76530P 1.40
CA3065	1.75 SN76533N 1.60
CA4031P	2.88 SN76680N 0.75
CA4102	3.32 SN76680N 0.75
CA4250	3.50 SN76686N 0.80
CA4400	2.98 SKT015 6.50
CA4422	3.07 TA1708P 3.20
LC7120	5.33 TA7120P 2.20
LC7130	5.28 TA7130P 2.20
LC7137	5.16 TA7130P 1.65
LM380N	0.80 TA7172 1.80
LM1303N	2.52 TA7193 5.50
HA1151P	3.12 TA7172P 1.80
MC1307P	1.85 TA7176 2.50
MC1310P	1.85 TA7202P 4.10
MC1312P	1.50 TA7204P 1.86
MC1327P	1.25 TA7205AP 1.50
MC1330P	0.83 TA7208P 3.27
MC1349P	1.85 TA7210P 6.50
MC1350P	1.20 TA7222P 1.88
MC1351P	2.50 TA7230P 3.80
MC1352P	1.50 TA7237P 1.60
MC1357P	2.88 TA7310P 0.80
MC1358P	1.30 TA7609P 4.28
MC1496L	1.15 TA7611AP 2.88
ML231B	2.10 TA2623 2.48
ML232B	2.10 TA310A 2.68
ML237B	2.30 TA4550 3.38
MRP475	5.35 TA570 2.80
MRP475	5.20 TA611A12 3.50
MRP477	1.00 TA6630S 3.90
NE555	0.25 TA6818 1.70
C-mos 555	0.88 TA700 2.80
NE566	0.90 TA720P 1.30
SAA1024	5.35 TA100 2.80
SAA1025	8.40 FM FILTER 1.20
SA5560A	2.50 TBA120 AS 1.30
SA5560S	1.85 S.S.A.SB 1.30
SA5570S	1.85 Q.T.U.U.Q 1.32
SA5580	2.85 TBA120B 1.30
SA5590	2.85 TBA231 1.45
SC9503P	1.10 TBA281 2.65
SL432A	4.00 TBA395 1.20
SL901B	5.20 TBA480Q 1.50
SL917B	7.25 TBA400 2.30
SN1327Q	1.10 TBA120 1.30
SN16003N	2.44 TBA510Q 2.60
SN76013N	1.90 TBA520/Q 1.60
SN76023ND	2.90 TBA530/Q 1.30
SN76033N	2.45 TBA540/Q 1.40
SN76110N	1.12 TBA550/Q 1.52
SN76115N	2.00 TBA560/Q 1.60
SN76131N	1.65 TBA560/Q 1.60

UBA570	1.50	UPC1181H	1.60
TBA618X1	4.50	UPC1185H2	3.75
TBA673	2.40	UPC1212C	1.30
TBA700	2.85	UPC1230H	1.90
TBA750	2.80	UPC1350C	4.25
TBA800	1.60	UPC1357C	4.40
TBA820P	1.10	UPC1378H	4.40
TBA110S	1.20	UPC202H	2.80

PLUGS & SOCKETS	
Metal Cover Plug 0.18	1.88
Plastic Coax Plug 0.14	3.00
Mini Line Socket 0.50	3.90
Single Jack	4.00
Socket	0.80
Plastic Phone 0.10	3.12
F.M. Plugs	1.85
P.255 Plugs	0.20
Reducer	0.15

SOLDERING SECTION	
Antex 15W iron 5.00	7.00
Antex 18W iron 5.20	7.00
Antex 25W iron 5.00	7.00
Antex elements 2.00	4.50
Antex bits 0.95	3.50
Antex stands 1.90	2.70
Soldersucker 4.50	0.65
Nozzles	0.50

PRESETS	
0.25W Type 100R-4M7	2.50
W & H 10p ea. 10/90p	2.98
0.1W Type 100R-1M	2.98
W & H 7p ea. 10/65p	3.20

TERMINAL BLOCKS	
2 amp 12 way	0.19
5 amp 12 way	0.20
10 amp 12 way	0.40
15 amp 12 way	0.46
32 amp 12 way	0.90

NI-CAD	
Universal Ni-Cad charger, charges PP3, AA, C, D	£5.00



MULTIMETER SPECIAL
 Russian type U4324 (20,000 O.P.V.)
 DC Volts: 0.6, 1.2, 3, 12, 30, 60, 600, 1200.
 AC Volts: 3, 6, 15, 60, 150, 300, 600, 900.
 DC Curr. M/A: 0.06, 0.6, 6, 30, 300, 3000.
 AC Curr. M/A: 0.3, 3, 30, 300, 3000.
 DC Resistance: 0.2, 5, 50, 500, 5000K.
 level dB: -10 to +12
 Supplied with rechargeable batteries.
 Price £12.00 incl. of p/p & VAT.

TELEPHONE SPECIAL
 B.T. Approved Telephone Plug & 4-core Lead £1.50
 B.T. Approved Telephone Secondary Socket £3.20
 B.T. Plug only £0.85

NI-CAD CHARGER
 Universal Ni-Cad charger, charges PP3, AA, C, D
 Price £5.00

Rechargeable Batteries
 PP3 £4.45 / £16.00
 AA £0.95 / £8.00
 HP11 £2.30 / £8.50
 HP2 £2.35 / £8.75

CHART RECORDER SPECIAL
 brand new 3 channel pen recorder, complete with charts. Full spec. upon request only
 price £40 + £10 p/p & VAT.

FUSES Prices per 10
 1 1/2" Quick Blow, 100, 150, 250mA £1.30, 1.1, 1.25, 1.5, 2, 2.5, 3, 10, 15A
 55p, 1" Time Delay, 100mA £3.50, 150mA £2.25, 250, 300, 500, 600, 750, 800mA £1.84, 1.1, 1.25, 1.5, 1.6, 2A £1.84, 2.5A, 3.15, 3.5A £2.82.
 20mm Quick Blow, 100, 125, 160, 200, 250, 315, 400, 500, 630, 800mA.
 1.1, 1.25, 1.5, 2, 2.5, 3.15, 4, 5, 6.3A, 40p, 20mm Time Delay, 100, 125, 150, 160, 200mA £1.80, 250, 315, 400, 500, 630, 800mA, £1.00, 1.1, 1.25, 1.6, 2, 2.5, 3.15, 4, 5, 6.3A 85p, 1" Mains, 2, 3, 5, 7, 10, 13A 85p.
 Manufacturers please note - we can offer very competitive prices. Quantities of 20mm Quick Blow & Time Delay range - apply for quotation.

REPLACEMENT TV MAINS DROPPERS
 GEC2010 6R + 15R + 17R + 70R + 63R + 188R 0.95
 GEC 2018 1R + 15R + 19R + 70R + 188R 1.15
 Philips 6B 22R + 58 R 0.80
 Philips 70A 6R + 12R + 84R 1.68
 Philips 300 118R + 148R (with link) 0.85
 Philips 300 30R + 125R + 2.85K 1.08
 RRI A640 250R + 14R + 156R 50W 1.05
 RRI A810 302R + 70R + 6.2R 0.78
 Thorn 1500/3500 6R + 1R + 100R Fused 1.25
 Thorn 8000 56R + 1K + 47R + 12R 0.95
 Thorn 8500 1K5 + 40R + 50R 1.28

MULTISECTION ELECTROLYTICS
 THORN 850 100+300+100+16/300V 1.80
 1400 150+100+100+100+150/320V 1.20
 150 150+150+100/300V 30.00
 3000 100/60V 0.56
 3500 170/40V+100+100/350V 1.70
 8000 400/350V 2.10
 8000/8500 2500+2500/63V 1.35
 8000 700/250V 2.10
 1000/70V 2.05
 9000 400/400V 0.28
 9000 200/250V 1.50
 Timer Amp 4700/25V 0.52
 DECCA/03/30/400+350V 3.70
 GEC 2047 2048 2083 2084 2104 2.22
 200+200+150+50/300V 0.75
 600/250V 1.95
 ITT/KB 220/100V 2.15
 200+200+75+25/350V 1.5
 PHILIPS G8 600/300V 1.70
 G8 G9 600/300V 1.50
 300+300/300V 1.50
 G9 220/63V 1.25
 EKCO T148 125+200+100+32/275V 1.65
 691 Series 200+300/350V 2.10
 600/300V 1.80
 RANK 300+300/300V 2.05
 AB23 2500+2500/30V 0.95
 220/400V 1.78
 600/300V 1.78

I.C. SOCKETS
 D11 to D11 8 pin 0.08 0.70/10
 14 pin 0.10 0.95/10
 16 pin 0.11 1.00/10
 22 pin 0.21 1.95/10
 28 pin 0.30 2.75/10
 40 pin 0.34 3.10/10

CO-AXIAL CABLE
 50ohm UR43 type 34p per metre
 75ohm UR202 type 22p per metre
MINIATURE MULTI-CORE
 4-core 37p per metre
 5-core 45p per metre

TWIN FIGURE 8
 Grey & Clear 10p per metre
TEST LEAD WIRE
 Red & Black 38p per metre

Fuseholders
 20mm Panel Mounting 0.28
 20mm Chassis Mounting 0.06
 1" Panel Mounting 0.35
 1" Chassis Mounting 0.10
 Carline 1" holder 0.10

SERVICE AIDS Excel Polish 0.76
 ALL SERVICE/ Fire Extinguisher 0.80
 PRODUCTS 640g 2.80
 Switch Cleaner 0.88 Video Head 0.88
 Circuit Fuzzer 0.96 Cleaner 0.88
 Foam Cleaner 0.84 Solids Mop (Std) 0.72
 Aero Klene 0.78 Solde Mop 1.12
 Silicone Grease (L/Gauge) 0.72
 (Tube) 1.60 HeatSink Comp 1.06
 Antistatic Spray 82 Additional P&P on Plastic Seal 0.88 above 30p 0.22

RESISTORS - CARBON FILM 5%
 1W R2 to 10M (E2 Range) 2p each 15p/10 75p/100
 1W R2 to 10M (E4 Range) 2p each 15p/10 75p/100
 1W R2 to 10M (E6 Range) 7p each 65p/10 6.00/100
 2W R2 to 10M (E2 Range) 8p each 15p/10 75p/100

RESISTOR KITS - each value individually packed
 1W pack 10 each value E12 - 10R to 1M 610 pieces 5.00
 1W pack 10 each value E24 - 10R to 1M 358 pieces 3.00
 1W pack 10 each value E12 - 2R to 2M 735 pieces 6.00
 1W pack 5 each value E12 - 2R to 2M 365 pieces 3.50
 1W pack 5 each value E12 - 2R to 1M 353 pieces 18.00
 2W pack 5 each value E6 - 10R to 2M 317 pieces 18.00

RESISTORS - WIREWOUND, Generally 5%
 2.5W - 0.22 to 270R - Available in preferred values 0.20
 1W - 10R to 10K - Available in preferred values 0.21
 0.5W - 0.47R to 22K - Available in preferred values 0.25
 0.1W - 10R to 22K - Available in preferred values 0.29
 17W - 10R to 22K - Available in preferred values 0.37

VDRs, etc.	
E296Z2	0.28
017	0.28
E298CD	0.25
1/2A58	0.22
E298ED	0.22
1/2A58	0.22
A/262	0.22
A/262	0.22
A/265	0.22
FP268	0.22

E298Z2	
39/40/53 all 0.20	
E299DD/P116-	
P354	all 0.23
E299DH	
/P230	0.72
VA1015	0.20
VA1015/09/12	
VA1015/34/38Z	
VA1033/34/38Z	
VA1055/56/66/8/8	
675	all 0.23
VA1074	0.20
VA1077	0.31
VA1091	0.29

E298Z2	
VA1096/97/98	all 0.20
VA1103	0.32
VA1104	0.66
VA1108/09/10/11/12	all 0.24
VA8650	1.20
2322 554	
02271	0.59

RESISTORS - CARBON FILM 5%	
1W R2 to 10M (E2 Range)	2p each 15p/10 75p/100
1W R2 to 10M (E4 Range)	2p each 15p/10 75p/100
1W R2 to 10M (E6 Range)	7p each 65p/10 6.00/100


RESISTOR KITS	
1W pack 10 each value E12 - 10R to 1M 610 pieces	5.00
1W pack 10 each value E24 - 10R to 1M 358 pieces	3.00
1W pack 10 each value E12 - 2R to 2M 735 pieces	6.00
1W pack 5 each value E12 - 2R to 2M 365 pieces	3.50
1W pack 5 each value E12 - 2R to 1M 353 pieces	18.00
2W pack 5 each value E6 - 10R to 2M 317 pieces	18.00

RESISTORS - WIREWOUND, Generally 5%	
2.5W - 0.22 to 270R - Available in preferred values	0.20
1W - 10R to 10K - Available in preferred values	0.21
0.5W - 0.47R to 22K - Available in preferred values	0.25
0.1W - 10R to 22K - Available in preferred values	0.29
17W - 10R to 22K - Available in preferred values	0.37

D CONNECTORS	
9 15 25	way way way
Male	way way way
Solder	
75	1.00 1.50
33	Angle
1.40	2.00 2.40
Female	
Solder	
1.00	1.45 1.85
Angle	
1.50	2.00 2.40
Covers	
80	80 80

CAPACITORS	
Metallised Paper	
2n2F 500V AC 24p	
10nF 1000V DC 22p	
15nF 500V AC 80p	
15nF 300V AC 30p	
22nF 300V AC 32p	
100nF 1000V DC	
46p	
25C1302	1.40
HV Disc Ceramic (1)	
1kV 1.5nF	18p
8kV 10, 47, 56p	
82, 100, 120, 150, 180, 200, 220pF 30p	
270, 300pF	39p

VALVES	
DY802	0.88
DY86/87	0.75
ECC81	0.95
ECC82	0.85
ECC83	0.85
ECC84	0.65
ECC85	0.90
ECC88	0.95
ECF80	0.95
ECH81	0.75
ECH84	0.75
ECL82	0.75
ECL86	0.98
EF80	0.85
EF86	1.60
EF183	0.75
EF184	0.75
EH90	0.94
EL34	2.50
EL84	0.84
EL509	5.50
EM87	2.55
EV86/87	0.87
EV500A	1.65
PCC84	0.50
PCCB5	0.85
PCC89	0.74
PC1189	0.80
PCF80	0.75
PCF86	1.25
PCF200	1.95
PCF801	1.45
PCF802	0.85
PCF806	1.20
PCL82	0.90
PCL84	0.90
PCL86	0.98
PCL805/85	1.35
PD500	3.75
PFL200	1.35
PL33	1.50
PL36	1.45
PL81	0.85
PL82	0.75
PL83	0.65
PL84	0.75
PL95	2.00
PL504	1.20
PL508	2

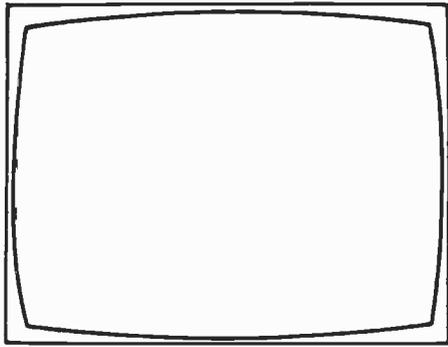

TELEVISION

EDITOR

John A. Reddihough

ADVERTISEMENT MANAGER

Roy Smith
01-261 6671

CLASSIFIED ADVERTISEMENTS

Barbara Blake
01-261 5897

Same old story

Two recently published reports draw attention to shortcomings in education and industrial training in the UK. The first, entitled *Competence and Competition*, was produced by the Institute of Manpower Studies for the National Economic Development Office and the Manpower Services Commission. It's the first report to have made a detailed comparison between education and training in the UK and its leading industrial competitors, the USA, W. Germany and Japan. The second, *Crisis Facing UK Information Technology*, has been published by the Economic Development Committee for the industry. It's scope is wider, covering research and development, investment policies and the availability of finance, but when it touches on labour it highlights the "acute national shortage of people with IT-related skills".

The reaction of many will probably be that there's nothing new about this. Reports published over the years have drawn attention to the same failings and have met with varying responses. Yet the Institute of Manpower Studies' report is particularly disturbing in that it relates education and training to economic and industrial performance. This is something that's not possible of precise analysis however. You can't say that if the UK had had X number of extra scientists/engineers it would have benefited by a measurable amount, or that because Japan has say X number of extra engineers in a particular industry that industry has done measurably better. It all depends on what you do with trained manpower for a start, and the policies and priorities of those who control investment and industry. Nevertheless an adequate supply of trained manpower is a basic essential, and one's heard growing complaints from the UK electronics industry in particular in recent years about the lack of graduates with engineering qualifications. There's a deeper and more worrying problem here. A marked improvement can't be achieved until graduates have acquired industrial experience and had a chance to permeate management and influence policy and investment decisions. To merely double the output of engineering graduates will have no lasting effect until it's possible to make full use of them. An increase is an essential first step however. The long-term problem is whether we might already have left it too late. Will the UK, as the IT report seems to suggest, have declined to "Third World status" before anything can be done? Have we already reached the point of "industrial no return"?

The problem is not only one of a shortage of graduates of course. Skills of all kinds are required if modern, technologically-orientated industry is to operate effectively. It's profoundly disturbing that the efforts of so many over a very long time to produce relevant courses, training and qualifications seem to have had so little impact. We have excellent institutions concerned with training and setting standards for engineers and technicians, yet the system has failed to deliver the goods.

The IMS study makes one feel that there may be a deeper problem. After all we're not Japanese or Germans. Maybe as a nation we are less disciplined, less motivated, less work orientated? Perhaps we place a greater value on freedom and doing our own thing in our own way? This can be beneficial. The UK has not lacked inventiveness and, when the crunch comes, we very often manage to get things done. Be that as it may the problem remains, and is starkly brought out in both these reports, that our main competitors have a great lead in training and industrial strategy, a fact that has very worrying implications for the future.

It's sometimes argued that there is no great advantage in duplicating the efforts of others. Why not buy in technology as required? There are two problems with this approach. First, if industry fails to develop new goods and technology it loses the benefits of experience and know-how. You could, over a number of years, reach a position where goods whose design and operation are not understood are merely being screwed together in the UK. This danger is known, but the question is whether the scale of the effort to overcome it is anywhere near sufficient. The second problem is that production engineering is not a UK strong-point, so that a future as an assembler of goods designed elsewhere doesn't hold out much hope.

There are several related issues. For example, who is to pay for increased expenditure on training? Firms understandably don't like spending a lot on training people who promptly go off elsewhere. The answer to that one is possibly in motivation and providing interesting jobs and career structures. All of which is easier said than done, especially when industry is strapped for funds as it often is. Perhaps there should be increased training levies? This again raises difficulties - it means that some firms are in effect being asked to subsidise the training requirements of others. All this is quite likely to lead to a situation where government blames industry for its failure to take the initiative while industry blames the government for exactly the same thing. Oh yes, and we all blame the educational system.

At least the reports mentioned have drawn attention to the real and long-term problems. The usual UK reaction is that it'll be all right on the day and that somehow we'll muddle through. There's reason to doubt whether our luck will hold this time. Nor is education and training the only aspect of the matter. There's also the problem of flexibility in work practice and employee deployment. This is a field where union restrictions and worker/management attitudes come in. In the short term, making the maximum use of the skill resources we've got is the only solution open to us.

CORRECTION - VIDEO INFO CARD 1

The audio output pins with a 5-pin DIN socket wired for mono operation are 3 and 5, not 3 and 4 as printed in this month's data card.

BUMPER ISSUE

The November issue will again have extra pages - and Video Info Card 2.

FRONT COVER

Our thanks to Crow of Reading Ltd. who kindly supplied the photograph of the Barco CTVM3 series monitor reproduced on this month's front cover.

System A Modulator

David Looser

With the impending close down of the 405-line transmitter network those of us with collections of early TV sets are having to make new arrangements to supply them with suitable signals. Typical of such initiatives is the method of recording 405-line video signals on tape described by Gareth Foster in the October 1983 issue. Whatever the scheme used, some method of converting baseband audio and video into a form suitable for feeding into the set's aerial socket is required.

The modulator described in this article was designed to perform this task with little degradation of the signal. Separate carrier generators and modulators are used for the sound and vision for best possible sound-on-vision and vision-on-sound performance. Crystal control of the oscillators was chosen to ensure stability and reduce alignment problems. The choice of Channel 1 (41.5MHz sound, 45MHz vision) was made because the vast majority of 405-line TV sets, including all pre-war models, can operate on this channel. Those with one of the few Ch. 4 "Birmingham" models of the late 40s should be able to modify the design for 58.25MHz sound and 61.75MHz vision without much difficulty.

Circuit Operation

Fig. 1 shows the vision modulator circuit. The 1V peak-to-peak video input is first amplified by Tr1/2 and then fed via the emitter-follower Tr3 to the d.c. restorer Tr4. The potentiometer in Tr4's base circuit varies the modulator bias and is adjusted so that the carrier is just extinguished on the sync pulse tips. Tr5 is connected in a Butler oscillator circuit operating at 45MHz. The output from the modulator chip is transformer coupled to the output socket via a 10dB pad and a 6dB combining network. The 10dB pads in this and the sound modulator circuit act as isolators to protect each modulator from the other's r.f. output.

The sound modulator circuit (see Fig. 2) is similar, with IC2 driving the modulator chip in push-pull to reduce distortion to a minimum. The audio sensitivity of 1V r.m.s. = 100 per cent modulation is set by the value of R1, which can be varied if desired. For example, with R1 at 100k Ω 100 per cent modulation is achieved with a 200mV r.m.s. input; with R1 at 1M Ω 2V r.m.s. equals 100 per cent modulation. The quiescent carrier level is set by the two biasing networks connected to the audio input pins 1 and 4 of the MC1496.

Both modulators generate 800mV of r.f. across the secondary windings of the output transformers T2 and T4 under maximum modulation conditions (peak white for video and the positive peak of a 1V sine wave for audio). Each modulator thus produces about 130mV of r.f. at the output socket, so about 20dB of extra attenuation will be needed when this is connected directly to the aerial socket of a set. This allows several sets to be driven via a passive splitter network if required.

It will be noticed from the above that the peak vision to average sound power ratio is 6dB (4:1) rather than the correct 7dB (5:1). This has never caused problems with any set I've used, but purists may if they wish increase the

loss in the sound modulator's output pad from 10dB to 11dB.

Construction

The prototype was constructed on a single Veroboard Eurocard with a "colander" ground plane. This is available from Verospeed (stock no. 10-2845H) but is fairly expensive (£5.60 trade). An alternative would be to use "solid construction" on a piece of plain copperclad board about 4 x 6in., preferably glassfibre. Start by fixing the coil formers to the copper side of the board, then glue the MC1496s to the board upside down. All the wire-ended components can then be soldered directly to the appropriate i.c. pins. A small soldering iron and a steady hand are essential. The video amplifier/d.c. restorer and the audio amplifier can be built on a small piece of Veroboard which is then mounted on the main board.

The transistor types are not critical. I used those specified because they were to hand. Any r.f. types should be suitable for the oscillators and any small-signal silicon general-purpose types for the video section. The non-electrolytic capacitors are all miniature ceramic types and the polarised capacitors bead tantalum or low-leakage electrolytics. The resistors are 0.25W, 5 per cent carbon or metal film types and the crystals were made to order by IQD Electronics - they cost about £6 each.

The transformers are constructed as follows. T1 and T3 have a primary consisting of 15 turns of 26 s.w.g. wire close wound on a 6mm former with a dust core. The secondaries consist of two turns of 26 s.w.g. wound over the "cold" end of the primary. T2 and T4 have primaries consisting of 12 turns of 26 s.w.g. close wound on a 6mm former with a dust core and a centre tap. The secondaries consist of three turns wound over the centre of the coil.

Alignment

Three alignment methods are possible depending on the equipment available.

The first method requires a video source (preferably a line repetitive waveform covering the full grey scale, such as a wedge or step-wedge pattern), an audio signal generator with an output adjustable over the range 0-1V, and an oscilloscope with a bandwidth of at least 50MHz. Connect the scope across the secondary of T2 and apply 12V d.c. to the vision modulator only. Adjust T1 and T2 for maximum r.f. output. These adjustments are very broad and not difficult to make. If the maximum signal is reached with the cores fully in or out it may be worth trying a different value for the tuning capacitor C1 or varying the number of turns.

Connect the video pattern generator to the video input and synchronise the scope's timebase to this input. Adjust the video bias control so that the r.f. output drops to zero, or as close to zero as possible, during the sync pulses. The scope should now display the modulated r.f. envelope shown in Fig. 3.

Transfer the scope to the secondary of T4 and the 12V supply to the sound modulator. Adjust T3 and T4 for

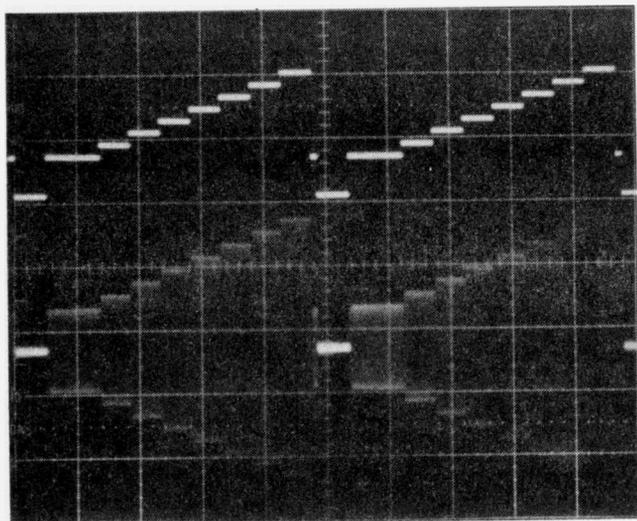


Fig. 3: Alignment traces: upper, video input, 0.5V/cm; lower, r.f. envelope, 200mV/cm.

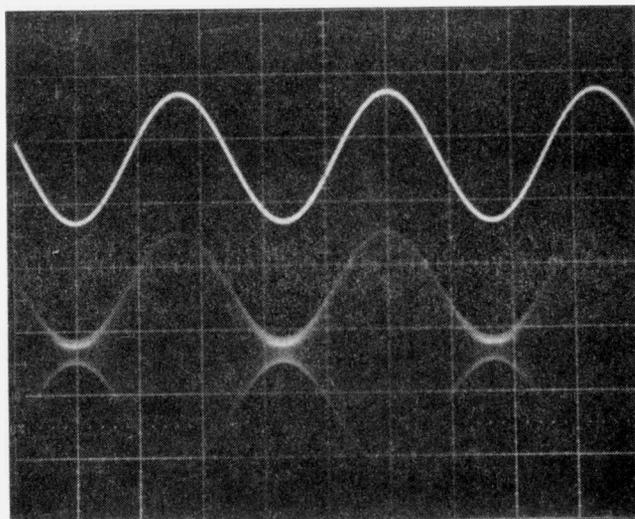


Fig. 4: Alignment traces: upper, sound sinewave input, 0.5V/cm; lower, r.f. envelope, 200mV/cm.

that the sync pulses crush, then back off the adjustment until the pulses regain their maximum amplitude. Check that the whites are not compressed – if necessary reduce the TV set's r.f. gain to ensure that this does not happen.

Connect an audio tone to the modulator's audio input socket. This tone should be heard from the speaker. Tune T3 and T4 for maximum output.

The third method requires a source of 405-line video, e.g. a pattern generator or tape, and a working 405-line

TV set. Connect the modulator to the video source and to the TV set (via a 20dB pad). Apply 12V to the modulator and tune it in on the TV set. Peak T1 and T2 for maximum contrast and adjust the video bias control for best grey-scale reproduction consistent with reliable synchronisation. It may be necessary to adjust the set's contrast control to make this possible. Connect an audio source, preferably a tone, to the modulator and adjust T3 and T4 for maximum volume.

Renovating the Philips N1700

Freddie Archer

Because the Philips N1700 is now obsolete, these machines can be obtained very cheaply, especially non-workers. I've renovated a number of them and would like to pass on the following tips on repairing these old but high-performance (when working!) VCRs.

A stock fault is a faulty head drum motor. They tend to develop tight bearings with age, something that can be aggravated by lack of lubrication of the head's own bearing. If the machine is working, check the voltage across the motor with the VCR switched to play but no tape inserted. The voltage should be $16V \pm 1.5V$. If it's more than 20V you'll soon have problems.

The next thing that happens is that the upper drum motor drive transistor TS201 (BD437) goes short-circuit collector-to-emitter due to overloading, thus placing the full 33V supply across the motor. When the BD437 goes short-circuit it usually does some damage to the U219 drum servo control module – typically cooked resistors, the partnering BD436 drive transistor going open-circuit and occasionally the 741 chip faulty. All this is repairable with care and replacements are available from Philips.

Now to the motor itself. Due to the tightness it may be unable to rotate the head drum at the correct speed. Before condemning it and buying a new one from Philips at around £30, try swapping over the drum and capstan motors! Crazy though this may sound, it usually works – the capstan motor leads an easier life and the two motors are identical. The pulley on the head drum motor can be a pig to remove. Once you've done all this and everything

works, clean and oil all that should be cleaned and oiled and you'll have little mechanical trouble in future use.

I've found that the signals sections are all very reliable. A problem that can occur is vertical lines appearing on heavily saturated primary colour scenes. The effect can be reduced by adjusting the chroma record current control R710. A compromise may be required due to chroma dropout.

The speed reduction modification described by Mike Phelan (*Television* April 1983) works quite well but is very dependent on 100 per cent good mechanics, which is not very likely on a four-six year old VCR.

Several problems can occur on the power supply/system control panel. Bad connections on IC101 ($\mu A723CA$) in the 12V regulator circuit can cause picture disturbance, a blank screen or over-saturated colour, all usually intermittent. Dry-joints on the electrolytics and bridge rectifiers can cause hum bars or a totally dead machine.

Bandpass video input and output are useful modifications to include. Articles on these appeared in the November 1979 and March 1981 issues of *Television*.

I hope these notes will help others to keep going what is probably the best luminance quality VCR that's been sold for domestic use. No other machine can achieve a 3MHz bandwidth without heavy peaking, which produces so much noise and ragged edges that in my opinion it's not worthwhile. Maybe I'm old-fashioned, but I'd rather see one hour of good quality vision than six or eight hours of muzzy, noisy pictures!

POST A PART ELECTRONICS

236 FURTHERWICK ROAD,
CANVEY ISLAND, ESSEX

Telephone 0268 690868
Telex 99305 ROSSER G.



TRADE COUNTER NOW OPEN

ORDERS DESPATCHED SAME DAY
ADD 60p P&P, THEN 15% VAT.

ADD POSTAGE FOR OVERSEAS ORDERS.
ORDERS WITH AEROSOLS, PLEASE ADD 25p PER CAN.

Thorn 100 20W (3500) R751 Safety Resistor	75p
Pye 713 Speaker 5" x 3" 701	1.00
Pye 713 Complete Tube Base Panel with Focus Slider & Leads	2.75
Pye 713 Control Knobs	4 for 50p
Tube Base Socket ITT CV32	50p
Tube Base Socket Thorn 3000/8000 etc	50p
IC Insertor 16 Pin	50p
Large IC Extractor	50p
Crystal 4.43MHz	65p
EHT Lead & Cap for Split Diode Lopt	90p
Anode Cap	47p
Sanyo Anode Cap Assy + Lead. 12TCD-CT-16	65p
Degauss Thermistors. PT37P. ITT/GEC	35p
Degauss VDR E299D/HP230 3000/8000	2.50
Casters Set of 4	1.90
Double Fuse Holder on Small Pax Board 20mm type	10p
Single Fuse Holder on Small Pax Board 20mm type	5p
Direct Panel Mounting 20mm Fuse Clips (pair)	15p
Single Fuse Holder on Small Pax Board. As per early 3000 mains input	6p
EHT Cable	Metre 25p
13A Plugs	12 for 4.80
BF259 with Heatsink	40p
TIP110 with Heatsink	40p
L129/130/131 Coil	10p
6MHz Ceramic Filter	25p
DL700 (Phonix) Chroma Delay Line	1.00
DL50 Chroma Delay Line	1.00
T9006A Lum. Delay Line	1.00
8K5/9K Lum. Delay Line	65p
Plastic Cover for 3K5 SP8385	5p
TX9 Back Ground Control 10K	15p
TX9 Gain Control 100R	15p
1500 Metal Chassis Supports Pair	4.00
Thorn 8K5 Focus Pot	2.40
Thorn 4000 Focus Pot	2.40
Thorn 182 9W (3K5) R752	30p

SERVICE AIDS

Ambersil MSA Silicone Grease	12oz 2.15
Ambersil Freezer	12oz 1.99
Ambersil Amberlube	6oz 1.89
Ambersil Ambertron	16oz 1.95
Ambersil Anti-Static Screen Cleaner	7oz 1.95
Ambersil 40+ Protective Lubricant	14.1oz 2.15
Ambersil Ambersilans Foaming Cleaner	13oz 1.26
Ambersil Circuit Lacquer	14oz 2.15

THICK FILM RESISTOR UNITS

3500 Thorn (5 Pin Connection) video	1.70
4000 Thorn (4 Pin Connection)	1.90
725/731 Pye (6 Pin Connection)	2.20
713 Pye (6 Pin Connection)	2.20

FUSES

20mm		1 1/2"	
50MA	10 for 70p	250MA	10 for 85p
315MA A/S	10 for 50p	750MA	10 for 65p
500MA	10 for 50p	7A	10 for 50p
1A	10 for 50p	10A	10 for 50p
2.5A	10 for 1.00	20A	10 for 50p
3.15A	10 for 1.00	50A	10 for 50p

Thorn Mains TX 3000/3500	7.50
Thorn Mains TX 8000/8500	10.00
Thorn S.D.P. 8000/8500	3.50
Thorn Scan TX 3000/3500	6.00
Thorn EHT TX 3000/3500	6.00
Thorn LPT 9600	12.00
Thorn LPT 1615	7.25
Thorn LPT 1590/91	7.25
Thorn LPT 1890/91	7.25
Thorn LPT 8000	9.00
Thorn LPT 8500	9.00
Thorn LPT TX9	9.85
Pye LPT 713	10.00
Pye LPT 725	9.85
Pye LPT 731	10.18
Philips LPT G9	8.80
Philips LPT G11	13.75
GEC LPT 3113	7.40
Diode Split LPT AT2076/35	14.75
Sanyo LPT AM-WM-21	6.75
Sanyo LPT AM-WM-4	7.30
Philips LPT G8	7.80
Sanyo LPT (CW21) 4-2751-44700	5.00
ITT LPT CV39	9.60
ITT LPT CV30	8.75
ITT LPT CV45	9.75
Baird 8750	10.25
Baird 8752	10.25
Korting AZ9100	10.25
Korting B92-170	10.25
Korting AZ2101	10.25
Korting AZ2103	10.25
Korting ZTR1001	10.25
Siemens V1155	11.75
Siemens V1152	11.75
Zanussi BS2222	10.25
Zanussi BS2223	10.25
Salora FR0057	10.25
Salora FR0029	10.25

300 Mixed Resistors	1.50
300 Mixed Capacitors	1.50
150 Mixed Electrolytics	2.00
100 W/W Resistors	1.00
20 Mixed Conv Pots	1.00
40 Mixed Pots	1.50
20 Mixed Sliders	1.00
40 Mixed Presets	60p
20 Mixed VDR & Thermistors	1.00
20 Mixed Ferrite Cores	50p
100 Mixed Ceramic Discs	1.00
20 Mixed Valve Bases	1.00

AC128	39	BC172	9	BC559	8
AC131	40	BC174B	23	BC595	8
AC138	40	BC177	24	BC633	22
AC141K	39	BC182LB	12	BC634	11
AC142K	38	BC183L	12	BD115	49
AC153	39	BC184L	13	BD131	30
AC176	33	BC187	24	BD132	16
AC178K/	35	BC204	15	BD133	59
AC128K	93	BC208	9	BD139	36
AC188	38	BC212L	9	BD140	38
AD142	1.18	BC213L	12	BD144	1.70
AD143	1.08	BC237	12	BD150	50
AD149	98	BC238B	8	BD163	98
AD161	32	BC238L	8	BD201	74
AD162	32	BC250A	78	BF224	78
AD263	1.05	BC251	8	BD203	78
AF127	45	BC252A	20	BD222	40
AF139	38	BC294	37	BD225	52
AF239	41	BC301	32	BD232	50
BC107	15	BC303	31	BD233	60
BC108	15	BC307	10	BD234	60
BC109	15	BC308	8	BD237	55
BC115	16	BC309	14	BD238	65
BC117	21	BC327	18	BD241	59
BC125	26	BC328	17	BD242	85
BC126	23	BC337	17	BD278A	81
BC139	27	BC338	17	BD386	68
BC141	34	BC347	8	BD433	71
BC142	30	BC394	8	BD437	83
BC143	31	BC454	8	BD592	1.20
BC147	12	BC455	8	BD589	1.20
BC148	12	BC456	10	BD677G	1.35
BC149	12	BC460	40	BD707	95
BC153	16	BC463	22	BD708	95
BC1540R	16	BC546	8	BDX10	93
BC154YL	16	BC547	12	BDY20	1.09
BC157	12	BC548	12	BDY82	99
BC158	12	BC549	8	BF137	20
BC159	15	BC557	10	BF153	20
BC171	9	BC558	10	BF154	25

INTEGRATED CIRCUITS

BRC1330	1.40	SN78013ND	1.80
BRC3064	1.00	SN78023N	1.80
BRC/M/200	1.00	SN78033N	2.00
BRC/M/300	1.00	SN78115	2.00
CA3060	1.58	SN78131N	1.58
LM1303P	1.48	SN78226N	1.25
ML231B	2.20	SN78227N	1.00
ML237B	2.00	SN78530P	1.30
ML239B	2.86	SN78622N	1.00
MC1327AP	1.25	SN78660N	80p
MC1358P	1.30	SN78666N	75p
MC1455P	18p	SN78744	1.92
MC14516BCP	60p	TA7117P	1.00
SAA1025	7.20	TA7109AP	2.80
SAA1124	4.50	TAA611	1.40
SAA5010	6.00	TBA1208	1.20
SL432A	1.80	TBA120C	1.20
SL1430	2.50	TBA120CQ	70p
SN15946N	60p	TBA120S	70p
SN74123N	65p	TBA120U	1.00
SN74154N	1.40	TBA395	1.00
SN78001N	1.40	TBA480Q	1.40
SN78110N	1.14	TBA510	1.90

Thorn 8/K5 ex equip panels	untested	Thorn 3/3K5 ex equip panels	untested
PSU	2.88	PSU	3.75
LTB	3.75	new	1.75
Video	4.00	Thorn 3K5 PSU bottom board	2.75
Chroma	2.00	PC206 new	2.75
FTB	2.75	Thorn 3K5 IF panel new	3.00
IF	1.75	Thorn 3/3K5 EHT & scan TX +	3.00
Conv. 3K	12.00	R2008B on alum chassis ex-	1.00
Conv. 3K5	5.00	equip	1.00
Autovox Decoder FG/01	new	Thorn 8/K5 damaged FTB for	1.25
boxed	5.00	spares	1.25
Thorn 4000 Convergence panel	untested	Thorn 8/K5 damaged decoder	2.25
ex-factory	5.75	for spares	2.25

UHF TV Aerial for portable	50p	Coax Plugs	10 for 1.65
Indoor Aerial Parabolic Type Reflector	2.50	Band Change Switch Assy, Pye 725	40p
to Help Combat Ghosting Problems	2.50	Flush Mounting TV/FM Diplexer	1.00
Line Connectors	38p	Switched Flush Fitting Aerial Outlet	1.00

10 Spark Gaps	1.00
10-16 pin Quil IC Socket	90p
20 Assorted TV Knobs	1.00
10-16 pin Quil to Dil IC Socket	90p
100 Mixed Diodes	1.00
50 Mixed Mica Washers	65p
300 Mixed Resistors & Capacitors	1.50
10-16 pin Dil to Dil IC Socket	1.00
50 Electrolytics & 50 Capacitors	1.00
50 Mixed Poly Capacitors	1.00
30 Mixed Neons & Bulbs	1.00

BF167	24	BFR62	28	NKT276	20
BF173	29	BFR81	29	NKT453	1.65
BF179	32	BFR87	25	OT112	1.92
BF180	33	BFR90	1.74	OT121	2.08
BF181	30	BFR91	2.08	R1038	80
BF184	30	BFR42	30	R1039	80
BF185	30	BFR43	30	R2008B	1.40
BF194	16	BFX38	40	R2010B	1.10
BF195	16	BFY50	30	R2030	1.30
BF196	16	BFY51	34	R2265	1.30
BF197	15	BFY52	34	R2305	80
BF198	19	BRC116	1.50	R2322	50
BF199	15	BRC1693	1.43	R2443	25
BF223	18	BU105	1.00	RCA16446	30
BF224	19	BU126	1.10	RCA16599	1.25
BF228	20	BU207	1.05	RCA16600	1.40
BF230	9	BU208	1.15	RCA16799	1.13
BF235	10	BU208A	1.15	RCA16800	1.42
BF257	20	BU407	1.30	RCA16802	1.38
BF257S	28	BU408	2.76	S1299	2.25
BF259	28	BU500	2.30	S680A/B	3.50
BF271	25	BU526	2.46	T6050V	1.30
BF272	11	BU807	2.94	T6052V	1.30
BF274	29	CI129	9	T9003V	1.25
BF337	34	CI172B	9	T9010V	1.45
BF338	40	ES386	54	T9053V	1.30
BF355	50	E9003	28	T9064V	1.10
BF361	21	E9005	25	T9039V	1.00
BF392	17	ME0404	10	TTC45X	50
BF422	47	ME0412	10	TTC46	40
BF423	53	ME0022	10	TTC106C	40
BF450	43	MJ2501	2.36	TTP29	42
BF453	53	MJ3001	2.21	TTP30	42
BF458	37	MJE182	47	TIP31	35
BF459	40	MJE340	50	TIP32	43
BF461	59	MJE520	50	TIP33	61
BF556B	35	MJE2955	1.40	TIP41	42
BF586	15	MJE3055	1.50	TIP42	45
BF594	16	NKT241W	8	TIP110	61
BF575	62	NKT241G	8	TIS91	25
BF582	31	NKT241Y	8	ZTX550	30

Pye 78+161	50p	EHT TRAYS	
Pye 147+260	50p	Thorn 3000	5.50
Thorn 56+1K+47+12	1.24	Thorn 8000	3.50
Thorn 50+40+1K5	60p	Thorn 8500	6.00
Thorn 128+16+1K7+	50p	Thorn 9000	7.90
116+462+126	50p	Thorn 9600	6.00
Thorn 120+72+300	50p	Thorn 900/950	1.50
RBM 250+14+58	63p	Pye 713 5 lead	5.97
(TV161)	90p	Pye 725	6.35
Pye 385+15+45 (713)	90p	Decca Bradford	5.00
Philips 2R2+682	90p	Baird 8750	7.10
Philips 47R	52p	Korting AZ9100	7.10
Thorn 350+20+148+	1.40	Philips G8 (520)	6.50
1K5+317	92p	Philips G8 (550)	6.50
Thorn 6+1+100	1.45	Universal	5.00
Thorn 3000 Metal	1.45		
Thorn 8/9500 Plastic	1.45		

MULTISECTION CAPACITORS

100+150+150	200+200+100
350V 50p	350V 55p
200+47	200+200+75+25
350V 65p	350V 60p
200+150+50	50+50+8
350V 60p	300V 55p
200+200+100	100+50+100
350V 50p	350V 55p
32+32+16	100+150+50
275V 52p	350V 55p
200+200+100+32	2500+2500 (Thorn 9K)
350V 70p	63V 1.20
100+50+150	150+150+100
350V 58p	300V 1.80
400+400	200V 72p
32+32+16	350V 52p
300+47	500+500 175V
350V 52p	Thorn TX9
200+200+100	175+100+100
350V 70p	350V
225+25	Thorn 3K5
350V 50p	400 400V Thorn 9K
200+200+100	2.25
350V 70p	470 250V
2	

MANTEL

Manchester's No. 1 in Ex-Rental TVs
Over 2,000 TVs in stock
Special Offer on Working Colour TV's

All sets are Serviced with repolished cabinets ready for sale

Philips G8 550s	22/26	£45
Philips 18"		£40
Philips G8 520s	22/26	£35
GEC S/State		from £35
Thorn 17" 8000		£30
Decca 30	18/20/22/26	£30
Japanese		from £30
Many other makes available from £25		

Discount on quantity

Ex Equipment Panels & Tubes Available

Deliveries may be arranged to the North and Scotland.

Ring for quote. Callers welcome.

419 Barlowmoor Road, Chorlton, Manchester 21 2ER.
Tel: 061 861 8501

Some Examples of UNTESTED TVs available

Thorn	10 for £125
Philips	6 for £90
Bush	6 for £80
GEC	6 for £60
Decca	6 for £60
Mono TVs avail. s/s	£4 each
New TV trolley stands.	
All sizes	£4.95
All Prices subject to V.A.T.	

SAVE MORE ON THESE TOP 50 INTEGRATED CIRCUITS

Type	Price £	Type	Price £	Type	Price £
2764	7.85	SAF1032P	3.99	TBA800	.79
4116 (150ns)	1.74	SAS560S	1.79	TBA950Q	1.65
74LS00	.43	SL901B	4.99	TDA1170	1.49
74LS32	.38	STK077	6.90	TDA1190	1.85
74LS157	.63	STK078	5.50	TDA1412	.95
74LS393	1.00	STK415	9.25	TD A2600	5.48
7805	.68	STK436	4.86	TD A2611	1.15
BA536	3.00	STK459	6.50	TD A2640	2.39
BA1330	1.75	STK461	7.10	TDA3560	5.10
HA1342	1.80	STK463	7.99	TD A9503	2.45
HA1366WR	1.55	TA7108P	1.39	TEA1009	.95
HA1368R	1.58	TA7205AP	.99	UPC1156H	1.40
HA1389	1.60	TA7222AP	1.59	UPC1181H	1.15
LA4460	1.65	TAA550	.45	UPC1185	2.80
LA4461	1.60	TBA530Q	.99	UPC1365	5.00
LM1011	2.90	TBA550Q	2.49	UPC2002	1.45
MC1327PQ	.95	TBA560CQ	1.05		

ASK FOR TRADE LIST, T.V., VIDEO & COMPUTER SPARES. EXPORT ORDERS WELCOME - OVER 4 MILLION ITEMS IN STOCK.



To Order:—
 Add £1.50 P & P then 15% VAT to total.
 P & P free on orders £20 & over. Export orders VAT zero + postage at cost.

PHONE (0772) 555034

TO: C.P.C. PLEASE SUPPLY YOUR TRADE PRICE LIST.

NAME

ADDRESS

T.V.11.



194-200 North Road, Preston, Lancashire, PR1 1YP, England. Telex 677122.

Please allow 7 days for delivery

TELEVISION/COMPUTER TRAINING

(FULL TIME COURSES APPROVED BY THE BUSINESS & TECHNICAL EDUCATION COUNCIL)

2 YEAR

BTEC National Diploma

ELECTRONIC &

COMMUNICATIONS ENGINEERING

(Electronics, Computing, Television, Video, Testing & Fault Diagnosis)

15 MONTHS

BTEC National Certificate

ELECTRONIC EQUIPMENT SERVICING

(Electronics, Television, Video Cassette Recorders, CCTV, Testing & Fault Diagnosis)

15 MONTHS

BTEC National Certificate

COMPUTING TECHNOLOGY

(Electronics, Computing Software/Hardware, Microelectronic Testing Methods)

9 MONTHS

BTEC Higher National Certificate (HNC)

COMPUTING TECHNOLOGY & ROBOTICS

(Microprocessor Based Systems, Fault Diagnosis, ATE, Robotics)

THESE COURSES INCLUDE A HIGH PERCENTAGE OF COLLEGE BASED PRACTICAL WORK TO ENHANCE FUTURE EMPLOYMENT PROSPECTS

Shortened Courses can be arranged for applicants with previous knowledge.

Full Prospectus from:

LONDON ELECTRONICS COLLEGE (Dept TF)
20 PENYWERN ROAD, EARLS COURT,
LONDON SW5 9SU. Tel: 01-378 8721

A Look at Monitors

Part 1

Eugene Trundle

There was a time when a TV was a telly and a monitor was regarded as being something to do with broadcasters and professional TV users – like cameras, mixing consoles, effects generators and so on. The emergence of home video changed this to some extent, now that Tom, Dick and Harry can generate, manipulate, record and playback their own TV pictures and programmes. Another factor contributing to the change has been the proliferation of home computers. The “high-density” data produced by many computers calls for a display system with higher than normal resolution capability.

A growing awareness of the shortcomings of present TV systems involving a PAL codec (coder/decoder), and of the definition limitations imposed by domestic VCR formats, has been brought about by the sight of crisp, sharp displays of teletext and Prestel data. Those who've seen demonstrations of digital, high-definition and high-quality CCTV pictures will appreciate this. Displays of non-coded images from such sources come as a revelation to those used to the average domestic TV picture, regardless of its source. We don't wish to denigrate the broadcasters and VCR manufacturers, who do a magnificent job within the constraints imposed upon them. These consist mainly of (a) the available system bandwidth and (b) the need for compatible operation, i.e. band sharing between the luminance and chrominance signals. The conventional set up is quite adequate for off-air, VCR- and disc-derived pictures, with the currently popular screen sizes (50-56cm average) and viewing distances (about 3m): in this context a high-definition picture tube and better circuitry would be largely wasted.

What is a Monitor?

Traditionally, a monitor has been a TV set shorn of its tuner and i.f. strip. This remains true of the simplest and cheapest monitors, which use conventional timebase, video and power supply circuitry as found in domestic TV sets and an ordinary picture tube. Mains isolation is the major additional requirement, though this is increasingly a feature of domestic TV sets. Many TV set/monitor conversions have been carried out, with mains isolation by means of a chopper transformer, or a 50Hz double-wound transformer with 1:1 turns ratio (when internally fitted, toroidal winding is usually required to prevent stray magnetic fields from upsetting the operation of the picture tube), or fast optocouplers to provide isolation at the video input terminals.

Purpose-designed Monitors

Purpose designed monitors vary tremendously in price. The more expensive ones have improved specifications compared to domestic sets in most possible respects. They can be expected to offer enhanced performance and extra facilities in the following areas.

(1) Video bandwidth. Depending on the intended application, monitor video channels may have bandwidths from 10 to 50MHz.

(2) Scanning geometry. Field and line scan linearity is

typically ± 2 per cent of picture height, 0.5 per cent with very expensive models. Also important are absence of ripple (i.e. 50 or 100Hz mains hum) on the raster and full correction of raster distortion (scan-error and pincushion effects).

(3) Breathing. Raster size should be virtually independent of beam current. This calls for very good e.h.t. regulation. Domestic TV sets have improved greatly in this respect in recent years but a good monitor will do better, with perhaps a maximum variation of 1.5mm in picture size from cut off to full rated beam current. More on this later.

(4) Black-level clamping. A driven clamp is better than a d.c. restorer. Any clamping carried out during the back porch of a composite, chroma-encoded signal needs a clamp softener in the form of a reactive or resonant circuit between the clamp and signal to prevent crunching of the colour burst.

(5) Tube resolution. Most monitors use high-definition tubes.

(6) Convergence tolerance. This depends on type of tube but can be better than a standard production tube by a factor of up to five.

(7) Stability. Drift of important electrical characteristics with time and temperature is minimised by careful design. A strict maintenance and recalibration timetable may be specified.

(8) Input facilities and interfacing. A general-purpose monitor will be able to accept a choice of input levels and types.

(9) Scan frequencies. As you go up the price scale you find instruments with 625/525-50/60 switching and automatic height compensation; field rates between say 38 and 80Hz, interlaced or not; and line scan rates up to 38kHz. These very high scanning frequencies are relevant only to wideband monitors with very high resolution tubes.

(10) Switchable scan amplitudes. An underscan mode will facilitate inspection of the extreme borders of the picture since they will be within the visible raster area. A 1:1 aspect ratio may be provided. See Fig. 1.

(11) Pulse cross facility. A useful feature of some professional and broadcast-standard monitors is their ability to display the line and field blanking periods and the signals these contain. This is done by switching delay monostables (about 10msec for the field, 20 μ sec for the line) into the sync pulse paths. This mode of operation shows sync dropouts, the burst, blanking, vertical interval test signals (VITS), reference and other test signals.

Other similar features on high-specification monitors include split screen, where the upper half of the display is in monochrome so that the effect of colour on a

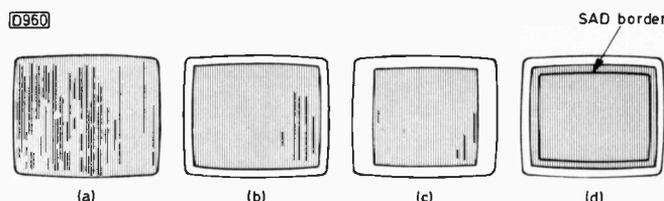


Fig. 1: Rasters. (a) Normal. (b) Underscanned. (c) With 1:1 aspect ratio. (d) SAD border on underscanned raster.

this use. At present there's no standard form of video connection, though the SCART socket (also known as the Euroconnector or peritelevision plug/socket) is being increasingly used. Details are given in the data card that accompanies this issue of *Television*. Some monitors have BNC connectors, some DIN, others a plug/socket type exclusive to the manufacturer.

EHT Regulation

Many very good monitors derive their e.h.t. supply from the line output stage in the conventional manner. Given careful design, this arrangement can provide excellent results, especially with an anti-breathing circuit that measures the beam current (typically via the tube's Aquadag return line) and applies a compensating bias to the width and height circuits to maintain constant picture size despite varying brightness levels. For consummate performance, a separate e.h.t. generator with a feedback stabilising loop can be used. One such circuit (from the Barco CTVM3 series) is shown in Fig. 2.

The e.h.t. voltage is measured at source via the potential divider Rt/P2/P3/R28, the sample thus obtained being applied to the base of the emitter-follower buffer transistor Q10. The output from this is passed via R17 and D4 to the base of comparator transistor Q4, whose emitter voltage is held constant by stabiliser IC3. Thus Q4's conduction depends on the e.h.t. voltage. To assist in stabilising the action, Q2 and D2 provide a constant-current supply. Q4 controls the base of Q3 which in turn drives the series regulator transistor Q100. This completes the stabilising loop, whose operating point is established by the setting of P2.

At switch-on the e.h.t. voltage will be zero and Q10 will be without base bias, i.e. it will be cut off. So a start-up system is required. Q4's base is then biased via R15 and D5. Once Q10 turns on and the voltage across R21 rises to 700mV Q6 conducts, reverse biasing D5.

There are several protective features built into the circuit. D9 provides flashover protection at the sampling point. In the event of excessive e.h.t., for example due to Q100 going short-circuit, Q1 will conduct, firing the crowbar thyristor Th1 as a result of which an h.t. fuse blows. In the event of excessive e.h.t. current the voltage across R9 will rise so that Q5 conducts, reducing the drive to Q3 and in turn Q100. To prevent a pumping action, Q5 is latched on by R4 and the 36V zener diode D3 until reset by switching the monitor on and off again.

Resolution

The ultimate aim with a TV display system is to reproduce very fine detail, the virtue of a monitor being largely judged on this basis. Ultimate resolution depends on many factors: we'll discuss the main ones briefly, starting with conventional 625/50 standard pictures.

The TV image consists of a mosaic of tiny dots of light, coloured or white as the case may be. The 625-line picture is made up of two interlaced fields, each consisting of 287.5 lines – the rest are taken up by the field blanking interval. Thus a total of 575 lines is available for the picture pattern, less a few lost at the top and bottom of the screen due to the overscan that's usual in most TV sets. The number of lines determines the absolute limit of the vertical definition but there are other limitations. Any detail fine enough to occupy only one scanning line will have a high degree of flicker, because its refresh rate will

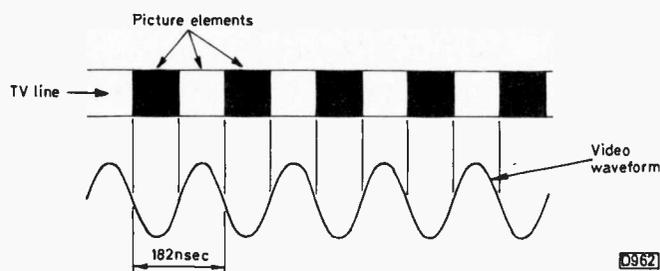


Fig. 3: TV scanning line with maximum detail, with the corresponding video waveform shown below.

be at frame frequency, i.e. 25Hz. Flickerless reproduction will occur only with vertical detail that occupies an even number of adjacent scanning lines. The interlace performance of the field timebase is also relevant: in the worst case (zero interlace, with the lines of each pair of fields superimposed), the effective vertical definition will be halved and a very coarse line structure will be seen.

There's a third factor to be considered before we go on to horizontal definition. This is the Kell factor. If the TV system is fault-free and correctly adjusted throughout, it's perhaps reasonable to expect that we should see 287 equally spaced white lines drawn on a blackboard at which a camera is pointed. This would represent the maximum possible vertical definition – 575 alternate black and white lines across the screen from top to bottom. We wouldn't see them however! Because the lines on the blackboard are unlikely to be exactly aligned with the scanning lines, and because at normal viewing distances the picture's line structure is not discernible, the practically realisable vertical definition is reduced by 25–30 per cent, leaving us with about 430 lines worth of effective vertical definition. This is relevant only to optically generated pictures: data displays are electronically generated on individual and precisely defined lines, and provided the viewer is close enough to the screen to see the individual scanning lines the Kell factor is irrelevant.

Horizontal Definition and Bandwidth

There's little point (in analogue TV pictures anyway) in having unequal vertical and horizontal resolutions, so optimum horizontal resolution equals the vertical resolving power. Theoretically, each picture element (pixel) will then be square. With the standard aspect ratio of 4:3, we should aim for $430 \times (4/3) = 573$ individual dots per scanning line.

Now the line blanking period is $12\mu\text{sec}$, which leaves $52\mu\text{sec}$ out of the total $64\mu\text{sec}$ line cycle as active picture time. Assuming the worst case (see Fig. 3), where the pixels along a scanning line are alternately black and white, this would mean changing the video signal from zero to white, then to black and finally back to zero in the space of two pixels. With 573 pixels per $52\mu\text{sec}$, one cycle of video signal must take place in $(52 \times 2)/573 = 0.182\mu\text{sec}$. This determines the video bandwidth required. One cycle in 182nsec equals $10^9/182\text{Hz}$, i.e. 5.5MHz, which is the bandwidth allotted to the luminance signal in broadcast television. If the video system can pass a sinewave at this frequency, we shall have somewhat rounded leading and trailing edges to each pixel. This is what happens with a conventional TV set. If the video channel can accommodate a 5.5MHz squarewave, our pixels will be truly square! The greater the monitor's video bandwidth, the sharper each pixel's "attack" and "decay"

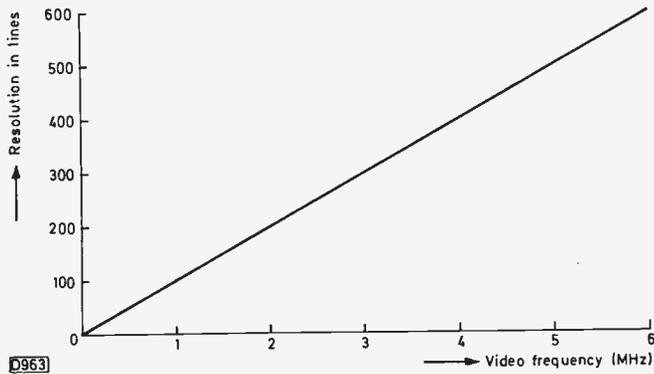


Fig. 4: Video signal frequency plotted against resolution in lines for the standard 625/50 system.

will be: provided the rest of the signal chain lives up to this, sharper edges will be seen. The broadcast channel can only just manage a 5.5MHz sinewave, so extra bandwidth is relevant only to video sources such as computers, text displays and so on. VCRs, video disc players and domestic cameras all have bandwidth restrictions and PAL coding systems, so high-quality display systems are wasted on them.

Next we need to relate bandwidth to rise time. Rise time is the time it takes for a system's output signal to get from ten to ninety per cent of its final level when the system is presented with a true step-waveform input. The formula is $t = 1/(2f_{max})$ where t is the rise time in μsec and f_{max} is the upper limit of the system's passband in MHz. Thus an amplifier whose -3dB limit is 5MHz will have a rise time of $1/(2 \times 5) = 0.1\mu\text{sec}$ or 100nsec. To convert the other way, $f_{max} = 1/2t$, i.e. an amplifier with a rise time of 20nsec can be expected to handle sinewaves with frequencies up to 25MHz.

The horizontal resolution capability of items like cameras, VCRs and picture tubes is very often quoted in terms of lines, and it's useful to relate this to video frequencies. Fig. 4 compares line resolution with video frequencies, and shows for example that a VCR with a horizontal resolution of 270 lines will easily resolve the 2.5MHz test card gratings while a monochrome camera rated at 400 lines should pick up the 4MHz gratings when viewing a test card. Sometimes a vertical definition figure is quoted, usually approximating to the horizontal figure. It will generally be less than the theoretically possible 575 lines (Kell corrected, 430 lines) due this time not to bandwidth limitations but to vidicon spot size, optical constraints in cameras and the use of identical field or line averaging techniques in other equipment.

Video Output Stages

In a class A video output stage – see Fig. 5 (a) – the bandwidth is limited by the considerable stray capacitance in the load. Stray capacitance is contributed by the transistor's body and its heatsink, the land area of the PCB, the wiring to and the construction of the tube pin and socket and associated spark gap, and the capacitance of the tube's cathode to adjacent electrodes, principally the heater and control grid cylinder. This lot can add up to 10pF or more, which has a reactance of less than $3\text{k}\Omega$ at 5.5MHz. It's not difficult to see the advantage of mounting the video output stages on the tube's base panel. The frequency at which the response falls to -3dB is given by $1/(2\pi CR)$, where C is the stray capacitance and R the load resistor, so for a 5.5MHz response the value of the load

resistor would need to be less than $3\text{k}\Omega$, which would make for very high dissipation in the video output transistor. In practice a higher value load resistor is often used, the resultant h.f. fall-off being compensated for my means of an inductive element in the collector load circuit or a low-value emitter decoupling capacitor – C1 in Fig. 5 (a) – to give frequency-selective negative feedback.

More significant though is the effect of stray capacitance on signal rise and fall times, which become unequal in a circuit of this type. Assuming c.r.t. cathode drive, the video output voltage is low for white, high for black. On the leading edge of a white picture feature Tr2 is being driven on, its low collector-emitter resistance quickly discharging the stray capacitance to give a fast fall time (attack) and a sharp leading edge to the object displayed. On a transition from white to black the tube's cathode voltage must rise sharply, and Tr2 is turned off to achieve this. The stray capacitance must charge to the new, higher voltage, and its only charging path is via R4. This RC combination forms a time-constant that permits only a relatively slow rise time and recovery to black. The result is a smeared trailing (right-hand) edge to white objects. This is acceptable in low-cost and small-screen TV sets and for low-definition graphics, but it's a non-starter for a self-respecting monitor.

The problem is overcome by using a "balanced" video output stage, of which there are two main types. One employs a complementary pair of npn/pnp high-voltage output transistors in a class B circuit. The more common circuit is the so-called class AB one in which an emitter-follower is added as an active load to a common-emitter transistor. A typical arrangement is shown in Fig. 5 (b): it's used by Microvitec in their range of monitors to provide an 18MHz bandwidth. This results in excellent analogue pictures and data displays.

Tr1 is a basic class A amplifier whose gain is set by the ratio of R6 to R1/2. R3/4/5 set the d.c. conditions. Tr1's load resistor R7 is effectively shunted by Tr2 on white-to-black transitions, providing a low-impedance path so that the load capacitance charges rapidly. As Tr1 turns off, D2 becomes reverse biased so that Tr2's emitter voltage rises quickly under the influence of the base bias provided by R7. Signal h.f. compensation at the input is provided by



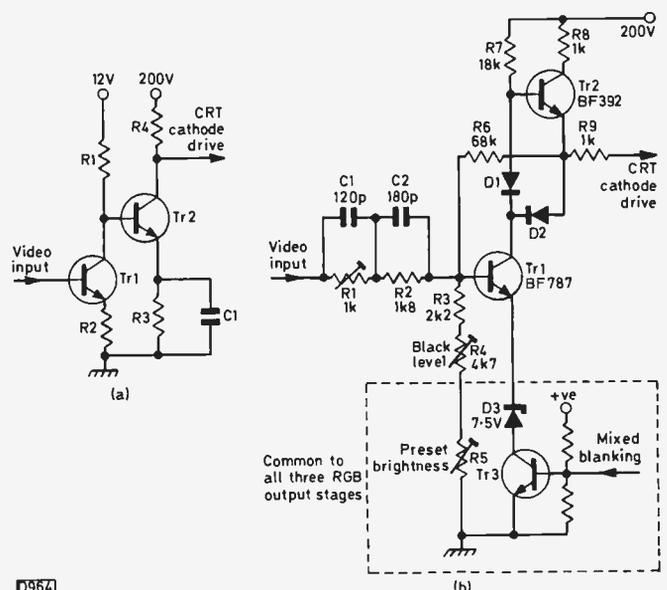


Fig. 5: Video output stages. (a) Simple class A circuit with driver. (b) Class AB circuit as used by Microvitec.

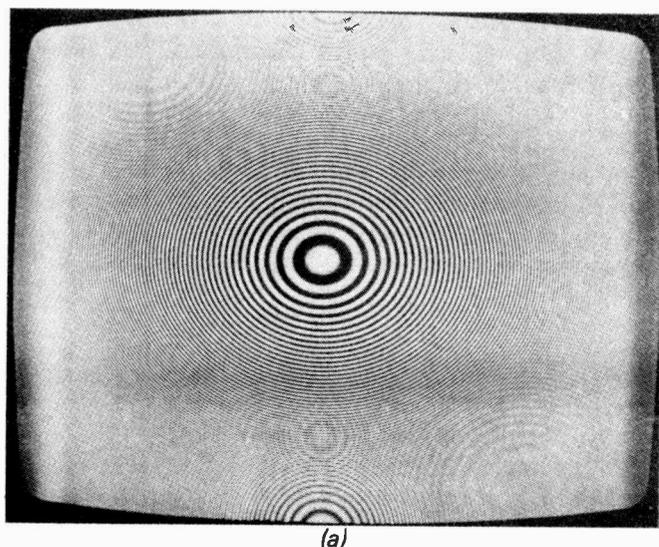

(a)

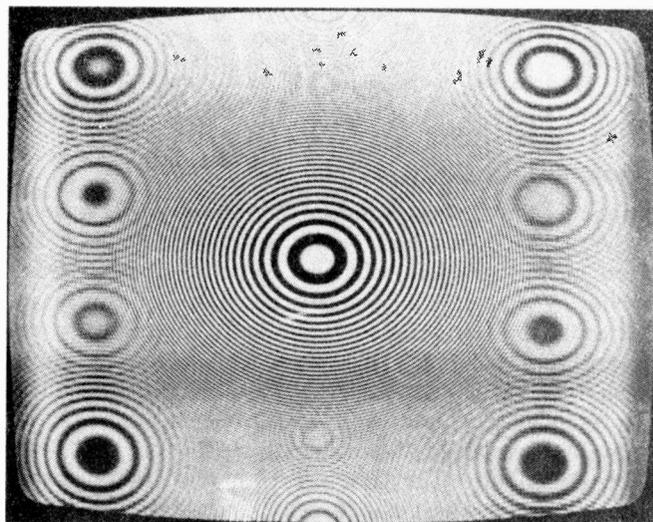

(b)

Fig. 6: Off-screen photos of a green zone-plate image. (a) Monitor display. (b) Display after passing through a PAL codec.

C1 and C2. Tr1's emitter is held steady at 7.5V by zener diode D3, whose ground connection is interrupted during the field and line blanking periods by switching off Tr3.

Colour Codec

The three colour coding systems in use (NTSC, PAL and SECAM) were all designed for compatibility with existing monochrome TV systems, and achieve this by means of a band-sharing arrangement in which the luminance and chrominance components are interleaved. What price do we pay for this bandwidth economy? The main visible effect is a degree of cross-colour on fine detail, be it test-card gratings or picture features like striped suits and distant railings. The effect of cross-colour is brought out in Fig. 6, where (a) shows a studio picture of a zone plate consisting of concentric and graded rings of primary green and (b) shows the result of passing the zone plate signal through a PAL codec. The cross-colour effect adds spurious patterns (in blue/yellow and red/green) centred on luminance frequencies corresponding to the colour subcarrier frequency. Also present in encoded pictures are more subtle effects like cross-luminance, a moving luminance dot pattern adjacent to chrominance transients.

The main problem with an encoding system such as PAL is the inherent definition limitation however. The chroma signal bandwidth is little more than 1MHz, permitting a maximum horizontal colour definition of about 100 lines. The vertical colour resolution is much better than this because of the 575 active line scan structure, though the signal averaging process carried out in the delay line circuit considerably reduces this. Even so, for colour we have unequal vertical and horizontal resolution, resulting in such effects as the half-coloured letter T, where the vertical bar is virtually colourless while the horizontal bar is coloured. This sort of thing is particularly noticeable in titles (and other small picture features) where there is no marked change in luminance between letter and background. Another characteristic of PAL and similar systems is the barely adequate chroma signal-to-noise ratio (most obtrusive on large coloured areas).

The presence of the 4.43MHz (for PAL) colour subcarrier means that a notch filter centred on this frequency has to be included in the luminance channel to remove the worst effects of dot-patterning in coloured

areas of the picture. This inevitably knocks out fine luminance detail as well, which is the second and less obvious definition penalty with shared-channel encoding.

What a catalogue of woes to lay at the door of the PAL system! With a normal moving picture however the original concept of PAL (and NTSC before it) works very well by coarsely brushing in colour over a relatively high-definition monochrome picture. Subjectively judged by those more interested in the programme material than in picking holes in the system it's quite adequate. There are special decoding systems that can remove cross-colour effects and offer higher luminance definition – by the use of sophisticated comb-filter techniques in both the chroma and luminance channels. These techniques are used in the better monitors, but they're expensive and the subjective improvement they offer is not sufficient to justify their use in domestic TV sets.

The main PAL defects come to light (literally!) where the chroma signal has no luminance back-up: where the picture consists mainly of coloured areas (a good example is computer graphics) the horizontal definition is effectively reduced by a factor of five. You can demonstrate this on an ordinary TV set by removing the luminance signal so that chroma only is displayed on the screen – the picture is very hazy and woolly. For a more graphic demonstration of the combined deficiencies of PAL encoding and VCR bandwidth limitation try recording data and graphics from a text adaptor, TV game or home computer on a VCR and play back the result – coloured areas resemble wobbly jellies full of maggots.

Modulation

The PAL and similar systems were conceived for broadcast use. Why do we go to all the trouble of PAL encoding a signal, modulating to u.h.f., then tuning, demodulating and decoding with two pieces of equipment less than a metre away, suffering all the above constraints in the process? Very simply, because the only signal access to the average TV set is via the aerial socket – and the live-chassis technique so widely used means that other forms of connection are dangerous. Now that the live-chassis era is disappearing we can look forward to much higher quality pictures where these are there to be had – if only we could standardise on connector types, signal exchange levels and similar interfacing details.

Fuses and Clocks

Further to the fuse blowing in the Toshiba V31B mentioned in the July Clinic, Toshiba report that they are aware of the problem which is caused by spiky mains supplies. They suggest changing the value of the mains filter capacitor from 0.1 μ F to 0.0047 μ F. Whether this cures the problem remains to be seen. I've since had three Sanyo VTC5150s and two Ferguson 3V35/36s that blew their mains fuses either for no apparent reason or because two-way mains adaptors were being used.

Thanks to Peter Clark for an explanation of the teletext clock problem, which we've seen once more. The difference was between local and national ITV magazines. D.S.

Hitachi VT19

Now to a few faults with the Hitachi VT19. A common problem is sound instability due to the audio switching relay contacts. Modified relays are now fitted and are supplied as spares. The following modification can also be made. Change resistors R462L and R462R from 2.2k Ω to 680 Ω and add diodes (type 1S2076 or 1SS133) between these resistors (IC405 end) and the bases of Q415L and Q415R, with the cathodes of the diodes to the bases of the transistors. These modifications may give further improvement or make it unnecessary to change the relay. Another fault is the timer microcomputer resetting due to the 10V regulator transistor Q1795 overheating and going open-circuit. Change the transistor to a 2SD468 or 2SD882. Also replace wire link K1788 (between pin 5 of RC1795 and the 10V line) with a diode (type 1S2076, 1S2473 or 1SS133), anode to pin 5, and decouple pin 5 with an 0.22 μ F capacitor (add between pins 4 and 5 of RC1795).

The final fault was with one of these machines that recorded perfectly: in playback however if the long/standard-play switch was in the long-play position and a standard-play cassette was inserted the machine wouldn't always switch to standard play. Now the position of this switch should affect only record: playback switching should be automatic. The switching in record and playback is controlled by IC908 (HA11768): during playback the off-tape control pulses are used to check at which speed the tape was recorded, either pin 15 or pin 16 of the i.c. going high to tell the machine to go into the LP or SP mode. A check showed that the control pulses at pin 7 were correct during the fault condition but the relevant pin wasn't going high. Replacing the i.c. cured the fault D.S.

Sanyo VTC9300

Failure to record was the fault with a Sanyo VTC9300. Playback and E-E were perfect but no picture at all was evident on record. A scope check quickly showed that the fault was on board W1 (the one on the left). Much fruitless time was then spent trying to trace the fault with the wrong circuit. The board fitted in this machine was the one used in the later VTC9300PN rather than the VTC9300P. Once the correct circuit was obtained it was a simple matter to trace the signal as far as Q4 which was open-circuit base-to-emitter. It was an obscure 2SA type

so an equivalent with a different pin layout was used. I checked the connections twice before fitting the transistor then put it in the wrong way round, causing myself a lot of unnecessary worry when the fault still seemed to be there. D.S.

Hitachi VT8500

An Hitachi VT8500 came in off rental. I was checking it over and had it on final test when I noticed that pause didn't operate on record though it was perfect on playback. On playback pause merely stops the capstan motor after shunting the noise bar off the screen. On record the tape is rewound slightly, the loading motor operating until the loading switch switches off - this is sufficient to disengage the pinch roller, the capstan motor being left running. In this machine however the loading motor wasn't running long enough to disengage the pinch wheel. The loading switch was operating correctly, but no matter how it was positioned it operated too soon.

The search for the cause of the problem was a long one, but after removal of the upper and lower cylinders, the capstan motor, the pinch roller, the tension band, various levers and the subchassis the machine was finally stripped down to the point where the fault was found - a small metal spring which controls the position of the arm that operates the loading switch was incorrectly fitted (probably during manufacture). A fault that had probably been on the machine for two years without being noticed, caused by a spring being about $\frac{1}{16}$ in. out of position, had taken at least four hours to fix. If the machine had been sent out with the fault it would have been odds on that the customer who took it would have been the one in a hundred who uses pause on record! D.S.

Fuse Blowing

I've had the same problem as Derek Snelling with the Toshiba V31B - fuse blowing. The capacitor change mentioned above provides the cure. You get the same problem with Sanyo VTC5000s and Toshiba V9600s. S.B.

Mitsubishi HS302

Intermittent timer operation and a tendency to shut down during play was traced to the take-up motor. If you have to change it note the height of the turntable before you remove this - so that it can be replaced at the same level after changing the motor! S.B.

Toshiba V8600

This Toshiba V8600 had a colour fault. It played back a prerecorded tape with no problem, which should have been the first clue. Replay of its own recordings was reasonable except for a bit of colour reversal - a flashing effect which could be removed by adjusting the a.c.c. control. The main fault could easily have been missed, no colour in still picture. Regular readers will have notes on the still-picture circuits of this machine pinned up all over the workshop as we've reported a few brain teasers in this area in past issues. The signal levels around IC204, Q228 and the delay line X204 were checked to no avail, so the

record a.c.c. level was monitored. Guess what – no pilot burst! The fault was due to the CX130 switching i.c. (IC202) which is used to insert the pilot burst. Funny how the machine managed to replay its own recordings in colour – normally the colour-killer operates when the pilot burst is absent. S.B.

Toshiba V5470

This machine was one of our rental stock. I'd just fitted new heads, belts, etc. when I noticed that it was not recording video. As new heads had just been fitted, maybe they were intermittent or something . . . anyway, to get to the point there was little or no f.m. reaching the record amplifier, which is on the audio board, from the video board. So checks were made on the video board. There was f.m. at the modulator (pin 30, IC401) but no output from the two transistors that follow this (Q404/5). The coupling capacitor C419 (0.022 μ F) turned out to be leaky, upsetting the bias conditions at the base of Q404. S.B.

Hitachi VT9500

Failure to record was the fault on this machine so checks were made around IC201. The signal level at the input to the record amplifier (pin 28) was only a few hundred millivolts and the output at pin 25 was not much better. The i.c. was replaced, with some difficulty, after which we had 4V peak-to-peak at pin 25. Much better. S.B.

JVC HR7700

No nothing was the problem and there was a cassette in the machine. The fact that there was no eject drive was not surprising as the 23V unregulated motor supply line was missing. Fuse F5 had blown and a replacement did the same thing. The reservoir capacitor C36 was short-circuit – or at least very leaky. S.B.

Sharp VC9700

The problem with this one was no line sync in both forward and reverse visual search. A check was made on the drum servo frequency-to-voltage converter i.c. It was working correctly but the off-tape control pulses were unstable in frequency – all over the place they were! The visual search presets couldn't be set of course: the fault was due to the reel motor. A replacement restored stability once everything was set up. I replaced the idler pulley while I was about it. S.B.

Hitachi VT8000

The fault with this machine was failure to record. On test we found that there were no E-to-E signals. A further check showed that the "not playback 12V" supply was missing – this supplies the tuner, the i.f. panel and the presetter board, and comes from regulator transistor Q066 on the system control panel. The cause of the problem was that R069 (1.5k Ω , $\frac{1}{2}$ W) which feeds the reference zener diode in the regulator circuit had gone open-circuit. Replacing this restored all functions to normal. M.S.B.

Panasonic NV777

If there's lack of line lock, check whether the drum PG pulse is present at TP2006. If not, replace the drum. If the

PG pulse is present, check whether the switching pulse is present at TP2011. If not, suspect IC2003 (AN6346N). If the switching pulse is all right, check the squarewave output at pin 27 of IC2001 (MN6168VIA). If this is missing, replace IC2001. If it's present, check IC2010 (AN6677) by replacement. J.C.

Sanyo VTC5000

For no results, check the mains fuse F5201 (315mA). If this is open-circuit and a replacement blows, check the switch-mode power supply chip IC5101 (STK7216) by replacement. J.C.

Blaupunkt RTV211

Smoking was the reported complaint. This was found to be due to a loose screw, as a result of which diode D1007 had gone short-circuit. After replacing several components the machine still didn't work, due to no output from the STR1096 9V regulator i.c. There's a Blaupunkt depot just down the road, so I called in for a replacement. One of the technicians there said it couldn't be the i.c. as it never goes faulty. Well, if you're reading this Gordon – it was the i.c.! L.H.

Sharp VC9300

The fault was no rewind. Fast forward was all right but when the rewind button was pressed the machine continued in fast forward. The system control board was released, and on trying again the machine started off in fast forward then went into rewind. The culprit turned out to be relay R7751 which changes the polarity across the reel motor – it's energised in rewind and was sticking. L.H.

Sony C9

The tuner produced no signals and there was no clock and no programme numbers. As a start, the control voltage to the tuner was checked and found to be missing. It comes from the collector of transistor Q101 on panel TU24. Finding no voltage here either, I checked back to the 38V source on the power supply panel (board D). The source is pin 3 of a d.c.-to-d.c. converter circuit which is a sealed unit. Again there was no voltage, and although I managed to open the unit it was difficult to carry out any tests. A replacement converter module cleared all the faults on the machine. I.H.

Sony C5

The head drum motor on this machine had stopped. I could get it to start by pressing fast forward or rewind then going straight into the play mode, or by pressing play and then spinning the drum by hand. The machine would then work all right until stopped.

There's a head drum motor start-up circuit on servo panel AS-6. When the machine is switched on, pin 18 of IC1 (CX186) should initially be at 10.8V, dropping to 7.2V when the drum rotates. In fact there was no voltage at pin 18. The start-up circuit is connected to pin 21 of the i.c. and consists of an RC network and a link via D1 to the drum rotation detection circuit. The voltage at pin 21 was only 0.8V at switch on instead of 10.4V – it drops to 1.8V when the drum starts to rotate. A check on the components connected to pin 21 revealed that the diode was short-circuit. I.H.

Letters

CHOPPER SUBSTITUTE

The BDX32 seems to be a suitable alternative to the 2SC1942 as the chopper transistor in the Hitachi NP6C chassis (Service Bureau, July). I've used it in a number of these sets with no callbacks. In the event of intermittent power supply operation caused by suspected dry-joints the only cure seems to be to clean all the joints on the power supply section of the board and resolder them. Note that connections G1 and G3 on the power supply/deflection board go to the signals board and not to "CPT board T" as shown on page 22 of the manual (no. 338) for Model CWP132.

Paul Hardy,
Reading, Berks.

VINTAGE HI-FI

Our antiquarian Chas E. Miller's article "A Vintage Hi-Fi TV Sound Unit" with its impedance matching problem took me back to the mid-fifties when I worked in the McMichael research and development department. I remember building a push-pull amplifier to evaluate the performance of a pair of ECL80 valves: Mullard claimed 3W undistorted output into a 12k Ω anode-to-anode load with 200V h.t. My efforts at producing this output failed however. I was stuck at 2.5W until, in desperation, a 15k Ω transformer was tried. Then, eureka, we had the 3W. This information was passed on to Mullard who sent us an amended specification, so Chas's "rule of thumb" is spot on.

Incidentally, McMichael were in the forefront of radio receiver design, producing dual-speaker sets in the early thirties - anyone remember the "Twin Supervoxx"? Having

found that twin speakers improved sound quality I've always used them, both for radio and TV, just one pair, the siting not affecting the illusion of sound coming from the screen. In mono days I used an RS matching transformer with three isolated windings for interfacing. Nowadays with stereo I use a simple system that may interest readers as it entails only a changeover relay, see Fig. 1. Most stereo equipment has 8 Ω outputs with one lead being common, so the normally closed relay contacts parallel the speakers for TV use. When the stereo amplifier is switched on the relay coil is energised and the contacts connect the speakers to the stereo outputs. I use a 240V mains relay, e.g. RS 348-762. The problem of TV sets with direct output can be overcome by the use of a suitable transformer for isolation - RS supply one that's useful up to 15 Ω . This system will not give bass response from TV equal to stereo but is an improvement on the TV speaker.

William Harrison,
Windsor, Berks.

COMPONENT TESTER MODIFICATION

I've built the component tester described in the June issue and am using it with a Telequipment D61 oscilloscope. The tester's X output was far too great for this scope on external trigger, also the $\times 5$ X amplifier does not operate on external trigger. I've therefore modified the tester as shown in Fig. 2. This seems to work all right and it's useful to have the extra X amplitude with high-value capacitors. Perhaps there are better ways of doing things?

Dr. J. Rankin,
Harpenden, Herts.

BASEBAND LINKS

I agree with Eugene Trundle (letters, August) that the loss of picture quality as a result of feeding PAL coded signals from a VCR etc. via a u.h.f. link rather than at baseband is small, even negligible. I believe however that there are good reasons for adopting the baseband approach. If one wishes to connect two or three VCRs or other video sources, e.g. a disc player, to one TV set simultaneously there's often insufficient range of modulator tuning adjustment for each double-sideband output to be given a clear piece of spectrum. This is particularly true when, as occurs in this area, the local TV transmissions are in this part of the band. In addition, whereas a baseband connection can just be plugged in and used, a u.h.f. output needs to be tuned in, which can be time consuming - especially with an unfamiliar search-tune system.

There's also the question of sound. For many years now I've listened to TV sound via an external hi-fi amplifier and speakers, so I'm perhaps more critical than most of TV receiver sound quality. In my experience the modulator-demodulator link is responsible for a significant part of the loss of sound quality when using a VCR. Problems include poor frequency response due to inaccurate pre-emphasis, video buzz - particularly when using still frame, shuttle search etc. - and background whistles.

There should be no need for tangles of wires. A combined audio/video connecting lead is easily arranged and results in only one extra connection between the VCR and the TV set. The problem of sound leakage can only be due to the well-known reluctance of TV set manufacturers to spend any money on the audio side of their products. A properly engineered audio switch within the TV set should

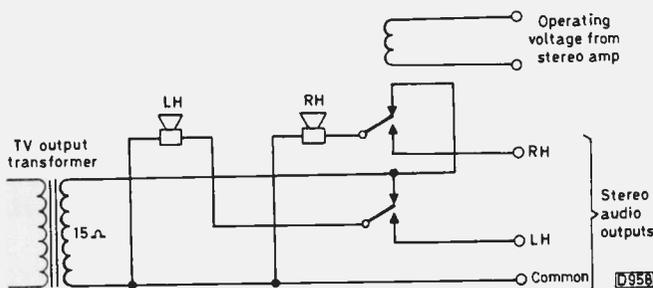


Fig. 1: Relay-operated dual-speaker system for mono/stereo operation.

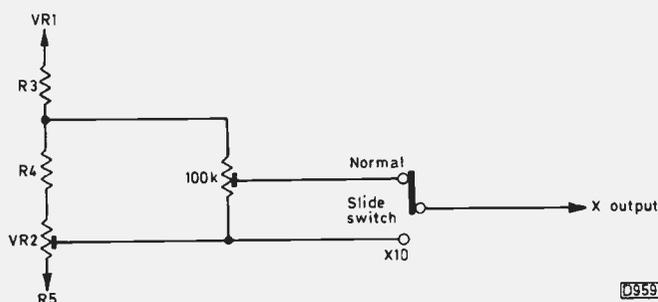


Fig. 2: Modification to the scope component test unit.

cause no problems and will, I believe, result in noticeable improvement in sound quality.

I use a modified Philips Model 1250 (K30 chassis) which accepts baseband signals from a Grundig 2 × 4 Super and a modified Philips N1700. Video and audio switching is performed within the TV set, the selected video signal being fed to the PAL decoder and the selected audio signal to a socket at the back. The audio is

then connected to the auxiliary input of my Quad 44 preamplifier. The internal audio amplifier in the TV set is not connected, as the volume control used with the TBA120 is not available for external inputs. I haven't bothered to make alternative arrangements for this because I wouldn't use them anyway.

*David Looser,
Ipswich*

On being fooled

Les Lawry-Johns

Just when you think you've completely mastered a particular chassis and feel that it can't hold any more heartache for you, one comes in and grabs you by the short and curlies. I'm sure it's done to deflate one's ego – if it ever gets a chance to inflate.

The T20

A Rank T20 sat on the bench and looked at me. I looked back and sneered. "I'll have you done and working in five minutes" I told it. The sheet said no results. Well, what else would it say?

I whipped the back cover off, plugged it in and waited to see if the tube's heaters glowed. They didn't. I applied the meter to the body of the BU208A line output transistor, expecting to find an unenergetic 200V. The reading was low. This suggested that the BU208A was short-circuit: removing the collector screw and checking with the ohmmeter showed that it was. So I fitted another and disconnected the tripler, just in case. I switched on and the heaters glowed. A nice rushing noise came from the speaker. I advanced the lead to the tripler input. The tube's heater went out and the sound died.

I removed the lead and the set remained quite dead. So I switched it off and on again. Still nothing and the reading across the new BU208A was low. I stamped my foot in anger and the cat ran out through the kitchen window. Another BU208A up the spout. I fitted a second one and a new tripler. All was ready. Switch on, buzz, nothing. The voltage at the collector of the BU208A was this time 200V. So I went through the usual routine: check the resistors, the low-value one over on this side and the high one over on that; check the EW modulator diodes; check the line driver transistor and its supplies. I disconnected the new tripler just in case. The sound boomed out and the heaters lit. After checking a few capacitors I connected the tripler again. Set dead but the BU208A lived on.

Think. If the new tripler is at fault why isn't it hurting the BU208A? It must be passing a high current through the protection circuit. Fit another tripler. Just the same. Think again. Something connected with the tripler has happened, probably as a result of the original faulty one. This means removing the panel yet again to check through the small items on the protection subpanel. I felt angry and wished the cat was around so that I could kick it.

I shouted out to Honey Bunch "bring the bloody cat in".

"Oh no, not for you to kick it" bawled back H.B. "She's your little pet and the only time you want to kick her is when you can't do your job properly. Kick yourself instead."

I did and it hurt. So I took the panel out and carefully checked the small items on the subpanel. 5D5 was leaky (read both ways). "It's all right dearest, call Spock in, it wasn't her fault it was 5D5."

"Heaven protect us from him" mumbled H.B.

Thought: if a faulty tripler can murder a hefty BU208A it can certainly do in a 1N4148 diode.

The G11

Ah well, a dear old Philips G11 won't be any trouble at all. Probably a short-circuit BU208A, defective 470 μ F h.t. reservoir capacitor, possibly a short-circuit BY223 EW modulator diode and maybe a faulty BD238 EW modulator driver transistor over on the other side. No bother, nice after the agony of the T20.

Take the back off and note that the two 3·15A mains fuses have shattered. Simple, just check the bridge rectifier diodes. Two short-circuit. In went a couple of BY127s and two 3·15A fuses. Bob's your uncle.

Bob's not my uncle and never was. Bang went the two fuses. Check more thoroughly. A short-circuit OT121 thyristor. Well I never. Fit a new one and check carefully for shorts with the degaussing plug out. No shorts found. Fit two new fuses and switch on. Bang.

"Bring that bloody cat in here. She's spoilt rotten and I'm going to let her know who's who around here. This shouldn't happen to a dog. And where is the dog anyway? Never around when he's wanted."

"Ben can't help you dear. The cat can't and neither can I. Besides that the cat's busy eating the dog's toast.

"Why doesn't she eat her own food?"

"She has."

Bloody rotten cat. Everyone's spoilt in this place. Even H.B. It's only me who's not spoilt, flogging myself to death to keep that lot happy. It's not fair.

"It's probably a dry-joint" said H.B. as she went upstairs to talk to the bird. Oh yes, the bird's spoilt as well.

I looked at the G11 again. It looked back out of the corner of its tube and laughed. I'd a spare power panel and was sorely tempted to fit it and forget the whole thing. But no, too easy. Taking the easy way out is not on. At least not till the going gets really rough. I had time. All I needed was patience.

Check the h.t. fuse to ensure it's the right value. I once found a piece of wire across the fuseholder, reflecting the load back to the mains fuses. Not so this time. It was 1A and there were no shorts up top. So we were still on the power panel. Something was shorting on load and didn't live too far from the mains input. Recheck the diodes, recheck the thyristors. I'd replaced one, why not the other? I did and the fuses still went bang. I went through that board with a fine toothcomb, disconnecting this, that and the other, until my attention was caught by a fairly low reading that should have been high with the other components out of circuit. Then I saw it. A black mark on one of the VDRs. It was reading 15 Ω when it shouldn't. So that was it. Voltage dependent be buggered. The battle

was over and we were short of 3-15A fuses. "Come on then nice pussy, there's a pretty girl."

Tinker Tim

A truck pulled up outside. On the back were a load of bits of metal and a couple of old fridges. I groaned to myself. Tim had been over the tip and had no doubt found a discarded TV set he thought I would make as good as new for next to nothing. In he came with a Decca CTV – 18in. Bradford chassis.

"This belongs to my next door neighbour. Asked me to run it down to the best bloke I know."

"You mean the cheapest cheapskate in town Tim."

"Oh no Lawry. We all know you're a fair bloke who's got to make a living."

So I looked at it. It didn't have a plug on the end of the lead, so I proceeded with caution. The meter recorded a dead short across the mains. I took the back off and slid out the chassis. A light shone on the on/off switch showed the brown and blue leads connected together on one tag. Charming.

Teletopics

VCR NEWS

VCR deliveries in the UK showed a further slight fall in the first quarter of 1984. As mentioned in the June Teletopics, deliveries in the final quarter of 1983 fell by 40 per cent in comparison with the same quarter in 1982. The reduction in the first quarter of 1984 was 44 per cent. It seems that the entire W. European market is experiencing a downturn: European Commission figures show a decline of just over 20 per cent in deliveries during the first five months of the year compared to 1983. The Japanese Ministry of International Trade and Industry, which is responsible for overseeing the EEC-Japanese agreement on VCR deliveries, has as a result authorised Japanese VCR manufacturers to lower prices by 5-7 per cent. In contrast, the UK TV market during the first quarter was buoyant, with CTV deliveries up 15.8 per cent (55 per cent in the case of small-screen colour sets).

The point at which the VCR market reaches saturation in the UK is open to speculation. A recent Key Note report suggests that saturation will occur when 60 per cent of households have a VCR, and that this level will not be reached until the next decade.

New releases include the first VHS machines from Pye and Toshiba. The Pye 65VR20 is a front loader with wired remote control and a suggested price of around £420. The Toshiba machines, Model V55B with manual control and V57B with remote control, are being assembled at Toshiba's Plymouth plant from JVC kits. The suggested prices are £450 and £490 respectively. Sony's SLHF100UB Beta hi-fi model, which was first shown at Cetex earlier this year, is now in the shops with a price tag of just under £600. The helical-track sound recording system is similar to that used in VHS hi-fi machines.

Alps Electric, a leading Japanese manufacturer of parts for VCRs, is considering establishing a factory in the UK. Discussions on grants and financial assistance are taking place between the firm and the Department of Trade and Industry.

"Well I'll leave it with you Lawry and call back later."

I shone a light on the volume control again and noted that it was of completely the wrong type: 50kΩ linear instead of 500kΩ logarithmic. Oh well. Out it came and a new control was fitted, wiring the leads to the volume control as found (not to the switch of course). Back went the panel and after a few precautionary checks I switched the set on. Turn up the volume but there's no sound. Turn it down and the sound comes up loud and clear. How can anyone do this sort of thing? I took it out again and reversed the outer contact leads. The sound was now o.k.

Only the height and linearity needed adjustment, despite a distinct crack around the glass base of the PL508 field output valve. We've seen this before however and know that the vacuum's not impaired despite the appearance. I wrote out what I considered to be a very moderate bill (daft really). When Tim returned he threw up his hands in horror. "The old boy'll never pay nearly a tenner for it. He only wanted you to look at it."

I won't tell you how the conversation went after that, but I shan't have the pleasure of Tim's company again. There was no old boy, don't worry about that!

The subject of VCR protection was mentioned in this column last July (Videotek's "cassette" which can be locked and loaded into a machine). AVF Ltd. of Dixon Street, Wolverhampton WV2 2BX have now introduced the Videoguard, a lockable, wall-mounted bracket which can be adjusted to suit most VCRs. The price is around £30. Grundig's new VHS model comes with a built-in lock, and it's understood that other manufacturers are likely to follow suit. Some lock designs permit the machine to make timed recordings despite being locked.

Dealers who stock prerecorded tapes and are unsure which of these might be "video nasties" can obtain a list of some 62 titles from the Metropolitan Police, A3(1) Branch, New Scotland Yard, Broadway, London SW1H 0BG. The list has been prepared by the Director of Public Prosecutions and is periodically updated.

TV SETS

An old TV brand name, Philco, will shortly reappear in the UK. In the fifties Philco TV sets were produced at Chigwell, Essex. When the plant was closed in 1962 Thorn acquired the brand name and marketed Philco sets for a couple of years before dropping it. Recent Philco colour sets have been produced at Milan in a factory acquired by the Italian Philco company from Telefunken two years ago. Philco claim to have 12.5 per cent of the Italian CTV market at present. 22in. Philco sets are to be imported and distributed to independent dealers by CIH. If the move is successful the complete range of models, with tube sizes from 14 to 27in., will be made available in the UK.

Sinclair's 2in. monochrome TV sets, which have previously been available only via mail order, are now being supplied to retail outlets. The suggested price has been increased by £20 to £99.95. Akai is planning to enter the TV field. Sony has introduced in Japan a set whose picture can be reversed from left to right via remote control – it's intended for use in barbers' shops etc. where viewers may be watching programmes via a mirror.

The SGS-Ates 250V RGB output chip (see Teletopics, March) has now gone into production. The type number is TDA8150.

ITT have issued a safety warning concerning models CB502, CB602, CB702, CB0506, CB0606, CB9504 and

CB9604 fitted with control panel types CMC50, CMC54, CMC63 and CMC67. The problem is due to the soldering of the on/off switch. All sets should be modified as follows whenever servicing is carried out. (1) Disconnect from the mains and remove the back. (2) Withdraw the control assembly (four screws). (3) On the CMC50 and CMC54, remove the push-button assembly from the control panel (two screws). (4) Solder four wires (two brown and two blue, approximately 12cm long) to the unused connections on top of the on/off switch, ensuring that the brown leads connect to the live and the blue leads to the neutral terminals. (5) Route these four wires the shortest distance around the PCB to the solder side. (6) Solder to corresponding live and neutral connections at PC lands farthest from the on/off switch solder joints. (7) Strap each positive and negative cable pair together, using a cable tie as close to the soldered connections as possible. (8) Reassemble and test.

CABLE AUTHORITY CHIEF

The government has appointed Richard H. Burton, until last year chairman of Gillette Industries, to be chairman of the Cable Authority which is to license new cable TV companies and supervise services. A second batch of cable licences is expected to be issued during the autumn. A deputy chairman, chief executive and five other authority members are still to be appointed.

Of the eleven originally licensed cable operators, only four have plans to start services soon.

INTERFERENCE



The Department of Trade and Industry has taken over from British Telecom control of the Radio Interference Service, which has been renamed the Radio Investigation Service to reflect its activities more accurately. The RIS at present has some 260 field investigators who check on interference to authorised broadcasting, land mobile radio and emergency services. From now on the RIS will form part of the DTI's Radio Regulatory Division.

The Home Office plans to abolish licensing for various low-power radio devices that include garage-door openers, radio-microphones, radio aids for the deaf and some types of anti-shoplifting tags. Stringent controls on type approval for such devices would remain in force, and manufacturers/importers would have to prove compliance before licence-free appliances could be sold. The DTI has issued a green paper to interested parties for comment. The present licensing regulations will continue until an exemption order is made.

SATELLITE TV

The five firms selected by the government to form a "third force", along with the BBC and the ITV companies, in setting up a UK satellite TV service are Thorn EMI, Granada TV Rentals, S. Pearson, the Virgin Group and Consolidated Satellite Broadcasting. The various parties involved in the proposed UK DBS service have already held meetings at the BBC and have set up working groups to consider various aspects of the project - one of these groups is considering the technical standards to adopt. The Home Secretary has called for a report on the progress of negotiations between the parties by the end of September. Latest estimates put the capital investment required at around £580 million. It seems that the commercial "third force" would prefer a larger stake in the project than initially proposed.

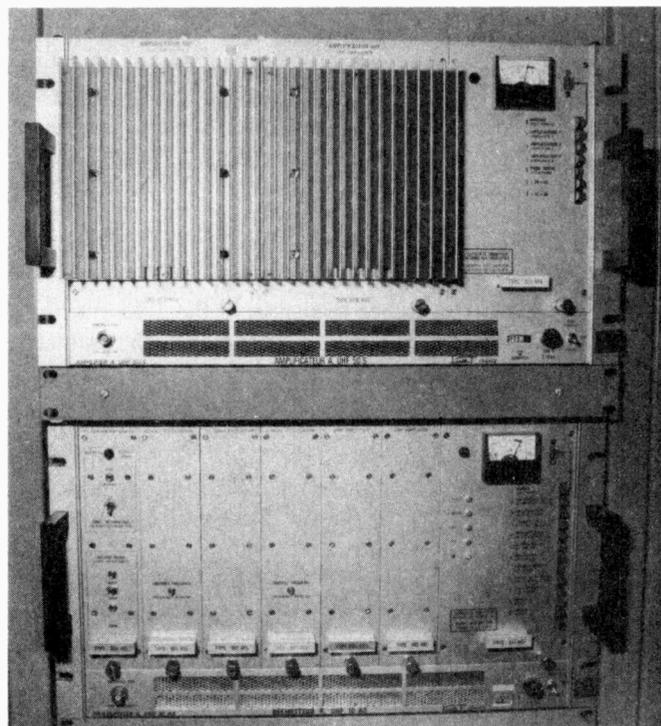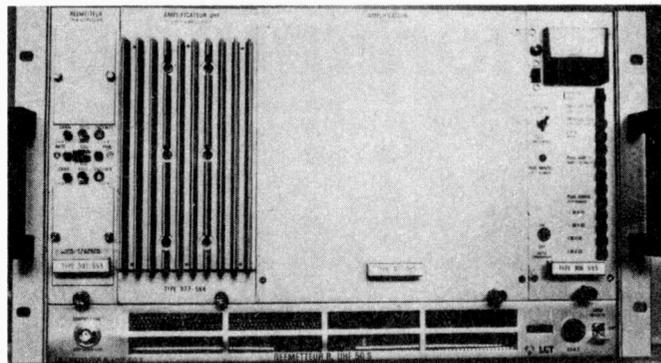Peter Gray, managing director of Satellite TV Antenna



The stolen transmitters: top, the Ch. 4 unit; below, the ITV units.

Systems, says that his firm will be able to supply a complete domestic satellite TV installation - dish, downconverter and receiver - for about £250 when the service starts. He feels that the cost will fall below £100 once demand has developed. Interesting to compare this with the £320 suggested by Luxor recently. There's a large element of guesswork in this sort of thing at present of course.

TRANSMITTER THEFT

Two transmitters have been stolen from the Ivybridge relay station near Ermington, Devon. These were used for ITV and Ch. 4 broadcasts - the older BBC transmitters were left. The Ch. 4 transposer is of LGT (French) make, serial no. 92, receives on ch. 32 and transmits on ch. 49 at 50W. The ITV transmitter consists of two units, both of LGT make: low-power transposer serial no. 9 which receives on ch. 25 and transmits on ch. 42, and amplifier serial number 238. Both sets of equipment were removed by unscrewing from drawer/cabinet frames, with connectors unscrewed and left behind. The equipment is understood to be worth £20,000 and could be used for pirate TV operation. Anyone with any information on this equipment should contact Detective Inspector John Alford, Devon and Cornwall Constabulary, Police Station, Plympton, Plymouth PL7 3AJ (telephone Plymouth 336 471).

Panoramic Spectrum Display

Denis G. Mott

Occasionally in my line of work quantities of multiband varicap tuners have to be repaired and tested. Unless sophisticated test equipment is available, laborious manual realignment is required after transistors and/or varicap diodes have been replaced.

To simplify matters I devised the spectrum display system described in the following article. It's applicable to ATV and DX-TV as well as to tuner alignment. A commercial 1GHz spectrum analyser would cost many hundreds of pounds. The unit described below can be constructed for a fraction of this outlay. A block diagram of unit is shown in Fig. 1.

Description

Many varicap tuners are available in the UK, but there are few Band I/III/u.h.f. types. For the DX-TV enthusiast however a multiband analyser is of greatest use. Fortunately Grundig's European tuners are available, e.g. type 29500-027-07. This incorporates a pin diode attenuator with a control range of 0 to -16dB. The voltage required to tune from ch. 21 to ch. 68 is 0-30V; the tuner requires a 15V supply for Band selection, and 0-12V to operate the attenuator.

As a Grundig tuner was selected for the project it was common sense to partner this with a Grundig i.f. module which will be correctly matched. I.F. module type 29301-022-44 was adopted. Various SAW filters are available for different bandwidths: some to note are OFW431 (4.5MHz), OFW361 (5.5MHz) and OFW362 (6MHz). By earthing pin 7 of the i.c. and taking the output from pin 12, the i.f. amplifier is used as a peak detector, i.e. the a.g.c. system is altered to peak-level detection.

A scope with a Y bandwidth of d.c. to 10MHz is more than adequate. An Hitachi V212 was used, but many similar scopes could be adapted. The drawback with most modern scopes is that a sweep output socket is not provided. In the V212 the sawtooth sweep can be taken from the junction of R551/IC550 pin 15. Unfortunately it's an a.c. waveform (see Fig. 2), so modification is necessary before it can be used to provide the 0-30V tuning voltage for the tuner. This is done by using capacitive coupling, a d.c. restorer, and an operational amplifier to produce the ramp shown in Fig. 3. The circuit is shown in Fig. 4. Depending on the type of scope used, ramps of various amplitudes will be encountered. If it's necessary to alter the amplifier's gain, change the value of the feedback resistor RG.

Use

The flat bottom at the start of the ramp (wait period) is important. This ensures that the varicap diodes are completely discharged (the tuning circuit is of high impedance, with some small stray capacitance in the circuit). If the diodes are not allowed to discharge, the lower end of the band will be missed. The d.c. level preset can be adjusted to alter the wait period - its effect on the display is to shift this to the left or right depending on the length of the wait. The scope's timebase sweep should be about 10msec/cm

for minimum display flicker while allowing the varicap diodes time to discharge fully. If a faster sweep is used the diodes will not recover and the start of the sweep will be chopped off.

Fig. 5 shows the spectrum of an internal cable signal distribution system we use. Peak 1 is ch. 37, peak 2 ch. 44, peak 3 ch. 47, peak 4 ch. 55 and peak 5 ch. 68. The signal input level at the aerial socket is 1mV except for ch. 47.

The equipment described consists at present of a group of modules forming part of another piece of equipment that's used for aligning tuners. The more adventurous enthusiast could add a frequency marker and a more elaborate attenuator, thus achieving a more definitive signal measuring set.

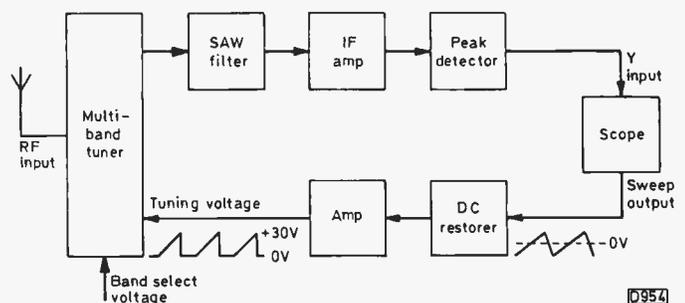


Fig. 1: Block diagram of the unit.

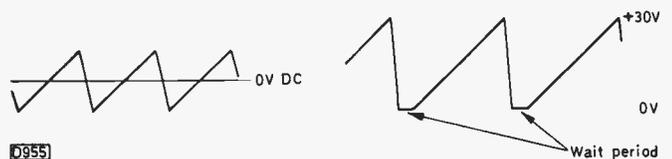


Fig. 2 (left): A.C. sawtooth waveform.

Fig. 3 (right): Waveform obtained after processing.

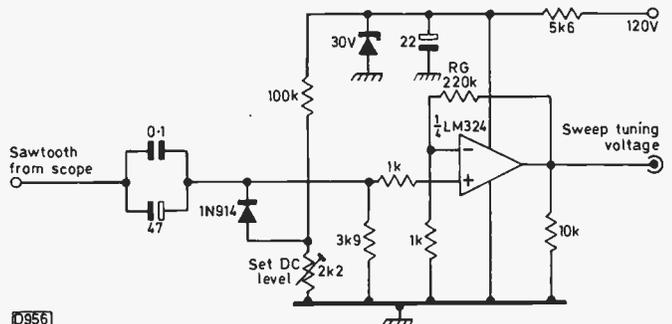


Fig. 4: D.C. restorer and amplifier circuit.

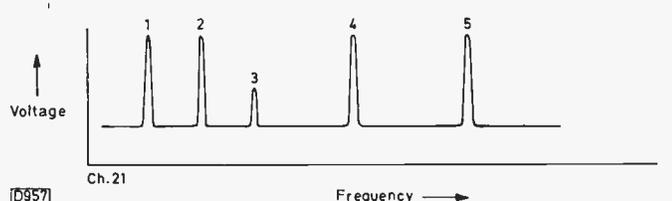


Fig. 5: Spectrum display of a cable signal distribution system - see text.

Pre-War Television

Harold Peters

"As I was saying before we were interrupted..." Leslie Mitchell's opening words when 405-line television recommenced after the 1939-45 war began an era of technology and discovery that this magazine has covered faithfully, from the conversion of VCR97 radar c.r.t.s to TV use at the beginning to the current offerings of ECS-1. But what of those three years of TV before the war, when the technical features of TV broadcasting were being established? My boyhood days were spent in SE London, which gave me a view of those eventful years...

Crystal Palace

It was 1936. "The Crystal Palace is on fire!" Pausing only to finish scorching my gym shorts for tomorrow's PE I rushed to join neighbours at the local vantage point, a railway footbridge from which we used to get a free view of the celebrated "Brocks Benefit" firework displays. I was witnessing the ultimate in bonfires, the destruction of Crystal Palace itself.

As the hot ash from three miles away rained down upon us we queried how something built entirely of iron and glass could catch fire so readily. We didn't know then about the spontaneous combustion of decades of rubbish that had been swept through the gaps in the Palace's wooden floorboards, so we laid the blame fairly and squarely on "that Mr. Baird" who had been carrying out television experiments in part of the building close to the South Tower. We were not the only ones to do so apparently, as the papers next day put great stress on the fact that Baird's experimental work had suffered little damage in the conflagration.

Low-definition TV

Baird wasn't exactly Top of the Pops in the early thirties. For several evenings we were deprived of our wireless entertainment while the BBC allowed him to transmit his experimental 30-line low-definition TV broadcasts. These took up prime listening time, with the vision content radiated (it sounded like bagpipes warming up) on the National programme while the accompanying sound (meaningless to anyone without a Nipkow disc set) hogged the alternative Regional programme.

Even if you had a Nipkow disc set only one eye at a time could watch the tiny 2 x 2in. picture, while the rest of the family stood in mortal danger of being impaled by the flying disc as it spun loose from its spindle, loosened by progressive attempts at controlling the motor speed to obtain a stationary picture.

Alternative Systems

Rumour had it that Baird's work at Crystal Palace involved a much higher definition picture, including colour. However true it was, the real breakthroughs were taking place in the EMI laboratories at Hayes. In addition to developing the 405-line TV system we are only just dismantling today, the EMI team had discovered a way of detecting approaching aircraft. They called this Radiolocation (later Americanised to Radar), and with

Hitler's sabre rattling the full import of their work was not wasted on the military of the time. So secrecy became a problem, especially with factories making high-frequency equipment.

EMI's development of the 405-line system embraced the whole package – cameras, transmitters, receivers, outside broadcast units and the tubes and circuitry required. It's incredible to reflect that the whole lot, which still forms the basis of the world's TV systems as we know them today, was developed in the comparatively short time span of eighteen months.

Getting the BBC to adopt the EMI system was not a straightforward business however. The BBC has a history of backing the wrong horses (405 lines postwar, NTSC colour in the early sixties, EMI Percival stereo radio and lately Extended-PAL for satellite TV), and they owed a certain allegiance to Baird who'd promised them a high-definition system. A Royal Commission had failed to make a decision between the two systems, so when the BBC's TV service started in November 1936 it was on a trial basis, one week with the Baird 202-line system, the next week with the EMI 405-line system, and so on. Many of the first TV sets produced to receive the service were switchable, 202/405 dual standard receivers.

There was soon little doubt as to what the outcome of this trial operation would be. The problem that Baird had was that he could offer TV only via an intermediate film process. The studio, in darkness, was scanned by a flying spot of light, its reflected output being recorded on 35mm cine film. This film was rapidly processed and passed through a telecine machine whilst still wet, with a delay of about a minute – at the end of a programme the artists could nip round the back to see the last few seconds of their performance as it went out. It followed too that the sound quality was reduced, to the same order as current cinema sound, since it had to be delayed to synchronise with the vision. The equipment was clumsy and immobile. By comparison the EMI system offered a choice of viewpoints from three mobile cameras mounted on rubber tyred dollies or a standard Vinten film studio crane, with mixing facilities similar to those used for sound broadcasting. The cameras operated satisfactorily in natural (cloudy) daylight and with stage lighting, and under studio conditions with lighting as used by the film industry they could be stopped down to give a very good depth of focus.

The 405-line Specification

Even looked at fifty years on, the original 405-line specification is impressive. The number of lines was chosen so that it would be easy to divide down from the line scan rate of 10,125Hz (c/s in those days) to a field rate of 25Hz. Interlacing was used to reduce flicker, and blanking periods were provided so that the scanning spot would be blacked out during the line and field flyback times. For a 1V peak-to-peak signal, white was 1V, black 0.3V and anything "blacker than black" was used for synchronisation. Gamma correction of the grey scale was provided to compensate for the Ia/Vg characteristics of valves and c.r.t.s. The transmitters at Alexandra Palace were amplitude modulated with positive video (i.e. white

represented 100 per cent modulation), using a 45MHz carrier and double-sideband operation. The sound also used a.m., with a 41.5MHz carrier. I seem to remember that the transmitter and its twin stacked arrays of wire dipoles managed about 16kW e.r.p. of vision. It soon became clear that the initial "line of sight" reception predictions were wholly wrong – good results were obtained in the Bromley/Beckenham area which was in shadow from the transmitter by virtue of the Upper Norwood ridge.

Alexandra Palace

There were two studios and a telecine suite at Ally Pally. Both studios were tiny by today's standards, and each control room ran three cameras. Both studios could be linked for major productions, and to make this possible the multicore cables that connected the cameras to the control rooms and thence to the master sync pulse generator were made identical in length to avoid phase errors in mixing. In the original Emitron and Super-Emitron camera tubes the gun was mounted at an angle to the target, instead of the gun/target/photocathode being in line as in the later orthicon type tubes. This meant that unless corrected the image would be trapezoidal in shape and darker at one end than the other. This fact accounted for the gentle and intimate production techniques that were used. Every shot had to be corrected by the operator on the "racks" (one operator per producer, sitting in front of the producer). He corrected for "tilt and bend" distortion by introducing variable sawtooth waveforms as the scene changed.

As now, the cameraman sitting on the dolly merely composed the picture and carried out optical focusing, looking at the scene upside down in an optical viewfinder coupled to the lens. This arrangement permitted a degree of "overscan" so that he could see the other cameras approaching his field of view before they got into his picture. To chop from one camera to another was impractical. Slow dissolves of between five-ten seconds were made, during which the rack operator had time to correct the distortions without perceptibly disturbing the viewer. This quiet method of presentation became so well established that when the orthicon type tube (the first was the CPS Emitron) came on the scene in the early fifties almost all the critics accused the producers of "restless editing". Though most film was shot at 24 f.p.s., telecine ran at 25 f.p.s.: the change in sound pitch was regarded as being acceptable.

Outside Broadcasts

One of the first big TV events was the Coronation of King George VI. For this, two OB units were commissioned. One of them, MCR1, was ready by the day. Each unit was housed in three single-decker bus shells, one a control van for the three cameras and sound, another as an equipment tender and the third a generator van to provide the current. A coaxial cable had already been laid through central London, to be within reach of theatreland and the Olympia exhibition building. This cable conveyed the video signal from the events happening close to its route via Broadcasting House to Ally Pally.

Events off the cable route called for the services of a fourth van, the vision transmitter, which provided an off-air link on what is now Ch. 2 to a reception point on Highgate Hill where it was demodulated and piped as

video via coaxial cable to Ally Pally – image rejection techniques were not good enough at the time to allow a pickup receiver to be co-sited on the A.P. mast. The OB unit's transmitting aerial was a horizontally-polarised H type mounted atop a standard Merryweather fire escape ladder.

The Programmes

What of the programmes we watched in the pre-war era? It didn't take long for a pattern to emerge. Up to two hours of general interest programmes in the afternoon, with evening transmissions from 7-10p.m. Saturday night was variety night and because of the intimate nature of the medium Cabaret Cruise became quite popular. Commander A.B. Cambell (later of the Brains' Trust) hosted the show on the deck of a cruise ship with music provided by the BBC Television Orchestra. Plays were performed twice, on Sundays and Thursdays, to justify the settings. They had intervals between acts and a warning bell, as in a theatre bar, to tell of their resumption – a habit carried on almost to the coming of ITV in the fifties.

C.H. Middleton planted vegetables in a patch dug out of the lawn in the A.P. grounds, becoming the forerunner of Gardeners' World, and the three presenters were Leslie Mitchell, whose voice was already familiar from Movietone News, blonde Jasmine Bligh who would go anywhere and try anything, and Elizabeth Cowell who added dignity to any occasion. They would always walk on in evening dress, approaching the camera from a full length view and stopping well before their waists went off the bottom of the screen. Strangely, this three-quarter length view is currently used by the Russians seen via Gorizont!

The precursor of Tonight and Nationwide was Picture Page: Joan Miller operated a dummy video switchboard to introduce celebrities who happened to be in town. Corny? Well, it seemed all right at the time!

The two classic OBs were Wimbledon, which hasn't changed a bit, and the Boat Race. The two OB units were used for the latter event, one at Putney for the start and the other at Mortlake on the finishing line. In between, while the boats were out of sight from either end, we were taken back to the studio where we were shown the progress of the race with a pointer and map whilst listening to John Snagge's radio commentary.

Jasmine Bligh's visits to London Zoo were popular, as were excerpts from West End shows. Even then the entertainment profession was canny about letting you see the whole thing. The pantomime from the Grand Theatre, Croydon, became an annual event at Christmas. It ended in disaster one year when MCR1 suffered a major equipment fire and MCR2 overheated and failed. Another major event was Radiolympia, the early autumn radio show where the latest sets were on show to the public.

The Sets

The pre-war sets had screen sizes of 5-12in. with prices ranging from £28 to £100 – much the same as today, but with the spending power of the pound thirty times as great. Even with wages averaging around £3 a week, 20,000 homes had TV by the summer of 1939.

Flyback e.h.t. had not come into use, the mains derived (lethal) e.h.t. supply being of some 5-8kV. Subdued room lighting was needed, but it was not as dark as at the flicks. Most valves were octal based though some sets had the

old, large 7-pin types. Both t.r.f. and superhet circuits were used, with the i.f.s going no higher than 10MHz. Blocking oscillator or thyatron timebase generators were employed and magnetic deflection was the rule, though one or two electrostatic tubes were used. Philips nearly gave the radar game away by offering a set with a green screen! Radiogram cabinets were often adapted, with a mirror in the lid and the tube mounted vertically with the field coils reversed.

Being "Saturday boy" at a local dealer, most of my viewing was done on our demonstration model – a 5in. Cossor with no sound! To get sound you had to connect the audio output to the pick-up socket of your radio receiver. Many cheap sets did it this way. At the other end of the range, Baird had linked with Scophony to market a rear projection set with a ground glass screen measuring about 2ft 6in. x 2ft. The modulated light beam scanned the screen via a rotating mirror drum and you had to turn the sound up to cover the motor's noise!

Test Cards

I cannot remember seeing a test card as such. There was the tuning signal which was transmitted on film five minutes before the start of programmes. This had a mid-grey background, two small grey scales and a central circle which contained vertical focusing bars. I doubt if the edge was castellated. At times a mixed programme of documentary films was put out in the mornings for demonstration purposes. An electronic pattern consisting of a black cross on white, known to the BBC as "art bars", was available from the master pulse generator by taking suitable squarewaves from the counting chain.

At the end of evening programmes the radio symphony concerts would sometimes be radiated in sound only to take advantage of the full bandwidth v.h.f. transmissions. I was never up late enough to see what, if anything, was transmitted on the vision channel at the same time.

Radiolympia 1939

As previously mentioned, the various models available were shown annually at Radiolympia, which was more of a public affair than a trade show. Extended television hours permitted demonstrations throughout most of the show's opening time and as the years progressed things got more sophisticated. In 1939 a closed-circuit TV network and a huge theatrical set gave us the thrill of being in on a live broadcast. Even programmes for radio listeners, such as the Kentucky Minstrels, were televised within the exhibition. Lionel Gamlin, the first announcer to introduce humour to the work and survive the wrath of Lord Reith, acted as the anchor man.

Close Down

The queues were missing however. The antics of Mickey Mouse on the huge Scophony Baird screen attracted no attention. People gathered around the few battery portables that could pick up outside news bulletins despite Olympia's screening. It was Saturday, September 2nd.

Next day Chamberlain made his famous speech, the sirens sounded their first warning wails, and one very frightened youth ran indoors to find his gas-mask case. The world's first public television service had come to a halt.

next month in

TELEVISION

ANOTHER BUMPER ISSUE!

The November issue will contain Video Info Card 2 and extra pages.

● ALL ABOUT LENSES

Many find the subject of lenses confusing, but an understanding of their action is essential for successful camera work. Vivian Capel describes lens types and characteristics and how to get the best from them.

● COLOUR MONITORS

Part 2 of our Monitors feature concentrates on display devices and standard signal formats. The various types of colour tubes in use and their capabilities are described.

● VCR REMOTES

Derek Snelling surveys the various types of remote control used with VCRs and provides guidance on fault conditions.

● VARIABLE FREQUENCY SOUND UNIT

A variety of sound-vision spacings are used for satellite TV, varying from 5.5-7MHz. For reception of these signals a variable frequency demodulator is thus required. Hugh Cocks describes a suitable circuit using a TDA1190Z chip.

● GRUNDIG'S VHS MACHINE

Steve Beeching on the technical features of Grundig's VS200 VHS machine.

● SIMPLE PROJECTS

Uncle Jim's Patent Tube Tester – Jim Littler describes a simple tester/reactivator using the mains transformer from the Decca 10/30 chassis. Peter Dolman has devised a 30V battery eliminator using a spare line oscillator coil. Roger Bunney provides details of an i.f. selectivity unit to replace the G8 type.

PLUS ALL THE REGULAR FEATURES

ORDER YOUR COPY ON THE FORM BELOW:

TO
(Name of Newsagent)

Please reserve/deliver the November issue of TELEVISION (£1), on sale October 17th, and continue every month until further notice.

NAME

ADDRESS

.....

.....

Servicing the Grundig 2x4 Super

Part 4

Mike Phelan

The motor connection board behind the tape deck is probably the most awkward of the modules to work on – there are plugs and sockets connected to both the top and bottom edges. The best that can be done is to pull the board up as far as it will go, to the extent of the leads.

A couple of important points here. The insulating sheet must always be replaced, otherwise the “tea-tray” will short out any long leads on the print side of the panel. Also make sure that the plugs are correctly fitted – there’s one spare edge connector at the bottom, next to plug L6. Fortunately most machines have plug connection diagrams on the tea-tray and on the head preamplifier cover below the deck.

Various troubles can be encountered on this board – autostop failures come high on the list. As the cassette is of the turnover type, the two sensors are stacked one above the other – the roles are reversed when the cassette is turned over. They operate by sensing the difference in reflection between the normal tape and the stop foils.

Two operational-amplifiers are wired as a type of comparator, with the two optosensors connected to opposite sense inputs of each. The other two inputs are connected to a potential divider. The outputs close electronic switches in the key/switch scans to the microcomputer. See Fig. 7.

Failure of either autostop will result in the end of the tape being pulled out of the reel. This can be repaired quite easily. Grundig cassettes use adhesive tape to attach the ends, Philips cassettes use a small plastic peg – don’t lose it.

For autostop testing and adjustment a useful tool consists of a strip of Paxolin or similar material with a piece of tape and stop foil glued to each end – see Fig. 8 (a). With a cassette inserted, first check that the voltage at test point MA1 (top of panel) is about 2.5V. Remove the cassette, lower the carriage by operating the switch on the front flap, engage fast forward or rewind and use the foil on the gadget to reflect on to the stop sensor. The voltage at MA1 should rise to about 4V or drop to about 1.2V depending on which sensor is energised: one sensor only will cause the machine to stop, depending of whether fast forward or rewind was selected. Problems are usually due to wires broken off a sensor, adjustment of the preset BEA or, less frequently, failure of the operational amplifier IC1210 (LM324). The gadget prevents pulling the ends out of your entire tape collection – the speed at which this machine winds doesn’t give you much time to find the stop key if test point MA1 doesn’t do its stuff! Another cause of problems here, sometimes intermittent, is a hairline crack across edge connector L3 due to rough handling.

The other half of IC1210, together with transistors T1248 and T1251 (BD616 or BD898), drive the two reel motors. Two control voltages come from the microcomputer. In the event of failure of either transistor replace them both, together with IC1210, and before switching on check R1211/R1232 (both 2.7Ω) for being open-circuit.

The two reel tacho signals are amplified and converted to fixed width pulses on this panel – if either is absent or

low in amplitude the autostop will be slow to operate and the “P-time” indication may give strange readings or display “cass” even with a tape inserted. Low reel motor torque on playback is usually the result of the 12V supply being low – see Part 1, July. For APF and fast wind, T1254 switches the supply to 20V.

The loading motor is driven from IC1230 (L293B) which occasionally goes short-circuit, causing the power supply to trip – check by disconnecting plug CP3.

Up to now we’ve not had any problems with the head motor drive circuit, though the motor itself sometimes develops an intermittent fault, refusing to start and locking up. This is caused by a shorted turn in one of the stator windings. Two different motors (Siemens and Papst) have been fitted: the stators are of different diameters but are interchangeable provided the rotor is also changed.

The Deck

The tape deck is very robust. The lower drum and all tape guides are mounted on a massive casting which also provides screening for the head preamplifier. The DTF will try to compensate for any tape path errors, so it’s not much use looking at the shape of the f.m. envelope – the only way to check the tape path is to look at the DTF waveforms on the two slipping brushes, using a double-beam scope. The active period should be as nearly flat as possible (see Fig. 9).

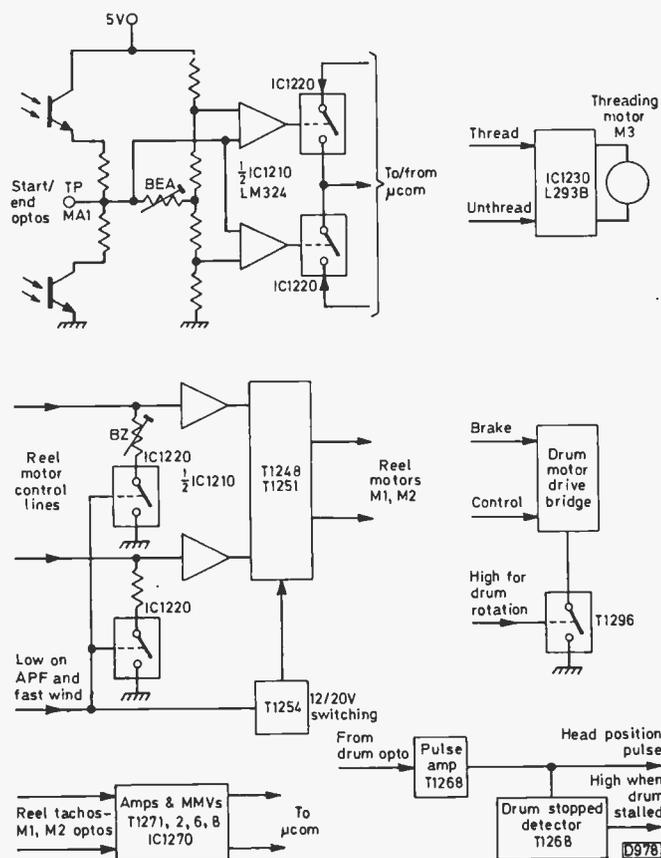


Fig. 7: Motor connection board block diagram.

D979

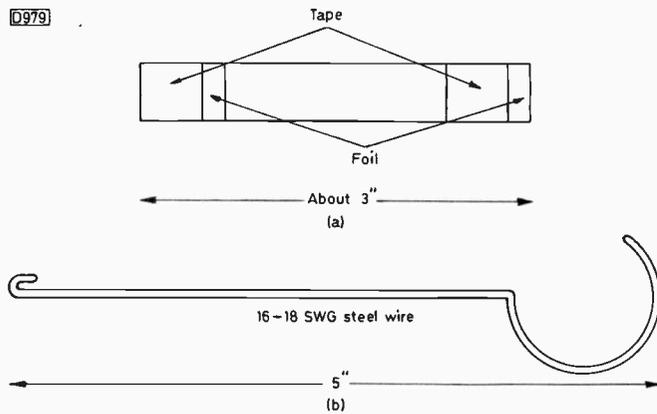


Fig. 8: Simple servicing aids.


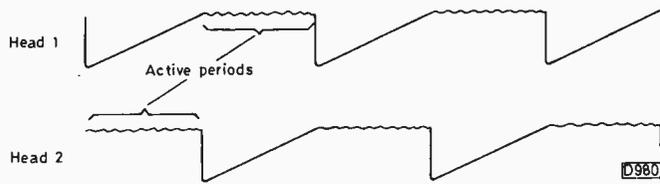


Fig. 9: DTF waveforms at slipping brushes.

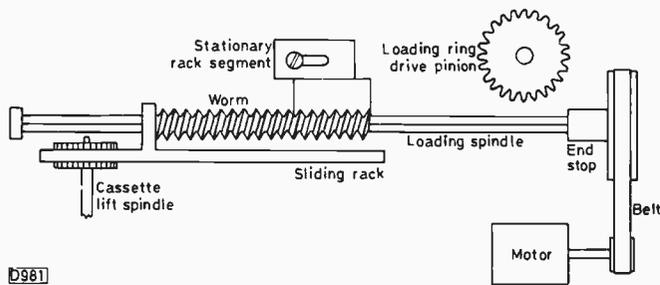

D981

Fig. 10: The loading mechanism.

Don't be tempted to twiddle any of the tape guides: most tape path problems can be blamed on things like ridges of tape oxide on the capstan or in the lower drum groove.

There are various switches associated with the tape deck. Two of them correspond with the unload and after load switches on VHS machines, but their operation is slightly different. Conductive segments on the loading ring short out the switch contacts, which occasionally lose their tension and need bending slightly. If the unload switch doesn't close the machine won't accept a cassette and the reel motors will rotate all the time. If the other switch isn't making the only apparent effect is that the tape will unthread in record pause.

There's another switch that's operated by the end of the loading rack. Any problems here will result in the ring oscillating in stop, fast forward and rewind.

Occasionally the cassette flap fails to close completely when there's a cassette inserted. This is usually because the leads to the microswitch under the lower flap are protruding and being trapped when the carriage descends.

It's possible for the two sides of the cassette carriage to get out of step with each other - in other words the carriage is tilted. The removal method may not be obvious, making it very hard to take out and replace the cassette lift. The only special tool required is a wire hook - see Fig. 8 (b). Remove the transparent front flap, unhook the two long springs and remove them. The carriage will then lift out. When replacing it, engage the first tooth on each rack with the marked pinion tooth, then hook each

spring on to the gadget after passing the latter up from below the deck in the space where the spring goes. Hook the top end of the spring on, then pull the lower end through and hook it on. Replace the flap and away you go!

While on the subject of the cassette lift, one common fault is that after ejecting a cassette the machine immediately reloads. The eject slides are smeared with a slightly sticky grease that collects dust. As a result they stick. If the cassette doesn't slide forward on ejection the microswitch recloses and the cassette is loaded again. The cure is to clean off all the grease then apply a light smear of Vaseline. With no grease at all the machine is quite capable of firing a cassette across the room!

Head replacement is simple, but follow the directions about shims on the spindle given in the manual. Too few and the head will come to a grinding halt after an hour or so as the casting expands and the two sections of the rotary transformer rub together. Be careful not to lose the aluminium collar from inside the motor, and replace the spring with its largest diameter section next to the rotor. The screw needn't be very tight, but lock it with a dab of cellulose paint. Make sure that all wiring is securely clipped in position and can't foul any rotating parts.

Loading Mechanism

This article would not be complete without a description of the loading mechanism (see Fig. 10) which combines the two tasks of loading the cassette, i.e. lowering the cassette lift, and tape threading, i.e. turning the loading ring. This is achieved with the minimum of parts. The worm is free to slide on the spindle but can't turn independently of it due to a longitudinal flat on the latter. The sliding rack operates the cassette lift by turning its spindle. The drive is shown in the rest position in Fig. 10, i.e. with no cassette inserted. When a cassette is inserted the motor runs and the worm turns, screwing itself along the stationary segment and allowing the rack to follow it under tension from the two springs that pull the cassette lift down. Once the cassette is down the worm is up against the end stop and just clear of the stationary rack segment: it's now engaged with the loading ring drive pinion. Because the worm has screwed itself along the segment, it does the same with the pinion, but the latter doesn't turn (yet). When the motor is energised again (on selecting playback etc.) the worm drives the loading ring. There's also a locking bolt (not shown), operated by the sliding rack, to retain the loading ring at its extremes of travel.

Faults here are unusual. The adjustment of the segment is critical however: it must engage the worm cleanly when the latter is just entering the pinion. If not, the end tooth of the segment and the end of the worm thread get damaged. This process is self-perpetuating, the mechanism doing machine-gun impressions on completion of loading.

In Conclusion

Finally, someone asked for further details on the recording we made for dropout adjustment (page 556, Part 2). The small piece of adhesive tape we stuck on the lower drum, about half way round, towards the top, where the tape travels, was about 1/4 in. square. Don't use Sellotape: masking tape is suitable. And don't forget to remove it!

That's all for now on the Grundig. Next month a little chat about cameras, in particular the Ferguson 3V06/3V17/3V20.

ECONOMIC DEVICES, PO BOX 228, TELFORD TF2 8QP

18029	1.58	2SC1061	0.54	2SD8986	2.67	AN320	4.97	BC171	0.10	BD186	0.38	BF137	0.11	BLY49	2.00	BY203/20	0.18
18181	1.13	2SC1096	1.05	40406	0.45	AN322	4.30	BC172	0.09	BD188	0.66	BF152	0.28	BR100	0.20	BY206	0.22
18182	1.10	2SC1104	2.80	40694	1.39	AN331	2.99	BC172B	0.24	BD175	0.39	BF153	0.52	BR101	0.37	BY207	0.17
18334	0.80	2SC1106	4.12	40695	1.39	AN337	3.99	BC173	0.15	BD177	0.29	BF154	0.23	BR103	0.45	BY210-400	0.24
18336	0.72	2SC1114	5.81	40636	0.86	AN340P	3.06	BC174B	0.24	BD179	0.49	BF157	0.23	BR888	0.58	BY210-800	0.27
18446	0.89	2SC1124	1.10	40871	1.39	AN355	3.36	BC177	0.18	BD181	0.90	BF158	0.16	BRC-M-300	1.50	BY210-900	0.30
18800	1.25	2SC1151A	4.29	40872	1.39	AN362	1.47	BC178	0.23	BD182	0.90	BF159	0.16	BRC116	0.80	BY223	0.85
18799	2.16	2SC1152	4.25	60857	1.10	AN511	2.34	BC179	0.08	BD184	1.10	BF167	0.28	BRC1300	1.80	BY224-400	0.90
18801	0.86	2SC1157	4.12	74LS132	0.72	AN5132	3.99	BC182	0.23	BD187	0.48	BF173	0.30	BRC300	1.82	BY225-100	0.79
18802	1.03	2SC1162	0.95	74LS136	0.85	AN5250	3.33	BC182B	0.09	BD188	0.25	BF177	0.50	BRC4444	1.12	BY226	0.28
18803	4.81	2SC1172	1.92	74LS157	0.79	AN5435	2.80	BC182L	0.09	BD189	0.35	BF178	0.38	BRC4444	1.12	BY227	0.44
18905	1.35	2SC1195	2.83	74LS161AN	1.18	AN5610	6.75	BC182LB	0.12	BD190	0.59	BF178	0.38	BRC5296	0.70	BY228	0.54
17074	6.00	2SC1213	0.75	74LS196	1.25	AN5613	3.72	BC183	0.09	BD201	0.54	BF179	0.32	BRC6100	0.75	BY255	0.97
17127	3.91	2SC1226	1.32	74LS200	0.25	AN5620X	4.63	BC183L	0.09	BD202	0.54	BF180	0.32	BRC62	0.98	BY298	0.25
17376	1.43	2SC1306	0.85	74LS244	1.65	AN6320N	3.89	BC183LB	0.23	BD203	0.54	BF181	0.29	BRC83	0.98	BY299	0.25
1N4001	0.85	2SC1307	1.35	74LS300	0.29	AN6342	1.36	BC184	0.09	BD204	0.54	BF182	0.30	BRC94	0.98	BY4764	0.76
1N4002	0.85	2SC1316	3.40	74LS367	1.05	AN6344	4.88	BC184L	0.09	BD207	1.00	BF183	0.35	BRX44	0.54	BYV56	0.30
1N4003	0.85	2SC1384	0.49	74LS373	1.55	AN6363	10.20	BC184LB	0.23	BD208	1.00	BF184	0.39	BRX49	0.45	BYX10	0.28
1N4004	0.85	2SC1383	1.39	74LS447	1.05	AN6551	0.56	BC186	0.18	BD222	0.44	BF185	0.35	BRX49	0.45	BYX10	0.28
1N4005	0.85	2SC1398	0.51	74LS573	0.39	AN6552	0.52	BC187	0.24	BD225	0.44	BF185	0.35	BRX49	0.45	BYX10	0.28
1N4006	0.85	2SC1410	2.17	74LS74	0.39	AN7145	2.24	BC204	0.14	BD228	0.57	BF195	0.12	BRX49	0.45	BYX10	0.28
1N4007	0.85	2SC1413	3.88	74LS75	0.52	AN7150	2.02	BC207	0.12	BD229	0.63	BF196	0.15	BRX49	0.45	BYX10	0.28
1N4148	0.85	2SC1505	0.56	74LS86	0.49	AN7151	2.05	BC212	0.10	BD231	0.45	BF197	0.14	BSS38	0.30	BYX94	0.85
1N4448	0.12	2SC1578	6.67	74LS90	0.75	AN7156	2.05	BC212B	0.23	BD232	0.44	BF198	0.15	BSTBD1409	2.48	BYV56	1.09
1N5401	0.12	2SC1617	3.35	74LS92	0.75	AN7158	2.34	BC212L	0.09	BD234	0.38	BF199	0.15	BSTBD1405	4.37	BZV15-C12	0.72
1N5402	0.13	2SC1670	2.84	74LS93	0.75	AN7218	1.49	BC212LB	0.23	BD235	0.45	BF200	0.33	BSTC0146	2.25	BZV15-C12R	0.72
1N5403	0.14	2SC1678	1.25	74LS95B	0.85	AP58076	4.25	BC213	0.09	BD236	0.45	BF216	0.32	BSTC0233	2.25	BZV15-C24	0.72
1N5404	0.15	2SC1810	1.40	7805 TO-220	0.63	AS560S	1.43	BC213L	0.09	BD237	0.38	BF218	0.50	BSTC0246	4.51	BZV15-C24R	0.72
1N5408	0.18	2SC1815	0.41	7805 TO-3	1.05	AU106	1.96	BC213LB	0.23	BD238	0.29	BF222	0.15	BSTC0246	0.71	BZV15-C30R	0.72
1N914	0.85	2SC1829	2.01	7806	0.88	AU110	1.96	BC214	0.09	BD239	0.44	BF224	0.15	BSTC03146	0.71	BZV15-C40	0.72
1S44	0.06	2SC1875	4.77	7808	0.54	AU113	2.15	BC214L	0.12	BD240	0.36	BF224	0.59	BSTC03146	0.71	BZV15-C40R	0.72
1S5012A	0.73	2SC1891	3.35	7812 TO-3	1.05	AY102	2.62	BC214LB	0.23	BD240D	0.47	BF240	0.15	BSTC0343	2.79	BZV15-C12	0.72
1S821	0.09	2SC1929	2.25	7812 TO-220	1.05	AY105K	1.89	BC225	0.24	BD241	0.45	BF241	0.15	BSTC0343	3.06	BZV15-C12R	0.72
2S82	1.94	2SC1942	5.70	7815	0.55	AY106	1.98	BC237	0.09	BD242	0.45	BF241	0.15	BSTC0343	2.79	BZV15-C12R	0.72
2N1302	0.24	2SC1946	1.11	7818	0.55	BA102	0.30	BC238	0.09	BD243	0.44	BF245A	0.33	BSTC0343	0.71	BZV15-C12R	0.72
2N1303	0.34	2SC1953	4.75	7824	1.75	BA1310 (IC)	1.72	BC238A	0.09	BD243A	0.44	BF255	0.59	BSTC0343	0.71	BZV15-C12R	0.72
2N2218	0.38	2SC1957	0.86	AC107	0.86	BA1320 (IC)	1.22	BC238B	0.09	BD244	0.44	BF256	0.25	BSTC0343	0.71	BZV15-C12R	0.72
2N2219A	0.29	2SC1959	0.36	AC117	0.39	BA1330 (IC)	1.82	BC251A	0.15	BD244A	0.44	BF256LC	0.25	BSTC0343	0.71	BZV15-C12R	0.72
2N2222	0.34	2SC1962	1.75	AC122K	0.39	BA145	0.17	BC252	0.12	BD245C	0.08	BF257	0.25	BSTC0343	0.71	BZV15-C12R	0.72
2N2646	0.75	2SC1969	2.92	AC128	0.28	BA154	0.08	BC258	0.22	BD246C	0.08	BF258	0.25	BSTC0343	0.71	BZV15-C12R	0.72
2N2904	0.32	2SC2027	2.67	AC138	0.08	BA155-01	0.12	BC261A	0.20	BD253	0.95	BF259	0.30	BSTC0343	0.71	BZV15-C12R	0.72
2N2905	0.39	2SC2028	1.91	AC141	0.26	BA156	0.12	BC262	0.45	BD278A	0.00	BF262	0.51	BSTC0343	0.71	BZV15-C12R	0.72
2N2906	0.34	2SC2029	1.49	AC142K	0.39	BA157	0.17	BC267	0.45	BD317	1.96	BF263	0.51	BSTC0343	0.71	BZV15-C12R	0.72
2N3053	0.24	2SC2057	1.07	AC151	0.25	BA159	0.12	BC294	0.45	BD318	2.08	BF264	0.33	BSTC0343	0.71	BZV15-C12R	0.72
2N3054	0.90	2SC2073	1.40	AC153	0.30	BA182	0.17	BC301	0.36	BD375	0.38	BF271	0.30	BSTC0343	0.71	BZV15-C12R	0.72
2N3055	0.55	2SC2078	1.25	AC153K	0.36	BA222 (IC)	1.26	BC302	0.12	BD377	0.23	BF271	0.30	BSTC0343	0.71	BZV15-C12R	0.72
2N3055H	0.77	2SC2091	0.59	AC176	0.17	BA284/2	0.15	BC303	0.39	BD379	0.69	BF274	0.18	BSTC0343	0.71	BZV15-C12R	0.72
2N3442	1.05	2SC2122A	4.85	AC176K	0.40	BA301 (IC)	0.92	BC307	0.04	BD380	0.69	BF274	0.18	BSTC0343	0.71	BZV15-C12R	0.72
2N3702	0.12	2SC2141	1.69	AC179	0.25	BA302	1.06	BC307A	0.14	BD410	5.40	BF336	0.27	BSTC0343	0.71	BZV15-C12R	0.72
2N3703	0.12	2SC2166	1.35	AC183	0.65	BA311 (IC)	0.96	BC308	0.12	BD412	0.74	BF337	0.36	BSTC0343	0.71	BZV15-C12R	0.72
2N3704	0.12	2SC2216	0.62	AC186	0.30	BA312 (IC)	0.96	BC308A	0.09	BD418	0.76	BF338	0.36	BSTC0343	0.71	BZV15-C12R	0.72
2N3705	0.12	2SC2233	2.20	AC186K	0.50	BA313 (IC)	1.28	BC309	0.15	BD433	0.33	BF356	0.36	BSTC0343	0.71	BZV15-C12R	0.72
2N3706	0.12	2SC2271	3.84	AC187	0.35	BA316	0.07	BC317A	0.11	BD434	0.39	BF362	0.54	BSTC0343	0.71	BZV15-C12R	0.72
2N3707	0.14	2SC2278	1.03	AC187-01	0.40	BA317	0.07	BC323	0.32	BD435	0.42	BF363	0.54	BSTC0343	0.71	BZV15-C12R	0.72
2N3711	0.14	2SC2335-KIT	7.61	AC187K	0.39	BA318	0.08	BC327	0.10	BD436	0.42	BF371	0.45	BSTC0343	0.71	BZV15-C12R	0.72
2N3771	1.85	2SC2526	1.70	AC188	0.33	BA328 (IC)	0.80	BC328	0.15	BD437	0.41	BF391	0.36	BSTC0343	0.71	BZV15-C12R	0.72
2N3772	1.55	2SC2551	0.95	AC188-01	0.40	BA333 (IC)	1.24	BC337	0.08	BD438	0.44	BF393	0.90	BSTC0343	0.71	BZV15-C12R	0.72
2N3773	1.65	2SC2570	1.80	AC188K	0.39	BA401 (IC)	0.58	BC338	0.12	BD441	1.29	BF417	1.20	BSTC0343	0.71	BZV15-C12R	0.72
2N3819	0.28	2SC2570A	0.95	AC193K	0.59	BA511 (IC)	1.98	BC380	0.30	BD442	0.56	BF418	1.70	BSTC0343	0.71	BZV15-C12R	0.72
2N3823	1.06	2SC2644A	4.38	AC194K	0.59	BA521 (IC)	1.81	BC388	0.23	BD447	0.54	BF422	0.26	BSTC0343	0.71	BZV15-C12R	0.72
2N3904	0.56	2SC2671	1.99	AD140	0.96	BA532 (IC)	1.88	BC440	0.99	BD508	0.54	BF423	0.26	BSTC0343	0.71	BZV15-C12R	0.72
2N3908	0.56	2SC2728	0.95	AD142	0.96	BA536 (IC)	2.72	BC441	0.41	BD510	1.29	BF435	0.49	BSTC0343	0.71	BZV15-C12R	0.72
2N4101	1.10	2SC372	1.27	AD143	0.96	BA6304A (IC)	2.65	BC454	0.32	BD510	0.45	BF450	0.30	BSTC0343	0.71	BZV15-C12R	0.72
2N4240	3.00	2SC373	1.05	AD145	1.45	BA843 (IC)	3.80	BC455	0.32	BD518	1.36	BF451	0.26	BSTC0343	0.71	BZV15-C12R	0.72
2N4443	1.35	2SC383	1.20	AD149	0.81	BAV10	0.10	BC460	0.38	BD519	1.36	BF457	0.37	BSTC0343	0.71	BZV15-C12R	0.72
2N4444	1.12	2SC388	0.45	AD161	0.30	BAV18	0.10	BC461	0.42	BD529	0.38	BF458	0.35	BSTC0343	0.71	BZV15-C12R	0.72
2N4914	0.85	2SC41	1.99	AD162	0.30	BAV19	0.10	BC462	0.27	BD530	0.80	BF459	0.35	BSTC0343	0.71	BZV15-C12R	0.72
2N5064	0.84	2SC458	0.55	AD262	0.95	BAV20	0.10	BC463	0.58	BD533	0.80	BF460	0.35	BSTC0343	0.71	BZV15-C12R	0.72
2N5253	0.45	2SC495	0.83	AF114	2.24	BAV21	0.17	BC464	0.58	BD534	0.36	BF469	0.27	BSTC0343	0.71	BZV15-C12R	0.72
2N5294	0.45	2SC508	3.36</														

ECONOMIC DEVICES, REGISTERED OFFICE: 14, BEE LANE, FORD HOUSE, WOLVERHAMPTON WV10 6LF.

ESM532C	4.18	LM1303P/N	1.50	MPSU05	0.78	SAAS010	4.90	SN74190	1.81	TB029V	4.41	TBA395	1.35	TDA1230	2.93	TDA9503	2.80
ESM632C	4.18	LM1310P/N	1.25	MPSU10	0.78	SAAS012	6.50	SN7420N	0.20	TB032V	0.89	TBA3950	1.80	TDA1235	3.52	TDA9513	2.40
ESM732C	4.18	LM3085N	0.77	MPSU55	0.90	SAAS020	5.25	SN7430	0.38	TB033V	0.73	TBA396	1.80	TDA1270	2.84	TES27	1.25
ETT8016	2.85	LM317CKC	1.30	MPSU56	0.30	SAAS030	7.50	SN7440N	0.24	TB035V	0.86	TBA400	2.17	TDA1327A	1.85	TES38	0.36
ETTR0616	2.16	LM339N	0.88	MPSU80	1.20	SAAS040A	14.75	SN7473	0.56	TB036	0.44	TBA440P	1.55	TDA1327B	1.65	TE626	1.35
FDN500	5.25	LM3407	1.29	MR510	0.30	SAAS050	8.50	SN7474N	0.72	TB037	1.91	TBA480	1.42	TDA1330	1.60	TEA1002	3.15
FT3055	1.05	LM3407S	0.75	MR812	0.80	SAAS061B	1.80	SN7490AN	0.93	TB041V	0.86	TBA4800	1.67	TDA1365	6.35	TEA1009	0.96
GF758	0.82	LM3407T12	0.75	MR914	0.46	SAA700	3.00	SN75110N	0.75	TB044V	0.86	TBA500P0	4.95	TDA1412	1.95	TEA1020SP	5.34
GF759	1.02	LM3407S	0.75	MSSD7002	0.85	SAB1009B	4.53	SN78001ANQ	2.25	TB045	1.09	TBA510	1.56	TDA1420	0.48	TEA1078	0.46
GF761	0.78	LM342N	0.56	MVS420	0.62	SAB1046P	3.66	SN78003N	2.81	TB049	1.10	TBA510S	6.39	TDA1470	2.63	TIC106C	0.55
GH3F	1.05	LM384AN01	1.34	MVS480	0.20	SAB3011	7.34	SN78013N	3.63	TB052V	0.76	TBA520	1.67	TDA1512	2.20	TIC106M	0.55
HA11211	2.30	LM567CN	1.30	MVS480-02	0.55	SAB3012	5.34	SN78013ND	2.25	TB058	0.46	TBA5200	1.35	TDA1670	3.65	TIC1160	0.80
HA11215	4.00	LM748	1.65	ME545B	2.95	SAB3013	3.28	SN78013NDG	0.87	TB059	1.05	TBA530	0.86	TDA1770	5.56	TIC44	0.85
HA11225	3.90	LM8360	2.78	ME545B	3.80	SAB3021	12.34	SN78023N	2.35	TB069	1.09	TBA5300	0.98	TDA1908	1.25	TIC45	0.70
HA11226	7.56	LM8361	1.48	ME5534N	1.48	SAB3022B	11.18	SN78023ND	1.04	TB070V	0.86	TBA540	0.86	TDA1908	2.95	TIC47	0.70
HA11229	2.51	M1024	2.55	ME555	0.34	SAB3023B	12.34	SN78033N	2.33	TB071V	2.16	TBA5400	1.15	TDA1910	2.38	TIP120	0.96
HA11236	3.80	M1025	4.70	ME556	0.75	SAB3024	4.77	SN78033ND	2.36	TB072V	0.87	TBA550	1.95	TDA1910	2.54	TIP110	0.96
HA11244	4.70	M1124	2.54	ME560N	3.16	SAB3029	4.75	SN78110N	1.13	TB073V	1.27	TBA550Q	2.25	TDA1950	2.54	TIP112	0.80
HA11244	4.32	M1130	4.06	ME565N	1.20	SAB3210	2.93	SN78115AN	1.46	TB073V	5.81	TBA560C	0.86	TDA2002	1.20	TIP117	0.86
HA1125	3.90	M191	5.74	ME845BN	3.80	SAB4209	12.75	SN78131A	1.74	TB074V	1.52	TBA560CQ	1.15	TDA2003	1.05	TIP120	0.73
HA11251	3.38	M193	18.55	ME846N	3.80	SAF1031	2.90	SN78228D	1.20	TB076	0.98	TBA570A	1.55	TDA2006	1.25	TIP126	0.96
HA1137W	2.57	M51102L	4.02	ME850N	3.94	SAF1032	5.30	SN78228ND	2.97	TB078V	1.29	TBA570Q	1.35	TDA2010	2.79	TIP27	1.30
HA1138	3.56	M5115P	4.34	ME845BN	3.80	SAF1039	11.86	SN78227N	0.68	TB079V	1.26	TBA625A	1.97	TDA2020	2.75	TIP295	0.78
HA1144	2.50	M51231P	2.79	MP1106	4.90	SAF1104	7.02	SN78228N	2.97	TB080V	6.15	TBA625B	1.97	TDA2030	1.65	TIP29A	0.41
HA1144	6.38	M5124P	4.38	OA200	0.10	SA5500	1.88	SN78231	2.31	TB081V	1.26	TBA625C	1.97	TDA2140	1.44	TIP29B	0.47
HA1156	1.23	M5134-3341	3.75	OA202	0.10	SA5505	2.97	SN78242	4.75	TB082V	2.51	TBA641A12	3.75	TDA2150	5.63	TIP29C	0.50
HA11580	7.00	M51394P	6.25	OA47	0.10	SA5507	2.85	SN78243	4.75	TB083V	1.97	TBA641B1	2.87	TDA2151	1.75	TIP305	0.85
HA1160	3.45	M5142P	4.38	OA90	0.07	SA5570	1.61	SN78322	2.50	TB084V	2.80	TBA651	2.00	TDA2160	3.64	TIP30A	0.41
HA1166	3.08	M5143P	6.06	OA91	0.08	SA5570S	0.90	SN78390	2.63	TB085V	2.94	TBA673	2.35	TDA2161	1.88	TIP30B	0.63
HA1167	5.13	M5144P	3.42	OA95	0.08	SA5570T	2.50	SN78396	2.63	TB086V	1.35	TBA700Q	2.19	TDA2190	3.11	TIP31B	0.35
HA11711	16.13	M51513L	2.06	OC28	0.96	SA5580	4.90	SN78510N	0.95	TB087V	4.36	TBA720	2.85	TDA2510	1.82	TIP31C	0.63
HA11713	6.70	M51515BL	3.10	OC29	1.35	SA55800	2.62	SN78530P	1.90	TB088V	4.26	TBA720T	1.75	TDA2520	2.15	TIP32B	0.35
HA11714	7.05	M51516L	3.40	OC35	0.96	SA5590	4.55	SN78532N	1.90	TB089V	1.58	TBA750Q	1.46	TDA2521	2.15	TIP32C	0.86
HA11715	7.05	M51517L	2.90	OC36	1.16	SA55900	2.32	SN78533N	1.56	TB090V	1.58	TBA760	1.58	TDA2522	2.81	TIP33C	1.25
HA11718	6.79	M5152L	1.00	OC44	0.40	SA5680	1.20	SN78540N	1.90	TB091V	1.60	TBA780	3.00	TDA2523	2.75	TIP34	3.07
HA11724	15.60	M51522	4.90	OC45	0.40	SA56800	2.50	SN78544	1.80	TB092V	0.80	TBA780AP	0.70	TDA2524	4.50	TIP41A	1.39
HA11725	16.80	M5191P	4.49	OC75	0.40	SA5680S	1.20	SN78545	4.55	TB093V	2.84	TBA810AS	1.46	TDA2525	2.96	TIP41B	0.28
HA1180	4.00	M5192	2.80	ON 188	1.70	SA56910	1.20	SN78546	3.15	TB094V	1.52	TBA810S	1.46	TDA2530	2.19	TIP41C	0.44
HA1203	1.56	M53273P	0.92	ON 236	2.90	SA5670	2.50	SN78549N	3.15	TB095V	3.35	TBA810T	1.65	TDA2532	2.51	TIP42A	0.39
HA1306	1.74	M53274P	1.20	OT112	0.90	SA56700	1.20	SN78549	2.35	TB096V	1.35	TBA820	0.83	TDA2533	2.09	TIP42B	0.71
HA1322	1.74	MA06	0.97	OT121	0.70	SA5670S	1.20	SN78550	0.30	TB097V	4.05	TBA820M	1.65	TDA2540	1.95	TIP42C	0.44
HA1339	1.76	MA8001	0.74	PD144	2.03	SA56710	1.20	SN78551	1.35	TB098V	1.95	TBA890	1.95	TDA2541	1.95	TIP47	0.85
HA1342	1.90	MB3705	1.62	PT1017	2.43	SA56800	2.30	SN78552	2.80	TB099V	4.95	TBA900	2.25	TDA2545Q	3.16	TIP48	0.83
HA1350	2.87	MB3712	2.65	PT2014	2.76	SA56810	1.30	SN78553N	1.10	TB100V	1.41	TBA920	1.50	TDA2560	1.97	TIP49	3.28
HA1385	3.65	MB3713	1.30	PT6042	1.82	SBA550B	1.95	SN78611	2.35	TB101V	1.36	TBA920Q	2.10	TDA2571A	2.81	TIS43	1.21
HA1386WR	1.62	MB3730	2.94	R1038	1.99	SBA750	1.46	SN78622	2.35	TB102V	3.85	TBA940	1.70	TDA2571B	2.95	TIS49	0.22
HA1387	3.20	MC13002	4.66	R1039	1.99	SC9488P	1.90	SN78623	1.50	TB103V	1.64	TBA950	2.55	TDA2576A	2.58	TIS91	0.26
HA1388	1.69	MC1303P	1.96	R2008B	1.20	SC9503	1.90	SN78623	0.82	TB104V	5.34	TBA970	1.80	TDA2577	5.34	TLO71CP	2.02
HA1388R	1.66	MC1307P	1.90	R2009	1.46	SC9504P	1.46	SN78630	2.31	TB105V	1.40	TBA970Q	2.85	TDA2581	1.95	TMS1000NL	10.78
HA1370	2.97	MC1310P	1.25	R2001B	1.20	SC9511P	1.90	SN78640	3.85	TB106V	3.37	TBA990	1.98	TDA2582	1.98	TMS3748NS	11.86
HA1377	2.80	MC1327P	1.20	R2029	1.20	SC9575	1.20	SN78650N	1.24	TB107V	0.58	TBA990Q	2.80	TDA2590	2.80	TMS5116	1.87
HA1389	1.62	MC1330P	1.23	R2030	1.20	SG264A	4.38	SN78651	1.35	TB108V	0.54	TBA990T	1.93	TDA2591	2.80	TV106	1.20
HA1389R	1.74	MC1349P	1.20	R2257	2.16	SG613	7.88	SN78680N	2.25	TB109V	1.20	TBA990T	1.93	TDA2592Q	2.80	TV106B	1.70
HA1392	2.68	MC1350P	1.10	R2265	1.95	SG629	6.28	SN78685N	1.35	TB110V	1.15	TCA001	3.29	TDA2593Q	2.24	U05G	2.03
HA1397	2.97	MC1351P	0.75	R2305	1.07	SG633	9.37	SN78686N	0.98	TB111V	1.15	TCA150	1.62	TDA2594	2.80	U143M	2.80
HA1398	2.88	MC1352P	1.01	R2306	1.23	SI-1020N	4.76	SN78705	3.98	TB112V	0.85	TCA160B	1.62	TDA2595	5.00	U3700	0.55
HA1406	1.40	MC1357P	1.95	R2322	1.26	SI-1125HD	10.70	SN78705N	3.99	TB113V	3.51	TCA270Q	1.95	TDA2610	2.50	U3700C	0.44
HA17723	5.40	MC1358P	1.95	R2323	1.23	SI-1130N	6.30	SN78707N	3.99	TB114V	8.04	TCA270S	1.55	TDA2611A	1.25	UA723CA	5.02
HF6403DAF	2.25	MC14001	7.15	R2348	1.82	SKB2/08	0.76	SN78709	4.65	TB115V	4.85	TCA270S	1.65	TDA2611AQ	2.05	UA783PC	3.06
HD4480	15.80	MC14011	0.23	R2354A	1.82	SKE2F 1/04	1.20	SN78730	4.95	TB116V	2.10	TCA290A	2.85	TDA2612Q	4.25	UA783PC	1.07
HD44801A05	15.90	MC14013	0.37	R2354B	1.82	SKE2G 2/04	0.95	SN78730	4.23	TB117V	4.53	TCA420A	1.90	TDA2620	1.96	UAA170	2.14
HM6231	8.50	MC14016CP	0.37	R2441	1.23	SKE2G 3/04	0.95	SN78810N	6.82	TB118V	5.66	TCA440	1.85	TDA2630	2.34	UAA180	2.14
HM6232	2.71	MC14025	0.54	R2443	0.80	SKE4F 1/02	1.26	SN78920N	2.65	TB119V	4.25	TCA4500A	1.90	TDA2631	2.48	ULN2165	1.35
HM9102	7.92	MC14049UBC	0.52	R2461	2.10	SKE4F 1/06	0.66	SN94041	3.43	TB120V	4.80	TCA530	1.85	TDA2640	2.25	ULN2216F	7.00
HM9104	2.94	MC1438R	0.95	R2477	0.92	SKE4F 2/06	0.60	SN94042	3.95	TB121V	2.53	TCA640	2.83	TDA2643	6.93	ULN2216F	1.95
HT4207	15.80	MC14493P	2.56	R2501	1.16	SKE4F 2/08	2.10	SP686	1.50	TB122V/P	1.28	TCA650	1.65	TDA2651	2.95	UPC1001H	2.50
IS689	1.87	MC14510BAL	3.15	R2540	1.00	SKE4G 2/10	0.87	ST4441C	2.27	TB123V	2.25	TCA680B	2.84	TDA2652	7.05	UPC1002H	5.74
IS751	1.87	MC14556B	3.15	R2540X	3.00	SKE5F 3/02	1.05	STK0029	3.42	TB124V	4.44	TCA730	3.63	TDA2653	2.83</		

Long-distance Television

Roger Bunney

July was quiet to start with but sporadic E activity increased towards the end and continued into early August. Unfortunately the period produced little by way of exotic reception and tropospheric propagation did little to excite or inspire. The SpE log of identified reception is as follows:

- 8/7/84 RAI (Italy) chs. IA, B; JRT (Yugoslavia) E3; TVE (Spain) E2.
- 9/7/84 RAI IA.
- 10/7/84 RAI IA, B.
- 11/7/84 RAI IA; TVE E3.
- 13/7/84 TVE-2 E2; RAI IA.
- 14/7/84 TSS (USSR) R1, 2; SR (Sweden) E2; TVE E2, TVE-2 E2.
- 15/7/84 TVE E2, 3, 4; TSS R1, 2.
- 16/7/84 CST (Czechoslovakia) R1, 2; TVP (Poland) R1; TSS R1.
- 17/7/84 TVE E2; SR E2.
- 18/7/84 RAI IA.
- 19/7/84 RAI IA, B; TVE E4; JRT E4; MTV (Hungary) R1; CST R1.
- 20/7/84 +PTT (Switzerland) E2; RAI IA, B; TVE E2, 3, 4; TSS R1, 2; NRK (Norway) E2, 3, 4; SR E2, 3, 4; TVP R1.
- 21/7/84 DR (Denmark) E3, 4; ARD (West Germany) E2; ORF (Austria) E2a; RAI IA, B; TVE E2, 3, TVE-2 E2; MTV R1; CST R1, 2; TSS R1, 2; TVP R1, 2; NRK E2, 3; SR E2, 3, 4.
- 22/7/84 RAI IA, B; TVE E2, 3, 4; CST R1; ORF E2a; ARD E2; MTV R1.
- 23/7/84 RAI IA; TVR (Rumania) R2; JRT E3, 4; ORF E2a; TSS R1, 2.
- 24/7/84 TSS R1, 2; CST R1, 2; TVP R1, 2; SR E2, 3; NRK E2, 3; YLE (Finland) E2; DR E3, 4; ORF E2a; RAI IA; TVE E2, 3, 4; +PTT E3; ARD E2, 4.
- 25/7/84 RAI IA, B; YLE E2; TSS R1, 2; NRK E2, 3.
- 26/7/84 RAI IA, B; TVE E2; ARD E2; NRK E2, 3; TSS R1; RTM (Morocco) E4; NTV (Nigeria) E3.
- 27/7/84 TSS R1, 2; TVE E2, 3, 4; RTP (Portugal) E3.
- 29/7/84 TVE E3, TSS R1, 2; ORF E2a; MTV R1.
- 30/7/84 CST R1; TVE E2, 3, 4.
- 31/7/84 RAI IA, B; TVE E2, 3, 4; JRT E3, 4; TSS R1, 2; TVP R1, 2, 3; CST R1, 2; ARD E2; DFF (East Germany) E4; JTV (Jordan) E3. Signals noted up to ch. R4.
- 1/8/84 TVE E2, 3, 4; RAI IA; TVR R2; ARD E2; EPT (Greece) E3.
- 2/8/84 RAI IA; TVE E2, 3, 4.
- 4/8/84 CST R1, 2; ARD E2; NRK E2; RAI IA; TVE E4.
- 5/8/84 +PTT E2, 3; RAI IA, B; MTV R1; TVE E3; DFF E4; SR E2; RUV (Iceland) E4; EPT E3.
- 6/8/84 RAI IA, B; TVP R1, 2, 3; TSS R1, 2, 3; MTV R1; CST R1, 2; ORF E2a; SR E2; NRK E2.

CST was noted on August 4th with a studio insert identification similar to the RAI corner one, the letters S and P initially then expanding to give the complete name. At 1030 BST on the same day I logged a possible exotic ch. E4 signal from the SE – a slow-fading signal going to a flag and then further programme material. The following day Cyril Willis received Middle Eastern/Indian type

music on ch. E4 at 1400 but there was no accompanying picture.

The most exotic reception occurred on the 26th. Arthur Milliken (Wigan) received Morocco ch. E4 at 1857 BST onwards, the PM5544 test pattern going on to an announcer, the Koran and then cartoons. At 1900 Paul Barton (Harrogate) received dancing Africans in tribal dress on ch. E3; the signal was swamped by TVE at 1903. The African signal is most likely to have come from Sokoto, Nigeria.

There were several tropospheric lifts but few of consequence. Band III signals from Denmark and Norway were received in the eastern UK on the 19th. The 25th was more productive, with DFF ch. E6 and several ARD Band III/u.h.f. stations. High-level French u.h.f. signals were received along the south/east coasts during the weekend of the 28/29th, but the only unusual signal was a 435MHz ATV one – F3LP Le Havre. It's unfortunate that there's so little UK ATV activity during the mornings whenever there's a reasonable lift – many opportunities for DX contact are being lost.

My thanks to the following for sending in reports: Paul Barton (Harrogate), Cyril Willis (Cambridge), Arthur Milliken (Wigan), Iain Menzies (Aberdeen), Dave Shirley (Hastings), Ian Johnson (Bromsgrove), Bill Cotterill (Tipton), Simon Hamer (Powys). Too late for mention in last month's column was Tim Anderson's suspected reception at Bexhill of NTV ch. E3 – at 1851 BST on July 6th, with an African news announcer.

News In Brief

An experimental Chinese satellite is in orbit at 125°E, relaying a single TV and fifteen radio channels. Does anyone know the downlink frequencies being used? . . . Spain is to have a private TV channel by 1985 though the transmitters will be operated by a central organisation . . . ARD/ZDF (WG) are to carry data which will automatically initiate video recording in conjunction with a suitably equipped receiver – the system is to be introduced at the 1985 Berlin Fair . . . Czechoslovakia is considering a DBS service to start later in the decade, with tests planned for 1987 . . . Insat-B is relaying AIR from Delhi at 1800-2300 local time, operating at 2.5GHz . . . The 50.05MHz RSGB beacon GB3NHQ should now be in operation at Potters Bar, Herts.

Interference

The RSGB reports that a new form of fluorescent light is causing interference due to a built-in l.f. oscillator. In some of these lights the oscillator runs all the time whilst in others it's used just at start up. The interference is wideband and can reach 80MHz.

The problem of interference generated by home computers has been mentioned in previous columns. The Department of Trade and Industry comment that they recognise the need to limit spurious signals generated by data processing equipment but an international standard will not be available for some years. Meanwhile work on a UK standard has gone ahead due to the increasing use of data equipment in offices and industry, and a draft document has been circulated – an extended British Standard (BS6527) is due shortly. The DTI doesn't say whether this will cover domestic data processing equipment and add that BS specifications are not legally binding unless referred to in statutory regulations. There's thus no recourse at present against users/manufacturers of home computers that cause interference. I nevertheless feel that

if interference occurs in recognised bands action should be possible. As soon as I receive a copy of BS6527 I'll pass on any relevant information. Thanks to the DTI for their cooperation.

Quite by coincidence we received a press release the other day on a new product designed to combat interference radiated by plastic encased electronics. Decospray of Charlton, London SE7 have formulated a spray-on pure zinc metal coating for plastic surfaces to prevent radiation. Interesting to note that the product has been used on radio/radar dish reflectors. I'm awaiting further information - whether the price is such that enthusiasts will be able to afford it remains to be seen.

New Networks

France: Provisional plans for the Canal Plus service are as follows:

Channel	Vision carrier	Sound carrier	Channel	Vision carrier	Sound carrier
5	176MHz	182.5MHz	8	200MHz	206.5MHz
6	184MHz	190.5MHz	9	208MHz	214.5MHz
7	192MHz	198.5MHz	10	216MHz	222.5MHz

Main station channel allocations are as follows:

- Ch. 5: Gex, Le Havre, Toulouse Pic du Midi.
- Ch. 6: Chamrousse, Hyeres, Niort, Paris Eiffel Tower.
- Ch. 7: Bayonne, Rennes.
- Ch. 8: Bourges.
- Ch. 9: Caen, Gap, Nancy.
- Ch. 10: Limoges.

Further main stations will have frequency offsets.

At present, films are being transmitted as test material. The only Band I outlets will be in Corsica - Bastia ch. 2 and Ajaccio ch. 4.

Denmark: Gosta van der Linden provides the following provisional channel assignments for the Danish u.h.f. network.


Station	Channels	E.R.P.
Aarhus	23, 26, 54	800kW
Bornholm	56, 59	800kW
Bramminge	50, 58, 68	200kW
Fyn	22, 25, 58	800kW
Hillerod	53, 56, 67	100kW
Jyderup	48, 51, 65	800kW
Kibeek	43, 46, 66	800kW
Kobenhavn	31, 34, 60	800kW
Logumkloster	29, 32, 67	100kW
Nakskov	49, 52, 63	100kW
Salling	28, 59, 62	800kW
Sundeved	24, 27, 60	800kW
Tinghoj	29, 44, 47	500kW
Vejle	30, 33, 64	500kW
Vendsyssel	32, 35, 63	800kW
Vordingborg	39, 42, 66	800kW

The higher channels will be used initially.

From our Correspondents . . .

Tim Anderson recently moved from Stroud to Bexhill. Obviously his French TV reception increased dramatically despite using fixed aerials at the time of writing. He's bought an SX200n scanner, having also considered an AR2001. Though the AR2001 seems to be ideal for DXing, with its wide/narrow bandwidth at a.m./f.m., we've received conflicting reports on it. Comments from users would be welcome.

SOUTH WEST AERIALS

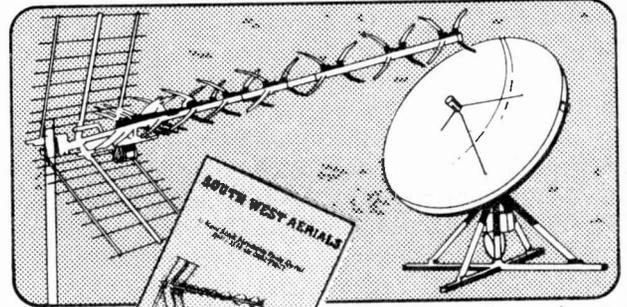

This catalogue is your key to solving a host of television and radio reception problems. We shall be delighted to forward your copy on receipt of 54p.

EQUIPMENT & PROFESSIONAL ADVICE

South West Aerials offer a unique blend of the best equipment and impartial professional advice.

Examples from our range:

TRIAx BB Grid waveband 4 bay stacked bowtie UHF Aerial (works well down to 435MHz for ATV) £22.80
 TRIAX 721/UHF stripline stacking Filter, for stacking 2 x BB Grid Aerials only 0.2dB through loss £11.95

(Wide range of specialist filters and combiners available)

LABGEAR CM7060 Ultra Low Noise 1.8dB W/B UHF Masthead Amplifier with 10dB gain...£11.50
 POLYTRON 'in line' Double Notch Filters for Bands 1, 2, 3, 4 and 5 (28-42dB attenuation) state type required...£14.75
 NEW 'COLOROTOR' Offset Aerial Rotator complete with Control Console, uses 3-core cable...£39.95
 SB100 Alignment/Support Bearing for above Rotator to increase head load...£13.95
 Also available Black & White and Colour Multi-Standard VHF/UHF Televisions and Video Recorders (SAE or ring stating requirement)

We are THE DXing Specialists, advice given on ALL reception problems (SAE please)

All prices inclusive of VAT and Carriage. Delivery 7-10 days Access & Visa welcome



SOUTH WEST AERIALS (T)

11, Kent Road, Parkstone,

Poole, Dorset, BH12 2EH. Tel: 0202 738232.



TV LINE OUTPUT TRANSFORMERS

PRICES INCLUDE VAT & CARRIAGE

Delivery by return of post.

RANK BUSH MURPHY A774 with stick rectifier 9.78 A816, T16, T18, Z712, Z715 10.35 T20, T22, T26, Z179, A823 11.50 Z718 Basic unit 13.50 T24e, T24h split diode P.O.A.	ITT: VC200, VC205, VC207 9.20 VC300, 301, 302, 400, 401, 402 9.20 CVC1, CVC2 (FORGESTONE) 11.50 CVC5, CVC7, CVC8, CVC9 series 9.20 CVC20, CVC30, CVC32, CVC45 9.20 CVC40 split diode 16.74 FT110, FT111. P/no AT2063/02 11.50
DECCA: 1210, 1211, 1511 11.50 1700, 2001, 2020, 2401, 2404 9.20 CS1730, 1733, 1830, 1835 9.20 30, 70, 80, 90, 100, 110, 130 Series 9.20	PYE: 169, 173, 569, 368 series 9.20 CT200, CT200/1, CT213 series 10.35 725-731, 735, 737, 741 Series 9.78
FERGUSON, THORN: 1590, 1591 9.20 1690, 1691. built in rect. 9.78 1600, 1615, 1700 series 11.78 1790 mono portable 9.20 3000, 3500, 8000, 8500, 8800 P.O.A. 9000, 9200, 9300 series 12.00 9500, 9600, 9650 series 10.99 9800, TX9, TX10 series P.O.A. MOVIESTAR 3781, 3787 12.00	PHILIPS: 170, 210, 300 series 9.20 320 series 9.78 TX, T8 mono series P.O.A. KT2, KT3 series colour 9.20 G11 series split diode P.O.A. G8 and G9 Series £9.20
FIDELITY: FTU12 mono 10.35 CTV14R, CTV14S colour 15.83	BINATONE: 9909 mono 13.04 GRUNDIG: most models in stock NORDMENDE: FC125, Z206, Z306 11.50 SANYO: CTP5101, TJ series 11.50 SHARP: C1851H, C2051H 12.32 TELETON: TH14 mono 13.68 TOSHIBA: C800, C800B 19.45 TANDBURG: 190, CTV2-2, CTV3-3 P.O.A. TELEFUNKEN: most models in stock LINE OUTPUT TESTER 16.79
G.E.C. 2047 to 3135 mono 7.50 1201H, 1501H, 2114, 3133, 3135 9.20 DUAL & SINGLE hybrid col. 10.00 SINGLE STO solid state 12.00 SINGLE STO split diode P.O.A.	Tidman Mail Order Ltd., 236 Sandycroft Road, Richmond, Surrey. Approx. 1 mile from Kew Bridge. Phone: 01-948 3702 Mon-Fri 9 am to 12.30 pm & 1.30-4.30 pm Sat 10 am to 12 noon.
INDESIT: 24EGB hybrid 9.50 12LGB, 12SGB mono portables 10.35	
WINDINGS TYNE: main winding 6.80 RBM: T20, T22, T26, Z179 6.33 WALTHAM: W125 eht winding 2.37 KORTING: hybrid winding 6.90	

A "down under" DX-TV group is planned by James Cotterill of 15/246 Buffalo Road, Ryde, NSW, Australia 2112. He hopes that anyone in Australia and the Far East interested in this will get in touch with him. A monthly newsletter with reception and news information is promised. Include return postage if you write! Alan Duchatel plans to start a new French DX magazine, covering both f.m. radio and TV. Further information will be passed on when received. Incidentally Alan received two Canadian ch. A2 transmissions at his home near Bourdeaux between 2300-0130 French Summer Time (BST plus one hour) on June 30th, via multiple-hop SpE. One programme was in English with CBC captions, the other in French about fishing in the Japanese Sea. He used an AR2001 for the sound.

Imported TV Receivers

Many DX-TV enthusiasts use small-screen monochrome, v.h.f./u.h.f., dual-standard sound receivers such as those from Plustron, Vega, Hitachi and Panasonic. They incorporate most of what's required for simple DX reception and are inexpensive. At the other end of the scale a number of enthusiasts are using Scandinavian v.h.f./u.h.f. colour sets of Salora or Luxor manufacture. The current Salora chassis provides a wide range of options – system L SECAM, NTSC at 3.58 or 4.43MHz, 5.5/6/6.5MHz f.m. and 6.5MHz a.m. sound and all forms of teletext can be included via appropriate boards. Most models are fitted with multiband tuners and the on-board microcomputer tuning system provides for a hundred preprogrammed channels. Further details can be obtained from Salora (UK) Ltd., Techno Trading Estate, Swindon, SN2 6EZ. The Luxor SX9 chassis was described in the January 1984 issue of this magazine and offers similar facilities to the Salora range. Luxor (UK) Ltd. can be contacted at 87/9 Farnham Road, Slough, Berks SL1 4UL – their receivers have an established following in UK DX-TV circles at present.

In view of the facilities that these sets offer a price of £600 or so seems reasonable, especially with arm-chair remote control! My thanks to the two companies for sending much valuable and interesting information on their current ranges. I'd be interested to hear from enthusiasts who use these multi-standard "domestic" sets.

ATV at 24cms

As previously mentioned I've succeeded with reception of f.m. video in the 1.3GHz ATV band. The results at this low microwave frequency have been less than startling to date, the farthest signal received having come from some 12 miles away, albeit with just a few watts at the transmitter end and using the normal u.h.f. aerials and head amplifiers for reception – hardly the ideal arrangement! The BATC advocate the use of f.m. in this band, though some of the repeaters use a.m. The 23/24cm band covers 1240-1325MHz with a gap at 1260-1270MHz.

Although an f.m. demodulator is best for f.m. video, slope detection with an a.m. demodulator gives pictures that should be good enough to enable sources to be identified. Various aerials are available, such as loop Yagis, though the prices seem high. I'm looking into this and hope to be able to present a simple (and cheap) solution shortly. Down conversion from 1.3GHz is the main problem for the DXer however. I've looked at three currently available solutions.

Fortop have several units available for use in this band. The TVC1300 is a GaAsfet receiver/downconverter tun-

ing across 1240-1325MHz with very low noise and an output at 50MHz (for use with their TVIF50 f.m. video i.f. system). It requires 12V at 250mA, is completely stable and is housed in a diecast box. This provides a very high performance front end for a retail price of £79.95 plus £2.50 post and packing.

The CQ Centre, an amateur radio emporium, has available a ready built 23/24cm converter in a diecast box with BNC aerial input and Belling-Lee output sockets – output is at ch. 36 nominal. You tune the TV receiver, which acts as a tunable i.f. strip, to either side of ch. 36 to cover the band. Examination of the PCB inside shows a single r.f. stage, mixer and oscillator with an on-board voltage stabiliser – the converter accepts 12-24V d.c. and draws 24mA at 12V. This was the first converter I tried and it worked immediately. It appeared to be stable throughout the band and I consider it excellent value. An outboard preamplifier could be added to improve the noise performance. I experienced little by way of breakthrough problems from the local group A channels – the nearest here is ch. 31. Those with a strong local ch. 33 signal might experience breakthrough either via the unit or after it. Input bandpass filtering is incorporated and should attenuate all but the strongest ch. 33 signals. Apart from this minor reservation I feel that the unit can be thoroughly recommended as a starter: the price is £29.95 including postage.

The Solent Scientific 23/24cm converter kit is priced in the same range. I obtained one of these and after construction and alignment found it worked well, giving pictures two grades up on the CQ one. The kit comes with a high-quality PCB and the electronic components required and the recommendation to house it in a diecast box (RS509-939 advised as the board fits it exactly) – this and the other hardware could add £6-7 if bought new from a retailer. The main advantage, apart from the multi-stage r.f. amplifier, is that the output can be adjusted to lie in a locally empty section of the band, thus avoiding breakthrough etc. The alignment instructions are clear and easy to follow. There are three r.f. amplifier stages (2SC3358, NE21936, BFR91) so there's plenty of gain and a good low-noise performance. This lot is followed by a diode mixer, BFR96 oscillator and BFR91 u.h.f. amplifier. The unit takes 120mA at 12V which is supplied by a two-transistor voltage stabiliser. It's an upmarket design and certainly gives upmarket performance. Construction should take two-three hours, casing another hour and alignment perhaps half an hour. Clear instructions and a phone number for queries should ensure satisfactory results. The kit costs £34.95 plus £1 pp. It's also available assembled and aligned at £48.95 uncased or £62.95 cased and fitted with BNC sockets. A 24cm transmitter is available for alignment use.

I've tried the CQ and Solent converters on signals and they work well. I've not tried the Fortop converter but I do use their 435MHz products whose quality is first class. Addresses: Fortop Ltd., 9 Ryebrook Grove, Chell, Stoke-on-Trent, Staffs; CQ Centre, 10 Merston Park Parade, Kingston Road, London SW19; Solent Scientific, 75 Chalk Hill, West End, Southampton SO3 3BY. Include an sae with enquiries.

Solent also have available a u.h.f. video/tunable audio f.m. receiver suitable for 23/24cm and satellite reception. I hope to report on this later in the year.

Information on the BATC (British Amateur Television Club) can be obtained from 13 Church Street, Gainsborough, Lincs.

TV Fault Finding

Mick Dutton, Graham Colebourn, B.Sc.,
Malcolm Burrell, P. J. Bradford,
Nick Lyons, M. S. Barakat, John Coombes,
Robin D. Smith and Philip Blundell, Eng. Tech.

ITT CVC32 Chassis

This set led us a merry dance for several weeks. The symptom was an unstable picture on all channels except BBC-1: the set was extremely sensitive – to the point where a tap on the floor ten feet away would put it right – and as soon as the back was removed the fault had gone. We eventually solved the problem by looking at the board layout. There are link wires between the number one tuning preset and all the others – this link was dry-jointed. The exterior of the joint looked perfect, but a touch of solder provided a permanent cure.

The set came back a while later with a different fault – intermittent no results. This turned out to be due to a dead spot on the line hold control, as a result of which the line oscillator would occasionally fail to start. **M.D.**

Kingsonic R96 Monochrome Portable

The problem was intermittent field collapse. When the set was switched on it would produce a picture that was excessively high and rolling, but after a few seconds the raster would collapse to two inches in the lower half of the screen with a bright line across the centre. The field timebase voltages were correct up to the driver transistor, but in the output stage they were wavering erratically. We traced the problem to a low-gain output transistor (Q503). Replacing this provided a cure, but the customer had left the set running in the fault condition with the result that there was a burn mark on the tube. **M.D.**

Grundig CUC120 Chassis

The set would lose line sync when warm. We solved this one with the aid of a hairdryer and a can of freezer: C2711 (0.022 μ F) was leaky when warm. **M.D.**

Decca 130 Chassis

The customer's complaint was "lines on the picture". When we arrived at the house we took one look and loaded the set in the back of the car. The problem was excessive field scan with black lines across the centre of the screen. Diagnosis was made difficult because the raster kept blanking out due to the operation of the protection circuit in the TDA1670 field timebase i.c. We removed D301 to stop the blanking action and looked more closely at the fault. The voltages in the field timebase were about right while the height and linearity controls seemed to have some effect. Replacing the i.c. and the flyback diode D302 made no difference and we spent a long time checking this, that and the other. In the end we decided that the fault must be in the output side of the circuit. We started bridging components one by one and when C303

(0.22 μ F) was bridged we were rewarded with a normal picture. This capacitor is part of the scan impedance matching network. A few days later we had to replace a faulty field timebase chip in a Ferguson TX9 and noticed that the circuit is similar – this stirred a recollection that we'd reported on the same basic fault once before in the magazine. **M.D.**

Grundig 7200GB

Three of these sets have been our way recently. The first came in with a very distorted keystone raster and misconvergence: the picture was narrower at the top than at the bottom. The fault was on the convergence board where the print from pin K5 to the red/blue tilt control was open-circuit.

There was no EW correction on the second set. This was traced to Tr498 (BC237), Di498 (39V zener diode) and R493 (8.2k Ω) which was burnt.

The complaint with the third set was field cramping. It also had an EW fault. The connection between the two is that both circuits are powered from the 36V line. Clearing the EW fault cured the field trouble as well. **M.B.**

Philips 20C934 (KT3 Chassis)

We had to repair one of these sets (KT3 chassis with remote control, Model 20C934) because arcing at the mains switch had killed the CMOS clock oscillator chip (IC806) on the Telco remote control decoder panel. The customer subsequently complained about unreliable operation. The set would often come on with either no colour and no sound or gaudy colour and deafening sound, normal control being restored after a minute or two. The new CD4001 oscillator was refusing to start promptly and we found that the circuit used – Fig. 1(a) – is called "less than perfect" in the National CMOS guide because it doesn't always start up properly when low-value capacitors are employed. It can easily be converted to the "sure-fire" design by lifting the end of the 16k Ω resistor (R804) nearest IC806 and wiring it to the unused pin 11 as shown in Fig. 1(b). This three-gate oscillator arrangement always starts – unless you fail to observe CMOS handling precautions when carrying out the modification! **G.C.**

ITT CVC1200 Chassis

The picture on this set was negative: the sound was normal, and both the brightness and contrast controls had some effect. We suspected a fault in the vision demodulator area within the r.f./i.f. module but replacing this made no difference. A new decoder panel cleared the fault so we refitted the original one and checked around the TDA3561 i.c. A large line pulse was found to be present, superimposed on the normal signal, at the luminance input pin 10. This caused some confusion since the pulse was not present at the emitter of the luminance delay line driver transistor T860. Changing the i.c. made no difference and the pulse was still present when the delay line was disconnected. It turned out that the luminance coupling capacitor C865 (0.047 μ F) had a heavy

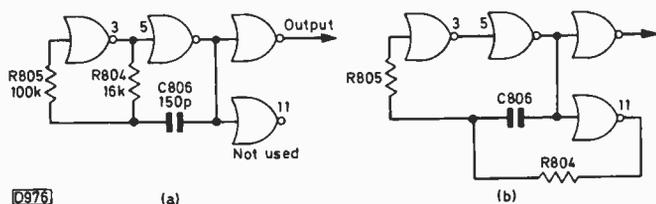


Fig. 1: CMOS gate oscillator circuits.

leak, as a result of which pin 10 of the i.c. was being loaded down through R865 (1.5k Ω). M.D.

Fidelity CTV14R

Intermittent tuning drift was the problem with this set. After a couple of hours spent taking voltages, prodding around and replacing various items we decided to consult Fidelity's Technical Department. It was suggested that we remove the control board and go over the print side with methylated spirit and a toothbrush. This worked – it appears that the problem is to do with flux on the soldered connections. P.J.B.

Pye 731 Chassis

A Pye set fitted with the 731 chassis wouldn't start – because it had incinerated the power supply panel output socket 876. The solution to this was simple enough, to cut away the burnt areas and hard wire in connections. With this done the set started but produced no picture, in fact no e.h.t. The h.t. fuse F971 in series with the line output stage hadn't blown but was found to be 1.25A instead of the 800mA it should have been. The AVO showed that just over 1A was flowing, a clear indication in this chassis that something is amiss, 600mA being the norm here. Disconnecting the tripler solved the problem and highlights the consequences of careless servicing. With the 1.25A fuse fitted the set would have kept running with the faulty tripler until sufficient additional damage had been done to the line output stage for even this value fuse to blow. In this chassis there's a factor of only two in the current drawn by the line output stage driving a faulty as opposed to a good tripler, so correct fuse rating is vital. In most chassis the difference is greater than this, but that shouldn't be taken as a licence to fit higher values unless recommended by the manufacturers.

A couple of days later the set was back as only the picture highlights were displayed – smeary and mainly purple. The first anode voltages had disappeared. In later versions of the chassis the first anode presets are 470k Ω instead of the 1M Ω used in earlier versions. A series resistance is included in these sets in the supply to the presets. It consists of two resistors, 390k Ω and 270k Ω , of which only the 390k Ω resistor is normally in circuit. By means of a wire link the 270k Ω resistor can be added in parallel with the 390k Ω resistor to give additional range of control. If the 390k Ω resistor has gone open-circuit, as this one had, don't expect the 270k Ω resistor (if it's in circuit) to last long – being rated at only $\frac{1}{2}$ W, it can't stand the load on its own. In this case I replaced both with a single 330k Ω 1W resistor. This usually gives adequate range. These are safety components, so don't stray too far from the original specification, i.e. don't use resistors rated at more than 1W or a single resistor of less than 180k Ω . N.L.

Philips 320 Chassis

It's unusual but you do get sets that run with faults in the line output stage. Here's a case of the dreaded Philips 320 monochrome chassis. When the set arrived it was dead from the power supply onwards. It's not often that a 320 comes in with a working power supply, but I suppose there's a first time for everything. A hole was seen in the resistor that feeds the line output stage – the cement job with the "safety pin" on it – and, surprise, surprise, it was open-circuit. The replacement got steaming hot when the

set was switched on, and the line output department made a lot of noise. Despite this the set would tune, provide sound, and though there was no picture the tube's heater was brightly lit. With a set in this condition, i.e. the line output stage operating after a fashion but no picture, I always turn the brightness to minimum, wait for about ten seconds, then slowly advance the control while carefully watching for any trace of a picture.

Most sets give conclusive results with this test, enabling you to condemn the line output transformer without further ado. This one didn't! A very large, very dim picture could just be discerned. Well it's obvious I thought, the e.h.t. stick must be faulty. So I changed it and the fault remained. Attention was then turned to the transformer, whose primary winding was red hot. Replacing the transformer restored correct operation. But what of the line output transistor, a delicate violet in these sets? Surely it couldn't have survived feeding a transformer with shorted turns? Well it had, and does to this day! N.L.

Rank T20 Chassis

The cause of the fault on this set was a well known one, but the symptoms that arose whilst tracing it were nevertheless confusing. When switched on the set would degauss, just start to rustle up and that was it. Various checks were made in the line output stage without success, so the business of bridging the start up capacitor 4C19 in the line oscillator circuit was resorted to – use a wirewound resistor of around 6.8k Ω with a rating of say 7W. Scope checks then revealed that the oscillator was working all right but there was no drive at the base of the line driver transistor due to the over-voltage trip working.

The over-voltage subpanel was removed and the set supplied via a variac. We then found that we had almost everything except field scan, a check on the supply to the field output stage revealing that it was high at about 45V instead of 36V. Hence the operation of the trip. The high voltage was due to the light loading as a result of no timebase operation. The fact that we were still operating the line oscillator via the 6.8k Ω resistor from the h.t. rail provided the clue – no 12V supply. 4R16 in the 12V regulator circuit had struck again. N.L.

Some Quickies

GEC PIL/20AX Chassis: It's been said before in these pages but we've also had it from time to time: if you find the chopper transistor short-circuit, check that the driver transistor's base bias resistor R515 (150k Ω) hasn't gone high in value or the new BU126 will short in a matter of seconds.

ITT CVC20 Chassis: No 24V supply was traced to D24 (BYX71-350) in the EW modulator circuit being open-circuit – though it read all right in circuit.

ITT CVC32 Chassis: Intermittent line collapse and intermittent shut-down was traced to a dry-joint on the line driver transformer L10/11. R.D.S.

ITT CVC8 Chassis

An ITT set fitted with the ever poisonous PCL86 audio valve had been giving both myself and the customer the run around for a few weeks. The sound would go off for about an hour once a week, usually during the opposite end of the week to when I was trying to find the cause of the fault. In the end I just changed the valve and this

cured the problem. Why on earth didn't manufacturers stick with the known and very reliable PCL82? It's too late to complain now I suppose - that technology long since sank from setmaking. N.L.

Pye 697 Chassis

There was a raster but no picture on this Pye hybrid colour set. Quietly dabbing about with the scope showed that no vision signal was coming from the i.f. strip, due it turned out to the 33.5MHz trap coil L10 in the detector circuit being dry-jointed. Unbelievable: all those years' service before a joint that was poor even to the eye finally gave up. I'm not grumbling though. It's seldom that I find a dry-joint so quickly. N.L.

Binatone 01/9909

The complaint was that the picture "goes into lines and keeps drifting". Checks and component substitutions in the line sync and oscillator circuits failed to cure the problem and we then noticed that the line output transistor overheated when the timebase was running at the wrong speed. The transistor was o.k. but the efficiency diode D503 (1N4004) was found to have a reverse leakage reading of 8MΩ. Replacing this cured the fault. M.S.B.

Decca DV9357 (131 Chassis)

We've had two common faults on these sets, which use the frequency synthesis tuning system 30. Channel display shows r and will not tune in: transistor QR16 leaky. Will

not remember channel numbers or analogue settings: rectifier diode DE05 short-circuit (removes the -23V supply to the EAROM P.B.

Bush BC6004

In the event of no sound or picture, first check that the mains bridge rectifier D856 is producing 300V across its reservoir capacitor C858. If this is all right fault-finding gets more difficult - this set, which was supplied to Rank by Saba, uses a combined switch-mode power supply/line output stage known as the Wessel circuit. In a recent case we found that the 122V line output stage supply was low and the set tripping. Quite a few components turned out to be faulty. On the sync/control module R967 (680Ω) had burnt up, C967 (1μF) was leaky and D968 (BAX13) short-circuit - these items are connected between the 122V line and chassis. In the line output circuit the isolation diode D687 (SKE4F1/10) and the 122V reservoir capacitor C836 (100μF) were short-circuit. It's also worth checking the sampling resistor R836 (2.7Ω) which can go open-circuit under this sort of fault condition.

In the event of intermittent fuse blowing, check for dry-joints at the line deflection module plug/socket. J.C.

Decca 100 Chassis

In the event of reduced height with slight foldover, check the field output transistors by substitution then check R371 (2.2kΩ) in the second driver transistor's base biasing network - it tends to overheat and go open-circuit. Use a ½W replacement and check D309, D311 and Tr309 which can be damaged in the process. J.C.

CAPACITORS 91 5 x .0047/1500 AB23 Chassis 1.50 92 10 x 220MFD 16V Elect 0.50 93 10 x .047MFD 400V Mult Pol 0.50 94 5 x 4.7/100V C514 T3500 1.25 95 5 x .47/1000 Dublier 3.00 97 10 x 0.1/2000V W/E 2.00 98 5 x 1/250 Supp TTT etc. 1.50 EHT TRAYS 50 ITT CVC 5/9 3.00 51 Decca 1730/1830 5.00 52 Decca 80 Series 4.50 53 GEC 2040 Hybrid 4.50 54 T1500 5 Stick 3.50 55 Thom 9000 7.00 56 Thom 1400 2.00 57 Philips G9 3.50 58 Universal ITT Type 4.50 59 5 x TV11 EHT Rec for PTV's 1.00 60 3 x TV45 EHT Rec Z718 1.00 61 ITT CVC 45 4.00 63 RRI Z179 3.00 64 Pye 691/697 3.50 65 Pye CT200 4 Lead 3.50 66 Pye CT200 5 Lead 4.50 67 Korting 90 DGR Hyb 5.00	68 Grundig 3010/15003.00 69 Thom 3500 7.50 70 Thom 8500 5.40 71 Philips G8 6.30 72 Pye 731 4.50 89 10 x Anti Track EHT Cap 2.00 INTEGRATED CIRCUITS 140 5 x TDA440 3.00 141 5 x TBA120AS 1.80 142 5 x TBA540 4.00 143 5 x TBA540Q 4.00 145 5 x TBA560 3.50 146 5 x TBA810S 3.00 147 5 x TBA920Q 4.50 148 5 x TBA990 3.25 149 5 x TBA520Q 4.00 150 5 x TBA530 4.25 151 5 x TBA950 4.50 154 10 x TCA270SQ 4.00 155 5 x MC1327Q 2.50 160 TDA1170 1.35 161 TDA1190 1.90 162 TDA1006A 1.45 164 TDA1035 1.83 165 TDA1044 2.23 166 TDA1190 1.90 167 TDA1412 0.90 172 TDA2002 1.80 173 TDA2020 2.50 174 TDA2030 2.15 178 TDA2523 2.35	179 TDA2532 2.40 180 TDA2540 1.85 181 TDA2541 2.67 182 TDA2560 3.28 183 TDA2571 2.15 184 TDA2591 0.98 185 TDA2583 2.23 190 TDA2600 4.00 191 TDA2611 1.24 192 TDA2640 2.35 210 ETR6018 2.28 211 ETR6016 2.28 212 BTT6018 2.28 220 SL9018 Int Circuit 5.00 LINE OUTPUT TX 001 Philips G8 7.50 002 Decca 30 Series 7.00 003 Decca 100 Series 6.50 004 ITT CVC 25/30/32 7.00 005 Philips G9 7.50 006 RRI T20 9.92 007 RRI A823 7.00 008 RRI Z718 18" 18.95 009 RRI Z718 20/22/26" 18.95 010 RRI A774 Mono 10.87 011 Thom 1690/91 7.00 012 Thom 1615 6.50 013 ITT CVC 45 6.50 014 Phil TX Chass. 5.00 015 RRI Ranger 1/2 5.00 016 ITT CVC 5/9 8.50 017 Philips E2 Chass. 5.00 018 Thom 9000 12.00 019 Thom 9500/9600 8.50 020 Polish 161 Mono 6.00 021 Thom 3500 Scant 4.50 022 Thom 8500 11.00 023 Thom 1590/91 8.50 024 Thom 1500 15KV 4.00 025 GEC 2040/2100 Hybrid CTV 4.00 026 Bush 161 Mono 5.00 027 GEC Single Std Mono 5.00 028 Pye 691 (wired) 5.00	030 GEC 2100 Hybrid 4.00 032 Thorn T x 9 Chass. 14.50 033 Philips KT3 8.00 034 RRI T24 Chass. 14.00 035 Sanyo CTP5101 9.50 037 Split Diode EHT Lead 1.35 PUSH BUTTON UNITS 110 Pye 713 4 Way 7.87 111 Pye 715 5 Way 11.95 112 Phil G8 Square 12.75 113 Phil G8 Sloping 14.50 114 Thom 9000 2.50 115 Thom 1615 4 Way 7.87 116 Decca 6 Way 6.95 117 Decca 4 Way 6.95 118 GEC 2110 6 Way 7.95 119 GEC 2136/7 Tapered 7.95 120 ITT CVC5 9.25 121 ITT CVC8 11.45 122 ITT 6 Way with V.C.R. 7.95 123 RRI A823 etc. 7.95 124 Hitachi 4 Way 7.95 125 RRI T20 6 Way 8.95	SPECIFIC COMPONENTS 351 Thorn 1591 Speaker 2.00 352 Thorn 1600 Dropper 0.50 353 T x 10 Preset 3.00 354 T x 10 CRT Base Assy 4.00 355 3" Round BR Speaker 1.00 358 5 x Tho/3500 200 Conv. Pot. 1.00 359 5 x Tho/3500 50R Conv. Pot. 1.00 360 5 x TCE3500 A1 Rectifier 0.75 362 T9000 Rem. Receive Assy 5.00 363 T3500 Mains TX 5.00 364 T8500 Mains TX 7.50 365 T8500 (PLastic) Cut Out 1.50 370 Pye 731 Thick Film Resis. 1.50 371 Pye 713/731 Vis. Gain Mod. 6.50 372 Pye 731 3R3 50W Metal cld. 1.29 373 100K x3 Drawer P'set Alt Pye 731 2.00 378 Grundig 5010/6010 Vid Mod. 4.00 384 5 x 10R Phil. G8 Conv. Pot. 2.40 385 5 x 15R Phil. G8 Conv. Pot. 2.40 386 5 x Phil. G8 2k x 2 Lin. Bright. 2.50 387 5 x Phil. G8 10k Log. Colour 2.50 388 5 x Phil. G8 47k Log. Vol. 2.50 389 G8 Plastic Mains Switch 0.75	390 G8 Metal Mains Switch 1.23 391 G8 Line Stor/Eql. Coil 2.25 392 G8 R/G Symetry Coil 3.33 397 20 x 3.15A A/S 20mm Fuse 1.50 398 20 x 800MA A/S 20mm Fuse 1.50 399 20 x 2.5A A/S 20mm Fuse 1.40 400 20 x 2A A/S 20mm Fuse 1.40 401 20 x 1A A/S 20mm Fuse 1.40 402 20 x 1.25A A/S 20mm Fuse 1.40 403 5 x RRI T20 Tube Base 4.35 410 Phil. G11 E/W Load/Coil 1.50 411 Phil. G11 Bridge TX 1.50 412 Philips G11 Type 1.00 413 10 x TDA2600 IC Holder 1.50 415 PAL.KT3 Speaker 1.50 435 10 x Decca 30 10R Fusible 0.50 436 5 x Decca 30 3R9 Modulohm 1.75 437 Decca 30 47k Vol.+Switch 1.25 453 5 x 5R Universal Conv. Pot. 1.00 454 5 x 20R Universal Conv. Pot. 1.00 455 5 x 100R Universal Conv. Pot. 1.00 456 5 x 470R Universal Conv. Pot. 1.00 457 10 x 100k Tun/Pres TCE etc. 3.00 458 10 x 100k Tuner Preset G8 3.00 459 ELC1043/05 Tuner 6.00	460 ELC1043/06 Tuner 6.00 461 U321 New Tuner 7.95 462 U322 New Tuner 7.95 463 98003 Posister 0.99 464 98009 Posister 0.99 465 Mull.DL50 Delay Line 0.95 466 5 x VA1104 2.70 469 Cut Out Metal GEC 2100 1.00 470 5 x GEC2100 3 Lag Thermist. 1.00 479 5 x Gen. Purp. Rotary Switch 3.80 480 5 x Gen. Purp.Push/Switch. 3.75 481 20 x Neons GEC etc. 2.25 482 5 x Univ. Aerial SKT. Kit 5.50 483 10 x Metal Coax Plug 1.70 484 Focus Unit 7.20 485 Foc/Unit Thom 8500 Type 1.25 486 4.43Mhz Crystal 0.40 488 10 x Ring Type Spk/Gap 1.50 489 TX10 Chass. Focus Unit 7.00 497 De-Soldering Pump 3.50 498 1 x 10 Trimming Tool 1.00 TRANSISTOR/DIODES 230 10 x AC128 1.50 235 50 x BC213L 2.50 250 10 x BD124 9.50 251 10 x BD131 1.50 270 10 x BU208A 1.50 271 10 x BU208 7.50 272 10 x BU326 10.00 273 5 x BU205 3.75 280 25 x 2N3055 (Texas) 7.50 281 10 x 2N2905 (Equiv. BC161/303) 0.50 290 10 x BT106 9.00 292 5 x BT119 4.50 293 5 x BT120 4.50 335 50 x BY127 3.00 Diodes 340 25 x TIP41A 6.50 341 25 x TIP41C 7.00
--	--	--	--	---	---	---

All components are A1 quality from prime manufacturers, and are dispatched by post same day as order received together with any refund due. All goods should be delivered within 4 working days.
Please add 15% VAT and 90p P & P

QUICK SAVE T.V. SPARES

MUXTON HOUSE, MUXTON, TELFORD, SALOP.
REG. OFFICE ONLY. CALLERS STRICTLY BY APPOINTMENT. UK ONLY. PLEASE QUOTE STOCK NO.

VCR Servo Systems

Part 2

Eugene Trundle

We ended last month with an account of the single-motor system used in the Sony SL8000 and Sanyo VTC9300. We'll turn next to the separate-motor systems used in some of the earlier VHS machines.

Simple Two-motor System

The Hitachi VT5000 is a representative example of this type of machine. It uses separate d.c. motors to drive the capstan and drum, both belt coupled and servo controlled. The reference is provided by a 32.765kHz quartz crystal. Fig. 10 shows the system in block diagram form.

Starting with the drum servo (top), during record it's necessary to phase the head rotation to the incoming field sync pulses. These, after division by two and delay by an MMV (record head-switching adjustment), provide a narrow pulse which is used to sample a ramp initiated by the drum PG pulse. The output from the phase comparator sample-and-hold circuit is applied to the motor drive amplifier via an operational amplifier. This constitutes the phase control loop. The system is the same during playback except that the reference signal is this time derived from the crystal oscillator, after division by 1,310 (count down to 25Hz). The tracking control, via the MMV, adjusts the reference/drum phase relationship.

There's also a drum speed control system. This is a simple feedback loop which operates on the principle that increased mechanical loading on the drum motor will reduce its speed and its effective resistance. The negative-going voltage across the motor is applied to the inverting

input of the operational amplifier, increasing the motor drive to compensate. The motor is thus accelerated quickly from standstill and maintained at about the correct speed.

The operation of the capstan servo on record is quite simple. All that's required is constant speed in the face of varying loads. When the capstan is running at the correct speed, the capstan FG generates a 126Hz signal. This is divided by six to give 21Hz sampling pulses. A 21Hz ramp is produced from the reference oscillator's output after division by 1,560. The error voltage produced by the phase comparator circuit is fed to the motor drive amplifier via another operational amplifier.

During playback the capstan servo has an additional task - tracking phase control. The head drum is locked to the crystal oscillator, so if phase lock between the off-tape control track pulses and the oscillator is established, correct tracking will be achieved. This time the oscillator's output is divided by 1,310, to 25Hz, and is used to trigger a ramp which is sampled by the off-tape control pulses. The situation now is that the capstan phase is determined by the off-tape control pulses and the reference signal while the drum phase is controlled by the PG pulses and the reference signal, the latter as it were becoming the common denominator. The tracking control thus achieves its purpose even though it operates via the drum servo.

Capstan speed control is the same in record and playback and is a little more elaborate than the drum speed control system, consisting of a full loop rather than simple negative feedback. The capstan FG rate is propor-

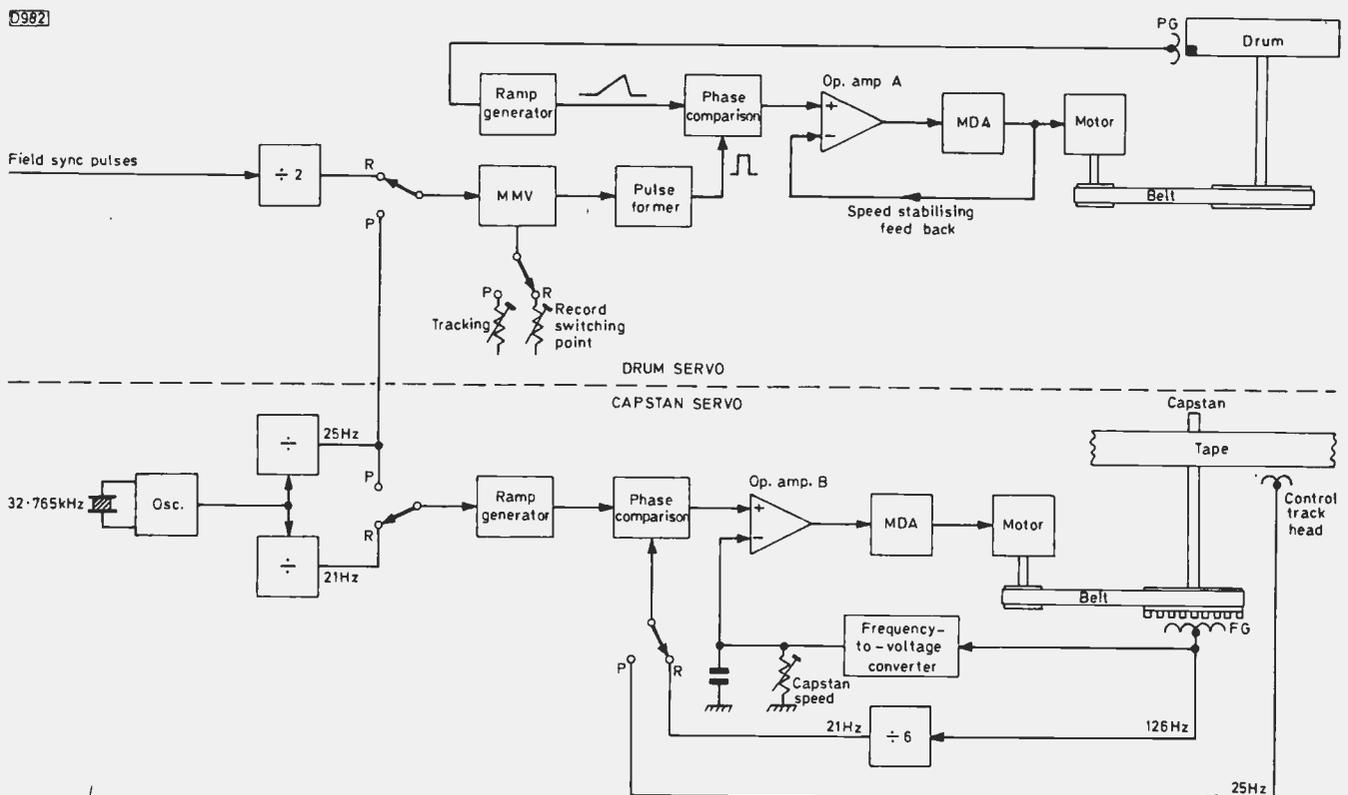


Fig. 10: Block diagram of the servo system used in the Hitachi VT5000 to control two d.c. motors.

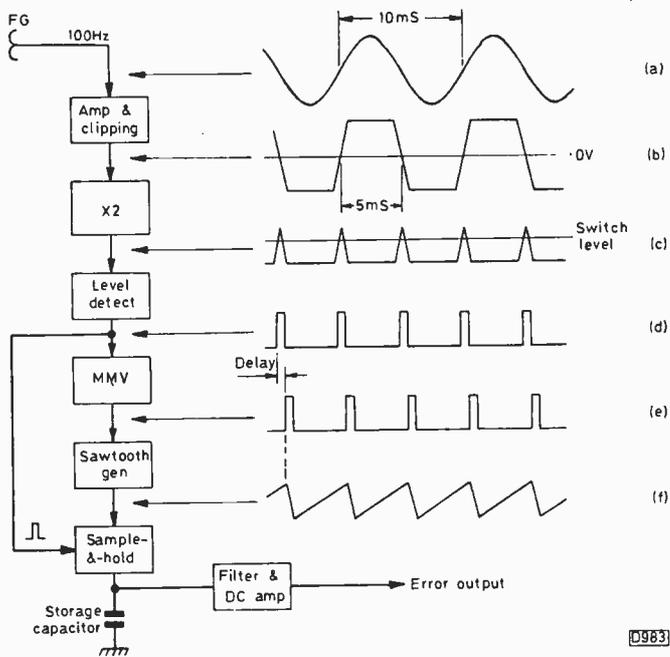


Fig. 11: Speed control system used in the Hitachi VT8000. This employs frequency-to-voltage conversion by means of a ramp and sample system. The duration of the ramp is set by the FG frequency.

tional to speed, the loop maintaining it at 126Hz. A frequency-to-voltage converter produces across the storage capacitor an error voltage which is applied to the inverting input of the operational amplifier: the speed control sets the circuit's operating point. This arrangement deals very effectively with speed changes outside the range of the phase control loop.

Four Loops

The dual-loop servo system just described has become the standard in later machines for both the capstan and drum servos. Let's examine the speed control system used in the Hitachi VT8000, see Fig. 11 – a similar arrangement is used for both servos and operates in both record

and playback. We'll consider the drum servo as it's not complicated by trick-speed switching.

With the drum rotating at 1,500 r.p.m. the drum FG produces a 100Hz sinewave output – waveform (a). This is amplified and clipped to produce waveform (b). The following doubler circuit effectively inverts everything above the zero line, rather like a bridge rectifier, to produce waveform (c). The level detector then produces trigger pulses, (d), which are coincident in time with the zero crossings of the original FG waveform. Next comes a fixed-period MMV which produces a slightly delayed pulse, (e), that in turn triggers a sawtooth generator. Now the longer the ramp, (f), the higher its amplitude: if we sample its final level just before the "flyback", i.e. just before the sawtooth generator is triggered, we shall have a voltage that's proportional to the time lapse between the FG pulses, i.e. the FG frequency. Trigger pulse (d) always occurs at the top of the sawtooth waveform and is used as the sampling pulse.

This ramp and sample system is quite different from the basic sort described earlier in that both the ramp and the sampling pulse are derived from the same source – a sort of electronic incest. The key to this is that the frequency of the whole system is variable. If the drum slows down, the FG frequency will fall below 100Hz and the 5msec intervals between trigger pulses will get longer. Sawtooth (f), having a constant rate of rise, will achieve a higher voltage by the time it's sampled. Thus the error voltage will rise and, fed to the motor, will increase its speed to compensate. The process works in the same manner in reverse, so a constant motor speed is achieved.

The error output from the speed correction loop is simply added to the error output from the phase control loop, which is quite conventional, using its own sample-and-hold phase detector system (see Fig. 12). The drum PG pulses are converted to ramps and fed to a phase comparator whose other input is the divided-by-two field sync pulses during record, thus achieving head/sync pulse phasing, and the counted down output from the crystal oscillator during playback. The capstan FG is locked to the crystal reference during record. During playback the capstan phase, relative to the reference, is governed by the

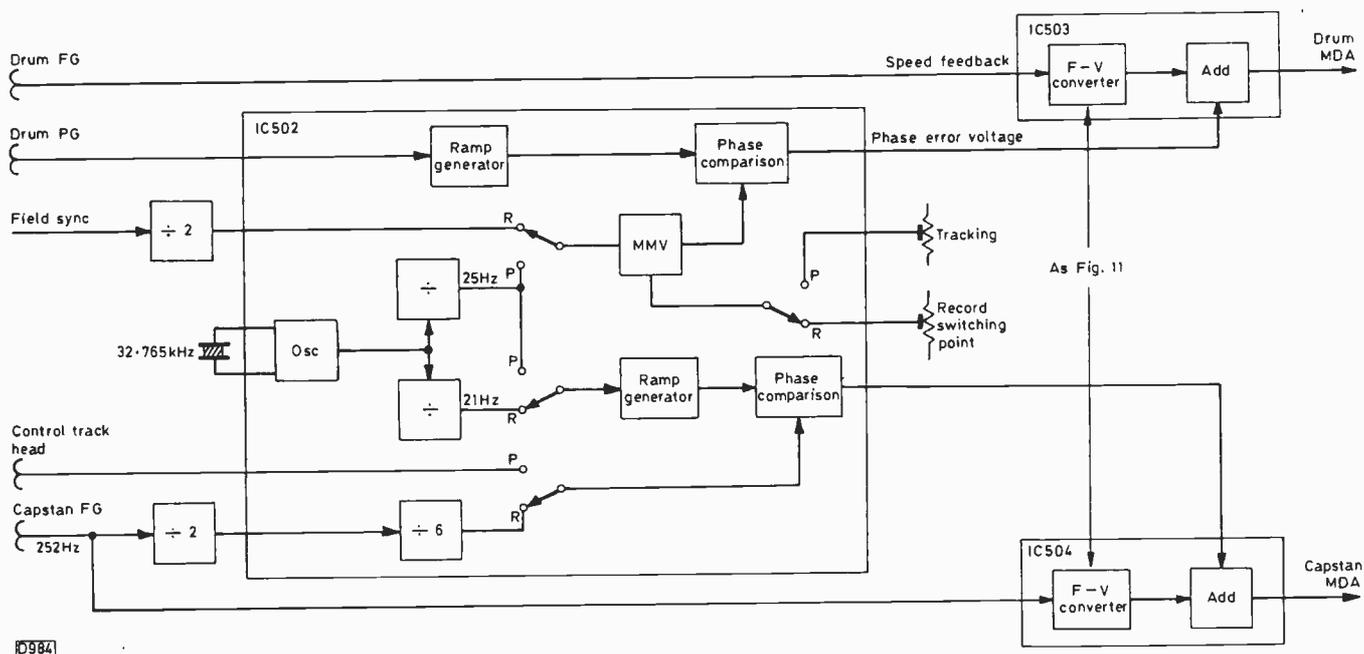


Fig. 12: Addition of the phase and speed control signals. The four-loop system used in the Hitachi VT8000.

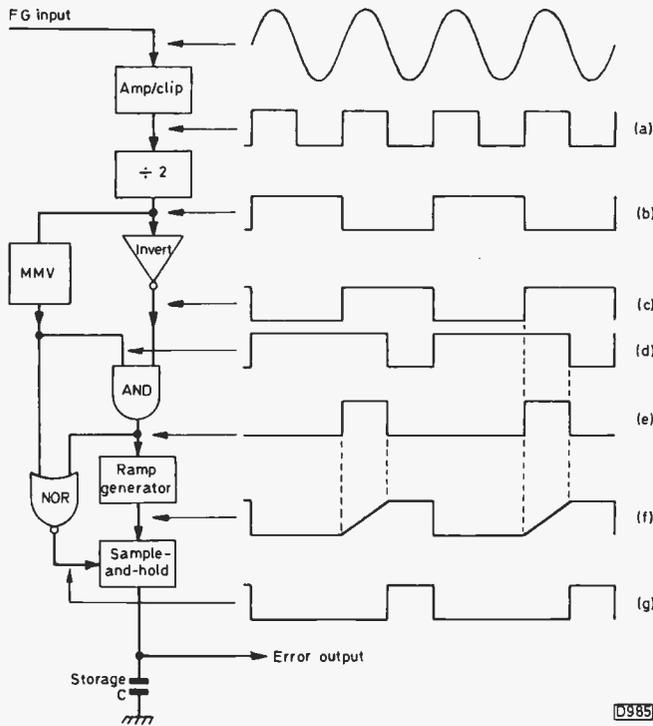


Fig. 13: Frequency-to-voltage conversion technique used in the Panasonic NV7000.

off-tape control track pulses. This arrangement is similar to that used in the VT5000.

The Panasonic NV7000

An alternative approach is used in the Panasonic NV7000, whose speed loop is shown in Fig. 13. Both the capstan and drum are fitted with FGs, which generate 504Hz and 200Hz outputs respectively at normal speeds. Taking the drum loop as our example, the FG signal is first converted to a squarewave, then halved in frequency by a bistable. The output, waveform (b), is fed to an inverter and an MMV. The outputs from these, (c) and (d), are applied to the inputs of an AND gate whose output goes high only when (c) and (d) are both high. Hence waveform (e). During the high period of waveform (e) a constant-slope ramp generator is enabled, and because the on period of the MMV - waveform (d) - is fixed, any variation in FG rate will alter the ramp duration. Thus the terminal ramp voltage is proportional to the FG rate. It remains only to sample the ramp voltage at its highest point to produce an error voltage. Sampling pulse (g) comes from a NOR gate whose inputs are (d) and (e). The storage capacitor providing the hold function charges to the peak ramp voltage, which is the speed error voltage.

In describing the NV7000's speed control loop we said that the MMV's period is fixed. This is not wholly true. It's

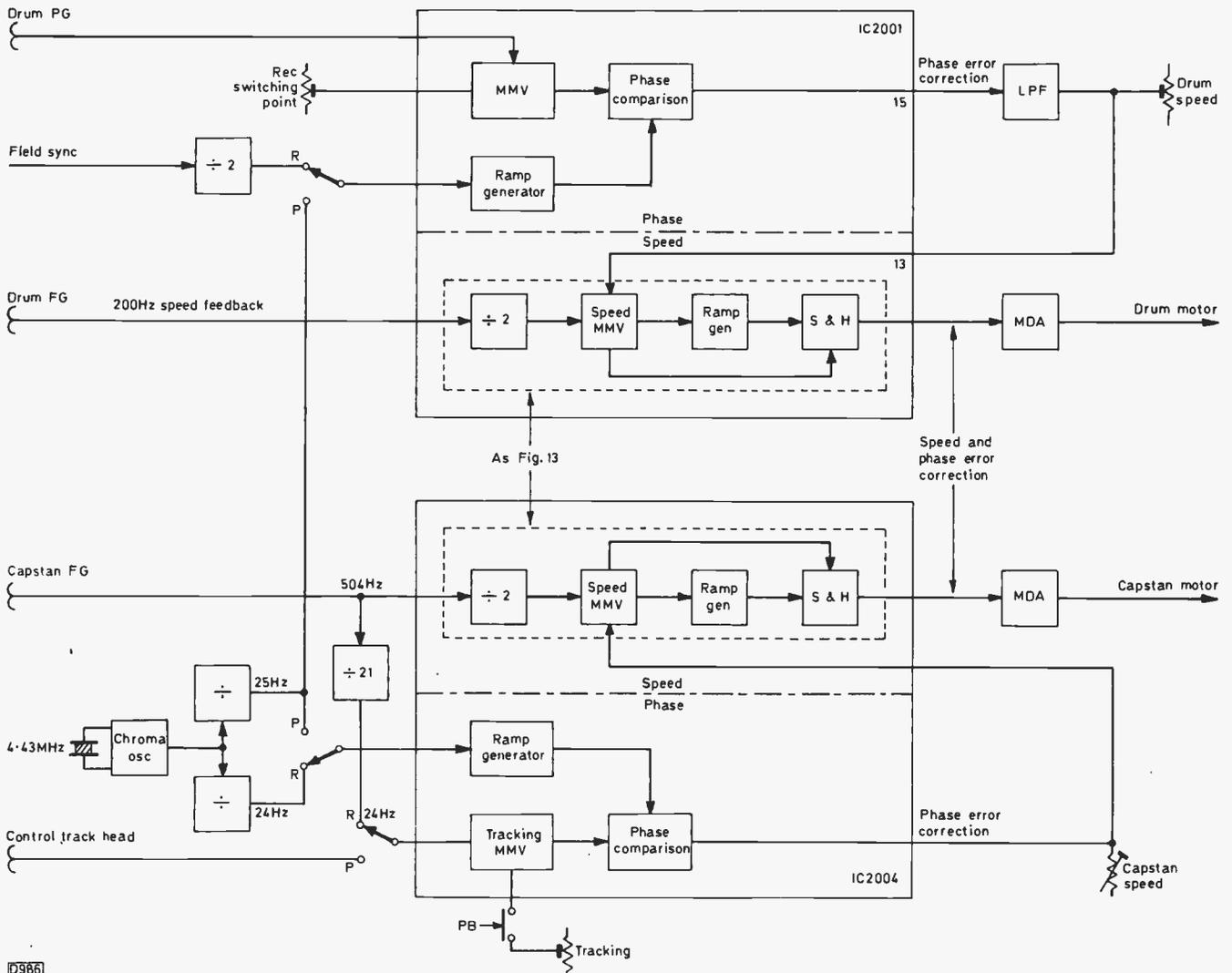


Fig. 14: Phase loops operating on the speed MMVs - Panasonic NV7000. The 4.43MHz chroma reference crystal also provides the servo reference signals.

period is governed by two influences, the free-running speed preset and the phase servo control voltage. Study of the waveforms shown in Fig. 13 will show that the motor's speed depends on the MMV's on/off period, so this is a convenient point to introduce the bias level control (free-running speed adjustment) and the control voltage for the phase correction loop. These are shown in the more detailed block diagram (Fig. 14), where the items in Fig. 13 are shown within broken outlines.

Looking at the drum servo (top), we can see that the idea is to phase the drum PG pulses with a reference, the field sync pulses during record and 25Hz reference pulses derived from the 4.43MHz chroma crystal oscillator after division during playback. The reference pulse triggers a ramp which is sampled by a PG-derived pulse whose timing is adjustable to set the record switching point. The resultant error voltage leaves the chip at pin 15 and, after filtering, is added to the adjustable speed bias voltage. This combined voltage re-enters the chip at pin 13 to vary the period of the speed MMV.

The capstan phase control works similarly. Rotation of the capstan is controlled basically by the crystal derived reference, which is used to generate a ramp. During record this is sampled by the capstan FG pulses while during playback the off-tape control track pulses do the sampling after undergoing an adjustable delay in the tracking MMV. The capstan phase error voltage is fed, along with the set-speed bias, to the capstan speed MMV. Thus as with the drum servo the output from the speed loop provides both speed and phase correction.

Dual-loop Complexities

Why go to all this trouble with the speed control loops when a simple frequency-to-voltage converter suffices in some machines? One answer is improved noise immunity, but what's more important is stability and freedom from drift. There's also the need for trick-speed modes such as multiple speed playback (fast, slow etc.). By inserting dividers into the loop the capstan speed can be set to a multiple of its normal speed while phase lock is maintained: in machines which include these features the servo circuits are arranged to facilitate this. In all cases the heart of an FG-fed speed control loop is some form of frequency-to-voltage converter while the essence of the phase loop is a phase or timing detector.

Digital Servos

There's another way of carrying out these frequency and phase measuring actions - by means of a counting system rather than an analogue ramp arrangement. The basic idea is simple enough. Fig. 15 shows the rudiments of a counting servo whose essential components comprise a couple of counters, a latch, a comparator and an SR (set/reset) bistable. The output from a servo of this type consists of a squarewave whose mark-space ratio is proportional to the error.

In the elementary system shown in Fig. 15 the reference pulse is used to enable counter 1 which will start to count clock pulses from 0000 upwards. If it's a ten-bit counter the maximum count will be 2^{10} , i.e. 1,024. At the clock rate of 1MHz the counter will take about 1msec to reach its full count. Before this happens however the sample pulse appears and activates the latch. In effect this stops the count and dumps the total into the comparator's hold register. If the sample pulse comes 500 μ sec after the

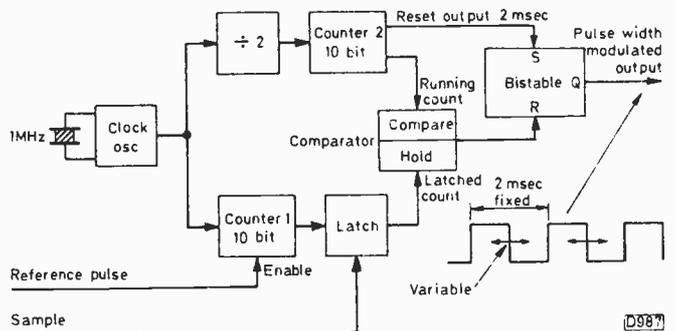


Fig. 15: Simplified outline of a digital servo used to provide phase control.

reference pulse the count will have reached about 512 (binary 100000000). The latch operates and binary 512 is loaded into the comparator as an indication of the time lapse between the arrival of the two pulses.

Now consider the top half of Fig. 15. After emerging from the divide-by-two stage the clock pulses are at 500kHz. These are fed to a second ten-bit counter which also counts from zero to 1024, resetting itself each time it reaches the full count. This count and reset process is continuous for counter 2, and because it's counting 500kHz (2 μ sec period) pulses it resets at $1,024 \times 2\mu\text{sec} = 2\text{msec}$ intervals. Each time it resets a trigger pulse is applied to the set input of the SR bistable, setting the bistable's output high. The continuous count going on in counter 2 is also fed to the comparator, which looks for coincidence between the number in its hold register and the running count. After 1msec counter 2 will have reached 512 so that the counts in the two halves of the comparator match. Bingo! The comparator output produces a pulse which is applied to the SR bistable's reset input, and the output from the bistable goes low. The bistable is being set and reset at 1msec intervals, producing an output with a 1:1 mark-space ratio.

Consider what happens if the motor runs slightly fast. The sample pulse will come close on the heels of the reference pulse, giving counter 1 little time to accumulate a count before the latch operates. So a low number, say 250, will be loaded into the hold register of the comparator. Counter 2, after setting the bistable high when it passed 0, will take only half a millisecond to reach 250 when the comparator detects count coincidence and resets the bistable low again, where it sits for 1.5msec before being set high again by counter 2. Thus the mark-space ratio of the output squarewave has become 1:3. It works the other way round as well, when the motor speed is slow. The rising edges of the output waveform shown in Fig. 15 always occur at 2msec intervals, when counter 2 sets the bistable, the position of the falling edges being determined by the time interval between the reference and sample pulses.

This pulse-width modulated pulse train can be converted to a d.c. voltage proportional to error by being passed through a low-pass RC filter. The result (see Fig. 16) is an error voltage that can be used to control the motor in the same way as in the other servos we've looked at.

Digital Speed Control

The first machines to use digital servos (examples include the Toshiba V5470 and Hitachi VT6500) used conventional feedback systems in the speed loop of one or

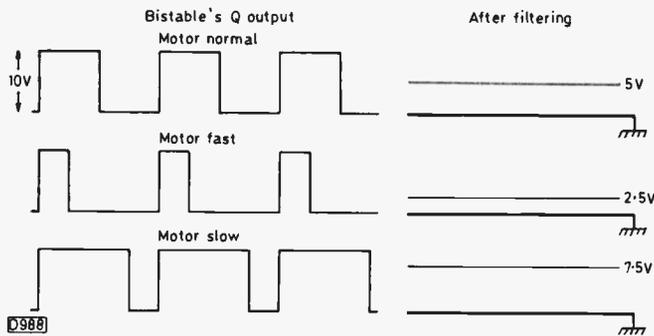


Fig. 16: Low-pass filtering (integration) produces a d.c. error voltage proportional to the mark-space ratio of the squarewave output from the SR bistable.

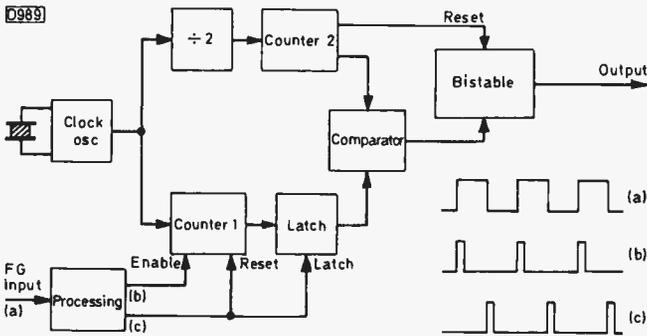


Fig. 17: Digital servo arranged for speed control. The FG pulses operate both counter 1 and the latch.

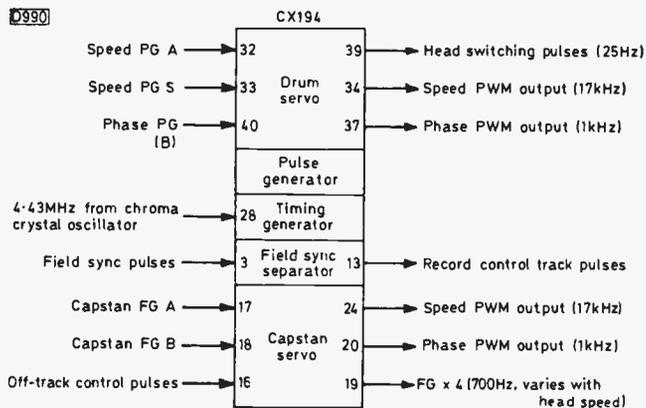


Fig. 18: LSI servo chip used in the Sony F1 and C9. These machines have no drum servo as such: regularly positioned magnets on the drum give six pulses per revolution to PGs A and S. Because the PG S coil is offset by 30° under the drum its pulse lags A by 3msec and the speed loop works to maintain this interval. PG B provides one pulse per drum revolution for phase control.

both servos: later models are fully digitalised for the speed and phase loop of both servos. The basic digital servo we've just described is suitable for use in only a phase correction loop since fundamentally it measures time. For application as a frequency-to-voltage converter in a speed control loop it can be adapted as shown in Fig. 17. Waveform (a) is the squared FG signal. Its rising edge produces waveform (b) which starts counter 1 while its falling edge produces waveform (c) which resets the counter and operates the latch. The latched count will be inversely proportional to the FG frequency and will sit in the comparator's register until counter 2 catches up with it. The rest of the action is the same as before. In practice the speed control pulse-width modulator bistable works at a higher rate (4-17kHz) than the 1kHz or so of a

conventional phase control PWM. In all cases the bistable rate is set by the number of bits in the recirculating counter (counter 2 in our examples) and the clock rate, and is chosen to give an appropriate sampling rate for the loop in question.

In the Panasonic NV777 the counter bit capacities and clock rates vary with the different loop requirements, ranging from eight bits counting $f_{ck}/2^8$ in the capstan servo speed loop to ten bits counting $f_{ck}/2^4$ in the drum servo phase loop. This machine also has some ROM in the digital servo chip to hold "start count from" information. This is addressed by a mode select line. The MN6168VIA i.c. used for this purpose also has a self-oscillate arrangement in the drum phase counter circuit to maintain correct conditions should the field sync pulse momentarily disappear due to noise or interference.

Comparisons

Digital operation brings several advantages. Amongst these are: elimination of the ramp capacitor; zero drift with time and temperature; the elimination of several presets including the record switching point control and the sampling position control; a lower component count; and the opportunity to introduce programmable counting systems to cater for different modes of operation. In a digital servo the traditional ramp is replaced by a count-up circuit while a count coincidence detector in conjunction with a PWM replaces the traditional phase detector.

It's not necessary to know very much about digital circuit operation because the operations take place within an i.c. which (see Fig. 18) can be regarded as a black box. All we can do is to inspect the input and output signals. These i.c.s promise to be reliable animals and we would expect most troubles that may arise to be due to other items such as crystals and motors. Table 1 shows the servo arrangements used in a representative selection of VCRs produced over a period of several years.

Trick Servo Operation

If we define trick playback as any mode in which the tape isn't moving at the same speed as during record, we have still frame, frame advance, cue and review (search functions), slow-motion and high-speed playback on the list. The LP mode and clever-edit facilities are more the concern of the syscon than the servo department. In the trick playback modes (Sony call them jog modes) the rotating video heads are still scanning the tape but because the tape speed is not the same as during record the head scan and video track angles will diverge. This will result (apart from noise bands due to track crossing) in a change in the number of lines per field. The reason for this can be seen in Fig. 19. Now if a TV set starts to see a video signal with non-standard timing, luminance/chrominance registration will first be upset then line lock will be lost. To prevent these things happening, speed compensation is applied to the drum motor (speed up in forward trick, slow down in reverse trick) to maintain the correct line speed. This is all that's required in the drum servo and is easily arranged in the servo loop - usually by providing switched preset potentiometers, sometimes by means of a programmable divider in the reference pulse path to the drum phase loop.

So trick-speed operation mainly concerns the capstan servo. For cue or review the syscon decides the motor direction and its supply voltage is increased by a factor of

Table 1: Comparison of servo arrangements used in different VCRs.

Servo type	Philips N1500	Sanyo VTC9300	Ferguson 3V00	Sony C7	Hitachi VT5000	Hitachi VT8000	Sharp VC9500	Ferguson 3V01	Hitachi VT9500	Panasonic NV333	Toshiba V8600	Sanyo VTC5000	Ferguson 3V23	Panasonic NV777	Hitachi VT6500, VT11	Panasonic NV200	Sony F1, C9
Mains reference	X	X			X	X		X	X		X	X		X			
Crystal reference			X		X	X	X	X	X	X	X	X	X	X	X	X	X
4.43MHz reference				X						X							X
Capstan PB control	X			X	X	X	X		X	X	X	X	X	X	X	X	X
Drum PB control		X	X					X									
Capstan PG	X		X		X	X	X	X	X	X	X	X	X	X	X	X	X
Drum PG	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X
Capstan FG				X	X	X	X	X	X	X	X	X	X	X	X	X	X
Drum FG					X	X	X	X	X	X		X	X	X	X	X	*
Speed and phase loops				X		X	X	X		X	X	X	X	X	X	X	X
Digital servo											X			X	X	X	X

* Drum PG for speed control – see Fig. 18.

two or three. If phase control is applied from a divided down off-tape control track pulse it will be possible to lock the noise bars and hold them steady in these modes. This is done in the Sanyo VTC5000 for example, though an alternative approach is to operate the search functions via the reel drive with the pinch roller disengaged, as in the Toshiba V8600 and Ferguson 3V29 etc. The latter uses the capstan motor to drive the reels and manages to lock mistracking bars by means of a reel servo working on the off-tape control track pulses.

During still-frame operation the capstan is stopped, and for a noise-free display the stopping point is determined by the relative positions of the noise bar in the replay f.m. envelope and the 25Hz head switching squarewave. This will put the noise into the field blanking interval, and because this will obliterate any field sync pulse present a

synthetic field sync pulse is generated from the head switching or head PG pulse and is added to the video output signal. Slow motion consists of a series of still frames, with the capstan motor stepping forward at intervals under the control of the off-tape control track pulses so that a new, correctly aligned track is presented in the path of the head sweeps.

We've been able to mention trick-speed servo operation only briefly here. It's hoped to be able to present more detail on the basic principles in a later article.

Book Notices

The 1983-84 volume of **Radio and Television Servicing** has been published by Macdonald at £22.50. It contains over 850 pages of servicing data for current radio and TV sets and audio equipment (but not VCRs). This series of books has been going for thirty years now.

Servicing Digital Circuits in TV Receivers, by R. Fisher, has been published by Newnes at £13.95. Bob Fisher is a lecturer in digital and television electronics at Plymouth College of Further Education and has written for this magazine from time to time. The book has 270 pages and is a thorough guide to digital techniques as applied to TV receivers, including teletext, Prestel, remote control and tuning systems. There's not a lot on actual servicing – the book is rather an introduction and useful reference standby written with the needs of service personnel in mind.

Servicing Monochrome Portable Television, by G. R. Wilding, has been published by Newnes at £13.50. This book contains some 135 large pages and falls into two sections: first a practical description of the circuitry used in monochrome portable sets, with guidance on fault symptoms and causes; secondly service data, including circuit diagrams and board layouts, for a representative selection of monochrome portables.

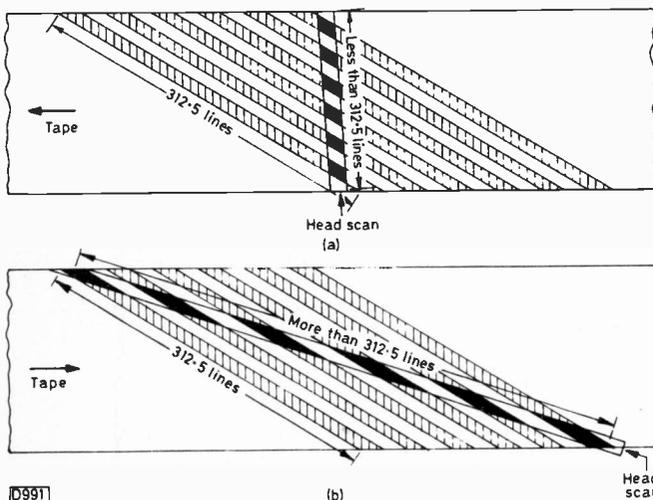


Fig. 19: Video head path with respect to the tracks in (a) cue and (b) review. It can be seen how noise bars arise, also why drum speed correction is required to maintain the correct line scanning rates in these modes.

Service Bureau

Requests for advice in dealing with servicing problems must be accompanied by a £1.00 postal order (made out to IPC Magazines Ltd.), the query coupon from page 679 and a stamped addressed envelope. We can deal with only one query at a time. We regret that we cannot supply service sheets nor answer queries over the telephone.

PANASONIC TC492G

When the set is first switched on it remains dead. You have to operate the on/off switch several times to get it going.

This effect is usually caused by dry-joints around the chopper transformer T801 or the chopper transistor Q801. Some of the leads that connect to the board are of iron to inhibit heat transfer, and they don't solder well. Disconnect them and apply "Tinmans flux" or something similar before retinning and resoldering.

SONY KV1810UB

The screen is modulated from left to right, starting black on the left-hand side then changing linearly to white at the right-hand side. The video circuits have been scoped but nothing wrong can be found. The electrolytics in the brightness circuit have been changed.

The effect is not uncommon in these sets and is generally due to a dried up electrolytic in one of the line output transformer derived supply lines. Check by substitution in the following order C543 (4.7 μ F, 350V, 200V supply - C596 in the Mk. II version), C546 (470 μ F, 25V, 18V supply) and C534 (0.068 μ F, 1.5kV, first anode supply).

GRUNDIG 5010

After the cutout operated a check was made for shorts or anything obviously amiss. As nothing untoward could be found the trip was reset and the set switched on. This time there was a small picture, lacking an inch or so all round, with horizontal foldover in the middle. The only other clue is that R545/6 are blackened and smoked when the set was on.

R545/6 form part of the first anode supply network which is fed from the "earthy" end of the line output transformer's e.h.t. overwinding. The fact that they are burning means that a heavy ripple current is flowing in the overwinding. The e.h.t. tripler is the first suspect, then the first anode supply reservoir capacitor C521. Check the presets R547-9 for damage, also the beam limiter sensing components Di521 and R521.

SHARP 12P-26H

There's sound but no raster - just a faint raster can be seen if the brightness control is turned up slowly to a point where a loud clicking noise starts. When the brightness control is further advanced the raster disappears and the rate of the clicks increases.

The symptom suggests that the e.h.t. rectifier is breaking down under load. An alternative possibility is that the

tube itself is defective. Before checking either of these items, examine the e.h.t. feed lead and the Aquadag earthing.

HITACHI CNP190

There are intermittent brightness variations accompanied by small (not more than two per cent) variations in picture size. The brightness can increase or decrease, and the variations may occur at switch on or after several hours' running. The sound is not affected.

It's likely that the h.t. voltage is varying slightly, but the cause of this may be difficult to trace. Concentrate on the series regulator circuit, checking zener diode CR40 and CR39 which is in series with it, also the potential divider network R910/1/2. Use of heat and freezer spray in this area and on the transistors should narrow the area of search.

BEOVISION 3400 CHASSIS

The fault is intermittent line drive. When the set goes off the lower PL509 in the line output stage overheats. On touching the line driver transistor's connections with the meter probe drive is restored. The transistor has been replaced, also the two silver mica capacitors in the line generator circuit. We've also checked the screened lead to the PL509.

Check thoroughly for dry-joints in the area of the line generator and driver. Then try replacing 2TR2 which drives the emitter of the driver transistor, and the driver's protection diode 2D20. Other suspects include 2D3 which could be leaky, shorting the output from the TAA790 line generator chip, the 13V zener diode 2D1 and the chip itself.

PYE 697 CHASSIS

If the mains voltage drops (indicated by the brightness of the house lights dimming) the picture slowly disappears, returning when the voltage is restored. The PL509 line output valve glows cherry red when the picture goes. The controls have been turned up fully to avoid the problem but the picture takes five-ten minutes to appear while the colour is weak for another twenty minutes or so.

This series of sets is very voltage conscious. If the mains supply regularly falls below 220V a.c., fit an autotransformer to ensure that the set receives 240V. If the mains supply is reasonable, check the heater supply, especially the VA1026 thermistor R304. If this is all right the PCF802 line oscillator could be stopping intermittently.

PHILIPS N1700

The sound is o.k. but the picture is unstable, with intermittent field roll and pulling. The instructions for servo adjustment given in the manual are not very clear.

Ensure that the ruler on the lower drum is free of tape oxide, especially at the ends under the plastic guides. Then adjust the servos as follows. (1) Adjust R9 (drum servo module) so that the picture gap (head overlap point, visible on the picture as a slight horizontal disturbance) is within three lines of the bottom of the picture. This can be done by making trial recordings and playing them back. The adjustment affects record only, and is very critical. (2) Adjust the drum servo ripple control R2 for minimum ripple (scope at test point B31). (3) Short out the control

head (link A41/2), play back a known good tape and adjust R7 (balance control) in the capstan servo module until noise passes through the picture very slowly. Remove the short. (4) Adjust the capstan servo ripple control R3 for minimum ripple (scope at test point B32). (5) Adjust R38 (tracking range adjustment) in the capstan servo sync module for maximum f.m. at plug F21 – this is on panel 71, below panel 51 on the right-hand side. Carry out this adjustment with the tracking control at centre and a recording made on the machine.

TEST CASE

262

Each month we provide an interesting case of television servicing to exercise your ingenuity. These are not trick questions but are based on actual practical faults.

A lucrative and growing trade is being done by some TV and video workshops in converting foreign equipment for UK use. Products from across the Atlantic are not really practical candidates for conversion, and equipment intended for use in other parts of the world can be difficult – we had to turn away an Australian colour set a while ago because it was fitted with a v.h.f. tuner and the estimated time and expense involved in finding and fitting a u.h.f. tuner and station selector/potentiometer bank made the whole thing uneconomic. With equipment designed for use in continental Europe and the Middle East however modification can be a practical proposition. Incidentally, it's amazing how many multi-standard VCRs and TV sets can't get a grip on 6MHz sound.

Our concern this month is with a certain Sharp VCR – the W. German version of the VC3300. It's designed to work on the PAL-G standard, whose main difference from our own system I is the 5.5MHz sound-vision spacing. The conversion was required in a hurry by an itinerant civil engineer, and the job was entrusted to a small service company with little experience of this sort of thing. It seemed straightforward enough to them – once the considerable problems of physical access were overcome!

What they did was to adjust the intercarrier generator coil in the VCR's u.h.f. modulator to 6MHz, which was easily done by replaying a good tape and twiddling for best sound via a UK-type TV set. The sound receiver section of the VCR was then tackled. New 6MHz ceramic filters were fitted in the intercarrier sound take-off and the video channel 6MHz notch filter positions. The two-leg second intercarrier sound filter in the video channel was replaced with the special UK type available from Sharp spares. Finally, the quadrature coil was adjusted for best E-E sound and the r.f. modulator department was given a

tweak. On test all went well on all functions, and only slight adjustment was needed to the audio E-E and audio playback level potentiometers to equalise the sound levels. The two proprietors of the service outfit were well pleased with their efforts, and returned the VCR to its owner with a flourish.

Pride comes before the fall, doesn't it? The roving customer returned a few weeks later, after sojourns in London and elsewhere. He was not very happy, and demonstrated to our startled pair recordings made since the conversion. They were marred by patterning effects and in some cases a degree of caption buzz. Thinking that the quadrature coil's alignment was perhaps not spot on they checked this on a "Ceefax in vision" daytime transmission, only to find that their original alignment was correct.

With a little help from a friend, they finally realised the source of the trouble, and in doing so had a basic lesson in TV theory! Where had they gone wrong? In their new-found wisdom they now offer full-specification conversions with a guarantee of no spurious effects. You shouldn't need the Sharp circuit to puzzle this one out: answer next month!

ANSWER TO TEST CASE 261

– page 618 last month –

A Rank colour set fitted with the T20A chassis was in the spotlight last month. After some consultation between site and workshop we'd reached the point where the line oscillator's start-up circuit had been overridden and the line driver transistor was operating normally, though the line output stage was still dormant. It will perhaps be remembered that the set had earlier "eaten" a BU208A line output transistor for reasons unknown . . .

Both these symptoms had a common cause in the BU208A's base feed resistor 5R8 (1Ω) which was found to be open-circuit and dry-jointed to boot. Whether the bad joints led to its failure or whether it overheated to crystallise the solder is open to question, but there was no doubt that its original spasms had caused overheating and the eventual failure of the previous line output transistor. There's a nice little 4W resistor in there now (it's not a BEABed component!) and we don't expect any further trouble, especially as 4C19 and the notorious 4R16 (910Ω) were replaced at the same time by way of a little preventive medicine.

QUERY COUPON

**Available until 17th October 1984.
One coupon, plus a £1.00 (inc. VAT)
postal order, must accompany EACH
PROBLEM sent in accordance with the
notice printed on page 678.**

TELEVISION OCTOBER 1984

Published on approximately the 22nd of each month by IPC Magazines Limited, King's Reach Tower, Stamford Street, London SE1 9LS. Filmsetting by Trutape Setting Systems, 220-228 Northdown Road, Margate, Kent. Printed in England by The Riverside Press Ltd., Thanet Way, Whitstable, Kent. Distributed by IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. Sole Agents for Australia and New Zealand – Gordon and Gotch (A/sia) Ltd.; South Africa – Central News Agency Ltd. Subscriptions: Inland £11, overseas (surface mail) £12 per annum, payable to Quadrant Subscription Services Ltd., Oakfield House, Perymount Road, Haywards Heath, Sussex RH16 3DH. "Television" is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to currency exchange fluctuations and VAT, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever. ISSN 0032-647X.

The World of

“TELEPANELS”

52 Mount Pleasant Road, Chigwell, Essex.
Telephone 01-729 0506.



COMPARE OUR PRICES!

COMPARE OUR SERVICE!

	IF	TUNER	DECODER	G8/G9 DECODER IF COMBINED	LINE OUTPUT	POWER	CONVERG	FRAME	VIDEO	6 WAY TUNER SWITCH BANK
PHILIPS G.8	5.00	4.50	7.00	15.00	14.00	8.00	5.00	5.00		3.50
THORN 3000/3500	2.00	5.75	4.00		8.00	8.00	5.00	6.00	5.00	1.75
GEC 2110	10.00		5.00		12.00	6.00	5.00	5.00	5.00	5.00
PYE 731	8.00		10.00		18.00	10.00	7.00	8.00		4.50
PUSH Z/718	7.50	6.50	14.00		24.00	3.00	5.00	14.00		
BIJSH T/20	7.50	6.50	14.00		19.00	19.00	5.00	14.00		
DECCA BRADFORD	3.00		7.00			4.00		FRAME TIME BASE £4		

TRIPLERS FOR ALL MODELS £3.00 SPEAKERS £1.50

P+P 1 PANEL £1.50 2 PANELS OR MORE £3.00

CASH WITH ORDER - PLEASE

POST OFF YOUR CHEQUE NOW! & YOUR PANELS SENT BY RETURN OF POST!!!

TELEPART

Telegen-1

PRICE

- * EXCEPTIONALLY LIGHT AND DURABLE
- * POCKET SIZE FOR OUTSIDE SERVICE
- * PP3 BATTERY POWER SOURCE
- * FIVE DIFFERENT TEST PATTERNS FOR COLOUR & MONO TV
- * CROSSHATCH GRID * DOT MATRIX
- * WHITE RASTER
- * HORIZONTALS * VERTICLES
- * 3.5mm JACK SOCKET FOR OPTIONAL P.S.U.



A lightweight, extremely portable and versatile pattern generator for black/white and colour T.V. alignment and service at the customer's home. At the turn of a switch, the generator can provide five essential test patterns for correct installation, fast checks and repairs. Pattern stability is first class and compares favourably with other more costly bulky generators only suitable for bench work. The generator is pocket size measuring 10 x 7.5 x 4 cm and weighs only 190 grams. Switched 3.5 mm jack socket allows use of external power supply with battery in situ.

Telegen-2

PRICE

- * EXCEPTIONALLY LIGHT & DURABLE
- * COMPACT 10 x 12 x 4.5 cms
- * RED RASTER * GREEN RASTER
- * BLUE RASTER
- * COLOUR BARS
- * 3.5 mm JACK SOCKET FOR P.S.U.
- * PROVIDES UHF SIGNAL APPROX. CHANNEL 35



Telegen 2 is a colour bar generator at a very modest price and yet is extremely effective, stable and durable. It is the perfect compliment to Telegen 1, giving colour bars arranged in the following sequence: white, yellow, cyan, green, magenta, red, blue and black. The unit provides a signal in the UHF band approx. Channel 35 and requires a supply of 14 to 18 volts D.C.

Power Supply

A switchable power supply ideally suited to both Telegen 1 and Telegen 2.

PRICE £3.95 (Subject to V.A.T.)
POST AND PACKING £1.25 + V.A.T.

32 TEMPLE STREET, WOLVERHAMPTON
WV2 4AN. TEL: (0902) 773122

ELECTRON GUNS TV TUBE COMPONENTS

If you are Rebuilding or Manufacturing TV tubes - We are the leading suppliers of Electron Guns and TV Tube Components to the TV Tube Industry. We specialise in all aspects of Electron Mount Technology.

Our product range includes more than 250 gun types for Colour, In Line, Mono and Display Tubes along with Mount Parts, Bases, Getters, Seal-offs, and all other associated items for TV Tube Production.

A Full Technical Back-up and Advisory Service is available to all customers World-wide.

Please request our current catalogues and Data Information.



GRIFTRONIC
EMISSION LTD

NEW ROAD,
STUDLEY,
WARWICKSHIRE B80 7LY
ENGLAND.

Telephone: 052-785 2684 or 2639 Telex: 336924 Grifem G.

2 YR. GUARANTEE **APOLLO** 20/30 AX

TRADE AND QUANTITY DISCOUNTS


FREE LOCAL DELIVERY - SAME DAY FITTING SERVICE £20.
FAST MAIL ORDER GB 2-3 DAYS - OVERSEAS ON REQUEST.

A47 32/343X 470 BCB22	£37
470 ESB22/EFB22/ERB22	£45
A51-161X	£45
A51-220X/192X	£37
510 JKB22/JEB22/JDB22/ALB22	£45
A56-120X/123/140/410	£38
560 DZB22/HB22/AKB22	£45
A63-120X	£39
A66-120X A67-120X/140/150/200X	£39
20AX A56-500X/510X A66-500X/510X	£48
30AX A56-540X/A66-540X	£48

If your tube type is not in stock we can arrange collection - rebuilding + redeliver


PLEASE PHONE BEFORE CALLING

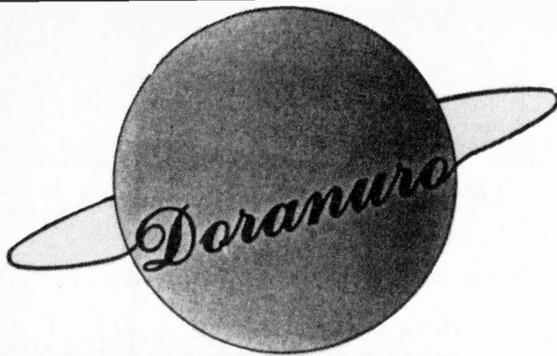061-799 0854. 24 hour answering service
43 Clarke Crescent, Little Hulton, Worsley, Nr Manchester M28 6XL



ENFIELD TRANSFORMERS LIMITED

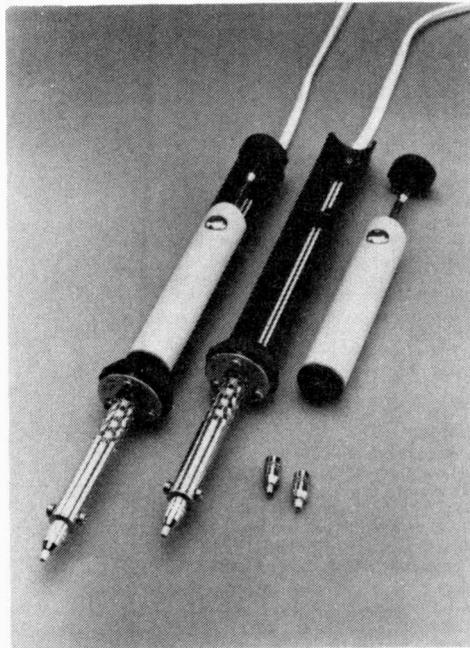7 CENTENARY ESTATE, JEFFREYS ROAD, ENFIELD, MIDDLESEX EN3 7UF.
Tel: 01-805 5438 & 01-805 6078
Telex: 261295



**NEW PRODUCTS
NEW PRODUCTS**

THE BEST THING SINCE BUTTERED TOAST – A MUST FOR TODAY'S 40 AND 60 PIN I.C. NO MORE THREE HANDED DE SOLDERING – IDEAL EVEN ON DOUBLE SIDED PRINT SONY VIDEO AND GEC ETC.

SA-6

Revolutionary new electric desoldering iron combines the ease and portability of a hand-held, manual, desolder pump, with performance of an industrial desolder station. This unique AC powered compact tool features portable, one-hand desoldering eliminating the need for a separate soldering iron and desolder pump. No air line required. Essential for all tool kits, field service technicians, and repairmen, as well as production applications. Vacuum chamber is easily removed for cleaning or replacement. Replacement tips available. Tool is supplied with SAT-6-059 tip; diameter .059 inch (1,5mm).

Model No.	INPUT VOLTAGE	
SA-6-115	115V AC 50/60Hz	
SA-6-230	230V AC 50/60Hz	

NOZZLE	NOZZLE HOLE DIAMETER	
	INCH	MM
SAT-6-059	.059	1,5
SAT-6-070	.070	1,77

FEATURES:

- Self contained suction power and heating element. 30 watt.
- Economical.
- Lightweight 4oz. (113gms).
- Compact size 10¼ inches (26cm).
- Replacement nozzles available.

**AVAILABLE ONLY FROM
DORANURO – SEND TODAY**

NAME	
ADDRESS 1	
ADDRESS 2	
ADDRESS 3	
POST CODE	
SA-6-230	QTY @ £16.00
SAT-6-059	QTY @ £1.95
SAT-6-070	QTY @ £1.95
SUB TOTAL	
POST & PACKING & INS:	95
SUB TOTAL	
VAT @ 15%	
TOTAL ENCLOSED	
PLEASE RUSH THIS ORDER TO ME BY RETURN OF POST	

**ALMOST UN-CLOGABLE, THIS
TOOL WILL BECOME INVALUABLE
ONCE USED**

NO WORKERS!

WITH OVER 1,000 ARRIVING WEEKLY WE DON'T HAVE TIME

ALL SETS UNTESTED

WE ARE ONE OF THE OLDEST ESTABLISHED EX-RENTAL DEALERS WITH THE SAME RENTAL COMPANY FOR OVER 15 YEARS.

LOW SUMMER PRICES

GEC S/State.....	£15
GEC Hybrid.....	£8
BUSH 1 and 2 Chip.....	£10
DECCA.....	from £10
AUTOVOX.....	£15
NORDMENDE.....	£15
SALORA S/State, some Remotes.....	£15
SALORA Hybrid.....	£8
TANDBERG S/State Dual Tuners.....	£20
TANDBERG Hybrid Dual Tuners.....	£8
PHILIPS G8.....	from £10
17" THORN.....	£15
22/26" THORN.....	from £10
MONO 20" S/STD.....	£5
MONO 24" and D/STD.....	£1

BEST DEAL IN U.K.

**CASH ONLY,
IT DOESN'T BOUNCE!**

MIXED LOADS DIRECT FROM SOURCE AVAILABLE AT KEEN PRICES

FRANK FORD

(TV TRADE DISPOSALS)
SCHOOL LANE, GUIDE,
BLACKBURN, LANCS.
Telephone: 0254 64489

TV TUBE POLISHING

AT

Your Own Premises
with our DIY Polishing Kit

The Kit includes:

Everything you need to polish approx. 25" tubes to a high standard. Detailed instructions on how to do the polishing. All you require is an Electric Drill.

Kit Price £45 inc P&P and VAT.

Available from Luton only.

*Depends on depth and area to be polished.

TV TUBES TUBE POLISHING

FREE DELIVERY*

Quality, High Temperature Reprocessing

Colour Tubes	One year guarantee (optional extension up to three years)	Two year guarantee (optional extension up to four years)
Delta		
90° up to 20"	£26	£29
90° up to 22"	£30	£33
90° up to 25"	£32	£35
110° 25"	£33	£36
(fast heat, narrow neck) in Line & PIL		
Up to 20"	£36	£42
Up to 22"	£38	£44
Up to 25"	£40	£46

All tubes exchange glass required.

Your good, working tubes with scratches or small chips, can be POLISHED with our purpose built polishing equipment. Only £7 per tube.

Delivery charge on colour tubes: Within 40 miles of Luton.

1 tube £4. 2 or more tubes FREE DELIVERY*

Nationwide delivery available, charges on application.

Please add 15% VAT to all prices. Callers welcome. Please phone first.

WELL VIEW

114-134 Midland Rd,
Luton, Beds.

Open Mon-Fri 8am-6pm, Sat 9am-5pm. Tel. 0582-410787

Your Local Tube Stockist:

Well View, Southampton. Tel. 0703 331837.

Retach Ltd., Northwood, Middx. Tel. 09274-27019

West One Distributors Ltd., Chesham, Buckinghamshire.

Tel. 0494-778197

Rushden Rentals Ltd., Rushden, Northants. Tel. 0933-314901

Daventry Rentals, Daventry, Northants. Tel. 03272 77436

Rea & Holland, Ipswich, Suffolk. Tel. 0473 827562

WANTED A56/A66-510X/540X Old glass for cash

SATELLITE RECEIVING EQUIPMENT

1.9M, 2.5M and 5M Harrison Dishes
Sat-Tec R5000 4GHz Receivers
Avcom COM-2B 4GHz Receivers
California Amplifier 4GHz LNAs
Chaparral Feed Horns

Components: Chip capacitors and Resistors, Microwave Substrate, PTFE etc.

HARRISON ELECTRONICS

22 Milton Road,

Westcliff-on-Sea, Essex SS0 7JX.

Telephone: Southend (0702) 332338

IRISH TV NOTICE (SUMMER SALE)

We can supply in good working order Bush, Pye and Ferguson from £60, Philips G.8. From £80, Decca from £90, B/White £25, Re-Gunned C.R.T.s from £40 (We have our own Re-Gunning plant). 500 sets to choose from. Fresh stocks weekly. Phone now for full price list to Ireland's largest distributor of used TVs to the trade.

ALL PRICES INCLUDE V.A.T.

We can deliver to any part of Ireland.

TELE SPARES LTD.

Unit 113, Elm Road,
Western Industrial Estate,
Dublin 12, Ireland.

Telephone: Dublin 521211/521756.

JOHN GREEN TELEVISIONS

FOR BEST QUALITY EX-RENTAL TVs

ALL SETS IN A1 WORKING ORDER

BUSH 20"-22"	Single/Double IC Decoder	ALL £20 + VAT
DECCA 17"-26"	6 Button, Varicap Tuner Hybrid Chassis	ALL £25 + VAT
FERGUSON 17"	Solid State	ALL £25 + VAT
GEC 22"	Plastic or Wood Cabinet 6 Button, Solid State	ALL £30 + VAT
PHILIPS 550	Solid State	ALL £30 + VAT

DISCOUNT ON ORDERS OVER 10

PHONE NOW ON

BLACKPOOL 696266

**JOHN GREEN TELEVISIONS
1 CORNFORD ROAD, MARTON, BLACKPOOL
TEL. BLACKPOOL 696266**

CentreVision

TEL: 0222-44754
SLOPER ROAD
LECKWITH
CARDIFF CF1 8AB

OPPOSITE CITY FOOTBALL
GROUND
5 MINS FROM M4

★ WORKING SETS ★

TELEVISION/VIDEO
(VHS + BETA)
MOST IN WORKING ORDER
WITH STAND

- | | |
|------------------------------------|------|
| ★ ITT CD752 REMOTE | £115 |
| ★ PHILIPS G11 (some remote) | £65 |
| ★ GEC STARLINE 22-20 (Remote) | £55 |
| ★ PYE CHELSEA | £38 |
| ★ THORN 9000 20" | £39 |
| ★ DECCA 22" BLACK
FRONT VERICAP | £30 |
| ★ RANK T20 REMOTE | £65 |
| ★ OFF THE PILE SETS FROM | £8 |

PRICES SUBJECT TO VAT

OPENING HOURS:
MONDAY - FRIDAY 9.00 - 5.30
SATURDAY 9.00 - 1.00

**CUSTOMER CAN'T PAY?
DONT LOSE HIM FIT A TV METER**



COINAGE
AVAILABLE
10p
50p
£1

COMPLETELY VARIABLE TIMINGS

Alberice METERS
LIMITED

MANUFACTURERS OF TV COIN OPERATED
METERS CONTACT (0202) 674272
87-89 Sterte Avenue,
Poole, Dorset. BH15 2AW.
Telex: 418253 LUMIC G

ATTENTION!!!

**CHROMA VISIONS OFFER TO THE
EXPORT AND HOME MARKET**

We have a large quantity of GEC CTV's, UHF and VHF, all in excellent working condition, with excellent tubes and cabinets. No tubes are boosted. Also in stock are brand new, boxed, TV and Video Stands from £4.00 each. TV sets ideal for rental or retail market.

Enquiries please ring:

021 784 2561

811A Ashwood Heath Road, Birmingham.

P.S: WE DO NOT SELL ANY RUBBISH

MAIL ORDER ADVERTISING

British Code of Advertising Practice
Advertisements in this publication are required to conform to the British Code of Advertising Practice. In respect of mail order advertisements where money is paid in advance, the code requires advertisers to fulfil orders within 28 days, unless a longer delivery period is stated. Where goods are returned undamaged within seven days, the purchaser's money must be refunded. Please retain proof of postage/despatch as this may be needed.

Mail Order Protection Scheme

If you order goods from Mail Order advertisements in this magazine and pay by post in advance of delivery, Television will consider you for compensation if the Advertiser should become insolvent or bankrupt provided:

- (1) You have not received the goods or had your money returned; and
- (2) You write to the Publisher of Television summarising the situation not earlier than 28 days from the day you sent your order and not later than two months from that day.

Please do not wait until the last moment to inform us. When you write, we will tell you how to make your claim and what evidence of payment is required.

We guarantee to meet claims from readers made in accordance with the above procedure as soon as possible after the Advertiser has been declared bankrupt or insolvent.

This guarantee covers only advance payment sent in direct response to an advertisement in this magazine not for example, payment made in response to catalogues etc., received as a result of answering such advertisements. Classified advertisements are excluded.

AA117 9p	BC182L 6p	BD225 31p	BU110 110p	TIP42A 22p	2N2484 20p	2SC1969 130p	IN.4002 4p	LM323K 420p	PCL85 55p	4032 67p	4506 110p
AA119 9p	BC183 6p	BD232 31p	BU111 140p	TIP42C 25p	2N2646 38p	2SC2029 120p	IN.4003 4p	LM723 32p	PCL86 55p	4034 145p	4507 45p
AA132 9p	BC183L 6p	BD234 32p	BU126 70p	TIP47 40p		2SC2078 120p	IN.4004 4p	78HGKC 570p	PCL805 55p	4035 70p	4508 125p
AC107 28p	BC184 6p	BD237 21p	BU204 70p	TIP48 40p	2N2904 20p	2SC2122A 200p	IN.4005 4p	78H05KC 520p	PFL200 85p	4038 71p	4510 57p
AC126 17p	BC184L 6p	BD238 24p	BU205 70p	TIP110 40p	2N2905 20p	2SC2352 27p	IN.4006 4p	78GUIC 190p	PL36 80p	4040 57p	4511 57p
AC127 15p	BC184L 6p	BD433 28p	BU208 75p	TIP112 54p	2N2906 18p	2SD234 37p	IN.4007 5p	79GUIC 215p	PL504 95p	4041 40p	4512 57p
AC128 25p	BC212L 6p	BD437 28p	BU208A 80p	TIP115 45p	2N2907 18p	2SK135 400p	IN.4148 2p	79HGKC 670p	PL508 190p	4042 58p	4513 120p
AC129K 15p	BC213 6p	BD535 38p	BU208B 120p	TIP117 56p	2N3019 28p	TAT205 150p	IN.5400 9p		PL519 450p	4043 57p	4514 110p
AC141K 23p	BC213L 6p	BD536 38p	BU209 120p	TIP121 46p	2N3053 18p	UPC575 100p	IN.5401 10p	VALVES	PY81 70p	4044 56p	4516 65p
AC142K 23p	BC214 6p	BD537 40p	BU406 85p	TIP122 47p	2N3054 35p		IN.5402 10p	DY87 53p	PY88 48p	4047 65p	4518 65p
AC153K 23p	BC214L 6p	BD538 40p	BU407 75p	TIP125 47p	2N3055 32p		IN.5403 11p	DY802 45p	PY88 48p	4048 49p	4520 65p
AC176 18p	BC237 7p	BDX32 100p	BU408 100p	TIP126 56p	2N3440 58p		IN.5404 11p	EC82 40p	PY88 48p	4049 40p	4522 60p
AC176K 20p	BC238 7p	BDX65 80p	BU500 110p	TIP127 56p	2N3442 85p		IN.5405 12p	EC83 43p	PY88 48p	4050 40p	4526 60p
AC187 15p	BC300 16p	BF180 16p	BU526 80p	TIP127 56p	2N3440 58p		IN.5406 13p	EC84 40p	PY88 48p	4051 62p	4527 60p
AC187K 20p	BC301 18p	BF181 18p		TIP147 100p	2N3702 9p		IN.5407 13p	EC85 40p	PY88 48p	4052 61p	4528 65p
AC188 17p	BC302 18p	BF183 20p		TIP2955 34p	2N3703 9p		IN.5408 13p	EC88 49p	PY88 48p	4053 61p	74 SERIES
AC188K 23p	BC303 18p	BF184 20p		TIP3054 34p	2N3704 9p			EC88A 49p	PY88 48p	4054 85p	7400 22p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3705 9p			EC88B 49p	PY88 48p	4055 85p	7401 16p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3706 9p			EC88C 49p	PY88 48p	4056 85p	7402 18p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3707 9p			EC88D 49p	PY88 48p	4057 85p	7403 22p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3708 9p			EC88E 49p	PY88 48p	4058 85p	7404 18p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3709 9p			EC88F 49p	PY88 48p	4059 85p	7405 10p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3710 9p			EC88G 49p	PY88 48p	4060 85p	7406 100p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3711 85p			EC88H 49p	PY88 48p	4061 85p	7407 80p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3712 85p			EC88I 49p	PY88 48p	4062 85p	7408 25p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3713 85p			EC88J 49p	PY88 48p	4063 85p	7409 20p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3714 85p			EC88K 49p	PY88 48p	4064 85p	7410 20p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3715 85p			EC88L 49p	PY88 48p	4065 85p	7411 35p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3716 85p			EC88M 49p	PY88 48p	4066 85p	7412 35p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3717 85p			EC88N 49p	PY88 48p	4067 85p	7413 35p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3718 85p			EC88O 49p	PY88 48p	4068 85p	7414 35p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3719 85p			EC88P 49p	PY88 48p	4069 85p	7415 35p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3720 85p			EC88Q 49p	PY88 48p	4070 85p	7416 35p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3721 85p			EC88R 49p	PY88 48p	4071 85p	7417 32p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3722 85p			EC88S 49p	PY88 48p	4072 85p	7418 32p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3723 85p			EC88T 49p	PY88 48p	4073 85p	7419 32p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3724 85p			EC88U 49p	PY88 48p	4074 85p	7420 22p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3725 85p			EC88V 49p	PY88 48p	4075 85p	7421 25p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3726 85p			EC88W 49p	PY88 48p	4076 85p	7422 25p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3727 85p			EC88X 49p	PY88 48p	4077 85p	7423 15p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3728 85p			EC88Y 49p	PY88 48p	4078 85p	7424 15p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3729 85p			EC88Z 49p	PY88 48p	4079 85p	7425 15p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3730 85p			EC88AA 49p	PY88 48p	4080 85p	7426 25p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3731 85p			EC88AB 49p	PY88 48p	4081 85p	7427 28p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3732 85p			EC88AC 49p	PY88 48p	4082 85p	7428 28p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3733 85p			EC88AD 49p	PY88 48p	4083 85p	7429 60p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3734 85p			EC88AE 49p	PY88 48p	4084 85p	7430 60p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3735 85p			EC88AF 49p	PY88 48p	4085 85p	7431 60p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3736 85p			EC88AG 49p	PY88 48p	4086 85p	7432 60p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3737 85p			EC88AH 49p	PY88 48p	4087 85p	7433 60p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3738 85p			EC88AI 49p	PY88 48p	4088 85p	7434 60p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3739 85p			EC88AJ 49p	PY88 48p	4089 85p	7435 60p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3740 85p			EC88AK 49p	PY88 48p	4090 85p	7436 60p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3741 85p			EC88AL 49p	PY88 48p	4091 85p	7437 60p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3742 85p			EC88AM 49p	PY88 48p	4092 85p	7438 60p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3743 85p			EC88AN 49p	PY88 48p	4093 85p	7439 60p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3744 85p			EC88AO 49p	PY88 48p	4094 85p	7440 60p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3745 85p			EC88AP 49p	PY88 48p	4095 85p	7441 60p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3746 85p			EC88AQ 49p	PY88 48p	4096 85p	7442 60p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3747 85p			EC88AR 49p	PY88 48p	4097 85p	7443 60p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3748 85p			EC88AS 49p	PY88 48p	4098 85p	7444 60p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3749 85p			EC88AT 49p	PY88 48p	4099 85p	7445 60p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3750 85p			EC88AU 49p	PY88 48p	4100 85p	7446 60p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3751 85p			EC88AV 49p	PY88 48p	4101 85p	7447 60p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3752 85p			EC88AW 49p	PY88 48p	4102 85p	7448 60p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3753 85p			EC88AX 49p	PY88 48p	4103 85p	7449 60p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3754 85p			EC88AY 49p	PY88 48p	4104 85p	7450 60p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3755 85p			EC88AZ 49p	PY88 48p	4105 85p	7451 60p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3756 85p			EC88BA 49p	PY88 48p	4106 85p	7452 60p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3757 85p			EC88BB 49p	PY88 48p	4107 85p	7453 60p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3758 85p			EC88BC 49p	PY88 48p	4108 85p	7454 60p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3759 85p			EC88BD 49p	PY88 48p	4109 85p	7455 60p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3760 85p			EC88BE 49p	PY88 48p	4110 85p	7456 60p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3761 85p			EC88BF 49p	PY88 48p	4111 85p	7457 60p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3762 85p			EC88BG 49p	PY88 48p	4112 85p	7458 60p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3763 85p			EC88BH 49p	PY88 48p	4113 85p	7459 60p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3764 85p			EC88BI 49p	PY88 48p	4114 85p	7460 60p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3765 85p			EC88BJ 49p	PY88 48p	4115 85p	7461 60p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N3766 85p			EC88BK 49p	PY88 48p	4116 85p	7462 60p
AC188K 23p	BC303 18p	BF184 20p		TIP3055 34p	2N						

CENTRAL T.V.

SPECIAL OFFER ON WORKING SETS READY FOR RE-SALE

FULL WORKING SETS

50, 550 22"	£1,000
50, 520 22"	£750
10, ITT CVC5/8	£170
10, Decca 20/30 22/30	£150
10, Pye 200 18"	£200
10, Pye Chelseas	£250
10, Pye 222	£200
10, G.E.C. Solid State	£200
10, Thorn 8500	£180
10, Bush Double Chip	£120
10, Jap sets	£250

LARGE OR SMALL ORDERS

RING FOR PRICES

All Prices Exclusive of V.A.T.

UNTESTED T.V.s

SPECIAL 50 SET PRICE ON:

Philips 550 26"	£250
Philips 520 26"	£200
G8 520 22"	£350
Thorn 26"	£150
10 Japanese sets	£180

ALSO VHS VIDEOS!!

Reconditioned Betamax.

Brand new 14" Colour Portables in Unopened Boxes.

G11s, ITT Remote, 9000s.

RING FIRST AND PLACE YOUR ORDER READY FOR COLLECTION.

MANY MORE BARGAINS IN STOCK

BIRMINGHAM – 021-622 1023 or 622 1517

LONDON – 01-807 4090 or 884 1314

COLOURTRADE

MANY YEARS OF SUPPLYING TRADE

WORKING COLOUR TVs

PHILIPS 550	£35.00
BUSH	£25.00
BUSH 2718	£45.00
THORN 22" U-CAP	£35.00
THORN 8-800	£45.00
JVC 20"	£35.00
GEC ... ITT ... DECCA ... etc!	

DISCOUNT FOR QUANTITY

WIDE RANGE OF MAKES AND MODELS
ARRIVING DAILY — ALL WITH GOOD
CABINETS — MANY TO CLEAR FROM
'ONLY' **£5.00**. MIXED LORRY LOAD OF
SETS DELIVERED TO YOUR DOOR
DIRECTLY FROM SOURCE!

TELEPHONE NOW

021-359 0449

COLOURTRADE

**221 Bridge Street West,
Hockley,
Birmingham B19 2YU**

TELETRADERS

Forde Road, Brunel Industrial Estate,
Newton Abbot, Devon
Telephone: (0626) 60154

**The Best Quality Sets Available
Anywhere**

All First Class working order and excellent
cabinets.

Philips G8 550	£40
Philips G11	£85
GEC Solid State	£35
Thorn 3500 Electronic 22"	£35
Thorn 9000	£60
Thorn 8800	£45
Thorn 9800	£55
Thorn 1500 Mono 20" very clean	£6

**Full spares back-up of tubes and panels —
Bulk terms to other wholesalers**

☆ ☆ ☆

THE NO. 1 WHOLESALE IN THE SOUTH

SETS & COMPONENTS

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact **COLES-HARDING & CO**, 103 South Brink, Wisbech, Cambs. 0945 584188. Immediate settlement.

JAPANESE COLOUR TVs. Panasonic, Hitachi, Mitsubishi, Toshiba, Sharp. Fully refurbished. Trade only. J.M. Pearson Television. 0484 863489.

SECOND HAND Colour TV spares and tubes. Most makes. Telephone Southport (0704) 74411. Anytime.

PANELS UNTESTED at giveaway prices. S.a.e. for list. Working G8 & JVC from £40.00. **CAMBER TELEVISION CENTRE**, Lydd Road, Camber, Sussex 0797 225457.

Trent Tubes

31 RADCLIFFE ROAD,
WEST BRIDGFORD, NOTTINGHAM
TEL: (0602) 813329
THE QUALITY REBUILDER

TWO YEAR GUARANTEE FOUR YEAR OPTION EXTRA

ALL Standard delta types (A56-120 - A66-120 etc)

One price £26.50

A51-161 - A51-163

£37.00

A51-510 A56-510 A66-51 A51-570 A56-610 A66-610 etc.
£40.00

A56-540 - A66-540 £49.00 (complete)

560 DZB Z £42.00

MONOS £16.50

1000's of other types available
Japanese types our speciality

Large DISCOUNTS available. Delivery Service.
EVERY Tube ELECTRONICALLY & PICTURE
TESTED before despatch

All prices exchange + VAT

Agent: H. DONNOR, Peterborough, Phone 0733 71809

PANELS

GOOD WORKING
POST PAID NO VAT

Make	Power Supply	Line Panel	T.Base Panel	Decoder D	IF Tripler	Convergence
Thorn 3500	£12.00	£9.50	£6.50	£5.00	£3.00	£4.00
Thorn 8500	£6.00	-	£9.50	£11.00	-	£4.00
GEC S/S	£6.50	£11.00	£6.50	£8.50	£11.00	£4.00
Bush Twin						
Chip	£6.50	£6.50	£6.50	£11.00	£6.50	£4.00
Oecca						
Bradford	£6.50	£6.50	£6.50	£8.50	£6.50	£4.00

TUBES

£29.00

INCLUSIVE, REGUNS TWO YEAR
GUARANTEE, QUANTITY
DISCOUNTS

£14.50

SIX MONTH GUARANTEE
SLIGHTLY USED

A56-120 A56-140 A51-110 A49-191 A47-342 or 343

A44-270-1 A66-120 A67-120 (All 26" add £5)

IN-LINE 51-161 From £35 plus 100's more

Delivery £5 per tube. British Isles.

No need to spend £5 returning old tube
if you buy from us.

U-VIEW TUBES,

29 Warmsworth Road,
Doncaster, Yorkshire DN4 0RP.

Tel: 0302-855017.

Callers ring first: Open every day including Sunday

SATELLITE TV RECEIVER

Receives 4GHz band. Ideal for demonstration terminal in U.K. 100 degree Kelvin LNA. £392 + VAT (+ Carr). LNA/down converter PCB's stocked for the constructor. SAE data.

HUGH COCKS TV SERVICES,

Cripps Corner, Robertsbridge,
Sussex TN32 5RY. Tel. 058083 317.

TELEVISION

No other consumer magazine in the country can reach so effectively those readers who are wholly engaged in the television and affiliated electronic industries. They have a need to know or your products and services.

The prepaid rate for semi display setting £6.30 per single column centimetre (minimum 2.5 cms). Classified advertisements 37p per word

GENERAL TELEVISION TRADE SALES FACTORS

3-5 UNION ST.
DONCASTER

Telephone:
(0302) 68416

Regular weekly supplies of good quality TVs, all with excellent cabinets, we look after our sets, we don't knock them about, as you'll see if you call, suitable for re-sale or rent. Working or off the pile. We're always happy to see you, whether its for one TV or one hundred and one.

MONDAY TO SATURDAY 9 to 5.30

GOOD SETS
GOOD SERVICE
CALL & SEE US YOU
WON'T BE DISAPPOINTED
Special Prices on Philips G8's &
Other Lines

STANDS, LEGS,
SLOTMETERS, PANELS,
TUBES ETC.



PHONE
NOW
(0302) 68416

RANK
SABA
KORTING
THORN
EKCO
ETC.

PHILIPS
PYE, JAPANESE
DECCA, GRUNDIG
GEC, ITT

EXCELLENT MOTORWAY ACCESS FROM MOST PARTS
VIA M1 OR A1
WE'RE ONLY A SHORT DRIVE AWAY

WOODSDALE COMPONENTS

RANK BUSH MURPHY

TRANSFORMERS

Line Output

Z718 (T703A, T706A)

New (Complete) £20.50

Less Focus Module and
Rectifier £10.50

T20, T22 (T705A) £11.00

T26 (T705B) £11.00

Switch Mode

T114A/B £8.00

Genuine RBM Units.

AERIALS

UHF Aerials P & C Wideband 4 Bay

Bowtie (12.5 dB) £20.00

Above with built-in Broadband amp.

(27dB) plus stabilised power

supply £45.00

Prompt Postal Service.
Add 15% VAT to all prices.
DISCOUNT for QUANTITIES.

34 Field End Road, Eastcote,
Pinner, Middlesex. HA5-2QT.
Tel: 01-868 5580.

N. Skehan

Agents Office. Callers by appointment only.

WIZARD DISTRIBUTORS

MANCHESTER

Visit our trade counter and see the huge range of components inc. tubes and video heads. Only minutes from the town centre and motorway routes. Fast friendly service and technical assistance available. Come in and see our trade counter special offers.

Open Monday to Friday 9 am to 4.45 pm
Trade Only

EMPRESS STREET WORKS
Empress Street
Manchester M16 9EN

Tel: 061-872-5438, 061-848-0060

TRADE-TEL

TV DISPOSALS

Tel: 051-709 1734

G8550s from £8.00
Polished & Tested £30.00
UNIT B11A South West
Brunswick Dock
Liverpool L3
Merseyside

SERVICE PAGES

(minimum 12 words), box number 70p extra. All cheques, postal orders etc., to be made payable to Television, and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Dept., Television Room 2612, IPC Magazines Limited, Kings Reach Tower, Stamford Street, London SE1 9LS. (Telephone 01-261 5846).

SCREENPLAY *Bursting with Stock!*

Guaranteed - Complete Sets from £10.00
 Trade Workers from £25.00
 Panels By Post from £3.00
 Mono's from £1.00
 Stands - Aerials - Accessories Etc.


WORKING SETS

Phone us first for quantity, we can give an UNBEATABLE PRICE!!!

OPEN 5 DAYS -

Phone:

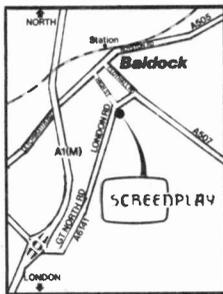Baldock 894905,
 SECTION THREE, UNIT FOUR, SERL COMPLEX,
 LONDON ROAD, BALDOCK, HERTS.



COLOUR TV PANELS Fully Tested & Working

	IF	CDA/ Video	Decoder	LTB	Line Board	Power
GEC 2040	3.50	3.50	4.00	5.00	-	-
DECCA 13/30	3.00	-	7.00	5.00	-	4.00
BUSH A823	4.00*	-	10.00*	5.00*	2.50	4.00
THORN 8/8½	-	-	10.00	5.00	-	5.00
PYE 205	3.00	3.50	5.00	10.00	-	-
THORN 3/3½	5.00	5.00	5.00	5.00	-	10.00
G6	6.00	-	8.00	7.00	15.00	5.00

*Please specify prefix A or Z.

Please add 15% VAT to above prices, then add post + packing.
 Post + Packing: 1 panel £1.50; 2 panels £2.25; 3 panels £3.00 etc.

Hybrid panels do not include valves.

Also a vast selection of modern working and non-working TVs at low prices. Please ring for current stock.

Terms cash with order.

GOLCAR T.V. SERVICES (formerly LAVITE LTD.),

Old C of E School, Church Street, Golcar, Huddersfield. Tel.: 0484 643273

Callers by appointment only.

WETSTED TUBES

PRESENTS AN UNBEATABLE OFFER

£26 ALL DELTAS ONE PRICE

£40 ALL P.I.L. ONE PRICE

* SPECIAL CRT POLISHING SERVICE WHILE U WAIT Only £5

* ALL DELTA SIZES FROM STOCK

* DISCOUNT FOR ORDERS OF 5 CRTs OR OVER

* FREE DELIVERY WITHIN 20 MILE RADIUS OF MAIDSTONE

Ring Now

Maidstone 872400

or visit our factory.

Unit 32, Branbridges Ind Est.
 East Peckham, Kent.

* Agents required in South

Prices do not include VAT

REBUILT COLOUR TUBES

EXAMPLE PRICES DELTA

All sizes up to 22" — £28.00
 26" From — £32.00

All In Line P.I.L. Mono Gaming Machine
 C.R.T.s 560EGB22 56-611-510JKB22

20 AX £40.00

30 AX £48.00

Fast U.K. Delivery

Call or Phone:

RE-LIFE T.V. TUBES

PLANE STREET,
 OLDHAM, LANCs.

061-665 2668

Wholesalers REG in North & South Wales
 Competitive Prices

GRUNDIG, WORKING FROM £40. Reconditioned panels from £4. Remote handsets wanted. Tequipment oscilloscopes. Ochre Mill 0785 814643.

TELEVISION

Trade & Retail supplies of s/h colour & mono TVs. Most makes available, workers or non-workers

SOUTHPARK DISTRIBUTORS

Unit 4 Rubastic Road,
 Brentpark Industrial Estate,
 Southall, Middx. UB2 5LL.
 01-574 4631, Ext 28

A.B.D. TELEVISIONS

Suppliers of colour and mono televisions to the trade.

Workers and non-workers:

Pye Chelsea, Philips, Pye, GEC, Thorn 8500, 8800, 9000 and 9600, Bush T20 and TT22, ITT 600 series, Japanese, Hitachi, Nat. Pan J.V.C.

Many other modern sets by popular manufacturers.

For quotation and prompt service:

Ring Notts (0602) 864627

UNIT 3+3A,

Meadow Trading Est.

Meadow Lane,

Nottingham NG3 3HQ.



- * Britain's most reliable source of quality TVs.
- * Hundreds of working polished TVs.
- * GEC Starline
- * Decca 80
- * Decca 88
- * Decca 100
- * Pye G11
- * Thorn 8800
- * Pye 222 Series

All working and polished.

These are not from major companies. A lot are from hotels and have had very little use.

Excellent reliable sets for rental.

Krystal Marketing Ltd.
 Breedon Cross
 Storage,
 Dele Road, Selly Oak,
 Birmingham B29 6AQ.

Phone 021-471 3023
 Telex 335540-G
 Ask for Les

N.W. ELECTRONICS

25 YEARS SUPPLYING THE TRADE

HUGE STOCKS OF COLOUR TV'S 2000 NOW IN STOCK

ROCK BOTTOM PRICES. ALL MAKES, ALL MODELS.

90% WORKERS (off the pile)

GENUINE REPOSSESSIONS AND EX RENT, NOW IN STOCK!

PYE KT 3, PHILIPS G11, G8, BUSH T20, 22, 718, GEC, 2010, 2201, 2002, 2659, HITACHI, SANYO, PYE 222 THORN 9000, 3500, 8800 ETC.

SPECIAL OFFERS

BUSH 2 chip 20"/22" Exc. CAB Cond. GENUINE CHANGE OVERS **£15 EACH**
(special quotes on bulk orders) . . . Single Chip **£10.**

PHILIPS 26" G8 EXC. COND. 550 model_____	£20 each	BUSH 718 PIL TUBE_____	£28
BUSH 22" REMOTE 718 ONLY_____	£30	BUSH T20 LIKE NEW_____	£60
HITACHI 20" MODEL 190 EXC. CAB_____	£20	in lots of 10_____	£50
THORN 9000 PIL TUBE_____	£35	in lots of 50_____	£45

VHS VIDEO

SHARP 7300, 8300, 9300. FERGUSON 3V28 3V22. SONY BETA.

MONO TV'S £1 each (lots of 25)

BUSH, GEC, PYE, PHILIPS ETC. THORN 1500 **£4**. THORN 1600 **£12** (like new).

REFURBISHED TV'S TO ORDER

PHILIPS G11 **£80** BUSH T20/22 **£70** GEC 2010 **£38**

LATER MODELS PHONE FOR QUOTATION

WHITE GOODS

HOOVER TWINS FROM **£6**. HOTPOINT 1460 FROM **£10**.

AUTOS ALL MAKES FROM **£10**

SPARES! SPARES! TV PANELS

	I.F.	DECODER	LINE O/P	POWER	CONVERG.	VIDEO	FRAME T3
BUSH 2 CHIP	3.00	8.00	6.00	3.00	3.00	—	5.00
3000/3500	2.00	4.00	8.00	8.00	5.00	5.00	6.00
G8	5.00	7.00	14.00	8.00	5.00	—	5.00
	with sound panel						
GEC 2110	10.00	5.00	12.00	6.00	5.00	5.00	5.00
BUSH 718	8.00	15.00	25.00	3.00	5.00	—	15.00
BUSH T20	8.00	15.00	20.00	20.00	5.00	—	15.00

P&P 1 panel £1.50, 2 panels £2.00, 3 panels £2.50 etc. Quick Despatch - C.W.O. please

ALL PRICES PLUS VAT.

CASH ONLY - DELIVERY CAN BE ARRANGED

(0274) 688458 OPEN 6 DAYS A WEEK

Unit 12, Wharfedale Road
M606 Euroway Estate
Bradford

OPEN MON-SAT 9-5.30
Don't forget! We are open
all day Saturday!

TORBAY (TRADE) T.V.

Have now moved to larger premises.
Good quality small screen colour
TVs Chelsea's, 560, 207, 9000, etc.

178 Union Street,
Torquay, Devon.
Tel. (0803) 22767.

THORN 9000 PANELS TESTED & WORKING

TUNER HEAD	£4
TUNER PANEL	£6
DECODER	£15
POWERLINE	£20
FRAME	£15

Prices + VAT. Postage £1.50

GOLCAR T.V. SERVICES

Old C of E School,
Church Street,
Huddersfield, West Yorkshire.

Always hundreds in stock	COUNTY DURHAMS ONLY	All markets catered for
	WHOLESALE	
	UNTESTED	WORKING
G8 520	From £12.00	From £20.00
G8 550	From £12.00	From £30.00
GEC S/S	From £15.00	From £25.00
All Hybrids	From £12.00	From £20.00
Jap	From £20.00	From £30.00

All sets sold as working are fully prepared to
the highest standards and are ready for retail or
rental.

REGUNNED TUBES

Up to 22" Delta	£27.00	2 yr guarantee
Up to 26" Delta	£30.00	"
Pil & Inline	£45.00	"

All tubes are regunned to the highest specifica-
tions. We are the best because we want our
customers to come back.

INTERTEL

Unit 27 Whessoe Road,
Darlington (0325) 486896
Co. Durham.

T.V. SPARES, PANELS AND MANUALS PHILIPS · GRUNDIG

TELEVIEW 01-994 5537
194, Acton Lane, London W.4.

Sandwell T.V. Centre

1000's of T.V.'s at tremendously low prices.
mono's from £1.00. --- colour from £7.00.
WORKING HYBRID £15-
Brunswick Park rd. Wednesbury: off jct. 9. M6.

tel. no.
021502
3016

TELEVISION TUNER REPAIRS

BRITISH, EUROPEAN
JAPANESE ETC.

ELC 1043/05 TUNERS
AS NEW £4.60 inc.

MEN-TU ELECTRONICS LTD.
SALTERNS LANE,
FAREHAM, HANTS.

Tel: 0329-235116

WORKING CTV's

The Best & Cheapest in Lancashire

I.E. Decca 18" to 26"	£24.00
GEC 20" to 26"	£30.00
Philips G8 22" to 26"	£25.00
Bush 20" to 26" 2 chip	£18.50

All sets are tested & working

Many more makes & types available.
Working mono's only £3.50. Non work-
ers available.

Phone: John Powney
at Kirkham, near Preston
(0772) 683392.

Thorn 3000/3500
Thorn 9000
UNIVERSAL
1 year guarantee

TRIPLERS
£4.50 inc. p&p

The UNIVERSAL TRIPLER can be used in most
G.E.C., I.T.T., Pye, Rank, Decca & Continental
sets.

WING ELECTRONICS

15 Waylands, off Tudor Rd, Hayes End, Middlesex

OBSOLETE NEW BOXED VALVES 50 for £10.
Retiring engineer. Plus postage. Details Box TV 188.

COLOUR BAR GENERATOR

Pal Colour Generator with 11 patterns plus sound. Grey
scale, Colour Bars, Red, Green & Blue Raster, Cross-
hatch, Dots, Chequer Board, Black Raster, White Raster,
Half Black & White £75.90.



Line Transformer Tester	£11.50
B/W Generator, Crosshatch, Peak White, Dots, Half Black & White and Grey Scale	£18.50
In Circuit Transistor Tester	£14.25
Capacitance Meter measures 10pF to 1µF complete with moving coil meter	£14.75

S.A.E. for details. - Prices include P&P & VAT.

C.M.J. ELECTRONICS

Unit 8, 16 Union Mill Street, Horseley Fields,
Wolverhampton WV1 3DW.
Tel: (0902) 871563

Thorn Colour TVs - Most models

Decca 1051/2 (100 series)

Philips 660 etc (G11) 550 (G8 Series 05)

ASSORTED GEC/BUSH/PHILIPS/JAP etc

Working or guaranteed untested basis

Competitive prices/good cabinets/top quality

If your standards are as high as ours, we want to deal with
you - regularly!

REPOSSESSED TV CENTRES LTD 061-273 2854

335-341 Stockport Rd, Longsight, Manchester 13.

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Television for

insertions. I enclose Cheque/P.O. for £

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd and made payable to Television)

CAT. HEADING

Send to: Classified Advertisement Dept

NAME

TELEVISION

Classified Advertisement Dept, Room 2612,
King's Reach Tower, Stamford Street,
London SE1 9LS. Telephone 01-261 8846.

ADDRESS

Rate
37p per word, minimum 12 words. Box No. 70p extra.

Company registered in England. Registered No. 53626. Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS.

10/84

IRISH DEALERS

Most brand names of UHF - VHF
Colour & B/W working.

Clean sets at very keen prices.
Delivery arranged.

Quantity discount.

(SPECIALISTS IN EXPORT ORDERS)

TV TRADE SALES

E.D.I. House,
Kylemore Park West,
Dublin 10.
Tel. 01.264139 Ext 11.

BRAND NEW Monochrome 20ins 110 degrees CRT's
£10 each. 25% off Ten's. 01-897 2606 anytime.

TELEVISION

RANK BUSH MURPHY TV PANELS

Repair, exchange, sales service, prompt efficient service. All chassis covered. New PCB available to replace burnt T20 line Panel. We charge only £16 to repair switch mode power supply. Ring Monday to Saturday and ask for Mr. Kheli.

T. K. Panels Service,
31 Bronte Paths, Stevenage, SG2 0PG.
Tel. (0438) 61567.

EAST ANGLIA SUPPLIES

Fully working colour TVs from £25.00 plus VAT straight from our retail shelves. Most makes are available and small regular orders are welcome. Personal services guaranteed and if we can help you boost your rental or retail trade we would be delighted.

Free delivery available
(only petrol charged).

Contact John, Dave or Steve at
Barry T.V. Services

on Cambridge 69215
or Ely 61462

ELECTRON GUNS OF THE HIGHEST QUALITY

Available in many types and variations for domestic T.V., camera tubes, industrial, military, scientific research applications, and electron microscopes. Unmatched for quality, we have 26 years experience in the T.V. tube industry. You can have the benefit of this by contacting:

ELECTRON EMISSION PRODUCTS LTD.,
Strangford Road, Seaham,
County Durham SR7 8QE.

Telephone: 0783 819312

Telex: 537681/2/3 ELECTRON

TRADE COLOUR TV's ALWAYS 200 IN STOCK

Colour from £5.00 Mono £2.00

BRAND NEW VIDEOS
V2022 and V2023
VHS and BETA

Just in
20" + 22" GEC

Boxed with stand £85.00

ALL STOCK CHANGES WEEKLY

(0934) 514047/512792/27560

P&R SUPPLIES, Unit 5,
Worle Industrial Estate,
Weston-Super-Mare. Exit 21 M5.

STARLITE ELECTRONICS

NOW MOVED TO:
WILLOWS FARM,
A13 RAINHAM, ESSEX.
Rainham 23225 also
Hornchurch 50238.

- TV TUBES -

2 year guarantee
Most types available

Japanese including Sony

Ex-Rental TVs from£15.00
Untested Panels.....£4.00

CANVEY COLOUR TUBES

Unit 3, Charfleets House, Charfleets Industrial Estate, Canvey Island, Essex.
Tel: Canvey Island (0268) 690577

CURRENT PRICE LIST

DELTA TUBE TYPE FROM £27.50 to £31.50

INLINE TUBE TYPE FROM £35.00

MONO TYPES P.O.A.

ALL PRICES EXCLUSIVE OF VAT.

All Tubes Guaranteed for 2 YEARS and Reprocessed
to Original Manufacturers Specifications.

ELECTRONIC SUPPLIES

MOVING WAREHOUSE LARGE STOCKS OF COMPONENTS
TO CLEAR

Record changers 240v From £4.85 + P&P £3.00
Transcription decks 12v or 240v From £5.50 + P&P £3.00
Pair speakers H13W8J04 Teak From £5.00 + P&P £3.00
Pair empty speaker cabinets H11W7J05 £2.50 + P&P £2.00
Service bench pack mixed components, nuts, bolts, washers,
leads, bulbs, magnifier plugs etc. £5.00 + P&P £1.80

Send 17p stamp for Catalogue to:

18 LEUCHA ROAD,
LONDON WALTHAMSTOW E17 or
Phone 01-821 3912 after 6.30 evenings

Trade enquiries for bulk purchase welcome

PL802 Valve New£5.00
PL802 Solid State Plug in replacement Module£4.50
BT106 Thyristor£0.75 BU126 Transistor£0.75
2SC643AY Transistor £0.70 R2008B Transistor£0.80
R2010B Transistor£0.80 SL901B Integrated Circuit £4.00
VAT INC. ADD £0.50 P&P

ACORD ELECTRONICS LTD
UNIT 2-3 ENTERPRISE PARK
SLYFIELD, GUILDFORD GU1 1RB

MULTISTANDARD Colour Television. LUXOR
VHF/UHF TV/monitors to most standards, including
PAL/L/SECAM/L (UK/French) option. 20", 22" & 26"
from £280. ex VAT. PORTATEL CONVERSIONS
LTD., 25 Sunbury Cross Centre, Sunbury, Middlesex.
Tel. 09327 88972.

AERIALS

PARABOLIC DISH accurate 5 foot spun aluminium
with mounts. £225 or near offer. Phone Alcester (0789)
764040.

CLEARVIEW AERIALS

Clearview have pleasure in announcing a full and
comprehensive range of signal amplification equip-
ment. For example: low noise electronically remote
controlled masthead pre-amp 1.6db noise. CH. 17-69.
Set side amplifiers, distribution amplifiers, notch filters
4 in 1 or 2 in 1 etc. Combiners for 2 UHF aerials 3db
gain or 4 db gain. Trade and retail.

Send large SAE for our comprehensive catalogue

CLEARVIEW AERIALS,
173 Kings Road,
Kingston Upon Thames, Surrey.

AERIAL BOOSTERS

B45H/G-UHF TV next to the set fitting, gain about
20db, PP3 battery or 8V to 14V/working. Price £8.70.
P&P 30p.

UHF TV BOOSTER MODULE. PCB ready made up to
cover the complete UHF TV band. Gain 10db, noise
1.9db. 8V to 14V/W. Price £2.50. P&P 30p.

AMPLIFIED SET TOP AERIALS. Trebles the gain,
fully portable, price includes batteries. Price £9.70.
P&P 50p.

CAPACITOR PACKS. Mixed C280 & Electrolytics,
values from .01uf to 500uf. Price per pack of 150
capacitors £2.00. P&P 50p.

ELECTRONIC MAILORDER,
62 Bridge Street, Ramsbottom,
Lancashire, BLO 9AG.
Tel: Ramsbottom (070 682) 3036.

S.A.E. for leaflets. Access/Visa Welcome.

EQUIPMENT FOR SALE

★ VIDEO FADER UNIT ★

- ★ SUITABLE FOR ALL VIDEO TAPE FORMATS
- ★ PRODUCE YOUR OWN HOME VIDEO
- ★ ALLOWS TAPE ASSEMBLY AT BLACK LEVEL
- ★ FULL COLOUR T.V. BANDWIDTH
- ★ MAINTAINS FULL SYNCHRONISM
- ★ OPERATES ON 12 VOLTS DC (P.S.U. AVAILABLE IF REQUIRED)
- ★ UNIQUE PRESENTATION
- ★ FULLY GUARANTEED
- ★ ONLY £59.95 INCLUDING P&P or send large S.A.E. for full spec
- ★ FIRST OF AN EXCITING RANGE OF NEW PRODUCTS AVAILABLE EXCLUSIVELY FROM:

LEAP PRODUCTS
5A London Road,
Loughton, Milton Keynes MK8 0AE
Please allow up to 28 days for delivery

SERVICE PAGES

SERVICE SHEETS

TELEVISION SERVICE SHEET SPECIALISTS

Thousands of British, European, and Japanese models in stock.

Colour £2.00 Mono £1.50 (post free)

Manual prices on request.

Send stamped envelope for free catalogue and enquiries

SANDHURST TV SERVICES (MAIL ORDER)

49C Yorktown Road, Sandhurst, Camberley, Surrey GU17 7AG

30,000 SERVICE SHEETS IN STOCK ALSO COLOUR MANUALS AVAILABLE

TV Sheets, Black and White, also Radiograms, Record Players, Music Centres. Japanese models in stock. Curcuit diagrams only. Also Tape Recorders etc etc., ALL AT £3. Please forward s.a.e. Send cheque or P.O.

C. CARANNA, 71 BEAUFORT PARK, LONDON NW11 6BX.

TECHNICAL INFO SERVICES - 76 Church St - Larkhall - Lanarks

(By return of post service in most cases.)

Sole suppliers of the Unique Comprehensive T.V. Practical Course and The Complete Radio Repair and Servicing Course **ONLY £9.50 each.**

We stock every published service sheet plus produce more ourselves. All service sheets are top quality, full-size sheets supplied in complete sets. £3.50 + I.s.a.e. for CTV or Music Centres - £2.50 + I.s.a.e. any others.

WORLD'S LARGEST COLLECTION SERVICE MANUALS

Can be seen at our premises any evening 4-6pm. Manuals from 1930 to the latest issue. Col + Mono TVs, Videos, Audio, Com + Test Eqpt. in stock for immediate despatch - Over 400 diff. CTV - Over 200 diff video!

Sample CTV prices: G8 or Pye 697 or A823 or Autovox early (poor copy) at £7.50 each

Most manuals are unobtainable anywhere else.

WORLD'S BIGGEST PUBLISHER OF TV/VIDEO REPAIR MANUALS

British CTV Integrated Repair System (3/5) **£85**
Foreign CTV Integrated Repair System (2/4) **£60**
Mono TV Integrated Repair System (2/6) **£70**
Video Integrated Repair System (2/10) **£49**

First figure for giant collections of circuits/layouts in binders. 2nd figure for number of repair manuals. Other items not shown.

The Complete Integrated TV Repair System - covering TVs colour & mono, British & foreign, circuits, layouts, repair data plus much servicing data. Around £300-worth **ONLY £220**

Free 50p magazine with pricelists, etc. to every query or order - please enclose s.a.e.

FOR FAST QUOTES - PHONE 0698 883334

BELL'S TELEVISION SERVICES for service sheets on Radio, TV, etc. £1.50 plus S.A.E. Service manuals on colour TV and Video Recorders, prices on request. S.A.E. with enquiries to B.T.S., 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 55885.

***** SERVICE PAGES SERVICE PAGES

This space could cost you as little as £4.44 (i.e. 12 words at 37p). Complete the coupon or ring 01-261 5846 NOW!

SERVICE PAGES SERVICE PAGES

FOR SALE

BEST VALUE IN SECONDHAND TV'S SETS CLEANED AND SOAK TESTED

DISCOUNT FOR VAN LOAD DIRECT FROM SOURCES

MAKES

Philips G8's, 2 chip Bush/Murphy
Thorn 3000, 3500
Thorn 8800, 9000, 9600, touch tune sets etc.
Bush 720's, Philips G11, ITT CVC 35
Pye 18", 22"
GEC Solid State, all types
Japanese, Hitachi, National Panasonic
ITT CVC 5/8/9
Decca Broadford
GEC/Pye Hybrid

COMPLETE NON-WORKERS

£14
£13
£25
£50
£16
£16
£15
£14
£10
£5

WORKING

£25
£22
£40
£70
£26
£28
£28
£28
£20
£10

Mono in batches of 20 at £2.00
SPECIAL OFFER! Thorn 3500 26" £5
Philips G8's 26" £5 Pye 205 26" £4

Other makes available on request. Discount for quantity.

* Tubes tested all sizes at £8.00 each

* Good quality stands at £2.00 each

MAKES	POWER		LINE		TIBASE		VIDEO		DECODER		CONVERG		IF		TRIPLER WORKING
	W	N/W	W	N/W	W	N/W	W	N/W	W	N/W	W	N/W	W	N/W	
Thorn 3500	6	3	6	3	4	1.50	4	1.50	3	1.50	4	1.50	4	1.50	2.50
Philips G8	6	2.50	12	6	6	3			6	3	6	4	4	2	2.50
Pye S/S	8	6	15	10	5	3			10	5	6	3	10	5	3.00
GEC S/S	6	4	11	8	5	3	5	3	5	3	4	3	10	8	3.00
Decca (H)	6	3			6	3			8	4	4	2	3	1	2.50
Pye (H)	8	4	8	4	4	2			6	3	4	2	3	1.50	2.50
GEC (H)	6	3			6	3			6	3	4	2	3	1	2.50

* W - Working fully tested panel

* Express delivery, subject to availability

* N/W - Non-working panel

* Add 15% VAT P&P 1 panel 1.50, 2 panels 2.00, 3 panels 2.50 etc.

ELASTIC YARN

SABA CO LTD., Elastic Yarn Buildings, Derby Road, Sandiacre, Notts. Tel: (0602) 397555.

FOR SALE CONTINUED

THANDAR SC110 10MHz Scope a.c. Adaptor and manual. £100 + post. Tel. 021 459 9011.

TOP QUALITY TELEVISIONS SCOTTISH TRADERS

★ Wide range of CTV's in good working order from £25 e.g. Thorn 3500, 8500, 8800, Bush, Philips G8, GEC S/S CTV etc.

★ Plenty of working and complete non-working sets at competitive prices.

★ Ready to sell or to rent.

★ Special Offer Bush quantity of over 10 at £5 each.

For further information telephone

M. S. VISION

72 Robertson Street

Glasgow.

Telephone: (041) 221-2146.

PATTERN GENERATOR PROGRAM for Spectrum 16/48K. Colour Bars, Crosshatch, Dots, Chequer Board, Red, Green, Blue, Black, White Rasters. Send £3.50 for tape to GW TV'S, 1 Eachard Road, Cambridge CB3 0HZ.

TELEVISION 1969 TO DATE. Various Service Manuals, bits/pieces. Reasonable offer secures. Phone Portscatho 684 evenings.

TELEMECHANICS TELEMATX 2352 Projection TV early 1950's, any offers. Phone 042129 2394.

BOOKS AND PUBLICATIONS

FULL SIZE TOP QUALITY service sheets £2.50 + I.s.a.e. CTV/Music Centres £3.50 + I.s.a.e. Repair data almost any named TV/Video £10.50 inc. circuits. I.s.a.e. brings any quite free magazine/pricelists. TIST, 76 Churches, Larkhall, Lanarkshire. Tel. 0698 883334.

"RADIO AND TELEVISION SERVICING" books, new editions for the last 6 years always in stock. Prices on request. BELLS TELEVISION SERVICES, 190 Kings Road, Harrogate, N. Yorkshire. Tel. 0423 55885.

RADIO AND TELEVISION SERVICING BOOKS. New 74/75 £15. 76/77, 77/78, 78/79, 79/80, 80/81, 81/82, 82/83, 83/84 £22.50 each. Free delivery. U-VIEW, 29, Warmsworth Road, Doncaster. 0302 855017. Callers ring first.

VIDEO

VIDEO RECORDERS

VHS 125 Betamax £100.
Colour TVs £12.50.

SMITH'S ELECTRONICS

43 Park Parade, Harlesden, London NW10.
01-965 1230 01-961 3997

ARE YOU A TV ENGINEER WHO WANTS TO KNOW ABOUT VIDEO RECORDERS?

THEN YOU NEED

"DOMESTIC VIDEO CASSETTE
RECORDERS A SERVICING GUIDE"
by S. R. BEECHING

Available for only £15.50 inc. p&p

From: **NEWARK VIDEO CENTRE,**
108 London Rd., Balderton, Newark, Notts.
Tel: 0636 71475 ACCESS OR VISA

***** SERVICE PAGES SERVICE PAGES

PLEASE MENTION TELEVISION WHEN REPLYING TO ADVERTISEMENTS.

SERVICE PAGES SERVICE PAGES

MISCELLANEOUS

BURGLAR ALARM EQUIPMENT. Latest discount catalogue out now. Phone C.W.A.S. ALARM 0274 731532.

ELECTRON GUNS

QUALITY AMERICAN Electron Guns TV & VDU etc. Technical advice. APEX ELECTRONICS 0602 813329. Sole UK & European distributor.

WANTED

WANTED. We will clear any amount of colour sets from small Rental Companies, Hotels, etc. Please phone P & R Domestic Electrical Clearance Supplies, Weston Super Mare (0934) 514047.

SITS VACANT

RADIO, TV, ELECTRONIC SERVICING

Don't do it—teach it!

You had a good trade training, you've spent the last five or more years working and gaining practical experience, where do you go from here?

One answer is, down to the Skillcentre in Deptford, South London where we'll train you to teach your skills to others. It's a fascinating and rewarding

opportunity with the satisfaction of helping others and an inclusive salary which starts at £7,762 rising to £9,210.

We may even be able to help with relocation expenses if you need to move home.

It's easy to find out more - **just phone Jill Whitehead at the Manpower Services Commission on 01-836 1213 extension 211.**



Manpower Services Commission

07/STA/8

Helping you to help yourself

VHS VCR's WANTED

**QUANTITIES PURCHASED
WOLVERHAMPTON (0902 405103)**

When replying to Television Classified Advertisements please ensure:

- (A) That you have clearly stated your requirements.
- (B) That you have enclosed the right remittance.
- (C) That your name and address is written in block capitals, and
- (D) That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

**EMCO - EUROSONIC - GRUNDIG - TELETON + ALL BRITISH MAKES
ETC. ETC. ● ALL SPARES READILY AVAILABLE ●**

IMMEDIATE CREDIT AVAILABLE — TRADE ONLY

If you are a trader simply phone for the part you require and we will send it - no quibble - no hold up for status check. Satisfy us over the phone that you are a trader and we will supply almost any TV component by return "off the shelf". e.g. LOPTX - EHT trays - droppers - OSC coils - switches - cans - smoothers - I.C.'s, etc. etc.

**YOU CAN BE 95% SURE WE CAN SUPPLY ANY
TV COMPONENT BY RETURN
IF YOU NEED SPARES FAST - RING NOW!**

ACCESS AND BARCLAYCARD ACCEPTED.

Applies to U.K. only.

TELEPART (W'TON)

**32 TEMPLE STREET,
WOLVERHAMPTON (0902) 773122**

COLOUR TELEVISIONS

THORN 9000, 9200, 9600 Remote Control

PYE 420/450, G11

MANY OTHER TYPES

Working panels and tubes available.

REBUILT TUBES

Delta - In Line - PIL.

SOUTHBRIDGE TV CENTRE

120, Selhurst Rd., London, S.E.25.

Tel: 01-771 3535.

Ex-Rental Colour TVs

PHILIPS 26" - 520 from £4
26" - 550 from £8
22" - 520 from £8
22" - 550 from £12
Van loads direct from source

All makes and models many working!
Inc. Thorn 8800/9000, Pye 222, GEC 2147

For price list Tel **K.L.W. Ltd**

SOUTH

Francis 0582 24177

17 West Side Centre

LUTON

NORTH

Pauline 0274 665670

Thornbury

BRADFORD

TEL-X BLACKBURN

FOR THE VERY BEST IN
TELEVISION DISPOSALS

Decca Thorn Pye Bush
Philips ITT GEC + Remotes

☆ ☆ ☆ ☆ ☆ ☆ ☆ ☆

HUNDREDS TO CHOOSE FROM
WORKERS FROM **£25.00**
Off the Pile from **£ 8.00**

☆ ☆ ☆ ☆ ☆ ☆ ☆ ☆

DELIVERIES ARRANGED ON QUANTITY

TEL-X BLACKBURN

Unit P3, Roe Lee Industrial Estate,
Whalley New Road,
Blackburn, Lancs.

Tel: 0254 679984

1,000 EX-RENTAL COLOUR TV's AVAILABLE

Philips 550's	£18	Philips 520's	£14
Pye Chelsea Series	£15	Pye 725	£15
GEC s/state	£15	Japanese	£18
ITT Hybrid	£14	Decca Bradfords	£12

Mono (single standard) **£2**
Philips 1700 VCR's **£20**
Various Beta VCR's **£50**
All above subject to V.A.T.

Free delivery London area

★ **SPECIAL** ★

MIXED LOADS DELIVERED DIRECT FROM SOURCE
UNTESTED AND INCLUDING WORKERS **£15** + V.A.T.

ALSO STANDS, PANELS, TESTED TUBES

SOUTH LONDON TELEVISION

Mission Hall, Southey Road,
London SW19.

Telephone: 01-543 5437

If an
advertisement
is wrong
we're here to
put it right.

If you see an advertisement
in the press, in print, on
posters or in the cinema
which you find unacceptable,
write to us at the address
below.

The Advertising ✓
Standards Authority.

ASA Ltd, Dept 3
Brook House, Torrington Place,
London WC1E 7HN

LONDON'S LARGEST TELEVISION WHOLESALE...

with over 4½ thousand sq. feet.

"TELEMANN"

8-10 RHODA STREET,
(Off Bethnal Green Road)
LONDON E.2. FREE CAR PARK
TEL: 01-739 2707

ALL MAKES IN STOCK AND GUARANTEED
COMPLETE

The only wholesaler with a
guaranteed single price. If the sets
work or not our price is the same!
Free delivery to the London area.

**Telephone 01-739 2707 –
NOW!**

Philips VCR 1700 with new boxed
1½ hour cassette and mains lead
£45. Single standard mono's £3.


PHILIPS 22" (Model 520) Parcel of ten **£15**
PHILIPS 22" (Piano Key 550) Parcel of ten **£20**
JAPANESE MODELS 18"-20" **£30**

FREE DELIVERY TO THE LONDON AREA!

DISPLAY ELECTRONICS

UNIT 4, SWAN WHARF,
WATERLOO ROAD,
UXBRIDGE, MIDDLESEX.
UXBRIDGE 55800

Your Accessible Regunner

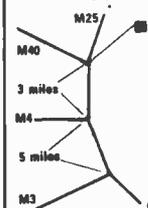

UXBRIDGE

Constructional Work on the
Poyle/Uxbridge section of
the M25 is now in progress
and when completed we
shall be less than 10 minutes
from: M3/M25 junction 2/12
M4/M25 junction 4/14
M40/M25 junction 1/15

1984 PRICE LIST

Delta types

90° up to 19"	£33
90° up to 22"	£36
90° up to 26"	£39
110° up to 22"	£42
110° up to 26"	£45

In-Line types

Up to 22"	£46*
Up to 26"	£49*

*Multipole 30AX ADD £6.

'Specials' may have a gun surcharge

QUALITY CHECK LIST

- ☆ BRAND NEW GUNS
- ☆ HOT PUMPED
- ☆ RF BOMBED
- ☆ PULSE FLASHED
- ☆ EMISSION STABILISED

REGUNNERS SINCE THE '60s
TO MAJOR AIRLINES, M.O.D., UNIVERSITIES,
INDUSTRY AND OF COURSE TO THE TV
TRADE IN GENERAL

SENDZ COMPONENTS

TO ORDER SEE BACK PAGE

Thorn Spares	BY 237	5p
9000 Frame panel	BY 254	10p
9000 Cyclops panel	BY 255	30p
8000/8500 timebase panel	BY 298	10p
8800 convergence panel	BY 299	10p
8500 convergence panel	BY 406	8p
4000 Chroma	BY 527	20p
4000 Power supply	BY 407a	10p
1600 Mains lead, switch	BY 602	10p
3500 6 push button + cable form	F 247	10p
1.50	XK 3102	50p
T605 1vNPN T066 80v/6A	XK 3123	50p
9000 Sound output panel	Hiachi 2A/1500V metal case wire end	20p
3500 Focus unit		
3500 Mains Trans		
3500 2amp thermal cutout		
3500 IF panel		
3500 Frame panel		
3500 Line panel		
3500 A1 Diode		
Export 3500 IF panel		
IC board with set of SN74LS		
4000 Tube base		
3500 A1 pots		
Beam limiter panel		
3500 Power panel with Y969		
3 Way regulated adaptor 240V 6V/5.9V/300mA		
Rank/Toshiba preh unit 0354		
2 banks of 3 PB unit, Pye 731		
4 Push button unit preh		
6 Push button VHF/UHF for v/cap. GEC-Decca type		
7 Push button for CVC5 ITT		
KT3 12 Push button unit		
KT3 (Export) 12 P.B.U		
6 Push button Unit Thorn		
6 Push button unit for GEC 2040 and ELC 1043/05		
Hearing aid unit		
6 Push button unit PYE 713		
7 Lamps for P.B./Unit		
Mains Droppers		
G8 2R2+68R		
G8 47R 15 watt		
Pye 731 3+56+27R		
Pye 3R5/15R/45R		
Thorn 50/17/1K5		
120/20/20/48/117		
270/10/6 for Thorn 4000		
18/320/70/39		
Thorn 50-40R-1K5		
Ae Socket & Lead		
GEC, ITT, Philips, Pye		
7x3 Thorn		
Rank Toshiba Tube Bases		
Speakers		
6x4 G11	25 ohm	70p
5 1/2x2 1/2	3 ohm	1.00
5x3	80 ohm	70p
5x3	50 ohm	50p
5x3	35 ohm	70p
6x4	15 ohm	1.00
7x3	70 ohm	1.00
5x3	8 ohm	70p
7x3	16 ohm	1.00
5" dia	16 ohm	1.00
5" dia	8 ohm	1.50
6 1/2" dia	4 ohm	1.50
6 1/2" dia	3 ohm	1.50
2 1/2" dia	8 ohm	75p
3" dia	8 ohm	75p
4 1/2" sq.	15 ohm	75p
KT3 speaker		75p
3" dia	15 ohm	30p
K30		
OF-550		10p
OF-513		10p
Diodes		
BY 127		10p
BY 133		10p
BY 134		10p
BY 164		50p
BY 176		25p
BY 179		40p
BY 184		25p
BY 187		10p
BY 190		40p
BY 196		10p
BY 198		10p
BY 204/4		8p
BY 206		8p
BY 208/800		8p
BY 210/400		5p
BY 210/800		10p
BY 223		60p
BY 224/600: 4.8A/600v bridge		50p
BY 226		15p
BY 227		15p
BY 228		20p
BY 229/400		30p
International Rectifier EHT Diodes		
6A/600V Stud Diodes		20p
6A/1000V Stud Diodes		20p

Thorn Mains Isolator unit for 70-80U. Ex-speaker	£2	150/3500	10p
NEW GEC 20AX Power Supply Switch Mode	£12.00	1800/4KV	5p
Complete new GEC portable chassis M1201H/M1501H with P.B.U./v.cap/LOPTI	£10	4.7m/5KV	10p
Field + Jungle panel for GEC 3133/3135	£1.50	170/8KV	10p
GEC 2110 line panel with transformer	£7.00	180/8KV	10p
GEC 2110 tuner unit + IF Panel	£12.00	210/8KV	10p
Pye/Chelsea Line on panel	£12.00	210/10KV	10p
Pye 713 IF panel and tuner	£12.00	210/12KV	10p
Pye 713 Chroma	£7.00	1000/12KV	10p
Pye/Chelsea Timebase panel with LOPTI	£10.00	1200/12KV	10p
Pye 731 Frame Panel	£5.00		
Pye 731 Convergence Panel	£5.00		
Pye 731 line O/P panel with transformer + tripler	£12.00		
Pye 731 Chroma	£10.00		
Pye 731 IF panel + tuner	£10.00		
Pye 607/205 Line panel with transformer	£10.00		
Pye CDA/205 panel	£6.00		
GEC portable chassis + LOPTI 2114 New	£4.00		
Thorn 1613/1713 chassis	9.75		
Hills 520 multimeter + case. 20,000V/volt, fuse diode protected + logic test facility. 10meg/1200 volt	£19.50		
NEW MULLARD TELETEX			
Decoder Panel (VM6230)	£15.00		
Panel 6101	£15.00		
Panel 6330	£15.00		
G8 Tuner Unit + Panel	£6.00		
G8 Convergence Panel (late type)	£12.00		
G8 Line O/P Panel	£12.00		
G8 Power Supply	£6.00		
G8 6 Pinning P/B.U	£8.00		
G8 IF & Chroma	£12.00		
G8 Chroma	£6.00		
G11 IF Detector	£3.00		
G11 Selector gain module	£3		
Complete CVC 825 Chassis (both panels)	£40.00		
AEC V/Cap Resistor Unit UHF with IC SAS660 SAS670	£3.00		
Z714 RANK IF Panels 6MHz 1 LC	£3.00		
SL437F	£3.00		
Z909B RANK IF Panels	£3.00		
Export 5.5MHz 2 I.C.'s	£2.50		
TBA1205B TCA2705Q	£2.50		
Z743 RANK IF Panel	£2.50		
Export 5.5MHz 3 I.C.'s	£2.50		
TBA750+SC9504P+SC9503P	£1.50		
Pye G11 Front panel with transducer, pots, tuner pots, 6 pb switch + lead	£5.00		
GEC V/cap VHF/UHF tuner and IF + sound O/P PC 706B3	£12.00		
GEC Line O/P PC 659B3	£6.00		
GEC Power Supply (Export)	£10.00		
G11 dynamic correction panel	£6		
CVC 20 Front panel with sliders + mains input panel	£4		
CVC 40 PUSH BUTTON ASSY with sliders: complete with lamp assy + pots	£14		
CVC 5 Mains on/off + 5 pots	£2		
Universal Focus. Fits Pye, Thorn and Decca Units.	£3.00		
Large Type	75p		
Decca Small	75p		
KT3 Focus Unit	75p		
K30 Focus Pot	75p		
CVC 32 Focus Unit	25p		
Focus Rod	25p		
G11 focus	£2.00		
ITT Small for use with Split Diode	50p		
TV11	50p		
Remo TV12SP	50p		
TV13	50p		
TV14	50p		
TV18	60p		
TV20	£1.00		
TV45	50p		
Thorn 14/1500 rec stick	5p		
16 Button Key Pad 1 to 0 + * + # + 4 blank (Cherry)	£3.00		
Condensers			
470/16	6p		
1500/16	20p		
3300/16	20p		
10000/16	25p		
15000/16	50p		
3300/18	20p		
47/25	5p		
470/25	5p		
680/25	5p		
1000/25 Radial	10p		
1500/25	10p		
3300/25	20p		
4700/25	25p		
5000/25	25p		
3500/30	25p		
470/35	6p		
2200/35	25p		
100/40	5p		
220/40	5p		
400/40	20p		
1250/40	20p		
1500/40	20p		
2500/40	25p		
2000/50	20p		
1250/50	25p		
2000/50	25p		
3000/50	25p		
3300/50	25p		
Infra Red and Ultrasonic G11 Teletext Decoder Panel	£30		
RANK & ITT Mains Remote On-Off Switch (720R)	£1.50		
RANK & ITT Mains Remote Switch 2865 ohm	£1.50		
RANK & ITT Remote Switch 2800 ohm	£1.50		
G11 Mains Switch	50p		
4 amp Mains Switch	25p		
GEC Mains Switch 4 amp	30p		
KT3 Mains Switch	£1.00		
THORN Rotary Mains Switch	50p		
G8 Mains Switch	75p		
Thyristor 600/4 amp C106/2	24p		
G11 Preh Red LED P/Buton for C.H. Change	20p		
RANK TOSHIBA Transducers TPC-2011	50p		
CVC 5 Mains on/off	£2.00		
+250K+100K+500K+50K+500K Pot on Panel	£12.00		
Thorn 12 or 24 volt battery convertor for portable colour T/V	Post £1		
TELETEX DECODER			
I.C. SAA 5051	£1.00		
I.C. SAA 5042	£1.00		
I.C. SAA 5030	£1.00		
I.C. SAA 5020 etc.	£18.00		
DISPLAYS			
4040 Clock	£1		
7seg Red LED	50p		
2 digit LED 8.8	50p		
2 digit LED ±1.8 with panel +	£1.00		
MCL4511	£1.50		
4700/63	10p		
250/64	10p		
3300/70	50p		
1/100	5p		
1/100 x 10	30p		
22/100	10p		
4.7M/100	5p		
470/100	70p		
2000/100	75p		
470/100	10p		
47/160	50p		
800/160	50p		
1/250 Pulse	10p		
G11 0.47/250	10p		
2.2 250v	10p		
3n3/250 A.C.	20p		
33/250P	20p		
39/250V	25p		
4n7/250 tested 5KV	15p		
91/250	35p		
91/400	30p		
22/250	15p		
47/250	10p		
100/250	20p		
G11 470/250V	£1.75		
GEC600/250	60p		
700/250	£1		
800/250	£1		
32/300	20p		
4/350	5p		
8/350	8p		
12/300	10p		
4.7M/350v	25p		
16/350	25p		
33/350	10p		
50/350	10p		
220/350	30p		
300/350	40p		
400/350	50p		
10/375	10p		
22/375	15p		
220/385	75p		
330/385 CVC 820HT	60p		
0.1/400	15p		
KT3 E/W .39/400	20p		
.56K/400v	20p		
470p/400	10p		
22/400	10p		
8/400	15p		
33/400	20p		
400/400	40p		
394K/400V	25p		
220/450	40p		
47/500	25p		
0.1/600	15p		
.047/600	15p		
0.047/1000	10p		
0.01/1000	10p		
0.1/1000	10p		
15/1000	20p		
47/250V A.C.	10p		
.001K/1250	10p		
0.0047/1500	10p		
.005/1500	10p		
.0105/1500	10p		
1n8/1500	15p		
2n0/1500	10p		
2n2/1500	15p		
G11.11000/1500	15p		
0.1/1600	15p		
G11.8200/2KV	15p		
0.1/2KV	20p		
10n/2KV	15p		
3n9/2KV	15p		
0.0015/2KV	10p		
5n2/2KV	10p		
6n2/2KV	15p		
2n0/2KV	15p		
2n2/2KV	15p		
7500p/2KV	10p		
4n7/2KV	15p		
8n2/2KV	15p		
0.0082/2500	15p		
Multi-Caps			
470/250 G11	10 for £15		
Thorn 3500	£1.75		

