


NOVEMBER 1984

Australia \$1.80, New Zealand \$2.20, Malaysia \$5.50 **£1.00**

TELEVISION

SERVICING·PROJECTS·VIDEO·DEVELOPMENTS

EXTRA PAGES + DATA CARD

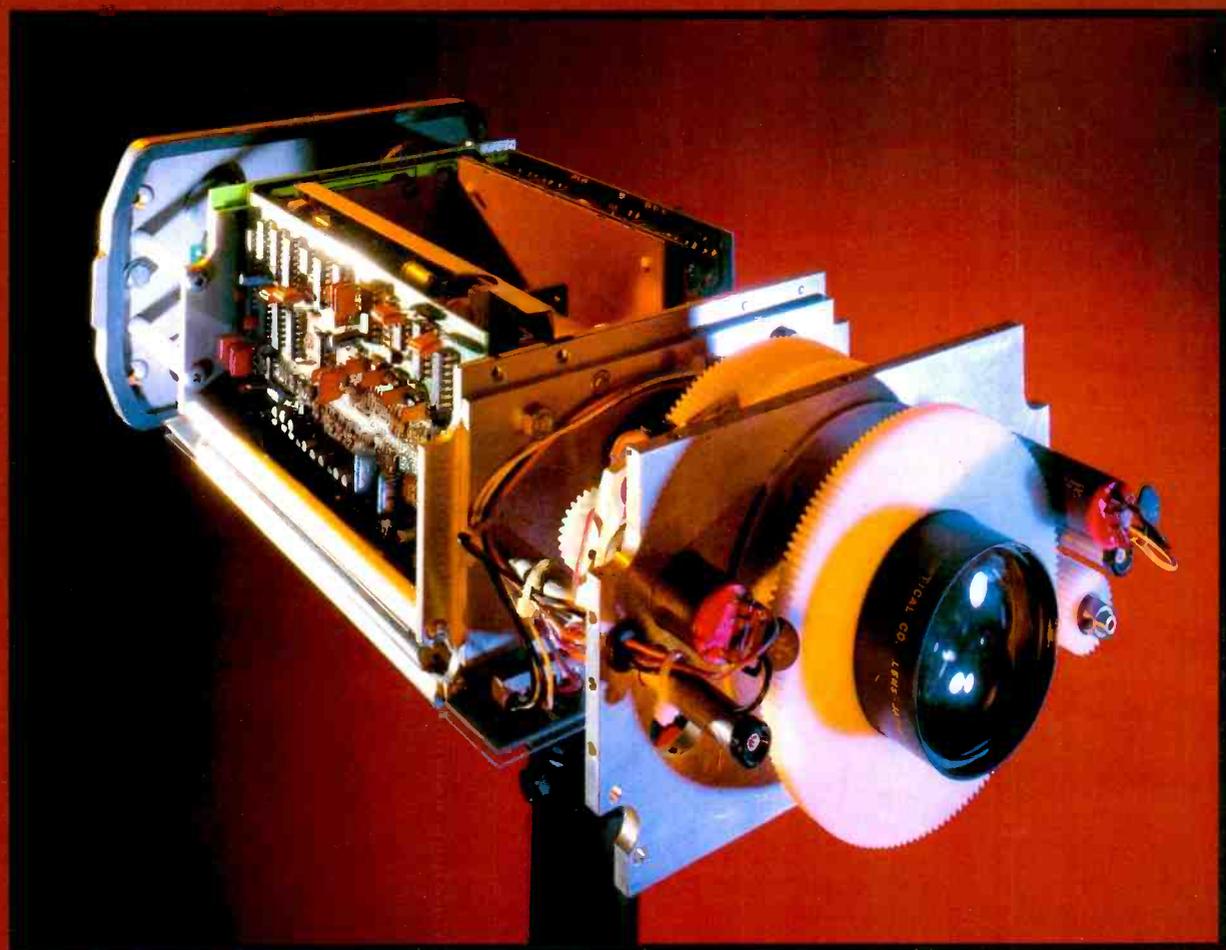

All about Lenses • DX-TV
Remote Control for VCRs
Variable IF Sound Channel
Grundig's VHS Machine
Simple CRT Tester/booster
VCR Clinic • TV Fault Finding

MANOR SUPPLIES

NEW MKV PAL COLOUR TEST GENERATOR FOR TV & VCR.

TEST DEMONSTRATIONS AT 172 WEST END LANE




- ★ 40 different patterns and variations.
- ★ Broadcast transmission accuracy (fully interlaced sync pulses with correct picture blanking).
- ★ EBU colour bars, BBC colour bars, whole rasters & split bars (specially useful for VCR service), white, yellow, cyan, green, magenta, red, blue and black.
- ★ Chequerboard.
- ★ Mono outputs with border castellations, cross hatch, grey scale, vertical lines, horizontal lines and dots.
- ★ UHF modulator output plugs straight into receiver aerial socket.
- ★ Additional video output for CCTV & VCR.
- ★ Facilities for sound output.
- ★ Easy to build kit, standard parts. Only 2 adjustments. No special test equipment required.
- ★ Mains operated with stabilised power supply.
- ★ All kits fully guaranteed with back-up service.
- ★ Also available with VHF Modulator.

Price of Kit **£70.00**
 De Luxe Case (10"×6"×24") **£7.40**
 Optional Sound Module (6MHz or 5.5MHz) **£3.90**
 Built & Tested in De Luxe Case including Sound Module **£105.00**

SPECIAL TEST REPORT 'TELEVISION' DEC. 1982

Post/Packing £2.50
 Add VAT 15% TO ALL PRICES

PAL COLOUR BAR GENERATOR (Mk4)

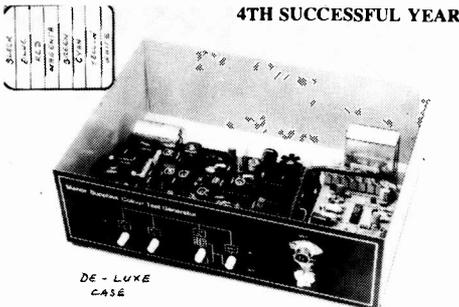

- ★ Output at UHF, applied to receiver aerial socket.
- ★ In addition to colour bars R-Y, B-Y etc.
- ★ Cross-hatch, grey scale, peak white and black level.
- ★ Push button controls, battery or mains operated.
- ★ Simple design, only five i.c.s on colour bar P.C.B.

PRICE OF MK 4 COLOUR BAR GENERATOR KIT **£30.00**. DELUXE CASE **£7.40**. BATT HOLDERS **£2.80**. MAINS SUPPLY KIT **£4.20** (Combined P&P **£2.20**).

MK 4 DE LUXE (BATTERY) BUILT & TESTED **£58.00** + **£2.20** P & P.
 MK 4 DE LUXE (MAINS) BUILT & TESTED **£68.00** + **£2.20** P & P.
 VHF MODULATOR (CH 1 to 4) FOR OVERSEAS **£5.75**.
 EASILY ADAPTED FOR VIDEO OUTPUT & C.C.T.V.
 (ADD VAT 15% TO ALL PRICES)

MANOR SUPPLIES TELETEXT ADAPTOR KITS (LESS CASE)

MK 1 (Texas XMII) remote control **£120.00** p.p. **£3.00**.
 MK 2 (Mullard) infra red remote control **£150.00** p.p. **£3.00**.
 Further details on request. Tel 01-794 8751/7346

Goods available if in stock immediately over shop counter (Mail order between 3 days and 1 week from receipt of order).

TV SERVICE SPARES

BACKED BY TWENTY YEARS EXPERIENCE & STAFF OF TECHNICAL EXPERTS

TELEVISION MAGAZINE PROJECT PARTS. COLOUR PORTABLE, MONO PORTABLE, MONITOR, TEST GENERATORS, ETC.

- THORN TX10 Teletext Interface Panels suitable for Mullard Decoders **£2.50** p.p. **£1.00**.
 THORN TX10 Facia Control Panel incl. Remote Control receiver **£7.50** p.p. **£1.50**.
 THORN TX10 type Remote & Tuning Control Panel **£9.40** p.p. **£1.50**.
 THORN TX10 Series Facia Control Panel with 8 position Channel Selector **£5.00** p.p. **£1.50**.
 PHILIPS UHF Modulator (Audio & Video Input) **£15.00** p.p. **£1.00**.
 SAW FILTER IF AMPLIFIER PLUS TUNER complete and tested for T.V. Sound & Vision. **£28.50** p.p. **£1.20**.
 THORN TX9, TX10 Saw Filter IF Panel. **£8.50** p.p. **80p**.
 PAL DECODER KIT for RGB Monitors **£27.00** p.p. **£1.00**.
 SPECIAL OFFER TEXAS XMII Teletext Decoder New & Tested at reduced price. **£40.00** p.p. **£1.60**.
 TELETEXT 23 Button De-Luxe Handset with 5 yds Cable. **£6.80** p.p. **£1.20**.
 XMII Stab. Power Supply. **£3.80** p.p. **£1.20**.
 CROSS HATCH UNIT KIT, Aerial Input type, incl. T.V. sync. and UHF Modulator, Battery Operated, also gives Peak White & Black Levels, can be used for any set. **£12.00** p.p. **80p**. (Alum. Case **£2.55**, De Luxe Case **£6.80** p.p. **£1.40**). ADDITIONAL GREY SCALE Kit **£2.90** p.p. **45p**.
 UHF SIGNAL STRENGTH METER KIT **£20.00** (VHF version also available). Alum. Case **£2.55**. De Luxe Case **£7.40** p.p. **£1.80**.
 CRT TESTER & REACTIVATOR PROJECT KIT For Colour & Mono **£28.00** p.p. **£2.80**.
 BUSH Z718 BC6100 series IF Panel **£5.00** p.p. **90p**.
 BUSH A816 IF Panel (Surplus) **£1.65** p.p. **90p**.
 DECCA 80 Series IF, Frame, T.B. **£5.00** p.p. **£1.40**.
 GEC 2040 Convergence Panels, Decoder Panels. **£2.50** p.p. **£1.80**.
 GEC 2040 IF Panels **£2.80** p.p. **£1.60**.
 GEC 2110 Convergence Panels **£5.00** p.p. **£1.80**.
 GEC "20AX" Series Switch Mode Power Supply **£5.00** p.p. **£1.80**.
 PYE 691-7 CDA Panels. Makers tested stock. **£6.00** p.p. **£1.45**.
 PYE 725 T.B. Unit. Makers tested stock. **£20.00** p.p. **£2.80**.
 THORN TX9 Panels ex factory for small spares. Includes I.C.s & Semiconductors etc. **£5.00** p.p. **£2.00**.
 THORN TX9 Panels salvaged ex factory for spares incl. LOPT & Mains Transformers. **£10.00** p.p. **£2.80**.
 THORN TX9 Panels ex factory salvaged complete cond. **£20.00** p.p. **£2.80**.
 THORN TX10 T.B. Panels salvaged ex factory. **£15.00** p.p. **£3.00**.
 THORN TX10 IF/Decoder Panels salvaged ex factory. **£15.00** p.p. **£2.00**.
 THORN 3000/3500 Power supply unit. New cond. **£10.00** p.p. **£2.80**.
 THORN 8000/8500 IF/Decoder Panels salvaged **£3.20** p.p. **£1.80**.
 THORN 8000/8500 Frame T.B. Panels salvaged/spares **£2.50** p.p. **£1.40**.
 THORN 9000 Series Control & Receiver Unit **£6.80** p.p. **£1.80**.
 THORN 9000 IF/Decoder Panels Salvaged. **£5.00** p.p. **£1.60**.
 THORN 9000 Series. Long panel facia unit incl. 6 Position Channel Selector & Loudspeaker **£6.00** p.p. **£2.00**.
 PHILIPS G8/G9 IF/Decoder Panels for small spares **£1.50** p.p. **£1.40**.
 G8 Decoder Panels salvaged **£3.80**. Panels for spares **£1.75** p.p. **£1.40**.
 G9 Scan Panel. Basic PCB in Fibreglass **£14.50** p.p. **£1.80**.
 G11 Frame Panels. IF Panels **£18.00** each p.p. **£2.00**.
 GRUNDIG 8630 Series Varicap Tuners **£5.00** p.p. **£1.00**.
 VARICAP. U321, U322, ELC1043/06, ELC1043/5 **£6.80** p.p. **80p**. G.I. type (equiv. 1043/05) **£3.50** p.p. **80p**. Makers Varicap Controls PYE CT200 4PSN **£7.50**, BUSH 4PSN **£4.80**, DECCA 4PSN **£5.80** p.p. **80p**.
 SPECIAL OFFER ELEVEN POSITION Varicap Control Unit UHF/VHF **£1.80** p.p. **£1.00**.
 BUSH "TOUCH TUNE" Varicap Control Z179, Z718 types **£3.80** p.p. **95p**.
 G8 Decoder Panels salvaged **£3.80**. Panels for spares **£1.75** p.p. **£1.40**.
 VARICAP VHF MULLARD ELC 1042, PHILIPS, **£6.90** p.p. **80p**.
 UHF/625 TUNERS, many different types in stock. DECCA Bradford 5 position, MULLARD 4 position **£2.50**, JAP Rotary **£4.80** p.p. **£1.80**.
 TV SOUND IF Panels **£6.80** p.p. **£1.00**.
 LOPT TESTER, Service Dept approved **£15.50** p.p. **£1.20**.
 LOPTS New and guar. P/P Mono **£1.35**, Colour **£1.50**, Bobbins **80p**.
- | | | | |
|-------------------------------------|--------------|----------------------------------|---------------|
| BUSH 161 to 186 (twin panel)..... | £5.90 | R.B.M. A823 | £4.90 |
| BUSH, MURPHY 774 series | £8.50 | R.B.M. Z179 | £9.80 |
| BUSH, MURPHY A816 series | £8.50 | R.B.M. T20, T22 | £9.80 |
| FERG., HMV, MARCONI, ULTRA | | R.B.M. T20, T22 Bobbin | £5.60 |
| 950, 1400, 1500, 1580, 1590, 1591 | £5.90 | DECCA Bradford (state Mod No)... | £8.80 |
| THORN 1600, 1615, 1690, 1691 | £9.15 | DECCA 80, 100 | £8.80 |
| GEC 2000 to 2038 series | £6.80 | GEC 2028, 2040, 2100 | £5.80 |
| GEC series 1 & 2 | £8.00 | GEC 2110 series | £10.60 |
| INDESIT 2024EGB | £7.65 | ITT CVC 5 to 9, CVC20 | £9.80 |
| ITT/KB VC200, 300 | £7.65 | ITT CVC25, CVC30 series | £8.80 |
| MURPHY 1910 to 2414 (twin panel) | £5.90 | PYE 691-697 (state model no.)... | £10.00 |
| PHILIPS 170, 210, 300 series | £7.65 | PYE 713, 715 | £6.80 |
| PYE, INVICTA, EKCO, FERR. | | PYE 725 (90°) 731 to 741 | £9.20 |
| 368, 169, 569, 769 series | £7.65 | PHILIPS G8 | £8.80 |
| SPECIAL OFFER | | PHILIPS G9 | £10.80 |
| DECCA 20/24, 1700, 2000, 2401 | £3.80 | PHILIPS 570, 571 | £6.80 |
| GEC 2114J/Junior Fineline | £2.80 | THORN 3000/3500 SCAN, EHT ... | £6.90 |
| PYE 40, 67 | £1.75 | THORN 8000/8500/8800 | £12.90 |
| KB VC ELEVEN (003) | £1.75 | THORN 9000 to 9600 | £12.90 |
| KB VCI | £2.80 | THORN 9800 | £19.05 |

OTHERS AVAILABLE, PRICES ON REQUEST. ALSO LOPTS. TRIPLERS Full range available. Mono & Colour. Special Offer: Thorn 8000 (2 lead) EHT Tray **£2.80** p.p. **80p**. TRANSDUCTORS suitable for G8, A823, Bradford etc. **£1.50** p.p. **60p**. 6-3V CRT Boost Transformers for Colour & Mono **£5.00** p.p. **£1.20**. CALLERS WELCOME AT SHOP PREMISES THOUSANDS OF ADDITIONAL ITEMS, ENQUIRIES INVITED LARGE SELECTION TESTED COLOUR PANELS POPULAR MODELS Telephone 01-794 8751, 794 7346


MANOR SUPPLIES

172 WEST END LANE, LONDON, N.W.6.

NEAR: W. Hampstead Tube Stn. (Jubilee) Buses 28, 159, C11 pass door W. Hampstead British Rail Stn. (Richmond, Broad St.) (St Pancras, Bedford) W. Hampstead (Brit. Rail) access from all over Greater London.

Mail Order: 64 GOLDERS MANOR DRIVE, LONDON N.W.11.

PLEASE ADD VAT 15% TO ALL PRICES

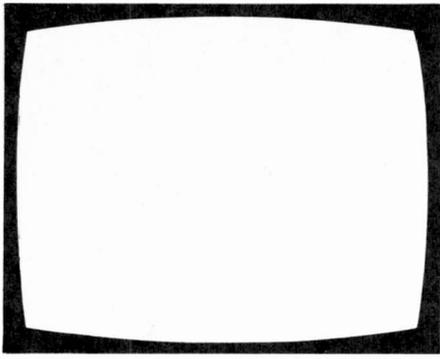

TELEVISION

November
1984

Vol. 35, No. 1
Issue 409

COPYRIGHT

©IPC Magazines Limited, 1984. Copyright in all drawings, photographs and articles published in *Television* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Television* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

CORRESPONDENCE

All correspondence regarding advertisements should be addressed to the Advertisement Manager, "Television", King's Reach Tower, Stamford Street, London SE1 9LS. Editorial correspondence should be addressed to "Television", IPC Magazines Ltd., King's Reach Tower, Stamford Street, London SE1 9LS.

SUBSCRIPTIONS

An annual subscription costs £11 in the UK, £12 overseas (by surface mail). Send orders with payment to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex, RH16 3DH.

BINDERS AND INDEXES

Binders (£4.50) and Indexes (45p) can be supplied by the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. Prices include postage and VAT. In the case of overseas orders, add 60p.

BACK NUMBERS

Some back issues are available from the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF at £1.20p inclusive of postage and packing.

QUERIES

We regret that we cannot answer technical queries over the telephone nor supply service sheets. We will endeavour to assist readers who have queries relating to articles published in *Television*, but we cannot offer advice on modifications to our published designs nor comment on alternative ways of using them. All correspondents expecting a reply should enclose a stamped addressed envelope. Requests for advice on dealing with servicing problems should be directed to our Queries Service. For details see our regular feature "Service Bureau". Send to the address given above (see "correspondence").

this month

- 9 **Leader**
- 10 **Variable I.F. Sound Channel** *Hugh Cocks*
A tunable sound channel for the reception of satellite TV transmissions.
- 12 **CRT Tester/Booster** *Jim Littler*
A simple circuit using the mains transformer from the Decca Bradford chassis.
- 15 **Grundig's VHS Machine – Model VS200** *Steve Beeching, T. Eng.*
A review of the first VHS machine designed in Europe.
- 16 **The Tangle Web** *Les Lawry-Johns*
A little monochrome portable causes more trouble than a whole host of colour TVs. Also a strange colour tube defect.
- 17 **Teletopics**
- 19 **30V Battery Eliminator** *Peter H. Dolman, T. Eng.*
A simple oscillator plus rectifier circuit that produces a 30V tuning supply.
- 20 **All About Lenses** *Vivian Capel*
To get the most out of a video camera it's as well to know something about lenses. Basic optics plus a look at the features found on video cameras.
- 23 **A Look at Monitors, Part 2** *Eugene Trundle*
This concluding instalment is concerned mainly with monochrome and colour displays and standard monitor inputs.
- 28 **VCR Clinic**
Reports on VCR faults and servicing from Steve Beeching, T. Eng., Derek Snelling, Philip Blundell, Eng. Tech., Les Harris, John Coombes and Dewi James.
- 30 **Letters**
- 34 **Remote Control for VCRs** *Derek Snelling*
A review of VCR remote control systems with notes on faults and suggestions for adding remote control.
- 37 **The US Scene in the Fifties** *Chas E. Miller*
A look at the techniques used in US TV sets in the fifties, with a full NTSC decoder circuit of the period.
- 39 **Next Month in Television**
- 40 **Long-distance Television** *Roger Bunney*
Reports on DX conditions and reception, news from abroad and details of an i.f. selectivity unit.
- 43 **TV Fault Finding**
Notes on TV receiver faults from M.S. Barakat, Peter H. Dolman, T. Eng., Mick Dutton, Jim Rainey, Philip Blundell, Eng. Tech. and Malcolm Burrell.
- 45 **Pye/Philips Remote Control Systems** *Harold Peters*
A guide to the bewildering variety of remote control systems that have been used with Pye, Philips and Dynatron receivers.
- 48 **Service Bureau**
- 49 **Test Case 263**

OUR NEXT ISSUE DATE DECEMBER WILL
BE PUBLISHED ON NOVEMBER 21

P. V. TUBES

PLEASE NOTE OUR NEW ADDRESS - COME AND SEE US
 104 ABBEY STREET, ACCRINGTON, LANCS BB5 1EE.
 Tel: 0254 36521/32611 Telex: 635562 Griffin G (For P.V.)

HOW TO ORDER
 ADD 75p per order P+P (U.K.). Heavier parcels e.g. cable, service aids, degaus, coils please allow £1.30 P+P (U.K.). Export orders charged at cost. First Class Mail is used whenever possible. Add 15% VAT to total except where it states zero rate.

Goods are despatched on the day we receive your order. If for any reason we are out of stock we will try to inform you as quickly as possible. We try our best to give a speedy, fair and efficient service. V.A.T. invoice on request. Give us a ring - we'll give you service. Please ask if what you need is not listed - we will try to help. Prices are subject to change without notice.

SEMICONDUCTORS

AC107	35	BC558	9	BF355	56
AC126	30	BCY72	13	BF362	68
AC127	32	BD115	45	BF363	72
AC128	32	BD116A	61	BF371	30
AC128K	40	BD124P	79	BF392	35
AC141K	39	BD131	50	BF422	34
AC142K	38	BD132	49	BF423	46
AC176	35	BD133	60	BF435	35
AC176K	35	BD135	38	BF457	35
AC186	41	BD136	38	BF458	43
AC187	38	BD137	38	BF459	43
AC187K	38	BD138	35	BF460	86
AC188	35	BD139	35	BF462	86
AC188K	39	BD140	44	BF469	66
AD143	82	BD144	1.70	BF470	66
AD161	54	BD150	60	BF597	10
AD162	54	BD159	65	BF575	54
AD161/62 MP	1.15	BD166	52	BF758	54
AF106	49	BD179	70	BRF39	27
AF114	89	BD182	1.20	BRF40	27
AF118	1.20	BD183	75	BRF79	85
AF121	75	BD201	85	BRF90	1.74
AF124	48	BD202	91	BT42	39
AF125	46	BD203	80	BT43	39
AF126	46	BD204	99	BFW10	60
AF127	38	BD222	46	BFX29	42
AF139	58	BD223	56	BFX84	40
AF178	1.54	BD225	47	BFX85	30
AF239	60	BD232	68	BFX86	30
AL102	2.00	BD233	60	BFX88	46
AI006	2.50	BD234	63	BFY50	30
AI013	2.00	BD235	60	BFY51	30
BC107	20	BD236	65	BFY52	24
BC108	20	BD237	57	BFY90	95
BC109	20	BD238	65	BR100	34
BC114	12	BD243	85	BR101	45
BC115	17	BD244	85	BR103	45
BC116A	16	BD410	79	BR303	1.46
BC117	30	BD434	74	BR4443	94
BC118	24	BD437	86	BR4444	98
BC119	36	BD438	94	BR46	40
BC139	28	BD507	52	BRY39	56
BC140	32	BD508	55	BRYS5	45
BC141	26	BD509	56	BRYS6	56
BC142	30	BD510	60	BSV57B	89
BC143	31	BD278A	81	BSW67	68
BC147	13	BD517	80	BT100	1.65
BC148	9	BD520	75	BT101	1.20
BC149	12	BD535	82	BT102/500	1.20
BC157	16	BD536	91	BT106	1.60
BC158	16	BD696A	1.49	BT108	1.69
BC159	15	BD697	1.24	BT109	99
BC160	25	BD695	1.39	BT116	1.21
BC161	28	BD698	1.50	BT119	3.66
BC170B	15	BD707	95	BT120	3.66
BC171	15	BDX32	2.10	BT151/800	1.20
BC172	15	BF115	38	BU104	2.00
BC173	12	BF117	36	BU105	1.58
BC174	10	BF125	26	BU108	1.80
BC177	27	BF127	47	BU124	1.90
BC178	26	BF154	23	BU126	1.75
BC182L	9	BF158	18	BU204	1.68
BC183L	12	BF160	27	BU205	1.42
BC184L	14	BF167	24	BU206	1.80
BC186	18	BF173	22	BU208	1.60
BC187	18	BF177	52	BU208A	1.65
BC204	10	BF178	46	BU208D	2.20
BC208	13	BF179	28	= BU800	
BC209	10	BF180	39	BU208/02	2.10
BC212	9	BF181	39	BU326A	1.75
BC212L	13	BF182	36	BU407	1.70
BC213	13	BF183	29	BU426	3.07
BC214	10	BF184	36	BU500	2.30
BC237	14	BF185	36	BU526	2.46
BC238	14	BF194/394	16	BU508	3.20
BC251A	18	BF196	16	BU806	1.40
BC252	12	BF196	16	BU807	2.94
BC261	18	BF197	16	BUW84	1.45
BC262	18	BF198	18	BUW91A	3.84
BC300	50	BF199	21	BUX84	1.50
BC301	53	BF200	35	E1222	40
BC303	33	BF224	25	MCR101	45
BC307	20	BF225	20	MCR220	1.50
BC308	25	BF241	25	ME0411	20
BC323	99	BF256	55	MJE340	68
BC327	18	BF257	28	MJE520	50
BC328	18	BF258	25	MJ3000	1.98
BC337	18	BF259	35	MPSA92	35
BC338	18	BF262	84	MR814	45
BC461	30	BF263	75	MR854	55
BC547	13	BF271	24	MR475	2.46
BC548	13	BF273	24	MR479	2.60
BC532	30	BF274	24	ON447	9.90
BC549	8	BF336	36	ON448	9.90
BC550	7	BF337	41	OT112	1.91
BC557	8	BF338	41	OT121	1.91

INTEGRATED CIRCUITS

R2008B	1.90	AN2140	3.91	SN76003N	2.49
R2010B	1.92	AN240	3.84	= SN76013N	
R2265	1.50	AN318	3.98	SN76023N	2.00
R2322	62	AN262	2.45	SN76110N	1.15
R2323	67	AN301	5.15	SN76115N	2.27
R2461	1.50	AN7150	3.97	SN76131N	2.00
R2540	2.80	AN6340	7.85	SN76226DN	2.00
RCA16334	99	AN6341N	5.10	SN76227N	1.18
RCA16029	99	AN6344	7.85	SN76533N	1.70
RCA16039	99	BA521	2.80	SN76033N	2.49
RCA16091	2.95	BA536	3.00	SN76544N	2.35
RCA16092	99	CA555	46	SN76650N	80
RCA16090	96	CA556	84	SN76666N	80
RCA16041	84	CA741	25	SN76530A	1.47
RCA16334	90	CA748	45	STK015	6.25
RCA16335	99	CA748	45	STK032	13.25
RCA16799	99	HA1151	3.89	STK043	11.05
RCA16957	2.88	HA1322	2.65	STK453	5.65
TIC45	57	HA1342	2.49	STK435	9.06
TIC46	60	HA1306N	2.60	STK436	5.50
TIL32	65	HA1366WR	2.80	STK437	7.85
TIL78	48	HA1392	3.95	STK459	8.20
TIP29C	43	HA11219	2.49	STK441	8.10
TIP30A	47	HA11244	1.98	STK461=465	9.60
TIP30C	43	LA4031P	3.21	STK463	14.30
TIP31C	55	LA4032P	2.90	SW153	2.74
TIP32C	42	LA4102	3.37	TA7050P	95
TIP33B	75	LA4250	3.57	TA7051P	95
TIP34B	1.06	LA4400	3.05	TA7063P	2.20
TIP41C	47	LA4422	3.28	TA7074P	1.00
TIP42C	50	LA4422	3.28	TA7108P	3.43
TIP47	70	LC7120	5.87	TA7120P	2.43
TIP120	65	LC7137	5.50	TA7129AP	3.76
TIP2955	90	LM1011	3.25	TA7130P	1.93
TIP3055	63	LM1340T	75	TA7141P	95
TIS91	21	LM1303N	2.63	TA7146P	5.67
TU106/02	1.80	2N918	82	TA7193P	4.67
2N696	21	2N9304	28	TA7171P	1.85
2N918	82	2N905	51	TA7172P	1.85
2N9304	28	2N3054	60	TA7173P	1.85
2N905	51	2N3055	60	TA7176P	2.50
2N3054	60	2N3702	11	TA7202P	4.27
2N3055	60	2N3703	10	TA7204P	3.77
2N3702	11	2N3705	10	TA7205AP	3.72
2N3703	10	2N3706	17	TA7208P	3.40
2N3705	10	2N5294	48	TA7210P	6.60
2N3706	17	2N5296	48	TA7222	2.42
2N5294	48	2N5298	69	TA7227P	3.74
2N5296	48	2S8337	1.86	TA7228P	5.98
2N5298	69	2N5496	63	TA7228P	5.98
2S8337	1.86	2N6107	81	TA7310P	2.78
2N5496	63	2N6109	75	TA7609P	4.39
2N6107	81	2SA715	1.98	TA7611AP	2.92
2N6109	75	2SC495	1.10	TA8310	58
2SA715	1.98	2SC496	1.31	TA8310	2.83
2SC495	1.10	2SC643A	1.50	TA8320	2.00
2SC496	1.31	2SC1096	1.72	TA8550	55
2SC643A	1.50	2SC1172Y	2.20	TA8530	3.90
2SC1096	1.72	2SC1173Y	1.68	TA8400S1	1.96
2SC1172Y	2.20	2SC1306	2.73	TA84800	1.50
2SC1173Y	1.68	2SC1307	3.00	TA8510	3.00
2SC1306	2.73	2SC1449	1.67	TA8520(Y)	1.68
2SC1307	3.00	2SC1520	2.80	TA8530(Q)	1.38
2SC1449	1.67	2SC1678	2.67	TA8540	1.68
2SC1520	2.80	2SC1909	2.90	TA8550(Q)	1.58
2SC1678	2.67	2SC1953	1.44	TA8560Q	1.59
2SC1909	2.90	2SC2028	1.82	TA8570	1.79
2SC1953	1.44	2SC2029	2.60	TA8690	1.50
2SC2028	1.82	2SC2078	2.90	TA8641Bx1	3.50
2SC2029	2.60	2SC2091	1.73	TA8673	2.45
2SC2078	2.90	2SC2166	2.34	TA8700	2.12
2SC2091	1.73	DEC1	2.20	TA8720	2.64
2SC2166	2.34	DEC2	2.20	TA8750	2.98
DEC1	2.20	THY15/80	2.20	TA890	1.62
DEC2	2.20	THY15/85	2.20	TA810AS	1.10
THY15/80	2.20	THY15/85	2.20	TA820M	1.25
THY15/85	2.20	BU208B	2.20	TA890	3.94
BU208B	2.20	BUW81A	3.84	TA920(Q)	3.00
BUW81A	3.84			TA950(2X)	3.05
				TA970	4.09
				TA990	1.90
				TBA1406	2.44

DIODES

AA119	9	UPC1180C	1.84	AA119	9
BA102	17	UPC1181H	1.62	BA102	17
BA145	13	UPC1182H	2.95	BA145	13
BA148	17	UPC1183H	1.38	BA148	17
BA154	6	UPC1185H	3.66	BA154	6
BA155	14	UPC1188H	2.20	BA155	14
BA156	25	UPC1190G	1.06	BA156	25
BA317	16	UPC1197C	1.06	BA317	16
BAX13	4	UPC1198C	84	BAX13	4
BAX16	8	UPC1200V	1.18	BAX16	8
BB105B	30	UPC1211V	2.70	BB105B	30
BB105G	30	UPC1212V	1.34	BB105G	30
BY126	12	UPC1215V	1.66	BY126	12
BY127	11	UPC1216V	1.20	BY127	11
BY164	45	UPC1217G	1.80	BY164	45
BY176	85	UPC1218H	1.80	BY176	85
BY179	63	UPC1223C	2.20	BY179	63
BY182	87	UPC1225H	2.00	BY182	87
BY184	55	UPC1226C	1.50	BY184	55
BY199	28	UPC1227V	1.20	BY199	28
BY206	14	UPC1228H	5.4	BY206	14
BY210/600	20	UPC1230H	3.94	BY210/600	20
BY210/800	33	UPC1238V	1.16	BY210/800	33
BY223	28	UPC1245V	1.35	BY223	28
BY227	90	UPC1255H	1.92	BY227	90
BY298	22	UPC1259C	6.98	BY298	22
BY299	22				

**CUSTOMER CAN'T PAY?
DONT LOSE HIM FIT A TV METER**



COINAGE
AVAILABLE
10p
50p
£1

COMPLETELY VARIABLE TIMINGS

Alberice METERS LIMITED

MANUFACTURERS OF TV COIN OPERATED
METERS CONTACT (0202) 674272
87-89 Sterte Avenue,
Poole, Dorset. BH15 2AW.
Telex: 418253 LUMIC G

**HOCKLEY DISCOUNT
TELEVISIONS**

94 Soho Hill, Hockley,
Birmingham B19 1AE
Telephone: 021-551-2233

**BEST QUALITY SETS AVAILABLE
AT UNBEATABLE PRICES**

Philips G8, G11, Bush T22, GEC, Starline,
Japs., Deccas, Pye 222s, BRC 9000, 9600,
9800, Sony, latest Hitachi, ITT, CVC30,
CVC45, plus remote control models.

PRICES START FROM £6
WORKING SETS FROM £18
FROM OUR SHOWROOM

DISCOUNT ON QUANTITY

**NORTHERN T.V.
DISTRIBUTORS**
Unit 2, Perth Court,
Team Valley Ind. Estate,
Gateshead, Tyne & Wear
Telephone: 091-487 5389

Opening hours 9 - 7 Monday - Saturday
Sundays by appointment.

**FREE CAREER
BOOKLET**

**Train for success in Electronics
Engineering, T.V. Servicing,
Electrical Engineering—or running
your own business!**

ICS have helped thousands of ambitious people to move up into higher paid, more secure jobs in the fields of electronics, T.V., electrical engineering—now it can be your turn. Whether you are a newcomer to the field or already working in these industries, ICS can provide you with the specialised training so essential to success.

Personal Tuition and 80 Years of Success

The expert and personal guidance by fully qualified tutors, backed by the long ICS record of success, is the key to our outstanding performance in the technical field. You study at the time and pace that suits you best and in your own home.

You study the subjects you enjoy, receive a formal Diploma, and you're ready for that better job, better pay.

**TICK THE FREE BOOKLET YOU
WANT AND POST TODAY**

**ELECTRONICS
ENGINEERING**

A Diploma Course, recognised by the Institute of Engineers & Technicians as meeting all academic standards for application as an Associate.

**T.V. & AUDIO
SERVICING**

A Diploma Course, training you in all aspects of installing, maintaining and repairing T.V. and Audio equipment, domestic and industrial.

**ELECTRICAL
ENGINEERING**

A further Diploma Course recognised by the Institute of Engineers & Technicians, also covering business aspects of electrical contracting.

**RUNNING YOUR
OWN BUSINESS**

If running your own electronics, T.V. servicing or electrical business appeals, then this Diploma Course trains you in the vital business knowledge and techniques you'll need.

Name

Address

ICS ICS
Dept. EGSB4
160 Stewarts Road,
London SW8 4UJ.

01-622 9911
(all hours)

WE WILL ONLY SUPPLY TOP QUALITY, BRANDED COMPONENTS. REPUTATION COUNTS WITH US

G.G.L. COMPONENTS
 108 SCOTLAND ROAD, CARLISLE, CUMBRIA CA3 9EY
 PHONE (0228) 20358/39693

BUY WITH



E.H.T. TRAYS	
RBM T20/22A	7.35
RBM A823	7.85
PHILIPS G8-550	6.90
PHILIPS G9	6.45
THORN1500-3S	4.25
THORN1500-5S	4.55
THORN3000/3500	7.75
THORN8000	4.00
THORN8500/8800	6.90
THORN9000	8.40
PYE 731	6.50
DECCA 2230	6.30
DECCA 80	6.30
DECCA 100	6.75
ITT CVC 20/30	6.85
Universal	5.90

INTEGRATED CIRCUITS	TYPE PRICE (£)	TYPE PRICE (£)	TYPE PRICE (£)	TYPE PRICE (£)	TRAN-SISTORS	TYPE PRICE	TYPE PRICE	LINE D/P TR.										
LA3122	2.10	TBA520	1.30	STK0050	7.50	UCP1185H2	3.30	BR100	18	RBM T20/22A	12.20							
LA3301	1.97	TBA530	1.00	STK011	7.35	UCP1188H	3.30	BR101	32	RBM Z718 18/20/22								
LA4350	1.93	TBA540	1.27	STK014	7.65	UCP1190C	2.10	BR103	55		22.95							
LA4031	1.66	TBA550	1.40	STK015	7.15	UCP1198H	1.30	BT106	1.15	PHILIPS G8	7.90							
LA4031P	2.45	TBA560Q	1.60	STK016	7.45	UCP1200V	1.90	BD131	33	BT116	1.30	PHILIPS G9	8.75					
LA4032	2.34	TBA7500Q	2.45	STK020	9.05	UCP1200V	1.85	AC128K	30	BU126	1.78	PHILIPS G11	13.50					
LA4051	2.79	TBA800	80	STK032	11.32	UCP1211C	4.05	AC187K	30	BD201	80	BU204	1.50	THORN 1590/1	8.68			
LA4101	1.88	TBA810AS	1.15	STK035	12.67	UCP1215V	2.50	AD149	70	BD202	70	BU205	1.42	THORN 1690/1	9.88			
LA4102	1.97	TBA820	1.40	STK036	12.67	UCP1216V	2.00	AD161	42	BD203	70	BU206	1.35	THORN 1615	9.75			
LA4400	2.80	TBA890	2.95	STK043	11.33	UCP1217G	3.35	AD162	42	BD234	40	BU208A	1.40	THORN TX10	12.50			
LA4420	1.94	TBA920Q	1.50	STK050	20.75	UCP1218H	2.75	AF127	36	BD222	50	BU208/02 1.70	PYE 731/713 (110)	10.20				
LA4422	2.75	TBA950/2X	2.65	STK070	21.95	UCP1222	2.05	AU110	2.10	BD232	50	BU205	1.42	THORN 1690/1	9.88			
LA4430	1.93	TBA990	1.55	STK077	8.56	UCP1223	3.40	AU113	3.50	BD233	37	BU407	1.12	ITT CVC 1-9	9.60			
LA4460	2.95	TCA270S	1.30	STK078	8.45	UCP1225	3.10	BC107	14	BD234	40	BU500	1.80	DECCA 2230	8.30			
LA4461	2.95	TCA900	1.95	STK082	9.75	UCP1226	2.55	BC108	14	BD235	32	BU526	2.20	DECCA 80	8.58			
MB3712	2.30	TCA940	1.55	STK086	12.89	UCP1227	2.10	BC109	14	BD236	40	BU826	3.20	DECCA 100	8.58			
MB3713	2.25	TDA1002A	1.50	STK415	9.66	UCP1230H	3.45	BC141	26	BD237	40	R2008B	1.45	ITT CVC 20	7.75			
MB8719	5.20	TDA1003A	2.80	STK433	7.25	UCP1245	1.99	BC142	23	BD238	39	R2010B	1.45	ITT CVC 25/30/32	8.00			
MC1327A	1.60	TDA1004A	2.70	STK435	7.75	UCP1250	2.45	BC143	25	BD410	50	R2540	2.35	ANTI-SURGE FUSES				
MC1358P	1.00	TDA1035	3.20	STK437	7.77	UCP1350C	4.50	BC147	09	BD434	50	TIP31C	46	A/S20MM 80MA	2.75			
MC1330P	0.90	TDA1044	3.10	STK439	7.86	UCP1353C	2.60	BC148	09	BD437	70	TIP32C	47	100, 160, 200MA	1.70			
ML2318	1.95	TDA1170	1.80	STK441	9.52	UCP1356C2	3.05	BC157	10	BD438	78	TIP33B	80	315, 400, 500, 630				
ML232B	1.70	TDA1412	0.90	STK443	11.33	UCP1358H	3.05	BC158	11	BD707	1.05	TIP41C	48	800MA, 1A, 1.25, 1.6,				
ML237	2.50	TDA2020	2.95	STK459	9.55	UCP1363C	3.20	BC159	11	BDX32	1.65	TIP42C	48	2A	1.20			
ML238	4.22	TDA2522	1.80	STK463	10.88	UCP1365C	5.05	BC160	22	BF194	12	TIP2955	70	2, 3.15, 4, 5A	1.35			
TA7072P	2.75	TDA2523	2.25	STK501	8.98	UCP1366C	2.85	BC172	10	BF195	13	TIP3055	55	NEW VALVES				
TA7108P	2.10	TDA2530	2.10	UPC41C	2.95	UCP1367C	2.85	BC177	22	BF196	11	TV106/02 160	DY802	72	1N4001-7	0.07		
TA7120P	2.05	TDA2532	2.20	UPC554C	1.30	UCP1368C	3.76	BC182	10	BF197	11	2N3054	55	PCF802	86	1N5401-8	0.12	
TA7129	3.00	TDA2540	1.95	UPC555H	0.70	UCP1370C2	3.80	BC182L	11	BF198	11	2N3055	50	PCL82	80	BZ261-range	0.18	
TA7139	1.20	TDA2560	1.80	UPC566H3	2.10	UCP1373H	1.20	BC183L	11	BF241	15	2SC1172Y		PCL84	81	BZ78-range	0.11	
TA7139P	2.80	TDA2581	1.70	UPC577H	3.00	UCP1377C	4.60	BC184L	11	BF256LC	25			PCL805	90			
TA7157P	3.00	TDA2590	2.25	UPC585C	1.40	UCP1378H	3.80	BC208	12	BF258	25	2SC2029	2.80	PCL86	81			
TA7171P	3.40	TDA2591	2.70	UPC1009H	2.15	UCP1384C	5.50	BC212L	10	BF259	26	2SC2078	2.20	PLF200	1.35			
TA7172P	3.40	TDA2593	2.30	UPC1017G	2.55	UCP20021H	2.20	BC213L	10	BF337	28	2SC2078	2.00	PL504	1.50			
TA7176AP	2.90	TDA2600	5.50	UPC1018C	1.15			BC214L	10	BF338	30	2SC1969	2.45	PL508	2.90	PYE IF GAIN MOD	7.85	
TA7193P	4.20	TDA2611A	1.50	UPC1025H	3.30			BC237	11	BF458	30			PL509/519	5.65	EAV COIL G11	1.65	
TA7202P	3.00	TDA2640	1.80	UPC1026C	1.45			BC337	11	BF459	36			PY88	69	VA1104	0.70	
TA7203P	3.00	TDA3560	5.10	UPC1028H	2.15			BC338	10	BFR90	1.60			PY500A	1.90	G8 TRANSDUCTOR	2.25	
TA7205AP	1.60	SAS560S	1.83	UPC1031H	2.40			BC547	10	BFY51	22			PY81/800	69	G8 ON/OFF SW.	1.40	
TA7208P	2.20	SAS570S	1.90	UPC1032H	0.85													
TA7210P	5.60	SAS580	2.40	UPC1035C	2.50													
TA7222P	1.70	SL901B	4.80	UPC1042C	2.40													
TA7223P	3.15	SL917B	6.95	UPC1043C	2.45													
TA7227	4.65	SN76003N	2.05	UPC1156H	2.45													
TA7310P	1.70	SN76013N	1.80	UPC1168C	2.70													
TA7313P	2.10	SN76013N	1.80	UPC1170C	1.55													
TA7313P	2.10	SN76023N	1.80	UPC1176C	2.15													
TAA550	28	SN76110N	90	UPC1177H	2.30													
TBA120AS	70	SN76226DN	1.45	UPC1178C	2.20													
TBA120SB	90	SN76227N	1.00	UPC1180C	3.05													
TBA120U	1.00	SN76660N	65	UPC1181H	2.20													
TBA395	1.25	STK0039	6.45	UPC1182H	2.35													
TBA396	85	STK0040	5.95	UPC1183H	2.35													

DIODES	
BY127	1.10
BY133	1.15
BY164	40
BY179	50
BY210/800	30
BY223	86
BY227M	23
BYX10	20
BYX55/600	26
BYX71/600	78
0A90	07
1N4001-7	07
1N5401-8	12
BZ261-range	18
BZ78-range	11

SUNDRIES	
PYE IF GAIN MOD	7.85
EAV COIL G11	1.65
VA1104	0.70
G8 TRANSDUCTOR	2.25
G8 ON/OFF SW.	1.40

Available also a range of 2SA/B/C/D Transistors. Phone or write for lists.

ORDERING
 Please Add 50p For P/P U.K.
 Add 15% VAT to This Total.
 Export Orders - Cost.
 DELIVERY BY RETURN ON ALL STOCK ITEMS.

INCREASE YOUR PROFITS IMPROVE YOUR SERVICE WITH RELIABLE COST EFFECTIVE TEST EQUIPMENT

LEADER LCT-910A C.R.T. TESTER-REJUVENATOR
 Our top selling instrument is designed to readily test the various characteristics and rejuvenation of both colour and B/W C.R.T's.

- ★ Tests for shorts and leakage between electrodes.
- ★ Tests cathode emission characteristics.
- ★ Separately checks condition of guns.
- ★ Removal of shorts and leakage between electrodes.
- ★ Checks heater warm-up characteristics.
- ★ Rejuvenation of low emission cathodes with automatic timing.
- ★ Super rejuvenation with manual control.
- ★ Complete with tube base adaptors.

Size: H 230mm W 330mm D 120mm.



PRICE £186 + £27.90 VAT

THE VERY LATEST SC110A LOW POWER, FULLY PORTABLE OSCILLOSCOPE.

The new Thandar SC110A represents a break-through in oscilloscope development. The SC110A is ONLY TWO INCHES thick and weighs under two pounds, yet retains the standard features and controls of a bench oscilloscope. **FITS IN A BRIEFCASE**

Full Sized Performance

- ★ 10 MHz bandwidth
- ★ 10 mV per division sensitivity
- ★ Full trigger facilities are provided including TV frame, or TV filtering.
- ★ Runs on 4 to 10V DC via disposable batteries, re-chargeable cells, or AC adaptor.
- ★ Size 255mm x 148mm x 50mm.

PRICE £165.00 + £24.75 VAT

Accessories: Carry Case £5.95 + £0.89 V.A.T.
 x 1 Probe £7.50 + £1.13 V.A.T.
 x 10 Probe £8.50 + £1.28 V.A.T.
 x 1 x 10 Switched Probe £10.50 + £1.58 V.A.T.
 AC Adaptor £6.95 + £1.04 V.A.T.

ALSO AVAILABLE
 Analogue Multimeters
 Digital Multimeters
 Oscilloscopes
 Signal Generators
 Digital Frequency Meters
 Pattern Generators
 CRT Tester/Rejuvenator
 T.V. Field Strength Meter
 Digital Capacitance Meter
 LARGE S.A.E.
 FOR COMPLETE LIST.

LEADER HIGH VOLTAGE METER EHT PROBE
 Measures up to 40 K.V. D.C. with SAFETY BUILT IN METER

PRICE £28.00 + £4.49 VAT

LOPT TESTER
 BK's REVOLUTIONARY DYNAMIC 'LOPT' TESTER
 Revolutionary L.O.P.T. tester. Operates in dynamic mode which actually tests the L.O.P.T. under high voltage conditions without de-soldering or removal.
 Size 75x100x40 mm. Supply 240V AC

PRICE £25.99 + £3.VAT

CRT TESTER-REJUVENATOR
 BK's C.R.T. TESTER-REJUVENATOR
 Tests and rejuvenates blue, green & red guns separately. Fitted with delta and P.I.L. sockets. Compact size 120x65x60 mm. Supply 240V AC

PRICE £32.00 + £4.80VAT

HAMEG HM 203-4 20MHz DUAL TRACE OSCILLOSCOPE

SPECIFICATION:

- ★ BANDWIDTH DC-20MHz
- ★ SENSITIVITY CH1, CH2 2mV-50V/DIV
- ★ TIMEBASE 40ns to 0.2S CH
- ★ TRIGGER DC-40MHz Auto-Normal-TV
- ★ CALIBRATION OUTPUT
- ★ CH1 ADD AND INVERT FACILITY
- ★ ALT/CHOP SWITCH
- ★ LARGE RECTANGULAR SCREEN 8 x 10 cms.
- ★ BUILT IN SEMICONDUCTOR COMP. TESTER
- ★ SIZE 285mm x 145mm x 380mm.
- ★ SUPPLY 110-125-220-240V AC 50-60Hz

WITH COMPONENT TESTER

PRICE £264.00 + £39.60 VAT

2 YEAR WARRANTY

Optional probes as above

U.K. Post Paid, Export orders welcome, please deduct V.A.T. and enquire for Overseas carriage cost. Barclaycard/Access orders welcome, or Cheque, Bank Draft, etc., with order please. Large S.A.E. for technical leaflets of complete range. Delivery normally within 7 days.

B. K. ELECTRONICS Dept. 'T', UNIT 5, COMET WAY, SOUTHEND-ON-SEA, ESSEX. SS2 6TR TEL: 0702-527572

TELEVISION/COMPUTER TRAINING

(FULL TIME COURSES APPROVED BY THE BUSINESS & TECHNICAL EDUCATION COUNCIL)

2 YEAR

**BTEC National Diploma
ELECTRONIC &
COMMUNICATIONS ENGINEERING**
(Electronics, Computing, Television, Video, Testing & Fault Diagnosis)

15 MONTHS

**BTEC National Certificate
ELECTRONIC EQUIPMENT SERVICING**
(Electronics, Television, Video Cassette Recorders, CCTV, Testing & Fault Diagnosis)

15 MONTHS

**BTEC National Certificate
COMPUTING TECHNOLOGY**
(Electronics, Computing Software/Hardware, Microelectronic Testing Methods)

9 MONTHS

**BTEC Higher National Certificate (HNC)
COMPUTING TECHNOLOGY & ROBOTICS**
(Microprocessor Based Systems, Fault Diagnosis, ATE, Robotics)

**THESE COURSES INCLUDE A HIGH PERCENTAGE OF COLLEGE
BASED PRACTICAL WORK TO ENHANCE FUTURE EMPLOYMENT
PROSPECTS**

**Shortened Courses can be arranged for
applicants with previous knowledge.**

Full Prospectus from:

**LONDON ELECTRONICS COLLEGE (Dept TF)
20 PENYWERN ROAD, EARLS COURT,
LONDON SW5 9SU. Tel: 01-378 8721**

TOP TWENTY VIDEO SPARES

Cassette lamp (Ferg/JVC)	£1.80	Video head (Ferg) (state model)	£37.50
Cassette lamp (Panasonic)	£1.80	Video head (Panasonic) (state model)	£39.50
Take-up clutch (Ferg)	£6.50	Head cleaning fluid	£1.50
Belt kit (Sony/Toshiba early)	£6.50	Head cleaning sticks (each)	50p
Belt kit (Ferg) (state model)	£6.50	Head cleaning tapes (VHS/Beta)	£5.95
Belt kit (Panasonic NV7000)	£6.50	Loading Belt (SL8000)	£1.50
Belt kit (Sanyo 9300)	£6.50	Loading Belt (Sanyo 9300)	£1.50
Rewind kit (Sony C7)	£6.95	Overhaul kit (Ferg) (state model)	£19.95
Reel idler (Sharp VC)	£3.45	Overhaul kit (Sony) (state model)	£19.95
Video head (Sony C7)	£39.50	Overhaul kit (Sharp) (state model)	£19.95

TELEVIDEO SERVICES

NOTTINGHAM (0602) 226070

76 Wollaton Rd., Beeston, Nottingham

Please add 50p post & packing and then add 15% VAT to total

ALL ORDERS DESPATCHED BY RETURN OF POST

VIDEO HEADS

MONOLITH
electronic products

HIGH QUALITY UNIVERSAL VIDEO HEAD
REPLACEMENTS FOR ALL VHS AND BETAMAX
VCR MACHINES

VHS Part No. 3HSS (5mm Centre Hole) £29.95 PRICE
VHS Part No. 4HSS (15mm Centre Hole) £29.95 EACH
BETAMAX Part No. PS3B £38.95 EX.
REPLACEMENT KIT (17 Pieces Boxed) £17.35 V.A.T.
PLEASE ADD 15% V.A.T. PLUS P&P £2.00 PER ORDER
OUR FULL CATALOGUE AVAILABLE ON REQUEST.

Please allow between 14 and 28 days for delivery.

AUDIO + VIDEO HEADS - MOTORS - PARTS

Suppliers to most U.K. Distributor/Service Organizations

THE MONOLITH ELECTRONICS CO. LTD
5-7 Church Street, Crewkerne, Somerset TA18 7HR, England
Telephone Crewkerne (0450) 74321 Telex 46306 MONLTH G



CHROMAVAC

QUALITY REBUILDS

**SPECIAL
OFFERS**
THIS MONTH
ONLY

Get on the hot-line today!

SUPERIOR QUALITY TUBES

051

428 8777

DELTA RE-BUILDS

most types of Inline Re-builds or
new ex-stock

★ 2 YEAR WARRANTY
★ 4 YEAR OPTIONAL

Delta Rebuilds

Up to 19"	£24
Up to 22"	£28
Up to 26"	£32
110° up to 22"	£32
110° up to 26"	£34
Low focus	£30
A47 342 New	£32

Delta only. Less 7½% 5+
Less 10% 10+ and over

Inline Rebuilds

Up to 22"	£40
Up to 26"	£45
Bonded Coil	+£5

ALL SIZES OF
NEW MONO TUBES
AT COMPETITIVE
PRICES

IN LINE TYPES EX-STOCK SELECTION NOT REBUILDS

370 HFB	£45	560 DMB	£62
370 HUB	£45	AXT 56-001	£62
420 CSB	£45	560 ATB	£65
420 EDB	£45	660 AB	£65
420 EZB	£45	A67-701	£65
420 ERB	£45	670 CZB	£65
510 UFB/A51-590	£55	H6817	£65
A51-570	£55		
A51-210	£55		
510 VSB	£60		
AXT 51-001	£60		
560 DYB	£62		
560 EGB	£62		
560 CGB	£62		

CARRIAGE
£5 Singles, 2-3 £10, 4 £12
10 £15, 10+ Carriage paid
EXCLUSIVE OF VAT
TERMS
Cash with order

QUANTITY
DISCOUNT
AVAILABLE
Ask for details

★ OUR TECHNICAL DEPT. WILL ADVISE YOU ON
PROBLEMS. YOU MAY ENCOUNTER ON FITTING
INLINE TUBES

DELIVERY: Ex stock items immediate dispatch on receipt of order.
Others allow 14 days.


THE COMPANY WHO PUT HIGH STANDARDS FIRST

CHROMAVAC

CHROMAVAC LTD. UNIT 7, BEAR BRAND COMPLEX,
ALLERTON ROAD, WOOLTON, LIVERPOOL 25
Ask for MR. BUTTERWORTH ON: 051-428 8777

EAST CORNWALL COMPONENTS

ZENER DIODES 400mV Plastic 3V-75V 8p each, 10/75p 1.3W Plastic 3V-200V 15p each, 10/17p 1.5W Flange 4.7-47V £1.40 2.5W Plastic 7.5-75V £1.26 each 20W Stud 7.5-75V 87p each £1.31 each		INTEGRATED CIRCUITS - (IC) EACH AN240P 3.42 SN76282DN 1.80 AN214Q 3.88 SN76227N 1.10 AN7150 2.90 SN76530P 1.40 CA3065 1.75 SN76533N 1.60 CA4031P 2.88 SN76650N 1.05 CA4102 3.30 SN76650N 0.75 CA4250 3.50 SN76666N 0.80 CA4400 2.98 STK015 6.50 CA4422 3.07 TA7108P 3.20 LC7120 5.33 TA7120P 2.20 LC7130 5.26 TA7129AP 3.65 LC7137 5.16 TA7130P 1.65 LM3800 0.80 TA7172 1.80 LM1303N TA7208P 3.27 HA1151P 3.12 TA7172P 1.80 MC1307P 1.85 TA7176 2.50 MC1310P 1.85 TA7202P 4.18 MC1312P 2.25 TA7204P 1.86 MC1327P 1.25 TA7205AP 1.50 MC1330P 0.83 TA7208P 3.27 MC1349P 1.85 TA7210P 1.68 MC1350P 1.20 TA7222P 3.88 MC1351P 2.50 TA7223P 1.86 MC1352P 1.50 TA7227P 1.50 MC1357P 2.88 TA7310P 5.80 MC1358P 1.30 TA7308P 4.28 MC1496L TA7911AP 2.86 ML231B 2.10 TAA263 2.48 ML232B 2.10 TAA310A 2.68 ML237B 2.30 TAA550 0.50 MRF475 2.50 TAA570 1.99 MRF475 2.50 TAA570 1.99 MRF477 2.50 TAA570 1.99 NE555 0.50 TAA661B 1.70 C-mos 555 0.88 TAA700 2.80 NE556 0.80 TAA840 3.38 SAA1024 5.35 TAD100 2.00 SAA1025 8.40 FM FILTER 1.30 SAS560A 2.20 TAA121 AS, 1.20 SAS560S 2.85 S.S.A.S.B 1.20 SAS570S 1.85 Q.T.U.U.Q 1.32 SAS580 2.85 TBA120B 1.30 SAS590 2.82 TBA231 1.45 SC9503P 1.10 TBA281 2.65 SL4324 4.00 TBA395 1.60 SL9019 2.20 TBA480Q 1.50 SL917B 7.25 TBA400 2.30 SL1327Q 1.10 TBA510 2.60 SN76003N 2.44 TBA510Q 2.60 SN76013N 1.90 TBA520/Q 1.60 SN76023N 2.90 TBA530/Q 1.60 SN76033N 2.10 TBA540/Q 1.60 SN76110N 1.12 TBA550/Q 1.52 SN76155N 2.00 TBA560/Q 1.70 SN76131N 1.65 TBA560CQ 1.60		UPC1181H 1.60 UPC1185H2 3.75 UPC1212C 1.30 UPC1228H 0.54 UPC1230H 3.90 UPC1350C 4.25 UPC1367C 3.40 UPC1378H 4.40 UPC2002H 2.80		D CONNECTORS 9 15 25 Male Solder .75 1.00 1.50 Angled 1.40 2.00 2.40 Female Solder 1.00 1.45 1.85 Angled 1.50 2.00 2.40 Covers 80 80 80		PLUGS & SOCKETS Metal Co-ax Plug 0.18 Plastic Co-ax Plug 0.10 Metal Line Socket 0.50 Single Junc Socket 0.80 Plastic Phono 0.10 F.M. Plugs 0.20 PL259 Plugs 0.38 Reducer 0.15 Low loss splitter 1 in. 2 out 1.00		SOLDERING SECTION XS25 Wett Iron complete with steel and plug attached 7.20 CX18W, as above 7.00 Antex 15W iron 5.00 Antex 18W iron 5.00 Antex 25W iron 5.00 Antex elements 2.00 Antex bits 0.95 Antex stands 1.90 Solder stands 4.50 Nozzles 0.65		TERMINAL BLOCKS 2 amp 12 way 0.19 5 amp 12 way 0.20 10 amp 12 way 0.40 15 amp 12 way 0.46 32 amp 12 way 0.90		MULTIMER SPECIAL Russian type U4324 - (20,000 O.P.V.) AC Volt: 0.6, 1.2, 3, 12, 30, 60, 600, 1200. DC Volt: 0.3, 0.6, 1.5, 3, 15, 30, 60, 300. DC Curr: M.A. 0.06, 0.6, 6, 60, 600, 3000. AC Curr: M.A. 0.3, 3, 30, 300, 3000. DC Resistance: 0.2, 5, 50, 500, 5000K. level dB: -10 to +12 Supplied with rechargeable batteries. Price £12.00 incl. of p/p & VAT.		MULTISECTION ELECTROLYTICS THORN 850 100+300+100+16/300V 1.80 1400 150+100+100+100+150/320V 1.70 1500 150+150+100/300V 0.56 3000 1000/300V 1.70 3000 175/400V+100+100/350V 2.10 8000/8500 2500+2500/63V 1.35 8000 700/250V 1.50 8000 700/250V 0.58 9000 400/400V 2.25 Timer Amp 4700/25V 0.70 DECCA40/30 400+400/350V 2.45 GEC 2047 2048 2083 2084 2104 3.52 600/250V 1.50 200+200+150+50/300V 2.32 600/250V 1.50 200+200+75+25/350V 2.15 220/180V 1.56 PHILIPS G8 600/300V 1.70 G8 600/300V 1.50 G11 470/250V 1.50 G2200/63V 1.26 T148 125+200+100+32/275V 2.85 691 Series 200+300/350V 2.15 300+300/300V 2.05 AB23 2500+2500/30V 0.98 220/400V 1.75 600/300V 1.78		VDRs, etc. E2952Z 01/ 0.28 02/ 0.28 E298CD 0.25 /A258 0.22 /A260 0.22 /A262 0.22 /A265 0.22 /P268 0.22 E298ZD 0.22 /A258 0.22 /A260 0.22 /A262 0.22 /A265 0.22 /P268 0.22 E298ZD/P116 1.56 P254 all 0.23 E299DH 0.72 /P230 0.72 /P120 0.92 VA1033/34/38/ 1.26 39/40/53 all 0.20 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.20 VA1103 0.32 VA1104 0.72 VA1108/09/10/ 11/12 all 0.24 VA1055/56/66/ 1.80 67/5 all 0.23 VA1074 0.20 VA1077 0.31 VA1091 0.29 VA1096/97/ 98 all 0.	
---	--	---	--	---	--	---	--	--	--	---	--	--	--	---	--	---	--	---	--

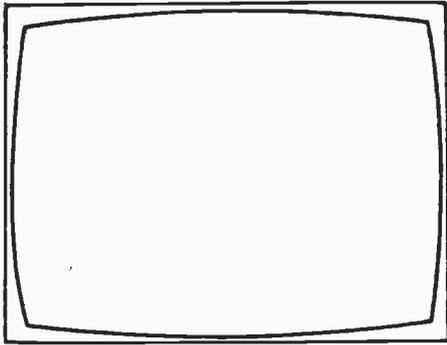

TELEVISION

EDITOR

John A. Reddihough

ADVERTISEMENT MANAGER

Roy Smith
01-261 6671

CLASSIFIED ADVERTISEMENTS

Barbara Blake
01-261 5897

COVER PHOTO

Our cover photo this month shows the Frowds Surveyor VI CCTV camera with the covers removed. The Surveyor VI is a versatile, fully weather-proofed camera with circuit refinements to maintain the performance over a wide range of lighting conditions. It's designed for continuous unattended operation in industrial or open-air environments. Our thanks to Frowds Ltd., 4 Northarbour Road, Cosham, Portsmouth, Hants PO6 4TJ.

VIDEO SERVICING

Mike Phelan's Video Servicing feature will be resumed next month.

PIN CONNECTIONS

The pin connections for the LM324 i.c. (Fig. 4, page 658) were omitted last month. Pin 4 is the supply input and pin 11 chassis. Gate one's connections are pin 1 output, 2 - input, 3 + input.

TEST PATTERN GENERATOR

We have been asked to make it clear that the cost of the set of preprogrammed EPROMs for the Test Pattern Generator project (May-September 1984) from JRW Developments is £29 inc. VAT - this is for the four 2532s, not three as stated in the article. This price will be held while stocks last. It may be necessary to increase the price at a later date.

Whatever happened to Prestel?

Well it's still going, just about, but has hardly made the impact the Post Office expected when it started the service five years ago. The original plan was for some 100,000 installations during the first year, with escalating growth thereafter. Had all gone well we might have seen say two million installations after five years. The actual figure is some 45,000. Whatever went wrong?

Prestel arrived at the time when Information Technology was considered to be the thing of the moment. We were entering an information orientated society. Or so some dreamers thought. We would soon have vast amounts of information at our fingertips and the availability of this information would change our way of life. You can make out a case for this. If you're in the market for a house or a car for example, wouldn't it be nice to dial up the details of what you want and can afford and have the relevant items on offer flashed on the screen before you? No more trudging between estate agents and car dealers.

Yes indeed, but how often do you buy a house or a car? Not all that frequently. So the expensive system sits there awaiting its occasional use. Ah, but then there's the weekly shopping, banking, and all that other information for one's use. Banking maybe. The dreary procession to the bank to then stand around in a slow-moving queue is something we could all do without. Except that the banks have already moved to change that, with their cash dispensers, credit cards and so on. Shopping? A failure of psychology here. Yes, it would be nice to go out armed with a list of keenest prices and special offers, but the idea was that you'd do it all by dialling from home. Shopping however is part of a way of life. A chance to get out and look around. Meet a few people and get up to date with the local gossip. The better retailers know all this and have put a lot of thought into shop layout and presentation, to their own benefit and it seems to the public's approval. I wouldn't care to say how many times over the years I've read articles suggesting that the end of department stores and Oxford Street is imminent. Yet people still flock to Oxford Street, stores are full, and it's likely that this will continue for many years to come. Shops may theoretically be a rather inefficient mode of goods distribution, and can be frustrating and time wasting. But to get in amongst the goods, to see and sample what you want, is more attuned to human needs than dialling up for a printout on the screen.

If what you're after is impartial guidance in the home, then *Which?* does a far better job. And here you have another point that was overlooked by the information technology enthusiasts. We were assured that the printed word would soon be a thing of the past. Information would be provided by computers rather than journalists, and would be dialled up instead of being typeset, printed and carted around in the form of great bundles of paper. How inefficient! Yet in practice the printed page is a far more appropriate means of presenting information than the TV screen. Just compare the amount of information you can get into a page with what you can get on to a TV screen. Then you can flick through a paper, magazine or book, which will hopefully be presented in a logical form to assist with the information seeking quest. You can go back to the bit you were unsure about - or the point where you fell asleep! If you buy a publication regularly you know what to expect and how to use it. Information held in a computer is a rather different matter. You've got to know exactly what you want at the outset, then you've got to know how the computer stores it, i.e. how to ask the computer for what you want. Prestel involves a rather laborious search system for getting the information out - always assuming that it's there to start with. And going through the procedure can be expensive and time consuming.

Which brings us to cost, another drawback with Prestel. The information and the equipment to get it don't exactly come cheap. So interesting the public in it involves the hard sell. The PO, more recently British Telecom, haven't been exactly successful here. But then the public is rightly suspicious of new ideas and services, and is generally conscious of prices and value for money. Information as a cold collection of facts is hard to sell. How do you convince the man in the high street that he's starved of information? How do you go about selling him a databank he doesn't understand let alone feel a need for?

The basic problem with Prestel has been its blunderbuss approach. Trying to sell to the public at large something as unspecific as "information" is hardly likely to be a success. It seems that Prestel has learnt this lesson and that the sales pitch will in future rely on selling specific information to identified markets - a recent example of this is the Farmlink service. But even here it will meet with strong competition from the established information providers - the specialist press, which has been a growth area of publishing in recent years. Back to the point that the printed page can do it better!

Prestel has been a failure as a mass information service, though there's reason to feel that it may have a viable future as a provider of specialised information. To overcome the problem of the cost of equipment - a classic chicken-and-egg situation - it might be better to have Prestel available in the high street for use when it's wanted, which for most people would not be very often. You could then go along to get the information you want when you want it. True this is not the armchair access concept that was fundamental to the original idea of viewdata. That might come later if and when the cost of the technology falls dramatically. What in fact went wrong with Prestel was that the idea and the technology arrived before its usefulness could be properly assessed.

Variable IF Sound Channel

Hugh Cocks

Satellite TV transmissions use a variety of frequencies for the associated sound channel, the sound subcarrier frequency varying between 5.5MHz and 7.5MHz (see Table 1). Since there's no standard frequency, reception calls for a tunable demodulator with high sensitivity – especially with the new 11GHz services. Good sensitivity is a must as the sound subcarrier that accompanies the f.m. video is generally transmitted at a reduced level: as often as not the whole transmission is weak, which can lead to buzzing and noise if the input preselection and gain are not all they could be.

Basic Design

The sound channel described in this article uses a TDA1190Z i.c. which in addition to the demodulator includes an audio amplifier. The advantage of this is a low component count. Other intercarrier sound i.c.s such as the TBA120 should work just as well with the same tuning and preselection arrangements. A Philips G8 chassis sound selectivity module is used for input tuning: it's still available cheaply and is simple to modify for external tuning with varicap diodes. The module can easily be mounted on the PCB that holds the demodulator i.c. As a bonus, the quadrature coil for the i.c. consists of a redundant coil removed from the module. The circuit can also be used as a 4.5MHz-6.5MHz terrestrial TV intercarrier sound channel with no problem. If reception of only part of the band is required, e.g. Gorizont 7MHz and 7.5MHz, or the 6.5-6.8MHz range, ordinary low-capacitance swing v.h.f. tuning diodes such as the BB103-BB109 series can be used. If the full band is required, h.f. tuning diodes such as the KV1235 must be used. These are available from Ambit International.

The Selectivity Module

The original circuit of the Philips U500 sound selectivity module is simple (see Fig. 1). The output from the video detector enters at pin 4 and is then split two ways, going to the base of the BF194 transistor (some units use equivalents) and via L3 to pin 5 (feed to the video processing chip in the G8). When used in the G8, the chroma signal is taken from the emitter of the transistor, via pin 8. L1, L2 and the associated components form a top-capacitance coupled bandpass tuned circuit for the sound signal which is tapped from the junction of C2, C3. A 12V supply is fed

in at pin 2: pins 3, 6 and 7 are connected to chassis.

Since the chroma output is no longer required, the gain of the unit can be increased by decoupling the transistor's 560 Ω emitter resistor. A 100pF decoupling capacitor, connected from pin 8 to chassis, seems to provide optimum results – a higher value causes buzzing on sound, probably due to the chip being overloaded. The capacitor can be fitted on the print side or, more elegantly, on the main board.

Coil L3 and its associated tuning capacitor are removed from the board. This leaves pin 5 free, which is useful for feeding in the tuning voltage. When 30 turns have been removed from L3 it can be used as the quadrature coil. Do this carefully, ensuring that there's a good soldered joint on the securing pin when the unwanted turns have been removed.

If the full range is required, using h.f. diodes, remove C1 and take eight turns off each side of the centre-tapped coil L1 (16 turns in all). Solder 0.0047 μ F (nominal) d.c. blocking capacitors to each side of the coil with a varicap diode between – see Fig. 2. The 100k Ω (nominal) d.c. feed resistors can go straight into the holes left by L3 and its associated capacitor. Ensure that the diode is inserted the right way round or very odd tuning effects will cause head scratching later. If only partial coverage is required, using v.h.f. diodes, leave C1 in circuit but remove the same number of turns from L1.

Remove 20 turns from L2 and change C2/3 to around 82pF each (leave at 270pF with a v.h.f. diode). Since one side of this coil is connected to chassis only a single feed resistor and blocking capacitor are required. The tuning feed for the diode used with this coil has to come a little way over, either from the same point as the resistor going to D1 or from the hole left by L3's tuning capacitor. Mount the resistor by the diode and run a wire over to the d.c. input point.

The tuning diodes can be tucked in neatly by the coils so that the original can just fit over – if you can get one (most have long gone unfortunately). Be very careful not to short anything out. When removing the coils for modification be careful not to peel the print – this is easily done. When resoldering, ensure coil d.c. continuity at the print itself to avoid problems later. Also double check that the d.c. feed resistors are of high value (100k Ω or more) as odd effects will occur if the tuned circuits are accidentally damped by using a low-value resistor. The modules themselves are reliable. The worst problem is hairline cracks at points of most mechanical stress. On one occasion a noisy transistor had to be replaced.

Demodulator/AF Circuit

The demodulator/a.f. circuit is conventional, see Fig. 3. Be careful with the layout if using Veroboard etc. as instability may arise. Ensure that after modification the quadrature coil has d.c. continuity or weak hissing will be noted at low volume settings – with everything cutting out at normal levels! The Philips quadrature coil is best glued to the board vertically, with short leads (use resistor offcuts) taking the connections through. There's provision

Table 1: Satellite sound subcarrier frequencies.

Gorizont (Russia) 7MHz, 7.5MHz.
US Forces TV 6.8MHz (low-deviation radio channel around 6MHz).
TV5 (France) 6.6MHz (wide deviation).
RAI (Italy) 6.6MHz.
Teleclub (Switzerland) 6.5MHz, 5.5MHz (unused at present).
Intelsat services 6.6MHz, 6.65MHz.
Argentina 6.3MHz.
Libya 6.2MHz.
Spain 6.6MHz, 6.65 MHz.

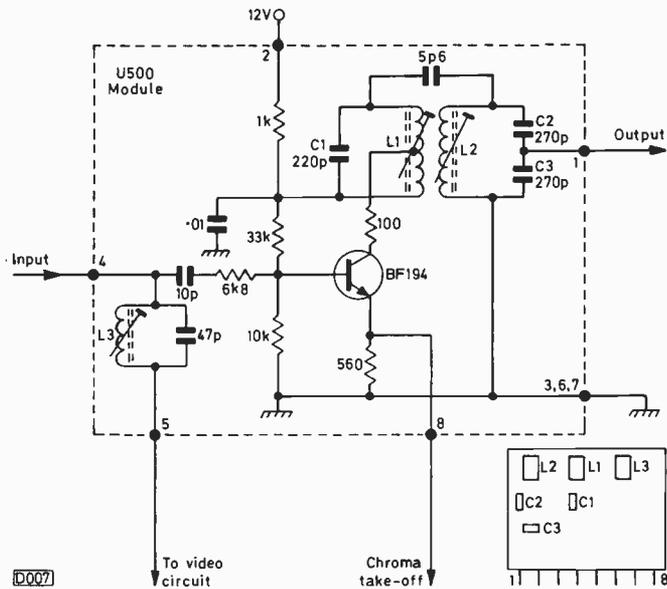


Fig. 1: Circuit of the U500 sound selectivity module.

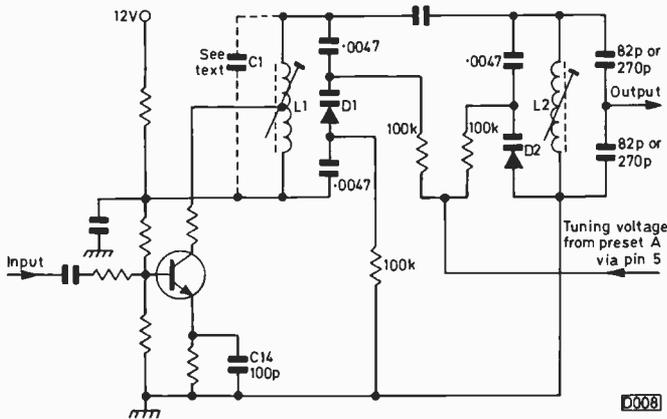


Fig. 2: Selectivity module after modification.

on the board (Fig. 4) for the coil to lie horizontally, but this makes access to the core difficult. The speaker coupling capacitor C4 can give rise to instability at highish

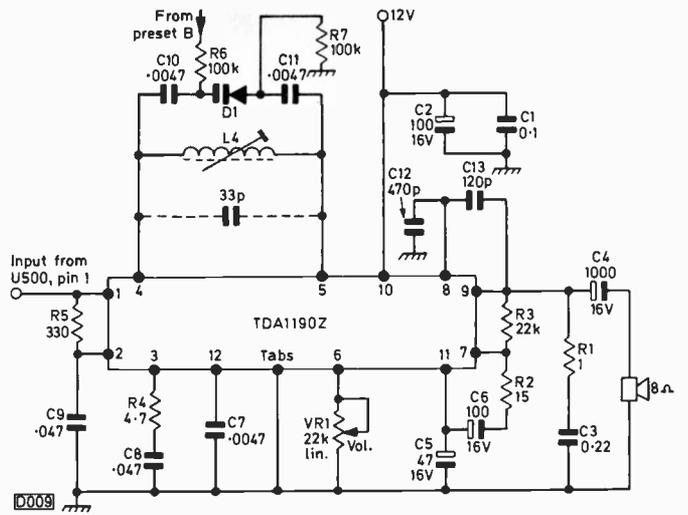


Fig. 3: Demodulator and a.f. circuit.

volume (screeching). C3 in the Zobel network across the speaker can do similar things – without this network virtually nothing occurs apart from low-level buzzing.

There's no damping resistor across the quadrature coil as the audio seems to be better without one, probably due to the *Q* being lowered a little by the diode. If the audio is a little distorted or a diode is not going to be used (fixed tuning) a damping resistor can be added. Start with 10kΩ and reduce the value till distortion is no longer heard. Add a 33pF tuning capacitor when using a v.h.f. diode.

The resistors are all 0.25W types. Note that with some i.c.s there's weak sound at minimum setting of the volume control and that volume increase is very sudden when the control is advanced. Top and bottom presets may be a good idea here. If a u.h.f. modulator or TV monitor that requires a low-level input is to be used, turn the volume control setting down a little.

The PCB has space for four presets to enable two sound channels to be switched by means of a front-panel mounted rotary switch (see Fig. 5). Modification for continuous tuning is simple. Don't link A to B, and solder in only two presets, one for quad coil tuning and the other

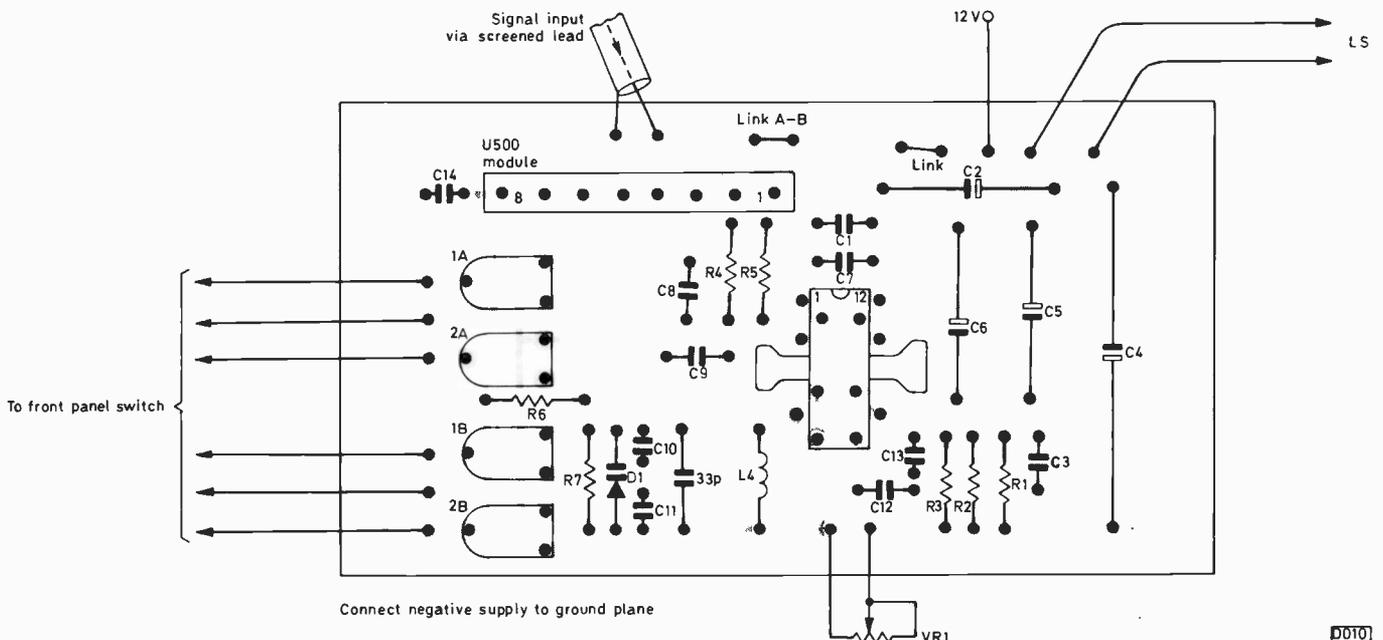


Fig. 4: Component layout. The components are mounted on the groundplane side of the board. Board actual size.

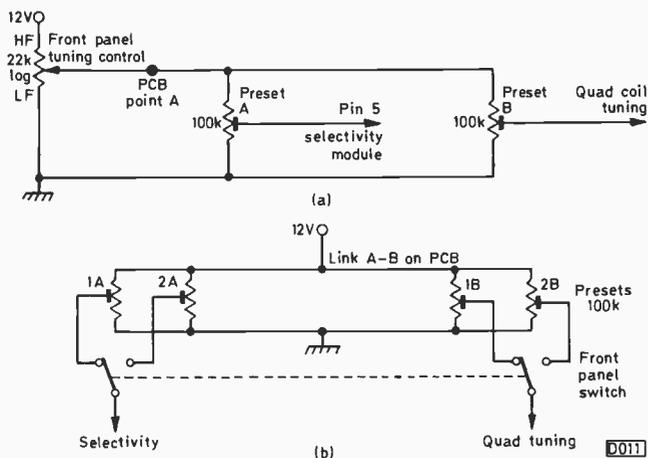


Fig. 5: Alternative tuning arrangements. (a) For continuous tuning, (b) for two-position switched tuning.

for selectivity. Wire the outputs into the tuning voltage inputs. Use a front panel potentiometer for tuning – link the 12V supply to this and take the slider back to point A on the board. The presets then serve for tracking.

Testing and Setting Up

Before trying the unit out, check that the tuning voltage is reaching the diodes and that they have been inserted the right way round. Turn up the volume and check that a good hiss is obtained without squegging/instability at high volume. If this is heard check the components previously mentioned. Tuning across the band will probably produce some noise variation. In the absence of a signal generator or satellite signal, connect a 6MHz UK sound TV signal and see that the tuned circuits peak up well.

To some extent the setting of L2 is not critical. The diode appears to make a difference only at the top end of the band, above 7MHz. Indeed a low-swing v.h.f. type can sometimes be better. The h.f. types are sold in blocks of three however, so it may be best to experiment. Tuning below the 6MHz UK signal will reveal the PAL subcarrier at 4.43MHz as a distinct buzz at one point. The voltage required to go from 4.5MHz to 7.5MHz is rarely more than 4.9V, so limiting presets in series with the tuning potentiometer may be useful.

To set up on Gorizont, ensure a “smooth” transition from the 7MHz TV sound channel to the 7.5MHz radio channel with no background from the unwanted subcarrier. With BB103s used to tune from 7MHz to 7.5MHz the action of the quadrature coil diode will be very sharp with only a small voltage change, but the preselection diodes will require virtually the full 0-12V swing, so set the 7MHz preselection preset to zero volts and peak L2 and L1, then adjust the 7.5MHz preset for best signal, again with no background from the 7MHz channel (easy to get with the tracking slightly off). Note that the Gorizont audio always sounds slightly distorted due to the pilot tone compression system used (for an expansion circuit, see Nick Harrold’s article in the December 1983 issue).

The 6.5-6.8MHz subcarriers from other satellites are easily tuned in and there’s no compression to worry about. Indeed one service promises stereo sound using a multiplex system by the time this is read. The unit should be highly sensitive with 4.5MHz (ever hopeful in the UK!), 5.5MHz and 6.5MHz terrestrial DX signals.

The board can be installed in the TV set, taking the

place of the existing sound circuits. Ensure that the feed to the old circuit is removed or some loading may occur at 6MHz, causing loss of sensitivity.

On very marginal signals the use of a phase-locked loop detector circuit can be an advantage (see page 85, December 1983) – it can be preceded by the modified selectivity module – though one has to say that the difference is not very great in practice unless the deviation is restricted (as can happen with certain American signals). In this case the quadrature circuit will produce a lot more noise.

Component Sources

The KV1235 varicap diodes are described as “triple a.m. tuning” types and are available (order code 12-12355) from Ambit International, 200 N. Service Road, Brentford, Essex CM14 4SG at £2.75 plus VAT for three. Range is 30-450pF from 8-2V. Check the cathode/anode connections with a meter – the body indication is vague. Sendz have a good stock of the obsolete BB103 type (cathodes banded). The BB109 type (15-42pF nominal) is available from Ambit (order code 12-01095) at 27p each plus VAT (cathodes banded). U500 selectivity modules are available from Manor Supplies (probably without can) at about £3 each tested. Ready etched boards can be supplied by Hugh Cocks TV Services, Cripps Corner, Robertsbridge, Sussex. Made up units may be available.

My thanks to Dave Lewis for his assistance with the experimentation and in developing the unit.

CRT Tester/Booster

Jim Littler

This simple unit was designed to test and reactivate tubes. It’s cheap to make and simple to use. The mains transformer was taken from a scrap Decca Bradford chassis.

In the test position the grid and cathode of the gun being checked are connected to chassis while some 60V is applied to the first anode. The meter (0.5 or 1mA f.s.d.) indicates the current flow, which for a good gun should be about 100µA.

In the reactivate mode h.t. is applied to the relevant grid while the cathode is connected to chassis. The current flowing via the cathode-grid “diode” will light the pygmy bulb L1 (240V, 15W). When the “diode” conducts, the dead coating is stripped from the cathode. As a result cathode emission is increased – this can be confirmed by switching to the test position. Never reactivate for more than five seconds. Don’t try a second reactivation or the tube could die a violent death.

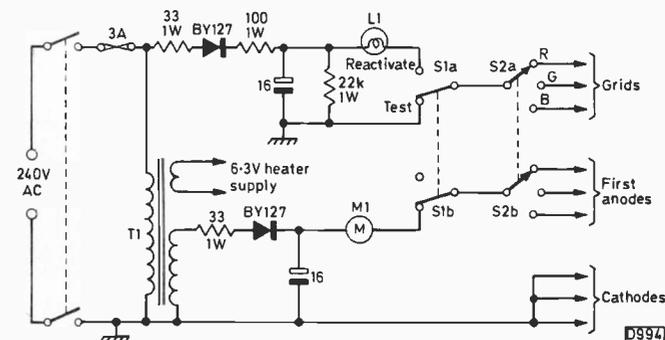


Fig. 1: C.R.T. tester/booster circuit.

POST A PART ELECTRONICS

236 FURTHERWICK ROAD,
CANVEY ISLAND, ESSEX
Telephone 0268 690868
Telex 99305 ROSSER G.



TRADE COUNTER NOW OPEN

ORDERS DESPATCHED SAME DAY
ADD 60p P&P, THEN 15% VAT.
ADD POSTAGE FOR OVERSEAS ORDERS.
ORDERS WITH AEROSOLS, PLEASE ADD 25p PER CAN.

Thorn 10Q 20W (3500) R751 Safety Resistor	75p
Pye 713 Speaker 5" x 3" 70Ω	1.00
Pye 713 Complete Tube Base Panel with Focus Slider & Leads	2.75
Pye 713 Control Knobs	4 for 50p
Tube Base Socket ITT CVC32	45p
Tube Base Socket Thorn 3000/8000 etc	50p
IC Inserter 16 Pin	50p
Large IC Extractor	50p
Crystal 4.33MHz	65p
EHT Lead & Cap for Split Diode Lopt	90p
Anode Cap	47p
Sanyo Anode Cap Assy + Lead, 12TCD-CT-16	65p
Deausage Thermistors, PT37P, ITT/GEC	35p
Deausage VDR E299D/HP230 3000/8000	25p
Casters Set of 4	1.90
Double Fuse Holder on Small Pax Board 20mm type	10p
Single Fuse Holder on Small Pax Board 20mm type	5p
Direct Panel Mounting 20mm Fuse Clips	(pair) 15p
Single Fuse Holder on Small Pax Board, As per early 3000 mains input	6p
EHT Cable	Metre 25p
13A Plugs	12 for 4.80
BF259 with Heatsink	14p
TIP110 with Heatsink	40p
LI29/130/131 Coil	10p
8MHz Ceramic Filter	25p
DL700 (Philips) Chroma Delay Line	1.00
DL500 Chroma Delay Line	1.00
T9006A Lum Delay Line	1.00
8K5 Lum Delay Line	1.00
Plastic Cover for 3K5 SP8385	65p
TX9 Back Ground Control 10K	15p
TX9 Gen Control 100R	15p
1500 Metal Chassis Supports Pair	40p
Thorn 8K5 Focus Pot	2.40
Thorn 4000 Focus Pot	2.75
Thorn 18Q 9W (3K5) R752	30p

SERVICE AIDS	
Ambersil MSA Silicone Grease	12oz 2.15
Ambersil Freezer	12oz 1.99
Ambersil Amberlube	6oz 1.89
Ambersil Ambertron	16oz 1.95
Ambersil Anti-Static Screen Cleaner	7oz 1.95
Ambersil 40+ Protective Lubricant	14.1oz 2.15
Ambersil Amberclens Foaming Cleaner	13oz 1.26
Ambersil Circuit Lacquer	14oz 2.15

THICK FILM RESISTOR UNITS	
3500 Thorn (5 Pin Connection) video	1.70
4000 Thorn (4 Pin Connection)	1.90
725/731 Pye (6 Pin Connection)	2.20
713 Pye (6 Pin Connection)	2.20

FUSES			
50MA	20mm	14"	
315MA A/S	10 for 70p	250MA	10 for 65p
500MA	10 for 50p	750MA	10 for 65p
1A	10 for 50p	7A	10 for 50p
2.5A	10 for 1.00	10A	10 for 50p
3.15A	10 for 1.00	20A	10 for 50p
		50A	10 for 50p

Thorn Mains TX 3000/3500	7.50
Thorn Mains TX 8000/8500	10.00
Thorn S.O.P.T. 8000/8500	3.50
Thorn Scan TX 3000/3500	6.00
Thorn EHT TX 3000/3500	6.00
Thorn LOPT 9600	12.00
Thorn LOPT 1615	7.25
Thorn LOPT 1590/91	7.25
Thorn LOPT 1690/91	7.25
Thorn LOPT 8000	9.00
Thorn LOPT 8500	9.80
Thorn LOPT TX9	9.80
Pye LOPT 713	10.00
Pye LOPT 725	9.85
Pye LOPT 731	10.18
Philips LOPT G9	8.80
Philips LOPT G11	13.75
GEC LOPT 3113	7.40
Diode Split LOPT AT2076/35	14.75
Sanyo LOPT AM-WM-21	6.75
Sanyo LOPT AM-WM-4	7.30
Philips LOPT G8	7.80
Sanyo LOPT (CW21) 4-2751-44700	5.00
ITT LOPT CVC5-9	9.60
ITT LOPT CVC30	8.75
ITT LOPT CVC45	8.75
Baird 8750	10.25
Baird 8752	10.25
Korting AZ9100	10.25
Korting BS2-170	10.25
Korting AZ2101	10.25
Korting AZ2103	10.25
Korting ZTR1001	10.25
Siemens V1155	11.75
Siemens V1823	11.75
Zanussi BS2222	10.25
Zanussi BS2223	10.25
Salora FR057	10.25
Salora FR029	10.25

300 Mixed Resistors	1.50
300 Mixed Capacitors	1.50
150 Mixed Electrolytics	2.00
100 W/W Resistors	1.00
20 Mixed Conv Pots	1.00
40 Mixed Pots	1.50
20 Mixed Sliders	1.00
40 Mixed Presets	60p
20 Mixed VDR & Thermistors	1.00
20 Mixed Ferrite Cores	50p
100 Mixed Ceramic Discs	1.00
20 Mixed Valve Bases	1.00

AC128	39	BC172	9	BC569	8	BF173	24	BFR62	28	NKT276	20
AC131	40	BC174B	23	BC595	8	BF179	29	BFR81	29	NKT453	1.65
AC138	40	BC177	24	BCK33	8	BF180	32	BFR80	25	OT112	1.92
AC141K	39	BC182LB	12	BCX34	22	BF181	30	BFR91	1.74	OT121	2.08
AC142K	38	BC183L	12	BD115	11	BF184	30	BF142	30	R1039	80
AC153	39	BC184L	13	BD131	49	BF185	30	BF243	30	R2008B	1.40
AC176	33	BC187	24	BD132	46	BF196	16	BFY30	40	R2010B	1.10
AC176K/		BC204	15	BD133	59	BF196	16	BFY51	34	R2265	1.30
AC128K	93	BC208	9	BD139	36	BF197	15	BFY52	34	R2305	80
AC188	38	BC212L	9	BD140	38	BF198	19	BR116	1.50	R2322	50
AD142	1.18	BC213L	12	BD144	1.70	BF199	15	BR193	1.43	R2443	25
AD143	1.08	BC237	12	BD150	50	BF223	18	BU105	1.00	RCA16445	30
AD149	98	BC238B	8	BD153	98	BF224	19	BU126	1.10	RCA16589	30
AD161	32	BC238L	8	BD201	74	BF238	20	BU207	1.05	RCA16600	1.40
AD182	32	BC250A	15	BD203	78	BF240	9	BU208	1.15	RCA16799	1.13
AD263	1.05	BC251	8	BD204	99	BF241	21	BU208A	1.15	RCA16800	1.42
AF127	45	BC252A	20	BD222	48	BF256	10	BU326A	1.30	RCA16802	1.38
AF139	38	BC294	37	BD225	52	BF256S	20	BU407	1.70	S1299	2.25
AF239	41	BC301	32	BD232	50	BF257	28	BU408	2.76	S28000	1.25
BC107	15	BC303	31	BD233	60	BF259	28	BU500	2.30	S6080A/B	3.50
BC108	15	BC307	10	BD234	60	BF271	25	BU520	2.46	T6050V	1.30
BC109	15	BC308	8	BD237	55	BF274	11	BU607	2.84	T6052V	1.30
BC115	16	BC309	14	BD238	65	BF337	29	CI129	9	T9039V	1.25
BC117	21	BC327	18	BD241	59	BF338	34	CI172B	9	T9010V	1.45
BC125	26	BC328	18	BD244	85	BF355	40	ES325V	54	T9032V	1.50
BC126	23	BC327	17	BD278A	81	BF362	50	E9003	28	T9054V	1.00
BC139	27	BC338	17	BD386	68	BF391	21	E9005	25	T9039V	1.10
BC141	34	BC347	8	BD433	71	BF394	16	ME0404	10	TIC45X	50
BC142	30	BC394	8	BD437	83	BF422	47	ME0412	10	TIC46	48
BC143	31	BC454	8	BD589	1.20	BF423	53	ME6002	10	TIC106C	40
BC147	12	BC455	8	BD592	1.20	BF450	43	MJ2501	2.36	TIP29	42
BC148	12	BC456	10	BD677G	1.35	BF453	53	MJ3001	2.21	TIP30	42
BC149	12	BC460	40	BD707	95	BF458	37	MJE182	47	TIP31	35
BC153	16	BC463	22	BD708	95	BF459	40	MJE340	50	TIP32	43
BC1540R	16	BC546	8	BDX10	93	BF461	59	MJE520	50	TIP33	61
BC154YL	16	BC547	12	BDY20	1.09	BF568B	35	MJE2855	1.50	TIP41	42
BC157	12	BC548	12	BDY62	99	BF596	15	MJE3065	1.50	TIP42	61
BC158	12	BC549	8	BF137	81	BF598	16	NKT241W	8	TIP110	61
BC159	15	BC557	10	BF153	20	BF757	62	NKT241G	8	TIS91	25
BC171	9	BC558	10	BF154	25	BFR52	31	NKT241Y	8	ZTX550	30

INTEGRATED CIRCUITS							
BRC1330	1.40	SN76013ND	1.80	TBA530	1.26	TDA2002	2.80
BRC3064	1.00	SN76023N	1.80	TBA540	1.00	TDA2030	2.10
BRC/M/200	1.00	SN76033N	2.00	TBA5500	1.82	TDA2522	2.10
BRC/M/300	1.00	SN76115	2.00	TBA5600	1.50	TDA2530	2.61
CA3060	1.58	SN76131N	1.58	TBA641	2.05	TDA2540	3.50
LM1303P	1.48	SN76226N	1.25	TBA720A	2.50	TDA2560	3.00
ML231B	2.20	SN76227P	1.00	TBA750	2.49	TDA2581	3.50
ML237B	2.00	SN76530P	1.30	TBA800	2.20	TDA2611A	1.95
ML239B	2.86	SN76622N	1.00	TBA810S	1.62	TDA2640A	2.90
MC1327AP	1.25	SN76660N	80p	TBA810AS	1.00	TDA2690A	1.50
MC1358P	1.30	SN76666N	75p	TBA920	1.00	TDA3560	6.00
MC1455P	18p	SN76744	1.82	TBA950	2.08	TDA9503	2.90
MC14516BCP	60p	TA7117P	1.00	TBA1440	1.95	TCEP100	3.48
SA41025	7.20	TA7109AP	1.00	TCA270SA	1.92	TEA1009	1.95
SA41124	4.50	TAA611	1.40	TCA270C	1.05	MC14426P	4.50
SA45010	6.00	TBA120B	1.20	TCA270CQ	1.05	MC14514	5.00
SL432A	1.80	TBA120C	1.20	TDA1004A	4.00	UA758CP	2.66
SL1430	2.50	TBA120CQ	70p	TDA1035T	3.50	ULN2165	1.30
SN15846N	60p	TBA120S	70p	TDA1037	2.72	ULN2216A	1.25
SN74123N	65p	TBA120U	1.00	TDA11705	1.50	UPC1365C	5.75
SN74154N	1.40	TBA395	1.00	TDA1200	2.42	SC9488P	1.40
SN76001N	1.40	TBA480Q	1.40	TDA1270	2.76	SC9511P	1.40
SN76110N	1.14	TBA510	1.90	TDA1327	2.53	SW153	2.50

Thorn 8/8K5 ex equip panels	untested	Thorn 3/3K5 ex equip panels	untested	Thorn 4000 PSU panel ex-factory	2.50
PSU	2.88	PSU	3.75	Thorn 3K5 beam limiter board	1.75
FTB	3.75	LTB	3.75	new	1.75
Decoder	4.00	Video	2.50	Thorn 3K5 PSU bottom board	2.75
		Chroma	2.00	PC206 new	2.75
Thorn 9K ex equip panels	untested	FTB	2.75	Thorn 3K5 IF panel new	3.00
PSU	12.00	Conv. 3K	1.75	Thorn 3/3K5 EHT & scan TX +	1.80
Decoder	5.00	Conv. 3K5	3.00	R2008B on alum chassis ex-equip	3.75
		Autovox Decoder FG/01 new	5.00	Thorn 8/8K5 damaged FTB for spares	1.25
Thorn 9K6 ex equip panel	untested	boxed	5.00	Thorn 8/8K5 damaged decoder	2.25
Decoder	5.75	Thorn 4000 Convergence panel ex-factory	3.75	for spares	

10 Spark Gaps	1.00
10-16 pin Quil IC Socket	90p
20 Assorted TV Knobs	1.00
10-16 pin Quil to Dil IC Socket	90p
100 Mixed Diodes	1.00
50 Mixed Mica Washers	65p
300 Mixed Resistors & Capacitors	1.50
10-16 pin Dil to Dil IC Socket	1.00
50 Electrolytics & 50 Capacitors	1.00
50 Mixed Poly Capacitors	1.00
30 Mixed Neons & Bulbs	1.00

BF167	24	BFR62	28	NKT276	20
BF173	29	BFR81	29	NKT453	1.65
BF179	32	BFR87	25	OT112	1.92
BF180	33	BFR90	1.74	OT121	2.08
BF181	30	BFR91	2.08	R1038	80
BF184	30	BF142	30	R1039	80
BF185	30	BF243	30	R2008B	1.40
BF196	16	BFY30	40	R2010B	1.10
BF196	16	BFY51	34	R2265	1.30
BF197	15	BFY52	34	R2305	80
BF198	19	BR116	1.50	R2322	50
BF199	15	BR193	1.43	R2443	25
BF223	18	BU105	1.00	RCA16445	30
BF224	19	BU126	1.10	RCA16589	30
BF238	20	BU207	1.05	RCA16600	1.40
BF240	9	BU208	1.15	RCA16799	1.13
BF241	21	BU208A	1.15	RCA16800	1.42
BF256	10	BU326A	1.30	RCA16802	1.38
BF256S	20	BU407	1.70	S1299	2.25
BF257	28	BU408	2.76	S28000	1.25
BF259	28	BU500	2.30	S6080A/B	3.50
BF271	25	BU520	2.46	T6050V	1.30
BF274	11	BU607	2.84	T6052V	1.30
BF337	29	CI129	9	T9039V	1.25
BF338	34	CI17			

MANTEL

Manchester's No. 1 in Ex-Rental TVs
Over 2,000 TVs in stock
Special Offer on Working Colour TV's

All sets are Serviced with repolished cabinets ready for sale

Some Examples of UNTESTED TVs available

Philips G8 550s 22/26 £45
 Philips 18" £40
 Philips G8 520s 22/26 £35
 GEC S/State from £35
 Thorn 17" 8000 £30
 Decca 30 18/20/22/26 £30
 Japanese from £30
 Many other makes available from £25

Thorn 10 for £125
 Philips 6 for £90
 Bush 6 for £80
 GEC 6 for £60
 Decca 6 for £60
 Mono TVs avail. s/s £4 each
 New TV trolley stands.
 All sizes £4.95
 All Prices subject to V.A.T.

Discount on quantity

Ex Equipment Panels & Tubes Available

Deliveries may be arranged to the North and Scotland.

Ring for quote. Callers welcome.

419 Barlowmoor Road, Chorlton, Manchester 21 2ER.
Tel: 061 861 8501

TELEPART

Telegen-1

- PRICE £17.20 (Inc. VAT)
 * EXCEPTIONALLY LIGHT AND DURABLE
 * POCKET SIZE FOR OUTSIDE SERVICE
 * PP3 BATTERY POWER SOURCE
 * FIVE DIFFERENT TEST PATTERNS FOR COLOUR & MONO TV
 * CROSSHATCH GRID * DOT MATRIX
 * WHITE RASTER
 * HORIZONTALS * VERTICLES
 * 3.5mm JACK SOCKET FOR OPTIONAL P.S.U.



A lightweight, extremely portable and versatile pattern generator for black/white and colour T.V. alignment and service at the customer's home. At the turn of a switch, the generator can provide five essential test patterns for correct installation, fast checks and repairs. Pattern stability is first class and compares favourably with other more costly bulky generators only suitable for bench work. The generator is pocket size measuring 10x 7.5x 4 cm and weighs only 190 grams. Switched 3.5 mm jack socket allows use of external power supply with battery in situ.

Telegen-2

- PRICE £34.45 (Inc. VAT)
 * EXCEPTIONALLY LIGHT & DURABLE
 * COMPACT 10 x 12 x 4.5 cms
 * RED RASTER * GREEN RASTER
 * BLUE RASTER
 * COLOUR BARS
 * 3.5 mm JACK SOCKET FOR P.S.U.
 * PROVIDES UHF SIGNAL APPROX. CHANNEL 35



Telegen 2 is a colour bar generator at a very modest price and yet is extremely effective, stable and durable. It is the perfect compliment to Telegen 1, giving colour bars arranged in the following sequence: white, yellow, cyan, green, magenta, red, blue and black. The unit provides a signal in the UHF band approx. Channel 35 and requires a supply of 14 to 18 volts 0.C.

Power Supply

A switchable power supply ideally suited to both Telegen 1 and Telegen 2.

PRICE £4.55 (Inc. VAT)

POST AND PACKING £1.44 (Inc. VAT)

32 TEMPLE STREET, WOLVERHAMPTON
WV2 4AN. TEL: (0902) 773122

ATTENTION!!!

CHROMA VISIONS OFFER TO THE EXPORT AND HOME MARKET

We have a large quantity of GEC CTV's, UHF and VHF, all in excellent working condition, with excellent tubes and cabinets. No tubes are boosted. Also in stock are brand new, boxed, TV and Video Stands from £4.00 each. TV sets ideal for rental or retail market.

Enquiries please ring:

021 784 2561

811A Ashwood Heath Road, Birmingham.

P.S: WE DO NOT SELL ANY RUBBISH

2 YR. GUARANTEE APOLLO 20/30 AX

TRADE AND QUANTITY DISCOUNTS

FREE LOCAL DELIVERY — SAME DAY • FITTING SERVICE £20.
 FAST MAIL ORDER GB 2-3 DAYS — OVERSEAS ON REQUEST.

A47 32/343X 470 BCB22	£37
470 ESB22/EFB22/ERB22	£45
A51-161X	£45
A51-220X/192X	£37
510 JKB22/JEB22/JDB22/ALB22	£45
A56-120X/123/140/410	£38
560 DZB22/HB22/AKB22	£45
A63-120X	£39
A66-120X A67-120X/140/150/200X	£39
20AX A56-500X/510X A66-500X/510X	£48
30AX A56-540X/A66-540X	£48

If your tube type is not in stock we can arrange collection - rebuilding + redeliver

PLEASE PHONE BEFORE CALLING

061-799 0854. 24 hour answering service

43 Clarke Crescent, Little Hulton, Worsley, Nr Manchester M28 6XL

Grundig's VHS Machine

— Model VS200

Steve Beeching, T. Eng.

At last we have a truly European VHS machine, not one designed in Japan or built from a Japanese kit of parts. It's typically Grundig and looks like their 2080 V2000-format machine — in fact it appears to be a VHS machine built into a V2000 chassis. The systems control and power supply arrangements are thoroughbred Grundig designs developed from the previous machines. The new sections, new to Grundig that is but familiar to many of us, are the VHS parts, but even these are more characteristic of Grundig than the Nipponese.

It was strange to see the V2000 machine's tape transport system with its U-wrap mechanics re-engineered to the VHS tape track standard. A new set of i.c.s has been developed by Grundig and Mullard. These are as follows: TDA3750 colour a.f.c. and phase-locked loop; TDA3760 VHS colour record/playback processor; TDA3771 video signal switching and level clamping; TDA3780 VHS f.m. modulator.

Tuning is similar to that used with current Grundig TV sets — auto search and store or select the programme number and punch in the u.h.f. channel number. So that programmes can be monitored, the machine will produce E-E pictures without going into record. This is done by using the programme plus and minus buttons and then manually stepping through the channels. But you can't then go into record without first cancelling E-E with the stop button followed by "programme number select" and then "record", record starting when output monitoring returns. Not difficult to cope with, but a curious arrangement nonetheless.

One very nice facility is the ultra-long life power source (which I haven't found yet) that enables you to unpack the machine, fit a plug and switch it on to find that the clock and date are set correctly. The date is set as part of the programmable timer which allows for seven programmes over a year. My God! 365 Crossroads!

An interesting feature is the EPROM. Early versions are designated E42. Later ones are designated E43 and contain a whole host of extra service codings. The primary coding, 8500, enables the customer to lock the machine with a four digit number. The machine won't operate until that number is re-entered, unless you know the way to overcome it... no tales! Andy reckons that the kids will be punching all sorts of numbers in so that their parents can't watch their video nasties and we'll have to cancel the codes. It could bring in a nice little income that could. Other 8500 codes allow for continuous playback or recording and various special servicing features. 8508 for example inhibits all safety functions, so that if say a microswitch or end sensor is playing up operation can be continued during fault finding. I'm not sure about a keyboard fault though.


The picture quality is fairly good, certainly acceptable enough for me to be able to record and replay programmes without being aware of visual impairment. On a test pattern, a static picture or a picture with hard contrast detail, such as bare tree branches against a light sky, you may find that there's excessive detail correction. There's an internal correction adjustment for "best visible response". The problem is what's the best setting? Sets with

soft tubes will want a sharper response: others, like my 40in. Cinema 9050 unit, will require less. It would have been better to have had a preset sharpness control at the rear rather than an internal preset.

These comments are not based on a single machine. We've had several, and some points have been taken up with Grundig. When we recorded a test tape on a centre tolerance JVC HR7200 we found that the colour frequency was off by about 150Hz. The Grundig machines wouldn't replay it in colour while other VHS machines would. I think the heads are incorrect on one machine: certain prerecorded tapes play back with black speckles on peak white edges and the machine will not clear the picture noise on still frame — a similar problem occurred with the first batches of HR7650s and their Ferguson equivalents. Another machine is excellent, with no speckles and perfect still frame. There's no jitter on either of these machines.

The VS200 will assemble edit all recordings. This is a very neat function. If a series of timed recordings is made the replay is free of any disturbances at the joints. A fellow reviewer commented on a time delay with the audio muting when an edit occurs, but there's no break on the actual recording, only on the E-E monitoring. An investigation revealed that this is due to the series of operations that occur when record start is selected. The tape threads up, rewinds slightly, then plays so that the new and already recorded signals are phased. The machine finally goes into record to give a beautiful edit. This takes ten-twelve seconds, during which the E-E audio is muted. It's not a significant problem and you can be sure that the signal is being recorded about ten seconds after you give the order.

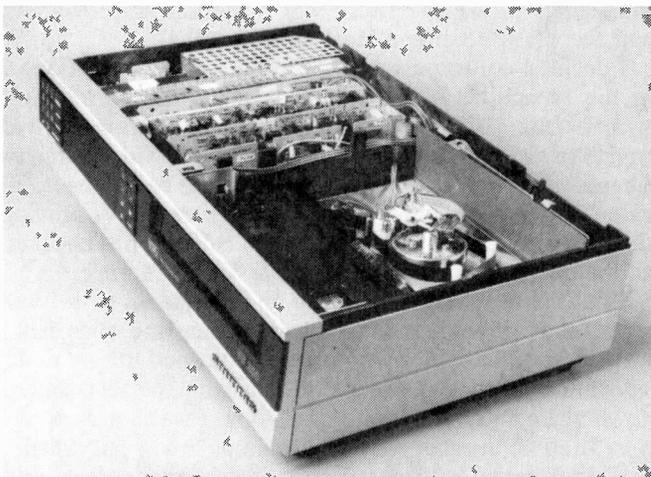I certainly like this Grundig VHS machine. The teething problems are doubtless due to early production problems. Versions with stereo and VHS hi-fi sound are expected to follow. I hope that Grundig and Mullard will develop frequency interleaving between tracks to reduce noise: less edge emphasis will then be needed, with edge noise reduced to the level found on current JVC machines.



Inside Grundig's first VHS machine, Model VS200, which was produced from the drawing board in just seven months and is of more than 95 per cent European origin. The recommended retail price is £459.

The Tangled Web

Les Lawry-Johns

We'd known Mr. Spyder for a number of years and had always been on good terms with him. So when he popped in with his daughter's rather old monochrome portable we had no hesitation about accepting it for repair, even though it was a Thorn 1580 with valves and things in it.

"It goes all right for about half an hour, then funny things happen. Sort of goes into oscillation if you know what I mean."

So he left it with me and the hours of frustration started. Work on it till something else demands attention, put it on one side and go back to it later. This dragged on all over the weekend. The complicated colour sets that came in were repaired in no time with no bother worth mentioning. A new line output transformer here, a new tripler there, a replacement bridge rectifier, new tuner selectors – all run of the mill jobs that any fool could do. But that little portable had me by the short and curlies. Maybe it was because I've not been feeling too well lately and my mind's a bit cloudy. So on I blundered. As Mr. Spyder said, it went into oscillation after half an hour, first showing a very noisy picture.

My diagnosis was that the fault was in either the tuner or the a.g.c. circuit. I plugged in a spare tuner but the oscillation proceeded apace. So I checked the voltage at the collector of the a.g.c. transistor VT8. It was nearly 2V instead of 0.5V. All the associated components were checked and the main suspects changed, including the transistor itself. Something stirred in my mind. The transistor is gated on during the line flyback periods by pulses from the line output transformer. So I went over to the other side to ensure that the transformer's pulse winding (tags B and C) and its connections were intact and good. They were. Back to the i.f. strip.

The voltages around the i.f. transistors were correct but I changed the transistors just in case. I checked the decoupling, using a 33 μ F electrolytic and an 0.01 μ F capacitor as appropriate. All the capacitors were in order. In a fit of temper I decoupled the collector of the first i.f. transistor to chassis with the 33 μ F electrolytic, expecting the signals to vanish. There was a marked improvement and reception became almost normal!

I decided not to pursue this red herring and put it down to the capacitor's inductance. The a.g.c. transistor's base samples the voltage at the emitter of the video driver transistor VT5. Maybe the fault lay in the video circuits. There was a heavy negative voltage at the collector of the video output transistor VT6 instead of some 85V, proving that the whole thing was in a state of oscillation. I checked all the decoupling but nothing made any difference.

I put the chassis the right way up and looked at it. I was aware that something simple was eluding me and that I was too stupid to put my finger on it. I turned the set on its side once more and the picture became perfect. Put it down again and it burst into oscillation. I was amazed. Up, o.k. Then all buggery let loose again as it was put down.

A little voice said check the a.g.c. gating pulses right back to source. I looked at the small figure of E.T. He was pointing his finger at me as usual. So I plodded back across the panel from the pulse coupling/a.g.c. capacitor C55 to the source of the pulses, a potential divider across

the transformer's pulse winding. The resistors checked o.k. individually, but the reading across all three was high when it should have been low, i.e. the d.c. resistance of the pulse winding. But I'd already checked the winding which was in order. At last the penny dropped and I stared at the connecting leads, each in its Sistoflex sleeving. The sleeves are fitted to ward off the heat from the PL81 and PY81 valves, but the wire inside had burnt through and made only when the set was cold – or when it was turned on its side, sometimes.

A new lead dressed well away from the valves completed a very simple repair and left me feeling guilty. Why? Because of the severe line pulling that had accompanied the oscillation. This should have led to an early check on the reference pulses at source since they are also used in the flywheel line sync circuit. I'd put this down to severe video oscillation distorting the sync pulses. Live and learn.

When Mr. Spyder came back for the set he laughed as I told him what a headache it had been. "Just a little thing like that" he said.

"Clear off" I said, or words to that effect.

Another Headache

Now you wouldn't think that a Decca Bradford (30 series) could give one a nasty turn. Normally they're no sooner in than out again. A shorted boost capacitor here, a faulty sound output stage there, no real trouble. Not until Mrs. Footrot arrived that is. Her son carried in the 22in. Bradford and didn't say a word. Mrs. Footrot made up for his silence.

"You put a new tube in this set three years ago. Here's the guarantee card showing that it still has another year to run. I'll leave it here until Saturday, so please give me a chit to say that you have it. You can't trust anyone these days." She rabbitied on in a similar vein for quite some time before I could get a word in.

"What's wrong with the set please, Mrs. Footrot?"

"Oh yes, the colours are funny and keep changing. It's like watching disco lights."

So they departed and I took a look at the disco lights. It frightened me. At first only the corners flashed their impurity at me, then the centre joined in with an odd pulsing effect, the colours continuously changing. I pulled the green and blue drive leads off to leave the red display on its own. The screen showed a patch of red in the centre changing to green and blue while the outside corners were pulsing all three colours.

"Degaussing" I thought and showed it to Honey Bunch. She said she'd never seen anything like it in her life and I had to confess that I hadn't either.

"What does that?" she asked.

"The degaussing coils are being charged and discharged at a rapid rate when they shouldn't be" I explained weakly. H.B. trotted off to feed the bird and change his (her?) water, leaving me to check the degaussing components carefully.

They were all in order. I unplugged the feed to the degaussing circuit from the on/off switch. The display

continued apace. It was as if a dozen powerful magnets were being constantly moved about in front of the tube. I took the shield, coils and degaussing components complete from another set and fitted the lot in Mrs. Footrot's set. Still the same and I now knew what the trouble was,

though I didn't like to admit it. So I replaced the scan coils and the purity magnets. Still the same, confirming that the tube would have to be replaced. This restored normal operation. What the hell was going on inside that tube to make it produce such a display? Does anyone know?

Teletopics

CED FADE OUT

The CED video disc system, which was launched in the UK by RCA, Hitachi and GEC in October 1983, is being phased out. The original plan was to sell 25,000 machines during the 1983 pre-Christmas selling period and a further 100,000 machines this year but in the event only some 5,000 have been sold. The 40,000 players held in stock by Hitachi are to be sold off at £99 each, with 20 free discs. Discs will continue to be sold as long as stocks last – the present catalogue lists 250 titles.

RCA are reported to have made a loss of \$580 million on the CED disc system. Some 700,000 players have been sold in the USA since the system was launched there in 1981. RCA have announced that they will continue to manufacture discs for the US market for at least three years or as long as there is sufficient demand.

DBS PROGRESS

A report to the Home Secretary by the DBS consortium (the BBC, the ITV companies and five non-broadcasting companies) says that considerable progress has been made with plans to launch the UK's DBS service. Agreement has been reached on making £350,000 available for the project's next stage, and a business plan has been drawn up. This envisages a profit of £300 million over a ten-year period after substantial losses initially (£320 million during the first four years). One assumption made is that viewers would be prepared to pay £20 a month, to include the cost of the receiving equipment, for three DBS channels. A more pessimistic projection suggests that the service would still find it hard to make a profit after fifteen years.

RTEEB EXAMINATION CHANGES

Two new practical tests, at Part III level of Course 224 (Electronics Servicing), have been announced by the Radio, Television and Electronics Examinations Board. The tests are on VCR and colour television servicing.

TAKE-OVER BID FOR FIDELITY

An agreed bid for Fidelity Radio, valuing the company at £14.1 million, has been made by Caparo Industries which had built up a 32.4 per cent stake in the company in recent months. Caparo Industries is a diversified engineering group headed by Mr. Swraj Paul who says that the aim in taking over Fidelity would be to get his group into "slightly higher technology". A counter bid was considered by Amstrad but was dropped on the grounds that the companies have similar product ranges and the same customer base. Since the Amstrad factory at Shoeburyness is at present being expanded the company is not interested in acquiring Fidelity's manufacturing capacity. Amstrad's chairman Alan Sugar commented that Fidelity would be "a bargain at the price Caparo is offering". Fidelity had a difficult time during its last financial year, due mainly to problems with test specifications for its cordless tele-

phones and a difficulty with its new CTV chassis (a timebase i.c. that has been designed in failed to perform to specification initially).

MARKET BLUES

The VCR, TV and other consumer electronics markets have been distinctly weak in recent months. VCR sales/rentals for 1984 are expected to end up at around 1.55 million compared to the level of 2.2 million reached in both 1982 and 1983. CTV sales/rentals are expected to be roughly the same as in 1983, though a peak was reached in the early months of the year. The situation is highlighted by comments made at the Thorn-EMI plc Annual General Meeting by Chairman and Chief Executive Peter Laister. For Ferguson, sales of TV sets and VCRs have so far been "substantially lower" this year than last. Thorn's rental operations have fared rather better however. Thorn claim to have 25 per cent more subscribers per outlet than any of the competition in the rental field and are maintaining CTV subscribers overall. In fact Thorn claim to be increasing their share of both the TV and VCR rental market. Peter Laister's comments on "new opportunities such as cable and satellite" are interesting. "In such cases we will invest to the extent of marking our position in their future, but will place limits on our short-term costs."

PHILIPS' TV MILESTONE

Philips, the world's largest TV manufacturer, has now produced over one hundred million TV sets – that doesn't include those produced during the pre-war period! To mark the event, simultaneous presentations of 100 sets each were made at Eindhoven and in London. The Dutch sets were presented to Princess Margriet for use by the Red Cross while the UK sets were presented to the National Society for the Prevention of Cruelty to Children which is celebrating its centenary this year. Philips' Electronics UK chairman Anton Poot commented that it took 35 years for Philips to produce its first 100 million sets but that the second 100 million should be produced in under ten years – "every three seconds day and night a Philips set is sold somewhere in the world".

TV DODGER CAMPAIGN

The Home Office has started a new campaign to catch TV licence dodgers. A fleet of 22 new vans, each costing more than £20,000 and ten times more sensitive than previous ones, will tour cities and major towns. Other elements in the campaign are computerised records that show unlicensed households, an increased maximum fine and a TV commercial.

TELETEXT ADVANCES

According to research carried out by the ITV teletext service Oracle more than two million homes in the UK now have sets equipped for teletext reception. This represents a market penetration of ten per cent. Market penetration is highest in the London area, at 22 per cent, and in the socio-economic class AB, at 27 per cent, though

the greatest growth at present is "down-market". Oracle's research is being continued and is part of its campaign to sell teletext advertisements. It claims a daily audience of two million who watch an average of almost two hours a week, and says that 74 per cent of Oracle users report seeing teletext advertisements.

PRE-WAR TV – THE MARCONI CONTRIBUTION

Our article on pre-war television last month omitted to mention the Marconi Company's considerable contribution to the early development of television in the UK. By chance an interesting article on the subject appears in the September issue of the Marconi Broadcasting Division's publication *The Undistorted Truth*.

The Marconi Company set up a television research group in 1930, and in 1932 transmitted from Chelmsford on the 25m band a low-definition (50 lines, 12.5 frames/sec) head-and-shoulders picture which was received in Australia. More significantly the company had by 1932 produced a v.h.f. transmitter operating at 44.7MHz and capable of being modulated at 250kHz for TV use. The joint Marconi-EMI Television Company that developed the 405-line system was formed in March 1934.

ANGLIA CONSUMER WALLCHART

The second issue of the Anglia Consumer Wallchart, featuring many new items, is now available free of charge from Anglia Consumer, Burdett Road, Wisbech, Cambs PE13 2PS (telephone 0945 63281). Amongst the new items are a new range of teletext i.c.s, an extended range of audio i.c.s, and a competitively priced universal tripler.

TV CHIPS

Developments in i.c.s for TV and related uses continue apace. Mullard have developed a new videotext chip, type SAA5350, for level three text systems (broadcast teletext is level one). Level three text offers DRCS (dynamically redefinable character sets), i.e. the incoming signals contain data to programme the decoder's character generator, enabling foreign alphabets and improved graphics to be displayed (each character cell is based on a 12 x 10 dot matrix). The SAA5350 is known as a EUROM and offers many additional features including an 80 characters per row option in colour, multi-page memory, broadcast standard sync, serial and parallel attribute storage and cursor and smooth scroll.

The new Siemens TDA6000 chip for use in the i.f. section of a TV set has been developed for "hi-fi quality vision and sound". It uses frequency-phase-locked loop synchronous demodulation to ensure that no matter how complex the signal a weighted intercarrier signal-to-noise ratio of 50dB is achieved – even with superimposed text there's no crackle from the speaker. The performance specification includes 1° differential phase and one per cent differential gain (typical values for a tuning range of 1MHz and 150 per cent a.m.).

Mitsubishi have introduced a combined i.f./colour decoder i.c., type M51307SP, for use in NTSC receivers. This is claimed to be a world first and is intended primarily to enable more compact 14 and 15in. sets to be produced. Mitsubishi Electric plan to produce 200,000 of these 52-pin i.c.s a month. European i.c. manufacturers are known to be working on similar chips for PAL signals – Mullard's i.c. will be the TDA4501.

Philips have described a frame store, charge-coupled device i.c. for adding memory capability to TV sets. The

chip is referred to as an MPIP (multiple picture in picture) i.c. and would enable the viewer to see nine channels at a time on the screen, view one "main" channel while monitoring three others in a strip at the side, or monitor just one extra channel in a small box at the corner.

THORN-EMI's NEW RESEARCH DIRECTOR

Dr. K.W. Gray, B.Sc., Ph.D. has been appointed Director of Research for Thorn-EMI plc, responsible for the Central Research Laboratories at Hayes, Middlesex and for advising the company generally on research and technology. Kenneth Gray was previously Deputy Director of the Royal Signals and Radar Establishment, Malvern, the largest electronics technology research laboratory in Europe. The development of stereo recording techniques and electronic, high-definition television broadcasting in the period from the late twenties to the mid-thirties have been amongst the many achievements of the Central Research Laboratories.

EEV's MASSIVE TV DISPLAY

EEV plan to enter a field at present dominated by the Japanese – large TV displays for use at race-tracks, sports stadia, etc. The company has spent £1m on developing a 27 x 20ft prototype screen that weighs twenty tons, claiming that the resolution is twice as good as competitive displays whilst the device consumes only a quarter of the power. The screen, called Starvision, uses some 10,000 miniature c.r.t.s assembled in groups of eight per glass module. This is a highly specialised field – only some thirty large, outdoor TV displays are in use worldwide, mainly in the USA – but EEV hope to achieve sales of about three a year.

DIY TELECINE

The Tele-Cine Converter, which costs only around £50, has been introduced by Markplan Ltd. (Old Colony House, South King Street, Manchester M2 6DQ, telephone 061-832 2765) to enable the images on slides and 8 or 16mm cine films to be transferred to videotape. It uses precision optics to transfer the film projector's output to a high-contrast rear projection screen from which the video camera records. The camera's controls can be used to compensate for faded film images and a bonus is easy editing and the possibility of adding zoom and soft-focus effects.

FIRST WIDEBAND CATV SERVICE STARTS

Thorn-EMI's subsidiary Swindon Cable has started the first wideband cable TV service in the UK, offering 13 channels initially (the network has 32-channel capacity). The 13 channels consist of BBC-1 and -2, Channel 4, three ITV channels, the Premier feature film channel, Music Box, Screen Sport, Children's Channel, a local Swindon programme, local teletext and a stereo radio channel. The service will eventually be available to 53,000 households, the cost of cabling being between £14m and £18m: 5,000 households will be able to receive the service by the end of the year. The basic charge to viewers is £8 per month, plus £7 extra for Premier (which is not available separately). Nearly a third of those initially contacted have agreed to take the service.

TRAINING TAPES

Flintdown Ltd. (Montauban Chambers, 339 Clifton Drive South, Lytham-St. Annes FY8 1LP, telephone 0253 725

499) have produced three videotape programmes on the theory and practice of colour TV. Part 1 deals with the colour signal itself, with a detailed account of NTSC and PAL encoding; Part 2 covers PAL decoding, with practical demonstrations of decoder fault conditions; Part 3 covers receiver installation and setting up. The cassettes are available in all formats. An additional audio-visual tape/slide programme covers soldering techniques.

CCTV CAMERA CONTROL SYSTEM

Pelco Coaxitron, a low-cost, computerised system for the remote control of up to sixteen CCTV cameras, has been introduced by Norbain Imaging Ltd. (Norbain House, Boulton Road, Reading, Berkshire RG2 0LT, telephone 0734 864 411). The control signals use the video coaxial line to avoid extra cabling: pan and tilt, auto-scan, variable-speed zoom, focus/iris/auto-iris setting, on/off switching, wash wipe and infra-red illumination can all be controlled. The system is a preprogrammed, non-addressable one using an intermediate video switcher to address the cameras.

NEW TVs

The new Salora DigiComputer range incorporates a microcomputer to provide an "automatic equalising system". This enables the user to preset the colour, contrast, brightness and sound levels separately on each of 27 channels to cater for different input sources. The basic J chassis is used, featuring the Ipsalo-2 circuit (see *Television*, September 1984). Other features include parallel sound and a tuning system that covers 100 channels with 27 storage positions. A full range of optional extras is available.

The recently introduced Ingersoll Model XK510 is a combined 4½in. monochrome receiver, m.w. and f.m. radio receiver and a digital alarm clock with twelve-hour red LED display. The suggested price is around £130.

The 1120 9in. colour portable is the first set from Philips to be fitted with the new flat, square type tube. Its suggested price of £260 may seem on the high side but the set's features include mains/battery operation, 60 channel presets with direct access via a keypad beneath the screen, and a comprehensive set of sockets to enable the set to be used as a domestic or professional monitor.

BACK INJURY

The problem of back injury due to lifting TV sets has come up again with the case of Colin Flowerday who is claiming damages against Visionhire – regular readers will recall Harry Todd's case against Radio Rentals. Colin Flowerday says the injury occurred whilst carrying a Philips 520 series G8 set which he estimates weighed some 60lbs. He is now a permanent invalid.

VCR LOCKS

Mention of VCR locks was made in this column last month, in particular the lock fitted to the new Grundig Model VS200. We have been asked by Robert E. Barwick, a freelance electronics engineer from Stockport, to mention that he filed a patent application covering VCR locking techniques on November 4th, 1984. Bob Barwick's Roblock system provides selective VCR disablement so that the machine will still make timed recordings. He is of the opinion that Grundig's lock infringes his patent and is in dispute with Grundig over the matter.

30V Battery Eliminator

Peter H. Dolman, T.Eng.

The 15V battery eliminator circuit featured in the letters page recently (August) prompts me to report on a similar project, this time a 30V battery eliminator for use with the well-known Rank u.h.f. signal strength meter (Mastercare have been selling these off cheaply). The latest version of this instrument uses two batteries, a 9V PP7 for the receiver circuitry and a 30V B123 to supply the varicap tuning voltage.


The B123 is expensive and difficult to obtain. To overcome the problem the circuit shown in Fig. 1 was devised. It enables the 30V supply required to be obtained from the PP7 and uses readily available components. The circuit consists of an oscillator and rectifier, the oscillator being built around the line oscillator coil used in the Z504 timebase panel (Rank A823A chassis). The circuit can be built on a small piece of Veroboard – use 0.5W hystab resistors.

Output is 30-36.5V for 9V supply variations between 5.5-9V. Operation is maintained with a supply exceeding 9V, which is desirable as new batteries can deliver potentials somewhat above the rated value. The ripple is less than 20mV. Circuit operation is dependable over a wide temperature range: it's tolerant of inadvertent reversal of the 9V supply polarity and shorting of the 30V output.

A 27V zener diode should be added across the tuning potentiometer in the signal strength meter to ensure that the channel tuning range remains 21-68 regardless of

battery ageing effects down to 5.5V. Even below this the meter is usable, the most noticeable effect being loss of sensitivity – this falls off fairly rapidly below 7V (the manufacturers recommend that the battery should be replaced when its on-load voltage falls below 7.5V).

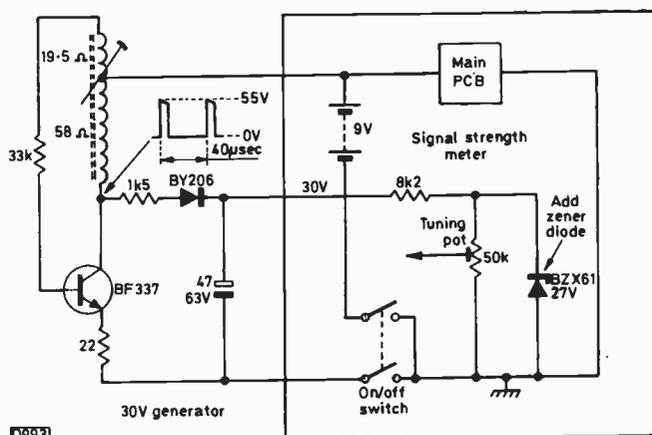Adjust the coil for maximum output, on load, measured at the cathode of the BY206 rectifier diode. The tuning is extremely flat – correct adjustment corresponds to a collector waveform period of around 40µsec.



D9931

Fig. 1: Oscillator circuit used to obtain a 30V tuning voltage supply from a 9V battery.

All About Lenses

Vivian Capel

Increasing use is being made of video cameras in conjunction with VCRs, in particular with portable machines. The electronic aspects have been touched upon in other articles, but what about the big chunk of expensive looking optics that sits at the front of the thing? Photographic enthusiasts will have few difficulties in mastering its use since they'll be familiar with all features except for the zoom facility. Those whose experience is limited to the simpler types of film camera may find the lens and its various adjustments rather more daunting – in fact many good shots can be lost while the operator is fiddling with the various controls, trying to get everything right. The ability to make quick adjustments to capture fleeting shots comes with experience in handling a camera, but an understanding of the lens – what it does, how it works and its limitations – goes a long way towards obtaining successful results. We'll start off with some basic optics.

Refraction

Contrary to popular belief, the speed of light is not constant. It slows down when it passes through a dense, transparent material such as glass. If the light falls on to the glass surface perpendicularly there's no observable effect: if it strikes at an angle however the ray is bent. When the ray leaves the glass on the other side it's again bent, assuming that the path of the light is not at right angles to the glass surface. A perpendicular path is known in optics as the normal. The bending effect is termed refraction and the amount of bending a given material causes is termed its refractive index. The latter is the ratio of the velocity of light in the material to that of light in a vacuum. A vacuum thus has a refractive index of 1. Air at sea level has an index figure of approximately 1.0003, but the difference between this and a vacuum is so small that it's usually taken to be 1. The figure for water is about 1.33, and for glass 1.5. Glass varies according to its composition however: flint glass has a high refractive index while the figure for crown glass, which is made without metallic additives, is lower. As we shall see, this can be very useful.

The angle at which a light ray strikes a glass surface relative to the normal is termed the angle of incidence (see Fig. 1), while the angle from the normal of the refracted ray within the glass is its angle of refraction. The one depends on the other: if the angle of incidence changes, so does the angle of refraction (to be more technical, the sine of the angle of refraction is equal to the sine of the angle of incidence divided by the material's refractive index).

Convex Lens

It follows from this that if a bunch of parallel light rays is directed on to a curved glass surface the angle through which each ray is bent will differ – because the curvature encountered by each ray differs. If the surface is convex, there will be a point at which the rays converge after emerging from the other side of the glass. A glass plate with one convex side thus acts to concentrate or focus the light passing through it at some point on the far side. It

forms a simple lens. If the second side is also convex (see Fig. 2) the rays will again be bent, bringing the focal point closer to the lens. It's the convention with such a lens to regard the right-hand curve (on the left) as positive and the left-hand curve (on the right) as negative. Despite this they bend the rays in the same direction – because at the first intersection the rays pass from a low-density medium (air) to a high-density one (glass) while at the second intersection the passage is from high to low density.

Lens Power

The total curvature of the lens is obtained by subtracting the reciprocal of the radius of one curve from that of the other: when this is multiplied by the difference between the refractive indexes of the materials (glass and air) we get the power of the lens. The unit of power is the dioptre. Power is also equal to the reciprocal of the focal length in metres. Thus a lens with a focal length of 1 metre has a power of 1 dioptre.

Concave Lens

A lens may have one or both surfaces concave instead of convex. These will diverge the beams instead of converging them (see Fig. 3). With such a lens the beams are considered to come from an imaginary focal point at the front of the lens, the distance between this point and the lens being taken as its focal length. Such a lens is said to be negative while a convex lens which converges the light rays is termed positive.

Chromatic Aberration

The angle of refraction is determined by the wavelength of the light as well as its angle of incidence and the refractive index of the glass: short wavelengths (blues) are refracted at slightly different angles to the longer ones (reds). As a result, the image produced by a simple lens has coloured outlines, red on one side and blue on the other. This is called chromatic aberration.

The colour separation produced by a positive (convex) lens can be corrected to some extent by following it with a negative (concave) one. As both lenses have the opposite effect, the positive one must be the stronger to achieve a convergent effect from the combination. By making the convex lens of crown glass (low refractive index) and the concave lens of flint glass (high refractive index) almost complete cancellation of colour fringing is achieved. Two such lenses cemented together to form a single unit are called achromatic, literally "colourless". This doesn't mean that the lens won't transmit a coloured image of course: it means that the lens doesn't split white light up into the colour primaries.

Focus

In considering the focal point we referred to a bunch of parallel light rays. Only rays that come from very distant objects can be considered to be almost parallel however.

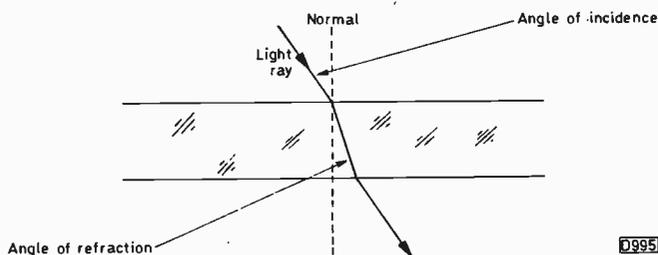


Fig. 1: When a ray of light strikes a dense medium such as glass it's refracted. The angle of refraction away from the normal is dependent on the angle of incidence.

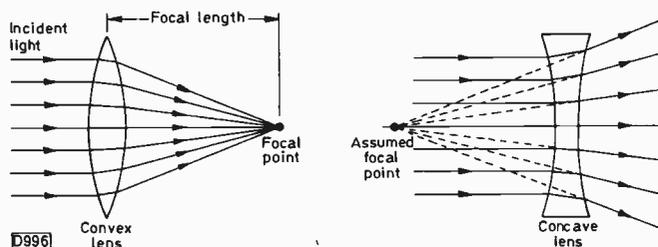


Fig. 2 (left): When parallel rays encounter a convex glass surface they are bent inwards. The angle of refraction is greater for the outside rays than for the inner ones because the angle of incidence is greater, due to the surface curvature. Thus all the rays converge at a certain point (the focal point).

Fig. 3 (right): With a concave lens the rays are refracted outwards and appear to come from a single point.

All other rays are divergent: the closer you are to their point of origin, the more divergent they are. With a lens consisting of several elements, the light source may be a few feet from the first (called the objective) lens element, but the source for succeeding elements is much closer – the lens immediately in front. The focused image produced by a lens appears at a distance from it that depends on the lens's focal length and the distance between the lens and the light source. The actual relationship is based on the reciprocal of each dimension: the reciprocal of the distance of the focused image from the lens is equal to the sum of the reciprocals of the focal length of the lens and the distance of the object in front of it.

Thus in theory a lens or lens system can produce a truly focused image only when the object is at a certain distance in front of the lens. In practice however anything from a few feet to infinity is in reasonable focus, because the geometry of divergent rays is such that their deviation from the parallel state at such distances is negligible. For nearby objects the deviation is much greater of course. Many simple lenses are of the fixed focus variety: they save the fuss of focusing each shot but cannot be used for close work unless an extra lens is added. Variable focus lenses have a movable element that changes the focal length of the whole system, permitting close-quarter focusing. Moving objects that are close must stay at the same distance however otherwise they'll go out of focus, since focusing is critical with close objects.

Macro Facility

With some lenses it's possible to extend the distance between the optical system and the rest of the camera by means of either an add-on tube or a built-in spacing arrangement. This is called a macro facility and allows very close focusing – to within millimetres from the lens. Stamps, photographs and other small, flat objects can thus

be brought into focus. At such very close distances the lens itself may obstruct the light, making it necessary to use back lighting or some other special means of illumination. An add-on lens can be used to achieve closer than normal focusing with a camera that doesn't have a macro facility – alternatively if the camera has a detachable C-mount lens this can be unscrewed a few turns – be careful not to unscrew it too far.

Depth of Field

Depth of field is the axial distance over which objects remain in focus and is a particularly important factor. With a shallow field, objects remain in focus within confined limits only, being defocused before and beyond these limits. A deep field has much wider limits.

Now depth of field is inversely proportional to the square of the magnification. As a camera lens reduces the size of the focused image, it follows that its depth of field is directly proportional to the square of this reduction in size. So the smaller the image, the deeper the field. Hence a video camera with a $\frac{1}{2}$ in. pickup tube has a deeper field of focus than a 35mm film camera in the same conditions, though not as deep as an 8mm cine camera's field.

Another consequence of this is that because a high-magnification (telephoto) lens has a low reduction factor its field of focus is shallow. As it's proportional to the square of the magnification, the field depth reduction with a $\times 8$ zoom will be 64 times from wide angle to telephoto. Careful focusing is thus required with telephoto settings. An out-of-focus background for special effects is sometimes obtained by using a telephoto lens focused on a close-up foreground. Field depth is further restricted by using a large aperture setting.

Another telephoto characteristic is foreshortening – the foreground is magnified less than the background. The result is that they appear to be closer together than normal while movement towards the camera seems to be slow. Wide-angle lenses have the opposite effect: the backgrounds appear to be more distant and smaller, with the speed of moving objects that approach the camera appearing to be faster.

Blooming

Individual lens elements are commonly given a coating, or "bloom", of magnesium fluoride which is deposited in a vacuum chamber. A more accurate and expensive method is electron beam coating (EBC) – a layer is built up to the required amount by successive microcoatings. Why is this necessary?

When light strikes a polished glass surface some of it is reflected, at angles governed by the angles of incidence. With a multi-element lens system internal reflections can cause loss of light transmission in addition to producing ghosts or multiple images and all sorts of undesirable effects. Blooming is done to prevent such reflections. The thickness and nature of the coating has to be carefully chosen and its application rigidly controlled.

Aperture

Even with a video camera that incorporates automatic sensitivity control circuitry it's necessary to be able to regulate the amount of light that passes through the lens. Without this either the tube would be overloaded in bright sunlight, causing flattened highlights, or dim, noisy pic-

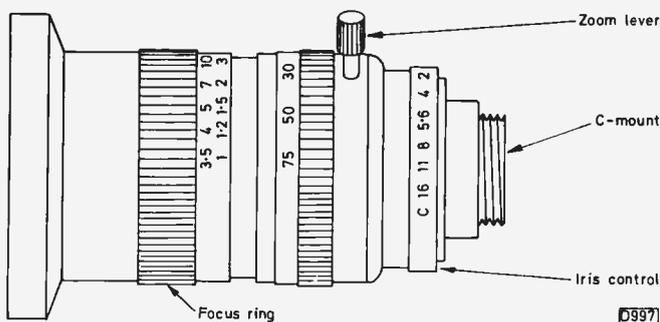


Fig. 4: A typical detachable zoom lens. The first control from the end is the focus ring, which is calibrated in feet and metres. More adjustment is needed at the near end of the scale than the distant one, as the wider spacing of the calibration shows. Next is the zoom control, which is sometimes calibrated with focal length. Finally there's the iris control, which is marked with the *f* numbers. The C position denotes closed, i.e. no light enters.

tures would be obtained at low light levels – possibly both conditions might be experienced. For this reason most lens systems incorporate an iris consisting of several leaves of matt black metal arranged so that the central aperture between them can be enlarged or reduced. Others with automatic aperture control by means of an electronic eye usually employ a single leaf in which there's a widening channel to admit an increasing amount of light as the leaf is advanced.

Specific aperture openings have values which are specified by *f* number. These are based on the ratio of focal length to aperture diameter and determine the amount of light admitted. There are click stops on some lenses with manually controlled apertures, though the iris is continuously variable. Stop numbers are *f*1.4, *f*2, *f*2.8, *f*4, *f*5.6, *f*8, *f*11, *f*16 and *f*22. The lower the number the larger the aperture: each stop up reduces the amount of light by half. The largest aperture for a particular lens may not correspond with a standard *f* number, while the cost of a lens rises dramatically with small increases in maximum aperture. Large apertures are useful for film but are not necessary for video cameras using modern, high-sensitivity pickup tubes.

Zoom Lenses

Amateur photographers will be familiar with most of what's been said so far. There's one feature of the video camera lens that will probably be new – except perhaps to cine enthusiasts. This is the zoom feature (see Fig. 4). By means of this the view can be changed from a wide-angle, distant scene to a narrow-angle, close-up one without moving the camera. This is done without materially affecting either the focus or the amount of light passing through the lens, and is accomplished by a complex arrangement of lens elements. A dozen or more individual optical units assembled in groups are required, relative movement between the groups producing the zoom effect.

Focus is not always maintained over the whole range with the cheaper zoom lenses, so there may be loss of definition at one or both extremes. Lenses for home video use are generally not made to the same standard as photographic ones: since VCR definition limitations tend to mask lens defects, a better and much more expensive lens will give no observable improvement. Another factor is that the aperture is not, as it should ideally be, kept constant over the whole zoom range. This is known as ramping and is more prevalent over large zoom ranges. A

video camera's automatic sensitivity control circuits compensate for minor changes, so this is less of a problem than with film.

The focal length of the lens is changed when the zoom control is operated. Zoom lenses are usually rated by their focal length, a typical example being 12.5-75mm. The lower figure is the wide-angle setting and the larger the telephoto one. Notice that in this example the ratio is 6:1 – the zoom is said to have this range. The largest range for amateur lenses is around 10:1. For lower price cameras the range may be as low as 2:1. This will still give useful results however. Excessive use of zoom is irritating and is usually due to inexperience. The full zoom range is rarely required.

The principal advantage of a zoom lens is that framing of the picture can be achieved without having to get closer to or farther away from the subject. Remember the points made earlier about foreshortening: if good perspective and separation of the foreground and background are desired, it's often better to use a medium- to wide-angle setting and get closer to the subject physically. Another factor to bear in mind is that with high magnification settings the slightest movement produces an unsteady picture. Always use a tripod for these. Unsteadiness has much less effect with wide-angle settings.

Two viewing angle figures are often quoted for each zoom limit, one horizontal and the other vertical – because the picture is wider than it is high. Typical horizontal angles are 38° at 12.5mm, 27° at 25mm, 7° at 75mm, 5° at 11mm and 4.5° at 110mm – these vary between models.

A motorised zoom gives a smooth zoom in or out and can be stopped at any point. Many enthusiasts prefer manual operation however, as the zoom can be slowed towards the end, giving a more pleasing effect than the abrupt stop of a motor. In addition the speed can be varied to suit the subject, from a dramatic quick zoom in to a leisurely, almost imperceptible inching forward or backward. A two-speed motor zoom is an improvement but still lacks the flexibility of manual control.

How Lenses Come

Most CCTV cameras are sold without the lens. You buy the model you want then choose the lens, which is screwed in and can be changed over for another at any time. Because of the complications introduced by motor zooms, auto-irises and other such features, most home video cameras have integrated lenses that cannot be changed.

Used surveillance monochrome CCTV cameras can often be bought cheaply. This is a way of getting into home video shooting at minimum expense. Always ask to see the camera demonstrated via a video monitor, and watch out for vidicon tube burns. These show up as white patches that don't move as the camera is swung round.

Most video cameras are fitted with a $\frac{3}{4}$ in. pickup tube, though some have 1in. tubes. Lenses intended for 1in. tubes can be used with a $\frac{3}{4}$ in. tube camera, though the angle of view will be narrower than that quoted for the lens. The reverse, i.e. using a $\frac{3}{4}$ in. tube lens with a 1in. tube camera, cannot be done successfully.

Whatever the lens on your camera, it's worth experimenting with the various features. Try the effect of different settings, noting such characteristics as depth of focus, minimum distance focus and foreshortening. You'll then appreciate its limitations and strengths and will be able to use it to best effect when making serious recordings.

A Look at Monitors

Part 2

Eugene Trundle

Part 1 last month was mainly concerned with monitor requirements – resolution and other characteristics. This month we shall concentrate on displays, in particular with the various types of colour tubes used in monitors, and the input standards in use.

Monochrome Monitors


Monochrome monitors are used mainly as computer display devices. An increasing trend is to use a green-phosphor tube, the P31 type (medium short persistence) being the most common. Green is generally accepted as being the most restful colour to watch and corresponds to the greatest sensitivity of the human eye in terms of brightness and definition. If a long-persistence green phosphor (P39 type, decay about 50msec) is used, the interline flicker mentioned earlier is considerably reduced, though too long a persistence will leave noticeable comet tails when scrolling the display. Some monitors have green light filters over what's basically a black-and-white screen. This is cheap but inferior on the grounds that some of the phosphor light is wasted while the long persistence characteristic of some green phosphors is not present. Amber phosphors (type LA) are also appearing in the latest monochrome monitors. For black-and-white monitors in professional applications, particularly where they are used alongside colour monitors, it's important that the colour temperature of the light emitted is illuminant D – most

domestic monochrome tubes give a very cold, bluish image.

In a conventional monochrome tube the electron beam diameter is typically 0.2–0.4mm at the point where it strikes the phosphor screen, and this is well suited to a 625/50 standard display. Indeed, too small a spot diameter will leave dark spaces between the scanning lines, which can be a definite disadvantage. The ideal scanning spot diameter is that which permits the lines of a correctly interlaced raster to just touch one another. For a 51cm (20in.) tube this is 0.5mm and for a 37cm (14in.) tube 0.3mm. An ordinary monochrome tube and video amplifier can cope with 80 character per line data (see later) without too much difficulty.

Conventional picture tubes suffer from various forms of scanning spot aberration, mainly as a result of the deflection mechanism. For very high resolution applications, high-grade tubes are available with special gun assemblies that have high-quality electron lenses providing a small spot size. Special scan yoke assemblies are also available to minimise deflection defocusing and astigmatism. Some quite inexpensive monitors (the Ferguson 12in. green screen Model MM02 for example) have dynamic focusing – a line-rate parabola is fed to the tube's focus electrode to compensate for the longer beam path at larger deflection angles.

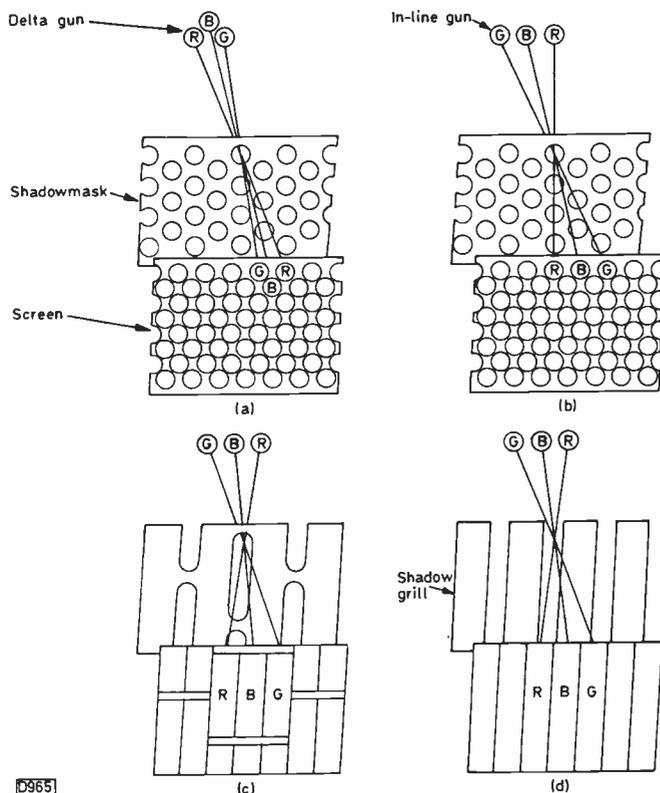Using the above techniques, allied sometimes to magnetic focusing with an axial coil carrying a preset and fed with a stabilised current, the resolution can if required be pushed well beyond 1,000 lines without too much difficulty.



Colour Monitors

Apart from the last sentence, the foregoing comments also apply to colour monitors. In this case however the crucial limiting factor for resolution with a shadowmask tube of whatever type is the dot structure on the screen. It's well known that the colour screen consists of a glass faceplate whose rear surface is coated with a matrix of phosphor dots or a series of vertical stripes (the principle remains the same, but to simplify the description we'll stick to dots for the moment). The dots are arranged in groups of three (triads) and plainly no pixel can be smaller than one triad. So the dot spacing determines the tube's resolution capability – dot spacing is the distance between the centres of each triad group and corresponds to the holes in the shadowmask (whether they're circular, rectangular or, as in the Trinitron tube, continuous slots). The triad groups can be arranged in four ways, as shown in Fig. 7. The delta-gun arrangement – Fig. 7 (a) – is still very much alive in the world of monitors, being used for very high-quality, high-definition picture monitors where the ultimate in performance is required: a broadcast grade 1 monitor may be regarded as virtually a measuring instrument. Versions of delta-gun tubes are available with four times as many dots as conventional colour tubes. A 51cm tube of this type (0.31mm dot spacing) can resolve 770 TV lines on a total of 1.32 million triads – four million individual dots!

Fig. 7: The four alternative gun/mask/screen shadowmask tube configurations, (a) delta gun, (b) dots with in-line gun, (c) striped screen with slots and in-line gun, (d) Trinitron system.


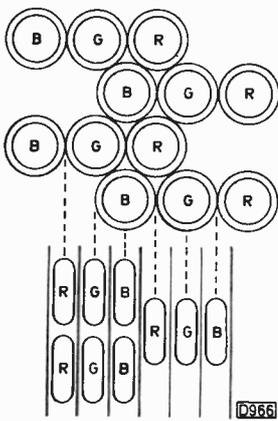


Fig. 8 (left): To achieve the same order of resolution, a striped screen tube needs a finer "triad" structure than a delta-format tube.

Fig. 9 (below): Resolution capabilities of various types and sizes of colour tubes. A pixel width of two triads is assumed for reliability and readability. In practice display lines can, with difficulty, be discerned down to one triad per pixel.

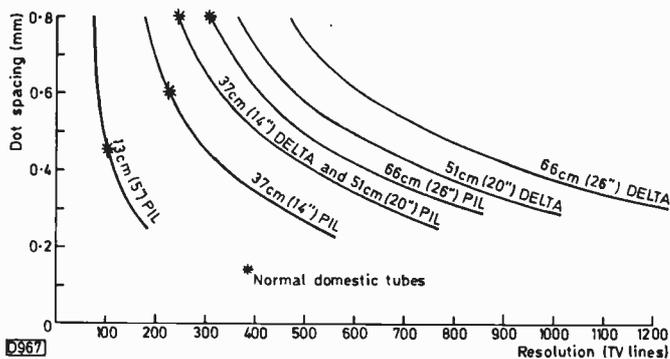

The in-line dot system - Fig. 7 (b) - combines the advantages of the in-line gun approach (no dynamic convergence adjustments) with the high resolution capabilities of the delta-gun tube and is a good compromise for high-quality monitors. Its resolution performance falls between those of the delta and slot systems. The latter, Fig. 7(c), is the standard arrangement used in current consumer TV tubes.

Slot tubes are in fact the most common types found in monitors and share with the Trinitron type - Fig. 7 (d) - the advantage over delta-gun tubes of higher brightness for a given beam current. This stems from the greater "transparency" of the shadowmask (an improvement of around 20 per cent). The reason for the poorer horizontal resolution capabilities of slot-mask, in-line gun tubes (compared to delta- and in-line dot types with a comparable phosphor pitch) is shown in Fig. 8. From this it can be appreciated that for the same subjective fineness in the picture structure the width of each phosphor stripe must be about half the diameter of the individual phosphor dots in the delta format. This however is traded off against vertical resolution, which in the slot tube is not limited by the dot structure - the horizontal tie bars between triads are negligibly thin (30-100 microns, i.e. 0.03-0.1mm) compared with the scanning lines themselves. So the vertical pixel count depends on beam diameter and scanning line structure. This is also the case with the Trinitron of course.

Dot Pitch

For consumer tubes the standard stripe pitch is 0.6mm for small screens, i.e. 37cm (14in.), and 0.8mm for 51, 56 and 66cm (20, 22 and 26in.) screens. Thus a 37cm tube will have almost 1,500 vertical phosphor stripes across its display width of about 281mm, giving 500 as a theoretical maximum number of pixels per scanning line. A 26in. 20AX or 30AX tube has 650 triads per 444mm display width and a 20in. (404mm display width) tube some 505.

Taking this last figure and harking back to our previous calculations on line structure and pixels, with 430 lines as a practical vertical definition figure and 570 or so dots along each line, the broadcast analogue picture has some $430 \times 570 = 245,000$ pixels. No problem with resolving the scanning lines themselves but the stripe pitch, with its 500 triads across, will considerably reduce the total available pixel count - in fact to below 150,000 because to avoid what might be called a "horizontal Kell" one broadcast pixel ideally needs to cover the width of two phosphor triads. That's why you won't see the 5.25MHz test card gratings on an ordinary colour TV screen - and in many cases miss the 4.5MHz ones too, even with no luminance notch filter in operation.

The worst performers in this respect are the very small 13 and 15cm (5 and 6in.) colour tubes used in mini-portable colour sets. With these the dot pitch is not reduced in proportion to screen area - in fact they have a screen matrix comparable with those of their bigger brothers. These tubes can resolve only 100-200 lines per picture width, though higher resolution types are available for use in mini-monitors, VTR editing consoles and as viewfinders in colour TV cameras.

To increase the display's information density a finer dot pitch is required. Slot-mask tubes are available with an 0.43mm pitch, giving about 860 dots per line in the 51cm size and 650 dots per line in the 37cm size; and with an 0.31mm pitch, which gives almost 900 dots per line in the 37cm size. These are known as medium- and high-resolution types respectively. To indicate the relative costs of these tube types, the current Microvitec price list quotes £199, £299 and £440 respectively for 37cm monitors in standard-, medium- and high-resolution grades. The differences are very largely accounted for by the tube prices alone. Fig. 9 indicates the resolution capabilities of some

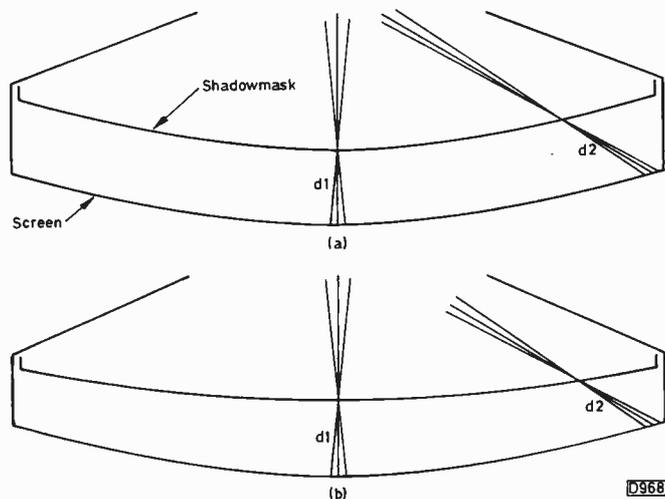


Fig. 10: (a) Constant mask/screen spacing used with earlier delta-gun tubes. Distance d_2 is greater than d_1 , and the phosphor dots are more widely spaced at the extremes of the display. (b) When the mask and screen have different radii distances d_1 and d_2 remain the same and the dot pitch is uniform over the entire screen area.

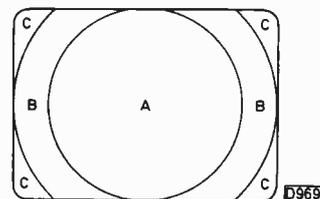


Fig. 11: Convergence error zones.

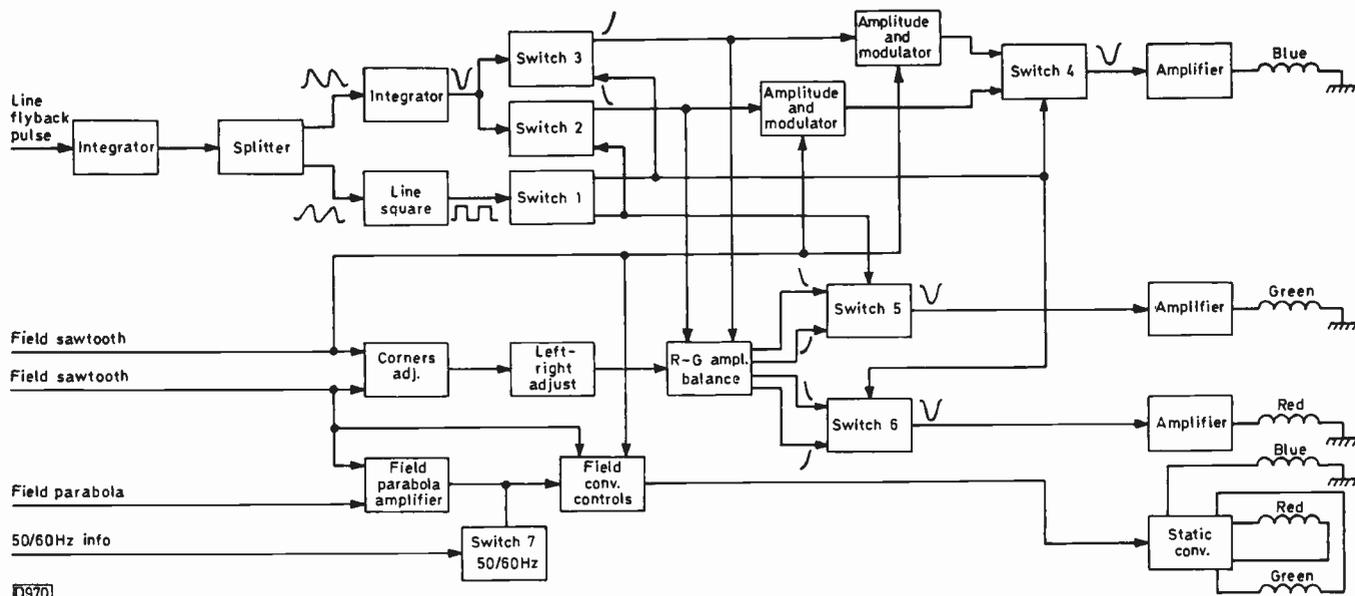


Fig. 12: Block diagram of the precision convergence system used by Barco with high-resolution delta-type tubes.

typical tubes in terms of lines per picture width. It's interesting to relate this to Fig. 4.

Pitch Grading

In earlier delta-gun tubes the spacing between the shadowmask and the phosphor layer was constant – see Fig. 10 (a) – which meant that the dot spacing was wider towards the edges and corners of the screen. It's easy to see why. The three beams cross over at the mask aperture and then diverge on to their own phosphor dots. At large deflection angles the divergent paths (mask to phosphor) are longer, so the three beams spread farther before striking the screen: hence the need for progressively larger triads towards the extremes of the display. The situation is a little more complex in practice due to the mechanics of the deflection process and the need to provide a larger guard band (for beam landing tolerance, i.e. purity) at the edges of the display. The latter requirement is achieved by making the mask holes 5–10 per cent smaller in these areas. This grading technique marginally reduces both the brightness and resolution at the extremes of the picture.

Most in-line gun tubes have mask and screen radii that result in a constant path length for the diverging beams as shown in Fig. 10 (b). This avoids the need for pitch grading, though I'm told that the new FS (flat, square) tubes have some grading.

Beam Diameter

In an ordinary colour tube the beam diameter is about 0.45mm at its focal point, and in conjunction with an 0.6 or 0.8mm stripe spacing this is adequate. Beam diameter (or scanning spot size) depends on several factors, the main one being beam current. To maintain a small spot size, a monitor's beam current limiter circuit comes into operation at a lower level (450–600 μ A total for the three beams, depending on screen size) than in a conventional TV set in order to prevent defocusing. For medium- and particularly high-resolution tubes an additional design feature is a special gun incorporating a high-performance electron-optic lens to ensure a very finely focused scanning spot. The scanning yoke requirements are also more stringent with these tubes, not only with regard to deflec-

tion defocusing and astigmatism but also in terms of convergence performance.

Convergence

There's little point in improving one aspect of a system without upgrading the rest of the links in the chain to match. If the capabilities of a high-grade tube's fine dot structure are to be exploited fully the convergence performance must also reach a high standard, ideally converging to within half a pixel over the entire screen area. This goal is unapproachable with current tube technology! The best high-definition, in-line gun tubes can achieve maximum error figures of 0.3, 0.8 and 1mm in zones A, B and C shown in Fig. 11. This compares with about 0.4, 1.2 and 2.2mm respectively with a production domestic tube. Top-flight delta-gun tubes manage, in conjunction with fairly complex dynamic convergence circuits and controls, to contain the errors within 0.3, 0.5 and 0.7mm for a 51cm screen and 0.3, 0.4 and 0.6mm for a 37cm screen. Corner convergence is far less critical for picture reproduction than for data displays, where small characters and fine detail can reach right to the screen edges.

A block diagram of the convergence system used in the Barco delta-gun monitor is shown in Fig. 12. A line flyback pulse enters at the upper left in the diagram and is first integrated to produce a sawtooth, then polarity split to provide complementary sawtooth waveforms. The negative sawtooth is further integrated to form a parabola. The positive sawtooth goes to a threshold switch whose output is a squarewave – high for the first half of the line scan, low for the second half. Complementary squarewaves go to switches 2 and 3 whose outputs consist of the first and second halves of the parabola respectively. Each half is separately controlled in amplitude and, for corner convergence purposes, is modulated by an adjustable field-rate sawtooth before recombination at switch 4 and application to the output amplifier and blue horizontal dynamic convergence coil.

The red-green line dynamic convergence system uses the same half parabolas from switches 2 and 3: each is processed in a voltage-controlled attenuator i.e. which has two outputs and two control lines. For each chip, one control line sets the amplitude of both outputs while the

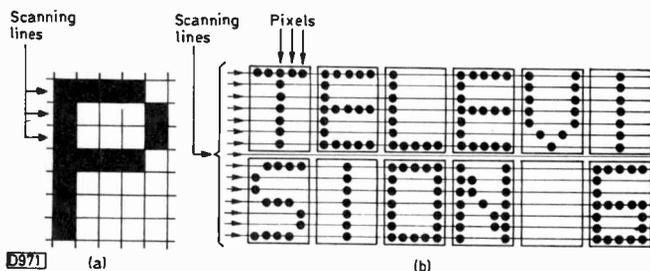


Fig. 13: (a) 7×5 dot matrix used for data displays. (b) Dots, cells and their relationship to the TV raster.

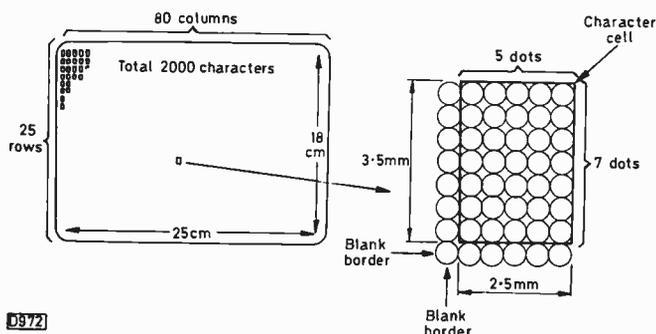


Fig. 14: Character structure for an 80-column display, related to a 37cm screen. Beam diameter is of the order of 0.45mm.

other determines the ratio between them. The two half parabolas are combined in switches 5 and 6 for application to the red and green output stages and convergence coils.

Field dynamic convergence is conventional so far as compass points N, S, E and W are concerned: a transistor switch 7 equalises the operation for 50/60Hz scan rates.

Corner convergence adjustments are based on the action of a pair of diode clamps, across each of which appears only one half of the vertical sawtooth waveform: thus one bank of controls operates on only the upper half of the display while a second bank operates on the lower half. The carefully shaped half sawtooth waveforms pass into the previously mentioned electronic attenuator chips as control voltages.

In all there are 22 dynamic convergence controls, ten of which are concerned with corner convergence. Three additional controls are provided for static convergence. Nine i.c.s and thirteen transistors are used in the circuit.

Colour Phosphors

A monitor will normally have phosphor emission colours that match the transmission parameters. These colours are much more relevant to analogue picture monitors of course than to those intended for data display. The normal standards are specified by the EBU and are known as the EBU chromaticity co-ordinates. For data monitors different co-ordinates can be used, especially where longer phosphor decay times are required to suppress interline flicker in high-definition displays.

We touched on phosphor persistence when discussing monochrome tubes. Standard persistence as used in ordinary colour tubes is JEDEC classification P22. The red decay is about 1msec, green $150\mu\text{sec}$ and blue $100\mu\text{sec}$, in each case to ten per cent of initial brightness. Colour tubes for data display are available with longer persistence of up to 150msec – except for the blue phosphor, where no material has yet been found that combines the correct primary colour with a long decay time. Hence the “long-

persistence, short-blue” type tube whose characteristic is better flicker performance combined with a tendency to show a yellow comet tail effect on scrolling characters. Long persistence phosphors have a lower lumen efficiency than medium and short types, giving about 50 per cent less light output for the equivalent beam energy.

Computer Displays

In a 625/50 standard TV display the basic pixel count is approximately $575 \times 575 \times (4/3) = 440,000$: provided the video amplifier and display tube are up to it, more pixels can be introduced by increasing the dot count per scanning line. For the purpose of displaying characters and graphics, the raster is divided into rows and characters, the information density possible depending on the number of these. Starting with the simplest displays, i.e. standard teletext, Prestel and low-price computers, the screen area is divided into 23 rows of information with each row containing a maximum of forty characters. So the information density is 920 characters. Each character can be regarded as a cell which consists of a matrix of dots: these dots are the basic TV pixels. There are various cell arrangements, 7×10 , 7×9 and particularly 5×7 being common. The letter P in a 5×7 dot matrix is shown in Fig. 13 (a), and the arrangement of the character cells across the screen in Fig. 13 (b). To separate adjacent characters and rows, a single line of blank dots is inserted beside and below each character cell. Thus each complete 5×7 cell is in fact 6×8 pixels.

We’ve already seen that each pixel-dot needs to cover two phosphor triads to ensure adequate resolution and visibility. 40-column text is easily reproduced by standard-resolution tubes, as witnessed by the excellent teletext displays on domestic TV sets. The next step is 80-column text, e.g. mode 0 with the BBC microcomputer. Here we have 25 rows, giving a total data density of 2,000 characters. In this mode each 5×7 matrix cell is about 2.5mm wide and 3.5mm high on a 37cm screen (see Fig. 14), so a high-resolution tube with 720 or 800 dot capability across its screen width is required. A standard-resolution tube will display 80-column text, but it’s tiring to decipher and not suited to long-term viewing.

Computers used for fine graphics in CAD, imaging, mapping and simulation can generate 132-column graphics (even more for special purposes like digital high-resolution TV) so a very high-resolution tube is required, preferably larger than 51cm if this sort of data density is to be discerned and appreciated!

Character-generator Outputs

Whether the data source is off-air, off-line, a microcomputer or a full-blown computer, the data displayed is generated inside a character generator chip. The video signals from this consist of square pulses that are precisely timed with respect to the line and field scanning rates. Plainly, the higher the column count the narrower the pulses. In the case of a colour display they are separately generated for R, G and B, and will usually be at TTL level, i.e. 5V on, 0V off. Simple on/off signals used to control each tube gun can give the three primary colours plus, in combination, their complementaries and white, i.e. a total of eight distinctive colours – white, yellow, cyan, green, magenta, red, blue and black, corresponding to the standard colour bars.

Most ordinary home computers costing £100–£200

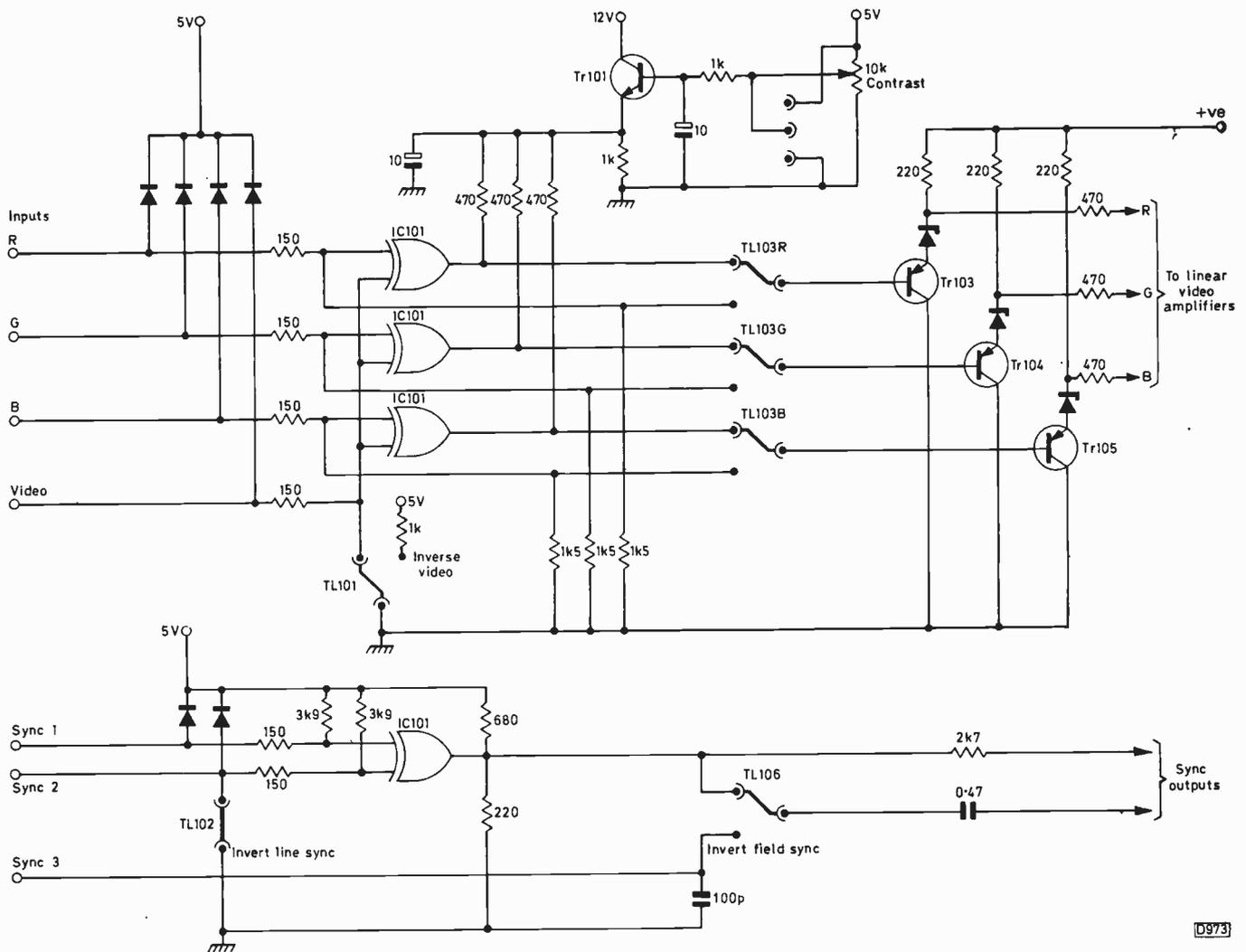


Fig. 15: Representative computer monitor video input circuitry. TTL or linear operation is selected by means of links TL103R/G/B. The exclusive-OR gates in IC101 invert the video pulses when link TL101 is changed and the line sync pulses when TL102 is present. Transistor Tr101 forms the upper leg of a resistive attenuator for contrast control in the TTL mode. Tr103/4/5 and the accompanying zener diodes provide level-shifting and temperature compensation.

provide these eight colours. Some computers, i.e. the Amstrad 464, have two levels of drive for each RGB output. These extra levels give a total of 27 colours. Other sources offer Y plus RGB outputs, with the separate Y signal setting the brightness of each colour, typically with two levels to give 16 colours (WYCGMRBB plus eight half tones). The Acorn Electron, BBC B and Commodore 64 provide 16 colours in this way. The Sinclair Spectrum is unusual in having YUV access only, so that an interfacing circuit is required to convert to RGB drive. Some commercial monitors (e.g. the Microvitec 1431/MZ) have a suitable converter built in. Alternatively an interface unit can be made up – see for example John de Rivaz's article in the July issue.

Sockets

There are several standards for monitor input signal levels and a wide variety of socket types. For professional monitors in analogue applications the BNC socket is most popular, usually with looped-through outputs to corresponding BNC output sockets. DIN and BNC sockets are used on TV receiver/monitors and I've come across phono socket inputs on small monochrome monitors. Professional data monitors are often fitted with a Cannon 9-pin D-type socket, while commercial monitors for home

computers tend to use a standard 6- or 7-pin 240° DIN socket. What's important here is to ensure that you have the correct connecting lead to link computer and monitor! Monitor manufacturers are very helpful in this area. Finally the SCART socket is making a welcome appearance on all types of AV equipment.

Inputs

Regarding input signals for monitors, the standards that have been established are as follows.

- (1) Composite video. Video signal plus sync (7:3 ratio), 1V peak-to-peak at 75Ω. This applies to most monochrome monitors.
- (2) CVBS. Input signal encoded to the PAL or other standard. Vision/sync/burst ratio 7:3:3, total 1V p-p at 75Ω.
- (3) RGB-linear. Separate wideband analogue inputs for R, G and B at 1V/75Ω. A separate composite sync input is usually provided, looking for sync pulses of between 1V and 8V peak. Positive or negative sync is in most cases catered for by means of a rear-mounted switch or movable links. Some monitors will accept sync with the analogue input (called composite RGB) in which case the sync pulses are generally taken from the G channel. For data and graphics display in this mode, 1V corresponds to on and 0.3V to off, as opposed to TTL-linear.

The above three analogue standards are usually acceptable within an amplitude tolerance of $\pm 6\text{dB}$.

(4) RGB-TTL. This is the most common mode for computer operation. The separate RGB inputs are designed to take TTL pulses (0V off, 5V on, into $1\text{k}\Omega$ or $1.5\text{k}\Omega$) direct from the output pins of a character generator chip. In practice the computer's outputs have interfacing buffer stages to protect the chip. To eliminate hash, computer noise or possible shading effects, the monitor's RGB amplifiers (now operating in effect as switches)

change state at about 1V, input level variations above this threshold having no effect on the brightness level. An input circuit operating in this way is shown in Fig. 15. It's important to remember that this "switched" RGB mode can offer only eight colours (including white and black), and that for 16 or more colour displays recourse must be made to RGB-linear inputs.

(5) TTL-linear. This mode permits brightness control by the computer. It has the 5V for white capability of the RGB-TTL mode but no two-state threshold switch.

VCR Clinic

Toshiba V9600

After replacing some prematurely worn video heads on a Toshiba V9600 (not an uncommon occurrence) and an upper drum cylinder I noticed that the head drum still rotated after stop had been selected. This explained why the heads had worn to a frazzle. I suppose that when the customer stopped the machine and left it the heads just kept on going. The capstan motor did too. There was no tape transport as the pinch roller was off. Attention was directed to the systems control section and it transpired that whilst motor control pin 7 of the microcomputer chip IC601 went from high to low when play was selected it didn't go back to high when stop was selected. The chip (TMP4320P-6202) was changed to the satisfaction of all concerned.

A point worth noting is the video head heights. When the tracking control was rotated the f.m. replay levels from the two heads rose and fell in opposite directions with the test tape. This results in a noisy picture. Head height adjustment is very critical and should not be attempted without experience. On some occasions it's given extended head life to a V9600 where poor picture has been due to differential heights and not just wear. **S.B.**

Grundig 2 x 4 Super

A Grundig 2 x 4 Super produced very spotty pictures when monitored in the record mode. Unfortunately we changed the tuner before we discovered that the trouble was due to the i.f. preamplifier transistor TR2302 (BF324) in the i.f. can. **S.B.**

Sony C7

Andy was singing a variation on "We'll meet again some SONY day" as he carried in a C7 from Geoff. It needed – no, not a rewind kit – new heads. After fitting the heads replay was interrupted by much muting of the sort usually caused by tape edge damage. This time the cause was a worn control track head. So a new audio/control track unit was fitted – personally I'd have preferred to fit just the head itself rather than half a machine. **S.B.**

Ferguson 3V29/3V30

A few cases of failure to erase the sound on Ferguson 3V29/30s have come in recently. In three machines this was due to the wires that go into the plug on the erase head. Crimped connectors are used, and the wires fell out with a gentle pull. In two cases the trouble was due to dry-

Reports from Steve Beeching, T. Eng., Derek Snelling, Philip Blundell, Eng. Tech., Les Harris, John Coombes and Dewi James

junctions where the small PCB solders on to the erase head.

Another problem that's beginning to show on these machines is failure to complete loading. The arms load fully but the mechanism doesn't operate enough to close the after-load switch. This is caused by the loading belt. **D.S.**

Hitachi Eject Mechanism

Here's a problem you may get with the eject mechanism on certain Hitachi models. On some of these the eject is damped by a hydraulic clutch. If the VCR is kept in a warm position the oil in the clutch tends to thin and run out, with the result that after about twelve months the cassette housing comes up like a rocket. I've had this on a VT11 and a VT9500 so far. The clutch is sealed and thus has to be replaced. **D.S.**

Sanyo VTC5150

The fault on this machine was no colour on playback. A burst with the hairdryer and freezer proved that IC1009 (M51439P) was heat sensitive, but a replacement was just the same. When the fault was present there was no chroma signal at pin 27 (TP1016). Voltage checks were next made around the i.c., the only discrepancy being at pin 26. When the resistor connected to this pin (R1297, $12\text{k}\Omega$) was checked it was found to be high in value at some $40\text{k}\Omega$. **P.B.**

Ferguson 3V35

A rather unusual fault came my way recently on a Ferguson 3V35. The problem was no playback, though E-E and record worked satisfactorily. We took the machine to the workshop and removed the top so that tests could be carried out. A quick check showed that the fault was still present. I decided to check the playback 9V supply: the transistor that switches this is on the luminance/chrominance board, which is mounted upside down at the top of the machine, over the video heads. Because of its position and the presence of ventilation holes directly over the board dust tends to gather here. This one was thick with it. A paintbrush was used to clear the dust so that the relevant transistor could be located when lo and behold the fault disappeared. No dry-joints could be found, and anyway the board hadn't been tapped, just brushed. I can only conclude that some of the fluff or dust was of a conductive nature – the machine's been back with the

customer now for some three weeks with no recurrence of the problem. **D.S.**

Hitachi VT33E

This machine would work in all modes except fast forward. After making a few checks I decided to change the systems control board to speed up diagnosis. This made no difference however. The capstan/reel drive i.c. is on the power supply panel, and on changing this one the fault went. Three data lines go to pins 10, 11 and 12 of the capstan drive i.c. (M545484): 11 and 12 were shorted together due to a solder short under PG112. **L.H.**

Ferguson 3V31

This machine would run all right for about twenty five minutes on playback. Its drum speed would then increase. This was traced to the μ PC1458 dual operational amplifier i.c. (IC13) – pin 7 went high in the fault condition. **L.H.**

Toshiba V8600

A V8600 came in from one of the branches with the complaint that playback of prerecorded tapes was o.k. but a noisy picture was produced when its own recordings were replayed. I decided to check around IC401 (TA7637P) which contains the f.m. modulator (amongst other things). As the f.m. waveform (TP202) was crushed the i.c. was replaced, but this made no difference. The f.m. comes out at pin 30, and on making some voltage checks there was found to be a 2V difference between pin 30 and TP202. R400 which links these points was 1k Ω instead of 100 Ω . **L.H.**

Toshiba V8600

A couple of faults we've had with this machine. Picture jumping in the record, playback and still modes has been caused by the TM4217P servo i.c. (IC501). If the on indicator is not alight or flashes on and off check R816 (15 Ω) which may be intermittent or open-circuit. **J.C.**

Sanyo VTC5300

In the event of failure to load or unload, try moving the guide ring. If this produces the required action replace the loading belt. **J.C.**
See also page 607, September – *Editor*.

Toshiba V9600

Problems we've had with this machine have been as follows.

No results: Check fuse F804 (500mAT). The fuse can blow due to transients on the power supply. This usually happens with the machine in the standby mode.

Luminance smearing: Check IC201 (TA7637P) by replacement.

Smearing on playback: Check IC104 (TA7636) by replacement.

Ejects cassettes: Check the cassette in switch S651 on the loading unit. If the switch is all right check whether the spring has dropped off the switch lever. The lever sometimes cracks.

No colour on playback: Check the pilot burst removal i.c. (IC206, TA7347P).

No rewind or slow rewind: Check the rewind idler assembly. The idler wheel can be changed on its own but it's best to replace the idler clutch assembly complete.

Capstan running at full speed: Check crystal X961 (2.968MHz) on the servo clock panel (U961).

No line lock: Check the adjustment of T961 on the servo clock panel (U961). Adjust for a stable picture on reverse search.

All function lights on, cassette loading and unloading automatically: Check the voltages around the microcomputer i.c. (IC601). If o.k. check the clock frequency (455kHz) at pins 24/5. If this is missing replace the ceramic resonator (Z601). **J.C.**

Mitsubishi HS303

We've had the following faults on this model.

For tape looping, no cue or review, poor rewind or a noise bar on the screen check for a faulty reel motor.

In the event of no record, playback all right, check the carrier set trimmer VC2B0 (50pF) in the f.m. modulator circuit (Y/C panel) by replacement – it can go high impedance.

If the drum speed is unlocked and the capstan speed varies, check IC4A0 (AN6350) by replacement.

If the capstan runs fast and won't switch off, check the waveform at pin 7 of IC4A1 (AN6341N). If this is missing, replace the i.c. If not, check the capstan drive transistor Q4A3 (2SC2603).

For displaced colour/cogging/intermittent snowy picture in the playback mode check for a squarewave at pin 25 of IC4A0. If this is missing check back to pins 9/10 of IC4A6 (TC4066BP), then pin 11, pin 7 of plug/socket VH and back to the junction of diodes D601/2. Next check that the 4.43MHz oscillator is producing an output (TP6N) – check with a frequency counter at pin 3 of IC603 (AN6342N). Trouble here is likely to be due to the 4.43MHz crystal (X601). Trimmer VC601 (45pF) is also suspect. **J.C.**

Sony C7

These machines tend to blank off the sound and vision when playing back their own recordings – the problem can occur at the beginning, end or middle of the tape and is due to slight wear on the control head and perhaps insufficient control head amplifier gain. To improve matters the gain of the control amplifier (AS3 board) can be increased by changing the value of R123 from 1.5k Ω to 2.7k Ω and replacing D30 with a 180 Ω resistor.

Channel display stuck on ch. 18 was traced to gate chip IC7 on the timer board. **D.J.**

Hitachi VT19

We've had a few cases where the counter display clears itself in the fast forward and rewind modes. This is due to the microcomputer i.c. IC2010 which should be replaced (type HD38805A27). **D.J.**

Panasonic NV370

The problem we had with one of these machines was that it went into fast forward when the play button was pressed and into fast rewind when record was selected. There was also no eject. The culprit was C6011 on the syscon board – it was open-circuit. **D.J.**

Letters

THE IPSALO-2 CIRCUIT

I was particularly interested in the description of the Ipsalo-2 circuit in the September issue. Its principle of operation is covered by British Patent Specification number 1 502 074 which was filed in April 1976. This patent was the result of further development work following an earlier patent, the work being carried out whilst I was working at Texas Instruments Ltd. in the early 70s. It's interesting to note the effect of time on design objectives. The earlier patent minimised the number of then high-cost power semiconductors while the later one minimised the use of by then high-cost wound components and had to provide mains isolation.

From the designer's point of view the system has several advantages over the more common arrangement with separate switch-mode power supply and line output stages. Only one transformer instead of two is required, and in addition high leakage inductance (wide spacing) is necessary between the primary and secondary windings for good isolation. Energy is transferred to the deflection side of the circuit during the flyback, resulting in a longer efficiency diode conduction time and hence better scanning linearity.

Eight years is a long time in the television industry, and it's gratifying to find that even after such a time Salora considers the idea worth putting into production. What happened to the earlier patent? That one lapsed some years ago but lives on in service engineers' memories not as a number but in the name Syclops!

*M.J. Maytum,
Willington, Bedford.*

THORN TX9 CHASSIS

In reply to the query raised by Robin D. Smith in the September issue (TV Fault Finding, page 594), D66 is not required on the PC1040 main panel (TX9 chassis) due to the revised circuitry around the mains rectifier thyristor. With the later circuit configuration D67 also carries out the function previously performed by W66, i.e. preventing the thyristor's protection capacitor C142 affecting the zero crossing point of the rectified mains.

*John Jameson, Technical Publications,
Thorn EMI Ferguson Ltd., Enfield.*

MUSIC CENTRES

I'm prompted to write to you following the mention in Les's column (June) of premature failure of SN76003 i.c.s and their replacement, after appropriate circuit modifications, with SN76023s. I too used to have this problem with what I assume is the same chassis (Fidelity). There seem to be three failure modes with these units. (1) Customer induced, due to lengthening the speaker leads and shorting them out. (2) Excessive h.t. voltage. (3) Customers again, unplugging and replacing the speaker plugs with the unit switched on.

There's not much one can do about the first problem except replace the i.c.s and tell the owner not to do it again, but it's a good opportunity to carry out the modifications described below. The problem of excessive h.t. is easily put right though I find the reason for it

inexplicable. There are two ways to reduce the h.t., which can be anything up to 32V – 28V is common – instead of the 24V specified. One is to insert a dropper resistor in the lead from the transformer's secondary winding – about 15Ω, wirewound works well. It's far easier to unwind a layer of turns from the secondary winding however. Fortunately it's easy to get at, doesn't take more than a few minutes to do and works well. The third problem, with the speaker plugs, can (other than not doing it!) be cured by adding a 1k-2.2kΩ resistor across each speaker socket, inside the case. This has negligible effect in normal use compared to the 8Ω or so of the speaker but prevents the coupling capacitor charging so quickly when the speaker is plugged in that the i.c. is destroyed. It takes only a minute, and prevents bouncers – particularly as most customers will never admit to having done it in the first place, which can lead to an embarrassing argument. This last modification is also well worthwhile with Stereosound music centres using TDA2611 i.c.s.

Fidelity chassis often use a cluster of components to deliver 12.5V to the preamplifier stages. These components often cause problems. An uprated transistor will help, but a once and for all solution is to fit a 12V i.c. voltage stabiliser (50p from Sendz) and ditch all the other bits. I keep meaning to try one of these in a Ferguson 3816 (1590 chassis). A 6V voltage stabiliser is a very worthwhile addition to those green and yellow Philips clock radios: it makes such a vast improvement that one wonders why they were not fitted in the first place – but of course they were not invented then!

None of this has much to do with TV, but I would guess that most engineers get involved in these related fields from time to time and may well do so more often as TV sets become more reliable.

*Alan J. Gamble,
Ormskirk, Lancs.*

HEATHKIT GR9900

There seems to be considerable difficulty in obtaining i.c.s for use in the Heathkit GR9900 12in. monochrome portable – in particular the SN76001 which was used in the audio and field output positions. There appear to have been several versions of this i.c., the type required having heatsink tabs. One faulty chip I have is labelled SNX76001ND which no one seems to have heard of. Have other readers had to replace these i.c.s? Have they any suggestions about what to use?

*Dr. R.C. Armstrong, FZS,
Holme-on-Spalding-Moor, York.*

COMPONENT TESTER

In the letters page last month Dr. Rankin described a modification to the component tester to reduce the X output. The simplest way to do this is to use a switch as

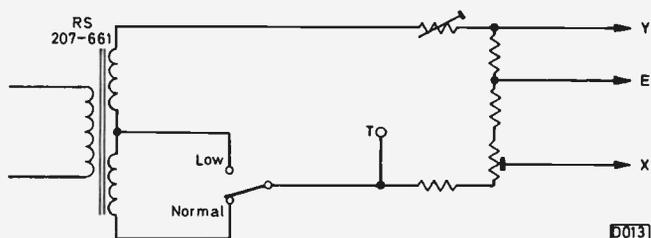


Fig. 1: Suggested method of reducing the output voltage provided by the component tester.

shown in Fig. 1. This will also reduce the Y output, but nevertheless works well. Dr. Rankin's method would appear to be perfectly satisfactory. Normally however it shouldn't be necessary to reduce the output. I've used and tested the unit with a wide variety of scopes, including the Telequipment D61. Large numbers of workshops use this model, which is one of the best service scopes around. Variations did occur with the D61 - some for example had 5mm sockets instead of BNC inputs - and this might account for Dr. Rankin's experience. It's important to use the correct RS mains transformer as a slight increase in the a.c. output voltage could cause problems.

I hope other users are obtaining good results with their component testers.

David Botto,
Bournemouth, Dorset.

SOUND TROUBLES

Sorry to disagree with Les Lawry-Johns (October issue) but the volume control in the Decca 30 series chassis is 50kΩ linear. I find it puzzling that the sound came up loud and clear with the wrong type fitted. Also Nick Lyons mentions trouble with the PCL86 used in the IIT CVC8 chassis. Wouldn't it have been simpler to change this 90p valve in the first place rather than pay repeated visits to the set?

C.P. Bird,
Selby, N. Yorks.

Editorial note: Sorry for the confusion. It was a 1730, not an 1830. The 1730, as with the earlier 10 series chassis, uses a 500kΩ semi-log volume control. The 1830 and other 30 series sets use a 50kΩ linear volume control with other changes in the coupling network between the intercarrier sound i.c. and the PCL82.

WORTH NOTING

A couple of problems I've had recently may be of interest to other readers. The first concerned a GEC 3133 monochrome portable with start-up problems - it's the set with the "switch mode pump" circuit. The trouble was traced to the boost diode D205 (BYX55/300) which was short-circuit, holding down the start-up supply. The second problem was with a Decca colour set fitted with the 90 series chassis. Due to severe internal flashover a new tube and a new beam cut-off transistor (Tr213) had to be fitted. Result - no picture but a blank raster with flyback lines when the first anode preset was advanced. Two days later I discovered that the PC board printing for the connections to Tr213 was the wrong way round. Naughty that!

C.A. Jackson,
Sutton-on-Forest, York.

MODEL NUMBERS

I find the servicing articles in your magazine most helpful but there's one big difficulty - relating the chassis types you always quote to the set on the bench, which often has a model number and nothing else. A case in point is the Grundig GSC100 and GSC200 chassis dealt with in the September issue. Couldn't you publish some tables of model numbers linked to chassis, as Thorn do from time to time in *Ferguson Feedback*?

Thanks anyway for all the gen - I always read Les before all else! Incidentally I'd like to find good homes for

BILLINGTON VALVES

Irwin Drive, Horsham, W. Sussex RH12 1NL

Mail Order Only; No Callers Please

Specialist Valve and Vintage Service
NEW, BOXED, GUARANTEED VALVES

3AT2B	£4.60	ECH84	£0.70	EY86/7	£0.65	PCF801.Mul	£2.35	PL95	£2.00
6J5	£2.50	ECL80.Maz	£1.40	EY500A	£1.50	PCF80+	£0.60	PL504+	£0.95
6SJ7M	£5.50	ECL82+	£0.58	EZ80	£1.00	PCF802	£0.60	PL508	£1.90
12BY7A	£3.15	ECL84	£0.90	EZ81	£1.00	PCF805	£1.80	PL509.Mul	£7.00
12HG7	£4.20	ECL86	£0.95	GY501	£1.45	PCF806	£1.15	PL519+	£4.45
17DW4A	£3.75	ECL85	£1.00	GZ32	£1.60	PCF808.Maz	£1.65	PL802T	£4.50
21LUB	£5.10	EF80+	£0.30	GZ34.Mul	£3.45	PCH200.Maz	£1.45	PL802	£6.90
30FL1/2	£1.50	EF80.Mul	£1.20	KT88(USA)	£12.00	PCL81	£2.00	PY88	£0.50
30FL12	£1.60	EF85	£0.35	KT88(UK)	£16.00	PCL82	£2.00	PY500A+	£1.60
DY86/7.Mul	£1.50	EF85.Mul	£1.75	KT66(USA)	£8.50	PCL83.Mul	£2.50	PY81/800	£0.69
DY87+	£0.53	EF89.Mul	£2.10	PC86.Maz	£1.45	PCL84.Mul	£2.00	PY801	£0.69
DY802	£0.85	EF95.Mul	£5.75	PC88	£0.75	PCL84	£0.80	U26.Maz	£1.70
EAB80.Mul	£1.25	EF183	£1.00	PC92	£3.00	PCL85+	£0.90	UCC85.Mul	£1.60
ECC81	£1.10	EF184	£0.50	PC97	£1.00	PCL86+	£0.80	UCH81.Maz	£2.20
ECC82	£0.95	EH90	£0.90	PCC84	£0.50	PCL905+	£1.00	UCL82.Mul	£1.70
ECC83	£0.76	EL34.Mul	£3.45	PCC89	£0.70	PD500	£2.90	UCL83	£1.85
ECC84	£0.80	EL84+	£0.70	PCC189	£0.70	PFL200.Maz	£1.30	UF89.Mul	£2.50
ECC85	£0.95	EL90	£1.80	PCC805	£1.30	PFL200+	£0.85	UL41.Mul	£4.60
ECC88	£0.95	EF86	£1.40	PCF82.Maz	£1.50	PL36	£0.80	UY85.Maz	£1.30
ECF80	£0.74	EL509	£6.90	PCF86	£1.20	PL81.Maz	£0.90	X78	£18.00
ECF82	£0.85	ELL80	£20.50	PCF200.Mul	£3.45	PL83	£0.80		
ECH81+	£0.50	EM87	£2.30	PCF800	£1.35	PL84	£0.75		

+ Denotes imported brand of valve. Mul = Mullard, Maz = Mazda

S.A.E. QUOTATION ON ANY TYPE NOT LISTED

New valves are guaranteed 90 days. If denoted "Mul", "Maz", valves supplied are assured to be Mullard, Mazda respectively. Types denoted "+" are imported brands. All other types are good quality brands.

All valves listed are in stock at time of going to press. Discounts on 25+ of one type.

USED VALVES Tested working. Clean. Boxed. 28 days guarantee. At 20p: DY87, EB91, ECL80, EF80, EF183, EF184, PCC189, PFL200, PY33, 6F23. At 25p: GY501, PCF808, PCL82, PCL84, PL36, PL504, PY81/800, PY801, U191. At 100p: PCF200, PCL83, PD500, PY500, PZ30.

We have in stock Cathode Ray Tubes, Valve Sockets, certain transistors and I.C.s: S.A.E. for quotation on your requirements.

We can supply, from stock, virtually any valve - radio, TV, audio, transmitting. Send S.A.E. for quotation by return or 35p for October catalogue.

WE ARE KEEN TO PURCHASE ALL TYPES OF VALVES.
Please add 60p post + packing, then add VAT @ 15%.

the following: G6 not working, Pye hybrid working, several 405-line sets some working, 405-line signal generators, many reel-to-reel tape recorders and lots of junk - mostly free to callers.

E.J. Gordon Madgwick,
Thursdays, Whitmore Vale,
Hindhead, Surrey GU26 6JA.

Editor's comment: Most manufacturers produce a few basic chassis which are used in large numbers of different sets, hence our use of chassis type numbers for identification. To tabulate models would in some cases be difficult without going into other aspects such as control and tuning arrangements etc. For the record the GSC100 was used in Models 1514GB, 4415GB, 6215GB, 6415GB and 6615GB; the GSC200 was used in Models 1644GB, 1645GB, 4245GB, 4445GB, 6245GB and 6445GB.

MORE ON PLUGTOPS

I read with interest the letter from C.A. Burrows concerning burning of the neutral pin in mains plugs - also previous letters commenting that the neutral pin seems to undo itself. May I suggest that the reason for these effects is simply electron flow? Remember that electrons flow from negative to positive. One doesn't get a shock from the neutral side of the supply because one's already charged to this potential - it's the potential difference at the positive side that draws current and gives you a shock.

Wasn't it a gentleman named Ampere who said that current flows from positive to negative? We now know better!

Rothley Stevens, Radio and Television,
Coventry.

ECONOMIC DEVICES, PO BOX 228, TELFORD TF2 8QP

18029	1.58	ZSC1061	0.54	2SD8988	2.87	AN320	4.97	BC171	0.10	BD186	0.38	BF137	0.11	BLY46	2.88	BY203/20	0.10
18181	1.13	ZSC1096	1.06	40408	0.45	AN322	4.38	BC172	0.09	BD188	0.06	BF152	0.28	BR100	0.28	BY206	0.17
18182	0.13	ZSC1104	2.00	40594	1.39	AN331	2.99	BC172B	0.24	BD175	0.39	BF153	0.52	BR101	0.37	BY207	0.22
18334	1.00	ZSC1106	4.12	40595	1.39	AN337	3.99	BC173	0.15	BD177	0.39	BF154	0.23	BR103	0.45	BY210-400	0.24
18335	0.72	ZSC1114	5.61	40636	0.86	AN340P	1.86	BC174B	0.24	BD179	0.44	BF157	0.23	BR888	0.58	BY210-800	0.27
18446	0.88	ZSC1124	1.18	40871	1.39	AN355	3.06	BC177	0.10	BD181	0.90	BF158	0.16	BRC-M-300	1.50	BY210-800	0.30
18800	1.25	ZSC1151A	4.29	40872	1.39	AN382	1.47	BC178	0.23	BD182	0.90	BF159	0.16	BRCC116	0.00	BY223	0.05
18799	2.16	ZSC1152	4.25	60057	1.18	AN5111	2.34	BC179	0.23	BD183	0.90	BF160	0.28	BRCC130	1.00	BY224-400	0.90
18801	0.80	ZSC1157	4.12	74LS132	0.72	AN5132	3.99	BC182	0.00	BD184	1.10	BF167	0.34	BRCC300	1.82	BY225-100	0.79
18802	1.03	ZSC1162	0.95	74LS138	0.85	AN5250	3.33	BC182B	0.23	BD187	0.40	BF173	0.30	BRCC443	1.12	BY226	0.28
18803	4.31	ZSC1172	1.92	74LS157	0.79	AN5435	2.00	BC182L	0.09	BD189	0.35	BF177	0.50	BRCC444	1.12	BY227	0.44
18805	1.35	ZSC1195	2.83	74LS161AN	1.10	AN5610	6.75	BC182LB	0.10	BD190	0.59	BF178	0.36	BRCC5298	0.76	BY228	0.54
17074	6.00	ZSC1213	0.75	74LS198	1.25	AN5613	3.72	BC183	0.09	BD201	0.54	BF179	0.32	BRCC6109	0.75	BY225	0.97
17127	3.91	ZSC1226	1.32	74LS200	0.25	AN5620X	4.63	BC183L	0.09	BD202	0.54	BF180	0.32	BRCC82	0.96	BY298	0.25
17376	1.43	ZSC1308	0.85	74LS244	1.65	AN6320N	3.89	BC183LB	0.23	BD203	0.54	BF181	0.29	BRCC83	0.90	BY299	0.25
1N4001	0.05	ZSC1307	1.35	74LS30	0.29	AN6342	1.36	BC184	0.09	BD204	0.54	BF182	0.30	BRCC84	0.90	BY476A	0.76
1N4002	0.05	ZSC1316	3.40	74LS367	1.05	AN6344	4.00	BC184L	0.09	BD207	1.00	BF183	0.35	BRCC85	0.54	BYW56	0.36
1N4003	0.05	ZSC1384	0.49	74LS373	1.55	AN6363	10.20	BC184LB	0.23	BD208	1.00	BF184	0.39	BRCC86	0.45	BYX10	0.20
1N4004	0.06	ZSC1383	1.39	74LS47	1.05	AN6551	0.56	BC186	0.24	BD222	0.44	BF185	0.35	BRCC87	0.50	BYX55-350	0.40
1N4005	0.07	ZSC1398	0.51	74LS73	0.39	AN6552	0.52	BC187	0.12	BD225	0.44	BF194	0.15	BRCC88	0.50	BYX55-800	0.25
1N4006	0.07	ZSC1410	2.17	74LS74	0.39	AN7145	2.84	BC204	0.14	BD228	0.57	BF195	0.12	BRCC89	0.30	BYX71-350	0.87
1N4007	0.07	ZSC1413	3.00	74LS75	0.52	AN7150	2.22	BC207	0.12	BD229	0.63	BF196	0.15	BRCC90	1.17	BYX71-800	0.65
1N4148	0.03	ZSC1505	0.56	74LS86	0.49	AN7151	2.85	BC212	0.10	BD231	0.45	BF197	0.14	BSS38	0.30	BYX94	0.10
1N4448	0.12	ZSC1578	0.67	74LS90	0.75	AN7156	2.85	BC212B	0.23	BD232	0.44	BF198	0.15	BSTBD1409	2.40	BY956	1.89
1N5401	0.12	ZSC1617	3.35	74LS92	0.75	AN7158	2.34	BC212L	0.00	BD234	0.30	BF199	0.15	BSTBO1405	4.37	BZV15-C12	0.72
1N5402	0.13	ZSC1670	2.04	74LS93	0.75	AN7218	1.49	BC212LB	0.23	BD235	0.43	BF200	0.33	BSTCO146	2.25	BZV15-C12R	0.72
1N5403	0.14	ZSC1678	1.25	74LS95B	0.65	AP58076	4.25	BC213	0.09	BD236	0.45	BF216	0.32	BSTCO223	2.25	BZV15-C24	0.72
1N5404	0.15	ZSC1810	1.40	7805 TO-220	0.03	AS5805	1.43	BC213L	0.09	BD237	0.30	BF218	0.32	BSTCO246	4.51	BZV15-C24R	0.72
1N5408	0.18	ZSC1815	0.41	7805 TO-3	1.05	AU106	1.96	BC213LB	0.23	BD238	0.29	BF222	0.50	BSTCO233	3.91	BZV15-C30R	0.72
1N914	0.05	ZSC1829	2.01	7806	0.06	AU110	1.96	BC214	0.09	BD239	0.44	BF224	0.15	BSTCO3146	0.71	BZV15-C30R	0.72
1S44	0.06	ZSC1875	4.77	7808	0.54	AU113	2.15	BC214L	0.12	BD240	0.36	BF227	0.59	BSTCC0143	2.79	BZV15-C11	0.54
1S5012A	0.73	ZSC1891	3.35	7812 TO-3	0.54	AY102	2.82	BC214LB	0.23	BD2400	0.47	BF240	0.15	BSTCO0843	3.00	BZV15-C12	0.54
1S921	0.90	ZSC1929	2.25	7812 TO-220	1.05	AY105K	1.89	BC225	0.24	BD241	0.45	BF241	0.15	BSTCO0843	2.86	BZV15-C15	0.54
2582	1.24	ZSC1942	0.75	7815	0.55	AY106	1.92	BC227	0.09	BD242	0.45	BF244	0.23	BSTCO0843	0.30	BZV15-C20	0.54
2N1302	0.24	ZSC1946	4.11	7818	0.55	BA102	0.30	BC238	0.09	BD243	0.44	BF245A	0.54	BSTCO0843	0.30	BZV15-C24	0.54
2N1303	0.34	ZSC1953	1.75	7824	0.55	BA1310 (IC)	1.72	BC238A	0.11	BD243A	0.44	BF255	0.13	BSTCO0843	0.30	BZV15-C24R	0.54
2N2218	0.20	ZSC1957	0.86	AC107	0.06	BA1320 (IC)	1.22	BC239B	0.06	BD244	0.44	BF256	0.25	BSTCO0843	0.45	BZV15-C24R	0.54
2N2219A	0.39	ZSC1959	0.36	AC117	0.39	BA1330 (IC)	1.82	BC251A	0.15	BD244A	0.77	BF256LC	0.44	BSTCO0843	0.45	BZV15-C24R	0.54
2N2222	0.34	ZSC1982	1.75	AC123K	0.39	BA146	0.17	BC252	0.12	BD245C	0.60	BF257	0.30	BSTCO0843	0.45	BZV15-C24R	0.54
2N2846	0.75	ZSC1989	2.92	AC128	0.28	BA154	0.00	BC256	0.22	BD246C	0.74	BF258	0.29	BSTCO0843	1.46	BZV15-C24R	0.54
2N2904	0.32	ZSC2027	0.67	AC138	0.08	BA155-01	0.12	BC261A	0.20	BD253	0.95	BF259	0.30	BSTCO0843	1.20	BZV15-C24R	0.54
2N2905	0.39	ZSC2028	1.91	AC141	0.26	BA156	0.12	BC262	0.20	BD278A	0.60	BF262	0.51	BSTCO0843	1.31	BZV15-C24R	0.54
2N2906	0.34	ZSC2029	1.49	AC142K	0.39	BA157	0.17	BC287	0.45	BD317	1.96	BF263	0.51	BSTCO0843	1.31	BZV15-C24R	0.54
2N3053	0.24	ZSC2057	1.87	AC151	0.25	BA159	0.12	BC294	0.45	BD318	2.00	BF264	0.33	BSTCO0843	2.25	BZV15-C24R	0.54
2N3054	0.30	ZSC2073	1.40	AC153	0.30	BA182	0.17	BC301	0.36	BD375	0.30	BF271	0.10	BSTCO0843	2.25	BZV15-C24R	0.54
2N3055	0.55	ZSC2078	1.25	AC153K	0.36	BA222 (IC)	1.26	BC302	0.30	BD377	0.23	BF273	0.10	BSTCO0843	1.52	BZV15-C24R	0.54
2N3055H	0.77	ZSC2091	0.59	AC176	0.17	BA284/2	0.15	BC303	0.34	BD379	0.09	BF274	0.18	BSTCO0843	1.80	BZV15-C24R	0.54
2N3442	1.85	ZSC2122A	4.05	AC176K	0.40	BA301 (IC)	0.92	BC307	0.09	BD380	0.09	BF324	0.16	BSTCO0843	1.80	BZV15-C24R	0.54
2N3702	0.12	ZSC2141	1.09	AC179	0.25	BA302	0.90	BC307A	0.14	BD410	0.44	BF336	0.27	BSTCO0843	2.25	BZV15-C24R	0.54
2N3703	0.12	ZSC2166	1.35	AC183	0.05	BA311 (IC)	1.86	BC308	0.12	BD412	0.57	BF337	0.36	BSTCO0843	2.25	BZV15-C24R	0.54
2N3704	0.12	ZSC2216	0.82	AC186	0.30	BA312 (IC)	0.96	BC308A	0.09	BD418	0.76	BF338	0.36	BSTCO0843	1.80	BZV15-C24R	0.54
2N3705	0.12	ZSC2233	2.20	AC186K	0.50	BA313 (IC)	1.28	BC309	0.15	BD433	0.33	BF356	0.36	BSTCO0843	2.25	BZV15-C24R	0.54
2N3706	0.12	ZSC2271	3.84	AC187	0.35	BA316	0.07	BC317A	0.11	BD434	0.39	BF362	0.54	BSTCO0843	2.25	BZV15-C24R	0.54
2N3707	0.14	ZSC2278	1.83	AC187-01	0.40	BA317	0.87	BC323	0.92	BD436	0.42	BF363	0.54	BSTCO0843	2.25	BZV15-C24R	0.54
2N3711	0.14	ZSC2286-KT	7.81	AC187K	0.39	BA318	0.00	BC327	0.15	BD436	0.42	BF371	0.45	BSTCO0843	2.79	BZV15-C24R	0.54
2N3771	1.85	ZSC2325	1.70	AC188	0.33	BA328 (IC)	0.80	BC328	0.10	BD437	0.41	BF391	0.36	BSTCO0843	2.25	BZV15-C24R	0.54
2N3772	1.55	ZSC2351	0.95	AC188-01	0.40	BA333 (IC)	1.24	BC337	0.00	BD438	0.44	BF393	0.90	BSTCO0843	1.47	BZV15-C24R	0.54
2N3773	1.85	ZSC2370	1.00	AC188K	0.39	BA401 (IC)	0.50	BC338	0.10	BD441	1.29	BF417	1.20	BSTCO0843	1.25	BZV15-C24R	0.54
2N3819	0.28	ZSC2370A	0.95	AC193K	0.59	BA511 (IC)	1.90	BC380	0.36	BD442	0.56	BF418	1.70	BSTCO0843	2.20	BZV15-C24R	0.54
2N3823	1.86	ZSC264A	4.38	AC194K	0.59	BA521 (IC)	1.81	BC388	0.23	BD507	0.54	BF422	0.26	BSTCO0843	2.20	BZV15-C24R	0.54
2N3904	0.56	ZSC2671	1.99	AD140	0.96	BA532 (IC)	1.00	BC440	0.99	BD508	0.54	BF423	0.26	BSTCO0843	4.82	BZV15-C24R	0.54
2N3908	0.56	ZSC2728	0.95	AD142	0.96	BA536 (IC)	2.72	BC441	0.40	BD509	1.29	BF436	0.49	BSTCO0843	4.44	BZV15-C24R	0.54
2N4101	1.10	ZSC372	1.27	AD143	0.96	BA6304A (IC)	2.85	BC454	0.32	BD510	0.45	BF450	0.36	BSTCO0843	5.44	BZV15-C24R	0.54
2N4240	3.80	ZSC373	1.85	AD145	1.45	BA843 (IC)	3.00	BC455	0.32	BD518	1.36	BF451	0.26	BSTCO0843	2.70	BZV15-C24R	0.54
2N4443	1.35	ZSC383	1.20	AD149	0.81	BAV10	0.10	BC460	0.30	BD519	1.36	BF457	0.37	BSTCO0843	1.80	BZV15-C24R	0.54
2N4444	1.12	ZSC388	0.45	AD161	0.30	BAV18	0.10	BC461	0.42	BD529	0.30	BF458	0.35	BSTCO0843	2.25	BZV15-C24R	0.54
2N4914	0.85	ZSC41	1.99	AD162	0.30	BAV19	0.10	BC462	0.27	BD530	0.80	BF459	0.35	BSTCO0843	1.90	BZV15-C24R	0.54
2N5084	0.84	ZSC458	0.55	AD262	0.95	BAV20	0.10	BC463	0.58	BD533	0.80	BF460	0.54	BSTCO0843	1.90	BZV15-C24R	0.54
2N5293	0.45	ZSC485	0.83	AF114	2.24	BAV21	0.17	BC464	0.58	BD534	0.36	BF468	0.27	BSTCO0843	2.52	BZV15-C24R	0.54
2N5294	0.45	ZSC508	3.36	AF115	0.79	BAV12	0.10	BC465	0.58								

ECONOMIC DEVICES, REGISTERED OFFICE: 14, BEE LANE, FORD HOUSE, WOLVERHAMPTON WV10 6LF.

All goods should be delivered within 4 working days.

ESM532C	4.18	LM1302P/N	1.58	MPSU50	0.78	SAA5010	4.98	SN74190	1.81	TB029V	4.41	TBA395	1.25	TDA1230	2.93	TDAA9503	2.80
ESM832C	4.18	LM1310P/N	1.25	MPSU10	0.78	SAA5010	4.98	SN7420N	0.80	TB032V	1.00	TBA395Q	1.00	TDA1235	3.52	TDAS9513	2.40
ESM732C	4.18	LM3085N	0.77	MPSU55	0.90	SAA5020	5.25	SN7430	0.20	TB033V	0.73	TBA396	1.00	TDA1270	2.84	TE527	1.25
ETTR016	2.05	LM317CXC	1.38	MPSU56	0.90	SAA5030	7.50	SN7440N	0.24	TB035V	0.67	TBA400	2.10	TDA1327A	1.65	TE538	0.36
ETTR016	2.18	LM339N	0.80	MPSU80	1.20	SAA5040A	14.75	SN7473	0.58	TB036	0.44	TBA440P	1.05	TDA1327B	1.05	TE626	1.35
FND500	5.25	LM3407	1.29	MRS10	0.30	SAA5050	8.50	SN7474N	0.72	TB037	1.91	TBA480	1.42	TDA1370	1.80	TEA1002	3.15
FT3055	0.85	LM3407S	0.75	MRS12	0.60	SAA581B	1.80	SN7480AN	0.53	TB041V	0.86	TBA480Q	1.47	TDA1365	6.35	TDA1009	0.96
GF758	1.02	LM3407T	0.75	MRS14	0.40	SAA700	3.80	SN75110N	0.75	TB044V	0.86	TBA500PQ	1.85	TDA1412	0.95	TEA1009S	5.34
GF759	1.82	LM3407S	0.75	MSSD7002	0.65	SAB1008B	4.53	SN76001ANQ	2.25	TB045	1.80	TBA510	1.55	TDA1420	1.40	TEA1067	0.46
GF761	0.78	LM342N	0.58	MVS240	0.52	SAB1046P	3.06	SN76002N	2.25	TB049	1.00	TBA510S	0.39	TDA1470	2.63	TC106C	0.55
GK3F	1.05	LM384N01	1.84	MVS480	0.30	SAB301	7.34	SN76013N	3.63	TB052V	1.70	TBA520	1.87	TDA1512	2.20	TC106M	0.55
HA11211	2.30	LM5678CN	1.30	MVS480-02	0.50	SAB3012	5.34	SN76013ND	2.25	TB058	0.46	TBA520Q	0.46	TDA1670	3.65	TC116D	0.80
HA11215	4.00	LM746	1.85	MES458	2.95	SAB3013	3.28	SN76013NDG	0.87	TB059	1.85	TBA530	0.86	TDA1770	5.56	TC44	0.85
HA11225	3.90	LM830	2.78	MES458	3.00	SAB3021	7.18	SN76022N	2.35	TB061V	1.89	TBA530Q	0.85	TDA1905	1.25	TC45	0.70
HA11228	7.50	LM8361	2.78	MES534N	1.40	SAB3022B	12.34	SN76023ND	1.84	TB063V	1.89	TBA540	0.98	TDA1906	2.95	TC47	0.70
HA11235	2.51	M1024	2.55	MES55	0.34	SAB3023B	11.18	SN76029N	2.33	TB065V	2.18	TBA540Q	1.15	TDA1910	1.15	TC48	0.90
HA11235	3.80	M1025	4.70	MES56	0.75	SAB3024	4.77	SN76105N	2.36	TB067V	0.87	TBA550	1.95	TDA1910	2.20	TC49	0.46
HA1124	4.70	M1124	2.54	MES580N	1.10	SAB3205	3.18	SN76110N	1.13	TB069V	1.27	TBA550Q	2.25	TDA1950	2.54	TC50	0.80
HA11244	4.32	M1130	4.86	MES95N	3.20	SAB3210	2.93	SN76115AN	1.46	TB073V	5.81	TBA560C	0.86	TDA2002	1.29	TC51	0.80
HA1125	3.90	M191	5.74	ME9458N	3.00	SAB4205	12.75	SN76131	1.74	TB074V	1.52	TBA560CQ	1.15	TDA2003	1.05	TC52	0.70
HA11251	3.30	M193	18.55	ME946N	3.00	SAF1031	2.30	SN762280N	1.20	TB076	0.92	TBA570	1.15	TDA2004	2.52	TC53	1.80
HA1137W	2.57	M51102L	4.82	ME950N	3.94	SAF1032	5.80	SN76227N	0.80	TB078	1.29	TBA570A	1.95	TDA2006	1.25	TC54	0.96
HA1138	3.56	M5115P	4.34	ME9458N	3.00	SAF1039	11.86	SN76229N	2.97	TB079	0.35	TBA570Q	1.25	TDA2010	2.79	TC55	1.38
HA11414	2.58	M51231P	2.73	MP1106	4.80	SAS5010	7.82	SN76231	2.31	TB083V	1.25	TBA625A	1.97	TDA2020	2.75	TC56	0.78
HA1144	6.38	M5124P	4.38	OA200	0.10	SAS540	1.80	SN76242	4.75	TB085	0.18	TBA625B	1.97	TDA2030	1.85	TC57	0.41
HA1156	1.23	M5134-341	3.75	OA202	0.10	SAS580S	2.97	SN76243	4.75	TB086	2.56	TBA625C	1.97	TDA2140	1.44	TC58	0.50
HA11580	7.80	M51394P	8.25	OA47	0.10	SAS580T	2.85	SN76322	2.51	TB087	1.83	TBA641A12	3.75	TDA2150	5.83	TC59	0.47
HA1180	3.45	M5142P	4.38	OA90	0.87	SAS570	1.81	SN76360	1.97	TB089	0.82	TBA641BX1	2.87	TDA2151	1.75	TC60	0.85
HA1186	3.80	M5143P	6.86	OA91	0.80	SAS570S	0.80	SN76390	2.80	TB090	0.83	TBA651	2.00	TDA2161	3.84	TC61	0.41
HA1187	5.13	M5144P	3.42	OA95	0.80	SAS570T	2.50	SN76396	2.83	TB091	2.94	TBA673	2.35	TDA2161	1.80	TC62	0.83
HA11711	10.13	M51513L	2.86	OC28	0.96	SAS580	4.41	SN76510N	0.95	TB092	1.35	TBA700D	2.19	TDA2190	3.11	TC63	0.35
HA11713	6.70	M51515BL	3.10	OC29	1.95	SAS5800	2.82	SN76530P	1.90	TB093	4.36	TBA720	2.85	TDA2510	1.82	TC64	0.83
HA11714	7.85	M51516L	3.40	OC35	0.95	SAS590	4.55	SN76532N	1.80	TB094	4.36	TBA730	1.75	TDA2520	2.15	TC65	0.35
HA11715	7.85	M51517L	2.90	OC36	1.18	SAS5900	2.32	SN76533N	1.54	TB095	1.58	TBA750D	1.46	TDA2521	2.15	TC66	0.86
HA11718	6.73	M5152L	1.80	OC44	0.40	SAS800	2.50	SN76540N	1.80	TB096	1.58	TBA780	1.35	TDA2522	2.81	TC67	0.20
HA11724	15.80	M51522	4.90	OC45	0.40	SAS8000	1.28	SN76544	1.80	TB097	0.80	TBA780	3.80	TDA2523	2.75	TC68	1.87
HA11725	18.80	M5191P	4.49	OC75	0.40	SAS800S	1.28	SN76545	4.55	TB098	0.78	TBA800	0.80	TDA2524	4.50	TC69	0.40
HA1180	4.80	M5192	2.80	ON188	1.70	SAS8610	1.28	SN76546	3.15	TB099	2.84	TBA810AS	1.46	TDA2525	2.90	TC70	0.44
HA1203	1.58	M53273P	0.92	ON236	2.90	SAS8670	1.28	SN76548N	3.15	TB100	1.52	TBA810S	1.46	TDA2526	2.19	TC71	0.44
HA1306	1.74	M53274P	1.20	OT112	0.98	SAS8700	1.28	SN76549	2.35	TB101	3.35	TBA810T	1.46	TDA2532	2.51	TC72	0.39
HA1322	1.74	MA06	0.97	OT121	0.70	SAS8705	1.28	SN76550	0.30	TB102	1.35	TBA820	0.83	TDA2533	2.89	TC73	0.71
HA1339	1.70	MA8001	0.74	PD144	2.43	SAS8710	1.28	SN76551	1.35	TB103	4.85	TBA820M	1.85	TDA2540	1.95	TC74	0.44
HA1342	1.80	MB3705	1.82	PT1017	2.83	SAS8800	2.30	SN76552	2.80	TB104	1.95	TBA890	1.85	TDA2541	1.95	TC75	0.85
HA1350	2.37	MB3712	2.85	PT2014	1.76	SAS8810	1.30	SN76800	1.10	TB105	4.95	TBA900	2.25	TDA2545Q	3.18	TC76	0.48
HA1385	3.85	MB3713	1.38	PT8042	2.82	SBA5508	1.95	SN76611	2.35	TB106N	1.41	TBA920	1.50	TDA2560	1.97	TC77	3.28
HA1386WR	1.82	MB3730	2.94	R1038	1.99	SBA750	1.96	SN76820	2.35	TB107P	1.36	TBA920D	2.10	TDA2571A	2.81	TC78	1.21
HA1387	3.62	MC13002	4.86	R1039	1.99	SC9488P	1.46	SN76822	1.50	TB108P	3.85	TBA940	1.70	TDA2575A	2.95	TC79	0.80
HA1388	1.89	MC1303P	1.96	R2008B	1.28	SC9503	1.50	SN76823	0.82	TB1093P	1.84	TBA950	1.55	TDA2576A	5.58	TC80	2.82
HA1388R	1.86	MC1307P	1.90	R2009	1.20	SC9504P	1.46	SN76830	2.31	TB1102P	1.54	TBA970	2.80	TDA2577	5.31	TC81	0.26
HA1370	2.97	MC1310P	1.25	R2001B	1.28	SC9511P	1.20	SN76840	3.85	TB1108P	1.40	TBA970Q	2.98	TDA2581	1.95	TMS1000NL	16.78
HA1377	2.80	MC1327P	1.20	R2029	1.20	SCR957	1.20	SN76850N	1.24	TB1109	3.37	TBA990	1.85	TDA2582	1.98	TMS3748NS	11.76
HA1389	1.82	MC1330P	1.23	R2030	1.20	SG284A	4.38	SN76851	1.35	TB1120P	0.58	TBA990Q	1.95	TDA2590	2.80	TMS4116	1.87
HA1389R	1.74	MC1349P	1.20	R2257	2.16	SG613	7.00	SN76858N	2.25	TB1122B/P	0.54	TBAZ31	2.33	TDA2591	2.80	TV106	1.20
HA1392	2.80	MC1350P	1.10	R2265	1.95	SG629	6.28	SN76865N	1.35	TB1124P	1.20	TC4001	1.29	TDA2591Q	2.20	YG810B	2.70
HA1397	2.57	MC1351P	0.75	R2305	1.87	SG633	9.30	SN76866N	0.98	TB1130P	2.15	TC4063BP	3.94	TDA2593	2.84	YU1016	1.83
HA1398	2.80	MC1352P	1.81	R2306	1.23	SI-1020N	4.76	SN76705	3.38	TB1136AP	1.15	TCA150	1.82	TDA2594	2.80	YU143M	2.80
HA1406	1.80	MC1357P	1.95	R2322	1.26	SI-1125HD	16.70	SN76705N	3.99	TB1137P	0.85	TCA180B	1.82	TDA2600	5.00	U3700	0.55
HA17723	5.48	MC1358P	1.55	R2323	1.23	SI-1130N	6.30	SN76707N	3.99	TB1141AP	3.51	TCA270	1.55	TDA2610	1.55	U3700Q	0.55
HBF4030AF	2.25	MC14001	7.15	R2348	1.82	SKB2708	0.70	SN76709	4.65	TB1146P	8.84	TCA270S	1.95	TDA2611A	1.23	UA723CA	5.82
HD4480	15.80	MC14011	0.23	R2354A	1.82	SKE2F 1/04	1.26	SN76709N	4.95	TB1146P	5.10	TCA270SA	1.85	TDA2611AQ	2.55	UA758PC	3.87
HD44801A05	15.80	MC14013	0.37	R2354B	1.82	SKE2G 2/04	1.26	SN76730	4.23	TB1149P	2.18	TCA290A	2.85	TDA26120	4.25	UA783PC	1.06
HME231	8.50	MC14018CP	0.37	R2441	1.23	SKE2G 3/04	0.95	SN76810N	0.62	TB1153P	4.53	TCA420A	1.98	TDA2620	1.94	UA8170	2.14
HME232	7.71	MC14025	0.54	R2443	0.80	SKE4F 1/02	1.26	SN76820N	2.63	TB1161P	5.86	TCA440	1.85	TDA2630	2.36	UA8180	2.14
HMS102	2.92	MC14049UBC	0.52	R2461	2.18	SKE4F 1/06	0.86	SN9401A	3.45	TB1162P	4.25	TCA4600A	1.95	TDA2631	2.40	ULN2185	1.35
HMS104	2.94	MC1438R	0.95	R2477	0.92	SKE4F 2/06	2.10	SN9402	3.95	TB1169	4.80	TCA530	1.80	TDA2640	2.25	ULN2204	7.80
HT4207	15.80	MC14493P	2.56	R2501	1.18	SKE4F 2/06	0.80	SP886	0.50	TB1171P	2.53	TCA640	2.83	TDA2643	6.93	ULN2218F	1.95
IS689	1.87	MC14510BAL	3.15	R2540	1.80	SKE4G 2/02	0.87	STA441C	2.27	TB1172P	1.20	TCA650	1.85	TDA2651	2.95	UPC1001H	2.50
IS751	1.87	MC14558BCP	3.15	R2540C	3.80	SKE5F 3/10	1.45	STK0029	3.42	TB1176P	2.25	TCA680B	2.83	TDA2652	7.85	UPC1009C	5.74
ITV2003	0.20	MC1712	3.52	R2615	0.00	SL1310	2.85	STK0039	4.00	TB1193P	4.44	TCA7					

Remote Control for VCRs

Derek Snelling

Since the remote control systems used with VCRs rarely if ever seem to get mentioned in VCR Clinic I thought a short survey of such systems and some common faults would be of interest. The remote control systems used in VCRs fall into two categories, the wired type and infra-red ones. We'll look at the wired type first.

Wired Systems

The simplest are those with a screened lead and jack plug connection to the VCR. Examples are the Hitachi VT8000/VT8300/VT9300 and the Ferguson 3V29/3V30, plus the equivalents in other ranges. The one used in the VT8300 is typical: it consists of a thick-film resistor network in a ladder configuration, the various resistors

being switched by push switches – see Fig. 1. At the VCR end the Hitachi and Ferguson systems differ slightly. With the VT8300 the remote control unit is simply connected in the line from the front panel switches to the command decoder i.c., in parallel with the panel switches. In the Ferguson 3V29/3V30 however the remote and front panel switches are connected to separate comparator/converters in IC3 before being combined to address the microcomputer IC2 – see Fig. 2.

The wired remote control units used with the Mitsubishi HS303, HS304 and early Panasonic NV7000s have multicore cables with DIN-like plugs to connect them to the VCR. The NV7000 unit consists of a duplicate of the front panel controls, i.e. a dozen switches and diodes arranged as a matrix, a simple system that unfortunately

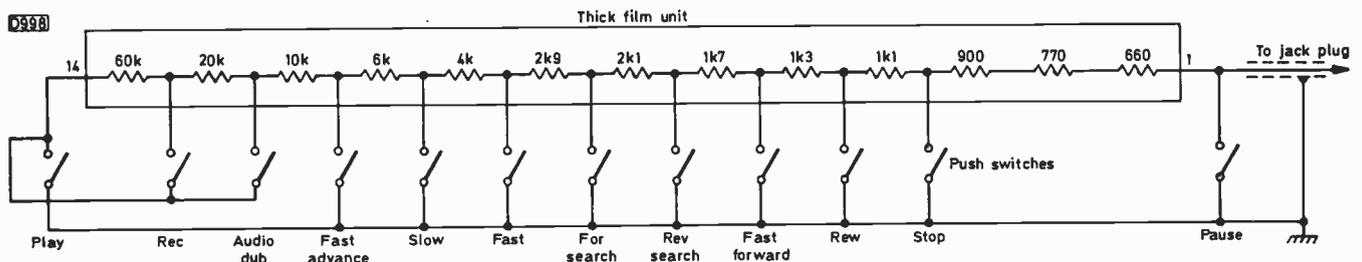


Fig. 1: Circuit of the Hitachi VT8300's remote control handset.

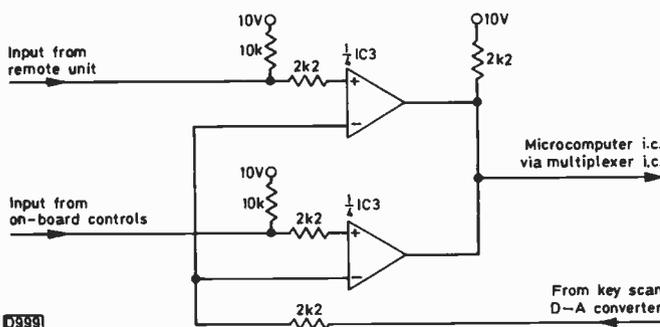


Fig. 2: Arrangement used in the Ferguson 3V29 to combine the remote and on-board control commands.

calls for eight connecting wires – see Fig. 3. The arrangement used with the HS304 is even simpler, containing just six switches and no diodes: it requires five connecting leads – see Fig. 4.

Faults

Faults with wired remote control systems are usually easy to trace. The Ferguson 3V29/3V30 arrangement is particularly unreliable. The plug is prone to disintegrate or, less obviously, to develop a crack around the outer conductor. The wire has a tendency to break or leak between the core and the screen – this latter fault causes

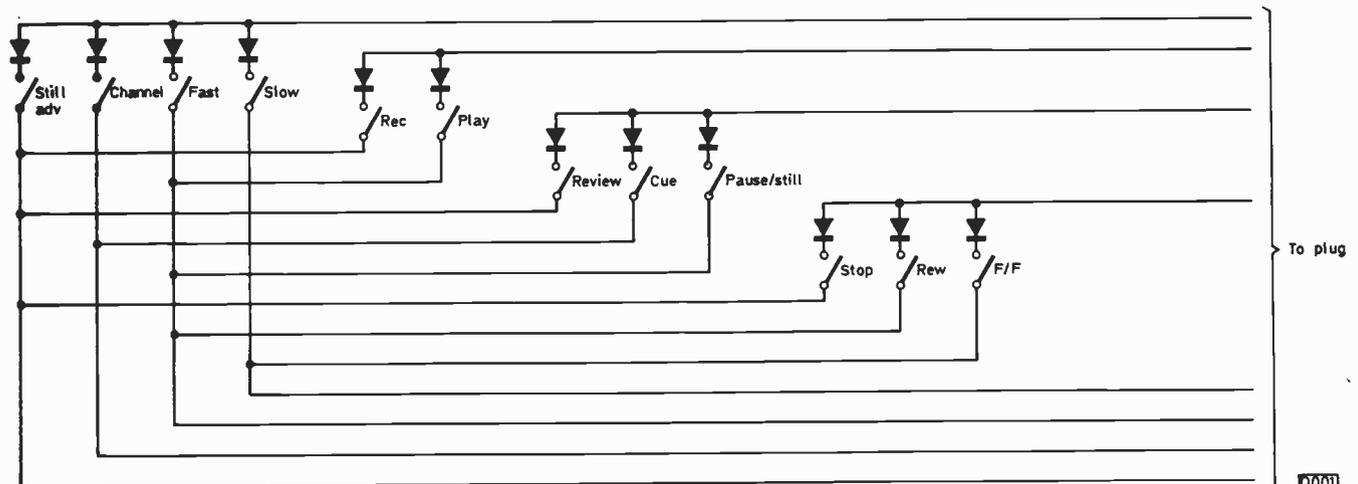


Fig. 3: Multicore cable remote control switch circuit used with the Panasonic NV7000.

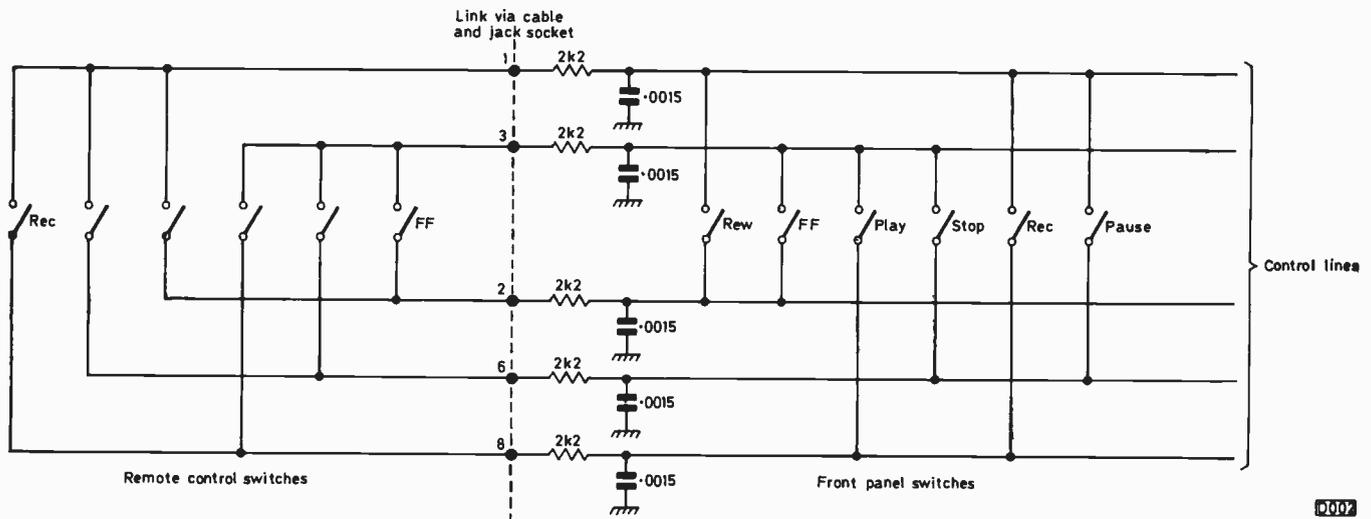


Fig. 4: Remote/on-board switching circuit, Mitsubishi Model HS304.

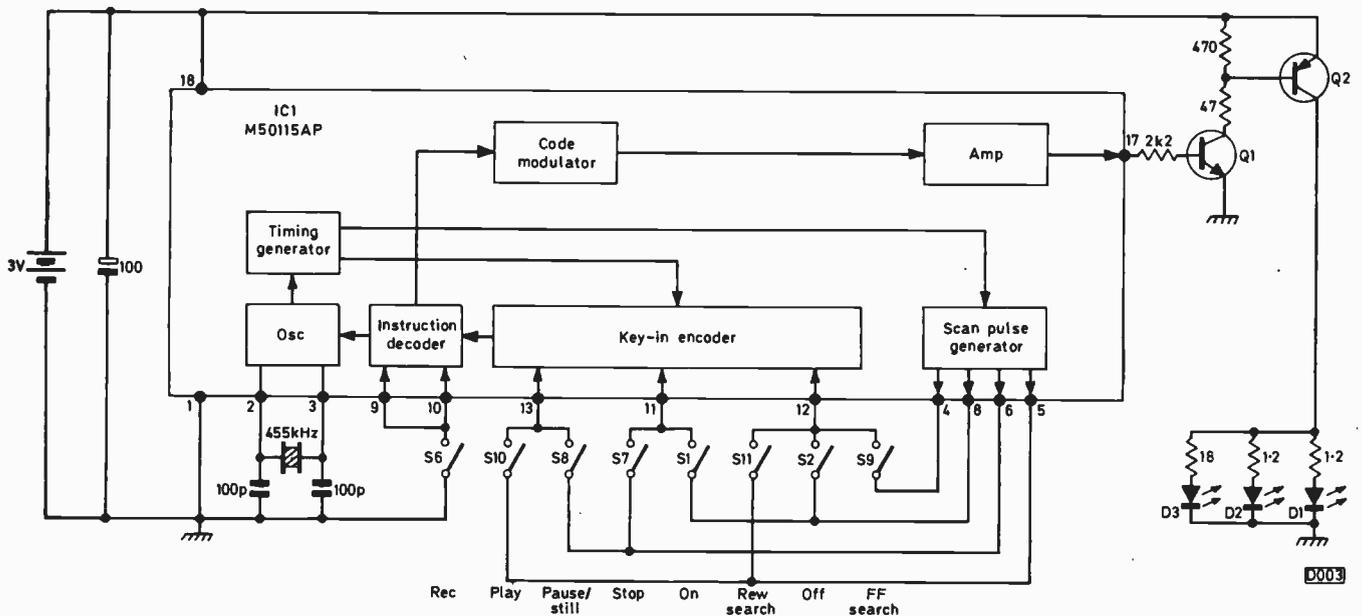


Fig. 5: Infra-red remote control transmitter circuit, Ferguson Models 3V35/3V36.

incorrect functions. Finally the switches themselves can go leaky. I've not as yet had a faulty thick-film resistor network.

I've had a few switch failures with the Hitachi units. Otherwise the system is reliable. With the Panasonic unit I've had a wire come off in the plug (I assume): this however means replacing the lead as the plug is a solid, moulded on block that comes only with a new cable.

It's possible of course that a faulty socket or other part of the machine might be encountered, but I have to report that with wired remote control systems the faults I've come across have all been due to the handset.

Infra-red Remote Control

Most current infra-red remote control handsets use a single encoder/oscillator i.c. and a few external transistors to drive the LEDs. The unit used with the Ferguson 3V35/3V36 VCRs is typical - see Fig. 5. IC1 contains an oscillator and the necessary encoder for the key matrix. The encoded output at pin 17 passes to Q1 and then to Q2 which drives the transmitter LEDs D1/2 and the indicator LED D3. Other infra-red remote control units

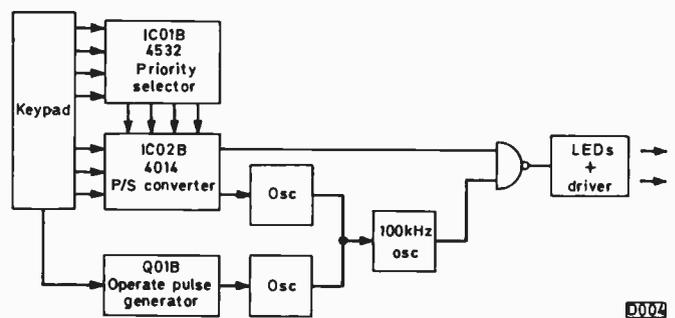


Fig. 6: Block diagram of the infra-red remote control transmitter used with the Hitachi VT8500.

use different i.c.s, and may have a separate transistor to drive the indicator LED, but are generally similar.

The remote control transmitter used with the Hitachi VT8500 is rather different however, using six i.c.s and five transistors (see Fig. 6). When a button is pressed, an input is applied to IC01 or IC02. These i.c.s provide encoding and parallel-to-serial conversion. Button operation also brings into action several multivibrators formed from gates. These provide clock pulses, synchronisation and the

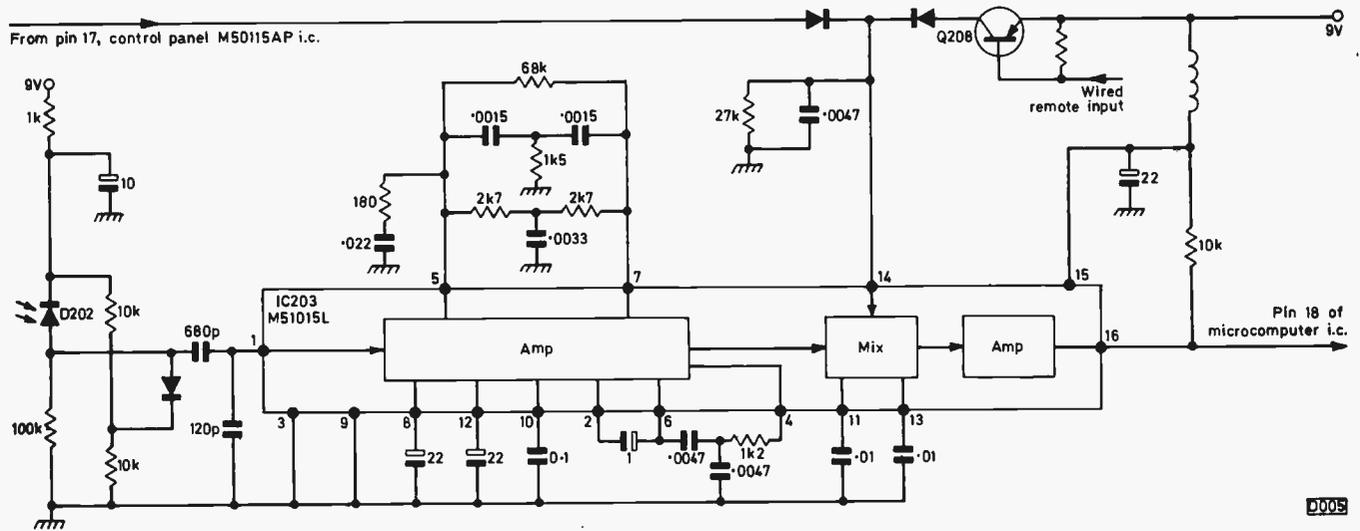


Fig. 7: Infra-red remote control receiver circuit, Ferguson Model 3V35.

carrier. A conventional transistor LED driver circuit is used.

VCRs with infra-red remote control differ rather more at the receiver end. Fig. 7 shows the circuitry used in the Ferguson 3V35/3V36. The remote input is detected by D202 and then passed to IC203 where it's amplified and mixed with the output from the VCR's own keyboard – the two sets of signals are of course the same at this point. The output from IC203 is decoded by the microcomputer i.c. The Panasonic NV7000's optional infra-red remote receiver system uses two i.c.s and a transistor in the detector/amplifier channel, the pulses from this going to another large i.c. and a number of gates which appear to the machine as a key matrix (this optional remote receiver is attached to the side of the machine, being plugged into the wired remote socket, so it's output has to appear like that from a wired unit). The Mitsubishi HS320 has an i.c. preamplifier on a small subpanel, the output from this being fed to a couple of filters and then the command decoder i.c. The decoded outputs pass to the mechanism control i.c.

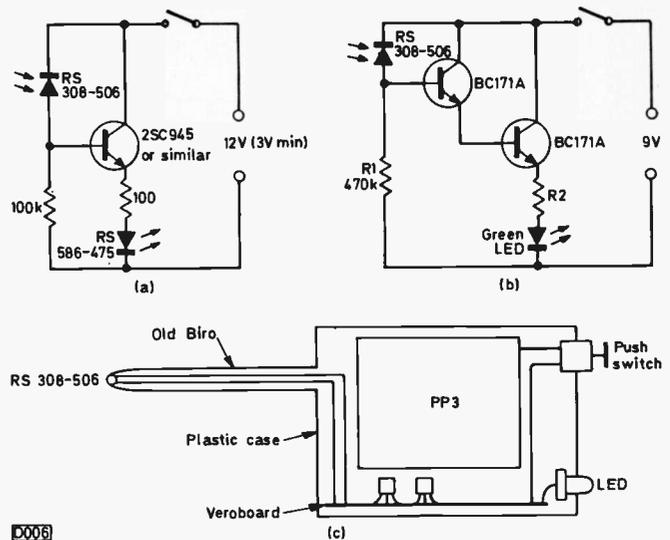


Fig. 8: Infra-red detector arrangements that can be used for test purposes. Adjust the value of R1 in (b) for the sensitivity required; add R2 if necessary to control the brightness and current.

Faults

By far the most common trouble with an infra-red remote control system is simply a flat battery. The Hitachi VT8500 can be particularly heavy on batteries, and a small modification was introduced to reduce consumption – pin 10 of IC01B should be connected to chassis. The only faults I've had have been dry-joints on the output LEDs with the Hitachi VT8500, faulty buttons on a similar unit, and a faulty button on a Mitsubishi HS320 handset (the buttons here take the form of a rubber keypad and the whole thing has to be replaced).

Infra-red Detector

If you want to be able to tell whether an infra-red remote control handset is producing an output the circuits shown in Fig. 8 should be helpful. The LED lights up when an infra-red transmission is detected (note however that this doesn't mean correct information is being transmitted). The two-transistor circuit is much more sensitive but can be affected by sunlight. Check with known good remote transmitter units to get an idea of the detection range to expect and how brightly the LED lights. The circuits are also useful for checking the infra-red LEDs

used instead of cassette lamps in most current VHS machines. I built mine in a plastic box used to supply record player cartridges, with the detector mounted on the end of a Biro. No originality is claimed for these circuits – in fact the single-transistor one has appeared in an Hitachi technical bulletin.

Adding Remote Control

Finally a few words for those whose VCR has no remote control but are perhaps wondering about the possibility of adding this feature. A wired remote system is fairly easy to make: if your machine uses a ladder resistor network, duplicate this and wire the remote output across the existing control network. A matrix type remote control will require multicore cable plus a plug and socket but is otherwise simple. Check whether facilities for remote operation are already fitted, as they are in the Hitachi VT33, Ferguson 3V29 and Panasonic NV333 for example.

Infra-red remote control is rather more tricky. In some machines, such as the Ferguson 3V38, the holes for the infra-red receiver used in more expensive models are

provided on the circuit board. A transmitter unit will have to be bought or built however, so the proposition is not really economic. If your machine doesn't have more upmarket relatives with remote control, then even if you build a transmitter and receiver you've got the problem of matching its output to the machine's control circuitry.

Getting an output that the machine's microcomputer will understand is likely to be very difficult.

For those with mechanical keyboard type machines the only kind of remote operation that's feasible is a pause control by means of a switch wired across the microswitch used for the purpose in the machine.

The US Scene in the Fifties

Chas E. Miller

For this vintage article I'm going to cross the Atlantic to take a look at the US scene in the fifties. After several false starts, due mainly to arguments about standards, regular scheduled TV transmissions started in the USA on July 1st, 1941 – from just two transmitters, both in New York. The start was slow, with only four transmitters in operation by the spring of 1942 and sales of TV sets then standing at around 10,000. It was not long after that World War II halted further expansion. Nevertheless the later start to TV in the USA, compared to the UK, enabled advantage to be taken of a number of technical developments. To start with, 525 lines instead of 405, giving better definition. Then negative-going video modulation, which gave immunity from electrical interference and improved synchronisation – the sync pulses represent 100 per cent modulation and thus peak transmitter power. There was f.m. for the TV sound channel, and the higher field frequency of 60Hz – corresponding to the 60Hz standard for US mains supplies. The basis of US broadcasting, that the listener or viewer should have the right to a wide choice of stations, meant that multichannel tuners were in use long before they were in the UK. In their wake came vision a.g.c. to compensate for different signal strengths, and flywheel sync to stabilise the operation of the line timebase. Even so, when looking at representative US receiver circuits of the fifties one notes a more than passing resemblance to contemporary UK practice, especially of the slightly dotty kind.

Valve as Dropper

An example was the use of a valve as a high-wattage resistor (see *The Case of the Curious Cossor*, February 1984). But at least the Yanks got the valve to do two useful jobs. The sound output pentode was used as a dropper by tapping the h.t. supply for the i.f. stages from its cathode. With an h.t. supply of 240V at the anode of the sound output valve the cathode voltage was typically 135V. A resistive potential divider produced a supply of about 130V to bias the valve's control grid. Since the effective voltage across the valve was only some 100V, it seems odd that a 240V h.t. line was chosen in the first place. Why didn't they settle for about 120V, which would have been easy to obtain from the standard 110/120V mains supplies? A parallel situation was to be seen in contemporary Ultra UK sets which used an elaborate voltage doubler circuit to obtain an h.t. supply of 435V which was promptly dropped back to 260V with the use of resistors!

Focus Arrangements

Another way of getting the sound output valve to do two things was to include it in an electromagnetic focus

circuit. Philips did this over here, by using the focus coil to provide the valve's anode and screen grid voltages. The focus control adjusted the bias applied to the valve. US practice was to connect the coil in series with the cathode of the valve, with a variable wirewound resistor in parallel. This was simpler, but again sharply reduced the effective voltage across the valve. In addition the cathode would be at a fairly high potential, increasing the risk of a heater-cathode short.

Receiver Circuits

Initially, separate sound and vision i.f. channels were used, but it was not long before the intercarrier system became general. This seemed puzzling to UK engineers at the time – we'd not then had any experience of f.m., even for radio. We couldn't figure out why the sound signal was tapped from the anode of the video output valve! Just as odd seemed the use of a triode as a sound i.f. amplifier. Crystals were only just beginning to be used as detectors. Video amplifiers were similar in most respects to those found in UK sets, with slight modifications to extend the frequency response to upwards of 4MHz. The unusual feature in this stage was the use of a variable cathode bias resistor as the contrast control.

Tubes

Both grid and cathode c.r.t. drive were in vogue, and what tubes they could be! The smallest was of 10in. diameter, the largest 30in. Bearing in mind that this was in the days of narrow deflection angles, the overall size of a 30in. tube must have been awesome (the length for round c.r.t.s was usually at least half as much again as the diameter). I saw one of these monsters at an exhibition many years ago: I've never handled one, which I don't regret in the least!

Timebases

E.H.T. supplies had by the fifties developed along the same lines as in the UK, with line flyback e.h.t. the norm. In fact the circuit of a typical US line timebase differed little from a UK one. The main difference was that parallel heater chains survived longer in the US than they did here. This was presumably due to the low mains supply voltages, which made power transformers almost essential to get a reasonable h.t. voltage: if you had a transformer for the h.t. supply, you might as well use it for l.t. supplies as well.

Triode field output valves were often used, with autotransformer coupling to the coils. The anode supply might be taken from the boost rail, which in those days ranged from about 350V to 550V. At around the same

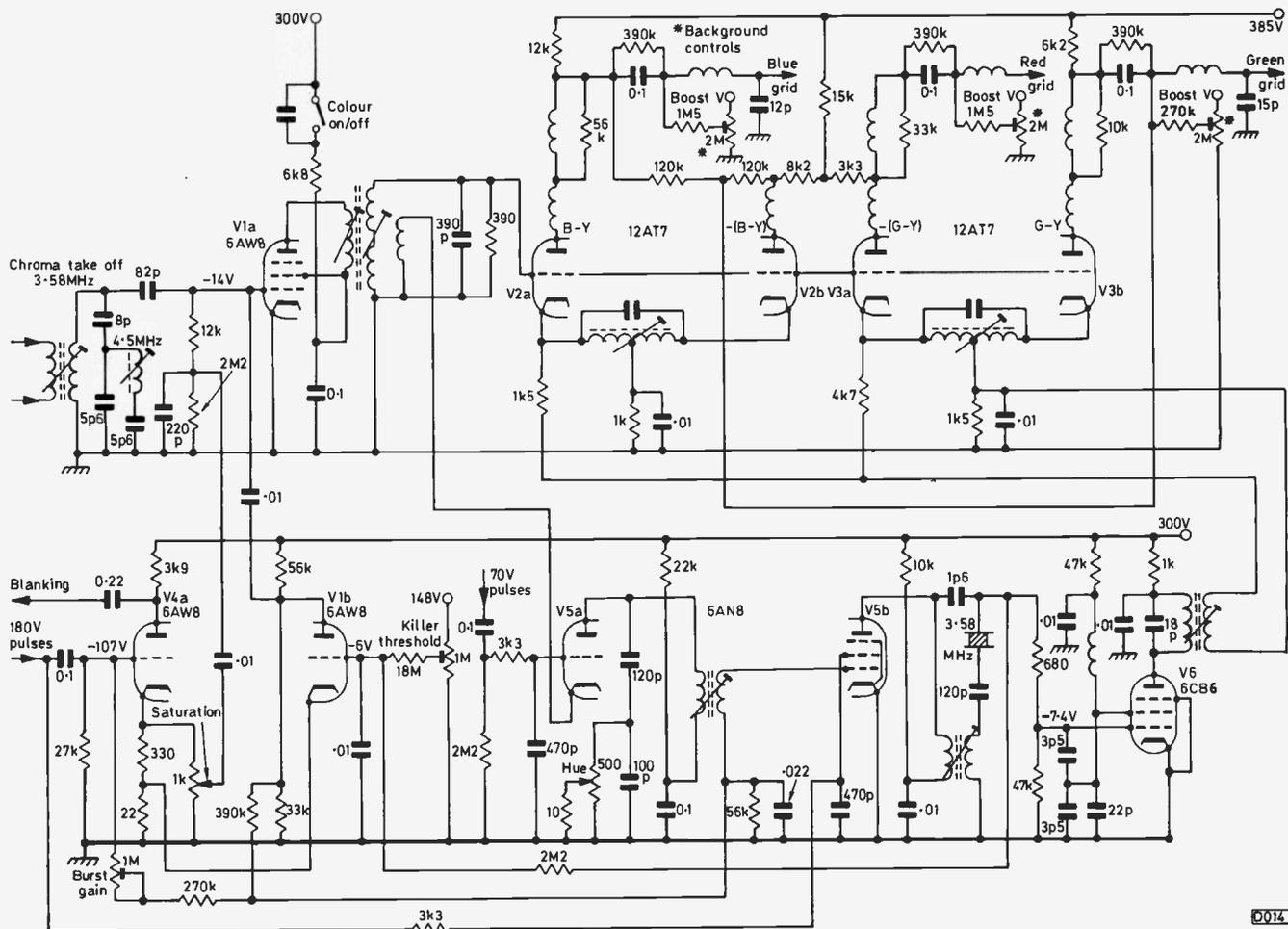


Fig. 1: The colour decoder circuit used in late-production 1957 RCA Super and Special models. The burst/reference signal section was simplified by the use of a passive subcarrier regenerator, hence no need for an a.p.c. loop. Demodulation was carried out on the B - Y and G - Y axes, with matrixing to obtain the R - Y colour-difference signal. Only a single chroma amplifier stage was used.

time the celebrated Plessey 12in. chassis, used in countless badge-engineered models in the UK, also employed a triode (6L18) field output valve: it was operated with an anode voltage of only 230V, as there was no boost line in this chassis.

Tuners

US tuner units initially had to cover only the v.h.f. channels A2-A13, so they were not unlike the turret tuners used in UK receivers in the mid-fifties. The use of u.h.f. came much earlier than in the UK however, though it was not popular to start with. This isn't surprising if the tuner circuit I have to hand is at all typical. It employed a crystal mixer with a simple triode oscillator and no r.f. amplification, so what the gain was like is anyone's guess. In the event, the situation that developed was not unlike that in the UK when BBC-2 first went on air a dozen years later. After an initial boom, viewers decided that the u.h.f. stations didn't offer a sufficiently attractive alternative to the existing v.h.f. services to make it worth their while to install converters and aerials. Only in areas where there were no v.h.f. stations did u.h.f. really take off. By the mid-fifties nearly a hundred u.h.f. stations had closed down, and a much larger number that had been authorised never went on air at all. About a hundred were active, mainly in areas that lacked v.h.f. competition or operated by non-commercial organisations.

The twelve v.h.f. channels could support over 600

separate stations in the USA, but the FCC wanted to allocate even more. The only way to do this was to use u.h.f., which with 70 channels could provide another 1,500 outlets. Thus arose a typical chicken-and-egg situation. Would-be station operators would not use u.h.f. because there were so few receivers capable of u.h.f. reception (an "insignificant proportion of the nation's 56 million sets" according to one report), while the public would not buy u.h.f. sets because there were so few stations for them to tune to. One proposed solution was to reallocate the existing v.h.f. stations so that some of them would have to use u.h.f.: not surprisingly their owners protested vigorously and the idea was shelved. Eventually Congress took a hand, and in mid-1962 President Kennedy signed a bill requiring that henceforth all TV receivers produced must incorporate a u.h.f. tuner.

Colour

The big event in the fifties however was the start of colour TV - regular transmissions, using the NTSC system, commenced in December 1953. The foregoing comments on contemporary US monochrome receivers might suggest that colour sets when they came would be extremely complicated beasts, especially as virtually no semiconductor devices were used. Not a bit of it! My first impression when I looked at the circuit diagram of the RCA Super series was that it had been considerably simplified to clarify the operation. This was not the case

however. Everything was there, and the valves and components really were as sparse as they appeared to be at a first glance. What we'd call the decoder used just ten valve sections and a handful of capacitors, resistors and coils – see Fig. 1. This circuit, dating from 1957, may possibly have looked complex at the time. Today it looks ridiculously unsophisticated. Let's take a closer look.

The chroma take-off transformer, in the anode circuit of a video amplifier at the end of the i.f. strip, was tuned to 3.58MHz. A 4.5MHz sound trap was incorporated at this point. The chroma signal thus developed was applied to the control grid of V1a, a tuned amplifier with a bandwidth of 500kHz. This drove the grids of the four triodes V2/3 used for synchronous demodulation. We'll return to these in a moment.

A coil in V1a's anode tuned circuit fed the cathode of the burst gate/amplifier triode V5a, which was gated on by 70V line-frequency pulses applied to its grid. The burst signal developed in its anode circuit was applied to V5b for further amplification. This pentode was also gated, at its screen grid. A phase shift network in the coupling between these two valves provided hue control, with a range of $\pm 45^\circ$. The subcarrier regenerator was of the passive type, i.e. the output from V5b drove the tuned circuit that included the 3.58MHz crystal. V6 amplified the reference signal and drove the cathodes of the synchronous detector triodes via transformers that provided the required phase conditions.

A rather odd aspect of the circuit was the use of pulses to provide gain control in both the chroma and burst channels and colour killing. 180V line flyback pulses were applied to the grid of V4a, which developed a negative voltage of -107V at this point by grid current action. The negative bias thus produced was applied to the control grid of V5b via the burst gain preset to control the gain of the burst amplifier. The positive-going pulses developed at the cathode of V4a were similarly used for saturation control and colour killing. The 1k Ω colour control fed the pulses to the control grid of the chroma amplifier V1a, developing a bias voltage of -14V at this point. Obviously the greater the amplitude of the pulses the greater the bias voltage developed. A second pulse feed was applied to the cathode of the colour-killer triode V1b. On a monochrome transmission the amplified pulses appearing at its anode produced a sufficiently negative bias at the control grid of V1a to cut it off. The reference oscillator circuit, being of the driven type, was active only when the bursts were present. The negative bias then produced at the control grid of V6 was applied to the grid of V1b, cutting this triode off so that V1a was left under the control of the saturation potentiometer. All rather crude but no doubt effective.

Back to the synchronous detector triodes. These conducted on the negative-going tips of the 3.58MHz waveforms applied to their cathodes, producing the B-Y signal at the anode of V2a, the G-Y signal at the anode of V3b, and the R-Y signal after mixing in the anode circuits of V2b/V3a. The high-level outputs produced by these triode synchronous detectors drove the tube's grids without need for further amplification. Colour-difference drive was used of course, with the luminance signal applied to the tube's cathodes.

So there we have it. Colour as well for only five and a half bottles. NTSC has been referred to as "never twice the same colour", though you have the hue control to get it right. One wonders how things are today in the US: maybe someone over there would care to comment?

next month in

TELEVISION

● SERVICING THE SONY KV1612UB

This interesting 16in. colour portable is fitted with infra-red remote control as standard. In some respects it's rather more anglicized than the Sony sets we've covered before, with i.c.s such as the TBA120U, TBA1440G and μ PC1365C, but other sections are thoroughly Sony. David Botto on the servicing aspects.

● TELETALK ON COLOUR

Malcolm Burrell's commentary concentrates on colour, from the early days when there were excellent bright displays but considerable variation from set to set to today's "rather mediocre" but consistent standard.

● VIDEO SERVICING

This time Mike Phelan takes a look at video cameras and the problems they present to the service engineer. In particular setting up can be a lot more critical than with most consumer electronics equipment.

● TAMING THE SONY KV1810UB

There can be few service engineers who don't greet the request to repair a Sony KV1810UB with some trepidation. The reason for this is the tendency of the expensive gate controlled switch devices used in the chopper and line output circuits to commit hara-kiri. It's possible to modify the set to get rid of these troublesome devices however. Bernard Pruden gives full details of how to change over to the use of transistors.

● THE VIEW MASTER

Vintage TV takes a look at an early kit for the constructor. The View Master appeared on the scene in 1949 as a design sponsored by a number of component manufacturers. It was simple by contemporary standards but capable of excellent results.

PLUS ALL THE REGULAR FEATURES

ORDER YOUR COPY ON THE FORM BELOW:

TO
(Name of Newsagent)

Please reserve/deliver the December issue of TELEVISION (£1), on sale November 21st, and continue every month until further notice.

NAME

ADDRESS

.....

.....

Long-distance Television

Roger Bunney

August was an extremely productive month, with excellent Sporadic E openings during the earlier part and a really dramatic period of tropospheric reception towards the end. Lots of news, so without further ado here's the August UK SpE log:

- 7/8/84 TVE (Spain) chs. E2, 3, 4; RAI (Italy) IA; ORF (Austria) E2a; TSS (USSR) R1; CST (Czechoslovakia) R2.
- 8/8/84 RAI IA; JRT (Yugoslavia) E3, 4; ORF E2a; +PTT (Switzerland) E2; MTV (Hungary) R1; TVP (Poland) R1; TSS R1; TVE E2.
- 9/8/84 TVP R1; CST R2; TSS R1, 2; SR (Sweden) E2; RUV (Iceland) E4; NRK (Norway) E2, 3; TVE E2; RAI IA.
- 10/8/84 TVE E2, 3, 4; JRT E3; RAI IA; DFF (East Germany) E4; TVP R1, 2; TSS R1, 2; CST R2; SR E2.
- 11/8/84 TSS R1, 2; TVP R1, 2; CST R1; SR E2, 3, 4; NRK E2, 3, 4; MTV (Hungary) R1; ORF E2a; +PTT E2; RAI IA; TVE E2, 3, 4; TVE-2 E2; RTP (Portugal) E3; ARD (West Germany) E3.
- 12/8/84 TVE E2, 3; TVE-2 E2; RAI IA, B; DFF E4; SR E2; NRK E2; TSS R1.
- 13/8/84 RAI IA; CST R1; NRK E2.
- 14/8/84 CST R1; DR (Denmark) E3; RAI IA.
- 15/8/84 TVP R1; CST R1; TSS R1; NRK E2.
- 16/8/84 CST R1, 2; TVE E2.
- 17/8/84 TVP R1; TVE E2.
- 18/8/84 TSS R1; CST R1; NRK E2; +PTT E2.
- 19/8/84 RAI IA, B; TVE E2, 3, 4; TVP R1.
- 20/8/84 TVE E2, 3; RAI IA; JRT E3, 4; MTV R1; ARD E2; TSS R1, 2.
- 21/8/84 ORF E2a; TVP R1; TVE E2, 3, 4.
- 22/8/84 TVP R1.
- 23/8/84 CST R1.
- 24/8/84 RAI IA; TVE E2, 3, 4; MTV R1, 2.
- 27/8/84 TVE E2, 3, 4; RAI IA, B.
- 28/8/84 RAI IA.
- 30/8/84 TSS R1, 2.
- 31/8/84 RAI IA; TSS R1.
- 1/9/84 SR E2.

Pressure remained high during most of August, resulting in two periods of good tropospheric conditions. The first was from the 10th to the 17th, when many enthusiasts received Holland, Belgium, Denmark and numerous Norwegian Band III stations almost daily. In the best locations reception at over 500 miles was possible using relatively simple equipment. From the letters I've received it's clear that many relatively new enthusiasts achieved their first "real" tropospheric results. Of particular interest, Cyril Willis (Ely) received system M (525 lines, 60 fields) signals from the AFRTS/AFN base at Shape, Holland, on ch. E34. He found that his valved KB Featherlight receiver locked well without any adjustment. I owned the set myself at one time and remember some years back receiving ch. A2 (system M) signals on many occasions when the conditions in the F2 layer were good.

After a brief lull a further period of enhanced tropospheric activity started on the 20th, with signals from

much of central Europe though with a tendency for reception on a north/south path to predominate. Conditions peaked on the 25th/26th with Band III and the u.h.f. channels literally jammed. Examples of reception on the 25th include Switzerland and the French Canal Plus programme (in colour on ch. F5) in Scotland, plus teletext DX from W. Germany at the same location. Iain Menzies (Aberdeen) comments that ZDF, NDR, WDR, DR, RTB/BRT, NOS and NRK signals filled the band. A bonus was RTL Plus (Luxembourg) on ch. E7. Norwegian Band III signals reached as far as the southern UK while, unusually, NOS/RTB/BRT were well received on ch. E4 over much of the UK as far as the W. Midlands and north Scotland. Unfortunately I missed this opening as I'd just gone on holiday. Typical, but a good time was had by most, with the main W. European Band III and u.h.f. transmitters received with varying degrees of clarity. On the amateur radio front, I gather that the Faroe Islands were received in the UK and the Shetlands in the London area during this opening.

An interesting sea path opened on July 4th when Dave Last (Truro) had two-way contact at both 144 and 435MHz with EA8XS in Las Palmas, Canary Islands. On the following day EA8XS was received in S. Wales!

Dave Shirley (Hastings) reports that there's an Antenne 2 (TDF) programme called "Le Club du Television du Monde" every Thursday night at 2035 French time. It includes programme examples from overseas TV services with station logos, opening/closing routines etc.

My thanks to the following for sending in reports: Cyril Willis (Ely), Dave Shirley (Hastings), Iain Menzies (Aberdeen), Simon Hamer (Powys), Keith Chaplin (Barrow-on-Soar), Paul Barton (Harrogate), Bill Cotterill (Tipton) and Alan Beech (Dollar, Scotland).

For the record, Dave Shirley received RAI-1 ch. IF Udine, N. Italy via tropospheric propagation on May 5th last at 1300 BST, the programme material consisting of a football match and interviews with Roma FC players. G3COJ had two-way contact with W6JKV/OX (Greenland) at 50MHz on June 24th (2308 GMT). On June 30th/July 1st GJ3YHU at St. Lawrence, Jersey, Channel Islands had two-way contact with 46 stations along the US/Canadian eastern seaboard between 2234-0057 GMT, again at 50MHz.

News Items

UK: Racal are applying for planning permission for lattice masts, typically 30m high, throughout the UK to carry PMR and communications aerials for the cellular radio service. The siting seems quite close: in south Hampshire for example a mast two miles north of Southampton has been approved and permission is being sought for another 19 miles away at West Cowes, Isle of Wight. Many of the services will operate in Band III.

The British Amateur Television Club has produced a booklet entitled "Introducing Amateur Television" for all new members. Membership details can be obtained from BATC, Grenehurst, Pinewood Road, High Wycombe, Bucks HP12 4DD - include s.a.e. with enquiries.

France: Canal Plus scrambling will include suppression of the a.m. sound carrier. A decision on DBS standards is being kept open though narrow-band MAC transmissions have been carried within the normal system L bandwidth by the Rennes "Reseau 4" v.h.f. transmitter. Breakfast TV may start this autumn.

Belgium: The French TV5 satellite downlink channel now

has scrambled vision: a 1-2 μ sec delay on a random basis is introduced at the beginning of each line, giving the appearance of several overlapping pictures. A digital signal is incorporated in the field blanking interval to synchronise the descrambler's random generator. Canal Plus has been seen using a similar type of scrambling. The Brussels TV5 output on ch. E56 is unscrambled but cable operators have to do their own unscrambling. A Pay-TV service for French speaking Belgium is being planned by RTBF and the Dupuis publishing company: descramblers would cost 2,500Bf and the programme content would consist mainly of feature films on a rotating schedule.

Luxembourg: The Coronet consortium is to commence its DBS service in the summer of 1986 using a medium power satellite (-50dBW) at 19°W.

Satellites: The common SRG/ORF/ZDF programme via ECS is to start on December 1st, with five and a half hours' programming daily. The Japanese firm Uniden, noted for its CB rigs, has entered the 4GHz satellite field with a complete TVRO package which is marketed under the Unisat label. Prices are expected to drop to the extent that later next year an upmarket TVRO package should cost much the same as a full-feature VCR. Uniden also intends to produce 12GHz equipment. The Electra Company which manufactures Bearcat scanners has also entered the 4GHz TVRO market.

Spain: New EBU listings - TVE-1 Madrid ch. E49, TVE-2 Madrid ch. E55, 117kW e.r.p. horizontal in both cases.

IF Selectivity Unit

The U800 i.f. selectivity module from the Philips G8 chassis has been widely used by DXers to obtain reduced i.f. bandwidth - essential where channels are close (e.g. E2/R1 vision) in order to minimise signal overlap and floating images. The idea is to incorporate the unit between the tuner and the main i.f. strip, with the module modified for narrow/normal operation. Unfortunately the module is no longer available: to overcome this problem Paul Barton has designed an alternative (see Fig. 1).

The coils can be tuned to provide a very narrow i.f. passband of some 1MHz. This will result in degraded picture quality of course, so a compromise is required between quality and minimum adjacent channel interference. The bandwidth can be widened to some 3-4MHz by adding 1.5k Ω damping resistors across L1 and L2. Alignment is relatively easy and is best done on an actual signal. L1 and L2 have a sharp peaking, notch-like effect whereas L3 has a relatively flat response. Tune to a steady fringe

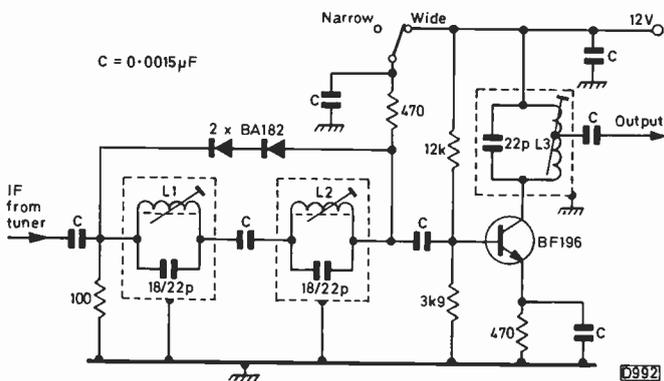


Fig. 1: Circuit of Paul Barton's i.f. selectivity module. L1 and L2 consist of 15 turns, close spaced, of 28 s.w.g. wire on a 3/16in. (4.5mm) former with core. L3 is the same but centre tapped.

SOUTH WEST AERIALS



NEW 1985 CATALOGUE 60p

SOUTH WEST AERIALS proudly announces its NEW 1985 CATALOGUE - fresh from the printers and packed with Aerials, Amplifiers, Components and Hardware, lots more Filters and Multi-Standard TV's. Whilst retaining most of the established and popular lines, we have taken the opportunity to include lots of new exciting items based on the experience of many years successful trading as the Premier Aerial Mail Order Company, and relating to what you the customer is seeking.

We are pleased to announce a replacement to the recently discontinued Export Band 1 & 3 combined Aerials - the new Fernseh-Antenna model DR1712 - available exclusively from us. A new introduction is an attractively priced replacement to the discontinued Hirschmann RO250 Rotator.

We are active TV/FM DXing specialists - your guarantee of honest and knowledgeable advice.

Our New high quality Catalogue (regarded by many as a reference in its own right) is priced only 60p - no enthusiast should be without a copy. Customer Consultancy service available for DXing, difficult, and general reception queries (include SAE please). ACCESS & BARCLAYCARD orders welcome. Delivery 7-10 days.



SOUTH WEST AERIALS (T)

11, Kent Road, Parkstone,
Poole, Dorset, BH12 2EH. Tel: 0202 738232.





signal or a local signal attenuated to give a weak, noisy (but non-fading) signal. Peak L3 first. Though its response is flat, picture improvement should be seen. Note the definition. Peak L1 at the l.f. end (core in) and L2 at the h.f. end (core out). Balance L3 and observe the picture, preferably on a test pattern so that the bandwidth reduction can be assessed. If a smeary picture lacking detail is seen, the bandwidth is likely to have been considerably narrowed. Stagger tuning L1 and L2 will then increase the bandwidth to the extent you consider necessary. Personally I feel that a bandwidth of 2MHz provides a reasonable compromise.


Paul found that the ET021 tuner likes to see a 100 Ω resistor across its output. 3-30pF trimmers could be used in place of the 18/22pF tuning capacitors to give a wider range of alignment where alternative coil formers are used. The unit exceeds the performance of two peaked G8 units in series: it can easily separate ch. R1 vision from a strong local ch. B2 signal. Let us know how you get along with it.

Satellite TV Services

An increasing number of TV programmes are available to the satellite TV enthusiast, particularly in the 12GHz band. There are the well-known three Gorizont channels at 4GHz, and in the not too distant future Arabsat signals will be available with channels in the 2.6 and 4GHz bands. It may be helpful to list present and future channels intended for downlinking to cable operators at 11-12GHz. The London based Sky Channel has been on air since April 1982. It uses Oak/Orion scrambling and is downlinked by transponder six on ECS-1. Other ECS-1

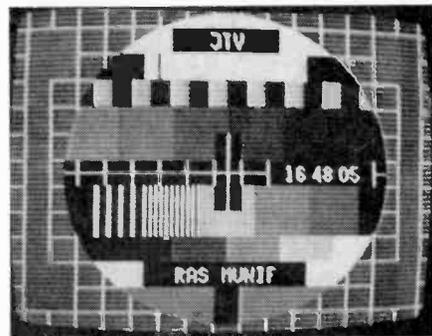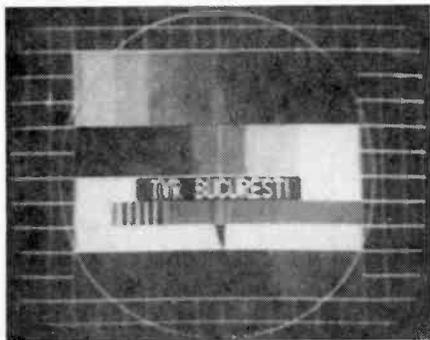

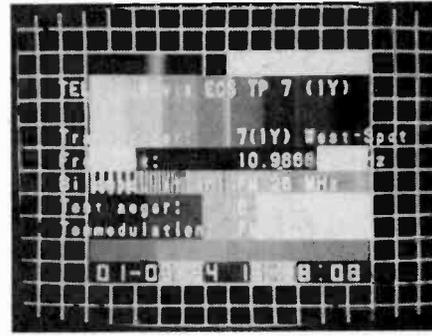Left: TVR (Rumania) FUBK test pattern, Bucharest ch. R2, received by Ryn Muntjewerff in Holland. Centre: Syrian news announcer received by Petri Pöppönen in Finland. Right: Ras Munif-Ajlun, Jordan ch. E9 500kW, received in Cyprus by Marios Colocassides, with Syrian co-channel.



Left: 4GHz (C band) satellite reception by Frank Lumen in Denver, Colorado. Centre: Another example of Frank Lumen's C band reception of signals from Los Angeles. Right: Satellite reception in Europe - ECS-1 transponder 7 downlink signal, Teleclub programme source.

transponders in use are as follows: 12 - Thorn-EMI "Music Box" pop video programme; 4 - French-language TV5; 10 - PKS, a German entertainment programme from Frankfurt; 7 - PaySat, a Swiss feature film channel. The TV5 service is scrambled at times using a system called Discret-1 (see News Items, Belgium). Planned ECS services are: Euro-TV, a Dutch based movie/entertainment channel due to start this autumn; a German-language programme compiled by ZDF from the various German TV networks, using transponder 2 and probably with system SIS/PCM2 scrambling; and Esselte, a Swedish channel expected to be on air early next year, using transponder 9. There's also a vague plan for a European service to be called Eurikon, originating from Hilversum.

Other UK based services in operation are: TEN with nine hours of movies and other entertainment daily from Intelsat 4W; the Premier movie channel from Intelsat 6W; and Screen Sport, six hours daily, from Intelsat 3W.

Planned for next summer are a Childrens channel, a telesoftware channel, and a 24-hour World News Network channel run by Visnews. W.H. Smith plan to start a Games Network with computer games and business data, and Wyvern TV (Swindon) plan to start a channel offering general programmes and documentaries.

From our Correspondents . . .

Frank Lumen of Denver, USA (formerly Glasgow) has been successful with reception from several satellites, using a 1.8m dish and 4GHz (C band) receiver. He reports that the Olympic Games kept the communications craft busy - Frank logged signals going to all parts of the globe, many from Intelsat 4 at 53°W.

Wenlock Burton (Victoria, Australia) comments on the problem of interference produced by computers. Apparently the TRS80 and Apple 2 microcomputers have to be

fitted with an r.f. shield for sale in the USA in order to comply with stiff FCC regulations. The shields are omitted from export versions, apparently due to relaxed or non-existent radiation regulations. The Australian Department of Communications plans to clear TV channels 3, 4, 5 and 5a and establish extra channels between the existing 9, 10 and 12. A stereo TV sound system using a second carrier spaced at 242kHz above the main sound carrier, with 50kHz deviation, has been approved.

Keith Chaplin of Barrow-on-Soar, Leics had considerable success during the recent SpE and tropospheric openings. He's well equipped, with a Vega 402D, a dual-sound/teletext Luxor receiver, wideband aerials for Bands I/III and u.h.f., amplifiers, a rotor and more importantly a clear take-off at 500ft a.s.l. from south to north!

Nick Harrold (Essex) recently visited the Canary Islands to assist with the installation of a large satellite dish for TV reception high up on a mountain. The installation belongs to some exiled Canadians who wanted to watch AFRTS from Intelsat at 1°W. In addition to this it was found that virtually noise-free pictures could be obtained from Satcom 2R at 72°W.

Tropical Aurora

An article on this subject appeared in a N. American radio magazine recently. It seems that in equatorial regions the extreme outer fringe of the ionosphere thickens and is rendered reflective by constant, direct solar bombardment. The phenomenon occurs at ±15° of the Equator and is similar to a polar aurora. Strong v.h.f. signals are reflected, giving incident signals with a characteristic fluttery quality, present at times when F2 layer activity is low. One result is that many Argentinian paging stations operating in the 40MHz spectrum are well received in N. America.

TV Fault Finding

Reports from Peter H. Dolman, T.Eng.,
M.S. Barakat, Jim Rainey, Malcolm Burrell,
Philip Blundell, Eng.Tech. and Mick Dutton

Panasonic TC2203 (U1) and TC2205 (U2)

A common fault with these sets is normal sound, blank screen. There are three likely causes. (1) The 7.5V zener diode D351 which links the emitters of the RGB output transistors to chassis. (2) The 6V zener diodes D818 and D819 (D857/8 is the U2 chassis) which provide the reference voltage in the 12V regulator circuit. What usually happens is that the zener characteristics change, as a result of which the regulator's output rises to 13V or more, producing saturation in the TDA2530 i.c. (IC301). Note that if the regulator's output falls below 10V the result is loss of colour. (3) If R621 (82k Ω) is open-circuit the TDA2530 will receive no clamp pulses at pin 8. The result is blanking (no modulation).

The TDA1104SP field timebase i.c. in the U2 chassis can cause loss of raster – it contains a safety circuit. To check, probe pin 8 with the meter switched to its lowest d.c. range to shunt the safety blanking pulses. You may then find loss of field scan or partial field collapse.

A small picture with a hum bar and sound that varies in sympathy with the contrast and brightness in the U2 chassis means that the 160V line reservoir/smoothing electrolytics C852 (100 μ F, 250V) and C857 (47 μ F, 250V) are defective. I usually replace them with 350V or 400V types.

Sound fading with the U2 chassis can be due to any of the following items on the remote control decoder panel: transistors Q1003/4 (both type BC237B), D1008 (OA91), D1006 (5V zener diode) and R1015 (12k Ω).
M.S.B.

Rank Z718 Chassis

This set suffered from poor EW correction and bent verticals. The width and raster correction controls worked but seemed to adjust rather critically, while the verticals straightened out only at low contrast control settings. The e.h.t. regulation also seemed to be worse than usual, with a fair degree of blooming.

The EW correction circuit is called upon to do quite a lot in this chassis – regulation and breathing compensation as well as raster correction. Checks revealed that the waveforms at the base and collector of 4VT16 were similar instead of being inverted at the collector. So although it was possible to get a poor but tolerable raster shape by adjusting the controls the sense of the width and breathing correction was incorrect. Replacing 4VT16 and setting up the circuit restored normal operation. P.H.D.

Sharp C2092

This set entered the service department suffering from amnesia: its digital tuning system was able to search for and lock to the required channel but the tuning point couldn't be stored – thus all was lost on channel change. A breathtaking 13 i.c.s and 20 transistors are used in the tuning, control and memory circuit, supplied from five l.t. rails... Investigation revealed that the 10V rail was low at around 6.5V, due to lack of drive to Q1019 from I1010 (see Fig. 1). The cause of this was traced to R1072 (33k Ω) being open-circuit – the voltage at pin 2 of the i.c. had

fallen to less than 1V instead of being clamped to 15V by D1017. A 1W type is suggested rather than 0.5W as originally fitted.
P.H.D.

Amstrad 22in. CTV

Poor field lock has been a problem with a few of these sets, but the recommended method of setting up the hold control is not exactly obvious. First set the field hold control RV801 to mid-position, then connect a meter (preferably a digital one) to measure the voltage at the junction of RV805/R816 with respect to chassis. Adjust RV801 for a reading of 15.1V. This cures the fault. J.R.

Finlux 9510

A new set came into the workshop to have a teletext decoder fitted. When it was tested however it wouldn't work correctly in the mix mode – instead of the picture appearing behind the text there was a grey background. Substitution proved that the decoder was at fault, so scope comparisons were made between the two boards. The only signal that differed on the faulty board was the blue drive signal to the TV set. This was 1V too large and didn't respond to adjustment of the blue text amplitude control Pt4 which turned out to be open-circuit. The TDA3560 colour decoder i.c. in the set must have been objecting to the excessive signal input.
P.B.

ITT80 – 90° Chassis

The problem with this set (Model CC1814) was intermittent colour on channel 8 only. This would normally be due to a faulty 1N4148 diode in the tuning potentiometer circuit, but in this case the picture was hooking at the top as well. The cause was C721 (100 μ F) being low in value – this electrolytic decouples the supply to the TDA9503 line generator i.c.
P.B.

ITT CVC1204 Chassis (CVC1200 Series)

The latest ITT service bulletin has a fault-finding procedure for these sets, so when one came in I pounced on it, thinking that the repair would be easy. It wasn't. The set was dead, so I removed the scan coil plug and loaded the h.t. reservoir capacitor C733 with a 60W bulb. The h.t. read 20V then, after a couple of seconds, the switch-mode power supply shut down with a cheep. This proved that the power supply was at fault, and as the guide suggested I

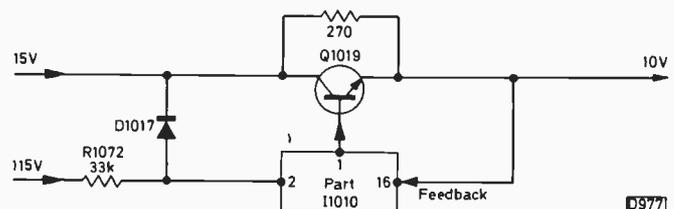


Fig. 1: 10V regulator used in the Sharp Model C2092's digital tuning system.

went on to replace the various diodes and transistors, getting nowhere in the process. In desperation I resorted to plan A and got the scope out. This showed that the supply was oscillating faster and faster until it gave a cheep and shut down. All likely looking capacitors were changed to no avail so I rang Mr. ITT. He said that the switch-mode power supply transformer itself set the frequency of oscillation, though he didn't sound too sure about what was wrong. Anyway a new transformer restored normal operation – three cheers for Mr. ITT! **P.B.**

Philips 1250

This set is fitted with the K30 chassis and has teletext and full remote control. The customer's complaint was no picture except via their VCR. On investigation we found that there was no tuning on channels 1-4 though the VCR worked correctly via channel 12. We were able to tune in TV stations on the other channel positions so the problem was to do with the first four positions. The fact that the correct LED display was being shown suggested that the key pad, encoder and TMS1000 microcomputer i.c. were working correctly and providing the appropriate digitally coded outputs for the tuning drawer. This incorporates three decoder i.c.s, one for every four channels. The problem was due to the failure of the SN29770BN responsible for selecting channels 1-4. **M.D.**

Grundig CUC40 Chassis

Field collapse was the problem here. We soon found this one. D2758 (SKE2F1/01) on the deflection subpanel was open-circuit, leaving the output section of the TDA2655B field timebase chip with no power supply. **M.D.**

ITT CVC1200 Chassis

We've had several of these sets in the workshop recently. On the whole they seem to be reliable. Two have had faulty BU208D line output transistors and several have had tuner/i.f. module faults such as tuning drift and snowy pictures. The TDA3561 decoder i.c. occasionally gives lack of one colour, usually intermittently. On remote-control sets the push-button mains switch is soldered to the printed panel and we've had one burn up caused by a bad joint, just like earlier ITT sets.

One colour weak with flyback lines in this colour has been caused by the BF393 transistor in the relevant output stage going short-circuit. When this happens the collector resistor usually burns up.

One fault that lead us a merry dance was due to transformer Tr712 which couples the drive to the switch-mode power supply board. It went open-circuit intermittently, the result being a small raster with the h.t. supply falling from 117V to about 80V. The fault would come and go when the chassis was flexed.

One new set was found to have a cracked tube. This produced a pretty display of fireworks but also did quite a lot of damage. The tuner/i.f. module wouldn't tune in, two of the video output stages had blown up, there was no colour due to the failure of the TDA3561, and there was only a blank raster in the picture mode with the teletext display normal. After a lot of searching we found that R503 (39k Ω) in the beam limiter circuit was open-circuit. Replacing this didn't provide a cure but when the associated decoupling capacitor C503 (0.056 μ F) was bridged a

normal picture returned. When C503 was removed it was found to have no inside – and there was a burn mark on the board where it had been.

A common fault is a blank raster due to no h.t. supply to the RGB output stages. This is caused by rectifier diode D505 (BA159) going short-circuit as a result of which the 1.5 Ω surge limiting safety resistor R514 goes open-circuit. **M.D.**

Grundig 5010 Series

I've never been very fond of these sets, though I'm now beginning to get to grips with them. One we had would work for half an hour and then go dead, leaving channel selector number 4 illuminated. After some time the set would start working again and automatically switch to the channel 1 position. A search for dry-joints didn't reveal anything so some voltage checks were made. This led us to the transistors in the 15V regulator circuit (Tr635/6). Changing them cured the problem.

Another of these sets would occasionally blow its cutout. The usual checks for dry-joints around the commutating transformer etc. didn't help. Eventually with the chassis hinged down I noticed an arc in the area of one of the thyristor holder fixing screws. One of the ceramic capacitors was earthed to this and cleaning its tag and tightening the screw solved the problem. **M.B.**

GEC 1402

These GEC 14in. portables are fitted with the ITT CVC801 chassis. One came in recently with no sound when switched on: after a couple of minutes there was distorted sound. The TDA1035T sound channel i.c. is in the r.f./i.f. module. On taking this to pieces and checking around in the sound section I found that C228 (100 μ F) was leaky.

The problem with another of these sets was intermittent low-frequency whistle from the line timebase area. Careful probing led us to the linearity coil L505, but soaking in resin and repositioning it failed to cure the fault. It took only half an hour to remove, unwind, then rewind the coil. This produced a complete cure. **M.B.**

Thorn 1696 Chassis

The complaint was that the field scan became cramped, mainly at the top, when the set had warmed up. Well, there's not a lot in the circuit! Replacing the TDA1044 field timebase chip made no difference; the resistors were all within tolerance; and none of the capacitors gave any indication of being leaky. There was a production modification to cure cramping – R67 was changed from 33k Ω to 27k Ω . So I checked this and found that it was 27k Ω . Perhaps if I changed it back? This did the trick! There was still some slight non-linearity at the bottom of the picture so I changed R65 (15k Ω) and obtained much better results – perhaps this was a tolerance problem (the set was almost new). **M.B.**

Philips KT3 Chassis

I've had a number of interesting faults with these sets recently. In one case (Phase II version) there was no green and a scope check showed that the TDA3560 decoder i.c. wasn't producing a green output signal. The green clamp

reservoir capacitor C45 (0.022 μ F) was leaky.

Another problem was tripping when first switched on. I eventually removed the field scan coil plug and the tripping stopped. Changing the yoke cured the problem though resistance measurements failed to reveal the cause of the trouble.

I always hate remote control faults! The set concerned was fitted with the Telco remote control decoder panel and the fault was no remote or front panel control. I

grabbed the only chip available and plugged it in – the SAF1032P. Fortunately this restored everything to normal.

As most of you in the field will know, a dead KT3 usually means that the 4.7 Ω surge limiter resistor R291 is open-circuit. Before leaving the rectifier panel and starting on the switch-mode department a quick check on the 12V zener diode D300 could save you time. In a recent dead set case I found that it was short-circuit. **M.B.**

Pye/Philips Remotes

Harold Peters

I simply couldn't believe it. Knowing the Pye G11 like the back of my hand I dived into a Philips G11 offering the same facilities and found myself in a strange new world. The front end was totally different. This led me to check up on what goes with each set, and I was dismayed to find eighteen different, incompatible combinations in use with the G11 chassis alone. Philips have used about a dozen basic systems with forty incompatible subdivisions. Let's start at the beginning.

Dynatrons

The earliest remote control systems you're likely to encounter are the wired ones used in certain Dynatron models. A screened, multicore cable links the hand unit to the set: if it should pass close to high electric fields or an unbalanced mains supply hum will be induced on the varicap tuning line. There are two versions, the later one with a mains standby switch, and they don't interchange. A loose shorting plug hangs inside the set, permitting the assembly to be removed for service without leaving the set inoperative (second version only).

Some hybrid Dynatron models were fitted with an ultrasonic (US from now on) full remote system, and again there were two versions. The earlier had buff handsets, a totally screened receiver unit and analogue controls with only eight abrupt steps. The later version had black handsets, an open receiver board and twenty-step analogue controls. Pressing a button sent out one US tone for a certain time, after which it changed to a second frequency. Cats and dogs usually left the room.

Philips G8 and G9 Chassis

A simple "pinger" unit was employed with the G8 and G9 chassis. The handset has a mechanical tuning fork which is plucked each time the button is pressed. Gives sequential channel changing via an i.c. inside the touchbutton panel on the set. Effective, but so is a bunch of keys.

There was a restricted issue of G9 sets with teletext, using the Tifax module. The handset did teletext only, with no analogue controls or channel change. Tifax modules can be identified by having to press a page button before the page number.

The G11

A most bewildering series of remote control arrangements was used with the G11 chassis: simple remote, full

remote, three phases of teletext and a viewdata version all in US form, then full remote, teletext and viewdata in infra-red form (IR from now on). Pye and Philips sets have different front ends, resulting in eighteen incompatible combinations. We'll look at the US range first, ignoring the few viewdata sets that had a modem beneath in the legstand plinth. US systems can select six channels, IR eight.

Philips sets with US remote control have a common tuner drawer for the simple remote, full remote and teletext versions. Pye sets have a common front control panel for simple and full remote, and the same board for teletext but with differences in the volume control: a separate PCB contains the touch-tune i.c. (it's in the tuner drawer in Philips models). Simple remotes use a two-tone system – 39kHz mutes the sound, 37kHz changes channel. Handsets mostly need tuning up and the touch-button i.c.s can stick on one channel. Full remotes use fifteen precise frequencies from 33kHz to 44kHz, divided down from a 4.43MHz crystal. Most of these tones produce an audible note when a working handset is held close to the ear.

Handset faults are common and expensive to cure. A coarse, audible tone suggests a faulty transducer. Any fluid will kill off the keypads immediately. Totally dead handsets could have a loose i.c. For poor range, try the transducer, the position of the receiving transducer in its tube, and C9 (4.4 μ F) and C13 (22 μ F) in the receiver i.c. can.

Teletext systems with US remote control came in three phases. Phase 1 (white label) has development type i.c.s (numbers begin M...), no double-height facility and three buttons are missing from the handset. Incompatible with later types. Phase 1½ (yellow label) has SAA type i.c.s, double-height facility and a small regulator board that plugs into the side of the decoder panel. Compatible with phase 1½ (green label) after removing the regulator board.

There were full remote and teletext versions of the G11 IR system, with common front ends though different for Philips and Pye. Hence four combinations. The teletext system is phase 2 (blue label). This is as phase 1½ but with an SAA5040A i.c. in place of the SAA5040 for eight channels. There were Pye and Philips viewdata versions with a three-tier modem inside the set and an extra button on the handset. For the workshop a teletext handset can be converted for viewdata use by making a small hole in the keypad where the extra button comes and pressing the bubble beneath with a ball pen.

Note that with phase 1, 1½ and 1½ teletext decoders the power supply comes from a large chopper board on the floor of the cabinet. Power for the phase 2 decoder comes from the line output transformer which has extra windings

– the line scan panel is distinguished by the blue fibreglass board with two extra pins coded blue and yellow.

K Series Chassis

The G11 was the last Croydon design. The subsequent K (Kleuren) chassis are of European design adapted to standard I (with suffix /05 or /15 after the model number). There are several remote control systems, all IR, including Long, Telco, VST and TRDIV.

Long comes in two versions. The 868 used with the projection set and video centre selects 29 channels, with coloured horizontal bars superimposed across the picture to assist the tuning. The F8 is at present confined to Model 3761.

Telco (KT3, K30 and K12 chassis) is a twelve-channel system using the same RC4 command codes as Long 868. The other facilities are standby mute, three analogue controls and a granny button. Identified by absence of knobs (all pushbutton) and coming out of mute when channels are changed.

The handsets for these systems have an aversion to fluids. Failure of the SAF1032 i.c. on the Telco decoder panel is not uncommon.

RC5 Handset Code

VST, TRDIV, a system we'll call RC5 Teletext and some simple remote systems use a handset code called RC5 – the handset numbers all start RC5. In a showroom, any RC5 handset will affect all RC5 sets, but not necessarily in the same way!

The Mullard teletext decoder boards respond to handset codes such as those generated by the G11 and Thorn chassis. RC5 was primarily developed for Continentals who like to have forty channels at their fingertips. For use with Mullard teletext boards an interpreter is required to translate RC5 into English. This takes the form of a TMS1000 microcomputer i.c. on a panel between the controls and the teletext decoder. The TMS1000s come in two mask versions which are incompatible. Philips Service issue only mask MP0096, with fitting instructions for earlier boards. So on KT3/K30 sets the signal from the handset goes from the eyeball IR receiver to the control panel then to the encoder/CCAM (computer-controlled analogue memory) panel (hinged on the control panel back on the KT3), next to the TMS1000 board and finally to the teletext decoder.

VST and TRDIV

Up-market models apart, VST is the current system for all remotes and teletext models. The MSM5840H chip on the VST board does the combined work of the control, the encoder/CCAM and the TMS1000 boards on RC5 KT3s. Tuning is by a yellow band that moves across the screen from ch. 21 (left) to ch. 68 (right) and stops at all stations. When you get to one you want it can be stored in any of twenty programme cells. Granny setting of the analogue controls is done in the same way. The VCR cell is 0: the a.f.c. doesn't like double-sideband signals much and may shoot past the VCR or computer signal (if this happens, go round again and slow the action down with the fine tuner +/- buttons just before the VCR etc. signal arrives). Memory is retained by a nicad battery on the board. Remember this when servicing – the memory is still going when you have the board in your hand. There's a

systematic fault-finding procedure that can be followed after grounding pin 16 of the microcomputer i.c. VST boards in the CTX, K35 and KT4 chassis don't interchange.

TRDIV is the up-market version of VST, with many extra code possibilities that come in handy with stereo models and the set that has a built-in teletext printer. It's distinguished from the VST systems by the ability to select channels by number, to store them in fifty different cells, and the absence of an on-screen tuning bar. Some models have "Supertext" which is the ability to store teletext page numbers in cells – this doesn't improve the access time (only a bank of RAMs on the teletext panel would make that possible). The microcomputer i.c. doesn't have the same service mode facility as with VST, but under certain fault conditions shows error indications on the 99-digit display in "calculator overload" fashion.

Simple IR Remotes

Simple IR remotes offer channel selection by stepping up/down, volume control and standby. KT3s use a TMS1000 board and Telco handset codes. CTX sets use a similar circuit with RC5 codes. Monochrome TX sets use much the same arrangement as in the CTX chassis. Incidentally the CTX/S has a large ELC2003 tuner and is produced in Singapore. The CTX/E has a small U411 tuner and is produced in Europe. There are many electrical differences between the two versions.

Simple US Remote

Finally a simple US remote control system was used with two TX 12in. portables, giving channel change and standby only. The action is very slow and the electronics consist of discrete components on a subpanel.

List of Models

Table 1 lists the various remote-controlled models and the systems used.

Testing Handsets

When it comes to testing handsets in the workshop, the usual trouble is to find a set with which to check them. Apart from the early Dynatrons and simple remotes, which call for a frequency counter, most types can be dealt with using very simple test gear.

For US handsets, use a good transducer connected to a scope's Y amplifier (set to near maximum gain) to receive the signals. The scope's screen will tell you all about the handset's performance, range and, roughly, its operating frequency. A typical US display consists of bursts of about 10mV peak-to-peak amplitude.

To test IR handsets use the same set-up but with an eyeball type IR receiver (eyeball plus IR preamplifier) – the best one to use is from the eight-way G11 remotes or teletext units. Connect the preamplifier's output pin to the scope's Y input, set at about 2V/div. Power for the receiver can be from a 9V handset battery (it takes only 5mA). Pulse trains of about 5-7V amplitude should be seen with a working handset. The eyeball receiver mentioned above, using discrete components, will test any IR system. Other receivers with decoder chips work well only with their own system.

A small meter unit reading 10V or 30mA interposed between the battery and the handset under test gives a

Service Bureau

Requests for advice in dealing with servicing problems must be accompanied by a £1.00 postal order (made out to IPC Magazines Ltd.), the query coupon from page 49 and a stamped addressed envelope. We can deal with only one query at a time. We regret that we cannot supply service sheets nor answer queries over the telephone.

ITT CVC9 CHASSIS

We've had the same problem with several of these sets – poor convergence of blue verticals and, more important, a bowing of the red and green horizontal lines, particularly on the right of the screen about a third of the way down. Most of the relevant components on the convergence panel have been checked but they all seem to be within tolerance.

Sometimes the blue verticals on one side of the screen fall on the "wrong" side of the yellow crosshatch so that no blue width adjustment will get it right. The trick is to rotate the radial convergence yoke to equalize the error, then readjust the blue lateral dynamic convergence. For the red/green bowing effect D58z and D59z are worth checking, but the problem is probably due to tolerances in the scan yoke/tube combination. Try to distribute the error along the line, even off-setting the static convergence a tiny bit if necessary.

PANASONIC U1 CHASSIS

This set (Model TC2203) was completely dead. Checks in the power supply revealed that D809 and D818 were short-circuit, so these components were replaced and the set powered via a variac. We find that the h.t. voltage reaches the correct figure of 160V with a mains input of only 120V.

D812 should first be replaced as it could have been damaged when D809 went short-circuit. Then check the h.t. preset R810 which could be at fault. The range of the regulator in this chassis is very good however, and you may well find that with the h.t. set at 160V it will remain constant with a mains input right up to 240V. If the h.t. rises above 170V as the input is increased, check the error amplifier transistor Q803 and the chopper transistor Q801 which could be leaky or short-circuit.

ITT CVC20

The tripler was sparking to chassis and the power supply then tripped. A new tripler was fitted but all we have is a weak, colourless picture with the brightness control turned up. The contrast control has no effect at all.

The sparking tripler will have damaged components in the beam limiter circuit. Replace D3 and C7 and if necessary check the transistors T1 and T2.

RANK T20 CHASSIS

The fault on this set is intermittent though it's now present most of the time. The picture disappears, leaving just snow or maybe a faint, snowy picture, as though there's a severe loss of gain. The aerial and tuner connections seem to be o.k., and I've tried feeding the signal to the collectors

of the transistors in the tuner. I've also tried new i.f. transistors. Heat and cold don't affect the fault and no amount of tapping will cure it.

Arm yourself with a 10k Ω potentiometer and a 6V or 9V battery so that you can apply a variable bias to the tuner's a.g.c. input. Adjust for maximum gain, probably around 2-3V. If a noise-free picture can be maintained with the a.g.c. thus overridden, suspect the TCA270Q vision demodulator/a.g.c./a.f.c. chip. If the snow persists, change the tuner.

PHILIPS N1700

The problem is intermittent field jitter. Constant adjustment of the tracking control minimises the problem.

This symptom is usually due to a fall-off in the video f.m. envelope at the beginning of the head scans, so that the field sync pulses are noisy or partially obliterated. It may be that head cleaning and careful adjustment of the head entry guide will clear the fault. If not it's likely that the heads are worn, with the result that there's insufficient tape penetration at the extremes of the head wrap.

ITT CVC32 CHASSIS

There's a wasp-waisted picture, also a white band across the top of the screen. The field hold and height controls had to be set to maximum but a new BU208 put that right by bringing the voltages up.

The wasp-waisted effect is almost certainly due to failure of the 320V supply reservoir capacitor C35 (220 μ F). More remote possibilities are C37 (10 μ F) and the 12V zener diode D801 – these components stabilize the 12V supply to the switch-mode power supply control i.c.

SIEMENS FC211/SHARP VC9700

With this combination I get picture pulling on prerecorded tapes – some tapes won't play at all. Any ideas for modifications in the TV set's line sync circuit?

Our experience has been that these Siemens sets are not very happy with VCR operation. The line timebase is unusual in employing a BR101 SCS as the oscillator. You could try reducing the values of the capacitors in the flywheel sync filter circuit. The ones to go for are C2 and C27, both 4.7 μ F – try 2.2 μ F or 1 μ F. C9 could also be reduced from 0.01 μ F to say 0.0047 μ F.

SHARP C2072

There's occasional colour dropout on change of station or scene. Changing channels four or five times restores the colour. The set's tuning has been checked and doesn't seem to play a part in the fault condition.

Earth TP803 when the fault is present. If this results in horizontal bands of colour it may well be that the reference oscillator has drifted, in which case adjustment of R811 (preferably by the method given in the manual) may be all that's required. If the result is no colour, check Q801 and Q802 (both 2SA495) before suspecting the decoder chip I801 (RH-1X0063CE).

FERGUSON 3V00

There's a distinct left-right movement of the picture on playback, with smearing of the reds to the left of the image. At worst the picture is unwatchable.

The usual causes of this fault are wear of the pinch roller or incorrect back tension adjustment. Remove the pinch roller, taking great care not to apply any downward pressure on the screw, and check against a straight edge.

Any wear will be shown by light passing between the two. Adjustment of the back tension can be done only with the correct jigs. Less likely causes of the trouble are either motor defective or a tape path fault causing the lower edge of the tape to ripple as it passes the control head.

TEST CASE

263

Each month we provide an interesting case of television servicing to exercise your ingenuity. These are not trick questions but are based on actual practical faults.

Mrs. Waghorn rents a little Japanese colour set from us and has done so for many years. Like most of its ilk, it has given very little trouble. Until a week ago that is. "It keeps going into lines dear - I haven't seen the nine o'clock news for days. Come and have a look at it." So off we went.

It's a Panasonic TC481GR - M6A chassis, similar to the TC333G - and in our experience is a very well behaved model. It was behaving the day we called. Good line lock, clear pictures - another intermittent fault! We wondered about Dave, six doors along. He's got a CB rig, and if the rig itself is legal the aerial it's hooked to certainly isn't. The BBC themselves would have been proud of Dave's transmitting aerial. We got him to fire up his rig, and with his "1-4 for a copy . . . 1-4 for a copy" ringing in our ears we went hotfoot back to the Waghorn residence. The TV was quite unaffected. We set up the line hold and away we went.

The inevitable phone call came next morning. It was arranged that the set would be left running and that we would call later in the day. That afternoon we finally saw the effect - complete loss of line hold, and the best the line hold control R511 could do was to straighten the picture momentarily before it took off again, with a wild squealing from the line output section. We loaded up the set and bore it back to the peace and privacy of the workshop.

The line oscillator and flywheel sync circuits are quite conventional, consisting of a transistor sinewave oscillator stage and a double-diode discriminator circuit, with the usual filtering etc. We decided that the germanium discriminator diodes D501/2 were the most likely culprits, so in went a matched pair of OA91s. Four hours later we found that the picture was jittering sideways with a "false line lock" effect. Strangely, cooling the oscillator section had no effect on the fault. While it was present we took the opportunity to monitor the line sync pulses, which were correct, and the flyback sample pulses, which were of correct amplitude but out of lock as the timebase had once more become totally unhinged. The line hold control's track was checked and found to work smoothly, and a physical assault on the line oscillator coil T501 with the

handle of a screwdriver had no effect. Finally the picture came back into lock and stayed there.

Next came the weary business of substitution and soak tests. The oscillator circuit tuning and coupling capacitors C510 and C509 were exonerated in this way, as were most of the components in the flywheel sync discriminator and filter circuits, including the reservoir capacitor C506 and the anti-hunt capacitor C507. Supply filter capacitor C508 was also proved innocent by substitution.

By way of experiment we connected a low-impedance voltage source to the oscillator in place of the error output voltage from the sync circuit. While sync was of course lost, the line frequency remained reasonably constant. Armed with this useful clue we finally struck gold and cured the problem once and for all. It's only fair to add that in most sets using circuitry of this type the fault couldn't arise. What was the cause of the trouble? You'll know next month - if you don't suss it out meanwhile.

ANSWER TO TEST CASE 262 - page 679 last month -

We were in the conversion business last month, with a W. German Sharp VCR of the VC3300 variety. You'll perhaps recall that our enterprising lads had converted its intercarrier sound strip to 6MHz by changing the filter and retuning, and had changed the relevant traps in the video circuits.

Traps in fact were the key to the remaining problem! The vision i.f. strip includes a series of filters and traps for tuning and rejection. In common with most current i.f. designs, bandpass shaping is carried out by a SAW filter - its designation is SF1501. By leaving the original SAW filter in circuit, the adjacent sound and vision filtering and the co-sound notch were all at the wrong frequencies. While this had little effect in the "quiet" area of the local workshop, it was otherwise in some of the districts in which the machine had been used - hence the patterning and buzzing effects.

A complete cure was achieved by replacing the SAW filter with one of the type used in UK machines. This had to be done at no charge of course, which removed the profit from the job. The old bits are being held on to in case the owner ever decides to return to W. Germany with the machine - any ideas as to how to retune the modulator sound to 5.5MHz spot on?

QUERY COUPON

**Available until 21st November 1984.
One coupon, plus a £1.00 (inc. VAT)
postal order, must accompany EACH
PROBLEM sent in accordance with the
notice printed on page 48.**

TELEVISION NOVEMBER 1984

Published on approximately the 22nd of each month by IPC Magazines Limited, King's Reach Tower, Stamford Street, London SE1 9LS. Filmsetting by Trutape Setting Systems, 220-228 Northdown Road, Margate, Kent. Printed in England by The Riverside Press Ltd., Thanet Way, Whitstable, Kent. Distributed by IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. Sole Agents for Australia and New Zealand - Gordon & Gotch (A/sia) Ltd.; South Africa - Central News Agency Ltd. Subscriptions: Inland £11, overseas (surface mail) £12 per annum, payable to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex RH16 3DH. "Television" is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to otherwise exchange fluctuations and VAT, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever. ISSN 0032-647X.

CAPACITORS 91 5 x .0047/1500 AB23 Chassis 1.50 92 10 x Z20MFD 16V Elect 0.50 93 10 x .047MFD 400V Mul Pol 0.50 94 5 x 4.7/100V C514 T3500 1.25 95 5 x .47/1000 Dublier 3.00 97 10 x 0.1/2000V W/E 2.00 98 5 x 1/250 Supp ITT etc. 1.50	68 Grundig 3010/15003.00 69 Thorn 3500 7.50 70 Thorn 8500 5.40 71 Philips G8 6.30 72 Pye 731 4.50 89 10 x Anti Track EHT Cap 2.00	179 TDA2532 2.40 180 TDA2540 1.65 181 TDA2541 2.67 182 TDA2560 3.28 183 TDA2571 2.15 184 TDA2591 0.98 185 TDA2593 2.23 190 TDA2600 4.00 191 TDA2611 1.24 192 TDA2640 2.35 210 ETT8016 2.28 211 ETT8016 2.28 212 BTT8018 2.28 220 SL9018 Int Circuit 5.00	030 GEC 2100 Hybrid 4.00 032 Thorn T x 9 Chass. 14.50 033 Philips KT3 8.00 034 RRI T24 Chass. 14.00 035 Sanyo CTP5101 9.50 037 Split Diode EHT Lead 1.35	SPECIFIC COMPONENTS 351 Thorn 1591 Speaker 2.00 352 Thorn 1600 Dropper 0.50 353 T x 10 Preset Drawer 3.00 354 T x 10 CRT Base Assy 4.00 355 3" Round 8R Speaker 1.00 358 5 x Tho/3500 200 Conv. Pot. 1.00 359 5 x Tho/3500 50R Conv. Pot. 1.00 360 5 x TCE3500 A1 Rectifier 0.75 362 19000 Rem. Receive Assy 5.00 363 T3500 Mains TX 5.00 364 T8500 Mains TX 7.50 365 T8500 (Plastic) Cnt Holder 1.50 370 Pye 731 Thick Film Resis. 1.50 371 Pye 713/731 Vis. Gain Mod. 6.00 372 Pye 731 3R3 50V Metal cld. 1.29 373 100K x3 Drawer P'set Alt Pye 731 2.00 378 Grundig 5010/6010 Vid Mod. 4.00 384 5 x 10R Phil. G8 Conv. Pot. 2.40 385 5 x 15R Phil. G8 Conv. Pot. 2.40 386 5 x Phil. G8 2k x2 Lin. Bright. 2.50 387 5 x Phil. G8 10k Log. Colour 2.50 388 5 x Phil. G8 47k Log. Vol. 2.50 389 G8 Plastic Mains Switch 0.75	390 G8 Metal Mains Switch 1.23 391 G8 Line Stor/Eql. Coil 2.25 392 G8 R/G Symetry Coil 3.33 397 20 x 3.15A A/S 20mm Fuse 1.50 398 20 x 800MA A/S 20mm Fuse 1.50 399 20 x 2.5A A/S 20mm Fuse 1.40 401 20 x 1A A/S 20mm Fuse 1.40 402 20 x 1.25A A/S 20mm Fuse 1.40 403 5 x RRI T20 Tube Base 4.35 410 Phil. G11 E/W Load/ Coil 1.50 411 Phil. G11 Bridge TX 1.50 412 Philips G11 Speaker 1.00 415 PALKT3 Speaker 1.50 416 10 x TDA2600 IC Holder 1.50 417 PALKT3 Speaker 1.50 436 5 x Decca 30 10R Fusible 0.50 437 Decca 30 47k Vol. +Switch 1.25 453 5 x 5R Universal Conv. Pot. 1.00 454 5 x 20R Universal Conv. Pot. 1.00 455 5 x 100R Universal Conv. Pot. 1.00 456 5 x 470R Universal Conv. Pot. 1.00 457 10 x 100k Tun/Pres TCE etc. 3.00 458 10 x 100k Tuner Preset G8 3.00 459 ELC1043/05 Tuner 6.00	480 ELC1043/06 Tuner 6.00 461 U321 New Tuner 7.95 462 U322 New Tuner 7.95 463 98003 Posister 0.99 464 98009 Posister 0.99 465 Mull.DL50 Delay Line 0.95 466 5 x VA1104 2.70 468 Cut Out Metal GEC 2100 1.00 470 5 x GEC2100 3 Lag Thermist. 1.00 479 5 x Gen. Purp. Ro- tary Swtch. 3.00 480 5 x Gen. Purp.Push/ Swtch. 3.75 481 20 x Neons GEC etc. 2.25 482 5 x Univ. Aerial Skt. Kit 5.50 483 10 x Metal Coax Plug 1.70 484 Focus Unit T20 Type 1.25 485 Foc/Unit Thorn 8500 Type 1.00 486 4.43Mhz Crystal 0.40 488 10 x Ring Type Spk/ Gap 1.50 489 TX10 Chass. Focus Unit 7.00 497 De-Soldering Pump 3.50 498 1 x 10 Trimming Tool 1.00
EHT TRAYS 50 ITT CVC 5/9 3.00 51 Decca 1730/1830 5.00 52 Decca 80 Series 4.50 53 GEC 2040 Hybrid 3.00 54 T1500 5 Stick 3.50 55 Thorn 9000 7.00 56 Thorn 1400 2.00 57 Philips G9 3.50 58 Universal ITT Type 4.50 59 5 x TV11 EHT Rec for PTV's 1.00 60 3 x TV45 EHT Rec Z718 1.00 61 ITT CVC 46 4.00 63 RRI Z179 3.00 64 Pye 691/697 3.50 65 Pye CT200 4 Lead 3.50 66 Pye CT200 5 Lead 4.50 67 Korting 90 DGR Hyb 5.00	INTEGRATED CIRCUITS 140 5 x TDA440 3.00 141 5 x TBA120AS 1.80 142 5 x TBA540 4.00 143 5 x TBA540Q 4.00 145 5 x TBA580 3.50 146 5 x TBA810S 3.00 147 5 x TBA920Q 4.50 148 5 x TBA990 3.25 149 5 x TBA520Q 4.00 150 5 x TBA530 4.25 151 5 x TBA950 4.50 154 10 x TCA270SQ 4.00 155 5 x MC13270L 2.50 180 TDA1170 1.35 161 TDA1190 1.90 162 TDA1006A 1.45 164 TDA1035 1.83 185 TDA1044 2.23 186 TDA1190 1.90 167 TDA1412 0.90 172 TDA2002 1.80 173 TDA2020 2.50 174 TDA2030 2.15 178 TDA2523 2.35	LINE OUTPUT TX 001 Philips G8 7.50 002 Decca 30 Series 7.00 003 Decca 100 Series 6.50 004 ITT CVC 25/30/32 7.00 005 Philips G9 7.50 006 RRI T20 9.92 007 RRI A823 7.00 008 RRI Z718 18" 18.95 009 RRI Z718 20/22/26" 18.95 010 RRI A774 Mono 10.87 011 Thorn 1690/91 7.00 012 Thorn 1615 6.50 013 ITT CVC 46 6.50 014 Phil TX Chass. 5.00 015 RRI Ranger 1/2 5.00 016 ITT CVC 5/9 8.50 017 Philips E2 Chass. 5.00 018 Thorn 9000 12.00 019 Thorn 9500/9600 8.50 020 Polish 161 Mono 6.00 021 Thorn 3500 Scant450 5.00 022 Thorn 8500 11.00 023 Thorn 1590/91 8.50 024 Thorn 1500 15KV 4.00 025 GEC 2040/2100 Hybrid CTV 4.00 026 Bush 161 Mono 5.00 027 GEC Single Std Mono 5.00 028 Pye 691 (wired) 5.00	PUSH BUTTON UNITS 110 Pye 713 4 Way 7.87 111 Pye 715 6 Way 11.95 112 Phil G8 Square 12.75 113 Phil G8 Sloping 14.90 114 Thorn 9000 2.50 115 Thorn 1615 4 Way 7.87 116 Decca 6 Way 6.95 117 Decca 4 Way 6.50 118 GEC 2110 6 Way 7.95 119 GEC 2136/7 Tapered 7.95 120 ITT CVC5 9.25 121 ITT CVC8 11.46 122 ITT 6 Way with V.C.R. 7.95 123 RRI A823 etc. 7.95 124 Hitachi 4 Way 7.95 125 RRI T20 6 Way 8.95	SMOOTHING CAPACITORS 80 220/400 CVC32/ T20 1.20 81 200+300 Pye 691 2.00 82 600/300 Phil G8 1.90 83 175+100+100 T3500 1.50 84 2000/100 Volt 0.50 85 470 Mfd G11 1.50 86 400+400 Decca 30 2.50 87 200+200+75+25 ITT CVC5/9 1.50 88 400/400V Tho 9000 1.50 89 4700/25 Thorn 1590/ 91 0.60	TRANSISTOR/DIODES 230 10 x AC128 1.50 235 50 x BC213L 2.50 250 10 x BD124 9.00 251 10 x BD131 1.60 270 10 x BU208A 8.50 271 10 x BU208 7.50 272 10 x BU326 10.00 273 5 x BU205 3.75 280 25 x 2N3055 (Texas) 7.50 281 10 x 2N2905 (Equip. BC161/303) 0.50 290 10 x BT106 Thyristor 9.00 292 5 x BT119 4.50 293 5 x BT120 4.50 335 50 x BY127 Diodes 3.00 340 25 x TIP41A 6.50 341 25 x TIP41C 7.00	

All components are A1 quality from prime manufacturers, and are dispatched by post same day as order received together with any refund due. All goods should be delivered within 4 working days.

Please add 15% VAT and 90p P & P

QUICK SAVE T.V. SPARES

MUXTON HOUSE, MUXTON, TELFORD, SALOP.

REG. OFFICE ONLY. CALLERS STRICTLY BY APPOINTMENT. UK ONLY. PLEASE QUOTE STOCK NO.

COLOURTRADE

MANY YEARS OF SUPPLYING TRADE

WORKING COLOUR TVs

PHILIPS 550	£35.00
BUSH	£25.00
BUSH 2718	£45.00
THORN 22" V-CAP	£35.00
THORN 8-800	£45.00
JVC 20"	£35.00
GEC ... ITT ... DECCA ... etc!	

DISCOUNT FOR QUANTITY

WIDE RANGE OF MAKES AND MODELS
ARRIVING DAILY — ALL WITH GOOD
CABINETS — MANY TO CLEAR FROM
'ONLY' £5.00. MIXED LORRY LOAD OF
SETS DELIVERED TO YOUR DOOR
DIRECTLY FROM SOURCE!

TELEPHONE NOW

021-359 0449

COLOURTRADE

221 Bridge Street West,
Hockley,
Birmingham B19 2YU

It's easy to
complain about
advertisements.
But which ones?

Every week millions of advertisements appear in print, on posters or in the cinema.

Most of them comply with the rules contained in the British Code of Advertising Practice.

But some of them break the rules and warrant your complaints.

If you're not sure about which ones they are, however, drop us a line and we'll send you an abridged copy of the Advertising Code.

Then, if an advertisement bothers you, you'll be justified in bothering us.

The Advertising Standards Authority. ✓
If an advertisement is wrong, we're here to put it right.

ASA Ltd, Dept 2 Brook House, Torrington Place, London WC1E 7HN

This space is donated in the interests of high standards of advertising.

The World of

“TELE PANELS”

52 Mount Pleasant Road, Chigwell, Essex.
Telephone 01-729 0506.



COMPARE OUR PRICES!

COMPARE OUR SERVICE!

	IF	TUNER	DECODER	G8/G9 DECODER IF COMBINED	LINE OUTPUT	POWER	CONVERG	FRAME	VIDEO	6 WAY TUNER SWITCH BANK
PHILIPS G.8	5.00	4.50	7.00	15.00	14.00	8.00	5.00	5.00		3.50
THORN 3000/3500	2.00	5.75	4.00		8.00	8.00	5.00	6.00	5.00	1.75
GEC 2110	10.00		5.00		12.00	6.00	5.00	5.00	5.00	5.00
PYE 731	8.00		10.00		18.00	10.00	7.00	8.00		4.50
PUSH Z/718	7.50	6.50	14.00		24.00	3.00	5.00	14.00		
BUSH T/20	7.50	6.50	14.00				5.00	14.00		
DECCA BRADFORD	3.00		7.00			4.00		FRAME TIME BASE £4		
DECCA 80	12.00	P.O.A.	14.00		12.00	10.00		14.00		P.O.A.

Other makes of panels — telephone for prices!

TRIPLERS FOR ALL MODELS £3.00 SPEAKERS £1.50

P+P 1 PANEL £1.50 2 PANELS OR MORE £3.00

CASH WITH ORDER — PLEASE

POST OFF YOUR CHEQUE NOW! & YOUR PANELS SENT BY RETURN OF POST!!!

ELECTRON GUNS TV TUBE COMPONENTS

If you are Rebuilding or Manufacturing TV tubes — We are the leading suppliers of Electron Guns and TV Tube Components to the TV Tube Industry. We specialise in all aspects of Electron Mount Technology.

Our product range includes more than 250 gun types for Colour, In Line, Mono and Display Tubes along with Mount Parts, Bases, Getters, Seal-offs, and all other associated items for TV Tube Production.

A Full Technical Back-up and Advisory Service is available to all customers World-wide.

Please request our current catalogues and Data Information.

GRIFTRONIC EMISSION LTD
NEW ROAD, STUDLEY,
WARWICKSHIRE B80 7LY
ENGLAND.

Telephone: 052-785 2684 or 2639 Telex: 336924 Grifem G.

TV LINE OUTPUT TRANSFORMERS

FAST RETURN OF POST SERVICE

RANK BUSH MURPHY Z146 A640 dual std mono 7.00 Bush A792, A793 single std mono 7.00 A774 single std mono 7.00 A816 solid state mono 9.00	PHILIPS 170 series dual std mono 7.00 210 300 series mono 7.00 G8 & G9 series colour 8.00 PYE 368, 169, 569, 769 mono 7.00 725-741 colour 8.00 WALTHAM 125 9.00
DECCA MS1700 2001 2020 2401 mono 7.00 MS2404 2420 2424 mono 7.00 CS1730 1733 colour 8.00 CS1830 1835 colour 8.00 '30' series Bradford colour 8.00 80 series colour 8.00 100 series colour 8.00	REWIND SERVICE - available for most continental types, i.e. Kuba, Luxor, Korting, Tyne, BerrySkantic, K80 £15.00 inc pp, VAT. Old lopt required. WINDINGS SOVEREIGN FARA £15.00 PLUSTRON PALLADIUM 14" colour overwind RANK BUSH MURPHY T20a T22, T26 Pri & Sec 6.00 Z718 primary state 18" or 22" 6.00 Z718 EHT overwind 7.00 ULTRA THORN 1690-1691 EHT overwind 7.00 1590 EHT overwind 6.00 PYE 173P, 174P, 175P, T57 chassis EHT overwind 8.00 or send old LOPT for rewind £10.00
FERGUSON HMV MARCONI 1600 8.00	PRICES INCLUDE P.P. & 15% VAT
G.E.C. 2047 to 2105 7.00 2000 to 2064 dual std mono 7.00 DUAL STD hybrid colour 8.00 SINGLE STD hybrid colour 8.00	
Indesit 20EGB 24EGB mono 9.00	
KB - ITT VC200 VC205 VC207 mono 7.00 CVC5 CVC7 CVC8 CVC9 col. 8.00 CVC20 series colour 8.00 CVC30 CVC32 series colour 8.00 CVC45 8.00	

All lopts and windings are new and guaranteed

Open Mon.-Fri. 9 to 5.30 pm
Delivery normally by return.

**PAPWORTH
TRANSFORMERS**

80 Merton High Street,
London SW19 1BE

S.A.E. all enquiries
Barclaycard and
Access welcome



For orders
placed
at the
post office
Trans
cash
506 4656

01-540 3955

SEND NO MONEY

Your order despatched C.O.D. from our comprehensive stocks of Audio, Video and T.V. spares.

Price list sent with your first order.

Simply phone us
0934-419147

Freeway Components, The Airport
Weston Super Mare, Avon BS24 8RA

CentreVision

TEL: 0222-44754
SLOPER ROAD
LECKWITH
CARDIFF CF1 8AB

OPPOSITE CITY FOOTBALL
GROUND
5 MINS FROM M4

★ WORKING SETS ★

TELEVISION/VIDEO
(VHS + BETA)
MOST IN WORKING ORDER
WITH STAND

- ★ ITT CD752 REMOTE £115
- ★ PHILIPS G11 (some remote) £65
- ★ GEC STARLINE 22-20 (Remote) £55
- ★ PYE CHELSEA £38
- ★ THORN 9000 20" £39
- ★ DECCA 22" BLACK
FRONT VERICAP £30
- ★ RANK T20 REMOTE £65
- ★ OFF THE PILE SETS FROM £8

PRICES SUBJECT TO VAT

OPENING HOURS:
MONDAY - FRIDAY 9.00 - 5.30
SATURDAY 9.00 - 1.00

TV TUBE POLISHING AT

Your Own Premises
with our DIY Polishing Kit

The Kit includes:
Everything you need to polish approx. 25" tubes to a high standard. Detailed instructions on how to do the polishing. All you require is an Electric Drill.

Kit Price £45 inc P&P and VAT.
Available from Luton only.

**Depends on depth and area to be polished.*

TV TUBES TUBE POLISHING
FREE DELIVERY*

Quality, High Temperature Reprocessing

Colour Tubes	One year guarantee (optional extension up to three years)	Two year guarantee (optional extension up to four years)
Delta		
90° up to 20"	£26	£29
90° up to 22"	£30	£33
90° up to 26"	£32	£35
110° 26"	£33	£36
(fast heat, narrow neck)		
In Line & PIL		
Up to 20"	£36	£42
Up to 22"	£38	£44
Up to 26"	£40	£46

All tubes exchange glass required.

Your good, working tubes with scratches or small chips, can be POLISHED with our purpose built polishing equipment. Only £7 per tube.

Delivery charge on colour tubes: Within 40 miles of Luton.

1 tube £4. 2 or more tubes FREE DELIVERY ★

Nationwide delivery available, charges on application.

Please add 15% VAT to all prices. Callers welcome. Please phone first.

WELL VIEW

114-134 Midland Rd,
Luton, Beds.

Open Mon-Fri 8am-6pm, Sat 9am-5pm. Tel. 0582-410787

Your Local Tube Stockist:

Well View, Southampton. Tel. 0703 331837.

Retach Ltd., Northwood, Middx. Tel. 09274-27019

West One Distributors Ltd., Chesham, Buckinghamshire.

Tel. 0494-778197

Rushden Rentals Ltd., Rushden, Northants. Tel. 0933-314901

Daventry Rentals, Daventry, Northants. Tel. 03272 77436

Rea & Holland, Ipswich, Suffolk. Tel. 0473 827562

WANTED A56/A66-510X/540X Old glass for cash

TUNERS + TUNERS

- ★ If you repair sets regularly - phone us today and we will dispatch immediately - no need to send cash 'up front'.
- ★ All tuners dispatched by first class post for receipt by you the next day.
- ★ All popular tuners/tuner repairs supplied 'off the shelf'.
- ★ Unusual types repaired same day as received (subject to spares availability).

TELEPART

32 Temple Street,
Wolverhampton, WV2 4LJ.
Phone: (0902) 773122.

TUBESURE LTD

UNIT 11,
MIDDLEMORE INDUSTRIAL ESTATE
SMETHWICK, WEST MIDLANDS

Tel: 021-558 7777

- ★ REBUILDERS OF HIGH QUALITY CRT'S INCLUDING THOSE FOR PROJECTION SETS & GAMING MACHINES
- ★ MANY PIL TUBES IN STOCK NOW
- ★ SUBSTANTIAL DISCOUNTS FOR QUANTITY ORDERS
- ★ TWO YEAR GUARANTEE

DISTRIBUTORS REQUIRED
ANY AREA CONSIDERED



TEL-X BLACKBURN

FOR THE VERY BEST IN
TELEVISION DISPOSALS

Decca Thorn Pye Bush
Philips ITT GEC + Remotes

☆ ☆ ☆ ☆ ☆ ☆ ☆ ☆

HUNDREDS TO CHOOSE FROM
WORKERS FROM **£25.00**
Off the Pile from **£ 8.00**

☆ ☆ ☆ ☆ ☆ ☆ ☆ ☆

DELIVERIES ARRANGED ON QUANTITY

TEL-X BLACKBURN

Unit P3, Roe Lee Industrial Estate,
Whalley New Road,
Blackburn, Lancs.
Tel: 0254 679984

VIDEO CASSETTE RECORDER SERVICING COURSES

6 WEEKS FULL-TIME
(Jan 7th to Feb 15th)

Intensive course intended for qualified television service engineers or applicants with similar background.

The course combines the advantages of industrial and academic training and includes a high percentage of practical work.

Selected applicants will be eligible for a full grant from MSC under TOPS to cover tuition fees and maintenance.

(Refresher and beginners courses also available in Electronics, TV and Video from 3 to 15 months with high Practical content commencing Jan and April – full-time & evenings).

Prospectus from:

LONDON ELECTRONICS COLLEGE (Dept TVC)
20 PENYWERN ROAD, EARLS COURT,
LONDON SW5 9SU. Tel: 01-373 8721

TELETRADERS

Forde Road, Brunel Industrial Estate,
Newton Abbot, Devon
Telephone: (0626) 60154

The Best Quality Sets Available
Anywhere

All First Class working order and excellent cabinets.

Philips G8 550	£40
Philips G11	£85
GEC Solid State	£35
Thorn 3500 Electronic 22"	£35
Thorn 9000	£60
Thorn 8800	£45
Thorn 9800	£55
Thorn 1500 Mono 20" very clean	£6

Full spares back-up of tubes and panels –
Bulk terms to other wholesalers

☆ ☆ ☆

THE NO. 1 WHOLESALE IN THE SOUTH

TV DISTRIBUTORS NORTHERN

★ ★ ★

LEEDS NEWEST WHOLESALE IS NOW OPEN
WORKING COLOUR TVs

PHILIPS 550	£35.00
THORN 8000	£30.00
THORN 8800	£45.00
JVC 20"	£35.00
HYBRID MIXED	£8.00

GEC – DECCA – ITT – PYE

OFF THE FLOOR PRICES AVAILABLE ON REQUEST

For further details:

Telephone now: 0532 624996

TV DISTRIBUTORS NORTHERN

Unit 10, Ashley Trading Estate, Buslingthorpe Green, Leeds LS7 2HG

SATELLITE RECEIVING SYSTEMS

1m and 2m glassfibre dishes
other sizes available.

Feeds, support and mounting systems.
Low noise amplifiers, downconverters.
Complete terminals for 4 Ghz, other frequencies available.

Demonstrations by appointment.

L & S Bear Electronics Ltd.
Yeo Lane, Colley Lane,
Bridgwater, Somerset.

Telephone: Bridgwater (0278) 421719

CENTRAL T.V.

STAR BUY★
30 PHILIPS G8/520 22" £270

STAR BUY★
25-PHILIPS G8 520 22" £450

25-PHILIPS G8 550 22" £550

ALL SETS SOLD ARE WORKING & READY TO

STAR BUY★
10 FERGUSON 3V22 VIDEOS £1500

IN PERFECT WORKING ORDER

EXPORT ENQUIRIES WELCOME ON TV's & VIDEOS
 BRAND NEW & GRADE 'B' 14", 16", 22" CTV's & VIDEOS
 LATE MODEL T.V.'s ● PHILIPS G11 ● ITT REMOTE
 JAPANESE & DECCA 80/100 SERIES

LORRY LOAD DIRECT FROM SOURCES DELIVERED TO YOUR DOOR

HOT LINE: 01 807 4090
01 884 1314

HOT LINE: 021 622 1023
021 622 1517

Cedar House, Nobel Road,
 Eley Estate, Edmonton, London.

48/52, Pershore Street,
 Birmingham.

THE ONE TO WATCH...

The easiest way to receive
TELEVISION every month is to start
 an annual subscription.

Your copy will be delivered direct to

your door regularly—enabling you to
 keep fully in the picture with the very
 latest technology and servicing
 techniques.

SUBSCRIPTION RATES

U.K. £11.00
 Overseas £12.00

**COMPLETE
 AND POST
 THIS
 ORDER FORM
 TODAY!**

TELEVISION

SUBSCRIPTION ORDER FORM

Complete this form and
 post it, with payment or
 credit card authorisation
 to:

Television
 Subscription Dept.
 Oakfield House,
 35 Perrymount Road,
 Haywards Heath,
 West Sussex RH16 3DH

POST COPIES TO:

NAME: _____

ADDRESS: _____

POST CODE: _____

I enclose my cheque/P.O. payable to IPC Magazines Ltd. for £. _____
 Charge my credit card A/C at quoted rate

_____   

Card valid from: _____ to _____

Signature _____ **23**

Annual Subscription Rates	
U.K.	£11.00
Overseas	£12.00



**MYSTERY, MAGIC
AND SUSPENSE...
ADVENTURE
LOGIC AND LUCK**

Test your skill with the new
fantasy adventure game

**"THE TOWER
OF TERROR"**
IN

**ON
SALE
NOW**



NEW

PROTEUS 65p
1291
A Complete Fantasy Adventure Game Magazine



**LONDON'S LARGEST
TELEVISION WHOLESALER . . .**
with over 4½ thousand sq. feet.

"TELEMANN"

8-10 RHODA STREET,
(Off Bethnal Green Road)
LONDON E.2. FREE CAR PARK
TEL: 01-739 2707

PHILIPS 22" Parcel of 10
G8/550 (Piano Keys) **£15** EACH

(THE SAME PARCEL IN A 26" £13 each)

★ **FREE DELIVERY TO THE LONDON AREA** ★

THE only wholesaler with a guaranteed
single price. If the sets work or not our
price is the same!

CALLERS WELCOME! or TELEPHONE BARRY:
01-739 2707 → ² LINES! ← **01-739 3123**

Genuine **"CASH DISCOUNTS"** for quantities

FURTHER SPECIAL OFFERS . . .
PHILIPS VCR 1700 **£30.00**
PIL C/R/ TUBES **£19.50** + guaranteed
MONO 24" (parcel of 10) **£2.50**

FREE CAR PARK + NO YELLOW LINES OUTSIDE!

SATELLITE RECEIVING EQUIPMENT

1.9M, 2.5M and 5M Harrison Dishes
Sat-Tec R5000 4GHz Receivers
Avcom COM-2B 4GHz Receivers
California Amplifier 4GHz LNAs
Chaparral Feed Horns

Components: Chip capacitors and Resis-
tors, Microwave Substrate, PTFE etc.

HARRISON ELECTRONICS

22 Milton Road,
Westcliff-on-Sea, Essex SS0 7JX.
Telephone: Southend (0702) 332338

MAIL ORDER ADVERTISING

British Code of Advertising Practice
Advertisements in this publication are required to conform to the British Code of Advertising Practice. In respect of mail order advertisements where money is paid in advance, the code requires advertisers to fulfil orders within 28 days, unless a longer delivery period is stated. Where goods are returned undamaged within seven days, the purchaser's money must be refunded. Please retain proof of postage/despatch as this may be needed.

Mail Order Protection Scheme
If you order goods from Mail Order advertisements in this magazine and pay by post in advance of delivery, Television will consider you for compensation if the Advertiser should become insolvent or bankrupt provided:

- (1) You have not received the goods or had your money returned; and
- (2) You write to the Publisher of Television summarising the situation not earlier than 28 days from the day you sent your order and not later than two months from that day.

Please do not wait until the last moment to inform us. When you write, we will tell you how to make your claim and what evidence of payment is required.

We guarantee to meet claims from readers made in accordance with the above procedure as soon as possible after the Advertiser has been declared bankrupt or insolvent.

This guarantee covers only advance payment sent in direct response to an advertisement in this magazine not for example, payment made in response to catalogues etc., received as a result of answering such advertisements. Classified advertisements are excluded.

AA117 9p	BC182L 6p	BD225 31p	BU110 110p	TIP42A 22p	2N2484 20p	2SC1969 130p	IN.4002 4p	LM323K 420p	PCL85 55p	4032 67p	4506 110p
AA119 9p	BC183 6p	BD232 31p	BU111 140p	TIP42C 25p	2N2486 38p	2SC2029 120p	IN.4003 4p	LM723 32p	PCL86 55p	4034 145p	4507 45p
AA127 28p	BC184 6p	BD234 32p	BU126 70p	TIP47 40p	2N2904 20p	2SC2078 120p	IN.4004 4p	78HGKC 570p	PCL805 55p	4035 70p	4508 125p
AC126 17p	BC184L 6p	BD238 24p	BU206 70p	TIP48 40p	2N2905 20p	2SC2122A 200p	IN.4005 4p	78H05KC 520p	PFL200 85p	4038 71p	4510 57p
AC127 15p	BC212 6p	BD433 24p	BU208 75p	TIP110 47p	2N2906 18p	2SC2352 27p	IN.4006 4p	78GU1C 190p	PL36 90p	4040 57p	4511 57p
AC128 15p	BC212L 6p	BD437 28p	BU208A 80p	TIP112 54p	2N2907 18p	2SD234 37p	IN.4007 5p	78GU1C 215p	PL504 95p	4041 50p	4512 57p
AC128K 23p	BC213 6p	BD535 38p	BU208D 120p	TIP115 45p	2N2926 8p	2SK135 400p	IN.4148 2p	79GU1C 150p	PL508 190p	4042 58p	4513 120p
AC141K 23p	BC214 6p	BD536 38p	BU208E 120p	TIP117 56p	2N3019 20p	MB3712 150p	IN.5400 9p	79HGKC 670p	PL519 450p	4043 57p	4514 110p
AC142K 23p	BC214L 6p	BD537 38p	BU209 85p	TIP120 43p	2N3053 18p	TA7205 90p	IN.5401 10p		UPC575 100p	4044 56p	4516 65p
AC153K 23p	BC215 6p	BD538 38p	BU209A 85p	TIP121 46p	2N3054 35p	DIODES	IN.5402 10p	VALVES		4047 65p	4518 65p
AC176 18p	BC237 7p	BDX32 100p	BU407 75p	TIP125 47p	2N3055 32p	AA119 9p	IN.5403 11p	DY87 53p	Y88 48p	4048 49p	4520 65p
AC176K 20p	BC238 7p	BDX85 80p	BU408 100p	TIP126 56p	2N3058 38p	AA119 9p	IN.5404 11p	DY82 45p	Y88 48p	4049 49p	4522 60p
AC187 15p	BC300 16p	BF180 18p	BU500 110p	TIP127 56p	2N3440 58p	BY100 40p	IN.5405 12p	ECC82 40p	Y88 48p	4050 49p	4526 60p
AC187K 20p	BC301 18p	BF181 18p	BU526 80p	TIP147 100p	2N3442 85p	BY103 32p	IN.5406 13p	ECC83 43p	Y88 48p	4051 62p	4527 60p
AC188K 23p	BC302 18p	BF183 20p		TIP147 100p	2N3702 9p	BY126 6p	IN.5407 13p	ECC84 40p	Y88 48p	4052 61p	4528 65p
AC188 23p	BC303 18p	BF184 20p	C106D 23p	TIP255 56p	2N3703 9p	BY127 8p	IN.5408 13p	ECC85 40p	Y88 48p	4053 61p	4529 65p
AC191 40p	BC327 6p	BF185 20p		TIP305A 38p	2N3704 9p	BY133 8p		ECC86 40p	Y88 48p	4054 61p	4530 65p
AD142 60p	BC328 6p	BF194 5p	MJ2500 100p	TIP305B 34p	2N3705 9p	BY164 22p	LOW PROFILE SOCKETS	ECC87 40p	Y88 48p	4055 61p	4531 65p
AD149 45p	BC328 6p	BF196 5p	MJ2501 110p	TIP305C 34p	2N3706 9p	BY176 85p	8 pin 6p	ECC88 40p	Y88 48p	4056 61p	4532 65p
AD161 22p	BC357 6p	BF199 6p	MJ2955 55p	TIP305D 34p	2N3707 9p	BY179 35p	14 pin 8p	ECC89 40p	Y88 48p	4057 61p	4533 65p
AD162 22p	BCY32 150p	BF200 16p	MJ3000 115p	TIP305E 34p	2N3708 9p	BY182 32p	16 pin 9p	ECC90 40p	Y88 48p	4058 61p	4534 65p
AF124 25p	BCY33 150p	BF240 16p	MJ3001 115p	TIP305F 34p	2N3709 9p	BY184 32p	18 pin 12p	ECC91 40p	Y88 48p	4059 61p	4535 65p
AF125 25p	BCY34 150p	BF241 12p	MJ3002 115p	TIP305G 34p	2N3711 85p	BY187 32p	20 pin 14p	ECC92 40p	Y88 48p	4060 61p	4536 65p
AF127 25p	BCY42 20p	BF255 10p	MJ3003 115p	TIP305H 34p	2N3712 90p	BY196 20p	22 pin 16p	ECC93 40p	Y88 48p	4061 61p	4537 65p
AF139 22p	BCY56 15p	BF256 18p	MJ3004 115p	TIP305I 34p	2N3713 100p	BY206 11p	24 pin 18p	ECC94 40p	Y88 48p	4062 61p	4538 65p
AF239 22p	BCY70 16p	BF257 18p	MJ3005 115p	TIP305J 34p	2N3819 25p	BY207 11p	28 pin 20p	ECC95 40p	Y88 48p	4063 61p	4539 65p
AL112 70p	BCY71 16p	BF258 18p	MJ3006 115p	TIP305K 34p	2N3866 68p	BY208 18p	40 pin 25p	ECC96 40p	Y88 48p	4064 61p	4540 65p
AL113 80p	BCY72 16p	BF259 18p	MJ3007 115p	TIP305L 34p	2N4031 25p	BY210 22p		ECC97 40p	Y88 48p	4065 61p	4541 65p
AS215 100p	BD115 25p	BF336 20p	MJ3008 115p	TIP305M 34p	2N4036 25p	BY223 120p	ZENERS	ECC98 40p	Y88 48p	4066 61p	4542 65p
AS217 100p	BD124P 50p	BF337 20p	MJ3009 115p	TIP305N 34p	2N4037 25p	BY225 18p	400MV	ECC99 40p	Y88 48p	4067 61p	4543 65p
AU110 110p	BD124 110p	BF338 20p	MJ3010 115p	TIP305O 34p	2N4443 76p	BY226 18p	BZY88 Range	ECC100 40p	Y88 48p	4068 61p	4544 65p
AY102 180p	BD128 35p	BF362 30p	MJ3011 115p	TIP305P 34p	2N4444 76p	BY227 19p	2V7 to 3V 6p	ECC101 40p	Y88 48p	4069 61p	4545 65p
AY106 180p	BD131 25p	BF422 21p	MJ3012 115p	TIP305Q 34p	2N5061 20p	BY228 32p	1.3W Zeners	ECC102 40p	Y88 48p	4070 61p	4546 65p
	BD132 25p	BF458 19p	MJ3013 115p	TIP305R 34p	2N5294 30p	BY228 32p	BZX61 Range	ECC103 40p	Y88 48p	4071 61p	4547 65p
	BD135 20p	BF459 19p	MJ3014 115p	TIP305S 34p	2N5296 30p	BY228 32p	2V7 to 3V 12p	ECC104 40p	Y88 48p	4072 61p	4548 65p
	BD136 20p	BF459 19p	MJ3015 115p	TIP305T 34p	2N6106 40p	BY228 32p		ECC105 40p	Y88 48p	4073 61p	4549 65p
	BD137 20p	BF459 19p	MJ3016 115p	TIP305U 34p	2N6107 40p	BY228 32p		ECC106 40p	Y88 48p	4074 61p	4550 65p
	BD138 20p	BF459 19p	MJ3017 115p	TIP305V 34p	2N6109 40p	BY228 32p		ECC107 40p	Y88 48p	4075 61p	4551 65p
	BD139 20p	BF459 19p	MJ3018 115p	TIP305W 34p	3N128 55p	BY228 32p		ECC108 40p	Y88 48p	4076 61p	4552 65p
	BD140 20p	BF459 19p	MJ3019 115p	TIP305X 34p	3N143 85p	BY228 32p	VOLTAGE REGULATOR	ECC109 40p	Y88 48p	4077 61p	4553 65p
	BD141 20p	BF459 19p	MJ3020 115p	TIP305Y 34p		BY228 32p	7805 35p	ECC110 40p	Y88 48p	4078 61p	4554 65p
	BD142 20p	BF459 19p	MJ3021 115p	TIP305Z 34p		BY228 32p	800MV 35p	ECC111 40p	Y88 48p	4079 61p	4555 65p
	BD143 20p	BF459 19p	MJ3022 115p	TIP305AA 34p	JAPANESE TRANSISTORS	BY228 32p	7812 35p	ECC112 40p	Y88 48p	4080 61p	4556 65p
	BD144 20p	BF459 19p	MJ3023 115p	TIP305AB 34p	600	BY228 32p	7818 35p	ECC113 40p	Y88 48p	4081 61p	4557 65p
	BD145 20p	BF459 19p	MJ3024 115p	TIP305AC 34p	2SA73 30p	BY228 32p	7824 35p	ECC114 40p	Y88 48p	4082 61p	4558 65p
	BD146 20p	BF459 19p	MJ3025 115p	TIP305AD 34p	2SA104 32p	BY228 32p	7905 35p	ECC115 40p	Y88 48p	4083 61p	4559 65p
	BD147 20p	BF459 19p	MJ3026 115p	TIP305AE 34p	2SA198 22p	BY228 32p	7912 40p	ECC116 40p	Y88 48p	4084 61p	4560 65p
	BD148 20p	BF459 19p	MJ3027 115p	TIP305AF 34p	2SA203 30p	BY228 32p	7915 40p	ECC117 40p	Y88 48p	4085 61p	4561 65p
	BD149 20p	BF459 19p	MJ3028 115p	TIP305AG 34p	2SB54 25p	BY228 32p	7918 40p	ECC118 40p	Y88 48p	4086 61p	4562 65p
	BD150 20p	BF459 19p	MJ3029 115p	TIP305AH 34p	2SB77 32p	BY228 32p	7924 40p	ECC119 40p	Y88 48p	4087 61p	4563 65p
	BD151 20p	BF459 19p	MJ3030 115p	TIP305AI 34p	2SB837 120p	BY228 32p	7805 35p	ECC120 40p	Y88 48p	4088 61p	4564 65p
	BD152 20p	BF459 19p	MJ3031 115p	TIP305AJ 34p	2SB8405 22p	BY228 32p	7812 28p	ECC121 40p	Y88 48p	4089 61p	4565 65p
	BD153 20p	BF459 19p	MJ3032 115p	TIP305AK 34p	2SC460 21p	BY228 32p	7815 28p	ECC122 40p	Y88 48p	4090 61p	4566 65p
	BD154 20p	BF459 19p	MJ3033 115p	TIP305AL 34p	2SC495 60p	BY228 32p	7818 28p	ECC123 40p	Y88 48p	4091 61p	4567 65p
	BD155 20p	BF459 19p	MJ3034 115p	TIP305AM 34p	2SC573 40p	BY228 32p	7424 28p	ECC124 40p	Y88 48p	4092 61p	4568 65p
	BD156 20p	BF459 19p	MJ3035 115p	TIP305AN 34p	2N1711 24p	BY228 32p	7905 40p	ECC125 40p	Y88 48p	4093 61p	4569 65p
	BD157 20p	BF459 19p	MJ3036 115p	TIP305AO 34p	2N2218A 24p	BY228 32p	7912 45p	ECC126 40p	Y88 48p	4094 61p	4570 65p
	BD158 20p	BF459 19p	MJ3037 115p	TIP305AP 34p	2N2219 24p	BY228 32p	7915 48p	ECC127 40p	Y88 48p	4095 61p	4571 65p
	BD159 20p	BF459 19p	MJ3038 115p	TIP305AQ 34p	2N2221 23p	BY228 32p	7918 48p	ECC128 40p	Y88 48p	4096 61p	4572 65p
	BD160 20p	BF459 19p	MJ3039 115p	TIP305AR 34p	2N2222 23p	BY228 32p	7924 48p	ECC129 40p	Y88 48p	4097 61p	4573 65p
	BD161 20p	BF459 19p	MJ3040 115p	TIP305AS 34p	2N2223 23p	BY228 32p	7912 45p	ECC130 40p	Y88 48p	4098 61p	4574 65p
	BD162 20p	BF459 19p	MJ3041 115p	TIP305AT 34p	2N2224 23p	BY228 32p	7915 48p	ECC131 40p	Y88 48p	4099 61p	4575 65p
	BD163 20p	BF459 19p	MJ3042 115p	TIP305AU 34p	2N2225 23p	BY228 32p	7918 48p	ECC132 40p	Y88 48p	4100 61p	4576 65p
	BD164 20p	BF459 19p	MJ3043 115p	TIP305AV 34p	2N2226 23p	BY228 32p	7924 48p	ECC133 40p	Y88 48p	4101 61p	4577 65p
	BD165 20p	BF459 19p	MJ3044 115p	TIP305AW 34p	2N2227 23p	BY228 32p	7912 45p	ECC134 40p	Y88 48p	4102 61p	4578 65p
	BD166 20p	BF459 19p	MJ3045 115p	TIP305AX 34p	2N2228 23p	BY228 32p	7915 48p	ECC135 40p	Y88 48p	4103 61p	4579 65p
	BD167 20p	BF459 19p	MJ3046 115p	TIP305AY 34p	2N2229 23p	BY228 32p	7918 48p	ECC136 40p	Y88 48p	4104 61p	4580 65p
	BD168 20p	BF459 19p	MJ3047 115p	TIP305AZ 34p	2N2230 23p	BY228 32p	7924 48p	ECC137 40p	Y88 48p	4105 61p	4581 65p
	BD169 20p	BF459 19p	MJ3048 115p	TIP305BA 34p	2N2231 23p	BY228 32p	7912 45p	ECC138 40p	Y88 48p	4106 61p	4582 65p
	BD170 20p	BF459 19p	MJ3049 115p	TIP305BB 34p	2N2232 23p	BY228 32p	7915 48p	ECC139 40p	Y88 48p	4107 61p	4583 65p
	BD171 20p	BF459 19p	MJ3050 115p	TIP305BC 34p	2N2233 23p	BY228 32p	7918 48p	ECC140 40p	Y88 48p	4108 61p	4584 65p
	BD172 20p	BF459 19p	MJ3051 115p	TIP305BD 34p	2N2234 23p	BY228 32p	7924 48p	ECC141 40p	Y88 48p	4109 61p	4585 65p</

SETS & COMPONENTS

NEED R.S. COMPONENTS for your project. No account? We will supply. Phone 0376 519208.

GRUNDIG MILLIVOLTMETERS 100µ/300v. Working order £15 + £3.00 P&P. Also P.S.U.'s isolating transformers, etc. S.A.E. Lists. S.H.E., 5 St Josephs Park, Ballycruttie, Downpatrick BT30 7EN.

11GHz Satellite TV Receiver

Receives 'Music Box' Pop music TV Channel on ECS satellite. Can be supplied with or without dish (1.5M minimum in most of UK). Stereo sound decoders available shortly for this channel. *Phone or write for more details.*

HUGH COCKS TV SERVICES,
Cripps Corner, Robertsbridge,
Sussex TN32 5RY.
Tel: 058083 317.

SECOND HAND Colour TV spares and tubes. Most makes. Telephone Southport (0704) 74411. Anytime.

BRAND NEW Monochrome 20ins 110 degrees CRT's £10 each. 25% off Ten's. 01-897 2606 ANYTIME.

JABCO

SWITCH MODE POWER SUPPLY

Self oscillating with outputs isolated from mains. Model A-8v-plus 18v-plus 125v or 150v. Capable of running up most modern T.V.s. Independent of its own P.S., many of which need trigger pulses from the Line T.B.

Fit this P.S. complete into SONY 1340, 1810, 2000 and others for complete reliability.

Model A £32 VAT and postage included. Model B has an optional 200v output in addition, £34 inclusive. Full circuit & instructions. JABCO LOPT Tester still £16.50 inclusive.

J. BAKER & CO.

1 Old Shoreham Road, Southwick,
Sussex BN4 4RD.
Tel: Brighton 593315

GRUNDIG, WORKING FROM £40. Reconditioned panels from £4. Remote handsets wanted. Tequipment oscilloscopes. Ochre Mill 0785 814643.

MULTISTANDARD Colour Television. LUXOR VHF/UHF TV/Monitors to most standards, including PAL/L/SECAM/L (UK/French) option. 20", 22" & 26" from £280. ex VAT. PORTATEL CONVERSIONS LTD., 25 Sunbury Cross Centre, Sunbury, Middlesex. Tel. 09327 88972.

WETSTED TUBES PRESENTS AN UNBEATABLE OFFER

£26 ALL DELTAS ONE PRICE

£40 ALL P.I.L. ONE PRICE

* SPECIAL CRT POLISHING SERVICE
WHILE U WAIT **Only £5**

* ALL DELTA SIZES FROM STOCK
* DISCOUNT FOR ORDERS OF 5 CRTs OR OVER

* FREE DELIVERY WITHIN 20 MILE RADIUS OF MAIDSTONE

Ring Now
Maidstone 872400

or visit our factory.
Unit 32, Branbridges Ind Est.
East Peckham, Kent.

* Agents required in South
Prices do not include VAT

TELEVISION

No other consumer magazine in the country can reach so effectively those readers who are wholly engaged in the television and affiliated electronic industries. They have a need to know or your products and services.

The prepaid rate for semi display setting £6.30 per single column centimetre (minimum 2.5 cms). Classified advertisements 37p per word

COLOUR TV PANELS Fully Tested & Working

	IF	CDA/ Video	Decoder	LTB	Line Board	Power
GEC 2040	3.50	3.50	4.00	5.00	-	-
DECCA 13/30	3.00	-	7.00	5.00	-	4.00
BUSH A823	4.00*	-	10.00*	5.00*	2.50	4.00
THORN 8/8½	-	-	10.00	5.00	-	5.00
PYE 205	3.00	3.50	5.00	10.00	-	-
THORN 3/3½	5.00	5.00	5.00	8.00	-	10.00
G8	6.00	-	8.00	7.00	15.00	5.00

*Please specify prefix A or Z.

Please add 15% VAT to above prices, then add post + packing.
Post + Packing: 1 panel £1.50; 2 panels £2.25; 3 panels £3.00 etc.

Hybrid panels do not include valves.

Also a vast selection of modern working and non-working TVs at low prices. Please ring for current stock.

GOLCAR T.V. SERVICES (formerly LAVITE LTD.),

Old C of E School, Church Street, Golcar, Huddersfield. Tel.: 0484 643273

Callers by appointment only.

Terms cash with order.

Trent Tubes

31 RADCLIFFE ROAD,
WEST BRIDGFORD, NOTTINGHAM
THE QUALITY REBUILDER

PHONE: (0602) 813329

ALL TUBES CARRY A TWO YEAR GUARANTEE
EXTENDABLE TO FOUR

All Sizes of Standard Deltas
ONLY £27.50 (A56-120 - A66-120 etc).

A51-161 - A51-163 **£39.00**

A56/66 510 (20 AX) **£42.00**

A56/66 540 (30 AX) **£49.00**

560 DZB 22 **£43.00**

JAPANESE Types OUR SPECIALITY

1000's more available, VDUs, MONO's, Industrial etc.

EXCHANGE PANEL SERVICE

STOCKISTS

Peterborough
H. DONNOR
0733 71809

Derby
VTA WORKSHOPS
0332 369132

All prices + VAT & Exchange

TORBAY (TRADE) T.V.

Have now moved to larger premises.
Good quality small screen colour
TVs Chelsea's, 560, 207, 9000, etc.

178 Union Street,
Torquay, Devon.
Tel. (0803) 22767.

TELEVISION TUNER REPAIRS

BRITISH, EUROPEAN
JAPANESE ETC.

ELC 1043/05 TUNERS
AS NEW £4.60 inc.

MEN-TU ELECTRONICS LTD.
SALTERNS LANE,
FAREHAM, HANTS.

Tel: 0329-235116

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact COLES-HARDING & CO, 103 South Brink, Wisbech, Cambs. 0945 584188. Immediate settlement.

ELECTRONIC SUPPLIES

MOVING WAREHOUSE LARGE STOCKS OF COMPONENTS
TO CLEAR

Record changers 240v From £4.85 + P&P £3.00
Transcription decks 12v or 240v From £6.50 + P&P £3.00
Pair speakers H13W8JD4 Teak From £5.00 + P&P £3.00
Pair empty speaker cabinets H11W7JD5 £2.50 + P&P £2.00
Service bench pack mixed components, nuts, bolts, washers,
leads, bulbs, magnifier plugs etc. £5.00 + P&P £1.80

Send 17p stamp for Catalogue to:

18 LEUCHA ROAD,
LONDON WALTHAMSTOW E17 or
Phone 01-521 3912 after 6.30 evenings
Trade enquiries for bulk purchase welcome

A.B.D. TELEVISIONS

Suppliers of colour and
mono televisions to the
trade.

Workers and
non-workers:

*Pye Chelsea, Philips, Pye,
GEC, Thorn 8500, 8800,
9000 and 9600, Bush T20
and TT22, ITT 600 series,
Japanese, Hitachi, Nat.
Pan J.V.C.*

Many other modern sets
by popular
manufacturers.

For quotation and
prompt service:
Ring Notts (0602) 864627
UNIT 3+3A,
Meadow Trading Est.
Meadow Lane,
Nottingham NG3 3HQ.

SERVICE PAGES

(minimum 12 words), box number 70p extra. All cheques, postal orders etc., to be made payable to Television, and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Dept., Television Room 2612, IPC Magazines Limited, Kings Reach Tower, Stamford Street, London SE1 9LS. (Telephone 01-261 5846).

TRADE-TEL TV DISPOSALS

Tel: 051-709 1734
G8550s from £8.00
Polished & Tested £30.00
**UNIT B11A South West
Brunswick Dock
Liverpool L3
Merseyside**

REBUILT COLOUR TUBES

EXAMPLE PRICES DELTA
All sizes up to 22" — £28.00
26" From — £32.00

*All In Line P.I.L. Mono Gaming Machine
C.R.T.s 560EGB22 56-611-510JKB22*

20 AX £40.00
30 AX £48.00

Fast U.K. Delivery
Call or Phone:

RE-LIFE T.V. TUBES
PLANE STREET,
OLDHAM, LANCS.
061-665 2668

*Wholesalers REG in North & South Wales
Competitive Prices*

TRADE COLOUR TV's ALWAYS 200 IN STOCK

Colour from £5.00 Mono £2.00

BRAND NEW VIDEOS
V2022 and V2023
VHS and BETA

Just in

20" + 22" GEC

Boxed with stand £85.00

ALL STOCK CHANGES WEEKLY

(0934) 514047/512792/27560

P&R SUPPLIES, Unit 5,

Worle Industrial Estate,

Weston-Super-Mare. Exit 21 M5.

**T.V. SPARES, PANELS
AND MANUALS**
PHILIPS · GRUNDIG

TELEVIEW 01-994 5537
194, Acton Lane, London W.4.

GENERAL TELEVISION TRADE SALES

3-5 UNION ST.
DONCASTER

FACTORS

Telephone:
(0302) 68416

Regular weekly supplies of good quality TVs, all with excellent cabinets, we look after our sets, we don't knock them about, as you'll see if you call, suitable for re-sale or rent. Working or off the pile. We're always happy to see you, whether its for one TV or one hundred and one.

MONDAY TO SATURDAY 9 to 5.30

**GOOD SETS
GOOD SERVICE
CALL & SEE US YOU
WON'T BE DISAPPOINTED**
Special Prices on Philips G8's &
Other Lines

STANDS, LEGS,
SLOTMETERS, PANELS,
TUBES ETC.



**PHONE
NOW**
(0302) 68416

RANK
SABA
KORTING
THORN
EKCO
ETC.

**EXCELLENT MOTORWAY ACCESS FROM MOST PARTS
VIA M1 OR A1
WE'RE ONLY A SHORT DRIVE AWAY**

Sandwell T.V. Centre

1000's of T.V.'s at tremendously low prices.
mono's from £1.00. --- colour from £7.00.
WORKING HYBRID £15-
Brunswick Park rd. Wednesbury off jct. 9. M6.

tel. no.
021-502
3016

CANVEY COLOUR TUBES

Unit 3, Charfleets House, Charfleets Industrial Estate, Canvey Island, Essex.
Tel: Canvey Island (0268) 690577

CURRENT PRICE LIST

DELTA TUBE TYPE FROM £27.50 to £31.50
INLINE TUBE TYPE FROM £35.00
MONO TYPES P.O.A.

ALL PRICES EXCLUSIVE OF VAT.

All Tubes Guaranteed for 2 YEARS and Reprocessed
to Original Manufacturers Specifications.

TELEVISION

Trade & Retail supplies of
s/h colour & mono TVs.
Most makes available,
workers or non-workers

SOUTHPARK DISTRIBUTORS

Unit 4 Rubastic Road,
Brentpark Industrial Estate,
Southall, Middx. UB2 5LL.
01-574 4631, Ext 28

N.W. ELECTRONICS

25 YEARS SUPPLYING THE TRADE

HUGE STOCKS OF COLOUR TV'S 2000 NOW IN STOCK

ROCK BOTTOM PRICES. ALL MAKES, ALL MODELS.

90% WORKERS (off the pile)

GENUINE REPOSSESSIONS AND EX RENT, NOW IN STOCK!

PYE KT 3, PHILIPS G11, G8, BUSH T20, 22, 718, GEC, 2010, 2201, 2002, 2659, HITACHI, SANYO, PYE 222 THORN 9000, 3500, 8800 ETC.

SPECIAL OFFERS

BUSH 2 chip 20"/22" Exc. CAB Cond. GENUINE CHANGE OVERS **£15 EACH**
(special quotes on bulk orders) . . . Single Chip **£10.**

PHILIPS 26" G8 EXC. COND. 550 model.....	£20 each	BUSH 718 PIL TUBE.....	£28
BUSH 22" REMOTE 718 ONLY.....	£30	BUSH T20 LIKE NEW.....	£60
HITACHI 20" MODEL 190 EXC. CAB.....	£20	in lots of 10.....	£55
THORN 9000 PIL TUBE.....	£35	in lots of 50.....	£50

VHS VIDEO

SHARP 7300, 8300, 9300. FERGUSON 3V28 3V22. SONY BETA.

MONO TV'S £1 each (lots of 25)

BUSH, GEC, PYE, PHILIPS ETC. THORN 1500 **£4**. THORN 1600 **£12** (like new).

REFURBISHED TV'S TO ORDER

PHILIPS G11 **£80** BUSH T20/22 **£70** GEC 2010 **£38**

LATER MODELS PHONE FOR QUOTATION

WHITE GOODS

HOOVER TWINS FROM **£6**. HOTPOINT 1460 FROM **£10**.

AUTOS ALL MAKES FROM **£10**

WORKING T.V. PANELS

	I.F.	DECODER	LINE O/P	POWER	CONVERG.	VIDEO	FRAME T3
BUSH 2 CHIP	3.00	8.00	6.00	3.00	3.00	—	5.00
3000/3500	2.00	4.00	8.00	8.00	5.00	5.00	6.00
G8	5.00	7.00	14.00	8.00	5.00	—	5.00
	with sound panel						
GEC 2110	10.00	5.00	12.00	6.00	5.00	5.00	5.00
BUSH 718	8.00	15.00	25.00	3.00	5.00	—	15.00
BUSH T20	8.00	15.00	20.00	20.00	5.00	—	15.00

P&P 1 panel £1.50, 2 panels £2.00,
3 panels £2.50 etc. Quick Despatch - C.W.O. please
ALL PRICES PLUS VAT.

**CASH ONLY - DELIVERY CAN BE
ARRANGED**

**(0274) 688458 OPEN 6 DAYS
A WEEK**

**Unit 12, Wharfedale Road
M606 Euroway Estate
Bradford**

**OPEN MON-SAT 9-5.30
Don't forget! We are open
all day Saturday!**

WORKING COLOUR T.V's
TO THE TRADE FROM

£15

LARGE SELECTION OF
COLOUR T.V's INCLUDING
GOOD DISPLAY OF WORKING
SETS, MANY LATE MODELS, IN
OUR SHOWROOM

DELIVERY CAN BE ARRANGED

PHONE MARK WOODWARD 0299-250161

TRADE, UNIT 40,
HARTLEBURY TRADING ESTATE,
NR. KIDDERMINSTER, WORCS.

COLOUR BAR GENERATOR

Pal Colour Generator with 11 patterns plus sound. Grey
scale, Colour Bars, Red, Green & Blue Raster, Cross-
hatch, Dots, Chequer Board, Black Raster, White Raster,
Half Black & White **£75.90.**



Line Transformer Tester **£11.50**
B/W Generator, Crosshatch, Peak White, Dots, Half
Black & White and Grey Scale **£18.50**
In Circuit Transistor Tester **£14.25**
Capacitance Meter measures 10pF to 1µF complete with
moving coil meter **£14.75**

S.A.E. for details. - Prices include P&P & VAT.

C.M.J. ELECTRONICS

Unit 8, 16 Union Mill Street, Horseley Fields,
Wolverhampton WV1 3DW.
Tel: (0902) 871563

Thorn 3000/3500
Thorn 9000
UNIVERSAL
1 year guarantee

TRIPLERS
£4.95 inc. p&p

The UNIVERSAL TRIPLER can be used in most
G.E.C., I.T.T., Pye, Rank, Decca & Continental
sets.

WING ELECTRONICS

15 Waylands, off Tudor Rd, Hayes End, Middlesex

**STARLITE
ELECTRONICS**

NOW MOVED TO:
WILLOWS FARM,
A13 RAINHAM, ESSEX.
Rainham 23225 also
Hornchurch 50238.

- TV TUBES -

2 year guarantee
Most types available

Japanese including Sony

Ex-Rental TVs from**£15.00**

Untested Panels.....**£4.00**

WOODSDALE COMPONENTS
RANK BUSH MURPHY

TRANSFORMERS

Line Output
Z718 (T703A, T706A) **£20.50**
New (Complete)
Less Focus Module and
Rectifier **£10.50**
T20, T22 (T705A) **£11.00**
T26 (T705B) **£11.00**
Switch Mode
T114A/B **£8.00**

Genuine RBM Units.

AERIALS

UHF Aerials P & C Wideband 4 Bay
Bowtie (12.5 dB) **£20.00**
Above with built-in Broadband amp.
(27dB) plus stabilised power
supply **£45.00**

Prompt Postal Service P&P Paid.

Add 15% VAT to all prices.

DISCOUNT for QUANTITIES.

34 Field End Road, Eastcote,
Pinner, Middlesex. HA5-2QT.
Tel: 01-868 5580.

N. Skehan

Agents Office. Callers by appointment only.

JAPANESE COLOUR TVs. Panasonic, Hitachi, Mitsub-
ishi, Toshiba, Sharp. Fully refurbished. Trade only.
J.M. Pearson Television. 0484 863489.

WORKING CTV's

The Best & Cheapest in Lancashire

I.E. Decca 18" to 26" **£24.00**
GEC 20" to 26" **£30.00**
Philips G8 22" to 26" **£25.00**
Bush 20" to 26" 2 chip **£18.50**

All sets are tested & working

Many more makes & types available.
Working mono's only £3.50. Non work-
ers available.

Phone: John Powney
at Kirkham, near Preston
(0772) 683392.

**WIZARD DISTRIBUTORS
MANCHESTER**

Visit our trade counter and see the huge range
of components inc. tubes and video heads.
Only minutes from the town centre and motor-
way routes.
Fast friendly service and technical assistance
available.
Come in and see our trade counter special
offers.

Open Monday to Friday 9 am to 4.45 pm
Trade Only

EMPRESS STREET WORKS
Empress Street
Manchester M16 9EN

Tel: 061-872-5438, 061-848-0060

SCREENPLAY

*Your Friend in the
TV Business*

Guaranteed - Complete Sets
Trade Workers
Panels by Post
Mono's
Stands Aerials Accessories Etc.

from £5.00
from £25.00
from £3.00
from £1.00

TO CLEAR

BUSH SINGLE/DOUBLE CHIP 5 for £25.00

BRADFORD DECCA 5 for £45.00


PHONE US FIRST FOR WORKING SETS IN
QUANTITY, WE'LL GIVE AN UNBEATABLE
PRICE.

OPEN 6 DAYS 10-6.30pm/10-5.00pm SAT.

Phone:

Baldock 894905

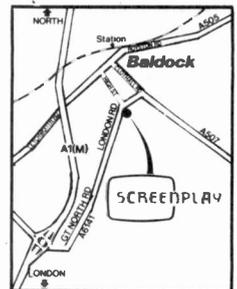**SECTION THREE, UNIT FOUR, SERL COMPLEX,
LONDON ROAD, BALDOCK, HERTS.**



ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Television for

insertions. I enclose Cheque/P.O. for £

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd and made payable to Television)

CAT. HEADING

NAME

ADDRESS

.....

TELEVISION

Classified Advertisement Dept., Room 2612,
King's Reach Tower, Stamford Street, London
SE1 9LS. Telephone 01-261 5846.

Rate
37p per word, minimum 12 words. Box No. 70p
extra.

Company registered in England. Registered No. 53626. Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS.

11/84

PANELS

**GOOD WORKING
POST PAID NO VAT**

Make	Power Supply	Line Panel	T.Base Panel	Decoder D	IF Tripler	Convergenca
Thorn 3500	£12.00	£9.50	£8.50	£5.00	£3.00	£4.00
Thorn 8500	£8.00	-	£9.50	£11.00	-	£4.00
GEC S/S	£8.50	£11.00	£8.50	£8.50	£11.00	£4.00
Bush Twin						
Chip	£6.50	£6.50	£6.50	£11.00	£6.50	£4.00
Decca						
Bradford	£6.50	£6.50	£6.50	£6.50	£6.50	£4.00

TUBES

£29.00

INCLUSIVE, REGUNS TWO YEAR GUARANTEE. QUANTITY DISCOUNTS

£14.50

SIX MONTH GUARANTEE SLIGHTLY USED

A56-120 A56-140 A51-110 A49-191 A47-342 or 343
A44-270-1 A66-120 A67-120 (All 26" add £5)

IN-LINE 51-161 56-500 or 510 £48. One year guarantee. Plus 100's more, ring first.

Delivery £5 per tube. British Isles.
No need to spend £5 returning old tube if you buy from us.

**U-VIEW TUBES,
29 Warmsworth Road,
Doncaster, Yorkshire DN4 0RP.
Tel: 0302-855017.**

Callers ring first: Open every day including Sunday

RANK BUSH MURPHY TV PANELS

Repair, exchange, sales service, prompt efficient service. All chassis covered. New PCB available to replace burnt T20 line Panel. We charge only £16 to repair switch mode power supply. Ring Monday to Saturday and ask for Mr. Kheili.

**T. K. Panels Service,
31 Bronte Paths, Stevenage, SG2 0PG.
Tel. (0438) 61567.**

EAST ANGLIA SUPPLIES

Fully working colour TVs from £25.00 plus VAT straight from our retail shelves. Most makes are available and small regular orders are welcome. Personal services guaranteed and if we can help you boost your rental or retail trade we would be delighted.

Free delivery available
(only petrol charged).

Contact John, Dave or Steve at
Barry T.V. Services
on Cambridge 69215
or Ely 61462

**! YOU HAVE TRIED THE REST
NOW TRY THE BEST !**

Quality 6 Button TVs on Offer

Ultra 6725 22"	GEC S/S
Furg. 3738 22" T/T	ITT CK505
Furg. 3749 22"	Philips 550 22"
Furg. 3722 22"	Bush T20

Also 17" 8000 various models + many more to choose from.

SCARBOROUGH TV TRADERS CO LTD
85 Columbus Ravine, Scarborough,
N. Yorks. 0723 368087.
1 hour from A64/A1 junction

TELEVISION



- * Britain's most reliable source of quality TVs.
- * Hundreds of working polished TVs.
- * GEC Starline
- * Decca 80
- * Decca 88
- * Decca 100
- * Pye G11
- * Thorn 8800
- * Pye 222 Series

All working and polished. These are not from major companies. A lot are from hotels and have had very little use.

Excellent reliable sets for rental.

Krystal Marketing Ltd,
Breedon Cross
Storage,
Dale Road, Selly Oak,
Birmingham B29 6AQ.

Phone 021-471 3023
Telex 335540-G
Ask for Les

Always hundreds in stock COUNTY DURHAMS ONLY WHOLESALE All markets catered for

	UNTESTED	WORKING
G8 520	From £12.00	From £20.00
G8 550	From £12.00	From £30.00
GEC S/S	From £15.00	From £25.00
All Hybrids	From £12.00	From £20.00
Jap	From £20.00	From £30.00

All sets sold as working are fully prepared to the highest standards and are ready for retail or rental.

REGUNNED TUBES

Up to 22" Delta	£27.00	2 yr guarantee
Up to 26" Delta	£30.00	"
Pil & Inline	£45.00	"

All tubes are regunned to the highest specifications. We are the best because we want our customers to come back.

INTERTEL

Unit 27 Whessoe Road,
Darlington (0325) 486896
Co. Durham.

VIDEO

**ARE YOU A TV ENGINEER WHO WANTS
TO KNOW ABOUT VIDEO RECORDERS?**

THEN YOU NEED

**"DOMESTIC VIDEO CASSETTE
RECORDERS A SERVICING GUIDE"**
by S. R. BEECHING

Available for only £15.50 inc. p&p

From: **NEWARK VIDEO CENTRE,**
108 London Rd., Balderton, Newark, Notts.
Tel: 0636 71475 **ACCESS OR VISA**

VIDEO RECORDERS

VHS 125 Betamax £100.
Colour TVs £12.50.

SMITH'S ELECTRONICS

43 Park Parade, Harlesden, London NW10.
01-965 1230 01-961 3997

BOOKS AND PUBLICATIONS

RADIO AND TELEVISION Servicing Books, 30 volumes: 1955-1983. Sensible offers please. Tel. Burnham-on-Sea, 780020.

FULL SIZE TOP QUALITY service sheets £2.50 + I.s.a.e. CTV/Music Centres £3.50 + I.s.a.e. Repair data almost any named TV/Video £10.50 inc. circuits. L.s.a.e. brings any quite free magazine/pricelists. TIST, 76 Churches, Larkhall, Lanarkshire. Tel. 0698 883334.

RADIO AND TELEVISION SERVICING BOOKS. New 74/75 £15. 76/77, 77/78, 78/79, 79/80, 80/81, 81/82, 82/83, 83/84 £22.50 each. Free delivery. U-VIEW, 29, Warmsworth Road, Doncaster. 0302 855017. Callers ring first.

"**RADIO AND TELEVISION SERVICING**" books, new editions for the last 6 years always in stock. Prices on request. BELLS TELEVISION SERVICES, 190 Kings Road, Harrogate, N. Yorkshire. Tel. 0423 55885.

RADIO AND T.V. SERVICING 1967-68 to 1975-76. Mr. D. CLARK, 100 Shepherd Street, Northfleet, Kent. Phone Gravesend 25910.

AERIALS

CLEARVIEW AERIALS

Clearview have pleasure in announcing a full and comprehensive range of signal amplification equipment. For example: low noise electronically remote controlled masthead pre-amp 1.6db noise. CH. 17-69. Set side amplifiers, distribution amplifiers, notch filters 4 in 1 or 2 in 1 etc. Combiners for 2 UHF aerials 3db gain or 4 6db gain. Trade and retail.

Send large SAE for our comprehensive catalogue

CLEARVIEW AERIALS,
173 Kings Road,
Kingston Upon Thames, Surrey.

AERIAL BOOSTERS

B45H/G-UHF TV next to the set fitting, gain about 20db, PP3 battery or 8V to 14V/working. Price £9.70. P&P 30p.

UHF TV BOOSTER MODULE. PCB ready made up to cover the complete UHF TV band. Gain 10db, noise 1.9db. 8V to 14V/W. Price £2.50. P&P 30p.

AMPLIFIED SET TOP AERIALS. Trebles the gain, fully portable, price includes batteries. Price £9.70. P&P 50p.

CAPACITOR PACKS. Mixed C280 & Electrolytics, values from .01uf to 500uf. Price per pack of 150 capacitors £2.00. P&P 50p.

ELECTRONIC MAILORDER,
62 Bridge Street, Ramsbottom,
Lancashire, BL0 9AG.
Tel: Ramsbottom (070 682) 3036.

S.A.E. for leaflets. Access/Visa Welcome.

SATELLITE TELEVISION DISHES

1.2 Metre diameter, kit of 12 aluminium segments with rivets and mounting bracket. Ready to assemble with full instructions. (Limited number available). £89.95 including carriage in U.K. and Eire. Overseas please enquire.

W. N. JONES,
2 Ty'n Rhos, Gaerwen, Anglesey,
Gwynedd, LL60 6HL, Wales.

SERVICE PAGES

SITUATIONS VACANT

TELEVISION SERVICE SHEET SPECIALISTS

Thousands of British, European, and Japanese models in stock.
 Colour £2.00 Mono £1.50 (post free)
 Manual prices on request.

Send stamped envelope for free catalogue and enquiries

SANDHURST TV SERVICES (MAIL ORDER)
 49C Yorktown Road, Sandhurst, Camberley, Surrey GU17 7AG

30,000 SERVICE SHEETS IN STOCK ALSO COLOUR MANUALS AVAILABLE

TV Sheets, Black and White, also Radiograms, Record Players, Music Centres.
 Japanese models in stock. Circuit diagrams only. Also Tape Recorders etc etc.,
ALL AT £3. Please forward s.a.e. Send cheque or P.O.

C. CARANNA, 71 BEAUFORT PARK, LONDON NW11 6BX.

BELL'S TELEVISION SERVICES for service sheets on Radio, TV, etc. £1.50 plus S.A.E. Service manuals on colour TV and Video Recorders, prices on request. S.A.E. with enquiries to B.T.S., 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 55885.

SERVICE PAGES SERVICE PAGES
 This space could cost you as little as £4.44 (i.e. 12 words at 37p). Complete the coupon or ring 01-261 5846 NOW!
SERVICE PAGES SERVICE PAGES

FOR SALE



For a great deal!

VAN LOAD DIRECT FROM SOURCES

Remember all sets cleaned and soak tested. Most makes available, any quantity e.g. GEC, Bush, Decca, ITT, Pye etc.
WORKING SETS FROM £20 upwards. e.g. GEC 2110 £25 min of 6 and etc.

COMPLETE NON-WORKERS from £10 in quantities.
 Black/White in batches of 10 at £1.50 each.


SPECIAL OFFER!

26" GB/3500/HYBRIDS
 QUANTITIES OF 10 @ £5 each

SPARE PARTS AVAILABLE AT COMPETITIVE PRICES.
 PLEASE SEE SEPT/OCT ISSUES.

N.B. Add 30p extra per panel.

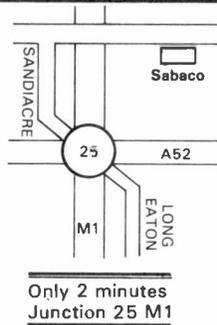ALL PRICES SUBJECT TO VAT & AVAILABILITY.



Sabaco
 Elastic Yarns Building,
 Derby Road, Sandiacre,
 Nottingham.

Open 6 days a week
 9.30 a.m. — 6.00 p.m.

Telephone: (0602) 397555

TOP QUALITY TELEVISIONS SCOTTISH TRADERS

- ★ Wide range of CTV's in good working order from £25 e.g. Thorn 3500, B500, 8800, Bush, Philips GB, GEC S/S CTV etc.
- ★ Plenty of working and complete non-working sets at competitive prices.
- ★ Ready to sell or to rent.
- ★ **Speial Offer** Bush quantity of over 10 at £5 each.

For further information telephone
M. S. VISION
 72 Robertson Street
 Glasgow.
 Telephone: (041) 221-2146.

TUBE REGUNNING. All plant and equipment. Will not split. £3000. 0932 223426 WALTON.

PYE 205 COMPLETE. Some working. 18 remaining plus assorted spares. Buyer collects. £150.00 o.n.o. RENTACET of Amptill. 0525 403466.

WANTED

SERVICEABLE ERASE HEAD for Akai X100D reel to reel T/R. Also motor for Philips RN712 I.C.E. Bognor Regis 862242.

WANTED. We will clear any amount of colour sets from small Rental Companies, Hotels, etc. Please phone P & R Domestic Electrical Clearance Supplies, Weston Super Mare (0934) 514047.

WANTED CONTINUED

VHS VCR's WANTED

QUANTITIES PURCHASED
 WOLVERHAMPTON (0902 405103)

EQUIPMENT FOR SALE

COMPLETE TUBE re gunning plant in good working order. Electric ovens. Re guns 15 colour (Sony Trinitron, Pil, in line etc). Tubes in 24 hour cycles. Only £6000 plus VAT. Free training provided. Tel. 0582 410787.

BUSINESS FOR SALE

BOOMING TV/VIDEO Business, Kent. Absolutely unique! Audited turnover £71,500. Current year predicted £120,000+. Gross profit 150%! Behind-the-scene secrets just cannot be copied. Must sell quickly for family reasons. Full written details: Box TV189.

SERVICE PAGES SERVICE PAGES
 PLEASE MENTION TELEVISION WHEN REPLYING TO ADVERTISEMENTS.
SERVICE PAGES SERVICE PAGES

MISCELLANEOUS

BURGLAR ALARM EQUIPMENT. Latest discount catalogue out now. Phone C.W.A.S. ALARM 0274 731532.

D.I.Y. Projection TV kits. Gives 60inch picture, RF/Video input. For details phone 0376 519208.

C.R.T. REACTIVATOR. New special introductory offer. £27.50 + P.P. £1.50. TELE CENTRE, 398 South Road, Sheffield S61AG.

The Theory and Practice of PAL Colour Television in three important Video Cassette Programmes

- Part 1. The Colour Signal
- Part 2. The Receiver Decoder
- Part 3. Receiver Installation

VHS★★★V2000★★★
 BETAMAX★★★UMATIC

For full details telephone

0253 725499 (Day)
0253 712769 (Night)

Or send for precis details

FLINTDOWN CHANNEL 5
 339 CLIFTON DRIVE SOUTH,
 LYTHAM ST ANNES FY8 1LP
 (enclosing this advert)

NAME

ADDRESS

..... TEL:

All diodes at 10p or less in this list 20 of one type £1.00		Min 12 volt Relays 75p	ZTX 384 10p ZTX 451 10p ZTX 550 10p MJ 2253 60p MJE 3040 60p MJE 2209 10p SP 8385 50p	PHILIPS DIY HOME SECURITY ALARMS KITS Send for details. Prices £54 to £112.						
OA 47 8p OA 90 8p IN 60 5p IN 541 5p IN 914 3p IN 2069a 10p IN 2070 10p IN 4001 3p IN 4002 3p IN 4003 4p IN 4004 4p IN 4005 4p IN 4006 4p IN 4007 5p IN 4148x40 £1 IN 4448x40 £1 IN 4722 10p IN 4751 10p IN 5235 10p IN 5254 10p IN 5349 10p IN 5392 10p IN 5928B 10p LAV 30 10p IM 72255 10p IR 106a 20p IR 3051 10p IS 164 10p IS 921 10p IS 3011a 10p IS 3072a 10p IS 5024a 50p IS 5030 50p ITT 921 10p ITT 923 10p ITT 1075 10p ITT 2001 10p ITT 2002 10p ITT 4150 10p ZE 1.5 10p ZF 3, 3.3, 4.3, 10, 11, 12, 15, 33, 43, 47, 82 10p ZPD 3.9, 4.7, 5.6, 10, 47 10p ZPY 8v2, 12, 16, 24, 43, 47, 56 10p ZTK 22 10p ZTK 33 10p ZTK 33a 10p ZW 13 12p ZW 27 10p ZW 4-3 10p ZW 310 10p ZX 68 30p ZY 47 10p ZY 72 10p AA 113 10p AA 119 8p AA 144 10p BA 102c 10p BA 157 8p BA 159 8p BA 173 8p BA 182 8p BA 201 8p BA 202 8p BA 243 8p BA 248 8p BA 316 8p BA 318 5p BAV 10 10p BAV 21 10p BAW 21 10p BB 103 10p BB 105Ax12 £1 BB 105Bx12 £1 BB 105Gx12 £1 BB 121a 10p BRC 83c13 10p BZX 46c22 15p BZX 61 9-1 6p BZX 61c110 6p BZX 61c20 10p BZX 61c30 10p BZX 61c220 10p BZX 70c6v2 8p BZX 70c12 20p BZX 70c33 8p BZX 79c3v9, 4v7, 5v1, 5v6, 6v2, 6v8, 7v5, 11, 12, 30, 47 10p each BZX 83c4v3, 5v6, 8v2, 12, 13, 24, 27, 33 10p each BZX 84c6v8x10 30p BZX 85c8v2 10p BZX 88c8v7, 3v9, 4v3, 6v2, 8v2, 12 10p each 1A/1600V 10p CV 8617 10p	Y 716 10p Y 729 30p Y 730 10p Y 827: 6A/1KV 20p Y 860 30p Y 933 5p Y 969 50p Y 997 30p R 1038 40p R 1039 40p R 2009 80p R 2010b £1 R 2029 50p R 2210 60p R 2257 60p R 2265 50p R 2305 50p R 2306 50p R 2322/2323 pair 80p R 2323 15p R 2396 50p R 2461 80p R 2030 50p R 2443=BD124 40p R2737 40p R2738=TIP41 30p R2775=TIP41c 40p R3129=TIP47 40p S 2008b 80p BU 105/04 8p BU 108 £1 BU 124 50p BU 126 80p BU 180 65p BU 204 70p BU 205 £1 BU 206 £1 BU 207 £1 BU 208 80p BU 208 on heat sink 70p BU 208A £1.10 BU 208D 90p BU 222 £1 BU 326 £1 BU 407 60p BU 426V 60p BU 500 £1.10 BU 508A 75p BU 526 75p BU 807 £1 BUX 84 50p BUW 84 30p BUY 71 £1 TIC 106a 30p TIC 116m 40p TIC 116v/1003 35p TIC 126N 40p TIC 206m 30p TIC 225S 40p TIC 226E 40p TIC 226m 30p TIC 236m 30p TICV 106D (T092 case 2A/400V) 10p TIP 29 20p TIP 30 35p TIP 30A 35p TIP 30B 40p TIP 30C 45p TIP 31 30p TIP 32 25p TIP 33B 50p TIP 33C 70p TIP 34A 50p TIP 34B 60p TIP 34C 70p TIP 35B 50p TIP 35C 70p TIP 35D 80p TIP 36 50p TIP 36C 70p TIP 41B 40p TIP 41D 70p TIP 42/BRC 6109 30p TIP 48 40p TIP 49 30p TIP 57 30p TIP 102 30p TIP 112 30p TIP 115 30p TIP 117 50p TIP 120 35p TIP 125 35p TIP 130 30p TIP 131 25p TIP 136 30p TIP 140 50p TIP 147 50p TIP 640 50p TIP 2955 35p T 6032 30p T 6036 40p T 6040 40p T 6047 40p T 6049 40p T 6051 40p T 6052 40p T 9004 40p T 9005 40p ZTX 102c 10p ZTX 107 10p ZTX 108c 10p ZTX 109k 5p ZTX 213 5p ZTX 341 10p ZTX 342 10p	U 19885 40p U 3832 15p U 3845 15p MR 508 10p MR 501 10p MR 502 10p BCW 71R 30p BYF 1202 10p BYF 1204 10p BYF 3126 40p BYF 3214 40p BYX 10 6p BYX 36/600 35p BYX 38/300 25p BYX 55/350 10p BYX 55/600 (Bead) 10p BYX 71/350 20p BYX 71/600 50p BYX 72/300 20p BYX 36/600 50p BYV 95B 10p BYV 95C 12p BYZ 106 10p BPW 41 15p BYW 56 2A/1000v G11 8p BZU 15/24 54p BZY 93c75 50p BZV 15/18 30p BZV 15/30 30p BZW 70c6v2 10p BZX 79.3v 10p Bush thyristor RCA 76122 £1 ITT computer bookset 2020 £2 G8 20 turn 100K pot 35p Transformer 240v/20v-500Ma 75p Viewdata torroids £6 CVC 20 tube base £2 Tube Base Rank & G11 £1.20 Sanyo tape motor 75p Swiss made 250rpm/240V motor very small 75p Mono scan coil 110° small neck £1.50 Infra red led 60p LD57CA 15p Mono scan coil £3 G 8 transductor £1 AT 4041/41 transductor £1 2K5 Lin pot with 40mm spindle 20p 1982 Hitachi Ae isolator 50p Mullard FM decoder 1401 £1 Philips service pack, flat films, 57 condensers 56nf-2.2uf £2 VHF 3 Transistor rotary tuner £1 DX-TV £1 15K-20 turn pots 20p Thorn panel 6x100 pot + changeover switch (Irish) 50p Battery converter TA 75 for colour TV. 12/24v Thorn 3787 £6 Thorn 3500 2A cut out 75p Stereo GEC amp 20 watt + pre-amp with 4 pots + mains power unit with circuit £6	10 Mixed TV & radio speakers £5 + £2 post 8Ω 4" speakers £1 4700/10v x 10 50p 68/16 x 10 50p 150/16 x 10 50p 47/25 x 10 50p 220/25 x 10 50p 1/250 x 10 50p 8000/30v 50p 470/40v x 10 £1 22/100v x 10 £1 100/350v 70p 400/350v 70p 47/500v 25p 1/600v 25p .022/1kv 10p	VIEW DATA PANELS NEW 19 I.C. £5 Philips GP422.4CH (£40 cost) £6 Stereo Dynamic Cartridge 12 Volt Aerial Changer over Relays £1 GEC Hitachi V/Cp tuner, after 1979 Series £8 6 Push Button Unit for GEC 2100 Series Replacement for Touch Button Unit £12	8 SEG LED Display with driver I.C. LM1071 50p 20AX GEC Split Diode lead £1.00 GEC Dynamic 20AX Convergence C2233H-R223GH £2.00 Mullard Broadband R.F. power modules VHF. BGY33 £15 UHF. BGY22E £5 PT4236C £5 PT9783	Various Tools and Accessories £1.00 Philips Neon Lamps for TV sets 5p Freeze £1.00 Foam Cleaner £1.00 Contact Cleaner £1.00 Push Button Mains 75p 12 Volt Lorin Full Remote Relay Switch £1.00 Mains timer, 13 amp -- up to 2 hours: easy to use, plugs into socket £3.00 Sellotape PVC Electric Insulation 25mm x 20M 50p 50mm x 20M 70p ITT CVC £8.25 Chassis £40.00	SPECIAL OFFERS UNTIL OCTOBER 10 x G11 Cap 470/250 £15.00 Soldering iron 6w/23w £2.50 240 volt 25 watt Burgess solder iron kit £8.00 Weller solder iron 15 watt/25 watt £5.00 2 way baby alarm/intercom with long leads £5 Philips universal battery tester/charger, fuse/bulb tester To Clear £4 Eisenmann NICAD CHARGER 5.5V/150 ma £2 12V Nicad pack. "AA" £2.50 Hitachi 7.2v/1.8A Nicad pack £6.00 Hitachi TP 007 Battery pack 7.2v/1.6A £7 Hitachi Silver Oxide Battery G13 UCC357 IEC SR44 1.5V 60p 70ML Silicone Sealer (clear) £1 100 Coax Plugs £10.00 De-solder pump + 2 nozzels £5.20 Plastic box for i.c.s with anti-static pad 6"x3"x1" 75p Can of handy oil 'mobil' 40p Flat Red LED 12p 500gm 60/40 solder reel £7 Clearweld glue pack 30p Dual v/u meter -20 - +10db £1 3 x C90 Cassettes 70p K30 thermistor 232266298009 75p GEC Mains Power Supply R.E.G. £3.00	75R/25 Watt 25p 18R/11 Watt 25p 120R/17 Watt 20p Front End Music Center. VHF/MW/LW 13"x3 1/2" £3 Output Stage for music center £5 SONY 1400KV Chroma Panel £6 SONY 1400KV Tuner unit £3.50 SONY 1400KV Touch button unit £3.50 Texas Viewdata Decoder VDP 12/80 Issue 3 with all IC's £10.00	100 Fuses £2.00 100 W/W Res. £1.50 BF 195 20 for £1 10 x 20 Turn 100k pots. Rank £2 Thorn 9 volt power supply regulated £3.00 BF 470 20 for £2 20 Slider Knobs 70p 6 Mixed UHF Aerial Isolating Sockets, some with long leads. Fit ITT, GEC, Philips, Pye £1.00	Mixed Packs TO66 12 Power Trans RCA 16182 NPN Replacement for BD124 and Mounting Kits £1.00 50 Mixed AC series Transistor £4.50 15 Panel mount rocker switch 250V/10A £1.50 25 Panel Mount Bulbs & Neons £1.50 10A £1.50 Mixed ribbon cables £1.00 25 LED red/yellow/green £1.50 20/C Holders £1.20 20 Large LED Red £1.00 20 Small LED Red £1.00 10x20 Turn 100K Pots £1.00 100 Transistor £2.50 20 Convergence Pots 80p 100 Sticks £1.00 10 Thermistors 50p 20 Slider Pots £1.00 30 Presets 50p 15 VDR + thermistors, degaussing, HT, etc. £1.00 40 glass reed switch £1 10 press to make switch 70p 40 Pots £1.50 10 Gun Switches 50p 5 Tube Bases £1.00 1,000 Diodes, Condensers, Resistors on Bandolier £2.00 Lucky Dip 600 gram £1.00 Jungle Bag 5Kg £3.00 20 Knobs £1.00 40 Pots, 1/4"+6mm spindles for audio/TV £3 20mm Fuse Holders 20 for £1 Chassis Mount IN4001/6 100 mixed £2.50 EHT Diodes, small 20 for £1

CB Radio transistor
16119 2A/40v.50Meg
5 for £1.

SPECIAL OFFER
Decca-TTT etc.
FEO4/1/250AC/4
Mains filters
(grey type) x 4
£1

BRIDGES
SKB 2/08 L5A 30p
KBL 005 30p
KBL 02 30p
KBP 04 30p
W02 15p
W004 15p
W005 20p
GEC remote panel. Main transformer 3/1c SAA 1025/SN 74141/TBA 231 £6
AT 2076/35 £7
AT 2076/55 GEC split diode transformer £10
AT 2048/11 LOPTI Mullard £2.50

SENDZ COMPONENTS
TO ORDER SEE BACK PAGE

SENDZ COMPONENTS

TO ORDER SEE BACK PAGE

Thorn Spares		BY 237	5p
9000 Frame panel	£8	BY 254	10p
9000 Cyclops panel	£1.50	BY 255	30p
8800/8500 timebase panel	£8	BY 298	10p
8800 convergence panel	£6	BY 299	10p
8500 convergence panel	£6	BY 406	8p
4000 Chroma	£20	BY 527	20p
4000 Power supply	£3	BY 407a	10p
1600 Mains lead, switch		BY 602	10p
3500 6 push button + cable form	£1.50	F 247	10p
9000 Sound output panel	£1	XK 3102	50p
3500 Focus unit	£1.50	XK 3123	50p
3500 Mains Trans	£4	Hitachi 2A/1500V metal case wire end	20p
3500 2amp thermal cutout	75p		
3500 IF panel	£2		
3500 Frame panel	£3		
3500 Line panel	£3		
3500 A1 Diode	20p		
Export 3500 IF panel	£2		
IC board with set of SN74LS	£4		
4000 Tube base	£1		
3500 A1 pots	50p		
Beam limiter panel	£1.50		
3500 Power panel with Y969	£1		
3 Way regulated adaptor 240V	£3.50		
6V/7.5/9V/300mA			
Rank/Toshiba preh unit 0354	£9.50		
2 banks of 3 PB unit, Pye 731	£2		
4 Push button unit preh	£1.00		
6 Push button VHF/UHF for v/cap, GEC-Decca type	£7.00		
7 Push button for CVC5 IIT	£8.00		
KT3 12 Push button unit	£2.00		
KT3 (Export) 12 P.B.u	£2		
6 Push button Unit Thorn	£1.00		
6 Push button Unit fits GEC & Decca etc.	£6.00		
6 Push button unit for GEC 2040 and ELC 1043/05	£6.00		
Hearing aid unit	£3		
6 Push button unit PYE 713	£7.00		
7 Lamps for P.B./Unit	10p		
Mains Droppers			
G8 2R2+68R	£1.25		
G8 47R 15 watt	75p		
Pye 731 3+56+27R	50p		
Pye 3R5/15R/45R	50p		
Thorn 50/17/1K5	£1.00		
120/20/20/48/117	£1.00		
270/10/6 for Thorn 4000	50p		
18/320/70/39	£1.10		
Thorn 50-40R-1K5	50p		
Ae Socket & Lead			
GEC, IIT, Philips, Pye	25p		
7x3 Thorn	£1		
Rank Toshiba Tube Bases	30p		
Speakers			
6x4 G11	70p		
54x24	3 ohm	£1.00	
5x3	80 ohm	70p	
5x3	50 ohm	50p	
5x3	35 ohm	70p	
6x4	15 ohm	£1.00	
7x3	70 ohm	£1.00	
5x3	8 ohm	70p	
7x3	16 ohm	£1.00	
5" dia	16 ohm	£1.00	
5" dia	8 ohm	£1.50	
6 1/2" dia	4 ohm	£1.50	
6 1/2" dia	3 ohm	£1.50	
2 1/2" dia	8 ohm	75p	
3" dia	8 ohm	75p	
4 1/2" sq.	15 ohm	75p	
KT3 speaker	75p		
3" dia	15 ohm	60p	
K30			
OF-550	10p		
OF-513	10p		
Diodes			
BY 127	10p		
BY 133	10p		
BY 134	10p		
BY 164	50p		
BY 176	25p		
BY 179	40p		
BY 184	25p		
BY 187	10p		
BY 190	40p		
BY 196	30p		
BY 198	10p		
BY 204/4	8p		
BY 206	8p		
BY 208/800	8p		
BY 210/400	5p		
BY 210/800	10p		
BY 223	60p		
BY 224/600: 4.8A/600v bridge	50p		
BY 226	15p		
BY 227	15p		
BY 228	20p		
BY 229/400	30p		
International Rectifier EHT Diodes	20p		
6A/600V Stud Diodes	20p		
6A/1000V Stud Diodes	20p		

NEW PYE 725 line O/P panel with L.O.P.T. & Tripler	£10.00	150/3500	10p
Thorn Mains Isolator unit for 70-80Ω. Ex-speaker	£2	1800/4KV	5p
NEW GEC 20AX Power Supply Switch Mode	£12.00	4.7nf/5KV	10p
Complete new GEC portable chassis M1201H/M1501H with P.B.U./v.cap/LOPTI	£10	170R/8KV	10p
Field + Jungle panel for GEC 3133/3135	£1.50	180R/KV	10p
GEC 2110 line panel with transformer	£7.00	210/8KV	10p
GEC 2110 tuner unit + IF Panel	£12.00	1000/10KV	10p
Pye/Chelsea Line op panel	£12.00	210/12KV	10p
Pye 713 IF panel and tuner	£7.00	1000/12KV	10p
Pye 713 Chroma	£10.00	1200/12KV	10p
Pye/Chelsea Timebase panel with LOPTI	£10.00		
Pye 731 Frame Panel	£5.00		
Pye 731 Convergence Panel	£5.00		
Pye 731 line O/P panel with transformer + tripler	£12.00		
Pye 731 Chroma	£10.00		
Pye 731 IF panel + tuner	£10.00		
Pye 607/205 Line panel with transformer	£10.00		
Pye CDA/205 panel	£6.00		
GEC portable chassis + LOPTI 2114 New	£4.00		
Thorn 1613/1713 chassis	9.75		
Hills 520 multimeter - case, 20,000Ω/volt, fuse diode protected + logic test facility. 10mR/1200 volt	£19.50		
NEW MULLARD TELETEX			
Decoder Panel (VM6230)	£15.00		
Panel 6101	£15.00		
Panel 6330	£15.00		
G8 Tuner Unit + Panel	£6.00		
G8 Convergence Panel (late type)	£12.00		
G8 Power Supply	£6.00		
G8 6 Sloping PBU	£8.00		
G8 IF & Chroma	£12.00		
G8 Chroma	£6.00		
G11 IF Detector	£3.00		
G11 Selector gain module	£3		
Complete CVC 825 Chassis (both panels)	£40.00		
AEC V/Cap Resistor Unit UHF with I.C. SAS660 SAS670	£3.00		
Z714 RANK IF Panels 6MHz 1 I.C. SL437F	£3.00		
Z909B RANK IF Panels			
Export 5.5MHz 2 I.C.'s			
TBA1205B TCA270Q	£2.50		
Z743 RANK IF Panel			
Export 5.5MHz 3 I.C.'s			
TBA750+SC9504P+SC9503P	£1.50		
Pye G11 Front panel with transducer, pots, tuner pots, 6 pb switch+lead	£5.00		
GEC V/cap VHF/UHF tuner and IF+ sound O/P PC 706B3 (Export)	£12.00		
GEC Line O/P PC 659B3	£6.00		
GEC Power Supply (Export)	£10.00		
G11 dynamic correction panel	£6		
CVC 20 Front panel with sliders + mains input panel	£4		
CVC 40 PUSH BUTTON ASSY with sliders: complete with lamp assy + pots	£14		
CVC 5 Mains on/off + 5 pots	£2		
Universal Focus. Fits Pye, Thorn and Decca Units.			
Large Type	75p		
Decca Small	75p		
KT3 Focus Unit	75p		
K30 Focus Pot	75p		
CVC 32 Focus Unit			
Focus Rod	25p		
G11 focus	£2.00		
IIT Small for use with Split Diode	50p		
Revmo TV12SP	50p		
TV13	50p		
TV14	50p		
TV18	60p		
TV20	£1.00		
TV45	50p		
Thorn 14/1500 rec stick	5p		
16 Button Key Pad 1 to 0 + * + # + 4 blank (Cherry)	£3.00		
Condensers			
470/16	6p		
1500/16	20p		
3300/16	20p		
10000/16	25p		
15000/16	50p		
3300/18	20p		
47/25	5p		
470/25	5p		
680/25	5p		
1000/25 Radial	10p		
1500/25	10p		
3300/25	10p		
4700/25	25p		
5000/25	25p		
3500/30	20p		
470/35	6p		
2200/35	25p		
100/40	5p		
220/40	5p		
400/40	20p		
1250/40	20p		
1500/40	20p		
2500/40	20p		
1000/50	20p		
1250/50	25p		
2000/50	20p		
3000/50	25p		
3300/50	25p		
Infra Red and Ultrasonic G11 Teletext Decoder Panel			
RANK & IIT Mains Remote On-Off Switch (720R)	£1.50		
RANK & IIT Mains Remote Switch 2865 ohm	£1.50		
RANK & IIT Remote Switch 2800 ohm	£1.50		
G11 Mains Switch	50p		
4 amp Mains Switch	25p		
GEC Mains Switch 4 amp	30p		
KT3 Mainswitch	£1.00		
THORN Rotary Mains Switch	50p		
G8 Mains Switch	75p		
Thyristor 600/4 amp C106/2	24p		
G11 Preh Red LED P/Buttons for C.H. Change	20p		
RANK TOSHIBA Transducers TPC-2011	50p		
CVC 5 Mains on/off			
+250K+100K+500K+500K Pot on Panel	£2.00		
Thorn 12 or 24 volt battery convertor for portable colour T/V	£12.00		
	Post £1		
TELETEX DECODER			
I.C. SAA 5051			
I.C. SAA 5042			
I.C. SAA 5030			
I.C. SAA 5020 etc.	£18.00		
DISPLAYS			
4040 Clock	£1		
7seg Red LED	50p		
2 digit LED 8,8	50p		
2 digit LED + 1.8 with panel + MC14511	£1.00		
4700/631	£1.50		
250/64	10p		
3300/70	30p		
.1/100	5p		
1/100 x 10	10p		
22/100	5p		
4.7M/100	20p		
470/100	70p		
2000/100	75p		
470/160	10p		
800/160	50p		
1/250 Pulse	10p		
G11 0.47/250	10p		
2.2 250v	10p		
3n3/250 A.C.	10p		
.33/250V	20p		
.39/250V	15p		
4n7/250 tested 5KV	25p		
.91/250	35p		
.91/400	30p		
22/250	15p		
47/250	20p		
100/250	10p		
G11 470/250V	£1.75		
GEC600/250	£1		
700/250	£1		
800/250	40p		
32/300	20p		
4/350	5p		
8/350	10p		
12/300	10p		
4.7M/350v	10p		
16/350	25p		
33/350	20p		
50/350	10p		
220/350	30p		
300/350	40p		
400/350	50p		
10/375	10p		
22/375	15p		
220/385	75p		
330/385 CVC 820HT	60p		
0.1/400	15p		
KT3 E/W .39/400	20p		
.56K/400v	20p		
4700pf/400	10p		
.22/400	10p		
8/400	15p		
33/400	20p		
400/400	20p		
394K/400V	20p		
220/450	40p		
.47/500	25p		
0.1/600	15p		
.047/600	15p		
0.047/1000	10p		
0.01/1000	10p		
0.1/1000	10p		
.15/1000 A.C.	20p		
.001K/1250	10p		
0.0047/1500	10p		
.005/1500	10p		
.0105/1500	10p		
1n8/1500	15p		
2n0/1500	10p		
2n2/1500	15p		
G11.11000/1500	15p		
0.1/1600	15p		
G11.8200/2KV	15p		
0.1/2KV	20p		
10n/2KV	15p		
3n9/2KV	15p		
0.0015/2KV	10p		
5n2/2KV	20		

Tuner Units

G8 Tuner	£7
GEC or Hitachi 6 push button unit 2110 Conversion	£12
GEC 2110 V/Cap	£6
ELC 1043/06 (AEG)	£6
ELC1043/05 Mullard	£6.00
ELC1043 (Ex Panel)	£3.75
ELC1042	£5.00
ELC2000	£7.00
ELC2004	£10.00
ELC2006	£10.00
GEC Tuner V/Cap Hitachi After 1979 ETS48, ET547	£10.00
U322 (UHF)	£4.00
V314 (VHF)	£5.00
U321	£6
U341 UHF	£7.00
U411 UHF	£7.00
U.V. 411 Tuner	£10.00
ELC1043/05 Thorn	£5.90
Small V/Cap Mitsumi	
UHF	£4.00
VHF	£3.00
G8 Tuner	£6.00
Portable & rotary Tuners Sanyo & Mitsumi UHF	£5.00
6003 Bush V/Cap Tuner	£10.00
NSF-UHF/VHF Varicap (old type)	£8.00
Mosfit UHF/VHF (new type)	£8.00
SONY 1400KV Tuner unit	£3.50
Thorn Tuner PANEL with 6x100K pots + cursors NO TUNER	£1.00
HITACHI 20 Turn Pot	40p
U321 on panel	£6.00
Tuner unit VHS Sylvania GTR Videon MTS 900	£2.50
Mullard Video Modulator. Application, video tape recorders, TV cameras, video games, closed circuit TV, C.C.I.R. system. Data supplied.	£10.00
VT 100 Sound Tuner Kit. TV. Viosound. The latest design in low noise fitted with DNR, RF output and audio	£30.00
Sylvania UHF VHF F6013 (Fits Rank)	£6.00
Sylvania F6003	£6.00
Sylvania UHF F4720B	£6.00
Sylvania VHF 900	£6.00
Decca Bradford Tuner 5	£4.00
Button Small Tuner DX 175-220MHz Auto Changeover	£5.00
9000 Thorn Tuner on Panel	£7.00
D.P.D.T. switch Black knob: Chassis or PCB mount	4p
each or 40 for £1.00	

SENDZ COMPONENTS

63 Bishopstegnton, Shoeburyness, ESSEX SS3 8AF
SAME DAY SERVICE
All Items subject to availability.
No Accounts : No Credit Cards
Postal Order/Cheque with order
Add 15% VAT, then £1 Postage
Add Postage for overseas
Callers: To shop at 212 London Rd., Southend. Tel. 0702-332992
Open 9-1/2.30-6. G.V.M.T + school orders accepted on official headings add 10% handling charge.

THORN 1400 4P.B. Mech. Tuner	BFR39	15p
THORN 1500 4P.B. Mech. Tuner	BFR52	7p
THORN 1590 4P.B. Mech. Tuner	BFR79	15p
THORN 3500 4P.B. Mech. Tuner	BFR81	15p
THORN 8000 4P.B. Mech. Tuner	BFR87	10p
THORN 8500 Mech. Tuner	BFS60	10p
	BRC-M-200	40p
	BRC-M-300	50p
	BRC 1330	75p
	BRC 3064	£1.00
	BTT822	£1.00
	BTT6016	£1.20
	BTT6018/ML237B	£1.50
	BTT6218	£1.50
	BTT8124	£1.00
	BTT8224	£1.00
	CA270AE	50p
	CA270CW	50p
	CA270CE	50p
	CA920AE	£1.00
	CA1310	50p
	CA3065Q	50p
	CA3089Q	50p
	CA3094AE	50p
	CA3123	50p
	CA3146	£1.00
	CA3189	£1.00
	CBF16848	50p
	CD4510	50p
	DM7492	50p
	HA1196	40p
	HA1370	£2.00
	HA11223	40p
	HEF4001	10p
	HEF4011AF	10p
	HEF4053B	30p
	M913	£2.00
	MI024=AAA	£2.00
	MI025=AAA	£2.00
	MC476p	£1.00
	MC1307	75p
	MC1312	75p
	MC1330	75p
	MC1349	50p
	MC1352	£1.00
	MC1358	£1.00
	MC1402	15p
	MC14013	25p
	MC14016	25p
	MC14066	30p
	MC14514	50p
	MC1748	80p
	MEM4956	£1.00
	ML231	£2.50
	ML236E	£1.50
	ML237B	£1.50
	ML238B	£4.00
	ML239	£3.00
	MM5387	£1.00
	MM5611	£1.00
	MM5840	75p
	N64100	£1.00
	NE545B (Dolby)	75p
	NE555P	60p
	NE555	60p
	IL-1	20p
	OPT600	20p
	OPT601	20p
	SAA661	£1.75
	SAA 1020	£4.00
	SAA 1021	£4.00
	SAA 1024	£2.50
	SAA 1025	£2.50
	SAA 1073	£3.00
	SAA 1074	£3.00
	SAA 1075	£3.00
	SAA 1124	£2.00
	SAA 1130	£2.50
	SAA 1174	£3.00
	SAA 1176	£3.00
	SAA 1250	£3.00
	SAA 1251	£4.00
	DL20A 80p	DL600 £1.00
G8 (Old Type)	DL700	£1
DL700	BTT822	£1.00
UDL11	30p	
10x630mA fuse	75p	
Luminance Delay Line (CVC 45)	25p	
10x2A fuse	50p	
10x3.15 fuse	50p	
10x500mA	80p	
10x1 amp	80p	
20 3.15 AS Fuses	£1.70	
Co-Ax Joim	15p	
Co-Ax Belling Lee Plug	12p	
Co-Ax Splitter	£1.00	
UHF Modulator CCIR	£3.00	
Infra Red Emitting Diode	20p	
NE286H Small Neon Lamps GEC & Philips	5p	
Mullard 5 Watt Amps. LP1162 New	75p	
	T.V. Tubes	
12" A31/300 Hitachi	£10	
15" A38/170W Hitachi	£8	
18" Hitachi PIL tube with scan coils 470 KCB22-TC03	£25	
	Integrated Circuits	
AC76003	£1.50	
AM25LS23PC	10p	
BAV40	40p	

SAA1272	£3.00	
SAA1276	£3.00	
SAA5000	£1.50	
SAA5000A	£1.50	
SAA5012A	£5.00	
SAA5020	£3.50	
SAA5030	£5.00	
SAA5040	£3.50	
SAA5040A	£4.40	
SAA5050	£3.50	
SAF1032p	£2.50	
SAF1039	£2.00	
SAS560	£2.00	
SAS660	£1.00	
SAS760	£1.00	
SL901B	£5.00	
SL918	£6.20	
TA7122	£1.15	
TAA320A	50p	
TAA470	£1.50	
TAA570	75p	
TAA611B	£1.50	
TAA621	£2.00	
TAA661	£1.75	
TAA641	£1.50	
TA7117	50p	
TA7120P	50p	
TA7315AP	50p	
TA7607AP	40p	
TA7609P	50p	
TBA120A	40p	
TBA120AS	50p	
TBA120SA	40p	
TBA120B	40p	
TBA120SB	40p	
TBA120SQ	£1.00	
TBA120U	75p	
TBA120Q	30p	
TBA120C	40p	
TBA1411	£1.00	
TBA231	75p	
TBA395Q	50p	
TBA396Q	£1.00	
TBA396	75p	
TBA440P	£1.00	
TBA1440C	£1.00	
TBA480Q	£1.00	
TBA520	£2.00	
TBA530	£2.00	
TBA540	£1.00	
TBA550Q	£1.75	
TBA560CQ	£2.00	
TBA570	£1.50	
TBA625	50p	
TBA641	£2.00	
TBA651	£2.00	
TBA673	£1.00	
TBA720A	£1.50	
TBA750Q	£1.50	
TBA780	£1.50	
TBA800	50p	
TBA810AS	60p	
TBA810S	60p	
TBA820	60p	
TBA890	£1.00	
TBA900	£1.50	
TBA920	£1.50	
TBA950	£1.50	
TBA990Q	£1.00	
TMS1000NL	£4.00	
TMS1943 (clockchip)	£1.00	
TMS9980	£4.00	
TMS9901	£1.00	
TMS2716JL	£1.00	
TMS3529	£1.00	
TMS4014	70p	
TX-01	£1.00	
TMS9902	£1.20	
ULN2216	75p	
SN29848	50p	
SN29770BN	£1.00	
SN29771BN	£1.00	
SN29772BN	£1.00	
SN7402N	£1	
SN7472N	£1	
SN74107	£1.00	
SN74167	70p	
SN7472N	20p	
SN75108AN	£1.00	
SN76001	£1.00	
SN76003	£1.00	
SN76013ND	£1.50	
SN76018	£1.00	
SN76008	£1.00	
SN76023N	£1.50	
SN76033	£1.50	
SN76110N	£1	
SN76115AN	50p	
SN76131	50p	
SN76141N	£1.00	
SN76226	£1.00	
SN76227N	60p	
SN76228N	£1.00	
SN76270	£1.00	
SN76532N	50p	
SN76544N	£2.00	
SN76545	£3.50	
SN76546	£1.00	
SN76550	30p	
SN76552	30p	
SN76570	£1.00	
SN76620	50p	
SN76650	50p	
SN76660N	40p	
SN76620AN	50p	
SN76666	£1.00	
SN76705N	£1.00	
SN76707N	75p	
SN76708AN	75p	
SN76720	£1.00	
UA783P3C	40p	
BT100A/02	70p	
BT138/10A	40p	
BT146	30p	
TBA540Q	£1.50	
TCA270	£1.00	
TCA270Q	£1.00	
TCA640	£1.00	
TCA660	£1.00	
TCA270S	£1.00	
TCA270SQ	£1.00	
TCA740	£1.00	
TCA800	£2.00	
TCA830	£1.00	
TCEP100	£2.25	
TCE120CQ	£1.00	
TDA440Q	£1.00	
TDA1003A	£1.00	
TDA1010	£1.00	
TDA1060A	£1.50	
TDA1072	£1	
TDA1150	30p	
TDA1170	£1.00	
TDA1190	£1.00	
TDA1327A	£1.00	
TDA1412	50p	
TDA2003	80p	
TDA2004	£2	
TDA2010	£1.00	
TDA2140	£3.50	
TDA2030	£2.00	
TDA2525	£1.00	
TDA2640	£2.00	
TDA2522	£1.00	
TDA2530	£1.50	
TDA2532	£1.00	
TDA2540	80p	
TDA2541	£1.00	
TDA2571AQ	£2.50	
TDA2575A	£1.00	
TDA2581	£2.50	
TDA2590	£1.00	
TDA2593	£1.00	
TDA2560	50p	
TDA2600	£5.00	
TDA2611	£1.00	
TDA2653	£1.00	
TDA2602	£1.00	
TDA2640	£2.00	
TDA2680	£1.00	
TDA2690	£1.00	
TDA2593	£1.00	
TDA3190	£1.00	
TDA3560	£4.00	
TDA3571Q	£1.50	
TDA9403	£3.00	
TDA3651AQ	£3	
SN74LS 125AN	30p	
SN74LS 248	30p	
SIL4516	50p	
SNI6861NG	50p	
SNI6862AN	£1.00	
SNI6964AN	50p	
SN29764AN	£1.00	
UA721	40p	
UA7300	40p	
RG30G	10p	
MPSA14	10p	
MPSA43	10p	
MJ13005	30p	
MJE51T	25p	
MJE340	28p	
MJE660	25p	
MJE661	25p	
MJE3055	£1.00	
MJE2801	30p	
MJE2955	50p	
MJE13005	30p	
Sanikron Diode	30p	
SKE2G2/04	30p	
	Transistors	
A1222	15p	
A1223	15p	
AC106	15p	
AC121	15p	
AC124	15p	
AC128	15p	
AC137	15p	
AC151	15p	
AC131	15p	
AC138	15p	
AC152	15p	
AC153K	15p	
AC142K	15p	
AC169	15p	
AC176	15p	
AC176K	15p	
AC178K	15p	
AC179	15p	
AC186	15p	
AC187K	15p	
AC188	15p	
AC188K	15p	
ACV21	25p	
AD143	50p	
AD149	50p	
AD161/162	pair 40p	
AF139	25p	
AF181	£1.00	
AF239	25p	
AF367	25p	
ALI02	£1.75	
BC161	30p	
BD507	50p	
BD509	30p	
BD510	30p	
BD517	30p	
BD519	30p	
BD534	30p	
BD535	30p	
BD544D	30p	
BD562	30p	
BD610	40p	
BD646	50p	
BD676A	30p	
BD678	50p	
BD681	25p	
BD807	20p	
BD826	50p	
BD948	30p	
BDX75	20p	
BDX32	£1.25	
BF115	20p	
BF121	20p	
BF127	20p	
BF137	20p	
BF157	20p	
BF160	20p	
BF161	20p	
BF164	60p	
BF179	30p	
BF180	20p	
BF181	20p	
BF182	20p	
BF184	20p	
BF194	10p	
BF195	10p	
BF196	10p	
BF197	12p	
BF198	10p	
BF199	10p	
BF200	10p	
BF222	10p	
BF224	15p	
BF238	15p	
BF240	16p	
BF244	10p	
BF245b	20p	
BF256	10p	
BF257	10p	
BF258	25p	
BF262	15p	
BF263p	15p	
BF264	15p	
BF271	10p	
BF273	10p	
BF274	10p	
BF324	25p	
BF337	50p	
BF355	30p	
BF362	30p	
BF363	15p	
BF367	15p	
BF391	15p	
BF394	15p	
BF419	30p	
BF423	15p	
BF448	30p	
BF450	30p	
BF458	30p	
BF459	30p	
BF468	30p	
BF469	30p	
BF470	30p	
BF480	20p	
BF594	10p	
BF597	10p	
	TV Crystals	
4MHz	£1.00	
4.433-619	£1.00	
6MHz	£1.00	
8.867238	£1.50	
CVC 9 power supply board	£1.50	
CVC 20/2 mains panel	£2.00	
ITT Mains Filter .1/250v/ CVC 20 to 45 chassis 50p		
Pots 10 k with Switch 25p		
Pots 47 k with Switch 25p		
Mullard Surface Wave Filter RW 153P Colour	40p	
Mullard Surface Wave Filter RW 154 Colour		