

FEBRUARY 1985

Australia \$1.80 New Zealand \$2.20, Malaysia \$5.50

£1.10

TELEVISION

SERVICING·PROJECTS·VIDEO·DEVELOPMENTS

★ EXTRA PAGES THIS MONTH ★



Servicing the Panasonic TC2205
Low-noise 11GHz Converter
Workshop Decoder Alignment
Service Briefs • DX-TV
High-power UHF Transmitters
VCR Clinic • TV Fault Finding

MANOR SUPPLIES

MKV PAL COLOUR
TEST GENERATOR FOR TV & VCR.

TEST
DEMONSTRATIONS
AT 172
WEST END LANE



- ★ 40 different patterns and variations.
- ★ Broadcast transmission accuracy (fully interlaced sync pulses with correct picture blanking).
- ★ EBU colour bars, BBC colour bars, whole rasters & split bars (specially useful for VCR service), white, yellow, cyan, green, magenta, red, blue and black.
- ★ Chequerboard.
- ★ Mono outputs with border castellations, cross hatch, grey scale, vertical lines, horizontal lines and dots.
- ★ UHF modulator output plugs straight into receiver aerial socket.
- ★ Additional video output for CCTV & VCR.
- ★ Facilities for sound output.
- ★ Easy to build kit, standard parts. Only 2 adjustments. No special test equipment required.
- ★ Mains operated with stabilised power supply.
- ★ All kits fully guaranteed with back-up service.
- ★ Also available with VHF Modulator.



Price of Kit **£70.00**
De Luxe Case (10"×6"×2¼") **£7.40**
Optional Sound Module (6MHz or 5.5MHz) **£3.90**
Built & Tested in De Luxe Case including Sound Module **£105.00**

SPECIAL TEST
REPORT
'TELEVISION'
DEC. 1982

Post/Packing £2.50
Add VAT 15% TO ALL PRICES

PAL COLOUR BAR GENERATOR (Mk4)

4TH SUCCESSFUL YEAR

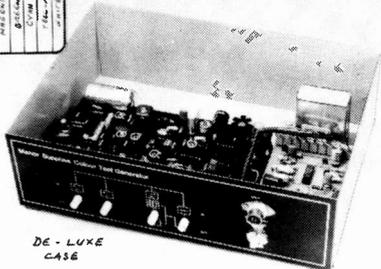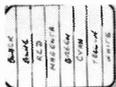

- ★ Output at UHF, applied to receiver aerial socket.
- ★ In addition to colour bars R-Y, B-Y etc.
- ★ Cross-hatch, grey scale, peak white and black level.
- ★ Push button controls, battery or mains operated.

PRICE OF MK 4 COLOUR BAR GENERATOR KIT **£30.00**. DELUXE CASE **£7.40**. BATT HOLDERS **£2.80**. MAINS SUPPLY KIT **£4.20** (Combined P&P **£2.20**).

MK 4 DE LUXE (BATTERY) BUILT & TESTED **£58.00** + **£2.20** P & P.
MK 4 DE LUXE (MAINS) BUILT & TESTED **£68.00** + **£2.20** P & P.
VHF MODULATOR (CH 1 to 4) FOR OVERSEAS **£5.75**.
EASILY ADAPTED FOR VIDEO OUTPUT & C.C.T.V.

TELETEXT EXTERNAL ADAPTOR KIT (Less case)
with cable remote control **£120.00** p.p. **£3.00**

THORN TX10, teletext
Mullard Decoder panel + Interface **£35.00** p.p. **£1.80**
THORN TX10, PHILIPS G11 PRESTEL
Mullard Units VM 6230, 6330 plus Line Coupler & Interface **£60.00**
p.p. **£2.50**

Goods available if in stock immediately over shop counter (Mail order between 3 days and 1 week from receipt of order). ADD VAT 15%

TV SERVICE SPARES

BACKED BY TWENTY YEARS EXPERIENCE & STAFF OF
TECHNICAL EXPERTS

LOPTS, TRIPLERS, PANELS, TUNERS, SELECTORS ETC.

THORN 9000 Fault Finding Guide **£1.00** p.p. 30p.
SPECIAL OFFER NEW VALVES
Branded makes, PCF80, PY88, PFL200, PCL84 FOUR for **£2.00** p.p. 80p.
THORN TX10 Facia Control Panel incl. Infra Red Remote Control receiver **£7.50** p.p. **£1.50**.
THORN TX10 type Remote & Tuning Control Panel **£9.40** p.p. **£1.50**.
THORN TX10 Series Facia Control Panel with 8 position Channel Selector **£5.00** p.p. **£1.50**.
PHILIPS UHF Modulator (Audio & Video Input) **£15.00** p.p. **£1.00**.
SAW FILTER IF AMPLIFIER PLUS TUNER complete and tested for T.V. Sound & Vision. **£28.50** p.p. **£1.20**.
THORN TX9, TX10 Saw Filter IF Panel. **£7.50** p.p. 80p.
PAL DECODER KIT for RGB Monitors **£27.00** p.p. **£1.00**.
TELETEXT DECODERS New & Tested Mullard VM 6101 **£30.00**, Texas XM11 **£40.00** p.p. **£1.60**.
TELETEXT 23 Button De-Luxe Handset with 5 yds Cable. **£6.80** p.p. **£1.20**.
5V Stab. Power Supply. **£3.80** p.p. **£1.20**.
TELETEXT Infra Red Handset (5000 System) **£26.80** p.p. **£1.20**, suit TX9, TX10, etc.
CROSS HATCH UNIT KIT, Aerial Input type, incl. T.V. sync. and UHF Modulator, Battery Operated, also gives Peak White & Black Levels, can be used for any set. **£12.00** p.p. 80p. (Alum. Case **£2.55**, De Luxe Case **£6.80** p.p. **£1.40**.) ADDITIONAL GREY SCALE KIT **£2.90** p.p. 45p.
UHF SIGNAL STRENGTH METER KIT **£20.00** (VHF version **£22.00**). Alum. Case **£2.55**, De Luxe Case **£7.40** p.p. **£1.80**.
CRT TESTER & REACTIVATOR PROJECT KIT For Colour & Mono **£28.00** p.p. **£2.80**.
BUSH Z718 BC6100 series IF Panel **£5.00** p.p. 90p.
BUSH A816 IF Panel (Surplus) **£1.65** p.p. 90p.
DECCA 80 Series IF, Frame, T.B. **£5.00** p.p. **£1.40**.
GEC 2040 Convergence Panels, Decoder Panels, **£2.50** p.p. **£1.80**.
GEC 2040 IF Panels **£2.80** p.p. **£1.60**.
GEC 2110 PANELS Frame **£8.50**, Preset (Touch Tune) Control **£5.00**, Convergence **£5.00** p.p. **£1.80**.
GEC "20AX" Series Switch Mode Power Supply **£5.00** p.p. **£1.80**.
PYE 691-7 CDA Panels. Makers tested stock. **£6.00** p.p. **£1.45**.
THORN TX9 Panels ex factory for small spares. Includes I.Cs & Semiconductors etc. **£5.00** p.p. **£2.00**.
THORN TX9 Panels salvaged ex factory for spares incl. LOPT & Mains Transformers. **£10.00** p.p. **£2.80**.
THORN TX9 Panels ex factory salvaged complete cond. **£20.00** p.p. **£2.80**.
THORN TX10 T.B. Panels salvaged ex factory. **£15.00** p.p. **£3.00**.
THORN TX10 IF/Decoder Panels salvaged ex factory. **£15.00** p.p. **£2.00**.
THORN 3000/3500 Power supply P.C.B. **£3.50** p.p. **£1.00**.
THORN 8000/8500 IF/Decoder Panels salvaged **£3.20** p.p. **£1.80**.
THORN 8000/8500 Frame T.B. Panels salvaged/spares **£2.50** p.p. **£1.40**.
THORN 9000 IF/Decoder Panels Salvaged. **£5.00** p.p. **£1.60**.
THORN 9000 Series. Long panel facia unit incl. 6 Position Channel Selector & Loudspeaker **£6.00** p.p. **£2.00**.
PHILIPS G8/G9 IF/Decoder Panels for small spares incl 1Cs **£2.50** p.p. **£1.60**.
G11 PANELS, Ex Rental SCAN (incl LOPT) **£28.00** p.p. **£2.50**.
G11 PANELS, Power, Frame, IF, Decoder, **£18.00** each. p.p. **£2.00**.
GRUNDIG 8630 Series Varicap Tuners **£5.00** p.p. **£1.00**.
VARICAP. U322, ELC1043/5 **£7.80** p.p. 80p. Makers Varicap Controls PYE CT200 4PSN **£7.50**, BUSH 4PSN **£4.80**, DECCA 4PSN **£5.80**, 6PSN **£6.80** p.p. 80p. etc.
BUSH "TOUCH TUNE" Varicap Control Z179, Z718 types **£3.80** p.p. 95p.
VARICAP UHF-VHF ELC2000S **£9.80**, BUSH **£7.80** p.p. 90p.
VARICAP VHF PHILIPS. **£6.90**. ELC 1042 **£7.80** p.p. 80p.
UHF/625 TUNERS, many different types in stock. DECCA Bradford 5 position, MULLARD 4 position **£2.50**, JAP Rotary **£4.80** p.p. **£1.80**.
TV SOUND IF Panels **£6.80** p.p. **£1.00**.
LOPT TESTER, Service Dept approved **£15.90** p.p. **£1.20**.
LOPTS New and guar. P/P Mono **£1.35**, Colour **£1.50**, Bobbins 80p.

| | | | |
|--|-------|-------------------------------------|--------|
| BUSH 161 to 186 (twin panel) | £5.90 | R.B.M. A823 | £4.90 |
| BUSH, MURPHY 774 series | £8.50 | R.B.M. Z179 | £9.80 |
| BUSH, MURPHY A816 series | £8.50 | R.B.M. T20, T22 | £5.60 |
| FERG., HMV, MARCONI, ULTRA | | R.B.M. T20, T22 Bobbin | £8.80 |
| 1400, 1500, 1590, 1591 | £5.90 | DECCA Bradford (state Mod No) | £8.80 |
| THORN 1600, 1615, 1690, 1691 | £9.15 | DECCA 80, 100 | £8.80 |
| GEC 2000 to 2038 series | £6.80 | GEC 2028, 2040, 2100 | £5.80 |
| GEC series 1 & 2 | £8.00 | GEC 2110 series | £10.60 |
| INDEST 2024EGB | £7.65 | ITT CVC3 5 to 9 CVC20 | £9.80 |
| ITT/KB VC200, 300 | £7.65 | ITT CVC25, CVC30 series | £8.80 |
| MURPHY 1910 to 2414 (twin panel) | £5.90 | PYE 691-697 (state model no.) | £10.00 |
| PHILIPS 170, 210, 300 series | £7.65 | PYE 713, 715 | £6.80 |
| PYE, INVICTA, EKCO, FERR. | | PYE 725 (907) 731 to 741 | £9.20 |
| 368, 169, 569, 769 series | £7.65 | PHILIPS G8 | £8.80 |
| | | PHILIPS G9 | £10.80 |
| | | PHILIPS 570, 571 | £6.80 |
| | | PHILIPS KT3 | £12.50 |
| | | THORN 3000/3500 SCAN, EHT | £6.90 |
| | | THORN 8000/8500/8800 | £12.90 |
| | | THORN 9000 to 9600 | £12.90 |

OTHERS AVAILABLE. PRICES ON REQUEST. ALSO LOPTS.
TRIPLERS Full range available. Mono & Colour.
Special Offer: Thorn 8000 (2 lead) EHT Tray **£2.80** p.p. 80p.
TRANSDUCTORS suitable for G8, A823, Bradford etc. **£1.50** p.p. 60p.
6-3V CRT Boost Transformers for Colour & Mono **£5.40** p.p. **£1.20**.
THORN TX10 focus control **£8.80** p.p. 80p.
THORN 8000 mains input choke **£6.80** p.p. **£1.40**.
CALLERS WELCOME AT SHOP PREMISES
THOUSANDS OF ADDITIONAL ITEMS, ENQUIRIES INVITED
LARGE SELECTION TESTED COLOUR PANELS POPULAR MODELS
TELEVISION MAGAZINE PROJECT PARTS & REPLACEMENTS STILL
AVAILABLE

Telephone 01-794 8751, 794 7346

MANOR SUPPLIES

172 WEST END LANE, LONDON, N.W.6.

NEAR: W. Hampstead Tube Stn. (Jubilee) Buses 28, 159, C11 pass door
W. Hampstead British Rail Stns. (Richmond, Broad St.) (St. Pancras, Bedford)
W. Hampstead (Brit. Rail) access from all over Greater London.

Mail Order: 64 GOLDERS MANOR DRIVE, LONDON N.W.11.

PLEASE ADD VAT 15% TO ALL PRICES



TELEVISION

SUBSCRIPTION SERVICE

A TV licence enables a householder to enjoy viewing without fear of interruption by callers from the BBC detector van. In the same way a subscription to Television enables you to update yourself on the latest developments without fear of interruption because copies have been sold out.


A regular subscription overcomes this problem. You know how annoying it can be when you have a gap in an important series of monthly articles. Why not avoid sell-out disappointment by arranging for Television to be delivered to you direct from the publisher? Just fill in the the order form overleaf and post in the addressed envelope attached. Then leave us to do the rest.

GIFT SUBSCRIPTIONS

A subscription to Television makes an ideal gift for someone in the same line as yourself. All you have to do is complete the appropriate section of the order form and post in the same way. When we receive it, then we take over. We'll even send a card announcing your gift with your own personal message on it.

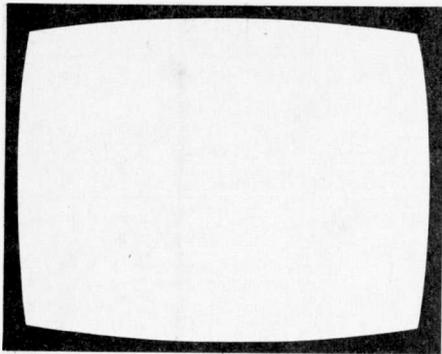TELEVISION
Subscription Service
...we'll keep you posted.





TELEVISION

February
1985

Vol. 35, No. 4
Issue 412

COPYRIGHT

© IPC Magazines Limited, 1985. Copyright in all drawings, photographs and articles published in *Television* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Television* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

CORRESPONDENCE

All correspondence regarding advertisements should be addressed to the Advertisement manager, "Television", King's Reach Tower, Stamford Street, London SE1 9LS. Editorial correspondence should be addressed to "Television", IPC Magazines Ltd., King's Reach Tower, Stamford Street, London SE1 9LS.

SUBSCRIPTIONS

An annual subscription costs £11 in the UK, £12 overseas (by surface mail). Send orders with payment to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex, RH16 3DH.

BINDERS AND INDEXES

Binders (£4.50) and Indexes (45p) can be supplied by the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. Prices include postage and VAT. In the case of overseas orders, add 60p.

BACK NUMBERS

Some back issues are available from the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF at £1.20p inclusive of postage and packing.

QUERIES

We regret that we cannot answer technical queries over the telephone nor supply service sheets. We will endeavour to assist readers who have queries relating to articles published in *Television*, but we cannot offer advice on modifications to our published designs nor comment on alternative ways of using them. All correspondents expecting a reply should enclose a stamped addressed envelope. Requests for advice on dealing with servicing problems should be directed to our Queries Service. For details see our regular feature "Service Bureau". Send to the address given above (see "correspondence").

this month

- 185 Leader**
- 186 Vintage TV: The Mighty RGDs** *Chas E. Miller*
For a brief period after the war RGD, then an independent company, produced high-class console TV sets. A look at the circuitry and the firm's history
- 188 TVT Transistor Equivalents Books** *Eugene Trundle*
Finding equivalents for the vast range of transistors used in consumer electronics equipment can be a problem. ET recommends the books he uses.
- 191 Battle with a Thorn 9000** *J. W. Cheshire*
A particularly difficult case of Syclops circuit failure in the 9000.
- 192 Video Servicing** *Mike Phelan*
Colour signal processing in a camera using the colour separation by phase system.
- 193 Next Month in Television**
- 194 Hints on the ITT CVC5-CVC9 Series** *Chris Avis*
These sets seem to be the great survivors from the era of hybrid CTVs. Hints based on experience gained renovating them.
- 196 Servicing the Panasonic TC2205** *David Botto*
Large numbers of these sets (U2 chassis) were produced and sold. A panel by panel guide to servicing.
- 200 Low-noise 11GHz Converter** *Hugh Cocks*
This simple downconverter, using a Mitsubishi oscillator/mixer module, gives good results for TV reception in the 11GHz band. Details of the unit, the feedhorn required and how to go about getting signals.
- 204 Workshop Decoder Alignment System** *Denis G. Mott*
Use of the output from a colour pattern generator with an oscilloscope to give a vector display gives a simple and accurate method of decoder alignment.
- 206 Another Smash Hit** *Les Lawry-Johns*
More window trouble – the small one this time. Then troubles with customers who know best.
- 207 Letters**
- 210 Tuning in the Philips TRD IV System** *Michael Pitt*
This sophisticated remote control/tuning system can present problems if you don't know exactly how to set it up.
- 211 VCR Clinic**
Reports from Derek Snelling, Philip Blundell, Eng. Tech., Paul Hardy, Mike Phelan and Steve Beeching, T. Eng.
- 213 Teletopics**
- 216 Service Briefs**
- 218 High-power UHF Transmitters** *Nigel Cawthorne, MIEE, C.Eng.*
The techniques used to generate 1-55kW at u.h.f.
- 220 TV Fault Finding**
Reports from Steve Beeching, T. Eng., Chris Avis, John Coombes, Philip Blundell, Eng. Tech., Paul Hardy and Mick Dutton.
- 222 Long-distance Television** *Roger Bunney*
- 225 Service Bureau**
- 227 Test Case 266**

OUR NEXT ISSUE DATED MARCH WILL
BE PUBLISHED ON FEBRUARY 20

P. V. TUBES

HAVE MOVED

104 ABBEY STREET, ACCRINGTON, LANCBS BB5 1EE.

Just phone
your order
through, we
do the rest.



Buy with

Telephone: Accrington (0254) 36521
Accrington (0254) 32611
Telex: 635562 Griffin G (For P.V.)

SUPPLIERS
OF TELEVISION COMPONENTS

TRADE COUNTER OPEN MON-FRI 9 a.m.-5 p.m. SAT 9.30 a.m.-5 p.m. TRADE COUNTER CLOSED WEDNESDAY p.m.

| VARICAP TUNERS | SWITCHES & ACCESS. | DO YOU KNOW WE'VE GOT LOTS OF NEW THINGS! | PHILIPS KT3 SPECIFICS | SPECIFIC COMPONENTS |
|---|---|--|--|---|
| ELC1043-05 8.40 ELC1043-06 8.40 ELC2003 16.50 Philips G8/G9 10.50 Philips G11 (U321) 8.50 U322 7.20 U341 9.50 Rank T20 13.00 | On/off gen. purpose 4A 75 G8 on/off 1.38 G11 on/off 1.58 G11 on/off remote 1.58 Gen. purpose rotary 66 Thom T9 9/10 1.06 GEC 2040 98 Thom 1591 push on/off 2.90 Rank tuner buttons 1 1/2" x 1/2", 2" x 1/2", 2" x 3/8" Rank drive cams 35 GEC 2110 tuner neons 15 Thom 3500 A1 beam 20 GEC 2110 A1 cont. R/B/G 70 ITT CVCS on/off 1.24 ITT mains switch + solenoid 4.50 Rank mains switch + solenoid 4.50 | Decca speaker 16R 4.50 8R 3.75 B+K tube bases Dynascan No. 3 9.50 No. 13 11.11 No. 6 11.08 No. 14 16.78 No. 8 10.08 No. 23 13.86 L5 7" x 3 3/8" speaker 4.25 C12 computer cass. 10.60 C18 computer cass. 33 5 1/4" floppy disc s/s s/d 1.61 15R fused res. G9 5.50 G11 line in coil 2.95 G11 pot G2 R.G.B. 5.30 G11 line scan panel 54.00 G11 power panel 37.50 G11 timebase panel 37.50 G11 bridge trans. 97 G11 EW correc. coil 1.95 G11 final anode lead 1.50 G11 focus unit 5.80 G11 39R 3W resistor 60 G11 RGB 10G diodes 50 Labgear CM7091 UHF/VHF colour bar gen. 116.00 Televista up converta 37.20 | KT3 posistor 1.50 Mains electrolytic 225/25 380V 2.50 Selector unit Mod. 933 13.42 On/off switch Mod. 933 3.20 Tripler 10.65 Luminance chroma panel 24.00 2003 IF module 14.95 U321 IF module 13.50 R.G.B. tube 10.30 Sound panel 8.50 Power panel 10.60 Mains input panel 14.30 Line sync panel 10.20 Mark II chroma panel 16.50 Sound module 8.50 LOPT 9.70 Focus unit 3.50 | Philips G8 knobs sm/g 50 90° transductor 2.60 Thom 1591 speakers sm 4.10 lg 4.50 Thom 1500 controls 59 390K frame 470K line contrast 1k5 each Focus control Thom/GEC 1.83 Thom 9000 focus unit 5.95 Thom 8500 focus unit 4.75 Thom Tx10 focus cont. 9.00 Decca bridge trans. 1.97 Decca 30 width cont. 50 Decca 2M2 HT cont. 25 Rank T20 focus cont. 2.20 Pye 731 HF choke 6.50 Delay lines DL20, DL60, DL700, DL50 7.20 CRT tube base 2.70 EHT final anode cap 53 Euro supply 1234 5.80 A1 gun switches 70 On/off switch 2.60 Selector unit 1002 (late) 9.90 Hand set 1201 14.50 Hand set 1234 14.50 Diode ZTX 33B 90 DL 20 delay line 2.20 |
| PUSH BUTTON ASS. Decca 4 way 6.88 6 way 7.50 GEC 2110 6 way 7.98 GEC Slim 6 way 6.50 GEC/ITT/PYE 7 way 14.50 Pye 4 way (713/15) 9.00 Pye 6 way (207/715) 16.00 Pye 697 repair kit 9.00 Pye 725-735 11.00 Pye 725-735 with tuning head 14.60 Philips G8 (early) 15.50 Philips G8 (late) 13.90 Rank A823 10.75 Rank T20A 9.75 Hitachi 4 way 10.75 Philips G11 unit 23.00 Philips KT3 14.50 Philips KT30 10.30 ITT CVC 8/9 (mod) 12.00 ITT 6 way with VCR 8.90 Thom 9000 switchback 5.30 | EAGLE MULTIMETERS KEW 7N 6.75 KEW 14 9.00 KEW 20 14.50 EM5 11.95 EM20A 15.95 EM10 13.95 MM50 31.25 Bench MM100 44.50 Meters MMT20 21.50 MM150 75.00 T1206 intercom 8.50 MMC100 21.95 Case TS350 21.95 | SUNDRY EQUIPMENT Test Lead Set 4.20 Degaussing Coil Stick 17.00 Signal Injector 4.00 Elect. Circuit Tester 1.50 5A Choc Bloc (12) 40 Fuse Wire 5A, 15A, 30A 05 4-way 13A Mains Conn. 5.00 Safe Block (mains) 7.00 13A Plug Top (box 10) 4.80 Portable Oscilloscope 155.00 Probes (x10) 10.90 Probes (x1) 10.90 CRT Tester/Rejuv. 172.00 KHP30 Meas. Probe 30kV 32.00 Bell Wire (100m) 5.00 Mains Cable (circular 100m) (2 core) 10.75 (3 core) 13.25 Factory recon. Avo meters 119.00 Avo Batteries 2.20 Vero Board 2.59 Isolating trans. 500vA 240V 40.00 Solder 500g 7.00 D.I.Y. Solder 45 Solder Sucker 6.50 Nozzles 81 Dynascan CRT Res. 455.00 | K30 SPECIFICS K30 LOPT 17.50 K30 focus unit 2.90 K30 EHT lead 5.90 Selector unit 1002 (early) 11.20 TMS 1000 panel 1234 11.00 Euro decoder panel 1234 46.00 Power supply 1234 23.50 A1 gun switches 70 On/off switch 2.60 Selector unit 1002 (late) 9.90 Hand set 1201 14.50 Hand set 1234 14.50 Diode ZTX 33B 90 DL 20 delay line 2.20 | Phono Plugs 12 DIN Plugs 3 pin 22 4 pin 22p 180° 5 pin 20p 5 pin 20 Car Aerial Plug 18 2.5mm Jack Plug 14 3.5mm Jack Plug 14 Stand Jack Plug 20 Stereo Jack Plug 36 Coax Plugs each 1.80 ten 4.80 PL259 1.80 Reducers for PL259 16 3 Line Connectors 16 |
| FREEZE AIDS SERVISOL Freeze-It 1.02 SUPER SERVISOL 82 SERVISOL Foam Cleanser 89 SERVISOL Plastics Seal 1.00 SERVISOL Silicone Grease 1.08 SERVISOL Tubes Silicone Grease 1.64 SERVISOL Aero Klene 84 SERVISOL Aero Duster 1.10 SERVISOL Excal Polish 88 SERVISOL Video Head Cleanser 82 Super 40 1.50 Fire Extinguisher 640G 2.50 Heat Sink Compound 25G 1.08 Silicone Rubber Tube 110G 2.98 Solda Mop standard reel 74 | ANTEX SOLDERING EQUIPMENT C15W Iron 240V 4.41 C240 Element 1.80 Bits 102 90 106 90 820 90 821 90 CS17W Iron 240V 4.41 CS240 Element 2.25 Bits 1100 90 1101 90 1106 90 XS25W Iron 240V 4.59 XS240 Element 2.25 Bits 50 90 51 90 Temp. Controlled 30W Iron CSTC 10.50 40W Iron XSTC 10.50 Unit for above TCSU1 32.64 Stand 2.00 MLXS Auto Repair Kit 6.30 | DATA BOOKS (Zero VAT) TVT 80 A-Z only 3.75 TVT 80 2N-2S only 4.00 TVT 80/80 A-Z/2N-2S (pair) 7.50 LIN IC Books (data only not equiv.) LIN1 5.95 LIN2 5.95 2M Fly Lead 70 4M Fly Lead 1.20 10M Fly Lead 1.90 Figure 8 Mains Lead 62 Computer to TV 97 7 pin din to 5 pin din 98 5 pin din to 5 pin din 98 | PLUGS Phono Plugs 12 DIN Plugs 3 pin 22 4 pin 22p 180° 5 pin 20p 5 pin 20 Car Aerial Plug 18 2.5mm Jack Plug 14 3.5mm Jack Plug 14 Stand Jack Plug 20 Stereo Jack Plug 36 Coax Plugs each 1.80 ten 4.80 PL259 1.80 Reducers for PL259 16 3 Line Connectors 16 | |
| ELECTROLUBE PRODUCTS Electrolube Adhesive 62 Electro-Mech lubricant 1.49 Elect. cleaning solvent 1.52 Freezer 1.49 Foam cleanser 1.12 Heat transfer compound 1.14 Silicone compound 1.94 Special contact fluid (Snorkell) 3.20 Permagard 1.52 Elec. mech. lubricant pen 74 | WELLER Heat gun 12.00 Heat gun tips (pair) 57 3/16" Iron tips 25W (MTS) 57 | LABGEAR CM7261 Power Unit 12V 11.24 CM7262 Reg. Power Unit 12V 12.25 CM7060 MHA 10db 12V W/B 9.86 CM7065 VHF/UHF MHA W/B 12V 14.34 CM7067 UHF 12V MHA (Specify A-B or C/D) 10.72 CM7068 UHF 12V MHA High Gain (Specify A-B or C/D) 15.95 CM7053 Behind Set UHF Amp. (Mains) 13.01 CM7054 Behind Set UHF Amp. (Battery e.g. Caravans) 10.42 CM7043 Second Set Amp. UHF 12.12 CM7093 Behind Set UHF Amp. 3 Sets 15.27 CM7063 Dist. Amp. VHF/UHF 17db/output 12V 22.17 CM7108 VHF/UHF 8+1 Dist. Amp. 43.26 CM9700 27mhz CB Suppress. 4.05 CM6011 Outdoor Splitter (2 way) W/B 7.63 CM9003 Flush Single Outlet 1.47 CM9010 Flush Twin Outlet 1.95 CM9034 UHF Group Filters with DC Through Pass (state A/B/C/D) 7.69 CM7042 6 Way Passive Splitter 10.97 CM7042 TV Games Combin. 2.95 CM9009 Flush TV/FM Outlet 3.05 CM7091 Col. Bar Gen. 121.80 | OFFICIAL ORDERS ACCEPTED FROM SCHOOLS, LOCAL AUTHORITIES ETC. | P.V. MICROCOMPUTER CENTRE Why not pay us a visit and see our range of Micros, Software Books and Peripherals. Please ring for prices. Spectrum 48K Vic 20 Oric Commodore 64 We are also authorised dealers for the BBC Micro and accessories. |
| VIDEO Video care kits 3.50 VHS E30 video tape 3.06 VHS E60 video tape 4.00 Sootch E120 video tape 5.00 E180 video tape 4.50 Beta L500 video tape 4.90 Beta L750 video tape 5.80 Philips VCC 240 6.20 Philips VCC 360 8.30 Philips VCC 480 10.21 Philips LVC 1700 15.10 | VIDEO HEADS 3HSS VHS 32.50 4HSS VHS 32.80 PS3B Beta/Sony 42.00 | WE HAVE A FULL RANGE OF AERIALS AND ACCESSORIES FROM TRADE COUNTER AERIAL EQUIPMENT Outdoor Splitter 5.50 Plastic Tape 50 F.M. Plugs 25 Set Top Aerial 2.30 Loop Aerial 1.00 Mast Amp/Power Unit WB 18.00 Aerial Isolator Kit 2.08 Attenuator 6dB, 12dB, 18dB 1.80 27MHz Filter 50dB 2.10 Cable Clips 7mm per 100 1.18 Outlet Outlets 80 Surface Splitter 1.70 A Splitter 1.70 100M Coax 15.00 per 10 1.80 J Bolts 30 1" U Bolts 25 | SHEILA'S SURPRISES SHARP VIDEO HEADS £55 VC2300 VC6300 VC7300/7700/7750 VC8300 VC220/381/383/388/9100/9200/9500 VC3300/9700 SANYO VIDEO HEADS £45 VTC 9300/9500 VTC 5300/5000 VTC 5350 VTC 5500 VTC 9350 REMOTE CONTROL HAND UNITS Grundig Telepilot 200/300 18.87 Grundig Telepilot 12/16 13.87 Philips G11 Teletext 23.80 Philips G11 non-Teletext 22.00 Decca 100 23.80 Philips KT2/KT3 13.87 JVC/Ferguson TX 10 16.87 TELEPHONE JACK SOCKETS 5.00 Complete with details connecting diagram. We also have a full range of telephone fixing accessories. Please ring for prices. PLEASE ORDER FROM LATEST COPY OF MAG. TO AVOID PRICE INCREASES | |
| AUDIO HEADS AND MOTORS Mono record/playback 4.32 Stereo playback 4.79 Stereo record/playback 4.99 Stereo record/playback (Dolby) 6.90 Mono/stereo erase 2.25 Electronic/rotation clockwise motors 6V MD6515 4.95 9V MD9516 4.95 12V MD12517 4.95 | STATIONERY (Zero VAT) Service Call Pad (100) 1.20 Repair Ticket (100) 3.90 Job Card (100) 2.50 Rental Payment Card (50) 3.50 Rental Agreements (100) 3.50 H.P. Agreements (100) 3.50 Maintenance Agreement (100) 3.50 | ANTIFERRENCE SB11 Splitter 1.91 COB11 Outlet 80 CS200 Combiner/Splitter 3.03 CS1000 Combiner/Splitter 6.15 PU1240 Power Unit 11.00 UP1300 MHA 8.25 X52U Xtboost 11.63 4 way VHF/UHF Amp 33.75 6 way VHF/UHF Amp 42.00 XG8 High Gain Aerial A-B-CD-WB 16.00 | | |

P. V. TUBES

104 ABBEY STREET, ACCRINGTON

TEL: 0254
36521/32611

T.T.L. 74LS SERIES

| | | | | | | | | | |
|--------|----|---------|------|---------|------|---------|------|---------|------|
| 74LS00 | 58 | 74LS37 | 35 | 74LS92 | 65 | 74LS160 | 90 | 74LS245 | 2.30 |
| 74LS02 | 58 | 74LS38 | 35 | 74LS93 | 60 | 74LS161 | 85 | 74LS251 | 65 |
| 74LS03 | 58 | 74LS40 | 35 | 74LS94 | 80 | 74LS162 | 4.04 | 74LS253 | 95 |
| 74LS04 | 58 | 74LS42 | 80 | 74LS109 | 58 | 74LS163 | 85 | 74LS257 | 1.20 |
| 74LS05 | 58 | 74LS47 | 85 | 74LS112 | 50 | 74LS164 | 85 | 74LS258 | 95 |
| 74LS08 | 58 | 74LS48 | 83 | 74LS113 | 44 | 74LS165 | 1.50 | 74LS259 | 1.70 |
| 74LS09 | 58 | 74LS49 | 83 | 74LS114 | 70 | 74LS173 | 1.32 | 74LS273 | 1.90 |
| 74LS10 | 58 | 74LS51 | 33 | 74LS123 | 80 | 74LS174 | 85 | 74LS283 | 1.30 |
| 74LS11 | 58 | 74LS54 | 43 | 74LS125 | 85 | 74LS175 | 85 | 74LS293 | 1.20 |
| 74LS13 | 37 | 74LS55 | 60 | 74LS126 | 60 | 74LS191 | 1.02 | 74LS352 | 1.40 |
| 74LS14 | 46 | 74LS73 | 60 | 74LS132 | 63 | 74LS192 | 1.30 | 74LS353 | 1.40 |
| 74LS15 | 33 | 74LS74 | 65 | 74LS138 | 63 | 74LS193 | 1.30 | 74LS365 | 75 |
| 74LS20 | 35 | 74LS75 | 65 | 74LS139 | 65 | 74LS194 | 75 | 74LS366 | 82 |
| 74LS21 | 35 | 74LS76 | 65 | 74LS151 | 85 | 74LS197 | 95 | 74LS367 | 1.65 |
| 74LS22 | 44 | 74LS78 | 65 | 74LS153 | 85 | 74LS240 | 2.20 | 74LS368 | 65 |
| 74LS26 | 44 | 74LS83A | 89 | 74LS155 | 65 | 74LS241 | 2.20 | 74LS373 | 1.40 |
| 74LS27 | 35 | 74LS86 | 39 | 74LS156 | 1.02 | 74LS242 | 2.20 | 74LS374 | 1.55 |
| 74LS30 | 35 | 74LS85 | 98 | 74LS157 | 78 | 74LS243 | 2.20 | 74LS393 | 1.20 |
| 74LS32 | 90 | 74LS90 | 1.22 | 74LS158 | 65 | 74LS244 | 2.20 | 74LS670 | 1.78 |

VOLTAGE REG.

| | |
|-------|----|
| 7805 | 78 |
| 7806 | 78 |
| 7808 | 78 |
| 7812 | 78 |
| 7815 | 78 |
| 7818 | 78 |
| 7824 | 78 |
| 78L05 | 68 |
| 78L08 | 68 |
| 78L12 | 68 |
| 78L16 | 68 |
| 78L24 | 68 |
| 7905 | 98 |
| 7906 | 98 |
| 7908 | 98 |
| 7912 | 98 |
| 7915 | 98 |
| 7918 | 98 |
| 7924 | 98 |
| 79L05 | 72 |
| 79L12 | 72 |
| 79L15 | 72 |
| 79L24 | 72 |

MAINS DROPPERS

| | |
|--------------------------------|------|
| DECCA 20 | 2.48 |
| DECCA 27R/47R | 1.40 |
| DECCA 56R/68R | 1.40 |
| R.B.M. A823 56R/68R | 94 |
| R.B.M. 161 | 82 |
| GEC 2000/2018 | 70 |
| GEC 27840 | 64 |
| PYE 713/15 3R5/15/45R | 1.84 |
| PYE 725/31 3R0/56R/27R | 1.04 |
| PYE 725 56R/27R | 1.75 |
| PHILIPS 210/5050 30R/125R/2K85 | 93 |
| PHILIPS 210/5051 -118R/148R | 50 |
| PHILIPS G8/5083 2R2/68R | 95 |
| THORN 1400 | 1.20 |
| THORN 1500 | 1.38 |
| THORN 1600 | 1.77 |
| THORN 3500 | 1.24 |
| THORN 8000 | 1.36 |
| THORN 8500 | 1.30 |
| THORN 9800 | 1.30 |
| DECCA 3R9 Modulohm | 60 |

NEW VALVES

| | | | | | | | |
|-------|------|--------|-------|--------|------|----------|------|
| 30FL2 | 1.70 | EF183 | 99 | PCF800 | 1.38 | PL508 | 2.90 |
| DY802 | 96 | EF184 | 1.09 | PCF801 | 1.13 | PL509/19 | |
| DY867 | 66 | EH90 | 1.02 | PCF802 | 1.12 | | 5.30 |
| ECC81 | 1.08 | EL34 | 3.50 | PCF805 | 1.80 | PY88 | 81 |
| ECC82 | 98 | EL84 | 1.05 | PCF806 | 1.30 | PY500A | 2.30 |
| ECC83 | 1.07 | EY867 | 68 | PCF808 | 1.63 | PY800/1 | 69 |
| ECC84 | 80 | EY500A | 1.50 | PCH200 | 1.45 | UCH81 | 2.25 |
| ECC85 | 98 | EZ80/1 | 56 | PCL82 | 1.20 | UCL83 | 1.85 |
| ECC88 | 1.35 | GY501 | 1.45 | PCL84 | 1.20 | UY85 | 1.32 |
| ECF80 | 80 | GZ34 | 3.50 | PCL86 | 92 | PL802T | 4.00 |
| ECF82 | 88 | KT66 | 8.50 | PCL805 | 1.09 | 40K26 | 5.30 |
| ECH81 | 1.60 | KT88 | 12.00 | PD500 | 2.93 | 21L8L | 3.00 |
| ECH84 | 1.66 | PC32 | 3.00 | PFL200 | 1.86 | 17DW4A | 1.60 |
| ECL80 | 84 | PC37 | 1.65 | PL36 | 1.87 | 3AT2B | 5.00 |
| ECL82 | 1.30 | PC85 | 85 | PL81 | 1.94 | 12BY7A | 3.75 |
| ECL86 | 1.99 | PC805 | 1.40 | PL83 | 1.43 | 12HG7 | 3.20 |
| EF80 | 95 | PCF80 | 1.00 | PL84 | 84 | | |
| EF86 | 1.96 | PCF200 | 1.35 | PL504 | 1.65 | | |

THER-MISTORS

| | |
|----------|------|
| VA1104 | 75 |
| VA1040 | 75 |
| VA8650 | 55 |
| VA1039 | 35 |
| GEC Dual | |
| Pecistor | 1.68 |
| GEC Dual | |
| 2040 | |
| (CK1) | 1.98 |

'4000 B' SERIES CMOS

| | | | | | | | | | |
|-------|----|--------|------|-------|------|-------|------|-------|------|
| 4001B | 21 | 4032B | 1.04 | 4072B | 22 | 4511B | 76 | 4539B | 77 |
| 4002B | 21 | 4035B | 80 | 4073B | 22 | 4513B | 1.68 | 4543B | 96 |
| 4008B | 72 | 4038B | 99 | 4075B | 22 | 4516B | 1.88 | 4551B | 96 |
| 4011B | 21 | 4040B | 72 | 4076B | 80 | 4518B | 76 | 4556B | 48 |
| 4012B | 21 | 4042B | 58 | 4077B | 22 | 4519B | 64 | 4560B | 1.76 |
| 4013B | 30 | 4043B | 71 | 4078B | 22 | 4520B | 76 | 4561B | 74 |
| 4014B | 74 | 4044B | 71 | 4081B | 22 | 4521B | 1.68 | 4566B | 1.20 |
| 4015B | 76 | 4046B | 96 | 4093B | 43 | 4522B | 88 | 4580B | 3.60 |
| 4016B | 31 | 4047B | 70 | 4094B | 1.56 | 4526B | 88 | 4581B | 1.84 |
| 4017B | 66 | 4049UB | 32 | 4099B | 1.20 | 4527B | 1.20 | 4582B | 80 |
| 4018B | 72 | 4050B | 32 | 4160B | 72 | 4528B | 88 | 4583B | 1.00 |
| 4020B | 76 | 4051B | 72 | 4161B | 72 | 4529B | 1.04 | 4584B | 40 |
| 4021B | 70 | 4052B | 72 | 4162B | 72 | 4530B | 62 | 4585B | 88 |
| 4022B | 70 | 4053B | 72 | 4163B | 72 | 4531B | 72 | 4597B | 1.84 |
| 4023B | 21 | 4060B | 96 | 4502B | 72 | 4532B | 1.00 | 4598B | 2.40 |
| 4024B | 50 | 4066B | 43 | 4505B | 1.88 | 4536B | 2.64 | 4599B | 2.00 |
| 4025B | 21 | 4068B | 22 | 4510B | 76 | 4538B | 1.04 | | |

I.C. SOCKETS

| | |
|--------|----|
| 8 way | 22 |
| 14 way | 29 |
| 16 way | 32 |
| 18 way | 32 |
| 20 way | 32 |
| 22 way | 32 |
| 24 way | 34 |
| 38 way | 45 |
| 40 way | 84 |

CRYSTALS & FILTERS

| | |
|-----------|------|
| 6Mhz | 74 |
| 5.5Mhz | 74 |
| 4.3Mhz | 1.30 |
| 8.8Mhz | 1.30 |
| 9.94Mhz | 6.00 |
| 10.692Mhz | 6.00 |

MULTITURN POTS

| | |
|-------------|----|
| 100K | 55 |
| GEC TCE | 55 |
| PHILIPS G8 | |
| DECCA, RANK | 55 |



THERMAL CUT OUT

| | |
|---------------------|------|
| THORN 3000 2A Metal | 1.60 |
| GEC 2040 Metal | 2.50 |
| THORN 8000 Plastic | 2.35 |

L.E.D.'s

| | |
|---------------------------|----|
| 5mm Red, Green, Yellow | 14 |
| T1 3/4 Amber | 22 |
| T1 3mm Red, Green, Yellow | 14 |
| Flashing Red CQX21 | 62 |
| CQX22 | 66 |
| 3 Colour VJ18P | 76 |
| Panel Clips 3mm | 4 |
| 5mm | 4 |

DISC CERAMIC CAPS

| | |
|----------------------------|-----|
| 8kV (12kV) | |
| 39pF, 200pF | 40p |
| 150pF, 220pF, 180pF, 250pF | |

POLYESTER CAPS

| | |
|-------------|-----|
| 250V 0.01mF | 12p |
| 0.1mF | |
| 0.22mF | |
| 400V 0.01mF | 12p |
| 0.1mF | |
| 0.22mF | |

TANTALUM CAPACITORS

| | | |
|------|--------|------|
| 6.3V | 47mF | 42 |
| | 100mF | 90 |
| 16V | 10mF | 28 |
| | 22mF | 22 |
| | 47mF | 1.03 |
| 25V | 22mF | 46 |
| 35V | 0.1mF | 13 |
| | 0.22mF | 13 |
| | 0.47mF | 13 |
| | 1mF | 17 |
| | 2.2mF | 13 |
| | 4.7mF | 26 |
| | 10mF | 57 |

CONVERGENCE POTS

| | |
|-----------------------|----|
| 3W/5R-6R8-10R-15R-20R | |
| 50R-100R-200R-500R | 60 |

METRIC CONVERGENCE POTS

| | |
|--------------------|----|
| PHILIPS G8 | |
| 5R-10R-15R-20R-50R | 60 |

LINE OUTPUT TRANS.

| | |
|----------------------|--------|
| R.B.M. T20A | 13.95 |
| R.B.M. A774 Mono | 11.74 |
| R.B.M. Z179 | 15.00 |
| R.B.M. Z718 22" | 19.50 |
| PHILIPS 320 | 8.70 |
| PHILIPS 210/300 Mono | 10.00 |
| PHILIPS G8 | 8.75 |
| PHILIPS G9 | 7.75 |
| PHILIPS G11 | 13.50 |
| PYE 697 (Printed) | 14.50 |
| PYE 713/731 | 10.00 |
| PYE 725 90" | 10.50 |
| PYE 169 | 10.00 |
| DECCA 80/100 | 8.58 |
| DECCA 1700 | 9.00 |
| DECCA 1730 | 8.58 |
| DECCA 2230 | 8.58 |
| GEC 2110 | 16.75 |
| GEC 2040 | 9.50 |
| ITT CVC 1-9 | 10.85 |
| ITT CVC 25/30/32 | 8.65 |
| ITT CVC 20 | 8.60 |
| THORN 3000 EHT | 9.95 |
| THORN 3000 SCAN | 7.95 |
| THORN 8000 | 11.33 |
| THORN 8500 | 11.33 |
| THORN 9000 | 10.65 |
| THORN 3000/3500 | |
| Mains | 10.00 |
| THORN 1591 | 8.68 |
| THORN 1691 | 9.68 |
| THORN TX10 | 12.50 |
| THORN 1615 | 9.75 |
| PHILIPS KT3 | 9.70 |
| RANK BUSHRANGER | £10.00 |
| PYE 741 | 8.20 |
| B+O (2000, 3000) | 12.70 |
| B+O (3000 EHT) | 18.90 |

RECTIFIER TRAYS

| | |
|-----------------------------------|-------|
| THORN 950 Mk II | 4.25 |
| THORN 1400 3 Stick | 5.20 |
| THORN 1500 3 Stick | 5.20 |
| THORN 1500 5 Stick | 5.29 |
| THORN 1600 | 4.95 |
| THORN 3000/3500 | 7.98 |
| THORN 8000 | 5.28 |
| THORN 8500/8900 | 7.15 |
| THORN 9000 | 7.93 |
| DECCA 1730/1830 | 4.48 |
| DECCA 30 | 6.76 |
| DECCA 80 | 6.60 |
| DECCA 100 | 7.50 |
| UNIVERSAL ITT or REMO | |
| GEC 2100 | 7.40 |
| GEC 2200 (20AX) | 6.50 |
| GEC 2040/2028 | 6.60 |
| GEC 2110 Pre Jan '77 | 7.00 |
| GEC 2110 Post Jan '77 | 7.00 |
| PHILIPS G8 Short Focus Lead | 6.75 |
| PHILIPS G8 Long Focus 550 | 6.75 |
| PHILIPS G9 | 6.37 |
| Pye/Philips K3 Tripler | 10.65 |
| PYE 691/3 | 6.58 |
| PYE 713/4 Lead | 8.79 |
| PYE 713 Doubler 5 Lead | 8.79 |
| PYE 731/725 | 7.60 |
| R.B.M. A823 (plug in) AV | 7.60 |
| KORTING (similar to Siemens TVK1) | |
| ITT KB CVC5/9 | 6.90 |
| ITT KB CVC20/25/30 (Mullard) | 5.95 |
| RR1 T20 | 6.80 |

REPLACEMENT ELECTROLYTICS

| | |
|---------------------------------------|------|
| PYE 169 (200/200/100/32) | 3.40 |
| PHILIPS 320 (400/400/200V) | 2.74 |
| DECCA 30 (400/400/350V) | 3.40 |
| DECCA 80 (400/350V) | 3.97 |
| DECCA 100 (800/250V) | |
| DECCA 1700 (200/200/400/350V) | 4.83 |
| PHILIPS G8 (600/300V) | 2.30 |
| PHILIPS G9 (600/300V) | 2.21 |
| PHILIPS G11 (470/250V) | 2.90 |
| PYE 691/7 (200/300/350V) | 2.70 |
| PYE 731 (600/300V) | 2.31 |
| RBM A823 (2500/2500/30V) | 1.66 |
| RBM A823 (600/300V) | 2.83 |
| RBM Z146 (300/300/350V) | 3.55 |
| RR1 T20A (220/400V) | 2.00 |
| ITT CVC5/9 (200/200/75/25) | 2.98 |
| ITT CVC 20 (220/400V) | 2.00 |
| PHILIPS G8 Short Focus Lead | 2.94 |
| PHILIPS G8 Long Focus 550 | 1.19 |
| GEC 2040 (1000/2000/35V) | 4.10 |
| GEC 2040 (300/300/150/100/50) | |
| THORN 3500 (400/400V) | 1.30 |
| THORN 950 (100/300/100/16/275V) | 1.83 |
| THORN 1400 (150/100/100/100/150/320V) | |
| THORN 1500 (150/150/100/300V) | 2.20 |
| THORN 1500 (12/300V) | 31 |
| THORN 3500 (175/100/100/400/350V) | 2.78 |
| THORN 3500 (1000/63V) | 86 |
| THORN 3500 (1000/70V) | 86 |
| THORN 8000/8500 (2500/2500/63V) | 3.38 |
| THORN 8000/8500 (700/250V) | 2.31 |
| THORN 8000/8500 (400/350V) | 2.56 |
| THORN 9000 (400/400V) | 3.28 |
| GEC (200/200/150/50) | 2.64 |
| PHILIPS 69 2200/63V | 1.25 |
| | |

P. V. TUBES

PLEASE NOTE OUR NEW ADDRESS - COME AND SEE US
104 ABBEY STREET, ACCRINGTON, LANCS BB5 1EE.

Tel: 0254 36521/32611 Telex: 635562 Griffin G (For P.V.)

HOW TO ORDER

ADD 75p per order P+P (U.K.). Heavier parcels e.g. cable, service aids, degaus. coils please allow £1.30 P+P (U.K.). Export orders charged at cost. First Class Mail is used whenever possible. Add 15% VAT to total except where it states zero rate.

Goods are despatched on the day we receive your order. If for any reason we are out of stock we will try to inform you as quickly as possible. We try our best to give a speedy, fair and efficient service. V.A.T. invoice on request. Give us a ring - we'll give you service. Please ask if what you need is not listed - we will try to help. Prices are subject to change without notice.

SEMICONDUCTORS

| | | | | | | | |
|---------------|------|-----------|------|---------------|------|----------|------|
| AC107 | 35 | BC558 | 9 | BF355 | 56 | OT121 | 1.91 |
| AC126 | 30 | BCY72 | 13 | BF362 | 68 | R2008B | 1.90 |
| AC127 | 32 | BD115 | 45 | BF363 | 72 | R2010B | 1.92 |
| AC128 | 32 | BD116A | 65 | BF371 | 30 | R2265 | 1.50 |
| AC128K | 40 | BD124P | 79 | BF392 | 35 | R2322 | 62 |
| AC141K | 39 | BD131 | 50 | BF422 | 34 | R2461 | 67 |
| AC142K | 38 | BD132 | 49 | BF423 | 46 | R2540 | 2.80 |
| AC176 | 35 | BD133 | 60 | BF435 | 35 | RC4558 | 2.20 |
| AC176K | 35 | BD135 | 38 | BF457 | 35 | RCA16334 | 99 |
| AC186 | 41 | BD136 | 38 | BF458 | 43 | RCA16029 | 99 |
| AC187 | 38 | BD137 | 38 | BF459 | 43 | RCA16039 | 99 |
| AC187K | 38 | BD138 | 35 | BF460 = BF462 | 86 | RCA16091 | 2.95 |
| AC188 | 35 | BD139 | 35 | BF469 | 46 | RCA16092 | 99 |
| AC188K | 39 | BD140 | 44 | BF470 | 66 | RCA16040 | 96 |
| AD143 | 82 | BD144 | 1.70 | BF597 | 10 | RCA16041 | 84 |
| AD161 | 54 | BD150 | 60 | BF757 | 54 | RCA16334 | 90 |
| AD162 | 54 | BD159 | 65 | BF758 | 54 | RCA16335 | 99 |
| AD161/62 MP | 1.15 | BD166 | 52 | BF759 | 54 | RCA16336 | 99 |
| AF106 | 49 | BD179 | 70 | BF939 | 27 | RCA16957 | 2.88 |
| AF114 | 89 | BD182 | 1.20 | BF940 | 30 | TIC45 | 9.00 |
| AF118 | 1.20 | BD183 | 75 | BF979 | 85 | TIC46 | 65 |
| AF121 | 75 | BD201 | 85 | BF990 | 1.74 | TIL32 | 60 |
| AF124 | 48 | BD202 | 91 | BF42 | 39 | TIL78 | 48 |
| AF125 | 46 | BD203 | 80 | BF43 | 39 | TIP29C | 43 |
| AF126 | 46 | BD204 | 99 | BFW10 | 60 | TIP30A | 47 |
| AF127 | 38 | BD222 | 46 | BFX29 | 40 | TIP30C | 43 |
| AF139 | 58 | BD223 | 56 | BFX84 | 42 | TIP31C | 55 |
| AF178 | 1.54 | BD225 | 60 | BFX85 | 30 | TIP32C | 42 |
| AF239 | 60 | BD232 | 68 | BFX86 | 30 | TIP33B | 30 |
| AL102 | 2.00 | BD233 | 60 | BFX88 | 46 | TIP34B | 1.06 |
| AU106 | 2.50 | BD234 | 63 | BFY50 | 30 | TIP41C | 47 |
| AU113 | 2.00 | BD235 | 60 | BFY51 | 30 | TIP42C | 50 |
| BC107 | 20 | BD236 | 65 | BFY52 | 24 | TIP47 | 70 |
| BC108 | 20 | BD237 | 57 | BFY90 | 95 | TIP120 | 65 |
| BC109 | 20 | BD238 | 65 | BR100 | 34 | TIP2955 | 60 |
| BC114 | 12 | BD243 | 85 | BR101 | 45 | TIP3055 | 93 |
| BC115 | 17 | BD244 | 85 | BR103 | 83 | TIS91 | 2.10 |
| BC116A | 16 | BD410 | 79 | BR303 | 1.46 | TU106/02 | 1.80 |
| BC117 | 30 | BD434 | 74 | BRC4443 | 94 | 2N696 | 21 |
| BC118 | 24 | BD437 | 86 | BRC4444 | 98 | 2N918 | 82 |
| BC119 | 36 | BD438 | 94 | BRX46 | 40 | 2N904 | 51 |
| BC139 | 28 | BD507 | 92 | BRX39 | 56 | 2N905 | 28 |
| BC140 | 32 | BD508 | 55 | BRY55 | 45 | 2N3054 | 60 |
| BC141 | 26 | BD509 | 56 | BRY58 | 57 | 2N3055 | 60 |
| BC142 | 30 | BD510 | 60 | BSR59 | 1.80 | 2N3702 | 11 |
| BC143 | 31 | BD278A | 81 | BSV57B | 89 | 2N3703 | 11 |
| BC147 | 13 | BD517 | 60 | BSW67 | 68 | 2N3705 | 10 |
| BC148 | 9 | BD520 | 75 | BT100 | 1.65 | 2N3706 | 10 |
| BC149 | 12 | BD535 | 82 | BT101 | 1.20 | 2N3708 | 17 |
| BC157 | 16 | BD536 | 91 | BT102/500 | 1.20 | 2N5294 | 48 |
| BC158 | 16 | BD696A | 1.49 | BT106 | 1.60 | 2N5296 | 48 |
| BC159 | 15 | BD697 | 1.24 | BT108 | 1.69 | 2N5298 | 69 |
| BC160 | 25 | BD695 | 1.39 | BT109 | 99 | 2SB337 | 1.86 |
| BC161 | 28 | BD698 | 1.50 | BT116 | 1.21 | 2N5496 | 53 |
| BC170B | 15 | BD707 | 95 | BT119 | 3.66 | 2N6107 | 75 |
| BC171 | 15 | BDX32 | 2.10 | BT120 | 3.66 | 2N6109 | 81 |
| BC172 | 15 | BF115 | 38 | BT151/800 | 1.20 | 2SA715 | 1.98 |
| BC173 | 12 | BF117 | 36 | BU104 | 2.00 | 2SC495 | 1.10 |
| BC174 | 10 | BF125 | 26 | BU105 | 1.58 | 2SC496 | 1.31 |
| BC177 | 27 | BF127 | 47 | BU108 | 1.80 | 2SC643A | 1.50 |
| BC178 | 26 | BF154 | 23 | BU124 | 1.90 | 2SC1096 | 1.72 |
| BC182L | 9 | BF158 | 18 | BU126 | 1.75 | 2SC1172Y | 2.20 |
| BC183L | 12 | BF160 | 27 | BU204 | 1.50 | 2SC1173Y | 1.69 |
| BC184L | 14 | BF167 | 24 | BU205 | 1.42 | 2SC1306 | 2.73 |
| BC186 | 18 | BF173 | 22 | BU206 | 1.80 | 2SC1307 | 3.00 |
| BC187 | 25 | BF177 | 52 | BU208 | 1.80 | 2SC1449 | 1.57 |
| BC204 | 10 | BF178 | 46 | BU208A | 1.65 | 2SC1520 | 68 |
| BC208 | 13 | BF179 | 28 | BU208D | 2.20 | 2SC1678 | 2.57 |
| BC209 | 10 | BF180 | 39 | BU800 | 2.50 | 2SC1909 | 2.90 |
| BC212 | 9 | BF181 | 39 | BU208/02 | 2.10 | 2SC1953 | 1.44 |
| BC212L | 13 | BF182 | 36 | BU326A | 1.75 | 2SC2028 | 1.82 |
| BC213 | 13 | BF183 | 29 | BU407 | 1.70 | 2SC2029 | 2.60 |
| BC214 | 10 | BF184 | 36 | BU426 | 3.07 | 2SC2078 | 2.90 |
| BC237 | 14 | BF185 | 36 | BU500 | 2.30 | 2SC2091 | 1.34 |
| BC238 | 14 | BF194/394 | 16 | BU526 | 2.46 | 2SC2166 | 2.73 |
| BC251A | 18 | BF195 | 16 | BU508 | 3.20 | DEC1 | 2.20 |
| BC252 | 12 | BF196 | 16 | BU806 | 1.40 | DEC2 | 2.20 |
| BC261 | 18 | BF197 | 16 | BU807 | 2.94 | THY15/80 | 2.20 |
| BC262 | 18 | BF198 | 18 | BUW84 | 1.45 | THY15/85 | 2.20 |
| BC300 | 50 | BF199 | 21 | BUW91A | 3.84 | BUW81A | 3.84 |
| BC301 | 53 | BF200 | 35 | BUX84 | 1.50 | | |
| BC303 | 33 | BF224 | 25 | E1222 | 40 | | |
| BC307 | 20 | BF225 | 20 | MCR101 | 45 | | |
| BC308 | 25 | BF241 | 25 | MCR220 | 1.50 | | |
| BC323 | 99 | BF256 | 55 | ME0411 | 20 | | |
| BC327 | 18 | BF257 | 28 | MJE340 | 68 | | |
| BC328 | 18 | BF258 | 25 | MJE520 | 50 | | |
| BC337 | 18 | BF259 | 35 | MJ3000 | 1.98 | | |
| BC338 | 18 | BF262 | 84 | MPSA92 | 35 | | |
| BC461 | 30 | BF263 | 75 | MR814 | 45 | | |
| BC547 | 13 | BF271 | 24 | MR854 | 55 | | |
| BC548 | 13 | BF273 | 24 | MR475 | 2.46 | | |
| BCX32 = BC637 | 39 | BF274 | 26 | MR479 | 2.60 | | |
| BC549 | 8 | BF336 | 36 | ON447 | 99 | | |
| BC550 | 7 | BF337 | 41 | ON448 | 99 | | |
| BC557 | 8 | BF338 | 41 | OT112 | 1.91 | | |

INTEGRATED CIRCUITS

| | | | | | |
|------------|-------|----------------------|-------|----------|------|
| AN214Q | 3.91 | SN76023N | 2.00 | TCA760 | 2.30 |
| AN240 | 3.84 | SN76110N | 1.15 | TCA270SQ | 2.50 |
| AN318 | 3.98 | SN76115N | 2.27 | TCA800 | 3.10 |
| AN262 | 2.45 | SN76131N | 2.00 | TCA830 | 2.44 |
| AN301 | 5.15 | SN76226DN | 2.00 | TCA830S | 1.75 |
| AN715Q | 3.97 | SN76227N | 1.18 | TCA900 | 2.20 |
| AN6340 | 7.85 | SN76533N | 1.70 | TCA910 | 2.20 |
| AN6341N | 5.10 | SN76533N | 2.49 | TCA940 | 1.95 |
| AN6344 | 7.85 | SN76544N | 2.35 | TDA440 | 2.20 |
| BA521 | 2.80 | SN76650N | 1.05 | TDA1002 | 1.95 |
| BA536 | 3.00 | SN76660N | 80 | TDA1003A | 1.50 |
| CA555 | 4.6 | SN76666N | 80 | TDA1004A | 3.35 |
| CA556 | 84 | STK015 | 6.25 | TDA1006A | 2.50 |
| CA741 | 25 | STK032 | = | TDA1005 | 3.60 |
| CA748 | 45 | STK078 | 13.25 | TDA1010 | 1.54 |
| CA3065 | 1.80 | STK043 | 11.05 | TDA1035 | 4.70 |
| HA1151 | 3.89 | STK433 | 5.65 | TDA1044 | 4.37 |
| HA1322 | 2.65 | STK435 | 9.06 | TDA1060A | 4.44 |
| HA1342 | 2.49 | STK436 | 5.50 | TDA1062 | 1.56 |
| HA1306N | 2.60 | STK437 | 7.85 | TDA1083 | 1.68 |
| HA1366VWR | 2.80 | STK439 | 6.62 | TDA1170S | 3.00 |
| HA1392 | 3.95 | STK459 | 8.20 | TDA1190 | 3.50 |
| HA11219 | 2.49 | STK441 | 8.10 | TDA1180 | 2.91 |
| HA11244 | 1.98 | STK461 = 465 | 9.60 | TDA1200 | 2.95 |
| LA4031P | 3.21 | STK463 | 14.30 | TDA1220A | 2.12 |
| LA4032P | 2.90 | SW153 | 2.74 | TDA1270 | 3.95 |
| LA4102 | 3.37 | TA7050P | 95 | TDA1327 | 1.70 |
| LA4250 | 3.57 | TA7051P | 95 | TDA1352B | 1.60 |
| LA4400 | 3.05 | TA7063P | 2.20 | TDA1412 | 1.20 |
| LA4422 | 3.28 | TA7074P | 1.00 | TDA1415 | 1.40 |
| LC7130 | 5.93 | TA7108P | 3.43 | TDA1470 | 4.67 |
| LC7120 | 5.87 | TA7120P | 2.43 | TDA1770 | 5.60 |
| LC7137 | 5.93 | TA7129AP | 3.76 | TDA2002 | 2.80 |
| LM1011 | 3.25 | TA7130P | 1.93 | TDA2003 | 1.20 |
| LM1340T | 2.75 | TA7141P | 95 | TDA2004 | 2.52 |
| LM1303N | 7.63 | TA7146P | 4.67 | TDA2006 | 1.78 |
| MB3712 | 1.95 | TA7193P | 5.67 | TDA2010 | 2.00 |
| MC1307 | 1.99 | TA7171P | 1.85 | TDA2140 | 5.95 |
| MC1310P | 1.60 | TA7172P | 1.85 | TDA2150 | 2.22 |
| MC1327 | 1.70 | TA7173P | 1.85 | TDA2020 | 4.66 |
| MC1349 | 2.93 | TA7176P | 2.50 | TDA2030 | 2.80 |
| MC1350 | 1.50 | TA7202P | 4.27 | TDA2521 | 4.17 |
| MC1352 | 1.75 | TA7204P | 3.77 | TDA2522 | 2.40 |
| MC1358P | 1.50 | TA7205AP | 3.72 | TDA2523 | 3.40 |
| MC1495L | 3.00 | TA7208P | 3.40 | TDA2524 | 2.25 |
| MC13002 | 3.90 | TA7210P | 6.60 | TDA2525 | 4.00 |
| MC14018BCP | 66 | TA7222 | 2.42 | TDA2530 | 2.70 |
| MC14049UB | 43 | TA7223P | 3.74 | TDA2532 | 2.56 |
| MCF7742 | 1.35 | TA7227P | 5.98 | TDA2540 | 3.84 |
| MCF7812 | 1.35 | TA7228P | 5.98 | TDA2541 | 3.84 |
| ML231 | 2.20 | TA7310P | 2.78 | TDA2560 | 3.50 |
| ETTR0616 | 2.20 | TA7609P | 4.39 | TDA2571 | 2.56 |
| ML232 | 2.20 | TA7611AP | 2.92 | TDA2576 | 3.75 |
| ML236 | 5.55 | TAA300 | 58 | TDA2579A | 3.75 |
| ML237 | 2.30 | TAA310 | 2.83 | TDA2577 | 3.25 |
| ML238 | 2.50 | TAA320 | 2.00 | TDA2581 | 3.30 |
| ML239 | 6.00 | TAA550 | 55 | TDA2582 | 2.60 |
| ML920 | 4.12 | TAA630 | 3.90 | TDA2590 | 3.25 |
| ML922 | 3.29 | TAA8400S1 | 1.96 | TDA2591 | 2.95 |
| ML928 | 2.18 | TAA661B | 1.20 | TDA2592 | 2.95 |
| MM5387ANN | 4.15 | TBA120A | 80 | TDA2600 | 5.30 |
| MM5402N | 6.65 | (A), (S), (AS), (SA) | | TDA2610 | 3.20 |
| MMF475 | 2.50 | TBA120B | 1.37 | TDA2611A | 1.95 |
| MMF477 | 10.00 | TBA120S | 1.30 | TDA2640 | 2.92 |
| MS1513L | 2.80 | TBA120T | 95 | TDA2652 | 7.31 |
| MS1515L | 3.28 | TBA120U | 1.10 | TDA2653 | 5.90 |
| SA11025 | 4.40 | TBA395 | 1.20 | TDA2680 | 3.40 |
| SA11124 | 2.50 | TBA396 | 80 | TDA2690 | 1.35 |
| SA11250 | 3.94 | TBA440N | 2.75 | TDA3190 | 2.00 |
| SA11251 | 4.90 | (TBA1441) | | TDA3500 | 6.90 |
| SA15000 | 4.39 | TBA440P | 1.50 | TDA3560 | 6.00 |
| SA15010 | 6.30 | TBA480Q | 2.50 | TDA3561 | 6.50 |
| SA15012 | 6.50 | TBA510 | 3.00 | TDA3571 | 3.75 |
| SA15020 | 5.90 | TBA520(Q) | 1.68 | TDA3651A | 4.50 |
| SA15030 | 8.25 | TBA530(Q) | 1.38 | TDA3950 | 3.50 |
| SA15050 | 8.50 | TBA540 | 1.68 | TDA4420 | 4.22 |
| SA15070 | 8.25 | TBA550(Q) | 1.58 | TDA4600 | 2.95 |
| SA15080 | 8.25 | TBA560(Q) | 1.58 | TDA9503 | 2.50 |
| SA15090 | 8.25 | TBA570 | 1.79 | TEA1002 | 3.50 |
| SA15100 | | | | | |

WE WILL ONLY SUPPLY TOP QUALITY, BRANDED COMPONENTS. REPUTATION COUNTS WITH US

G.G.L. COMPONENTS
108 SCOTLAND ROAD, CARLISLE, CUMBRIA CA3 9EY
PHONE (0228) 20358/39693

BUY WITH



| E.H.T. TRAYS | |
|----------------|-------|
| RBM T20/22A | 7.35 |
| RBM A823 | 7.85 |
| PHILIPS G8-550 | 7.90 |
| PHILIPS G9 | 6.45 |
| PHILIPS KT3 | 10.00 |
| THORN1500-3S | 5.05 |
| THORN1500-5S | 5.40 |
| THORN3500 | 8.25 |
| THORN8000 | 5.20 |
| THORN8500/8800 | 7.60 |
| THORN9000 | 8.70 |
| PYE 731 | 7.30 |
| DECCA 2230 | 7.20 |
| DECCA 100 | 7.20 |
| ITT CVC 20/30 | 6.85 |
| Universal | 5.90 |

| INTEGRATED CIRCUITS | TYPE | PRICE (£) | TYPE | PRICE (£) | TYPE | PRICE (£) | TYPE | PRICE (£) | TRANSISTORS | TYPE | PRICE | TYPE | PRICE | LINE O/P TR. | TYPE | PRICE |
|---------------------|-----------|-----------|----------|-----------|-----------|-----------|-----------|-----------|-------------|------|--------|------|-----------------------|--------------|--------------------------|-------|
| AN103 | LA4031 | 1.95 | STK036 | 12.67 | TBA800 | 80 | UPC1176C | 2.10 | BC548 | 10 | BR100 | 18 | RBM T20/22A | 12.20 | TYPE | PRICE |
| AN214 | LA4032 | 2.25 | STK043 | 11.33 | TBA810AS | 1.15 | UPC1177H | 2.35 | BC557 | 10 | BR101 | 32 | RBM 2718 18/20/22 | | BY127 | 10 |
| AN240 | LA4051 | 2.25 | STK050 | 20.75 | TBA820 | 1.40 | UPC1178C | 2.20 | BC558 | 10 | BR103 | 55 | | | BY133 | 15 |
| AN253 | LA4101 | 1.88 | STK077 | 8.56 | TBA890 | 2.95 | UPC1180C | 3.05 | AC127 | 22 | BD124P | 70 | PHILIPS G8 | 7.90 | BY164 | 40 |
| AN255 | LA4102 | 1.97 | STK078 | 8.45 | TBA920Q | 2.65 | UPC1181H | 2.20 | AC128 | 22 | BD131 | 33 | PHILIPS G9 | 8.75 | BY179 | 60 |
| AN315 | LA4112 | 2.97 | STK082 | 9.75 | TBA950/2X | 1.55 | UPC1182H | 2.35 | AC187K | 30 | BD132 | 33 | PHILIPS G11 | 13.50 | BY210/800 | 30 |
| AN337 | LA4201 | 2.95 | STK086 | 12.89 | TCA270S | 1.30 | UPC1183H | 2.35 | AC188K | 33 | BD201 | 80 | THORN 1590/1 | 8.68 | BY227M | 23 |
| AN338 | LA4400 | 2.80 | STK415 | 9.66 | TCA900 | 4.10 | UPC1185H2 | 3.30 | AD149 | 70 | BD202 | 70 | THORN 1690/1 | 9.68 | BYX10 | 20 |
| AN360 | LA4420 | 1.94 | STK433 | 7.25 | TCA940 | 1.55 | UPC1188H | 3.30 | AD161 | 42 | BD203 | 70 | THORN 1615 | 9.75 | BYX55/600 | 26 |
| AN632 | LA4422 | 2.75 | STK435 | 7.75 | TDA1002A | 1.50 | UPC1190C | 2.10 | AD162 | 42 | BD204 | 83 | THORN TX10 | 12.50 | OA90 | 07 |
| AN710 | LA4430 | 1.93 | STK437 | 7.77 | TDA1003A | 2.80 | UPC1198H | 1.30 | AF127 | 36 | BD222 | 50 | PYE 731/713 (110) | 10.20 | IN5401-7 | 07 |
| AN714 | LA4460 | 2.95 | STK439 | 7.86 | TDA1004A | 2.70 | UPC1200V | 1.90 | AU110 | 3.10 | BD232 | 50 | PYE 725 (90) | 10.20 | IN5401-8 | 12 |
| AN715 | LA4461 | 2.95 | STK441 | 9.52 | TDA1035 | 3.20 | UPC1208C | 1.85 | AU113 | 4.60 | BD233 | 37 | ITT CVC 1-9 | 9.60 | BZV88-range | 11 |
| AN7120 | MB3712 | 2.30 | STK443 | 11.33 | TDA1044 | 3.10 | UPC1211C | 4.05 | BC107 | 14 | BD234 | 40 | DECCA 2230 | 8.30 | MOTORS | |
| AN7140 | MB3713 | 2.25 | STK459 | 9.55 | TDA1170 | 1.80 | UPC1215V | 2.50 | BC108 | 14 | BD235 | 32 | DECCA 100 | 8.58 | 6-9-12-13.2V Motors 5.00 | |
| AN7145 | MB8719 | 5.20 | STK461 | 9.95 | TDA1170 | 1.80 | UPC1216V | 2.00 | BC109 | 14 | BD236 | 43 | DECCA 100 | 8.58 | | |
| AN7150 | MC1327A | 1.00 | STK463 | 10.88 | TDA2004A | 4.35 | UPC1217G | 3.35 | BC141 | 26 | BD237 | 40 | ITT CVC 20 | 7.75 | | |
| AN7151 | MC1358P | 1.60 | STK501 | 8.98 | TDA2020 | 2.95 | UPC1218H | 2.75 | BC142 | 23 | BD238 | 39 | ITT CVC 25/30/32 | 8.00 | | |
| HA1137 | MC1330P | 90 | TA7072P | 2.75 | TDA2522 | 1.80 | UPC1222 | 2.05 | BC143 | 25 | BD239 | 47 | ANTI-SURGE FUSES | | | |
| HA1144 | ML231B | 1.95 | TA7108P | 2.10 | TDA2523 | 2.25 | UPC1223 | 3.40 | BC147 | 09 | BD434 | 50 | A/S20MM 80MA | 2.75 | | |
| HA1151 | ML232B | 1.70 | TA7120P | 2.05 | TDA2530 | 2.10 | UPC1226 | 2.55 | BC148 | 09 | BD437 | 70 | 100, 160, 200MA | 1.70 | | |
| HA1156 | ML237 | 2.50 | TA7129 | 3.00 | TDA2532 | 2.20 | UPC1227 | 2.10 | BC157 | 10 | BD438 | 78 | 315, 400, 500, 630, | | | |
| HA1166 | ML238 | 4.22 | TA7130P | 1.20 | TDA2540 | 1.95 | UPC1230H | 3.45 | BC158 | 11 | BD707 | 1.05 | 800MA, 1A, 1.25, 1.6, | | | |
| HA1197 | SAA1024 | 2.55 | TA7139P | 2.80 | TDA2560 | 1.80 | UPC1245 | 1.99 | BC159 | 11 | BDX32 | 1.65 | 2A, 2.5, 3A, 4.5A | 1.35 | | |
| HA1199 | SAA1125 | 4.70 | TA7157P | 3.00 | TDA2581 | 1.70 | UPC1250 | 2.45 | BC160 | 22 | BF194 | 12 | TV106/02.160 | | | |
| HA1202 | SAA1250 | 3.85 | TA7171P | 3.40 | TDA2590 | 2.25 | UPC1350C | 4.50 | BC172 | 10 | BF195 | 13 | 2N3054 | 55 | | |
| HA1201 | SAA1251 | 5.20 | TA7172P | 3.40 | TDA2591 | 2.70 | UPC1353C | 2.60 | BC177 | 22 | BF196 | 11 | 2N3055 | 50 | | |
| HA1306 | SAA5010 | 5.10 | TA7176AP | 2.90 | TDA2593 | 2.30 | UPC1356C2 | 3.05 | BC182 | 11 | BF197 | 11 | 2SC1172Y | | | |
| HA1319 | SAA5012 | 5.70 | TA7193P | 4.20 | TDA2600 | 5.50 | UPC1358H | 3.05 | BC183 | 11 | BF198 | 14 | | 1.85 | | |
| HA1322 | SAS560S | 1.83 | TA7202P | 3.00 | TDA2611A | 1.50 | UPC1363C | 3.20 | BC184 | 11 | BF241 | 15 | 2SC2029 | 2.00 | | |
| HA1325 | SAS570S | 1.90 | TA7203P | 3.00 | TDA2640 | 2.30 | UPC1366C | 2.85 | BC208 | 12 | BF256L | 25 | 2SC2078 | 2.20 | | |
| HA1338 | SAS580 | 2.40 | TA7204P | 1.80 | TDA3560 | 5.10 | UPC1367C | 2.85 | BC212L | 10 | BF258 | 25 | 2SC1969 | 2.45 | | |
| HA1339 | SAS590 | 2.40 | TA7205AP | 1.60 | UPC41C | 2.95 | UPC1370C2 | 3.80 | BC213L | 10 | BF259 | 26 | | | | |
| HA1342A | SL901B | 5.65 | TA7208P | 2.20 | UPC554C | 1.30 | UPC1373H | 1.20 | BC214L | 10 | BF337 | 28 | | | | |
| HA1366 | SL917B | 6.95 | TA7210P | 5.60 | UPC555H | 0.70 | UPC1377C | 4.60 | BC237B | 11 | BF338 | 30 | | | | |
| WWR | SN76003N | 2.30 | TA7222P | 1.70 | UPC566H3 | 2.10 | UPC1378H | 3.80 | BC337 | 11 | BF458 | 30 | | | | |
| HA1368 | SN76013N | 2.30 | TA7223P | 3.15 | UPC577H | 3.00 | UPC1384C | 5.50 | BC338 | 10 | BF459 | 36 | | | | |
| HA1371 | SN76023N | 2.30 | TA7227 | 4.65 | UPC585C | 1.40 | UPC2002H | 2.20 | BC547 | 10 | BFR90 | 1.60 | | | | |
| HA1374 | SN76110N | 90 | TA7310P | 1.70 | UPC1009H | 2.15 | | | | | BFR90 | 1.60 | | | | |
| HA1377 | SN76226DN | 1.45 | TA7313P | 2.10 | UPC1017G | 2.55 | | | | | BFR90 | 1.60 | | | | |
| HA1388 | SN76227N | 1.00 | TAA550 | 28 | UPC1018C | 1.15 | | | | | BFR90 | 1.60 | | | | |
| HA1397 | SN76660N | 65 | TBA120AS | 70 | UPC1025H | 3.30 | | | | | BFR90 | 1.60 | | | | |
| HA11211 | STK0039 | 6.45 | TBA120SB | 90 | UPC1026C | 1.40 | | | | | BFR90 | 1.60 | | | | |
| KIA7127 | STK0040 | 5.95 | TBA120U | 1.00 | UPC1028H | 2.15 | | | | | BFR90 | 1.60 | | | | |
| HA11221 | STK0050 | 7.50 | TBA395 | 1.25 | UPC1031H | 2.85 | | | | | BFR90 | 1.60 | | | | |
| LA1201 | STK011 | 1.88 | TBA396 | 85 | UPC1032H | 0.85 | | | | | BFR90 | 1.60 | | | | |
| LA1230 | STK014 | 7.65 | TBA520 | 1.30 | UPC1035C | 2.50 | | | | | BFR90 | 1.60 | | | | |
| LA1365 | STK015 | 7.15 | TBA530 | 1.00 | UPC1042C | 2.40 | | | | | BFR90 | 1.60 | | | | |
| LA2200 | STK016 | 7.45 | TBA540 | 1.27 | UPC1043C | 2.45 | | | | | BFR90 | 1.60 | | | | |
| LA3122 | STK020 | 9.05 | TBA550 | 1.40 | UPC1156H | 2.45 | | | | | BFR90 | 1.60 | | | | |
| LA3201 | STK032 | 11.32 | TBA560Q | 1.60 | UPC1168C | 2.70 | | | | | BFR90 | 1.60 | | | | |
| LA3350 | STK035 | 12.67 | TBA750Q | 2.45 | UPC1170C | 1.55 | | | | | BFR90 | 1.60 | | | | |

| DIODES | |
|-------------|----|
| BY127 | 10 |
| BY133 | 15 |
| BY164 | 40 |
| BY179 | 60 |
| BY210/800 | 30 |
| BY227 | 86 |
| BY227M | 23 |
| BYX10 | 20 |
| BYX55/600 | 26 |
| OA90 | 07 |
| IN5401-7 | 07 |
| IN5401-8 | 12 |
| BZV88-range | 11 |

| SUNDRIES | |
|-----------------|------|
| PYE IF GAIN MOD | 7.85 |
| E/W COIL G11 | 1.65 |
| VA1104 | 69 |
| G8 TRANSDUCTOR | 2.25 |
| G8 ON/OFF SW | 1.40 |

TELEPART

Telegen-1

- PRICE £17.20 (Inc. VAT)
 * EXCEPTIONALLY LIGHT AND DURABLE
 * POCKET SIZE FOR OUTSIDE SERVICE
 * PP3 BATTERY POWER SOURCE
 * FIVE DIFFERENT TEST PATTERNS FOR COLOUR & MONO TV
 * CROSSHATCH GRID * DOT MATRIX
 * WHITE RASTER
 * HORIZONTALS * VERTICLES
 * 3.5mm JACK SOCKET FOR OPTIONAL P.S.U.



A lightweight, extremely portable and versatile pattern generator for black/white and colour T.V. alignment and service at the customer's home. At the turn of a switch, the generator can provide five essential test patterns for correct installation, fast checks and repairs. Pattern stability is first class and compares favourably with other more costly bulky generators only suitable for bench work. The generator is pocket size measuring 10 x 7.5 x 4 cm and weighs only 190 grams. Switched 3.5 mm jack socket allows use of external power supply with battery in situ.

Telegen-2

- PRICE £34.45 (Inc. VAT)
 * EXCEPTIONALLY LIGHT & DURABLE
 * COMPACT 10 x 12 x 4.5 cms
 * RED RASTER * GREEN RASTER
 * BLUE RASTER
 * COLOUR BARS
 * 3.5 mm JACK SOCKET FOR P.S.U.
 * PROVIDES UHF SIGNAL APPROX. CHANNEL 35



Telegen 2 is a colour bar generator at a very modest price and yet is extremely effective, stable and durable. It is the perfect compliment to Telegen 1, giving colour bars arranged in the following sequence: white, yellow, cyan, green, magenta, red, blue and black. The unit provides a signal in the UHF band approx. Channel 35 and requires a supply of 14 to 18 volts D.C.

Power Supply

A switchable power supply ideally suited to both Telegen 1 and Telegen 2.
 PRICE £4.55 (Inc. VAT)
 POST AND PACKING £1.44 (Inc. VAT)
 All goods should be delivered within 4 working days.
32 TEMPLE STREET, WOLVERHAMPTON
WV2 4LJ. TEL: (0902) 773122

FREE CAREER BOOKLET

Train for success, for a better job, better pay
 Enjoy all the advantages of an ICS Diploma Course, training you ready for a new, higher paid, more exciting career.
 Learn in your own home, in your own time, at your own pace, through ICS home study, used by over 8 million already!
 Look at the wide range of opportunities awaiting you. Whatever your interest or skill, there's an ICS Diploma Course there for you to use.
 Send for your FREE CAREER BOOKLET today—at no cost or obligation at all.

GCE Over 40 'O' and 'A' Level subjects from which to choose. Your vital passport to career success.

| | |
|--|--|
| COMPUTER PROGRAMMING <input type="checkbox"/> | RADIO AMATEUR'S LICENCE <input type="checkbox"/> |
| ELECTRONICS <input type="checkbox"/> | INTERIOR DESIGN <input type="checkbox"/> |
| COMMERCIAL ART <input type="checkbox"/> | WRITING FOR PROFIT <input type="checkbox"/> |
| TV, RADIO & AUDIO SERVICING <input type="checkbox"/> | CAR MECHANICS <input type="checkbox"/> |
| BOOK-KEEPING & ACCOUNTANCY <input type="checkbox"/> | |

Please send FREE DETAILS for the course ticked above.

Name


Address

P.Code

ICS ICS Dept. EGS25
 8 Elliot Place
 Clydeaway Centre
 Glasgow G3 8EF

041 221 2926
 or 01 622 9911
 (all hours)

CACC

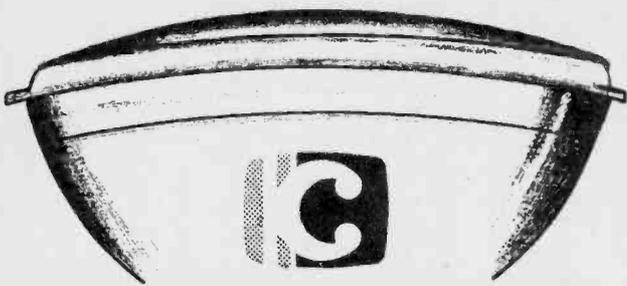

CHROMAVAC

QUALITY REBUILDS

SPECIAL OFFERS!
ON
INLINE

Get on the hot-line today!

SUPERIOR QUALITY TUBES **051 428 8777**
DELTA RE-BUILDS
most types of Inline Re-builds or new ex-stock
★ 2 YEAR WARRANTY
★ 4 YEAR OPTIONAL

Delta Rebuilds

- Up to 19" £28
- Up to 22" £30
- Up to 26" £34
- 110° up to 22" £34
- 110° up to 26" £38
- Low focus +£2
- A47 342 New £34

Delta only. Less 7½% 5+
Less 10% 10+ and over

Inline Rebuilds

- Up to 22" £40
- Up to 26" £45
- A56 - 540x £56
- A66 - 540x £58
- Bonded Coil +£5

ALL SIZES OF
NEW MONO TUBES
AT COMPETITIVE PRICES

IN LINE TYPES EX-STOCK SELECTION NOT REBUILDS

- 370 HFB £45
- 370 HUB £45
- 420 CSB £45
- 420 EDB £45
- 420 EZB £45
- 420 ERB £45
- 510 UFB/A51-590 £55
- A51-570 £55
- A51-210 £55
- 510 VSB £60
- AXT 51-001 £60
- 560 DYB £62
- 560 EGB £62
- 560 CGB £62

- 560 DMB £62
- AXT 56-001 £62
- 660 AB £65
- A67-701 £65
- 670 CZB £65
- H6817 £65
- 370 KRB £55

CARRIAGE
£5 Singles. 2-3 £10. 4 £12
10 £15. 10+ Carriage paid
EXCLUSIVE OF VAT
TERMS
Cash with order

QUANTITY DISCOUNT AVAILABLE
Ask for details

★ OUR TECHNICAL DEPT. WILL ADVISE YOU ON PROBLEMS YOU MAY ENCOUNTER ON FITTING INLINE TUBES
DELIVERY: Ex stock items immediate dispatch on receipt of order. Others allow 14 days.

THE COMPANY WHO PUT HIGH STANDARDS FIRST



CHROMAVAC LTD. UNIT 7, BEAR BRAND COMPLEX,
ALLERTON ROAD, WOOLTON, LIVERPOOL 25
Ask for Mr Butterworth or Betty Ford ON: 051-428 8777


| BULK BUYERS LIST | | PRICES ARE FOR 100+ OF ONE TYPE OR A MINIMUM OF £10 PER LINE ITEM | |
|------------------|------|---|------|
| BF181 | 0.16 | MPS5172 | 0.05 |
| BF182 | 0.16 | MPS5651 | 0.05 |
| BF183 | 0.16 | MPS5611 | 0.05 |
| BF184 | 0.16 | MPS5615 | 0.05 |
| BF185 | 0.05 | MPS5616 | 0.10 |
| BF186 | 0.05 | MPSA14 | 0.13 |
| BF187 | 0.10 | MPSA18 | 0.12 |
| BF188 | 0.10 | MPSA20 | 0.12 |
| BF189 | 0.10 | MPSA22 | 0.12 |
| BF190 | 0.10 | MPSA24 | 0.12 |
| BF191 | 0.10 | MPSA26 | 0.12 |
| BF192 | 0.10 | MPSA28 | 0.12 |
| BF193 | 0.10 | MPSA30 | 0.12 |
| BF194 | 0.10 | MPSA32 | 0.12 |
| BF195 | 0.10 | MPSA34 | 0.12 |
| BF196 | 0.10 | MPSA36 | 0.12 |
| BF197 | 0.10 | MPSA38 | 0.12 |
| BF198 | 0.10 | MPSA40 | 0.12 |
| BF199 | 0.10 | MPSA42 | 0.12 |
| BF200 | 0.10 | MPSA44 | 0.12 |
| BF201 | 0.10 | MPSA46 | 0.12 |
| BF202 | 0.10 | MPSA48 | 0.12 |
| BF203 | 0.10 | MPSA50 | 0.12 |
| BF204 | 0.10 | MPSA52 | 0.12 |
| BF205 | 0.10 | MPSA54 | 0.12 |
| BF206 | 0.10 | MPSA56 | 0.12 |
| BF207 | 0.10 | MPSA58 | 0.12 |
| BF208 | 0.10 | MPSA60 | 0.12 |
| BF209 | 0.10 | MPSA62 | 0.12 |
| BF210 | 0.10 | MPSA64 | 0.12 |
| BF211 | 0.10 | MPSA66 | 0.12 |
| BF212 | 0.10 | MPSA68 | 0.12 |
| BF213 | 0.10 | MPSA70 | 0.12 |
| BF214 | 0.10 | MPSA72 | 0.12 |
| BF215 | 0.10 | MPSA74 | 0.12 |
| BF216 | 0.10 | MPSA76 | 0.12 |
| BF217 | 0.10 | MPSA78 | 0.12 |
| BF218 | 0.10 | MPSA80 | 0.12 |
| BF219 | 0.10 | MPSA82 | 0.12 |
| BF220 | 0.10 | MPSA84 | 0.12 |
| BF221 | 0.10 | MPSA86 | 0.12 |
| BF222 | 0.10 | MPSA88 | 0.12 |
| BF223 | 0.10 | MPSA90 | 0.12 |
| BF224 | 0.10 | MPSA92 | 0.12 |
| BF225 | 0.10 | MPSA94 | 0.12 |
| BF226 | 0.10 | MPSA96 | 0.12 |
| BF227 | 0.10 | MPSA98 | 0.12 |
| BF228 | 0.10 | MPSA100 | 0.12 |
| BF229 | 0.10 | MPSA102 | 0.12 |
| BF230 | 0.10 | MPSA104 | 0.12 |
| BF231 | 0.10 | MPSA106 | 0.12 |
| BF232 | 0.10 | MPSA108 | 0.12 |
| BF233 | 0.10 | MPSA110 | 0.12 |
| BF234 | 0.10 | MPSA112 | 0.12 |
| BF235 | 0.10 | MPSA114 | 0.12 |
| BF236 | 0.10 | MPSA116 | 0.12 |
| BF237 | 0.10 | MPSA118 | 0.12 |
| BF238 | 0.10 | MPSA120 | 0.12 |
| BF239 | 0.10 | MPSA122 | 0.12 |
| BF240 | 0.10 | MPSA124 | 0.12 |
| BF241 | 0.10 | MPSA126 | 0.12 |
| BF242 | 0.10 | MPSA128 | 0.12 |
| BF243 | 0.10 | MPSA130 | 0.12 |
| BF244 | 0.10 | MPSA132 | 0.12 |
| BF245 | 0.10 | MPSA134 | 0.12 |
| BF246 | 0.10 | MPSA136 | 0.12 |
| BF247 | 0.10 | MPSA138 | 0.12 |
| BF248 | 0.10 | MPSA140 | 0.12 |
| BF249 | 0.10 | MPSA142 | 0.12 |
| BF250 | 0.10 | MPSA144 | 0.12 |
| BF251 | 0.10 | MPSA146 | 0.12 |
| BF252 | 0.10 | MPSA148 | 0.12 |
| BF253 | 0.10 | MPSA150 | 0.12 |
| BF254 | 0.10 | MPSA152 | 0.12 |
| BF255 | 0.10 | MPSA154 | 0.12 |
| BF256 | 0.10 | MPSA156 | 0.12 |
| BF257 | 0.10 | MPSA158 | 0.12 |
| BF258 | 0.10 | MPSA160 | 0.12 |
| BF259 | 0.10 | MPSA162 | 0.12 |
| BF260 | 0.10 | MPSA164 | 0.12 |
| BF261 | 0.10 | MPSA166 | 0.12 |
| BF262 | 0.10 | MPSA168 | 0.12 |
| BF263 | 0.10 | MPSA170 | 0.12 |
| BF264 | 0.10 | MPSA172 | 0.12 |
| BF265 | 0.10 | MPSA174 | 0.12 |
| BF266 | 0.10 | MPSA176 | 0.12 |
| BF267 | 0.10 | MPSA178 | 0.12 |
| BF268 | 0.10 | MPSA180 | 0.12 |
| BF269 | 0.10 | MPSA182 | 0.12 |
| BF270 | 0.10 | MPSA184 | 0.12 |
| BF271 | 0.10 | MPSA186 | 0.12 |
| BF272 | 0.10 | MPSA188 | 0.12 |
| BF273 | 0.10 | MPSA190 | 0.12 |
| BF274 | 0.10 | MPSA192 | 0.12 |
| BF275 | 0.10 | MPSA194 | 0.12 |
| BF276 | 0.10 | MPSA196 | 0.12 |
| BF277 | 0.10 | MPSA198 | 0.12 |
| BF278 | 0.10 | MPSA200 | 0.12 |
| BF279 | 0.10 | MPSA202 | 0.12 |
| BF280 | 0.10 | MPSA204 | 0.12 |
| BF281 | 0.10 | MPSA206 | 0.12 |
| BF282 | 0.10 | MPSA208 | 0.12 |
| BF283 | 0.10 | MPSA210 | 0.12 |
| BF284 | 0.10 | MPSA212 | 0.12 |
| BF285 | 0.10 | MPSA214 | 0.12 |
| BF286 | 0.10 | MPSA216 | 0.12 |
| BF287 | 0.10 | MPSA218 | 0.12 |
| BF288 | 0.10 | MPSA220 | 0.12 |
| BF289 | 0.10 | MPSA222 | 0.12 |
| BF290 | 0.10 | MPSA224 | 0.12 |
| BF291 | 0.10 | MPSA226 | 0.12 |
| BF292 | 0.10 | MPSA228 | 0.12 |
| BF293 | 0.10 | MPSA230 | 0.12 |
| BF294 | 0.10 | MPSA232 | 0.12 |
| BF295 | 0.10 | MPSA234 | 0.12 |
| BF296 | 0.10 | MPSA236 | 0.12 |
| BF297 | 0.10 | MPSA238 | 0.12 |
| BF298 | 0.10 | MPSA240 | 0.12 |
| BF299 | 0.10 | MPSA242 | 0.12 |
| BF300 | 0.10 | MPSA244 | 0.12 |
| BF301 | 0.10 | MPSA246 | 0.12 |
| BF302 | 0.10 | MPSA248 | 0.12 |
| BF303 | 0.10 | MPSA250 | 0.12 |
| BF304 | 0.10 | MPSA252 | 0.12 |
| BF305 | 0.10 | MPSA254 | 0.12 |
| BF306 | 0.10 | MPSA256 | 0.12 |
| BF307 | 0.10 | MPSA258 | 0.12 |
| BF308 | 0.10 | MPSA260 | 0.12 |
| BF309 | 0.10 | MPSA262 | 0.12 |
| BF310 | 0.10 | MPSA264 | 0.12 |
| BF311 | 0.10 | MPSA266 | 0.12 |
| BF312 | 0.10 | MPSA268 | 0.12 |
| BF313 | 0.10 | MPSA270 | 0.12 |
| BF314 | 0.10 | MPSA272 | 0.12 |
| BF315 | 0.10 | MPSA274 | 0.12 |
| BF316 | 0.10 | MPSA276 | 0.12 |
| BF317 | 0.10 | MPSA278 | 0.12 |
| BF318 | 0.10 | MPSA280 | 0.12 |
| BF319 | 0.10 | MPSA282 | 0.12 |
| BF320 | 0.10 | MPSA284 | 0.12 |
| BF321 | 0.10 | MPSA286 | 0.12 |
| BF322 | 0.10 | MPSA288 | 0.12 |
| BF323 | 0.10 | MPSA290 | 0.12 |
| BF324 | 0.10 | MPSA292 | 0.12 |
| BF325 | 0.10 | MPSA294 | 0.12 |
| BF326 | 0.10 | MPSA296 | 0.12 |
| BF327 | 0.10 | MPSA298 | 0.12 |
| BF328 | 0.10 | MPSA300 | 0.12 |
| BF329 | 0.10 | MPSA302 | 0.12 |
| BF330 | 0.10 | MPSA304 | 0.12 |
| BF331 | 0.10 | MPSA306 | 0.12 |
| BF332 | 0.10 | MPSA308 | 0.12 |
| BF333 | 0.10 | MPSA310 | 0.12 |
| BF334 | 0.10 | MPSA312 | 0.12 |
| BF335 | 0.10 | MPSA314 | 0.12 |
| BF336 | 0.10 | MPSA316 | 0.12 |
| BF337 | 0.10 | MPSA318 | 0.12 |
| BF338 | 0.10 | MPSA320 | 0.12 |
| BF339 | 0.10 | MPSA322 | 0.12 |
| BF340 | 0.10 | MPSA324 | 0.12 |
| BF341 | 0.10 | MPSA326 | 0.12 |
| BF342 | 0.10 | MPSA328 | 0.12 |
| BF343 | 0.10 | MPSA330 | 0.12 |
| BF344 | 0.10 | MPSA332 | 0.12 |
| BF345 | 0.10 | MPSA334 | 0.12 |
| BF346 | 0.10 | MPSA336 | 0.12 |
| BF347 | 0.10 | MPSA338 | 0.12 |
| BF348 | 0.10 | MPSA340 | 0.12 |
| BF349 | 0.10 | MPSA342 | 0.12 |
| BF350 | 0.10 | MPSA344 | 0.12 |
| BF351 | 0.10 | MPSA346 | 0.12 |
| BF352 | 0.10 | MPSA348 | 0.12 |
| BF353 | 0.10 | MPSA350 | 0.12 |
| BF354 | 0.10 | MPSA352 | 0.12 |
| BF355 | 0.10 | MPSA354 | 0.12 |
| BF356 | 0.10 | MPSA356 | 0.12 |
| BF357 | 0.10 | MPSA358 | 0.12 |
| BF358 | 0.10 | MPSA360 | 0.12 |
| BF359 | 0.10 | MPSA362 | 0.12 |
| BF360 | 0.10 | MPSA364 | 0.12 |
| BF361 | 0.10 | MPSA366 | 0.12 |
| BF362 | 0.10 | MPSA368 | 0.12 |
| BF363 | 0.10 | MPSA370 | 0.12 |
| BF364 | 0.10 | MPSA372 | 0.12 |
| BF365 | 0.10 | MPSA374 | 0.12 |
| BF366 | 0.10 | MPSA376 | 0.12 |
| BF367 | 0.10 | MPSA378 | 0.12 |
| BF368 | 0.10 | MPSA380 | 0.12 |
| BF369 | 0.10 | MPSA382 | 0.12 |
| BF370 | 0.10 | MPSA384 | 0.12 |
| BF371 | 0.10 | MPSA386 | 0.12 |
| BF372 | 0.10 | MPSA388 | 0.12 |
| BF373 | 0.10 | MPSA390 | 0.12 |
| BF374 | 0.10 | MPSA392 | 0.12 |
| BF375 | 0.10 | MPSA394 | 0.12 |
| BF376 | 0.10 | MPSA396 | 0.12 |
| BF377 | 0.10 | MPSA398 | 0.12 |
| BF378 | 0.10 | MPSA400 | 0.12 |
| BF379 | 0.10 | MPSA402 | 0.12 |
| BF380 | 0.10 | MPSA404 | 0.12 |
| BF381 | 0.10 | MPSA406 | 0.12 |
| BF382 | 0.10 | MPSA408 | 0.12 |
| BF383 | 0.10 | MPSA410 | 0.12 |
| BF384 | 0.10 | MPSA412 | 0.12 |
| BF385 | 0.10 | MPSA414 | 0.12 |
| BF386 | 0.10 | MPSA416 | 0.12 |
| BF387 | 0.10 | MPSA418 | 0.12 |
| BF388 | 0.10 | MPSA420 | 0.12 |
| BF389 | 0.10 | MPSA422 | 0.12 |
| BF390 | 0.10 | MPSA424 | 0.12 |
| BF391 | 0.10 | MPSA426 | 0.12 |
| BF392 | 0.10 | MPSA428 | 0.12 |
| BF393 | 0.10 | MPSA430 | 0.12 |
| BF394 | 0.10 | MPSA432 | 0.12 |
| BF395 | 0.10 | MPSA434 | 0.12 |
| BF396 | 0.10 | MPSA436 | 0.12 |
| BF397 | 0.10 | MPSA438 | 0.12 |
| BF398 | 0.10 | MPSA440 | 0.12 |
| BF399 | 0.10 | MPSA442 | 0.12 |
| BF400 | 0.10 | MPSA444 | 0.12 |
| BF401 | 0.10 | MPSA446 | 0.12 |
| BF402 | 0.10 | MPSA448 | 0.12 |
| BF403 | 0.10 | MPSA450 | 0.12 |
| BF404 | 0.10 | MPSA452 | 0.12 |
| BF405 | 0.10 | MPSA454 | 0.12 |
| BF406 | 0.10 | MPSA456 | 0.12 |
| BF407 | 0.10 | MPSA458 | 0.12 |
| BF408 | 0.10 | MPSA460 | 0.12 |
| BF409 | 0.10 | MPSA462 | 0.12 |
| BF410 | 0.10 | MPSA464 | 0.12 |
| BF411 | 0.10 | MPSA466 | 0.12 |
| BF412 | 0.10 | MPSA468 | 0.12 |
| BF413 | 0.10 | MPSA470 | 0.12 |
| BF414 | 0.10 | MPSA472 | 0.12 |
| BF415 | 0.10 | MPSA474 | 0.12 |
| BF416 | 0.10 | MPSA476 | 0.12 |
| BF417 | 0.10 | MPSA478 | 0.12 |
| BF418 | 0.10 | MPSA480 | 0.12 |
| BF419 | 0.10 | MPSA482 | 0.12 |
| BF420 | 0.10 | MPSA484 | 0.12 |
| BF421 | 0.10 | MPSA486 | 0.12 |
| BF422 | 0.10 | MPSA488 | 0.12 |
| BF423 | 0.10 | MPSA490 | 0.12 |
| BF424 | 0.10 | MPSA492 | 0.12 |
| BF425 | 0.10 | MPSA494 | 0.12 |
| BF426 | 0.10 | MPSA496 | 0.12 |
| BF427 | 0.10 | MPSA498 | 0.12 |
| BF428 | 0.10 | MPSA500 | 0.12 |
| BF429 | 0.10 | MPSA502 | 0.12 |
| BF430 | 0.10 | MPSA504 | 0.12 |
| BF431 | 0.10 | MPSA506 | 0.12 |
| BF432 | 0.10 | MPSA508 | 0.12 |
| BF433 | 0.10 | MPSA510 | |

INCREASE YOUR PROFITS IMPROVE YOUR SERVICE WITH RELIABLE COST EFFECTIVE TEST EQUIPMENT

LEADER LCT-910A C.R.T. TESTER-REJUVENATOR

Our top selling instrument is designed to readily test the various characteristics and rejuvenation of both colour and B/W C.R.T.s.

- * Tests for shorts and leakage between electrodes.
- * Tests cathode emission characteristics.
- * Separately checks condition of guns.
- * Removal of shorts and leakage between electrodes.
- * Checks heater warm-up characteristics.
- * Rejuvenation of low emission cathodes with automatic timing.
- * Super rejuvenation with manual control.
- * Complete with tube base adaptors. Size: H 230mm W 330mm D 120mm.

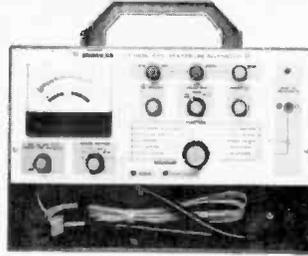


PRICE £186 + £27.90 VAT

LOPT TESTER

BK's REVOLUTIONARY DYNAMIC 'LOPT' TESTER

Revolutionary L.O.P.T. tester. Operates in dynamic mode which actually tests the L.O.P.T. under high voltage conditions without de-soldering or removal. Size 75x100x40 mm. Supply 240V AC


PRICE £25.99 + £3.VAT

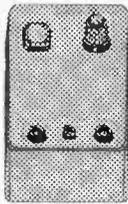


CRT TESTER-REJUVENATOR

BK's C.R.T. TESTER-REJUVENATOR Tests and rejuvenates blue, green & red guns separately. Fitted with delta and P.I.L. sockets. Compact size 120x65x60 mm. Supply 240V AC

PRICE £32.00 + £4.80VAT

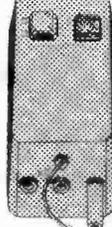

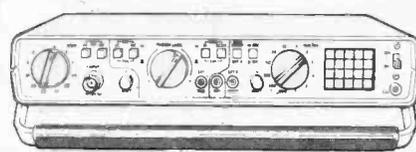THE VERY LATEST SC110A LOW POWER, FULLY PORTABLE OSCILLOSCOPE.



The new Thandar SC110A represents a breakthrough in oscilloscope development. The SC110A is ONLY TWO INCHES thick and weighs under two pounds, yet retains the standard features and controls of a bench oscilloscope. **FITS IN A BRIEFCASE**

Full Sized Performance

- * 10 MHz bandwidth
- * Full trigger facilities are provided including TV frame, or TV filtering.
- * Runs on 4 to 10V DC via disposable batteries, re-chargeable cells, or AC adaptor.
- * Size 255mm x 148mm x 50mm.

PRICE £165.00 + £24.75 VAT

Accessories: Carry Case £5.95 + £0.89 V.A.T.

- * 1 Probe £7.50 + £1.13 V.A.T.
- * 10 Probe £8.50 + £1.28 V.A.T.
- * 1/x x 10 Switched Probe £10.50 + £1.58 V.A.T.
- * AC Adaptor £6.95 + £1.04 V.A.T.

ALSO AVAILABLE
Analogue Multimeters
Digital Multimeters
Oscilloscopes
Signal Generators
Digital Frequency Meters
Pattern Generators
CRT Tester/Rejuvenator
T.V. Field Strength Meter
Digital Capacitance Meter
LARGE S.A.E.
FOR COMPLETE LIST.

LEADER HIGH VOLTAGE METER EHT PROBE

Measures up to 40 K.V. D.C. with **SAFETY BUILT IN METER**




PRICE £28.00 + £4.49 VAT

*** FULLY GUARANTEED**

HAMEG HM 203-5 20MHz DUAL TRACE OSCILLOSCOPE

SPECIFICATION:

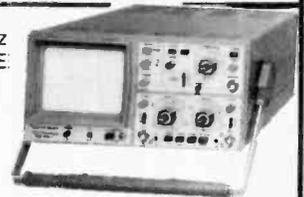- * BANDWIDTH DC-20MHz
- * SENSITIVITY CH1, CH2 2mV-50V/DIV
- * TIMEBASE 40ns to 0.25 CM
- * TRIGGER DC-40MHz Auto-Normal-TV
- * CALIBRATION OUTPUT
- * CH1 ADD AND INVERT FACILITY
- * ALT/CHOP SWITCH
- * LARGE RECTANGULAR SCREEN 8 x 10 cms.
- * BUILT IN SEMICONDUCTOR COMP. TESTER
- * SIZE 285mm x 145mm x 380mm.
- * SUPPLY 110-125-220-240V AC 50-60Hz



WITH COMPONENT TESTER

PRICE £264.00 + £39.60 VAT
Optional probes as above

2 YEAR WARRANTY

U.K. Post Paid, Export orders welcome, please deduct V.A.T. and enquire for Overseas carriage cost. Barclaycard/Access orders welcome, or Cheque, Bank Draft, etc, with order please. Large S.A.E. for technical leaflets of complete range. Delivery normally within 7 days.




B. K. ELECTRONICS Dept. 'T'

UNIT 5, COMET WAY, SOUTHEON-ON-SEA, ESSEX. SS2 6TR TEL: 0702-527572



| | | | | | | | | | | | |
|------------|------------|-------------|-------------|-------------|--------------|------------|----------|-----------|--------------|---------------|--------------|
| AA117 9p | BC328 6p | BFX85 20p | TIP112 54p | 2N3773 100p | BYX70500 31p | DY802 45p | 4042 55p | 7482 70p | 74LS367 52p | HA-1368 190p | TCA270 40p |
| AA119 9p | BC575 15p | BFX87 15p | TIP115 45p | 2N3819 25p | BYX70800 36p | ECC82 40p | 4043 87p | 7485 45p | 74LS389 85p | LA-1201 120p | TCA800 80p |
| AA332 9p | BCY32 150p | BFX88 15p | TIP117 56p | 2N3866 68p | BYX71600 80p | ECC83 40p | 4044 66p | 7486 28p | 74LS570 130p | LA-1365 170p | TCA940 85p |
| AC107 25p | BCY33 180p | BFY50 14p | TIP120 43p | 2N4031 25p | OA47 6p | ECC84 40p | 4047 65p | 7489 100p | | LA-3301 180p | TDA1170 90p |
| AC126 17p | BCY34 150p | BFY51 14p | TIP121 46p | 2N4036 25p | OA90 4p | ECC85 40p | 4048 49p | 7490 38p | | LA-3350 150p | TDA1412 60p |
| AC127 15p | BCY42 180p | BFY52 14p | TIP122 47p | 2N4037 25p | OA91 4p | ECC86 40p | 4049 45p | 7491 38p | | LA-4032 180p | TDA2002 80p |
| AC128 15p | BCY56 18p | BFY56 25p | TIP125 47p | 2N4443 76p | OA200 7p | ECC88 52p | 4050 40p | 7493 35p | | LA-4032 180p | TDA2003 180p |
| AC128K 23p | BCY70 16p | BFY57 25p | TIP126 56p | 2N4444 76p | OA202 7p | ECL80 52p | 4051 62p | 7495 48p | | LA-4051 250p | TDA2020 140p |
| AC141K 18p | BCY71 16p | BFY54 25p | TIP127 56p | 2N4061 20p | IN914 2p | ECL82 59p | 4052 61p | 7497 30p | | LA-4101 140p | TDA2030 140p |
| AC142K 22p | BCY72 16p | BFY90 14p | TIP147 100p | 2N5294 30p | IN4001 4p | ECL84 87p | 4053 61p | 74107 52p | | LA-4101 140p | TDA2522 90p |
| AC153K 23p | BD115 26p | BR100 14p | TIP2955 34p | 2N5296 30p | IN4002 4p | | 4054 85p | 74111 52p | | LA-4420 150p | TDA2530 90p |
| AC176 18p | BD124P 50p | BSX20 15p | 2N6106 38p | 2N6106 40p | IN4003 4p | ECL85 87p | 4055 90p | 74116 85p | | LA-4430 150p | TDA2532 90p |
| AC176K 20p | BD124 110p | BT106 90p | 2N6107 40p | 2N6107 40p | IN4004 4p | ECL86 45p | 4056 85p | 74119 85p | | LA-4101 140p | TDA2030 140p |
| AC178K 15p | BD128 35p | BT109 90p | 2N6108 40p | 2N6108 40p | IN4005 4p | ECL87 53p | 4057 85p | 74122 40p | | LA-4101 140p | TDA2522 90p |
| AC187K 20p | BD131 25p | BT116 100p | TIS44 40p | 3N128 55p | IN4006 4p | ECL88 34p | 4068 42p | 74123 20p | | NE555 20p | TDA2530 90p |
| AC188 17p | BD132 25p | BT119 100p | TIS61 15p | 3N143 65p | IN4007 5p | ECL89 43p | 4068 42p | 74125 20p | | NE566 40p | TDA2690 80p |
| AC188K 23p | BD135 20p | BU120 100p | TIS88A 45p | 3N143 65p | IN4148 2p | EFL183 45p | 4069 27p | 74126 25p | | AN-214P 200p | SN7603N 140p |
| ACY18 48p | BD136 20p | BU104 100p | TIS93 15p | 3N143 65p | IN4148 2p | EFL184 53p | 4070 27p | 74127 25p | | AN-240P 150p | SN7603N 140p |
| ACY19 48p | BD137 20p | BU105 80p | TIS91 18p | 3N143 65p | IN4148 2p | EFL184 53p | 4071 27p | 74141 55p | | AN-380 120p | SN7603N 140p |
| AD142 48p | BDY92 100p | BU108 100p | TIS93 18p | 3N143 65p | IN4148 2p | EFL184 53p | 4072 27p | 74145 70p | | AN-7110 150p | SN7603N 140p |
| AD149 48p | BD138 30p | BU111 140p | TK30 25p | 25A73 32p | IN5402 10p | EY87 31p | 4073 27p | 74155 45p | | AN-7114 170p | SN76110N 70p |
| AD161 22p | BD139 20p | BU126 70p | TK1010 88p | 25A198 32p | IN5403 11p | PC7 100p | 4074 27p | 74155 45p | | AN-7115 180p | SN76115 70p |
| AD162 22p | BD144 90p | BU204 76p | VN10KM 60p | 25A203 30p | IN5405 12p | PC85 42p | 4076 70p | 74157 45p | | AN-7120 150p | SN7800D 52p |
| AF125 25p | BD150 30p | BU208 75p | VN46AF 88p | 25B54 25p | IN5406 13p | PCF80 52p | 4077 27p | 74160 50p | | AY3-1250 300p | TA-7120 110p |
| AF127 25p | BD151 30p | BU208 75p | VN88AF 115p | 25B85 22p | IN5407 13p | PCF80 52p | 4078 27p | 74161 50p | | AY3-8810 360p | TA-7200 200p |
| AF139 22p | BD157 38p | BU208A 80p | VN89AF 110p | 25B85 22p | IN5408 13p | PCF80 52p | 4082 27p | 74173 50p | | AY3-8912 400p | TA-7203 240p |
| AF239 22p | BD166 30p | BU208B 80p | TK1010 88p | 25C480 21p | IN5409 13p | PCF80 52p | 4083 27p | 74174 50p | | AY3-8912 400p | TA-7203 240p |
| AL112 70p | BD175 30p | BU236 120p | TK1010 88p | 25C480 21p | IN5410 13p | PCF80 52p | 4084 27p | 74175 50p | | AY3-8912 400p | TA-7203 240p |
| AL113 80p | BD176 30p | BU236 120p | TK1010 88p | 25C480 21p | IN5411 13p | PCF80 52p | 4085 27p | 74176 50p | | AY3-8912 400p | TA-7203 240p |
| AS215 100p | BD177 32p | BU240 76p | TK1010 88p | 25C480 21p | IN5412 13p | PCF80 52p | 4086 27p | 74177 50p | | AY3-8912 400p | TA-7203 240p |
| AS217 100p | BD181 45p | BU408 100p | TK1010 88p | 25C480 21p | IN5413 13p | PCF80 52p | 4087 27p | 74178 50p | | AY3-8912 400p | TA-7203 240p |
| AU110 110p | BD182 60p | BU408 100p | TK1010 88p | 25C480 21p | IN5414 13p | PCF80 52p | 4088 27p | 74179 50p | | AY3-8912 400p | TA-7203 240p |
| AY102 180p | BD183 60p | BU408 100p | TK1010 88p | 25C480 21p | IN5415 13p | PCF80 52p | 4089 27p | 74180 50p | | AY3-8912 400p | TA-7203 240p |
| AY106 180p | BD183 60p | BU408 100p | TK1010 88p | 25C480 21p | IN5416 13p | PCF80 52p | 4090 27p | 74181 50p | | AY3-8912 400p | TA-7203 240p |
| BA145 10p | BD202 38p | MJ2500 100p | TK1010 88p | 25C480 21p | IN5417 13p | PCF80 52p | 4091 27p | 74182 50p | | AY3-8912 400p | TA-7203 240p |
| BA148 10p | BD203 42p | MJ2501 110p | TK1010 88p | 25C480 21p | IN5418 13p | PCF80 52p | 4092 27p | 74183 50p | | AY3-8912 400p | TA-7203 240p |
| BA154 13p | BD222 31p | MJ2502 110p | TK1010 88p | 25C480 21p | IN5419 13p | PCF80 52p | 4093 27p | 74184 50p | | AY3-8912 400p | TA-7203 240p |
| BB101 13p | BD225 31p | MJ3000 115p | TK1010 88p | 25C480 21p | IN5420 13p | PCF80 52p | 4094 27p | 74185 50p | | AY3-8912 400p | TA-7203 240p |
| BB103 16p | BD232 31p | MJ3001 115p | TK1010 88p | 25C480 21p | IN5421 13p | PCF80 52p | 4095 27p | 74186 50p | | AY3-8912 400p | TA-7203 240p |
| BB105B 16p | BD234 32p | MJE23A 30p | TK1010 88p | 25C480 21p | IN5422 13p | PCF80 52p | 4096 27p | 74187 50p | | AY3-8912 400p | TA-7203 240p |
| BB205B 24p | BD237 21p | MJE30A 30p | TK1010 88p | 25C480 21p | IN5423 13p | PCF80 52p | 4097 27p | 74188 50p | | AY3-8912 400p | TA-7203 240p |
| BC107 7p | BD238 24p | MJE350 30p | TK1010 88p | 25C480 21p | IN5424 13p | PCF80 52p | 4098 27p | 74189 50p | | AY3-8912 400p | TA-7203 240p |
| BC108 7p | BD243 28p | MJE520 30p | TK1010 88p | 25C480 21p | IN5425 13p | PCF80 52p | 4099 27p | 74190 50p | | AY3-8912 400p | TA-7203 240p |
| BC109 7p | BD243 28p | MJE295K 90p | TK1010 88p | 25C480 21p | IN5426 13p | PCF80 52p | 4100 27p | 74191 50p | | AY3-8912 400p | TA-7203 240p |
| BC115 10p | BD235 38p | OC28 100p | TK1010 88p | 25C480 21p | IN5427 13p | PCF80 52p | 4101 27p | 74192 50p | | AY3-8912 400p | TA-7203 240p |
| BC118 11p | BD236 38p | OC29 80p | TK1010 88p | 25C480 21p | IN5428 13p | PCF80 52p | 4102 27p | 74193 50p | | AY3-8912 400p | TA-7203 240p |
| BC140 19p | BD237 40p | OC35 100p | TK1010 88p | 25C480 21p | IN5429 13p | PCF80 52p | 4103 27p | 74194 50p | | AY3-8912 400p | TA-7203 240p |
| BC141 19p | BD238 40p | OC36 120p | TK1010 88p | 25C480 21p | IN5430 13p | PCF80 52p | 4104 27p | 74195 50p | | AY3-8912 400p | TA-7203 240p |
| BC142 19p | BD239 40p | OC37 100p | TK1010 88p | 25C480 21p | IN5431 13p | PCF80 52p | 4105 27p | 74196 50p | | AY3-8912 400p | TA-7203 240p |
| BC143 19p | BD240 40p | OC45 80p | TK1010 88p | 25C480 21p | IN5432 13p | PCF80 52p | 4106 27p | 74197 50p | | AY3-8912 400p | TA-7203 240p |
| BC147 19p | BD241 40p | OC71 30p | TK1010 88p | 25C480 21p | IN5433 13p | PCF80 52p | 4107 27p | 74198 50p | | AY3-8912 400p | TA-7203 240p |
| BC148 19p | BD242 40p | OC72 50p | TK1010 88p | 25C480 21p | IN5434 13p | PCF80 52p | 4108 27p | 74199 50p | | AY3-8912 400p | TA-7203 240p |
| BC149 19p | BD243 40p | OC200 180p | TK1010 88p | 25C480 21p | IN5435 13p | PCF80 52p | 4109 27p | 74200 50p | | AY3-8912 400p | TA-7203 240p |
| BC157 19p | BD244 40p | R2008B 80p | TK1010 88p | 25C480 21p | IN5436 13p | PCF80 52p | 4110 27p | 74201 50p | | | |

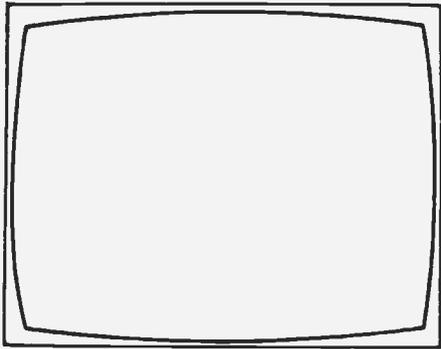

TELEVISION

Fifty Years of Uproar

It seems that some things never change. Since the dawn of TV, we've been plagued by an apparently endless series of standards battles. Back in 1935 in the UK it was a question of 240 or 405 lines, amongst other things. In order to come to a decision on this the government of the day in 1934 set up a Royal Commission under Lord Selsden to recommend which system to adopt. The Commission duly reported in April 1935 but felt itself unable to come to a definite conclusion, which was probably fair enough. Work on the two contending systems (Baird and Marconi-EMI) was still continuing apace and producing worthwhile improvements. Would it be fair or right to suddenly halt the race? Instead the Commission recommended that a public service should start as soon as possible (in order to avoid further delay) using both systems alternately week by week, which is what duly happened in November 1936. While the Marconi-EMI system would appear to have been the obvious choice now, with its much greater number of lines, it must at the time, with the small, primitive tubes and circuitry of the period, have been rather less than obvious what to do for the best. And of course the rivals didn't exactly help in the task of arriving at an objective decision. It's usually possible to pull the wool over people's eyes: with a completely new technology the scope for doing this is great indeed!

Much the same sort of confusion reigned on the other side of the Atlantic – and took even longer to resolve. The Federal Communications Commission was set up in June 1934 to deal with the increasing demands on broadcasting frequencies – up to that time anything above 30MHz was free to experimenters to do what they liked with. One of the first things the FCC did was to establish TV bands – two, 42-56MHz and 60-86MHz. RCA had been transmitting experimental all-electronic TV as early as 1933 – with 240 lines, moving to 343 in 1936. By 1936 the US Radio Manufacturers' Association had proposed 441 lines, though the first demonstration that this was practical was not given until 1937 – by Philco. The industry was not united however and the FCC was no more prepared than the Selsden Commission to come to a decision on its own. There thus followed a period of experimental services that continued until 1940, when the RMA set up the National Television Standards Committee (NTSC) to establish an agreed standard. To be fair to both Selsden and the FCC, they were not presented with easy choices and the consequences of making wrong decisions could have been serious.

The Americans didn't have quite so much difficulty when it came to a decision on colour, the next major step, since by that time the NTSC had been established. Contrast this with what happened in Europe a decade later! There was to be a right battle of the standards in Europe in the early sixties, between NTSC, PAL, SECAM and one or two other proposals. And none of the systems would stand still. They kept on evolving as Europe decided, if that's the right word, that a common standard was not to be. In retrospect one feels that there was probably rather an unnecessary amount of smoke and din as this battle raged. Both PAL and SECAM have turned out to be perfectly good systems. Would it have made much difference if the UK had adopted SECAM? Probably not. But of course there was commercial interest, not to mention national pride, present to make the matter of coming to a decision difficult.

If anything the pace of these standards confrontations seems to have increased in recent times. We've had teletext systems, VCR formats and TV stereo sound systems to keep the pot boiling. At least teletext wasn't a problem in the UK: the development work was done by the broadcasting authorities who got together at an early stage to agree upon a joint standard. Getting this accepted elsewhere has been a different matter however. As alternatives were proposed, the FCC soon gave up any attempt at making a recommendation, suggesting instead that broadcasters decide for themselves what to do. That hasn't exactly helped to get teletext started in N. America, since setmakers are reluctant to produce a multiplicity of decoders for different systems and public confidence is lacking.

The Japanese, having avoided broadcast standards battles by adopting NTSC after the war, have more recently had their own standards battle in the VCR field: This is strange in a way: the Ministry of International Trade and Industry usually manages to achieve some sort of industrial consensus. On this occasion however it failed to impose itself on the rivalry between Matsushita and Sony.

For the time being the stereo TV sound standards contest seems to be a bit of a non-event. Right now interest has moved to standards for satellite TV broadcasting – not so much in the UK, where after an initial skirmish between extended-PAL and MAC the latter system has been accepted, but in Europe where despite EBU backing for MAC there's no sign at present of any agreement. It's not necessary to have a common European standard of course, but it would simplify matters for everyone if one could be agreed upon.

Before too long we shall probably find ourselves in the middle of a battle about high-definition TV standards. The Japanese have put a lot of work into the NHK 1,125-line system, which has been tried out via satellite. From a UK point of view however this development will have to wait till more broadcasting bandwidth becomes available or we find a signal companding/expanding system that's cheap.

Why does the world of TV have to lose so much sweat over these endless debates? Couldn't some nice committees of "wise men" sort things out? If only things were that simple! In the end it's the public that wins or loses from all this warring. At least it keeps the authorities on their toes, probably to everyone's benefit.

EDITOR

John A. Reddihough

ADVERTISEMENT MANAGER

Roy Smith
01-261 6671

CLASSIFIED ADVERTISEMENTS

Barbara Blake
01-261 5897

Vintage TV: The Mighty RGDs

Chas E. Miller

The picturesque Shropshire town of Bridgnorth has many claims to fame: it has a most remarkable leaning tower – the remains of an old castle – that overlooks the headquarters of one of Britain's largest private steam railways; and its unusual split levels, called High Town and Low Town, are connected by one of the few funicular railways to be found away from seaside resorts. It has also at various times played host to two of the best known names in radio – curiously enough, they were once rivals in the high-quality market. These two are Decca and RGD. The former is still going strong, though now under the ownership of Tatung. RGD is all but forgotten however, though it survived for several years after the demise of the original firm in the form of badge-engineered sets from first Regentone then STC and ITT. RGD was nevertheless at one time well established at the top end of the quality market, along with HMV and Decca.

The Radiogramophone Development Company was founded in the 1930s to do exactly what its title suggested. By the end of the decade its products were justly famed, combining advanced radio and record-player sections with magnificent cabinet work. After the hiatus of the war years the theme was revived: its zenith was probably reached with a model introduced in 1948 costing almost £300 – at that time you could have bought a good van to deliver the radiogram for around £350! It was only natural that RGD should diversify into television, which was just beginning to hint at its eventual domination of home entertainment and still called for cabinets that were “pieces of furniture” rather than being functional. Typical then was the RGD Model B2351T, a large console set with a 12in. tube designed for use in the Sutton Coldfield channel 4 area. A matching record-player unit was available if required, also a built-in radio adaptor that gave a choice of four preset stations.

A good deal of thought had been given to ease of service, one result being that you could swing the front of the cabinet up and away for simple access to the c.r.t. and other components.

Basic Circuitry

A superhet circuit was employed for vision and sound reception, the total number of valves in the chassis for all purposes being 23. In addition a solitary Westector diode was used as a sound interference suppressor. The Westector was not a crystal diode but a miniature metal rectifier developed in the 30s by the Westinghouse Company. A power supply unit equipped with a large double-wound transformer supplied h.t. voltages of 250V, 260V, 330V and 380V for various purposes. The transformer's heater windings for the two h.t. rectifiers and the c.r.t. were tapped to give a choice of voltages so that alternative types could be used – that was a time when valves and tubes were in short supply. The e.h.t. was generated by an EL33 r.f. oscillator with an overwinding on the transformer feeding an EY51 rectifier. This circuit produced 7kV, and in the days before Aquadag tube coating became general high-voltage capacitors had to be used to smooth the e.h.t. These could hold a charge that called for

respectful treatment!

The aerial input was transformer coupled to a straight 6F13 r.f. pentode operating as a common vision/sound signal amplifier and was then passed to a second 6F13 that did duty as a frequency changer – in conjunction with a 6L18 triode oscillator. Two 6F13 i.f. amplifiers were followed by a 6D1 diode demodulator.

The Unusual Bits

Now while most of the circuitry in the B2351T was reasonably straightforward and conventional, the video coupling and interference suppression arrangements were decidedly quirky. The arrangement is shown in Fig. 1. V11 (6F14) is the video amplifier, whose response is tailored by L3 and C19. The video load is split between R26 and R27, with the result that only half of the available video signal was fed via C22 to the grid of the c.r.t. The entire video signal was fed to the sync separator, via C23 and V15A. The idea of this odd arrangement was to ensure that an adequate level of sync signal was fed to the sync separator whatever the setting of the contrast control, which set the first i.f. amplifier's cathode bias.

V15A was biased to conduct on the sync tips, acting as a limiter and in effect as the sync separator, feeding the following 6F14 which RGD referred to as the sync separator but which would more accurately be called a sync pulse amplifier. V15B provided d.c. restoration, and since both sections of V15 conducted during the sync pulses they also acted as the video d.c. restorer, linked to the c.r.t.'s grid via R35.

Now to the ingenious vision interference limiter circuit which used the two diodes in V14 (6D2). The video signal was coupled via C25 to the anode of V14B which was biased so that it conducted when an interference spike above peak white appeared. As a result, it passed a pulse via C26 to the c.r.t.'s cathode to cancel the pulse at the c.r.t.'s grid. R63 provided a variable bias for V14B's anode while V14A produced a bias voltage dependent on signal level for V14B's cathode. This was done by switching V14A on during the line sync pulse period by means of a line-frequency pulse coupled via C37 – the sync pulse tip is a measure of the signal level at the anode of V11. All rather ingenious and akin to some of the a.g.c. techniques that were to come much later. If you didn't want this little lot to work you simply opened switch S2.

A small pulse tapped from the cathode of the field oscillator was fed to the c.r.t.'s cathode via C24 for field flyback suppression – an early example of a soon to become general practice.

The Rest of the Set

The sound i.f. signal was tapped from the cathode of the first i.f. amplifier and fed to a two-stage amplifier employing 6F15 vari-mu pentodes. Another 6D2 acted as detector and a.g.c. rectifier. An unusual feature of the sound channel was the use of a variable cathode bias resistor in the first sound i.f. stage as the volume control instead of a control acting at a.f. – an archaic system even

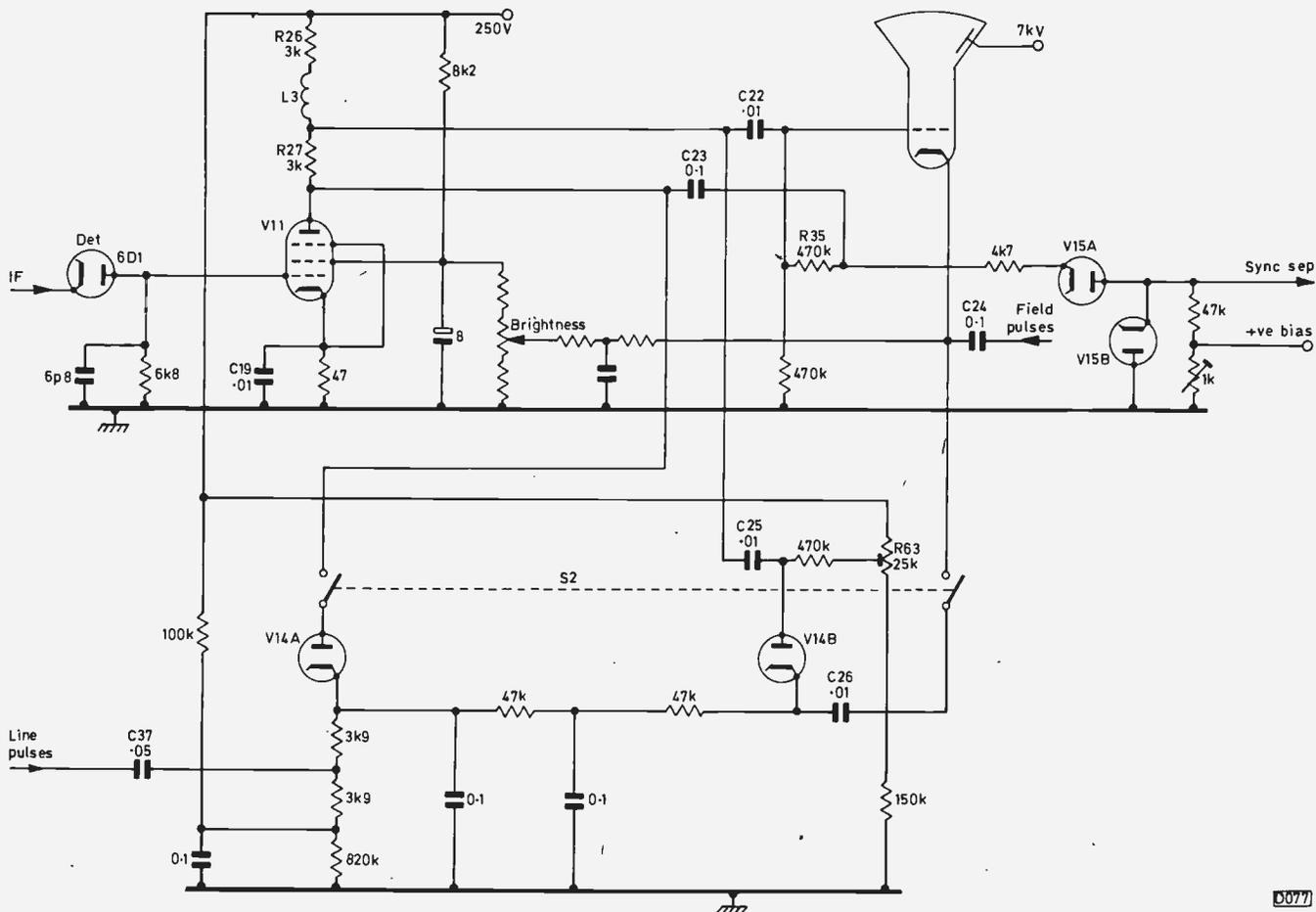


Fig. 1: The video and vision interference limiter circuitry used in the RGD B2351T.

then. The gain was reckoned to be adequate enough for it to be unnecessary to use an a.f. amplifier prior to the 6P25 high-slope audio output tetrode.

The timebases were straightforward but care was taken with the sync signal. The first 6F14 sync pulse separator/amplifier was followed by a 6F13 that amplified and shaped the field sync pulses. Both timebase generator stages used gas-discharge triodes (thyatron) whose initial advantage of simplicity tended to be marred by erratic operation as they aged. The time-constant for a thyatron oscillator was set by an RC network between the anode and cathode, working in conjunction with a hold control that was connected to chassis.

The line and field output stages were very similar, owing much to contemporary a.f. designs, with simple two-winding output transformers. Considering that line output valves – an EL38 in this case – had had to be specially developed to withstand the high flyback voltage that appeared at the anode, it took a surprisingly long time for designers to cotton on to the idea of flyback derived e.h.t.! The circuitry in these output stages looks very sparse to the modern eye. The width and height controls consisted of variable cathode bias resistors while line linearity was controlled by means of a variable RC network connected across the scan coils.

The c.r.t. was electromagnetically focused, the coil and its variable shunt resistor being connected in series with the h.t. supply, on the negative side, so that the entire h.t. current flowed through them. Whether this made for better focus stability is open to question: possibly the large current flowing through the coil made it less sensitive to the small variations caused by changes in the operating conditions of individual valves.

The B2351T was capable of providing long and faithful service. I remember one that continued to soldier on after fifteen years use. Many engineers who had to deal with the older types of set will no doubt agree that a.c. only operation, where all the valves have low-voltage heaters, made for longevity. In addition, grid modulation of the c.r.t., with the cathode at or near the heater voltage, helped to prolong its useful life. In the vintage years c.r.t. heater-cathode shorts were fairly common, and where cathode modulation was employed the picture degradation could be serious enough to necessitate tube replacement. It was some time before low-capacitance heater transformers were introduced to alleviate the problem. In the intervening period it was not unknown for engineers to make up a small phase-inverting stage, built on the classic tobacco-tin chassis, to enable the drive to be transferred from the cathode to the grid. This sort of thing was justified since the cost of a tube in those days was much more in real terms than that of a modern colour c.r.t.

The 1700/1800

Grid modulation was one of several design features that were retained in the succeeding 1700/1800 series of models that were prefixed B, H or L to signify use in the Birmingham, Holm Moss or London areas. Changes in the receiver section included the use of a 12AT7 double-triode as mixer and local oscillator, with the sound signal tapped from the mixer's anode circuit. There was only one stage of sound i.f. amplification, but this time a stage of a.f. amplification was included between the detector and the output valve. A simple single-diode vision interference

limiter circuit was used, but the video/sync coupling arrangements were the same as in the B2351T. A single sync separator/amplifier pentode was used but the timebases were otherwise much the same as before – though flyback e.h.t. this time put in an appearance. It was not obtained from an overwinding on the line output transformer however: instead, two EY51s were connected in a voltage-doubling circuit fed from the anode of the EL38 line output valve. This arrangement produced 6.5kV. The power supply was considerably simplified, with metal rectifiers powered directly from the mains used for h.t. rectification. A transformer was included, but was used for the heater supplies and mains adjustment only.

Demise of RGD

Regular readers of this column will know that I have little love for the live-chassis type of circuit, not least

because a manufacturer's resort to this nasty economy so often presaged its demise. Regretfully, this proved to be the case with RGD. It was soon to be taken over by Regentone, and the 1953 and subsequent RGD models were fitted with Plessey chassis. Eventually Regentone itself succumbed and became part of STC. It was during this latter period that the RGD brand was briefly revived, with an advertising campaign that majored on Really Great Developments!

With hindsight, it's doubtful whether the original RGD firm could have survived much longer than it did, whatever the economies made. The approach that had made the firm famous – excellence of workmanship, especially with the cabinets – proved to be its undoing, as it was with many similar concerns. The public's enthusiasm for TV sets as pieces of furniture was rapidly waning in favour of less bulky mass-produced sets that nevertheless gave bigger and brighter pictures.

TVT Transistor Equivalents Books

Eugene Trundle

For those in the electronics field, particularly those in the maintenance and repair side of the business, a perennial problem is finding data and equivalents for the many types of transistors that have been used in equipment over the years. How do you tackle a twelve-year old Mitsontachi with a leaky 2SB41, or an obscure continental monster that's murdered its little BC219? What when you've blown up your entire stock of BU105s in a lambs to the slaughter session and wonder whether a BDX32 is a suitable sacrificial offering?

A specialist W. German publisher, ECA, regularly produces books of comparison tables. They are updated annually and the subject of this note is the current TVT 84/85 set. It consists of two pocket-sized volumes with baby wise-owls on their covers: there's an earnest and endearing preface that's a literal translation from the German. Volume 1 (A-Z, 317 pages) covers mainly European devices with AC-ASZ, BC-BUY and C-ZTX prefixes. Volume 2 (2N-∞, 487 pages) caters for American and Japanese types prefixed 2N-2SA, 2SB, 2SC, 2SD, 2SK and 3N on, ending with the five-digit 40000 series perpetrated by RCA. Between them the books list about 12,000 transistor types.


The coverage is comprehensive and I've seldom failed to find listed any transistor I've come across in domestic (and much other) equipment. For each type listed we get information on its type (ge/si), manufacturer(s), construction (npn/pnp/n-fet etc.), case style (TO3, TO18, SOT25 etc.) and lead-out identification. Also given are applications (general purpose, i.f., TV deflection etc.) and brief electrical details (voltage, current and dissipation ratings). Where relevant other parameters are given, such as gain, cut-off frequency or switching time. For virtually every type listed there's at least one equivalent given – sometimes up to nine – drawn from a wide range of manufacturers and species. Case styles and pinning diagrams are given for each of these. If a complementary device (to make a matched npn/pnp pair) is available for the listed transistor its type number is also specified.

I've been using this series of books for some years now and wouldn't be without them. The few transistors I've failed to find have generally been in very new equipment

released since the current book was compiled. I've yet to find a misprint or error, though the criteria for transistor comparison must necessarily be broadly based and some of the suggestions for high-power switching transistors are not, I find, very good ones. For instance a BU208 is given as being a suitable substitute for a 2SC1942: o.k. on paper no doubt, but the BU208 will have a short and pyrogenic life in certain Japanese switch-mode power supply circuits! This is probably to do with the transit or recovery time of the devices.

The only serious criticism I have is that the books tend to fall apart after a certain amount of use. They're not really robust enough to stand up to regular workshop and field use – and abuse. Loose leaves are the first symptom, followed by partial disintegration.

In spite of this they represent very good value for money and should find a useful place on the workbench or design desk – and particularly in the roving toolbox. The set of two costs about £7.30 to the trade. They are available from HRS Electronics, SEME Electronics, Mastercare, PV Tubes etc., also by mail order from the Modern Book Co. (telephone 01 402 9177). For those interested, similar equivalents/data books on diodes and on thyristors etc. are also published by ECA – details can be obtained from the suppliers mentioned above.

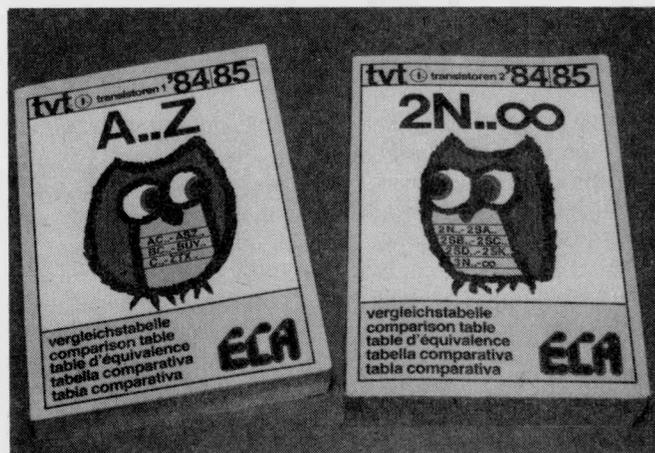

The 1984/5 TVT transistor equivalents books.

POST A-PART ELECTRONICS
6 CHAPMAN COURT, CHARFLEETS ROAD,
CANVEY ISLAND, ESSEX SS8 0PQ.
Telephone 0268 690868
Telex 99305 ROSSER G.



TRADE COUNTER NOW OPEN

ORDERS DESPATCHED SAME DAY
ADD 60p P&P, THEN 15% VAT.
ADD POSTAGE FOR OVERSEAS ORDERS.
ORDERS WITH AEROSOLS, PLEASE ADD 25p PER CAN.

| | |
|--|-------------|
| Thorn 100 20W (3500) R751 Safety Resistor | 75p |
| Pye 713 Speaker 8" x 3" 702 | 1.00 |
| Pye 713 Complete Tube Base Panel with Focus Slider & Leads | 2.75 |
| Pye 713 Control Knobs | 4 for 50p |
| Tube Base Socket ITT CVC32 | 45p |
| Tube Base Socket Thorn 3000/8000 etc | 50p |
| IC Insertor 16 Pin | 50p |
| Large IC Extractor | 50p |
| Crystal 4.43MHz | 65p |
| EHT Lead & Cap for Split Diode Lopt | 90p |
| Anode Cap | 47p |
| Sanyo Anode Cap Assy + Lead. 12TCD-CT-10 | 65p |
| Deгаuse Thermistors FT37P, ITT/GEC | 35p |
| Deгаuse VDR E2900/HP230 3000/8000 | 25p |
| Casters Sat of 4 | 1.90 |
| Double Fuse Holder on Small Pax Board 20mm type | 10p |
| Single Fuse Holder on Small Pax Board 20mm type | 5p |
| Direct Panel Mounting 20mm Fuse Clips | (pair) 15p |
| Single Fuse Holder on Small Pax Board. As per early 3000 mains input | 6p |
| EHT Cable | Metre 2.5p |
| 13A Plugs | 12 for 4.80 |
| BF259 with Heatsink | 14p |
| TIP110 with Heatsink | 40p |
| LT29/130/131 Coil | 10p |
| 6MHz Ceramic Filter | 25p |
| DL700 (Philips) Chroma Delay Line | 1.00 |
| DL50 Chroma Delay Line | 1.00 |
| 19066A Lum. Delay Line | 1.00 |
| 8K5/9K Lum. Delay Line | 65p |
| Plastic Cover for 3K5 SP3865 | 5p |
| TX9 Back Ground Control 10K | 15p |
| 1500 Metal Chassis, Supports Pair | 10p |
| Thorn 8K5 Focus Pot | 2.40 |
| Thorn 4000 Focus Pot | 2.75 |
| Thorn 1821 9W (8K5) R752 | 30p |

SERVICE AIDS

| | |
|-------------------------------------|-------------|
| Ambersil M54 Silicone Grease | 12oz 2.15 |
| Ambersil Freezer | 12oz 1.99 |
| Ambersil Amberlube | 6oz 1.89 |
| Ambersil Ambertron | 16oz 1.95 |
| Ambersil Anti-Static Screen Cleaner | 7oz 1.95 |
| Ambersil 40+ Protective Lubricant | 14.1oz 2.15 |
| Ambersil Amberclens Foaming Cleaner | 13oz 1.26 |
| Ambersil Circuit Lacquer | 14oz 2.15 |

THICK FILM RESISTOR UNITS

| | |
|-------------------------------------|------|
| 3500 Thorn (5 Pin Connection) video | 1.70 |
| 4000 Thorn (4 Pin Connection) | 1.90 |
| 725/731 Pye (6 Pin Connection) | 2.20 |
| 713 Pye (6 Pin Connection) | 2.20 |

FUSES

| | | | |
|-----------|-------------|-------|------------|
| 50MA | 10 for 70p | 250MA | 10 for 65p |
| 315MA A/S | 10 for 50p | 750MA | 10 for 65p |
| 500MA | 10 for 50p | 7A | 10 for 50p |
| 1A | 10 for 50p | 10A | 10 for 50p |
| 2.5A | 10 for 1.00 | 20A | 10 for 50p |
| 3.15A | 10 for 1.00 | 50A | 10 for 50p |

| | |
|--------------------------------|-------|
| Thorn Mains TX 3000/3500 | 7.50 |
| Thorn Mains TX 8000/8500 | 10.00 |
| Thorn S.O.P.T 8000/8500 | 3.00 |
| Thorn Scan TX 3000/3500 | 6.50 |
| Thorn EHT TX 3000/3500 | 6.00 |
| Thorn LOPT 8000 | 12.00 |
| Thorn LOPT 8185 | 7.25 |
| Thorn LOPT 1590/91 | 7.25 |
| Thorn LOPT 1690/91 | 7.25 |
| Thorn LOPT 8000 | 9.80 |
| Thorn LOPT 8500 | 9.80 |
| Thorn LOPT TX9 | 9.85 |
| Pye LOPT 713 | 10.00 |
| Pye LOPT 725 | 9.85 |
| Pye LOPT 731 | 10.18 |
| Philips LOPT G11 | 8.80 |
| GEC LOPT 3113 | 13.75 |
| Diode Split LOPT AT2076/35 | 7.40 |
| Sanyo LOPT AM-WM-21 | 6.75 |
| Sanyo LOPT AM-WM-4 | 7.30 |
| Philips LOPT G8 | 7.80 |
| Sanyo LOPT (CW21) 4-2751-44700 | 5.00 |
| ITT LOPT CVC5-9 | 9.60 |
| ITT LOPT CVC30 | 8.75 |
| ITT LOPT CVC45 | 9.75 |
| Bekrd 8750 | 10.25 |
| Bekrd 8752 | 10.25 |
| Korting AZ9100 | 10.25 |
| Korting B92-170 | 10.25 |
| Korting AZ2101 | 10.25 |
| Korting AZ2103 | 10.25 |
| Korting ZTR1001 | 10.25 |
| Siemens V1155 | 11.75 |
| Siemens V1823 | 11.75 |
| Zanussi BS2222 | 10.25 |
| Zanussi BS2223 | 10.25 |
| Salora FR0057 | 10.25 |
| Salora FR0029 | 10.25 |

| | |
|----------------------------|------|
| 300 Mixed Resistors | 1.50 |
| 300 Mixed Capacitors | 1.50 |
| 150 Mixed Electrolytics | 2.00 |
| 100 W/W Resistors | 1.00 |
| 20 Mixed Conv Pots | 1.00 |
| 40 Mixed Pots | 1.50 |
| 20 Mixed Sliders | 1.00 |
| 40 Mixed Presets | 60p |
| 20 Mixed VDR & Thermistors | 1.00 |
| 20 Mixed Ferrite Cores | 50p |
| 100 Mixed Ceramic Discs | 1.00 |
| 20 Mixed Valve Bases | 1.00 |

| | | | | | | | | | | | |
|---------|------|---------|----|--------|------|--------|----|---------|------|----------|------|
| AC128 | 39 | BC172 | 9 | BC559 | 8 | BF167 | 24 | BFR62 | 28 | NKT276 | 20 |
| AC131 | 40 | BC174B | 23 | BC595 | 8 | BF173 | 29 | BFR81 | 29 | NKT453 | 1.65 |
| AC138 | 40 | BC177 | 24 | BCX33 | 22 | BF179 | 32 | BFR87 | 25 | OT112 | 1.92 |
| AC141K | 39 | BC182LB | 12 | BCX34 | 11 | BF180 | 33 | BFR90 | 1.74 | OT121 | 2.08 |
| AC142K | 38 | BC183L | 12 | BD115 | 49 | BF185 | 30 | BFR91 | 2.08 | R1038 | 80 |
| AC153 | 39 | BC184L | 13 | BD131 | 30 | BF189 | 16 | BFR98 | 40 | R2018B | 1.10 |
| AC176 | 33 | BC187 | 24 | BD132 | 46 | BF195 | 16 | BFY50 | 30 | R2030 | 70 |
| AC176K/ | 32 | BC204 | 15 | BD133 | 59 | BF196 | 16 | BFY51 | 34 | R2265 | 1.30 |
| AC128K | 93 | BC206 | 9 | BD139 | 36 | BF197 | 15 | BFY52 | 34 | R2305 | 80 |
| AC188 | 38 | BC212L | 9 | BD140 | 38 | BF198 | 19 | BRC1116 | 1.50 | R2322 | 50 |
| AD142 | 1.18 | BC213L | 12 | BD144 | 1.70 | BF199 | 15 | BRC1693 | 1.43 | R2443 | 25 |
| AD143 | 1.08 | BC237 | 12 | BD150 | 50 | BF223 | 18 | BU105 | 2.00 | RCA16446 | 30 |
| AD149 | 98 | BC238B | 8 | BD163 | 98 | BF224 | 19 | BU126 | 1.10 | RCA16599 | 1.25 |
| AD161 | 32 | BC238L | 8 | BD201 | 74 | BF228 | 20 | BU207 | 1.05 | RCA16600 | 1.40 |
| AD162 | 32 | BC250A | 15 | BD203 | 78 | BF240 | 9 | BU208 | 1.15 | RCA16799 | 1.13 |
| AD263 | 1.08 | BC251 | 8 | BD204 | 99 | BF241 | 21 | BU208A | 1.15 | RCA16800 | 1.42 |
| AF127 | 45 | BC252A | 28 | BD222 | 48 | BF255 | 10 | BU326A | 1.30 | RCA16802 | 2.38 |
| AF139 | 38 | BC294 | 37 | BD225 | 52 | BF263 | 29 | BU407 | 1.70 | S1239 | 2.25 |
| AF239 | 41 | BC301 | 32 | BD232 | 50 | BF257 | 28 | BU408 | 2.76 | S28000 | 1.28 |
| BC107 | 15 | BC303 | 31 | BD233 | 60 | BF259 | 28 | BU500 | 2.30 | S6080A/B | 3.50 |
| BC108 | 15 | BC307 | 10 | BD234 | 60 | BF271 | 25 | BU526 | 2.46 | T6050V | 1.30 |
| BC109 | 15 | BC308 | 8 | BD237 | 55 | BF274 | 11 | BU807 | 2.94 | T6052V | 1.30 |
| BC115 | 16 | BC309 | 14 | BD238 | 66 | BF337 | 29 | C1129 | 9 | T9003V | 1.25 |
| BC117 | 21 | BC327 | 18 | BD241 | 59 | BF338 | 34 | C1172B | 9 | T9010V | 1.45 |
| BC125 | 26 | BC328 | 18 | BD244 | 85 | BF355 | 40 | ES386 | 54 | T9053V | 1.30 |
| BC126 | 23 | BC337 | 17 | BD278A | 81 | BF362 | 50 | E9033 | 28 | T9054V | 1.10 |
| BC138 | 27 | BC338 | 17 | BD386 | 88 | BF391 | 21 | E9035 | 25 | T9039V | 1.00 |
| BC141 | 34 | BC347 | 8 | BD433 | 71 | BF394 | 16 | ME0404 | 10 | TC45X | 50 |
| BC142 | 30 | BC394 | 8 | BD437 | 83 | BF422 | 47 | ME0412 | 10 | TC46 | 48 |
| BC143 | 31 | BC454 | 8 | BD592 | 120 | BF423 | 53 | ME0422 | 10 | TC106C | 40 |
| BC147 | 12 | BC455 | 8 | BD589 | 120 | BF450 | 43 | MAJ2501 | 2.26 | TIP29 | 42 |
| BC148 | 12 | BC456 | 10 | BD676G | 1.35 | BF453 | 53 | MAJ3001 | 2.21 | TIP30 | 42 |
| BC149 | 12 | BC460 | 40 | BD707 | 95 | BF458 | 37 | MAJ182 | 47 | TIP31 | 35 |
| BC153 | 16 | BC463 | 22 | BD708 | 95 | BF459 | 40 | MAJ340 | 50 | TIP32 | 43 |
| BC1540R | 16 | BC546 | 8 | BDX10 | 93 | BF461 | 58 | MAJ520 | 50 | TIP33 | 61 |
| BC154YL | 16 | BC547 | 12 | BDY20 | 1.09 | BF556B | 35 | MJE2965 | 1.40 | TIP41 | 42 |
| BC157 | 12 | BC548 | 12 | BDY82 | 99 | BF596 | 15 | MJE3065 | 1.50 | TIP42 | 45 |
| BC158 | 12 | BC549 | 8 | BF137 | 20 | BF694 | 16 | NKT241W | 8 | TIP110 | 61 |
| BC159 | 15 | BC557 | 10 | BF153 | 20 | BF757 | 62 | NKT241G | 8 | TIS91 | 25 |
| BC171 | 9 | BC558 | 10 | BF154 | 25 | BFR52 | 31 | NKT241Y | 8 | ZTX550 | 30 |

INTEGRATED CIRCUITS

| | | | | | | | |
|------------|------|----------|------|----------|------|----------|------|
| BRC1330 | 1.40 | SN7613ND | 1.80 | TBA530 | 1.26 | TDA2002 | 2.80 |
| BRC3064 | 1.00 | SN76023N | 1.80 | TBA540 | 1.00 | TDA2030 | 2.10 |
| BRC/M/200 | 1.00 | SN76033N | 2.00 | TBA5500 | 1.82 | TDA2522 | 2.10 |
| BRC/M/300 | 1.00 | SN76115 | 2.00 | TBA560C | 1.50 | TDA2530 | 2.61 |
| CA3060 | 1.58 | SN76131N | 2.50 | TBA641 | 2.95 | TDA2540 | 3.50 |
| LM1303P | 1.48 | SN76226N | 1.25 | TBA651 | 2.50 | TDA2581 | 3.00 |
| LM231B | 2.20 | SN76227N | 1.00 | TBA720A | 2.49 | TDA2591 | 1.96 |
| LM237B | 2.00 | SN76530P | 1.30 | TBA750 | 1.82 | TDA2611A | 1.95 |
| ML239B | 2.86 | SN76822N | 1.00 | TBA800 | 2.60 | TDA2640 | 2.90 |
| MC1327AP | 1.25 | SN76866N | 70p | TBA810S | 1.20 | TDA2650A | 1.50 |
| MC1356P | 1.30 | SN76668N | 85p | TBA810AS | 2.00 | TDA2680 | 6.00 |
| MC1455P | 18p | SN76744 | 1.82 | TBA920 | 2.08 | TDA9503 | 2.90 |
| MC14516BCP | 60p | TA7117P | 1.00 | TBA950 | 1.95 | TCEP100 | 3.48 |
| SAA1025 | 7.20 | TA7109AP | 2.80 | TBA1440 | 1.92 | TEA1009 | 1.95 |
| SAA1124 | 4.50 | TAA611 | 1.40 | TC4270SA | 1.05 | MC14426P | 4.80 |
| SAA5010 | 6.00 | TBA120B | 1.20 | TC4270C | 1.05 | MC14429P | 4.50 |
| SL432A | 1.80 | TBA120C | 1.20 | TCA270C | 1.05 | MC14514 | 5.00 |
| SL1430 | 2.50 | TBA120CX | 70p | TDA1004A | 4.00 | UA758PC | 2.50 |
| SN15846N | 60p | TBA120S | 70p | TDA1035T | 3.50 | UA1008A | 2.66 |
| SN74123N | 65p | TBA120U | 1.00 | TDA1037 | 2.72 | ULN2166 | 1.30 |
| SN74154N | 1.40 | TBA295 | 1.00 | TDA1200 | 1.50 | UPC1365C | 5.75 |
| SN76001N | 1.40 | TBA480Q | 1.40 | TDA1270 | 2.42 | SC9488P | 1.40 |
| SN76110N | 1.14 | TBA510 | 1.90 | TDA1327 | 2.76 | SC9511P | 1.40 |

| | | | | | | | | | |
|-----------------------------|----------|-----------------------------|---|--|--|------------------------------|------|---------------------------------|------|
| Thorn 8/8K5 ex equip panels | untested | 2.88 | PSU | 3.75 | Thorn 3K5 ex equip panels | untested | 2.50 | Thorn 4000 PSU panel ex-factory | 2.50 |
| FTB | 3.75 | LTB | 3.75 | new | 1.75 | Thorn 3K5 beam limiter board | 1.75 | | |
| Decoder | 4.00 | VCD5-9 | 2.50 | Thorn 3K5 PSU bottom board | 2.50 | PC206 new | 2.75 | | |
| Thorn 9K ex equip panels | untested | 5.00 | Conv. 3K | 3.75 | Thorn 3K5 IF panel new | 3.00 | | | |
| PSU | 12.00 | Conv. 3K5 | 3.75 | Thorn 3/3K5. EHT & scan TX + R2008B on alum chassis ex-equip | 1.80 | | | | |
| Decoder | 5.00 | Autovox Decoder FG/01 boxed | 5.00 | Thorn 8/8K5 damaged FTB for spares | 1.25 | | | | |
| Thorn 9K6 ex equip panel | untested | 5.75 | Thorn 4000 Convergence panel ex-factory | 3.75 | Thorn 8/8K5 damaged decoder for spares | 2.25 | | | |

| | | | |
|--|------|-------------------------------------|-------------|
| UHF TV Aerial for portable | 50p | Coax Plugs | 10 for 1.65 |
| Indoor Aerial Parabolic Type Reflector | 2.50 | Band Change Switch Assy, Pye 725 | 40p |
| to Help Combat Ghosting Problems | 3.90 | Rush Mounting TV/FM Diplexer | 1.00 |
| Line Connectors | 2.50 | Switched Rush Fitting Aerial Outlet | 1.00 |

| | |
|----------------------------------|------|
| 10 Spark Gaps | 1.00 |
| 10-16 pin Quil IC Socket | 90p |
| 20 Assorted TV Knobs | 1.00 |
| 10-16 pin Quil to Dil IC Socket | 90p |
| 100 Mixed Diodes | 1.00 |
| 50 Mixed Mica Washers | 65p |
| 300 Mixed Resistors & Capacitors | 1.00 |
| 10-16 pin Dil to Dil IC Socket | 1.00 |
| 50 Electrolytics & 50 Capacitors | 1.00 |
| 50 Mixed Poly Capacitors | 1.00 |
| 30 Mixed Neons & Bulbs | 1.00 |

| | | | | | |
|-------|----|---------|------|----------|------|
| BF167 | 24 | BFR62 | 28 | NKT276 | 20 |
| BF173 | 29 | BFR81 | 29 | NKT453 | 1.65 |
| BF179 | 32 | BFR87 | 25 | OT112 | 1.92 |
| BF180 | 33 | BFR90 | 1.74 | OT121 | 2.08 |
| BF185 | 30 | BFR91 | 2.08 | R1038 | 80 |
| BF189 | 16 | BFR98 | 40 | R2018B | 1.10 |
| BF195 | 16 | BFY50 | 30 | R2030 | 70 |
| BF196 | 16 | BFY51 | 34 | R2265 | 1.30 |
| BF197 | 15 | BFY52 | 34 | R2305 | 80 |
| BF198 | 19 | BRC1116 | 1.50 | R2322 | 50 |
| BF199 | 15 | BRC1693 | 1.43 | R2443 | 25 |
| BF223 | 18 | BU105 | 2.00 | RCA16446 | 30 |
| BF224 | 19 | BU126 | 1.10 | RCA16599 | 1.25 |
| BF228 | 20 | BU207 | 1.05 | RCA16600 | 1.40 |
| BF240 | 9 | BU208 | 1.15 | RCA16799 | 1.13 |
| BF241 | 21 | BU208A | 1.15 | RCA16800 | 1.42 |
| BF255 | 10 | BU326A | 1.30 | RCA16802 | 2.38 |
| BF263 | 29 | BU407 | 1.70 | S1239 | 2.25 |
| BF257 | 28 | BU408 | 2.76 | S28000 | 1.28 |
| BF259 | 28 | BU500 | 2.30 | S6080A/B | 3.50 |
| BF271 | 25 | BU526 | 2.46 | T6050V | 1.30 |
| BF274 | 11 | BU807 | 2.94 | T6052V | 1.30 |

The World of

“TELE PANELS”

52 Mount Pleasant Road, Chigwell, Essex.
Telephone 01-729 0506.



COMPARE OUR PRICES!

COMPARE OUR SERVICE!

| | IF | TUNER | DECODER | G8/G9 DECODER IF COMBINED | LINE OUTPUT | POWER | CONVERG | FRAME | VIDEO | 6 WAY TUNER SWITCH BANK |
|-----------------|-------|--------|---------|---------------------------------|----------------|-------|---------|--------------------------|-------|-------------------------------|
| PHILIPS G.8 | 5.00 | 4.50 | 7.00 | 15.00 | 14.00 | 8.00 | 5.00 | 5.00 | | 3.50 |
| THORN 3000/3500 | 2.00 | 5.75 | 4.00 | | 8.00 | 8.00 | 5.00 | 6.00 | 5.00 | 1.75 |
| GEC 2110 | 10.00 | | 5.00 | | 12.00 | 6.00 | 5.00 | 5.00 | 5.00 | 5.00 |
| PYE 731 | 8.00 | | 10.00 | | 18.00 | 10.00 | 7.00 | 8.00 | | 4.50 |
| PUSH Z/718 | 7.50 | 6.50 | 14.00 | | 24.00 | 3.00 | 5.00 | 14.00 | | |
| BUSH T/20 | 7.50 | 6.50 | 14.00 | | | | 5.00 | 14.00 | | |
| DECCA BRADFORD | 3.00 | | 7.00 | | | 4.00 | | FRAME TIME BASE £4 | | |
| DECCA 80 | 12.00 | P.O.A. | 14.00 | | 12.00 | 10.00 | | 14.00 | | P.O.A. |

Other makes of panels — telephone for prices!

TRIPLERS FOR ALL MODELS £3.00 SPEAKERS £1.50

P+P 1 PANEL £1.50 2 PANELS OR MORE £3.00

CASH WITH ORDER — PLEASE

POST OFF YOUR CHEQUE NOW! & YOUR PANELS SENT BY RETURN OF POST!!!

TRADE COLOUR TVs Always 2000 in stock

GEC Starline £45

GEC Remote £65

2020 Videos £79

All sets have been fully serviced by
factory trained engineers and in perfect
working order with excellent cabinets

Deliveries arranged and export orders
welcome

Deliveries weekly to any part of Ireland

ALL STOCK CHANGES WEEKLY!

We also clear bankrupt stock
Dealers returns, catalogue returns and
small rental companies, cash waiting

P&R SUPPLIES

Unit 5, Worle Industrial Centre,
Weston-Super-Mare, Avon

1 minute off exit 21, M5

(0934) 514047/512792/513633

TUNERS + TUNERS

- ★ If you repair sets regularly — phone us today and we will dispatch immediately — no need to send cash 'up front'.
- ★ All tuners dispatched by first class post for receipt by you the next day.
- ★ All popular tuners/tuner repairs supplied 'off the shelf'.
- ★ Unusual types repaired same day as received (subject to spares availability).

TELEPART

32 Temple Street,
Wolverhampton WV2 4LJ.
Phone: (0902) 773122.

SEND NO MONEY

Your order despatched C.O.D. from our comprehensive stocks of Audio, Video and T.V. spares.

Price list sent with your first order.

**Simply phone us
0934-419147**

Freeway Components, The Airport
Weston Super Mare, Avon BS24 8RA

Video Servicing

Mike Phelan

This month we'll discuss some of the signal circuits used in a domestic colour video camera. To do so, we must first take a look at the various bits at the front of the vidicon tube, i.e. in front of the photoconductive target. See Fig. 1. Though we've shown these items separately they are actually integral with the tube and therefore irremovable.

Optical Filters

The IR filter comes first. It attenuates light wavelengths beyond visible light - this is necessary as the vidicon is slightly sensitive to such rays and if steps to attenuate them weren't taken the colour rendering of an object would depend on its temperature! Despite the filter, most cameras will show whether an IR remote control transmitter is operating - quite a useful test.

The crystal filter is actually a low-pass optical filter. Without it interference patterns between fine detail in the image and the stripe filter would be generated, giving a similar effect to cross-colour on a TV set. The filter removes the high frequencies optically.

Mounted somewhere in this assembly is the OB (optical black), an opaque, L-shaped solid or plated mask that gives a reference black level at the end of each scanning line and field.

Colour Separation

Most domestic cameras with a vidicon tube use one of two systems for separating the colour: one is based on phase, the other on amplitude. The phase system is used on the simpler cameras at the lower end of the price range

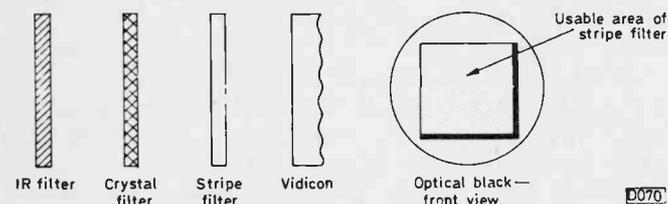


Fig. 1: Elements at the front of a colour vidicon tube.

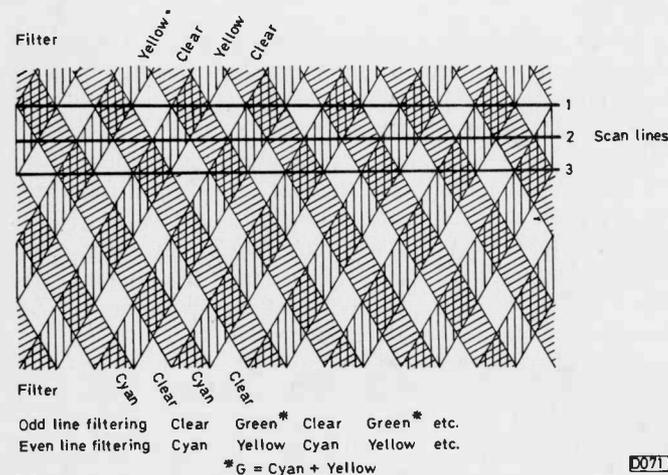


Fig. 2: Phase colour filter arrangement.

but can nevertheless give very good results. As the stripe filter format varies with the two systems we will discuss them separately, starting with the phase system used in the Sharp XC30, the Ferguson 3V17 and equivalents, and some National Panasonic models. See Fig. 2. The pitch of the stripes is typically 40.2 microns. You will appreciate from this that the height and linearity must be correct, as the filter has to be scanned in accordance with the precise stripe pattern.

Phase System

The colour stripe filter works as follows. The yellow section passes cyan (B + G), the cyan section passes yellow (R + G), the clear section passes all light (R + B + G) while only G is passed where the yellow and cyan sections overlap (we'll call this G). As a result, a signal consisting of G information with a subcarrier containing R and B information is obtained - with, on a monochrome picture, a pattern that repeats itself on alternate lines. Because of the stripe angle, the actual signal phase is repeated every four lines, i.e. if you draw a vertical line down the filter from say a yellow diamond you will encounter another yellow diamond four scan lines lower down.

The carrier frequency can be calculated from:

$$f = \frac{\text{width of scanning line (mm)} \times 1,000}{\text{pitch of filter } (\mu\text{m}) \times \text{active line period } (\mu\text{sec})}$$

To give the figures:

$$\frac{7.45 \times 1,000}{40.2 \times 51.75} = 3.58\text{MHz.}$$

Luminance Signal

To obtain a luminance signal, a low-pass filter follows the preamplifier. This gives us the G signal together with average values of R and B to feed to the luminance channel.

Colour Signal Processing

The composite signal is applied to the chroma processing circuit, see Fig. 3. The first section of the circuit, comprising $\pm 90^\circ$ shifts, a 64 μsec delay line and two subtract circuits, produces R and B signals, still on a 3.58MHz carrier. This is followed by detection to produce R and B video signals, the addition of a -Y signal from the luminance channel to produce the two colour-dif-


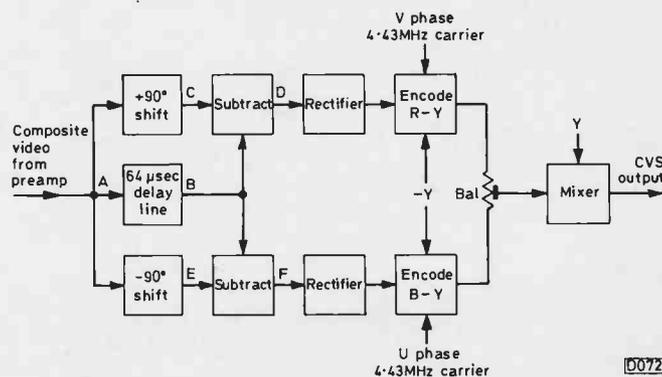


Fig. 3: Block diagram of the colour signal processing arrangement in a camera using phase colour separation.

D703


A Signal on line 1

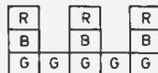


B Delayed signal from previous line




C (A + 90°)

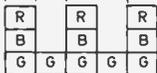

D (B - C)

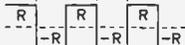

E (A - 90°)

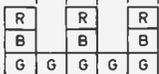

F (B - E)

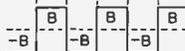


Fig. 4: How the phase colour separation system works.

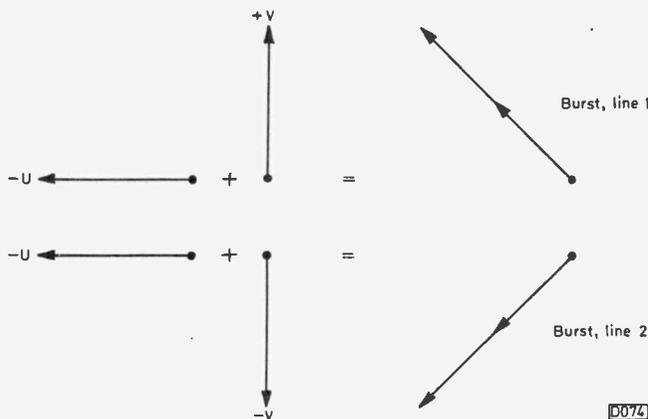


Fig. 5: Forming the burst signal.

ference signals R-Y and B -Y, then quadrature modulation on to a 4.43MHz carrier. When the result of these operations is added to the luminance signal we get a standard composite PAL output.

Fig. 4 shows how the R and B signals are produced. A is the signal on the line being scanned and B the signal from the previous line, present at the output from the delay line. The G component is constant (d.c.) irrespective of the phase shifts introduced and thus cancels out in the subtractive processes carried out in each channel. These subtractive processes also cancel out the unwanted R and B signals in each channel - due to the angle of the filter stripes the signals lead or lag by 90°. As a result we have at D and F the R and B signals on 3.58MHz carriers. Detection is usually carried out within an i.c., followed by filtering to remove the carriers. We thus get the two signals required for coding into PAL form.

The PAL Subcarriers

You will remember from our look at camera circuits last month that the sync and subcarrier generator (SSG) i.c. provides the two subcarriers required for V and U encoding, i.e. 4.43MHz subcarriers with the correct phase relationships, so all we need is a couple of balanced modulators to which the -Y signal is also fed (so that we get R-Y and B -Y chroma, not R and B).

- continued on page 199

next month in TELEVISION

● **ELECTRONIC SPEECH FOR TVs**

Sets that talk back to you to acknowledge control instructions have already been marketed. Until recently the cost of electronic speech for domestic equipment was prohibitive, but several large-scale speech processor i.c.s have now become available. David Botto describes what they do and provides details of how to use them - with a simple circuit that gives excellent results.

● **KV1820 GCS CONVERSION**

Keith Cummins bought a non-working Sony KV1820 with a dud gate controlled switch in the line output stage. Replacing it hardly seemed to be an economic proposition, but why not use a cheap and cheerful BU208A instead? This turned out to be a thoroughly satisfactory solution after a bit of modification.

● **MANUAL LACE-UP FOR THE N1500**

The original domestic VCR, the Philips N1500, can be obtained cheaply and provides the experimenter with a way of getting into video. One of the trouble spots in the N1500 is its lacing arrangement - a cord prone to wear and a fragile mechanism driven by plastic gearwheels that fracture and break. The lot can be replaced with a reliable manual lace-up system, as John de Rivaz explains.

● **DYNAMIC WIDTH CONTROL**

George Wilding describes the contrasting approaches to dynamic width correction used in recent Thorn chassis.

● **ADDING A SECOND REFLECTOR**

Ivor Nathan had a serious reception problem - a weak signal and ghosting due to a newly erected tall building. Adding a second reflector to the aerial array provided a complete solution.

PLUS ALL THE REGULAR FEATURES

ORDER YOUR COPY ON THE FORM BELOW:

TO (Name of Newsagent)

Please reserve/deliver the March issue of TELEVISION (£1.10), on sale February 20th, and continue every month until further notice.

NAME

ADDRESS

Hints on the ITT CVC5-9 Series

Chris Avis

The ITT CVC5-CVC9 series of hybrid colour chassis continues to be popular – many of my customers are still happy with sets purchased new twelve years ago, and rumour has it that even the editor possesses one. An excellent three-part article on these chassis by none other than ET appeared in *Television* nine years ago (November 1975–January 1976). It's not my intention to trundle out the same details again but to provide some useful hints based upon my own experience of reconditioning these sets.

Power Supply

The mains filter capacitor C257 in the CVC5 may be cut adrift or missing due to a previous short-circuit and a so-called service engineer's short cut. Drill an additional small hole through the PCB and fit an RS type 114-115 (0.1 μ F, 250V a.c.) for greater reliability. Later chassis use a 1 μ F three-pin type: if yellow and 220V, replace immediately with the 250V grey/white type.

The CVC5's on/off switch is an integral part of the control assembly and cannot be replaced separately. Complete assemblies are at present available from Sendz Components for £2.

Check the mains transformer's mounting bolts, which are frequently loose. They can be responsible for an annoying 50Hz buzz when loose.

The h.t. reservoir/smoothing electrolytic can C271/3/5/6 is returned to chassis via a soldered lug on the line output stage screening cage. Dry or cracked soldering here causes loud arcing when the set is switched on – this can be devastating to the nervous owner. Resoldering will correct the condition but I also run a length of insulated wire down the board vertically from the top earthed foil area to the bottom, terminating at the earthy end of C302, breaking the insulation and soldering the wire to all earthed foil points en route, including C271 etc. This avoids various intermittent faults that can occur through poor chassis return connections on this board. By the way, this is also a useful dodge with the Bush A774 hybrid monochrome chassis.

Line Timebase

This may be old hat to many readers, but it's well worth resoldering all the connections on the line output transformer panel, including the transformer's mounting lugs. Erratic joints here can cause many strange, baffling faults, especially via winding L104-7 which distributes line-frequency pulses far and wide.

Oldly solders may never die but old solders do, particularly if the battle has been hot. The soldering to R424 (in parallel with the scan-correction capacitor – it damps the capacitor's inductance) is often such a casualty, causing board damage in extreme cases. If the resistor's mounting lugs are too charred or oxidised for reliable soldering, replace it with an 11W type (RS156-440 etc.) which can be accommodated at an angle – the long mounting wires, suitably bent, are useful for bridging damaged connection areas on the board.

If the original 0.47 μ F, 1kV boost capacitor (C310) is still fitted, replace it – the capacitor becomes increasingly prone to failure with old age (I can sympathize). Use a polypropylene replacement (e.g. RS114-626) for maximum reliability (at a price). A disc ceramic capacitor is more reliable than the original rod type in the fifth harmonic tuning position (C308).

Another geriatric symptom is hairline fractures in the PCB foil in the area around the line output stage valves (PY500A, PL509) – plus more old solders under the valve bases. Don't forget the line output valve's cathode resistor R423 (10 Ω): poor connections here will cause contrast variations – or disappearance – as a result of the action of the beam limiter circuit.

Modifications for VCR use have appeared previously in *Television* (ET again, May 1982). In case you don't have the issue, here they are: change C288 to 820pF, C290 to 0.1 μ F and R395 to 47k Ω .

Focus problems are usually caused by the three resistors in the circuit – R429 and R431 (both 4.7M Ω) and R276 (2.2M Ω). In addition, the VDR rod itself can be responsible while C318 (210pF) which decouples the slider can be leaky.

Field Timebase

In my experience the field timebase is quite reliable apart from the usual PCL805 troubles and the field sync diode D46. If the latter is still an OA91, replace it with a more reliable 1N4002 etc. If the output pentode's cathode decoupler C247 has a black case . . . we can bypass further comment.

The height and/or linearity presets are often erratic: replacements can with advantage be mounted on the print side of the board for ease of adjustment and a cooler environment.

Many early bottom timebase boards were cracked in the area of the field hold control due to the unwise use of a control knob designed to protrude through a small hole in the back cover, but which didn't when the cover was refitted by an innocent engineer: the result was horizontal thrust on the field hold control and multiple fractures. Worth checking if intermittent line sync and field faults are present.

Mysterious Loss of Sync

If removal of and refitting the CVC7/8/9 chassis for tube replacement results in a mysterious loss of line and field sync, check that the extra metal support bracket at the bottom of the cabinet is located *between* the screened edges of the i.f./chroma panel and the timebase board and not on the inside edge of the latter where it can short against the TO5 case (collector) of the sync separator transistor T42.

The Decoder

Decoder faults received detailed coverage in ET's November 1975 article. Personally, I've found this area of

the set to be pretty reliable. For absent or erratic colour, replace the chroma amplifier transistor T28 (suitable types BF597, BF299 etc.) before going farther into the decoder. Assuming that no twiddle-happy fingers have got there first, only two adjustments are normally required. First, using a colour bar signal move the colour control to minimum and balance the colour control bridge circuit by adjusting the trimmer C160 with a non-metallic tool for a neutral grey scale. Then put a squirt of Servisol on the chroma delay gain preset R214 and adjust this, with L68, for minimum Hanover blinds (use cyan for R214 and magenta for L68).

Ageing colour drive presets are now increasingly troublesome on all versions, sometimes making stable grey scale adjustment impossible even when the first anode presets are o.k. If they are touchy, remember the TUC principle - Terminate Unworthy Components: better still, remember "one out, all out" and change all three! The CVC5 uses standard 5kΩ (4.7kΩ) presets in the collector circuits of the RGB output transistors: later versions with a considerably modified demodulator/matrixing circuit have three miniature 2.2kΩ presets at the TDA1327A i.c.'s outputs.

The RGB output transistors are BD115 (BF337 etc.) types with their TO5 cases clamped to vertical heatsinks. Each pair of clamp screws passes through a strip of plastic intended to prevent the transistor's leads shorting to the sides of the heatsink holes. These strips will often be found to have disintegrated, with consequent loose clamping and poor heatsinking. If the plastic remains are excavated, the mounting screws can be tightened directly on to the heatsink, ensuring that the case of each transis-

tor is positioned so that the base and emitter leads are central in the heatsink holes.

Front Controls

Two unreliable channel selector units were used in early models, causing tuning drift and erratic signals. Replacements for the seven-way round button unit are available from Sendz at £8. Conversion kits for the awful five-button-plus-thumbwheel units cost around £12, but I've successfully adapted many sets to use the cheaper GEC tapered button unit which will fit with a little modification.

Slider controls, when fitted, can be erratic but are sufficiently exposed for successful cleaning if care and thoroughness are exercised. A small ball of Duraglit wadding held in long tweezers can be negotiated along the carbon and metal tracks which can then be cleaned off with a similarly held wad of toilet tissue soaked in methylated spirit. A smear of silicone grease will protect the surfaces and aid smooth running of the sliders.

Previous clumsy servicing may have broken some of the slider assembly escutcheon mounting latches, leaving it secured by little more than the central knobs. The repair method depends on the extent of the damage. A combination of heat-welding with an iron and/or drilling and securing with small binder screws is usually sufficient, but ensure that the screws don't penetrate through the front of the control panel!

In Conclusion

Teletext, in-line gun tube and Digivision these chassis

| CAPACITORS | | INTEGRATED CIRCUITS | | SPECIFIC COMPONENTS | | TRANSISTOR/DIODES | | |
|-------------------------------|------|------------------------------|-------|--------------------------------|-------|--|-------|------|
| 91 5 × .0047/1500 AB23 | 3.00 | 140 5 × TDA440 | 3.00 | 351 Thorn | 1.591 | 390 G8 Metal Mains Switch | 1.23 | |
| Chassis | 1.50 | 141 5 × TBA120AS | 1.80 | Speaker | 2.00 | 391 G8 Line Stor/Eq | 2.25 | |
| 92 10 × 220MFD 16V | 0.50 | 142 5 × TBA540 | 4.00 | 352 Thorn | 1.600 | Coil | 2.25 | |
| Elect | 0.50 | 143 5 × TBA540Q | 4.00 | Dropper | 0.50 | 392 G8 R/G Symetry | 3.33 | |
| 93 10 × .047MFD 400V | 0.50 | 145 5 × TBA560 | 3.50 | 353 T × 10 Preset | 3.00 | 397 20 × 3.15A A/S 20mm Fuse | 1.50 | |
| Mul Pol | 0.50 | 146 5 × TBA810S | 3.00 | 354 T × 10 CRT Base Assy | 4.00 | 398 20 × 800MA A/S 20mm Fuse | 1.50 | |
| 94 5 × 4.7/100V C514 | 1.25 | 147 5 × TBA920Q | 4.50 | 355 3" Round BR Speaker | 1.00 | 399 20 × 2.5A A/S 20mm Fuse | 1.40 | |
| T3500 | 1.25 | 148 5 × TBA990 | 3.25 | 358 5 × Tho/3500 200 Conv. Pot | 1.00 | 400 20 × 2A A/S 20mm Fuse | 1.40 | |
| 95 5 × 47/1000 | 3.00 | 149 5 × TBA520Q | 4.00 | 359 5 × Tho/3500 50R Conv. Pot | 1.00 | 401 20 × 1A A/S 20mm Fuse | 1.40 | |
| Dubilier | 3.00 | 150 5 × TBA530 | 4.25 | 360 5 × TCE3500 A1 Rectifier | 0.75 | 402 20 × 1.25A A/S 20mm Fuse | 1.40 | |
| 97 10 × 0.1/2000V | 2.00 | 151 5 × TBA950 | 4.50 | 362 T9000 Rem. Receive Assy | 5.00 | 403 5 × RRI T20 Tube Base | 4.35 | |
| W/E | 2.00 | 154 10 × TCA270SQ | 4.00 | 363 T3500 Mains TX | 5.00 | 410 Phil. G11 E/W Load/Coil | 1.50 | |
| 98 5 × 1/250 Supp ITT etc. | 1.50 | 155 10 × MCI327Q | 2.50 | 364 T8500 Mains TX | 7.50 | 411 Phil. G11 Bridge TX | 1.50 | |
| EHT TRAYS | | LINE OUTPUT TX | | PUSH BUTTON UNITS | | 412 Philips G11 Speaker | | 1.00 |
| 50 ITT CVC 5/9 | 3.00 | 001 Philips G8 | 7.50 | 110 Pye 713 4 Way | 7.87 | 413 10 × TDA2600 IC Holder | 1.50 | |
| 51 Decca 1730/1830 | 5.00 | 002 Decca 30 Series | 7.00 | 111 Pye 715 6 Way | 11.95 | 415 PALKT3 Speaker 15R Fusible | 0.50 | |
| 52 Decca 80 Series | 4.50 | 003 Decca 100 Series | 6.50 | 112 Phil G8 Square | 12.75 | 436 5 × Decca 30 3R9 Modulohm | 1.75 | |
| 53 GEC 2040 Hybrid | 3.00 | 004 ITT CVC 25/30/32 | 7.00 | 113 Phil G8 Sloping | 14.98 | 437 Decca 30 47k Vol.+ Switch | 1.25 | |
| 54 T1500 5 Stick | 3.50 | 005 Philips G9 | 7.50 | 114 Thom 9000 | 2.80 | 453 5 × 5R Universal Conv. Pot | 1.00 | |
| 55 Thom 9000 | 7.00 | 006 RRI T20 | 9.92 | 115 Thom 1615 4 Way | 2.57 | 454 5 × 20R Universal Conv. Pot | 1.00 | |
| 56 Thom 1400 | 2.00 | 007 RRI A823 | 7.00 | 116 Decca 6 Way | 6.95 | 455 5 × 100R Universal Conv. Pot | 1.00 | |
| 57 Philips G9 | 3.50 | 008 RRI Z718 18" | 18.95 | 117 Decca 4 Way | 6.50 | 456 5 × 470R Universal Conv. Pot | 1.00 | |
| 58 Universal ITT Type 4.50 | 4.50 | 009 RRI Z718 20/22/26" | 18.95 | 118 GEC 2110 6 Way | 7.95 | 457 10 × 100k Tun/Pres TCE etc. | 3.00 | |
| 59 5 × TV11 EHT Rec for PTV's | 1.00 | 010 RRI A774 Mono | | 119 GEC 2136/7 Tapered | 7.95 | 458 10 × 100k Tuner Preser G8 | 3.00 | |
| 60 3 × TV45 EHT Rec | 1.00 | 011 Thom 1690/91 | 7.00 | 120 ITT CVC5 | 9.25 | 459 ELC1043/05 Tuner | 6.00 | |
| 61 ITT CVC 45 | 4.00 | 012 Thom 1615 | 6.50 | 121 ITT CVC8 | 11.45 | All components are A1 quality from prime manufacturers, and are dispatched by post same day as order received together with any refund due. All goods should be delivered within 4 working days. | | |
| 63 RRI Z179 | 3.00 | 013 ITT CVC 45 | 6.50 | 122 ITT 6 Way with V.C.R. | 7.95 | Please add 15% VAT and 90p P & P | | |
| 64 Pye 691/697 | 3.50 | 014 Phil TX Chass. | 5.00 | 123 RRI A823 etc. | 7.95 | QUICK SAVE T.V. SPARES | | |
| 65 Pye CT200 4 Lead | 3.50 | 015 RRI Ranger 1/2 | 5.00 | 124 Hitachi 4 Way | 7.95 | MUXTON HOUSE, MUXTON, TELFORD, SALOP. | | |
| 66 Pye CT200 5 Lead | 4.50 | 016 ITT CVC 5/9 | 8.50 | 125 RRI T20 6 Way | 8.95 | REG. OFFICE ONLY. CALLERS STRICTLY BY APPOINTMENT. UK ONLY. PLEASE QUOTE STOCK NO. | | |
| 67 Koring 90 DGR | 5.00 | 017 Philips E2 Chass. | 5.00 | SMOOTHING CAPACITORS | | 230 10 × AC128 | | |
| Hyb | 5.00 | 018 Thom 9000 | 12.00 | 80 220/400 CVC32/T20 | 1.20 | 235 50 × BC213L | 2.50 | |
| | | 019 Thom 9500/9600 | 8.50 | 81 200+300 Pye 691 | 2.00 | 250 10 × BD124 | 9.00 | |
| | | 020 Polish 161 Mono | 6.00 | 82 600/300 Phil G8 | 1.90 | 251 10 × BD131 | 1.60 | |
| | | 021 Thom 3500 Scant | 4.50 | 83 175+100+100 | 1.50 | 270 10 × BU208A | 8.50 | |
| | | 022 Thom 8500 | 11.00 | T3500 | 1.50 | 271 10 × BU208 | 7.50 | |
| | | 023 Thom 1590/91 | 8.50 | 84 2000/100 Volt | 0.50 | 272 10 × BU326 | 10.00 | |
| | | 024 Thom 1500 15KV | 4.00 | 85 470 Mfd G11 | 1.50 | 273 5 × BU205 | 3.75 | |
| | | 025 GEC 2040/2100 Hybrid CTV | 4.00 | 86 400+400 Decca 30 | 2.50 | 280 25 × 2N3055 (Texas) | 7.50 | |
| | | 026 Bush 161 Mono | 5.00 | 87 200+200+75+25 ITT CVC5/9 | 1.50 | 281 10 × 2N2905 (Equiv. BC161/303) | 0.50 | |
| | | 027 GEC Single Std Mono | 5.00 | 88 400/400V Tho 9000 15/0 | 1.50 | 290 10 × BT106 | 9.00 | |
| | | 028 Pye 691 (wired) | 5.00 | 89 4700/25 Thom 1590/ | 0.80 | 292 5 × BT119 | 4.50 | |
| | | | | 91 | | 293 5 × BT120 | 4.50 | |
| | | | | | | 335 50 × BY127 | 3.00 | |
| | | | | | | Diodes | 3.00 | |
| | | | | | | 340 25 × TIP41A | 6.50 | |
| | | | | | | 341 25 × TIP41C | 7.00 | |

aren't, but they're good nevertheless – and long may they last!

ET adds: We still get a lot of complaints about 100Hz hum bars – it doesn't need much ripple on the 20V line to cause this effect. It's best to check the AD161 20V supply series regulator transistor T46 by substitution. If the trouble

persists, check C263 (10 μ F) and the driver transistor T45 (BC170B). Short-circuit turns in the mains transformer can sometimes overrun the AD161: if the c.r.t. heater voltage is in excess of 6.8V r.m.s., this is likely. All this assumes that the reservoir capacitor C262 (500 μ F) and bridge rectifier are o.k.

Servicing the Panasonic TC2205

David Botto

Large numbers of these 22in. sets were sold. The A56-540X 110° picture tube gives excellent colour and monochrome pictures and the sound quality is good, with 10W audio output. Magic-line tuning is a feature of the set.

Access

To gain access for servicing, remove the back cover (four screws), take out two screws from the rear edge of the bottom chassis, unfold two plastic runners and the chassis will slide towards you.

The circuit boards are identified by letters which we'll refer to in this article. On the left, looking in from the rear, is the vertically mounted A panel which contains the tuner, sound and vision i.f. departments, the colour decoder and RGB output stages, the luminance and the magic-line circuits. By taking the lead clamps from the c.r.t. wires and turning the two little plastic clips at each side of the chassis top – don't try to pull them out – you can hinge panel A down, making it easy to work on.

To work on the underside of the bottom E timebase/power supply/audio amplifier panel, first undo the cable ties to the deflection coils, control drawer, etc. – make sure you note their exact positions. The panel can then be turned forwards through 90°, giving access to the print side. Two little knobs slot into the plastic runners, holding the panel securely.

PANEL E

The power supply circuit is shown in Fig. 1. It's of the self-oscillating chopper type with the chopper transformer T801 providing mains isolation. Connector CO2ZS/P links the 240V a.c. input to the little Z panel on which the mains fuse F801 (3.15AT), the on/off switch and the mains filter components are mounted. The output from this panel goes to the main E board via connectors CO1ZS/P and CO1ES/P. Once on the main panel the supply goes via the 4.7 Ω surge-limiting resistor R802 on one side and the switch contacts of relay RY1001 on the other to the bridge rectifier D801-2 (two double diodes, type TVSMI1SR) whose reservoir capacitor is C808. The positive side of this d.c. supply is taken to the collector of the BU326A chopper transistor Q801 via the 'primary winding (P1/2) of the chopper transformer. The negative side of this supply is not taken to chassis: treat it with respect as you can get a nasty shock!

At switch on rectifier D803 (TVSRH1B) passes positive-going mains frequency pulses to the base of Q801, via C810/R805/R821/L804, to get the circuit started. Once the circuit starts to oscillate, feedback is via winding B1/2 on the transformer. Thyristor Q803 (TVSTF340MA) is used to switch the chopper transistor off at the end of each

cycle. Rectifier diode D804 produces a negative bias voltage of about -0.2V for the gate of this thyristor. The key component is R814 (1 Ω , 3W wirewound) which is connected in Q803's cathode circuit. When Q801 switches on, its emitter current flows through this resistor, and because of Q801's inductive load a sawtooth voltage is developed across R814. Once Q803's cathode is at -0.7V with respect to its gate Q803 fires, shorting the base and emitter of Q801 so that it's switched off. Q803 then turns off and when point B1 on the transformer swings positively Q801 switches on again.

Power is taken from the secondary winding S1-4 on the transformer, with rectifier diodes D852, D851 and D853 providing 195V, 160V and 25V d.c. supplies respectively.

Regulation is carried out by D809, Q802 and the associated circuitry which provides a second bias source for the gate of Q803. R809 (+B adjustment) is used to set the h.t. obtained from the power supply. The supply for this part of the circuit is obtained from winding F1-2 on the chopper transformer, with rectification by D810/C815. As the voltage developed across this winding varies, so the conduction of Q802 and the firing point for Q803 change.

Protection Circuit

The other thyristor in the circuit, Q804, provides over-load protection. There are two ways in which it can be brought into conduction. If a fault in the power supply results in increased output voltages from the transformer, zener diode D814 will conduct, firing Q804 and thus shorting the base and emitter of Q801 so that it switches off. This protects Q801 and the circuits powered by the d.c. supplies obtained from the transformer. A heavy load or short across one of the d.c. lines on the other hand will reduce the output obtained from D810. As a result Q805 will switch off and D816 will conduct, switching Q804 on to stop the circuit. If you accidentally short one of the d.c. outputs obtained from the transformer you'll have to switch the set off and wait for about 45 seconds before switching on again.

Dealing with a Dead Set

What to do if the set is dead? First examine the mains fuse on board Z. It sometimes fails for no apparent reason. Provided it's not blackened, a replacement may well restore normal operation. Don't forget to disconnect the mains first, as F801 is live even with SW801 in the off position. Then soak test the set for at least one day.

If the receiver is trying to start up or is dead with the fuse o.k., you have to decide whether the power supply is faulty or there's an overload elsewhere. This is easy to do with the TC2205, but you'll need a variac or tapped input transformer and a digital multimeter.

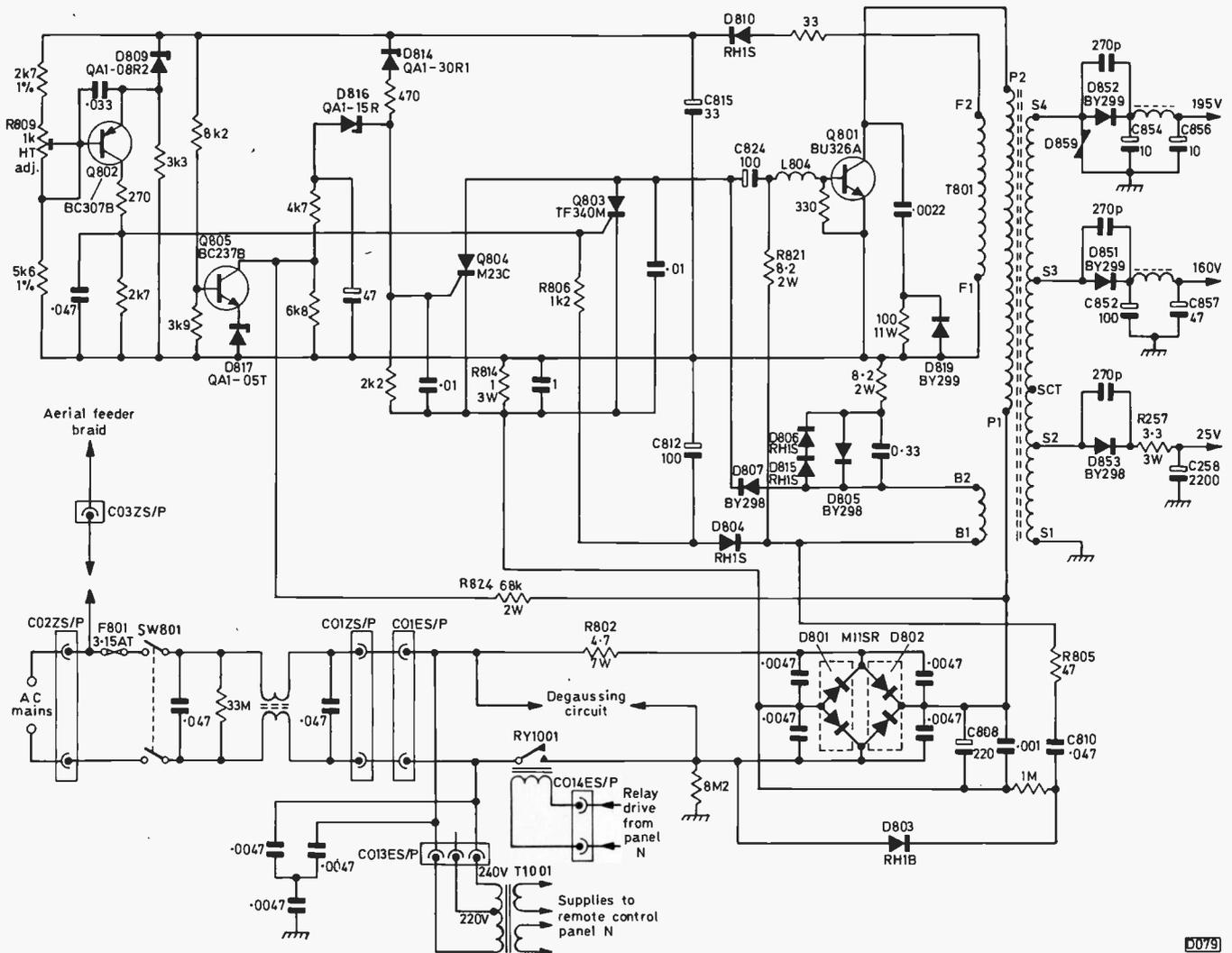


Fig. 1: The switch-mode power supply circuit used in the Panasonic Model TC2205 (chassis U2). It's not immediately apparent, but R824 is Q805's collector load resistor. Note that the circuit diagram in the manual shows R814 connected incorrectly (blob missing).

Connect the receiver to the a.c. mains supply via the variac/transformer, with the a.c. input set to 150-160V. Monitor the voltage at the cathode of D851. If it's low or zero, disconnect the mains supply then disconnect one end of the chunky 22Ω, 20W ceramic resistor R559 which is on top of the line output transformer. This disables the line output stage. Try again with the mains connected. If the voltage at the cathode of D851 is now at the normal level you've a line output stage fault. The 195V h.t. line can be isolated by removing connector CO5ES/P. The 25V line is protected by the special 3.3Ω fusible resistor R257 which will open if a fault is loading this supply.

If no outputs are obtained from the chopper transformer you've a power supply fault. Open-circuit the protection zener diodes D814 and D816. If the power supply now works normally, suspect transistors Q802 and Q805, both of which have been known to fail. Then check diodes D814, D816, D806, D815, D809 and D817. If you find one of these to be faulty don't leave it at that – check them all. The reliable way to do this is to use a component tester. C815 can leak, giving various weird effects. Finally check thyristors Q803/4.

The chopper transistor Q801 rarely fails. When it does, R802 usually goes as well, also D816. So check these before fitting a new BU326A.

The 195V supply reservoir capacitor C854 can cause

two nasty faults – an unstable picture, or a bright raster with the sound o.k.

Before leaving the power supply it's as well to check all the electrolytics for signs of drying out or leakage. C856, C852, C857 and C258 have been known to cause various puzzling effects such as the sound stopping at one level no matter what you do!

The Line Timebase

The line generator resides in IC501 (TDA2591). The drive pulses emerge at pin 3 and are fed via choke L501, R514 and C517 to the base of the driver transistor Q501 (2SC2085) which is transformer coupled (T501) to the BU208A line output transistor Q551.

The line output transformer T551 is of the diode-split type. D552 (APB0515) and D553 (BY299) are the EW modulator diodes. Various d.c. supplies are obtained from T551. D554 (BY299) and C557 (2,200μF) provide a 24V supply for the field timebase and the EW drive circuit. D557 (TVSRC2) and C563 (820pF) provide an 800V supply for the tube's first anode presets. D556 (BY298) and C558 (470μF) provide an 18V supply which goes to the AN320 magic-line i.c. (IC901) and the 12V regulator transistor Q851 (2SC1847). T551 also powers the tube's heaters.

The line output transformer is very reliable but has been known to fail. Substitution is the only reliable test. The line output transistor Q551 can also fail, but doesn't do so often. It's best checked with a component tester.

Before condemning IC501 (we've never had one fail) check the 18V rectifier D556 (BY298), its surge limiting resistor R560 (1 Ω , 0.5W), diode D856 (TVSRM1ZM) which is in series with the supply to this i.c. and, for corrosion or loss of capacitance, the electrolytic capacitors associated with the i.c. - C507 (4.7 μ F, 25V), C510 (100 μ F, 16V) and C516 (10 μ F, 16V).

If you've a line timebase fault that causes a dead set or one that tries to start then cuts out, tilt board E forward to examine the print side. Trace an imaginary line from the centre of the line output transformer 1.5-3in. towards the centre of the panel, checking carefully for print cracks. If all is well check D552. If it's faulty, fit the later type TVS2715M. Change capacitors C560 (0.33 μ F, 400V polyester) and C561 (1 μ F, 250V electrolytic) and measure the value of the special resistor R561 (180 Ω , 2W, type ERQ2CJ181). These components are in the scan circuit. Also measure the value of R770 (4.7 Ω , 2W type ERQ2CJ4R7) which is in series with the EW drive. After failure of D552 it's important to change the EW driver transistor Q753 (BD237) to avoid later problems.

Field Timebase Faults

Complete or partial field collapse is almost always due to IC401 (TDA1104SP). Replace it with the later type TDA1106. This i.c. can also blank out the picture, leaving the sound o.k. The voltage at pin 7 should be 1.4V: it goes via D303 (1N4148) and R319 (1.5k Ω) to pin 9 of IC601 in the decoder section on panel A. If the voltage at pin 7 of IC401 is 10V, replace this i.c. after first checking the spark gaps on the c.r.t. base. Then check the 24V supply surge limiting resistor R556 (2.2 Ω , 0.5W fusible).

Voltage Adjustment

After working on board E be sure to check the 195V, 160V and 24V lines with a digital voltmeter, adjusting R809 as necessary.

PANEL A

Signals board A lives a quiet life and seldom requires attention. The bulk of the circuitry is contained in six i.c.s.

IF Strip

The vision i.f. department is in IC101 (TDA2540). The output from this i.c. can be checked by feeding the set with a colour bar signal and connecting a scope, via a 10:1 probe, to test point A7. If all's well the complete picture waveform should be seen.

Magic-line Tuning

A 39.5MHz reference signal from pins 8 and 9 of IC101 is taken via transformer T102, C133 (100pF) and R121 (220 Ω) to pin 7 of the AN320 magic-line i.c. (IC901). The amplified signal is developed across coil L901. A line-frequency pulse is fed to pin 14 to synchronise a sawtooth generator within the i.c. The magic-line pulse appears at pin 6 and is fed via D902 and R332 to the TDA2530 matrixing/RGB preamplifier i.c. A green band that narrows as the receiver is tuned correctly appears on the

screen when the AFC/ML switch is set to ML. R902 adjusts the minimum width of the line. Very occasionally IC901 fails. Little else seems to fail in the magic-line circuit.

The Decoder

The good design of the TC2205 makes colour faults easy to find. First examine the print near the pins of the decoder chips IC601 (TDA2560), IC602 (TDA2522) and IC301 (TDA2530) for dry-joints, then all the small electrolytics in the vicinity for corrosion. Next make some quick checks with an oscilloscope, connected via the 10:1 probe, and a colour bar input to the set.

The chroma signal is transformer coupled to pins 1 and 2 of IC601: pin 1 should show the familiar "cotton-reel" colour bars. The same waveform, amplified, should be present at pin 6 (test point A10). If the waveforms at pins 9, 10 and 15 are correct - they are clearly shown on the circuit in the manual - move on to IC602. This operates in conjunction with an 8.86MHz crystal. The reference oscillator signal should be present at pin 10 while the three colour-difference signals should be present at pins 1, 2 and 3. To override the colour-killer, short pin 16 to chassis, i.e. link test points A14/15. The final i.c. (IC301) does the matrixing and drives the 2SC1819 RGB output transistors (Q351-3). These i.c.s can occasionally fail.

Predominance of one colour can be caused by failure of one of the RGB output transistors. Strange colours and puzzling variation of colour shades can be caused by the BZX61C7V5 zener diode D351 which biases the emitters of the RGB output transistors. It has a habit of becoming intermittent before failing completely.

REMOTE CONTROL

Board N contains complex circuitry for channel selection and remote control. It's mostly within three i.c.s and is easy to service - when it does need attention, which is not often. Mains a.c. from connector CO13ES/P on panel E feeds the remote control mains transformer T1001 whose outputs are fed to board N via connector CO82. The transformer's two secondary windings feed separate rectifiers, D1004 which produces 24V for the relay and D1005 which, along with the two zener diodes D1006 (5V, type TVSQA105SV) and D1007 (12V, type TVSQA112RV), produces 5V and 12V supplies for the remote control circuitry. Relay RY1001 (on board E) operates when pin 16 of IC1001 (SN76730N) goes high. If it doesn't, check the relay driver transistor Q1005 (BC237B) first. The 5V and 12V supplies are both present when RY1001's switch contacts are open.

In the TC2205s we've handled only once has IC1051 (AN5010) failed, causing channel changing problems. A logic probe is useful, but the easiest way to service this board is to check all the transistors and diodes first - this is easy and quick to do - then inspect the print for dry-joints. Only then suspect the i.c.s.

We haven't had remote receiver (board GR) failure yet, nor a defective infra-red handset - except when the customer forgets to renew the batteries!

FINAL TOUCHES

Finally, do make sure you replace all the connecting cables and ties in their correct positions, and apply a thin coat of circuit varnish to any joints you've soldered.

Video Servicing

— continued from page 193

The only remaining thing to be done is to produce a burst centred on the $-U$ axis with a $\pm 45^\circ$ swing on alternate lines. This might seem to be a bit of a problem, but as Fig. 5 shows all that's necessary is to pass the unmodulated subcarriers through each encoder during the burst period. The modulators used for encoding are of the balanced type, as required for the PAL suppressed subcarrier system, i.e. with no $R-Y$ and $B-Y$ signals fed into the encoders no carrier comes out. This condition is set by the i.c.'s d.c. levels, which are sometimes adjustable by means of a carrier balance control. Thus if we upset the d.c. levels during the pack porch period we get a subcarrier output, which is exactly what's wanted. The burst flag output from pin 11 of the HD44007A SSG i.c. is used for this purpose.

As Fig. 5 shows, the U subcarrier is on the $-U$ axis while the V subcarrier swings $\pm 90^\circ$ with respect to the U axis on alternate lines. Adding the two gives us the correct bursts.

Phase Shifting

Simple, isn't it? No? Well let's go back to Figs. 3 and 4. Each line contains the same green information, so if we subtract the outputs on successive lines we will be left with R and B only. Thus each line will consist of either alternate blocks of R and B or alternate blocks of $R+B$ and no signal. The angle of the stripe filter advances the blocks half a block from line to line. Taking each pair of blocks as one cycle, the filter is introducing a 90° phase shift (a 90° phase shift equals a quarter of a cycle). The $+90^\circ$ shift circuit moves alternate lines half a block, lining up $R+B$ with B and empty blocks with R : subtract one from t'other and the B s cancel leaving us with $+ \text{ and } - \text{ half cycles of } R - \text{ at a frequency of } 3.58\text{MHz}$. The -90° shift circuit moves the alternate blocks the other way so that $R+B$ lines up with R and the empty blocks with B :

this time the R s cancel, leaving B . With a picture containing colour information the three signal levels will vary of course, but the principle still holds.

Block Diagram for the 3V17

Fig. 6 shows in block diagram form the chroma processing arrangements used in the 3V17 camera. IC7 contains a buffer stage and the two phase shifters — the phase shift is adjustable by means of external trimmers. The phase shifted outputs go to the subtractor i.c.s IC9 and IC15 which also receive the output from the delay line after amplification by IC8. IC9 and IC15 are balanced modulators rather than amplifiers, their gains being variable in three ways. The shading inputs at pin 1 come from the SSG i.c. — we'll explain why next month, after looking at the alternative colour system. Pin 5 of each i.c. goes to a switched bank of resistors for daylight/artificial light control (there's no optical correction filter in the 3V17) and to a colour tint control potentiometer. These both vary the gain of the i.c.s — the former in two fixed increments, the latter differentially. Two presets $R\text{-bal}$ and $B\text{-bal}$ are provided: they are adjusted to ensure that no signal comes out when there's no colour input.

After amplification by IC10/16 and detection by IC11/17 (the filters are connected to pins 2, 3 and 4) the signals pass to IC12/18 for addition of the $-Y$ signal and non-linear amplification (gamma correction) to compensate for the fact that the vidicon's sensitivity and the c.r.t.'s light output are neither linear — more on this when we get to the luminance signal. These i.c.s are also fed with the burst flag to sit on the signal, which is clamped to the sync level — the burst period then represents a chroma signal consisting of equal amplitude R and B components.

IC13/19 are balanced modulators fed with the respective subcarriers. The 4.43MHz outputs are then added, the encode-balance control providing a means of swinging the chroma and burst phase a little way either side of the mean axis. Finally IC14 is a straightforward amplifier whose output goes to IC4 to be mixed with the luminance.

Next month the alternative (step-energy level) chroma system and mysterious things like shading etc.

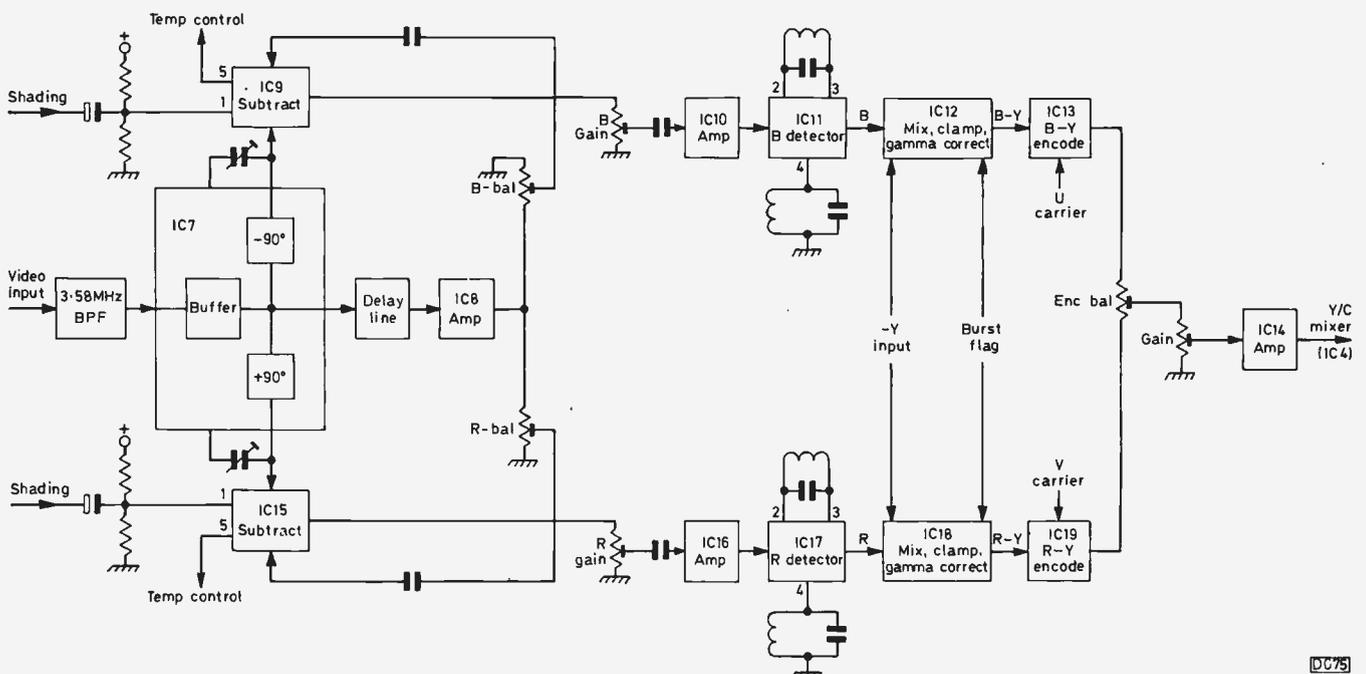


Fig. 6: Block diagram of the colour signal processing system used in the Ferguson 3V17 camera.

Low-noise 11GHz Converter

Hugh Cocks

Many transmissions in the 10.95-11.7GHz band are now receivable at relatively high signal levels from the ECS-1 satellite. The present article describes a simple low-noise downconverter: a later article will describe a low-noise amplifier to go with it – it's not as difficult to build as may at first be thought, provided you have some experience of r.f. construction techniques and are nimble with a soldering iron. The bandpass filter between the LNA and the LNC uses a high-precision waveguide system: arrangements have been made for the supply of this to readers as a ready-made unit since it has to be manufactured to exact tolerances, even down to the make of waveguide employed. The receiver section is very similar to that described by Nick Harrold in the October 1983-January 1984 issues of *Television*. The downconverter's i.f. output is adjustable to a certain extent. Fig. 1 shows the downconverter in block diagram form.

Oscillator/mixer Module

The local oscillator/mixer module is manufactured by Mitsubishi and is available off the shelf at a very reasonable price. It was originally designed to detect radar signals and is very small – see photo 1. The local oscillator consists of a gallium-arsenide FET with dielectric resonator while a Schottky diode is used as the mixer. See Fig. 2.

Dielectric resonators are relatively recent and form the heart of all modern LNC oscillators. The resonator is a little smaller than an Aspirin: it's made from a ceramic based material and is fixed on the board between the gate and drain connections of the FET. When placed in a cavity, a stable output with very low frequency drift – of the order of 2-5MHz over a very wide temperature range – is obtained. The frequency can be adjusted by means of a small disc that's a variable distance from the resonator, being mounted on the end of a screw thread. Adjusting the screw so that the disc moves closer to the resonator increases the oscillator frequency. The module used here can be tuned over a range of about 1GHz, from 10.4-11.4GHz, though individual units vary a little.

The module's input is in waveguide form (see photo 2): for some peculiar reason WG17 waveguide is used (US WR75 standard) with a WG16 (WR90) flange. The flange is made from heavy-gauge tinplate – a cheaper version is available with no flange. The module is thus easy to join to an aerial feedhorn or LNA/bandpass filter assembly with waveguide output.

Instead of using the conventional probe to pick up the signal in the waveguide and link it to the circuit, a wedge-shaped piece of metal that divides the waveguide in two is used. The rear end of the wedge is connected to the stripline on which the mixer diode is mounted (it also forms the d.c. return for the mixer's bias). The wedge tapers away at the flange end. As the wedge profile rises farther into the waveguide section the incoming r.f. is forced up the wedge. Since the divided waveguide is beyond the cut-off frequency at 11GHz the r.f. goes on to the stripline. The rear of the wedge is just visible in photo 1, connected to the stripline. The wedge and a tuning screw (fully closed) can be seen in photo 2.

The mixer diode requires an external bias. This can be used to advantage on weak signals, especially when an LNA is not used. The small tuning screw at the front of the assembly also helps with very weak signals.

Noise Figure

The unit's noise figure is 7.5-8dB, with a little spread for individual modules. Surprisingly good pictures can be had using a 1.8m dish and no LNA (see photo 3). Adding an LNA/bandpass filter assembly will reduce the noise figure to 2.5-3.5dB, giving excellent pictures with a 1.8m dish (see photo 4).

Modifications to the Module

The Mitsubishi module comes with a low-pass filter at the output, giving a roll-off above 600MHz. To remove this, take off the cover (secured by four bend-over pieces of metal, see photo 1) and cut the lead to the 2pF feedthrough capacitor. Next drill out the capacitor carefully, preferably with a hand drill. A stout piece of wire with plastic insulation can then be soldered to the output point and passed through the hole – soldering to the PCB is not easy as it's ceramic, causing quite bad heat loss at the iron bit. The bit should be grounded to the converter module as the Schottky diode is inclined to go short-circuit if there's a potential difference between these two items.

Two very thin pieces of track between the diode mixer and the output form a choke. Bridge the second, longer one with a piece of wire (resistor offcut). It's best to leave the short one, feeding the diode, in place. Both the diode and transistor are epoxy encapsulated. When soldering

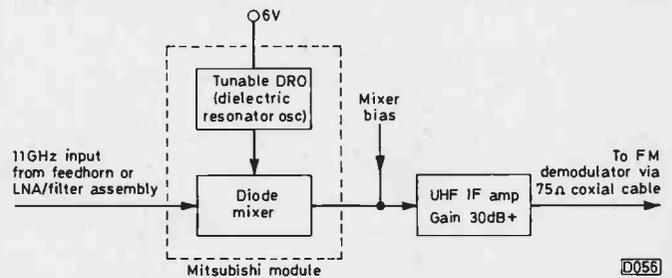


Fig. 1: Block diagram of the downconverter/u.h.f. i.f. amplifier system. The oscillator can be tuned over approximately 10.4-11.4GHz.

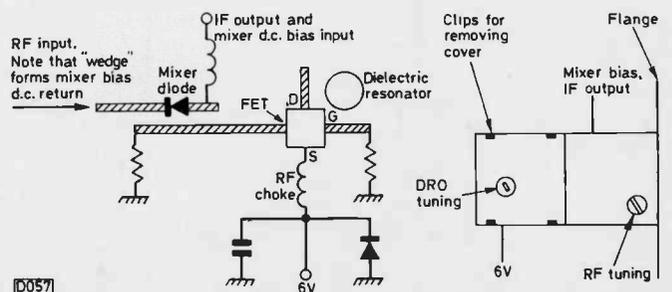


Fig. 2: Left, approximate circuit of the Mitsubishi FO-UP-11K oscillator/mixer module. Right, pin connections.

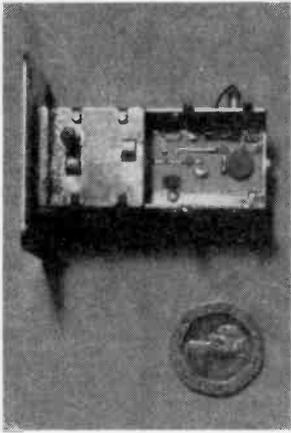


Photo 1 (left): Oscillator/mixer module with the cover removed. Note the resonator on the PCB.

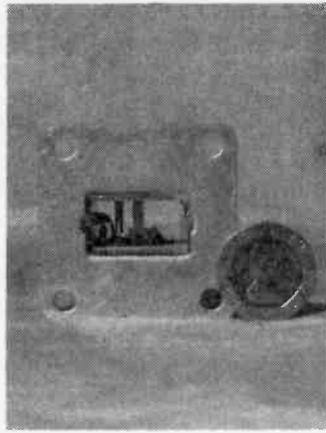


Photo 2 (right): The module's input – the wedge and tuning screw can be seen.

inside the unit be very careful not to short out the incoming stripline from the waveguide to the GaAsFET bias line – they are very close together and if they do short across it's difficult to remove the short with this type of board.

This completes the modifications to the module. Replace the lid. It's advisable at this point to unscrew the front tuning screw (not the oscillator screw) until it's right out: otherwise a notch in the response will be present somewhere in the middle of our frequency range.

UHF Amplifier

Due to the low level of the signal from the mixer diode it's essential to follow this with a high-gain amplifier mounted immediately after the mixer stage. The circuit used (see Fig. 3) is very similar to that described by Roger Bunny in the April 1984 issue, in this case with an emitter-follower output stage. Build the two stages in a small tinfoil can mounted right at the module's output connection, using u.h.f. construction techniques. The amplifier's output can then be fed to a suitable wideband u.h.f. amplifier whose body is soldered to the rear of the first amplifier's can – a Labgear CM7066 is suitable or, to cut the size down, an OM335 or OM361 can be used. The gain should extend to above 1GHz. Solder the tinfoil of the first can to the module with the i.f. pin coming through the floor. Don't use too much heat – the official recommendation is to keep the heating time down to a

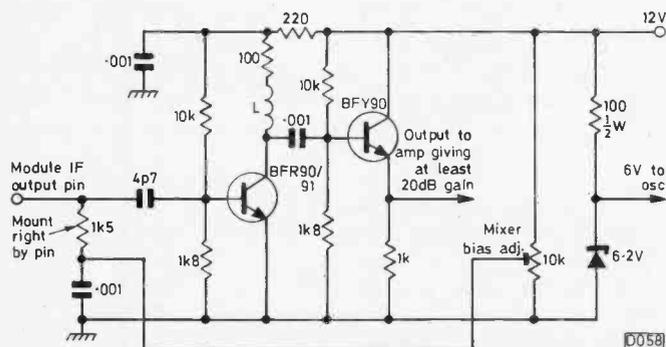


Fig. 3: U.H.F. i.f. preamplifier and mixer bias circuits. Take the output to a further wideband u.h.f. amplifier with a gain of at least 20dB. An additional amplifier prior to the receiver may help as well. Coil L consists of two turns 1/8in. diameter wound on a resistor.

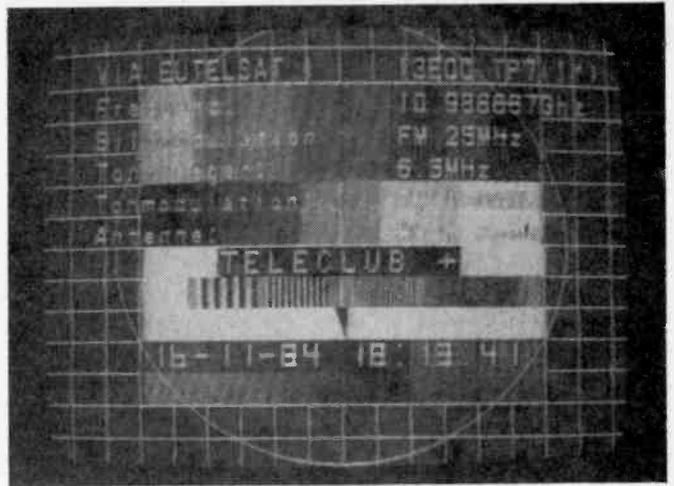


Photo 3: Teletext signal received with no LNA using a 1.8m dish.

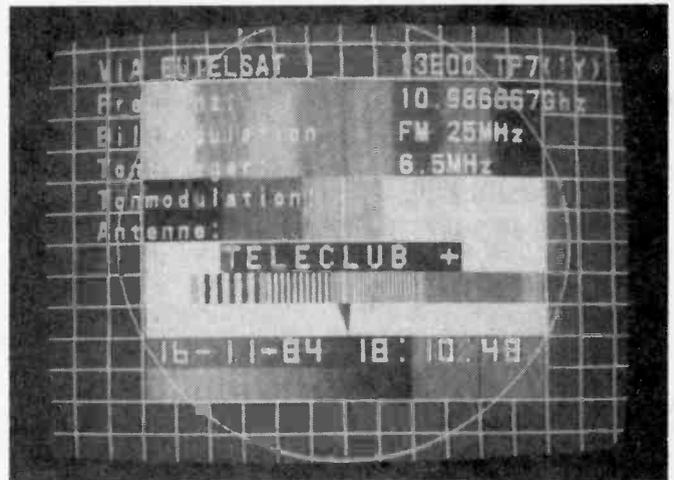


Photo 4: Same signal as shown in Fig. 3 but this time received with the addition of an LNA.

five minute period if possible, though I've never destroyed a module yet even when using very heavy duty soldering irons. It's essential for the first amplifier can to be right by the module otherwise local u.h.f. station breakthrough will be bad. You could make the first amplifier stage's base bias variable so that the system's noise figure can be optimised, though this doesn't in practice seem to help very much.

The Schottky diode requires forward bias. A preset and series feed resistor are included for this purpose. The bias required varies from the low to the high end of the band: less is required at the top end while almost maximum is required at the lower end. It can also vary depending on the i.f. used. The preset can be located anywhere that's convenient after the series feed resistor and decoupling capacitor. If a u.h.f. amplifier bias preset is also used the two can be mounted together. Test the amplifier thoroughly before connecting it to the module. Applying a screwdriver to the input connection should nowadays give good local signal reception unless you live in a very screened location.

The module application note recommends the use of a 100Ω resistor to chassis at the i.f. output connection to facilitate matching. On all the units I've tried this merely reduces the signal levels considerably. The diode's output impedance is supposedly quite high, but a fair match into the first amplifier stage is obtained. Some optimisation

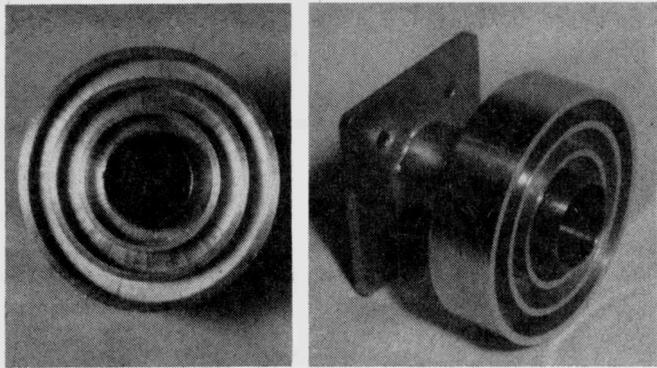


Photo 5 (left): Scalar feedhorn, showing front rings.

Photo 6 (right): Side view of the horn – the rings are adjustable with respect to the waveguide pipe.

could no doubt be obtained with the coupling.

The module requires a 6V supply which is easily obtained by means of a 100Ω, ½W resistor (minimum rating) and 6.2V zener diode connected across the 12V rail. The 6V consumption is quite high – around 50-60mA – and the GaAsFET chip may be quite warm in operation.

Testing the Module

To check that the oscillator is working, remove the mixer diode bias and power the oscillator, after checking that its d.c. consumption is 50-60mA or so. When a meter on a very low voltage range is connected to the output pin a reading of up to ±0.5V should be obtained, varying when one's hand is placed over the flange. This shows that the oscillator is working. Don't look down the waveguide when the unit is working as some of the oscillator signal comes out and can cause eye damage if you look for any length of time at a very close distance.

Connect the mixer bias and the u.h.f. amplifier to the output pin. You'll find that there's no additional noise when the module is powered and no LNA is used.

The oscillator is set at around 10.46GHz when the module leaves the factory. No problem should be had in checking this if a suitable signal generator is to hand – but more than likely it won't be! A 4GHz signal generator will give a good output at the third harmonic and should enable some checking to be done. If you've no gear at all, set the mixer bias at nearly maximum: you can be fairly confident that the unit will convert 11GHz to around 550-600MHz, which is the signal of interest for testing.

It's likely that the local u.h.f. transmissions will be at a very high level. Use good quality cable, as short in length as possible, with the u.h.f. amplifiers well screened. If group A signals are still intrusive, the i.f. output can be tuned to a quiet part of the band (see later).

Feedhorns

The standard "burglar alarm" horn will fit on the front of the module but is not particularly efficient for picking up signals from a dish. A scalar feedhorn (see Fig. 4) will give 1-2dB more. This consists of a series of rings mounted on a circular pipe: the position of the rings is adjustable and can be optimised once signals have been found. Ready made feedhorns can be purchased from the suppliers listed at the end of this article. These generally have a WG17/WR75 flange which matches the module's waveguide but not the flange holes. All you need to do is

to drill out the holes in the module a little.

If you construct the scalar ring this is easiest to do using copper sheet, though it can be tedious to say the least! The pipe is easiest made from 22mm diameter copper tube. If you are worried about oscillator leakage from the waveguide, with the pipe exactly 0.64in. in diameter the incoming satellite signals will pass down it without attenuation but steep attenuation will occur below 10.7GHz. If you are tuned to the top end of the ECS-1 band however the oscillator will be at 10.9GHz to obtain an 800MHz i.f. output so there will still be radiation. Note that the 0.64in. pipe tolerance is very precise: some reaming out of smaller bore pipe may be necessary, in which case ensure that the inside finish is smooth – microwave signals hate rough insides and any sort of corrosion.

A scalar feedhorn will generally cope with a dish down to 0.33 f/d ratio (ratio of the focal point to the diameter). A lot of surplus "radar" dishes are around 0.25 f/d, which means that the focus point is right at the rim of the dish. It's very difficult for a scalar feedhorn to see the entire surface of this type of dish so it's better to employ a subreflector feed system. It'll be fine for finding signals however – it's just that your 1.8m dish will give signals akin to those obtained with a 1.5m dish!


The flange can be attached directly to the end of the pipe. You can experiment with circular to rectangular transitions, but for a basic system a circular pipe going straight on to a rectangular flange will work. The addition of some tuning screws in the horn near the flange may help a little, more so if there's mismatching into an LNA. The ideal diameter for the screws is 6BA – the nut can be glued to the pipe with epoxy. The easiest way to hold the screw in place while drying is to attach the screw to the nut, screw it into the pipe and tape the assembly over whilst checking that it's at 90° to the pipe.

Finding the Signals

We now come to the hardest part of all, initially locating the ECS-1 satellite with an unknown converter, an unknown dish which will have a beamwidth of around 1° and an i.f. possibly not known to within 100MHz! If possible use a dish of at least 1.8m, preferably of fibreglass or solid construction. The performance of petal dishes at around 11GHz is erratic, and the construction will usually result in a loss of at least 6dB.

The easiest signal to find initially is the Swiss Teleclub at approximately 10.99GHz with vertical polarisation (see photos 3-4). It's on test pattern all day until around 1815 GMT and after closedown at around 2330. The pattern conveniently lists the signal's characteristics. Vertical polarisation corresponds to the narrow side of the waveguide being vertical. The polarisation is not actually dead horizontal/vertical unless one is directly beneath the satellite: for the UK there will be an offset of 5-10°. You

Fig. 4: Scalar feedhorn – construction of rings. The height of the rings is 8mm. Up to seven rings can be used – experiment for best results. Slide the assembly over the waveguide pipe and optimise reception for the individual dish.

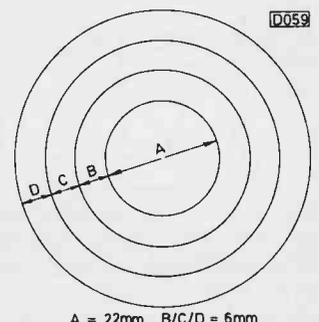

won't need to worry about this for initial setting up. With a dish on a polar mount the polarisation can be set at exactly vertical/horizontal at due south and will keep to the correct offset on any satellite to the east or west as the dish is swung round.

The approximate co-ordinates for ECS-1 at 13° east over the equator are 30° elevation and 163° ETN (east of true north) for London, corresponding to a local hour angle of 14.5°E on a polar mount. An accurate inclinometer is highly recommended. Set the dish elevation (if on an azimuth/elevation mount), then swing the dish through the estimated azimuth position, varying the elevation setting by half a degree or so on each swing. With this method the satellite will be found sooner or later provided the dish and the electronics are both working normally.

Mount the converter feedhorn at the focus of the dish, allowing up to 5mm backward and forward movement for peaking the focus. In general the focus will occur 0.5-1cm inside the feedhorn. Take all the receiving equipment out to the dish and connect some form of signal strength indicator – due to the sharpness of the beamwidth and the fact that the adjustments are more critical than at 4GHz a signal strength meter is invaluable. Fig. 5 shows a simple circuit using a diode detector and an operational amplifier which can be used to drive a meter.

As the oscillator in the module is adjusted, the Teleclub signal will appear at around 550-600MHz. If this band is congested (local group A signals at high strength), screw the DRO plate out by approximately 1.5 turns. This will lower the oscillator signal by some 200MHz, giving an i.f. output at around 750-800MHz. If you use an f.m. receiver that's been used for Gorizont reception the picture should lock immediately, possibly with a slight energy dispersal flicker. The normal (as opposed to the Russian) energy dispersal standard is at half field rate with a narrow deviation. This should be removed by the d.c. clamping action in the TV set but may still be present if the signal is weak.

Once the signal has been found, peak the focus and dish alignment. Then screw the module's front tuning screw in (as mentioned earlier, this should be screwed fully out initially). The signal should disappear when the screw is approximately half way in, reappearing as the screw goes in farther. A small peak will be found just prior to the notch and this will give a worthwhile increase in signal strength. The exact position will vary for different frequencies of course. The mixer bias (and u.h.f. amplifier bias if fitted) should also be optimised for best results.

If you are feeding the LNC's output to a standard u.h.f. TV set and using slope detection, finding the signal initially will be more difficult. The images will look

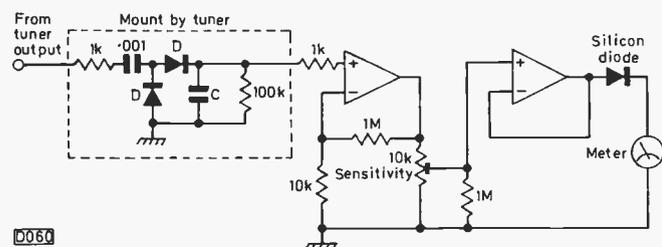


Fig. 5: Signal strength meter circuit. Diodes D type OA90 or similar. C is 0.001µF – if the readings vary a lot with the video content, increase the value of C to 0.1µF or more. The 10kΩ potentiometer adjusts the meter's sensitivity. Any type of operational amplifier will do.

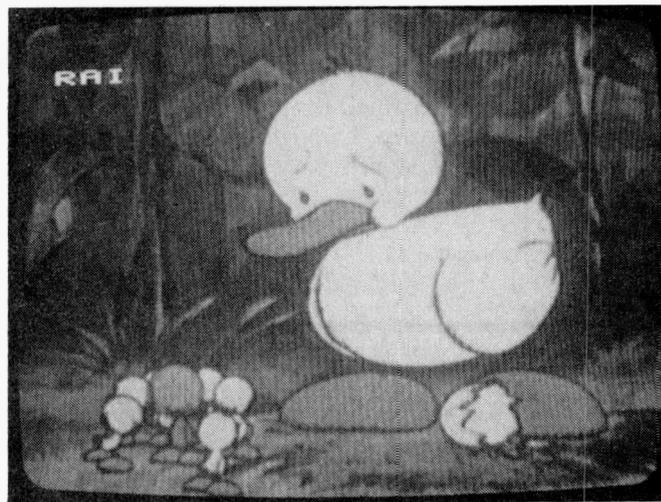


Photo 7: RAI-1 received via ECS-1.

weaker than they really are and will have the characteristic energy dispersal flicker.

It may take some time to find the satellite the first time (it took me two hours) due to the combination of unknown factors. It's worthwhile having an assistant to tune around while you are moving the dish – or vice versa.

If the polarisation is changed to horizontal, RAI-1 (Italy) should be found at around 11.005GHz, just above Teleclub and possibly a little weaker. At 11.175GHz Euro-TV (Holland) will be found, at present on test with colour bars. The Belgian Esselte service is at 11.15GHz with vertical polarisation. If the oscillator tuning (DRO) is set to give Teleclub at around 600MHz, Euro-TV should be present at around 770MHz, though some tweaking of the tuning screw for optimum results may be needed. TV5 (France) and Sky Channel are at the top of the band with horizontal polarisation, at 11.47GHz and 11.65GHz respectively. Screw the oscillator plate about two turns (possibly three turns) clockwise for the same i.f. as the lowband signals. PKS (Germany – to be renamed in 1985) is present at 11.51GHz and Music Box at 11.674GHz, both with vertical polarisation.

Results

With a 1.8m dish and a good feed, fair pictures will be seen on Teleclub, Euro-TV, TV5, PKS, Music Box and Sky Channel (the latter with Oak Orion coding). To get approaching noise-free signals a 3m dish is required. Using an LNA with bandpass filter will enable the dish size to be reduced to 1.5-1.8m for good to perfect pictures – a following article will describe this assembly. Building an LNA using stripline techniques is much easier now that GaAsFETs with a good noise figure are available, though the cost of the three GaAsFETs required is over £100. Supply delays often seem to happen, so if you intend to build the LNA we suggest you order the GaAsFETs now. The bandpass filter is ready-made in waveguide: it's not possible to adopt the DIY approach here due to the exact tolerances required. As mentioned earlier on, arrangements have been made to supply this item. The LNA case is built up from tinplate in a similar fashion to the downconverter modules and should not present any problems.

Suppliers

The GaAsFETs – two NE71083, one NE70083 – are

available from Microwave Modules Ltd., Brookfield Drive, Aintree, Liverpool L9 7AN (telephone 051 523 4011).

LNA boards, assemblies etc, will be available from Hugh Cocks TV Services, Cripps Corner, Robertsbridge, Sussex TN32 5RY (telephone 0580 083 317).

Downconverter modules, type FO-UP-11K without flange or FO-UP-11KF with flange, are available from Aspen Electronics Ltd., 2 Kildare Close, Eastcote, Ruislip, Middx HA4 9UR (telephone 01 868 1188). Order

a data sheet at the same time.

SP Antenna Systems, 3 Woolpack Corner, Biddenden, Ashford, Kent (telephone 0223 291 090) can supply feedhorns and 2m fibreglass dishes.

North East Satellite Systems, Cropton, Pickering, N. Yorks (telephone 075 15 598) can supply feedhorns and 1m/1.5m solid dishes.

STS Ltd., Baugh Farm, Church Lane, Downend, Bristol (telephone 0272 560 775) can supply feedhorns and dishes.

Workshop Decoder Alignment System

Denis G. Mott

Since the advent of colour television one of the greatest problems for service engineers has been the diagnosis of faults in the decoder. In colour TV receiver production there are problems with alignment and fault finding when an assembled decoder is defective. The following notes are applicable to both the repair and production of PAL decoders.

The earliest decoders used in the UK employed discrete component circuitry without an i.c. in sight. These had many presets and coils to twiddle. The next generation might have one or two i.c.s plus discrete component sections. This reduced the coil and preset count but there was still enough to provide the twiddler with his fun. The latest generation of single-chip decoders have few presets for the phantom twiddler. This latest generation generally produces only RGB outputs however and is not suited to the alignment procedure to be described.

Basic System

In our company decoders are assembled, aligned and repaired in a fully illuminated work area with each engineer testing, aligning and repairing up to seventy decoders a day. The boffins from the development laboratory, led by Rod Allison, came up with the following test/alignment method. It uses the Leader LCG399 colour pattern generator which can be set, by means of some internal switches, to give a colour-bar signal in which the lower half of the screen has bars that are 180° out of phase

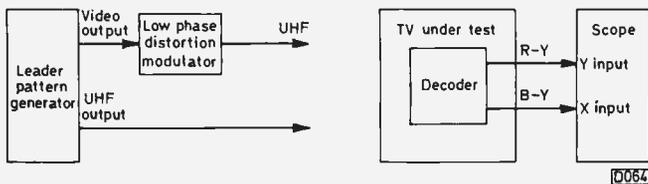


Fig. 1: Block diagram of the alignment system.

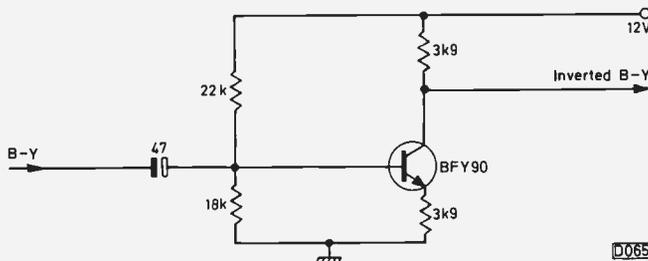


Fig. 2: Simple signal inverter circuit.

– the lowest few lines can be set for luminance only, to act as a reference. The system adopted is shown in block diagram form in Fig. 1.

The pattern generator can be connected directly to the TV set being tested, via the generator's r.f. output socket. Where multi-output distribution is required however the 1mV of r.f. output is not enough for passive splitting, while if an active distribution system is used phase shift can occur, causing problems with decoder alignment. Instead, the video output from the generator is fed to a low phase distortion modulator with an r.f. output of 10mV, which is reduced by splitter attenuation to 1mV.

Signal Inverter Circuit

The display scope is connected to the decoder as follows, with the timebase switched off: R – Y to the Y input, B – Y to the X input. In some circumstances it may be necessary to invert the colour difference outputs from the decoder. A suitable circuit is shown in Fig. 2.

Alignment Procedure

Now to alignment. The following procedure is based on the Network Models NWC1401/NWC1402, whose decoder circuit is shown in Fig. 3. A very similar decoder is used in the Grundig GSC100/GSC200 chassis. The procedure should be applicable to any decoder using the TDA2510 and TDA2521/2 i.c. combination – and of course the basic operation of PAL decoders is similar in all sets.

- (1) 6MHz sound trap. Unless the phantom twiddler has been at it this will never require setting. If it does require a tweak, disconnect the video input, connect a 6MHz input and adjust L2 for minimum signal with the scope connected to TP1.
- (2) Reference oscillator frequency. Connect the video input to the decoder, feed in the special colour-bar signal, short TP2 and TP3 together and to chassis and adjust trimmer C23 for stationary colour bars – just as you would when setting up a line timebase with flywheel sync.
- (3) Burst level. Connect the scope to TP2 and adjust the burst amplitude to 500mV with R30.
- (4) Phasing adjustments. A graticle is used with the scope giving a vector display. Connections are as shown in Fig. 1. With a correctly adjusted decoder the display shown in Fig. 4 should be seen. If there's a fault condition or misalignment the display could look something like Fig. 5. Turn the colour control to maximum and concentrate on

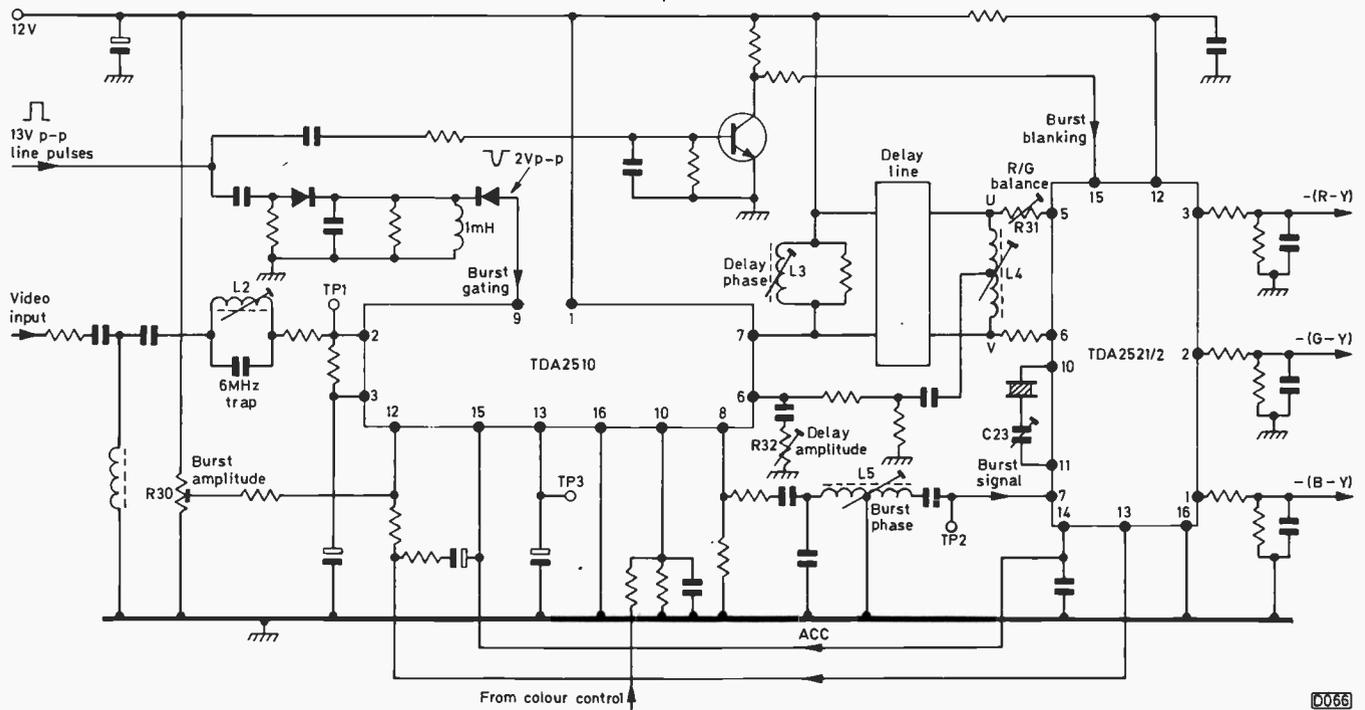


Fig. 3: The two-chip decoder used in Network Models NWC1401 and NWC1402 (simplified circuit).

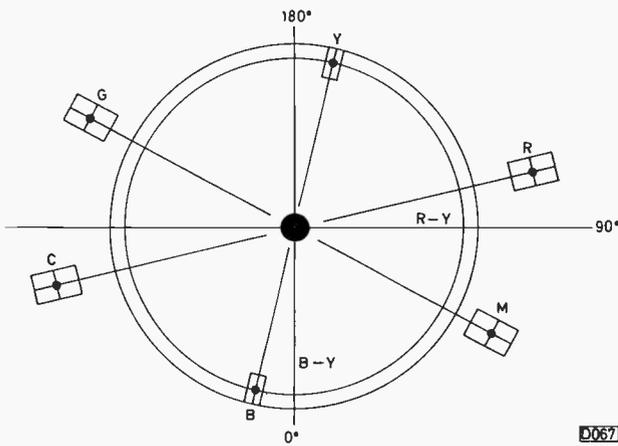


Fig. 4: Scope vector display obtained with a correctly adjusted decoder. The display arises from the fact that the scope's X and Y axes coincide with the B - Y and R - Y axes respectively: with a colour bar signal of the type used outer dots are obtained at the phase positions corresponding with the colours in the pattern.

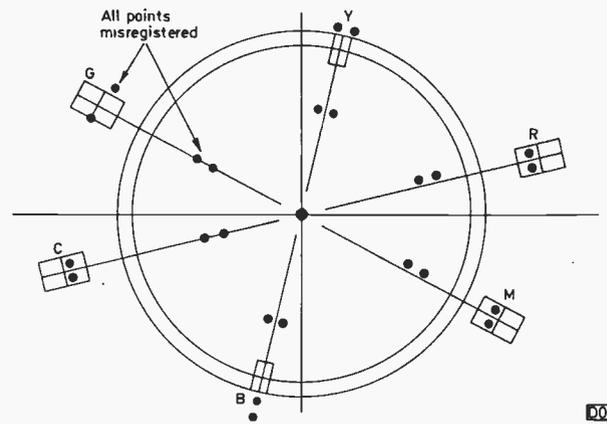


Fig. 5: Type of display obtained with a misaligned or faulty decoder.

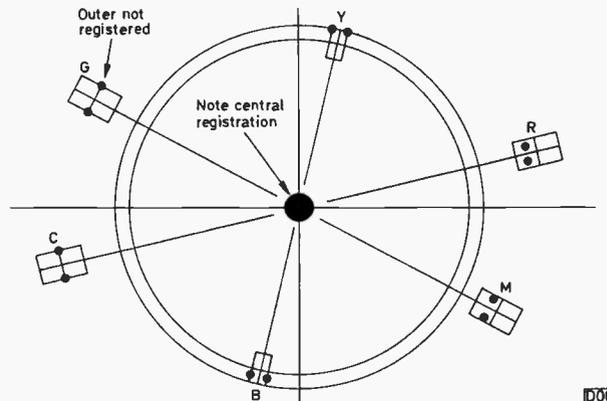


Fig. 6: Initial phasing adjustments.

the central area, adjusting R32 (delay amplitude) and L5 (burst phase) to reduce the area covered, as in Fig. 6.

Reduce the colour control setting to bring the outer dots into view. Adjust L3 (delay line phase) and L4 (matrixing coil) so that the outer dots register. Then give R32 and L5 a final tweak.

(5) R/B balance. Use the scope to monitor the R - Y and B - Y outputs as before, but set the timebase to approximately $20\mu\text{sec}/\text{cm}$. Adjust R31 (R/B balance) for a ratio of R = 4cm, B = 5cm. This final adjustment should produce a TV display with reasonably colourless squares in the lower region - compare with the luminance only signal at the bottom.

In Conclusion

Try the system first with a known good decoder. This will enable you to find out what effects what in your

decoder. The system was designed with the Leader LCG399 in mind, but there are probably other generators that give the same type of signal.

Finally, my thanks to R. Allison, J. Clarke and Network Industries Ltd.

Another Smash Hit

Les Lawry-Johns

After another long and weary day of mending TVs then watching TV in the evening we at last got to bed and dropped off into a deep sleep. We were awakened at one o'clock in the morning by a loud crash. I leapt out of bed and rushed down the stairs shouting at the top of my voice, informing the window smashers that they were born of unmarried parents. Such was the speed of my descent (naked as usual) that the smashers fled before taking a thing. I was hardly in a fit state to run out into the street so, after taking note of which window had been smashed, I ran back upstairs to pull my trousers on (having rung the police). There followed the usual clearing up operation, which was especially hard on Honey Bunch because she'd worked so well and long decorating the windows with Christmas decorations. They'd looked nice, very very nice.

We cleared up the mess and boarded the window (the small one this time), had a cup of tea and returned to bed, laying awake for a long time as we half expected another crash. I was plotting ways of laying a grid inside the windows connected to a 25kV e.h.t. supply. Something less I decided, in case I should hurt myself. Why anyone finds it worthwhile smashing the windows beats me: we always take the expensive bits out every night. They must do it for fun. So the grids will go up. I wonder whether that will stop them? Somehow I doubt it.

That Evening

We felt a bit depressed the following evening so we went next door to the Coach and Horses for a drink. Sylvia the landlady served us and she and HB chatted for a while about knitting patterns. Then HB went over to the fruit machine and lost some money while dreaming about making some. I sat at the bar and dreamed, waking with a start as I heard myself snoring. Just then Tony walked in. He's an avid reader of this magazine and has been for some years.

"You're slipping Les" he greeted me. I sat up straight and wiped the sleep from my eyes. "no you fool, not off your stool, I mean your articles are getting a bit dreary. You've lost your zest, your get up and go if you know what I mean."

I nodded miserably. "I know what you mean Tony. My get up went down and my go just went – some time ago. Sorry, very sorry."

Tony looked a bit mystified, then tried again. "No Les, we know you're getting on a bit and probably feel a bit jaded. But it used to be fun reading your adventure stories – how you won the Battle of Britain single handed, how you fought the Red Baron in the first war when he said your Camel was sippy, how you passed wind through the Great Wall of China. We never have any of that old tripe now. What's happened?"

"Well the editor didn't think he should print the last one about when we got lost up the Yukon and bumped into Eskimo Nell. He said it was too rude and I think he was right. I mean who wants to read what Dead Eye Dick had in his hand?" Tony gave a cough and turned away as

Sylvia approached with the drinks. Sylvia doesn't like naughty songs and always looks daggers at me when I start to sing the Lobster Song. We all have to be on our best behaviour when Sylv's around. That's why Dave sends her upstairs sometimes, when the boys start telling each others' fortunes.

So we had a couple and called it a day, HB having scooped up all our change and bunged it back into the machine that kept telling her to leave the combinations to it to decide. But she wouldn't listen.

Next Day

Next day there was a long procession of idiots who each knew exactly what was wrong with their sets and didn't like it when I told them they were wrong. One chap said his fuse had gone. I spent some time proving that it was the line output transformer that was blowing the 800mA fuse in his G8, then he said he didn't want it done anyway. I helped him out with the set and he then turned and said he felt he should give me something for my trouble. So he pulled this orange out of his pocket and handed it to me. I gave it back saying I don't like oranges. Then he pulled this ten penny piece out. I told him to b...r off. Is it any wonder I get dispirited at times?

Look what happened when a chap brought in his ITT CVC9 (20in. version). He complained about the focusing and said he thought it was the tube. I chided him for thinking such a thing. "The smaller 20 and 22in. tubes in these sets last forever." I mean, just everyone knows that the resistors in the focus network change value and that if it isn't the one on the tube base it's one of the 4.7M Ω ones in series with the focus control. So I checked the 2.2M Ω resistor on the tube base panel and it was all right. I took off the line output stage cover and checked the two 4.7M Ω resistors. They were all right. So I changed the focus VDR itself and the decoupling capacitor for good measure. No change. I thought the resistors could be telling lies so I fitted some new ones. All to no avail and the voltage was spot on. I didn't believe the meter – it's played tricks before – so changed the tripler. The focus was as bad as ever and I had to conclude that the tube was indeed at fault.

"I thought you said the tubes last forever . . ."

A Lecture from Les

Having proved that I know nothing about ITT sets I'll now give you a bit of advice which you probably don't need.

Whenever you get a CVC32 or one of that ilk in for service for whatever reason, always check the small subpanel over the top of the scanning coils. Take it out (unclip it) and turn it over to check the contacts on the print side. You'll be glad you did (well I'm always glad that I do anyway). There's always one contact at least that's about to cause trouble. End of lecture.

Finale

We have a couple of large blocks of flats opposite the shop and I'm often asked to "pop over" to check a TV set or something. They never know the make or model number so if I do go I have to lug quite a load of stuff with me in order to be reasonably sure of doing the job. By the time I've walked over to the flats, gone up to say the seventh floor, then walked along the corridors I'll prob-

ably be feeling a bit puffed. You repair the set, replacing maybe a fuse and a transistor, then test it and line it up. Then you pack your kit bags as it were and prepare to leave. The lady has a pound note in her hand and is saying

"I must pay you something". You don't want to offend, so you decline the reward and leave. As you go out of the door you hear her call out "if we get any other little jobs I'll give you a shout" . . .

Letters

DISCO-LIGHT EFFECT

Les Lawry-Johns mentioned a disco-light effect in the November issue. I've seen similar effects several times, due to loose shadowmasks in tubes. The mask seems to become partially detached within the c.r.t. and gets too hot. This leads to expansion with loss of purity etc. due to movement of the mask from its correct plane.

A tube with this fault will sometimes give a perfectly good display when the set is switched on from cold, going berserk as the shadowmask heats up. A similar effect can be produced by placing a shadowmask from a scrap tube against the face of a good working c.r.t. and moving it about. By keeping the mask still, the individual triad structure of the phosphor dots can be seen. To date I've seen this fault only in delta-gun tubes.

M.J. McHugh,
Hednesford, Staffs.

N1700 TIMER RECORDINGS

It doesn't seem to be too well known that to make an unattended recording of more than two hours on a Philips N1700 VCR all one has to do after setting the timer is to make sure that the time setting switch is not returned to the "lock" position. In any other position the recording will be started by the electronic clock and will continue to the end of the tape, being switched off by the stop foil. May I add that the speed reduction modification given in the April 1983 issue of *Television* works very well.

E.A. Evans,
Taunton, Somerset.

THE VIEW MASTER

I found Chas E. Miller's vintage TV article on the View Master (December) very nostalgic – I built one of these sets by way of a return to electronics after radio in the 20s followed by a period at University and then war work. Chas has clearly described one of the later models however – I believe there were several. The first appeared in approximately 1946, just after the war, when both Pye and Ekco had 9in. table model t.r.f. sets that sold for about £45. This first model – the one I built – was rather less sophisticated than the one described by Chas Miller. The e.h.t. (7kV) was obtained from a mains transformer instead of being flyback derived, there was electromagnetic focusing, and a full-wave rectifier was used for the h.t. supply. The set nevertheless gave superb results in the area covered by the Alexandra Palace transmitter.

At this time, and for two-three years, there was no question of being able to obtain a 12in. tube – unless you were friendly with someone "in the know". The 9in. size was the order of the day, without internal aluminising (ion burn was very common) and external Aquadag coating, so that high-voltage capacitors were required to smooth the 50Hz e.h.t. The first commercially available receiver with flyback e.h.t. was the Pye B18T, a 9in. table model released in July 1948. The valve e.h.t. rectifier was

encapsulated with the line output transformer in bitumen.

Finally, *Wireless World* about this time designed and described a real DIY television set. In contrast with the View Master, everything that could be made by the constructor was described, even the scan yoke. There was flyback e.h.t. with a voltage tripler that employed metal rectifiers. It was originally a t.r.f. design, but a superhet version followed – very useful for frequency changing as the Birmingham transmitter had by then come into service.

J.B. Haley, Ph.D., C.Chem., F.R.S.C.,
Fleet, Hants.

AIRBORNE TV

In the December issue Roger Bunney mentioned airborne TV experiments carried out during the 1960s. A British book published in 1949, *The Television Guide* by Dr. W. Summer, gave details of American transmissions during the 1940s. The Stratovision project as it was called was undertaken by the Westinghouse Corporation, and the pictures of the aeroplane and the transmitter on board indicate that at least the experiment got off the ground. A map showed that virtually all the States could be covered by fourteen aircraft: a 1kW transmitter at 30,000 feet was said to have a service area radius of 400 miles across, giving the same signal as a 50kW ground-based transmitter.

Incidentally, recent discussion of pre-war television may have given the impression that the Americans used the 525-line standard from the start. This is not so: the pre-war system used 441 lines.

Finally a request. I'm assembling a collection of broadcast test card material and have already acquired more than a dozen different monoscope tubes and as many 35mm slides. I'd be pleased to hear from anyone who has items to dispose of.

Andrew Emmerson,
71 Falcutt Way,
Northampton NN2 8PH.

Editorial note: The effective starting date for regular TV services in the USA was July 1st, 1941 – with 525 lines. Previous services were allowed by the FCC on an experimental basis only. They used 441 lines, though RCA had used 240 and 343 lines for demonstration purposes in the early 1930s. An excellent and very detailed article on the early days of TV in the USA appeared in the March 1982 issue of *Radio-Electronics*.

Book Note

The second edition of the *Antenna Engineering Handbook*, edited by Richard C. Johnson and Henry Jasik, has been published by the McGraw-Hill Book Company at £76. This sumptuous book contains 1,408 pages and deals with just about every type of aerial, with the emphasis on design rather than installation etc. The material is of US origin, which means for example that in the section on TV receiving aerials the use of 300Ω twin feeder is assumed and US channels are specified.

ECONOMIC DEVICES, PO BOX 228, TELFORD TF2 8QP

| | | | | | | | | | | | | | | | | | |
|---------|------|-------------|--------|-------------|------|--------------|-------|---------|------|--------|------|---------|------|-----------|------|-----------|------|
| 16029 | 1.50 | ZSC1061 | 0.54 | ZSD898B | 2.67 | AN320 | 4.97 | BC171 | 0.10 | BD166 | 0.38 | BF137 | 0.11 | BLY49 | 2.00 | BY203/20 | 0.18 |
| 16181 | 1.13 | ZSC1066 | 1.05 | 40408 | 0.45 | AN322 | 4.38 | BC172 | 0.09 | BD168 | 0.66 | BF152 | 0.28 | BR100 | 0.20 | BY206 | 0.17 |
| 16182 | 1.13 | ZSC1104 | 2.60 | 40594 | 1.39 | AN331 | 2.99 | BC172B | 0.24 | BD175 | 0.39 | BF153 | 0.52 | BR101 | 0.37 | BY207 | 0.22 |
| 16334 | 0.86 | ZSC1106 | 4.12 | 40595 | 1.39 | AN337 | 3.99 | BC173 | 0.15 | BD177 | 0.39 | BF154 | 0.23 | BR103 | 0.45 | BY210-400 | 0.24 |
| 16335 | 0.72 | ZSC1114 | 5.01 | 40636 | 0.86 | AN340P | 1.06 | BC174B | 0.24 | BD179 | 0.44 | BF157 | 0.23 | BR888 | 0.58 | BY210-600 | 0.27 |
| 16446 | 0.89 | ZSC1124 | 1.10 | 40871 | 1.39 | AN355 | 3.36 | BC177 | 0.18 | BD181 | 0.90 | BF158 | 0.16 | BRC-M-300 | 1.58 | BY210-800 | 0.30 |
| 16600 | 1.25 | ZSC1151A | 4.25 | 40872 | 1.39 | AN362 | 1.47 | BC178 | 0.23 | BD182 | 0.90 | BF159 | 0.16 | BRC116 | 0.60 | BY223 | 0.85 |
| 16799 | 2.16 | ZSC1152 | 4.25 | 60957 | 1.10 | AN5111 | 2.34 | BC179 | 0.23 | BD183 | 0.90 | BF160 | 0.28 | BRC1300 | 1.60 | BY224-400 | 0.90 |
| 16801 | 0.86 | ZSC1157 | 4.12 | 74LS132 | 0.72 | AN5132 | 3.99 | BC182 | 0.06 | BD184 | 1.10 | BF167 | 0.34 | BRC300 | 1.82 | BY225-100 | 0.79 |
| 16802 | 1.03 | ZSC1162 | 0.95 | 74LS138 | 0.85 | AN5250 | 3.33 | BC182B | 0.23 | BD187 | 0.48 | BF173 | 0.30 | BRC4443 | 1.12 | BY226 | 0.28 |
| 16803 | 4.81 | ZSC1172 | 1.92 | 74LS157 | 0.79 | AN5435 | 2.80 | BC182L | 0.09 | BD189 | 0.35 | BF177 | 0.50 | BRC4444 | 1.12 | BY227 | 0.44 |
| 16905 | 1.35 | ZSC1195 | 2.83 | 74LS161AN | 1.18 | AN5610 | 6.75 | BC182LB | 0.12 | BD190 | 0.59 | BF178 | 0.35 | BRCS296 | 0.70 | BY228 | 0.54 |
| 17074 | 6.00 | ZSC1213 | 0.75 | 74LS196 | 1.25 | AN5613 | 3.72 | BC183 | 0.09 | BD201 | 0.54 | BF179 | 0.32 | BRCS109 | 0.75 | BY225 | 0.97 |
| 17127 | 3.91 | ZSC1226 | 1.32 | 74LS20 | 0.25 | AN5620X | 4.63 | BC183L | 0.23 | BD202 | 0.54 | BF180 | 0.32 | BRCS2 | 0.98 | BY298 | 0.25 |
| 17376 | 1.43 | ZSC1306 | 0.85 | 74LS244 | 1.65 | AN6329N | 3.89 | BC183LB | 0.09 | BD204 | 0.54 | BF182 | 0.29 | BRCS3 | 0.98 | BY299 | 0.25 |
| 1N4001 | 0.05 | ZSC1307 | 1.35 | 74LS30 | 0.29 | AN6342 | 1.36 | BC184 | 0.09 | BD207 | 1.00 | BF183 | 0.35 | BRCS4 | 0.98 | BY276A | 0.76 |
| 1N4002 | 0.05 | ZSC1316 | 3.40 | 74LS367 | 1.05 | AN6344 | 4.68 | BC184L | 0.23 | BD208 | 1.00 | BF184 | 0.39 | BRCS4 | 0.98 | BY4656 | 0.30 |
| 1N4003 | 0.05 | ZSC1364 | 0.49 | 74LS373 | 1.55 | AN6363 | 10.20 | BC184LB | 0.23 | BD222 | 0.44 | BF185 | 0.35 | BRCS4 | 0.98 | BY476A | 0.76 |
| 1N4004 | 0.06 | ZSC1383 | 1.39 | 74LS47 | 0.09 | AN6551 | 0.56 | BC186 | 0.24 | BD222 | 0.44 | BF185 | 0.35 | BRCS4 | 0.98 | BY476A | 0.76 |
| 1N4005 | 0.07 | ZSC1398 | 0.51 | 74LS73 | 0.39 | AN6552 | 0.52 | BC187 | 0.18 | BD225 | 0.44 | BF194 | 0.15 | BRCS4 | 0.98 | BY476A | 0.76 |
| 1N4006 | 0.07 | ZSC1410 | 2.17 | 74LS74 | 0.39 | AN7145 | 2.04 | BC204 | 0.14 | BD228 | 0.57 | BF195 | 0.12 | BRCS4 | 0.98 | BY476A | 0.76 |
| 1N4007 | 0.07 | ZSC1413 | 3.68 | 74LS75 | 0.52 | AN7150 | 2.22 | BC207 | 0.10 | BD229 | 0.63 | BF196 | 0.15 | BRCS4 | 0.98 | BY476A | 0.76 |
| 1N4148 | 0.03 | ZSC1505 | 0.56 | 74LS86 | 0.49 | AN7151 | 2.05 | BC212 | 0.10 | BD231 | 0.45 | BF197 | 0.14 | BRCS4 | 0.98 | BY476A | 0.76 |
| 1N4448 | 0.12 | ZSC1578 | 6.67 | 74LS90 | 0.75 | AN7156 | 2.05 | BC212B | 0.23 | BD232 | 0.45 | BF198 | 0.15 | BRCS4 | 0.98 | BY476A | 0.76 |
| 1N5401 | 0.12 | ZSC1617 | 3.35 | 74LS92 | 0.75 | AN7158 | 2.34 | BC212L | 0.09 | BD234 | 0.38 | BF199 | 0.15 | BRCS4 | 0.98 | BY476A | 0.76 |
| 1N5402 | 0.13 | ZSC1670 | 2.84 | 74LS93 | 0.75 | AN7218 | 1.49 | BC212LB | 0.23 | BD235 | 0.43 | BF200 | 0.32 | BRCS4 | 0.98 | BY476A | 0.76 |
| 1N5403 | 0.14 | ZSC1678 | 1.25 | 74LS95B | 0.85 | AP58076 | 4.25 | BC213 | 0.09 | BD236 | 0.45 | BF216 | 0.32 | BRCS4 | 0.98 | BY476A | 0.76 |
| 1N5404 | 0.15 | ZSC1810 | 1.40 | 7805 TD-220 | 0.63 | AS5605 | 4.03 | BC213L | 0.09 | BD237 | 0.38 | BF218 | 0.32 | BRCS4 | 0.98 | BY476A | 0.76 |
| 1N5408 | 0.18 | ZSC1815 | 0.21 | 7805 TO-3 | 1.05 | AU106 | 1.96 | BC213B | 0.23 | BD238 | 0.29 | BF222 | 0.50 | BRCS4 | 0.98 | BY476A | 0.76 |
| 1N914 | 0.05 | ZSC1829 | 2.01 | 7806 | 0.66 | AU110 | 1.96 | BC214 | 0.09 | BD239 | 0.44 | BF224 | 0.15 | BRCS4 | 0.98 | BY476A | 0.76 |
| 1S44 | 0.06 | ZSC1875 | 4.77 | 7808 | 0.54 | AU113 | 2.15 | BC214L | 0.12 | BD240 | 0.36 | BF237 | 0.59 | BRCS4 | 0.98 | BY476A | 0.76 |
| 1S5012A | 0.73 | ZSC1891 | 3.35 | 7812 TD-3 | 0.54 | AY102 | 2.62 | BC214LB | 0.23 | BD240D | 0.47 | BF240 | 0.15 | BRCS4 | 0.98 | BY476A | 0.76 |
| 1S921 | 0.09 | ZSC1929 | 2.25 | 7812 TD-220 | 1.05 | AY105K | 1.89 | BC225 | 0.24 | BD241 | 0.45 | BF241 | 0.15 | BRCS4 | 0.98 | BY476A | 0.76 |
| 2582 | 1.94 | ZSC1942 | 5.70 | 7815 | 0.55 | AY106 | 0.55 | BC227 | 0.09 | BD242 | 0.45 | BF244 | 0.23 | BRCS4 | 0.98 | BY476A | 0.76 |
| 2N1302 | 0.24 | ZSC1945 | 4.11 | 7818 | 0.55 | BA102 | 0.30 | BC238 | 0.09 | BD243 | 0.44 | BF245A | 0.33 | BRCS4 | 0.98 | BY476A | 0.76 |
| 2N1303 | 0.34 | ZSC1953 | 1.75 | 7824 | 0.55 | BA1310 (IC) | 1.72 | BC238A | 0.11 | BD243A | 0.50 | BF255 | 0.18 | BRCS4 | 0.98 | BY476A | 0.76 |
| 2N2218 | 0.38 | ZSC1957 | 0.86 | AC107 | 0.66 | BA1320 (IC) | 1.22 | BC239B | 0.08 | BD244 | 0.44 | BF256 | 0.28 | BRCS4 | 0.98 | BY476A | 0.76 |
| 2N2219A | 0.29 | ZSC1959 | 0.36 | AC117 | 0.39 | BA1330 (IC) | 1.82 | BC251A | 0.15 | BD244A | 0.77 | BF256LC | 0.35 | BRCS4 | 0.98 | BY476A | 0.76 |
| 2N2222 | 0.34 | ZSC1962 | 1.75 | AC123K | 0.39 | BA145 | 0.17 | BC252 | 0.12 | BD245C | 0.68 | BF257 | 0.30 | BRCS4 | 0.98 | BY476A | 0.76 |
| 2N2646 | 0.75 | ZSC1969 | 2.92 | AC128 | 0.28 | BA154 | 0.08 | BC258 | 0.22 | BD246C | 0.74 | BF258 | 0.29 | BRCS4 | 0.98 | BY476A | 0.76 |
| 2N2904 | 0.32 | ZSC2027 | 2.67 | AC138 | 0.08 | BA155-01 | 0.12 | BC261A | 0.20 | BD253 | 0.95 | BF259 | 0.30 | BRCS4 | 0.98 | BY476A | 0.76 |
| 2N2905 | 0.39 | ZSC2028 | 1.91 | AC141 | 0.26 | BA156 | 0.12 | BC262 | 0.20 | BD278A | 0.60 | BF262 | 0.51 | BRCS4 | 0.98 | BY476A | 0.76 |
| 2N2906 | 0.34 | ZSC2029 | 1.49 | AC142K | 0.39 | BA157 | 0.17 | BC287 | 0.45 | BD317 | 1.96 | BF263 | 0.51 | BRCS4 | 0.98 | BY476A | 0.76 |
| 2N3053 | 0.24 | ZSC2057 | 1.07 | AC151 | 0.25 | BA159 | 0.12 | BC294 | 0.45 | BD318 | 2.08 | BF264 | 0.33 | BRCS4 | 0.98 | BY476A | 0.76 |
| 2N3054 | 0.90 | ZSC2073 | 1.40 | AC153 | 0.30 | BA182 | 0.17 | BC301 | 0.36 | BD375 | 0.38 | BF271 | 0.30 | BRCS4 | 0.98 | BY476A | 0.76 |
| 2N3055 | 0.55 | ZSC2078 | 1.25 | AC153K | 0.36 | BA222 (IC) | 1.26 | BC302 | 0.30 | BD377 | 0.23 | BF273 | 0.18 | BRCS4 | 0.98 | BY476A | 0.76 |
| 2N3056H | 0.77 | ZSC2091 | 0.59 | AC176 | 0.17 | BA2842 | 0.15 | BC303 | 0.34 | BD379 | 0.69 | BF274 | 0.18 | BRCS4 | 0.98 | BY476A | 0.76 |
| 2N3442 | 1.05 | ZSC2122A | 4.65 | AC176K | 0.40 | BA301 (IC) | 0.92 | BC307 | 0.09 | BD380 | 0.69 | BF324 | 0.16 | BRCS4 | 0.98 | BY476A | 0.76 |
| 2N3702 | 0.12 | ZSC2141 | 1.69 | AC179 | 0.25 | BA302 | 0.90 | BC307A | 0.14 | BD410 | 0.44 | BF336 | 0.27 | BRCS4 | 0.98 | BY476A | 0.76 |
| 2N3703 | 0.12 | ZSC2166 | 1.35 | AC183 | 0.65 | BA311 (IC) | 1.06 | BC308 | 0.12 | BD412 | 5.70 | BF337 | 0.36 | BRCS4 | 0.98 | BY476A | 0.76 |
| 2N3704 | 0.12 | ZSC2216 | 0.62 | AC186 | 0.30 | BA312 (IC) | 0.96 | BC308A | 0.09 | BD418 | 0.76 | BF338 | 0.36 | BRCS4 | 0.98 | BY476A | 0.76 |
| 2N3705 | 0.12 | ZSC2233 | 2.20 | AC186K | 0.50 | BA313 (IC) | 1.28 | BC309 | 0.15 | BD433 | 0.33 | BF355 | 0.36 | BRCS4 | 0.98 | BY476A | 0.76 |
| 2N3706 | 0.12 | ZSC2271 | 3.64 | AC187 | 0.35 | BA316 | 0.07 | BC317A | 0.11 | BD434 | 0.39 | BF362 | 0.54 | BRCS4 | 0.98 | BY476A | 0.76 |
| 2N3707 | 0.14 | ZSC2278 | 1.03 | AC187-01 | 0.40 | BA317 | 0.07 | BC323 | 0.92 | BD435 | 0.42 | BF363 | 0.54 | BRCS4 | 0.98 | BY476A | 0.76 |
| 2N3711 | 0.14 | ZSC2335-KIT | 7.61 | AC187K | 0.39 | BA318 | 0.08 | BC327 | 0.15 | BD436 | 0.42 | BF371 | 0.45 | BRCS4 | 0.98 | BY476A | 0.76 |
| 2N3771 | 1.85 | ZSC2526 | 1.70 | AC188 | 0.33 | BA328 (IC) | 0.80 | BC328 | 0.10 | BD437 | 0.41 | BF391 | 0.36 | BRCS4 | 0.98 | BY476A | 0.76 |
| 2N3772 | 1.55 | ZSC2551 | 0.95 | AC188-01 | 0.40 | BA333 (IC) | 1.24 | BC337 | 0.08 | BD438 | 0.44 | BF393 | 0.90 | BRCS4 | 0.98 | BY476A | 0.76 |
| 2N3773 | 1.65 | ZSC2570 | 1.80 | AC188K | 0.39 | BA401 (IC) | 0.96 | BC338 | 0.10 | BD441 | 1.29 | BF417 | 1.20 | BRCS4 | 0.98 | BY476A | 0.76 |
| 2N3819 | 0.28 | ZSC2570A | 0.95 | AC193K | 0.59 | BA511 (IC) | 1.96 | BC360 | 0.30 | BD442 | 0.56 | BF418 | 1.70 | BRCS4 | 0.98 | BY476A | 0.76 |
| 2N3823 | 1.06 | ZSC2644 | 4.38 | AC194K | 0.59 | BA521 (IC) | 1.81 | BC368 | 0.23 | BD507 | 0.54 | BF422 | 0.26 | BRCS4 | 0.98 | BY476A | 0.76 |
| 2N3904 | 0.56 | ZSC2671 | 1.99 | AD140 | 0.56 | BA532 (IC) | 1.88 | BC440 | 0.99 | BD508 | 0.54 | BF423 | 0.26 | BRCS4 | 0.98 | BY476A | 0.76 |
| 2N3908 | 0.56 | ZSC2728 | 0.95 | AD142 | 0.56 | BA536 (IC) | 2.72 | BC441 | 0.40 | BD509 | 1.29 | BF435 | 0.49 | BRCS4 | 0.98 | BY476A | 0.76 |
| 2N4101 | 1.10 | ZSC372 | 1.27 | AD143 | 0.56 | BA6304A (IC) | 2.85 | BC454 | 0.32 | BD510 | 0.45 | BF450 | 0.30 | BRCS4 | 0.98 | BY476A | 0.76 |
| 2N4240 | 3.00 | ZSC373 | 1.05 | AD145 | 1.45 | BA843 (IC) | 3.60 | BC455 | 0.32 | BD518 | 1.36 | BF451 | 0.26 | BRCS4 | 0.98 | BY476A | 0.76 |
| 2N4443 | 1.35 | ZSC383 | 1.20 | AD149 | 0.81 | BAV10 | 0.10 | BC460 | 0.38 | BD519 | 1.36 | BF457 | 0.37 | BRCS4 | 0.98 | BY476A | 0.76 |
| 2N4444 | 1.12 | ZSC388 | 0.45 | AD161 | 0.30 | BAV18 | 0.10 | BC461 | 0.42 | BD529 | 0.60 | BF458 | 0.35 | BRCS4 | 0.98 | BY476A | 0.76 |
| 2N4914 | 0.65 | ZSC41 | 1.99 | AD162 | 0.30 | BAV19 | 0.10 | BC462 | 0.27 | BD530 | 0.60 | BF459 | 0.35 | BRCS4 | 0.98 | BY476A | 0.76 |
| 2N5064 | 0.64 | ZSC458 | 0.55 | AD262 | 0.95 | BAV20 | 0.10 | BC463 | 0.58 | BD533 | 0.60 | BF460 | 0.54 | BRCS4 | 0.98 | BY476A | 0.76 |
| 2N5293 | 0.45 | ZSC495 | 0.83 | AF114 | 2.24 | BAV21 | 0.17 | BC464 | 0.58 | BD534 | 0.36 | BF469 | 0.27 | BRCS4 | 0.98 | BY476A | 0.76 |
| 2N5294 | 0.45 | ZSC508 | 3.36 | AF115 | 0.79 | BAV12 | 0.10 | BC465 | 0.58 | BD535 | 0.44 | BF470 | 0.28 | BRCS4 | 0.98 | BY476A | 0.76 |
| 2N5296 | 0.40 | ZSC515A | 1.28 | AF116 | 0.79 | BAV13 | 0.10 | BC477 | 0.25 | BD536 | 0.55 | BF471 | 0.28 | BRCS4 | 0.98 | BY476A | 0.76 |
| 2N5297 | 0.45 | ZSC537 | 0.49</ | | | | | | | | | | | | | | |

ECONOMIC DEVICES, PO BOX 228, TELFORD TF2 8QP

| | | | | | | | | | | | | | | | |
|------------|-------|------------|-------|-----------|------|------------|-------|------------|------|------------|------|-----------|------|-----------|-------|
| ESM532C | 4.18 | LM1303P/N | 1.50 | MPSU05 | 0.78 | SN74190 | 1.81 | T6029V | 4.41 | TBA395 | 1.35 | TDA1230 | 2.93 | TDA9503 | 2.60 |
| ESM632C | 4.18 | LM1310P/N | 1.25 | MPSU10 | 0.78 | SN7420N | 6.50 | T6032V | 0.89 | TBA395Q | 1.00 | TDA1235 | 3.52 | TDAS913 | 2.40 |
| ESM732C | 4.18 | LM3065N | 0.77 | MPSU55 | 0.90 | SN7430 | 0.20 | T6033V | 0.73 | TBA396 | 1.80 | TDA1270 | 2.64 | TES27 | 1.25 |
| ETTR616 | 2.85 | LM3170CK | 1.30 | MPSU56 | 0.30 | SN7440N | 7.50 | T6035V | 0.24 | TBA400 | 1.17 | TDA1327A | 1.65 | TES38 | 0.36 |
| FT3065 | 2.16 | LM339N | 0.68 | MPSU60 | 1.20 | SN7450A | 14.75 | T6036V | 0.66 | TBA400P | 2.15 | TDA1327B | 1.65 | TES26 | 1.35 |
| FND500 | 5.25 | LM3407 | 1.29 | MR510 | 0.30 | SN7474N | 8.50 | T6037V | 1.91 | TBA480 | 1.42 | TDA1330 | 1.60 | TEA1002 | 3.15 |
| FT3065 | 1.05 | LM3407S | 0.75 | MR812 | 0.60 | SN7490AN | 1.80 | T6041V | 0.86 | TBA480Q | 1.67 | TDA1365 | 6.35 | TDA1009 | 0.96 |
| GF758 | 0.82 | LM3407T | 0.75 | MR914 | 0.46 | SN75110N | 3.00 | T6044V | 0.86 | TBA500PQ | 1.55 | TDA1412 | 0.95 | TEA1020SP | 5.34 |
| GF759 | 1.02 | LM3407S | 0.75 | MSSD7002 | 0.65 | SAB1009B | 4.53 | SN76001ANQ | 1.09 | TBA510 | 1.99 | TDA1420 | 1.48 | TIC1087 | 0.46 |
| GF761 | 0.78 | LM342N | 0.56 | MVS240 | 0.52 | SAB1046P | 3.66 | SN76003N | 2.61 | TBA510S | 1.10 | TDA1470 | 2.63 | TIC1086 | 0.55 |
| GH3F | 1.65 | LM384N01 | 1.84 | MVS480 | 0.30 | SAB3011 | 7.34 | SN76013N | 3.83 | TBA520 | 0.76 | TDA1512 | 2.20 | TIC1086 | 0.55 |
| HA11211 | 2.30 | LM567CN | 1.30 | MVS480-02 | 0.55 | SAB3012 | 5.34 | SN76013NDG | 2.25 | TBA520Q | 1.35 | TDA1670 | 3.05 | TIC1160 | 0.80 |
| HA11215 | 4.60 | LM748 | 1.65 | ME545B | 2.95 | SAB3013 | 3.28 | SN76023N | 8.07 | TBA530 | 0.86 | TDA1770 | 5.66 | TIC44 | 0.65 |
| HA11225 | 3.90 | LM8360 | 2.78 | ME545B | 3.80 | SAB3021 | 7.18 | SN76023N | 2.35 | TBA530Q | 1.09 | TDA1905 | 1.25 | TIC45 | 0.70 |
| HA11226 | 7.56 | LM8361 | 1.78 | ME5534N | 1.48 | SAB3022B | 12.34 | SN76023ND | 1.04 | TBA540 | 0.96 | TDA1908 | 2.95 | TIC47 | 0.70 |
| HA11229 | 2.51 | M1024 | 2.55 | ME555 | 0.34 | SAB3023B | 11.18 | SN76033N | 2.33 | TBA540Q | 2.16 | TDA1910 | 2.38 | TIP120 | 0.56 |
| HA11235 | 3.60 | M1025 | 4.70 | ME556 | 0.75 | SAB3024 | 4.77 | SN76105N | 2.26 | TBA550 | 1.95 | TDA1940 | 2.54 | TIP110 | 0.48 |
| HA1124 | 4.70 | M1124 | 2.54 | ME5560N | 3.16 | SAB3209 | 4.75 | SN76110N | 1.13 | TBA550Q | 2.25 | TDA1950 | 2.54 | TIP112 | 0.80 |
| HA11244 | 4.32 | M1130 | 4.86 | ME565N | 1.20 | SAB3210 | 2.93 | SN76115AN | 1.46 | TBA560C | 0.86 | TDA2002 | 1.20 | TIP117 | 0.86 |
| HA1125 | 3.90 | M1191 | 5.74 | ME645BN | 3.80 | SAB4209 | 12.75 | SN76131 | 1.74 | TBA560CQ | 1.15 | TDA2003 | 1.05 | TIP120 | 0.73 |
| HA11251 | 3.38 | M1193 | 18.55 | ME646N | 3.80 | SAF1031 | 2.30 | SN762260N | 1.20 | TBA570 | 1.55 | TDA2004 | 2.52 | TIP121 | 1.08 |
| HA1137W | 2.57 | M51102L | 4.02 | ME650N | 3.94 | SAF1032 | 5.60 | SN76227N | 0.68 | TBA570A | 1.35 | TDA2006 | 1.25 | TIP126 | 0.96 |
| HA1138 | 3.56 | M5115P | 4.34 | ME645BN | 3.80 | SAF1039 | 11.66 | SN76228N | 2.97 | TBA570Q | 1.25 | TDA2010 | 2.79 | TIP127 | 1.30 |
| HA11414 | 2.50 | M51231P | 2.79 | MP1106 | 4.80 | SAS5010 | 7.62 | SN76231 | 2.31 | TBA625A | 1.97 | TDA2020 | 2.75 | TIP2955 | 0.78 |
| HA1144 | 6.38 | M5124P | 4.38 | OA200 | 0.10 | SAS560 | 1.68 | SN76242 | 4.75 | TBA625B | 1.16 | TDA2030 | 1.65 | TIP299 | 0.41 |
| HA11560 | 1.23 | M5134-8341 | 3.75 | OA202 | 0.10 | SAS560S | 2.97 | SN76243 | 4.75 | TBA625C | 2.56 | TDA2140 | 1.44 | TIP298 | 0.57 |
| HA1160 | 7.80 | M5139AP | 6.25 | OA47 | 0.10 | SAS560T | 2.85 | SN76252 | 2.51 | TBA641A12 | 3.75 | TDA2150 | 5.63 | TIP29C | 0.40 |
| HA1166 | 3.08 | M5142P | 6.38 | OA90 | 0.07 | SAS570 | 1.61 | SN76360 | 1.97 | TBA641B1X1 | 2.07 | TDA2151 | 1.75 | TIP3055 | 0.65 |
| HA1167 | 5.13 | M5143P | 6.66 | OA91 | 0.08 | SAS570S | 0.00 | SN76390 | 2.80 | TBA651 | 1.60 | TDA2160 | 3.64 | TIP30A | 0.47 |
| HA11711 | 16.13 | M51513L | 2.06 | OC28 | 0.96 | SAS570T | 2.50 | SN76396 | 2.63 | TBA673 | 2.94 | TDA2161 | 1.68 | TIP30B | 0.63 |
| HA11713 | 6.70 | M51518L | 3.10 | OC29 | 1.95 | SAS580 | 4.41 | SN76510N | 0.95 | TBA7000 | 1.35 | TDA2190 | 3.11 | TIP31B | 0.35 |
| HA11714 | 7.05 | M51518L | 3.40 | OC35 | 0.96 | SAS590 | 2.62 | SN76530P | 1.90 | TBA720 | 4.36 | TDA2510 | 1.82 | TIP31C | 0.63 |
| HA11715 | 7.05 | M51517L | 2.90 | OC36 | 1.16 | SAS590Q | 2.32 | SN76532N | 1.80 | TBA730 | 4.36 | TDA2520 | 2.15 | TIP32B | 0.35 |
| HA11718 | 6.79 | M5152L | 1.00 | OC44 | 0.40 | SAS660 | 2.30 | SN76533N | 1.56 | TBA7500 | 1.58 | TDA2521 | 2.15 | TIP32C | 0.66 |
| HA11724 | 15.60 | M51522 | 4.90 | OC45 | 0.40 | SAS660 | 1.20 | SN76540N | 1.80 | TBA760 | 1.46 | TDA2522 | 2.81 | TIP33C | 1.25 |
| HA11725 | 16.60 | M5191P | 4.49 | OC75 | 0.40 | SAS660Q | 1.20 | SN76544 | 1.60 | TBA780 | 0.80 | TDA2523 | 2.75 | TIP34 | 1.37 |
| HA1180 | 4.68 | M5192 | 2.00 | ON188 | 1.70 | SAS660S | 1.20 | SN76545 | 4.55 | TBA780Q | 0.78 | TDA2524 | 4.50 | TIP41A | 0.09 |
| HA1203 | 1.56 | M53273P | 0.92 | ON236 | 2.90 | SAS670 | 1.20 | SN76546N | 3.15 | TBA810AS | 2.84 | TDA2525 | 2.96 | TIP41B | 0.28 |
| HA1306 | 1.74 | M53274P | 1.20 | OT112 | 0.58 | SAS670Q | 1.20 | SN76549N | 3.15 | TBA810S | 1.52 | TDA2526 | 2.19 | TIP41C | 0.44 |
| HA1322 | 1.74 | MA06 | 0.97 | OT121 | 0.70 | SAS670S | 0.70 | SN76549 | 2.35 | TBA810T | 1.46 | TDA2532 | 2.51 | TIP42A | 0.39 |
| HA1339 | 1.76 | MA8001 | 0.74 | PD144 | 2.03 | SAS6710S | 1.20 | SN76551 | 1.35 | TBA820 | 3.35 | TDA2533 | 2.09 | TIP42B | 0.71 |
| HA1342 | 1.80 | MB3705 | 1.62 | PT1017 | 2.43 | SAS6800 | 1.30 | SN76551 | 1.35 | TBA820M | 1.65 | TDA2540 | 1.95 | TIP42C | 0.64 |
| HA1350 | 2.97 | MB3712 | 2.65 | PT2014 | 2.76 | SAS6810 | 2.30 | SN76570 | 2.80 | TBA870 | 4.95 | TDA2541 | 1.95 | TIP47 | 0.45 |
| HA1365 | 3.65 | MB3713 | 1.30 | PT6042 | 1.82 | SBA550B | 1.95 | SN76611 | 1.10 | TBA900 | 2.25 | TDA2545 | 3.16 | TIP48 | 0.83 |
| HA1366WR | 1.62 | MB3730 | 2.94 | R1038 | 1.99 | SBA750 | 1.46 | SN76622 | 2.35 | TBA900Q | 1.41 | TDA2550 | 2.81 | TIP49 | 3.28 |
| HA1367 | 3.20 | MC13002 | 4.66 | R1039 | 1.99 | SC9488P | 1.90 | SN76622 | 1.50 | TBA920Q | 1.36 | TDA2571A | 2.81 | TIS43 | 1.21 |
| HA1368 | 1.69 | MC1303P | 1.96 | R2008B | 1.30 | SC9503 | 1.50 | SN76623 | 0.62 | TBA940 | 3.85 | TDA2571B | 2.95 | TIS90 | 0.22 |
| HA1368R | 1.66 | MC1307P | 1.90 | R2009 | 1.20 | SC9504P | 1.46 | SN76630 | 2.31 | TBA950 | 1.64 | TDA2576A | 2.58 | TIS91 | 0.26 |
| HA1370 | 2.97 | MC1310P | 1.25 | R2001B | 1.20 | SC9511P | 1.90 | SN76640 | 3.85 | TBA970Q | 1.40 | TDA2576B | 5.37 | TL071CP | 2.02 |
| HA1377 | 2.68 | MC1327P | 1.20 | RC209 | 1.20 | SCR957 | 1.20 | SN76650N | 1.24 | TBA970Q | 0.58 | TDA2581 | 2.80 | TMS1000NL | 10.76 |
| HA1389 | 1.62 | MC1330P | 1.23 | RC2030 | 1.20 | SG264A | 4.38 | SN76651 | 1.35 | TBA990 | 3.37 | TDA2582 | 1.98 | TMS3748NS | 11.68 |
| HA1389R | 1.74 | MC1349P | 1.20 | R2257 | 1.16 | SG613 | 7.28 | SN76660N | 2.25 | TBA990Q | 1.40 | TDA2590 | 2.80 | TMS4116 | 1.87 |
| HA1392 | 2.68 | MC1350P | 1.10 | R2265 | 2.95 | SG629 | 6.88 | SN76666N | 1.35 | TBA990Q | 0.58 | TDA2591 | 2.80 | TV106 | 1.20 |
| HA1397 | 2.97 | MC1351P | 0.75 | R2305 | 1.07 | SG6533 | 9.76 | SN76666N | 0.98 | TBA990Q | 1.15 | TDA2591Q | 2.80 | TV6010B | 2.70 |
| HA1398 | 2.68 | MC1352P | 1.01 | R2306 | 1.23 | SH-1020N | 4.37 | SN76666N | 3.38 | TCA1700 | 1.15 | TDA2593 | 2.24 | U06G | 1.03 |
| HA1406 | 1.80 | MC1357P | 1.95 | R2322 | 1.26 | SH-1125HD | 10.70 | SN76705N | 3.99 | TCA1700P | 0.85 | TDA2594 | 2.80 | U143M | 2.80 |
| HA17723 | 5.40 | MC1358P | 1.55 | R2323 | 1.23 | SH-130N | 6.30 | SN76707N | 3.99 | TCA1713P | 3.51 | TDA2600 | 5.00 | U3700 | 0.55 |
| HB44030AF | 2.25 | MC14001 | 7.15 | R2348 | 1.82 | SKE2F 1/04 | 1.26 | SN76709N | 4.65 | TCA1717P | 8.04 | TDA2610 | 2.53 | U3700C | 0.44 |
| HD4480 | 15.60 | MC14011 | 0.23 | R2354A | 1.82 | SKE2F 2/04 | 0.95 | SN76730 | 4.23 | TCA220A | 2.10 | TDA2611AQ | 4.25 | UA723CA | 5.02 |
| HD44801A05 | 15.90 | MC14013 | 0.37 | R2354B | 1.82 | SKE2G 3/04 | 0.95 | SN76730N | 4.23 | TCA2700 | 1.55 | TDA2612 | 2.55 | UA758P3C | 3.06 |
| HM6231 | 8.50 | MC14016CP | 0.37 | R2441 | 1.23 | SKE2G 3/04 | 0.95 | SN76810N | 0.62 | TCA2700P | 4.53 | TDA2612Q | 4.25 | UA763P3C | 1.07 |
| HM6232 | 7.71 | MC14025 | 0.54 | R2443 | 0.80 | SKE4F 1/02 | 1.26 | SN76920N | 2.63 | TCA440 | 1.95 | TDA2620 | 2.34 | UA8180 | 2.14 |
| HM9102 | 2.92 | MC14049UBC | 0.52 | R2461 | 2.10 | SKE4F 1/06 | 0.66 | SN94041 | 3.45 | TCA4500A | 1.65 | TDA2630 | 2.48 | UJN2165 | 1.35 |
| HM9104 | 2.94 | MC1438R | 0.95 | R2477 | 0.92 | SKE4F 2/06 | 2.10 | SN94042 | 3.95 | TCA530 | 1.80 | TDA2630 | 2.25 | ULN2204 | 7.00 |
| HT4207 | 15.60 | MC14433P | 2.56 | R2501 | 1.16 | SKE4F 2/08 | 0.60 | SP8385 | 0.50 | TCA640 | 2.63 | TDA2640 | 6.93 | ULN2216F | 1.95 |
| IS879 | 1.87 | MC14510BAL | 3.15 | R2540 | 1.80 | SKE4G 2/02 | 0.87 | STA4411 | 2.27 | TCA650 | 1.28 | TDA2651 | 2.95 | UPC1001H | 2.50 |
| IS751 | 1.67 | MC145566CP | 3.15 | R2540X | 3.00 | SKE5F 3/10 | 1.45 | STK0029 | 3.42 | TCA660B | 2.25 | TDA2652 | 7.05 | UPC1009C | 5.74 |
| ITT2003 | 0.20 | MC1712 | 3.52 | R2615 | 0.60 | SL1310 | 2.85 | STK0039 | 4.00 | TCA730 | 4.44 | TDA2653 | 2.95 | UPC1020H | 2.12 |
| K174YP | 2.95 | MC7724CP | 3.17 | RC4195NB | 1.96 | SL1327E | 1.20 | STK0050 | 4.96 | TCA740 | 3.25 | TDA2654 | 3.24 | UPC1025H | 2.49 |
| KA2101 | 2.65 | MC7818C | 1.98 | RC416029 | 1.82 | SL1430 | 1.26 | STK0059 | 6.48 | TCA750 | 2.24 | TDA2655B | 3.15 | UPC1026C | 1.24 |
| KC582C | 3.45 | MC7824CP | 4.25 | RC416083 | 4.81 | SL1430T | 2.10 | STK0080 | 8.32 | TCA760B | 2.79 | TDA2660 | 2.24 | UPC1028B | 0.90 |
| KC582C | 3.45 | MC7824M12 | 0.75 | RC416334 | 0.92 | SL1432 | 2.25 | STK011 | 3.86 | TCA800Q | 1.95 | TDA2661 | 2.24 | UPC1030H | 2.06 |
| KC583C | 4.80 | MC7824M24 | 0.85 | RC416335 | 1.23 | SL1414 | 3.35 | STK013 | 7.04 | TCA800Q | 1.25 | TDA2670 | 2.50 | UPC1031H2 | 8.05 |
| L129V | 1.78 | MCR101 | 0.60 | RC416600 | 1.25 | SL432A | 3.12 | STK014 | 7.14 | TCA830S | 1.95 | TDA2670A | 1.76 | UPC1031H | 6.00 |
| LA1111AP | 0.80 | MCR106/5 | 1.17 | RC416799 | 6.00 | SL437 | 6.00 | STK015 | 5.12 | TCA900 | 1.85 | TDA2670B | 2.30 | UPC1032H | 0.94 |
| LA1210 | 1.38 | MCR2207 | 1.34 | RC416801 | 0.86 | SL439 | 2.25 | STK016 | 4.82 | TCA910 | 1.50 | T | | | |

Tuning in the Philips TRD IV

Michael Pitt

In the good old days when all that was needed to tune in a colour set was a little patience and short finger nails life was nice and easy. Just twiddle until something appeared on the screen. Not so now! Philips have revolutionised the idea of tuning your shiny new one-eyed monster to give any amount of TV channels. The TRD IV remote control system is, as the Americans would say, a whole new ball game. It was first introduced with the K35 chassis and has since been used with various versions of the KT4 and K40 chassis. Tuning one of these sets in is probably more awesome than any field fault you care to mention. Quite apart from initial tuning, our firm has quite a few K35s out in the field and the customers will occasionally have a bash at tuning. The result is that one of our field engineers has to make a call. It's true to say that they'd rather spend the afternoon at the dentist.

The first thing that's necessary in the world of Philips is an understanding of inane symbols. Philips seem to need these in order to have a series of blips and squiggles that will fit into their neatly hidden control flaps. Fig. 1 provides a guide. There now follows a beginner's guide to tuning.

Method A

Let's start at the beginning. Switch the receiver on and, using what Philips call search method A, press the button marked c/p. The red LED display will show 01. Press the same button again and the display will change to 21, 69 or any number in between. Press the button marked with the symbol for open memory and the display will start to flash.

What have we achieved so far? We've chosen programme number one, we've switched over to the channel scale 21-69, we've opened the memory and we now want to lock the BBC-1 channel to the memory's programme one position.

Press the search tuning button and a vertical yellow bar should appear on the left-hand side of the screen and slowly edge its way across to the right-hand side. As it travels, so the tuning moves up the band, from channel 21 to channel 69. In our case the local channels are 40 BBC-2, 43 ITV, 46 BBC-1 and 50 Channel 4 (Sutton Coldfield). So the first local channel we come to is 40. At this point the set will lock to this channel as programme one, the yellow line will disappear and the sound will be heard for the first time (the sound is muted until an aerial-supplied signal is received).

But we wanted to lock BBC-1 as programme one. Instead we've got BBC-2 as this programme. No problem! Simply press search tuning again and the display will move up to the next local channel, 43 in our case. Press it a third time and it will move up to the next channel, our BBC-1 channel 46. When you get there, push the store button (the one with the diamond symbol) and the memory will close, with BBC-1 locked as programme number one. The display will cease to flash.

To check that this is so, press the c/p button once to see that the programme is number one, displayed as 01, and press again to see 46 displayed.

With method A the selected programme number appears first and the channel that's locked to it afterwards. Method B reverses this – the channel selected must appear first, then the programme number.

Method B


Method B, the "alternative method, direct channel selection", is no harder to follow. Let's assume this time that you're called to tune in the customer's VCR – we are assuming that the input to the set is at u.h.f.

Switch on the VCR's test signal, then turn your attention back to the TV set's control panel. Press the c/p button for a channel figure between 21 and 69 on the LED display. Now with most VCRs the u.h.f. output is at around channels 36-39. Press the search tuning button and watch as the yellow line moves across to the right-hand side of the screen and the figures in the display move up towards 36-39. When the VCR's signal is reached the test signal will appear on the screen, the yellow line will disappear and you can choose which programme number to use. Say 00 as recommended by Philips.

Press the c/p button once again and the display will change to a flashing number between 00 and 89 (49 on some models). Get the display to 00 by using the buttons marked c/p – and +. Then press the store button (diamond symbol). You've now locked the VCR's output as programme 00.

If the customer decides to connect his VCR via the SKART socket, simply select 00, set the changeover switch to AV and the VCR's video and audio signals will be taken via the SKART plug/socket. No tuning is required.

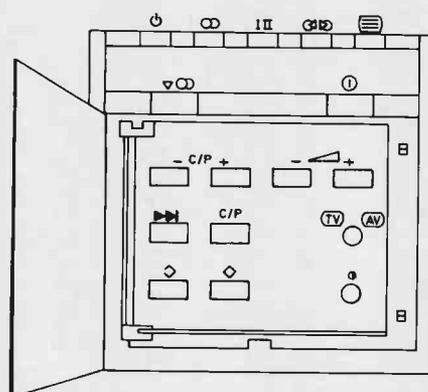Combining a Philips VCR and CTV has the advantage that you can control both via a single remote control unit.



| | | | |
|-----------|---------------------------|---------|---------------------------|
| C/P | Channel/programme | ⊖ ⊕ | Stereo reception |
| ▶▶ | Search tuning | I II | Second language reception |
| ◇ | Memory open | ⊗ ⊙ | Spatial sound |
| ◇ | Store | ≡ | Teletext |
| ▽ ⊖ | Stereo/mono | ● | Contrast |
| ⓪ | Mains on/off | - / + | Volume up/down |
| (TV) (AV) | Aerial/SKART signal input | - C/P + | Channel/programme up/down |
| ⓪ | Standby/message received | | |

Fig. 1: Philips' on-set controls with the TRD IV remote control system – and what the symbols mean.

Most of the later Philips slim-line handsets have the necessary buttons for play, record, fast wind in either direction and of course VCR channel change.

One of the sets we handle is the 22CS3850. This is not just your average 22in. CTV. Apart from the automatic tuning covered above it has teletext, a 48-button handset, a stereo sound decoder, four loudspeakers, spatial (extended) sound effect, second language reception, a jack socket for private listening with the main speakers on or off and a whole range of audio plugs/sockets at the rear. All in all quite a set – or more a way of life!

Harold Peters adds: One of the problems we've had with the TRD IV system is initial tuner drift – the tuning

system seems to need a bit of time to "burn in". The symptoms you get are confusing – "picking" all over the screen on certain channels only, i.e. it looks more as if there's a timebase fault present than tuning drift. To cure, open the memory, go from programme to channel then back to programme again and press store. What happens is that in the channel position the local oscillator is controlled by frequency synthesis, counting down from a crystal, while in the programme position the tuner is controlled by a voltage stored in the memory. As the tuning "burns in", the voltage required for a given channel varies slightly. Note that in the programme mode there's no full stop in the display: in the channel mode a full stop appears behind the channel number.

VCR Clinic

Hitachis

A couple of general points about Hitachi VCRs. First the wires to the plugs and sockets on all Japanese produced Hitachi machines. These use resistor colour coding, i.e. pin one is the brown wire, pin 2 the red wire, etc. The exception is the use of pink instead of green for pin 5. This system makes identification of the various plug pins much easier. Secondly the more recent service manuals. Dotted around the various circuits are power supply lines that end abruptly with a circle in which the voltage is shown: if the red circle is not coloured in the centre this indicates that the voltage is coming in at this point; if it's solid red it's a voltage source.

Front-loading Hitachi machines react to fault conditions in the following ways:

- (1) If front loading is not completed within ten seconds the cassette is ejected.
- (2) If front unloading or unthreading is not completed within ten seconds the machine switches off.
- (3) If threading is not completed within ten seconds the machine goes into the stop mode.

The current Hitachi range is as follows:

VT33: A front-loading machine that's similar to the VT11 but with only one microcomputer i.c. instead of two in the system control section and an extra i.c. in the servo section for visual search. It has instant record timing and a one-programme, 14-day timer. The VT11's handset will work with this machine.

VT35: A two-speed version of the VT33 with skew correction for picture search in the long-play mode. There's no indication at the front as to whether the machine is in the standard or long-play mode. On record there's a push button on the front for speed selection: on playback it's automatic. There's infra-red remote control, auto tuning for the TV channels and a five-programme, 14-day timer. The display dims automatically when the operate button is switched off.

VT57: A five-head version of the VT35. The extra head is used for super-fine still.

VT88: A hi-fi stereo machine which records stereo sound on both the hi-fi and conventional sound tracks with automatic or variable level controls affecting both systems. Dolby is fitted but operates on only the conventional sound track. The machine can be used as a sound only recorder, in which case it switches to a slower speed (equivalent to long play) to give up to eight hours of hi-fi

Reports from Derek Snelling, Paul Hardy, Philip Blundell, Eng. Tech., Mike Phelan and Steve Beeching, T. Eng.

sound. Unlike the Panasonic machine described in the January issue, it doesn't appear to have a hold circuit. Drop-outs of less than $\frac{1}{25}$ th of a second are ignored; with a drop out of $\frac{1}{25}$ -2 seconds the sound is muted; with a longer drop-out the machine switches to conventional sound. There's auto tuning.

VT7: This is a two-speed portable machine that slots into a tuner/mains unit to make a VCR with a conventional appearance. There's infra-red remote control, an instant record timer, reverse play at standard speed, and slow and still in the standard play mode only. No skew correction is incorporated, so long-play search is in monochrome with skew distortion. The auto tuning handles up to eighty channels and an LCD display continues for up to an hour after switch-off using the charge held in two $1\mu\text{F}$ capacitors. The r.f. converter is switchable for PAL G or I, a point to watch out for if the customer complains of no sound. As a battery saving feature, if the machine is left on battery in the stop mode the machine automatically switches off after five minutes. Finally the date in the form of three pairs of numbers can be recorded on the tape. **D.S.**

Mitsubishi HS306

One of the current range of models we handle is the Mitsubishi HS306, a mid-range front-loading machine with an acceptable though not outstanding picture. Two common faults have already put in an appearance, and we've had one or two other fault experiences.

The first common fault is squeaking/noise during play. Its cause is the head earthing spring: a spot of MS (conductive) grease on the end cures the fault. This simple job is made to last twenty minutes however by difficulty in gaining access to the head. The top must first be removed (four screws), next the front (one screw, eight clips), then the front control panel which is connected to the main panel by ribbon cable (three screws), after this the main panel (seven screws) and finally the head cover (four screws). This dismantling is also necessary when the head needs cleaning, though it's just possible to do a bit of cleaning from the side if the cleaning stick is long enough. Incidentally, two slots near the rear of the machine hold the main panel vertically for servicing.

The second common fault is that the cassette door sticks

open. Along the front edge of the main board there's a metal bar on which the capstan drive i.c. is mounted. Part of the mounting consists of a piece of adhesive cloth tape. This comes unstuck, hangs down and the cassette door then sticks to it. The cure is simply to cut away the surplus tape.

Two of these machines have had low-gain pictures, both on the TV channels and in the E-E mode, due to faulty aerial signal amplifiers.

One-off faults have included no fast forward or rewind due to the spring coming off the fast forward/rewind arm, and no channel changing due to a dry-jointed transistor on the control panel. Both these faults were on UK-assembled stock machines. The failure rate with our machines is already approaching twenty per cent: small, silly faults perhaps, but they require a service call and twenty minutes work. A recent example was a dead machine due to blown mains fuses. As with everything else on this machine the top, front, panel and main panel have to be removed, plus in the case of the fuses a small, clear plastic cover that seems to defy all attempts to take it off.

D.S.

VCR Fronts

A word on fronts. Most of them nowadays have buttons consisting of a square or oblong piece of plastic with one or two small plastic "hinges", i.e. thin pieces of plastic $1/16$ - $1/8$ in. wide, along one edge. These are not very strong and are easily damaged by heavy-handed customers. We've had five machines recently with a broken off button – two Mitsubishi HS700s, two Toshiba V31Bs and a Toshiba V33B. An indication perhaps that manufacturers have reduced the amount of plastic too much?

D.S.

Sanyo VTC9300

The customer complained of intermittent timed recordings: in fact the fault turned out to be the pinch roller solenoid dropping out. In the fault condition the voltage at the collector of Q810 (see Fig. 1) disappeared. It was also missing at the cathode of D814, though there was 12V at its anode. The cause of this trouble is usually either the regulator or Q810, also sometimes Q816/7/D817. On this occasion however it seemed that D814, which provides the holding current for the coil, was responsible. To prove the point the collector of Q810 was shorted to chassis with the machine working normally: the voltage at the anode of D814 dropped to about 9V, so a short was not respon-

sible. Replacing D814 cleared the fault – it was apparently going open-circuit intermittently.

P.H.

Sharp VC7300

Ever seen a ghosting picture that isn't due to an aerial fault? This machine had two test cards side-by-side recorded on the cassette though it recorded and played back normally when I first tried it. After a couple of hours on E-to-E the tuning drifted, and when it was retuned the ghosted picture appeared. A few minutes spent with the freezer proved that filter SF1501 on the tuner/i.f. panel was the cause of the problem.

These filters are used in many of the circuits in Sharp VCRs and can be responsible for such faults as poor a.f.c. and intermittent colour on playback.

P.B.

Sharp XC30 Camera

It's not very often you come across a camera fault that's not due to a broken cable. This was one of the few! It was producing sync and burst but no video at all. Following the flow-chart in the manual I first checked for video at TP3. Nothing doing. Then to the collector of Q102 where the vidicon's target voltage was low at 18V. The voltages at the base of the vidicon were normal, so I disconnected the wire from the target pin to the preamplifier. This restored the target voltage to normal. There was a short from the target connector to the screening shield – a quick bend soon put that right. Phew! – I thought I'd a faulty vidicon for a few minutes.

P.B.

Ferguson 3V23/JVC HR7700

The problem with this VCR was no tape transport, with the reel motor trying to run the whole machine on its own. In a case like this it's simplest to replace all ten motor drive and power supply switching transistors. The cost won't be much more than that of the parts and it'll save large-scale failure when you come to power up the machine.

S.B.

Grundig 2 × 4 Super

If the chopper circuit in the power supply fails, check C401 which couples the drive from the TDA4600 i.c. to the base of the BU208A chopper transistor – it may be open-circuit. In one of these machines the cause of failure to rewind and tape damage was the turntable having become unglued from the supply motor spindle.

S.B.

Amstrad 7000, Sanyo VTC9300

A couple of points arising from the December VCR clinic. First the Amstrad 7000 (Orion) shares the same reel subdeck as the Sharp VC381 and VC9300 – and the same idler pulley problem. Secondly, a further problem that's beginning to show up on the Sanyo VTC9300 is intermittent loss of the playback f.m. due to the set luminance record current preset having a noisy track.

M.P.

Panasonic WV3000 Camera

The power and low-light LEDs were on and the monitor screen was blank. The camera's 9V supply was present but the vidicon was without h.t. or e.h.t. The high-voltage section is driven by Q123 (see Fig. 2) whose collector

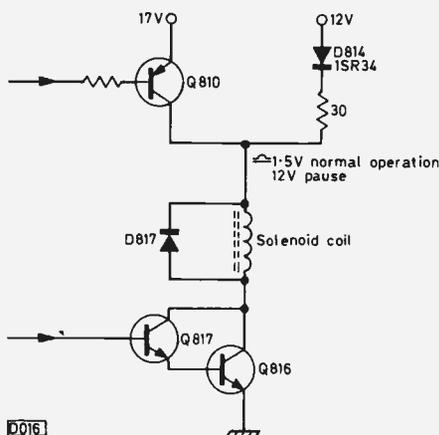


Fig. 1: Pinch roller solenoid circuit, Sanyo VTC9300.

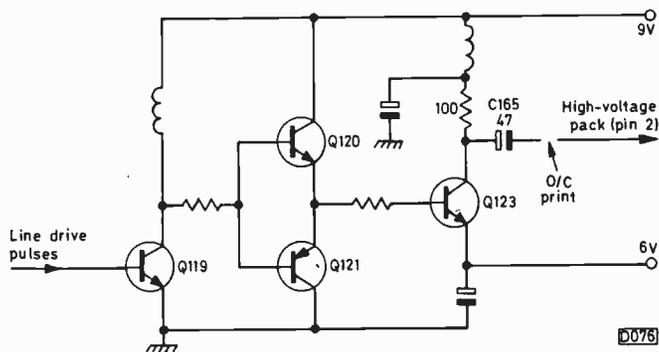


Fig. 2: High-voltage pack drive circuit, Panasonic video camera type WV3000.

waveform was o.k. There was no drive at pin 2 of the high-voltage pack however, due to open-circuit print between C165 and pin 2. **M.P.**

JVC HRD110

On all these machines and most of its forbears to date it's been possible to set the programmable timer once the machine has been powered. On this particular machine however we discovered – by accident – that the timer could be set only when a cassette had been inserted. There were no other problems and everything else worked fine. Andy has persuaded me to leave it alone. Odd. **S.B.**

Toshiba V9600

A tape got tangled in this machine, jamming the threading motor assembly which stalled and blew the motor drive transistors to Kingdom come. I didn't want to risk losing too many transistors so I replaced the motor assembly and

transistors, switched on – and promptly wiped out some more. After much searching I found that I'd got two plugs reversed. The motor drive connection was plugged into the syscon input and the plug that should have been there (cassette compartment down detector switch) was across the motor drive output. This shorted the output, to the dismay of the transistors. The cause of the original problem, the slack tape that jammed everything up, was a dead spot on the reel motor which occasionally refused to run. Only eight months old too! **S.B.**

Murphy MVR7007/Sanyo VTC5300

For intermittent stopping in record or play, check that the tape counter is free. Its drive spindle is attached to the rotation detector, and if it sticks the machine cuts out. **S.B.**

Panasonic NV850

This hint from a friend concerns the Panasonic NV850. The r.f. signal is muted during playback. If you want it, short the base of Q707 to chassis. **S.B.**

JVC HRD110

While a new machine was being tested we found that the station indicator lights remained on the selected channel when the VCR was at off. Transistor Q5 on the timer panel was leaky. **S.B.**

Ferguson 3V29/JVC HR7200

This machine came to us in Saba livery. It entered pause when record was selected. The cause was the main microcomputer i.c. It's not an unusual fault – something to watch out for. **S.B.**

Teletopics

CABLE UPDATE

The Information Technology Advisory Panel, whose 1982 report encouraged the government to back the idea of cabling the UK, has decided to carry out a further study with a view to finding out what went wrong. Work on the study started in January and its conclusions will be sent to the Home Office and the Department of Trade and Industry.

Robert Maxwell's plan to buy BET's Rediffusion cable interests became entangled in legal problems because his holding company Pergamon is registered in Liechtenstein rather than the UK. A way round the difficulty was found – and BET knocked £2m off the price. The networks are mainly up-graded four-channel ones and are expected to be pushed by Mr. Maxwell's publishing interests – the Mirror newspaper group.

Windsor Television, which was planning to install one of the more sophisticated cable systems, including specialised business and industrial communications services and a local telephone service in competition with British Telecom, has decided to postpone further capital investment for six months. The franchise area had been extended to include Staines, Ashford and Heathrow Airport and cabling costs would call for some £35 million. The company hopes that it will be clearer by the summer

whether such an investment would be justified. Its shareholders include GEC and Currys.

DBS LATEST

The report prepared for the participants – the BBC, the ITV companies and the five non-broadcasting companies – in the proposed UK DBS system, outlining a "business plan", has been approved and sent to the Satellite Broadcasting Board for forwarding to the Home Secretary. Its main concern is the cost of the satellite system which was to have been provided by Unisat, a consortium of British Aerospace, GEC-Marconi and British Telecom, under the earlier proposals for an initial BBC-only DBS service – the cost has virtually doubled since 1982. The report comes to the conclusion that a DBS service would not be economically viable at the satellite system cost suggested by Unisat – £80 million a year for three satellites. Alternative quotes from abroad have been about half that from Unisat and the report recommends putting the provision of the satellite system out to international tender. One quote was received from a UK firm, Britsat, for the supply of an RCA system providing five channels with a twelve year life.

The DBS project is at present based on an assumed ten year life, but the report feels that this would need to be extended to around fifteen years to take into account the high initial investment required and a slow audience build up – some three million subscribers are foreseen by the project's sixth year, with the cost of a receiving installation

falling to well below £300. At present the future of the project appears to depend on whether the cost of the transmitting hardware can be brought down: if it does go ahead the start of the service is likely to be put back a couple of years.

A further complication relates to the transmitting standard to be adopted. C-MAC had originally been suggested but it's now likely that a compromise between proposals put forward by France and the UK will be adopted in the interests of establishing a European standard. Until this has been sorted out the design of receiving i.c.s cannot be finalised and go forward for testing and evaluation.

The contract between the European Telecommunications Satellite Organisation (EUTELSAT) and the European Broadcasting Union came into effect on November 19th. Under the terms of the agreement, which will last for ten years, EUTELSAT will provide two transponders on its satellites on an exclusive, full-time basis for the transmission of Eurovision TV signals between the member countries of the EBU.

A range of SAW bandpass filters for use in DBS receivers has been introduced by Oakbury Components: the i.f.s are 70, 134 and 610MHz.

Several firms in the USA have withdrawn from or curtailed their plans for DBS services on the grounds of unacceptable business risk.

EUROPEAN VCR MARKET

Figures have been agreed between the EEC and the Japanese Ministry of International Trade and Industry for the export of Japanese VCRs to Europe during 1985. This will be the final year of a three-year agreement that started in 1983. For 1984 a total European market of 6.35 million machines was assumed. In the event, it turned out to be about 4.5 million. The agreement was that it would be shared on the following basis: 3.95 million complete machines from Japan; 1.1 million kits from Japan for European assembly; 1.3 million European produced machines (Philips, Grundig). For 1985 a market of 5 million machines has been assumed, shared on the basis: 2.25 million complete machines from Japan; 1.7 million kits from Japan for European assembly; 1.4 million European produced machines.

Japanese exports of complete machines to Europe in 1984 were some 3.15 million rather than the 3.95 million envisaged, and the planned 1985 figure of 2.25 million represents a considerable fall in expectations compared to a year ago. Even so Philips has protested – on the basis that the European market in 1985 is likely to take around 4.5 million rather than 5 million machines, and that of these 1.5 million should be allocated to European production.

Despite the reduced European market, ITT has announced plans to produce VCRs in Europe in conjunction with the Italian state owned consumer electronics holding company REL. The plant will be in Rome and is expected to be complete by the end of this year. Initial capacity will be 100,000 machines a year.

Grundig report a loss of 286m DM in the year to March 31st 1984, on turnover down 9 per cent. This compares with a profit of 65m DM in 1982-3. The report for 1983-4 was delayed following disagreement between Grundig and Philips, who took control of Grundig on April 1st 1984, over the valuation of large stocks of unsold VCRs and TV sets. Grundig's V2000 machines were excellent but don't seem to have done it much good. It's ironical that the

Japanese/EEC VCR agreement was originally designed to protect the V2000 system: in its final year it's being used to enable Philips and Grundig to get going with VHS production.

NEW VIDEO EQUIPMENT

A new version of the Sony Betamovie camcorder, Model BMC200PK, includes auto-focusing. The suggested price is around £1,000. The new Sony mid-range VCR, Model SLF30, replaces the C20 and C30. It's just 3.25in. high and has a recommended price of around £400. Panasonic's latest VCR, Model NV430B, is a mid-range machine with IR remote control and a suggested price of £544.50. Sharp have introduced a new "user-friendly" VCR, Model VC488HD, with hi-fi sound to sell at around £750. A time-lapse VCR of RCA manufacture, Model TC3700, has been announced by Norbain Imaging Ltd. It has ten different speeds and can record up to twenty days of time-lapse recordings on a single tape. It's intended for industrial/CCTV use.

VIEWDATA

Richard Hooper of Prestel had some forthright comments to make at the recent Videotex International Conference in Amsterdam. He argued that to start a viewdata system off as a service for the general public was misguided, defining it instead as a "low-cost, easy-to-use way of editing, storing and displaying information". He went on to comment that other countries around the world appear to be making exactly the same mistakes that Prestel made in the UK. Take the W. German Bildschirmtext system for example – and aren't the Germans always supposed to be interested in technology for technology's sake? The Bundespost initially expected to have a million subscribers by the end of 1986 and regarded the service as a communications system for public use. So far there are only some 20,000 subscribers, mainly business users. The parallel with Prestel is uncanny. It will be interesting to see how the Japanese system, called Captain, takes off: the service started recently with an initial 5,000 installations, after a lengthy trial period.

NEW TV SETS/MONITORS

Panasonic have introduced a 20in. set, Model TXC21, fitted with a high-resolution FS type tube. Of particular interest is the higher than normal resolution and wideband RGB circuits to give clear characters and graphics. The full specification includes stereo sound and teletext. Suggested price is £611.

Two new Mitsubishi monitors, Models C6920 and C9918, offer delta-gun tubes and line scan rates of up to 1,000 and 2,000 lines respectively, with stable convergence and low raster distortion. Tubes with different phosphors can be fitted to order, including one with a red, green and white phosphor combination for character display use. The line rates extend to 28-35kHz with field rates of 40-70Hz. Details can be obtained from Mitsubishi Electric (UK) Ltd., Industrial Sales Division, Hertford Place, Maple Cross, Rickmansworth, Herts.

A 14in. colour set, Model C1-338F, has been added to the Samsung range. The first set to be released in the new Italian manufactured Philco range is a 22in. model with remote control, frequency-synthesis tuning, a wood cabinet, SKART socket and optional teletext. A 16in. colour

set with stereo sound, remote control, a telescopic aerial, multiple input/output sockets and optional teletext has been added to the Saba range.

SERT's TWENTY YEARS

The Society of Electronic and Radio Technicians (SERT), which was established in 1965, is to hold its twentieth anniversary banquet at The Worshipful Companies of Glaziers and Scientific Instrument Makers Hall in London on February 12th, with His Royal Highness the Duke of Kent as Guest of Honour. Present membership of the Society is over 8,500, in the UK and many overseas countries. Radio and TV servicing engineers account for about 11.5 per cent of the membership.

MULLARD CRT CONTROL UNIT

Mullard have introduced a combined focus/first anode control unit for use with colour TV sets and monitors. Optimum accuracy is ensured by integrating the resistors on a shared cermet substrate. The easy to mount plastic case saves assembly time and cuts costs: mounting is quick and efficient – the unit is simply pressed on to a PCB designed to mate with it. Four snap-locks secure the assembly while pins mounted on the board penetrate pads of conductive rubber for electrical connection. The h.t. input and focus output are connected by pressing the cable into another conductive rubber pad. There's an option for connecting the A1 potentiometer via board-mounted pins or the same method as used for the h.t. input and focus output. Three versions are available for use with lo-bri, high-bri and super hi-bri tubes.

VCR RELIABILITY

Last month we mentioned a *Which?* report on VCR reliability based on European experience. The November issue of the US magazine *Radio-Electronics* reports on some reliability checks carried out in the USA. According to its report, the overall defect rate for one major manufacturer's machines sold over an eighteen month period was 4.7 per cent: there were service calls to 6.3 per cent of the machines but 25 per cent of these were due to user misuse. This seems rather better than European experience, but then rental plays a much larger part in Europe, especially the UK, and it's been proved in the past that rented equipment is more likely to produce service calls. The same company reported that service calls to its cameras were lower at 2.9 per cent over eighteen months: a camera has far fewer mechanical parts of course – it seems that belts were a major problem with VCRs.

Head life is quoted as 1,000-3,000 hours depending on tape quality and cleaning practices. It seems that audio enthusiasts, used to frequent audio head cleaning, are a bit of a problem since they regularly have a go at their VCR heads as well.

COMBINED VCR/MONITORS

Markplan (Old Colony House, South King Street, Manchester M2 6DQ) have introduced a self-contained VHS-format VCR/12in. colour monitor, called the Videoport, which is primarily intended for sales presentations. Price is £1,495. A version with tuner, camera and microphone inputs sells for £1,695. A 20in. version with lockable



The 20in. Markplan Videoport combined VCR/monitor – it's intended primarily for public demonstrations.

security flap is intended for demonstrations in hotels, shopping malls and exhibitions. Automatic tape repetition is a feature of this version – it's available as an optional extra with the small-screen models. Brabury have introduced a similar unit, the Compact Model MCM37A, which combines a 14in. colour monitor and Panasonic NV180 VCR. An alternative version, the Compact Executive, offers additional features such as video/audio recording, switch-selected underscan (reduced picture size) and use as a monitor for RGB or composite PAL inputs.

TV CONTROL CENTRE

Ross Electronics (49-53 Pancras Road, London NW1) have introduced a device called a TV control centre, with five coaxial sockets and one phono socket that can be interconnected by means of six slider switches, enabling a TV set to be connected to VCRs, TV games and home computers (at r.f.). The aim is to avoid plugging and unplugging multiple leads. A chart is supplied to show the positions of the six slide switches for various purposes. The price quoted is £32.

IN BRIEF

Dixons take-over bid for Currys has succeeded, after a two-month battle and last minute court action . . . Rationalisation at ITT has led to the close down of the last vestiges of set assembly at Basildon. Production is now concentrated at the W. German Bochum plant. Mike Foster and David Cavey, managing and commercial director respectively, have left . . . Toshiba and Westinghouse Electric are to set up a c.r.t. plant with an annual production capacity of 1.6 million units in the USA. Production will start next year to meet the expected growing demand for terminals in the US . . . Production of the Sinclair pocket TV set at Timex's Dundee plant is now running at 300-500 a day. Large-scale production started late last year (the set was announced towards the end of 1983) after problems with the tube and main i.c.

Service Briefs

The following notes are based on servicing information issued by ITT, Philips and Thorn EMI Ferguson during the past year.

ITT

CVC30 chassis: The use of a non-approved replacement line output transformer can result in higher than specified l.t. voltages. This can cause field foldover at the bottom of the raster. ITT point out that the transformer is a safety component which must be replaced with an approved type to comply with the electrical equipment safety regulations.

CVC40 chassis: Failure of the BU126/TE1233 chopper transistor T807 is usually due to failure of one or other of the following resistors on power supply control panel CMP40: R808 and R809, both 220k Ω , R829 30k Ω and R833 1.5M Ω . These items may go high-resistance only when warm. Their replacement is recommended whenever the chopper transistor has failed. R818 (62k Ω) should be replaced whenever T807 has gone short-circuit.

R808 and R809 can be responsible for tripping, sometimes intermittent, when high in value. Tripping can also be caused by the 1N4148 diodes D8 and D10 associated with the chopper driver transformer being leaky.

Philips

VCR VR2220: The third harmonic of the erase oscillator can interfere with the DTF signals, causing tracking difficulties, when the machine is used in the sound dubbing mode. To overcome the effect retune the oscillator coil L5004 from 60kHz to 62.5kHz following the procedure laid down in the manual.

VCRs VR2220/VR2324/VR2334: The cause of strong patterning during playback on a few of these machines has been traced to contact between the deck screening cover and the side of head amplifier can A420. Ensure that contact between the can and/or the earth tag at the top of the can does not occur when refitting the screen – if necessary fit a strip of tape to the side of the can.

VCR VR2324: Tracking difficulties/picture interference have in a few cases been traced to poor actuator slipping contact. If this fault arises, remove the bridge assembly and clean the slip-ring with a lint-free cloth and a fluid such as Fomblin Freon. If this fails to cure the problem check and if necessary adjust the head height (see manual for details).

VCR VR2334: The original DTF control i.c., type P8049H, is no longer available. The later replacement version incorporates a programme with continuous DTF control during changes between different playback modes. When fitting the later type, R3142 and R3144 in the actuator feedback loops must be changed from 1.2M Ω to 820k Ω : potentiometers R3141 and R3143 will require adjustment (see manual).

G11 chassis: The following summary lists faults that are encountered from time to time in the field timebase.

Intermittent bottom cramping: Check C2083 (15 μ F) in the feedback circuit for loss of capacitance or open-circuit.

Random line pairing in the top half of the raster: Check coupling capacitor C2072 (4.7 μ F) between pins 2 and 3 of the TDA2600 i.c. for being open-circuit.

A black triangle at the top left of the scan: This is caused by a high-resistance joint at the earthy end of resistors R2104/5 which are in series with the scan coils.

Random interference on the field scan: This is caused by dirty/tarnished TDA2600 holder contacts. Don't try to clean the contacts – replace the holder.

Failure of the TDA2600 i.c.: The field timebase i.c. may fail due to an h.t. surge or e.h.t. flashover. In addition, poor holder contacts can cause actual or apparent failure of the i.c. The holder should be replaced if there's any doubt about its condition. If an e.h.t. flashover is suspected, clean around the e.h.t. cap. H.T. surges are usually caused by the type of h.t. reservoir capacitor (C4029, 470 μ F) used in some sets and can also kill the BU208A line output transistor. If C4029 is a Pye CCL or ITT KV3253T, fit an STC type CT347 250 L07 BUS. Loose mains supply connections can also be responsible for h.t. surges. Check for a defective on/off switch, an intermittent fuse holder or poor mains plug/socket connections.

Violent picture pulsating on high contrast scenes, sometimes intermittent, has been traced to the h.t. decoupling capacitor C3129 in the line output stage.

K30/K35 chassis: Loss of EW correction is normally due to dry-joints on the EW amplifier output transistor T1490 (BD234). Alternatively the preceding transistor T1485 (BC548) may be leaky.

If the fault on a set fitted with the TRDIV remote control system is intermittent loss of sound and vision with the channel display showing E1, check for dry-joints on the line output transformer before tackling (if necessary) the remote control panel.

CTX-E chassis: Earlier versions used a mains bridge rectifier. For improved reliability a half-wave rectifier, type BY527, is used in later production.

A problem with sets using the VST remote control system is intermittent switching to standby. Check zener diode D6770 (BZX79-B5V1) on the VST panel for leakage – it must be a Philips/Mullard type. Change C2335 on the main panel from 0.01 μ F to 0.1 μ F.

KT4 chassis: An 0.0018 μ F ceramic capacitor has been added between the base and emitter of transistor T7129 (BC558) in the protection circuit to prevent h.t. hiccups when transient spikes are present on the mains supply.

A BZX79/C27 zener diode (D6106) and 2.7k Ω resistor (R3106) have been added in series between pin 4 of the TDA3650 field timebase i.c. (IC7110) and the junction of R3109 and pin 5 of socket L53 to suppress flyback lines when the set is used for VCR playback. The cathode of the zener diode goes to pin 4 of the i.c. The lines may be more noticeable in the still picture mode. If necessary add the components on the print side of the timebase panel, adjacent to IC7110.

KT4/K40 chassis: The following modifications are suggested for problems that may arise when sets fitted with

these chassis are used with a VCR. For ragged verticals, increase the value of R3193 to 10k Ω . For picture jumping/unsteady field, add a 100k Ω resistor in parallel with C2206 (10 μ F). For loss of colour in the slow/still modes (VHS machines), change C2193 from 1 μ F to 4.7 μ F.

K12 and K12Z chassis: Intercarrier sound/audio preamplifier/tone control i.c. type TDA2790 used in these chassis is no longer available. Various component changes must be made in the peripheral circuitry when a TDA2791, which has superseded the TDA2790, is used for replacement purposes.

Thorn

TX9 chassis: Increase in the value of R165 (300k Ω) or R166 (0.68 Ω) can be the cause of chopper transistor failure (PC1044 panel). It's important to use replacements from Thorn as both resistors have special characteristics.

Interference on sound due to 27MHz CB transmissions, amateur SSB operation in the 144MHz band or possibly PMR can be cured by adding a capacitor with very short leads from pin 8 of the TDA1035 sound i.c. to chassis. The value depends on the source of the interference: 0.001 μ F at 27MHz, 470pF at 144MHz and something between these values for PMR.

The value of the 12V rail decoupler C915 on the U725 remote control receiver panel (PC1548) has been increased from 0.1 μ F to 10 μ F to eliminate a striation effect due to line pulse ripple.

TX10 chassis: The following points all relate to sets fitted with the PC1560 main panel (plastic surround, TDA2578A sync i.c.). Line whistle can be caused by vibration of the ferrite beads on the leadouts of diode D743 in the BU508A line output transistor's base circuit. Secure the beads with a blob of adhesive. To avoid bent verticals at high contrast levels, an underboard link has been added between the earthy ends of C742 and C745. R756 has been changed from 4.7k Ω to 6.8k Ω to overcome severe line ragging/sync pulling when a set is used for VCR playback. The new resistor value alters the sync slicing characteristic. To prevent interference to 27MHz CB transmissions, C779 (0.1 μ F, 400V metal polyester) has been added between pins 9 and 4 of IC772 (field output). If it's necessary to add this capacitor, keep the leads as short as possible.

TX90 chassis: Failure of the line output transistor TR112 can be caused by high-voltage spikes. To eliminate the problem the efficiency diode D113 has been changed to an avalanche type. It's a specially selected version of the BYV95 coded OGF721, part no. 00V4-631.

Here's one for fault connoisseurs. What happens (except at low beam current) when the ferrite core falls out of the line driver transformer (T103)? Answer, loss of field lock and sound! The reason for this is that the loss of inductance in T103 shifts the line drive phase to the extent that the coincidence detector in the TDA4500 i.c. (IC102) drops out, muting the sound and disabling the field sync separator.

Since the posistor in the degaussing circuit takes some time to cool down, degaussing at switch on may not occur when a set that's warm is moved to a new position, leading to purity problems. This has led to

some complaints. It should be pointed out that the impurity will be corrected whenever the set is switched on from cold.

The following items relate to the remote control version of the chassis (Model 37141, main panel PC1140, remote control receiver panel PC1139). To deal with tuner drift at the high end of the u.h.f. band, R102 and C101 on panel PC1140 have been changed to 2.7M Ω and 0.1 μ F respectively; on panel PC1139 C921 is deleted, C919 becomes 1 μ F, R930 is replaced with a wire link, R975-7 become 2.4k Ω , R910 15k Ω and R950 10k Ω . Under high ambient temperature conditions continuous channel stepping may occur when a TA127 battery converter is in use. To overcome this problem a diode, type PH425, circuit reference D913, has been added in place of link 925 on panel PC1139 between the junction of C906/R919 (anode) and the junction of R993/D904.

To overcome a few isolated cases where a set fitted with the TA127 converter but being operated from the mains has failed to switch to standby on command from the remote control transmitter a 1N4001 diode has been added in series with R6 on the converter, cathode to the junction of R7/R21 etc. When the board layout is revised the diode type will be PH425.

Cases where a set has switched on from standby without a command from the remote control transmitter have occurred. The production modification to avoid this is the addition of a 4.7 μ F non-polarised electrolytic across D124 on main panel PC1140. When the PC1139 remote control receiver panel is revised the capacitor will be mounted here as C929 with a value of 10 μ F (non-polarised).

Model MC01: A random dot pattern may be experienced when this set is used for off-air reception in conjunction with a TA127 battery converter. This can be eliminated by adding an 0.01 μ F capacitor to the underside of converter panel PC1129 between the 85V output and the earth print.

TX100 chassis: Under certain field fault conditions a black raster may be obtained due to the action of the sandcastle pulse circuit. As a check switch off, turn the brightness/contrast/colour controls to minimum, disconnect PL14 (field scan coils), switch on, allow to warm up, then slowly increase the brightness. If a white line appears, check the field timebase.

1790 chassis: An 8.2pF capacitor (C59) has been added between the emitter of the i.f. preamplifier transistor TR1 and the adjacent earth print to eliminate instability.

VCRs 3V35/36: Two different non-interchangeable types of reel idler assembly have been used. They can be identified by inspecting the idler pulley whose centre boss is white (early type) or black (later type). The correct part number must be specified when ordering replacements.

To prevent colour shift in the search mode, R488 has been replaced by a 1SS133 diode (cathode to IC405, pin 12).

3V24: Vision buzz on sound can usually be cured by readjusting the 6MHz sound offset coil in the u.h.f. modulator. To gain access to make the adjustment, extension lead set A (part no. 01X0-034-152) is required. Tune for minimum buzz/maximum sound.

High-power UHF Transmitters

Nigel Cawthorne, M.I.E.E., C.Eng.

High-power u.h.f. transmitters are a world of their own! Powers range from about 1kW up to 55kW peak sync, at 470-860MHz. Special techniques are required to generate such high powers at these frequencies, and because of the distortion introduced by the output amplifying device a great deal of "precorrection" is required, i.e. the input to the final amplifier is deliberately distorted to compensate for the output device's nonlinearity so that the correct output waveform is obtained. A block diagram for a typical u.h.f. TV transmitter is shown in Fig. 1. Note that power in broadcast and professional communications transmitters means power at the transmitter's output, not d.c. input power as often quoted for amateur transmitters.

Klystron Operation

In the UK, the output stages of most high-power u.h.f. TV transmitters employ either a four- or a five-cavity klystron. This type of tube employs the velocity-modulation principle and is tuned by adjusting the resonant cavities. The operating voltage required for a klystron is high – about 22kV for a 25kW klystron. In addition to the high levels of r.f. power, klystrons generate a lot of heat. Thus cooling is required – this can be achieved by a combination of steam vapour cooling (where water is brought to boiling point by the heat dissipated at the klystron's collector) plus air cooling for the cavities.

With some types of r.f. amplifier the efficiency is defined as the amount of r.f. output power in watts as a percentage of the d.c. input power. Because of the nature of the video waveform, this is not a practical measure for a TV transmitting amplifier. As the mean level of the TV waveform varies with picture content, a TV transmitter's power is quoted as peak-sync power (with negative-going modulation, the sync pulse tip corresponds to maximum output power).

The efficiency of a klystron amplifier is quoted as its

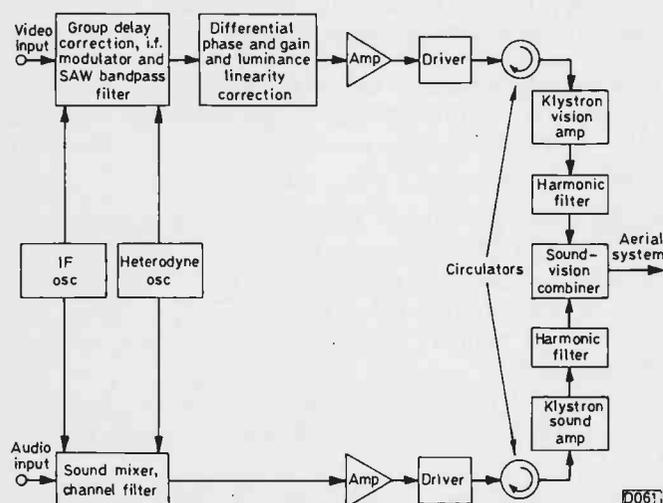


Fig. 1: Block diagram of a high-power u.h.f. TV transmitter using i.f. modulation and klystron output stages. The sound and vision channels are both shown: the outputs from the two klystrons are combined.

"beam conversion efficiency", which is a measure of the peak-sync power as a percentage of the amplifier's d.c. input. When klystron u.h.f. TV transmitters were first being installed in the UK in the early 1960s the efficiencies were often well below thirty per cent. In those days over 130kW was taken from the mains supply to generate a 40kW peak-sync signal. Increasing energy costs have encouraged klystron designers to strive for increased beam conversion efficiency in order to reduce the electricity bills.

Two klystron characteristic curves are shown in Fig. 2. In both the nonlinearity increases as the maximum output level (saturation) is approached. Early klystrons were operated with the sync tip near saturation level, where nonlinearity becomes severe, and the video part of the waveform on the linear part of the characteristic.

One method of increasing the klystron's efficiency is to alter the characteristic used for different parts of the signal waveform. This is known as pulsing the klystron. In this mode curve A (Fig. 2) applies during the sync period and curve B during the video part of the waveform. This alteration to the klystron's operation is achieved by applying a control voltage to one of its electrodes. Which electrode is used depends on the klystron's design – it can be the modulation anode, a grid or an annular control electrode. Since the video part of the waveform gets much closer to the klystron's saturation region in curve B the overall efficiency is increased but a greater degree of input waveform predistortion is required to achieve a linear output.

As a further improvement on this technique, the suggestion has been put forward to vary the characteristic continuously throughout the entire range of the input signal. This approach would require dynamic correction, i.e. the amount of predistortion applied would be different for each input level. The idea has not been tried in practice and the marginal improvement in overall efficiency might not compensate for the added complexity of the system.

Transmitter Systems

With ever increasing energy costs the transmitter operator becomes more and more concerned with klystron efficiency. When considering the type of transmitter to install, the operator has to take into account not only the capital cost but also the "cost of ownership". This includes the cost of replacement output devices, maintenance staff and energy. In the long term, remembering that a broadcast transmitter will normally be in service for at least twenty years, the cost of ownership is likely to be the most significant factor in choosing between one type of transmitter and another.

Some u.h.f. TV transmitters with output powers of up to 20kW employ rugged water-cooled tetrodes instead of klystrons. They are cheaper and don't require the complex cavity arrangements, but the operating life and gain are much less. With the present programme transmission times in the UK, a year's service is equivalent to about 7,000 operating hours. This is the typical life of a tetrode,

which would thus require annual replacement. The IBA report that their klystrons have life times of up to 70,000 hours.

The drive required depends on the type of output device used. Klystrons have gains in excess of 40dB, which means that a 25kW amplifier requires a drive of only about 22W. This is relatively easy to obtain from a solid-state amplifier with today's technology, even at 860MHz. For a tetrode to provide an output of 20kW an input of about 700W is required. Even with current technology this sort of drive is still obtainable only from another valve. So a tetrode transmitter usually employs two tetrodes, one as the driver and the other as the output device.

Most of what has been said above applies to the vision signal only. The relationship between sound output power and vision peak sync output power varies from country to country. The vision-to-sound power ratio in the UK is 5:1, so that with a 25kW peak sync vision output the sound level will be 5kW.

The sound and vision signals in a high-power u.h.f. transmitter are usually amplified separately and then fed to a sound-vision combiner. If the sound and vision signals are handled by a common amplifier it has to operate in a very linear mode to avoid intermodulation products. As indicated above, this is inefficient in terms of energy conversion.

Co-siting the BBC and IBA transmitters usually means that the programmes for all four channels go from separate transmitters to a common aerial system. For this purpose the outputs from the sound-vision combiners are

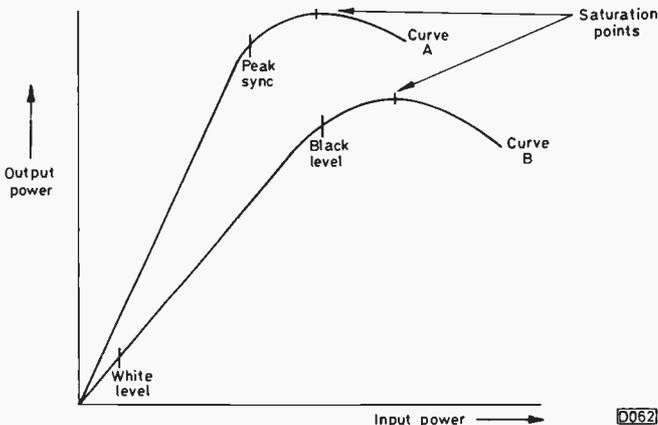


Fig. 2: Klystron power characteristic curves. Efficiency can be increased by pulsing the klystron so that its characteristic is altered for different parts of the input signal waveform.


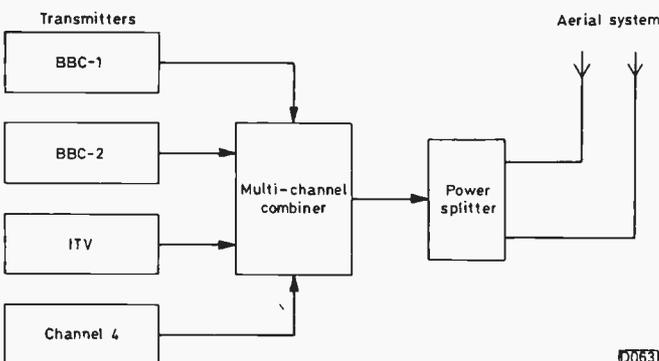


Fig. 3: Combining the outputs from four transmitters to drive the aerial system.

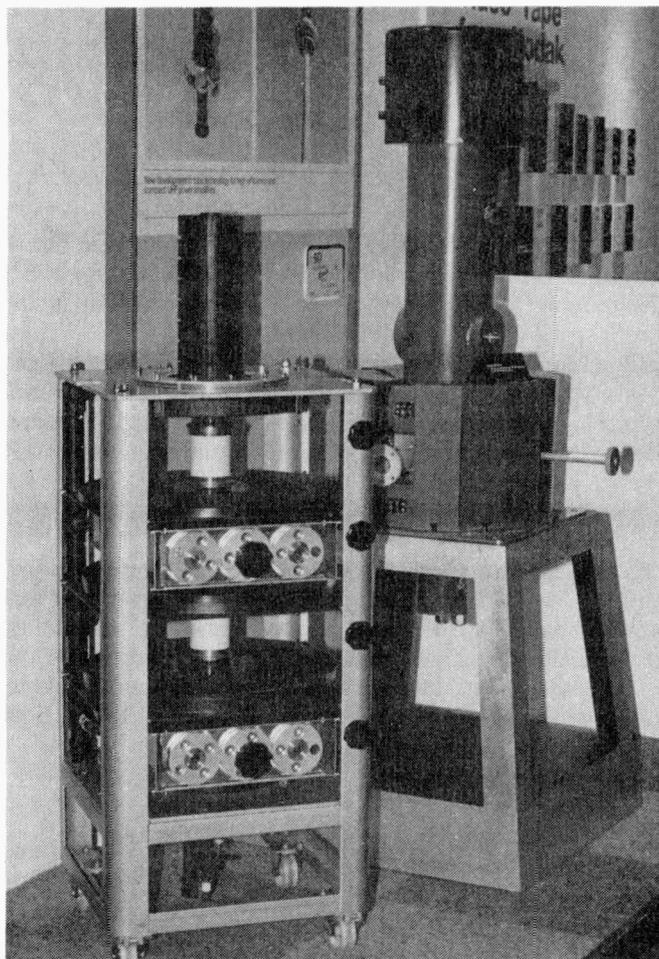

High-power devices for u.h.f. TV transmitters: a four-cavity klystron on the left and a klystrode on the right. Klystrons are tuned by adjusting the cavities: two of the four cavities of the device on the left are shown in position. The klystrode is a new, experimental type of amplifying device that combines some of the features of a tetrode and a klystron output amplifier.

fed to a channel combiner (see Fig. 3). It's common practice to follow the combiner with a power splitter so that two separate coaxial cable runs feed the two halves of the aerial system.

The use of an aerial system that's split into two halves increases the station's inherent reliability – should failure of one of the feeders or one part of the aerial occur, the station will still remain in operation at reduced power.

The aerial's radiation pattern is set for optimum coverage. In the vertical plane the main lobe is usually declined by a degree or so to the horizon. Where there are viewers close to the mast a technique called null-fill is used – the signal might otherwise pass right over their heads.

The coverage of the UK's u.h.f. service is now well in excess of 99 per cent of the population. Nevertheless the designers of klystrons, tetrodes and transmitters continue to try to improve the efficiency of their products. Orders continue to come from overseas countries where u.h.f. networks are being extended, and also for replacement purposes in the UK where the original high-power u.h.f. transmitters are now nearing twenty years' service.

Future developments will probably include more efficient klystrons, higher power tetrodes and more advanced computer-controlled dynamic correction systems in which the output device's inherent nonlinearities are continuously corrected via computer-controlled feedback.

TV Fault Finding

Reports from Steve Beeching, T. Eng., Philip Blundell, Eng. Tech., Chris Avis, John Coombes, Paul Hardy and Mick Dutton

Grundig Gremlins

I don't usually write about TV sets in the magazine but as a result of modifying a lot of Grundig receivers for RGB TV/monitor use I've come across a few recurrent faults. First, small colour portables fitted with the CUC95 chassis: in the event of no power and the BU208A chopper transistor being short-circuit, check R646 (270k Ω) after replacing the BU208A – it's probably gone high in value. Secondly, for intermittent standby and generally silly things at switch on with the CUC120/CUC220 chassis, change the h.t. preset R647 in the power supply to a ceramic type. Some sets may produce a funny runway effect – a vertical path with black and white "things" rushing down the screen on each side. In this event change the TDA2595 sync/line oscillator i.c. (deflection panel 29504-007.25) which can lock the line oscillator out of phase when interrupted by spikes and channel changing. S.B.

Mitsubishi CT2627

The current range of sets seem to be prone to a sound fault – the sound goes louder or begins to oscillate intermittently. This is due to a poor screen connection on audio plug FF. P.B.

ITT CVC800 Chassis

If you come across a CMD800 decoder that produces *very* bad Hanover blinds, remember what Uncle Les once said – beware the blue tant! In this case C307 (10 μ F), the only tantalum capacitor on the panel. Don't think (as I did) that as it decouples the 12V supply to the TDA3560 it can't possibly cause the fault – it can. Check it by substitution: it will read o.k. on the meter. P.B.

Thorn 1500 Chassis

In my opinion the 1500 chassis was undoubtedly the best hybrid monochrome chassis ever produced. It still springs the occasional surprise, however, like these two cases recently encountered.

The first was said by the owner to have cut out and illuminated the wall behind it. It also lit up my bench quite well, with all the valve heaters glowing like November 5th. Heater supply rectifier W7 and boost diode V4 were quickly eliminated and the fault was eventually traced to the mains dropper – not open-circuit but short-circuit! When the dropper had originally been wound, the adjacent but isolated heater and surge limiter sections (R111, R116) had been almost bridged across by a whisker of resistance wire concealed under protective coating. Years of heating and cooling had eventually closed this unusual thermostat, placing the h.t. voltage across the heater chain. This undesirable link was removed by penknife surgery: fortunately the tube and valves lived to tell more Tales of the Unexpected.

The second 1500 had excessive contrast and sync crushing, even with the preset contrast control R34 at minimum. After the usual culprits in the video output

stage had been eliminated I found that the bias voltage at the base of the video driver transistor VT8 (TP2) was over 9V instead of 5-8V. This voltage comes from the junction of R79 (317 Ω) and R136 (62 Ω) at the earthy end of the heater chain. R136 had increased in value to over 100 Ω : two 120 Ω , 1W resistors in parallel soon biased VT8 in favour of a good picture. C.A.

Rank T20 Chassis

For intermittent tripping, first check that the over-voltage trip preset 5RV1 is correctly adjusted. If this is all right, check the following items in the order given: the line driver transistor's emitter diode 5D1 (ITT2002) which could be open-circuit intermittently; 5R13 (330 Ω) in the tripler circuit for being open-circuit; zener diode 5D2 (BZX79-B36) on the trip subpanel for being defective. If the set trips at switch on however check whether 7R11 (220 Ω) in the snubber network across the chopper transistor on the power supply panel is open-circuit.

For lack of width, check 4R69 (82k Ω) in the width circuit then make sure that the EW loading coil 5L1 hasn't got shorted turns and if this is o.k. check the EW correction coupling capacitor 5C15 (1 μ F) for being open-circuit.

Intermittent loss of colour can be due to a decoder fault of course, but if the trouble persists after fitting a replacement panel check whether the line pulse is present at plug 3Z6 (pin 8). If the pulse is present at the socket side but not the plug check for a dry-joint or poor lead connection. A less obvious cause of this fault is 4C24 (0.01 μ F) in the line generator circuit – check it by substitution. J.C.

Thorn 3000 Chassis

You still come across these sets in regular use giving quite good results. One came my way recently. The chopper transistor was short-circuit and as I could find no shorts and the h.t. fuse F603 was intact I replaced the transistor, reset the cutout, disconnected the tripler, and removed W615 in the monostable oscillator circuit to ensure that the h.t. would come up to only about 40V. Thinking I'd done enough by way of protective measures I switched on. Pop – another short-circuit chopper transistor. The h.t. fuse was still intact, so an overload in the line output stage etc. was unlikely. Another chopper transistor was inserted but this time I left its collector disconnected from the 300V input. On switching on the chopper drive waveform was found to be all right, so it appeared that something went wrong as the 60V h.t. line came up. With W615 disconnected about the only thing I could think of was the dynamic trip. Sure enough the TIC46 thyristor and its associated 1S921 diode were both leaky. No other fault could be found and with replacement dynamic trip components fitted the set worked a treat. P.H.

Grundig C7400 (CUC70 Chassis)

The problem was no sound with snow on the picture. The channel display LED would light at switch on but would

go out after a few seconds. We dismantled the chassis and considered how we were going to gain access to the tuning panel which stands vertically in the centre of the mother board. Our best bet seemed to be to start by checking the supply voltages on the mother board since these are readily accessible. The 15V supply was missing and on tracing back to the regulator (IC681) we found that it was dry-jointed. A touch of solder cured the problem. A point to note on these new Grundig sets is that it's important to quote the model number's prefix letter (C in this case) when ordering spares or service information as this indicates which chassis is fitted in the set. **M.D.**

Thorn 1615 Chassis

The customer's complaint was no picture and on examination we found that there was normal sound and a very dim line down the centre of the screen. The scan-correction capacitor C136 (0.15 μ F) turned out to be open-circuit. **M.D.**

Thorn TX10 Chassis

The volume or colour would suddenly alter or the set would go into standby when it had warmed up. Things would return to normal if the reset button was pressed. We thought this would be an easy one – change the focus control which can cause interference to the remote control system as a result of internal arcing. Not so however. The trouble was eventually traced to a dry-joint at pin one of the line output transformer. **M.D.**

Amstrad CTV2200

One of these sets came in dead as a result of a crack in the print around the mains filter transformer T501. The customer also complained that there was intermittent field roll. This was cured by adjusting VR805 – for 15V at TP22. The adjustment has to be done carefully if top foldover with teletext lines is to be avoided.

Dead set was the complaint on another of these receivers. When we switched on we heard the power supply and line timebase start up and shut down. We suspected an overload in one of the auxiliary circuits fed from the line output transformer and found that the 12V rectifier diode D806 (DFC10E) was short-circuit. **M.D.**

Grundig 8240

Absence of blue was the symptom and checks at the tube base showed that the trouble was in the RGB module. This chassis uses complementary-symmetry RGB output stages driven by a TBA530 chip (module 29301-046-01). The voltage at the base of the lower transistor in the blue output stage was very low while the other voltages in the stage were high. Moving back to the TBA530 we found that the blue feedback voltage at pin 9 was missing. Further checks led us to R1958 (470k Ω) which was open-circuit. **M.D.**

Hitachi CWP132 (NP6C Chassis)

The problem with this set was that the line speed would vary. In the fault condition there was a noise that sounded like internal arcing coming from the line output transformer but we found it impossible to take voltage measurements or make scope checks because everything

is so interrelated. So we ordered and fitted a new line output transformer, all to no effect. After a lot of component changing and soak testing we came to the conclusion that the problem lay in the line oscillator stage. When the 2SA844 line oscillator transistor TR702 was replaced the fault had cleared, though the transistor measured perfectly out of circuit. **M.D.**

Fidelity CTV14S

The initial complaint was no results. On investigation we found that R828 (10 Ω , 2W) in the h.t. line was open-circuit. A replacement overheated, indicating an overload in the line output stage, and on further investigation we found that the 25V supply rectifier D34 (RGP10B) was short-circuit.

Another of these sets would change channel when the remote control unit was used but on occasion failed to do so when the button on the front of the set was used. This was traced to poor soldering where the front panel switch pin is connected – the soldering looked perfect but was completely dry around the pin. **M.D.**

Decca 120-140 Series

The customer complained that the set would shut off after about five minutes or sometimes the sound level and picture width would alter. We found that in the fault condition the power supply was shutting down – also the remote control receiver was erratic, causing the sound level to alter. If the chassis was tipped or flexed anywhere the fault could be made to come and go: we eventually traced the problem to a break in the leg of C813 (0.01 μ F) which decouples pin 4 of the TDA4600 chip in the power supply. **M.D.**

Philips G8 Chassis

We thought we knew most of the problems on the G8 chassis, but this one caught us out. The fault was top field cramping – the set was fitted with the later type of timebase panel with BD131 field output transistors. The mid-point voltage was correct, but the bias preset was at nearly one end of its track instead of the usual mid-position. All the voltages were roughly correct so we worked back to the field oscillator stage. This uses a BRY56 silicon controlled switch and voltage checks are difficult here. Instead we made cold checks on the semiconductor devices. This showed that D4443 (OA47) was slightly leaky, and on replacing it we were rewarded with full field scan and the mid-point voltage setting up correctly with the control at its centre position.

Two days later we had a set with exactly the same symptom. Without thinking we replaced the OA47, but this time the fault remained. Looking at the circuit more closely we noted that the diode is forward biased by R4441, and on checking this we found that its value had increased from 27k Ω to 100k Ω . We changed this and left the new diode in for good measure. **M.D.**

Fidelity ZX3000 Chassis

The problem, intermittent field roll, was traced to the TDA8180 field/line processor i.c. being a poor fit in its holder. We've since had other faults, such as line jitter and intermittent no results, due to poor pin contact here. **M.D.**

Long-distance Television

Roger Bunney

November was a depressing month for both reception and weather. The high winds damaged a number of DXing installations while the rain damped any chances of enhanced tropospheric propagation, at least in our part of western Europe. Finnish readers on the other hand report a very good tropospheric opening with some quite spectacular results – see letters later. There was a slight lift over the UK on the 27th, and the prevailing high-pressure systems at the time of writing this (December 8th) suggest that a period of tropospheric reception lasting for several days lies ahead.

The mid-month Leonids meteor shower produced the expected increase in MS reception though the E layer ionisation wasn't very intense this time. Hopefully the December/January MS will be more lively! Sunspot activity has been almost non-existent though there was an increase towards the end of the month. Disturbances on the sun produced Auroral activity during the 13-17th: this was particularly intense in the north on the 16-17th, with reception of Scandinavian stations in Band I and TSS (USSR) chs. R1/2 on the 16th.

The brief SpE log is as follows:

8/11/84 DFF (E. Germany) ch. E4.
 9-10/11/84 CST (Czechoslovakia) R1.
 15/11/84 +PTT (Switzerland) E2.

17/11/84 YLE (Finland) E2.
 18/11/84 Unidentified ch. R1/E2 signals.
 20/11/84 RUV (Iceland) E4. There was a widespread opening from late afternoon through to 2100.
 23/11/84 NRK (Norway) E2, 3.
 24/11/84 SR (Sweden) E2, 3.
 25/11/84 SR E2. Various ch. E3/4/R2 signals during the early evening.
 26/11/84 SR E2.
 28/11/84 RTVE (Spain) E2; unidentified ch. R1 signal.



Thanks to Tony Privett (Basingstoke), Iain Menzies (Aberdeen), Hugh Cocks (E. Sussex), Roger Pates (Nottingham), Dave Shirley (Hastings) and Simon Hamer (Powys) for sending in reports during this rather bleak month.

Mobile ATV




Allan Latham (G8CMQ) went mobile here in south Hampshire during the month, transmitting f.m. video at 10W on 1.286GHz from a car with an omni-array atop St. Boniface Down, Isle of Wight. P5 pictures were received in Southampton and P4 pictures in Brighton some 55 miles away.

From our Correspondents . . .

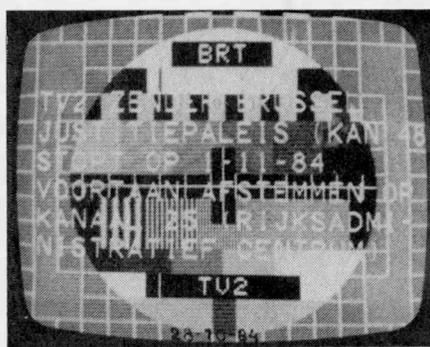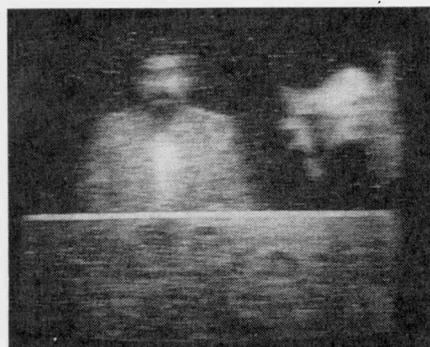Ryn Muntjewerff (Holland) has received a QSL confirming his reception of SVF, the Faroe Islands TV Service. The QSL mentions that test transmission times are 0800-1200 local time on Mondays, Tuesdays, Fridays and Saturdays and that programme transmission times are 1900-2330 on Tuesdays, Fridays, Saturdays and Sundays.



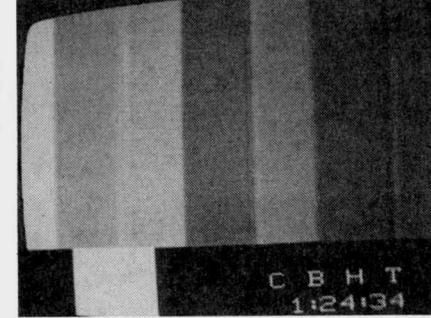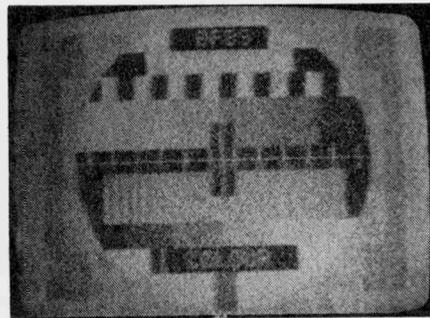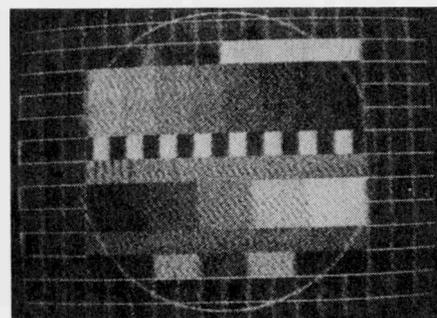Left: Unidentified Arabic ch. E2 signal received by Petri Pöppönen in Lahti, Finland at 1256 GMT on July 21st last. Centre: BRT-TV (Belgium) ch. E48 closure notice with instruction to retune to ch. E25. Photo from Ryn Muntjewerff, Holland. Right: Another photo from Ryn Muntjewerff, this time the new American Forces TV logo used on ch. E70 in Holland.



Left: The NDR-1 (W. Germany) test pattern received by Seppo Pirhonen in Helsinki, Finland on November 12th last at 1355 GMT (ch. E50). Centre: An even more remarkable reception by Seppo Pirhonen, BFBS W. Germany ch. E51 on November 11th at 2330 GMT – the transmitter power is only 10W. Right: Satellite reception at 4GHz by Frank Lumen in Denver Colorado – the Canadian network programme feed via the Anik-B satellite.

The studio was operated by just three people until October 1984 – a further seven have now been taken on. Ryn's Dutch reception was the farthest to date. The transmitter network is at present as follows:

| Station | channel | e.r.p. | Station | channel | e.r.p. |
|--------------|---------|--------|------------|---------|--------|
| Husareyn | E6 | 10kW | Eysturhovd | E11 | 10W |
| Slaettafjall | E7 | 10W | Punthavn | E7 | 1W |
| Saksun | E8 | 1W | Hesturin | E9 | 100W. |
| Eioiskollur | E8 | 10W | Nakkur | E10 | 1W |
| Stoolafjall | E10 | 200W | Hvalba | E10 | 1W |
| Brunaskaro | E11 | 10W | | | |

Petri Pöppönen (Lahti, Finland) had an excellent summer with much Band I reception from the Middle East. Of several excellent quality photos showing announcers we've selected a less clear one in the hope that someone might be able to identify the source – reception was at 1256 GMT, July 21st on ch. E2. During June Petri logged an Arabic station with the identification EBT, suspected as being Dumyat, Egypt ch. E4 at 0.9kW e.r.p.

Seppo Pirhonen (Helsinki) reports that a strong tropospheric opening occurred on November 11-13th, with excellent quality signals from the USSR, Poland, Czechoslovakia and W. Germany. Of the W. German signals one is almost certainly BFBS Celle on ch. E51. The distance is over 900 miles – from a 10W transmitter!

Finally, a request for help. Gareth Foster requires the circuit of a 405-line "Radar Video and Sync Generator, Model L" – it's a single-channel (B1) type. Maybe someone has some information on this?

Interference

I had problems with a 49-71MHz cordless phone over one weekend during the month under review. The source was eventually traced and the operators made aware of the situation and the new Telecommunications Bill. Since then there's been no further trouble.

News Items

UK: It turns out that "Channel 36" was a firm called Waveview Holdings Ltd. who, following their successful pirate TV transmissions, have been granted a test and development certificate by the DTI. Waveview Holdings are developing a "suitcase size" transmitter for the export market, expected to cost considerably less than conventional transmitters. The firm can be contacted at 67 Westow Street, Upper Norwood, London SE19. No further pirate TV transmissions will be carried out by Waveview.


A further sixty licences for UK 50MHz amateurs were issued at the end of November.

The DTI is to license low-power wideband radio alarms in the 173.2-173.35MHz band. These will be in addition to the low-power telemetry and tele-control equipment that's likely to be decontrolled shortly.

Norway: The Band I network is to be closed down progressively by the end of 1986. The authorities have granted 25 experimental 50MHz amateur licences for transmissions outside TV hours.

France: One technical magazine has published a design for a Canal Plus decoder and another plans to do so. Canal Plus obtained a court order preventing the sale of the first magazine though some copies were distributed. Interest in Canal Plus in continental Europe has been

SOUTH WEST AERIALS

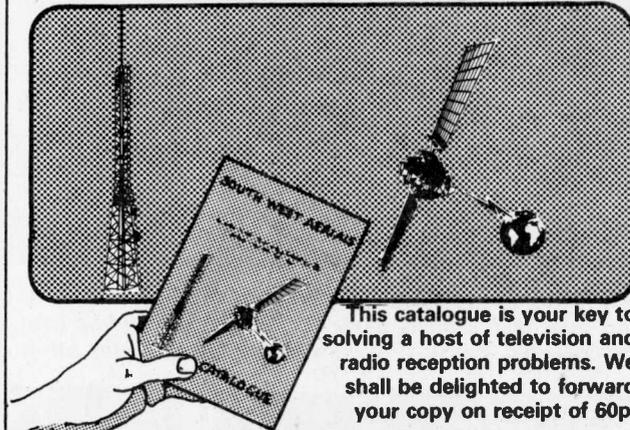

This catalogue is your key to solving a host of television and radio reception problems. We shall be delighted to forward your copy on receipt of 60p.

EQUIPMENT & PROFESSIONAL ADVICE

South West Aerials offer a unique blend of the best equipment and impartial professional advice.

Examples from our range:

| | |
|--|--------|
| WOLSEY HG36 'Quicksilver' Grouped UHF Aerial, 18dB High Gain; f/b ratio 28dB average (state group required A, B or CD) | £34.70 |
| WOLSEY 'Quantum' 300 30dB High Gain Grouped UHF Masthead Amplifier, (state group required A, B or CD) | £17.58 |
| WOLSEY 002 24 volt Matching Power Supply Unit for above Amplifier | £13.25 |
| TRIAx MTH13 Wideband Band 3 Aerial with twin reflector, 11.9dB gain very rugged construction | £36.60 |
| TRIAx 4000/3LN Wideband Band 3 Masthead Amplifier, 22dB gain with a low Noise figure of only 2.3dB | £29.80 |
| TRIAx 601/60 Power Supply Unit for above Amplifier | £11.75 |
| UNISON AR250 Rotator complete with Control Console (uses 3 core cable) | £42.25 |

(Alignment Bearing available for above to increase head loading)
Also available Black & White and Colour Multi-Standard VHF/UHF Televisions and Video Recorders (SAE or ring staking requirement)

We are THE DIXING Specialists, advice given on ALL reception problems (SAE please)
All prices inclusive of VAT and Carriage Delivery 7-10 days Access & Visa welcome



SOUTH WEST AERIALS (T)

11, Kent Road, Parkstone,

Poole, Dorset, BH12 2EH. Tel: 0202 738232.



TV LINE OUTPUT TRANSFORMERS

PRICES INCLUDE VAT & CARRIAGE

Delivery by return of post.

| | | | |
|--------------------------------------|--------|---|---------|
| RANK BUSH MURPHY | | ITT: VC200, VC205, VC207 | 9.20 |
| A774 with stick rectifier | 9.78 | VC300, 301, 302, 400, 401, 402 | 9.20 |
| A816, T16, T18, Z712, Z715 | 10.35 | CVC1, CVC2 (FORGESTONE) | 11.50 |
| T20, T22, T26, Z179, A823 | 11.50 | CVC5, CVC7, CVC8, CVC9 series | 9.20 |
| Z718 Basic unit | 13.50 | CVC20, CVC30, CVC32, CVC45 | 9.20 |
| T24e, T24h split diode | P.O.A. | FT110, FT111. P/no AT2063/02 | 11.50 |
| DECCA: 1210, 1211, 1511 | 11.50 | PYE: 169, 173, 569, 368 series | 9.20 |
| 1700, 2001, 2020, 2401, 2404 | 9.20 | CT200, CT200/1, CT213 series | 10.35 |
| CS1730, 1733, 1830, 1835 | 9.20 | 725-731, 735, 737, 741 Series | 9.78 |
| 30, 70, 80, 90, 100, 110, 130 Series | 9.20 | PHILIPS: 170, 210, 300 series | 9.20 |
| FERGUSON, THORN: 1590, 1591 | 9.20 | 320 series | 9.78 |
| 1690, 1691, built in rect. | 9.78 | TX, T8 mono series | P.O.A. |
| 1600, 1615, 1700 series | 11.78 | KT2, KT3 series colour | 9.20 |
| 1790 mono portable | 9.39 | G11 series split diode | P.O.A. |
| 3000, 3500, 8000, 8500, 8800 | P.O.A. | G8 and G9 Series | £9.20 |
| 9000, 9200, 9300 series | 12.00 | K30 | £P.O.A. |
| 9500, 9600, 9650 series | 10.99 | BINATONE: 9909 mono | 13.04 |
| 9800, TX9, TX10 series | P.O.A. | FINLUX 9560, 9670 | 13.91 |
| MOVIESTAR 3781, 3787 | 12.00 | GRUNDIG: most models in stock | |
| FIDELITY: FTU12 mono | 10.35 | NORDMENDE: FC125, Z206, Z306 | 11.50 |
| CTV14R, CTV14S colour | 15.83 | SANYO: CTP5101, 5103, TJ series | 11.50 |
| G.E.C. 2047 to 3135 mono | 7.50 | SHARP: C1851H, C2051H | 12.32 |
| 1201H, 1501H, 2114, 3133, 3135 | 9.20 | TELETON: TH14 mono | 13.68 |
| DUAL & SINGLE hybrid col. | 10.00 | TOSHIBA: C800, C800B | 19.45 |
| SINGLE STD solid state | 12.00 | TANDBURG: 190, CTV2-2, CTV3-3 | P.O.A. |
| SINGLE STD split diode | P.O.A. | TELEFUNKEN: most models in stock | |
| INDESIT: 24EGB hybrid | 9.50 | LINE OUTPUT TESTER | 16.79 |
| 12LGB, 12SGB mono portables | 10.35 | | |
| WINDINGS | | | |
| TYNE: main winding | 6.80 | | |
| RBM: T20, T22, T26, Z179 | 6.33 | | |
| WALTHAM: W125 eht winding | 2.37 | | |
| WALTHAM: W190, W191 eht coil | £6.00 | | |
| KORTING: hybrid winding | 6.90 | | |



Tidman Mail Order Ltd.,
236 Sandycombe Road,
Richmond, Surrey.

Approx. 1 mile from Kew Bridge.

Phone: 01-948 3702

Mon-Fri 9 am to 12.30 pm &
1.30-4.30 pm

Sat 10 am to 12 noon.

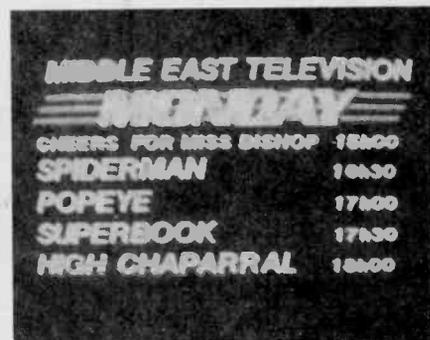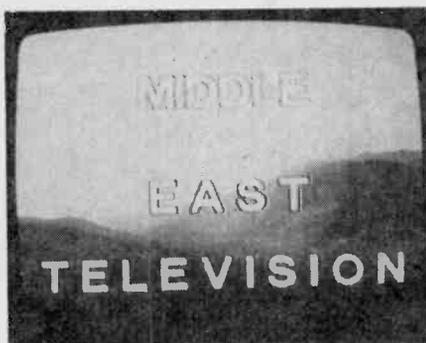

Left: European satellite reception at 11.65GHz – the Sky Channel logo received by North East Satellite Systems on one of their own dish aerials, from ECS-1. Centre: Middle East Television ch. E12 identification received in Cyprus by Marios E. Colocassides. Right: Another Marios Colocassides photo, this time a Middle East Television programme guide.



Left: Pirate TV in South London – the Thameside TV tuning caption on ch. E28, received last October. Centre: Unidentified Arabic signal, possibly a Dubai news announcer, received by Ryn Muntjewerff on May 23rd last on ch. E2. An example of double-hop SpE reception. Right: Further exotic reception by Ryn Muntjewerff last May (24th). This time Aramco TV ch. E3 from Dhahran, Saudi Arabia.

widespread. The Canal Plus PM5544 pattern carries “TDF” at the top and “RESEAU 4” at the bottom.

Middle East: English language military communications on 40.86, 44.88, 44.94, 45, 45.12 and 46.9MHz are often heard during SpE openings. They appear to originate from UN forces in the Lebanon.

In brief: RTL (Luxembourg) has been seen in Holland on ch. E64 (unlisted) – tests suggest that the Dudelage E7 transmitter’s e.r.p. is nearer 140kW . . . A high-power GDR (E. Germany) transmitter is now in operation on ch. E51 . . . The SBS-TV ch. 0 Sydney and Melbourne transmitters are due to close in 1986.

Meteor Showers 1985

Our thanks to the British Astronomical Association for the following 1985 meteor shower dates:

| | |
|----------------|---|
| Lyrids | April 19-25th, peaking on the 22nd. |
| May Aquarids | April 24th-May 20th, peaking on the 5th. |
| Delta Aquarids | July 15th-August 20th, peaking on the 28-29th. |
| Perseids | July 23rd-August 20th, peaking on the 12th. |
| Giacobinids | October 7-10th, peaking on the 8th at 1300 GMT. |
| Orionids | October 16-26th, peaking on the 21st. |
| Taurids | October 20th-November 30th, peaking on the 1-5th. |
| Leonids | November 15-20th, peaking on the 17th. |
| Geminids | December 7-15th, peaking on the 13th. |
| Ursids | December 17-24th, peaking on the 22nd. |

The Quadrantids shower occurred on January 1-6th. The Giacobini-Zinner comet will be present this year, the

Earth passing inside its orbit on September 5th. This could well produce a significant shower.

Satellite TV Publications

Satellite TV News ceased publication during the last week of November, leaving something of a void for satellite TV enthusiasts. Those interested in the subject should find *Satellite Orbit International*, published monthly in the US at \$4 a copy, of interest. For details write to Comm Tek Publishing company, PO Box 1048, Hailey, Idaho, USA 83333.

UHF Modulators

A convenient range of u.h.f. modulators is produced by Astec. I’ve been using one recently after constructing a distribution amplifier (one input, three outputs) to a BATC design for use with my video camera. One output goes to the 435MHz transmitter and another via the modulator to a TV set – providing a sort of poor man’s viewfinder for the camera. The Astec modulators generally provide an output on ch. E36 – some models have sound facilities as well. A technical specification sheet can be obtained from Thame Components Ltd., Thame Park Road, Thame, Oxon OX9 3XD.

ATV Handbook

A revised and updated version of the *Amateur Television Handbook* has been published by the British Amateur Television Club. Earlier editions were very successful and soon sold out. The new edition has been completely revised and includes information on new i.c.s and 24cm f.m. ATV. This highly recommended publication is available for £2.40 including post from 14 Lilac Avenue, Leicester LE5 1FN.

Service Bureau

Requests for advice in dealing with servicing problems must be accompanied by a £1.50 postal order (made out to IPC Magazines Ltd.), the query coupon from page 227 and a stamped addressed envelope. We can deal with only one query at a time. We regret that we cannot supply service sheets nor answer queries over the telephone.

PHILIPS G11 CHASSIS

The fusible resistor R5406 in the supply to the sound output transistors keeps springing open and the heatsink for the transistors gets hot. The current doesn't seem to be excessive however and the voltages are all about right.

The fusible resistor could be over-reacting. Try cleaning the contacts and renewing the solder blob – use 60/40 standard solder. The output transistors can suddenly develop leakages when warm, flash over and reform, so replace them if the fusible resistor repair doesn't work. It should be possible to hold the heatsink with your fingers without getting scorched.

ITT CVC9 CHASSIS

When the contrast is turned up to get a reasonable picture the raster bulges outwards at the sides, causing bent verticals. Line pairing at the top of the screen also occurs. These symptoms are not present at low contrast. Turning up the brightness has a similar effect.

We have seen this combination of symptoms on several occasions and have traced the cause to the earthing of the c.r.t.'s graphite coating. Check the spring contacts and the continuity to the c.r.t. base panel and the chassis metal. If all this is satisfactory the tripler is suspect for internal discharge at high beam current. Before condemning it, check the associated components R426 (470 Ω) and C309 (330pF).

HITACHI NP6C CHASSIS

The mains rectifier produces 340V which is present at the collector of the chopper transistor but there's no 110V output from the power supply. The circuitry seems rather complicated – can you suggest some simple checks?

The fault is becoming quite common on these sets. There's a start-up multivibrator that produces an initial burst of oscillation, until C910 has charged. By then the h.t. should be present and normal operation should start. The trouble spots are in the chopper control feedback network – resistor R937 (220 Ω), the thick-film voltage divider module CP901 (HM9102) and the error detector transistor TR907 (2SC458). It's best to replace these, taking care over the soldering. Also desolder, flux, tin and resolder all the tags on the chopper transformer T902 and the line output transformer T703.

JVC HR7200EK

When the stop button is pressed at the end of a short recording, i.e. not a full reel, the tape unwinds from the head on to the left-hand spool as normal but the right-hand spool also unwinds for approximately ten seconds.

This results in the loss of the final ten seconds of the initial recording when a subsequent recording is made. The problem occurs throughout the length of the tape, i.e. the tail end of the previous recording is always lost. We have to let the machine continue to run for ten-twelve seconds after the end of each item recorded.

This isn't a fault but is inherent in the design – the microcomputer i.c. is programmed to do this to ensure that when stop is selected with the tape threaded, near to or at the end of the tape, the leader splice is wound back so that it cannot contact the video head if play or record is selected. It also avoids tape looping.

THORN 8800 CHASSIS

This set was fitted with a regunned tube and then reconverged. The monochrome picture is perfect but when the colour control is turned up there's an effect like co-channel interference or bad interlacing. It's most noticeable on yellows and all colours down to magenta. The darker fields are clear.

The set's suffering from Hanover bars. If adjusting the delay amplitude potentiometer R167 and (carefully) coils L115 and L119 at the delay line input and output don't clear the effect, the delay line itself is suspect. Before replacing it, check the jointing and condition of the associated components.

PHILIPS G8 CHASSIS

After the set has been on for a time the convergence over the top half of the screen becomes incorrect. Adjusting the controls restores the convergence and produces a very good picture, but when the set is next switched on convergence is again lost as the set warms up.

The problem is due to dynamic convergence drift and will almost certainly be cured by replacing the clamp transistors T1910 and T1914.

ITT CVC25/3 CHASSIS

When the set is switched on several thin black lines appear on the upper half of the picture. These persist until eventually about half an inch at the top and bottom of the picture are lost. This condition continues for some time, though switching off and on produces a full picture – but with the black lines. Eventually the condition clears and the set gives a fault-free picture for a couple of hours. After that the problem returns.

There are several possibilities for this one. First, check the tuner a.g.c. smoothing capacitor C205 (220 μ F) by substitution. It's on the CMU30 tuner module. If necessary, go on to check the 12V supply: adjust R104 for 12V and check C71 (470 μ F) and C72 (10 μ F). Finally, examine the field timebase. Module CMF25 can be checked by substitution and the FT3055 output transistors by spraying with aerosol freezer.

THORN TX9 CHASSIS

The picture has shifted to the right, by about a quarter of the picture width. We suspect the TDA9503 sync separator/line oscillator chip. Any other suggestions before we order a replacement?

The usual cause of this trouble is change of value in one or other of R212 and R217 (both 220k Ω) in the flyback pulse feed to the phase detector in the i.c. Other items worth checking are R218/9 (both 10M Ω), R213 (82k Ω) and C172 (0.01 μ F) which could all affect the picture centring.

SANYO VTC5000

This machine will not complete, without cutting out, any of the following functions: rewind, fast forward, record or play. It will occasionally play or record a full cassette, but once a function cuts out it becomes increasingly more difficult to restart the machine. Usually it's necessary to put the set on standby for several hours before trying again. Rewind seems to aggravate the fault condition more than the other functions do. When the machine cuts out, the stop button must be manually pressed before the stop mode is actually entered.

A very common cause of this problem is failure of the reel motor. It's not expensive and is easy to fit if you have the right hex wrench (VJ0108). If replacing the motor fails to cure the fault you'll have to check the deck sensor inputs to the microcomputer i.c. in the sycon department.

GEC 2114

The l.t. rail, line hold control and line oscillator coil have all been set up correctly. Line hold is o.k. for about an hour, then starts to slip.

In our experience the most common problem in the line section of this little portable is dried-up and aged electrolytics. We suggest you replace C224 (1 μ F) and C226 (10 μ F) in the reactance stage and would be surprised if this did not cure the problem.

THORN 8500 CHASSIS

After about twenty minutes a narrow, broken band of colours jitters up and down about four inches from the left-hand side of the screen, accompanied by bands of very fine lines extending across the picture. The interference sometimes moves slowly down the screen and at other times upwards.

These symptoms suggest that some form of arcing or sparking is occurring within the set – it may be visible if the set is examined in darkness. The main areas of suspicion are the power supply panel (check for dry-joints, particularly on choke L701 and the electrolytics C704/6) and the high-voltage areas of the line output stage, around the e.h.t. rectifier and focus circuit. Also check that the tube's Aquadag coating is firmly bonded to chassis via the c.r.t. base panel.

SONY KV1810UB Mk II

When the set is first switched on there are momentary variations in both the height and width, with a popping noise on the sound. This happens every few seconds, but after about ten minutes stable conditions are achieved.

The fault seems to be h.t. flutter, which is often caused by a noisy thermistor (Th601, type TH4700) in the error sensing circuit. Replacing it and setting VR601 for 130V at L603 should clear the problem.

FERGUSON 3292

Prerecorded cassettes are played back in monochrome only, though colour is o.k. with the machine's own recordings. I've tried slight adjustment of the 4.43MHz VXO preset on playback and have also changed the AN236 and AN305 i.c.s.

It would seem that the machine is making non-standard recordings and that the fault is the same on record and playback. Check that the connections to one of the video heads are not reversed, and for the presence of the drum flip-flop pulses at TP222 (scope or

meter plus diode probe, or alternatively 0.1 μ F to TP19 on the audio-servo PCB). If missing, trace the wiring back to the servo PCB. If the fault is still present the only course is to attempt to set up the oscillators in the colour circuitry as laid down in the manual, using a frequency counter. This will either cure or pinpoint the cause of the fault.

THORN 1590 CHASSIS

When the set is switched on the height begins to decrease slowly until after about five minutes there's complete field collapse. Switch off, try again half an hour later, and the same thing happens. The field output transistors have been replaced.

The first suspect is the field oscillator isolation diode W3 which can leak to give this symptom. If a replacement fails to cure the fault, suspect protection diode W4, driver transistors VT17/18 and the linearity amplifier transistor VT16 in that order. Note that problems with these semiconductor devices are often not shown up by making cold resistance checks.

SONY KV1340UB

The problem with this set is a very bright line, about a quarter of an inch wide, across the centre of the screen. The picture is otherwise good, with no distortion. The brightness control varies the intensity of the line along with the rest of the screen.

We suggest you disconnect R165 on board C to prove that nothing strange is happening in the field flyback blanking circuit. If the line remains it's likely that some form of crossover distortion is occurring in the field output stage, though this is very rare. Suspects would be the driver and output transistors Q509/510/901, the supply decoupler C525 (33 μ F) and the electrolytics in the field output stage – C545/6/7.

THORN 9600 CHASSIS

The chopper transistor keeps going short-circuit, blowing the mains fuse. This happens at switch on. The diodes that shape the chopper transistor's drive have been replaced, also the components in the snubber network and the overshoot clipping network. The rectifiers fed from the chopper transformer have been disconnected in turn, but the fault persists.

If the chopper transistor's drive is not square it will quickly succumb. We suggest you check R518 (1 Ω) and R521 (100 Ω) in the chopper transistor's base circuit and R514/5 (both 39k Ω) which bias the base of the driver transistor. Make sure that all the joints in the area are good. A variac is very useful when tackling a fault of this sort.

PHILIPS N1700

The machine runs for a short time on either record or playback then switches off. After resetting it the machine will run for a longer period then do the same thing. The picture and sound are otherwise perfect.

Check R101 (1.2 Ω) in the power supply (bottom panel) – a replacement must be of this exact value. If the playback picture breaks up prior to the fault, check whether the drum or capstan stops rotating or slows down – the drum spindle bearing and both motors are suspect. Other possibilities are loss of either the drum or capstan servo pulses: if both pulses are present the collectors of TS109 and TS111 in the power supply should be at not more than 3.4V with the tape running.

TEST CASE

266

Each month we provide an interesting case of television servicing to exercise your ingenuity. These are not trick questions but are based on actual practical faults.

Last autumn we had some very stormy weather in this locality. In its wake came the usual crop of equipment damaged by voltage spikes and static charges (up the mains and down the aerial lead respectively). In the main most older TV sets are reasonably immune to this sort of thing: mains filter capacitors and aerial isolator assemblies might be found carbonised, with the rest of the set intact and ready to go. The latest equipment seems to be much more vulnerable to storm damage, with i.c.s and transistors falling like skittles once the high voltage has found its way on to a printed panel.

A patient that escaped lightly was a Ferguson colour portable fitted with the TX90 chassis. It seemed that the surge had come up the a.c. power line since both fuses on the mains transformer had failed and a quick check on the four rectifier diodes D120-3 showed that D120 had welded itself up – it was a dead short. This item and the fuses were replaced and after a cursory glance at the picture (Saturday afternoon sports programme!) the little set was sent on its way. Our customer sent off a claim to his insurance company that same day.

The set came back on Monday with a note that said "wiggly picture, required ASAP". Now Monday morning is not our best time, so the set was put on the bench to warm up while we sorted out the job cards and brewed some coffee. An hour later we returned to the set whose picture was by now wiggling nicely – but only in the bottom left-hand corner! Each curve was accompanied by a pretty impurity pattern. Our first thought was that the degaussing thermistor might have suffered as well, but if this was the cause of the problem why was the effect confined to a corner at the bottom of the picture? Disabling the degaussing circuit proved that it had nothing to do with the fault.

With the back off we realised that the mains transformer T101 was mounted just behind the screen area affected. We also noticed a strong smell of hot varnish. It was almost too hot to touch! Plainly the transformer was overloaded in some way and was generating a sufficiently strong magnetic field to upset the c.r.t. beam landing. We had a known good TX90 in the workshop so we compared the d.c. resistances of the mains transformer primary windings. This failed to provide any clue and we came to the conclusion that the transformer in the faulty set had developed shorted turns. Since both sets had been

dismantled we tried swapping the transformers over. Surprise, surprise! The good transformer in the faulty set soon began to heat up while the suspect transformer in the guinea-pig set behaved impeccably, running cool with no effect on beam landing.

The cause of the trouble was found without too much difficulty, and there's little doubt that the damage was done at the same time that D120 was destroyed by a mains surge or spike. As well as underlining our laxity in releasing the set without thoroughly examining the picture, this case highlights the effectiveness of a certain section of the Ferguson set's circuit design.

Watch this space next month for the solution!

ANSWER TO TEST CASE 265 – page 163 last month –

The problem with our Decca CS2230 (Bradford chassis) was simple enough – a short-circuit from the line output transformer's primary winding to chassis. As a result the boost diode was overheating and the h.t. fuse would then blow. The stock-fault cause of this trouble is a short-circuit boost reservoir capacitor (C436), but you'll remember that we'd checked this and also the fifth harmonic tuning capacitor C435.

With the meter connected between pin 12 of the line output transformer and the chassis metal we next disconnected, one at a time, all the wires to the primary winding. Continuity was still indicated on the meter, and it wasn't until we removed the fixing screws to release the transformer assembly that the meter's pointer dropped back – the transformer itself was internally shorted to the core and frame! Close examination then revealed a degree of rusting and corrosion on the metal U bolt that holds the ferrite core moulding together.

Even then we weren't completely out of the woods! By some ghastly mistake, the Weyrad transformer fitted as a replacement was of the type intended for use in small-screen models with 20kV e.h.t. It worked, but with lack of width, poor e.h.t. regulation and other troubles. It was some time – after replacing many peripheral components – before we realised what had happened. The stores man was promptly taken to task over this . . .

If you've got a faulty hybrid TV set please don't bring it to us – we can't afford to take it on except on a five-minute guarantee basis!

QUERY COUPON

**Available until 20th February 1985.
One coupon, plus a £1-50 (inc. VAT)
postal order, must accompany EACH
PROBLEM sent in accordance with the
notice printed on page 225.**

TELEVISION FEBRUARY 1985

Published on approximately the 22nd of each month by IPC Magazines Limited, King's Reach Tower, Stamford Street, London SE1 9LS. Filmsetting by Trutape Setting Systems, 220-228 Northdown Road, Margate, Kent. Printed in England by The Riverside Press Ltd., Thanet Way, Whitstable, Kent. Distributed by IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. Sole Agents for Australia and New Zealand – Gordon and Gotch (A/sia) Ltd.; South Africa – Central News Agency Ltd. Subscriptions: Inland £11, overseas (surface mail) £12 per annum, payable to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex RH16 3DH. "Television" is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to currency exchange fluctuations and VAT, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever. ISSN 0032-647X.

TRAINING COURSES

TELEVISION & VIDEO SERVICING

THESE FULL-TIME COURSES INCLUDE A HIGH PERCENTAGE OF COLLEGE BASED PRACTICAL WORK TO ENHANCE FUTURE EMPLOYMENT PROSPECTS

VIDEO CASSETTE RECORDER SERVICING 6 WEEKS FULL-TIME (April 22nd to May 31st)

Intensive course intended for qualified television service engineers or applicants with similar background. The course combines the advantages of industrial and academic training and includes a high percentage of practical work. Selected applicants will be eligible for a full grant from MSC under TOPS to cover tuition fees and maintenance.

12 MONTHS LEC Diploma TELEVISION & VIDEO SERVICING (Basic Electronics, TV, VCR, CCTV, Testing & Fault Diagnosis)

6 MONTHS LEC DIPLOMA TELEVISION & VIDEO SERVICING

(Suitable for applicants with previous electronics training - e.g. BSC, HND, CGLI, B/TEC, etc.)
(All the above courses commence on April 22nd & Sept. 16th)

ADDITIONAL FULL-TIME COURSES
APPROVED BY THE BUSINESS &
TECHNICIAN EDUCATION COUNCIL
(These courses commence on April 22nd &/or Sept. 16th)

2 YEAR BTEC National Diploma (OND) ELECTRONIC & COMMUNICATIONS ENGINEERING

(Electronics, Computing, Television, Video, Testing & Fault Diagnosis)

15 MONTHS BTEC National Certificate (ONC) ELECTRONIC EQUIPMENT SERVICING

(Electronics, Television, Video, Cassette Recorders, CCTV, Testing & Fault Diagnosis)

15 MONTHS BTEC National Certificate (ONC) COMPUTING TECHNOLOGY

(Electronics, Computing Software/Hardware, Microelectronic Testing Methods)

9 MONTHS BTEC Higher National Certificate (HNC) COMPUTING TECHNOLOGY & ROBOTICS

(Microprocessor Based Systems, Fault Diagnosis, ATE, Robotics)

Full Prospectus from:

LONDON ELECTRONICS COLLEGE (Dept TF)
20 PENYWERN ROAD, EARLS COURT,
LONDON SW5 9SU. Tel: 01-373 8721

NORTH WALES TELEVISION SUPPLIES FLINT 5878



Working sets from £25
Untested sets from £15
Mono £4
Portable £15



Unit 32,
Manor Industrial Estate,
Bagillt, Clwyd.

ELECTRON GUNS TV TUBE COMPONENTS

If you are rebuilding or Manufacturing TV tubes - We are the leading suppliers of Electron Guns and TV Tube Components to the TV Tube Industry. We specialise in all aspects of Electron Mount Technology.

Our product range includes more than 250 gun types for Colour, In Line, Mono and Display Tubes along with Mount Parts, Bases, Getters, Sealoffs, and all other associated items for TV Tube Production.

A Full Technical Back-up and Advisory Service is available to all customers World-wide.

Please request our current catalogues and Data Information.



NEW ROAD,
STUDLEY,
WARWICKSHIRE B80 7LY
ENGLAND.

Telephone: 052-785 2684 or 2639 Telex: 336924 Grifem G.

SATELLITE RECEIVING SYSTEMS

1m and 2m glassfibre dishes
other sizes available.

Feeds, support and mounting systems.
Low noise amplifiers, downconverters.
Complete terminals for 4 Ghz, other
frequencies available.

Demonstrations by appointment.

L & S Bear Electronics Ltd.
Yeo Lane, Colley Lane,
Bridgwater, Somerset.
Telephone: Bridgwater (0278) 421719

CENTRAL T.V.

LATE MODEL T.V. NOW IN STOCK

**G.11 REMOTE + TEXT, ITT REMOTE, THORN 9600, 9800,
BUSH T20/T22/T26, DECCA 80/100, G.E.C. IN LINE**

SPECIAL OFFERS ON WORKING SETS

| | |
|-----------------------|------|
| 10 550 G8 22" | £220 |
| 10 520 G8 22" | £180 |
| 10 ITT CVC 5-8-9..... | £180 |
| 10 DECCA HYBRID..... | £180 |
| 10 BUSH MIXED | £140 |
| 10 THORN 8500 | £250 |

SPECIAL OFFERS ON OFF THE PILE SETS

| | |
|---------------------------|------|
| 10 550 G8 22" | £130 |
| 10 520 G8 22" | £90 |
| 10 ITT CVC 5-8-9..... | £120 |
| 10 DECCA HYBRID..... | £120 |
| 10 BUSH MIXED | £90 |
| 10 THORN 8500 | £170 |
| 10 THORN 3000, 3500 | £100 |

VHS VIDEOS – 100's IN STOCK

BRAND NEW 14" AND 16" PORTABLES

BRAND NEW PYE 20", 22", 26" WITH STEREO – TEXT – REMOTES

MANY MORE BARGAINS IN STOCK – PHONE AND HAVE *YOUR* ORDER READY FOR COLLECTION
LORRY LOADS DIRECT FROM SOURCES DELIVERED TO YOUR DOOR

HOT LINE BIRMINGHAM

021-622 1023

021-622 1517

48/52 PERSHORE STREET
BIRMINGHAM B5 4RR

HOT LINE LONDON

01-807 4090

01-884 1314

CEDAR HOUSE, NOBEL ROAD,
ELEY ESTATE, EDMONTON, LONDON

Ex-Rental Colour TVs

PHILIPS

26" – 520 from £4 22" – 520 from £8
26" – 550 from £8 22" – 550 from £12

All makes and models many working!

Inc. Thorn 8800/9000, Pye 222, GEC 2147

Van loads direct from source

Thorn VHS Video Cassette Recorders from £95 each.

For price list & DETAILS:

TEL KLW Ltd.

SOUTH

Francis
0582 24177
17 West Side Centre
LUTON

YORKS

Pauline
0274 665670
1043 Leeds Road
Thornbury
BRADFORD

LANCS

Frank
0925 826387
Priestwood Court
Risley Ind. Estate
Junction 11 M62
WARRINGTON

SCOTLAND

Matt
0698 282141
Peacock Cross
Ind. Estate
Burnbank Road
Hamilton

TV LINE OUTPUT TRANSFORMERS

FAST RETURN OF POST SERVICE

| RANK BUSH MURPHY | PHILIPS |
|----------------------------------|---|
| Z146 A640 dual std mono 8.00 | 170 series dual std mono 8.00 |
| Bush A792, A793 | 210 300 series mono 8.00 |
| single std mono 8.00 | G8 & G9 series colour 8.00 |
| A774 single std mono 8.00 | PYE 368, 169, 569, 769 mono 7.00 |
| A816 solid state mono 9.00 | 725-741 colour 8.00 |
| DECCA | WALTHAM 125 9.00 |
| MS1700200120202401 mono 7.00 | REWIND SERVICE - available for most continental types, i.e. Kuba, Luxor, Korting, Tyne, Berry Skantic, K80 £15.00 inc pp, VAT. Old lopt required. |
| MS2404 2420 2424 mono 7.00 | WINDINGS |
| CS1730 1733 colour 8.00 | SDVEREIGN FARA £15.00 |
| CS1830 1835 colour 8.00 | PLUSTRON PALLADIUM |
| '30' series Bradford colour 8.00 | 14" colour overwind |
| 80 series colour 8.00 | RANK BUSH MURPHY |
| 100 series colour 8.00 | T20a T22, T26 Pri & Sec 6.00 |
| FERGUSON HMV MARCONI | Z718 primary state 18" or 22" 6.00 |
| 1600 8.00 | Z718 EHT overwind 7.00 |
| G.E.C. | ULTRA THORN |
| 2047 to 2105 7.00 | 1690-1691 EHT overwind 7.00 |
| 2000 to 2064 dual std mono 7.00 | 1590 EHT overwind 6.00 |
| DUAL STD hybrid colour 8.00 | Waltham 190 EHT overwind 8.00 |
| SINGLE STD hybrid colour 8.00 | PRICES INCLUDE |
| Indesit 20EGB 24EGB mono 9.00 | P.P. & 15% VAT |
| KB - ITT | |
| VC200 VC205 VC207 mono 7.00 | |
| CVC5 CVC7 CVC8 CVC9 col. 9.00 | |
| CVC20 series colour 8.00 | |
| CVC30 CVC32 series colour 8.00 | |
| CVC45 8.00 | |

All lopts and windings are new and guaranteed

Open Mon.-Fri. 9 to 5.30 pm
Delivery normally by return.

S.A.E. all enquiries
Barclaycard and
Access welcome

For orders placed at the post office
Trans cash
505 4856

PAPWORTH TRANSFORMERS

80 Merton High Street,
London SW19 1BE

01-540 3955



NO WORKERS!

WITH OVER 1,000 ARRIVING
WEEKLY WE DON'T HAVE TIME

ALL SETS UNTESTED

WE ARE ONE OF THE OLDEST
ESTABLISHED EX-RENTAL
DEALERS WITH THE SAME RENTAL
COMPANY FOR OVER 15 YEARS.

| | |
|------------------------------------|----------|
| GEC S/State | £15 |
| GEC Hybrid | £8 |
| BUSH 1 and 2 Chip | £10 |
| DECCA | from £10 |
| AUTOVOX | £15 |
| NORDMENDE | £15 |
| SALORA S/State, some Remotes | £15 |
| SALORA Hybrid | £8 |
| TANDBERG S/State Dual Tuners | £20 |
| TANDBERG Hybrid Dual Tuners | £8 |
| PHILIPS G8 | from £10 |
| 17" THORN | £15 |
| 22/26" THORN | from £10 |
| MONO 20" S/STD | £5 |
| MONO 24" and D/STD | £1 |

BEST DEAL IN U.K.

**CASH ONLY,
IT DOESN'T BOUNCE!**

MIXED LOADS DIRECT FROM
SOURCE AVAILABLE AT
KEEN PRICES

FRANK FORD

(TV TRADE DISPOSALS)
SCHOOL LANE, GUIDE,
BLACKBURN, LANCS.
Telephone: 0254 64489

CentreVision

TEL: 0222-44754
SLOPER ROAD
LECKWITH
CARDIFF CF1 8AB
OPPOSITE CITY FOOTBALL GROUND
5 MINS FROM M4
TELEVISION/VIDEO
(VHS + BETA)
FROM £165

| | |
|---------------------------------|------|
| ★ ITT CD752 REMOTE | £115 |
| ★ PHILIPS G11 | £50 |
| ★ GEC STARLINE 22-20 (Remote) | £35 |
| ★ PYE CHELSEA | £25 |
| ★ THORN 9000 20" | £39 |
| ★ DECCA 22" BLACK FRONT VERICAP | £25 |
| ★ RANK T20 REMOTE | £50 |
| ★ PHILIPS 550 | £25 |

PRICES SUBJECT TO VAT

OPENING HOURS:
MONDAY - FRIDAY 9.00 - 5.30
SATURDAY 9.00 - 1.00

T.V. DISTRIBUTORS NORTHERN (LEEDS)

Large stock of good quality ex rental/part
exchange colour TV's.

THORN, ITT, PHILIPS, GEC, PYE,
DECCA, BUSH, JVC

★ ★ ★
GOOD DISCOUNT FOR QUANTITY

★ ★ ★
TEL: LEEDS (0532) 624996
TV DISTRIBUTORS NORTHERN,
UNIT 10, Ashley Trading Estate,
Buslingthorpe Green, Leeds LS7 2HG.

IRISH TV NOTICE (EX RENTAL T.V. SALE)

We can supply in good working order Bush, Pye and
Ferguson from £60, Philips G.8. From £80, Decca from
£90, B/White £25, Re-Gunned C.R.T.s from £40 (We have
our own Re-Gunning plant). 500 sets to choose from.
Fresh stocks weekly. Phone now for full price list to
Ireland's largest distributor of used TVs to the trade.

ALL PRICES INCLUDE V.A.T.
We can deliver to any part of Ireland.

TELE SPARES LTD.

Unit 113, Elm Road,
Western Industrial Estate,
Dublin 12, Ireland.
Telephone: Dublin 521211/521756.

MANTEL

Manchester's No. 1 in Ex-Rental TVs
VHS Video now in stock

Working sets ready for re-sale

| | | |
|-----------------|-------------|-----|
| Philips G8 550s | 22/26 | £45 |
| Philips 18" | | £40 |
| Philips G8 520s | 22/26 | £35 |
| GEC S/State | from | £35 |
| Thorn 17" 8000 | | £30 |
| Decca 30 | 18/20/22/26 | £30 |
| Japanese | from | £30 |

Many other makes available
 from £25

Discount on quantity

Some Examples of UNTESTED TVs available

| | | |
|------------------------------|--------|---------|
| Thorn | 10 for | £125 |
| Philips | 6 for | £90 |
| Bush | 6 for | £80 |
| GEC | 6 for | £60 |
| Decca | 6 for | £60 |
| Mono TVs avail. s/s | | £4 each |
| New TV trolley stands | | |
| All sizes | | £4.95 |
| All Prices subject to V.A.T. | | |

Ex Equipment Panels & Tubes Available
Over 2,000 TVs in stock

Ring for quote. Callers welcome.

419 Barlowmoor Road, Chorlton, Manchester M21 2ER.
Tel: 061-861 8501

TV TUBE POLISHING AT

Your Own Premises
 with our DIY Polishing Kit

The Kit includes:
 Everything you need to polish approx. 25* tubes to a high standard. Detailed instructions on how to do the polishing. All you require is an Electric Drill.

Kit Price £45 inc P&P and VAT.
 Available from Luton only.

*Depends on depth and area to be polished.

TV TUBES TUBE POLISHING
FREE DELIVERY*

Quality, High Temperature Reprocessing

| Colour Tubes | One year guarantee (optional extension up to three years) | Two year guarantee (optional extension up to four years) |
|--------------------------|---|--|
| Delta | | |
| 90° up to 20" | £26 | £29 |
| 90° up to 22" | £30 | £33 |
| 90° up to 26" | £32 | £35 |
| 110° 26" | £33 | £36 |
| (fast heat, narrow neck) | | |
| In Line & PIL | | |
| Up to 20" | £36 | £42 |
| Up to 22" | £38 | £44 |
| Up to 26" | £40 | £46 |

All tubes exchange glass required.

Your good, working tubes with scratches or small chips, can be **POLISHED** with our purpose built polishing equipment. **Only £7 per tube.**

Delivery charge on colour tubes: Within 40 miles of Luton.

1 tube £4. 2 or more tubes **FREE DELIVERY** ★

Nationwide delivery available, charges on application.

Please add 15% VAT to all prices. Callers welcome. Please phone first.

WELL VIEW

114-134 Midland Rd,
 Luton, Beds.

Open Mon-Fri 8am-6pm, Sat 9am-5pm. Tel. 0582-410787

Your Local Tube Stockist:

Well View, Southampton. Tel. 0703 331837.

Retach Ltd., Northwood, Middx. Tel. 09274-27019

West One Distributors Ltd., Gt. Missenden, Buckinghamshire.
 Tel. 024 06 3609

Rushden Rentals Ltd., Rushden, Northants. Tel. 0933-314901

Daventry Rentals, Daventry, Northants. Tel. 03272 77436

Rea & Holland, Ipswich, Suffolk. Tel. 0473 827562

WANTED A56/A66-510X/540X Old glass for cash

HOCKLEY DISCOUNT TELEVISIONS

**94 Soho Hill, Hockley,
 Birmingham B19 1AE.**

Telephone: 021-551-2233

PRICES START FROM £6
WORKING SETS FROM £18
FROM OUR SHOWROOM

DISCOUNT ON QUANTITY
BEST QUALITY SETS AVAILABLE
AT UNBEATABLE PRICES

**PHILIPS G8 550 FITTED WITH
 REGUNNED TUBES £38**

Philips G8, G11, Bush T22, GEC, Starline, Japs.,
 Decca 1800, Pye 222s, BRC 9000, 9600, 9800,
 Sony, latest Hitachi, ITT, CVC30, CVC45, plus
 remote control models.

NORTHERN T.V. DISTRIBUTORS

**Unit 2, Perth Court,
 Team Valley Ind. Estate,
 Gateshead, Tyne & Wear**
Telephone: 091-487 5389

Opening hours 9 - 7 Monday - Saturday
 Sundays by appointment.

Have you one of these?



Then you need one of these

Best Guide to Microcomputer Software

SOFTWARE INDEX

1984 No. 5 £1.50

Now with 5,000 programs
more educational, games, business & personal
management listings than ever before!

ON SALE NOW!

TELETRADERS

Forde Road, Brunel Industrial Estate,
Newton Abbot, Devon
Telephone: (0626) 60154

The Best Quality Sets Available
Anywhere

All First Class working order and excellent
cabinets.

| | |
|--------------------------------|-----|
| Philips G8 550 | £40 |
| Philips G11 | £85 |
| GEC Solid State | £35 |
| Thorn 3500 Electronic 22" | £35 |
| Thorn 9000 | £60 |
| Thorn 8800 | £45 |
| Thorn 9800 | £55 |
| Thorn 1500 Mono 20" very clean | £6 |

Full spares back-up of tubes and panels –
Bulk terms to other wholesalers



THE NO. 1 WHOLESALER IN THE SOUTH

VIDEO HEADS MONOLITH electronic products

HIGH QUALITY UNIVERSAL VIDEO HEAD
REPLACEMENTS FOR ALL VHS AND BETAMAX
VCR MACHINES

VHS Part No. 3HSS (5mm Centre Hole) £29.95 PRICE
VHS Part No. 4HSS (15mm Centre Hole) £29.95 EACH
BETAMAX Part No. PS3B £38.95 EX.
REPLACEMENT KIT (17 Pieces Boxed) £17.35 V.A.T.
PLEASE ADD 15% V.A.T. PLUS P&P £2.00 PER ORDER
OUR FULL CATALOGUE AVAILABLE ON REQUEST.

Please allow between 14 and 28 days for delivery.

AUDIO + VIDEO HEADS - MOTORS - PARTS
Suppliers to most U.K. Distributors/Service Organizations

THE MONOLITH ELECTRONICS CO. LTD

5-7 Church Street, Crewkerne, Somerset TA18 7HR, England
Telephone Crewkerne (0460) 74321 Telex 46306 MONLTH G

2 YR. GUARANTEE **APOLLO** 20/30 AX

TRADE AND QUANTITY DISCOUNTS

FREE LOCAL DELIVERY — SAME DAY ● FITTING SERVICE £20.
FAST MAIL ORDER GB 2-3 DAYS — OVERSEAS ON REQUEST.

| | |
|----------------------------------|-----|
| A47 32/343X 470 BCB22 | £37 |
| 470 ESB22/EFB22/ERB22 | £45 |
| A51-161X | £45 |
| A51-220X/192X | £37 |
| 510 JKB22/JEB22/JDB22/ALB22 | £45 |
| A56-120X/123/140/410 | £38 |
| 560 DZB22/HB22/AKB22 | £45 |
| A63-120X | £39 |
| A66-120X A67-120X/140/150/200X | £39 |
| 20AX A56-500X/510X A66-500X/510X | £48 |
| 30AX A56-540X/A66-540X | £48 |

If your tube type is not in stock we can arrange collection - rebuilding + redeliver

PLEASE PHONE BEFORE CALLING

061-799 0854. 24 hour answering service
43 Clarke Crescent, Little Hulton, Worsley, Nr Manchester M28 6XL

SETS & COMPONENTS

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact COLES-HARDING & CO, 103 South Brink, Wisbech, Cambs. 0945 584188. Immediate settlement.

JAPANESE COLOUR TVs. Panasonic, Hitachi, Mitsubishi, Toshiba, Sharp. Fully refurbished. Trade only. J.M. Pearson Television. 0484 863489.

SATELLITE TV. 4GHz-11GHz low noise downconverters, receivers and parts for the instructor. S.A.E. Data Lists: H. COCKS, Cripps Corner, Robertsbridge, Sussex. Tel. 058083-317.

SECOND HAND Colour TV spares and tubes. Most makes. Telephone Southport (0704) 74411. Anytime.

MULTISTANDARD Colour Television. LUXOR VHF/UHF TV/Monitors to most standards, including PAL/L/SECAM/L (UK/French) option. 20", 22" & 26" from £280. ex VAT. PORTATEL CONVERSIONS LTD., 25 Sunbury Cross Centre, Sunbury, Middlesex. Tel. 09327 88972.

GRUNDIG SETS, PANELS, MANUALS. Nordmende and Teleguipment spares, manuals. Ochre Mill. Tel. 0785 814643.

A.B.D. TELEVISIONS

Suppliers of colour and mono televisions to the trade.

Workers and non-workers:

Pye Chelsea, Philips, Pye, GEC, Thorn 8500, 8800, 9000 and 9600, Bush T20 and TT22, ITT 600 series, Japanese, Hitachi, Nat. Pan J.V.C.

Many other modern sets by popular manufacturers.

For quotation and prompt service:

Ring Notts (0602) 864627

UNIT 3+3A,

Meadow Trading Est.

Meadow Lane,

Nottingham NG3 3HQ.

FOR SALE

CRT Regunning Plant:
Comprising of:-

- 2 x Ovens,
 - 2 x Vacuum Pumps and Diffs,
 - 1 x Spot Kicker,
 - 1 x Getter Fireer,
 - 1 x Welding Machine,
 - 1 x Annealing Oven,
 - 1 x Precision Emission Tester,
 - 1 x Let Down Station,
 - 1 x Custom Built Extraction System,
- All gun and glass stock, plus goodwill. Plus many other items.

To be sold as a complete lot,
£6,500.

Contact: Mr Adolpho on
0622 872400

TELEVISION

No other consumer magazine in the country can reach so effectively those readers who are wholly engaged in the television and affiliated electronic industries. They have a need to know of your products and services.

The prepaid rate for semi display setting £6.30 per single column centimetre (minimum 2.5 cms). Classified advertisements 37p per word

SCREENPLAY

Your Friend in the TV Business

NEW YEAR CLEARANCE

26" SOLID STATE 3 ASSORTED ONLY £28.00

JAPANESE 20" ONLY £25.00

MONO'S . . . 1500/1600/MISCELLANEOUS

5 FOR ONLY £19.00

STANDS, AERIALS, ACCESSORIES ETC.

PANELS BY POST


RECONDITIONED AND PRE-CALIBRATED FOR THORN/PHILIPS ETC.

WORKING SETS TO ORDER (UNBEATABLE PRICE)
CHOICE! - WEEKLY DELIVERIES OF DIVERSE STOCK.
PHONE US NOW FOR A STRAIGHT ANSWER.
OPEN 6 DAYS 10-6.30pm/10-5.00pm SAT.

Phone:

Baldock 894905

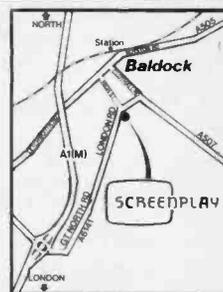SECTION THREE, UNIT FOUR, SERL COMPLEX,
LONDON ROAD, BALDOCK, HERTS.



IRISH TV TRADE

CAN WE BE OF SERVICE TO YOU?

Regular supplies of Quality Colour TVs

LOWEST PRICES

Working Sets from £18

Non-working Sets from £8

FREE DELIVERY ANYWHERE

contact:

J. M. G. Electronics

Omagh, Co. Tyrone,
Northern Ireland.
Omagh (0662) 46032 night
Omagh (0662) 47911 day



Thorn 3000/3500
Thorn 9000
UNIVERSAL
1 year guarantee

TRIPLERS
£4.95 inc. p&p

The UNIVERSAL TRIPLER can be used in most G.E.C., I.T.T., Pye, Rank, Decca & Continental sets.

WING ELECTRONICS

15 Waylands, off Tudor Rd, Hayes End, Middlesex

QUALITY SETS from Cornwall. Workers/non workers. Spares, panels etc. Details: Ring 0726-81-5389.

T.V. SPARES, PANELS
AND MANUALS
PHILIPS · GRUNDIG

TELEVIEW 01-994 5537
194, Acton Lane, London W.4.

UPCONVERTERS. VHF-UHF converter. PC mod. ule. 12V supply required. Very sensitive unit. Suit UK sets abroad. DX etc. £14.95 inc PP. S.A.E. DATA, H. COCKS, Cripps Corner, Robertsbridge, Sussex. Tel. 058083-317.

CANVEY COLOUR TUBES

Unit 3, Charfleets House, Charfleets Industrial Estate, Canvey Island, Essex.

Tel: Canvey Island (0268) 690577

CURRENT PRICE LIST

DELTA TUBE TYPE FROM £27.50 to £31.50

INLINE TUBE TYPE FROM £35.00

MONO TYPES P.O.A.

ALL PRICES EXCLUSIVE OF VAT.

All Tubes Guaranteed for 2 YEARS and Reprocessed to Original Manufacturers Specifications.

SERVICE PAGES

(minimum 12 words), box number 70p extra. All cheques, postal orders etc., to be made payable to Television, and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Dept., Television Room 2612, IPC Magazines Limited, Kings Reach Tower, Stamford Street, London SE1 9LS. (Telephone 01-261 5846).

TUBES

£29.00 INCLUSIVE, REGUNS TWO YEAR GUARANTEE, QUANTITY DISCOUNTS
£14.50 SIX MONTH GUARANTEE SLIGHTLY USED
 A56-120 A56-140 A51-110 A49-191 A47-342 or 343
 A44-270-1 A66-120 A66-140 (410) A67-120 (All 26" add £5)
 No need to spend £5 returning old delta tube.

PROFESSIONAL STICK
DE GAUSSING COILS £19.50
 INCLUSIVE
 FREE DELIVERY

U-VIEW TUBES, 29, Warmsworth Road, Doncaster, Yorkshire DN4 0RP. Tel: 0302 855017.
 Callers ring first, open every day including Sunday

SONY AND HITACHI

All sizes **£66 INCLUSIVE**
 Some in stock send old glass later. Other in-lines from **£30**. 99.9% of tubes we have a new gun for, plus new 16" tubes **£66**. Other in-lines in stock. 56 500-10 51-161 51-570 66-540
 Radio and television servicing books (MacDonalds). New 74/75 **£15**; 76/77, 77/78, 78/79, 79/80, 80/81, 81/82, 82/83, 83/84 **£22.50**. Except tubes **£5** each.

STARLITE ELECTRONICS

NOW MOVED TO:
 WILLOWS FARM,
 A13 RAINHAM, ESSEX.
 Rainham 23225 also
 Hornchurch 50238.

- TV TUBES -
 2 year guarantee
 Most types available
 Japanese including Sony
 Ex-Rental TVs from**£15.00**
 Untested Panels.....**£4.00**

TELEVISION

Trade & Retail supplies of s/h colour & mono TVs. Most makes available, workers or non-workers

SOUTHPARK DISTRIBUTORS

Unit 4 Rubastic Road,
 Brentpark Industrial Estate,
 Southall, Middx. UB2 5LL.
 01-574 4631, Ext 28

COLOUR TV PANELS Fully Tested & Working

| | IF | CDA/ Video | Decoder | LTB | Line Board | Power |
|-------------|-------|---------------|---------|-------|---------------|-------|
| GEC 2040 | 3.50 | 3.50 | 4.00 | 5.00 | - | - |
| OECCA 13/30 | 3.00 | - | 7.00 | 5.00 | - | 4.00 |
| BUSH A823 | 4.00* | - | 10.00* | 5.00* | 2.50 | 4.00 |
| THORN 8/8½ | - | - | 10.00 | 5.00 | - | 5.00 |
| PYE 205 | 3.00 | 3.50 | 5.00 | 10.00 | - | - |
| THORN 3/3½ | 5.00 | 5.00 | 5.00 | 8.00 | - | 10.00 |
| GB | 6.00 | - | 8.00 | 7.00 | 15.00 | 5.00 |

*Please specify prefix A or Z.

Please add 15% VAT to above prices, then add post + packing.
 Post + Packing: 1 panel £1.50; 2 panels £2.25; 3 panels £3.00 etc.

Hybrid panels do not include valves.

Terms cash with order.

Also a vast selection of modern working and non-working TVs at low prices. Please ring for current stock.

GOLCAR T.V. SERVICES (formerly LAVITE LTD.),
 Old C of E School, Church Street, Golcar, Huddersfield. Tel.: 0484 643273
 Callers by appointment only.

EAST ANGLIA SUPPLIES

Fully working colour TVs from £25.00 plus VAT straight from our retail shelves. Most makes are available and small regular orders are welcome. Personal services guaranteed and if we can help you boost your rental or retail trade we would be delighted.

Free delivery available
 (only petrol charged).

Contact John, Dave or Steve at
Barry T.V. Services
 on Cambridge 69215
 or Ely 61462

REBUILT COLOUR TUBES

EXAMPLE PRICES DELTA
 All sizes up to 22" — **£28.00**
 26" From — **£32.00**

All In Line P.I.L. Mono Gaming Machine
 C.R.T.s 560EGB22 56-611-510JKB22

20 AX **£40.00**
 30 AX **£48.00**

Fast U.K. Delivery

Call or Phone:

RE-LIFE T.V. TUBES
 PLANE STREET,
 OLDHAM, LANCS.
 061-665 2668

Wholesalers REG in North & South Wales
 Competitive Prices

COUNTY DURHAMS ONLY WHOLESALE

| | UNTESTED | WORKING |
|-------------|-------------|-------------|
| G8 520 | From £12.00 | From £20.00 |
| G8 550 | From £12.00 | From £30.00 |
| GEC S/S | From £15.00 | From £25.00 |
| All Hybrids | From £12.00 | From £20.00 |
| Jap | From £20.00 | From £30.00 |

All sets sold as working are fully prepared to the highest standards and are ready for retail or rental.

REGUNNED TUBES

| | | |
|-----------------|--------|----------------|
| Up to 22" Delta | £27.00 | 2 yr guarantee |
| Up to 26" Delta | £30.00 | " |
| Pil & Inline | £45.00 | " |

All tubes are regunned to the highest specifications. We are the best because we want our customers to come back.

INTERTEL

Unit 27 Whessoe Road,
 Darlington (0325) 486896
 Co. Durham.

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Television for

insertions. I enclose Cheque/P.O. for £

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd and made payable to Television)

| | | | |
|--|--|--|--|
| | | | |
| | | | |
| | | | |

CAT. HEADING

NAME

ADDRESS

.....

TELEVISION

Classified Advertisement Dept., Room 2612,
 King's Reach Tower, Stamford Street, London
 SE1 9LS. Telephone 01-261 5846.

Rate
 37p per word, minimum 12 words. Box No. 70p
 extra.

N.W. ELECTRONICS

25 YEARS SUPPLYING THE TRADE

Bonanza Clearance!!! New Year Prices...

100's of good class HP Repos and
Ex Rental Colour TV's reduced to
ROCK BOTTOM PRICES!

| | | | |
|---------------------------|---------|-------|---------|
| Bush T20 (Excellent Cabs) | was £60 | | NOW £40 |
| Bush 718 P.I.L. Tube | was £30 | | NOW £25 |
| Bush 2 Chip Decoders | was £15 | | NOW £8 |
| Philips G8 | was £28 | | NOW £23 |
| Philips G11 | was £70 | | NOW £55 |
| GEC 2010 | was £25 | | NOW £20 |
| Thorn 3500 | was £12 | | NOW £8 |



Hybrids £5 all makes!  Many more inc Pye KT30, Ferguson TX etc.

Video

VHS – Sharp 7300, 8300, 9300. Ferguson 3V28, 3V22.
Sony Beta.

Mono TV's £1 each (lots of 25)

Thorn 1500 £4, 1600 £12. Discount for Quantity (like new).
No cheques.

White goods

Hoover Twins from £6. Hotpoint 1460 from £10.
Autos all makes from £10.

SPARES! SPARES! TV PANELS

| | I.F. | DECODER | LINE O/P | POWER | CONVERG. | VIDEO | FRAME T3 |
|------------------|-------|---------|----------|-------|----------|-------|----------|
| BUSH 2 CHIP | 3.00 | 8.00 | 6.00 | 3.00 | 3.00 | — | 5.00 |
| 3000/3500 | 2.00 | 4.00 | 8.00 | 8.00 | 5.00 | 5.00 | 6.00 |
| G8 | 5.00 | 7.00 | 14.00 | 8.00 | 5.00 | — | 5.00 |
| with sound panel | | | | | | | |
| GEC 2110 | 10.00 | 5.00 | 12.00 | 6.00 | 5.00 | 5.00 | 5.00 |
| BUSH 718 | 8.00 | 15.00 | 25.00 | 3.00 | 5.00 | — | 15.00 |
| BUSH T20 | 8.00 | 15.00 | 20.00 | 20.00 | 5.00 | — | 15.00 |

P&P 1 panel £1.50, 2 panels £2.00, 3 panels £2.50 etc. Quick Despatch – C.W.O. please.

All prices plus VAT

CASH ONLY – NO CHEQUES
DELIVERY CAN BE

ARRANGED TRADE ONLY

(0274) 688458 OPEN 6 DAYS A WEEK

Unit 12, Wharfedale Road
M606 Euroway Estate
Bradford

OPEN MON-SAT 9-5.30
Don't forget! We are open
all day Saturday!

TOSHIBA V9640B VIDEO, mint cond. £190.00. Scotch 3m 832 photocopier. VGC £190.00. 01-897 2602.



- * Britain's most reliable source of quality TVs.
- * Hundreds of working polished TVs.
- * GEC Starline
- * Decca 80
- * Decca 88
- * Decca 100
- * Pye G11
- * Thorn 8800
- * Pye 222 Series

All working and polished. These are not from major companies. A lot are from hotels and have had very little use. Excellent reliable sets for rental.

Krystal Marketing Ltd,
Breedon Cross
Storage,
Dale Road, Selly Oak,
Birmingham B29 6AQ.

Phone 021-471 3023
Telex 335540-G
Ask for Les

WIZARD DISTRIBUTORS TV & VIDEO SPARES

Visit our trade counter and see the huge range of components inc. tubes and video heads. Only minutes from the town centre and motorway routes. Fast friendly service and technical assistance available. Come in and see our trade counter special offers.

Open Monday to Friday 9 am to 4.45 pm
Trade Only

EMPRESS STREET WORKS

Empress Street

Manchester M16 9EN

Tel: 061-872-5438, 061-848-0060

WOODSDALE COMPONENTS RANK BUSH MURPHY TRANSFORMERS

Line Output

Z718 (T703A, T706A)

New (Complete) £20.50

Less Focus Module and

Rectifier £10.50

T20, T22 (T705A) £11.00

T26 (T705B) £11.00

Switch Mode

T114A/B £8.00

Genuine RBM Units.

AERIALS

UHF Aerials P & C Wideband 4 Bay

Bowtie (12.5 dB) £20.00

Above with built-in Broadband amp.

(27dB) plus stabilised power

supply £45.00

Prompt Postal Service P&P Paid.

Add 15% VAT to all prices.

DISCOUNT for QUANTITIES.

34 Field End Road, Eastcote,

Pinner, Middlesex. HA5-2QT.

Tel: 01-868 5580.

N. Skehan

Agents Office. Callers by appointment only.

COLOUR BAR GENERATOR

Pal Colour Generator with 11 patterns plus sound. Grey scale, Colour Bars, Red, Green & Blue Raster, Crosshatch, Dots, Chequer Board, Black Raster, White Raster, Half Black & White, Mains Powered. £75.90

OUTPUTS PROVIDED

UHF OUTPUT
VIDEO OUTPUT
SOUND OUTPUT
LINE PULSE
FIELD PULSE



Line Output Transformer Tester £11.50

B/W Generator, Crosshatch, Peak White, Dots, Half

Black & White and Grey Scale £18.50

In Circuit Transistor Tester £14.25

Capacitance Meter measures 10pF to 1µF complete

with moving coil meter £14.75

Car Alarms £12.50

S.A.E. for details. - Prices include P&P & VAT.

C.M.J. ELECTRONICS

Unit 8, 16 Union Mill Street, Horseley Fields,

Wolverhampton WV1 3DW.

Tel: (0902) 871563

Trent Tubes

31 RADCLIFFE ROAD,

WEST BRIDGFORD, NOTTINGHAM

THE QUALITY REBUILDER

PHONE: (0602) 813329

ALL TUBES CARRY A TWO YEAR GUARANTEE

EXTENDABLE TO FOUR YEARS

All Sizes of Standard Deltas

ONLY £27.50 (A56-120 - A66-120 etc.)

A51-161 - A51-163 £39.00

A55-66 500/510 (20 AX) £42.00

560 DZB 22 £43.00 - 560 EGB 22-510 VLB 22 £45.00

1000's more available. VDUs, MONOs, Industrial etc.

WE NOW REBUILD SONY TUBES

Phone for details

STOCKISTS

Peterborough: H. DONNOR Derby: VTA WORKSHOPS

0733 71809 0332 369132

TECHNICAL ADVICE SERVICE

All prices + VAT & Exchange

Suppliers to Broadcasting Authorities

Quantity Discounts

T.V PANELS

REPAIR EXCHANGE SALES SERVICE

PRICES FOR REP. EXC. AS FOLLOWS

| Chassis | IF | Decoder | Line Scan | Power Supply | Frame |
|-------------|----|---------|-----------|--------------|-------|
| Philips G11 | 18 | 16 | 20 | 18 | 16 |
| Bush T20 | X | 12 | 16 | 15 | 12 |
| Bush T26 | X | 16 | 18 | 15 | X |
| Bush 718 | X | 12 | 18 | X | 12 |

All panels are repaired and aligned according to rank std.

Ring for prices to buy panels. Prices shown inclusive of postage, etc.

All panels guaranteed for 3 months.

T. K. PANELS SERVICE

31 Bronte Paths, Stevenage (0438) 61567

TELEVISION

GOOD QUALITY TRADE
TVs COLOUR OR MONO
SUITABLE FOR SALE OR
RE-RENT, WIDE CHOICE
OF MAKES AND
MODELS

GENERAL
FACTORS

UNION STREET
DONCASTER
DN1 3AE

TEL (0302)
68416

GOOD MOTORWAY ACCESS

EX-RENTALS TELEVISIONS IN BULK

Most makes including late models.
MONITEC 0299 400233.

WORKING CTV's

The Best & Cheapest in Lancashire

I.E. Decca 18" to 26" £24.00
GEC 20" to 26" £30.00
Philips G8 22" to 26" £25.00
Bush 20" to 26" 2 chip £18.50

All sets are tested & working

Many more makes & types available.
Working mono's only £3.50. Non
workers available.

Phone: John Powney
at Kirkham, near Preston
(0772) 683392.

TRADE COLOUR TVs ALWAYS 200 IN STOCK

Colour from £5.00 Mono £2.00
Tested colour tubes from £5.00 plus p+p

BRAND NEW VIDEOS

V2022 and V2023

VHS and BETA

Just in

20" + 22" GEC

Boxed with stand £85.00

ALL STOCK CHANGES WEEKLY

(0934) 514047/512792/27560

P&R SUPPLIES, Unit 5,

Worle Industrial Estate,

Weston-Super-Mare. Exit 21 M5.

TELEVISION TUNER REPAIRS

BRITISH, EUROPEAN
JAPANESE ETC.

ELC 1043/05 TUNERS
AS NEW £4.60 inc.

MEN-TU ELECTRONICS LTD.
SALTERS LANE,
FAREHAM, HANTS.

Tel: 0329-235116

VIDEO

ARE YOU A TV ENGINEER WHO WANTS
TO KNOW ABOUT VIDEO RECORDERS?

THEN YOU NEED

"DOMESTIC VIDEO CASSETTE
RECORDERS A SERVICING GUIDE"
by S. R. BEECHING

Available for only £15.50 inc. p&p

From: NEWARK VIDEO CENTRE,

108 London Rd., Balderton, Newark, Notts.

Tel: 0636 71475 ACCESS OR VISA

When replying to Classified Advertisements please ensure:

- (A) That you have clearly stated your requirements.
- (B) That you have enclosed the right remittance.
- (C) That your name and address is written in block capitals, and
- (D) That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

AERIALS

EVERYTHING NECESSARY for multi-outlet systems. Filters, diplexers, amplifiers, etc. Use trade gear and save pounds. Catalogue 50p (refundable). Professional system planning/advise £5.00 (refundable). Quick queries free. Wrights Aerials, 43 Greavesike Lane, Micklebring, Rotherham.

CLEARVIEW AERIALS

Clearview have pleasure in announcing a full and comprehensive range of signal amplification equipment. For example: low noise electronically remote controlled masthead pre-amp 1.6db noise. CH. 17-69. Set side amplifiers, distribution amplifiers, notch filters 4 in 1 or 2 in 1 etc. Combiners for 2 UHF aerials 3db gain or 4 6db gain. Trade and retail.

Send large SAE for our comprehensive catalogue

CLEARVIEW AERIALS,
173 Kings Road,
Kingston Upon Thames, Surrey.

AERIAL BOOSTERS

B45H/G-UHF TV next to the set fitting, gain about 20db, PP3 battery or 8V to 14V/working. Price £8.70. P&P 30p.

UHF TV BOOSTER MODULE. PCB ready made up to cover the complete UHF TV band. Gain 10db, noise 19db. 8V to 14V/W. Price £2.50. P&P 30p.

SET/TOP AERIAL and matching aerial booster (trebles the gain). Price £8.70. P&P 50p.
SINCLAIR SPECTRUM COMPUTER. DC on/off unit, can be fitted in seconds. Saves unplugging the DC socket. Price £2.70. P&P 30p.

ELECTRONIC MAILORDER,
62 Bridge Street, Ramsbottom,
Lancashire, BL0 9AG.
Tel: Ramsbottom (070 682) 3036.
S.A.E. for leaflets. Access/Visa Welcome.

BOOKS AND PUBLICATIONS

FULL SIZE TOP QUALITY service sheets £2.50 + l.s.a.e. CTV/Music Centres £3.50 + l.s.a.e. Repair data almost any named TV/Video £10.50 inc. circuits. L.s.a.e. brings any quite free magazine/pricelists. TIST, 76 Churches, Larkhall, Lanarkshire. Tel. 0698 883334.

"RADIO AND TELEVISION SERVICING" books, new editions for the last 6 years always in stock. Prices on request. BELLS TELEVISION SERVICES, 190 Kings Road, Harrogate, N. Yorkshire. Tel. 0423 55885.

RADIO AND TELEVISION SERVICING BOOKS. New 74/75 £15. 76/77, 77/78, 78/79, 79/80, 80/81, 81/82, 82/83, 83/84 £22.50 each. Free delivery. U-VIEW, 29, Warmsworth Road, Doncaster. 0302. 855017. Callers ring first.

FOR SALE

TRADE ONLY

Closing down warehouse. All stocks to be cleared.

TV Components, Audio, Wire, Electrical, Racking, Etc.

Offers are invited for bulk purchase of stocks listed above.

No reasonable offer refused.

Send for catalogue to:

ELECTRONIC SUPPLIES

18 Leuca Road, Walthamstow E17 7LG or
Telephone: 01-521 3912, after 6.30 evening.

GUARANTEED 90% WORKING

100's of GEC 2110/2111 stripped to spares

| Decoder | Line Output | Power | Convergence | Tram-Time | Tripler |
|--------------|-------------|-------|-------------|-----------|---------|
| 13.00 single | £4.00 | £2.50 | £2.50 | £3.00 | £2.50 |
| combined | | | | | |

Other types e.g. Bush, G8, Thorn 8500, Pye, GEC Hybrid
all non-working/complete.

| Decoder | Line | Power | Conver- | Frame | IF | Tripler |
|---------|-------|-------|---------|-------|-------|---------|
| | | | gence | | | |
| Bush | £5.00 | £5.00 | £3.00 | £3.00 | £3.00 | £2.50 |
| G8 | £3.00 | £5.00 | £4.00 | £3.00 | £5.00 | £2.50 |
| 3500 | £3.00 | £4.00 | £4.00 | £3.00 | £2.00 | £2.50 |
| Thorn | | | | | | |
| GEC | £3.00 | £5.00 | £4.00 | £2.00 | £2.00 | £2.50 |
| Pye | £3.00 | £5.00 | £5.00 | £2.00 | £2.00 | £2.50 |

SABACO, Elastic Yarns Building,
Derby Road, Sandiacre, Notts.
Tel. (0602) 397555

FOR SALE CONTINUED

B.R.C. 2,000 TV, good picture. Several spare boards. Manual for the same. Also Philips N1501 V.C.R. 2 tapes. £100 the lot. Buyer collects. TV Box 192.

PHILIPS VR2020 video heads £45. Philips LVC150 video tape for N1500/N1700 etc. £13. All items new & unused post free. Mr. McHUGH, 16 Copperperkins Road, Hednesford, Staffs. WS12 5NW.



Sabaco

For a great deal!

VAN LOAD DIRECT FROM SOURCES

Remember all sets cleaned and soak tested. Most makes available, any quantity e.g. GEC, Bush, Decca, ITT, Pye G11, T22, 9000, 9800 etc. Mixed sizes.

WORKING SETS FROM £20 upwards. e.g. GEC 2110 £25 min of 6 and etc. Bush non workers complete in quantity £8.00 each. Black face deccas non workers complete in quantities at £12.00 each.

COMPLETE NON-WORKERS from £10 in quantities.

Black/White in batches of 10 at £1.50.

SPECIAL OFFER!

26" G8/3500/HYBRIDS


QUANTITIES OF 10 @ £5 each

SPARE PARTS AVAILABLE AT COMPETITIVE PRICES.

PLEASE SEE SEPT/OCT ISSUES.

N.B. Add 30p extra per panel.

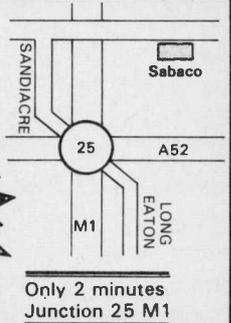ALL PRICES SUBJECT TO VAT & AVAILABILITY.



Only 2 minutes
Junction 25 M1

Sabaco
Elastic Yarns Building,
Derby Road, Sandiacre,
Nottingham.

Open 6 days a week
9.30 a.m. — 6.00 p.m.

Telephone: (0602) 397555

SERVICE SHEETS

TELEVISION SERVICE SHEET SPECIALISTS

Thousands of British, European and Japanese models in stock.

Colour £2.00 Mono £1.50

Manual prices on request.

All our prices include post and packing costs.

Send stamped envelope for free catalogue and enquiries.

SANDHURST TV SERVICES (MAIL ORDER)

49C Yorktown Road, Sandhurst, Camberley, Surrey GU17 7AG

Alba, Cossor, Baird, GEC, 30,000 SERVICE SHEETS IN STOCK ALL AT £3.00 + SAE
Defiant, Echo, Ferguson, Philips etc. etc. ALSO COLOUR MANUALS AVAILABLE AT £6.00 EACH

TV Sheets, Black and White, also Radiograms, Record Players, Music Centres. Japanese models in stock. Circuit diagrams only. Also Tape Recorders etc., etc. Please forward s.a.e. Send cheque or P.O.

C. CARANNA, 71 BEAUFORT PARK, LONDON NW11 6BX.

TECHNICAL INFO SERVICES - 76 Church St - Larkhall - Lanarks

(By return of post service in most cases.)

Sole suppliers of the Unique Comprehensive T.V. Practical Course and The Complete Radio Repair and Servicing Course ONLY £9.50 each.

We stock every published service sheet plus produce more ourselves. All service sheets are top quality, full-size sheets supplied in complete sets. £3.50 + l.s.a.e. for CTV or Music Centres - £2.50 + l.s.a.e. any others.

WORLD'S LARGEST COLLECTION SERVICE MANUALS

Can be seen at our premises any evening 4-6pm. Manuals from 1930 to the latest issue. Col + Mono TVs, Videos, Audio, Com + Test Eqpt. in stock for immediate despatch - Over 400 dif. CTV - Over 200 dif video!

Sample CTV prices: G8 or Pye 697 or AB23 or Autovox early (poor copy) at £7.50 each

Most manuals are unobtainable anywhere else.

WORLD'S BIGGEST PUBLISHER OF TV/VIDEO REPAIR MANUALS

| | |
|--|-----|
| British CTV Integrated Repair System (3/5) | £85 |
| Foreign CTV Integrated Repair System (2/4) | £80 |
| Mono TV Integrated Repair System (2/6) | £70 |
| Video Integrated Repair System (2/10) | £49 |

First figure for giant collections of circuits/layouts in binders, 2nd figure for number of repair manuals. Other items not shown.

The Complete Integrated TV Repair System - covering TVs colour & mono, British & foreign, circuits, layouts, repair data plus much servicing data. Around £300-worth ONLY £220

Free 50p magazine with pricelists, etc. to every query or order - please enclose s.a.e.

FOR FAST QUOTES - PHONE 0698 883334

SERVICE PAGES SERVICE PAGES

PLEASE MENTION TELEVISION WHEN REPLYING TO ADVERTISEMENTS.

SERVICE PAGES SERVICE PAGES

BELL'S TELEVISION SERVICES for service sheets on Radio, TV, etc. £1.50 plus S.A.E. Service manuals on colour TV and Video Recorders, prices on request. S.A.E. with enquiries to B.T.S., 190 Kings Road Harrogate, N. Yorkshire. Tel. (0423) 55885.

SITUATIONS VACANT

WANTED EXP TV ENGINEER to work in Northern Ireland starting February 1985 to service ex-rental televisions. Must have good exp on most sets including British and Japanese. Good wages and accommodation. Write to TV Box No. 190.

HONEYWELL NEDD DYNAMIC

Experienced Electronic Engineers

to join their highly skilled team responsible for troubleshooting high technology videographic systems. Our benefits package is most attractive, including company car and five weeks holiday. For further details contact:

Richard Gould,
Honeywell Control Systems Ltd.,
Honeywell House, Charles Square,
Bracknell, Berks RG12 1EB.
PLEASE QUOTE REF. T/56/PCD.

WANTED

WANTED: Quantity Pye Philips G11. Televisions also Ferguson videos. Telephone 04024 58513.

WANTED. We will clear any amount of colour sets from small Rental Companies, Hotels, etc. Please phone P & R Domestic Electrical Clearance Supplies, Weston Super Mare (0934) 514047.

To Advertise
on these
pages ring
Mandi
01-261 5846

MISCELLANEOUS

BURGLAR ALARM EQUIPMENT. Latest discount catalogue out now. Phone C.W.A.S. ALARM 0274 731532.

The Theory and Practice of PAL Colour Television in three important Video Cassette Programmes

Part 1.

The Colour Signal

Part 2.

The Receiver Decoder

Part 3.

Receiver Installation

VHS★★★V2000★★★

BETAMAX★★★UMATIC

For full details telephone

0253 725499 (Day)

0253 712769 (Night)

Or send for precise details

FLINTDOWN CHANNEL 5
339 CLIFTON DRIVE SOUTH,
LYTHAM ST ANNES FY8 1LP
(enclosing this advert)

NAME

ADDRESS

..... TEL:.....

If an
advertisement
is wrong
we're here to
put it right.

If you see an advertisement in the press, in print, on posters or in the cinema which you find unacceptable, write to us at the address below.

The Advertising 
Standards Authority.

ASA Ltd, Dept 3
Brook House, Torrington Place,
London WC1E 7HN

IRISH T.V. DEALERS

Large selection of fully reconditioned precision in-line UHF-VHF colour T.V.s at keen prices

Also in stock: Dual Standard Beta & VHS Video Recorders

Quantity discount. Delivery arranged.

(Limited amount of spare panels, components, button units, etc.)

**SPECIALISTS IN
OVERSEAS ORDERS**

T.V. TRADE SALES

EDI House, Kylemore Park West,
Ballyfermot, Dublin 10.

Tel: 264139 ext. 11.

(Open 10 a.m.-5.30 p.m.)

COLOUR TELEVISIONS

THORN 9000, 9200, 9600 Remote Control

PYE 420/450, G11

MANY OTHER TYPES

Working panels and tubes available.

REBUILT TUBES

Delta - In Line - PIL.

SOUTHBRIDGE TV CENTRE

120, Selhurst Rd., London, S.E.25.

Tel: 01-771 3535.

EMCO - EUROSonic - GRUNDIG - TELETON + ALL BRITISH MAKES
ETC. ETC. ● ALL SPARES READILY AVAILABLE ●

IMMEDIATE CREDIT AVAILABLE — TRADE ONLY

If you are a trader simply phone for the part you require and we will send it — no quibble — no hold up for status check. Satisfy us over the phone that you are a trader and we will supply almost any TV component by return "off the shelf", e.g. LOPTZ — EHT trays — droppers — OSC coils — switches — cans — smoothers — I.C.'s, etc. etc.

**YOU CAN BE 95% SURE WE CAN SUPPLY ANY
TV COMPONENT BY RETURN
IF YOU NEED SPARES FAST — RING NOW!**

ACCESS AND BARCLAYCARD ACCEPTED.

Applies to U.K. only.

TELEPART (W'TON)

32 TEMPLE STREET,
WOLVERHAMPTON (0902) 773122

| 20AX Line lin coil 50p | | G11 470M/250V SP £1 each | BD 517 30p | PHILIPS DIY HOME SECURITY ALARMS KITS | | 8 SEG LED Display with driver I.C. LM1017 50p | |
|---|--|--|---|---|--|---|--|
| GEC switch mode trans 20AX | | Min 12 volt Relays 75p | BD 519 30p | Send for details. Prices £54 to £112. | | 20AX GEC Split Diode lead £1.00 | |
| ITT CVC20 etc mains switch 60p | | Y 933 5p | BD 534 30p | 10 Mixed TV & radio speakers £4 | VIEW DATA PANELS NEW 19 I.C. £5 | GEC Dynamic 20AX Convergence C2233H-R223GH £3.00 | |
| ITT 2,800 mains remote switch 50p | | Y 969 50p | BD 595 30p | 2x Hi-Fi Philips car tune up tweeter EN8320 £10 | Philips GP422.4CH (£40 cost) £6 | Mullard 12.5V/170 Mc/s 45 watt BLW60 £5.00 | |
| 2110 GEC Power Panel £8.00 | | R 1038 40p | BD 610 30p | ITT CVC45 8 way resistor unit for w/cap £3 | Stereo-Dynamic Cartridge | BLW60C £5.00 | |
| Line o/p frame panels GEC 20AX £10.00 | | R 1039 40p | BD 646 30p | 4700/10v x 10 50p | 12 Volt Aerial Changer over Relays 144 Mc/s 45 watts 50p | Mullard Broadband R.F. power modules VHF. BGY33 £15 | |
| GEC 20 AX Transductor £1.00 | | R 2009 80p | BD 678 30p | 68/16 x 10 50p | GEC Hitachi V/Cap tuner, after 1979 Series £8 | UHF. BCY22E £5 | |
| All diodes at 10p or less in this list 20 of one type £1.00 | | R 2010b £1 | BD 681 30p | 150/16 x 10 50p | 6 Push Button Unit for GEC 2100 Series Replacement for Touch Button Unit £12 | £5 PT4236C | |
| OA 47 8p | | R 2029 50p | Voltage Regulators +5V/UA78P05SC 30p | 220/25 x 10 50p | | £5 PT8706C | |
| OA 90 8p | | R 2310 60p | -5V/LM79M05CP 25p | 1/250 x 10 50p | | £5 PT9783 | |
| IN 60 5p | | R 2305 50p | +8V/79M08c 30p | G8 Speaker £1 | | | |
| IN 541 5p | | R 2306 50p | +10v/78LA10 20p | 8000/30v 50p | | | |
| IN 914 3p | | R 2322/2323 pair 15p | LM 337 30p | 470/40v x 10 £1 | | | |
| IN 2069a 10p | | R 2396 50p | LM 342/18 30p | 22/100v x 10 £1 | | | |
| IN 2070 10p | | R 2461 80p | LM 340T 5.0 50p | 100/350v 70p | | | |
| IN 4001 3p | | R 2030 50p | +12V/LM 340T12 50p | 400/350v 70p | | | |
| IN 4002 3p | | R 2443=BD124 40p | +15V/78M15 15p | 47/500v 25p | | | |
| IN 4003 4p | | R 2737 40p | +18V/MC78M18 20p | 1/600v 25p | | | |
| IN 4004 4p | | R 2738=TTP41 30p | +24V/78M24 30p | .022/1kv 10p | | | |
| IN 4005 4p | | R 2739=TTP41c 40p | MC 7724cp 40p | | | | |
| IN 4006 4p | | R 3129=TTP47 40p | MC 7824 40p | | | | |
| IN 4007 5p | | S 2008b 80p | TIS 90 10p | | | | |
| IN 4148x40 £1 | | BU 105/04 80p | TIS 91 20p | | | | |
| IN 4448x40 £1 | | BU 108 £1 | TIS 92 20p | | | | |
| IN 4722 10p | | BU 124 50p | TIS 93 20p | | | | |
| IN 4751 10p | | BU 126 80p | U 19885 40p | | | | |
| IN 5235 10p | | BU 180a 65p | U 3832 15p | | | | |
| IN 5254 10p | | BU 204 70p | U 3845 15p | | | | |
| IN 5349 10p | | BU 205 £1 | MR 508 10p | | | | |
| IN 5392 10p | | BU 206 £1 | MR 501 10p | | | | |
| IN 5928B 10p | | BU 207 £1 | MR 502 10p | | | | |
| IAV 30 10p | | BU 208 80p | BCW 71R 30p | | | | |
| IM 72Z55 10p | | BU 208 on heat sink £1.10 | BYF 1202 10p | | | | |
| IR 106a 20p | | BU 208D £1 | BYF 1204 10p | | | | |
| IR 3051 10p | | BU 222 £1 | BYF 3126 40p | | | | |
| IS 164 10p | | BU 326 £1 | BYF 3214 40p | | | | |
| IS 921 10p | | BU 407 60p | BYX 10 6p | | | | |
| IS 3011a 10p | | BU 426V 60p | BYX 36/600 35p | | | | |
| IS 3072a 10p | | BU 500 £1.10 | BYX 38/300 25p | | | | |
| IS 5024a 50p | | BU 508A £1.20 | BYX 49/600R 75p | | | | |
| IS 5030 50p | | BU 526 £1 | BYX 55/350 10p | | | | |
| ITT 921 10p | | BU 807 £1 | BYX 55/600 (Bead) 10p | | | | |
| ITT 923 10p | | BUX 84 50p | BYX 71/300 20p | | | | |
| ITT 1075 10p | | BUW 84 30p | BYX 71/600 50p | | | | |
| ITT 2001 10p | | BUY 71 £1 | BYX 72/300 20p | | | | |
| ITT 2002 10p | | TIC 106a 30p | BYX 36/600 50p | | | | |
| ITT 4150 10p | | TIC 116m 40p | BYX 95B 10p | | | | |
| Rank Panels | | TIC 116n/Y 1003 35p | BVY 95C 12p | | | | |
| Z904 Line £10 | | TIC 126N 40p | BYZ 106 10p | | | | |
| Z905B Decoder £10 | | TIC 206m 30p | BPW 41 15p | | | | |
| Z736 Tuner I.F. £10 | | TIC 225S 40p | BYW 56 2A/1000V G11 8p | | | | |
| A805 Conv. £2 | | TIC 226E 40p | BZU 15/24 54p | | | | |
| T136A Scan Drive £10 | | TIC 226m 30p | BZY 93c75 50p | | | | |
| Z780 Line O/P £10 | | TIC 236m 30p | BZV 15/18 30p | | | | |
| Z968 | | TICV 106D (T092 case 2A/400V) 10p | BZV 15/30 30p | | | | |
| AA 113 10p | | TIP 29 20p | BZW 706v2 10p | | | | |
| AA 119 8p | | TIP 30 35p | BZX 79.3v 10p | | | | |
| AA 144 10p | | TIP 30A 35p | Bush thyristor RCA 76122 £1 | | | | |
| BA 102c 10p | | TIP 30B 40p | ITT computer bookset 2020 £2 | | | | |
| BA 157 8p | | TIP 30C 45p | G8 20 turn 100K pot 35p | | | | |
| BA 159 8p | | TIP 31 30p | Transformer 240v/20v-500Ma 75p | | | | |
| BA 173 8p | | TIP 32 25p | Viewdata torridals £6 | | | | |
| BA 182 8p | | TIP 33B 50p | CVC 20 tube base £2 | | | | |
| BA 201 8p | | TIP 33C 70p | Tube Base Rank & G11 £1.20 | | | | |
| BA 202 8p | | TIP 34A 50p | Sankyo tape motor 75p | | | | |
| BA 243 8p | | TIP 34B 60p | Swiss made 250ppm/240V motor very small 75p | | | | |
| BA 248 8p | | TIP 34C 70p | Mono scan coil 110" small neck £1.50 | | | | |
| BA 316 5p | | TIP 35B 50p | Infra red led LD57CA 15p | | | | |
| BAV 10 10p | | TIP 35C 70p | Mono scan coil £3 | | | | |
| BAV 21 10p | | TIP 35D 80p | G 8 transductor £1.25 | | | | |
| BAW 21 10p | | TIP 36 50p | AT 4041/41 transductor £1 | | | | |
| BB 103 10p | | TIP 36C 70p | 2K5 Lin pot with 40mm spindle 20p | | | | |
| BB 105A x 12 £1 | | TIP 41B 70p | 1982 Hitachi Ae isolator 50p | | | | |
| BB 105B x 12 £1 | | TIP 41D 70p | Mullard FM decoder 1401 £1 | | | | |
| BB 105G x 12 £1 | | TIP 42/BRC 6109 30p | Philips service pack, flat films, 57 condensers 56nF-2.2uf £2 | | | | |
| BB 121a 10p | | TIP 49 30p | VHF 3 Transistor rotary tuner DX-TV £1 | | | | |
| BRC 83c13 10p | | TIP 57 30p | 15K-20 turn pots 20p | | | | |
| BZX 46c22 15p | | TIP 100 30p | Thorn panel 6x100 pot + changeover switch (Irish) 50p | | | | |
| BZX 61 9-1 6p | | TIP 102 30p | Battery converter TA 75 for colour TV. 12/24v Thorn 3787 £6 | | | | |
| BZX 61c110 6p | | TIP 112 30p | Thorn 3500 2A cut out 75p | | | | |
| BZX 61c20 10p | | TIP 115 50p | Stereo GEC amp 20 watt + pre-amp with 4 pots + mains power unit with circuit £6 | | | | |
| BZX 61c30 10p | | TIP 117 30p | | | | | |
| BZX 61c220 10p | | TIP 120 35p | | | | | |
| BZX 70c2 8p | | TIP 125 35p | | | | | |
| BZX 70c12 20p | | TIP 130 30p | | | | | |
| BZX 70c33 8p | | TIP 131 25p | | | | | |
| BZX 79c3v9, 4v7, 5v1, 5v6, 6v2, 6v8, 7v5, 11, 12, 30, 47 10p each | | TIP 136 30p | | | | | |
| BZX 83c4v3, 5v6, 8v2, 12, 13, 24, 27, 33 10p each | | TIP 140 50p | | | | | |
| BZX 84c6v8 x 10 30p | | TIP 147 50p | | | | | |
| BZX 85c8v2 10p | | TIP 640 50p | | | | | |
| BZX 88c1v7, 3v9, 4v3, 6v2, 8v2, 12 10p each | | TIP 2955 35p | | | | | |
| 1A/1600V 10p | | T 6032 30p | | | | | |
| 2 amp bridge rec. wire end 15p | | T 6036 40p | | | | | |
| CV 8617 10p | | T 6040 40p | | | | | |
| Y 716 10p | | T 6047 40p | | | | | |
| Y 729 30p | | T 6049 40p | | | | | |
| Y 730 10p | | T 6051 40p | | | | | |
| Y 827: 6A/1KV 20p | | T 6052 40p | | | | | |
| Y 860 30p | | T 9004 40p | | | | | |
| | | T 9005 40p | | | | | |
| | | ZTX 102c 10p | | | | | |
| | | ZTX 107 10p | | | | | |
| | | ZTX 108c 10p | | | | | |
| | | ZTX 109k 5p | | | | | |
| | | ZTX 213 5p | | | | | |
| | | ZTX 341 10p | | | | | |
| | | ZTX 342 10p | | | | | |
| | | ZTX 384 10p | | | | | |
| | | ZTX 451 10p | | | | | |
| | | ZTX 550 10p | | | | | |
| | | MJ 2253 60p | | | | | |
| | | MJE 3040 60p | | | | | |
| | | MJE 2209 10p | | | | | |
| | | SP 8385 50p | | | | | |
| | | SAB 3205 £1.00 | | | | | |
| | | SAB 4209 £1.00 | | | | | |
| | | SPECIAL OFFER CVC 21 Chassis complete £35 | | | | | |
| | | Computer Transformer 20v/2.25A; 20v/1.5A; 17/1.5A; 19/1.5A; 28/0.5A £3 | | | | | |
| | | BD 517 30p | | | | | |
| | | BD 519 30p | | | | | |
| | | BD 534 30p | | | | | |
| | | BD 595 30p | | | | | |
| | | BD 610 30p | | | | | |
| | | BD 646 30p | | | | | |
| | | BD 678 30p | | | | | |
| | | BD 681 30p | | | | | |
| | | Voltage Regulators +5V/UA78P05SC 30p | | | | | |
| | | -5V/LM79M05CP 25p | | | | | |
| | | +8V/79M08c 30p | | | | | |
| | | +10v/78LA10 20p | | | | | |
| | | LM 337 30p | | | | | |
| | | LM 342/18 30p | | | | | |
| | | LM 340T 5.0 50p | | | | | |
| | | +12V/LM 340T12 50p | | | | | |
| | | +15V/78M15 15p | | | | | |
| | | +18V/MC78M18 20p | | | | | |
| | | +24V/78M24 30p | | | | | |
| | | MC 7724cp 40p | | | | | |
| | | MC 7824 40p | | | | | |
| | | TIS 90 10p | | | | | |
| | | TIS 91 20p | | | | | |
| | | TIS 92 20p | | | | | |
| | | TIS 93 20p | | | | | |
| | | U 19885 40p | | | | | |
| | | U 3832 15p | | | | | |
| | | U 3845 15p | | | | | |
| | | MR 508 10p | | | | | |
| | | MR 501 10p | | | | | |
| | | MR 502 10p | | | | | |
| | | BCW 71R 30p | | | | | |
| | | BYF 1202 10p | | | | | |
| | | BYF 1204 10p | | | | | |
| | | BYF 3126 40p | | | | | |
| | | BYF 3214 40p | | | | | |
| | | BYX 10 6p | | | | | |
| | | BYX 36/600 35p | | | | | |
| | | BYX 38/300 25p | | | | | |
| | | BYX 49/600R 75p | | | | | |
| | | BYX 55/350 10p | | | | | |
| | | BYX 55/600 (Bead) 10p | | | | | |
| | | BYX 71/300 20p | | | | | |
| | | BYX 71/600 50p | | | | | |
| | | BYX 72/300 20p | | | | | |
| | | BYX 36/600 50p | | | | | |
| | | BYX 95B 10p | | | | | |
| | | BVY 95C 12p | | | | | |
| | | BYZ 106 10p | | | | | |
| | | BPW 41 15p | | | | | |
| | | BYW 56 2A/1000V G11 8p | | | | | |
| | | BZU 15/24 54p | | | | </ | |

SENDZ COMPONENTS

TO ORDER SEE BACK PAGE

| | | | | | | | | | | | |
|--|--|---|--|---|--|--|--|---|--|--|--|
| Thorn Spares 9000 Frame panel £8 9000 Cyclops panel £1.50 8000/8500 timebase panel £8 8800 convergence panel £6 8500 convergence panel £6 4000 Chroma £20 4000 Power supply £3 1600 Mains lead, switch 3500 6 push button + cable form £1.50 T605 1vNPN T066 80v/6A 10p 9000 Sound output panel £1 3500 Focus unit £1.50 3500 Mains Trans £4 3500 2amp thermal cutout 75p 3500 1F panel £2 3500 Frame panel £3 3500 Line panel £3 3500 A1 Diode 20p Export 3500 IF panel £2 1C board with set of SN74LS £1 4000 Tube base £4 3500 A1 pots 50p Beam limiter panel £1.50 3500 Power panel with Y969 £1 3 Way regulated adaptor 240V 6V/ 7.5/9V/300mA £3.50 Rank/Toshiba preh unit 0354 £9.50 2 banks of 3 PB unit, Pye 731 £2 4 Push button unit preh £1.00 6 Push button VHF/UHF for v/cap. GEC-Decca type £7.00 7 Push button for CVC5 ITT £8.00 KT3 12 Push button unit £2.00 KT3 (Export) 12 P.B.U. £2 6 Push button Unit Thorn £1.00 6 Push button Unit fits GEC & Decca etc. £6.00 6 Push button unit for GEC 2040 and ELC 1043/05 £6.00 Hearing aid unit £3 6 Push button unit PYE 713 £7.00 7 Button Unit GEC with Lamps £7 | | BY 602 10p F 247 10p XK 3102 50p XK 3123 50p Hitachi 2A/1500V metal case wire end 20p 20.AX GEC Degaussing Panel 809 with PT37 £1.00 Line Transformers 2 J/Pots 3.500 1 off each type £3.00 G8 Symmetry Coil £2.00 G8 Trans. Philips £7.00 G11 Split Diode £12.00 CVC820 Split Diode ITT £10.00 Thorn B/W AD5308F + Stik + Lead £1.50 GEC 2040 £3.00 GEC 2110 £7.00 Mullard AT 2036 £1.50 Pye 169 Line Trans £3.00 Pyc mono £3.00 Rank mono T704A £3.50 GRC 20 AX Split Diode Trans. £7.00 CVC20 ITT £3.50 AT2080/15 £3.50 CVC30 ITT £3.50 CVC32 Line Tran £4.75 CVC800 Line Trans £6.00 CVC40 Slip/Diode £12.00 GEC Portable G10T2041 £3.00 GEC Portable G10T2046 £3.00 EHT Split Diode Leads ITT £1.00 EHT Cable/Metre 20p Exp panel "14" Fidelity portable £5 | | 6 Diode Universal Triplers £3.25 NEW PYE 725 line O/P panel with L.O.P.T. & Tripler £10.00 Thorn Mains Isolator unit for 70-80W. Ex-speaker £2 NEW GEC 20AX Power Supply Switch Mode £12.00 Complete new GEC portable chassis M1201H/M1501H with P.B.U./v.cap/LOPTI £10 Field + Jungle panel for GEC 3133/3135 £1.50 GEC 2110 line panel with transformer £7.00 GEC 2110 tuner unit + 1F Panel £7.00 Pye/Cheslea Line on panel £12.00 Pye 713 IF panel and tuner £7.00 Pye 713 Chroma £10.00 Pye/Cheslea Timebase panel with LOPTI £10.00 Pye 731 Frame Panel £5.00 Pye 731 Convergence Panel £5.00 Pye 731 Chroma £10.00 Pye 731 IF panel + tuner £10.00 Pye 607/205 Line panel with transformer £10.00 Pye CDA/205 panel £6.00 GEC portable chassis + LOPTI 2114 New £4.00 Thorn l613/1713 chassis 9.75 Hills 250 multimeter + case. 20,000W/volt, fuse diode protected + logic test facility. 10meg/1200 volt £19.50 NEW MULLARD TELETEXT Decoder Panel (VM6230) 10p Panel 6101 50p Panel 6330 50p G8 Tuner Unit + Panel 30p G8 Convergence Panel 10p (late type) £12.00 G8 Power Supply 40p G8 6 Sloping PBU £8.00 G8 IF & Chroma £12.00 G8 Chroma £6.00 G11 IF Detector £3.00 G11 Selector gain module £3 Complete CVC 825 Chassis (both panels) £40.00 AEC V/Cap Resistor Unit UHF with 25p IC SAS660 SAS670 £3.00 Z714 RANK IF Panels 6MHz 1 I.C. £3.00 SL437E £3.00 Z909B RANK IF Panels 75p Export 5.5MHz 2 I.C.'s 75p TBA1205B TCA27050 £2.50 Z743 RANK IF Panel 60p Export 5.5MHz 3 I.C.'s 70p TBA750+SC9504P+ £1.50 SC9503P £1.50 Pye G11 Front panel with transducer, pots, tuner pots, 6 pb switch+lead £5.00 GEC V/cap VHF/UHF tuner and IF + sound O/P PC 706B3 (Export) £12.00 GEC Line O/P PC 659B3 £6.00 2110 GEC Power Panel £8.00 GEC Power Supply (Export) £10.00 G11 dynamic correction panel £6 CVC 20 Front panel with sliders + mains input panel £4 CVC 40 PUSH BUTTON ASSY with sliders: complete with lamp assy + pots £14 CVC 5 Mains on/off + 5 pots £2 Universal Focus. Fits Pye, Thorn and Decca Units. 75p Large Type 75p Decca Small 75p KT3 Focus Unit 75p K30 Focus Pot 75p TX10 Focus Units £6.00 CVC 32 Focus Unit 75p 3500 Thorn Focus Unit £1.00 G11 focus £2.00 ITT Small for use with Split Diode 50p TV11 50p Remo TV12SP 50p TV13 50p TV14 50p TV18 60p TV20 £1.00 TV45 50p Thorn 14/1500 rec stick 5p 16 Button Key Pad 1 to 0 + * + # + 4 blank (Cherry) £3.00 | | 250/64 10p 330/70 50p 1/100 5p 1/100 x 10 10p 4.7M/100 5p 470/100 20p 200/100 70p 470/100 70p 47/160 15p 470/100 75p 600M/300V £1.00 800/160 50p 1/250 Pulse 5p G11 0.47/250 10p 2.2 250v 10p 3.3/250V 10p 39/250V 25p 4n7/250 tested 5KV 35p 91/250 30p 91/400 15p 22/250 15p 47/250 20p 100/250 20p G11 470/250V £1.75 GEC 600/250 60p 700/250 61p 600M/300 £1.00 800/250 40p 32/250V 5p 4/350 5p 8/350 8p 12/300 10p 4.7M/350v 10p 16/350 25p 33/350 20p 50/350 10p 220/350 30p 300/350 40p 400/350 50p 10/375 15p 22/375 15p 200/385 75p 330/385 CVC 820HT 60p 0.1/400 10p KT3 E/W 39/400 20p -56K/400v 20p 4700p/400 10p 22/400 10p 8/400 15p 33/400 15p 400/400 40p 394K/400V 20p 220/450 20p 47/500 25p 0.1/600 15p 0.047/600 15p 0.01/1000 10p 0.1/1000 10p -15/1000 20p .47/250V A.C. 10p .001K/1250 10p 0.0047/1500 10p .005/1500 10p .0105/1500 10p 1n8/1500 15p 2n0/1500 15p 2n2/1500 15p G11.11000/1500 .01/1600 15p G11.8200/2KV 15p 0.12/KV 20p 10n/2KV 15p 39p/2KV 15p 0.0015/2KV 15p 6n/2KV 15p 2n0/2KV 15p 2n2/2KV 15p 7500p/2KV 10p 4n7/2KV 10p 8n2/2KV 15p 0.0082/2500 15p 150/3500 15p 180/4KV 5p 4.7n/5KV 10p 170/8KV 10p 180/8KV 10p 210/8KV 10p 1000/1KV 10p | | NEW GRUNDIG SPARE PANELS Mod Number From £5 to £10 Send for panel number SC4127 £7.00 SC4237 £5.00 SC6217 £12.00 SC6237 £7.00 Multi-Caps 10 for £15 470/250 G11 10p Thorn 3500 £1.75 175/100/100/350v £1.75 KT3/200/25/25/385v £1.00 300+300+150+100+50MFD 350V £2 47/200/350v 60p 150/150/100/100/320v £2.00 2500/2500/63v 50p 470/470/250v 50p 150/200/200/300v 70p 400/400/200v £1.75 300/100/100/16/275v £1.50 100/200/325v 40p 150/150/100/375v £1.50 300/300/100/32/32/300v 2.00 150/200/30v 50p Jelly pot Thorn 00D4013 £3 150/150/100/100/320v £2.00 100/350 + 300/200/100/16/275v £2.00 300+300/300 £1.00 225+25/380 GEC £70p 200/100/100/350v £1.50 500/500/25v 75p 150/150/100/300v 50p 200/150/150/300v 1.00 ITT Panels CVC 40/2 Chassis, new £30, complete with infrase panel £3.00 CVC 820 Line O/P Panel £3.00 CVC 20 Mains Panel £1.00 ITT 8 & 6 Push Button Unit £10.00 CVC40/2 New Chroma Panel £2.00 CMA 10 £2.00 CMA 11 £2.00 CMA 30 £2.00 CMA 40 £1.50 CMC 10/2 £5.00 CMC 16 £4.00 CMC 38 £8.00 CMC 45 £1.50 CMC 47 £1.00 CMC 52 £15 CMC 57 £6.00 CMC 58 £8.00 CMC 59 £8.00 CMC 67 £3.75 CMC 67/2 £4.00 CMC 68 £4.00 CMD 12 £10 CMD 32 £5.00 CMD 33 £5.00 CMD 40 £5.00 CMD 41 £5.00 CMF 25 £2.00 CMF 26 £2.00 CMF 40 £2.00 CMH 10 £1.50 CMH 31 £1.00 CMK 12 (untested) £4.00 CMK 30 (untested) £4.00 CMN 20 £1.50 CMN 21 £1.50 CMN 40 £1.00 CMN 45 25p CMP 10 £2.00 CMP 11 £4.00 CMP 40 £2.00 CMS 11 £2.00 CMS 40 £2.00 CMU 12 £10.00 CMU 14 £8.00 CMU 30 £7.00 CMU 45 £7.00 CMZ 30 £5.00 GMA 90 £5.00 GEC 120 £2.50 GMR 64 £5.00 -TMN 2 £2.00 VCA 20 £10 VCA 21 £10.00 VMC 25 £3.00 VMC 34 £5.00 VMC 44 + 45 £4.00 VMC 51 £5.00 Hand Sets Transducer Hand Set Insert, crystal, transducer, SAA 1124 & lead £3.50 8 C.H. Ultrasonic GEC Full Remote C2014H/C2219H £15.00 New Replacement for G11 Ultrasonic Full Remote £12.00 Thorn 4000 insert with 7 buttons £5.00 Decca RC 11 £14.00 Decca RC 12 £14.00 G11 Infra-red full teletext £19.00 G11 Ultrasonic full teletext for G20c 674/02 and G22c 66/02 £16.00 G9 Philips R/C Transmitter £8.00 Rank, Infra-red £10.00 Dynatron-Full remote CTV 62, 63, 64 £19.00 Hitachi infra red handset £18 Philips/Fits: K12 26C 797/1ST 66K 7228/7324; K12 26C 797/1ST 66K 1826 £12.00 G11. Full remote top button assy. £12.00 G11. Full remote repair service (exchange unit) £12.00 Philips infra red full remote 9 channel for 60 CP2605 £6.00 Philips infra red full remote 12 channel for 60 CP2605 £12.00 Philips Key Pad set KT3/K30 £3.00 KT3/K30 T/Text £15.00 KT3/K30 Full remote £15.00 KT3 Power supply £4.00 Hitachi 8 button unit with resistor unit, Last year mod. £7.00 GEC infra-red 2236-2026 £4.00 GEC push pad hand set button blobs 10p each | | | |
| Mains Droppers G8 2R2+68R £1.25 G8 47R 15 watt 75p Pye 731 3+56+27R 50p Pye 3R5/15R/45R 50p Thorn 50/17/1K5 £1.00 120/20/20/48/117 £1.00 20V/10/6 for Thorn 4000 50p 18/320/70/39 £1.10 Thorn 50-40R-1K5 50p Ae Socket & Lead £1 GEC, ITT, Philips, Pye 7x3/4 Thorn 25p Rank Toshiba Tube Bases 30p | | Triplers 8500 Triplers £6.50 11 TEZ Rank £3.00 G9 Philips £4.00 GEC 2110 £4.00 3500 Thorn £3.00 9000 Thorn £5 9500 Thorn £4.50 2040 GEC £3.50 GEC TVM25 Tripler £2.00 Universal Tripler £5.00 TVK 769 £3.00 G8 Philips (Mullard) with cap £6.00 CVC 825 ITT CVC 2025/30/32 £3.50 Decca 80 100 £4.50 Grundig TVK 52 £2.50 11TBQ Pye 731 £3.00 11THY £4.00 D22 for Pye 18" colour portable £4.00 LP 1193/63 £4.00 BG 100/41 £3.25 BG 100/61 £3.25 KT3 BG200/43 £3.50 T/text ultrasonic rec'r panel £14.00 Video cassette lamps on lead. 12-14V. 50p or 3 for £1.00 20 for £5.00 200 for £25.00 GEC 8 touch unit assy complete with all I.C.'s + pots £4.00 G11 E.W. Transformer 50p G11 E.W. coils £1.00 G11 Transient Suppressors 245V 10 for £1.00 G11 Scan Coils £5.00 G11 100K tuner pots 12 for £1 KT3 IF panel £6.00 KT3 line OSC transformer £1 KT3/K30 infra-red receiver head £3 K30 drawer unit with IC's (home) £10 K30 drawer unit with IC's (export) £10 KT3 AE Sockets 25p KT3 receiver panel £8 KT3 line driver transformer 50p Decca 80/100 IF panel £5 NPN PNP 80V 6 Amp TO66 O.P. Trans. pair 25p | | Speakers 6x4 G11 25 ohm 70p 5 1/2x2 1/2 3 ohm £1.00 5x3 80 ohm 70p 5x3 50 ohm 50p 5x3 35 ohm 70p 6x4 15 ohm £1.00 7x3 70 ohm £1.00 5x3 8 ohm 70p 7x3 16 ohm £1.00 5" dia 16 ohm £1.00 5" dia 8 ohm £1.50 6 1/2" dia 4 ohm £1.50 6 1/2" dia 3 ohm £1.50 2 3/4" dia 8 ohm 75p 3" dia 8 ohm 75p 4 1/2" sq. 15 ohm 75p KT3 speaker K30 75p 3" dia 15 ohm 60p | | Diodes BY 127 10p BY 133 10p BY 134 10p BY 164 50p BY 176 25p BY 179 40p BY 184 25p BY 187 10p BY 190 40p BY 196 30p BY 198 10p BY 204/4 8p BY 206 8p BY 208/800 8p BY 210/400 5p BY 210/800 10p BY 223 60p BY 224/600: 4.8A/600v bridge 50p BY 226 15p BY 227 15p BY 228 20p BY 229/400 30p BY 237 5p BY 254 10p BY 255 30p BY 298 10p BY 299 10p BY 406 8p BY 527 20p BY 407a 10p | | Diodes G770/HV34 6KV 3 for 8p 6A/600V Stud Diodes 20p 6A/1000V Stud Diodes 20p | | DISPLAYS 4040 Clock £1.00 7seg Red LED 50p 2 digit LED 8.8 50p 2 digit LED =1.8 with panel + MCL4511 £1.00 1000/1KV £1.50 Infra Red and Ultrasonic G11 Teletext Decoder Panel £30 RANK & ITT Mains Remote On-Off Switch (720R) £1.50 RANK & ITT Mains Remote Switch 2865 ohm £1.50 RANK & ITT Remote Switch 2800 ohm £1.50 G11 Mains Switch 50p 4 amp Mains Switch 20p GEC Mains Switch 4 amp 30p KT3 Mains Switch £1.00 THORN Rotary Mains Switch 50p G8 Mains Switch 20p Thyristor 600A amp C1062 24p G11 Preh Red LED P/Button for C.H. Change 20p RANK TOSHIBA Transducers TPC-2011 50p CVC 5 Mains on/off + 250K + 100K + 500K + 500K Pot on Panel £2.00 Thorn 12 or 24 volt battery connector for portable colour TV £12.00 Tape Heads R/Play/Back Mono/Stereo £1.00 | |

SENDZ COMPONENTS

63 Bishopsteignton,
Shoeburyness, ESSEX SS3 8AF
SAME DAY SERVICE

All items subject to availability.
No Accounts - No Credit Cards
Postal Order/Cheque with order
Add 15% VAT, then £1 Postage
Add Postage for overseas

Callers: To shop at 212 London Rd.,
Southend. Tel. 0702-332992

Open 9-1/2.30-6. GVMT + school orders accepted on official
headings add 10% handling charge.

| Tuner Units | |
|--|--------|
| GEC 6 Push Button Unit | £6 |
| ITT 6 Push Button Unit | £6 |
| DECCA 6 Push Button Unit | £6 |
| G8 Tuner | £7 |
| GEC or Hitachi 6 push button unit 2110 Conversion | £12 |
| GEC 2110 V/Cap | £6 |
| ELC 104306 (A&G) | £6 |
| ELC 104305 Mullard | £6.00 |
| E1C1043 (Ex Panel) | £3.75 |
| ELC1042 | £5.00 |
| ELC2000 | £7.00 |
| ELC2004 | £10.00 |
| ELC2006 | £10.00 |
| GEC Tuner V/Cap Hitachi Alter | |
| 1979 ET548, ET547 | £10.00 |
| U322 (UHF) | £4.00 |
| V314 (VHF) | £5.00 |
| U321 | £6 |
| U341 UHF | £7.00 |
| U411 UHF | £7.00 |
| U.V. 411 Tuner | £10.00 |
| ELC104305 Thom | £5.90 |
| Small V/Cap Mitsumi | |
| UHF | £4.00 |
| VHF | £3.00 |
| G8 Tuner | £6.00 |
| Portable & rotary Tuners Sanyo & Mitsumi UHF | £5.00 |
| 6003 Bush V/Cap Tuner | £10.00 |
| NSF-UHF/VHF Varicap (old type) | £8.00 |
| Moshi UHF/VHF (new type) | £8.00 |
| SONY 1400KV Tuner unit | £3.50 |
| Thorn Tuner PANEL with 6x100k pots & cursors NO TUNER | £1.00 |
| HITACHI 20 Turn Pot | 40p |
| U321 on panel | £6.00 |
| Tuner unit VHS Sylvania GTR | |
| Video MTS 900 | £2.50 |
| Mullard Video Modulator. | |
| Application, video tape recorders, TV cameras, video games, closed circuit TV, C.C.I.R. system, Data supplied. | £10.00 |
| VT 100 Sound Tuner Kit. TV. Visiound. The latest design in low noise fitted with DNR, RF output and audio | £30.00 |
| Labgear Teck-Verta (VHF) in (UHF) out | £12.00 |
| Sylvania UHF E4720B | £6.00 |
| Sylvania VHF 900 | £6.00 |
| Decca Bradford Tuner 5 Button | £4.00 |
| Small Tuner DX 175-220MHz Auto Changeover | £5.00 |
| 9000 Thorn Tuner on Panel | £7.00 |
| D.P.D.T. switch Black knob: Chassis or PCB mount | 4p |
| each or 40 for £1.00 | |

| | |
|---|-------------|
| TI THORN 1400 4P.B. Mech. Tuner | 20p |
| THORN 1500 4P.B. Mech. Tuner | 40p |
| THORN 1590 4P.B. Mech. Tuner | 50p |
| THORN 3500 4P.B. Mech. Tuner | 75p |
| THORN 8000 4P.B. Mech. Tuner | 1.00 |
| TI THORN 8500 Mech. Tuner | 1.00 |
| All new & boxed. | £4.00 each |
| Delay Lines | |
| DL20A 80p | DL600 £1.00 |
| G8 (Old Type) | £1 |
| DL600 | £1.00 |
| DL710 | £1.00 |
| UDL11 | 30p |
| KT 3 Luminescence | 75p |
| Luminance Delay Line (CVC 45) | |
| 10x630ma fuse | 25p |
| 10x2A fuse | 50p |
| 10x3.15 fuse | 50p |
| 10x500mA | 80p |
| 10x1 amp | 80p |
| 10x1.6 amp | 80p |
| 20 3.15 AS Fuses | £1.70 |
| Co-Ax Joint | 15p |
| Co-Ax Belling Lee Plug | 12p |
| Co-Ax Splitter | £1.00 |
| UHF Modulator CCIR | £3.00 |
| Infra Red Emitting Diode | 20p |
| NE2861 H Small Neon Lamps GEC & Philips | 5p |
| Mullard 5 Watt Amps. LP1162 | 75p |
| T.V. Tubes | |
| 12" A31/300 Hitachi | £10 |
| 15" A38/170W Hitachi | £8 |
| 18" Hitachi PIL tube with scan coils 470 KCB22-TC03 | £25 |
| 10" Green tube scan coils & line trans | £6.00 |
| Integrated Circuits | |
| AC76003 | £1.50 |
| AM25LS23PC | 10p |
| BAV40 | 40p |

| | |
|----------------|-------|
| MRI1366 | 20p |
| BRC-M-200 | 40p |
| BRC-M-300 | 50p |
| BRC 1330 | 75p |
| BRC 3064 | £1.00 |
| BIT822 | £1.00 |
| BT16016 | £1.20 |
| BT6018/ML237B | £1.50 |
| BT16218 | £1.50 |
| BT1824 | £1.00 |
| BT1824 | £1.00 |
| CA270AE | 50p |
| CA270CW | 50p |
| CA270CE | 50p |
| CA920AE | £1.00 |
| CA1310 | 50p |
| CA306SQ | 50p |
| CA3089E | 50p |
| CA3094E | 50p |
| CA3123 | 40p |
| CA3146 | £1.00 |
| CA3189 | 40p |
| CBF16648 | 50p |
| CD4510 | 30p |
| DM7492 | 50p |
| HA1196 | 40p |
| HA1370 | £2.00 |
| HA11223 | 40p |
| HEF4011 | 10p |
| HEF40111AF | 10p |
| HEF4053B | 30p |
| M913 | £2.00 |
| MI024= SAA | £2.00 |
| MI025= SAA | £2.00 |
| MC4707 | £1.00 |
| MC1307 | 75p |
| MC1312 | |
| MC1330 | 75p |
| MC1349 | 50p |
| MC1352 | £1.00 |
| MC1358 | £1.00 |
| MC14002 | 15p |
| MC14013 | 25p |
| MC14016 | 25p |
| MC14066 | 30p |
| MC14514 | 50p |
| MC1748 | 80p |
| MEM4956 | £1.00 |
| ML231 | £2.50 |
| ML236E | £1.00 |
| ML237B | £1.00 |
| ML238B | £4.00 |
| ML239 | £2.00 |
| MM5387 | £1.00 |
| MM5611 | £1.00 |
| MM5840 | 75p |
| MR1366 | 20p |
| N64100 | £1.00 |
| NE545B (Dolby) | 75p |
| NE555P | 60p |
| NE555 | 60p |
| IL-1 | 20p |
| OPT600 | 20p |
| OPT601 | 20p |
| SAA611 | 50p |
| SAA661 | £1.75 |
| SAA1020 | £4.00 |
| SAA1021 | £4.00 |
| SAA1024 | £2.50 |
| SAA1025 | £2.50 |
| SAA1073 | £3.00 |
| SAA1074 | £3.00 |
| SAA1075 | £3.00 |
| SAA1124 | £2.00 |
| SAA1130 | £2.50 |
| SAA1174 | £3.00 |
| SAA1176 | £3.00 |
| SAA1250 | £3.00 |
| SAA1251 | £4.00 |
| SAA1272 | £3.00 |
| SAA1276 | £3.00 |
| SAA5000 | £1.50 |

| | |
|--------------|-------|
| SAA5000A | £1.50 |
| SAA5012A | £5.00 |
| SAA5020 | £3.50 |
| SAA5030 | £5.00 |
| SAA5040 | £3.50 |
| SAA5040A | £4.40 |
| SAA5050 | £3.50 |
| SAF1032p | £2.50 |
| SAF1039 | £2.00 |
| SAS560 | £2.00 |
| SAS660 | £1.00 |
| SAS670 | £1.00 |
| SL901B | £5.00 |
| SL918 | £6.20 |
| TA7122 | £1.15 |
| TAA320A | 50p |
| TAA470 | £1.50 |
| TAA570 | 75p |
| TAA611B | 50p |
| TAA621 | £2.00 |
| TAA661 | 50p |
| TAA661 | £1.50 |
| TA7117 | 50p |
| TA7120P | 50p |
| TA7315AP | 50p |
| TA7607AP | 40p |
| TA7609P | 50p |
| TBA120A | 40p |
| TBA120AS | 50p |
| TBA120SA | 40p |
| TBA120B | 40p |
| TBA1205B | 40p |
| TBA1205Q | £1.00 |
| TBA120U | 75p |
| TBA120Q | 30p |
| TBA120C | 40p |
| TBA1441 | £1.00 |
| TBA231 | 75p |
| TBA395Q | 50p |
| TBA396Q | £1.00 |
| TBA396 | 75p |
| TBA440P | £1.00 |
| TBA1440C | £1.00 |
| TBA480Q | £1.00 |
| TBA520 | £2.00 |
| TBA530 | £2.00 |
| TBA540 | £1.00 |
| TBA550Q | £1.75 |
| TBA560CQ | £2.00 |
| TBA570 | £1.50 |
| TBA625 | 50p |
| TBA641 | £2.00 |
| TBA673 | £2.00 |
| TBA720A | £1.50 |
| TBA750Q | £1.50 |
| TBA780 | £1.50 |
| TBA810AS | 50p |
| TBA810S | 60p |
| TBA820 | 60p |
| TBA890 | £1.00 |
| TBA900 | £1.50 |
| TBA920 | £1.50 |
| TBA920Q | £1.50 |
| TBA950 | £1.50 |
| TBA990Q | £1.00 |
| TMS1000NL | £2.00 |
| TMS1943 | £1.00 |
| (clock chip) | £1.00 |
| TMS9980 | £4.00 |
| TMS9901 | £1.00 |
| TMS2716JL | £1.00 |
| TMS3529 | £1.00 |
| TMS3720ANS | £3.00 |
| TMS4014 | 70p |
| TX-012 | £1.00 |
| TMS9902 | £1.20 |
| ULN2216 | 75p |
| SN29848 | 50p |
| SN29770BN | £1.00 |
| SN29771BN | £1.00 |
| SN29772BN | £1.00 |
| SN7402N | £1 |
| SN7472N | £1 |
| SN74107 | £1.00 |
| SN74107 | 70p |
| SN7472N | 20p |
| SN75108AN | £1.00 |
| SN76001 | £1.00 |
| SN76003 | £1.00 |
| SN76013ND | £1.50 |
| SN76018 | £1.00 |
| SN76008 | £1.00 |
| SN76023N | £1.50 |
| SN76033 | £1.50 |

| | |
|-------------|-------|
| SN76110N | £1 |
| SN76115AN | 50p |
| SN76131 | 50p |
| SN76141N | £1.00 |
| SN76226 | £1.00 |
| SN76227N | 60p |
| SN76228N | £1.00 |
| SN76270 | £1.00 |
| SN76532N | 50p |
| SN76544N | £2.00 |
| SN76545 | £3.50 |
| SN76546 | £1.00 |
| SN76550 | 30p |
| SN76552 | 30p |
| SN76570 | £1.00 |
| SN76620 | 50p |
| SN76650 | 50p |
| SN76660N | 40p |
| SN76620AN | 50p |
| SN76646 | £1.00 |
| SN76705N | £1 |
| SN76707N | 75p |
| SN76708AN | 75p |
| SN76720 | £1.00 |
| UA783P3C | 40p |
| BT100A02 | 40p |
| BT138/10A | 70p |
| BT146 | 30p |
| TBA540Q | £1.50 |
| TCA270 | £1.00 |
| TCA270Q | £1.00 |
| TCA640 | £1.00 |
| TCA660 | £1.00 |
| TCA270S | £1.00 |
| TCA270SQ | £1.00 |
| TCA740 | £1.00 |
| TCA800 | £4.00 |
| TCA830 | £1.00 |
| TCEP101 | £2.25 |
| TDA120CQ | £1.00 |
| TDA1003A | £1.00 |
| TDA1010 | £1.00 |
| TDA1060A | £1.50 |
| TDA1072 | £1 |
| TDA1151 | 30p |
| TDA1170 | £1.00 |
| TDA1190 | £1.00 |
| TDA1200 | 75p |
| TDA1327A | £1.00 |
| UPC1365 | £3.00 |
| UPC1365 | £3.00 |
| TDA1412 | 50p |
| TDA2003 | 80p |
| TDA2044 | £2 |
| TDA2010 | £1.00 |
| TDA2140 | £1.00 |
| TDA2030 | £2.50 |
| TDA2525 | £1.00 |
| TDA2640 | £2.00 |
| TDA2522 | £1.00 |
| TDA2530 | £1.50 |
| TDA2532 | £1.00 |
| TDA2540 | 80p |
| TDA2541 | £1.00 |
| TDA2571AQ | £2.50 |
| TDA2575A | £1.00 |
| TDA2581 | £2.50 |
| TDA2590 | £1.00 |
| TDA2593 | £1.00 |
| TDA2600 | £5.00 |
| TDA2611 | £1.00 |
| TDA2653 | £1.00 |
| TDA2002 | £1.00 |
| TDA2640 | £2.00 |
| TDA2680 | £1.00 |
| TDA2690 | £1.00 |
| TDA2593 | £1.00 |
| TDA3190 | £1.00 |
| TDA3560 | £4.00 |
| TDA3571O | £1.50 |
| ULN2216 | £3.00 |
| TDA3651A | £3 |
| SN74LS125AN | 30p |
| SN74LS248 | 50p |
| SIL4516 | 50p |
| SN1686-1NG | 50p |
| SN1686-2AN | £1.00 |
| SN16964AN | £1.00 |
| SN29764AN | £1.00 |
| UA721 | 40p |
| UA7300 | 40p |
| RGP30G | 10p |
| MPSA44 | 10p |
| MPSA43 | 10p |
| MJ1300S | 30p |
| MJE51T | 25p |
| MJE340 | 25p |
| MJE661 | 25p |
| MJE363 | 15p |
| MJE3055 | £1.00 |

| Philips Cartridges | |
|---|----------|
| GP412 | £6.00 |
| GP412/11 | £6.00 |
| GP406 | £6.00 |
| Transistors | |
| A1222 | 15p |
| A1223 | 15p |
| AC106 | 15p |
| AC121 | 15p |
| AC124 | 15p |
| AC128 | 15p |
| AC137 | 15p |
| AC151 | 15p |
| AC131 | 15p |
| AC138 | 15p |
| AC152 | 15p |
| AC153K | 15p |
| AC142K | 15p |
| AC169 | 15p |
| AC176 | 15p |
| AC178K | 15p |
| AC179 | 15p |
| AC186 | 15p |
| AC187K | 15p |
| AC188 | 15p |
| AC188K | 15p |
| AC191 | 15p |
| AD143 | 50p |
| AD149 | 50p |
| AD161/162 | pair 20p |
| AF139 | 25p |
| AF181 | £1.00 |
| AF239 | 25p |
| AF367 | 15p |
| AL102 | £1.75 |
| BC161 | 30p |
| BD507 | 30p |
| BD509 | 30p |
| BD510 | 30p |
| BD517 | 30p |
| BD519 | 30p |
| BD534 | 30p |
| BD535 | 30p |
| BD544D | 30p |
| BD562 | 30p |
| BD610 | 30p |
| BD626 | 30p |
| BD676A | 30p |
| BD678 | 30p |
| BD681 | 25p |
| BD807 | 25p |
| BD826 | 50p |
| BD948 | 50p |
| BDX75 | £1.25 |
| BDX32 | £1.25 |
| BF115 | 20p |
| BF121 | 20p |
| BF127 | 20p |
| BF157 | 20p |
| BF157 | 20p |
| BF160 | 20p |
| BF161 | 20p |
| BF169 | 60p |
| BF179 | 20p |
| BF180 | 20p |
| BF181 | 20p |
| BF182 | 20p |
| BF184 | 20p |
| BF194 | 10p |
| BF195 | 10p |
| BF196 | 10p |
| BF197 | 12p |
| BF198 | 10p |
| BF199 | 10p |
| BF200 | 10p |
| BF222 | 10p |
| BF224 | 15p |
| BF238 | 10p |
| BF240 | 16p |
| BF244 | 10p |
| BF256 | 10p |
| BF256 | 10p |
| BF258 | 25p |
| BF263 | 15p |
| BF269 | 25p |
| BF274 | 15p |
| BF276 | 10p |
| BF277 | 10p |
| BF324 | 25p |
| BF337 | 30p |
| BF350 | 30p |
| BF358 | 30p |
| BF459 | 30p |
| BF468 | 30p |
| BF469 | 30p |
| BF470 | 30p |
| BF480 | 50p |
| BF594 | 10p |
| BF597 | 10p |
| TV Crystals | |
| 4MHz | 50p |
| 4.433-619 | £1.00 |
| 6MHz | 50p |
| 8.867238 | 50p |
| Large or small 50p each | |
| GEC Power Panel TV106 Thermistor PT34 New £1.00 | |
| L.C. Holders | |
| DIL - DIL | |
| 40 Pin x 4 | £1.00 |
| 42 Pin x 5 | £1.00 |
| 28 Pin x 10 | 80p |
| 16 Pin x 10 | 70p |
| 24 Pin x 5 | 75p |
| 14 Pin x 10 | 70p |
| 18 Pin x 10 | 80p |
| DIL - QIL | |
| 16 Pin x 10 | £1.00 |
| 18 Pin x 10</ | |