


SEPTEMBER 1985

Australia \$1.80, New Zealand \$2.20, Malaysia \$5.50 £1.10

TELEVISION

SERVICING·PROJECTS·VIDEO·DEVELOPMENTS

SEEKING AGENTS
\$1.90
BARKLY ST. FCRAV

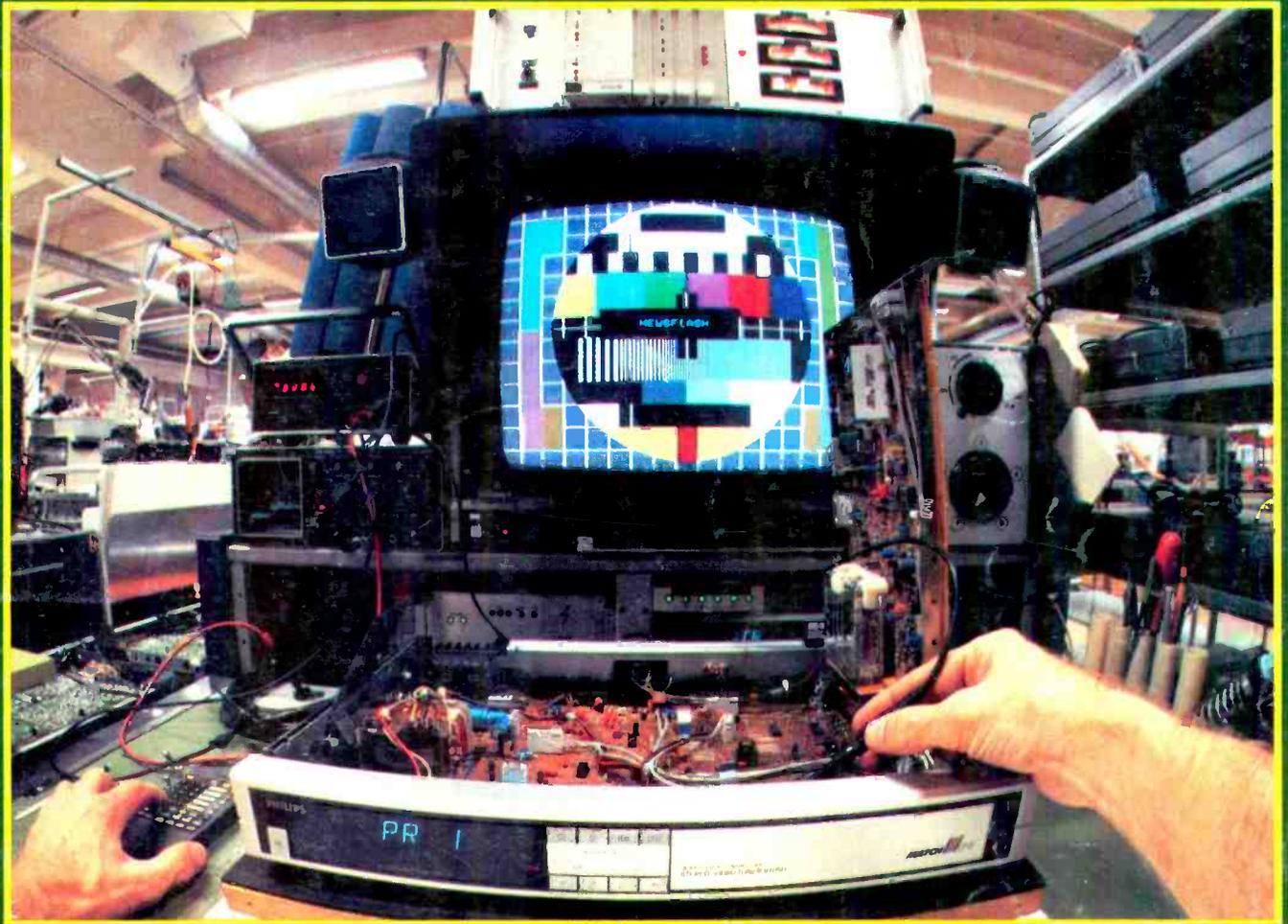

**An Approach to Adding Teletext
Quick Steps in TV Servicing
VCR Clinic • A Visit to MCES
Variable Stabilized HT Supply
A Case of Liquid Spillage
TV Fault Finding • DX-TV**

MANOR SUPPLIES

**MKV PAL COLOUR
TEST GENERATOR FOR TV & VCR.**

TEST
DEMONSTRATIONS
AT 172
WEST END LANE




- ★ 40 different patterns and variations.
- ★ Broadcast transmission accuracy (fully interlaced sync pulses with correct picture blanking).
- ★ EBU colour bars, BBC colour bars, whole rasters & split bars (specially useful for VCR service), white, yellow, cyan, green, magenta, red, blue and black.
- ★ Chequerboard.
- ★ Mono outputs with border castellations, cross hatch, grey scale, vertical lines, horizontal lines and dots.
- ★ UHF modulator output plugs straight into receiver aerial socket.
- ★ Additional video output for CCTV & VCR.
- ★ Facilities for sound output.
- ★ Easy to build kit, standard parts. Only 2 adjustments. No special test equipment required.
- ★ Mains operated with stabilised power supply.
- ★ All kits fully guaranteed with back-up service.
- ★ Also available with VHF Modulator.

Price of Kit **£70.00**
Case (10"×6"×2¼") app. **£7.40**
Optional Sound Module (6MHz or 5.5MHz) **£3.90**
Built & Tested in Case including Sound Module **£105.00**

SPECIAL TEST
REPORT
'TELEVISION'
DEC. 1982

Post/Packing £2.50
Add VAT 15% TO ALL PRICES

PAL COLOUR BAR GENERATOR (Mk4)

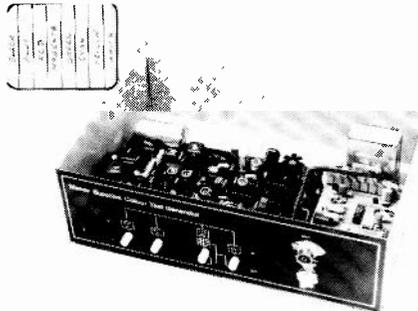

- ★ Output at UHF, applied to receiver aerial socket.
- ★ In addition to colour bars R-Y, B-Y etc.
- ★ Cross-hatch, grey scale, peak white and black level.
- ★ Push button controls, battery or mains operated.

★ Simple design, only five i.c.s on colour bar P.C.B.
**PRICE OF MK 4 COLOUR BAR GENERATOR KIT
£30.00, CASE £7.40, BATT HOLDERS £2.80, MAINS
SUPPLY KIT £4.20 (Combined P&P £2.20).**

MK 4 (BATTERY) BUILT & TESTED £58.00 + £2.20 P & P.
MK 4 (MAINS) BUILT & TESTED £68.00 + £2.20 P & P.
VHF MODULATOR (CH 1 to 4) FOR OVERSEAS £5.75.
EASILY ADAPTED FOR VIDEO OUTPUT & C.C.T.V.

GEÇ TELETEXT EXTERNAL ADAPTOR UNIT
Complete & ready for use. Converts any TV into a Teletext Receiver with Infra-Red Remote Control (incl. 25 Button Handset) **£130.00** p.p. £3.00
TELETEXT EXTERNAL ADAPTOR KIT (Less case) TEXAS
with cable remote control **£120.00** p.p. £3.00
THORN TX10, teletext
Mullard Decoder panel + Interface **£35.00** p.p. £1.80
THORN TX10, PHILIPS G11 PRESTEL
Mullard Units VM 6230, 6330 plus Line Coupler & Interface **£50.00** p.p. £2.50
Goods available if in stock immediately over shop counter (Mail order between 3 days and 1 week from receipt of order). ADD VAT 15%

TV SERVICE SPARES

BACKED BY TWENTY YEARS EXPERIENCE & STAFF OF
TECHNICAL EXPERTS

LOPTS, TRIPLERS, PANELS, TUNERS, SELECTORS ETC.

PHILIPS G11 PANELS (tested).
Power, frame, IF, decoder **£18.00** each p.p. £2.00.
Scan Panel **£28.00** p.p. £2.80.
PHILIPS G11 PANELS ex rental (untested).
Power, frame, IF, decoder **£10.00** each p.p. £2.00.
SPECIAL OFFER Philips, Pye KT3 Series infra-red remote control handsets ex rental (untested) Teletext or normal versions available **£2.50** p.p. 80p (5 for **£10** p.p. £1.50). CTX, K35 Teletext + Video **£5.00** p.p. 80p.
THORN 9000 Fault Finding Guide **£1.00** p.p. 30p.
TX10 Remote & Tuning control panel (1515) **£9.40** p.p. £1.50
THORN TX10 Facia Control Panel incl. Infra Red Remote Control receiver **£7.50** p.p. £1.50.
THORN TX10 Series Facia Control Panel with 8 position Channel Selector **£5.00** p.p. £1.50.
PHILIPS UHF Modulator (Audio & Video Input) **£15.00** p.p. £1.00.
SAW FILTER IF AMPLIFIER PLUS TUNER complete and tested for T.V. Sound & Vision. **£28.50** p.p. £1.20.
THORN TX9, TX10 Saw Filter IF Panel. **£7.50** p.p. 80p.
PAL DECODER KIT (Video to RGB) for Monitors **£27.00** p.p. £1.00.
PAL ENCODER KIT (RGB to Video) **£18.50** p.p. £1.30.
TELETEXT DECODERS New & Tested Mullard VM 6101 **£30.00**, Texas XM11 **£40.00**, KT3 Tested **£30.00**, Untested **£5.00** p.p. £1.60
TELETEXT 23 Button De-Luxe Handset with 5 yds Cable. **£2.50** p.p. £1.20.
5V Stab. Power Supply **£3.80** p.p. £1.20.
CROSS HATCH UNIT KIT, Aerial Input type, incl. T.V. sync. and UHF Modulator, Battery Operated, also gives Peak White & Black Levels, can be used for any set. **£12.00** p.p. 80p. (Alum. Case **£2.55**, De Luxe Case **£6.80** p.p. £1.40.) **ADDITIONAL GREY SCALE Kit** **£2.90** p.p. 45p.
UHF SIGNAL STRENGTH METER KIT **£22.00** (VHF version **£24.00**). Alum. Case **£2.55**, De Luxe Case **£7.40** p.p. £1.80.
CRT TESTER & REACTIVATOR KIT For Colour & Mono with Panel Meter Indicator - can be adapted for latest CRT's **£28.60** p.p. £2.80.
BUSH A823 Convergence, Time Base Panels **£5.00** each. p.p. £1.80.
BUSH Z718 BC6100 series IF Panel **£5.00** p.p. 90p.
BUSH A816 IF Panel (Surplus) **£1.00**, 5 for **£4.00** p.p. 90p.
GEC 2040 Decoder Panels. **£1.50** p.p. £1.80.
GEC 2110 PANELS Frame **£8.50** p.p. £1.40. Sound **£2.50** (tested) p.p. 80p.
GEC 20AX Switch Mode Power Supply **£5.00**, IF-Decoder **£12.50** p.p. £1.80.
PYE 691-7 CDA Panels. Makers tested stock. **£6.00** p.p. £1.45.
THORN TX9 Panels ex factory for small spares. Includes I.Cs & Semiconductors etc. **£3.00** p.p. £1.80.
THORN TX9 Panels salvaged ex factory for spares incl. LOPT & Mains Transformers. **£10.00** p.p. £2.80.
THORN TX9 Panels ex factory salvaged complete cond. **£20.00** p.p. £2.80.
THORN TX10 T.B. Panels salvaged ex factory. **£15.00** p.p. £3.00.
THORN 3000/3500 Power supply P.C.B. **£3.50** p.p. £1.00.
THORN 8000/8500 IF/Decoder Panels salvaged **£3.20** p.p. £1.80.
THORN 9000 IF/Decoder Panels Salvaged. **£5.00** p.p. £1.60.
THORN 9000 Series. Long panel facia unit incl. 6 Position Channel Selector & Loudspeaker **£6.00** p.p. £2.00.
PHILIPS G8/G9 IF/Decoder Panels for small spares incl ICs **£2.50** p.p. £1.60.
G11 PANELS, Ex Rental SCAN (incl LOPT) **£28.00** p.p. £2.50 (tested).
G11 PANELS, Power, Frame, IF, Decoder. **£18.00** each. p.p. £2.00 (tested).
GRUNDIG 8630 Series Varicap Tuners **£5.00** p.p. £1.00.
VARICAP, ELC1043/5 **£7.80** p.p. 80p. Makers Controls **PYE CT200** 4PSN **£7.50**, **BUSH 4PSN** **£4.80**, **DECCA 4PSN** **£5.80**, **6PSN** **£6.80** p.p. 80p. etc.
BUSH "TOUCH-TUNE" Varicap Control Z179, Z718 types **£3.80** p.p. 95p.
VARICAP UHF-VHF ELC2000S **£9.80**, **BUSH** **£7.80** p.p. 90p.
VARICAP VHF PHILIPS. **£6.90**, ELC 1042 **£7.90** p.p. 80p.
UHF/625 TUNERS, many different types in stock: **DECCA** Bradford 5 position, **MULLARD** 4 position **£2.50**, **JAP** Rotary **£4.80** p.p. £1.80.
TV SOUND IF Panels **£6.80** p.p. £1.00.
LOPT TESTER, Service Dept approved **£15.90** p.p. £1.20.
LOPIS New and guar. P/P Mono **£1.35**, Colour **£1.50**, Bobbins 80p.

BUSH 161 to 186 (twin panel)	£5.90	R. B. M. T20, T22	£9.80
BUSH , MURPHY 774 series	£9.80	R. B. M. T20, T22 Bobbin	£5.60
BUSH , MURPHY A816 series	£9.80	DECCA Bradford (state Mod No.)	£8.80
FERR. , HMV , MARCONI , ULTRA		DECCA 80, 100	£8.80
1400, 1500, 1590, 1591	£5.90	GEC 2110 series	£10.60
THORN 1600, 1615, 1690, 1691	£9.15	ITT CVC 5 to 9, CVC20	£9.80
GEC 2000 to 2038 series	£6.80	ITT CVC25, CVC30 series	£8.80
GEC series 1 & 2	£8.00	ITT CVC45	£9.80
INDESIT 20/24 EGB	£7.65	PYE 691-697 (state model no.)	£10.00
ITT/KB VC200, 300	£7.65	PYE 713, 715	£6.80
MURPHY 1910 to 2414 (twin panel)	£5.90	PYE 725 (90P) 731 to 741	£9.20
PHILIPS 170, 210, 300 series	£7.65	PHILIPS G8	£8.80
PYE , INVICTA , EKCO , FERR.		PHILIPS G9	£10.80
368, 169, 569, 769 series	£7.65	PHILIPS 570, 571	£6.80
SPECIAL OFFER		PHILIPS KT3	£9.80
DECCA 20/24, 1700, 2000, 2401	£3.80	THORN 3000/3500 SCAN, EHT	£6.90
GEC 2114/Junior Fireline	£2.80	THORN 8000, 8500, 8800	£12.80
PHILIPS 320	£2.80	THORN 9000 to 9600	£12.90
RBM A823	£4.80	THORN 9800	£19.80
GEC 2028, 2040, 2100	£4.80	THORN TX9	£14.80

OTHERS AVAILABLE, PRICES ON REQUEST. ALSO LOPTS.
TRIPLERS Full range available, Mono & Colour.
Special Offer: Thorn 8000 (2 lead) EHT Tray **£2.80** p.p. 80p.
6-3V CRT Boost Transformers for Colour & Mono **£5.40** p.p. £1.20.
THORN TX10 focus control **£8.80** p.p. 80p.
THORN 8000 mains input choke **£6.80** p.p. £1.40.
CALLERS WELCOME AT SHOP PREMISES
THOUSANDS OF ADDITIONAL ITEMS, ENQUIRIES INVITED
LARGE SELECTION TESTED COLOUR PANELS POPULAR MODELS
TELEVISION MAGAZINE PROJECT PARTS & REPLACEMENTS
STILL AVAILABLE

Telephone 01-794 8751, 794 7346


MANOR SUPPLIES

172 WEST END LANE, LONDON, NW6 1SD

NEAR: W. Hampstead Tube Stn. (Jubilee) Buses 28, 159, C11 pass door
W. Hampstead Brit. Rail Stn. (Richmond, Dalston, Stratford)
W. Hampstead Brit. Rail Stn. (St. Pancras, Bedford)

Access from all over Greater London.

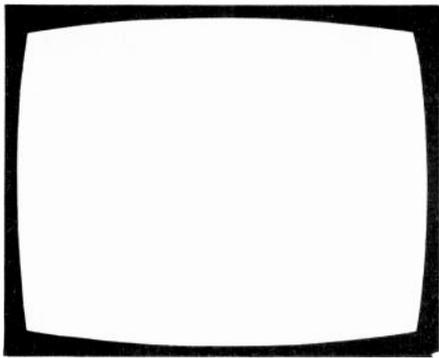Mail Order: **64 GOLDERS MANOR DRIVE, LONDON NW11 9HT**
PLEASE ADD VAT 15% TO ALL PRICES



TELEVISION

September
1985

Vol. 35, No. 11
Issue 419

COPYRIGHT

© IPC Magazines Limited, 1985. Copyright in all drawings, photographs and articles published in *Television* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Television* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

CORRESPONDENCE

All correspondence regarding advertisements should be addressed to the Advertisement manager, "Television", King's Reach Tower, Stamford Street, London SE1 9LS. Editorial correspondence should be addressed to "Television", IPC Magazines Ltd., King's Reach Tower, Stamford Street, London SE1 9LS.

SUBSCRIPTIONS

An annual subscription costs £13 in the UK, £15 overseas (by surface mail). Send orders with payment to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex, RH16 3DH.

BINDERS AND INDEXES

Binders (£4.50) and Indexes (45p) can be supplied by the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. Prices include postage and VAT. In the case of overseas orders, add 60p.

BACK NUMBERS

Some back issues are available from the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF at £1.20p inclusive of postage and packing.

QUERIES

We regret that we cannot answer technical queries over the telephone nor supply service sheets. We will endeavour to assist readers who have queries relating to articles published in *Television*, but we cannot offer advice on modifications to our published designs nor comment on alternative ways of using them. All correspondents expecting a reply should enclose a stamped addressed envelope. Requests for advice on dealing with servicing problems should be directed to our Queries Service. For details see our regular feature "Service Bureau". Send to the address given above (see "correspondence").

this month

- 611 Leader**
- 612 Letters**
Including comments on microcomputer programs, more on the Ferguson 3787 and soft-start for the Philips G8 chassis.
- 617 The Vet's Problem** *Les Lawry-Johns*
On BO and other matters.
- 618 A Visit to MCES** *Steve Beeching, T.Eng.*
MCES now provides a VCR head drum reconditioning service. Steve's visit to see what's involved reveals much about the intricate business of head alignment.
- 620 TV Fault Finding**
Reports from Mick Dutton, Larry Ingram, Keith Hamer and Garry Smith
- 621 Approaches to TV Servicing** *S. Simon*
Quick steps that will remedy most fault conditions on the ITT CVC800/CVC801 series chassis and the Thorn 3000 through to the 9800 chassis.
- 623 Next Month in Television**
- 624 An Approach to Adding Teletext** *Keith Cummins*
How to assess a set's suitability for adding teletext reception facilities, with practical details on converting the Sony Model KV1820UB to provide teletext. In addition to a teletext interfacing circuit there's a simple remote channel change circuit and a sound mute system.
- 634 VCR Clinic**
Fault reports from Derek Snelling, Eugene Trundle, Les Grogan and Hugh Allison.
- 636 The Lid off Microcomputers, Part 5** *Mike Phelan*
This time a look at disc drive systems and printers.
- 638 Teletopics**
News, comment and developments.
- 640 A Case of Liquid Spillage** *Nick Lyons*
VCRs are often written off due to the damage caused to the innards by liquid spillage. It was possible to restore this Sharp machine to normal, reliable operation however.
- 641 A Variable Stabilised HT Supply** *Gordon Haigh*
An external regulated supply that can be set to give a variable h.t. output to suit different chassis is a useful aid to fault diagnosis. The design is based on the thyristor circuit used in the Philips G8 chassis.
- 642 Long-distance Television** *Roger Bunney*
Reports on DX conditions and reception and news from abroad. June 1985 was remarkable for SpE reception.
- 645 Service Bureau**
- 646 Test Case 273**

OUR NEXT ISSUE DATED OCTOBER WILL
BE PUBLISHED ON SEPTEMBER 18

P. V. TUBES

HAVE MOVED

Just phone
your order
through, we
do the rest.

Buy with



Telephone: Accrington (0254) 36521
Accrington (0254) 32611
Telex: 635562 Griffin G (For P.V.)

SUPPLIERS
OF TELEVISION COMPONENTS

104 ABBEY STREET, ACCRINGTON, LANCBS BB5 1EE.

TRADE COUNTER OPEN MON-FRI 9 a.m.-5 p.m. SAT 9.30 a.m.-5 p.m. TRADE COUNTER CLOSED WEDNESDAY p.m.

VARICAP TUNERS		SWITCHES & ACCESS		DID YOU KNOW WE'VE GOT LOTS OF NEW THINGS!		PHILIPS KT3 SPECIFICS		SPECIFIC COMPONENTS		
ELC1043-05	8.40	On/off gen. purpose 4A	75	Decca speaker 8R	3.75	KT3 posistor	1.50	Philips G8 knobs sm/g	50	
ELC1043-06	8.40	G8 on/off	1.38	B+K tube bases Dymascan		Mains electrolytic 225/25 380V	2.50	90° transductor	2.60	
ELC2003	16.50	G11 on/off	1.58	No. 3	9.50	Selector unit Mod. 933	13.42	Thom 1591 speakers sm	6.20	
Philips G8/G9	10.50	G11 on/off remote	1.58	No. 5	9.09	On/off switch Mod. 933	3.20	Thom 1591 speakers lg	6.20	
Philips G11 (U321)	8.50	Gen. purpose rotary	6.66	No. 6	11.08	Luminance chroma panel	24.00	Thom 1500 controls	59	
U322	7.20	Thom Tx 9/10	1.96	No. 8	10.08	2003 IF module	14.95	390K frame 470K line contrast 1k5	each	
U341	9.50	GEC 2040	0.08	No. 13	11.11	U321 IF module	13.50	Focus control Thom/GEC	2.95	
Rank T20	13.00	Thom 1591 push on/off	2.90	No. 14	16.63	R.G.B. panel	10.30	Thom 9000 focus unit	5.95	
PUSH BUTTON ASS.		Rank tuner buttons	35	L5 7"x3 3/4" speaker	4.25	Sound panel	8.50	Thom 8500 focus unit	4.00	
Decca 4 way	6.88	Rank drive cams	15	C15 computer cass.	30	Power panel	10.60	Thom Tx10 focus cont.	9.75	
6 way	7.50	GEC 2110 tuner neons	20	C20 computer cass.	33	Mains input panel	14.30	Decca bridge trans.	1.97	
GEC 2110 6 way	7.98	Thom 3500 A1 beam	70	5 1/4" floppy disc s/s s/d	1.61	Line sync panel	10.20	Decca 30 width cont.	1.97	
GEC Slim 6 way	6.50	GEC 2110 A1 cont. R/B/G	58	15R fused res. G9	55	Mark II chroma panel	16.50	Decca 2M2 HT cont.	25	
GEC/ITT/PYE 7 way	14.50	ITT CVCS on/off	1.24	G11 line in coil	2.95	Sound module	8.50	Rank T20 focus cont.	4.95	
Pye 4 way (713/15)	9.00	ITT mains switch + solenoid	4.50	G11 pot G2 R.G.B.	5.00	LOPT	9.70	Pye 731 HF choke	6.50	
Pye 6 way (207/715)	16.00	Rank mains switch + solenoid	4.50	G11 line scan panel	54.00	Focus unit	3.50	Delay lines DL20, DL60, DL700, DL50	37.50	
Pye 697 repair kit	9.00	Rank T20 on-off switch	1.95	G11 power panel	37.50	Infra Red Teletext remote hand set	18.87	CRT tube base	1.40	
Pye 725-735	11.00	EAGLE MULTIMETERS		G11 bridge trans.	97	K30 SPECIFICS		EHT final anode cap	53	
Pye 725-735 with tuning head	14.60	KEW 7N	7.50	G11 EW correc. coil	1.95	K30 LOPT	17.50	6.3V CRT boost trans.	5.80	
Philips G8 (early)	15.50	KEW 14	9.95	G11 final anode lead	1.50	K30 focus unit	2.90	Focus rod	1.25	
Philips G8 (late)	13.90	KEW 20	14.50	G11 focus unit	5.80	K30 EHT lead	8.30	Focus holder	2.80	
Rank A823	10.75	EM5	11.95	G11 39R 3W resistor	60	K30 EHT lead	2.90	AFC unit G8	8.00	
Rank T20A	9.75	EM20A	15.95	G11 RGB 10G diodes	50	Selector unit 1002 (early)	11.20	IF gain module	9.00	
Hitachi 4 way	10.75	EM10	13.95	Televetra up converta	37.20	TMS 1000 panel 1234	13.00	C.O.A. panel	20.00	
Philips G11 unit	26.50	MM150	31.25	G11 47K pot plus switch	65	Euro decoder panel 1234	46.00	G8 rear convy. panel	23.00	
Philips KT3	14.50	MM100	44.50	Dynascan	399	Power supply 1234	23.50	Philips K35 Tuner drawer	10.00	
Philips KT30	10.30	MM150	21.50	SUNORY EQUIPMENT		A1 gun switches	70	PLUGS AND SOCKETS		
ITT CVC 8/9 (mod)	12.00	MM120	89.00	Test Lead Set	4.20	On/off switch	2.60	5 pin DIN plugs 180°	20	
ITT 6 way with VCR	8.90	MM150	89.00	Degaussing Coil Stick	17.00	Selector unit 1002 (late)	9.90	5 pin DIN chassis sockets 180°	28	
Thom 9000 switchback	5.30	T1206 intercom	8.50	Signal Injector	4.00	Hand set 1201	16.00	5 pin DIN line sockets 180°	28	
Decca 7 way piano key replacement kit	19.50	MMC100	21.95	Elect. Circuit Tester	1.50	Hand set 1234	16.00	5 pin DIN plugs 360°	28	
SERVICE AIOS		TS350	25.00	5A Choc Bloc (12)	40	Diode ZTX 33B	90	5 pin DIN chassis sockets 360°	28	
SERVISOL Freeze-It	1.14	ANTEX SOLDERING EQUIPMENT		Fuse Wire 5A, 15A, 30A	05	DL 20 delay line	2.20	5 pin DIN line sockets 360°	28	
SERVISOL Foam Cleanser	96	CS15W Iron 240V	6.20	4-way 13A Mains Conn.	5.00	Solda Mop Stnd.		74		
SERVISOL Plastics Seal	1.08	C240 Element	2.75	Safe Block (mains)	8.50	Sidcutters sm.	1.20	7 pin DIN plugs	35	
SERVISOL Silicone Grease	1.20	Bits 102	1.10	13A Plug Top (box 10)	4.80	Long Nose Pliers	1.20	7 pin DIN chassis sockets	36	
SERVISOL Tubes Silicone Grease	1.64	Bits 106	1.10	Probes (x10)	10.90	SM Torch	42	8 pin DIN plugs	36	
SERVISOL Aero Klene	90	Bits 820	1.10	Probes (x1)	10.90	Quick Set Adhesive	75	8 pin DIN chassis sockets	64	
SERVISOL Aero Duster	1.20	Bits 821	1.10	Bell Wire (100m)	10.90	Sg. Neon Screwdriver	40	8 pin DIN line sockets	55	
SERVISOL Excol Polish	92	CS17W Iron 240V	6.40	Mains Cable (circular 100m) (2 core)	5.00	Lm. Neon Screwdriver	65	Phono plugs	12	
SERVISOL Video Head Cleanser	86	CS240 Element	2.75	(3 core)	10.75	Min. Screwdrivers	15	Phono chassis sockets	10	
Super 40	1.14	Bits 1100	1.10	Factory recon. Avo meters	74	I.C. Inserters	1.18	Phono line sockets	20	
Fire Extinguisher 640G	2.86	Bits 1101	1.10	Avo Batteries	2.95	Automatic Wire Strippers	5.95	2.5mm Jack plugs	11	
Heat Sink Compound 25G	1.08	Bits 1106	1.10	Vero Board	2.59	Scarf Leads	2.95	2.5mm Chassis sockets	14	
Silicone Rubber Tube 110G	2.98	XS25W Iron 240V	6.50	Isolating trans. 500vA 240V	40.00	Scarf Leads	3.50	2.5mm Line sockets	17	
Solda Mop standard reel		XS240 Element	2.75	Solder 500g	7.00	TA51 Car Battery Leads/port. TV Thom 1690/91	4.47	3.5mm Jack plugs	24	
ELECTROLUBE PRODUCTS		Bits 50	1.10	D.I.Y. Solder	45	TA51 Car Battery Leads/port. TV Thom 1613/1615	3.66	3.5mm Stereo chassis sockets	18	
Electrolube Adhesive	62	Temp. Controlled		Solder Sucker	6.50	Car Battery Leads/port. TV Philips	3.95	3.5mm Stereo line sockets	28	
Electro-Mech lubricant	1.49	30W Iron CSTC	16.95	Nozzles	81	Universal Car Accessory Cable	1.99	3.5mm Stereo jack plugs	36	
Elect. cleaning solvent	1.62	40W Iron XSTC	16.95	Trim Tools		DATA BOOKS (Zero VAT)		6.3mm Stereo jack line sockets	25	
Freezer	1.49	Unit for above TCSU1	68.95	Plastic	16	Pair of A-Z/2N2S TVT80	8.50	Standard mono jack plugs	20	
Foam cleanser	1.12	Stand	2.10	Metal End	30	LIN IC Books (data only not equiv.)	5.95	Loud speaker plugs 2 pin	10	
Heat transfer compound	1.14	MLXS Auto Repair Kit	8.40	OFFICIAL ORDERS ACCEPTED FROM SCHOOLS, LOCAL AUTHORITIES ETC.		LIN1	9.95	I.D.C. plugs 36 conn.	5.90	
Silicone compound	1.94	WELLER		WE HAVE A FULL RANGE OF AERIALS AND ACCESSORIES FROM TRADE COUNTER AERIAL EQUIPMENT		2M Fly Lead	70	I.D.C. sockets 36 conn.	6.90	
Special contact fluid (Snorkell)	3.20	Heat gun	12.00	Outdoor Splitter	5.50	4M Fly Lead	1.20	8NC plugs	1.15	
Permagard	1.52	Heat gun tips (pair)	57	Plastic Tape	50	10M Fly Lead	1.90	Coax plugs Each 18p Pack of ten	1.80	
Elec. mech. lubricant pen	74	3/16" Iron tips 25W (MT5)	57	F.M. Plugs	25	Figure 8 Mains Lead	62	Line connectors	16	
VIDEO		LABGEAR		Set Top Aerial	2.30	Computer to TV	97	Coax female plugs	120	
Video care kits	3.50	CM7261 Power Unit 12V	11.24	Loop Aerial	1.00	Figure 8 Mains Lead	62	Double ended female sockets	18	
VHS E30 video tape	3.06	CM7262 Reg. Power Unit 12V	12.25	Moop Amp/Power Unit WB	18.00	Reducers for the PL259	16	FM plugs	25	
VHS E60 video tape	4.00	CM7060 MHA 10db 12V W/B	9.86	Aerial Isolator Kit	2.08	CASSETTE DRIVE BELTS		35m 35	46mm 37	57m 37
Scotch E120 video tape	5.00	CM7065 VHF/UHF MHA W/B 12V	14.34	Attenuator 6dB, 12dB, 18dB	1.80	35m 35	46mm 37	57m 37		
E180 video tape	4.50	CM7066	13.38	27MHz Filter 50dB	2.10	66m 39	110m 59	76m 43		
Beta L500 video tape	4.90	CM7067 UHF 12V MHA (Specify A-B or C/D)	10.72	Cable Clips 7mm	per 100 1.18	90m 43				
Beta L750 video tape	5.80	CM7068 UHF 12V MHA High Gain (Specify A-B or C/D)	15.95	Single Outlets	80	SHEILA'S SURPRISES		SHARP VIDEO HEADS £55		
VCC 240	6.20	CM7053 Behind Set UHF Amp. (Mains)	13.01	Surface Splitter	1.70	VC2300	£55	We are now stocking a range of Thom New Life tubes. Please ring for prices and carriage costs.		
VCC 360	8.30	CM7054 Behind Set UHF Amp. (Battery e.g. Caravans)	10.42	A Splitter	70	VC6300				
VCC 480	10.21	CM7043 Second Set Amp. UHF	12.12	100M Coax	15.00	VC7300/7700/7750				
Philips LVC 1700 1200	15.10	CM7093 Behind Set UHF Amp. 3 Sets	15.27	Coax Plugs	per 10 1.80	VC8300				
VIDEO HEADS		CM7063 Dist. Amp. VHF/UHF 17db/output 12V	22.17	1" U Bolts	30	VC220/381/383/388/9100/9300/9500				
3HSS VHS	32.50	CM7108 VHF/UHF 8+1 Dist. Amp.	43.26	J Bolts	25	VC3300/9700				
4HSS VHS	32.80	CM9700 27mhz CB Suppress.	4.05	ANTIFERENCE		VTC 9300/9500				
PS3B Beta/Sony	42.00	CM6011 Outdoor Splitter (2 way) W/B	7.63	SB11 Splitter	2.37	VTC 5300/5000				
VIDEO RECORDER HEADS		CM9003 Flush Single Outlet	1.47	COB11 Outlet	96	VTC 5350				
Philips V2000	57.00	CM9010 Flush Twin Outlet	1.95	CS1000 Combiner/Splitter	6.15	VTC 5500				
Philips 1700	57.00	CM9034 UHF Group Filters with CD	7.69	PU1240 Power Unit	11.65	VTC 9350				
Video lamps	1.30	CM7042 TV Games Combin.	2.95	UP1300 MHA	9.09	REMOTE CONTROL HAND UNITS				
3V23 Cassette Lamp with plug	1.95	CM9009 Flush TV/FM Outlet	3.05	XS2U Xtraset	14.56	Decca 100/101 Ultra Sonic Non Teletext	£23.80			
VIDEO DRIVE BELT KITS		CM7091 Col. Bar Gen.	121.80	4 way VHF/UHF Amp	40.71	Grundig Telepilot 12 Series Infra Red	£13.87			
JVC HR3330/3600	4.50	CM9006 VHF/UHF Diplexer	3.60	6 way VHF/UHF Amp	50.68	Grundig Telepilot 8 Series Infra Red	£25.10			
JVC HR3360/3660	4.50	STATIONERY		X8 High Gain Aerial A-B-CD-WB	17.10	Grundig Telepilot 160 Series Infra Red	£18.87			
JVC HR7650	4.50	Service Call Pad (100)	1.99	REMOTE CONTROL TESTER £29.94		Grundig Telepilot 300 Infra Red	£18.87			
Panasonic NV300	4.50	Repair Ticket (100)	3.90			Philips KT3/K30 Infra Red Non Teletext	£18.87			
Panasonic NV7000	4.50	Job Card (100)	2.50			Philips G11 Ultra Sonic Non Teletext	£22.00			
Sony SLC7/SLJ7	4.50	Rental Payment Card (50)	3.50			Philips G11 8 Way Infra Red Teletext	£23.80			
Sony SL8000/8080	4.50	H.P. Agreements (100)	3.50			Philips G11 Ultra Sonic 31 buttons	£27.00			
Toshiba V7540	4.50	Maintenance Agreement (100)	3.50			Philips G11 Ultra Sonic 2 function	£21.00			
Ferguson HR3330/3600	4.50	Rental Agreements (100)	3.95			Thom TX10/JVC Infra Red Teletext	£16.87			
Video head cleaner	86					Philips KT3 Infra Red Teletext Remote Hand Set	£18.87			
Sanyo video motor	20.00									
AUDIO HEADS AND MOTORS										
Mono record/playback	4.32									
Stereo playback	4.79									
Stereo record/playback	4.99									
Stereo record/playback (Dolby)	6.90									
Mono/stereo erase	2.25									
Electronic/rotation clockwise motors										
6V MD6515	4.95									
9V MD9516	4.95									
12V MD12517	4.95									

TEL: 0254 36521/32611
104 ABBEY STREET, ACCRINGTON

P. V. TUBES

T.T.L. 74LS SERIES

74LS00	58	74LS37	35	74LS92	65	74LS160	90	74LS245	2.30
74LS02	58	74LS38	35	74LS93	60	74LS161	85	74LS251	65
74LS03	58	74LS40	35	74LS107	80	74LS162	4.04	74LS253	95
74LS04	58	74LS42	80	74LS109	58	74LS163	85	74LS257	1.20
74LS05	58	74LS47	85	74LS112	50	74LS164	85	74LS258	95
74LS08	58	74LS48	83	74LS113	44	74LS165	1.50	74LS259	1.70
74LS09	58	74LS49	33	74LS114	70	74LS173	1.32	74LS273	1.90
74LS10	58	74LS51	33	74LS123	80	74LS174	85	74LS283	1.30
74LS11	58	74LS54	43	74LS125	85	74LS175	85	74LS293	1.20
74LS13	37	74LS55	60	74LS126	60	74LS191	1.02	74LS352	1.40
74LS14	46	74LS73	60	74LS132	63	74LS192	1.30	74LS353	1.40
74LS15	33	74LS74	65	74LS138	83	74LS193	1.30	74LS365	75
74LS20	35	74LS75	65	74LS139	65	74LS194A	75	74LS366	82
74LS21	35	74LS76	65	74LS151	85	74LS197	95	74LS367	1.65
74LS22	35	74LS78	65	74LS153	85	74LS240	2.20	74LS368	65
74LS26	44	74LS83A	89	74LS155	65	74LS241	2.20	74LS373	1.40
74LS27	35	74LS86	99	74LS156	1.02	74LS242	2.20	74LS374	1.55
74LS30	35	74LS85	38	74LS157	78	74LS243	2.20	74LS393	1.20
74LS32	90	74LS90	1.22	74LS158	65	74LS244	2.20	74LS670	1.78

VOLTAGE REG.

7805	78
7806	78
7808	78
7812	78
7815	78
7818	78
7824	78
78L05	68
78L08	68
78L12	68
78L24	68
7905	98
7906	98
7908	98
7912	98
7915	98
7918	98
7924	98
79L05	72
79L12	72
79L15	72
79L24	72

NEW VALVES

30FL2	1.70	EF183	99	PCF200	1.35	PL504	1.65
DY802	98	EF184	1.39	PCF800	1.38	PL508	2.90
ECC81	1.08	EL34	3.50	PCF801	1.13	PL509/19.5	30
ECC82	98	EL84	1.25	PCF805	1.02	PY88	81
ECC83	1.07	EY86/7	68	PCF806	1.30	PY800/1	69
ECC84	80	EY500A	2.25	PCF808	1.63	UCH81	2.25
ECC85	98	EZ80/1	56	PCH200	1.45	UCL83	1.82
ECC88	1.35	GY501	1.45	PCL82	1.20	UY85	1.35
ECF80	1.30	GZ34	3.50	PCL84	1.20	PL802T	4.00
ECF82	88	KT66	8.50	PCL86	92	40KD6	5.30
ECH81	1.60	KT77	8.50	PC1805	2.09	21LU8	3.00
ECH84	1.66	KT88	12.00	PD500	2.93	17DW4A	1.60
ECL80	84	PC92	3.00	PFL200	1.86	3AT2B	5.00
ECL82	1.30	PC97	1.65	PL36	1.87	12BY7A	3.75
ECL86	1.99	PCC85	85	PL81	94	12HG7	3.20
EF80	95	PCC805	1.40	PL83	1.43		
EF86	1.96	PCF80	1.00	PL84	84		

MAINS DROPPERS

DECCA 20	2.48
DECCA 27R/47R	1.40
DECCA 56R/68R	1.40
R.B.M. A823 56R/68R	94
R.B.M. 161	82
GEC 2000/2018	70
GEC 27840	64
PYE 725/31 3R0/56R/27R	1.84
PYE 725 56R/27R	1.04
PHILIPS 210/5050 30R/125R/2K85	1.75
PHILIPS 210/5051 -118R/148R	93
PHILIPS G8/5081 47R Section	90
PHILIPS G8/5083 2R2/68R	95
THORN 1400	1.20
THORN 1500	1.38
THORN 1600	1.77
THORN 3500	94
THORN 8000	1.24
THORN 8500	1.36
THORN 9800	1.30
DECCA 2R5	96
DECCA 3R9 Modulohm	60

CRYSTALS & FILTERS

6Mhz	74
5.5Mhz	74
4.3Mhz	1.30
8.8Mhz	1.30
9.94Mhz	6.00
10.692Mhz	6.00

MULTITURN POTS

100K	55
GEC TCE	55
PHILIPS G8	
DECCA, RANK	55

THERMAL CUT OUT

THORN 3000 2A Metal	2.20
GEC 2040 Metal	2.50

L.E.D.'s

5mm Red, Green, Yellow	14
T1 1/4 Amber	22
T1 3mm Red, Green, Yellow	14
Flashing Red CQX21	62
CQX22	66
Panel Clips 3mm	4
5mm	4

DISC CERAMIC CAPS

8kv (12kV)	
39pF, 200pF	
150pF, 220pF	
180pF, 250pF	
63V/100V	
A range of pref. values 22pF-4700pF	12p

POLYESTER CAPS

250V 0.01mF	12p
0.1mF	
0.22mF	
400V 0.01mF	12p
0.1mF	
0.22mF	

TANTALUM CAPACITORS

6.3V	47mF	42
	100mF	90
16V	10mF	22
	22mF	28
	47mF	1.03
25V	22mF	46
35V	0.1mF	13
	0.22mF	13
	0.47mF	13
	1mF	13
	2.2mF	17
	4.7mF	26
	10mF	57

CONVERGENCE POTS

3W/5R-6R-10R-15R-20R	
50R-100R-200R-500R	60

METRIC CONVERGENCE POTS

PHILIPS G8	
5R-10R-15R-20R-50R	60

REPLACEMENT ELECTROLYTICS

PYE 169 (200/200/100/32)	3.74
PHILIPS 320 (400/400/200V)	3.02
DECCA 30 (400/400/350V)	3.74
DECCA 80 (400/350V)	4.37
DECCA 100 (800/250V)	2.53
PHILIPS G8 (600/300V)	2.44
PHILIPS G9 (600/300V)	3.19
PHILIPS G11 (470/250V)	2.97
PYE 691/7 (200/300/350V)	2.55
PYE 731 (600/300V)	1.83
RBM A823 (2500/2500/30V)	3.12
RBM A823 (600/300V)	3.91
RBM Z146 (300/300/350V)	2.20
RR1 T20A (220/400V)	3.28
ITT CVC5/9 (200/200/75/25)	2.20
ITT CVC 20 (220/400V)	2.14
GEC 2110 (600/250V)	1.31
GEC 2040 (1000/2000/35V)	4.51
GEC 2040 (300/300/150/100/50)	3.3
THORN 3500 (400/40V)	2.02
THORN 950 (100/300/100/16/275V)	3.07
THORN 1400 (150/100/100/150/320V)	2.42
THORN 1500 (150/150/100/300V)	35
THORN 1500 (12/300V)	3.06
THORN 3500 (175/100/100/400/350V)	95
THORN 3500 (1000/63V)	95
THORN 3500 (1000/70V)	95
THORN 8000/8500 (2500/2500/63V)	3.72
THORN 8000/8500 (700/250V)	2.55
THORN 8000/8500 (400/350V)	2.82
THORN 9000 (400/400V)	3.61
GEC (200/200/150/50)	2.91
PHILIPS 69 2200/63V	1.38
THORN 4700 P/C 25V	1.32
THORN 1591/1691 4700/25V	1.32
G11 Capacitor 7N5 1500V	1.40

RECTIFIER TRAYS

THORN 950 Mk II	4.25
THORN 1400 3 Stick	5.20
THORN 1500 3 Stick	5.20
THORN 1500 5 Stick	5.29
THORN 1600	4.95
THORN 3000/3500	7.98
THORN 8000	5.28
THORN 8500/8800	7.15
THORN 9000	8.70
DECCA 1730/1830	4.48
DECCA 30	6.76
DECCA 80	6.60
DECCA 100	7.50
UNIVERSAL IIT or REMO	6.00
GEC 2100	7.40
GEC 2200 (20AX)	6.50
GEC 2040/2028	6.60
GEC 2110 Pre Jan '77	7.00
GEC 2110 Post Jan '77	7.00
PHILIPS G8 Short Focus Lead	6.75
PHILIPS G8 Long Focus 550	6.75
PHILIPS G9	6.37
Pye/Philips K3 Tripler	10.65
PYE 691/3	6.58
PYE 713/4 Lead	8.79
PYE 713 Doubler 5 Leac	8.79
PYE 731/725	7.60
R.B.M. A823 (plug in) AV	7.60
KORTING (similar to Siemens TVK1)	6.90
ITT KB CVC5/9	7.32
ITT KB CVC20/25/30 (Mullard)	6.65
RRI T20	6.80
ITT CVC45	8.65

RECTIFIER STICKS

TV11	90	TV18	1.10
TV13	90	TV20	1.23

LINE OUTPUT TRANS.

R.B.M. T20A	13.95
R.B.M. A774 Mono	11.74
R.B.M. Z179	15.00
R.B.M. Z718 22"	19.50
PHILIPS 320	8.70
PHILIPS 210/300 Mono	10.00
PHILIPS G8	8.75
PHILIPS G9	7.75
PHILIPS G11	13.50
PYE 697 (Printed)	14.50
PYE 713/731	10.00
PYE 725 90"	10.50
PYE 169	10.00
DECCA 80/100	8.58
DECCA 1700	9.00
DECCA 1730	8.58
DECCA 2230	8.58
GEC 2110	16.75
GEC 2040	9.50
ITT CVC 1-9	10.85
ITT CVC 25/30/32	8.65
ITT CVC 20	8.60
THORN 3000 EHT	9.95
THORN 3000 SCAN	7.95
THORN 8000	11.33
THORN 8500	11.33
THORN 3000/3500	
Mains	10.00
THORN 1591	8.68
THORN 1691	9.68
THORN TX10	15.00
THORN 1615	9.75
PHILIPS KT3	9.70
RANK BUSHRANGER Early T16A	£10.00
RANK BUSHRANGER Late T18A	£10.00
PYE 741	8.20
B+O (2000, 3000)	12.70
B+O (3000 EHT)	18.90
ITT CVC 45	9.50

FUSES

1 1/4" QUICK BLOW	
100ma	73
250ma-500ma-750ma-1A	60
1.5A-2A-2.5A-3A-5A	60
1 1/4" ANTISURGE	
250ma, 500ma, 600ma, 630ma, 750ma, 850ma,	
1A, 1.25A, 1.5A, 2A	1.70
2.5A, 3A, 5A	2.70
20mm ANTISURGE	
80ma	4.80
100ma	2.50
160ma, 200ma	2.20
315ma, 500ma, 630ma, 800ma, 1A, 1.25A, 1.6A,	
2A	1.30
2.5A, 3.15A, 4A, 400ma, 5A	1.90
20mm QUICK BLOW	
100ma, 250ma, 500ma, 630ma, 800ma	90
1A, 1.25A, 1.6A, 2A, 2.5A, 3.15A, 5A	60
1" MAINS	
2A, 3A, 5A, 10A, 13A	1.00

NEW MONO TUBES

MULL. A31/510 110" 12"	18.50
MULL. A34/510 110" 14"	20.00
A50/120WR 110" 20"	18.50
A61/120WR 110" 24"	20.50
VEGA 12" 90" (Jap Types)	15.00

MULLARD COLOURX*

18" A47/343X	59.00
19" A49/120X	53.00
20" A51/110X	53.00
22" A56/120X	46.00
25" A63/200X	55.00
26" A66/120X	65.00
26" A67/120X	65.00
22" A56/500X	60.00
A51 570X	72.00
A56 510	67.00
A66 510	92.00

WHILE STOCKS LAST NEW TUBES

ATX 56-001	95.00
ATX 51-00X	95.00
A56/610	95.00

REBUILT COLOUR TUBES

ALL AVAILABLE EX-STOCK ON GLASS FOR GLASS EXCHANGE FROM TRADE COUNTER. SOME TYPES AVAILABLE WITHOUT EXCHANGE FOR SMALL GLASS CHARGE

17" A44/271X	32.00
18" A47/342X (Low Focus)	32.00
18" A47/343X (Std Focus)	32.00
20" A51/110X	30.00
19" A49/120X	30.00
22" A56/120X	30.00
22" A55/14X	30.00
25" A63/200X	34.00
26" A66/120X	34.00
26" A67/120X	34.00
22" A56/140X (410X) 110"	36.00
26" A66/140X (410X) 110"	36.00
20" A51/161X	60.00
22" A56/510X	50.00
A56 540X	89.00
A66 540X	75.00
A66 500X	64.00

P.I.L. TUBES - we can rebuild your own glass - please ring for quotes. Carriage cost on tubes £10 + VAT

SKELETON PRE-SET POTS

Standard or miniature	
Horizontal or Vertical	
100R-2M2	16p

WIREWOUND RESISTORS*

4W 1R-10K	24p
7W 1R-22K	26p
11W 1R-22K	29p
17W 1R22K	32p

(Preferred values)*

SLIDER POTENT

P. V. TUBES

PLEASE NOTE OUR NEW ADDRESS - COME AND SEE US
 104 ABBEY STREET, ACCRINGTON, LANCBS BB5 1EE.
 Tel: 0254 36521/32611 Telex: 635562 Griffin G (For P.V.)

HOW TO ORDER

ADD 75p per order P+P Goods are despatched on the day we receive your order. If for any reason we are out of stock we will try to inform you as quickly as possible. We try our best to give a speedy, fair and efficient service. V.A.T. (U.K.). Export orders charged at cost. First Class Mail is used whenever possible. Add 15% VAT to total except where it states zero rate.

SEMICONDUCTORS

AC107	35	BC558	9
AC126	30	BCY72	13
AC127	32	BD115	45
AC128	32	BD116A	65
AC128K	40	BD124P	79
AC141K	39	BD131	50
AC142K	38	BD132	49
AC176	35	BD133	35
AC176K	35	BD135	38
AC186	41	BD136	38
AC187	38	BD137	38
AC187K	38	BD138	35
AC188	35	BD139	35
AC188K	39	BD140	44
AD143	82	BD144	1.70
AD161	54	BD150	60
AD162	54	BD159	65
AD161/62 MP	1.15	BD166	52
AF106	49	BD179	70
AF114	89	BD182	1.20
AF118	1.20	BD183	75
AF121	75	BD201	85
AF124	48	BD202	91
AF125	46	BD203	80
AF126	46	BD204	99
AF127	58	BD222	46
AF139	58	BD223	56
AF178	1.54	BD225	47
AF239	60	BD232	68
AL102	4.90	BD233	60
AJ106	2.50	BD234	63
AJ113	5.20	BD235	60
BC107	20	BD236	65
BC108	20	BD237	57
BC109	20	BD238	65
BC114	17	BD243	85
BC115	17	BD244	85
BC116A	16	BD410	79
BC117	30	BD434	74
BC118	24	BD437	86
BC119	36	BD438	94
BC139	28	BD507	52
BC140	32	BD508	55
BC141	26	BD509	56
BC142	30	BD510	60
BC143	31	BD278A	81
BC147	13	BD517	60
BC148	9	BD520	75
BC149	12	BD535	82
BC157	16	BD536	91
BC158	16	BD969A	1.49
BC159	15	BD697	1.24
BC160	52	BD695	1.39
BC161	28	BD698	1.90
BC170B	15	BD707	1.50
BC171	15	BDX32	2.10
BC172	15	BF115	3.0
BC173	12	BF117	3.6
BC174	10	BF125	26
BC177	27	BF127	47
BC178	26	BF154	23
BC182L	9	BF158	18
BC183L	12	BF160	27
BC184L	14	BF167	24
BC186	35	BF173	22
BC187	25	BF177	52
BC204	10	BF178	46
BC208	13	BF179	28
BC209	10	BF180	29
BC212	9	BF181	39
BC212L	13	BF182	36
BC213	13	BF183	29
BC214	10	BF184	36
BC237	14	BF185	36
BC238	14	BF194/394	36
BC251A	18	BF195	16
BC252	12	BF196	16
BC261	18	BF197	16
BC262	18	BF198	16
BC300	50	BF199	21
BC301	53	BF200	25
BC303	33	BF224	25
BC307	20	BF225	20
BC308	25	BF241	25
BC323	99	BF256	55
BC327	18	BF257	28
BC328	18	BF258	25
BC337	18	BF259	35
BC338	18	BF262	84
BC461	30	BF263	75
BC547	13	BF271	24
BC548	13	BF273	24
BCX32 = BC637	39	BF274	24
BC549	8	BF336	46
BC550	7	BF337	31
BC557	8	BF338	41

BF355	56	R2265	1.50
BF362	68	R2322	62
BF363	72	R2323	67
BF371	30	R2461	1.50
BF392	35	R2540	2.80
BF422	34	RC4558	2.20
BF423	46	RCA16334	90
BF435	35	RCA16029	99
BF457	35	RCA16039	99
BF458	43	RCA16092	99
BF460 = BF462	46	RCA16040	96
BF469	86	RCA16041	84
BF470	66	RCA16334	90
BF597	10	RCA16335	90
BF597	10	RCA16957	2.88
BF597	10	TIC45	60
BF597	10	TIC46	60
BF597	10	TIL32	65
BF597	10	TIL78	48
BF597	10	TIP29C	43
BF597	10	TIP29C	43
BF597	10	TIP30A	47
BF597	10	TIP30C	43
BF597	10	TIP30E	43
BF597	10	TIP31C	55
BF597	10	TIP32C	42
BF597	10	TIP33B	75
BF597	10	TIP34B	60
BF597	10	TIP41C	47
BF597	10	TIP42C	50
BF597	10	TIP47	70
BF597	10	TIP120	65
BF597	10	TIP2955	90
BF597	10	TIP3055	63
BF597	10	TIS91	21
BF597	10	TU106/02	1.80
BF597	10	TN696	21
BF597	10	TN918	82
BF597	10	TN2904	51
BF597	10	TN2905	28
BF597	10	TN3054	60
BF597	10	TN3055	60
BF597	10	TN3702	11
BF597	10	TN3703	10
BF597	10	TN3705	10
BF597	10	TN3706	10
BF597	10	TN3708	17
BF597	10	TN5294	48
BF597	10	TN5296	48
BF597	10	TN5298	69
BF597	10	TN5337	1.86
BF597	10	TN5496	53
BF597	10	TN6107	75
BF597	10	TN6109	81
BF597	10	TN715	1.98
BF597	10	TN2495	1.10
BF597	10	TN2496	1.31
BF597	10	TN2497	1.50
BF597	10	TN2498	1.72
BF597	10	TN2499	1.67
BF597	10	TN2500	1.68
BF597	10	TN2501	2.57
BF597	10	TN2502	2.90
BF597	10	TN2503	1.44
BF597	10	TN2504	1.82
BF597	10	TN2505	2.50
BF597	10	TN2506	2.90
BF597	10	TN2507	1.34
BF597	10	TN2508	2.73
BF597	10	TN2509	2.73
BF597	10	TN2510	2.20
BF597	10	TN2511	2.20
BF597	10	TN2512	2.20
BF597	10	TN2650	2.20

TRADE ANNOUNCEMENT

**FERGUSON
3V16/3V22
VHS VIDEOS**

**THORN
8800/9000/9600
COLOUR TV's**

MAINLY REMOTE CONTROL
HAND UNITS NOW AVAILABLE

**MINIMUM PURCHASE 5 UNITS
LOWEST PRICES IN U.K.**



**OTV TRADE DIVISION
OTV HOUSE
144 LEA BRIDGE ROAD
LONDON E5 9RB**

Telephone: Bob Munson 01-985 6111

CENTRAL T.V. & VIDEO WHOLESALE

The No. One for late model T.V. & Video's at the lowest prices can now offer soft touch & remote video records at very cheap prices.



★ ★ ★ SPECIAL OFFER THIS MONTH ★ ★ ★

22" Stereo-Text Brand New in Box £270

14" Portable Brand New in Box £110



Working C.T.V.

Philips G11 660 22" £45
 Philips G8 550 22" £20
 Thorn 9000 £35
 Thorn 8800 £25
 Thorn 8500 £22



Untested C.T.V.

Philips G11 660 22" £35
 Philips G8 550 22" £9
 Thorn 9000 £20
 Thorn 8800 £15
 Thorn 8500 £13

Special price on Decca Solid State Untested from £20



PRICES BASED ON QUANTITY AND EXCLUSIVE OF 15% VAT



Large stocks of B. Grade T.V. & VIDEO
 20"-22" TEXT, 20"-22"-26" REMOTE, 14" PORTABLE

Many more bargains in stock. Phone and have your order ready for collection, lorry loads direct from sources. Delivered to your door. All sets have first class cabinets.

HOTE LINE LONDON

01-807 4090

01-884 1314

CEDAR HOUSE, NOBLE RD.,
 ELEY ESTATE,
 EDMONTON, LONDON

HOT LINE

0291-271000

UNITE 4

BULWARK INDUSTRIAL ESTATE,
 CHEPSTOW,
 GWENT

WE WILL ONLY SUPPLY TOP QUALITY, BRANDED COMPONENTS. REPUTATION COUNTS WITH US

G.G.L. COMPONENTS
108 SCOTLAND ROAD, CARLISLE, CUMBRIA CA3 9EY
PHONE (0228) 20358/39693

BUY WITH



E.H.T. TRAYS

DECCA 80	7.20
DECCA 100	7.35
ITT CVC 20/30	6.85
PHILIPS G8-550	7.90
PHILIPS KT3	9.75
RBM 8500/8800	7.50
THORN 9000	8.70
Universal	5.95

INTEGRATED CIRCUITS

TYPE	PRICE (£)
AN214	1.95
AN301	3.45
AN303	3.45
AN305	3.50
AN7110	1.93
AN7114E	2.33
AN7115E	2.37
AN7116	2.35
AN7145	3.25
BA312	1.25
BA511A	1.95
BA521	1.85
BA532	1.95
BA536	2.55
HA1166	2.65
HA1322	2.10
HA1338	2.78
HA1339	2.40
HA1342A	2.20
HA1366 W/W/R	1.95
HA1370	2.75
HA1374	2.45
HA1377	3.80
HA1388	4.20
HA1397	3.90
LA1201	1.75
LA1203	2.30
LA1365	2.45
LA3350	1.65
LA4031	2.45
LA4032	2.30
LA4101	1.50
LA4102	1.95
LA4400	2.50
LA4430	2.45
LA4440	3.55
LA4460	2.95
LA4461	2.95
MB3712	2.30
MB3713	2.25
ML231B	2.35
ML232B	2.55
ML237B	2.50
ML238B	4.22
SA1124	3.45
SA1125	4.70
SA1150	3.85
SA1251	4.95
SA1501	5.10
SA5012	5.70
SAF1032P	3.25

TYPE PRICE (£)

SAF1039P	4.55
SAS560S	1.95
SAS570S	1.95
SAS580S	2.40
SAS590S	2.40
SL901	5.65
SL907	7.35
STK0039	6.45
STK0040	5.95
STK0050	7.50
STK077	7.25
STK078	7.45
STK082	9.75
STK415	9.66
STK435	7.75
STK433	6.50
STK435	6.75
STK437	7.25
STK439	7.55
STK441	8.50
STK459	7.35
STK461	7.95
STK463	9.30
STK465	9.95
TA7193P	4.30
TA7202	2.25
TA7203P	2.25
TA7204P	1.90
TA7205AP	1.40
TA7208P	1.95
TA7222AP	1.85
TA7223P	2.85
TA7227P	2.95
TA7310	1.55
TA7313	1.45
TA8A550	.43
TBA120AS	.95
TBA120SB	.90
TBA120T	1.25
TBA120U	1.00
TBA520	1.30
TBA540	1.37
TBA550	2.45
TBA560	1.60
TBA720A	2.65
TBA725A	2.45
TBA800	.80
TBA810	1.35
TBA820	1.40
TBA890	2.95
TBA920	1.50
TBA950	2.65

TYPE PRICE (£)

TCA270	1.55
TCA800	5.45
TCA940	1.55
TDA1002	1.50
TDA1003	2.80
TDA1006A	2.95
TDA1035T	2.75
TDA1037	1.95
TDA1044	3.10
TDA1170	1.80
TDA1270	2.20
TDA2002	1.85
TDA2003	2.33
TDA2004	3.15
TDA2006	2.25
TDA2020	2.95
TDA2190M	4.95
TDA2522	1.80
TDA2523	2.25
TDA2530	2.10
TDA2532	2.20
TDA2540	1.95
TDA2560	1.80
TDA2581	2.15
TDA2582	2.20
TDA2591	2.30
TDA2593	2.30
TDA2594	2.95
TDA4500	5.85
TDA2600	5.95
TDA2611A	1.50
TDA2640	2.40
TDA3560	5.10
TDA3561A	5.35
TDA3562A	5.50
TDA4600	2.85
TDA9503	2.35
UPC555C	.70
UPC566C	2.10
UPC585C	1.40
UPC1031H	2.95
UPC1032H	.95
UPC1156H	2.45
UPC1181H	2.20
UPC1182H	2.20
UPC1185H	3.30
UPC1230H	3.95
UPC1238H	2.35
UPC1350C	4.50
UPC1353C	2.60
UPC1365C	5.05
UPC1377C	4.60
UPC2002H	1.85

TRAN-SISTORS PRICE

BC107	14
BC108	14
BC109	14
BC141	26
BC142	23
BC143	25
BC147	09
BC148	09
BC157	10
BC158	11
BC159	11
BC182L	11
BC183L	11
BC184L	11
BC212L	10
BC213L	10
BC237	11
BC327	11
BC328	12
BC337	11
BC338	10
BC357	10
BC558	10
BD124M	1.05
BD131	.33
BD132	.33
BD201	.80
BD202	.70
BD203	.70
BD204	.83
BD222	.50
BD225	.55
BD232	.50
BD233	.37
BD234	.40

TYPE PRICE

BD235	.32
BD236	.43
BD237	.40
BD238	.39
BD410	.50
BD434	.50
BD437	.70
BD438	.70
BF194	1.05
BF195	12
BF196	11
BF197	11
BF241	15
BF256LC	25
BF258	25
BF259	26
BF337	28
BF338	30
BF458	30
BF459	36
BF757	75
BFR90	1.60
BR100	18
BR101	32
BR103	55
BR303	2.95
BT106	1.15
BT116	1.30
BT151/	1.00
800R	1.10
BU126	1.78
BU205	1.42
BU208A	1.45
BU208D	1.85
BU326A	1.48
BU407	1.12
BU407D	1.45
BU500	1.80

TYPE PRICE

BU508A	1.95
BU526	2.00
BU826A	3.20
R2010B	1.45
R2540	2.35
TIP31C	.46
TIP32C	.47
TIP33	.80
TIP34	.48
TIP41C	.48
TIP42C	.48
TIP47	.75
TIP2955	70
TIP3055	70
2N3055	70
2N3773	3.45
15/80H	2.25
15/85R	2.25
2SA 771	2.35
2SA 835	1.55
2SB 618	2.45
2SC 867A	3.25
2SC 1034	4.85
2SC 1061	1.15
2SC 1114	4.75
2SC 1124	.97
2SC 1316	3.20
2SC 1413A	3.95
2SC 1739	2.45
2SC 1942	2.95
2SC 1962	1.65
2SC 1969	1.95
2SC 2078	1.55
2SC 2335 (Kit)	7.55
2SC 2369	3.25
2SC 257	2.45
2SD 588A	1.97
2SD 725	7.95
2SD 870	5.95

THORN SPARES AVAILABLE

DECCA 80	7.95
DECCA 100	8.50
ITT CVC 20	7.75
ITT CVC 25/30/32	8.00
ITT CVC 45	8.45
PHILIPS G8	8.75
PHILIPS G11	13.50
PHILIPS KT3	9.95
PHILIPS K30	16.50
RBM T20A	11.50
THORN 1615	9.75
THORN 1690/1	9.65

DIODES

TYPE	PRICE
BY127	10
BY133	15
BY164	40
BY179	65
BY210/800	30
BY223	86
BY227M	23
BY229/600	87
BY284/400	24
BY299/800	25
BYX10	20
BYX55/600	26
BYX71/600	93
SKE4F/206	80
SKE5F/10	1.45
W005	55
1N4001-7	87
1N5401-8	16

SONY SPARES

C5/C7 Rewind Kit	4.65
C5/C7 Belt Kit	3.50
C6 Rewind Kit	4.35
C7 Pinch Roller	4.85
SG 613/6533	8.95
CX 143A	6.95

CASS MOTORS

6V C/W	5.00
9V C/W	5.00
12V C/W	5.00
13.2V C/W	4.85

SUNDRIES

G8 TRANSDUCTOR	2.25
G8 ON/OFF SW.	1.40
G11 E/W Coil	1.65
G11 Lin Coil	1.80
G11 Bridge Coil	1.35
G11 EHT Lead	2.25
PYE IFT Gain M00	7.85
ITT On/Off SW	1.10
THORN On/Off SW	1.00
CUT OUT 2A	1.95
TX10 FOCUS UNIT	8.95
VCR Pilot Bulb	7.70

VALVES

PCF802	1.09
PCL82	.97
PCL85	1.03
PCL86	1.07
PL504	1.59
PL508	2.99
PL509/519	5.99
PY500A	2.25

TV ELECTROLYTICS

DECCA 30(400/400)350V	3.99
DECCA 80-80/100(400)350V (800)250V	3.99
PHILIPS G8(600)300V	2.65
PHILIPS G9(2200)63V	1.45
PHILIPS G11(470)250V	2.20
RBM A823(2500/2500)30V	1.65
RBM T20A(220)400V	2.35
THORN 1690/1(4700)25V	.94
THORN 3500(1000)70V	.99
THORN 9000(400)400V	3.10

PUSH BUTTONS/ NEW TUNERS

DECCA/ITT 6 way	7.95
PHILIPS G8 S/L	14.90
PHILIPS G8 S/Q	12.00
PYE-G11 P/B	8.50
HITACHI 4 way	8.95
ITT CVC5 Button	10.40
ITT CVC8/9	12.80
1043/05	8.95
U321	8.35
U322	7.40

Available also a range of 2SA/B/C/D Transistors. Phone or write for lists.

ORDERING
Please Add 50p For P/P U.K.
Add 15% VAT To This Total.
Export Orders - Cost.
DELIVERY BY RETURN ON ALL STOCK ITEMS.

INCREASE YOUR PROFITS IMPROVE YOUR SERVICE WITH RELIABLE COST EFFECTIVE TEST EQUIPMENT

LEADER LCT-910A C.R.T. TESTER-REJUVENATOR

Our top selling instrument is designed to readily test the various characteristics and rejuvenation of both colour and B/W C.R.T's.

- ★ Tests for shorts and leakage between electrodes.
- ★ Tests cathode emission characteristics.
- ★ Separately checks condition of guns.
- ★ Removal of shorts and leakage between electrodes.
- ★ Checks heater warm-up characteristics.
- ★ Rejuvenation of low emission cathodes with automatic timing.
- ★ Super rejuvenation with manual control.
- ★ Complete with tube base adaptors.

Size: H 230mm W 330mm D 120mm.




PRICE £210 + £31.50 VAT

LOPT TESTER


BK's REVOLUTIONARY DYNAMIC 'LOPT' TESTER
Revolutionary L.O.P.T. tester. Operates in dynamic mode which actually tests the L.O.P.T. under high voltage conditions without de-soldering or removal.
Size 75x100x40 mm. Supply 240V AC

PRICE £25.99 + £3.37 VAT

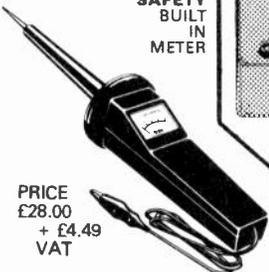LEADER HIGH VOLTAGE METER EHT PROBE
Measures up to 40 K.V. D.C. with SAFETY BUILT IN METER



PRICE £28.00 + £4.49 VAT

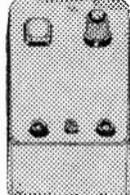


CRT TESTER-REJUVENATOR

BK's C.R.T. TESTER-REJUVENATOR
Tests and rejuvenates blue, green & red guns separately. Fitted with delta and P.I.L. sockets. Compact size 120x65x40 mm. Supply 240V AC

PRICE £32.00 + £4.80 VAT

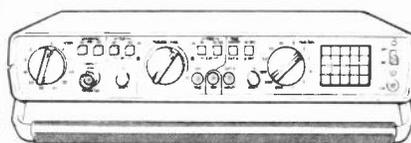THE VERY LATEST SC110A LOW POWER, FULLY PORTABLE OSCILLOSCOPE.



The new Thandar SC110A represents a break-through in oscilloscope development. The SC110A is ONLY TWO INCHES thick and weighs under two pounds, yet retains the standard features and controls of a bench oscilloscope. **FITS IN A BRIEFCASE**

Full Sized Performance

- 10 MHz bandwidth
- Full trigger facilities are provided including TV frame, or TV filtering
- Runs on 4 to 10V DC via disposable batteries, re-chargable cells, or AC adaptor
- Size 255mm x 148mm x 50mm.

PRICE £165.00 + £24.75 VAT

Accessories: Carry Case £5.95 + £0.89 V.A.T.
 × 1 Probe £7.50 + £1.13 V.A.T.
 × 10 Probe £8.50 + £1.28 V.A.T.
 × 1 × 10 Switched Probe £10.50 + £1.58 V.A.T.
 AC Adaptor £6.95 + £1.04 V.A.T.

HAMEG HM 203-5 20MHz DUAL TRACE OSCILLOSCOPE

SPECIFICATION:

- *BANDWIDTH DC-20MHz
- *SENSITIVITY CH1, CH2 2mV-50V/DIV
- *TIMEBASE 40ns to 0.25 CM
- *TRIGGER DC-40MHz Auto-Normal-TV
- *CALIBRATION OUTPUT
- *CH1 ADD AND INVERT FACILITY
- *ALT/CHOP SWITCH
- *LARGE RECTANGULAR SCREEN 8 x 10 cms.
- *BUILT IN SEMICONDUCTOR COMP. TESTER
- *SIZE 285mm x 145mm x 380mm.
- *SUPPLY 110-125-220-240V AC 50-60Hz



WITH COMPONENT TESTER

PRICE £270.00 + £40.50 VAT
Optional probes as above

2 YEAR WARRANTY

SPECIAL OFFER SUMMER SALE

MINIMUM LOTS OF 20

DECCA 20" VARICAP	£10
DECCA 22" MECHANICAL	£8
DECCA 22" VARICAP	£10
DORIC 20" & 22"	£10 each
SALORA 22" HYBRID	£4.50
SALORA 26" TOUCH TUNE	£10
BUSH A823 20" & 22"	£5 each
GEC 2110 22" & 26"	£12 each

TOUCH TUNE VCRs and other CTVs also available.

All Plus VAT

Please allow 14 days for delivery

SOUTHPARK DISTRIBUTORS

Unit 4 Rubastic Road,
Brent Park Industrial Estate,
Southall, Middlesex UB2 5LL

Tel: 01-574 4631

FREE CAREER BOOKLET

Train for success, for a better job, better pay!

Enjoy all the advantages of an ICS Diploma Course, training you ready for a new, higher paid, more exciting career.

Learn in your own home, in your own time, at your own pace, through ICS home study, used by over 8 million already!

Look at the wide range of opportunities awaiting you. Whatever your interest or skill, there's an ICS Diploma Course there for you to use.

Send for your FREE CAREER BOOKLET today — at no cost or obligation at all.

GCE		Choose from over 40 'O' and 'A' level subjects.	<input type="checkbox"/>
COMPUTER PROGRAMMING	<input type="checkbox"/>	CAR MECHANICS	<input type="checkbox"/>
BOOK-KEEPING & ACCOUNTANCY	<input type="checkbox"/>	INTERIOR DESIGN	<input type="checkbox"/>
POLICE ENTRANCE	<input type="checkbox"/>	HOTEL MANAGEMENT	<input type="checkbox"/>
ELECTRONICS	<input type="checkbox"/>	COMMERCIAL ART	<input type="checkbox"/>

Please send FREE DETAILS for the courses ticked above.

Name _____

Address _____

P. Code _____



Dept. EGS95, 312/314 High St., Sutton, Surrey SM1 1PR. Tel: 01-643 9568/9 or 041-221 2926 (all hours).



CHROMOVAC

QUALITY REBUILDS

SPECIAL OFFERS!
ON
INLINE

Get on the hot-line today!

SUPERIOR QUALITY TUBES

DELTA RE-BUILDS

051
428 8777

most types of Inline Re-builds or new ex-stock

★ 2 YEAR WARRANTY
★ 4 YEAR OPTIONAL

Delta Rebuilds

Up to 19"	£28
Up to 22"	£30
Up to 26"	£34
110° up to 22"	£34
110° up to 26"	£38
Low focus	+£2
A47 342 New	£28
17FHP New	£30
470EB New	£30
Delta only. Less 5% 5+	

Inline Rebuilds

Up to 22"	£40
Up to 26"	£45
A56 - 540x	£56
A66 - 540x	£58
Bonded Coil	+£5

ALL SIZES OF
NEW MONO TUBES
AT COMPETITIVE PRICES

IN LINE TYPES EX-STOCK SELECTION NOT REBUILDS

Please enquire types not listed

370 HFB-A37-590	£45	560 DMB	£62
370 HUB	£45	AXT 56-001	£62
AXT 37-001	£45	660 AB	£65
420 CSB	£45	A67-701	£65
420 EDB-A42-590	£45	670 CZB	£65
420 EZB	£45	A66-540	£65
420 ERB	£45	420FSB	£55
470 KUB	£50		
510 UFB/A51-590	£55		
510 VSB	£60		
AXT 51-001	£60		
560 DYB-560 DTB	£62		
560 EGB	£62		
560 CGB	£62		

CARRIAGE
£5 Singles, 2-3 £10, 4 £12
10 £15, 10+ Carriage paid
EXCLUSIVE OF VAT
TERMS
Cash with order

QUANTITY DISCOUNT AVAILABLE
Ask for details

★ OUR TECHNICAL DEPT WILL ADVISE YOU ON PROBLEMS YOU MAY ENCOUNTER ON FITTING INLINE TUBES

DELIVERY: Ex stock items immediate dispatch on receipt of order. Others allow 14 days.

THE COMPANY WHO PUT HIGH STANDARDS FIRST

CHROMOVAC

CHROMAVAC LTD. UNIT 7, BEAR BRAND COMPLEX,
ALLERTON ROAD, WOOLTON, LIVERPOOL 25

Ask for Mr Butterworth or Betty Ford ON: 051-428 8777

EAST CORNWALL COMPONENTS

85

NEW 1985 CATALOGUE will be available July/August - range of components greatly increased - over 125 pages fully illustrated. Price £1.00 per copy (free upon request with orders over £15). Includes 50p Credit Note, Special Offer Sheets, Order Form and Pre-Paid Envelope. Order your copy now - will be despatched as soon as available.

SERVICE AIDS

ALL SERVISOL PRODUCTS	0.98
Switch Cleaner	1.14
Circuit Freezer	0.98
Foam Cleanser	0.96
Aero Klene	0.96
Silicone Grease (Tube)	1.64
Antistatic Spray	0.98
Plastic Seal	1.08
Excel Polish	0.92
Fire Extinguisher 640g	2.80
Video Head Cleaner	0.86
Solda Mop (Sd)	0.74
Solda Mop (L/Gauge)	0.74
Heat Sink Comp	1.08
Additional P&P on above 30p each	

PLUGS & SOCKETS

Metal Co-ax Plug	0.18
Plastic Co-ax Plug	0.14
Metal Line Socket	0.52
Single Junc Socket	0.80
Plastic Plug	0.15
F.M. Plugs	0.20
25W Plugs	0.38
Reducer	0.15
Low loss splitter 1 in 2 out	1.00

SOLDERING SECTION

Soldering Station complete with 30W or 40W iron (state which)	49.95
XS25 Wait iron complete with steel and plug attached	7.20
CS 18W, as above	7.00
Antex 15W iron	5.00
Antex 18W iron	5.00
Antex 25W iron	5.20
Antex elements	2.00
Antex bits	0.95
Antex stands	1.90
Soldersucker	0.65
Nozzles	0.65

TERMINAL BLOCKS


2 amp 12 way	0.19
5 amp 12 way	0.20
10 amp 12 way	0.40
15 amp 12 way	0.46
32 amp 12 way	0.90

VALVES

Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)
DY802	0.88	AC127	0.30	A/B or C	0.12	BC303	0.32	BD375	0.32	BF271	0.26	BT108	1.30	BYX55/600	0.33
DY88/87	0.75	AC128	0.30	BC113	0.14	BC307	0.10	BD410	0.10	BF273	0.18	BT109	1.18	BYX71/600	1.18
EC881	0.95	AC129K	0.34	BC114	0.12	BC308A	0.10	BD434	0.88	BF274	0.32	BT116	1.25	BYZ12	0.42
EC882	0.95	AC132	0.55	BC115	0.12	BC309	0.12	BD436	0.68	BF275	0.32	BT119	3.62	BYZ19	0.88
EC883	1.10	AC141	0.88	BC116	0.15	BC327	0.14	BD437	0.76	BF336	0.26	BT120	3.60	E1222	0.40
EC884	0.65	AC141K	0.40	BC117	0.22	BC328	0.14	BD438	0.75	BF337	0.26	BT121	3.62	E5024	0.30
EC885	0.90	AC142	0.26	BC118	0.17	BC337	0.12	BD439	0.68	BF338	0.26	BT138/600	1.30	GET872	0.48
EC888	0.95	AC142K	0.48	BC119	0.30	BC338	0.12	BD517	0.56	BF355	0.42	BT151/600R	0.90	IT744	0.04
ECF80	0.95	AC151	0.45	BC140	0.28	BC350	0.14	BD520	0.66	BF363	0.82	BT151/300R	1.15	IT72002	0.11
ECH81	0.75	AC152	0.45	BC141	0.42	BC441	0.32	BD707	0.88	BF371	0.27	BU74000R	1.75	IT802	0.20
ECH84	0.75	AC176	0.28	BC142	0.30	BC461	0.32	BDX18	2.35	BF422	0.38	BU104	2.00	MEU21	0.60
ECL82	0.75	AC176K	0.48	BC143	0.30	BC547	0.12	BDX32	2.10	BF450	0.38	BU105	1.20	MJ400	1.25
ECL86	0.98	AC187	0.42	BC147	0.08	BC548	0.12	BF115	0.32	BF457	0.33	BU105/02	1.50	MJ2955	0.90
EF80	0.85	AC187K	0.45	A or B	0.10	BC549	0.12	BF117	0.54	BF458	0.36	BU108	1.80	MJ3000	1.98
EF86	1.60	AC188	0.44	BC148	0.08	BC551	0.17	BF119	0.82	BF459	0.44	BU124	1.75	MJ3400	0.60
EF183	0.75	AC188K	0.50	A or B	0.10	BC550C	0.18	BF120	0.38	BF489	0.22	BU126	1.60	MJE240	0.60
EF184	0.75	AC190	0.88	BC149	0.09	BC557	0.12	BF123	0.40	BF490	0.42	BU133	1.80	MJE370	0.88
EH90	0.94	AD142	1.10	BC157	0.10	BC558	0.12	BF125	0.42	BF491	0.22	BU204	1.35	MJE520	0.48
EL34	3.25	AD143	1.10	BC158	0.10	BCX34	0.27	BF127	0.38	BF495	0.22	BU205	1.30	MJE2955	0.99
EL84	0.69	AD149	0.92	BC159	0.10	BCY70	0.15	BF152	0.16	BF611	0.32	BU206	1.70	MJ3055	0.70
EL509	7.85	AD162	0.48	BC161	0.30	BCY72	0.18	BF157	0.23	BF612	0.28	BU208	1.95	MPS101	2.58
EM87	2.55	AD161/AD162	0.98	BC168B	0.10	BCZ10	1.68	BF158	0.22	BF619	0.17	BU208/02	2.05	MRF479	5.20
EY86/87	0.67	AF106	0.48	BC169C	0.12	BC211	1.45	BF159	0.24	BF790	0.38	BU209/02	1.75	MRP477	10.00
EY500A	1.65	AF114	2.10	BC170	0.14	BD124P	0.80	BF160	0.23	BF743	0.38	BU407	1.65	OA47	0.10
PCC84	0.50	AF115	2.10	BC170B	0.12	BD130Y	0.68	BF167	0.30	BF745	0.79	BU407D	1.80	OA90	0.08
PCC85	1.35	AF116	0.50	A or B	0.10	BD131	0.34	BF173	0.25	BF746	0.76	BUX80	3.70	OA91	0.09
PCC89	0.74	AF117	0.10	BC171	0.10	BD132	0.34	BF177	0.42	BF747	0.44	BUX90	1.75	OA92	0.18
PCC189	0.85	AF118	0.85	A or B	0.08	BD131/BD132	0.95	BF178	0.30	BF748	0.30	BUY64	2.60	OA200	0.06
PCF80	0.75	AF121	0.62	BC172	0.08	BD135	0.32	BF179	0.32	BF780	3.56	BUY68B	1.98	OA202	0.15
PCF86	1.25	AF124	0.48	A or B	0.12	BD136	0.36	BF180	0.35	BF784	0.24	BY101	1.40	OC25	2.10
PCF200	1.95	AF125	0.48	BC177	0.07	BD137	0.36	BF181	0.35	BF785	0.26	BY118	1.10	OC26	1.70
PCF501	1.45	AF127	0.48	BC178A	0.22	BD138	0.38	BF182	0.32	BF786	0.26	BY122	0.68	OC28	1.50
PCF802	1.00	AF127	0.48	BC178B	0.22	BD139	0.38	BF183	0.32	BF787	0.26	BY127	0.12	OC29	2.47
PCF806	1.20	AF139	0.68	A/B or C	0.09	BD140	0.38	BF184	0.32	BF788	0.26	BY127	0.12	OC35	1.75
PCL82	0.90	AF178	0.68	BC182L	0.09	BD144	1.60	BF185	0.32	BF790	0.21	BY133	0.16	OC36	1.75
PCL83	2.50	AF239	0.68	A/B or C	0.09	BD145	1.82	BF194	0.08	BF791	0.21	BY135	0.25	OC42	0.72
PCL84	1.30	AF279S	0.68	BC183	0.09	BD150A	0.51	BF195	0.10	BF792	0.21	BY164	0.44	OC42K	1.40
PCL85/85	1.35	AL102	2.50	A/B or C	0.10	BD159	0.65	BF196	0.10	BF793	0.40	BY179	0.67	OC44	0.72
PD500	3.75	AL113	2.20	A/B or C	0.12	BD165	0.45	BF198	0.14	BF794	0.90	BY182	0.86	OC45	0.58
PFL200	1.35	ASV80	1.75	BC184L	0.10	BD175	0.60	BF199	0.16	BR100	1.00	BY184	0.40	OC71	0.50
PL33	1.50	AU110	1.40	A/B or C	0.10	BD182	1.00	BF200	0.26	BR101	0.40	BY189	0.75	OC72	0.52
PL36	1.45	AY102	4.32	BC207	0.15	BD183	1.10	BF222	0.40	BR103	0.58	BY198	0.44	OC200	2.46
PL81	0.85	BA110	0.67	BC208	0.16	BD184	1.10	BF224	0.20	BR103	0.58	BY198	0.44	OC202	2.20
PL82	0.75	BA117	0.40	BC212	0.12	BD201	0.72	BF224J	0.16	BR139	0.38	BY206	0.24	ORP12	0.85
PL83	0.65	BA129	0.38	A/B or C	0.10	BD202	0.87	BF229	0.20	BR156	0.86	BY210/400	0.25	R20108	1.50
PL84	0.75	BA148	0.16	BC212L	0.08	BD204	0.80	BF241	0.20	BR161	0.86	BY210/400	0.25	R20108	1.50
PL95	2.00	BA154	0.08	A/B or C	0.10	BD222	0.80	BF244	0.26	BSS17	0.56	BY210/600	0.26	SHG1.5	0.40
PL504	2.20	BA155	0.10	BC213	0.09	BD225	0.86	BF244A	0.28	BSS27	0.92	BY210/800	0.30	TIC44	0.40
PL508	2.40	BA156	0.08	A or B	0.10	BD232	0.45	BF244C	0.24	BSS19	0.34	BY223	0.10	TIC45	0.45
PL509/519	1.80	BA157	0.14	A or B	0.10	BD233	0.60	BF245	0.28	BSS20	0.34	BY227	0.26	TIC46	0.48
PY88	1.80	BA164	0.08	A or B	0.10	BD234	0.62	BF245A	0.28	BSS21	0.62	BY229	0.30	TIC47	0.70
UY500A	2.40	BB104B	0.52	BC237	0.11	BD235	0.63	BF256	0.40	BSS22	0.62	BY238	0.68	TIC106A	0.46
U26	1.90	BB105B	0.30	BC238	0.12	BD236	0.63	BF257	0.32	BT100A/02	0.94	BYX10	0.24	TIP30A	0.46
UCH81	0.90	BB105G	0.48	BC239C	0.14	BD237	0.65	BF258	0.30	BT101/300	1.15	BYX36/150	0.22	TIP31C	0.54
UCL82	1.70	BB110B	0.48	BC251	0.12	BD238	0.56	BF259	0.32	BT101/500	1.25	BYX36/600	0.28	TP32	0.40
6J5CT	1.75	BC107	0.10	A/B or C	0.14	BD241	0.60	BF262	0.30	BT102/300	1.35	BYX48/300	0.27	TP32C	0.60
6J5T	2.20	BC108	0.12	BC301	0.32	BD243A	0.63	BF263	0.30	BT102/500	1.65	BYX49/300	0.47	TP33A	0.63
30FL12	1.60	BC109	0.10	BC302	0.32	BD244A	0.65	BF270	0.30	BT106	1.50	BYX55/300	0.29	TP34A	0.72

INTEGRATED CIRCUITS (E) EACH

AN240P	3.42	SN76225DN	1.80	TBA750	2.85
AN214Q	3.88	SN76227N	1.10	TBA750	2.80
AN7150	2.90	SN76530P	1.40	TBA800	1.60
CA3065	1.75	SN76533N	1.60	TBA810P	1.10
CA4031P	3.88	SN76650N	1.05	TBA820	1.60
CA4102	2.30	SN76660N	0.75	TBA880	3.88
CA4400	2.98	SN76666N	0.70	TBA920Q	3.00
CA4422	3.07	STK015	6.50	TBA950/2A	3.05
LC7120	5.33	TA7108P	3.20	TBA970	4.05
LC7130	5.26	TA7120P	2.20	TBA990	1.88
LC7137	5.16	TA7129AP	3.65	TCA2705A	4.02
LM3800	1.65	TA7130P	1.65	TCA2705A	4.02
LM1303N	2.52	TA7172	1.80	TCA2705A	4.02
HA1151P	3.12	TA7173	5.50	TCA940	1.90
MC1307P	1.95	TA7174	1.80	TDA440	3.80
MC1310P	1.85	TA7176	2.50	TDA1002	1.90
MC1312P	2.25	TA7202P	1.85	TDA1003A	5.50
MC1327P	1.25	TA7204A	1.86	TDA1006A	2.50
MC1330P	0.83	TA7205AP	1.57	TDA1035S	4.50
MC1349P	1.85	TA7208P	3.27	TDA1044	4.30
MC1351P	1.50	TA7222P	2.12	TDA1170S	3.00
MC1352P	2.50	TA7223P	3.68	TDA1190	3.50
MC1357P	2.88	TA7227P	5.60	TDA1210Q	3.10
MC1496L	1.15	TA7310P	1.80	TDA1327A	1.66
ML231B	2.10	TA7611AP	2.88	TDA1352A/B	1.56
ML232B	2.10	TA7623	2.46	TDA1412	1.20
ML233B	2.30	TA7650	0.50	TDA2002	2.80
MR475	2.50	TA8570	1.99	TDA2020	4.60
MR479	5.20	TA8611A12	3.50	TDA2030	2.78
MR479	5.20	TA8611A			

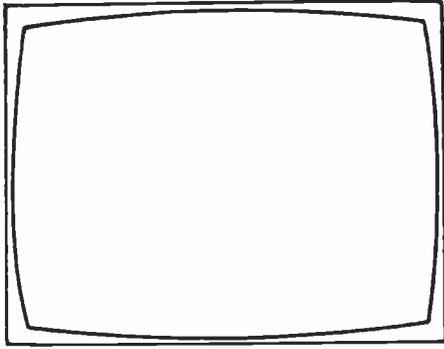

TELEVISION

EDITOR

John A. Reddihough

ADVERTISEMENT MANAGER

Roy Smith
01-261 6671

CLASSIFIED ADVERTISEMENTS

Barbara Blake
01-261 5897

Please note that the telephone numbers above are for contact with the advertisement departments only. Editorial enquiries should be sent to the editor at the address given on page 601.

COVER PHOTO

This month's cover photo shows adjustment and final checking of a Philips Matchline video tuner/source selector in the Philips factory at Norrköping, Sweden. The Matchline TV system was launched in European markets last year. There are three Matchline models at present on sale in the UK, the 6620, 6720 and 6820 (20, 22 and 26in. screens respectively): they are complete sets with teletext, remote control and optional speaker arrangements. Our thanks to Philips for permission to reproduce the photograph, which was taken using a fish-eye lens.

CORRECTION

An error occurred in line 180 of the Commodore 64 Test Pattern Program published last month: CHR\$(152) should be followed by a semicolon, not a colon.

ADDRESS PLEASE

Would Mr. R. S. Narwan of Visionhire please send his address (omitted from VCR fault notes) to the editorial department.

NO MORE GLAMOUR?

It's difficult to recall a time of woe quite like the present in the electronics industries of the West. There've been downturns before, in particular a chip glut that led to severe price cutting in the early seventies, but there's not previously been a period in which business has been poor generally throughout the electronics industry.

The chipmakers have been doing badly for some time. The latest news on this front comes from Texas Instruments, the world's largest semiconductor manufacturer, which made a loss of \$3.9m on turnover down by 16 per cent during the second quarter of the year. Texas Instruments has cut back on its investment plans, laid off another 1,800 employees, and is expecting a further business deterioration in the third quarter.

Poor sales of semiconductor devices reflect poor business in the computer field. We all know about the collapse of the microcomputer market. It seems that the makers of large computers haven't been doing all that well either. IBM's half year results show profits down by 15 per cent though turnover was up slightly – by two per cent. Reduced earnings during the period have also been reported by Honeywell, Burroughs, Data General, NCR and Control Data. Lay-offs and shut-downs have been widely reported.

The major electronics and computer group Hewlett-Packard has announced that most of its US operations will be closed for one or two days a month from August – its 45,000 US employees are expected to take unpaid time off during the shut-downs. In Europe Philips, the only truly multinational European-based electronics group, has reported "appreciably lower" income in the second quarter of 1985 compared to 1984, mainly due to the performance of its US subsidiaries. The UK scene has been one of declining profits, with STC – owners of ICL since last year – reporting a loss for the six months to June 30th. In this case the computer side of the business (ICL) is said to have "performed satisfactorily", the problems being on the components, telecommunications and submarine cable sides of the business. The components industry worldwide seems to have been doing poorly, as one would expect when end-product business is in decline. Reports on the European telecommunications industry comment on increased competition and lower profits, and we all know that with the exception of the Japanese it has been hard to make any money out of producing consumer electronics products in recent times. In this field the Japanese continue to report improved results. Matsushita, the world's largest manufacturer of electrical/electronic consumer goods, has reported pre-tax profits up by 17 per cent during the first half on turnover up 11 per cent. Matsushita's largest single line is VCRs: sales of these increased by 20 per cent and "continued strength" in this market is reported.

Even the Japanese consumer goods manufacturers seem to be concerned about future prospects however. As mentioned in Teletopics last month, both Matsushita and Sony have announced plans to diversify substantially into other fields, specifically component manufacture and industrial electronics. In view of the weak state of electronics markets generally one wonders how successful this policy will turn out to be – and about its implications in terms of increased competition.

Is all this woe just a temporary phenomenon? Certainly there's pessimism about the prospects for an upturn in the immediate future. It's nevertheless worth making the point that many of the reduced profit figures that have been reported have been made on increased turnover, indicating severe competition rather than a market collapse. Mullard's managing director Ivor Cohen has commented that "in terms of fundamental usage of electronic components the trend is not far from the usual pattern". But it's difficult to see the electronics industry returning to the high growth rates experienced during recent decades.

Most of the present pessimism originates in the USA, in particular from the computer industry. It's contagious because the US is still the world's largest market. One tends to feel that if US chip and computer manufacturers can't make a good living, what hope is there for the rest of us? Nevertheless conditions in the US economy in recent months have been rather different from those elsewhere. A boom phase has come to an end, and the excessive value of the dollar has had depressing implications for the competitiveness of much US industry. More logical exchange rates would doubtless help, but these are subject to uncontrollable shifts in currency demand – and, in the case of the dollar, the effect of the budget deficit.

It would probably be true to say that the electronics industry worldwide will never again be a very comfy place in which to operate. Excessive investment has led to over capacity, and this is something that's very hard to deal with – which firms would willingly forgo the chance to have a share in the next generation of electronic components/equipment? In the past, stockmarkets have often given electronics firms "glamour stock" ratings. The glamour has quite definitely gone for the time being. Perhaps this doesn't matter too much. The situation in the industry is nevertheless disconcerting, since through much of the post-war era it's been in the forefront of economic advance. Are we to expect a continuation of the present worldwide economic stagnation until some other industry comes along to take the lead?

Letters

NOTES ON RANK CHASSIS

The problem of ringing on the left-hand side of the screen with the Rank T20 chassis came up on the July issue problems page. The cause in every case I've come across has been 5C17 (0.47 μ F) open-circuit or more often intermittent – it's the same type of capacitor that blows the BD131 line driver transistor in the older A823 series chassis. It's easy to check 5C17: just bridge the PC connections with an 0.1 μ F capacitor and the lines will disappear.

On the subject of the A823, I've always cured the IBA's "new" teletext lines by changing the value of the field flyback tuning capacitor 5C35 (5C34 in the A823A chassis) from 2.2 μ F to 0.47 μ F – there's often a spare, i.e. redundant, 0.47 μ F capacitor on the convergence panel (7C1).

I recently had a T22 with a star-shaped crack in the neck of the A56-510X tube and a black mark in the plastic convergence clamp. Suffolk Tubes mentioned the Philips G11 when I took the tube to them for regunning, i.e. the problem of C4029. I haven't found any likely capacitor trouble in the T22 and have put extra polythene under the clamp to increase the gap length. I reckon it's tube weakness rather than anything else, but no one's going to admit it!

*D. A. Ferriday, Rowlands Radio,
Rowlands Castle, Hants.*

THE NORDMENDE FV1/90° CHASSIS

I was sorry to read (June issue) of Les Lawry-Johns' problems with a set (Ferguson 3787) fitted with the NordMende FV1/90° chassis. As importer for NordMende television sets in Ireland we've distributed thousands of sets using this chassis, both manual and remote control versions, and while I would hesitate to be the expert Les is seeking perhaps the following points would help him and others in a similar position.

With a dead set, check that h.t. is reaching the anode of the flyback thyristor DA12. The usual culprit is one of the thyristors in the line output stage, DA12 or DA14 – if one of them proves to be faulty, change them as a pair. These thyristors can cause other problems, for example a tendency to blow the TDA1170 field timebase chip on an irregular basis: if you have a set with a blown TDA1170 the odds are that DA12 or DA14 was the cause. Faulty output thyristors can also give you a set with no raster but plenty of e.h.t. and arcing at spark gap VA26: if this is experienced, be prepared to refurbish the line output stage completely to be confident of not seeing the set again. In this instance the capacitors in the gate circuits of the two thyristors – CA13, CA15 and CA16 – should be changed.

The set that gave Les such a headache had the top core of the line output transformer missing. This situation is now quite common with these sets since they are fairly lightweight portables and get moved around a fair bit. The missing core will normally be found in the bottom of the set, but note that there's a mica insulator at each of the junctions of the two cores: these must be positioned correctly before regluing. Such repairs to the transformer are not always successful and in some cases a replacement

is the only answer. Similarly if the loose core is found to be damaged in any way it's best to discard the transformer, as a replacement will prove to be the only long-term solution.

The e.h.t. adjustment must be checked after any work is carried out on the line output stage. Set RZ13 for 55V d.c. at pin 10 of the line output transformer with the contrast and brightness controls at minimum. At this setting the e.h.t. and all the other voltages derived from the line output stage are correct.

Finally a problem that can cause some trouble. An earthing strip runs to the right-hand side of the sound and line oscillator panels, from the top of the chassis to the bottom. If either of these panels, more especially the line oscillator panel, is removed the strip can become dry-jointed. This can cause intermittent start-up, random cutting out, and persistence of the e.h.t. at switch off – the latter condition can eventually lead to a burn in the tube. Soldering a wired bridge between the chassis and the part of the main panel to which the anode of DA06 is connected is a good idea whenever one of these sets requires attention.

Apart from the above there are no real pitfalls waiting to trap the unwary. Despite their advancing years, the excellent pictures these sets give will amply justify the work involved in returning them to a fully working condition.

*Anthony Cronin, Service Manager,
Reynolds Electronics Limited,
Dundalk, Co. Louth.*

BBC MICRO PROGRAM

The pixels produced by the BBC microcomputer are not quite square and in order to produce a true circle it's necessary to increase the lengths in the horizontal direction by 8.4 per cent. In Patrick Kniveton's program for example (July issue, page 516) the following lines should be changed:

```
790 PLOT5, 1.084 * 350 * COS C, 350 * SIN C
800 PLOT5, 1.084 * 352 * COS C, 352 * SIN C
```

Similar changes should be made in PROCcard. This technique will improve the appearance of many designs which use circles (or squares) which would otherwise be stretched vertically. Incidentally, this means that the aspect ratio of the active part of the raster is 1.15:1 rather than 1.25:1 as suggested by the co-ordinate size of the screen (1280:1024).

The colons in lines 100-180 should be the double-bar character found on the key above the pound sign key on the BBC micro.

*Alan Pemberton,
Sheffield.*

PROGRAMMING OFFER

Following my article on a Spectrum test card program it became apparent that many readers with home computers don't have the time or inclination to write programs for them. If readers with ideas for programs that may be suitable for publication in *Television* would like to write in I would be willing to write the program and let the first reader with the idea have a copy for evaluation. Programs about VAT, bookkeeping etc. are excluded as there are many of these already in circulation. I mainly use a

Spectrum computer but can also produce programs in BASICODE2, the BBC's computer esperanto system that will run text and numbers programs on most home computers. BASICODE2 will not produce colour or graphics however, so it would not be suitable for test card or colour bar programs. A BASICODE2 kit is available for £3.95 from the BBC: it covers most popular makes in one booklet and cassette.

*John de Rivaz, B.Sc. (Eng.),
Truro, Cornwall.*

THORN TX90 TIP

Anyone using a Ferguson 14in. colour set (TX90 chassis) as a monitor may be interested in a modification from Ferguson to shift the picture slightly to the right – useful with computers. Simply short out R106.

*Derek Snelling,
Brownhills, Staffs.*

SOFT START FOR THE G8

Several articles on the Philips G8 chassis have appeared in *Television* over the years, the most recent being excellent articles by Tony Thomson in the May issue and Dennis Apple in the July issue. I agree that when correctly adjusted, and provided the tube is good, these sets are still capable of providing very worthwhile results. One problem with this chassis however is the omission of a soft-start circuit in the power supply. In fact on several examples of these sets I've been alarmed by the tendency for the h.t. line to overshoot the correct 205V at switch on, causing a large surge current and strain on the line output and related stages.

When repairing a G8 with a picture jitter fault recently (the fault was caused by defective zener diodes in the power supply, D1397 and D1371) I decided to look at the possibility of adding a soft-start circuit. After some investigation I discovered that the power supply circuit is very similar to that used in the GEC C2110 series which do have soft start.

In both cases the operation of the power supply is controlled by sensing the d.c. output and mains input voltages and adjusting the firing point of a thyristor to compensate for varying load and changing mains input conditions. Both circuits have a 7.5V zener diode in series with the emitter of the control transistor to provide temperature stabilisation – D1371 in the case of the G8. If the components shown in Fig. 1 are added to the G8 power supply circuit, in parallel with D1371, the result will be soft start, with the output voltage rising from zero to 205V in about two seconds.

The operation of the circuit is as follows. At switch on Tr1 shunts D1371. This delays the firing point of the thyristor until very late in the positive-going half-cycle of the mains, the result being minimum output voltage. As


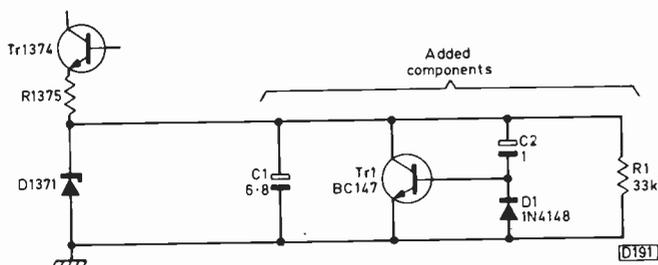


Fig. 1: Soft-start circuit for the Philips G8 chassis.

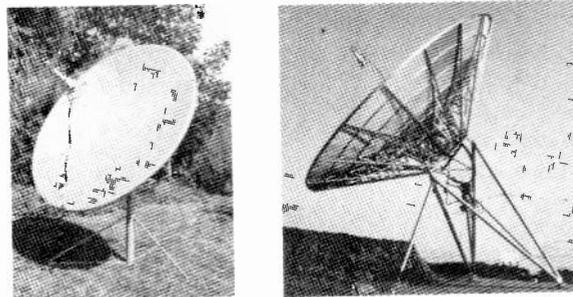

4 + 11GHz SATELLITE TV RECEIVING EQUIPMENT
LNA's LNC's RECEIVERS, FEED HORNS ETC.
Dealer enquiries welcome

For further details contact

HARRISON ELECTRONICS

22 MILTON ROAD, WESTCLIFF-ON-SEA, ESSEX SS0 7JX Tel: (0702) 332338

C2 charges the shunt is slowly removed, until at the end of the soft-start period normal control action is restored. D1 and R1 provide rapid discharge of C2 at switch off: C1 is included to prevent ripple across D1371 from forward biasing D1.

The action of the circuit appears to be completely compatible with most versions (see note below) of the G8's power supply and does not affect the operation of the overvoltage trip and the setting up procedure. The extra components are normally readily to hand and can easily be added on the print side of the panel. Note that some very early versions of the G8 had D1371 in the base instead of the emitter circuit of Tr1374: these cannot be modified in the way described. In some other versions the positions of R1375 and D1371 are transposed – check that the anode of D1371 is connected to chassis.

In conclusion I feel that this modification will increase the life and reliability of a G8 considerably.

*D. R. Bracknell,
Farnborough, Hants.*

CONVERGENCE ERROR POSSIBILITY

A number of microcomputer test pattern programs have appeared in the magazine recently. I'm sure these are excellent but would like to point out a possible source of error. Much convergence circuitry consists of reactive components which are frequency dependent. When setting up the convergence of a colour set these components are supplied with waveforms at line frequency, adjustment being made for optimum convergence of the displayed raster. As most modern colour receiver line timebases will lock with a frequency error of up to ± 20 per cent from the correct frequency the accuracy of the alignment will depend on the accuracy of the computer's sync generator.

*B. D. Webb,
Havant, Hants.*

BUZZING TRANSFORMERS

Hugh Allison's report on a mains transformer with lamination buzz interested me as I've just cured a really noisy one in a disco deck. Toroidal transformers, C cores and vacuum impregnation have made this a rare fault nowadays, but it was common in the days of valves, when home radios had transformers with stacks held by bolts. Hugh's tormentor would appear to be a U-clamp version. The cure for open types is a few taps from a clouting iron to the end of the stack – varying the tension of the bolts

sometimes helps. I learnt this in the "good old days" (?) when a tester was allowed twenty minutes to put a radiogram with record changer through its paces – the pay was 6.4p per hour, 7.2p for troubleshooters, and we worked a 47 hour week . . .

*William Harrison,
Windsor, Berks.*

BBC MICRO PROGRAM

Users of the BBC Micro Test Pattern program (July) should be cautioned that the circles it produces aren't circular! Instead of being square, the graphics units produced by the BBC micro are rectangles with a height:width ratio of 13:12 when displayed on a correctly adjusted TV set or monitor. To produce a properly proportioned circle, the program should be written as if to plot an ellipse with a height of 12/13 its width. The following modifications to Patrick Kniveton's program will have the desired effect:

```
790 PLOT5, 350*COSC,323*SINC
800 PLOT5, 352*COSC,325*SINC
1460 PLOT85, 315*COSED,291*SIND
1510 PLOT5, 320*COSC,295*SINC
1560 PLOT85, 309*COSEF,285*SINF
1700 DRAW-60,280
```

I hope that not too many BBC Micro owners have been diligently adjusting the aspect ratio of their monitors using the program published!

*Richard Russell, M.A., C.Eng. M.I.E.R.E.,
Gravesend, Kent.*

VIDEOTAPE WARNING

In view of the poor availability and greater cost of V2000 type cassettes I decided to try my hand at transferring the tape from a new VHS E120 cassette to a VCC240 cassette – they both use half inch wide tape so I could see no reason why this shouldn't work. Accomplishing the transfer was a very fiddly job and when I tried the cassette in my V2000 recorder the results were hopeless: only a very weak and noisy monochrome picture with very poor sync was obtained. The tape had not been damaged during the transfer because when I put it back in the VHS cassette and tried it in a VHS machine it still worked well.

I'm rather puzzled about this. Although there's about twice as much information stored on a V2000 tape as there is on a VHS tape used in the standard way, half-speed recordings are now made on some VHS machines. I assume therefore that there are fundamental differences in the composition of the tapes, making them incompatible. My advice to anyone thinking of trying this idea is not to bother – and I'm not inclined to try it with a Beta tape.

*M. Catchpole,
Broughton Radio (Worthing).*

AERIAL SOCKET PROBLEM

An aerial rigger friend recently rang me very worriedly. He had fitted a mains-powered aerial amplifier and the fuse had blown when the set was switched on. When I called to help I found that the trouble was due to the chassis being, as so often today, at half mains potential, i.e. approximately –170V d.c., while the negative side of the aerial socket was not isolated – in fact it was directly connected to chassis. This raises several points of interest.

First, the technical aspects. The negative side of the aerial socket was at –170V from a bridge rectifier while the aerial amplifier was connected to earth, thereby taking the negative side to earth. One could leave the amplifier's earth disconnected, but this would be negligent since it's designed to have an earth connection. Or one could use a battery-powered amplifier. But what if a masthead amplifier is required as well? Assuming you fit a battery-powered amplifier you must remember that the coaxial plug and cable will be at –170V. These are exposed and potentially lethal. Thus an insulated coaxial plug is required as a minimum. But even this isn't safe!

The obvious and I believe correct action is to fit an isolated socket. But if the set is under guarantee doesn't this invalidate it? The set in question was an Hitachi one. Other sets use similar techniques.

Secondly there's the legal side of the question. Under the present liability laws the last person to service a TV set or any other equipment must ensure its safety. Who is liable in the event of someone coming into contact with a coaxial plug on a set of this type? Does responsibility lie with the aerial rigger, the service engineer or the setmaker? Personally I believe it would be the setmaker's responsibility. What are your views?

*Rothley Stevens,
Coventry.*

COMMODORE 64 PROGRAM

May I, with acknowledgements to D. J. Jackson (letters, June), offer the following version of his Commodore 64 colour bar program? The entry is considerably simplified – the result is the same. Incidentally I assume that the opening statement on line 15, PRINT"s", is intended to be a clear-the-screen command for which the keystrokes are "SHIFT – CLEAR HOME". This command prints as a reversed heart – see the second statement on line 10 of my program – but in any event in neither program is it strictly necessary.

```
5 REM COLOUR BAR SHORTENED ENTRY
10 POKE53280,11:PRINT"♥"
20 FORB=1TO8:READA:GOSUB40:NEXT
30 GETA$:IFA$=""THEN30
40 FORY=0TO24:FORX=ZTOZ+4:
   POKE1024+X+40*Y,160:POKE55296+X+40*Y,A:
   NEXTX,Y
50 Z=Z+5:RETURN
60 DATA0,6,2,4,5,3,7,1
```

I trust this simplified entry will encourage more readers to try it.

*R. A. Ramsden,
London N8.*

SETS FOR DISPOSAL

Owing to a move to a smaller house I have for disposal the following sets: three Thorn colour receivers fitted with the 2000 chassis, two working well, and a Ferranti 20T4 table type projection set dating from about 1954. As the 2000 was the first large-screen, all solid-state chassis to go into production and the 20T4 is certainly a venerable item I'm wondering if they would be of interest to a TV collector or historian. No payment would be required but they would have to be collected by appointment.

*C. E. Williams, 6 Swallowdale, Wightwick,
Wolverhampton, WV6 8DT.*

POST A PART ELECTRONICS

6 CHAPMAN COURT, CHARFLEETS ROAD,
CANVEY ISLAND, ESSEX SS8 0PQ.

Telephone 0268 690868
Telex 99305



TRADE COUNTER OPEN

ORDERS DESPATCHED SAME DAY
ADD 75p P&P, THEN 15% VAT.
ADD POSTAGE FOR OVERSEAS ORDERS.
ORDERS WITH AEROSOLS, PLEASE ADD 25p PER CAN.

Thorn 10Q 20W (3500) R751 Safety Resistor	75p
Pye 713 Speaker 5" x 3" 70Ω	1.00
Pye 713 Complete Tube Base Panel	
with Focus Slider & Leads	2.75
TX9 Complete Tube Base Panel	2.75
TX10 Complete Tube Base Panel	3.75
TX30 Complete Tube Base Panel	4.75
Pye 713 Control Knobs	4 for 50p
Tube Base Socket ITT CVC32	45p
Tube Base Socket Thorn 3000/8000 etc	50p
IC Insertor 16 Pin	50p
Large IC Extractor	50p
Crystal 4.43MHz	65p
EHT Lead & Cap for Split Diode Lopt	90p
Anode Cap	47p
Sanyo Anode Cap Assy with Lead. 12CTDC-CT-1G	65p
Degauss VDR E299D/HP230 3000/8000	25p
Degauss Thermister CB-RDH (TX90)	1.80
Control Knob Thorn TX90	4 for 2.00
On/Off Knob Thorn TX90	65p
Push Button Assy Thorn TX90	9.80
Tube Neck Correction Assy. 20AX AT1081	5.00
EHT Cable	Metre 25p
B7259 with Heatsink	14p
TI110 with Heatsink	40p
L129/130/131 Coil	10p
6MHz Ceramic Filter	25p
DL700 (Chroma) Chroma Delay Line	1.00
DL50 Chroma Delay Line	1.00
T9006A Lum. Delay Line	1.00
8K5/9K Lum. Delay Line	65p
Plastic Cover for 3K5 SP8385	5p
TX9 Back Ground Control 10K	15p
TX9 Gain Control 100R	15p
Thorn 2000 Focus Pot	1.00
Thorn 9000 Focus Pot	3.75
Thorn 9600 Focus Pot	2.00
Thorn 8K5 Focus Pot	2.40
Thorn 4000 Focus Pot	2.75
Thorn TX10 Focus Pot (New Type)	9.00

SERVICE AIDS	
Ambersil MS4 Silicone Grease	12oz 2.15
Ambersil Freezer	12oz 1.99
Ambersil Amberlube	6oz 1.89
Ambersil Ambertron	16oz 2.25
Ambersil Anti-Static Screen Cleaner	7oz 1.95
Ambersil 40+ Protective Lubricant	14.1oz 2.15
Ambersil Ambersilens Foaming Cleaner	13oz 1.26
Ambersil Circuit Lacquer	14oz 2.15

THICK FILM RESISTOR UNITS	
3500 Thorn (5 Pin Connection) video	1.70
4000 Thorn (4 Pin Connection)	1.90
725/731 Pye (6 Pin Connection)	2.20
713 Pye (6 Pin Connection)	2.20

FUSES	
20mm	1/4"
50MA 10 for 70p	250MA 10 for 65p
250MA 10 for 50p	750MA 10 for 65p
315MA 10 for 50p	7A 10 for 50p
500MA 10 for 50p	10A 10 for 50p
2.5A 10 for 1.00	20A 10 for 50p
3.15A 10 for 1.00	50A 10 for 50p

Thorn Mains TX 3000/3500	7.50
Thorn Mains TX 8000/8500	10.00
Thorn Mains TX 9000 (T701)	10.00
Thorn Mains TX 9600 (T512)	10.00
Thorn S.O.P.T 8000/8500	3.50
Thorn Scan TX 3000/3500	6.00
Thorn EHT TX 3000/3500	6.00
Thorn LOPT 9000	10.00
Thorn LOPT 9600	12.00
Thorn LOPT 1615	7.25
Thorn LOPT 1590/91	7.25
Thorn LOPT 1630/91	7.25
Thorn LOPT 8000	9.80
Thorn LOPT 8500	9.80
Thorn LOPT TX9	9.85
Thorn LOPT TX10	19.00
Thorn LOPT TX90	13.75
Pye LOPT 713	10.00
Pye LOPT 725	9.85
Pye LOPT 731	10.18
Philips LOPT G9	8.80
Philips LOPT G11	13.75
GEC LOPT 3113	7.40
Diode Split LOPT AT2076/35	14.75
Sanyo LOPT AM-WM-21	6.75
Sanyo LOPT AM-WM-4	7.30
Philips LOPT G8	7.30
Sanyo LOPT (CW21) 4-2751-44700	7.80
ITT LOPT CVC5-9	5.00
ITT LOPT CVC30	8.75
ITT LOPT CVC45	9.75
Baird 8750	10.25
Baird 8752	10.25
Thorn Line Drive TX. TX9 (T2)	3.00
Thorn Line Drive TX. 8K etc. (T402)	1.85
Thorn Line Drive TX. 9K (T705)	2.00
Thorn Switch Mode TX. 9K6 (T511)	3.75
Thorn Input Choke TX9 (L64)	4.00
Thorn Choke TX90 (L120)	2.95

300 Mixed Resistors	1.50
300 Mixed Capacitors	1.50
150 Mixed Electrolytics	2.00
100 W/W Resistors	1.00
20 Mixed Conv Pots	1.00
40 Mixed Pots	1.50
20 Mixed Sliders	1.00
40 Mixed Presets	60p
20 Mixed VDR & Thermistors	1.00
100 Mixed Ceramic Discs	1.00
20 Mixed Valve Bases	1.00

AC128	39	BC174B	23	BCX33	22	BF167	24	BFR62	28	NKT276	20
AC131	40	BC177	24	BCX34	22	BF173	24	BFR62	28	NKT453	1.65
AC138	40	BC182LB	12	BD115	49	BF179	32	BFR87	25	OT112	1.32
AC141K	38	BC183J	12	BD131	49	BF186	33	BFR90	1.74	RI038	80
AC142K	38	BC184L	12	BD133	46	BF184	30	BFR91	2.08	RI039	80
AC153	39	BC187	24	BD133	46	BF185	30	BFR91	2.08	RI038	80
AC176	33	BC204	15	BD139	36	BF194	16	BFX38	40	R2008B	1.40
AC176K/	33	BC208	9	BD140	36	BF195	16	BFY50	30	R2010B	1.10
AC128K	93	BC212L	9	BD144	1.70	BF196	16	BFY51	34	R2305	80
AC188	38	BC213L	12	BD150	50	BF197	15	BFY52	34	R2322	50
AD142	1.18	BC237	12	BD163	98	BF198	98	BRC116	1.50	R2443	25
AD143	1.08	BC238B	8	BD201	74	BF199	15	BRC1693	1.43	RCA16446	30
AD149	98	BC238L	8	BD203	78	BF223	78	BU105	1.00	RCA16599	1.25
AD161	32	BC250A	15	BD204	99	BF224	19	BU126	1.10	RCA16799	1.40
AD162	32	BC251	8	BD222	48	BF238	20	BU207	1.05	RCA16799	1.13
AD263	1.05	BC252A	20	BD225	52	BF240	9	BU208	1.15	RCA16800	1.42
AF127	45	BC294	37	BD232	50	BF241	21	BU208A	1.15	RCA16802	1.38
AF139	38	BC301	32	BD233	60	BF255	10	BU226A	1.30	RCA16815	1.20
AF239	41	BC303	31	BD234	60	BF256LB	38	BU407	1.70	SP8385	65
BC107	15	BC307	10	BD237	55	BF256S	20	BU408	2.76	S1299	2.25
BC108	15	BC308	8	BD238	65	BF257	28	BU500	2.30	S2800	1.25
BC109	15	BC309	14	BD241	59	BF259	28	BU526	2.46	T6050V	1.30
BC115	16	BC327	18	BD244	85	BF271	25	BU806	1.80	T6052V	1.30
BC117	21	BC328	18	BD278A	81	BF274	11	BU807	2.94	T9003V	1.25
BC125	26	BC337	17	BD386	68	BF337	29	C1129	9	T9010V	1.45
BC126	23	BC338	17	BD433	71	BF338	34	C1172B	9	T9036V	1.30
BC139	27	BC347	8	BD437	83	BF355	40	E5386	54	T9044V	1.00
BC141	34	BC394	8	BD592	1.20	BF362	50	E9003	28	T9039V	1.10
BC142	30	BC454	8	BD589	1.20	BF391	21	E9005	25	TI45X	50
BC143	31	BC455	8	BD677G	1.35	BF394	16	ME0404	10	TI45X	48
BC147	12	BC456	10	BD679	1.42	BF421	47	ME0412	10	TI106C	42
BC148	12	BC460	40	BD701	1.04	BF423	53	ME6002	10	TP29	42
BC149	12	BC463	22	BD702	1.12	BF460	43	MJ2501	2.36	TP30	35
BC153	16	BC546	8	BD707	95	BF453	53	MJ3001	2.21	TP31	35
BC1540R	16	BC547	12	BD708	95	BF458	37	MJE340	50	TP32	43
BC154YL	16	BC548	12	BD839	1.30	BF459	40	MJE520	50	TP33	61
BC157	12	BC549	8	BDX10	3	BF461	59	MJE2955	1.40	TP41	42
BC158	12	BC557	10	BDY20	1.09	BF566B	35	MJE3055	15	TP42	45
BC159	15	BC558	10	BDY82	99	BF596	15	NKT241W	8	TI110	61
BC171	9	BC559	8	BF137	20	BF694	16	NKT241G	8	TS91	25
BC172	9	BC595	8	BF153	20	BF757	62	NKT241Y	8	ZTX550	30

INTEGRATED CIRCUITS							
BRC1330	1.40	SN7613ND	1.80	TBA530	1.26	TDA2002	2.80
BRC3064	1.00	SN76023N	1.80	TBA540	1.00	TDA2030	2.10
BRC/M/200	1.00	SN76033N	2.00	TBA5500	1.82	TDA2522	2.10
BRC/M/300	1.00	SN76115	2.00	TBA560C	1.56	TDA2530	2.61
CA3060	1.58	SN76131N	1.58	TBA651	2.05	TDA2540	3.50
LM1303P	1.48	SN76226N	1.25	TBA720A	2.49	TDA2566	3.50
ML231B	2.20	SN76227N	1.00	TBA750	2.49	TDA2581	3.00
ML237B	2.00	SN76530P	1.20	TB8000	1.60	TDA2591	1.96
ML239B	1.26	SN76622N	1.00	TB810S	1.00	TDA2611A	1.95
MC1327AP	2.85	SN76680N	80p	TB810AS	1.00	TDA2644	2.90
MC1358P	1.30	SN76666N	75p	TBA920	2.00	TDA2699A	1.50
MC1455P	18p	SN76744	1.92	TBA950	1.55	TDA2560	6.00
MC14516BCP	60p	SY153A	2.50	TBA1440	1.92	TCEP100	3.48
SAA1025	7.20	TA7117P	1.00	TCA2705A	1.85	TEA1009	1.95
SAA1124	4.50	TA7109AP	2.80	TCA2700C	1.85	MC14425P	4.80
SA5010	6.00	TAA611	1.40	TCA2700Q	1.95	MC14544	4.50
SL432A	1.80	TBA120B	1.20	TDA1004A	4.80	UA758PC	2.50
SL1430	2.50	TBA120C	1.20	TDA1035T	3.50	UA1008A	2.66
SL1432	2.50	TBA120Q	70p	TDA1037	2.72	UA1008A	2.66
SN15846N	60p	TBA120S	70p	TDA1170	2.15	ULN2185	1.30
SN74123N	80p	TBA120U	1.00	TDA1170S	1.50	UPC1355C	5.75
SN74154N	1.40	TBA395	1.00	TDA1200	2.42	SC9488P	1.40
SN76001N	1.40	TBA480Q	1.40	TDA1270	2.76	SC9511P	1.40
SN76110N	1.14	TBA510	1.90	TDA1327	2.53	SW153	2.50

Thorn 8/8K5 ex equip panels untested	2.88	Thorn 3/3K5 ex equip panels untested	3.75	Thorn 4000 Convergence panel ex-factory	3.75
PSU	3.75	PSU	3.75	Thorn 4000 PSU panel ex-factory	2.50
FTB	4.00	FTB	2.50	Thorn 3K5 beam limiter board	1.75
Decoder	4.00	Video Chroma	2.00	new	1.75
Thorn 9K ex equip panels untested	12.00	IF	3.75	Thorn 3/3K5 EHT & scan TX + R2008B on alum chassis ex-factory	1.80
PSU	5.00	Conv. 3K5	3.75	Thorn 8/8K5 damaged FTB for spares	1.25
Decoder	5.75	Autovox Decoder FG01 boxed	5.00	Thorn 8/8K5 damaged decoder for spares	2.25
UHF TV Aerial for portable	50p	Coax Plugs	10 for 1.65		
Indoor Aerial With Reflector	2.50	Band Change Switch Assy, Pye 725	40p		
to Help Combat Ghosting Problems	38p	Coax Cable Low Loss	Metre 22p		
Line Connectors	38p	Switched Flush Fitting Aerial Outlet	1.00		

10 Spark Gaps	1.00
10-16 pin Quil IC Socket	90p
20 Assorted TV Knobs	1.00
10-16 pin Quil to Dil IC Socket	90p
100 Mixed Diodes	1.00
50 Mixed Mica Washers	65p
300 Mixed Resistors & Capacitors	1.50
10-16 pin Dil to Dil IC Socket	1.00
50 Electrolytics & 50 Capacitors	1.00
50 Mixed Poly Capacitors	1.00
20 Mixed Valve Bases	1.00

BF154	25	BFR52	31	NKT276	20
BF167	24	BFR62	28	NKT453	1.65
BF173	24	BFR81	29	OT112	1.32
BF179	32	BFR87	25	OT121	2.08
BF186	33	BFR90	1.74	RI038	80
BF184	30	BFR91	2.08	RI039	80
BF185	30	BFR91	2.08	RI038	80
BF194	16	BFX38	40	R2008B	1.40
BF195	16	BFY50	30	R2010B	1.10
BF196	16	BFY51	34	R2305	80
BF197	15	BFY52	34	R2322	50
BF198	98	BRC116	1.50	R2443	25
BF199	15	BRC1693	1.43	RCA16446	30
BF223	78	BU105	1.00	RCA16599	1.25
BF224	19	BU126	1.10	RCA16799	1.40
BF238	48	BU207	1.05	RCA16799	1.13
BF240	9	BU208	1.15	RCA16800	1.42
BF241	21	BU208A	1.15	RCA16802	1.38
BF255	1				

TRADE ANNOUNCEMENT

CHROMA VISION (Manchester) NOW OPEN!!!

95 LANGWORTHY RD, SALFORD M6 5PH. Tel. No. 061-736-6333

811 WASHWOOD HEATH RD, WARD END, BIRMINGHAM 8. Tel. No. 021-784-2561

Large range of late model TV's and Videos at low, low prices

THORN AND PHILIPS TELE-TEXT, REMOTES AND BASICS

★ PHILIPS

Working			Untested	
G11 660	£45	Tested G11	G11 660	£35
G8 550 22"	£20	Tubes	G8 550	£12
G8 520 22"	£15		G8 520	£8
G8 560 20"	£30		G8 560	£20

★ THORN

9600	£38	Tested Thorn	9600	£30
9000	£28	9000 Tubes	9000	£20
8800	£20		8800	£15

★ PYE

G11	£55	Tested 22" 26"	G11	£45
222 22"	£20	Delta Tubes	222 22"	£15
725 20"	£25		725 20"	£20
Chelsea 18"	£25		Chelsea 18"	£20

★ ITT

CVC 30	£38	Buy in one's	CVC 30	£30
CVC 20/3	£35	or 100's	CVC 20/3	£25
CVC 20	£30		CVC 20	£25

★ GEC

In line (Starline)	£50	And Many More, i.e. Bush T20	£35
G.E.C. 2201	£25	Decca 100	£35. Japs, Tandburg etc.


Too many to list! Why not come along and have a look

**★ WORKING & SERVICED!!! VHS VIDEOS 100's IN STOCK
1000's MORE UNTESTED SETS OFF THE PILE**

★ Lorry loads direct from source ★ Delivery arranged

All prices subject to V.A.T.

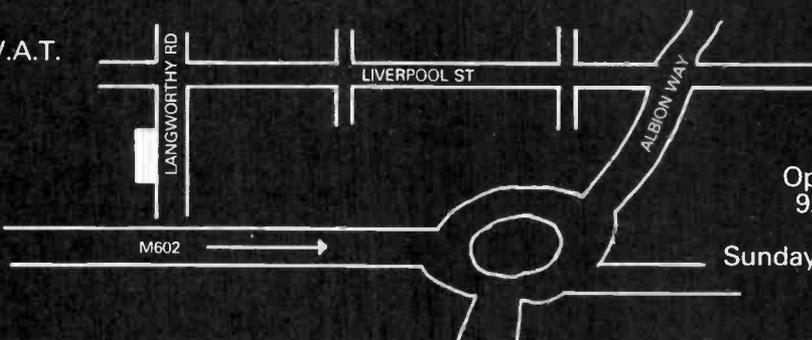WE ARE HERE
Only 2 minutes from
end of motorway



Open 6 days a week
9.30 a.m.-6.30 p.m.

Sundays by appointment

The Vet's Problem

Les Lawry-Johns

Not BO but B&O – one that gave me almost as much heartache as that NordMende. If it had been anyone else's I'd have told him to take it back where he got it from, but he's such a nice chap and we do have a dog, a cat and a bird. That bird is definitely female by the way: she doesn't talk but makes a lot of noise. You can't touch her unless she's having one of her freak outs, when she hunches her shoulders, sticks her neck out and babbles away in some strange alien tongue. You can then stroke her till she comes to. She then straightens up and lashes out with her beak. I think it's part of the mating game but she hasn't got one (so far).

The Spiders

Which brings me to the next horror story. Upon removing the B and O's rear shell – release bottom catches, lift up and off the top tongues – I caught sight of a long brown envelope stuck to the right side of the chassis. Removing the envelope and opening it I found a folded booklet with the circuit details. Inside the fold were the bodies of two spiders which must have been there a long time: one was complete but only the shell of the other remained, no doubt the male who had provided the female with her last meal.

The Set

The actual repair (having buried the spiders with due ceremony) turned out to be something of an ordeal, as the fault was intermittent. The set would suddenly trip (partially) after it had been on for quite some time, the picture shrinking and then returning rapidly to normal. It didn't shut off to enable proper tests to be made. The power unit is at bottom centre and was removed so that we could try to make some voltage checks. After a long time it transpired that the voltage at the collector of the chopper transistor remained steady while the base and emitter voltages varied, suggesting an overload. I rather doubted this, feeling that the fault was in the power supply itself.

Cold tests were out of the question as the fault was of such an intermittent nature, so we invoked Dante's Law: go where the heat is. This proved valid and the fault no longer occurred when the chopper driver transistor, BD something or other, was replaced. My fading memory suggests that we fitted a BD203 but I could be wrong. I can't check up on it as the circuit is back inside the set, at the vet's home (sans spiders), and I don't have another copy to jog my memory. I've even forgotten the model number and as no bill was presented I can't look up the copy.

Who's a Ninny?

Next balls up. Who was it who completely stripped down a Fidelity IS100 audio stack system to get at the cassette head in order to solder one wire on, then put it all together again only to find that removal of two screws from the front cassette cover exposes the head and just

gives room to resolder? I won't tell you who it was but I won't do it again.

Mack and Millie's G11

You remember me calling at Mack and Millie's house, parking on the pavement and getting a rocket from Millie . . .

"Curb crawlers are creepy Les but pavement parkers are putrid."

"Only two wheels, Millie."

"Half a wheel is enough – MORE THAN ENOUGH!"

Well they don't seem to have much luck with their G11. They phoned to report "a white line across the screen".

So along I went and parked in their driveway. I'd taken with me a spare timebase panel (upper left) and some fuses. I checked the second fuse up on the line output panel. It was intact. I checked the soldering to the base of the TDA2600 field timebase i.c.'s holder, and as this seemed to be o.k. I fitted my spare panel. After this I switched on, confidently expecting to see a full raster. Just a white line. Feeling a bit deflated, I tapped the top centre dynamic convergence correction panel. The line flicked to a full raster then collapsed again. Oh dear, I've brought the wrong panel.

I removed the correction panel and examined it closely for cracks and dry-joints. As there didn't seem to be any I refitted the panel and without clipping it down switched on to see if a bit of probing might help to identify the culprit. There was a good, full picture. It wouldn't collapse until I clipped it down. So I unclipped it and told them I'd be back on the morrow with a replacement but that the set would meanwhile be all right as I'd taken the pressure off the trouble spot.

Next day I returned with the required panel and to save time I ran the car up on the pavement outside. I fitted the panel and prepared to depart. Millie said she had to collect her grandchildren from school and came out with me to get her car from the garage.

"THAT CAN'T BE YOUR CAR STUCK UP ON THE PAVEMENT AFTER ALL I'VE SAID!"

"After all you've shouted Millie. See you in court dear."

The Repair

Back at the shop it took an ohmmeter to locate the intermittently open-circuited track, very near to connector 15A4. A jumper lead was quickly soldered in place to put paid to any further hanky-panky.

A Solution

I'm fed up with the way this country's going. Everybody seems to be convinced that unless they put up prices, charges, wages – everything every year – they'll be uneconomic and go under. What we need is a universal catch phrase for use at every check out, written on every invoice and bill. Everybody together then, "LESS TEN PER CENT". Salaries, wages, fares, charges. O.K., some won't do it, some perhaps can't. They'll be the unpopular minority. Leave marked up prices as they are, but subtract ten per cent at the time of payment. "Less ten per cent, less then per cent" – can't you just hear it? I can hear the objections: importers etc. But it could be done if we really wanted to. All right we don't. But dafter things have happened.

A Visit to MCES – VCR Head Alignment Principles

Steve Beeching, T. Eng.

Regular readers will recall that I had a problem over obtaining suitable video heads when I was busy rebuilding some VHS machines earlier this year. The VCRs were of the very early type, with a round video drum turntable. The later type with relay connector pins wouldn't fit. I needed a supply of the earlier type of drum with the PCB type terminal connector.

This was when I came across the video head drum reconditioning service provided by MCES of Stretford near Manchester. Provided a drum is in good condition and is not scratched or marked they will fit new ferrite tips for less than half the cost of a new head assembly.

I was sceptical about the idea of replacing head tips because of the accurate alignment required but nevertheless decided to try a few. The results they provided were very good, much better than I had expected. It seemed worth investigating further and I was invited along to MCES to see for myself.

MCES's Services

MCES are fairly well known in the TV trade for their tuner, teletext and remote control panel repair services. They now handle VCR aerial booster amplifiers and modulators in addition to providing the drum reconditioning service. The investment that was required to install equipment for tuner repair work was considerable but the cost of equipment for fitting video heads is very high indeed, well into six figures. At the time of writing a single alignment jig console is in use; a second is on order for delivery this autumn and a third is due next spring.

The alignment equipment is situated in a room entered via an air lock of two doors, though you are not obliged to wear a space suit! Air conditioning maintains a clean air supply and the temperature is stabilised to maintain correct alignment conditions.

Head drums sent to MCES are first stripped of the old tips, then washed in detergent and dried. This is followed by further cleaning in an ultrasonic bath. New heads are then fitted, ready for aligning.

Alignment Console

The alignment jig (see Fig. 1) has a central turntable on which the drum to be aligned is clamped. Microscope lenses are situated at either side, precisely 180° apart. Cameras are fitted to the lenses, the images being displayed on two monitors mounted above and behind the lenses. A view of each video head tip is thus seen, along with vertical and horizontal cursor lines that seem to be electronically generated. There are also three digital readouts, two beneath the monitors and a third in the centre.

Head Projection

A micrometer vernier adjuster on the left-hand lens moves it towards and away from the drum. It's used to measure the head tip projection. The head tip is first

moved out of the way by revolving the turntable. The lens is then adjusted to focus on the drum surface. The projection counter is zeroed, the lens is moved out again and is refocused upon the head tip when this has been revolved back into view. Correct focus occurs when a special moiré interference pattern appears – at the precise focal point on both surfaces. The distance moved by the vernier adjuster is displayed by the digital projection counter. For correct alignment the tip projection from the drum is 51.5µm. The projection of both tips is set by the same lens – the drum is revolved on the turntable by 180° to bring the second head into view.

Head Differential Adjustment

The 180° differential is set to a lateral tolerance of 1µm by adjusting the head tips so that they sit between two vertical cursor lines displayed on each monitor, the cursor lines having been calibrated to exactly 180°. If one head is out of specification, the cursor line is set to centralise the gap within the pair on the left-hand monitor, using an electronic shift of both the left-hand and right-hand pairs of lines in tandem, thus maintaining calibration. The gap shown on the right-hand monitor is then moved into the cursor area by means of the lens vernier adjuster, the counter beneath the right-hand monitor showing the lateral shift in microns. Each head is then adjusted by half this figure to bring them into line. This is repeated a number of times, gradually adjusting the heads so that they are 180° apart to within a lateral tolerance of 1µm.

Head Height

An interesting point I learnt is the difference in head tip height between different types of drums. MCES had determined their own 0µm reference level then measured a large number of standard production heads to obtain an accurate height value above this reference, including production spreads.

The counter in the centre is used for height adjustment. The right-hand microscopic lens can be moved up and down by a vernier adjuster, the counter reading the

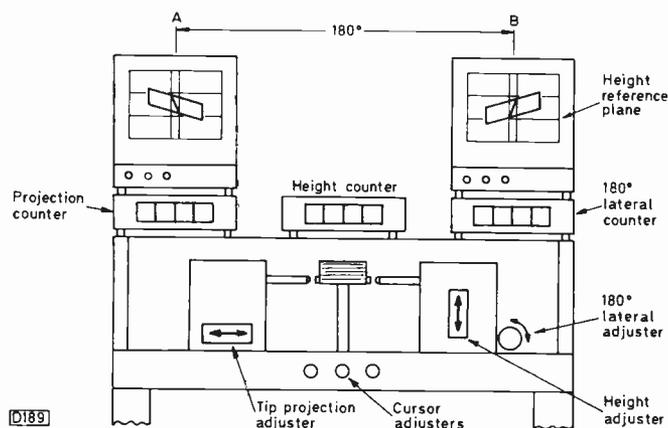


Fig. 1: Layout of the head alignment console.

amount of this adjustment. The difference in height between the two heads in the drum is measured by first setting the lower edge of one head tip on a horizontal cursor line on the right-hand monitor. The drum is then rotated through 180° and the counter zeroed. The lens is adjusted so that the lower edge of the second head is aligned on the same cursor, the amount of adjustment being displayed on the counter. The height difference between the two heads on a drum is kept to within 2µm, though the overall height of the pair may be within 5µm of the value for a particular type of drum.

In general, the height of Hitachi head tips is 36µm while for Panasonic the figure is 45µm. JVC head heights are 54µm (F), 62µm (J), 64µm (L) and 66µm (M): the early D types are 104µm and the G10 series 95µm. In terms of replacement drums this means that replacing an F type with a G10 type will result in the new head tips being 41µm higher in the VCR. This is almost a track width, and the audio/sync head will require lateral adjustment to set the tracking range to compensate, using a standard test tape as a reference. MCES ensure that reconditioned heads for Ferguson/JVC machines have head tip heights that conform with the suffix letter to within ±5µm. They have found that other "general purpose" heads do not conform to any height specification, some being more than 12µm out. Whether or not this is critical depends on the engineer's ability to set the tracking range by the audio/sync head.

VCR Adjustments

One normally sets up the PG switching points and the response of the replay preamplifiers as necessary after drum replacement. The preset tracking control is set for maximum f.m. output on replay of the machine's own recordings with the main tracking control set midway. The final adjustment, to compensate for head tip height difference, is to replay a standard reference tape and adjust the audio/sync head laterally (sideways).

Tip Thickness

So that the heads are suitable for a wide range of models, MCES use a ch. 1 head tip that's 60µm thick and a ch. 2 head tip 80µm thick (thickness being the track width). This makes the heads equally suitable for standard or slow motion/still picture machines. Note that whilst the two heads have a width greater than the standard 49µm track the alignment of their lower edges on the same plane ensures that the recorded tracks are 49µm wide – by over recording of the excess track width. The head gaps are glass filled, and in order to maintain consistent quality all head tips come from the same Japanese manufacturer.

In Conclusion

After alignment, the drums are vacuum packed in polystyrene boxes for long shelf life.

MCES have spent a lot of time and money on ensuring that their reconditioned head drums are of high quality. Output is at present limited – at least until more alignment jigs have been installed – due to the careful quality control exercised. They have a large quantity of JVC drums in stock awaiting reconditioning but are short of Hitachi, Panasonic and Sharp drums – they'd welcome surplus drums. MCES can be contacted at 42-46 Moss Road, Stretford, Manchester (061-865 6021).

BILLINGTON VALVES

23 Irwin Drive, Horsham, West Sussex RH12 1NL
Mail Order only – No Callers

CLOSING DOWN FEBRUARY 1986 – CLEARANCE OF REMNANT STOCK AT BARGAIN PRICES!

These wholesale prices when buying 10 or more of one type. EF80 30p, ECC82/12AU7 35p, GY501 £1, PCF802 50p, PCL 82 60p, PCL84 40p, PCL805 50p, PCL86 50p, PL504 90p, PL508 £1.70, PL509 £4.25, PY500A £1.50, PY88 40p, PY81/800 60p, PY801 60p. Please add post/packing @ 70p and VAT @ 15% to all orders (wholesale or retail).

TRADE/EXPORT ENQUIRIES WELCOME. Please ask for wholesale price on any type not listed.

Retail Prices:	EF80	ECC82	GY501	PCF802	PCL 82	PCL 84	PCL 805	PL 504	PL 508	PL 509	PY 500A	PY 88	PY 81/800	PY 801	
EF80	£0.30	ECC82	£0.35	GY501	£1.00	PCF802	£0.50	PCL 82	£0.60	PCL 84	£0.40	PL 504	£0.90	PL 508	£1.70
ECC82	£0.35	GY501	£1.00	PCF802	£0.50	PCL 82	£0.60	PCL 84	£0.40	PL 504	£0.90	PL 508	£1.70	PL 509	£4.25
GY501	£1.00	PCF802	£0.50	PCL 82	£0.60	PCL 84	£0.40	PL 504	£0.90	PL 508	£1.70	PL 509	£4.25	PY 500A	£1.50
PCF802	£0.50	PCL 82	£0.60	PCL 84	£0.40	PL 504	£0.90	PL 508	£1.70	PL 509	£4.25	PY 500A	£1.50	PY 88	£0.40
PCL 82	£0.60	PCL 84	£0.40	PL 504	£0.90	PL 508	£1.70	PL 509	£4.25	PY 500A	£1.50	PY 88	£0.40	PY 81/800	£0.60
PCL 84	£0.40	PL 504	£0.90	PL 508	£1.70	PL 509	£4.25	PY 500A	£1.50	PY 88	£0.40	PY 81/800	£0.60	PY 801	£0.60
PL 504	£0.90	PL 508	£1.70	PL 509	£4.25	PY 500A	£1.50	PY 88	£0.40	PY 81/800	£0.60	PY 801	£0.60		
PL 508	£1.70	PL 509	£4.25	PY 500A	£1.50	PY 88	£0.40	PY 81/800	£0.60	PY 801	£0.60				
PL 509	£4.25	PY 500A	£1.50	PY 88	£0.40	PY 81/800	£0.60	PY 801	£0.60						
PY 500A	£1.50	PY 88	£0.40	PY 81/800	£0.60	PY 801	£0.60								
PY 88	£0.40	PY 81/800	£0.60	PY 801	£0.60										
PY 81/800	£0.60	PY 801	£0.60												
PY 801	£0.60														

ALL VALVES (WHOLESALE/RETAIL) ARE NEW, BOXED, PERFECT AND GUARANTEED 90 DAYS.

MUL/MAZ denotes Mullard/Mazda brand;
† denotes foreign made valve

WE CAN SUPPLY CRTs FOR CTV, SCOPES AND VDUs – SAE FOR QUOTATION. ALSO UNUSUAL VALVE TYPES, EG: FOR JAPANESE AUDIO/TV EQUIPMENT, AND RUSSIAN NUMBERED TYPES – SAE FOR QUOTATION

Please allow 7 days for delivery.

WANTED: We require a quantity of valves PX4, PX25 to fulfil an outstanding order. We will pay high prices for these, in any quantity large/small (including equivalents PP3/250, PP5/400, DA30)

TV LINE OUTPUT TRANSFORMERS

PRICES INCLUDE VAT & CARRIAGE

Delivery by return of post.

RANK BUSH MURPHY	
A774 with stick rectifier	9.78
A816, T16, T18, Z12, Z115	10.35
T20, T22, T26, Z179, A823	11.50
Z718 Basic unit	13.50
T24e, T24h split diode	P.O.A.
DECCA: 1210, 1211, 1511	11.50
1700, 2001, 2020, 2401, 2404	9.20
CS1730, 1733, 1830, 1835	9.20
30, 70, 80, 90, 100, 130 Series	9.20
FERGUSON, THORN: 1590, 1591	9.20
1690, 1691. built in rect.	9.78
1600, 1615, 1700 series	P.O.A.
1790 mono portable	P.O.A.
3000, 3500, 8000, 8500, 8800	P.O.A.
9000, 9200, 9300 series	12.00
9500, 9600, 9650 series	10.99
9800, TX9, TX10 series	P.O.A.
MOVIESTAR 3781, 3787	12.00
FIDELITY: FTV12 mono	10.35
CTV14R, CTV14S colour	15.83
G.E.C. 2047 to 3135 mono	9.20
1201H, 1501H, 2114, 3133, 3135	9.20
DUAL & SINGLE hybrid col.	10.00
SINGLE STD solid state	12.00
SINGLE STD split diode	P.O.A.
INDESIT: 24EGB hybrid	9.50
12LGB, 12SGB mono portables	10.35
WINDINGS	
TYNE: main winding	6.80
RBM: T20, T22, T26, Z179	6.33
WALTHAM: W125 eht winding	2.37
WALTHAM: W190, W191 eht coil	£6.00
KORTING: hybrid winding	6.90
ITT: VC200 to VC402	9.20
CVC1, CVC2 (FORGESTONE)	11.50
CVC5, CVC7, CVC8, CVC9 series	9.20
CVC20	10.35
CVC25, CVC30, CVC32, CVC45	9.20
CVC40, CVC1200, 1210, 1215	P.O.A.
FT110, FT111. P/no AT2063/02	11.50
PYE: 169, 173, 569, 368 series	9.20
CT200, CT200/1, CT213 series	10.35
725-731, 735, 737, 741 Series	9.78
PHILIPS: 170, 210, 300 series	9.20
320 series	9.78
TX, T8 mono	P.O.A.
G8 and G9 Series	9.20
KT2, KT3. series colour	9.20
G11, K30. split diode	P.O.A.
BINATONE: 9909, 9798, 9860	P.O.A.
DORIC Mk3	11.50
FINLUX 9560, 9670	P.O.A.
GRUNDIG: most models in stock	
NORDMENDE: FC125, Z206, Z306	11.50
SANYO: 5101, 5103, 7118, 7130	P.O.A.
SHARP: C1851H, C2051H	P.O.A.
TOSHIBA: C800, C800B	19.45
TANDBURG: 190, CTV2-2, CTV3-3 P.O.A.	
TELEFUNKEN: most models in stock	
LINE OUTPUT TESTER	16.79
Tidman Mail Order Ltd., 236 Sandycroft Road, Richmond, Surrey. Approx. 1 mile from Kew Bridge. Phone: 01-948 3702 Mon-Fri 9 am to 12.30 pm & 1.30-4.30 pm Sat 10 am to 12 noon.	

TV Fault Finding

Reports from Mick Dutton, Larry Ingram,
Keith Hamer and Garry Smith

Philips K30 Chassis

Tripping was the complaint with this set. We checked the diodes in the line output stage, the line output transistor, and swapped the power supply panel. There was no obvious fault so we decided to lift the line output transistor's collector to see whether the power supply then produced the correct output. As the h.t. voltage was right we came to the conclusion that the line output transformer was probably defective, but the fault was still present when a replacement had been fitted. Drastic action was now called for so we supplied the set via a variac and removed R7354 to disable the excess current trip. We increased the supply slowly and a small, bottle-shaped raster appeared: the h.t. started to fall despite increasing the supply. The penny then dropped. The output from the mains bridge rectifier was low at only 220V instead of 285V because the reservoir capacitor C1560a (200 μ F) had gone completely open-circuit. **M.D.**

Grundig 8610

This was one of the last models to use a thyristor line output stage. It has an in-line gun tube and an EW diode modulator module. The symptoms were bends in the centre of the raster, similar to a hum effect, and not quite enough width. After no more than fifteen minutes the bends went and just enough width was obtained – none of the adjustments gave any more width. No voltage readings or scope displays gave any clues, except that the output from the EW module seemed to be a little on the low side. A great many things were tried before we discovered that the culprit was the +D (36V) supply reservoir capacitor. Obvious when you realise that the +D supply to the field output stage is derived from the EW modulator circuit, but not at the time! **L.I.**

ITT CVC45/1 Chassis

"Dead" said the job card but on switching the set off it momentarily came to life, suggesting that the line timebase was all right. A replacement power supply panel was to hand and fitting this restored normal operation. The offending item turned out to be R809 (220k Ω) in the trip circuit: it was completely open-circuit. **K.H.-G.S.**

Hitachi/GEC NP8CQ Chassis

Intermittent chroma on one of these sets was traced to an uncropped lead on R620 on the main panel – it's part of the field flyback pulse coupling network. The rear plastic panel support retaining strip was pressing against the lead, causing it to short intermittently to jumper lead J723. **K.H.-G.S.**

Thorn TX9 Chassis

This receiver (PC1040 main panel) was dead and on inspection the mains input filter choke L64 was found to be short-circuit. There was also some evidence of burning. Replacement of the choke revived the set but after a short soak test it would intermittently go dead. The trouble was found to be due to the mains rectifier thyristor CSR1

(T9053V): freezing it brought the set back to life, heat it and the set went dead again. The only other snag was a badly fitting back cover: those top turnbuckles are something of a nuisance. **K.H.-G.S.**

Pye 725/735 Series Chassis

The main complaint was that the sound level fluctuated, especially at low settings of the volume control. The field engineer had already checked the plug/socket connections at the front control subpanel. Movement of the volume control at low settings produced the fault so a replacement was fitted. On soak test the fault was still found to be present however. A TBA750Q intercarrier sound/audio amplifier i.c. is used, with the slider of the d.c. volume control linked to pin 13 which is decoupled by C238 (10 μ F). This electrolytic gave a leaky reading, replacement providing a complete cure. After replacing the usual first anode supply feed resistors and a couple of the presets, which had fallen in value, the overall picture quality was much improved. **K.H.-G.S.**

Thorn TX10 Chassis

The fault with this set was e.h.t. but no raster. The tube's first anode voltages at pins 5, 7 and 11 on the base panel were correct but the voltages at all three cathodes were high at 200V instead of 120-150V. The voltages at the emitters of TR651/2/3 in the RGB output stages were all higher than the correct 2-2V and it turned out that the green LED D657, which should link them to chassis, was open-circuit. This LED acts as a voltage stabilizer. **K.H.-G.S.**

GEC C2110 Series

The complaint was intermittent colour. Fortunately the colour was absent when we switched on. Our luck soon vanished however when the colour suddenly returned a few seconds later. Then it disappeared again.

Attention was directed to the small subpanel that bridges the upper and lower decoder panels. Slight movement of this made the chroma come and go and examination revealed dry-joints at both ends of C251 (0.33 μ F), which is connected to pin 13 of the TBA540Q reference oscillator i.c. In fact the capacitor could be pulled from the panel with very little effort. Thinking back, we came across the same fault some years ago. The capacitor in question is a green rectangular block type bearing the name "FILMCAP". **K.H.-G.S.**

Thorn TX9 Chassis

We've encountered two cases of an effect not unlike sound-on-vision on receivers fitted with this chassis. When the first one came along a fault on the i.f. subpanel was suspected and a replacement board cleared the fault. The culprit was traced with the help of a can of freezer. In both cases it turned out to be C38 (0.22 μ F) in the a.g.c. circuit. This capacitor sits directly below the SAWF. **K.H.-G.S.**

Approaches to TV Servicing: Quick Steps

S. Simon

Last month in this series we discussed the ITT CVC20 chassis. This time we propose to dwell for a little while on the later CVC800-CVC801 chassis employed in models such as the CT0500 etc. But before doing so we should make good an unforgivable omission that occurred in the original Approaches article which dealt with several chassis including the Philips G11. Sorry. Whenever a set fitted with this chassis is serviced the colour of the 470 μ F h.t. reservoir capacitor C4029 should be checked – it's at the upper centre of the lower right power board. If it's red or green, remove it (three tags). Examine the rivets of these tags. If they appear at all blackened, fit a new capacitor – one with larger rivets. If there's no sign that arcing has occurred, apply a screwdriver blade to the rivet and hit the screwdriver's handle with a heavy object such as a hammer to indent the rivet on to the tag. Only the red and unmarked tags require this treatment – the yellow tag is unused. It's essential that the rivet makes good contact with the tag as arcing here can and does harm the BU208A line output transistor, the TDA2600 field timebase chip and the tube. Most of you will already know about this, but there may be one or two who don't.

ITT CVC800/CVC801 CHASSIS

The CVC800/CVC801 chassis employ a switch-mode power supply that can cause some headaches – and severe depression – on occasions. Many factors can cause complete shut down, and some can be difficult to trace. Routine steps to take are to check that the mains supply is reaching the bridge rectifier and that this is producing some 300V or so across its reservoir capacitor C658 (220 μ F). This voltage should be present at the collector (body) of the BU126 chopper transistor (right side front). The similar looking transistor farther to the rear of the panel is the BU208 line output transistor, which is driven by a secondary winding on the chopper transformer. The BU126 is driven by a small transformer whose secondary winding is connected between its base and emitter. The emitter of the BU126 is also connected to pin A of the chopper transformer. 110V should be present at the output from this transformer, pin C. This output is taken to a point marked +110V on the lower part of the board.

Now note this. It's marked +110V and that's what it should be. If a reverse or pulsed reading is obtained, as it often is, it's most likely that the h.t. smoothing capacitor C757 is open-circuit. This is a 10 μ F electrolytic and one of 450V rating should be fitted as a replacement. Failure of this capacitor is becoming quite common on these and several related ITT chassis that use a switch-mode power supply.

If on the other hand the voltage is d.c. but very low, remove the scan coils plug (the one with the loop on it) from the horizontal panel and try again. This action disconnects the h.t. supply to the line output stage. If the 110V supply is then restored, check for shorts in the line output stage, starting with the BU208 output transistor. This simple line of attack will be found to be successful in a surprising number of cases.

In cases where the 300V supply is present at the body of

the BU126 but there's no output at the +110V point, the condition of the driver stage should be checked. Look for the driver transistor T750, a BC546A, just below the small transformer it drives. The 300V line supplies its collector via the 33k Ω wirewound resistor R752. Check these items carefully before continuing the search by checking the transistors, diodes etc. in the rest of the switch-mode power supply.

We cannot speak with any authority about the rest of these sets simply because we've not had any troubles worth speaking about. These few remarks should help to clear up most faults in the power supply however. Remember that 10 μ F electrolytic.

THORN 3000/3500 CHASSIS

The first switch-mode power supply to appear in a UK TV set was that in the Thorn 3000-3500 series chassis. Many of these sets are still giving sterling service. Although they are often considered to be unworthy of serious servicing attention, the condition of the tube should really be the deciding factor. The power supply and line timebase panels are available at very reasonable prices if a repair proves too difficult or time consuming. A replacement panel can be fitted if held in stock, the repair being completed when time permits.

Several items on an old power supply panel may need to be replaced. Neglect to do so may cause trouble later – being a lazy person myself, I know only too well what the penalties are. Reverse the panel and examine the condition of the large multisection main electrolytic can. Bumps and corrosion are a sure sign of trouble to come and one or two of the tags may be found badly burnt. Replace this item then turn the unit over and examine the 1,000 μ F, 63V electrolytic at the front end. All too often this is responsible for failure to start up. A voltmeter connected to the positive tag should record 45V. If the electrolytic has dried up a lower voltage reading will be obtained and this will prevent the chopper firing.

Small Picture

Quite often the fault is a small picture with the bottom folded up. This may be intermittent. The voltage at the h.t. fuse (should be 60V) may be low when the fault occurs. One common cause of this is often overlooked. The large preset (red) at the rear of the power supply is the main voltage control. To the right of it there's a small preset. This is the item to replace (R631). It's in series with the main preset.

Serrated Picture

Other, smaller electrolytics on the power supply panel can become open-circuit or partially open-circuit. The 140 μ F, 75V h.t. smoothing capacitor C619 for example. This causes serrated verticals. A word of warning. Don't just slap a similar capacitor across the suspect while the set is working unless the test capacitor is already charged: switch the set off, wire the test capacitor across the suspect

and then switch on to note the effect. If the serrations are still present, move over to the line timebase panel where you may well find that the core of L502 has dropped out on to the decoder panel. If it has dropped out and can be found, refit it and seal it in. No more dropouts.

No HT

If there's a high voltage at the body of the chopper transistor but nothing at the h.t. fuse (F603) proceed as follows. First check the voltage at the right side tag of the rear upper "dropper" resistor. The reading should be 12V. If the reading is very low, check at the second tag from the right where you should find 45V. If this is also low, remember what we said about the 1,000 μ F electrolytic (C607). If however the voltage at the inner tag is approximately correct but the voltage at the right side tag is low, the dropper section concerned (R607, 100 Ω) should be running hot. If it's cold, waste no time – fit a new 100 Ω section. Nearly always however you'll find it running hot, the usual cause being an emitter-collector short in the chopper driver transistor VT605 (E1222) – under the left side with a heatsink on it. There are other possibilities, including the dynamic trip, but VT605 is the usual cause.

Attention may need to be paid to the diode in series with VT605's emitter. This can go open-circuit, as a result of which VT605 ceases to conduct – thus leaving the right side tag of the dropper at a higher than normal voltage. The voltage at this tag is therefore a key check.

The second thing to do is to ensure that the 30V line is present and correct. Check the 30V regulator transistor VT601 (front right) and its base and emitter tags which may be dry-jointed. Still at the right front, note the diode in front of the 400 μ F electrolytic – the 30V zener diode W605. There should be 30V at its cathode and 0.7V at its anode. This 0.7V is part of the start-up cycle: it switches the delay transistor VT602 (BC184LC) on. This item is another suspect that will often be found faulty.

Another essential for the chopper circuit to get going is pulses from the line oscillator. Hence the power supply cannot be checked on its own: you need the upper right side line timebase panel if a test rig is being used.

THORN 8000 SERIES

The following notes should prove helpful when servicing the 8000, 8000A, 8500 and 8800 chassis. We must start with an item found only in the 8000 and 8000A – the extreme left side "dropper", a black wirewound vertically mounted. The one in the 8000 has two main sections. The bottom consists of two 6 Ω elements to make up the 12 Ω surge limiter required at the input to the thyristor (via a BY127 diode). The upper 47 Ω section is the h.t. smoothing resistor. In the event of a "no results" condition, start at the dropper. Check for a.c. at the bottom tags. It's very common to find that one of the 6 Ω sections is open-circuit. The temptation to transfer the tag connections and use only the active 6 Ω section must be resisted. The makers intended 12 Ω and 12 Ω it should be. Well perhaps 10 Ω can be permitted, but not less. A 10 Ω , 17W wirewound resistor could be used to bridge the faulty sections or a 4.7 Ω resistor to shunt the open-circuit section only.

The upper 47 Ω section in the 8000 can give trouble, but the stress is more on the lower 6 Ω sections. We mentioned the BY127 diode in series with the BRC4443

thyristor. This diode is suspect, also its contact with the panel – this will often be found burnt away. When a BRC4444 thyristor is fitted you may find that the BY127 has been omitted.

The 8500 and 8800 chassis don't have the 12 Ω dropper section. A VA1104 thermistor is used instead as the surge limiter. This device tends to corrode and fall apart, leaving the thyristor with no a.c. supply.

One may ask why no h.t. should result in no sound? It's because in these chassis the MJE340 sound output transistor is supplied from the h.t. line, with transformer coupling to the speaker. This means that the transistor must be a high-voltage type, MJE340 or equivalent.

Whereas the power panel is fitted under the tube, in the centre, in the 8000 and 8000A, the panel is at the left side in the 8500 and 8800. This makes access much easier.

Also at the top left is the a.c. input panel which carries the fuses, l.t. rectifiers, mains filter capacitor C801 and the degaussing components. If the mains fuse F802 has failed and is blackened, suspect C801 – disconnect one end to check. In some cases its appearance leaves no doubt. If there's no a.c. supply at the fuse, check at the on/off switch and if the supply is present here move over to the rear centre red button cutout: an overload, e.g. a short-circuit line output transistor (VT401), will trip this rather than blow the fuse.

EHT but No Picture

If the symptoms are e.h.t. rustle but no picture, with normal sound, the first test to make is at the tube base – to ascertain whether the first anode supplies are present. Their absence is the usual cause of these symptoms. Check the rectifier circuit on the lower left of the right side timebase panel. The small 3.3k Ω resistor (R402) in series with the BY184 rectifier diode may present a scorched appearance and when measured prove to be open-circuit. The most frequent cause of this is that the 0.047 μ F reservoir capacitor C401, to the right, has gone short-circuit. A replacement must be rated at 1kV at least, the capacitance being of secondary importance.

Line Output Stage Hint

One last hint on these chassis. When you're faced with an inactive line output stage though the line oscillator and driver stages are working, don't immediately jump for the line output transistor. Check it by all means, but pay particular attention to the reading between the base and emitter. This should be very low both ways round due to the low value resistors and the driver transformer's secondary winding. These resistors may need to be checked.

THORN 9000 CHASSIS

The 9000 chassis was discussed in some detail in our last servicing series (see the May 1983 issue), so we'll make these notes very brief and to the point. Apart from any minor routine repairs that may be necessary, say to the switch selector unit where cleaning may be required, the more troublesome repairs centre around the power supply and the tripler.

The Syclops Circuit

There are two items to check first in the power supply. One is the centre section Syclops transistor VT701

(R2540) which lives in its heatsink house. The great thing to remember is that the base and emitter pins are not soldered but clip into the holder, the collector being secured by two screws. If the transistor hasn't gone short-circuit (this blows the mains fuse) try removing it then bending the base and emitter pins slightly to improve their contact before refitting it. Screwed to the side of the heatsink housing is the second villain, the SKE4F diode which is connected in series with VT701. It will often be found short- or possibly open-circuit. A replacement for this is the SKE5F3.10.

A general check on the diodes on the centre section usually pays dividends, particularly on the right side where one of the EW modulator diodes W711/W712 may be found decomposed. A BYX71-600 may be used as the replacement, neatly soldered under the panel, observing the polarity.

Weak Points

These models tend to develop dry-joints under the rear of the main panel, particularly in the region of the the interconnecting plugs, scan coils etc. The other weak point is the e.h.t. tripler, which is screwed to the upper metal support strut. This proximity of 25kV to a chassis member leads to all too frequent breakdown of the insulation, the consequent arcing and sparking leaving one in little doubt as to the source of the trouble.

THORN 9600 CHASSIS

This unwise siting of the tripler was rectified in the later 110° 9600 chassis. Failure of the tripler is far less common in this chassis. The weak link here is diode W810 in the EW modulator circuit. Again a BYX71-600 can be used.

THORN 9800 CHASSIS

The 9800 chassis is a very close relative of the earlier 8800 chassis: it has similar panels and a 90° delta-gun tube. There is one important difference. The 45V supply is derived from the line output transformer instead of from the mains. As a result, a start-up circuit is required. This makes a difference to the fault-finding routine.

Start by listening carefully at the moment of switching on. If the e.h.t. rustles up momentarily or a pulse of sound is heard one knows that the start-up circuit is working. If there's no noise other than the degaussing buzz, the start-up circuit should receive attention. For this purpose an external source of 24V is most useful. First check the mains input and make sure that some 200V is present at the anode of the thyristor (via diode W704 which should be carefully checked for condition, soldering etc. if necessary). Then identify socket 4 on the decoder panel and apply the external 24V supply to pin 5 (mauve lead), negative to chassis of course. If the receiver fires up and continues to work when the external supply is disconnected the start-up circuit is at fault and should be carefully checked. You may well find that R814 (470Ω) on the right side of the upper left degaussing/start-up panel is open-circuit.

Unlike the 8800, the 9800 chassis has a separate line output stage panel with a diode-split line output transformer. As with the 9000 series chassis, dry-joints in this area can be a problem. Lift the panel to gain access to the connector etc. A dry-joint on connection 851-10 is the usual cause of field collapse.

next month in

TELEVISION

● FIELD TIMEBASES SURVEYED

The start of a new series in which field timebases through the TV era will be reviewed – beginning appropriately enough with the electrostatic deflection system used at the start of TV broadcasting in 1936. The aim is to bring out the main requirements for linear field deflection and the ways in which these are met in practice. From valves the series will progress through transistors to the i.c. circuits widely used at present. A surprising variety of circuits have been used and there are many small but important points of detail to note. The authors are Stanley Amos and Eugene Trundle.

● G11 FAULT-FINDING GUIDE

Dennis Apple recently provided much useful information on the Philips G8 chassis (July issue). He's now put together an extensive fault-finding guide on the G11 chassis. The information is presented in tabular form for easy reference to symptoms and causes.

● TV LINE SELECTOR UNIT

Many lower-priced scopes have good wideband deflection systems but poor triggering facilities. This is particularly a disadvantage if you want to examine the insertion test signals transmitted during the field flyback period. This unit gives good TV triggering and can also provide X-scan and bright-up signals.

● TEST REPORT

Eugene Trundle reviews an unusual soldering iron whose very small bit can generate a great deal of heat – the dissipation capability is around 70-80W. It's versatile and easy to use once the method of heat control has been mastered.

PLUS ALL THE REGULAR FEATURES

ORDER YOUR COPY ON THE FORM BELOW:

TO (Name of Newsagent)

Please reserve/deliver the October issue of TELEVISION (£1.10), on sale September 18th, and continue every month until further notice.

NAME

ADDRESS

An Approach to Adding Teletext

Keith Cummins

I recently decided to try to interface a Tifax XM11 module and wired keypad with a Sony Model KV1820UB. The exercise was successful and the majority of this article relates to it. Consideration will also however be given to the general problems that such interfacing raises, in the hope of assisting readers first to assess the viability of a proposed modification and secondly to carry it out successfully.

In my case the Sony set with its Trinitron tube was working reliably, producing a well-converged picture – regular readers may recall the GCS/transistor line output stage modification I carried out in this set (see March 1985 issue). The set seemed to be a more suitable candidate for teletext conversion than my other one (a B and O set) for reasons that will become clearer later.

The Tifax module and wired remote control keypad were obtained from Manor Supplies. Examination of the keypad showed that in addition to the teletext controls there are four channel selector buttons and a sound muting facility. This led to a knock-on situation: in addition to incorporating teletext it seemed sensible to build in remote channel selection and sound muting. There seemed little point in having a remote control keypad some of whose controls did nothing. The result of this has been the design of a relatively simple remote channel selection facility and sound muting. This part can stand alone if required, not having to be part of the complete teletext modification.

In order to assess whether or not a proposed modification will be viable we have to carry out a feasibility study – which is a nice way of saying engage brain before grabbing the sidecutters and soldering iron. This feasibility study may involve a lot of thought before anything is done, the objects being (a) to identify the problems and (b) to see whether there are viable solutions. It could happen for example that there isn't a viable solution to a problem that has been identified: far better to think this through in the first place rather than do a lot of work on something that won't yield satisfactory results.

Tube Drive

Take for example a hybrid colour set with colour-difference tube drive (my B and O set fell into this category). The colour-difference output stages that drive the tube's grids must provide a large voltage swing, which is incompatible with a wide bandwidth. For ordinary colour reception this doesn't matter since the colour-difference signals are of reduced bandwidth anyway – the tube gets its high-definition information from the full-bandwidth luminance signal that drives the cathodes.

If we tried to use the colour-difference output stages for teletext the reduced bandwidth would result in very poor text definition, though the graphics wouldn't be too bad. Is there an answer? There's usually a solution of some sort to a problem. In this case it would involve changing over to RGB tube drive. This would mean dematrixing the colour-difference and luminance information and designing new output stages. It could be done, but what a tremendous amount of work it would involve! It just

wouldn't be worth it, particularly if the existing set was working very nicely thank you. Further, unless one is prepared to carry out careful design and testing it's possible that the end result would be a TV set that gave results inferior to those before the modification was carried out.

The Sony Trinitron tube requires RGB drive – there are separate cathode connections but only a single grid connection. As a result Sony sets look interesting from the point of view of teletext modification – because of their tube drive arrangements and good convergence, which is especially important with a text display.

Other Receiver Considerations

From the channel selection point of view the KV1820UB uses a varicap tuner, which lends itself to remote control operation. This is another point in the set's favour.

Further investigation is needed however before we can feel confident that the set is a "good bet". There are other aspects to be considered, some of which can still leave us taking calculated risks.

One such factor is the amplitude and phase response of the i.f. strip – if unsatisfactory, the result could be reduced eyeheight and the risk of data corruption. It's not easy to assess these factors by looking at a test card: a receiver whose i.f. characteristics are unsuitable for text can still produce a respectable picture.

In modern sets the performance in this area is maintained by the use of a SAW i.f. bandpass filter and synchronous demodulation. A look at the circuit diagram shows that the KV1820UB has conventional i.f. shaping filters between the i.f. preamplifier and the main i.f. strip while demodulation is carried out in IC201 (CX100D) – and the circuit doesn't tell us much about what goes on inside this device.

While it looked as if little could be done with the demodulator it was possible to hedge our bets in the selectivity circuits. One problem that affects the phase/

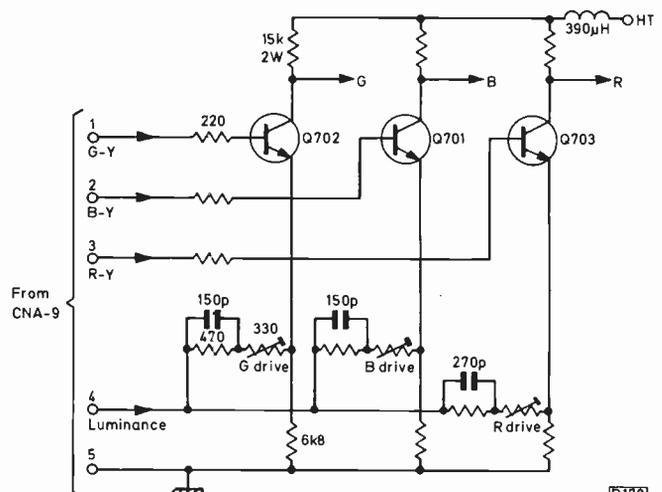


Fig. 1: RGB output stage circuits, Sony Model KV1820UB.

amplitude characteristic adversely is asymmetry in the slope of the i.f. response around the 39.5MHz vision carrier frequency. The slope is a necessary part of satisfactory vestigial sideband reception, but it often slopes away too quickly from the ideal shape because of the presence of the 41.5MHz trap which was included to prevent breakthrough of the old channel 1 sound carrier. Since 405-line transmissions have now ceased there's no need for this trap which can thus be removed. The circuit used in the KV1820UB allows the trap to be removed completely without need for further modification. All that remains in circuit is a 6.8Ω resistor.

I decided to remove this trap (T204) before doing anything else. Removing the screening plate from the bottom of the PCB is a tedious task since it's soldered down in several places. Solder wick and patience are required. Once the plate is off it's easy to unsolder the trap can and remove it. The plate must then be replaced.

The Video Signal

Having done this I decided to take a look at the video waveform just ahead of the luminance delay line. The scope, a Philips 3215, was connected to the junction of L301/R314: by manipulation of the timebase speed and with the TV sync facility in use it was possible to look at the teletext lines. Use of the $\times 10$ expansion revealed pulses of approximately the right height (70 per cent of peak white) with rounding at the top and bottom. Between there was an area of fast transitions, indicating that the teletext decoder's data slicer shouldn't have much difficulty in seeing the difference between data highs and lows. My faith in this "poor man's eyeheight" check seems to have been justified, since error-free text reception was achieved over a wide range of input signal levels when the modifications had been completed. There was no need to alter the i.f. response and none of the i.f. adjustments were touched.

The above test also suggested a suitable point for extracting a video feed to drive the Tifax module, via an emitter-follower. The latter was incorporated on the interface panel. A positive-going video signal of between 1.2-7V is required to drive the Tifax module: the nominal signal level at the point mentioned in the KV1820UB is 2.8V, positive-going. All very nice and convenient. An emitter-follower with a level-control potentiometer as its emitter load is all that's needed. Had the signal level been too small, or inverted, it would have been necessary to include an amplifier (inverting or not as required) ahead of the emitter-follower.

Up to this point the modifications to the KV1820UB had been minimal – only the 41.5MHz trap had been removed. It remained to work out what was needed (apart from the video feed) to interface the teletext decoder with the set.

Inserting the Text Signals

The next critical problem concerned substitution of the text information in place of the normal picture. Examination of the KV1820UB's circuit diagram showed that matrixing of the colour-difference and luminance signals takes place on the c.r.t. base panel, on which the RGB output stages are mounted (panel C). The luminance signal is applied via drive potentiometers to the emitters of the RGB output transistors while the colour-difference signals are applied to their bases (see Fig. 1). As the drive

potentiometers vary the gain they also affect the amplification given to the signals at the bases. An important point is that while the colour-difference signals are bandwidth limited there's no bandwidth limiting in the RGB output stages themselves, whether looked at from the emitters or bases.

As a consequence of this we can consider using the text signals to drive the bases of the RGB output transistors while connecting their emitters to a d.c. reference level in the text mode. As the output stages are on their own board, it's a simple business to break into the interboard connections (connector CNA-9) to introduce the teletext interfacing. This arrangement was found to work well in practice.

Interfacing

Now to the details of the interfacing. The Tifax module's outputs are at TTL level (5V) and have to be translated to any other level that may be needed – the d.c. level on the colour-difference drive lines in the KV1820UB is typically 7V. There are also TTL monochrome and blanking signals that need level shifting. Furthermore it's a good idea to buffer the Tifax module to reduce the chances of damage due to calamities elsewhere – including such horrors as flashovers.

The requirements of the interfacing unit thus become clearer. We have to buffer the digital signals; switch between digital and analogue (ordinary picture) video; and feed the selected signals as drives to the RGB output stages.

Simple switches or maybe even relays could be used to switch between the digital and analogue signals were it not for the fact that the switching has to be controlled by the blanking signal, which comes from the Tifax module. One of the facilities provided by the module is boxed display of subtitles or newflashes. For this purpose it's necessary to cut a hole or holes in the picture and insert the text. This involves blanking on a line-by-line basis, which calls for fast electronic switching. Relays and suchlike are out: solid-state analogue gates are in! Now analogue gates are not very tolerant of voltage transients, so to be careful when taking their outputs to the c.r.t. drive circuits it's advisable to include emitter-follower buffer stages to protect against the transients that occur with tube flashovers.

In the particular case under consideration it's also necessary in the text mode to switch out the luminance signal and substitute for it a d.c. voltage. Variation of this d.c. voltage provides control over the text background level.

Tifax Module Connections

Before describing the interface board in detail we should first consider the Tifax module's needs.

The Tifax module has pins marked 1 to 22 (see Table 1). There is no connection to pin 9 while pins 11 and 14 are intended for polarising key positioning. Pins 1 to 8 connect to the keypad. When the equipment is first switched on, pins 3 and 8 have to be linked temporarily to "initialise" the decoder in the picture mode.

There are two 0V connections and two 5V supplies are required, one for the digital circuits and the other, with extra smoothing, for the analogue signal processing. There are five outputs, RGB, monochrome and blanking, and inputs for the video and for a line pulse.

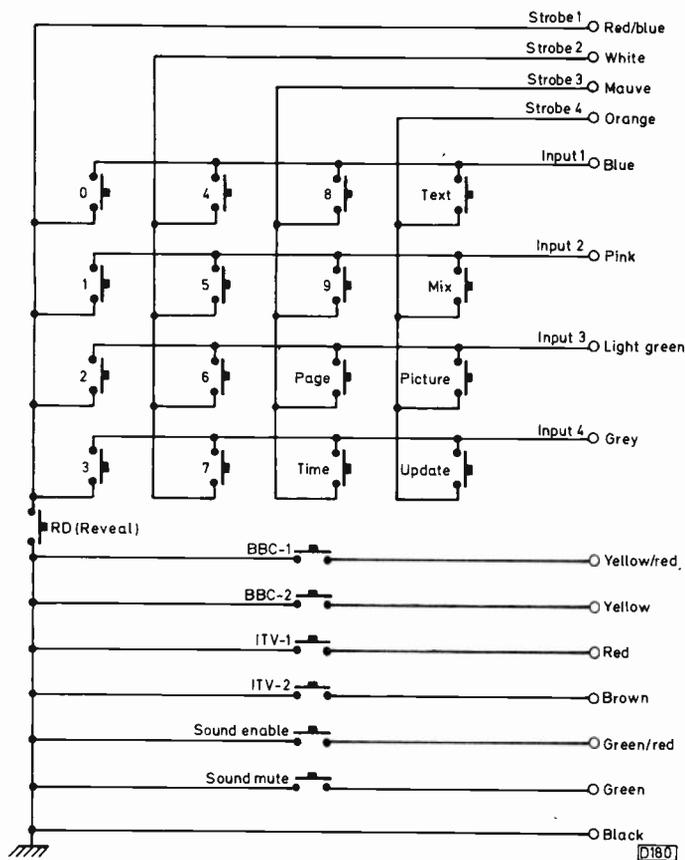


Fig. 2: Circuit of the keypad.

It's possible for the Tifax module to consume nearly 1A at 5V. Since it's not easy to provide such a supply in a TV set unless this is done at the initial design stage a separate power supply forms part of the interfacing exercise. The same unit provides the 12V supply required by the analogue and some digital parts of the interface board and by the separate channel selector board.

The keypad operates by either cross-connecting the control lines from the Tifax module in a 4 x 4 matrix or by pulling lines down to 0V (for audio control and channel selection) - see Fig. 2.

The interface board has four i.c.s, six transistors and 26 connections. These are listed in Table 2.

Interfacing Circuit

The circuit of the interface board is shown in Fig. 3. We'll start by considering the situation during normal picture reception, when the board is "transparent" to the TV set's signals and the set behaves as though nothing had been done to it.

The three colour-difference signals come on to the board at connections 1, 2 and 3 and pass via the 4053 triple changeover analogue switch chip IC2 to the three emitter-followers Tr2, Tr3 and Tr4. They leave the board at connections 12, 13 and 14, going to the bases of the RGB output transistors. The d.c. level is maintained, except for an approximately 0.6V offset introduced by the base-emitter voltage difference of the three emitter-follower transistors. The signals pass through the three analogue switches because the switching bus line is high. This switching bus is the key to the changeover process and we'll give more details when we come to the text mode.

The luminance signal comes on to the board at connection 9 and passes via one section of a second 4053 (IC3) to emitter-follower Tr5. This is a pnp device since it needs to be "on its head" to supply the emitters of the RGB output transistors. Diode D4 is included to provide flashover protection. Note that the combination Tr5/D4 performs the same function as Q305/D303 in the KV1820UB.

So when the switching bus is high the interface is transparent to picture video and in effect we've done nothing - the TV picture appears as normal.

When we come to viewing text we first need to know the normal conditions of the Tifax module's outputs. The three RGB and the monochrome outputs are all open-collectors which pull active low, i.e. they are high until something happens. The blanking output is normally low and goes high when blanking is required.

You'll see that the outputs from the Tifax module are returned to the 5V line via resistors R1-5. The outputs are also connected to five of the inputs of the 7416 TTL hex inverter buffer chip IC1. This chip has open-collector outputs that can withstand 15V, though the chip is operated from a 5V supply.

When the user presses "text" on the handset the blanking input at connection 8 goes high and pin 12 of IC1 goes low. This is the switching bus line, which is otherwise held at 12V via R11. When the switching bus line goes low the states of the four analogue switches in IC2 change over. As a result Tr2/3/4 are linked to pins 2/4/6 of IC1 instead of to input connections 1/2/3. As the outputs from IC1 try to rise to 12V they are caught by diodes D1/2/3 whose cathodes are taken to the pnp emitter-follower Tr1. This transistor's base voltage is set by VR2, which can be varied to determine how far the outputs from IC1 are allowed to move in the positive direction. By this means the amplitude of the text signal drive to the RGB output stages is adjusted, i.e. VR2 sets the text signal brightness. It's a preset control since there's no need to adjust the text display once it has been set up satisfactorily.

In the text mode the luminance signal is disconnected by its analogue switch (in IC3). In its place a d.c. level set by VR1 is introduced. This is the text background control which sets the pedestal level on which the text signal sits in the video stages. For initial setting up test points 1 and 2 are linked, forcing the switching bus low. With no text present VR1 can be set for a true black background in readiness for the text when it appears.

The switching process, including the creation of subtitle boxes as mentioned earlier, is under the control of the blanking signal. The Tifax decoder also has a "mix" mode in which text is superimposed upon the picture. In this mode the monochrome signal, after passing through two inverting buffer stages to get its polarity right, cuts character shaped holes in the main picture. Because the Tifax module's RGB outputs all go low together in this mode the result is an inlay of monochrome text and graphics. Personally I don't like this mode very much, preferring the picture or text on its own.

Note that this interface arrangement allows the set's picture controls to work normally in the picture mode: they have no control over the text display, which is preset as described above.

Rest of the Circuitry

Now to the other circuitry on the interface board. The Tifax module needs a carefully smoothed 5V supply for its analogue circuits. This is provided by the decoupling

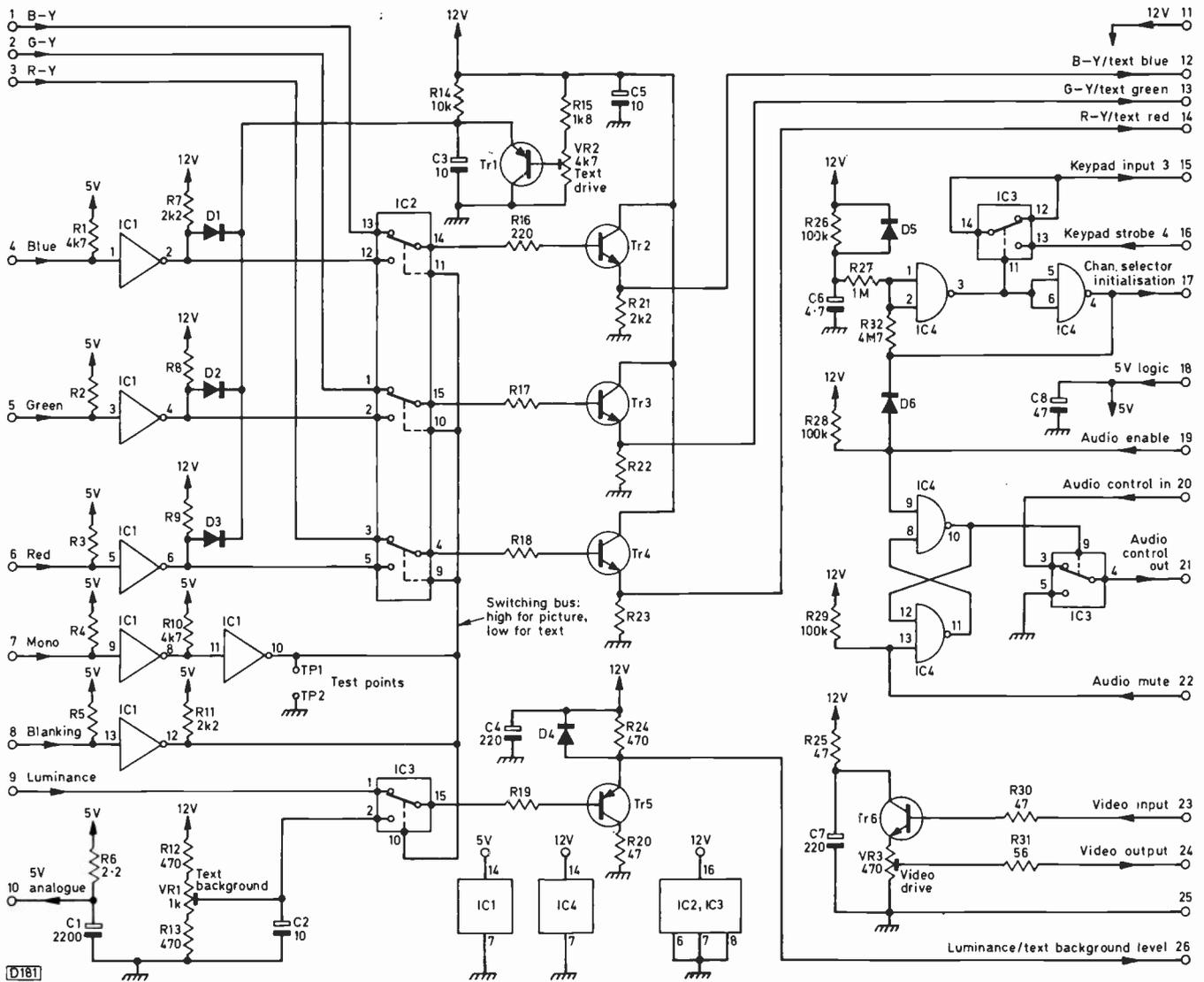


Fig. 3: Interface board circuit.

network R6, C1 which is fed from the logic 5V supply.

Buffering and level adjustment of the video drive to the Tifax module are provided by the emitter-follower Tr6. The video input comes from board A in the receiver as described earlier – see Fig. 4. The transistor's base is biased positively by the standing voltage of around 4V. R25 and C7 filter the supply to this transistor. Screened lead is used to link the video to and from the interface board.

A latch circuit using two sections of a 4011 quad dual NAND gate i.c. to control an analogue switch is used for audio muting. This switch can handle a.f. or d.c. audio level control. The KV1820UB uses a d.c. volume control which sets the voltage at pin 13 of the CX095C intercarrier sound chip IC203. The analogue switch passes either the d.c. voltage corresponding to the required volume, i.e. the voltage from the volume control, or 0V which corresponds with zero volume. Lines from the keypad set the latch one way or the other to give audio enable or mute. In common with all latch circuits of this type the circuit could settle in either of its two states at switch on. To overcome this difficulty an initialisation circuit is used to set it in the enable condition when the set is switched on.

As mentioned earlier, the Tifax module also needs initialising at switch on. This is done by momentarily linking keypad input 3 to keypad strobe 4 to ensure that

the TV set starts off in the picture mode – otherwise there's a possibility that it would start off in the mix mode. The last remaining analogue switch is used to carry out this procedure. It's controlled by a Schmitt trigger circuit that uses the two remaining parts of the 4011 chip as inverters. At switch on C6 is discharged; it then charges to 12V via R26. While it's charging, pin 3 of IC4 is high, closing the analogue switch to initialise the Tifax module. Pin 4 of the i.c. is low, taking pin 9 low via D6 to set the audio mute latch in the audio enabled position. The output from pin 4 also leaves the panel at connection 17, passing to the channel selector board which will be described later. When C6 has charged to the level at which the gate connected to R27 and R32 starts to invert, the circuit rapidly switches to its opposite state because of the positive feedback via R32. Initialisation of the Tifax module and the audio mute circuit is thus achieved and these circuits are ready to accept commands from the keypad. At switch off C6 discharges via D5 into the collapsing 12V line.

C4 decouples the 12V line and C8 the 5V line.

Channel Selector Circuit

The circuit of the remote channel selection board is shown in Fig. 5. Its main components are a quad latch

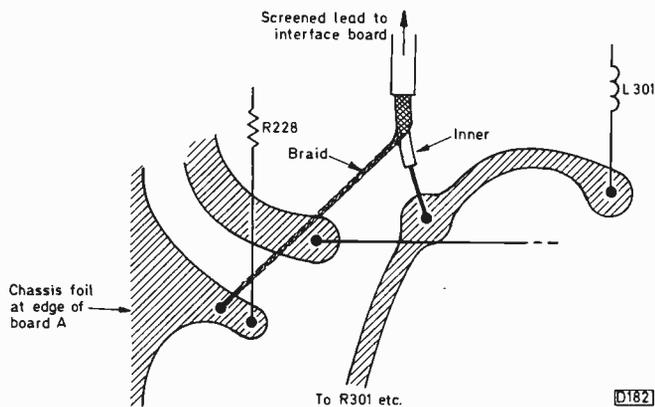


Fig. 4: Method of tapping the video from board A in the Sony Model KV1820UB.

(IC2), a four-input dual NAND gate (IC1) and four relays with their drivers. The function of the channel selector is to remember which channel selection button on the keypad has been pressed. This is achieved as follows.

The four channel selection lines from the keypad are taken to data inputs D1-4 of the 4042 quad latch IC2. These lines will be at 12V, via R3-6, until one is taken to 0V by pressing one of the channel selector buttons. The four lines are also connected to the four inputs of one of the NAND gates. When a button is pressed, the appropriate data line goes low. Let's say that the BBC-1 button has been pressed. Thus pin 4 of IC2 goes low and because one of its inputs has gone low pin 13 of IC1 goes high. This latter excursion is differentiated by C3 and R8 and used to clock IC2 via R7. When the button is released, the D1 latch has clocked in a low while the other three latches have clocked in highs. The outputs (inverted-Q) at pins 3/9/12/15 are applied to the bases of the relay driver transistors Tr1-4. These outputs go high when the clocked-in data is low. Thus having pressed the BBC-1 button we ensure that the output at pin 3 is high. Tr4 then switches

on, closing RL4. If another button is pressed the pattern of clocking three highs and a low into IC2 is changed. The appropriate output pin goes high and the associated relay operates.

Initialisation is used to ensure that the same channel, BBC-1, is selected at switch on. When the system has been powered and can accept a clock pulse the back edge of the initialisation pulse from the interface board is coupled to the other half of IC1, which is used as a simple inverter, via the differentiating network C2, R2 and R1. This positive-going edge produces a momentary low at pin 1, forcing a low on to the BBC-1 select line via D1. Thus the set always comes on tuned to BBC-1.

The four relays used are of the reed type – those in the prototype had a resistance of 1k Ω . Quenching diodes D2-D5 are fitted to limit the back-e.m.f. when the driver transistors switch off.

One side of the relay contacts is taken to the local/remote switch SW1 which enables either the keypad or the original channel selector buttons to be used. The other sides of the relay contacts go direct to the sliders of the tuning potentiometers on their PCB. The system could be extended to control more channels by using say two 4042 chips and a common clock generator with an eight-input NAND gate (4068). Another gate or maybe a transistor could be used for initialisation.

The Power Supply

The last bit of circuitry is the power supply, which is shown in Fig. 6. This is very simple, using a transformer with a 9.0-9V secondary winding rated at 1A. Its primary winding is connected to the switched 240V supply from the set's on/off switch. One half of the secondary winding feeds a bridge rectifier whose reservoir capacitor is C2. This is followed by a 78H05 5V regulator, a chunky device with very low ripple on its output – a prime requirement with the Tifax module. It's very much underrun in this application and should therefore prove very reliable. The

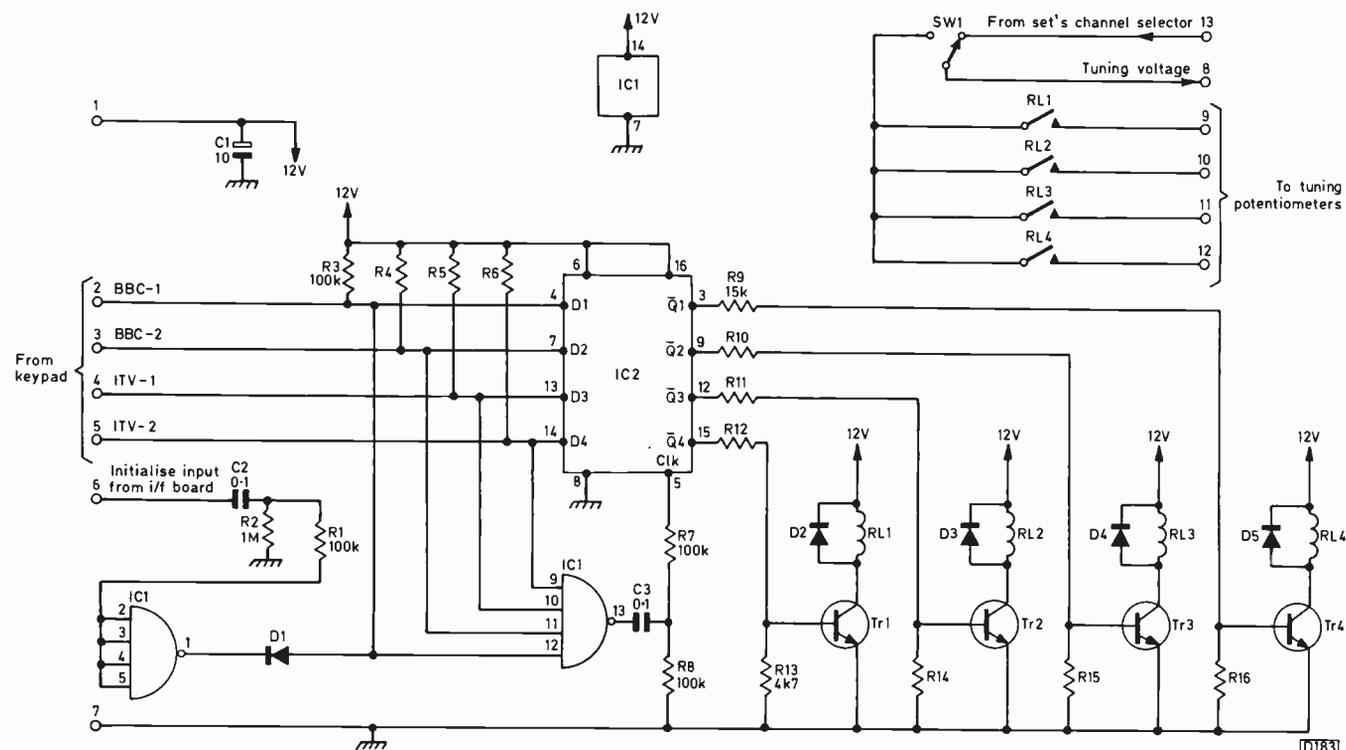


Fig. 5: Remote channel selector circuit.

Table 1: Tifax module connections

Pin	Connected to	Coded
1	Keypad input 1	Blue
2	Keypad input 4	Grey
3	Keypad input 3 and pin 15, interface board	Light green
4	Keypad input 2	Pink
5	Keypad strobe 1	Red/blue
6	Keypad strobe 2	White
7	Keypad strobe 3	Mauve
8	Keypad strobe 4 and pin 16, interface board	Orange
9	No connection	
10	Pin 10, interface board (analogue 5V)	Blue
11	Polarising key connection – not used	
12	Chassis	Black
13	Chassis	Black
14	As 11	
15	Line pulse from TV set	Screened
16	Pin 24, interface board (video input)	Screened
17	Pin 4, interface board (blue output)	Blue
18	Pin 5, interface board (green output)	Green
19	Pin 6, interface board (red output)	Red
20	Pin 7, interface board (mono output)	White
21	Pin 8, interface board (blanking output)	Brown
22	Pin 4 power supply/pin 18 interface board (logic 5V)	Red

Tifax module is intolerant of excessive voltage and could end up as a write-off in the event of regulator failure. Note that the 78H05 is in a TO3 can.

Some readers may not have come across the crafty use of the other half of the secondary winding with a half-

Table 2: Interface board connections.

Pin	Connected to	Coded
1	CNA-9 pin 2, KV1820UB	—
2	CNA-9 pin 1, KV1820UB	Plain White
3	CNA-9 pin 3, KV1820UB	—
4	Pin 17, Tifax module	Blue
5	Pin 18, Tifax module	Green
6	Pin 19, Tifax module	Red
7	Pin 20, Tifax module	White
8	Pin 21, Tifax module	Brown
9	CNA-9 pin 4, KV1820UB	—
10	Pin 10, Tifax module	Blue
11	Pin 3, power supply	Orange
12	Pin 2, KV1820UB board C	Blue
13	Pin 1, KV1820UB board C	Green
14	Pin 3, KV1820UB board C	Red
15	Pin 3, Tifax module	Light green
16	Pin 8, Tifax module	Orange
17	Pin 6, ch. select board	Pink
18	Pin 22, Tifax module/pin 4 power supply (logic 5V)	Red
19	Keypad	Green/red
20	Slider of TV set's volume control	
21	CNA-1 pin 2, KV1820UB	
22	Keypad	Green
23	Junction L301/R301 on board A, KV1820UB	Screened
24	Pin 16, Tifax module	Screened
25	Chassis	Black
26	Pin 4, KV1820UB board C	White

Note: Some of the colour codes are suggestions only.

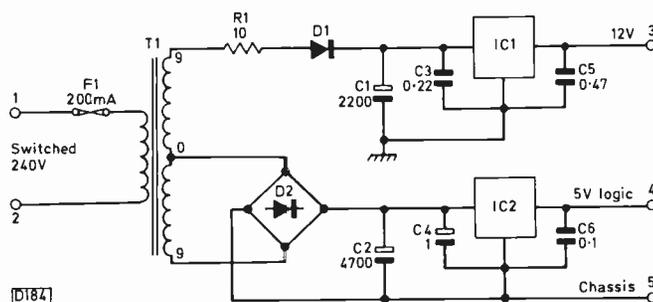


Fig. 6: Circuit of the power supply for the Tifax decoder and the interface and remote channel selector panels.

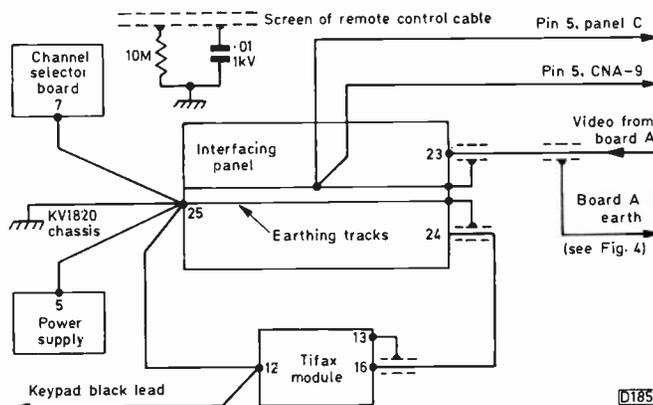


Fig. 7: Recommended earthing arrangements.

wave rectifier (D1) as a means of getting 12V. If you think about what happens in a bridge rectifier you will note that one of the diodes completes the path to chassis while the top end of the secondary is at 18V r.m.s. above 0V. This enables the half-wave rectifier to work: because of the low load on the 12V supply, half-wave rectification is acceptable. In this case C1 is the reservoir capacitor which is followed by a 7812 regulator. A word of warning if you're not familiar with these regulators: don't be tempted to leave out any of the decouplers C3/4/5/6 – the devices can "hoot" and put noise on the lines. In extreme cases they can damage themselves and fail.

Construction

The power supply can be built on a small chassis which doubles up as a heatsink for the bridge rectifier and the regulators, then fitted in the vacant area behind the loudspeaker.

The earthing arrangements are important – see Fig. 7. Component layout is not critical, though common sense should prevail. The basic sketches (Fig. 8) show the positions of the main components. I used Veroboard but haven't given all the track cuts and component locations: constructors may well have their own ideas and different TV sets will need different shaped boards. My opinion is that if you need a detailed board layout you're not ready for this kind of exercise! Component lists are provided.

The Big Question

Could you fit teletext to your TV set? The foregoing remarks and technical details should help you to make up your mind. Knowledge of the pitfalls helps enormously if success is to be achieved. There is always an element of risk, and we have to live with this. If you don't want the teletext bit you can still use the remote channel selector

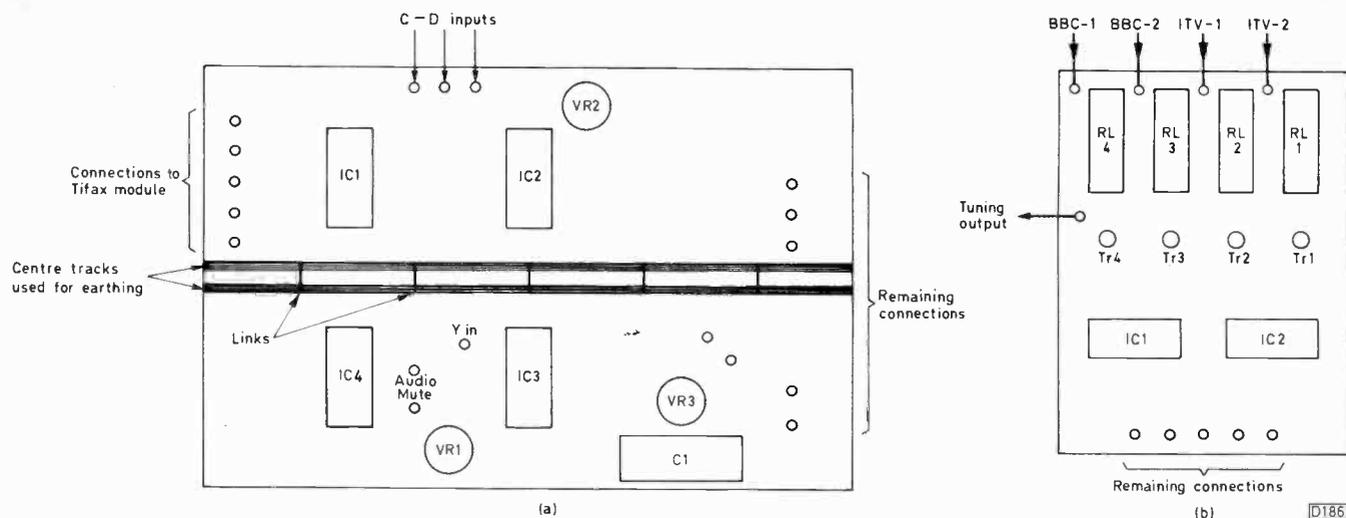


Fig. 8: Basic board layouts: (a) interface panel; (b) remote channel selector panel.

section on its own (provided you lay on local initialisation). Even the sound mute bit could come in useful somewhere.

Hopefully I've provided some ideas which you will find useful about interfacing. As I said at the beginning, the smart thing is to identify the problems carefully in the first place, to ensure that you don't come across a difficulty that makes it pointless to go any further with the exercise.

Testing

It's a good idea to test the separate assemblies on the bench before incorporating them in the TV set, applying

voltages to the inputs and seeing for example that the outputs follow. Likewise test the power supply on dummy load before installing it. Make sure that all the other parts work properly in the set before fitting the Tifax module. Remember that without the Tifax module fitted you'll have to pull the blanking input low to get the switching bus to go high and select pictures. Also, because of the d.c. offsets introduced by the interfacing circuitry, you may have to adjust the first anode voltages - VR705 in the KV1820UB. By tackling the job in this way I found that I had only one change to make after everything had been connected up - that was to change the values of R7-9 on the interface board from the original 4.7kΩ to 2.2kΩ to

Components list

Interface board

Resistors:

R1-R5	4.7k
R6	2.2, 1/2W
R7-R9	2.2k
R10	4.7k
R11	2.2k
R12, R13	470
R14	10k
R15	1.8k
R16-R19	220
R20	47
R21-R23	2.2k
R24	470
R25	47
R26	100k
R27	1M
R28, R29	100k
R30	47
R31	56
R32	4.7M
0.3W 10% unless otherwise indicated	

Presets

VR1	1k
VR2	4.7k
VR3	470

Capacitors

C1	2200, 10V
C2, C3	10, 16V
C4	220, 16V
C5	10, 16V
C6	4.7, 16V tant
C7	220, 16V
C8	47, 10V

Semiconductor devices:

IC1	7416
IC2, IC3	4053
IC4	4011
D1-D6	1N4148
Tr1, Tr5	BC212L
Tr3-4, Tr6	BC109B

Sundries:

IC carriers, Veroboard, link wire, terminal pins

Channel selector board

Resistors:

R1	100k
R2	1M
R3-R8	100k
R9-R12	15k
R13-R16	4.7k
All 0.3W 10%	

Capacitors:

C1	10, 16V
C2, C3	0.1, 30V ceramic

Semiconductor devices:

IC1	4012
IC2	4042
D1-D5	1N4148
Tr1-Tr4	BC109B

Hardware:

SW1	SP change-over
RL1-RL4	12V, 1k reed relays with single-make contacts
Veroboard, i.c. carriers, etc.	

Power supply

Semiconductor devices:

IC1	7812
IC2	78H05
D1	1N4002
D2	2A bridge, 100V p.i.v.

Resistor:

R1	10, 0.3W, 10%
----	---------------

Hardware:

F1	200mA, 20mm, slow fuse with carrier
T1	Pri. 240V a.c.; sec. 9.0-9V, 1A
Aluminium chassis/heatsink wire, etc.	

ensure a fast enough pull-up (the character verticals were a bit weak).

Care and planning cannot be stressed enough – imagine how you'd feel if the Teletext decoder blew up because of a power supply fault or a wrong connection!

Remember too that because of the use of a mains bridge rectifier in the KV1820UB the chassis is always live. So the use of a mains isolating transformer when testing is essential.

Teletext Operation

Finally, here are some "driving instructions" for the teletext facility.

(1) With the TV set running normally, select the channel appropriate to the service required, i.e. BBC-1 for Ceefax pages from 100, BBC-2 for Ceefax pages from 200, ITV for Oracle pages from 100 and Ch. 4 for Oracle pages from 400.

(2) Press the text button. The picture will disappear and a few random characters will appear on the screen.

(3) Press the page button, followed by the page number. To get the index pages, call up 100 on BBC-1, 200 on BBC-2 and 100 on either ITV or Ch. 4.

(4) Wait for the page to appear. When you want another page, press page again and enter the new number via the keypad. The page number called up appears at the top left-hand corner of the screen. When the required page is found the rolling numbers at the top centre of the screen stop, frozen at the number called up.

(5) To hold a page, press page but do not enter a new number. To continue a series of pages, re-enter the page number (the one at the top of the screen).

(6) The real-time clock at the top right of the screen gives an idea of the signal integrity. If it jumps and changes data, the signal is suspect. A good test of the system is the clockcracker page 391 on Oracle, 197 on Ceefax.

(7) Alarm clock. Ceefax provides an alarm clock facility on page 196. The time is entered using the 24-hour clock, by pressing the time button after first selecting the page.

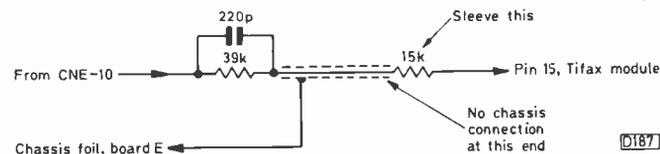


Fig. 9: Providing the line pulse required by the Tifax decoder.



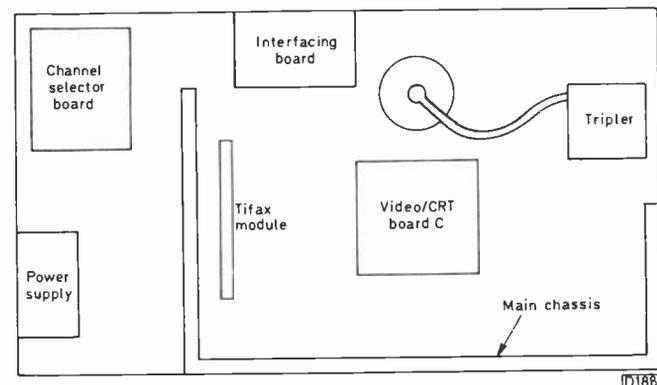
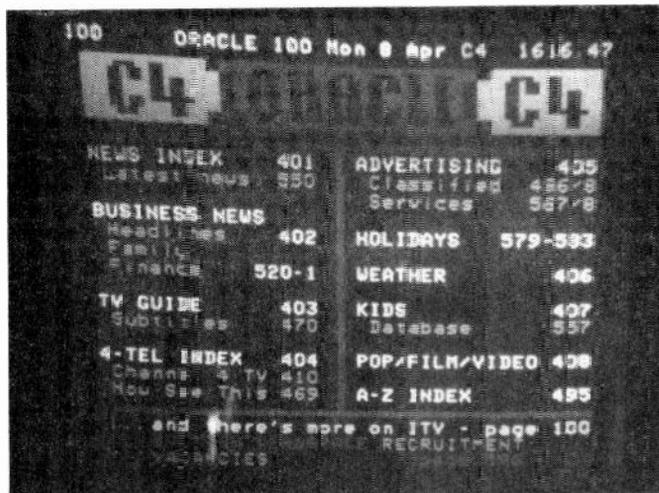


Fig. 10: Positions of the extra panels and the Tifax module in the Sony Model KV1820UB.

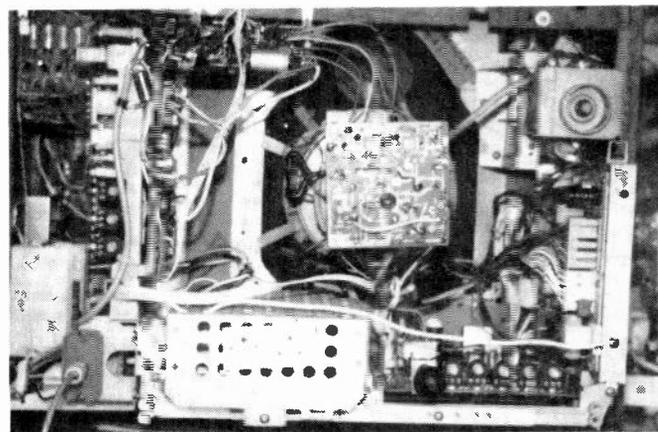

Teletext on the Sony KV1820UB.

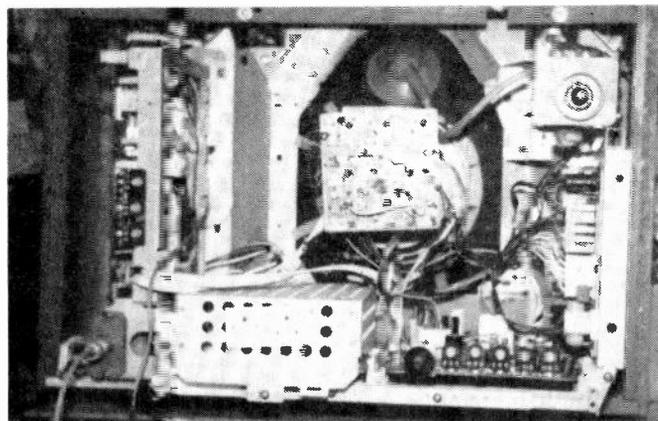

The Sony KV1820UB before (top) and after (bottom) adding teletext and remote channel selection/sound muting.

Instructions are given on the alarm clock page.

(8) A page can be called up at a particular time, e.g. the stock market figures which are constantly changing. First enter the page, then press time and enter the time via the keypad. Get back to the picture by pressing update. Upon returning at the specified time – by pressing text – the updated page will be found.

(9) Switching between text and picture is done by pressing the appropriately marked buttons.

(10) The reveal facility is labelled RD (reveal data?) on the keypad. This is used under instruction from the screen to give answers to puzzles, riddles, etc. – mainly on the fun pages.

(11) Missing characters or a garbage display of nonsense is generally caused by noisy or ghostly signals.

ECONOMIC DEVICES, PO BOX 228, TELFORD TF2 8QP

16181	1.04	2SC1124	1.26	2SD348	16.13	AN5435	3.08	BC186	0.27	BD222	0.49	BF195	0.14	BSR59	1.29	BZK79 RANGE	0.10
16182	1.04	2SC1151A	4.72	2SD350	5.20	AN5610	7.43	BC187	0.20	BD225	0.49	BF196	0.17	BSS38	0.59	BZY88 RANGE	0.10
16334	0.51	2SC1152	4.68	2SD350A	2.29	AN5612	3.51	BC204	0.16	BD228	0.63	BF197	0.17	BSTBD1409	2.73	C106D	0.46
16335	0.80	2SC1162	1.05	2SD353	7.50	AN5613	4.1	BC207	0.11	BD229	1.05	BF198	0.17	BSTC0146	2.48	C1129	0.50
16446	0.98	2SC1172	2.22	2SD389	2.41	AN6320N	4.28	BC212	0.14	BD231	0.50	BF199	0.17	BSTC0246	6.99	CA1310E	2.78
16600	1.38	2SC1191	2.20	2SD401	3.55	AN6326	3.98	BC212B	0.26	BD232	0.50	BF200	0.17	BSTC0233	6.12	CA3044	3.50
16799	2.88	2SC1195	3.26	2SD451	2.42	AN6342	1.61	BC212L	0.10	BD234	0.42	BF216	0.36	BSTC1233	4.34	CA3046	2.06
16801	1.54	2SC1213	0.89	2SD588A	1.99	AN6344	5.87	BC212LB	0.26	BD237	0.47	BF218	0.36	BSTC1463	6.09	CA3060	1.65
16802	1.14	2SC1226	1.86	2SD600	3.25	AN6363	16.00	BC213	0.10	BD238	0.45	BF222	0.56	BSTCC0143	3.79	CA3065	1.29
16803	5.30	2SC1306	1.98	2SD621	12.67	AN6551	0.68	BC213L	0.10	BD239	0.45	BF224	0.17	BSTCC0643	3.47	CA3089	0.83
16905	0.86	2SC1307	1.98	2SD636	0.40	AN6552	0.68	BC213LB	0.15	BD240	0.37	BF237	0.65	BSV57B	3.39	CA3089E	1.43
17074	6.60	2SC1316	4.10	2SD657	2.80	AN7115	2.52	BC214	0.10	BD241	0.39	BF240	0.17	BSW68	0.60	CA3090	1.38
17127	3.51	2SC1364	0.49	2SD679	3.35	AN7145	2.80	BC214L	0.14	BD242	0.50	BF241	0.17	BSX19	0.34	CA3094	2.20
1N4001	0.06	2SC1383	1.20	2SD731	2.11	AN7146	9.90	BC214LB	0.26	BD243	0.50	BF244	0.47	BSX20	0.34	CA3131EM	3.12
1N4002	0.06	2SC1398	0.84	2SD787E	0.62	AN7150	2.45	BC225	0.40	BD243A	0.37	BF245A	0.37	BSX21	0.87	CAH76023N	6.60
1N4003	0.06	2SC1410	2.39	2SD811	5.54	AN7151	2.26	BC237	0.10	BD244	0.51	BF256	0.20	BSY52	0.50	CBF16848N-07	1.56
1N4004	0.04	2SC1413	3.55	2SD823	1.98	AN7156	2.40	BC238	0.10	BD244A	0.85	BF256	0.28	BSY79	0.51	CD4001	0.38
1N4005	0.08	2SC1505	1.00	2SD856	6.61	AN7158	6.75	BC238A	0.13	BD245C	0.99	BF256LC	0.42	BT100A	1.61	CD4002	0.27
1N4006	0.08	2SC1578	8.74	2SD869	7.17	AN7218	1.64	BC239	0.12	BD246C	0.86	BF257	0.34	BT106	1.18	CD4008	1.06
1N4007	0.07	2SC1617	3.89	2SD898B	7.45	AP58076	4.68	BC239B	0.12	BD253	1.05	BF258	0.33	BT108	1.45	CD4011	0.29
1N4148	0.04	2SC1670	3.13	40408	0.50	AS5605	1.58	BC251A	0.25	BD278A	0.70	BF259	0.34	BT109	1.45	CD4012	0.24
1N4448	0.05	2SC1678	1.98	40594	1.53	AU113	2.97	BC252	0.10	BD317	2.60	BF262	0.57	BT112	2.48	CD4013	0.47
1N5401	0.14	2SC1810	1.70	40595	1.53	AY105K	2.08	BC258	0.25	BD318	2.59	BF263	0.57	BT113	2.48	CD4016	0.45
1N5402	0.15	2SC1815	0.66	40636	1.43	AY106	1.09	BC261A	0.22	BD375	0.42	BF264	0.37	BT116	1.20	CD4017	0.82
1N5403	0.16	2SC1829	2.22	40871	1.53	BA130	0.14	BC262	0.22	BD377	0.26	BF271	0.34	BT119	1.76	CD4020	1.23
1N5404	0.15	2SC1855	1.88	40872	1.53	BA1310	1.98	BC287	0.50	BD379	0.76	BF273	0.20	BT120	2.17	CD4021	0.39
1N5408	0.35	2SC1875	4.77	60857	1.21	BA1320	1.38	BC294	0.50	BD380	0.76	BF274	0.20	BT121	2.48	CD4023	0.28
1N914	0.04	2SC1891	3.69	7ALS30	0.32	BA1330	2.75	BC301	0.45	BD410	0.49	BF324	0.23	BT122	2.48	CD4025	0.64
IS44	0.09	2SC1893	3.02	7805 TD-220	0.63	BA145	0.19	BC302	0.53	BD412	6.27	BF336	0.33	BT123	1.98	CD4028	0.84
IS5012A	0.81	2SC1929	2.25	7805 TD-3	1.16	BA148 DIDD	0.33	BC303	1.04	BD418	0.84	BF337	0.36	BT125	2.48	CD4047	1.06
IS921	0.10	2SC1942	5.70	7806	0.73	BA154	0.40	BC307	0.18	BD433	0.41	BF338	0.40	BT126	2.48	CD4049	0.58
2N1302	0.27	2SC1945	4.53	7808	2.39	BA156	0.05	BC307A	0.18	BD434	0.43	BF355	0.69	BT128	2.48	CD4050	0.55
2N1303	0.38	2SC1953	1.93	7812 TD-3	0.64	BA157	0.22	BC308	0.14	BD435	0.49	BF362	0.60	BT128P	3.07	CD4052	0.75
2N2218	0.42	2SC1957	0.95	7812 TO-220	1.16	BA159	0.12	BC308A	0.11	BD436	0.60	BF363	0.60	TBA970	3.06	CD4053	0.80
2N2219A	0.40	2SC1959	0.31	7815	0.64	BA182	0.19	BC309	0.17	BD437	0.41	BF371	0.50	BT151-800R	1.15	CD4059	0.24
2N2222	0.38	2SC1962	1.93	7818	0.70	BA222	1.66	BC317A	0.13	BD438	0.49	BF391	0.50	BT151 500R	1.38	CD4081	0.35
2N2646	0.80	2SC1969	2.92	7824	0.64	BA284/2	0.17	BC327	0.15	BD441	1.42	BF393	1.25	BT16018	2.42	CD4093	0.72
2N2904	0.36	2SC1985	1.75	AC107	0.73	BA301	0.87	BC328	0.11	BD442	0.66	BF417	0.84	BT16218	2.42	CD4511	1.10
2N2905	0.43	2SC1983 TR	7.00	AC117	0.43	BA302	1.24	BC337	0.08	BD507	0.60	BF418	1.87	BT18024	4.43	CP5521	17.83
2N2906	0.38	2SC2009	0.34	AC123K	0.43	BA311	1.32	BC338	0.12	BD509	1.42	BF422	0.29	BT18124	4.89	CV12E	3.07
2N3053	0.27	2SC2029	2.33	AC128	0.34	BA312	0.97	BC360	0.34	BD510	0.75	BF423	0.29	BT18214	5.99	CX034	11.83
2N3054	0.99	2SC2027	1.42	AC138	0.09	BA313	0.76	BC368	0.12	BD518	1.50	BF435	0.54	BT18224	2.97	CX085D	3.14
2N3055	0.61	2SC2028	2.11	AC141	0.29	BA317	0.04	BC440	1.09	BD519	1.50	BF450	0.35	BU105	1.50	CX104	9.64
2N3055H	0.85	2SC2057	1.18	AC142K	0.43	BA318	0.09	BC441	0.42	BD529	1.32	BF451	0.29	BU106	2.48	CX108	8.16
2N3442	1.16	2SC2073	1.54	AC151	0.28	BA328	4.77	BC454	0.36	BD530	1.10	BF457	0.41	BU108	1.50	CX109	7.86
2N3702	0.14	2SC2078	2.39	AC153	0.34	BA333	1.37	BC455	0.36	BD533	0.67	BF458	0.39	BU109	2.25	CX121	11.83
2N3703	0.14	2SC2091	1.30	AC176	0.30	BA401	0.64	BC460	0.42	BD534	0.53	BF459	0.52	BU110	5.69	CX130	5.55
2N3704	0.14	2SC2122A	5.12	AC179	0.28	BA511	2.18	BC461	0.47	BD535	0.77	BF460	0.39	BU111Y	1.46	CX131	11.83
2N3705	0.14	2SC2141	1.86	AC183	0.72	BA521	2.02	BC462	0.30	BD536	0.61	BF469	0.31	BU1124	1.38	CX134	11.04
2N3706	0.14	2SC2166	1.98	AC187	0.39	BA524	8.21	BC463	0.64	BD537	0.74	BF470	0.55	BU126	0.90	CX136	11.49
2N3707	0.16	2SC2216	0.69	AC187K	0.43	BA526	7.98	BC464	0.64	BD538	0.67	BF471	0.31	BU134S	4.57	CX137	11.83
2N3711	0.11	2SC2233	2.20	AC188	0.37	BA532	1.91	BC465	0.62	BD544B	0.83	BF472	0.33	BU204	1.58	CX139	11.83
2N3771	2.04	2SC2271	4.01	AC188-01	0.44	BA536	3.44	BC477	0.34	BD580	1.17	BF479	0.61	BU205	1.08	CX157	4.84
2N3772	1.71	2SC2278	1.17	AC188K	0.43	BA6304A	2.92	BC478	0.32	BD590	1.17	BF480	0.60	BU206	1.27	CX158	4.10
2N3773	2.29	2SC2314	0.84	AC193K	0.65	BA843	3.96	BC479	0.41	BD598	1.25	BF491	0.49	BU207	1.65	CX170	7.62
2N3819	0.40	2SC2335	10.41	AC194K	0.65	BAV18	0.65	BC532	0.28	BD677	0.53	BF496	0.64	BU208	1.12	CX177	6.75
2N3823	1.17	2SC2526	1.87	AD140	1.06	BAV19	0.21	BC546	0.17	BD679	0.57	BF505	0.43	BU208/02	1.97	CX506	9.33
2N3904	0.62	2SC2551	1.26	AD145	1.60	BAV20	0.11	BC547	0.10	BD680	0.76	BF509	0.40	BU208A	1.12	CX507	7.62
2N3908	0.62	2SC2570	2.39	AD149	0.90	BAV21	0.34	BC548	0.10	BD681	1.48	BF523	0.21	BU208D	1.43	CX755	12.95
2N4101	1.33	2SC2570A	1.05	AD161	0.56	BAX12	0.11	BC549	0.10	BD695	2.30	BF594	0.27	BU209	1.93	CX758	7.62
2N4240	3.30	2SC2578	6.75	AD162	0.45	BAX13	0.11	BC550	0.40	BD696	2.47	BF595	0.27	BU226	2.45	E1693	2.59
2N4444	0.90	2SC264A	4.82	AD262	1.05	BAX16	0.11	BC556	0.16	BD697	3.60	BF596	0.27	BU312	2.38	DEC1	2.20
2N4914	0.72	2SC2671	1.99	AF114	2.47	BB119	0.17	BC557	0.10	BD698	1.85	BF597	0.18	BU326	2.00	DEC2	2.20
2N5064	0.71	2SC2728	0.95	AF115	1.24	BC107	0.13	BC558	0.10	BD699	3.49	BF617	1.05	BU326A	2.20	E1222	0.40
2N5293	0.50	2SC2785	0.75	AF117	0.75	BC107B	0.11	BC559	0.10	BD700	3.70	BF618	1.10	BU326S	2.20	E5024	0.28
2N5294	0.50	2SC372	1.40	AF118	1.20	BC108	0.15	BC560C	0.14	BD702	3.70	BF694	0.22	BU406	1.49	E5386	0.25
2N5296	0.49	2SC373	1.16	AF127	0.50	BC108B	0.15	BC635	0.36	BD707	1.06	BF757	0.59	BU407	0.82	E5529	0.25
2N5297	0.50	2SC383	1.33	AF139	0.53	BC109	0.12	BC636	0.20	BD709	1.12	BF758	0.65	BU407D	1.29	E8021	1.29
2N5298	0.61	2SC388	0.50	AF178	1.45	BC109B	0.15	BC637	0.24	BD710	0.80	BF759	0.47	BU412	5.29	E9003	0.46
2N5490	1.49	2SC394V	0.81	AF179	0.55	BC113	0.14	BC638	0.20	BD707	0.34	BF760	0.65	BU426	1.90	E9005	0.50
2N5496	0.59	2SC41	2.19	AF180	0.55	BC116A	0.25	BC639	0.20	BD809	0.75						

ECONOMIC DEVICES, PO BOX 228, TELFORD TF2 8QP

HA1338	7.50	M1130	5.35	NE646N	2.98	SAS560	1.85	SN76620	2.59	TA7109	3.71	TC4053BP	4.34	TD2611AQ	2.81	TIP30C	0.40
HA1339	2.23	M191	6.32	NE650N	4.34	SAS560S	1.85	SN76622	1.65	TA7120P	0.64	TC4150	1.79	TD2612CQ	4.81	TIP30A	0.34
HA1342	2.23	M193	18.55	NE654BN	4.18	SAS560T	5.42	SN76623	0.89	TA7122B/P	0.92	TC4180B	1.79	TD2620	1.96	TIP31B	0.58
HA1350	3.27	M51102L	6.35	NP1106	4.80	SAS570	1.78	SN76630	2.55	TA7124P	2.34	TC4270Q	1.71	TD2630	1.96	TIP31C	0.30
HA1365	4.02	M5115P	5.24	OA200	0.11	SAS570P	2.61	SN76640	4.24	TA7130P	1.27	TC4300S	2.15	TD2631	2.73	TIP32B	0.29
HA1366WFR	1.86	M51231P	3.04	OA202	0.11	SAS570T	5.42	SN76651	1.49	TA7136AP	1.27	TC4370S	1.85	TD2640	2.59	TIP32C	0.40
HA1367	4.32	M5124P	4.02	OA47	0.14	SAS580	2.85	SN76660N	2.48	TA7137P	0.98	TC4390A	2.39	TD2643	12.12	TIP33C	0.80
HA1368	1.90	M5134-9341	4.13	OA90	0.08	SAS5800	2.89	SN76665N	1.49	TA7141AP	3.87	TC4420A	2.16	TD2651	2.95	TIP34	1.18
HA1368R	1.98	M51394P	11.97	OA91	0.09	SAS590	2.89	SN76666N	1.41	TA7146P	4.23	TC4440	1.62	TD2652	6.96	TIP41A	0.49
HA1370	3.71	M5142P	5.49	OA95	0.09	SAS5900	2.57	SN76705N	1.34	TA7148P	1.67	TC4500A	2.15	TD2653	6.18	TIP41B	0.31
HA1374A	8.80	M5143P	7.33	OC28	2.52	SAS560	2.96	SN76707N	4.39	TA7149P	3.26	TC4530	2.16	TD2654	4.73	TIP41C	0.45
HA1377	3.96	M5144P	3.77	OC29	2.15	SAS6600	1.33	SN76709	5.12	TA7161P	6.23	TC4640	10.26	TD2655B	3.47	TIP42A	0.79
HA1389	2.39	M51513L	2.56	OC35	1.06	SAS660S	1.33	SN76709N	5.45	TA7162P	2.59	TC4650	2.04	TD2660	2.47	TIP42B	0.49
HA1389R	2.05	M51515BL	3.23	OC36	1.28	SAS6610	1.33	SN76730	4.66	TA7169	9.54	TC4660B	3.30	TD2661	2.47	TIP42C	0.62
HA1392	3.90	M51516L	3.95	OC44	0.35	SAS670	3.96	SN76810N	0.60	TA7171P	2.79	TC4730	3.81	TD2670	2.48	TIP47	0.85
HA1394	3.95	M51517L	3.71	OC45	0.18	SAS6700	1.33	SN76920N	2.90	TA7172P	1.41	TC4740	2.48	TD2670A	1.94	TIP48	0.92
HA1397	3.76	M5152L	2.88	OC75	0.44	SAS670S	1.33	SN94041	5.54	TA7176P	2.48	TC4750	1.93	TD2680	3.20	TIP49	3.61
HA1398	3.98	M51522	5.39	ON188	1.87	SAS6710	1.87	SN94042	4.35	TA7193AP	6.67	TC4800	5.95	TD2690A	2.65	TIP55A	1.35
HA1406	2.07	M5191P	4.94	ON236	1.06	SAS6800	2.53	SP8385	0.55	TA7193P	4.95	TC4800Q	5.95	TD2780AQ	5.14	TIS43	3.84
HA1452	1.63	M5192	2.20	OT112	1.32	SAS6810	1.43	STA441C	2.75	TA7201P	2.71	TC4830S	2.38	TD2790Q	6.52	TIS90	0.21
HA17723	5.94	M5194AP	5.74	OT121	1.00	SBA550B	1.54	STK0029	5.54	TA7202P	2.47	TC4900	2.04	TD2791	2.50	TIS91	0.29
HB4030AF	2.48	M53273P	1.02	PD144	2.24	SBA750	1.61	STK0039	5.35	TA7203P	2.18	TC4910	1.65	TD2795	2.76	TMS1000NL	11.86
HD38750A53	8.71	M53274P	1.33	PT2014	3.04	SC9488P	3.04	STK0050	7.67	TA7204P	2.16	TC490E	2.93	TD3000T	2.55	TMS3748HS	16.13
HQ4480	17.16	MA06	1.07	PT5006	2.48	SC9503	1.65	STK0059	7.13	TA7205	1.38	TC530	3.89	TD3030A	1.49	TMS4116	2.06
HD44801A05	17.49	MA8001	0.82	PT6042	1.79	SC9504P	1.95	STK0080	9.16	TA7206P	6.25	TC527	1.86	TD3190	21.68	TV106	1.76
HEF4001P	0.67	MB3705	1.79	R1038	2.19	SC9511P	2.09	STK011	3.96	TA7207P	3.34	TC682	1.08	TD3300B	6.27	UY6010B	2.97
HEF4001BP	0.67	MB3712	1.85	R1039	2.19	SC9517	1.33	STK013	7.75	TA7208P	2.15	TC683	1.08	TD3300	4.45	Y05G	1.14
HEF4011	0.29	MB3713	1.69	R2008B	1.33	SG264A	5.26	STK014	8.84	TA7210P	3.58	TC684	1.08	TD3501	12.09	U143M	3.08
HEF4528	0.00	MB3730	3.25	R2009	1.99	SG613	8.75	STK015	7.75	TA7211P	3.63	TCEP100Q	10.25	TD3506	9.99	U37003	0.49
HM6231	9.81	MC13002	6.22	R2001B	1.33	SG625	8.27	STK016	6.91	TA7215P	2.57	TCEP100	9.61	TD3510	6.55	UA723CA	5.53
HM6232	8.89	MC1303P	2.16	R2029	1.33	SG6533	10.31	STK022	5.25	TA7217AP	1.38	TD190	0.95	TD3520	9.14	UA758PC	5.29
HM9102	3.22	MC1307P	1.92	R2030	1.33	SI-1125HD	13.85	STK025	8.27	TA7222	1.95	TD3F700H	6.60	TD3521	13.39	UA783PC	3.28
HM9104	3.24	MC1310P	1.30	R2257	2.36	SI1125H	7.50	STK040	8.70	TA7227P	2.81	TD3F800H	4.86	TD3540	2.86	UAA170	2.35
HM9105	3.24	MC1322P	1.33	R2265	1.19	SKE2F 104	1.39	STK043	10.48	TA7229P	3.45	TD3F800R	3.66	TD3560	5.00	UAA180	2.46
HT4207	17.16	MC1330P	1.69	R2305	1.49	SKE2G 204	0.95	STK054	7.13	TA7233P	4.26	TD3F900H	4.16	TD3561	6.50	ULN2165	1.39
IT7203	0.22	MC1349P	0.81	R2306	1.26	SKE2G 304	1.05	STK070	22.31	TA7240AP	6.75	TD41003A	1.79	TD3561A	7.20	ULN2204	7.45
K174YP	3.46	MC1350P	1.21	R2322	0.59	SKE4F 102	1.39	STK077	7.67	TA7242P	7.57	TD41005A	2.22	TD3571A	6.54	ULN2216F	2.15
KA2101	2.92	MC1351P	1.33	R2323	2.01	SKE4F 106	0.73	STK078	8.52	TA7314	5.94	TD41006A	1.69	TD3571Q	2.83	UPC1009C	6.32
KC581C	6.32	MC1352P	1.12	R2348	2.06	SKE4F 206	0.05	STK082	11.86	TA7325P	0.98	TD41010	1.33	TD3576	7.09	UPC1001H	7.25
KC582C	3.97	MC1357P	2.15	R2354A	2.01	SKE4F 208	0.84	STK086	10.89	TA7609	3.17	TD41011	2.40	TD3590	6.79	UPC1026C	1.24
KC583C	5.54	MC1358P	1.30	R2354B	1.36	SKE4F 210	1.26	STK2101	6.32	TA7676P	2.81	TD41028	2.45	TD4350B	1.54	UPC1028H	2.00
L129V	0.25	MC14001	2.40	R2441	2.01	SKE4G 202	0.96	STK2110	7.33	TA7676P	2.81	TD41029	4.89	TD4050A	3.47	UPC1020H	2.77
L200CV	1.69	MC14013	0.41	R2443	0.89	SKE5F 3/10	1.60	STK2230	7.70	TA7676P	1.16	TD41035T	2.56	TD41809P	1.92	UPC1020H	2.90
LA1111AP	0.88	MC14016CP	0.84	R2461	1.00	SL1310	3.14	STK415	7.70	TA7676P	1.27	TD41034B	2.42	TD4A260	1.54	UPC1032H	0.47
LA1201	1.02	MC14011	0.26	R2477	1.02	SL1327E	1.33	STK433	4.55	TA7676P	0.80	TD41037	2.96	TD4A280	7.20	UPC1030H	2.27
LA1210	1.56	MC14025	0.80	R2501	1.28	SL1430	1.39	STK435	5.94	TA7676P	1.82	TD41037D	3.25	TD4A290	4.40	UPC1031H	8.58
LA1230	2.87	MC14049UBC	0.58	R2540	3.90	SL1430T	2.31	STK436	7.21	TA7676P	0.37	TD41041	2.16	TD4A400	4.97	UPC1031H2	6.00
LA1320	2.87	MC1438R	1.05	R2540X	1.38	SL1432	2.25	STK437	7.80	TA7676P	1.74	TD41044	2.31	TD4A400	2.27	UPC1154H	1.93
LA1352	1.54	MC14459P	2.82	R2615	3.47	SL414	3.69	STK439	8.31	TA7676P	1.30	TD41047	4.10	TD4A420	3.95	UPC1156H	2.96
LA1357N	6.49	MC14556BPC	3.47	RCA195NB	2.16	SL432A	3.09	STK441	11.28	TA7676P	2.48	TD41054AM	1.21	TD4A422	8.32	UPC1185H	2.94
LA1363	3.02	MC1712	3.88	RCA18063	5.30	SL437	7.43	STK443	10.29	TA7676P	4.24	TD41059B	0.80	TD4A430	4.78	UPC1182H	1.82
LA1364	6.21	MC7724CP	2.01	RCA18029	2.01	SL439	2.48	STK459	9.40	TA7676P	1.59	TD41060	2.59	TD4A431	2.27	UPC1186H	1.05
LA1365J	3.44	MC7818C	2.18	RCA18334	1.02	SL480	2.30	STK460	10.75	TA7676P	2.50	TD41062	3.06	TD4A432	2.27	UPC1181H	1.25
LA1378	6.52	MC7824CP	4.68	RCA18335	1.36	SL490	2.37	STK461	9.68	TA7676P	2.50	TD41104	6.55	TD4A400	2.87	UPC1213C	0.97
LA1385	1.87	MC78M12	0.83	RCA18600	2.38	SL901B	8.32	STK463	11.53	TA7676P	4.83	TD41151	2.87	TD4A600	2.84	UPC1217C	2.49
LA1387	7.60	MC78M24P	0.94	RCA18799	1.36	SL917B	11.56	STK465	10.31	TA7676P	2.87	TD41170S	2.57	TD4A610	3.11	UPC1212C	1.72
LA3155	1.25	MCR100	0.38	RCA18801	0.95	SL918A	9.07	STK466	11.77	TA7676P	2.52	TD41170S	2.52	TD4A620	4.46	UPC1251C	1.81
LA3300	1.54	MCR101	0.67	RCA18802	1.08	SN16961N-07	2.72	STR441	10.73	TAG232-600	0.73	TD41180	2.90	TD4A500	2.73	UPC1353	7.05
LA3301	1.41	MCR106/5	1.57	RCA17028	2.48	SN16969	3.63	STR453	8.16	TAG262-600	1.06	TD41190	2.48	TD45700	2.51	UPC1350C	1.87
LA3350	1.43	MCR2207/7	2.28	RCA17074	1.95	SN16985	8.95	STR6020	8.31	TA6120	1.05	TD41190Z	2.11	TD49000	2.92	UPC1355C	2.13
LA3361	1.23	ME0402	0.17	RCA17376	1.58	SN16996N	6.04	T6007V	0.95	TA6120A	1.06	TD41200A	1.17	TD49403	5.15	UPC1362	7.15
LA4030P	4.20	ME0404	0.26	RCA60857	4.95	SN29715N	6.04	T6007	0.62	TA6120AS	1.24	TD41220	1.95	TD49503	2.92	UPC1365	8.70
LA4031P	3.20	ME0404/2	0.47	RGP10	0.50	SN29716N	3.66	T6016	0.40	TA6120S	1.05	TD41230	3.23	TD49513	5.48	UPC1366	6.54
LA4032P	1.92	ME0411	0.28	RT402	1.58	SN29717N	7.19	T6017	0.72	TA6120SB	1.05	TD41235	3.88	TE527	1.34	UPC1360C	4.51
LA4050P	1.57	ME0412	0.24	RT905A	2.38	SN29722	11.95	T6018V	0.72	TA6120T	0.95	TD41270	3.74	TE538	1.40	UPC1458	8.66
LA4051P	1.79	ME4102	0.50	SO280	2.14	SN29723AN	7.65	T6021	0.40	TA6120U	2.50	TD41327A	1.50	TE626	0.49	UPC2022	1.88
LA4100	1.25	ME546B	10.02	SO281	1.75	SN29744N	2.29	T6022V	3.92	TA61440	2.03	TD41327B	1.76	TEA1002	3.47	UPC30C	2.51
LA4101	1.30	ME6002	0.26	SI299	4.74	SN29764AN	1.38	T6026	0.98	TA61440G	7.02	TD41330	1.82	TEA1009	1.86	UPC32C	4.94
LA4																	

Ferguson 3V29

This machine had an interesting fault. When switched on channel 1 would come up as normal but the machine would then select channel 8 and stay there no matter which programme button was pressed. Spillage was at first suspected, but a thorough clean of the preset panel did no good. A check with the remote control unit then showed that channel change this way was also inoperative. Checks around the UPC1362C i.c. on the panel (IC201) proved that the oscillator was working and that pulses were present when the buttons were pushed, but a replacement chip made no difference. Further checks showed that the voltages at pins 2 and 3 were incorrect though the most significant difference was at pin 13, which was low at 3V. The voltage at this pin should normally be high at 9V, going low when channel change is pressed on the remote control unit, initiating channel change and preventing further channel change until the pin goes high. Further investigation showed that diode D221 was leaky, a replacement curing the problem. **D.S.**

Mitsubishi HS700

The complaint with a Mitsubishi HS700 was "smoking". When the machine was stripped down and set to play we found that the drum didn't revolve and that the HA11715 drive i.c. had gone up in smoke. A replacement was fitted and worked all right for a couple of days after which it went up in smoke again. This time when we replaced it the head went flat out – a few seconds of this would cause the i.c. to overheat and go up in smoke. The fault was traced to IC4P0 (TL082CP). **D.S.**

Mitsubishi HS306

On the subject of fuse blowing (see VCRs and the Mains Supply, July), the rating of the mains fuses in the Mitsubishi HS306 has now been officially increased to 630mA (previously 400mA). **D.S.**

Hitachi VT5000

This machine had nasty intermittent mechanical problems. It would sometimes refuse to come out of the pause mode, going to stop instead after a few seconds: in addition speed variations were sometimes present during record or playback. These things were all caused by the after-load switch S931 – its contact was erratic. The speed variations occurred because of insufficient pinch roller pressure against the capstan, due in turn to the slightly premature termination of the loading process. **E.T.**

Sony SLC9/F1

We were left with an excruciating noise from the threading mechanism after we'd sorted out the primary fault on one of these machines. It sounded exactly as if the teeth of a cog were catching against a stray cable. In these models a small threading motor belt drives a tight little assembly of gears whose final drive simultaneously turns the threading ring clockwise and the slider arm (carrying the pinch roller) anticlockwise. It's not easy to see down into this

lot, so we carefully dismantled the threading drive system. It looked all right, and no problems could be felt when we rotated things by hand.

Back together it all went, but the results were exactly the same as before. After a great deal of investigation the problem was traced to the loading pulley. This plastic member consists of a pulley and cog moulded in one piece. The cog section had a tiny radial crack between two teeth: the resultant irregular tooth spacing had caused the shocking rattle. Sony part no. X-3670-087-0. **E.T.**

Sanyo VTC5000

The complaint with this machine was no colour. We so seldom encounter real colour faults on VCRs these days that we find ourselves a bit rusty when it comes to the principles of colour-under systems! It wasn't necessary to look very far in this case however. The fault was present in both record and playback, and we found that the signal from the sub-mixer in IC1006 (pin 30) was virtually non-existent. Both the sub-mixer inputs were present and correct – 4.43MHz at pin 27 and the divided-by-eight voltage-controlled oscillator output at pin 26. The voltages at pins 26-30 of the i.c. were also correct, so what was happening to the mixer's 5.12MHz output? It was getting lost in T1010, the first half of the bandpass filter. The tiny signal downstream at C1179 increased as we wound the core of T1010 right out: either this little transformer had developed short-circuit turns or the tiny resonant capacitor built into it had gone bad. Since the transformer is connected to the 9V rail there was no effect on the voltage at pin 30 of the i.c. A replacement transformer (part no. 4-259V-20800) cured the problem. **E.T.**

Sharp VC381

The motors used in Sharp VCRs have not distinguished themselves in the reliability stakes. A recent example occurred in a VC381 which suffered from intermittent failure to rewind and sporadic tape spillage during unthreading – when the supply spool would fail to take up the slack from the returning guide poles. These symptoms are often down to a worn reel idler, but on several occasions we've found that the reel motor has been at fault. The problem seems to be due to the design of the brushgear and commutator: its effect is to make the motor lazy and current hungry, sometimes to the point where one of the power supply fuses F901 or F902 (on panel PWB-0) blows. Miraculously, the reel motor drive chip IC706 seems to survive all this. A modified motor is now being supplied for replacement purposes by Sharp and its spares agents. **E.T.**

Ferguson 3V29/30, JVC HR7200/7300

One or two mechanical faults are beginning to occur with some regularity now that these machines are three or so years old. A slipping loading belt can give rise to misleading symptoms: the machine will thread up (but not quite fully) on play, then after a few seconds of nothing signal-wise unthreading will take place, the machine going to stop. The clue here is that the loading motor continues to

The Lid off Microcomputers

Part 5

Mike Phelan

Last month we talked about storing computer programs on ordinary audio tape cassettes. This has the advantage of using tapes that are readily available and comparatively cheap. In addition, if the microcomputer doesn't have a built-in cassette recorder any small mono cassette recorder can in most cases be used. There are exceptions however. One popular make of home microcomputer requires a special dedicated cassette recorder that contains part of the interfacing circuitry. Note that we said a mono recorder: with stereo machines the track width is less and the output is thus more susceptible to the effects of azimuth errors and pinholes in the tape's oxide coating. A good treble response is necessary. Different machines vary in their degree of tolerance on all these points.

On the debit side, loading from tape is slow – with some machines a complex game can take twenty minutes. More importantly the tape must be played or fast wound to the part required if there's more than one item on it. If we have stored a file of data on tape, say names and addresses etc., we cannot load just one name and address, we must continue loading until the required information appears.

Disc Systems

These disadvantages can be solved by using one or more disc drives. These come in several sizes: the one that can be added to the Amstrad CPC464 is a three inch floppy disc drive. The discs themselves are made from flexible plastic sheeting and are covered on both sides with magnetic oxide. They are permanently fitted in rigid plastic cases – see Fig. 1. The slot in the case enables the disc drive to gain access to the disc surface to read and write (play and record) information. With a three inch disc these slots (one on each side) are normally covered by metal shutters which slide back when the disc is put in the drive. These discs have a capacity of 180Kbytes per side. On this machine there is only one head, so only one side can be used at a time. When the disc is inserted the centre, exposed part is gripped by two limbs to rotate it: the head is lowered into a position where it just contacts the disc.

The head is mounted on a sliding carriage that travels radially along the slot, from the centre to the periphery, under the control of a servo-operated stepping motor and the spiral track. Head position and disc rotation are controlled by the computer and disc drive electronics.

A new disc is totally blank and must be "formatted". This process remagnetises the disc in such a way that it's divided into 40 concentric tracks and nine radial sectors (see Fig. 2), giving a total of 360 sectors each of which can hold 512 bytes, i.e. 180Kbytes per side. Formatting can be thought of as the equivalent to ruling lines and columns on a sheet of paper before use. The alignment or index hole tells the electronics, with the aid of an optical sensor, the rotational position of the disc.

The total of 180Kbytes is a lot of information in such a small space, so the data is stored in a very compact form. The head gap is quite small and, for good h.f. response, the rotational speed is quite rapid. The system is intolerant of disc wear, dust and damage (such as fingermarks on

the oxide coating) but is very reliable when looked after properly.

Two of the disc's tracks are reserved for a special purpose. These are the directory and file allocation table. Between them they hold information on the files on the disc, on what type of files they are and on what sectors and tracks the files occupy. Thus if the computer looks here first it can rotate the disc and move the head directly to the required sector and track. In this way the two disadvantages of tape storage are overcome – loading speed is typically a few seconds.

The DD1 disc drive used with the CPC464 needs an interface for connection to the computer – the newer CPC664 has a built-in disc drive in place of the cassette deck. A second disc drive can be added to either machine to enable discs to be copied.

Copying and formatting cannot be done using the microcomputer's resident language, BASIC. Renaming or erasing files or copying single files only are useful features. For all these purposes a disc operating system, like another language, is needed. There are various disc operating systems: the one used with the Amstrad machines is CP/M, which stands for Control Program for Microcomputers. Part of it resides permanently in the disc drive ROM – this part is sufficient only to load the rest of the program from a CP/M disc, or to give the appropriate error message when a disc is not inserted or the disc doesn't contain CP/M. The disc drive contains the CP/M command processor and other CP/M programs to do things like formatting and copying discs.

When a disc drive is fitted the microcomputer starts off with BASIC as normal, selecting CP/M from BASIC as required. Alternatively some but not all CP/M commands can be operated from BASIC – the converse is not true. Note that the disc drive must be switched on before the computer for the latter to recognise the drive's presence. Any or all the CP/M programs can be copied on to a disc: there is also a facility to embed a command line so that, when CP/M is entered, a command can be executed automatically.

Copying can be done with only one disc drive, but it's a laborious business as the source and destination discs have to be swapped several times. This is because only so many tracks at a time can be read into the RAM: the discs are then swapped over and the information written out to the second disc.

In contrast, with most business machines the operating system(s) and language(s) have to be loaded in before use. There could be several of each – some languages are available only with a particular operating system. Some of these machines use a hard disc system with a capacity of 5 or 10Mbytes per disc – this is a sealed item that never comes out of the machine. One way of arranging things is for the operating system to start, automatically, a program that loads a language, then to execute a program that allows the user to select various languages and/or programs. After switching on, the next thing to appear is a menu of choices – after a minute or so since some 640K of RAM takes more than a second or two for the machine to check.

Unless the fault is a fairly obvious one it's best not to

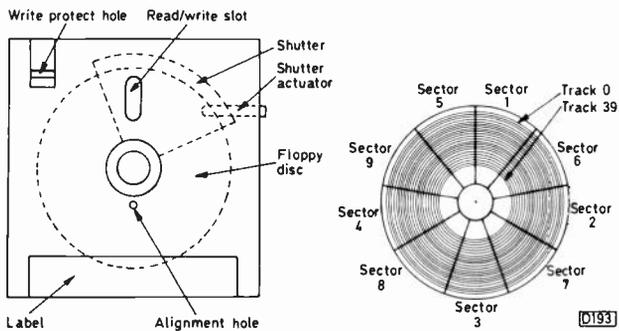


Fig. 1 (left): Three inch floppy disc.

Fig. 2 (right): Arrangement of tracks and sectors.

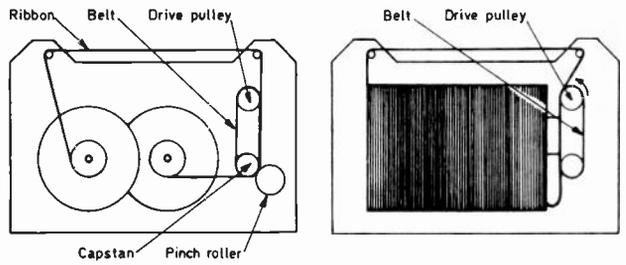


Fig. 7: Two types of ribbon cassette.

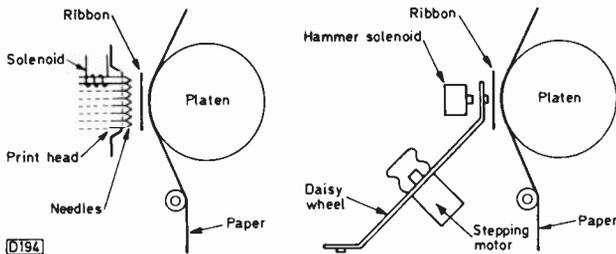


Fig. 3 (left): Matrix printer operation.

Fig. 4 (right): Daisy wheel printer operation.

used to drive the print head laterally – another stepper motor drives the platen that feeds the paper.

The daisy wheel printer (see Fig. 4) is slower, usually noisier, but gives better quality printing. It works like a modern typewriter. The daisy wheel itself is made of springy plastic or metal and has as many radial arms as there are characters in the character set: each arm has a typeface character at its end, which is struck by a solenoid-operated hammer. A stepper motor rotates the wheel to bring the required character in front of the hammer, the rotational position of the wheel being optically sensed by a short arm or wide gap. The daisy wheel can be quickly changed to get a different typeface – thus the characters printed out may not be identical to those appearing on the monitor's screen.

The printer/plotter (see Fig. 5) is much slower but is quieter than either of the above: it can draw or print in a mixture of different colours. It draws the characters rather than printing them, using four miniature coloured ball-point pens mounted on a rotating head that tilts forward to contact the paper. The usual method of rotating the head to bring a different colour into use is to traverse the head to a position past the margin, where it contacts a detent or pawl that rotates it through 90°. Printing and drawing are done by a combination of lateral movement of the pen head and vertical movement of the paper, by rotating the platen in either direction. Often the software can select up to 64 sizes of letters as well as the colour.

All printers require some fairly sophisticated electronics to translate the serial or parallel code from the computer into the various mechanical operations required. Provision is also usually made for feeding one line or form length by switches, or taking the printer "off line" – in effect pausing it. Switching back on line enables the printer to carry on where it left off. Some printers have error lights to show things like "no paper" etc. As a rule an error takes the printer off line.

Printers can develop faults and require regular cleaning – paper, dust and fragments accumulate. Daisy wheels must be cleaned because the typefaces become clogged with ink. Ribbons can be on a spool or in a cassette, fabric or plastic. The spool type operates like that in a typewriter, the direction of travel reversing when either end is reached – eyelets in the ribbon reverse the drive. Fig. 6 shows the arrangement.

The cassette type of ribbon (see Fig. 7) usually travels with the print head. They don't usually auto-reverse – the extra drive tension when the ribbon reaches one end operates a warning light. Others store the ribbon in concertina form, as an endless loop from which it's pulled by a flat belt. This type just gets progressively fainter. Both types can sometimes be obtained for a given printer, the once-only type being plastic based, the other usually fabric based. The plastic ribbon has just a coating of ink rather than being soaked in it, so there will be a bare

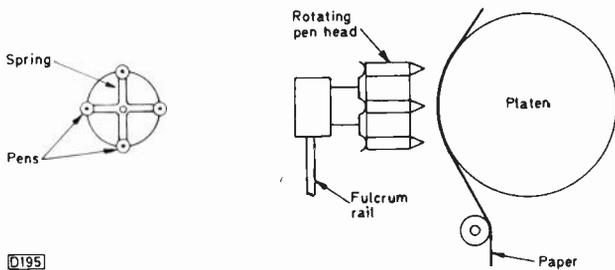


Fig. 5: Printer/plotter system.

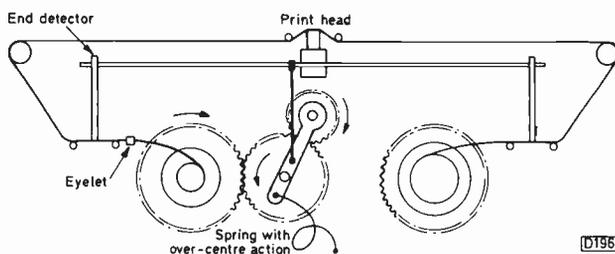


Fig. 6: Ribbon reversing mechanism.

attempt to carry out repairs to disc drives – though we said that about Band III tuners at one time!

Printers

The other popular peripheral for the home microcomputer is a printer. There are basically three types, matrix, daisy wheel and printer/plotter – there are also some very sophisticated types that are used for commercial purposes.

The matrix printer (see Fig. 3) is usually the cheapest and fastest in operation. Printing is done by a vertical row of steel pins operated by tiny solenoids. Each character is constructed from say a 6 x 8 matrix of dots. This means six printing operations, one for each vertical row of up to eight dots: between each the print head moves laterally the width of one dot or slightly less. A stepper motor is

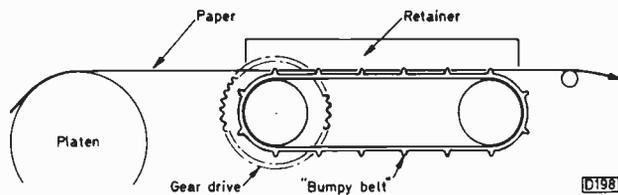


Fig. 8: Tractor feed arrangement.

patch where a character has been printed.

Sheet and tractor feeds are common printer accessories. The sheet feeder prints out on separate sheets, e.g. for letters: the cut sheets are stored in a bin, loaded automati-

cally, then ejected into another bin. The feeder usually has its own motor and electromagnetic clutch. The tractor feed transports the perforated edge sheets that we think of as typical computer printout. To appreciate the reason for using this arrangement, consider printing out fifty feet of continuous sheet, relying on the platen for drive. There's no way of ensuring that the paper will travel squarely so before the fifty feet could be printed there would be an awful crumpling noise, as the paper would have gradually crept over to the right or left. The use of tractor feed gives positive paper transport via the perforations, using two drives best described as "plastic belts with bumps on"! It's usually driven by gears on the platen - see Fig. 8.

Next month the Amstrad monitor and fault finding.

Teletopics

FIRST QUARTER RESULTS

Sales of colour sets to the public during the first quarter of 1985 rose by over 7.5 per cent in comparison to the same period last year, though deliveries to the trade decreased (there was a certain amount of destocking). So while the high street tills were ringing away merrily there's been increased financial pressure on setmakers. VCR deliveries increased by 7.6 per cent, with about a sixth being UK assembled. CTV imports decreased slightly despite a continuing trend towards small-screen sets, which now account for approaching fifty per cent of deliveries to the trade.

ECONOMIES ALL ROUND IN BROADCASTING

The BBC has announced economies to meet the financial problems it faces following the less than asked for increase in the licence fee. The aim is to spend more on programmes and the provision of extended services while cutting down severely on the office and engineering side. Some 4,000 of the present 25,500 staff jobs are expected to go while over 1,000 of the 7,000 staff engaged in programme making are to be transferred to a contract basis. The proposals are described by the director general Alasdair Miln as the "most radical changes in thirty years". Engineering research and the design and production of in-house equipment are to be cut back; catering, cleaning, security and building maintenance are to go to outside tender if this is cheaper; and a ten per cent cut in secretarial jobs is to be sought. In addition, more programmes will be bought in from independent producers and the regional structure is to be changed, with single management teams for regional TV and local radio.

On the positive side, a full daytime BBC-1 service is to be introduced next year; there's to be a twenty per cent increase in news magazine budgets, both national and regional; an extra £3 million a year is to be devoted to the production of "blockbuster" TV drama; the local radio chain in England is to be completed as a matter of priority; and Radio 1 at v.h.f. is to be started as an "urgent" priority. As an economy on the radio side, Radio-2 will be broadcast by all local radio stations after 7 p.m.

As a result of the IBA's intention to increase the charges it makes to the ITV companies by five per cent more than the rate of inflation, the Independent Television Companies Association has been in talks with the

BBC and the IBA on ways of cutting costs. Suggestions include shared transmitter costs, privatising the provision of transmitters or allowing the ITV companies to own instead of rent the transmitters; a reduction in the research and development work carried out at the IBA's Crawley Court engineering centre, with equipment research carried out by industry under contract; and a proposal that the IBA should be allowed to fund its capital investment by means of long-term commercial loans instead of via rentals from the ITV companies.

UK SATELLITE TV MOVES

The Satellite Broadcasting Board has been wound up, since there's at present no industry for it to regulate. It was chaired by the IBA's chairman Lord Thomson, who has been asked by the government to investigate whether companies might be interested in starting a DBS service organised by the IBA. It's understood that this time those intending to start such a service would be able to put out to tender the provision of a satellite system - the government's insistence that a UK satellite system provided by Unisat should be used was the main stumbling block that led to the collapse of the proposed consortium of 21 DBS service.

Sky Channel, which is at present available to over three and a half million cable TV subscribers in twelve European countries, is to extend its broadcasting hours. The service will run from 7.45 a.m. to 12 p.m. on weekdays and 7 a.m. to 12 p.m. at the weekends, UK time.

VIDEO CAMERA MARKETS

A survey of international video camera markets has been published at £25 by Euromonitor Market Direction, 87-88 Turnmill Street, London EC1M 5QU. It points out that while VCR market penetration in the UK is high camera sales have been weak - a mere 35,000 last year out of total world sales of 1,165,000. Most video cameras are sold in W. Germany, Japan and the USA.

VCR TARIFF INCREASE

EEC industry ministers have agreed to increase the tariff on imported VCRs from 8 to 14 per cent from next year. A compensation plan, required by GATT regulations, includes a proposal to reduce the tariff on imported semiconductor devices from 17 to 14 per cent. Not unexpectedly, the proposed increase in VCR tariffs has come in for criticism from the Electronics Industry Association of Japan and from South Korean trade ministry officials. Counter measures are being considered by South Korea while Japanese manufacturers are expected

to concentrate on increasing the output from their European plants.

Philips is to set up a joint venture with the South Korean manufacturer Dongwon Electronics to build a plant to produce VHS machines for sale in the Far Eastern and US markets. Initial plans are for production to start at 500,000 machines a year, rising to a million a year by 1989. The plant would require an investment of \$50 million and would be 70 per cent owned by Philips.

DTI RADIO SERVICE CHANGES

The Department of Trade and Industry has decided to alter the services provided by its Radio Investigation Service. More resources are to be devoted to tracing those who operate without a licence or fail to keep to the terms of their licence, and there's to be a phased withdrawal from dealing with domestic radio/TV reception problems. A booklet is to be issued to help members of the public to deal with their own problems. Business users are to be charged a commercial rate for RIS advice and domestic users will be charged a call-out fee of £21 to investigate cases of poor reception.

FERGUSON'S PROBLEMS

The reduced profit announced by Thorn EMI for the year to March 31st, despite an increase in turnover, has been partially attributed to the Ferguson consumer electronics side of the business – also to difficulties at Inmos, which Thorn EMI bought during the year. A provision of £28 million has been made for reorganisation at Ferguson, which will involve job losses of around 1,000 and rearranged production facilities. In future the Enfield plant will produce subassemblies – remote control and tuning systems etc. – with all complete receiver assembly work being carried out at the Gosport plant.

The problems at Ferguson, which have continued into the first quarter of the present financial year, are put down mainly to over-capacity in the UK television manufacturing industry: profits fell from £85.3 million to £65.5, with the situation worsening towards the end of the year. The retail and rental side announced increased profits however, up from £77.9 million to £86.6 million.

Sir Graham Wilkins has replaced Peter Laister as chairman and chief executive of Thorn EMI.

The Ferguson service department at Chadderton, Lancashire has been closed down with a loss of fifty jobs: the trade counter and dealer training school remain in operation.

TELETEXT PROMOTION

The industry and broadcasters are combining to promote teletext set sales this autumn. The aim is for one million teletext set sales/rentals over the next twelve months. According to the latest IBA annual report over 2.6 million homes now have a teletext set, i.e. over eight million people have access to teletext.

Both the BBC and the IBA are planning to use spare teletext capacity to provide commercial services.

DEMONSTRATION TVRO PACKAGES

Both Luxor and Salora have introduced demonstration 11GHz band satellite receiver packages for sale to dealers. Details can be obtained from Luxor (UK) Ltd., 87-89 Farnham Road, Slough, Berks, SL1 4UL; and Salora (UK) Ltd., Techno Trading Estate, Swindon, Wilts, SN2

6EZ. Several 11GHz satellite channel programme providers, including Premiere and Music Box, have set up a marketing company called Galaxy Satellite Television. A demonstration agreement charge from Galaxy costs £25 a month (this is included in the Salora package).

NEW MULLARD LINE OUTPUT TRANSISTORS

The BU506 and BU706 line output transistors from Mullard are lower-current rated versions of the established BU508A, intended for use in small- and medium-screen size sets. Both transistors have the same electrical characteristics – 3A rated collector saturation current and 1.5kV maximum collector-emitter voltage – the difference being in the encapsulation. The BU506 is housed in a TO220 pack and the BU706 in a SOT93A pack.

PUBLICATIONS NOTED

The latest issue of the BATC's journal *CQ-TV*, no. 131, includes an interesting practical article on converting the Thorn TX90 chassis for receiver/monitor use. A PCB for the interface circuit is available from the author. For British Amateur Television Club membership details, write to D. Lawton, Grenehurst, Pinewood Road, High Wycombe, HP12 4DD.

A new catalogue is available from Anglia Components, Burdett Road, Wisbech, Cambs. PE13 2PS.

A brief but helpful introduction to DX-TV, "TV DX for Beginners" by Simon Hamer, is available from HS Publications, 7 Epping Close, Derby DE3 4HR at £1.65 including post and package. Airmail despatch is extra. Roger Bunney's more substantial publication "Long Distance Television Reception (TV-DX) for the Enthusiast" (Bernard Babani Publishing Ltd.) is at present out of print – a new edition is expected shortly.

VIDEO NEWS

The latest VCRs from Ferguson, Models 3V44 and 3V45, replace the 3V38 and 3V39. They are slim-line models featuring simple operation and use the same basic chassis as the JVC HRD140. The 3V45 incorporates remote control. Grundig has added a hi fi machine, Model VS380, to its VCR range: the suggested retail price is around £650. A version of the Sony Super Beta machine (see *Teletopics*, July), Model SLHF950, is to be released in the UK with a suggested price of just under £800: the performance is claimed to be of almost broadcast standard. Canon is to launch an 8mm camcorder in the UK this autumn.

BUSINESS MOVES

ITT Consumer Products (UK) has relocated its head office in Basildon in a move that takes it from premises shared with STC. The new address and telephone number are: ITT Consumer Products (UK), Paycocke Road, Basildon, Essex, telephone 0268 27788. The service departments remain at Chester Hall Lane, Basildon; East Kilbride, Glasgow; and Kearsley, Bolton.

NordMende consumer electronics products are in future to be handled in the UK by Hayden Laboratories Ltd. (0753 888447) who will take on all outstanding guarantee commitments. Previously NordMende (and Saba) products were handled by the European Electronics Corporation of Aylesbury, which has now ceased to trade. NordMende, Saba – and the European Electronics Corporation – are all part of the Thomson Brandt group.

A Case of Liquid Spillage

Nick Lyons

The spillage of liquids on to and into electrical equipment is always bad news. The situation will be much worse if the equipment is on at the time of the spillage, though many liquids will cause bad corrosion when the equipment is off. I find that soft drinks and household cleansers are the usual cause of the trouble, closely followed by cups of tea. Really, accidents are almost bound to happen – and children will be children.

The result of one such accident appeared on the workbench recently – a very sad looking Sharp VC381H. The owner seemed unsure of the nature of the spillage. I tend to think it was a soft drink, but whatever it was it had certainly done considerable damage. The company from whom the machine had originally been purchased – a large retail chain – had declared it to be a write off, being more costly to repair than to replace. This had rather upset the owner as the machine was not that old, so he'd brought his custom to me.

Layout

For those not familiar with this machine I'll give a brief outline of its layout. The majority of the electronics are arranged on two large boards. The lower one encompasses the entire bottom of the machine and is mounted foil side down, component side up. It's mainly concerned with the servo systems. One nice feature of this board is that all the "tweaks" are at the rear right-hand corner. Thus with the top cover off and the top PCB hinged up, which takes but a minute, the full range of servo adjustments can be immediately performed without the usual tedious business of hunting around the board for the various VRs.

The other major board sits foil side up beneath the top cover: it's about two thirds the area of the lower board and carries the circuitry for signal processing from off-tape r.f. through to composite video. Off-air demodulation, the power supply etc. are arranged on much smaller boards dotted around the chassis.

The liquid had entered the machine through the ventilation holes in the top cover, mainly on the right-hand side. It had run over the print side of the top board, dripping off the right-hand side of this on to the board beneath. The lacquer on the foil side of the top board had saved the print, though some of the soldered joints were blackened.

Repairs

The first step was to clean up the panels, then assess the damage. Most of the crystalline deposits were removed with the dust brush: sponging the panel down with a damp (not wet) cloth removed the rest and much of the staining. The contaminated areas were next washed down with isopropanol – we use this for head cleaning and have a quantity on hand – aided by an old toothbrush to make sure that the isopropanol got everywhere. The isopropanol served more than one purpose: it helped remove the remaining contamination and, being volatile, readily evaporated driving off the remaining water. Not being enough of a solvent it didn't damage the board – if

you use too much on the foil side it makes the lacquer go sticky.

The next move was to plug the machine in and see what happened. The good news was that the machine threaded up and went into the play mode, the bad news was that there was no picture. Video information was present however, in the form of a pattern that looked as if the monitor's line hold control was grossly misadjusted. This was obviously due to the speed of something or other being wrong. Well, the sound seemed to be of the correct pitch, so the capstan circuit was probably o.k. When we looked at the head drum beneath the workshop fluorescent lights it appeared as just a blur. I should perhaps point out that the strobing effect of the mains supply in relation to the head drum can be a useful aid to fault diagnosis. Because of the strobe effect the larger drum details should appear to be virtually stationary, slight apparent rotation being caused by the difference between the machine's 50Hz reference and the mains frequency. As these features were just blurs the drum must have been running grossly off speed. It's usually possible to see whether a drum is running very slow. This one appeared to be running too fast however. To test this I rested a finger lightly on the upper rim of the drum to slow it down, gradually increasing the pressure. Sure enough when the drum was slowed down sufficiently the picture dropped into lock. In monochrome, but a picture nonetheless.

This gave me a clue as to where to start. The head drum servo circuitry is on the bottom board, in an area that had been badly contaminated. Close examination revealed that some of the legs of the relevant IZ003GE i.c. had rotted through. Substantial corrosion of the legs of the surrounding transistors and diodes had also taken place. There are only a few passive components in this area. I took the decision to replace these as well.

This time switching on produced a fully locked monochrome picture. Further investigation was required on the upper panel therefore. Suspicions centred on the HA1178INT chroma chip IC501. Unfortunately the manual doesn't give the waveforms to be expected with this i.c. so a bit of educated guesswork was required: some of them didn't look too good, so the chip was replaced. At this point colour returned. It would stay for hours and hours then twitter up and down in level, subsequently disappearing.

Much alternate freezing and heating of the components in the area of IC501 and IC502 revealed little of help, so the wrong conclusion that the replacement chip was faulty was drawn – the machine would work for entire days with the first replacement. After tediously working around one component after another with the freezer, using a piece of card to shield adjacent components from the spray, I eventually found that filter unit FL503 was the culprit. The agents supplied an alternative type: maybe the original type has given trouble elsewhere.

And trouble elsewhere was exactly what was happening in the shuttle-search department. This had a tendency to go from play into search in either direction, but wouldn't change direction. Replacing miniature relay RY7751

Long-distance Television



Roger Bunney

The month of June 1985 was one of the most intense ever for Sporadic E reception, with openings on all days. Arabic signals were received in profusion and there have been numerous mystery signals. Without further ado herewith the log, which is extensive.

- 6/6/85 RAI (Italy) ch. IA, B; JRT (Yugoslavia) ch. E3; ORF (Austria) E2a, E3; NCT (private commercial station at Udine, North Italy) IA; EPT (Greece) E3; +PTT (Switzerland) E2, 3; MTV (Hungary) R1, 2; DFF (GDR) E4; ARD (West Germany) E2; CST (Czechoslovakia) R1; TVP (Poland) R1, 2; TSS (USSR) R1, 2; SR (Sweden) E2, 3, 4; TVE (Spain) E2, 3, 4.
- 7/6/85 TVE E2, 3; RAI IA, IB; RTP (Portugal) E2, 3; TVE-2 E2; JTV (Jordan) E3.
- 8/6/85 RAI IA, IB; TVE E3; JRT E3, 4; TVP R1; CST R1; TSS R1; SR (Sweden) E2, 3, 4; RUV (Iceland) E3, 4; NRK (Norway) E2, 4 - SR carried a programme called MTV during the day!
- 9/6/85 RAI IA, IB; TVE E2, 3, 4; TVR (Rumania) R2; TVP R1, 2; MTV R1; CST R1; TSS R1, 2; YLE (Finland) E4.
- 10/6/85 SR E2, 3; TSS R1, 2, 3, 4; NRK E2, 3; TVP R1, 2, 3; ORF E2a; CST R1; MTV R1; JRT E3, 4; RAI IA, IB; +PTT E2; TDF (France) L3; TVE E2, 3, 4; RTP E3; DR (Denmark) E3, 4.
- 11/6/85 ARD E2, 3; DR E3; +PTT E3; CST R1, 2; MTV R1; RTS (Albania) IC; JRT E3; DFF E4; TVP R1; SR E2, 3, 4; NRK E2, 3, 4; YLE E3, 4; TSS R1, 2, 3, 4; TVE E2, 3, 4; TVE-2 E2; RTP E2, 3; TVR R2; RUV E3, 4.
- 12/6/85 YLE E3, 4; TSS R2; SR E2, 3, 4; DR E3; NRK E2, 3; MTV R1; TVR R2; JRT E4; TVE E2, 3, 4; RTP E2, 3; TVE-2 E2; RAI IA, IB.
- 13/6/85 TVE E2, 3, 4; RAI IA; JRT E3, 4; NCT IA; ORF E2a; CST R1; MTV R1; TVP R1; TSS R1, 2; SR E2, 3, 4; NRK E2, 3; YLE E3, 4.
- 14/6/85 RTP E3; RAI IA, IB; JRT E3, 4; NCT IA; ORF E4; TVE E2, 3, 4; TDF L3; ARD E2; EPT E3; TVP R1; TSS R1, 2; SR E2, 3, 4; NRK E2, 3; RUV E4; CST R1, 2; MTV R1; DR E3, 4.
- 15/6/85 RAI IA, IB; ARD E2; +PTT E2; MTV R1; ORF E2a; NCT IA; JRT E3; EPT E3; TVE E2, 3, 4; RTP E3; CST R2; SR E2, 3; NRK E2, 3, 4.
- 16/6/85 ORF E2a, 3, 4; RTS IC; RAI IA, IB; JRT E3; ARD E2; TVR R2, 3, 4; CST R1, 2, 4; DFF E4; MTV R1, 2, 4; TVP R1, 2, 3; DR E3; JRT E3; TSS R1, 2, 3, 4;

- SR E2, 3, 4; NRK E2, 3, 4; TVE E2, 3, 4.
- 17/6/85 RAI IA, IB; JRT E3, 4; RTS IC; ORF E2a; TVE E2, 3, 4; CST R1, 2; TVP R1, 2, 3; TSS R1, 2, 3, 4; NRK E2; YLE E3; SR E2, 3, 4; RUV E3, 4; ARD E2.
- 18/6/85 TSS R1, 2, 3, 4; CST R1, 2; DFF E4; TVP R1, 2; DR E3; YLE E3, 4; SR E2, 3, 4; NRK E2, 3, 4; +PTT E2, 3; RUV E4; EPT E3; RAI IA, IB; TVE E2, 3; RTP E3.
- 19/6/85 TSS R1, 2; TVP R1; ARD E2, 3, 4; CST R1; RAI IA, IB; TVE E2, 3, 4; RTP E2, 3; JRT E3; NRK E3.
- 20/6/85 RAI IA; ORF E2a; EPT E3; JRT E3, 4; JTV E3; MTV R1, 2; TSS R1, 2, 3; SR E2, 3, 4; CST R1, 2; TVE E4; DFF E4.
- 21/6/85 RAI IA; TVE E2, 3, 4; RTP E2, 3; JRT E3; JTV E3; CST R1, 2; DFF E4; TSS R1; SR E2; TVP R1, 2; NRK E2, 4; also Arabic signals on chs. E2, 3, 4 carrying a similar programme.
- 22/6/85 MTV R1, 2; CST R1; ORF E2a; RAI IA, IB; SR E3; DR E3; TVE E2, 3, 4.
- 23/6/85 RAI IA, IB; RTP E3; TVE E3; JRT E3, 4; JTV E3; ORF E4; SR E3.
- 24/6/85 RAI IA, IB; TSS R1, 2; EPT E3; JRT E3; TSS R1, 2; TVP R1; TVE E2, 3; RTP E3; DR E3; SR E2, 3, 4; JTV E3; UAE E2.
- 25/6/85 DR E3; TVP R1; SR E2, 3, 4; TSS R1, 2; RAI IA.
- 26/6/85 TSS R1, 2, 3, 4; YLE E3, 4; MTV R1, 2; CST R1; TVP R1, 2; DFF E4; ORF E2a; JRT E3, 4; NRK E2, 3; SR E2, 3, 4; RAI IA, IB; TVE E2, 3, 4; EPT E3; DR E3; +PTT E2, 4; ARD E2, 3; RTP E2, 3; RUV E4.
- 27/6/85 NRK E2, 3, 4; RUV E3, 4; TVP R1; DR E3; JRT E3; RAI IA, IB; TVE E2, 4.
- 28/6/85 TVE E2, 3, 4; RAI IA, IB; +PTT E2; JRT E3; EPT E3; RTP E3; MTV R1; TSS R1, 2, 3, 4, 5; DFF E4; ARD E2; RUV E4; NRK E2, 3, 4; TVP R1, 2; YLE E3; CST R1, 2.
- 29/6/85 TSS R1, 2; TVP R1, 2; SR E3; RAI IA, IB; NCT IA; TVE E2, 3.
- 30/6/85 TVP R1, 2; CST R1, 2; ORF E2a; TSS R1, 2.
- 1/7/85 RAI IA, IB; TVE E3, 4.
- 2/7/85 TSS R1; RAI IA, IB; JRT E3, 4.
- 4/7/85 TSS R1.

Now to various points of interest. Ryn Muntjewerff (Holland) received Bulgarian TV (BT) on ch. R3, at 1410 CET on June 5th. The test card was followed by a clock with studio identification at 1429, news at 1430 and fade out at 1445. From 0825-0840 BST on June 12th Bill Cotterill (Tipton) received a coloured announcer with a programme on satellite dishes and equipment on ch. E3. Any ideas? Mike Gaskin (Caterham) logged the TSS clock at plus four hours UK time (plus one hour Moscow time) on ch. R1, at 0600 BST on June 19th. Despite the low power of the ch. L3 TDF/Canal Plus relay stations signals from several of them have been received in the UK. Mike Gaskin reports that at Caterham Band III

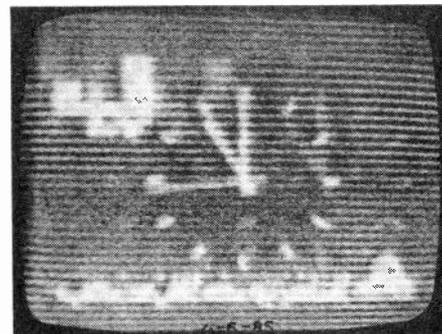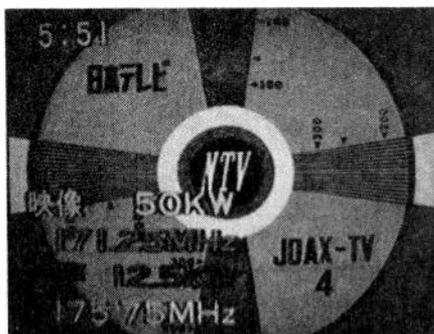

Left: NHK identification (Japan). Centre: NTV test card (Japan). Photos taken by Gordon McCrae during a recent visit. Right: Syrian clock, ch. E3, received by Ryn Muntjewerff (Holland) on May 20th at 1927 GMT.

suffers invasion from a British Telecom speaking clock: this must be the start of Band III PMR tests.

Tim Anderson (St. Leonards) logged TVE ch. E9 via meteor scatter on June 6th! At the time of writing this (on July 4th) the humid, hot weather is producing enhanced tropospheric propagation, though with thunderstorms forecast it seems unlikely that there will be reception over long distances. On several occasions during June SpE propagation occurred in the 144MHz band but there have been no reports to date of SpE activity in Band III. At 0200 GMT on June 23rd the RSGB 50MHz beacon was heard across the Atlantic in both Washington and Maine.

An extensive log covering a busy period. My thanks to the following for sending in details of their reception: Cyril Willis (Downham), Trevor Rose (Lowestoft), Dave Shirley (Hastings), Allan Beech (Dollar), Reg Roper (Torpoint), Joe Dickson (Belfast), Bill Cotterill (Tipton), Keith Chaplin (Barrow/Soar), Tony Privett (Basingstoke), Mike Gaskin (Caterham), Ian Johnson (Bromsgrove), Roger Pates (Nottingham), Iain Menzies (Aberdeen), Tim Anderson (St. Leonards), Simon Hamer (Powys) and Ryn Muntjewerff (Holland).

Frank Lumen (Denver, Colorado) paid us a two-day visit during the month. He told us that he can receive entertainment quality programmes on approximately 150 channels from nineteen 4GHz satellites via his 12ft dish!

The 50MHz Amateur Band

The Minister for Industry and Information Technology has announced that the band 50-50.5MHz is to be devoted to amateur radio. No information is available at the time of writing on permitted powers and modes of operation, though rumours suggest that Class A licence holders only will be able to use the band.

With the present excellent SpE conditions in mind, this announcement raises the question of interference to DX-TV reception in Band I. The relatively small band allocation given to amateur radio means that notching out the majority of amateur signals should be fairly easy, though ch. R1 vision at 49.75MHz could suffer excessive attenuation if a poorly made filter is used. To this end, details of a very simple ferrite toroid notch filter are given below. It provides a notch depth of 26dB: -10dB at +0.5MHz, -5dB at +1MHz, -2dB at +2MHz and -0.8dB at +3MHz. Alternatively a quarter-wave stub filter could be employed: a 3.9ft length of 75Ω, 0.8 velocity factor cable would provide attenuation at 50.4MHz. The stub filter is simply a length of coaxial cable connected at one end to the feeder between the aerial and the receiver, with the other end left open-circuit. It produces signal cancellation due to the 180° phase reversal at resonance.


The toroid notch filter is simple to make using an Ambit/Circuit T50-12 ferrite toroid. Wind ten turns of 26 s.w.g. enamelled wire around the toroid, with a centre-tap at turn five. The aerial is connected (inner coaxial cable conductor) to the centre tap and a 2-20pF or 3-30pF subminiature trimmer is connected across the coil - take the output from either end of the winding. The filter can be housed in a small diecast box with coaxial sockets: it covers the whole of Band I.

News Items

Scandinavia: Swedish TV broadcasting is to be reorganised. From March 1986 the various regional centres will opt out of the network for their own programme blocks. Use of the whole v.h.f.-f.m. band is being

SOUTH WEST AERIALS

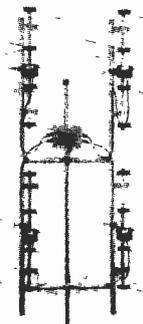**TRIAx BB QUAD GRID 16
BAY DEEP FRINGE
STACKED BOWTIE
ARRAY FOR WIDEBAND
UHF RECEPTION.**



Triax stacked bowtie aerial systems offer the most consistent overall performance for high gain wideband UHF reception. The above Quad-stack 16 bay array gives 18.1dB very high gain for extreme long distance fringe reception with an excellent front/back ratio of 28dB. The wide capture area ensures optimum signal gathering - essential for fringe and scattered signal working. The 'Grid' is available in single, twin or quad formation. Our 'UHF DX Package 1' comprises 2 'Grids', stripline stacking filter, cross support boom and clamp. The 'UHF DX Package 2' comprises 4 'Grids' stacking filter, cross support booms and clamps. South West Aerials provides both the 'know-how' and equipment for the TV/FM DXing enthusiast and for ALL types of domestic installation.

Send for a copy of our Comprehensive 1985 CATALOGUE only 60p.

TRIAx single 'Grid' UHF Wideband Aerial 12.5dB Gain (470-860MHz)	£24.10
TRIAx 'UHF DX Package 1' twin 'Grid' 8 bay Wideband UHF Array 15.3dB Gain, 470-860MHz (includes all hardware/filter etc)	£54.80
TRIAx 'UHF DX Package 2' quad 'Grid' 16 bay Wideband UHF Array 18.1dB Gain, 470-860MHz (includes all hardware/filter etc)	£84.10
TRIAx 40055 High Gain (25dB) Wideband UHF Masthead Pre-Amplifier, very low noise figure: 1.5-1.9dB	£26.25
TRIAx 50/160 Matching 240v AC Power Unit for use with above amplifier	£11.95
UNISON AR250 'offset' Aerial Rotator, complete with Control Console	£44.15

DXers! still available PHILIPS G6 VISION SELECTIVITY, SOUND SELECTIVITY & VISION GAIN MODULES, all at £2.50 each or £4.50 for 2, all in screening cans. Multi-Standard VHF/UHF Televisions and Video Recorders available (SAE please and state requirement). We are The TV/FM DXing Specialists, advice given on ALL reception problems (SAE please)

All prices inclusive of VAT and Carriage

Delivery 7-10 days

ACCESS & VISA Mail and Telephone orders welcome



SOUTH WEST AERIALS (T)

11, Kent Road, Parkstone,

Poole, Dorset, BH12 2EH. Tel: 0202 738232.



reorganised in Finland, with the Finnish first programme at the bottom of the band, followed by regional, local and Swedish language programming at the top end.

Belgium: A German language programme was transmitted for the first time on May 25th by Belgischer Rundfunk, using the identification BRF and the familiar BRT/RTB logos. There are plans for this to be a regular service from Brussels on ch. E45 at 1kW, with possibly a 1,000kW ch. E42 transmitter at Liege coming into operation at a later date. The government proposes to allow advertising on the radio/TV services. Programme interruption would not be allowed and advertising periods would not exceed eight minutes. Cable networks would be expected to comply with the regulations.

W. Germany: Radio Bremen is now using a ch. E45, 10kW e.r.p. transmitter instead of the former ch. E5 outlet in Band III.

Portugal: Because of interference caused by current transmissions it's proposed to move RTP-TV from Band I to Band III/u.h.f. when funds allow. Local radio has now been legalised and nearly 30 independent commercial local radio stations have been set up.

Tunisia: Following agreement between the Tunisian and Italian governments, RAI-1 is to be transmitted by eight high- and low-power stations in Tunisia.

Middle East: Both Jordan and Kuwait are carrying out teletext test transmissions, using the French Antiope system.

USA: The land mobile radio lobby has petitioned the FCC for greater use of Bands IV/V for mobile radio. At present chs. A14-20 are shared between TV and mobile radio in thirteen of the larger cities. The lobby want to extend this and eventually to open the whole of the 470-

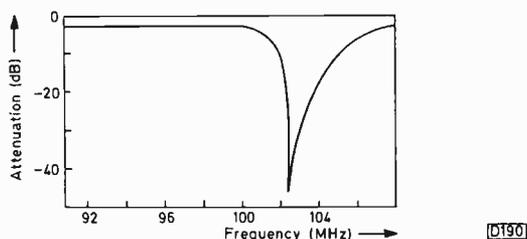
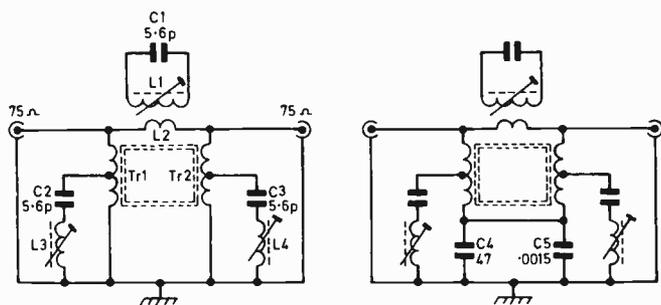


Fig. 1 (top left): Czech notch filter.
 Fig. 2 (top right): Version for use with a d.c. feed.
 Fig. 3 (above): Response of the notch filter.

806MHz band (chs. A14-69) for land mobile use, arguing that the band is under utilised by broadcasters.

Australia: SBS-TV network transmitters at Wollongong (ch. 59), North Wollongong (ch. 44), Newcastle (ch. 55), Brisbane (ch. 28), Gold Coast (ch. 61), Adelaide (ch. 28) and Adelaide Foothills (ch. 43) came into operation on June 30th. Transmitters at Perth (ch. 28) and Hobart (ch. 28) are due to open next January. There is talk of ABC-TV transmitting for 24 hours a day once the Aussat satellite becomes operational.

Publications

The 1985 edition of the IBA's *Transmitting Stations – a pocket guide* is now available, free of charge, from the Engineering Information Department, IBA, Crawley Court, Winchester, Hants SO21 2QA. Include a foolscap s.a.e. with requests.

The second edition of my DX-TV book, published by Bernard Babani (BP52), has sold out. A revised and expanded third edition is in preparation and should be available in the late autumn.

From our Correspondents . . .

Gordon McCrae of Kesh Electronics, Kesh, Fermanagh has entered the satellite TVRO field, offering a range of dishes and electronics. Following a recent visit to Japan he reports that sales of satellite TV equipment there are at present very slow, with only NHK available on a 12GHz downlink.

Mohammed Hanif is able to receive Oman chs. E7 and E10, Abu Dhabi ch. E9 and Bombay ch. E12 on a fairly regular basis in Karachi but experiences considerable interference from the local ch. E4 outlet. He would like to contact other enthusiasts in Pakistan to share experiences and develop filters: letters sent in to us will be forwarded.

Satellite TV

Transponder 9 on the Intelsat bird at 1°W is now carrying a new 4GHz TV channel, SEB TV. This AFRTS programme/entertainment feed is intended for US forces

in Italy. The signal is reported as being "very strong" – thought to be a spot beam at 30dBW, with the sound at 6.8MHz. Sky Channel has been received in the Canary Islands using a 4.5m dish. This is very good going considering the footprint and has produced considerable interest – two cable firms in Gran Canary are putting Sky on to their networks.

French Channel Allocations

In future French system L channel allocations will be denoted as L2, L3 etc. instead of F2, F3 – the frequency allocations remain the same, i.e.:

Ch.	Vision MHz	Sound MHz	Ch.	Vision MHz	Sound MHz
L2	55.75	49.25	L7	192	198.5
L3	60.5	54	L8	200	206.5
L4	63.75	57.25	L9	208	214.5
L5	176	182.5	L10	216	222.5
L6	184	190.5			

All system E (819-line) transmitters in Bands I/III have now been taken out of service. The Monaco ch. F10 system E transmitter has been replaced with a ch. L8 transmitter (50kW e.r.p. with horizontal polarisation) for the TMC-1 service.

The following Canal Plus transmitters are now in operation: Le Plessis-Robinson ch. L 3 (16W H), Clermont Ferrand ch. L4 (75W H), Mont Brian ch. L4 (70W H), Étampes ch. L4 (15W H), Le Mans ch. L5 (200kW V), Lille ch. L5 (200kW H), Toulouse/Pic du Midi ch. L5 (100kW H), Gex ch. L5 (30kW V), Le Havre ch. L5 (2kW H), Paris/Eiffel Tower ch. L6 (100kW H), Cherbourg ch. L6 (8kW H), Hyeres/Cap Benat ch. L6 (2kW H), Rouen ch. L7 (65kW H), Bordeaux ch. L8 (50kW H), Nantes ch. L9 (300kW V), Caen ch. L9 (200kW H), Lyon/Mt. Pilot ch. L10 (400kW H), Saint Raphael ch. L10 (70kW V), Saint-Etienne ch. E38 (10kW H), Paris-East ch. E53 (5kW H).

Czech Notch Filter

As previously mentioned in this column, Czech f.m. radio stations are being moved from the 68-73MHz band to 87.5-108MHz – this is part of a general move in E. Europe to Band II for f.m. radio. Unfortunately problems have arisen. Communal TV systems aligned to receive W. European Band III transmitters (low-level fringe reception) have been suffering from second harmonic interference and severe head amplifier overloading due to nearby Czech Band II transmissions which are often 70-80dB higher in level.

Various filters have been designed to overcome the problem and a particularly interesting circuit (see Fig. 1) appeared recently in the Czech magazine *Amatorsk Radio*. It provides an attenuation of 45dB over a bandwidth of 1MHz, with an insertion loss of 2dB at ± 2 MHz. The circuit consists of a lightly coupled absorption trap (L1, C1) with series acceptor circuits L3, C2 and L4, C3 tapped via a four-turn toroid at either side of the absorption trap. Fig. 2 shows a version for use where a d.c. feed to a masthead amplifier is required. All the coils are wound using 26/24 s.w.g. enamelled wire. Tr1 and Tr2 have four turns, centre tapped, on a single toroid (Cirkit FXHO balun core). L1, L3 and L4 consist of 6½ turns on a 7mm former (Maplin 351/8BA). L2 consists of a half turn positioned at the centre of L1. A single hole toroid could be used.

Service Bureau

Requests for advice in dealing with servicing problems must be accompanied by a £1.50 cheque or postal order (made out to IPC Magazines Ltd.), the query coupon and a stamped addressed envelope. We can deal with only one query at a time. We regret that we cannot supply service sheets nor answer queries over the telephone.

PHILIPS G11 CHASSIS

The trouble is field roll which is difficult to stop with the field hold control. When the picture does stop rolling there's a blank space at the bottom of the screen (three-four inches). Lock cannot be held for long.

The two 4.7 μ F electrolytics C2080 and C2072 mounted close to the TDA2600 field timebase i.c. can cause this fault. Also check for dirty field hold and height controls and intermittent contacts in the TDA2600's holder. The holder nowadays needs replacement more frequently than the chip.

THORN 3500 CHASSIS

This set gives quite a good picture but the voltage across the beam sensing resistor is 1.8V with the aerial out and 2.2V with the aerial in instead of 1.3V. By disconnecting circuits I've found that the voltage returns to normal when the line scan coils are disconnected. Are these suspect? – there doesn't seem to be anything wrong with them and they both measure 5 Ω . Also a small bending of the verticals on the right-hand side can be seen with a test pattern.

It's unlikely that the yoke is faulty – the balanced readings really exonerate them. Much more likely is short-circuit turns in the shift coil L504 which can be removed as a check. If the voltage across R907 then returns to normal and the picture centring is reasonable L504 can be left out. The bent verticals on the right may well be due to a faulty transducer – T751. Also check the associated 120 Ω resistor R773.

ITT CVC32 CHASSIS

The line output transistor blows after about four hours. Until then the picture is first rate and steady. The h.t. voltage is correct.

The problem seems to be due to excessive dissipation in the BU208. Try replacing R1101 (0.47 Ω) which is in series with its base and C56 (0.1 μ F) which decouples the supply to the line driver transistor. If this fails to do the trick it could well be that the driver transformer has short-circuit turns. The waveform at the collector of the line driver transistor would be most revealing.

SONY KV2206UB

When the on switch is pressed the standby light comes on instead of channel one. If you press the channel change or use the remote control the standby light just flickers or goes out, none of the channels coming on. Jabbing the on button a few times sometimes produces channel one, the set

then working normally. The on switch and the small make-and-break switch that should produce channel one both work correctly.

Transistor Q003 on board M2 should turn off when on is invoked from the standby mode. To turn it off a low from pin 6 of IC001 is required. If this low occurs, Q003 is suspect. If the low does not occur the chip (SAA5010) is suspect. Before condemning it, check that 5V is present at pin 24, that input data is present at pin 22, and that the oscillator is running – waveform 33 at pin 18.

ITT CVC9 CHASSIS

With the brightness and contrast controls adjusted for normal viewing the picture along the centre horizontally is pulled towards the edges, giving bowed edges and wavy verticals. Retard either control and normal linearity is restored. The width is otherwise correct.

This symptom is sometimes present in the ITT hybrid colour chassis and is to some extent inherent in the design. We've found that it occurs if the c.r.t.'s outer Aquadag coating is not properly earthed to chassis via the c.r.t. base panel. If all is well here and the beam limiter control is correctly adjusted check R426h (470 Ω) in the e.h.t. adjustment tapping arrangement then try fitting a new universal type e.h.t. tripler.

GRUNDIG CUC95 CHASSIS

The problem is that this set persistently destroys the TDA4600 chopper control i.c. There is nothing obviously wrong with the chopper circuit and the only possible clue is that the e.h.t. appears to be on the high side, going by the noises.

It's unusual for the i.c. to blow in this type of circuit – it's the chopper transistor that normally takes the brunt of any malfunctioning. We suggest you replace the BU208A chopper transistor along with the associated base feed components C631 (100 μ F) and R631 (0.68 Ω), also R646 (270k Ω) which is connected to pin 4 of the i.c. It may be that the output voltage is excessive due to the tuning capacitor C634 (0.0022 μ F, 2kV) being open-circuit, so replace this too. Before applying power, make a resistance check on the rectifier diodes fed from the chopper transformer.

THORN 9000 CHASSIS

After about half an hour the picture takes on a slight greenish fuzziness, with a definite green ghost to the right of whites. From then on the picture corrects itself every few seconds but after a few hours the fault stays.

Interchange the red and green tube drive leads (at the top of the signals panel), turn down the colour and watch

QUERY COUPON

Available until 18th September 1985.
One coupon, plus a £1.50 (inc. VAT)
cheque or postal order, must accompany EACH PROBLEM sent in accordance with the notice printed above.

TELEVISION SEPTEMBER 1985

in monochrome. If the fault remains in green the tube is probably faulty – before replacing it, check that the contacts at the tube base socket are good. If the symptom now appears in red, check the 560pF correction capacitor C175 in the green channel (the most likely suspect) then if necessary the presets R190 and R194 and transistors VT106 and VT109 in the green output stage. Check carefully for dry-joints in this area of the panel.

TEST CASE

273

Each month we provide an interesting case of television servicing to exercise your ingenuity. These are not trick questions but are based on actual practical faults.

When colour TV systems were first being considered one of the main criteria was compatibility with monochrome reception. In 1985 this factor has lost much of its significance. The ratio of monochrome to colour sets in use is now very low indeed. New large-screen monochrome sets are almost non-existent – try and find one in a retail shop! – small-screen portables accounting for such sales activity as still exists. On the servicing front too the repair of monochrome sets is becoming rare and the demand for such nostalgic hardware as PL504 and PY88 valves has virtually dried up. We had occasion recently to get out these very items however: readers who can drag themselves away from their microcomputers and s.h.f. dishes may be interested in the problem we had.

The set was an ITT model fitted with the VC200 chassis. The symptom was straightforward: lack of width – the 50cm tube was underscanned by about 3cm on each side, while a degree of ballooning was present on high-brightness scenes. This was a fairly common problem with the VC200 and similar chassis, the usual cause being a defect in the width control circuit. The preset width control was in order however – indeed the control worked to some extent. The two high-value resistors that provide the d.c. feed to the control, R159A/B, were then confidently changed – with virtually no effect on the width. In went the aforementioned PL504 and PY88 bottles, along with a PCF802 line oscillator valve for good measure. These produced a small increase in scan amplitude but it was plain that we hadn't got to the source of the fault. Off we went for some coffee and a service manual.

On our return the abnormally high temperature of the two new valves in the line output stage, after ten minutes' running, indicated that we had been barking up the wrong tree in investigating the width stabilisation loop. We decided that the problem was due to excess line output stage loading and kicked off by replacing the e.h.t.

rectifier stick – getting a sharp nip and spilling the coffee in the process. The stick having been proved innocent we went on to carefully examine other suspect components for signs of distress, checking them either by measurement or substitution. The boost capacitor C137, third harmonic tuning capacitors C135/C141, scan-correction capacitor C138 and the l.t. supply rectifier and reservoir capacitor D9/C132 were all checked, but no defects were found. The h.t. voltage at the anode of the PY88 was on the low side, but this was to be expected in view of the excessive line output stage current flowing through section R106 of the dropper resistor.

What was left other than the line output transformer? Resistance checks on the windings are seldom conclusive in such cases so a replacement was prescribed. We didn't have one in the stores (plenty of digital i.c.s and VCR head drums but no VC200 LOPTs), so we cannibalised a scrap set with a dud tube. Fitting didn't take long, though we removed the wire links to the print side of the board, beneath the transformer – these can arc to the transformer's windings. Lo and behold the trouble was still present when we switched on again!

Maybe we should have swapped the chassis over? We didn't, but fitting one other component from the scrap set got the patient going. What was it? Answer next month.

ANSWER TO TEST CASE 272 – page 582 last month –

We dropped so many clues last month that most readers must have solved the Mitsubishi CT2206TX puzzle! The set features remote control and having obtained the infra-red handset we were able to demonstrate more clearly what was going on. As with all modern remote-control systems, the analogue function commands (brightness, volume etc.) are decoded by a chip, in this case an SAA5010, which produces squarewave outputs whose mark-space ratios vary when the appropriate up/down buttons on the remote handset are operated.

The longer we dwelt on the "colour-up" button the thinner the grey lines on the display became. When we held the "colour-down" button the grey lines increased in width to a point where we had a black-and-white picture with narrow, diagonal lines of bright, locked colour superimposed. What was happening of course was that the colour up/down squarewave from the command decoder chip was finding its way to the colour decoder section of the set. The cause was failure of the colour command integrating capacitor C752 (10 μ F, 50V). Normally an RC low-pass filter integrates the squarewave output from the chip to produce a d.c. control voltage whose level depends on the mark-space ratio. With C752 open-circuit integration was not taking place and raw pulses were being passed to the colour control line.

The interference frequency is governed by the SAA5010's clock oscillator of course: this runs with no particular relationship to any other signals in the set, hence the unlocked grey bars.

Published on approximately the 22nd of each month by IPC Magazines Limited, King's Reach Tower, Stamford Street, London SE1 9LS. Filmsetting by Trutape Setting Systems, 220-228 Northdown Road, Margate, Kent. Printed in England by The Riverside Press Ltd., Thanet Way, Whitstable, Kent. Distributed by IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. Sole Agents for Australia and New Zealand – Gordon and Gotch (A/sia) Ltd.; South Africa – Central News Agency Ltd. Subscriptions: Inland £13, overseas (surface mail) £15 per annum, payable to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex RH16 3DH. "Television" is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to currency exchange fluctuations and VAT, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever. ISSN 0032-647X.

VCR's

£50



VHS System—Minimum quantity 20
This special offer ends Sat 31st Aug



KLW Ltd
& Associates

NORTH
Tritel
1043 Leeds Road
Thornbury
Roundabout
Bradford
Tel: 0274 665670

SOUTH
Westside TV Centre
29/31 West Side Centre
Luton
Tel: 0582 24177

SCOTLAND
Acorn TV
Unit 4
Peacock Cross
Industrial Estate
Burnbank Road
Hamilton
Tel: 0698 282141

LONDON
Wembley TV Centre
Unit 4 Mill Works
Fourth Way
Off South Way
Behind Wembley Stadium
Wembley
Tel: 01 903 7587

UNTESTED EX-RENTAL CTVs OVER 1500 WEEKLY

WITH THIS QUANTITY WE DO NOT
HAVE TIME TO PLAY ABOUT.

NO BUMPED TUBES
BEST SOURCE IN U.K.
COLOUR TVs FROM £3
VIDEO RECORDERS
FROM £60

TANDBURG S/S CTVs
DUAL TUNERS IDEAL FOR
EXPORT
VIDEO RECORDERS FROM £50:
SONY C5: C6: C7 & C9
PANASONIC : SHARP
FERGUSON : GRUNDIG ETC.

CALL & SEE OUR SELECTION
DELIVERY ARRANGED FOR
BULK PURCHASES
LOAD DIRECT FROM SOURCE
AT VERY KEEN PRICES

22"/26" TELETEXT VIEWDATA
COLOUR IN STOCK NOW

CASH ONLY

FRANK FORD
(TV TRADE DISPOSALS)
SCHOOL LANE
GUIDE
BLACKBURN, LANCS
TEL: 0254 64489

TELEPOST



Telegen-1

PRICE £18.35 (Inc. VAT)
*EXCEPTIONALLY LIGHT AND DURABLE
*POCKET SIZE FOR OUTSIDE SERVICE
*PP3 BATTERY POWER SOURCE
*FIVE DIFFERENT TEST PATTERNS FOR
COLOUR & MONO TV
*CROSSHATCH GRID *DOT MATRIX
*WHITE RASTER
*HORIZONTALS *VERTICALS
*3.5mm JACK SOCKET FOR OPTIONAL
P.S.U.

A lightweight, extremely portable and versatile pattern generator for black/white and colour T.V. alignment and service at the customer's home. At the turn of a switch, the generator can provide five essential test patterns for correct installation, fast checks and repairs. Pattern stability is first class and compares favourably with other more costly bulky generators only suitable for bench work. The generator is pocket size measuring 10 x 7.5 x 4 cm and weighs only 190 grams. Switched 3.5 mm jack socket allows use of external power supply with battery in situ.

Telegen-2

PRICE £34.45 (Inc. VAT)
*EXCEPTIONALLY LIGHT & DURABLE
*COMPACT 10 x 12 x 4.5 cms
*RED RASTER *GREEN RASTER
*BLUE RASTER
*COLOUR BARS
*3.5 mm JACK SOCKET FOR P.S.U.
*PROVIDES UHF SIGNAL APPROX.
CHANNEL 35



Telegen 2 is a colour bar generator at a very modest price and yet is extremely effective, stable and durable. It is the perfect compliment to Telegen 1, giving colour bars arranged in the following sequence: white, yellow, cyan, green, magenta, red, blue and black. The unit provides a signal in the UHF band approx. Channel 35 and requires a supply of 14 to 18 volts D.C.

Power Supply

A switchable power supply ideally suited to both Telegen 1 and Telegen 2.
PRICE £4.55 (Inc. VAT)

ALL ITEMS POST AND PACKING £1.44 (Inc. VAT)
All goods should be delivered within 4 working days.
32 TEMPLE STREET, WOLVERHAMPTON
WV2 4AN. TEL: (0902) 773122

CLEARANCE SALE

Massive Savings

TELEVISION

Secondhand and ex rental. Many to
clear at **£5** and **£10**.

New but faulty or marked remote control
Teletext from only **£90**.

AUDIO

Music centres, Hi-Fi, Radios, Cas-
settes, etc., etc.
Many to choose from.

VIDEOS

VHS and SONY

Several models and types at various
prices. Stocks are constantly
changing.

Please phone now for further details:

COLOURTRADE
221, Bridge St. West, Hockley, Birmingham, B19 2YU.
Telephone 021-359 0449

MANTEL

**No 1 for Quality TVs & Videos
100s of V.H.S. Videos in stock**

Large Quantities of Late Model Thorn TVs. All
with first class cabinets.

TELE-TEXT/ULTRASONIC/INFRARED/REMOTES
All at UNBEATABLE PRICES for QUANTITY & QUALITY

Also Philips G11/Pye G11/Basic/Remote/TELE-TEXT

Some examples of QUALITY working TVs

THORN 8800 ***** £25
THORN 8800 (remote) ***** £30
THORN 9000 ***** £30
THORN 9000 (remote) ***** £35
THORN 9600 ***** £40
THORN 9600 (full feature remote) *** £45

THORN 9600 TELETEXT from £75
(VARIOUS MODELS)
THORN 9900 ***** £50
THORN 9900 f/f remote ***** £60
PHILIPS G11 ***** £55

(prices quoted are based on quantity)

NO DEALER TOO LARGE OR SMALL. SINGLES SOLD

**Brand New Remote Control Hand Sets Available for the
majority of British & European TV sets.**

1000s of UNTESTED Colour TVs

I.E. DECCA 30s
GEC 2110
GRUNDIG
TANBERGS

G8s 520s-550s
Thorn 3500/8000/8500
TT
PYE, ETC.

(Many of these untested TVs just switch on)

ALL AT LOW LOW PRICES

**VAN LOADS DELIVERED DIRECT FROM SOURCE
RING FOR QUOTE**

New TV Trolley Stands **£4.95** Also Video Stands **POA**
Colour TV panels & tubes available

All prices subject to V.A.T.

CALLERS WELCOME

Export Orders Welcome for those Countries using the P.A.L. System

**419 BARLOW MOOR ROAD,
CHORLTON, MANCHESTER M21 2ER.**

TEL: 061-861 8501

TV LINE OUTPUT TRANSFORMERS

FAST RETURN OF POST SERVICE

RANK BUSH MURPHY
Z146 A640 dual std mono 7.00
Bush A792, A793
single std mono 7.00
A774 single std mono 7.00
A816 solid state mono 8.00

DECCA
MS1700 2001 2020 2401 mono 7.00
MS2404 2420 2424 mono 7.00
CS1730 1733 colour 8.00
CS1830 1835 colour 8.00
'30' series Bradford colour 9.00
80 series colour 7.00
100 series colour 7.00

FERGUSON HMV MARCONI
1600 8.00

G.E.C.
2047 to 2105 7.00
2000 to 2064 dual std mono 7.00
2147 single std 9.00

Indesit 20EGB 24EGB mono 7.00

KB - ITT
VC200 VC205 VC207 mono 8.00
CVC5 CVC7 CVC8 CVC9 col. 9.00
CVC20 series colour 7.00
CVC30 CVC32 series colour 6.50
CVC45 6.50
FT100 FT110 state p/no. 10.00
TXV80 10.00

PHILIPS
170 series dual std mono 8.00
210 300 series mono 8.00
G8 & G9 series colour 8.00
KT2 8.00
PYE 368, 169, 569, 769 mono 8.00
725-741 colour 8.00

WINDINGS
Autovox 2282 2693 8.00
Crown 14CX25 15.00
KB VC300 overwind 7.00

RANK BUSH MURPHY
T20a T22, T26 Pri & Sec 6.00
Z718 primary state 18" or 22" 6.00
Z718 EHT overwind 8.00
SONY 1320UB overwind 15.00

SOVEREIGN FARA £15.00
PLUSTRON PALLADIUM
14" colour overwind

ULTRA THORN
1690-1691 EHT overwind 5.00
1590 EHT overwind 5.00
Waltham 190 EHT overwind 6.00

**PRICES INCLUDE
P.P. & 15% VAT**

All lopts and windings are new and guaranteed

Open Mon.-Fri. 9 to 5.30 pm
Delivery by return.

**PAPWORTH
TRANSFORMERS**

80 Merton High Street,
London SW19 1BE



REWIND SERVICE
S.A.E. all enquiries
Barclaycard and
Access welcome



For orders
placed
at the
post office
Trans
cash
506 4856

01-540 3955

LONDON'S LARGEST
TELEVISION WHOLESALE...
with over 4½ thousand sq. feet

"TELEMANN"

8-10 RHODA STREET (off Bethnal Green Road)
LONDON E2. FREE CAR PARK

SPECIAL OFFER!!

Parcel of 25 Monos £1.00
Parcel of 10 Philips 22" G8 550 £15.00
Parcel of 10 Decca Bradfords £8.00
Parcel of 10 Japs Colour £20.00

LORRY LOADS DELIVERED DIRECT FROM
SUPPLIERS — NO CHARGE FOR DELIVERY!

01-739 2707 → 2 LINES ← 01-739 3123

FREE CAR PARK + NO YELLOW LINES OUTSIDE!

TUNERS + TUNERS

- ★ If you repair sets regularly — phone us today and we will dispatch immediately — no need to send cash 'up front'.
- ★ All tuners dispatched by first class post for receipt by you the next day.
- ★ All popular tuners/tuner repairs supplied 'off the shelf'.
- ★ Unusual types repaired same day as received (subject to spares availability).

TELEPART

32 Temple Street,
Wolverhampton WV2 4LJ.
Phone: (0902) 773122.

TRAINING COURSES

TELEVISION & VIDEO SERVICING

THESE FULL-TIME COURSES INCLUDE A HIGH PERCENTAGE OF COLLEGE BASED PRACTICAL WORK TO ENHANCE FUTURE EMPLOYMENT PROSPECTS

VIDEO CASSETTE RECORDER SERVICING 6 WEEKS FULL-TIME

(September 16th to October 25th)

Intensive course intended for qualified television service engineers or applicants with similar background.

The course combines the advantages of industrial and academic training and includes a high percentage of practical work.

Selected applicants will be eligible for a full grant from MSC under TOPS to cover tuition fees and maintenance.

6 MONTHS

LEC DIPLOMA

TELEVISION & VIDEO SERVICING

(Suitable for applicants with previous electronics training — e.g. BSC, HND, CGLI, B/TEC, etc.)

(Course commences on Sept. 16th)

ADDITIONAL FULL-TIME COURSES
APPROVED BY THE BUSINESS &
TECHNICIAN EDUCATION COUNCIL

(These courses commence on Sept. 16th)

2 YEAR

BTEC National Diploma (OND)

ELECTRONIC &

COMMUNICATIONS ENGINEERING

(Electronics, Computing, Television, Video, Testing & Fault Diagnosis)

15 MONTHS

BTEC National Certificate (ONC)

ELECTRONIC EQUIPMENT SERVICING

(Electronics, Television, Video Cassette Recorders, CCTV, Testing & Fault Diagnosis)

15 MONTHS

BTEC National Certificate (ONC)

COMPUTING TECHNOLOGY

(Electronics, Computing Software/Hardware, Microelectronic Testing Methods)

9 MONTHS

BTEC Higher National Certificate (HNC)

COMPUTING TECHNOLOGY & ROBOTICS

(Microprocessors, Microcomputer Fault Diagnosis, Robotics & Control Systems, CAD/CAM & CAE Principles).

OVERSEAS STUDENTS ARE CHARGED THE
SAME TUITION FEES AS UK STUDENTS

Full Prospectus from:

LONDON ELECTRONICS COLLEGE (Dept TF)
20 PENYWERN ROAD, EARLS COURT,
LONDON SW5 9SU. Tel: 01-373 8721

HITACHI VHS COLOUR CAMERAS

Mains Only Tested/
Working

VHS VIDEOS

FERGUSON

3V00, 3V22, 3V23, 3V16, 3V29,
3V30, 3V31, 3V32, 3V35

NATIONAL PANASONIC
NV8600, 8610, 2000, 7000,
370, 333, 2010

SHARP

620, 630, 640, 2300 H T/P

BETAMAX

SANYO VTC 9300, 5000, 5300

SONY C5, C6, C7, C9
and SL F1UB T/P

Also Bush, Toshiba, Hitachi and Blau Punkt

PLUS

17" 18" 20" 22" 26" Hybrid/
Solid State CTVs
Remote Control & Teletext

Discount for Quantities

Complete loads delivered from pick up point

**JOHN CARTER
(Electrical) LTD
FURNACE ROAD,
GALLOWES INN,
ILKESTON**

Phone: 0602 303124

D.I.Y. TV TUBE POLISHING

with our DIY Polishing Kit

The Kit includes everything you need to polish approx. 25* tubes to a high standard. Detailed instructions on how to do the polishing. All you require is an Electric Drill.

Kit Price £49 inc P&P and VAT. Available from Luton only.
**Depends on depth and area to be polished.*

AQUADAG COATING £17.25 per litre inc P&P and VAT. Sufficient for approx 100 tubes.
Available from Luton only.

TV TUBES FREE DELIVERY*

5% DISCOUNT ON TUBES COLLECTED FROM LUTON
Quality, High Temperature Reprocessing

TUBE SIZE	DELTA i.e. A51-110X A56-120X A66-120X	DELTA SPECIALS i.e. 510GLB22 A47-342X A67-150X	IN LINE & PIL i.e. A51-161X A51-570X A56-510X A66-510X	HITACHI IN LINE i.e. 490DVB22 510VLB22 560DZB22	SONY TRINITRON
UP TO 20"	£30	£32	£40	£44	£58
UP TO 22"	£34	£36	£42	£46	£64
UP TO 26"	£36	£38	£44	£48	£70

All tubes sold with 1 or 2 year guarantee, with optional extension by extra 2 years. Prices shown are for 12 months guarantee.

All tubes exchange glass required.

Your good, working tubes with scratches or small chips, can be **POLISHED** with our purpose built polishing equipment. From £7 per tube.

Delivery charge on colour tubes: Within 40 miles of Luton.

1 or 2 tubes £6. 3 or more tubes **FREE DELIVERY***

Nationwide delivery available, charges on application.

Please add 15% VAT to all prices. Callers welcome. Please phone first.

WELL VIEW

114-134 Midland Rd,
Luton, Beds.

Open Mon-Fri 8am-6pm, Sat 9am-1pm. Tel. 0582-410787.

Your Local Tube Stockist:

Well View, Southampton. Tel. 0703 331837.

H. K. Television, London, E.2. Tel. 01-729 1133.

Ex rental TV supplier to the trade.

West One Distributors Ltd., Gt. Missenden, Buckinghamshire.
Tel. 024 06 3609

Rushden Rentals Ltd., Rushden, Northants. Tel. 0933 314901

Daventry Rentals, Daventry, Northants. Tel. 03272 77436

Rea & Holland, Ipswich, Suffolk. Tel. 0473 827562

WANTED A56/A66-510X/540X Old glass for cash

APOLLO MANCHESTER

FAST MAIL ORDER GB 3-4 DAYS ALL AREAS PLEASE PHONE FOR COST
FREE LOCAL DELIVERY SAME DAY ● FITTING SERVICE £20

2 YR GUARANTEE - QUANTITY DISCOUNTS - PILL GLASS BOUGHT

A47 342/343X - 470 BCB22/CTB22/BGB22	£39
470-ESB22/EFB22/ERB22/FTB22	£49
A51-220X/192X	£39
A51-161X/162/163/168	£49
510-JKB22/JEB22/JDB22/JGB22/ALB22/GLB22	£49
510-VLB22 (E53), DTB22/001/RFB22/RCB22/SFB22	£49
A51-570X/580/001/210/241	£49
A56-120X/123/140/410	£39
560-DZB22(E53)/HB22/AKB22/TB22/AWB22	£49
560-ETB22/DTB22/CSB22/DMB22/DNB22	£49
A56-611X/615X	49
A66-120X/A67-120X/140/150/200/410	£39
20AX - A56-500X/510X - A66-500X/510X	£49
30AX - A56-540X - A66-540X	£53

If your tube type is not in stock we can arrange collection - rebuilding + redeliver

PLEASE PHONE BEFORE CALLING

061-799 0854. 24 hour answering service

43 Clarke Crescent, Little Hulton, Worsley, Nr Manchester M28 6XL

MAIL ORDER ADVERTISING

British Code of Advertising Practice

Advertisements in this publication are required to conform to the British Code of Advertising Practice. In respect of mail order advertisements where money is paid in advance, the code requires advertisers to fulfil orders within 28 days, unless a longer delivery period is stated. Where goods are returned undamaged within seven days, the purchaser's money must be refunded. Please retain proof of postage/despatch as this may be needed.

Mail Order Protection Scheme

If you order goods from Mail Order advertisements in this magazine and pay by post in advance of delivery, Television will consider you for compensation if the Advertiser should become insolvent or bankrupt provided:

- (1) You have not received the goods or had your money returned; and
- (2) You write to the Publisher of Television summarising the situation not earlier than 28 days from the day you sent your order and not later than two months from that day.

Please do not wait until the last moment to inform us. When you write, we will tell you how to make your claim and what evidence of payment is required. We guarantee to meet claims from readers made in accordance with the above procedure as soon as possible after the Advertiser has been declared bankrupt or insolvent.

This guarantee covers only advance payment sent in direct response to an advertisement in this magazine not for example, payment made in response to catalogues etc., received as a result of answering such advertisements. Classified advertisements are excluded.

AA117	9p	BC337	6p	BF184	20p	BFY57	25p	TIP32A	24p	2N 1131	28p	BY296	20p	7818	35p	PCL805	55p	LA-4461	180p	TBA560	100p	74LS22	17p
AA119	9p	BC338	6p	BF185	20p	BFY58	25p	TIP32C	28p	2N 1132	28p	BY298	20p	7824	35p	PFL200	85p	LA-5112	120p	TBA570	100p	74LS24	38p
AA120	9p	BC339	6p	BF186	20p	BFY59	25p	TIP33	50p	2N 1133	24p	BY299	20p	7828	35p	PL578	25p	LM301	20p	TBA800	100p	74LS24	38p
AC107	28p	BCY32	150p	BF195	5p	BLY48	85p	TIP34	50p	2N 1711	24p	BV476	90p	7912	40p	PL82	45p	LM311	35p	TBA810S	60p	74LS27	17p
AC126	17p	BCY33	150p	BF196	6p	BLY49	85p	TIP41A	22p	2N 2102	50p	BYX10	15p	7915	40p	PL83	32p	LM324	35p	TBA820	75p	74LS28	17p
AC127	15p	BCY34	150p	BF197	7p	BR100	14p	TIP41C	25p	2N 2160	300p	BYX55/350	30p	7918	40p	PL84	50p	LM325	45p	TBA820	75p	74LS30	17p
AC128K	23p	BCY35	150p	BF198	6p	BR101	14p	TIP42A	22p	2N 2184	24p	BYX70/300	30p	7924	40p	PL85	40p	LM339	40p	TBA850	100p	74LS32	17p
AC141K	30p	BCY36	150p	BF199	6p	BSX20	15p	TIP42C	25p	2N 2219	24p	BYX55/800	32p	78L05	28p	PL500	110p	LM339	40p	TBA900	100p	74LS32	17p
AC142K	30p	BCY37	150p	BF200	6p	BSX25	15p	TIP47	40p	2N 2221	23p	BYX70/300	30p	78L12	28p	PL504	95p	LM348	60p	TCA270	40p	74LS33	28p
AC176	18p	BCY72	18p	BF240	10p	BSX26	18p	TIP48	40p	2N 2222	23p	BYX70/500	32p	78L15	28p	PL508	170p	LM380	100p	TCA800	200p	74LS37	17p
AC176K	20p	BCY72	18p	BF241	10p	BSX27	18p	TIP49	40p	2N 2223	23p	BYX70/500	32p	78L18	28p	PL509	170p	LM382	100p	TCA800	200p	74LS37	17p
AC176K	20p	BCY72	18p	BF242	10p	BT106	90p	TIP51	120p	2N 2484	20p	BYX71/600	80p	78L24	28p	PL515	140p	LM382	100p	TDA1170	100p	74LS40	17p
AC176K	20p	BCY72	18p	BF243	10p	BT109	90p	TIP52	120p	2N 2646	40p	O4A7	40p	79L05	40p	PL588	48p	LM387	100p	TDA1412	60p	74LS42	39p
AC176K	20p	BCY72	18p	BF244	10p	BT116	90p	TIP53	120p	2N 2904	20p	O4A8	40p	79L12	45p	PL590A	180p	LM709DIL	30p	TDA2002	80p	74LS47	70p
AC176K	20p	BCY72	18p	BF245	10p	BT119	100p	TIP54	140p	2N 3019	28p	O4A9	40p	79L15	45p	PL590A	180p	LM709DIL	30p	TDA2002	80p	74LS47	70p
AC188	17p	BD128	35p	BF258	18p	BT120	100p	TIP105	65p	2N 2906	18p	O4A20	7p	LM309K	100p	PL590A	180p	LM741DIL	18p	TDA2020	140p	74LS51	17p
AC188K	23p	BD132	35p	BF259	18p	BT100A	110p	TIP106	65p	2N 2907	18p	O4A20	7p	LM317K	220p	PL590A	180p	AN-240P	150p	TDA2030	140p	74LS54	17p
AC188K	23p	BD132	35p	BF259	18p	BT100A	110p	TIP106	65p	2N 2907	18p	O4A20	7p	LM317K	220p	PL590A	180p	AN-240P	150p	TDA2030	140p	74LS54	17p
AC188K	23p	BD132	35p	BF259	18p	BT100A	110p	TIP106	65p	2N 2907	18p	O4A20	7p	LM317K	220p	PL590A	180p	AN-240P	150p	TDA2030	140p	74LS54	17p
AC188K	23p	BD132	35p	BF259	18p	BT100A	110p	TIP106	65p	2N 2907	18p	O4A20	7p	LM317K	220p	PL590A	180p	AN-240P	150p	TDA2030	140p	74LS54	17p
AC188K	23p	BD132	35p	BF259	18p	BT100A	110p	TIP106	65p	2N 2907	18p	O4A20	7p	LM317K	220p	PL590A	180p	AN-240P	150p	TDA2030			

WD-TV 100's of WORKING COLOUR TVs

DECCA · PHILIPS G8 & G11
BUSH · PYE s/s · ITT · THORN
8800 9000 9600 · GEC s/s
KORTING · JAPS

PRICES FROM

£15 + VAT

Videos

Always Available

Tested Tubes All sizes from

£10 + VAT

Always Scrapping Down
Decca, Philips & Thorn
- Spares Always Available

WD-TV

TV Warehouse
(former Tritel Place),
The Chestnuts,
Watling Street (A5),
Hockliffe, Bedfordshire.
(Jnct. 12 M1 - 3 miles)

Tel: 0525 210768 & 210686.

CentreVision


TEL: 0222-44754
SLOPER ROAD
LECKWITH
CARDIFF CF1 8AB
OPPOSITE CITY FOOTBALL GROUND
5 MINS FROM M4
TELEVISION/VIDEO
(VHS + BETA)
FROM £85

- ★ ITT CD752 REMOTE WORKING **£90**
- ★ PHILIPS G11 FROM **£40**
- ★ GEC STARLINE 22-20 (Remote) **£35**
- ★ PYE CHELSEA **£25**
- ★ THORN 9000 20" **£35**
- ★ DECCA 22" BLACK FRONT VERICAP **£15**
- ★ RANK T20 REMOTE **£48**
- ★ PHILIPS 550 IN 10's **£18**

PRICES SUBJECT TO VAT

OPENING HOURS:
MONDAY - FRIDAY 9.00 - 5.30
SATURDAY 9.00 - 1.00

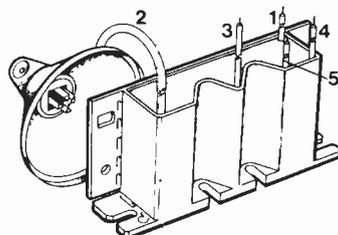UK 'Universal' TRIPLER from £5.00 inc post & VAT



BWARE IMITATIONS

- 1x10 (£5.00 each) **£50.00**
- 1x 5 (£5.50 each) **£27.50**
- 1x 3 (£5.75 each) **£17.25**
- 1x 2 (£5.95 each) **£11.90**

NB: Includes Post & VAT

1. Input 200mm. 2. Output 780mm. 3. Focus 390mm. 4. Pulse 390mm. 5. Earth 390mm.
Instruction sheet available on request

Strictly cash with order.
Goods despatched by return.
Access Barclaycard accepted

TELEPART 32 TEMPLE STREET
WOLVERHAMPTON WV2 4LJ
PHONE (0902) 773122

VIDEO HEADS MONOLITH electronic products

HIGH QUALITY UNIVERSAL VIDEO HEAD
REPLACEMENTS FOR ALL VHS AND BETAMAX
VCR MACHINES

- VHS Part No. 3HSS (5mm Centre Hole) **£29.95** PRICE
 - VHS Part No. 4HSS (15mm Centre Hole) **£29.95** EACH
 - BETAMAX Part No. PS3B **£38.95** EX.
 - REPLACEMENT KIT (17 Pieces Boxed) **£17.35** V.A.T.
- PLEASE ADD 15% V.A.T. PLUS P&P £2.00 PER ORDER
OUR FULL CATALOGUE AVAILABLE ON REQUEST.

Please allow between 14 and 28 days for delivery.

AUDIO + VIDEO HEADS - MOTORS - PARTS
Suppliers to most U.K. Distributors/Service Organizations

THE MONOLITH ELECTRONICS CO. LTD
5-7 Church Street, Crewkerne, Somerset TA18 7HR, England
Telephone Crewkerne (0460) 74321 Telex 46308 MONLTH G

VHS VIDEOS

3V16/3V22 Untested, off the pile **£85 each** (no minimum quantity)

★★★★★★

THORN 8800/9000/9600's – £25 each

★★★★★★

DECCA 80/100's & ITT S/S – £25 each

★★★★★★

PHILIPS 550's – £10 G11's – £35

★★★★★★

PYE CHELSEA'S/PHILIPS 571 etc. 18" – £15

All sets off the pile, untested and including workers. Prices based on singles. Quantity rates available. Free delivery London area, other areas negotiable. All prices exclusive VAT.

**SOUTH LONDON TELEVISION,
Mission Hall, Southey Road,
London SW19. Tel: 01-543 5437**

OSCILLOSCOPES

COSSOR CDU150. Dual Trace 35MHz Solid State. Portable 8x10cm display. With Manual **£200**
S.E. LABS SM111. Dual Trace 18MHz Solid State. Portable AC or External DC operation 8x10cm display. With Manual **£150**
ADVANCE OS250TV. Dual Trace 10MHz. With Manual **£150**
TELEQUIPMENT SS4A. Single Trace 10MHz. Solid State. With Manual **£110**
TELEQUIPMENT D43. Dual Trace 25MHz. With Manual **£110**
TELEQUIPMENT S43. Single Trace 25MHz. With Manual **£75**

PHILIPS DIGITAL MULTIMETERS

4 digit, auto ranging. Complete with batteries and leads **(p&p £5)**
TYPE PM2517E (LED) **£75**
TYPE PM2517X (LCD) **£95**

MULTIMETERS

UNBELIEVABLE – AVO 8 Mk IV and AVO 9 Mk IV, complete with batteries & leads. **FOR ONLY £65**
AVO TEST SET No 1 (Similar to Avo8 Mk3). Complete with batteries, leads & carrying case **£80**
AVO Model 7x Complete with batteries, leads & carrying case **£40**
AVO Model 73. Pocket Multimeter (Analogue) 30 ranges. Complete with batteries & leads **£25**
AVO 72 – Similar to above but no AC current range. With batteries & leads **£18**

AVO TRANSISTOR ANALYSER CT446. Suitcase style – battery operated (batteries not supplied). With Information **ONLY £20 EACH**

AVO TRANSISTOR TESTER TT169
Handheld, GO-NO GO for In-situ Testing Complete with batteries, leads & instructions. (p&p £3) **NOW ONLY £12**

MARCONI RF MILLIVOLTMETER TF2603 50KHz-1500MHz; 1mV-3V. FSD **£175**

MARCONI ELECTRONIC VOLTMETER TF2604 20Hz-1500MHz; AC/DC; Ohms AC300mV-300V. FSD **£95**

MARCONI VALVE VOLTMETER TF2600 10Hz-10MHz; 1mV-300V. FSD **£40**

NEW EQUIPMENT

HAMEG OSCILLOSCOPE 605. Dual Trace 60MHz. Delay Sweep. Component Tester **£515**
HAMEG OSCILLOSCOPE 203.5 Dual Trace 20MHz Component Tester **£270**

BLACK STAR FREQUENCY COUNTERS P&P **£4**
Meteor 100 – 100MHz **£99**
Meteor 600 – 600MHz **£126**
Meteor 1000 – 1GHz **£175**
BLACK STAR JUPITOR 500 FUNCTION GENERATOR. Sine/Square/Triangle. 0.1Hz – 500KHz. P&P **£4** **£110**

HUNG CHANG DMM 6010. 3½ digit. Hand held 28 ranges including 10 Amp AC/DC. Complete with batteries & leads. P&P **£4** **£33.50**
MULTIMETER type U4324. 33 ranges Complete with batteries and leads P&P **£4** **£16**

OSCILLOSCOPES PROBES. Switched x1; x10. P&P **£2** **£11**

ADVANCE AM/FM Signal Generator type SG63. 7.5 – 230MHz **£75**
ADVANCE AM Signal Generator type 62 150KHz – 220MHz **£35**
METRIX WOBBLULATOR type 210. 5 – 220MHz **£20**

LABGEAR COLOUR BAR GENERATOR. CM6037 **£60 P&P £2**
LABGEAR CROSSHATCH GENERATOR. CM6004. **£15 P&P £2**
LABGEAR CROSSHATCH GENERATOR. CM6038. Input 240V AC or 6V DC **£25 P&P £2**

WAYNE KERR COMPONENT BRIDGE. B521 (CT375) L 100uH – 500KHz; C 1pF – 5F; R 1 milliohm – 1000 Mohm **£35**
HUNTS CAPACITANCE ANALYSER & RESISTANCE BRIDGE type CR3B **£20 P&P £7**


LABGEAR UHF FIELD STRENGTH METER CM6016 **£50 P&P £5**
LABGEAR DEGAUSSER COILS E5186 **£10 P&P £3**

VIDEO MONITORS

KGM 9" GREEN SCREEN – USED. Good condition. **£40 each**

REBUILT TUBES?

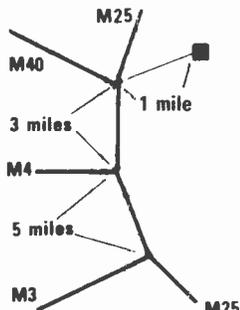Come to one of the most experienced firms in the business. We have been rebuilding cathode ray tubes for industry, broadcasting authorities, major airlines, M.O.D. universities, and, of course, the TV trade in general since the '60's.



WE ARE LOCATED IN ◀ UXBIDGE

At probably the most accessible part of S.E. England. Construction work on the Poyle/Uxbridge section of the M25 is now in progress. When completed we shall be less than 10 minutes from M3/M25 junction 2/12. M4/M25 junction 4/14. M40/M25 junction 1/15.

**LOCAL AREA MAP AND PRICE LIST
AVAILABLE ON REQUEST**

DISPLAY ELECTRONICS LTD.

UNIT 4, SWAN WHARF,
WATERLOO ROAD,
UXBRIDGE, MIDDLESEX.
UXBRIDGE (0895) 55800.

STEWART OF READING
110 WYKEHAM ROAD, READING, BERKS RG6 1PL
Telephone: 0734 68041

Callers welcome 9 a.m. to 5.30 p.m. Monday to Saturday inclusive

HOCKLEY DISCOUNT TELEVISIONS

GOOD NEWS! We have now expanded our Midlands Branch
THAT MEANS! More bargains for you & more selection

We now have **HUGE STOCKS** of TV's & **V.H.S. VIDEOS**

LORRY LOADS DELIVERED DIRECT FROM SOURCE!

Prices start from **£6.00**

Working Sets from **£12.00**

Unlimited Selection of:

Philips G8's & G11's
Pye Solid State
Pye Chelsea
G.E.C. Solid State
Rediffusion Mk. I & Mk. III

Thorn 8800, 9000
9600, TX9, TX10
Latest Hitachi
I.T.T. CVC30, CVC45
Bush T20, T22

Midlands Branch: HOCKLEY DISCOUNT TELEVISIONS, 94 Soho Hill, Hockley, Birmingham, B19 1AE.
Tel. 021-551-2233 - **Ask for Jazz**

North-East Branch: NORTHERN T.V. DISTRIBUTORS, Unit 2, Perth Court, Eleventh Avenue, Team Valley Trading Estate, Gateshead, Tyne & Wear. Tel. 091-487 5389 - **Ask for Joe**

SUMMER BARGAINS

10 BUSH 2 CHIP	£50
10 PHILIPS G8 550	£150
10 DECCA 6-BUTTON 20"	£70
10 REDIFFUSION MARK 1 REVAMP	£120
10 THORN 8000 17"	£150

ALSO BUSH T20, G11, 9000, 9600, 9800,
GEC STARLINES

PL509 £1.50, PY500 £1
ELC 1043 Tuners Ex-panel £2.50
RING FOR QUOTE

ALL + VAT

TELETRADERS

Forde Road, Brunel Industrial Estate,
Newton Abbot, Devon
Telephone: (0626) 60154

THE NO. 1 WHOLESALE IN THE SOUTH

SATELLITE RECEIVING SYSTEMS

1m and 2m Parabolic Dishes, other sizes available.

A range of other components available, eg, LNAs, Downconverters, receivers, for both 4 and 11 GHz. Complete Terminals for ECS and Intelsat, both single channel and tunable versions.

Terminals for other frequencies available.

Demonstration by appointment.

L & S Bear Electronics Ltd
Yeo Lane, Colley Lane,
Bridgwater, Somerset.

Telephone: Bridgwater (0278) 421719

TOP TWENTY VIDEO SPARES

Cassette lamp (Ferg/JVC).....	£1.80	Video head (Ferg) (state model).....	£37.50
Cassette lamp (Panasonic).....	£1.80	Video head (Panasonic) (state model).....	£39.50
Take-up clutch (Ferg).....	£6.95	Head cleaning fluid.....	£1.50
Belt kit (Sony) (state model).....	£6.50	Head cleaning sticks (each).....	50p
Belt kit (Ferg) (state model).....	£6.50	Reel Drive Pulley (Sanyo VTC5000).....	£8.88
Belt kit (Panasonic) (state model).....	£6.50	Reel Motor (Sanyo VTC5000).....	£14.20
Belt kit (Sanyo 9300).....	£6.50	Reel Motor (Sharp).....	£12.96
Rewind kit (Sony C7).....	£6.95	Overhaul kit (Ferg) (state model).....	£19.95
Reel idler (Sharp VC).....	£3.45	Overhaul kit (Sony) (state model).....	£19.95
Video head (Sony C7/C5).....	£39.50	Overhaul kit (Sharp) (state model).....	£19.95

Most spares available for Hitachi, Panasonic, Sony, Sanyo, Sharp etc.
Prices on request.

TELEVIDEO SERVICES NOTTINGHAM (0602) 226070

76 Wollaton Rd., Beeston, Nottingham

Please add 50p post & packing and then add 15% VAT to total
ALL ORDERS DESPATCHED BY RETURN OF POST

Send 22p stamp for full catalogue.

EMCO - EUROSONIC - GRUNDIG - TELETON + ALL BRITISH MAKES
ETC. ETC. ● ALL SPARES READILY AVAILABLE ●

IMMEDIATE CREDIT AVAILABLE — TRADE ONLY

If you are a trader simply phone for the part you require and we will send it - no quibble - no hold up for status check. Satisfy us over the phone that you are a trader and we will supply almost any TV component by return "off the shelf", e.g. LOPTZ - EHT trays - droppers - OSC coils - switches - cans - smoothers - I.C.'s, etc. etc.

**YOU CAN BE 95% SURE WE CAN SUPPLY ANY
TV COMPONENT BY RETURN
IF YOU NEED SPARES FAST — RING NOW!**

ACCESS AND BARCLAYCARD ACCEPTED.

Applies to U.K. only.

TELEPART (W'TON)

32 TEMPLE STREET,
WOLVERHAMPTON (0902) 773122

IRISH T.V. DEALERS

(PLEASE NOTICE)

LARGE SELECTION OF RECONDITIONED PRECISION-IN-LINE UHF-VHF COLOUR TVs, SOME WITH RE-GUN TUBES FITTED, "CABINETS RESTORED TO A1 CONDITION". PRICES START @ £60.00 VAT INCLUDED. ALSO 20" & 22" RE-GUN TUBES IN STOCK, QUANTITY DISCOUNT, DELIVERY ARRANGED.

(EXPORT SPECIALISTS)

**T.V. TRADE SALES
E.D.I. HOUSE
KYLEMORE PK. WEST
DUBLIN 10.
Tel: 01-264139**

ALSO

**T.V.T.S.
CLOVER PLACE
COLLEGE ST.
KILLARNEY.
Tel: 064-33655**

**IRISH T.V.
DEALERS & ENGINEERS**

Make extra money selling
Ex-Rental Colour TV's.

NEW LOW summer prices. Off the pile from **£30**, good working order from **£50**, all prices **VAT INCLUSIVE**. Most leading makes in stock, fresh stocks weekly. Delivery to any part of Ireland.

Export orders welcome for countries using PAL System. We also stock VHS Videos and regunned Colour tubes.

TELE SPARES LTD.

Unit 113, Elm Road,
Western Industrial Estate,
Dublin 12, Ireland.
Telephone: Dublin 521211/521756.

WORKING PANELS TO CLEAR

Sets of 4 panels £15 inc. VAT & P&P

RBM Chassis A802 - Single chip

RBM Chassis A823 - Dual chip

Decca 30 series - Mechanical tuner

Decca 30 series - Varicap tuner

Quantities of second hand valves available

Please allow 14 days for delivery

**Southpark Distributors,
Unit 4, Rubastic Road,
Southall, Middlesex.
01-574 4631, Extn. 28**

Callers Welcome

N.G.T. COLOUR TUBES

First Independent Rebuilder with
B.S.I. CERTIFICATION

DELTA - IN-LINE - PIL - BONDED YOKE
including

AXT Series, DZB series 20AX - 30AX
A56 610/67 610 series, A51 570/580/590X
A51 161X, Sony types etc.

- ★ Rebanded with new adhesives
- ★ Excellent high voltage clean-up
- ★ Accurate alignment of Gun and Yoke for optimum convergence

N.G.T. ELECTRONICS LTD.,
120 SELHURST ROAD, LONDON SE25
Phone: 01-771 3535.

25 years experience in television tube rebuilding.

The World of . .

**P+P 1 PANEL £1.50
2 PANELS OR MORE
£3.00**

"TELEPANELS"

52 Mount Pleasant Road, Chigwell, Essex. Tel: 01-729 0506.



	IF	TUNER	DECODER	G8/G9 DECODER IF COMBINED	LINE OUTPUT	POWER	CONVERG	FRAME	VIDEO	6 WAY TUNER SWITCH BANK
PHILIPS G.8	5.00	4.50	7.00	15.00	14.00	8.00	5.00	5.00		3.50
THORN 3000/3500	2.00	5.75	4.00		8.00	8.00	5.00	6.00	5.00	1.75
GEC 2110	10.00		5.00		12.00	6.00	5.00	5.00	5.00	5.00
PYE 731			10.00		18.00	10.00	7.00	8.00		4.50
BUSH Z/718	7.50	6.50	14.00		24.00	3.00	5.00	14.00		
BUSH T/20	7.50	6.50	14.00		19.00	19.00	5.00	14.00		
DECCA BRADFORD	3.00		7.00			4.00		4.00		
DECCA 80	12.00	POA	14.00		12.00	10.00		14.00		POA

POST OFF YOUR CHEQUE NOW! AND YOUR PANELS SENT BY RETURN OF POST!!!

SETS & COMPONENTS

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact COLES-HARDING & CO, 103 South Brink, Wisbech, Cambs. 0945 584188. Immediate settlement.

PANELS TESTED & GUARANTEED, 1,000s of panels for all makes and models, British/Foreign ready for despatch. If you need a panel fast, telephone Brighton 33367/33512. We'll be amazed if we haven't got what you want.

HITACHI, Mitsubishi, Panasonic, Sony, Toshiba, JVC, Sharp, Sharp fully refurbished. PEARSON TELEVISION. 0484 863489. Delivery arranged.

USED TEST EQUIPMENT. Crosshatch generators, scopes, EHT probes, marker generators, etc. at bargain prices. Send SAE for lists CIRCLE TV CO, 80 Merton High Street, London SW19 1BE, 01-540 9553.

OSCILLOSCOPE TELEQUIPMENT S54A good working order. £85, no probes. Northallerton (0609) 3406.

R.B.M. A823 PANELS. S.A.E. for details: SCHOFIELD, 28 St Albans Road, St Annes, Lancs. FY8 1TH.

THORN GEC Deccas stripped for spares. Panels, tuners from £2.50, phone for prices. WELLINGTON, Dartford 0322 337212.

GRUNDIG TELEVISIONS, telequipment oscilloscopes. Also spares. Manuals. Panel exchange. Ochrehill. 0785 814643.

QUALITY SETS FROM CORNWALL. Workers/non workers. Spares, panels, etc. Details ring 0726 81 5389.

PHILIPS G11 AND BUSH T20 regular supplies. For prices phone 01-845-2036.

WOODSDALE COMPONENTS RANK BUSH MURPHY TRANSFORMERS

Line Output

Z718 (T703A, T706A)	
New (Complete)	£19.00
Less Focus Module and Rectifier	£10.50
T20, T22 (T705A)	£11.00
T26 (T705B)	£11.00
TDA2190 Plug-in Replacement module suitable for Bush T22/T26 and any set using same device	£6.00
Switch Mode T114A	£6.00

Genuine RBM Units.

Prompt Postal Service P&P Paid.

Add 15% VAT to all prices.

DISCOUNT for QUANTITIES.

34 Field End Road, Eastcote, Pinner, Middlesex. HA5-2QT.

Tel: 01-868 5580.

N. Skehan

Agents Office. Callers by appointment only.

HALTON TV TRADE DISPOSAL

Wide range of TVs available. Working and non-working.

TRADE ONLY

(We have NO retail outlet)

St Michaels Industrial Estate, Widnes
Tel. 051 423 1577

TELEVISION

No other consumer magazine in the country can reach so effectively those readers who are wholly engaged in the television and affiliated electronic industries. They have a need to know of your products and services.

The prepaid rate for semi display setting £6.30 per single column centimetre (minimum 2.5 cms). Classified advertisements 37p per word

NORTHERN IRELAND DEALERS

COME AND SEE OUR LARGE RANGE OF
S/H COLOUR TVs AT LOWEST PRICES EVER

CONTACT:

S. M. ELECTRONICS

11 SANDHOLES ROAD, COOKSTOWN, CO. TYRONE

Telephone: Cookstown 06487/64277

Open: Mon.-Sat. 9.00 am-6.00 pm (Closed Wednesday)

EAST ANGLIA SUPPLIES

For your fully serviced colour televisions ready for sale or rent at realistic prices with free delivery (just petrol charged) anywhere for sensible sized orders.

G11s from £70 + VAT	MANY OTHER
KT3s from £85 + VAT	MAKES
K30s from £95 + VAT	REGULARLY
ITTs from £50 + VAT	STOCKED AND
Decca from £50 + VAT	CHEAPIES FROM
T20s from £50 + VAT	ONLY £25 + VAT
9000s from £35 + VAT	FULLY SERVICED.
VHS Videos.	
Ferg 3V29, 3V30	
NatPan NV2000, NV2010	

Contact John, Dave or Steve for personal friendly attention on
0223 69215 or 0353 61462



- * Britain's most reliable source of quality TVs.
- * Hundreds of working polished TVs.
- * GEC Starline
- * Decca 80
- * Decca 88
- * Decca 100
- * Pye G11
- * Thorn 8800
- * Pye 222 Series

All working and polished. These are not from major companies. A lot are from hotels and have had very little use. Excellent reliable sets for rental.

Krystal Marketing Ltd,
Breedon Cross
Storage,
Dale Road, Selly Oak,
Birmingham B29 6AQ.

Phone 021-471 3023
Telex 335540-G
Ask for Les

INDEPENDENT TELEVISION AND VIDEO COMPANY

LARGE STOCKS TO CLEAR
EVERY WEEK

COMPETITIVE PRICES

EXAMPLES:
B&W 20"-24" From £1.00

COLOUR:
Bush 1-2 I.C. £4.00
Philips 520-550, 26" £6.00
Thorn 3500 £6.00
GEC-Decca-ITT £6.00

Philips 550 22" £10.00
Pye 18"-20"-22" £10.00
GEC 20"-22" 26" £12.00
Thorn 8800-9000-9800 £15.00

Many Other Modern Sets
and VHS Videos

PHILIPS G11 - ITT - Bush T20-T22-
T26, Hitachi, Nat. Pan. - Sony
Off Pile from £40

Phone Frank: Nottingham
(0602) 864627

Unit 3

Meadow Trading Estate,
Meadow Lane,
Nottingham NG2 3HQ.

SERVICE PAGES

(minimum 12 words), box number 70p extra. All cheques, postal orders etc., to be made payable to Television, and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Dept., Television Room 2612, IPC Magazines Limited, Kings Reach Tower, Stamford Street, London SE1 9LS. (Telephone 01-261 5846).

COLOUR TV PANELS Fully Tested & Working

	IF	CDA/ Video	Decoder	LTB	Line Board	Power
GEC 2040	3.50	3.50	4.00	5.00	-	-
DECCA 13/30	3.00	-	7.00	5.00	-	4.00
BUSH A823	4.00*	-	10.00*	5.00*	2.50	4.00
THORN 8/8½	-	-	10.00	5.00	-	5.00
PYE 205	3.00	3.50	5.00	10.00	-	-
THORN 3/3½	5.00	5.00	5.00	8.00	-	10.00
G8	6.00	-	8.00	7.00	15.00	5.00

*Please specify prefix A or Z.

Please add 15% VAT to above prices, then add post + packing.
Post + Packing: 1 panel £1.50; 2 panels £2.25; 3 panels £3.00 etc.

Hybrid panels do not include valves.

Terms cash with order.

Also a vast selection of modern working and non-working TVs at low prices. Please ring for current stock.

GOLCAR T.V. SERVICES (formerly LAVITE LTD.),
Old C of E School, Church Street, Golcar, Huddersfield. Tel.: 0484 643273
Callers by appointment only.

SCREENPLAY Your Friend in the TV Business

COLOUR SETS FROM £5.00
MONOS FROM £3.00
PANELS BY POST - PRE-CALIBRATED
WORKING SETS TO ORDER

Phone Baldock 894905
SECTION 3, UNIT 4,
SERL COMPLEX,
LONDON ROAD,
BALDOCK, HERTS.

OPEN 6 DAYS 10-6.30pm/10-5pm SAT.

NORMAN ENTERPRISES LTD

Weston-Super-Mare, Avon.
Tel: 418545/413991

Colour TVs fully engineered with a special care on tubes

Hitachi 217 Remote Control ...	£95
Thorne 9000 Remote Control	£45
Pye G11	£49
Rank T20	£40
Pye Chelsea 6 Button	£35
Pye 725	£40
Pye 721	£35
Thorne 9600	£55
Thorne 9200	£55
Bush T20 Remote Control	£55

All above prices include hand sets. All plus VAT.
Ready for sale.

Phone now, limited number each month. All the above off the pile, less a 3rd

WORKING CTVs THE BEST & CHEAPEST IN LANCASHIRE

SPECIAL OFFER

Working Decca Bradford Including Black Fronts
18" 20" 22" 26" ONLY £20.00 each in 6 units

Working GEC Plastic & Wooden. All models
20" 22" 26" ONLY £22.00 each in 6 units

Working Bush 20" 22" 26"
ONLY £15.00 each

Philips G8 (520) 22" & 26"
ONLY £20.00 each

Plus many more makes & sizes in stock, inc. Tanburg, Nordmerde, Thorn.

1st COME 1st SERVED

ALL SETS TESTED & WORKING

CALL
JOHN POWNEY
TRADE TV SALES & SERVICE
Unit 31 Progress Industrial Estate,
Kirkham, nr Preston
(0772) 683392

UNTESTED PANELS FOR ALL MAKES OF TV
£1.25 per panel plus post & packing

Trent Tubes

31 RADCLIFFE ROAD, WEST BRIDGFORD, NOTTINGHAM
PHONE: (0602) 813329

ALL tubes guaranteed for 2 YEARS
EXTENDABLE TO 4 YEARS
THE QUALITY REBUILDER

All STANDARD DELTAS (A56, A66/120 etc.)
ONE PRICE £30.00

A51-161 - A51-163 £43.00

A51-A56-A66/500/510 (20AX)
One price £43.00

A56-A66/540 (30AX) £49.00

560DZB22, 560EGB22, 510VLB22 £46.00

SONY TYPES FROM £55.00

1000's more types available. VDUs, MONOs, Industrials etc.

Suppliers to Broadcasting Authorities
& National Companies

QUANTITY DISCOUNTS. All Prices + VAT + Exchange

WE SPECIALISE IN JAPANESE TYPES

STOCKISTS

Peterborough
H Donnor
0733 71809

N & S Ireland
Conway Bros
Cookstown
064 8763771

IRISH T.V. DEALERS

Brand new re-gunning plant now in operation.

— TOP CLASS TUBES —

B/W - Delta - In-Line - P.I.L.

Distributors: KELLEHER'S T.V.

Kanturk, Co. Cork

Store open 9 to 8 pm. Sunday 10-1 pm.

Tel. 029-50046 - Catalogue and Expert Advice

GEMINI TUBES

THE PRICE IS RIGHT
FOR QUALITY REBUILDS
ALL WITH 2 YEAR WARRANTY

Phone now on St. Helens 37672

Or call at Unit 3,

Delphwood Drive,

Sherdley Road Ind. Estate,

St. Helens.

TELFORD ELECTRICAL SPARES & SERVICE

GENUINE SONY SPARES	SINCLAIR COMPUTER PRODUCTS
VIDEO HEADS	Beswick FUSES
TRANSFORMERS	INSTRUMENTS
E.H.T. TRAYS	AERIAL PRODUCTS
AUDIO PRODUCTS	RESISTORS
CAPACITORS	VALVES
TUNERS Vancap & Push Button	SEMICONDUCTORS Integrated Circuit & Socket
SEMICONDUCTORS Diode	TUBES Monochrome & Regunned Colour
SOLDERING IRONS	SOLDER & ACCESSORIES

TESS SERVICE

UNIT 42,
HEATH HILL INDUSTRIAL ESTATE,
DAWLEY, TELFORD, SHROPSHIRE TF4 2RH
Telephone: Telford (0952) 501619

TRADE COUNTER OPEN 6 DAYS EACH WEEK

Television
Video
Audio
Microwave

Try Us.
We endeavour to provide a fast delivery of top quality components for the keenest price.

N.W. ELECTRONICS

25 YEARS SUPPLYING THE TRADE

**COLOUR TV'S AND VIDEOS
H.P. REPOS AND EX. RENTALS**

**ANNUAL CLEARANCE
ROCK BOTTOM PRICES**

PYE G11 EXC CAB.....	£45	BUSH 718.....	£22
BUSH T20/26 CH.....	£35	BUSH 2 CHIP.....	£8
HITACHI 191.....	£20	GRUNDIG 5010.....	£10
FERGUSON TX (NOT D.E.R. Etc.).....	£65	PYE KT3.....	£50
GEC 2010.....	£20	GEC 2213.....	£35
PYE 222.....	£25	THORN 3000.....	£7
PHILIPS 550.....	£20	GRUNDIG G415/4206	

Best Stock in the Country — over 2000 in stock (90% of our TV's Switch on)

REFURBISHED TV'S



BUSH T20/T26£50,
G11....£55, PYE KT3....£75,
Others done to order.
DISCOUNT FOR QUANTITY

VIDEO

SHARPS 7300, 8300, 9300, HITACHI, VT11
FERGUSON 3V29 (Not Ex D.E.R. etc.)
SANYO, SONY, BETA



100's PX HOOVER JUNIOR VACS

— All models in stock

full reconditions HOOVER JUNIORS (Like new) £27

**TEL. 0274 688458
UNIT 12, Wharfedale Rd
M606 Euroway Estate
Bradford**

CASH ONLY

**OPEN 6 DAYS
SAT 9-5.30**

TELEVISION

GOOD QUALITY TRADE TVs COLOUR OR MONO SUITABLE FOR SALE OR RE-RENT, WIDE CHOICE OF MAKES AND MODELS

GENERAL FACTORS

UNION STREET
DONCASTER
DN1 3AE

TEL (0302)
68416

GOOD MOTORWAY ACCESS

NOW OPEN FOR THE BEST QUALITY AND BEST PRICES IN BIRMINGHAM.

WORKING AND NON-WORKING TVS AND VIDEOS IN STOCK.

RING SINGH - 021-772 2733

WILTSGROVE LIMITED (Next Door to UNCLE'S)
128-130 Ladypool Road,
Sparkbrook,
Birmingham B12 8JA.

BRISTOL TELEVISION TRADE DISTRIBUTORS (BTDD)

4 Victoria Street
(Bristol Bridge) BS1 6BN

Ex-rental/trade in TV sets, supplier to trade only, wide range, large quantity, right price, regular supply.

Tel: (0272) 25266

T.V. SPARES, PANELS AND MANUALS PHILIPS · GRUNDIG

TELEVIEW 01-994 5537
194, Acton Lane, London W.4.

TUBES

£29.00 INCLUSIVE, REGUNS TWO YEAR GUARANTEE, QUANTITY DISCOUNTS SIX MONTH GUARANTEE SLIGHTLY USED

£14.50 A56-120 A56-140 A51-110 A49-191 A47-342 or 343 A44-270-1 A66-120 A66-140 (410) A67-120 (All 26" add £5)

No need to spend £5 returning old delta tube. Slightly used in-line tubes from £29. Six months guarantee.

IN-LINE 1 YEAR GUARANTEE TOSHIBA NEW SI-110 47-342 47-343
51-161 **£45** inclusive
51-510 **£29** inclusive
51-570 Special discounts for more than 2
56-500

SPECIAL OFFER MULLARD **£64** inclusive
56-540
66-500

SONY £66 inclusive
330AB · 470 KLB · FWB · DLB · KTB · KLB 520 HB · TB · KB · LB · NB · MB · 570 HB EB · DB · GB · JB
MOST IN STOCK, IMMEDIATE DELIVERY

HITACHI

490DKB22 **£34**
560DZB22 **£49**
Plus 490 DVB 510 or 560 VLB

Philips G11s

Panels from £10.00, Breaking for spares, Push button units, Tube bases for sale or exchange etc All good working order.

RADIO and TELEVISION SERVICING BOOKS

(MacDonalds). New 74/75 £15; 75/76, 76/77, 77/78, 78/79, 79/80, 80/81, 81/82, 82/83, 83/84 £22.50.

FREE DELIVERY

Except Tubes £5 each. All prices are inclusive

U-VIEW

29, Warmsworth Road, Doncaster,
Yorkshire DN4 0RP. Tel: 0302 855017.
Callers ring first, open every day including Sunday
1/2 a mile from A1

COLOUR BAR GENERATOR

Pal Colour Generator with 11 patterns plus sound. Grey scale, Colour Bars, Red, Green & Blue Raster, Cross-hatch, Dots, Chequer Board, Black Raster, White Raster, Half Black & White, Mains Powered. **£75.90**

OUTPUTS PROVIDED
UHF OUTPUT
VIDEO OUTPUT
SOUND OUTPUT
LINE PULSE
FIELD PULSE



Same as above plus RGB output **£81.50**
Line Output Transformer Tester **£11.50**
BW Generator, Crosshatch, Peak White, Dots, Half Black & White and Grey Scale UHF output **£18.50**
Same as above but with Video Output **£20.50**
Capacitance Meter measures 10pF to 1µF complete with moving coil meter **£14.75**
Car Alarm with built in Siren **£20.50**
S.A.E. for details. - Prices include P&P & VAT.

C.M.J. ELECTRONICS

Unit 8, 16 Union Mill Street, Horseley Fields,
Wolverhampton WV1 3DW.
Tel: (0902) 871563

EX-RENTAL

TV G11 } £30 PLUS VIDEO Sony C6 } £65
T22 } MANY Sanyo 5000 }
T26 } MORE VHS }

ALL UNTESTED MIN 5's

TRADE TV - 0842 23292

T.V PANELS

REPAIR EXCHANGE SALES SERVICE
PRICES FOR REP. EXC. AS FOLLOWS

Chassis	IF Decoder	Line Scan	Power Supply	Frame
Philips G11	18	16	20	18
Bush T20	X	12	16	15
Bush T26	X	16	18	15
Bush 718	X	12	18	X

All panels are repaired and aligned according to rank std.

Ring for prices to buy panels. Prices shown inclusive of postage, etc.

All panels guaranteed for 3 months.

T. K. PANELS SERVICE

31 Bronte Paths, Stevenage (0438) 61567

Thorn 3000/3500
Thorn 9000
UNIVERSAL
1 year guarantee

TRIPLERS
£4.95 inc. p&p

The UNIVERSAL TRIPLER can be used in most G.E.C., I.T.T., Pye, Rank, Decca & Continental sets.

WING ELECTRONICS

15 Waylands, off Tudor Rd, Hayes End, Middlesex

ONE MONTH ONLY OFFER

INTERTEL TRADE TVs

ALL SOLID STATES

- ONE PRICE ONLY

£16.00 + VAT
(Off Pile Price)

DIRECT FROM SOURCE DELIVERIES ARRANGED DISCOUNTS ON QUANTITY MOST MAKES AVAILABLE

INTERTEL

UNIT 27

WHESOE ROAD
DARLINGTON
CO DURHAM

HOT LINE
DARLINGTON
0325
486896

VIDEO & HI-FI ELECTRONICS

379 EDGWARE ROAD
LONDON W2
TEL. 01-258 0328

ALL VHS PARTS AVAILABLE
EXAMPLES:

VIDEG HEADS

JVC, Ferguson, Akai, Saba, Telefunken £35.00
Sony (Betamax) £45.00
National Panasonic £45.00

INTEGRATED CIRCUITS

UPC 1365C £7.30
UPD 553C £14.75
UPD 552C £10.56
HA 11711 £14.20

Many other parts available. Send SAE for list.
ALL PRICES INCLUSIVE OF VAT
ADD £2.00 FOR P&P

STARLITE ELECTRONICS

NOW MOVED TO:
WILLOWS FARM,
A13 RAINHAM, ESSEX.
Rainham 23225 also
Hornchurch 50238.

- TV TUBES -

2 year guarantee

Most types available

Japanese including Sony

Ex-Rental TVs from £15.00
Untested Panels £4.00

VIDEO

EX RENTAL VHS VIDEOS

★ ★ ★

100's IN STOCK

★ ★ ★

CONTACT MICK ON 021-772 1591

WANTED

WANTED Copies of Television magazine. Top prices paid. 041-423 1600 anytime.

WANTED. For new small business, regular supplies of good ex-rental videos - colour TVs, trade repair enquiries welcome. Doncaster 0302 744330.

WANTED. HAMEG HM 203, 20 MHz, dual trace, oscilloscope in good condition. Telephone Orpington 39260.

WANTED. EX RENTAL colour TVs. Any quantity. Prompt collection, cash paid. Sheffield 754865.

SERVICE MANUAL or circuit for Heathkit 10-12U oscilloscope. 041-424 0435.

BUSINESS FOR SALE

RETIREMENT

Opportunity for self motivated TV engineer to own his established business by the sea. Excellent premises, location and potential try.

£8,000 all in.

SEATON (0297) 20201.

VIDEO TV. HI FI SHOP NW6

+ Stock Rooms/Workshop.
T/O exceeding £115,000 p.a. (£4,000 from repair).
Main dealership.

12 years new lease. Rent £2,300 p.a.
PRICE £25,000 FOR QUICK SALE

Please reply to:
TV BOX 197

TV - VIDEO - AUDIO SALES & SERVICE North Humberside

Double fronted shop, spacious luxury three bedroomed accommodation.
UNOPPOSED DEALERSHIP -
GREAT POTENTIAL

£46,000 freehold + S.A.V. if required.
Offers considered.

Details: Box No. TV 198

RETAIL BUSINESS FOR SALE

Bournemouth: established sixteen years: excellent retail outlet producing substantial profits. Situated busy main road and comprising large showroom and workshops with spacious luxury 3 bedroom flat over. Immaculate property. Retirement sale.

FREEHOLD AT

£95,000

0202 - 35653

TELEVISION

FOR SALE



Sabaco

For a
great deal!

VAN LOAD DIRECT FROM SOURCES

ALL SETS OFF THE PILE

Most makes/sizes available

e.g. Black faced Decca £10,
Thorn 8800/9000 etc. £20,
B/W £1.

All above offers minimum
quantity of 10 sets or more.

ALL PRICES SUBJECT TO
VAT & AVAILABILITY.

VHS VIDEOS

with guarantee


in good

working order.

Ferguson 3V22

from £100. Any

quantity

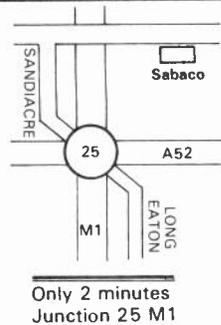

Sabaco
Saba House,
46A Derby Road, Sandiacre,
Nottingham.

Open 6 days a week
9.30 a.m. - 5.45 p.m.

Telephone: (0602) 397555

DEVONICS

Quality Rebuilt Tubes

2 YEAR WARRANTY

In line from £41

Deltas from £30

UNUSED TUBES ex stock
complete with scan coils

370 KRB 22

A51 JAR00X02

560 DYB 22

£40 ea + £5 carr + VAT

2A BARTON HILL ROAD,
TORQUAY TQ2 8JH

0803 - 33035

UNIVERSAL AVOMETER AVO 8, excellent inclusive case, battery leads £85.50. 01-843 9942.

RETAILER HAS GOOD QUALITY part exchange colour televisions to clear. 0494 814317.

NEW 3 - Saticon tubes, Hitachi H. 4105 current price £268 will accept £168 ono. Phone 0534 72626 day, 0534 62733 evening.

ADVANCE OS3000 oscilloscope, dual beam, delayed time base, ext. trigger, reliable instrument £300. 01-204 2752.

WORKING COLOUR/B&W Televisions, also panels, good prices. FOUR ACES ELECTRONICS, 74 Old Oak Comon Lane, London W3. 01-749 9338.

SERVICE SHEETS

Alba, Cossor, Baird, GEC,
Defiant, Echo, Ferguson, Philips etc. etc.

30,000 SERVICE SHEETS IN STOCK ALL AT £3.00 + SAE
ALSO COLOUR MANUALS AVAILABLE AT £6.00 EACH

TV Sheets, Black and White, also Radiograms, Record Players, Music Centres. Japanese models in stock. Circuit diagrams only. Also Tape Recorders etc. Car radios also in stock. Radio Mobile, Sharps etc., Philips, Car Radios Service sheets £3 + SAE. Manuals £6 + SAE. Old radios AM/FM and Valves. Ferguson, Pye, Please forward s.a.e. Send cheque or P.O. Sanyo. Mono C. CARANNA, 71 BEAUFORT PARK, LONDON NW11 6BX. Old transistors, TV.

TELEVISION SERVICE SHEET SPECIALISTS

Thousands of British, European and Japanese models in stock.

Colour £2.00 Mono £1.50

Manual prices on request.

All our prices include post and packing costs.

Send stamped envelope for free catalogue and enquiries.

SANDHURST TV SERVICES (MAIL ORDER)

49C Yorktown Road, Sandhurst, Camberley, Surrey GU17 7AG

SERVICE PAGES

BELL'S TELEVISION SERVICES for service sheets on Radio, TV, etc. £1.50 plus S.A.E. Service manuals on colour TV and Video Recorders, prices on request. S.A.E. with enquiries to B.T.S., 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 55885.

METERS

AVON METERS

We buy and sell and repair TV coinmeter. Reasonable prices, one year guarantee.

213 Cheltenham Road,
Redland, Bristol.
0272-425281

METERS. Reconditioned 10p/50p available from stock. Contact THE METER CO. (Poole) LTD. (0202) 683498.

BOOKS AND PUBLICATIONS

"RADIO AND TELEVISION SERVICING" books, new editions for the last 6 years always in stock. Prices on request. BELLS TELEVISION SERVICES, 190 Kings Road, Harrogate, N. Yorkshire. Tel. 0423 55885.

MACDONALDS R & TV BOOKS. New 74/75 £15. 75/76, 76/77, 77/78, 78/79, 79/80, 80/81, 81/82, 82/83, 83/84, 85/86 £22.50. Free delivery. U-VIEW, 29 Warmsworth Road, Doncaster. 0302 855017.

REPAIR SERVICE

PRINTED PANEL REPAIR SERVICE

Printed panels and remote control handsets repaired. Most makes and models serviced.

RING 0934 418545
for Price List or Quotation.

MISCELLANEOUS

GET SHARP PARTS FAST

TELEPHONE

0734 - 876444

TELEX 848953

SHARP

Main U.K. Spare Parts Distributor

Audio-TV-Video ★ Microwave ★ Photo-copier ★ Typewriter

All U.K. model spares available. Same day despatch of orders received before 1pm.

Microwave, photocopier and typewriter spares to authorised service dealers/centres only.

WILLOW VALE ELECTRONICS LTD.,
11 Arkwright Road, Reading, Berks.



The Theory and Practice of PAL Colour Television in three important Video Cassette Programmes

Part 1.

The Colour Signal

Part 2.

The Receiver Decoder

Part 3.

Receiver Installation



VHS★★★V2000★★★

BETAMAX★★★UMATIC

For full details telephone

0253 725499 (Day)

0253 712769 (Night)

Or send for precise details

FLINTDOWN CHANNEL 5

339 CLIFTON DRIVE SOUTH,

LYTHAM ST ANNES FY8 1LP

(enclosing this advert)

NAME

ADDRESS

TEL:

SOLE SUPPLIERS TV/VIDEO Repair manuals/circuits, 1000s s/manuals supplied by return. S/sheets £2.50 except CTV/m.centres/stereos £3.50. LSAE with every order/query please brings free price list/magazine inc s/sheet - or phone 0698 884585 (883334 outside business hours) TIST, 76 Church Street, Larkhall, Lanarkshire.

PHILIPS G8 Tested panel clearance. Power £5. I.F. £4.75. Tuner £3. Chroma £6.50. Signal £15. 520 Triplers £1.75. Focus £1.25. Control knobs 5p. Mains switch/controls unit £2.25. Thorn 3000 IF 2-50. Un-tested power £4.50. S.A.E. for list of other parts and service manuals. MR McHUGH, 16 Copperkins Road, Hednesford, Staffs WS12 5NW.

SATELLITE TV

The difficult part made easy!

LNB

(Block Down Converter)

i/p 3.7-4.2 GHz

o/p (IF) 400-900 MHz

Send SAE for details to:

OXMANN LTD.

West End Industrial Estate,


West End, Witney,

Oxon OX8 6UA.

BURGLAR ALARM EQUIPMENT. Latest discount catalogue out now. Phone C.W.A.S. ALARM 0274 731532.

NICAD CELLS AA/HP7 500MA/Hr, pack of 4 £1.80 4 pks £6.00 Ex-equip tested & guaranteed. NICAD CHARGER + 4 AA's and holder £6.00. CROYDON DISCOUNT ELECTRONICS, 40 Lower Addiscombe Road, Croydon CR0 6AA.

AERIALS

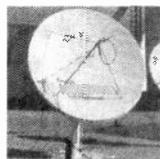

Euro-Sat

Parabolic Dish Antennas

(Parent company est. in

TV communications since 1969)

SATELLITE TVRO ANTENNAS

TOP QUALITY SOLID

GLASSFIBRE DISH ANTENNAS

1M. DIA 11-12.4 GHZ BANDS £77.00

1.2M. DIA 11-12.4 GHZ BANDS £83.00

2M. DIA 11-12.4 GHZ BANDS £215.10

3M. DIA 11-12.4 GHZ BANDS £437.00

All dishes come complete with feed support

Trade & Export Enquiries Welcome

Prices do not include delivery

Euro-Sat

107 Cross Street, Sale, Cheshire, England.

Tel. 061-437 2631 061-881 4249

AERIAL BOOSTERS

B45H/G-UHF TV next to the set fitting, gain about 20db, PP3 battery or 8V to 14V/working. Price £8.70. P&P 30p.

UHF TV BOOSTER MODULE. PCB ready made up to cover the complete UHF TV band. Gain 10db, noise 1.9db. 8V to 14V/W. Price £2.50. P&P 30p.

SET/TOP AERIAL and matching aerial booster (trebles and gain). Price £8.70. P&P 50p.

Video Transmitters. This will transmit good quality pictures and sound more than 30ft (SAE for 1969 details)

ELECTRONIC MAILORDER,

62 Bridge Street, Ramsbottom,

Lancashire, BL0 9AG.

Tel: Ramsbottom (070 682) 3036.

S.A.E. for leaflets. Access/Visa Welcome.

CLEARVIEW AERIALS

Tunable masthead amplifiers for FM and Band 3 (mostest) gain 30dB. NF 0, 7dB and UHF incl. amateur band gain 30dB NF. 1, 6dB. 15dB and 26dB masthead ampl. WB, grouped NF 2dB splitters, combiners, notchfilters, diplexers etc. Trade and retail.

Send large SAE for our comprehensive catalogue

CLEARVIEW AERIALS,

173 Kings Road,

Kingston Upon Thames, Surrey.

SATELLITE T.V. RECEPTION EQUIPMENT

Throughout Ireland

2m G.R.P. dish with feed support and polar mount. 11GHz block downconverters and indoor receivers. PAL/SECAM colour T.V.'s with in-built receiver.

KESH ELECTRICS LTD.

Main St., Kesh, Co. Fermanagh, N. Ireland

Phone Kesh (03656) 31449.

EVERYTHING NECESSARY for multi-outlet and high gain installations. Cables, outlets, splitters, channelpass filters, diplexers, masthead amplifiers, distribution amplifiers, brackets, masts, aerials, etc. Use trade gear and save pounds. Catalogue 50p (refundable). Professional advice. WRIGHTS AERIALS, 43 Greaves Sike Lane, Micklebring, Rotherham.

SERVICE PAGES SERVICE PAGES
PLEASE MENTION TELEVISION WHEN
REPLYING TO ADVERTISEMENTS
SERVICE PAGES SERVICE PAGES

<p>TDA2008 £2 Philips small stereo headphones £4 Stereo Philips headphones Electret N6325 £13 SN76545N (Tynr IC) £3.50 TCEP100 4000 Thorn i.c. £1.75 Rank UHF 4 push button tuner £4 GIRC power supply PC743B £10 Rank front panel Z950 £5 Power panel 8.500 Thorn £5 Fidelity mains switch & lead and filter panel £1 Fidelity mono lopt with diode FBS1245AE £3 6 TAG print mains switch PRE111 1983 IIT £7.50 T134A Lopt panel £10 Rank T601A tuner on panel £6 Scan control panel Z544 £3 Rank Z582 IF £3 Rank convergence Z910 £3 GEC IF tuner panel PC786B £12.50 ML 232 I.C. on panel touch unit Fidelity £3 Hitachi power panel PC036A £1 Rank IF 742 £3 Rank decoder Board MTS 2001 Tuner & IF £12. Z733 Rank mains in put-panel £1 G11 Chroma Can 3113 108 25300 £3 20AX Line In coil 50p GEC switch mode trans 20AX ITT CVC20 etc mains switch 60p ITT 2,800 mains remote switch 50p 2110 GEC Power Panel £8.00 Line of frame panels GEC 20AX £10.00 GEC 20 AX £10.00 Transductor IIT CVC40 Push Button Unit & Mains Switch £8</p>		<p>1A/1600V 10p 2 amp bridge rec. wire end 15p CV 8617 10p Y 716 10p Y 729 10p Y 730 10p Y 737: 6A/1KV 20p Y 860 30p Y 933 5p Y 969 50p Y 997 30p Min 12 volt Relays 75p R 1038 40p R 1039 40p R 2010B 80p R 2019 40p R 2210 60p R 2257 60p R 2265 50p R 2305 50p R 2306 50p R 2322/2323 pair 80p R 2323 15p R 2396 50p R 2461 80p R 2030 50p R 2443=BD124 40p R2737 40p R2738=TP41 30p R2775=TP41c 30p R3129=TP47 40p S 2008b 80p 2SD898B £1</p>		<p>G11 condenser £1.75 300M + 700 320V £1.80 200 + 100 + 100 + 50 300V 50p 150 + 200 + 250M 300V 50p Chassis complete £3.50 Computer Transformer 20v/2.25A; 20v/1.5A; 17/5A; 19/5A; 28/0.5A £3 Mains ViewData Torroids £3.75 240V/240v/6V/4 amp/6v 500m/a in/out 40p Mains trans 240/12v-0-12v 2 amp £3.50</p>		<p>HITACHI CPT2225 CHASSIS WITH TELETEX £30 10 Mixed TV & radio speakers £4 Philips car radio speaker door pair £7 2x Hi-Fi Philips car tune up tweeter EN8320 £10 ITT CVC45 8 way resistor unit for v/cap £3 4700/10v x 10 50p 68/16 x 10 50p 150/16 x 10 50p 47/25 x 10 50p 220/25 x 10 50p 1/250 x 10 50p G8 Speaker £1 8000/30v 50p 470/40v x 10 50p 22/10v x 10 50p 100/35v 70p 400/35v 70p .47/50v 25p 1/600v 25p .022/1kv 10p VIEW DATA PANELS NEW £3</p>		<p>MODEM Line Terminal Unit VM6501 £6 Designed to work at 1200/75 or 1200/1200. Diagram and Connection Data Supplies Indicator Tube ITT 58705 £1 8 Seg Display FND500 Mullard 12.5V/170 Mc/s 45 watts 20p BLW60C Mullard Broadband R.F. power modules UHF: BG722E £10.00 PT4236C, PT8706C, PT9783 £3 ITT Micro Phone M5 50p with switch Sub-min Relay low voltage 50p Mains relay coil 230v 30p Philp PP3 batteries 10 for £3 12v battery holders A.A. 50p 1.5 battery T/V 12v 2 pin battery lead 30p</p>	
<p>Rank Panels Z904 18" Line Panel £10 Z905B Decoder £10 Z736 Tuner I.F. £10 A805 Conv. 7/8 £2 T136A Scan Drive £10 Z780 Line O/P £10 Z968 £10 Z582 I.F. Panel £5</p>		<p>STR454 £2 2SC940 £1 BU 105/04 80p BU 108 £1 BU 124 50p BU 126 80p BU 181a 65p BU 204 70p BU 205 £1 BU 206 £1 BU 207 £1 BU 208 80p BU 208A £1.10 BU 208D 90p BU 222 £1 BU 326 £1 BU 407 60p BU 426V 60p BU 500 £1.10 BU 508A £1.20 BU 526 75p BU 807 £1 BU 824 50p BUW 84 30p BYW 2048-9 £1</p>		<p>Voltage Regulators +5V/UA78PO55C 30p -5V/LM79MO5CP 25p -8V/79M08C 30p +6V/78M06C 30p +10v/78LA10 20p LM 337 30p LM 342/18 30p LM 340T 5.0 50p +12V/LM 340T12 50p +15V/78M15 15p +18V/MC78M18 20p +24V/78M24 30p MC 7724cp 40p MC 7824 40p</p>		<p>Various Tools and Accessories T/V V/Aerial 3000 or 750 £1.50 L.C.D. clock display with alarm + D/P push mains switch 20p each Mains lead & two pin socket for radio cassette 35p 3 Video Leads £1.00 Xcelitr cutter £3.90 T/V loop aerial 75p Radio Telescopic Aerial £1.00 Philips Neon Lamps for TV sets 5p Freeze £1.20 Foam Cleaner £1.20 Contact Cleaner £1.20 Cans of Anti Static, Degrease Cleaner and Anti Corona All at £1.20 Push Button Mains 75p Lorlin Full Remote Relay Switch fit most T/V sets, mains 4 tag, 2 tag 12 volt £1.00 Mains timer, 13 amp — up to 2 hours; easy to use, plugs into socket £3.00 Sellotape PVC Electric Insulation 50mm x 20M 70p Screen locking agent, large can £1.50 20 GEC Service Manuals £5.00 Red E.H.T. LAED and Anode Cap £1.00 10 x G11 Cap 470/250 £15.00 Weller solder iron 15 watt/25 watt £5.00 2 way baby alarm/intercom with long leads £5 Philips universal battery tester/charger, fuse/bulb tester To Clear £4.50 12V Nicad pack. "AA" £6.00 Hitachi 7.2v/1.8A Nicad pack £7.00 Hitachi TP 007 Battery pack 7.2v/1.6A £6 Hitachi Silver Oxide Battery G13 UCC357 IEC SR44 1.5V 60p 70ML Silicone Sealer (clear) £1 100 Coax Plugs £12.00 De-solder pump + 2 nozzles £5.20 Plastic box for i.c.s. 6"x3"x1/2" 50p Can of handy oil 'mobil' 40p Flat Red LED 12p 500gm 60/40 solder reel £7 Clearweld glue pack 30p Dual v/u meter -20 + 10db £1 K30 thermistor 232266298009 75p GEC Mains Power Supply R.E.G. £3.00 1Kg reel of solder £8.00</p>			
<p>Rank Power Panel 300+300m with diodes degaussing £3 BA 301 £1 TA 4127 £1 HD 3884 2A23 £3 TA 4184 £1 TA 2125 £1 TA 4190 £1 TA 4138 £1 TA 4196 £1 TA 4174 £1 TA 4139 £1 TA 4198 £1 TA 4167 £1 TA 4199 £1 BA 546 £1 BA 328 £1 TA 4176 £1 TA 4145 £1 TA 4191 £1 HA 11710 £1 TA 4188 £1 TA 4197 £1 TA 4183 £1 TA 4197 £1 TA 4183 £1 TA 4195 £1 TA 4175 £1 TA 4177 £1 TA 4192 £1 TA 4146 £1</p>		<p>TIC 106a 30p TIC 116m 40p TIC 116n/Y 1003 35p TIC 126N 40p TIC 206m 30p TIC 225S 40p TIC 226E 40p TIC 226m 30p TIC 236m 30p TICV 106D 10p (C1092 case 2A/400V) TIP 29 20p TIP 30 35p TIP 30A 35p TIP 30B 40p TIP 30C 45p TIP 31 30p TIP 32 25p TIP 33B 50p TIP 33C 70p TIP 34A 50p TIP 34B 60p TIP 34C 70p TIP 35B 50p TIP 35C 70p TIP 35D 80p TIP 36 50p TIP 36C 70p TIP 41B 40p TIP 41D 40p TIP 42/BRC 6109 40p TIP 48 40p TIP 49 30p TIP 57 30p TIP 100 30p TIP 102 30p TIP 115 50p TIP 117 50p TIP 120 35p TIP 125 35p TIP 130 30p TIP 131 25p TIP 136 30p TIP 140 50p TIP 640 50p TIP 2955 35p T 6032 30p T 6036 40p T 6040 40p T 6047 40p T 6049 40p T 6052 40p T 9004 40p T 9005 40p</p>		<p>TTS 90 10p TTS 91 20p TTS 92 20p TTS 93 20p U 19885 40p U 3832 15p U 3845 15p MR 508 10p MR 501 10p BCW 71R 30p BYF 1202 10p BYF 1204 10p BYF 3126 40p BYF 3214 40p BYX 10 6p BYX 36/600 25p BYX 38/300 75p BYX49/600R 75p BYX 55/350 10p BYX 55/600 (Bead) 20p BYX 71/350 50p BYX 71/600 50p BYX 72/300 50p BYX 36/600 50p BYV 95B 10p BVV 95C 12p BYZ 106 10p BPW 41 15p BYW 56 2A/1000v G11 8p BZU 15/24 54p BZY 93/75 50p BZV 15/18 30p BZV 15/30 30p BZW 70c6v2 10p BZX 79.3v 10p</p>		<p>75R/25 Watt 25p 18R/11 Watt 25p Front End Music Center. VHF/ M/W/LW 13"x3 1/2" £3 Output Stage for music center £5 SONY 1400KV Chroma Panel £6 SONY 1400KV Tuner unit £3.50 SONY 1400KV Touch button unit £3.50 12 Volt Mains Trans 500M/A £1.00 18V or 12 Volt Mains Trans 500M/A 75p Texas Viewdata Decoder VDP 12/8/1 Issue 3 with all IC's £10.00</p>			
<p>The Service Engineers Guide to Teletex £1.50 Teletex Colour Training Manual £3 Mains Trans C. Core 240v 4v+4v 4v04v 2AMP 12v Lamp £2 Mullard split diode AT2076/80 £6 4 Types Fidelity front panels with i.c. & pats £2 each Amstrad TV chassis Complete damaged print £5 + £5 post BB 103 10p BB 105A x 12 £1 BB 105B x 12 £1 BB 105G x 12 £1 BB 121a 10p 47 10p each</p>		<p>Bush thyristor RCA 76122 £1 Transformer 240v/20v-500Ma 75p Chassis type Transformer 240v/12 Volts 500m/a 75p CVC 20 tube base £2 Tube Base Rank & G11 6v-9v-13v tape motor 75p Swiss made 250rpm/240V motor very small 75p Infra red led LD57CA 15p Mono scan coil £3 G 8 transductor £1.25 AT 4041/41 transductor £1 VHF 3 Transistor rotary tuner DX-TV £1 15K-20 turn pots 20p Thorn panel 6x100 pot + changover switch (Irish) 50p Battery converter TA 75 for colour TV. 12/24v Thorn 3787 £6 Thorn 3500 2A cut out 50p</p>		<p>SPECIAL OFFER Decca-ITT etc. FEO4/U250AC/4 Mains filters (grey type) x 4 80p</p>		<p>Quantity Reductions BY204/4 25 for £1.00 BY206 25 for £1.00 W005 bridge 20 for £2 KT3 touch button black 6 for £1 G11 touch button red 6 for £1 K30 full remote Dawer Ass with 3 I.C. £7.00 K30 VHF. UHF Dawer Ass £6.00 BY298 3 amp/fast/R 20 for £1.50 BU126 10 for £6.00 BU205 10 for £8.00 BU105 10 for £6.00 25C2122A 10 for £8.00 BF458 10 for £1.00 BD136 20 for £1.25 BF224 20 for £1.40 OAA91 40 for £1.00 BYX10 100 for £4.00 KT3 multiceps 10 for £7.50 50 Ceramic Condensers £1.50 Mixed Mounting Kit for Power Transistors 50p 300 Condensers £1.50 300 Resistors £1.50 150 Electrolytics £2.00 15 Bulbs 40p Antistatic Discloth 5 for £1 100 Diodes £1.50</p>			
<p>A 823A chassis Scan drive £5 IF £3 Scan control panel NEW A31/510 tubes with s/coil £6 + £2 post</p>		<p>SKB 2/08 L5A 30p KBL 005 30p KBL 02 30p KBP 04 30p W02 15p W004 15p W005 20p AT 2076/35 £7 AT 2076/55 GEC split diode transformer £10 AT 2048/11 LOPT1 Mullard £2.50</p>		<p>Plastic Boxes 4 3/4 x 4 x 1 x 3/4 50p 100 Fuses £2.00 100 W/W Res. £1.50 BF 199 20 for £1 10 x 20 Turn 100k pots. Rank £2 Thorn 9 volt power supply regulated £3.00 BF 470 20 for £2 20 Slider Knobs 70p 6 Mixed UHF Aerial Isolating Sockets, some with long leads. Fit IIT, GEC, Philips, Pye £1.00</p>					
<p>SENDZ COMPONENTS TO ORDER SEE BACK PAGE</p>		<p>Mixed PCKA TO66 12 Power Trans RCA 16182 NPN Replacement for BD124 and Mounting Kits £1.00 50 Mixed AC series Transistor £4.50 15 Panel mount rocker switch 250V/10A £1.50 25 Panel Mount Bulbs & Neons £1.50 10A £1.50 25 LED red/yellow/green £1.50 20/C Holders £1.20 20 Large LED Red £1.00 20 Small LED Red £1.00 10x20 Turn 100K Pots £2.50 100 Transistor 80p 20 Convergence Pots 80p 10 Thermistors 50p 20 Slider Pots £1.00 30 Presets 50p 15 VDR + thermistors, degaussing, HT, etc. £1.00 40 glass reed switch £1 10 press to make switch 70p 40 Pots £1.50 5 Tube Bases £1.00 1,000 Diodes, Condensers, Resistors on Bandolier £2.00 Lucky Dip 600 gram £1.00 Jungle Bag 5Kg £5.00 20 Knobs £1.00 20mm Fuse Holders Chassis Mount 20 for £1 IN4001/6 100 mixed £2.50 EHT Diodes, small 20 for £1</p>							

SENDZ COMPONENTS

TO ORDER SEE BACK PAGE

Thorn Spares	
New 9000 Decoder	£8.50
9000 Frame panel	£8
9000 Cyclops panel	£1.50
8000/500 timebase panel	£8
8800 convergence panel	£6
8500 convergence panel	£6
4000 Power supply	£3
1600 Mains lead, switch	
3500 6 push button + cable form	£1.50
T805 1V1PN T066 80V/6A	10p
9000 Sound output panel	£1
3500 focus unit	£1.50
3500 Mains Trans	£4
3500 cut outs	10 for £4
3500 IF panel	£2
3500 Frame panel	£3
3500 Line panel	£3
3500 A1 Diode	£2
Export 3500 IF panel	20p
IC board with set of SN74LS	£1
4000 Tube base	£4
3500 A1 pots	50p
Beam limiter panel	£1.50
3500 Power panel with Y969	£1
7.5V regulated adaptor 240V 6V	£3.50
Rank Toshiba preh unit	£9.50
0354	£2
2 banks of 3 PB unit, Pyc 731	£2
4 Push button unit pre-h	£1.00
6 Push button VHF/UHF for v/cap. GEC-Decca tube	£7.00
7 Push button for CVC5 ITT	£8.00
KT3 12 Push button unit	£2.00
KT3 (Export) 12 P.B.U.	£2
6 Push button Unit Thorn	£1.00
6 Push button Unit fits GEC & Decca etc.	£6.00
Hearing aid unit	£3
6 Push button unit PYE 713	£7.00
7 Button Unit GEC with Lamp	£7
Bush T515A 6 button unit with Pos & mains lead 6 push buttons. Bush	£6.00
Mains Droppers	
G8 2R2+6R8	£1.25
G8 4R 15 watt	75p
Pyc 731 3+56+27R	50p
Pyc 3K5/15R/45R	50p
Thorn 5017/1K5	£1.00
1292/2048/117	£1.00
270/106 for Thorn 4000	50p
18320/7039	£1.10
Thorn 50-40R-1K5	50p
Ae Socket & Lead	50p
GEC, ITT, Philips, Pyc	25p
7x3/4 Thorn	£1
Rank Toshiba Tube Bases	30p
Speakers	
Pair 25 watt 4Ω speaker & tweeter in cabinet	£15.00
6x4 G11 25 ohm	£1.00
51x2 212 3 ohm	£1.00
5x3 80 ohm	70p
5x3 50 ohm	50p
5x3 35 ohm	70p
6x4 15 ohm	£1.00
7x3 70 ohm	£1.00
8x5 8 ohm 15 watt	£2
8x5 8 ohm	£1
7x3 8 ohm	70p
5" dia 16 ohm	£1.00
5" dia 8 ohm	£1.50
6 1/2" dia 4 ohm	£1.50
6 1/2" dia 3 ohm	£1.50
2 3/4" dia 8 ohm	75p
3" dia 8 ohm	75p
4 1/2" sq. 15 ohm	75p
KT3 speaker K30	75p
3" dia 15 ohm	60p
1690 5x3 12 ohm	£1
K45 Philp 15 ohm	75p
K30 15 watt	£1
KT3-K30	
OF-550 F.W.	10p
OF-513 correction	10p
OF-557	50p
Diodes	
BY 126	10p
BY 127	10p
BY 133	10p
BY 134	10p
BY 164	50p
BY 176	25p
BY 179	40p
BY 184	25p
BY 187	10p
BY 190	10p
BY 196	30p
BY 198	30p
BY 204/4	10p
BY 206	8p
BY 208/800	8p
BY 210/400	5p
BY 210/800	10p
BY 223	60p
BY 224/600 4.8A 600k bridge	50p
BY 226	15p
BY 227	15p
PHILIPS NE511N	30p
BY 237	5p
BY 254	10p
BY 255	30p
BY 298	10p
BY 299	8p
BY 406	8p
BY 527	20p
BY 407a	10p
BY 602	10p
F 247	10p
KN 3102	50p
International Rectifier EHT Diodes	G770/HV34 6KV 3 for 8p
6A/600V Stud Diodes	20p
6A/1000V Stud Diodes	20p

NEW 161Z THORN Chassis with IC's & AU113	£8.00
30V Power Supply 500M/A 4x2 1/2	£2.50
Pyc 731 Power Panel	£13
6 Diode Universal Triplers	£3.25
NEW PYE 725 line O/P panel with L.O.P.T. & Tripler	£10.00
Thorn Mains Isolator unit for 70-80W. Ex-speaker	£2
NEW GEC 20AX Power Supply Switch Mode	£12.00
Complete new GEC portable chassis M1201H/M1501H with P.B. U./v.cap/LOPTI	£11.50
Field + Jungle panel for GEC 3133/3135	£7.00
GEC 2110 line panel with transformer	£12.00
GEC 2110 tuner unit + IF Panel	£12.00
Pyc/Chelsea Line on panel	£12.00
Pyc 713 IF panel and tuner	£7.00
Pyc 713 Chroma	£10.00
Pyc/Chelsea Timebase panel with LOPTI	£10.00
Pyc 731 Frame Panel	£5.00
Pyc 731 Convergence Panel	£5.00
Pyc 731 Chroma	£10.00
Pyc 731 IF panel + tuner	£10.00
Pyc CDA/205 panel	£6.00
GEC portable chassis + LOPTI 2114 New	£4.00
Thorn 1613/1713 chassis	9.75
G9 Power Panel	£6.00
Mono RANK Chassis 127A NEW	£10.00
NEW MULLARD TELETEX	
Decoder Panel (VM6230)	£15.00
Panel 6101	£15.00
Panel 6310	£15.00
G8 Tuner Unit + Panel	£5.00
G8 Convergence Panel	£12.00
(late type)	£12.00
G8 Power Supply	£6.00
G8 6 Sloping PBU	£8.00
G8 IF & Chroma	£10.00
G8 Chroma	£6.00
G11 IF Detector	£3.00
G11 Selector gain module	£3
Complete CVC 825 Chassis (both panels)	£40.00
AEC V/Cap Resistor Unit UHF with IC	£3.00
SAS600 SAS670	£3.00
Z714 RANK IF Panels 6MHz 1 I.C.	£3.00
SL437F	£3.00
Z909B RANK IF Panels	£2.50
Export 5.5MHz 2 I.C.'s	£2.50
TBA1205B TCA2705Q	£6.00
K35 IF	£6.00
Z743 RANK IF Panel	£1.50
Export 5.5MHz 3 I.C.'s	£1.50
FBA750+SC9504P + SC9503P	£1.50
Pyc G11 Front panel with transducer, pots, tuner pots, 6 pb switch + lead	£5.00
Pyc 6 button switch portable	£1.00
GEC V/cap VHF/UHF tuner and IF + sound O/P PC 706B3 (Export)	£12.00
GEC Line O/P PC 659B3	£6.00
2110 GEC Power Panel	£8.00
GEC Power Supply (Export)	£10.00
G11 universal correction panel	£6
CVC 20 Front panel with sliders + mains input panel	£4
CVC 40 PUSH BUTTON ASSY with sliders - complete with lamp assy + pots	£14
CVC9 slider pots panel	£14
CVC 5 Mains on/off + 5 pots	£2
Universal Focus Fits Pyc, Thorn and Decca Units	£2
Large Type	75p
Decca small	75p
KT3 Focus Unit	75p
K30 Focus Pot	75p
TX10 Focus Units	£6.00
CVC 32 Focus Unit	75p
Fidelity Focus Unit 14R-14S	30p
3500 Thorn Focus Unit	£1.00
ITT Small form with Split	47/100K
Z718 Bush Focus	£2.00
Diode	50p
TV11	50p
Remo TV125P	50p
TV13	50p
TV14	50p
TV18	60p
TV20	£1.00
TV45	50p
Thorn 14/1500 rec stick	5p
G7000 Philips Video Games Packs	
111 types	£8.00 each
G11 drawer ASS 3 pots Mains switch and lead	£2.00
Line O/P panel GEC 2217/2218/2213/2214/2226/2227/2228	£10
CLOCK DISPLAY	
4 SEG ACDM45	£1.00
4000 thick film	£2.00
DISPLAYS	
4040 Clock	£1.00
7seg Red LED	50p
2 digit LED 8.8	50p
2 digit LED -1.8 with panel + MCT4511	£1.00
4040/63	£1.50
CVC 20-25-30 Mains Switches	75p
Infra Red and Ultrasonic G11 Teletext Decoder Panel	£30
RANK & ITT Mains Remote On/Off Switch (720R)	£1.50
RANK & ITT Mains Remote Switch 2865 ohm	£1.50
G11 Remote Switch 2800 ohm	£1.50
RANK Mains Switch	50p
4 amp Mains Switch	25p
GEC Mains Switch 4 amp	25p
KT3 Mains Switch	£1.00
THORN Rotary Mains Switch	25p
G8 Mains Switch	25p
Thyrister 600/4 amp C106/2	25p
G11 Preh Red LED P/Button for C.H. Change	25p
RANK TOSHIBA Transducers TPC-2011	20p
Mains Switch ITT Long Type Print	75p
Mains Switch GEC Long Type TAG	75p
Thorn 12 or 24 volt battery convertor for portable colour TV	£6.00
Tape Heads R/Play/Back Mono/Stereo	£1.00

9V Power Supply THORN 9V 200 M/A	£2.00
Rank Secam Decoder Panel UHF & VHF	£2.50
1115A	£13.00
NEW GRNDING SPARE PANELS	
Set No. SC4127, SC4337, SC6217, SC76237	
GRINDING MODULAR TYPES	
Tuner IF AF TRX LOUP TP amplifier	£1.50
Tuning board Colour RGB LED Board	£2.00
Deflection Board	£2.00
From £3 to £8	
Multi-Caps	
4.700/75 6 amp Rip	£2.00
3500 300M + 300M	£1.00
4000 400M	60p
350V 400M	60p
Thorn 3500	£1.00
175/100/100/350K	£1.00
K13/200/250/385V	£1.00
300 + 300 + 150 + 100 + 50MFD	£1.00
350V	£2
47/220/350V	60p
150/150/100/100/320K	£2.00
2500/2500/63V	50p
150/200/200/300K	70p
400/400/200V	£1.70
300/100/100/16.275V	£1.50
100/200/325V	40p
150/150/100/375V	£1.50
800/500/100/32.42/300K	2.00
150/200/300K	50p
Jelly pot Thorn 100/44013	£3
150/150/100/100/320K	£2.00
100/350 + 300/200/100/16.275V	£2.00
225 + 25/380 GEC	70p
300/300/300/350K	£1.50
500/500/25V	50p
150/150/100/300K	75p
200/150/150/300K	1.00
ITT Panels	
CVC 40/2 Chassis, new £30, complete with intrabase panel	£3.00
CVC 820 Line O/P Panel	£3.00
CVC 20 Mains Panel	£1.00
ITT 8 & 6 Push Button Unit	£10.00
CVC 40/2 New Chroma Panel	£2.00
CMA 10	£2.00
CMA 11	£2.00
CMA 30	£2.00
CMA 40	£2.00
CMA 10/2	£1.50
CMA 16	£4.00
CMA 38	£8.00
CMA 45	£1.50
CMA 47	£1.00
CMA 52	£15
CMA 57	£6.00
CMA 58	£8.00
CMA 59	£8.00
CMA 67	£3.75
CMA 67/2	£4.00
CMA 68	£4.00
CMD 12	£10
CMD 32	£5.00
CMD 33	£5.00
CMD 40	£5.00
CMD 41	£5.00
CMD 800	£10.00
CMF 25	£2.00
CMF 26	£2.00
CMF 40	£2.00
CMH 10	£1.50
CMH 31	£1.00
CMK 12 (untested)	£4.00
CMK 30 (untested)	£4.00
CMN 20	£1.50
CMN 21	£1.00
CMN 40	£1.00
CMN 45	£2.50
CMP 10	£2.00
CMP 11	£4.00
CMP 40	£2.00
CMS 11	£2.00
CMS 40	£2.00
CMU 12	£10.00
CMU 14	£8.00
CMU 30	£7.00
CMU 45	£7.00
CMV 30	£5.00
GMA 90	£2.50
GMC 12D	£2.50
GMR 64	£5.00
TMN 2	£2.00
VCA 20	£10
VCA 21	£10.00
VMC 26	£3.00
VMC 34	£5.00
VMC 44 + 45	£4.00
VMC 51	£5.00
Hand Sets	
G11 Ultrasonic Teletext Handset	£24.00
8 C.H. Ultrasonic GEC Full Remote C20141/C221911	£15.00
New Replacement for G11 Ultrasonic Full Remote	£12.00
Thorn 4000 insert with 7 buttons	£5.00
Decca RC 11	£14.00
Decca RC 12	£14.00
G11 Infra-red full teletext	£24.00
RANK Infra-red	£10.00
Dynatron-Full remote CTV 62, 63, 64	£19.00
Hitachi infra red handset	£18
Philips full remote KT7, 16C/28/200/334, 7228/7324, K12 26C 797/157 56K 1826	£12.00
G11 Full remote top button assy	£12.00
G11 Full remote repair service (exchange unit)	£12.00
Philips infra red full remote 9 channel for 60	£6.00
Philips infra red full remote 12 channel for 60	£12.00
CP2605	50p
Philips Key Pad set KT3 K30	£3.00
KT3K30 FT Text	£15.00
KT3K30 Full remote	£15.00
KT3 Power supply	£4.00
Hitachi 8 button unit with resistor unit Last year mod	£7.00
GEC infra-red 2236-2026	£4.00
GEC push pad hand set button blobs 10 each	£1.00
Pye & Philips handset KT3-K30 chassis	£5.00
RC 4001-RC 5150-RC 5176-RC 5171-RC 5177	£5.00
Special Price	£13.00
ITT Hand Set with TV-Teletext-VCR	£12.00

