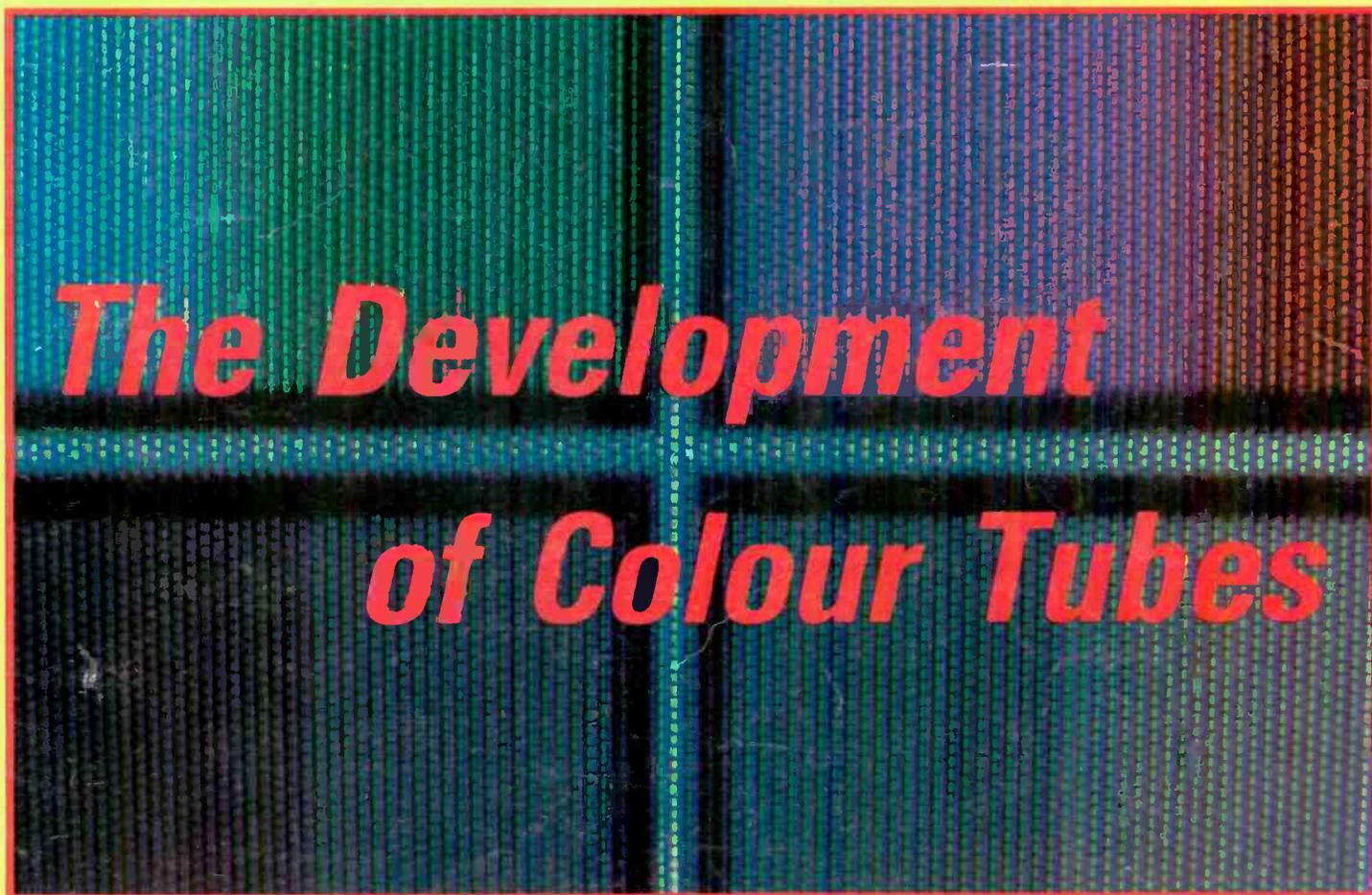


**JUNE 1986**

Australia \$2, New Zealand \$2.50, Malaysia \$5.75 **£1.20**

# **TELEVISION**

**SERVICING·PROJECTS·VIDEO·DEVELOPMENTS**



***Also inside:***


**Servicing the NordMende  
F10 and F11 Chassis**

**Video Signal Processing**

**Microcomputer Servicing • DX-TV**

**VCR Clinic • TV Fault Finding**

# THE 'TELEVISION' PHOTO SERVICE

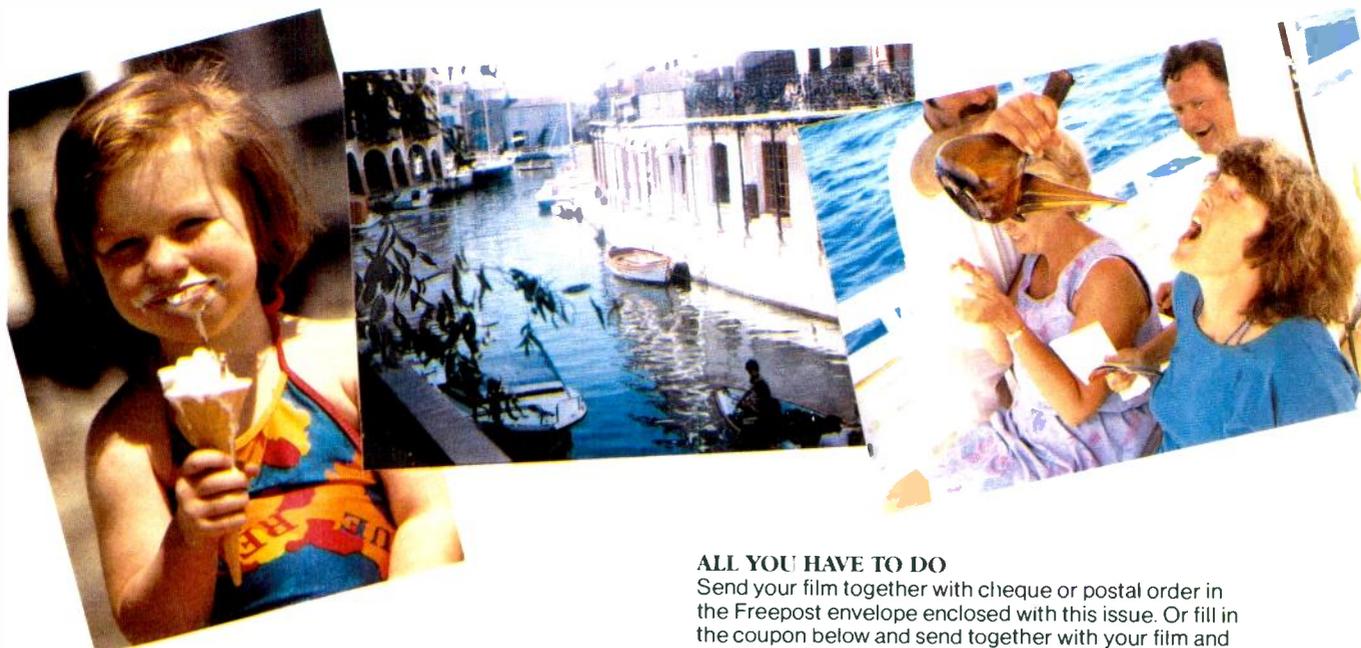

So many readers have taken advantage of this award-winning service that the economies made are being passed on to you. Despite inflation, prices for Superprints are the same as for last year, and prices for standard size prints are even lower! Here is the price range—and remember, Superprints give you 30 per cent more picture area.

No. of Exposures	Superprints (inc. 15% VAT)	Standard size prints (inc. 15% VAT)
12—15	£1.65	£1.49
20—24	£2.20	£1.99
36	£2.95	£2.49

Plus 30p post and packing.  
Extra set of prints (any size) £1.40.

## RELIABILITY AND QUALITY

All our prints are made on super high-gloss Kodak paper. They are checked at every processing stage for accurate colour reproduction by the Kodak Monitoring Service—a Gold Award Winner in both 1984 and 1985. After allowing for postal and peak-period delays, you should normally expect your prints by First Class return post after seven to ten days.

## ALL YOU HAVE TO DO

Send your film together with cheque or postal order in the Freepost envelope enclosed with this issue. Or fill in the coupon below and send together with your film and remittance in a strong envelope to: Readers Photo Service, FREEPOST, PO Box No. 42, Brunel Road, Newton Abbot, Devon TQ12 4XJ. All popular makes and sizes of film are accepted, and you have a full money-back guarantee. Credit is given for prints that do not come out.

## PERSONALISED SERVICE

Readers know we care for their prints. If you have any queries, phone 0626 67150.

## SPECIAL FILM OFFER

Even if you do not have an exposed film ready for processing, you can obtain films from us at highly competitive prices. Fresh Kodacolor VR Film for colour prints from only £1.99. Konica SR High Resolution Film for colour prints from £1.50 and when you order three you get another one FREE.

To take advantage of this offer, you must use the special order form on this page.

## Sizes of Photos (Approx.)

Superprint sizes: 4" x 4" (126) 4" x 5" (110 and Disc) 4" x 6" (135)  
Standard print sizes: 3.5" x 3.5" (126) 3.5" x 4.5" (110 and Disc) 3.5" x 5" (135)

## USE THIS LABEL IF YOU HAVE NO ENVELOPE OR PASS TO A FRIEND. IT IS USED TO ENCLOSE YOUR PRINTS.



TO ORDER NEW KODACOLOR FILM				
Please write quantity required in the box(es) below.				
	size	each	qty	amount
Kodacolor VR film for Colour Prints	126.24	£1.99		
	110.24	£1.99		
	135.24	£1.99		
	135.36	£2.49		
	15 Disc	£1.99		
Cheque/PO payable to				£
READERS PHOTO SERVICE				
Name				
Address				
Post Code				

TO ORDER NEW KONICA FILM				
Please write quantity required in the box(es) below.				
	size	each	cuty 4 for 3	amount
KONICA SR film for Colour Prints	126.24	£1.50		£4.50
	110.24	£1.50		£4.50
	135.24	£1.50		£4.50
	135.36	£2.20		£6.60
	15 Disc	£1.50		£4.50
Cheque/PO payable to				£
READERS PHOTO SERVICE				
Name				
Address				
Post Code				

TO SEND FILMS FOR PROCESSING	
I enclose	..... films for processing.
Please send	(tick boxes)
SUPERPRINTS	<input type="checkbox"/>
Standard Prints	<input type="checkbox"/>
EXTRA SET OF PRINTS	<input type="checkbox"/>
I enclose cheque/PO for	£..... made payable to
READERS PHOTO SERVICE.	
ENCLOSE ORDER FORMS & PAYMENT FOR NEW FILMS TOO IF REQUIRED.	
Name	
Address	
Post Code	



# TELEVISION

June  
1986

Vol. 36, No. 8  
Issue 428

## COPYRIGHT

© IPC Magazines Limited, 1986. Copyright in all drawings, photographs and articles published in *Television* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Television* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

## CORRESPONDENCE

All correspondence regarding advertisements should be addressed to the Advertisement Manager, "Television", King's Reach Tower, Stamford Street, London SE1 9LS. Editorial correspondence should be addressed to "Television", IPC Magazines Ltd., King's Reach Tower, Stamford Street, London SE1 9LS.

## SUBSCRIPTIONS

An annual subscription costs £14 in the UK, £17 overseas (by surface mail). Send orders with payment to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex, RH16 3DH.

## BINDERS AND INDEXES

Send orders for binders (£4-50) and indexes (75p) to the Editorial Office, Television, IPC Magazines Ltd., King's Reach Tower, Stamford Street, London SE1 9LS. Prices include VAT and postage. Add 60p for overseas orders.

## BACK NUMBERS

Some back issues published during the last six months are available from the Editorial Office at £1-40 inclusive of postage and packing. Address as above.

## QUERIES

We regret that we cannot answer technical queries over the telephone nor supply service sheets. We will endeavour to assist readers who have queries relating to articles published in *Television*, but we cannot offer advice on modifications to our published designs nor comment on alternative ways of using them. All correspondents expecting a reply should enclose a stamped addressed envelope.

Requests for advice on dealing with servicing problems should be directed to our Queries Service. For details see our regular feature "Service Bureau". Send to the address given above (see "correspondence").

## this month

- 485 Leader**
- 486 Modern Receiver Circuitry, Part 3** *J. LeJeune*  
The way in which the signals at the output from the vision detector are separated and processed, including an account of the operation of a modern single-chip PAL decoder and a look at RGB output circuits.
- 488 Next Month in Television**
- 489 Grundig's Satellite TV Receiver** *Steve Beeching, T. Eng.*  
A preview of Grundig's approach to satellite TV reception.
- 490 Letters**
- 494 Servicing the NordMende F10/F11 Chassis** *Christopher Holland*  
This major European CTV chassis features some novel circuitry, specifically a step-up chopper power supply and a thyristor field output stage. An account of the operation of these circuits and guidance on fault finding.
- 498 Teletopics**  
News, comment and developments.
- 500 The Development of Colour Tubes, Part 1** *Eugene Trundle*  
This initial instalment outlines the evolution of the different types of colour tube from the earliest delta-gun type to the 45AX - via the Trinitron, PIL, 20AX and 30AX types.
- 504 Servicing Teletext Decoders, Part 5** *Mike Phelan*  
How to go about fault finding, with specific reference to the initial Philips/Mullard chip set. Interpreting display errors and using an ASCII table to relate errors to data lines and memory locations. Notes on the effects of LSI chip faults.
- 510 VCR Clinic**  
Reports from Christopher Holland, Les Harris, Philip Blundell, Eng. Tech., Steve Illidge and Mick Dutton.
- 512 LCD TVs from Citizen**  
How Citizen's pocket TV set produces a picture on its 18,000 pixel liquid-crystal display.
- 513 TV Fault Finding**  
Reports from Alan Shaw, Michael Dranfield and Philip Blundell, Eng. Tech.
- 514 Long-distance Television** *Roger Bunney*  
Reports on DX reception and conditions, news and a review of the Fringe Electronics f.m. radio preamplifier.
- 517 Other things and other places** *Les Lawry-Johns*  
Les takes a break from TV matters and heads for far off Dersingham - in a rather roundabout way.
- 518 Servicing Sinclair Microcomputers, Part 2** *Ken Taylor*  
Complete circuit for the ZX81, along with a detailed fault-finding procedure and data on chip pin conditions. An easy way to get acquainted with microcomputer servicing techniques.
- 523 Service Bureau**
- 524 Test Case 282**

OUR NEXT ISSUE DATED JULY WILL  
BE PUBLISHED ON JUNE 18

# MANOR SUPPLIES

MKV PAL COLOUR  
TEST GENERATOR FOR TV & VCR.

TEST  
DEMONSTRATIONS  
AT 172  
WEST END LANE




- ★ 40 different patterns and variations.
- ★ Broadcast transmission accuracy (fully interlaced sync pulses with correct picture blanking).
- ★ EBU colour bars, BBC colour bars, whole rasters & split bars (specially useful for VCR service), white, yellow, cyan, green, magenta, red, blue and black.
- ★ Chequerboard.
- ★ Mono outputs with border castellations, cross hatch, grey scale, vertical lines, horizontal lines and dots. UHF modulator output plugs straight into receiver aerial socket.
- ★ Additional video output for CCTV & VCR.
- ★ Facilities for sound output.
- ★ Easy to build kit, standard parts. Only 2 adjustments. No special test equipment required.
- ★ Mains operated with stabilised power supply.
- ★ All kits fully guaranteed with back-up service.
- ★ Also available with VHF Modulator.

Price of Kit **£70.00**  
Case (10"×6"×2¼") app. **£8.60**  
Optional Sound Module (6MHz or 5.5MHz) **£3.90**  
Built & Tested in Case including Sound Module **£108.00**

SPECIAL TEST  
REPORT  
'TELEVISION'  
DEC. 1982

Post/Packing £2.50  
Add VAT 15% TO ALL PRICES

## PAL COLOUR BAR GENERATOR (Mk4)

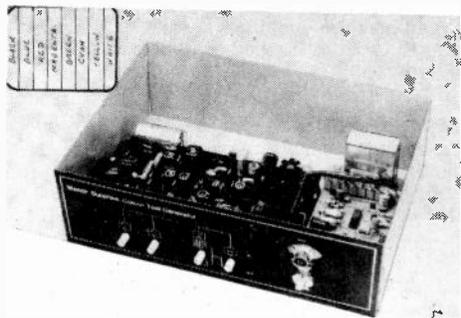

- ★ Output at UHF, applied to receiver aerial socket.
  - ★ In addition to colour bars R-Y, B-Y etc.
  - ★ Cross-hatch, grey scale, peak white and black level.
  - ★ Push button controls, battery or mains operated.
  - ★ Simple design, only five i.c.s on colour bar P.C.B.
- PRICE OF MK 4 COLOUR BAR GENERATOR KIT £30.00. CASE £8.60. BATT HOLDERS £4.20. MAINS SUPPLY KIT £4.20 (Combined P&P £2.20).**

MK 4 (BATTERY) BUILT & TESTED £58.00 + £2.20 P & P.  
MK 4 (MAINS) BUILT & TESTED £68.00 + £2.20 P & P.  
VHF MODULATOR (CH 1 to 4) FOR OVERSEAS £5.75.  
EASILY ADAPTED FOR VIDEO OUTPUT & C.C.T.V.

ADD  
VAT  
15%

THORN TX9 MK2/3, TX10, teletext  
Mullard Decoder panel + Interface **£35.00** p.p. £1.80  
THORN TX10, PHILIPS G11 PRESTEL, TELETEXT  
Mullard Units VM 6230, 6330 plus Line Coupler & Interface **£38.00**  
p.p. £2.50

EXTERNAL TELETEXT ADAPTOR  
(RADOFIN) with cable remote control. Fully tested. **£150.00** p.p.  
£3.00. Plugs into aerial socket of any T.V.  
SPECIAL OFFER (shop customers only).  
SURPLUS 'AYR' TELETEXT EXTERNAL ADAPTOR UNITS.  
Ideal for experimental use **£50.00**.

## TV SERVICE SPARES

BACKED BY TWENTY YEARS EXPERIENCE & STAFF OF  
TECHNICAL EXPERTS

LOPTs, TRIPLERS, PANELS, TUNERS, SELECTORS ETC.  
SPECIAL OFFER Ex rental T.V. Sound & Vision Tuner Units. Ideal as front  
end for Monitors, Portable Video, HiFi, etc. Deluxe Cabinet, mains  
operated, 8 position selector, Saw Filter IF. Only **£15.00** p.p. £2.80.  
SPECIAL OFFER Mullard/Philips quality UHF modulator (audio & video  
input) ex new equipment **£5.00** p.p. £1.00.

PHILIPS G11 PANELS (tested).  
Power, frame, IF, decoder **£18.00** each p.p. £2.00. Scan Panel **£28.00** p.p. £2.80.  
PHILIPS G11 PANELS ex rental (untested).

Power, frame, IF, decoder **£10.00** each p.p. £2.00.  
PHILIPS HANDSETS ex rental (untested) CTX, K4, K35 etc. Teletext +  
Video **£5.00** p.p. 80p.

THORN 9000 Fault Finding Guide **£1.00** p.p. 30p.  
THORN REMOTE CONTROL HANDSETS  
8800/9800 (2-button) **£10.00**; TX9 ULTRASONIC (3-button) **£15.00**; TX9,  
TX10 Infra red **£18.00**; TX9, TX10 Infra red Teletext **£20.00**, p.p. £1.20.

TX10 Remote & Tuning control panel (1515) **£9.40** p.p. £1.50  
TX9/TX10 Teletext interface panel (1524) **£5.00** p.p. 80p.

THORN TX10 Facia Control Panel incl. Infra Red Remote Control receiver  
**£7.50** p.p. £1.50.  
THORN TX10 Series Facia Control Panel with 8 position Channel Selector  
**£6.50** p.p. £1.50.

SAW FILTER IF AMPLIFIER PLUS TUNER complete and tested for T.V.  
Sound & Vision. **£28.50** p.p. £1.20.  
THORN TX9, TX10 Saw Filter IF Panel. **£5.00** p.p. 80p.

PAL DECODER KIT (Video to RGB) for Monitors **£27.00** p.p. £1.00.  
PAL ENCODER KIT (RGB to Video) **£18.50** p.p. £1.30.  
TELETEXT DECODERS New & Tested Mullard VM 6101 **£30.00**, Texas  
XM11 **£40.00**, KT3 Tested **£30.00**, Untested **£5.00** p.p. £1.60

CROSS HATCH UNIT KIT, Aerial Input type, incl. T.V. sync. and UHF  
Modulator, Battery Operated, also gives Peak White & Black Levels, can  
be used for any set. **£12.00** p.p. 80p. (Alum. Case **£2.90**, De Luxe Case **£6.80**  
p.p. £1.40.) ADDITIONAL GREY SCALE Kit **£2.90** p.p. 45p.

UHF SIGNAL STRENGTH METER KIT **£22.00** Alum. Case **£2.90**. De  
Luxe Case **£8.60** (Built & Tested **£46.50**) p.p. £2.30.

CRT TESTER & REACTIVATOR KIT For Colour & Mono complete with  
Case, Panel Meter Indicator - can be adapted for latest CRTs **£29.50** p.p.  
£2.80.

BUSH A823 Convergence, Time Base Panels **£5.00** each. p.p. £1.80.  
BUSH Z718 BC6100 series IF Panel **£5.00** p.p. 90p.  
BUSH A816 IF Panel (Surplus) **£1.00** p.p. 90p, 5 for **£4.00** p.p. £1.40.

GEC 2040 Decoder Panels, **£1.50** p.p. £1.80.  
GEC 2110 PANELS Frame **£8.50** p.p. £1.40. Sound **£2.50** (tested) p.p. 80p.  
GEC 20AX Line Time Base **£18.00**. IF-Decoder **£12.50** p.p. £2.00.  
PYE 691-7 CDA Panels. Makers tested stock. **£6.00** p.p. £1.45.

THORN TX9 Panels ex factory for small spares. Includes I.C.s &  
Semiconductors etc. **£3.00** p.p. £1.80.  
THORN TX9 Panels salvaged ex factory for spares incl. LOPT & Mains  
Transformers. **£10.00** p.p. £2.80.

THORN TX9 Panels ex factory salvaged complete cond. **£20.00** p.p. £2.80.  
THORN 3000/3500 Power supply P.C.B. **£3.50** p.p. £1.00.

THORN 8000, 8500, 8800 IF Decoder Panels Tested **£10.00** p.p. £2.30.  
THORN 8000/8500 IF/Decoder Panels salvaged **£3.20** p.p. £1.80.  
THORN 9000 IF/Decoder Panels Salvaged. For spares **£2.50** p.p. £1.80.  
THORN 9000 Frame Time Base **£8.50** p.p. £1.80.

PHILIPS G8/G9 IF/Decoder Panels for small spares incl ICs **£2.50** p.p. £1.60.  
G11 PANELS, Ex Rental SCAN (incl LOPT) **£28.00** p.p. £2.50 (tested).  
G11 PANELS, Power, Frame, IF, Decoder, **£18.00** each. p.p. £2.00 (tested).  
GRUNDIG 8630 Series Varicap Tuners **£5.00** p.p. £1.00.

U321, ELC1043/5 **£7.80** p.p. 80p. Makers Controls PYE CT200 4PSN **£7.50**,  
BUSH 4PSN **£4.80**, DECCA 4PSN **£5.80**, 6PSN **£6.80** p.p. 80p. etc.  
BUSH "TOUCH TUNE" Varicap Control Z585, 710 **£3.80** p.p. £1.00.  
VARICAP UHF-VHF ELC 2000S **£9.80** p.p. £1.00.

UHF/625 TUNERS, many different types in stock. DECCA Bradford 5  
position, MULLARD 4 position **£2.50**, JAP Rotary **£4.80** p.p. £1.80.  
TV SOUND IF Panels **£6.80** p.p. £1.00.

LOPT TESTER, Service Dept approved **£15.90** p.p. £1.20.  
LOPTS New and guar. P/P Mono **£1.35**, Colour **£1.50**, Bobbins 80p.

BUSH, MURPHY 774 series ..... **£9.80**  
BUSH, MURPHY A816 series ..... **£9.80**  
FERG., HMV, MARCONI, ULTRA  
1500, 1590, 1591, 1612, 1613, 1712 ..... **£4.80**

THORN 1600, 1615, 1690, 1691 ..... **£9.15**  
GEC series 1 & 2 ..... **£8.00**  
INDESIT 2024EGB ..... **£7.65**  
ITT/KB VC200, 300 ..... **£7.90**  
PHILIPS 170, 210, 300 series ..... **£7.65**

PYE, INVICTA, EKCO.  
368, 169, 569, 769 series ..... **£7.65**  
SPECIAL OFFER  
DECCA 1700, 2001, 2020, 2401, 2420 **£3.80**  
GEC 2114J/Junior FineLine ..... **£2.80**  
PHILIPS 320 ..... **£2.80**

RBM A823 ..... **£4.80**  
GEC 2028, 2040, 2100 ..... **£4.80**  
PYE 713, 715 ..... **£6.80**  
PHILIPS 570, 571 ..... **£6.80**

R.B.M. T20, T22 ..... **£9.80**  
R.B.M. T20, T22 Bobbin ..... **£5.60**  
DECCA Bradford (state Mod No.) ..... **£8.80**  
DECCA 80, 100 ..... **£8.80**  
FIDELITY ZX2000, 3000 ..... **£16.00**  
GEC 2110 series ..... **£10.60**  
ITT CVC 5 to 9, CVC20 ..... **£9.80**  
ITT CVC25, CVC30 series ..... **£8.80**  
ITT CVC45 ..... **£9.80**

PYE 691-697 (state model no.) ..... **£10.00**  
PYE 725 (90°) 731 to 741 ..... **£9.20**  
PHILIPS G8 ..... **£8.80**  
PHILIPS G9 ..... **£9.80**  
PHILIPS KT3 ..... **£9.80**  
THORN 3000/3500 SCAN, EHT ..... **£6.90**  
THORN 8000, 8500, 8800 ..... **£12.80**  
THORN 9000 to 9600 ..... **£12.90**  
THORN 9800 ..... **£19.80**  
THORN TX9 ..... **£14.80**

OTHERS AVAILABLE, PRICES ON REQUEST.  
TRIPLERS Full range available. Mono & Colour.  
Special Offer: THORN 3000/3500 EHT Tripler **£2.50** p.p. £1.30.  
6-3V CRT Boost Transformers for Colour & Mono **£5.90** p.p. £1.40.  
THORN TX10 focus control **£8.80** p.p. 80p.

CALLERS WELCOME AT SHOP PREMISES  
THOUSANDS OF ADDITIONAL ITEMS, ENQUIRIES INVITED  
LARGE SELECTION TESTED COLOUR PANELS POPULAR MODELS  
Goods available if in stock immediately over shop counter (Mail order  
between 3 days and 1 week from receipt of order). ADD VAT 15%

Telephone 01-794 8751, 794 7346

## MANOR SUPPLIES

172 WEST END LANE, LONDON, NW6 1SD  
NEAR: W. Hampstead Tube Stn. (Jubilee) Buses 28, 159, C11 pass door  
W. Hampstead Brit. Rail Stn. (Richmond, Dalston, Stratford, N. Woolwich)  
W. Hampstead Brit. Rail Stn. (St. Pancras, Bedford)  
Access from all over Greater London.

Mail Order: 64 GOLDERS MANOR DRIVE, LONDON NW11 9HT  
PLEASE ADD VAT 15% TO ALL PRICES INCL P+P

**INCREASE YOUR PROFITS IMPROVE YOUR SERVICE WITH RELIABLE COST EFFECTIVE TEST EQUIPMENT**


**ALSO AVAILABLE**  
 Analogue Multimeters  
 Digital Multimeters  
 Oscilloscopes  
 Signal Generators  
 Digital Frequency Meters  
 Pattern Generators  
 CRT Tester/Rejuvenator  
 T.V. Field Strength Meter  
 Digital Capacitance Meter  
**LARGE S.A.E.**  
**FOR COMPLETE LIST.**

**LEADER LCT-910A  
 C.R.T. TESTER-REJUVENATOR**

Our top selling instrument is designed to readily test the various characteristics and rejuvenation of both colour and B/W C.R.T's.


- ★ Tests for shorts and leakage between electrodes.
- ★ Tests cathode emission characteristics.
- ★ Separately checks condition of guns.
- ★ Removal of shorts and leakage between electrodes.
- ★ Checks heater warm-up characteristics.
- ★ Rejuvenation of low emission cathodes with automatic timing.
- ★ Super rejuvenation with manual control.

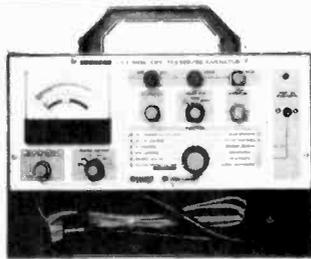★ Complete with tube base adaptors.  
 Size: H 230mm W 330mm D 120mm.



PRICE £260 + £39 VAT

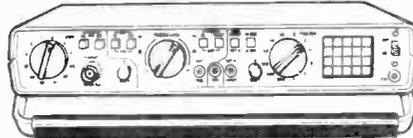**THE VERY LATEST SC110A LOW POWER,  
 FULLY PORTABLE OSCILLOSCOPE.**



The new Thandar SC110A represents a break-through in oscilloscope development. The SC110A is ONLY TWO INCHES thick and weighs under two pounds, yet retains the standard features and controls of a bench oscilloscope. **FITS IN A BRIEFCASE**

- Full Sized Performance**
- \* 10 MHz bandwidth
  - \* Full trigger facilities are provided including TV frame, or TV filtering.
  - \* Runs on 4 to 10V DC via disposable batteries, re-chargeable cells, or AC adaptor.
  - \* Size 255mm x 148mm x 50mm.

PRICE £165.00 + £24.75 VAT

- Accessories:** Carry Case £5.95 + £0.89 V.A.T.  
 x 1 Probe £7.50 + £1.13 V.A.T.  
 x 10 Probe £8.50 + £1.28 V.A.T.  
 x 1/x 10 Switched Probe £10.50 + £1.58 V.A.T.  
 AC Adaptor £6.95 + £1.04 V.A.T.


**LOPT TESTER**

**BK's REVOLUTIONARY DYNAMIC  
 'LOPT' TESTER**  
 Revolutionary L.O.P.T. tester. Operates in dynamic mode which actually tests the L.O.P.T. under high voltage conditions without de-soldering or removal.  
 Size 75x100x40 mm. Supply 240V AC

PRICE £25.99 + £3.90 VAT


**LEADER HIGH VOLTAGE  
 METER EMT PROBE**

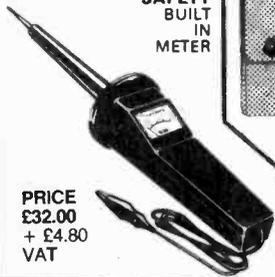Measures up to 40 K.V. D.C. with **SAFETY BUILT IN METER**



PRICE  
 £32.00  
 + £4.80  
 VAT


**\* FULLY GUARANTEED**

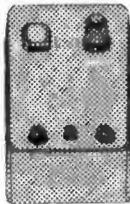

**CRT TESTER-REJUVENATOR**

**BK's C.R.T. TESTER-REJUVENATOR**  
 Tests and rejuvenates blue, green & red guns separately. Fitted with delta and P.I.L. sockets. Compact size 120x65x60 mm. Supply 240V AC

PRICE £32.00 + £4.80 VAT

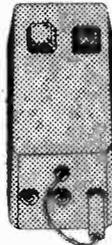

**HAMEG HM 203-5 20MHz  
 DUAL TRACE OSCILLOSCOPE:**

- SPECIFICATION:**
- \*BANDWIDTH DC-20MHz
  - \*SENSITIVITY CH1, CH2 2mV/50V/DIV
  - \*TIMEBASE 40ns to 0.2S CM
  - \*TRIGGER DC-40MHz Auto-Normal-TV
  - \*CALIBRATION OUTPUT
  - \*CH1 ADD AND INVERT FACILITY
  - \*ALT/CHOP SWITCH
  - \*LARGE RECTANGULAR SCREEN 8 x 10 cms.
  - \*BUILT IN SEMICONDUCTOR COMP. TESTER
  - \*SIZE 285mm x 145mm x 380mm.
  - \*SUPPLY 110-125-220-240V AC 50-60Hz



**WITH COMPONENT  
 TESTER**

PRICE  
 £270.00 + £40.50 VAT

Optional probes as above

**2 YEAR WARRANTY**

U.K. Post Paid, Export orders welcome, please deduct V.A.T. and enquire for Overseas carriage cost. Barclaycard/Access orders welcome, or Cheque, Bank Draft, etc., with order please. Large S.A.E. for technical leaflets of complete range. Delivery normally within 7 days.



**B. K. ELECTRONICS** Dept. 'T',

UNIT 5, COMET WAY, SOUTHEND-ON-SEA,  
 ESSEX. SS2 6TR TEL: 0702-527572



**Universal Semiconductor Devices Ltd.**

17 GRANVILLE COURT, GRANVILLE ROAD,  
 HORNSEY, LONDON N4 4EP, ENGLAND.  
 TEL 01-348 9420/9425 \* TLX. 25157 usdco g



WE OFFER ONE OF THE LARGEST RANGES OF SEMICONDUCTORS AT HIGHLY ECONOMICAL PRICES. THE FOLLOWING SEMICONDUCTOR TYPES ARE AVAILABLE FROM STOCK. IF WE DON'T STOCK WHAT YOU NEED THEN WE CAN GET IT FAST FROM OUR FACILITIES IN WEST GERMANY AND USA UPON REQUEST.

- TRANSISTORS - BIPOLARS - GERMANIUM AND SILICON**
- SMALL SIGNAL
  - POWER
  - DARLINGTONS - ALL SHAPES AND SIZES
  - VHF/UHF DEVICES - ALL SHAPES AND SIZES

- FETS - POWER MOSFETS**
- UNIUNIONS

- DIODES - GERMANIUM AND SILICON**
- RECTIFIERS AND BRIDGES
  - OPTO-ELECTRONIC DEVICES
  - LEDS OF ALL SHAPES AND SIZES

**THYRISTORS AND TRIACS - ALL**

- SHAPES
- SIZES
- RATINGS

- INTEGRATED CIRCUITS:**
- CONSUMER - DIGITAL/ANALOGUE
  - MICROPROCESSORS AND PERIPHERALS
  - IC SOCKETS

**JAPANESE COMPONENTS - VAST RANGE OF DISCRETES AND CONSUMER IC's.**

MAIL ORDER CUSTOMERS: PLEASE SEND FOR OUR COMPREHENSIVE PRICE LIST, ENCLOSING £1.00 IN STAMPS, CHEQUE OR POSTAL ORDER.

CATALOGUE SENT FREE OF CHARGE, WHEN REQUESTED ON OFFICIAL LETTERHEAD (WITHOUT REFUND), TO OEM'S, SCHOOLS, COLLEGES, UNIVERSITIES, GOVERNMENT INSTITUTIONS, COMPUTER FIRMS, ELECTRONIC REPAIR FIRMS AND DISTRIBUTORS.

**SPECIAL DISCOUNTS AND PAYMENT TERMS ARE AVAILABLE TO ABOVE INSTITUTIONS.**

PLEASE ENQUIRE FOR QUANTITY DISCOUNTS.  
**WE WELCOME TELEPHONE AND TELEX ENQUIRIES!**



**MAKE YOUR INTERESTS PAY!!**

Train at home for one of these Career Opportunities

More than 8 million students throughout the world have found it worth their while! An ICS home-study course can help you get a better job, make more money and have more fun out of life! ICS has over 90 years experience in home-study courses and is the largest correspondence school in the world. You learn at your own pace, when and where you want under the guidance of expert 'personal' tutors. Find out how we can help YOU. Post or phone today for your **FREE INFORMATION PACK** on the course of your choice. (Tick one box only!)

Electronics <input type="checkbox"/>	Radio, Audio & TV Servicing <input type="checkbox"/>
Basic Electronic Engineering (City & Guilds) <input type="checkbox"/>	Radio Amateur Licence Exam (City & Guilds) <input type="checkbox"/>
Electrical Engineering <input type="checkbox"/>	Car Mechanics <input type="checkbox"/>
Elec. Contracting/Installation <input type="checkbox"/>	Computer Programming <input type="checkbox"/>
<b>GCE over 40 'O' &amp; 'A' level subjects</b> <input type="checkbox"/>	

Name: \_\_\_\_\_

Address: \_\_\_\_\_

P. Code \_\_\_\_\_



International Correspondence Schools,  
 Dept. EGS66, 312/314 High St., Sutton, Surrey  
 SM1 1PR. Tel: 01-643 9568 or 041-221 2926  
 (both 24 hours).



# P. V. TUBES

104 ABBEY STREET, (0254) 36521  
ACCRINGTON, LANCs BB5 1EE. 32611

## SONY PARTS

### SEMICONDUCTORS

Diode CV12E	GEN	2.34
Diode GH3F	KV-GEN	1.42
Diode IS1555	GEN	25
Diode U05G	KV1810UB	96
Diode V11N	KV1810UB	96
Diode 10E2	GEN	25
Thyristor SG-264A	KV-GEN	4.08
Thyristor SG629	KV1810UB	6.42
Thyristor SG-6533	KV-GEN = SG613	13.20
8X342	SLC7UB	4.08
CX104A	KV1810UB	5.28
CX136A	VTR-GEN	7.74
CX143A	SLC5/7UB	7.20
CX186	SLC5UB	2.34
M51231P	KV2200UB	2.34
STK2129	STRYX50L	13.20
TCP4621AF6	SLC6UB	13.87
TDA2578A	KV2752UB	3.24

Please ask for any part not listed.

UPC 1394C	KV2060/62U	2.34
UPD 546C107	SLC7UB	16.98
UPD 547C049	SLC7UB	8.94
TL494CN	SLC7UB	5.28
2SA 771	TAF5A	2.34
2SA 835	GEN	1.42
2SA 1027R	ICF-C820L	25
2SA 1175	SLC7UB	89
2SB 733	KV2204UB	96
2SB 740C	TCK88B	96
2SB 856	GEN	1.42
	SY8-724-375-01	25
2SC 403C	GEN	25
2SC 867A	GEN	2.34
2SC 1034	GEN	5.28
2SC 1061 =	GEN	2.94
2SC1986	GEN	5.28
2SC 1114	GEN	96
2SC 1124	GEN	3.18
2SC 1316	GEN	25
2SC 1362-7	GEN	25
2SC 1364	GEN	25
	SY8-729-341-34	7.38
2SC 1413A	KV-GEN	25
2SC 1475	KV1810UB	1.42
2SC 1982	GEN	1.42
	SY8-725-900-00	25
2SC 2009	GEN	7.38
2SC 2278	GEN	96
2SC 2335 Krt	SLC7	3.18
2SC 2369	SLC5/7UB	3.18
2SC 2551	KV-GEN	96
2SC 2785	AG-7UB	25
2SC 3153	KV2060UB	4.08
2SD 257	ST5150	2.34
2SD 725	KV2204/2704	8.94
2SD 773	BM715T	25
2SD 774	SL/HMK	96
2SD 870	KV2704E	6.42
2SD 1164	SLC6UB	96
2SD 1497-02	KV2252/2752	4.08
2SD 1497-06	KV2252/2752	4.08

### SUNDRIES

UHF Tuner BT-871	KV1810UB	37.20
Rooster Antenna	SLC7UB	31.38
RF Modulator	SLC6UB	60.38

### SONY REMOTE CONTROLS

SLC5UB	19.80
SLC6UB	17.40
SLC7UB	42.00

### VIDEO/AUDIO HEADS

Ace Assembly	SLC7UB	24.10
Ace Assembly	SLC6UB	47.22
	SYA-676-104-6A rep	6.20
	SYA-676-205-5A rep	6.20
Video Head DRS-21R	SLC9UB	43.20
Video Head DSR-35A	SLC20/30/40UB	41.34
Video Head DSR-36R	SLC5/C6/7UB	42.00
Video Head DSR-43A	SL8000UB	46.74
Head Record-Play-back	PP128-3602C/GEN	13.87
Head Record-Play-back	181-3602D/TC/HMK3000	4.12

### SPECIFIC COMPONENTS

Philips G8 knobs sm/ig	50
90° transistor	2.60
Thom 1591 speakers sm/ig	6.20
	6.20
Thom 1500 controls	59
390K frame 470K line	2.95
Focus control Thom/GEC	8.40
Thom 9000 focus unit	4.75
Thom 8500 focus unit	10.20
Thom Tx10 focus cont.	1.97
Decca bridge trans.	

### MECH. REPLACEMENT PARTS

Drum Assembly Main	SLC7UB	192.52
Idler Kit/Rewind Kit	SLC7/C5UB	5.95
Idler Kit/Rewind Kit	SLC6UB	3.95
Forward Assembly	SLC6UB	3.18
Gear Kit	SLC9UB	8.94
Guide Pin Kit	SLF1/C9UB	5.28
Pinch Roller	TC-GEN	9.60
Pinch Roller	TC204SD	1.42
Pinch Roller	HMK44/44B	1.42
Pinch Roller	TCK55	96
Cassette Holder		
Assembly	TCK44	1.42
Lever Forward		
Assembly	WM2	96
F/Wheel Assembly	WM2	3.18
Limiter Assembly	SLC7UB	2.34
Idler Assembly	SLC7UB/C5/3000	1.42
Brake Assembly	SLC7UB	1.42
Pulley Loading		
Thrust Bearing	SLC6UB	96
Assembly	HMP70	3.18
Screw Cassette Lid	WM2	25
Coil Spring	WM2	25
Battery Lid	WM2	96
Lid Timer	SLC7UB	96
Gear Kit	SLC9UB	96
Threading Gear	SLT6ME	96
C5 C7 Capstan Motor		34.00
C7 Drive Motor		32.95

### BELTS

Belt	WMR2	96
Rubber Belt	TC-GEN	96
Take Up Belt	TC-GEN	96
Drive Belt	TC-GEN	96
Midway Pull Belt	TC-GEN	96
Capstan Belt	TC92	96
Capstan Belt	TC135/136SD	96
Flat New Belt	TC186SD	96
Capstan Belt	TC-GEN	96
Capstan Belt	HST300	96
Take Up Belt	HMK3000UK	96
BelT Capstan	HMK3000UK etc	96
Fast Forward-Rewind		
Belt	VO2850P	1.62
Forward Belt	VO2850P	1.62
Motor Belt	VO2850P	1.62
Capstan Belt	VP200	4.32
Forward Belt	SLC7UB/SLC5UB	25
Capstan Belt	SL8000UB	96
Extension Belt	SL8000UB	2.34
Drum Belt	SL8000UB	1.52
Fast Forward Idler Belt	SLC7UB	96
Threading Belt	SLC7UB	25
Capstan Belt	SLC7UB/CS	96
Eject Belt	SLC7UB	25
Counter Belt	SLC7UB	25
Fast Forward Belt	SLT7ME	96
Forward Belt	SL8000UB	96
Belt	SLC6UB	96
Fast Forward Belt	SLC6UB	96
Counter Belt	SLC6UB	96
Threading Belt	SLC6UB	96
Relay Belt	SLC6UB	96
Capstan Belt	SLC6UB	96
Belt	PS-5520 etc	3.18

### SWITCHES

Switch, Filter	KV2022UB	96
Switch, P.B. Channel	1820/2 & 1340	18.66
Switch, Push Power	KV-GEN	1.20
Switch, Push	SL8000UB	96
Switch, Push Button		
Power	KV14/2060UB	3.68
Switch, Power	KV2022UB	4.08
Switch, Slide Record	SL8000UB	96
Switch, Slide Record-Playback	SL8000UB	1.42
Switch, Push	KV1612UB	4.08
Switch, Push	KV4	5.50
Button, Stop/Eject	WM-GEN	96
Knob, Control	SLC7UB	96

### MANUALS (Zero VAT)

Instruction Manual	SLC9UB	2.00
Instruction Manual	SLC6UB Mk 2	2.00
Instruction Manual	SLC7UB	2.00
Instruction Manual	SLC5UB	2.00
Instruction Manual	SL6UB	2.00
Instruction Manual	KV2212UB/E2	2.00
Instruction Manual	KV2705UB	2.00
Service Manual	HMK3000	8.25
Service Manual	KV1810UB Mk 1	8.25
Service Manual	KV1400UB	8.25
Service Manual	SLC7UB	8.25
Service Manual	SLC5UB	8.25
Service Manual	SLC6UB	8.25
Service Manual	SLC9UB	8.25
Service Manual	SLC6UB Mk 2	8.25

IF Gain module	9.00
C.D.A. Panel	20.00
G8 rear conv. panel	23.00
Decca 30 width cont.	50
Decca 2M2 HT cont.	25
Pye 731 HF choke	6.50
Delay lines DL20, DL60, DL50, DL700	2.20
CRT tube base	1.40
EHT final anode cap	5.50
6.3V CRT boost trans.	5.80
Focus rod	1.25
Focus holder	2.20
AFC unit G8	8.82
Decca Speaker 8R	3.75
G11 47k pot plus switch	85
15R fused res. G9	55
G11 line in coil	3.80
G11 pot G2 R.G.B.	5.30
G11 line scan panel	54.00
G11 power panel	37.50
G11 timebase panel	37.50
G11 bridge trans.	2.35
G11 EW correc. coil	1.95
G11 final anode lead	3.20
G11 focus unit	6.80
G11 39R 3W resistor	69
G11 RGB 10G diodes	69

## THORN/FERGUSON SEMI-CONDUCTORS

Diode GL4850	TX10	74
Thyristor TIC45X	TX9	1.18
Diode 19022W	TX9	43
(Thyristor T9053V)	TX9 = T9054V	1.10
(Thyristor T9054V)	TX9	6.81
AN6360	3V29	23.22
HA11741	3V32	7.10
M293	TX90	6.88
M50790SP	3V35	3.92
M54544L	3V32	4.88
MC13002	38030	2.74
MC14493	TX9/TX10	11.43
MM1219	3V36	3.44
TDA1236	TX10	6.00
TDA3652	TX90	5.84
TD4500	TX9/TX10/TX100	1.89
SL490	3V35	30
DTC144WF	ICE9000	3.20
R2540	TX90	69
TIP112H	TX9	3.43
T5051V	TX9	38
T6089V	TX100	1.46
T6071	TX9	3.64
T9063V	TX90	1.14
19064V	TX90	20.76
UP0553C 164	3V29	17.13
UP07519G 031 036	3V36	11.06
UP07538C 020	3V38	8.74
10 Volt T05	3V29	

### MANUALS Please check for availability

Service Manual	TCE1690/1691	5.60
Service Manual	TCE1790	1.14
Service Manual	TCE9600	10.05
Service Manual	TCE9800	7.54
Service Manual	TX9	29.04
Service Manual	TX10	40.00
Service Manual	TX90	11.30
Service Manual	TX100	11.20
Service Manual	3V00 Stocks in soon	17.50
Service Manual	3V16	26.24
Supplement to 3V00		
Stocks in soon	3V22	1.28
Service Manual	3V23	30.62
Service Manual	3V24	28.42
Service Manual	3V29	29.00
Instruction Manual	3V29	3.28
Service Manual	3V00	17.50
Instruction Manual	3V29	3.28
Service Manual	3V30	14.91
Instruction Manual	3V30	2.65
Service Manual	3V31	25.84
Instruction Manual	3V35	1.63
Service Manual	3V35/3V36	27.20
Supplement to 3V35	3V38	1.24
Supplement to 3V35/3V38		
3V38		90
3V42		23.94
3V43		30.72

### V.C.R. BELTS

Counter Belt 1	3292/3V00/3V16/3V22	60
Counter Belt 2	3292/3V00/3V16/3V22	60
Reel Drive Belt	3292/3V00/3V16/3V22	1.00
Relay Belt	3V00	2.79
Capstan Belt	3292/3V00/3V01/3V16/3V22	3.28
Unloading Belt	3292/3V00/3V16/3V22	60
Drum Motor Belt	3292/3V00/3V16/3V22	2.79
Cassette Drive Belt	3V23	60
Capstan Belt	3V29/3V30	1.62
Loading Belt	3V23	60
Loading Belt	3V29/3V30	60
Loading Belt	3V35/3V36/3V38	60
Tape Spool Drive		
Belt	3V35/3V36/3V38	60
Take Up Clutch Belt	3V29/3V30/3V35/3V36/3V38	60
Capstan Belt	3V35/3V36/3V38	1.21

### VIDEO HEADS

Upper Drum Assmb	3292/3V00	35.94
Upper Drum Assmb	3V22	35.94
Upper Drum Assmb	2200/3660/3V16/3V23/3V24/3V31/3V35/3V36/3V38/3V39	35.94
Upper Drum Assmb	3V29/3V30	35.74

### VIDEO LAMPS

Tuning Indicator	TX9	62
Lamp	3292/3V00	3.66
Cassette Lamp	3V16	1.53
Cassette Lamp		
Holder	3V16	60
Cassette Lamp	3V23	1.95
Cassette Lamp		
Holder	3V29/3V30/3V31/3V32	60
Cassette Lamp	3V29/3V30	1.41
Cassette Lamp	3V31/3V32	1.60

### PHILIPS KT3/K30 PARTS

KT3 positor	1.80
Mains electrolytic 225/25 380V	3.00
Selector unit Mod. 933	16.10
On/off switch Mod. 933	3.84
Tripler	12.80
Luminance chroma panel	28.00
2003 UF module	17.94
U321 IF module	16.20
R.G.B panel	12.87
Sound panel	10.62
Power panel	21.48
Mains input panel	17.16
Line sync panel	21.19
Mark II chroma panel	19.80
Sound module	10.20
LOPT	9.70
Focus unit	3.68

### V.C.R. MOTORS

Capstan Motor	3292/3V00/3V01/3V16	51.45
Drum Motor	3292/3V00/3V01/3V16/3V22	43.49
SMP Reel Motor	3V23	32.79
Cassette Housing		
Motor Assembly	3V23	18.32
Capstan Motor	3V23	52.81
Loading Motor	3V23/3V24/3V29/3V30	8.56
Reel Motor	3V29/3V30	27.32
Lower Drum Motor	3V29/3V30	32.79
Assembly	3V29/3V30	78.72
Cassette Motor	3V35/3V36/3V38	6.92
Motor Control Motor	3V35/3V36/3V38	5.95
Capstan Motor	3V35/3V36/3V38	23.90

### REMOTE HANDSETS

T723 Non Text	3767/3788	38.80
T725 Non Text	20A2/2282/3781/37041/37081/37101/3714/37351/37361/37371	19.40
T731 Text and Stereo	20A4/2284/37063/37093/37433/37493	20.01
T736 Text	20A3/2203/3795/3796/37003/37103/37353/37363/37373/37953/37963	31.60

### SWITCHES

On/Off Switch	TX9	2.98
On/Off Switch	TX10	2.74
Focus Unit		

# P. V. TUBES

104 ABBEY STREET, ACCRINGTON

TEL: 0254  
36521/32611

## SUNDRY VIDEO ACCESS.

VHS Drum Motor	25.50
VHS Capstan Motor	25.50
Sanyo 5000 Reel Motor	12.95
VHS Idler	5.95
Video Lamps	1.41
3V23 Lamps with Plug	1.95
Video Care Kit	3.50
Universal Copying Kit	5.50
Video Head Cleaner	90
Sharp Reel Motor	15.60
Reel Idler (Sharp)	2.48
381/383/386/9100/9300/9500	
Sanyo Reel Drive Pulley	6.95
JVC Clutch Ass.	6.95

## WE HAVE A FULL RANGE OF AERIALS AND ACCESSORIES FROM TRADE COUNTER AERIAL EQUIPMENT

Outdoor Splitter	5.50
Plastic Tape	50
F.M. Plugs	25
Set Top Aerial	2.30
Loop Aerial	1.00
Aerial Isolator Kit	2.08
Attenuator 6dB, 12dB, 18dB	1.80
27MHz Filter 50dB	2.10
Cable Clips 7mm	per 100 1.18
Single Outlets	80
Surface Splitter	1.70
A Splitter	70
100M Coax	15.00
Coax Plugs	per 10 1.80
1" U Bolts	30
J Bolts	25

## SUNDRY EQUIPMENT

Test Lead Set	4.20
Degaussing Coil Stick	19.00
Signal Ejector	4.00
Elect. Circuit Tester	1.50
5A Choc Bloc (12)	40
Fuse Wire 5A, 15A, 30A	05
4-way 13A Mains Conn.	5.00
Safe Block (mains)	8.50
13A Plug Top (box 10)	4.80
Probes (x10)	10.90
Probes (x1)	10.90
Micro Pliers	4.20
Micro Cutters	5.00
Phillips Switchable Probes (x1, 2x10)	13.25
Factory recon. Avo meters	119.00
Avo Battery	2.95
Vero Board	2.59
LG Solder Sucker	6.20
Solder 500g	7.00
D.I.Y. Solder	45
Solder Sucker Antistatic	5.40
Nozzles	81
Trim Tools	
Metal End	30
Solda Mop Strnd.	74
Sidcutters sm.	1.20
Long Nose Pliers	1.20
Surge Protector Plug	12.50
Quick Set Adhesive	75
Sm. Neon Screwdriver	40
Lg. Neon Screwdriver	65
I.C. Inserters	1.18
Automatic Wire Strippers	6.95
Scart Plugs	2.95
Scart Leads	3.50
TA81 Car Battery Leads/port. TV	1690/91 Thom 4.47
TA51 Car Battery Leads/port. TV	1613/1615 Thom 3.66
Car Battery Leads/port. TV Philips	3.95
Universal Car Accessory Cable	1.99
Dynascan 467 Rejuv. Testers	399
Dynascan 470 Testers	299

## FILAMENT LAMPS

<b>HES ROUND BULBS</b>	15p
L23m x D11mm	
6.5V 0.3A	
12V 2.2W	
<b>LILLIPUT (L.E.S.) BULBS</b>	12p
L20m x D5mm	
6V 0.025A	
12-14V 0.1A	
<b>CAPLESS LAMPS</b>	28p
L11mm x D4m	
6V 0.04A	
12V 0.04A	
<b>TUBULAR LAMPS CAPPED</b>	31p
L31mm x D6.3mm	
6.3V 0.15A	
6.3V 0.25A	
6.3V 0.3A	
8V 0.15A	
8V 0.25A	
8V 0.3A	
12V 0.15A	
12V 0.25A	
12V 0.2A	

## VIDEO PINCH ROLLERS

PANASONIC NV7000	4.38
PANASONIC NV8300-333-370-777	4.35
SANYO VT0300-VB57000	4.35
SANYO C7-J7-SL77	4.35
JVC TCE 3V00-01-06-16-23-24	
JVC HR2200-3320-3330	4.35
3660-1100-7700	4.35
AKAI VS9700	4.35
HITACHI VT5000	4.35
SHARP VC6300-6500	4.35

## VIDEO BELT KITS

VEKIT 1 AKAI JVC	VS9300-VS9500-VS9800	4.50
	HR3300/HR3320/HR3330/HR3360	3.00
	TCE 8903-3V00-3V16-3V22	3.50
VEKIT 2 PANASONIC	NV7000B/NV7200B	3.00
VEKIT 3 SONY	SLC5:SLC5EC:SLC5CH:SLC5E1:SLC5E:SLC5SA:SLC5UB:SLC7E:SLC7UB:SLC7EC:SLC7F:SLC7:SLC5:SLC7:SLT9MWER:SL8000AS:SL8000E:SL8000SA:SL8000JB:SL8000AN:SL8500:SL8600:SL8600A:SL3000UB	4.50
VEKIT 5 SONY	NV3000B	4.00
VEKIT 6 PANASONIC	NV3000B	3.00
VEKIT 7 SANYO	9300P	4.25
VEKIT 8 PANASONIC	NV2000B	3.75
VEKIT 9 PANASONIC	NV8500B/NV8510B:	
	V011	4.25
VEKIT 10 TOSHIBA	V8600	3.00
VEKIT 11 SHARP	VC7300	3.50
VEKIT 12 SHARP	VC6300/VC6600	4.00
VEKIT 13 SANYO	VT5000	1.95
VEKIT 14 SANYO	VT5000	2.50
VEKIT 15 JVC	HR7650	2.50
VEKIT 19 HITACHI	VT8000	1.12
VEKIT 20 HITACHI	VT11/33	2.15
VEKIT 21 HITACHI	9500	1.12

## VIDEO IDLER TYRES

Sony	O Dia	I Dia	Width	
SONY	23.7	17.4	4.9	50p
SONY	24.2	18	5.1	50p
HITACHI	31.8	25	4.9	52p
HITACHI	39.5	30	4.2	52p
PANASONIC	37	27	3.9	52p
PANASONIC	34.5	27	3.1	50p
AKAI	26	20	3.9	50p
JVC	32.8	3.4	3.9	56p
JVC	23.9	4.8	4	56p

## REPAIR KITS

Remote control handsets for Philips sets KT3/K30 chassis inc. foil unit button matrix and instructions.

Phillips part numbers:  
Foil 212 275 82 or 212 275 83.

Button matrices: 432 370 37 or 432 370 38.

No. 1 without Teletext.  
No. 2 with Teletext

£4.50

## REMOTE CONTROL HAND UNITS

Some are original some are compatible types.

DECCA 100/101 US Non T.Text	US8513	23.80
GRUNDIG TELEPILOT 12 IR	RTP20	13.87
GRUNDIG TELEPILOT 8 IR	RTP05	25.10
GRUNDIG TELEPILOT 160 IR	RTP06	25.10
GRUNDIG TELEPILOT 300 IR	RTP07	18.87
PHILIPS G11 US Non Text	US8263	22.00
PHILIPS G11 8 way IR Text	IR8435	23.80
PHILIPS G11 US 31 Button	69117187	27.00
PHILIPS G11 US 2 function	US8518	21.00
PHILIPS KT3/30 IR Text 1234	IR1234	19.87
PHILIPS KT3/30 IR Non Text 1201	IR1201	19.87
THORN TX10/JVC IR Text	TP8431R	22.00
Remote Control Tester		29.94

## DATA BOOKS (Zero VAT)

Pair of A-Z/N2S TV180	8.50
LIN IC Books (data only not Equiv.) LINI	5.95
IC equivalent booklet E3.25 and transistor equivalent booklet E3.25	
TDV1 Trans. Data Dictionary	7.50

## TURNTABLE DRIVE BELTS ALL £1.20

TB42 Most Thorens Models	
TB23 Most Philips Models	
TB50 Most Garrard Models	
TB70 Most Hitachi Models	
TB60 Some Sanyo Models	
TB01 Most Panasonic, Sony, Pioneer, Technics and Sansul.	
TB03 Most BSR	

## VIDEO HEADS

3HSS UHS	30.00
4HS VHS	31.00
PS3B Beta/Sony	35.00
Philips V2000	64.00
Philips 1700	64.00
Sanyo 9300/9455/9500	53.00
Sanyo 5000/5300/5400	53.00
Toshiba V5470A BDP	50.00
Toshiba 9600 Upper Ass.	12.50
Toshiba 9600	50.00
Sharp 2300	58.00
Sharp 6300	58.00
Sharp 7300/7700/7750	58.00
Sharp 8300	58.00
Sharp 3300/9700	56.00
Hitachi HVI1	35.62
Hitachi VT33E	35.62
GEC 4004	35.62
Hitachi VT11/GEC 4100	35.62
Beta eccentricity gauge	50.00

## VIDEO TAPE

SKC E180	3.20
L750	3.20
Scotch E30	3.66
E60	4.00
E120	5.00
E180	4.50
Beta L750	5.80
240 While	6.20
360 Stocks	8.30
480 Last	10.21
LVC 1700/ Philips 1200	17.50

## NEW LABGEAR

* CM7271-MHA 15db	8.66
* CM7274 4 Way Dist.	21.45
* CM7082 UHF VHF DA	65.69
* CM7080/10 UHF MHA	15.71

## SERVICE AIDS

SERVISOL Freeze-It	1.20
SUPER SERVISOL	1.04
SERVISOL Foam Cleanser	1.02
SERVISOL Plastics Seal	1.14
SERVISOL Silicone Grease	1.30
SERVISOL Tubes Silicone Grease	1.66
SERVISOL Aero Klene	1.94
SERVISOL Aero Duster	1.28
SERVISOL Excel Polish	96
SERVISOL Video Head Cleanser	90
Super 40	1.66
Fire Extinguisher 640G	3.08
Heat Sink Compound 25G	1.10
Silicone Rubber Tube 110G	2.98
Solda Mop standard reel	77

## ANTEX SOLDERING EQUIPMENT

C15W Iron 240V	6.20
C240 Element	2.75
Bits 102	1.10
Bits 106	1.10
Bits 820	1.10
Bits 821	1.10
CS17W Iron 240V	6.40
CS240 Element	2.75
Bits 1100	1.10
Bits 1106	1.10
Bits 1106	1.10
XS25W Iron 240V	6.50
XS240 Element	2.75
Bits 50	1.10
Bits 51	1.10
Temp. Controlled	
30W Iron CSTC	16.95
40W Iron XSTC	16.95
Unit for above TCSU1 Stand	2.10
MLXS Auto Repair Kit	8.40
Cordless Gas Iron	19.50
Tips for Gas Iron	5.00
25 Watt Philips Iron	5.50

## WELLER

Heat gun	15.95
Heat gun tips (pair)	57
3/16" Iron tips 25W (MT5)	57

## AUDIO HEADS AND MOTORS

Mono record/playback	4.32
Stereo playback	4.79
Stereo record/playback	4.99
Stereo record/playback (Dolby)	6.90
Mono/stereo erase	2.25
Electronic/rotation clockwise motors	
6V MD6515	4.95
9V MD9516	4.95
12V MD12517	4.95

## CASSETTE DRIVE BELTS

35m 35	46mm 37	57m 37
66m 39	110m 59	76m 43
90m 43		

## SOCKETS ELECTRICAL BA

320A Single Gang	1.30
320B Single Switched	1.95
320C Two Gang	2.53
320D Two Switched	3.92
Switches	
320E One Gang/One Way	80
320F One Gang/Two Way	1.05
320G Two Gang/Two Way	1.78

## CABLES 100m

F031 2 Core Round .75mm <sup>2</sup>	15.47
F032 3 Core Round .5mm <sup>2</sup>	15.75
F035 3 Core Round 1.25mm <sup>2</sup>	28.21
F041 Speaker 7/0 2mm	3.90
Coaxial 75R	13.50

We have a fully equipped computer store - Come and visit us -



**WE WILL ONLY SUPPLY TOP QUALITY, BRANDED COMPONENTS. REPUTATION COUNTS WITH US**

**G.G.L. COMPONENTS**  
 108 SCOTLAND ROAD, CARLISLE, CUMBRIA CA3 9EY  
 PHONE (0228) 20358/39693

**BUY WITH**



E.H.T. TRAYS	
DECCA 80	7.20
DECCA 100	7.35
ITT CVC 20/30	6.85
PHILIPS G8-550	7.90
PHILIPS KT3	7.95
RBM T20/T22A	7.35
THORN 8500/8800	7.60
THORN 9000	8.70
Universal	5.95

INTEGRATED CIRCUITS	TYPE	PRICE (£)
AN214	STK0039	6.45
AN301	STK0040	5.95
AN303	STK0050	7.50
AN305	STK0077	7.25
AN7110	STK0078	7.45
AN7114E	STK082	9.75
AN7115	STK2129	8.50
AN7116	STK415	9.66
AN7145	STK430	7.75
BA312	STK432	5.95
BA511A	STK433	6.50
BA521	STK435	6.75
BA532	STK437	7.25
BA536	STK439	7.55
HA1166	STK441	8.50
HA1322	STK459	7.35
HA1338	STK461	7.95
HA1339	STK463	9.30
HA1342A	STK465	9.95
HA1366 W/W/R	TA7193P	4.30
HA1374	TA7204P	1.90
HA1377	TA7205AP	1.40
HA1388	TA7222AP	1.95
HA1397	TA7223P	2.85
LA1201	TA7227P	2.85
LA1230	TA7310	1.55
LA1365	TA7313	1.45
LA3350	TAA550	4.3
LA4101	TAA551	4.3
LA4102	TAA552	4.3
LA4400	TAA553	4.3
LA4430	TAA554	4.3
LA4440	TAA555	4.3
LA4445	TAA556	4.3
LA4460	TAA557	4.3
LA4461	TAA558	4.3
MB3712	TAA559	4.3
MB3713	TAA560	4.3
ML2318	TAA561	4.3
ML2328	TAA562	4.3
SA11250	TAA563	4.3
SA11251	TAA564	4.3
SA11252	TAA565	4.3
SA11564	TAA877	4.3
SA11565	TAA878	

# HUSSAIN CENTRAL TV LTD

## SALE SALE SALE OF THE CENTURY

BEST QUALITY AT THE LOWEST PRICES IN BRITAIN TODAY

G11 · 660	£25	ITT CVC 20/30	£15
PYE G11	£30	DECCA 80/100	£15
G11 REMOTE (with hand set)	£45	ITT REMOTE (with hand set)	£30
G11 TEXT (with hand set)	£55	TX TEXT (with hand set)	£55
G11 ELECTRONIC TUNER	£30	THORN 9000 REMOTE	£15
THORN 9600	£25	THORN 9200	£27
THORN 8800	£10	THORN 9800	£15
PYE 222	£10	G8 22"	£10
GEC SOLID STATE	£10	GEC STARLINE	£15

**MANY MORE LATE MODEL TVs IN STOCK INC.  
REMOTE, TEXT, STEREO TEXT AND 14", 16" PORTABLES**

*All TVs have excellent cabinets*

**VHS: Working.** Bring your own tape and try them yourself at **£65**

**Untested Electronic VHS £90**

**Working Electronic VHS £135** Ferguson 3V29, Hitachi 8000, J.V.C. 7200

### ALSO IN STOCK

**PANASONIC** 7200, 7000, 2000, 2010, 366, NV777

**HITACHI** VT14, VT11, 9700, 9500, 8700, 8500, 8300

**FERGUSON** 3V31, 3V30, 3V23

**ELECTRONIC Beta Full working £60**

**Untested Beta from £35**

**PLUS MANY MORE LATE MODEL VIDEOS IN STOCK**

Prices are subject to 15% VAT

*Deliveries arranged on quantity or call at our branches  
for fast and friendly service from the professionals*

**BIRMINGHAM**  
48-52 PERSHORE ST.  
021-622 1023  
021-622 1517

**PRESTON**  
UNIT 439  
OAKSHOTT PLACE  
WALTON SUMMIT IND. EST.  
M6 JUNCTION 29.  
0772 312101

**LONDON**  
CEDAR HOUSE  
NOBEL RD.  
ELEY ESTATE  
EDMONTON N18 3BH.  
01-807 4090  
01-884 1314

**CHEPSTOW**  
UNIT 4  
BULWARK IND. EST.  
GWENT.  
0291 271000



# SPECIAL OFFER THIS MONTH

PHILIPS YEARS AHEAD  
THE CREDIT CARD CALCULATOR  
SOLAR POWERED £6.00

NEW PHILIPS SBC 1833 Solar & Battery Powered Calculator £10.00

## NEW PANELS

K30 Mains Switch remote	£1.00
K35 Mains Switch remote	75p
K35 Aerial Socket and Plug in Lead to Tuner	£1.50
KT3-K30 Slider Pots 4.7ku 47ku	20p each
LARGE Focus Pots Fits Pvc, GEC, ITT, Decca	50p
G8 Power Supply Panel	£4.00
THORN 4000 LOPT Panel	£15.00
THORN 9000 Line Panel	£12.00
THORN 8000-8500-8800 Decoder	£10.00
GLASS BEADS Diodes 200v/1.2A	25 for £1.00
G11 IF Panel	£9.00
THORN 9600 Line Panel	£12.00
G11 Decoder Panel	£8.00
POWER SUPPLY 731	£6.00
G11 611 Condenser 470/250V ITT	£1.50
G9 Power Panel	£3.50
G8 Line Panel	£12.00
G8 6 Push Button	£9.00
KT4-KT3-K30 Handset Replacement	£8.00
HT520 METER 20,000 Fuse Diode Protector Logic Test Facility	£15.90
9000 SERIES Decoder 01 929 014 080 Thorn	£5.00
THORN TX remot panel. 51 C. ML923-SL 490-MC14528B-MC14493P-SL470 & Main Trans	£5.00
20AX GEC LOPT Panel with Split Diode	£4.00
LOPT Split Diode 2432871	£7.00
RANK T20 Focus Pot	75p
RANK 718 Focus Pot	£1.00
THORN 9000 LOPT Panel	£12.00
28" LOPT Split Diode 2432301	£8.00
16" LOPT Split Diode 2433481	£6.00
Ex Panel Split Diodes 2432871/2432981	£5
HITACHI Mains Switch	50p
HITACHI AE Socket	30p
1 CONDENSER Axial Leads 450 A/C 1200 D/C	15p
MAINS TRANSFORMER 240v in/20v/8v	£1.00
GREEN FLAT, NEC. LED's	3p each 100 for £2
12+12V 2.RVA Print 1"x1"	75p
8+8V 1 Amp Print	75p
HITACHI 6 x 4 - 80 Speaker	50p
ET596 UHF V/CAP Tuner, small	£2.50
FIDELITY Panels with I.C.	£1.00
FIDELITY LOPT Split Diode AT2076/80	£3.00
FIDELITY FBS 1245AE LOPT Mono	£1.00
FIDELITY Split Diode FCC2015BE	£5.00
HI-FI MICROPHONE N8501 Philip	£8.00
G8 TUNER V/CAP on Panel	£3.50
G8 SPEAKER	75p
4000 TRIPLERS	£3.50
9,000 SPEAKER	£1.00
5 AMP METERS, AC, DC	£2.00
THORN 9000 Sound OP Panel	£30p
ONE I.C. K35 Decoder	£7.00
THICK FILM, Hitachi RB-32 4A	£2.00
K30 IF/K35 IF	£3.00
THICK FILM, Hitachi Frame	£5.00
THORN Lopt 8500-8800	£4.00
TX9 THORN Tuner Panel with ICS Pots	£3.00
80 Ω THORN Speaker	15p
Split Diode 2433752	£6.00
BY223 Replacement	30p
THORN CHASSIS 1600-1700 Series Mono	£10.00
THORN 1600 Rec. & Anode Cap	50p
KT3-K30 Slider Pots 4.7k/47kC	£1.00 for 10
ET-614 UHF V/CAP Tuner	£2.00
6 x 2 1/4 SPEAKER 5W Hitachi 80	50p
K35 20 Turn Pots	6p each
HITACHI & GEC 20k Pots	20 for £1.00
KT3 K30 Speaker	30p
K35 Sound O/P Panel Plug in	£3.00
K35 12 way Push Button Unit	£1.50
K35 L.O.P.T. Split Diode	£6.00
RANK T20 Front Panel	£6.00
G8 6 Button Unit, New Type	£9.00
6 off LED DISPLAYS, Mixed	£1.00
HAND SET TESTER, Infra Red	£8.00
PHILIPS SBC 471 2 Way Stereo Headphone with Volume Controls	£17.00
AERIAL SPLITTER with filter	£1.00
DYNAMIC STEREO HEADPHONE EM 6146	£10.00
PHILIPS UNI DIRECTIONAL Dynamic Microphone	£10.00
20 TURN POT'S with Band Switch	10p
PUSH BUTTON Mains Switch with Screw Holes Fixing	4 for £1
PYE 713 Line Trans	£4.50
PYE 731 Line Trans	£3.50
800v DIODES at 3 amps. Glass Beads	6p each, 20 for £1.00
PYE 6 Touch Button Unit for G11 with IC and Cable Forms	£10.00
KT3 Line Output Transformer	£5.00

# SENDZ COMPONENTS

63 BISHOPSTEIGNTON,  
SHOEBURYNES, ESSEX SS3 8AF.

SAME DAY SERVICE

All items subject to availability. No Accounts: No Credit Cards. Postal Order/  
Cheque with order. Add 15% VAT, then £1 Postage. Add Postage for Overseas.

Callers: To shop at

212 LONDON ROAD, SOUTHEND. Tel. 0702-332992

Open 9-1/2.30-6. G.V.M.T. + school orders accepted on official headings. Add 10% handling charge.



# CHROMOVAC

## QUALITY REBUILDS

**SPECIAL OFFERS**  
ON  
INLINE

Get on the hot-line today!

SUPERIOR QUALITY TUBES **061 681 2959**  
**DELTA RE-BUILDS**  
most types of Inline Re-builds or  
new ex-stock  
PRICES SUBJECT TO  
GLASS EXCHANGE

### Delta Rebuilds

Up to 19"	£28
Up to 22"	£30
Up to 26"	£34
110° up to 22"	£34
110° up to 26"	£38
Low focus	+£2
A47 342 New	£28
17FHP New	£30
470EHB New	£30
Delta only. Less 5% +	

### Inline Rebuilds

Up to 22" .. From	£40
Up to 26" .. From	£45
A56 - 540x	£56
A66 - 540x	£58
Bonded Coil	+£5

ALL SIZES OF NEW AND  
REBUILT MONO TUBES  
AT COMPETITIVE PRICES

### IN LINE TUBES EX-STOCK SELECTION NOT REBUILDS

Please enquire types not listed

370 HFB-A37-590	£45	AXT 56-001	£62
370 HUB	£45	660 AB	£65
AXT 37-001	£45	A67-701	£65
420 CSB	£45	670 CZB	£65
420 EDB-A42-590	£45	A66-540 with coil	£85
420 EZB	£45	420FSB	£55
420 ERB	£45		
470 KUB	£50		
510 UFB/A51-590	£55		
510 VSB	£60		
AXT 51-001	£60		
560 DYB-560 DTB	£62		
560 EGB	£62		
560 CGB	£62		
560 DMB	£62		

QUANTITY  
DISCOUNT  
AVAILABLE  
Ask for details

★ ASK FOR DETAILS. OUR TECHNICAL DEPT.  
WILL ADVISE YOU ON PROBLEMS YOU MAY  
ENCOUNTER ON FITTING INLINE TUBES  
DELIVERY: Ex stock items immediate dispatch on receipt of order.  
Others allow 14 days.

THE COMPANY WHO PUT HIGH STANDARDS FIRST

# CHROMOVAC

CHROMAVAC LTD., PUMP STREET,  
HOLLINWOOD, OLDHAM OL9 7LR

Ask for Mr Butterworth ON: 061-681 2959



# EAST CORNWALL COMPONENTS



NEW 1986 CATALOGUE is now available - range of components greatly increased - over 136 pages fully illustrated. Price £1.00 per copy (free upon request with orders over £15). Includes 50p Credit Note, Special Offer Sheets, Order Form and Pre-Paid Envelope. Order your copy now - will be sent within 7 days.

**ORXY PORTASOL**  
PORTABLE GAS SOLDERING IRON  
Powered by ordinary lighter fuel. 60 mins. cont. use, adj. temp. 10/60W. Price £13.90

**CHART RECORDER SPECIAL**  
Brand new 3 channel pen recorders complete with charts. Full spec. upon request. Once only price £40 + £10 p&p + VAT.

**SERVICE AIDS**  
Switch Cleaner 1.24  
Circuit Freezer 1.40  
Foam Cleanser 1.14  
Aero Kleene 1.14  
Plastic Seal 1.34  
Excel Polish 1.16  
Antistat Spray 1.24  
Aero Duster 1.48  
Super 40 1.86  
Video Head Cleaner 1.86

**SELECTION**  
1.10 XS25 W iron kit/complete with steel & plug attached 10.00  
1.50 CS 18W, as above 9.90  
1.66 Antex 15W iron 5.25  
Antex 18W iron 5.90  
Antex 25W iron 5.75  
Antex elements 2.75  
Antex bits 0.90  
Antex stands 2.10  
Soldersucker 4.50  
Spair nozzles for 1.02  
Soldersucker 0.65

**SONY T.V. & VIDEO SPARES**  
Kider Kit SL5.SLC7 (Rewind Kit) A-670-634-8A SL6 (Rewind Kit) A-670-639-1A £4.80  
Video Head SLC7B A-676-208-8A £3.06  
SL5.SG6C7 A-676-212-9A £45.05  
Motor Kit MT General X-354-931-41 £14.44  
Limiter Assembly SLC7UB X-363-311-00 £2.45  
Power Switch KV General 1-554-820-11 £5.50

Diodes ICs Thyristors Belts Transistors Switches Remote Controls Instruction & Service Manuals  
**POTENTIOMETERS**  
Carbon Track Rotary 0.25W Log & 1 in values. All 1/4in Spindle 20ml Body dia Shaft 2" long  
4K7 2M2 Single Gang Log .40 10/3.50  
1K - 2M2 Single Gang Lin .30 10/3.50  
5K - 2M2 Single Gang DP Switch Log 1.05 10/9.50  
5K - 2M2 Double Gang Log & Lin 1.25 10/10.50

**VALVES**  
KT88(G.E.C.) 19.00  
PC32 3.00  
PC900 1.40  
PC888 0.80  
AC231 4.50  
AC241 1.98  
DAF96 1.98  
DF96 2.95  
DK96 2.95  
DM71 2.65  
DY86/87 0.85  
DY807 0.85  
CV850 2.80  
CV4015 2.50  
E180F 6.50  
EAB0C80 0.90  
EAF42 1.50  
EB91 1.30  
EB41 1.30  
EBF80 2.00  
ECC81 1.00  
ECC82 1.00  
ECC83 1.00  
ECC84 1.00  
ECC85 1.00  
ECC86 1.00  
ECC88 1.25  
ECC89 1.00  
ECC90 1.00  
ECC91 1.00  
ECC92 1.00  
ECC93 1.00  
ECC94 1.00  
ECC95 1.00  
ECC96 1.00  
ECC97 1.00  
ECC98 1.00  
ECC99 1.00  
ECC100 1.00

**JUNE SPECIAL OFFER**  
4-WAY EXTENSION SOCKET - 3 pin Sockets - fused and with neon indicator  
PRICE ..... £3.50 each  
With orders of £5.00 and over - only one per order  
**WATCH FOR JULY SPECIAL OFFER**

**DRY CELL BATTERIES**  
AA 1.5V 15p ea 10/12p ea  
C 1.5V 70p pack of 2  
10/68p pack of 2  
D 1.5V 80p pack of 2  
10/75p pack of 2  
PP3 9V 65p ea 10/60p ea  
Button Type for Multimetres - Set of 3 for £1.50

**RECHARGEABLE BATTERIES**  
AA (HP7) 95p 10/ 85p each  
C (HP11) £2.14 10/£1.98 each  
D (HP2) £2.30 10/£2.10 each  
PP3 £3.75 10/£3.65 each

**RESISTORS - CARBON FILM 5%**  
1W 10R to 10M (E12 Range) 2p each 15p/10 75p/100  
1/2W 2R2 to 10M (E24 Range) 2p each 15p/10 75p/100  
1W 10R to 2M2 (E12 Range) 7p each 55p/10 6.00/100  
2W 10R to 2M2 (E12 Range) 8p each 70p/10 6.00/100

**RESISTOR KITS - each value in individual y packed**  
1W pack 10 each value E12 - 10R to 1M 610 pieces 3.75  
5W pack 5 each value E12 - 10R to 1M 305 pieces 5.25  
1/2W pack 10 each value E12 - 2R2 to 2M2 730 pieces 7.95  
1/2W pack 5 each value E12 - 2R2 to 2M2 365 pieces 4.75  
1W pack 5 each value E12 - 2R2 to 1M 353 pieces 15.25  
2W pack 5 each value E6 - 10R to 2M2 317 pieces 18.50


**RESISTORS - WIREWOUND. Generally 5%**  
2.5W - 0.22 to 270R - Available in preferred values 0.15  
4W - 150 to 10K - Available in preferred values 0.18  
7W - 0.47R to 22K - Available in preferred values 0.18  
11W - 1R to 22K - Available in preferred values 0.18  
17W - 1R to 22K - Available in preferred values 0.24

**FUSES Prices per 10**  
20mm Quick Blow. 100, 125, 160, 200, 250, 315, 400, 500, 630, 800mA, 1, 1.25, 1.6, 2, 2.5, 3.15, 4, 5, 6.3A, 40p. 20mm Time Delay. 100, 125, 160, 200mA £1.80, 250, 315, 400, 500, 630, 800mA £1.00, 1, 1.25, 1.6, 2, 2.5, 3.15, 4, 5, 6.3A 85p. 1\* Mains. 2, 3, 5, 7, 10, 13A 85p.

**REPLACEMENT TV MAINS DROPPERS**  
GEC2010 8R + 15R + 17R + 70R + 63R + 188R 0.95  
GEC 2018 10R + 15R + 19R + 70R + 188R 1.15  
Philips G8 2.2R + 68R 0.80  
Philips G9 6R + 124R + 84R 0.80  
Philips 300 118R + 148R (with link) 0.68  
RRI A640 250R + 14R + 156R 50W 1.05  
RRI A816 302R + 70R + 6.2R 0.78  
Thorn 1500 350R + 20R + 148R + 1.5K + 317R 1.34  
Thorn 3000/3500 6R + 1R + 100R Fused 0.93  
Thorn 500 56R + 1K + 47R + 12R 0.95  
Thorn 8500 1K5 + 40R + 50R 1.28

**TRANSISTORS - DIODES**

Type	Price (£)						
BC516	0.48	BC118	0.16	BC178	0.26	BU126	1.40
BC547	0.12	BC119	0.28	BC180	0.12	BU133	1.90
BC548	0.10	BC120	0.28	BC181	0.10	BU204	1.30
BC549	0.10	BC121	0.28	BC182	0.12	BU206	1.30
BC550	0.10	BC122	0.28	BC183	0.10	BU208	1.30
BC551	0.10	BC123	0.28	BC184	0.10	BU210	1.30
BC552	0.10	BC124	0.28	BC185	0.10	BU212	1.30
BC553	0.10	BC125	0.28	BC186	0.10	BU214	1.30
BC554	0.10	BC126	0.28	BC187	0.10	BU216	1.30
BC555	0.10	BC127	0.28	BC188	0.10	BU218	1.30
BC556	0.10	BC128	0.28	BC189	0.10	BU220	1.30
BC557	0.10	BC129	0.28	BC190	0.10	BU222	1.30
BC558	0.10	BC130	0.28	BC191	0.10	BU224	1.30
BC559	0.10	BC131	0.28	BC192	0.10	BU226	1.30
BC560	0.10	BC132	0.28	BC193	0.10	BU228	1.30
BC561	0.10	BC133	0.28	BC194	0.10	BU230	1.30
BC562	0.10	BC134	0.28	BC195	0.10	BU232	1.30
BC563	0.10	BC135	0.28	BC196	0.10	BU234	1.30
BC564	0.10	BC136	0.28	BC197	0.10	BU236	1.30
BC565	0.10	BC137	0.28	BC198	0.10	BU238	1.30
BC566	0.10	BC138	0.28	BC199	0.10	BU240	1.30
BC567	0.10	BC139	0.28	BC200	0.10	BU242	1.30
BC568	0.10	BC140	0.28	BC201	0.10	BU244	1.30
BC569	0.10	BC141	0.28	BC202	0.10	BU246	1.30
BC570	0.10	BC142	0.28	BC203	0.10	BU248	1.30
BC571	0.10	BC143	0.28	BC204	0.10	BU250	1.30
BC572	0.10	BC144	0.28	BC205	0.10	BU252	1.30
BC573	0.10	BC145	0.28	BC206	0.10	BU254	1.30
BC574	0.10	BC146	0.28	BC207	0.10	BU256	1.30
BC575	0.10	BC147	0.28	BC208	0.10	BU258	1.30
BC576	0.10	BC148	0.28	BC209	0.10	BU260	1.30
BC577	0.10	BC149	0.28	BC210	0.10	BU262	1.30
BC578	0.10	BC150	0.28	BC211	0.10	BU264	1.30
BC579	0.10	BC151	0.28	BC212	0.10	BU266	1.30
BC580	0.10	BC152	0.28	BC213	0.10	BU268	1.30
BC581	0.10	BC153	0.28	BC214	0.10	BU270	1.30
BC582	0.10	BC154	0.28	BC215	0.10	BU272	1.30
BC583	0.10	BC155	0.28	BC216	0.10	BU274	1.30
BC584	0.10	BC156	0.28	BC217	0.10	BU276	1.30
BC585	0.10	BC157	0.28	BC218	0.10	BU278	1.30
BC586	0.10	BC158	0.28	BC219	0.10	BU280	1.30
BC587	0.10	BC159	0.28	BC220	0.10	BU282	1.30
BC588	0.10	BC160	0.28	BC221	0.10	BU284	1.30
BC589	0.10	BC161	0.28	BC222	0.10	BU286	1.30
BC590	0.10	BC162	0.28	BC223	0.10	BU288	1.30
BC591	0.10	BC163	0.28	BC224	0.10	BU290	1.30
BC592	0.10	BC164	0.28	BC225	0.10	BU292	1.30
BC593	0.10	BC165	0.28	BC226	0.10	BU294	1.30
BC594	0.10	BC166	0.28	BC227	0.10	BU296	1.30
BC595	0.10	BC167	0.28	BC228	0.10	BU298	1.30
BC596	0.10	BC168	0.28	BC229	0.10	BU300	1.30
BC597	0.10	BC169	0.28	BC230	0.10	BU302	1.30
BC598	0.10	BC170	0.28	BC231	0.10	BU304	1.30
BC599	0.10	BC171	0.28	BC232	0.10	BU306	1.30
BC600	0.10	BC172	0.28	BC233	0.10	BU308	1.30
BC601	0.10	BC173	0.28	BC234	0.10	BU310	1.30
BC602	0.10	BC174	0.28	BC235	0.10	BU312	1.30
BC603	0.10	BC175	0.28	BC236	0.10	BU314	1.30
BC604	0.10	BC176	0.28	BC237	0.10	BU316	1.30
BC605	0.10	BC177	0.28	BC238	0.10	BU318	1.30
BC606	0.10	BC178	0.28	BC239	0.10	BU320	1.30
BC607	0.10	BC179	0.28	BC240	0.10	BU322	1.30
BC608	0.10	BC180	0.28	BC241	0.10	BU324	1.30
BC609	0.10	BC181	0.28	BC242	0.10	BU326	1.30
BC610	0.10	BC182	0.28	BC243	0.10	BU328	1.30
BC611	0.10	BC183	0.28	BC244	0.10	BU330	1.30
BC612	0.10	BC184	0.28	BC245	0.10	BU332	1.30
BC613	0.10	BC185	0.28	BC246	0.10	BU334	1.30
BC614	0.10	BC186	0.28	BC247	0.10	BU336	1.30
BC615	0.10	BC187	0.28	BC248	0.10	BU338	1.30
BC616	0.10	BC188	0.28	BC249	0.10	BU340	1.30
BC617	0.10	BC189	0.28	BC250	0.10	BU342	1.30
BC618	0.10	BC190	0.28	BC251	0.10	BU344	1.30
BC619	0.10	BC191	0.28	BC252	0.10	BU346	1.30
BC620	0.10	BC192	0.28	BC253	0.10	BU348	1.30
BC621	0.10	BC193	0.28	BC254	0.10	BU350	1.30
BC622	0.10	BC194	0.28	BC255	0.10	BU352	1.30
BC623	0.10	BC195	0.28	BC256	0.10	BU354	1.30
BC624	0.10	BC196	0.28	BC257	0.10	BU356	1.30
BC625	0.10	BC197	0.28	BC258	0.10	BU358	1.30
BC626	0.10	BC198	0.28	BC259	0.10	BU360	1.30
BC627	0.10	BC199	0.28	BC260	0.10	BU362	1.30
BC628	0.10	BC200	0.28	BC261	0.10	BU364	1.30
BC629	0.10	BC201	0.28	BC262	0.10	BU366	1.30
BC630	0.10	BC202	0.28	BC263	0.10	BU368	1.30
BC631	0.10	BC203	0.28	BC264	0.10	BU370	1.30
BC632	0.10	BC204	0.28	BC265	0.10	BU372	1.30
BC633	0.10	BC205	0.28	BC266	0.10	BU374	1.30
BC634	0.10	BC206	0.28	BC267	0.10	BU376	1.30
BC635	0.10	BC207	0.28	BC268	0.10	BU378	1.30
BC636	0.10	BC208	0.28	BC269	0.10	BU380	1.30
BC637	0.10	BC209	0.28	BC270	0.10	BU382	1.30
BC638	0.10	BC210	0.28	BC271	0.10	BU384	1.30
BC639	0.10	BC211	0.28	BC272	0.10	BU386	1.30
BC640	0.10	BC212	0.28	BC273	0.10	BU388	1.30
BC641	0.10	BC213	0.28	BC274	0.10	BU390	1.30
BC642	0.10	BC214	0.28	BC275	0.10	BU392	1.30
BC643	0.10	BC215	0.28	BC276	0.10	BU394	1.30
BC644	0.10	BC216	0.28	BC277	0.10	BU396	1.30
BC645	0.10	BC217	0.28	BC278	0.10	BU398	1.30
BC646	0.10	BC218	0.28	BC279	0.10	BU400	1.30
BC647	0.10	BC219	0.28	BC280	0.10	BU402	1.30
BC648	0.10	BC220	0.28	BC281	0.10	BU404	1.30
BC649	0.10	BC221	0.28	BC282	0.10	BU406	1.30
BC650	0.10	BC222	0.28	BC283	0.10	BU408	1.30
BC651	0.10	BC223	0.28	BC284	0.10	BU410	1.30
BC652	0.10	BC224	0.28	BC285	0.10	BU412	1.30
BC653	0.10	BC225	0.28	BC286	0.10	BU414	1.30
BC654	0.10	BC226	0.28	BC287	0.10	BU416	1.30
BC655	0.10	BC227	0.28	BC288	0.10	BU418	1.30
BC656	0.10	BC228	0.28	BC289	0.10	BU420	1.30
BC657	0.10	BC229	0.28	BC290	0.10	BU422	1.30
BC658	0.10	BC230	0.28	BC291	0.10	BU424	1.30
BC659	0.10	BC231	0.28	BC292	0.10	BU426	1.30
BC660	0.10	BC232	0.28	BC293	0		

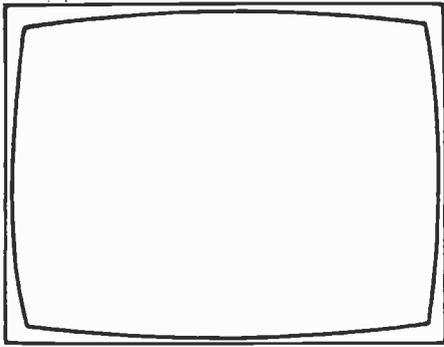

# TELEVISION

## More on Spares

No apologies for returning to the subject of spares so soon: it's likely to be an increasing headache for all concerned – setmakers, stockists, repairers and customers. Let's look at it first from the setmaker's point of view, prompted once more by Ferguson who have just announced that spares for the 14in. colour portable Model 3787 will no longer be supplied by them – nor will any repair work be undertaken. That's the popular little Movie Star portable fitted with a NordMende chassis, dating from the period in the early seventies when thyristor line output stages were all the rage amongst Continental setmakers.

The fact that these sets are now some ten years old highlights the problems. A setmaker of any size will have introduced a vast range of models over such a time scale. Just think of some of the permutations – different tube sizes and tuning arrangements, remote control, teletext and more recently stereo sound capability. Dealers and their customers expect to be able to order spares of every description: not just droppers, LOPTs and various safety specials but knobs that fall off and various bits of trim. Anything in fact that might be required to restore a set in for service to its original condition. This implies the need to stock thousands and thousands of different TV spare parts – spares also for a wide range of VCRs, radio and audio equipment. In terms of storage space and handling the costs involved are enormous. It's no use saying reorder when necessary from component manufacturers. They too alter their ranges, while the cost of ordering small quantities is prohibitively high even for the largest setmakers. Then there's the fact that many components are supplied to meet the specification for a particular model/chassis. We're thinking not just of safety components but of items shaped to fit particular PCB assemblies, cabinet mouldings and so on. There have been jokes in the past about computers running the show and part numbers as long as your arm: they just serve to emphasise the difficulties.

The vastly increased reliability of modern chassis hasn't helped in this respect. Cool running and low power consumption mean that sets can be expected to give years and years of service with comparatively few breakdowns. It's also a fact that a ten or fifteen year old set can still look quite new. But failures are inevitable from time to time and then the hassle starts. Just what is a fair time after which to put up the no longer available sign? Ten years sounds a nice round figure and seems to be the sort of time scale manufacturers now have in mind. After all if you've had ten years' service from a set you've not done badly, particularly in view of the modest initial price of consumer electronics equipment. But one has to admit that though this sounds reasonable it's not likely to assuage the customer who can't get his set repaired for want of some perhaps fairly minor item.

The repairer doesn't have to go back to the original maker for parts of course, though special items, whether to meet a safety requirement or an exacting performance specification – flyback tuning capacitors, the chopper and line output transistors used in some sets, and so on – are likely to cause problems. Increasingly, setmakers are farming out the supply of spares to specialist distributors. This ensures that spares are readily available around the country and has the advantage from the stockists point of view that he's not obliged to hold stocks of any and everything that might be required. He knows that a good range of tuners, LOPTs, triplers, droppers, electrolytics and transistors will meet the vast majority of calls for parts. Experience will provide a guide to what to stock for particular models and the independent distributor has no obligation to search for an obscure item for an unusual set. For the most part repairers can, as they've always done, rely on various standard component lines. We hope that doesn't sound too complacent, being all too well aware of the frustrations that can arise when a customer can't be provided with the sort of service you aim to give.

When you come to think of it the service nowadays being provided by specialist component suppliers is remarkably cheap and efficient. While a setmaker buys components in bulk to feed to his computer-controlled production lines the stockist has to locate, pack, despatch and invoice items on an individual basis. It's amazing how they manage to do it and not surprising that a special screw, belt or plastic moulding can bring with it quite a hefty bill. This all reflects the incredibly tight costing that modern mass production brings with it: what costs the setmaker pennies must cost you pounds.

The problems all too lightly touched upon above are likely to involve us all in increasing problems of one sort or another. A year or so back some readers were contemplating the idea of providing computerised fault finding and data services, but no computer will solve the problem of the missing part. Anything for which there's an obvious need is likely to be made available by someone or other – think of the universal tripler and the solid-state PL802 for example. Alternatives for most electronic components could probably be found – if only one could lay hands on the original performance specification and they could be made to fit the bracket, board or other mounting requirement!

## INDEX TO VOLUME 35

Copies of the index to volume 35 (November 1984 – October 1985) of *Television* are now available from the editorial office at 75p each. The index includes full lists of VCR Clinic and TV Fault Finding items. Would readers please note that indexes are not available until approximately six months after the last issue concerned. We've already had a number of requests for the index to volume 36 – despite the fact that four issues have still to be written, prepared and printed . . .

## EDITOR

John A. Reddihough

Please note that the telephone numbers below are for contact with the advertisement departments only. Editorial enquiries should be sent to the editor at the address given on page 473.

## ADVERTISEMENT MANAGER

David W.B. Tilleard  
01-261 6671

## SECRETARY

Janet Reeve  
01-261 6671

## CLASSIFIED ADVERTISEMENTS

Pat Bunce  
01-261 5942

## ADVERTISEMENT COPY AND MAKE-UP

Ron Scorey  
01-261 6035

## CAN YOU HELP?

A friend of ours requires a volume-on/off knob and a turnlock-tuning knob for a Philips RM712 car radio. Can anyone supply these? Does anyone know the agents or a source of spares for Tensai TVs?

## CORRECTION

A correction to the c.r.t tester/booster circuit published last month appears on page 493.

## FRONT COVER

This month's cover photograph shows a close up of a test pattern displayed on the screen of a PIL type tube.

# Modern Receiver Circuitry

## Part 3: Video Signal Processing

J. LeJeune

The use of integrated circuits has enabled some sophisticated techniques to be adopted in TV receivers, techniques that might not have appeared had the use of discrete component circuitry continued. For a good few years now video signal processing in TV sets has been carried out in i.c. form: while RGB output chips have been devised, the advantage at the end of the video chain still lies with discrete component circuitry, due to the dissipation and high voltages involved.

### Filtering the Video Signal

The output obtained from the vision detector of a colour receiver consists of the baseband luminance signal (50Hz-5.5MHz), the chrominance signal on its 4.43MHz carrier with sidebands extending some 1.1MHz on either side, and the 6MHz intercarrier sound signal which is a beat frequency between the vision and sound i.f. carriers (39.5MHz and 33.5MHz). We'll return to the sound signal in a later article. The chrominance subcarrier and its sidebands are interleaved with the upper luminance signal frequencies: because of the line structure of the TV picture, there are gaps in the luminance signal spectrum into which the chrominance signal is slotted.

The various components of the vision detector's output have to be separated for individual processing. Filtering arrangements vary from chassis to chassis but a typical way of going about this is shown in Fig. 1. The composite video signal is fed to the base of transistor Q1 via the bridged-T notch filter L3/C6/C7/R10 which removes the 6MHz intercarrier sound signal. The chrominance signal feed is via C2, the attenuator R8/R7 and C4 to the following signal processing i.c., with the series rejector circuit C3/L2 included to remove the l.f. video components - this arrangement is used in preference to a lossy bandpass acceptor circuit. C2 is of low value to contribute to the filtering. Q1 provides the sync and luminance feeds. It's made unresponsive to signals at the 4.43MHz chroma subcarrier frequency by the inclusion of the parallel tuned circuit L1/C1 in its emitter circuit: this introduces frequency selective negative feedback, reducing the stage gain at 4.43MHz. The unbypassed resistor R5 provides overall negative feedback - Q1 has low gain but good linearity and is primarily used as a buffer to prevent interaction between the sound and chroma subcarrier rejectors. Delay line DL1 is incorporated in the luminance signal path to compensate for the different bandwidths of the chrominance and luminance signal circuits.

### Luminance-chroma Processing Chip

Today's sets generally use a single chip to process both the chrominance and luminance signals. A good example of this type of i.c. is the Mullard TDA3560. Fig. 2 shows a block diagram of this widely used i.c.

Processing of the luminance signal is straightforward: amplification with d.c. clamping to restore the correct conditions following a.c. coupling (C5, Fig. 1), d.c. contrast control, then matrixing with the colour-difference

signals to provide R, G and B signals for the output stages.

Before we look at the processing of the chrominance signal let's just recap on its composition. Two colour-difference signals, B - Y and R - Y, are transmitted. At the transmitter these signals amplitude modulate two 4.43MHz subcarriers which have a phase difference of 90° - this means that when one subcarrier is at its peak the other is at zero. The two signals are then added to give the composite chroma signal - the technique is known as quadrature amplitude modulation. There's further complication with the PAL system since the phase of the R - Y signal is shifted by 180° on alternate lines. About ten cycles of 4.43MHz subcarrier (the colour burst) are transmitted during the post line sync pulse back porch period to act as a reference for the decoding process. The only modulation on this carrier is the 180° PAL signal swings, as a result of which the phase of the burst swings  $\pm 45^\circ$  on alternate lines.

Within the TDA3560 the chroma signal is fed first to a gain-controlled amplifier (a.c.c. - automatic chrominance control). The control potential is obtained by rectifying the colour burst since this is not amplitude modulated. The burst signal has to be separated from the chroma signal for this purpose: this is done by using a suitably timed line pulse to open a gate. The separated burst signal is also applied to a phase detector which is part of a phase locked loop controlling the phase and frequency of a reference oscillator. In earlier decoders this oscillator operated at 4.43MHz: for reasons that will become clear shortly in the TDA3560 and similar chips the frequency is 8.86MHz.

Returning to the chroma channel itself, the signal is next subjected to saturation and contrast control - the latter so that the correct luminance to chroma ratio is maintained. The control stage is gated by the burst gate pulse so that operation of the contrast and saturation controls does not affect the amplitude of the burst. The chroma signal then leaves the i.c. for application to the delay line circuit which serves two purposes: it separates the B - Y and R - Y components of the signal and, by averaging the signal over pairs of lines, converts any phase error to slight desaturation. The separated signals are then

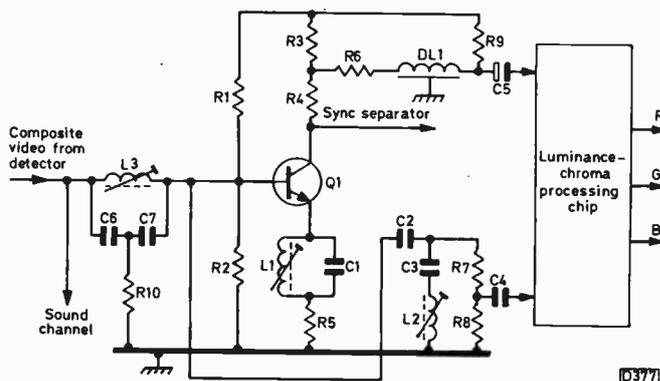


Fig. 1: Separating the outputs from the vision detector.

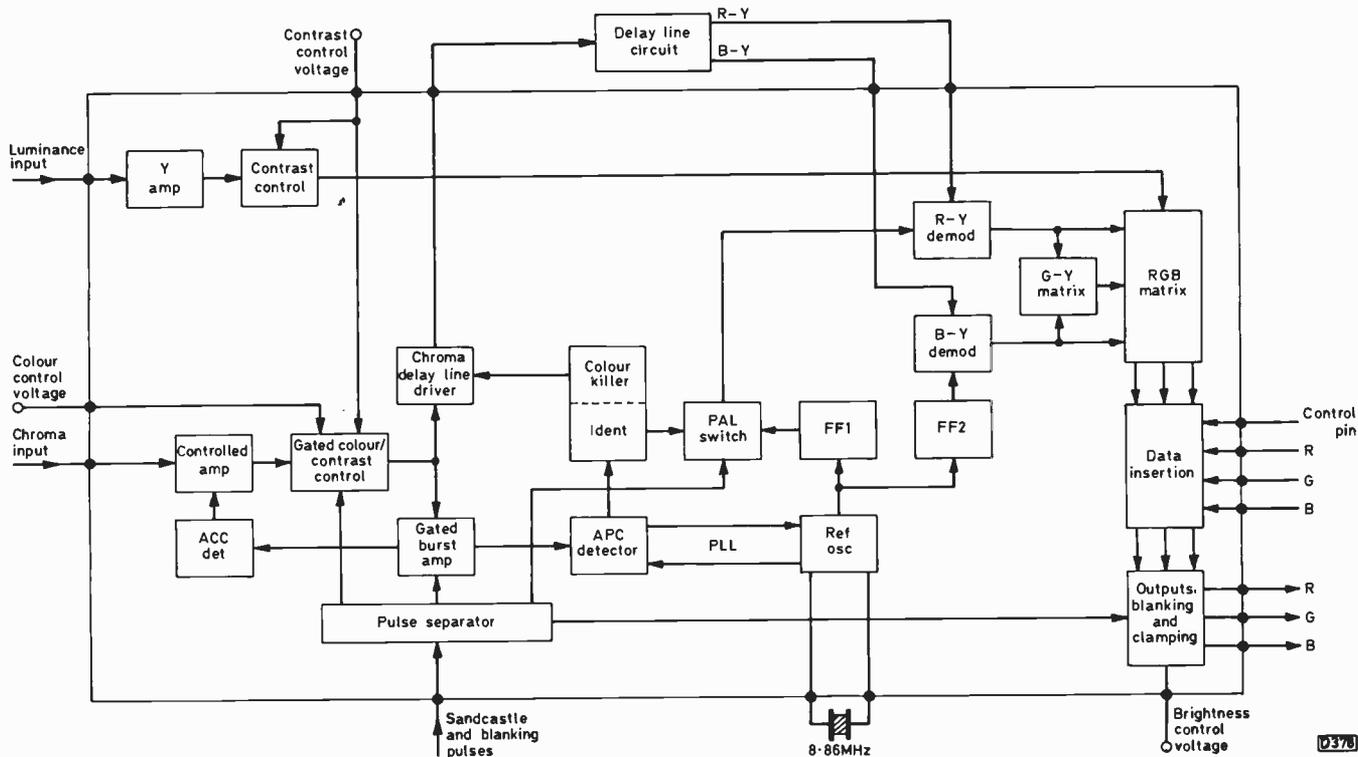


Fig. 2: Block diagram of the TDA3560 luminance and chroma signal processing chip.

applied to two synchronous demodulators. These require inputs from the reference oscillator, which takes us back to the a.p.c. loop.

The main purpose of the colour burst is to synchronise the reference oscillator which drives the synchronous demodulators. These operate on the sample-and-hold principle, sampling the modulated colour-difference signals at the peaks of the carriers to detect their amplitudes. The reference signal drives to the demodulators must have a phase difference of  $90^\circ$  – the same as the original carriers at the transmitter. In earlier decoders this was achieved by incorporating a  $90^\circ$  phase shift network in one of the reference signal feeds. The use of an 8.86MHz oscillator avoids the need for this and provides more accurate results: its output is fed to two flip-flops which provide

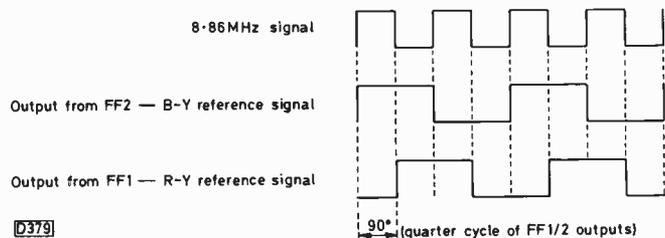


Fig. 3: Obtaining quadrature reference signals to drive the R – Y and B – Y demodulators by using two flipflops to divide by two the output from an 8.86MHz oscillator. FF2 is positive-going edge triggered to produce an in-phase 4.43MHz signal; FF1 is negative-edge triggered to produce a signal with a  $90^\circ$  phase difference.

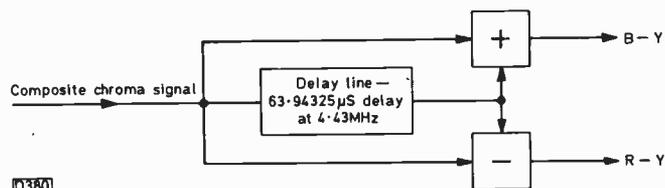


Fig. 4: Principle of the chroma delay line circuit.

division by two. By taking opposite polarity outputs from the flip-flops two drive signals with an exact  $90^\circ$  phase difference are obtained. See Fig. 3.

It's also necessary to invert the drive to the R – Y demodulator on alternate lines to counter the effect of the  $180^\circ$  switching at the transmitter. This must be synchronised with the switching at the transmitter. The burst swings provide an identification signal for this purpose: the 7.8kHz (half line frequency) ident signal synchronises the PAL switch (inverter) which is driven by line frequency pulses.

The presence of the burst/ident signals is a convenient way of establishing that the transmission is a colour rather than a monochrome one. No burst means no colour: the colour-killer then switches off the chroma delay line driver stage. If this is not done the a.c.c. circuit will operate the chroma amplifier at maximum gain and the monochrome display will be marred by colour noise.

Fig. 4 shows the operation of the delay line circuit. The composite chroma signal is fed directly and via the one-line duration delay line to add and subtract networks. Because of the R – Y signal inversion ( $180^\circ$  shift) on alternate lines the R – Y signal cancels out in the adder circuit while the B – Y signal cancels out in the subtract circuit.

### Matrixing and Data Insertion

The third colour-difference signal (G – Y) is obtained by matrixing the demodulated R – Y and B – Y signals. The luminance signal is then added to obtain RGB signals. These pass to the data insertion circuit which consists of three fast electronic changeover switches – they can operate at 10MHz. The state of all three switches is controlled by the voltage at the insertion control pin – 1.5V at this pin changes the switches from off-air RGB to external inputs, the mode generally used for teletext. For mix-mode teletext a monochrome version of the text is fed

# next month in TELEVISION

## ● SERVICING THE PANASONIC NV7000

Though a fairly early VCR, dating from 1981-2, this machine was of advanced design. It had direct-drive motors, Dolby noise reduction, full cable remote control, slow motion and back-space edits. David Botto has handled large numbers of these machines and provides servicing notes and advice based on this experience.

## ● COLOUR TUBE DEVELOPMENTS

Eugene Trundle continues his series with a detailed look at colour tube electron gun technology and the developments that have taken place in this area over the years. Just about everything has changed, from the heaters to the electron lens arrangements. Tube neck magnet systems are also considered: did you know why a combination of two-, four- and six-pole magnets is required?

## ● MODERN RECEIVER CIRCUITRY

The line output stage, which does so much more than just provide horizontal scanning, has always been a bit of a mystery to those not versed in TV technology. The need for EW modulation with 110° tubes has further complicated matters. Tuning is a key to line output stage operation but more than one frequency is involved – the line scan, flyback and harmonic frequencies in fact. J. LeJeune provides an account of the various things that go on in the line output stage.

## ● SERVICING SONATEL/MR MONO PORTABLES

Sonatel monochrome portables were distributed by House of Carmen and were amongst the first to break the £50 price barrier. They were widely sold through the big retail chains and via mail order catalogues. When House of Carmen took over Morphy Richards the sets were sold under this well known brand name. Ian Rees provides detailed information on common faults and how to deal with them, also on adding a.g.c. to some models.

PLUS ALL THE REGULAR FEATURES

ORDER YOUR COPY ON THE FORM BELOW:

TO.....  
(Name of Newsagent)

**Please reserve/deliver the July issue of TELEVISION (£1.20), on sale June 18th, and continue every month until further notice.**

NAME .....

ADDRESS .....

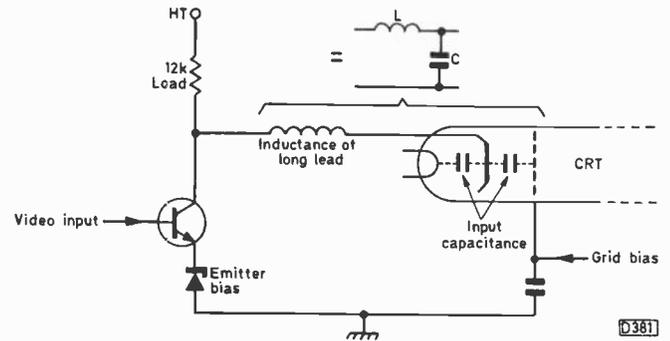


Fig. 5: How long video leads and a tube's input capacitance form a low-pass filter that attenuates h.f. components of the signal.

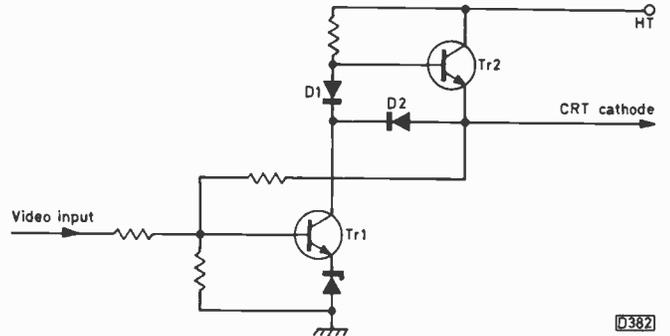


Fig. 6: Basic class AB video output circuit.

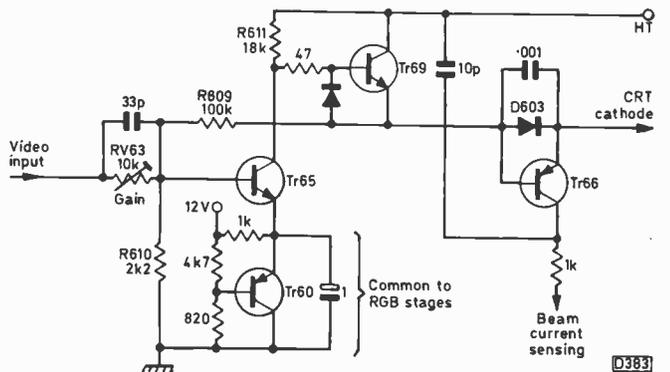


Fig. 7: Video output circuit used in the Thorn TX100 chassis.

to the insertion control pin. From the data insertion section the RGB video signals pass to the i.c.'s output stages where line and field flyback blanking is carried out.

## Video Output Circuits

The external RGB output stages drive the tube's cathodes. For optimum results the tube's heater-cathode and cathode-grid capacitances must be charged and discharged in the shortest possible time. It helps to mount the RGB output stages on the tube base panel. This eliminates the long leads otherwise required – these long leads, in conjunction with the tube's input capacitances, form low-pass filters that affect the set's h.f. performance – see Fig. 5.

The problem with a simple class A output stage of the type shown in Fig. 5 is that while the tube's input capacitance is quickly discharged on a negative-going signal transition, when the output transistor is rapidly driven to saturation, on a positive-going transition when the transistor is switched off the capacitance has to charge via the load resistor, which is typically about 12kΩ in

value. Class AB output stages are favoured as a way of overcoming this disadvantage. Fig. 6 shows the basic circuit. Adding the emitter-follower transistor Tr2 in Tr1's collector circuit provides a method of rapidly charging the tube's input capacitance on positive-going transitions. Another advantage of the circuit is reduced dissipation.

Fig. 7 shows one of the RGB output stages used in the Thorn TX100 chassis. The pnp transistor Tr60 is used to hold the emitters of all three output transistors at 2.5V. Video from the chroma-luminance processing i.c. is applied to the base of the output transistor Tr65 via RV63: negative feedback via R609 sets the gain of the amplifier and stabilises the d.c. operating conditions. No adjustment of the grey-scale black level is required because the stage is designed to operate with the later TDA3562A

processor i.c. which incorporates automatic black-level control. If such adjustment was required, R610 could be made variable. Tr65 provides a peak-to-peak drive of 150V at the base of the emitter-follower transistor Tr69. Up to this point the circuit follows a similar arrangement to that shown in Fig. 6. The final transistor Tr66 serves a dual function. It provides signal coupling to the tube via its base-emitter junction, acting as an emitter-follower on negative-going transitions – diode D603 provides coupling on positive-going transitions. The other function is to provide feedback from its collector to the beam current sensing (in the TDA3562A chip) and beam limiting circuits. The feedback to the chip is part of the black-level correction system. The power consumption of the stage is around 600mV.

## Grundig's Satellite TV Receiver

Steve Beeching, T. Eng.

Grundig will be launching a new satellite TV receiver during the May trade shows in London. I was pleased to be present at a prelaunch appraisal with a friend of mine who has already looked at a number of satellite receiver systems.

The receiving dish was pointed at Eutelsat-1 F1 (ECS-1). Various programmes are available from this satellite. All were very well received – with the exception of scrambled transmissions for which at the time decoders had not been made available.

The main television set was a Grundig Model M70 with a 28in. FS tube and a CTI decoder – this is an automatic PAL/NTSC/Secam decoder with a variable luminance delay line for correct luminance-chrominance registration (to put the red back on top of the snooker balls).

The pictures from the Italian channel RAI were stunning – not only because of the scantily clad ladies running about but also due to the shots being live from the studio and the wide TV bandwidth being used.

The satellite receiver itself is the size of a midi hi-fi unit – 320 × 70 × 270mm – which is quite compact. It's a 29-station programmable receiver with the capability to tune each programme through the full 950-1,750MHz bandwidth in 99 channel steps. Channel selection is by means of an IR remote control unit.

The range of controls and inputs is comprehensive. There are two dish aerial inputs at the rear, X and Y. While the inputs can be from separate dishes the intended use is with a dual head end at the dish, i.e. a dish with two low-noise converters fitted, one for vertical and the other for horizontal signal polarisation. Selection of either is programmable via each input.

There are two scart connectors and a six-pin AV DIN socket. One scart socket is for use with a VCR and the other for connection to the main TV set (with the AV DIN socket as an alternative). Through connection via a relay is available when the satellite receiver is off. When in operation the VCR can record the channel currently being received: so you can watch a terrestrial programme (BBC-1, ITV etc.) on the main TV set while recording a satellite TV broadcast.

The low-noise converters at the dish are each fed with 15V at 250mA via the connecting cables: the power supply to them can be switched off by a small switch at the rear of the unit. There's also a switch to select only input X in

the event of a single low-noise converter being used.

The unit uses a standard VCR type modulator and combiner amplifier – there's an audio level preset mounted below the modulator. The terrestrial TV aerial can be plugged in and the output next to it connected to any standard u.h.f. TV set. The additional satellite TV outputs are modulated on to u.h.f. channels in the region ch. 31-39, adjustable. We found that the modulator was good enough to be able to decode Italian teletext on a standard receiver.

There's a four-state voltage output for dish switching: 0V dish 1, horizontal; 3V dish 1, vertical; 6V dish 2, horizontal; 9V dish 2, vertical. The switching is done at the head end by h.f. relays.

Each programme (1-29) can be set not only to the required satellite channel (1-99) but also for input X or Y, for de-emphasis d1 or d2 and for deviation h1 or h2. The inputs from the low-noise converters are in the band 950-1,750MHz (first i.f.). X or Y input selection is by switching voltages of +5V or -5V to bias on or off two pin diodes in the signal paths. After signal selection an a.g.c. stage caters for a range of between 47dB/μV to 75dB/μV. A second mixer then produces an output at 480MHz which, after two stages of i.f. amplification, is converted to baseband video by the f.m. demodulator. An a.f.c. output is fed to the microcomputer as a reference: the tuning is microcomputer controlled, using a phase-locked loop synthesiser. The input to the loop is from the local oscillator and the frequency of operation is set by the microcomputer: tuning drift is thereby eliminated, the range of control being sufficient to accommodate any drift in the low-noise converters.

The sound circuit caters for carriers at 4.5MHz or in the range 6-7MHz. A wideband phase-locked loop is used. Any channel can be set for 4.5MHz or 6.5MHz and stored in the memory. The 6.5MHz carrier can be in the range 6-6.5MHz: the phase-locked loop is arranged to demodulate within these limits without need for adjustment. The carrier is mixed to produce a 10.7MHz sound i.f. signal which is demodulated by a standard TBA120 chip with an error signal fed back to the mixer – all this path is within the PLL.

The ECS-1 satellite at present carries eleven channels. Two of these are on east spot beams and were thus very faint, two were scrambled and the others were received

with excellent pictures – albeit a 2m dish was being used. No adjustments to the TV set or the satellite receiver were necessary – reception of the whole band was simply by changing channels via the remote control unit. Different signal polarisation, de-emphasis, sound carriers and colour systems were all taken care of. My friend remarked how good it was – and he's not easily impressed.

---

# Letters

## WHY NO TEST CARDS?

Despite following the normal TV engineer's traditionally moderate line, after the events this week I really feel it's time to put pen to paper in a letter of complaint to the broadcasting authorities. I hope it will in no small way be supported by your good selves and the majority of *Television's* readers. In a nutshell, where have all our test cards gone? Since their disappearance from the BBC channels in what seems an age ago I've noticed little complaint or comment in these pages. Why hasn't anyone questioned the need for two channels of text consisting of repeated information every ten minutes or so on most days of the week? Apart from the occasional "glimpse" on Channel 4 it seems that test cards are now considered to be pointless.

Anyone involved in front line servicing will know this situation is far from ideal. At the time of writing a typical morning's programmes consist of BBC-1 text, BBC-2 text, ITV black-and-white film, Ch. 4 text. This situation doesn't allow the engineer let alone the customer evaluate the performance of a TV set or VCR.

So please BBC reconsider your policy and bring back our Effy at least on one channel. A display even every half hour would help, but please don't consider her redundant. I and many other engineers will tell you that this is far from the truth.

*Keith Lane,  
Southsea, Portsmouth.*

**Editorial comment:** Whenever this comes up the broadcasting authorities tend to comment that it's not their job to provide a pattern generator that's expensive in terms of power consumption. But a portable pattern generator doesn't allow the complete transmission path to be assessed. There seems to be no reason why the broadcasters shouldn't oblige the trade in the way suggested: the present situation is unsatisfactory indeed.

## TELETEXT TROUBLES

I have some further news concerning XM11 teletext decoder problems. Suddenly, about three weeks before Easter, the problem I'd had with missing rows of data on BBC-2 vanished. Text has been fine on this channel ever since. The period of malfunction was about three months. A problem with ITV text, i.e. not getting it right first time, still comes and goes but I've now noticed that this occurs only with networked information – locally generated text from TVS is always right first time. Throughout this period of difficulty BBC-1 and Ch. 4 text have always been o.k.

So what can I conclude from this? First I don't believe anything has changed locally, neither do I think the receiver was ever suspect. The broadcasters assured me

that everything was o.k. at their end, which prompted me to look into the possibility that something might be wrong at my end. I believe, from what I've heard, that the XM11 may be less tolerant of variations in transmission parameters than later designs. I feel that this is the root of the problem, even though the broadcasters would deny it.

The original fault showed every fourth row missing. Later this changed to every fifth row, before the problem disappeared altogether. Perhaps something changed as a result of a three-monthly maintenance schedule somewhere. I doubt whether I'll ever find positive proof of my suspicions and will just have to be thankful that the fault has gone away.

*Keith Cummins,  
Southampton.*

## MICROCOMPUTER FAULTS

Further to my letter in the March issue, here's some more information on microcomputer faults.

The Sinclair Spectrum's power supply seems to be responsible for a number of faults. The main item that fails is, as I stated, a ZTX450 transistor (TR4). On later versions of the board it's a ZTX650. TR5 (ZTX213), diode D15, the 7805 regulator chip and even the inductor itself have been known to fail. With all these failures there's no buzzing noise from the inductor. A screen full of horizontal black-and-white lines can be caused by failure of the Z80A microprocessor chip or the ROM. These components should be available from advertisers in the pages of *Sinclair User* magazine.

The BBC computer has a strip of stiff conductors that link the keyboard to the main board. Repeated movement of this strip due to the addition of ROMs to the expansion sockets located beneath the keyboard can lead to failure of areas of the keyboard.

VIC20 computers have given us the following faults. Every other numeral not working (1 o.k., 2 u/s etc.): the 6522A chip in position UBA1 faulty. Poor or no colour: suspect the modulator or the Commodore chip. Intermittent loss of picture at switch-on: the 7402 chip in position UB9 sensitive.

*G. Jackson,  
Hyde, Cheshire.*

## COMMODORE 64 TIP

Problems with home computers have been featured in recent issues. Here's one relating to the Commodore 64. It may save other readers a small fortune. The trouble is loading problems, with the computer not waiting for the play key to be pressed before going into the play or save mode. The I/O port for the cassette unit is in the 6510 CPU, along with the data direction registers. If you type in this one-line program:

```
10 print peek (1): GOTO 10
```

the computer should, if working properly and with no cassette keys depressed, respond with a solid row of 55s. What you're more likely to see is a row of continuously changing numbers. Obviously something weird and wonderful is going on inside the chip. Next shock, phone Commodore and ask the price of a replacement chip: twenty four pounds!

A small modification (bodge) has so far proved very successful however. R1 (3.3k $\Omega$ ) is connected to pin 25 of the chip: it's a pull-up resistor connected to the cassette sense line. Wire a 47k $\Omega$  preset in series with this resistor

# POST A PART ELECTRONICS

6 CHAPMAN COURT, CHARFLEETS ROAD,  
CANVEY ISLAND, ESSEX SS8 0PQ.

Telephone 0268 690868  
Telex 99305



TRADE COUNTER OPEN

ORDERS DESPATCHED SAME DAY  
ADD 75p P&P, THEN 15% VAT.  
ADD POSTAGE FOR OVERSEAS ORDERS.  
ORDERS WITH AEROSOLS, PLEASE ADD 25p PER CAN.

Thom 10Ω 20W (3500) R751 Safety Resistor	75p
Pye 713 Speaker 5" X 3" 70Ω	1.00
Pye 713 Complete Tube Base Panel with Focus Slider & Leads	2.75
Pye 725 Complete Tube Base Panel	1.25
TX9 Complete Tube Base Panel	2.75
TX10 Complete Tube Base Panel	3.75
TX90 Complete Tube Base Panel	4.75
Pye 713 Control Knobs	4 for 50p
Tube Base Socket ITT CVC32	50p
Tube Base Socket Thom 3000/8000 etc	50p
IC Inserter 16 Pin	50p
Large IC Extractor	50p
Crystal 4.43MHz	65p
EHT Lead & Cap for Split Diode Lopt	90p
Anode Cap	47p
Sanyo Anode Cap Assy with Lead, 12TCC-CT-1G	65p
Degauss VDR E299D/HP230 3000/8000	25p
Degauss Thermister C8-ROH (TX90)	1.00
Control Knob Thom TX90	4 for 2.00
On/Off Knob Thom TX90	65p
Push Button Assy Thom TX90	9.00
Tube Neck Connection Assy, 20AX AT1081	25p
EHT Cable	Metre 14p
BF255 with Heatsink	40p
TI110 with Heatsink	10p
L129/130/131 Coil	10p
6MHz Ceramic Filter	25p
DL1700 (Philips) Chroma Delay Line	1.00
DL50 Chroma Delay Line	1.00
T9006A Lum Delay Line	1.00
8K5/9K Lum. Delay Line	65p
Plastic Cover for 3K5 SP8385	5p
TX9 Back Ground Control 10K	15p
TX9 Gain Control 100R	15p
Thom 2000 Focus Pot	1.05
Thom 9000 Focus Pot	2.00
Thom 8K5 Focus Pot	2.75
Thom 4000 Focus Pot	2.40
Thom TX10 Focus Pot (New Type)	9.00

### SERVICE AIDS

Ambersil MS4 Silicone Grease	12oz 2.15
Ambersil Freezer	12oz 1.99
Ambersil Amberlube	6oz 1.89
Ambersil Ambertron	16oz 2.25
Ambersil Anti-Static Screen Cleaner	7oz 1.35
Ambersil 40+ Protective Lubricant	14.1oz 2.15
Ambersil Amberclens Foaming Cleaner	13oz 1.26
Ambersil Circuit Lacquer	14oz 2.15

### THICK FILM RESISTOR UNITS

3500 Thom (5 Pin Connection) video	1.70
4000 Thom (4 Pin Connection)	1.30
725/731 Pye (6 Pin Connection)	2.20
713 Pye (6 Pin Connection)	2.20

### FUSES

20mm		1 1/4"	
50MA	10 for 70p	250MA	10 for 65p
250MA	10 for 50p	750MA	10 for 65p
315MA	10 for 50p	7A	10 for 50p
500MA	10 for 50p	10A	10 for 50p
2.5A	10 for 1.00	20A	10 for 50p
3.15A	10 for 1.00	50A	10 for 50p

Thom Mains TX 3000/3500	7.50
Thom Mains TX 8000/8500	10.00
Thom Mains TX 9000 (T701)	10.00
Thom Mains TX 9600 (T512)	10.00
Thom Scan TX 3000/3500	3.50
Thom EHT TX 3000/3500	6.00
Thom LOPT 9000	10.00
Thom LOPT 9600	12.00
Thom LOPT 1590/91	7.25
Thom LOPT 1690/91	7.25
Thom LOPT 8000	9.80
Thom LOPT 8500	9.80
Thom LOPT TX9	9.85
Thom LOPT TX10	19.00
Thom LOPT TX90	13.75
Pye LOPT 713	10.00
Pye LOPT 725	9.85
Pye LOPT 731	10.18
Philips LOPT G9	8.80
Philips LOPT G11	13.75
GEC LOPT 3113	7.40
Diode Split LOPT AT2076/35	14.75
Sanyo LOPT AM-WM-21	6.75
Sanyo LOPT AM-WM-4	7.30
Philips LOPT G8	7.80
Sanyo LOPT (CW21) 4-2751-4470	5.00
ITT LOPT CVC3-3	9.60
ITT LOPT CVC30	8.75
ITT LOPT CVC45	9.75
Baird 8750	10.25
Baird 8752	10.25
Thom Line Drive TX TX9 (T2)	3.00
Thom Line Drive TX 8K etc. (T402)	1.85
Thom Line Drive TX 9K (T705)	3.00
Thom Switch Mode TX 9K6 (T511)	3.75
Thom Input Choke TX9 (L54)	4.00
Thom Choke TX90 (L120)	2.95

300 Mixed Resistors	1.50
300 Mixed Capacitors	1.50
150 Mixed Electrolytics	2.00
100 W/W Resistors	1.00
20 Mixed Conv Pots	1.00
40 Mixed Pots	1.50
20 Mixed Sliders	1.00
40 Mixed Presets	60p
20 Mixed VDR & Thermistors	1.00
100 Mixed Ceramic Discs	1.00
20 Mixed Valve Bases	1.00

AC128	39	BC174B	23	BCX33	22	BF173	25	BFR52	31	NKT276	20
AC131	40	BC177	24	BCX34	22	BF167	24	BFR62	28	NKT453	1.65
AC138	40	BC182LB	12	BD115	49	BF179	32	BFR87	29	OT112	1.92
AC141K	39	BC183L	12	BD131	49	BF180	33	BFR90	25	OT121	2.08
AC142K	39	BC184L	12	BD132	49	BF181	30	BFR91	2.08	R1038	80
AC153	39	BC187	24	BD133	50	BF184	30	BFT42	30	R2008B	1.10
AC176	33	BC204	15	BD139	36	BF194	16	BFX38	40	R2010B	1.40
AC176K/	33	BC208	9	BD140	38	BF195	16	BFY50	30	R2265	1.30
AC128K	53	BC212L	9	BD144	1.70	BF196	16	BFY51	34	R2305	80
AC188	38	BC213L	12	BD150	50	BF197	15	BFY52	34	R2322	50
AD142	1.18	BC227	12	BD163	98	BF198	98	BRC116	1.50	R2443	25
AD143	1.08	BC238B	8	BD201	74	BF199	15	BRC1693	1.43	RCA16445	30
AD149	98	BC238L	8	BD203	78	BF223	18	BU105	1.00	RCA16589	1.25
AD161	32	BC250A	15	BD204	99	BF224	19	BU126	1.18	RCA1680D	1.40
AD162	32	BC251	8	BD222	48	BF238	20	BU207	1.05	RCA16799	1.13
AD263	1.05	BC252A	20	BD225	52	BF240	9	BU208A	1.15	RCA1680D	1.42
AF127	45	BC284	37	BD232	50	BF241	21	BU208A	1.15	RCA16802	1.38
AF139	38	BC301	32	BD233	60	BF255	10	BU326A	1.30	RCA16815	1.20
AF239	41	BC303	31	BD234	60	BF256LB	38	BU407	1.70	SP8385	2.65
BC107	15	BC307	10	BD237	55	BF256S	20	BU408	2.76	S1299	2.25
BC108	15	BC308	8	BD238	65	BF257	28	BU500	2.30	S28000	1.25
BC109	15	BC309	14	BD241	59	BF259	28	BU526	2.46	T6050V	1.30
BC115	16	BC327	18	BD244	85	BF271	25	BU806	1.80	T6052V	1.30
BC117	21	BC328	18	BD278A	81	BF274	11	BU807	2.94	T9003V	1.25
BC125	26	BC337	17	BD386	68	BF337	29	C1128	9	T9010V	1.45
BC126	23	BC338	17	BD433	71	BF338	34	C1172B	9	T9033V	1.30
BC139	27	BC347	83	BF355	40	BF356	54	T9054V	1.10	T9059V	1.10
BC141	34	BC394	8	BD582	1.20	BF362	50	E9003	29	T9093V	1.10
BC142	30	BC454	8	BD589	1.20	BF391	21	E9005	25	TIC45X	50
BC143	31	BC455	8	BD677G	1.35	BF394	16	MEQ404	10	TIC46	46
BC147	12	BC456	10	BD679	1.42	BF422	47	MEQ412	10	TIC106C	40
BC148	12	BC460	40	BD701	1.04	BF423	53	ME6002	10	TIP29	42
BC149	12	BC463	22	BD702	1.12	BF450	43	MJ2501	2.36	TIP30	42
BC153	16	BC546	8	BD707	95	BF453	53	MJ3001	2.21	TIP31	35
BC1540R	16	BC547	12	BD708	95	BF458	37	MJE340	50	TIP32	43
BC154YL	16	BC548	12	BD839	1.30	BF459	40	MJE350	50	TIP33	61
BC157	12	BC549	8	BDX10	1.03	BF461	59	MJE2955	1.40	TIP41	42
BC158	12	BC557	10	BDY20	1.09	BF556B	35	MJE3055	1.50	TIP42	45
BC159	15	BC558	10	BDY32	89	BF586	15	NKT241V	8	TIP110	61
BC171	9	BC559	8	BF137	20	BF694	16	NKT241G	8	TIS91	25
BC172	9	BC555	8	BF153	20	BF757	62	NKT241Y	8	ZTX550	30

### INTEGRATED CIRCUITS

BRC1330	1.40	SN7613ND	1.80	TBA530	1.26	TDA2030	2.10
BRC2064	1.00	SN76023N	1.80	TBA540	1.00	TDA2522	2.10
BRC/M/200	1.00	SN76033N	2.00	TBA560C	1.82	TDA2530	2.61
BRC/M/300	1.80	SN76115	2.00	TBA641	2.05	TDA2560	3.50
CA3060	1.58	SN76131N	1.58	TBA651	2.50	TDA2581	1.90
LM1303P	1.48	SN76226N	1.25	TBA720A	2.49	TDA2951	3.06
LM231B	2.20	SN76227N	1.00	TBA750	1.00	TDA2811A	1.95
ML237B	2.00	SN76530P	1.30	TBA800	1.62	TDA2640	2.90
ML239B	2.85	SN76622N	1.80	TBA810S	1.80	TDA2690A	1.50
MC1327AP	1.25	SN76660N	90p	TBA810AS	1.00	TDA3560	6.00
MC1358P	1.38	SN76666N	80p	TBA920	2.88	TDA4500	5.00
MC1455P	18p	SN76744	1.82	TBA950	2.54	TDA9503	2.90
MC14516BCP	60p	SY153A	2.50	TBA1440	1.92	TCEP100	3.40
SAA1025	7.20	TA7117P	1.00	TCA2705A	1.05	MC14426P	4.80
SAA1124	4.50	TA7109AP	2.80	TCA270C	1.05	MC14429P	4.50
SAAS010	6.00	TAA611	1.40	TCA270CII	1.85	MC14514	5.00
LA432A	1.00	TBA120B	1.20	TDA1035T	1.05	UA758PC	2.50
SL1430	2.50	TBA120C	1.20	TDA1037	2.72	UNL2165	1.30
SL1432	2.50	TBA120CQ	70p	TDA1170	2.15	UNL2216A	1.25
SN15846N	60p	TBA120S	70p	TDA1170S	1.76	UPC1365C	1.75
SN74123N	65p	TBA120U	1.00	TDA1200	2.42	SC9488P	5.40
SN74154N	1.40	TBA295	1.00	TDA1270	2.76	SC511P	1.40
SN76001N	1.40	TBA480Q	1.40	TDA1327	2.53	SW153	2.50
SN76110N	1.14	TBA510	1.90	TDA2002	2.80		

Thom 8/8K5 ex equip panels untested	2.88	PSU	3.75	Thom 3/3K5 ex equip panels untested	3.75	Thom 4000 Convergence panel ex-factory	3.75
FTB	3.75	LTB	3.75	Video	2.50	Thom 4000 PSU panel ex-factory	2.50
Decoder	4.00	Chroma	2.00	Thom 3K5 beam limiter board new	1.75		
Thom 9K ex equip panels untested	12.00	IF	1.75	Thom 3/3K5 EHT & scan TX + R2008B on alum chassis ex-equip	1.80		
PSU	5.00	Conv. 3K	3.75	Thom 8/8K5 damaged FTB for spares	1.25		
Decoder	5.00	Conv. 3K5	5.00	Thom 8/8K5 damaged decoder for spares	2.25		
Thom 9K6 ex equip panel untested	5.75	Autovox Decoder FG/01 boxed	5.00				

10 Spark Gaps	1.00
10-16 pin Quil IC Socket	90p
20 Assorted TV Knobs	1.00
10-16 pin Quil to Dil IC Socket	90p
100 Mixed Diodes	1.00
50 Mixed Mica Washers	65p
300 Mixed Resistors & Capacitors	1.50
10-16 pin Dil to Dil IC Socket	1.00
50 Electrolytics & 50 Capacitors	1.00
50 Mixed Poly Capacitors	1.00
20 Mixed Valve Bases	1.00

BF154	25	BFR52	31	NKT276	20
BF167	24	BFR62	28	NKT453	1.65
BF179	32	BFR87	29	OT112	1.92
BF180	33	BFR90	25	OT121	2.08
BF181	30	BFR91	2.08	R1038	80
BF184	30	BFT42	30	R2008B	1.10
BF185	30	BFT43	30	R2010B	1.40
BF194	16	BFX38	40	R2030	70
BF195	16	BFY50	30	R2265	1.30
BF196	16	BFY51	34	R2305	80
BF197	15	BFY52	34	R2322	50
BF198	98	BRC116	1.50	R2443	25
BF199	15	BRC1693	1.43	RCA16445	30
BF223	18	BU105	1.00	RCA16589	1.25
BF224	19	BU126	1.18	RCA1680D	1.40
BF238	20	BU207	1.05	RCA16799	1.13
BF240	9	BU208	1.15	RCA1680D	1.42
BF241	21	BU208A	1.15	RCA16802	1.38
BF255	10	BU326A	1.30	RCA16815	1.20
BF256LB	38	BU407	1.70	SP8385	2.65
BF256S	20	BU408	2.76	S1299	2.25
BF257	28	BU500	2.30	S28000	1.25
BF259					

# CHROMAVISION

## MANCHESTER and BIRMINGHAM

061-736 6333      021-784 2561



**WORKING VIDEOS**  
100's IN STOCK

**HUNDREDS OF ELECTRONIC VIDEOS WORKING**  
NOW IN STOCK

**WORKING, NON WORKING + UNTESTED TV's**  
AT LOW, LOW PRICES  
MOST MAKES

**THORN, ITT,**  
**BUSH, PHILIPS, ETC.**


**WORKING SETS FROM £25.00**  
TELETEXT, REMOTES, BASICS  
ALSO COLOUR PORTABLES, NORDMENDE, T.X. ETC.

**CLOCK TRIMS FOR 3V16/22 VCRs £2.00**

**CASH ONLY**

**CHROMAVISION, 95 LANGWORTHY RD, SALFORD, MANCHESTER M6 5PH**

All prices subject to V.A.T.

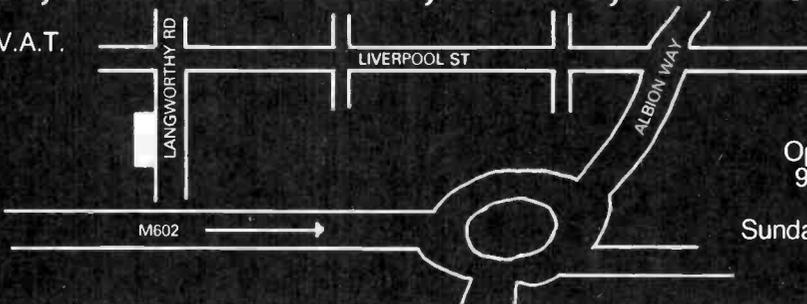

**WE ARE HERE**  
Only 2 minutes from  
end of motorway

Open 6 days a week  
9.30 a.m.-6.30 p.m.

Sundays by appointment

# TELEPART

## Telegen-1

PRICE £18.35 (Inc. VAT)  
\* EXCEPTIONALLY LIGHT AND DURABLE  
\* POCKET SIZE FOR OUTSIDE SERVICE  
\* PP3 BATTERY POWER SOURCE  
\* FIVE DIFFERENT TEST PATTERNS FOR  
COLOUR & MONO TV  
\* CROSSHATCH GRID \* DOT MATRIX  
\* WHITE RASTER  
\* HORIZONTALS \* VERTICLES  
\* 3.5mm JACK SOCKET FOR OPTIONAL  
P.S.U.



A lightweight, extremely portable and versatile pattern generator for black/white and colour T.V. alignment and service at the customer's home. At the turn of a switch, the generator can provide five essential test patterns for correct installation, fast checks and repairs. Pattern stability is first class and compares favourably with other more costly bulky generators only suitable for bench work. The generator is pocket size measuring 10 x 7.5 x 4 cm and weighs only 190 grams. Switched 3.5 mm jack socket allows use of external power supply with battery in situ.

## Telegen-2

PRICE £34.45 (Inc. VAT)  
\* EXCEPTIONALLY LIGHT & DURABLE  
\* COMPACT 10 x 12 x 4.5 cms  
\* RED RASTER \* GREEN RASTER  
\* BLUE RASTER  
\* COLOUR BARS  
\* 3.5 mm JACK SOCKET FOR P.S.U.  
\* PROVIDES UHF SIGNAL APPROX.  
CHANNEL 35



Telegen 2 is a colour bar generator at a very modest price and yet is extremely effective, stable and durable. It is the perfect compliment to Telegen 1, giving colour bars arranged in the following sequence: white, yellow, cyan, green, magenta, red, blue and black. The unit provides a signal in the UHF band approx. Channel 35 and requires a supply of 14 to 18 volts D.C.

## Power Supply

A switchable power supply ideally suited to both Telegen 1 and Telegen 2.

PRICE £4.55 (Inc. VAT)

ALL ITEMS POST AND PACKING £1.44 (Inc. VAT)

All goods should be delivered within 4 working days.

**32 TEMPLE STREET, WOLVERHAMPTON**  
WV2 4AN. TEL: (0902) 29022

# SADELTA

## FIELD STRENGTH METER

### MODEL TC-402

THE SADELTA FIELD STRENGTH METER TC-402 has been designed to measure the signal levels delivered by the antenna to a TV or FM receiver, in order to test the performance of the antenna and evaluate the best conditions during installation etc. To facilitate measurements, the tuning frequency readout is shown on a digital display.



## FEATURES

- Covering FM and all TV bands (UHF/VHF) including CATV freq.
- Digital tuning display (3 digits) for direct frequency readout.
- Accurate 10 turn tuning potentiometer.
- Built-in loudspeaker enables monitoring of sound in AM/FM.
- Meter measurement in voltage and dB from 20uV (26dB/uV).
- Continuity tester 0-500 Ohms.
- Fully portable (battery).
- Sturdy carry case.

PRICE £249 + £37.35 VAT

U.K. POST PAID, export enquiries welcome, Visa/Access or cheque with order, payable to B.K. Electronics. Official orders welcome from Govt. Depts., Colleges, P.L.C.s etc. Large S.A.E. for technical leaflets of complete range delivery normally within 7 days.

**B. K. ELECTRONICS** Dept. 'T'

UNIT 5, COMET WAY, SOUTHEND-ON-SEA,  
ESSEX. SS2 6TR TEL: 0702-527572

and adjust it until the row numbers stabilise at 55 (again all cassette keys up). The trick is also worth knowing since with many 64s this 40-pin chip is soldered in. It not only saves a fortune in chip, also a fortune in solder!

D.C.J. Tilley,  
London E2.

### RC HANDSET CHECK

Here's a tip I've been using for the past three years when servicing remote control handsets. If you have a suspect handset in a customer's house and would like to check that it's the unit and not the TV set take a radio - if you have a car radio this will do - and tune it to an MW station with no modulation. Press the buttons on the handset: if the unit is working you'll hear a whistle as you do so. If you use a car radio the handset must be near the aerial.

William G. Lockett, Eng. Tech.,  
Rhyl, Clwyd.

### GRUNDIG SPARES

In the April Service Bureau column two possibilities were given for the problem of increasing sound with the Grundig 6010TD. These answers (manual control paddle-switches becoming leaky or a faulty SB2 memory module) were absolutely correct. You went on to say however that spares for these 13-14 year old sets are becoming difficult to obtain.


Well, a quick phone call to Grundig, using the number given in your TV/VCR spares guide, revealed that both the paddle-switch (part no. 29501.110.01) and the SB2 memory module (*correct* part no. 9.47041,1101) are available ex stock, as is the complete remote control receiver module (part no. 29301.012.01) for those who need the "module exchange" repair system.

Alternatively anyone requiring Grundig TV parts would be pleasantly surprised if he consulted your classified advertisement columns. Our company has had a small but regular advertisement for a number of years. We can supply *any* part for the 6010 and have a fairly comprehensive module exchange scheme for many sets from 1970 to the current chassis.

Grundig thyristor line timebase sets such as the 6010 tend to lead a healthy existence, with excellent colour, superb picture and decent sound - provided they are carefully treated for the dry-joint syndrome at intervals of about five years. They are far too good to pension off in the prime of life because of fears of scarce spares.

Les Austin, Ochre Mill Technical Services Ltd.,  
Lower Moddershall, Stone, Staffs.

### CRT BOOSTER CORRECTION

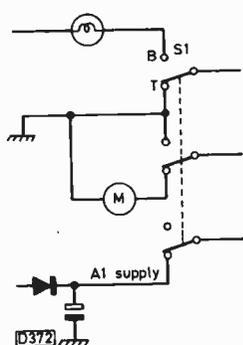

Please note an error in the simple c.r.t. booster/tester circuit shown in my article last month. The

Fig. 1: Correction to the simple c.r.t. tester/booster circuit featured last month (see page 450). An extra pole on S1 switches off the first anode supply in the boost position.

'boost/test switch S1 should be a three-pole two-way switch, the third pole removing the 90V supply to the first anodes during reactivation (see Fig. 1).

Jim Littler,  
Wigan, Lancs.

### HITACHI NP81CQ CHASSIS

In the April TV Fault Finding column fellow sufferer Les Grogan mentioned top cramp on these sets due to C608 going open-circuit. We've also had this fault. Another top cramp fault in this chassis and in the CPT2051 (not the E variety) also produces gross nonlinearity in the middle part of the raster. This is due to R614 (150kΩ) in the feedback network going open-circuit - a clue is given by the fact that the collector voltage of the top field output transistor is far too high. In one chassis (which one I forget) the set will be left tripping due to the guard circuit if R614 is removed to see whether this leaves the fault unchanged. Some chassis in this family use what looks like a half-watt job which usually doesn't fail: other sets use smaller resistors which do fail.

J.R. Armagh,  
Portadown, Craigavon.

### NORDMENDE FV/SK2 CHASSIS

I've had a couple of these sets in for repair lately. My patience was more than severely tried during the hours spent fixing them: perhaps some of the faults and symptoms may be of interest to others.

(1) Barrel distortion, i.e. bowing in from both sides. The trouble is in the EW modulator panel P. Check for open-circuits in resistor RP36 (1Ω safety type), coil LP30 or the EW modulator driver transistor TP04 (BD544B or 2N6107). The transistor *has* to be one of these two types. I tried several similar silicon pnp power transistors but they all broke down after a short period, taking the safety resistor with them. (*Editor's note:* some sets have a fuse in the RP36 position.)

(2) Dead set. This had me for a long time until eventually the second set came in and I was able to do some panel swapping. I'd originally thought that the trouble lay in the thyristor line output module U and had taken out every thyristor and tested it, all to no avail. The set just sat there dead until the horizontal line generator module Z was swapped. In went a new TDA2590 i.c. and the set sprang to life. I gritted my teeth.

(3) After a few minutes the set would lose tuning with jumping neons and hum on the field scan. Tapping hard in the bottom right-hand corner of the main PCB (track side) would restore normal operation for a few minutes. I eventually found that CA30 (2,200μF), the 36V supply reservoir capacitor, was coming adrift - the ring making contact for the negative side of the capacitor had parted from the main body.

(4) Touch tuning trouble with intermittent and jumping tuning (neons varying) was inevitably the SAS580/SAS590 pair. Correct tuning was obtained when these i.c.s were replaced.

It seems that the NordMende SK2 chassis is reliable but tricky to repair if you're not familiar with the circuitry. Both the faulty sets have now been working normally for some time, fortunately. Ploughing through has given me the confidence to work on the chassis again!

Des Walsh,  
Carrigaline, Co. Cork.

# Servicing the NordMende F10/F11 Chassis

Christopher Holland

Despite its prominence in several West European markets the NordMende brand name has made relatively little impact in the UK, though NordMende chassis have appeared in sets sold with other names on the cabinet – most notably the Ferguson 3787 colour portable. This lack of market impact has not been helped by the fact that different firms have acted as importers/agents at various times. In addition NordMende TV sets have traditionally been v.h.f./u.h.f. receivers, which means extra complication and cost in the UK market. NordMende is a leading brand in Ireland however and it's interesting that their colour chassis have always been at the forefront of TV receiver technology – some of the circuit techniques used in these chassis will be new to many TV technicians.

## Chassis Specification

The F10/11 series chassis have been in production since 1981. They are to be found in other makes of set, notably Thomson and Saba. Hitachi have also used the F11 chassis in some of their sets for markets where v.h.f./u.h.f. receivers are required. The design brief was to produce an international chassis with a single mother board on to which colour decoder, tuner and sound decoder panels could be fitted to suit the requirements of individual countries. Remote control sets can be converted for teletext use by fitting the relevant panel. All sets have a scart socket for direct connection of composite video, RGB or audio signals.

The F10 chassis was designed for use with 90° tubes in sizes from 14 to 22in., the F11 for 110° tubes in sizes from 20 to 27in. The F11 thus requires a higher output from its power supply and an EW correction circuit. Otherwise it's essentially the same as the F10. There's a later version of the F11, the F11B: more on this later.

The notes in this article will be based on the F10 chassis, with F11 chassis differences noted in brackets as they arise. Most of the circuitry is fairly conventional, particularly the signal stages, and can be quite easily understood by referring to the appropriate circuit diagram. The only areas where these chassis vary greatly from normal practice are in the power supply and field output stages. We'll look at these in greater detail.

## Power Supply Circuit

The power supply is of the step-up chopper type: the voltage level supplied to the chopper circuit by a mains transformer and bridge rectifier is raised to and stabilised at a level suitable for the line output stage which then produces other d.c. lines. Line flyback pulses provide the necessary switching. The principle of the chopper arrangement is shown in Fig. 1: the complete circuit is shown in Fig. 2.

The bridge rectifier delivers a d.c. level of 80V (F11 – 100V) to coil LP01. When the chopper transistor TP01 is switched on current flows through the transistor and this coil. Consequently energy builds up in the coil in the form of an electromagnetic field. When the chopper transistor is switched off by a flyback pulse from the line output

transformer the voltage at its collector will swing positively due to the collapsing field around LP01. This positive-going pulse is rectified by DP14 which charges CP14 to produce the 109V h.t. line (F11 – 140V). As is usual with W. German sets, this is referred to as the U1 rail. Note that the h.t. obtained in this way results from a combination of the 80V (100V) d.c. supply and the switching action of TP01.

The centre-tapped secondary winding on the mains transformer supplies a bridge rectifier which provides a 24V line (F11 – 31V) to power the audio output stage. The centre-tap is used to provide an 11.5V line for start-up purposes. This feeds the emitter of TP21 via diodes DP21, DP24 and DP03, with a chassis return via RP26, RP24 and RP21. The current flowing through RP26 develops a voltage to switch TP21 on, as a result of which CP10 charges via DP12. This line starts up the TDA1950 sync/line oscillator chip via RP27. During the start-up period the collector of the line driver transistor TL01 is fed from the centre tap via DP13. Once the line output stage comes into operation a line output transformer derived 13V supply takes over from the 11.5V line, via diode DP15. RP25 is included in series with CP10 to provide a slow-start action.

When CP10 has charged sufficiently transistor TP05 will switch on, charging CP12 via RP23. The positive-going voltage developed across CP12 will eventually switch on TP06, and in turn TP02 and the chopper transistor TP01 will switch on. Positive-going line flyback pulses are fed to the base of TP04, which is thus switched on once per line scan, discharging CP12. Drive to the chopper transistor is thus provided by the sawtooth waveform generated across CP12. The charging of CP12 is controlled by TP05 whose base samples the h.t. voltage whilst its emitter is held at a constant voltage by zener diode DP20 and DP19. Regulation is thus achieved since TP01's switch-on time is determined by the conduction of TP05: TP01 is switched off by negative-going line flyback pulses which are applied to its base via diodes DP43 and DP42. Note that this power supply arrangement is very tolerant of varying mains supply voltages. The mains level is monitored via the 11V start-up tap on the mains transformer: diodes DP21, DP24, DP03 and resistor RP07 provide a d.c. bias at the base of TP04 proportional to the level of the mains

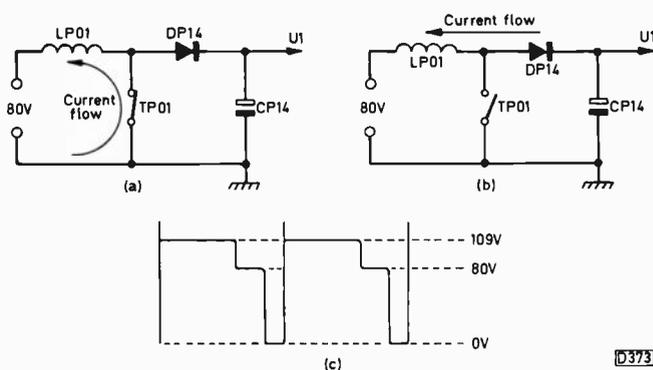


Fig. 1: Principle of the step-up power supply. (a) Chopper transistor on. (b) Chopper transistor off. (c) Waveform at the collector of TP01.



however and the following notes should prove helpful.

Any line output stage problems that cause the d.c. supplies derived from the line output transformer to rise in value will result in TP18 conducting, thus switching off the line oscillator via TP21. In this condition the full U1 value of 109V (F11 – 140V) is not developed due to the absence of line pulses. As there's no load on the power supply the U8 80V supply will rise to almost 90V. Note also that if there's a power supply fault that prevents the step-up switching taking place, e.g. transistor TP01 open-circuit, the 80V present on the U1 line is enough to allow the line output stage to operate. The result is a small raster with a severe hum bar. These symptoms are a sure sign that the line timebase is operating correctly and that the fault is in the power supply.

## Fault Notes

The following is a comprehensive list of the problems most likely to be encountered when working on sets fitted with these chassis.

**Set dead, fuse FP02 blown:** Check whether the chopper transistor TP01 is short-circuit. If it has to be replaced, check the other transistors in the power supply and resistor RP06 before switching on. A short-circuit line output transistor will also blow this fuse (the F10 chassis uses a BU208D, the F11 a standard BU208 and the F11B a BU508AV).

**Set dead, fuse FP02 intact:** Check for 80-90V (F11 100-110V) at the collector of the line output transistor. If absent check for broken tracks around the diode-split line output transformer – it's heavy and in early sets the PCB was not very well supported in this area. Check for 11V at the collector of the line driver transistor TL01. If there are no line pulses at pin 2 of the TDA1950 chip IL01 check the d.c. level at pin 14. This is normally 12V but 8V will enable the line oscillator to start up. The start-up voltage is obtained from the 11V tap on the mains transformer via transistor TP21. If sufficient voltage is present at pin 14 but there's no output at pin 2, change the i.c.

**Set dead, remote control models:** Check whether transistor TP21 is being switched off by the front remote control decoder panel. If so, suspect the 400kHz crystal first with microcomputer controlled systems.

**Set pulsing on/off:** Remove the field scan coil plug (connector BF01). If the set now starts up with field collapse there's no field sawtooth for modulation by the line flyback pulses so the line output stage is being loaded down. Check resistors RF12 and RF15 followed by the transistors in the field timebase. The culprit could also be thyristor DF08 loading the line output stage via winding 4-7 on the transformer.

If the set continues to pulse with the field scan coils disconnected check resistor RP11 in the power supply. If this is open-circuit the h.t. line will be too high. The supplies derived from the line output transformer will also be too high with the result that transistor TP18 will switch on. A fault of this type can be seen by monitoring the U1 line with an analogue meter: the voltage will flick between 80-130V as the set pulses on and off (F11 – 100-160V). If the power supply appears to be all right check for something in the line output stage causing TP18 to operate the trip circuit. The line output stage can be checked by disconnecting the base of the chopper transistor TP01: if the set now starts up, albeit with a reduced raster size and a hum bar, the line output stage is all right.

**Line tearing with excessive h.t. ripple:** Check the U8

supply reservoir capacitor CP11 – it could be dry-jointed. Also check CP12.

**Field collapse:** The usual field collapse symptom of a thin horizontal line across the centre of the screen is not often encountered with the type of circuit used in these chassis. If experienced check for something open-circuit between the anode of thyristor DF08 and the field scan coils via coil LP01 – this coil is a separate winding on the same former as the coil used in the switch-mode power supply and the PCB tracks to its pins should be checked.

**Picture shifted upwards, with field roll:** This is the most common field fault with these sets: it's caused by transistor TF09's d.c. biasing being incorrect. Check RL52 (15 $\Omega$  – this is the U3 supply surge limiter resistor), RF20, RF21 and RF10, also the height preset control PF02. In earlier chassis PF02 was a 100 $\Omega$  preset: it was changed to 47 $\Omega$  with a fixed 47 $\Omega$  resistor in series.

The transistors used in the field timebase seldom give trouble: unfortunately when they do they often appear to be good when checked with an ohmmeter, so substitution is the only effective test.

**Uncontrollable field roll:** Check transistor TF02 and capacitor CF01.

**No raster except for a wide horizontal band near the bottom of the screen:** Check whether the U4 (200V) supply surge limiter resistor RL51 (39 $\Omega$ ) is open-circuit.

**E.H.T. but no raster:** Check RL54 if the tube's heaters are out. If the tube's first anode voltage is absent or low (should be 350-400V) check the adjustment of the lower preset on the diode-split line output transformer: if adjustment is not possible the transformer will have to be replaced. Otherwise check transistor TV81 (BC557B) and resistor RV82 (10 $\Omega$ ) on the tube base panel. Note that a fault in any of the three RGB output stages on the tube base panel can cause the TDA3506 RGB matrixing i.c. IV02 to cut off all three guns, thus giving a blank raster.

**Excessively bright raster with flyback lines and no luminance:** Check for excessive first anode voltage. If this cannot be adjusted, or adjusts to the correct level then drifts again, replace the diode-split line output transformer. This fault can also be caused by failure of the TDA3506 RGB matrixing i.c. IV02: first check whether its d.c. supply resistor RV23 (10 $\Omega$ ) is open-circuit. In the unlikely event of IV02 failing after replacement check whether CV91 (0.001 $\mu$ F) on the tube base panel is short-circuit.

**One primary colour weak:** Check CV38, CV39 or CV40 (0.68 $\mu$ F) associated with the TDA3506 chip as appropriate. Could also be caused by the chip itself.

**Excess of one primary colour:** Check CV47, CV48 or CV49 (0.022 $\mu$ F) associated with the TDA3506 i.c. as appropriate.

**No colour:** Suspect the 4.43MHz crystal QC02 or the AN5620X colour decoder chip IC01 on the PAL decoder panel. If the positive-going line flyback pulses are missing at pin 7 of this i.c. check transistor TL41 (BC548B).

**Raster but no noise spots:** Suspect the combined tuner/i.f. block which produces a composite video signal at pin 23, but first check the d.c. supply to the tuner. Can also be caused by the TEA2014 video switching chip IV03 – this i.c. is used to switch off the video signals from the tuner/i.f. block and switch in the signal from the scart connector when the correct switching level is connected to pin 8 of this connector.

**No tuning:** Before changing the tuner block, check that the U1 supply is reaching the front panel where it feeds the 33V zener diode (the circuit reference number for this

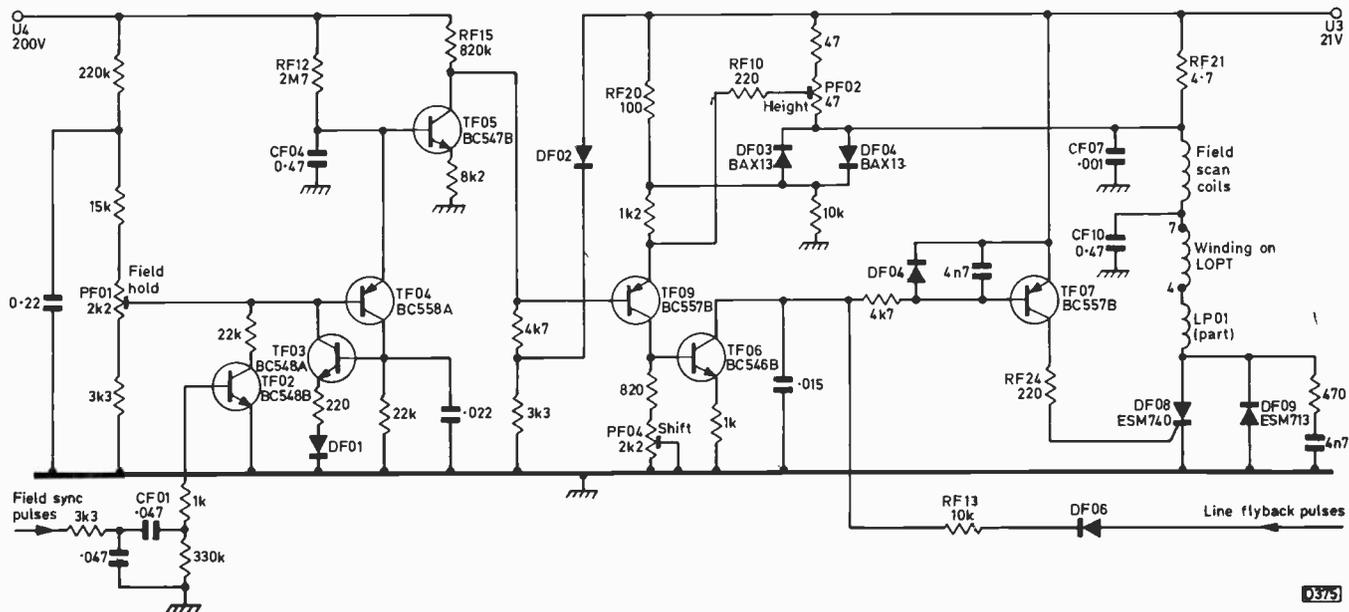


Fig. 3: Complete field timebase circuit, F10 chassis. RF12 is 3.3Ω in the F11 chassis – there are other minor variations.

diode varies with different models). If the U1 supply is not present at the front panel check RL53 (100Ω) and CP24 (0.01μF). Check the 33V zener diode itself, also the u.h.f./v.h.f. band selection circuit on the front panel. The usual culprit however is the tuner block itself. Note that it is also almost the only cause of tuning drift.

**No sound:** These sets all have a sound mute system which operates when no video signal is received. It compares the composite video signal with line flyback pulses within the TDA1950 chip: if the sync pulses in the video signal don't coincide with the flyback pulses pin 7 of this i.c. goes to 0V (it's normally at 11V) and the sound is muted via pin 2 of the TBA120UB intercarrier sound i.c. This muting circuit should be kept in mind when fault finding: for example, on a set with no sound and a video fault don't chase a sound fault as the muting circuit will operate due to the absence of the video signal. The muting circuit can also give clues however: for example, a set with no video but good sound means that the fault is in the latter part of the video channel, certainly after pin 6 of the TEA2014 switching chip IV03 (this is the take-off point for the video feed to the muting circuit).

Where there's no sound and the muting is not in operation, i.e. pin 7 of the TDA1950 chip is at 11V, check the TDA2006 audio output chip IS01. Note that many of these sets have been built with stereo use in mind: a second audio output chip is often fitted but not connected up – this is a convenient source of a replacement if you do

0376

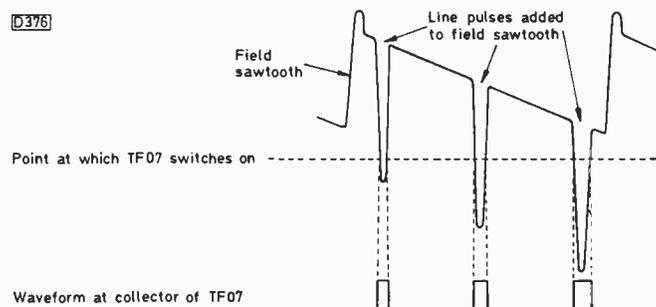


Fig. 4: Showing the way in which adding line pulses (three only shown) to a field sawtooth waveform gives pulse width modulation at the collector of TF07 so that DF08 is switched on progressively earlier as the field scan progresses.

not have one readily to hand.

## Spares

The agents for NordMende sets in Ireland are Reynolds Electronics Ltd., Finnabair Industrial Park, Dundalk, Co. Louth (042 31 281). The UK agents are Hayden Laboratories Ltd., Hayden House, Chiltern Hill, Chalfont St. Peter, Gerrards Cross, Bucks SL9 9UG (0753 888 447).

TV LINE OUTPUT TRANSFORMERS		
PRICES INCLUDE VAT & CARRIAGE		
Delivery by return of post.		
<b>BAIRD:</b> 8290, 8752, 8773	10.44	<b>ITT:</b> VC200 to VC402 9.20 CVC1, CVC2 (FORGESTONE) 11.50 CVC5, CVC7, CVC8, CVC9, CVC20 10.35 CVC25, CVC30, CVC32, CVC45 9.20 CVC800, 1100, 1150 P.O.A. CVC1200, 1204, 1210, 1215, 2600 P.O.A.
<b>RANK BUSH MURPHY</b> A774 with stick rectifier 9.78 A816, T16, T18, Z712, Z715 10.35 T20, T22, T26, Z179, A823 11.50 Z718 Basic unit 13.50		<b>PYE:</b> 169, 173, 569, 368 9.20 CT200, CT200/1, CT213 10.35 725-731, 735, 737, 741 9.78
<b>DECCA:</b> 1210, 1211, 1511 11.50 1700, 2001, 2020, 2401, 2404 9.20 CS1730, 1733, 1830, 1835 9.20 30, 70, 80, 90, 100, 120, 130 9.20		<b>PHILIPS:</b> 170, 210, 300 series 9.20 320 series 9.78 TX, T8, TX2, TX3 mono P.O.A. G8 and G9 Series 9.20 KT2, KT3, series 9.20 G11, K30, split diode P.O.A.
<b>FERGUSON, THORN:</b> 1590, 1591 9.20 1690, 1691, built in rect. 9.78 1600, 1615, 1700, 1790 P.O.A. 3000, 3500, 8000, 8500, 8800 P.O.A. 9000, 9200, 9300 series 12.00 9500, 9600, 9650 series 10.99 9800, TX9, TX10 series P.O.A. MOVIESTAR 3781, 3787 12.00 TX10 focus unit 10.25		<b>BINATONE:</b> 9909, 9860, 9488 P.O.A. DORIC Mk3, Mk1 11.50 FINLUX 9560, 9670 P.O.A. GRUNDIG: most models in stock P.O.A. NORDMENDE: 8290, Z206, Z306 P.O.A. SANYO: 5101, 5103, 7118 P.O.A. SHARP: C1851H, C2051H P.O.A. TOSHIBA: C800, C800B P.O.A. TANDBURG: 190, CTV2, CTV3 P.O.A. TELEFUNKEN: most models in stock P.O.A. HITACHI: 1471, CPB260, 2501 P.O.A. SIEMANS: FF series P.O.A.
<b>FIDELITY:</b> FTV12 mono 10.35 ZX2000 ZX3000 P.O.A.		<b>Tidman Mail Order Ltd.,</b> 236 Sandycombe Road, Richmond, Surrey. Approx. 1 mile from Kew Bridge. Phone: 01-948 3702 Mon-Fri 9 am to 12.30 pm & 1.30-4.30 pm Sat 10 am to 12 noon.
<b>G.E.C.</b> 2047 to 3135 mono 9.20 1201H, 1501H, 2114, 3133, 3135 9.20 DUAL & SINGLE hybrid col. 10.00 SINGLE STD solid state 12.00 SINGLE STD split diode P.O.A.		<b>WINDINGS</b>
<b>INDESIT:</b> 24EGB, 12LGB, 12SGB 10.35		<b>TYNE:</b> main winding 6.80 <b>RBM:</b> T20, T22, T26, Z179 6.33 <b>WALTHAM:</b> W125 eht winding 2.37 <b>WALTHAM:</b> W190, W191 eht coil 6.00 <b>KORTING:</b> hybrid winding 6.90 <b>THORN:</b> 8000, 8500, 8800 eht 6.70

# Teletopics

## **AGREED UK STEREO TV STANDARD**

The BBC has been carrying out tests on a digital stereo sound system of its own design since late 1983 – we last reported on the subject in this column in August 1984, after tests to confirm the system's compatibility with non-stereo receivers had been carried out. The system that's been evolved is called 728-Nicam (near instantaneous compansion) and has been agreed by the IBA. It's at present awaiting approval by the Department of Trade and Industry. Since transmitters are already installed at Crystal Palace a London area service could be started in a matter of weeks: it would take some years to convert all the BBC/IBA transmitters. It's understood that Thorn EMI Ferguson has a decoder chip set at an advanced stage of development and that incorporating stereo sound would add about £30 to the cost of a receiver.

The system uses a single carrier spaced at 6.55MHz above the vision carrier, with four-phase shift-key modulation: the transmitted data rate is 728Kbits/sec. The original analogue sound signal is sampled at a rate of 32,000 times a second, the samples being converted to 14-bit words. To get the signal into the spectrum space available 10 bits are transmitted along with a signal to indicate to the receiver the compansion that has taken place. As a result the receiver can reconstruct and decode the original 14-bit samples. One advantage of the system is its compatibility with the MAC standard proposed for satellite TV transmissions.

## **DBS PROGRESS**

The IBA has now advertised for contractors to provide three new TV services by satellite transmission, to be receivable throughout the UK. Applicants have been invited to submit proposals by August 29th with a view to the IBA selecting and appointing contractors by the end of the year with services coming into operation by 1990. Applicants have been invited to apply for a contract to provide all three services – with a variety of programming between the three channels – to be financed either by advertising, by subscription or a combination of the two. Those proposing to provide fewer than three services are asked to indicate what forms of co-operation they would plan with other contractors. Applications have also been invited for contracts to provide teletext DBS services, both from those applying for the programme contracts and others. The government intends to introduce legislation so that the contracts would last for up to fifteen years, under the terms of the Cable and Broadcasting Act 1984.

Meanwhile the election of a new government in France has called into question the Maxwell group's plans (see last month) to provide programmes on two of the French TDF-1 satellite's channels. Mr. Maxwell maintains that he has a binding contract but the new government has indicated that it plans to cancel this, with six months' notice, and open the allocation of TDF-1's DBS channels to competitive tendering.

## **INTERNATIONAL TRADE**

The effects of the rise in the value of the yen, mentioned in our leader last month, are already showing through. Matsushita has reported the first fall in sales and profits

for eleven years, during the first quarter of its financial year which ended on February 20th. Consolidated profit fell by 19.3 per cent and sales by 8.7 per cent. Domestic sales fell by only 1.1 per cent while overseas sales recorded a decline of 16 per cent – sales of video/TV equipment fell by 17.2 per cent. Reduced colour receiver exports to China and a sluggish demand for components were given as contributory factors. Matsushita proposes to increase overseas selling prices and transfer some production to other south east Asian countries.

Sanyo is increasing the prices of its VHS VCRs in the UK by between £30 and £50 depending on model and predicts that other Japanese manufacturers will be doing the same.

The Thomson group is to cut its workforce in European colour receiver plants by between 20 and 25 per cent – about 1,000 jobs in W. German plants will go, 550 jobs in France and 300 in Spain. Last year Thomson's consumer electronics group made a loss of £30 million on sales of some £2.1 billion. The overall proposal is to cut the workforce from 8,500 to around 7,000. Thomson, whose brands include NordMende, Saba and Telefunken, is one of Europe's two largest CTV manufacturers: colour TV accounts for roughly fifty per cent of Thomson's estimated annual consumer electronics output. Europe's other major consumer electronics manufacturer, Philips, plans to close a number of TV manufacturing plants.

Matsushita has announced the development of a 1Mbit video DRAM. Mass production is expected to start by the end of the year. Two such chips are required to store a TV field.

## **THORN-JVC DEAL**

An agreement has been reached between Thorn EMI Ferguson and JVC for the manufacture at Ferguson plants of colour receivers to meet JVC's requirements in the UK and continental European markets. Under the terms of the agreement a range of products incorporating JVC's newly developed BX chassis will be manufactured by Ferguson with technical and production support from JVC: the new manufacturing operation will be managed by Ferguson and will require substantial additional equipment and dedicated production facilities. A new production line to be installed at Gosport will be able to produce over 200,000 sets a year. Enfield will supply PCBs and High Wycombe cabinet mouldings.

## **ORION'S UK PLANT**

The Orion Electric Corporation of Japan is to set up a VCR/TV manufacturing plant at Kenfig Hill, South Wales – the 50,000 square feet factory was previously used by computer manufacturer Dragon Data. The first phase of the operation will be the installation of a production line for VHS VCRs: production is expected to be running at a rate of 10,000 machines a month by the end of the year. A CTV line will probably be added next year to produce sets for sale in the UK and continental Europe. Assistance tied to the number of jobs created will be provided by the Welsh Development Agency. Orion products will continue to be distributed in the UK by L and M Raymond of Watford. Sales are mainly to major retailers – Orion VCRs are sold by Dixons under their Saisho brand name.

## **TV SYSTEMS TESTED**

With the co-operation of Swindon Cable Ltd. IBA engineers recently demonstrated for the first time successful distribution of full-capacity MAC TV signals via a mod-

ern, operational cable system. Full-resolution MAC-encoded vision with digital sound at a data rate of 20-25Mbits/sec were inserted at the head end of Swindon Cable's multichannel system, using the EBU's "cut and rotate" scrambling system. A receiver connected to an existing domestic socket outlet produced pictures without any significant degradation.

A demonstration of the MUSE system has been carried out by RAI and NHK at Turin. The Japanese MUSE (multiple subnyquist sample encoding) system has been developed to enable high-definition TV signals to be transmitted using standard satellite TV channel bandwidths. Reception of MUSE-encoded signals via a noisy satellite transmission path is said to have produced pictures virtually identical to the original HDTV ones.

### **NEW FILM CABLE CHANNEL**

British Telecom is to offer cable operators a new film channel, with material sourced from MGM/UA, Paramount and Universal initially. It will compete with Robert Maxwell's Premiere channel, with which MirrorVision was recently amalgamated. Distribution of the new channel to cable operators will be via cassette rather than satellite transmission.

### **VCR SERVICING VIDEOCASSETTES**

Flintdown Ltd. (Mountauban Chambers, 339 Clifton Drive South, Lytham St. Annes FY8 1LP) has produced a series of seven cassettes on servicing domestic VCRs. The series consists of (1) an overview of VCR systems, (2) servo control systems, (3) colour recording systems, (4) frequency modulation, (5) VHS, Betamax, V2000 and Video 8, (6) component video and (7) VCR faults. Each cassette is available in any standard format and costs £35 plus VAT - a discount of 10 per cent is given on a complete set of seven cassettes.

### **VIDEO EQUIPMENT**

JVC has launched a midi-sized hi-fi VCR, Model HRD470, which is expected to retail at around £600. The tape deck has been rotated through 180° to give front-loading of the cassette end first.

Kodak is test marketing some electronic still picture systems in the USA. A disc recorder-player enables 50 TV fields from a TV set or other video source to be recorded on a standard 2in. floppy disc. Recording is triggered by remote control. A companion printer produces prints of any recorded field on instant colour film. There's also a film to disc transfer service which enables 35mm colour film negatives to be recorded on disc for playback via the recorder-player.

Grundig has introduced a combined colour receiver/VCR unit, Model TVR5000, which is expected to sell at around £950. The VCR incorporated is the new VS300 which features auto tape time select, electronic locking and can record two programmes up to a year ahead.

### **AMSTRAD TAKES OVER SINCLAIR'S COMPUTER INTERESTS**

Amstrad has bought the world-wide rights to Sinclair Research's current computer interests. Sinclair is now a research organisation without marketing operations. A computer under development by Sinclair will be offered to Amstrad at a later date.

Amstrad is to continue production of the Spectrum computer in the UK for the present. Sales of the QL will

continue while stocks last but this machine will probably be phased out. Interesting that Amstrad decided not to take on Sinclair's pocket monochrome TV set. Amstrad paid £5 million for the right to use the Sinclair brand name and current stocks.

### **TV/VCR SPARES GUIDE**

Some corrections and an addition to the spares guide published with our April issue. Spares for recent NEC products are available from NEC Business Systems (Europe) Ltd., NEC House, 164-166 Drummond Street, London NW1 3HP or from SEME Ltd., Unit 2E, Saxby Road Industrial Estate, Melton Mowbray, Leics. Models include CTVs 12T311, 20T772, 20T773, 14T412, 14T1406, CT1404, FS1901, FS1902, CT1416 and FS1502 and VCRs PVC744E and PVC746E (Beta) and N830EK, N831EK, N833EK, N9013 and N9014 (VHS). Spares for earlier NEC models distributed in the UK by Cap Ten are available from Tech Semco.

The address we gave for Tensai was the last known one. It appears that this company is no longer represented in the UK. Don't use the phone number we gave - it's been transferred to a domestic user.

Spares for three Gold Star monochrome portables, Models VW300, VR317 and VR700, are available from Uni-Com Electronics, Station Road, Edenbridge, Kent TN8 6EW (0732 865 238).

CPC of Preston was mentioned in the Letters column last month as a supplier of spares for Sinclair microcomputers. The full address is CPC Electronic Component Distributors, 194-200 North Road, Preston, Lancs (0772 555 034). CPC are also official spares stockists for Fidelity, Ferguson, Philips, Pye and Sony.

### **TVRO EQUIPMENT**

Megasat's new top-of-the-range satellite TV receiving system is said to be the only totally automatic remote-controlled system on the market with a computer-generated "menu" of programmes presented on the screen for user selection. Any programme can be selected by remote control without the user leaving his chair. The remote control system includes the motorised dish and automatic polarisation. Price is £2,645 including VAT (plus installation). The Megasat system is available from Harrods, Wallace Heaton and Lasky's Tottenham Court Road and Brent Cross stores.

NEC's NESAT satellite TV receiver system is now available with an automatic aerial tracking system. The actuator motor is linked by cable to a microprocessor controlled tracker unit which can be located anywhere in the vicinity of the TV set. An LED display shows the dish position.

Sat-Tel has developed a battery-operated satellite TV signal meter to simplify dish installation. The meter, called the Skyhound, plugs directly into the LNC's output and in addition to the meter display has a variable audio pitch indicator.

A new transistor from Mullard, type BFG195, has a transition frequency of typically 7.5GHz and a unilateral power gain of 12dB at 2GHz. It can handle a power dissipation of 0.5W and is said to have the highest, presently available power handling capability for this category of transistor. The four-lead, dual-emitter transistor is intended for applications in high-gain wideband systems up to 2GHz, e.g. in the first i.f. section of a satellite TV receiver.

# The Development of Colour Tubes

Part 1

Eugene Trundle

The picture tube is the very heart of a colour set or monitor, its characteristics dictating not only the shape and size of the set but the design of every other section of the receiver apart from the tuner, the i.f. amplifier and the control system. Even the sound system is related to the tube in that the loudspeaker usually has to be accommodated alongside and its shape, size and magnetic field must conform, while the audio amplifier is (or should be) tailored to the type of loudspeaker in use.

## The Early Days

Colour picture tubes have been with us since late 1949, when Dr. Harold B. Law made the first shadowmask tube at the RCA company's Princeton, New Jersey laboratories. The picture was small, about 11cm in diameter, and the resolution and convergence performance were very poor by today's standards. Most of the ingredients of subsequent tube technology were there however: three guns, one for each primary colour; a tri-colour phosphor screen; and above all the shadowmask. In one form or another the shadowmask has been present behind our screens ever since.

The original RCA design was based on an idea by A. C. Schroeder, patented by him, for a delta-gun/mask/triad-phosphor-dot screen configuration. A much earlier patent for a colour display tube, filed in Germany by Werner Flechsig in 1938, proposed the shadowmask in an aperture-grille form: this uncannily anticipated the Trinitron tube introduced by Sony of Japan some thirty years later.

The first delta-gun tubes had an internal phosphor-dot screen which was flat, as was the shadowmask mounted some 1.2cm behind it: the curved glass faceplate acted merely as a clear window. It wasn't until 1954 that tubes with the phosphors deposited on the rear of the curved faceplate went into production. These had a deflection angle of 70°, a circular 21in. (53cm) screen, a huge 51mm diameter neck and a metal cone. An all-glass version went into production three years later.

## Tube Evolution

Gradual improvements in the phosphors, mask and faceplate light transmission characteristics were introduced before the next big step in 1964, the 90° deflection tube with a rectangular 25in. (63cm) screen. This was followed shortly after by a 19in. (49cm) version. The popular 22in. (56cm) 90° tube came in 1967.

1968 was a significant year. In April the Sony Trinitron tube was released, initially in a 33cm (13in.) rectangular format with 90° deflection. With its in-line gun assembly and striped phosphor screen it was the precursor of all the current tube designs: a grille with slots from top to bottom performed the same function as the shadowmask. The rest of the world followed: RCA's PIL (precision in-line) tube with its slotted shadowmask and striped screen was introduced in 1972 and was followed over the next few years by many variants. The great advantage of the PIL tube was the elimination of the need for the convergence

circuitry required with delta-gun tubes.

The first 110° shadowmask tube was introduced in 1969 – especially for Europe, as the US market wasn't at that time into wide-angle colour tubes. It was a delta-gun tube with a thick neck (36.5mm). 110° tubes with 29mm neck diameters appeared as early as 1970. The seventies saw a succession of developments: saddle-toroidal yokes in 1973; internal magnetic shields, quick-heat cathodes and the Philips 20AX tube in 1974; "soft flash" in 1977; the Philips 30AX system with no need for setmaker or service technician adjustments in 1978, along with pincushion-distortion free (pin-free) tubes from Japan. In 1979 the mini-neck tube (22.5mm diameter) came from Japan and in 1982 Toshiba introduced the FST (flat square tube) screen. To bring us up to date, the Philips 45AX tube was introduced in 1984 and in 1985 Sanyo demonstrated small, prototype beam-indexing tubes – this type of tube has a single gun with switched RGB inputs and no shadowmask (the idea is not new but its realisation has always proved difficult, mainly because of the problem of switching the video signals at the high frequency required).

## The Delta-gun Tube

Since we're going to describe the components and techniques used in colour tubes in some depth it's important that their basic operation and principles are understood. Although delta-gun tubes are now obsolete as far as domestic TV sets are concerned they are still in production for use in monitors and advanced computer displays since they are capable of giving very high definition displays when fitted with a fine-pitch shadowmask. Let's start then with a brief rundown on delta-gun tubes.

The virtue of all types of direct-viewing colour displays (as opposed to multi-tube projection systems) is that the tube used simultaneously produces on its screen light in the three primary colours red, green and blue. This implies the presence on the screen of three different phosphors, and the trick is to ensure that the electron beam from each gun strikes only the appropriate phosphor material. Hence the shadowmask which, for each beam, casts a shadow over the phosphors the beam shouldn't reach. The delta-gun tube has three electron guns arranged in equilateral triangular formation in the tube's neck – see Fig. 1. The guns are each tilted towards the tube's major axis so that their electron beams converge at the shadowmask. Because the beams come from three different "aiming points" their approach angles differ: this is the key to the operation of the mask (see Fig. 2). The beams cross over at the shadowmask and diverge beyond it, each to strike its correct phosphor dot.

## Colour Purity

So far as the mask and screen are concerned the origin of the beams is not the delta-gun assembly itself but a point in space in the tube neck, at the centre of the deflection yoke, called the deflection centre. By fitting a lamp at the apparent source of each beam in turn the positions of all the phosphor dots for each colour can be

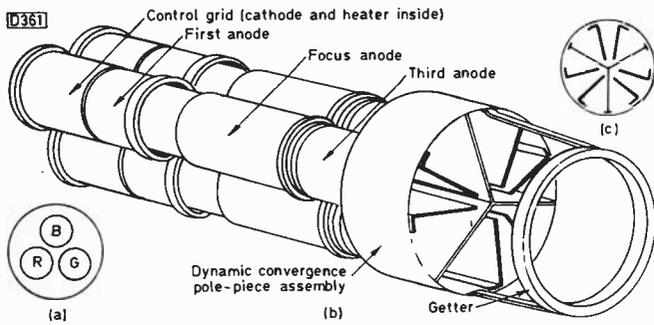


Fig. 1: The thick-neck, delta-gun arrangement. (a) Positions of the three guns in the tube neck. (b) Configuration of the gun electrodes and convergence pole-pieces. (c) Axial view of the pole-pieces mounted at the end of the guns: the pole-pieces guide the magnetic fields from the adjacent radial convergence coils.

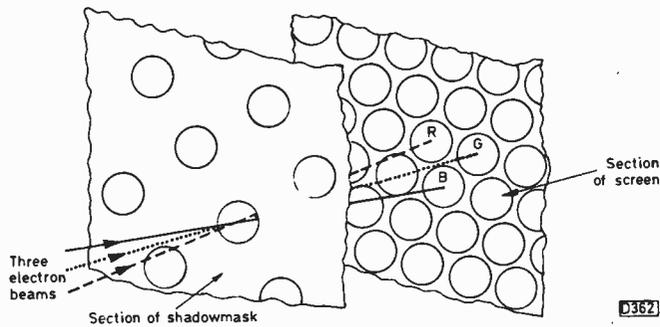


Fig. 2: Trajectories of the beams in a delta-gun tube. In practice each beam is larger than one shadowmask hole.

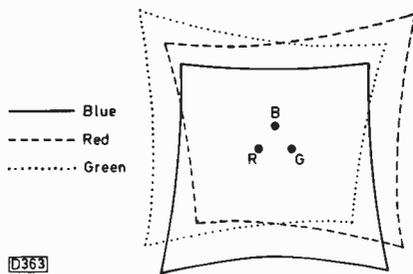


Fig. 3: The inherent raster geometry errors with a delta-gun tube.

fixed photographically with reference to the perforated shadowmask. This is done during manufacture and ensures that provided each beam is correctly aligned at the deflection centre perfect colour purity will be produced in operation, with no overshooting of the electron beams on to phosphor dots of the wrong colour at any point on the screen. Purity setting is easy to adjust: we manipulate a pair of ring magnets to align the beam trajectories through the deflection centre, then adjust the position of the deflection centre itself by sliding the deflection yoke along the tube's axis.

### Convergence

The problem with the delta-gun picture tube configuration is its inherent registration errors. The three rasters, red, green and blue, are traced out by separate electron beams coming through the deflection centre at three different angles – each is subject to different aberrations in the scanning process. This results in the complex raster geometry errors shown in Fig. 3. Each colour raster has a different combination of trapezium and pincushion distortion. To pull these odd and divergent rasters into registra-

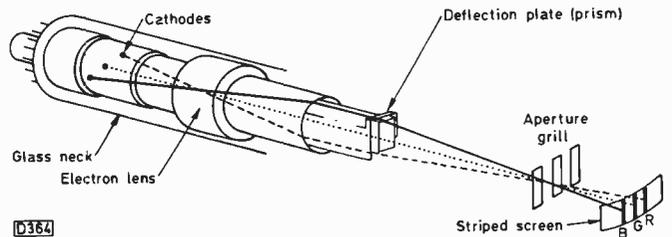


Fig. 4: Principle of the Trinitron tube.

tion, i.e. to overlay them, calls for individual and close control over the positioning of all three beams as they enter the deflection field. A static magnetic field will suffice to pin together the raster centre points (static convergence) but to make the edges of the three individual rasters register each beam must be subjected to a continuously varying magnetic field (dynamic convergence). A parabolic correction waveform is required to iron out the pincushion distortion while a sawtooth correction waveform will cancel trapezium distortion. Hence the "tilted sawtooth" current waveforms in the radial dynamic convergence correction yoke. These are required at both line and field rate, and must be adjustable in amplitude and tilt – and in shape in the case of the blue horizontal correction waveform for 90° tubes and for most functions with 110° tubes.

The difficulties, the compromises necessary, the expense of providing the convergence hardware, the skill needed in aligning the many presets, the power loss in the entire convergence network and its vulnerability to drift prompted the tubemakers to investigate different arrangements for the picture tube. The goal was to produce a tube that has an inherent self-converging characteristic. So long as there are three beams travelling along the tube on different paths this is very difficult! The solution adopted was to mount the guns in line so that the three beams travel abreast and to build correction into the tube and its yoke, something that calls for a very high degree of manufacturing accuracy. Before we come to the self-converging PIL tube however we should look at the first in-line tube to be mass produced, the Sony Trinitron.

### The Trinitron Tube

The principles of the Trinitron tube are shown in Fig. 4. The tube has several advantages over the delta-gun type of tube. These spring from its use of a single in-line electron gun assembly and an aperture-grill form of shadowmask. The electron gun has three separate cathodes arranged side-by-side: all the other electrodes are common to the three beams. This facilitates the use of a single, large-diameter electron lens (see later) in the centre of which the beams cross over, making for minimum aberration and a reduction of the scanning spot size (in comparison with the delta-gun tube) of about 25 per cent. The two diverging outer beams are redirected by an electronic prism (a set of electrostatic deflection plates) so that they converge and cross over at the aperture grille.

The aperture-grille shadowmask consists of a metal sheet with a large number of evenly-spaced vertical slits to provide shadowing for groups of three (RGB) phosphor stripes. This form of construction has little stiffness in the vertical direction and has thus to be kept under considerable tension to prevent sag or buckle. One consequence is that a parabolic faceplate contour cannot be used – Trinitron faceplates have a cylindrical contour with the

vertical profile straight. The transparency of the aperture grille was about 33 per cent greater than that of the shadowmasks used in contemporary delta-gun tubes, giving a brighter image for a given beam current. This and the 25 per cent smaller spot diameter gave the Trinitron tube a considerable advantage, which was widely acclaimed.

Having the three beams in the same horizontal plane brings two benefits: first the purity is virtually unaffected by horizontal magnetic fields such as the Earth's; secondly the need for vertical convergence correction disappears because the deflected beam trajectories remain in a single horizontal plane. The fact that the three beams are very close together on their journey through the deflection field also minimises horizontal misregistration of the three rasters. Total errors are reduced to those shown in Fig. 5. The standing voltage on the prism electrodes is adjusted to achieve correct static convergence on the vertical centre line, leaving a relatively simple dynamic convergence correction problem which can be solved by applying a parabolic waveform to the prism electrodes, see Fig. 6. Minor trimming is carried out by tilting the deflection yoke and adjusting the line-rate (and, in large-screen versions, field-rate) sawtooth current in a single four-pole convergence coil associated with the deflection yoke. These are purely trimming adjustments to take up tube and yoke manufacturing tolerances, not correction for inherent geometrical errors as in delta-gun tubes.

### The PIL Tube

The Trinitron design showed the advantages of the in-line gun configuration. It was not long before the PIL tube came along. The main differences between the two tubes are as follows: in the PIL tube there are staggered crossties in the mask assembly (see Fig. 7) to provide sufficient mechanical rigidity to enable a conventional parabolically curved faceplate to be used, and the elimination of all need for dynamic convergence correction. This is achieved by a very special deflection yoke design in which the density of the magnetic flux in the tube's neck is not homogeneous, as in a monochrome or delta-gun tube, but astigmatic.

The degree of deflection applied to an electron beam is proportional to the deflection field's magnetic flux density. To scan a picture tube horizontally and vertically both deflection field strengths change continuously according to a sawtooth law, but at any given instant the total flux density present is proportional to the distance from screen centre to the point at which the beams strike the screen. If the magnetic field required is carefully distributed in the tube's neck it's possible to achieve good convergence all over the screen area. Fig. 8 shows the effect of a uniform deflection field in a tube cross-section: the three beams converge at the screen centre and since each is affected equally by the deflection field they will converge at a point along a circular line (the image field) whose radius is the deflection centre to screen centre spacing. Beyond this crossover point the beams will diverge, striking the relatively flat tube screen at points a, b and c.

The operating principle of the PIL tube depends on a special deflection yoke design which produces magnetic flux lines distributed in the tube's neck in the manner shown in Fig. 9, which is again a tube cross-section drawn looking from above the tube to show horizontal deflection. In this astigmatic field the deflection force acting on

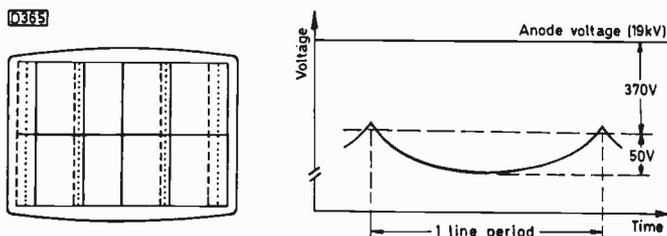


Fig. 5 (left): The Trinitron tube's basic convergence errors. The absence of crossover with the R and B verticals is due to the use of an astigmatic vertical deflection field.

Fig. 6 (right): Voltage and waveform applied to the prism electrodes to correct the misregistration shown in Fig. 5.

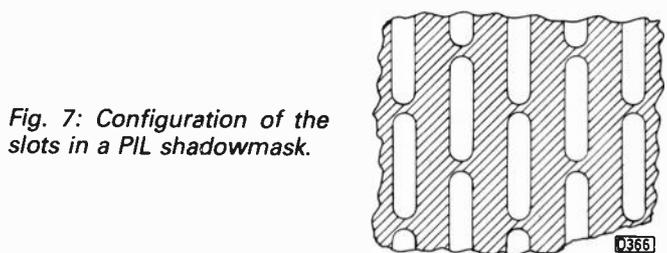


Fig. 7: Configuration of the slots in a PIL shadowmask.

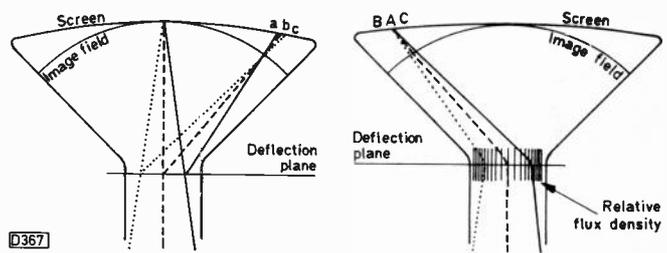


Fig. 8 (left): An in-line gun array projecting three beams through a homogeneous deflection field.

Fig. 9 (right): With careful distribution of the deflection field flux density, convergence is automatically achieved over the entire screen area.

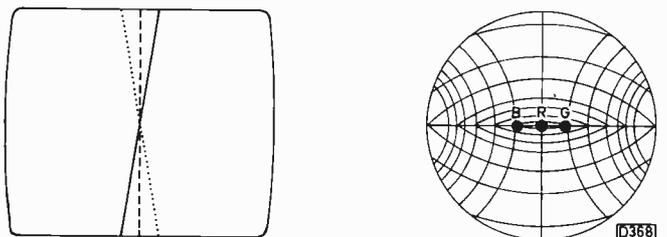


Fig. 10 (left): Errors arising from vertical deflection of in-line beams by a homogeneous magnetic field.

Fig. 11 (right): Opposing astigmatic line and field deflection fields in a fully self-converging yoke/tube system.

a given beam depends on the path taken by the beam through the deflection field. The centre beam, taking this first, passes through the relatively weak field in the middle of the deflection centre and is deflected to point A on the screen. The right-hand beam will start to turn left as it enters the deflection field. It then passes into an area of reduced flux. As a result the deflection force acting on it is reduced and it turns through a lesser angle than the centre beam. If the flux density in the deflection field is tailored to be just right the beam will converge with the centre beam at point A instead of crossing the centre beam's path to strike the screen at some point B. As the left-hand beam starts to turn left it encounters an increasingly strong magnetic field. This bends it farther to the left with the result that it's aimed precisely at point A on the screen

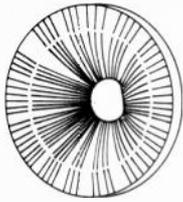


Fig. 12 (left): Earliest form of toroidal deflection yoke for a PIL tube.

Fig. 13 (right): Saddle-wound yoke for a 110° 20AX self-converging tube, showing the horizontal deflection coils.

– if it passed through a homogeneous field it would strike the screen at some point C. The same principle applies when the three beams are deflected to the right instead of to the left.

Now for vertical deflection. As the beams are deflected upwards or downwards from screen centre the yoke-to-screen beam path becomes progressively longer, which would lead to horizontal displacement of the three images due to crossover of the beams before they reach the screen, see Fig. 10. To counter this the horizontal lines of magnetic flux, which produce the vertical deflection, are given an increasing vertical component away from the tube's axis – the field is increasingly barrel shaped.

The horizontal and vertical field patterns required are shown in Fig. 11. These astigmatic fields are achieved by the deflection yoke's winding pattern: the configuration of the toroidally-wound yoke is shown in Fig. 12. The effective field pattern (and hence dynamic convergence trimming) can be adjusted by tilting the front (screen) end of the deflection yoke to achieve optimum registration of the three rasters. In the original PIL tube design this was carried out at the tube factory, using a yamming jig (YAM = Yoke Alignment Machine), after which the yoke was wedged and sealed to the tube with a thermosetting adhesive. The tube and yoke thus became effectively a single assembly and replacement tubes came with sealed on yokes. In subsequent designs the yoke and tube were treated as separate components, with alignment left to the setmaker or TV technician.

Purity (initial alignment of all three beam paths) and static convergence (individual control of the effective point of origin of the two outer beams) is provided by a combination of two-, four- and six-pole magnets mounted on the tube's neck behind the deflection yoke. These were sealed in the original type of PIL tube but can be adjusted in later in-line tube designs.

To summarise, the PIL type tube trades the complications of delta-gun tube convergence for very tight manufacturing tolerances in both the tube and yoke design. We'll return to both of these later, but before doing so we must examine the approach taken by Philips/Mullard in their 20AX in-line tube design.

## 20AX System

This was the first European successor to the delta-gun tube. It has three separate guns mounted in-line in a thick tube neck (36.5mm diameter). The deflection angle is 110° (the deflection angle with the original, smaller screen size PIL tubes was 90°: the later larger screen tubes have 110° deflection). With the 20AX tube the manufacturing tolerances are sufficiently tight not to require any tilting of the yoke assembly. Instead, manufacturing tolerances are taken up by introducing adjustable sawtooth currents at

line and field rate in a four-pole convergence correction coil built on to the deflection yoke and by differential adjustment of the sawtooth scanning currents flowing in the separate halves of each deflection coil pair. These current controls are provided by half a dozen preset potentiometers or links. Static convergence and purity are catered for by a cluster of two-, four- and six-pole ring magnets of similar design and working on the same principles as those used with the PIL tube.

## The 30AX Design

All the adjustments required with the 20AX tube were eliminated when the next Philips design, the 30AX, came along some four years later. This is similar in principle to its predecessor but with such close yoke design tolerances that dynamic convergence trimming adjustments are no longer necessary. The cluster of ring magnets on the tube neck was replaced by a special magnetic ring mounted inside the tube, on the top of the triple-gun assembly. This has a combination of two-, four- and six-pole fields printed into it during manufacture, using a computer-controlled external magnetising jig. These fields are "customised" for each tube, which is thus brought to design centre tolerance in respect to picture geometry, purity and static convergence: the magnetic characteristics of the ring do not drift during the tube's life. With the 30AX system any tube will work with any yoke (for a given tube size) without need for setting-up adjustment – the yoke is precision located by three bosses moulded into the tube's glass flare.

20AX and 30AX tubes use saddle-wound yokes with the distribution of the wires controlled by the precision mandrel on which they are wound. Fig. 13 shows the winding pattern for the 20AX tube: it's the "bunching" of the individual wires that provides the astigmatic deflection field required.

## FS Tubes

The next significant change in tube design came in 1982 with the FST glass envelope. This was pioneered by Toshiba of Japan and involved increasing the radius of the faceplate to make it flatter while squaring off the corners in order to approach the rectangular shape of the transmitted picture more closely. The reduced bracing effect of the flatter faceplate necessitated an increase of around 30 per cent in the thickness of the front glass and a corresponding increase in tube weight. Benefits of the new design include reduced reflections from the tube screen, a greater angle of legibility and less pattern distortion in the picture. The characteristics of the FS tube were described in an article in the June 1985 issue of *Television*.

## The 45AX

The latest example of an FS type tube is the Philips/Mullard 45AX design, in which the triple-gun assembly and thick neck have finally been abandoned in favour of single-gun, narrow-neck technology.

This article has briefly set the scene in outlining the main developments in colour tube technology over the years. Next month we will start to look in greater detail at the individual components that go to make up a picture tube and its deflection system. This will give greater insight into design philosophy and the continuing quest for better performance with lower power consumption.

# Servicing Teletext Decoders

## Part 5: Fault Finding

Mike Phelan

In this concluding article in the present series we'll examine methods of tackling faults that affect teletext reception. By now many readers will be well versed in servicing digital circuitry since this is becoming more and more common in consumer electronics equipment. An in-depth knowledge of this is not essential for teletext servicing however. There are two main reasons for this. First the use of LSI chips means that we cannot go down to gate-level fault-finding: most decoder faults are caused by failure of one of the LSI or memory chips. Secondly there's the advantage that since teletext is basically a display function the screen usually tells us what's happening. Thus many faults can be diagnosed without even removing the set's back cover.

It must be said at the outset that many of the faults that affect teletext reception are not caused by a decoder malfunction. Ignoring for the moment faults with the power supplies, earths etc. we should emphasise that the digital signal obtained from the vision detector must be of good quality with few errors: thus everything from the transmitter to this point must be working reasonably well.

Faults in the early stages of the set show up as text display errors, such as wrong characters or graphic blocks, possibly not on all channels and possibly very intermittent. Incorrect characters can be caused by a decoder fault but in his case the errors repeat themselves, i.e. either the fault occurs at the same screen position, the same character or group of characters are wrongly displayed or maybe rows or columns are repeated. More on this later.

Starting at the front, the aerial must provide a ghost-free signal. It's difficult laying down any hard and fast rules here: various things affect reception and the type of set is also relevant. It's true to say however that signal

strength is not the most important thing: excessive patterning due to beats with other transmissions, i.e. cross-modulation, and ghosts – especially those close to the original signal – can wreak havoc with teletext reception.

The tuner and i.f. strip must have good h.f. performance. In general this means that if we were to look at the reproduction of a perfect staircase signal, using a perfect oscilloscope, there would be slight overshoot on each step but it would be possible to tune the vision detector to obtain square corners. Every stage from the aerial socket to the vision detector has a bearing on this. To return to teletext versions of the Philips G11 chassis, which we took as our basic example of a teletext receiver, in these the i.f. panels (incorporating the tuner) were selected for teletext performance and so labelled. This doesn't mean that an i.f. strip not so labelled won't work – it probably hasn't been tested for text performance.

### G11 Teletext Conversion

We'll digress here for a moment to mention, for the benefit of anyone wishing to make up a teletext G11, that the other differences lie in the colour decoder, the text power supplies and the additional remote control circuitry. The colour decoder has the RGB interfacing panel described in Part 1 added – this can be done on a non-teletext panel by removing the links to the bases of the RGB output transistors.

### Power Supply Arrangements

In early models with ultrasonic remote control there's a separate power supply panel that lives in the bottom of

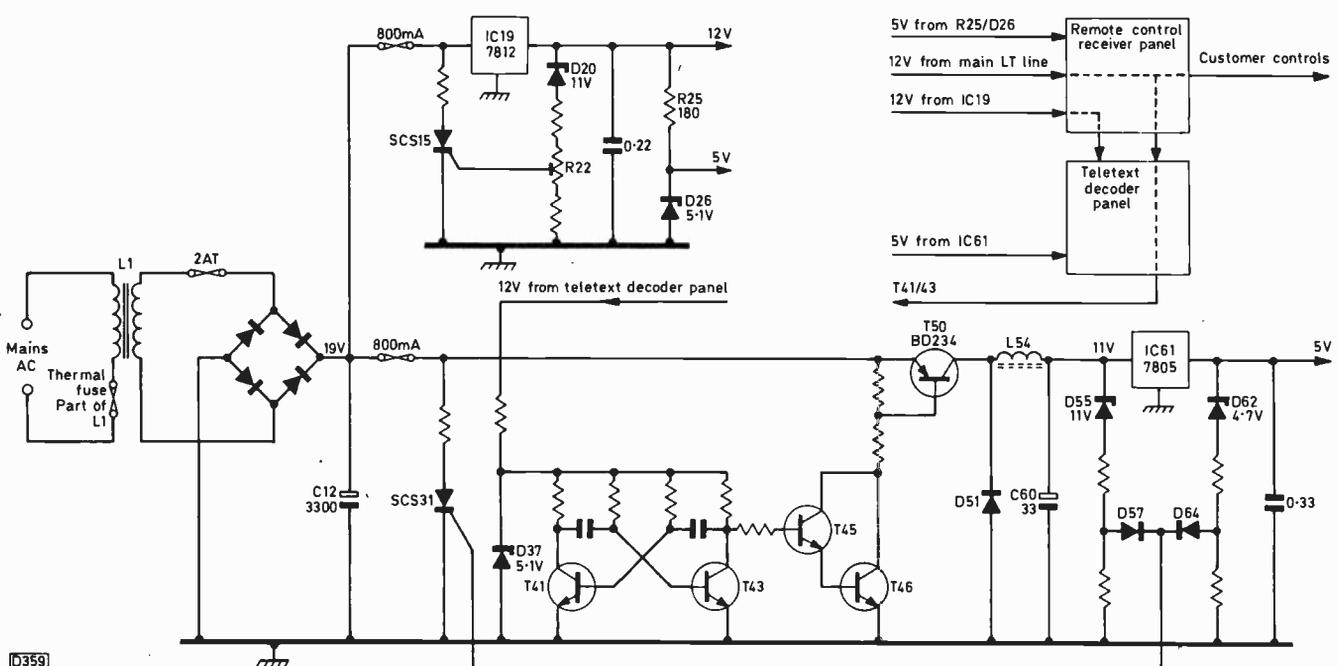


Fig. 1: The teletext decoder/remote control power supply arrangement used in early teletext versions of the Philips G11 chassis. The circuit is shown in basic outline only.

# PROTECT YOUR WORKSHOP & HOME WITH RISCAMP SECURITY MODULES



## A COMPLETE SECURITY SYSTEM FOR ONLY £39.95 + V.A.T.



contains:  
Control Unit  
Enclosure & mechanical fixings  
Key Switch & 2 keys  
LEDs  
5" Horn Speaker  
4 high quality surface mounting Magnetic Switches

CA 1250  
HW 1250  
KS 3901  
LED  
MS 588  
MS 1025

With only a few hours of your time it is possible to assemble and install an effective security system to protect your family and property at the amazingly low cost of £39.95 + V.A.T. No compromises have been made and no corners have been cut. The outstanding value results from volume production and direct supply. Assembly is straightforward with the detailed instructions provided. When installed you can enjoy the peace of mind that results from a secure home. Should you wish to increase the level of security, the system may be extended at any time with additional magnetic switches, pressure pads or ultrasonic sensors. Don't wait until it's too late - order today.

## EXTENDED SYSTEM CS 1370 Price £62.50 + V.A.T.

This system contains, in addition to the CS 1370, an ultrasonic detector type US 5063 - its enclosure, an additional horn speaker and a further 2 magnetic switches. This system represents outstanding value for money for the high level of security provided.

## SELF-CONTAINED ULTRASONIC ALARM UNIT CK 5063 only £37.00 + V.A.T.



Requires no installation. Easily assembled using our professionally built and tested modules.

- Adjustable range up to 25ft
- Built-in entrance and exit delay
- Built-in timed alarm
- Key operated switch Off/ Test and Operate
- Provision for an extension speaker
- Fully self contained
- Uses US 5063 PSL 1865 Key Switch 3901
- 3" Speaker 3515

Now you can assemble a really effective intruder alarm at this low price using tried and tested Riscamp modules. Supplied with full instructions, the kit contains everything necessary to provide an effective warning system for your house or flat. With a built-in LED indicator and test position the unit is easily set up requiring no installation. It may simply be placed on a cupboard or desk. Movement within its range will then cause the built-in siren to produce a penetrating 90db of sound or even 110db with an additional speaker. All parts included and supplied with full instructions for ease of assembly. Size 200 x 180 x 70mm. Order as CK 5063.

## ALARM CONTROL UNIT CA 1250



Price £19.95 + V.A.T.

The heart of any alarm system is the control unit. The CA 1250 offers every possible feature that is likely to be required when constructing a system whether a highly sophisticated installation or simply controlling a single magnetic switch on the front door.

- Built-in electronic siren drives 2 loud speakers
- Provides exit and entrance delays together with fixed alarm time
- Battery back-up with trickle charge facility
- Operates with magnetic switches, pressure pads, ultrasonic or IR units
- Anti tamper and panic facility
- Stabilised output voltage
- 2 operating modes full alarm anti tamper and panic facility
- Screw connections for ease of installation
- Separate relay contacts for external loads
- Test loop facility

## HARDWARE KIT HW 1250



only £9.50 + V.A.T.

This attractive case is designed to house the control unit CA 1250 together with the appropriate LED indicators and key switch. Supplied with the necessary mounting pillars and punched front panel, the unit is given a professional appearance by an adhesive silk screened label. Size 200 x 180 x 70mm.

## SIREN & POWER SUPPLY MODULE PSL 1865



only £9.95 + V.A.T.

A complete siren and power supply module which is capable of providing sound levels of 110db at 2 metres when used with a horn speaker. In addition the unit provides a stabilised 12V output up to 100mA. A switching relay is also included so that the unit may be used in conjunction with the US 5063 to form a complete alarm.



## TIMER SWITCH & POWER SUPPLY MODULE DP 3570 Price £13.95 + V.A.T.

The DP 3570 consists of an adjustable timer switch and stabilised 12V power supply for use in a wide range of applications including security lighting control and automatic switching. The timer section of the module provides switching of loads up to 3A for pre-set times, the duration of which may be set by the user to between 10 secs and 5 mins. The timed period may be triggered by the opening of a loop or the closing of external contacts with the timed period commencing instantaneously or delayed to provide a form of entrance delay. The power supply section of the module provides a 12V output of up to 250mA which is sufficient for most applications. The module operates from either 240V a.c. supply or a 12V battery for which trickle charge facilities are included. Connections to the module are by means of screw terminal connectors with no soldering needed.

For mounting the unit an attractive moulded enclosure is available.

ME 357 only £2.85 + V.A.T.

## INFRA-RED SYSTEM IR 1470 only £25.61 + V.A.T.

Consisting of separate transmitter and receiver both of which are housed in attractive moulded cases, the system provides an invisible modulated beam over distances of up to 50ft operating a relay when the beam is broken. Intended for use in security systems but also ideal for photographic and measurement applications. Size 80 x 50 x 35mm.

## DIGITAL ULTRASONIC DETECTOR US 5063



only £13.95 + V.A.T.

This advanced module uses digital signal processing to provide the highest level of sensitivity whilst discriminating against potential false alarm conditions.

## ULTRASONIC MODULE ENCLOSURE



only £2.95 + V.A.T.

Suitable metal enclosure for housing an individual ultrasonic module type US 5063 or US 4012. Supplied with the necessary mounting pillars and screws etc. For US 5063 order SC 5063 for US 4012 order SC 4012.

# RISCAMP THE SECURITY SPECIALISTS!

**FULL RANGE OF ACCESSORIES STOCKED SEND SAE FOR DETAILS**

**RISCAMP LIMITED**

Dept. TV6  
51 Poppy Road,  
Princes Risborough,  
Bucks. HP17 9DB  
Princes Risborough (084 44) 6326

Add 15% to all prices  
Units 75p post and packing to all orders Saturday 9.00 to 1.00 p.m.  
Units on demonstration Order by telephone or post  
Shop hours 9.00 to 5.30 p.m. using your credit card  
Closed Wednesdays  
Please allow 7 days for delivery

the cabinet - a simplified circuit is shown in Fig. 1. The mains transformer feeds a bridge rectifier which produces 19V across C12. IC19 provides a regulated 12V supply from the 19V supply: this voltage is used to power the remote control receiver and is also passed to the VIP chip in the decoder. R25 drops this supply to 5V for the M911 remote control decoder chip. The 19V supply is also fed to the emitter of the chopper transistor T50. This is part of a series chopper circuit with L54 the reservoir inductor and D51 the "efficiency diode". The 11V output developed by the chopper is applied to the 5V regulator IC61 whose output powers the rest of the teletext decoder. At least it does once the line timebase has started up. The delay is necessary to allow C12 to become fully charged before the chopper starts. Note that the supply for the 18kHz astable multivibrator T41/43 comes from the set's main 12V line, which is derived from the line output transformer. So T50 is without drive until the line output stage is operative. There's elaborate over-voltage protection - teletext decoders were worth a fortune at that time!

Later models with infra-red remote control have a simpler arrangement - the decoder's 5V supply is derived from an extra winding on the line output transformer, making the line output panels non-compatible. The pulses from the line output transformer are fed to a small panel at the bottom of the cabinet. This panel contains a large diode, a 5V regulator and a few other bits. The teletext decoder's 12V supply comes from the set's main 12V line via the remote control receiver.

Servicing either of these power supplies should pose no problems, but we'll mention the effect of either teletext decoder supply being absent: no 5V rail produces a bright blank raster, no 12V supply gives absence of text only.

Needless to say any voltage change or defective decoupling can cause some very strange faults indeed! The moral is to check both lines, preferably with a scope, when presented with an inexplicable fault symptom.

### Misadjusted Clock Coil

An odd effect occurs when the 6.93MHz clock coil is incorrectly adjusted: the errors increase towards the right-hand side of the screen. This shows up clearly when the clockcracker page is selected. Don't forget that adjustment will have no visible effect until the page is reselected. Leave any adjustments on the decoder alone unless absolutely necessary.

### Memory Faults

Most of the faults on the G11's teletext decoder panel are due to the 2102 memory chips. If wrong characters are persistently displayed at a particular row/column position one of the memory cells is stuck at one or zero. Many characters wrong but always the same errors means that one of the data bits is stuck. This may occur during read or write but this makes no practical difference. If row or column address pins are shorted to either rail groups of text will be repeated.

A "hard" RAM failure means the device is permanently damaged. This sort of thing usually occurs during the initial test period - the so-called burn-in. There are on the other hand "soft" failures that recover or occur only once. Soft failures can be caused by mains noise, static, c.r.t. flashovers or cosmic particles. No, we're not entering the realms of science fiction: it's a fact that our seven

**Table 1: ASCII code for the SAA5050.**

Dec.	Binary	Means	Dec.	Binary	Means	Dec.	Binary	Means	Dec.	Binary	Means
0	0000000		32	0100000	Space	64	1000000	@	96	1100000	—
1	0000001	Red*	33	0100001	!	65	1000001	A	97	1100001	a
2	0000010	Green*	34	0100010	"	66	1000010	B	98	1100010	b
3	0000011	Yellow*	35	0100011	£	67	1000011	C	99	1100011	c
4	0000100	Blue*	36	0100100	\$	68	1000100	D	100	1100100	d
5	0000101	Magenta*	37	0100101	%	69	1000101	E	101	1100101	e
6	0000110	Cyan*	38	0100110	&	70	1000110	F	102	1100110	f
7	0000111	White*	39	0100111	'	71	1000111	G	103	1100111	g
8	0001000	Flash	40	0101000	(	72	1001000	H	104	1101000	h
9	0001001	Steady	41	0101001	)	73	1001001	I	105	1101001	i
10	0001010	End box	42	0101010	*	74	1001010	J	106	1101010	j
11	0001011	Start box	43	0101011	+	75	1001011	K	107	1101011	k
12	0001100	Normal height	44	0101100	,	76	1001100	L	108	1101100	l
13	0001101	Double height	45	0101101	-	77	1001101	M	109	1101101	m
14	0001110		46	0101110	.	78	1001110	N	110	1101110	n
15	0001111		47	0101111	/	79	1001111	O	111	1101111	o
16	0010000		48	0110000	0	80	1010000	P	112	1110000	p
17	0010001	Red†	49	0110001	1	81	1010001	Q	113	1110001	q
18	0010010	Green†	50	0110010	2	82	1010010	R	114	1110010	r
19	0010011	Yellow†	51	0110011	3	83	1010011	S	115	1110011	s
20	0010100	Blue†	52	0110100	4	84	1010100	T	116	1110100	t
21	0010101	Magenta†	53	0110101	5	85	1010101	U	117	1110101	u
22	0010110	Cyan†	54	0110110	6	86	1010110	V	118	1110110	v
23	0010111	White†	55	0110111	7	87	1010111	W	119	1110111	w
24	0011000	Conceal	56	0111000	8	88	1011000	X	120	1111000	x
25	0011001	Norm. graphics	57	0111001	9	89	1011001	Y	121	1111001	y
26	0011010	Sep. graphics	58	0111010	:	90	1011010	Z	122	1111010	z
27	0011011		59	0111011	;	91	1011011	←	123	1111011	¼
28	0011100	Black backg'd	60	0111100	<	92	1011100	½	124	1111100	
29	0011101	New backg'd	61	0111101	=	93	1011101	→	125	1111101	¾
30	0011110	Hold graphics	62	0111110	>	94	1011110	↑	126	1111110	÷
31	0011111	Release graphics	63	0111111	?	95	1011111	#	127	1111111	■

\* Alphanumerals. † Graphics.

Notes: Graphics see Fig. 2. ASCII = American Standard Code for Information Interchange.

2102s, innocently sitting there, are occasionally hit by charged particles from space or from other sources – even i.c.s emit them! The result can simply be that one of the cells is flipped over without damage. More often however one of the gate layers is punctured: this is not always permanent.

Equipment for fault-finding can consist of just a meter (or logic probe) and, most importantly, an ASCII table (see Table 1 and Fig. 2). It's important to know which memory chip deals with which bit. We refer to the bits of a byte by number, starting with the left-most bit which is also referred to as the most significant bit (MSB) as it represents 64. This is bit number one. The least significant bit (LSB), the right-most one, is equal to one. This is bit seven (our character set is a seven-bit one so we don't use a full-sized byte, i.e. one with eight bits). The RAM chips in this decoder are numbered IC6671-IC6677: IC6671 is

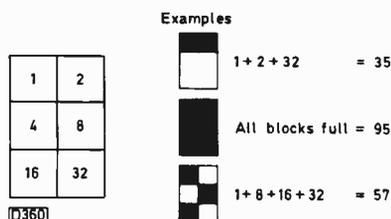


Fig. 2: Graphics characters are from 33 to 127 (ASCII code) and are built of six blocks. To ascertain the ASCII value of a graphic, add together the blocks and add 32 to the total. These are displayed if preceded by attribute 30 (hold graphics).

for bit seven, IC6672 for bit six, etc.

In the event of wrong characters note at least two wrong characters and decide what they should have been. Then see what the difference is in the binary ASCII code. You should find that only one bit differs between the correct and incorrect versions, and that this applies to all the wrongly displayed characters. Note that some characters will be correct despite the presence of the fault: these correspond to the ones in which the stuck cell or data line is stuck at the correct level. For example, bit seven stuck at one means that the even numbered codes can't be displayed. The displayed alphabet will consist of AACCEE etc. At the other end, bit one stuck at zero will make it impossible to count above 63, so that codes from 64 to 127 will be displayed as zero to 63. This means that the alphabet cannot appear. All you'll get is numerics, attributes and some punctuation marks. Clearly the possibilities are legion. For example, bit two stuck causes all letters to be in upper or lower case: bit two stuck at zero makes an attribute of anything with bit one low – this gives a very strange display, with psychedelic colours everywhere – whereas if bit two is stuck high the display is in monochrome with everything in lower case and no graphics.

The way in which the errors are displayed depends on whether a memory cell or data line is stuck. If a memory cell is stuck, one location only will show errors. A stuck data line will affect the whole screen. Returning to our earlier example of bit seven stuck high, if say row six column two shows D when it should show C one memory cell is defective and will produce display errors only when

it should contain an even code. If the bit seven data line is high however no even codes will be displayed anywhere on the screen.

When row or column address lines are stuck the effect is that groups of rows or columns are repeated depending on which bit is stuck or missing. The addresses can count only in steps of 2, 4, 8, 16 or 32, remembering the bit of wizardry carried out in this decoder to make the RAMs compatible with the screen format. Problems here are usually due to faults in either one of the three 74LS chips in the row/column address decoder or because one of the five little white chokes in the column address lines is open-circuit. A logic probe with a pulse indication is useful here. The chokes can safely be shorted out.

There are many other fault possibilities. When two pins of one of the 2102 memory chips short together internally there will be all sorts of weird effects, the usual one being an almost blank screen with just one character repeatedly displayed at random. Check by removing each RAM i.c. in turn, followed by reselecting a page: when the faulty i.c. has been removed the display will return to the one byte missing condition, as when a data line is stuck low.

So this part of the decoder is not too bad after all – a little thought and detective work will sort out any problems.

### LSI Chip Faults

The various LSI chips can fail. The VIP and TIC chips usually give a blank screen with no text and the TAC chip inability to select text or pages. An interesting variation occurs when an SAA5040 is fitted instead of an SAA5040A. The only difference is that the status displays

## SATELLITE RECEIVING SYSTEMS

1m and 2m Parabolic Dishes, other sizes available.

A range of other components available, eg, LNAs, Downconverters, receivers, for both 4 and 11 GHz. Complete Terminals for ECS and Intelsat, both single channel and tunable versions.

Terminals for other frequencies available.

Demonstration by appointment.

**L & S Bear Electronics Ltd**

Yeo Lane, Colley Lane,

Bridgwater, Somerset.

Telephone: Bridgwater (0278) 421719

for channels two and three (BBC-2/ITV) are transposed – the converse is also true of course.

The TROM chip is first in the firing line in the event of any c.r.t. flashovers, so the output pins are prone to getting stuck. The funny one is when pin 16 (TLC – transmitted large characters) which is connected to the TIC chip gets stuck, either due to a duff TIC or TROM chip: the RACK stops and the header row is repeated all down the screen. Remember that the outputs can be high, low or open-circuit. No luminance output affects only the mix mode: the result is not too obvious – the picture can be seen through the text. No blanking output (pin 25) gives mix mode instead of text; if this pin is stuck high there's text only, with no picture; if stuck low the text in the mix mode is faint. The results of the RGB outputs packing up should be fairly obvious.

**SPEND AT LEAST £1000 IN TOTAL ON**

- \* VCR's — £55 each (minimum quantity 20)
- \* Portable CTV's — £45 each
- \* TX9 TX10 — £35 each
- \* 9600 — £25 each

**& you get from us**

**YES FREE**

**£1000 Cheque**

to spend on Hotel Accommodation for business or holidays at selected hotels – you pay only for breakfast and dinner.  
OPEN 6 DAYS WEEKLY AND SUNDAY BY APPOINTMENT AT



## Kent Ledgerwood Wholesale Ltd.

**BRADFORD TRITEL TV**  
1043 Leeds Road  
Thornbury Roundabout  
BRADFORD  
Tel: 0274 665670

**LEEDS TRITEL DISCOUNT STORES**  
Long Row  
Horsforth  
LEEDS

Tel: 0532 590252

**SCOTLAND TRITEL TV**  
Unit 4  
Peacock Cross

Industrial Estate  
Burnbank Road  
HAMILTON

Tel: 0698 282141

**Now Open in London at:-**

**UNIT 1E, WATERLOO ROAD, STAPLES CORNER, LONDON NW2**



Tel: 01 208 2063

# ECONOMIC DEVICES, PO BOX 228, TELFORD TF2 8PQ

1580H	3.30	2SA940	1.81	2SC535	0.79	AF180	0.55	BA656	0.99	BC560C	0.14	BDC63A	1.96	BFY52	0.27	BYQ1-350	0.72
1585R	3.30	2SA940-2	2.14	2SC536	0.29	AF181	0.53	BA7100	16.05	BC635	0.36	BDY20	1.21	BFY79	0.49	BY94	1.14
16039	0.79	2SA950	0.72	2SC537	0.54	AF186	0.53	BA841A	10.82	BC636	0.42	BDY81	1.18	BFY90	0.61	BY956	1.20
16181	1.04	2SA951	1.26	2SC605L	1.16	AF239	0.43	BA843	3.96	BC637	0.24	BF115	0.40	BLY49	0.22	BZ933C	1.86
16182	1.04	2SA966-Y	1.16	2SC620	1.46	AF279	0.88	BA854	5.76	BC639	0.20	BF117	0.66	BR60	0.20	BZ98 RANGE	0.18
16334	0.98	2SA999	1.36	2SC643A	1.57	AN113	1.36	BAV18	0.21	BC640	0.24	BF118	0.40	BR01	0.75	BZ961 RANGE	0.18
16335	0.94	2SB774	1.15	2SC668	0.64	AN115	3.98	BAV19	0.11	BC879	0.39	BF121	0.67	BR03	0.75	BZ975 RANGE	0.10
16446	0.98	2SB185	1.13	2SC681	1.40	AN155	1.89	BAV20	0.31	BC880	0.31	BF123	0.13	BR03	1.26	CI06D	0.46
16600	1.38	2SB375	3.87	2SC682	1.88	AN206	2.58	BAV21	0.34	BCX34	0.40	BF127	0.13	BR03	1.26	CI06M	0.76
16802	1.27	2SB400	0.40	2SC684	1.85	AN208	3.55	BAW62	0.19	BCY70	0.30	BF137	0.29	BR03	2.01	CI129	2.58
17052	5.61	2SB405	1.83	2SC693	0.63	AN210	2.28	BAX12	0.44	BCY71	0.21	BF153	0.58	BR03	0.77	CA3046	0.83
17053	5.61	2SB407	3.24	2SC710	0.69	AN211	3.25	BAX13	0.11	BCY72	0.20	BF154	0.26	BR03	0.77	CA309A	3.25
17074	9.30	2SB449B	6.93	2SC711A	0.50	AN214Q	2.75	BAX16	0.11	BD115	0.46	BF157	0.33	BR03	1.08	CA309AQ	2.20
17089	5.35	2SB511	2.50	2SC717	1.28	AN231	14.65	BC107	0.13	BD116	0.70	BF158	0.18	BR03	2.19	CA3131EM	3.12
17127	3.51	2SB54	1.39	2SC734	1.43	AN234	5.92	BC107A	0.13	BD124	1.31	BF159	0.18	BR03	2.08	CBF16848N-071	1.56
17376	1.58	2SB546	3.75	2SC783	3.95	AN236	3.78	BC107B	0.18	BD124P+KIT	0.69	BF160	0.39	BR03	0.53	CD4001	0.27
17523	1.32	2SB56	2.80	2SC783	3.95	AN239	5.88	BC108	0.15	BD131	0.42	BF167	0.39	BR03	0.53	CD4002	0.38
17524	1.32	2SB618A	2.22	2SC790Y	1.64	AN240P	1.52	BC108B	0.15	BD132	0.53	BF177	0.35	BR03	0.53	CD4008	1.35
1N4001	0.06	2SB631	3.25	2SC828	0.28	AN241	1.71	BC109	0.12	BD133	0.53	BF177	0.35	BR03	0.53	CD4011	0.29
1N4002	0.06	2SB643	0.54	2SC867A	3.05	AN245	4.49	BC108B	0.15	BD135	0.53	BF178	0.40	BR03	0.53	CD4012	0.24
1N4003	0.06	2SB669	3.67	2SC876	0.96	AN253	2.97	BC109C	0.12	BD136	0.26	BF179	0.36	BR03	0.53	CD4013	0.47
1N4004	0.06	2SB681	3.96	2SC930	0.54	AN260	3.85	BC113	0.14	BD137	0.36	BF180	0.32	BR03	0.53	CD4016	0.46
1N4005	0.08	2SB695	1.98	2SC935	0.13	AN262	1.98	BC119	0.36	BD138	0.46	BF181	0.32	BR03	0.53	CD4017	0.82
1N4006	0.08	2SB75	1.04	2SC936	0.66	AN272	7.92	BC126	0.20	BD139	0.34	BF182	0.39	BR03	0.53	CD4020	1.23
1N4007	0.07	2SB774	0.65	2SC940	4.86	AN281	6.65	BC132	0.14	BD140	0.37	BF183	0.39	BR03	0.53	CD4021	0.39
1N4148	0.04	2SB819	0.89	2SD1128	2.90	AN295	5.52	BC135	0.18	BD144	1.70	BF184	0.43	BR03	0.53	CD4022	0.64
1N4448	0.05	2SC1034	6.75	2SD1138	0.90	AN301	5.55	BC137	0.18	BD150	1.25	BF185	0.39	BR03	0.53	CD4023	0.28
1N5401	0.14	2SC1050	5.06	2SD1273	1.25	AN302	3.99	BC138	0.34	BD157	0.67	BF194	0.14	BR03	0.53	CD4025	0.64
1N5402	0.14	2SC1096	1.16	2SD1453	0.75	AN303	4.39	BC139	0.28	BD160	1.60	BF195	0.14	BR03	0.53	CD4028	0.84
1N5403	0.16	2SC1104	3.98	2SD152K	2.64	AN305	9.47	BC140	0.45	BD163	0.71	BF196	0.17	BR03	0.53	CD4040B	0.05
1N5404	0.16	2SC1106	4.54	2SD198	3.87	AN315	2.46	BC141	0.34	BD165	0.62	BF197	0.16	BR03	0.53	CD4047	1.06
1N5408	0.35	2SC1114	6.75	2SD234	0.49	AN316	5.53	BC142	0.34	BD166	0.62	BF198	0.17	BR03	0.53	CD4049	0.46
1N914	0.04	2SC1116	4.95	2SD235	0.80	AN318	6.27	BC143	0.33	BD168	0.73	BF199	0.17	BR03	0.53	CD4052	0.78
IR3403	5.00	2SC1124	1.26	2SD24	2.29	AN320	5.47	BC147	0.08	BD175	0.60	BF200	0.37	BR03	0.53	CD4056	0.35
IS1555	0.20	2SC1129	0.34	2SD257	2.59	AN321	2.25	BC148A	0.10	BD179	0.49	BF218	0.36	BR03	0.53	CD4069	0.29
IS44	0.10	2SC1131	0.30	2SD292	2.54	AN322	5.85	BC148B	0.13	BD181	0.99	BF224	0.17	BR03	0.53	CD4070	0.66
IS5012A	0.81	2SC1158	3.53	2SD315	2.59	AN331	4.59	BC148C	0.11	BD182	0.99	BF237	0.65	BR03	0.53	CD4081	0.76
IS921	0.10	2SC1162	1.05	2SD325D	1.95	AN337	5.37	BC149	0.11	BD183	0.99	BF249	0.17	BR03	0.53	CD4093	0.32
2N1303	0.38	2SC1172	2.22	2SD348	16.13	AN340P	1.17	BC149B	0.13	BD184	1.21	BF241	0.17	BR03	0.53	CD4511	1.14
2N2219A	0.40	2SC1195	3.26	2SD350	5.20	AN355	5.98	BC153	0.14	BD187	0.53	BF245	0.49	BR03	0.53	CD4528	2.00
2N2222	0.38	2SC1212A	1.97	2SD350A	7.80	AN362	1.75	BC154	0.14	BD189	0.69	BF245A	0.37	BR03	0.53	CD4556	3.47
2N2646	0.80	2SC1213	0.89	2SD353	2.50	AN370	3.95	BC159	0.36	BD190	0.69	BF245B	0.49	BR03	0.53	CR02AM-8	1.55
2N2904	0.36	2SC1226	1.46	2SD389	2.41	AN5010	5.70	BC160	0.40	BD201	0.53	BF246A	2.52	BR03	0.53	CV12E	3.07
2N2905	0.43	2SC1293	0.90	2SD401	2.55	AN5111	2.92	BC161	0.28	BD202	0.60	BF255	0.20	BR03	0.53	CO995D	3.14
2N2906	0.38	2SC1306	1.98	2SD414	1.98	AN5120N	4.50	BC168	0.36	BD203	0.50	BF256	0.28	BR03	0.53	CK104	9.64
2N2926	0.15	2SC1316	4.10	2SD471	2.13	AN5132	4.39	BC169C	0.16	BD204	0.59	BF256LB	0.42	BR03	0.53	CK108	10.50
2N3053	0.27	2SC1317	0.87	2SD560	2.95	AN5250	2.89	BC170	0.16	BD207	1.79	BF256LC	0.42	BR03	0.53	CK109	7.86
2N3054	0.99	2SC1364	0.49	2SD588A	1.99	AN5435	3.08	BC171	0.11	BD208	1.23	BF257	0.34	BR03	0.53	CK130	8.76
2N3055	0.61	2SC1383	1.20	2SD600	3.25	AN5610	7.43	BC172	0.13	BD222	0.49	BF258	0.36	BR03	0.53	CK134	11.49
2N3442	1.16	2SC1391	2.45	2SD601R	0.85	AN5612	3.81	BC172B	0.27	BD225	0.49	BF259	0.34	BR03	0.53	CK136	11.04
2N3702	0.14	2SC1398	0.84	2SD613	1.03	AN5613	3.80	BC173	0.17	BD228	0.63	BF262	0.57	BR03	0.53	CK139	11.83
2N3703	0.14	2SC1413A	3.05	2SD621	12.67	AN5630	3.95	BC174B	0.27	BD229	1.05	BF263	0.57	BR03	0.53	CK157	4.94
2N3705	0.16	2SC1446	1.25	2SD636	0.56	AN5701N	1.66	BC177	0.20	BD232	0.50	BF271	0.34	BR03	0.53	CK158	4.10
2N3706	0.14	2SC1447	2.07	2SD639-R	0.85	AN6250	2.95	BC178	0.26	BD234	0.42	BF273	0.20	BR03	0.53	CK177	6.75
2N3707	0.16	2SC1475	0.37	2SD655	0.96	AN6300	7.00	BC179	0.26	BD237	0.47	BF274	0.20	BR03	0.53	CK187	5.26
2N3711	0.11	2SC1505	1.00	2SD657	2.85	AN6310	8.74	BC182	0.09	BD238	0.47	BF324	0.23	BR03	0.53	CK188	12.95
2N3771	2.04	2SC1514	1.37	2SD661A	4.28	AN6320N	4.28	BC182L	0.10	BD239	0.45	BF336	0.33	BR03	0.53	CKX885	6.85
2N3772	1.71	2SC1579D	1.25	2SD731	2.46	AN6340	6.46	BC182LB	0.14	BD240	0.37	BF337	0.40	BR03	0.53	DEC1	2.20
2N3773	2.29	2SC1578	8.74	2SD773	0.33	AN6341	4.00	BC183L	0.11	BD241	0.38	BF338	0.40	BR03	0.53	DEC2	2.20
2N3819	0.42	2SC1583	1.17	2SD811	5.54	AN6342	1.61	BC183LB	0.26	BD242	0.39	BF355	0.49	BR03	0.53	DS3486N	4.33
2N3823	1.17	2SC1617	3.89	2SD823	1.98	AN6363	16.00	BC184	0.14	BD243A	0.37	BF362	0.66	BR03	0.53	DS3487N	4.33
2N3904	0.62	2SC675	1.41	2SD837	1.20	AN6371	6.50	BC184L	0.13	BD243C	0.79	BF363	0.60	BR03	0.53	E1222	2.20
2N3908	0.62	2SC1678	1.98	2SD841	3.85	AN6387	7.95	BC184LB	0.26	BD244	0.51	BF371	0.50	BR03	0.53	E5024	0.28
2N4101	1.33	2SC1741	1.25	2SD856	2.26	AN6531	1.95	BC186	0.27	BD244C	0.79	BF391	0.25	BR03	0.53	E5386	0.25
2N4240	3.30	2SC1810	1.70	2SD857Q	1.84	AN6551	1.35	BC187	0.28	BD245C	0.99	BF417	0.84	BR03	0.53	E9003	0.46
2N4444	0.90	2SC1815	0.66	2SD882	1.50	AN6552	0.68	BC204	0.16	BD246C	0.99	BF418	1.87	BR03	0.53	ENM3108P	5.15
2N5293	0.50	2SC1826	0.85	2SD894	1.50	AN6610	2.40	BC207	0.14	BD253	1.05	BF422	0.29	BR03	0.53	FSD500	4.78
2N5294	0.50	2SC1829	2.22	2SD898	5.45	AN6677	6.60	BC212	0.11	BD278A	2.80	BF423	0.52	BR03	0.53	GC374	1.65
2N5296	0.49	2SC1875	2.95	2SK105H	2.15	AN7111	1.45	BC212B	0.26	BD317	2.60	BF450	0.35	BR03	0.53	GD243	4.95
2N5297	0.50	2SC1881K	2.98	2SK152	2.95	AN7114E	5.94	BC213L	0.10	BD318	2.85	BF451	0.29	BR03	0.53	GF58	0.84
2N5298	0.16	2SC1883	3.02	2SK34	0.76	AN7115	1.75	BC213LB	0.15	BD375	0.42	BF457	0.41	BR03	0.53	GH3F	1.82
2N5771	1.81	2SC1906	0.98</														

# TEL 0902 712083      TELEX 338490

HA1374	4.80	LR3419	9.37	NE565N	1.33	SKE4F208	1.24	STK3042	11.05	TA7312P	2.45	TD62105P	2.50	TD43560	5.00	TJA2000	6.98
HA1377	3.96	LR3471	9.37	NE645BN	3.35	SKE4F206	0.85	STK3044	5.70	TA7313AP	1.50	TD62104P	2.50	TD43571Q	2.83	TV106	1.76
HA1389R	2.05	LU1141	7.27	NF1106	5.61	SKE4F210	1.24	STK4019	4.50	TA7314	5.94	TD62706P	4.50	TD43576	7.09	TV6010B	2.97
HA1392	2.39	LU52012	5.25	OA202	0.11	SKE4G202	0.96	STK430	11.75	TA7323P	3.02	TD41001B	2.31	TD43580	5.79	U05G	1.14
HA1394	3.90	LU52011	4.95	OA47	0.14	SKE5F310	1.60	STK433	5.45	TA7325P	1.15	TD41003A	2.25	TD43581	6.45	ULN2204	11.45
HA1397	3.76	M193	12.75	OA95	0.09	SKS110	2.15	STK4332	8.25	TA7339P	1.35	TD41005A	2.22	TD43585	7.50	UPA53C	4.94
HA1398	3.96	M21C	1.00	OC28	2.95	SL1310	0.09	STK436	5.94	TA7340P	5.06	TD41005A	2.11	TD43582	5.46	UPA500	4.95
HA1406	2.07	M23C	0.83	OC29	2.15	SL1414	3.89	STK436	12.25	TA7607AP	13.90	TD41010AF	4.25	TD43581AQ	2.96	UPC1009C	6.32
HA1452	1.63	M293	0.15	OC36	1.29	SL432A	3.44	STK437	7.00	TA7609	3.28	TD41011	2.40	TD43581	3.30	UPC1025H	2.90
HBF4030AF	2.48	M293	0.15	OC44	0.35	SL439	2.48	STK4372	3.85	TA7611AP	4.00	TD41010	1.15	TD43581A	2.65	UPC1026C	1.24
HD14538	2.07	M51102L	6.35	OC45	0.18	SL471	3.28	STK439	8.31	TA7622AP	8.94	TD41011A	5.25	TD43590	3.95	UPC1028H	2.00
HD38702-A2	7.45	M5115P	5.24	OC72	0.44	SL480	3.14	STK441	11.25	TA7628P	5.62	TD41028	2.45	TD44050B	3.95	UPC1020H	0.77
HD38750A53	8.71	M51203L	3.15	OC75	0.44	SL490	3.14	STK443	10.29	TA7629P	7.50	TD41034B	2.42	TD44280	7.20	UPC1032H	2.62
HD38750A-7	7.25	M51231P	3.04	ONZ36	1.06	SL901B	8.32	STK457	13.45	TA7630P	2.98	TD41035S	2.95	TD44290	4.47	UPC1042C	8.95
HD38800A50	14.09	M5134-9341	4.13	ON782	1.98	SL918A	9.07	STK460	14.83	TA7640AP	1.19	TD41037	1.98	TD44420	5.01	UPC1156H	5.84
HD44801A05	17.49	M51353P	5.25	PT021	1.45	SN16861A0N	4.95	STK461	9.08	TA7672P	1.75	TD41037D	3.25	TD44422	8.32	UPC1161C	4.50
HEF4001BP	0.67	M51381P	4.50	PT6042	2.98	SN16862AN	2.98	STK463	11.53	TA7676P	2.81	TD41044	2.62	TD44427S	2.00	UPC11278H	1.82
HISH1010	8.59	M51393AP	7.78	PT8504	4.98	SN16866AN	10.25	STK466	11.77	TA7726P	10.25	TD41047	4.10	TD44440	2.87	UPC1186H	1.05
HISH1004	6.00	M51394P	11.97	R1038	2.19	SN29717N	7.19	STK4833	16.95	TAA320A	1.27	TD41059B	0.80	TD44440	2.87	UPC1181H	1.25
HISH1002	9.50	M5142P	5.45	R1039	2.19	SN29716N	3.06	STK501	6.32	TAA350A	0.80	TD41054M	1.21	TD44442	4.85	UPC1185H	2.54
HM6231	9.01	M5144P	4.29	R2008B	1.33	SN29715N	6.04	STK502	5.74	TAA570	1.74	TD41060	2.60	TD44450	7.30	UPC1188H	6.95
HM6232	8.89	M51513L	2.56	R2009	1.98	SN29722	11.95	STK5314	9.48	TAA621AX1	2.48	TD41082	3.25	TD44600	2.84	UPC1213C	0.99
HM6251	5.70	M51515BL	3.23	R2010B	1.33	SN29723AN	7.85	STK5730	3.95	TAA621A12	2.14	TD41151	1.22	TD44610	2.80	UPC1212C	1.72
HM7103	2.46	M51517L	2.71	R2029	1.33	SN29764AN	1.38	STK7216	12.67	TAA661B	1.00	TD41170S	2.25	TD44620	4.46	UPC1225H	3.25
HM9032	3.22	M5192	3.20	R2030	1.93	SN29767	4.98	STK772	6.95	TAA691	8.58	TD41190	2.11	TD44550	4.78	UPC1230	7.24
HM9012	3.22	M51944P	5.74	R2257	2.38	SN29770BN	4.24	STR1096	11.50	TAA700	3.75	TD41190Z	3.96	TD44570	2.60	UPC1238	2.98
HM9015	3.24	M5231L	1.95	R2265	1.49	SN29772BN	4.91	STR4090	4.75	TAA930	4.07	TD41200	1.50	TD44720S	2.25	UPC1263	3.46
HT4207	17.16	M53274P	1.33	R2305	1.18	SN29771BN	4.93	STR440	9.05	TAA970	2.83	TD41235	3.88	TD448190	3.47	UPC1277H	5.85
HT4208	18.25	M54532P	2.15	R2322	0.59	SN29791	1.67	STR441	7.45	TAA110	2.52	TD41236	4.30	TD449403	3.15	UPC1278H	4.05
IN5401	0.11	M54544L	4.75	R2323	0.76	SN29798N	5.56	STR451	4.15	TAG232-600	0.73	TD41270	3.76	TD449503	2.52	UPC1351C	1.80
IR2403	0.25	M58478P	6.75	R2354A	2.01	SN2709	0.44	STR453	8.96	TAG626-600	1.06	TD41327A	1.33	TD449513	2.44	UPC1350C	1.40
IR2C05	4.25	M58485P	10.74	R2354B	2.01	SN7400N	0.34	STR454	7.50	TBA120AS	1.24	TD41412	1.05	TD41033	2.08	UPC1353	7.83
IR3P06	2.25	MA06	1.07	R2443	0.88	SN7401N	0.36	STR6020	8.31	TBA120SB	1.05	TD41420	1.55	TD41081	6.01	UPC1355C	2.15
IR3P08	4.95	MA8001	0.82	R2461	1.50	SN7402N	0.65	T6029V	5.75	TBA120T	0.95	TD41440	3.45	TE626	1.49	UPC1363	4.20
IR94568	6.25	MA8003	1.16	R2540	2.31	SN7404AN	0.24	T6035V	0.73	TBA120U	2.50	TD41470	3.16	TEA1002	3.47	UPC1362	7.75
IS751	2.05	MB3705	1.98	R2540X	3.30	SN7408N	0.27	T6036	0.67	TBA120A	1.05	TD41470P	4.25	TEA1009	1.86	UPC1365C	6.98
ITT425	0.18	MB3712	1.05	R2615	0.67	SN7410N	0.27	T6037	2.11	TBA120B	2.03	TD41506	7.45	TEA1014	3.15	UPC1366	7.14
ZD0030GE	5.37	MC3713	1.69	RCA16029	2.01	SN74121	1.80	T6044V	0.95	TBA1441	1.62	TD41510	5.90	TEA1020SP	8.21	UPC1360C	4.51
ZD0020GE	5.93	MC3730	3.25	RCA16600	1.38	SN7413N	0.37	T6045	1.20	TBA1440G	1.20	TD41512	2.89	TIC106C	0.61	UPC1378H	4.25
K1241P	3.46	MC13002	2.55	RCA16802	1.00	SN74141N	2.85	T6049	1.45	TBA1441	1.75	TD41515	16.60	TIC106M	0.77	UPC141C	3.75
KA7Y09	2.92	MC13109	3.25	RCA17074	6.60	SN74151AN	1.51	T6052V	0.67	TBA240A	3.99	TD41559	3.15	TIC116Y100	2.07	UPC1458	8.66
KC581C	6.32	MC1327P	1.33	RCA17376	1.58	SN74154AN	1.27	T6058	0.59	TBA395	1.10	TD41670	4.88	TIC44	0.72	UPC151C	2.95
KC582C	3.97	MC1330P	1.69	RCA17524	0.83	SN74190	2.00	T6059	0.65	TBA395Q	1.10	TD41770	6.05	TIC45	0.77	UPC2002	1.48
KC583C	5.54	MC1350P	1.61	RCA17523	0.83	SN7420N	0.34	T6030V	1.25	TBA396	0.80	TD41905	1.76	TIC47	0.35	UPC30C	2.51
L200CV	1.69	MC1351P	3.96	RCA2060	2.00	SN7430	0.49	T9005V	2.38	TBA400	2.38	TD41908	2.52	TIP120	1.06	UPC324C	4.70
LA1201	1.02	MC1352P	2.50	RG01-15	0.70	SN7440N	0.27	T9011V	0.49	TBA400P	2.45	TD41940	1.95	TIP110	0.85	UPC32C	4.94
LA1210	1.56	MC1357P	2.15	RG10	0.50	SN7472	1.54	T9013V	7.96	TBA480Q	1.30	TD41950	4.75	TIP112E	0.53	UPC339C	4.90
LA1230	2.87	MC1358P	1.30	RG30M	0.59	SN7474N	8.44	T9014V	2.60	TBA500P	6.58	TD42005	5.08	TIP112	0.88	UPC41C	4.10
LA1320	2.87	MC14001	2.40	RT402	1.58	SN7490AN	0.93	T9016	1.02	TBA510	1.67	TD42006	1.55	TIP117	0.95	UPC4558C	2.15
LA1352	1.75	MC14013	0.41	RT905A	2.38	SN74LS26N	0.53	T9019W	1.98	TBA520	1.94	TD42004	2.27	TIP121	0.87	UPC474	5.11
LA1357N	11.07	MC14493P	3.44	S1299	5.74	SN76001N	1.65	T9034V	1.38	TBA520G	1.68	TD42002	0.90	TIP126	0.73	UPC54C	1.85
LA1363	7.25	MC14494P	2.15	S175	31.48	SN76013ND	2.48	T9035V	1.39	TBA530	1.30	TD42003	1.75	TIP132	1.40	UPC566H	2.95
LA1364	3.02	MC14497	3.65	S2062D	2.07	SN76023N	5.15	T9051	7.45	TBA530	1.30	TD42010	1.85	TIP137	1.50	UPC574	3.25
LA1365J	3.44	MC14510BAL	3.75	S2800D	5.54	SN76023ND	3.96	T9054V	1.15	TBA540	1.15	TD42020	2.77	TIP29	0.66	UPC575C2	2.40
LA1385	1.94	MC14511BCP	1.10	S2802	3.47	SN76033N	4.15	T9057V	0.70	TBA540Q	1.15	TD42030	1.99	TIP2955	0.95	UPC576H	2.58
LA1387	7.80	MC14528BCP	2.70	S2818	4.05	SN76110N	0.90	T9062V	0.49	TBA560C	1.60	TD42140	1.59	TIP29A	0.46	UPC577H	1.25
LA3155	1.25	MC1712	3.88	S3702S	6.15	SN76115AN	1.61	T9064	1.51	TBA560CQ	1.80	TD42150	6.20	TIP29B	0.63	UPC578C	7.35
LA3301	1.41	MC15192	13.50	S40V	10.89	SN76131	1.92	TA6002	4.35	TBA570Q	1.60	TD42151	1.93	TIP29C	0.40	UPC580C	4.13
LA3350	1.43	MC7724CP	3.49	S8080B	8.80	SN76227N	1.33	TA7027	4.80	TBA570A	1.71	TD42160	4.01	TIP29D	0.75	UPC587C2	1.34
LA3361	1.23	MC7818C	2.18	SA8063	5.17	SN76226DN	1.98	TA7050	1.74	TBA61A112	4.13	TD42161	1.85	TIP3055	0.75	UPC592H	2.15
LA3365	3.98	MCR1007	1.85	SAA1006	4.75	SN76228N	3.27	TA7051	1.74	TBA61B72	3.03	TD42170	2.98	TIP30A	0.41	UPC595	2.95
LA3390	4.25	MCR106-5/6	0.85	SAA1025	1.76	SN76242	5.23	TA7054	2.55	TBA651	1.76	TD42190	4.95	TIP30C	0.16	UPC596	1.98
LA4030P	4.20	MCR2207	2.28	SAA1025	2.40	SN76243	4.81	TA7061AP	1.27	TBA673	2.60	TD42270	4.65	TIP31A	0.34	UPD1514C	8.95
LA4031P	3.20	ME0402	0.17	SAA1024	2.80	SN76396	2.90	TA7061AP	1.27	TBA700	1.85	TD42510	7.85	TIP31B	0.38	UPD2819C	4.98
LA4032P	2.35	ME0404/2	0.47	SAA1075	6.15	SN76533N	2.47	TA7069	3.13	TBA720	1.55	TD42520	2.37	TIP31C	0.50	UPD4013B	4.80
LA4100	1.25	ME0411	0.28	SAA1121	5.24	SN76532N	2.95	TA7070P	1.83	TBA730	3.50	TD42522	3.46	TIP32A	0.53	UPD4066B	4.95
LA4101	1.30	ME0602	0.26	SAA1124	3.25	SN76545	4.87	TA7072P	2.57	TBA750Q	2.90	TD42524	4.50	TIP32B	0.68	UPD8049C-1	19.25
LA4102	2.81	ME0610	0.28	SAA1130	4.99	SN76546N</											

# VCR Clinic

*Reports from Christopher Holland, Les Harris, Philip Blundell, Eng. Tech., Steve Illidge and Mick Dutton*

## JVC HRD140 – Ferguson 3V44/45

The latest generation of JVC VCRs have been around for about a year. Though proving to be reliable a fair number have appeared in our workshops in recent months. I'd hesitate to describe the following as stock faults: we've nevertheless encountered most of them more than once.

First a note about the circuit protectors used in the power supply. These look like two-legged transistors and appear to go open-circuit for little or no reason. Different sets of symptoms occur when the various d.c. lines produced by the power supply panel are absent. With any VCR that appears to be non-functional or has all the motors spinning at switch on, first check the unswitched 12V line and the switched 5V and 12V lines. Replacement of the appropriate circuit protector will normally provide a complete cure. Note that it's also easy to cause them to fail while you're working on a machine. The unswitched 12V line remains throughout the machine even when the front operate switch is at off, and there's no on-off switch at the back. Don't let the meter's probe slip while checking the output at plug CN3 of the power supply. Absence of the switched 5V line with the relevant circuit protector intact can be caused by Q10 and D3 on the power supply panel.

The use of resistors in place of circuit protectors is not recommended. Even very small value resistors will produce a voltage change that can interfere with normal working. Here's an example. The problem with the machine was that the drum motor would not spin when the tape loaded to the heads. This was eventually traced to someone having used a 4.7Ω resistor in place of a circuit protector in the switched 12V line.

Some other problems. The tape loading half way to the heads then returning to the cassette is due to the absence of drum pickup head pulses. I've had the lead open-circuit at the head, also a defective head where the pin fell out of the head body. If the machine plays for a few seconds then unloads, with fast forward or rewind for only a few seconds, the take-up pulses are missing: I've twice had Q1 on the deck terminal faulty – on both occasions the transistor checked o.k. on an ohmmeter.

The symptoms associated with absence of the switched 12V line are that the operate indicator comes on as soon as the machine is plugged in, the drum and capstan motors turn, the machine switching itself off after a few seconds. Should these symptoms continue after replacing the appropriate circuit protector, or if the protector is intact, check the outputs from the two loading sensors. These should give d.c. levels of 0V and 12V at pins 34 and 35 of the main microcomputer chip. If either level is wrong yet both loading arms are back in the cassette housing the timing of the gear train from the loading motor has slipped. Ideally you'll need a second open VCR to see how to put it all back together again. Why does the timing slip? Check that the back-tension arm is not fouling the left-hand loading arm during the unloading procedure.

Two problem areas with the previous generation of JVC machines were the cassette housing and a tendency for the video heads to clog with dirt very easily. The latest machines do not suffer from these problems to the same extent. If you have to remove the screening plate over the heads for any reason, take care when replacing it – it's

very easy to dry-joint Q1 on the head motor driver amplifier panel but very difficult to resolder this properly. There speaks the voice of experience!

On one occasion when I thought I had an instance of dirty heads the culprit turned out to be IC102, which is really a luminance subassembly soldered in at right-angles to the main PCB. Each to his own way of removing it. I've also had this assembly cause picture overloading after a few seconds of play, a squirt of freezer putting things right again for a further few seconds.

A case of failure to record was caused by the 9V line to pin 2 of IC101 being absent: Q111 had gone open-circuit.

An unusual problem was a VCR with no tuner channel change, being stuck on number one. A few preliminary checks failed to bring anything to light so as I'd a similar machine already on the bench I swapped the front panels. This didn't cure the fault. Back went the original front, whereupon I inadvertently discovered that the timer indicator wasn't responding to the timer switch. Deciding to follow this lead instead took me to pin 51 of the main microcomputer chip. Due to some form of corrosion there was a leak to pin 52, the 5V supply line. Cleaning the print provided a cure. A few weeks later another machine came in with the same fault symptoms and the same cause as well.

Another unusual problem was poor playback pictures with the machine's own recordings. The f.m. waveform at TP106 was continually varying in amplitude, with the output from one head occasionally disappearing altogether. The effect on the screen was that the pictures would fade into noise maybe twice or three times a minute. Examination of the record f.m. signal showed that nothing was amiss and the odd thing was that the noise appeared at different points when the same recording was played again. The answer was that no control pulses were being recorded. The cause: R438 was missing – it had never been fitted. This would have been easy to miss during a quick visual check as the picture was stable for up to twenty seconds at a time. Very good these digital servos!

There we have it then. All in all the best machine developed by JVC to date, and by quite a margin. The only design problems from a servicing point of view appear to be the bottom cover retaining screws, which can be awkward to remove, and the relatively inaccessible motor driver amplifier panel. There's also a knack to removing the bracket which holds the combined aerial amplifier/r.f. modulator unit. A weak point here appears to be the external aerial connection centre pins. We've found them to be broken on a greater number of machines than we would expect – potentially a very expensive repair. Otherwise these machines will in years to come greatly lighten the workload of harassed video engineers.

C.H.

## Ferguson 3V29/30 – JVC HR7200/7300

There have been various comments in these pages in recent months concerning the problem of loading motor belt slippage in these very popular machines. Perhaps the following notes will help. We've had a large number of

these machines through our workshops over the years and have found that a contributory factor seems to be dust on the motor and worm pulleys – the fault often occurs with VCRs that have a dusty interior, though not exclusively so. Before replacing the belt clean both pulleys and examine the two cogs that protrude into the upper part of the chassis and engage the loading rings – clean out any grit that's become embedded in hardened grease. Take care not to get any of the grease from the worm drive on the replacement belt.

Another point I've noticed is that belt slippage can occur as the machine warms up: on many occasions I've left a VCR on soak test while trying to trace a servo fault or whatever and after playing a three hour tape once or twice have found that the machine refuses to load. Most customers don't put their machines to this sort of extended use, but a case could perhaps be made for belt changing whenever one of these VCRs is brought in for service. Don't ask me how a belt stretches as a VCR warms up. Maybe the motor would be a more likely candidate for suspicion. Changing the belt however has always in my experience provided a complete cure.

Finally, I see a lot of VCRs that have been "looked at" elsewhere. A few intriguing solutions to this problem have been noted. I cannot comment on belt boiling as it's difficult to tell when a belt has been boiled, but bending the contacts of the after-loading switch is very popular: it doesn't work. Neither does replacing D3, an 11V zener diode on the mechacon panel, with a higher voltage type – the loading arms will come out of the cassette housing like greyhounds out of their traps but the belt will still slip. What will work is removing the loading motor from its bracket and elongating the bracket mounting holes using a needle file. I did this once with a local customer's machine when we'd no spare belts and told him to come back when the problem recurred: that was over a year ago, and I've not seen him since. Maybe he just didn't want to return to someone who confessed to carrying out a temporary repair. It's quicker of course to replace the belt. C.H.

### Sharp VC581

This was a good one! At stop the capstan rotated backwards and when play was selected the capstan stopped . . . Investigation started at the capstan forward/reverse switching i.c. (IC701) where the reverse select pin 2 was found to be high all the time. The track was traced back to D7018 via wire link J20 which was shorting to link J25. These links are at the right-hand side of the mother board. P.B.

### Panasonic NV7000

The fault with this machine was no sound in the E-E mode. Checks in the sound section revealed that the audio mute circuitry was operating: pin 1 of connector P4009 was high at approximately 5V. The cause of the trouble was the quad, two-input nand gate chip IC6010. Replacing this provided a complete cure. S.I.

### Panasonic NV333

The capstan wouldn't lock in the playback mode. Both the reference and capstan FG signals were present and on checking the d.c. voltages around the capstan servo chip IC2003 the voltage at pin 16 was found to be low at about half the correct level. Tracing this voltage back to its

source we found that the 9V supply to connection E on the system control board was missing. The cause was Q6003 being open-circuit: this transistor acts as a switch, supplying 9V except when the machine is in the record mode. S.I.

### Hitachi VT8000

On pressing the play button the drum motor would creep up to speed slowly, in an irregular manner. The capstan motor would then start, again in a very erratic manner. The 9V supply at PG502/6 and the 12V supply at PG502/7 were both low. The cause was traced to R054 on the system control board being high in value. S.I.

### Sharp VC8300

We had two of these in during the same day. The first wouldn't switch off, with the operate light always on. Q902 was found to be short-circuit. The second machine would lose the playback picture – the screen intermittently became a blank white raster. This was traced to dry-joints on plug/socket connector CD on board PWB-C. M.D.

### Sharp VC7700

The complaint was no play. The machine would lace up then unlace after about three seconds. We checked the inputs to the microcomputer chip and found that the source of the trouble was a false signal from the slack sensor mounted on the pinch roller bracket. Replacing this cured the problem. M.D.

### Panasonic NV370 with TX5500

We delivered a new Panasonic NV370 VCR and TX5500 colour receiver. This set employs a budget-type search tuning system that's difficult to fine tune exactly. We tuned in the TV channels, but when the VCR was tuned in there was loud intercarrier buzz on the ITV channel (41) in the E-E mode. We tried shifting the modulator frequency but this didn't help. It was possible to cure the problem by fine tuning the set but when the video channel was reselected the buzz returned. The problem remained even when both the TV set and the VCR were exchanged. As Panasonic had no suggestions we resorted to opening the VCR's modulator in the customer's house and adjusting the sound coil and video level potentiometer for no buzz. This cured the problem but means that the VCR is no longer compatible with other TV sets (low sound). M.D.

### Hitachi VT33

The problem with this machine, which had been faulty from new, was a ringing on playback of its own recordings. I replaced IC201 but the fault remained: this meant I had to think! A check through the recording signal path revealed that R222, which damps L204, was 270k $\Omega$  instead of 150 $\Omega$ . Replacing this resistor produced correct operation. L.H.

### Philips VHS VCR with Thorn TX9

A Philips VHS machine would work all right with any other set but on playback of some recordings via a set fitted with the Thorn TX9 chassis the top of the picture pulled and there was a white band at the top. The

problem was cured by fitting a 10dB attenuator between the TV set and the VCR. L.H.

### GEC V4004/Hitachi VT33

The problem with this machine was intermittent loss of colour on playback. After a few checks I suspected the

colour processing chip IC203 as I've had this fail before, but the fault remained when a new HT4239 was fitted. On making voltage checks at Q217 and Q358 I found that the 9V collector supply was only 5V, due to choke L215 in the supply line being open-circuit – the 5V was coming from pin 27 of IC203 via the base-collector junction of Q217! Normal operation was restored after replacing L215. L.H.

## LCD TVs from Citizen

Pocket TV sets using liquid-crystal panels to produce the picture have been on sale in Japan and the USA for some time. Late last year Casio released an LCD set in the UK and the 1985-6 Tandy catalogue lists two such sets, one by Casio and another by Citizen. Citizen are now marketing the set themselves in the UK and we have been lent one to see how it performs.

The present model has a 2.7in. (diagonal) screen with just over 18,000 pixels (picture elements). A model with 3.5in. screen, more pixels and incorporating f.m. radio is due for release shortly and a colour set is expected by the end of the year. The current model measures just  $7.5 \times 135 \times 23.6$ mm ( $15/16 \times 5\frac{3}{8} \times 3$ in.) and weighs approximately 230g (270g with batteries). It consumes 0.4W and can be operated from four size AAA batteries, an a.c. adaptor, a car battery or an optional NiCd rechargeable battery pack. Battery life is approximately ten hours with continuous use of four AAA alkaline batteries. There's a video input jack, earphone jack, external aerial jack and a.c. adaptor jack.

The LCD panel is illuminated from the rear and produces the picture by either allowing the light through or blocking it to a greater or lesser extent. Natural light (outdoors), a back-lighting attachment or other light source can be used. The panel consists of two sheets of glass with a gap of about 0.3 mil between them: the twisted nematic (TN) liquid crystal material fills the gap between these sheets. Two sheets of polarising material cover the rear and front surfaces of the panel. Inside the

panel are 122 horizontal row elements backing one glass sheet and 148 vertical column elements backing the other sheet. The intersections of the row and column elements produce the pixels.

Light entering the rear of the panel is first polarised, i.e. only light waves polarised in one direction are allowed through by the rear polarising sheet (ordinary light has random polarisation). The effect of the TN liquid crystal material is to change the polarisation of the light by  $90^\circ$ . The second polarising sheet at the front allows this light through. Control of the panel's light transmission is achieved by applying an electric field to each row/column intersection, i.e. pixel, in turn. The fields alter the alignment of the liquid crystal molecules with the result that the light transmission characteristic changes.

A block diagram of the Citizen receiver is shown in Fig. 1. The top part is conventional – a tuner, i.f. strip and audio amplifier – the rest is not. The LCD panel requires row and column drive, and there are 122 rows not 625 lines. The heart of the set is the control i.c. which provides synchronised timing for the display drives and converts the analogue video signal to a four-bit digital signal. This signal is then processed in the column driver i.c., using shift registers, latches and pulse-width modulation. The digital video signal is alternately stored in two shift registers, the switching being at  $0.3\mu\text{sec}$ . When a complete line of video signal has been stored it's read out at a rate that conforms with the row timing. It's then converted to pulse-width modulation to drive the column electrodes. The row drive circuit addresses the row electrodes in sequence: when a row is switched on, the column electrodes apply the pulse-width modulation to the pixels in that row.

The brightness of the display is varied in two ways, by the pulse-width video modulation and by the brightness control which sets the amplitude of the pulses applied to the column electrodes. Note that the brightness control has to vary several voltages so that its operation does not affect the pixel address switching.

It's necessary to generate higher voltages than the 6V input: the varicap tuning system requires 38V while the row address system requires up to 19V. An LC oscillator and two rectifier circuits produce these higher voltages.

Some sophisticated electronic technology is used in the set and the construction is a masterpiece of miniaturisation – the PCBs use surface-mounted component technology. We found the set to be sensitive, using its built-in rod aerial, and easy to tune. What of the picture? We feel that any attempt at lengthy viewing would not be easy on the eyes. But then the set is not meant as a main TV picture source, rather as a portable picture source to refer to as and when the user wishes to do so. The limited resolution unfortunately makes most lettering illegible.

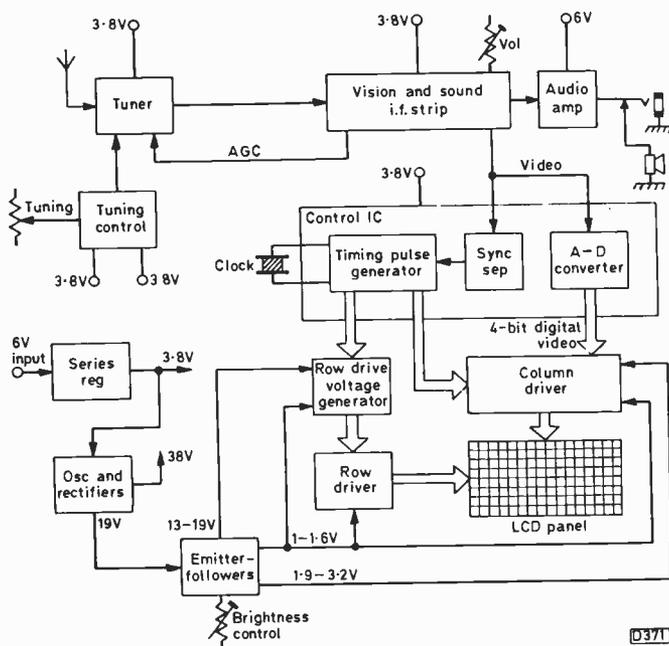


Fig. 1: Block diagram of Citizen's LCD TV receiver.

# TV Fault Finding

Reports from Alan Shaw, Michael Dranfield and Philip Blundell, Eng. Tech.

## Thorn TX100 Chassis

This is the best TV chassis produced to date by Thorn-EMI-Ferguson. It's used in sets fitted with various types of tube, certain component values being changed to suit. As with most new TV chassis there's no such thing as a common "stock" fault. Anyone with experience of the later TX9 and the TX10 chassis will be at ease with the TX100. I hope the following notes will be of interest to those who are not too familiar with Ferguson colour sets.

One interesting feature is the automatic grey-scale adjustment. If you reduce the height of the picture you'll see three test lines above the picture area. These test lines (23, 24 and 25) are used to produce a beam current of  $10\mu\text{A}$  to set the c.r.t. cut-off point for each gun. The only variable controls are for the highlights. A start-up delay circuit (TR3 etc.) earths pin 18 of the colour decoder chip when the set is first switched on to prevent the rapid warm-up c.r.t. producing a bright picture that drifts down to black level.

The power supply is built around the popular TDA4600-2 self-oscillating chopper control chip. A replacement must have the suffix -2: the early TDA4600 will not work in the chassis. Start up is via a thyristor (SCR1) which provides a supply to pin 9 of this chip – around 5-6V at this pin is sufficient to get the circuit going. D10 stops SCR1 working once the chopper circuit comes into operation. When the h.t. voltage rises so does the voltage across pins 10-8 of the chopper transformer: this voltage controls the mark-space ratio of the output from the chip. The chopper circuit's normal operating frequency is 20kHz, rising to 60kHz with remote-control versions in standby and dropping to 4kHz when there's a heavy load on the 119V line, e.g. a short-circuit line output transistor.

Important servicing note: the 15V regulator chip IC9, the sound channel chip IC5 and the field output chip IC6 are all temperature conscious – never apply freezer to any of them under fault conditions. IC6 will automatically turn off when the temperature exceeds  $175^{\circ}\text{C}$ . If you apply freezer you'll turn it back on, with possibly alarming results – the i.c. can literally explode, with consequent damage to the board.

Faults we've had to date are as follows. (1) Blown mains fuse due to the chopper transistor TR6 being leaky or short-circuit. Check the TDA4600-2, R121 ( $27\Omega$ ) and R114 ( $0.47\Omega$  or  $0.39\Omega$  depending on chopper transformer), also R115 ( $330\text{k}\Omega$  or  $270\text{k}\Omega$  depending on chopper transformer) – repeated failure of TR6 is likely if this latter resistor is out of tolerance. (2) Grainy picture due to the r.f. amplifier transistor in the tuner or the SL1432 i.f. preamplifier chip IC1 being faulty. (3) Intermittent field collapse due to C95 ( $0.01\mu\text{F}$ ) being intermittently leaky. (4) A small picture due to D28 (BY299) being leaky – this diode is present only in 110° models. A.S.

## Some Quickies

**Ferguson TX90 chassis:** We've had a couple of these portables in with the mains fuse blown due to one of the c.r.t. fixing screw washers trapping the degaussing coil and shorting it to the earthed c.r.t. rimband.

**ITT CVC32 chassis:** Blank raster, sound o.k. Check

whether R28 ( $820\Omega$ ,  $\frac{1}{2}\text{W}$ ) on the mother board is open-circuit.

**Amstrad CTV1400/Orion 14PC portable:** Intermittent flashing and drifting is usually caused by faulty eight-way channel selection switches but can also be due to a faulty tuning potentiometer bank. Note that while they look the same the potentiometers in non-remote control models are  $100\text{k}\Omega$  each while those in remote-control versions are  $20\text{k}\Omega$  each.

**Pye 725/737 chassis:** For weak field sync check C941 ( $4.7\mu\text{F}$ ).

**Thorn 9000 chassis:** Line off speed. C715 ( $22\mu\text{F}$ , 275V) open-circuit.

**Philips KT4/K40 chassis, remote control versions.** Unable to tune any stations, on-screen line not moving and no channel display – the 5V regulator on the VST panel is open-circuit. Remote receive light permanently lit, channel change slow to react – D6103 (BA317) on the VST panel leaky. A.S.

## Thorn TX90 Chassis

A few of these sets have been in for repair with the same fault – intermittent collapse of the bottom half of the field scan and height variations from the bottom upwards. This is caused by dry-joints around the field output transistors. As there aren't many components in the field output stage we generally resolder the lot. M.D.

## GEC C2110 Series

Some quickies on these sets.

**Field collapse:** Check the voltage at the collector of the discharge transistor TR452. If abnormally high (33V) change R455 ( $470\text{k}\Omega$ ).

**Slight field jitter at the top of the picture:** Replace the mid-point voltage preset P454 ( $470\Omega$ ).

**Height shrinks as the set warms up:** Change the field driver transistor TR453 (AC188).

**Picture only ten inches high, with unlocked colour and distorted sound:** Replace the 40V supply rectifier D601 on the line timebase panel. A BY210-800 is suitable.

**Loss of one primary colour with a dark picture, the relevant first anode voltage being low:** Replace the tube base spark gap associated with the missing colour. M.D.

## Thorn 1790 Chassis

We've had a lot of these sets in for repair lately, all with the no results symptom. In every case the cause has been bad cracking around the mains transformer. One set came in with an intermittent fault: no signals, no video and a jumping picture. When the fault eventually appeared we found that the 90V rail was missing. This was traced to a crack around one of the line output transformer's pins. M.D.

## Philips G9 Chassis

There was a very odd fault on this set. The top quarter of the field scan was missing: it wasn't compressed or folded

over, and the rest of the picture was normal. The set was left on and after ten minutes the scan had filled more of the screen, leaving a circular patch at the top left. A quick timebase panel swap proved that the fault was in this area and a number of electrolytics in the field timebase were changed: the fault was cleared when C22 (10 $\mu$ F) and C51 (47 $\mu$ F) were replaced. Surprisingly if either one of these capacitors was replaced the fault remained: the two capacitors had to be replaced as a pair and we couldn't find anything wrong with the originals. **M.D.**

(Editorial note: In this chassis changes in the conditions in the field timebase affect the line blanking.)

### Philips KT3 Chassis

This set led me a merry dance: there were intermittent black lines at the top of the picture. As usual the fault disappeared as soon as the chassis was disturbed. Over a

period of time the decoder panel and the blanking transistor were replaced to no avail. Then one day the test card was on when the fault appeared and I noticed that the top of the picture was bending over to the right. Examination of the soldering on the sync separator and i.f. modules revealed that C2148 at the input to the TDA2540 chip, inside the i.f. can, hadn't been soldered in. **P.B.**

### Philips K35 Chassis

This set had no colour till you turned up the brightness. Then along with the colour came flashing horizontal lines. Substitution proved that the fault was in the decoder module. A new TDA3560 decoder chip stopped the flashing lines but a replacement for C66 (100 $\mu$ F) was required to bring back the colour – this electrolytic decouples the 12V supply to the chip. **P.B.**

# Long-distance Television

**Roger Bunney**

March was another relatively quiet month but now that April is here there should be increasing Sporadic E activity – mid-April SpE openings usually indicate a good season ahead. A brief outline of SpE signal propagation is given later in the column for the benefit of new readers.

The repeat performance 27 days after the massive Aurora on February 8th produced little by way of reception here in the south – I noted only heavy patterning from the north on chs. E2/R1 on March 6th. Iain Menzies, well placed in Aberdeen, logged AR signals on the 6th, 7th and 9th, but only NRK (Norway) chs. E2/3 and TSS (USSR) ch. R1, during the later evening periods. NRK/TSS signals were again logged via AR on March 17th, 20th, 22nd, 23rd and 26th. Further information on the February aurora has come to hand. On the 8th a Swedish amateur (SM6PU) heard a US amateur (K1TOL) operating at 50.11MHz (time 0050-0052). SM's aerial was aimed at 279°. During the midnight period K1TOL heard the UK 50MHz beacon on Anglesey (GB3SIX). This shows that transatlantic DX-TV reception must have been possible in Band I, though it would have been of poor quality.




There was minimal SpE propagation during March. The best days were the 18th with TVE (Spain) ch. E3 and TVP (Poland) ch. R1, both at 1220-1230, and the 27th with SR-1 (Sweden) ch. E3.

Tropospheric propagation matched the poor weather conditions. There was a slight lift on the 14/15th, giving enhanced reception from France. Dave Shirley at Hastings and Tim Anderson at St. Leonards claim the first reception in the UK of the new French local stations. Dave logged TV5 from Lens on ch. E51 at 0200 on the 15th, with a PM5544 pattern carrying the identifications "TDF" and "RES 5". On the following night he received the Lens TV6 signal on ch. E54, this time on programme with a "TV6" insert at the top right corner, then the PM5544 pattern with similar identifications though "RES 6". The signals were not visible until stronger main network TDF transmitters came on air.

Not an exciting month then, but by the time this is read things should be happening. During the strong gales over the weekend of the 22nd/23rd Cyril Willis's aerial system collapsed: repairs are in hand.
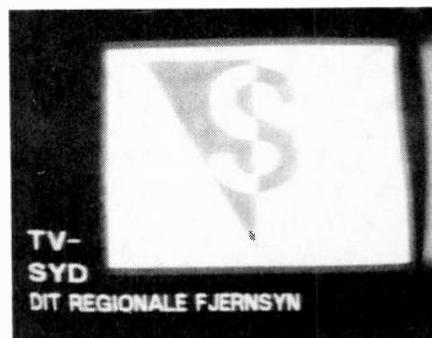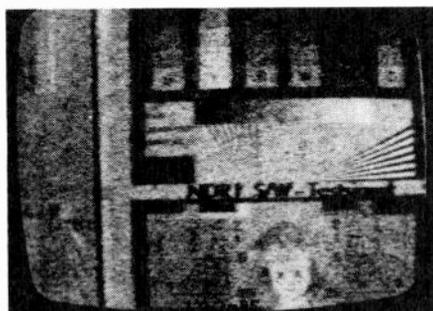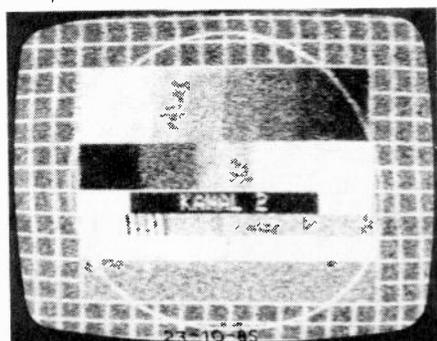
### News Items

**UK:** Gloomy news concerning Band III. It appears that up to five mobile radio networks are to be established in the London area with up to twenty channels each. Regional networks with up to nineteen channels are to be established in Birmingham, Merseyside, Nottingham, Leeds and Central Scotland. National Radiophone should be in operation by the end of the year, covering the London area to the M25 with four transmission sites using twenty channels each.



Left: The FUBK test pattern in use by Copenhagen on ch. E56 at 200W – a French signal transmitted during the October tropospheric opening. Centre: An unusual test card received from Hamburg, ch. E9, in early 1985. Right: A Danish regional identification on ch. E7. Photographs of reception by Ryn Muntjewerff in Holland.

**Ireland:** The Republic is permitting an experimental amateur radio allocation at 50-51.75MHz, on a limited basis – about twenty operators will be allowed to operate in the first phase, provided there's no interference to cable TV and the RTE-1 outlet at Maghera.

**France:** A seventh TV network (TV7) is expected to start operations in mid-1987, with programme linking by satellite.

**Spain:** Full daytime transmissions are planned. We understand that Breakfast TV will be via the TVE-1 transmitters.

**In brief:** China is to launch a TV/communications satellite . . . RTM (Morocco) is now testing all day on chs. E25/6, using the PM5544 pattern . . . SBS-TV (Australia) started services from Hobart (Tasmania) and Perth during March, on ch. 28: a new ch. 10 commercial service is planned for Perth.

### Satellite TV News

There's been a severe fall off in sales of satellite TV receiving equipment in the USA, mainly because of uncertainty caused by the increased use of scrambling. There have been redundancies in at least two equipment manufacturers – Amplica and Birdview Satellite Communications have announced redundancies approaching forty per cent. The latter company says advances in equipment technology mean that fewer manufacturing personnel are required. There's also a general move to Ku band (11.7-12.2GHz) operation by cable programme originators in the USA in order to avoid their material being received without payment by those with C-band TVROs. Major NBC feeds have recently been transferred to the SBS-3 satellite at 95°W (transponder 1) in preference to adopting scrambling in Band C. Anderson Scientific has produced a "low-cost video stabiliser" which will unscramble VideoCipher 2 and Oak-Orion transmissions – the former has digitally encrypted sound, which is likely to pose a problem.

The AUSSAT satellite is now relaying ABC-TV (Victoria) TV programmes on a full-time basis. Interesting that Tony Dunnett in North Island, New Zealand has received the C-band downlink at his company's NZ location. Tony's company (SAT-TEL – no connection with the UK firm of the same name) makes dishes in sizes up to 3m and LNAs down to 50°K.

### Fringe Electronics FM Radio Preamplifier

Fringe Electronics Ltd. (Fringe House, 50 Mansfield Road, Clipstone, Notts NG21 9EQ) has introduced a mains-operated, set-back preamplifier intended for use with f.m. radio equipment: the noise figure quoted is 1.9dB and the claimed gain is typically 20dB. I've recently had one for assessment. Internally the single stage of amplification, using a bipolar transistor, has bandpass input tuning and a tuned collector load circuit. A voltage stabiliser is incorporated and the circuitry is built on a high-quality, low-loss PCB. I've no criticism of the construction. The noise could be checked only subjectively but measurements of gain were made. Over the 88-108MHz band the gain varied from 22dB to 23.5dB, comfortably exceeding the claimed figure. Gain was also checked at various frequencies outside the band to assess the response to known or possible sources of high-level interference. These tests indicate that the unit should minimise if not eliminate all but the strongest local sources of interference. At 41MHz the gain was -25dB, at 50MHz -18dB, at 65MHz -5dB, at 75MHz +7.5dB, at



**HAVE YOU A COPY OF  
OUR CATALOGUE?  
IF NOT, WHY NOT  
SEND FOR ONE TODAY.  
ONLY 65p**

### EQUIPMENT & PROFESSIONAL ADVICE

Aerial Techniques offer a unique blend of the best equipment and impartial professional advice for Television/FM DXing or simply better domestic reception.

**LABGEAR UPCONVERTERS** ideal for TV-DXing, used but guaranteed in good working order, mains powered, limited stock ..... £17.95  
**WB5/FD – Wideband Band 1 (47-68MHz) VHF Aerial**, 5 element, high gain with folded dipole for correct matching ..... £38.60  
**TRIAx 720/B1 Stacking Filter**, for stacking two Band 1 Aerials, to increase system gain ..... £13.15  
**ANTIFERRECE UP1300 VHF masthead amplifier (40-230MHz)** for Bands 1, 2 & 3. Gain 19dB, low noise figure of only 2.5dB ..... £16.90  
**Matching power supply unit (12V)** for use with above amplifier ..... £12.33  
**'NEW' AR250 'offset' Aerial Rotator** complete with latest type of Control Console, features continuous indication of beam/aerial heading, uses 3 core cable ..... £45.68  
**SB100 Alignment/Support bearing** for above Rotator, allows greater aerial head loads to be used ..... £16.85  
**'NEW' BEST OF CO-TV** book by John Wood ..... £3.50

Whether your need is for local or fringe reception, alternative channels, TV/FM DXing, or for a distribution system, Aerial Techniques is the 'one stop' address for all equipment.

All prices inclusive of VAT and Carriage. Delivery 7-10 days.  
**ACCESS & VISA** Mail and Telephone orders welcome.



**AERIAL TECHNIQUES (T)**  
 11, Kent Road, Parkstone,  
 Poole, Dorset, BH12 2EH. Tel: 0202 738232.



146MHz -17dB, at 160MHz -28dB and at 170MHz -43dB: 50 and 146MHz were chosen in view of current or pending amateur radio operations while 75, 160 and 170MHz were chosen since they relate to PMR activity.

Checks with weak signals above 100MHz in all instances gave a very clean improvement to a signal that had previously been just above the noise level. In general a weak signal at the noise level was raised to give acceptable, "cleanish" mono reception. I found no evidence of overloading at the bottom end of the band despite the presence of very strong signals locally – this was when listening to weak commercial/BBC stations between strong local ones. It's possible however that the gain could be too great for use with inferior tuners/receivers with bipolar front ends (and thus more susceptible to overloading). My own receiver, a mid-range Sanyo with MOSFET front end, gave no problems. I tested the amplifier thoroughly with a view to DX-FM use and the results were excellent.

The unit comes blisterpacked and sells for £15.75 plus VAT. With appropriate splitters it could also be used in a distribution network.

### Old Sets for Disposal

Two elderly sets have recently been passed on to me – they'll be dumped if no one wants them! The first is a mid-fifties Ekco mains/battery portable, Model TMB272. It was working when put into store many years ago. The other is a set I know better – a Bush TV62 in a Bakelite cabinet. I used this type of receiver for many years and can recommend it despite it being made back in 1957: it works, the screen lights up and the cabinet is uncracked –

it'll be a collector's item in years to come! These sets are free but must be collected (Southampton area). If interested, drop us a line with s.a.e. The TV62 can be converted to 625-line operation but it would be nice to see it left as a memorial to 405 lines.

### New Book

The latest publication from the BATC (available from 14 Lilac Avenue, Leicester LE5 1FN) is "The Best of CQ-TV". It contains the more important and innovative articles that have appeared over the last five years in the BATC journal *CQ-TV* - interest in amateur TV has increased greatly in recent years and back copies of the magazine are now generally unavailable. The articles cover operation at both 70cm (435MHz) and 23cm (1.3GHz), f.m. and a.m. video, test equipment and even a vision mixer, with full circuit diagrams and with some PCBs offered to members. I truly recommend this 100-page (A5 format) book: it's well worth the £3.50 (including UK postage) price, being packed with information. Overseas readers should send a London based bank draft and include sufficient extra postage.

### Australian Channel Allocations

Robert Copeman (Melbourne) has sent us an up-to-date listing (May 1986) of the Australian v.h.f. and u.h.f. TV channel allocations (see Table 1). The B/G system applies, i.e. with 5.5MHz sound-vision spacing and also PAL colour. Note that the use of Band II for TV is being gradually phased out as the number of f.m. radio stations using the band increases.

### From our Correspondents . . .

First a couple of corrections. In the December 1985 column we showed a Tele Malta Corporation test pattern received by Mel Thurlbourn whilst he was in the area and suggested that the power of the ch. E10 transmitter was 10kW. Edmond Friggieri tells us that the power is less than 2kW. In the April issue we showed a slide received by Marios Colocassides in Cyprus and captioned it as being from Tunisia. We got the channel right (ch. E33) but the transmission was from Beirut.

In the April column we mentioned a query about reception of an AFRTS signal in Rastanura, Saudi Arabia, on ch. E27. A London-based reader has solved this mystery for us. The source of the signal is a 100W transmitter owned/operated by the Omani Prime Min-

ister. It's of Acrodyne manufacture and is fed with signals from an 11m Scientific Atlanta Intelstat (B standard) earth station. Apparently there are several such receive-only stations dotted around the Gulf area, privately owned by prominent people. The Omani transmitter broadcasts the AFRTS-Southern Europe service for the benefit of local residents, taking the feed (without censorship) from transponder 9 on Intelstat V F-02. There were plans at one stage for a similar service in Abu Dhabi. Interesting that in Turkey the AFRTS relay is delayed for 24 hours for censorship purposes - even for US Forces!

### Sporadic E Propagation

The "season" for Sporadic E propagation normally extends from about the second week in May to mid-August, with sometimes a minor spell of activity in mid-April and another period in mid-December. The ionosphere's E layer is some 70 miles above the Earth during the day and though reflective to short-wave signals is generally transparent to v.h.f. signals. M.W. signals are normally absorbed by the D layer during the day, though reflection from the E layer occurs after dark when the D layer disperses. Reflection of v.h.f. signals from the E layer occurs when ionised clouds are present. These occur at random and cannot be forecast. Incident Band I signals can be reflected over great distances, typically 500-1,500 miles in a single hop. The higher the intensity of the ionisation the higher the signal frequency that can be reflected. Reflection of Band III signals occurs only rarely: reflection of Band II radio signals is rather more common.

During an opening the reflective clouds vary in number and may be stationary or move at some speed. As a result the signal reflections will vary: the skip conditions change and alternative signals may appear on a channel. With widespread reflection the result is severe interference. Reflective conditions can last for minutes or hours. There's a greater chance of SpE activity when the weather is humid and thundery.

Since SpE signals can be very strong a simple wideband dipole will often suffice for reception: two fixed dipoles mounted at right angles will allow switched coverage of all directions. Alternatively a two-element wideband system with a rotator can be used. Aerial height need not be high - the signals tend to arrive at an angle relative to horizontal - but it's best to have the aerial at 20ft or so to clear nearby objects. Most signals start off horizontally polarised, but a propagation shift tends to occur. The general rule however is to mount the aerials horizontally. We hope to feature shortly a wideband Band I/III design as a DIY project.

Double-hop reflection will bring in signals from 2,000 miles or beyond, signals from the Middle East often being seen in the UK. Use of an indoor preamplifier will often help with weaker signals. Local interference tends to occur in Band I and is best filtered out before amplification: provided premium quality coaxial cable is used there will be little loss and the optimum signal/noise ratio will be maintained.

A 625-line receiver with v.h.f. coverage can be used or alternatively a u.h.f. receiver, preferably with single-knob, slow-motion tuning, can be used in conjunction with an upconverter. Improved results will be obtained by using a narrow i.f. bandwidth to reduce adjacent channel interference. Finally a commercial: my DX-TV book, published by Babani publications, is at present out of print - a new edition is expected shortly.

**Table 1: Australian TV channel allocations.**

Ch.	Freq. (MHz)	Ch.	Freq. (MHz)	Ch.	Freq. (MHz)
0	45-52	33	561-568	53	701-708
1	56-63	34	568-575	54	708-715
2	63-70	35	575-582	55	715-722
3	82-92	39	603-610	56	722-729
4	94-101	40	610-617	57	729-736
5	101-108	41	617-624	58	736-743
5A	137-144	42	624-631	59	743-750
6	174-181	43	631-638	60	750-757
7	181-188	44	638-645	61	757-764
8	188-195	45	645-652	62	764-771
9	195-202	46	652-659	63	771-778
10	208-215	47	659-666	64	778-785
11	215-222	48	666-673	65	785-792
28	526-533	49	673-680	66	792-799
29	533-540	50	680-687	67	799-806
30	540-547	51	687-694	68	806-813
31	547-554	52	694-701	69	813-820
32	554-561				

# Other things and other places

Les Lawry-Johns

There's more to life than TV sets, though there are times when this is none too obvious. Anyway, I thought you wouldn't mind if for a change I told you about some other things and places.

## The Coat

One of these things is my overcoat. It was made to measure in 1938 by M. Burton and cost 37/6d. For those of you who want that in present day money it comes to one pound thirty seven and a half pence (I think). That coat is as good as new and still fits. It's double breasted and waisted. I've worn it twice during the last thirty years, which all goes to show how many funerals I've attended. Not quite true that, because an overcoat isn't needed in summer. Jealousy will get you nowhere. Oh yes, black melton.

## The Journey

Next places. A couple of weeks ago the phone rang during the evening. HB answered it. She sounded a bit excited and I heard her say "We'll come up and get it". Since her daughter Colleen was with us at the time she didn't say anything more about the conversation. After Colleen had left I was told all about it. Colleen had always wanted a small Dachsund and we'd sent out signals a month or two back in the hope of getting one for her birthday. One of the signals had now been answered: there were three puppies ready to leave their mother and we could have our pick. All we had to do was to hang up the Closed sign and pop up to Dersingham. Lovely, but where's that?

I consulted my AA New Book of the Road. It's just up from Kings Lynn, near the Wash. My eye wandered down the A10 to Ely, thence to Cambridge and Theydon Bois to pick up the M25 to Dartford Tunnel. Not far. Any idiot could do it with a full tank of petrol.

On the following Tuesday the tank was full, the oil was checked and we were ready to go. Colleen arrived at nine thirty and we were off. First to the Dartford Tunnel which is practically on our doorstep. I missed it. We circled round and after a slight detour through Bexley we got there. Never mind, we were on our way in my safe and strong hands. Straight up the M25 towards Theydon Bois, steer to the right and up the M11 and on our way to Cambridge. On and on like the brave six hundred my Grandad used to sing about. Harlow came and went, then Bishop's Stortford. Flashing along the motorway while other cars flashed past as though we were standing still.

Undeterred we fought our way up past Cambridge and on to Ely, my eyes like diamonds behind my new specs (first time wearing them for two years), though I must admit they were getting tired. King's Lynn loomed up and we went round a roundabout and took the A149 past Castle Rising on the left and finally hit Dersingham. By now the Ouse was ousing all over the place and had been

for some time: waterways to the right of us, waterways to the left. On we went, past the fish and chip shop, slowly now, looking for the flags. At last we found them and turned into our destination. A man was waiting at the gate. He'd been waiting for a long time.

HB jumped out and greeted him profusely. I was amazed. Then Colleen did the same. I got out and we shook hands like gentlemen.

"This is my Uncle Roy" said HB.

"Well I'm buggered" said I.

"This is my husband."

"Well I'm buggered" said Roy.

HB hadn't even said we were going to relatives.

Into the house where Roy's wife greeted us warmly. Colleen looked at the large box on the floor from which some whimpering issued. "Goodness, aren't they beautiful!" she cried. One had a black patch on its back. She leaned over and picked him up, then realisation dawned. "He's yours" we told her.

We had lunch and gossiped. I finished off my whisky and started on some wine. They'd a lovely garden where the birds were well catered for. While we were admiring its features we saw a bag containing a marrow and some beans being passed over the wall on a rope. Roy took the bag in and came out with a bottle of home-made wine. It was tied to the rope and pulled over the wall. Nary a word was said.

"Does that happen often?" I queried.

"Several times a week – the wife makes good wine."

"So I'd noticed."

By now it was almost two and I was beginning to wonder how long it would take to get back. So with Dacksy in a box and plenty of food for him we took our leave and departed, heading for King's Lynn. Somehow I took the wrong road and we went through miles and miles of country. There wasn't much sun but what there was I kept to the right of me so I knew we were going south. Eventually we arrived at Ely. HB glanced at the petrol gauge. "We're half empty."

I'd also been looking at it. "We're half full" I said.

We were well on the way to Cambridge now, but instead of bypassing it I found myself in the town centre. So many bikes, I've never seen so many. We went round the market square just for fun and headed out of town, eventually finding the M11. Down we hurtled while cars flashed by in the outer lane. The petrol gauge by now read very low. It suddenly occurred to me that there are no filling stations on these motorways. I didn't want to go off and get lost again; I also knew that an empty reading meant that there were still two gallons on board. But at the speed we were going they wouldn't last very long. So I gritted what teeth I had and slowed down. We crept along the M25 and under the Dartford Tunnel. Then along the A3 till we were able to fill up just three miles from home. We were glad to be back. Dacksy had slept all the way and even Douggie (Colleen's husband) likes him.

So much for the trip and its confusions. I don't know how ET manages it: from one end of England to the other about twice a week. But I'm not that bad at navigation. JAR gets lost trying to find his way from one side of London to the other (almost) on a good day with the light behind him . . .

## Oven Problem (Microwave)

You remember HB's sister Dot – her with the brown eyes? Well Dot has a microwave oven with two bulbs in it.

These are in series which means they are rated at 125V (20W). One went so they both went out. HB brought the good one down so that we could match it. We couldn't. Not only because we don't have any 125V bulbs but also because the base is slightly larger than the normal SES.

So HB trudged around the town, getting the same

response. One shop assistant gave her detailed instructions on how to get to our own shop, which pleased her no end. Our wholesalers don't seem to have them either, so Dot's going to have to make do with a one lamp (240V) oven with the other lamp shorted out. If we can find a 240V lamp with that unusual base.

# Servicing Sinclair Microcomputers

## Part 2

Ken Taylor

Last month we considered some of the i.c.s used in microcomputers and ended with a block diagram of the simplest computer possible. It had just a Central Processing Unit (CPU – the microprocessor), a Read Only Memory (ROM) that contained the operating instructions, a Random Access Memory (RAM) for storing the program and data and an Uncommitted Logic Array (ULA) for doing all the hardware jobs, including interfacing with the TV modulator and the tape input/output ports. Fig. 5 last month was in fact a block diagram of the Sinclair ZX81 microcomputer which is probably the simplest possible home computer design. We'll now examine this model as an introduction to computer servicing.

In producing such a simple computer Sinclair Research introduced several features which make both the circuitry and operation rather different from that of the more usual type of microcomputer. For instance, where have all the other chips one might expect to find gone? The ones that generate the TV display signals and the decoder chips that decide whether it's the ROM or RAM you want? Or the special that looks after the keyboard? They all seemed to be essential in the Amstrad machine described in this magazine last year. In the ZX81 these jobs are all shared between the CPU and the specialised circuitry in the ULA, the timing and decision making being carried out by the former. There's a penalty to be paid for doing things in this simplified way however: the time the CPU has available for processing the program is severely limited. In fact whenever there's a display present the CPU is free only for the period of the field flyback – for the rest of the time it's producing the line sync and display details!

### Sinclair ZX81 Circuit

So when you study the ZX81's circuit details (Fig. 1) remember that this is a very specialised machine with a component count unlike most other microcomputers, though it does have a standard CPU and a system that functions in the same way despite looking so different.

Further examination of Fig. 1 will help to explain some of the differences and clear up many of the problems described above. You'll see that the ULA chip is connected to the TV and tape circuits directly at pins 16 and 20. It can decode the address lines and then enable either the RAM or the ROM via one of the Chip Select (CS) lines at pins 12 and 13. It also assists the CPU in reading the keyboard, via the KBD0-KBD4 lines. These link the ULA to the keyboard via a five-pin socket (KB1) that's not shown in the diagram. This PCB-mounted socket connects the keyboard "tails" to these lines while an eight-pin socket (KB2), also not shown, connects the other keyboard tails to diodes D1-8. The ULA also produces

the 3.25MHz clock signal from the 6.5MHz ceramic filter (X1) connected to pin 35.

The machine has only 1Kbyte of RAM fitted to the board. Provision is made for this to consist of either one 4118 memory chip or two 2114 chips. There's also provision for fitting a 2Kbyte RAM for the export model. The usual memory extension consists of a 16K unit which plugs into the edge connector at the back of the machine. Fitting an extension memory disables the internal 1K memory however – the following test procedure assumes that only the internal memory is in use.

The data lines to the ROM and RAM and some of the ROM address lines incorporate buffer resistors. These enable the lines to be used by more than one device without conflict. They are very useful in a fault situation for determining which device is still functioning satisfactorily. Lines downstream of these resistors are given an identifying accent, e.g. A1'. The edge connector also has these identifications on some of the contacts to show which side of the resistors link up with them.

There have been at least three versions of the PCB. Fig. 1 represents the issue one board but I've experienced no difficulty in identifying the circuitry on later boards. They vary a little in layout but the component numbers on the boards seem to be the same. One of the only differences on the issue three board is the use of individual resistors in place of packs RP1 and RP3 – R35-42 and R43-47 respectively. There's a photograph of an early version of the issue one board, without component numbers, on page 162 of the ZX81 BASIC Programming Book that was supplied with every machine. This photograph shows all the i.c.s mounted in sockets, which certainly isn't the case with later boards. Note also that the ULA is called the "Sinclair Computer Logic" which is a less standard but perhaps more sensible name.

The power supply unit is separate from the computer and connects to it via a 3.5mm jack plug. It's not shown in Fig. 1 but is a simple d.c. unit that gives very little trouble – except for the moulded jack. If you have one that's been changed, make sure that the tip is positive.

### Initial Checks

When the computer is first switched on the display should consist of a white-on-black K (inverse K) cursor at the bottom left of the screen.

If it doesn't, carry out the following simple checks. Remove any extension memory plugged into the rear connector. Check the power supply – the plug should provide an open-circuit voltage of about 14V, tip positive. If the plug has been changed for a solder-on type it's easy to check the on-load voltage which should be about 11V. This will show whether an overload or open-circuit con-

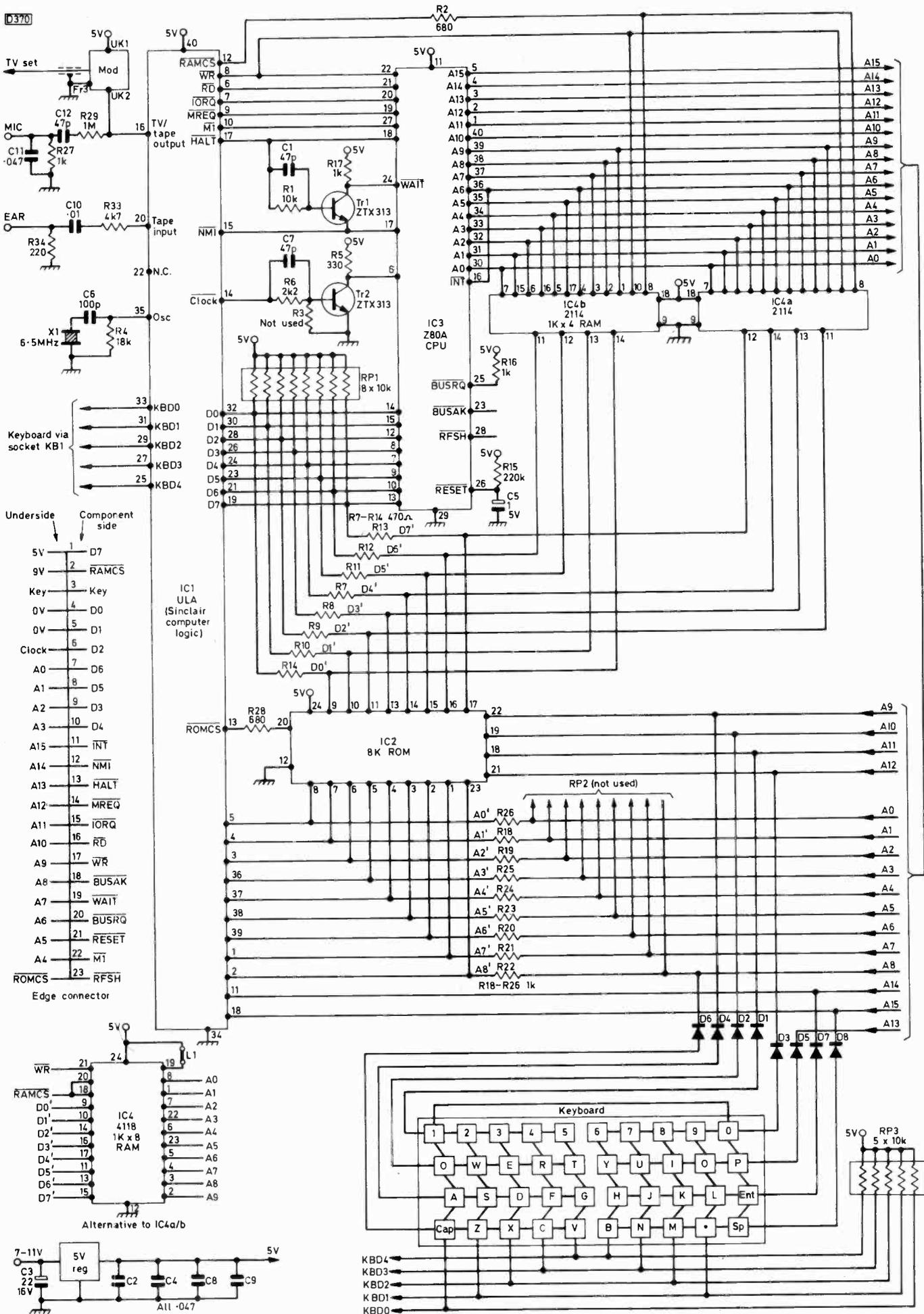


Fig. 1: Basic circuit diagram for the Sinclair ZX81 microcomputer.

dition is present in the machine. In the latter case suspect that the plug has at some time been connected with reversed polarity – this often blows the 5V regulator and saves the rest of the circuitry.

Check the tuning. The modulator is usually set to channel 36 quite accurately, but sweep the band in case the tuning has moved or been altered. If there's no output signal from the ULA the modulator's output will consist of carrier only, devoid of even sync signals. In this case the indication on the TV screen will be negligible.

### Dismantling the ZX81

If you haven't found the fault by now you'll have to make internal tests. This means dismantling the unit. First remove the four screws from the base. Three of these should be hidden under rubber feet – if these are still there (the two at the front and the one at back left). Lift


off the base and remove the two screws securing the PCB. If you turn the board over towards the front the keyboard tails can be removed from the two sockets. Treat these plastic strips with the utmost care – they are very easily damaged (more about this later).

With the board completely removed the TV and power supply leads can be reconnected. Initialisation of the computer to give the inverse K cursor display occurs without the keyboard being connected, so we can leave it disconnected until the fault has been found.

### Fault Finding

Table 1 provides a quick fault-finding sequence: the numbers refer to the following paragraphs which give details of the procedure. Remember that there can often be more than one fault present, so repeat the sequence if necessary.

Table 1: ZX81 fault-finding sequence.

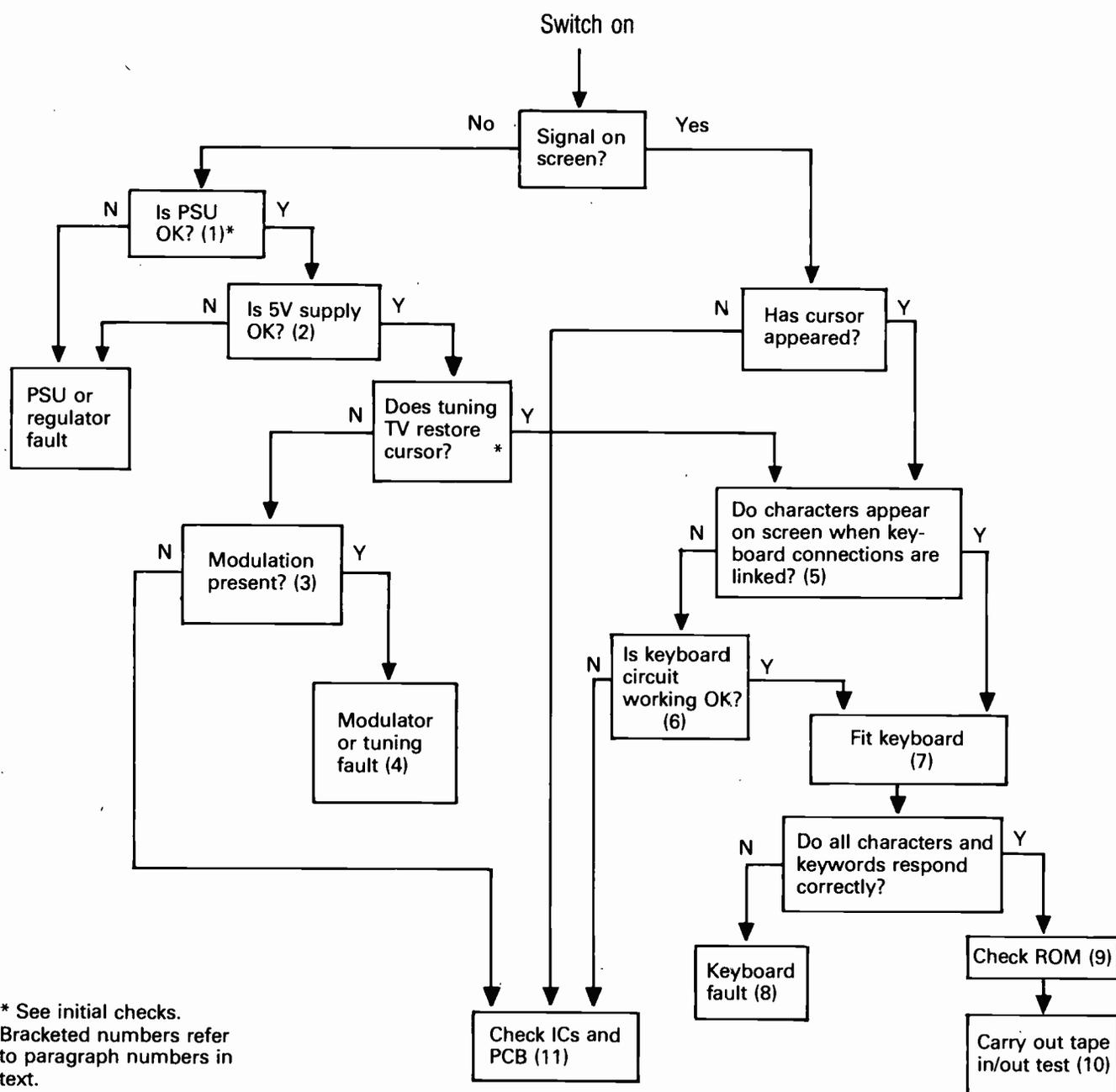

(1) The power supply should provide about 11V at 400mA on load. Less than 7V will be insufficient for the regulator to function correctly. An excessive current reading indicates a fault on the board.

(2) The regulator should deliver 5V to each of the i.c.s on the board. Its heatsink normally runs hot to the touch, but not unbearably so.

(3) The signal from pin 16 of the ULA chip to the modulator should give a 'PH' indication on the logic probe (see Table 2). An oscilloscope should display a signal of 2V peak amplitude from the peak to the bottom of the sync pulses. Inverse K will produce a very faint signal near the end of the field trace.

(4) If the modulation signal is present but the TV output is absent check the modulator's supply voltage and the tuning adjustment screw – this should be approximately 3mm down inside the former.

(5) If the cursor is present, connect one of the contacts of the small keyboard socket KB1 to a contact on the large socket KB2. Check whether a character or keyword appears on screen. Don't worry about shorting more than one connector in either of the sockets as this won't cause any damage to the computer – but it won't produce a display either as the software checks that only one key (apart from the shift key) is being pressed before it produces a screen display.

(6) Two faults that can affect the keyboard circuit are shorts between the lines or open-circuit lines or diodes. They can be identified by their effect on the system. Open-circuits affect only the keys they connect (see Fig. 1). A short effectively holds one key on, disabling the whole keyboard. Faults can occur anywhere in the circuit, from the address bus side to the diodes to the ULA chip's KBD pins. Check for shorts where the PCB tracks run obliquely under socket KB1. The resistance between these KBD tracks should be a few thousand ohms.

(7) The keyboard connection tails are very vulnerable, so to avoid unnecessary work make a thorough check that the computer is working satisfactorily before reconnecting the keyboard. Connect each contact on the small five-pin socket KB1 to at least two contacts on eight-pin socket KB2, checking the screen entries. Finally make sure that the tails are not splitting across (see following paragraph) and that the metallised contacts at the ends are in good condition. Then reconnect the keyboard by turning the case face down, front towards you, with the PCB laid component side up on the case so that the edge connector is at the front left: loop the tails over and push them carefully into the sockets, with a slight rocking movement. Don't push too hard or the plastic will buckle and split. When both tails have been fitted turn the PCB over on to its screw pillars and secure with two short screws.

(8) Often one bank or row of the keyboard fails to operate. This is usually due to cracks across the plastic tails severing one or more of the tracks. If the crack is near the end of the tail a clean square cut can sometimes be made, removing the fault. If not too short the tail can then be refitted. As mentioned above the end contacts of the tails should be checked to make sure that there's a good contact for the connectors. If the ends look a little dirty don't be tempted to apply a liquid solvent cleaner – some of these attack the plastic (they don't soften it, they completely disintegrate it!).

If a satisfactory repair proves to be impossible a new keyboard will have to be fitted. These are readily obtainable and are easy to fit to the case with the self-adhesive backing.

(9) Here's a simple ROM check to establish that all the

## A FEW WORDS TO ALL ELECTRONICS ENGINEERS IN SEARCH OF A NEW CAREER PATH TRAK TRAINING AT KALAMAZOO...

An intensive, full time 20 week course based at our Watford Training Centre, that gives people with a good practical electronics background the chance to break into a challenging new area of work. Computers... or, to be exact, micro-computer repair and maintenance – a field that's growing nationwide, which means excellent job opportunities. Funded by the MSC, the course is just one of TRAK's specialist computer training programmes, tailor-made to meet the needs of industry, commerce and government, for today and the future.

The course which commences shortly is free, and government sponsorship is available for successful candidates.

To qualify for a place you should be aged over 19, trained to TEC, C&G or equivalent level, and live within daily travelling distance of Watford.

Find out how re-training with TRAK can help your future career prospects by coming along to our informal **Open Day** at the TRAK TRAINING CENTRE (Former Lloyds Bank Building), Church Street, Off Watford High Street, Watford, on Monday 2nd June between 10am – 5pm.

If you can't make it, ring Kerry Gregson on 021-475 2191, ext. 2013.

**Kalamazoo**  
business systems

**trak**  
Training Towards  
Tomorrow

bytes of memory are being read correctly. Although it's unlikely that a ROM fault could continue to be present at this point in the test sequence without being detected the check will set your mind at rest. Enter and run the program below – it takes just over a minute to run. Check that the answer printed out is 855106. If the answer is 854885 the ROM is an early version. To prove this enter: PRINT SQR .25 (square root of a quarter). An answer of 1.359 instead of .5 proves that the ROM is an early type which has a few faults. Any other answer to the program indicates a ROM error. Here's the program:

```
10 FAST
20 LET L = 0
30 FOR N = 0 TO 8191
40 LET L = L + PEEK N
50 NEXT N
60 PRINT L
```

(10) At this stage it remains only to check the tape save/load operation and box up the computer. Put in a short program – the one above will do – and save it on tape. Switch off the machine to clear it, then restart and load the program. These operations are both described in Chapter 16 of the BASIC Programming Book supplied with the ZX81.

If the tape tests o.k. the case can be assembled, the four screws fitted and the rubber feet restuck in their sockets. (11) This is the stage you'll probably end up at if the computer has suffered major damage. You've proved that the fault lies in one or more of the chips or on the PCB.

First check whether the computer has been repaired previously. If you find evidence of modifications or soldering, check the board carefully for solder splashes, shorted

tracks etc. Where Sinclair Research fitted i.c. sockets originally I've found that they fitted them to all the i.c.s. So if you find a board that has sockets for some of the i.c.s treat it with suspicion – it's probably been modified.

I don't intend to tell you how to extract a suspect i.c. but let me tell you one of the pitfalls of the method I use in order to illustrate an elusive fault condition. I use a sucker on each pin of the i.c. and having removed most of the solder finally free each pin with a pair of pliers and if necessary the use of solderwick. This often leaves the odd pin still slightly secured in the hole: as the i.c. is carefully removed it's important to free any such pins before they lift and break the print. It's very easy to end up with a print crack on the top of the board and if undetected this crack will be covered when the socket is fitted. So if you have a particularly difficult fault, make sure that this hasn't happened. Check the signals at the i.c. pins and at the line end (the next component) to ensure track continuity.

### Checking the ICs

Next, i.c. checks. Table 2 lists the conditions at each pin of the i.c.s. The readings were taken using the Tandy Micronta logic probe featured in last November's issue of *Television*. The computer was at the inverse K cursor stage and the supply for the probe was taken from the 5V rail – I always fit a short wire with a small loop to the 5V plated-through hole near the regulator.

To simplify checking, the pins are listed in numerical order in Table 2 though quick checks at selected pins might speed up the testing. For example I always make an initial check on the 5V and chassis pins of all the i.c.s, then the reset line and memory request pins of the CPU and the cell select and read pins of the ROM and RAM chips. But this is only my own view of what are the more important checks or those most likely to lead to a fault indication. All the pin signals are listed, even those directly connected to the pins of other i.c.s, as this makes for easier checking. As mentioned earlier when describing the circuit some data and address lines incorporate buffer resistors between the i.c.s. These can be very useful as failure of an i.c. at one end of a resistor won't affect the i.c. at the other end, so you can establish with certainty which i.c. is faulty.

It's often easy to locate a fault or anomaly in the signals on the lines but very difficult to establish the reason. The unnecessary removal of a 40-pin i.c. is a non-profitable pastime to be avoided if possible. Other approaches can be adopted. One that has been with us since the earliest days of printed circuits is to cut the track. This is useful for tracing shorts, the computer equivalent of which is the loss of a logic signal. When deciding where to make the cut remember what was previously said about track cracks under sockets and try to avoid making any cut that would subsequently be covered by a socket. Another method of checking a suspect i.c. is to mount a good one on top piggy-back fashion: the legs should be sprung in and care taken to ensure that there's contact at all the pins of the suspect i.c. This doesn't always work but it's worth a try when you have two or three suspect soldered-in i.c.s. The method complements track cutting as it's particularly effective with open-circuit chips.

One last tip. When you suspect that ULA chip and don't have a spare – I usually suspect the item for which I don't have a replacement – remember that the TV screen will be bright if the ULA is all right, even if all the other

**Table 2: Signals on the i.c. pins.**

Pin	IC1 (ULA)	IC2 (ROM)	IC3 (CPU)	IC4a/b (RAM)
1	P	P	P	P
2	P	P	P	P
3	P	P	PL	P
4	P	P	P	P
5	P	P	P	P
6	P	P	P	P
7	PH	P	P	P
8	PH	P	P	P
9	P	P	P	L
10	P	P	P	P
11	P	P	H	P
12	P	L	P	P
13	P	P	P	P
14	P	P	P	P
15	PH	P	P	P
16	PH	P	P	P
17	P	P	PH	P
18	P	P	P	H
19	P	P	P	
20	L	P	PH	
21	P	P	P	
22	OC	P	PH	
23	P	P	H	
24	P	H	PH	
25	H		H	
26	P		H	
27	H		P	
28	P		P	
29	H		L	
30	P		P	
31	H		P	
32	P		P	
33	H		P	
34	L		P	
35	H		P	
36	P		P	
37	P		P	
38	P		P	
39	P		P	
40	H		P	

P = pulse, high and low LEDs lit.  
 PH = pulse and high LEDs lit.  
 PL = pulse and low LEDs lit.  
 H = high LED lit.  
 L = low LED lit.  
 OC = no LED lit (open-circuit).

chips are defective. So a bright screen without a cursor usually means that you should look elsewhere for the fault.

### Spares

The above paragraph reminds me that I mentioned in the introduction to this series last month that Sinclair spares are readily available. The supplier I use is PV Tubes, 104 Abbey Street, Accrington, Lancs BB5 1EE – 0254 36 521 or 0254 32 611. I find that when in a hurry a phone call quoting my Access card number will rush a spare to me – sometimes by the following morning. (Editorial note: the full address of CPC, mentioned in Roger Burchett's letter last month, is CPC Electronic Component Distributors, 194 North Road, Preston, Lancs – 0772 555 034).

This concludes the notes on servicing the ZX81. Next month we'll start on the Spectrum and Spectrum Plus.

# Service Bureau

*Requests for advice in dealing with servicing problems must be accompanied by a £1-50 cheque or postal order (made out to IPC Magazines Ltd.), the query coupon and a stamped addressed envelope. We can deal with only one query at a time. We regret that we cannot supply service sheets nor answer queries over the telephone.*

## SONY KV2704UB

There are vertical stripes right across the screen, darker on the left-hand side and more noticeable on a plain raster than a picture. There are also outlines to the left-hand side of verticals. These are more noticeable on faces and clothes. An outdoor aerial is in use, directly aligned with the transmitter.

For the striations we suggest you check the damping components in the line scan and EW modulator circuits – R828 (10Ω, 2W), R831 (2.2kΩ) and C834 (0.01μF). If these are in order suspect ripple on a supply line – the 250V supply reservoir capacitor C825 (22μF) is a strong possibility. Scope checks on the supply lines and at the c.r.t. electrodes should lead you in the right direction. If the ghosting effect is still present when the striations have been cleared, try the aerial with another set. If this gives ghost-free reception we would suspect the SAW filter SWF201.

## THORN 9000 CHASSIS

The problem with this set is mains fuse blowing. Replacing the Syclops transistor restores normal operation, but only for a few days or weeks.

The cause of this trouble is generally either latched sockets on the base and emitter pins of the Syclops transistor, dry-joints on the Syclops and/or line output transformer, or intermittent failure of diode W702 or W704 in the Syclops circuit. These things should all be checked, the diodes preferably by substitution.

## PANASONIC NV366

The front panel controls frequently lock up – the cassette cannot be removed and all functions except for the clock and programmer are inoperative. Switching off the power for a lengthy period of time restores normal operation until the next lock-up.

Assuming that the supply lines are all present and correct, it sounds as if the syscon microcomputer chip is coming unhinged. Check first that its 5V supply (pin 39) is present and correct, with no ripple/hash. If all is well here you could try a mains “conditioner” before condemning the chip itself (MN1405VKK). A conditioner is likely to help only if you live in an area with a noisy mains supply. You’ll most likely find one at the local computer shop – it goes between the VCR’s mains plug and socket.

## GRUNDIG 8610

The picture is bright and sharp but there’s a red background with red flyback lines. Interchanging the red and green drives changes the background to green with green

flyback lines. The effect is more noticeable with dark scenes and monochrome film.

Your R-G transposition check leaves little doubt that the problem lies on the RGB panel. Most often this inability to reach black level is due to a changed value component in the relevant R/G/B clamp/feedback circuit. R1916 (100kΩ) and R1918 (470kΩ) are the first suspects. R1902 (220kΩ) which with R1901 biases the base of the pnp transistor in the red output stage is also well worth checking. Make sure that the red drive control R1911 is in order, then if necessary check C1912 (4.7μF), C1914 (0.22μF) and the clamp pulse coupling capacitor C1917 (0.1μF).

## RANK T20 CHASSIS

The channel indicator is stuck on 0. All touch contacts seem to try channel selection but 0 remains.

We suggest you dismantle and thoroughly clean the touch contacts, the associated insulating surfaces and even the back of the touch pads. If the fault remains on reassembly it’s likely that the SAS580/590 chips are faulty – we generally replace them as a pair (take precautions against static charges when handling them).

## THORN 9600 CHASSIS

Occasionally the set functions perfectly. Usually however after switching on it starts up then shuts down. In the shut-down condition voltages are still present at all major points.

The most common cause of this fault is dry-joints on the PCBs. Check the pins of the chopper transformer T512 carefully, then the pins of the line output transformer T801. If necessary check the line drive connecting pins of plug/socket 810 and the jointing and condition of the 0.47Ω series resistor R510.

## SANYO CTP7118

The set has an appetite for e.h.t. triplers – a replacement lasts for only about six months. This happened again recently and an examination showed that the casing had burnt through from the inside, near the fixing lugs. R764, which is in series with the EW driver transistor, also needed replacement. This time the new tripler lasted for only half an hour however. The line output transistor, EW modulator diodes and small passive components in the line output stage all seem to be o.k. – we suspect the line output transformer. The h.t. is correct at 150V though excessive demand from the line output stage pulls this down to about 70V.

We would agree that the line output transformer T602 is probably faulty – we’ve had this happen with more than one of these sets. It’s likely however that a faulty tripler ruined the transformer rather than the reverse. There

## QUERY COUPON

Available until 18th June 1986.  
One coupon, plus a £1-50 (inc. VAT) cheque or postal order, must accompany EACH PROBLEM sent in accordance with the notice above.

TELEVISION JUNE 1986

should be no more trouble when both have been replaced, but make sure that terminals D and M on the tripler are wired correctly (incorrect connection of these is a common mistake).

# TEST CASE

## 282

*Each month we provide an interesting case of TV/video servicing to exercise your ingenuity. These are not trick questions but are based on actual practical faults.*

It's been a long and weary winter and on this spring day everyone in the workshop seemed to be out. Resident Workshop Sage (RWS) was gallivanting in Wales, RT (Real Technician) had taken a precious day's holiday to dig his garden while TS (Techno-Supersleuth) was out on the road fitting a teletext retrokit to a Sony TV set two villages away. The harassed Service Manager eyed the trainee with a beady eye: now was his chance to shine and put some of his college learning to practical use. Problem: his bench was equipped only for audio servicing. SM rigged up a portable 200W isolating transformer, then the mirror from the washroom, and supplied a conductive wristband – the latter a pointless if impressive gesture since there were unlikely to be any chips vulnerable to static in the motley collection of TVs in the waiting-repair queue.

The first of them was an ageing Pye colour set fitted with the 725 chassis. It was accused of intermittent low gain, the symptom being spasmodically snowy pictures. The trainee was in trouble from the moment he switched on! It took some time for the picture to appear, and when it did it was small and fluttering in size. Once tuned in the sound was present but was somewhat overwhelmed by a squeal from the area of the power supply circuitry on the right-hand panel. With these symptoms present the question of snowy pictures seemed somewhat irrelevant. Plainly the power supply department – a thyristor mains rectifier/regulator – was in pain. A circuit diagram was found and a brief study of the arrangements was made.

The trainee decided that a check on the 170V h.t. line at fuse F971 would be a good start, especially as it's so accessible at the centre of the baseboard. The voltage here was found to be low and varying – its average level seemed to be around 140V. The current passed by the fuse was less than 500mA, so the trainee rightly concluded that the problem was not due to any excessive loading on the line. His next move was to squirt all the components in the PSU with freezer. This made the picture contract a little more. A few minutes of poking and prodding in the PSU was terminated when the phone rang. It was TS! He knew all about Pye TVs! Could he suggest anything for

the small, fluttering picture on the Pye 725?

TS was full of suggestions. Kick off by backing down the overvoltage trip potentiometer; if the picture still flutters check the trigger diac's 8.2M $\Omega$  bias resistor R924; make sure that the feedback resistor R897 hasn't changed value; then suspect the diac (D892) and the thyristor (D888) said he. Magic thought the trainee as he walked back to his bench with a new spring in his step. Alas for pride! So much for experience! None of these things did any good at all. With a new BR100 trigger diac and BT116 thyristor, with the overvoltage trip transistor VT881 taken out of circuit, with replacement resistors in the R924 and R897 positions – and several others – the problem remained. The control transistor VT902 was changed, also its 7.5V reference zener diode, but the fault remained.

Further thought led to a careful check on the huge 3-3 $\Omega$  surge limiter resistor R978. It measured 3.21 $\Omega$ . A mighty muffler was procured and substituted for the h.t. reservoir and smoothing capacitors C880 and C877 in turn. It made little difference. An oscilloscope was brought into play and hooked to various points in the PSU, with confusing and inconclusive results. The main message provided by the waveforms was that the h.t. voltage was fluttering and that the conditions around the control transistor VT902 were also fluttering. The one crucial and revealing point in the power supply circuitry never saw the scope probe! What was it? Where did the fault lie? See next month!

### ANSWER TO TEST CASE 281

– page 452 last month –

The Hitachi VT33 VCR described last month was suffering from intermittent loss of drum servo lock, the effect being confined to the record mode. The fault condition was related to the white content of the off-air picture being received and recorded. The steps taken during the diagnostic procedure were logical and sensible – almost to the end! The cursory check of the video signal being received by IC202 on the Y/C board was inadequate. With a new i.c. fitted the symptoms remained the same. A more careful check was then made on the video waveform at the input to the Y/C panel. The field-rate display on the scope revealed that the video signal had a d.c. level that wandered wildly, with the field sync pulses on such a steep gradient that they fell across the same scope screen graticule as much of the video signal itself – the effect of poor l.f. response.

The same sorry waveform was present at the i.f./detector panel's video output, but not at the output from the video detector i.c. itself or at any of the three subsequent video amplifier transistors Q851/2/3. What had happened was that the video output coupling capacitor C859 (470 $\mu$ F, 6.3V) had dried up and gone low in value, knocking off the l.f. response.

The simple test to prove all this? The technician should have injected a baseband signal at the video input socket. This would have produced consistently good drum servo locking during record.

Published on approximately the 22nd of each month by IPC Magazines Limited, King's Reach Tower, Stamford Street, London SE1 9LS. Filmsetting by Trutape Setting Systems, 220-228 Northdown Road, Margate, Kent. Printed in England by the The Riverside Press Ltd., Thanet Way Whitstable, Kent. Sole Agents for Australia and New Zealand – Gordon and Gotch (A/sia) Ltd.; South Africa – Central News Agency Ltd. Subscriptions: Inland £14, overseas (surface mail) £17 per annum, payable to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex RH16 3DH. "Television" is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to currency exchange fluctuations and VAT, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever. ISSN 0032-647X.

# 3 WEEK FULL-TIME

# COURSES

HIGH PERCENTAGE OF PRACTICAL WORK  
INTENDED FOR QUALIFIED SERVICE ENGINEERS.

## VCR SERVICING

NEXT COURSE STARTS ON JUNE 30th – TUITION FEE £575

## MICROCOMPUTER SERVICING

NEXT COURSE STARTS ON JULY 21st – TUITION FEE £690

*(MSC grants available on JTS/ATS training schemes, subject to approval. If you are unemployed, or are currently employed and require retraining, or updating, you or your employer may be eligible for financial assistance under one of the above schemes.)*

Further details from:

### LONDON ELECTRONICS COLLEGE (VC Dept.)

20 Penywern Road, Earls Court, London SW5 9SU

Tel: 01-373 8721

## LOOK AHEAD!

WITH MONOLITH MAGNETIC TAPE HEADS

DOES YOUR VCR GIVE WASHED OUT NOISY PICTURES – ITS PROBABLY IN NEED OF A NEW HEAD – FAST FROM OUR EX-STOCK DELIVERIES. SAVE £££'s ON REPAIR CHARGES.

Our replacement video heads fit most models of VHS or Betamax VCR's. Following our replacement guide and with a practical ability, you can do the whole job in your own home with our head replacement kit.



VIDEO HEAD REPLACEMENT KIT



VMC-02 KIT ONLY £19.95 inc. VAT. + £2.50 p&p  
(Kit does not include video head)

TELEPHONE US NOW FOR INFORMATION OF THE REPLACEMENT HEAD FOR YOUR VIDEO RECORDER. **CATALOGUE:** For our full Catalogue of Replacement Video and Audio Cassette/Reel to Reel Heads, Motors, Mechanisms, etc. Please forward 50p p&p.

**THE MONOLITH ELECTRONICS CO. LTD.**  
5-7 Church Street, Crewkerne, Somerset TA18 7HR, England.  
Telephone: Crewkerne (0460) 74321 Telex: 46306 MONLTHG

## TV LINE OUTPUT TRANSFORMERS

FAST RETURN OF POST SERVICE

<b>RANK BUSH MURPHY</b> A816 solid state mono 9.00 CROWN 14CX25 15.00	<b>PHILIPS</b> 170 series dual std mono 8.00 210 300 series mono 8.00 G8 & G9 series colour 8.00
<b>DECCA</b> MS1700200120202401 mono 7.00 MS2404 2420 2424 mono 7.00 CS1730 1733 colour 9.00 CS1830 1835 colour 9.00 '30' series Bradford colour 9.00 80 series colour 8.00 100 series colour 8.00	<b>PYE 368, 169, 569, 769 mono 8.00</b> 725-741 colour 8.00 <b>SANYO 5101 &amp; 5103 10.00</b> <b>REDIFFUSION Doric Mk.3 10.00</b>
<b>FERGUSON HMV MARCONI</b> 1600 8.00	<b>WINDINGS</b> Autovox 2282 2693 8.00
<b>G.E.C.</b> 2047 to 2105 7.00 2000 to 2064 dual std mono 7.00 2147 single std 9.00	<b>RANK BUSH MURPHY</b> A640, A793, A774 overwind 6.00 T20a T22, T26 Pri & Sec 6.00 Z718 primary state 18" or 22" 6.00 Z718 EHT overwind 8.00 <b>SONY 1320UB overwind 15.00</b>
<b>Indesit 20EGB 24EGB mono 8.00</b>	<b>SOVEREIGN FARA</b> £15.00 14" colour overwind
<b>KB - ITT</b> VC200 VC205 VC207 mono 8.00 CVC5 CVC7 CVC8 CVC9 col. 9.00 CVC20 series colour 8.00 CVC30 CVC32 series colour 8.00 CVC45 8.00 FT100 FT110 state p/no. 10.00 TXV80 10.00	<b>ULTRA THORN</b> 1690-1691 EHT overwind 7.00 Waltham 190 EHT overwind 6.00
	<b>PRICES INCLUDE P.P. &amp; 15% VAT</b>

All lopts and windings are new and guaranteed

Open Mon.-Fri. 9 to 5.30 pm  
Delivery by return.

**PAPWORTH TRANSFORMERS**

80 Merton High Street,  
London SW19 1BE

**REWIND SERVICE**  
S.A.E. all enquiries  
Barclaycard and  
Access welcome



For orders placed at the post office  
**Trans cash**  
506 4856

01-540 3955



## **HITACHI VHS COLOUR CAMERAS**

**Mains Only Tested/  
Working**

### **VHS VIDEOS**

#### **FERGUSON**

**3V00, 3V22, 3V23, 3V16, 3V29,  
3V30, 3V31, 3V32, 3V35**

**NATIONAL PANASONIC  
NV8600, 8610, 2000, 7000,  
370, 333, 2010**

#### **SHARP**

**620, 630, 640, 2300 H T/P**

### **BETAMAX**

**SANYO VTC 9300, 5000, 5300**

**SONY C5, C6, C7, C9  
and SL F1UB T/P**

**Also Bush, Toshiba, Hitachi and Blau Punkt**

### **PLUS**

**17" 18" 20" 22" 26" Hybrid/  
Solid State CTVs**

**Remote Control & Teletext**

**Discount for Quantities**

**Complete loads delivered from pick up point**

**JOHN CARTER  
(Electrical) LTD  
FURNACE ROAD,  
GALLOWS INN,  
ILKESTON**

**Phone: 0602 303124**

## **CINEMA VISION PROJECTION UNITS**

★ ★ ★ ★

Philips, Grundig,  
Toshiba, National  
Panasonic and ITT. 40",  
45" and 78" screens.  
Floor and suspended  
models. New boxed and  
used. Quantity of test  
equipment.

Oscilloscopes, cross  
hatch – pattern – colour  
match – colour bar –  
and signal generators.  
Avo and Taylor test  
meters. Televerters slot  
meters.

### **RADIO TELEPHONE SYSTEMS**

★ ★ ★ ★

**John Carter (Electrical) Ltd.,  
Furnace Road,  
Gallows Inn,  
Ilkeston,  
Derbyshire.  
Phone 0602 303124**

# UNTESTED EX-RENTAL CTVs OVER 1500 WEEKLY

WITH THIS QUANTITY WE DO NOT  
HAVE TIME TO PLAY ABOUT.

**NO BUMPED TUBES**

**BEST SOURCE IN U.K.**

**COLOUR TVs FROM £3**

**VIDEO RECORDERS  
FROM £60**

TANDBURG S/S CTVs  
DUAL TUNERS IDEAL FOR  
EXPORT

VIDEO RECORDERS FROM £50:  
SONY C5: C6: C7 & C9  
PANASONIC : SHARP  
FERGUSON : GRUNDIG ETC.

CALL & SEE OUR SELECTION  
DELIVERY ARRANGED FOR  
BULK PURCHASES  
LOAD DIRECT FROM SOURCE  
AT VERY KEEN PRICES

**22"/26" TELETEXT VIEWDATA  
COLOUR IN STOCK NOW**

**CASH ONLY**

**FRANK FORD**  
(TV TRADE DISPOSALS)  
SCHOOL LANE  
GUIDE  
BLACKBURN, LANCS  
TEL: 0254 64489

## ★★ CHANGE OF ADDRESS ★★

ALL ORDERS SHOULD NOW BE SENT TO OUR NEW ADDRESS SHOWN BELOW

### TOP 50 VIDEO SPARES

CASSETTE LAMP (FERG/JVC) .....	£1.80	PINCH ROLLER (SANYO) .....	£7.95
CASSETTE LAMP (PANASONIC) .....	£1.80	PINCH ROLLER (SONY C5/C7) .....	£5.95
CASSETTE LAMP (SHARP, 9300 ETC) .....	£2.15	VIDEO HEAD DRUM (FERG) .....	£37.50
BELT KIT SONY (STATE MODEL) .....	£6.50	VIDEO HEAD DRUM (PANASONIC) .....	£39.50
BELT KIT FERGUSON (STATE MODEL) .....	£6.50	VIDEO HEAD DRUM (PAN NV366) .....	£56.95
BELT KIT SHARP (STATE MODEL) .....	£6.50	VIDEO HEAD DRUM (HITACHI) .....	£39.95
BELT KIT PANASONIC (STATE MODEL) .....	£6.50	VIDEO HEAD DISC (SONY C5/C6/C7) .....	£39.50
BELT KIT SANYO (9300, 5300, 5400) .....	£6.50	VIDEO HEAD DISC (SONY SL8000) .....	£44.50
BELT KIT SANYO (5000) .....	£1.99	VIDEO HEAD DISC (SANYO) .....	£49.50
BELT KIT HITACHI (STATE MODEL) .....	£6.50	VIDEO HEAD (SHARP 7300, 7700) .....	£51.58
REWIND KIT SONY C5/C7 .....	£6.95	VIDEO HEAD (SHARP 9300, 381 ETC) .....	£49.90
REWIND KIT SONY C6 .....	£6.95	VIDEO HEAD (TOSHIBA 9600) .....	£49.95
REEL IDLER (SHARP, 9300, 381, ETC) .....	£3.90	VIDEO HEAD (TOSHIBA 8600) .....	£54.60
FF/REW IDLER (HITACHI VT-11, ETC) .....	£5.50	REEL DRIVE PULLEY (SANYO 5000) .....	£8.88
FF/REW IDLER (HITACHI VT8000) .....	£4.72	REEL MOTOR (SANYO 5000 ETC) .....	£14.20
FF/REW IDLER (HITACHI VT9300) .....	£4.75	REEL MOTOR (SHARP 9300, 381, ETC) .....	£15.30
REEL IDLER (FERG, 3V29/30) .....	£3.45	CAPSTAN MOTOR (SONY C5/C7) .....	£39.95
PLAY IDLER (HITACHI 9300) .....	£6.50	A.C.E. HEAD (SONY C5/C7) .....	£26.45
FF/REW IDLER (NAT/PAN NV370) .....	£4.50	CAPSTAN MOTOR FERG/JVC 3V22 ETC .....	£36.45
REEL IDLER (NAT/PAN) STATE MODEL .....	£3.45	DRUM MOTOR FERG/JVC 3V22 ETC) .....	£36.60
PLAY IDLER (NAT/PAN) STATE MODEL .....	£4.72	TAKE-UP CLUTCH (FERG/JVC) .....	£6.95
PLAY CLUTCH (PAN NV7000) .....	£5.50	CLUTCH ASSY (FERG 3V29/30) .....	£4.50
PINCH ROLLER (FERG) .....	£5.95	AUDIO RELAY (SONY C5/C7) .....	£3.95
PINCH ROLLER (SHARP) .....	£7.90	HEAD CLEANING STICKS .....	£0.50
PINCH ROLLER (PANASONIC) .....	£5.95	HEAD CLEANING FLUID .....	£1.50

MOST SPARES AVAILABLE FOR HITACHI, PANASONIC, SONY, SANYO, SHARP ETC.  
RING FOR AVAILABILITY.

### TELEVIDEO SERVICES

NOTTINGHAM (0602) 226070  
145 STATION RD, BEESTON, NOTTINGHAM.

Please add 50p post & packing and then add 15% VAT to the total.

ALL STOCK ITEMS ARE DESPATCHED BY RETURN OF POST

Send 17p stamp for full list

## CREWE WHOLESALE TV

77 COLERIDGE WAY, CREWE  
Tel: 0270 582924

**G11s** working..... **£50**

**GEC** ..... from **£11**

Delivered in Bulk

**BUSH T20 T22 and 24s**

**ITT CVC 20 Upwards**

**Series 3 DORIC**

working ..... from **£40**

**Remote + Text Available**

**Large range of**

**THORN from 8800 upwards.**

**Price and availability on request**

**CASH ONLY UNLESS BY  
PRIOR ARRANGEMENT**

**ALL PRICES + 15% VAT**

AN1270	£1.75	CX143A	£7.50	HA11788	£4.50	M54543L	£2.75	TA1736P	£1.00	UPC1028H	£0.90	2SAB99	£0.75	2SC1427	£0.30
AN203	£2.20	CX157	£3.95	HA11816NT	£6.50	M54548L	£6.75	TA1737P	£0.80	UPC1031H	£1.80	2SA940	£0.80	2SC1505	£0.70
AN210	£1.75	CX158	£3.50	HA11828NT	£9.50	MB3705	£1.60	TA1739P	£1.50	UPC1032H	£1.50	2SA952	£0.35	2SC1546	£0.30
AN211A	£2.25	CX160	£2.50	HA112035	£9.50	MB3712	£1.50	TA1745P	£1.80	UPC1035C	£1.20	2SA1015	£0.30	2SC1664	£2.50
AN2140	£1.80	CX161A	£2.50	HA12413	£2.50	MB3730	£1.75	TA1746P	£2.50	UPC1037H	£1.20	2SA1102	£1.90	2SC1662	£0.30
AN217B	£2.20	CX162	£2.40	HA13402	£1.50	MB3731	£2.50	TA1750P	£1.80	UPC1043C	£1.20	2SA1103	£1.90	2SC1741	£0.30
AN225W	£2.75	CX170	£5.50	HA13403	£3.50	MB3731	£2.50	TA1752P	£1.70	UPC1158H	£1.70	2SA1104	£1.90	2SC1815	£0.25
AN236	£2.50	CX181	£3.50	HA13430A	£3.50	MB3756	£2.00	TA1773P	£1.60	UPC1158H	£1.60	2SA1105	£2.25	2SC1826	£0.60
AN2390	£3.80	HA1124A	£2.75	HA11111P	£0.80	MB8719	£3.50	TA1776P	£1.50	UPC1161C	£0.75	2SA1106	£2.50	2SC1849	£0.30
AN240P	£1.50	HA1125	£1.50	LA1201	£0.85	PLL01A	£2.30	TA1793P	£3.50	UPC1163H	£0.60	2SA1198	£0.35	2SC1945	£0.50
AN241P	£1.50	HA1127	£1.75	LA1222	£0.80	PLL03A	£4.95	TA17200	£2.00	UPC1167C	£0.90	2SB22	£0.40	2SC1946A	£0.50
AN247P	£1.50	HA1130	£1.50	LA1230	£1.50	SH-1125H	£7.50	TA17201	£2.00	UPC1168C	£1.40	2SB25	£0.70	2SC1957	£0.30
AN259	£2.75	HA1151	£1.40	LA1232	£1.50	SK013	£3.75	TA17202P	£2.00	UPC1170H	£1.40	2SB311V	£0.80	2SC1969	£1.30
AN262	£1.50	HA1156	£1.10	LA1230	£1.50	SK013	£3.75	TA17203P	£1.80	UPC1171C	£1.20	2SB45	£2.60	2SC2021	£0.60
AN271A	£2.50	HA1166	£1.60	LA1365	£1.20	SK1014	£3.25	TA17204P	£1.10	UPC1177C	£1.20	2SB45	£2.60	2SC2026	£0.60
AN274	£2.50	HA1196	£3.75	LA1368	£2.20	SK1015	£5.00	TA17205AP	£1.00	UPC1177H	£1.00	2SB45	£2.60	2SC2075	£0.25
AN295	£3.25	HA1197	£1.50	LA1460	£1.95	SK1016	£4.75	TA17207P	£1.50	UPC1178C	£1.00	2SB426	£1.00	2SC2078	£0.75
AN303	£2.50	HA1199	£1.60	LA2200	£1.75	SK1020	£4.50	TA17208P	£1.50	UPC1180C	£1.40	2SB426	£1.00	2SC2091	£1.70
AN313U	£2.75	HA1306W	£1.60	LA3101	£1.60	SK1022	£5.25	TA17214P	£2.50	UPC1182H	£1.00	2SB426	£1.00	2SC2092	£0.60
AN315	£2.00	HA1319	£2.00	LA3155	£0.95	SK1022	£5.25	TA17215P	£1.80	UPC1185H	£2.20	2SB536	£0.95	2SC2098	£0.95
AN316	£3.50	HA1322C	£1.60	LA3160	£0.90	SK1025	£6.75	TA17215P	£1.80	UPC1185H	£2.20	2SB536	£0.95	2SC2166	£0.95
AN318	£4.75	HA1339A	£1.60	LA3201	£0.95	SK1041	£6.50	TA17217AP	£1.20	UPC1186	£0.80	2SB536	£0.95	2SC2238	£0.65
AN331	£2.75	HA1342A	£1.70	LA3300	£1.40	SK1077	£3.95	TA17220P	£1.75	UPC1187V	£1.30	2SB536	£0.95	2SC2278	£0.20
AN360	£1.20	HA1366W	£1.50	LA3301	£1.20	SK1078	£3.95	TA17222AP	£1.20	UPC1190C	£0.95	2SB536	£0.95	2SC2335	£1.50
AN362L	£1.50	HA1366WR	£1.50	LA3350	£1.20	SK1080	£7.20	TA17223P	£1.95	UPC1191H	£0.95	2SB536	£0.95	2SC2365	£2.25
AN366P	£1.50	HA1367	£2.25	LA3361	£1.20	SK1082	£9.25	TA17225P	£2.50	UPC1198H	£0.70	2SB754	£2.50	2SC2540	£12.75
AN610P	£1.75	HA1368	£1.60	LA4030P	£2.00	SK1086	£9.25	TA17225P	£2.50	UPC1215V	£1.25	2SB7720	£0.90	2SC2570	£0.70
AN612	£1.75	HA1368R	£1.65	LA4031P	£1.40	SK1430	£4.75	TA17226P	£2.20	UPC1216V	£0.95	2SC373	£0.30	2SC2577	£1.90
AN5722	£1.50	HA1370	£2.75	LA4032P	£1.40	SK1433	£4.50	TA17227P	£1.50	UPC1217G	£1.60	2SC373	£0.30	2SC2578	£2.20
AN5730	£1.85	HA1374	£2.20	LA4051P	£1.50	SK1435	£5.00	TA17229P	£3.00	UPC1217G	£1.60	2SC373	£0.30	2SC2578	£2.20
AN5732	£1.85	HA1377A	£2.20	LA4100	£1.00	SK1436	£5.00	TA17230P	£2.75	UPC1218H	£1.30	2SC373	£0.30	2SC2578	£2.20
AN5753	£1.95	HA1388	£2.35	LA4101	£1.00	SK1437	£5.00	TA17232P	£2.75	UPC1218H	£1.30	2SC373	£0.30	2SC2578	£2.20
AN6250	£2.75	HA1389	£1.75	LA4102	£1.00	SK1439	£5.50	TA17310P	£1.40	UPC1222C	£0.90	2SC451	£0.70	2SC2584	£2.20
AN6344	£4.30	HA1389R	£1.40	LA4110	£1.40	SK1441	£6.00	TA17312P	£1.30	UPC1223C	£1.75	2SC451	£0.70	2SC2584	£2.20
AN7105	£2.20	HA1392	£2.30	LA4112	£2.30	SK1443	£6.95	TA17313AP	£1.75	UPC1225H	£1.60	2SC451	£0.70	2SC2584	£2.20
AN7110	£4.00	HA1394	£2.75	LA4120	£2.50	SK1457	£5.50	TA17315AP	£1.75	UPC1229C	£1.25	2SC451	£0.70	2SC2584	£2.20
AN7114E	£1.60	HA1397	£2.50	LA4125	£2.00	SK1459	£5.75	TA17325P	£0.85	UPC1229C	£1.25	2SC451	£0.70	2SC2584	£2.20
AN7115E	£1.60	HA1398	£2.35	LA4140	£2.00	SK1460	£5.75	TA17328	£1.60	UPC1229C	£1.25	2SC451	£0.70	2SC2584	£2.20
AN7120	£1.40	HA1457W	£2.00	LA4182	£2.00	SK1461	£5.50	TA17307AP	£2.75	UPC1227V	£0.95	2SC451	£0.70	2SC2584	£2.20
AN7130	£1.50	HA11215A	£4.25	LA4192	£1.95	SK1463	£7.40	TA17308	£3.30	UPC1230H	£2.50	2SC451	£0.70	2SC2584	£2.20
AN7145M	£1.80	HA11221	£2.20	LA4200	£1.50	SK1465	£8.50	TA17309P	£2.30	UPC1238V	£0.85	2SC451	£0.70	2SC2584	£2.20
AN7146M	£1.85	HA11223W	£3.80	LA4220	£1.20	SK10025	£4.95	TA17511	£2.75	UPC1245V	£1.00	2SC451	£0.70	2SC2584	£2.20
AN7154	£1.75	HA11225	£1.95	LA4230	£1.75	SK10029	£4.35	TA17588P	£1.50	UPC1277H	£2.75	2SC451	£0.70	2SC2584	£2.20
AN7156H	£2.40	HA11226	£2.00	LA4400	£1.90	SK10039	£4.25	UHC0001	£4.80	UPC1278H	£2.50	2SC451	£0.70	2SC2584	£2.20
AN7158N	£2.25	HA11423	£4.75	LA4420	£1.40	SK10040	£5.50	UHC0004	£4.80	UPC1350C	£1.20	2SC451	£0.70	2SC2584	£2.20
AN7168	£1.50	HA11701	£4.50	LA4422	£1.20	SK10049	£5.75	UPC016C	£2.50	UPC1356C	£1.50	2SC451	£0.70	2SC2584	£2.20
AN7310	£0.80	HA11702	£4.90	LA4430	£1.30	SK10059	£6.00	UPC20C	£2.20	UPC1356C	£1.50	2SC451	£0.70	2SC2584	£2.20
AN7311	£1.00	HA11703	£4.50	LA4440	£2.20	SK10080	£6.50	UPC30C	£2.00	UPC1358H	£1.80	2SC451	£0.70	2SC2584	£2.20
BA301	£0.75	HA11704	£4.75	LA4460	£1.75	SK10028	£6.50	UPC41C	£2.00	UPC1360C	£1.60	2SC451	£0.70	2SC2584	£2.20
BA311	£0.95	HA11705	£6.50	LA4461	£1.75	SK10209	£6.75	UPC554C	£1.25	UPC1363C	£1.95	2SC451	£0.70	2SC2584	£2.20
BA313	£0.75	HA11706	£6.50	LA4500	£2.00	SK10230	£6.90	UPC555	£0.60	UPC1366C	£1.50	2SC451	£0.70	2SC2584	£2.20
BA318	£0.70	HA11710	£5.50	LA4505	£2.50	SK10240	£6.75	UPC561C	£0.60	UPC1366C	£1.50	2SC451	£0.70	2SC2584	£2.20
BA402	£1.30	HA11711	£9.50	LA6458	£0.90	SK13042	£6.50	UPC566H	£0.60	UPC1367C	£2.00	2SC451	£0.70	2SC2584	£2.20
BA511A	£1.80	HA11713	£6.00	LA7300	£1.95	SK15211	£6.75	UPC571	£1.95	UPC1368H	£1.75	2SC451	£0.70	2SC2584	£2.20
BA514	£1.75	HA11714	£5.75	LA7306	£2.20	SK15421	£6.50	UPC573C	£2.20	UPC1370C	£1.95	2SC451	£0.70	2SC2584	£2.20
BA521	£1.75	HA11715	£6.25	LC7120	£3.50	SK15451	£6.75	UPC574J	£0.35	UPC1373H	£0.95	2SC451	£0.70	2SC2584	£2.20
BA527	£1.50	HA11716	£6.25	LC7130	£3.50	SK15720	£6.80	UPC579H	£1.00	UPC1378H	£0.95	2SC451	£0.70	2SC2584	£2.20
BA532	£1.50	HA11717	£6.00	LC7131	£3.75	SK15730	£6.75	UPC579H	£1.00	UPC1382C	£1.75	2SC451	£0.70	2SC2584	£2.20
BA536	£2.25	HA11718	£4.75	LC7136	£2.75	TA17050P	£0.80	UPC577	£0.80	UPC1384C	£2.50	2SC451	£0.70	2SC2584	£2.20
BA612	£1.80	HA11724	£18.25	LC7137	£2.75	TA17051P	£0.80	UPC580	£2.75	UPC1458C	£0.90	2SC451	£0.70	2SC2584	£2.20
BA1310	£1.75	HA11725	£16.00	M5106P	£2.25	TA17054	£1.70	UPC585C	£0.95	UPD277	£4.50	2SC451	£0.70	2SC2584	£2.20
BA1320	£1.25	HA11726	£15.00	M5115P	£3.50	TA17063	£0.80	UPC592	£0.95	2SA103	£0.60	2SC451	£0.70	2SC2584	£2.20
BA1330	£1.75	HA11727	£9.50	M5134P	£2.75	TA17066	£1.50	UPC596C	£1.70	2SA350	£0.35	2SC451	£0.70	2SC2584	£2.20
BA604	£2.20	HA11736	£16.00	M5155P	£2.90	TA17070P	£1.40	UPC598	£2.00	2SA495	£0.30	2SC451	£0.70	2SC2584	£2.20
CX0642	£5.50	HA11745	£9.00	M5155	£2.25	TA17073	£2.25	UPC1001H	£2.25	2SA539	£0.30	2SC451	£0.70	2SC2584	£2.20
CX0658	£2.50	HA11747	£9.50	M51513L	£1.95	TA17074P	£1.95	UPC1009C	£1.20	2SA562	£0.30	2SC451	£0.70	2SC2584	£2.20
CX0758	£2.20	HA11747ANT	£9.50	M51514AL	£1.75	TA17104P	£1.35	UPC1017G	£1.35	2SA634	£0.30	2SC451	£0.70	2SC2584	£2.20
CX095C	£2.80	HA11749	£4.50	M51515BL	£2.50	TA17108	£1.50	UPC1018C	£0.95	2SA643	£0.35	2SC451	£0.70	2SC2584	£2.20
CX100D	£1.50	HA11750	£5.00	M51516L	£2.50	TA17109	£2.30	UPC1020	£1.75	2SA673	£0.35	2SC451	£0.70	2SC2584	£2.20
CX101G	£1.50	HA11753NT	£3.50	M51517L	£2.50	TA17119	£1.75	UPC1023H	£2.30	2SA684	£0.60	2SC451	£0.70	2SC2584	£2.20
CX130	£4.50	HA11758NT	£3.50	M51518L	£1.75	TA17120P	£1.75	UPC1024H	£3.00	2SA699A	£2.30	2SC451	£0.70	2SC2584	£2.20
CX136	£5.50	HA11768	£4.50	M51521AL	£1.75	TA17123P	£1.00	UPC1026C	£1.00	2SA762	£1.95	2SC451	£0.70	2SC2584	£2.20

## T. POWELL

**16 PADDINGTON GREEN,  
LONDON W2 1LG**

# BOLTEN LTD.

45/46 London House,  
271, King Street, London W6 9LZ.  
Tel: 01-748 4137 (2 lines)  
Telex: 262421 BOLTEN G

## Video Heads

Sony C5/C7/T7 .....	£31.95
Ferguson/JVC (Universal) .....	£30.95
National Panasonic (Universal) .....	£30.95
National Panasonic (370/380) .....	£33.95
Hitachi .....	£33.95
Sanyo .....	£44.95
Fisher VHS Genuine .....	£51.95
Akai (most Models) .....	£30.95
Sharp .....	£44.95

Heads suitable for many other Brands also available.  
Please call for full list.

Belt Kits (Most Models) .....	£3.99
Remote Controls for T.V.	
Grundig/Philips .....	£16.95
Video Cable Kit	
(any model to any model) .....	£7.50
Pinch Wheels (Various Models) .....	£5.95

Please add 15% VAT plus £1.00 p&p per order.

Delivery within 7-14 days  
subject to availability



# SPRING SPECIALS

10 BUSH 2 CHIP	£50
10 BUSH T20	£250
10 REDIFFUSION MARK 3	£250
10 REDIFFUSION MARK 1	
REVAMP	£120
10 THORN 8000 17"	£150

## LARGE QUANTITIES OF BETA VIDEOS

RING FOR SPECIAL PRICES

ALL + VAT

# TELETRADERS

Forde Road, Brunel Industrial Estate,  
Newton Abbot, Devon  
Telephone: (0626) 60154  
THE NO. 1 WHOLESALE IN THE SOUTH

## IRISH T.V. DEALERS

(PLEASE NOTICE)

LARGE SELECTION OF RECONDITIONED PRECISION-IN-LINE UHF-VHF COLOUR TVs,  
SOME WITH RE-GUN TUBES FITTED, "CABINETS RESTORED TO A1 CONDITION".  
PRICES START @ £60.00 VAT INCLUDED. ALSO 20" & 22" RE-GUN TUBES IN STOCK,  
QUANTITY DISCOUNT, DELIVERY ARRANGED. VIDEO HEADS ALSO IN STOCK.

(EXPORT SPECIALISTS)

T.V. TRADE SALES  
E.D.I. HOUSE  
KYLEMORE PK. WEST  
DUBLIN 10.

ALSO

T.V.T.S.  
CLOVER PLACE  
COLLEGE ST.  
KILLARNEY.

Tel: 0001-264139 (Local calls 01-)

Tel: 064-33655

## THE FULL THORN RANGE

now available from

## SOUTHPARK DISTRIBUTORS

Unit 4 Rubastic Road,  
Southall, Middlesex  
01 574 4631 EXT 28

9K-9K6-TX9-TX10 TEXT &  
FULL REMOTE ALSO VIDEOS  
V.H.S. & BETA. LOTS OF  
WORKERS FOR BUSY DEALERS

## TUNERS + TUNERS

- ★ If you repair sets regularly – phone us today and we will dispatch immediately – no need to send cash 'up front'.
- ★ All tuners dispatched by first class post for receipt by you the next day.
- ★ All popular tuners/tuner repairs supplied 'off the shelf'.
- ★ Unusual types repaired same day as received (subject to spares availability).

**TELEPART**

32 Temple Street,  
Wolverhampton WV2 4LJ.  
Phone: (0902) 29022.

**PHILEX**

Replacement  
VHS & BETA  
Video Components

- ALIGNMENT TAPES
- VIDEO HEADS
- PINCH WHEELS
- DRIVE MOTORS
- CLUTCH ASSY.
- BELTS

**NEW MODEL!**  
**SHARP UNIVERSAL for -**

HE02-HE05-HE04-HE00  
9700-9300-9500-9600

**DISTRIBUTORS**

- A... ELECTRONICS - London
- CCS (MASTERCARE) LTD - High Wycombe
- CFC LTD - Preston
- CCOPERS - Dublin
- CCOMPONENT BUREAU - Cambridge
- CHARLES HYDE & SONS LTD - York
- DOUBLE 'D' DISTRIBUTORS - Poole
- HFS ELECTRICAL CO LTD - Birmingham
- JF SPECIALISTS - Middlesbrough
- KL ROY BROS. - Dublin
- MONOLITH ELECTRICAL CO LTD - Somerset
- NORTHERN IRELAND ELECTRONICS - Belfast
- PV TUBES - Accrington
- NORMAN ROSE - London
- PACT - Peterborough
- RADIO SUPPLIES - Hartlepool
- SEME - Melton Mowbray
- TAIT COMPONENTS - Glasgow
- WILLOWVALE ELECTRICAL LTD - Reading
- WZARD - Manchester
- McLELLAND - Leeds

**NEW VIDEO RANGE**

**3HSS-(V) UNIVERSAL TYPE**

- JVC-AKAI-FERGUSON-SABA
- TELEFUNKEN-THOMSON
- BRANDT-ELECTRONIQUE
- GRAETS-NORDEMNDE
- CONTINENTAL-EDISON
- PATHE-MARCONI

**3HSS-(H) UNIVERSAL TYPE**

- NATIONAL-PANASONIC

**3HSS-UI-(H) TYPE**

- NAT.-PAN-NV370-NV28C

**3HSS-3-(H) TYPE**

- NAT.-PAN-NV330-NV77

**PS-38-(S) TYPE**

- SONY-VEGA-TOSHIBA-NEC

**HITACHI**

- H1V1-8000-9300-9500
- VT33-V711

**ORIGINAL**

**SANYO FISCHER**

- 9350-5000-5350-6500
- 9300-9455-9500

**SHARP TYPE**

- HE02-HE05-HE04-HE00
- 9700-9300-9500-9600 AND OTHERS

**PHILEX 01 631 0985**

# HOCKLEY DISCOUNT TELEVISIONS

We give "The Best Deals" that's why we have the cleanest reputation in the trade!!!

Prices start From **£6.00** Working sets From **£12.00**

OR

Lorry loads delivered from **SOURCE**

We have huge stocks of TV's + V.H.S. Videos to offer, including:-

- Philips G8's, G11's ..... Thorn 8000, TX9,
- Pye Solid State ..... 9000, 9600, TX10,
- Pye Chelsea ..... Latest Hitachi
- G.E.C. Solid State ..... I.T.T. CVC30, CVC45,
- Rediffusion MkI, MkIII ..... Bush T20, T22

**ALSO**

**VIDEO + T.V. STANDS AVAILABLE!**

**DON'T HESITATE TO CONTACT US BECAUSE YOU WILL NEVER LOOSE!!**

**MIDLANDS BRANCH:-**

Hockley Discount Televisions,

94 Soho Hill, Hockley, Birmingham B19 1AE.

021-551-2233 - Ask for Jazz



**NORTH-EAST BRANCH:-**

Northern TV Distributors, Unit 2, Pert Court,

11th Ave, Team Valley,

Gateshead, Tyne & Wear.

091-487-5389 - Ask for Joe



## TVS TRADE SERVICES BROMSGROVE

Large selection of quality clean TV & Video always in stock, including:

BUSH T20/24 DECCA 80/100

GEC STARLINE

HITACHI ITT (full remote)

PHILIPS G8

PHILIPS G11 PHILIPS KT3

THORN 9600 including TELETXT

THORN 8800 THORN 9000

(remote) (remote)

THORN TX

**VHS VIDEO from £85 (working)**

We specialise in working sets, fully serviced and ready to deliver to your customer's home. Spares back up service available to customers. You've seen the junk, so why not now come and pay us a visit - we think you will be pleasantly surprised by our prices and the quality of our equipment. Delivery service available.

**STOP PRESS**

Electronic Video including Ferguson 3V29/30, Amstrad 7000, Sharp 9300, now in stock at unbeatable prices. We also specialise in direct loads delivered to your door direct from source.

For further details phone:

**COLIN BROOMFIELD,**

**UNIT 7, STATION STREET,**

**BROMSGROVE, WORCS.**

**(0527) 37037/71186**



**OSCILLOSCOPES**  
 COSSOR CDU150. Dual Trace 35MHz Solid State. Portable 8x10cm display. With Manual ..... £200  
 TELEQUIPMENT D61 Dual Trace 10MHz With Manual ..... £150  
 ADVANCE OS250TV. Dual Trace 10MHz With Manual ..... £160  
 S.E. LABS SM111. Dual Trace 18MHz Solid State. Portable AC or External DC operation 8x10cm display. With Manual ..... £150  
 TELEQUIPMENT D43. Dual Trace 15MHz. With Manual ..... £100  
 TELEQUIPMENT S54A. Single Trace 10MHz. Solid State. With Manual ..... £110  
 TELEQUIPMENT S43 Single Trace 25MHz With Manual ..... £75

**PHILIPS DIGITAL MULTIMETERS**  
 4 digit, auto ranging. Complete with batteries and leads (p&p £5)  
 TYPE PM2517X (LCD) ..... £75

**MULTIMETERS**  
 AVO 9 Mk4 (Identical to AVO 8 Mk4 but scaled differently) Complete with Batteries & Leads ..... £55  
 AVO 8 Mk2 Complete with Batteries & Leads £45  
 Above items in GOOD WORKING ORDER - appearance not A1 hence the price.  
 AVO TEST SET No 1 (Military version of AVO 8) Complete with batteries, leads & Carrying Case ..... £65  
 AVO Model 7x. Complete with batteries, leads & carrying case ..... £40  
 AVO Model 73. Pocket Multimeter (Analogue) 30 ranges. Complete with batteries & leads ..... £18  
 AVO 72 - Similar to above but no AC current range. With batteries & leads ..... £10

**AVO TRANSISTOR TESTER TT169**  
 Handled. GO/NO GO for In-situ Testing. Complete with batteries, leads & instructions. (p&p £3) NOW ONLY £12

**PROFESSIONAL 9" GREEN SCREEN MONITORS**  
 made by KGM for REUTERS Gives quality 80 column x 24 line display. Composite video in. Cased. Good condition ..... ONLY £32 each  
**DISK DRIVE PSU 240V 1A; 5V 1.6A & 12V 1.5A**  
 Un-used. Only £10.00 each (P&P £2)  
 Qwerty keyboard (as in Lynx Micro). Push to make. Cased ..... £5 each (P&P £2)  
 Various 5 1/4" Floppy Disk Drives and Stepping Motors Available.

**LABGEAR COLOURMATCH PATTERN GENERATOR**  
 Type CM6038-DB Crosshatch/Grey Scale/Blank Raster. Mains or Battery ..... ONLY £12 each (P&P £2)

**ADVANCE AM/FM SIGNAL GENERATOR Type SG63A**  
 7.5-230MHz ..... £75  
**ADVANCE AM SIGNAL GENERATOR SG62B.** 150 KHz-220MHz ..... £45  
**ADVANCE AM SIGNAL GENERATOR Type 62**  
 150KHz-220MHz ..... £30  
**METRIX WOBBULATOR Type 210.** 5-220MHz & 440-880MHz ..... £20  
**PHILIPS WOBBULATOR GM28775** 5-220MHz & 440-880MHz ..... £100  
**LABGEAR COLOUR BAR GENERATOR CM6037 (P&P £4)** ..... £60  
**VIDEO CIRCUITS V31A CRT ANALYSER/BOOSTER (Scratched Case)** ..... £50  
**WAYNE KERR COMPONENT BRIDGE BS21 (CT375)**  
 100uH-500KH; 1pF-5F; 1 milliohm-1000Mohm ..... £35  
**RACAL 32MHz UNIVERSAL COUNTER TIMER Type 836** with Manual ..... £50  
**MARCONI TP2604** (Later version of TF 1041 VTM) 20KHz-1500MHz; AC/DC/Ohms AC 300mV-300V FSD ..... £60  
**MARCONI VALVE VOLTMETER TP2600** 10Hz-10MHz; 1mV-300V FSD ..... £40  
**PHILIPS COLOURBAR GENERATOR type 5501 (P&P £5)** ..... £100  
**PHILIPS COLOURBAR GENERATOR type 5508.** Video out. Many Functions ..... £125  
**TES FIELD STRENGTH METER type HC661** in Carrying Case (P&P £5) ..... £60

**ISOLATING TRANSFORMER**  
 240V in - 240V Out 500VA  
 £15 each P&P £5

**NEW EQUIPMENT**  
**HAMEG OSCILLOSCOPE 605.** Dual Trace 60MHz. Delay Sweep. Component Tester ..... £515  
**HAMEG OSCILLOSCOPE 203.5.** Dual Trace 20MHz. Component Tester ..... £270  
 All Other Models Available.

**BLACK STAR FREQUENCY COUNTERS P&P £4**  
 Meteor 100 - 100MHz ..... £39  
 Meteor 600 - 600MHz ..... £128  
 Meteor 1000 - 10Hz ..... £175  
**BLACK STAR JUPITOR 500 FUNCTION GENERATOR.** Sine/Square/Triangle. 0.1Hz - 500KHz. P&P £4 ..... £110

**HUNG CHANG DMM 6010.** 3 1/2 digit. Hand held 28 ranges including 10 Amp AC/DC. Complete with batteries & leads. P&P £4 ..... £33.50

**OSCILLOSCOPES PROBES.** Switched x1; x10. P&P £2 ..... £11

This is a VERY SMALL SAMPLE OF STOCK. SAE or Telephone for Lists. Please check availability before ordering. CARRIAGE all units £12. VAT to be added to Total of Goods & Carriage.

**STEWART OF READING**  
 110 WYKEHAM ROAD, READING, BERKS RG6 1PL  
 Telephone: 0734 68041  
 Callers welcome 9 am-5.30 pm Mon.-Fri. (until 8 pm Thurs.)

**DISPLAY ELECTRONICS LTD.**

★ Do you use cathode ray tubes?  
 ★ Can't find a replacement or shocked by the cost?  
 ★ It may well be that a rebuilt tube will solve your problem.

Come to one of the most experienced firms in the business. We have been rebuilding cathode ray tubes for industry, broadcasting authorities, major airlines, M.O.D. universities, and, of course, the TV trade in general since the '60's.

**WE ARE LOCATED IN UXBRIDGE**

At probably the most accessible part of S.E. England. The nearest junction of the M25 is only about 1 mile away and we are less than 10 minutes from the interchanges on the M25/M3, M25/M4, M25/M40.

Why not telephone Terry Smith on Uxbridge (0895) 55800, to discuss your requirements?

**DISPLAY ELECTRONICS LTD.**  
 UNIT 4, SWAN WHARF,  
 WATERLOO ROAD,  
 UXBRIDGE, MIDDLESEX.

**D.I.Y. TV TUBE POLISHING**  
 with our DIY Polishing Kit

The Kit includes everything you need to polish approx. 25" tubes to a high standard. Detailed instructions on how to do the polishing. All you require is an Electric Drill.

**Kit Price £49 inc P&P and VAT. Available from Luton only.**  
 \*Depends on depth and area to be polished.

**TV TUBES FREE DELIVERY\***  
**5% DISCOUNT ON TUBES COLLECTED FROM LUTON**  
 Quality, High Temperature Reprocessing

TUBE SIZE	DELTA i.e. A51-110X A56-120X A66-120X A67-120X	DELTA SPECIALS i.e. A47-342X 470CTB22 510GLB22 A56-410X A66-410X A67-150X A67-200X	IN LINE & P.L. i.e. 470ESB22 470ERB22 A51-161X A51-570X 510JKB22 560AKB22 A56-510X A66-510X	HITACHI IN LINE etc. AXT37-001 AXT51-001 AXT56-001 510VAB22 510VLB22 510VSB22 A51-421X A51-426X A51-580X A51-590X A51-610X A51-701X	HITACHI IN LINE etc. A56-540X A56-615X A56-711X 560BYB22 520KB22 560ZB22 560EB22 560FB22 560GAB22 A66-540X A67-711X	SONY TRINITRON 330AB22 400FB22 470EB22 470DLB22 470FWB22 520KB22 520NB22 520SB22 570EB22 570HB22 680DB22 680EB22
UP TO 20"	£30	£32	£40	£44	£58	
UP TO 22"	£34	£36	£42	£46	£64	
UP TO 26"	£36	£38	£44	£48	£70	

*Tube types not listed, please enquire.*

All tubes sold with 1 or 2 year guarantee, with optional extension by extra 2 years. Prices shown are for 12 months guarantee. All tubes exchange glass required. Your good, working tubes with scratches or small chips, can be POLISHED with our purpose built polishing equipment. From £7 per tube. Delivery charge on colour tubes: Within 40 miles of Luton. 1 or 2 tubes £6. 3 or more tubes FREE DELIVERY\* Nationwide delivery available, charges on application. Please add 15% VAT to all prices. Callers welcome. Please phone first.

**WELL VIEW** 114-134 Midland Rd, Luton, Beds.  
 Open Mon-Fri 8am-6pm, Sat 9am-1pm. Tel. 0582-410787.  
 Your Local Tube Stockist:  
 Well View, Southampton. Tel. 0703 331837.  
 H. K. Television, London, E.2. Tel. 01-729 1133.  
 West One Distributors Ltd., Gt. Missenden, Buckinghamshire. Tel. 024 06 3609  
 Rushden Rentals Ltd., Rushden, Northants. Tel. 0933 314901  
 Rea & Holland, Ipswich, Suffolk. Tel. 0473 827562.  
 Phone between 12-2p.m., & 6-9 p.m.  
 WANTED A56/A66-510X/540X, Hitachi and Sony, old glass for cash

**CentreVision**  
 TEL: 0222-44754  
 SLOPER ROAD  
 LECKWITH  
 CARDIFF CF1 8AB  
 OPPOSITE CITY FOOTBALL GROUND  
 5 MINS FROM M4

**FERGUSON**  
**VHS VIDEO**  
**£65**

**MANY ELECTRONIC VIDEOS IN STOCK**  
**MANY TOP QUALITY REMOTE CONTROL WORKING TV's.**  
**PHONE FOR LATEST PRICES**  
**PRICES SUBJECT TO VAT**  
**OPENING HOURS:**  
**MONDAY - FRIDAY 9.00 - 5.30**  
**SATURDAY 9.00 - 1.00**

# THE WORLD OF..... "TELEPANELS"

52 Mount Pleasant Road, Chigwell, Essex, 1G7 5ER. Tel: 01-729 0506.

**WORKING  
PANELS  
GALORE!**

## GRAND OPENING OFFER SUPER WORKING PANELS

## FOR THE PHILIPS G11

**P+P 1 PANEL £1.75  
2 PANELS OR MORE  
£3.50**

**N.B. All panels  
despatched by  
recorded delivery  
to avoid loss.**

	IF	TUNER	DECODER	G8/G9 DECODER IF COMBINED	LINE OUTPUT	POWER	CONVERG	FRAME	VIDEO	6 WAY TUNER SWITCH BANK
PHILIPS G.8	5.00	4.50	7.00	15.00	14.00	8.00	5.00	8.00		3.50
THORN 3000/3500	2.00	5.75	4.00		8.00	8.00	5.00	6.00	5.00	1.75
GEC 2110	10.00		5.00		12.00	6.00	5.00	5.00	5.00	5.00
PYE 731			10.00		18.00	10.00	7.00	8.00		4.50
BUSH Z/718	7.50	6.50	14.00		24.00	3.00	5.00	14.00		
BUSH T/20	7.50	6.50	14.00		19.00	19.00	5.00	14.00		
PHILIPS G11	14.50 <small>WITH COMBINED SOUND MODULE</small>		12.00		19.00	19.00	5.00	11.50		
DECCA 80	12.00	POA	14.00		12.00	10.00		14.00		POA

**POST OFF YOUR CHEQUE NOW! AND YOUR PANELS SENT BY RETURN OF POST!!!**

**EMCO - EUROSONIC - GRUNDIG - TELETON + ALL BRITISH MAKES  
ETC. ETC. ● ALL SPARES READILY AVAILABLE ●**

### IMMEDIATE CREDIT AVAILABLE — TRADE ONLY

If you are a trader simply phone for the part you require and we will send it - no quibble - no hold up for status check. Satisfy us over the phone that you are a trader and we will supply almost any TV component by return "off the shelf", e.g. LOPTZ - EHT trays - droppers - OSC coils - switches - cans - smoothers - I.C.'s, etc. etc.

**YOU CAN BE 95% SURE WE CAN SUPPLY ANY  
TV COMPONENT BY RETURN  
IF YOU NEED SPARES FAST — RING NOW!**

ACCESS AND BARCLAYCARD ACCEPTED.

*Applies to U.K. only.*

**TELEPART (W'TON)**

**32 TEMPLE STREET,  
WOLVERHAMPTON (0902) 29022**

## APOLLO LANCASHIRE

MAIL ORDER GB 3-4 DAYS PHONE FOR COST SONY TYPES  
LOCAL DELIVERY - 2 YR GUARANTEE - PILL GLASS BOUGHT  
PORTABLES. 37-590, AXT 37001, 370HUB, NEW £65 INC. DELIVERY

A47 342/343X - 470 BCB22/CTB22/BGB22/DHB22	£39
470-ESB22/EFB22/ERB22/FTB22	£53
A51-220X/192X	£39
A51-161X/162/163/168	£53
510-JKB22/JEB22/JDB22/JGB22/ALB22/GLB22	£53
510-VLB22(ES5) DTB22/001/RFB22/RCB22/SFB22	£53
A51-590 New	£56
A51-570X/580/001/210/241	£53
A56-120X/123/140/410	£39
560-DZB22(ES6)/HB22/AKB22/TB22/AWB22	£56
560-ETB22/DTB22/CSB22/DMB22/DNB22	£53
A56-611X/615X	£53
A86-120X/A87-120X/140/150/200/410	£39
28AX - A56-500X/510X - A66-500X/510X	£53
38AX - A56-540X - A66-540X	£56

PLEASE PHONE BEFORE CALLING  
LOCAL DELIVERY FROM ACCRINGTON, LANCs.

Phone enquiries and letters to:

**Apollo, The Potters Wheel,  
Mullion Cove, Mullion, Nr. Helston, TR12 7ET.  
0326 240781**

## JUST OPENED

FOR

South Yorkshire/Derbyshire Dealers

Come and see our range of  
Colour TVs **from £6**

## BARGAINS GALORE

South Yorks Trade Supply, Anderson House, Cally-  
white Lane, Dronfield, Sheffield, S18 6XR.

**PHONE 0246 411325  
Chesterfield**

## SETS & COMPONENTS

**XM 11 - £20 NEW.** Tested repair spares XM12 transistors - lowest prices. SAE for list BURLINGTON TV, 17 High Street, Bridlington, E. Yorks. (0262) 673374.

**NEW AND SECONDHAND COLOUR TV SPARES.** Panels & Tubes most makes also panel repair service. Tel. Southport (0204) 74411 anytime (24hr).

**GRUNDIG 2x4 SUPER VIDEO** remote control VIF-K1 with tele-pilot TPV355. Brand new, boxed. £12.95 p&p £2 (plugs straight in). STAN WILLETTS, 37 High Street, West Bromwich, West Midlands B70 6PB. Tel. 021 553 0186.

**OCHRE MILL TECHNICAL.** Genuine GRUNDIG spares, massive stocks, sensible prices, fast helpful service. **OSCILLOSCOPES** manuals testgear **TELEQUIPMENT PHILIPS.** 0785 814643.

**CASH PAID** Now for your surplus TV spares, transistors, I.C.'s etc. Tel. MR. FORSHAW, 0902 29022.

**HITACHI, MITSUBISHI,** Panasonic, Sony, Toshiba, JVC, Sharp, fully refurbished. **PEARSON TELEVISION.** 0484 863489. Delivery arranged.

**PHILIPS G11 AND BUSH T20** regular supplies. For prices phone 01-845-2036.

**THORN, GEC, DECCA's** stripped for spares. Panels, Tuners from £2.50. Phone for prices: **WELLINGTONS,** Dartford 0322 337212.

**TURN YOUR SURPLUS** capacitors, transistors, etc., into cash. Contact **COLES-HARDING & CO,** 103 South Brink, Wisbech, Cambs. 0945 584188. Immediate settlement.

### WORKING CTVs THE BEST & CHEAPEST IN LANCASHIRE SPECIAL OFFER

Working Decca Bradford Including  
Black Fronts

18" 20" 22" 26" **ONLY £20.00 each** in 6 units

Working GEC Plastic & Wooden. All models  
20" 22" 26" **ONLY £22.00 each** in 6 units

Working Bush 20" 22" 26"  
**ONLY £15.00 each**

Philips G8 (520) 22" & 26"  
**ONLY £20.00 each**

Plus many more makes & sizes in stock,  
inc. Tanburg, Nordmende, Thorn.

1st COME 1st SERVED

**ALL SETS TESTED & WORKING**

CALL

**JOHN POWNEY**

**TRADE TV SALES & SERVICE**

Unit 31 Progress Industrial Estate,  
Kirkham, nr Preston  
(0772) 683392

**UNTESTED PANELS FOR ALL MAKES OF TV**  
**£1.25 per panel plus post & packing**

# TELEVISION

No other consumer magazine in the country can reach so effectively those readers who are wholly engaged in the television and affiliated electronic industries. They have a need to know of your products and services.

The prepaid rate for semi display setting £6.78 per single column centimetre (minimum 2.5 cms). Classified advertisements 40p per word (minimum 12

## FYLDE T.V. AND VIDEO DISTRIBUTORS

Unit 7, Arkwright Court.

Blackpool/Fylde Industrial Estate  
Very End of M55 left at roundabout.

## UNLIMITED SELECTION OF

<b>THORN</b> 8800	<b>PHILIPS</b> G11
8800 R/C	G11 R/C
9000	G11 TTX
9000 R/C	<b>GEC</b> S/S
9600 R/C	<b>JVC</b> 20"
9600 TTX	<b>MONO's</b> 20" + 24"

## AND MANY MORE

**TRADE WORKERS TO ORDER**

**PHONE BLACKPOOL**

**(0253) 64413**

## SCREENPLAY Your Friend in the TV Business

**COLOUR SETS FROM £5.00**

**MONOS FROM £3.00**

**PANELS BY POST - PRE-CALIBRATED**

**WORKING SETS TO ORDER**

Phone Baldock 894905

SECTION 3, UNIT 4,

SERL COMPLEX,

LONDON ROAD,

BALDOCK, HERTS.

OPEN 6 DAYS 10-6.30pm/10-5pm SAT.

## HALTON TV TRADE DISPOSAL

Wide range of TVs available.  
Working and non-working.

**TRADE ONLY**

(We have NO retail outlet)

St Michaels Industrial Estate, Widnes  
Tel. 051 423 1577

Thorn 3000/3500  
Thorn 9000  
**UNIVERSAL**  
1 year guarantee

**TRIPLERS**  
**£4.95** inc. p&p

The UNIVERSAL TRIPLER can be used in most G.E.C., I.T.T., Pye, Rank, Decca & Continental sets.

**WING ELECTRONICS**

15 Waylands, off Tudor Rd, Hayes End, Middlesex

# SERVICE PAGES

words), box number 70p extra. All prices plus 15% VAT. All cheques, postal orders etc., to be made payable to Television, and crossed "Lloyds Bank PLC". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Dept., Television Room 204B (H.H.), IPC Magazines Limited, Kings Reach Tower, Stamford Street, London SE1 9LS. (Telephone 01-261 5942).

**G.11s Pye & Philips £35**

**ITT Full Remote £35**

**T/TEXT Infra Red**

**GEC Modern 2242-2642 Types Mint £35**

ALSO ON STOCK

THORN, DECCA, BDFD, 80-88-100, PYE CHELSEA 222, TTT CVC 20, 23, 30, 32 Remote, PANASONIC, HITACHI, TANDBERG, GRUNDIG, GEC 2002, 2242, 2642, 2202, and many others, changing daily.

**VIDEO AS AVAILABLE. FROM £20.**

**VHS** HITACHI, 9500, 9300, VT9, 8500, 8300, 8000, PANASONIC, 366, 7200, TRIUMPH 9500, JVC, FERGUSON.

**BETAMAX** SONY C5-C6, C7, SANYO, 5000, TOSHIBA.

**2000 SYSTEM** PHILIPS 2020, 2021, 2022, GRUNDIG 244.

STANDS, SLOT METERS, PANELS, SETS FOR SPARES, CLEARANCE COLOURS CHEAP.

PRICES BASED ON QUANTITY. ALL PLUS VAT.

**GENERAL FACTORS**

UNION STREET,  
DONCASTER, SOUTH YORKS.  
0302-49583

CASH NO CHEQUES.  
ONLY 2½ MILES FROM  
(A1M) FOR M18-M1.  
10 am to 5 pm Daily

**NORMAN ENTERPRISES LTD**  
Weston-Super-Mare, Avon.  
Tel: 413991/418545

Colour TVs fully engineered with a special care on tubes

Hitachi 217 Remote Control ..... £85  
Thorne 9000 Remote Control £42.50  
Pye G11 ..... £47.50  
Rank T20 ..... £42.50  
Pye Chelsea 6 Button ..... £27.50  
Pye 725 ..... £37.50  
Pye 721 ..... £27.50  
Thorne 9600 ..... £45  
Thorne 9200 ..... £42.50  
Bush T20 Remote Control ..... £49.50  
Bush T24 ..... £55.50

## SPECIAL OFFER

20" ITT Pill Tubes completely engineered, superb. Spotless condition cabinets. 200 only.

**£49.50** + VAT.

All above prices include hand sets if available. Ready for sale.

Phone now, limited number each month. All the above off the pile, less a 3rd

## EXPRESS PANELS

A highly skilled staff using specialized service jigs and some of the most up to date techniques and test equipment available means we can save you time, money and heartache.

EXAMPLES FROM OUR RANGE (exch. basis)

Bush T20/22/26 power supply £14.75	Sony 1820/2000/2204 power supply £16.75
G11 power supply £14.60	GEC 20AX/30AX power supply £14.75

All prices subject to VAT, P&P FREE (if orders over £10.00). Panels also available for outright sale, discount for quantities (any mix) all panels guaranteed 3 months, are chemically cleaned and print re lacquered, and have no damaged print etc, so they not only work they look good too. Send S.A.E. for NEW CATALOGUE or ring with your requirements.

TRADE SERVICE AVAILABLE for VCR's.

Callers by appointment only. Telephone orders accepted using Access & Visa.

021-359 3753

ARGO SERVICES (B.HAM) 53,  
Lawley St, B.Ham B4 7XH



## EAST ANGLIA SUPPLIES (BARRY T.V. SERVICES)

WE SPECIALISE IN LATE MODEL TELEVISIONS AND V.H.S. VIDEOS.

T.V.'s  
G11's, KT3, K30, K35, CTX.  
Other makes available.

VIDEOS  
Ferg 3V29, 3V30, 3V35, 3V36.  
Nat Pan 2000, 2010, 333.  
Hitachi 8000.  
Mitsubishi - various models.

All items fully serviced and ready for sale or rent in excellent condition. Free delivery for sensible size orders (petrol only charged).

Phone today for prices and availability to:  
CAMBRIDGE 69215

## STARLITE ELECTRONICS

WILLOWS FARM,  
A13 RAINHAM, ESSEX.  
Rainham 23225 also  
Hornchurch 50238.

EX RENTAL TVs  
UNTESTED FROM £15.00  
WORKING TVs £20.00  
RE-GUNNING TUBES

2 year guarantee  
Most types available  
including Sony



## B.G. COMPONENTS

T.V. & VIDEO SPARES

We supply spares for most makes including Sony and Fidelity all at competitive prices.

We also stock a comprehensive range of rebuilt C.R.T.'s including Hitachi and Sony.

Open Monday-Saturday.

Hill Street, Oldham OL4 2AG.  
061-624 1753.

# BESCO LTD T/A NORTH WEST ELECTRONICS

25 YEARS SUPPLYING THE TRADE

**NEW TRADE SHOWROOM NOW  
OPEN. WORKING TVS AND VIDEOS  
ON SHOW.**

**H.P. REPOS AND EX. RENTALS  
COLOUR TV'S AND VIDEOS**

### Refurbished TV's

BUSH T20/T26 ..... £45  
G11 ..... £50  
PYE KT3 ..... £65

Others done to  
order.

**DISCOUNT FOR  
QUANTITY**

### Annual Clearance Rock Bottom Prices

PYE G11 EXC CAB. £40	PYE KT3..... £50
BUSH T20/26 CH..... £35	GEC 2213..... £30
HITACHI 191..... £20	THORN 3000..... £7
FERGUSON TX	GRUNDIG G415/4206
(NOT D.E.R. Etc.) £65	Best Stock in Country
GEC 2010..... £20	over 2000 in stock (90%
PYE 222..... £20	of our TV's Switch on)
PHILIPS 550..... £15	Special Price Quoted
BUSH 718..... £20	For Bulk Purchases
BUSH 2 CHIP..... £8	From Source.
GRUNDIG 5010..... £10	

### Video

SHARPS 7300, 8300  
9300, HITACHI,  
VT11, FERGUSON  
3V29

(Not Ex D.E.R. etc.)

**SANYO, SONY,  
BETA**

20/22" BUSH T20/22 MODEL EXC CABINETS IN 100 LOTS £25 EACH + VAT  
EX EQUIPMENT BUSH PANELS NO EXCHANGE REQUIRED

	IF	Decoder	Line Scan	Power Supply	Frame
T20/22	X	14	18	17	14
T26	X	16	20	17	X

All prices inclusive of postage but plus VAT  
Cheque with order please


LAUREL STREET, LEEDS ROAD,  
BRADFORD, W. YORKSHIRE BD3 9TP.

**5 MINS FROM MOTORWAY**

100's PX  
**HOOVER JUNIOR  
VACS**  
All models in stock

**Tel (0274)  
660995**

NORTH  
WEST  
ELECTRONICS

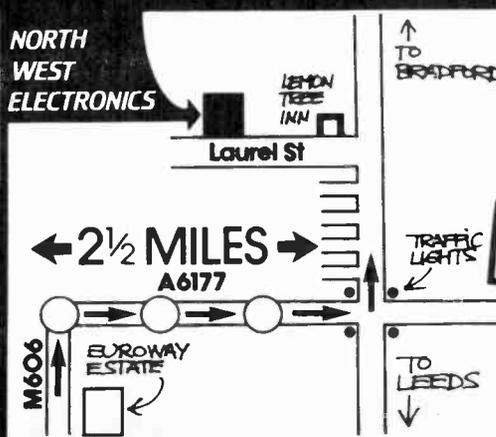

**P.X. WASHERS  
COOKERS  
ETC**

**CASH ONLY**

**OPEN 6 DAYS  
SAT 9-5.30**

# PRICE BUSTERS IN BIRMINGHAM FOR

TESTED AND UNTESTED TV'S AND VIDEO'S

ALSO AVAILABLE DIRECT LORRY LOAD

**RING - 021-772 2733**

## WILTSGROVE LIMITED

(Next Door to UNCLE'S DISCOUNT STORE)

128-130 Ladypool Road,  
Sparkbrook, Birmingham B12 8JA.

### CASH ONLY

"STOP PRESS"

NOW IN STOCK ELECTRONIC VIDEO'S AT UNBEATABLE PRICES

## TUBES

NEW OR REGUNS

ONE YEAR GUARANTEE

14" FROM £45 370 - KRB - LHB - HGB - HFB - HUB - BRB - EGB - EFB - GUB - AXB 37 - 001 - AXM 37 - 001 - 37 - 565 - 570 - 552 - 554 - 590 - A34 EAC 00X.

Broken Tube We Can Help.

16" 420 EDB - EFB - CZB, 42 - 001, 42 - 556.

20" 51 - 161 £40, 51 - 500 - 554 - 570 - 575 - 580 - 590 - 51 - 001 AXT - 510 JKB - VB - UFB - RJB - UDB - HWB - 510 ABUB from £45.

22" 56 - 500 £45, 56 - 540 - 610 - 611 - 615 - 700 - 712 - 560 EGB - DAB - DMB - BYB - EGB - TB - GAB - AXB - ETB - HB - DYB - ATB - BMB - HW 56 - 001 AXT. FROM £45.

26" 66 - 500 - 510 - 540 £55.

HITACHI 510 HWB - VLB - VSB - 560 DZB - HWB - 490 DKB22 Deltas £29.

SONY £65 Cash & Carry only.

DELTA £25.00 Reguns. One year guarantee

£14.50 Slightly used. 6 month guarantee.

A56-120 A56-140 A51-110 A49-191 A47-342 or 343

A44-270-1 A66-120 A66-140 (410) A67-120

(All 26" add £5)

PROFESSIONAL STICK

DE-GAUSSING COILS

£19.50 (1 YEAR GUARANTEE)

Philips G11 AND DECCA 100

Panels from £10.00. Breaking for spares. Push bottom units.

Tube bases. All good working order.

RADIO and TELEVISION SERVICING BOOKS (MacDonalds). New 74/75, 75/76, 76/77, 77/78, 78/79, 79/80, 80/81, 82/83, 83/84, 84/85. See our special offer advert under Books.

FREE DELIVERY

Except Tubes £3 each. All prices are inclusive

U-VIEW

29, Warmsworth Road, Doncaster, Yorkshire DN4 0RP. Tel: 0302 855017. Callers ring first, open every day including Sunday 1/2 a mile from A1

# LOOK!

## IMPORTANT

### DON'T FORGET WE SPECIALISE IN PHILIPS

PHILIPS 2020/21

TESTED, WORKING AND BAGGED.

WITH INSTRUCTION BOOK & CABLES. **£45.00**

VHS & BETA MODELS 100's AVAILABLE

COMPLETE Machines for Spares **£10.00**

## TELEVISIONS

Off Pile		Tested Working Cleaned
G8's	£15.00	£22.00
BUSH T20/22	£35.00	£55.00
PYE G11's	£35.00	£55.00

**TELEVISION WORLD,**

Thornton Road, Bradford, West Yorkshire

Telephone 0274 722499

Why Waste Time *Ring in an order and it will be waiting.*

## WIZARD DISTRIBUTORS MANCHESTER TV & VIDEO SPARES

We stock spares for THORN, PHILIPS, PYE, RANK, GEC, SHARP, SONY, DECCA + ITT.

FIDELITY SPARES MAIN DISTRIBUTOR.

Did you know we also stock

FUSES	ICs
TUBES	TOOLS
AERIALS	VIDEO LEADS
AEROSOLS	AUDIO LEADS
RESISTORS	SEMICONDUCTORS
CAPACITORS	SERVICE MANUALS
VALVES	TEST EQUIPMENT
HANDSETS	TV/VIDEO TROLLEYS

AND MUCH MORE

Counter open Monday-Friday 9am-4.45pm

**TRADE ONLY**

EMPRESS STREET WORKS,

EMPRESS STREET,

MANCHESTER M16 9EN.

Tel: 061-872 5438; 061-848 0060.

## TV TUBES

NEW AND REBUILT. ALL BOXED

DELTA TYPES:- **£15 TO £25**

P.I.L. TYPES:- **£25 TO £35**

OLD GLASS NOT REQUIRED

FREE DELIVERY IN LONDON

FOR ORDERS OVER £100

PHONE FOR QUOTE

**CALEDONIAN RADIO**

208 Caledonian Road, London N1.

Tel: 01-837 0631

# Trent Tubes

For Professionally Rebuilt Tubes  
From WEST BRIDGFORD ELECTRONICS LTD.,  
39A RADCLIFFE ROAD, WEST BRIDGFORD, NOTTINGHAM  
NC2 5FF TEL: (0602) 813329

TWO year guarantee extendable to FOUR years  
THE PROFESSIONAL REBUILDER

ALL STD DELTAS ONE PRICE £32.00

A51-161 - A51-163 £43.00

A51-A56-A66/500/510 (20AX)  
One price £43.00

560DZB 510VLB etc £48.00

A56-A66/540 (30AX) £49.00

SONY TYPES FROM £55.00  
SPECIALIST SONY SERVICE

1000's more types available. VDUs, MONOs, Industrials etc.

Suppliers to Broadcasting Authorities,  
Government depts & National Companies and Manufacturers

ALL PRICES EX WORKS + VAT & EXCHANGE

WE SPECIALISE IN JAPANESE TYPES

INSURED DELIVERY SERVICE AVAILABLE

QUANTITY DISCOUNTS

TECHNICAL ADVICE SERVICE AVAILABLE

Agents, wholesalers required high discount rates

# TELEVISION

COME OVER TO DATEL LTD.  
FOR GREAT DEALS ON SUPER SETS

- ★ 96 CHASSIS IN 5's £30.00 ★
- ★ VHS VIDEO'S FROM £50.00 ★

All Thorn range in stock from 8.8 to TX 10 Stereo

Large stocks of working TV's and Video's.

Phone or call in today. You won't be disappointed.

*Delivery to you can also be arranged.*

Also complete postal service for all Thorn range of panels and spares. All panels and spares for mech. videos.

**DATEL LTD. 0245 469779**

2 Oyster Place, Montrose Rd., Dukes Park Ind. Est., Chelmsford, Essex

**INDEPENDENT TELEVISION  
AND VIDEO COMPANY**  
LARGE STOCKS TO CLEAR  
EVERY WEEK  
COMPETITIVE PRICES

EXAMPLES:

B&W 20"-24"	From £1.00
COLOUR:	
Bush 1-2 I.C.	£4.00
Philips 520-550, 26"	£6.00
Thorn 3500	£6.00
GEC-Decca-ITT	£6.00

Philips 550 22"	£10.00
Pye 18"-20"-22"	£10.00
GEC 20"-22" 26"	£12.00
Thorn 8800-9000-9800	£15.00

Many Other Modern Sets  
and VHS Videos

PHILIPS G11 - ITT - Bush T20-T22-  
T26, Hitachi, Nat. Pan. - Sony  
Off Pile from £40

Phone Frank: Nottingham  
(0602) 864627

Unit 3  
Meadow Trading Estate,  
Meadow Lane,  
Nottingham NG2 3HQ.

## AT LAST! QUALITY USED TELEVISIONS & VIDEOS

EXCELLENT CABINETS & GOOD WORKERS  
TELETEXT & REMOTES (BOTH WITH HANDSETS)  
THORN TX 9600, 9000, 9200, 8800 & 8000  
BUSH T20 & Z TYPE PHILIPS G11

**WORKING VHS VIDEOS FROM £85**  
NON WORKING VIDEOS FROM £50  
MONITEC

The Heathlands, Kidderminster Road, Bewdley, Worcs. Tel. 0299 400233/400933

### LOOK HEAR TV

THE BEST TRADE WAREHOUSE IN THE EAST  
MIDLANDS FOR QUALITY TV'S AND VIDEOS

LARGE SELECTION COLOUR TV'S,  
VHS VIDEOS. ANY QUANTITY.  
ELECTRONIC VIDEOS TO ORDER

#### SPECIAL OFFERS

THORN 9000 working inc. handset £35 + VAT  
3V22 with new head, working £120 + VAT

OPEN: Mon-Sat 10-5.30, Sunday 10-12.30

CASH ONLY PLEASE

Unit 4, King Street Buildings,  
King Street, Enderby, Leicester.  
Only 5 mins from Junction 21, M1  
Ring ADRIAN BALMER on  
LEICESTER (0533) 867530

### PRECISION VISION LTD.

For:

- ★ LATE MODEL USED COLOUR TVs
- ★ REFURBISHED TO HIGH STANDARDS
- ★ BECOME ONE OF OUR REGULAR  
HIGHLY SATISFIED CUSTOMERS
- ★ EARLY COLOUR TVs FROM £5

Unit 10, Chiltern Business Centre,  
Garsington Road, Cowley, Oxford  
(next to B.L. Works).  
Phone 0865 711966

### PHILIPS VIDEO SPARES

Model VR 2324. Brand new unused includes  
power supply tuner, timer clock, R.F. panels,  
cabinet, electronics only, no mechanism £35  
inc VAT and postage.

EFJAY PRODUCTS

13 Placehouse Lane, Old Coulsdon, Surrey  
Phone: Downland (07375) 55287 anytime

### IRISH T.V. DEALERS

New re-gunning plant

- TUBES -

Super View - Delta - In-line - P.I.L.

CHRIS KELLEHER'S T.V.

Kanturk, Co. Cork

Large stock G.8 - Decca - Ferg - T.V.'s UHF/VHF

029-50046 - Cash/Carry

# SERVICE PAGES

## COLOUR BAR GENERATOR

Pal Colour Generator with 11 patterns plus sound. Grey scale, Colour Bars, Red, Green & Blue Raster, Cross-hatch, Dots, Chequer Board, Black Raster, White Raster, Half Black & White, Mains Powered. **£75.90**

### OUTPUTS PROVIDED

UHF OUTPUT  
VIDEO OUTPUT  
SOUND OUTPUT  
LINE PULSE  
FIELD PULSE



Same as above plus RGB output **£81.50**  
Line Output Transformer Tester **£11.50**  
B/W Generator, Crosshatch, Peak White, Dots, Half Black & White and Grey Scale UHF output **£18.50**  
Same as above but with Video Output **£20.50**  
Capacitance Meter measures 10pF to 1µF complete with moving coil meter **£14.75**

### CRT TESTER/RE-GENERATOR SEND S.A.E.

S.A.E. for details. Prices include VAT.  
Postage on Colour Bars £1.75, others 75 pence.

## C.M.J. ELECTRONICS

Unit 8, 16 Union Mill Street, Horseley Fields,  
Wolverhampton WV1 3DW.  
Tel: (0502) 871563

## TRADE TVs

Yorkshire New Outlet  
Ex-Rental & Repossessed TVs  
Colour From £10  
Mono From £2

TRADE REPAIRS AND SPARES  
WANTED VIDEOS IN QUANTITY

## TELEFIX

Ellingthorpe Street,  
Wakefield Road, Bradford 4.  
Phone: 0274 480281 or 733373.

## BOURNEMOUTH

LARGE STOCKS OF NICE  
CLEAN WORKING SETS,  
MOST MAKES AND SIZES.  
FAIR PRICES – TRADE ONLY

WAREHOUSE OPEN:  
Mon-Fri 9-1, 2-5

HILLIER'S, UNIT 2A,  
11-15 FRANCIS AVENUE,  
WALLISDOWN. TEL: 0202 581932

## BUSINESS OPPORTUNITES

WELL ESTABLISHED (19 YEARS) Video, Audio, Hi Fi Sales & Service Business for sale in popular N. Devon resort. T/O £62,000 (without V.A.T.). Only £12,500 for quick sale plus S.A.V. Details: Box No 216.

## TV VIDEO-AUDIO SALES AND SERVICE BUSINESS FOR SALE

Modern premises shop and workshop. Good class North London area. Ideal for ambitious engineer. Established 30 years, new lease.

PRICE **£18,500** + S.A.V.  
Details: Box 201

## VIDEO & HI-FI ELECTRONICS

379 EDGWARE ROAD  
LONDON W2  
TEL. 01-258 0328

ALL VHS PARTS AVAILABLE. EXAMPLES:

### VIDEO HEADS

JVC, Ferguson, Akai, Saba, Telefunken ..... **£35.00**  
Sony (Betamax) ..... **£45.00**  
National Panasonic ..... **£45.00**  
All Hitachi heads from ..... **£42.00**

### INTEGRATED CIRCUITS

UPC 1365C ..... **£6.30**  
UPD 553C ..... **£10.20**  
UPD 552C ..... **£9.56**  
HA 11711 ..... **£10.50**

All makes of idlers, pressure rollers, clutch assembly and motors in stock.

Many other parts available. Send SAE for list.

ALL PRICES INCLUSIVE OF VAT  
ADD £2.00 FOR P&P

## T.V. SPARES, PANELS AND MANUALS

PHILIPS · GRUNDIG

TELEVIEW 01-994 5537  
194, Acton Lane, London W.4.

PLEASE

MENTION

TELEVISION

WHEN

REPLYING

TO

ADVERTISEMENTS

## VIDEO

## V.H.S. VIDEO'S 100'S IN STOCK

Famous brands:

JVC · PANASONIC · FERGUSON

Also stockists of Grade B Units, Micro-waves, Hi-Fi, Radio/Cassettes etc. etc.

CONTACT MICK ON:

**021-772 1591**

## SITUATIONS WANTED

EXPERIENCED, LONDON TRAINED Television, electronics technician seeks employment in Australia. Reply to: D. CHETTY, Box 208, Ladysmith 3370, South Africa.

## METERS

METERS. Reconditioned 10p/50p available from stock. Contact THE METER CO. (Poole) LTD. (0202) 683498.

TELEVISION METERS. All types required for cash. We collect. P & J WALES, Tel. (0803) 25832.

## AVON METERS

We buy and sell and repair TV coinmeter. Reasonable prices, one year guarantee.

213 Cheltenham Road,  
Redland, Bristol.  
0272-425281

## WANTED

WANTED VIDEO'S, Portables, colour TV etc. Any quantity. Immediate collection, cash paid. Tel. Stoke on Trent 416401.

CASH PAID now for your surplus TV spares, transistors, I.C.'s etc. Tel. MR. FORSHAW. (0902 29022).

GOLD PLATED SCRAP WANTED. Scrap edge connectors, circuit boards, anything considered. Contact P & F TURNER & SONS. Tel. Oxford (0865) 50293.

WANTED FOR CASH. Ex rental colour televisions and videos. Large or small quantities. Will collect. Tel. 0272 211179.

JVC 7600 MS VIDEO RECORDER, condition immaterial. Also video head assembly for Grundig 4004 VCR. Cash available. Tel. 042 523027.

TUNGSRGRAMS TELEMODEL F2277 Mk II chassis 470146 copy of S/S required urgent. Box No 214.

WANTED TECHNICAL PUBLICATIONS, Service Manuals. Circuits. Trader ERT Service Sheets – Fault Guides. Box No 217.


WANTED VIDEOS, Sanyo VTC 5000. Hitachi 8000 series. Any condition/quantity. Cash paid. Box No 218.

WANTED  
Ex RENTAL COLOUR  
TVs IN BULK  
QUICK COLLECTION  
Phone 0742 312832  
(Sheffield)  
IN STRICTEST CONFIDENCE
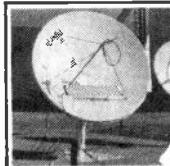
## AERIALS

**MULTI-OUTLET/MULTI-CHANNEL** Installations. Large or small distribution systems. Equipment and/or consultancy by post or on site. Catalogue (full of trade know-how and trade equipment) £1 (refundable). **WRIGHTS AERIALS**, 43 Greaves Sike Lane, Micklebering, Rotherham. (0709) 813419.

**EXPANDING AERIAL MANUFACTURER** with capacity invites enquiries from wholesalers and contractors. Highly competitive prices for TV/FM Aerials, masts, brackets etc. Replies to Box No 215.



**Euro-Sat**  
**Parabolic Dish Antennas**  
*(Parent company est. in TV communications since 1969)*  
**SATELLITE TVRO ANTENNAS**  
**TOP QUALITY SOLID GLASSFIBRE DISH ANTENNAS**  
**TRADE PRICES**

1M. DIA 11-12.4 GHZ BANDS	£77.00
1.2M. DIA 11-12.4 GHZ BANDS	£93.00
2M. DIA. 11-12.4 GHZ BANDS	£215.10
3M. DIA 11-12.4 GHZ BANDS	£437.00

Trade & Export Enquiries Welcome  
 Prices do not include delivery

**Euro-Sat**  
 107 Cross Street, Sale, Cheshire, England.  
 Tel. 061-437 2631 061-881 4249

## AERIAL BOOSTERS

**B45-UHF TV** next to the set fitting. Gain 10dbs (trebles gain), works off PP3 type battery or 8V to 14V working. Price complete (excluding battery) £5.70.

**Beam Video** This will beam good quality pictures and sound more than 30ft. Price complete (excluding battery) £10.50

We also make aerial boosters for VHF/FM radio £7.70, and VHF television, prices £7.70 & £8.70, p&p 50p per order.

**ELECTRONIC MAILORDER,**  
 62 Bridge Street, Ramsbottom,  
 Lancashire, BL0 9AGT.

Tel: Ramsbottom (070 682) 3036. (24 hr).  
 Phone for leaflets. Access/Visa Welcome.

## SATELLITE TELEVISION

Buy direct from the manufacturers, low cost, full band satellite TV systems. Full band system £650 + VAT and Carriage

Write or telephone for details or call in at our factory showroom

**NETWORK SATELLITE SYSTEMS LTD.**  
 Unit 7-8, Newburnbridge Ind. Estate,  
 Hartlepool, Cleveland  
 Tel. 0429 274239 or 869366

## REPAIR SERVICE

**INSTRUMENT REPAIRS**, Oscilloscopes, generators, multimeters & more. Phone **VIKING ELECTRONICS**, 0394 450006.

## PRINTED PANEL REPAIR SERVICE

for example: G11 - T20 - AX PSU - £15.00  
 G11 - T20 - AX - LTB - £16.00

Most makes and models covered.

**RING 0934 418545**

for price list or quotation

## BRISTOL - SOUTH WEST SOUTH WALES

Scratched and chipped CRTs can be Re-polished.

Tel: 0454 778635 for details

## SERVICE SHEETS

# SERVICE MANUALS, SERVICE SHEETS

For Television, Radio and V.C.R.'s. Prices from £2.00 inclusive of VAT.  
 Send large s.a.e. for free catalogue with your enquiries, Mail Order only.

**TECHNICAL DEPARTMENT, YOLANCEN LIMITED,**  
 1 Buckingham Street, York YO1 1DW.

## TECHNICAL INFO SERVICES (T) - 76 Church St., Larkhall, Lanarkshire ML9 1HE.

World's Sole Publishers of Comprehensive TV/Video Repair Manuals & Largest Known Stockists of Service Manuals and Service Sheets for all kinds of equipment both British and Foreign from 1935 to latest issues.

Big Catalogues of thousands of Service Sheets & Manuals + Chassis Guide + £4 Vouchers - saves time and expense £3.

Any published single service sheet for **£2.50** + Isae except ctv/mus-c/combis from **£3.50** + Isae.  
 A selection from our stocks of thousands of Service Manuals ready for despatch by return post.  
 Any Sony: Hitachi ctv from **£8.50**, Thom 3000/3500 **£9.50**, Thom 8000/8004/8500/8600 **£9.50**, Philips G8 complete **£9.50**, Decca 30/31 **£8.50**, Ferguson/JVC 1st video **£19.50** or 3V00 types basic manual **£19.50**. Any Finlandia: Tyne CTV **£9.50** each. Rank A823 complete **£9.50**.

COMPREHENSIVE PRACTICAL TV REPAIR MANUAL **£9.50** PRACTICAL RADIO SERVICING & REPAIR COURSE **£9.50**  
 THE 11 TUNBRIDGE REPAIR MANUALS **ONLY £88** THE 5 McCOURT REPAIR MANUALS **ONLY £55**  
 ANY SET OF 5 INDIVIDUAL VIDEO REPAIR MANUALS FOR **£12.50** OR ALL 3 SETS (15 MANUALS) FOR **£36**.

## UNIQUE COLLECTIONS OF CIRCUITS, LAYOUTS, ETC. . . . FANTASTIC VALUE

British ctv from hybrids to modern (3 binders) **£55** Videos, all types (3 binders) **£58** . . . any 1 for **£20**  
 Mono TV (2) **£35** Foreign ctv (2) **£35** Domestic Eqpt (2) **£35** Portable British ctv (1) **£20**.

## COMPLETE REPAIR SYSTEMS . . . huge savings from published prices

British ctv 3 binders of Circuits plus 6 Repair Manuals plus ref books, etc. **for only £140**

Foreign ctv 2 binders of Circuits plus 4 Repair Manuals, etc. **for only £65**

Videos 3 binders plus 15 individual Repair Manuals cover all the commonest models **for only £85**

Complete Integrated T.V. Repair System **only £250** or in 12 sections at **£25 per section**.

Contents: 8 binders of circuits/16 Repair Manuals/dozens of other manuals . . . Any new publications from us within 1 year of ordering 1st section will be added at no extra charge.

<b>NEW</b> - PRACTICAL TRANSISTOR - From beginners/students elementary theory to more advanced. Huge section British/Foreign equivalents/alternatives/other data. <b>£4.50</b> + £1 P&P.	<b>NEW</b> - VIDEO REPAIR SYSTEM 3 <b>£28</b> - Binder of Circuits alone <b>£20</b> 5 Repair Manuals <b>£12.50</b> 3V31/32 Philips VDP & all early Sharps. Pan 7200 etc.	<b>NEW</b>
---	---	------------

Repair data/Circuits/Service data almost any individual	mono tv <b>£12.00</b>	basic ctv <b>£16.00</b>	video <b>£25.00</b>
Repair data/Circuits almost any individual	mono tv <b>£10.50</b>	ctv <b>£12.00</b>	video <b>£10.50</b>

**LSAE BRINGS ANY REQUESTED QUOTATION - FULLER DETAILS - FREE MAGAZINE - PRICE LISTS ETC.**  
**PHONE 0698 884585 Mon-Fri before 5pm or 0698 883334 any other time - FOR FAST QUOTES**

**BELL'S TELEVISION SERVICES** for service sheets on Radio, TV, etc. £1.50 plus S.A.E. Service manuals on colour TV and Video Recorders, prices on request. S.A.E. with enquiries to B.T.S., 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 505885.

\*\*\*\*\*  
**SERVICE PAGES SERVICE PAGES**  
 PLEASE MENTION TELEVISION WHEN REPLYING TO ADVERTISEMENTS  
**SERVICE PAGES SERVICE PAGES**  
 \*\*\*\*\*

## TELEVISION SERVICE SHEET SPECIALISTS

Thousands of British, European and Japanese models in stock.

**Colour £3.00 Mono £2.00**

Manual prices on request.

All our prices include post and packing costs.

Send stamped envelope for free catalogue and any enquiries.

**SANDHURST TV SERVICES (MAIL ORDER)**

**57 High Street, Sandhurst, Camberley, Surrey GU17 8HB.**

## MISCELLANEOUS

**NOW TOTAL SPARES SUPPORT FOR**



FROM



ALL from STOCK

(Subject to availability from Fidelity)

**CABINETS \* KNOBS \* TUNERS \* CONTROLS \* CRT'S \* TRANSFORMERS  
 SEMI'S \* I.C.'S \* CAPACITORS \* REMOTES \* TRIMS \* END USER PARTS**

Tel:  
 0734  
 876444

**Willow Vale Electronics Ltd**  
 11 Arkwright Road, Reading, Berkshire RG2 0LU

Tel:  
 0734  
 876444

**GENUINE FIDELITY PARTS AT STANDARD FIDELITY TRADE PRICES**

GET  
**SHARP PARTS FAST**

TELEPHONE  
**0734 - 876444**  
TELEX 848953



**SHARP**  
Main U.K. Spare Parts Distributor

Audio-TV-Video ★ Microwave ★ Photo-copier ★ Typewriter

All U.K. model spares available. Same day despatch of orders received before 1pm.  
Microwave, photocopier and typewriter spares to authorised service dealers/centres only.  
**WILLOW VALE ELECTRONICS LTD.,**  
11 Arkwright Road, Reading, Berks.

**MAIL ORDER MANUALS**

**BURROWS SERVICE**  
33 HANCOCK ROAD,  
LONDON SE19 3JN.

£1 LISTS (Refundable on orders)

**C.R.T. REBUILDING  
PLANT AND EQUIPMENT**

Installation, commissioning, training and technical after sales assistance.

**C.R.T. INTERNATIONAL**  
136 Badmington Road,  
Coalpit Heath,  
Bristol BS17 2SZ  
Tel: 0454 778635

SOLE SUPPLIERS TV/VIDEO Repair manuals/circuits, 1000s s/manuals supplied by return. S/sheets £2.50 except CTV/m.centres/stereos £3.50. LSAE with every order/query please bring free price list/magazine inc s/sheet - or phone 0698 884585 (883334 outside business hours) TIST, 76 Church Street, Larkhall, Lanarkshire.

*The Theory and Practice of PAL Colour Television in three important Video Cassette Programmes*

- Part 1.**  
The Colour Signal  
**Part 2.**  
The Receiver Decoder  
**Part 3.**  
Receiver Installation

VHS★★★★V2000★★★  
BETAMAX★★★★UMATIC



For full details telephone  
**0253 725499 (Day)**  
**0253 712769 (Night)**

Or send for precis details  
**FLINTDOWN CHANNEL 5**  
339 CLIFTON DRIVE SOUTH,  
LYTHAM ST ANNES FY8 1LP  
(enclosing this advert)

NAME .....  
ADDRESS .....  
TEL: .....

**SITUATIONS VACANT**

**TELEVISION ENGINEER**

Experienced engineer required for bench & field work on industrial and domestic video equipment. Good salary and prospects for the right person.

BUPA membership and bonus scheme.

For application forms please write (with brief career history) to:

**Mr. Colin Lippitt,**  
E.S. Video Ltd.,  
5 Mead Lane,  
Farnham, Surrey GU9 7DY.

**BOOKS AND PUBLICATIONS**

A-Z LIST OF MANUFACTURERS ADDRESSES. All major TV, audio etc plus many hard to get ones. Send Cheques/PO for £3.75 to DOWNS ELECTRONICS, 135 Main Street, Newton Grange, Midlothian EH22 2PF.

"RADIO AND TELEVISION SERVICING" books, new editions for the last 6 years usually in stock. Prices on request. BELLS TELEVISION SERVICES, 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 505885.

**SPECIAL OFFER**

MACDONALDS RADIO & TV SERVICING BOOKS, NEW 74-75, 75-76, 76-77, 77-78, 79-80, 80-81, 82-83, 83-84, 84-85.

Macdonalds Price	£24.30 delivered
OUR PRICE	£22.50 delivered
Two or more	£21.00 each
Full set of 10	£199.00

Prices include delivery

**U-VIEW, 29 Warmsworth Road,**  
Doncaster, Yorkshire DN4 0RP.  
Tel. 0302-855017. Callers ring first

**"THE HOME SATELLITE TV  
INSTALLATION &  
TROUBLESHOOTING  
MANUAL 1986"**

One of the latest and best American books which gives all the practical advice every TV service engineer will need to earn a living in the future.

This 313 page text explains how the satellites operate and provides all the information for installation of a dish system, and is complete with several hundred illustrations.



To order  
Send cheque for £23. COD also available.  
**J. Vincent Technical Books,**  
24 River Gardens, Purley,  
Reading RG8 8BX. Tel: 0734 414468.

**FOR SALE**

2 SETS OF FULLY RECONDITIONED tube re-gunning plants for sale. Training provided. From only £3,995. Tel. 0582-410787.

PHILIPS 2020 A/V ADAPTOR. V2000 Video Tapes. Miscellaneous VR2022 spares PM2517 digital meter including various accessories. Telephone 074632 406.

PRACTICAL TELEVISION 1967/83 Complete R/TV servicing 1968/77. Good condition. Offers. Tel. 0483 60580.

COL-PATT GEN EP686B, mint, other instruments, compo's, RTS Vols, service data. S.A.E. WILLOW HOUSE, Conway Road, Llandudno.

**DEVONICS**  
Quality Rebuilt Tubes  
**2 YEAR WARRANTY**

470 ERB22	£43
510 KCB22	£45
A51-161/500/510/ 570/580/590X	£45
560 AKB/DZB/TB22	£45
A56-500/510X	£45
A56-540X	£53
A66-500/510X	£46
A66-540X	£53
670 XB22	£46

Deltas from £30  
Plus carriage and VAT  
**2A BARTON HILL ROAD,**  
TORQUAY TQ2 8JH  
**0803 - 33035**

**FOR INFORMATION ON  
CLASSIFIED ADVERTISING  
PLEASE RING PAT BUNCE  
01-261 5942**

 **Sabaco** For a great deal!

**TRY US YOU'LL LIKE US  
TOP QUALITY TV'S & VIDEO'S AT  
ROCK BOTTOM PRICES**

**VAN LOAD DIRECT FROM SOURCES  
ALL SETS & VIDEO'S OFF THE PILE  
(Mostly switch-ons)**

**Largest selection of 4000/8800/9000/9200/  
9600/Ferg TX9/TX10 Stereo Teletext  
Colour Portables**

**Mainly teletext and remote with handset.**

**Also Pye KT30/G11/T20/T26/Hitachi/  
Philips 550/Grundig & many more.  
BRAND NEW SETS AT LOW PRICES**

## VHS VIDEO'S

**Good Working Order from 3V22, 3V23,  
3V29 Portable Video's etc.**



**Also a selection of brand new video &  
E180 video tapes**

**OPENING HOURS:**

**MONDAY TO SATURDAY 9am to 5.30pm  
SUNDAY 10am to 4 pm**

**CASH ONLY All goods subject to VAT & availability  
PHONE NOW FOR UP TO DATE COMPUTERISED PRICES  
AND DELIVERY DAYS, BE HERE WHEN LORRY ARRIVES  
FOR FIRST CHOICE — PHONE US NOW ON:**

**(0602) 397555**

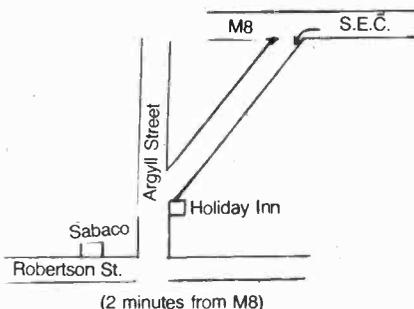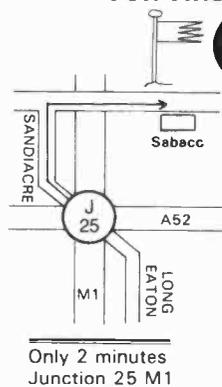

**Head Office:  
Sabaco  
Saba House,  
46A Derby Road,  
Sandiacre, Nottingham  
(0602) 397555**

**Sabaco  
75 Robertson Street,  
Glasgow  
(041) 221-2146**

## MAIL ORDER ADVERTISING

### British Code of Advertising Practice

Advertisements in this publication are required to conform to the British Code of Advertising Practice. In respect of mail order advertisements where money is paid in advance, the code requires advertisers to fulfil orders within 28 days, unless a longer delivery period is stated. Where goods are returned undamaged within seven days, the purchaser's money must be refunded. Please retain proof of postage/despatch as this may be needed.

### Mail Order Protection Scheme

If you order goods from Mail Order advertisements in this magazine and pay by post in advance of delivery, Television will consider you for compensation if the Advertiser should become insolvent or bankrupt provided:

- (1) You have not received the goods or had your money returned; and
- (2) You write to the Publisher of Television summarising the situation not earlier than 28 days from the day you sent your order and not later than two months from that day.

Please do not wait until the last moment to inform us. When you write, we will tell you how to make your claim and what evidence of payment is required.

We guarantee to meet claims from readers made in accordance with the above procedure as soon as possible after the Advertiser has been declared bankrupt or insolvent.

This guarantee covers only advance payment sent in direct response to an advertisement in this magazine not for example, payment made in response to catalogues etc., received as a result of answering such advertisements. Classified advertisements are excluded.

**If an  
advertisement  
is wrong  
we're here to  
put it right.**

If you see an advertisement in the press, in print, on posters or in the cinema which you find unacceptable, write to us at the address below.

**The Advertising Standards Authority** ✓

ASA Ltd, Dept 3  
Brook House, Torrington Place,  
London WC1E 7HN

# SIGHT & SOUND

STOKE-ON-TRENT 0782 335262

FERGUSON 3V23  
 NAT-PAN 7200  
 NAT-PAN 366  
 HITACHI 8600  
 HITACHI  
 NAT-PAN 2010

Factory Reconditioned | G11  
 Infra Red Video | T-20  
 Cord Remote Video | THORN 9600  
 Infra Red Video | G11 TEXT  
 Cord Remote Video | COLOUR PORTABLES  
 Basic Video | THORN 9000

200 Always in Stock  
 100 Always in Stock  
 Always in Stock  
 100 in Stock  
 In Stock  
 Always in Stock

**SATISFACTION GUARANTEED**  
**FRIENDLY SERVICE – NO GIMMICKS**  
**PERSONAL ATTENTION – ASK FOR JOHN SAHOTA**

## REPOSSESSED T.V. CENTRES LTD.

061-273-2854


### YOUR CHOICE

**MINT WORKING SETS.** These arrive at our premises in A1 working order, cabinets are superb. .... **£45 to £70**

**GUARANTEED UNTESTED SETS.** These are just as they arrive, in good condition with plenty of plug in workers. We do not sort them as we have our separate source of working sets. .... **£10 to £35**

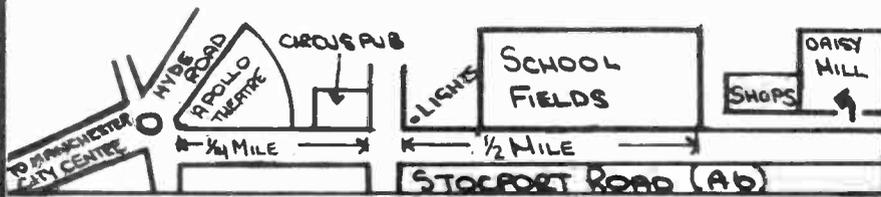**VHS Videos in stock.**

*Well stored in large centrally heated premises. Ample viewing space and stored only four high!  
 Come and have a look round.*



**TRADE WAREHOUSE,  
 DAISY WORKS,  
 345 STOCKPORT ROAD,  
 LONGSIGHT,  
 MANCHESTER M13 0LF**

**ALSO AT  
 335-341 STOCKPORT ROAD  
 (NEXT DOOR)**

## N.G.T. COLOUR TUBES

*First Independent Rebuilder with  
 B.S.I. CERTIFICATION*

**DELTA – IN-LINE – PIL – BONDED YOKE**  
 including  
 AXT Series, DZB series 20AX - 30AX  
 A56 610/67 610 series, A51 570/580/590X  
 A51 161X, Sony types etc.

- ★ Rebanded with new adhesives
- ★ Excellent high voltage clean-up
- ★ Accurate alignment of Gun and Yoke for optimum convergence

**N.G.T. ELECTRONICS LTD.,**  
 120 SELHURST ROAD, LONDON SE25  
**Phone: 01-771 3535.**

*25 years experience in television tube rebuilding.*

**LONDON'S LARGEST  
 TELEVISION WHOLESALE...  
 with over 4½ thousand sq. feet**

## "TELEMANN"

*Export  
 orders  
 welcomed*

**8-10 RHODA STREET (off Bethnal Green Road)  
 LONDON E2. FREE CAR PARK  
 SPECIAL OFFER!!**

- Parcel of 25 Monos ..... £1.00 each
- Parcel of 10 Philips 22" G8 550 ..... £15.00 each
- Parcel of 10 Decca Bradfords (6 buttons) ..... £12.00 each
- Parcel of 10 Japs Colour ..... £20.00 each

**LORRY LOADS DELIVERED DIRECT FROM SUPPLIERS  
 NO CHARGE FOR DELIVERY IN THE LONDON AREA!**

**01-739 2707 → 2 LINES ← 01-739 3123**

**FREE CAR PARK + NO YELLOW LINES OUTSIDE!**



# SENDZ COMPONENTS

TO ORDER SEE BACK PAGE

<b>Thorn Spares</b>		K35 Decoder	£8
New 9000 Decoder	£8.50	K35 Sound OP	£4
9000 Frame panel	£8	K35 Split Diode 3122-138-35930	£10.00
9000 Cyclops panel	£1.50		
8000/8500 timebase panel	£8		
8800 convergence panel	£6		
8500 convergence panel	£6		
4000 Power supply	£3		
1600 Mains lead, switch			
3500 6 push button + cable form	£1.50		
7605 1V NPN T066 80V/6A	10p		
9000 Sound output panel	£1		
3500 Focus unit	£1.50		
3500 Mains Trans	£4		
3500 cut outs	10 for £4		
3500 IF panel	£2		
3500 Frame panel	£2		
3500 Line panel	£3		
3500 A1 Diode	20p		
Export 3500 IF panel	£2		
IC board with set of SN74LS	£4		
4000 Tube base	£4		
3500 A1 pots	50p		
Beam limiter panel	£1.50		
3500 Power panel with Y969	£1		
3 Way regulated adaptor 240V 6V/	£1		
7.5V/9/30mA	£3.50		
Rank/Toshiba preh unit 0354	£9.50		
2 banks of 3 PB unit. Pye 731	£2		
4 Push button unit preh	£1.00		
6 Push button VHF/UHF for	£7.00		
v/cap. GEC-Decca type	£8.00		
7 Push button for CVCs ITT	£7.00		
G8 Push Button Unit	£10.00		
KT3 12 Push button unit	£2.00		
KT3 (Export) 12 P.B.U.	£1.00		
6 Push button Unit Thorn	£1.00		
6 Push button Unit fits GEC			
& Decca etc.	£6.00		
Hearing aid unit	£3		
Rank Z718 4 P/B/Unit MECH	£4		
7 Button Unit GEC with Lamps	£7		
Bush T515A 6 button unit with Pos	£6.00		
& mains lead, 6 bush buttons. Bush	£6.00		
697 Push Button Unit	£6.00		
<b>Mains Droppers</b>			
G8 2R2+68R	£1.25		
G8 47R 15 watt	75p		
Pye 731 3+56+27R	50p		
Thorn 50/17/1K5	£1.00		
120/20/20/48/117	£1.00		
27/10/6 for Thorn 4000	£1.00		
18/32/70/79	£1.10		
Thorn 50-40R-1K5	£1.50		
Ae Socket & Lead	£2.00		
GEC, ITT, Philips, Pye	25p		
7x 33/4Thorn	£1		
Thorn 1600-1700	£1.50		
Rank Toshiba Tube Bases	30p		
<b>Speakers</b>			
6x4 G11	25 ohm	£1.00	
51/2x2 1/2	3 ohm	£1.00	
5x3	80 ohm	70p	
5x3	50 ohm	50p	
5x3	35 ohm	70p	
6x4	15 ohm	£1.00	
7x3	70 ohm	£1.00	
8x5	8 ohm 15 watt	£2	
8x5	8 ohm	£1	
5x3	8 ohm	70p	
7x3	16 ohm	£1.00	
5" dia	16 ohm	£1.00	
5" dia	8 ohm	£1.50	
6 1/2" dia	4 ohm	£1.50	
6 1/2" dia	3 ohm	£1.50	
2 3/4" dia	8 ohm	75p	
3" dia	8 ohm	75p	
4 1/2" sq	15 ohm	75p	
KT3 speaker	K30	75p	
3" dia	15 ohm	60p	
1690 5x3	12 ohm	£1.00	
K45 Philips	15 ohm	75p	
K30 15 watt		£1	
<b>KT3-K30</b>			
E.W. correction	10p		
OF-513	10p		
OF-557	50p		
<b>DIODES</b>			
BY 126	10p		
BY 127	10p		
BY 133	10p		
BY 134	10p		
BY 164	10p		
BY 176	25p		
BY 179	40p		
BY 184	25p		
BY 187	10p		
BY 190	40p		
BY 196	30p		
BY 198	10p		
BY 204/4	10p		
BY 206	8p		
BY 208/8/1	5p		
BY 210/4/1	5p		
BY 210/8/1	10p		
BY 223	60p		
BY 224/6/1: 4.8A/600v bridge	50p		
BY 226	15p		
BY 227	15p		
BY 229/4/0	30p		
BY 237	5p		
BY 254	10p		
BY 255	30p		
BY 298	10p		
BY 299	10p		
BY 406	8p		
BY 527	20p		
BY 407a	10p		
BY 642	10p		
F 247	10p		
XK 3102	50p		
BYV 28/200	20p		
80V/2.75 amps	10p		
International Rectifier EHT Diodes	G770/HV34 6KV	3 for 8p	
6A/600V Stud Diodes	20p		
6A/1000V Stud Diodes	20p		

NEW Pack THORN 17 off Manual	£5.00
NEW 1617 THORN Chassis with ICs & AU113	£5.00
30V Power Supply 500mA 4x2 1/4	£2.50
Pye 731 Power Panel	£13
6 Diode Universal Triplers	£4.00
NEW PYE 725 line O/P panel with L.O.P.T. & Tripler	£10.00
NEW GEC 20AX Power Supply Switch Mode	£12.00
Complete new GEC portable chassis M1201H/M1501H with P.B.U./v.cap/LOPT1	£10
Fiedal Jungle panel for GEC 3133/3135	£1.50
GEC 2110 line panel with transformer	£7.00
GEC 2110 tuner unit + IF Panel	£12.00
Pye/Chelsea Line on panel	£12.00
Pye 205 T/unit	£3.90
Pye 205 Line on panel	£7.50
Pye 713 IF panel and tuner	£7.00
Pye 713 Chroma	£10.00
Pye/Chelsea Timebase panel with LOPT1	£10.00
Pye 731 Frame Panel	£5.00
Pye 731 Convergence Panel	£5.00
Pye 731 Chroma	£10.00
Pye 731 IF panel + tuner	£10.00
Pye CDA/205 panel	£6.00
GEC portable chassis + LOPT1 2114 New	£4.00
Thorn 1613/1713 chassis	9.75
G9 Power Panel	£6.00
Mono RANK Chassis 127A NEW	£10.00
NEW G9 Frame Panel	£10.00
NEW G11 IF Panel	£7.00
G8 Tuner Unit + Panel	£4.00
G8 Power Supply	£5.00
G8 6 Sloping PBU	£8.00
G8 IF & Chroma	£6.00
G8 Chroma	£3.00
G11 IF Detector	£3.00
G11 Selector gain module	£3
Complete CVC 825 Chassis (both panels)	£40.00
AEC V/Cap Resistor Unit UHF with IC	£1.25
SA5660 SA5670	£3.00
Z714 RANK IF Panels 6MHz 1 L.C.	£3.00
SL437F	£3.00
Z909B RANK IF Panels	£2.50
Export 5.5MHz 2 L.C.'s	£6.00
TBA1205B TCA27050	£6.00
K35 IF	£6.00
Z743 RANK IF Panel	£1.50
Export 5.5MHz 3 L.C.'s	£1.50
TBA750+SC9504P+	£1.50
SC9503P	£1.50
Pye G11 Front panel with transducer	£5.00
pots, tuner pots, 6 pb switch+lead	£5.00
Pye 6 button switch portable	£1.00
GEC V/Cap VHF/UHF tuner and IF+	£12.00
sound O/P PC 706B3 (Export)	£6.00
GEC Line O/P PC 659B3	£6.00
2110 GEC Power Panel	£8.00
GEC Power Supply (Export)	£10.00
G11 dynamic correction panel	£6
CVC 20 Front panel with sliders +	£4
mains input panel	£4
CVC 40 PUSH BUTTON ASSY with	£10
sliders: complete with lamp assy +	£9.00
pots	£9.00
CVC9 slider pots panel	50p
CVC 5 Mains on/off + 5 pots	£2
Universal Focus. Fits Pye, Thorn and	£2
Decca Units.	£2.00
T147 Rank tube base on panel	£1.00
Z718 Focus Unit	£1.50
T20 Focus Unit	£1.00
Large Type	75p
Decca Small	75p
KT3 Focus Unit	75p
K30 Focus Pot	75p
K30 Tube base on panel	£1.00
TX10 Focus Unit	£7.00
CVC 32 Focus Unit	75p
Fidelity Focus Unit 14R-14S	30p
3500 Thorn Focus Unit	£1.00
ITT Small for use with Split	£2.00
Z718 Bush Focus	£2.00
Diode	50p
Revlo TV12SP	50p
1600 Thorn EHT Rec and Lead	50p
TV13	50p
TV14	50p
TV18	60p
TV20	£1.00
TV45	50p
Thorn 14/1500 rec stick	5p
G11 drawer ASS 3 pots Mains switch	£2.00
and lead	£2.00
K30 Drawer Ass with pots cable	£1.00
form	£1.00
Line O/P panel GEC 2217/2218/2213/	£10
2214/2226/2227/2228	£10
4040 Clock	£1.00
7seg Red LED	50p
2 digit LED 8.8	50p
2 digit LED +1.8 with panel +	£1.00
MCL4511	£1.50
4700/63	£1.50
250/64	10p
CVC 20-25-30 Mains Switches	£3.00
Infra Red and Ultrasonic G11 Teletext Decoder Panel	£7.50
RANK & ITT Mains Remote On-Off Switch (720R)	£1.50
RANK & ITT Mains Remote Switch 2865 ohm	£1.50
RANK & ITT Remote Switch 2800 ohm	£1.50
G11 Mains Switch	50p
4 amp Mains Switch	25p
GEC Mains Switch 4 amp	30p
KT3 Mains Switch	£1.00
THORN Rotary Mains Switch	£1.00
G8 Mains Switch	75p
Thyrister 600/4 amp C1062	24p
G11 Preh Red LED P/Buton for C.H. Change	20p
RANK TOSHIBA Transducers TPC-2011	50p
Mains Switch ITT Long Type Print	75p
Mains Switch Philip Long Type TAG	75p
Mains Switch GEC Long Type TAG	75p
Thorn 12 or 24 volt battery converter for portable colour 17V	£6.00

Tube Thermaph 167	£1.00
Rank Scam Decoder Panel UHF & VHF	£13.00
TT15A	£13.00
<b>Multi-Caps</b>	
4,700/75 6 amp Rip	£2.00
350V 300M + 300M	£1.00
400V 400M	60p
350V 400M	60p
Thorn 3500	£1.00
175/100/100/350V	£1.00
KT3/200/25/25/385V	£1.00
300+300+150+100+50MFD	£1.00
350V	£2
47/220/350V	60p
150/150/100/100/100/320v	£2.00
2500/2500/63v	50p
150/200/200/300v	70p
400/400/200v	£1.70
300/100/100/16/275v	£1.50
100/200/325v	40p
150/150/100/375v	£1.50
300/300/100/32/320/300v	2.00
150/200/30v	50p
Jelly pot Thorn 00D4/013	£3
150/150/100/100/320v	£2.00
100/350 + 300/200/100/16/275v	£2.00
225+25/380 GEC	70p
200/100/100/350v	£1.50
500/500/25v	50p
150/150/100/300v	75p
200/150/150/300v	1.00
ITT 8 and 6 Push Button	£1.00
Pye 725 LOPTs	£6.00
Pye 731 LOPTs	£6.00
Thorn 8500-8800 LOPTs	£5.00
<b>CMD 800 Chassis. No tuner</b>	
CMD 800 Chassis. No tuner	£20.00
<b>TAG 226/600</b>	
TAG 226/600	50p
BD 650	50p
UPC 574	30p
BSS 38	30p
<b>WT 456</b>	
WT 456	£1.00
<b>LM 317T</b>	
LM 317T	30p
<b>AF 114</b>	
AF 114	50p
<b>FET Power VN88AF</b>	
FET Power VN88AF	50p
<b>PHILIPS SBC 469 Stereo Microphone</b>	
PHILIPS SBC 469 Stereo Microphone	£23.00
Meters Hills 520	£17.00
Meters Hills 420	£15.00
Infra-red Tester Handset	£12.00
<b>Infra Red</b>	
Infra Red	£1.00
Hanset Tester	£1.00
Works at 24 feet - Sound repeater.	
Works off 9 volt battery	£8.00
Fits in top pocket.	
<b>Repaired Handsets</b>	
Philips K4-K35, RC5350-RC5300,	£10.00
RC5370, RC5375, repaired same day	
RC4001 Full Remote KT3 K30 Teletext	£9.00
Handsets exchanged	
<b>GEC Full Remote Infra-red, 1983 models</b>	
GEC Full Remote Infra-red, 1983 models	£15.00
<b>Timers, 60 mins, small</b>	
Timers, 60 mins, small	£1.00
<b>G11 Ultrasonic Teletext Handset</b>	
G11 Ultrasonic Teletext Handset	£24.00
RC2014/1C2219H	£15.00
New Replacement for G11 Ultrasonic	
Full Remote	£12.00
Thorn 4000 insert with 7 buttons	£5.00
Decca RC 11	£14.00
Decca RC 12	£14.00
G11 Infra-red full teletext	£24.00
Dynatron-Full remote CTV 62, 63, 64	£19.00
Hitachi infra red handset	£18
Philips full remote KT3, 16C928/20C934;	
7228/7324; K12 26C 797/1ST 66K	
1826	£12.00
G11, Full remote top button assy.	£12.00
G11, Full remote repair service (exchange unit)	£12.00
Philips infra red full remote 9 channel for	£6.00
60 CP2605	
Philips infra red full remote 12 channel for	£12.00
60 CP2605	
K35	£3.00
KT3/K30 T/Text	£15.00
KT3/K30 Full remote	£15.00
KT3 Power supply	£4.00
Hitachi 8 button unit with resistor unit.	
Last year mod.	£7.00
GEC infra-red 2236-2026	£4.00
GEC push pad hand set button blobs	10p
each	50p
Pye & Philips handset KT3-K30 chassis.	
NO RC5150-RC5176-RC5171-RC5177.	
<b>Special Price</b>	

# SENDZ COMPONENTS

63 Bishopsteignton,  
Shoeburyness, ESSEX SS3 8AF  
SAME DAY SERVICE

All items subject to availability.  
No Accounts : No Credit Cards  
Postal Order/Cheque with order  
Add 15% VAT, then £1 Postage  
Add Postage for overseas

Callers: To shop at 212 London Rd.,  
Southend. Tel. 0702-332992

Open 9-12.30-6. GVMT + school orders accepted on official  
headings add 10% handling charge.

Tuner Units	
G8 6 Button Unit	£9
V/Cap Rank UHF Z776T/Unit	£5
V/Cap Rank UHF Z773T/Unit	£5
NEW G8 Tuner V/Cap	£3.50
T20 6 Push Button Unit	£7
ELC2000 on Panel	£2.50
ELC 6 Push Button Unit	£6
ITF 6 Push Button Unit	£6
DECCA 6 Push Button Unit	£6
GEC or Hitachi 6 push button unit 2110 Conversion	£8
GEC 2103 V/Cap	£5
ELC1043 (Ex Panel)	£3.75
ELC1042	NEW £5.50
ELC2000	NEW £4.00
ELC2004	NEW £8.00
ELC2006	NEW £6.00
GEC Tuner V/Cap Hitachi After 1979 ETS48, ETS47, ETS46, ETS41B	£8.00
ASTEC UM1183	£10.00
V314 (VHF)	£5.00
V317 (VHF)	£5
V334 (VHF)	£5
U321	£6
U341 UHF	£7.00
U342 (UHF)	£5
U411 UHF	£7.00
U.V. 411 Tuner	£10.00
U.V. 415	£7.00
U.V. 417	£7.00
Small V/Cap Mitsumi	£4.00
UHF	£3.00
Portable & rotary Tuners Sanyo & Mitsumi UHF	£5.00
NSF-UHF/VHF Varicap (old type)	£8.00
Mosfet UHF/VHF (new type)	£8.00
UEF-B31 Fidelity V/Cap T/Unit	£6.00
UHF-VHF V/Caps on panel Thorn Tuner PANEL with 6x100K pots & cursors NO TUNER	£1.00
HITACHI 20 Turn Pot	40p
U321 on panel	£6.00
Tuner unit VHS Sylvania GTR Videon MTS 900	£2.50
Mullard Video Modulator. Application, video tape recorders, TV cameras, video games, closed circuit TV, C.C.I.R. system. Data supplied.	£10.00
VT 100 Sound Tuner Kit. TV Viosound. The latest design in low noise fitted with DNR, RF output and audio	£30.00
Sylvania UHF F4720B	£6.00
Sylvania VHF 900	£6.00
Small Tuner DX 175-220MHz	

BF694	10p	BC107	10p	BC527	10p
BF758	30p	BC108	10p	BC532	10p
BF784	30p	BC109	5p	BC546	10p
BFT34	15p	BC113	10p	BC547	10p
BFT84	8p	BC114	10p	BC548	10p
BFW11	20p	BC115	10p	BC556	10p
BFX29	20p	BC116	10p	BC557	10p
BFX84	25p	BC117	20p	BC558	10p
BFY50	25p	BC119	20p	BC559	10p
BFY52	25p	BC125	10p	BC635	10p
BFY90	25p	BC126	10p	BCX31	25p
BLY49	25p	BC139	10p	BCX32/36 Pair	75p
BPW41	25p	BC140	20p	BCX32	25p
BRC116	25p	BC141	25p	BD116	25p
BRX43	15p	BC143	25p	BD124	30p
BRX48X	15p	BC147	25p	BD138	30p
BRX56	30p	BC148	10p	BD130Y (metal)	20p
BSS68	10p	BC149	10p	BD131	30p
BSY79	10p	BC153	10p	BD132/238	10p
BSY95a	10p	BC154	10p	BD135	25p
BTY80	20p	BC157a	10p	BD136	30p
BXX19	10p	BC158	10p	BD140	30p
BXX20	17p	BC159	10p	BD176	25p
FT3055	30p	BC171	25p	BD182	£1.00
TCE82	5p	BC172	10p	BD183	70p
2N930	5p	BC177	10p	BD202	60p
2N221	8p	BC178	10p	BD204	60p
2N222	8p	BC179	10p	BD207	60p
2N2906	10p	BC183	10p	BD211	20p
2N3055	40p	BC184	10p	BD222	30p
2N3566	10p	BC194	10p	BD228	30p
2N3702	10p	BC204	10p	BD226	20p
2N3711	10p	BC207	10p	BD234	30p
2N383	50p	BC212	10p	BD235	30p
2N3904	15p	BC213	10p	BD239	30p
2N4355	10p	BC214	10p	BD240	30p
2N4442	£1.00	BC237	10p	BD243c	30p
2N4444	£1.00	BC238	10p	BD244	30p
2N5296	40p	BC239	10p	BD250a	30p
2N5983	30p	BC250	8p	BD252	8p
2N6099	40p	BC251	10p	BD253B	50p
2N6109	40p	BC252	10p	BD331	30p
2N6130	50p	BC262	10p	BD373b	20p
2N6133	20p	BC263b	20p	BD416	20p
2N6348	20p	BC298	10p	BD433	25p
2N6398	10p	BC301	30p	BD437	25p
2X 2N6099 on heat sink	50p	BC303	30p	BD439	30p
2SA437	20p	BC307	7p	BD678	30p
2SB407 Sanyo	10p	BC308	7p	BD681	30p
2SB474	30p	BC309	7p	BD682	30p
2SB566	10p	BC327	10p	BF761	30p
2SC381	10p	BC328	10p	BF769	30p
2SC458	50p	BC328/338 pair	15p	BF819A	30p
2SC515	10p	BC338	10p	BF858	30p
2SC523	10p	BC347	10p	BF871	30p
2SC533	10p	BC349b	10p	BF893	15p
2SC5940	£1.00	BC350	20p	BF952	7p
2SC1030	£1.00	BC365	20p	BF979	15p
2SC1520	25p	BC384	20p	BF981	15p
2SC1546	20p	BC394	20p	BFR87	10p
2SC1725	20p	BC413	10p	BFS40	10p
2SC2068	20p	BC414	10p	BFT42	20p
2SC2073	8p	BC416	10p	BFT57	20p
2SC2122A	£1.00	BC440	30p	MR1366	20p
2SC2229	15p	BC455	25p	BRC-M-200	40p
2SC2688	30p	BC456	25p	BRC-M-300	40p
2SC3750	15p	BC462	10p	BRC 1330	30p
2SD180 TO3 8W/6A	15p	BC463	10p	BTC 3064	£1.00
2SD200	£2.00	BC478	10p	BT1822	£1.00
2SD787	30p			BT16016	£1.20
2SD880	30p			BT6018	£1.50
2SK30A	10p			ML237B	£1.50
				BT16218	£1.50
				BT18124	£1.00

Auto Changeover	
9000 Thorn Tuner on Panel	£7.00
THORN 1400 4P.B. Mech. Tuner	£5.00
THORN 1500 4P.B. Mech. Tuner	£5.00
THORN 1590 4P.B. Mech. Tuner	£5.00
THORN 3500 4P.B. Mech. Tuner	£5.00
THORN 8000 4P.B. Mech. Tuner	£5.00
THORN 8500 Mech. Tuner	£5.00
All new & boxed.	£4.00 each
Delay Lines	
DL20A 80p	DL600 £1.00
G8 (Old Type)	£1.00
DL600	£1.00
DL700	£1.00
UDL11	30p
KT 3 Luminescence	75p
Luminance Delay Line (CVC 45)	
10x630ma fuse	25p
10x500ma	80p
10x1 amp	80p
Co-Ax Joint	15p
Co-Ax Belling Lee Plug	12p
Co-Ax Splitter	£1.00
UHF Modulator CCIR	£3.00
Infra Red Emitting Diode	£3.00
NE286H Small Neon Lamps GEC & Philips	5p
Mullard 5 Watt Amps. LP1162	75p
New	

T.V. Tubes	
12"7110" 31/510 with coils	£5
4.5" tube NEC 120ANB4	£8
12" A31/300 Hitachi	£10
15" A38/170W Hitachi	£8
18" Hitachi PIL tube with scan coils 470 KCB22-TC03	£25
10" Black and white tube scan coils & line trans	£6.00

Integrated Circuits	
AC76003	£1.50
AM25LS23PC	10p
BAV40	40p

BTT8224	£1.00
BU22A	£1.00
CA270AE	50p
CA270CW	50p
CA270CE	50p
CA920AE	£1.00
CA1310	50p
CA3046	50p
CA3065Q	50p
CA3069AE	50p
CA3123	50p
CA3146	£1.00
CA3189	40p
CBF16848	50p
CD4510	30p
DM7492	30p
HA1196	40p
HA1370	£2.00
HA11223	30p
HEF4001	10p
HEF4011AF	10p
HEF4051B	10p
HEF4066	20p
HEF4528	20p
HD3890C	£3.00
K5731D 1001012	£1.00
LA3220	50p
LM1011N	£1.00
LM8361	£3.00
M913	£2.00
M1024=SA	£2.00
M1025=SA	£2.00
MC4769	£1.00
MC1307	75p
MC1312	75p
MC1330	75p
MC1349	50p
MC1352	£1.00
MC1358	£1.00
MC14002	£1.00
MC14013	75p
MC14016	25p
MC14066	25p
MC14514	50p
MC1748	80p
MEM4956	£1.00
ML231	£2.50
ET16016	£2.00
ML232	£2.00
ML236E	£1.00
ML237B	£1.00
ML238B	£4.00
ML239	£2.00
ML926	£1.00
MM5387	£1.00
MM5387	£1.00
MM5611	£1.00
MM5840	£3.00
MS4013	£6.00
MM5290N-4	£6.00
MM5108N	£4
MRI366	20p
N64100	£1.00
NE588C	£1.00
NE555	60p
HD3890C	£3.00
IL-1	20p
OPT600	20p
OPT601	£1.00
SAA611	£1.00
SAA661	£1.75
SAA1020	£4.00
SAA1021	£4.00
SAA1024	£2.50
SAA1025	£2.50
SAA1073	£3.00
SAA1074	£3.00
SAA1075	£3.00
SAA1124	£2.00
SAA1130	£2.50
SAA1174	£2.50
SAA1176	£3.00
SAA1203	£4.00
SAA1251	£3.00
SAA1272	£3.00
SAA1276	£3.00
SAA3027P	£4.00
SN76119A	£1.50
SAB3013	£2.00
SAB3210	£2.00
SAB4209	£2.00
TBO0124	£1.00
SAA5001A	£1.50
SAA5010	£2.20
SAA5021	£3.50
SAA5030	£5.00
SAA5040	£3.50

Thyristors	
BT15100R	80p
BT106 Plastic	30p
BT106 Metal	£1.20
BT119	£1.00
BT120	£1.00
BR4443	75p
G11 Thyristor	60p
Decou 80-100	60p
2N4444	£1.00
MCR72-6	25p
GT112	£1.00
TF320M	£1.00
HC8441	£2.00
17052	£2.00
170881	£2.00
170897	£2.00
17083R	£2.00
SP2M	50p
MCR72-6	50p

Filters	
5-5MHz	15p
6MHz	30p
I.C. Heat Sink	20 for £1
20xTO5 Heat Sink	£1.00
CVC 9 power supply board	£1.50
CVC 202 mains panel	£2.00
ITT Mains Filter .125W/ CVC 20 to 45 chassis	50p
Pots 10 k with Switch	25p
Mullard Surface Wave Filter RW 153P Colour TV Filter	40p
Mullard Surface Wave Filter RW 154 Colour TV Filter	40p

Thermistors	
GN Degaussing	35p
Philips type VA1104	£3.00
ITTP226312	15p
PTH451 AOR	15p
PT37P Fils Pte & PT34	20p
Degaussing Thermistor (fits most sets)	25p
GEC Double Thermistor	25p

SAA5040A	£3.00
SAA5043	£4.00
SAA5050	£3.50
SAF1032p	£2.50
SAF1039	£2.00
SAS560	£2.00
SAS660	£1.00
SAS670	£1.00
SAS580	75p
SAS590	75p
SAS3210	£2.00
SL437F	£4.00
SL901P	£4.50
SL918	£4.50
TA7122	£1.15
TAA320A	50p
TAA470	£1.50
TAA570	75p
TAA611B	£1.00
TAA621	£2.00
TAA661	£1.00
TAA641	£1.50
TA7108P	£1.00
TA7117	50p
TA7120P	50p
TA7315A	50p
TA7607AP	50p
TA7609P	50p
TBA120A	40p
TBA120AS	40p
TBA120SA	50p
TBA120B	40p
TBA120SB	40p
TBA120T	50p
TBA120U	£1.00
TBA120Q	30p
TBA120C	40p
TBA1441	£1.00
TBA231	75p
TBA405Q	50p
TBA360Q	£1.00
TBA396	75p
TBA440P	£1.00
TBA1440C	£1.00
TBA480Q	£1.00
TBA501	£2.00
TBA530	£2.00
TBA540	£1.00
TBA550Q	£1.75
TBA560CQ	£1.00
TBA570	£1.50
TBA625	£2.00
TBA641	£2.00
TBA651	£2.00
TBA673	£2.00
TBA720A	£1.50
TBA750Q	£1.50
TBA780	£1.50
TBA800	£1.50
TBA810AP	60p
TBA811S	60p
TBA820	60p
TBA890	£1.00
TBA920	£1.50
TBA920Q	£1.50
TBA950	£1.50
TBA990Q	£2.00
TMS1943 N2L (clockchip)	£1.00
TMS9013	£4.00
TMS9901	£1.00
TMS2708JG45	