

A BEGINNER'S GUIDE TO RADIO

1/-

Vol 29 No. 565

DECEMBER, 1953

EDITOR:

F.J. CAMM

PRACTICAL WIRELESS

The  FULL-COMPASS
Electronic ORGAN




IN THIS ISSUE :

AN ECONOMY QUALITY AMPLIFIER
A REMOTE CONTROL UNIT
A VARIABLE BANDWIDTH FILTER
A SUBSTITUTION CHECKER

INTERFERENCE-FREE RADIO
GRID DRIVE
MODERN SHORT-WAVE BATTERY
RECEIVERS

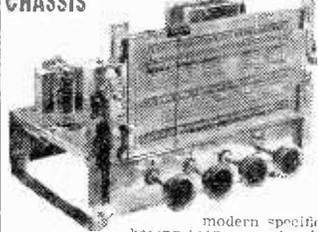A COMPLETELY ASSEMBLED "ALL-WAVE" SUPERHET CHASSIS



modern specification, great attention has been given to the quality of reproduction which gives excellent clarity of speech and music on both Gram and Radio, making it the ideal replacement chassis for that "old Radiogram," etc.

MODEL B.3.—A 3-valve 3 waveband Superhet Receiver, for operation on A.C. mains 100-120 volts and 200-250 volt, employing the very latest miniature valves. It is designed to the most modern specification, great attention has been given to the quality of reproduction which gives excellent clarity of speech and music on both Gram and Radio, making it the ideal replacement chassis for that "old Radiogram," etc. Brief specifications:—Model B.3.—Valve line up, 6BE6, 6BA6, 6AT6, 6BW6, 6X4. Waveband Coverage, Short 10-50, Medium 187-550, Long 900-2,000 metres. Control(s): (1) Volume with on/off; (2) Tuning (five-wheel type); (3) Wave change and Gram; (4) Tone 3 position switch operative on Gram and Radio). Negative Feedback is employed over the entire audio stages. Chassis size 11in. x 7in. x 8in. high. Dial 4in. x 4in. Price, complete and READY FOR USE, excluding speaker, £12 12-. (Carr. and Pkg. 7/6 extra.)

MODEL B.3. P.P.—This model is the B.3. Receiver but incorporates two 6AV6 VALVES in PUSH-PULL, resulting in really excellent quality reproduction up to approximately 6 watts. Price £15 15-. (Plus 7/6 carr. and ins.)

MODERNISE YOUR OLD RADIOGRAM FOR

£ 23


We offer this Autochanger complete with Model B.3 3-waveband as advertised together with 10in. p.m. Speaker for £23 plus 10/- carr. and ins. or with B3P1 Model for £26 --, plus 10/- carr. and ins.

£9/19/6

(plus 7/6 carr. and Ins.) Normal price £19 10 0

- With separate Crystal-heads for STANDARD and L.P. Records.
- Incorporating Pick-up Weight Adjustment.
- Will autochange on 7in., 10in. and 12in. Records not intermixed.
- Minimum baseplate size 15in. x 12in. with height above 4in. and below 6in. complete.
- Brand new in maker's cartons, complete with mounting instructions.

3-SPEED AUTOCHANGE UNIT

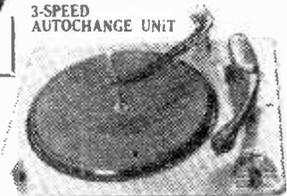


The Collaro 3RC, 521

"PERSONAL SET" BATTERY ELIMINATOR

A complete kit of parts to build a Midget "All-dry" Battery Eliminator, giving approx. 60 volts and 1.4 volts. This Eliminator is for use on A.C. mains and is suitable for any 4-valve Superhet Receiver, for requiring H.F. and L.T. voltages as above or approx. to 60 volts. The kit is quite easily and quickly assembled and is housed in a light aluminium case, size 4in. x 14in. x 3in. Price of complete kit with easy-to-follow assembly instructions, 42/6. In addition we can offer a similar COMPLETE KIT to provide approx. 90 volts and 1.4 volts. Size of assembled Unit 7in. x 2 1/2in. x 1 1/2in. Price 47/6.

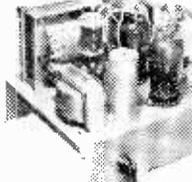A 4-VALVE QUALITY "PUSH-PULL" 6-8 watt AMPLIFIER for A.C. mains.



Incorporating Negative Feedback, Filter Input Circuit and employing 6V6s in Push-Pull. A simple arrangement is provided to enable either a magnetic-crystal or lightweight pick-up to be used, and is suitable for use with Standard or long-playing records. A tone control is incorporated, and the 10-watt output transformer is designed to match 2 to 15 ohm speakers. The overall size of the assembled chassis is 10in. x 8in. x 7 1/2in. high and full practical diagrams are supplied. Price, including drilled chassis and valves of complete kit, £6 17/6. Price of assembled chassis, supplied ready for use, £3 12/6. Full descriptive leaflets are available separately for 1/-.

COMPLETE KIT for 12 WATT HIGH FIDELITY "Push-Pull" AMPLIFIER

Designed for A.C. mains 200 to 250 volts, employs 6 valves plus remote controlled negative feedback, and comprises a main amplifier chassis and a remote controlled Pre-amplifier and Tone Control Unit, incorporating four control—bass, treble, main volume or mixing control, and a radio, gram, microphone selector switch. This control unit measures only 7 x 4 x 2in. The measured frequency range of the amplifier with this unit shows an excellent response from 14,000 cycles down to 20 cycles, the bass and treble controls allowing independent control of gain at both ends of the frequency range from zero to a gain of 50. It can be seen, therefore, that ample correction is provided to suit any type of pick-up with any type of recording. Input voltage for maximum output is 70 mV. 6.3 volts at 2 amps, and 30 mA. H.T. is provided for tuning unit.



etc. Price of complete kit, Amplifier and Control Unit, including drilled chassis and valves—£14. Complete specification and layout 2/-. We can also supply completely assembled and ready for use at £17. Please add 7/6 carr. and insurance. THIS AMPLIFIER COMPARES WELL WITH THE WILLIAMSON AND SIMILAR DESIGNS AT A FRACTION OF THE COST.

GENUINE REDUCTION

- The Collaro Model 3RC 514, 3-speed non-autochange Record Player, (Normal price £12 6/.)

£6/19/6

(Plus 5/- carr. and ins.)


- Incorporating the NEW ORTHO-DYNAMIC HI-FI Magnetic Head filled with TWIN ALLOY STYLUS AND MATCHING TRANSFORMERS, TOGETHER WITH PICK-UP WEIGHT ADJUSTMENT. These Units are quite new and contained in maker's original cartons, complete with mounting template.



A COMPLETE 4 VALVE T.R.F. CHASSIS

including a 5" P.M. SPEAKER AND VALVES

£6/9/6 (plus 7/6 carr. and ins.)

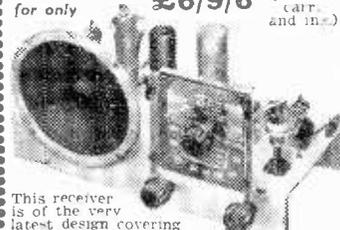

This receiver is of the very latest design covering both Long and Medium Wavebands and includes the modern BVA miniature valves. The line up being 12BA1—12AT6—12AB—5W4. It incorporates Permeability Tuned Coils thus ensuring excellent selectivity and sensitivity. The overall size of the complete chassis including Speaker is 10in. x 11in. x 8 1/2in. An attractive Bakelite Ivory finished Cabinet, size 11in. x 3 1/2in. x 6in. is available for 18/6 (plus 2/6 carriage and insurance).

A DUAL CHANNEL PRE-AMPLIFIER and TONE CONTROL UNIT

This comprehensive PRE-AMPLIFIER and TONE CONTROL UNIT provides full control of Bass and Treble in conjunction with a main Volume Mixer Control. Can be used with any Amplifier and any Pick-up, the range of frequency control provided by the unit affording ample compensation for all types of Pick-up and all natures of recordings, i.e., English, American and Long-Playing, without recourse to Pick-up correction. The extreme flexibility of the Bass and Treble Controls is such that the level of Bass and Treble can be set to suit any conditions irrespective of the volume output of the Amplifier. The Unit measures only 7in. x 4in. x 2in., including self-contained Power Supply, and can be accommodated either on or away from the main Amplifier, i.e., in the front panel of a Cabinet or any other position. Price, including drilled chassis, valves (6SN7 and 6J5), £3 18/9. Complete assembly data is available separately for 1/3. Completely assembled and ready for use, 25/5-.

STOP PRESS !!

A COMPLETELY ASSEMBLED CHASSIS OF A 3 WATT A.F. AMPLIFIER WITH SELECTIVE FEEDBACK for A.C. Mains operation

£4/9/6 (plus 5/- carr. and ins.)

- Designed for good quality Gram. reproduction up to a maximum output of 3 Watts.
- The selective feedback circuit incorporates separate Bass and Treble Controls.
- New Valves are used, the line up comprising the new Mullard types EF90, EL41, EZ40.
- Suitable P.M. Speakers are available at 16/-, 18/6, 25/- and 34/4.

Taylor Model 45B Valve Tester

A comprehensive valve tester which may be used to measure the mutual conductance of most types of British, American and Continental receiving valves. Supplied complete with detailed instruction book and separate valve chart giving full testing data for over 3,000 different valves. Long scale, sensitive moving coil meter with illuminated dial.

TESTING FACILITIES :

Mutual Conductance. Two ranges are provided. 0-3 mA/V and 0-15 mA./V.

Cathode Leakage. Tests for Heater/Cathode insulation up to 10 megohms, with heater hot.

Emission. Rectifiers and Diodes may be tested for emission. Inter Electrode Shorts. Short circuits between electrodes are shown on the meter.

Heater Continuity. Meter indicates continuity of heater or filament.

Gas Test. Press button "gas" test shows abnormal positive or negative grid current.



PRICE **£25 - 10 - 0**

or £3/16/6 deposit and 10 monthly payments of £2/8/9.

PROMPT DELIVERY

TAYLOR PRODUCTS INCLUDE :

Multirange A.C./D.C. Test Meters ; Signal Generators ; A.C. Bridges ; Circuit Analysers ; Cathode Ray Oscillographs ; High and Low Range Ohmmeters ; Output Meters ; Insulation Testers ; Moving Coil Instruments.

Write for catalogue.

ELECTRICAL INSTRUMENTS LTD.

MONTROSE AVENUE, SLOUGH, BUCKS. Tel: Slough 21381. Grams: Taylins, Slough.

BRITISH MADE

BRIMAR VALVES

*More Reliable
than EVER*



Brimar's long experience in the manufacture of special quality TRUSTWORTHY valves is now being reflected throughout the entire Brimar Range.

Improved production methods, new and better assembly jigs, tighter control on the composition of materials, and the closer supervision of vital processes have resulted in valves with more uniform characteristics, greater mechanical strength and a higher standard of reliability as shown in the 6AL5.

This valve and its direct equivalents have been used for sound and vision detection and noise limiting in the majority of T.V. Receivers manufactured since the war and is extensively employed in this season's models.

Because of its improved performance the Brimar 6AL5 is also used widely in Industrial Electronic Equipment, Computers, Navigational Aids, Test Equipment, etc.

Use the **BRIMAR 6AL5**—the improved replacement
—at **NO EXTRA COST**



now is the time to

BRIMARIZE!

BRIMAR	FERRANTI	MAZDA	MARCONI OSRAM	MULLARD
6AL5	DD5	6D2	D77 D152	EB91

Standard Telephones and Cables Limited FOOTSCRAY, KENT

FOOTscray 3333

AS SPECIFIED.


BY THE DESIGNER OF THE "BIRTHDAY SET"



S.L.8 SPIN
WHEEL DRIVE

S.L.8. Spin Wheel Drive, precision slide rule with 3 band scale gives perfect control. Ratio 24-1. Constant velocity coupling eliminates Condenser strain and provides isolation from vibration and noise. Glass scale $9 \times 4\frac{1}{2}$ with florentine bronze escutcheon. Price 27/6 complete.

E.2 TYPE
CONDENSER
AS SPECIFIED,
14/-.

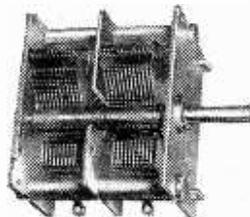

GANG CONDENSERS. Available as 1, 2 or 3 gang, 490 p.F nominal capacity with Cadmium plated steel frame, aluminium vanes; matched and standardised to close limits. Low loss non-hygroscopic insulation. Prices from 9/-.

Other capacities available Please write for further details.



KINGSWAY · WADDON
SURREY · ENGLAND

Telephone · CROYDON 2754-5

JACKSON BROS.

(LONDON) LIMITED

MAKERS OF
PRECISION COMPONENTS

Telegrams: WALFILCO,
SOUPHONE, LONDON

BUILD A TAPE RECORDER THAT REALLY WORKS WELL

Designed by the man who gave us the "Viewmaster" home-constructed television, and shown stage-by-stage in the same clear, fool-proof manner—send to:

Smith's
of
EDGWARE ROAD

For Flack's 28-page "Soundmaster" booklet with six-stage construction sheets, amplifier circuit, price lists, etc.

6/6 post free.

H. L. SMITH & CO., LTD.

287/9 Edgware Road, London, W.2.

Tel.: PADDINGTON 5891. Hours: 9 to 6.

Thursday 1 o'clock.

Near Edgware Road Stations, Metropolitan and Bakerloo.

R O M

INDUCTANCE BRIDGE KIT 42/6

50 u/Hy.—1,000 u/Hy.
1,000 u/Hy.—20 M/Hy.
20 M/Hy.—400 M/Hy.
400 M/Hy.—8 Hy.
5 Hy.—100 Hy.

TREBLE AND BASS BOOST CHOKES
VIDEO CHOKES; SCRATCH FILTERS
R.F. COILS; SMOOTHING CHOKES
WHISTLE FILTERS; AUDIO, R.F.
A.C. INDUCTANCES IN GENERAL

RES/CAP. BRIDGE KIT 31/6

5 Megohms—50,000 ohms.
100,000 ohms—1,000 ohms
1,000 ohms—10 ohms

50 mfd.—2 mfd.
1 mfd.—.01 mfd.
.01 mfd.—.0005 mfd.

BOTH KITS ARE CALIBRATED READY FOR USE
Each fully variable range separately scaled for direct reading

I.F. ALIGNER KIT 15/-

Tunes over 465 Kc/s range of I.F. frequencies.


PRE-TUNED READY FOR USE

Post & packing 1/6 in each case. Cash with Order or C.O.D.

SIMPLE ASSEMBLY. FULL INSTRUCTIONS & DIAGRAMS.
ALL KITS ARE SELF-CONTAINED

**RADIO MAIL 4, RALEIGH STREET,
NOTTINGHAM**

Illustrated Leaflets on request.

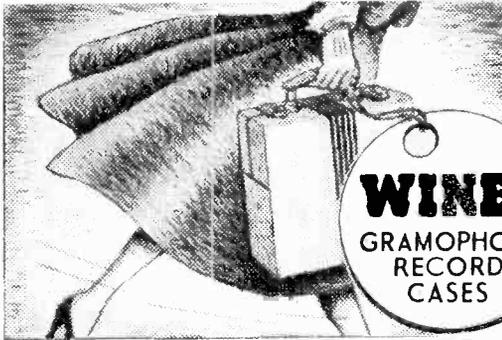

WINEL
GRAMOPHONE
RECORD
CASES

Essential for the Safe Storage, Simple Reference and Handy Carriage of Gramophone Records. Wide assortment of Sizes and Colours. Write for illustrated catalogue, and name and address of nearest Retailer.

HENRY ELWIN LTD.
(DEPT. M2)

Makers of Top Quality Record Cases, Albums, Cabinets and Covers.

NOTTINGHAM

SOUTHERN RADIO'S WIRELESS BARGAINS

- TELESONIC** 4-valve battery portable. Complete with 4 Hivac valves. In metal carrying case. Easily convertible to personal portable. £2, including conversion sheet.
- TRANSMITTER-RECEIVERS**, Types "38" Mark II and III. "18" Mark III still available as previously advertised. Also R109 RECEIVERS. See last issue of "P.W."
- MINISCOPES**, G.E.C. M861B, brand new, complete in carrying case with plugs. £12/10.-
- BOMBSIGHT COMPUTERS**. Just arrived, new parcel of this useful unit. Ex-R.A.F. Brand New. Contains GYRO MOTORS, REV. COUNTERS, GEAR WHEELS, etc., etc. Worth pounds to model makers, experimenters, etc., etc.. £3/5.-
- CRYSTAL MONITORS**, Type 2. Brand new in transit case. Less Crystals. 8/-
- LUFBRA HOLE CUTTERS**, adjustable $\frac{1}{8}$ in. to $\frac{3}{8}$ ins. For use on wood, metal, plastic, etc.. 5/9.
- THROAT MICROPHONES**. Brand new. Magnetic with Long Lead and Plug. 4/6. Button type, ex U.S.A. 4/6.
- RESISTANCES**. 100 assorted useful values, wire-ended, 12/6 per 100.
- CONDENSERS**. 100 assorted values tubular, metal and mica. 15/- per 100.
- PLASTIC CASES**, 1 1/4 in. by 10 1/2 ins. Transparent. Ideal for maps, display, photos, etc.. 5/6.
- STAR IDENTIFIERS**, Type I A-N. Covers both hemispheres. Complete in case. 5/6.
- WESTCOTTS WX-6 and W112**, 1/- each.
- AERIAL FILTER UNITS**, Marconi P.O. specification. 4/6.
- CONTACTOR TIME SWITCHES**, 2 impulses per sec. Thermostatic control. Complete in sound proof case, 11/6.
- REMOTE CONTROL**, for use with above, 7/6.
- DIMMER CONTROLS**. Bakelite covered, wire wound. Brand new, 1/3 each.
- MAGNETIC RELAYS SWITCH**, bakelite, 5c/723. 2/5.
- SPECIAL OFFER TO EXPERIMENTERS**—TWELVE METERS and AIRCRAFT INSTRUMENTS. Only needs adjustment or cases broken. Twelve Instruments (including 3 brand new aircraft instruments), 35/-.

Full list of Radio Books 21d.

HUNDREDS OF FURTHER LINES FOR CALLERS.

SOUTHERN RADIO SUPPLY LTD.,

11, LITTLE NEWPORT STREET, LONDON, W.C.2.

GERrard 6653.

The solder for all
**HOME TELEVISION
CONSTRUCTOR SETS**

Designers of television constructor sets know that the efficiency of their equipment depends on the solder used by the constructor—that's why they recommend Ersin Multicore for trouble-free, waste-free soldering. Ersin Multicore, the only solder containing three cores of extra-active, non-corrosive Ersin Flux, is obtainable from all leading radio shops. Ask for Cat. Ref. C.16018, 18 S.W.G. 60 40 High Tin Television and Radio Alloy. The size 1 Carton contains 55 feet of solder, costs 5/-.



Ersin Multicore Solder

In case of difficulty in obtaining supplies, please write to:

MULTICORE SOLDERS LTD. MULTICORE WORKS, MAYLANDS AVE., HEMEL HEMPSTEAD, HERTS. • Boxmoor 3636 (3 lines).

BARTON'S (Radio) LIMITED


(DEPT. PW) 42 . TOTTENHAM COURT ROAD . LONDON . W1
 QUALITY GOODS • MONEY BACK GUARANTEE • PROMPT DESPATCH

TERMS OF BUSINESS: Cash with order, (or C.O.D. Post item only); all orders for small items totalling over £2 post free unless otherwise stated.


Telephones: LANGHAM 1151/2

BUILD YOUR OWN RADIO!

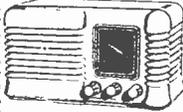We can supply all the parts (including valves, 3in. moving coil speaker, cabinet, chassis and everything down to the last nut and bolt) to enable YOU to build a professional looking radio at a total cost of **£5.15.0** plus 26 of this is a 3 valve plus metal rectifier T.R.F. Receiver with a valve line up as follows—6K7 (H.F.), 6J7 (Det.) and 6V6 (Output).



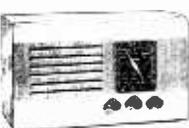The dial is illuminated and when assembled the receiver presents a very attractive appearance. Coverage is for the medium and long wave-



bands. Operates on 200/250 volt A.C. mains. The chassis is punched and drilled ready to mount the components. There is a choice of any of three attractive cabinets 12in. long, 5in. wide by 6in. high as follows—Either Ivory or Brown Bakelite. Wooden, finished in walnut. Complete and easy to follow point to point, and circuit wiring diagrams supplied. Circuit diagrams and priced parts list available separately if required at 1/-.

To those who want the above Receiver ready built we can supply it at **£6.19.6** plus 36 p.k.g., carr., ins.

SENSATIONAL REDUCTIONS!

The Famous COLLARO RC3/521 GRAMOPHONE UNIT

A 3-speed Auto Changer, complete with two separate high fidelity Crystal Plug-in heads, one for long playing records and one for standard records. Will play 7" 10" and 12" records. Each head is fitted with a permanent jewel tipped stylus. These Units are BRAND NEW, guaranteed and in original manufacturers cartons.



£9.19.6 plus 76 packing, carriage and insurance. (Normal List Price £16 10 0)

The COLLARO AC3/514 GRAMOPHONE UNIT—3 speed

Single Record Player Complete with LATEST ORTHO-DYNAMIC MAGNETIC PLUG-IN PICK-UP HEAD and matching transformer. The unit is designed for playing L.P. and Standard Recordings. Either Stylus can be brought into use by simply pressing a switch.

A limited quantity of these are available at the ridiculously low price of—**£6.19.6** plus 76 p.k.g., carr., ins.

MICROPHONE TRANSFORMERS
 Ratio 100:1. Mu. metal. Has innumerable uses, 1/11. plus 6d. post, packing.

MAINS TRANSFORMERS
 Semi shrouded drop through type fitted with tapped voltage panel, primary tapped 200/10 v., 220/30 v., 240/50 v., 350/0-350 at 150 mA. L.T.'s 6 v. at 2-3 amps., 4 v. at 2-3 amps., 30 v. at 0.5 amps. Dimensions above chassis 3in., below chassis 3in., width 3in., depth 3in. Price 22/6, plus 1/6 packing and postage.

SELENIUM RECTIFIERS
 300 v. 75 mA., can be used in series or voltage doubling to give any required voltage. 8/6, plus 6d. post and packing.

LOUDSPEAKERS

PLESSEY, 6in. dia. 3 ohms	12/6
8in. dia. 3 ohms	13/6
FLAC, 5in. dia. 3 ohms	13/6
10in. dia. 3 ohms	22/6
All plus 1/6 p.k.g., carr.	
TRUVON, 12in. dia. 2-3 ohms. BRAND NEW IN MANUF. CARTON, 47/6 plus 2/6 p.k.g., carr.	

MAINS NOISE SUPPRESSOR KIT
 Consisting of 2 specially designed chokes and 3 condensers. Extremely effective, cuts out all mains noise. Can be assembled in existing receiver or separately as desired. Complete with plus 1/- circuit diagram. **5/9** p.c.

FILAMENT TRANSFORMERS
 6.3 v. 1 amp. 5/11 ; 6.3 v. 3 amp. 8/11 ; 6.3 v. (with 4 v. and 2 v. tappings), 1 amp. 7/6. All plus 1/- p.p.

- T/V TECHNOLOGY
- RADIO ENGINEERING
- ELECTRONICS
- RADIO SERVICING

There's a big future in T.V. and Radio. Act now! Increase your knowledge. Back up experience with a sound theoretical background. I.C.S. offer courses of instruction in—

T/V TECHNOLOGY
 ADVANCED SHORT-WAVE RADIO
 RADIO ENGINEERING
 RADIO SERVICE ENGINEERING
 RADAR
 ELEMENTARY ELECTRONICS

I.C.S. will also coach you for the following examinations:—

B.I.R.E.; P.M.G. Certificate for Wireless Operators; Radio Servicing Certificate (R.T.E.B.); C. & G. Telecommunications, etc., etc.

DON'T DELAY—WRITE TO-DAY for free descriptive booklet, stating which subject or examination interests you. Fees include all books needed. Examination students coached until successful. Reduced terms for H.M. Forces.

Dept. 170D, I.C.S., 71, Kingsway, W.C.2.

INTERNATIONAL CORRESPONDENCE SCHOOLS,
 (Dept. 170D), International Buildings, Kingsway,
 London, W.C.2.

Please send booklet on.....

Name..... Age.....

(Block letters, please)

Address.....



G2AK This Month's Bargains G2AK

MULTI-METER BASIC UNIT.—400 Microamp. F.S.D., scaled 8 ranges A.C./D.C. volts. HI and LO ohms, complete with rectifier made by Triplett. U.S.A. Only 32/6, post free.

SHADED POLE MOTORS for tape recorders or gram. units. With voltage tapping plate 200/250 volts, 3-hole fixing. Our price 12/6 ea. or 21/- pair. Post and pkg. on either, 1/6.

SPECIAL TRANSFORMER OFFER.—Pri. 115, 210, 240v. Secs. 260/260 v. 100 mA., 6.3 v. 3 A. and 6.3 v. 1 A. for 6X5 rectifier. Universal mounting. Limited quantity. 17/6 ea., post free.

Special Offer. T.V. 1/2 in. Coaxial Cable, 11d. yd. or 9/6 per doz. yds., or 9d. per yd. in 100-yd. coils. P. & P., 1/6.

Special Valve Offer. Kit of 4 midget valves 1.4 v., 1 each 1S5, 1R5, 1T4 and 1S4, 30/- or 8/6 ea. separately. 807's, 12/6 ea. or 2 for 22/6. Most of the 1.4 v. range available at 8/6 ea.

L.T. Transformers. 230 v. Primaries. 12 v. 1.5 A., 12/6; 6.3 v. tapped at 4 v., 1.5 A., 8/-; 6.3 v. 2.5 A., 12/6; 6.3 v. 6 A. and 5 v. 4 A., 25/-.

Twin Feeder. 300 ohm 150 watt rating, 6d. yd. Minimum quantity, post free, 20 yards; otherwise, P. & P., 1/6.

Morse Practice Sets, with double action buzzer, output for phones, excellent key, require only 4 1/2 v. battery. As new, 7/6 ea. P. & P., 1/-.

Germanium Diodes. B.T.H., 2/-; G.E.C., 2/6 ea.
Soundmaster, Lane, Bradmatic and all other Tape Recorder parts available. Ex-stock. State your requirements.

Deaf-Aid Crystal mike units, 12/6 ea.

V.H.F. FANS. Air space Co-axial Cable. 150 ohm, good to 600 Mc/s; normal price, 3/11 per foot. Our Price, 20 yard coil. £1. Very limited quantity available.

Postage free on all orders over £1 except where specifically stated. **PLEASE PRINT YOUR NAME AND ADDRESS.**

C. H. YOUNG, G2AK

All callers: 110 Dale End, Birmingham (CEN 1635)

Mail Orders: 102, Holloway Head, Birmingham 1 (MID 3254)

THE SENSATION OF THE RADIO SHOW


A chorus of praise from
both experts and public!

Stentorian HIGH FIDELITY UNIT

When we showed our new High Fidelity units at the Radio Show, we knew we had something exceptional to offer — the experts who had tested these speakers had been most enthusiastic about their merits.

But — we did not anticipate such an overwhelming response from the public, far in excess of any reaction we have experienced in the past 27 years. Without exception, visitors to our Stand were amazed that a performance of so high a quality could be made available at popular prices.

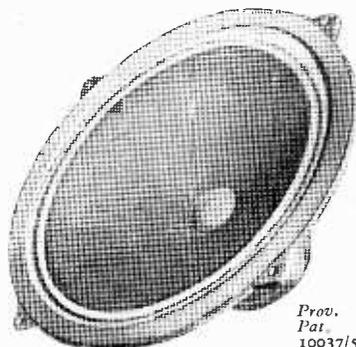This new range has been developed to take full advantage of the television sound transmissions and high fidelity recordings now available. The cone is made from uncured cambric and bonded pulp, the whole being completely cured together and made into one composite cone by a new manufacturing process. The speakers are all fitted with high flux density Alcomax magnets and are completely dustproof.



Prov.
Pat.
10037/53

- Model H.F. 610 (6" unit) £2 · 10 · 6
- Model H.F. 810 (8" unit) £3 · 0 · 6
- Model H.F. 912 (9" unit) £3 · 7 · 0
- Model H.F. 1012 (10" unit) £3 · 13 · 6

Including Tax

Write for leaflet giving full technical details and the experts' opinions, or ask your dealer to demonstrate. Alternatively, these speakers may be heard at our London Office, 109 Kingsway, W.C.2, any Saturday between 9 and 12 noon.



WHITELEY ELECTRICAL RADIO CO. LTD · MANSFIELD · NOTTS

SOUND MASTER SERVICE

The Sound Master is an entirely new Portable Tape Recorder which has been produced especially for the Home Constructor by the designer of the famous View Master Televisor.

Full constructional details are now available.

INSTRUCTION ENVELOPE,
6/6d. post free.

WRITE NOW for our fully detailed price list.

We carry full stocks of all items needed for the Sound Master and can offer a

RETURN OF POST SERVICE.

FULL HIRE PURCHASE FACILITIES
AVAILABLE on complete or part kits.


WATTS RADIO
(Weybridge), LTD.,

8, Baker Street, Weybridge, Surrey.

Armstrong

Offer to the enthusiast who requires
the highest quality reproduction their
increasingly popular

2 outstanding
new
models

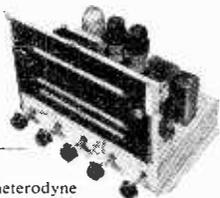

FC.38 8 Valve Superheterodyne chassis giving 8 watts push-pull output with negative feedback and separate BASS and TREBLE lift controls. WAVE RANGE—16-50 metres, 190-550 metres and 1,000-2,000 metres. PRICE—£23 13s. including tax.

RF.41 10 valve Superheterodyne chassis giving 10 watts push-pull output with negative feedback and separate BASS and TREBLE lift controls, also a highly sensitive R.F. stage before the mixer. WAVE RANGE—12-90 metres, 190-550 metres and 800-2,000 metres. PRICE—£31 19s. 8d. including tax.



Both High Class Chassis at an economical price giving AMAZING Realistic Radio and Record Reproduction from the modern records.



ARMSTRONG WIRELESS & TELEVISION CO. LTD.

WARLTERS ROAD, HOLLOWAY, LONDON, N.7.


Telephone NORTH 3213/4.

2 New MODELS

~~acos~~ quality crystal
microphones at a
reasonable price

MIC 33-1: A crystal hand or desk omni-directional microphone for the high quality public address and tape recording field, incorporating a specially designed acoustic filter giving a response flat from 30 to 7,000 c.p.s.


RETAIL PRICE £2-10-0d.

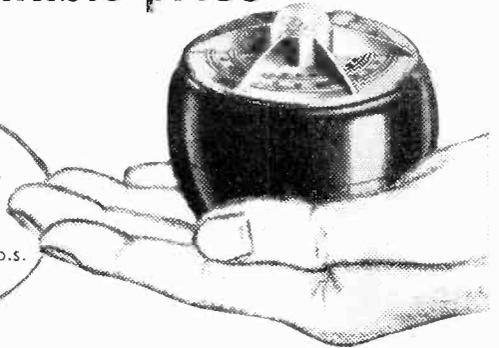

Ideal for tape and disc recording,
P.A. and amateur radio.

MIC 35-1: A general purpose hand microphone of robust construction with substantially flat response from 50 to 5,000 c.p.s. Suitable for recording apparatus. Public Address equipment etc.

RETAIL PRICE £1-5-0d.

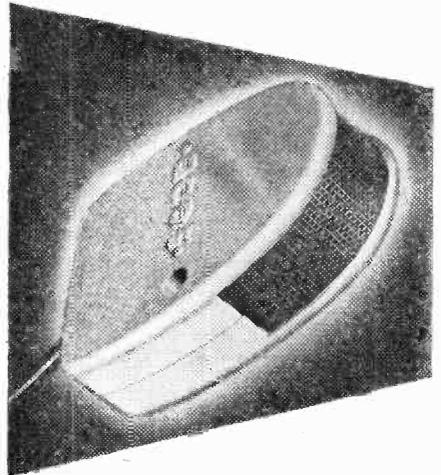

always well ahead

ACOS devices are protected by patents, patent applications and registered designs in Great Britain and abroad.

GOSMOCORD LIMITED • ENFIELD • MIDDLESEX

Practical Wireless

EVERY MONTH
VOL. XXIX, No. 566, DECEMBER, 1953

Editor F. J. CANN

22nd YEAR
OF ISSUE

COMMENTS OF THE MONTH

By THE EDITOR

TV Interference with Sound Radio

EVER since the TV service began to develop viewers have complained of interference from the ignition systems of motor-cars, electro-medical apparatus, hair dryers and vacuum-cleaners. Little publicity has been given to the interference with ordinary broadcast reception caused by the timebases of TV receivers. This form of interference is far more widespread than is generally known, because it would appear that listeners are less vocal in their complaints than viewers. Now that there are over 2,500,000 television receivers in operation, the problem has reached proportions of national dimensions and it is not surprising that the Radio Industry Council has appointed an Interference Suppression Sub-committee to deal with the matter. Many readers of this paper also operate television receivers, and they should take care to shield all those parts of TV receivers which are prone to cause trouble in this direction. This does not imply that home-constructed receivers are more likely to cause this form of interference than commercial receivers. On the contrary, all receivers designed in our laboratories and described in our associated journal, "Practical Television," are interference-tested and all parts likely to give rise to interference are adequately shielded.

Readers may be interested to know that in the last issue of the General Post Office Return of Interference Complaints, radiation from television receiver timebases heads the list of offenders, after the normal causes of inefficient aerial and earth systems, interference due to loose wiring in the house, or faulty receivers.

All television receiver designers are now endeavouring to work on the tentative lists of radiated fields which have been proposed by BREMA, and the British Standards Institution have appointed a sub-committee to deal with radio interference susceptibility of receiving equipment, working under the technical com-

mittee dealing with radio-interference suppression. We draw attention to this matter because the number of TV receivers is increasing at a rate which will make such interference intolerable to listeners. We hope that every reader of this journal will make quite sure that his receiver is not an offender.


HOME RECORDING—A THREAT

IN a recent announcement the Musicians Union threatened that unless operators of home-recording apparatus get the permission of an artist to record his or her performance, action would be taken in cases brought to its notice. Strictly, of course, it is breaking the law.

The union has received many complaints from its members, and it intends to take prompt and vigorous action to prevent what it considers to be an infraction of its members' rights.

The secretary has sent a letter to all recording instrument manufacturers

asking them to pass on the warning to retailers and customers. It is estimated that there are 30,000 home-recording amateurs in this country whose hobby mainly consists of recording the voices and the instruments of their favourite radio performers, either on wax, tape or disc. There have been instances of amateurs selling recordings of a broadcast by a famous conductor and of the Coronation ceremony. The union, however, is going too far when it says that it opposes the making of records at home, even those which are made for fun. It will never be able to stop it, and if the union threatens action in all the cases brought to its notice it will never be out of the Law Courts. We know that there is a practice of swapping and selling discs and tapes privately recorded from BBC programmes. The law seems to be that, provided such recordings are not performed publicly, they are quite valid legally and the maker is free from risk of action.—F.J.C.

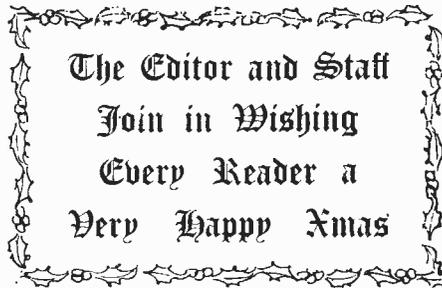



ROUND the WORLD of WIRELESS

Broadcast Receiving Licences

THE following statement shows the approximate number of sound receiving licences issued during the year ended August, 1953. The grand total of sound and television licences was 13,056,689.

Region	Number
London Postal	... 1,709,307
Home Counties	... 1,459,179
Midland	... 1,308,033
North Eastern	... 1,697,723
North Western	... 1,329,989
South Western	... 1,025,772
Wales and Border	... 662,488
Total England and Wales	... 9,192,491
Scotland	... 1,111,616
Northern Ireland	... 213,479
Grand Total	... 10,517,586

Stars on Sound

THE big names in show business will be found this winter not on TV but sound radio. Although only Jewel and Warriss and Eric Barker have been booked for a television series, the stars due to be heard regularly on sound include Frankie Howerd, Ted Ray and Kitty Bluett, Peter Brough and Archie Andrews, Bernard Braden and Barbara Kelly, the Goons, Vic Oliver with Terry Thomas and the Lyon family, and the ever-popular "Take It From Here."

The main reasons for the apparent shunning of television programmes are time and money. A top-rate variety artist can appear nightly on the stage and record sound programmes on Sunday or during the daytime, but an evening spent on a live TV show plus a whole day's rehearsal time eliminates the possibility of appearing in a regular stage variety bill.

Royal Military College

THE Royal Military College of Science, which was established in 1947, at Shrivenham, Berkshire, is the first experiment of its kind in the world. One of its chief objects is the

training of young regular officers in the scientific principles on which the weapons of to-morrow will be designed. The big modern laboratories are packed with elaborate and special apparatus giving more opportunity for practical experiments than any other British university.

When students leave the college they are sent to posts in the Army and Ministry of Supply to act as links between the service departments and the back-room scientists.

B.I.R.E.

THE following meetings will be held during November:

London Section.—Wednesday, November 11th, 6.30 p.m., at the London School of Hygiene and Tropical Medicine, Keppel Street, Gower Street, W.C.1: "A Symposium of Papers on Vibration Methods of Testing Electronic Components and Equipment."

North-eastern Section.—Wednesday, November 11th, 6 p.m., at the Institution of Mining and Mechanical Engineers, Newcastle-upon-Tyne: "Principles of Electronic Computing Machines." —Dr. B. V. Bowden (Manchester College of Technology).

West Midlands Section.—Tuesday, November 24th, 7.15 p.m., at the Wolverhampton Technical College, Wulfruna Street, Wolverhampton: "Remote Control Devices and Servomechanisms." —A. E. W. Hibbitt (Muirhead, Ltd.).


Trainee from India

MR. NRIPESH CHANDRA BAGCHI, M.Sc., A.Inst.P., Assistant Director in charge of the X-ray laboratory of the Government of India's Test House at Alipore, Calcutta, has arrived in the United Kingdom for training made available under the Colombo Plan Technical Co-operation scheme in modern industrial radiographic practice and the use of industrial X-ray plant for testing metal structures which has recently been installed at Alipore.

Mr. Bagchi will spend about five months at various institutions in the United Kingdom.

R.S.G.B. Exhibition

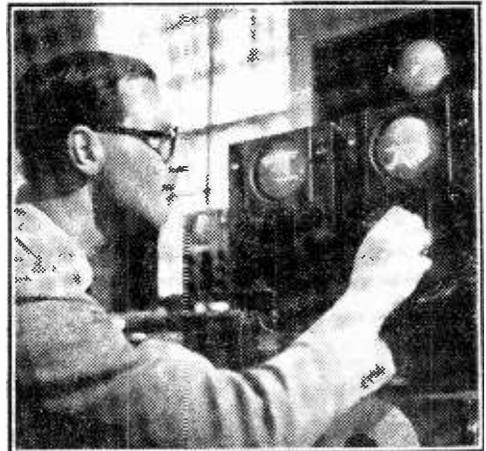THE Seventh Annual Amateur Radio Exhibition organised by the Incorporated Radio Society of Great Britain, will be held at the Royal Hotel, Woburn Place, W.C.1, from Wednesday, November 25th to Saturday, November



In one of the laboratories at the Shrivenham Military College, Berks, are three radar screens. Across two of them move patterns transmitted by instruments at the other end of the laboratory. The top screen is the face of a "radar clock" whose hands tick off the minutes and seconds, the hands being strips of green light and the works a circuit of radio valves.

28th. The Exhibition will be opened at noon on the 25th by Mr. Rene Klein, founder-member and vice-president.

As in past years the exhibition will be supported by a number of companies who specialise in the provision of valves, apparatus, equipment and publications for the radio amateur. In addition the Services will be represented. Members of the R.S.G.B. will exhibit a wide range of home constructed equipment of modern design.

Staff's Support

REPRESENTATIVES of the BBC Staff Association have informed the BBC "that the Association would support any reasonable measures deemed necessary to preserve broadcasting from the adverse effects of sponsoring and commercialism, subject to the preservation of existing standards of efficiency and condition of service."

Ever Ready, Ltd.

MR. C. G. WHITE has been elected to the Board of the Ever Ready Co. (Great Britain), Ltd.

Mr. White joined the company in 1925 and has been export manager for the last fifteen years.

Home Service Coverage

AS part of its plan to make local improvements in the coverage of the Home Service, the BBC is building a new low-power transmitting station at Hampstead near Cromer. The new station will have a power of 2 kW, and it is hoped to bring it into service before the end of the year.

For technical reasons it must use the same wavelength as the Northern Home Service, 434 metres (692 kc/s), and it will therefore carry that service. The transmitter will be provided with a directional aerial system designed to give a good service in Sheringham, Cromer, North Walsham, Aylsham and Reepham, without affecting reception of the Moorside Edge transmissions in North-west Norfolk and along the Lincolnshire coast.

Traffic Control

WHEN the roadway on London Bridge was resurfaced recently, portable radio sets were used by City police to control the traffic. The work took six weeks


to complete and was carried out in three stages so that only one-third of the width of the bridge was under repair at one time.

Indian Experts' Visit

WHILE in London for the recent C.C.I.R. Conference, two members of the Indian delegation visited the Southend works of E. K. Cole, Ltd.

One of the visitors was the

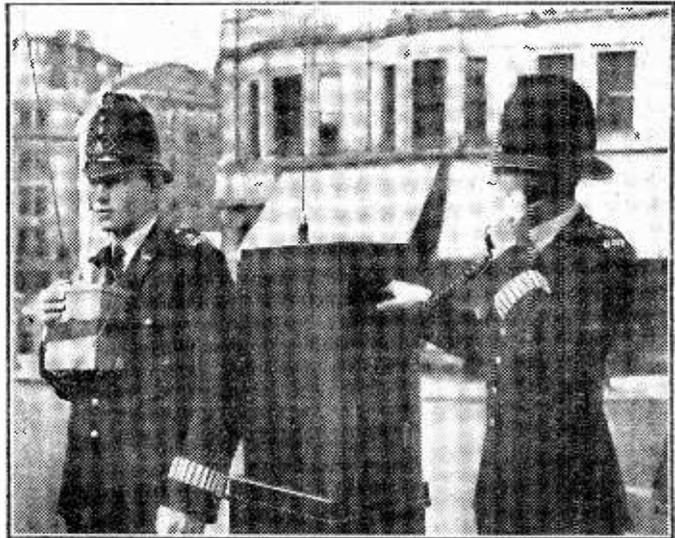on. Interference was so great that reception was completely ruined until Mr. Bovill's new aerial, specially concealed in a picture frame, stopped all atmospheric noises immediately. The aerial has been demonstrated at the Radio Show and will cost approximately 37 shillings.



Two police constables control traffic on London Bridge by portable radio.

chairman of the delegation, Mr. B. V. Baliga, M.Sc., who is wireless adviser to the Indian Government and, until a year ago, chief engineer to All India Radio. Mr. Nerurker, B.(Eng.), a research engineer with All India Radio and a member of the C.C.I.R. Indian delegation, accompanied Mr. Baliga on his visit to Southend. C.C.I.R. is the international committee responsible for the allocation of ether for broadcast purposes and for the laying down of standards.

New Type Aerial

MR. CHARLES BOVILL, 41-year-old inventor of Morden, Surrey, has introduced a new method of receiving radio signals without interference from electrical gadgets such as hair-dryers, sewing machines, electric razors, etc.

In a test demonstration, three radio sets were connected to an indoor aerial while several electrical appliances were switched

Propaganda Stations

IT is reported that Russia is planning to construct a group of radio stations round the East European countries under her influence. These stations will be used to counteract propaganda broadcasts from Western nations.


At Koepenick, near Berlin, a 1,000-kilowatt transmitter is being built and seven 300-kilowatt transmitters will be erected on the frontiers of Bulgaria and Greece, Hungary and Yugoslavia; Austria and Yugoslavia, and West Germany and Czechoslovakia.

Change of Address

WT. HENLEY'S TELEGRAPH WORKS CO., LTD., have announced that the new address of their Glasgow branch is 149/153, North Street, Glasgow, C.3.

These premises are considerably larger than those vacated and general stocking facilities have been greatly improved.

AN Economy QUALITY AMPLIFIER

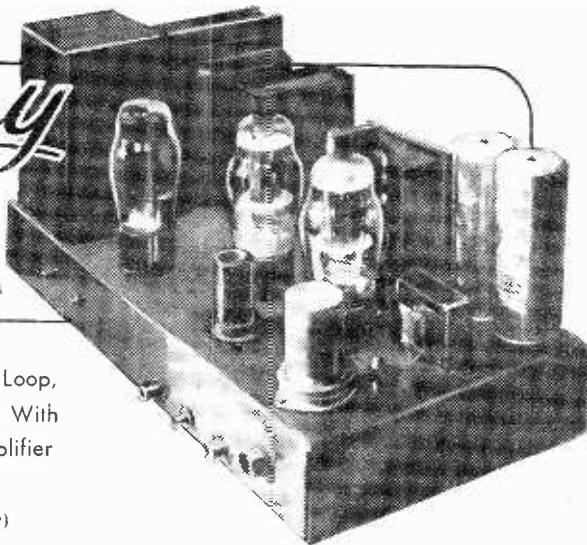

A High Gain, Low Cost, Four Feedback Loop, Main Amplifier, 6½ Watts Output With Negative Feedback Tone Control Preamplifier

By C. J. White, Assoc. Brit. I.R.E.

(Continued from page 674, November issue)

WHILST being pleased with this result it was at once apparent that still more improvement could be made. The gain of V1 was increased to 520 times: the feedback in the main loop increased to 23db and the input requirement brought down to 0.4 volts R.M.S. for 6 watts output, and it is with these constants that the amplifier is now put forward. The reduction of the input requirement is particularly useful in that whilst maintaining the very high quality it enables the requirements of the pre-amplifier tone control stages to be eased. Though no mention as yet has been made of the associated tone control stage, and actually either can be used independently (apart from power supplies), it has been kept constantly in mind that the main amplifier has to be supplied with a distortionless input and in its turn supply power to such a stage which when connected to the main amplifier will not cause either hum or instability.

The complete circuit diagram of the main amplifier was given last month. Starting from the output end it will be seen that the output transformer which is especially designed for this amplifier and supplied by the Radio Supply Company, Wellington Street, Leeds, has provision for two output impedances 3.4 and 12-20 ohms, that is the two nominal impedances 3.5 and 15 ohms. If an 8 ohm output impedance is required, a special model is supplied, it being felt that as 3.5 and 15 ohms loudspeakers are in the majority the transformer can be designed with this in mind and the price kept correspondingly low. The transformer has two secondary windings brought out, each of 3.5 ohms so that when connected in parallel the output impedance is 3.5 ohms and when in series 15 ohms. Two jack


sockets are wired across two wirewound 15 ohms resistors in the cathode circuit of the output valves, the value of these resistances is not critical, anything from 10 to 25 ohms will be perfectly satisfactory, but they must be matched. They provide a measure of negative feedback but are really provided to enable the output valve currents to be matched by the potentiometer VR2. Connect the jack plug to a voltmeter, preferably with a low reading of 0-1 or at most 0-10 volts, the actual reading with 15

ohm resistances will be of the order of 0.75 volts, then plug in jack 1, and then jack 2, and adjust potentiometer VR2, repeating until both readings are exactly the same. The operation is extremely easy, keeping in mind that a reduction of one will result in an increase of the other. It is possible, of

course, that the two valves are so far mis-matched that no position of VR2 will cause the currents to equal each other. Here the best advice is that another valve should be obtained and the best pair of three used. In the writer's experience it is very rare that a complete match cannot be obtained in this way, and it is fortunate that this valve, whilst so good is also so cheap that it enables one to purchase three,

TEST FIGURES

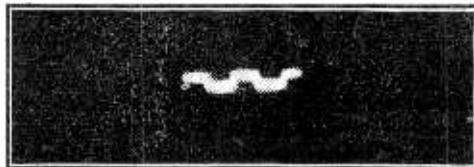Input 0.4 R.M.S. v. at 1,000 c/s per 6 watts output across 15 ohms.
Hum level 90db down (50 c/s and 100 c/s in proportion of approximately 3-2).
Distortion measured on a wave analyser: at 1,000 c/s—no detectable harmonic content: at 50 c/s less than .05 per cent. For 6 W. at 1,000 c/s distortion .27 per cent. (R.M.S. value of harmonic components).



A square wave at 2 kc/s as reproduced on a 'scope through this amplifier.

the spare one going towards making another pair when the time comes to replace. The cathode end of resistance R19 which provides the bias for the two output valves is also connected to the moving arm of the humdinger across the heater supply to V1 and V2. There are very good reasons for this in that in the first place it relieves the cathode heater PD of V2 by the amount of bias on V3 and V4, and in the second it prevents hum being introduced via the PD between the heater and cathode of V1 and/or the heater/cathode of the preamplifier, i.e., it reverses the sign of the PD caused by the cathode bias without affecting the grid bias.

From V4 and V3 to V2 is straightforward. V2 is the 6J5 concertina phase splitter, with the load in both anode and cathode circuits. Bias is provided automatically by the difference between the cathode/H.T.—volts of V2 and the anode/H.T.—volts of V1. The two resistances R9 and R10 are the only

plus the use of C11 and R22 can be described as stabilisers: they control the stability of the amplifier at very high or supersonic frequencies, particularly when long wires are used for loud-speaker extensions. The adjustment of feedback on changing to either output impedance is semi-automatic, use the tap between the two resistances R21 and R20 for 3.5 ohms or use the free end of R20 for 15 ohms.

Power Supplies

Dealing now with power supplies and construction in general it might be as well to say that even though we are constructing an Economy Amplifier the old adage still holds good, that often the cheapest now is not the cheapest in the long run. This factor of

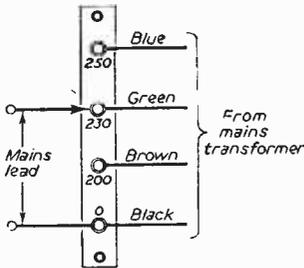


Fig. 7.—The paxolin tag strip.

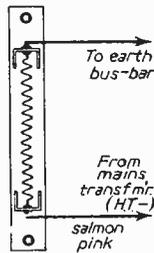


Fig. 8.—H.T. fuse paxolin holder.

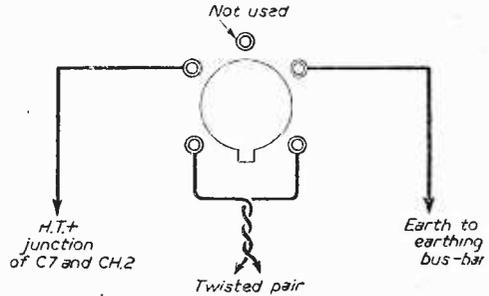


Fig. 6.—Wiring for the preamp. power socket connection.

others where, although the tolerance does not matter, they can be 12 to 20 KΩ without making appreciable difference; they must be matched.

Coming now to the EF54 V1, it will be seen that the anode is taken straight to the grid of V2 without the usual condenser and that the anode load of V1 is also in reality the grid leak of V2. In the preparatory work it was found that in order to get the best of the excellent performance of this circuit it was necessary to use resistances of plus and minus 5 per cent. It was very quickly realised how difficult it is to procure these and additionally the tolerance between different specimens of V1 made it essential that, for the constructor to reproduce the results of the laboratory, some means must be provided whereby the very highest degree of accuracy could be easily controlled by the constructor and yet be flexible enough to cover the largest of tolerances in V1. The answer to this problem was found in the use of a variable potentiometer to feed the screen of V1. In order to prevent the screen being taken to cathode potential a 5 KΩ resistance R7 is inserted in the cathode side of the variable arm VR1 of the potentiometer formed by R6 and VR1. The only instruction in the use of this potentiometer is that it should be rotated until the sound is loudest; there is no need to touch it further unless a valve is changed or on alterations of a major character. For those who like to adjust critically such controls, it is best done on a tuning note, either BBC or record, and at somewhere close to maximum output. By this very simple means, plus the use of R8, the Ea, Es and Ec of V1 are all corrected and the proper bias automatically supplied to V2. C1 and R5

reliability was kept to the forefront in the gathering together of the component parts. The mains transformer used has a safety factor of nearly 200 per cent., that is it can supply nearly twice the power which is actually drawn from it and after a long soak test of 48 hours continuous running in a closely confined space it was still cool to the touch—it was also mechanically quite quiet which if not so can be quite a bugbear in small rooms. The main smoothing choke, a specially selected ex-government type, has an even greater safety factor, with the reservoir condenser, surely the *bête noire* of all


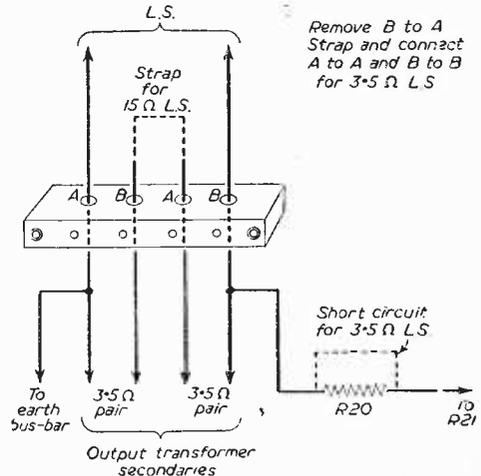


Fig. 9.—Loudspeaker output terminal block.

designers. of paper construction the only really reliable type to serve as such. Farther down the H.T. line are the two smoothing condensers C7 and C8 and here it must be categorically stated that no reduction in working voltage or capacity can be tolerated; they are comparatively expensive, but will be found cheap in the long run. One point here which will be surprising to some, is that they should be purchased with insulating washers together with the corresponding large soldering tags and fitted with the metal soldering tag slipped on first, then the insulating washer and then mounted through the chassis with the H.T. negative wire coming up through the chassis to connect to the soldering tags both strapped together. It may seem strange to go to this trouble of isolating the cans from the chassis when the cans are at H.T.—potential, but one of the reasons for the quite negligible hum level is the care taken to avoid multiple earth returns and this is one very easily overlooked point where it takes place. Before leaving the power supply it will be as well to mention the mains transformer, in that accurate centre tapping of the heater

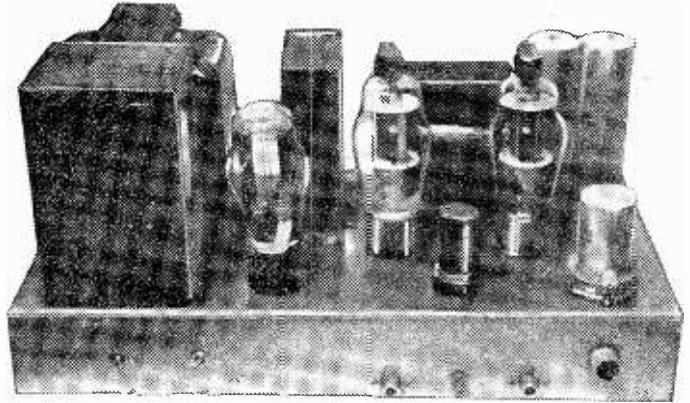windings is secured by the use of humdingers. These are best adjusted when using the pre-amplifier with all gain and bass controls at maximum. In order to cater for the use of the alternative type of output valve,



Rear view of the complete amplifier.

the transformer has two heater windings of 6.3 volt 1 amp. which are to be connected in parallel for the 807 and in series for the 1625.

(To be continued)

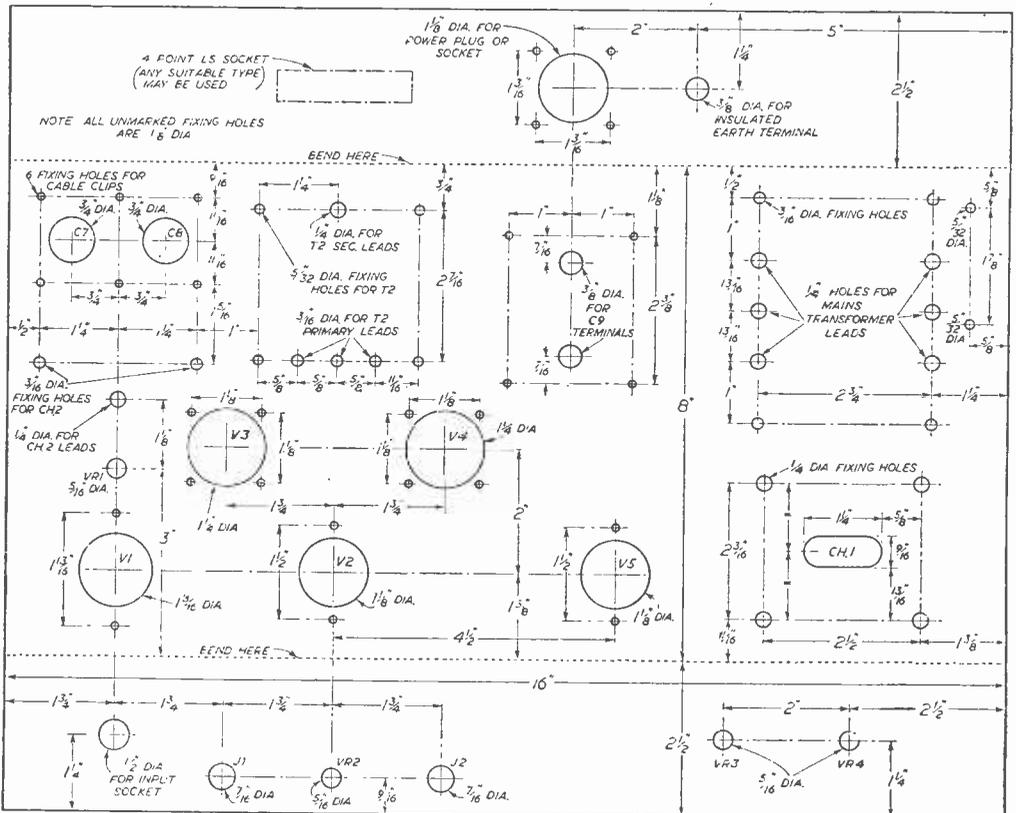


Fig. 10.—Chassis drilling data.

A REMOTE CONTROL UNIT

OPERATING A RADIO RECEIVER FROM EXTENSION LOUDSPEAKERS

By David Boswell, B.Sc.

THOSE who have extension loudspeakers in the home know the irritation of having to walk into another room to switch the receiver on and off, or change a station. A simple solution to the problem is to make or buy another set. Yet if it is desired to have listening facilities in one or possibly two bedrooms as well as the kitchen, then a set for each room becomes an expensive luxury!

The system of remote control described here enables the operator to effect mains switching in the parent set and gives a choice of two stations, by the use of a single push-button beside the extension loudspeaker. The number of speakers need only be limited by the handling capacity and degree of matching required of the receiver sound output stage.

It is the relay which makes this possible. The primary operating circuit is shown in Fig. 1 and this is energised so that it triggers a cyclic sequence of three relays with three successive pulses. Fig. 2 shows the chain of events. It will be seen that it is necessary to have a 3-core cable run to each speaker in place of the usual twin lead. The author used a 1/036in. screened twin, but any cable capable of handling 3 amps or more will do. If convenient earthing points are available near the set and the extensions, they can be utilised as a third line, but the secondary of the output transformer must not be earthed if this method is adopted.

The use of a battery obviates the dangers inherent in passing mains voltages through the extension leads, battery drain being negligible owing to the fact that current passes only when the push-button is held depressed.

Operation

A single-pole change-over contact, break before make, is all that is required on the primary relay (Fig. 3). This switch operates high resistance relays X, Y and Z in sequence from a simple power supply consisting of a half-wave rectifier, three smoothing condensers and a resistance chain to suit the type of relay available. Post Office type 3,000 of resistance 10,000 ohms, were fitted successfully without any heating, buzzing or contact troubles. It should be mentioned that 8 μ F proved satisfactory for the particular relays used. In general, these condensers should be of sufficient value to give ade-


quate smoothing and enable the relay to stay energised while its power source is being altered by change-over contacts on another relay, yet not so large that they upset the sequencing.

When a remote push-button is depressed for the first time, relay X energises through Z₂, Z₃ and X₁, holding on through X₂ and Z₄. When the button is released Relay Y energises through X₁ and holds on via X₃, Y₁ and Y₃. In addition to those contacts required for the sequence operations, Relay Y carries a single pole make and two single-pole change-over contacts. The single pole is connected across the mains switch in the set, while the change-overs alter the tuning circuits from manual to pre-set. See Figs. 3 and 4.

Pressing the remote push-button a second time energises Relay Z through Y₂ and Z₂; Z₁ and Z₃ are its hold on contacts. Relay Z alters Relay X's hold-on circuit so that when the push-button is released, X is de-energised. Relay Y still holds on due to the position of the changeover switch on the primary relay, while two extra pairs of make contacts on Relay Z are used to switch further pre-set capacities into the tuning circuits of the receiver.

The final part of the sequence occurs when the push-button is pressed a third time. Relay Y cannot now hold on as Relay X is already released and immediately the primary relay is operated, it falls out. This prevents Relay Z from holding on through Y₄. Upon release of the button, Z de-energises

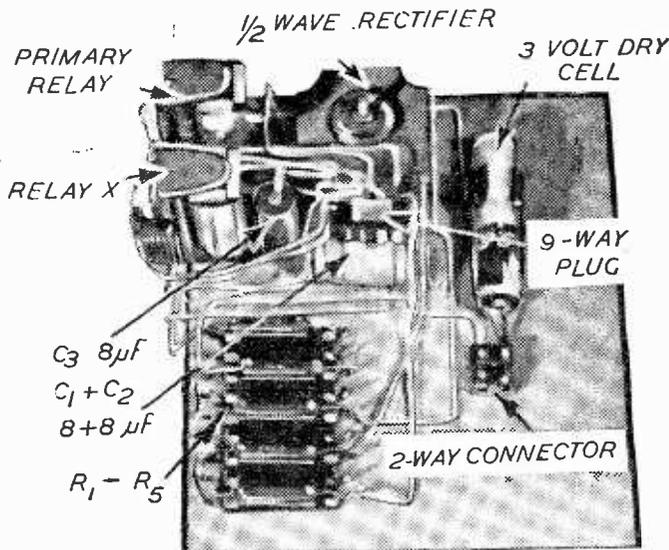*Enjoy Your Xmas Listening
with the Aid of this Distant
Controlling Device.*



Details of the complete unit.

and the whole circuit is dead, but ready for recycling.

Modifications to the Receiver

The position and mounting of components must, of course, vary with circumstances, but it is advisable to adhere to the block diagram in Fig. 4 when grouping them. Relays Y and Z must be as close as possible to the receiver tuning condenser—in many sets the space immediately above it is free and

conditions, and will probably be above 47 KΩ. Unless a separate switch is fitted to the parent loudspeaker, it will perform in parallel with any of the extensions that are working, but if the receiver volume control/mains switch is of the single-pole type, a double-pole one in its place can be used to switch both mains and speaker. Should the set already be fitted with a double-pole switch and it is not an A.C./D.C. model where the chassis is live, one of the poles may be used in the previous manner without danger. It is essential, however, to arrange that the mains-switching pole is always in the "LINE," side of the mains and not in the neutral.

Fig. 5 shows the modified circuit of the first two valves of a typical T.R.F. receiver. In the case of a superhet the oscillator grid on the mixer is treated in essentially the same manner as that of V₂.

After completing all modifications, the pre-set condensers C₁, C₃, C₅ and C₆, should be adjusted to give maximum volume on Light and Home programmes when the appropriate relays are operating. It will probably be necessary to adjust the trimmers on the main two-gang tuning condenser to offset the additional capacity caused by extension of the grid leads to Relays Y and Z. The use of screened leads may be found desirable, although no hum or feed-

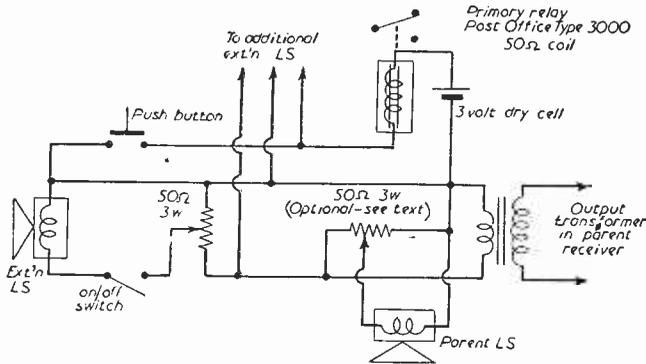


Fig. 1.—Primary operating circuit.

suitable. The operating relay, power supply and Relay X, may be mounted on a sub-chassis and supported in the set, or alternatively fitted into a separate box. In the latter case, an 11-way lead is required to connect them to Relays Y, Z and the loudspeaker, in the set.

In most receivers the volume control carries the mains switch, and when the latter is off the control is in its minimum sound position. When the remote control is functioning some means of gaining full volume must be found, so that it can be regulated entirely by the local potentiometer on the extension speaker. The simplest way is to interchange the two outer leads on the volume control so that when the mains switch approaches the off position, maximum sound is obtained. The momentary surge of sound that may occur when switching off at the set, can be avoided, if so desired, by first manually detuning away from the station in use.

A further method of overcoming this problem would be to unsolder the centre lead from the volume control and connect it to the non-earthed outer. This will deliver full volume to the sound output stage of the receiver, and control can then be effected through a low resistance potentiometer in the parent loudspeaker coil circuit (Fig. 1), as with the extensions. If, when using the set in the normal way, one or both of the stations selected for remote control suffer bad sound distortion at full volume, it is advisable to insert the stopper resistance, R_s in Fig. 5. This attenuates the signal applied to the grid of V₁ under remote control operation only. Its value can be determined by a simple experiment in local

back occurred in the author's receiver with unscreened P.V.C. insulated wire.

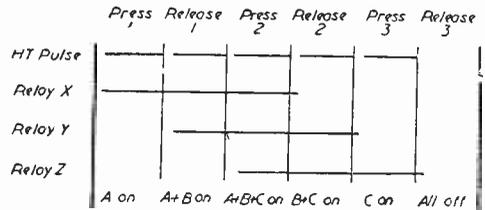


Fig. 2.—Operation sequence.

back occurred in the author's receiver with unscreened P.V.C. insulated wire.

In conclusion it must be said that this article is

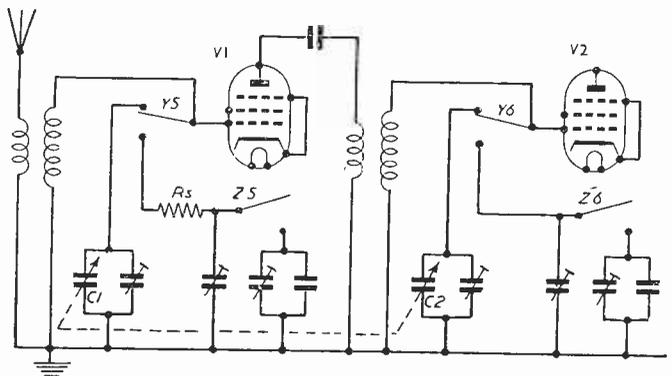


Fig. 5.—Showing how the relays Y and Z are used to alter tuning from manual (using C₁ and C₂) to pre-set, for Light and Home programmes.

intended mainly as a guide and the examples to illustrate one particular solution of the problem. It is certainly possible to achieve similar results using solenoid-operated wafer-type switches, or even multiple bank Post Office Uniselectors, instead of relays. These switches have the advantage that they

current 12 times as large is needed to operate them. This would mean a very much larger power unit. The ex-W.D. solenoid-operated switch No. 10DB 6338, is a useful basis for this alternative type of system, though it should be borne in mind that the ordinary bakelite wafer is not suitable for handling 240 volt mains.

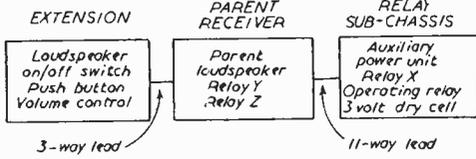


Fig. 4.—Block diagram of the arrangement.

do not require continuous energising current from their D.C. supply, but they are expensive, and whereas the relay system uses say 50 mA., while the set is on, a

The relay unit need not cost more than £2 15s. 0d. to build (excluding leads and speakers). If the extensions are used for three hours every day and a three-volt battery purchased once a year, the annual cost of running the system would be less than 2s. 6d., whereas an extra radio, besides its higher initial cost, uses twice as much electricity. For these reasons a remote control can be an economic proposition, but it is also an amusing and instructive exercise in the art of using relays. There is no reason why a unit capable of selecting more than two stations should not be designed.

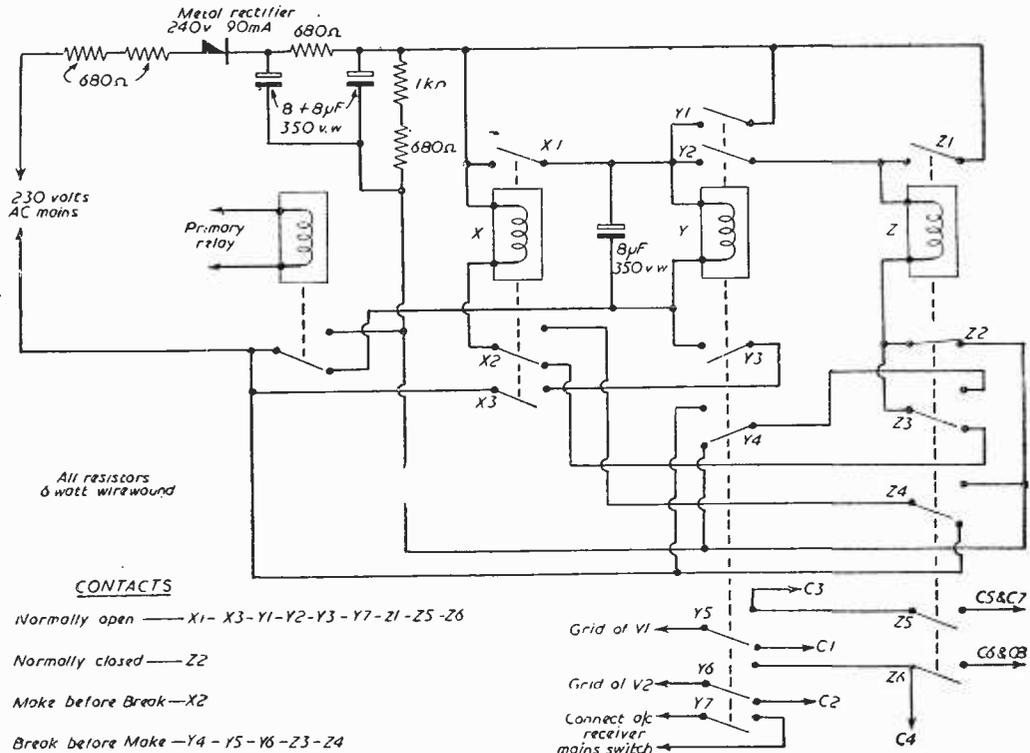


Fig. 3.—Cycling sequence circuit.

The Entirely New 12th Edition of The Famous Standard Work

THE PRACTICAL WIRELESS ENCYCLOPÆDIA

By F. J. CAMM

Considerably enlarged, amplified and entirely re-written and re-illustrated. Complete Television Section, with theoretical and constructional data.

All the facts, figures, and constructional data of Radio and Television—Definition, Terms—Units—Principles, Circuits, etc.

Over 300,000 copies sold Price 21/- or 21/11 by post from:


GEORGE NEWNES, LTD., Tower House, Southampton Street, Strand, W.C.2.

A VARIABLE BANDWIDTH FILTER

A SELECTIVITY MODIFICATION FOR THE R1155 OR ANY RECEIVER OF SIMILAR TYPE

By J. Cook

IT is probable that there are a number of radio enthusiasts who, like the author, own an R1155 or similar communications type receiver and require the receiver to perform the dual function of band searching, perhaps on the "Ham" bands, when the full sensitivity and selectivity is needed, as well as providing day-to-day listening on local or other powerful stations. It may then be found that such a receiver is not wholly satisfactory due to the restriction in bandwidth, not usually necessary in this role, and the consequent loss of quality. The employment of two or more efficient I.F. stages in a receiver usually provides a highly selective (i.e., narrow bandwidth) response curve, the R1155's being in the order of 4 kc/s to 6 kc/s total bandwidth for 6 db. attenuation. Inevitably audio response suffers as the normal bandwidth radiated by broadcast stations is 9 kc/s (double sideband) for the medium waveband, the loss of the higher frequencies being audibly apparent by the lack of brilliance in reproduction. This debasing of quality is particularly objectionable

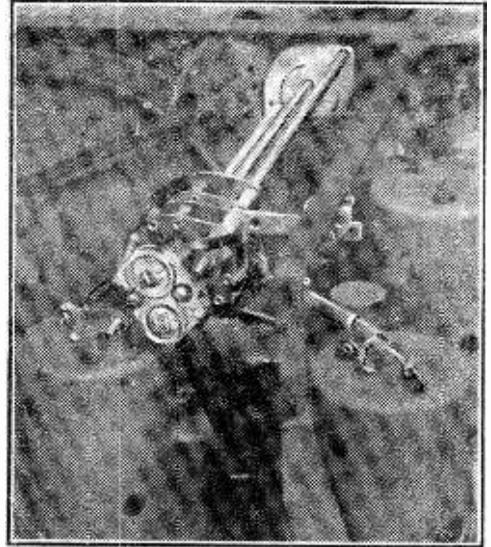

The additional switch and wiring are clearly seen here.

on musical programmes.

More advanced communications receivers utilise several methods to obtain variable selectivity—this being the answer to the problem. Quite often some mechanical device is employed to vary the coupling between I.F. coils or an electrical equivalent using tertiary coils or, particularly on American receivers, a frequency selective filter using a special type of

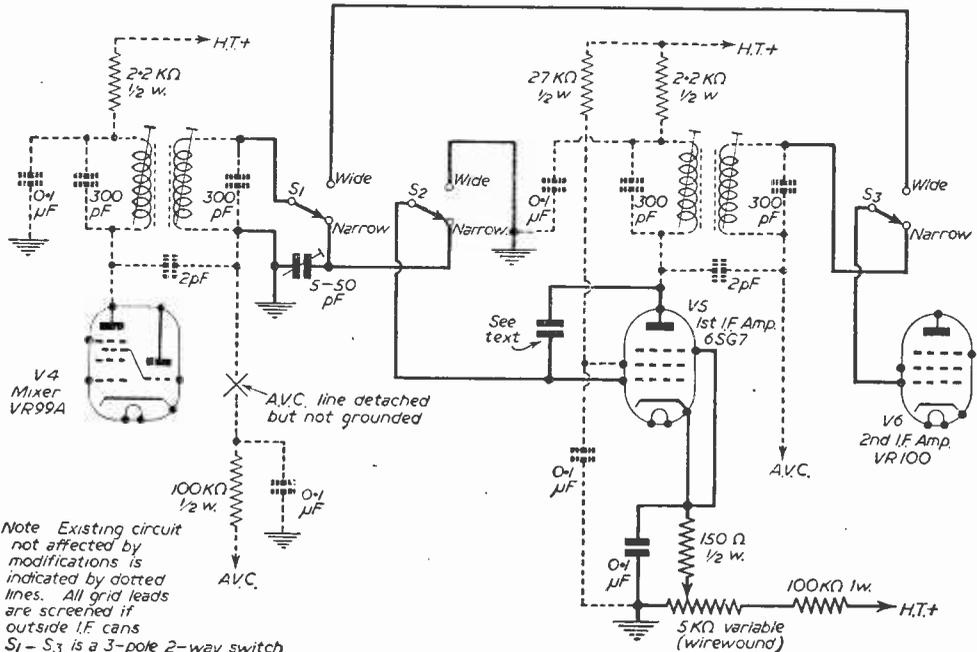


Fig. 1.—General details of the modification.

piezo-electric quartz crystal in a "gate" circuit. Sometimes a combination of these methods is used with some complicated switching by the manufacturer; but it is very difficult to incorporate any of these devices once a receiver is manufactured because of the restriction in space imposed by the average chassis layout and lack of room inside I.F. screening cans for extra components—usually all adding up to an impracticable proposition. Besides this the procurement of crystals for a rather odd and peculiar I.F. frequency like the R1155's 560 kc/s is no easy or cheap matter.

The compromise scheme described here has been successfully applied to an R1155 receiver by the author to obtain variable selectivity and is, of course, equally applicable to receivers of a similar type where this facility is required, subject to reasonable mechanical adaptability.

The Circuit

The circuit illustrated at Fig. 1 offers two means of varying the I.F. response curve to obtain a wide or narrow bandwidth at will. As will be seen, the first I.F. stage can be completely by-passed by a switching arrangement whilst the secondary of the first I.F. transformer may be tuned off peak on to one of the sidebands; the primary cannot be treated likewise (as it should be) because it would affect the narrow band performance. The wide bandwidth so obtained will not be without some loss of gain as one I.F. stage only is now being used—however, this is the characteristic of all variable selectivity systems and is, in any case, unimportant when listening to local stations. The correct sideband must, however, be chosen when tuning in. The second method provides assistance at the other listening extreme when it is found that the 4 kc/s to 6 kc/s bandwidth of the two I.F. stages is insufficient to obtain satisfactory separation of some, usually more distant, transmissions. Both I.F. stages are utilised, the first I.F. being brought back into operation by the selector switch and this stage is made regenerative by deliberately introducing positive feedback between the anode and control grid of the pentode which is now an

American metal valve 6SG7, it being more suitable for this application than the original VR100. Regeneration is controlled by a variable gain control in the cathode lead of the 6SG7 and as this gain control is advanced to near oscillation point a sharply peaked I.F. response is obtained, asymmetrically placed about the mid-point, providing substantially single side-band reception remarkably similar to the crystal gate filter characteristic though, unhappily, without the phasing facility of the crystal whereby the best side band may be selected. Nevertheless, carefully used it can be of very great value in rejecting unwanted signals.


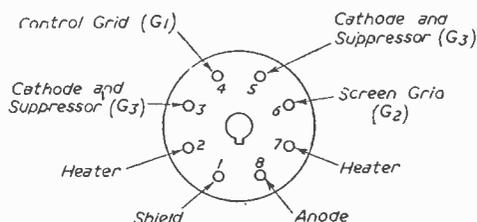


Fig. 2.—Details of the base connections of the 6SG7.

Modification Details

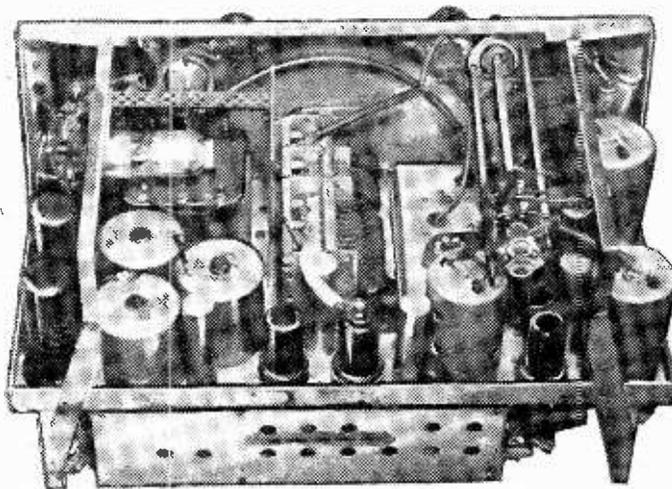(i) Switching circuit. As indicated the output from the secondary of the first I.F. transformer can be passed through to either the grid of the first or second I.F. amplifier at will by selecting the appropriate switch position. Provision has to be made to ground the grid of the first I.F. amplifier when it is not operating on the wide band position whilst the by-pass lead, which is isolated when both valves are used on the narrow band position, is connected to a small preset condenser so that when used, i.e., in parallel with the first I.F. secondary winding and enables the slightly smaller valve and stray capacities associated with the narrow position to be equalled to the wide position and thus maintain alignment of both circuits. This condenser is a small preset component of the high stability ceramic or Phillips type, variable between about 5 to 50 pF, and is mounted on to the ends of the lateral rods of the switch assembly. A standard long spindle type of wafer wave-change switch is used with the wafers reset to the rear of the switch if necessary in such a manner that they are located immediately above the first and second I.F. cans—it being essential that all wiring is screened, as short as possible and with input and output leads physically removed from each other as far as is practicable to avoid instability, etc. If the switch has more than the two positions required it can, in most cases, be adapted to a two-position movement by appropriate bending of the unused "stop" lugs on the frame of the assembly. The wiring connections are most conveniently made inside the I.F. cans first and leaving



A general view of the modified receiver 1155.

the connections to the switch until last. The switch is bolted to the front panel and also braced towards the rear on to the chassis protecting rail. (See Fig. 2.)

(ii) Re-alignment. This is carried out in the first instance with only the second I.F. valve switched in (wide) and the cores of the first I.F. transformer are peaked to the appropriate I.F. using a signal generator if available; otherwise by tuning in a local non-fading station (A.V.C. off!) and peaking the I.F.'s for maximum response as observed on the tuning indicator—always assuming the R1155 oscillator to be correctly aligned before commencement of operations. The secondary of the first I.F. transformer is then detuned slightly from optimum by about 2 kc/s to broaden the response on one of the sidebands. If no signal generator is available or is not accurate enough, the effect is evident audibly by the increase of brilliance in reproduction, especially on a "live" studio broadcast of music; it is, after all, the ear which will be the final judge of the results obtained. Finally, with both I.F.'s working (narrow) the four windings of the first and second I.F. transformers are all peaked for maximum signal, but using only the preset condenser to peak the secondary of the first transformer and not touching the slug core in the transformer. It should be unnecessary to adjust the third I.F. transformer as it is not in any way concerned with these modifications. All alignment operations should be done with a suitable trimming tool—a plastic knitting needle suitably filed served admirably in the author's case.

(iii) Regenerative I.F. stage. This circuit is dealt with last because it is essential that the I.F. amplifiers should be quite stable before this modification is introduced and the wiring to the selectivity switch above is perfectly capable of introducing uncontrolled regeneration if the wiring has not been carefully carried out! If all is well, control of regeneration in the first I.F. stage is effected by dispensing with the present biasing arrangements for that stage and taking the cathode to ground via a variable cathode bias potentiometer; this may be located anywhere convenient on the front panel. In view of this arrangement it is impracticable to use the A.V.C.

BBC Monitoring Service

THE BBC monitoring service, developed during the war to listen to broadcast transmissions from foreign countries for intelligence purposes, was retained after the conclusion of hostilities as a source of information for BBC news bulletins and Press information, as well as for the benefit of government departments. The main monitoring and office facilities of the service are at Caversham Park, Reading, with a remote engineering interception station $3\frac{1}{2}$ miles to the north at Crowsley Park, in an electrically quiet area where an extensive directional aerial system can be provided. Signals from this station are relayed by landline to Caversham.

The General Electric Co. Ltd., which since the war has already supplied the BBC with 54 communication receivers for both sites, has recently supplied a further 30 receivers of an improved design. Twenty-eight of these have been installed in the main receiving bays at Crowsley Park and two on the new supervisory console table in the main listening room at Caversham. This is the first major installation of the new version of the G.E.C. communication

line of the R1155 which has a standing bias of some three volts or so; the A.V.C. lead is disconnected from the secondary of the first I.F. transformer and the winding is grounded at that end, the redundant A.V.C. components (100,000 ohm resistor and 0.1 μ F condenser) may either be removed or remain "floating." The 6SG7, which is used in place of the VR100, is a single-ended valve and thus it is necessary to rewire the socket, which need not be changed as it is also of the octal-based variety. The valve is made regenerative by soldering a short length of insulated wire— $\frac{1}{16}$ in. to $\frac{1}{8}$ in.—to the anode pin and placing the free end in close proximity to the grid pin. The position of this wire is adjusted in such a manner that the feedback so introduced just brings the valve to the verge of oscillation when the gain control is advanced to maximum when, besides greatest gain, greatest selectivity—with one sideband partially suppressed—will be obtained. Backing the control off to about mid-point will provide the normal gain and double sideband working associated with the R1155.

In practice these two modifications should enable the user to obtain a much more flexible performance from his receiver allowing reception of many stations which would otherwise be "swamped" whilst being able to listen to interference-free transmissions with high-fidelity reproduction, especially if a good amplifier is employed.

In connection with the latter remark, a note regarding the rather unusual appearance of the R1155 illustrated on page 737 may be appropriate to conclude this article as readers may well be puzzled by this. Besides the selectivity modifications described here the set has been completely remodelled to incorporate two triode connected 6L6's in push-pull, an "S" meter with separate meter amplifier to present an indication irrespective of A.V.C. and also to reverse the current to present conventional left to right presentation instead of the usual reversed action, voltage regulator, variable delay A.V.C., noise-limiter, infinite-impedance detector, R.F. gain control, aerial trimmer and several other new features.

receiver, which incorporates many circuit refinements and additional facilities.

Technical Details of the New Receiver

The new receiver (the BRT 400 D) is a 14-valve superheterodyne receiver with a frequency range which has been modified to suit BBC requirements, 150-385 kc/s and 0.51-30.0 Mc/s in six bands. The input impedance is 75 ohms on all bands.

Selectivity has also been adjusted to suit the BBC. There are six switched bandwidths, overall bandwidths for 6 db attenuation being 5.5 kc/s, 9.0 kc/s, 13.0 kc/s for telephony and 0.5 kc/s, 1.0 kc/s and 2.0 kc/s for telegraphy, the last three positions with a crystal filter in circuit between the mixer and I.F. amplifier.

In the new receivers the local oscillator frequency stability has been improved. They were all subject to an extended drift test, the specification requiring that oscillator frequency drift should not exceed 5 kc/s measured at 29 Mc/s, 3 kc/s measured at 19 Mc/s and 2 kc/s measured at 8 and 3 Mc/s. In practice, when the receivers reach a stable operating temperature, drift figures much lower than these are normally obtained.



'AVO' Precision ELECTRICAL TESTING INSTRUMENTS

Registered Trade Mark.

A dependably accurate instrument for testing and fault location is indispensable to the amateur who builds or services his own set.

The UNIVERSAL AVOMINOR

(as illustrated) is a highly accurate moving-coil instrument, conveniently compact, for measuring A.C. and D.C. voltage, D.C. current, and also resistance; 22 ranges of readings on a 3-inch scale. Total resistance 200,000 ohms.

Size: 4 3/4 ins. x 3 3/4 ins. x 1 1/4 ins.
Nett weight: 18 ozs.

Complete with leads, interchangeable prods and crocodile clips, and instruction book.

Price: £10 : 10 : 0

The D.C. AVOMINOR

is a 2 1/2-inch moving coil meter providing 14 ranges of readings of D.C. voltage, current and resistance up to 600 volts, 120 milliamps, and 3 megohms respectively. Total resistance 100,000 ohms.

Size: 4 1/4 ins. x 3 3/4 ins. x 1 1/4 ins.
Nett weight: 12 ozs.

Complete as above
Price: £5 : 5 : 0

D.C. Voltage
0—75 millivolts
0—5 volts
0—25 "
0—100 "
0—250 "
0—500 "

A.C. Voltage
0—5 volts
0—25 "
0—100 "
0—250 "
0—500 "

D.C. Current
0—2.5 milliamps
0—5 "
0—25 "
0—100 "
0—500 "

Resistance
0—20,000 ohms
0—100,000 "
0—500,000 "
0—2 megohms
0—5 "
0—10 "

GUARANTEE: The registered Trade Mark "Avo" is in itself a guarantee of high accuracy and superiority of design and craftsmanship. Every new Avominor is guaranteed by the Manufacturers against the remote possibility of defective materials or workmanship.

Sole Proprietors and Manufacturers:—
AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT CO., LTD.
Winder House, Douglas Street, London, S.W.1. Phone: VICTORIA 3404-9



ELECTROLYTIC CONDENSERS

The choice of T.C.C. Condensers by so many knowledgeable manufacturers is testimony to their worth.

'LECTROPACK' ETCHED FOIL ELECTROLYTICS

Cap. µF.	Peak Wkg.	Length	Dia.	Type No.
8-32	275	2 1/4 in.	1 in.	CE34HE
60-100	350	4 1/4 in.	1 3/4 in.	CE37LEA
8-16	450	2 3/4 in.	1 in.	CE34PEA
32-32	450	4 1/4 in.	1 3/4 in.	CE37PE
100-100	350	4 1/4 in.	1 3/4 in.	CE36LEA



'PICOPACKS' MINIATURE ELECTROLYTICS (Plain Foil)

Capacity µF.	Peak Wkg. Volts	Dimensions		Type No.
		Body Lgth.	Dia.	
8	6	1 1/4 in.	.25 in.	CE72A
20	12	1 1/4 in.	.34 in.	CE30B
30	15	1 1/4 in.	.43 in.	CE71B
10	25	1 1/4 in.	.34 in.	CE30C
5	50	1 1/4 in.	.34 in.	CE30D
2	150	1 1/4 in.	.34 in.	CE30G
1	350	1 1/4 in.	.34 in.	CE30N

(Regd.)

THE TELEGRAPH CONDENSER CO. LTD.

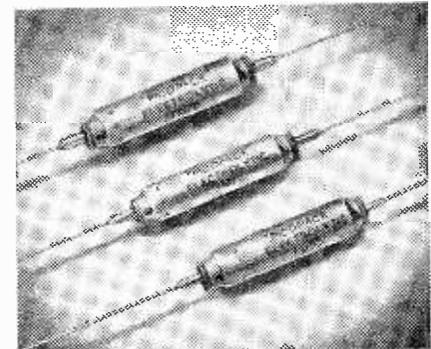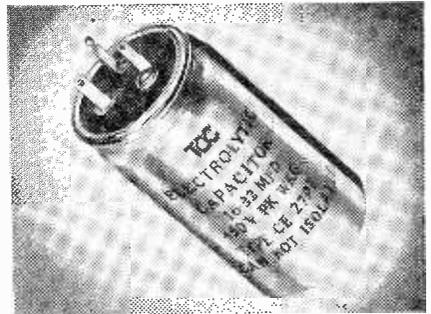Radio Division: North Acton, London, W.3. Tel: Acorn 0061



NEW ARRIVALS

AERIALS. Copper plated steel, 12in. long. x 19 sets. Interlock to any length. 2d. each. Post 6d. on 1 dozen.

CRYSTALS. Brand-new Germanium crystals, by B.T.H. Long wire ends. 2/3, post 6d.

INDICATOR UNITS. Ex W.D., but brand-new condition. Valves and C.R. tubes removed but otherwise complete. Units include indicators type 6C and type 62, power unit 657 and C.R. unit design L. Price 12/6 each, carriage 4/6.

CONDENSERS. New and unused. 32 mfd., 450 V.D.C. Cardboard case. 3/9, post 9d.

AMPLIFIERS. Brand-new (ex W.D. unused). Contains EF36, 2 transformers, 400 ohm relay, volume control, various condensers, resistors, etc. Case measures 5in. x 5in. 9/6, post 1/6.

RECORDS. Overseas Broadcast Programme Recordings. New or as new. From 3/6 each, or in sets. Send for list.

CAR RADIO TRANSFORMER. Unused, store soiled. 6-volt and 12-volt primary, both with standard secondary. 7/9, post 2/3.

MICROPHONE TRANSFORMER. Ex W.D. but unused and brand-new condition. In fully shielded case. 3/9, post 9d.

PICK-UP TRANSFORMER. New and unused. E.M.I. type. Fully shielded. 3/9, post 1/-.

SURPLUS AND SALVAGE VALVE SALE

8/9 :	8/9 :	6/9 :	5/9 :	3/9 :
154	EY51	KTW63	6V5	12S17
155	EL91	ECC91	EB91	EF36
3V4	EF92	UF4	6Y41	EL149
35Z4	X66	EFA5	LL2	VP23
6K7	6F15	27-SU	12SK7	VT501
10F1	KT74	7Y4	OZ4	6SA7
6BW6	EF91	7C6	77	RL37
EF50	1R5	2LO DDT	PEN 220A	37
6F15	1T4	5P41	KTW61	CV6
20D1	EAF42	7H7	RKR72	6SH7

C.W.O.
OR
C.O.D.

DUKE & CO.,

621, ROMFORD ROAD,
LONDON, E.12. GRA. 0677.

STAMP FOR CATALOGUE.
MONEY BACK GUARANTEE.

RECEIVER CHASSIS

6 WAVE BAND 5 valve superhet chassis. Fly wheel tuning, negative feedback. Valve line-up : 6AT6, 6BW6, 6BE6, 6BA6 and 6X4. 15 guineas. Chassis measures 11in. x 7in. x 8in. Will drive any type of low impedance (2-5 ohm) P.M. speaker. Terms available.

3 WAVE BAND model. same specifications as above. 12 guineas.

3 WAVE BAND 5 valve superhet radiogram chassis at £10/17/6, including FREE Bin. speaker. Valve line-up: ECH42, EF41, EBC41, EL41 and EZ40.

SALVAGE AND RECONDITIONED RADIOGRAM CHASSIS with end-drive controls. Valve line-up as above. £7/17/6, including FREE speaker. Carriage in each case 4/6.

PORTABLE UNIVERSAL CHASSIS. 5 valve superhet. Valve line-up: 12BE6, 12AT6, 12BA6, 12A6 and 35W4. Frame arial. £5/19/6, carriage 3/6.

BARGAIN CORNER

TUNING CONDENSERS. Store soiled but tested. Standard size. 2-gang. 0005 mfd. 2/9, post 6d.

O.P. TRANSFORMERS. Store soiled. Match all normal O.P. valves to 2-5 ohm speech coil. 1/9, post 9d.

I.F. TRANSFORMERS. Unused. Standard cans. 465 kc/s. 3/9 each, post 6d.

FIXED RESISTORS. Mixed parcel of popular sizes from 1 to 2 watts. New. 10/- 100, post 9d.

T.V. TUBES. All makes and sizes from £3. Personal callers only as each one is shown working.

AUTO-CHANGERS. Salvage and reconditioned 3-speed auto-changer units. £7/17/6, carriage 4/6.

THE HAM'S SHOP, Definitely the Cheapest Radio, Television and Electrical Shop in Gt. Britain

58a, KING STREET, BELFAST, NORTHERN IRELAND

RECEIVERS.—H.R.O. complete with Power Pack. £20.0.0. H.R.O. without Power Pack. £16.0.0. 208 converted for 10, 15, 20 and 40 meters. £12.10.0 (complete). R1155 complete with Power Pack. £8.10.0 : R1155 without Power Pack. £6.10.0 : CR300, complete with Power Unit. £22.10.0.

TRANSMITTER RECEIVERS.—Hellicrafter type CH1-15022. for Shipping Bd. Complete with 12 v. power pack. £25.0.0.

TRANSmitters.—Type 18, £6.10.0 (complete). Type 53, not complete. 17/6 each.

INDICATOR UNITS.—Type 62. £4.10.0 (complete) : Type 62 (less Valves and VR97). £2.0.0 : Type 6A, complete with Valves. £3.0.0 (without Valves). £1.5.0 : Modulator Units type 53, not complete. 17/6 : 1154, not in order. 10/- for parts only for breaking up.

AMPLIFIERS.—"Parmeco" 12 v. input 25 watts. £4.10.0.

C.R. TUBES.—VCR97. £1.15.0 : 5CP1. £1.5.0 : ACR8. £1.10.0.

TELEVISION RUBBER MASKS.—10in., 4/6 each.

POCUS MAGNETS.—P.M. 10 : Electromagnetic. 12 6.

TRANSFORMERS.—425-0-425, 250 Mil. 6.3 volts. 10 amp. 4Kv. at 3 Mil., 5 v. at 4 amp. 2 and 4 v. at 5 amp., £2.10.0. (CANNOT BE REPEATED) (plus 7/6 carriage).

METAL RECTIFIERS.—220 volts. 100 mil., 5 6 each. 6 volts at 5 amp., 12/6 : 13 volts. 100 mil., 1 4 each. 1 3 each.

CHOKES.—150 mil. 4/- each (CANNOT BE REPEATED).

WIRE WOUND RESISTORS WITH SLIDER.—300 ohms. 50 w., 1 3 each.

WIRE WOUND RESISTORS (1 doz. assorted lots). 10 K., 50 K., 20 K., 75 K., 5 K., and 350 ohms. 10/- per doz. (CANNOT BE REPEATED). Also a large selection of 1, 1 and 2 watt Resistors from 6d. High Voltage Valve Holders, 5 pin. 1 6 each.

COILS of enamelled wire approx. 7 ozs. 32 gauge. 1 01.

CONDENSERS.—6 mid. 2 kV., working. 4 6 : 1 plus 1. 2.5 kV., working. 5 : 1.2kV., 2 6 : 01 5 kV., 3 6 : 1.4 kV., 4 6 : 1.500 v., 6d. : 30 mid. 12 v. working. 1 6 : 200 mfd. 6 v., working. 1 6.

METERS.—150 Mil., 10/- : 3.5 kV. volts. £1.5.0 : 5 kV. Electrostatic. £2.5.0.

CONDENSERS.—3 gang. 00037. 3/- each.

Crystal Monitors. 6/6 each. Rev. Counters. 1 6 each. Photo Flash Bulbs. 1 3 each. Relays 625 ohms. 3 6 each. Soldering Paste pound tins. 2 6 each. Systoflex. 2/- per doz. Paxolene Coil Formers, 3in. x 11 and 61 x 11. and 5 x 1. 6d. and 8d. each. Double Pole Knife Switches. 1/- each. Pick up and Sockets. 3d.

CHASSIS WITH COMPONENTS. 6/- each.

THOUSANDS OF OTHER BARGAINS

Packing and Carriage extra. Please enclose S.A.E. with enquiries. Deliveries with 14 days.

ALWAYS AT YOUR SERVICE

BEST WISHES TO ALL OUR CUSTOMERS

BUILD THIS AMAZING RADIO

POWERFUL! PERSONAL! PORTABLE!

● Selective tuning.

● Acorn low drain valve.

● Loud clear tone.

● Long range.

● No earth.

● Short aerial, 2ft.


● Welded steel case.

● Easy to assemble.

● All parts for this set are sold separately.

MAIL ORDER ONLY

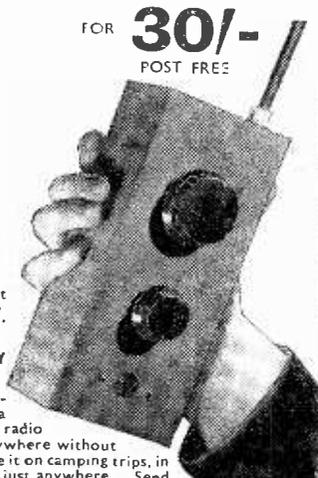This little set was designed to give you a real personal portable radio that you can enjoy anywhere without disturbing others. Use it on camping trips, in bed, in your office, or just anywhere. Send 2/- for layout, Wiring diagram and Component Price List.



R. C. S. PRODUCTS

11, OLIVER ROAD, LONDON, E.17



On Your Wavelength

By Thermion

Birthday Echoes

I CONTINUE to receive belated letters from remote quarters of the earth from readers suffering from nostalgia as a result of reading our Birthday Number. They remind me of something which I did not mention in my brief resumé of my association with the journal. For example, one reader in an isolated shack in New South Wales tells me that he is still using the three free gift spanners which we presented with every copy of this journal in the early '30s. His only drill gauge is one we presented during that same period. He still has the pocket tool kit which we had specially manufactured for readers, and has on file every blueprint from No. 1 to date. He tells me that he has made a profitable business out of manufacturing sets for his friends, drawing most of his components from this country.

Others remind me of controversial topics which I had forgotten. All of them remember my long, sustained attack on jazz when it was first spawned upon the ether. One asks what my views are now. They have not changed but become intensified. After all, in its early years there were only two well-known bands creating their cacophonous shindy on the air. Members of each band, however, soon saw that there was money in it and broke away and themselves formed bands until to-day there are literally dozens of them.

Gilbert Harding, no doubt, could probably express himself on this matter more vociferously than I. I am heartily sick and sated with listening to announcements about somebody "and his band." Evidently the BBC took some note of my campaign which I carried on for a number of years for we have fewer of them now. Unfortunately, this form of radio annoyance has been replaced by something equally irritating. I am referring to the general tendency of the BBC to introduce parlour games into the programmes, such as "Down You Go," "What's My Line?" etc. Sooner or later we shall have musical chairs and charades.

Gilbert Harding

I FEEL sorry for Gilbert Harding in some ways. I am sure that his endeavour to convince us that rudeness is wit is well-intentioned and that he does not really intend what he says. The venom with which he threw an aspistras out of the window because he did not like it would be understood, I think, by most men who hate flowers and plants inside the house. I like rump steaks, but I do not want them to decorate my room. However, my dear Gilbert, you must remember where to stop. Radio audiences cannot answer back, but others can. To modify an old saying "a little ill humour now and then is welcomed by the wisest men."

Advance of Tape Recording

I MUST say that I was very surprised to learn that there are 30,000 amateurs in this country operating home-made tape recorders. I do not know whether the Sound Recording Association would support these figures, but judging from the increasing volume of correspondence we receive on this subject I do not think the estimate is far out. Large numbers of the tape recorder described in our companion journal, "Practical Mechanics," are being built as I know from the manufacturers of some of the components. The number is likely to increase. In view of the copyright position, however, some amendments to the Copyright Law will have to be made or a system of licence fees instituted, although how the latter could be brought about eludes me. Perhaps it could be effected by imposing a levy on each recording head sold.

Electronic Organs

ANOTHER branch of electronics which is gaining popularity is that concerned with electronic musical instruments and particularly electronic organs. The one made by my colleague, Mr. W. J. Delaney, is a first-class job, and although I spent 11 years learning the piano and the organ and have naturally through lack of practice lost some of the digital dexterity with which I could perform musical acrobatics on the keyboard, I was astonished at the speed with which one could play fast runs on this organ. Unlike the piano or the organ which require some considerable depression of the keys before the note emerges, the slightest touch on an electronic organ is sufficient to produce the note. Of course, such instruments are only suitable for music specially written for the organ, since it is not possible to hold the note as, say, with a piano, by means of the sostenuto pedal. The quality, however, of the instrument to which I have referred is in my opinion equal to that of a professional instrument and I am not surprised that it is being built in large numbers.


Sponsored Programmes

I LISTENED the other day to a most interesting talk by one most intimately associated with either sponsored or commercial TV. He explained how it would work, but the impression left on my mind was that whoever operated this alternative programme was going to tell the advertiser what he could have in the way of publicity. I can assure him that unless the advertiser can obtain adequate publicity he is not going to pay large fees for programme time in order that the operators can make large profits. The sensible view must be adopted that advertisers must get their money back and that will not happen if they merely get a mention. Of course, some programmes will be mutilated by the interlarding of trade puffs, but in programmes of the variety type where a pause between each item can be regarded as an interval, I see no reason why bunkum pills by boloney should not have their mention.

SHORT-WAVE SECTION

MODERN SHORT-WAVE BATTERY RECEIVERS

By T. W. Dresser

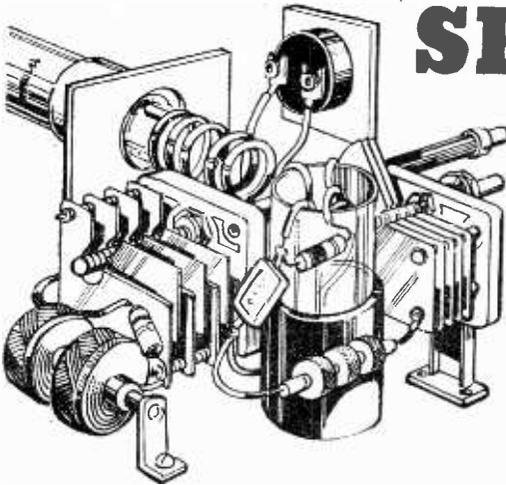

As a direct consequence of various circuits published by the writer in PRACTICAL WIRELESS he has been asked by a number of correspondents for an up-to-date battery receiver. This article, therefore, is in a way a reply to these readers, but it is hoped it will also be of interest to others who may have no mains supply or who, for reasons of their own, prefer battery operation. Before going any further, however, it should be made clear that the writer has no intention of attempting to duplicate, in battery form, the kind of arrangement found in certain receivers advertised as suitable for use on A.C., D.C., and battery operation. The quality of reproduction from many of these sets is, to say the least, appalling, and very few readers of PRACTICAL

WIRELESS would tolerate it for long. Nor is it necessary to do so. With the enormous range of good-class components and valves available to-day to battery users both quantity—as regards the number of stations receivable—and the quality, from the audio response viewpoint, are not difficult to achieve.

Without much doubt the best-known battery circuit is that of the three-valve T.R.F., consisting of R.F., detector and output stages, and there have been many variations on this theme, although there is still plenty of scope for experimenting with them. The circuit of such a combination is shown in Fig. 1, and while, basically, it cannot claim any originality there are some points in which it is a departure from the orthodox. For instance, the ganged tuning condenser is split stator type with one section of $380\mu\text{F}$ and a much smaller section, on the same rotor shaft, of $10\mu\text{F}$. In use the large section tunes the medium-waveband only and is switched out on shorts, where the $10\mu\text{F}$ section is used alone. Seven bands are covered, the medium-waveband and six short-wavebands as follows: 3.5 to 4 Mc/s., 6.9 to 7.4; 13.95 to 14.45, 20.5 to 21.9, 27 to 30, and 48 to 55 megacycles or, in wavelengths, 75 to 85.7

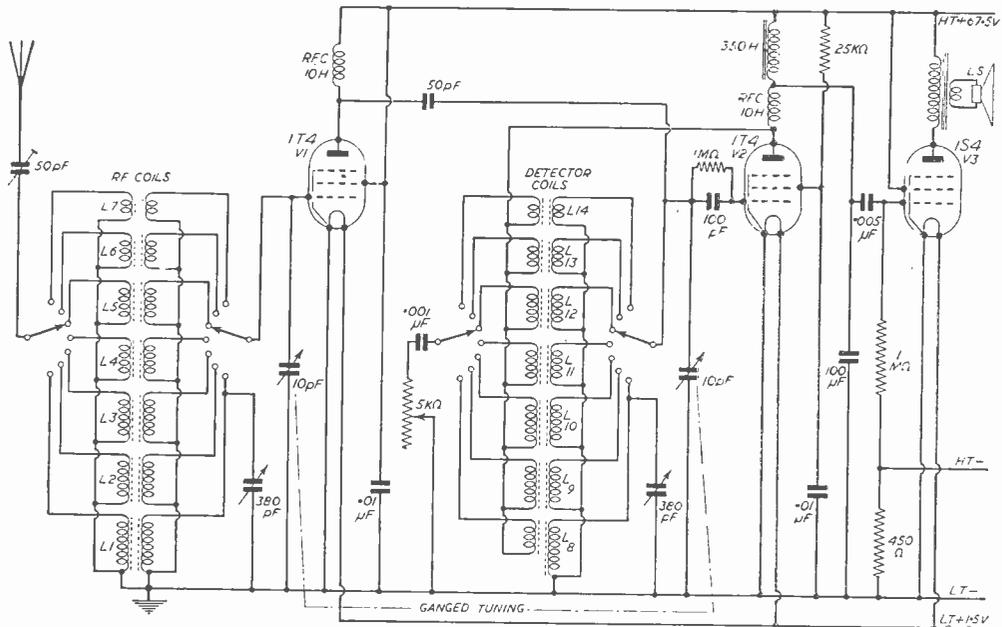


Fig. 1.—The most reliable general type of circuit for the beginner.

Layout

Returning to the original circuit the controls are : main tuning, bandswitch, reaction /on-off switch and aerial tuning. No volume control is necessary as slightly detuning will serve the same purpose. The components, with the exception of the 3in loud-speaker, are all mounted on an aluminium chassis of rather unusual dimensions, 6.5in. x 7.5in. x 2.5in. deep, as shown in Fig. 3. These dimensions have the advantage of keeping the receiver compact and the wiring short as well as assisting in below chassis screening. The bandswitch is placed immediately below the tuning gang and the coils are close up on each side so that the slug screws do not foul the tuning condenser. The screens between the coil banks are extended to one side of the chassis to isolate the R.F. valve wiring from that of the detector and also to act as supports for the reaction control and the aerial trimmer. The latter, incidentally, has one of the moving-plate tips bent so that it may be shorted out when required by fully closing it. The shafts of these two controls are of bakelite rod used with a brass coupling collar.

Reaction

The particular reaction circuit in this receiver is extremely quiet in operation and does not affect tuning to any noticeable extent. The parallel-fed coil is in series with a .001 μ F fixed condenser and the by-passing effect of the latter is controlled by the 5000 ohm potentiometer, giving very smooth reaction. This is helped considerably by the L.F. coupling, which is an impedance arrangement instead of the usual R.C. or transformer method. The choke required for this purpose should be of not less than 350 Henries, and could be higher with advantage. Such chokes, however, are rare and in their absence an ordinary intervalve transformer with its primary

and secondary connected in series will serve as well. When the coils have been wound and checked they

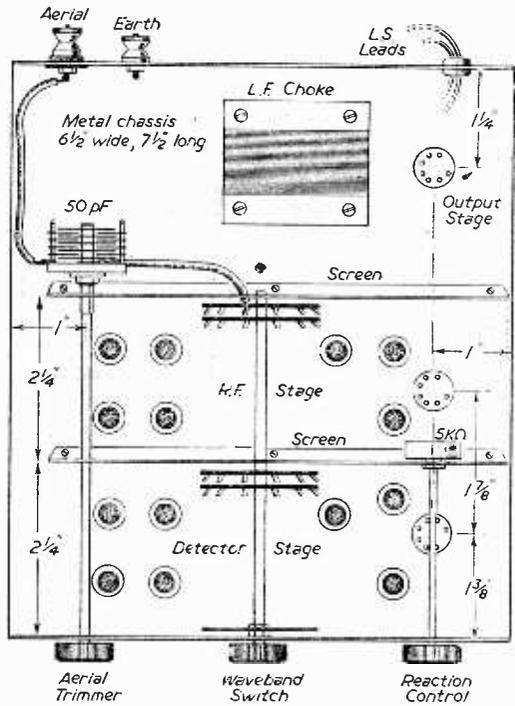


Fig. 3.—General layout arrangement.

• COIL DATA

Frequency	Primary	Secondary	Grid	Reaction
Broadcast	L1 25	100*	L8 100*	33*
3.5 to 4 Mc/s	L2 7	85 close-wound	L9 85 c.w.	28 c.w.
6.9 to 7.4 Mc/s	L3 5	45 turns spaced to 3/8 in.	L10 45 turns spaced to 3/8 in.	18 c.w.
13.95 to 14.45 Mc/s	L4 3	22 turns spaced to 3/8 in.	L11 22 turns spaced to 3/8 in.	9 c.w.
20.5 to 21.9 Mc/s	L5 3	15 turns spaced to 3/8 in.	L12 15 turns spaced to 3/8 in.	6 c.w.
27 to 30 Mc/s	L6 2	11 turns spaced to 3/8 in.	L13 11 turns spaced to 3/8 in.	5 c.w.
48 to 55 Mc/s	L7 1 1/2	6 turns spaced to 3/8 in.	L14 6 turns spaced to 3/8 in.	3 c.w.

* Hank (or wave wound) with 36 enamel S.W.G. All other coils wound with 34 enamel S.W.G. All formers Denco polystyrene dust cored, 1/2 in. diameter.

should be coated with polystyrene dope to prevent turns slipping and to keep out humidity.

A rough method of checking the wiring when putting the receiver into service is to touch a finger to the detector grid, when there should be a strong squeal and then to the R.F. valve grid which will result in a pronounced hum from the speaker. Next, turn the reaction control slowly until the usual rushing noise, indicating that the detector is oscillating, is heard. If there is no oscillation when the control is fully advanced the reaction winding should be moved nearer the grid winding, and if this is still insufficient add a turn or two to the reaction winding. It is possible that at the point of oscillation a strong howl will appear. A 50,000 ohm resistor across the L.F. choke will cure the trouble, and all that there remains to be done then is to tune in a station on each band and adjust the coil cores for maximum signal strength.



TRANSMITTING TOPICS

THIS MONTH THE PROBLEMS OF GRID DRIVE ARE DEALT WITH

By O. J. Russell, B.Sc. (G3BHJ)

ONE aspect of amateur transmitter operation is the vexed question of grid drive. All too frequently one hears remarks about "low grid drive," inability to obtain the rated grid milliamps on the more H.F. bands—and, of course, there is always the man who is able to obtain a phenomenal number of milliamps of grid current. Drive problems, like the poor, are always with us, and it is as well to examine this question of grid drive from first principles. A small dash of sound basic principles will be found superior to any amount of confused reasoning. Some of the conflicting matter that has appeared in the past has not served to clarify this matter. The following points are, in fact, presented for the genuine enquirer who is anxious to progress along sound lines to an understanding of how he may obtain the most efficient operation of his apparatus.

Grid drive is usually measured, in amateur practice, by observing the grid current reading of the driven stage. Providing the bias and other voltages are exactly as prescribed by the valve manufacturer, the P.A. stage is then operating under its optimum conditions. However, if one cannot meet exactly the maker's voltage ratings, things may be a little difficult. For example, if the grid bias is too low, a much higher value of grid current results. However, no one imagines that a reduction in bias provides "more drive." True, the R.F. output of the stage may increase, but this is at the expense of efficiency. In extreme cases the anode dissipation of the stage may be exceeded and the valve damaged, even though the total input would be within rating if the bias and drive were correct. Clearly correct drive is obtained *only* when the grid current is as specified at the specified bias value. Here again, with modern tetrode and pentode stages there is no merit at all in running with the correct bias, but with increased grid current. Output may actually be reduced, and the valve damaged. With triodes gross

over-running is not so serious, but with sensitive multigrid valves, high grid currents are dangerous to valve life. Furthermore, of course, T.V.I. harmonics are intensified by overdrive.

Grid Drive Power

The point is that grid current is only half the story. The real factor is the R.F. grid driving power. This is obtained only when bias and grid current are as specified by the maker. However, the amateur views the "rated grid drive power" figures quoted by makers with suspicion. His experience is that far more driving power has to be available than the maker claims. Thus, the popular 807 is quoted at some quarter of a watt grid drive for full R.F. output. On this basis it seems that a quite inefficient driver taking less than a watt of power would be more than adequate to drive an 807 to some 60 watts input. However, practical experience soon shows that the driving stage must provide far more R.F. output than the figure listed by the maker for the P.A. stage valve.

Here again, however, it must be firmly understood that the maker's drive figure is a value representing the actual R.F. drive power required *in the absence of any other sources of R.F. loss*. Accordingly, the practical value of drive power which the driver must supply is dependent upon several other conditions. Thus the frequency of operation, bias circuit losses and coupling circuit losses must all be carefully considered. Fortunately for the amateur all these points have been considered ages ago, and the

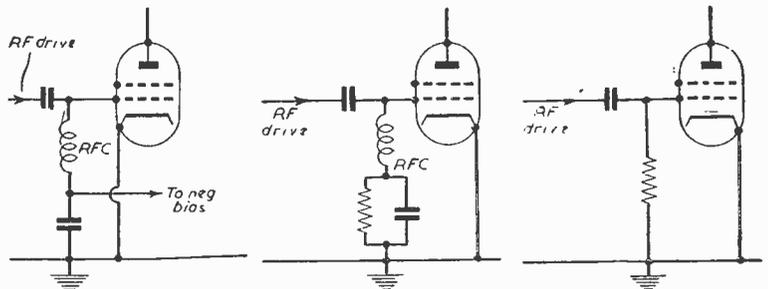


Fig. 1 (left).—Fixed bias circuit. Fig. 2 (centre).—By-passed grid-leak bias. Fig. 3 (right).—Un-by-passed grid-leak bias.

practical conclusions are quite simple. The minimum drive power required at relatively low frequencies, as for 1.8 and 3.5 Mc/s operation, should be at least *three* times the maker's quoted drive power figure. However, as the frequency is raised, additional losses must be considered, so that for 7 Mc/s and 14 Mc/s operation *five* times the rated maker's drive figure is required, while on 21 Mc/s and 28 Mc/s the available drive power should be at least *eight* times the rated drive figure. This presupposes that valves capable of efficient operation at these frequencies are used. Most modern valves; such as the

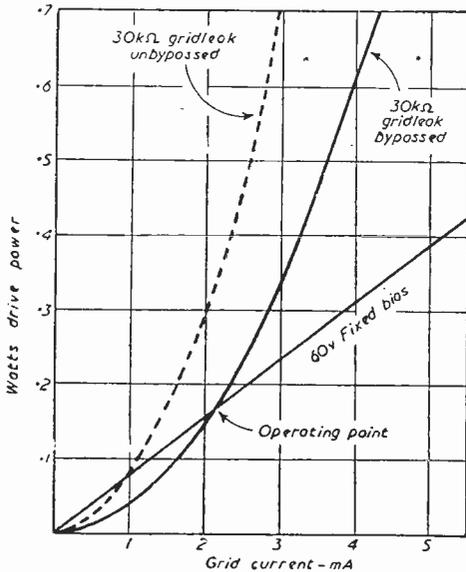


Fig. 4.—807 grid drive power requirements for the cases of 60 volts fixed bias, by-passed 30,000 ohm grid-leak, and for a 30,000 ohm grid-leak un-by-passed.

807, satisfy these requirements. When operation is extended to V.H.F. or U.H.F. it may become necessary to provide *twenty* or *thirty* times the nominal drive power from the driver stage. It is, of course, on the higher frequencies that drive becomes difficult, particularly as it is difficult to obtain good output from the driver stage itself on the higher frequencies. It is, in any case, clear that inadequate drive may be due, to a too optimistic reliance upon the quoted maker's drive figure as a guide to operation on the short-wave and ultra-short-wave regions of the spectrum. The multiplying factors suggested will be found suitable for the average amateur rig. In fact, a really efficient layout would reduce these factors. A really inefficient layout, of course, is very wasteful of drive power, particularly if stray capacities are high.

Grid Bias

A further point to observe is that the grid driving power depends somewhat upon the type of bias arrangement in use to obtain the grid bias. The circuit diagrams illustrate three common methods. These are battery bias, grid-leak bias with the leak by-passed to R.F., and grid-leak bias with the leak

not by-passed to R.F. The differing behaviour of these arrangements is shown in the graph, which represents the R.F. grid power of an 807. It is assumed that 2 mA. represents the optimum grid current, and that 60 volts is the required bias. Both in the fixed bias case and the by-passed grid-leak case the R.F. grid drive power is the same at the selected operating point. However, with the grid-leak an increase in drive grid current represents a greater drive power requirement than for fixed bias, while at lower grid currents the grid-leak bias case takes less power than the fixed bias case. It can be seen, therefore, that grid-leak bias is to some extent self-compensating for changes in grid drive power. If more drive is applied, this is opposed by the increased bias developed across the grid-leak, while if the drive falls slightly the bias also falls, and to some extent offsets the loss of drive. This is a useful feature of grid-leak bias, and it is often employed in conjunction with fixed bias. The fixed bias keeps the P.A. from drawing excessive anode current when drive is removed, while when the drive is applied the grid-leak makes up the extra bias required for Class C operation.

'Phone Operation

It will be noticed that an un-by-passed grid-leak is wasteful of drive, as the grid-leak is itself a load on the R.F. source, so that R.F. power is wasted in the grid-leak. The use of an un-by-passed grid-leak is quite common in low-level driver stages, but if used for the P.A. stage the extra power loss may unduly reduce drive at the higher frequencies where drive is critical. If drive is a bit difficult, therefore, an improvement may be effected by by-passing the grid-leak to R.F. Furthermore, of course, the grid drive power figures on the graph are equivalent to those quoted by the maker, and under any given conditions they should be multiplied by the factors previously given in order to obtain the actual drive power that should be available. The operating conditions here chosen for the 807 are suitable for C.W. operation at medium inputs. For 'phone operation, or for full-power C.W. working, the operating point of 3 mA. at 60 volts should be chosen. For grid-leak bias this would then require a grid-leak of 20,000 ohms to provide the 60-volt bias at 3 mA. grid current.

A CHRISTMAS GIFT FOR YOUR FRIENDS AND RELATIONS—


At the present time when many of the good things of life are either very expensive or in short supply, the Christmas Season presents many problems—but when it comes to buying gifts, there is one simple and effective solution—you can arrange for us to send your friends and relations who share your interest in wireless, PRACTICAL WIRELESS every month from Christmas to the end of 1954.

Gift Subscriptions are not only original—they give pleasure and act as a reminder of your good wishes the whole year through.

An attractive Greetings Card will be sent at Christmas time in your name with the first Gift Copy.

It is simple to arrange, for we can send subscriptions to any address, at home or abroad, at the annual rate of 13/6d. (Canada 13/-).

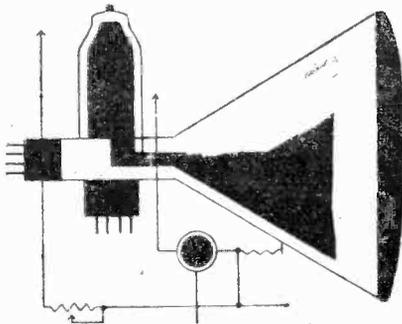Write to the Subscription Manager, PRACTICAL WIRELESS (Dept. G.2.), Tower House, Southampton Street, Strand, London, W.C.2, enclosing the addresses of your friends with remittance to cover and we will do the rest.



**Smith's
for
current
"know how"**

From Smith's shops and book-stalls you can quickly obtain technical books on the latest developments in circuit design, new components, methods and new theories. Books not actually in stock can usually be supplied within a day or so.

Smith's Postal Service can send books to any address at Home or Overseas. Lists of the standard works on any subject gladly supplied upon request.

**W. H. Smith
& Son**

FOR TECHNICAL BOOKS

HEAD OFFICE: STRAND HOUSE, LONDON, W.C.2

**Five Tips
FOR FASTER
SOLDERING**

TRIGGER-FEED SOLDERGUN

The Wolf Type 51 with its trigger-feed action is indispensable to all modern assembly

GENERAL INDUSTRIAL PURPOSES

Type 21—complete with chisel bit and perfectly balanced easy-grip handle. Heavy Chrome finish. Net weight 7 1/2 oz.

FINE INSTRUMENT WORK

Type 31—complete with two bits, one straight and one angular—easily interchangeable. Net weight 8 oz.

FINE TO MEDIUM WORK

Type 41—complete with easily adjustable diagonal bit—the temperature can be controlled by extending or shortening the bit. Net weight 8 oz.

MEDIUM TO HEAVY WORK

Type 71—complete with square section bit, heavy chrome finish, plastic easy-grip handle. Net weight 9 1/2 oz.

EXTRA HEAVY WORK

Type 81—complete with 1 1/2 oz. bit and easy-grip plastic handle heavy chrome finish. Net weight 2 lb.

SOLDERING IRONS

Models 21 and 31 also available with straight handles and heat deflecting skirt. Ask for models 22 and 32

**Wolf Electric
SOLDERGUNS
AND SOLDERING IRONS**

★ Obtainable from all leading tool merchants and factors.

WOLF ELECTRIC TOOLS LTD

PIONEER WORKS · HANGER LANE · LONDON · W.5
Branches: Birmingham Manchester Leeds Bristol Glasgow · Tel. Perivale 5631-4


Sound advice to home constructors...

1. Build a **GOOD** set
2. Use **MULLARD** Valves & Tubes

If you are devoting many hours of leisure time to building a set, build a *good* set, one that will repay you with first class results.

And to be sure of getting first class results choose Mullard Valves and Mullard Long-Life TV Tubes — the best that money can buy.

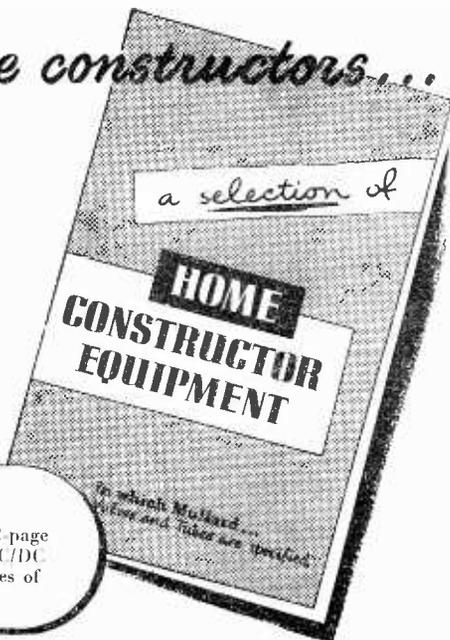An interesting list of equipment — it covers TV and sound receivers, I.F. Amplifiers and tape recorders — for which Mullard Valves and Tubes are specified, is available free of charge. Send a stamped addressed envelope to the address below for a copy of "A Selection of Home Constructor Equipment".



FREE! FROM YOUR DEALER

Available from your usual dealer is a free 32 page booklet, "The Universal Large Screen AC/DC Television", reprinted by Mullard from a series of articles by A. S. Torrance.



Mullard Ltd., Valve Sales Dept., Century House, Shaftesbury Avenue, London, W.C.2.

MVM 250

THE "TELE-VIEWER"

5 CHANNEL TELEVISOR

A Design of a Complete 12in. or 9in.

SUPERHET T.V. RECEIVER FOR THE HOME CONSTRUCTOR

This receiver has been developed after most careful research and affords a high standard of Television entertainment by producing a picture of *really outstanding* quality.

We confidently believe that not only have we achieved a T.V. Receiver that surpasses in efficiency any other designed for the home constructor, but that successful construction, even by the most inexperienced is assured by the step by step wiring detail and diagrams provided, and at about half the cost of the nearest comparable commercial receiver.

Here are some of the features which combine to make this such a fine receiver :

- The Superhet circuit easily tuned to any of the five channels, i.e. LONDON, SUTTON COLDFIELD, HOLME MOSS, WENVOE and KIRK-O-SHOTT'S. (The extreme ease of tuning is accomplished by the provision of pre-aligned I.F.T.'s.)

- A lifelike, almost stereoscopic, picture quality made possible by the following factors :

(a) Excellent band width of I.F. circuits. (b) A really efficient video amplifier. (c) C.R.T. Grid modulated from low impedance source, (d) High E.H.T. voltage (approx. 10 kV.)

The picture brilliance is also much above the average and enables comfortable viewing with normal room lighting or daylight.


- FIRM picture "HOLD" circuits (Frame-Line) ensure a steady picture, free from bounce or flicker even under the most adverse conditions met with in "fringe" areas and excellent "interlace" ensures the absence of "liney effect."

- Negative feedback is used in the audio frequency circuits which provide 2 3 watts of High Quality Sound.

- Entire receiver built on two chassis units, each measuring 14½in. x 6½in. x 3½in.

- Rigid C.R.T. mounting enables entire receiver to be safely handled with tube in position.

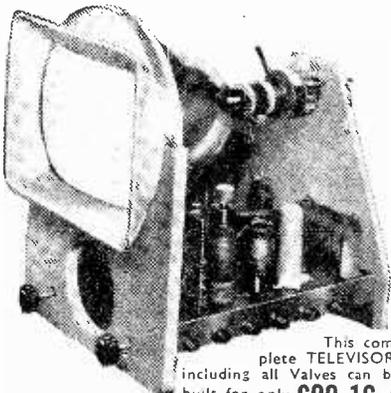- All pre-set controls are mounted on side of chassis enabling all adjustments to be carried out whilst facing the C.R. Tube. As no hire purchase terms are available the receiver can be bought in five separate stages (practical diagrams and circuits are provided for each stage) thus enabling hire purchase interest rates to be avoided.



This complete TELEVISOR, including all Valves can be built for only **£28-16-4** (plus cost of C.R.T.)

We can sometimes supply New Mullard 12in. C.R.T. at the specially reduced price of **£13/17/6**. These, when available, are for purchasers of the Televiewer only.

Complete set of ASSEMBLY INSTRUCTIONS is now available, price 5/- The instructions include really detailed PRACTICAL LAYOUTS, WIRING DATA AND COMPONENT PRICE LIST. ALL COMPONENTS ARE AVAILABLE FOR INDIVIDUAL PURCHASE. A CABINET WILL ALSO BE AVAILABLE.

STERN RADIO LTD.

109 & 115, FLEET STREET, E.C.4.

Tel. : CENTRAL 5812-3-4

A SUBSTITUTION CHECKER

A VERSATILE INSTRUMENT-FOR THE EXPERIMENTER

By H. R. Singh

VERY often a constructor is confronted with a receiver where a condenser or resistor has become faulty and beyond recognition due to over-heating or some similar contributory cause.

Where no service data is readily available one has to determine its value by trial and error. This is a long process and involves quite an amount of repetition work, together with a great deal of soldering. It is in such cases as this where a "Substitution Checker" is of great help.

The instrument to be described is unique in that, with only 20 resistors and 19 condensers a total of over 1,000 different circuit and component selections are possible. Thus, in the hands of the keen con-

structor it is a versatile little instrument which can be put to many more uses than that mentioned above. The components one at a time. Two switches, T1 and T2, suitably labelled "Bank 1" and "Bank 2," select either of the main switch banks to which the resistors and condensers are connected. In this way, all the components in either bank can be selected and transferred to their respective sockets indicated in "Red" and "Blue." With suitable coloured leads terminating in crocodile clips and plugs, these socket points can then be coupled to any section of the circuit under investigation.

Circuit Selection

Circuit selection is an easy matter and is made possible by the use of suitably designed coloured

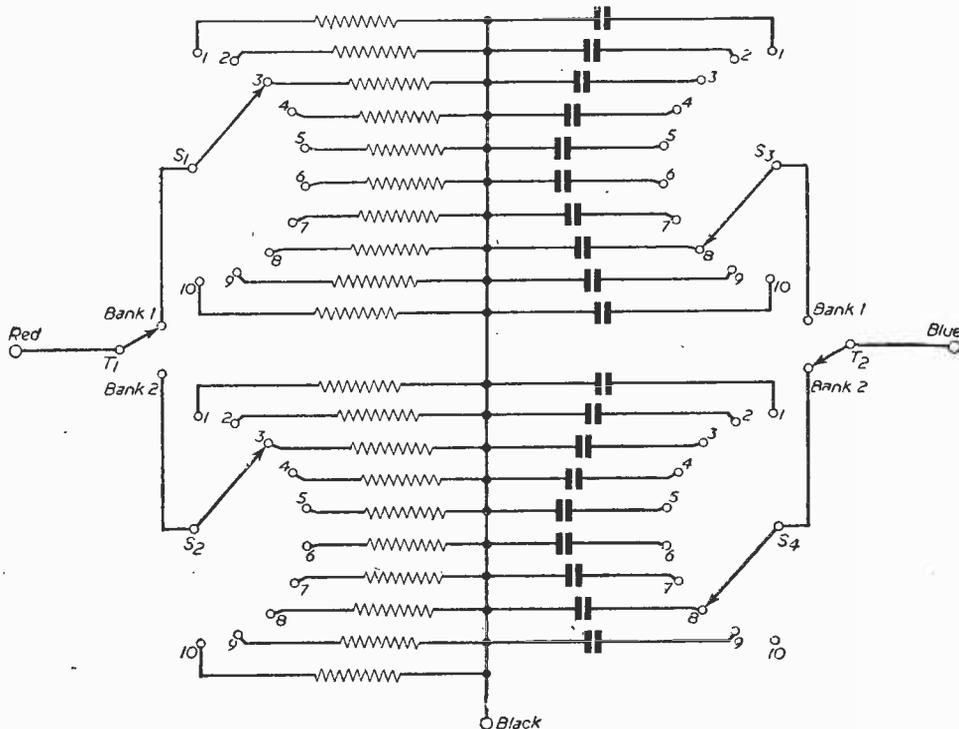


Fig. 1.—General theoretical circuit of the checker described in this article.

structor it is a versatile little instrument which can be put to many more uses than that mentioned above.

Circuit

The circuit of the instrument, which is practically self-explanatory, is shown in Fig. 1. It consists basically of two "selector" switches S1—S2 and S3—S4 (S1 and S2 are ganged together, so are S3—S4) to which are connected a selection of 20 resistors and 19 condensers. The function of these switches, as their name implies, is to select any one of

leads, shown in Fig. 2. The colour of the leads corresponding with the socket colours on the instrument panel.


Three leads should be made up, as shown at "a," one each in "red," "blue" and "black." And one as at "b" which can be any colour. The number of circuit combinations possible is shown in Fig. 3. It will be noted that there are five circuits altogether, and circuits "a," "b," "c" and "d" are selected by plugging in the appropriate coloured leads to Fig. 2 (a). To select the parallel circuit shown

at "e," Fig. 3, the lead of Fig. 2 (b) is required together with the "black" coloured lead which plugs into the black socket.

Component Selection

Having selected the circuit, it now remains to choose suitable component values. This can be done by first drawing up a table, as shown, on White Bristol board in Indian ink, and gluing it into position on the bottom of the case, so that it can be seen from a sitting position, when the instrument is resting on its back.

Bank 2 ...	27 K Ω	39 K Ω	50 K Ω	100 K Ω	220 K Ω	330 K Ω	470 K Ω	1 M Ω	2.2 M Ω	4.7 M Ω
Bank 1 ...	50 Ω	100 Ω	220 Ω	500 Ω	1.5 K Ω	3.3 K Ω	5 K Ω	10 K Ω	15 K Ω	20 K Ω
Selector Switch	1	2	3	4	5	6	7	8	9	10
Bank 1 ...	50 pF	100 pF	200 pF	300 pF	500 pF	.001 μ F	.002 μ F	.003 μ F	.005 μ F	.01 μ F
Bank 202 μ F	.03 μ F	.05 μ F	.1 μ F	.25 μ F	.5 μ F	2 μ F	8 μ F	25 μ F	—

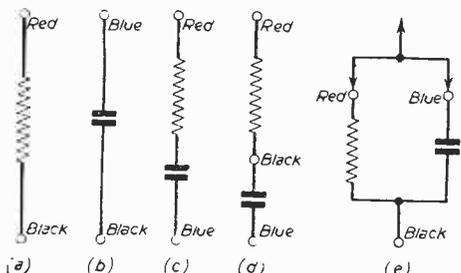

It will be seen that this table gives details of component values with respect to "selector" and "toggle" switch positions. Thus, if a 100 ohm resistor is called for, toggle switch T1 is switched to position marked "Bank 1" and selector switch is set to position "2" on the resistor dial. For a 470 K Ω resistor T1 is set to "Bank 2" and the selector to position "7." Similarly, selections can be made in the condenser range.

To illustrate the system somewhat more clearly,

COMPONENTS LIST

BANK 1		BANK 2	
R1—50 Ω	R6—3.3 K Ω	27 K Ω	330 K Ω
R2—100 Ω	R7—5 K Ω	39 K Ω	470 K Ω
R3—220 Ω	R8—10 K Ω	50 K Ω	1 M Ω
R4—500 Ω	R9—15 K Ω	100 K Ω	2.2 M Ω
R5—1.5 K Ω	R10—20 K Ω	220 K Ω	4.7 M Ω

BANK 1		BANK 2	
C1—50 pF	C6—.001 μ F	.02 μ F	.5 μ F
C2—100 pF	C7—.002 μ F	.03 μ F	2 μ F
C3—200 pF	C8—.003 μ F	.05 μ F	8 μ F
C4—300 pF	C9—.005 μ F	.1 μ F	25 μ F
C5—500 pF	C10—.01 μ F	.25 μ F	None

S1—S2—Two-pole, 10-way, two bank Yaxley Switch.

S3—S4—Two-pole, 10-way, two bank Yaxley Switch.

T1—T2—S.P.D.T. toggle switches.

2—Small pointer knobs.

3—Insulated sockets, Red, Blue and Black.

5—Plugs to suit above.

4—Crocodile clips.


let us arrange a complete switching for the parallel circuit of Fig. 4.

On the resistor range, set :—
T1 to Bank 1.
Selector to 4.

On the condenser range, set :—
T2 to Bank 2.
Selector to 9.

Use leads "a" (black) and "b" of Fig. 2.

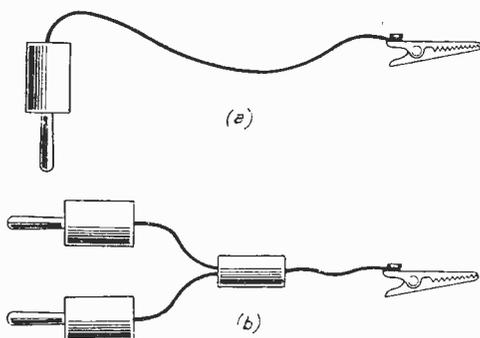The two crocodile clips can now be connected to the experimental circuit.




- (a) = 20 selections
- (b) = 19 "
- (c) = 380 "
- (d) = 380 "
- (e) = 380 "

Total selections = 1179

Figs. 2, 3 and 4.—Left, Details of the combinations which may be obtained on the worked example above.

Construction

No special considerations are required in the construction of this unit. As most constructors will have quite a number of spare parts in hand or obtain components cheaply from the surplus market, dimensions of which might differ from those used in the original, it was decided not to give any measurements. In the prototype, however, all switches and components were mounted on a 20 S.W.G. grey metal panel measuring 6in. x 9in., which was afterwards fitted into a hand-polished wooden case. Two dials were then made and fitted to the two range selector switches. Each dial has a 1/16in. thick Perspex cover with a small pointer knob. The dials were marked 1 to 10 with Indian ink on White Bristol board. In order that the instrument will present an all-round pleasing appearance, a symmetrical layout was maintained throughout.

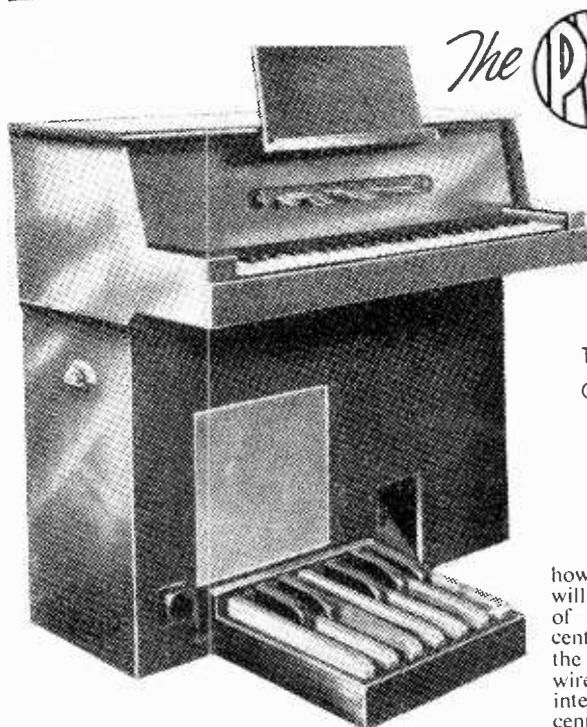

The  FULL-COMPASS
Electronic
ORGAN

This Month Constructional Details are
Given of the Mechanical Work Involved
in the Tab-board Assembly

By W. J. Delaney (G2FMY)

(Continued from page 680 November issue)

THE next step is to wire up the keys and distribution strip, but different keyboards will require slightly different treatment. A board was mentioned in the November issue to cover the keyboard and upon which are mounted the distribution strip, etc. Details of assembly are as follows: Beneath the distribution strip a sheet (or two or more odd pieces) of aluminium are mounted running the entire length of the strip, and being 4in. in width. The total width of the board should be such that there is left a space 5in. in width between the front cable run, and the edge of the aluminium strip just mentioned. Further pieces of aluminium are now cut and bent so that they may be mounted on either side of the distribution strip to form a box without a lid, the overall height being also 4in. A lid either in one length or two or more odd lengths will finally be needed. This should be clear from the illustration at the foot of page 679 last month.

Screw down the bottom piece of aluminium to allow the dimensions above mentioned and then complete the distribution strip by mounting in the upper row of holes 168 B.T.S. type Dubilier resistors of 10 M Ω each (20 per cent. tolerance). In the lower row mount the same number of 2.2 M Ω resistors. It will be noted that the number specified does not allow for three resistors to each note, and the upper octave (on the right viewing the distribution strip from the front) has only two channels provided for a reason which will be seen later. Bend forward the lower ends of the 2.2 M Ω resistors and if you wish to save some time and trouble at a later stage short lengths of coloured insulated sleeving may be slipped over the ends using an identical colour for all the centre resistors and other colours for the left- and right-hand ones. This is not essential,

however, as the holes are drilled at an angle and this will help to identify them. Attach the strip by means of the small brackets already mentioned, on the centre line of the aluminium strip with resistors to the front, and then, having already checked that the wires from the key contacts are electrically sound inter-connect them as follows. The contact in the centre of the three over each key is joined to the centre of the three resistors for that note, whilst the left-hand key contact is joined to the right-hand resistor of the group for the same note one octave lower. Similarly, the right-hand key contact is joined to the left-hand resistor of the group for the note one octave higher. To assist in identification the note values may be scratched on the top of the distribution strip starting from B at the extreme right and working downwards. Checking will be difficult here unless an ohm-meter reading in meg-ohms is available, so care is needed not to mix up the wires and connections. One advantage of this design is that it will be a fairly simple matter to sort out any errors at a later stage and correct them.

Tab Board

The most tedious and difficult part of construction is now completed, and it will well repay the constructor to spend considerable care and time over this part of the work, as no matter how good the rest is the entire operation depends upon clean key switching—all notes sounding with the same key movement, etc. The next part of the work, which is also mechanical and calls for some care for efficient working, is the tab board, by means of which the note range of the organ is selected and the tones controlled. This also may be seen in the illustration on page 679 already referred to, and for it one needs some more aluminium sheet, a length of $\frac{1}{2}$ in. silver steel rod, another piece of the $1\frac{1}{2}$ in. paxolin strip and some ex-government or P.O. switches. In the event of the latter being unobtainable, the switches may be made up by using strips of the phosphor bronze already referred to, some $\frac{1}{4}$ in. 6 B.A. bolts and nuts and some P.V.C. or paxolin tubing which will just fit over the 6 B.A. bolts.

To assist those who wish to construct the switches, the arrangement is shown in "exploded" form in Fig. 11 from which the assembly should be found fairly simple. The separate switches, of which 14 are simple closed-circuit components and one a triple assembly of the same arrangement, are mounted on the paxolin strip cut to 12½ in. in length, as shown in Fig. 10. When making or assembling these switches from dismantled standard components, use thin insulated strips between the contacts so that

in the sketch, and no exact dimensions can be given as it depends upon the type of spring which is used.

The ends of the silver steel rod are inserted into holes in the end cheeks, and to prevent the rod moving sideways small brass strips are screwed to the wood. Lengths of paxolin tubing or other tube are then inserted between each arm to act as distance pieces, and again, if paxolin is not available, ordinary thin bamboo or cane rods may be cut up. Fig. 11 shows a perspective view of the assembly, and the upper operating face is cemented on after the rocker arms have all been mounted and found to jump satisfactorily. The aim is to have these so that they only require a slight touch to jump from "down" to "up," and again some time must be spent in obtaining

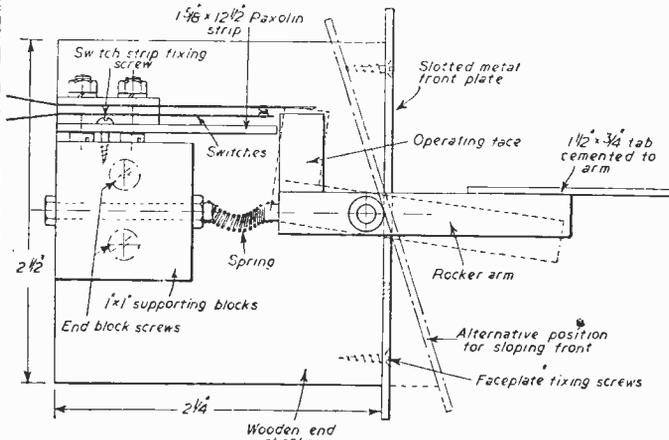


Fig. 9.—Details of the tab switches.

the contact points are normally closed. If it is desired to make silver contacts, the phosphor bronze strip should be drilled and a short length of silver wire riveted in the holes, but this is by no means essential, as already pointed out.

The next difficult job is to make the operating toggle. For these, ¼ in. Perspex sheet is cut to form 15 strips 2½ in. long and ¾ in. wide. A hole is drilled to take the ¼ in. silver steel rod as shown in Fig. 9, and it should here be pointed out that all illustrations are to scale so that the constructor can take off any item which is not actually given a dimension. The end nearest the hole is then filed round by taking off the corners of the Perspex with a file, and the resulting round "key" ¼ in. long is left approximately the diameter of a 6 B.A. bolt. Next, a number of short springs are required, and although the spring curtain rod obtainable from the popular stores may be used, it is rather heavy for the purpose and a lighter gauge is preferable. Most ironmongers carry stocks of springs and long ones may be cut down, and they may be pulled out to give the desired tension. Experiments should be carried out on a single key, mounted as shown in Fig. 9. A ¼ in. 6 B.A. bolt is pushed into a 1 in. by 1 in. block of hardwood and locked with a nut which will leave a short projecting piece. The spring is placed over this and over the round key on the end of the tab or rocker-arm. Using the spacing shown in Fig. 9, cut the spring so that it will provide a toggle action to the rocker arm. It should be slightly under compression and of such a length that as the end of the arm is lowered the spring will jump to a position above that shown

LIST OF COMPONENTS
For pre-amp unit, circuit

- RESISTORS**
(All Dufillier type B.T.S. ½ watt 20% except where stated.)
- Two at 2.2 Ω.
 - One at 4.7 KΩ.
 - Two 12 KΩ (10%).
 - Nine 47 KΩ.
 - One 22 KΩ.
 - Two 100 KΩ.
 - Two 220 KΩ.
 - Nine 470 KΩ.
 - Four 1 MΩ.
 - One 2.2 MΩ.
 - Three 10 MΩ.

- CONDENSERS**
(All T.C.C. except where stated.)
- Three at 100 pF (Type 101 SMP).
 - Two 2,700 pF (Type CM25).
 - Three 3,300 pF (Suflex, 500 v.w.).
 - One 4,700 pF (Suflex, 500 v.w.).
 - One .005 μF (Type 543).
 - Two .01 μF (Type CP33S).
 - Five .02 μF (Type CP33N).
 - Three .05 μF (Type CP37S).

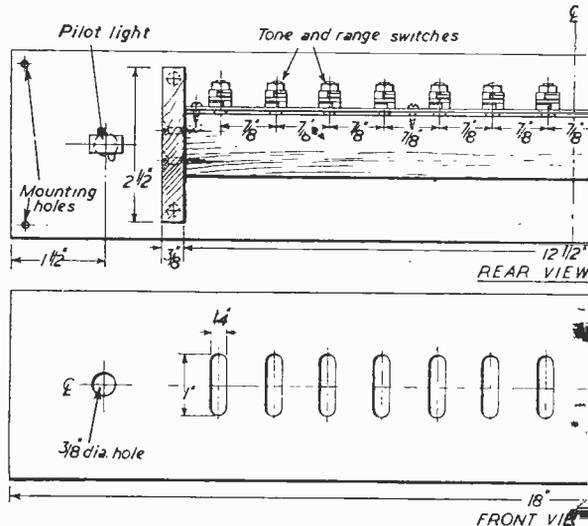


Fig. 10.—Details of the assembly

electrical side may be proceeded with. The next stage to be described will be the pre-amplifier, tone-control stage and vibrator. the theoretical circuit for which is given below. These three stages are mounted on one

the three stages are housed in a small metal chassis measuring 9in. by 4½in. A drilling and cutting diagram is given and it should be noted that a fixing flange is recommended so that the chassis may be

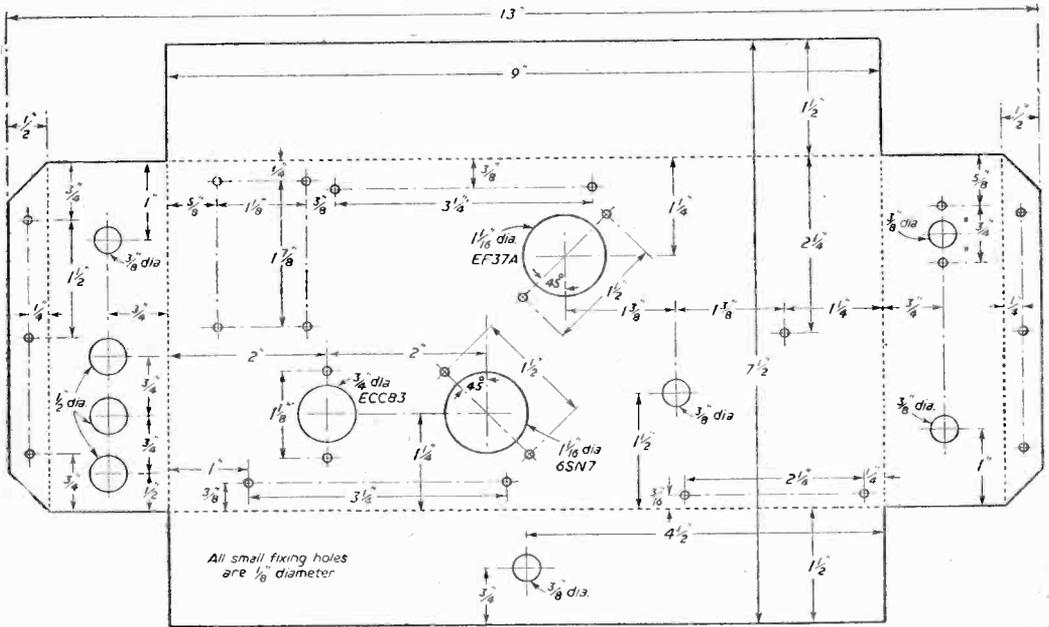


Fig. 12.—Chassis cutting and drilling details for the pre-amp.

chassis which fits between the screening box holding the distribution strip and the front cable run. Again, this may be seen in the illustration on page 679, and

finally fitted with a base cover. A list of parts is given and a wiring diagram will be given in the next issue.

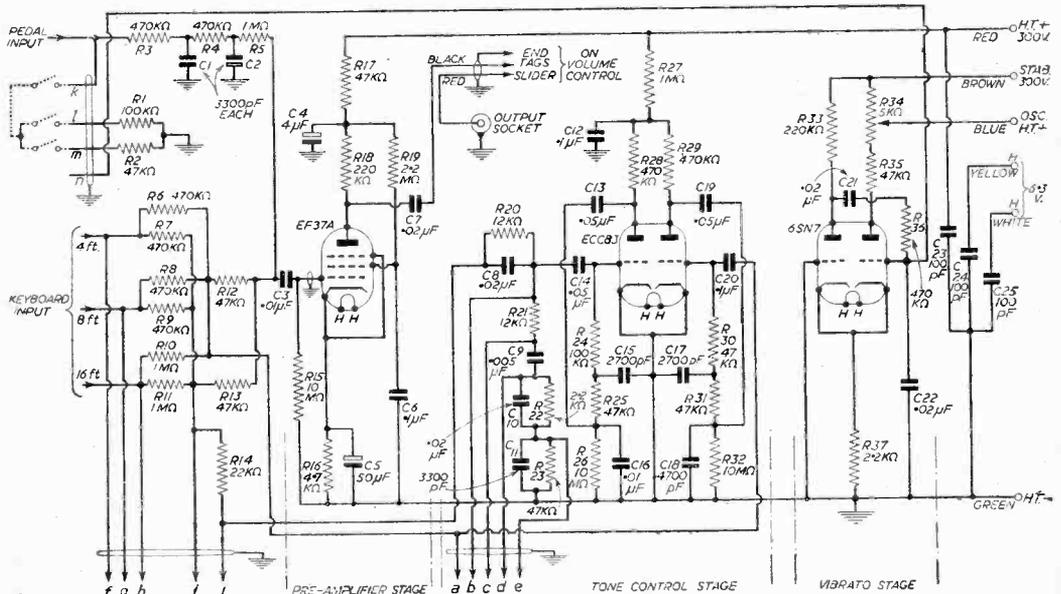


Fig. 13.—Circuit of the pre-amp unit, which includes the tone filter stage and the vibrato oscillator.

Great Britain's Valve Mail-Order House


Kindly mark Envelope PW 12



Table listing various vacuum tube types and their corresponding part numbers. Columns include tube types (e.g., AC HL, AC HLD, AC044) and their respective part numbers (e.g., EA59, EAC91, EAF42).

Subject to stock and price changes.

MINIATURE DUAL PURPOSE COILS

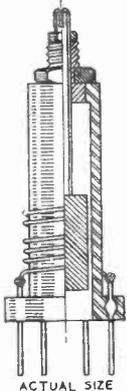

ACTUAL SIZE

- ★ Each coil can be used for either Chassis mounting or plugging into a standard Noval (9 pin) valveholder.
- ★ Litz windings where required on L.F. Ranges.
- ★ Complete range for superhet or straight receivers covering approx. 150 Kcs.—78 Mc.s.
- ★ The former and base are completely moulded in colour coded polystyrene.
- ★ The following colour code identifies the Coils:—
BLUE—Grid coil with aerial coupling winding. For R.F. or mixer, 3 1/2.
YELLOW—Grid coil with coupling for reaction or R.F. anode. Straight or Mixer following R.F., 3 1/2.
GREEN—Grid coil with reaction and coupling windings (6 pin), 4 9.
RED—Superhet Oscillator 465 Kc.s. 3 1/2.
WHITE—Superhet Oscillator 1.6 Mc.s. 3 1/2.
 (Note.—Range 6 and 7 can be used for various I.F.s.; no white coils are made for these ranges.)

- ★ Complete technical information on the coils and full instructions for their use is given in our **TECHNICAL BULLETIN DTB.4**, price 1/6.
- ★ Formers of the above coils complete with cores are available in the following colours: 4 pin. Blue, Yellow, Red, Clear; 6 pin. Green. Price 1/8.


RANGE	1	2	3	4	5	6	7
MC.S.	150/140	56/545	167/53	5/15	10.5/31.5	30/50	45/78
METRES	2000/750	580/194	180/57	60/20	28/9.5	10/6	6.6/3.8
WHEN USING A 1.6 MC I.F. RANGE 1 COVERS 1	COVERS 175/525MC. 1700/570M.						

Send for our General Catalogue, price 9d.

DENCO (CLACTON) LIMITED,
Old Road, Clacton-on-Sea, Essex.

COMPACT TV.

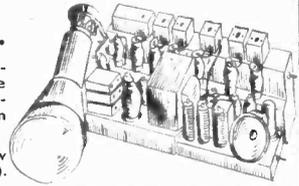
The NEW 1355 Conversion data for all five Channels, Sound, Vision, T.B.'s, Power, on one 1355 Chassis
NEW EDITION, now only 2/8! (post free).



METERS	TRANSFORMERS	NEW VALVES
0/500 μ A. scaled	multi-purpose components which may be used as H.D. output, intervalve or mains. giving approx. 24 v. ac. 2 A (4 tappings) and 300 v. 30 mA.	5U4G ... 7/6 L63 ... 5/6 H63 ... 5/6 6E5 ... 9/- 6S17 ... 6/6 0Z4 ... 4/6 6L7 ... 4/6 6H6 ... 3/6 6I7 ... 6/6 6X5 ... 8/6 1005 ... 3/6
0/150. in small sloping front black crackle cases. 12/6		
P.U. CHASSIS, with transformer, choke, condensers, relay, etc. 3/6	ONLY 5/- each (fully shrouded).	
STATIC SUPPRESSORS (plug-in) 3/6		

WILLARD ACCUMULATORS in non-spill transparent plastic cases, with built-in hydrometers. 2 V. 20 AH in sealed maker's cartons (measure 5 1/2 x 3 1/2 x 2 1/2). 12/6	CARBON MIKES , with 5fc. lead and switch. 3/6 and 5/-. DAMAGED METERS , 5 for 6/-. DINGHY Tx CHASSIS (partly stripped), 5/-. METER TEST LEADS (high insulation), 3/6 per pair.
--	---

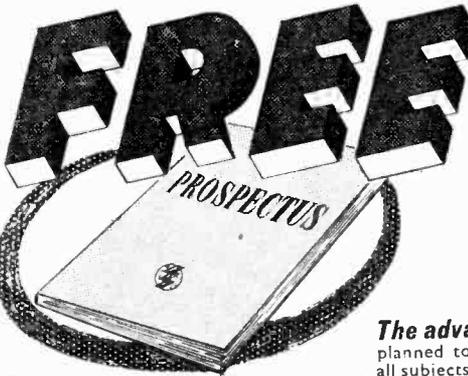RADIO EXCHANGE CO.
14 ST. MARY'S STREET, BEDFORD
Phone 5568



POST THE COUPON TODAY FOR OUR BROCHURE ON THE LATEST METHODS OF HOME TRAINING FOR OVER 150 CAREERS & HOBBIES

PRIVATE AND INDIVIDUAL TUITION IN YOUR OWN HOME

City and Guilds Grouped Certificate in Telecommunications: A.M. Brit. I.R.E. Examination, Radio Amateur's Licence, Radio and Television Servicing Certificates, General Radio and Television Courses, Radar, Sound Recording, etc. Also Courses in all other branches of Engineering and Commerce.

The advantages of E.M.I. training. ★ The teaching methods are planned to meet modern industrial requirements. ★ We offer training in all subjects which provide lucrative jobs or interesting hobbies. ★ A tutor is personally allotted by name to ensure private and individual tuition. ★ Free advice covering all aspects of training is given to students before and after enrolling with us.

NEW LEARN THE PRACTICAL WAY.
With many of our courses we supply actual equipment thus combining theory and practice in the correct educational sequence. Courses include: Radio, Television, Electronics, Draughtsmanship, Carpentry, Photography, and Commercial Art, etc.

Courses from £1 per month

POST THIS COUPON TODAY

Send without obligation your FREE book.
 E.M.I. INSTITUTES, Dept. 32K
 43 Grove Park Road, London, W.4.
 Phone: Chiswick 4417/8.

EMI INSTITUTES
The only Postal College which is part of a world-wide Industrial Organisation.

NAME _____
 ADDRESS _____
 SUBJECT(S) OF INTEREST _____

An Electrically-operated Coil-winder

FITTED WITH A TURNS COUNTER, THIS INSTRUMENT WILL WIND LAYER OR WAVE-FORM COILS


(Concluded from page 687, November issue.)

MOVEMENT is effected by means of a small threaded rod passing into the flanged piece and controlled by a little wheel fitted to a small bracket soldered to the lower plate (see Fig. 1). This provides for a minute adjustment of the angle of the two plates and therefore the pressure applied to the flanges of the wire-reel.

The illustration of the underside of the base plate shows the position of the motor and variable resistor. The tapped dropping resistor shown below the motor is necessary in the writer's case as the motor used was a 110v. type. There are many ex-Government 230v. motors on the market which are suitable for driving this machine. One of approximately 1/20th h.p. or more should be suitable and in the interests of smooth running and quietness it should be mounted on rubber bushes. A very small pulley is fitted to the motor and a belt from this connects to the largest pulley of the main pulley bank via the rectangular slot in the base plate. This arrangement reduces the speed at the main shaft—for the motor speed, assuming a high revving type, would be too fast—and at the same time imparts the utmost power to the machine. As will be seen, the whole base plate is surrounded with thick felt to ensure a smooth-running machine. The underside of the box, too, is fitted with rubber corners. A condenser of 0.01 μ F may be required across the brushes of the motor if interference is caused.

In order to control the speed of the motor a variable resistor is connected in series with it. This component must be capable of carrying the current of the motor and upon this figure will depend the value of resistor required. Another factor bearing on this point is the amount that the voltage has to be dropped before the motor ceases to work. So the best plan to adopt is to connect in series with the motor a 0.3 amp. tapped dropping resistor as used in A.C./D.C. sets. One of these is usually available and motors of the type required seldom take more than 0.3 amp. Then, with the motor on load, i.e., working the machine, adjust the tappings so that the winder is working as slowly as possible. Measure off this resistance and obtain a variable type of similar value. The one shown is of robust construction on ceramic former and has a value of 500 ohms. This heavy type of potentiometer or variable resistor is available from many advertisers.

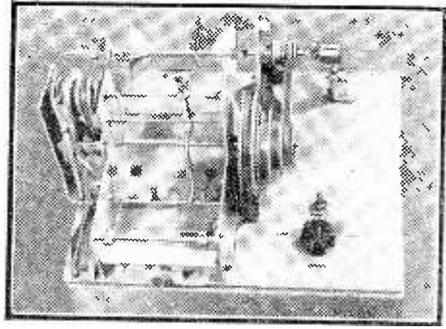The wave-winding attachment is worked by bevel gears driven by the main shaft (see Fig. 1). These



were taken from ex-Government gear, but if the reader finds them difficult to procure, such gears are often available in constructional toy spares. Alternatively, two small fibre pulleys, one running edge-wise on the flat periphery of the other, would undoubtedly work, as the power required is extremely small. The ratio, however, should be 1 to 1. The disc which provides the piston action is 11/16in. in dia. and has a 6 B.A. bolt soldered to the outer edge—radius 7/16in. A link rod loosely connected from this bolt is joined to a similar bolt soldered to the metal strip 3/4in. x 1/4in., which provides the necessary movement for this type of winding. The bolt is soldered 15/16in. from the top. The arm is swivel-connected to a small bracket bolted to the base plate.

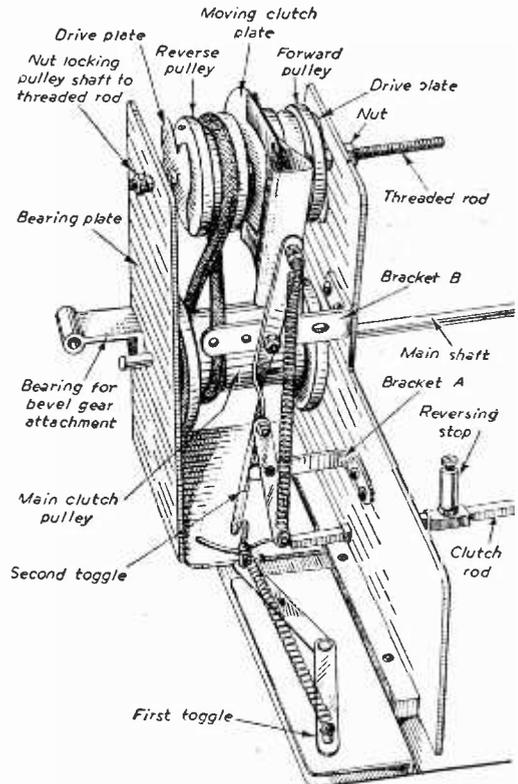


Fig. 7.—The complete clutch mechanism.

These bolts should be tapped into the base plate so that the wave-winding attachment may easily be fitted or removed. As mentioned before, a large pulley of $3\frac{1}{4}$ in. dia. is fitted to the bobbin shaft for wave-winding so that an even pattern is obtained. The belt from this pulley is joined to the $1\frac{13}{16}$ in. dia. pulley on the main shaft. When winding, the wire is passed through a small hole at the top of the strip and through the tube soldered to it.

The turns counter employed is a standard cyclometer driven by the bobbin shaft via a collar into which a pin $\frac{1}{2}$ in. long is soldered (Fig. 1). This pin engages the wheel on the cyclometer and, since it

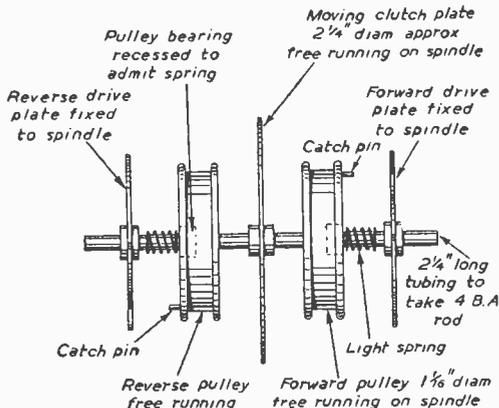


Fig. 8.—Detailed layout of part of the clutch mechanism. The parts have been spaced for clarity.

is not a direct drive, runs without vibration. The cyclometer needs a slight alteration before it can be used. Unscrew the end plate and this will reveal the tenths ring geared to the centre spindle. This gearing should be removed (leaving the tenths ring in position) and direct drive substituted. This was accomplished by the writer in the manner shown in Fig. 10. A small brass plate A, with a hole in the centre, is serrated at its outer edges so that it engages the inner aspect of the tenths ring. The cyclometer spindle fits through the hole in the plate and is soldered to it. All that remains is to make a bracket so that the counter lines up with the bobbin shaft.

Winding Back

If it is required to wind *back* from the bobbin on to the reel, a longer reel shaft should be kept handy with a pulley of any reasonable size attached. A *twisted* belt will give the desired result.

When using the machine for layer winding, the procedure is to mount the bobbin to be wound centrally on the bobbin spindle and grip the bobbin holders firmly while tightening up. Switch on and give the wire guide a trial run and adjust reversing stops so that the wire guide reverses its direction when it is in line with the ends of the bobbin. Fix the wire spool and feed the wire over the guide and secure the end to the bobbin. The purpose of the 3-bank pulley on the main shaft and the 2-bank pulley on the bobbin shaft is so that different ratios may be obtained between the traverse speed of the wire guide and the speed of the bobbin shaft. The wire guide travels at a constant speed, i.e., the speed of the main shaft, but, by means of the variable ratio

pulleys, the bobbin shaft may be run at various speeds in relation to it. Therefore, if fine wire is being used, a large number of turns would be required to fill the bobbin length. By using the large pulley on the main shaft and the small one on the bobbin shaft, the bobbin revolves at high speed. Alternatively, with thickish wire the bobbin can be made to run slower in relation to the wire guide so that a smaller number of turns can be accommodated in the same length of winding. In effect, therefore, we have a variable speed traverse of the wire guide. After a little experience one soon gets to know the best pulleys to use and in any case the wire is, to a large extent, self-accommodating because, due to the steady tension, each turn lays itself snugly against the previous one, and so on.

It is essential that the guide is brought as close to the bobbin as possible. That is the reason for the extension rod on the wire guide and it should under no circumstances be omitted.

One or two adjustments may be necessary to the clutch mechanism before it works smoothly. The toggles should work nicely if the specification is followed. The springs should be strong enough to produce a nice snap action but not so strong that undue pressure is required to work the toggles. The light springs fitted between the forward and reverse clutch pulleys and their associated drive plates should be strong enough to move the pulley away from the plate when the opposite pulley is engaged. The springs, when compressed, i.e., pulley engaged, should fit within the recessed portion of the pulley (see Fig. 7). Another point to watch in order that a smooth clutch action is ensured is to see that both toggles are lined up accurately when held in their dead-centre positions. The angle of the fork at the end of the first toggle may need some adjustment so that the arms pull over the second toggle when the first is just past dead centre.

The rubber bands on the clutch pulleys must be taut enough to prevent slip, but if too tight will prevent the pulley from being pushed against its drive plate by the moving clutch plate.

The link between the clutch actuating rod and the first toggle must have a free action where it joins the toggle.

In conclusion, it can be stated that practically any

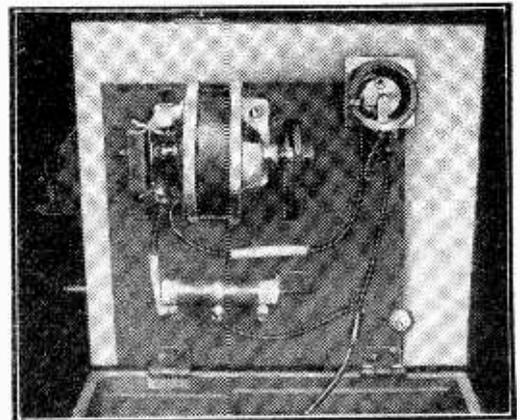


Fig. 9.—View of the underside of base plate showing felt surrounding the motor, and speed control.

-if you look for BIG RESULTS



You take no chances with OSMOR "Q" Range Coils—they're the results of patient scientific research plus the finest technical ability. Little wonder our customers are enthusiastic; they tell us these "mighty marvels in miniature" are super selective and sensitive to a degree they never thought possible. And we guarantee them! Note these "plus" points that pay handsome dividends every time!—


- ★ Only 1in. high.
- ★ Variable iron dust cores.
- ★ Low loss Polystyrene formers.

- ★ Packed in damp-proof containers.
- ★ Fitted tags for easy connection.

COILPACKS.—Now at new lower prices! A full range is available for Superhet and T.R.F. Mains or Battery. Size only 1½in. high x 3½in. wide x 2½in. Ideal for the reliable construction of new sets, also for conversion of the 21 RECEIVER, TR1196, TYPE 18, WARTIME UTILITY and others. Aligned and tested, with full circuits, etc. Fully descriptive leaflets available.



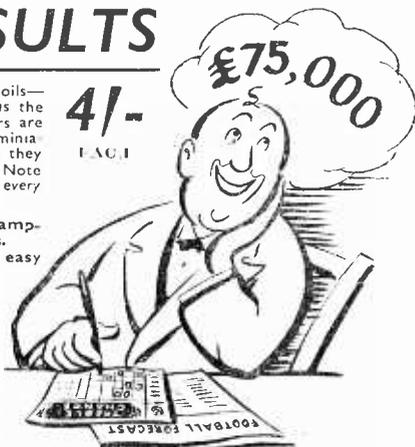"CORONET FOUR" The Osmor N.O. coil pack is specified (P.W. NOV. issue)



4/-
E.A.G.1

With OSMOR

Lines—you're on the right lines

A spotlight on just one of the range of Osmor "Q" coils.

H.F. CHOKE Type Q.C.1.

Frequency coverage 150 kc/s to 20 m/c. Iron dust core and single-screw fixing. Prototype tested and approved by M. G. Scroggie, B.Sc., M.I.E.E. Ideal as anode load in T.R.F. receivers for decoupling and general purposes.



Price 4/-

TWO for the Price of ONE! The NEW OSMOR CHASSIS CUTTER

of entirely new design. Cuts two sizes of holes with any one reversible punch and die; and can be operated with a spanner or tommy bar. Blanks easily removed. For use on Steel up to 18 s.w.g. Brass and Dural up to 16 s.w.g. Aluminium and Copper up to 14 s.w.g.



P. Pat. 1132153

Type	Hole Sizes	Price
1	1in. x 1½in.	19/6
2	2in. x 1½in.	18/9
3	3in. x 1½in.	22/6
4	1½in. x 2in.	27/3

Post and Packing 1/- (any type).

Tommy Bars.....1/3 each.

The OSMOR "JIFFY PUNCH"

For cutting smaller holes neatly and quickly with one blow of a light hammer.



P. Pat. 1132153

Type	Hole Size	Price
1	1in.	6/6
2	2in.	7/6
3	3in.	8/9

For use on Steel up to 20 s.w.g. Brass and Dural up to 18 s.w.g. Aluminium and Copper up to 16 s.w.g.

(Dept. P42) BRIDGE VIEW WORKS, BROUGH HILL, CROYDON, SURREY. Tel.: Croydon 5148/9

DIALS

Type A GLASS DIAL ASSEMBLY (as illus.), measuring 7 in. x 7in. (9½in. x 9½in. overall) mounts in any position on or above the chassis and works with any type of drive. Choice of two 3-colour scales—G1 (L.M.S.) or G2 (M.S.S.). Price complete, 24/6. Pulley assembly for right-angle drive if required, 1/9 extra. P. & P., 1/6.



METAL DIALS

Overall size 5½in. sq. Cream background, 3-colour Type M1, L.M.S. waves, M2, L. & M. waves, M3, M. & 2S waves. Price 3/6 each. Pointer, 1/6. Drum, Drive, Spring and Cord for use with both types of dials, 3/2.

We keep stocks of many radio components for use in published circuits, including:

"PRACTICAL WIRELESS"

Coronet "FOUR," Beginners' Superhet, Modern High Power Amplifier 2; Attaché Case Portable; R1155 Converter; A.C. Band-pass 3; Modern I-Valver; 3-Speed Autogram, etc., etc.

"WIRELESS WORLD"

No Compromise T.R.F. Tuner Midget Mains Receiver. Sensitive 2-Valve Receiver; Television Converter. (Special coils in cans available), etc., etc.

1.F.s. 465 kc. Permeability-tuned, with flying leads. Standard size 1½in. x 1½in. x 3½in. For use with OSMOR coilpacks and others, 14/6 pair. PREALIGNED, 1/6 extra.

Dear Reader,

We can't mention all our products here but shall be glad to receive your enquiries for Chassis, Tuning Condensers, Switches, Volume Controls, and all other Radio Components. If it's top quality components and a speedy, courteous service you are looking for—try Osmor. We really shall do our best for you.



OSMOR "JAR-RACK"

(If you're a generous husband you'll buy one or two for your wife's larder, she will appreciate the extra space they make!) Holds 1 lb. jam jars with or without lids. Easily removed, cannot fall out., just the thing for the tidy "HAM" or Radio Dealer.

Type 1 for wall-fixing, 6/9 each, holds 8 jars. (Jars are not supplied but are easily obtained.)

Length 24in., enamelled olive green.

Type 2 (as illustrated) for screwing under a shelf, 5/9 each, holds 6 jars.

Length 18in., enamelled green.

Post and packing, 1/- (either type).

(Trade supplied)

OSMOR "Station Separator"

Aerial plugs in here	Type	metres
	1	141-250
	2	218-283
	3	267-341
	4	319-405
Plug into Receiver	5	395-492
	6	455-567
	7	1450-1550
	8	410-550k/c

This is a device on the well-known "wave-trap" principle, which will reject an undesired signal when inserted in the aerial lead. Easily tuned to eliminate any one Station within the ranges stated. Fitting takes only a few seconds. Sharp tuning is effected by adjusting the brass screw provided.

7/6 Post Complete with full instructions—nothing to add.

Send 5d. 1stamps for FREE CIRCUITS and full list of coils, coilpacks and radio components.


FREE!

Osmor Radio Products Ltd.

BE PREPARED! Save TIME and MONEY with these PROFESSIONAL AIDS.

Speed the job with this BLACK & DECKER in. Electric Drill.


£2. 2s. with | & £1 monthly for order | 5 months
CASH PRICE, £6.5 0

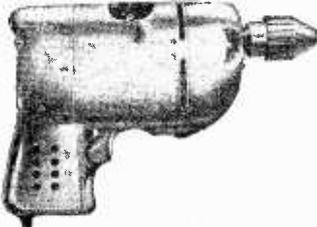

Present-day service demands a high-resistance meter. The PULLIN "100" is 10,000Ω per volt and has resistance ranges reading up to 1,000,000Ω on internal batteries. 4in. meter in handsome diecast case.

£3. 17s. with order and £1 monthly for 9 months.

CASH PRICE £11.11.0.

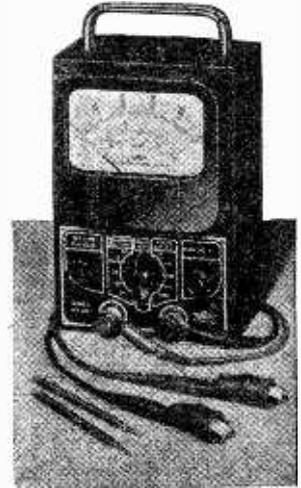

Full lists of other high grade equipment free on request.

EASY PAYMENT ORDER BLANK

To: **Frith Radiocraft, Ltd., Leicester**

DATE.....

Please supply.....
for which I enclose £ : : Deposit and agree to pay further monthly payments of £1 commencing on the first day of next month

No. of Pa'mts

P.W. Dec. 53. SIGNED (usual signature).....

NAME IN FULL (CAPITALS).....

ADDRESS

State if Householder If over 21 Occupation.....



PRATTS RADIO

1070 Harrow Road, London, N.W.10

Tel.: LADBroke 1734.

(Nr. Scrubs Lane)



AMPLIFIERS.—College General Purpose Units. **MODEL AC10E** (as illustrated) 40 watt, 4 valve unit. Neg. feedback. **SEPARATE** mike stage and **SEPARATE** mike and gram inputs, 2 faders and tone control. Input volts, mike .003 gram, 35 v., **£10.7.6.** **MODEL AC18E** 6 valve unit with P./P. output of 181 watts. **SEPARATE** mike stage and **SEPARATE** mike and gram inputs, 2 faders and tone control. Feedback over 3 stages. Input volts mike .003 gram, 3 v. **£15.5.0.** **MODEL AC32E**.—Spec. as AC18E, but with a larger output stage of 32 watts, **£18.18.0.** **MODEL U.10E**.—D.C./A.C. mains. P./P. output of 10 watts. Spec. as AC18E **£12.19.6.** All above amplifiers are COMPLETE with metal case, chrome handles, and outputs to match 3, 8 or 15 ohm speakers. All A.C. models have H.T. and L.T. output sockets for tuning units, etc. All amplifiers have sectionalised O/Trans, wound on super silicoz laminations. Power pack to operate the above from 12v bat. available.

QUALITY AMPLIFIER CHASSIS FOR RECORDS, ETC.—MODEL Q9C 6 valve unit with bass and treble controls. Inputs for radio, L.P. standard records. Output impd. to choice. This amplifier uses a Williamson 18 section output transformer. Output of 9 watts. Adjustable negative feedback. **£13.19.6.** **MODEL Q4C** 4 valve unit similar to Q9C. Output 4 watts. **£9.15.0.**

FULL RANGE OF PLAYERS, MOTORS, ETC. (LIST AVAILABLE). MICROPHONES, PICK-UPS, SPEAKERS AVAILABLE.

COLLEGE TRANSFORMERS, etc.—Filament, 6 v., 2 a., 8/9; 6 v., 3 a., 8/6; 12 v., 11 a., 8/6. Mats 2 x 350 v., 80 m.a., 0-4-5 v., 0-4-6 v.; 2 x 250 v., ditto, 2 x 275 ditto, all 17/6 each. 2 x 450 v., 250 m.a., 6 v., 6 v., 5 v., 49/6 (wt. 10 1/2 lbs.). **High Quality Output Transformers** Sectionalised CAL. 10,000 to 3, 8, 15 ohms. (P./P. 6V6, 6F6, etc.), 20 watt rating. Wt. 4 1/2 lbs., 18/6. CA2, 6,000 to 3, 8, 15 ohms, 30 watt rating (P./P. 6L6), wt., 5 1/2 lbs., 27/6. Williamson. Exact to spec. 1/6 or 3/6 ohms types, 75/6.


CHOKES.—60 m.a. 20 hv., 5/9; 60 m.a. 10 hv., 4/9; 100 m.a. 10 hv., 6/9; 150 m.a., 20 hv., 17/6; 250 m.a. 20 hv., 19/6. All goods are brand new, no surplus used. Amplifiers are carriage paid. Transformers, etc., postage up to 10/-, 6d.; £1, 1/-; above £2 free. Stamp for lists. State interest.

DIRECT FROM THE MANUFACTURER

DULCI RADIO/RADIOGRAM CHASSIS

Built to Highest Technical Standards
FULLY GUARANTEED

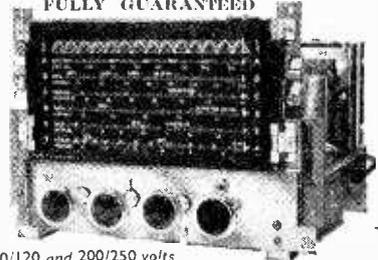All chassis 11 1/2 in. x 7 in. x 8 1/2 in. high. Latest type valves 6BE6, 6BA6, 6AT6, 6BW6, 6X4. Flywheel tuning. Negative feedback over entire audio section. Engraved knobs, 3 tone positions for radio and gram.



For A.C. Mains 100/120 and 200/250 volts

- Model B3.—1 Long, Medium, Short 5 Valves. Output 31 watt **£12/12/0**
- Model B3.—Plus Push Pull Stage 6 Valves. Output 6 watt **£15/15/0**
- Model B3.—Double Feature with P./Pull & R.F. Stage. 7 Valves. Output 6 watt **£18/18/0**
- Model B6.—(Six Wavebands, Med. Long, 4 Short. 3 Bandsread.) 5 valves. Output 31 w. **£15/15/0**
- Model B6.—Plus Push Pull Stage 6 Valves. Output 6 watt **£18/18/0**
- Model B6.—Double Feature with P./Pull & R.F. Stage. 7 Valves. Output 6 watt **£23/2/0**

ALL PRICES TAX PAID

Escutcheon for 9in. x 5in. dial, 4/9 extra. Matching speakers P.M. type 3 ohms, 8in. or 10in. available. Chassis sent under money back guarantee conditions against remittance. Free particulars from the manufacturers.

THE DULCI CO. LTD.,

99 VILLIERS RD., LONDON N.W.2. Telephone: Willesden 7773

coil, choke or transformer may be perfectly wound on this machine. As regards layer winding, mains transformers, of course, have to be interleaved so that the machine has to be stopped every two or three layers. There are many cases, however, L.F. chokes, output transformers, etc., where the winder may be left to do its work unaided.

Practical Details

For a medium- and long-wave coil it is best to start with the long-wave winding, so it is necessary to fix the honeycomb attachment to the machine—not forgetting the large bobbin shaft pulley—and disconnect the main clutch pulley.

The width of the honeycomb coil produced by the machine is about $\frac{1}{2}$ in., although the throw of the arm is much greater. So, having selected a suitable paxolin former, mount it on the bobbin spindle so that the winding arm, when perpendicular, is in line with the centre of the space allocated for the long wave coil. With regard to the guide tube through which the wire passes, it is essential that the inner aspect of each end is countersunk and perfectly smooth so that chafing of the wire is obviated.

From coil data tables wind on the required number of turns. It should be remembered that with a honeycomb pattern a turn is slightly longer than a straight pile wound turn, so that if a slightly larger frequency coverage is undesirable, the number of turns may be reduced.

The turns counter gives an exact indication. It reads to 9999 and a fifth figure shows tenths of a turn, so that there is plenty of scope for accuracy.

Having completed the long-wave winding, a coupling coil may be wound in the same manner if desired. Then remove the wave-winding attachment and its pulley. Tighten the screw in the main clutch pulley and this will put the traverse wire guide into action. The winder is switched on temporarily so that the wire guide may be brought to a position where it is in line with the start of the medium-wave winding. Then the wire is fed over the guide to the former and this winding may be completed.

L.F. Transformers

Intermediate-frequency transformers are easily made by adopting long-wave coil technique as outlined above.

At Fig. 12 will be seen a greatly enlarged section of a honeycomb coil showing the pattern produced.

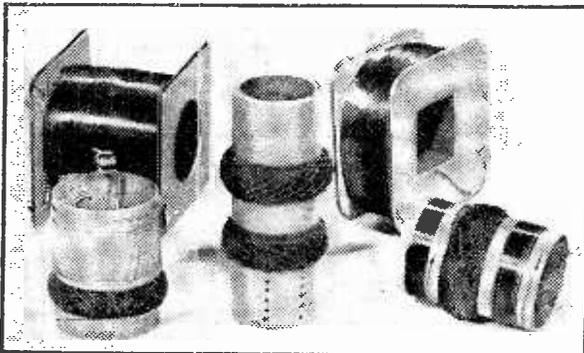


Fig. 11.—A group of typical coils wound on the machine.

Fig. 11 shows a group of various coils produced on the machine.

With the automatic reversing clutch in use for layer winding, a minimum winding length of about $\frac{1}{2}$ in. is available, which is handy for air-cored chokes as used in filter circuits, etc. High-frequency chokes may be wound in sections by moving the bobbin along the shaft after each section has been wound. If it is desired to pile wind into a narrow slot, this may be achieved by disregarding the wire guide. Before leaving the subject of honeycomb coils it may be mentioned that this type of coil may, with

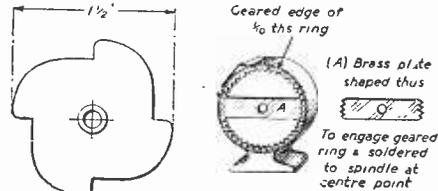


Fig. 10.—The modifications to the turns counter.

advantage, be coated with thin shellac varnish or dipped in wax and allowed to drain.

Transformers and Chokes

For such items as field coils, output transformers and L.F. chokes, the winder may be left unattended after completing the preliminary adjustments. These consist of setting the reversing stops for the length of winding required, using the approximately correct pulley ratio for the gauge of wire in use and roughly adjusting the wire tensioning device. Final adjustment of this latter feature is carried out during the early stages of winding. With regard to the pulley ratios, it will be found useful to keep a little reference data chart showing pulley ratios used for certain wire gauges.

When winding mains transformers it is unfortunate that full advantage may not be taken of the automatic feature because the machine has to be stopped to incorporate paper interleaving between windings. As is commonly known, commercial transformers are usually interleaved at every layer to ensure the utmost efficiency and service. After some years of transformer winding, however, it is the opinion of the writer that to interleave at two to three layers on the primary is sufficient. Using this procedure, only one failure has occurred, this on a transformer after eight years of service. The method seems to be justified as a time-saving factor when dealing with normal voltage transformers.

Concerning secondary windings, it is most advisable to interleave at every layer because the wire is usually fairly thick and this causes greater pressure of one layer upon the other, with the consequent risk of chafing insulation. Interleaving usually avoids this entirely. It should be mentioned that when using the winding machine any interleaving can, of course, be carried *in situ* and further winding proceeded with.

If correct interleaving paper is not available, tissue paper may be used successfully, but on no account should gummed paper be used.

It will, no doubt, be realised that there is a limit to the thickness of wire that can be wound on the machine. For example, it would be unreasonable to expect to wind 18 or 16 gauge, which is commonly used for 4-volt windings requiring a current of 3 to 5 amps. Fortunately, however, the number of turns is usually small and hand winding is not difficult. For this purpose the machine is still valuable, for after the primary has been completed and insulated (the same set-up being retained) the secondary may be proceeded with by turning the bobbin with the left hand and guiding the wire with the right. And one still has the advantages of a stable bobbin and a stable reel of wire, together

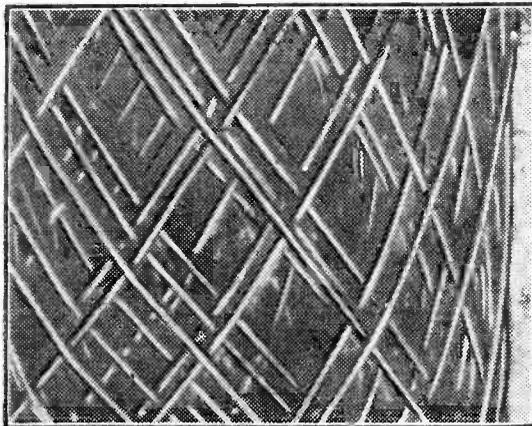


Fig. 12.—An enlarged view of the wave-winding produced on the machine.

with the fact that the turns counter is still functioning. Before starting to wind a transformer the bobbin cheeks should be drilled with a sufficient number of holes to avoid having to make them during winding—a distinctly awkward procedure. It is not difficult to visualise the approximate position of these holes, and in any case a few extra ones will be an advantage. Both ends of the bobbin should be used in an endeavour to even up the winding and to avoid lumpiness of the wound bobbin. During winding, a little judicious thought with regard to tappings will be useful. For instance, it is obviously better for a tapping to be taken from a turn lying near the end cheeks. This may often be easily arranged by spacing the turns so that the required turn comes in that position or by leaving the winding of that layer a little short. Incidentally, when dealing with thick wire carrying a heavy current, spacing of the turns is definitely an advantage.

Tapping Points

With regard to making the actual tappings, the following method may be adopted when using thick wire. Having reached the point where the wire is to be tapped, leave about 6 in. beyond this and then snip off. At the exact point where it will pass through the end cheek bend the wire to a right-angle and pass the free end through. Because the wire is thick it will not be temporarily self-retentive. Clean off the insulation at the angle and with a large pair of pliers press a flat into the wire. Clean off the free end of the wire on the reel and squeeze

flat. Then bend a small hook to engage the angle (see Fig. 13). The joint is soldered and will be very little thicker than the thickness of the wire. The joint should be insulated before proceeding. If it cannot be avoided to bring a tapping lead over previously wound turns, the wire must be extremely well insulated.

The design of a transformer is really quite simple providing certain laws are adhered to and having constructed it according to plan and with normal

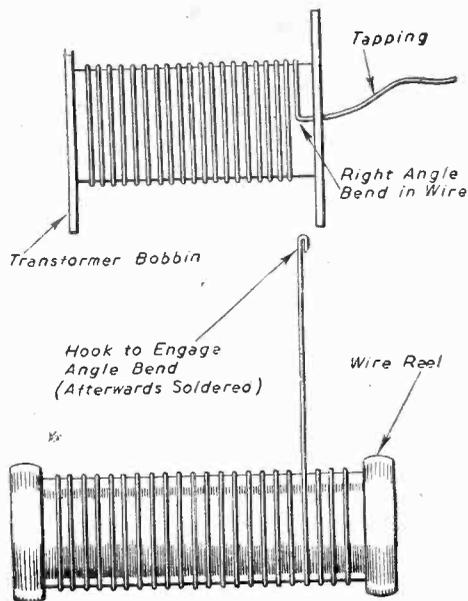


Fig. 13.—Method of making a tapping when using a heavy gauge of wire.

care one can be certain that it will perform correctly. Various data is necessary so that one can assess the core sizes, current carrying capacity of wire, etc., and in this respect one cannot do better than procure our publication "Coils, Chokes and Transformers." In this book will be found all the information required for designing any transformer, together with the necessary data sheets concerning wire and stallo stampings.

As useful as a Tool Kit—

8th (Fully Revised) Edition of the
PRACTICAL MOTORIST'S ENCYCLOPEDIA
By F. J. CAMM

With full section on Car Radio

400 pages, 493 Illustrations


17/6 or 18/- by post from :

GEORGE NEWNES, LTD., Tower House,
Southampton Street, Strand, W.C.2

RECEIVER 1132A

Contains EK32, 4 EF39, 6H6, 6J5, 3SP61, P61, in good condition. Fitted with tuning meter, slow-motion drive and dial. Complete, with Circuit Diagram, 50/- each, carriage, etc., 7/6.

RADIO CABINET

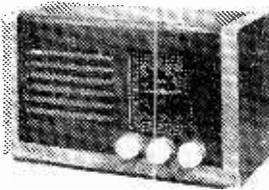


Complete with drilled chassis, dial drive and drum, backplate, spring, pointer. Size 11 1/2 in. x 7 in. x 5 in. Price 27/6 each.
 4 Position Rotary Switch, 30 amp ... 3/6
 Battery Charger Bulldog Clips ... 6d.
 465 Kc/5 I.F. Transformers, per pair ... 6/9
 Contact Valve Holders, Faxolin ... 3/d.
 Condenser Clips, all sizes ... 3d.
 2 Ratio Output Transformer ... 1/11
 1 mm. Sleeving, bright colours, yard Concordia, Bell Transformer, 3 v., 5 v., 8 v., 1 amp ... 7/6
 Reliance Choke 20H, 250 Ω 60 M/A ... 6/-
 H.F. Pile Wound Chokes ... 1/-
 Midget Choke 25H, 500 M/A 15 Ω , ... 2/-
 Ceramic Coil Formers, 1/2 in. dia., 1 in. long, 4 Ribs ... 5d.
 Dial Bulbs. Small BC Type. 6.5 v. 3 A. ... 6d.
 Vibrators 6 v. and 12 v. 4 pin UX Type ... 6/6

WIRE WOUND CONTROLS

Pre Set Types 500 Ω , 200 Ω , 1,000 Ω , each 1/9. Standard 5 Ω , 200 Ω , 1,000 Ω , 2,000 Ω , 5,000 Ω , 10K Ω , 20K Ω , 25K Ω , 50K Ω each 2/-.
 "SWAN" RADIO CABINET

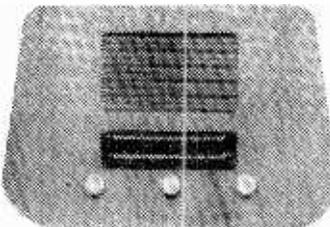Build a Radio in this up-to-date Cabinet. A modern looking Radio Cabinet complete with drilled chassis; dial drive and drum; back plate; dial; spring; pointer. Size 15 1/2 in. x 11 1/2 in. x 5 in. Price $\text{£}1/16/6$. Post and Packing 2/-.



We can supply a circuit diagram with all instructions for constructing a 3-valve plus metal rectifier T.R.F. receiver to operate on Long and Medium wavebands for 1/6. The complete kit can be supplied for $\text{£}6/6$.- Plus Packing and Post 2/6.

AUTO TRANSFORMER

0-10-120-200-230-250 v. 100 watts, 17/6 each.

VALVES

Guaranteed New and Boxed. Majority in Makers' Cartons


OZ4	7/-	7H7	8/6	U81	10/-
1A5GT	7/6	7R7	8/6	UB41	9/-
1C5GT	8/-	7S7	8/6	UBC41	11/6
1G6GT	6/9	7Y4	8/6	UF41	12/-
1L4	7/6	80	8/9	VR35	6/6
1LD5	6/9	807	8/9	EF39	7/6
1R5	8/-	8D2	2/9	EB34	3/6
1S4	8/-	954	2/-	EBC33	7/6
1S5	8/-	955	4/9	EF36	7/-
1T4	8/-	956	3/6	EK32	8/-
1U5	10/-	9D2	3/-	SP61	3/9
2155G	4/-	9001	6/3	SP41	3/9
2X2	5/3	9002	6/3	P61	3/6
3A4	9/-	9003	6/3	EF50	6/-
3D6	5/-	9004	6/3	EF50 Syl	8/-
3S4	9/6	10C1	11/-	EA50	2/6
3V4	3/-	10F9	11/-	VR102	7/6
4D1	3/-	10LD11	11/-	VR116	4/-
4Z	8/-	12A7	9/6	VR136	7/-
5U4G	8/6	12C8	9/-	VR137	5/9
5V4	9/-	12C9	9/-	VR150/30	10/-
5Y3GT	8/-	12H6	5/-	EL32	8/-
5Z3	8/6	12I5	6/-	VT105	4/6
5Z4G	8/6	12K7	9/-	PEN46	8/6
6A8G	10/6	12K8	9/-	VT501	6/-
6AC7	6/6	12SG7	5/6	YP23	8/6
6AK5	8/-	12SH7	5/6	VP133	8/6
6A6S	9/-	12SJ7	7/6	VU39	8/6
6AL5	8/-	12SK7	6/6	VU111	3/6
6AM6	8/-	12SR7	7/6	VU120A	3/6
6AT6	10/-	12SQ7	9/-	VU133	3/6
6B4	7/6	12Q7	9/-	W77	8/6
6B8	7/-	12Y4	7/6	W81	10/-
6BE6	11/-	12Z3	8/6	X18	9/-
6C4	8/-	150A	4/6	X65	13/-
6C5	7/6	15D2	4/-	Y63	9/-
6C6	7/3	20D1	10/6	12AX7	10/6
6D3	7/6	220 IPT	8/9	EF42	10/6
6D6	7/3	25A6G	9/-	EL81	10/6
6F6G	7/6	25L6GT	8/6	UL46	11/-
6F6M	8/6	25Z4G	9/-	X78	10/-
6F8G	7/-	35L6GT	9/6	EF42	10/-
6G6G	6/6	35Z3	9/6	EF40	10/-
6H6	4/6	35Z4GT	9/-	ECC40	9/6
6J5G	5/6	50L6GT	8/6	EL42	10/6
6J5GT	5/6	AC6Pen	5/6	6BW7	10/-
6J5M	6/-	CV71	1/-	EAC91	10/-
6J7G	6/6	DD13	4/6	EC91	9/-
6J7M	7/6	DDL4	4/-	IA3	8/-
6K7G	6/-	DET19	6/6	EY91	8/-
6K7GT	6/6	DH73M	9/-	12AH8	10/-
6K8G	9/-	DH81	10/-	EBF80	10/-
6K8GT	9/6	DL74M	9/6	6A88	10/-
6L6	9/6	EB41	10/-	6BA6	9/6
6L6G	9/6	EBC41	11/-	6BW6	10/-
6L7M	7/6	ECH42	10/6	EZ40	9/6
6N7	7/9	ECL80	11/6	7A7	8/6
6P26	10/-	EF36	7/-	7F7	8/6
6Q7G	9/6	EF41	10/-	IV	6/-
6Q7GT	9/6	EF80	11/6	1G4GT	6/-
6SA7GT	9/-	EM31	9/-	10P13	6/-
6S5T	8/9	EY51	12/-	ACSPENDD	8/-
6SH7	6/6	H63	7/9	6F1	10/-
6SJ7GT	9/6	HL23DD	8/-	HD24	8/-
6SK7	6/9	HL41	8/-	H30	8/-
6SL7	8/6	HL133DD	8/6	DD207	6/-
6SN7GT	10/-	KT33C	11/-	6C8	8/-
6SQ7	9/-	KTW61	8/9	HLDD1320	8/-
6SS7	8/-	KTZ41	6/9	L/63	8/-
6ST7	8/-	KTZ63	6/6	FC13	10/-
6U5	8/6	MH4	5/6	41MTL	7/6
6V6G	8/-	MS/PEN	5/-	77	7/-
6V6GT	8/-	Pen25	8/-	202DDT	7/6
6X4	8/-	Pen46	8/6	18	9/-
6X5GT	7/6	PEN220A/4	9	IA5	7/-
7B7	8/6	PL82	11/6	ID6	9/-
7C5	8/6	PY80	11/6		
7CS	8/6	U22	9/-		

COLLARO AC37

Gramophone motor, variable speed, manual adjustment. 4-pole shaded-pole type, 100/130 v., 200/250 v., complete with 10in. E.M.I. type turn-table. 46/- each, post 1/6.

MAINS TRANSFORMERS

3-WAY MOUNTING TYPE

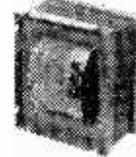

MT1
 Primary: 200-220-240 v.
 250 v. Secondaries: 250-0-250 v. 80 mA., 0-4 v. 5 amp., 6.3 v. 4 amp. 0-4-5 v. 2 amp., 17/6 ea.

MT2
 Primary: 200-220-240 v.
 350 v. Secondaries: 350-0-350 v. 80 mA., 0-4 v. 5 amp., 6.3 v. 4 amp., 17/6 each.

0-4-5 v. 2 amp. 17/6 each.


MT3

Primary: 200-220-240 v. Secondary: 30 v. 2 amps. Taps at 3 v., 4 v., 5 v., 6 v., 8 v., 9 v., 10 v., 12 v., 15 v., 18 v., 20 v., 24 v., 17/6 each.

EX-GOVERNMENT VOLUME CONTROLS

500 Ω , 600 Ω , 10K Ω , 20K Ω , 25K Ω , 50K Ω , 100K Ω , 1 meg Ω , 1/2 meg Ω , 1 meg Ω , 2 meg Ω . Each 1/-.

LOUDSPEAKER CABINETS

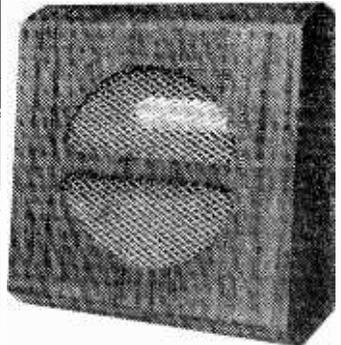

Available for 6'in. and 8'in. speaker units. Polished walnut finish. A very attractive cabinet at quarter of today's prices. Price: 6'in. Type Cabinet, 15/6 each. Price: 8'in. Type Cabinet, 19/6 each. See under loudspeakers for suitable speaker units.

LOUDSPEAKER UNITS

3in. Plessey Round Type for Portables	12/9
Elac 3in. square type. 2 to 3 Ω	13/6
5in. Units by Lectrona and Elac	12/3
Truvox 6in. Wafer Speaker, only 1 1/2 in. deep	20/-
6in. Elac with output transformer	16/6
8in. Units by Plessey and Elac	15/-
Lectrona 10in., 2 to 3 Ω	16/6
Rola/Celestion, 10in.	25/6
12in. Truvox BX11 Lightweight	57/6
Extension Loudspeaker in mottled bakelite case, suitable for bedrooms or kitchenettes	19/6
Plessey Mains Energised 8in. Unit, 1,500 Field	21/-

TERMS: Cash with order or C.O.D. Postage and Packing charges extra, as follows: Orders value 10/- add 9d.; 20/- add 1/-; 40/- add 1/6; above 40/- 2/-, unless otherwise stated. Minimum C.O.D. fee and postage 2/3. Illustrated Catalogue 6d. in stamps.

MAIL ORDER ONLY

ALPHA RADIO SUPPLY COMPANY 5/6 VINCE'S CHAMBERS, VICTORIA SQUARE, LEEDS 1

ANNOUNCING:

THE "ATOMIC" 3 VALVE ALL MAINS RECEIVER KIT

90/- Post Extra.

SEND 1/3 NOW FOR FULL INSTRUCTIONS: POINT-TO-POINT WIRING DIAGRAM AND CIRCUIT DIAGRAM, LIST OF PARTS AND GUARANTEE.

Complete 2 wave radio, in attractive bakelite cabinet. Hundreds already in daily use. Results guaranteed.

PARTS OBTAINABLE SEPARATELY.

The only tools required to construct this are, Soldering Iron, Screwdriver and Pliers.

VALUES by return:

OZ4	6/6	6B8	7-1U5	8/6	12Y1	7/6	EF91	10/6	
1A5gt	7/6	6BW6	8/6	6U5	8/6	15D2	4/-	EL32	7/6
1L5D	7/6	6BE6	8/6	6X4	8/6	25L2	8/6	EL91	8/6
1L4N	6/6	6BA6	8/6	6X5gt	7/6	35L6	10/-	HL2	3/6
1R5	8/6	6BR7	12/6	7C7	7/6	30L6gt	10/-	KT24	5/6
1S4	8/6	6C1	7/6	7D8	8/6	5L5	12/6	KT44	9/6
1S5	8/6	6C5g	6-7	7D9	7/6	7T	7/6	KT63	8/6
1T4	8/6	6CT1g	11/6	7Q7	7/6	7T	7/6	KT76	10/6
1G3	4/6	6G6	9-10	8D2	3-4	215SG	5-10	KTZ41	3-4
2C23	5-6	6F6	8/6	9D2	3-4	84GZ4	7/6	KTW61	7/6
2C34	4/6	6G6	7/6	8D3	8/6	807	12/6	N78	10/6
2V3g	3/6	6H6	3/6	8D6	7/6	956	3/6	P61	3/-
3D0	2/3	6J5	6/6	10F9	7/6	1626	4/-	PEN46	8/-
3S4	8/6	6K6	10-11	AR12	5-10	1632	7/6	PEN220A	8/-
4D1	3/-	6J7	9-12	12AT6	10/6	5763	10/6		5/-
5R4r	12/6	6K6	7/6	12A7	10/6	9002	5/6	QP21	7/6
5U9g	9/-	6K7gt	6/6	12AX7	10/6	9003	5/6	RK34	3/6
5Y3	10/-	6K7g	6/6	12AU7	10/6	A915	5/-	S130	5/-
5Z1	10/-	6K8m	10/6	12BA7	8/6	D1	2/6	SP41	3/6
6AB7	6/6	6L6	10/6	12BE6	8/6	D477	8/6	SP61	9/6
6AC7	10/-	6L6g	10/6	12C8	9-11	E148	3-4	TT11	5/-
6AC5	7/-	6Q7	10/6	12J5	5-10	EA50	3-4	VR116	3/6
6AK5	8/6	6SA7	9/6	12K7	12/6	3 for 5	V39A	10/6	3/6
6AK6	8/6	6SH7	8/6	12SK7	8/-	EB91	9/6	VU111	3/6
6AM6	8/6	6SL7	11/6	12SC7	5-10	EC32	10/6	VU120A	3/6
6AV3	8/6	6SN7	10/6	12SH7	5-10	EF36	6/6	VU133	3/6
6AU6	8/6	6SQ7	7/6	12S47	6-8	EF39	8/6	VU133	3/6
6AL5	8/6	6SS7	7/6	12SK7	8/-	EF50	5/6	U21	6/6
6B7	9/-	6V9g	9/-	12SQ7	9/6	EF54	5/6	W77	8/6

Please include small amount for postage.

The Ham's Shop with the helping hand—Tom Gamble (G3DBL)

NORMAN H. FIELD (Dept. B9), 68, Hurst Street, B'ham. 5.

CLYDESDALE PRICES SLASHED

RECEIVER CHASSIS Range 150-200 Mc/s.

Contains: 1 Transformer prim. 85M henries, sec. 155M henries. 5 coils in cans, 3 957 Acorn valves, 4 acorn valve bases, 9 1.0 valve bases, 125 μ F. miniature tuning condenser with knob and coupling, 4 co-ax. sockets. On metal chassis size 8 x 13 x 5 in. Weight 8 1/2 lb.

Ask for P.H940.

21/- EACH

POST PAID.

SUPPLY UNIT RECTIFIER for No. 43 Transmitter.

Ex. Cdn. Army in original wood case. Input 110V, a.c. 50/60 c/s 1.7K V.A. Output (HT1), 2.100V, 375mA.; (HT2) 500V, 400 mA. plus H.T. lines, 450V, 275V., also 383V., regulated and neg. bias 250V., 150V., 80V. Making three complete power supplies all fed via double choke condenser. Input circuits. Valves are 4 888A, 888, 5Z3, 6S4, 2 6A3, VR150 30 (Stab.) and 1V. (Time delay). The Complete unit mounted in metal case with lid shock mounted. Dim.: 2ft. 6in. x 1ft. 6in. x 1ft. Finish olive drab. Weight 420 lb.

Ask for P.H28.

£25 EACH

CARR. PAID.

EGG INSULATOR Type HG. 10H/153.

Standard, medium, large insulator finished in brown. 3in. long, 2 1/2in. max. dia.

Ask for P.E192.

1/9 EACH

POST PAID.

Box of 4 for 5/6. Gross lots for £7 4s.

SELSYNT MOTOR TYPE 5J/2512. Ref. No. W.325A.

230V, a.c. input single phase, torque transmission value 45lb in., with 1/2in. long 1/2in. shaft. Overall 12 1/2 x 7in. diam. With fixing base.

Ask for P.H83.

39/6 EACH

CARR. PAID.

POWER UNIT Type 266 in Transit Case.

Input 80V, 1.5K cps. a.c. Outputs H.T. 120V, d.c., bias 3 and 9V L.T., 2V. Smoothed and stabilised. Complete with 504G valve, VS110 stabiliser, 12V. 1A Metal Rectifier, etc., etc., in attractive metal case with handles. Dim.: 11 x 9 1/2 x 7 1/2 in.

Ask for P.E870.


22/6 EACH

CARR. PAID.

Order direct from

CLYDESDALE SUPPLY CO. LTD.

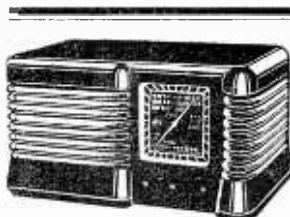2, Bridge St., Glasgow, C.5. Phone: SOUTH 2706/9
Visit our Branches in Scotland, England and N. Ireland.



CABINET as illustrated. 11 1/2 x 6 1/2 x 5 1/2, in walnut or cream, complete with T.R.F. chassis, 2 waveband scale, station names, new waveband, back-plate, drum, pointer, spring drive spindle, 3 knobs and back, 22/6. P. & P. 3/6.

AS ABOVE but complete with 5in. speaker and O.P. trans. (these speakers have been used but tested O.K.). 30-. P. & P. 3/6.

Metal rectifier 7/6. Gang with trimmers, 7/6. Medium and long T.R.F. coils 5/6. 3-ob-plate ex-Govt. valves, 3 wholders and circuit of an A.C. mains 3-valve plus rec. T.R.F. which can be built for approx. £4. 8/6. Heater trans. 6/-. Volume control with switch 3/6. Wave-change switch 2/-, 32 + 32 mid. 4/-, Bias condenser 1/-, Resistor kit 2/-. Condenser kit 4/-. Cabinet as illustrated above complete but with 5 valve Superhet chassis, 23/6. P. & P. 3/6.

As above but complete with new speaker and O.P. trans. to fit, 36/-, P. & P. 3/6. Medium and long-wave superhet coils with circuit, 6/6. Iron core 465 Kc. IF's, 7/6 pair. Miniature gang, 5/6. Volume control with switch, 4/-. Wave-change switch, 2/6. Heater trans. Pri. 230/250 v. 3 amp., 7/6, 5 valveholders, 2/-, 5 Obsolete Ex-Govt. valves with circuit, 14/6, 25 mfd. 25 wkt. condenser, 11d. 8 + 16 mfd. smoothing condenser, 3/6. Condenser kit (17), 7/6. Resistor kit (14), 3/6.

Standard Wave-change Switches, 6-pole 3-way, 2/-; 4-pole 3-way, 1/9; 5-pole 3-way, 1/9. Miniature 3-pole 4-way, 4-pole 3-way, 2/6.


Used C.R.T. Tubes, Heater cathode short 9in., 45/-. 12in., 75/-. Ion burn 9in., 35/-. 12in., 55/-. P. & P. on each 7/6. Valveholders, Paxolin octal, 4d. Moulded octal, 7d. EF50 ceramic, 7d. Moulded BTG slightly soiled, 6d. Octal amphenol, 7d. Octal pax., 4d. Mazda Amph., 7d. Mazda pax., 4d. BBA, BBA amphenol, 7d. BTG with screening can, 1/6. Trimmers, 5-40 pf., 5d.; 10-110, 10-250, 10-450 pf., 10d. Twin-gang .0005 Tuning Condensers, 5/-. With trimmers, 7/6. Midget .00037 dust cover and trimmers, 8/6.

P.M. SPEAKERS

	with trans.	less trans.
2 1/2in.	15/6
3in.	13/6
5in.	16/6
6in.	16/6
8in.	18/6
10in.	19/6

Post and packing on each of the above, 1/- extra. Crystal pick-up with Sapphire Trailer Verette, 21/- each; with volume control, 23/-; post and packing on each, 1/-.

Constructor's Parcel, comprising chassis 8in. x 4in. x 1 1/2in., with speaker and valveholder cut-outs, 5in. P.M. speaker with transformer, twin gang with trimmers, pair T.R.F. coils long and medium, iron core, four valveholders, 20 K. volume control and wave-change switch, 23/-, post and packing, 1/6. Output Transformers, Standard type, 5,000 ohms imp., 2-ohms speech coil, 4/9; Miniature type 421, 3/3. Multiratio 3,500, 7,000 and 14,000 2 ohms speech coil, price 5/6. 10-watt push-pull 6V6 matching 2 ohms speech coil, 7/-. Mains Transformers, primary 200-250 v. 280-0-280, 250 mA., 6 v. 6 amp., 5 v. 3 amp., drop-through, 29/6. P. & P. 3/-. Mains Trans. Pri., 200-250 v. Sec., 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24 and 30 volt at 2 amps., 13/-. P. & P. 1/6. 300-0-300 100 mA., 6 v. 3 amp., 5 v. 2 amp., 25/-. Germanium crystal diode, 2/3 post paid. Heater Transformer, Pri. 230-250 v. 6 v. 14 amp., 6/-; 2 v. 24 amp., 5/-, P. & P. each 1/-, 2, 4, or 6 volt 2 amp., 7/6. Garrard 3-Speed Record Changer, A.C. Mains 200/250 v. Two Crystal Heads, Brand New, P. & P. 3/6. £9/19/6.

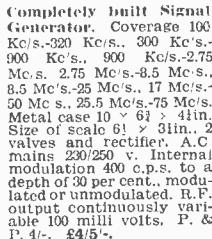

Completely built Signal Generator. Coverage 100 Kc/s-320 Kc/s., 300 Kc/s.-900 Kc/s., 900 Kc/s.-2.75 Mc/s., 2.75 Mc/s.-8.5 Mc/s., 8.5 Mc/s.-25 Mc/s., 17 Mc/s.-50 Mc/s., 25 Mc/s.-75 Mc/s. Metal case 10 x 6 1/2 x 4 1/2 in. Size of scale 8 1/2 x 3 1/2 in., 2 valves and rectifier, C.C. modulation 400 c.p.s. to a depth of 30 per cent., modulated or unmodulated. R.F. output continuously variable 100 milli volts. P. & P. 4/-. £4/5/-.

Terms of business:—Cash with order. Dispatch of goods within three days from receipt of order. Where post and packing charge is not stated, please add 6d. up to 10/-, 1/- up to 41 and 1/6 up to £2. All enquiries and Lists, stamped, addressed envelope.

D. COHEN

RADIO AND TELEVISION COMPONENTS

23, HIGH STREET, ACTON, W.3.
(Opposite Granada Cinema)

Hours of Business: Saturdays 9-6 p.m. Wednesdays 9-1 p.m.
Other days 9-4.30 p.m.

Interference-free Radio

LOCATING AND CURING RADIO'S GREATEST BUG-BEAR

By F. E. Apps

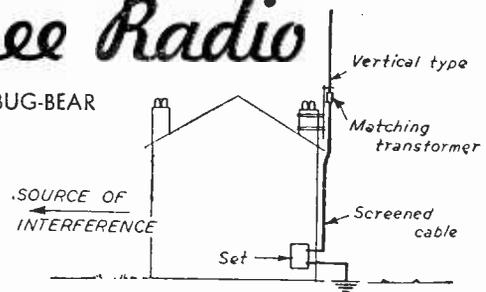
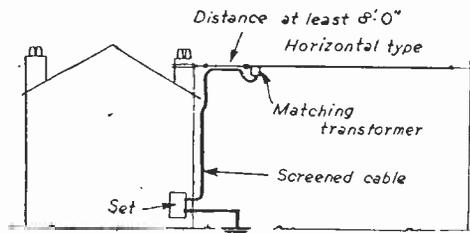


Fig. 1.—Aerial arrays for minimising interference.

THE goal of completely "interference-free" radio and television reception has yet to be reached. In fact, in the past few years it has become considerably worse, especially in large towns and built-up areas. One has to be drawn to the conclusion that it can never be attained until or unless the powers that be pass a law compelling all persons manufacturing, selling or operating any electrical apparatus liable to cause interference to radio or television reception, to fit the same with efficient suppressors. Unfortunately this law has yet to be passed, so until then we must carry on the struggle against pretty hopeless odds with the weapons we have at hand. This article hopes to show how to get the best from your set with the minimum of interference.

Radio

The fitting of an interference suppression circuit in radio receivers in this country is very uncommon, although in the United States most manufacturers fitted them, but from my own experience of them they were not very efficient and did not warrant the extra valve or valves that the circuit demanded. It is proposed not to deal with these circuits at all, but to try to procure better reception with the radio receiver as it stands.

Interference can reach the radio receiver either by radiation or it can be mains borne. If it is radiated interference it can reach the receiver either by the aerial, frame aerial, or plate aerial, or even by unscreened coils on the top of chassis. The aerial itself may even pick up interference from nearby metallic objects. This is often the case with indoor aerials where the aerial runs parallel with internal electric light wiring. In large towns, especially where factories abound, an outdoor aerial with screened down-lead is essential for good clear reception. The aerial itself, whether of the horizontal or the vertical type, must be well clear of the house, about 8ft. away is the minimum distance. The screened lead is connected to the aerial and to the receiver by means of matching transformers at either end. This type of aerial, the anti-interference type, is manufactured in this country by several firms and they are very efficient, indeed, and will even in the very worst possible conditions give one quite reasonably quiet reception (see Fig. 1). A point to remember is that many manufacturers now fit a plate aerial

on the inside of cabinet which is permanently connected. Disconnect this if fitting an outdoor interference aerial. It is as well to check that the interference is not coming from your own house before blaming outside sources. Faulty wiring, switches or any of your own electrical appliances may be causing trouble for you or your neighbours, so check up your own house first.

Locating the Source

The position where the aerial is to be erected is also of great importance. It should be placed as far away as possible from the suspected source of interference. It may be neon signs, trolleybus wires, electric railway, factory or a garage where charging plant is installed. If a portable set with a frame aerial is available the direction, or its reciprocal, of the interference can be found. Tune the set into its best position for interference, then revolve set until the interference reaches a maximum, when the interference will be in the plane of the frame. Thus, should the frame be pointing due north and south, the interference is coming from either of these two directions (see Fig. 2).

It may be necessary in some very bad interference areas to try various alternative positions and so arrive at a point where interference is at a minimum.

It is essential that the screened cable is soundly earthed. Use a rising main water pipe, or an earth rod or plate well buried in the ground. The aerial length for a horizontal type should be at least 20 to 30ft. in length. For the vertical type a rod of from 10 to 15ft. is all that is required.

Mains-borne Interference

The foregoing has only dealt with interference that is picked up by the aerial or aerial circuit, but there is another way in which a set can pick up quite a considerable amount of noise. This is mains-borne interference, and happily it is not quite so common as the aerial borne type. A method of checking whether the interference is either aerial or mains borne is as follows. Disconnect the aerial from the set, including the plate type, if used. With the set now tuned to a point where no signals are received, if interference is still being heard then it is probably being mains borne. The usual method of reducing this interference is by means of a suppressing circuit in the mains lead (Fig. 3). The condensers used must be of at least 500 V.D.C. working type. The chokes should be wound with about No. 26 D.S.C. on a 1in. former and consist of from 80 to 100 turns. The whole must be

well insulated from ground and fitted into a metal box which should be soundly earthed. Be careful to fit fuses and ensure that the whole is 100 per cent. safe before connecting up. Keep only the radio set in circuit with this suppressor. Don't connect, by means of adaptors, other electrical apparatus to it, as the chokes will not carry a lot of current and if overloaded will heat up and burn out. There are several types of these suppressors on the market and

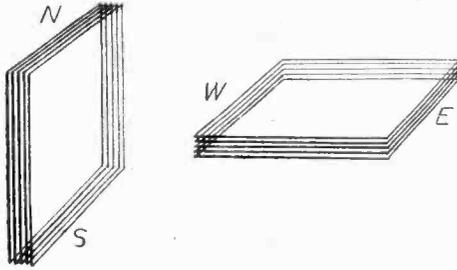


Fig. 2.—How a frame aerial may be used to locate the direction from which interference is coming.

they are made in various sizes for various current ratings.

There is nothing more we can now do to eliminate this troublesome interference. As I first mentioned in this article, the only real solution is for the Government to pass a law prohibiting, under penalty of a heavy fine, the manufacture, sale or use of any electrical apparatus which radiates or causes interference. When this is done, if ever, then the Post Office interference investigation department will be of some real use. At the present moment, all that it can do is to locate the interference for you and then ask the owners if they will please suppress it. If the owners say no then there is no more they can do. I would advocate that under the new law, if passed, the offending apparatus should be immediately put out of operation, and the owners be compelled to suppress it, or that the Post Office do the suppressing and present the owner with the bill for same.

Radio Servicing Certificate Examination

THE Radio Trades Examination Board and the City and Guilds of London Institute have announced that for the 1953 Radio Servicing Certificate Examination 309 candidates attended, of which 126 qualified for the award of the certificate. This figure includes 30 candidates who passed the practical test having been referred last year. 87 candidates were successful in the written papers, but were referred in the practical test.

The 1954 examination will be held on May 4th and 6th for the written papers, and May 15th for the practical test. The closing date for entries is February 1st, 1954, and regulations and forms of application may be obtained from the Secretary, Radio Trades Examination Board, 9, Bedford Square, W.C.1.

Change in Regulations

The following new regulations for entry to the Radio Servicing Certificate Examination have now been approved :

Television

Unlike radio, all television sets have a vision and sound interference suppression circuit. This acts as a complete cut-off for high level interference and is only of real use when the incoming signal is of good strength. It is more efficient on vision than it is on sound. In fact, on sound, if the interference level is high, the interference suppression circuit, if it does its job, will only cause bad quality reception, if not bad distortion. Normally, it is quite efficient for moderate interference level but in cases of heavy interference other methods are necessary.

In television, practically all interference is radiated and it is mostly from motor-car ignition systems, so

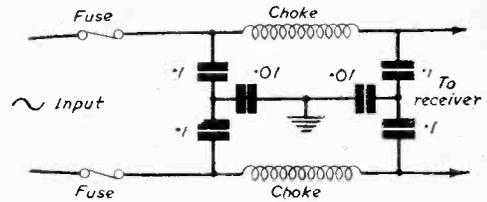


Fig. 3.—Typical mains interference suppressor circuit.

it is a case of positioning and orientation of aerial again. If on a main road where the traffic is heavy, the aerial should be placed as far back as is possible. Remember that a car will radiate interference up to about 100ft., and as the interference level drops rapidly as the distance away increases (almost inverse square law), only a few feet may mean quite an appreciable improvement. Where signal strength is high an indoor aerial may in some cases improve reception, but again the old method of trial and error must be used in positioning the same. I had an instance of this the other day. A friend of mine living on a busy main road was getting a lot of visual interference. He had tried an outdoor single dipole, and then a dipole and reflector type, but the interference was still bad. I tried an indoor aerial and after a few positionings of same found a place where the picture input was still good, but the interference level had diminished quite an appreciable amount.

In order to be eligible for the examination candidates must prove that :

- (a) They have had gainful full time occupation in commercial radio engineering or commercial radio service for a minimum period of 3 full years and be not less than 19 years of age on the February 1st preceding the examination they wish to sit, but will not be eligible for the award of the certificate until attaining the age of 21 years or
- (b) They have completed a course of technical instruction approved by the Board and have had one year's full time gainful occupation in radio service work provided they are not less than 19 years of age on the February 1st preceding the examination, but will not be eligible for the award of the certificate until attaining the age of 21 years.
- (c) That they have undergone an approved course of training in Her Majesty's Forces and have also had a minimum of six months commercial radio servicing or radio engineering experience.

This represents a reduction of the two years of full time gainful experience in the case of classes (A) and (B).

Volume Controls

Midget Eilewain type. Long spindles. Guaranteed 1 year. L.E.S.S. Sw. S.P. Sw. 3/- D.P. Sw. 4/- 4/9

ALL VALUES.—10,000 ohms to 2 Megohms.

BALANCED TWIN FEEDER per yd. 6d. 1/2
TWIN SCREENED FEEDER per yd. 1/- 80
50 OHM COAX CABLE, Ed. per yd. 1/4 in. dia.

TRIMMERS, Ceramic, 50, 70 pf., 8d.; 100 pf., 1/0; 250 pf., 1/6; 500 pf., 1/8.

RESISTORS.—All values: 1 w., 4d.; 1 w., 6d.; 1 w., 8d.; 2 w., 1/-; 1 w., 1/2; 2 w., 1/2; 1 w., 1/2; 2 w., 1/2.

WIRE-WOUND RESISTORS.—Best Makes. Miniature Ceramic Type—5 w., 15 ohm to 4 K., 1/9; 10 w., 20 ohm to 6 K., 2/3; 15 w., 30 ohm to 10 K., 2/9; 5 w., Vitreous, 12 K. to 2 K., 2/4.

WIRE-WOUND POTS. 3 WATT, FAMOUS MAKES. Pre-set Min. Tv. Type. Standard Size Pots, 2 1/2 in. Knurled, Slotted Knob. Spindle. High Grade All values 25 ohms to 30. All Values, 100 ohms to K. (50 K. and 100 K. Carbon Franch), 3 each. 50 K., 5/6; 100 K., 8/6.

O.P. TRANSFORMERS.—Tapped small pentode, 3/9. Heavy duty 70 ma., 4/6. Ditto, tapped, 4/9. L.F. CHOKES 10 h., 65 ma., 4/6. 20/25 ma., 10/150 ma., 12/6. 5 h., 250 ma., 15/-. 15 h., 100 ma., 10/6.

LYNX, choke, 3 h., 250 ma., 13/6. MAINS TRANS.—Made in own workshops to high grade specification. Fully interleaved and impregnated. Heater Trans., tapped prim., 0/200 v./250 v., 6.3 v. 1/1 amp., 7/6. 350/0-350, 80 ma., 6/3 v. 4 a., 5 v. 2 a., ditto 200/0-250, 30/-. Viewmaster, 400 v. type, 3/5. Teleking, 30/-. 150 v., 30/-. Coolest, 30/-. Super Visor, 30/-. SOUNDMAKER SPECIALS.—Mains Trans., 35/- L.F. Choke, 10/6. O.P. Trans., 5/6. Envelope, 6/6. QUALITY P.P.O.P. TRANS., 20 w., special Stalloy 3 a. bus. Sectionalised, low leakage windings, primary inductance 400 H., leakage inductance 0.075 H. Secondary impedance 2 and 15 ohms. Primary impedance to individual requirements, fully shrouded and terminated. 3 gns. Ditto, as above 15 v. output 2/1 gns. Part Post and Packing (all Chokes & Trans.), 1/- extra please.

WOODEN WALNUT CABINET.—12 in. x 7 in. x 5 in. complete with punched chassis, TRF or Superint. dial, back-plate, drum, drive, spring, potentiometer, etc. 25/6. Also post mounted, 30/-. TYANA.—Midget Soldering Iron, 200 220 v. or 230-250 v., 16/9. TYANA TRIPLE THREE.—Complete with detachable bench stand, 10/6. IDEAL FOR RADIO CONSTRUCTORS.

EX GOVERNMENT UNITS.—Our selection, 3 different. All containing useful parts, TO CLBAH, carr. paid, 15/-. Satisfaction guaranteed.

TAG STRIPS.—2 or 3-way, 2d.; 4 or 5-way, 3d.; 6-way, 4d.; 8 or 10-way, 6d.

GROUP TABBOARDS.—(2 1/2 in. wide.) 5-way, 8d.; 6-way, 1/-; 10-way, 1/6; 25-way, 2/6; 50-way, 4/6.

TERMINAL BLOCKS.—Moulded bakelite, 2-way, 8d.; 4 w., 1/6; 6 w., 2/3, etc., up to 12 w., 4/6.

MARY ANN Vacuum Cleaner Flexible Hoses, plated ends, 1 1/2 in. diam. fitting, 16/6. 12ft. appliance lead, switched-on and off combination adapter, 6/9.

TV AERIALS.—Full range popular types in stock. Aerialite, etc. All chambers. Indoor loft type Inv. T. 13/6. Outdoor single dipole, 3/6. H type with chimney hangers, etc. 9/6. X type Duplex, 7/11. Mast chimney hangers, etc., 8/9. Filing models available. Ask for quotations. 1/6.


80 ohm COAX CABLE STANDARD in. diam. Polythene insulated. REDUCED PRICE

9d. A YARD 7/10 P.P.O. (Gout. COAX PLUGS, 1.2 each SOCKETS, 1.2 each. LINE CONNECTOR, 1.2. OUTLET BOXES, 4.6.

ALL WAVE RADIOGRAM CHASSIS 3 WAVEBANDS LATEST MILLAR VALVES: S.W. 16 m.—50m. ECH 42, EF41. M.W. 200m.—500m. EBC 41, EL 41, EZ40 L.W. 500m.—2400m.

Brand New and Guaranteed with 10in. P.M. Speaker. A.C. 200,250 v. Four position Wave-change Switch, Short-Medium-Long-Trans. Slow Motion Tuning. Speaker and Pick-up connections. High Q iron-dust core coils, 465 kc/s P.F. Latest circuit technique delayed A.V.C. and Negative feedback. Output 4.2 watts, 5 ohms output transformer on chassis. (Chassis size 4 1/2 x 2 1/2 in. Glass Dial—10in. x 4 1/2 in. horizontal or vertical type available, lit by 2 Pilot Lamps. Colour Black. Station names, L.W. Green, M.W. Red, S.W. White. Four Knobs supplied. Walnut or Ivory to choice, aligned and calibrated.

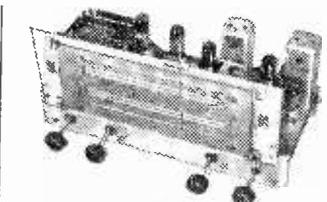PRICE, £10 15 0. Carriage and Insurance, 4/6. (Without 10in. Speaker, £9 15 0. Carr. & Ins., 4/6.)



ALL WAVE RADIOGRAM CHASSIS 3 WAVEBANDS LATEST MILLAR VALVES:

S.W. 16 m.—50m. ECH 42, EF41. M.W. 200m.—500m. EBC 41, EL 41, EZ40 L.W. 500m.—2400m. Brand New and Guaranteed with 10in. P.M. Speaker. A.C. 200,250 v. Four position Wave-change Switch, Short-Medium-Long-Trans. Slow Motion Tuning. Speaker and Pick-up connections. High Q iron-dust core coils, 465 kc/s P.F. Latest circuit technique delayed A.V.C. and Negative feedback. Output 4.2 watts, 5 ohms output transformer on chassis. (Chassis size 4 1/2 x 2 1/2 in. Glass Dial—10in. x 4 1/2 in. horizontal or vertical type available, lit by 2 Pilot Lamps. Colour Black. Station names, L.W. Green, M.W. Red, S.W. White. Four Knobs supplied. Walnut or Ivory to choice, aligned and calibrated. PRICE, £10 15 0. Carriage and Insurance, 4/6. (Without 10in. Speaker, £9 15 0. Carr. & Ins., 4/6.)

BARGAIN OFFERS RECOMMENDED FOR ABOVE CHASSIS GREAT REDUCTIONS

Brand New Collaro Autochanger, 3-speed Model, SRCS21. Twin High Fidelity Heads. For 7in. 10in. or 12in. Records. Spring Mounting. Superb Quality. List £16 10 0. Our Price 9/1 gns. post free. Ediswan 78 r.p.m. Single-player Gram Unit, High Impedance Magnet Pick-up. Press lever start for 10in. or 12in. records, auto stop. Listed 7 gns. Our Price £4 10.

NEW BOXED VALVES GUARANTEED ALL

Table listing various vacuum tube valves with their specifications and prices. Columns include valve type (e.g., 1A5, 1B5, 1C4), price, and other details.

Huge Stock B.V.A. Valves at 1951 low tax prices.

THIS MONTH'S SPECIAL OFFER

6K8, 6V6, 1R3, 1T4, EB91, 6AM6. Any Two 10/- SPECIAL PRICE PER SET. 6B4, 6AV6, 6BE6, 6AT7, 6X4, 40/-. 1R3, 1T4, 1R3 and 3R4, 30/-. 6K8, 6K7, 6Q7, 6V6, 3Z4 or 6X5, 40/-. VIEWMASTER, 12 valves, 66/10. With EY31, £7. TELEKING.—17 valves, 59/10. LYNX.—17 valves, 49. CORONET.—4 valves, 45/-. WAVE-DIAL ASSEMBLY, Type #14, 26/6. LINE COND.—2x, 100 ohms per foot, 2x, 60 ohms per foot, 2-way 1/6 a yard, 3-way 1/8 a yard. SLEEVING.—Various rollers, 1. 2 mm. 2d.; 3. 4 mm., 3d. vd.; 6 mm., 5d. yd. MAINS DROPPERS.—(Cin. x 1 1/2 in.) Adj. slides 3 amp. 750 ohms, 2 amp. 1,400 ohms, ea. 4/3. WAVE-CHANGE SWITCHES.—2 p. 2-way, 3 p. 2-way, 2/6; 2 p. 3-way, 4 p. 2-way, 3/6 etc.

CRYSTAL DIODE.—Very sensitive. G.E.C. 3/6. B.T.H. 2/6. H.R. PHONES (S.G. Brown), 15/6 p. P. and P., 3d. £1 orders post free. Lists 3d.

T.R.S. RADIO COMPONENT SPECIALISTS 307, WHITEHORSE ROAD, WEST CROYDON. Mail Order: 71, MEADLEY ROAD, EAST CROYDON

CONDENSERS.—New stock best makes. 0.01 mfd. 6Kv. T.C.C. 5/6. Ditto 12.5 kv., 9.6; .002 mfd. head 8 kv., 2.6; 2 pf., 400 pf., 8d.; .001, .005, .01, T.C.C. 500 v., 61 S. range 500 v., 62 N.S.P. 500 v. Tub., 1 into 350 v. Micanone con. 700 v., 9d.; .05 N.S.P. or Dubilier, 1 into 500 v. Hunts, 1/-; .25 mfd. 500 v. Hunter, 1/6; 5 mfd. 500 v. Hunts, 1/9.

SILVER MICA CONDENSERS.—10%. 100 pf. to 500 pf., 1/-; 500 pf. to 5,000 pf., 1/3. DITTO 1% (2-day service). 1.5 pf. to 500 pf., 1/9. 515 pf. to 1,000 pf., 2/-. ELECTROLYTICS ALL TYPES NEW STOCK.

Table listing electrolytic capacitors with their specifications and prices. Columns include voltage (e.g., 4,500 v. Hunt), type (e.g., Can Types Clips, 8d. ea.), and price.

SPECIALS.—Can Types. 500 mfd. 12 v. 3/-; 1,000 mfd. 12 v. 5/-; 2,000 mfd. 12 v. 4/6; 16 mfd. 700 v. Hunts, 6/6.

SENTERCEL RECTIFIERS. E.H.T. TYPE.—K1 25 2Kv., 4/3; K3/40 3/2 Kv., 1/6; K3/45 3/6 Kv., 1/6; K3/50 4Kv., 7/3; K3/100 5Kv., 12/6; K3/100 14 Kv., 18/-. MAINS TYPE.—RM1, 125 v., 60 ma., 4/-; RM2, 100 ma., 4/9; RM3, 120 ma., 5/6; RM4, 250 v., 5/6 ma., 16/-. KNOBS, GOLD ENGRAVED.—Walnut or Ivory, 1 1/2 in. diam., 1/6 each. "Focus", "Contrast", "Brilliance", "Brilliance—On-Off", "On-Off", "Synchronise", "Val. On-Off", "Tone", "Tuning", "Trebble", "Bass", "Wavechange", "Radio-Gain", "S. M. L. Gain", "Record-Play", "Brightnes", Ditto not engraved, 1/- each.

COILS.—Wearite "P" type, 2/6 each. Midget "Q" type, adj. dust core, 3/6 each. All ranges. REACTION COND.—0001, 0003, 0005 mfd., 3/6 ea. SURPLUS MAINS TRANS.—Prim. D-200 250 v.; Sec. 275-0-275 v., 60 ma., 6/3 v. 3 a., 6/3 v. 1 a., 10/6; 200/0-200 v., 80 m/a., 6/3 v. 3 a., 6/3 v. 1 a., 12/6. Oscilloscope Transf. Prim. 0-50 v., 4/-; 500 v. 15 ma., 5 v. 2 a., 5 v. 2 a., 4 v. 1 a., 17/6. VIBRATOR TRANS.—6 v. Injnt, 230 v. 50 m/a. output, 0/6. P. & P., 1/1.

BATTERY CHARGER.—200 250 v. Output 6 v. and 12 v. 11 amps. In steel case complete with fuse and leads, ready for use. OUR OWN MAKE. FULLY GUARANTEED. 35/-, P. & P., 1/1. CHARGER TRANSFORMER.—0-200,250 prim. sec. 0-9 v.-15 v. 1/1 amp., 13/6.

ACID HYDROMETER.—Brand new ex-Govt. 100 scale. Packed in metal case, 7in. x 1 1/2 in. dia., 4/6.

FULL WAVE BRIDGE SELENIUM RECTIFIERS.—6 or 12 v. 1 amp., 8/9; 2 a., 11/3; 3 a., 12/6; 4 a., 15/6.

C.R.T. HEATER ISOLATION TRANSFORMER.—Low leakage winding with 25% sec. boost, 2 v., 10/6; 4 v., 10/6; 6.3 v., 10/6; 12 v., 10/6.

H.F. MIDGET CHOKES.—10 H. M.L., 2/6 each. BIRMISTORS.—721 for 3 a. heater chains, 3/6. C22 for 15 a. or 2 a., 2/6.

ENAMEL WIRE.—1 1/2 lb. to 20, e.w.g., 2/-; 22 to 28 s.w.g., 2/-; 30 to 40 s.w.g., 3/6. SWITCH CAPACITOR Fluid, spirit spint. 3/9. 5in. RADIO SCREWDRIVERS.—Sheffield made blade, 2 1/2 in. x 1in. handle, 5,000 l., 4/1d.

TWIN GANG STANDARD SIZE.—With feet, 4000 p.f., 8/6; 1110 midget, 7/6. 375 p.f. midget twin gang, 6/6. BARGAIN—0005 mfd. twin gang, slightly soiled, 5/6.

RESISTOR TAG PANELS.—Clearance Panel from Brand New Units. A fair mixture of 1 1/2, 1 and 2 w. and w/resistors (average number 45-50). Sold by weight—once price while they last, 3/- per lb., P. & P., 9d. Satisfaction guaranteed or money refunded.

50 MICRO-AMP. MOVING COIL METER.—4 1/2 in. x 3 1/2 in. Flush Mounting, 3in. scale. By Marconi Inst. Ltd. A superb meter. BRAND NEW. Only 50/- ea. P. & P., 1/- extra.

LOUDSPEAKERS P.M. 3 OHM. 5in. Plessey, 12/6. 5in. Plessey, 13/6. 6in. Truvox, 14/6. P. & P., 9d. LECTRAON, 15/6. 10in. Lectraon, 25/-; 5in. G.E.C. Energised 70002 field with trans. 19/6.

BARGAIN VALUE I.F. TRANSFORMERS

465 Kc/s Slug tuning. Miniature. Circular. Can 2 1/2 in. by 1 1/2 in. diam. Fits oval V-holder cut out. High Q. and good bandwidth. By Pye Radio.

BRAND NEW 6/9 PAIR

5/- — 807 — 5/-

REDUCTION IN PRICES

EF 50
(VR 91)

4/-

6 FOR £1

7/6

6V6, EF30,	5U4G, EL32,	FW4/500, 6N7,	EBC33, 6X5,
SP61 2/6	SP41 2/6	EA50 2/-	DI 2/-
EB34 2/-	EC52 4/6	9001 4/6	Pen220 2/-
EF36 4/-	EC54 4/6	ECC31 5/6	L289A 5/-
EF8 6/6	RK34 2/-	VT104 4/-	3D6 3/-
EF54 5/-	HL2K 2/-	VT105 4/-	6AC7 7/6
6J5 4/6	6K7 6/-	SZ3 7/9	EK32 6/-
2D21 8/6	VT62 6/-	VR21 2/-	VR22 2/6
VR18 2/-	HL41 4/6	ILN5 4/6	ILD5 4/6
U22 2/6	U 7/-	EF91 9/-	6AG5 7/-
954 6/6	955 5/-	956 5/-	ECC32 5/-
IR5 8/-	IT4 8/-	IS5 8/-	3S4 8/-
6L6 12/-	6K8 11/6	6L6M 12/6	6Q7 8/3

AMPLIFIER, Type 1139A. Chassis. Valve line up. 1 EK32, 1 EBC33, 1 EL32. Less valves. 5/- carr. paid.
RECEIVER Type 1225. Chassis. 8 valve. 5 EF50, 1 EB34, 1 EF30, 1 EBC33. Less valves. 5/6, carr. paid.
RECEIVER Type 71. Chassis. Contains 4 EF50, 1 EL32, 1 EF30, 2 EF36 valves. Less valves. 5/6, carr. paid.

VINER'S (Middlesbrough)

Radio Electrical

26, EAST STREET, MIDDLESBROUGH

(Telephone: Middlesbrough 3418.)

"TYANA TRIPLE THREE"
SOLDERING IRON WITH DETACHABLE
BENCH STAND 19/6

The smallest high power soldering iron. Length only 8 1/2". Adjustable long bit dia. 3/8". Mains voltages, 100/110, 200/220, 230/250.

STANDARD TYANA SOLDERING IRON. Price retails at 16/9. Replacements, Elements and Bits always available. Voltage as above.

MAKE SOLDERING A PLEASURE!

BY USING THE "TYANA" SOLDERING IRON

British made by:—**KENROY LIMITED,**
152/297, Upper Street, Islington, London, N.1.
Telephone: Canonbury 4905-4663

SPARKS' DATA SHEETS

Constructional Sheets of Guaranteed and Tested Radio Designs.

NOTE NEW PRICES. POST FREE.

ALL DRY BATTERY DESIGNS. "MIDDY" 2-valve M/L wave, 2/9. "BOSUN" 3-valve M/L wave, 2/9. "SKIPPIT" 4-valve T.R.F. M/L wave, 2/9. "CHUMMY" 2-valve Portable M/L wave, 2/9. "CORVETTE" 4-valve All-wave Superhet, 2/9.

MAINS OPERATED. "CUB" AC/DC 2-valve + Rect. M/L wave, 2/9. "ENSIGN" ditto for A.C., 2/9. "ENTERPRISE" A.C. 3-valve + rect. T.R.F., 2/9. "QUINT EST" AC/DC 4-valve + rect. All-wave Superhet, 3/3. 3 watt A.C. Amplifier, 3/3. 10 watt ditto P/P Output, 3/9. 10 watt AC/DC P/P output, 3/9. "CRITERION" A.C. Radiogram M/L waves, 9 valves, 8-10 watts (3 sheets), 7/9.

COMPONENTS AND DRILLED CHASSIS SUPPLIED.

Send 21d. stamp for Latest List.

L. ORMOND SPARKS (P), 48A, HIGH STREET, SWANAGE, DORSET.

REP HIGH GAIN COILS

Dual Range Miniature Crystal Set Coil, 2/6, with Circuit. Dual Range Coil with Reaction, 4/-, with 2 Mains and 2 Battery Circuits. Matched Pair Dual Range T.R.F. Coils, 8/- pair. With Battery and Mains Circuits. — All coils wound on low loss formers. — Individually tested and guaranteed. — Post 3d. on all orders. — Trade supplied.

RADIO EXPERIMENTAL PRODUCTS, Ltd.
33, MUCH PARK ST., COVENTRY

TELEVISION

The advance of Radio Technique will offer unlimited opportunities of high pay and secure posts for those Radio Engineers who have had the foresight to become technically qualified. How you can do this quickly and easily in your spare time is fully explained in our unique handbook.

Full details are given of A.M. Brit. Lit. Ex. City & Guilds Exams., and particulars of up-to-date courses in Wireless Engineering, Radio Servicing, Short Waves, Television, Mathematics, etc., etc. We guarantee "NO PASS—NO FEE." Prepare for to-morrow's opportunities and future competition by sending for this very informative 144-page guide NOW—FREE and without obligation.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY
(Dept. 242).

17, Stratford Place, London, W.1.

5 in 3

Free leaflet tells how range extender gives 5 octaves from 3 octave electronic keyboard. Imitates whole orchestra. Is simply built from simple instructions. Get your free copy now. . . .

C & S, 10 Duke St., Darlington, Co. Durham



Magna Cartridge



Completely Tropicalised. Tested under extreme conditions of Heat and Humidity (125° F. with 95% humidity) without deterioration and loss of output.

- Output comparable to Crystal Pick-ups.
- Cantilever Styl Protecting Records and eliminating Needle-talk and surface noise.
- Styl easily replaceable.
- Will fit three-speed record changers and units.

No. 200. Price £1.10.0. P. Tax 9/9.
Now available as a complete Pick-up.
No. P.200. Price £2.5.0. P. Tax 14/9.

For full technical details write to:

ERWIN SCHARF

49-51a, De Beauvoir Road, London, N.1
Telephone: CLIsold 3434.

G.E.C. & B.T.H.
GERMANIUM

CRYSTAL DIODES

G.E.C. GLASS TYPE 5/16in. x 3/16in.
B.T.H. LATEST TYPE MOULDED IN THERMO-SETTING PLASTIC

Both Wire Ends for Easy Fixing.
4/6 each, postage 21d.

B.T.H. SILICON CRYSTAL VALVE

3/6 each, postage 21d.
Fixing Brackets 3d. Extra.

Wiring instructions for a cheap, simple but high quality Crystal Set included with each Diode and Crystal Valve.

COPPER INSTRUMENT WIRE
ENAMELLED, TINNED, LITZ,
COTTON AND SILK COVERED.

Most gauges available.

B.A. SCREWS, NUTS, WASHERS soldering tags, eyelets and rivets. EBONITE and BAKELITE PANELS. TUFNOL ROD, PAXOLIN TYPE COIL FORMERS and TUBES, ALL DIAMETERS.

Latest Radio Publications.
SEND STAMP FOR LISTS.

CRYSTAL SET
INCORPORATING THE SILICON
CRYSTAL VALVE

Adjustable Iron Cored Coil.
RECEPTION GUARANTEED
Polished wood cabinet, 15/-, post 1/-
A REAL CRYSTAL SET, NOT A TOY

POST RADIO SUPPLIES
33 Bourne Gardens, London, E.4



The Beginner's Guide to RADIO

The Eighth of a Series of Articles Specially
Written for Those Who Have Become
Interested in Radio for the First Time.
Explaining the Principles of Radio
Transmission and Reception

By F. J. CAMM

LAST month we dealt with simple tests, and there are one or two others which can be carried out. Suppose, for example, signals are not heard after the simple coil test explained last month, then the reaction circuit has broken down.

The reaction circuit consists of only a reaction condenser and coil, so that one can soon find any fault arising here, and the absence of reaction, when the maximum H.T. is applied to the valve, will show that the reaction circuit is faulty. Now pass on to the first L.F. stage. If, when one attaches the 'phones to the anode terminal of the detector valve, the signals are heard, proceed as follows: Remove the lead joining the anode terminal to the second valve, and join the 'phones to this as before described, taking one side of the 'phones direct to the H.T. battery in order to eliminate any decoupling resistances or other parts included in the anode circuit of the valve. If signals are still quite in order pass on to the following valve, and so on. If, however, nothing can be heard, the first thing to do is to test the valve. If it is correct, then the only components used to couple the detector valve to this one are the L.F. transformer or R.C.C. components. Substituting other parts is the easiest way of finding out what is wrong. If one cannot obtain substitutes, the primary and secondary windings of the L.F. transformer may be tested for breaks in the following way. Disconnect all leads from the transformers and then join one primary terminal to the positive socket of a grid bias or pocket-lamp battery. To the other primary terminal join one side of the 'phones. Now join the other lead of the 'phones to one side of a high resistance—such as a grid leak—and the other side of the resistance should be carefully touched on the 1½-volt socket. If a scratching sound can be heard in the 'phones then the primary is unbroken. If, however, nothing can be heard, try the 3-volt socket and gradually work upwards. Do not omit the resistance, and do not

apply too high a voltage. If nothing can be heard at 12 volts or so, then the primary is broken. Test the secondary similarly.

With a simple voltmeter and/or milliammeter, the receiver may be tested at each stage by including the meter or meters as shown last month. The figure showed how the voltage at the anode of a valve may be obtained by connecting a voltmeter across the valve. This will, sometimes, give a false reading in certain cases owing to the shunting effect of the resistance of the meter. However, if the voltmeter is connected across the anode load resistance the voltage drop which occurs will enable the anode current to be calculated by the simple application of Ohm's Law.

As also, if it is connected across the biasing resistor. Alternatively, if the anode circuit be opened and a milliammeter be joined in series (either at the H.T. or cathode end) the current indicated will enable the resistance values to be checked (knowing the voltage applied).

A microammeter in series with the grid of an L.F. valve will check whether or not the valve is running into grid current. If a resistance is to be checked it may be connected in series with a battery and milliammeter and its value calculated in the absence of an ohmmeter.

About Inductance

We have now obtained some practical elementary experience in building and testing a simple receiver, and we have also learned about the units of current resistance and pressure (amperes, ohms and volts). Although I have only briefly touched upon it I have also referred to the *capacity* of a condenser and the *inductance* of a coil. Condensers, as is well known are of two types—fixed and variable. The latter are always used in connection with an inductance for tuning purposes. We know that the unit of capacity is the farad; the unit of inductance is the henry, with sub-units of the *millihenry* (one-thousandth of a henry) and *microhenry* (one-millionth of a henry). When a pressure of 1 volt is induced through a coil and changes at the rate of 1 ampere per second it is said to have an inductance of 1 henry.

Now before we can understand what inductance means it is necessary to deal with what happens when current is passed through a wire. Until quite recently

SYMBOL

C =

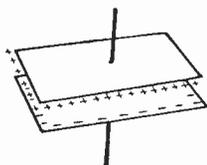


Fig. 32.—A capacitor, and a variable component which acts in exactly the same manner.

SYMBOL

L =



Fig. 33.—A simple inductance.

it was believed by scientists that an electric current was a kind of fluid which travelled through a circuit from the positive pole of a battery to the negative, whereas it actually passes in the reverse direction. It is general knowledge now that all matter, whether solid, liquid or gaseous is composed of atoms.

The atomic theory is that there are certain substances called elements which consist in their purer state entirely of atoms of one kind only. Copper is such an element and it consists of copper atoms and nothing else. Carbon is also an element and so is gold, silver and platinum. Substances which are not elements are called compounds and they are made up of groups of atoms of various kinds. Thus, water consists of hydrogen and oxygen, two atoms of hydrogen combining with one of oxygen, to form a *molecule* of water. It is for this reason that the chemical symbol of water is H_2O .

Although that is the basis of the atomic theory, recent investigations have shown that it is not strictly correct. Hitherto, it was thought that the atom was indivisible. We now know that it is and this discovery has revolutionised science for it has proved that all elements and compounds, whether solid, liquid or gaseous, *have the same components differently arranged.*

The atom is a body of unimaginable smallness and it has been calculated that if a drop of water were to be magnified to the size of the earth, the atoms composing it would appear to be about the size of a cricket ball. In reality, of course, it is more like a miniature solar system consisting of a "sun" with an attendant retinue of planets. The sun or central body is called the *nucleus* and the planets are known as *electrons*. An electron is a minute charge of negative electricity. It *is* electricity. The electrons rotate round the nucleus at a speed of about 1,000 miles per second and but for this high speed the nucleus which is positively charged, would attract the negative electrons and they would be pulled in towards it. Similarly, the earth would fall on the sun were it not for the high speed at which it rotates with the sun as its centre of rotation.

Matter in its normal state has all its atoms in a tranquil or inert condition. Each atom has its right amount of electrons rotating round it and there are no external electrical effects. If, by some means one of these atoms loses an electron its stability is upset. A little bit of negative electricity has been taken away and too much positive electricity remains. In other words equilibrium has been destroyed. The whole thus assumes an excessive positive charge and it at once endeavours to attract into its own system any

free electrons which happens to be in the neighbourhood. In this condition it is known as a positive *ion*. Conversely, if an atom is given an extra electron, then it has a superfluity of negative electricity and becomes a negative ion. All this leads up to my next point which is that a conductor, such as a copper wire, may be regarded as a substance containing electrons which are loosely bound to their respective nuclei and which, under the influence of some force, such as the electro-motive force of a battery or mains voltage, are easily made to move from one atom to another in a systematic manner.

In non-conductors, or insulators, the electrons are bound tightly to their nuclei and under the influence of the same force are very hard to move systematically, although they can be slightly displaced. Among good conductors of electricity are metallic substances, the atoms of which will readily part with an electron. A perfect insulator does not, of course, exist.

The force required to bring about a systematic movement of electrons is, of course, the *electro-motive force*. Now what happens when a current flows along a copper wire? The E.M.F. in this case is supplied by either the battery or the mains and is analogous to a pump circulating water through a pipe, the water eventually returning to the pump. In the battery the place of the pump is taken by the chemical action of the *electrolyte*, the substance in the cells which removes electrons from the positive plate and transfers them to the negative, whence they travel via the outside circuit back to the positive terminal.

At the negative terminal of a battery there is a superfluity of electrons. Let us trace one of them through a copper wire joined to each terminal of a battery. The electron rushes off the terminal and hits a copper atom, knocking an electron out of its orbit and taking its place. This displaced electron rushes against the next atom, driving out an electron as before and occupying its place. Thus a wave of collisions passes down the wire, until the detachable electron nearest the positive terminal is driven out of its place.

In addition to the effects caused within the wire by the passage of electrons, there is also another effect *outside* the conductor. When a current of electricity flows along a wire, the surrounding ether is in a state of strain. This is a magnetic strain, that is, the wire is surrounded by magnetic lines of force in the form of circles which are nearly concentric.

When the current is first switched on through the conductor, these lines of force spread out from the middle of the conductor, becoming larger and larger until they reach a maximum. Similarly, when the current is switched off the field of force gradually begins to diminish. This field of force may be regarded as a kind of invisible sleeve formed round the wire. The field of force is not in the least hampered by insulation.

Inductance

We have already seen that a current experiences difficulty in starting to flow and also in stopping. This means that a conductor, especially one in the form of a helix, solenoid or coil, resists any change in current which passes through it. Inductance is the electrical equivalent to inertia in mechanics. It is difficult to start a motor-car by pushing it, but once the motor-car is in motion it is equally difficult to stop it. The inductance of a length of wire depends on its form—how it is arranged or wound.

(To be continued)

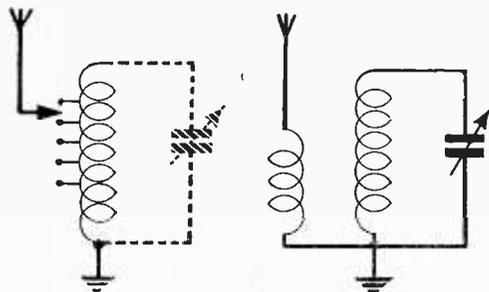


Fig. 34.—A simple aerial tuning circuit. Greater selectivity is obtained when a coupling coil is included and a tuning condenser is employed.



OPEN TILL 6 PM SATURDAYS

TELEPHONES: AMBASSADOR 4033 & PADDINGTON 3271/2

PREMIER RADIO Company

(REGD.) B. H. MORRIS & CO (RADIO) LTD. EST. 40YRS.
 THIS IS OUR ONLY ADDRESS (Dept. P.W.) 207 • EDGWARE ROAD • LONDON • W2 (THIS IS OUR ONLY ADDRESS)

BUILD A PROFESSIONAL LOOKING RADIO SET AT LESS THAN HALF TO-DAY'S PRICE

We can supply all the parts to help you.
 Dium (2 1/2 in. diam.) 1/6
 Driving head 1/6


- Double pointer 4d.
- Spring 3d.
- Nylon Cord (yard) 6d.
- 2/4 Front Plate 2/6



Engraved Glass Dial 180-550 and 800-2 200 m. With station names, new wavebands ... 1/6
 T.R.P. Coils, 180-550, 500-2 200 metres, pair 6/6
 Punched chassis 3-valve plus rectifier T.R.P. Cabinet, Bakelite, in Walnut or Ivory or Wooden in Walnut finish ... 37/6
 Packing and Insurance ... 2/6
SEND 1/8 FOR EASY TO FOLLOW POINT-TO-POINT DIAGRAMS AND CIRCUIT DIAGRAM which shows how YOU can build the Receiver illustrated above.

THE COMPLETE KIT

To construct a 3-valve plus rectifier T.R.P. Receiver for use on 230-250 v. A.C. mains can be supplied at **£5/19/6**, plus 2/6 packing and carriage. Each kit is complete in every detail, nothing has to be made or improvised. Easy to follow point-to-point diagrams are supplied making construction very simple. The Dial is illuminated and the Receiver housed in its Cabinet size (12 1/2 x 5 1/2 x 5 1/2 in.) presents an attractive appearance. The valve line-up is: 717A—H.F. Pentode. VR16—Detector. A17A—Output and Metal Rectifier.

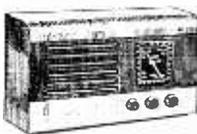

Waveband coverage is for the medium and long bands. Choice of 3 Cabinets: Bakelite in Walnut or Ivory, or Wooden in Walnut finish

WILLIAMSON AMPLIFIER KIT

A complete kit of parts for the construction of the latest version of this famous amplifier complete with valves output and mains transformers.

15 Gns.

Plus 7/6 pkg., carr. and ins.

WILLIAMSONS AMPLIFIER TRANSFORMERS (To specification)

The Output Transformer 2.6 ohms sec. £4 4-
 The Mains Transformer, PREMIER SP325A. £3 7/6.

'SPECIAL OFFER' CRYSTAL HAND MICROPHONE

High Impedance. Excellent frequency response, light weight gives very high quality results when used with tube recorders, amplifiers for any type of P.V. equipment. Complete with screen lead and plug. 37/6. Plus 2/6 pkg. & carr.



H.T. ELIMINATOR AND TRICKLE CHARGER KIT

All parts to construct an eliminator to give an output of 120 volts at 20 mA., and 2 volts to charge an accumulator. Uses metal rectifier. 37/6.

Govt. Surplus Ex. W.D. STEEL AERIALS
 Also ideal for fishing rods—ALL BRASS & W.E.W. 12ft. 3 1/2 in. sections of copper-plated steel highly flexible tapering 3/16 to 1/8 in. Brand new in container. Plug-in type. 6/9. Screw-in type. 7/9. Packing and carriage. 1/6. Insulated base. 2/6. Weighing waterproof carry-in case with shoulder sling. 2/6.

ACCUMULATORS

- Lead Acid Celluloid Non-Spill. 2 v. v. 7 amp. 3/6
- 2 volt 10 amp. (by famous maker) 4/11

Famous Set Manufacturer's surplus of—ELECTRIC GRAM UNITS

Two-speed, 33 1/3 and 78 r.p.m. For playing Standard and L.P. records. Complete with Turntable. For use on 200-250 v. A.C. mains. Each unit is in its original manufacturer's carton and is fully guaranteed. Limited quantity only available at approx. half list price.



£4.2.6
 Plus 2/6 pkg., carr., ins.

SPECIAL OFFER THE FAMOUS "CHANCERY" HIGH FIDELITY MICROCELL PICK-UP TYPE GPX for Standard and Long Playing



The Chancery Light Weight GPX Pick-up embodies certain unique features achieving a standard of performance not possible with normal magnetic or crystal pick-ups. The secret of the high standard of performance is in the use of the special microcell crystal cartridge assembly which has an unusually wide frequency response. The sapphire stylus is precision ground and semi-permanent. With two cartridges, 1 L.P. and 1 Standard. Price 52/6. Additional L.P. or Standard Cartridge can be supplied from stock at 12/6 each.
 Quality Crystal Pick-up Rothermel Type U48. Price 28/-. Plus 1/6 Pkg. and Carr.

GRAMOPHONE CABINETS—Portable

A fortunate purchase of a manufacturer's surplus stock enables us to offer this first grade cabinet made by a famous manufacturer at the ridiculously low price of **25/-**. Plus 2/6 pkg. and carr.

SPECIFICATION—

Substantial Wooden Case, Revolving Covered, metal Eng. wooden motor board already up to take a Gramophone Unit. Hand and clip supplied free. Almost any make of Rim Drive Unit can be accommodated with ease. Outside dimensions: Height (when closed), 5 1/2 in.; Length, 14 1/2 in.; Depth, 14 1/2 in.; Clearance space under motor board 2 1/2 in.; Clearance space from motor board to inside lid when closed, 2 1/2 in.

As a special offer for a limited period only the above Gramophone Unit, Pick-up and Cabinet assembled into a complete Portable Electric Gramophone ready to plug-in to your Radio or Amplifier can be supplied at **£7.19.6**. Plus 5/- Pkg., Carr., & Ins.

GRAMOPHONE UNITS

GARRARD Type 75. Latest 3-speed Autochange Unit complete with 2 Accos High Fidelity G.P.P.19 Pick-up Heads, 1 L.P. and 1 Standard. Plus 5/- pkg. & carr. **£14.19.6**

GARRARD Rim Drive 78 r.p.m., complete with magnetic pick-up and turntable ... **£5.19.6**

COLLARO 3-speed s.l.g. gram unit complete with head for L.P. and Standard recordings ... **£8.8.0**
 Packing and carriage on each of the above units, 2/6.

PREMIER MAINS TRANSFORMERS

All primaries are tapped for 200-230-250 v. mono-40-100 cycles. All primaries are screened. All L.T. are centre tapped.

- SP175B, 175-0-175 50 mA. 4 v. @ 1 a. 4 v. 25-
- @ 2-3 a. 4 v. @ 3-5 a. 28-
- SP301B, 300-0-300, 120 mA. 4 v. @ 2-3 a. 4 v. 29-
- SP350A, 250-0-250 100 mA. 5 v. @ 2-3 a. 4 v. 36-
- SP351, 250-0-250, 150 mA. 4 v. @ 1-2 a. 4 v. @ 2-3 a. 4 v. @ 3-4 a. 4 v. 36-
- SP352, 250-0-250 150 mA. 5 v. 2-3 a. 6.3 v. 2-3 a. 6.3 v. 2-3 a. 36-
- SP375A, 375-0-375, 250 mA. 6.3 v. @ 2-3 a. 6.3 v. @ 3-5 a. 3 v. @ 2-3 a. 4 v. @ 2-3 a. 4 v. 47-
- SP501, 500-0-500, 150 mA. 4 v. @ 2-3 a. 4 v. @ 2-3 a. 4 v. @ 2-3 a. 4 v. @ 3-5 a. 4 v. 55-
- SP501A, 500-0-500 150 mA. 5 v. @ 2-3 a. 6.3 v. 67 6
- SP425A, 425-0-425 200 mA. 6.3 v. @ 2-3 a. 6.3 v. @ 3-5 a. 5 v. @ 2-3 a. 6.3 v. 10/6
- 150-0-150 80 mA. 6.3 v. @ 4 a. 5 v. @ 2 a. 19/6
- 200-250-250, output 3 v. 30 v. @ 2 a. 17/6
- Charger, 2-6-12 v. @ 1.5 a. 32/6
- Mains Transformer, sub chassis mounted 355-0-325, 70 mA. 5 v. @ 2 a. 6.3 v. @ 2-3 a. 10/4
- E.H.T. Upright for VCR 87 tube, 2 500v. 50 mA. 2-0-200v. 1-1/2, 3-0-24, 2 a. 97 8
- Auto Transformer, 50 watt plus 1 pkx. & post. Input/Output 0-110-210-220-230-240-250 volts 7 6

LOUDSPEAKERS

- ELAC—2 1/2 in. dia. Moving Coil 15 ohms impeded. 15/-
- PLESSEY—3 in. dia., Moving Coil, 3 ohms impeded. 15/-
- ELAC—3 1/2 in. dia., Moving Coil 3 ohms impeded. 15/-
- ELAC—5 in. dia. Moving Coil, 3 ohms impeded. 14/6
- PLESSEY—5 in. dia., Mains Energised 3 ohms impeded. (600 ohms field) with Pentode Transformer. 22/6
- PLESSEY—5 in. dia., Mains Energised 3 ohms impeded. (600 ohms field) 18/6
- PLESSEY—1 1/2 in. dia. Moving Coil, 3 ohms impeded. £3 6
- GOODMANS—1 1/2 in. dia., Moving Coil, 15 ohms. £8/8
- Plus 5/- packing and carriage.
- VITAVOX—K 12-20 12 in. dia., Moving Coil, 15 ohms impeded. £11 11
- Plus 5/- packing and carriage.
- ALL 12 in. SPEAKERS TAX FREE.**

I132A RECEIVER UNITS

11 valve Superhet receiver covering 100 to 124 Mc/s, using four VR33, two VR65, and VR67, VR70, VR34, and VR57 valves. Fitted with Tuning meter, slow-motion drive, R.F. and L.F. Gain Control, etc. Circuit: R.F. amp. frequency changer, oscillator, and stab., 2-1 F. amps. H.F.O. Det. First audio and output. Brand New with complete instruction diagram.
 PRICE 59/6 plus 7/6 pkg. & carr. ins.

C.R. TUBES

VCR 516
 6 in. Blue picture. Heater 3 V. Anode 4 K.V. in Manufacturer's original Carton.
 PRICE £3/19/6
 Plus 5/- pkg., carr., ins.



VCR 517C

6 in. picture. This tube is a replacement for the VCR97 and VCR147. Guaranteed full size picture
 PRICE 35/- Plus 2/6 pkg., carr., ins.

1155 RECEIVERS
 Slightly soiled. In original case, complete with 10 valves. Frequency range 185 Mc/s - 75 K/c.s. in 5 wavebands.
£7.19.6 Pkg. & Carr. 10/6.

TERMS OF BUSINESS : CASH WITH ORDER OR C.O.D. OVER £1.
 Please add 1/- for Post Orders under 10/-, 1/6 under 40/-, unless otherwise stated.

AMPLIFIER for 200-250 A.C. in handsome radio cabinet 15in. x 11in. x 7in., provision for 6½in. speaker, 3v. (inc. rect.), 3 W. high gain with o.p. triodes. Wired ready for use. £4.12.6 (carr. 7/6).

SPEAKER, 6½in. P.M., 2-3 ohm for above, 12/6 (carr. 1/6 without amp.).

RECEIVER at £9.18.0 (carr. 7/6), 4v. (inc. rect.) plus crystal diode for 200-250 A.C. in cabinet above. for high quality reproduction of M.W. local and L.W. stations.

RECEIVER (ex-Govt.) R1124D. with all valves, 17/6 (carr. 5/-).

AUTO-CHANGER, 3-speed, £8.10.0 (carr. 7/6).

VARIABLE CONDENSERS, 2-gang, 6/-; 3-gang, 3/6.

HEADPHONES (H.R.), 15/- pair.

SPEAKERS, Post 1½ each, P.M. 2-3 ohm, 10in., 20/-; 5in., 12/6; 4in., 11/-; 8in., 17/6.

VOL. CONTROLS, 1.M. 2-pole sw., 4/-; ½ M. 1-pole sw., 3/-.

TAPE RECORDER AMPLIFIER, suits all tape decks. Leaflet on request. £12.12.0.

STEEL CHASSIS, size 7½in. x 5½in. x 1½in., with 2 int. octal valveholders; Transformer (300.0-300), Rectifying valve AZ31. Slightly used at 20/-.

T.C.C., 32-32 mf. 450v. can type, 5/-.

DUBILIER, 40-40-30 mf. 275v., can type, 2/-.

R.F. CHASSIS by famous manufacturer. Over 30 Condensers and Resistors, 3 coils, 3 Ceramic B7G holders. 5/- (1/- P. & P.).

SATISFACTION OR MONEY BACK

All Goods New except R1124D and Chassis.

GLADSTONE RADIO,
GLADSTONE PLACE, NEWTON
ABBOT, DEVON

THE CORONET AC4

COMPONENTS FOR THIS NEW RADIO RECEIVER IN STOCK
PRICE LIST AVAILABLE ON REQUEST

J. T. FILMER,
MAYFIELD ESTATE, BEXLEY, KENT
Tel.: Bexleyheath 7267

COMMUNICATIONS RECEIVER R.1155
The famous ex. Bomber Command Receiver known the world over to be supreme in its class. Covers 5-wave ranges 18.5-7.5 mc/s, 7.5-3.0 mc/s, 1,500-600 kc/s, 500-200 kc/s, 200-75 kc/s, and is easily and simply adapted for normal mains use. Full details being supplied. Aerial tested before despatch. These are BRAND NEW AND UNUSED IN MAKERS' ORIGINAL TRANSIST CASES. ONLY £11 19 6.

A few used receivers, also tested working before despatch, are available at £7 19 6. A few of the R.1155 model, also available. This is the latest version which covers the Trawler Bands, and in addition is fitted with ultra slow motion tuning. Used, but tested working before despatch. ONLY £17 19 6.

A factory made Power Pack, Output Stage and Speaker, contained in a black cracked cabinet to match the receiver, can be supplied at ONLY £5 10. Operates receiver immediately.

RECHASING RECEIVER & POWER PACK TOGETHER. Please add carriage costs of 10/6 for Receiver, and 5/- for Power Pack.

COMMUNICATIONS RECEIVER R.1224A. An ex. R.A.F. 5 valve Battery Superhet which covers 1.0-10.0 mc/s (30-300 metres), in 8 switched wave bands. Employs RF stage and 455 kc/s I.F., large Muirhead slow motion tuning dial, aerial trimmer, reaction BFO control, sensitivity control and H.I. impedance and 300 ohm line outputs. Exceptionally sensitive and selective. Complete with valves in wooden cabinet, with hinged lid, size 14½in. x 10½in. x 9½in. Finished in grey, with calibrated chart. Requires only 2 v. L.T., 9 v. B.B., 1.5 v. H.T. BRAND NEW IN MAKERS' PACKING. ONLY £9 19 6 (carriage, 7/6).

V.H.F. RECEIVER R.1132A. Covers 100-124 mc/s with variable tuning. Complete with all valves, and in BRAND NEW condition. ONLY 45/- (carriage, etc., 7/6).

POWER PACK T.P. 3. Used by the Services with the a.c. receiver. A standard 19in. rack mounting to match the receiver, this is for 200 250 v. 50 cycle mains with output of 250 v. D.C. 100 ma. and 6.3 v. 4 amps. It is fitted with H.T. current meter and voltmeter, and is a really superb unit, which can be used for a variety of sets. Tested working before despatch. ONLY 90/- (carriage, etc., 5/-).

RECEIVER 25/73. Part of the TR.1196. Covers 4.3-8.7 mc/s., and makes an ideal basis for an All Wave Superhet, full modification data being supplied. Complete with valves, 2 each EF36 and EF39, and 1 each EK32 and EBC33. ONLY 22/6 (postage, etc., 2/6).

RECEIVER R.1225. Covers 100-150 mc/s, and contains 5 valves EF50, 4 of EF39 and 1 of EB34, together with a multitude of short wave components. An excellent little breakdown unit for ONLY 25/- (postage, 2/6).

INDICATOR UNIT, TYPE 95. Exactly the same as the Type 62, but for 50 cycle operation. Built on a two-deck chassis, it contains VCR97 Tube with mu-metal screen, 16 valves SP61, 2 of EB31 and 4 of EA50, also shoals of components. In new condition. A snip at ONLY 59/6 (carriage, 7/6).

INDICATOR 62A. Another two deck chassis job, this contains VCR 97 tube with Mu-metal screen, 12 valves EF50, 4 of EF39, 2 of EA50 and 2 of EB31. IN NEW CONDITION IN MAKERS' TRANSIST CASES. ONLY 99/6 (carriage, etc., 10/-).

TRANSFORMERS. Ex. W.D. & Admiralty. Built to more than 50% safety factor, with normal A.C. Mains Primaries. All Brand New and Unused.

30 v. 0-330 100 ma., 4 v. 3 a. 22 6.
EHT 1,400 v. 2 ma., 520 v. 10 ma., 300 v. 10 ma., 2 v., 1.5 a. ... 21/-
L.T. 6.3 v. 7.7 a., 4.2 v. 2.5 a., 4 v. 1 a. ... 19/6
L.T. 4 v. 20 amps. C.T.

Please add 2/6 per transformer postage.
AVO MODEL 40 UNIVERSAL TEST METERS. Have had some use but every meter has been thoroughly checked and tested, and is GUARANTEED IN PERFECT WORKING ORDER. An ideal opportunity to acquire a first grade tester at low cost. ONLY £9 19 6.

C.W.O. Print name and address clearly. Amounts given for carriage refer to inland only.

U.E.I. CORPORATION,
133, Gray's Inn Road, London, W.C.1
(Phone : TELitmon 7937)
(Open until 1 p.m. Saturdays. We are 2 miles from High Holborn (Chancery Lane Station) and 5 mins. by bus from King's Cross.)

LYONS RADIO LTD.

3, GOLDHAWK ROAD, Dept. M.P.
SHEPHERDS BUSH, LONDON, W.12.
Telephone : SHEpherds Bush 1729

L.T. METAL RECTIFIERS.—Full wave bridge type, 6 v. or 12 v. 3 a., size 3½in. sq. x 1in. PRICE 12/6. Full wave C.T. types, 6 v. 1 a. PRICE 4/- 6 v. 1 a. PRICE 4/9.

EXTENSION SPEAKERS.—Standard low impedance moving coil 6½in. loudspeakers fitted in attractive cabinet with polished walnut finish, approx. size, 9 x 8½ x 4½ins. PRICE 35/-.

A.C. POWER UNITS.—Input 200-250 v. 50 cycle mains. Outputs: 6.3 v. for total loading of 4 a. and approx. 220 v. smoothed D.C. for total loading of 60 mA. A double section choke filter is incorporated to give exceptionally good smoothing and rectifier employed is a 5Z4. These power units are suitable for most communications receivers and will make a good standby unit for general use. Housed in metal cases, 8½ x 6½ x 4½ins. Made in our own workshops from first grade components. PRICE 70/- post 2/6.

ELECTROMAGNETIC MICROPHONES.—2in. dia. round hand type as fitted to air pilots oxygen mask, with on/off switch and short lead. PRICE 3/6, post 8d. Can be used with the A1368 described below.

AMPLIFIERS UNITS, TYPE A1368.—These are two valve A.F. amplifiers and can be used for intercom, purposes or as a microphone pre-amp. With slight mod. (details supplied) can also be used as a gramophone amplifier. Valves fitted are VR21 (210L.F.) and VR35 (QP21). Operated from 2 v. L.T., 90-120 v. H.T. and 9 v. G.B. Housed in neat metal cases, 7 x 5 x 4½ins., in good condition. A REAL SNIP AT ONLY 10/6, post 2/-.



Accurately tests High, Low and Grid Bias Batteries. Write for leaflet 29 M



WATERLOO RADIO
(Waterloo Bridge Roundabout).
35, TENISON WAY, S.E.1.

3 SPEED AUTOCHANGERS. Collaro 3RC 521. Supplied brand new in unopened cartons, complete. With L.P. and Standard pick-up heads. 100-250 v. A.C. Only a limited quantity available but one will be reserved for you on receipt of £1 deposit.

BARGAIN PRICE £9.19.8.
Carriage 7/6.

L.T. METAL RECTIFIERS. 6 or 12 volt. bridge, 1 amp., 4 1/2 in.; 1 amp., 5 1/2 in.; 2 amp., 7 1/2 in.; 3 amp., 8 1/2 in.; 4 amp., 10 1/2 in.; 6 amp., 14 1/2 in. H.W. R.M. 60 mA., 3/9; R.M2, 100 mA., 4/3; R.M3, 120 mA., 5/3; R.M4, TV Rectifier, 275 mA., 250 volt., 15/6.

VALVES. 6AM6, 6CH6, 6AL5, 6AU6, 6X1, 6BE6, 6BA6, 12BE6, 12BA6, 6B6, 6HW6, 6BW7, 6AT6, 1T4, 1U5, 12AT7, 3A4, 1B6, 6W7, U78, 7/6 each, any 3 for £1, your selection.

Overseas enquiries invited

TELETRON SUPER INDUCTOR COILS.


Miniature dust core type
Dual Wave TRF, 7-7, Super Het Coils for all Bands. AE & OSC. 6-Pr. Hi-Freq. crystal Transformer coils, triple wound for crystal diodes, 3/- ea. IFT's H.F. Chokes, etc. Stamp for list & Circuits.



The Teletron Co., 269, Nightingale Rd., London, N.9.

BENTLEY ACUSTIC Corp. Ltd.			
38, Chateauf Road, N.W.1. PRInthrose 9090.			
OZ4	4/6	607	8/6
1A5	4/-	6B7	8/6
1C4	8/-	6SA7	8/-
1C6	6/-	6SG7	6/-
1L4	5/6	6SH7	4/6
1LD5	5/6	6SJ7	8/-
1LN5	5/6	6SK7	4/6
2X2	5/-	6SL7	8/-
2D6	4/6	6SN7	8/6
5V4	8/6	6V3	7/-
5X4	11/6	6X3	7/-
5Y3	8/-	6Z4	7/6
6A7	8/6	7B7	7/-
6AG7	8/6	7C3	6/6
6B3G	4/-	7D3	7/-
6B8M	5/6	7E7	7/-
6CD9G	11/6	7F3	7/-
6CH6	6/6	7H7	7/-
6CG5	5/6	7J7	7/-
6CS5M	6/-	7K7	7/-
6C5	6/-	7L7	7/-
6C8	11/6	7Y4	7/-
6D6	6/-	10D1	4/-
6E6	7/-	12AT7	7/-
6F7	7/-	12AU7	9/-
6F9	6/6	12AX7	6/6
6HG8	2/-	12C3	8/6
6H6M	2/6	12H6	2/-
6J5G	5/-	12J5	4/-
6J5M	5/6	12K7	8/6
6J7G	5/-	12Q3	8/-
6K8	5/-	12Q7	8/-
6K7G	4/6	12SC7	5/-
6K7M	5/-	12SK7	7/6
6K8	9/-	12SL7	8/-
6L6	8/6	12SQ7	8/6
6L7	6/-	12SR7	7/-
6N7	5/6	12Y4	7/-

Programme Pointers

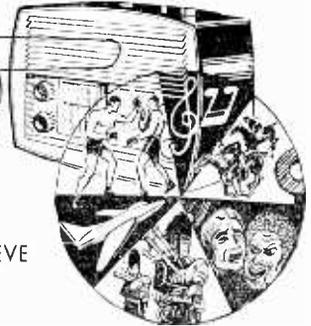

The Edinburgh Festival

THE Edinburgh International Festival has rightly and properly established itself amongst the leading festivals of the present day. And listeners should be particularly grateful for having a marvellous series of programmes brought to them in their homes. But like all worthwhile things—from Test matches to Promenade concerts, or from The Archers to Gilbert Harding—it cannot remain static; it will either advance or retire. Presuming it to be a certainty that it will do the former, the question will be—on what lines?

The composition of its programmes is, of course, no concern of mine except—and a big exception it is—in so far as they concern the franchise of radio listeners. As with the Proms, the tendency at Edinburgh would seem to be to get bigger and bigger, just for the sake of getting bigger. In my estimation, the Proms have greatly degenerated in recent years (the performance at the final concert of the season of Eileen Joyce in the Schumann was quite unbelievably bad, though the vast audience screamed and yelled its approval like any Wembley cup-final crowd does when its heroes score goals irrespective of the quality of the play), with symphonies, concertos, arias, scenas, overtures, suites, etc., etc., thrown at us in huge masses. They are no longer concerts of taste and discrimination as they once were. And Edinburgh is similarly heading that way and is leaning towards becoming a huge emporium. Is it necessary to go such vast distances to hear Beethoven's third concerto and Tchaikovsky's fifth symphony—works which are coming to us from all corners of the earth throughout the year? Surely, sirs, the answer is in the negative.

"Leisure Hour"

This is surely one of the most innocuous and goody-goody shows the BBC has ever mounted. Quite pleasant if pleasantness is all one wants, utterly harmless and unoffending. I heard Bransby Williams give a marvellous little sketch of an old salt who was a devil with the ladies. Gerald Moore is an entertaining broadcast raconteur, but his "solos" at the end of each reminded one more of a terribly shy child going up for her grade four than a radio pianist. Also, in his story of Kreisler never having played in Wigmore Hall, either Mr. Moore's or Kreisler's memory was at fault.

"A la Carte"

This was an amusing half-hour about food, interestingly read by Gladys Young, Carleton Hobbs and David Peel, and compiled by P. J. R. Wright. But, just imagine, nothing from Dickens, who tickled our palates more than any writer who ever lived.

The Theatre

And so to the theatre. What is a masterpiece? Surely as good a definition as any would be: A piece which, dealing with a major problem that its author thinks should be solved on the lines he expounds

By MAURICE REEVE

herein, continues to grip us and hold us long after the problem's solution has become part and parcel of our lives. Thus Dickens remains a great novelist and Ibsen, whose "Rosmersholm" recently enthralled us as much as ever, a great dramatist. Mary Wimbush, James Bale, Robert Harris and Malcolm Hayes gave full justice to the famous play.

A. E. W. Mason's "Witness for the Defence," though not a masterpiece, interested by virtue of its solid Edwardian atmosphere, and some capital acting parts which are as effective over the radio as they were over the footlights. The woman with a past will, I trust, ever be good entertainment. Renee Goddard, with Stanley Beard, David Peel and others, saw to it that, in this instance, she was.

Joseph Conrad's dramatic story of a Russian spy in London 50 odd years ago made a gripping radio play in the capable hands of Belle Crystall, Richard Hurdnall, Lewis Stringer, Ivan Sampson and many others. I wonder if Conrad was ever so slightly influenced, in ending the story, by Anna Karenina?

D. H. Lawrence's essay in dramatic writing, "The Widowing of Mrs. Holroyd," hardly seemed worth putting on, but "As you Like It" was a joy. How that text came over! like dewdrops or sun shafts.

"Earthquake in Greece"

This was not so good, and didn't capture the atmosphere to anything like the same degree. Whilst the remarks, and voice, of the distinguished person at the conclusion spoiled whatever effect of realism had previously been achieved. It was a production blunder.

"Civil Engineer"

If a voice symbolising Dunkirk, the odd round—in case—, the old home, in spite of, or what you will that's typical of British do-or-die-ism, few better than Leslie Perrins's could be found. It was, therefore, not surprising to hear its stoicism and resolution when turning on "Civil Engineer," a good feature chiefly dealing with last winter's floods, though his name was not advertised in *The Radio Times*.

Quiz

"What Do You Know?" is a good, smart, snappy feature, under a very capable chairman, Franklin Engleman. I wonder how many more varieties of the quiz it will be possible to devise? A good question for one of them might be, "why do the producers of the many Trollope serials leave out the apostrophe?" The "I cannots" and "I will nots," give them such a stilted air. I cannot (can't) say whether Trollope himself does, as I plead guilty to never having read him. But Dickens, and other contemporaries, certainly do not (don't).

OPEN TO DISCUSSION

The Editor does not necessarily agree with the opinions expressed by his correspondents. All letters must be accompanied by the name and address of the sender (not necessarily for publication).

Lining-up a Superhet

SIR—One of the amateur constructor's chief difficulties in aligning a newly-built "superhet" receiver is to know the optimum setting of the tuning gang for reception of a station around 250 metres and around 430 metres.

Manufacturers could greatly assist their customers if they provided information about their coils in one of two ways, and probably stimulate their sales thereby.

Method 1. (Adopted by Osmor for battery coil pack.) State the number of degrees out of 100 or 180 that the tuning gang should be opened from the fully-meshed position for reception of the North Regional and M.W. Light (usually approximately 70 deg. and 146 deg. open respectively).

Method 2. The provision of a cheap two- or three-waveband tuning scale in cardboard, with a central hole so that a push-on aeropointer could be used; for purposes of economy only two tracking points need really be marked per waveband.

I think it is a fair one for manufacturers to assume (a) that stray capacities average 25 pF., and (b) that a nominal 500 pF. gang makes 490 pF.—**MAJOR R. PAGE, R.A.E.C. (Bulford).**

The R184

SIR—Having for a long time past been a regular reader of PRACTICAL WIRELESS, I now wish to make use of the excellent section "Open to Discussion." I would like, through this medium, to get into touch with a fellow reader who has an A.M. receiver, type 184. I am informed that with modifications this unit tunes to the V.H.F. transmitter at Wrotham.—**PETER S. MATTHEW (West Wickham).**

Radio-controlled Models

SIR—I am glad to see an article in "Transmitting Topics" (October) on radio control of models. Interest in this branch of radio is on the increase. This is proved by the fact that Tyneside Group membership has increased 100 per cent. during the last 12 months.

I would like to draw your attention to a mistake in this article, which might be misleading to some people. Mention is made of "full permitted output of 5 watts" and again "the full 5 watts into the aerial." The Postmaster-General would not like this. The maximum power permitted is "5 watts

input to the valve or valves which drive the aerial." It will be a good transmitter (portable) indeed which will deliver even 4 watts into the aerial. As a matter of interest, 1 watt output is usually quite ample, and this figure is much more easy on power supplies.

Wishing you every success during your next 21 years.—**N. F. ARMSTRONG (Newcastle-on-Tyne, 3).**

Battery Super-regenerative Receiver

SIR—Readers may perhaps be interested in a battery version I have made of the Super-regenerative Receiver, designed by Mr. P. W. Moir, which appeared in your issue for February, 1952.

Having no mains, I hunted round for some battery acorns and was at last successful in obtaining some 958s and 959s.

The valve sequence in the set I have made is T.R.F. stage 959, det. 958, L.F. transformer coupled to 1T4, thus being R.C. coupled to a IS4 output.

I am using an 18 pF. tuning and 25 pF. R.F. stage condenser, both with slow motion.

The set runs on 90 volts H.T. and 1.5 L.T., and works a 9in. loudspeaker.

I hear the relay station of London and Uxbridge traffic control at full speaker strength (as well as 'planes of all kinds in transit to and from the U.S.A., and from the two "local" service stations (Naval and R.A.F.).

On 10-turn coils I can get both Wenvoe and Holme Moss sound, with a vertical dipole made from two legs of a discarded telescopic camera tripod.

I should have said that the two tuning condensers are both of the miniature split stator type.

The set is built on an aluminium chassis, 9in. by 9in., and is housed in a case, also of aluminium, made from the outer case of a TR9 sawn in half.—**C. A. C. CLARKE (Port Isaac).**


Medium-wave Reception

SIR—I feel that the BBC should make an effort either to add further medium-wave Light Programme transmitters or to increase the power of their present one, reception of which is far from good in many parts of the country. If good reception of the Light could be secured all over Britain on the medium waves there would no longer be any necessity for long-wave tuning in broadcast receivers. In fact, many household radios would only need arrangements for the medium waves, thus reducing the price of the set.—**B. DWYER (Leicester).**

(continued on page 777)

Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying surplus equipment. We cannot supply alternative details for constructional articles which appear in these pages. **WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE.** If a postal reply is required a stamped and addressed envelope must be enclosed with the coupon from page iii of cover.

EX-AM. RECEIVER TYPE R1155.

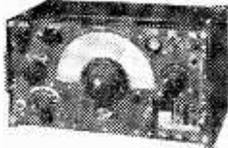

Brand new and unused. 5 Frequency ranges: 12.7-7.5 Mc/s; 7.5-3.0 Mc/s; 1,500-600 Kc/s; 500-200 Kc/s; 200-75 Kc/s. Supplied in maker's original wood transit case. LASKY'S PRICE £11 19 6. Complete. R-1155 Receivers. Second hand, aerial tested, £7 19 6. Carriage and packing 12 6 per unit extra, including 10 - which will be refunded on return of packing case.

FULLY ASSEMBLED POWER PACK AND OUTPUT STAGE FOR R1155 RECEIVERS.



For use on 200-250 volt A.C. mains. Wired and complete with valves. In steel case, black crackle finished, size: 12 x 5 1/2 x 7 in. LASKY'S PRICE, 79 6. Carriage 5/- extra. Power pack as above, complete with 6 1/2 in. loudspeaker. PRICE £25/5/0. Carriage 5/- extra.

SPECIAL C.R.T. OFFER

Brand new and unused 12in. ion trap type television cathode ray tubes. 6.3 volt heater, 7.9 kV, E.H.T. 35 mm. neck. Black and white picture. By famous manufacturer. PERFECT. £12 19 6. Carriage and insurance 15/- per tube extra.

TELEVISION SELENIUM RECTIFIERS

The very latest "Sentercell" S.T.C. range.

K3 40, 3.2 kV.	7 6
K3 45, 3.6 kV.	8 2
K3 50, 4.0 kV.	8 8
K3 100, 8.0 kV.	14 8
K3 160, 12.8 kV.	21 6

MAINS TRANSFORMERS

All 200-250 volts c.p.s. primary. Finest quality, fully guaranteed.

MBA/3. 350-0-350 v. 80 mA. 6.3 v. 4 a., 5 v. 2 a. Both filaments tapped at 4 volts. An ideal replacement type. Price, 18/-.

MBA/5. 350-0-350 v. 125 mA. 6.3 v. 4 a., 5 v. 3 a. With mains tapping board. Price, 27 6.

MBA/6. 350-0-350 v. 100 mA. 6.3 v. 3 a. 5 v. 2 a. With mains tapping board. Price, 22 6.

MBA/7. 250-0-250 v. 80 mA. 6.3 v. 3 a., 5 v. 2 a. Both filaments tapped at 4 volts. Price, 15/-.

MBA/8. SPECIAL OFFER. Drop through type. 235-0-225 v. 60 mA. 6.3 v. 3 a., 12 6.

AT.3. Auto transformer. 0-10-120, 200-230-240 volts, 100 watts. Price, 17/6.

CRYSTAL DIODES

Glass type. Wire ends. 1 6 each

AMPLIFIERS

4-Watt Model. Ex Government. Complete with 10 valves: 2 2L3; 1 6H5; 1 25Z6; 6 6SK7. For operation on 110 volts A.C. D.C. Balance and push pull. High, medium and low impedance inputs. A.G.C. etc. LASKY'S PRICE £5 19 6 complete. No circuits available. Carriage 10/- per unit extra.

50L5 ... 10/-
31Z1 ... 9/-
6AM6 ... 9/-
6H6 ... 2 6
EP50, Red New
Sylvania 10 6

151 ... 9/-	1A5 ... 9/-	6J7 ... 6 6	EF39 ... 7 6
351 ... 9/-	12K8 ... 8 6	HL2 ... 3 6	12K7 ... 10 6
1T1 ... 9/-	12Q7 ... 8 6	KT2 ... 3 6	6L7A ... 10 6
1R5 ... 9/-	6AL5 ... 9/-	6K3 ... 9 6	EA50 ... 2 6
1S5 ... 9/-	6K7 ... 8 6	U50 ... 9/-	13C33 ... 2 6
1C5 ... 9/-	1D5 ... 4 6	ECB35 ... 13 6	35L6 ... 10/-

VALUES. 10,000 IN STOCK AT THE LOWEST POSSIBLE PRICES. SOME EXAMPLES.

SPECIAL OFFER. 4 Valves: 1 each 1R5, 1T4, 1S5 and 3S4. LASKY'S PRICE 32/6. POST FREE.

DINGHY AERIALS, WITH REFLECTORS

Umbrella type, with wire mesh reflector. Complete with setting up instructions. Mast not supplied. Ex. American Air Corps. Ideal for short-wave reception. LASKY'S PRICE, 6/- POST FREE.

R.1132-A RECEIVERS

Supplied in maker's original wood transit case. Frequency coverage 100-124 Mc/s. 11 valves: 1 VR65, 1 VR66, 4 VR53, 2 VR54, 1 6J5, 1 V570, 1 VR37. Large tuning scale with slow motion drive. 0-5 mA. tuning meter, R.F. and L.F. gain controls, jack socket for line and phone. Totally enclosed in metal case, grey enamelled with plated handles. Size: 18 x 10 x 11in. Supplied with all valves, also circuit and calibration chart.

GRADE 1. Brand New 79 6. **GRADE 2.** Soldered 49 6. **GRADE 3.** secondhand 39 6. Carriage 10/- per unit extra.

LASKY'S TV. CONSTRUCTOR'S PARCEL

All brand new components by Ibranic. Comprises E.H.T. flyback line transformer, 7-10 kV, with ferroxcube core, and rectifier heater winding; scanning coils, frame output transformer, Elac focus unit with vernier adjuster, U37 EHT, rectifier 12in. cathode ray tube and ion trap, mesh and glass.

LASKY'S PRICE FOR THE COMPLETE PARCEL. £15 19s. 6d.

Carriage and insurance 15/- extra.

The Constructor's Parcel. As above but less cathode ray tube and ion trap.

LASKY'S PRICE, 79 6. Postage 3 6 extra.

DE LA NE TV. CABINETS.

For new ESI Mark II model. For 12in. tubes. Finished in beautiful reured walnut veneer, with either light, medium or dark polish. Supplied complete with mask, glass, back, speaker baffle and fret, casions and c.r.t. neck protector. Inside dimensions: 16 1/2 in. deep, 17 in. wide, 28 1/2 in. high. Overall height 32 in. and width 18 1/2 in. **LASKY'S PRICE. £5 10 0.** Carriage 12 6 extra.

LARGE SCREEN TV. CABINET

Specialy designed for use with the late-r large screen 16in. and 17in. c.r.t. tubes. Finished in figured walnut veneer, beautifully polished in either light, medium or dark shade. Supplied with back, speaker baffle and fret, casions and c.r.t. neck protector. Control panel aperture cut out at upper r.h. side. Inside dimen-

ROMAC 25 WATT AMPLIFIER

Complete with 7 valves, including 2 6L6 in push pull. Provision for high and low imp. microphone. Also fitted with long and medium wave radio tuner unit. For use on 200-250 v. 50 c.p.s. mains. BRAND NEW AND UNUSED. LASKY'S PRICE £25 0 0. Carriage 25/- extra.



COLLARO 3-SPEED AUTO CHANGERS



Brand new and unused in maker's original carton. Fitted with twin crystal heads. LASKY'S PRICE, £9 19 6. Carriage 3 6 extra.

BAFFLE RADIO CABINETS



Pleasing design, complete with drilled chassis, dial, drum drive and back. Finished in satin mahogany veneer, natural wolfish. Outside dimensions: 17 1/2 in. wide 11 1/2 in. high 5 1/2 in. deep. **LASKY'S PRICE, 36/-.** Carriage 2/- extra.

METAL RECTIFIERS

6 and 12 volt P.W. Bridge.	
0.6 a.	4 6
2 a.	9
3 a.	9 11
4 a.	12
6 a.	17 6
6 Volt centre tapped bridge.	
0.75 a.	3 9
1 a.	3 11

S.T.C. SENTERCELL RECTIFIERS

RM.1	3 10
RM.2	4 3
RM.3	5
RM.4	18

LOUDSPEAKERS

First Quality. All 7ohm speech coil. Less output trans.

3in.	15 6
4in.	10 6
5in.	13 6
6in.	13 6

Now available. 12in. Goodmans heavy duty 15 watts. 15 ohms. **LASKY'S PRICE, £5 19 6.** Carriage 3 6 extra.

9in. TABLE T.A. CABINET

Medium shade mahogany. Complete with back, safety glass and speaker fret. Internal dimensions, 19 1/2 in. high, 10 in. wide, 11 in. deep. **LASKY'S PRICE, 39 6.** Carriage 7 6 extra.

LE. TRANSFORMERS

465 Kc/s. Iron dust cores in cans, midge type. Size: 1 1/2 in. x 2 1/2 in. Price 9 8 per pair. WEARITE TYPE 530. 415-720 Kc/s. 10/- per pair. WEARITE TYPE 503. 150-170 Kc/s. 10/- per pair.

TEST PRODS. Fused, with fully retractable points. Price 41 11 per pair.

GRAM MOTORS. Rim drive. For 200-250 v. 50 c.p.s. Many uses. 9 6 each.

sions: 16 1/2 in. deep, 17 1/2 in. wide, 28 1/2 in. high. Overall height 32 in. and width 18 1/2 in. **LASKY'S PRICE, £5 10 0.** Carriage 12 6 extra.

CONDENSERS

Electrolytic Cans.	
16 mfd. 500 v.w.	3 6
24 mfd. 450 v.w.	3 11
32 mfd. 500 v.w.	5 11
60 mfd. 350 v.w.	3 6
64 mfd. 450 v.w.	4 11
8+8 mfd. 450 v.w.	3 11
8+16 mfd. 450 v.w.	3 11
16+16 mfd. 500 v.w.	4 6
16+16 mfd. 500 v.w.	4
16+24 mfd. 450 v.w.	4 11
16+32 mfd. 450 v.w.	4 9
20+20 mfd. 275 v.w.	2
32+32 mfd. 500 v.w.	4 11
32+32 mfd. 350 v.w.	2 11
60+100 mfd. 350 v.w.	7 6
250 mfd. 350 v.w.	4 11

MANY OTHER TYPES IN STOCK

Send us your requirements.

LASKY'S RADIO

Lasky's (Harrow Road), Ltd., 370, Harrow Road, Paddington, London, W.9
Telephones: CUNningham 1979-7211. All Depts.

MAIL, ORDER AND DESPATCH DEPARTMENTS: 485-487, HARROW ROAD, PADDINGTON, LONDON, W.10.

Hours: Mon. to Sat. 9.30 a.m. to 6 p.m.; Thurs. half day, 1 p.m. Postage and packing charges (unless otherwise stated): on orders value £1-1s. 0d. extra; £5-2s. 0d. extra; £10-3s. 6d. extra; over £10 carriage free unless specifically stated otherwise. All goods fully insured in transit.

Using the R1155

SIR,—I feel that my experiences with the R1155 might be of help to any would-be modifiers among your readers. I carried out Mr. Cruickshank's modification to the first R.F. stage, but using a 6AC7 instead of the EF50.

I found that, whereas signal levels generally had increased, so had the noise level. Thus, the signal/noise ratio was no better, if not worse.

Also, severe cross-modulation was found to be taking place on range 3 (M.W.), the Third Programme modulation being present on all signals. (I am close to a relay.)

I next tried an EF39 as first R.F., only to find signal levels lower than when using the original KTW62, and signal/noise only slightly improved.

The real solution was found by replacing the original KTW62 and building an external pre-selector, using, in the writer's case, a B7G 6F12.

The solution has several advantages:

- Greater signal levels.
- Better signal/noise ratio.
- Reduction of second channel interference.
- Pre-selector can be made to match any antenna (dipoles, etc.), whereas the R1155 will normally only match the long wire type.

A final hint is: use the 1155 with headphones for DX listening. It was designed for headphones, and works much more quietly when they are used.

All the above tests were carried out on the 14 Mc/s amateur band.—B. JENKINSON (Sheffield).

Re "A Plaintive Cry"

SIR,—I was surprised to note a part of Nottingham is still on D.C. and seeing the "Coronet A.C.4" is practically the same as Burne-Jones Ltd. supplied to the blind years ago, I would (in face of the BBC threat to put the West Region on the V.H.F. bands, thus putting all blind people's sets out of action for West Region) be pleased if you would supply diagrams of a good low-priced adaptor that could be put in the present medium/long waveband sets now in use.

This would save the N.I.B., London, a lot of worry and expense.—J. O. COLEMAN (radio repairer to Plymouth District N.I.B.).

A.C. Band-pass 3

SIR,—May I also offer my congratulations to you on designing the A.C. Band-pass 3.

I completed the set about seven months ago and I got extremely good results from it.

Later, I added the R.F. stage and volume was greatly increased.

I have also added a pair of short-wave coils, which give me a range of 12-30 metres.

This was the first all-mains receiver I ever made, as I am only 15 years old, and was rather hesitant about attempting such a set, because my only previous experience was with small battery sets utilising 2-volt valves (HL2, KT2, etc.). However, I am now looking forward to constructing your "Coronet Four" superhet, so please add my name to the list of satisfied constructors of such grand little circuits published in PRACTICAL WIRELESS.—J. OLIVER (Madeley, Shropshire).

News from the Clubs

RADIO SOCIETY OF GREAT BRITAIN

Gen. Sec.: John Clarricoats (G6CL), New Ruskin House, Little Russell Street, London, W.C.1.

London Meetings Programme:

NOVEMBER 20th. "The Television Society's New TV Station" by Messrs. H. de L. Banting; D. N. Corfield, D.L.C.(Hons.), A.M.I.E.E., and E. A. Dedman.

December 18th. Annual general meeting, followed by extraordinary general meeting.

January 29th, 1954. "Art and Science in Sound Reproduction," by Mr. F. H. Brittain, D.F.H. (Research Laboratories, The General Electric, Co., Ltd.).

February 26th. "Practical Aspects of Tape Recording," by Mr. S. A. Lacey (Research department, Murphy Radio, Ltd.).
March 26th. "Trustworthy Valves and Their Manufacture," by Mr. G. P. Thwaites, B.Sc.(Eng.) A.M.I.E.E., A.M.Brit.I.R.E.

EDINBURGH AMATEUR RADIO CLUB

Hon. Sec.: D. Black, 16, Edina Place, Edinburgh.

THE following programme has been arranged for this year:

- November 18th. R.S.G.B. lecture on tape.
- December 2nd. Audio Amplifiers, by T. Telford.
- December 16th. TV Construction, by C. Patrick.

The club station (GM3HAM) will operate every alternate week. New members and visitors welcomed. Club-rooms, 16, Bothwell Street (Downstairs), Easter Road.

WELLINGBOROUGH AND DISTRICT RADIO AND TELEVISION SOCIETY

Hon. Sec.: N. M. Seabrooke, 85, The Drive, Wellingborough, Northants.

NOVEMBER 19th. "The Commercial Side of Radio and Television." An informal discussion led by Mr. R. S. Marriott, manager of W.I.C.S. Radio/Electrical Dept.

December 18th. "Some Problems Affecting Reception of Radio and Television in This Area." Talk by Mr. A. C. Homer, Post Office Engineering Dept., Northampton.

January 21st. "Some V.H.F. Phenomena, With Demonstrations," by Mr. G. A. Wilford. N.B. This lecture will start promptly at 7.30 p.m., as some of the demonstrations may cause local interference with TV.

February 18th. "More About Electricity." A welcome return of Mr. M. Robins, lecturer on electrical engineering at Wellingborough Technical College.

March 18th. "Television Aerials." Talk by Mr. J. W. Hoble. **April 20th-23rd.** Hobbies and Careers Exhibition, at the Drill Hall, Wellingborough. The society has been asked to organise the Radio Hobby stand.

May 20th. Annual general meeting.

The club-room is situated above the Co-op. Society's Fruit Shop, Silver Street, Wellingborough. Meetings every Thursday, 7.30 p.m.

CLIFTON AMATEUR RADIO SOCIETY

Hon. Sec.: C. H. Bullivant, 25, St. Fillans Road, London, S.E.6.

AT the society's annual general meeting, held on September 11th, the following were elected as officers for the ensuing year: Chairman, J. Lambert (G3FNZ); Hon. Secretary, C. H. Bullivant (G3DIC); Hon. Treasurer, N. Moore; Committee, Messrs. E. Smith and D. Veasey.

The society continues to meet every Friday at 7.30 p.m. at the club-rooms, 225, New Cross Road, S.E.14, and new members and visitors are always welcome.

Preparations are in hand for participating in the M.C.C. during November, and a committee has been formed to arrange operators, log keepers, etc.

Recent events on Friday evening have included a talk on V.H.F. by one of our junior members, G3JRC, an entertaining quiz devised by G3FNZ and a Junk Sale. A full programme has been arranged by the committee covering the next few months, one of the highlights being a film show.

STOKE-ON-TRENT AMATEUR RADIO SOCIETY

Hon. Sec.: C. H. Parkes (G3EHM), 159, Belgrave Road, Longton, Staffs.

THE club premises are situated at the Cottage Inn, at the rear, in Oakhill. At present, the main object is to re-equip our workshop with a full range of tools and accessories so that any type of constructional work can be undertaken by members. This should fill a long-felt want.

The headquarters will also open on Tuesday nights for enthusiastic constructors. It is hoped that large quantities of tea will be readily available for members. All persons interested in joining the society are asked to write to the secretary and are invited to come along any Thursday night.

News from the Trade

New G.E.C. Flashers

LONDON and provincial cities and towns have fitted an increasing number of flashing signs and lights. The problem of preventing electrical interference from these flashing lights spoiling viewers' and listeners' enjoyment of television and radio programmes has become acute. The General Electric Co. Ltd., working in collaboration with the Post Office Engineering Department, has evolved a lampholder adaptor flasher with a built-in suppressor unit that has passed Post Office tests and complies with the relevant clauses of B.S.800 (limits of radio interference) covering television bands of 40-70 Mc/s. It is also highly effective on the broadcast radio bands. The price of the new flasher is 14s.

Ratings of the flasher are :

Volts	Watts
100/115	15/20
200/260	30/40
100/115	30/40
200/260	60/80
100/115	60/80
200/260	100

A special version of the unit suitable for use with Christmas and party decoration lamps has also been developed.—General Electric Co. Ltd., Magnet House, Kingsway, W.C.2.

Radio Mail Test Instrument Kits

THE recent appearance on the market of these kits has opened up new fields for constructors and others whose needs for really cheap test gear has not been catered for hitherto.

The latest addition is an Inductance Bridge Kit, priced 42s. 6d., covering from 50 μ Hy. to 100 Hy. in five ranges. This generous coverage compares well with the flexibility of the six range Res/Cap Bridge Kit supplied by the same firm at 31s. 6d., covering from 10 Ω to 5M Ω , and from 500 pF to 50 μ F.

Each kit is supplied with a ready calibrated panel, a separate direct reading scale being given for each range. Clear diagrams and comprehensive instructions make assembly remarkably easy with the simplest of tools.—Radio Mail, 4, Raleigh Street, Nottingham.

New Mullard Deaf Aid Valves

TINY valves, an inch long and thinner than an ordinary pencil, are the latest contribution of Mullard Ltd. to deaf aid design. Battery economy, making possible even smaller deaf aid appliances, has thus been achieved.

These new valves reduce low tension drain by 33 per cent. Filament consumption of previously

available Deaf Aid valves was 15 mA. These new valves, designated the Mullard DF64 and DL64, consume only 10 mA. filament current. They mark a significant advance in L.T. battery economy, the most pressing problem of deaf aid design. Batteries of a given size will now last longer, or smaller batteries may be used to give the same life as the standard batteries used with 15 mA. valves. In practice the L.T. current will now be 20 mA. for a three-stage amplifier using types DF64 and DL64, compared to 30 mA., using the 15 mA. types. The design rating of the L.T. voltage, 1.25 v., permits the use of any of the types of L.T. battery at present available, including mercury cells.

The potential reduction in battery size using the new Mullard valves is not confined to the L.T. cell. These new subminiatures have been specially designed to give optimum performance with H.T. supplies of 15 v., as opposed to 22½ v. in the case of current types. The valves themselves are smaller than their 15 mA. counterparts.—Mullard Ltd., Century House, Shaftesbury Avenue, W.C.2.

Teletron Coils

AMONG the range of precision-wound coils manufactured by the Teletron Company is a new triple-wound H.F. coil designed especially for use with the modern Germanium crystal diode. The design is such that minimum damping of the tuned section takes place and maximum selectivity with high sensitivity is obtained. A standard .0005 μ F tuning condenser should be used and the results are better than with the ordinary type of coil. The price is 3s.—The Teletron Co., 266, Nightingale Road, Edmonton, N.9.

Ediswan (Mazda) Valve Booklet

A NEW handy pocket-size booklet has been issued by the Edison Swan Electric Co. Ltd. In 64 pages it covers all the Mazda valves with principal characteristics, Mazda valve complements of standard television receivers, equivalents, etc. The booklet is available free of charge from any Ediswan district office.—Edison Swan Electric Co. Ltd., 155, Charing Cross Road, London, W.C.2.

Gillon Electric Ltd.

A NEW company under the above title has recently been formed by Mr. G. D. Gilbert and A. L. Leeson, late of Allen Components. They will specialise in the manufacture of radio and television components and the address is Rookstone Works, Rosemary Lane, Camberley, Surrey.

Editorial and Advertisement Offices :

"Practical Wireless," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Phone: Temple Bar 4383.

Telegrams: Newnes, Rand, London.


Registered at the G.P.O. for transmission by Canadian Magazine Post.

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Wireless." Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed: The Editor, "Practical Wireless," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Owing to the rapid progress in the design of wireless apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent. Copyright in all drawings, photographs and articles published in "Practical Wireless" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. "Practical Wireless" incorporates "Amateur Wireless."

R.S.C. 25 Watts "PUSH-PULL" QUALITY AMPLIFIER

We are proud to introduce our A II Quality Amplifier, which we consider to be the best value in amplifiers offered to-day. The volume of its high fidelity reproduction is completely controllable, from the sound of a quiet intimate conversation to the full, glorious volume of a great orchestra. Its sensitivity is so high that in areas of fair signal strength it can be operated straight from a crystal receiver. Entirely suitable for standard or long playing records in small homes or in large auditoriums. For electronic organ or guitar or for garden parties or dance bands. The kit is complete to the last detail, and includes easy to follow point-to-point wiring diagrams.

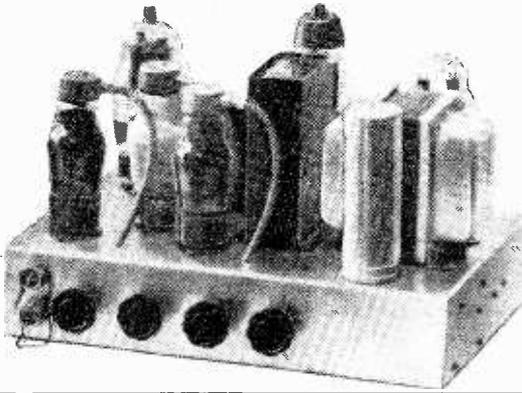Twin volume controls with twin input sockets allow



SIMULTANEOUS INPUTS for BOTH MICROPHONE and GRAM, or TAPE and RADIO. **SEPARATE BASS and TREBLE CONTROLS**, giving both LIFT and CUT. **FOUR NEGATIVE FED BACK LOOPS** with 15 db in the main loop from output transformer to voltage amplifier. Frequency response 50-20,000 c.p.s. HUM and **DISTORTION LESS THAN 0.5 per cent.** measured at 10 watts, six B.V.A. valves. Marconi Osram KT series output valves. A.C. only. 200-250 v. 50 c/s. Input, 120 v. H.T. LINE. Paper reservoir condenser. Compact chassis. Matched components. Size 14" x 10" x 9ins. Outputs for 3 or 15 ohm sprks. Available in kit form at the amazingly low price of 9 gns. Plus carriage 5-. Or Ready for use 53/- extra.

BATTERY SET CONVERTER KIT. All parts for converting any type of Battery receiver to All Mains A.C. 200-250 v 50 c/s. Kit will supply fully smoothed H.T. of 120 v 90 v, or 60 v at up to 40 mA, and fully smoothed L.T. of 2 v at 0.4a to 1 a. Price, complete with circuit, wiring diagrams and instructions, only 48/9. Or ready to use, 7/9 extra.

PERSONAL SET BATTERY SUPERSEDER KIT. A complete set of parts for construction of a Unit (housed in Metal Case) to replace Batteries where A.C. Mains supply is available. Input 200-250 v 50 c/s. Output 90 v 10 mA and 1.4 v 250 mA, fully smoothed. For 4-valve receivers. Price complete with circuit, only 35/9. Or ready for use, 42/6. Size of unit, 5 1/2 x 4 x 1 1/2 ins.

H.T. ELIMINATOR AND TRICKLE CHARGER KIT. Input 200-250 v A.C. Output 120 v 40 mA, fully smoothed, and rectified supply to charge 2 v acc. Price with steel case and circuit, 29/6. Or ready for use, 7/9 extra.

BATTERY CHARGER KITS. For mains 200-250 v 50 c/s. To charge 6 v acc. at 2 a. 25/6. To charge 6 or 12 v acc. at 2 a. 31/6. To charge 6 or 12 v acc. at 4 a. 49/9. Above consist of transformer, full wave rectifier, fuses, bushholders and steel case. Any type assembled and tested, 6/9 extra.

EX-GOVT. VALVES (NEW)

1T4	Each	6L6G	Each	35Z4GT	10/6
1R5	8/9	6Q7G	9/11	35L6GT	9/11
1S5	8/11	6SL7GT	11/9	D1	1/9
3S4	9/9	6V6G	8/9	RF36	5/11
5Y3G	8/9	6V6GT	8/9	RB91	9/9
5U4G	10/6	6X5GT	8/9	EP91	9/9
6Z4G	9/6	8D2	2/11	6U4	9/6
6AL5	9/9	807	6/11	EL32	6/11
6F6G	7/11	9D2	2/11	MU14	9/6
6AM6	9/9	954	1/11	MS Pen	5/9
6J5G	5/11	12K7G	10/6	RK31	1/11
6J7G	7/6	12SP4	5/9	SP1	2/9
6K7G	6/11	12Q7GT	10/6	SPU2	2/9
6K8G	11/9	15D2	5/9	VU120	2/11

ELECTROLYTICS (Current production. Not ex-Govt.)

Tubular Types		8μF 500 v	2/11
8μF 350 v	1/9	16μF 450 v	2/9
8μF 450 v	1/11	24μF 350 v	2/11
8μF 500 v	2/9	32μF 350 v	2/11
16μF 350 v	2/3	32μF 500 v	6/11
16μF 450 v	2/9	40μF 450 v	4/11
21μF 350 v	3/6	62μF 450 v	4/11
32μF 350 v	3/6	8-8μF 350 v	3/9
25μF 25 v	1/3	8-8μF 450 v	3/9
50μF 12 v	1/3	8-16μF 450 v	3/11
50μF 50 v	2/3	8-16μF 450 v	4/6
		16-16μF 450 v	4/11
		16-32μF 350 v	5/3
		32-32μF 350 v	4/11
		32-32μF 450 v	5/11

WILLIAMSON AMPLIFIER KIT. All parts to Author's spec. Only 14 gns.

Terms C.W.O. or C.O.D. NO C.O.D. under £1. Post 11 extra under £1.19 extra under £3. Open 9 to 5.30. Sats. until 1 p.m. List 6d. Trade List 5d. S.A.E. please with all enquiries.

A PUSH-PULL 3-4 watt HIGH-GAIN AMPLIFIER FOR £3/12/6. For mains input 200-250 v 50 c/s. Complete kit of parts including circuit, point to point wiring diagram, and instructions. Amplifier can be used with any type of Feeder Unit or Pick-up. This is not A.C./D.C. with "live" chassis, but A.C. only with 400-0-400 v trans. Output is for 2-3 ohm speaker. (We can supply a very suitable 10in. unit by R.A. at 31/-) The amplifier can be supplied ready for use for £1 extra. Carr. 2/6. Full descriptive leaflet, 6d.

BRAND NEW COLLARO 3 SPEED AUTOMATIC RECORD CHANGERS. Type RC3 521, complete with P.U. (2 plug-in crystal heads). Mains input 200-250 v. Limited number at only £9/19/6.

P.A. SPEAKERS. All 2-3 ohms. 8in. Goodmans, 14/9. 6in. Elac., 14/11. 6in. Plessey with 5,000 ohm trans., 14/11; 8in. Plessey, 15/9. 8in. R.A. Heavy Duty 18/9. 10in. Rola 29/6. 10in. Plessey, 18/6. 10in. R.A. 31 - 10in. Rola with 5,000 ohm output trans., 31/9. 12in. Truvox, 49/9.

R.S.C. MAINS TRANSFORMERS (FULLY GUARANTEED)

Inter-laced and Impregnated. Primaries 200-230-250 v 50 c/s Screened.

TOP SHROUDED, DROP THROUGH

250-0-250 v 70 mA, 6.3 v 2.5 a	12/11
260-0-260 v 100 mA, 6.3 v 2.5 a, 5 v 2 a	14/11
350-0-350 v 80 mA, 6.3 v 2 a, 5 v 2 a	17/9
350-0-350 v 60 mA, 6.3 v 2 a, 4 v 2.5 a, 14/11	14/11
250-0-250 v 100 mA, 6.3 v 4 a, 5 v 3 a, 29/9	29/9
300-0-300 v 100 mA, 6.3 v 4 v 4 a, c.t.	23/9
0-4-5 v 3 a	23/9
350-0-350 v 100 mA, 6.3 v 4 v 4 a, c.t.	29/9
0-4-5 v 3 a	29/11
350-0-350 v 150 mA, 6.3 v 4 a, 5 v 3 a	29/11
350-0-350 v 150 mA, 6.3 v 2 a, 6.3 v 2 a, 5 v 3 a	29/11

FULLY SHROUDED UPRIGHT

250-0-250 v 60 mA, 6.3 v 2 a, 5 v 2 a	16/9
Midget type 21-3-3in.	16/9
350-0-350 v 70 mA, 6.3 v 2 a, 5 v 2 a	18/9
250-0-250 v 100 mA, 0-4-3.3 v 4 a	25/9
0-4-5 v 3 a	25/9
250-0-250 v 100 mA, 6.3 v 6 a, 5 v 3 a	29/9
for RU355 conversion	29/9
300-0-300 v 100 mA, 0-4-6.3 v 4 a	25/9
0-4-5 v 3 a	25/9
350-0-350 v 100 mA, 0-4-3.3 v 4 a	25/9
0-4-5 v 3 a	25/9
350-0-350 v 150 mA, 6.3 v 4 a, 5 v 3 a	33/9
350-0-350 v 100 mA, 6.3 v 6 a, 6.3 v 3 a, 5 v 3 a	45/9
350-0-350 v 250 mA, 6.3 v 6 a, 4 v 8 a	45/9
0-2-6 v 2 a, 4 v 3 a, for Electronic Eng. Televisor	67/6
425-0-425 v 200 mA, 6.3 v 4 v 4 a, C.T., 6.3 v 4 v 4 a C.T., 0-4-5 v 3 a, Suitable Williamson Amplifier, etc.	51/-
450-0-450 v 250 mA, 6.3 v 6 a, 6.3 v 6 a, 5 v 3 a	65/9

OUTPUT TRANSFORMERS

Midget Battery Pentode 66 : 1 for 853, etc.	3/9
Small Pentode 5,000 0,000 30 Ω	3/9
Standard Pentode 5,000 0,000 Ω	4/9
Standard Pentode 0,000 Ω to 3 Ω	4/9
Multi-ratio 40 mA, 30 : 1, 45 : 1, 60 : 1, 90 : 1, Class B Push-Pull	5/6
Push-Pull 10-12 watts C/6 to 3 Ω or 15 Ω	15/9
Push-Pull 10-12 watts to match 6V6 to 3-5-8 or 15 Ω	16/9
Push-Pull 15-18 watts to match 6L6, etc. to 3 Ω or 15 Ω Speaker	22/9
Push-Pull 30 watts, sectionally wound 6L6, KT76, etc., to 3, or 15 Ω	47/9
Williamson type exact to Author's spec.	85/-

FILAMENT TRANSFORMERS
All with 200-250 v 50 c/s primaries 6.3 v 1.5 a, 5.9 : 6.3 v 2 a, 7/6 : 0-4-6.3 v 2 a, 7/9 : 12 v 1 a, 7/11 : 6.3 v 3 a, 9/11 : 6.3 v 6 a, 17/6 : 0-2-5-6.3 v 4 a, 16/9 : 12 v 3 a or 24 v 1.5 a, 17/6.

CHARGER TRANSFORMERS
All with 200-250 v 50 c/s Primaries : 0-9-15 v 1.5 a, 14/9 : 0-9-15 v 3 a, 16/9 : 0-15 v 6 a, 22/9 : 0-4-9-15-24 v 3 a, 22/9.

SMOOTHING CHOKES
250 mA 7-10 H 200 ohms, Fully Shrouded ... 16/9
250 mA 3-5 H 50 ohms ... 11/9
100 mA 10 H 175 ohms ... 6/11
80 mA 10 H 350 ohms ... 5/6
60 mA 10 H 400 ohms ... 4/11

H.T. TRANSFORMERS
2,500 v 5 mA, 2.0-2 v 1.1 a, 2.0-2 v 1.1 a, for VCR7, VCR17, ACR2X, etc. ... 35-5,000 v 1 mA 2 v 2 a ... 39/6

RADIO SUPPLY CO. (LEEDS) LTD. 32, THE CALLS, LEEDS, 2



Gives You a NEW Service

CREDIT PURCHASING

That piece of equipment you have long coveted
CAN BE YOURS AT LAST!

Our easy purchase CREDIT SALE scheme allows you to secure immediate delivery of your requirements after a down payment of only one-ninth of the purchase price instead of the compulsory one-third required under hire purchase schemes.

Pay off the balance over 9 months. Detailed below is a selection of merchandise available under this new scheme, but we can supply all electronic equipment in a similar manner. Send us your enquiries.

	Cash Price	To secure send only		Cash Price	To secure send only
Tape Recorders & Tables					
"Editor" Recorder	£47 5 0	£6 0 0	Acos GP20	£3 6 0	11 0
"Grundig" Recorder	£84 0 0	£10 13 0	Decca XMS W/2 Heads	£6 9 3	18 0
Lane Table	£17 10 0	£2 2 10	Leak Ruby 78 or LP	£11 11 0	£1 10 0
Truvox Table	£23 2 0	£2 19 0	Amplifiers		
Wearite Deck	£35 0 0	£4 9 0	Leak Point One	£23 7 0	£3 12 0
Loudspeakers					
Wharfedale W15	£15 10 0	£1 19 4	.. Varislope	£12 12 0	£1 12 4
.. W10CS	£9 15 0	£1 6 2	Quad Acoustical	£35 0 0	£4 9 0
.. W10CSB	£12 6 6	£1 11 10	Hartley Turner 20W	£35 0 0	£4 1 0
.. Super 8CS	£6 6 7	18 9	M.O.S. A8	£3 12 6	14 0
Goodmans Axium 150	£10 5 6	£1 7 0	Gramophone Units		
.. Axium 102	£9 18 0	£1 6 5	BSR Monarch Auto Changer 3 Speed	£16 10 0	£2 2 0
.. Audiom 90	£5 12 6	£1 3 0	.. Regent GU4/TOH 3 Speed	£9 4 11	£1 4 9
WB 12in. Concentric Duplex (less trans.)	£22 11 0	£2 17 11	.. MU10	£3 18 7	12 0
.. 10in.	£9 7 6	£1 4 11	.. MU14	£5 8 6	18 0
.. Tweeter Unit	£3 15 6	12 0	.. MU15	£3 0 0	10 0
Microphones					
Ronette 098 Ball Filtercel	£4 10 0	14 0	Connoisseur 3 Speed Motor Transcription	£21 7 3	£2 14 2
.. HM7 Hand	£4 7 6	14 3	Test Gear		
.. G210 Streamlined Filtercel	£4 19 6	15 3	Pullin Series 100 Test Set	£11 11 0	£1 10 0
.. R474	£15 15 0	£2 0 0	Amplon Test Meter	£5 0 0	15 0
.. R572	£9 19 6	£1 6 6	Advance E2 Generator	£28 0 0	£3 10 0
.. S742	£9 5 0	£1 4 3	.. H1	£25 0 0	£3 3 0
.. RFC	£8 15 0	£1 3 10	Avo Universal Avomitor	£10 10 0	£1 7 6
.. Burgoyne	£2 15 0	9 4	Cossor 1035 Oscilloscope	£33 10 0	£12 0 0
.. Coronation	£2 12 0	8 11	Radio Units, Receivers, etc.		
Cosmocord MIC 16-2	£12 12 0	£1 12 6	Burgoyne RG1 Superhet	£23 2 0	£2 19 0
Reslo Ribbon RV	£9 0 0	£1 4 0	.. RF1 Feeder	£3 12 6	11 4
Pick-Ups					
Ronette Miniweight W-2 Heads	£3 9 6	11 11	Leak Tuning-Unit	£35 0 0	£4 9 0
(14 kecs response)	£3 16 3	12 10	Chapman S5 Tuner	£21 8 8	£2 14 2
Connoisseur Super Lightweight (W-2 Heads)	£9 5 6	£1 5 0	Bush RG11A 3 Speed Auto Changer Gram.	£31 19 0	£7 17 6
			Ekco Portable MBP149	£21 10 0	£2 13 4

MAIL ORDER SUPPLY CO., The Radio Centre, 33, Tottenham Court Road, London, W.1.



NEW! RADIO, TELEVISION AND ELECTRONICS

LEARN THE PRACTICAL WAY
Instruction and Equipment

Here at last is the only real way of making home study really successful. Specially prepared equipment, which remains your property, is supplied thus combining theory and practice in the correct educational sequence. Whether your need be for career, hobby or general interest, here is the most efficient method for acquiring knowledge.

POST THIS COUPON TODAY

Please send me your FREE book on Practical Courses.
To: E.M.I. INSTITUTES, Dept. 32X
43 Grove Park Road, Chiswick, W.4.

NAME

ADDRESS

.....

.....


We will not worry you with personal visits.

Practical courses in many other subjects including:
Draughtsmanship.
Carpentry. Chemistry.
Photography.
Commercial Art.

EMI INSTITUTES
the only Postal College
which is part of a world-wide
Industrial Organisation.

If it's Components

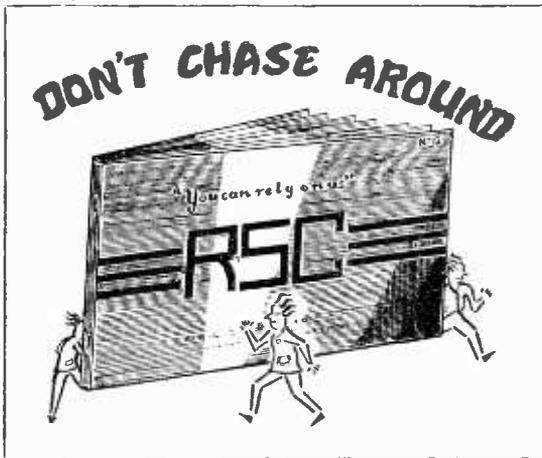AMPLIFIER CABINETS
BRIMISTORS
CABLE PLUGS
CHASSIS
CHASSIS CUTTERS
CHOKES
COAX CABLE
COAX FITTINGS
COILS
COIL CAN-FORMERS
COIL PACKS
CONDENSERS
CRYSTAL DIODES
E.H.T. UNITS/COILS
FEEDER CABLE
FOCUS UNITS
FUSE HOLDERS
GROUP BOARDS
HEADPHONES
I.F. FILTERS
INSTRUMENT WIRES
ION TRAPS
INSTRUMENTS
KNOBS
LINEARITY CONTROLS
LINE CORD
LOUDSPEAKERS
MAINS DROPPERS
METAL RECTIFIERS
MICROPHONES



NUTS AND ECLTS
PAX TUBE
PICK-UPS
POTENTIOMETER3
PUBLICATIONS
PULLEYS, DRUMS
RECORD PLAYERS
RECORDING HEAD3
RECORDING TAPE
RESISTORS
SCALES AND DRIVES
SCREWDRIVERS
SOLDERING IRONS
SPOT WOBBLERS
STUDDING
TAPE DECKS
TERMINAL PANELS
TOGGLE SWITCHES
TRIMMERS
TRIMMING TOOLS
TRANSFORMERS
TUBE MASKS
TUBES
VALVE CANS
VALVEHOLDERS
VALVES
VIBRATORS
VIEWMASTER PARTS
VOLT SELECTOR PANELS
WAVECHANGE SWITCHES

Write now for

CATALOGUE NO. 12 PRICE 1/-
● 70 PAGES ● 250 ILLUSTRATIONS

RADIO SERVICING CO.

82 SOUTH EALING ROAD, LONDON, W.5.

Next to Sth. Ealing
Tube Station

EALing 5737

HENRY'S

We have over 20,000 American and B.V.A. valves in stock.

ALL VALVES NEW AND GUARANTEED

SETS OF VALVES
Ten EF50 (Ex-Brand
New Units) 5/-
each 45 - Set
6K8C, 6K7G, 6Q7G,
5Z4G, 6V6G, (or
KT61) ... 37/6
1R5, 1S5, 1T4, 1S4
or (3S4 or 5V4) ... 30/-
TP25, HL23/DD,
VP23 PEN25 (or
QP25) ... 25/-
6K8C, 6K7G, 6Q7G,
25A9C, 25T5 or
25Z8G ... 37/6
12K8GT, 12K7GT,
12Q7GT, 35Z4GT,
35L6GT or 50L6GT 37/6 ..
12S4GT, 12K7GT,
12S0GT, 35Z4GT,
35L6GT or 50L6GT 37/6 ..
PX25, KT33C, KT66,
GU50 ... 12/6 each
PX25's Matched
Pairs ... 25/- pr.
TEN 6AM6 (EF90) 80/-

OZ4A	7/-	6K8GT	9/-	12SR7	7/6	EF50	5/-	CV54	5/-	
1G6	6/6	6L6G	8/6	14A7	8/6	(Ex-Unit-)	S130	7/6	S130	7/6
1R5	8/-	1R22	11/-	25Z8GT	8/6		7475(V570)			
1S4	8/-	6U5	7/6	25Z5	8/6	SP2	8/6	CV65	6/6	
1S5	8/-	6U5G	7/6	35Z4GT	8/6	VP2	8/6	VR150 30	8/6	
1T4	8/-	6L7	7/6	25A6	8/6	TD2A	8/6	CK510AX	5/-	
1A7GT	10/-	6N7GT	7/6	35L6	8/6	DK40	9/-	DI	2/-	
1C5	8/-	6Q7GT	8/6	50L6GT	8/6	UY11'	9/-	AC5PEN6	6/6	
11L5	8/-	6S37GT	8/6	42	8/6	4D1	4/-	AC9 PENDD	4/-	
2X2	5/-	6R7	8/6	43	8/6	8D2	4/-			
3V4	8/-	6X5G	8/6	75	8/6	8D2	4/-			
3S4	8/-	6S47GT	8/6	78	8/6	8D2	4/-			
5Z3	8/6	6S7GT	8/6	80	8/6	15D2	10/-			
5U4	8/6	6S7	7/6	89A	15/-	R3	8/6	PEN25	6/6	
5Z4	8/6	6SH7M	7/6	9001	6/-	D11	5/-	PEN36	7/6	
6A7G	8/6	6SK7GT	7/6	9002	6/-	D12	5/-	QP25	6/6	
6AC7	6/6	6SL7GT	9/-	9003	6/-	D63	5/-	QP230	8/-	
6AG5	7/6	6SN7GT	9/-	9004	6/-	KT2	5/-	SP61	4/-	
6ARC	8/6	6SC7	10/-	9006	6/-	KT61	8/6	SP41	4/-	
6AM6	9/-	6SS7	7/6	954	6/-	KTW51	7/6	HL23/DD	6/6	
6B8	7/6	6V8GT	7/6	955	6/-	U52	8/6	TP25	8/6	
6C4	8/6	7C5	8/6	956	7/6	U17	10/-	VP23	6/6	
6C5GT	5/-	7A7	8/6	129A	37/6	U19	10/-	VP41	7/6	
6C6	6/6	7C7	8/6	1240	50/-	Y63	8/6	U22	8/6	
6D6	6/6	7H7	8/6	931A	2/-	P2	4/-	ATP4	4/-	
6F6G	8/6	7B7	8/6	EA50	6/-	MU11	8/6	TP22	8/6	
6C6G	8/6	7S7	10/-	EF54	6/-	PX25	12/6	TH23	10/-	
6H6GT	5/-	12A9	7/6	(VR133)	6/-	KT38C	10/-	41MP	7/6	
6H6M	8/6	12C3	7/6	EF55	12/6	KT66	12/6	42SPT	6/6	
6H6GT	8/6	12H6	8/6	EB34	8/6	GU50	12/6	21SSG	4/-	
6J5M	8/6	12K7GT	8/6	EB33	8/6	XP2V	4/-	MS PENB	7/6	
6J6	9/-	12K8GT	8/6	EF36	6/6	XH(1.5)	4/-			
6AK5	9/-	12Q7GT	8/6	EF39	6/6	VU11	4/-			
6J7G	6/6	12S4GT	8/6	EK32	6/6	VU13	4/-			
6J7M	8/6	12S7GT	8/6	EF31	9/-	VU120A	4/-			
6K6	9/-	12SG7	7/6	EL32	7/6					
6K7G	6/6	12SH7	7/6	EF50	8/6					
6K7M	7/6	12SJT	8/6	EF50 (Red. Svl.)	10/-					
6K8G	8/-	12SK7	8/6							

SHADED-POLE MOTORS, 200/250 volts, ideal for Tape Decks, etc. 10/6

CATHODE RAY TUBES:
VCR97, Guaranteed full picture, 40"-carr. 2/-
VCR517, Guaranteed full picture with Mu-Metal screen, 40"-carr. 2/-
3BP1, Suitable for scopes and Tel. 25"-carr. 3/-
MU-METAL SCREEN for VCR97, 10/-
VCR139A (ACR10), 35/- Brand new.

25/73 TR 1196 RECEIVER UNIT—Complete with 6 valves, 2 EF36, 2 EF39, 1 EK32, EBC33. In new condition. Circuit and Conversion Data Free. 25/-, carriage paid.

RECEIVER R1355, As specified for "Expensive Television." Complete with 8 valves VR65 and 1 each 5U4G, VU120, VR92. Only 29/-, carriage 5/-. Or Brand new in original packing case, 55/-, plus 5/- carr.
RF24, 25/-; RF25, 25/-; RF26, 59/6; RF27, 59/6.

VCR517C Blue and White 6in. Tube. This Tube replaces the VCR97 and VCR517 without alteration and gives a full Blue and White picture. Brand new in original crates. 35/-, carr. free.

SEND POSTAGE FOR NEW 1953 COMPREHENSIVE 23-PAGE CATALOGUE : CONTAINING COMPONENTS & EX. GOVT. BARGAINS. Open Mon.-Fri. 9-6. Thurs. 1 p.m.

5 HARROW ROAD PADDINGTON, LONDON, W.2.

TEL. : PADDINGTON 1008/9, 0401.

RECEIVERS & COMPONENTS

VIEWMASTER Coils, all areas, 17/6 set, incl. choke; Viewmaster Valves, complete set of 12 as specified. £6/2/6; all Viewmaster Trans. and Chokes, list available; Output Trans., std. pentode, 5,000 ohms, 4/6; multi-ratio, p/pull, 6/9; Filament Trans., 6.3v at 1.5 amp 5/6, tapped 2v and 4v 6/6, 6.3v at 3 amp 8/9; Mains Trans., 350-0350, 6v, 5v, 4v, 4v, 80 ma, 21/6; Vol. Contrls., all values, 2/9; SP/switch, 3/9; w/spound, 3 watt, 5K, 25K, 100K, 4/3; Speakers, 3in., 11/-, 3in., 12/6, 5in., 12/6, 6in., 12/6, 8in., 13/6, 10in., 16/6, 12in., 42/6; Extn. Spkr., polished cabinet, with 5in unit and v/ctrl., 24/6; A.C. Mains Amplifier, complete kit of parts, incl. valves, 59/6; undrilled chassis, 6in., 4in., 3in., 2/9; 9in. x 6in. x 1in., 4/3; 12in. x 9in. x 2in., 6/6; Valve Guide, No. 2, 5/-; Metal Rees., RM1 4/3, RM2 4/6, RM3 5/6, RM4 16/6; L/voltage, 12v, 2 amp, 8/9. New list ready. **RADIO UNLIMITED**, Elm Road, London, E.17. (Key. 4813.)

M.C. METERS, 2in. sq., 5ma, 100ma, each 7/-; 2in. rd. 15v, AC, 100ma, 300ma, 150v, DC, 10/6 each; 2in. rd. 1v, AC, 8/6; Neos, 100v, SBC, 2/-; Ignitic Jacks, DPCO, 1/-; Condensers, 15kVw, one each, 750pf and 500pf, 4/-; 12v Relay Actuating toothed bakelite wheel, 3/6; 20k w/w Pots, 3in. dia., 3/6 lk ditto, 5/6. Valves at 2/6; VR54, 7193, HL2, CV6 CV45, VR92, VR66, 9004, 9006, 954, 956; at 4/-; KT44, MH4, VU111, VU120, 6AG5, 9001, VR65, 6SH7, at 5/6; VR91, VR36, VR137, AF13, VR56, VR57, VR53, 6J50, KTW63, H63, 955. Many others. Terms: Cash with order; immediate delivery; s.a.e. for lists and enquiries; post extra. **W. A. BENSON**, 308, Rathbone Rd., Liverpool, 13. (Callers only, Superadio (Wcpil), Ltd., 116, Whitechapel, Liverpool, 1.)

ELECTROLYTICS, capacity, voltage, size, type of mounting; price post paid, in that order: 16 + 32, 450/525, 1 1/2 x 2, clip, 5/-; 24 + 24 + 16, 350/425v, 1 1/2 x 2, clip, 4/9; 60 + 200, 275/350v, 1 1/2 x 4 1/2, clip, 6/6; 150, 1/2 x 1 1/2, clip, 1/1; 450v, 3 x 2, clip, 1/9; 500, 12v, 1 1/2 x 2 1/2, clip, 2/-; 8, 350v, 3 x 2, clip, 1/6; 6,000, 12v, 1 1/2 x 4 1/2, lug, 4/6; 100 + 200, 275/350v, 1 1/2 x 4 1/2, clip, 6/6; 32 + 32, 350/425v, 1 1/2 x 2, clip, 4/9; 8 + 16, 450/525v, 1 x 2, clip, 3/9; 2, 450/525v, 1 x 1 1/2, tag ends, 1/6; 2, 350v, 1 1/2 x 1 1/2, tag ends 1/3; 3,000, 6v, 1 x 3, clip, 3/6; 16, 450v, 1 1/2 x 2, tag ends, 2/9; 1,000, 6v, 1 x 2 1/2, clip, 2/9; 1,000, 275/350v, 1 x 3, clip, 3/6; 32, 450v, 1 1/2 x 2, clip, 3/9. All are All cans; some sleeved; new stock; all voltages WKG, with surge v where marked, Television! Set of 3 Components, comprising line output trans. with E.H.T. winding to give 7kV, using EY51 (heat-treated for EY51 also included) and fitted with video control. Scanning coils, low impedance line and frame, focus coil, optional high (10,000Ω) or low (200Ω). Set of 3, 42/-, plus 2/- postage. Diagram of line trans. supplied. T.V. Control Panels, Paxolin plate, 4 x 3in., carrying 5 slider type res., 3 Welwyn wire wound 10w (1K, 5K, 10K), and 2 carbon, (2 x 50K), complete with knobs for sliders, 6/- each; post paid. Universal Amplifiers, 8 valve, 20w, AC/DC, 200/250v, black and chrome chassis and cover, overall size, 15 x 7 x 7, first-class components, partridge O.P.T. and driver, Gardiner choke, Mu metal input trans., wired and tested, complete with all valves (2 x EF37, 4 x UR3C), and 15Ω output, high/low impedance input, £10/19/6; carr. paid. **RADIO CLEARANCE LIMITED**, 27, Tottenham Court Road, London, W.1. (Telephone: Museum 9188.)

RATES: 5/- per line or part thereof, average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless," Tower House, Southampton St., Strand, London, W.C.2.

VOLUME CONTROLS, Lng. Sp. Meg. 2/6; with S.P. Sw., 3/6; D.P. Sw., 5/6; Liu. Sp. D.P. Sw., 3/6; Preset 2 K, 20 K, 100 K, 1 Meg, 1/6; Wirewound, 25 K, 20 K, 1/9; Preset, 5 K, 25 K, 1/9; Mains Droppers, with Slider, 1,000 ohms, 2 A, 4/9; 750 ohms, 3 A, 4/9; Meters, Moving Iron, 0-15 volts, AC/DC, 2in., 8/6; Moving Coil, 2in., 0-0.5 amp, Thermo-couple, 7/6; Moving Coil, 2in., 0-200 micro-amps, 35/-; Ampilion 10-range Testmeter, moving coil, 1,800 ohms per volt, AC and DC volts, DC current, and ohms range, complete with instructions and test leads, only 25; Crystal Mike Units, 15/6; P.O. Relays, 200 ohm, 9/-; Electrolytics, 3 mfd., 450v, w., 1/11; 32/350, 2/9; 16 x 16/275, 3/-; 16 x 32/275, 3/6; 50/12, 1/3; 16/500 Card. Tub., 3/9. Please add 9d. postage under £2. Mail order only. **MASSEY**, 58, Wakefield Ave., Hull.

RADIO, Television and Test-gear bargains; tested components; no junk; state wants. Box No. 239, c/o **PRACTICAL WIRELESS**.

FREE TO READERS! Send 5d. postage for 4 BA Nut-driver and lists of Radio, Electrical, etc., goods. **ANNAKIN**, 25, Ashfield Place, Otley, Yorks.

RADIO SUPPLY CO. (LEEDS) LTD., 32, The Calls, Leeds, 2. Ex-Gov. Transmitter-Receiver, type TR9, complete with all valves, only 47/6, plus 5/- carr.; Moving Coil Meters, 0-5 amps, 11/9; Selenium Rectifiers, 2/6 v. ja. H.W., 2/11, 6/12v, ja H.W., 3/9; F.W. Bridge Types, 6/12v, 1a, 6/9, 6/12v, 1a, 7/9; 6/12v, 2a, 9/9; 6/12v, 4a, 17/9; 6/12v, 6a, 22/9; H.T. types, 120v, 40 ma, 3/14; 250v, 50 ma, (ex units), 5/9; 250/350v, 100 ma, 7/9; 350v, 50 ma, 6/11. M.E. Speakers, 2-3 ohms, 6in. Rola Field, 700 ohms, 11/9; 10in. R.A. Field, 600, 1,000, or 1,500 ohms, 23/9; Wire Wound Pots, 5, 20, 30 ohms, 1K, 5K, 50K, all with lin. spindles, 1/11 ea. Ex-Gov. C.R.T.s. VCR517C, 35/-, plus 5/- carr.; Ex-Gov. Block Paper Condensers, 4 mfd., 500v, 2/9; 4 mfd., 750v, 3/3, 4 mfd., 1,000v, 3/9; 4 mfd., 2,000v, 5/9; Ex-Gov. Conds., .01 mfd., .02 mfd., 5,000v, .02mfd., 8,000v, 1/9; .1 mfd., 2,500v, 3/6; Ex-Gov. M/T, 230v input, 350-0-350v, 200 ma, 6.3v, 6a, 5v, 3a, 27/9; Pye Co-ax. Plugs and Sockets, 5/9 doz. prs.; Ex-Gov. Accumulators, 2v, 16 A.H., 4/9. All goods guaranteed: c.w.o. or c.o.d. over £1; postage 1/1 under £1; under £3 add 1/9.

TELECOMMUNICATIONS Equipment (Pye) for sale; 1 Headquarters Station (PTC 704), aerial and feeder for same; 1 Mobile Station (PTC 113) and other items; hardly used from new; viewing any time. Please apply to Box 7034, c/o **CHARLES BARKER & SONS, LTD.**, 31, Budge Row, London, E.C.4., or phone Vange (Essex) 3261.

RECTIFIERS, 12v, 1 amp, 6/6; 1 amp, 2/6. List 4d. **CARTERS**, 578, Washwood Heath Rd., B'ham, 8.

TAPE RECORDING

TAPE RECORDING to disc, same day service, by B.B.C. engineers. Details free. **NORTH WALES RECORDING SERVICE**, Brynau Road, Llandudno

RECORDING WIRE, stainless steel, 3,600ft. reels, 5/6; constructional details, 1/6. **W. E. GRIFFITHS**, 12, Rossendale Ave., Blackley, Manchester.

WALNUT Radiogram Cabinets of distinction; stamp details. **R. SHAW**, 69, Fairlop Rd., E.11.

CONSULTANT will advise manufacturers, societies and amateurs on supply, production and design problems. Write in confidence, **BCM/CALN**, London, W.C.1.

WANTED, Tannoy P.A. System or similar, complete, less batteries. **HAMMOND**, 33, Fordington Ave., Winchester.

PANL, the air-drying black crackle, 3/6 from dealers or 4/6 direct. **L. MILLER**, 8, Kenton Park Cres., Kenton, Middx.

VALVES

NEW VALVES WANTED, small or large quantities; all Television Valves and ECL80, EF80, EBC33, FW4/500, VU39, KT61, TP25, PY82, 5Z4, etc., etc.. Prompt cash. **WM. CARVIS**, 103, North Street, Leeds, 7.

6V6G and **GT**, matched in pairs, new, boxed, 17/- per pair; p. and p. 1/-; **R. J. COOPER**, 32, South End, Croydon, Surrey.

OBsolete Radio and Television and Current, over 1,500 different types. **JOHN GILBERT RADIO**, 20, Extension, Shepherds Bush Market, London, W.12. (SHE. 3052.)

VALVES, Valves, Valves, to-day's keenest prices. Stamp for lists. Trade only. **A.W.F. RADIO PRODS.**, Tatler Chambers, Bradford, 1.

ARE YOU STUCK for obsolete or current Valves, Selenium Rectifiers, Meters? If so, write stating requirements, S.A.E. for list to **LAWRENCE**, 134, Cranley Gardens, N.10. (CLI. 6641 or TUD. 1404.)

A.M. FILTER UNITS, No. 90, brand new and unused valves and components, contains 2 6V6G, 5Z4G, 2VR92, other parts and components; internal P.P. for 220/230 50 cy. operation, second, 326-0-326v 65 ma, 5VZ4, 6.3 v, 1.2A (we know cases of running 1132 on this P.P.!), size, 14in. x 9in. x 3in. (no case); ltd. quantity; 35/6 each, post 2/-; less valves 15/6, post 2/-. Hundreds of bargains. Stamp for list. **THE RADIO SERVICES**, Lr. Bullingham, Hereford.

"VIEWMASTER" Valves, exact to specification, guaranteed new and boxed, comprising 5 EF50, 1 6P25, 1 KT61, 1 EBC33, 1 EB91, 2 6K25, 1 6P28, set of 12 £6/2/6, with EF91 7/- extra (post and insurance 2/-). 6AM6, EF91, 6F12, 277, 8D3, 6CA, L77, W77, EF92, 6AM5, EL91, 12AX7, 749; EB91, 6AL5, HVR2A, 6/9; 1.4v miniatures, 155, 1R5, 174, 3V4, 1L4, 3A4, 7/6; 354, 8/6; 6V6G, 6V6GT, 6F6G, KT63, Y63, 1C5GT, 1D35, EF39, EBC33, EF50, 20D1, 7B7, 7C5, 7H7, 7S7, 7/6; 5Z4G, 5U4G, 5Y3G, MU14, 7Y4, 7C6, U22, U78, DH77, 6AT6, 12AT7, ECC81, 6X4, 6BA6, 6BE6, 6BW6, 6J6, EC91, Pen46, PY82, 6LD20, 6X5GT, 8/6; EL38, PL38, 22/6; PZ30, GZ32, 6U4GT, 17/6; 6P25, N78, 15/-; U08, U25, 13/6; U16, EAC91, ECC91, 6AT, UBF80, PL83, 6F1, 6F14, 12/-; PL81, PL82, PY81, ECH42, UCH42, UL41, X65, 10F9, 10LD11, 10C1, 10C2, 11/-; ECL80, EF80, EY51, PY80, 6F15, 6C9, 10F1, 10P13, CY31, 43, KT33C, 6K8GT, 12K8GT, EAF42, R10, 10/6; 25Z25, 25Z26GT, EBC41, UBC41, UF41, 10/-; 6SN7GT, 6Q7GT, 12Q7GT, 12K7GT, 25Z4G, 25A6G, EF41, 9/6; 6K8G, U50, 5Y3GT, 25L6GT, 35L6GT, 50L6GT, 35Z4GT, 80, UU9, 4704, UY41, EZ40, 9/-; 6K7G, 6K8GT, EF8, 6/-; All new and boxed. Postage ad. per valve extra. **READERS RADIO**, 24, Colberg Place, Stamford Hill, London, N.16. (STA. 4587.)

ASTRAL RADIO PRODUCTS

SPECIAL OFFER.—Midget L.F.T.s, 465 Reels, 13 1/2 in. square x 1 1/2 in. high. BRAND NEW 6" pr.; High "Q" postage 6d.
F.R.F. Coils as used in original model, 3-band. All Dry 3 (April '53, P.W.), 6/6 pr., postage 6d.
Dual Wave H.F. Coil as used in original models. Summer All Dry Portable. Model 1 and 2 Valve, etc., 4/3 each, postage 6d.; or with 5 circuits, 5/-.
Osmor QC1 Choke, 4/-, postage 3d.
"K" Type Coils, A.E. and H.F., as used in original Model A.C. Bandpass, 3/3 per coil; and S.W. Band also available, postage 6d.
M.W. Frame Aerial, unsupported winding, 3/6 each.
M.W. Frame Aerial, Litz wound, high gain on Faxolin, 5/- each.
L. and M.W. Xtal Set Coil, 2/6 each.
Midget 50 pF. Trimmers, ceramic, 6d. each.
 All goods brand new and guaranteed. Trade enquiries invited.

138 THE RIDGEWAY, WOODINGDEAN, BRIGHTON, 7.

NEW GOODS ONLY

T-Tubular, Wire-Ends, C-Can, Tag Ends, CONDENSERS—Electric, 450 v. wkg., T. 1 mid., 2/6; T. 4, 3/-; T. 8, 2/6; T. 16, 4/-; C. 32, 5/10; C. 8-4, 4/6; C. 8-16, 5/6; C. 16-16, 6/-; 500 v. wkg., T. 2, 2/4; T. 4, 2/8; T. 8, 3/-; C. 16, 4/8; C. 32, 6/9; C. 8-8, 6/-; C. 8-16, 6/8; C. 16-16, 7/4; T. 25X25 v., 1/9; T. 25X50 v., 2/-; T. 50X50 v., 2/6; T. 50X12 v., 1/9; T. 100X50 v., 3/9; C. 100X350 v., 9/-
TUB. PAPER—500 v., wkg. up to .0005, 7d.; to .006, 8d.; to .04, 10d.; .05, 1.1; .2, .25, 1.4; .5, 2/-; 1, 2/8; S.B. Mica, 500 v. wkg., up to 100 pf., 8d.; to 500, 11/4; to 1,000, 1/-; 2,000, 3/00, 1.1

VOL. CONTROLS—L.P. Spdls. all values, 2/9; with Sw., 4/9; with DP. Sw., 5/6.
RESISTORS—Carb. all std. values, 20 per cent. tol.; watt. 4d.; 1 w., 5d.; 1 w., 7d.; 2 w., 1/-; Wirewound, 1 w., up to 5 k., 1/9; 5 w., to 5 k., 2/-; to 50 k., 2/6; 10 w., to 10 k., 2/8.
 Terms: Orders up to 10/- post. 6d., up to £1, post. 9d., over post free. Cash with order

RADIOELECTRON,

22, Frances Street, Scunthorpe, Lincs.

NEW M.C.R.I. 3in. Speaker, fitted, £12/10/-, 32, Belmont St., Newcastle-on-Tyne, 6.

SELL US your discarded 12in. Television Tube for 15/-, with Heater intact; weekly collections. Middlesex, Essex and Herts. Box No. 240, c/o PRACTICAL WIRELESS.

GOLD SPRAYED, expanded metal Speaker, fret 12in. x 12in. 4/6, 12in. x 9in. 3/6, 8in. x 6in. 1/6; add 1/- towards cost of postage and packing. SHARP'S (RADIO), 252, Chapel St., Salford, 3.

EDUCATIONAL

THE WIRELESS SCHOOL—Training in Wireless Telegraphy. RADIO HOUSE, Manor Gdns., N.7.

THE INSTITUTE of Practical Radio Engineers Home Study Courses are suitable for coming text for I.P.R.E. and other qualifying examinations. Fees are moderate. Syllabus of seven modern courses post free from SECRETARY, I.P.R.E., 20, Fairfield Road, London, N.8.

WORLD TRAVEL and adventure in the Merchant Navy. Young Men 15 years upwards, required for training in: Marine Wireless and Direction-finding at sea. (Trainees in forthcoming Registration Groups are eligible for Deferment of Military call-up.) Immediate sea-going positions on completion of training. Suitable candidates will be entered as Officers and must be prepared to sail to all parts of the world. Courses: Full or Part-time, also by Correspondence. Recognized by Ministry of Education. Scholarships available. Boarding and modern canteen facilities; low training fees. Send 1/- P.O. (stating age and height, etc.) for complete prospectus to: OVERSEAS HOUSE (Dept. 14), Brooks' Bar, Manchester, 16. (Tel.: MOSS-Side 2047.)

SITUATIONS VACANT

The engagement of persons answering these advertisements must be made through a local Office of the Ministry of Labour or a Scheduled Employment Agency if the applicant is a man aged 16-64, inclusive, or a woman aged 18-59, inclusive, unless he or she, or the employment, is exempted from the provisions of the Notification of Vacancies Order, 1952.

WIRELESS STATION SUPER-INTENDENT required by the Nigeria Government Posts and Telegraphs Department for one four of 18 to 24 months in the first instance. Commencing salary according to experience in scale, £264, rising to £1,392 a year. Gratuity £100/£150 a year; outfit allowance £60; free passages for officer and wife and assistance towards cost of children's passages or their maintenance in the U.K. Liberal leave on full salary. Candidates must have had wide practical experience of modern radio techniques and equipment, in particular V.H.F. multi-channel equipment. Write to the CROWN AGENTS, 4, Millbank, London, S.W.1. State age, name in block letters, full qualifications and experience and quote M2C/28927/PU.

MORSE CODE Training

Send for the Candler

BOOK OF FACTS

It gives details of all Courses which include Special one for securing Amateur Licence. CANDLER SYSTEM CO. Dept. 5L0 52b, Abingdon Road, London, W.8. Candler System Co., Denver, Colorado, U.S.A.

STAN WILLETTS

43, SPON LANE, WEST BROMWICH, STAFFS.
 Tel.: WES 2392

TRANS-RECEIVER No. 18.—New condition, complete with all valves, leased phones and mike. £6 10/-, post 7/6.

VALVES—Brand New Guaranteed.—X18, 6/6; N18, 6/6; 3D8, 2/3; 954, 1/6; XC34, 1/9; RKK4, 1/9; S04, 7/6; 6V6GT, 7/6; 6V6GT, 7/6; 8D3, 6/6; EC52, 4/9; 6K7G, 5/9; 6J7G, 5/9; KT2, 4/6; EA50, 1/9; R10, 7/6; 5F61, 3/6; 956, 2/-, Post 6d. .05 kV., 1.9 each, post 4d.; 8 mid. 450v., new, 1/6, 16 - doz.; 4 x 4 x 4, 350v., new, 1/6, 15 - doz.; 8 x 8, 500v., new, 2/6, 25 - doz.
GERMANIUM CRYSTAL DIODES—G.E.C. wire end, new, 2/- each, 18 - doz.
OUTPUT TRANSFORMERS—32-1, 55-1, 86-1, 60 mA., new, 3/6, post 9d.
5 THERMO COUPLE AMP METER—New, boxed, 5 11/-, post 6d.

11/- MIDGET COIL PACK KIT 11/-

Comprising chassis 3' x 2' x 11", switch, LMS iron cored coils, padders, trimmers, nuts and bolts, wire, sleeving, circuit diagram, 45Kc Brand new Int. Oct. Valveholders, 21d., 2/- doz.; Ali Can Electrolytics, 8 x 500, 1.3, 1/2 - doz.; 2 to 350 8d., 6/- doz.; 200 x 12 6d., 4/6 doz.; 100 x 8 3d., 2 - doz.; Coils, Coils, "P" Type 2, "Q" Type 2, 3, TRF 4, pr.; MSS Superhet 6 coils with circuit, 4/- set; HF Dual-wave 2.9, Crystal Coil L & M 2/-; Tub Cond. 1 x 500 3 - doz., 1 x 350 2.9 doz.; Asst. Grommets 6d., doz.; 2, 4 & 6 BA Nuts 2 - gr.; Brand new BA Nuts & bolts asst. 2 gr. 5/-; Ex-equip. BA nuts, bolts, washers 2 6lb. (approx. 500 pieces); PK self taps screws 2 6 gr.; 18 SWG Multicoiler 2 6 doz yds.; 1 m m sleeving 1 - doz yds.; 1 meg. vol. con. with DF sw. 1/-
2 WA SUPERHET & TRF RECEIVERS Superhet £6-10/-, TRF £5-5/- including all components, valves, cabinet, the lot. Book of instructions 1/6 post free.
 Latest list 3d. Min. P. & P. 1/-.

SUSSEX ELECTRONICS, PRINCES ST., BRIGHTON.

EVERYTHING FOR VIEWMASTER & SOUNDMASTER

ELECTROLYTICS—450v. wkg. (Std. New Stock), 4 mid. 1/6, 8 mid. 2/-, 16 mid. 3/-, 8-8 mid. 3/6, 8-16 mid. 4/-, 16-16 mid. 4/6. **P.M. LOUD-SPEAKERS** (3-ohms), 3in. 13/6, 5in. 14/6, 6in. 15/6, 8in. 18/6, 10in. 22/6.
GERMANIUM CRYSTAL DIODES 3/6, B.I.C., 0.1 mid. 3 kv. TV Condens. 10.6. **I.L.R. HEADPHONES**, 18.6. **SOLON Miniature SOLDERING IRONS**, 19.6. **5in. ENLARGERS** (for V837), 17.6. 10 h., 50 mA. **SMOOTHING CHOKES**, 5.6. 9in. Old Aspect **CREAM RUBBER MASKS**, 5.6. **WEARITE "P" COILS**, 3/-, ALL CLASSIS, 2in. deep, 6in. x 4in. 4/6, 8in. x 6in. 6/-, 10in. x 7in. 7/-, 12in. x 8in. 9/-, 14in. x 8in. 13/-, 16in. x 9in. 14/-, **E.L.A.C. F20 RINGS**, R17/MK. II 28/6. **R20 MK. II 30/-**, R25/MK. II 32/6. **TRANSFORMERS** (Mains input, Standard Primaries), 250-0-250v., 60 mA. 0-4-8.3v. 4 A., 0-4-5v. 2 A., 19/6; Ditto but 350-0-350v., 19/6; 250-0-250v. 100 mA., 6.3v. 3.5 A., by 2 A., 26/6; Ditto but 350-0-350v. 26/6.
MAINS TRANSFORMERS FOR PRE-AMPLIFIERS, TEST-GEAR, etc. PRIMARY, 230 240v. SECONDARIES, 0-250v. 30 mA. (for 250v. from a half-wave rectifier), 26/6. 6.3v. 1 A. Price new and guaranteed, 14/9.

ORDERS UNDER £1 please add 1/- P.&P. Orders £1 and over please add 1/9. FOR INSTANT SERVICE—WRITE:

CITY & SURAL RADIO
 101, HIGH ST., SWANSEA, GLAM.
 Telephone: Swansea 4677.

FIRST-CLASS RADIO COURSES . . . GET A CERTIFICATE!
QUALIFY AT HOME—IN SPARE TIME
 After brief, intensely interesting study undertaken at home in your spare time—YOU can secure your professional qualification. Prepare for YOUR share in the post-war boom in Radio. Let us show you how!

FREE GUIDE
 The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success-compelling qualifications as **A.M.Brit.I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs, Exams., Gen. Cert. of Educ., London B.Sc. (Eng.), A.M.I.P.E., A.M.I.Mech.E., Draughtsmanship** (all branches), etc., together with particulars of our remarkable Guarantee of Success.

SUCCESS OR NO FEE
 Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER 150,000 SUCCESSSES

NATIONAL INSTITUTE OF ENGINEERING
 (Dept. 461), 148, HOLBORN, LONDON, E.C.1

LEWIS

RADIO COMPANY

for

Cabinets

Send for our catalogue of R/G, T/V, Table, Speaker and Corner Cabinets.

Components

Send for our FREE 40 pp. catalogue of T/V and Radio components.

Chassis

Leaflet available on our 5V 3 W/B Superhet Radiogram Chassis.

Amplifiers

Send for details of our domestic type Amplifiers. 5 and 4½ watt.

Tape

Recorders

Full details of our new tape recorders available. Also heads, tape and mikes.

120, GREEN LANES,

PALMERS GREEN, LONDON, N.13

BOWes Park 6064

MICROGRAM AMPLIFIERS



£3.19.6 P. & P. 2/6d.

Fits inside your record player leaving room for speaker. Dimensions 10in. x 3½in. x 2½in. 4 watts quality output. Suitable for all speakers and with standard or L.P. pick-ups. Built-in power pack for 200-250 v. A.C. only. Valves 6J7 and 6V6 available at 20/- per pair extra, if required. Other models with neg. feedback, etc.

6d. stamp for illustrated details.

ELECTRO-ACOUSTIC LABS

TAIN-ROSS-SHIRE, SCOTLAND


RADIO UNLIMITED

"DEFESCO" AUDIO AMPLIFIER. Model AC2. Complete Kit of Parts incl. Valves for 3-stage A.C. mains amplifier. All components are of branded manufacture, not Ex-Govt. In Kit form. 59/6. Wired and tested. 75/- Matched Loudspeaker, 13/6.

COLLARIOR RC521.—A.C. Mains. 3-Speed Autochange Radiogram Unit. (Complete with Two Crystal Heads.) Tar paid £9.19.6 Post paid.

New Piezo-Electric Microphone. housed in Chromium plated Ball-type case, and with slide-action telescopic stand, with heavy base. 31 yds. 3-core screened cable supplied. £6.13.6 complete. Post paid.

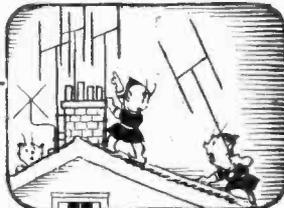New Boxed Valves. 1T4, 1S5, 1R5, 3S4, 6V6, 6J7, EF39, EF36, EBC33, EF50, EL32, 6BB, 7S7, 7B7, 7C6, 7Y4, 711 each. 6K8, 6Q7, KT33c, 12K7, 12K8, 12Q7, 35L6, 25L6, 35Z4, 5Z4, 5U4, U50, U14, 9.3 each. EF91, 7/6. EF91, 6/6. EL38, 15/-. KT66, 11/-, 6L6, 9/6. ARF12, 3/6. ELM ROAD, LONDON. E.17. (Key 4813)



The "Fluxite Quins" at Work
"What's the matter? You're nothing but moans
Get along and don't make any bones
Thanks to good old FLUXITE
We're doing all right
Have you room there for old Mrs. Jones'?"

See that FLUXITE SOLDERING PASTE is always by you—in the house—garage—workshop—wherever speedy soldering is needed. Used for over 40 years in Government works and by leading engineers and manufacturers. Of all ironmongers—in tins, from 1/- upwards.

FLUXITE

SOLDERING PASTE

A Staunch Companion to Fluxite Soldering Fluid.

SIMPLIFIES ALL SOLDERING

Write for Book on the Art of "SOFT" Soldering and for leaflets on CASE-HARDENING STEEL and TEMPERING TOOLS with FLUXITE.

FLUXITE LTD.

Bernonsey Street, London, S.E.1.

SEND

for the
"HOME CONSTRUCTOR"
Incorporating Circuit and FULL CONSTRUCTIONAL DETAILS

for Building Any or All of these FIRST-CLASS SUPERHETS:

- 3-Valve Feeder Unit (a) 2 Waveband (b) 3 Waveband
- 4-Valve Feeder Unit (3 Waveband with R.F. Stage).
- 5-Valve 2 W/Band Receiver (a) For A.C. Mains (b) For A.C./D.C. Mains.
- 5-Valve 3 W/Band Receiver (a) For A.C. Mains (b) For A.C./D.C. Mains.
- 6-Valve 3 W/Band Receiver (a) For A.C. Mains (b) For A.C./D.C. Mains.

Other Contents include:

How to Build an Efficient Crystal Set.

How to Make a 2 W/Band/Gram Coil Pack.

Circuits of Two Different TRF Receivers, and a 10 watt Quality Amplifier.

Detailed Instructions on Soldering; Simple Metalworking for Radio; General Constructional and Servicing Notes; Resistance Colour Code and How to Use It. Our fully illustrated Catalogue of High Class Components is included.

This is a Booklet no radio enthusiast need be without for the price is

ONLY 2/6 ONLY

SUPACOILS, 21, Markhouse Road, London, E.17.

VALVES

All Valves Guaranteed. 24 Hours Service.

2X2	4/6	42SPT	6/-	EF39	6/6
6X5	7/6	35Z4	9/6	6SN7	9/6
954	2/-	35L6	9/6	6L6	10/6
6A50	2/-	2X2	4/6	50L6	8/6
SP41	3/6	425PT	6/6	5U4G	8/6
SP61	3/6	LP2	4/6	807	8/6
MSPEN	5/-	KT24	4/6	ECL80	11/6
VR137	4/-	HP4101	5/6	EF80	11/6
6K7	5/6	DDL4	5/6	12K9	9/6
EF50 (Syl.)	7/-	IT4	8/-	12K7	9/6
VR116	4/6	IR5	8/-	KT33C	10/6
5Z4	4/6	354	3/-	EF91	9/-
VU39	8/6	1S5	8/-	41MTL	6/-
6Q7	9/-	6V6	8/-	MH4	5/-
Y63	8/6	6K3	9/6	12Q7	9/6

* Voltage Regulator Panel. 3d.

* G.E.C. crystal diodes, 2/-.

* Pvc plug and sockets, 6d. pair.

* Chokes, 10 henry 150 m.a., 5/6, plus 6d. post.

* Co-axial Cable, 80 ohm per ft., 8d. yd. (not W.D.).

* Twin Transparent Flex, 18/6 per 100 yds.

* RM1, 3/11; RM2 S.T.C., 4/6; RM4, 15/-.

* Gran V/C, W/S, 1 meg.-1 meg., 4/-.

* Amplion V/C, L/S, 1 meg., 2/-.

* SPEAKERS.—3in. Roja, 13/6; 3½in. Elac, 11/6; 5in. Elac, 12/6; 6in. Plessey, 12/6; 6in. Plessey, 13/6. Post 9d. per speaker.

* Standard Twin Gang Cond., .0005 5/6.

* Condenser Panel, 22 ½ watt resistors. 3 Westectors, 18 condensers, 4/9.

* Filament Transformers, 6.3 and 1.5 amps., 6/9. Post 6d.

* Toggle Switches, bakelite, S.P., 8d.

* Covert W.W. Pots., 1K, 2K, 2/-.

* Midget I.F., 465 kc/s, 8/6 per pair.


REX RADIO,

37, LOUIS STREET, LEEDS, 7.

Mail Order only

Catalogue 6d.

Servio presents The "Bristow"

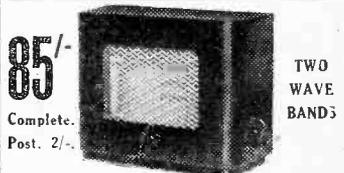

85/-

TWO WAVE BANDS

Complete.

Post. 2/-.

THE IDEAL RADIO KIT

A 3-Stage, 2-wave All-Dry Battery Set. Full Volume on a 5in. P.M. speaker, with one internal battery. Everything supplied including Polished wooden cabinet. Assembled with soldering iron, pliers and screwdriver. A Radio the size of an extension speaker. NO Trimming; wire up and switch on. Plans Separately. 2/-, Refunded with Kit.

SERVIO RADIO, 156/8 Merton Rd. Wimbledon, S.W.19. LIBerty 6525

G. L. ELECTRONICS

AMPLIFIERS.—A.C. 3 v. 4 w. 85.
T.A.P.—Rec. play amp. 4 w. 12 gns.
TAPE.—45 Push Pull 10 w., 18 gns. Tape head lams play or erase 1 track head set, 5/-; clamps, 7/6.
CHARGER.—Transformer, and rectifiers. 6.12 v. 2 a., 27/6; 6.12 v. 4 a., 37/6. Eliminator 120 v. 60 ma., 17/6. Grey steel cases above 7/6.
TRANSFORMERS.—Pri 200 230/250 v., 300-0-300 v. 60 ma., 5 v., and 6 v., 17/6. 350-0-350 v. 100 ma and 6 v., 22/6.
OUTPUT TRANSFORMERS.—3-8 15 ohm 6 k, 8 k, 10 k (state which). P. P. 15 watts, 15/-; 25 watt, 21/-.
CHOKES.—200 ma., 8 hry., 200 ohms, 10/6. Send S.A.E. for full lists.

16, PATTISON ROAD, LONDON, S.E.18.

(Woolwich 0387)

Practical Wireless BLUEPRINT SERVICE

PRACTICAL WIRELESS

	<i>No. of Blueprint</i>
CRYSTAL SETS	
1/6d. each	
1937 Crystal Receiver ...	PW71*
The "Junior" Crystal Set	PW94*
2s. each	
Dual - Wave "Crystal Diode"	PW95*

STRAIGHT SETS

Battery Operated	
One-valve : 2s. each.	
The "Pyramid" One-valver (HF Pen) ...	PW93*
The Modern One-valver	PW96*
Two-valve : 2s. each.	
The Signet Two (D & LF)	PW76*
3s. each.	
Modern Two-valver (two band receiver) ...	PW98*
Three-valve : 2s. each.	
Summit Three (HF Pen, D, Pen)	PW37*
The "Rapide" Straight 3 (D, 2 LF (RC & Trans))	PW82*
F. J. Camm's "Sprite" Three (HF, Pen, D, Tct)	PW87*
3s. each.	
The All-dry Three ...	PW97*
Four-valve : 2s. each.	
Fury Four Super (SG, SG, D, Pen)	PW34C*
Mains Operated	
Two-valve : 2s. each.	
Selectone A.C. Radiogram Two (D, Pow) ...	PW19*
Three-valve : 3s. 6d. each.	
A.C. Band-Pass 3 ...	PW99*
Four-valve : 2s. each.	
A.C. Fury Four (SG, SG, D, Pen)	PW20*
A.C. Hall-Mark (HF Pen, D, Push Pull) ...	PW45*

SUPERHETS

Battery Sets : 2s. each.	
F. J. Camm's 2-valve Superhet	PW52*
Mains Operated : 3s. 6d. each.	
"Coronet" A.C.4 ...	PW100*

SHORT-WAVE SETS

Battery Operated	
One-valve : 2s. each.	
Simple S.W. One-valver	PW88*
Two-valve : 2s. each.	
Midget Short-wave Two (D, Pen)	PW38A*
Three-valve : 2s. each.	
Experimenter's Short-wave Three (SG, D, Pow)	PW30A*
The Perfect 3 (D, 2 LF (RC and Trans)) ...	PW63*
The Band-spread S.W. Three (HF Pen, D (Pen), Pen)	
	PW68*

PORTABLES

1s. 6d.	
The "Mini-Four" All-dry (4 valve superhet)	PW

MISCELLANEOUS

2s. each.	
S.W. Converter-Adapter (1 valve)	PW48A*
(2 sheets), 7s. 6d.	
The P.W. 3-speed Autogram.	
The P.W. Electronic Organ (2 sheets), 7s. 6d.	

TELEVISION

The Practical Television Receiver, (3 sheets), 10/6	
The "Argus" (6in. C.R. Tube), 2/6	

AMATEUR WIRELESS AND WIRELESS MAGAZINE STRAIGHT SETS

Battery Operated	
One-valve : 2s.	
B.B.C. Special One-valver	AW387*
Two-valve : 2s. each.	
A modern Two-valver ...	WM409*
Mains Operated	
Two-valve : 2s. each.	
Consoelectric Two (D, Pen), A.C.	AW403

SPECIAL NOTE

THESE blueprints are drawn full size. The issues containing descriptions of these sets are now out of print, but an asterisk beside the blueprint number denotes that constructional details are available, free with the blueprint.

The index letters which precede the Blueprint Number indicate the periodical in which the description appears. Thus P.W. refers to PRACTICAL WIRELESS, A.W. to *Amateur Wireless*, W. M. to *Wireless Magazine*.

Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to PRACTICAL WIRELESS Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

*No. of
Blueprint*

SHORT-WAVE SETS

Battery Operated	
One-valve : 2s. each.	
S.W. One-valver for America	AW429*
Two-valve : 2s. each.	
Ultra-short Battery Two (SG, det Pen)	WM402*
Four-valve : 3s. each.	
A.W. Short Wave World-beater (HF Pen, D, RC, Trans)	AW436*
Standard Four - valver Short-waver (SG, D, LF, P)	
	WM383*
Mains Operated	
Four-valve : 3s.	
Standard Four-valve A.C. Short-waver (SG, D, RC, Trans)	WM391*

MISCELLANEOUS

Enthusiast's Power Amplifier (10 Watts) (3/-)	WM387*
Listener's 5-watt A.C. Amplifier (3/-) ...	WM392*
De Luxe Concert A.C. Electrogram (2/-) ...	WM403*

QUERY COUPON

This coupon is available until Dec. 7th, 1953, and must accompany all Queries, sent in accord with the notice on page 774.

PRACTICAL WIRELESS, Dec., 1953.

BE PREPARED

for a cold winter by making our low cost Electric Blanket. 27 yards of special heater wire and blueprint, 20s. Blueprint only 1/6.

**CONNECTING WIRE SNIP**

P.V.C. insulated 23 s.w.g. copper wire in 100ft. coils, 2/9 each. Colours available: Black, Brown, Red, Orange, Pink, Yellow, White, Transparent. 4 coils for 10/-.

**LAST FEW
£3 19 6**

The Lectross warms room as it dries clothes. Size 3 1/2 ft. wide, 3ft. high and 5in. deep. It has four stove-

enamelled rails and works on A.C. or D.C. mains, consuming 650 watts. Fully guaranteed. Price £3.19.6. plus 7/6 carriage.


SOMWEAVE

This really lovely loud-speaker fabric we offer at approximately a third of today's cost. It is 12in. wide and our price is 12/- per yard or panels 12in. x 12in., 1/9 each.

This is also very suitable for covering plain wooden cases, for portable radio amplifiers, etc.

MULTI-SPEED MOTOR


Works off A.C. or D.C. mains fitted with gear box any speed from 1 r.p.m. 12/6. post and pkg., 1/6.

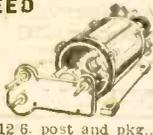**22% FLUORESCENT LIGHTING**

Complete kit comprises Hi-craft 40 watts control unit, starter lamp, lamp holders, clips and wiring diagram. Price less tube 22/6 plus 1/6 post. With tube 30/-, carriage and insurance 3/6. Tubes 7/6 each, carriage free, minimum quantity 5.

PLUGS FOR MODERN VALVE HOLDERS

Each is fitted with a rubber shroud. For BTG button base and type 2 for 8BA. Price 1/4 each, discounts for quantities.

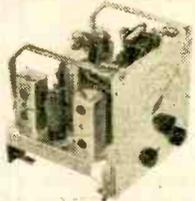BARGAINS OF THE MONTH**SUPERHET RADIO
by BEETHOVEN**


Extremely well built on chassis, size approx. 9 1/2 x 7 1/2 x 8 1/2, using only first-class components, fully aligned and tested—110-240 volt A.C. mains operation. Large clear edge-lit dial. Three wave bands covering 201-550, 35-129, 19-42 metres. Complete with five Mullard valves, frequency changer, double diode triode, pentode output and full wave rectifier. Complete with Rola loud speaker ready to operate. Special cash with order price this month, £7.17.6 carriage and insurance 7/6. Hire purchase terms, £3 deposit, balance over 12 months.

MULTI-METER KIT

The Multi-meter illustrated measures D.C. volts, D.C. M-Amps and ohms. It has a sensitivity of 200 ohms per volt and is equally suitable for the keen experimenter, service engineer or student. All the essential parts including 2in. moving coil meter, selected resistors, wire for shunts, 8 point range selector, calibrated scale, stick on range indicator and full instructions for making are available as a kit price 15/-, plus 9d. post and packing.

**HUGE NEW PURCHASE**


We have purchased another large quantity of the Collaro Auto record changer type R.C. 9521, three-speed suitable for all types of records and with the latest type crystal pick-ups. Buy one this month as you will not be able to again at this special price of £10.0.0. plus 7/6 carriage and insurance.

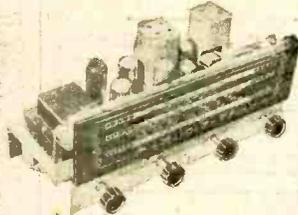THE "WINDSOR"

This is a 5 valve A.C. superhet, covering the usual long, medium and short wavebands. It has a particularly fine clear dial with an extra long pointer travel. The latest type local valves are used and the chassis is complete and ready to operate. 8in. speaker. Carriage and insurance 10/-, H.P. terms £3.7.0 deposit. Table model cabinet to suit—37/6 plus 3/6 postage and insurance.

TABLE RADIO CABINET

Due to a special purchase, we are able to offer this very fine cabinet, size approx. 16 x 16 x 7—walnut veneered and satin finished. Complete with 3 colour, 8 waveband glass scale at only 37/6, carriage and packing 3/6. We also have a limited quantity of the complete chassis to fit these cabinets, specifications 5 local valves, standard long—medium and short wavebands—A.V.C. 8in. speaker, A.C. mains operation. Price £9.19.6. plus 10/- carriage and insurance. H.P. terms £3.7.0 deposit, or with cabinet £4.0.0.

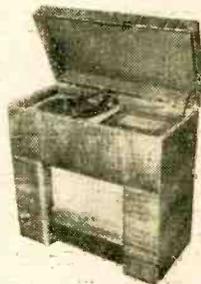
**AUTO-RADIOGRAM****29** GNS.

RADIOGRAM CABINET, Console Type Cabinet. With full grained walnut finish, will take standard type auto change gram unit. Price, £11.10.0. H.P. terms, £3.17.0 deposit, and 12 monthly payments of 16/9, plus 15/- carriage. **Radio Chassis to suit.** £8.19.6. H.P. terms, £3 deposit and 10 monthly payments of 13/-, plus 7/6 carriage.

Auto Change Units. For long-playing and standard records with suitable pick-up head, £11.11.0. **SPECIAL OFFER.** Cabinet Radio Chassis and Auto Changer, 29 gns. H.P. terms, £10.14.0 deposit and 12 monthly payments of £2.3.0.

**THE
"SUPERIOR" 15in.
BIG PICTURE**

Up to the minute TV
for only £37-10-0.

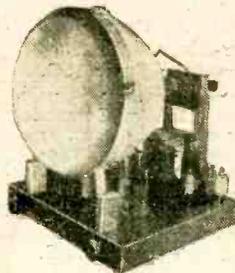

A 20 valve television for the amateur constructor, all components, valves and 15in. Cossor Cathode Ray Tube costs £37.10.0. plus £1 carriage and insurance or £12.10.0 deposit and 12 monthly payments of £2.11.6. Constructor's envelope giving full details and blueprint, 7/6. Returnable within 14 days if you think you cannot make the set.

**ELECTRONIC PRECISION EQUIPMENT**

42-46 WINDMILL HILL
RUISLIP MIDDLESEX ● 152-3, FLEET ST.
LONDON E.C.4.

Dept. 7.

also 29, STROUD GREEN ROAD, FINSBURY PARK.