

MAKING A 4-VALVE MIDGET PORTABLE

PRACTICAL ¹³

AUGUST
1957

EDITOR: F.J. CAMM

WIRELESS



CONTENTS

BUILDING AN AMATEUR
COMMUNICATIONS RECEIVER

AN OUTPUT INDICATOR

POINTERS ON BEAMS


A MAINS T.R.F. SHORT-WAVE
RADIO AND AUTOMATION

**CONDENSER LEADERSHIP
SINCE 1906**



**CONDENSERS &
PRINTED CIRCUITS**

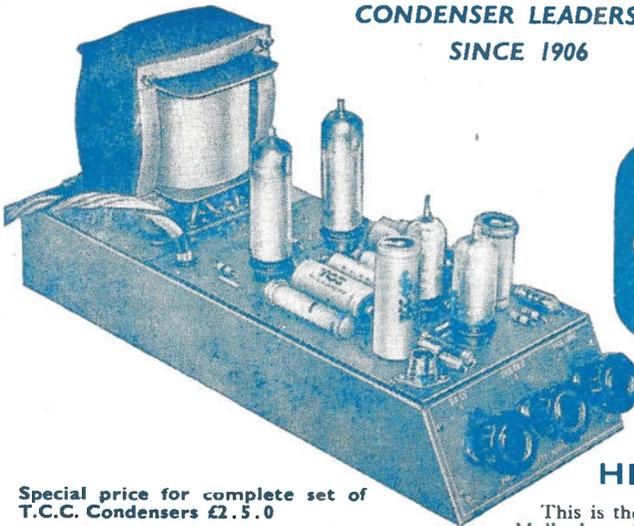**for the
MULLARD 510
HIGH QUALITY AMPLIFIER**



Special price for complete set of
T.C.C. Condensers £2.5.0
Printed Circuit complete with Control
Panel (approved by Mullard)
£1.2.6

Available from
leading dealers



This is the T.C.C. Printed Circuit version of the famous Mullard 510 Amplifier which, with the complete set of T.C.C. Condensers, has been specially developed for the home constructor. The simplicity of the construction renders it trouble-free, whilst its performance and appearance are enhanced. T.C.C. Condensers are used in the majority of Radio and T.V. receivers, and more and more designers are now specifying T.C.C. Printed Circuits.

THE TELEGRAPH CONDENSER CO. LTD

RADIO DIVISION NORTH ACTON · LONDON · W.3 Tel: ACORN 0061

**HIGH FIDELITY
AT REALISTIC
COST!**


H.F. 1012. 10" Hi-Fi Unit
£4. 19. 9 ▶

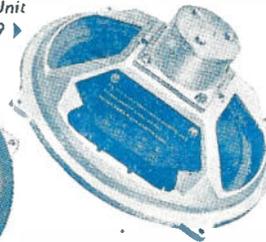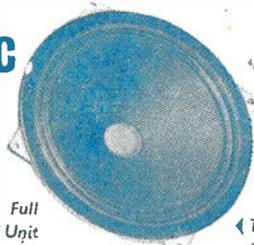

Tweeter Units
£4. 4. 0 & £12. 12. 0

See and hear these
and all other W.B. lines
at our London Office
(109 Kingsway, W.C.2)
any Saturday between
9 a.m. and 12 noon.

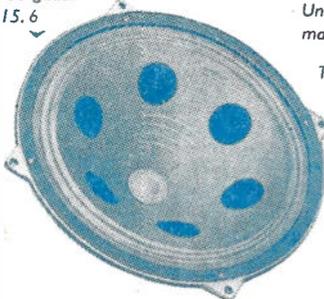H.F. 1214. Full
Range 12" Unit
14,000 gauss
£9. 15. 6



▶ T.816. Special 8" Mid-
Range and High Frequency
Unit. 16,000 gauss
magnet. £6. 10. 0

The New W.B.12
High Fidelity
Amplifier
Price £25



Ready to assemble
Cabinets from
£5. 10. 0

TV and Record Storage
Cabinets
£9. 14. 3 & £10. 4. 9



Details of all the outstanding W.B. products on request



WHITELEY ELECTRICAL RADIO CO. LTD · MANSFIELD · NOTTS



FOR VALVES GUARANTEED ALL TESTED BEFORE DISPATCH

Table listing various vacuum tube types and their specifications, including 6Z4, 6X4, 6X5, 6X6, 6X8, 6X9, 6Y4, 6Z5, 6Z6, 6Z7, 6Z99, 6Z100.

TRANSISTORS Suitable for audio work, yellow and green spot, 10.- each; red spot, 10.- each. 12.- for use up to 1.5 mc/s., blue spot, 15.- each. 17.- for use up to 1.5 mc/s., 8 mc/s., yellow and red spot, 21.- each.

JB gang condensers for transistor working. "0" gang, 1 or 2 gang, 365 PF swing, aluminium vanes, steel chassis. 1 gang, 7.6 each, 2 gang, 11.0 each, JB "00" twin gang condenser, 200 PF front section, 176 PF rear section, Price 9.6 each.

TELETRON transistor superhet coils. Set of IF and oscillator coils with ferrite rod 90 per cent (circuit included). Long wave loading coil to match, 4.6 each.

REPANCO OT1 Combined 1st IF and ONK coil, 11.8. T2 2nd IF Transformer (315 Kc/s), 6.-. Ferrite rod IF Transformer (315 Kc/s), 5.-. T4 Push Pull interstage transformer, 8.6. T5 Push Pull output transformer, 8.6. Circuits included with all types.

BSR MONARCH 4 speed automatic record changer unit plays 7in., 10in. and 12in. records automatically. 5 x 1 1/2 "MAGNATONE" selector, "Unit plate 12 1/2in. x 10 1/2in. 28.15.0 each, carriage 7.0.

Line Cord, 3 amp, 3 core, 12 ft yard. Line Cord, 2 amp, 3 core, 12 ft yard. Electric Buzzers in Bakelite Case, loud tone, 2.5 ea. Epicyclic Friction Drive with Brass Drum. For use with steel Dial Drive W. 12. ea.

Table listing various electronic components and their prices, including CMC42, CMC43, CMC44, CMC45, CMC46, CMC47, CMC48, CMC49, CMC50, CMC51, CMC52, CMC53, CMC54, CMC55, CMC56, CMC57, CMC58, CMC59, CMC60, CMC61, CMC62, CMC63, CMC64, CMC65, CMC66, CMC67, CMC68, CMC69, CMC70, CMC71, CMC72, CMC73, CMC74, CMC75, CMC76, CMC77, CMC78, CMC79, CMC80, CMC81, CMC82, CMC83, CMC84, CMC85, CMC86, CMC87, CMC88, CMC89, CMC90, CMC91, CMC92, CMC93, CMC94, CMC95, CMC96, CMC97, CMC98, CMC99, CMC100.

ELATONE INTERVAL TRANSFORMERS I.F. 35. Ratio 1-5.5. Primary 40-60H Parallel feed only. Coupling condenser, 25 mfd., 20v. x 1.2in. high, 10.- each. I.F. 36. Ratio 1-5.5. Secondary CT for Push-Pull connection: Specification as I.F. 35, 10.- each. I.F. 37. Ratio 1-3 Primary I.O.C. 3 mA. Muntzel core. Fitted with terminal panel 2 1/2in. x 1 1/2in. 10.- each. I.F. 38. With split secondary for Push Pull. Split, Sectionalised Windings ensure low leakage inductance and brilliant top note response. Primary current 20 mA. The I.F. 38 makes an excellent blocking oscillator transformer. 18.6 each.

COLLARO Four speed auto-change unit, a fully automatic changer with many advanced features. Unit plate, 12in. x 12 1/2in. 28.15.0 each, carriage 3.-.

PUBLICATIONS: Please include 4d. postage with single copies, each. No. 134, F.M. Tuner Construction, by W. J. May, East 40 Super Point to Point Wiring, Build High Fidelity Response, 32 Pages, All components for this circuit available 8/- each. 2.8 No. 135, How to Make Aerials for TV (Bands 1 and 3) and V.H.F. (Band 2), 24 Data for all Channels. Ten different designs for local fringe areas No. 100, A Comprehensive Valve Guide, Book No. 1, 48 pages. 5.- No. 121, A Comprehensive Valve Guide, Book No. 2 (Characteristics and Base Connections), 57 pages. 4.0 No. 105, Radiohobby "A" The Radio Colour Code Index for Radio and Television, 1.8 No. 125, Practical Transistors & Transistor Circuits, How to make your own transistors, 48 pages. 3.6 No. 133, A Comprehensive Valve Guide, Book No. 3, International Edition, 1,200 valves not previously listed are presented. 5.- No. 144, Valve and Television Tube Equivalents - Receiving & Transmitting - Industrial, 5.- No. 140, Television Servicing for Beginners, 49 pages of information. 4.6 No. 142, Modern TV Circuits and Fault Finding, 46 pages of information. 4.6 No. 133, Radio Controlled Models for Amateurs, 40 pages, 5.- Aircraft - Circuits, etc., 5.- High Quality Sound Reproduction, Includes 20-watt amplifier, PM Tuner, 12-couplers, etc., 3.8

Table listing various electronic components and their prices, including VY91, VY92, VY93, VY199, VY200.

COLLARO Model 3551, 3 speed single player, Automatic Stop, fitted with "Studio T" pick-up. Cream finish. 26.19.6 each. Post 2.-.

LOUDSPEAKER UNITS

Table listing various loudspeaker units and their prices, including Blac Square Type, 5 1/2in. units, 19.6; Electrons, Plessey, 5 1/2in. units, 17.6; Goodmans, Plessey, 6 1/2in. units, 17.6; Goodmans, R. & A., 8in. units, 19.6; Plessey, R. & A., Elac, 10in. units, 25.6; Plessey, 12in. units, 25.6; Robt 5in. x 8in. Elliptical Unit, 19.6; Elac 10in. x 6in., Elliptical Unit, 25.6; All above PM speakers are 2 to 5 ohms; RVC 12in. Heavy Duty 20 watt Model, 15 ohms, 25.6; 8in. x 6in. Elliptical Unit, 19.6; 6in. Mains Energised Speaker (Plessey), 17.6; 8in. Mains Energised Speaker (Plessey), 21.6; All have field coils of approx. 600 ohms. We have just received a few more 8in. speaker units by Goodmans, etc. PM Type: fitted with standard output transformers. Offered again at 21.6 each.

WB SPEAKERS

16" x 12" unit, 5 watts, 23.8 each, 14" x 12" unit, 10 watts, 20.9 each. Both fitted with universal speech coils matching to all transformers of 3 ohms, 7.5 ohms and 15 ohms.

CHASSIS

Aluminium Unfilled with Reinforced Cover. Available in the following sizes: 6in. x 4in. x 2 1/2in. 4.8; 8in. x 6in. x 2 1/2in. 6.8; 10in. x 7in. x 2 1/2in. 7.8; 12in. x 8in. x 2 1/2in. 8.8; 12in. x 6in. x 2 1/2in. 6.9; 12in. x 5in. x 2 1/2in. 6.6; 14in. x 8in. x 2 1/2in. 12.-; 14in. x 6in. x 2 1/2in. 8.6; 16in. x 10in. x 2 1/2in. 14.-; All are four-bolted, ideal for as 1 receivers, amplifiers, power packs, etc.

AMERICAN RELAY

45 ohms impedance with leads, No. A2042, 1.5 each.

IRON LEADS

Black and white flat iron leads, banded cut, 1.3 each.

POTENTIOMETER PANEL

Four potentiometers on Panel, 50 K ohms 512 x 750 ohms W.V. 25 K ohms Carbon, 250 ohms W.V. 25 A with long spindle, with leads of different colours terminating in an 11-pin plug, 7.6 each.

Wavox choke, max. current 160 mA D.C., resistance 125 ohms, 6.4 each. Westinghouse 1 mA Rectifier, wire code, 8d. each.

4-pin Vibrator Pack, complete with 4-pin Vibrator, 1.75 each. Plyer Side Cutters, 2.7 each. Minor Richards type Replacement Iron Elements, 8.8 each.

2 RANGE COLOUR VOLTMETER

15 MA max. current, 0-15 volts, 0-250 volts, moving coil 2 1/2 ohms per volt, complete with leads, 18.- each.

All these and many other interesting radio and TV components are listed in our CURRENT CATALOGUE which is available to you now. Send 1/- in stamps for your copy.

TRANSISTORS, RED SPOT, 10.- each. BLUE SPOT, 15.- each. PORTAGE AND PACKING 6d. per valve. SAME DAY SERVICE

ALPHA RADIO SUPPLY CO. logo and address information.

103 LEEDS TERRACE WINTOUN STREET LEEDS 7

TERMS: Cash with order or C.O.D. Postage and Packing charges extra, as follows: Orders value 10/- add 1/-; 20/- add 1/6; 40/- add 2/-; £5 add 3/- unless otherwise stated. Minimum C.O.D. fee and postage 3/-. All single valves postage 6d. Personal Shoppers Monday-Friday 9 a.m. to 5 p.m.

LASKY'S RADIO TRANSISTORS

at a reasonable price

Hermetically sealed and unaffected by temperature variations. Tested and guaranteed efficient. R.F. P.N.P. junction type, suitable for medium and low freq. oscillators, freq. changers and I.F. amplifiers (1.5 to 8 Mc/s). **21/-**
(Double spot—yellow and red.)


AUDIO P.N.P. junction Type, suitable for high gain and low freq. amplifiers, and for output stages up to 250 milliwatts. **10/-**
(Double spot—yellow and green.)
Post Free.

Special prices for 6 and over. Full operating data and circuit diagrams for receivers, oscillators, amplifiers, etc. with each Transistor.

MULLARD and BRIMAR Transistors in stock.

COMING SOON! LASKY'S FULLY TRANSISTORISED PORTABLE FOR HOME CONSTRUCTION, using 7 Transistors and 1 Germanium Diode. Watch for full details.

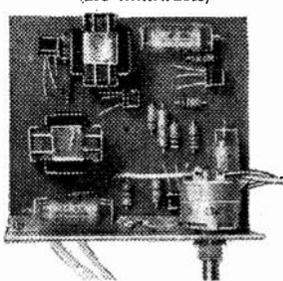LASKY'S TRANSISTOR AMPLIFIER KIT (200 milliwatts)



Miniature size: 3 1/2 in. x 3 1/2 in. Height can be under 1 in. Uses our hermetically sealed Transistors and operates from 6-volt battery. Output impedance 5 Ohms.

COMPLETE KIT including 4 Transistors, all brand new components, latest T.C.C. miniature condensers, PRINTED CIRCUIT and full instructions, **86/6**
Post Free.

FULL DETAILS, circuit diagram and shopping list, 1/-, post free. Free Demonstrations. All components available separately.

Brand New in makers' cartons



COLLARO 4-SPEED AUTO-CHANGER

Very latest 1957 model RC.456, incorporating auto and manual control enabling records to be played singly or up to 10, all sizes mixed, automatically. Complete with Studio crystal pick-up and sapphire stylus. List £13.17.0. **£9.15.0**
Carr. & Packing, 3/6 extra.

BRAND NEW AND PERFECT 16" METAL CONE C.R. TUBES

Type T901. Circular. Gives large black and white picture. 1 1/2 in. x 1 1/4 in. Guaranteed by us for 3 months. List £23.9.10. **£8.9.6**

Carr. & Ins. 22/6 extra. Full details on request.

RECTANGULAR C.R. TUBES

14in., £12.19.6. 17in., £14.19.6.

LASKY'S (HARROW ROAD) LTD.

42, TOTTENHAM COURT ROAD, W.1. Telephone: MUSeum 2605.
370, HARROW ROAD, PADDINGTON, W.9. LAD 4075 and CUN 1979.
Open all day SATURDAY. Half day Thursday.
PLEASE ADDRESS ALL MAIL ORDERS TO HARROW ROAD.

BENTLEY ACOUSTIC CORPORATION LTD.

EXPRESS SERVICE!!!

C.O.D. ORDERS RECEIVED BY 3.30 P.M. EITHER BY LETTER, TELE. OR WIRE, DESPATCHED SAME AFTERNOON.

THE VALVE SPECIALISTS 38, CHALCOT RD., LONDON, N.W.1

PrImrose 9090

FOR ONLY 6d. EXTRA PER ORDER WE WILL INSURE YOUR VALVES AGAINST DAMAGE IN TRANSPORT. ALL UNINSURED PARCELS AT CUSTOMERS' RISK.

024	6/-	6A47	6/8	6P12	9/-	6V6G	7/-	12J5GT	4/-	4IMP	12/6	6K523	8/6	6BC41	10/-	6L42	11/-	LN152	10/-	PY82	7/6	UL41	10/4
1A3	3/-	6A45	6/6	6F10	13/-	6V6GT	7/-	12J7GT	11/-	4JMTL	7/6	6K525	6/6	6BF80	9/6	6E121	15/-	LN309	12/6	PY83	9/6	UL46	15/-
1A5	6/-	6A47	12/6	6F16	9/6	6X4	5/-	12K8GT	8/6	5A45	10/-	6V63	10/6	6BF89	9/6	6E124	10/6	LN319	7/-	QP21	7/6	UO9	8/-
1A7	12/6	6A38	8/-	6F17	12/6	6X53GT	6/6	12K8GT	14/6	3CL6GT	8/6	6V85	12/6	6E125	12/6	6E129	5/-	MH4	7/6	QP22B	12/6	UY41	8/6
1D8	10/6	6A35	5/-	6F22	10/6	6Z4,81	12/6	12L7GT	8/6	57	8/6	6V428	30/-	6E134	6/-	6E134	7/6	MH4	7/6	QP25	10/6	UY85	10/6
1B5	11/-	6A48	7/6	6F23	12/6	6Z5	12/6	12K2A7	8/6	35	8/6	U1	8/6	6E131	15/-	6E140	10/6	MHL4	6/6	QS150/15	5/6	V1607	5/-
114	6/6	6A15	6/6	6F26	6/6	6J30L2	12/6	12P97	7/6	61BT	12/6	042	10/6	6E132	10/6	6E132	10/6	Y51	10/6	12/6	12/6	VL492A	25
1LD3	5/-	6A25	5/-	6H6G	2/6	7A7	12/6	12P97	7/6	61BT	15/-	043	5/-	6E133	8/6	6E136	10/6	M16	6/6	R12	12/6	VMP4G	15/-
1LN5	5/-	6A36	8/-	6H6M	3/6	7B7	8/-	12P97	6/6	72	4/6	077	6/6	6E135	8/6	6E138	6/6	M14	8/6	8D6	14/6	VP2(7)	12/6
1N5	11/-	6A25	7/6	6J34	5/-	7C5	8/6	12P97	8/-	77	8/-	DA392	11/-	6E138	8/6	6E140	8/-	N142	10/-	SP4(7)	15/-	VP4(7)	15/-
1R5	8/6	6A49	10/-	6J36GT	6/6	7C6	8/6	12P97	6/6	78	8/6	DAF91	7/6	6E139	7/6	6E141	10/6	N150	10/6	SP41	8/6	VP130	7/6
1R5	7/6	6A78	8/6	6J36GT	6/6	7HT	8/6	12P97	6/6	80	8/6	DAF96	9/6	6E139	8/6	6E140	11/6	N269	11/6	SP42	12/6	VP23	6/6
1T4	7/-	6B4	6/-	6J6	6/6	7Q7	8/6	12P97	8/6	88	8/6	DC930	7/6	6E144	12/6	6E144	12/6	N271	10/6	SP1	3/6	VP41	8/6
1U5	7/-	6B7	10/6	6J7G	6/-	7V7	8/6	12P97	10/6	8A2	15/-	DF33	11/-	6E145	8/6	6E145	8/6	N309	8/6	OC3	8/6	TH30C	25/-
2A3	12/6	6B8G	4/-	6K7G	5/-	7Y4	8/6	12Y4	10/6	120B2	15/-	DF91	7/6	6E146	8/6	6E146	8/6	N142	10/-	SP4(7)	15/-	VP4(7)	15/-
X28	4/-	6B8M	4/6	6K7GT	6/-	8Y3	8/6	14B7	10/6	210LF	3/-	DF96	8/6	6E147	12/6	6E148	12/6	N150	10/6	SP41	8/6	VP130	7/6
2H13C	7/6	6B48	7/6	6K8A1	8/-	9Y2	8/6	14B7	14/-	87	6/6	DR63	8/6	6E148	12/6	6E148	12/6	N269	11/6	SP42	12/6	VP23	6/6
2X2	4/6	6B86	7/6	6LD3	10/-	10P1	15/-	19H1	10/6	666A	12/6	DR78	8/6	6E149	12/6	6E149	12/6	N271	10/6	SP41	3/6	VP41	8/6
3A4	7/-	6B36	8/-	6L6G	8/-	10C2	13/-	19D1	12/6	885	10/6	DR77	8/6	6E149	12/6	6E149	12/6	N271	10/6	SP41	3/6	VP41	8/6
3A5	7/-	6B37	11/-	6L7M	8/-	10F1	15/-	20L1	13/6	926	3/-	DK32	12/6	6E149	12/6	6E149	12/6	N271	10/6	SP41	3/6	VP41	8/6
3B7	8/6	6B36	8/-	6L18	13/6	10F9	11/6	20L6GT	9/-	1203	7/6	DK91	8/6	6E149	12/6	6E149	12/6	N271	10/6	SP41	3/6	VP41	8/6
3C8	9/-	6B37	10/-	6N7	8/-	10F12	12/6	25Z46	9/-	4C33L	12/6	DK92	12/6	6E149	12/6	6E149	12/6	N271	10/6	SP41	3/6	VP41	8/6
3D4	9/-	6B36	10/-	6Q7G	8/6	10L13	8/6	33Z6GT	9/-	636	12/6	DK96	9/6	6E149	12/6	6E149	12/6	N271	10/6	SP41	3/6	VP41	8/6
3Q5GT	8/6	6B37	8/6	6Q47T	9/-	10P13	17/6	37	7/6	7193	5/-	D12	15/-	6E157A	8/6	6E157A	8/6	N271	10/6	SP41	3/6	VP41	8/6
3S4	8/-	6C4	7/-	6R7G	8/6	11E3	16/-	28D7	7/-	7475	7/6	DL38	9/6	6E159	8/6	6E159	8/6	N271	10/6	SP41	3/6	VP41	8/6
3V4	9/-	6C5	8/6	6B47	8/6	12A6	6/6	39	7/6	9002	5/6	DL92	8/6	6E159	8/6	6E159	8/6	N271	10/6	SP41	3/6	VP41	8/6
6U4	8/-	6C6	6/6	6B47	6/6	12A7	8/6	39C1	12/6	9003	5/6	DL94	9/6	6E159	8/6	6E159	8/6	N271	10/6	SP41	3/6	VP41	8/6
5V4	10/-	6C8	8/-	6B47	6/6	12A8H	10/6	39F3	12/6	9008	6/6	DL96	12/6	6E159	8/6	6E159	8/6	N271	10/6	SP41	3/6	VP41	8/6
6X4	10/-	6A8	12/6	6B47	8/6	12A76	10/6	39FL1	12/6	AC5PN	6/6	DL10	10/6	6E159	8/6	6E159	8/6	N271	10/6	SP41	3/6	VP41	8/6
5Y3	7/6	6C10	10/6	6B47	5/6	12A7	8/6	39F1	12/6	6/6	DL70	8/6	6E159	8/6	6E159	8/6	N271	10/6	SP41	3/6	VP41	8/6	
6Y4	10/-	6C8	7/6	6B47	8/6	12A7	7/6	39P12	13/6	AC/HL	6/6	PA50	2/-	6E154	5/6	6E154	5/6	N271	10/6	SP41	3/6	VP41	8/6
6Z3	12/6	6D6	6/6	6B47	7/6	12A7	7/6	39P12	13/6	DD1	15/-	EA76	6/6	6E154	5/6	6E154	5/6	N271	10/6	SP41	3/6	VP41	8/6
8Z4	8/6	6F1	15/-	6B47	7/6	12B48	9/6	33A/158M	AC/PA	8/6	EA76	6/6	6E154	5/6	6E154	5/6	N271	10/6	SP41	3/6	VP41	8/6	
6A8	10/-	6B8	9/6	6B47	14/-	12B8	10/6	30	A/50	10/-	EA91	9/6	6E154	5/6	6E154	5/6	N271	10/6	SP41	3/6	VP41	8/6	
6A87	8/-	6C7	10/6	6B47	7/6	12E1	3/6	35J51	12/6	AP4	7/6	EA442	10/6	6E154	5/6	6E154	5/6	N271	10/6	SP41	3/6	VP41	8/6
6AB8	10/-	6F8	10/6	6C7	8/6	12H9M	3/6	35A3	11/6	ATP4	3/6	EA44	2/6	6E154	5/6	6E154	5/6	N271	10/6	SP41	3/6	VP41	8/6
								35L6GT	8/-	AZ31	12/6	EB41	8/6	6E154	5/6	6E154	5/6	N271	10/6	SP41	3/6	VP41	8/6
								35Z3	10/6	B509	9/6	EB91	4/6	6E154	5/6	6E154	5/6	N271	10/6	SP41	3/6	VP41	8/6
								35Z4CT	8/6	B529	10/6	EB93	15/-	6E154	5/6	6E154	5/6	N271	10/6	SP41	3/6	VP41	8/6
								35Z4GT	8/6	BL63	7/6	EB93	7/6	6E141	10/6	6E141	10/6	N271	10/6	SP41	3/6	VP41	8/6

Terms of business:—Cash with order or C.O.D. only. Orders value £3 or more sent post/packing free. Orders below £3 please add 1d. per valve. C.O.D. orders:—Minimum fee, including post and packing, 3/-, plus 6d. are open for personal shoppers. Mon.-Fri. 8.30-5.30. Sat. 8.30-1 p.m.

Please enquire for any valve, germanium diode, or transistor not listed. 2d. stamp, please, or phone.

All valves new, boxed, tax paid, and subject to makers' guarantee. First grade goods only, no seconds or rejects. All orders received by first post despatched same day. S.A.E. for free complete list, with full terms of business.

Wanted!

QUALIFIED MEN AND WOMEN

Industry & Commerce offer their best posts to those with the necessary qualifications—such posts that will bring personal satisfaction, happiness, good money and security. As part of a modern industrial organisation, we have skilled knowledge of what is required in industry to-day and the best means of training personnel for its present day and future requirements. We specialise also in teaching for hobbies, new interests or part-time occupations in any of the subjects listed below. Make your own choice and write to us to-day for further information. There is no obligation of any kind.



The E.M.I. Factor's at Hayes, England.

The only Home Study College operated by a world-wide manufacturing organisation

EMI INSTITUTES

PERSONAL & INDIVIDUAL TRAINING IN—

- | | | | |
|---------------------------------------|-----------------------------------|------------------------------|----------------------------------|
| Accountancy | Customs Officer | Languages | Refrigeration |
| Advertising | Draughtsmanship | Management | Sales Management |
| Aeronautical Eng. | Economics | Maintenance Eng. | Sanitary Engineering |
| A.R.B. Licences | Electrical Eng. | Mathematics | Salesmanship |
| Art (Fashion, Illustrating, Humorous) | Electrical Installations | M.C.A. Licences | Secretaryship |
| Automobile Eng. | Electronics | Mechanical Eng. | Shorthand & Typing |
| Banking | Electronic | Motor Eng. | Short Story Writing |
| Book-keeping | Draughtsmanship | Painting & Decorating | Short Wave Radio |
| Building | Eng. Drawing | Photography | Sound Recording |
| Business Management | Export Heating & Ventilation Eng. | P.M.G. Certs. | & Reproduction |
| Carpentry | High Speed Oil Engines | Police Production Eng. | Telecommunications |
| Chemistry | Industrial Admin. | Production Planning | Television Time & Motion Study |
| City & Guilds Exams | Jig & Tool Design | Radar | Tracing |
| Civil Service | Journalism | Radio Amateurs | Welding |
| Commercial Subjects | | (C&G) Licence | Workshop Practice |
| Commercial Art & Drawing | | Radio & Television Servicing | Works Management and many others |

Also courses for GENERAL CERTIFICATE OF EDUCATION, A.M.I.H.&V.E., A.M.S.E., A.I.Brit.I.R.E., A.M.I.Mech.E., A.M.I.E.D., A.M.I.M.I., A.F.R.Ae.S., A.M.I.P.E., A.M.I.I.A., A.C.C.A., A.C.I.S., A.C.C.S., A.C.W.A., City & Guilds Examinations, R.T.E.B. Serv. Cert., R.S.A. Certificates, etc.

NEW! Courses with PRACTICAL EQUIPMENT

in RADIO · TELEVISION · MECHANICS CHEMISTRY · ELECTRICITY DRAUGHTSMANSHIP · PHOTOGRAPHY etc., etc.



COURSES FROM 15/- PER MONTH

POST THIS TODAY



E.M.I. INSTITUTES, Dept. 32K, London W.4.

NAME _____ AGE _____
(if under 21)

ADDRESS _____

Subject(s) with/without equipment _____

BLOCK CAPS PLEASE

AUG. 57 We shall not worry you with personal visits

IC 92

—Part of "His Masters Voice", Marconiphone, etc. etc.

R.S.C. BATTERY CHARGING EQUIPMENT

ASSEMBLED CHARGERS

6 v. 1 amp.	19/8
6 v. or 12 v. 1 amp.	25/9
6 v. 2 amps.	29/9
6 v. or 12 v. 2 amps.	38/9
6 v. or 12 v. 4 amps.	59/9
Above ready for use. Carr. 3/6. With mains and output leads.	

SELENIUM RECTIFIERS

612 v. 1 a. 4 1/11	I.T. Types H.V.
612 v. 2 a. 9.	6-12 v. 1 a. H.W. 2/9
612 v. 3 a. 11/9.	H.T. Types H.V.
612 v. 4 a. 14/9.	150 v. 40 mA. 3/9
612 v. 6 a. 19/9.	250 v. 50 mA. 5/9
612 v. 10 a. 25/9.	250 v. 80 mA. 7/9
612 v. 15 a. 35/9.	250 v. 150 mA. 9/9
	250 v. 250 mA. 11/9

BATTERY CHARGER KITS

Consisting of Mains Transformer, F.W. Bridge, Metal Rectifier, well ventilated steel case, Fuses, Fuse holders, Grommets, panels and circuit. Carr. 2/9 extra.

6 v. or 12 v. 1 amp.	22/9
6 v. 2 amps.	25/9
6 v. or 12 v. 2 amps.	31/6
6 v. or 12 v. 4 amps.	53/9

BATTERY CHARGER KIT

Consisting of F.W. Bridge Rectifier 612 v. 5 a. Mains Trans. 0-9-15 v. 6 a output and ammeter. 49/9. Post 3/-.

ASSEMBLED CHARGER

6 v. or 12 v. 2 amps. Fitted Ammeter and selector plug for 6 v. or 12 v. Louvred metal case, finished attractive hammer blue. Ready for use. With mains and output leads. Double Fused. Only Carr. 3/6. **47/9**

All for A.C. Mains 200-250 v., 50 c/c.s. Guaranteed 12 months.



Assembled 6 v. or 12 v. 4 amps. Fitted Ammeter and variable charge rate selector. Also selector plug for 6 v. or 12 v. charging. Double fused. Louvred steel case with stoved blue hammer finish. **75/-**
Ready for use with mains and output leads. Carr. 3/9

R.S.C. MAINS TRANSFORMERS (FULLY GUARANTEED)

Interleaved and Impregnated. Primaries 200-230-250 v. 50 c/c.s. Screened. TOP SHROUDED DROP THROUGH

250-0-250 v. 70 mA.	6.3 v. 2 a. 5 v. 2 a.	16/9
350-0-350 v. 80 mA.	6.3 v. 2 a. 5 v. 2 a.	18/9
250-0-250 v. 100 mA.	6.3 v. 4 a. 5 v. 3 a.	22/9
300-0-300 v. 100 mA.	6.3 v. 4 a. 5 v. 3 a.	22/9
350-0-350 v. 100 mA.	6.3 v. 4 a. 5 v. 3 a.	22/9
350-0-350 v. 100 mA.	6.3 v. 4 a. C.T.	23/9
0-4-5 v. 3 a.		23/9
350-0-350 v. 150 mA.	6.3 v. 4 a. 5 v. 3 a.	28/9

ELIMINATOR TRANSFORMERS
Primaries 200-250 v. 50 c/c.s.

120 v. 40 mA.	5-0-5 v. 1 a	15/9
90 v. 15 mA.	4-0-4 v. 500 mA	9/9

CHARGER TRANSFORMERS
All with 200-230-250 v. 50 c/c.s. Primaries:

0-9-15 v. 1 a.	11/9
0-9-15 v. 3 a.	17/9
0-9-15 v. 5 a.	18/9
0-9-15 v. 6 a.	23/9

SMOOTHING CHOKES

250 mA. 5 H 100 ohms	12/9
150 mA. 7-10-250 ohms	11/9
100 mA. 10 H 200 ohms	8/9
80 mA. 10 H 350 ohms	5/9
80 mA. 10 H 400 ohms	4/11

OUTPUT TRANSFORMERS
Midget Battery Pentode 66:1 for 354, etc. 3/9
Small Pentode, 5,000Ω to 3Ω 3/9
Small Pentode 7,800Ω to 3Ω 3/9
Standard Pentode, 5,000Ω to 3Ω 4/9
Standard Pentode, 7,800Ω to 3Ω 4/9
Push-Pull 10-12 watts 6V6 to 3Ω or 15Ω 15/9
Push-Pull 10-12 watts to match 6V6 to 3-5-8 or 15Ω 16/9
Push-Pull EL84 to 3 or 15Ω 16/9
Push-Pull 15-18 watts, 6L6, KT66 22/9
Push-Pull 20 watts, sectionally wound 6L6, KT66, etc. to 3 or 15Ω 47/9

MANUFACTURERS' SURPLUS MAINS TRANSFORMERS. Primaries 250-250 v. 50 c/c.s. Drop Through Chassis type. 250-0-250 v. 70 mA. 6.3 v. 2.5 a. 11/9.

SPECIAL OFFERS: Electrolytics. 22-32-52 mfd. 250 v. Duffinier small can. 2/9 ea. 150 mfd. 450 v. 3/9. Small .0005 mfd. 2-amp. 4/9 ea. Westinghouse Rectifiers 250 v. 250 mA. 7/9. CO-AXIAL CABLE. 75 ohm. (in. Bd. yd. Twin Screened Feeder 11d.yd.

EX-GOVT. TRANSP. 230/250 v. 50 c/c.s. HEAVY DUTY OIL FILLED suitable for electric welding or hot heating. Output 12 v. 80-100 amps. £6-19-6. Carr. 7/6.

EX-GOVT. SMOOTHING CHOKES

250 mA. 5 H 50 ohms	12/9
150 mA. 10 H 100 ohms	11/9
150 mA. 6-10 H 150 ohms Trop.	3/11
100 mA. 5 H 100 ohms	3/9

EX-GOVT. E.H.T. SMOOTHING CONDENSERS. .02 mfd. 5,000 v. Cans. 2/9; 1 mfd. 2,500 v. Bakelite Tubulars. 3-3.

EX-GOVT. METAL BLOCK (PAPER) CONDENSERS

4 mfd. 500 v. 2/8; 4 mfd. 1,000 v. 4/9	
8 mfd. 500 v. 4/8; 10 mfd. 500 v. 3/9	
4 mfd. 400 v. plus 2 mfd. 250 v. 1/11.	

EX-GOVT. ELECTROLYTICS. Removed from unused equipment. 8-18 mfd. 550 v. 1/3; 1,500 mfd. 8 v. 1/8; 100 mfd. 50 v. with clip. 9d.

EX-GOVT. DOUBLE WOUND STEP UP/STEP DOWN TRANSFORMERS. 10-0-100-200-220-240 v. to 5-0-7.5-115-135 v. or REVERSE. 80-100 mA. Only 11/9. plus 2/9 post. 10-0-100-200-220-240 v. to 9-0-110-122-136-148 v. or REVERSE. 200 watts, 35/8. plus 7/6 carr.

EX-GOVT. CASES. Size 14-10-8 in. high. Well ventilated black crackle finished. undrilled cover. IDEAL FOR BATTERY, CHARGER OR INSTRUMENT CASE. OR COVER COULD BE USED FOR AMPLIFIER. Only 9/9, plus 2/9 postage. Size 8 1/2 x 13 1/4 x 6 1/2 ins. with undrilled well ventilated cover, finished in stoved grey enamel. Suitable for charger or instrument case. 7/9, plus 2/9 post.

EX-GOVT. VALVES (NEW)

1T4	7/9	EF39	5/9	EF89	7/9
1S5	7/9	6V6G	7/9	EB91	8/9
354	8/9	6X4	8/9	EF36	8/9
5Y3G	8/9	6X5GT	7/9	EL32	3/9
5U6G	8/9	6L6G	11/9	EL91	5/9
5Z4G	8/9	607	7/9	KT44	8/9
6R7G	5/9	12A6	4/9	EB30	8/9
68J7G	8/9	15D2	4/9	EB29	8/9
68L7G	8/9	35Z4GT	9/9	EL84	10/9
68N7GT	8/9	MH4	4/9	SP61	2/9
6AT6	7/9	EC63	8/9	35Z4	8/9

EX-GOVT. UNIT RDF1. Brand new, cartoned. Complete with 14 valves, including 5Z4, E.H.T. rectifier. Transformer, Choke, etc. Only 29/9, carr. 7/6.

ELETTROLYTICS (current production) NOT EX-GOVT.

Tubular Types		Can Types	
8μF 450 v.	1/9	16 mfd. 350 v. 1/11	
8 mfd. 500 v. 2/6		8 mfd. 500 v. 2/8	
16μF 350 v.	2/3	16μF 450 v.	2/9
16μF 450 v.	2/9	32μF 350 v.	2/11
16μF 500 v.	3/9	32 mfd. 450 v. 4/9	
32μF 350 v.	3/9	100 mfd. 450 v. 4/9	
25μF 25 v.	1/3	8-8μF 450 v.	2/9
30μF 12 v.	1/3	8-16μF 450 v. 3/11	
50μF 25 v.	1/6	16-16μF 450 v. 3/11	
50μF 50 v.	1/9	32-32μF 350 v. 4/8	
100 mfd. 12 v. 1/8		32-32μF 450 v. 5/9	
100 mfd. 25 v. 2/3		100-100mfd. 350v. 4/9	
3,000 mfd. 6 v. 3/9		64-120mfd. 350v. 7/9	
9,000 mfd. 6 v. 3/9		100-275 mfd.	6/9

Many others in stock.

FILAMENT TRANSFORMERS

All with 200-250 v. 50 c/c.s. primaries 6.3 v. 1.5 a. 5/9; 6.3 v. 2 a. 6/9; 6.3 v. 2 a. 7/9; 12 v. 1 a. 7/11; 6.3 v. 3 a. 8/11; 6.3 v. 6 a. 17/8; 12 v. 3 a. or 24 v. 1.5 a. 17/8.

SMALL POINTED MAINS TRANSP. Removed from new Ex-Govt. units. Primary 0-200-230-250 v. Secs. 250-0-250 v. 60 mA. 6.3 v. 2 a. 11/9; 5 v. 2 a. Size 3 1/2 x 4 1/2 x 3 in.

R.S.C. BATTERY TO MAINS CONVERSION UNITS

Type BM1. An all-dry battery eliminator. Size 5 1/2 x 4 1/2 x 2 in. approx. Completely replaces batteries supplying 1.4 v. and 90 v. where A.C. mains 200-250 v. 50 c/c.s. is available. Suitable for all heavy portable receivers requiring 1.4 v. and 90 v. This includes latest low consumption types. Complete kit with diagrams, 39/9. or ready for use, 46/9.



Type BM2. Size 8 x 5 1/2 x 2 1/2 in. Supplies 120 v., 50 v. and 60 v., 40 mA. and 2 v. 0.4 a. to 1 amp. fully smoothed. Thereby completely replacing both H.T. batteries and I.T. 2 v. accumulators. When connected to A.C. mains supply 200-250 v. 50 c/c.s. SUITABLE FOR ALL BATTERY RECEIVERS normally using 2 v. accumulator. Complete kit of parts with diagrams and instructions 49/9. or ready for use 58/9.

H.T. ELIMINATOR AND TRICKLE CHARGER KIT.

Input 200-250 v. A.C. Output 120 v. 40 mA. Fully smoothed and rectified supply to charge 2 v. accumulator. Price with louvred metal case and circuit, 29/9. Or ready for use, 8/9 extra.

T.V. CABINETS. Leading manufacturers' surplus. Attractive designs. Walnut veneered, with doors for 15, 16 or 17 in. Tube. £3-19-6. Carr. 7/6.

MINIATURE MOTORS. 24-28 v. D.C. or A.C. made by Hoover Ltd., Canada. Size only 2 1/2 x 1 1/2 in. Spindle 1 1/2 in. long, 1/4 in. diam. Brand New. 9/9.

EXTENSION SPEAKERS

Ready for use in walnut veneered cabinet. Sin. 2.3 ohms. 35/9. Very limited number.




VOLUME CONTROLS with long (1 in. diam.) spindle, all values less switch. 2/8; with S.P. switch, 3/9; with D.P. switch, 4/6.

HUNTS MOLDSEAL CONDENSERS. .005 mfd. 400 v., .01 mfd. 400 v., .04 mfd. 500 v., 5/8 doz. (one type); 1 mfd. 350 v., 8d. ea.; 5 mfd. 500 v., 1/8 ea.

R.S.C. A8 ULTRA LINEAR 12 WATT AMPLIFIER

High-Fidelity Push-Pull Amplifier with "Built-in" Tone Control. Pre-amp stages, high sensitivity. Includes 4 valves (6F7 outputs). High quality, sectionally wound output transformer, specially designed for Ultra Linear operation, and reliable small condenser of current manufacture. **INDIVIDUAL CONTROLS FOR BASS AND TREBLE**; "Lift" and "Cut". Frequency response - 3db., 30-30,000 c/s. Six negative feedback loops. Hum level 7 db. down. ONLY 70 millivolts input required for P.U.I. OUTPUT Suitable for use with all makes and types of pick-ups and practically all microphones. Comparable with the very best designs. **FOR STANDARD OR LONG-PLAYING RECORDS.** **E7-15-0** **RECORDS.** **FOR MUSICAL INSTRUMENTS** such as **STRING BASS, GUITARS, etc. OUTPUT SOCKET** with plug provides 300 v. 20 mA. and 6.3 v. 1.5 A. For supply of a **RADIO FEEDER UNIT**. Size approx. 12-9-7 1/2". For A.C. mains 200-250 v. 50 c/s. Outputs for 15 and 15 ohm speakers. Kit is complete to last unit. Chassis is fully punched. Full instructions and point-to-point wiring diagrams supplied. Unpunched-plate value at £7 15 - , or factory built 45 - extra. Carriage 10 - . If required louvred metal cover with ?

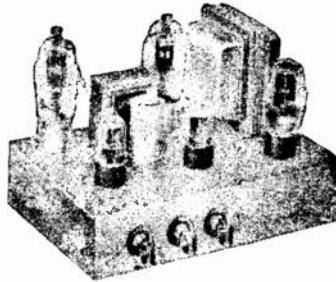

carrying handles can be supplied for 17 6. Additional input socket with associated Vol. control so that two different inputs such as Gram and 'Mike' or Tape and Radio can be mixed, can be provided for 13 - extra. Guaranteed 12 months. TERMS on assembled two input model: **DEPOSIT 25 6** and nine monthly payments 23 4. **HIGH-FIDELITY MICROPHONES** and **SPEAKERS** in stock. Keep cash prices or H.P. terms if supplied with amplifier.

COLLARO RC54 3-SPEED AUTO-CHANGERS with Studio 19-9-50. Brand New. For 110 v. 50 c/s. A.C. mains. Price £16 11 - . For 230-250 v. Auto Trans. only £7 15 - . Carr. 7 6.

COLLARO RC456 4-SPEED AUTO-CHANGERS with high fidelity Studio Pick-up. Latest model. Brand new. Cartoned. For 200-250 v. 50 c/s. A.C. mains. Our price £8 19 6. Carr. 5 6.

IG3 3-WATT GRAM AMPLIFIER. For use with above or any other single or auto-change units. A double wound mains transformer ensures that chassis and pick-up are completely separate. Latest type B.V.A. valves used. Output for 2-3 ohm speaker. For 200-250 v. 50 c/s. A.C. mains sensitivity 250 m.v. Indispensable hum. Size: 6-4-4 1/2". Controls: Vol. and Tone with switch. Guaranteed 12 months. Only 49 9.

SUPERHET FEEDER UNIT. Designed for high quality Radio Tuner Unit (especially suitable for use with our Amplifier). Delayed A.V.C. employed. The W.Ch. Sec. incorporates Gram position. Controls are: Tuning W.Ch. and Vol. Only 250 v. 15 mA. H.T. and L.T. of 6.3 v. and 100 v. required from amplifier. Size of unit 5-4-10 1/2". In. High. Simple alignment procedure. Point-to-point wiring diagrams, instructions and priced parts list with illustration. 2 6. Total building cost, £4 15 - . For descriptive leaflet send S.A.E.

LINEAR L46 MINIATURE 4.5 WATT 4C QUALITY AMPLIFIER. Suitable for use with Collaro, E.S.11, or any other record-playing unit, and most telephones. Total negative feedback 12 db. Separate Bass and Treble Control. For A.C. mains input of 200-250 v. 50 c/s. Output for 2-3 ohm speaker. Three minimum type Mullard valves used. Size of unit only 6-5-5 1/2". In. High. Chassis is fully isolated from mains. Output for 2-3 ohm speaker. Guaranteed for 12 months. Only 25 19 6 - or Deposit 22 - and five monthly payments of 29 - . Illustrated leaflet 3d.

LINEAR "DIATONIC" 10 WATT HIGH-FIDELITY PUSH-PULL ULTRA LINEAR AMPLIFIER. For 200-250-250 v. 50 c/s. A.C. Mains. Valve line-up ECC83, ECC83, EL84, EL84, E220 miniature Mullard. The unit has sectionally wound output transformer, separate Bass and Treble Controls, independent 'Mike' and Gram Input sockets are provided. Size is only 10-6-6 ins. Output Matchings for 5 and 15 ohm speakers. Finished in attractive silver Blue-Gray hamper. Only 12 6-8-5 - or Deposit 29 9 plus 10 - and 9 monthly payments of 28 9. Leaflet 3d.

Terms: C.W.O.D. or C.O.D. NO C.O.D. under £1. Post 19 extra under 22 - 2 9 extra under 25 - 8-11 - with all enquiries. Personal Shoppers (Not Postal) can also be supplied by Messrs. Myers (Middlesbrough), Linthorpe Rd., Middlesbrough.

R.S.C. 30 WATT ULTRA LINEAR HIGH-FIDELITY AMPLIFIER A10

A highly sensitive Push-Pull, high output unit with self-contained Pre-amp. Tone Control Stages. Certified performance figures compare equally with most expensive amplifiers available. Hum level 70 db. down. Frequency response - 3 db. 20,000 c/s. A specially designed sectionally wound ultra linear output transformer is used with 807 output valves. All components are chosen for reliability. Six valves are used, 6F8B, 6E6B, ECC83, 807, 807, 6X3. Separate Bass and Treble Controls are provided. Minimum input required for full output is only 12 millivolts so that **ANY KIND OF MICROPHONE OR PICK-UP IS SUITABLE.** The unit is designed for **CLUBS, SCHOOLS, THEATRES, DANCE HALLS, OUTDOOR FUNCTIONS, etc.** For use with Electro-CORIAN, GUITAR, STRING BASS, etc. For standard or long-playing records, **OUTPUT SOCKET PROVIDES L.T.** and **H.T.** for a **RADIO FEEDER UNIT.** Control is provided with associated Vol. control. Inputs such as Gram and 'Mike' can be mixed. Amplifier operates on 200-250 v. 50 c/s. A.C. Mains and has outputs for 5 and 15 ohm speakers. Complete kit of parts with fully punched chassis and point-to-point wiring diagrams and instructions. If required cover as for A8 can be supplied for 17 6. The Carr. 10 - amplifier can be supplied, factory built with 12 months' guarantee, for £219 18 6. TERMS: **DEPOSIT 28 11** and 9 monthly payments of 28 11.

R.S.C. 45 WATT 5 HIGH-GAIN AMPLIFIER

A highly sensitive 4-valve quality amplifier for the home, small club, etc. Only 50 millivolts input is required for full output so that it is suitable for use with the latest high-fidelity pick-up heads, in addition to all other types of pick-ups and practically all 'mikes'. Separate Bass and Treble Controls are provided. These give full long-playing record equalisation. Hum level is negligible being 7 db. down, 15 db. of negative feedback is used. H.T. of 300 v. 25 mA. and L.T. of 6.3 v. 1.5 A. is available for the supply of a Radio Feeder Unit, or Tape Deck pre-amplifier. For A.C. mains input of 200-230-250 v. 50 c/s. Output for 2-3 ohm speaker. Chassis is not fully K.I. is complete in every detail and includes fully punched chassis (with baseplate) with Blue hamper finish and point-to-point wiring diagrams and instructions. Exceptional value at only 24 19 - , or assembled ready for use 25 - extra, plus 3 6-arr.; or Deposit 22 6 and 5 monthly payments of 22 6 for assembled unit.



R.A.A. 20 WATT RE-ENTRANT SPEAKERS. 15 ohms or 600 ohms matching. For Outdoor work. Only 8 GNS. **P.M. SPEAKERS.** All 2-3 ohms. 5 in. Godmans, 17 8. 6 in. Godmans water type, 16 9. 8 in. Rola, 19 9. 10 in. Elac, 26 9. 12 in. Plessey, 29 11. 10 in. W.H. 12 in. Plessey 3 or 15 ohms type HF1012 10 watts, hi-fidelity type. Recommended for use with our A8 amplifier. £4 10 9. 12 in. Plessey 3 ohms 10 watts, 59 6.

PLESSEY DUAL CONCENTRIC 10 in. 10 ohm HIGH-FIDELITY SPEAKERS with built-in tweeter completely separate elliptical speaker with choke, condensers, etc.) providing extraordinarily realistic reproduction when used with our A8 or similar amplifier. Rated 10 watts. Price complete, only 25 17 6.

M.E. SPEAKERS 2-3 ohms. 8 in. R.A. 11 in. 600 ohms, 11 9.

P.M. SPEAKERS, 2-3 ohms. Suitable for use with L45, A5 or A7 amplifiers. Elac 7 x 4 in. elliptical, 16 9. Celestion 6 in. with high flux density magnet, 19 9. 12 in. Plessey, 29 11. 12 in. Plessey with high flux density magnet, 47 9. The latter is especially recommended.

R.S.C. 3-4 WATT A7 HIGH-GAIN AMPLIFIER

For 230-250 v. 50 c/s. Mains Input, Appearance and Specification, with exception of output wattage, as A5. Complete kit with diagrams, 23 15 - . Assembled 22 6 extra. Carr. 3 6.

THE SKYFOUR T.R.F. RECEIVER A design of a 3-valve Low and Medium wave 250-250 v. A.C. Mains receiver with selenium rectifier. It consists of a variable-tu high-gain H.F. stage followed by a low distortion audio band detector. Power pentode output is used. Valve line-up being 6K7, 5Y6, 6V6G. Selectivity and quality are well up to standard, and simplicity of construction is a special feature. Point-to-point wiring diagrams, instructions and parts lists. The receiver can be built for a maximum of £4 19 6. Including attractive Brown or Cream Bakelite or Walnut veneered wood cabinet 12 x 6 1/2 x 5 1/2. 22 - 2 9 extra under 25 - 8-11 - with all enquiries.

LT45 HIGH QUALITY TAPE DECK AMPLIFIER. For All Tape Decks with High Impedance, Playback and Erase Heads, such as Lane, Truvox, Ready for etc. Or for Collaro, Brenell, Use ONLY one type of Deck should be stated when ordering. Output is 45 watts. For 2-3 ohm speaker. For A.C. Carr. 7 6. Mains 200-250 v. 50 c/s. Positive compensated identification for recording level by Magic Eye. Recording facilities for 15, 7 1/2 or 3 1/2 in. per sec. Automatic equalisation at the turn of a knob. Linear frequency response of 1 3 db., 50-11,000 c/s. Negative feedback equalisation. Minimum hum. High output with completely effective equalisation and distortionless reproduction. Sensitivity is 12 millivolts. Any kind of crystal microphone is suitable. Only 2 millivolts minimum output required from recording head. Provision is made for feeding a 1 A. amplifier. Illustrated leaflet 6d. Special price quoted for above with Deck.

12 GNS.

RADIO SUPPLY CO. 32, THE CALLS, LEEDS, 2



Stern's introduce . . . A "fidelity" TAPE RECORDER WITH EVERYTHING—EXCEPT A HIGH PRICE

TESTED AND APPROVED AT THE TRUVOX LABORATORIES. IT INCORPORATES: The NEW TRUVOX Mk. IV TAPE DECK together with the "fidelity" MODEL HF/TR2 TAPE AMPLIFIER (both illustrated on this page), and a Rola 10in. x 6in. P.M. SPEAKER.

PRICE . . . including CRYSTAL MIKE and 1,200ft. reel of PLASTIC TAPE.

£49.10.0.

(OR £3 EXTRA WITH REV. COUNTER.)

*Plus £1.10/- carriage and insurance, of which £1 is refunded on return of Packing Case.)

BEFORE CHOOSING YOUR TAPE RECORDER YOU SHOULD HEAR THIS MODEL—TRULY "HI-FI" RECORDINGS ARE OBTAINABLE and it is comparable to much higher priced Recorders.
Alternatively send S.A.E. for ILLUSTRATED LEAFLET.

CREDIT SALE: Deposit £12.8- and 9 monthly payments of £4.10.8.
HIRE PURCHASE: Deposit £24.15- and 12 monthly payments of £2/5 11.

The "fidelity" TAPE AMPLIFIER Model HF/TR2 WITH POWER SUPPLY UNIT


PRICE **£16.0.0.**

(Carr. and ins. 6/-.)

H.P. TERMS: Deposit £8 and 9 months of a £1.

CREDIT TERMS:

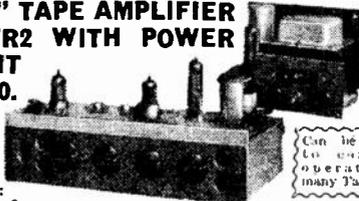Deposit £4 and 9 monthly payments of £1/8/4. When ordering, please advise make of deck in use. Send S.A.E. for full details.



Can be supplied to correctly operate with many Tape Decks.

The NEW TRUVOX MkIV TAPE DECK

THIS IS UNDOUBTEDLY ONE OF THE BEST TAPE DECKS ON THE MARKET. WE HAVE A FEW ONLY AVAILABLE.

PRICE (Plus 10/- carr. and ins.) **£27.6.0.**

EXCLUDING COUNTER CREDIT TERMS: Deposit £8 17- and 9 monthly payments of £2 10-.

H.P. TERMS: Deposit £13 13- and 12 monthly payments of £15 4.

WE ALSO HAVE A FEW DECKS WITH REV. COUNTERS. Price £30/0/-.

Send S.A.E. for details.



HOME CONSTRUCTORS

We can supply a COMPLETE KIT OF PARTS to build this TAPE AMPLIFIER for £12 (plus 5/- carr. and ins.). The Assembly Manual, Practical Diagrams, etc., are available for 2/6. WE MAKE SPECIAL PRICES TO PURCHASERS OF TAPE EQUIPMENT (i.e., buyers of Deck and Amplifier together, etc., etc.). . . SEND YOUR ENQUIRY TO US . . . H.P. and CREDIT SALE TERMS ARE AVAILABLE.

STERN RADIO LTD.

109 & 115, FLEET STREET, E.C.4
Tel.: FLEet 5812-3-4.

WEYRAD

"H" TYPE COILS— FOR MANUFACTURERS, SERVICE ENGINEERS AND INDIVIDUAL CONSTRUCTORS

A low-priced, soundly-designed Range of Coils, providing continuous coverage from 12 to 2,000 metres in 6 Bands.


The coils are supplied in individual aerial, H.F. transformer and oscillator versions for each band. Iron dust cores are adjusted by means of a threaded brass stem with a screwdriver slot which permits fine adjustment of inductance without the danger of damage to cores. Circuit connections are made to 4 tags at the end of the former. Single 6 B.A. mounting.

"H" type coils are recommended for many popular circuits including the "Practical Wireless" AC/DC 3-valve Superhet and are widely used for servicing and conversion purposes.

RETAIL PRICE.....**3/9** EACH

ILLUSTRATED FOLDER.....3d.

A.M./F.M. RECEIVER BOOKLET 2/6.

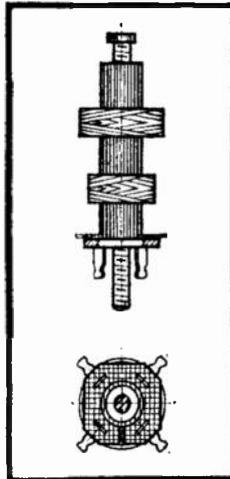

RANGES:

- Band 1—800-2,000 mtrs.
- Band 2—250-800 mtrs.
- Band 3—190-550 mtrs.
- Band 4— 90-250 mtrs.
- Band 5— 33-100 mtrs.
- Band 6— 16- 50 mtrs.
- Band 7— 12- 37 mtrs.

Coils are coded according to type and range:
HA 1=Band 1 aerial
HO 3=Band 3 oscillator

WEYMOUTH RADIO MANUFACTURING CO., LTD.
CRESCENT STREET, WEYMOUTH, DORSET

SUMMER SALE

STOCK OFFERED AT SENSATIONAL REDUCTION THIS MONTH

Superhet 5v. AC DC chassis. Medium and two short. Unused. Less valves. Uses standard octal range. Coil pack worth more. 27s. Carriage 6d.

Superhet 7 valve 5 waveband chassis. h.f. stage. Unused. Less valves & power pack. Slightly soiled. Coil pack worth twice as much. £2 15s. carriage and insurance 7s.

Rectifier Unit. EX Electric Supply Co. for working d.c. instruments, motorised equipment, etc. from a.c. mains. Power 200-240v. Output 200-240v. 25 amp. 35s. carriage 7s.

Rectifier Unit. as item above, but 2 amp. 25s. carriage 6s.

Rectifier Unit. as item above, but 10 ma. 20s. carriage 5s.

Filament Transformer. 200 primary, 2v. 5 amp. High voltage output. Secondary winding, so OK for tube filament 4s.

Filament Transformer. 600-11 amp. 230v. primary. 5s.

Transistor, new, tested. OK for I.F. 6s.

10v. Superhet 11 Metre. 14 Coils. Not unused. Complete with valves. Easily converted for Band III. 39 6s. carriage and packing 7s.

Germanium Diodes. 1001. With wire ends. 10d. each or 9s. doz.

Perspex Escutcheon for 12in. Tube. Embodies mask for tube, suits on 12in. cabinet. 0/6. post and insurance 2s.

12in. T.V. Cabinet by famous makers. Cost over £4 to make. 12s. carriage 1s.

Metal rectifier. 200-250, 60-80 ma. Ideal for mains set or instrument or to replace that expensive valve. 3s.

Superhet Coils. 1200 and medium. Aerial and oscillator circuit included. Per set 3s.

.0005 twin gang tuning condenser. 4/9. post 9d.

Midjet coils. Ideal for 60cm. x 3cm. cans with dust cores. 4s per doz.

Midjet I.F. Coils, dust covered, 1000 Hz. 465 Kcs. 5/6 per pair.

Standard size I.F. Coil. 0.5t. core. 495 Kcs. 4/6 pair.

Moving coil meter. 2 1/2in. full scale. Scaled 0-30 ma. 7/6 each.

Mullard 510. Output transformer. 27 6s. plus 2/6 post and packing.

Mullard 510. Mains transformer. 29 8s. plus 2/6 post and packing.

D.C. Rotary Converter. Doubles or halves voltage, e.g., 24v to 12v. or conversely. 45s. plus 3/6 carriage and insurance.

I.F. 25 Tuning Unit. New, unused and complete with valves. 9/6. post 2/6.

Hand magneto generator, as used on telephones. 9/6.

Powerful blower with motor, 24v. D.C. but can be operated off mains with rectifier. 15s. post and packing 2s.

As item above but with larger motor for 220v. 35s. post and packing 3s.

400 watt Step Down Transformer tapped output, 110-15v. 37 6s. carriage 6s.

500 watt Isolation Transformer. Mains in, mains out. (Make servicing safe.) 68 6s. post 5/6.

Coil pack for superhet 465 Kcs I.F. Medium and 2 short waves. 9 6s.

Fluorescent Tube 80 watt. Standard in all respects. Callers only. 8/6 each.

Fluorescent Tube 40 watt. See item above. 7 6s. each.

Fluorescent Tubes 20 watt. Standard in all respects. Callers only. 6/6 each.

Cathode Ray Tube, VCR 97. instrument type. 7 6s. each, carriage 3s.

Cathode Ray Tube, VCR 517. 8/6 each, carriage 2/6.

Where the value of your order for small articles exceeds £2, these are post free. Under £2 add sufficient to cover, and where carriage or postage specifically mentioned add this in any case.

.1 mfd. 350v. small tubular metal cased type, made by Duffiler. 2/6 per doz.

Welding Transformer. 12v. 50 amp. Continuous rating. Intermittent rating for spot welding 300 amps. Price 45s. carriage and packing 5s.

Mains Lead. Metal screened to stop interference. 8d. per yard.

10 core flexible cable. 230v. cores. Price 1 6s per yard.

7 core flexible cable 230v. cores. Price 1 3s per yard.

5 core flexible cable 230v. cores. Price 10d. per yard.

3-valve superhet chassis. Long and medium. Complete with valves. Unused but may need servicing. 25s. post and insurance 3/6.

Mains Transformer 250-0-250, 60-60 ma. 63v. Standard mains input. Half shrouded. 12 6s. post and insurance 2/6.

Many more bargains at all our branches. Please telephone before calling to pick up something special in case stocks have been cleared.

Precision Potentiometer 20k. ohms 10 watt, with large instrument knob. Price 8 8s.

Push Button Switch. 9 press. 2s. Knobs 11d. each.

50 assorted resistors. Well mixed and useful values, 1 and 1/2 watts. Price 5s. per 50.

50 assorted resistors. Well mixed and useful values. 1 watt. Price 6 6s per 50.

Cut-out in bakelite case. Suit C-12v. or 24v. Price 7 6s.

Automatic D.C. motor starter for remote control of motors or D.C. gear between 1 to 3kw. 110v. or 230v. £4s. carriage 7 6s.

Check meter. Movement only, made by Ferranti. New and unused. 7 6s. post and insurance 2/6.

Wire welder. Efficient hand grip tool with trigger switch, operates from 40 a.c. Price 4 8s.

Rotary switch, as used for hair driers, etc., 10 amp. 1/9 each.

Bakelite 5 amp electric wall switch. "Herafit". 9d. each or 8s. per dozen.

As item above, but two-way. Price 11d. each, or 10s. per doz.

Series, parallel and off-electric wall switch made by Crabtree. Price 1/3 each or 13/6 per doz.

25 amp switch plug made by Clix. Price 6/6.

5 amp 3 pin plug socket Herafit. 1s. each or 10s. per doz.

Vacuum pump, makes good compressor. Price 22 6s.

Hydraulic pump, creates immense pressure, motorised but 24v. Price 35s. carriage 7 6s.

Amplifier, ex-Government unit 100 contains one double triode and one triode. 6 6s. post and insurance 2/6.

Battery re-activator. If you use a battery portable this will save you pounds, operates from A.C. mains. 25s. post and insurance 2/6.

Thermion couple mounted on valve base, useful for experiments and schools. 6 6s. each.

Head-phones, lightweight American type HS 30. 22 6s. pair.

Check case, modern flat type (Movement exposed). 2 6s.

Midjet push-pull input transformer, and push-pull output transformer to match. 8s. the pair.

Octagonal speaker enclosure as specified by the G.E.C. for the metal cone, also suits any 8in. speaker, beautifully made but not polished. £5. Carriage and insurance 10s.

ELECTRONIC PRECISION EQUIPMENT, LTD.

Post orders to E.P.E., LTD., Dept. 7, Sutton Road, Eastbourne.

266. London Road, Croydon
Phone: CRO. 653
Half day, Wednesday.


42-46. Windmill Hill, Ruislip, Midds.
Phone: RUUSLP 5789
Half day, Wednesday.

152-3. Fleet Street, E.C.4.
Phone: FLEET 2833
Half day, Saturday.

29 Strand Green Rd., Finsbury Park, N.4.
Phone: ARCHWAY 1049
Half days, Thursday.

249. Kilburn High Road, Kilburn.
MAIDA VALE 4921.

MAXI-Q

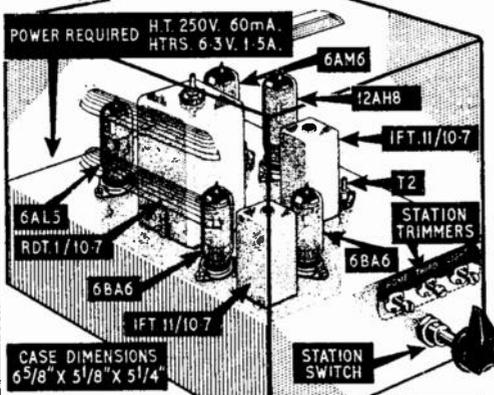

PRE-SET F.M. TUNER

STOP PRESS: "MAXI-Q" 60 kc s TAPE DECK OSCILLATOR COILS. TDO.1 - for high impedance Erase Heads (Truvox etc.), 5/-; TDO.2 - for low impedance Erase Heads (Brenell and Collaro), 5/-; *Trading Terms for direct Postal Orders. C.W.O. plus appropriate postal charge.*

V.H.F./F.M. HOME, LIGHT AND THIRD PROGRAMMES INSTANTLY SELECTED AT THE TURN OF A SWITCH

Full constructional details, point-to-point wiring diagrams and alignment instructions for building the "MAXI-Q" PRE-SET F.M. TUNER and also the VARIABLE TUNED version are given in Technical Bulletin DTB.8, 1, 6. Completely punched Chassis, Screens and Bronze finished Cover, 19. Station Indicator Plate, 1/1. 3-position Switch, 4.3. Station Condenser Trimmers, 3.9 pF. 2/- each. Complete set of RESISTORS and CONDENSERS for either version, 48/-.

RATIO DISCRIMINATOR TRANSFORMER, RDT. 1/10.7 Mc/s. Secondary winding of biñlar construction, iron dust core tuning, polystyrene former, silver mica condensers. Can size: 1in. sq. x 2 1/2in. high, 12.6.

I.F. TRANSFORMER, IFT. II/10.7 Mc/s. Miniature I.F. Transformer of nominal frequency 10.7 Mc/s. The "Q" of each winding is 90 and the coupling critical. Can size: 1 1/2in. x 1 1/2in. square, 6.6.

COILS TYPE L1, T1 and T2. Specially designed for use in this unit, are wound on polystyrene formers complete with iron dust core tuning, 3.11 each.

THE "MAXI-Q" PRE-SET F.M. TUNER, is available completely wired, assembled, valved and housed in a sturdily made bronze finished cover at £8.11.5, plus £3.8.7 P.T., total £12.0.0.

VARIABLE F.M. TUNER completely assembled, £11.0.0 including P.T. (carriage 3/-, terms c.w.o.).

GENERAL CATALOGUE covering technical information on full range of components, 1 - post free.

WORKS HOLIDAYS - GOODS CANNOT BE DESPATCHED FROM 27/7 TO 11/8/57.

DENCO (CLACTON) LTD.
(DEPT. P.W.) 357/9 OLD ROAD,
CLACTON - ON - SEA, ESSEX

PREMIER RADIO COMPANY

B. H. MORRIS & CO. (RADIO) LTD.

OPEN TILL 6 P.M. SATURDAYS

(Dept. P.W.8) 207, EDGWARE ROAD, LONDON, W.2


Telephone: AMBASSADOR 4033 PADDINGTON 3271-2

BUILD THESE NEW PREMIER DESIGNS

2-BAND T.R.F. RECEIVER

MAY BE BUILT FOR **£5.15.0** Plus 3/- Pk. & Post.

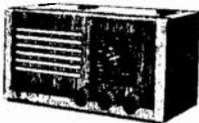3-Band Superhet Receiver may be built for **£7.19.6** plus pk. & carr. 3/-. These two receivers use the latest type circuitry and are fitted into attractive cabinets 12in. x 6 1/2in. x 5 1/2in. in either walnut or ivory bakelite or wood. Individual instruction books 1/- each, post free.



MULLARD AMPLIFIER KIT


Why not make the Best!

All the components for model 510, PLUS preamplifier on one chassis (total six valves) may be purchased for £12.12.0 plus pkg. & post 7/6, or preamplifier and tone control in a separate unit, £14.14.0 plus pkg. & post 7/6.

NOW SUPPLIED WITH ULTRALINEAR OUTPUT TRANSFORMER

Send for the Premier WIDE ANGLE TELEVISOR booklet, 3/6 post free.

Introducing the PETITE PORTABLE!

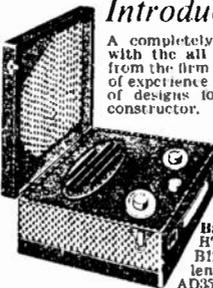

A completely new design with the all star feature from the firm with 45 years of experience in the supply of designs for the home constructor.

MAY BE BUILT FOR **£7.7.0** plus p. & p. 3/-

Batteries Extra HT 10 - (Type B126) or equivalent. LT 1 6 (Type AD35) or equivalent.

- ★ Size only 8in. x 8in. x 4 1/2in.
- ★ Weight, including Batteries, 5 1/2 lbs.
- ★ 4 Valves of the economy type.
- ★ Medium and long wave superhet circuit.
- ★ High Q Frame Aerials.
- ★ High sensitivity on both wavebands.
- ★ Prealigned I.F. Transformers.
- ★ 5in. Speaker of the latest type.
- ★ Automatic on/off switch operated by lid.
- ★ Components available separately, if desired.
- ★ Simple to construct, using normal soldering methods.
- ★ Mains Unit will be available later. Instruction book 1/6.

4-WATT AMPLIFIER

MAY BE BUILT FOR **£4.10.0** Plus 2/6 Pkg. & Carr.

Instruction Book 1/- post free. A steel case is now available, complete with engraved panel, for 15/6 extra. The amplifier may be supplied complete for £5.5.0 plus pkg. and post 3/6, or fitted in case at £6 plus pkg. and post 3/6. Engraved panel 3/6. Post free.


A NEW TAPE RECORDER

CREDIT TERMS: DEPOSIT £5 and 8 monthly payments of £4.18.6

H.P. TERMS: DEPOSIT £20 and 12 monthly payments of £1.17.1

Cash price £40 plus packing and carriage 2/-. Case finished in Brown and Antique Fawn. Size 15in. x 12 1/2in. x 7 1/2in. with the very latest type Continental fittings. For A.C. Mains 200-250 volts, 50 cycles. **SEND FOR LEAFLET**

COMPACT GRAM AMPLIFIER

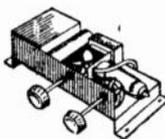

Suitable for any type of Pick-up Volume and tone control fitted with knobs. Overall size 7 1/2in. long x 3 1/2in. wide x 2 1/2in. high. Complete and ready for use.

£2.19.6

Plus packing & postage 2/6.

GRAM UNITS

B.S.R. 4-Speed Autochanger. £9.15.0 plus 5/- pkg. & post.
B.S.R. TUS 3-Speed £4.12.6 plus 2/6 pkg. & post.

PRACTICAL WIRELESS

EDITOR : F. J. CAMM

25th YEAR
OF ISSUE

BY THE EDITOR

EVERY MONTH
VOL. XXXIII, No. 608, AUGUST 1957
COMMENTS OF THE MONTH

PORTABLE V.H.F. AND CAR RADIO SETS

THE D.G. of the BBC, in an address to the Radio Industry in a speech to the R.I.C. of Scotland, said that the Radio Industry had been tardy in developing portable V.H.F. sets and car radio V.H.F. sets. He stated that he had seen excellent German portable V.H.F. sets five years ago, and by this time there should be many on the market in Britain. He said that the BBC had been ready to build V.H.F. transmitters immediately after the war, but had been prevented from doing so by financial policy of successful governments. What would have been the purpose of the industry producing V.H.F. sets before the BBC transmitters were ready? There are only comparatively few areas in this country where V.H.F. would have brought any benefit, and it was not to be expected that people would scrap existing receivers giving reasonably good quality reproduction and purchase V.H.F. receivers. Sir Ian here, however, was putting the cart before the horse. The industry is in business to make money. Its own market research, however, showed that there was little likelihood at the time of the public responding to a campaign to sell V.H.F.

THE RADIO SHOW

NEXT month's issue, on sale August 7th, will contain a preview of this year's show at Earls Court, which takes place from August 24th to September 7th. A cordial welcome is issued to all readers to visit us on our Stand No. 117.

THE NEW BBC CHAIRMAN

THE Headmaster of Rugby is to be the new chairman of the BBC governors and we hope he will be permitted to exercise greater authority than some of his predecessors have been enabled to do. In Reith's time the job was a sinecure, merely to comply with the terms of the Charter. Reith seemed to make the decisions. His notes to the staff commenced: "The Director-General has decided . . ." It seems to us that the Director-General should be there to carry out the decisions of the Governors.

WELSH RADIO STATION

A POST Office radio station is now being used to link the two BBC Welsh transmitters, in order to skip the Welsh mountains. Signals from the Wenvoe transmitter near Cardiff are received at the P.O. microwave station at Mynydd Pencarreg, near Lampeter, and are relayed to the new BBC West Wales Television transmitter at Blaen Plwy, near Aberystwyth. During the early stages of testing a "ghost" was seen on the picture transmissions, apparently caused by a cliff face on the 2,900 feet Brecon Beacons, situated some 6½ miles laterally from the direct path from Wenvoe. The unwanted image was eliminated by installing an aerial arranged so that it would not pick up reflections from the Brecon Beacons. F.J.C.

Our next issue, dated September, will be published on August 7th.

Editorial and Advertisement Offices : PRACTICAL WIRELESS

George Newnes, Ltd., Tower House,
Southampton Street, Strand, W.C.2.
Phone : Temple Bar 4363.
Telegrams : Newnes, Rand, London.
Registered at the G.P.O. for trans-
mission by Canadian Magazine Post.

SUBSCRIPTION RATES

including postage for one year
Inland - - - 18s. per annum.
Abroad - - - 16s. 6d. per annum.
Canada - - - 16s. per annum.

CONTENTS :

	Page
Editorial	365
Round the World of Wireless	366
A Mains T.R.F. Short Waver	368
Stereophonic Tape Recording	371
Making an Output Indicator	375
A Beginner's Short Wave Three	377
Four-valve Midget Portable	381
An Amateur Communications Type Receiver	385
A Simple Test Probe	389
An F.M. Feeder Unit	391
A Car Radio	397
Transmitting Topics	405
Radio and Automation	413
Open to Discussion	417
Programme Pointers	418
Trade News	421

The Editor will be pleased to consider articles of a practical nature. Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them in a stamped and addressed envelope if enclosed. All correspondence intended for the Editor should be addressed to: The Editor PRACTICAL WIRELESS, George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Owing to the rapid progress in the design of wireless apparatus and in our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in PRACTICAL WIRELESS is specifically reserved throughout the Commonwealth and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. PRACTICAL WIRELESS incorporates "Amateur Wireless."

Round the World of Wireless



By "QUESTOR"

Broadcast Receiving Licences

THE following statement shows the approximate number of Broadcast Receiving Licences in force at the end of April, 1957, in respect of receiving stations situated within the various Postal Regions of England, Wales, Scotland and Northern Ireland. The numbers include licences issued to blind persons without payment.

Region	Total
London Postal	1,172,439
Home Counties	1,171,933
Midland	895,918
North Eastern	1,164,715
North Western	872,509
South Western	737,992
Wales and Border Counties	464,228
Total England and Wales	6,479,734
Scotland	836,150
Northern Ireland	193,124
Grand Total	7,509,008

New Anglo-American Company

THE formation of a new company to manufacture transistors and other semi-conductors in England was announced recently in London. To be known as Semiconductors, Ltd., the new company has been formed by The Plessey Co., Ltd., and Philco Corporation of U.S.A.

This joint enterprise, which is likely to have a considerable bearing on the development of the transistor industry in this country, was undertaken following a comprehensive survey of the electronic industry in the United States.

This new Anglo-American company will have an initial paid-up capital of £500,000, of which 51 per cent. will be held by The Plessey Co., Ltd., and the remaining 49 per cent. by Philco Corporation.

The joint board of directors will be as follows: A. G. Clark (chairman), J. M. Skinner, Jr., J. F. Mallabar, L. J. Woods, A. E. Underwood and P. Marriage.

Pye for U.K. Atomic Energy Authority

PYE, LTD., are designing and supplying all the equipment for a laboratory for the Atomic Energy Authority at Dounreay, in which irradiated fuel elements from the Dounreay fast breeder reactor are to be examined.

The equipment to be supplied includes manipulators, universal

cutting machines, lathe, furnaces, X-ray and density measurement, inspection and material testing machines, optical and TV viewing facilities, and all the associated handling and shielding equipment: in fact, the complete laboratory, except for the concrete structure, is being supplied by Pye, Ltd.

Owing to the highly radioactive nature of the elements, which can only be handled by remote control, the laboratory is a cave of U-shaped form—a concrete cave with an area of 1,100 square feet. To form a biological shield, the walls of the cave are 4ft. 6in. thick, partly lined with steel.

For observation of the processes inside the cave there are windows at intervals in the dense concrete walls. These windows are composed of glass-walled tanks containing a saturated zinc-bromide solution, thus providing a shield from radioactivity equal to that of the walls, and at the same time permitting observation of all the processes. At each window, facilities are provided for Pye Master Slave Manipulators for remote handling of the elements. Pye manufacture these manipulators by agreement with AMF

Atomics, a division of the American Machine and Foundry Co.

Marconi Radio for B.O.A.C. Britannias

B.O.A.C. has ordered Marconi radio equipment for its fleet of Series 312 long-range Bristol Britannias, some of which are expected to be in passenger service in a few months' time. Each aircraft will have a dual Marconi transmitter/receiver installation for multi-channel H.F. communication, a high discrimination receiver and a dual radio compass.

The communication equipment, Type AD.307, is a multi-channel high-power transmitter/receiver, particularly suitable for pilot-operated radiotelephony. It is simple to operate; any one of 200 crystal-controlled channels can be selected, frequency changing being entirely automatic by self-tuning circuits. The equipment, which is

built in unit form to fit the standard aircraft racking, conforms to S.B.A.C. standards and meets all British Civil Airworthiness requirements. It is remotely controlled from two positions.

The receiver, Type AD.118, is intended for direct control only and is provided with a high discrimination scale. Particular attention has been devoted to obtaining a high degree of electrical and mechanical stability so that full use can be made of the high discrimination without constant scale checking.

Solartron to Manufacture Gunnery Trainer

AS a result of arrangements finalised by Mr. John E. Bolton, chairman and managing director of The Solartron Electronic Group, Ltd., Thames Ditton, Surrey, during his recent visit to the United States, Solartron will manufacture under licence in Britain the Rheem F.151 Gunnery Trainer.

The agreement is with the Electronics Division of the large Rheem manufacturing company of New York, whose many factories are spread out over the United States and several continents. This Division specialises in electro-mechanical equipment.

The gunnery trainer gives a full three-dimensional target representation in colour and is in many respects comparable to the Solartron Radar Simulator. The latter enables full-scale tactical radar naval, land or air exercises to be carried out without involving the heavy expenses of full-scale tactical exercises. The gunnery trainer, like the radar simulator, may be attached to a flight simulator.

The Late John V. Palmer

THE news of Mr. J. V. Palmer's recent death was received with sincere regret by his many friends at Mullard, Ltd.

John Palmer, who was 69, was for many years Manager of the Valve Division of Mullard Overseas Ltd., and contributed materially to its leading position in the export field to-day.

Joining the company in June, 1925, Mr. Palmer was appointed valve export Manager in 1926.

His ex-colleagues wish to associate themselves with the grief that will be felt by his family and numerous friends in and outside the industry.

At the funeral, the company was represented by three directors, Mr. S. R. Mullard, Mr. A. W. Welton and Mr. W. Benink, and other senior executives and former colleagues from the company attended.

Radio and TV Sales Recovery Maintained

RETAILERS' sales of radio and television sets and radiograms were higher all round in the first four months of this year than in corresponding period of 1956, according to the monthly retail

and credit sales, 53 per cent., for both radiograms and television receivers in March, fell to 50 per cent. and 52 per cent., respectively, in April. For radio receivers the percentage rose from 33 per cent. to 35 per cent.

BBC V.H.F. Station at Rowridge
THE BBC's new V.H.F. sound broadcasting station which has been built on the same site as the television station, at Rowridge, Isle of Wight, transmits the West of England Home Service on 92.9 Mc/s, the Light Programme on 88.5 Mc/s, and the Third Programme on 90.7 Mc/s, each with an effective radiated power of 60 kW. The transmissions are

On their stand of over 2,000 square feet, Pye showed a wide range of exhibits, including television transmission equipment for studio and industry, and fixed and mobile V.H.F. communications equipment.

Creation of an International Association of Cybernetics

THE First International Congress of Cybernetics, which was held at Namur from June 26th to 29th, 1956, met with a great success as much because of the number of participants as because of the quality of the work presented.

At the close of the Congress, it was decided to create an International Association of Cybernetics. The latter was constituted at Namur on January 6th, 1957. It counts at present over 1,000 members (of which 300 industrial firms), representing 26 different countries.

The aim of the Association is to ensure a permanent and organised liaison between researchers whose work in various countries is related to different sectors connected with Cybernetics.

It endeavours to promote the development of this science and of its technical applications, as well as the propagation of the results obtained in this field.

It utilises all adequate means for the achievement of these objects.

All enquiries should be sent to the Permanent Secretariate of the Association: 13, rue Basse-Mareille, Namur (Belgium).

Pye Multi-Channel Equipment for Venezuela

A CONTRACT for the supply of a six-channel radio-communication system has been awarded to Pye Telecommunications, Limited by the Socoony Mobil Oil Company de Venezuela. The system will be installed between the company's administration offices in Anaco and the oil field at Guico, a distance of approximately 25 miles.

The equipment will provide the company with a trunk connection between private automatic telephone exchanges at each terminal by means of a V.H.F. multiplex radio link. This link provides six telephone circuits, plus an engineers circuit simultaneously over a single pair of radio frequencies, and consists of Pye V.H.F. 50-watt F.M. transmitters and F.M. receivers at each exchange.

The new link will be connected into the public exchange at Anaco.



Testing the "Tellurimeter"—a micro-wave measuring instrument. It is claimed that this has an accuracy of 2in. to 6in. over distances ranging from 10 to 30 miles.

survey of the British Radio Equipment Manufacturers' Association—radio sets by 21 per cent., television receivers by 20 per cent. and radiograms by 42 per cent.

Retailers' sales of television receivers during April were 66,000, an increase of 6 per cent. on April, 1956, but a decrease on the previous month of 16 per cent. Sales of radiograms were 14,000, the same as in April, 1956, but a decrease of 30 per cent. on March this year. Radio receiver sales, at 78,000, showed an increase on April, 1956, of 20 per cent., but a decrease on the previous month of 6 per cent.

The proportion of hire purchase

horizontally polarised as at other V.H.F. sound broadcasting stations, which means that receiving aerials must be fixed horizontally.

The area served by this station has a population of nearly three million. It includes the counties of Hampshire and Dorset, most of Wiltshire, and substantial parts of Somerset, Berkshire, Surrey and Sussex.

Pye at the Poznan Fair, 1957

FOLLOWING their success at the Leipzig Spring Fair, in March, Pye, Limited, launched another export drive in Eastern Europe when they exhibited at the Poznan Fair in Poland in June.

A Mains T.R.F. Short Waver



By R. Crompton

THIS receiver was built primarily for use on wavelengths of 10-180 m. and is a fairly conventional T.R.F. type (Fig. 1)—6D6 (R.F.); 6SJ7 (Det.); 75 or 6SQ7 (L.F.); 42 or 6F6 (O.P.).

Denco cored coils plugging into Noval holders are used. They have proved most satisfactory in the prototype. Regeneration is controlled by varying the screen grid voltage of the detector valve and is smooth and silent.

Construction

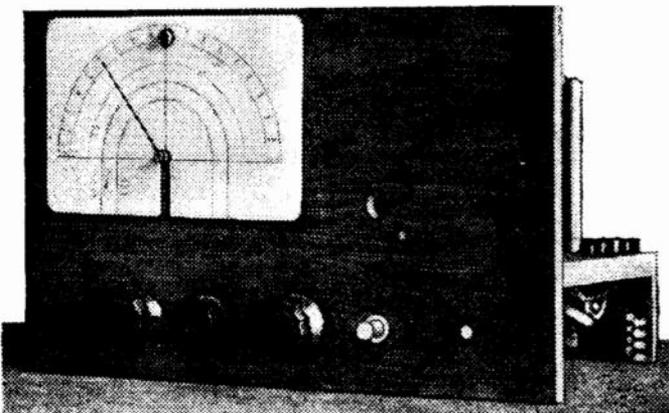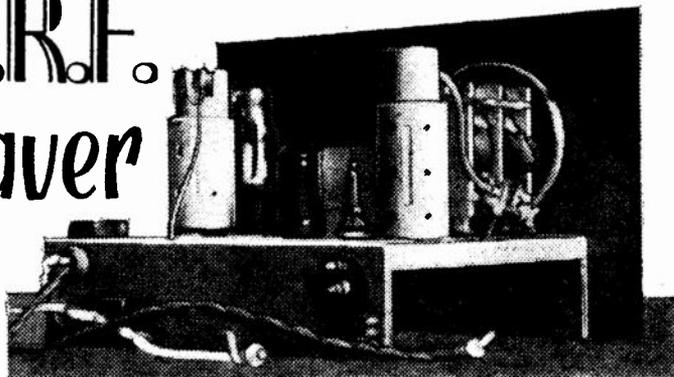The receiver is built on an aluminium chassis 10in. x 8in. x 2½in. (The power pack is separate.) All construction must be absolutely firm or frequency stability may be poor.



Three-quarter front view of the set.

Chassis drilling dimensions are given in Fig. 3, but the mounting of the gang capacitor is not shown since this depends on the type used by the constructor. The keyways of octal holders or the heater pins of UX6-type sockets face the rear runner of the chassis, with the exception of the keyway of the output valve which points towards the front right-hand corner of the chassis. The locators on the Noval holders face the gang capacitor.

LIST OF COMPONENTS

C1, C6—300 pF gang with ceramic insulation.
 C2, C7—30 pF ceramic trimmers.
 C3—0.1 μ F paper 200 v.
 C4, C5, C11—300 v. 0.1 μ F paper.
 C8, C9—100 pF mica or ceramic.
 C10—500 pF mica.
 C12, C13, C16—8 μ F 300 v. electrolytic.
 C14—0.05 μ F 500 v. paper.
 C15—25 μ F 12 v. electrolytic.
 C17—0.01 μ F 500 v. paper.
 C18—25 μ F 25 v. electrolytic.
 C19, C20—0.01 μ F 500 v. paper.
 C21, C22—8 + 8 μ F 450 v. electrolytic.

R1—600 Ω
 R2—20 K Ω wirewound pot.
 R3, R8, R15—100 K Ω
 R4, R12—1 K Ω
 R5—2.2 meg Ω .
 R6, R7—10 K Ω .
 R9—5 K Ω .
 R10—50 K Ω carbon pot. (Dubilier).
 R11—75 K Ω .
 R13—0.5 meg Ω .
 R14—2,200 Ω .


R16—20 K Ω .
 R17—0.22 meg Ω .
 R18—470 $\Omega \pm 10\%$ 1 watt.
 (Resistors $\pm 20\%$, ½ watt, unless otherwise stated.)

Valves

6D6, 6SJ7, 75, 42, and holders.
 NR1, MR2, 250 v. 60 mA metal rectifiers (2 DRM1 B's.).
 MT1 250-0-250 60 mA 6.3 v. 2.5 A. Tapped primary.
 Two UX6 valve screens and bases.
 2—Noval holders.
 M.E. speaker 600-1,000 Ω field 3 Ω ; with transformer to match 7,000 Ω to 3 Ω (85 : 1).
 Aerial-earth terminals, L.S. and 'phone sockets (preferably non-interchangeable), plugs and sockets for power pack.
 SW1, 250 v. 1 A toggle or "push-push", SW2, SW3.
 1—70 mA fuse, 1—2.5 A. fuse + holder.
 2—Dial bulb; 6.5 v. 0.3 A.
 ¼-in. dia. drive drum, cord and pulley to give 15 : 1 ratio.
 10in. x 8in. x 2½in. chassis.
 Nuts, bolts, wire, etc.

Wiring

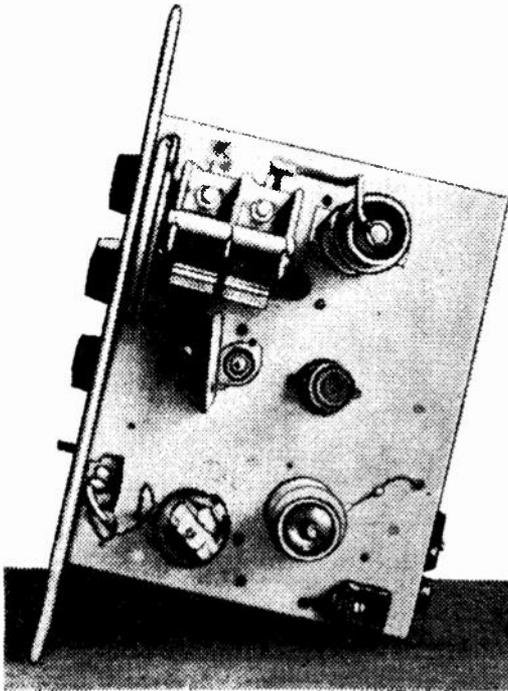Wiring of the heaters should be carried out first. Use twin flex and keep it close to the chassis. After this, any order of wiring may be used, but some



Another view of the receiver.

methodical system is preferable. Note that the grid capacitor of the L.F. valve is clipped to the rear runner of the chassis. All screened wiring shown on the

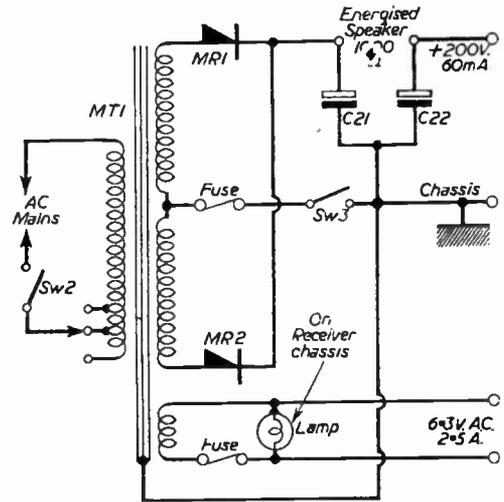


Fig. 2.—The power pack.

circuit diagram was carried out in coaxial cable which has low capacity losses. A 2in. long x 3in. high aluminium screen is mounted between the coil holders and a similar screen will be required for the trimmers if they are not within the screening of the gang capacitor itself. The medium-wave green coil has a 4 K Ω resistor across pins 3 and 4. Care is essential when soldering this.

Power Pack

The construction of the power pack is straightforward and needs little comment. Do not omit the H.T. switch and use it when changing coils. When the receiver and power pack have been completed and the wiring checked, plug in the medium-wave coils and attach 8ft. or so of wire to the aerial terminal.

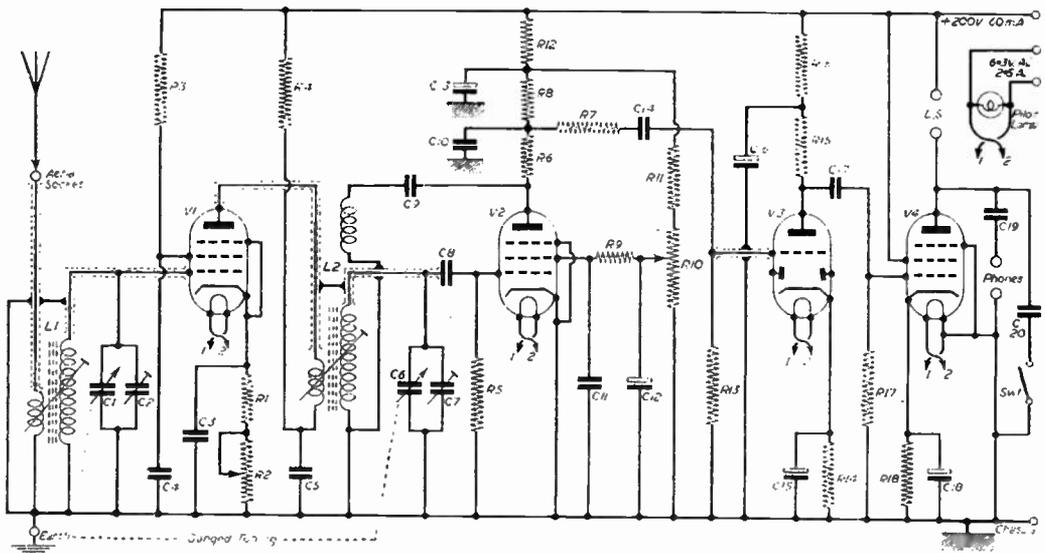


Fig. 1. Theoretical circuit of the Mains T.R.F. Short Waver.

Adjustment

Adjust the trimmers to minimum capacity with a non-metal tool, and screw the coil cores fully out. Tune a signal to zero-beat at the high-wavelength end of the scale and adjust the core of the blue coil to give maximum signal (it is best to turn the regeneration control back a little). If there is not a noticeable "peaking" of the signal, screw in the cone of the green coil a few turns and repeat. Then turn to the low wavelength end of the band and tune another signal to zero-beat. If the cone of the blue coil must be screwed in, increase the capacity of the R.F. trimmer; if it must be screwed out, increase the capacity of the det. trimmer. Repeat the whole process until the core of the blue coil needs no adjustment (or very little) at any part of the band. The stray capacities of the det. and R.F. circuits are now balanced and on other bands it is necessary only to adjust the coil cores.

Considerable benefit may be derived from tuned aerial systems such as dipoles on the short waves. Even a simple link coupling tuner on the writer's long wire

aerial gives an appreciable reduction in ignition noise on 20 metres.

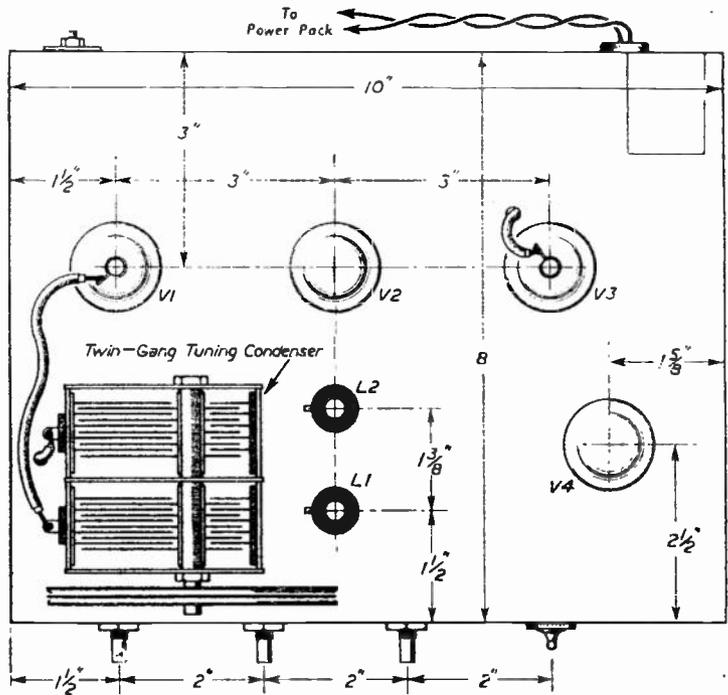


Fig. 3.--Details of the chassis and layout.

Machine for Printed Circuits

A NEW semi-automatic screen printing machine was the highlight of the demonstration of radio and electronic circuits printed by the screen printing method arranged by Gordon & Gotch Ltd. at Trapnax Works on May 23rd.


The machine is the SPS Model 90A which has been specially designed by the manufacturers for the production of printed circuits.

The machine has been specially designed to incorporate an extremely powerful suction over a relatively small area.

The printing base on the machine has a total of 10,000 special apertures. These are connected to an extremely efficient suction system from the vacuum turbine. This is capable of completely flattening material which is in a bowed condition.

This machine for producing printed circuits is equipped with an accurate precision micrometer with an adjustment of 1/16 in. in every direction. The height adjustment is up to 3 1/2 in. The electrical foot switch on the machine is entirely movable and can be placed in any desired position to suit the operator. This means that one person can operate the machine no matter what the job.

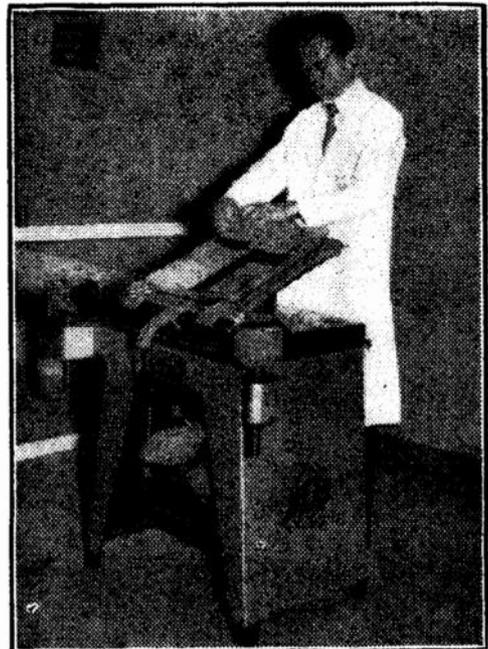SPS screen printing machinery and equipment is manufactured by the Siebdruckgerate von Holzschuher KG, of West Germany. Sole agents in the United Kingdom and Republic of Ireland for the SPS range are Gordon & Gotch Ltd., 39-40, Farringdon Street, London, E.C.4.



An operator printing a circuit on a laminated insulated sheet by means of a screen-printing process.

ust be perfectly synchronise 1, which is not a practical oposition under such conditions, so the obvious ay is to put both recordings side by side on the same pe. This appears to be reasonably simple—a order comprising one tape deck and two amplifiers. This basically is all it does mean, but unfortunately there are several things that do not work at quite as simply as they should.

Although I intend describing my own recorder I el that the majority of readers may have their own

another. Unfortunately this caused interaction between the two amplifiers, but was overcome by decoupling in the smoothing arrangement as shown in the circuit diagram. The two oscillators were tuned to the same frequency but at times there was a certain amount of drift and, finally, I settled on one oscillator only. This did not cause too much interaction during recording as might have been expected. The two erase heads were replaced by one covering the full width of the tape. Balancing was effected by

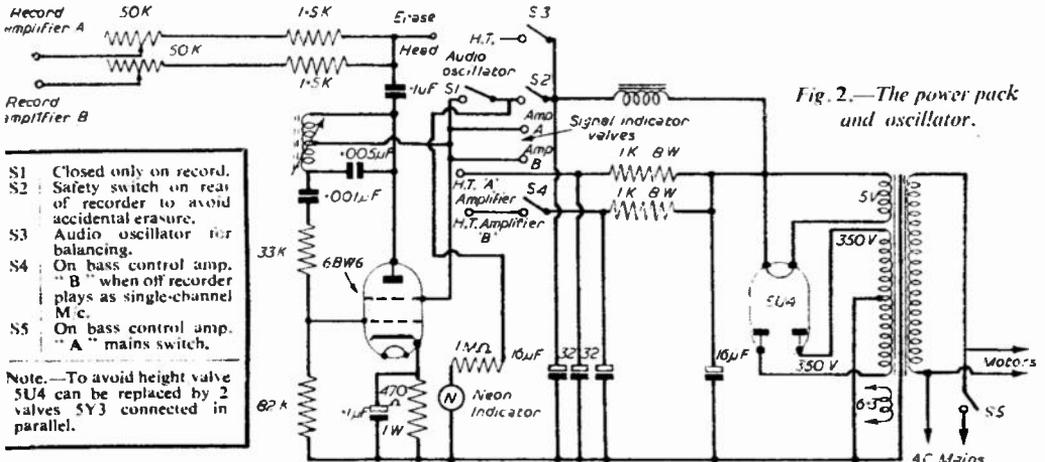


Fig. 2.—The power pack and oscillator.

- S1 Closed only on record.
 - S2 Safety switch on rear of recorder to avoid accidental erasure.
 - S3 Audio oscillator for balancing.
 - S4 On bass control amp. "B" when off recorder plays as single-channel M.c.
 - S5 On bass control amp. "A" mains switch.
- Note.—To avoid height valve 5U4 can be replaced by 2 valves 5Y3 connected in parallel.

leas as to the amplifier circuits and certain modifications in switching thus expanding the uses for the recorder to their own requirements. Bearing this in mind I would first like to discuss some of the problems experienced in the development of my own machine and how I was able to solve them.

My first attempt was not exactly spectacular. I bought two well-known amplifiers and a tape deck and fitted them into a large cabinet with two speakers forming a lid, removed the head assembly from the tape deck and fitted two record playback heads and two erase heads. This arrangement gave me my first stereophonic recordings but was far from satisfactory. It was too large and heavy for one person to carry. The mains hum was bad. Although the two recording amplifiers were independent there was interaction between them, resulting in a low-pitched whistle on the tape. Finally, there was no method of balancing the two amplifiers to give equal output on playback.

Size, perhaps, was the easiest difficulty to combat. As each other difficulty was overcome the size automatically became reduced. One power pack to supply both amplifiers cured most of the hum and it was eventually brought to a minimum by building both amplifiers on one chassis and the power pack on

the addition of an audio oscillator which could be fed to the input of both amplifiers and the resulting signals measured at the output of each by means of a meter. By use of a peak signal indicator in the first amplifier the volume could be set for recording in the usual manner employed in a single-channel recorder and, by the method just explained, the second amplifier could be set to record at equal volume.

Finally I decided once more to completely rebuild the recorder and build it up in the form it is today. The amplifiers were rebuilt on one small chassis and fitted on its side along the front of the tape deck. All the controls are fitted to a panel level with the tape deck itself and have been kept to a minimum. Separate volume, treble and bass controls are provided for each amplifier but all other switching is synchronised into a 10-button selector unit. Pressing the "play tape" button, for example, connects both amplifiers for playback, starts the motors running and completes the circuits for the speakers. All valves were replaced by modern miniature types.

As regards the circuits themselves very little need really be said as can be seen from the diagram. Switching could be reasonably simplified by con-

Switch functions in the circuit, Fig. 1.

Switches are normally open and in some cases contacts earthed. They are closed for the following purposes.

S1	Playback of tape.	S7	Gram or radio for recording.
S2	Balancing for playback.	S8	Amplifying gram or radio.
S3	Recording.	S9	Playback of tape amplifying gram or radio.
S4	Playback of tape.	S10	Switch located on rear of recorder for use of internal speaker.
S5	Balancing for recording.	S11	Balancing for recording and playback.
S6	Microphone for recording.		

trolling each item separately but this, however, would complicate operation. The press button is therefore the answer. At this point, may I say that as such a press-button unit is not on the market, two surplus units were purchased and adapted for this use. The "off" button is entirely mechanical as it only trips the "hold bar" and releases any other button which has previously been pressed down. The stop button is separate from the rest as it only applies D.C. to the motors bringing the tape to a standstill before the "off" button is pressed. Much trouble was caused through feedback in this unit but it was finally overcome by careful positioning of contacts and earthing of circuits which were not being used. Buttons are clearly marked with transfers and are mounted in a perspex panel which shows a diffused light when the main switch is on. They are marked as follows:

OFF --- BALANCE PLAY --- BALANCE RECORD --- PLAY GRAM --- PLAY TAP! --- RECORD MIC. --- RECORD GRAM. --- FAST FORWARD --- FAST REVERSE --- STOP.

Amplification in the first stage of each amplifier differed considerably due to tolerances in component values, and as these are only used for playback, it became necessary to have two balancing positions. For "Balance record," therefore, the balancing signal is fed to the grids of parts "B" of the 12AX7 valves and for "Balance play" to the grids of parts "A." As an extra stage of amplification is employed in the latter position, a reduced balancing signal is tapped off from a pre-set potentiometer.

The power pack chassis is fitted underneath the tape deck and includes the oscillator circuit for recording and the audio oscillator for balancing. All

connections between tape deck, amplifiers and power pack are by means of octal plugs and sockets. It will be noticed that two rectifiers have been used in parallel, but this is simply to save height. Resistance smoothing has been used for the amplifiers and choke for the oscillator.

Remaining Controls

The few remaining controls not already mentioned are on the back of the power pack chassis which are readily accessible from the back of the recorder. These consist of an on off switch for the internal speakers and a safety switch cutting the H.T. from the oscillator to avoid accidental erasure. A neon is employed to give indication when this safety switch is closed. Mains input socket, microphone sockets and various other inputs are also placed at the rear of the recorder. There is also a switch on the tape deck for "normal" or "stereophonic" reproduction. A dual meter has been fitted for signal level indication on both amplifiers during recording. As previously described one only is used for setting the volume controls, but during actual recording it is useful to be able to see what is going on on both channels at the same time. The tape deck has been completely rebuilt. Whilst two record-playback heads are quite satisfactory for making recordings and playing them back on the same machine, it must be remembered that the pre-recorded tapes on the market are recorded with the two tracks in line, one immediately above the other, and, therefore, a special head must be used for playing them. This type of head is rather expensive and could be added at a later date. Having two heads it will follow that one track will be at least the diameter of the head behind the other. Personally, I found the purchase of a "stacked" head was money well spent

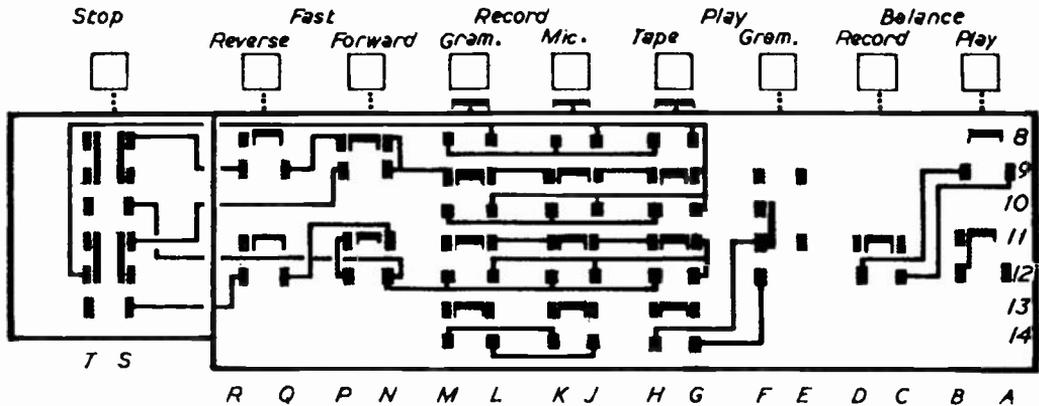


Fig. 3. - Press-button unit with buttons in "off" positions. View from top of amplifier chassis.

A9	H.T. audio oscillator.	M8	Capstan motor resistance.
A12	Potentiometer audio oscillator.	M10	Take up motor resistance.
B9	H.T. audio oscillator.	M14	H.T. supply for record oscillator.
B11	Contact G2.	P9	Take up motor resistance.
G14	Speaker amplifier "B"	S9	Rewind motor.
H14	Earth.	S12	Take up motor.
J14	H.T. peak signal indicator valves.	T8	Mains.
K14	Neon.	T9	Common motor supply.
L12	D.C. braking supply.	T10	Earth.
L14	H.T. record oscillator.	T11	Mains.

as the pre-recorded tapes are exceptionally good and the first one I bought was a great help to me in my experiments. The complete recorder now measures 17½in. × 15½in. × 7½in.

Two speakers built in separate cabinets fitting together for portability complete the equipment and for the sake of convenience, so that recordings can easily be played back for checking purposes, two small speakers are included one at either end of the recorder itself. It must be emphasised, however, that

at an angle of 60 to 90 degrees. These microphones are not unidirectional, however, but this may be overcome by placing a felt baffle on the back of each.

Basically, I consider the recorder to be finished, but who can say I might not think of an odd modification here and there? It has been built to suit my own requirements but, no doubt, some readers will consider certain modifications to be advantageous.

In conclusion I would say to the amateur recording enthusiast that if your recording stretches further

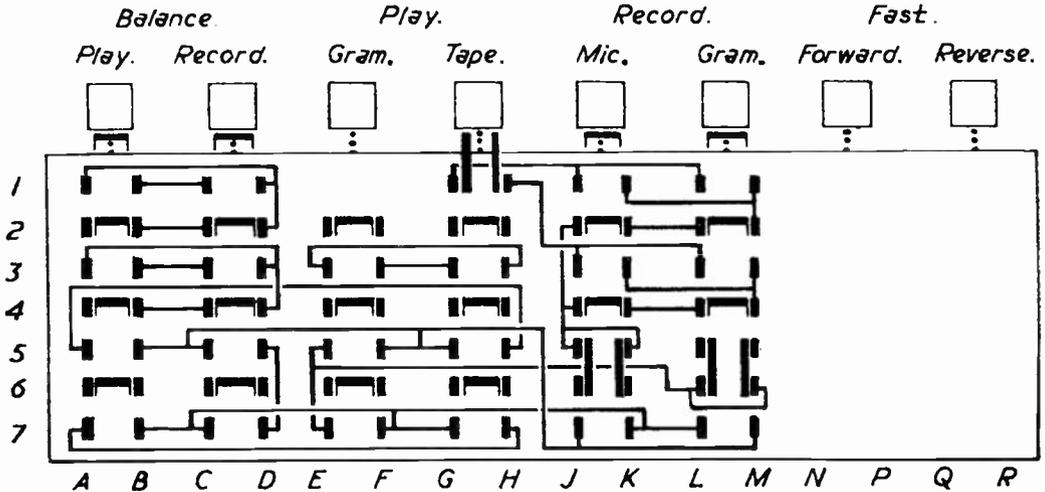


Fig. 4. - Press-button unit with buttons in "off" positions. View from bottom of amplifier chassis.

A2	Peak signal to meter amplifier "A."	H1	Head amplifier "B."
A4	Peak signal to meter amplifier "A."	H2	Grid part A, valve 1, amplifier "B."
B1	Balancing signal from output.	H5	Signal from anode part A, valve 1, amplifier "A."
B3	Balancing signal from output.	H7	Signal from anode part A, valve 1, amplifier "B."
D2	Meter.	J4	Earth.
D4	Meter.	J6	Microphone input amplifier "A."
D7	Audio oscillator.	J7	Grid part B, valve 1, amplifier "A."
E3	Speaker amplifier "A."	K1	Record output for head amplifier "A."
E5	Gram input.	K6	Microphone input amplifier "B"
F3	Earth.	M2	Record oscillator for head amplifier "A."
G1	Head amplifier "A."	M4	Record oscillator and output for head amplifier "B."
G2	Grid part A, valve 1, amplifier "A" and contact B11.		
G7	Grid part B, valve 1, amplifier "A."		

these internal speakers, although reproducing a slight stereophonic effect will not replace the use of the two conveniently spaced external speakers for normal playback. It will be seen that my aim has been for a versatile portable recorder even to the extent of the external speaker cabinets which, when assembled together, measure only 12½in. × 8½in. × 14in. They separate at an angle and contain 6½in. speakers. The quality of reproduction is surprisingly good, but many readers will agree that a recorder of this type is worthy of even better speakers.

Microphones

Finally, a word about microphones. I found the ribbon type was the most satisfactory. The first obvious thought, no doubt, is to place them well apart, but in actual fact best results are obtained by placing them side by side or one above the other, set

than the wireless and the gramophone then stereophonic recording will open up a new field of reality for you. I hope I have proved that perhaps the building of such a recorder is not as difficult as at first it might appear.

JOIN THE PRACTICAL GROUP

Edited by F. J. CAMM

PRACTICAL TELEVISION 1/3

PRACTICAL MECHANICS 1/3

Devoted to Mechanics, Science and Invention.

PRACTICAL MOTORIST & MOTOR CYCLIST 1/3

PRACTICAL HOUSEHOLDER 1/3



Making an OUTPUT INDICATOR

A USEFUL ACCESSORY FOR THE EXPERIMENTER By J. Brown

ONE of the main essentials for a radio set to make it work 100 per cent. is alignment. Many times the condensers across I.F. transformer windings alter in value as do the modern iron cored slugs. I.F.s, valve and component changes also affect this most important thing in radio. The instrument to be described was termed an output indicator for one reason—it indicates any change in the settings of the cores or capacitors of the I.F. transformer when being adjusted, and does not measure any particular voltage change. If it did it could rightly be called an "output meter." If accuracy is required, we can make R1-4 wirewound variable resistors, and the meter can be set using known A.C. voltages as standards, or even calibrating it against a multi-range meter. This little instrument will prove an asset to any "shack" or workshop. We will not, however, go into the signal source as this has been covered by many articles in the past. There are also many fine signal generators on the market

already built and calibrated for £6 and even less. Multi-range meters can be used for alignment, but have one disadvantage, e.g., the minimum range of most is 5 volts A.C., except in the case of the more expensive types which are "more professional." The aforementioned types when used for alignment on the 5 volts range are inadequate, as the signal source and the audio side of the set under repair have to be turned up to nearly maximum so as to get a reading on the meter. This means that we have the A.V.C. circuit coming into action, and it is this which we are trying to avoid. In the case of the indicator, the lowest range is approximately 1 volt A.C., hence these gain controls are in a much lower position. We have four ranges to select from, and the

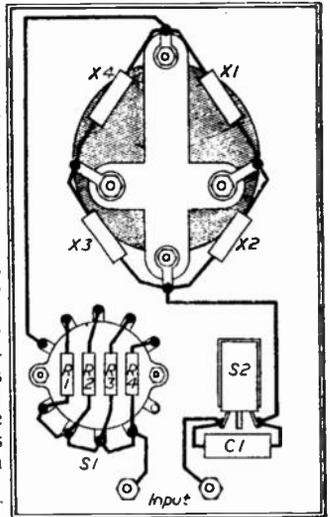


Fig. 2.—Layout and wiring.

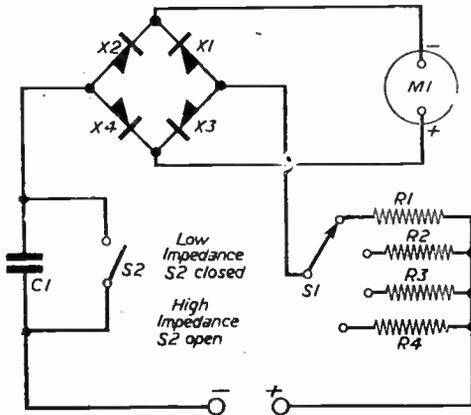


Fig. 1.—Theoretical circuit of the indicator.

COMPONENTS

- 1— $\frac{1}{2}$ amp. R.F. meter (reference 10A/8481)
 - 4—Crystal diodes (G.E.C. type).
 - 1—4-way Yaxley switch.
 - 1—S.P. switch.
 - 1—1 μ F paper condenser.
 - 4—Resistors (carbon):
 - R1—Made up 1.5 K Ω plus 100 ohms in series.
 - R2—Made up 1-10 K Ω plus 1-50 K in parallel.
 - R3—Made up 15 K Ω plus 1.5 K in series.
 - R4—Made up 50 K plus 30 K plus 2.5 K in series.
- Or four wirewound potentiometers:
- Suitable case made from a beverage cube container.
- 2—Terminals
 - 2—Crocodile clips.
 - Wire for leads.
 - 2—2BA solder tags.
 - 2—6BA solder tags.
 - 2—6BA nuts and bolts.

complete instrument could be built for approximately 30s. or less.

The Circuit

This is a bridge type circuit using crystal diodes as the meter rectifiers. The meter used was a surplus

input. This is via C1 which gives a path for the A.C. and isolates the D.C. and will pass 400 and 1,000 cycles which is the normal modulating frequency of the signal sources. In position 1 the indicator unit is connected to the speaker connections, either the speech coil or the extension L.S. sockets. In position

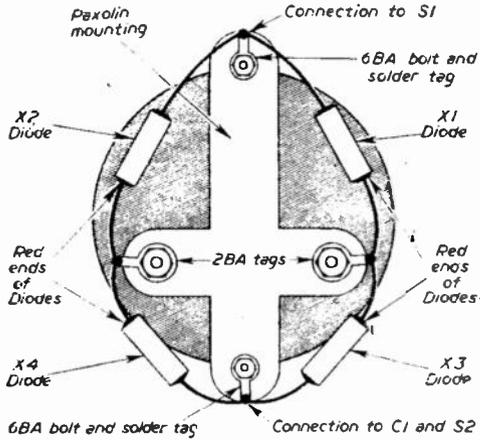


Fig. 3.—Details of the diode mount.

$\frac{1}{2}$ amp. R.F. meter, with the thermocouple removed. This, then, gives a 2 mA. movement, and as we are not concerned with measurement the scale calibration does not matter. We have four ranges : 1, approximately 1 volt ; 2, approximately 5 volts ; 3, approximately 10 volts ; 4, approximately 50 volts. These are selected by S1, a four-way single pole switch ; S2 selects the input required. In position 1, the input is low impedance for speech coil, extension L.S. connections. In position 2, we have a high impedance

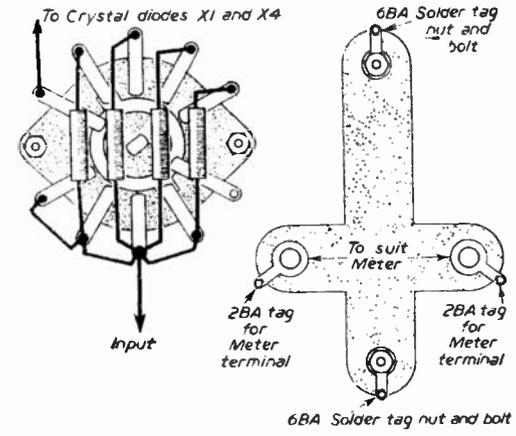


Fig. 5.—The switch, wiring and the diode mount.

2 the connections are : one leads to chassis, the other connects to the anode of the output valve, the D.C. is isolated by the condenser C1.

Great care must be taken when soldering in the diodes, as the heat destroys them. A thermal shunt must be used, or leave the wire ends long and insulate the surplus with sleeving.

Operation

Connect for either high or low impedance whichever is required ; set the signal source for the correct frequency ; keep input as low as possible to give a reading, trim the cores or the trimmers of the I.F. transformers for maximum reading on the indicator. During the operation, however, as the meter reading increases the audio control of the set must be turned down, so that the A.V.C. does not come into action.

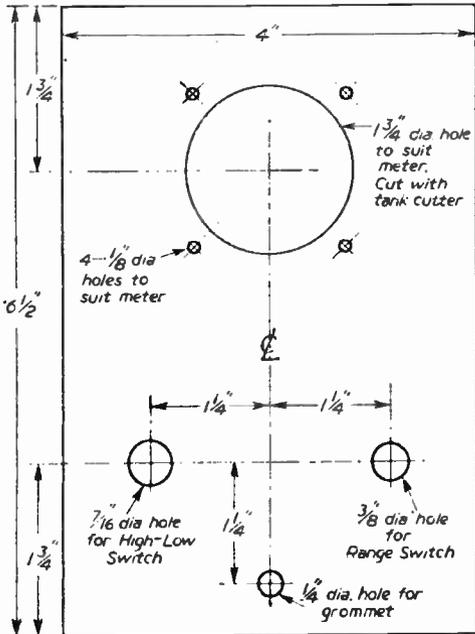


Fig. 4.—Details of the panel.

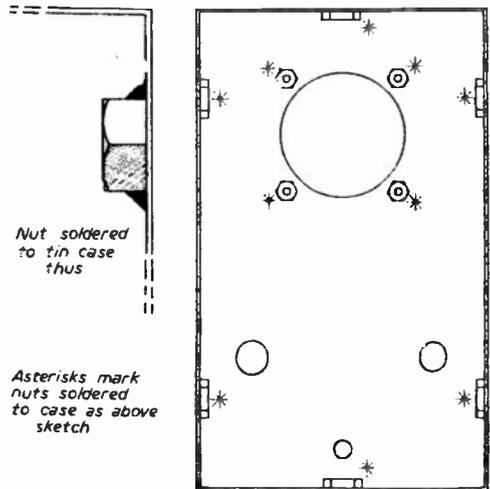


Fig. 6.—Details of the method of mounting.

A Beginner's SHORT-WAVE THREE

ADDING AN EXTRA L.F. STAGE TO THE RECEIVER DESCRIBED IN OUR ISSUE DATED NOVEMBER, 1956

By V. M. Meadows

IN the November and December, 1956, issues of this magazine, we published details of this A.C. operated short-wave receiver, which was designed specifically for the beginner in radio construction. Since that time, many requests have been received from readers who have built the receiver, asking that details be published on the addition of a further L.F. stage in order to increase the gain as a whole.

The addition of a further L.F. stage to the receiver will not only result in greatly increased audio gain

but will also increase the apparent range of the equipment. Signals which were previously only just audible will now become much stronger, and those formerly inaudible will now resolve themselves into intelligible signals.

Before proceeding with the circuit description and other details, however, it is as well to note that the bias resistor of V2 (R8 in the circuit of page 611, November, 1956, issue) should be of 270Ω and not $270\text{ K}\Omega$ as inadvertently stated in the component list. The substitution of this much lower value resistor will itself greatly increase the audio gain of the receiver, as it stands, before proceeding with the additional L.F. stage.

Circuit


This is shown in Fig. 1, from which it will be seen that a Brimar 6AT6 double diode triode has been utilised as the additional L.F. stage. The circuit is simple enough, and the extra components required have been kept to a minimum consistent with reasonable efficiency. It will be noted that both of the diode connections are left blank, no connections

COMPONENT LIST

Modifications to existing circuit
One $8\ \mu\text{F}$ Electrolytic, 350 v.,
wkg., T.C.C. type CE171E.
One $220\ \text{K}\Omega$ $\frac{1}{2}$ watt resistor.

6AT6 Stage

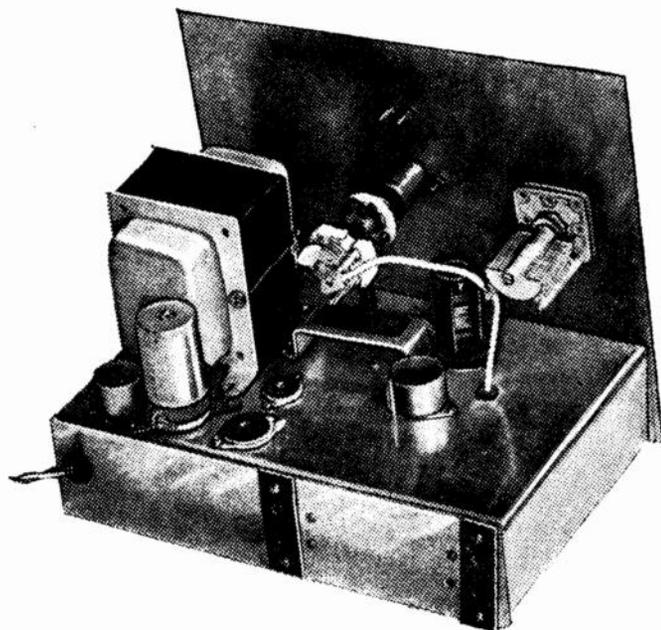
R10— $47\ \text{K}\Omega$, $\frac{1}{2}$ watt.
R11— $220\ \text{K}\Omega$, $\frac{1}{2}$ watt.
R12— $3\ \text{K}\Omega$, $\frac{1}{2}$ watt.
One B7G valveholder.
C11— $25\ \mu\text{F}$, Electrolytic, 50 v.,
wkg., T.C.C. type CF16DE.
C12— $0.01\ \mu\text{F}$, Tubular, T.C.C.,
type 37N.
C13— $0.1\ \mu\text{F}$, Tubular, T.C.C.,
type CP45N.
Valve—Brimar 6AT6.



Three-quarter rear view of the converted chassis.

to these being required. The valve functions very effectively as an L.F. triode—moreover, it is easily obtainable both on the new and the surplus market. The resistors R10 and R11 form the anode load with C12 acting as the coupling component to the output stage 6BW6. Bias for the stage is supplied by the components R12 and C11. C13 is the anode de-coupling capacitor. In this circuit, using the component values specified, the stage gain is approximately 42, this drive to the 6BW6 resulting in more than sufficient audio for the average den or shack. Consequently, more than enough gain is at hand over and above normal requirements—this being ideal; a little gain in reserve for that weak station being often all that is necessary in order to establish station identification.

Before proceeding with the wiring instructions for this stage, however, a few modifications will be required to that circuit of the receiver published in the November, 1956, issue of this magazine. Having drilled the necessary hole for the additional valveholder, the position for this being obvious from the illustration shown herewith, mount the valveholder with pins 1 and 7 nearest the rear wall of the chassis.

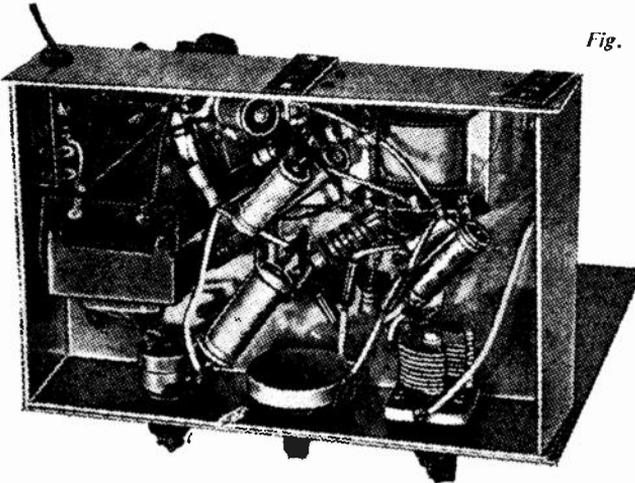

An underside view of the chassis after the conversion.

From pin 2 of the output 6BW6, unsolder the connection to the potentiometer R7. In place of this solder one end of a 220 K Ω half-watt resistor, and one end of C12 (the black end). Solder the other end of the 220 K Ω resistor to that earthed tag of the 6BW6. Connect the other end of C12 to pin 7 of the 6AT6. Having done this, solder that end of the lead from the potentiometer—previously removed from the output stage, and solder this to pin 1 of the 6AT6.

From the anode circuit of the detector stage (EF41) remove the condenser C3—an 0.01 μ F component. In its place insert an 8 μ F electrolytic condenser, T.C.C. type CE17LE, one end of this being soldered to the earthed connection of the potentiometer and the positive end to the junction of R2 and R3.

It may be noted here that the removed C3 may be used again as the C12 of the added circuit.

These are all the modifications necessary before proceeding with the wiring up of the added stage.

Wiring the 6AT6

We have already dealt with pin 1 of this valve above; the next thing to be completed is the heater

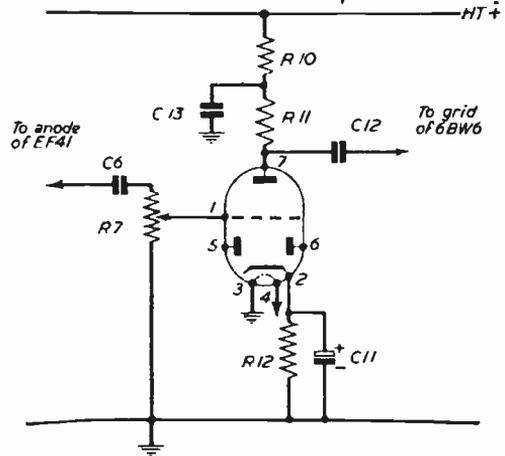


Fig. 1.—The circuit of the extra stage.

wiring. From pin 4 connect, by means of a short length of P.V.C. covered wire, to pin 1 of V1 (EF41). This wire should be the L.T. connection. Next, connect pin 3 of the 6AT6 to the central metal spigot of the valveholder, and from there to that earthed tag associated with V3. This should be done with a short length of bare wire.

To pin 2 of the 6AT6 solder one end of R12 and the positive end of C11. Solder the other end of R12 to the earthed tag of V3, and the other end of C11 to the earthed tag of the tag strip mounted on the rear chassis wall. Pins 5 and 6 of the 6AT6 are left blank and no attachments at all should be made to them. To pin 7 (to which is already soldered one end of C12), solder one end of R11, the other end of which is connected to a free tag of the tag strip on the rear chassis wall. Next, from this same tag, solder one end of R10, the other end of which should now be soldered to that tag of the tag strip containing the H.T. connection. From the junction of these two resistors, solder one end of C13, the negative end being soldered to pin 3 of the 6AT6.

This completes the actual wiring instructions for the addition of the extra audio stage. It will be found that layout is not at all critical and components do not necessarily have to be located as shown in the illustrations. Those readers who have not fitted the tag strip on the rear chassis wall will find no difficulty in wiring the stage provided they follow the circuit, as shown in Fig. 1.

NEWNES SHORT-WAVE MANUAL

7th Edition

6/-, or 6/6 by post from

GEORGE NEWNES, LTD :: Tower House, Southampton Street, London, W.C.2.

Let I.C.S. Train YOU!

● **COURSES ON :—**

RADIO and TELEVISION SERVICING · ELECTRONICS

● **EXAMINATION COURSES FOR :—**

P.M.G.'s CERTIFICATE (Marine Radio Operators)

C. & G. RADIO AMATEURS' EXAM.

(Amateurs' Transmitting Licence)

C. & G. RADIO SERVICING CERTIFICATE (RTEB)


BRIT. I.R.E., etc.

Whether you plan to have your own business, to become an electronics engineer or to take up a career in industry, an I.C.S. Course will help you to succeed. You learn at home in your own time, under expert tuition. Moderate fees include all books.

● **LEARN-AS-YOU-BUILD Practical Radio Course**

A basic course in radio, electronic and electrical theory backed by thorough practical training. You build a T.R.F. and a 5-valve superhet radio receiver, signal generator and multi-tester.

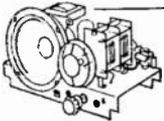
Other Learn-as-you-Build radio courses are available



5-VALVE SUPERHET RECEIVER

MULTI-TESTER

(sensitivity 1,000 ohms per volt)

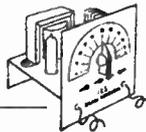

RF/AF SIGNAL GENERATOR

● **POST THIS COUPON TODAY** for FREE book on careers in Radio, etc., and full details of I.C.S. Courses.

INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 170H, International Buildings, Kingsway, London, W.C.2.

Name..... Age.....
(Block Letters please)

Address.....

Occupation..... 8.57

INTERNATIONAL CORRESPONDENCE SCHOOLS

VALVES · SAME DAY SERVICE

All Guaranteed New and Boxed

1.1v. midget, 1R5, 1R5, 1T4, 1U5, 3S4, DAF91, DF91, DK91, DL92, DL94 : ANY 4 for 27/6.

1A7GT	12/6	6L1H	13/-	D1	3/-	EF40	12/6	PL83	12/6
1C5GT	15/6	6Q7GT	9/6	1Y7	6/6	EP41	9/6	PEN46	6/6
1H5GT	11/-	68N7GT	7/6	DAC32	11/-	EF42	12/-	PL36	16/6
1N5GT	11/-	6L4GT	12/6	DAV36	8/6	EF50	6/6	PL38	22/6
1R5	8/6	6V8G	7/6	DC90	7/-	EP80	8/6	PL81	11/6
1S5	7/6	6V6GT	7/6	DF33	11/-	EF85	7/6	PL82	9/6
1T4	7/3	6X4	7/-	DP96	8/6	EF96	12/6	PL83	10/-
3Q4	8/-	6X5GT	6/6	DH76	8/6	EP89	10/-	PY80	9/-
3Q5GT	8/6	7B7	8/6	DH77	8/6	EP91	8/-	PY81	8/-
3S4	7/6	7C5	8/6	DK32	12/6	EP92	5/6	PY82	7/-
3V4	8/6	7C6	8/6	DK92	9/-	EL42	5/6	PY83	9/6
5U4G	8/6	7H7	8/6	DK96	8/6	EL38	22/6	PZ30	18/-
5Y3GT	7/6	7S7	8/6	DL33	9/6	EL41	10/-	SP41	3/6
5Z4G	9/-	7Y4	8/6	DL35	15/6	EL42	11/-	SP61	3/6
6AB6	7/6	10C2	13/-	DL36	8/6	EL34	8/6	U25	13/6
6AK5	4/6	10F1	15/-	DM70	8/6	EM34	10/-	U50	7/6
6AL5	6/6	12AH8	10/6	EABC80	7/6	EM80	10/-	U76	8/6
6AM5	5/-	12AT7	8/6	EAC91	8/-	EY51	10/6	U78	7/6
6AM6	6/-	12AU7	7/-	EAF42	10/6	EY96	9/6	UABC80	11/6
6AQ5	7/6	12AX7	9/-	E491	6/6	EZ40	8/-	UAF42	10/6
6AT5	8/6	12V6GT	11/6	EBC23	7/6	EZ41	10/6	UAC41	8/6
6AS	7/6	12V7GT	8/6	EB341	10/-	EZ80	8/6	URC41	8/6
6BB6	7/6	12K8GT	14/-	EBF80	8/6	EZ81	10/-	URF80	9/6
6BJ6	7/-	12Q7GT	8/6	EBF89	9/6	FW4.500	UCH42	10/3	10/3
6BW6	7/6	12Z3	7/6	EC81	8/6	12/-	UF41	10/6	10/6
6BX6	7/6	14S7	13/6	ECC82	7/-	GZ32	12/6	UF89	9/6
6CH6	7/-	25L6GT	9/-	EC93	9/-	KT53C	10/-	U11	10/6
6CI	15/-	28Z4GT	15/-	ECC84	10/6	KT44	6/6	U184	11/6
6FG6	8/6	22Z6GT	8/6	ECC85	8/6	KT63	6/6	UY21	15/6
6FI2	6/-	35L6GT	9/6	ECC90	12/6	KTW61	6/6	UY41	8/6
6FI3	13/-	35Z3	10/6	ECP82	11/-	MU14	8/6	UY85	10/6
6FI5	14/6	35Z4GT	8/-	ECH85	9/6	N78	12/6	VP41	7/6
6J6	5/6	35Z6GT	8/-	ECH42	10/-	P81	3/6	W76	8/6
6K7C	4/6	50L6GT	8/6	ECC81	8/6	PCC84	8/6	W77	5/6
6K7GT	6/-	80	8/6	ECL80	9/-	PCC80	8/-	X79	12/6
6K8G	7/6	1B6	18/6	EP37A	8/-	PCP82	11/6	Y63	6/6
6K8GT	9/6	CL33	16/6	EP9	6/-	1CL82	12/6	Z77	6/-

Postage 6d. per valve extra.

READERS RADIO

24, COLBERG PLACE, STAMFORD HILL, LONDON, N.16 STA. 4587

REPANCO

HIGH-GAIN COILS

DUAL-RANGE MINIATURE CRYSTAL SET COIL with circuit. Type DRX1. 2/6.

DUAL-RANGE COIL with Reaction. With 2 mains, 2 battery and transistor circuits. Type DRR2. 4/-.

MATCHED PAIR DUAL-RANGE T.R.F. COILS with Reaction. With battery, mains and feeder unit circuits. Type DRM3. 8/- pair.

PAIR DUAL-RANGE SUPERHET COILS with mains and battery circuits. Type SH4. 8/- pair.

FERRITE ROD AERIAL. Long and Medium wave. Complete with fixing brackets. Type FRI. 12/6.


MINIATURE I.F. TRANSFORMERS. Pre-aligned 465 kc/s. 13/16in. x 13/16in. x 1 1/2in. For battery or mains receivers. Type M5E : 12/6 pair.

EASY TO BUILD TRANSISTOR RECEIVERS

REPANCO "THREE DEE" TRANSISTOR RADIO. A new dual range radio with band pass tuning, using a crystal diode and 3 transistors. Easy wiring plans and instructions, 1/-, post free.

REPANCO "TRANSEVEN" latest type portable superhet, 7 transistor receiver with pre-set tuning for four stations. Easy wiring plans and instructions, 1/9, post free.

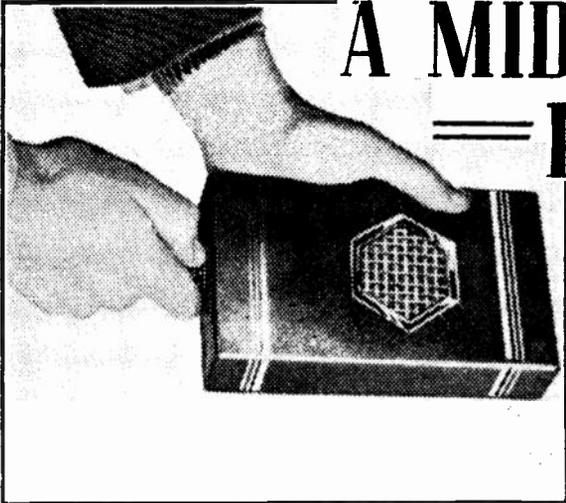RADIO EXPERIMENTAL PRODUCTS LTD. 33 Much Park St., Coventry. Telephone : 62572



A MIDGET 4-VALVE PORTABLE

A BATTERY-OPERATED
SELF-CONTAINED MIDGET

By T. Walker

Construction

The chassis is made out of sheet brass, and although the prototype set is made up of pieces soldered together, it is possible to make the chassis in one piece.

After cutting, bending and drilling the chassis, an insulated tag is riveted on to form the positive contact for the L.T. cell.

The valve holders are soldered to the chassis after cutting off the bolt tags.

The tags on the switch are cut off short, and short pieces of wire are soldered on to the tags that will be used. This must be done before fitting the switch, as it will not be possible to do this later, due to I.F.T.1 being mounted so near to this switch.

The loudspeaker is bolted to the chassis with a piece of brass gauze in between to form the grille, and the speaker tags face away from the switch.

The output transformer is bolted on, and also the tag strip soldered on to the chassis by V4 holder.

THIS is a superhet circuit, using the latest Mullard Economy 96 series valves. The total H.T. is only 7 mA and L.T. 125 mA.

To save switch contacts, instead of a tapped long and medium wave frame aerial, two separate frame aerials are used and the trimmers wired across each section.

Only one oscillator coil is used for both wavebands, and C15 and TC3 are switched in parallel to receive the long waves.

A.V.C. is applied only to the I.F. amplifier. There is no volume control, this being replaced by R5. To reduce volume the set is rotated to reduce signal pick up by the aerial.

The set indeed has only one control, this being a three-position switch, one off, two Home, three Light.

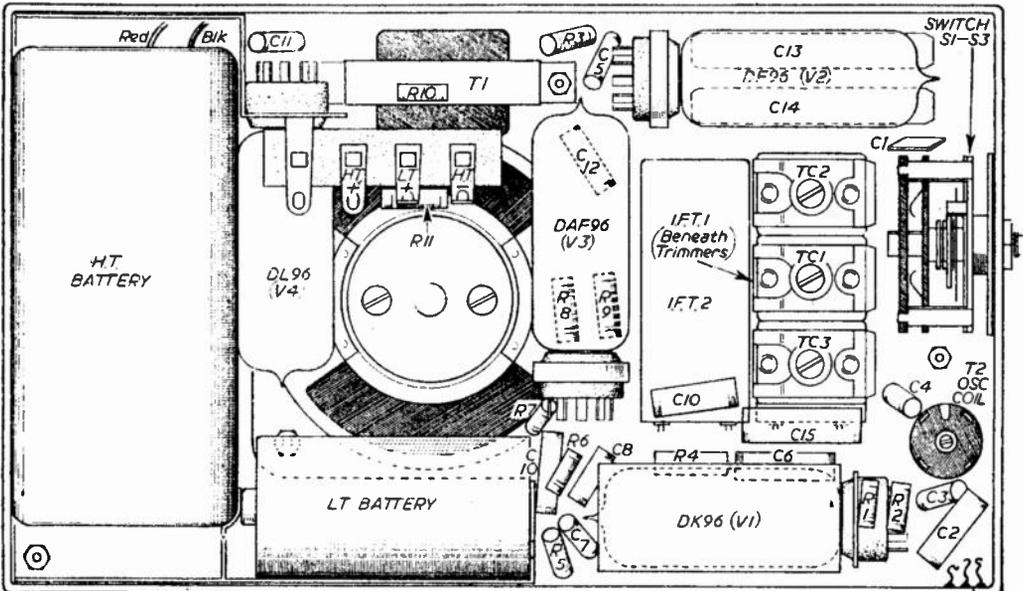


Fig. 2.- Layout of the receiver and identification of components. The circuit is on page 382.

FRAME AERIAL LEADS

SWITCH S1—S3
SHOWN IN HOME
SERVICE POSITION

H.T. CONSUMPTION
IS 7 mA.

L.T. CONSUMPTION
IS 125 mA.

BIAS VOLTAGE IS 3 V.

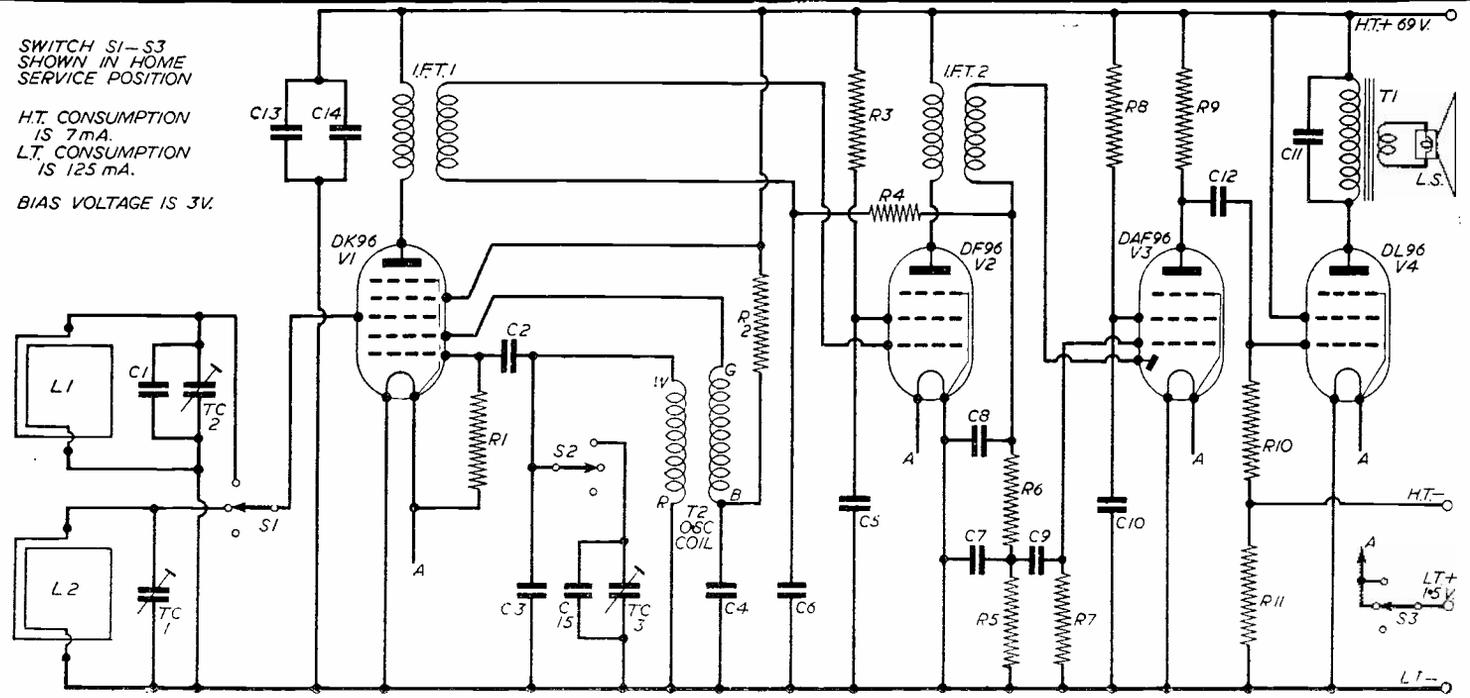



Fig. 1.—Theoretical circuit of the Portable Four.

COMPONENT LIST

- R1—47 K.
 - R2—10 K.
 - R3—10 K.
 - R4—2.2 M.
 - R5—680 K.
 - R6—47 K.
 - R7—3.3 M.
 - R8—3.3 M.
 - R9—1 M.
 - R10—1 M.
 - R11—470 ohms.
- All midget ½ watt
- C1—100 pF (Radio Spares).
 - C2—100 pF (Radio Spares).
 - C3—175 pF (Radio Spares).
 - C4—.01 μF (Hunts).
 - C5—.01 μF (Hunts).
 - C6—.01 μF (Hunts).
 - C7—50 pF (Radio Spares).
 - C8—50 pF (Radio Spares).
 - C9—.01 μF (Hunts).
 - C10—.01 μF (Hunts).
 - C11—.005 μF (Hunts).
 - C12—.01 μF (Hunts).
 - C13—2 F (Electrolytic TCC Picopack).
 - C14—2 μF (Electrolytic TCC Picopack).
 - C15—300 pF (Radio Spares).

- T1—Personal portable output transformer.
- T2—Weyrad HO3.
- S1 } 4 pole 3 way switch (ignore one pole.)
- S2 }
- S3 }
- Valves—DK96, DF96, DAF96, DL96 (Mullard).
- 4 valveholders—B7G moulded bakelite.
- L.T. is 1.5 v. Baby Cell. It is the next size above No. 8 cell.

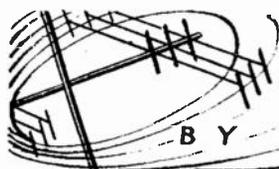- TC1 } 100 pF trimmer.
- TC2 }
- TC3 }
- IFT1 } Weyrad P6 2.
- IFT2 }
- I—four tag (one earth tag) strip.



On Your Wavelength

BY T H E R M I O N

The BBC Staff

IN the May issue I criticised the tendency of the BBC to alter the standard pronunciation of words and place names. I said that the Director General should really put some period to those snobbish Chelsea types who wish to give Kensington drawing-room type of pronunciation to words and place names, and I went on to criticise the sartorial accoutrements of some of the staff. My remarks were, of course, written in a humorous vein. The Secretary of the Association of Broadcasting Staff in a letter says that his attention has been called to my remarks, which are resented by the members of his union. He tells me that the general impression amongst his "engineering members" is that this journal is waging some kind of a campaign of denigration which they resent. I am sorry that he takes this view, for not one member of the BBC staff has written to me on the matter, and I should be glad to have from the Secretary the names and addresses of these objecting members. Does Mr. Littlewood really think that his union controls not only its members, but Press criticism? I have been associated with the BBC for rather more years than some of his members are old, and certainly for very many years longer than this comparatively small and new union. I have the highest respect for the BBC technicians. I was not referring to the technical side at all, but to the programme side—producers, announcers and to some extent those who broadcast. I seem to be far better informed about this matter than Mr. Littlewood. It may come as a surprise to him to know that many of the BBC technical personnel regularly contribute to this journal, and those who read my paragraph chuckled when they read it, but agreed with the general tenor of my comments. This journal is not waging a campaign of denigration against the technicians. It is, however, waging a campaign against the usurpation by the BBC of the right to set all dictionary pronunciations aside and adopt their own. As an Englishman I resent English pronunciations being changed capriciously. Mr. Littlewood also seems singularly unaware of criticisms similar to mine which have been going on for years. In the *Observer*, the other Sunday, there were quoted some comments of Sir Ernest Gowers in his presidential address to the English Association: "Today the word *incidentally* has become a vague word seemingly indispensable to BBC announcers. Fowler (author of *Modern English Usage*) had no patience with those who rejected the anglicised pronunciation of foreign words or place names and insisted on speaking them with the accent of a native of their country or origin. If he were alive today he would, no doubt, be disappointed that the BBC announcers evidently hold the opposite opinion." . . . Fowler had fought

affected or genteel pronunciations. The conviction seems now to be that when one is before a microphone the dignity of one's position demands, for example, the articulation of the "t" in often. . . . People are influenced by what they hear over the air. It would not be surprising if by the end of the century English and American pronunciation had become indistinguishable." The Americans have always found difficulty with their vowel sounds and have never really learned to speak English.

Any criticism of BBC programmes is always met with the rejoinder that the BBC is really understaffed, to provide a national service for seven days a week. Then why try? We are also told that there is one broadcasting employee to every 5,000 population. This proves precisely nothing, except to indicate that the BBC is overstaffed. By the same argument, at a particular moment, there is only one announcer to 50 million people in this country. These sort of figures mean nothing.

Music and Movement

AS a particular case in point, can anyone see what good purpose is served by that thoroughly inane scrvice to the schools in the morning "Music and Movement." It occupies class time which would be better used to teaching the children how to read and write, in view of the great amount of illiteracy in this country. Some thousands of teenagers cannot read or write today. Of course, if a census were taken at the schools the children will be all in favour of the programme, and I am certain that the teachers who tap this programme will also be in favour of it. They have nothing to do whilst the programme is on, and the children will naturally prefer it to some dry history lesson. The programme itself is imbecilic in its conception and certainly stupid in the way it is carried out. "Now, children! Spread yourselves all over the room. We are now going to hear some hopping music," etc., etc. What on earth is it intended to teach them? It will not teach them to dance. They will learn that soon enough from their local skiffle rock 'n' roll club. I seriously suggest to the BBC that they drop this nonsensical programme, which merely wastes school time. It is quite laughable to listen to. One wonders what sort of a person it is in the programme planning department who could be persuaded to put on such utter tripe.

MASTERING MORSE

By F. J. CAMM

1/-, by post 1/3


GEORGE NEWNES, LTD.,

Tower House, Southampton Street, Strand, W.C.2.

An Amateur Communications type Receiver

By F. G. Rayer

(Concluded from page 308 July issue)

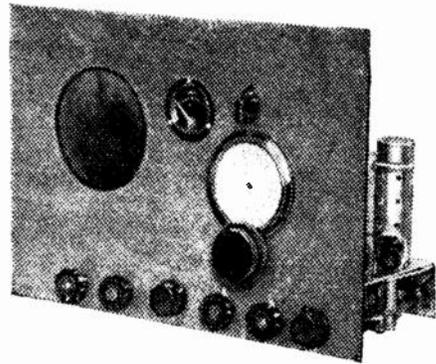

THE second wafer of the switch goes to the rear gang of tuning condenser, the top tag of which goes to R.F. valve grid. It is also connected to the fixed plates of the aerial trimmer.

Wafer 3 switches the R.F. valve anode to any of the five H.F. coil primaries. Wafer 4 switches the secondaries of these coils, and is also connected to mixer trimmer (Fig. 5) and the centre section of the tuning condenser. The top tag of the latter is taken to the 6L7 top can.

The two remaining wafers switch the oscillator coils, wafer 5 also being connected to the front section of the gang condenser. To wire in the M.W. coils it is only necessary to set the switch to its second position and connect the various coils to the appropriate tags throughout the switch sections. Fig. 5 shows the positions of the coils, these being arranged to avoid interaction and secure short wiring in the H.F. ranges. If the coils in each circuit position are located as far as possible with tags similarly placed, then the wiring of other ranges will be merely repetitive of that in the M.W. range. To secure additional screening on the L.W. and M.W. bands, the aerial coils of these are above the chassis.

The smaller oscillator coils have two separate windings in the type listed, but those for M.W. and L.W. have a single tapped winding, so that there are only three connections. Where two windings are provided the fourth tag is earthed. With the tapped coils this is not necessary since the tapping forms a common earthing point (via padder) for both sections. It will have been realised that the bands can easily be chosen to suit individual needs, and the Astral coils actually employed were those numbered 1, 2, 3, 5 and 6 in the following list:

Coil band number	Approx. waveband in metres	Required padder capacity
1	750-2,000	150 pF
2	190-570	500 pF
3	16-48	5,000 pF (.005 μ F)
4	12-36	" "
5	34-100	2,400 pF
6	90-270	900 pF
7	250-750	350 pF

In some cases the L.W. band may not be required, though it does increase the general utility of the receiver. The coils used (1, 2, 3, 5 and 6) give continuous tuning from 16 to 2,000 metres, except for the band between 570 and 750 metres, and are probably as suitable as any. Coil 7 would cover this band, if wanted. The No. 4 coil would also cover

up to the lower limit of the No. 5 coil, but the L/C ratio grows rather poor, so that the 16-48 metre coil is preferable.

As already mentioned, comparable coil types of other make can be used. In all cases it is essential to follow the maker's tag connecting data and recommendations upon padder values. In a few instances the latter may need to be obtained by wiring two condensers in parallel, e.g., 2,000 pF and 400 pF for 2,400 pF.

Operational Notes

It will be realised that a little care in operation is required if the maximum efficiency is to be obtained, when selectivity and sensitivity will very considerably exceed that of the average domestic superhet. This does not mean that tuning is difficult, since on a great number of stations there will be no need to touch trimmers or the R.F. and I.F. gain controls.

With the transformer set to suit the mains voltage, and valves in position, it is best to place the I.F. switch in the "Low" setting at first, to ensure some signal will be obtained, even under conditions of bad mis-alignment. It should then be possible to tune in the local station. The first and final I.F. transformers are now adjusted, with an insulated tool, to secure maximum indication on the tuning meter (minimum anode current). A metal tool must not be used, as its presence, especially in coils, influences resonance. If there is any tendency for any core or trimmer to come near the limit of its travel in either direction, then the other cores or trimmers are all adjusted a little and alignment repeated.

The switch is then turned to the "High" position and the other two transformers similarly adjusted for maximum signal on the meter. Their setting will be very critical. Due to the change in stray capacity in the switch positions, all transformers are then gone over again. When adjustment of any only serves to reduce signal strength, I.F. alignment is complete. When the switch is in the "Low" position one transformer circuit is slightly off peak, due to the extra capacity of the second I.F. valve, but this is no disadvantage.

In some coastal areas it may be desirable to peak the I.F.T.s at some frequency other than 465 kc/s to avoid local Morse, and a variation of 5 kc/s either way is normally quite feasible.

When the I.F.s are aligned, the aerial, mixer and oscillator circuits can be dealt with. This will prove relatively easy if the coils are correctly wired, with

the correct padder values, and each band is treated separately.

The 30 pF oscillator pre-set is left at about mid-way position and should not need further adjustment. A station of low wavelength on the band is tuned in, and the two panel trimmers are turned for maximum signal on the meter. They should come to rest at roughly mid-way position, if undue stray capacity between coil connections, etc., and chassis has been

quality components *exact* alignment throughout the swing of the condenser is not achieved.

If the aerial is other than a very short wire, a 25 pF fixed condenser should be included at the aerial socket so that the R.F. stage may tune sharply.


All other wavebands are then aligned in exactly the same way, the I.F. circuits not being touched again, however. On the S.W. bands, wrong core positioning may result in no signals being heard at first. If so, careful tuning should locate some station near the lower end of the band. The coil cores can then be adjusted, when tuning further up the band will be possible, with final alignment at a high wavelength. If it becomes increasingly necessary to close the panel trimmers as the receiver is tuned to higher wavelengths, this shows that the aerial and mixer coil cores need screwing in. The reverse effect shows they need withdrawing.

Should instability arise as either gain control is turned towards maximum, this shows that the circuit in question has long grid or anode leads, or that the valves are insufficiently screened. This test should be made with no signal, since any signal reduces gain, so that the set may only be unstable when tuned away from a station. Inaudible oscillation will be shown by a sudden drop in meter reading.

With the coils mentioned oscillation became a little fierce at the bottom of the S.W. bands. If this arises it can be cured by wiring a resistor in series with the oscillator winding of the coil or coils responsible. The resistor should be of quite low value (usually 30 to 100 ohms) as large values will prevent oscillation completely, so that reception ceases.

Aerials

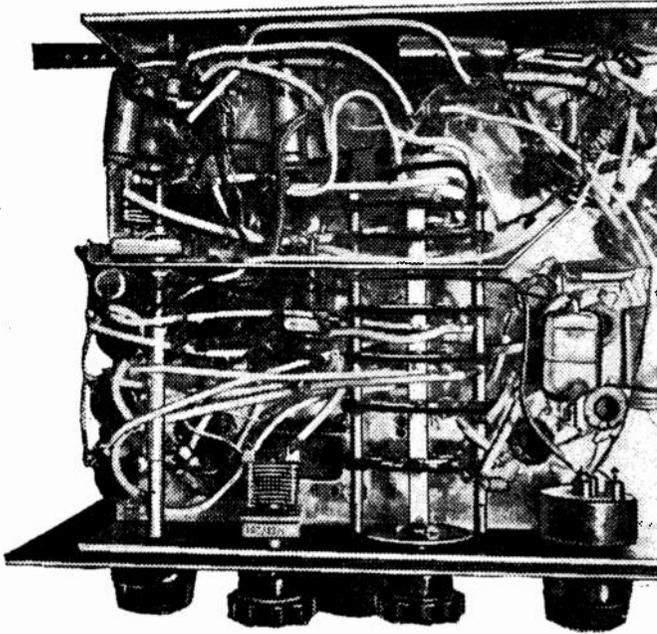
A final word on the question of aerials. Do not imagine that the larger the aerial the better the results. Many users of communication equipment find that best results are obtained by a short vertical wire. A heavy gauge or two lengths of 7/22 twisted may be supported from a length of wood sticking out from the side of the house, and the wire stretched from the top to bottom.



Some of the switch wiring.


avoided. Should one or both trimmers tend to peak near the fully open position, then the 30 pF pre-set can be screwed down a little. With the panel trimmers untouched, a high wavelength station is tuned in and the coil cores adjusted for maximum signal. The procedure is then repeated—e.g., trim at low wavelength, then adjust cores at a high wavelength. Alignment of the band will then be complete and tuning throughout can be with the main control. However, with weak stations it will be found that adjustment of the panel trimmers will often improve signal strength considerably, since even with good

PROFESSOR BOFFIN

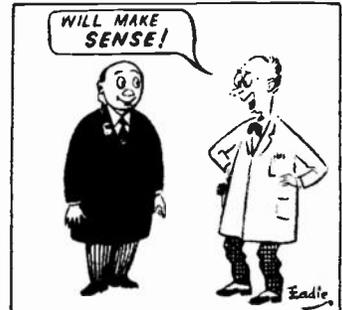

NEW! THE PRACTICAL WAY

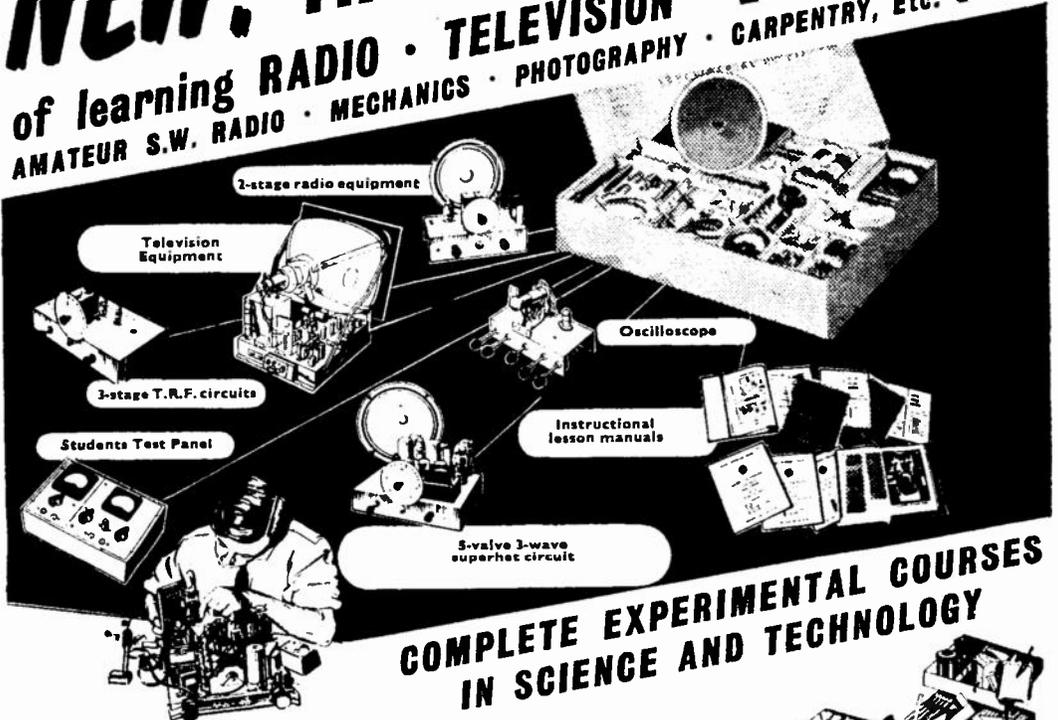of learning **RADIO • TELEVISION • ELECTRONICS**
AMATEUR S.W. RADIO • MECHANICS • PHOTOGRAPHY • CARPENTRY, Etc. Etc.



COMPLETE EXPERIMENTAL COURSES IN SCIENCE AND TECHNOLOGY

NEW... completely up-to-date methods of giving instruction in a wide range of technical subjects specially designed and arranged for self-study at home under the skilled guidance of our teaching staff.

NEW... experimental outfits and lesson manuals are despatched on enrolment and remain the student's property. A tutor is allotted to each student for personal and individual tuition throughout the course. In the case of radio and television, specially prepared components are supplied which teach the basic electronic circuits (amplifiers, oscillators, detectors, etc.) and lead, by easy stages, to the complete design and servicing of modern commercial radio and television receivers.

If you are studying for an examination, wanting a new hobby or interest, commencing a career in industry or running your own full-time or part-time business, these practical courses are ideal and may be yours for moderate cost. Send off the coupon to-day for a free Brochure and full details. There is no obligation whatsoever.

**The only Home Study
College run by
a World-wide
industrial
organisation.**



E.M.I.
Factories
at Hayes.

EMI INSTITUTES

-Part of "His Master's Voice", Marconiphone, etc., etc.

SUBJECTS

INCLUDE—

- RADIO • SHORT WAVE RADIO**
- TELEVISION • MECHANICS • CHEMISTRY**
- PHOTOGRAPHY • ELECTRICITY • WOODWORK**
- ELECTRICAL WIRING • DRAUGHTSMANSHIP**
- ART, etc.**

**COURSES FROM
15/- PER MONTH**

E.M.I. INSTITUTES Dept. 32X, London W.4

NAME _____ AGE _____
(if under 21)

ADDRESS _____

I am interested in the following subject(s) with/without equipment

AUG., 57 We shall not worry you with personal visits


FILL IN COUPON
FOR
FREE
PROSPECTUS



BLOCK
CAPS
PLEASE

101

I.T.A. CONVERTER. All I.T.A. stations, wired ready for use, complete with power pack, fine tuner, etc., £47/6, as illus. Metal cabinet, stove enamel grey hammer finish. Walnut cab., £417/6. Lizard rexine, £412/6. Chassis (less cab.), £4, all with two FCCB1. All plus 2/6 p. & p. (C.O.D. 1/6 extra). Clip-on I.T.A. aerial to existing mast, or mount in loft. 3 element. 27.-; 5E, 35.-; 8E, 55.-; low loss coaxial. 8d. yd. Terms on complete converters one-third down and 4 monthly payments of 18/6.

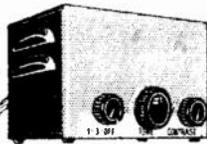

£5/10/- (2/6 p. & p. 1/6 C.O.D.)

RADIO SET. 4 valves, UY41, UAF42, UL41, UCH42. Covers 4 selected stations; aerial included. 200-250 v. A.C./D.C. mains. Chassis 9in. x 5in. x 2in. high (5½in. over speaker). 5in. F.M. speaker. On-off/vol. Walnut cabinet to fit, 20/-, 45/- down and 4 monthly payments of £1.

AUTOMATIC RECORD CHANGERS are in short supply. Collaro RC456 Studio "T" turnover crystal pick-up. 4-speed mixer. A.C. mains 200-250 v., see illus. ALSO Collaro single player AC3/554, 3-speed, turnover crystal pick-up with "T" head. £6/14/6 (3/6 p. & p.).



£8/16/6 (3/6 p. & p.)

GLADSTONE RADIO

AND a few of the latest B.S.R. "Monarch" 4-speed auto-changers at £8/12/6 (3/6 p. & p.). Terms on all players 50% down and balance plus 15/- in 5 equal monthly payments.

RECORD PLAYER. 4-speed autochanger.

- Built-in amplifier.
- Metal rectifier.
- Tone control.
- On-off/volume control.
- B.S.R. or Collaro changer.
- Smart rexine-covered cabinet.
- Cash price, £17/17/-.
- Terms £5 deposit and 7 monthly payments of 40/-.



POWER PACK for F.M., etc. 40/- (2/- p. & p.). 220 v. at 50 mA. 6.3 v. at 2½ amps. Ditto with two valve amplifier, £5 (carr. paid). Ample volume. Separate top and bass controls.

STOP PRESS! I.T.A. converter in bakelite case available for Philips' receivers at £5. 5. 0. (p. & p. 2/6; C.O.D. 1/6).

S.A.E. for our Sale bargain list—examples: 4 mfd. 602 v. block, 3/6; .1 mfd. 4 kV D.C. tub., 2/6; 1,000 pF and 2,000 pF ceramics, 4/- dozen. P.V.C. wiring wire, five colours, 10 yds. each 4/6; 2-gang variable, 3/6.

82b HIGH STREET, CAMBERLEY, SURREY



MODEL 1

D.C. VOLTAGE: 0 to 500 volts.
A.C. VOLTAGE: 0 to 500 volts.
D.C. CURRENT: 0 to 500 mA.
RESISTANCE: 0 to 20,000 Ω.
 Total resistance of meter: 200,000 Ω.
SENSITIVITY: 400 Ω/V.

MODEL 2

D.C. VOLTAGE: 0 to 1,000 volts.
A.C. VOLTAGE: 0 to 1,000 volts.
D.C. CURRENT: 0 to 500 mA.
RESISTANCE: 0 to 200,000 Ω.
 Total resistance of meter: 4 MΩ.
SENSITIVITY: 4,000 Ω/V.

Write for a free copy of the latest Comprehensive Guide to "Avo" Instruments.

'AVO' Precision

Electrical Testing Instruments

A dependably accurate instrument for testing and fault location is indispensable to the amateur who builds or services his own set.

The UNIVERSAL AVOMINOR

(as illustrated) is a highly accurate moving-coil instrument, conveniently compact, for measuring A.C. and D.C. voltage, D.C. current, and also resistance; 22 ranges of readings on a 3-inch scale.

Size: 4½ins. x 3½ins. x 1½ins.
 Nett weight: 18 ozs.

List Price: £12 : 0 : 0

Complete with leads, interchangeable prods and crocodile clips, and instruction book.

The D.C. AVOMINOR

is a 2½-inch moving coil meter providing 14 ranges of readings of D.C. voltage, current and resistance up to 600 volts, 120 milliamps, and 3 megohms respectively. Total resistance 100,000 ohms.

Size: 4½ins. x 3½ins. x 1½ins.
 Nett weight: 12 ozs.

Complete as above
 List Price: £5 : 5 : 0

Sole Proprietors and Manufacturers:—

AVO, LTD.

Formerly THE AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT CO. LTD.
 Avocet House, 92/96, Vauxhall Bridge Rd., London, S.W.1. VICTORIA 3404 (9 lines)

A Simple Test Probe

INSTRUCTIONS FOR MAKING A TEST PROBE FOR USE WITH MOST AMPLIFIERS TO FORM A VERY USEFUL AND INEXPENSIVE SIGNAL TRACER
By M. W. Kirby



Details of the assembly.

OFTEN in the course of radio and television servicing and construction it becomes desirable to test each stage in turn for signal continuity and also to get a rough idea of the quality and gain that each stage is giving. It is also useful, particularly in service work to be able to test for hum pick-up and the efficiency of the smoothing circuits. The most convenient way of testing for the above is by signal tracer, but not every experimenter has one of these, nor

damage the glass: this is shown in the illustration.) Then two 3ft. lengths of wire are connected on to the heater pins, the .01- μ F condensers soldered in place, and a short piece of sleeving pushed up to cover the pins. Next cut a piece of co-axial cable or screened lead about 3ft. long, push back the outer braid and strip $\frac{1}{4}$ in. of the inner lead and solder this to the cathode pin. The outer braid is the earth terminal for the two condensers, and also a 1ft. length of wire stripped for 1in., which will be the earthing strap to the case and form the earthing fly-lead for the probe. The case can conveniently be made out of a through-chassis electrolytic condenser sawn off at the base, the contents cleared out and a hole drilled in the end to take the probe and sleeving. The open end should then be filed smooth and two cuts made $\frac{1}{4}$ in. long and $\frac{1}{2}$ in. apart down the tube. The centre piece is lifted up to form a tag to which the earth wire may be connected. Now slide the assembly into the can and connect the earth wire to the tag. Fill with pitch or Chattertons compound and mould the end so that it forms a support for the wires. The base of the can may then be bound with tape to make a neat job. How the other ends of the wires are connected will depend upon the apparatus with which it is to be used, but if this will vary it will be a good idea to fit crocodile clips on all leads.

To test the probe, connect the heater leads A and B to a 6.3 volt supply and earth lead C to the earth of the amplifier and lead D to the input. Switch on the amplifier, and increase volume until there is a

does he have enough work to justify the cost of obtaining one.

The test probe described herein makes no pretence of being new or comprehensive, but it does have the advantage of extreme simplicity and fulfils quite efficiently the functions described above, although it can be built in a few minutes out of materials from the spares box. Any high impedance amplifier may be used, or even the amplifier of the set under test if the audio stages are not at fault. If desired a simple amplifier can be built for use with the probe and Fig. 2 shows a circuit which has given good results on test.

The circuit of the probe is shown in Fig. 1, an EA50 diode being used in preference to a germanium diode on account of its robustness. A length of 16 s.w.g. wire about 2in. long is soldered to the anode pin of the diode, and a piece of sleeving pushed over this so that it leaves about $\frac{1}{4}$ in. of wire showing at the end. (Remember to use long-nosed pliers when soldering the diode pins, or the heat will


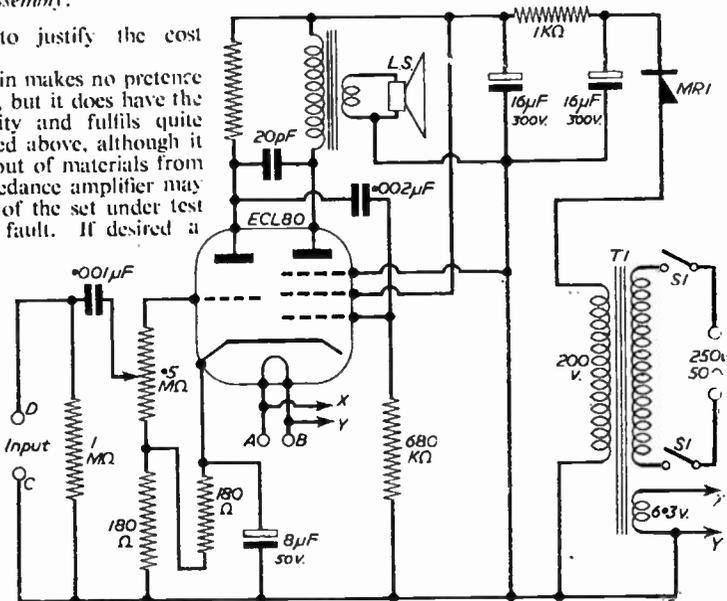


Fig. 2.- The circuit of an amplifier for the test probe.

light hum present. When the probe tip is touched with the finger a loud A.C. hum should be heard. Then connect the fly lead F to the chassis of a radio set and, without switching on, place the probe on the aerial tuning condenser, when the stations should be heard as the condenser is rotated. Next switch on, and trace the signal from the grid to the anode of each valve in turn and notice that as the output stage is approached it will become necessary to reduce the volume control of the amplifier. So much has already been written on the use of a signal tracer that there is no point in elaborating further, as instructions can be found in most books

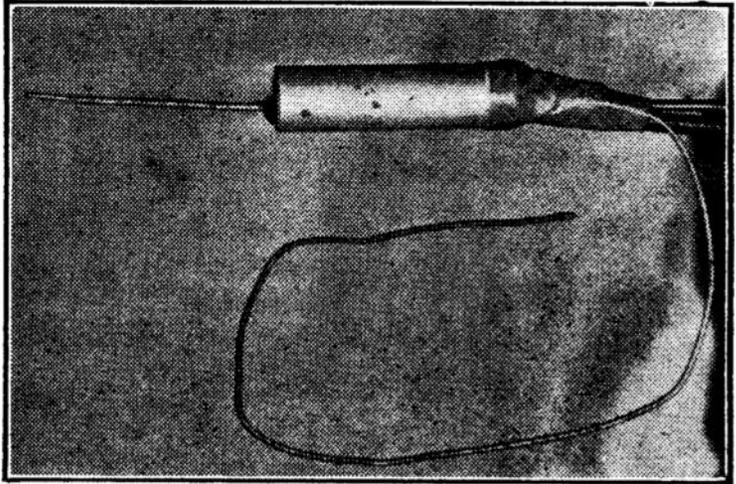

The finished test probe.

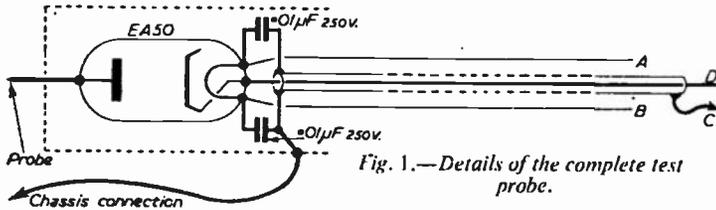


Fig. 1.—Details of the complete test probe.

New Versatile Tape Recorder

THE new Slectophon T-5 recording machine is believed to be the most versatile machine of its kind on the market.


It can be used in the home or in the office. This is because the length of the tape it uses can be varied to suit the application—whether it be for recording long-playing records or for office dictation. Its application includes, apart from these, recording conferences; "music-while-you-work" in factories and canteens; background music in shops, hotels and at exhibitions, etc.

It will reproduce through a microphone or from a radio. An attachment enables it to play and record gramophone records. Radio or disc recording can be done silently or otherwise.

The tape is housed in a book-shaped case, which can be stored in a library like a real book. This is known as a Tone-Book.

There are four Tone-Books, each housing different lengths of tape. As the machine has three speeds, the amount of recording depends on the book used and the speed. The books are known as Dictation, A, B and C. The dictation book (for office use) will record for 30 minutes at fast speed. Book C, on the other hand, will record for six hours at the same speed—making it ideal for recording long orchestral works and conferences. Fitted to each book is a register card, enabling a check to be kept of everything recorded.

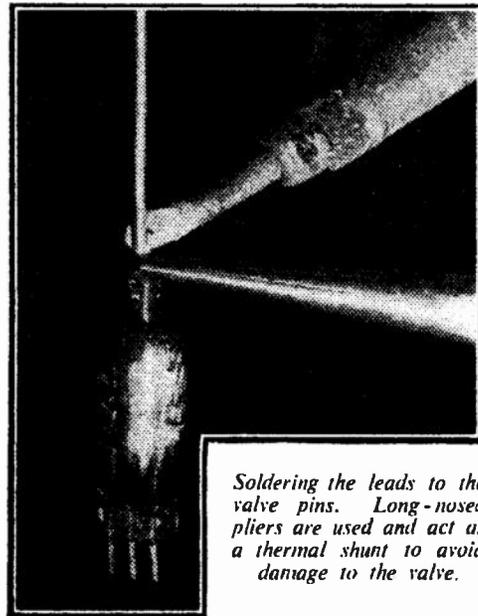The tape, 35mm. wide, has 70 tracks, each 0.3mm. wide. They are connected to form one uninterrupted sound track. When recording or play-back reaches the end of a track, it automatically carries on to the next, without any audible brake. A track-selector, controlled by a knob, enables any track to be chosen within a few seconds.



Soldering the leads to the valve pins. Long-nosed pliers are used and act as a thermal shunt to avoid damage to the valve.

on radio and television servicing. A word of warning: if the amplifier is not isolated from the mains and an A.C./D.C. set is being tested, make sure that the mains are connected in correct polarity or a short will result.

An FM Feeder Unit

DETAILS FOR MODIFYING THE POPULAR R.F.27 UNIT FOR F.M. RECEPTION

By Allen James

THE R.F.27 unit was originally designed as an R.F. amplifier and frequency converter for radar type equipments. It consists of an R.F. amplifier stage, a mixer and a local oscillator, and covers the frequency range of 60-80 Mc s.; the I.F. output being 7.75 Mc s.

The author has been using one of these units for some years now modified to cover the 56 Mc s amateur band. With the advent of F.M. to the Midlands the unit was redesigned to receive F.M. transmissions. When redesigning the unit the following points were aimed at, and in the author's opinion adequately fulfilled: freedom from interference and frequency drift, quality of reception, simplicity of operation and modification, and conversion cost as low as possible.

These points were fulfilled as follows:


Interference.—This is kept as low as possible by a double limiting action, first by the limiter valve V5, and secondly, by the flywheel effect of C39 in the ratio detector.

Frequency Drift. This is counteracted by use of coaxial cable for the oscillator tuned circuit, which produces a fairly stable oscillator. When the unit is first switched on a frequency drift will occur, and after about five to 10 minutes the frequency will remain almost rock steady; due to its high stability the local oscillator may be operated above or below the signal frequency as required.

Quality.—This is quite good if the transformer winding and alignment procedure is carefully carried out.

Simplicity of Operation.—Only the tuning dial, aerial input socket and audio output jack are mounted on the front panel.

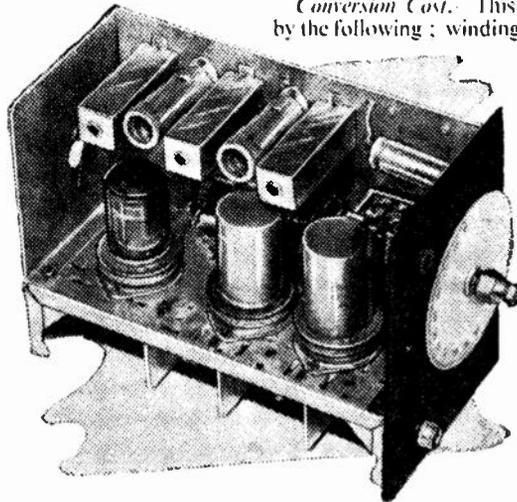Modification. The R.F. and frequency stages are easily converted and an I.F. amplifier, limiter and radio detector added.



The modified unit.

Conversion Cost. This is kept as low as possible by the following: winding coils and I.F. transformers, using low-priced valves which can be bought as type CV138 for as low as 5s. each, and by using the lowest possible number of components.

Circuit Description (see Figs. 2a & 2b)

The signal from the aerial is stepped up by the R.F. transformer L1, L2 and applied to the grid of V1 which is operating as a wide band R.F. amplifier. The signal from the anode of this valve is then passed on via C7 to the grid of V2 and its tuned circuit L3. VC2, V3 acts as an inverted Hartley coaxial oscillator of high stability, the output of which is fed through the capacitor C10 to the grid of V2. Additive mixing takes place within V2 and the resultant I.F. of 10.7 Mc/s appears at the anode. This signal is then transferred via coaxial cable to the primary of the first I.F. transformer. From the secondary of I.F.1 the signal

the output of which is fed through the capacitor C10 to the grid of V2. Additive mixing takes place within V2 and the resultant I.F. of 10.7 Mc/s appears at the anode. This signal is then transferred via coaxial cable to the primary of the first I.F. transformer. From the secondary of I.F.1 the signal

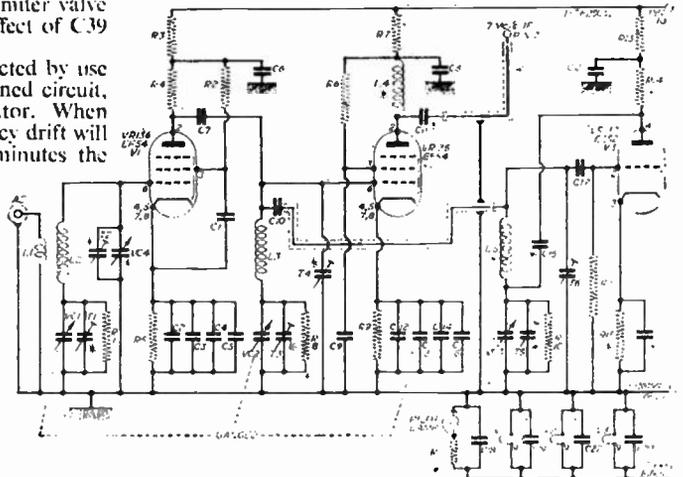


Fig. 1.— Circuit of the R.F.27 unit. Components marked * are omitted from modified circuit.

is applied to the grid of the first I.F. amplifier V4. Here the signal is amplified in the usual way and the amplified signal is then fed via T2 to the grid of V5. V5 is operated as a saturated R.F. amplifier. The purpose of this stage is to limit, not the F.M. signal, but electrical interference which is in most cases amplitude modulated (it also to a certain extent limits the voltage which appears across D1 and D2, as too high a voltage here will ruin the germanium diodes). The signal from the anode of V5 is now applied to the ratio detector, a description of which follows.


The Ratio Detector (Figs. 2b & 2c)

The ratio detector is essentially a phase discriminator, the coupling coil Lc taking place of the usual capacitor. When the F.M. carrier is at rest frequency, i.e. unmodulated, the following conditions exist: the voltage across the ends of the primary of T3 is 180 deg. out of phase. The voltage across the ends of the secondary is also 180 deg. out of phase, and the voltage injected by the centre tap is 90 deg. out of phase with reference to the ends of the primary: a state of balance therefore exists in the ratio detector. When the F.M. carrier is deviated, i.e. modulated, in one direction, the balance of phase across T3 secondary, with reference to the centre tap which remains at 90 deg., is upset. Vector addition of the voltage across T3 secondary will now show that the voltage across one half is greater than that of the voltage appearing across the other half; therefore on one half cycle a current will flow through one half of T3 secondary, through Lc, R20, C37, the A.F. load, earth and back via D2. On the next half cycle the current will flow from the other half of the secondary, via D1, R21 and C39 in parallel, earth, the A.F. load, C37 and R20, then through Lc and so back to the secondary; the current flowing round this part of the circuit is at audio frequency due to the rectifying action of D1 and D2, C38 being the R.F. by-pass capacitor.

There is also a direct current flowing round the ratio detector circuit, through D2, T3 secondary, D1 and R21. The current flowing through R21 causes a voltage drop R21 which charges up C39 to the D.C. level of the signal. The time constant of R21 and C39 is such that it will allow slow carrier height variations but will absorb rapid carrier height variations, which are usually due to electrical interference or amplitude modulation. C36 and R20 form the de-emphasis network and C37 is the isolation capacitor.

Modifications to the R.F.27 Unit

Fig. 1 shows the components which are omitted from the modified circuit. First remove the valves, then referring to Fig. 1, disconnect L1 from the aerial socket and unwind it from about L2, unsolder the leads to L2, L3 L4 and L5 and remove these coils from the unit. Now unsolder and remove all the ceramic trimmers with the exception of T6 in the oscillator section. Also remove the parallel resistors, R1, R8 and R10; the aerial trimmer capacitor VC4 is also removed. The dial is now removed, the moving part of which is released by a grub screw located at the bottom right hand side and a grub screw which is accessible when the bulb holder is removed. When the rotor is removed the four bolts holding the stator are exposed, remove this after first unsoldering the wire to the dial bulb. To remove the tuning gang, VC1, VC2 and VC3, unsolder the earth wires from the chassis end and take out the four bolts holding the gang; it may be found that packing pieces are used under some of these capacitors. These are used to keep the spindle in alignment and must be replaced in exactly the same positions when remounting the tuning capacitors. The screened cable and C11, which are connected between

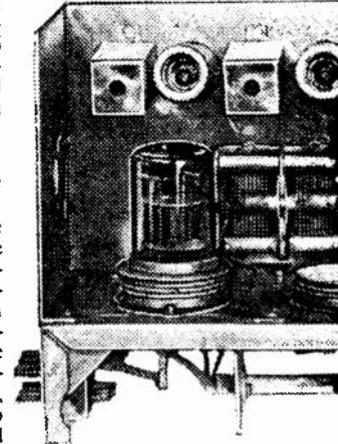

The complete


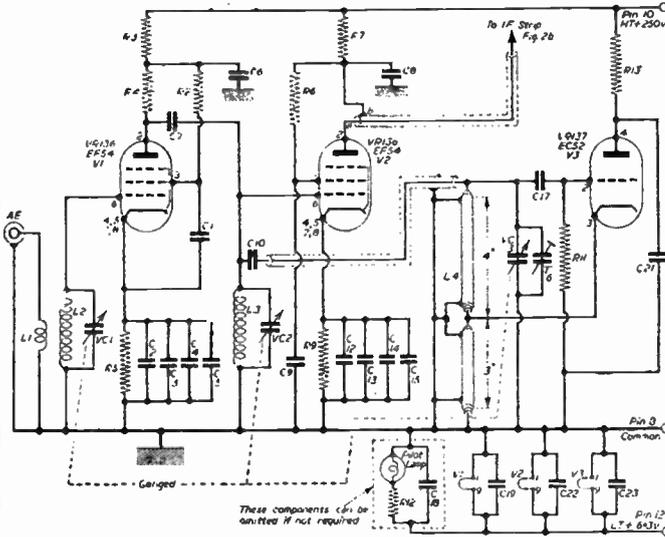


Fig. 2(a).—Modified R.F. unit.

- COMPONENTS**
 C25, 30, 31, 34—10 pF 2 per cent. silvered mica.
 L.E.M.
 C26, 27, 28—2,200 pF miniature ceramic. T.C. Hi-K.
 C29, 33—0.01 μF 200 v. D.C. T.C.C. CP.112.
 C32, 35—47 pF 2 per cent. silvered mica. L.E.M.
 C36—500 pF mica. Dubilier (C20 from R.F. unit).
 C37—0.02 μF 500 v. D.C. T.C.C. C.P.34 S.
 C38—330 pF ceramic. T.C.C. Hi-K.
 C39—4 μF 275 v. B.E.C. CE550 (with horizontal mounting clip).
 R16—1 K Ω ½ w. Dubilier.
 R17—150 Ω ½ w. Dubilier.
 R18—47 K Ω ½ w. Dubilier.

pin 7 on the Jones plug and pin 2 of V2, are removed and also the resistor and capacitor from the cathode circuit of V3, R15 and C20. R14 and C16 are now removed and the junction of R13 and C2 are taken directly to pin 4 on V3 as shown in Fig. 2a.

From the components removed only the following are re-used: the valves, the coilformers without cores, the tuning assembly and C20. The inductance of the coils is too high for the F.M. band, so they are stripped and rewound as shown in the coil table. The capacitors VC1, VC2 and VC3 are all reduced to approximately 27 pF by removing all but three rotor vanes on each: the rotor vanes are held to the spindle by a clamp construction method and can be easily removed by prising out with a pair of long-nosed pliers. Care should be taken not to damage the remaining plates and on completion of this operation each capacitor should be checked for short circuits. These components should now be placed in a safe place whilst the redrilling of the chassis takes place.

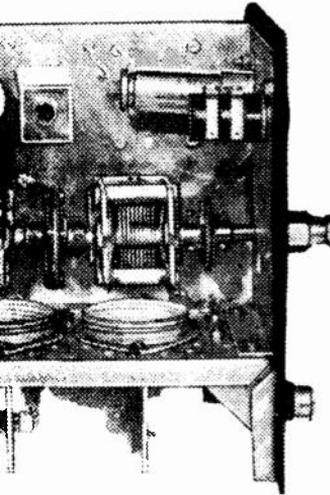

feeder unit.

The approximate positions of these are shown in Fig. 6.

Details of a new front panel are given in Fig. 4, and when completed this can be used as a template for drilling the front of the unit. Only the following holes should need drilling: Two front panel fixing holes; a hole for the output jack, two holes for fixing the coaxial socket; and fixing holes for the dial. If the original dial is used then turn it through 90 deg. and redrill holes for it. When the dial is remounted it will project about 1/2 in. above the new front panel, which, in the author's opinion, does not mar the appearance of the unit. The author used a different dial here, the original one being used on a piece of test equipment. Holes for mounting the tag panel (containing C18 and R12) if required, can easily be marked on to the front panel from the rear side and should be countersunk.

Wiring and Mounting Components

The I.F. transformers are now constructed as shown in the table. Readers may find it easier if first the coils are wound and fixed with Durofix. Then take 13 pieces of bare connecting wire about 7in. long and put a small blob of solder on the end of each, then pass these wires down through the holes in the top and base supports of the coil and pull each wire tight whilst soldering to the base, the ends of the coils are then wrapped around and soldered to the appropriate supports, and the capacitors mounted as shown, care being taken to ensure that no short circuits will appear between the coils and cans.

The I.F. transformers are now mounted together with the valveholders and C39. The tuning gang VC1, VC2 and VC3, and the inductors L2 and L3 are then replaced and soldered into the unit, as shown in Fig. 2a, keeping connecting wires as short as possible; the remainder of the unit, including metalwork and tag strips, is now bolted on.

Drilling Details

The drilling details are given in Fig. 3, to enable the unit to be laid flat it is necessary first to remove the front panel; this is held on by two bolts at the left-hand side and the two handles securing the bolts at the other side; also by two bolts holding the tag panel, containing C18 and R12, and the coaxial aerial socket. It will be noticed that no tag strip drilling details are given in Fig. 3. This is because of the various types of tag strips which are available. The height of the tag strips must not, however, exceed half-an-inch, otherwise they will not fit in the space available.

COMPONENTS LIST

- R19—68 KΩ 1/2 w. Dubilier.
- R20—100 KΩ 1/2 w. Dubilier.
- R21—22 KΩ 1/2 w. Dubilier.
- V4, V5—EF91, 6AM6, 6F12, or Z77.
- D1, D2—G.E.X. 44, G.E.X. 34, etc.
- J1—Jack socket.
- 2 B7G Valveholders with cans.
- 3 Aladdin coil formers with cans and cores. 2 3/4 in. high x 1/2 in. sq. (R.C.S.)

MISCELLANEOUS

- Screened cable. Coaxial cable.
- 3, 3-way flat mounting tag strips.
- Grommets, nuts, bolts, tags, etc.

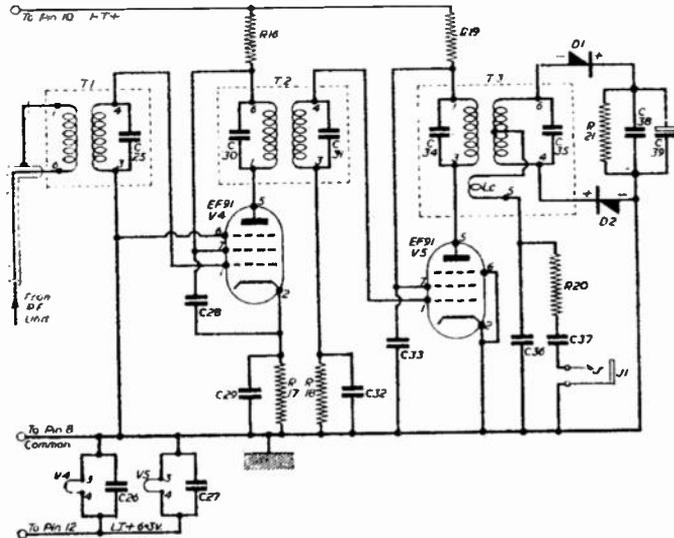


Fig. 2(b).—The additional unit to make up the feeder.

The coaxial cable in the oscillator stage, I.4, Fig. 2a, is made up as follows: Take 7in. or 75 Ω ½in. diameter coaxial cable and cut into two lengths of 3in. and 4in., cut off ½in. of outer sheath on each end and splay out the braiding: then lay the braiding back along the cable sheath, bind with connecting wire

long earth leads, sharp bends in the cable, and too much heat as polythene melts very easily.

The next operation worthy of mention is the coaxial cable between V2 anode and H.T., and the primary of T1. The author used thin 50 Ω TV cable,

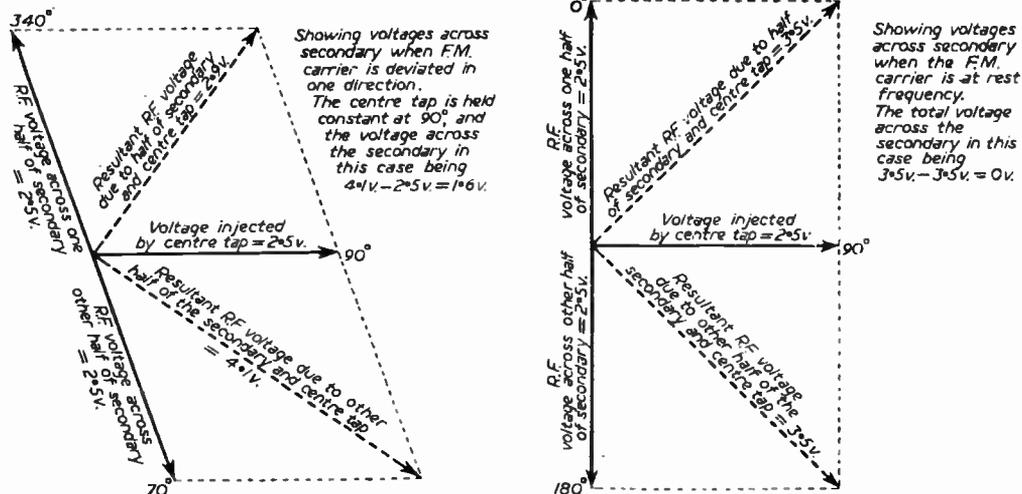


Fig. 2(c). How the detector works.

and lightly solder. After completing each soldering operation lay the coax. to one side to allow the polythene to reset. When wiring into the unit avoid

but almost any type of coaxial cable will be found suitable here.

(To be continued)


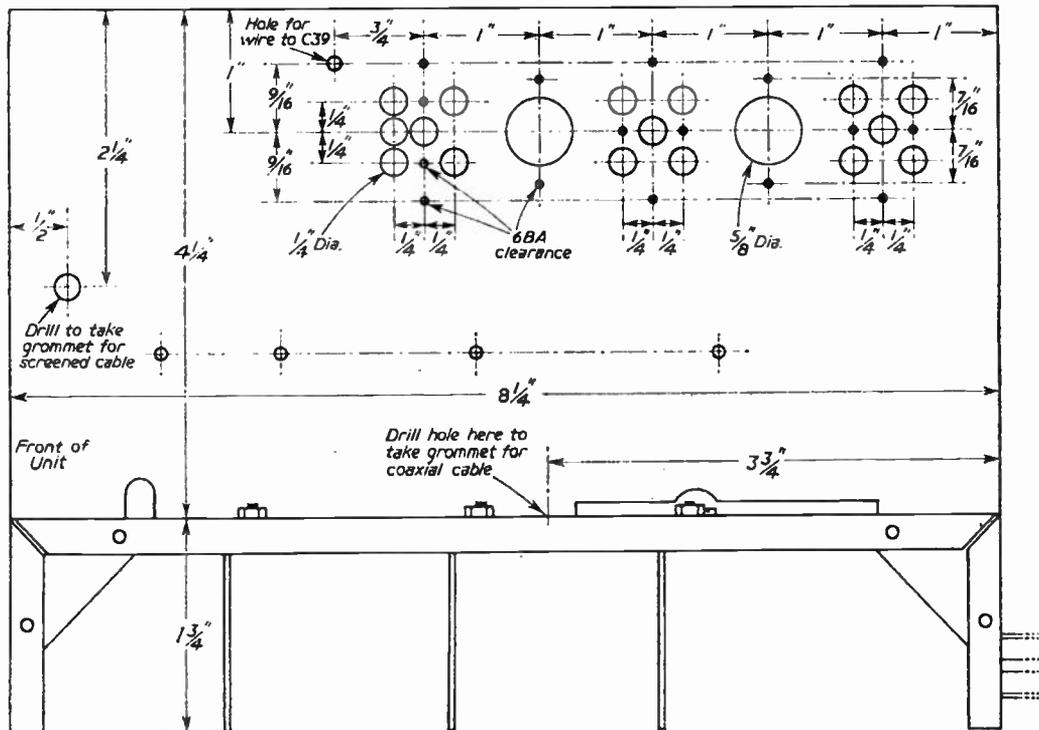


Fig. 3.— Details of the chassis and drilling.

BAND 3 T/V CONVERTER—185 Mc/s - 199 Mc/s

Suitable for London, Birmingham and Northern Transmissions

£2-5-0 post free

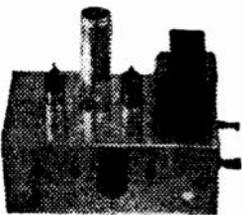

A highly successful unit (H World circuit), incorporating variable oscillator tuning, Midget BVA valves, etc. Chassis size 7 x 4 x 2 1/2 in. Thousands already in use. Suitable for most types of T.V. sets. TRF or Superhet. Kit of parts 45/- Blueprint 1 6, Power pack kit 30/- Switch kit (Band 1—Band 3 Ae switching),


6/6—All Post free. Wiring and aligning of above 20/- extra. Full range of Band 3 aerials in stock. Adaptors from 7.6 per set. Indoor or outdoor dipoles with 4 yds. cable, 13.9. Band 1—Band 3 crossover filter unit, 7/6. Variable attenuators 6 db—36 db. 7.6. BBC Break-through Filter, suitable for BBC pattern rejection, 8/6.

Volume Controls

Log. ratios, 10,000 ohms — 2 Megohms. Long spindles. 1 year guarantee. Midget BVA type. No. 88. 1 P.S.W. 1 P.S.W. 3/- 4/- Linear Ratio, 10,000 ohms — 2 Megohms. Less switch, 4/- each. Coax plugs, 1/2. Coax sockets, 1. Couplers 1/3. Outlet boxes, 4/6.

80 ohm COAX

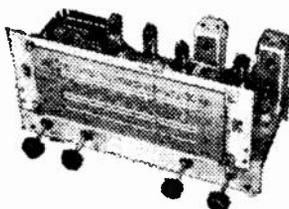STANDARD (in. diam. Polythen-insulated. GRADE "A" ONLY
8d. yd.
SPECIAL — Semiaut speed polythene. 80 ohm Coax (in. diam. Stranded core. Losses cut 40%
9d. yd.



ALL-WAVE RADIOGRAM CHASSIS

3 WAVEBANDS 5 VALVES
S.W. 16 in.—50 m. LATEST MIDGET BVA SERIES
M.W. 200 in.—500 m. LATEST MIDGET BVA SERIES
L.W. 800 in.—2,000 in. BAND new and great. A.C. 200/250 v., 4 pos. W.C. sw. short-Medium-Long-Tune. P.U. socket. High Q. short-core coils. Latest circuit technique, delayed AVC and neg. feedback. OP 4 watts. Chassis size, 13 1/2 x 5 1/2 x 2 1/2 in. 10 in. bor. or vert. station names. Walnut or Ivory knobs to choice. Aligned and calibrated ready for use. Sensitivity and Quality at Low Cost.
Chassis isolated from mains. FARGAIN 9 1/2 gns.
1 Carr. and ins., 4/8. PRICE 20/- and 25/-
8 or 10 in. speakers to match, 20/- and 25/-
7 Valve De Luxe, push-pull EL41 version. 7 watt output, 212/10/0. Carr. & ins. 5/-

ELECTROLYTICS ALL TYPES NEW STOCK

Tubular Wire Ends	Can Types, Clips 3d. etc.
25, 25 v., 50, 12 v., 1.8	324-32 350 v. B.E.C. 5/6
30/50 v., 4, 500 v., 2	324-32 350 v. T.C.C. 6/6
100/5 v., 2, 450 v., 5/-	84-84 450 v. T.C.C. 4/6
450 v. B.E.C. 2/3	84-84 450 v. Hunts 5/6
650 v. Dub. 2/6	164 164 450 v. T.C.C. 5/6
84-84 500 v. Dub. 4/6	324-32 500 v. Dub. 4/-
164 164 450 v. T.C.C. 5/6	324-32 450 v. Hunts 4/6
164 164 450 v. B.E.C. 3/6	324-32 450 v. T.C.C. 6/6
164 164 450 v. T.C.C. 4/6	250/250 v. B.E.C. 6/6
324/324 v. Dub. 4/6	604 100, 350 v. 11/0
324/324 v. Dub. 5/-	604 250, 275 v. 12/6
304 300/350 v. B.E.C. 6/6	1004 200, 275 v. 12/6

SUPERCEL RECTIFIERS. E.H.T. Type. Fly-Back Voltages. K/25 2 kV, 5/-; K/30 3.2 kV, 6/8; K/35 3.6 kV, 7/3; K/40 4 kV, 7/9; K/45 10 kV, 12/6, etc.

MAINS TYPES—RM1 125 v. 60 mA., 4/8; RM2 125 v. 100 mA., 6/8; RM3 125 v. 120 mA., 6/8; RM4 250 v. 250 mA., 16/6; RM4B type 270 mA., 17/6
ENGRAVED CONTROL KNOBS for (in. spindle, 1 1/2 in. diam. Walnut or Ivory. Gold filled. 16 Standard engravings, 1 1/2 in. Plain knobs to match above. 1 1/2 in. 10d. ea., 2 1/2 in. dia., 9d. ea. Superior Walnut or Ivory with gold ring, 1 1/2 in., 1. ea.; 1 in., 9d. ea. Pointer Knobs, Black with White Line, 9d.
MAINS TRANSFORMERS—Made in our own Workshops to Top Grade spec. Fully interleaved and impregnated. **RADIO AND AMPLIFIER TYPE**—250 v. 60 mA. P.W. sec., 5 v. or 6.3 v. 1 a. mct. 6/5 v. 2.5 a. set. Htr., 22/8, etc. C.B.T. HTR. **ISOLATION TYPE**—Low leakage with or without 25% sec. boost voltage. Ratio 1:1 or 1:1.25, 2 v., 4 v., 6 v. or 11 v., 10/6 ea. Ditto with mains primaries 200/250 v., 12/6. Special to order.
L.F. CHOKES—10 H. 85 mA., 5/-; 15 H. 100 mA., 10/6; 10 H. 120 mA., 10/6; 20 H. 150 mA., 15/6; 30 H. 10/6; 50 H. 10/6; 100 H. 10/6. **OUTPUT TRANSF.**—Standard pentode, 4/6; ditto tapped prim., 4/8; small pentode, 3/8; Midget battery pentode (HTR, etc.), 4/6.
LOUDSPEAKER—P.M.3 OFM 5 in. R. and A. 18/6; 6 in. Cel., 18/6; 7 x 4 in. Goodmans Elliptical 18/6; 8 in. Elar., 20/6; 10 in. R. and A. 25/-; 12 in. Plessey, 25/-; 12 in. Goodmans heavy duty Audio 50, 15 ohms, 26/-; 24 in. Elar., 17/6.

CARBON

10% Type, 1 w., 3d.; 1 w., 5d.; 1 w., 8d.; 2% Type, 1 w., 9d.; 5% Type, 1 w., 1/-; 10% Type, 1 w., 1/6; Hi-Stab, 1 w., 2/-

WIRE-WOUND

5 w. — 25 ohms—1/3 10 w. — 10,000 — 1/8 15 w. — 15,000 — 2/- 30 w. — 15,000 — 1/8 50 w. — 35,000 — 2/6 100 w. — 100 ohms—2/3

WIRE-WOUND POTS

Pre-set Min. T.V. Type Knurled Slotted Knob. All values 25 ohms to 20 K., 3/- ea. 50 K., 4/- Ditto Custom Track 50 K. to 2 Mfg., 3/- **CONDENSERS**—Mica or S. Mica. All pref. values 3 pf. to 600 pf., 6d. ea. Ceramic types, 2.2 pf. 5,000 pf. as available, 9d. each. Tubulars, 450 v. Hunts and T.C.C., 900 v., 901, 961, 961, 1,350 v. 9d. 9d. 9d. 1,500 v. Hunts T.C.C., 1/- 25 Hunts, 1/6. 5 Hunts, 1/6. 1,150 v. T.C.C. (Simplex), 3/6. 300 6 kV, T.C.C., 5/8. 300 20 kV, T.C.C., 9/6. **STANDARD 3-WAVEBAND COIL PACK**—Size 2 1/2 in. x 2 1/2 in. in depth, 4-pos. switching. Long, Med., short, Gram. Four-core coils prealigned for 465 Kc. I.F. Complete with trimmer, ready to use. A very sensitive and efficient coil pack. Manufacturers' Surplus. Bargain Offer, 27/6. **SOLO SOLDERING IRON**—300/220 v. or 230/250 v.) 25 watt Instrument type, 21/8. 65 watt Pentil Bit Type, 26/8. 65 watt Oxid Bit Type, 25/- Comprehensive stock of spares available.

RECORD PLAYER BARGAINS

Latest Model U.A.S. BSR Monarch 4-speed auto-changer 22.10.0, carr. 4/8. B.S.R. Three-speed Single Flyer Model T.U.S., 24.12.6, carr. 3/6. Cut mounting board 5/-, carr. 1/- Garrard and Colquhoun 4-speed Changers from 9/1 run. Carr. ins. 4/6. Ditto 4-speed Single Flyers from 27.10.0, carr. 3/6. As available.

SCOTCH ROY, EMITAPE, etc.

1,200 ft., 30". Long playing, 1,200 ft., 45". Paper tape, tape good quality, 1,200 ft., 12/6. Reels only, 5 in., 2 1/2 in., 4 1/2 in.

I.F. TRANSFORMERS—465 kc.

Brand new ex-manufacturers' Midget I.F.T. Size 2 1/2 in. x 1 1/2 in. dust core (using 1 1/2 wood coils, High Q. Bargain offer, 7/6 pair.

NEW VALVES GUARANTEED

1R5, 1747 6/DAF96	9/-	ECL80	10/6	1N752	10/6
6A5, 184 7/DF96	9/-	EP41	10/6	1N183	12/6
3A4, 3V4 8/DK96	9/-	EP80	10/6	1N1	12/6
5Z4	9/6	91156	8/-	EP86	12/6
6AT6	8/6	3L15	10/6	EP91	8/6
6X4	8/6	AIC20	9/6	EP128	15/6
6K8	8/6	BH91	8/6	EL41	10/6
6Q7	8/6	BU33	8/6	EL84	11/6
6AN7	8/6	EH14	10/6	EPY31	10/6
6V6	7/6	EC184	10/6	EP220	8/6
6X3	7/6	EP80	12/6	EP220	8/6
6X3	7/6	EP82	12/6	MC14	9/6
7Y5	6/-	EP112	10/6	PC84	10/6
7Y4	8/6	EP181	10/6	PC80	10/6

SPECIAL PRICE PER SET

1R5, 174, 185, 184 or 3V4 ... 27 6
DK96, DF96, DAF96, DL96 ... 35/-
6A5, 6K7, 6Q7, 6V6, 3Z4 or 6X3 ... 38/-

SPEAKER FEET

Expanded Bronze anodized metal. 4 in. x 5 in., 2/3; 12 in. x 5 in., 2/-; 12 in. x 12 in., 3/6; 12 in. x 16 in., 6/-; 24 in. x 12 in., 8/6, etc. **TUNING FRET** (Murphy pattern).—12 in. x 12 in., 2/-; 12 in. x 18 in., 3/-; 12 in. x 24 in., 4/-; etc.



RECORD PLAYER CABINET

Cabinet size 18 1/2 in. x 13 1/2 in. x 11 in. With motor board 12 1/2 in. x 12 1/2 in., 23.0.0, carr. 2.6. 2 valve amplifier to fit above, ready wired and tested with 6 1/2 in. speaker, 23.12.6, carr. 2/6. Record changers available to suit this cabinet.

5 in. P.M. SPEAKER

Ex-mfr's. units. R.M., Elar, Celestion, etc. All reconditioned and guaranteed. Ideal ext. unit. 7/6, post and packing 1/-.



F.M. TUNER-UNIT (87 mc/s—105 mc/s) by Jason.

As described in Radio Constructor. Designer Approved Kit of parts to build this modern highly successful unit, drilled chassis and J.B. dial, coils and case, 4 BVA miniature valves and all components, etc., for only 28.10.0 post free. **SUPERIOR TYPE GLASS DIAL** (as illustrated).—Calibrated in Mc/s. and edge lit by 2 pilot lamps, 12.8 extra. Illustrated handbook with full details, 2/- post free.

TRS RADIO COMPONENT SPECIALISTS (Est. 1946)

70 BRIGSTOCK ROAD, THORNTON HEATH, SURREY (THO 2188)

50 yards Thornton Heath Station. Buses 130A, 133, 159, 166 & 190.

Listed above are only a few items from our very large stock.

Send 3d. stamp today for Complete Bargain List.

Hours: 9 a.m.—6 p.m., 1 p.m. Wed.

OPEN ALL DAY SAT.



Terms: C.W.O. or C.O.D. Kindly make cheques, P.O.s., etc., payable to T.H.S. Post/Packing up to 1lb. 10, 1 lb. 1, 3lb. 1/6, 3lb. 2, 10lb. 2/6.

A WONDERFUL MONEY-SAVING OPPORTUNITY FOR READERS OF PRACTICAL WIRELESS!



**FULL LENGTH
FULL SIZE**

The Scientific Book Club is owned and controlled by Foyles, the world-famous book sellers.

LOOK AT THESE GREAT TITLES!

Recent and forthcoming selections include:

MEMOIRS OF A BIRDMAN
By Ludwig Koch
Published at 16s.
4s. TO MEMBERS

MEN WITH GOLDEN HANDS
By E. H. G. Lurz
Published at 12s. 6d.
4s. TO MEMBERS

A GUIDE TO THE EARTH'S HISTORY
By Richard Carrington
Published at 21s. 1
4s. TO MEMBERS

THE MEN BEHIND THE SPACE ROCKETS
By Heinz Garmann
Published at 18s.
4s. TO MEMBERS

—FILL IN THIS ENROLMENT FORM TO-DAY!—

To The Scientific Book Club, 121 Charing Cross Road, London, W.C.2

I wish to join the Scientific Book Club, and agree to purchase the book issued each month to members at a cost of 4s. (postage 9d.). I agree to continue my membership for a minimum of six books and thereafter until countermanded.

Prac. Wireless Aug. '57.

- *I will pay for selections on receipt.
Or if you wish to save time, postage and postal order costs you may send an advance subscription. 6 months 28s. 6d.; 12 months 57s.
- *I enclose 28s. 6d. 57s. (Strike out amount not applicable.)
* Place ✓ in the space above, as required.

NAME
(Block letters, please)

ADDRESS

Overseas enrolments (prices as for inland) should be accompanied by an advance subscription.

Now's the time to join the **SCIENTIFIC BOOK CLUB** You BUY Books published at 10/6, 12/6 and more—for **ONLY 4/-**

Each month, the Scientific Book Club brings to its members the fascinating story of the march of modern science, told in thoroughly dependable books by the front-rank scientific writers of our time—vivid, vital, constructive contributions to Man's unceasing struggle to solve the problems of the Universe. And although the ordinary editions of these books are sold to the general public at 10/6, 12/6 15/-, or more, THE PRICE TO MEMBERS OF THE SCIENTIFIC BOOK CLUB IS ONLY 4/-. Remember, too, that Scientific Book Club selections are full-length and unabridged. They are printed on good quality paper, well bound, with an attractive picture jacket. These are, we say with certainty, books that you will be glad to read, proud to own. The Scientific Book Club brings these great books to you each month; helping you to build up, at remarkably low cost, a first-class collection of scientific books. *Now is the time to join!*


FREE! You can obtain the famous GUINNESS BOOK OF RECORDS (published at 9s. 6d.) FREE if you enrol a friend in the Club. Send your friend's name and address with 4s. 9d (4s. plus 9d. postage) for first book, mentioning this offer, and your gift will be sent to you.

TELETRON TYPE FX. 25



Self-tuned, Dual-wave Ferrite Rod Aerial, 15 - each.

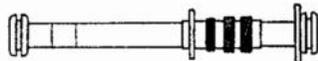Designed for use in pocket Transistor receivers. Descriptive folder with circuit-component layout, and wiring instructions for a three-Transistor regenerative receiver. Price 6d. NO aerial, earth or tuning condenser required. Operates speaker from 3 Penlight cells. All parts, including cabinet and chassis, available from component stockists.



Miniature Transistor IFTs & Osc. coil for 315 kc/s. 6-6 ea. FRM 2 Transistor Ferrite Rod Aerial, 10/-. Available from component stockists. Stamp for complete lists and circuits.

THE TELETRON Co. Ltd.
266 Nightingale Rd., London N.9
HOW 2527

COPPER WIRE

ENAMELLED, TINNED, LITZ, COTTON AND SILK COVERED. RESISTANCE WIRES.

1 oz., 2 oz. & 4 oz. REELS.

All gauges available.

E.A. SCREWS, NUTS, WASHERS, soldering tags, eyelets and rivets, EBONITE AND BAKELITE PANELS, TUFNOL ROD, PAXOLIN TYPE COIL FORMERS AND TUBES.

ALL DIAMETERS.

Latest Radio Publications. SEND STAMP FOR LISTS

SPECIAL OFFER

G.E.C., B.T.H. & WESTINGHOUSE
GERMANIUM CRYSTAL DIODES

1/- each. Postage 2!d.

Diagrams and three Crystal Set Circuits Free with each diode.

A large purchase of these fully GUARANTEED diodes from the manufacturers enables us to make this attractive offer.

CRYSTAL SET


INCORPORATING THE SILICON CRYSTAL VALVE

Adjustable Iron Cored Coil. RECEPTION GUARANTEED

Polished wood cabinet, 15/-, post 1/3 A REAL CRYSTAL SET, NOT A TOY

POST RADIO SUPPLIES

33 Bourne Gardens, London, E.4

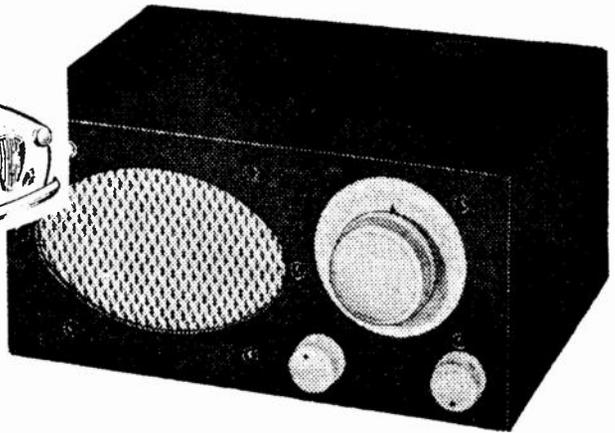

A MODIFIED VERSION OF OUR 1955 RECEIVER FOR A FORD "CONSUL"

By A. N. Robinson

(Concluded from page 327 July issue)

Aerial Connection

A TELESCOPIC aerial is mounted on the top of the offside wing just forward of the windscreen pillar and the co-axial cable is fed through the bulkhead to the R.H. end of the shelf, behind the instrument cluster, and so to the back of the set. The corresponding socket on the back of the chassis is turned through 90 deg. on a small block, to avoid an unnecessary and severe kink in the coaxial cable. If, for any reason, the aerial is mounted on the nearside of the car, it will be necessary to move this block slightly in a nearside direction and point the socket accordingly.

Power Supply

The use of a vibrator or a rotary converter can best be determined by the constructor. As there is very little space below the bonnet of a Consul, particularly when a heater has been fitted, the writer decided to install an ex-W.D. vibrator unit of Pye make in the boot, in the otherwise unused space to the offside of the spare wheel. This is fastened by bolts passing through the floor of the boot.

Heavy screened cables were used for L.T. feed and H.T. return and these were pulled through the appropriate channel in the roof, using a length of expanding curtain wire as a "fish." At the forward end they appeared on the shelf, close to the offside windscreen pillar, and were passed over the steering column, behind the instrument cluster, to the centre of the shelf, at which point the seven-pin plug was attached.

The L.T. feed from the voltage regulator terminal block and the earth connection are taken to the same point through an existing hole in the bulkhead to the right of the voltage regulator.

Installation

The installation of the set is extremely simple if the following sequence is observed. Remove the single Philips-head setscrew and nut securing the front edge of the shelf at the nearside end. This corner of the shelf should now be pressed downwards and a distance piece such as a screwdriver handle inserted to keep it down to increase the gap through which the set must be inserted. There is neither danger nor

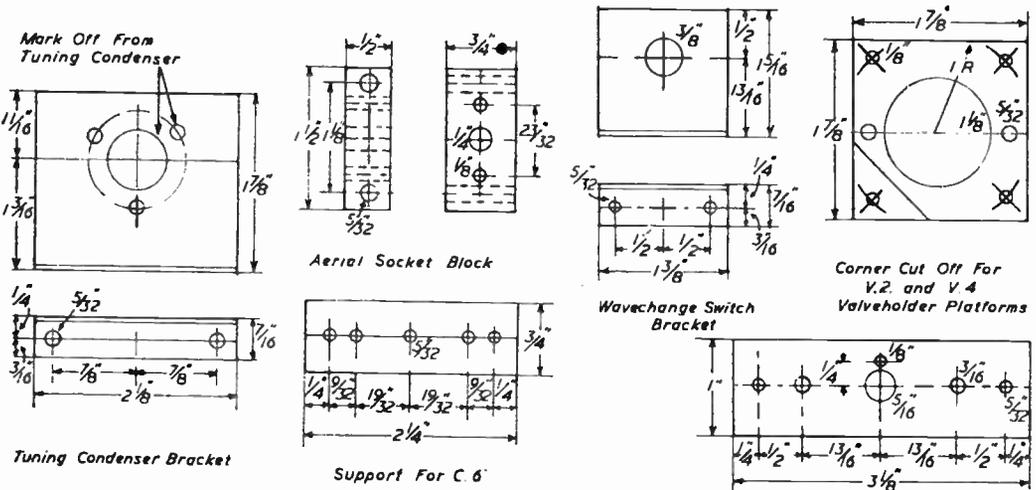


Fig. 8.—Details of the various brackets and other metal fittings.

Support For QOS170

difficulty in this operation which has been carried out at least a dozen times by the writer.

The set is now slid over the lip of the shelf, the left-hand end leading. In this position the seven-pin plug and the coaxial plug are inserted. The set can now be rotated to face forward, and slid along the shelf to the centre. Replace the Philips-head setscrew.

The prototype is fastened down by two unobtrusive external angle pieces on the sides at the front with small bolts passing downwards through the shelf thickness. These must be located clear of the heater and handbrake controls. In addition it is held down by a piece of eraser rubber wedged between the top

(Continued on page 401)

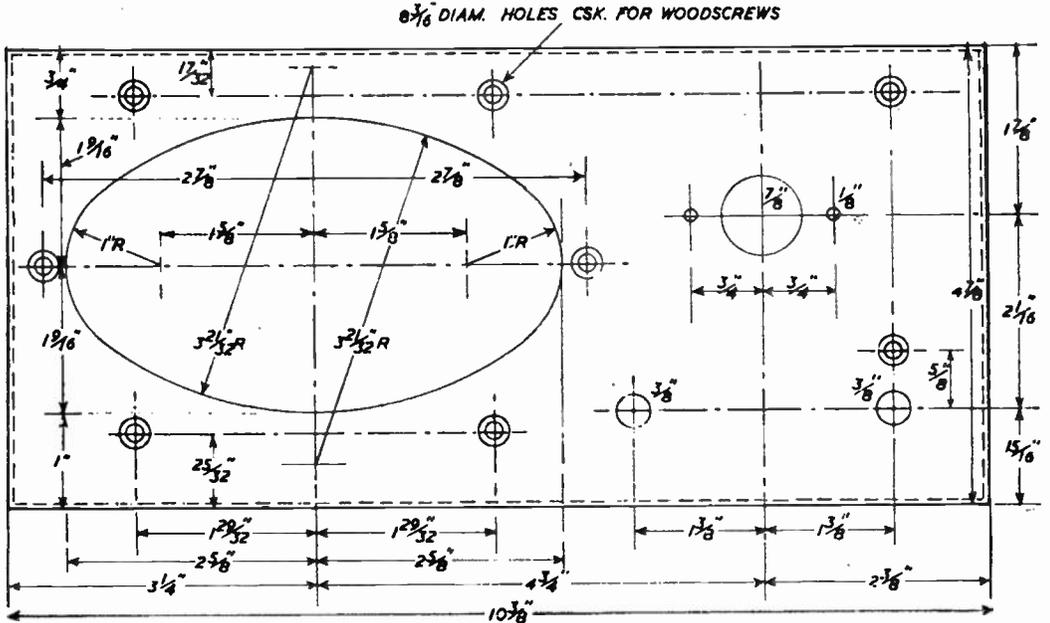


Fig. 7.—Details of the metal containing cabinet.


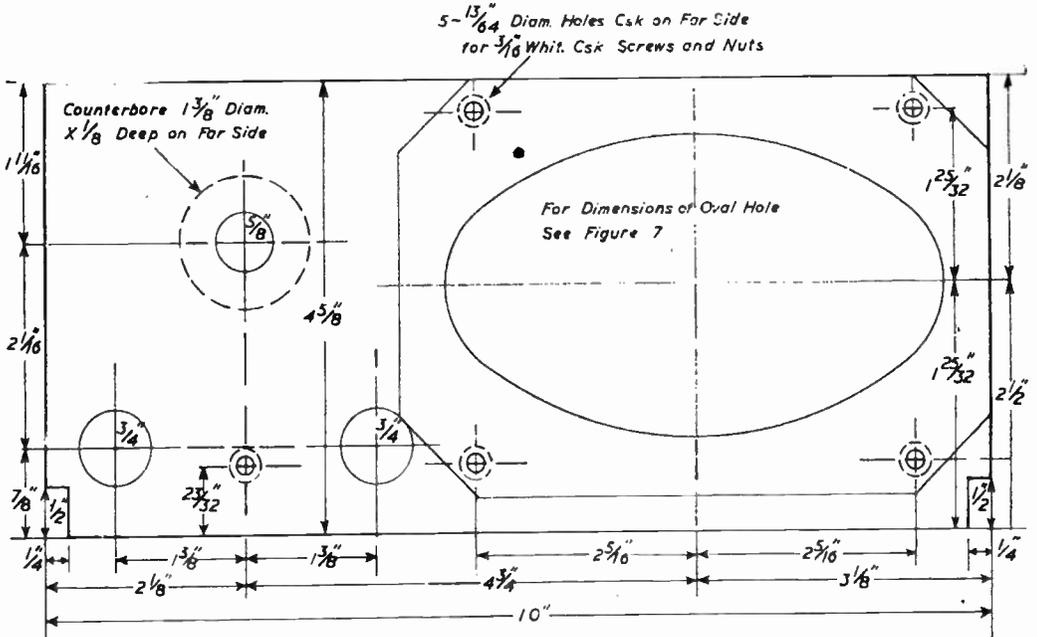


Fig. 4.—Details of the plywood panel, 1/2 in. thick, viewed from rear. Shaped area to be cut away to depth of 1 ply.

COMPLETE KITS of PARTS for the "HI-FI" ENTHUSIAST

The MULLARD "5-10" MAIN AMPLIFIER

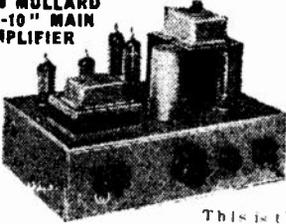

This is the very latest design and needs no recommendation from us. Our Kit is complete to Mullard's specification, including the latest GILSON ULTRA LINEAR OUTPUT TRANSFORMER and the entire MULLARD Valve line up. ALL SPECIFIED COMPONENTS are supplied. **PRICE OF COMPLETE KIT OF PARTS: £11.10.0.** (Plus 5/- carr. & ins.)

THE full SPECIFICATION and PRACTICAL BUILDING INSTRUCTIONS for these Units are available for 1/6 each. SPECIAL PRICE REDUCTION. We supply the two complete Kits—Mullard 5-10 and "fidelity" Preamplifier—for £16.16.0. We also supply both fully assembled and ready for use for £19.19.0.

STERN'S "fidelity" PREAMPLIFIER-TONE CONTROL UNIT
"A design for the music lover"



Briefly it has inputs for all types of MICROPHONES, HIGH and LOW GAIN PICK UFS and a RADIO TUNING UNIT It incorporates (a) GRAM EQUALISING CONTROL. (b) STEEPCUT FILTER. (c) Continuously variable BASS and TREBLE CONTROLS and a variable OUTPUT CONTROL which enables its use with any type of Amplifier. **PRICE OF COMPLETE KIT OF PARTS (Plus 5/- carr. and ins.) WE ALSO OFFER IT ASSEMBLED, READY FOR USE. £8.00.**

STERN'S "HIGH QUALITY" 8-10 WATT AMPLIFIER



Has power supply for Radio Tuning Unit.

PRICE OF COMPLETE KIT OF PARTS (Plus 5/- carr. & ins.) **£7.10.0.**

SUPPLIED ASSEMBLED and READY FOR USE **£9.10.0.** Proved one of the most popular models: yet offered to the HOME CONSTRUCTOR. Provides excellent reproduction up to 8 watts, employing 6V6's in push-pull, incorporating negative feedback. Provides for use of both 3 and 15 ohm speakers.

WE HAVE THE FULL RANGE OF DULCI CHASSIS IN STOCK



THE MODEL H.4. is illustrated but all Chassis and Tuners are similar—send S.A.E. for leaflets, H.P. and CREDIT SALE TERMS are available.

The following two RADIOGRAM CHASSIS are very well designed and reproduce most excellent quality on both Radio and Gram.

- MODEL H.3. A 3 Waveband AM FM CHASSIS **£20.17.0.**
- MODEL H.4. A 4 Waveband AM FM CHASSIS **£24.6.6.**
- TUNER UNIT CHASSIS
- THE F.M./F.TUNER CHASSIS with self-contained Power Supply **£17.10.3.**
- MODEL H.4.T. A 4 Waveband AM FM TUNER with self-contained POWER SUPPLY **£20.17.0.**
- MODEL H.11. A combined 4 Waveband AM FM Tuner incorporating a "Hi-Fi" Control Unit—Audio Preamplifier, which has switching and connections for Tape Replay, Gram equalising, Bass and Treble Controls, etc. **£29.3.10.**
- "HI-FI" AUDIO AMPLIFIERS

- MODEL G.A.4. A self-contained 4 watt Amplifier with adjustable Tone Control Box **£9.9.0.**
- MODEL D.P.A.L.D. A 10 watt Amplifier with separate Tone-Preamplifier Unit, incorporating Bass and Treble Controls and Gram equalising **£19.19.0.**


STERN'S "F.M." TUNING UNIT

A 5-valve Tuner incorporating the latest Mullard Permeability Tuning Heart and a "Magic Eye" Tuning Indicator.

PRICE ASSEMBLED **£14.10.0.** READY FOR USE. (Plus 7/6 carriage and insurance) TERMS: (a) Hire Purchase: Deposit £7.5.0 and 9 monthly payments of 15/-; (b) Credit: Deposit £3.12.6 and 9 monthly payments of £1.6.7.

THE COMBINED AM FM TUNER is precisely similar in appearance to the above and incorporates 7 valves. It provides complete coverage of F.M. Transmissions and MEDIUM WAVEBAND giving a good selection of foreign stations.

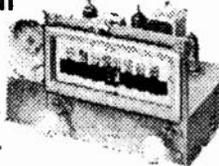PRICE **£16.18.0.** TERMS: (a) Hire Purchase: Deposit £9.9.0 and 10 monthly payments of £1.1.0. (b) Credit: Deposit £4.15.0 and 9 monthly payments of £1.14.7.



Expressly developed for very high quality reproduction of Gram Records and particularly suitable for high quality reproductions of the F.M. transmissions. Two models are available:

- (a) The "COMPACT 5-2" A Two-stage high sensitivity Amplifier having SEPARATE BASS AND TREBLE CONTROLS and designed to give up to approx. 5 watts with very pleasing quality. PRICE **£8.6.0.** (Plus 5/- carr. & ins.)
- (b) The "COMPACT 5-3" A Three-stage version of the "5-2" model but in this case having an additional stage and incorporating Negative Feedback. PRICE **£8.16.0.** (Plus 5/- carr. & ins.)


A separate POWER SUPPLY UNIT to operate with these amplifiers is available for £2.10.0. Has additional supply available for Radio Tuner, etc.

MODERNIZE YOUR OLD RADIOGRAM

- ★ THE LATEST A.M./F.M. RADIOGRAM CHASSIS.
- ★ A NEW 4-SPEED AUTOCHANGER.

THE NEW ARMSTRONG PB. 409 A.M./F.M. Radiogram Chassis

"A chassis for those who want the highest quality." ● A 9 valve line up employing the latest MULLARD preferred-type valves. ● Provides complete coverage of the V.H.F./F.M. Transmissions plus the Short, Medium and Long Wavebands. ● Has Push-Pull Output with Negative Feedback for 6 watts peak Output. ● Quick Action "Piano Key" Selectors and separate Bass and Treble Controls. ● Has "Magic Eye" Tuning Indicator. ● Dimensions 13in. x 9in. x 8in. high. Dial size 11in. x 5 1/2in. PRICE **£29.8.0.** TERMS: Credit £7.7.0 and 9 monthly payments of £2.14.0. (Plus 6/- carr. & ins.) H.P. £14.14.0 and 12 monthly payments of £1.7.3. SEND S.A.E. FOR ILLUSTRATED LEAFLET.

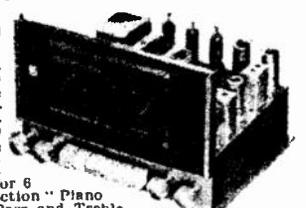

RECORD PLAYERS AT GREATLY REDUCED PRICES

THE VERY LATEST MODELS OFFERED AT GREATLY REDUCED PRICES
Send S.A.E. for ILLUSTRATED LEAFLET.


AN EXCEPTIONAL "CASH ONLY" OFFER £7.19.6.

THE NEW 4-SPEED B.S.R. MONARCH

- Complete with High Fidelity Crystal "Turn-over" Head which incorporates separate stylus for L.P. and 78 r.p.m. records. ● A "MIXER" Unit that will autochange on 5in., 10in. and 12in. records of same speed.
- Incorporates the Manual Control position.



STERN'S "COMPACT 5" AMPLIFIERS

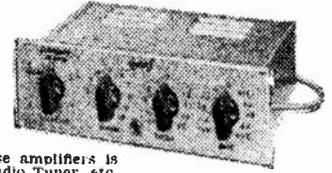

CALLERS ONLY
We have in stock various designs for HOME CONSTRUCTORS including F.M. Tuners, A.M./F.M. Tuners, Midget Battery Portable, Mains Units, etc., etc.

High "Q" Coils



4/- EACH
Iron dust cores. Clip in fixing. **EXTREMELY SMALL**
AMAZING EFFICIENCY
For Superhet T.R.F. or Transistor operation.

Potted Coils

Iron dust cores, clip-in fixing.
5/- EACH
THE LATEST in modern technique. Ideal for crystal tuners.

All coils for Collaro Tape

Transcriptor pre-amp. BIAS OSC. Coil
Type QT9
7/6



STATION SEPARATOR

HOME LIGHT-THIRD-LUX ETC.
10/6
Not a guaranteed cure but — A positive answer to selectivity problems.




STOP!

T.V. Patterning
10/6
An easily fitted—Simple Remedy



FERRITE Rod Aerials

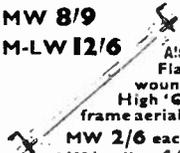MW 8/9
M-LW 12/6
Also Flat wound High 'Q' frame aerials
MW 2/6 each
LW loading 4/-



I.T.A. Converter

To fit inside T.V. KIT
65/- complete **£4**
Very efficient. Can be built in an evening. Full instructions etc.



Dial assembly for OSMOR Coils

24/6 Execution in bronze 4/-
Other dials 5/- x 5/-
3/6 each includes spot markings for trawler band.



OSMOR (Frequency Controlled) F.M. Switch-tuned Feeder.

Dimensions 4" x 4" (5 1/2" deep). A completely stable drift-free unit for adding to existing radio or H.F. amplifier.
EASY TO BUILD.
Wiring diagram & circuit on request.

OSMOR COILS FREE!
ARE BEST FOR Selectivity & Performance

Send 10d. (stamps) for fully descriptive literature including OSMOR DESIGNS — 5-Valve S'Het, Miniature ditto, Battery and Battery Mains Receiver, Mains T.R.F. S'Het and T.R.F. Feeders, Band 3 Converters, Wiring Diagrams, Chassis Templates, Coil & Coilpack information and price lists and information on circuits in "Wireless World," "Practical Wireless," "Radio Constructor." Full Circuits included. See also Classified Advs. on page 411.



(Dept. PW13) **418 BRIGHTON ROAD, SOUTH CROYDON, SURREY**
CROYDON 5148/9



"MY BENNETT COLLEGE TUTOR MIGHT HAVE BEEN IN THE ROOM"

PERSONAL POSTAL TUITION

- WHAT CAREER DO YOU WANT?**
- Architecture
 - Building
 - Chemistry
 - Commercial Art
 - Diesel Engines
 - Draughtsmanship
 - Electrical
 - Engineering
 - Electric Wiring
 - Forestry
 - Locomotive
 - Engineering
 - Machine Design
 - Mechanical
 - Engineering
 - Motor Engineering
 - Plumbing
 - Power Station Eng.
 - Quantity Surveying
 - Radio Engineering
 - Sanitary Science
 - Accountancy Exams
 - Book-keeping
 - Commercial Arith.
 - English
 - General Education
 - Geography
 - Journalism
 - Language
 - Mathematics
 - Modern Business
 - Methods
 - Police Subjects
 - Salesmanship
 - Secretarial Exams
 - Shorthand
 - Short Story Writing
 - and many others
- GENERAL CERTIFICATE OF EDUCATION
R.S.A. EXAMS.

Every Bennett College student enjoys this friendly, intimate coaching right through his course. A list of the courses are listed opposite. Tell us your subject. We will send you the Bennett College Prospectus and the famous FREE book "Train your mind to SUCCESS." This will show you how you can advance to a better future by Personal Postal Tuition. Fill in and post the coupon today.

BENNETT COLLEGE
(Dept. H. 104 PT) SHEFFIELD

Please write in plain letters.

Name:

Address:

Age:

Sex:

Occupation:

Subject:

Other:

Send me under 21

Post this coupon NOW!

ALTHAM RADIO CO. LTD.

Jersey House, Jersey Street, Manchester, 4.
Tel.: Central 7834, 5/6

WE OFFER:

- TRANSISTORS Famous red spot junction ... each 7/6
- RECEIVER R28/ARC5. 100 - 156mc/s ... £3
- TRANSMITTER BC950A. 100 - 124 mc/s two 832A valves etc. ... £7
- AMPLIFIER RCA. 50 watt (use with pre-amplifier) ... £10
- RECORD PLAYER HMV. 33 1/3 r.p.m. only in neat cabinet ... 55/-
- RECEIVER R3A/ARR2X. 234-285 mc/s (11 valves, complete with dynamotor, rack, control unit, etc.) ... £4

FREE TRANSISTOR for every £4 value purchased (two transistors for £8, etc.).

All goods new, original manufacturers' packing. Carriage Paid. Cash with Order.

WE WANT TO BUY:

All U.S.A. Test Sets prefixed TS, also APN3, APN9, ARC3, ARN7, ART13, BC221, BC788C.

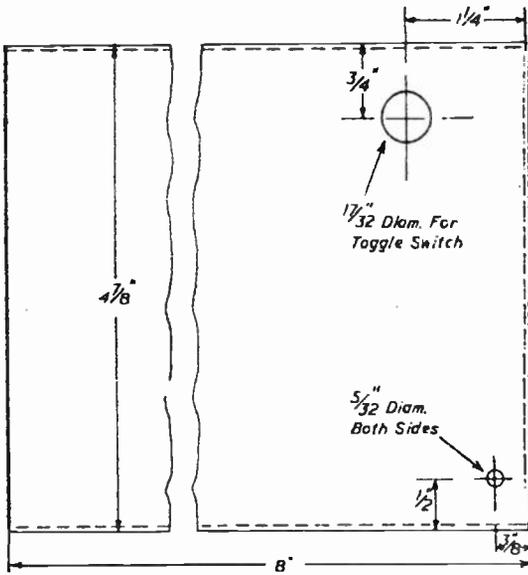


Fig. 7(a).—An extension of the case in Fig. 7.

of the casing and the underside of the windscreen wiper housing. The location of this is readily visible once the central ashtray has been removed.

Suppression of Interference

Very little suppression has been found necessary. Most interference will come from the sparking plug leads, and this will be in the form of a "plop" at every firing stroke. The simplest cure is to fit a suppressor of the TV type to the centre connection (i.e., the coil lead) of the distributor head. Incidentally, if the car is a late model, this type of suppressor will already have been fitted by the makers. If ignition interference should still be troublesome, separate suppressors should be fitted to the individual plug leads, as close as possible to the plugs themselves. "Cut-lead" types can be used here, but a more satisfactory job will be obtained by installing shrouded models.

The second principal source of trouble is the dynamo which emits a whine rising in pitch as engine revs. are increased. This can be eliminated by fitting a 1 μ F 150-volt condenser across the "D" terminal and earth, preferably directly on the dynamo itself. A suitable type—much more robust than the normal radio by-pass condenser—is marketed by Radiospares.

The voltage regulator will normally already have been suppressed by the makers, as will also the

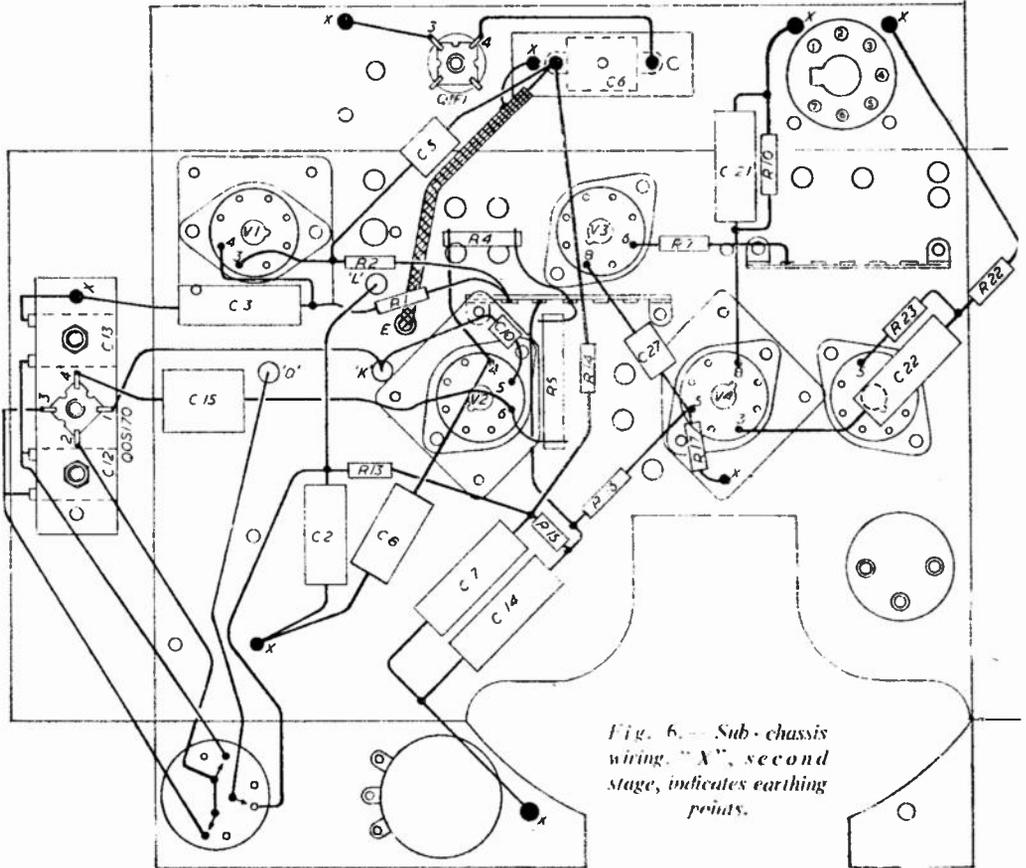


Fig. 6.—Sub-chassis wiring. "X", second stage, indicates earthing points.

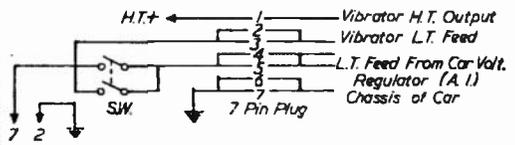
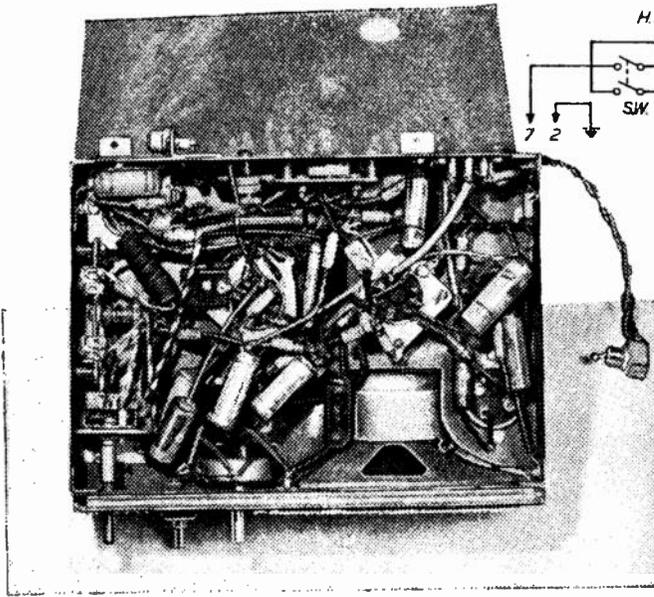


Fig. 9.—Details of wiring to the plug.

will produce a healthy crackle when in use and "blinking" indicators will produce a rhythmical clicking. The stop-light switch will be responsible for a click when the brake pedal is depressed, and braking may result in a slight hiss, presumably from the generation of static electricity, but this seems to be a freak effect and may be dependent on weather conditions.

General

All trimmer screwheads were liberally coated with beeswax after final adjustments had been made, and after continuous service over nearly a year no troubles have been experienced from vibration. Very little suppression has been found necessary, suppressors having been fitted only to the sparking plugs and the generator.

blower motor, if a heater has been fitted. A number of minor sources of interference remain, but as their effect is only of a transient or temporary nature, suppression has been ignored. The starter motor

a year no troubles have been experienced from vibration. Very little suppression has been found necessary, suppressors having been fitted only to the sparking plugs and the generator.

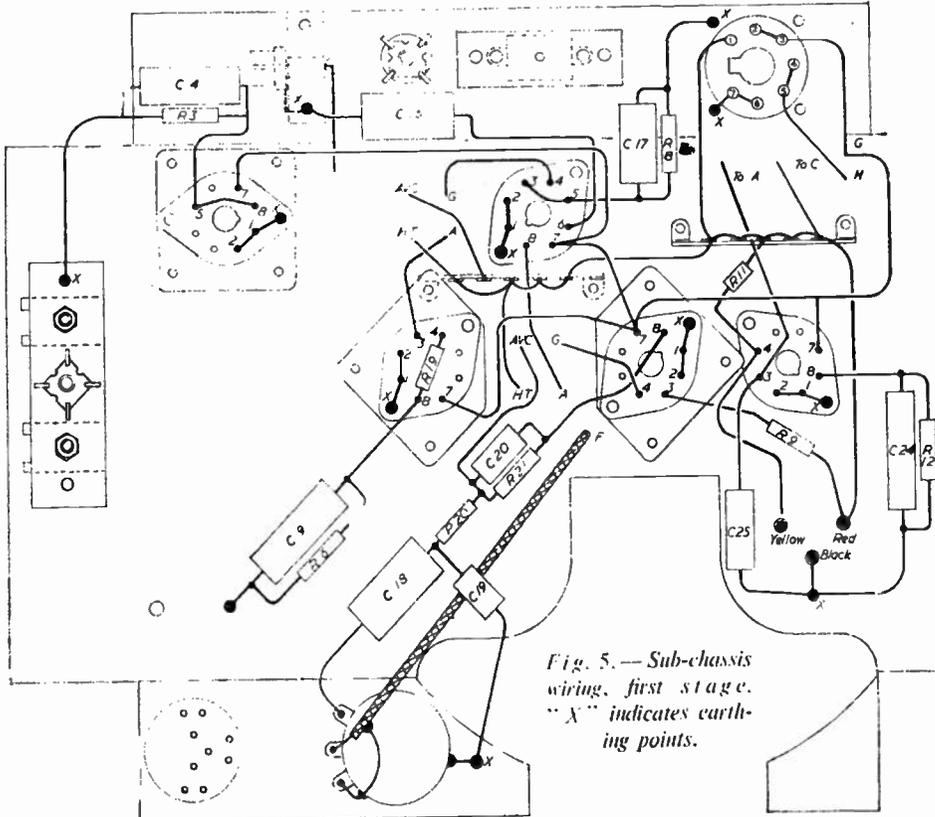



Fig. 5.—Sub-chassis wiring, first stage. "X" indicates earthing points.



A great little condenser!

THE JACKSON "00" TWIN CONDENSER

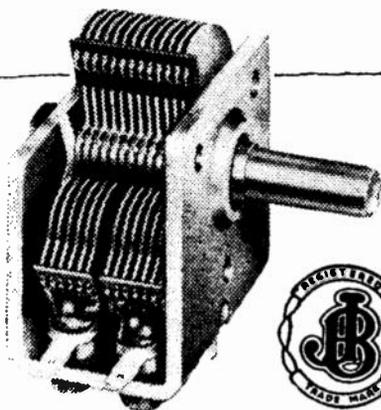Designed for use in miniature transistor receivers. The front (aerial) section is 208pf. to provide coverage for medium waves, and the rear section is 176pf. which may be padded to match the oscillator, very robust yet light weight. Front area 1 1/32in. x 1 17/32in. x 1 1/32in. deep. Price 9/6.




JACKSON BROS.
(London) Ltd.
Kingsway, Waddon, Surrey
Tel.: CR0ydon 2754/5

it's reliable...it's made by Jackson

Specify **DULCI** for perfection

GA4 High Fidelity Amplifier

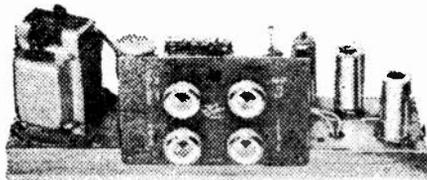

4 watt 4-valve circuit with a frequency response of 40-15,000 c.p.s. Neat Control Panel, size 6in. x 4in., on fly leads for individual mounting (main chassis, 14in. x 4in. x 5 1/2in.). Input selector switch matching to Radio L.P. and 78 r.p.m. records. Separate bass and treble controls, giving wide range of cut and lift. Volume Control. Rotatable Mains Transformer for hum cancellation. Price £9.9.0.

H4 Radiogram Chassis AM/FM

7 valve 4-wave band superbet with F.M. (V.H.F.). Magic eye tuning indicator. High sensitivity. Bell clear quality. Dial size 11 1/2in. x 5 1/2in. Sockets to connect Speaker (3 and 15 ohm). Pick-up, Aerial, Earth, F.M. Dipole and provide power for Gram. Motor from mains.




Price £24.6.6. inc. tax.

Also Model H3. Similar to H4 above, but with 3 wavebands. Price £20.17.0.

Stylised cabinets suitable for most DULCI products are available.

FULLY GUARANTEED


To satisfy the highest sense of sound

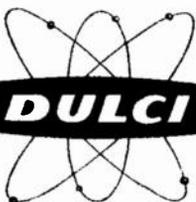

DULCI COMPANY LIMITED, 97-99 VILLIERS ROAD, LONDON, N.W.2.

TELEPHONE: WILLESDEN 6678/9

TRANSMITTING TOPICS

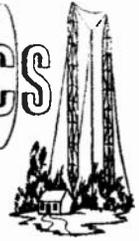

POINTERS ON BEAMS

By O. J. Russell, B.Sc., A.Inst.P. (G3BHJ)

THE "ultimate" in aerial systems for the average amateur, and indeed the keen S.W.L., is some form of directive beam array. At any rate, where space does not permit of unlimited long wires and rhombic arrays, but where space is available for some form of beam, the "dream" of the ham is a beam aerial. While on the subject of "long wire" aeri-als, however, it should not be forgotten that the "long wire" array is used at many stations consistently working DX in many directions, as apart from the main lobes, the long wire has good general coverage in many other directions as well. However, the long wire does have sharp "nulls" in some directions. This fact was brought home at G3BHJ very recently, when a long wire aerial was lengthened and shifted in direction by a mere 15 to 20 degrees. This reduced the 21 Mc/s signals at a local nearby amateur's QTH, a mere half mile or so, from a S9 plus 30 db to a mere S5 to S7 varying according to wind swaying the aerial from exact null position! Signals on the long wire in that particular direction, in fact, were three S points approximately down on the signal radiated from an odd length of wire lying on the shack floor and tuned up "for laughs" in local tests on the "null" properties of this particular long wire main aerial. This "null" effect was put to good use on reception, as the powerful local ground wave of the other station on reception on the long wire was reduced from an ear-splitting receiver-paralysing signal to a comfortably moderate loudness, thus

signals enhanced in the forward direction, but QRM arriving from the rear is greatly attenuated. Thus the attenuation of European signals on reception was a much valued aspect of the writer's 20 metre DX chasing with a three-element rotary. Further, of course, the attenuation of noise and even "jammer" QRM is a further boon of the "back to front" discrimination of a beam array. The combination of forward directivity on reception coupled with discrimination against rearward noise and QRM generally, thus effects a double advantage on reception. Coupled with the enhanced signal from one's own transmitter in the forward direction, a threefold gain is thus achieved in increasing solid DX QSOs. To drive home this point, consider two stations, each using simple two-element beams on both reception and transmission. A simple two-element beam may thus give a 5 db gain on transmission to the receiving point. If the receiving point also uses a simple beam giving a 5 db gain, the total "transmission path gain" is thus 10 db over the use of simple dipoles. This alone is equivalent to a tenfold increase in power of the transmitters, and points the moral that a relatively cheap aerial system gives at low cost the benefits otherwise derived only by a high cost increase in transmitter power, a change, say, from 100 watts to 1 kilowatt—a very expensive change! Furthermore, QRM arriving from the rear may be attenuated by ten or more db's. This possible 20 db gain on reception gives a "communication effectiveness" equivalent to a hundredfold increase in transmitter power as far as rearward QRM is concerned! This, of course, is old stuff to the

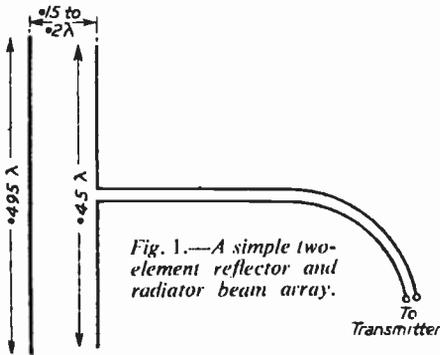


Fig. 1.—A simple two-element reflector and radiator beam array.

greatly facilitating mutual DX chasing activities on 21 Mc/s.

The twin points of directivity and reception serve to emphasise two of the important aspects of beam arrays. First there is the directional peaking of the radiated signal, a factor usually regarded as the only function of a beam. However, the directionality on reception serves a dual purpose, for not only are

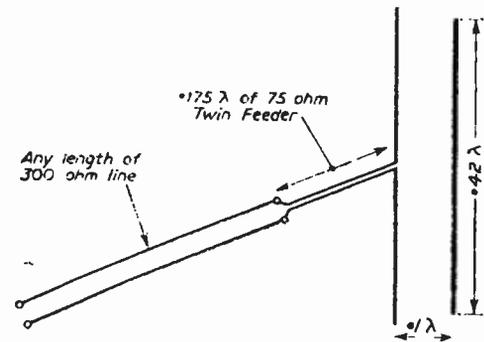


Fig. 2.—A close-spaced array with a transforming length line to match the low centre impedance to a "Flat" 300-ohm line.

hardened amateur, who is asked to bear with us, because we are primarily considering the beginner and tyro in this present article.

Word of Caution

Before the beginner fired with enthusiasm and thirsting for a 20 db increase in "communication effectiveness" rushes out and hangs a reflector wire behind his halfwave dipole, it is necessary to sound a note of caution. Even with the simplest beam, optimum results are not to be obtained without some care and attention to detail. Thus a "simple two-element beam" may produce some surprises. One surprise is that it can have gain, a little gain, in both directions at once, and thus give very little apparent boost in signals and show little, if any, "back to front" ratio. The "simple two-element beam," therefore needs a little further discussion and clarification if good results are to be obtained.

For a "two element" beam, there is a choice between a "radiator and reflector" array and a "radiator and director" array. As is widely known, a "radiator and director" two-element array can give slightly higher gain than a radiator and reflector array. However, there is a price to be paid for this slight increase in gain, as a director-radiator array is liable to have a sharper and more critical tuning adjustment plus a lower radiation resistance than a reflector-radiator array. Thus practically there is little to choose between the two, especially as less than a db of gain is involved. However, a director array is a closer spaced and therefore a compacter affair than a radiator-reflector combination two-element beam. In fact, a spacing of a tenth of a wavelength may be employed with a director plus radiator beam, whereas a spacing of .15 to .20 might be employed with a radiator-reflector array. However, this leads to the fact that variations in spacing of the elements in a two-element array may be compensated for by tuning adjustments of the parasitic radiator length. Thus both types of two-element array may be operated with wide variations in element spacings, provided the beam is "tuned up" for optimum results. The wider spaced arrangements will be far less critical than the closely spaced arrays. Generally, spacings of .1 to .15 wavelength are "close" spacings, while spacings of .2 or .25 or more are "wide" spacings. Unless compactness is a "must," therefore, the recommended "simple two-element beam" is a radiator plus reflector as shown in Fig. 1. No exact element lengths are laid down, however, as these will be subject to many varying factors. The old "cut-and-try" method is unbeatable in beam adjustment. Thus, if wire elements are used a pair of clippers will effect adjustment on trial beam before constructing the final version.

If aluminium or similar metal tube construction is used for the elements, a telescoping end portion of tube will enable "tuning-up" adjustments to be readily effected. In any case it should be stressed that dipole resonant lengths and parasitic element lengths also depend upon the diameter of the element used, so that specification of "exact" lengths would require a specification of the element diameter as well. For a two-element beam, resonating the dipole, and then adding the parasitic element and making a first trial adjustment for optimum forward gain is simple enough. The radiating dipole may then be trimmed to resonance at the centre frequency required, and the parasitic element adjusted for optimum back-to-front ratio consistent with reasonable gain. Such tests, while facilitated by a simple field strength

indicator, such as a germanium crystal rectifier and milliammeter, may be carried out on reception at a pinch. Even the crude but very serviceable indication given by a flash lamp bulb at the centre of a halfwave length of wire may be employed. In all cases, however, the "field strength indicator" should be as far away from the array as feasible, a full wavelength or more being satisfactory.

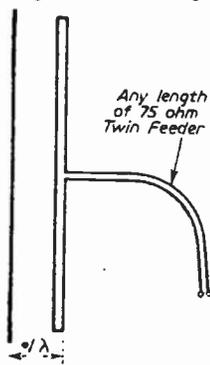


Fig. 3.-- A close-spaced array may have the radiator folded to match 75 ohms line.

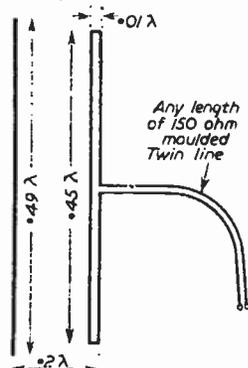


Fig. 4.-- A wide-spaced two-element beam may have a folded radiator to give a match to 150-ohm line.

Feeding the Aerial

Having decided upon a simple but two-element beam for initial tentative experiments, the question of "feeding the brute" rears its ugly head. Unfortunately, the feed impedance of the radiator may vary widely with the spacing, and to a lesser extent the tuning of the parasitic element. Thus a close spaced director plus radiator array may have a feed impedance of some 12 to 15 ohms, while a wide spaced array may have a feed point impedance of around 50 ohms. While the wide spaced array could be fed with twin low-impedance feeder without much harm, the close spaced array might be troublesome. Therefore, for a close spaced array, the recommended feed is via a quarterwave matching transformer of 75 ohm twin feeder cable. This will give a tolerable match up to a 300 ohm moulded twin feeder line. The propagation constant of the 75 ohm twin cable should be obtained from the makers, and the length of a quarter wavelength in free space multiplied by this to give the length to which the feeder should be cut. The propagation constant varies slightly from maker to maker, but in an emergency a value of 0.70 is close enough. Thus a length of 0.175 of a free-space wavelength should serve adequately. A "director plus radiator" beam might thus be as illustrated in Fig. 2. A further solution is to use a folded radiator element. If the folded element is made of the same diameter wire or tubing for both upper and lower limbs, this will quadruple the feed point impedance. Thus a two-element close spaced array might be fed by 75 ohm moulded twin feeder as in Fig. 3, while a wide spaced beam could be fed with 150 ohm twin feeder as shown in Fig. 4.

Compact Arrays

Having suffered from confined locations in the past, the question of "compact" beams immediately

(Continued on page 409)

YOU can build any of these at Low Cost!

R.C.S. VALVELESS "ALLTIME" RADIO BATTERYLESS



REALLY WORKS FOR LIFE!

Works without valves or batteries. Will never run down or burn out. Utilises sensational new Loopstick tuner. Will receive local stations any time. Permanent crystal diode in attractive case ... **17/6**
Full construction data, point-to-point circuit and price list of components, 1/6.

TRANSISTOR POCKET RADIO




The ideal low cost transistor pocket radio for the beginner. The Two-Stage circuit utilises the new R.C.S. VARILoopstick transistor coil. A specially designed miniature .0005 tuning condenser permits the receiver to be in a case which fits in the palm of your hand. Works for months off small battery costing 7d. Can be built in 30 minutes. PRICE **30/-**

All components are sold separately, full construction data, including plan to parts for 2/-.

1v. WORLD WIDE SHORT-WAVE RADIO

EXPLORE THE WORLD ON SHORT WAVES!

Can be built for from our list of components which can all be purchased separately, covers 10-100 metres and is capable of receiving speech and music from all over the world. Price includes the famous 954 acorn valve and one coil covering 40-100 metres. Provision is made to increase to two or three valves and all components are colour coded. Send 2/- for point to point wiring diagram, layout and price list.

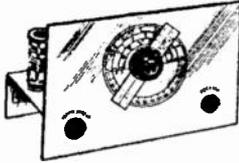

30/-

PERSONAL PORTABLE RADIO

THE SET FOR PERSONAL LISTENING

This little set was designed to give you a real personal portable radio that you can listen to anywhere without disturbing others. Use it on camping trips, in bed, in your office. Supplied with detachable rod aerial, it covers all the medium waves 200-500 metres. Average building time one hour. PRICE **30/-**
Send 2/- for specification, point to point circuit and parts price list.



Post and packing: Under 10/- add 9d.; under 40/- add 1/6; over POST FREE.

R.C.S. PRODUCTS (RADIO) LTD., 11, OLIVER ROAD, LONDON, E.17. (Mail Order only)

SOUTHERN RADIO'S WIRELESS BARGAINS

TRANSRECEIVERS. Type "18" Mark III. Two Units (Receiver & Sender). Complete with Six Valves, Microammeter, etc. in Metal Carrying Case. Untested, without guarantee but COMPLETE. £2.18.6.

RECEIVERS R109. Short Wave Receiver complete in Case with eight valves. Built-in Speaker and 6-volt Vibrator Pack. Untested without guarantee but COMPLETE. £2.18.6.

ATTACHMENTS for Type "38" Transreceivers. ALL BRAND NEW. Headphones, 15/6; Throat Microphones, 4/6; Junction Boxes, 2/6; Aerials No. 1, 2/6; No. 2, 5/-; Webbing, 4/-; Haversacks, 5/-; Valves—A.R.P.12, 4/6; A.T.P.4, 3/6. Set of FIVE VALVES, 19/- the set.

ATTACHMENTS for "18" Transreceivers. ALL BRAND NEW. Headphones, 15/6; Hand Microphone, 12/6; Aerials, 5/-; Set of SIX VALVES, 30/-.

RESISTANCES. 100 Assorted useful values. New wire end. 12/6.

CONDENSERS. 100 Assorted. Mica, Tubular, etc., 15/-.

BOMBSIGHT COMPUTERS. Ex-R.A.F. NEW. Hundreds of Components, Gears, etc. Ideal for Experimenters. £3.

LUFBRA HOLE CUTTERS. Adjustable 1/2 in. to 3/2 in. For Metal, Plastic, etc., 7/-.

QUARTZ CRYSTALS. Types F.T.241 and F.T.243. 2-pin, 1in. Spacing. Frequencies between 5 675 kcs. and 8 650 kcs. (F.T.243). 20 Mc/s and 38.8 Mc/s (F.T.241, 54th Harmonic), 4/- each. ALL BRAND NEW. TWELVE ASSORTED CRYSTALS, 45/-.

HOLDERS for both types, 1/- each. Customers ordering 12 crystals can be supplied with lists of frequencies available for their choice.

MORSE TAPPERS. Standard type, 3/6; Extra Heavy on Base, 5/6; Midget, 2/9.

TRANSPARENT MAP CASES. Plastic, 14in. x 10 1/2 in. Ideal for Maps, Display, etc., 5/6.

DINGHY AERIALS. Ex-U.S.A. Reflector Type, 4/6.

STAR IDENTIFIERS. Type 1 A-N covers both Hemispheres, 5/6.

CONTACTOR TIME SWITCHES. 2 Impulses per sec., in case, 11/6.

Postage or Carriage extra. Full List of RADIO BOOKS, 3d.

SOUTHERN RADIO SUPPLY LTD.

11, LITTLE NEWPORT ST., LONDON, W.C.2. GERard 6653

FREE TO AMBITIOUS ENGINEERS!

This 148-page Book

Have you sent for your copy?



'ENGINEERING OPPORTUNITIES'

is a highly informative guide to the best-paid Engineering posts. It tells you how you can quickly prepare at home on "NO PASS—NO FEE" terms for a recognised engineering qualification, outlines the widest range of modern Home-Study Courses in all Branches of Engineering and explains the benefits of our Employment Dept. If you're earning less than £18 a week you cannot afford to miss reading this unique book. Send for your copy to-day—FREE.

--- FREE COUPON ---
Please send me your FREE 148-page "ENGINEERING OPPORTUNITIES"

NAME
ADDRESS
.....
Subject or Exam. that interests me.....
British Institute of Engineering Technology
409B, College House, 29-31, Wright's Lane,
Kensington, W.8.


WHICH IS YOUR PET SUBJECT?

- Mechanical Eng.
 - Electrical Eng.
 - Civil Engineering
 - Radio Engineering
 - Automobile Eng.
 - Aeronautical Eng.
 - Production Eng.
 - Building, Plastics, Draughtsmanship, Television, etc.
- GET SOME LETTERS AFTER YOUR NAME!**
- A.M.I.Mech.E.
 - A.M.I.C.E.
 - A.M.I.P.E.
 - A.M.I.M.I.
 - L.I.O.B.
 - A.F.R.Ae.S.
 - B.Sc.
 - A.M.Brit.I.R.E.
 - CITY & GUILDS GEN. CERT. OF EDUCATION etc., etc.

BIET

SIGNAL GENERATOR

Coverage 130 kc/s. 84 Mc/s. Metal case 10in. x 6in. x 3in. Size of scale, 6in. x 3in. 2 valves and rectifier. A.C. mains 230-250 v. Internal modulation of 100 cps. to a depth of 30 per cent., modulated or unmodulated R.F. output continuous variable 100 mV to 10 V. C.W. and mod. switch, variable A.F. output and moving coil output meter. Grey hammer-finished case and white panel. Accuracy plus or minus 2%. £4 19.6 or 34 - deposit and final payment - 25 - P. & P. 1.6 extra.

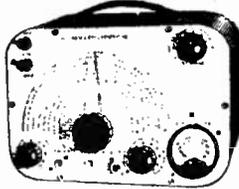


COMMERCIAL TELEVISION CONVERTER

SUITABLE ANY TV. except Phillips' ALL CHANNELS NO ADJUSTMENTS TO SET

Complete with built-in power supply 230-250 v. A.C. mains. Chrome finish case 5 1/2 in. long, 3 1/2 in. wide, 4 1/2 in. high, incorporating gain control and band switch. Illus. with cover removed.

£3. 19. 6 Plus P. & P. 2.6

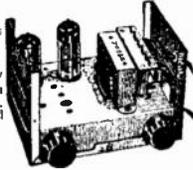

AC/DC MULTI-METER KIT



Complete 250 moving coil meter, scale graduated in A.C. P.C. volts, ohms and milliamperes. Voltage range A.C. D.C. 10, 0.1, 1, 10, 100, 1,000, 10,000. From panel, range switch, wire-wound potentiometer (zero setting) two toggle switches, resistors and meter resistor. In grey hammer-finish case.

19/6 Plus P. & P. 1.4

Point to point wiring diagram 15. See with kit.

4 VALVE ALL-DRY SUPERHET PORTABLE KIT

Incorporating Ferrite rod aerial Medium and long waves. In grey leatherette. Size 9in. x 7in. x 6in. Valve line-up: 1F1, 1R5, 1R5, 3V4. Complete kit of parts (less batteries).

£5. 19. 6 Plus Post & Packing 3/6



COMPLETELY BUILT PORTABLE AMPLIFIER

approx. size 6 1/2 in. x 2 1/2 in. incorporating 2 valves, contact-cooled metal rectifier, bass and treble lift controls. Plus double wound mains transformer 230-250 v. 39/6 P. & P. 3/6 8in. P.M. SPEAKER & O.P. TRANSFORMER, if purchased with the above, 18.6. Plus P. & P. 1.6.

COLLAR 4-SPEED AUTOMATIC CHANGER

Model 456 (suitable for use with above amplifier). A.C. mains, 230-250 v., turnover crystal head. Brand new, fully guaranteed.


£8. 19. 6 Plus P. & P. 5.

T.R.F. KIT in PLASTIC CABINET

3 valve plus metal rectifier, A.C. mains, 200-250 v. Medium and long waves. In pastel blue or brown. Valve line-up: 2 VR65s and VT22, 5S12a 15 1/2 in. long by 9in. high by 7in. deep.

£3. 19. 6 P. & P. 1.6

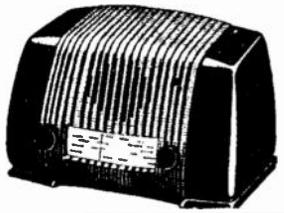Point to point wiring diagram 18. Free with kit



RADIO & T.V. COMPONENTS (Acton) LTD.

23, HIGH STREET, ACTON, LONDON, W.3
GOODS NOT DISPATCHED OUTSIDE U.K.

SUMMER SALE

'POPULAR' RADIO OR R GRAM CHASSIS 39/6



3 w/band and gram shell. 5 valve International Octal. Ideal for table gram, but still giving high quality output. 1 knob control. 8in. P.M. speaker. 7.9 with order. Set of knobs, 2. Chassis 12in. x 6in. x 7in. Less valves. Ins. & Carr. 3/6.

12 MONTHS GUARANTEE ON LATEST RECTANGULAR T.V. TUBES

We are now able to offer this wonderful guarantee, 6 months' full guarantee, 6 months' progressive. Made possible only by the improved high quality of our tubes. N.B.—All tubes are cash with order. Ins. & Carr. 15/6.

12in. T.V. TUBES, £8. Shortage may cause delay, enquire first. We may have alternative and can tell you delay if any. Ins. & Carr. 15/6.

CONVERT THAT 8in., 10in. or 12in. T.V. set to 11in., 15in. or 17in. See our catalogue for full details.

As a SPECIAL OFFER we can now supply 11in., 15in. and 16in. round type tube at £5. These tubes have a 3 months' guarantee. Ins. & Carr. 15/6.

STUMPER BARBAIN T.V. CHASSIS, 17in. £19.18.6

17in. rectangular tube on adapted chassis. Any or all channels. The TURRET TUNER can be added later as an extra at our special price, to chassis clients, 50". Chassis valve line-up (5 valves): 6SN7G, 6P25, EY1 and 2 302's. Others: £1.50, 6L8 and 74P's. These may be to your shelf. Chassis size: 11 1/2 in. x 7 1/2 in. 12 months' guarantee on the rectangular tube. 3 months' guarantee on the chassis and valves. All complete and working at any channel 1-5, but less valves. With 5 of the valves, £21.19.6. Complete with all valves, £25.19.6. Ins. & Carr. incl. tube, 25". Please state B.B.C. channels and I.T.A. channels if turret tuner required. Drawings FREE with order or 2/6.

14in. T.V. CHASSIS, TUBE AND SPEAKER, £13.18.6

As above, with 14in. round type tube, which you can convert later if you wish to a 17in. rectangular tube. With 5 valves, £15.18.6. Complete with all valves, £19.18.6. Ins. & Carr. 25" incl. tube.

Liverpool St. Stn. to Manor Park, 10 mins. FREE catalogue. OPEN SATURDAY ALL DAY.

DUKE & CO. (PW) 621 3, Romford Road, Manor Park, London, E.12.

EDDY'S (Nottm.) LTD.

(Dept. P.W.)

172, ALFRETON ROAD, NOTTINGHAM

THIS MONTH'S SPECIAL OFFERS

NEW AND GUARANTEED SPEAKERS

2 1/2 in., 15/11; 5 in., 16/11; 6 1/2 in., 16/11; 8 in., 17/11. All 2/- each extra Post and Packing.

1,200 FT. OF RECORDING TAPE at only 9/11 each, including reel. Post, etc., 1/- each.

Any Parcel Insured Against Damage in Transit, 6d. Extra.

NEW AND GUARANTEED VALVES

Post, etc., 6d. per valve Over £2 FREE.

1R5	7.6	757	8/11	DAF96	9/6	EL84	10.3
155	7.3	774	7/11	DF96	9.6	EY51	9.6
174	7.3	10F9	11.6	DK96	9.6	EY86	10.3
354	7.3	12AH8	10.6	DL96	9.6	EZ80	8.3
3V4	7/11	12AT6	9.	DM70	7/11	MU14	8.6
5U4G	7/11	12J76	9.6	EAC87	7.6	PCC84	8.
5Y3GT	7.3	12K76	8/11	EB91	6/11	PCL83	12.6
5Z4G	8.3	12Q76	9.3	ECC81	8/11	PCF80	8.6
6AT6	7.6	12J7	7/11	ECC83	8.3	PL82	8/11
6BA6	7.3	12SK7	6.	ECC84		PL83	11.6
6B6	7/11	35A5	10.6		10/11	PY80	8/11
6B86	3/6	35L6GT		ECC85	9.	PY81	8.3
6J5M	2/11		8/11	ECH81	8/11	PY82	8.3
6K76	2/11	35W4	8/11	ECH42	9.6	UBC41	8/11
6Q7G	8/3	35Z4GT	8.3	ECH35	9.	UCH42	9/11
6SK7	4/11	39/44	9.6	ECL80	8/11	UL41	9/11
6V6GT	5/11	41MP	11.6	EF80	8.3	UL84	9.6
6X4	6/11	807	3/11	EF50 (Syl.)		UF41	8/11
7B7	7/11	954	1/6		6/11	UBF80	9.6
7C5	7/11	955	3/11	EF41	9.3	UY41	7/11
7C6	7/11	956	2/11	EF91	6/11	YU11	9/11
7H7	7/11	958	3/11	EL32	5/11		1/6

IN STOCK—CARRIAGE EXTRA Not Working Televisions from 59/6. Working Televisions from £6.19.6.

arises. All but the most confined gardens will accommodate a ten-metre beam. The writer has even had a fixed ten-metre beam indoors with three elements. However, twenty-metre rotaries are a different proposition for indoor use, or even for many gardens or open spaces in city sites. The "loading coil" method may be employed to "cut down to size" a beam array for use in restricted sites. Element spacings may NOT be cut down, and due to the reduction of feed impedance a spacing of 0.15 wavelengths is suggested. Moreover, the element lengths should not be reduced to less than a quarter of a wavelength, and preferably a third of a wavelength or so should be used. For initial trials experimental loading coils should be used first to resonate the radiator, and then to resonate the reflector. It is suggested that a reflector type two-element beam be tried for a "compact" array. When initial tests have indicated the coil size required, they should then be made up. Heavy copper tube coils, self-supported, are recommended. Final tuning adjustments are best made by telescoping end pieces on tubular elements. Tube elements are in any case virtually necessary for "compact" coil loaded arrays, to assist in keeping the bandwidth of operation wide even with the reduced element lengths which tend to produce a low radiation resistance, and hence a sharper tuning beam of reduced bandwidth. Thick elements help to broaden the bandwidth of the beam, and reduce losses which may be quite high in beams of close spacing plus loaded "compact" elements. The use of a centre loading coil in the radiator has one feature that is an advantage, as it enables the feeder to be matched in by tapping across the centre turns of the coil (Fig. 5), or by using a link winding as in Fig. 6. The efficiency of the famous Moseley beams marketed by the American Moseley Electronics Corporation is greatly assisted by the use of this link coil centre-feeding system. The U.S.A. satellite project is in fact using many of these Moseley beams for timing signal and other communication links, a tribute to their efficiency.

A further method of broad banding a compacted beam is to use "skeleton" forms of "fat" elements, somewhat on the lines of the "fat" groundplanes previously described. While there is no space to describe the innumerable variants possible upon this theme of fattened elements, one typical illustration is shown in Fig. 7. This is coil loaded, and resonated by squeezing or pulling the coil turns. A radiator of this type may be fed by the link coil system referred to above, and a reflector of similar construction may be suitably spaced to provide a simple two-element compacted beam. Such an aerial should be docile and easy to load up on frequency. Due to the "broadbanding" effect of the skeleton "fat" elements, operation over a good bandwidth is feasible.

A beam of high gain and directivity is of little use if it cannot be operated over more than a narrow band frequency. Tubing elements rather than wire,

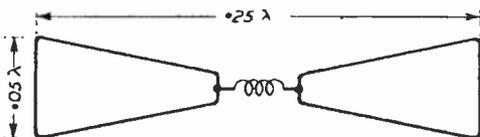


Fig. 7.—A loaded element may be broad-banded by skeleton "Fat" construction from bent wire.

or skeleton fat elements bent from number 10 gauge wire or thin tubing are the solution to broadbanding requirements, providing that the beam elements are not spaced too closely. For simple two-element beams the .10 to .20 spacing will be found satisfactory.

A More Complex Problem

In the case of three or more element beams the situation becomes more complex, as there is an almost unlimited number of combinations of element spacings

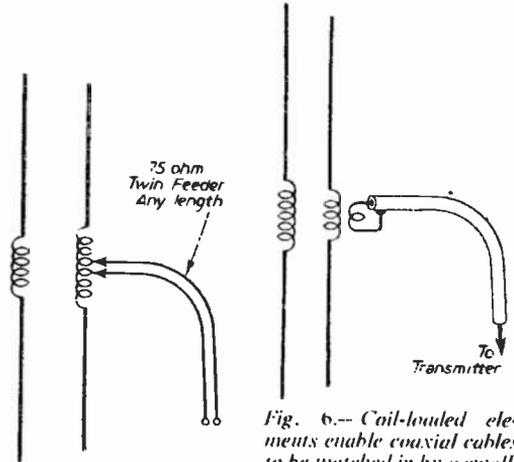


Fig. 5.— Compact coil loaded dipoles may be fed by tapping the feeder into the centre of the loading coil.

Fig. 6.— Coil-loaded elements enable coaxial cables to be matched in by a small, tightly coupled link winding wound over the loading coil, a very efficient and handy method of feeding "Compact" dipole" elements.

and tunings which will provide approximately the same gain, but often with marked variations of the dipole radiator feed impedance. Here again the use of two close spacing is to be avoided if possible. A close-spaced three-element beam may have little or no gain over a wide-spaced two-element beam that occupies about the same physical area. Moreover "compacting" techniques should also be applied with caution, as these become very tricky with close-spaced multiple-element beams. Indeed, a wide-spaced full-length element beam would probably perform about as well as a multiple-element beam with compacted elements and close spacing between elements. For a three-element beam a reflector spacing of around .15 wavelength plus a director spacing of .20 to .25 wavelengths is a good compromise

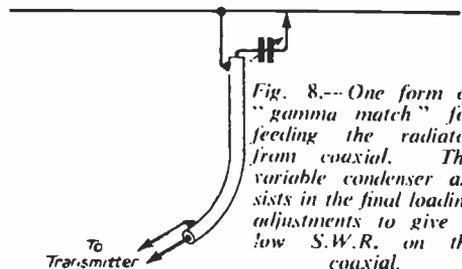


Fig. 8.— One form of "gamma match" for feeding the radiator from coaxial. The variable condenser assists in the final loading adjustments to give a low S.W.R. on the coaxial.

between gain and compactness. A reflector spacing of around .20 plus a director spacing of around .25 to .30 wavelengths will give slightly more gain.

A three-element wide-spaced beam will have a feed impedance of around 20 ohms, and folding the radiator element will provide a very good match into

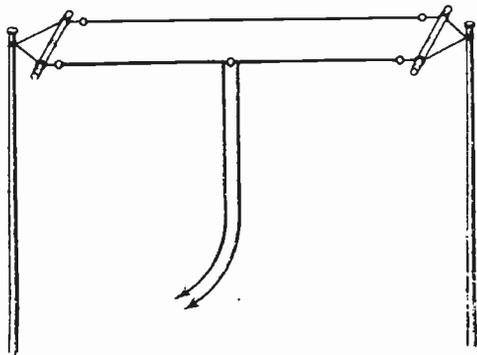


Fig. 9.—A "Flop-over" wire element beam supported on bamboo spreaders.

75-ohm twin cable. Despite the craze for coaxial cable, twin feeder is preferable for beam feeding, as the feed is symmetrical, and avoids the necessity for baluns, bazookas or Gamma Match feeds that are desirable with coaxial cable to avoid parasitic current effects to the coax outer sheath. The Gamma match is sketched in Fig. 8, as some may wish to try it. However, a variable condenser for cancelling residual inductive reactance at the "match" point is advisable to obtain the best transfer of power with a "flat" coaxial line.

A further idea for those in restricted locations, or those who cannot erect rotary beams, is the use of fixed or semi-fixed wire element beams. Thus a two-element "flop-over" beam strategically erected between spreaders, as shown in Fig. 9, would enable the beam to be turned over to cover two directions. Thus, in one direction W and VE might be covered in a N.W. direction, and ZB, ZS, CN8 and MP4 in a S.E. direction by flopping the beam over so that the director and radiator were changed over for the second direction to the rear. An even simpler and less energetic solution would be to clip on or off a short extra length of wire so that the director became a reflector. Providing the wire and clip were kept conveniently to hand, this would enable an all "electronic" switch of direction to be effected by the simple alteration of the effective length of the parasitic element by adding the experimentally determined length. It is a simple extension to this to devise a three-element fixed beam, the directivity of which could be reversed by removing the additional wire length from the reflector which would thus become a director, and attaching it to the erstwhile director to convert it to a reflector, thus again "electronically" reversing the direction of "fire" of the fixed beam array. Indeed, with some ingenuity, the resources of even a small garden, particularly on ten, could be exploited in turn with temporary "fixed reversible" wire beams to sample the DX possibilities of several different directions. Moreover, for some special feat, such as receiving or contacting a "rare DXpedition," a multiple-element fixed beam of high gain could be erected for the occasion, a

possibility several amateurs are interested in at the present time, including the writer! Yes, we mention reception, for the really keen SWL types who are the future "hams" of to-morrow will obtain pleasure from experiments with beams . . . even if only simple haywire "wire" affairs . . . in their searching of the

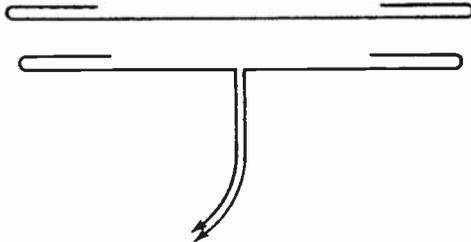


Fig. 10.—"Back-folding" of beam elements permits of compact arrays without use of loading coils.

short-wave bands. A "beam" array of some kind in fact need not be an expensive and elaborate rotary affair mounted on a 60ft. tower, and experiments with beams, even with three- and four-element beams, need not cost more than the cost of the wire and insulators involved. In fact, the writer some 10 years ago had a very nice three-element *Indoor* 10-metre beam made from wire elements. Try it sometime and remember that like other forms of "compacted" aerials, the ends of the elements, wire or tube, may be bent hanging down, or even doubled back (Fig. 10) to conserve space, even to halving the lateral spread of the beam elements. Let your motto be not to sigh for the unobtainable, but to *obtain* it in some form or other. You may *not* work or hear *all* the DX, but you will have fun and improved results over plain dipoles or lengths of wire. Assuming you have a restricted space you will not have a long wire, and even if you have, you might fill in the "nulls" earlier referred to, by a simple "wire element" two- or three-element beam.

PRACTICAL TELEVISION JULY ISSUE NOW ON SALE PRICE 1s. 3d.

The current issue of our companion paper, **PRACTICAL TELEVISION**, now on sale, contains a constructional article on a form of aerial which is very popular in America but which is not seen much in this country. Known as the *Rhombic* this type of aerial is very good for fringe areas, but occupies a fair amount of space. Those who are interested in aerial experiments will find this article full of valuable information.

Another article containing information which hitherto has been lacking is "TV without mains," a service engineer's account of methods of operating a TV receiver in districts which have no mains facilities.

A new frame pulse separator is also described, together with two separate articles on fault finding. One deals with A.G.C. circuits only, and the other with Fault Finding without Instruments.

A further explanation is given of Colour TV, together with details of a new test instrument which has been developed to test the "phase of colour" signals, whilst other articles deal with a Surplus Valve (the EF54), Smaller Picture Tubes, the Scottish TV Centre, and the usual features.

HOME RADIO OF MITCHAM

187 LONDON ROAD, MITCHAM, SURREY

MIT. 3282

Official Stockists for **EDDYSTONE** components and receivers and **PANDA** transmitters.

SUMMER DAYS AHEAD—have a gay holiday with the **HIWAYMAN** All-dry battery portable. 4 valves and high efficiency Ferrite rod aerial. Medium and Long Waves. Full constructional details and price list. **PRICE 1/6**. Total



building cost approx. **£7.10.0**.

All parts in stock for the **Repaco "Three Dee"** Dual Range Loudspeaker Transistor set. Constructional data and price list **Price 9d**.


IMMEDIATE DELIVERY. Limited number of the fabulous **QUAD F.M. Tuner £30.9.0**. Details on request.

MAGNETIC RECORDING TAPE

A by-return service of all types and sizes. E.M.I., BASF, Scotch Boy, Simon, Ferrovoice, MSS, AGFA, Ferrograph, Puretone, C.O.D or C.W.O. S.A.E. for full list.

The COMPANION

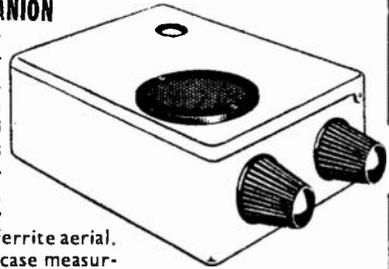A new Transistor Pocket Portable using 3 Transistors and employing reaction, permeability tuning, and Ferrite aerial. Neat Plastic case measuring only 4 1/2 in. x 3 in. x 2 in. Full Circuit Diagram, Wiring Details, Constructional Data and Price List, 9d. post paid.



JASON FM. Without doubt the most successful Home Constructor design ever produced. Complete kit of parts with valves, **£7.7.6**. Full constructional details with price list, price 2/-.

JASON ARGONAUT AM/FM tuner or receiver. All parts in stock. Full constructional data, price 2/-.

MORSE KEYS. New No. 2 Mk. III black bakelite keys with heavy duty adjustable brass contacts. Special purchase enables us to offer these at **ONLY 1/6 EACH**. Plus 6d. postage.

RST MAIL ORDER DEPARTMENT

211, Streatham Road, Mitcham, Surrey.
ALL VALUES LISTED ARE NEW STOCK. © CASH WITH ORDER AND POST FREE. MITCHAM 3047

B65 12/4	EP9 21/-	MKT165	17H81 10/6	GF1 15/-
D41 8/-	EP22 16/-	14L 14/-	CU183 15/6	GF12 7/-
DA132 0/6	EP37A 10/3	8M74 12/6	UP41 11/-	GF13 21/-
DA191 0/-	EP40 15/-	M114 10/-	UP69 12/6	8304 8/-
DA196 0/6	EP41 8/-	N17 15/9	UL41 10/-	8377 9/-
DF33 9/6	EP42 12/6	N78 11/8	UL84 11/-	8K7 8/-
DP97 9/-	EP80 9/6	N142 10/-	U198 21/-	8K8GT 12/-
DM20 0/6	EP85 9/6	N153 11/4	U194 7/6	8L1 12/6
DM91 8/9	EP86 12/6	N154 11/4	U195 7/6	8L60 12/-
DM96 9/-	EP89 11/8	N727 8/-	V22B 13/6	8L19 15/-
DM719 9/6	EP91 7/6	0274 5/8	W17 7/-	8L199 10/6
DM32 0/6	EP92 8/6	DM284 9/-	W77 12/-	8N70 7/-
DM91 8/-	EP95 14/-	DM280 8/6	W81M 12/-	8N7GT 7/6
DM92 10/6	EL38 24/6	DM282 11/4	W142 11/-	8N7GT 8/-
DM96 10/-	EL41 10/-	PC182 12/-	W19 9/6	8O4GT 11/6
DL23 9/6	EL42 9/-	PC183 15/6	W257 8/6	8X4 8/-
DL22 9/-	EL81 12/6	PL26 15/-	N18 8/3	8X5GT 9/6
DL22 8/-	EL84 9/-	PL28 24/6	X79 10/-	787 15/-
DL24 8/-	EL90 8/-	PL81 12/6	Z21 10/6	787 14/-
DL96 8/9	EM29 10/-	PL92 10/-	Z77 7/-	7Y4 9/6
KA50 1/9	EM31 10/6	PL93 11/4	Z152 8/6	8013 7/6
KAB280 8/6	EM83 15/-	PM24M 11/4	Z749 8/6	10K1 15/10
KAC91 10/9	EV31 11/6	PY30 8/3	Z0103 0/-	10K2 12/6
KAF42 11/-	EV34 10/-	EV91 9/6	H25 5/3	10K1 21/-
KH41 10/6	EV84 12/-	EV82 8/-	1P3 7/-	10K1D11 1/6
KB91 8/9	EV86 12/6	EV83 9/-	1P3 8/9	10P13 17/6
KHC41 9/3	EV91 9/-	PZ29 17/6	1T2 10/6	12A18 11/4
KB960 8/6	EZ35 9/6	R10 22/-	1T4 8/8	12A76 8/8
KB989 9/6	EZ40 8/-	R19 18/-	5Y44 10/6	12A77 9/-
KB121 21/-	EZ41 10/6	SP44 11/8	5Y97 8/6	12A77 9/9
KB131 21/-	EZ46 8/-	SP44 11/8	5Z44 10/6	12A77 12/6
KA21 8/6	EZ81 8/-	TP22 10/3	6AN7 14/-	12B46 8/8
KA33 10/6	EZ90 7/6	TP23 18/-	6AL5 5/9	12B66 9/6
KXC10 13/-	EV2 14/6	U16 11/6	6AM9 7/6	12B117 11/-
KB981 9/-	FC13 13/6	U75 7/6	6AN5 5/-	12B7 8/8
KC982 9/6	EV21 13/-	U142 7/6	6B35 8/-	12B7GT 9/-
KC983 10/-	GV32 11/6	U145 7/6	6AT6 9/3	12K8GT 10/8
KC984 10/9	H30 4/9	U147 9/6	6B8 4/-	12K8GT 12/-
KC985 9/9	H43 10/-	U155 8/6	6B84 8/6	12Q7 10/6
KC986 12/6	HBC30 8/6	U201 8/-	6BE6 8/3	12Q7GT 10/6
KC982 14/6	HJ22 11/6	U201 21/-	6B6 7/6	1407 8/-
KB921 21/-	HY9 7/-	CABC90	6B17 14/-	1501 14/-
KC985 12/6	KC982 10/-	6B16 8/4	6B16 8/4	20P2 21/-
KC982 9/-	KT3C 12/6	TA92 10/-	4B7 8/6	20F1 15/-
KC981 9/-	KT66 12/-	U111 8/-	6B5 8/6	20F5 12/6
KC180 9/6	LZ319 8/9	1BF90 11/6	8C186 27/-	2574 9/6
EC182 12/6	ML4 8/9	UC42 10/6	8D2 5/9	50L6 11/-

Quotation given for any types not listed. Obsolete and old types a speciality, send for lists.

CHASSIS

Let us supply the chassis for your set. We are specialists in this field and actual makers of aluminium chassis. Supplied either plain or with the large and awkward holes already drilled.

UNDRILLED ALUMINIUM CHASSIS

4 sides 1 1/2 in. deep	2 sides 2 in. deep
Welded Corners	7 in. x 4 in., 3/- ea.
7 in. x 4 in., 4/3 ea.	9 in. x 6 in., 4/- ea.
9 in. x 6 in., 5/6 ea.	11 in. x 7 in., 4/9 ea.
11 in. x 7 in., 6/6 ea.	13 in. x 9 in., 6/- ea.
13 in. x 9 in., 7/9 ea.	14 in. x 11 in., 7/6 ea.
14 in. x 11 in., 9/- ea.	16 in. x 14 in., 9/6 ea.

Send sketch of your requirements for prices by return to:—

Oliver & Randall Ltd.
53 Perry Hill, London, S.E.6

Radio and Automation

RADIO APPARATUS IS FINDING INCREASING USE IN MODERN COMMERCIAL PRACTICE. SOME DETAILS ARE GIVEN HERE

By F. E. Sonn

(Continued from page 344, July issue)

As stated in the previous article, automation, as we know it in the present day, would not be possible unless the electronic valve had been discovered. I will now go further and state that automation could not progress except for the invention of the electronic computer.

The Computer

This is an electronic machine, constructed to be

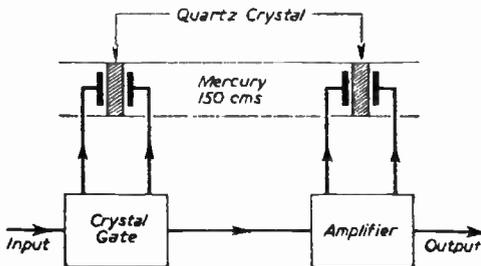


Fig. 1.—A simple form of delay circuit.

able to perform everything that can be done by a human operator equipped with a desk calculating machine, a set of volumes of tables, pencil and paper for recording intermediate results, and noting the required sequence of operations. Then he has to use his own brain for controlling these sequences until he gets a final result.

An electronic computer, if it is to be completely automatic, must be able to achieve this. Therefore, we may say that it must be able to perform the following operations:—

- (1) Arithmetical operations
- (2) Storage or memory.
- (3) Transfer data from one section to another.
- (4) Reception of data (incoming).
- (5) Supply of results.
- (6) Control.

Arithmetical Operations

Computers may be constructed to be binary or decimal, or both, by means of a binary/decimal matrix or vice versa. By binary is meant that numbers are represented in the scale of 2, and decimal in the scale of 10. For instance, in the binary scale the number 1011 would be $1 \times 2^3 + 0 \times 2^2 + 1 \times 2 + 1$ and the number 7601 in the decimal scale would be $7 \times 10^3 + 6 \times 10^2 + 0 \times 10 + 1$. Generally the

binary system is used, as components and circuits are fewer than in the decimal scale. In the case of a computer acting as a control for a machine tool it is necessary to use the decimal scale as the measurements of the various jobs to be done are practically always to a decimal place.

Memory or Storage

It often becomes necessary when a complex operation is being carried out by the computer, that results of one stage of the operation be stored for a short time, until another stage has been worked out. Then the two results are integrated and the machine carries on with the operation. This can be achieved in several ways.

Firstly, a delay line may be used. A simple form is shown in Fig. 1. Here the electric pulse is converted into an acoustic pulse in the mercury and reconverted at the other end into an electric pulse. If the electric pulse has a spacing of 1 micro second, 150 cms. of mercury would hold 1,000 pulses, which is enough, in a binary system, to represent 30 numbers of 10 decimal digits each, and the information thus becomes available one each milli second. As a pulse group may be required to circulate many thousands or more, before being used, the pulse shape may deteriorate to such an extent as to be unrecognisable: therefore the amplified pulse itself is not transmitted, but is used to open the crystal gate so as to allow a new pulse from the pulse generator to reach the end of the delay line.



The "baby brain"—the first desk-sized computer seen on this side of the Atlantic. It is designed to solve problems which are too complex for efficient solution on desk calculators, but too small for economical solution on "giant brains." This is a Burroughs machine.

Magnetic Storage

This is the method generally used. A magnetic tape or magnetic drum is used. These pass under a head which produces a magnetic field and magnetises the material with the data to be stored. There may be several writing heads and reading heads differently spaced so as to read or write at different positions on the tape or drum.

Some computers have two systems of storage. One, a high-speed storage of small capacity, mostly for arithmetical work, and a slow storage of much greater capacity with facilities for transfer between the two forms of storage.

The Pulse Generator

This is the heart of a computer, and here we go back to the thermionic valve as first used for radio.

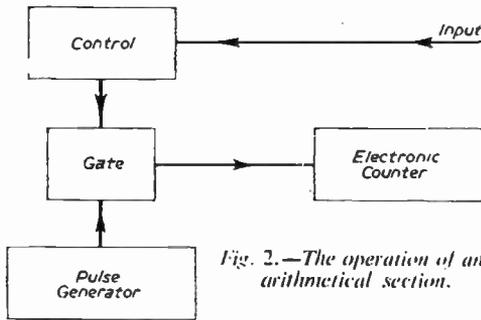


Fig. 2.—The operation of an arithmetical section.

The average pulse generator is generally a multi-vibrator circuit, although in small machines a squegging type oscillator is often used. An amplifier is also required to ensure a pulse of sufficient amplitude is transmitted. Pulses are produced at a rate of about 100,000 per second. (Different makes and types, of course, vary.) These pulses are routed by gates. If a

standard pattern of pulses is repeated every 20 pulse periods, that is, 0.2 milliseconds.

Operation (Arithmetical)

See Fig. 2. Here we see that the control opens or closes a gate according to the data supplied to it, and the pulses from the pulse generator then go to the electronic counter according to plan from control.

Control (Machine Tools)

Here we have automation doing a real job of work. Generally speaking the system used is as follows. A small computer is fed with the necessary data, as to measurements, in three dimensions. This is then transferred to a magnetic tape which is fed to the control box fitted to the machine tool. This control box is connected to an electronic servo-mechanism, which has absolute control over the work the tool has to do. It will keep it accurate to the data supplied by means of its error indicator (see Fig. 3). Under this method of control great accuracy and a definite

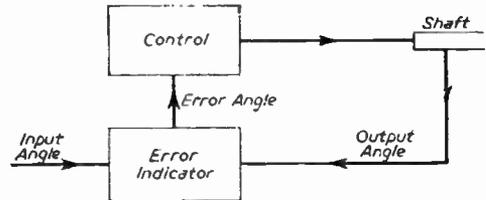


Fig. 3.—The servo-mechanical control.

saving in time and labour are achieved. Of course, in preparing the data for the machine a period of time is taken, but as this tape can be used time and time again, this period is reduced considerably.


Other Uses of Automation

Many other industries are now using automatic devices which are electronic in character. The railways, for instance, are using valves in track-signalling apparatus, and a new method of traffic control is being tested in which a train, with suitable white markings on it, is scanned as it passes by a control box, the movement of the train acting as the horizontal scan.

This is amplified and can be read on a C.R.T.

Office Equipment

There are now many firms making this type of equipment. One that has just come into use is the electronic calculator. This is similar to a computer, but it only deals with the four basic arithmetical operations in controlled sequences as desired. The results are produced in punched card form. There is also the large computer, which can nearly be considered as the automatic office. It consists of an integrated system of units. Information can be stored on magnetic files and daily information added. Statistics and reports can be prepared in accordance with a pre-set programme.

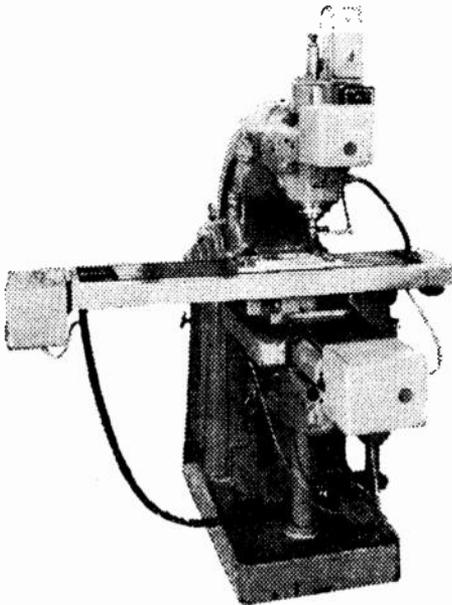

A standard vertical milling machine equipped with a complete three-dimensional control system, using magnetic tape.




THE LINEAR 'DIATONIC'

A 10-WATT HIGH FIDELITY ULTRA LINEAR AMPLIFIER WITH INTEGRAL PRE-AMP

A special feature is the compactness of the unit. Full advantage has been taken of latest component miniaturisation developments to produce a 10-watt Hi-Fi push-pull amplifier incorporating tone control pre-amplifier stages within the measurements of 10 x 6 x 6 in.

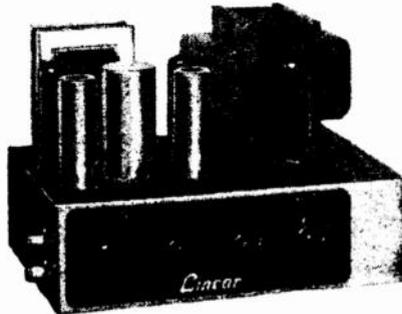In addition two high impedance input sockets are provided for microphone and gram, etc. Each input has its associated vol. control, five B.V.A. (Mullard) valves are employed. ECC83, ECC83, EL84, EL84, EZ81, H.T. and L.T. power supply point is included for a radio tuner.



FREQUENCY RESPONSE
± 2 d.b., 30-20,000 c.p.s.

MAXIMUM OUTPUT

In excess of 14 watts.
RATED OUTPUT 10 WATTS.

SENSITIVITY

Volume (1) 22 millivolts for rated output.
Volume (2) 220 millivolts for rated output.

TREBLE LIFT CONTROL
Continuously variable + 6 d.b. to - 13 d.b. at 12,000 c.p.s.

BASS CONTROL

Continuously variable + 13 d.b. to - 18 d.b. at 50 c.p.s.

HUM LEVEL

Referred to maximum output and including integral pre-amp - 60 d.b.

HARMONIC DISTORTION

0.19% measured at 6 watts.

NEGATIVE FEEDBACK

Total 32 d.b. including 24 d.b. in main loop.

L45 MINIATURE 4.5-WATT QUALITY AMPLIFIER

Size only 6 x 5 x 5 1/2 in. high. 12 d.b. Negative Feedback, Sensitivity 30 m.v. for full output. 3 Mullard valves. ECC83 Twin Triode, EL84 Power Output, EZ90 Rectifier. Separate Bass and Treble Controls. Mains switch incorporated in control. For 200-250 v. 50 c.p.s. A.C. Mains. An ideal unit for use with Gram. or 'Mike.' Output matching for 2-3 ohm speakers.
Retail Price **£5-19-6**

Also available: LG3 3-watt Gram Amplifier, 69/9. LT.45 Complete Tape Amplifier, 12 gns.

Weight 12 1/2 lbs. Power consumption 90 watts. For 200-230-250v. 50 c.p.s. A.C. mains. Outputs for 3- and 15-ohm speakers. Chassis finish stoved Blue-Grey hammer.

HIGHEST QUALITY! Retail price

MAXIMUM RELIABILITY!

AT A PRICE YOU CAN

12 GNS.

AFFORD. Available through your local dealer, or leading mail order firms. Send S.A.E. for descriptive literature.

TRADE AND EXPORT ENQUIRIES to

LINEAR PRODUCTS LTD. 5-9 MAUDE STREET, LEEDS, 2. Tel. 23116

Presenting the new HOMELAB range of SIGNAL GENERATORS

TYPE 2

100 kc/s. to 100 Mc/s CW or 400~ modulation. Audio signal for amplifier tests PRICE : **£4.10.0d., p. & p. 5/-**

TYPE 12

100 kc/s. to 130 Mc/s. Sine and square wave modulation at 1,000~. Sine or square wave signal for amplifier tests PRICE **£8.10.0d., p. & p. 5/-**

TYPE 20

An AM/FM signal generator covering all modern radio and TV requirements up to 240 Mc/s PRICE **£15.15.0d., p. & p. 5/-**

Send stamp for full details of above, and also our Mullard FM Tuner complete with power supply PRICE : **£12.0.0d.**

HOMELAB INSTRUMENTS LIMITED

615-617, HIGH ROAD, LEYTON, LONDON, E.10

Telephone : LEYtonstone 6851

TRANSISTORS

JUNCTION TYPE P-N-P

(British Manufacture)

RED-SPOT 800 kc/s Audio Frequency.....	10-
BLUE-SPOT 1.6 Mc/s Mixer and Frequency Changer...	15-
WHITE-SPOT 2.5 Mc/s R.F. and I.F. Amp.....	20-

All Transistors are Tested and Guaranteed.
N.B. The Red-Spot is similar to Mullard OC 71.

Superseding The Popular "Pre-Selected Transistor-Seven" The New "TRANSISTOR-8"

Push-Pull Portable Superhet.
Can be built for **£11/10/-**

This Portable 8 Transistor Superhet is tunable for both Medium and Long Waves and is comparable in performance to any equivalent Commercial Transistor Set. Simplified construction enables this set to be built easily and quickly into an attractive lightweight cabinet supplied.

TEN STAR FEATURES

- ★ 8 Specially Selected Transistors
 - ★ 250 Milliwatts Output Push-Pull
 - ★ Medium and Long Waves
 - ★ Internal Ferrite Rod Aerial
 - ★ 7 x 4 Elliptical High Resistance Speaker
 - ★ Drilled Plastic Chassis 8 1/2 x 2 1/2 in.
 - ★ Point to Point wiring and practical layout
 - ★ Economical. Powered by 7 1/2 v. battery
 - ★ Highly sensitive
 - ★ Attractive lightweight contemporary case
- N.B. Pair of OC 72's Supplied at additional cost of 40/-.

We can supply all these items including Cabinet for **£11 10/-**. All parts sold separately.

Send for circuit diagrams, assembly data, illustrations and instructions, and full shipping list. 1s.

Call and hear demonstration model.

"EAVESDROPPER"

THREE TRANSISTOR POCKET RADIO

(No Aerial or Earth required)

Pre-selected to receive the Light and Home Stations. Total cost, as specified including Transistors, Transformers, Coils, Condensers and Battery, etc., with circuit and plastic case.

All items sold separately. **77/6** POST FREE.
With single phone, 82 6. With Acos Mike, 90 -. With Min. Hearing Aid, 92 6.

THE TELETRON "COMPANION"

THREE-TRANSISTOR POCKET RECEIVER
MEDIUM AND LONG WAVES. NO AERIAL OR EARTH
Tuned R.F. Circuit. Aerial. Transformers. 3 Transistors. Drilled Plastic Chassis and Cabinet size 4 1/2 x 4 x 1 1/2 in., and all Components. Balanced Armature Output. Total cost

89/6

ALL PARTS SOLD SEPARATELY

TRANSISTOR SIGNAL TRACER

Complete Kit with 2 Transistors, Components, Phones with Circuit and plastic case. 42 6.

TRANSISTOR SQUARE WAVE GENERATOR

Complete Kit with 2 Transistors, Components, Circuit and plastic case. 25 -.

DIODES

B.T.H. GERMANIUM 1 6
M.I.L.A.R.D. 0.7A..... 2 6
IN21..... 3 6
IN22, IN23, IN21A..... 5 -

R.F. 21, 10 -.	R.F. 25, 12 6.
R.F. 26, 25 -.	Brand new with valves, cnrr. 2 6.

"HOMELIGHT" 2 TRANSISTOR PERSONAL PORTABLE

No Aerial or Earth Required
Pre-selected 2 Station Receiver

We can supply all components including 2 Transistors, Diode, Resistors, Condensers and Miniature Hearing Aid and Plastic Case size 4 1/2 x 2 1/2 x 1; and 1 1/2 v. Battery. **POK 55-**. All items sold separately.

"HOMELIGHT" ONE TRANSISTOR RECEIVER

Build this pre-selected set which is powered by No. 8 battery. Total cost, including Transistor, Coils, Diode, Plastic Case and H R single phone. 32 6.

SEND STAMPS FOR NEW 1957 28-PAGE CATALOGUE OPEN MONDAY to SAT. 9-6. THURS. 1 o'clock.

HENRY'S RADIO LTD.

5 HARROW ROAD, EDGWARE ROAD, LONDON, W.2
TEL.: PADDINGTON 1008-9, 0401

REPANCO HIGH GAIN TRANSISTOR COMPONENTS

FERRITE SLAB AERIAL TYPE FS2.—Super-sensitive aerial designed for transistor superhet portable receivers, for Long and Medium wave reception. Each winding with correctly matched coupling coil for transistor input. Slab size: 5 1/2 in. x 7 in. x 5/32 in. Complete with paxolin fixing brackets. 13/6.

COMBINED OSCILLATOR AND 1st I.F. TRANSFORMER TYPE OT1.—A fully-screened component 13/16 in. sq. x 1 1/2 in. I.F. frequency 315 kc/s. 11/6.

2nd I.F. TRANSFORMER (315 kc/s), Type TT2. 5/-.

3rd I.F. TRANSFORMER (315 kc/s), Type TT3. 5/-.

These components are wound with Litz wire and enclosed in iron dust pots with slug tuning, thus ensuring extremely high gain. Each coil is accurately matched to the preceding and following circuits.

PUSH-PULL INTERSTAGE TRANSFORMER TYPE TT4.—Ratio 1 : 1 centre tapped. Stack size 1 1/2 in. x 1-1/16 in. x 7/16 in. 8 6.

PUSH-PULL OUTPUT TRANSFORMER TYPE TT5.—Ratio 15 : 1 centre tapped. Stack size 1 1/2 in. x 1-1/16 in. x 7/16 in. Matched to 3-ohm speaker. 8/-.

Transistor portable circuit (theoretical and practical) enclosed with each REPANCO Transistor Component.

THE "TRANSEVEN," a new transistor portable for the Home Constructor using REPANCO Transistor Components. Easy wiring plans and instructions. 1/9 post free.

Mail Order and Trade :
RADIO EXPERIMENTAL PRODUCTS, LTD.,
33, Much Park Street, COVENTRY
Phone 62572

Wholesale Enquiries and Export:
REPANCO, LTD.,
O'Brien Buildings,
203-269, Foleshill Road, COVENTRY
Phone 40594

CONSTRUCTORS Still Say

!!IT'S THE BEST!!

THE
SUPEREX "55"
BATTERY PORTABLE



FOUR VALVE
SUPERHET

LONG AND
MEDIUM WAVE

CABINET SIZE:
10 1/2" x 8 1/2" x 4 1/2"

LARGE ELLIPTICAL
SPEAKER

BUILDING COST
Price **£7.15.0** plus 4/- carriage

Send 1/6 for SUPEREX "55"
CONSTRUCTION BOOKLET.

87G MINIATURE
VALVES

SIMPLE
CONSTRUCTION

SEND FOR FREE CATALOGUE.

SUPERIOR RADIO SUPPLIES
37 HILLSIDE, STONEBRIDGE, N.W.10.

Phone: ELGAR 3644.

Open to Discussion



The Editor does not necessarily agree with opinions expressed by his correspondents

A High-cycle Transformer

SIR.—Readers who are interested in using the high-cycle transformer described in the June issue by Mr. Stebbings may like to know that the transformer can easily be converted to an efficient heater transformer.


Only 23 turns are needed and there is ample room to accommodate them. These should be connected in series with the original 6.3 and 5 volt windings so that the voltages add up. This arrangement will give 6.3 volts when the H.T. winding is used as a primary as described in the article. If an output of 4 volts is also needed, then the new winding alone should be used. The gauge of the wire depends on the current required: 18 s.w.g. wire is sufficient for 3 amp consumption.—M. H. KUBBA (W.9).

Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying commercial or surplus equipment. We cannot supply alternative details for receivers described in these pages. WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE. If a postal reply is required a stamped and addressed envelope must be enclosed with the coupon from page iii of cover.

BBC Staff

SIR.—My attention has been called to the editorial in your June issue, to which members of this Association take very great exception. On the question of programme content, and the desirability or otherwise of broadcasting matter not specifically directed at the Lowest Common Multiple of popular intelligence, it is a job rather of the British Broadcasting Corporation than myself to reply to your strictures. One would have thought that the Corporation's many years' experience, and the high reputation which it has established among civilised people for the quality of its programmes would, however, be sufficient answer to criticisms of this kind.

Your criticisms of the quality of BBC staff, who are members of this Association, cannot so easily be disregarded. Let me assure you that the standard of appearance, whether sartorial or tonsorial, of the people who work in broadcasting is fully in keeping with their status as public servants. They include "people of ripe experience in the entertainment field and in the realms of literature," who in addition to these qualities combine a profound knowledge of broadcasting. Excluding staff employed on Britain's broadcasts abroad, a national service, available for practically three-quarters of the day, seven days a week, is accomplished on a statistical basis of one broadcasting employee to every 5,000 population.—T. L. LITTLEWOOD (General Secretary).

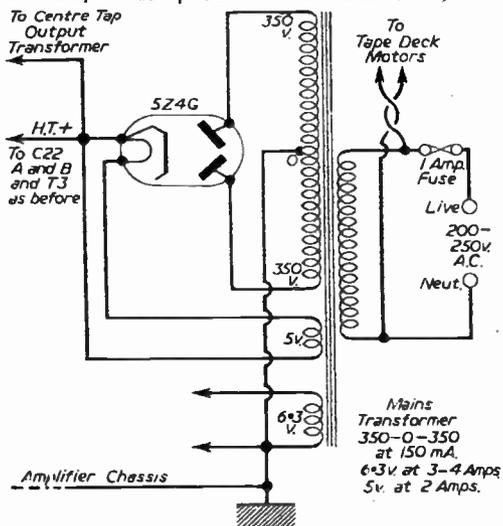

The power pack for the tape recorder.

A Power Pack for the Tape Recorder


SIR.—In reply to many letters asking for a design for a power pack for the tape recorder with isolating transformer, a circuit diagram is given above for a suitable unit.

The transformer should have a secondary winding of 350-0-350 volts at 150 mA, and a 6.3 volts 3-4 amps for heaters, and 5 volt 2 amp rectifier supply. The valve is a 5Z4G. No other extra components are required.—B. L. PHILLIPS (Preston).

R1155—Power Pack

SIR.—I should like to draw your attention to the power supply connections for the R1155 as given in the September, 1956, issue of your magazine. The heater should be 6.3 volts not 5.3 volts.

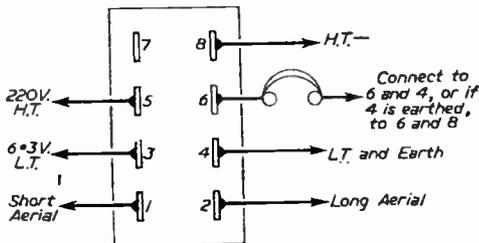If the H.T. + is connected to pin seven, then the D.F. stages are brought into operation. I suggest, however, that all connections are traced as various manufacturers have their own ideas about these connections.—N. A. CURREY (Bishop Auckland).



Connections to plug for R1155.

Programme Pointers



FOR those readers who are interested in classical music, "The Fifteenth Variation" was a tribute to Elgar on the occasion of the centenary of his birth. The analogy in the title lies in the finale of the immortal "Enigma Variations," the last of which is a self-portrait. Revised and introduced by Alec Robertson and produced by Charles Parker, it consisted of eulogies by a galaxy of musicians who knew him, and who filled an hour with their personal reminiscences of the master. It was done in the standard BBC formula of such programmes, and was one of the best of them that I can recall.

Should such a programme contain adverse as well as laudatory comment? Doubtless, this problem has been well thrashed out. Setting out as a "tribute," and not a "criticism," the answer would seem to be "no." The trouble is that it makes the programme very lopsided and mamby-pamby. Although Elgar, when he chose, could be an overwhelming genius, he had many detractors among practising musicians. Wouldn't their opinions, concluding with the defence, give such a programme much more bite and fillip, add zest to the desire to discuss it among listeners, and raise generally its level both as entertainment and instruction?

It is the same with their private lives. How cheering and comforting it would be to learn that these great men sometimes did as we ourselves do: arrive home a little bit "muddled," lose our temper over some trifle or other, or to be real human on occasion—as it is certain they were. But no, they must always be drawn as paragons of perfection, just as they must always be supremely great in everything they do in their particular line of work.

"The Critics"

I was surprised to hear "The Critics," one and all, fairly "lay in" to the new panel game, "My Word" which I had praised on this page. I thought they passed a harsh judgment. One of them said she could not hear a word chairman John Arlott said. This fairly staggered me.

Documentary

Another meritorious documentary was "The Fabulous Vidocq," with script by Eric Ewens, based on material supplied by P. J. Stead. Vidocq was the first chief of the modern Sûreté Nationale, having started his career in Napoleon's day as a spy and a detective. He was originally a convict. With Donald Wolfitt in the title rôle, an interesting and, at times, exciting narrative was assured.

"Any Answers," is advertised as "a radio correspondence column in which listeners add their comments to the views expressed in last Friday's 'Any Questions.'"

I wonder if it is really necessary? Granted that it is fairly amusing and entertaining, are not the questions sufficiently thrashed out by the four

Our Critic Maurice
Reeve. Reviews Some
Recent Programmes

experts who, in their chairman's frequently reiterated words, seldom agree, and whose wanderings from the original starting point "just aren't true?" What it really sets out to do is to animate the correspondence columns of a daily paper. The result, however, is to bring Mr. and Mrs. Muggins into our programmes, instead of leaving them quietly listening-in in their homes. The person who would read the paper at home aloud, would soon be "told off," by those he was hoping vainly to entertain.

Music

An anthology of words and music, inspired by that most romantic and appealing of birds, the lark, made it a pleasant half hour. Selected and presented by James Fisher and Geoffrey Grigson, it brought back nostalgic memories of summer evenings, the river and harvesting. It concluded, almost inevitably I suppose, with a bit of Vaughan Williams's "The Lark Ascending," for violin: a work I find boring and repetitious. So is the lark repetitive, you may well say. But, whereas the one has an ethereal and quite incomparable charm, the other is its naked bones.

The Bristol Old Vic Company gave Miles Malleson's translation of Molière's masterpiece, "Le Misanthrope," under the title "The Slave of Truth." Mr. Malleson compered. His translations are always diamond-bright and the original French atmosphere considerably anglicised. The Bristol players did it full justice, except that Rachel Robert's Célemène seemed a bit underplayed.

A new series has started of the panel game, "Call the Tune," under its old chairman, Joseph Cooper. The panel was made up of Joyce Grenfell, Stephan Potter and Wynford Vaughan-Thomas. Although specially designed on rather unsophisticated lines, no one among the three seemed to have an undue share of musical perception; not even Mendelssohn's "Fingal's Cave" overture was recognised. Mr. Cooper, as I remarked last season, makes a genial and hospitable chairman, though on this occasion his presiding remarks lacked spontaneity, and sounded as though read from a script. Dennis Brain was the guest.

The Proms will be with us again before this article is in print. One talks glibly, as a rule, of how life has changed since two world wars took a hand at changing it. But few things I can recall, mark those new shapes so completely as the massive, hippopotomium-dinosaur symphony concerts, that rightly draw the musically moronic to Kensington every late summer.

OSCILLATOR COILS, as specified for the "P.W." Hi-Fi recorder, the Hatfield Oscillator coil is the only one sold with a guarantee of "less than 0.03 of 1 per cent. distortion" using only one valve, and backed by an N.P.L. report, 10/6 post free. Patent app. for.

REJECTOR COILS, 40 db. rejection (in practice far better than "double T" circuit), 5/6 post free, or 15/6 with Osc. coil.

HATFIELD RADIO have been making tape recorders since 1952 and at present are offering two models:—

The **VIKING** at 46 gns. using the MOTEK deck and Hatfield coils as above.

The **VIKING Mark 3**, using the COLLARO Mark 3 deck and a unique method of coupling the amplifier to the deck which eliminates the bugbear of instability. Patent app. for, 52 gns.

COLLARO Mark 3 deck with Hatfield Pre-Amplifier built on and tested ready to use with your own amplifier, 28 gns. or with Motek deck, 26 gns.

Complete amplifiers to suit Lane or Brenell decks, £12.15.0.

Any of above decks supplied for cash or terms. 50 per cent. down and balance in 12 monthly payments, or one-sixth down and 8 m.p.s.

Call or write:—

HATFIELD RADIO

78 Stroud Green Rd., London, N.4. ARC 1593.



**TAPE RECORDING
HIGH FIDELITY
M8 RIBBON MICROPHONE**

A high quality microphone with good output. Size only 1 3/8" x 3 3/8", with inbuilt transformer.

Mounted by three-pin plug and socket on flexible fitting with internal leads. The ribbon, although extremely thin, is secure against reasonable acoustic shock.

Usual output impedance 30 ohms. Other impedances available. Three Alcomax III magnets. Treble stainless steel protecting gauzes.

£8 . 15 . 0 List Price

FILM INDUSTRIES LTD

90 BELSIZE LANE LONDON

Telegrams
Traasound, Haver

N.W.3

Telephone
HAMpstead 9632-3

SOUND ENGINEERS FOR 27 YEARS

LYONS RADIO LTD.

Dept. M.P., 3 GOLDHAWK ROAD,
SHEPHERDS BUSH, LONDON, W.12

Telephone: SHEPherds Bush 1729

HAND GENERATORS Mk. 2. Manually operated, originally designed to provide the operating voltages for the American Transceivers types 18 and 48 but, of course, suitable for a variety of other purposes. Nominal rating is H.T. 182 v. D.C. at 60 mA. and 3.1 v. D.C. at 0.3 A. (With suitable series loading would provide for 2 v. or 1.4 v. heaters. A built-in filter unit provides adequate smoothing and suppression. Ideal for portable rig. Weight of generator approx. 14 lbs. and size 6 1/2 x 6 1/2 x 5 1/2 in. In good condition and unused, with carrying haversack. PRICE 35/-, carriage 8/6 We can also supply the combined mounting legs and seat for these generators as a separate item. PRICE 7/6, carriage 2/6.

0/500 MICROAMMETERS. Moving coil type, 2 1/2 in. dia., bakelite cased. PRICE 17/6, post 1/3.

AMERICAN L.F.F. UNITS. Contains wealth of useful components, including relays, 10 valves (6-6SH7's, 2-719's, 2-610's) and a rotary converter rated at 480 v. D.C. output for 18 v. D.C. input. One end of converter is fitted with blower fan which operates from either 6 v. or 12 v. battery. The other end is fitted with a gear box, easily removed if desired, and the two driving shafts which protrude rotate at approx. 4 and 16 r.p.m. for 12 v. input and about half this for 6 v. input. In good condition. PRICE ONLY 30/-, carriage 5/-.

HOME WORKSHOP KITS. Quality tools by Bridges, includes equipment for power drilling, grinding, turning, polishing, etc. Complete kits from £9.8.6 to £23.12.0. Can be yours for as little as 30/- deposit. Send S.A.E. for full particulars.

**FIRST-CLASS
RADIO COURSES...**

GET A CERTIFICATE!

QUALIFY AT HOME—IN SPARE TIME

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure your professional qualification. Prepare for YOUR share in the post-war boom in Radio. Let us show you how!

FREE GUIDE

The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success-compelling qualifications as **A.M.Brit.I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs, Exams., Gen. Cert. of Educ., London B.Sc. (Eng.), A.M.I.P.E., A.M.I.Mech.E., Draughtsmanship (all branches)**, etc., together with particulars of our remarkable Guarantee of **SUCCESS OR NO FEE**

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

**FOUNDED 1885—OVER
150,000 SUCCESSES**

**NATIONAL INSTITUTE OF
ENGINEERING
(Dept. 441), 148, HOLBORN,
LONDON, E.C.1.**

ALFRED PADGETT

40, MEADOW LANE, LEEDS 11

Tel.: CLECKHEATON 99

SPECIAL OFFER.—Red Spot Transistors, 7/6 each. Crystal Diodes, 10d. each. Post 2/d. each.

MIXED RESISTORS. 5, 2, 1 and 1/2 watt types. Box of one dozen, 1/3. Post 9d.

HEADPHONES.—New, boxed, low resistance, 6/6 pair. Post 2/3.

DOUBLE SPRING H.M.V. CLOCK-WORK GRAM MOTOR.—Brand new! Less crank handle and turntable, 9/6. Post 3/-.

PRESS BUTTON UNIT with six G.P.O. type coloured wedge type lamp, 1/8. Post 2/-.

NEW WELL-MADE 100-1 SLOW-MOTION BRASS DRIVE. Fits 1 1/2 in. spindle. 6/6. Post 2/-.

MOTORS.—5 small Blower type, 8/-; Model makers' motors, 3/6, 5/-, 8/- and 12/-; All 12-24 volts. Post 2/- each.

MIXED B.A. NUTS AND BOLTS.—Half a pound box, 1/6. Post 1/6.

PAINT.—High gloss. Ideal for chassis Quick drying. Red, light blue, dark blue, black, green, yellow and all, 2/6 per pint tin. Post 2/-.

RADIO VALVES.—With 90 days' guarantee. Post 9d. per valve; doz. lots less 5% post free. 12S17M, 4/-; 12SG7M, 4/-; 12SH7M, 3/-; 12H6M, 1/3; 129K7M, 4/-; 12CBM, 4/-; 12A6M, 4/6; 9003, 2/6; 9004, 6d. 8D2, 1/-; 807 (BRIT), 4/-; VR150/30, 4/-; PEN46, 2/6; 964, 1/3; EF50, 3/-; VR136, 4/-; VR137, 1/3; EF36, 4/-; 6KT, 2/-; 6SH7, 6/-; 6CG, 3/6; 618M, 1/3; 6HG, 9d.; VR54, 9d.; 6D6, 3/-; 6C6, 3/-; 6J5M, 4/6; 6C4, 4/-; 6A5, 4/-; 6BB, 2/-; VR92, 9d.; VR85, 1/6; VR66, 1/-; KT2, 3/6; QP220, 3/6; 210LF, 1/6; DLS10, 2/6; SU4G, 8/6; CV63, 1/-; KT33, 6/-; 2X2, 1/6; VU111, 1/6; VU133, 1/6; AC6PEN, 2/6; 7199, 1/6; VS110, 1/6.

MULLARD TAPE AMPLIFIERS

We stock all the components for the Amplifiers as described in the Mullard Tape Recording Booklet.

RESISTOR KITS, LAB. All fixed and variable resistors as specified. Model A, 33.3. Model B, 31.9.

CONDENSER KITS, Model A, 33.3. Model B, 35.5. These kits are made up for the Brenell and Collaro Decks. If Lane or Truvox Decks are being used this must be stated when ordering.

OUTPUT TRANSFORMERS.—Giltson OP767, 25/6. Elstone OT/3, 21/-. Partridge SVO 1.60/-.

ELECTROM PLUGS AND SOCKETS. PO4 Chassis Plug, 3/6. 504T Flex Socket, 5/3.

IGRANIC JACK SOCKETS. P71, 3/4. P72, 3/10. Bulgin Jack Plugs to fit, 3/-.
BELLING LEE PLUGS AND SOCKETS. Speaker Sockets. L316 Red and Black, 1 each. L378 Plugs to fit, 10d. each. Co-Ax Socket L7345, 1/-. L6045, 1/3. L374 Plugs to fit, 1/3 each.

McMURDO VALVE HOLDERS. 2M9 U, 10d. XM9/UCI, 1/7. XM9/UGI, 2/3.

SWITCHES. Set of three for Model A, 32/6. One Switch for Model B, 16/6.

BULGIN TAG BOARDS. C120, 1/3. C125, 2/3.

EQUALISER PLUG AND SOCKET. Plug & 2/3 each Socket, 6d.

CERAMIC STAND OFF PILLAR. 1/- each.

OSCILLATOR COILS. Brenell, 8/-. Truvox TR98, 6/9.

CHASSIS. Denco. Fully drilled, Model A, 31/6. Model B, 31/6.

VALVES. EF86—Mullard, 24/4; Alternative, 15/-. ECC83—Mullard, 19/6; Alternative, 10/-. EMB1—Mullard, 18/1. EL84—Mullard, 16/-. Alternative, 12/-. OAT1 Diode, 4/-.

KNOBS.—Bulgin K370, 1/6 each. EMB1 ESCUTCHEON, 2/6.

SUNDRIES KIT. Contains all nuts, bolts, tags, wire, flex, solder, etc., 8/-.

FULLY DETAILED LIST is available free upon request. This gives prices for complete kits and details of Power Unit Components.

WATTS RADIO

8, Apple Market, Kingston-on-Thames, Surrey

Telephone: KINGSTON 4099

TECHNICAL TRADING CO.

Portsmouth's Radio and Tool Shop

250 v. 250 mA RECTIFIERS, Selenium 1 wave, square fins, 11/- 100 200 mfd. 275 vw. Cans, 5/6. 1 MEG. POT., D.P. sw. 31in. sp. smol. 3/6. RESISTANCES assorted, 1-3 w., 1.7 10-10 MΩ 2/- doz. 10 - 100. MIDGEET CERAMICS Tubular 10, 20, 50, 300, 3,000 pF., 5/- doz. 32. 32 250 v. 2.6, 15 10 350 v. 3/6. GOODMANS P.M. SPEAKER PINS, 5in., 17/-. 6in., 18/-. 7 x 4, 17/6. 6in. (F.M. Quality), 22/6. 10 x 6, 26/-. 10in., 25/-. 10 INCH CABINET SPEAKERS, Anti-Boom lined, size 14 x 18 x 7, 29/-. ARDENTE 12 VOLT AMPLIFIERS, 10 w., ECC83, ECC81, p.p. EL35/4. Very compact, ideal Street Broadcasts, complete, untested, 24 10/-. MAINS DITTO, by Parmeno, untested 24 15/-. VITAVOX RE-ENTRANT SPEAKERS, excellent for outside work, 29/-.

SPECIAL BARGAIN! 12 v. 4 amp. rect., 8/6 ea., 25 doz. Full wave iron selenium heavy compact type.

13 CHANNEL CONVERTERS, famous make, complete PCC81, PCC10, beaut. bakelite cabinet, adjustable all 13 freqs., tunable all channels, no extra coils required, 23 15/-. GERMANIUM CRYSTAL DIODES, famous make, tested, general purpose, polarity marked, 10d., p. & p. 3d., 8/6 doz.

GUARANTEED BOXED RADIO VALVES, 24 HOUR SERVICE.

5Y4GT	6/6	6K7GT	5/8	12AU7	11/8	EZ80	8/6
5Y4G	6/6	6K7M	6/6	12AX7	8/6	ECC85	8/6
6AR	9/8	6H6M	2/6	12K7GT	7/6	ECC82	4/6
6AC7	6/6	6L6G	8/6	12Q7CT	7/6	ECH12	6/6
6AC5	4/8	6L6M	9/6	12SK7	5/6	ECL81	8/8
6AC3	9/6	6N7	7/8	12V6GT	8/8	E836	4/6
6AK5	4/6	6SA7	7/6	12Y4GT	7/6	E837	7/6
6AM7	7/6	6SG7M	5/6	150	7/6	E838A	11/8
6BT	8/8	6SJ7	7/8	81	7/6	E839	5/6
6DA	6/8	6SK7GT	5/6	807 (1)	3/8	E850	2/8
6DU5	6/9	6SL7GT	6/8	807 (AM)	5/6	E850 (11)	3/8
6CT	4/8	6SN7GT	5/8	866A	11/8	E849	8/6
6CG5GT	6/6	6V6G	8/6	1C4	12/8	E845	5/6
6CR	5/6	6V6GT	7/6	1C1C	12/8	E846	9/8
6D6	5/6	6V6M	6/6	1E9	1/8	E891	7/6
6F6G	6/8	6X4	6/6	1E4	1/8	E892	5/6
6F7	8/8	6X5GT	5/6	1E5	7/6	E895	2/8
6F8M	5/6	6X7	7/6	1E6	4/8	E832	5/6
6G5GT	4/6	6Y6	7/6	1C3C51	9/6	E144	10/8
6H6	3/6	7D9	6/6	1C3C41	8/6	E143	4/6
6R	5/6	12A6M	6/6	1C3C42	7/6	EY51	10/8
6T7	5/6	12AT7	7/6	1C3C83	8/6	E240	7/6

Postage 1/- in £1 in £1 Speakers Trans. Min. 6d. No C.O.D. 10,000 OTHER BARGAINS TO CALLERS AT...

350/352 FRATTON ROAD, PORTSMOUTH

BENSON'S BETTER ARGAINS


Build a Car Radio, Cheaply and Simply

The basis is the Command Receiver 50mp 0.52-1.6 mc. (medium wave), consisting of 12NKT, 12N7, 12N8, 2N 12NKT, Demand amp 12NKT, Output 12A6, Size 1 1/2 x 2 1/2. Nobs. black crackle finish. Price 15/- (incl. post).
Receiver, with valve 87 B; automatic speaker trans., 4/6; gain potentiometer, with switch, 6/6; speaker jack 1/6; jack-plate 1/6; speaker 5in., 18/6; dynamo (500mg) 25 v. 10/6; 100-ohm 12 v. input, 10/6. Modification data and circuit diagram 1/6. Total 27/6 (incl. post).
VIBRATORS, Mains 250V, 12.5 v. 100 mA, 7/6. TROAT MICS, 2/6. 2 S. SUPPRESSORS, radio interference, 25A.M., 5/6 (incl. post).
BRAND NEW RP.28, 27, 27 1/2 (incl. post).
RP.28, 10 1/2 DYNAMOTORS (incl. post) 12 v. 250 v. 65 mA, and 65 v. 25 mA. **10 1/2 EDDY STONE,** 12 v. 100 mA, 25 v. 100 mA, 15/- (incl. post).
25 v. 100 mA, 4/6. 70 v. 250 mA, 6/6. 250 mA, 22 1/2. METAL RECTIFIERS: 250 v. 250 mA, 7/6; 500 v. 250 mA, 10/6; 1000 v. 250 mA, 12/6. **6 v. 1 A., 25/- 12 v. 2 A., Bridge, 30/- R1155 600 ohm, 4/6. R1155 5 M. TUNING DRIVES "N" type, brand new, 10/6. CHOKES, 1 1/2, 10/6; 10 1/2, 120 mA, screened, 7/6. 10 1/2, 100 mA, 8/6. 1 1/2, 250 mA, 4/6. 70 v. 250 mA, 6/6. 12 1/2. SWITCHES, water 1 pole 1 way, 1/6; 1 pole 2 way, 1/6; 1 pole 3 way, 1/6; 2 pole 2 way, 1/6; 2 pole 3 way, 1/6; 2 pole 4 way, 1/6; 2 pole 543 way, 1/6; 2 pole 544 way, 1/**

News from the Trade

COSMOCORD POLYSTYRENE MICROPHONE

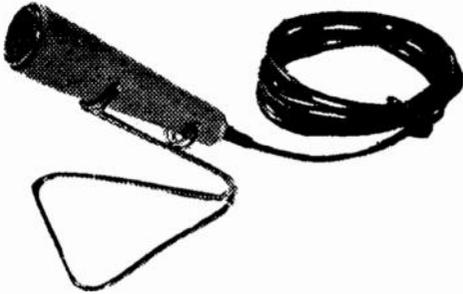A NEW type of microphone is now being manufactured by Cosmocord, Ltd., using Styron 475 polystyrene. These microphones are of unique style and are extremely compact and attractive in appearance. They have excellent tonal qualities, and are



The new Cosmocord polystyrene microphone.

particularly suitable for use in conjunction with most tape recorders.—Cosmocord, Ltd., Waltham Cross, Herts.

ELECTRONIC MIXER UNIT

THE latest thing for the tape-recording enthusiast is a four-channel electronic mixer unit incorporating a pre-amplifier. This device will extend the field of tape recording enormously, enabling the user independently to fade in or fade out up to three microphone inputs plus one additional channel. Under certain circumstances it is possible to control a total number of six microphones simultaneously.

This compact, self-contained unit can be put to a number of uses in conjunction with a tape recorder. For example, if you are producing a recorded play at home you can use two microphones for the actors' voices, one microphone for manual sound effects, and the additional channel for incidental music or recorded sound effects. Each control works independently and the user is thus able to fade the sound from any particular source at will. The Grundig GMU3 Electronic Mixer Unit also has the facility for monitoring by a pair of headphones and the built-in magic eye ensures that the recording is being made at the correct level.

These mixer units will operate with any past or present Grundig tape recorders and are suitable for use with most types of microphone. The complete unit costs 16 gns. and is obtainable from Grundig agents all over the country.—Grundig (Great Britain) Ltd., 39-41, New Oxford Street, London, W.C.1.

NEW R.C.A. VALVE

THE R.C.A. Electron Tube Division has recently announced a medium- μ twin triode designated as the 6350. It is a 9-pin miniature type designed for use in a wide variety of applications in electronic computers particularly of the high-speed digital type, and in other "on-off" control equipment.

In such service, the 6350 maintains its emission

capabilities even after long periods of operation under cut-off conditions, and, therefore, provides good consistency of plate current during its "on" cycles. Furthermore, balance of cut-off bias between the two units is closely controlled during manufacture. Production controls correlated with typical electronic computer operating conditions as well as rigorous tests for inter-electrode leakage, high-resistance and intermittent shorts, and cathode inter-face, insure long dependable performance from the 6350.

The 6350 has separate terminals for each cathode to facilitate flexibility of circuit arrangement, and a mid-tapped heater to permit operation from either a 6.3-volt or a 12.6-volt supply.

Technical bulletin for the 6350 is available upon request.—R.C.A., Gt. Britain, Ltd., Lincoln Way, Windmill Road, Sunbury-on-Thames, Middlesex.

NEW LOW-PRICED EKCO CAR RADIO

A NEW Ekco quality car radio receiver which, together with a styled installation kit, sells at only 20 gns. (tax paid), and can easily be fitted in practically any make or year of car, is announced by E. K. Cole, Ltd.

Exceptionally neat and compact, this new receiver, Model CR280, combines the receiver and power units in one assembly occupying no more space than the majority of receiver units alone.


The four-valve superhet receiver unit covers long and medium wavebands with excellent sensitivity and selectivity, while the high standard of reproduction is assisted by negative feed-back. Other features of the receiver unit include a self-rectifying synchronous vibrator, a glare-free floodlit scale, a single slide-action wavechange and easy-to-handle controls.

The standard receiver, finished in dove-grey with a chromium escutcheon, black scale with white figures and black control knobs, is attractively designed to blend with any fascia panel and interior.

Dimensions: 2in. high by 7in. wide by 7½in. deep.

A choice of four speaker assemblies is available, together with a wide range of aerials.

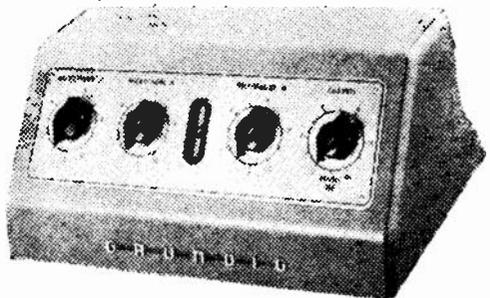Price: 20 gns. tax paid (including receiver and power unit together with installation kit styled for practically any type of car).—E. K. Cole, Ltd., Southend-on-Sea, Essex.




The Grundig electronic mixer unit.

MATCH TEST INDICATOR

A USEFUL type of symmetrical directional coupler employs coupled transmission lines. One physical form of the device employs lead-covered cable. The manufacture of such a coupler entails accurate milling of the flats on the cable, a great care in soldering lest the polythene insulant should melt.

By employing strip-line instead of cable, a printed circuit equivalent is possible and an actual coupler, comprising a through line and two auxiliary lines, has been manufactured. The instrument serves as a match indicator, reflectometer, and true output power monitor over the frequency range 150-500 Mc/s. Standing-wave ratios down to 1.2 to 1 can be measured at 500 Mc/s with an accuracy of 20 per cent. It is simple, compact and robust.

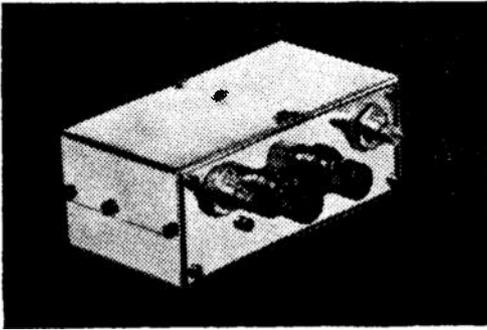The printed circuit is made from a laminated paper board copper clad on both sides. One side of the board consists of three short sections of transmission line, each having a characteristic impedance



The match test indicator.

of 75 ohms. On the other side of the board the copper is retained. The transmission lines are therefore single strip above an earth-plane type, with laminated-paper dielectric.

The middle strip-line carries the radio-frequency energy and the two auxiliary strip-lines, one on each side of the main line, are coupled to it by virtue of their mutual capacitances and inductances. The direction of the current so induced in each auxiliary line due to the couplings is such that the two components will tend to cancel in one direction and add in the opposite direction. The resulting voltages obtained across the auxiliary line terminations are, therefore, dependent on the direction of power flow in the main line, i.e., the unit will exhibit directional properties. — Millett, Levens Group, Stirling Corner, Barnet By-Pass, Borehamwood, Herts.

HIGH FIDELITY FABRICS

SIMPSON & GODLEE, of Manchester, long established as producers in the textile industry, recently appointed Austen W. Farrell to institute their New Fibres Development Division.

Under the family brand name of "Simplan," Farrell is designing "engineered" fabrics for the radio, television, furniture, motorcar and other industries, specifically to meet each industry's needs.

First into production after six months of preparatory work is a brand new radio and television high-fidelity fret fabric, featuring a combination of excellent acoustical and technical qualities with

outstanding artistic design created in Simpson and Godlee's own studios. The designs now available present new possibilities to the cabinet designer, with refreshingly novel styling and textures, but Simpson & Godlee welcome invitations to design fabrics exclusively to meet individual requirements.

"MY LADY CATHERINE" BATTERY PORTABLE

VIDOR announce an additional bright new colour combination for their very popular portable receiver "My Lady Catherine," which has enjoyed sensational sales.

The new colour is in Cambridge blue and light grey with attractive primrose yellow scales and trim. The price remains at 11½ guineas, deliveries to commence immediately.—Vidor Ltd., Eriih, Kent.

PHILIPS A.M. F.M. CAR RADIO

WHAT is believed to be the first A.M. F.M. car radio to be launched in this country by a leading manufacturer was introduced by Philips Electrical Ltd. on 1st June, 1957.

Known as Model X61V this new high quality receiver sells at a retail price of 49 gns. (list £37 16s. 8d. (including £2 9s. 6d. for Suppression Equipment) plus P.T. £13 12s. 4d.). It employs seven valves and rectifier and covers long, medium and F.M. wavebands. There are push buttons for station and waveband selection. An outlet socket for operating the "Philishave" dry shaver is incorporated.

A separate power supply unit is provided and the set can be adapted for 6-volt or 12-volt operation.

Specification

Valves—	A.M.	F.M.
R.F. Amplifier ...	EF89	ECC85
Frequency Changer ...	ECH81	
1st I.F. Amplifier ...	EF85	EF89
2nd I.F. Amplifier ...	—	EF85
3rd I.F. Amplifier ...	—	EF42
Detector and A.F. Amplifier ...	EABC80	EABC80
A.F. Output ...	EL84	EL84
Rectifier ...	Metal	Metal

Wavebands—Long 1,053-2,000 m. Medium 186-583m. F.M. 87.5-100 Mc/s.

Controls—On/off and volume. Tuning. Tone (continuously variable). Five push buttons for station and waveband selection.

Power Supply—6 v. or 12 v.

Consumption—55 watts.

Cabinet—Metal, dark grey lacquer. Chrome plated escutcheon.

Dimensions—Control Unit, 6½ in. x 2½ in. x 5½ in.

Power supply unit, 8½ in. x 3¾ in. x 5½ in.

Features—High Sensitivity.

Small dimensions for easy mounting.

Push button operation for station and waveband selection.

Speaker—7 in. complete with baffle and "Philite" housing.

Price—49 gns. (Tax paid).

—Philips Electrical Ltd., Century House, Shaftesbury Avenue, W.C.2.

WIRELESS COILS, CHOKES AND TRANSFORMERS

8th Edition.

Price 6/-, by post 6/9.

I DID IT MYSELF!

YOU will say—and it is so easy . . .

GET THE RODING HOME CONSTRUCTOR'S HANDBOOK



"If you want the best, and to save time and money!"

PRECISION WIREWOUND RESISTORS

Eureka Wound on strip: 1 to 1,000 ohms: 0.5%, 3/-; 0.2%, 4/3; 1 K to 5 K, 0.5%, 9/6; 0.2%, 4/9; 5 K to 20 K, 0.5%, 4/3; 0.2%, 6/-. Rated at 0.75 watts. For accuracy at high audio frequencies use 0.2% series which have non-inductive windings. Your value wound to order.

SWITCHED DECADE RESISTOR UNITS

Yaxley type switch with wirewound resistors mounted, the 100 ohm 1% unit having ten equal steps of 10 ohms 1%. Price 17/6. Ditto but 1,000 ohms max., 17/6. Ditto but 10,000 ohms max., 20/-.

RESISTANCE BOX STANDARDS

12 Wirewound Resistors, 1, 2, 2.5, 10, 20, 20, 50, 100, 200, 200, 500 ohms to give any value between 1 and 1,110 ohms in 1 ohm steps. 0.5%, 33/-; 0.2%, ± 0.01 ohm, 48/-; Ditto but 10 to 11,100 in 10 ohm steps. 0.5%, 34/-; 0.2%, 49/6. Ditto but 1 to 11,110 in 1 ohm steps (15 resistors) 0.5%, 45/-; 0.2%, ± 0.01 ohm, 65/-. Also available in 1, 2, 3, 4 and 1, 2, 4, 7 series at no extra cost. Ratio Arm Resistors 10, 10, 500 ohms (ratios 100, 10, 1, 0.1 and 0.01 to 1) per pair. 0.5%, 16/6; 0.2%, 24/-.

1% HIGH STABILITY RESISTORS

Any value from 100 ohms to 1 Megohm including non-standard values 1 w. 2/3. We don't care what the required value is so long as it is between the above limits; if we cannot supply one to the exact value we will supply two for use in combination, charging only for one.

We regret that we cannot take orders this month for anything other than those goods described above.

Postage extra. S.A.E. with enquiries please.

PLANET INSTRUMENT CO.

25, DOMINION AVE., LEEDS, 7.

Our series of unique LIFE-SIZE "EASY-AS-A.B.C." CONSTRUCTION SHEETS illustrate how really simple radio assembly can be for the Home Constructor! If you have average ability then you could tackle any, or all, of the LARGE RANGE OF GUARANTEED FITTINGS knowing that with the help of our pre-aligned units and prefabricated chassis, failure is virtually impossible!! No previous knowledge is necessary.

The latest issue of this Handbook is beautifully printed on glossy art paper with a full colour cover! Packed with technical data, set building and servicing hints, facts and formulae, resistance colour code, soldering hints, etc., together with descriptions, full parts lists and circuits of many modern receivers, tape recorder, feeder units, communications set, etc., etc. (for list see previous ads.). Send 2/6 (plus 4d. post).

Our renowned "Easy-as-A.B.C." FULL SIZE Construction sheets for any of these units are available FREE with orders enabling even the beginner to get professional results first time! Coil packs and I.F.T.s pre-aligned. We supply ALL parts for ALL circuits.

Thousands of satisfied customers all over the world!

NEVER BEFORE HAS THERE BEEN A BOOK SO VALUABLE TO NOVICE AND EXPERT ALIKE! GET YOUR COPY—DON'T DELAY—SEND 2/10 TODAY!

RODING LABORATORIES

(Dept. TC68) Bournemouth Airport, Christchurch, Hants

For the home constructor . . .

VALVES

6SH7	3/3	12SC7	6/-	6G6	3/-
1A5	5/6	OZ4	5/-	6SN7	6/6
6V6M	8/6	6AC7	6/-	954	1/9
VR56	5/-	VR54	2/-	12Y4	1/-
VT501	2/6	6H6	2/-	VR91	5/-
12H6	2/-	12SH7	2/9	(EF50)	
6L7	5/6	VT52	2/6	VR136	5/-
12A6	5/-	6J6	3/6		

On orders up to 4 please allow 3d. postage on each.
On quantities of 5 or over 1/- up to 12.

BATTERY INTERCOM-AMPLIFIER. Type AL368 A.M. REF. 10U/13025. Using 1-VR35 and 1-VR21. Power Regd. 120 v. H.T. 2 v. L.T. Size 7in. x 4 1/2in. x 4in. Fully valved in good condition, £1 each, post paid.

TOGGLE SWITCHES. Double Pole On-Off 230 v. 6 Amp. Panel fitting. Size 2in. x 1 1/2in. x 1 1/2in. depth behind panel. REF. 64-14. Price 2/6 each, post paid. New in packets.

MAINS CHANGING TRANSFORMER. (Admiralty Pattern) 230/100-110-130 v. Separate primary and secondary with earthed screen winding between. Totally enclosed in 7in. x 6in. x 8in. black steel case with detachable lid exposing terminal block and tapping link. Secondary very conservatively rated at 0.44 Amp. (core size 3 sq. in.). Tested to 2,000 volts. Weight 19 lb. Price £1 each, post paid.

CO-AXIAL CHANGE-OVER RELAY, Type 77A. Size 2in. x 4in. x 5 1/2in. Price 15/- post paid.

BLOCK CONDENSERS. 10 mfd. 500 v. wkg. Size 3in. x 4 1/2in. x 2 1/2in. Base mounting, 7/- post paid.

BC610 TUNING UNITS. 2-2.5 Mc/s., 10/- p. p.


CARBON HAND MICROPHONE. Type 4 with lead. New and boxed. 7/6 each, plus 1/- post.

PROOPS BROS. LTD. LANgham 0141.

Dept. 'P', 52, Tottenham Court Road, London, W.1.

Shop Hours: 9-6 p.m., Thursday, 9-1 p.m. Open all day Saturdays

BUILD THIS AUTHENTIC

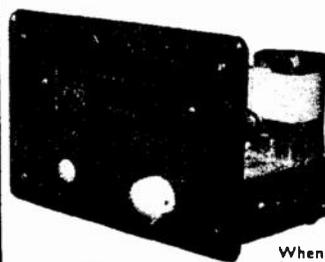

JASON F.M. KIT

4 VALVES

STABLE

EASY CON- STRUCTION

When built this famous Jason F.M. Tuner provides good sensitivity with freedom from drift and highest quality reproduction. Output 0.5 v. Chassis supplied ready punched, together with genuine exclusive Jason coil and dial assemblies, etc. Useful range—60 miles; fringe area version available. Book of the Jason F.M. Tuner (Data Publications), 2/- or 2/3 post free. Detailed price list on application.

Complete kit of quality components (less valves), £6.0.0.
Fringe-area version (less valves) £6.0.0.
Power-pack kit, £21.9.

● JASON "ARGONAUT" A.M.-F.M. KITS

For building as a tuning unit or complete self-powered receiver. Book by Data Publications, 2/- (2/3 post free).

FROM LEADING STOCKISTS, or in case of difficulty:

JASON MOTOR & ELECTRONIC CO.

328 Cricklewood Lane, London, N.W.2.

Phone: SPE 7050

RECEIVERS & COMPONENTS

AMERICAN TRIPLET METERS, 0.5, 0.00v, A.C., D.C., 0-250,000 ohms, D.C., M.A., etc. £5/10 each, U.S.A. Precision series 834-S Multi Range Volt-Ohm Milliammeter £8/10 each. All boxed with leads, etc. 0-250v, D.C. Moving Coil Pocket Voltmeter, 17.6, 6.500lbs. sq. in. Pressure Gauge, 5in. dial, 17.6, S.A.E. for list, etc. H. JAMES, 175, Brentnham Road, Wallingstone, E.17.

5,000 lin. Resistors, 1w., 10,000 ohms, £10. 3,000 1in Resistors, 88w., £7. 12,000 ass. Mica condensers, £15. 1,200 Electrolytic condensers, 25µf, 50v, £15. 3,000 Headbands, £10. 500 condensers, 600v, D.C., v.k.g., £10. 400 condensers, 0.1 mfd., 500V, D.C., v.k.g., £8. GRANGER, 251, Solihull Rd., Handsworth, Birmingham, 21.

T.V. TUBES, 30, with cathode heater shorts: 15 with burnt cathode. Ideal for testing, good picture, all types and sizes. Please enquire, DUKE & CO., 623, Romford Rd., Manor Park, E.12. (GRA 6677)

POWER IN PACKETS . . . Volts by the Ton . . . and still more Hls. tens of thousands of volts in a large variety of shapes and sizes. Our promise honoured owing to a further lucky buy, we reduce prices again on a large number of types. 2d. stamp for our illustrated catalogue or for reduced price quotation. Send now while stocks last. Fx. 90 x 14v. cylinder type H.F. 10 for 7/6, etc. etc. DIGGINS, 129/131, Radnor St., Halmie, Manchester, 15.

TRANSISTORS. Audio, 10; R.F. (2.5 Mcs.), 21; Interstat P.P. Trans., 8; Output Trans., 7.5. Full range Components. List. OSMABET, LTD., 14, Hillside Rd., Tottenham, London, N.15.

AMERICAN MAGAZINES. Year's subscription "Audio" 35. "High Fidelity" 50/. Spec. copies 4/ & 5/ ea. Cat. free. WILLEN LTD. (Dept. 40), 9, Drapers Grns., London, E.C.2

JASON FM TUNERS, new designed, complete, £9. Carriage, ins. pdg. Write with order. R. HOWES, 61, Cavendish Road, Brondesbury, London, N.W.6.

GENEROUS DISCOUNT Valves and CRT's. 12 months' guarantee. S.A.E. for lists. THE GREEN DOOR, 59, George St., Hyde, Cheshire.

ATTENTION! Our famous "Adaptatone" pre-Amp, is now fitted to the Collaro MK, IV Tape Deck and now incorporates push-pull oscillator, complete with power pack, 40 gns. Easy terms and full specification on request. SOUND TAPES VISION, The Tape Recorder and Hi-Fi Specialists, 71, Princes Street, London, W.2. (PAD 2367)

CHECK YOUR TAPE RECORDER. We supply standard Tapes recorded on the first 12001, with Hi-Fi frequency test recording at no extra cost. Scotch Boy, 60011, 21 x 1,200ft. 35/. BISPHAM RADIO LTD., 151, Red Bank Rd., Blackpool.

RATES: 5/6 per line or part thereof, average five words to line, minimum 2 lines, Box No. 1 - extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless," Tenner House, Southampton St., Strand, London, W.C.2.

OSMOR NEWS, F.M. Switch-tuned Frequency Controlled Tuning Unit. Circuits and full information available shortly on request. OSMOR RADIO PRODUCTS LTD., 418, Brighton Road, S. Croydon.

THE HIWAYMAN. A new super Portable Radio for the home constructor: all-dry, 4-valve superhet with Ferrite rod aerial, easy wiring diagrams and instructions, 1/6 (post pd.). RADIO EXPERIMENTAL PRODUCTS, LTD., 33, Much Park St., Coventry.

MAKING YOUR OWN? Telescopes, Enlargers, Projectors, or in fact, anything using lenses. Then get our booklets "How to use Ex-Gov. Lenses & Prisms," price 2/6 ea. Comprehensive lists of optical, radio and scientific equipment free for sale. H. W. ENGLISH, Rayleigh Rd., Hutton, Brentwood, Essex.

TAN IN 24 HOURS. Super-tonic Sunray Lamps. Ultra-bright infra-red combined; automatic exposure; controlled emission; all mains. Listed 4/7 10/. Our price, 80/-. S.A.E. illustrated brochure. Dept. 100. SCIENTIFIC PRODUCTS, Cleveleys, Lincs.

SERVICE MANUALS SHEETS. T.V. Radio for hire, sale and wanted. S.A.E. enquiries. W. J. GILBERT (P.W.), 24, Friarville Gardens, London, W.12.

MIDDLESBROUGH. Largest stocks on N-East coast. Radio, TV components, FM Kits, Gram. Cabinets, Tape Decks, Leak Amplifiers, Valves, etc. Callers only. PALMERS, 106, Newport Road. (Phone: 2096)

SERVICE SHEETS, Radio, T.V., 5,000 models. Lists 1/-; s.a.e. enquiries. TELRAY, 11, Moorland Bldg., Preston.

F.M. AERIALS direct from manufacturers. Examples: Indoor Telescopic Double with mast and base, 15/; Indoor "H" with mast and base, 22/6; I.V. Indoor Combined, 1 and 2 bands, 5 elements, 20-mile range, 35/; I.V. Indoor Band, 3 only, 27/6; all post free. Low Loss Cable, very cheap if ordered with above. Aerial Parts, Lists and data, 1/-. Special terms to aerial erectors. Write for details. Skyline Works, Burnall Road, Coventry. (Tel: 60418.)

LOUDSPEAKERS repaired promptly. MOLF, LOUDSPEAKER SERVICE, Billington Rd., Oxford.

When replying to Advertisements please mention

"PRACTICAL WIRELESS"

SITUATIONS VACANT

LABORATORY TECHNICIAN (Physics). Queen Mary College (University of London), Mile End Road, E.1. Salary according to ability on scale £380 p.a. by £15/20 to possible £545, subject to efficiency review at £455, plus London Weighting £20 or £30 according to age; pension scheme; 4 weeks annual leave. Letters only to REGISTRAR (PT), stating age, full details experience and present work.

F.M. You can have a happy and rewarding job testing, lining-up and being in the forefront of technical developments in F.M. Apply MUSEUM 8105.

YOUNG MEN wanted to engage in the construction of specialised audio equipment; experience in electronic chassis building and wiring an asset. Apply STAGESOUND (LONDON) LTD., 3, Dancy Place, Wardour St., W.1. (Tel: GER 5911.)

MINISTRY OF TRANSPORT AND CIVIL AVIATION. Trainee Communications Officers. Applications invited from men and women age at least 18. Candidates must have an elementary knowledge of radio communication principles, be able to send and receive morse signals at 20 words a minute; type or teleprint at 30 groups a minute; transmit and receive telephone messages. Weekly rates of pay whilst under training from £6/1/9 at age 18 to £8/17/6 (men) and £8/13/6 (women) at age 25 or over, plus free meals and accommodation. On successful completion of training course, annual salary will be £347 at 18; £568 at age 25 or over, rising to £706 for men; £349 at age 18; £536 at age 25 or over, rising to £637, for women; slightly lower rates at certain stations. Women's pay being improved under equal pay scheme. Appointments will be temporary (non-pensionable). Application form and further particulars from MINISTRY OF TRANSPORT AND CIVIL AVIATION (ESB/COM), Berkeley Sq., London, W.1.

RADIO TECHNICIANS IN CIVIL AVIATION. A number of appointments are available for interesting work providing and maintaining aeronautical telecommunications and electronic navigational aids at aerodromes and radio stations in various parts of the United Kingdom. Applications are invited from men aged 19 or over who have a fundamental knowledge of radio or radar with some practical experience. Training courses are provided to give familiarity with the types of equipment used. Salary £561/10/- at age 25 rising (subject to a practical test) to £671. The rates are somewhat lower in the Provinces and for those below age 25. Prospects for permanent pensionable posts for those who qualify. Opportunities for promotion to Telecommunications Technical Officer are good for those who obtain the O.N.C. in Electrical Engineering or certain City and Guilds Certificates. The maximum salaries for Telecommunications Technical Officers are Grade III, £830; Grade II, £980; Grade I, £1,190. Apply to the MINISTRY OF TRANSPORT AND CIVIL AVIATION (ESB) RT, Berkeley Square House, London, W.1, or to any Employment Exchange (quoting Order No. Westminster 2109).

SITUATIONS VACANT

ROLLS-ROYCE

DERBY

have vacancies for

ELECTRONIC TECHNICIANS

who have completed military service, to operate and maintain recording equipment used for Aero Engine Development. Good knowledge of basic principles of electronics necessary. Applicants accepted for these posts will be required to work alternate morning and afternoon shifts. The posts carry a salary of £600 per year upwards according to age and experience, together with additional payment for overtime and shift work. This is an excellent opportunity for men wishing to undertake varied and interesting work in an expanding section of the civil aero engine industry. Interviews can be arranged at any time, including evenings or Saturday morning, expenses paid. Apply:

The Manager (T.2), Technical Administration, Rolls-Royce Limited, Derby.

WANTED

GLASGOW. Cameras bought for cash or taken part exchange for Tape Recorders, Players, or Amplifiers. VICTOR MORRIS, 406, Argyle St., Glasgow, C.2.

WANTED.—Valves EY31, 6CH6, 10F1, 1F181, KT61, 6P1, FW4/500, 20D2, 20F2, 10P14. Prompt cash. WM. CARVIS LTD., 103, North St., Leeds, 7.

ALL TYPES of Valves required for cash. State quantity and condition. **RADIO FACILITIES LTD.**, 38, Chalcot Road, N.W.1. (PRImrose 9090.)

ASTRAL RADIO PRODUCTS

'HOME RADIO,' 32-page illustrated booklet. Simple wiring instructions for Crystal Set, 1, 2, 3 Valves, 2/-, post 3d. TRF COILS. Specified for 'Bedside Push-button 4,' 'All Dry 3 Band, 3,' 'Push-button 4,' etc., 6/6 pr., post 6d. Push-button Unit with modification data 7/-.

DUAL WAVE HF Coil. Specified for 'Summer All Dry Portable,' 'Modern 1 Valver,' 'Modern 2 Valver,' '117 G Battery Miniature,' etc., 4/3, post 3d.

IFTs. Miniature, 1" x 1 1/2" x 2 1/2" in cans. Extra high 'Q.' Special offer, 8/-, post 6d.

K COILS. 'AC, B' pass 3', 3/3 each, post 6d.

FRAME AERIALS. M.W. 5/-, post 4d.

COIL PACKS. L.M.S. 38/-, post 1/-.

Crystal Set Coils. L. & M.W. 2/6, post 3d.

82 Centurion Road, Brighton

RADIO AND TELEVISION COMPONENTS

All parts in stock for:
Viewmaster, Soundmaster, Telemek, etc.
Easy Terms available.
21d. stamp (only) for Catalogue.
JAMES H. MARTIN & CO.
FINSTHWATE, NEWBY BRIDGE,
CLIVERSTON, LANCs.

WANTED.—T/R Stations, types RT18/ARC-1, AN-ARC-3, TR1934, TR1935, TR1936, T/R1987, W/S82. Telephone and Telegraphic Terminal Units (tracked or encased), types 1+4 Mk 11, 1+1, S+Dx, 3 ChDx. **R. GILFILLAN & CO. LTD.**, 7, High Street, Worthing, Sussex. (Tel.: Worthing 30181.)

EDUCATIONAL

CITY AND GUILDS (Electrical, etc.) on "no pass—no fee" terms. Over 95% successes. For full details of modern courses in all branches of Electrical Technology send for our 144-page handbook—free and post free. B.I.E.T. (Dept. 242A), 29, Wright's Lane, London, W.8.

LEARN IT as you do it—we provide practical equipment combined with instruction in Radio, Television, Electricity, Mechanics, Chemistry, Photography, etc. Write for full details to **E.M.I. INSTITUTES**, Dept. PW47, London, W.4.

A.M.I.Mech.E., A.M.Brit.I.R.E., City and Guilds, etc. on "no pass—no fee" terms; over 95% successes. For details of exams, and courses in all branches of engineering, building, etc., write for 144-page handbook, free. B.I.E.T. (Dept. 242B), 29, Wright's Lane, London, W.8.

FREE! Brochure giving details of Home Study Training in Radio, Television, and all branches of Electronics. Courses for the Hobby Enthusiast, or for those aiming at the **A.M.Brit.I.R.E., City and Guilds, R.T.E.B.,** and other Professional examinations. Train with the college operated by Britain's largest Electronics organisation. Moderate fees. Write to **E.M.I. INSTITUTES**, Dept. PW28, London, W.4.

WIRELESS. See the world as a Radio Officer in the Merchant Navy; short training period; low fees; scholarships, etc., available. Boarding and Day students. Stamp for prospectus. **WIRELESS COLLEGE**, Colwyn Bay.

INCORPORATED Practical Radio Engineers home study courses of Radio and TV Engineering are recognised by the trade as outstanding and authoritative. Moderate fees to a limited number of students only. Syllabus of Instructional Text is free.

The Practical Radio Engineer journal, sample copy 2/-. 6,000 Alignment Peaks for Supercuts, 5/8. Membership and Entry Conditions booklet, 1/-. All post free from the **SECRETARY, I.P.R.E.**, 20, Fairfield Road, London, N.8.

T.V. and RADIO.—**A.M.Brit.I.R.E., City and Guilds, R.T.E.B. Cert., etc.** on "no pass—no fee" terms. Over 95% successes. Details of exams, and home training courses in all branches of radio and T.V.; write for 144-page handbook free. B.I.E.T. (Dept. 242G), 29, Wright's Lane, London, W.8.

MERCHANT NAVY Wireless School. Overseas House, Brooks' Bar, M/cr 16.

WIRELESS.—Day and Evening Class instruction for P.M.G. Certificate of Proficiency and Amateur Wireless Licence. Morse instruction only if required, also postal courses. Apply **BST, LTD.**, 179, Clapham Rd., London, S.W.9.

Coventry Technical College

SESSION 1957-58

ELECTRONIC ENGINEERING

Applications invited for entry to next three-year full-time course commencing September, 1957, from those requiring comprehensive training to an advanced level in **ELECTRONIC ENGINEERING**, qualifying them for technical posts in radio, telecommunications, television and industrial electronics. Syllabus will cover requirements of City and Guilds, Brit.I.R.E. and I.E.E. examinations. Entry age 16 or over.

Application forms and further information from:


Principal, Coventry Technical College.

The "TYANA"
Standard Soldering Iron



- Adjustable Bit.
 - Weight approx. 4 oz.
 - Heating Time 3 min.
 - 40 Watt economy Consumption.
 - Standard Voltage Ranges. 16.9
- Replacement Elements and Bits always available.

'DIPLOMA' HEAPHONES

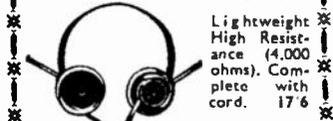

Ideal for CRYSTAL SETS and also for use with TAPE RECORDERS.

KENROY LIMITED

152/297 UPPER ST., ISLINGTON, LONDON, N.1.

Telephone: Canonbury 4905-4663

Transistor Techniques, by Gernsback Library, 12/-, postage 3d.

Transistors (Circuits and Servicing, by Bettridge, 2/6, postage 4d.

Basic Maths for Radio and Electronics, new edition, 17/6, postage 1/-.

Radio Control Mechanisms, by R. P. Stock, 4/6, postage 3d.

Radio Valve Data, by Wireless World, 5/-, postage 6d.


Frequency Modulated Radio, by Starley, 15/-, postage 9d.

Radio Servicing Pocket Book, by Molloy, 10/6, postage 6d.

UNIVERSAL BOOK CO.

12 Little Newport Street, London, W.C.2

(adjoining Lisle Street)

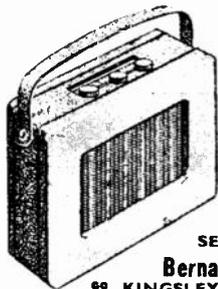BERNARDS OFFER:—4 VALVE SUPERHET BATTERY PORTABLE RECEIVER

CAN BE OBTAINED COMPLETE WITH BATTERIES

£8.19.6

IN KIT FORM LESS BATTERIES

£7.7.0 Including

Postage

BATTERIES CAN BE SUPPLIED SEPARATELY AT 11/6

- LONG AND MEDIUM WAVE
- LARGE ELLIPTICAL SPEAKER
- LATEST TYPE LOW-CONSUMPTION MINIATURE VALVES

SEND TO:—

Bernards Electrical Industries Ltd.

99, KINGSLEY RD., HOUNSLOW, MIDD.X.

RADIO HAM SHACK LIMITED

SPECIAL OFFER. COLLARO RC458 1 speed Autodancer. Latest model with turnover lead. Auto/Manual Switch. £9 10/- carriage paid.

TAYLOR INSTRUMENTS

67A Signal Generator, £22 10/-

71A Multimeter, £13 15/-

77A Multimeter, £17

88A Multimeter, £22 10/-

120A Pocket Multimeter, £9 15/-

171A Electronic Valve Voltmeter, £30.

Illustrated list of complete Taylor range on request.

Channel P37A Band 3 Pre-Amplifier, £6.

Collaro Studio Microphone, £2 5/-.

Also mikes by Geloso, Larchmont and Simon. Technical Books by Bernards and Norman Price. Send 6d. for our list of components, valves, band 3 aerials, etc., speakers and cabinets and Hi-Fi equipments.

155, SWAN ARCADE, BRADFORD 1, YORKS.

Solder with



"PERMATIP"

AND

"PERMABIT"

INSTRUMENTS

FOR

**GREATER
SOLDERING
EFFICIENCY**

The soldering bit which maintains its face indefinitely without attention. 25 models available for mains or low voltage supply. Bit sizes 3/32 to 3/8 inch. Full details in booklet S.P.10 from sole manufacturers:—

**LIGHT SOLDERING
DEVELOPMENTS LTD.,**

106, GEORGE STREET, CROYDON,
SURREY. Tel. CROydon 8588.

A really small RADIO RECEIVER

This radio receiver, although small enough to fit inside a matchbox, gives loud, clear reception of the BBC Home, Light and Third Programmes on the medium waveband, about 190-550 metres. No catwhiskers, valves or batteries are required, and the receiver works off a short indoor aerial in most districts. Many unsolicited testimonials.

PRICE **9/-** POSTAGE AND PACKING 6d. EXTRA

This offer applies only to Gt. Britain and Northern Ireland.

RADIO COMPONENT SERVICE,
No. 1, SUMMER'S ROAD,
BRISTOL, 2.

SALE

OF RADIO COMPONENTS, ETC.
END-OF-SEASON CLEARANCE
OF ODD LINES

FULL DETAILS WITH OUR
**HOME CONSTRUCTOR'S
HANDBOOK**

(Price 2/6, post paid)

which includes circuits of:

★1 PERHETS, 5- and 6-valve
Receivers.

★4-VALVE BATTERY SUPERHET.

★FEEDER UNITS, 2- and 4-valve
Superhet Feeder Units.

★AMPLIFIERS, 5-watt and 10-watt
quality Amplifiers.

★TWO-WAVEBAND Superhet
Coil Pack, Constructional details.

★CRYSTAL SET.

★SERVICING and Constructional
Hints, Formulae, Data, etc.

Send for your copy to-day!

SUPACOILS (Dept. PB.)

101, Markhouse Rd., London, E.17

Telephone: KEY 6386

Morse Code operating as a PROFESSION

25 years of teaching Morse Code is proof of the efficiency of the Candler System. Send 2d. stamp for Payment Plan, w.c. End Details of all Courses.

CANDLER SYSTEM CO., Dept. 500
F2b, Abingdon Road, London, W.9.
Candler System Co., Director, Colorado, U.S.A.

F M and Hi-Fi Components

DENCO F.M. TUNER circuits	1s. 6d.
RADIO CONST'R. F.M. "	2s. 0d.
MULLARD AMPLIFIERS "	3s. 6d.
G.E.C. 912 PLUS AMPLIFIER "	4s. 0d.
G.E.C. F.M. PLUS TUNER "	2s. 6d.

Separate price lists available on request to

J. T. FILMER 82 DARTFORD RD.,
DARTFORD, KENT.

Tel. Dartford 4057.

ANNALIN

Resistance Unit Type 231. Has 12 carbon resistors—80 ohm, 10³ ohm. Heavy steel case. For Trunk AF matching. 30 - Mainland only. Slow Motion Dials.—11¹/₂ diam. 50-1 New, 6-.

Throat Mikes.—Single unit, less band. New, 2-.

Potentiometers, 500 ohm, fine wire (low wattage) Knob, metal case, screened lead. New, 3-.

Smooth Chokes, 20 H, 60 ma, 300 ohm, 4 lb. 8-.

Above Post Free. Price lists of 300 snips. 25 ANFIELD PLACE, OTLEY, YORKS.

COVENTRY RADIO Component Specialists since 1925

We have now trebled the size of our premises in order to supply a larger range of Components, Amplifiers and Hi-Fi Equipment.

Send your enquires to:

189-191 Dunstable Road, Luton, Beds.

New Telephone No.: LUTON 7388-9

SERVICE SHEETS

1000's in stock

SALE or HIRE

Actual ones used by the trade.

Send S.A.E. with enquiry.

New Catalogue now in preparation. Reserve yours now, 1/6.

M. FOY

6, WYKEBECK GARDENS, LEEDS, 9

with the
"ASPDEN"
 Tape Deck and Amplifier Kits



YOU CAN BUILD YOUR OWN QUALITY TAPE RECORDER

TAPE DECKS, 2 speed, twin track, easy to assemble kits, fully complete with finest motor and Ferroxcube heads.

Model 521 for 5in. spools, kit, £7/10/-

Model 721 for 7in. spools, kit, £8/10/-

Either model assembled and tested 27/6 extra.

AMPLIFIER kit, 2½ watt, record/replay with two recording positions, neon indicator, etc., £5/18/- . Power pack kit for above £2/18/6 (both without valves). Carr. and packing extra.

Mr. C., of Dundee, writes:

"When I assembled your deck I was amazed at the very high quality of the appearance and of the action, which is smooth and silent. I can indeed say I got my money's worth."

THIS TAPE DECK AND AMPLIFIER IS BEING USED IN THE ANTARCTIC BY A MEMBER OF THE EXPEDITION.

Send a stamp for full particulars to:—

W. S. ASPDEN Stanley Works, back Clivedon Rd.,
 BLACKPOOL, LANCs.


BUILD THIS PORTABLE £7-7-0



Build the amazing "Hiwayman" 4 valves, all dry portable. Highly efficient and sensitive circuit covering all medium and long waves and using the latest type Ferrite Rod internal aerial. This is the ideal portable for summer use, and is powerful and yet economical. Easy-to-follow, step-by-step instructions enable it to be built by an absolute beginner. **TOTAL**

BUILDING COST (including all valves and beautiful rexine covered case) **ONLY £7/7/-** (Post, etc., 3/6). **PRICE PARTS LIST ETC., 1/6.**

BUILD THIS 'EAVESDROPPER' SPEAKER POCKET SET FOR ONLY 69/6!
BUILD THIS REMARKABLE LITTLE 3 TRANSISTORS SET FOR ONLY 69/6 (speaker insert extra). As shown in "RADIO CONSTRUCTOR." Size only 1in. x 3½in. x 6½in. including built-in speaker, and battery. Can be slipped easily into the pocket. Preset tuning to avoid cabinet projections (knobs, etc.). **USES FERRITE ROD AERIAL and needs no aerial or earth** (can be used also for private listening in, whilst travelling or at the Office, etc.). **TOTAL BUILDING COST (ONLY WHILST PRESENT SUPPLIES LAST !)** is 69/6, plus 2/6 Post, etc. (speaker insert extra). **PARTS SOLD SEPARATELY: PRICED PARTS LIST 1/6. SEND NOW BEFORE PRICE GOES UP!**
Cheques accepted. C.O.D. 1/6 extra.

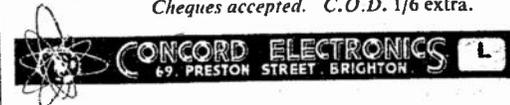

Train for a wonderful
 future in

ELECTRONICS...

...with E.M.I.

Every day the demand for the expert in electronics grows. Radio, television, radar and the whole field of industrial automation are rapidly expanding and the trained specialist assures for himself a well-paid career in this quickly developing profession. Here is your opportunity to enter for:—

3 YEAR COURSE TELECOMMUNICATIONS—Entrance standard G.C.E. Ordinary level or equivalent. This course trains Assistant Development Engineers to City and Guilds' Full Technological Certificate level and in addition includes theoretical and practical instruction on computer (digital and analogue), process control and automation. Next course commences 10th September 1957.

SCHOLARSHIPS

Boys who are not academically suited to a Degree course may, through the training offered in the Three-Year Course, achieve interesting in lucrative careers as senior electronic technicians in industry. In order to encourage students of this calibre the E.M.I. College of Electronics has decided to offer **TWO SCHOLARSHIPS THIS YEAR FOR THE ABOVE COURSE** in Telecommunications Engineering.

THE E.M.I. COLLEGE OF ELECTRONICS

Dept. 32, 10 Pembridge Square, London,

W.2. Telephone: BA Yswater 5131/2

The College is part of the E.M.I. Group... Britain's foremost electronic engineers... Pioneers of the world's first public television service



LA. 60

G2AK This Month's Bargains

CRYSTAL HAND MIKES in silver hammer case with polished grille and handle, complete with 4ft. screened lead. 22/6 post free.

100 kc/s **CRYSTALS**, by famous American makers in 3-pin based holder. New condition. Worth £3/10/0. **ONLY 25/-** post free.

HI-FI EQUIPMENT. Amplifiers, speakers, pick-ups by Gramplain, Leak, Quad, Rogers, R.C.A., Spectrone, W.B. Wharfedale, etc., available for immediate delivery.

HEADPHONES. H.R. Type 4,000 ohms, vary sensitive. Only 12/6 pr. Post 1/6. C.L.R. type (low res.) 8/6. Post 1/6.

AMERICAN BREAST MIKES. Swivel head, push to talk and lock-on switch. Excellent job. Only 12/6. Post 1/6.

BRITISH BREAST MIKES complete with pr. of H.R. 4,000 ohm phones in wooden carrying case. New W.D. stock, unrepeatable at 17/6. Post 2/-.

AERIAL WIRE. Copper, 7-25 stranded: 140ft., 10/-, 70ft. 5/-. Hard Drawn 14g.; 140ft., 17/-; 70ft., 8/6. P. & P. 2/-.

RIBBED GLASS 3in. AERIAL INSULATORS, 1/6 ea. or 6 for 7/6. 12 or more post free. Small Shell Porcelain, 4½d. ea. or 4/- doz.

CONDENSERS. 8 µF 600 v. Trop. 750 v. normal condensers. NEW, ex W.D. stocks, 5/6. P. & P. 1/6.

Absorption WAVEMETERS, 3 to 35 Mc/s in 3 switched bands. Complete with indicator bulb. 15/-, postage 1/-.

No C.O.D. on orders under £1.

PLEASE PRINT YOUR NAME AND ADDRESS

CHAS. H. YOUNG LTD.

Dept. 'P' 110, Dale End, Birmingham 4. (CEN. 1635)

Practical Wireless BLUEPRINT SERVICE

PRACTICAL WIRELESS

*No. of
Blueprint*

CRYSTAL SETS

2/- each	
1937 Crystal Receiver ...	PW71*
The "Junior" Crystal Set	PW94*
2/6 each	
Dual-Wave "Crystal Diode"	PW95*

STRAIGHT SETS

Battery Operated

One-valve : 2/6 each	
The "Pyramid" One-valver (HF Pen) ...	PW93*
The Modern One-valver	PW96*

Two-valve : 2/6 each	
The Signet Two (D & LF)	PW76*

3/6 each	
Modern Two-valver (two band receiver) ...	PW98*

Three-valve : 2/6 each	
Summit Three (HF Pen, D Pen)	PW37*

The "Rapide" Straight 3 (D, 2 LF (RC & Trans))	PW82*
---	-------

F. J. Camm's "Sprite" Three (HF, Pen, D, Tet)	PW87*
--	-------

3/6 each	
The All-dry Three ...	PW97*
Four-valve : 2/6 each	

Fury Four Super (SG, SG, D, Pen)	PW34C*
---	--------

Mains Operated

Two-valve : 2/6 each	
Selectone A.C. Radiogram Two (D, Pow) ...	PW19*

Three-valve : 4/- each	
A.C. Band-Pass 3	PW99*

Four-valve : 2/6 each	
A.C. Fury Four (SG, SG, D, Pen)	PW20*

A.C. Hall-Mark (HF Pen, D, Push Pull) ...	PW45*
---	-------

SUPERHETS

Battery Sets : 2/6 each	
F. J. Camm's 2-valve Superhet	PW52*

Mains Operated : 4/- each	
"Coronet" A.C.4	PW100*
AC/DC "Coronet" Four	PW101*

*No. of
Blueprint*

SHORT-WAVE SETS

Battery Operated

One-valve : 2/6 each	
Simple S.W. One-valver	PW88*

Two-valve : 2/6 each	
Midget Short-wave Two (D, Pen)	PW38A*

Three-valve : 2/6 each	
Experimenter's Short-wave Three (SG, D, Pow)	PW30A*

The Perfect 3 (D, 2 LF (RC and Trans)) ...	PW63*
--	-------

The Band-spread S.W. Three (HF, Pen, D, (Pen), Pen)	PW68*
--	-------

PORTABLES

2/-	
The "Mini-Four" All-dry (4-valve superhet)	

MISCELLANEOUS

2/6 each	
S.W. Converter-Adapter (1 valve)	PW48A*

The P.W. 3-speed Autogram (2 sheets), 8/-	
The P.W. Monophonic Electronic Organ (2 sheets), 8/-	

TELEVISION

The "Argus" (6in. C.R. Tube), 3/-	
The "Super-Visor" (3 sheets), 8/-	
The "Simplex"	3/6*
The P.T. Band III Converter	1/6*

All the following blueprints, as well as the PRACTICAL WIRELESS numbers below 94 are pre-war designs, kept in circulation for those amateurs who wish to utilise old components which they may have in their spares box. The majority of the components for these receivers are no longer stocked by retailers.

AMATEUR WIRELESS AND WIRELESS MAGAZINE

STRAIGHT SETS

Battery Operated

One-valve : 2/6	
B.B.C. Special One-valver	AW387*

Mains Operated

Two-valve : 2/6 each	
Consoelectric Two (D, Pen), A.C.	AW403

SPECIAL NOTE

THESE blueprints are drawn full size. The issues containing descriptions of these sets are now out of print, but an asterisk denotes that constructional details are available, free with the blueprint.

The index letters which precede the Blueprint Number indicate the periodical in which the description appears. Thus P.W. refers to PRACTICAL WIRELESS, A.W. to *Amateur Wireless*, W.M. to *Wireless Magazine*.

Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to PRACTICAL WIRELESS, Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

*No. of
Blueprint*

SHORT-WAVE SETS

Battery Operated

One-valve : 2/6 each	
S.W. One-valver for American	AW429*

Two-valve : 2/6 each	
Ultra-short Battery Two (SG, det Pen)	WM402*

Four-valve : 3/6 each	
A.W. Short Wave World-beater (HF Pen, D, RC, Trans)	AW436*

Standard Four-valver Short-waver (SG, D, LF, P)	WM383*
--	--------

Mains Operated

Four-valve : 3/6	
Standard Four-valve A.C. Short-waver (SG, D, RC, Trans)	WM391*

MISCELLANEOUS

Enthusiast's Power Amplifier (10 Watts) (3/6)	WM387*
---	--------

Listener's 5-watt A.C. Amplifier (3/6)	WM392*
---	--------


De Luxe Concert A.C. Electrogram (2 6)	WM403*
---	--------

QUERY COUPON

This coupon is available until Aug. 6th, 1957, and must accompany all Queries sent in accord with the notice on our "Open to Discussion" page. PRACTICAL WIRELESS, Aug. 1957.

EASY AS "A.B.C" — CHEAP TO MAKE!

LOOK!

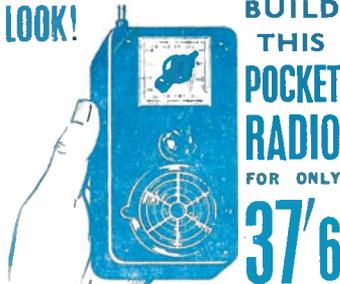

BUILD THIS POCKET RADIO FOR ONLY 37/6

AT LAST! in response to many requests we now present the **DOUBLE TRIODE "SKYPOCKET"**—a beautifully designed precision **POCKET RADIO**. No radio knowledge needed!—**EVERY SINGLE PART TESTED BEFORE DESPATCH**; our simple, pictorial plans take you step-by-step. This set has a remarkable sensitivity due to painstaking design. Covers all medium waves 200 to 650 Metres. Size only 5 1/2 in. x 3 in. x 2 1/2 in. In Strong, Transparent case with panel cover and ivory dial. A really personal-phone, pocket-radio WITH **DETACHABLE ROD AERIAL**. Self-contained all-dry battery operation. Average building time 1 hour. **Total Building Cost—including Case, Double Triode Valves, etc.**, in fact, everything down to the last nut and bolt—**ONLY 37/6**, with plans. Postage, etc., 2/- C.O.D. 1/6 extra. Parts sold separately. Priced Parts List, etc., 1/6. Demand is certain to be heavy—**SEND TODAY!**



47/6

Build this exceptionally sensitive double triode radio. Uses unique assembly system and can be built by anyone without any radio knowledge whatever in 45 minutes. Handsome black-crackle steel case with specially made black and gold dial with stations printed. Size of radio only 6 1/2 in. x 5 in. x 3 in. Covers all Medium and Long waves—uses only one all-dry battery. H.T. consumption only 1 to 1.5 mA. Uses personal phone. Ideal for Bedroom, Garden, Holiday, etc. Many unsolicited testimonials. Mr. Norton of Oxford writes: "Yesterday evening on the Medium waveband, I counted 32 separate stations; I am very pleased with the set, which is well worth the money. **BUILD THE "SKYROMA" NOW!** Total building cost—everything down to last nut and bolt—47/6 (Postage, etc., 2/-) with full set of clear, easy-to-follow plans. (Parts sold separately. Priced Parts Lists, etc., 1/6.)



107/6

Total building cost including choice of beautiful walnut veneered cabinet or ivory or brown bakelite. This is the lowest possible price consistent with high quality. No radio knowledge whatever needed... can be built by anyone in 2-3 hours, using our very simple easy-to-follow diagrams. The terrific new circuit of the **"OCEAN-HOPPER"** covers all medium and long waves with optional negative feedback. Has razor-edge selectivity, and exceptionally good tone. Price also includes ready drilled and punched chassis, set of simple easy-to-follow plans—in fact, everything! All parts sparkling brand new—no junk! Every single part tested before despatching. Uses standard octal-base valves: 6KT6 high-frequency pentode feedback into 6J5G anode-pent detector triode, coupled to 6V6G powerful output beam-power tetrode, fed by robust rectifier. For A.C. Mains, 200-250 Volts (low running costs—approximately 18 Watts!). Size 12 in. x 6 in. x 5 in. Build this long range powerful midgut **NOW**. All parts and set of plans, **£5.7.6**. (Post and packing 3/6.) Parts sold separately. Priced Parts List, 1/6.

Build This TRANSISTOR POCKET SET For Only 49/6!



FEW ONLY AT 92/6!

NEW in maker's sealed cartons!—limited quantity of the famous 3-speed record player units, exceptionally easy to fix, with lightweight pick-up, incorporating "Acos" crystal turnover head and separate sabre-tine styl for Standard and Long-Playing. With full instructions and fixing plans. Unbeatable price 92/6, plus 3/6 Post, Packing, etc. C.O.D. 2/- extra. **RUSH YOUR ORDER NOW—BEFORE IT'S TOO LATE!**



WE'VE DONE IT AGAIN!—our design department in response to a great many requests have designed this **"SKY-FLITE" VEST-POCKET RADIO** which gives a superb performance. It is highly sensitive, size only 4 1/2 in. x 3 1/2 in. x 1 in., the weight under 7 ozs.—yet it is a **TWO-STAGE**

receiver covering all medium waves, working entirely off a tiny "pen-light" battery, which costs 6d.—fits inside the case—and lasts many months. Uses personal phone and has push-button **LUMINOUS On/Off Switch**. Every part tested before despatch! **SPECIAL STEP-BY-STEP PLANS** for **ABSOLUTE BEGINNERS**. Total building cost including case, transistors, etc.—everything down to the last nut and bolt—**ONLY 49/6** with plans. Postage, etc., 2/- C.O.D. 1/6 extra. (Parts sold separately. Priced parts list, etc., 1/6.) As the building cost is absolutely "rockbottom" (it might increase later) **DEMAND WILL BE VERY HEAVY—RUSH YOUR ORDER TODAY!**

BUILD THIS TRANSISTOR SET FOR ONLY 35/-
VERY SPECIAL OFFER WHILE STOCK OF PARTS LASTS!—The "Sky-Scout" Pocket two-stage transistor set, size only 1 1/2 in. x 3 1/2 in. x 1 1/2 in. Covers all medium-waves and works entirely off tiny "pen-light" battery which costs 6d. and fits inside case. All parts tested before despatch. Can be built for 35/-, plus 2/- post and packing, including Case, Transistor, **STEP-BY-STEP PLANS FOR ABSOLUTE BEGINNERS**, nuts, bolts, etc. (C.O.D. 1/6 extra.) Parts sold separately, priced parts list, etc., 1/6. **VERY SIMPLE TO BUILD.**



ONLY £8-12-6

BRAND NEW — NOT SURPLUS! In maker's sealed cartons. Latest UAB "Monarch" 4-speed record-player complete with High-fidelity "turnover" head. Type HGP 37-1. Capacity of 10 Records, plays 12 in., 10 in. and 7 in. indormed in any order, 78, 45, 33 and 16 r.p.m. For A.C. mains 100 to 250 volts. Exclusive "magdisk" selector gives quickest and quietest change ever. With full instructions and fixing plans. Limited Quantity at **£8-12-6**, plus 4/6 Post, Packing, etc. **WHY PAY MORE? SEND NOW WHILE STOCKS LAST!**—modernise your radiogram and increase its value.

CONCORD ELECTRONICS
 69, PRESTON STREET, BRIGHTON.

Dept. PWL

Orders receive prompt attention. Cheques accepted. Cash on delivery 1/6 extra. Please print name and address in block letters Suppliers to Schools, Universities, Government and Research Establishments. Complete range of components and valves stocked. **CALLERS WELCOME.** Shop Hours: 9 a.m. to 6 p.m. (1 p.m. Thursday). Regret no C.O.D. abroad.