

• A SWITCHED F.M. TUNER •

PRACTICAL 1/3

MAY
1958

EDITOR: F.J. CAMM

WIRELESS



CONTENTS

A BEGINNER'S
CONSTRUCTIONAL COURSE

SERVICING THE COSSOR
529 & 540

TRANSISTORS IN PRACTICE

SIMPLE TONE CONTROL
CIRCUITS

SERVICING TRANSISTOR
SETS

THE IMPORTANCE OF
THE AERIAL

THE "WEYRAD" SIGNAL GENERATOR



AN INSTRUMENT OF HIGH ACCURACY AT LOW COST

- Coverage 100 Kc/s-70 Mc/s (on fundamentals).
- Accuracy better than $\pm 2\%$ on all ranges.
- Large, clearly calibrated scale.
- Modulated or C.W. output.
- 500 c/s A.F. source.
- S.G.M.I.—A.C. mains operation. Double wound, varnish-impregnated transformer, tapped 210/225/250 volts.
- S.G.B.I.—All dry battery operated.
- All components are by well-known manufacturers ensuring maximum reliability.
- Both types in quantity production.
- Illustrated leaflet available, price 2d.

WEYMOUTH RADIO MANUFACTURING CO., LTD.
CRESCENT STREET, WEYMOUTH, DORSET

*Trace the Trouble
in a Trice*

PIFCO

ALL-IN-ONE RADIOMETER

- ★ Circuit Test
- ★ L.T. & H.T. Tests
- ★ mA Test
- ★ Valve Test

Use the PIFCO All-in-One RADIOMETER for the practical testing of all types of radio and electrical apparatus. You can carry out continuity and resistance tests, check H.T., L.T., and G.B. voltages, also Household Appliances, Car Lighting Systems, Bell Circuits, etc. May be used on A.C. or D.C. mains.

Obtainable from your local dealer.
Write for informative folder to:—

PIFCO LTD., WATLING ST., MANCHESTER, 4
36-37, UPPER THAMES ST., LONDON, E.C.4

ONLY
32/6
COMPLETE

ADCOLA
PRODUCTS LIMITED
(Regd. Trade Mark)

SOLDERING EQUIPMENT

ILLUSTRATED

$\frac{3}{16}$ " Detachable
bit type (List
No. 64)

Protective Shield
(List No. 68)

Catalogues sent
FREE

Telephones:
MACaulay 4272
& 3101



British and
Foreign Pat.

Reg. Designs,
etc.

Head Office, Sales:

**ADCOLA
PRODUCTS
LTD.**

**Gauden Road,
Clapham High
St., London,
S.W.4**

EMI "HIS MASTER'S VOICE" MARCONIPHONE · COLUMBIA


Announce NEW PRACTICAL WAY OF LEARNING AT HOME

NEW — completely up-to-date methods of giving instruction in a wide range of technical subjects specially designed and arranged for self-study at home under the skilled guidance of our teaching staff.

NEW — experimental outfits and lesson manuals are despatched on enrolment and remain the student's property. A tutor is allotted to each student for personal and individual tuition throughout the course.

Radio and television courses, with which specially prepared components are supplied, teach the basic electronic circuits (amplifiers, oscillators, detectors, etc.) and lead, by easy stages, to the complete design and servicing of modern Radio and T/V equipments.

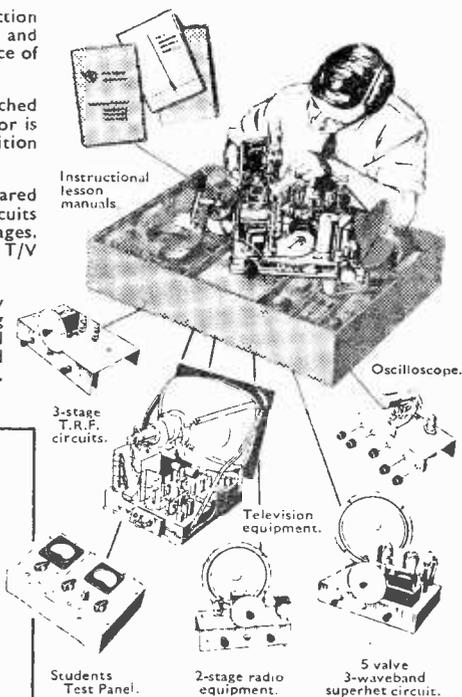If you are studying for an examination, wanting a new hobby or interest, commencing a career in industry or running your own full-time or part-time business, these practical courses are ideal and may be yours for moderate cost. Send off the coupon to-day for a free Brochure giving full details. There is no obligation whatsoever.



Courses with Equipment

RADIO · SHORT WAVE RADIO

TELEVISION · MECHANICS

CHEMISTRY · PHOTOGRAPHY

ELECTRICITY · CARPENTRY

ELECTRICAL WIRING · 'HI-FI'

DRAUGHTSMANSHIP · ART etc.

E.M.I. Factories at Hayes England.



EMI INSTITUTES

Fill in for **FREE BROCHURE**
E.M.I. INSTITUTES, Dept. 32 X, London, W.4.

Name _____ Age _____
 (if under 21)

Address _____

I am interested in the following subject(s) with/without equipment _____

(We shall not worry you with personal visits)

FREE

BLOCK CAPS PLEASE

MAY/58

The only Home Study College run by a World-wide industrial organisation

TOP QUALITY FULLY GUARANTEED VALVES

ALL GOODS LISTED ARE ACTUALLY IN STOCK

EXPRESS SERVICE ! ! !

C.O.D. ORDERS RECEIVED BY 3.30 P.M., EITHER BY LETTER, PHONE OR WIRE, DESPATCHED THE SAME AFTERNOON. ALL ORDERS RECEIVED BY FIRST POST DESPATCHED SAME DAY.

FOR ONLY 6d. EXTRA PER PARCEL WE WILL INSURE YOUR VALVES AGAINST DAMAGE IN TRANSIT. ALL UNINSURED PARCELS AT CUSTOMER'S RISK.

1A3	3/- 6AU6	10/6 6L6G	9/6 12AH7	8/- 135 51	12/6 D1	3 - ECC82	8/- EZB1	10/- PCF82	12/6 UBC41	9/6
1A5	6/- 6B4G	6/6 6L18	13/- 12AH8	10/6 35A5	11/- D42	10/6 ECC83	9/- FW4/800	PCL82	12/6 UBF80	9/6
1A7	15/- 6B7	10/6 6N7	8/- 12AT6	10/6 35L6GT	10/- D63	5 - ECC84	10/-	12/6 PCL83	17/6 UBF89	10/6
1D6	10/6 6B8G	4/6 6Q7G	11/- 12AT7	9/- 35V4	8/6 D77	6/6 ECC85	9/6 GZ30	10/6 PEN40DD	UCC85	10/6
1H5	11/- 6B8M	5/- 6Q7G	11/- 12A7	8/- 35Z3	10/6 DAC32	11/- ECC91	9/6 GZ32	12/6	25/- UCH42	11/-
1L4	6/6 6BA6	7/6 6R7G	10/- 12AX7	9/- 35Z4GT	8/- DAF91	8/- ECF80	13/6 GZ34	14/- PEN45	19/6 UCH81	11/6
1LD5	5/- 6BE6	7/6 6SA7GT	8/6 12BA6	9/- 35Z5GT	9/- DAF96	10/- ECF82	13/6 H30	5/- PEN46	7/6 UCL82	15/6
1LN5	5/- 6B16	8/- 6SC7	10/6 12BE6	10/- 41MTL	8/- DF33	11/- ECH35	9/6 H63	12/6 PL82	10/- UFA1	9/-
1N5	11/- 6BR7	11/6 6SG7GT	8/- 12E1	30/- 50C5	12/6 DF91	7/- ECH42	11/- HABC80	PL83	11/6 UF80	10/6
1R5	8/6 6BW6	9/6 6SH7	8/- 12J5GT	4/6 50L6GT	10/6 DF96	10 - ECH81	9/-	13/6 PM2B	12/6 UF85	10/6
135	8/- 6BW7	12/6 6S17	8/- 12J7GT	10/6 72	4/6 DH63	10/- ECL80	14/- HK90	10/- PM12	6/6 UF89	10/6
1T4	7/- 6BC4	12/6 6SK7GT	8/- 12K7GT	7/6 77	8/- DH76	7/6 ECL82	14/- HL23	10/6 PM12M	6/6 UL41	11/-
1U5	10/- 6C6	7/- 6SL7GT	8/- 12K8GT	78	8/6 DH77	8/6 EF36	6/- HL41	12/6 PY80	9/- UL46	15/6
2A7	10/6 6C5	6/6 6SN7GT	7/6	14/- 80	9/- DK32	15/- EF37A	9/- HL133DD	PY81	9/- UL84	11/6
2C26	4/- 6C6	6/6 6S57	8/- 12Q7GT	7/6 83V	12/6 DK91	8/6 EF39	6/-	12/6 PY82	9/- UY41	8/6
2D13C	7/6 6CB	12/6 6U4GT	14/- 12SA7	8/6 85A2	15/- DK92	12/6 EF40	15/- HVR2	20/- PY83	9/6 UY85	10/6
2X2	4/6 6C9	12/6 6U5G	7/6 12SC7	8/6 150B2	15/- DK96	10/- EF41	9/6 HVR2A	6/- QP21	7/- V1507	5/6
3A4	7/- 6C10	12/6 6U7G	8/6 12SG7	8/6 220P	10/6 DL2	15/- EF42	12/6 K135	8/6 QP25	15/- VLS492A	£3
3A5	12/6 6CH6	6/6 6V6G	7/- 12SH7	8/6 807	7/6 DL33	9/6 EF50(A)	7/- KT2	5/- QS150/15	VMP4G	15/-
3B7	12/6 6D6	6/6 6V6GT	8/- 12SJ7	8/6 956	3 - D 66	15/- EF50(E)	5/- KT33C	10/-	VP2(7)	12/6
3D6	5 - 6E5	12/6 6X4	7/- 12SK7	8/6 1203	7/- DL92	8/- EF54	5 - K44	15/- QVO4/7	VP4(7)	15/-
3Q4	9/- 6F6G	7/- 6XS5GT	6/6 12SQ7	8/6 4033L	12/6 DL94	9/- EF73	10/6 KT63	7/-	15/- VPI3C	7/6
3Q5GT	9/6 6F6GT	8/6 6Z4/84	12/6 12SR7	8/6 5763	12/6 DL96	10/- EF80	8/6 KTW61	8/- R12	12/6 VPA1	7/6
354	8 - 6F8	12/6 6Z5	12/6 12Y4	10/6 7193	5/- DLS10	10/6 EF85	9/6 KTW62	8/- SD6	12/7 VR105/30	
3V4	9/- 6F12	9/6 6Z0L2	12/6 14R7	10/6 7475	7/6 DM70	8/6 EF86	14/6 KTW63	8/- SP47	15/-	9/-
5U4	8/6 6F13	13/- 7A7	12/6 14S7	17/- 9002	5/6 EA50	2/- EF89	10/- KTZ41	8/- SP41	3/6 VR150/30	
5V4	12/6 6F16	9/6 7B7	9/- 19AQ5	11/- 9003	5/6 EA76	9/6 EF91	9/- KTZ63	10/6 SP42	12/6	
5X4	12/6 6F17	12/6 7C5	8/- 19H1	10/- 9006	6/- EABC80	9/- EF92	6/6 L63	6/- SP61	3/6 VT61A	5/-
5Y3G	8/- 6F32	10/6 7C6	8/- 20D1	16/- AC6PEN	7/6 EAC91	7/6 EL32	5/6 LN152	14/- SU61	12/6 VT501	5/6
5Y3GT	8/6 6F33	7/6 7H7	8/- 25L6GT	10/- AC/HL	EA42	10/6 EL41	11/- LZ319	14/- TP22	15/- W76	7/6
5Y4	12/6 6G6	6/6 7Q7	9/- 25Y5	10/6 DDD	15/- EB34	2/6 EL42	11/6 MH4	7/- U16	12/6 W81	6/6
5Z3	12/6 6H6GT/G	757	10/6 25Y5G	10/6 AC/PA	8 - EB41	8/6 EL81	11/6 MHL4	7/6 U18/20	12/6 X61	12/6
5Z4G	10/6	3/- 7V7	8/6 25Z5	10/6 AL60	10/- EB91	6/6 EL84	10/6 MHLD6	12/6 U22	8/- X65	12/6
5Z4GT	12/6 6H6M	3/6 7Y4	8/- 25Z4G	10/6 ALP4	7/6 EBC33	7/6 EL91	5/- ML4	12/6 U31	10/- X66	12/6
6A8	10/- 6J5G	5/- 8D2	3/6 25Z6G	10/- ATP4	5/- EBC41	10/- EM34	10/- ML6	6/6 U43	12/6 XD(1.5)	6/6
6A8B7	8/- 6J5GTG	5/6 8D3	9/- 28D7	7/- ATP4	12/6 EBF80	10/- EM80	10/6 MU14	10/- U50	8/- XFW10	6/6
6A8B8	14/- 6J5GTM	6/- 9D2	4/- 30	7/6 BL63	12/6 EBF89	9/6 EY51	OA10	12/6 U52	8/6 XFY12	6/6
6AC7	6/6 6J6	5/6 10C1	15/- 30C1	14/- CK505	6/6 EC52	5/6 (Small)	12/6 OA70	5/- U76	8/- XH(1.5)	6/6
6AG5	6/6 6J7G	6/- 10F1	19/6 30F5	12/6 CK506	6/6 EC54	6/- EY51	OA71	5/- U78	7/- XSG(1.5)	6/6
6AJ8	9/- 6J7GT	10/6 10F9	11/6 30FL1	12/6 CK523	6/6 EC70	12/6 (Large)	12/6 OC72	30/- U251	15/- Y63	7/6
6AK5	8/- 6K7G	5/- 10F18	12/6 30L1	12/6 CV63	6/6 ECC31	15/- EY66	17/6 P61	3/6 U404	10/6 Z63	10/6
6AL5	6/6 6K7GT	6/- 10LD3	9/6 30PI2	13/6 CV63	10/6 ECC32	10/6 EZ35	6/6 PABC80	15/- UABC80	Z66	20/-
6AP6	9/- 6K8G	8/- 10P3	17/6 31	7/6 CV85	12/6 ECC33	8/6 EZ40	8/- PCC84	10/-	10/6 Z77	9/-
6AQ5	7/6 6K8GT/G	11E3	15/- 33A/158M	CV271	10/6 ECC35	8/6 EZ41	10/6 PCC85	12/6 UAF42	10/6 Z719	12/6
6AT6	8/6	11/- 12A6	6/6	30/- CV428	30/- ECC81	9/- EZ280	9/6 PCF80	14/- UB41	12/7 Z729	14/6

TERMS OF BUSINESS:—CASH WITH ORDER OR C.O.D. ONLY. POST/PACKING CHARGES 6d. PER VALVE; ORDERS VALUE £3 OR MORE POST FREE. MINIMUM C.O.D. FEE AND POSTAGE 3/-. EACH ADDITIONAL VALVE 6d. EXTRA. WE ARE OPEN FOR PERSONAL SHOPPERS MON.-FRI. 8.30-5.30. SATS. 8.30-1 P.M.

ALL VALVES NEW, BOXED, TAX PAID, AND SUBJECT TO MAKERS' GUARANTEE. FIRST GRADE GOODS ONLY, NO SECONDS OR REJECTS. GOODS ARE ONLY SOLD SUBJECT TO OUR TERMS OF BUSINESS, OBTAINABLE FREE ON REQUEST. CATALOGUE OF OVER 1,000 DIFFERENT VALVES 6d.

When comparing our prices, remember just what we offer. Bentley valves are not only "GUARANTEED NEW AND BOXED," and "GUARANTEED TESTED AT TIME OF DESPATCH." Bentley valves are NEW, BOXED, AND SUBJECT TO THE MAKERS' STANDARD GUARANTEE AS WELL. Only our enormous turnover enables us to select the products of the world's finest manufacturers at lowest prices and pass the benefits on to YOU.

BENTLEY ACOUSTIC CORPORATION LTD.


THE VALVE SPECIALISTS

38 CHALCOT ROAD, LONDON, N.W.1.

PRImrose 9090

PLEASE ENQUIRE FOR ANY VALVE NOT LISTED. 3d. STAMP, PLEASE.

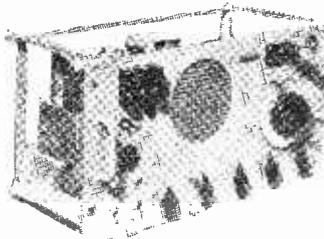SHORT WAVE COMMUNICATIONS RECEIVER
R.208. ONLY £6 - 19 - 6




This is a super short-wave receiver covering 5-30 metres (10-60 Mc/s). Uses 6 valves. Has I.F. stage, 2 I.F. stages, B.F.O., etc. Muirhead instrument drive, two internal power packs, mains and battery vibrator pack. Complete with own P.M. speaker. Provision for phones

and speaker muting. Complete in metal transit case; size approx. 21 x 18 x 12in.; weight 70lb. Suitable A.C. mains 100-250 and 6 volt battery. In perfect condition, practically unused. Tested before despatch and guaranteed. Handbook free with each. Price £6.19.6. carriage and insurance 15/-.


Famous Transmitter virtually given away

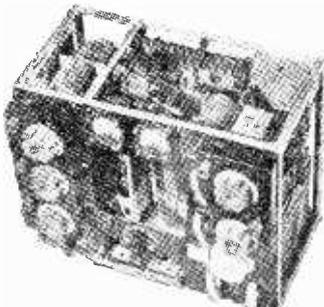The famous R1154N - unused but slightly soiled and not tested. Covers 200-500 Kcs, 3-5.5 Mc/s and 5.5-10 Mc/s. Has unique "click stop" mechanism (7 stops) and permits selected frequency to be held. Returned to, etc. Hartley Oscillator, Power Amplifier, Keying and Speech. Wonderful breakdown value. meters, relays, switches. Complete with valves - real bargain at 29 6 plus 10/- carriage.



SPEAKER BARGAIN

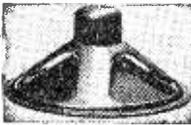12in. Hi fidelity loudspeaker. High flux. Permanent magnet type with standard 3 ohm speech coil. Will handle up to 12 watts. Brand new by famous maker. Price 32 6 plus 3/- post and insurance



The "CRISPIAN" Portable Radio





A 4-valve truly portable battery set with very many good features, as follows: ferrite rod aerials, low consumption valves, superhet circuit with A.V.C. ready-built and aligned chassis if required, beautiful two tone cabinet covered with I.C.I. rexine and Pyral. Guaranteed results on long and medium waves anywhere. All parts, including speaker and cabinet are available separately or if all ordered together the price is £7 15/- complete, or 35/- down and 7

payments of £1 0/0. post and ins. 3/-, ready built chassis 30/- extra. Instruction booklet free with parts or available separately, price 1/6.

CHARGING SWITCHBOARD

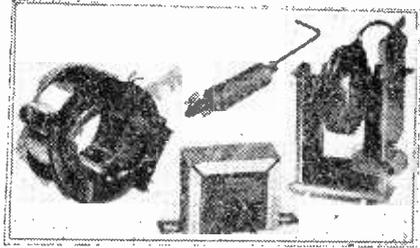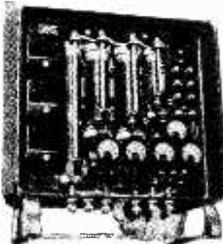Offered at about one-twentieth of original cost. This is an ex-Government switchboard. It contains three reverse current relays, one voltmeter, one main ammeter, two secondary ammeters and three variable resistors for controlling circuits. These are original cases. Price 23 15/-, Carr. 10/-.



FOUR ITEMS FOR THE PRICE OF ONE

This set of modern T.V. parts is equally suitable for modernising an old television or for building into a new one. Suitable for wide angle 14in. or 17in. tubes using EHT or £2-14 kv. The four items comprise: (1) Line output EHT transformer (2) 70 scanning coils on ferrite yokes, (3) Width control with ferrite core, (4) Frame output transformer. With these parts we also give free, complete circuit diagram of a modern television which uses them. We offer the whole lot at the price of the Line output transformer only, namely 57 6, plus 2 6 post and insurance.

All for less than the price of the cabinet

Fine walnut veneered table receiver cabinet complete with metal chassis, three colour glass scale, back plate and scale mounts, as illustrated but less knobs. Offered at less than the price of the cabinet, namely 39 6 plus 5/- carriage and insurance.



FLEX SNIP 14 36

Twin twisted D.V. lighting flex, 100 vd. coils £2 post free. White or maroon.


HI-FI SNIP

Infinite Wall Baffle

Nicely veneered and polished. Corner fitting (attaches to picture rail). Takes up no floor space. Gives really fantastic results with only low-priced 8in. speaker fitting for tweeter. Only 45/- each, carriage and insurance 3/6.



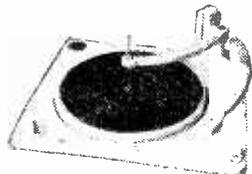Yours for 10/- down and 17 weekly payments of 10/- or cash price £8.10.0



The latest most up-to-date Record Player made by the famous B.S.R. Company. Using Hi-Fi Crystal Pick Up and fitted with every modern device. Definitely a record changer which will give years of trouble-free music. Not surplus but the current model. Price £8.10/- or 10/- deposit and 17 weekly payments of 10/-, carriage and insurance 5/-.

ELECTRONIC PRECISION EQUIPMENT LTD.
66 GROVE ROAD, EASTBOURNE

For Shop Address see Double Page Advertisement

W.D. CIRCUIT DETAILS

Diagrams and other information extracted from official manuals. All 1/6 per copy. 12 for 15/- American Service.

- Sheets**
- A.1134 R.109 78 receiver
 - BC.348 76 receiver
 - BC.312 R28/ARC5
 - R.103A R1116A
 - BC.392 RA-1B
 - RA-15 AR8D
 - R-208 AN/APA-1
 - R-1155 78
 - R-1124A 76
 - R-1132A R-1481 R.T.18
 - R-1147 CAY-46-AAM-
 - R-1224A RADAR
 - R-1082 A.S.B.-3
 - R-1355 Indicator 62A
 - B.C.1206-A/B Indicator A.S.B.3
 - B.453-A (or-B) Indicator 92
 - B.454-A (or-B) Indicator 6K
 - B.455-M-A (or-B) R.F. unit 24
 - Transmitter T1154 R.F. unit 26
 - Fifty-eight walkie R.F. unit 25
 - talkie R.F. unit 27
 - Frequency meter Wireless set No.19
 - B.C.221 Demobbed valves

THERMOSTATS



2in. x 1in. x 1 1/2in. high. Useful for the control of appliances such as convectors, gluepots, vulcanisers, hot plates, etc. Adjustable to operate over temperature range 50-250 deg. F., fitted with heavy silver contacts.


11 amp., 3/6; 5 amp., 8-6; 2 amp. OMB, 5/6; 15 amp. OMB, 15/- 15 amp. wall mounting type, 19/6.

SAPPHIRE NEEDLES

Unrepeatable bargain—new and perfect—two types available: miniature E.M.I. and Standard (trailer). Sale price 1/- each or 10/- doz.



TWIN FEEDER

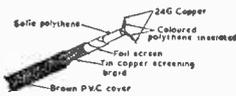

Ideal for FM down lead, as a twin microphone lead, etc. Sale price 6d. per yard. 80 ohm co-ax. low loss for Band III. 8d. per yard.

CHASSIS ASSEMBLY




Superhet Chassis, 3-waveband, coloured scale, scale pan, pulleys, driving head, springs, drum, etc. Scale size 1 1/2in. x 3 1/2in. Chassis size 1 1/2in. x 1 1/2in. x 2in. Price 15/- plus 1/6 post. Note: We can supply cabinet for this. Price 39/6 plus 5/- carr. and insurance.

CROCODILE CLIP for metering, etc. Has sharp point for piercing insulation without spoiling it. 8d. each or 7/- per dozen.

15 AMP. SLYDLOK panel mounting fuse and fuse carrier, 2/6.

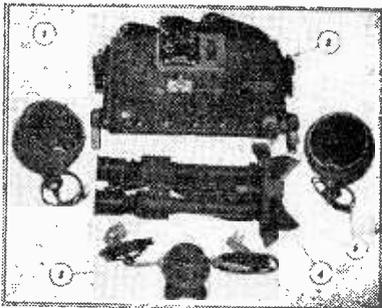DOUBLE POLE CONTACTOR on bakelite case, coil resistance 100 ohms, heavy duty silver contacts. 3/6.



TABBY EQUIPMENT COMPLETE

Complete equipment for seeing in the dark, as fitted to Army vehicles for night driving, etc. Complete working equipment comprises: 2 Infra Red Radiators, adjustable binoculars, powerpack for 6 or 12 volts, control units and inter-connection cables. Original cost probably around £100. Unused and in perfect order—£10, plus 10/- carriage and insurance. Mains power pack £4 extra.

PUBLICATIONS FOR CONSTRUCTORS

Title	Short Description	Price
Car Starter Charger	A 6-12 volt 5 amp battery 1/6 with overcharge position.	1/6
Chimelite	Door chimes and hall light 2/- combined.	2/-
I.T.A. Converter	A two valve unit suitable for converting any type of television.	1/6
Crispian	Four valve all dry battery 1/6 portable.	1/6
Economy Amplifier	Cheapest possible 3 valve mains amplifier.	1/6
Skysearcher	Cheapest possible 2.3 valve mains receiver for medium wave.	1/6
Economy Three	Three valve battery version of the Skysearcher.	1/6
F.M. Tuner	Good unit quality tuner based on the original Radio Constructor circuit.	1/6
Mini Radio	Four valve mains T.R.F. medium and long wave.	1/6
A.C./D.C. Multi-meter	15 range test meter for A.C. and D.C. volts, ohms and milliamperes.	1/6
Simplex	The simple transistor receiver for headphones.	9d.
Transistor Timer	For photographic and process timing.	9d.
Easy to Build T.V.	A modern set suitable for wide angle 14" or 17" tubes which can be assembled in an evening (only 24 solder joints to make).	3/6
Condenser Tester	Tester for all types of condensers, can also be used for reforming electrolytics.	9d.
C.R.T. Tester	A device for testing and re-activating television picture tubes.	9d.
Beginners' Superhet	A 4 valve mains operated receiver, simple to make and align.	5d.
Two Way Switch	Describes how to control a light from two points.	9d.
Moisture Operated Switch	Describes a switch which is operated by moisture.	9d.
Electric Blanket	Describes how to make a foolproof, waterproof electric blanket.	9d.
Anti-burst	Describes how pipes in lofts can be prevented from freezing.	9d.
Thermal Delay Switch	Shows circuits of process timer, sequence switch, overload relay, smoke control, etc.	9d.
Solder Gun	Shows how to make a 7 second solder gun.	9d.

Special Offer: All the above booklets and pamphlets, 12/6 or any ten at half price.

STOP PRESS ITEMS


R. & C. SUBSTITUTION BOX
As described in last month's issue—author describes this as second most used instrument on his bench. Kit of components with full instructions, £2.10.0, plus 2/6 post and insurance.

SIMPLETON

Electronic organ described in February issue. Kit of components as specified complete with valves but not chassis or case. £4.10.0, plus 3/6 post and ins.



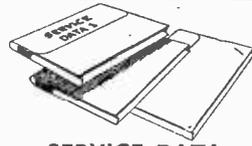
TV Masks
Latest type grey crystallate.
14in., 10", 17in., 12"
Plus 1/- Post.



SERVICE DATA

100 service sheets, covering British receivers which have been sold in big quantities and which every service engineer is ultimately bound to meet. The following makers are included: Aerodyne, Alba, Bush, Cossor, Ekco, Ever-Ready, Ferguson, Ferranti, G.E.C., H.M.V., Kolster Brandes, Lissen, McMichael, Marconi, Mullard, Murphy, Philco, Philips, Pye, Ultra. Undoubtedly a mine of information invaluable to all who earn their living from radio servicing. Price £1 for the complete folder.

Mains Isolation Transformer

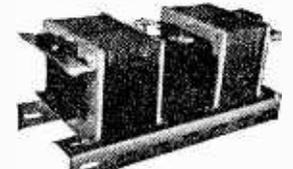

Makes servicing safe, also makes the adjustment for difference in mains voltage very simple. Input tapped 200-250 v., output tapped 200-250 v. Continuously rated at 500 watts, intermittent rating 2,000 watts. Cable entry by terminal blocks, two separate screens for suppressing mains interference. Size approximately 14in. x 6in. x 6in. weight approximately 40lbs. Price £5/12/6. Carriage and insurance 7/6 (up to 250 miles).

Sub-Miniature Electrolytics

These are extremely small—for instance 1 mfd is only approx. 1in. long by a little over 1in. diameter. Mainly developed for transistor receivers, price 2/9 each. Special quotes for quantities. The following values available but additional types are being added almost weekly: 1 mfd, 18 v., 1.5 mfd, 6 v., 2.5 mfd, 6 v., 6 mfd, 6 v., 5 mfd, 12 v., 8 mfd, 6 v., 10 mfd, 6 v., 16 mfd, 12 v., 25 mfd, 6 v., 25 mfd, 25 v., 32 mfd, 3 v.

Yaxley Switches

3-pole 2-way	1/3
12-pole, 2-way	1/6
3-pole, 3-way	1/6
9-pole, 3-way	2/-
2-pole, 4-way	2/-
6-pole, 4-way	2/6
4-pole, 5-way	2/6
2-pole, 6-way	2/6
1-pole, 7-way	2/6
1-pole, 12-way	2/6
6-position shorting switch	2/-
Double pole mains switch for attaching to Yaxley switches...	1/6	


Discount of 10% allowed where a dozen of one type ordered. Special quotes 144 or over.

Tube Tester and Re-Activator

We can supply all the main components for making this unit which will not only test Cathode Ray Tubes but also will re-activate them, supplied complete with full instructions. Price £3, plus 2/6 post and ins.

Transistor Timer

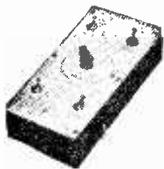All the parts for making transistorised Enlarging or Process Timer with constructional details. £2 10/-, plus 2/6 post and pkg.



Beginner's Superhet

All the component, including metal chassis, valves, metal rectifier, coils, tuning condenser, etc., etc. required to build the "Beginner's Superhet" as described in the January issue, are available as a parcel. Price £3, plus 3/- post and ins.



Condenser Tester and Re-Activator

This unit tests condensers under correct working conditions at proper voltages, it can also be used for "reforming" electrolytics. All basic parts and full instructions, 50/- plus 2/6 post and ins.

Band III Converter

Suitable for Wales, London, Midlands, North, Scotland, etc. All the parts including 2 EF80 valves, coils, fine tuner, contrast control, condensers, and resistors. Metal case available as an extra. Price only 19/6, plus 2/6 post and insurance. Data free with parts or available separately 1/6.



Making a Solder Gun

A 7-second solder gun of the type costing £2.4 was described in Elec. Mech. Only two essential parts are required—(a) transformer and (b) push switch. These we can supply at 13/6, plus 2/- post. The rest of the parts you will have in your own "junk" box. Copy of the article concerned given free with the kit.




A.C./D.C. Multimeter Kit
15 Basic Ranges

Measures A.C./D.C. volts, D.C. current and ohms. All the essential parts including metal case, zinc moving coil meter, selected resistors, wire for shunts, range selector, switches, calibrated scale and full instructions. Price 19/6, plus 2/6 post and insurance.



AM/FM Chassis

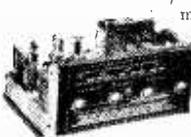

made by the famous McCarthy Radio. This employs a printed circuit in the F.M. Tuner section. It uses 8 valves and has a very attractive three colour dial, size approximately 12 x 5 1/2 in., covers four wavebands: 1000-2000 m., 200-550 m., 15-50 m., and 83-100 mc/s. This is a precision made chassis with four controls, tuner, volume, wavechange and tone, fully gear. Price £22 10/-, post and ins. 5/-.


19 Range Testmeter




Can be yours for only 10/- deposit and 19 payments of 10/- weekly. Like all AVO meters it is a very fine instrument: it has a sensitivity of 10,000 ohms per volt and 19 most useful ranges as follows—D.C. volts 0-1.000 (seven ranges), A.C. volts 0-1,000 (five ranges), 0-1 amp. (3 ranges), resistance 0-2 meg. (2 ranges), complete with test leads. Immediate delivery. Cash price £9.10.0 non-callers please add 3/6 post & ins.

14in. T.V. CABINET

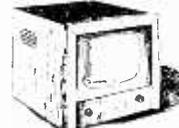14in. T.V. cabinet of the latest styling made for one of our most famous firms—beautifully veneered and polished—limited quantity 19/6 each. Carga and packing 2/6 extra.



NOW 2 MODELS Turret Tuner

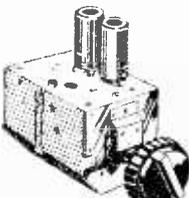


Brand new stock, not surplus, with coils for Band I and III complete with valves. Model 1 I.F. output 33.33 Mc/s. Series heaters. Model 2 I.F. output 16.19 Mc/s. Parallel heaters. With instructions and circuit diagram, 79/6. With knobs 3/6 extra, post and insurance 2/6.

THIS MONTH'S SNIP

A 10 valve unit complete with valves, unused but a little soiled only 19/6 plus 7/6 carriage and insurance. This unit, the RL135, contains a famous I.F. strip which is usable almost without modification for television. It is in fact an I.F. Amplifier for the R.F. units 24, 25, 26, 27, etc. Data is available showing how to make a television, etc., etc. Contains 10 tubes, transformers, coils, pot-meters, etc., etc. for gain not to be missed.

HUGE MINISTRY PURCHASE
R.1155—yours for £2 down.

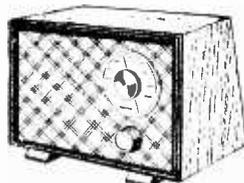Frequency 75 Kcs to 18 Mc. 10 valves metal case 10tube receiver cost 0.00 £20 to make—will give years of service, very little used. Price £10 of 5 payments of £2. (cash & bank) cas. 15/-.



THE SKYSEARCHER

This is a 2-valve plus-metal receiver set useful as an educational set for beginners, also makes a fine second set for the bedroom, workshop, etc. All parts, less cabinet, chassis and speaker, 19/6. Post and ins. 2/6. Data free with parts or available separately 1/6. 3-valve battery version also available at the same price.


ALL-MAINS AMPLIFIER




Powerful three-valve Mairs amplifier ideal for dances, parties, etc. Complete less chassis, cabinet and speaker (available if required)—data 1/6 (free with parts). Price 19/6, plus 2/6 post and insurance.

Simplex Transistor Kit

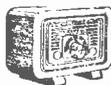Makes ideal bedroom radio, uses one transistor and one crystal diode. Complete less case 19/6, case 5/- extra post and ins. 1/6.



Complete Walkie-Talkie for £1.

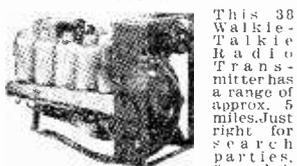

This 30 Walkie-Talkie Radio Transmitter has a range of approx. 5 miles. Just right for search parties, fire brigades, etc. Operates on dry batteries. Complete with five valves and in metal case. Size approx. 9" x 8" x 3 1/2". Un-used but not tested or guaranteed. £1 only, plus 2/6 post and insurance.

GLASS PANELS

Size 10 x 9 1/2—parcel of five panels, 7/6, plus 3/6 carriage.



ELECTRONIC PRECISION EQUIPMENT, LTD.

Post orders are dealt with from Eastbourne, so for prompt attention please send your orders to 66 Grove Road, Eastbourne, marked Department 7.

43-45, Windmill Hill, 66, Grove Road, 129, Stroud Green Rd., 266, London Road, 4, Guildship, Middx., Eastbourne, Sussex, 1, Croydon, (Phone: RUSLIP 5700) (PHONE: ARCHWAY 1049) (Phone: CRU 6554) Half day, Wednesday. Half day, Saturday. Half day, Thursday. Half day, Wednesday.

R.S.C. BATTERY CHARGING EQUIPMENT

ASSEMBLED CHARGERS
 6 v. 1 amp. 19/9
 6 v. or 12 v. 1 amp. 27/9
 6 v. 2 amps. 29/9
 6 v. or 12 v. 2 amps. 38/9
 6 v. or 12 v. 4 amps. 58/9
 Above ready for use. Carr. 3/6. With mains and output leads.

SELENIUM RECTIFIERS F.W. BRIDGE TYPES
 6/12 v. 1 a. 4/11 I.T. Types H.W. 24 v. 1 a. 1/11
 6/12 v. 2 a. 9/9 6-12 v. 1 a. H.W. 2/9
 6/12 v. 3 a. 11/9 H.T. Types H.W. 150 v. 40 mA. 3/9
 6/12 v. 4 a. 14/9 250 v. 50 mA. 5/9
 6/12 v. 5 a. 18/9 250 v. 80 mA. 7/9
 6/12 v. 10 a. 25/9 250 v. 250 mA. 11/9
 6/12 v. 15 a. 35/9

BATTERY CHARGER KITS
 Consisting of Mains Transformer, F.W. Bridge, Metal Rectifier, well ventilated steel case, Fuses, Fuse - holders, Grommets, panels and circuit. Carr. 2/9 extra.
 6 v. or 12 v. 1 amp. 22/9
 6 v. 2 amps. 25/9
 6 v. or 12 v. 2 amps. 31/6
 6 v. or 12 v. 4 amps. 53/9

BATTERY CHARGER KIT
 Consisting of F.W. Bridge Rectifier, 6/12 v. 5 a. Mains Trans., 0-9-15 v. 6 a. output and Ammeter. 49/9. Post 3/9.

ASSEMBLED CHARGER
 6 v. or 12 v. 2 amps.
 Fitted Ammeter and selector plug for 6 v. or 12 v. Louvred metal case, finished attractive hammer blue. Ready for use. With mains and output leads. Double Fused. Only Carr. 3/9. **49/9**

All for A.C. Mains 200-250 v., 50 c/c. Guaranteed 12 months.



Assembled 6 v. or 12 v. 4 amps.
 Fitted Ammeter and variable charge rate selector. Also selector plug for 6 v. or 12 v. charging. Louvred steel case with stoved blue hammer finish. Fused and ready for 75/- use with mains and output leads. Carr. 4/6. Credit Terms: Deposit 30/- and 4 monthly payments. 13/-

R.S.C. MAINS TRANSFORMERS (FULLY GUARANTEED)

Interleaved and Impregnated. Primaries 200-230-250 v. 50 c/c's. Screened.
TOP SHROUDED DROP THROUGH
 250-0-250 v. 70 mA. 6.3 v. 2 a. 5 v. 2 a. 18/9
 330-0-330 v. 80 mA. 6.3 v. 2 a. 5 v. 2 a. 18/9
 250-0-250 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. 23/9
 300-0-300 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. 23/9
 350-0-350 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. 23/9
 350-0-350 v. 100 mA. 6.3 v. 4 v. 4 a. C.T. 0-4-5 v. 3 a. 23/9
 350-0-350 v. 150 mA. 6.3 v. 4 a. 5 v. 3 a. 23/9

FULLY SHROUDED UPRIGHT
 250-0-250 v. 60 mA. 6.3 v. 2 a. 5 v. 2 a. 17/6
 Midret type 1/3-3 in. 26/9
 250-0-250 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. 26/9
 for R1355 conversion ... 31/-
 300-0-300 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. 26/9
 350-0-350 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. 26/9
 300-0-300 v. 130 mA. 6.3 v. 4 a. 6.3 v. 1 a. for Mullard 510 Amplifier ... 35/9
 350-0-350 v. 150 mA. 6.3 v. 4 a. 5 v. 3 a. 33/9
 350-0-350 v. 150 mA. 6.3 v. 2 a. 6.3 v. 2 a. 5 v. 3 a. 35/9
 425-0-425 v. 200 mA. 6.3 v. 4 a. C.T. 6.3 v. 4 a. C.T. 5 v. 3 a. Suitable Williamson Amplifier, etc. 49/9

FILAMENT TRANSFORMERS
 All with 200-250 v. 50 c/c's. Primaries 6.3 v. 1.5 a. 5/9; 6.3 v. 2 a. 7/6; 0-4-6.3 v. 2 a. 7/9
 12 v. 1 a. 7/11; 6.3 v. 3 a. 8/11; 6.3 v. 6 a. 17/6; 12 v. 3 a. or 2 1/2 v. 1.5 a. 17/6.

FUNCTION TRANSISTORS.
 Brand new R.F. Type 17/6. A.F. 7/6.
VOLUME CONTROLS with long (1/4 in. diam.) spindle all values less switch, 2/9; with S.P. switch, 3/9; with D.P. switch, 4/6.

H.T. ELIMINATOR AND TRICKLE CHARGER KIT. Input 200-250 v. A.C. Output 120 v. 40 mA. Fully smoothed and rectified supply to charge 2v. accumulator. Price with louvred metal case and circuit, 23/6, or ready for use, 8/9 extra.

CHARGER TRANSFORMERS
 All with 200-230-250 v. 50 c/c's Primaries :
 0-9-15 v. 1 a. 11/9; 0-9-15 v. 3 a. 16/9;
 0-9-15 v. 4 a. 19/9; 0-9-15 v. 6 a. 23/9.

SMOOTHING CHOKES
 250 mA, 5 H 100 ohms ... 12/9
 150 mA, 7-10 H 250 ohms ... 11/9
 100 mA, 10 H 200 ohms ... 8/9
 80 mA, 10 H 350 ohms ... 5/9
 60 mA, 10 H 400 ohms ... 4 11

OUTPUT TRANSFORMERS
 Midret Battery Pentode 66:1 for 354, etc. 3/9
 Small Pentode, 5,000 Ω to 3 Ω ... 3/9
 Small Pentode 7/8,000 Ω to 3 Ω ... 3/9
 Standard Pentode, 5,000 Ω to 3 Ω ... 4/9
 Standard Pentode, 7/8,000 Ω to 3 Ω ... 4/9
 10,000 Ω to 3 Ω ... 4/9
 Push-Pull 10-12 watts 6V6 to 3 Ω or 15 Ω ... 15/9
 Push-Pull 10-12 watts to match 6V6 to 3-5-8 or 15 Ω ... 16/9
 Push-Pull EL84 to 3 Ω or 15 Ω ... 16/9
 Push-Pull 15-18 watts, 6L6, KT66 22/9
 Push-Pull 20 watts, sectionally wound 6L6, KT66, etc., to 3 or 15 Ω 47/9

MAINS TRANSFORMER
 Manufacturers' surplus. Primaries 200-250 v. 50 c/c's. 375-0-375 v. 150 mA. 6.3 v. 4 a. C.T. 6.3 v. 1 a. Fully shrouded, 22/9.
 325-0-325 v. 100 mA. 6.3 v. 2.5 a. 5 v. 2 a. Drop through type 18/9. Postage on either type 2/9.

EX-GOVT. SMOOTHING CHOKES
 250 mA, 20 H 200 ohms ... 19/9
 250 mA, 5 H 50 ohms ... 12/9
 150 mA, 10 H 100 ohms ... 11/9
 150 mA, 6-10 H 150 ohms Trop. ... 6/9
 120 mA, 12 H 100 ohms ... 9/9
 100 mA, 5 H 100 ohms ... 3 11

R.S.C. BATTERY TO MAINS CONVERSION UNITS

Type BM1. An all-dry battery eliminator. Size 5 1/2 x 4 1/2 x 2 1/2 in. approx. Completely replaces batteries supplying 1.4 v. and 90 v. where A.C. mains 200-250 v. 50 c/c's is available. Suitable for all battery operated receivers requiring 1.4 v. and 90 v. This includes latest low consumption types. Complete kit with diagrams, 39/9, or ready to use, 48/9.



Type BM2. Size 8 x 5 1/2 x 2 1/2 in. Supplies 120 v. 40 v. and 60 v., 40 mA. and 2 v. 0.4 a to 1 amp. and 2 v. Fully smoothed. Thereby completely replacing both H.T. batteries and I.T. 2 v. accumulators. When connected to A.C. mains supply 200-250 v. 50 c/c's. **SUITABLE FOR ALL BATTERY RECEIVERS**

VEIS normally using 2 v. accumulator. Complete kit of parts with diagrams and instructions, 48/9, or ready for use, 58/6.

MINIATURE MOTORS. 24/28 v. D.C. or A.C. made by Hoover Ltd., Canada. Size only 2 1/2 x 1 1/2 in. Spindle 1 1/2 in. long. 1 1/2 in. diam. Brand New 9/8.

HEADPHONES. Brand new. Low resistance. Only 6/9 pr.

EX-GOVT. 50 WATT SPEECH AMPLIFIERS. For normal 200-250 v. A.C. mains. Complete with hand 'mike' with good length of lead and all valves. Ready for use. In wood transit cases. Only 9 Gns., carr. 15/-.

TANNOY RE-ENTRANT 8 WATT SPEAKERS. For use with above, 27/6 ea.

EXTENSION SPEAKERS

Ready for use in walnut veneered cabinet.
 6in. 2-3 ohms. 29 11.
 8in. 2-3 ohms. 35/9.
 Very limited number.



EX-GOVT. METAL BLOCK (PAPER) CONDENSERS.
 4 mfd. 350 v., 2/9; 4 mfd. 1,000 v., 4/9;
 8 mfd. 500 v., 4/9; 10 mfd. 500 v., 3/9;

ELIMINATOR TRANSFORMERS
 Primaries 200-250 v. 50 c/c's.
 120 v. 40 mA. 5-0-5 v. 1 a. ... 15/9
 90 v. 15 mA. 4-0-4 v. 500 mA. ... 9/9

THE SKYFOUR T.R.F. RECEIVER.
 A design of a 3-valve Long and Medium wave 230-250 v. A.C. Mains receiver with selenium rectifier. It consists of a high gain H.F. stage and low distortion anode bend detector. Power pentode output is used. Valve line-up 6K7, SP61, 6V6G. Selectivity and quality are well up to standard, and simplicity of construction is a special feature. Point-to-point wiring diagrams, instructions and parts lists, 1/9. Maximum building costs 24/19/6, including attractive Brown or Cream Bakelite or Walnut veneered wood cabinet 12 x 6 1/2 x 5 1/2 in.

EX-GOVT. DOUBLE WOUND STEP DOWN TRANSFORMERS.
 10-0-100-200-220-240 v. to 0-7-5-115-135 v. or REVERSE. 80-100 watts. Only 12/9, plus 2/9 post. 10-0-100-200-220-240 v. to 0-4-10-12-136-148 v. or REVERSE. 200 watts. 35/8, plus 7/6 carr. Both 50 c.p.s.

EX-GOVT. MAINS TRANSFORMER.
 Primary 0-10-120-210-220-230-240-250 v. 50 c.p.s. Secs. 275-0-275 v. 100 mA. 6.3 v. 7 a. 5 v. 3 a. Govt. ratins. 22/9. Following with 230-250 v. primaries, 400-0-400 v. 200 mA. 5 v. 3 a. 5 v. 2 a. 10/9; 230-0-230 v. 100 mA. 12.6 v. 1.5 a. 5 v. 2 a. 11/9; 12.6 v. 3 a. 5 v. 3 a. 9/9. Postage 2/9 on any type.

EX-GOVT. CASES. Size 14-10-8 1/2 in. high. Well ventilated, black crackle finished, undrilled case. IDEAL FOR BATTERY CHARGER OR INSTRUMENT CASE, OR COVER COULD BE USED FOR AMPLIFIER. Only 9/9, plus 2/9 postage. Size 8 1/2 x 13 1/2 x 8 1/2 in. with undrilled well ventilated cover, finished in stoved grey enamel. Suitable for charger or instrument case, 7/9, plus 2/9 post.

EX-GOVT. VALVES (NEW)

1R5	7/9	6J5	5/9	ECC91	4/9
1T4	7/9	6J6	4/9	EF80	7/9
1S5	7/9	6V6G	7/9	EB91	4/9
354	7/9	6X4	6/9	EF91	8/9
5Y3G	8/9	6X5GT	8/9	EL32	3/9
5U4G	8/9	6L6G	11/9	KT44	8/9
5Z4G	9/9	807	7/9	KT61	9/9
6KT7	6/9	12A6	7/9	EZ90	6/9
6S17GT	6/9	15D2	4/9	EL84	10/6
6SL6GT	8/9	35ZACT	8/9	FW4/500	9/9
6SN7GT	8/9	MH4	4/9	SP61	2/9
6AT7	7/9	ECC63	8/9		

SPECIAL OFFERS: Electrolytics. 32-32 mfd. 250 v. Dublier small can, 2/9 ea. 150 mfd. 450 v., 3/9. Small .0005 mfd. 2-gang, 4/9 ea. Westinghouse Rectifiers 250 v. 250 mA. 7/9. 4-8-ANAL. CABLE, 75 ohm. 1 1/2 in. 8d. yd. Twin-Screened Feeder 11d. yd.

ELECTROLYTICS (current production) NOT EX-GOVT.


Tubular Types		Can Types	
8 μF 450 v. ...	1/9	16 mfd. 350 v. 111	
8 mfd. 500 v. ...	2/8	16 mfd. 500 v. 2/9	
16 μF 350 v. ...	2/3	16 μF 450 v. ...	2/9
16 μF 450 v. ...	2/9	32 μF 350 v. ...	2/11
16 μF 500 v. ...	3/9	32 mfd. 450 v. 4/9	
32 μF 350 v. ...	3/9	160 mfd. 450 v. 4/9	
25 μF 25 v. ...	1/3	8-8 μF 450 v. ...	2/9
50 μF 12 v. ...	1/3	8-16 μF 450 v. 3/11	
50 μF 25 v. ...	1/6	16-16 μF 450 v. 4/11	
50 μF 50 v. ...	1/9	32-32 μF 350 v. 4/9	
100 mfd. 12 v. ...	1/9	32-32 μF 450 v. 5/9	
100 mfd. 25 v. ...	2/3	100-100 mfd. 350 v. 5/9	
1,500 mfd. 6 v. 1/8		100-200 mfd. ...	8/9
3,000 mfd. 6 v. 3/9		275 v. ...	8/9

R.S.C. A8 ULTRA LINEAR 12 WATT AMPLIFIER

High-Fidelity Push-Pull Amplifier with Built-in Tone Control, Pre-amplifier Stages, High sensitivity, 12 diode valves (807 outputs), High Quality sectionally wound output transformer specially designed for Ultra Linear operation, and a reliable small condenser of German manufacture. **INDIVIDUAL CONTROLS FOR BASS AND TREBLE**, "Lift" and "Cut." Frequency response 3db. 30-30,000 c/s. Six negative feedback loops. Hum level 71 db. down. Only 70 millivolts INPU required for **FULL OUTPUT**. Suitable for use with all makes and types of pick-ups and practically all microphones. Comparable with the very best designs.

For **STANDARD OR LONG PLAYING RECORDS**. For **MUSICAL INSTRUMENTS** such as **STRING BASS, GUITARS, etc.** **BETTER SOUND** with plug noise at 300, 20 mA and 6.3 v. 1.5 A. For supply of a **RADIO FEEDER UNIT**. Size approx. 12-9/16 in. For A.C. mains 200-250 v. 50 c/s. Outputs for 3 and 15 ohm speakers. Kit is complete but just not. Chassis is fully punched. Full instructions and point-to-point wiring diagrams supplied. Unapproachable value at **£7 15/-** or factory built 45/- extra. Carriage 10/-.

£7-15-0

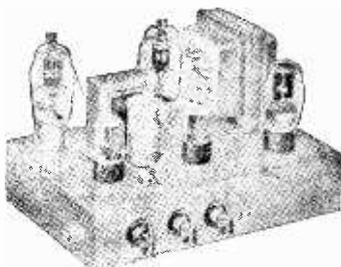

cutting handles can be supplied for 18/9. Additional input socket with associated Vol. control so that two different inputs such as Gram and 'Mike' or Tape and Radio can be mixed, can be provided for 13/- extra. Guaranteed 12 months. **TERMS** on assembled two input model: **DEPOSIT** 25/6 and nine monthly payments 25/6. **HIGH-FIDELITY MICROPHONES and SPEAKERS** in stock. Keep cash prices or Credit terms if supplied with amplifier.

COLLARO R54 3-SPEED AUTO-CHANGERS with Studio Pick-up Brand new. For 110 v. 50 c/s. A.C. mains. Price with 110 v. to 230-250 v. Auto Trans. only 7 Gns. Carr. 5/-.

COLLARO CONQUEST 4-SPEED AUTO-CHANGERS with large 60-110 Studio Pick-up. Latest model Brand new. Cartoned. For 200-250 v. 50 c/s. A.C. mains. Our price £9 19/3. Carr. 5/6. Credit Terms. Deposit 3 gns. and 6 monthly payments of 21/6.

COLLARO 4-SPEED SINGLE PLAYER with separate pick-up, as fitted to R54. For 200-250 v. A.C. mains. £4 12/6. Post 3/6.

LG3 MINIATURE 2-3 WATT GRAM AMPLIFIER. For use with above or any other single or auto-change units. Complete for 2-3 ohm speaker. For 200-250 v. 50 c/s. A.C. mains. Overall size 6 1/4 x 4 1/4 x 2 1/4 in. Controls: Vol. and Tone with switch. Guaranteed 12 months. Only 55/9.

SUPREME FEEDER UNIT Designed to a high quality Radio Tuner Unit especially suitable for use with any of our Amplifiers. Delayed A.V.C. employed. The W.C. Schw. incorporates Gram position. Controls are Tuning, W.C. and Vol. Only 250 v. 15 mA. H.T. and L.F. of 6.3 v. 1.5 A. and record from amplifier. Size of unit approx. 9-8/16 in. high. Simple alignment procedure. Point-to-point wiring diagrams, instruction and priced parts list with illustration. 2/6. Total building cost, £4 15/-. For descriptive leaflet send S.A.E.

LINEAR L45 MINIATURE 4.5 WATT QUALITY AMPLIFIER. Suitable for use with Collaro, B.S.R. or any other record-playing unit, and most microphones. Separate Red-back 12 db. separate Bass and Treble Controls. For A.C. mains input of 200-250 v. 50 c/s. Output for 2 ohm speaker. Three miniature Mullard valves used. Size of unit only 6-5/16 in. high. Output for 2 ohm speaker. Guaranteed for 12 months. Only £5 19/6. Send S.A.E. for illustrated leaflet. Credit Terms. Deposit 22/6 and 5 monthly payments of 22/6.

LINEAR "DIATONIC" 10-11 WATT HIGH FIDELITY PUSH-PULL ULTRA LINEAR AMPLIFIER. For 200-250 v. 50 c/s. A.C. mains. Valve line-up EC88, EC88, EL84, EL84, EL24, miniature Mullard. The unit has sectionally wound Pre-amplifier Tone Control stage and separate Bass and Treble Controls. Independent 'Mike' and Gram input sockets are provided. Size is only 7-5/16 in. high. Output for 3 and 15 ohm speakers. Only 12 GNS. or Deposit 20/9 plus 10/- carr. and 9 monthly payments of 26/9. Send S.A.E. for leaflet.

R.S.C. 45 WATT A5 HIGH-GAIN AMPLIFIER

A highly sensitive 4-valve quality amplifier for the home, small club, etc. Only 50 millivolts input is required for full output so that it is suitable for use with the latest high-fidelity pick-up heads, in addition to all other types of pick-ups and practically all 'mikes'. Separate Bass and Treble Controls are provided. These give full long-playing record equalisation. Hum level is negligible being 71 db. down. 15 db. of negative feedback is used. H.T. of 300 v. 25 mA. and L.F. of 6.3 v. 1.5 A. is available for the supply of Radio Feeder Unit or Tape Deck pre-amplifier. For A.C. mains input of 200-230-250 v. 50 c/s. Output for 2-3 ohm speaker. Chassis is not alive. Kit is complete in every detail and includes fully punched chassis (with baseplate) with Blue hammer finish and point-to-point wiring diagrams and instructions. Exceptional value at only £4 15/-, or assembled ready for use 25/- extra, plus 3/6 carr. or Deposit 22/6 and 5 monthly payments of 22/6 for assembled unit.



LINEAR LT45 HIGH QUALITY TAPE DECK AMPLIFIER. With "built in" power pack and output transformer. Ready for use with Tape Decks with High or Low Impedance. Playback and Erase Heads, such as Iano, Truvox, Aspen, Collaro, Carr. 7/6. Bremel, etc. For A.C. Mains 230-250 v. 50 c/s. Linear frequency response of 3 db. 50-11,000 c/s. Negative feedback equalisation. Illustrated leaflet 6d.

12 GNS.

SENSATIONAL OFFER STARR GALAXY 4 SPEED MIXER AC 10-4 CHANGER. A precision manufactured unit with a motor which virtually eliminates "wow" and rumble. Playing Desk size 11 1/2 x 10 1/2 in. Depth below on-board 2 in. Above 5 in. Fitted pick-up with dual sapphire tipped stylus. For 230-250 v. A.C. mains. **£3-19-6** opportunity. Only Brand new cartoned. Carr. 3/0

Terms: C.W.O. or C.O.D. NO C.O.D. under £1. Post 1/9 extra under £2; 2/9 extra under £5. All goods supplied subject to terms and guarantee as detailed in current catalogue. Open 9 to 5.30; Sats. until 1 p.m. Catalogue 61. Trade list 54. S.A.E. with all enquiries.

R.S.C. 30 WATT ULTRA LINEAR HIGH-FIDELITY AMPLIFIER A10

A highly sensitive Push-Pull high output unit with self-contained Pre-amp, Tone Control Stages. Certified performance figures compare equally with most expensive amplifiers available. Hum level 70 db. down. Frequency response - 3 db. 30-30,000 c/s. A specially designed sectionally wound ultra linear output transformer is used with 807 output valves. All components are chosen for reliability. Six valves are used, EF86, EF86, EC88, 807, 807, GZ33. Separate Bass and Treble Controls are provided. Minimum input required for full output is only 12 millivolts so that **ANY KIND OF MICROPHONE OR PICK-UP IS SUITABLE**. The unit is designed for **CLUBS, SCHOOLS, THEATRES, DANCE HALLS or OUTDOOR FUNCTIONS**, etc. For use with Electronic ORGAN, GUITAR, STRING BASS, etc. For standard or long-playing records. **OUTPUT SOCKET PROVIDED** L.T. and H.T. for a **RADIO FEEDER UNIT** control is provided so that two separate inputs such as Gram and 'Mike' can be mixed. Amplifier operates on 200-250 v. 50 c/s. A.C. Mains and has outputs for 3 and 15 ohm speakers. Complete kit of parts with fully punched chassis and point-to-point wiring diagrams and instructions. It required cover as for Carr. 10/-.

£10-19-6

A8 can be supplied for 18/9. The amplifier can be supplied, factory built with 12 months' guarantee, for £13.13.0. **TERMS: DEPOSIT** 36/- and 9 monthly payments of 31/-.


R.C.A. 20 WATT RE-ENTRANT SPEAKERS, 15 ohms or 600 ohms matching. For Outdoor work. Only 3 GNS. P.M. SPEAKERS. All 2-3 ohms, suitable for use with LG3, L45, A5 or A7 amplifiers. 5in. Goodmans, 7/9. 7 x 4 in. Elliptical Elac, 19/9. 6in. Goodmans, 17/9. 8 in. Rola, 19/9. 10in. R.A., 27/9. 10 x 6in. Elliptical Goodmans, 29/9. 12in. Plessey, 29/11. 10in. W.B. Selenorian '3 15 ohm type HF12 10 watts, hi-fidelity type. Recommended for use with our A8 Amplifier. £4/10/9. 12in. Plessey 3 ohms 10 watts. (12,000 lines) 59/6.

PLESSEY DUAL CENTRIC 12in. 15 ohm HIGH FIDELITY SPEAKER (12,000 lines) with built-in tweeter (completely separate elliptical speaker with choke, condensers, etc.) providing extraordinarily realistic reproduction when used with our A8 or similar amplifier. Rated 10 watts. Price complete, only 55/17/6.

M.E. SPEAKERS 2-3 ohms, 8in. R.A. Field, 600 ohms 11/9.

R.S.C. 3-4 WATT A7 HIGH-GAIN AMPLIFIER

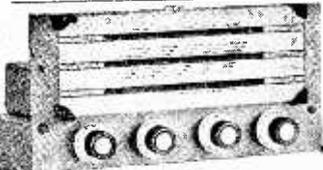For 230-250 v. 50 c/s. Mains input. Appearance and Specification, with exception of output wattage, as A5. Complete kit with diagrams. £3 15/- Assembled 22/6 extra. Carr. 3/6.



AM/FM RADIOGRAM CHASSIS HIGH QUALITY 6-8 WATT PUSH-PULL OUTPUT

For 200-250 v. Mains. Long wave, Medium, P.M. and Gram. Complete with 8 B.V.A. valves. Guaranteed 12 months. Only 22 GNS. Or Deposit £2 12/- and 9 monthly payments of £2 12/-.


(LEEDS) LTD., MAUDE ST., (opp. Parish Ch. School) LEEDS, 2

RADIO SUPPLY CO.

 "Q Coils" Iron dust cores 4/- Amazing efficiency	 Potted 5/- Coils Superhet, T.R.F. modern technique	Coils for Collaro Tape Officially recommended Transcripator pre-amp. O.S.C. 7/6	STATION SEPARATOR —A positive answer HOME, THIRD, LIGHT, Etc. 10/6	STOP! T.V. Patterning SIMPLE REMEDY 10/-
SCRATCH FILTER COIL 6/9 Whistle Filter 10/-	DUAL RANGE COILS T.R.F. S'HET } 7/6 ea.	OSMOR Mini-Magic F.M. Tuner Kit Complete £4-10-0	B.B.C. 1 VALVER Components 27/6 (Valve 10/- ex. including diagrams)	Also B.B.C. (T.V.) Filter Choke 7/6
FERRITE ROD AERIALS MW 8/9 M-L 12/9	I.T.A. Converter To fit inside T.V. FOR ALL SETS KIT Complete 65/- Very efficient! £4	Dial 24/6 complete ASSEMBLY	The World on a 1 Valve Short Waver Coil & Circuit 6/-	Experimental & Development Dept.
Special Coils for HAMS DESIGNERS MANUFACTURERS	OSMOR Satellite Switch-tuned F.M. Dimensions 4 1/2" x 4 1/2" A completely stable drift-free unit for adding to existing radio or Hi-Fi amplifier. Circuit & wiring diagram on request.		F.M. COILS For Osmor C'ts & Many Designs	

Thank "Q" FREE! Send 1/- (stamps) for fully descriptive literature AND OSMOR DESIGNS—5-Valve S'Het, Miniature ditto, Battery and Battery/Main Receiver, Mains T.R.F. S'Het and T.R.F. Feeders, Band 3 Converters, F.M. Tuners, Wiring Diagrams, Chassis Templates, Coil and Coilpack information and price lists and information on circuits in "Wireless World," "Practical Wireless," "Radio Constructor." Full Circuits included. See also classified Advs. on page 240.

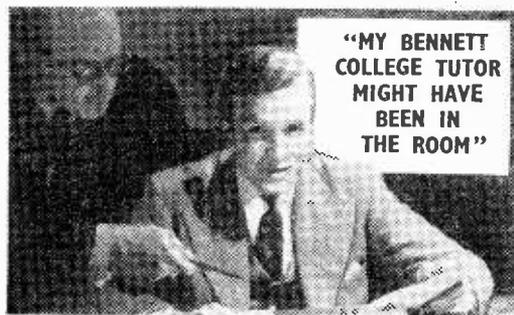OSMOR (Dept. P.W. 22) **418 BRIGHTON ROAD SOUTH CROYDON, SURREY**
CROYdon 5148/9



"MY BENNETT COLLEGE TUTOR MIGHT HAVE BEEN IN THE ROOM"

PERSONAL POSTAL TUITION

WHAT CAREER DO YOU WANT?

Architecture	Telecommunications
Building	Television
Carpentry	Wireless Telegraphy and Telephony
Commercial Art	
Diesel Engines	
Draughtsmanship	Book-keeping
Electric Wiring	English
Forestry	Geography
Locomotive Eng.	Journalism
Mechanical Eng.	Languages
Motor Engineering	Mathematics
Plumbing	Modern Business Methods
Quantity Surveying	Police Subjects
Radio Engineering	Salesmanship
Sanitary Science	Short Story Writing
Surveying	and many others

Every Bennett College student enjoys this friendly, intimate coaching right through his Course. A few of the Courses are listed opposite. Tell us your subject. We will send you The Bennett College Prospectus and the famous FREE book "Train your mind to SUCCESS." This will show you how you can advance to a better, finer future by Personal Postal Tuition. Fill in and post the coupon today.



Please send me the Prospectus on..... and my free copy of "Train your mind to SUCCESS."

NAME

ADDRESS

TOWN

☐ (if under 21) Please write in BLOCK letters

EXPRESS ELECTRONICS
ROSEDENE LABORATORIES
KINGSDOWN WAY, SELSDON, SURREY

VALVES NEW, TESTED AND GUARANTEED

IAC6	8/6	6BR7	10/6	12A7	8/6	EB91	6/9	KT66	11/-
IC1	7/6	6BW6	7/6	12AU7	7/6	EBCA1	10/-	IN17	7/6
IC2	8/6	6BW7	8/-	12AX7	8/-	EBF80	9/6	IN18	7/6
IC3	9/-	6CH6	7/-	12K7GT	8/-	ECC35	7/6	IN9	7/6
IF1	8/6	6C10	9/-	12K8GT	12/6	ECC81	8/6	PCC84	9/-
IF3	7/6	6D1	1/6	12Q7GT	8/-	ECC82	7/6	PCF80	10/6
IFD1	8/6	6D2	6/9	16A5	9/-	ECC83	8/6	PCF82	10/6
IFD9	7/6	6F12	6/-	25L6GT	8/6	ECC84	10/6	PL82	9/-
IP1	9/-	6F15	9/-	25Z4G	8/6	ECC80	10/6	PY81	8/6
IP10	7/6	6J5G	5/6	35L6GT	9/-	ECH82	10/6	PZ30	7/6
IP11	7/6	6J5GT	6/6	35W4	8/6	ECH41	10/-	US2	8/-
IRS	7/6	6K7G	5/6	35Z4GT	8/6	ECH81	8/-	U76	7/-
IT4	7/6	6K8GT	9/6	5763	10/6	EF37A	9/-	U78	7/6
IS5	7/6	6L6G	10/6	D77	6/9	EF39	5/-	UBC41	8/6
IUS	7/-	6Q7GT	8/6	DAF91	7/6	EF91	9/-	UCH42	10/-
3Q4	7/6	6SA7	8/-	DF91	7/6	EF80	8/6	UF41	8/6
354	7/6	6SL7GT	7/6	DF96	8/6	EF91	6/-	UL41	10/-
3V4	7/6	6SN7GT	8/-	DH76	8/-	EF92	5/6	UY41	7/6
SU4G	8/6	6V6G	7/6	DH77	7/6	EL37	19/6	W76	8/-
SY4G	7/-	6V6GT	7/6	DH142	8/6	EL38	20/-	W142	8/6
5Z4G	9/6	6X4	7/-	DH150	10/-	EL41	10/-	X17	7/6
6AL5	6/9	6X5GT	7/6	DK91	7/6	EY51	12/6	X18	8/6
6AM6	6/-	1757	8/6	DK92	8/6	EZ35	7/6	X142	8/6
6AT6	7/6	8D3	6/-	DK96	9/-	EZ40	8/-	X150	10/-
6BA6	7/6	12AH9	10/6	EA50	1/6	EZ80	8/-	Z77	6/-
6BE6	8/-	12AT6	8/6	EABC80	8/6	KT33C	8/6	ZD17	7/6

MATCHED PAIRS
ELB4 23/-, 6V6G and GT 17/-, 6BW6 18/- per pair.
Push Pull O.P. Transformers for above 3-15 ohm 14/6.

SETS OF VALVES

DK91, DF91, DAF91, DL92 or DL94.....	27/6
IRS, IT4, IS5, 354 or 3V4.....	27/6
6K8, 6K7, 6Q7, 6V6, 5Z4G.....	35/-
12K8, 12K7, 12Q7, 35L6, 35Z4.....	35/-

Postage and packing, 6d. Over £1 post free. C.O.D. 2/6.

Post this coupon NOW!

PREMIER RADIO COMPANY

Tel.: AMBassador 4033

B. H. MORRIS & CO. (RADIO) LTD.

Tel.: MUS. 3451

207 EDGWARE RD., LONDON, W.2 & 23 TOTTENHAM COURT RD., LONDON, W.1



The "Petite" PORTABLE

A completely new design with the all star feature from the firm with many years of experience in the supply of designs for the home constructor.

MAY BE BUILT FOR

£7.7.0

Plus p. & p. 3.-

Batteries Extra. H.T. 10- (type B126) or equivalent, I.T. 1.6 (type AD35) or equivalent.

★ Size only 8in. x 8in. x 4in. ★ Instruction Book 16 PAGES UNIT NOW AVAILABLE FOR ONLY 37.6 plus 2.- p.p.

THE NEW MERCURY SWITCHED F.M. TUNER

by Jason

Complete set of parts available with built and tested front end.

Price **£9.19.6** plus 2/6 pkg. & carr.

Lower Pack requirements 35 ma.


The NEW De - Luxe TAPE RECORDER TR3



for **£6.5.0** DEPOSIT & 8 MONTHLY PAYMENTS OF **£5.17.11** OR CASH **45 GNS.** plus 21/- post & pkg.

TRADE ENQUIRIES WELCOMED

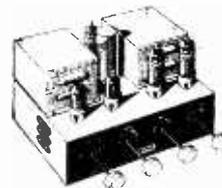Case finished in Red and Cream with gilt styling and fittings. Size 18in. x 15in. x 9in. for A.C. Mains 200.250 v. 50 cycles



BUILD THE 1-VALVE BATTERY RECEIVER

As shown on B.B.C. T.V. This receiver contains a DA36 valve and a pair of 4,000 ohm headphones, and is powered by a combined 674 and 1 1/2 volt battery. Price complete with headphones but less battery 45.-. Send for free diagram.


2-Volt 18Ah alkaline-cased ACCUMULATOR by Oldham, Dagenite, Exide. New and unused, unspillable. 7 1/4 x 4 x 2. Price 6.6, plus 1/6 p. & p.

SAVE POUNDS AND PUT IT TOGETHER YOURSELF!

Cabinet **£2.19.6**, plus 5.- pka. and post. Premier 1 valve Gram. Amplifier **£2.19.6**, plus 2.6 pkg. and post.

Premier 2 Valve Printed Circuit Amplifier **£3.5.6**, plus 2/6 pka. and post. 8in. x 6in. Speaker **27.6**, plus 1/6 pka. and post.

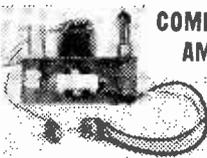Collaro 4-Speed Changer **£8.19.6**, plus 7.- pkg. and post. If a set of parts is purchased together pkg. and post will be 10.-.



COMPACT GRAM AMPLIFIER

Complete ready to connect to any type of Pick-up and Speaker (3 ohms, A.C. Mains 200V)

250 v. Volume and tone control on 8' extended leads. 1 valve. Overall size 7" long x 6" wide x 3 1/2" high.

Plus packing and postage 2/6. **£2.19.6**

 Visit our New
HI-FI SHOWROOM
 at
23 TOTTENHAM COURT RD.
 The best HI-FI Showroom
 in the district
 (2 minutes from Tottenham Court Road Underground Station)
 Tel.: MUS. 3451

WRITE FOR DETAILS OF PREMIER TAPE RECORDER KIT FOR ONLY **£38.15.0**.

4-WATT AMPLIFIER

MAY BE BUILT FOR **£4.10.0** Plus 2/6 Pkg. & Carr.

Instruction Book 1.- post free.

A steel case is now available, complete with engraved panel, for 15.6 extra. The amplifier may be supplied complete for **£5.5.0** plus pkg. and post 3/6, or fitted in case at **£6** plus pkg. and post 3/6.

2-BAND T.R.F. RECEIVER

MAY BE BUILT FOR **£5.15.0** Plus 3.- Pkg. & Post.

3-Band Superhet Receiver may be built for **£7.19.6** plus pkg. & carr. 3.-. These two receivers use the latest type circuitry and are fitted into attractive cabinets 12in. x 6in. x 6in. in either walnut or ivory bakelite or wood. Individual instruction books 1.- each. Post free.

8 WATT AMPLIFIER

This design includes 5 miniature valves of the latest types, an ultralinear output transformer suitable for Speakers of 3 and 15 ohms and a very attractive perspex front panel with gold lettering, complete set of parts.

Postage & packing 5.- extra. **£8.8.0** or **£10.19.6** built and tested. Send 1/6 for Booklet.

B.S.R. T.U.S 3-speed Record Player **£3.19.6** plus 2.6 post and packing. P.C. complete with arm, 36.-.

THE LATEST COLLARO 4-SPEED SINGLE PLAYER UNIT COMPLETE WITH PICK-UP AND TURNOVER CARTRIDGE **£4.12.6**, PLUS 2/6 PKG. & CARR.

Why not make the best! MULLARD AMPLIFIER KIT

Now supplied with ultralinear output transformer.

All the components for Model 510, plus pre-amplifier, on one chassis (total six valves), chassis gold hammer finished. May be purchased for **£12.12.0** plus pkg. and post 7.6. This version complete and tested **£15.15.0**. Or pre-amplifier and tone control in a separate unit **£14.14.0**, plus pkg. and post 7.6.

ADDRESS ALL MAIL ORDER ENQUIRIES TO: (Dept. P.W.) 207 EDGWARE RD., LONDON, W.2

AND NOW THERE ARE TWO

Stern's "fidelity"
TAPE RECORDERS



PRICE . . . Including CRYSTAL MIKE and 1,200ft. reel of PLASTIC TAPE. **£49.10.0** OR £3 EXTRA WITH REV. COUNTER.

CREDIT SALE: Deposit £12.8/- and 9 monthly payments of £4/10 8.
HIRE PURCHASE: Deposit £24/15 - and 12 monthly payments of £2/5 11

(Plus £1/10 - carriage and insurance of which

IT INCORPORATES: The NEW TRUVOX MK. IV TAPE DECK together with the "fidelity" MODEL HF/TR2 TAPE AMPLIFIER (both fully described on this page), and a Rola 10in. x 6in. P.M. Speaker.



PRICE . . . Including CRYSTAL MIKE and 1,200ft. reel of PLASTIC TAPE. **39 GNS.**

CREDIT SALE: Deposit £10.5/- and 9 monthly payments of £3/15.2.
HIRE PURCHASE: Deposit £20/10/- and 12 monthly payments of £1/18.-.

£1 is refunded on return of Packing Case.)

IT INCORPORATES: THE TRUVOX MK. III TAPE DECK together with correctly matched HF/TR1 TAPE AMPLIFIER and a 7in. x 4in. Speaker.


BEFORE CHOOSING YOUR TAPE RECORDER YOU SHOULD HEAR THESE MODELS—TRULY "HI-FI" RECORDINGS ARE OBTAINABLE. Alternatively send S.A.E. for ILLUSTRATED LEAFLET.

NEW TRUVOX Mk. IV TAPE DECK


ONE OF THE BEST DECKS ON THE MARKET. (Plus 10/- carriage and ins.) **£27.6.0.**

CREDIT TERMS: Deposit £8/17 - and 9 monthly payments of £2/10.-
H.P. TERMS: Deposit £13/13 - and 12 monthly payments of £1.5.4.

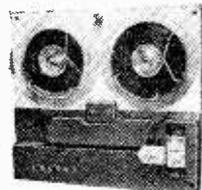WE ALSO HAVE A FEW DECKS WITH REV. COUNTERS. Price £30.9.-. Send S.A.E. for details.



A TAPE PRE-AMPLIFIER and ERASE UNIT

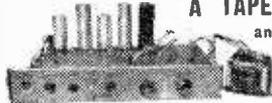

STERN'S MODEL HF/TR1 - A completely assembled Pre-amplifier with own Power Supply. Can be supplied correctly matched for use with Truvox or Collaro Decks and incorporates Recording Level Indicator and Monitoring facilities. Please send S.A.E. with any enquiry. **PRICE £11.10.0.** (Plus 5/- carriage and ins.)


RECORD PLAYERS

THE VERY LATEST MODELS ARE IN STOCK **MANY AT REDUCED PRICES!!!**
TRANSCRIPTION UNITS - AUTO-CHANGERS. SINGLE RECORD PLAYERS

Send S.A.E. for ILLUSTRATED STOCK LIST


SPECIAL CASH OFFERS!!

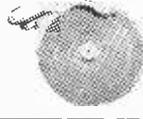The Latest Collaro 4 Speed Single Record Player. Incorporating the very popular STUDIO "O" CRYSTAL PICK-UP. For only **£6.19.6.**



(Plus 5/- carriage and ins.). Incorporates Auto-Stop and Plays 78 r.p.m. and all types of L.P. Records.

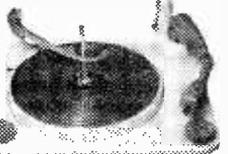THIS LATEST BRAND NEW B.S.R. MONARCH 4-SPEED AUTOCHANGER **£7.19.6.**



(Plus 5/- carriage and ins.)
• Minimum base-board size required 14in. x 12in. with height above 5 1/2in., & height below baseboard 2 1/2in.

WE ALSO HAVE A FEW ONLY

COLLARO 4-Speed "Mixer" Auto-changers. The Units are BRAND NEW and incorporate the STUDIO "O" Pick-up. **PRICE £8.15.0.** (Plus 5/- carriage and ins.)

WE HAVE THE FULL RANGE OF DULCI CHASSIS IN STOCK. Send S.A.E. for Leaflets.

"fidelity" TAPE AMPLIFIER HF/TR2 With POWER SUPPLY UNIT £16.0.0.

H.P. TERMS: Deposit £8 and 9 months of £1.
CREDIT TERMS: Deposit £4 and 9 monthly payments of £1.9.4. When ordering, please advise make of deck in use. Send S.A.E. for full details.



HOME CONSTRUCTORS

We can supply a COMPLETE KIT OF PARTS to build this TAPE AMPLIFIER for £12 (plus 5/- carriage and ins.). The Assembly Manual, Practical Diagrams, etc., are available for 2/6.


WE MAKE SPECIAL PRICES TO PURCHASERS OF TAPE EQUIPMENT (i.e. buyers of Deck and Amplifier together, etc., etc.). SEND YOUR ENQUIRY TO US . . . H.P. and CREDIT TERMS ARE AVAILABLE.

MODERNISE YOUR OLD RADIOGRAM

The NEW ARMSTRONG PB. 409 A.M./F.M. Radiogram Chassis

A VERY HIGH QUALITY CHASSIS EMPLOYING 9 LATEST B.V.A. VALVES. **£29.8.0.**

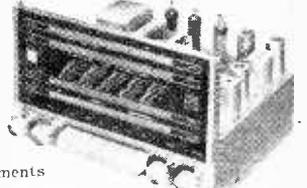Credit terms £7.7.0 and 9 monthly payments of £2.14.0. (Plus 6/- carriage & ins.)
H.P. £14.14.0 and 12 monthly payments of £1.7.3.
SEND S.A.E. FOR ILLUSTRATED LEAFLET.



"FRUSTRATED EXPORT ORDER"

The Corsor Model 527, X 4-Valve "A" Dry " Battery Portable. Offered **£6.15.0.** Plus 5/- carriage & Ins.


Consists of a 4-valve Superhet Receiver covering Medium Waveband 197-575 metres, and two Short Wavebands 13.6 to 136 metres. The new low consumption valves are incorporated and the whole is accommodated in an attractive robustly made case. Battery required is 90 volts and 1.4 volts (price 19/6) and is external to case.



STERN'S "F.M." TUNING UNIT

A 5-valve Tuner incorporating the latest Mullard Permeability Tuning Heart and a "Magic Eye" Tuning Indicator.

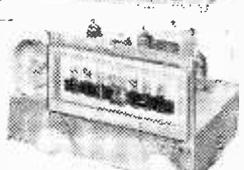PRICE ASSEMBLED £14.10.0.
READY FOR USE (Plus 7/6 carriage and insurance.)
TERMS: (a) Hire Purchase: Deposit £7.5.0 and 9 monthly payments of 18.4.
(b) Credit: Deposit £3.12.6 and 9 monthly payments of £1.8.7.



HOME CONSTRUCTORS


-You can build this unit for **£10.10.0.** Full Assembly Instructions are available for 1/6.

STERN RADIO

LIMITED (Dept. P.W.)
PLEASE SEND S.A.E. WITH ALL

1958 NEW LOOK MULLARD DESIGNS FOR THE "Hi-Fi" ENTHUSIAST

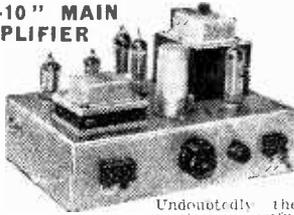The VERY POPULAR MULLARD "5-10" MAIN AMPLIFIER



Undoubtedly the most successful amplifier yet designed, and used in conjunction with the new Mullard Pre-Amplifier, an undistorted power output of up to 10 watts is obtained. Thoroughly recommended to the "Hi-Fi" enthusiast who contemplates a very high quality home installation. In addition the versatility of the equipment makes it quite suitable for use in small halls, etc. We supply complete to MULLARD'S Specification with specified valves and components and including the latest PARMKO Ultra-linear Output Transformer. Has power available to drive Radio Tuning Unit. **COMPLETE KIT OF PARTS £10.00** Alternatively, we supply **ASSEMBLED and TESTED (Carriage & Insurance 5/- extra.) £11.10.0** This "5-10" with the latest PARTRIDGE ULTRA-LINEAR OUTPUT TRANSFORMER for **£16.0 extra**

Please enclose S.A.E. if ILLUSTRATED and alternatively, the COMPLETE ASSEMBLY MANUALS and Practical Drawings, etc., are available at 1/6 each.

SPECIAL PRICE REDUCTIONS . . .

- (a) The COMPLETE KIT OF PARTS to build both the "3-3" MAIN AMPLIFIER and the 2-STAGE PRE-AMPLIFIER-CONTROL UNIT **£12.10.0**
- (b) The COMPLETE KIT OF PARTS to build both the "5-10" MAIN AMPLIFIER and the 2-STAGE PRE-AMPLIFIER-CONTROL UNIT **£15.15.0**

PRICES FOR THE "5-10" ARE SUBJECT TO £16.0 EXTRA IF THE PARTRIDGE TRANSFORMER IS REQUIRED.

THE NEW COMPLETE MULLARD "5-10" AMPLIFIER

ANOTHER NEW DESIGN, ILLUSTRATION NOT AVAILABLE AT TIME OF GOING TO PRESS.

This Amplifier is similar to the "5-10" illustrated above, but it has ALL CONTROLS incorporated on the Amplifier Chassis in the same way as the "3-3" (illustrated alongside), finished with our attractive PERSPEX FRONT PANEL, thus forming a complete Amplifier. We supply it complete to the MULLARD'S SPECIFICATION including specified Valves and components and incorporating the latest PARMKO ULTRA-LINEAR OUTPUT TRANSFORMER and switched inputs for 78 and L.P. Records, plus a Radio Tuning Unit. Extra power is available to drive the Tuning Unit.

Separate BASS and TREBLE CONTROLS provide excellent range of tone and we recommend the Amplifier to those with limited Cabinet spaces who require GENUINE HIGH QUALITY, at a higher volume level than the "3-3" but without the versatility of the separate Pre-Amplifier-CONTROL Unit. Main Amplifier. COMPLETE KIT OF PARTS, **£11.0.0** Alternatively, we supply **ASSEMBLED AND TESTED Credit Sale, Deposit £3.7.6 and 9 Monthly Payments of £1.4.11. H.P. Terms, Deposit £6.15.0 and 8 Monthly Payments of 19.3.** Send S.A.E. for ILLUSTRATED LEAFLET or alternatively, the COMPLETE ASSEMBLY MANUAL for 1/6.

109 & 115 FLEET ST., LONDON, E.C.4.
Telephone: FL Eet 5312 3/4
CORRESPONDENCE


MULLARD'S NEW 2-STAGE PRE-AMPLIFIER - TONE CONTROL UNIT



A completely new design employing two E86 valves, and in particular designed to correctly operate with the Mullard range of Power Amplifiers. Briefly it incorporates:
 ● Equalisation for the latest R.I.A.A. characteristics.
 ● Input for variable resistance.
 ● Magnetic Pick-Ups.
 ● Input for Crystal Pick-Ups.
 ● Input for Tape replay.
 (a) Direct from High Impedance Tape Head.
 (b) From a Tape Amplifier or Pre-Amplifier.
 ● Sensitive Microphone Channel.
 ● Wide range Bass and TREBLE Controls.
 ● Attractive Perspex front control panel.
 ● Our Kit is strictly to MULLARD'S SPECIFICATION. **COMPLETE KIT OF PARTS £6.0.0** Alternatively, we supply **ASSEMBLED and TESTED (Carriage & Insurance 5/- extra.) £8.0.0**

DESCRIPTIVE LEAFLETS are required; MANUALS, containing component Price Lists and Practical Drawings, etc., are available at 1/6 each.

THE NEW COMPLETE MULLARD "3-3"

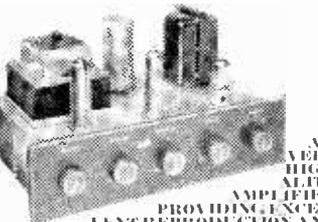


A VERY HIGH QUALITY AMPLIFIER PROVIDING EXCELLENT REPRODUCTION AND HAVING AN ATTRACTIVE PERSPEX FRONT PANEL. **COMPLETE KIT OF PARTS £7.10.0** (plus 6/6 coverage and insurance). Alternatively supplied **ASSEMBLED AND FULLY TESTED: £8.19.6** (plus 6/6 coverage and insurance).

The complete specification is available for 1/6. Developed from the very popular 3-valve 3-watt Amplifier designed in the Mullard Laboratories. Our kit is complete to MULLARD'S SPECIFICATION including supply of specified components, valves and a PARMKO OUTPUT TRANSFORMER. We also include switched inputs for 78 and L.P. records, plus a radio position. Extra power to drive a Radio Tuning Unit is also available.

THE IDEAL AMPLIFIER FOR A SMALL HIGH QUALITY INSTALLATION

WE ALSO SUPPLY SEPARATELY:
 (a) The 2-Stage (plus Rectifier) AMPLIFIER **£4.2.6**
 (b) THE PORTABLE CARRYING CASE **£3.17.6**
 (c) P.M. SPEAKER **18 9**
 Carriage and Insurance 4/- extra.
 We also have a smaller PORTABLE Case Ideal for Record Players. PRICE ONLY **£3.3.0** (plus 3/- carr. & ins.).

THE NEW MULLARD "3-3" MAIN AMPLIFIER

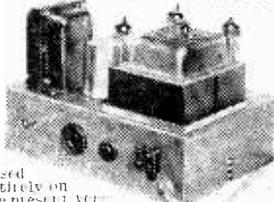

Based entirely on the best of the popular "3-3" model and designed to operate in conjunction with the new 2-stage PRE-AMPLIFIER (shown left); thus providing all the facilities associated with the more expensive "Hi-Fi" Equipment. We recommend it as the IDEAL HOME INSTALLATION where very high quality is desired at the lower volume level (up to 3 watts). We supply complete to MULLARD'S SPECIFICATION including the latest PARMKO Output Transformer, specified Valves and Components. Has power available to drive a Radio Tuning Unit. **COMPLETE KIT OF PARTS £7.0.0** Alternatively, we supply **ASSEMBLED and TESTED (Carriage & Insurance 5/- extra.) £8.0.0**


NOTE WE DO NOT USE SURPLUS OR CHEAP COMPONENTS IN ANY OF OUR MULLARD KITS OF ASSEMBLED UNITS.

HIGH QUALITY OF THIS NATURE HAS NEVER BEFORE BEEN OFFERED AT SUCH LOW COST.

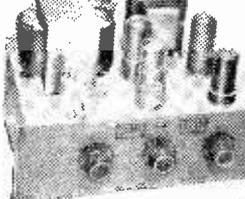- (a) The "3-3" and the 2-STAGE PRE-AMPLIFIER both ASSEMBLED and TESTED **£15.0.0**
 CREDIT: DEPOSIT £3.15.0 & 9 Monthly Payments of £1.7.6
 H.P.: DEPOSIT £7.10.0 & 9 Monthly Payments of 19/-
- (b) The "5-10" and the 2-STAGE PRE-AMPLIFIER both ASSEMBLED and TESTED **£18.18.0**
 CREDIT: DEPOSIT £4.15.0 & 9 Monthly Payments of £1.14.7
 H.P.: DEPOSIT £9.5.0 & 12 Monthly Payments of 17/6.

When ordering include an extra 7/6 to cover Carriage and Insurance

STERN'S "HIGH QUALITY" 8-10 WATT AMPLIFIER



Has power supply for Radio Tuning Unit. **COMPLETE KIT OF PARTS (plus 5/- carr. & ins.) £7.10.0** SUPPLIED, ASSEMBLED and READY FOR USE **£9.10.0**

Proved one of the most popular models offered to the HOME CONSTRUCTOR. Provides excellent reproduction up to 8 watts, employing 6V6s in push-pull, incorporating negative feedback. Provides use of both 3 and 15 ohm speakers.

SPECIAL CASH ONLY OFFER !!

This very attractive PORTABLE AMPLIFIER CASE, together with a good quality GRAM AMPLIFIER and a matched P.M. SPEAKER ALL for ONLY **£8.7.6** (plus 7/6 carr. & ins.).



The Amplifier consists of a 2-Stage design incorporating 3 modern B.V.A. valves and has separate BASS and TREBLE CONTROLS. The Portable Case will also accommodate almost any make of Auto-changer, and is attractively finished in Maroon and Grey Reflex.

EXCLUSIVE OFFER OF THE R. 107

THE ARMY'S FINEST COMMUNICATIONS RECEIVER

Just purchased from the Ministry of Supply, this magnificent 9 valve 3 Wave-band receiver gives World Wide Reception over a coverage of 1.2-17.0 Mc/s (18-25 metres), taking in several important Amateur Bands, Shipping Band, and part of the Medium Wave Band, including the B.B.C. Light Programme, sensitivity is 1 micro-volt on CW, and 2-6 micro-volts on RT. The controls include a Bandwidth Switch ("Wide" or "Narrow"), choice of A.V.C. and B.F.O., Audio Filter, R.F. Gain, Aerial Trimmer. Has built-in Output Stage with Internal Speaker, which can be switched out to use Headphones. Uses normal international Octal Valves. Incorporates A.C. Mains Power Unit for 100-250 volts, and Vibrator Pack for 12 volts D.C. In Grey Metal Case size 24" x 13" x 17". These sets are used, but in very good condition, thoroughly checked and aerial tested before despatch.

COMPLETE, READY TO SWITCH ON

£8-19-6

(Carriage 2/- England and Wales, rest of U.K. extra)

S.A.E. for Illustrated Leaflet.

COLLINS TCS TRANSMITTERS. Special offer of these famous American Transmitters. Frequency Range 1.5-12.0 Mc/s in 3 bands. Employs 7 valves. 2 of 1625 in P.A. Stage, 1625 buffer and 1625 modulator stage, 3 of 12A6 in Oscillator stage. Radio Telephone or Radio Telegraph. Provision for VFO or Crystal Control 4 Crystal positions. Has Plate and Aerial Current meters. IN BRAND NEW CONDITION. ONLY £12.10.0 (carriage, etc., 15/-).

COMMUNICATIONS RECEIVER R.1155.—The famous Bomber Command Set Covers 18.5-7.5 Mc/s, 7.5-3.0 Mc/s, 1.500-600 Kc/s, 500-200 Kc/s, 200-75 Kc/s. Late Model "B" fitted with Super Slow Motion Tuning. Slightly used, but in First-class Condition, aerial tested before despatch. 14-page booklet supplied giving circuits and notes, etc. (or available separately 1/3). ONLY £7 19 6 (carriage 10/6).

A.C. MAINS POWER PACK & OUTPUT STAGE.—In black metal case. Enables receiver to be operated immediately by just plugging in. WITH built-in speaker, £5/5/-, LESS speaker, £4/10/- (carriage 5/-).

6 v. VIBRATOR PACKS. Output approx. 100 v. at 30 mA., fully filtered and smoothed. Complete. ONLY 12/6.

R1155 SUPER SLOW-MOTION TUNING ASSEMBLY. As used on all late model 1155s. Easily fitted to "A" sets, etc. ONLY 12/6.

HIT TRANSFORMERS. 5.5 kV. (Rect.) with 2 v. 1 a. 79/6. 7 kV. (Rect.) with 2 v. 1 a. 89/6. 2.5 kV. (Rect.) with 2-0-2 v. 1.1 a., 2-0-2 v. 2 a. (for VCR97 tube, etc.). 42/6 (postage 2/- per trans.).

POCKET VOLTMETERS.—Read 0-15 volts and 0-300 volts A.C. or D.C. BRAND NEW AND UNUSED. ONLY 18/6.

CRYSTALS. British Standards 2-pin 500 kc/s, 15/-, Miniature 200 kc/s and 465 kc/s, 10/- each.

ROLA 6in. P.M. SPEAKER. Mounted in grey cracked metal cabinet 9in. x 9in. x 4in., with volume-control. Ideal for use with receiver, or as extension. BRAND NEW. ONLY 27/6. (Post 2/6).

MAINS ISOLATING TRANSFORMER. Manufactured by Vortexion. Fully shielded. Will provide true 1:1 ratio from nominal 230 v. Primary. Rated at 100 watts. BRAND NEW. ONLY 22/6. (Post 2/6).

HARRIS ELECTRONICS

(LONDON) LTD.

138 Gray's Inn Road, London, W.C.1.

(Phone TERminus 7937)

Please include carriage costs on ALL items.

(Open until 1 p.m. Saturdays. We are 2 mins. from High Holborn (Chancery Lane Station) and 5 mins. by bus from King's Cross)

Electronics FLEET ST. Ltd

152/3 Fleet St., London, E.C.4. Tel. FLE 2833

Business Hours: Weekdays, 9-6. Saturdays, 9-1.



2 valve A.C./D.C. 3 watt Amplifier designed for portable record player. Fully guaranteed—only 52/6. Post and packing 1/6.

ANOTHER SNIP OFFER

This well constructed portable amplifier cabinet in 2 tone colour with 3 watt A.C. amplifier, 6 1/2" P.M. speaker, output transformer, the four items for only £8.50. Post and packing 7/6. Cabinet will house most makes of auto-changers. Cabinet only 72/6. Post and packing 5/-.

PICK-UP OFFER

New lightweight pick-up with HGP 59/1 t/over cartridge and rest. 32/6. Post and packing 1/6.

CABINETS

A large stock of new design cabinets, speaker enclosures, portable and non-auto cabinets at reduced prices.

Perspex Filter Panels, 10" x 12 3/4" 4/6, 11 1/2" x 15 3/4" 6/6, 13 1/2" x 16 1/2" 8/6. Post and packing 1/-.

A SNIP



Precision made co-ax plugs and sockets. 2/- each, 3/6 pair. Post 6d.

50 Assorted Resistors, Ceramic, S/Mica & Tubular Condensers. 7/6.

12 Assorted Volume Controls. Popular values, Carbon/VV/wound & Presets only. 10/6.

25 Assorted Tag Strips from 2-way to 7-way. 3/6.

All Brand New, 36 Assorted B7G, B9A, B8A & 1/0ctal Valveholders. 15/-.

24 Standard 1 1/2 Fuses, 1a, 2a, 3a, 5a, 10a. 5/6.

Tygan Speaker, covering in attractive designs. 3/6 per sq. ft. Cut to your own size.

Nylon Drive Cord, 6 yds. 2/6.

Our new improved I.T.A. Converter with internal crossover filter. A reliable unit. £4.19.6, plus 2/6 post and packing. I.T.A. co-axial cable, 9d. yard, 8/6 per doz. yards.



Surplus stocks of Hi-Stab Resistors.

1/2 watt 1%	...	1/9
1/2 watt 1 1/2%	...	1/6
1/2 watt 2%	...	1/3
1/2 watt 2 1/2%	...	1/-
1/2 watt 5%	...	1/3
1/2 watt 5 1/2%	...	10d.

Brand New 2-Gang Pots. 1 M. and 1/2 M., 3in. spindle. 3/6.

Silicone-coated Droppers. .2 amp., 1.25 K/ohms, 3/11 each.

Air spaced trimmers. Pre-set and spindle types. 50PF, 10PF, 15PF, 20PF, 25PF, 150PF, 75PF, 2/- each, post 6d.

4 pole 3 way ceramic switch, 3/6, post 6d.

Micro Switches by Burgess, 2/3 each.

American Jack Plugs, 2/6 each

0-1 M/amp moving coil flush-mounting meter, 17/6.

0-100 amp 30 CPS 4 1/2" meter, £2.10.0.

0-50 amp moving iron 6" meter, £3.10.0. Brand new and boxed. Post and packing 1/6.

152/3 Fleet St.,
London, E.C.4.

Tel.:
FLE 2833

Electronics (FLEET ST.) Ltd

Business hours:
Weekdays, 9-6,
Saturdays 9-1.

H.P. Terms
available to
personal
Shoppers.

Visit the City's new acoustically designed

HI-FI Centre

This company is no longer one of the Elpreq Group, but for the convenience of customers we shall continue to stock most of their advertised lines.

AMPLIFIERS BY :

Armstrong, Rogers, Leak, Verdik, Dulci, Goodsell, W.B., Quad, etc.

VHF TUNERS BY :

Armstrong, Rogers, Leak, T.S.L., Goodsell, Dulci, etc.

PICK-UPS BY :

Acos, Leak, Lenco, Garrard, Collaro, B.J., Ortofon.

TRANSCRIPTION UNITS BY :

Collaro, Connoisseur, Garrard and Lenco.

A FULL RANGE OF HI-FI

SPEAKERS BY :

Goodman, Wharfedale, W.B., G.E.C., Lorenz, Plessey, etc.

1958 AM / FM RADIOGRAM CHASSIS

8 valve AM/FM chassis with printed circuit FM tuner section. Illuminated dial in 4 colours. Coverage 1,000-2,000 metres. 200-550 m., 15-50 metres. 88-100 mcs. Dimensions 13in. x 9in. x 6in. Fully guaranteed. £22.10.0. Post & packing 7/6.



A full range of Dulci Radiogram Chassis. Amplifiers, AM/FM Tuners in stock.

TAPE RECORDERS BY :

Grundig, Brennell, Verdik, Sonomag, etc.

All makes of tapes, take-up spools and recording accessories stocked.

ONE OF OUR REPEAT LINES

Brand new recording tape 1,200ft. Kraft paper base. 10/6 per spool. Postage 1/-.

TAKE-UP SPOOLS

New standard 5in. plastic take-up spools 3/- Standard 7in. plastic spools 3/9 Postage 6d.


MULLARD 3/3 AMPLIFIER

Completely assembled in stove enamel finish. £7.19.6. Postage and packing, 4/-.

COLLARO 4/564 4-speed single player with studio crystal t/over pick-up. A.C. mains, only £6.19.6 plus 5/- post and packing.

COLLARO JUNIOR 4-speed player with crystal t/over pick-up using HGP 59/1 cartridge. Our price £4.10.0 plus 4/- post and pkg.

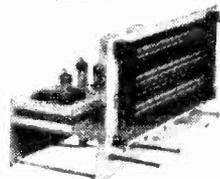BRAND NEW 5-VALVE SUPERHET RADIOGRAM CHASSIS



sockets. Our price £9.10.0. Post & pkg. 7/6

Complete with miniature valves. 3 wavebands, L.M. and Short, P/Up and extension speaker

AMAZING OFFER IN GRAM UNITS



Brand new in Maker's carton. The latest Collaro 4-speed auto-changer with studio t/over pick-up for limited period only. £7.19.6 plus 5/- post and packing.

CABINETS

A large stock of new design radiogram cabinets, speaker enclosures, portable auto and non-auto gram. cabinets at competitive prices. This new Hi-Fi cabinet in walnut finish will accommodate every auto changer or transcription turntable, every amplifier and most tuner units. Dimensions external. 20in. wide x 16in. deep x 29in. high with 12in. legs. Back and bottom ventilated. Price £9.9.0; without legs, £7.14.0.



NEW B.S.R. T.U.9 4-speed player unit using new B.S.R. Full-Fi crystal long playing and standard cartridges. Our price £4.12.6. Post and packing 4/-.

GARRARD 4-SPEED. 4-speed player unit with GC2 crystal cartridge for L.P. and standard playing. £7.10.0 plus 5/- post and packing.

BRAND NEW SPEAKER SNIP

12in. Plessey 3 ohms P.M. speaker. £1.12.6, plus 2/6 post and packing.
10in. Rola 3 ohms P.M. speaker. £1.14.6, plus 2/6 post and packing.
4in. Plessey 3 ohms P.M. speaker. £1.9, plus 1/6 post and packing.

CONSTRUCTOR'S BARGAINS

New range of sub-miniature capacitors for transistor circuits by well-known manufacturers.

1 uf 18 v.	2/6	16 uf 12.5 v.	3/6
1.6 uf 6 v.	2/6	25 uf 6 v.	3/6
2.5 uf 6 v.	3/-	8 uf 25 v.	3/6
5 uf 12.5 v.	3/-	32 uf 3 v.	3/6
8 uf 6 v.	3/6	25 uf 25 v.	3/6

Post and packing 6d.

SENSITIVE GERMANIUM DIODES

3 for 2/6. New GD3 Diodes, 2/6 each. Mullard OA71 Diodes, 6/- Postage 6d.

Junction type PNP Transistors. Red-spot audio freq., 6/6. Blue-spot mixer and freq. changer, 10/- White-spot R.F. stage, 20/-.


Stockists for all Teletron and Repanco transistor components, e.g., Transformers, I.F.T.s, Aerials, T.R.F. and Superhet Coils.



A popular tool for radio and handy repairs. **SOLDEX** solder dispenser. Saves solder waste, using fluxed solder sufficient for 600 small joints, 2/6, plus 6d. post. Solder refills available.

New .0005

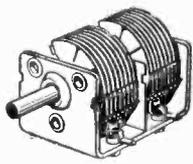miniature 2-gang tuning condensers by famous manufacturer. Only 6/9, postage 1/-.



.0005 single-gang tuning condenser, 4/9, postage 1/-.


10 amp. Panton D.P. switch, 5/6, postage 6d.

Small single-pole bakelite slide switch, 1/9, postage 6d.

New semi-midget Hi-Q 465 k/cs I.F. transformers, dust-core tuning by well-known maker. 5/6 pair, postage 1/-.

First of a new range of **COSSOR** KITS

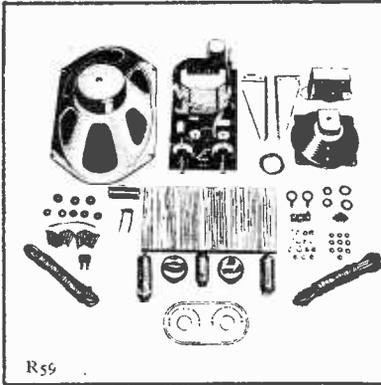**AN EASY-TO-ASSEMBLE
AMPLIFIER**
for the "Do-it-Yourself" enthusiast



This new Cossor kit consists of a printed board, two loudspeakers and all the components necessary to assemble a 3 watt high-quality amplifier. Fully illustrated easy-to-follow instruction manual included.


£9.15.0
(Including Tax)

NOW AT YOUR LOCAL COSSOR DEALER

Cossor Radio & Television Ltd., Cossor House, Highbury Grove, N.5.

BRIMAR 6BQ7A

The Brimar 6BQ7A is a double triode consisting of two independent high slope sections with similar characteristics. The valve is particularly useful as a cascode R.F. amplifier for television receivers and also as a combined oscillator and mixer for frequency modulation receivers. It can, of course, be used wherever high slope triodes are required, and features low interaction between the sections as an internal screen is provided which is brought out to a separate base pin.

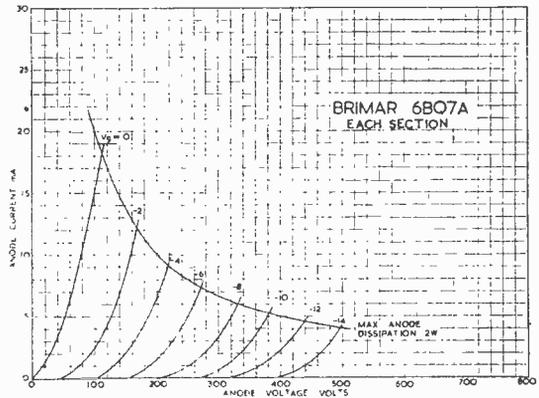

TYPICAL CHARACTERISTICS

Heater voltage.....	6.3 volts
Heater current.....	0.4 amp
Anode voltage.....	150 volts
Cathode bias resistor.....	220 ohms
Anode current.....	9 mA
Mutual conductance.....	6.4 mA/V
Amplification factor.....	39
Anode resistance.....	6,100 ohms
Grid cut-off voltage ($I_a = 10 \mu A$).....	-10 volts approx.

Write to the Publicity Department for a data sheet.

Standard Telephones and Cables Limited **FOOTSCRAY SIDCUP KENT** Footscray 3333

PRACTICAL WIRELESS

EVERY MONTH
VOL. XXXIV, No. 617, MAY 1953

EDITOR : F. J. CAMM

26th YEAR
OF ISSUE

COMMENTS OF THE MONTH

BY THE EDITOR

THE VOICE OF AMERICA

THE Voice of America is again broadcasting the Amateur Radio Show for fifteen minutes every week. The programme is devoted to the latest gossip on the amateur bands, interviews with radio amateurs round the world, propagation forecasts and discussions on the latest technical news of interest to radio amateurs and short-wave listeners. These programmes have been resumed after a lapse of a year. They commenced ten years ago. The programmes are radiated between 21.00 and 21.30 GMT every Tuesday, from WDSI, WLWO, WIWO (all U.S.A.) and Tangier and Morocco, and Munich, Germany.

The programme is repeated at 22.30 GMT on the long-wave transmitter at Munich.

THE REAL MIDGET

TINY pocket receivers are very popular in America, and several manufacturers cater for this market. A contributor in this journal recently invited comments as to whether there was a demand in this country for such tiny transistorised receivers operating from midget batteries of comparatively low voltage. From the response to those remarks, it is evident that there would be a large demand for such receivers which have a number of uses which cannot be catered for by the home receiver nor by the usual somewhat cumbersome battery portable. An examination of the English market, however, shows that only three makers have entered this market with receivers which can easily be slipped into the pocket. They give reasonable quality of reproduction through a midget loudspeaker or they may be used for earphone listening whilst the rest of the family is otherwise engaged and thus is not disturbed. All these midget receivers make use of transistors and printed circuits. We have received a reasonable demand for a P.W. design for a midget but before we could make arrangements for a printed circuit to be prepared we should need to be assured that the demand would justify manufacturers' going to the expense involved. If you are interested in a pocket midget, we should be glad if you would send us a postcard saying so. Address the postcard to Midgets, address as on this page.

RADIO SALES

ALTHOUGH TV licences approach the eight million mark, and thus bid fair to overhaul sound licences within a short time, we are glad to note that the sales of sound receivers do not show any marked diminution. This is surprising when we bear in mind that to some extent TV duplicates the sound service. The majority of viewers, however, seem more interested in watching I.T.V. than the BBC TV and the possession of a sound receiver is, therefore, a necessity. No doubt, in the distant future, the sound broadcasts will vanish altogether, except for shipping news and other programmes which do not need vision.—F. J. C.

Our next issue, dated June, will be published on May 7th.

Editorial and Advertisement Offices :
PRACTICAL WIRELESS

George Newnes, Ltd., Tower House,
Southampton Street, Strand, W.C.2.

© George Newnes Ltd., 1958.

Phone : Temple Bar 4363.
Telegrams : Newnes, Rand, London.
Registered at the G.P.O. for transmission by Canadian Magazine Post.

SUBSCRIPTION RATES

including postage for one year

Inland - - - 19s. per annum.
Abroad - - 17s. 6d. per annum.
Canada - - - 16s. per annum.

CONTENTS :

	Page
Editorial	179
Round the World of Wireless	180
A Beginner's Constructional Course	182
Tone Controls	186
A Communications Receiver On Your Wavelength ...	192
Transistors in Practice ...	195
Reconverting the R.D.F.1 ...	198
Converting the 19 Set ...	203
A Switched FM Tuner ...	205
Radio Components Show for 1958	209
Transmitting Topics ...	213
Servicing Transistor Sets ...	218
Servicing Radio Receivers, the Corsor 529, 540 ...	221
Open to Discussion ...	229
Programme Pointers ...	233
News from the Trade ...	234

The Editor will be pleased to consider articles of a practical nature. Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed: The Editor PRACTICAL WIRELESS, George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Owing to the rapid progress in the design of wireless apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in PRACTICAL WIRELESS is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. PRACTICAL WIRELESS incorporates "Amateur Wireless."

Round the World of Wireless



Broadcast Receiving Licences

THE following statement shows the approximate number of Broadcast Receiving Licences in force at the end of January, 1958, in respect of wireless receiving stations situated within the various Postal Regions of England, Wales, Scotland and Northern Ireland. The numbers include Licences issued to blind persons without payment.

Region	Total
London Postal	1,059,208
Home Counties	1,068,430
Midland	791,959
North Eastern	1,033,246
North Western	769,203
South Western	662,095
Wales and Border Counties	414,470
Total England and Wales	5,798,611
Scotland	762,592
Northern Ireland	181,824
Grand Total	6,743,027

Brabazon Premium

AT the annual parents' day and apprentices' prize-giving of A. C. Cossor Limited, Mr. K. E. Harris, technical director of Cossor Radar and Electronics Limited, presented the prizes, and himself received an ovation for the award to him of the British Institute of Radio Engineers Brabazon premium for the most outstanding contribution to radio and electronic devices for aircraft safety, for his paper "Some problems of Secondary Surveillance Radar Systems."

Broadcast Receiving Licences

DURING January the number of combined television and sound licences throughout Great Britain and Northern Ireland increased by 137,453 bringing the total to 7,898,247. Sound only licences total 6,743,027 including 327,266 for sets fitted in cars.

BBC Engineering Division Appointment

THE BBC announce the appointment of Mr. W. R. Fletcher, B.Sc. (Eng.), A.M.I.E.E., as Regional Engineer, North Region, in succession to Mr. B. H. Vernon, Assoc. M.I.R.E., who has retired owing to ill-

By "QUESTOR"

health after nearly thirty-five years' service with the Corporation.

Mr. Fletcher joined the Engineering Division of the BBC in 1936. He will be taking up his new duties in the summer, and, until he takes over, Mr. E. L. Lycett, M.B.E., the Assistant Superintendent Engineer, Sound Broadcasting, Outside Broadcasts, will be Acting Regional Engineer, North Region.

Radio Exports 100 per cent Up

A NEW high level was reached for exports of British radio equipment in 1957, it is announced by the Radio Industry Council. The value, £43.4 millions, exceeded the record total for 1956 of £40.2 m. by more than £3 m., and was nearly twice that for 1951 (over £22m.).

The continued rapid increase in the exports of sound reproducing equipment is largely due to the high reputation of British equipment in the American market, where "U.K. for Sound" is becoming a slogan.

30 Years With Cossor

W. J. G. BROWN, Cossor Radio & Television Limited representative for Middlesex and East Anglia, has just completed 30 years continu-

ous service with this company, dating from 1927, the year the famous Cossor "Melody Maker" range of radio kits was introduced. Mr. Brown (centre), is shown here being presented with a gold watch by the Marquess of Exeter, chairman of the Cossor Group of Companies, on behalf

of (left to right) Mr. J. S. Clark and Mr. H. Chisholm, joint managing directors of the Cossor Group of Companies, and Mr. H. C. Roberts, sales director of Cossor Radio and Television Limited.


Radio versus Rustlers

THE high incidence of cattle stealing in the Karamoja district of Uganda has led the police authorities to install a V.H.F. radio network as a means of forestalling the sporadic raids of local tribes on the herds of neighbouring villages. The system, which will be under the control of the native-recruited Uganda Police, uses Marconi equipment throughout. The network links up 14 local police posts with a headquarters post. Any suspicious activities observed by local constables are reported to the H.Q. post and a patrol is sent to investigate in radio-equipped vehicles.

B.I.R.E.

THE following meetings will take place during April, 1958:

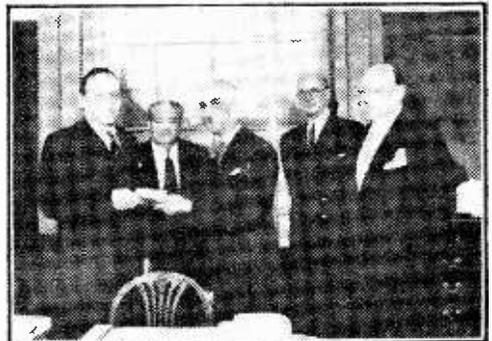London: London School of Hygiene and Tropical Medicine, Keppel Street, Gower Street, London, W.C.1. Tuesday, April 15th, at 6.30 p.m., "Factors in the Design of Airborne Doppler Navigation Equipment"—E. G. Walker. Wednesday, April 23rd, at 6.30 p.m., "Measurement of the Frequency Response of a



Mr. W. J. G. Brown of Cossor, receiving a gold watch after 30 years' service.

Nuclear Reactor" R. J. Cox, B.Sc., A.M.Brit.I.R.E., D. Harrison and R. B. Stevens, B.Sc., A.M.Brit.I.R.E.


North Eastern: Wednesday April 9th, at 6 p.m., Annual General Meeting followed by a programme of technical films.

Scottish: Thursday, April 17th, at 7 p.m., Institution of Engineers and Shipbuilders, 39,

The improved production in December was concentrated in other than 78 and 33 $\frac{1}{2}$ r.p.m. records, thus continuing the trend of recent months. For the three months October to December combined production of 78 r.p.m. showed virtually no change compared with the corresponding period of 1956. 33 $\frac{1}{2}$ r.p.m. were up by less than

Ltd. has been appointed to lead a team sponsored by the Scientific Instrument Manufacturers' Association of Great Britain which will visit Canada in mid-March.

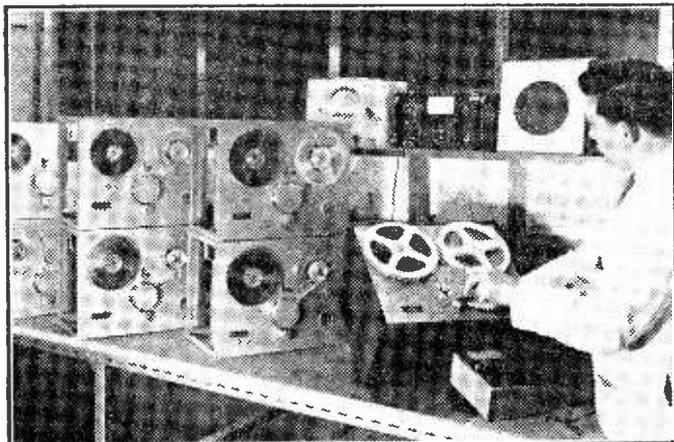The team, consisting of senior executives of seven S.I.M.A. member firms, will see the major industrial and scientific organisations in Toronto, Ottawa and Montreal. It will be the first group to follow up the successful visit of the Canadian Trade Mission to the United Kingdom last December.



The long playing tape decks referred to in the paragraph entitled "Heavy Duty Players"

Elmbank Crescent, Glasgow. Annual General Meeting followed by a programme of technical films.

South Midlands: Friday, April 25th, at 7 p.m., North Gloucestershire Technical College, Cheltenham. "The Automatic Factory"—J. A. Sargrove, M.Brit.I.R.E.

Gramophone Record Production

DECEMBER gramophone record production at 7.5 million (compared with 6.4 million in December 1956), brought the total for the year to 78.3 million compared with 66.5 million in 1956, an increase of 11.8 million (18 per cent.) and of 27.4 million (54 per cent.) compared with 1954.

Manufacturers' sales in December 1957, exclusive of purchase tax, amounted to £1.6 million, the total for the year being £14.1 million, an increase of £2.9 million (26 per cent.) over 1956. In value terms, exports during 1957 accounted for about 25 per cent. of total sales.

10 per cent, while production of other types expanded by over 90 per cent.

Heavy Duty Players

REFLECTOGRAPH continuous tape players, which reproduce music for entertainment or control frequencies for automation in factories, are now being manufactured by Multimusic Limited, a subsidiary of Multicore Solders Limited, at Hemel Hempstead. These machines are believed to be the first heavy duty continuous players to be produced in quantity in Britain. They will play up to two hours on each of two tracks on the tape, reversing automatically at the end of each track and continuing to operate until switched off. The reversal is achieved by a 20 cycle tone, which actuates relays in the machine but cannot be heard by the human ear.

Cossor Leads Team

MR. L. A. WOODHEAD, Director and General Manager of Cossor Instruments

Isle of Man V.H.F.

THE BBC's new V.H.F. sound broadcasting station at Douglas, Isle of Man, transmitting the North of England Home Service on a frequency of 92.8 Mc/s. was brought into regular service on Sunday, 9th March. The station has been working on an experimental basis since 20th December, 1957, while being completed, so that listeners in the Isle of Man with V.H.F. receivers could take advantage as soon as was possible of the improved reception provided by the V.H.F. transmissions.

The new transmitter is installed on the same site as the BBC's Douglas television station, and a single mast carries the transmitting aerials for both services. The effective radiated power is 6 kW and the transmissions are horizontally polarised, which means that receiving aerials should be fixed horizontally.

All-travelling-wave-tube Radio Links

THE G.P.O. has placed an order with Marconi's Wireless Telegraph Company Ltd. for the supply and installation of a single-way U.H.F. radio link between London and a point near Norwich. The link provides two broadband channels primarily intended for the conveyance of television signals, but, if the necessary return channels were provided, they could be used for telephony, each being capable of providing up to 600 high-grade telephone channels simultaneously.

It is hoped to bring the link into operation in the Spring of next year.

and tested. This wiring is not to be disturbed in any way.

Here is a suggested plan to follow. Earth to a separate tag attached with the valve holder pin No. 1 of V2. Earth pins 2, 5 and 6 to another tag (it is best to earth filaments on a separate tag to avoid hum troubles). Shorten the leads of R7 and R8 to about 1/2 in. and solder R7 to pin 4, and R8 to pin 3. Now join the ends of these condensers by a short length of wire running also to junction C9 and R6 (previously wired in the H.T. circuit). Now take pin 4 to earth via C10, which is held by its leads. Join pin 3 to earth via C15 in the same way. The wiring is now complete. Check with Figs. 9, 10 and 12. Check also as follows:

- Pin 1 to earth.
- Pin 2 to earth.
- Pin 3 through a 470k resistor to H.F. point.
- Pin 3 to earth via 100 pF condenser.
- Pin 4 through a 1 megohm resistor to H.T. point.
- Pin 4 to earth via .1 μ F condenser.
- Pin 5 to earth.
- Pin 6 to earth.
- Pin 7 already connected to C13 and R6 see under H.T. section.
- Pin 8 already connected to Tr1. see L.T. section.

Incidentally, this "round the clock" system of checking wiring is very useful even to the experienced man.

Testing the Completed One-valver

Take some ordinary high or low resistance phones. If you are buying do not buy C.L.R. ex-service phones, but search for D.L.R. types which are much more sensitive and useful. Solder carefully to the leads two .05 μ F condensers of 500v. or more working volts. To these condensers attach flying leads. Wrap the lot in insulated tape. When testing mains receivers one lead of these phones can be earthed to chassis and the other placed at various places, i.e., anodes, to test for L.F. signals. The phones are thus insulated from direct current voltage and can do no harm to wearer or receiver. It is not wise for the beginner to use phones on a mains receiver unless they are thus protected.

Connect one phone lead to chassis and the other to pin 3 of the valve just-wired up.

Plug in to mains the right way round, switch on at mains and at S1. Wait one minute. Connect a reasonably long aerial (50ft. or more) directly to the red tag of the PA2 coil. You should immediately hear the local station more or less irrespective of the position of the tuning condenser. The tuning is damped by the long aerial. Now attach the aerial to the flying lead from the condenser C1. Tune C5 and you should receive light and Home programmes easily and probably some Continental stations, but do not expect too much from this stage on its own. It is not even fitted with reaction. These should be very little hum. More will be said about this later.

If, on testing, no results are obtained proceed as follows:

1. Verify that the filament is heated to redness.
2. Verify that H.F. is arriving at junction R6

and C9 by shorting to earth temporarily with a screwdriver. A flash should be obtained.

3. Remove T.C. of V2 and touch with the finger. Loud hum and oscillations should come from the phones. If it does the fault most likely lies in the tuned circuit, PA2 coil and variable condenser. If hum is not apparent then the fault lies either with the valve or its pin connections, resistors or condensers.

Lastly, as the author has previously stated in this magazine, draw the complete circuit of Fig. 12 on paper and ink it in carefully line by line as it is checked against your receiver. In this way any fault is bound to be discovered unless you are reading the colour code of resistors wrongly, or have faulty components.

Checking the Voltages and Current (H.T.)

If you have a voltmeter you may check the voltage at junction R6 and C9 (approximately 280v.), and also at pins 3 and 4 of the valve. The readings will not be true ones (since the meter draws current through R7 and R8 when connected), but may be noted so that if you have


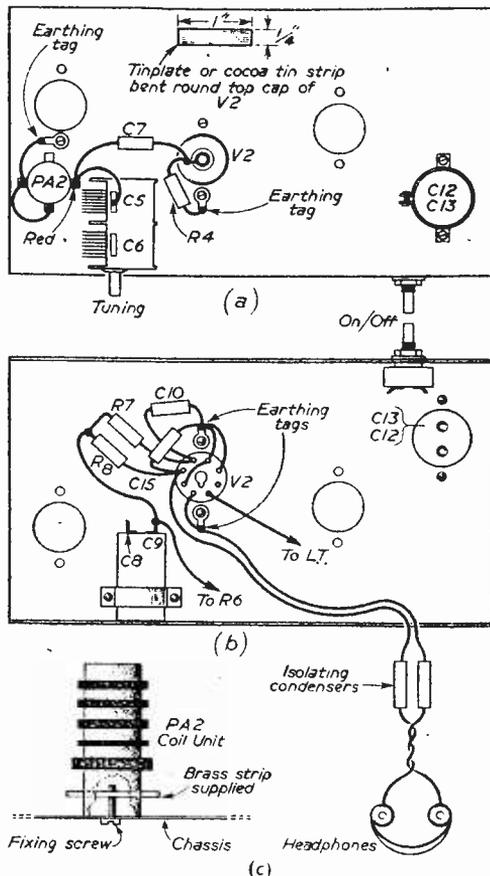


Fig. 10(a).—Wiring for Fig. 9. 10(b).—Underside of chassis (battery supplies not shown and previous wiring omitted). Fig. 10(c).—Details of coil fixing.

any future troubles you know what the readings should be with your meter. To check current insert the meter in the earth lead from pin 2, use low range of mA (about 10 mA first, for safety). It should be about $\frac{1}{2}$ mA.

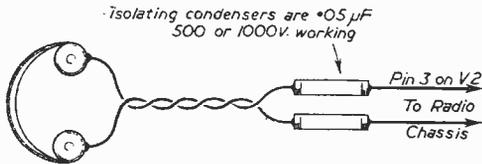Later, details will be given for adding an H.F. tuned amplifier and anode bend detection. After this the radio will receive dozens of stations on a few yards of aerial at good loudspeaker strength.



Note: All joints should be in junction box or well taped

Fig. 11.—Using headphones with safety.

When the receiver is wired and tested it should give satisfactory results, provided a decent aerial is used. If, in the future, this part of the radio should give trouble the maker will at least know how to test it with phones. The enthusiast will no doubt be anxious to get the receiver working a loudspeaker, with this in mind the output stage is added next.

The Output Stage

Another valve identical to that used for V2 is used. You cannot use an SP41 in one stage and an SP61 in another as the filaments are of different voltages. The SP41/61 is not really an output valve but it is cheap and gives good reproduction in a loudspeaker when used as an L.F. amplifier provided the signal input is kept down and not too much volume is expected. Later in this series a suggested output stage to give about 2 watts of power can be substituted. This latter stage uses a 6V6, and if you wish to use it you would be advised to keep to 6 volt filaments. The use of the SP41/61 valve also means economy in rectifying and smoothing the H.T. supply, while the symmetry of the bases throughout the set will enable you to build it with a minimum of error.

Mounting the Components.

Fix an ordinary (or multi-ratio) output transformer in the position shown in Fig. 14. Note that the laminations are at right angles to the filament transformer. This is to avoid "hum" pick up from the mains. Make sure it is mounted firmly.

Mount the valve base, with the tags in exactly the same positions as in V2 and with soldering tags underneath,

where the mounting nuts and bolts pass through. Make the holder dead central so that the valve pins cannot short to chassis. Three holes are needed through the chassis and these should be fitted with grommets. Sometimes one hole would do where three are shown, but the real beginner is advised to keep to separate holes for each wire.

The speaker is not part of the radio and can be mounted separately until the radio is completed, but room is allowed for a 5in. speaker if desired between C6 and C13 (Fig. 14). The speaker must be about 3 ohms impedance, 5in.

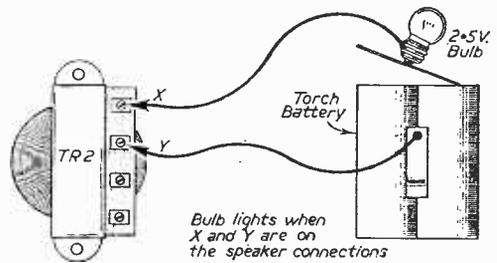


Fig. 13.—Testing to find the secondary winding.

is ideal but any size will do. If it is not fitted with a baffle or case lie it flat on its face on the bench to avoid damage to the speaker when testing the receiver.

Wiring Up the Output Stage

A theoretical circuit is given in Fig. 15 which adds on to the complete circuit already given (Fig. 12). Probably, by now, the beginner will feel he can work from the diagram in Fig. 15, but in case he cannot, a top view of the added wiring will be given next month.

The four tags on the transformer must be sorted out first. If it is a multi-ratio type directions will be supplied with it, and you

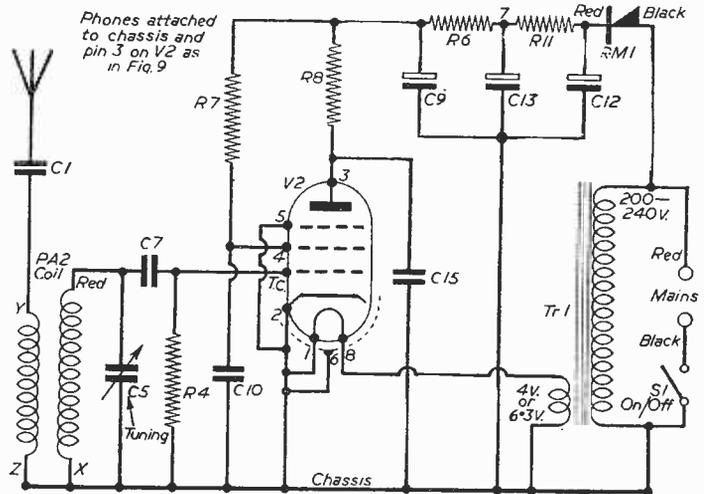


Fig. 12.—The complete detector stage circuit.

should choose a ratio as near to 80 : 1 as possible. Experiments with tappings on this transformer will do no harm if you are in doubt. With a standard type (used in the prototype) the thick wires go to the speaker and the thinner ones to the anode and H.F. You may test this transformer in a similar way to that described

circuit. Attach C14 (which must be a good new condenser, preferably any type but paper) to pin 3 of the detector valve (V2) and the other end as

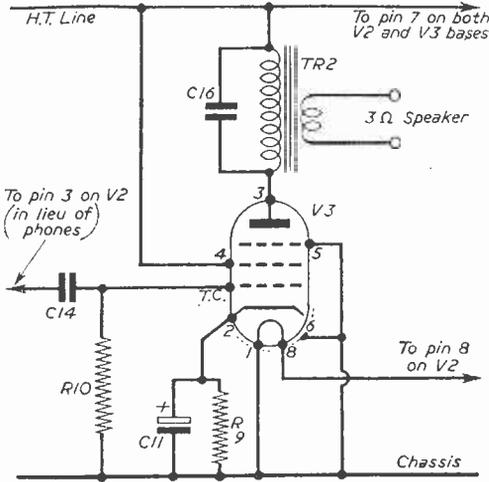


Fig. 15.—The output stage which is added to Fig. 12.

for the filament transformer using a flash lamp and torch battery (Fig. 13).

Here is a suitable plan for the beginner to follow. Earth pin 1 on valve 3 to earthing tag adjacent. Join pins 5 and 6 together and earth to the other chassis tag. Fix R9 in air between pin 2 and any earthed pin, i.e. pin 6. Fix C11 in the same position, i.e. between pin 2 and chassis noting that the plus or red side of this condenser must go to the pin and the negative to earth. This condenser must be of low working voltage type. If this condenser is largish you may fix an earthing tag in any convenient position, but when drilling verify that your drill will not penetrate through some component on the other side of the chassis. If the condenser has no apparent negative connection it is earthed through the fixing to chassis and cannot be suspended in air but must be fixed firmly to chassis with a suitable clip. Connect pin 3 via a grommet to the primary of the speaker transformer. Join pin 4 to pin 7. Join pin 7 to the pin 7 of the valve already wired (V2) to pick up an H.F. supply. Take a lead through another grommet from the other side of the transformer primary to pin 7 on V3 (the output valve). Join pin 8 (V2) to pin 8 (V3).

Now remove the phones from


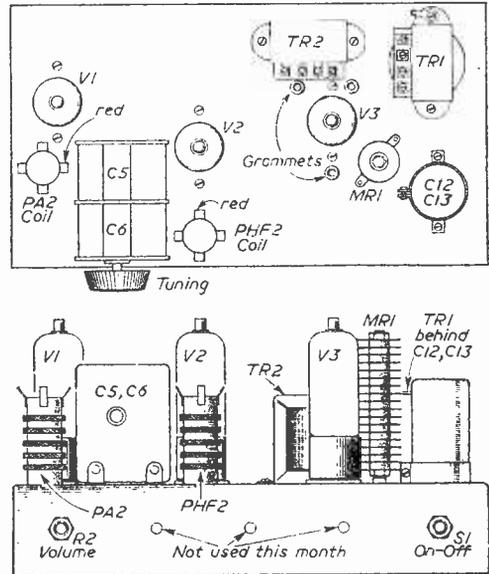


Fig. 14.—Top and front views of this month's development.

directly as possible via a grommet to the top cap of V3. If this condenser is faulty the valve will suffer and the output will be distorted. Metal cased condensers of the Sprague type are ideal as coupling capacitors. The functions of the components will be given later.

(To be continued)

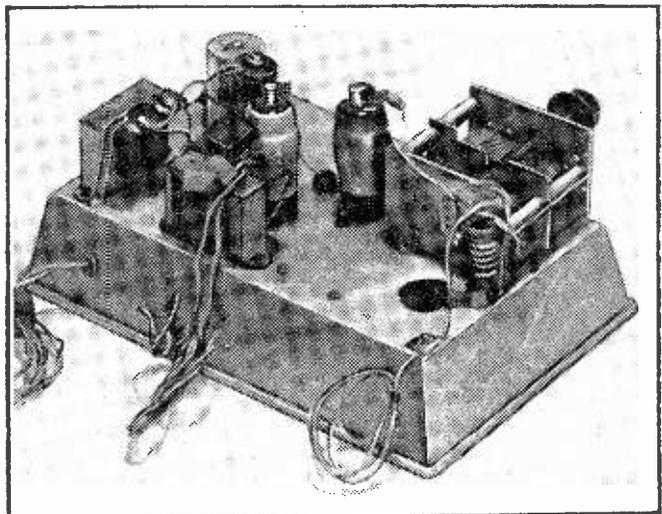

Rear view of the second stage.

SIMPLE TONE CONTROLS

HOW TO CALCULATE VALUES WITHOUT COMPLICATED MATHEMATICS

By H. C. Parr, M.A., F.R.C.O.

MANY amateurs with quite a wide general knowledge of audio amplifiers tend to leave the understanding and design of tone controls and tone correction networks to the experts, under the impression that their mathematics is not equal to the task. In the case of simpler examples this is an erroneous impression, and there is no real difficulty in predicting the frequency response of a given network, or designing one's own circuit to give a desired curve.

The basis of these simple tone controls is the behaviour of a condenser towards audio signals of

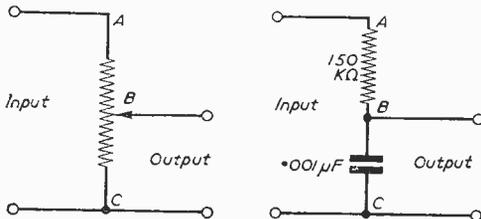


Fig. 1.—(Left) Simple volume control, and Fig. 2 (Right) Treble cut control.

different frequencies, the impedance it presents being inversely proportional to the frequency. Thus a .001 μF condenser has an impedance of 160 KΩ at 1,000 c.p.s., 80 KΩ at 2,000 c.p.s. and 40 KΩ at 4,000 c.p.s. Table I shows the approximate impedance in ohms represented by various common values at selected frequencies.

While some readers may like to cut this out and keep it for reference, others will find this unnecessary if they retain the one fact that 1 μF presents 16Ω at 10,000 cycles. Then, remembering that impedance is inversely proportional to capacity, and to frequency, it is possible to work out mentally every entry in Table I to the degree of accuracy required, which need never exceed about 10 per cent. in these applications.

Every simple tone correction network can be considered as a potential divider, of which the

simplest example is the ordinary volume control (Fig. 1). Suppose we set the movable contact, B, so that the resistance between B and C is 100 KΩ, i.e., one tenth of the total. Then, if we have as input an audio signal of 1 volt, say, since this voltage drops uniformly as we move from A to C, at B it must be 1/10 volt, and the signal is attenuated to one tenth.

Circuits

The degree of attenuation produced is always expressed in *decibels*, a measure which has many advantages over the plain ratio. One of these is the fact that it bears a closer relationship to the effect produced on the ear. Now the fundamental characteristic of the decibel scale is that the *ratio* of output to input is expressed as a *difference* of decibel level. To take the network of Fig. 1 as an example, an attenuation ratio of 1/10 corresponds to a decibel difference of 20 db., so that if the input level were described as 30 db., the output would be 10 db. But note that the zero of the decibel scale has no significance, and it would be just as correct to describe the input as 10 db., and the output as -10 db. Table II gives the decibel difference corresponding to various ratios of signal voltage.

Treble Cut

Now let us consider the simple "treble cut" circuit of Fig. 2. At low frequencies the condenser

TABLE II

Ratio	1	1 1/4	1 1/2	2	3	4	5	7	10	14	20	30	40	50
Db.	0	2	4	6	9	12	14	17	20	23	26	29	32	34

will have a high impedance and so provides practically the whole of the impedance between A and C, and there is no appreciable attenuation. For higher frequencies the impedance between B and C will decrease, and the ratio of output to input will fall, giving attenuation in the treble.

To describe this quantitatively we can draw up a table (Table III) obtaining the approximate attenuation at each of our selected frequencies. We know that the ratio of output to input is the ratio of the impedances BC to AC. The first of these is obtained directly from Table I for each frequency, but the second, being of a condenser and resistance in series, offers considerable difficulty if it is to be treated exactly. However, we can make a great simplification whenever we have such a series combination by assuming its impedance to be *equal to the larger of the two component impedances* at any particular frequency. We shall call this Rule 1. The effect of phase changes in the condenser actually makes this a better approximation than would at first sight appear, and the error never exceeds 3 db. Furthermore, it can be allowed for later when

TABLE I

c.p.s.	30	100	300	1,000	3,000	10,000
.1 μF	50K	16K	5K	1.6K	500	160
.05	100K	30K	10K	3K	1K	300
.02	250K	80K	25K	8K	2.5K	800
.01	500K	160K	50K	16K	5K	1.6K
.005	1M	300K	100K	30K	10K	3K
.002	2.5M	800K	250K	80K	25K	8K
.001	5M	1.6M	500K	160K	50K	16K
500 pF	10M	3M	1M	300K	100K	30K
200	25M	8M	2.5M	800K	250K	80K
100	50M	16M	5M	1.6M	500K	160K
50	100M	30M	10M	3M	1M	300K

the response curve is drawn. The second row of Table III is obtained in this way, and the third by dividing c.p.s.

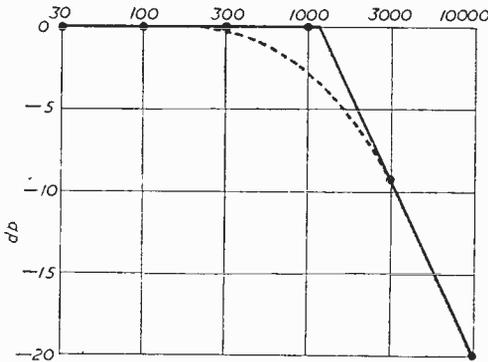


Fig. 3.—A frequency response curve.

(approximately) the second by the first. The attenuation in db. then comes from Table II, and has to be reckoned negative because it is an attenuation. This can now be plotted as the usual type of frequency response curve (Fig. 3). The frequency scale of such a diagram is always logarithmic, and since the frequencies we are considering, 30, 100, 300, etc., are roughly in geometric progression, the lines representing them are drawn practically equidistant.

This method of working always gives a graph of straight lines, with "sharp corners," but if we "smooth these out" a little, we are, in fact, com-pensating for the inaccuracy of Rule 1. The dotted curve in Fig. 3 is thus a more accurate representation, and the attenuation at 1,000 cycles.

TABLE V

c.p.s.	30	100	300	1,000	3,000	10,000
200 pF.	25M	8M	2.5 M	800K	250K	80K
XY (Rule 2)	400K	400K	400K	400K	250K	80K
XZ (Addition and Rule 1)	500K	500K	500K	500K	250K	100K
Ratio XZ/YZ	5	5	5	5	2½	1
Db.	-14	-14	-14	-14	-8	0

where the two impedances are equal, should be 3 db.

Bass Boost

Fig. 4 shows another common network. This

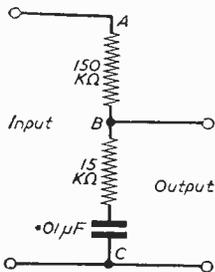


Fig. 4.—Bass boost circuit.

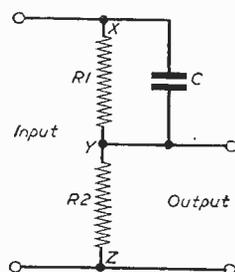


Fig. 6.—Treble boost circuit.

provides bass boost at 6 db. per octave (i.e., 6 db. each time the frequency is halved) exactly as is needed for correcting the bass in a tape play-back amplifier. It will be seen to differ from Fig. 2 in two respects. Firstly, the condenser has ten times its former value, so that the attenuation will be obtained at frequencies one tenth of those obtained from the first circuit. Secondly, the 15 KΩ resistor will prevent the impedance of BC ever falling below this value, and so will give a constant attenuation of 20 db. (for BC is then about one tenth of AC) at high frequencies. Table IV and Fig. 5 show the derivation of the response curve of this circuit. In Table IV, BC is obtained by applying Rule 1 to the condenser and the 15 KΩ resistor, and AC by applying it to the condenser and the total resistance, 165 KΩ. Note that the corners have again been rounded off in Fig. 5.

Now to illustrate the reverse procedure, let us design a treble boost circuit giving 14 db. boost, beginning at about 2,000 cycles. Fig. 6 is an obvious suggestion, the condenser behaving like an open circuit at low frequencies, and "letting more through" as the frequency rises. No simple circuit, of course, can actually produce "boost"; it can only attenuate

TABLE III

c.p.s.	30	100	300	1,000	3,000	10,000
BC (.001 μF)	5M	1.6M	500K	160K	50K	16K
AC (Rule 1)	5M	1.6M	500K	160K	150K	150K
Ratio	1	1	1	1	3	10
Db.	0	0	0	0	-9	-20

those frequencies we do not wish to boost. Choosing 100 KΩ as a suitable value for R2, it is easy to calculate R1. If the attenuation in the bass is to be 14 db., a voltage ratio of 1 to 5, R1 and R2 together must be five times 100KΩ and so R1 must be 400 KΩ. Now C is to take charge at above 2,000 c.p.s., and so its impedance must be comparable to R1 at this frequency. Putting it equal to this value, it must be 80 KΩ at 10,000 c.p.s., and from Table I we find C=200 pF.

We can now work out Table V to check the performance of this circuit. As R1 and C are in parallel, we are confronted by a new problem, but this

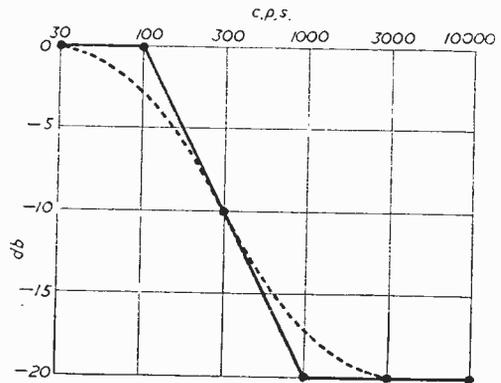


Fig. 5.—Response curve for bass boost circuit.

is solved as easily as the series case. We assume the resulting impedance to be equal to the lesser of the two component impedances, and call this Rule 2. This approximation is just as satisfactory as, and has similar consequences to, Rule 1, and is used to obtain the impedance XY in Table V. When adding the 100 KΩ, YZ, to these values to obtain the third row of our table, we must notice that the values for XY in the upper frequencies are, in fact, values of the impedance of C. XY is, therefore, capacitive, and Rule 1 must be applied to give XZ.

A curve could be drawn from the data of Table V, (see previous page) with the corners suitably rounded off, and would confirm that we have achieved the response desired.

Variables

Variable tone controls, even quite complicated ones, can usually be dealt with easily by considering separately the two circuits produced when the moving contact of the potentiometer is at either end of its travel. The bass boost/cut control of Fig. 7 becomes Fig. 8 and Fig. 9 when treated in this way, and each of these can be dealt with as outlined in the above paragraphs. The two response curves derived from Figs. 8 and 9 can be plotted on the same diagram, Fig. 10, to illustrate the effect of the bass control in its two extreme positions.

There is one further point which must be considered when tone control networks are to be included in amplifier circuits, and that is to ascertain what effect, if any, the internal impedance of the source,

TABLE IV

c.p.s.	30	100	300	1,000	3,000	10,000
.01 μF	500K	160K	50K	16K	5K	1.6K
BC (Rule 1)	500K	160K	50K	16K	5K	1.6K
AC (Rule 1)	500K	165K	165K	165K	165K	165K
Ratio	1	1	3 1/2	10	10	10
Db.	0	0	-10	-20	-20	-20

and the impedance of the load, will have on the performance of the network. This effect will be negligible if the source is of low impedance, and the load of high impedance, compared with the elements of the tone control itself. In other cases, however, they must be taken into consideration. Referring back to Fig. 4 for an illustration, it is clear that the source impedance of the input must be added to the resistance AB, and that the load impedance is in parallel with BC. We can suppose the network to be

supplied by a pentode stage with an anode load of 100 KΩ (via a coupling condenser, of course, whose effect on the signal should be negligible), and to be supplying the grid of the next valve, with a 500 KΩ grid leak,

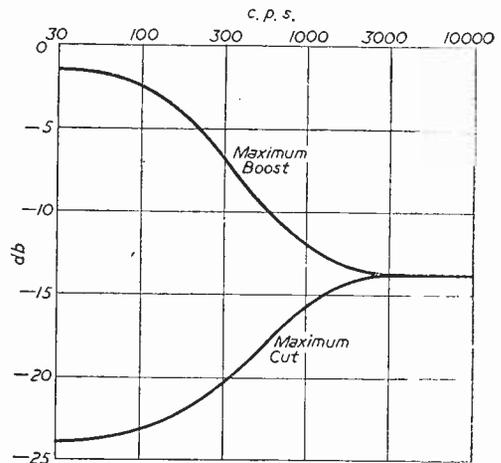


Fig. 10.—Curve of Bass Control Circuit

as in Fig. 11. It is a well known fact that a pentode stage acting as a source behaves as if the anode load were the internal resistance of the source, and so we must add 100 KΩ to the value of AB before we begin our calculations. As for the effect of 500 KΩ across BC, this need not be considered so long as it exceeds the impedance of the condenser (Rule 2). In the extreme bass, however, it prevents BC ever rising above 500 KΩ, and so maintains an attenuation of about 2 db. here.

To a mathematician the above methods will appear appallingly rough and ready, but to those of us who are not so familiar with jωt and the Argand Diagram, they will solve surprisingly complicated circuits with fair accuracy. The secret lies in knowing what may be neglected and what approximations may be made, and in this, as in so many activities, practice makes perfect.

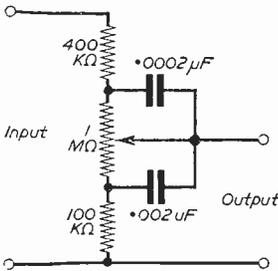


Fig. 7.—Bass boost-cut circuit.

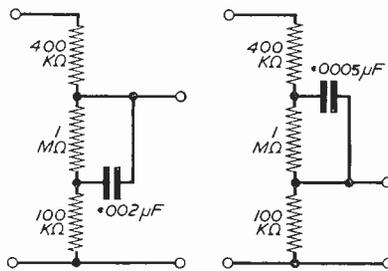


Fig. 8 and Fig. 9.—Rearrangement of the Fig. 7 circuit.

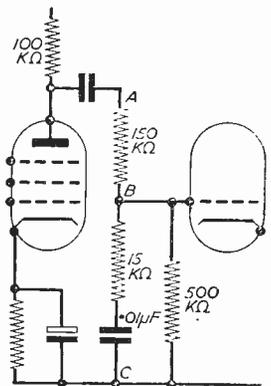


Fig. 11.—A pentode tone control stage.

A Communications Receiver

AN AMATEUR RECEIVER INCORPORATING THE R1155 CONVERTER

By R. H. Wright

MANY amateur constructors are frequently diverted from building a superheterodyne receiver because of the ensuing difficulties of alignment, unless one possesses, or has access to, a signal generator. However, if the R1155 converter described in the February issue of this magazine is followed by a suitable intermediate frequency amplifier, demodulator and audio-frequency amplifying stages, the whole will give an efficient superhet. receiver well within the building capacity of the average constructor.

If the full range of Denco octal-base plug-in coils are used, the receiver will give continuous coverage from .175 Mc/s to 31.5 Mc/s (1,700-9.5 metres), thus including the long, medium and short wave broadcast bands, trawlers and the 1.8, 3.5, 7, 14, 21 and 28 Mc/s amateur transmitting bands.

Fig. 1 shows the circuit of an amplifier suitable to follow the R1155 converter and which has an intermediate frequency of 465 Kc/s. The converter output is applied across grid and cathode of V1, the intermediate frequency amplifier, and the amplified signal from this valve is transformer coupled to one of the diodes of V2 for demodulation. R5 is the demodulator load resistor and the A.F. component of the signal now passes to

the grid of the triode section of V2 via the A.F. gain control (VR1). The output of this triode is resistor-capacity coupled (R7/C7/R9) to the output valve V4. Tone control (VR2/C8) is applied to the output and can prove useful in reducing the effects of interference.

Output can be applied to a loudspeaker or to a pair of low-resistance telephones through the output transformer, T1. If output to either loudspeaker or telephones is required, the output transformer should be of multi-ratio design.

Automatic gain control is provided from the second diode of V2, the I.F. signal being passed from the anode of the I.F. amplifier to this diode via C5 and the actual control voltage developed across R8. Since this resistor is returned to H.T.—instead of the cathode of V2—the A.G.C. voltage is delayed. This is preferable to simple A.G.C. which would reduce the amplification even on weak signals. A.G.C. may be switched off when not required by closing the switch, SW1.

C.W. Reception

For the reception of C.W. signals V3 operates as a beat-frequency oscillator in conjunction with the oscillatory circuit formed by L1/L2 and C12/C13. The B.F.O. signal is applied to the demodu-

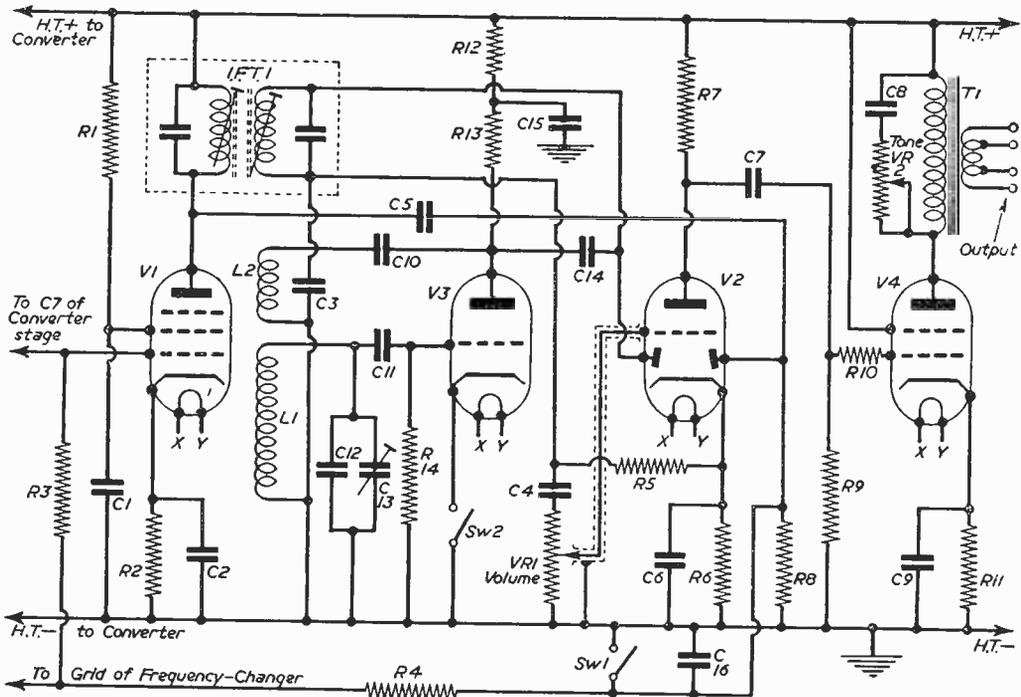


Fig. 1.—Amplifier section for use with the R1155 Converter.

Adjustment

In addition to the adjustments required for the converter originally the cores of the I.F. transformer, I.F.T.1, in the amplifier should be adjusted for maximum signal strength and C13 in the B.F.O. section adjusted to give an audio note of about 1,000 cycles on C.W. signals.

As already mentioned, Denco octal-base plug-in coils may be used to give continuous frequency coverage from .175 to 31.5 Mc/s (1,700-9.5 metres), but each oscillator coil requires a different value of padding capacitor. This is made easy for constructors since the end of the oscillator grid coil winding that is connected to the padding capacitor is taken to a different pin on the base of each coil and so the required padder may be permanently wired into position on the octal-valve base into which the coil is plugged. Actually, the padding capacitors may be omitted, though, if used, they do help to keep the two tuning capacitors in step. The table on page 190 shows the appropriate coil ranges and pins to which the padding capacitors are connected and also the padder values.

Two coils will be required for each range—
BLUE for aerial.
RED for oscillator.

Fig. 4 shows a suitable power unit for use with

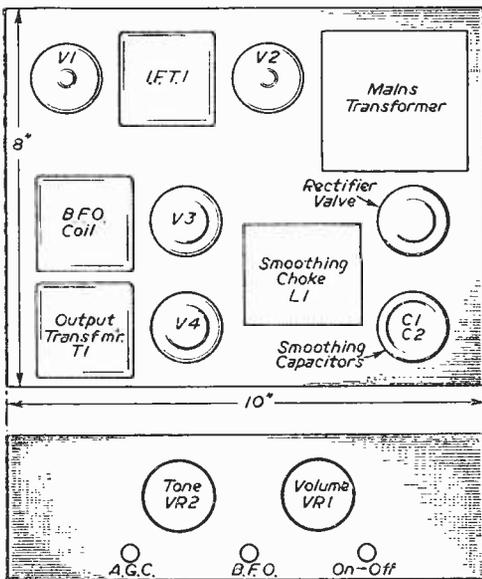


Fig. 2.—Chassis layout and panel control details.

the complete receiver though it may, of course, be operated from any existing power unit giving 6.3 volts at 3 amps for L.T. and 250 volts at 80 milliamps for H.T.

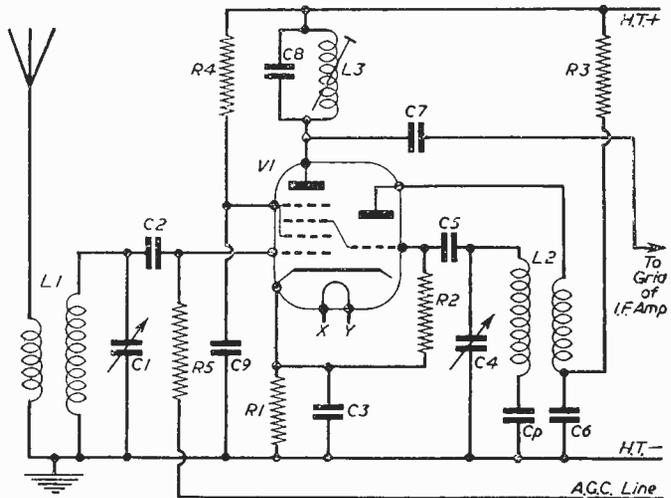


Fig. 3.—Frequency converter circuit for use with the amplifier shown on page 189.

New Transistor Factory

A MAJOR achievement by British industry lies behind the completion of a unique £300,000 transistor factory for Semiconductors Limited at Swindon, in readiness for the arrival of key production equipment valued at over £100,000, by chartered aircraft from America.

Formed only in May, 1957, by The Plessey Company Limited and the Philco Corporation in America, Semiconductors Limited will manufacture a wide range of silicon and germanium high frequency transistors, in their entirety, for the first time in this country, and such rapid progress has been made that the factory will be in production by the middle of this year.

During these past nine months logistic problems have been overcome, key personnel have been engaged and trained in the Philco transistor factory in America and a 40,000 sq. ft. factory, the construction of which started only six months ago, has been completed by the main contractors, Richard Costain Limited.

The factory is specially insulated and features an air conditioning plant which controls the ambient temperature to ± 2 deg. F, humidity ± 5 per cent, and by electrostatic and mechanical filtration controls ambient dust to less than one cubic micron per centimetre of air. Such features are indispensable to a production process of a highly reliable transistor.

Facilities are provided in the factory for supplying extremely pure water of 18 million ohms/centimetre resistivity. Ultra pure gases are piped through the plant and are available at strategically located points. To control dust, the assembly area is free from overhead piping, all services being brought up through the floor.



On Your Wavelength

BY THERMION

On Pronunciation

I HAVE often tilted at the BBC announcers' pronunciation of standard words. Mr. M. E. Northey of Oakhampton endeavours to support them. He says that if covenant is pronounced "kuvenant," Coventry should be pronounced "Kuventry," which only goes to show that he could not have read my comments closely. Of course, there are thousands of anomalies in the English language, but where all dictionaries have agreed on a particular pronunciation, I see no reason why the BBC should decide for itself upon a new pronunciation. There is no justification for Kuventry, which is a place name and is not so pronounced locally. There is no justification for Raif for Ralph, furrin for foreign, nor for any of the other words I have listed here from time to time. The dictionary must be our guide. A great deal of this mispronunciation is due to the fact that when our school teachers go to a training college they are not taught pronunciation, enunciation and diction. That can be the only explanation for a Yorkshire teacher pronouncing Mother as Moother, and book is boook. If the teachers do not speak correct English, the scholars cannot be expected to. I challenge any Yorkshireman or Lancastrian for that matter, to justify their pronunciations by quoting a dictionary. Mr. Northey seems to think that we should pronounce our words as we think fit. He does not want standardisation of pronunciation and presumably therefore as he wishes to dispense with the dictionary as a standard he is against standard spellings. In other words, we should spell and pronounce words as we think fit.

Service Sheets

MR. J. M. NEWBY of Shildon wishes to draw my attention and presumably yours to the fact that most manufacturers will not supply service sheets for their receivers, and that owners are therefore left to purchase the service sheets advertised at 4s. 6d. each. This sum, by the time poundage on postal orders and postage stamps are added, mounts up to over 5s. It sometimes costs 2s. 6d to 5s. deposit to borrow an instruction manual for a fortnight. Here is a chance for someone! Manufacturers obviously wish every purchaser to take his receiver to the dealer, and even a letter to the manufacturer asking for technical advice fails to produce any useful information. You are flobbered off with the name and address of your nearest agent. If people who bought radio and television receivers demanded service data before they purchased from the dealer, the dealers themselves would bring pressure to bear on the manufacturers. Dealers do not like losing sales! In this do-it-yourself age, the attitude of the manufacturers is out of joint with the times. It is unfortunate that some dealers have earned an unenviable

reputation for overcharging and there can be little surprise that public confidence in some of them is at a low ebb.

The Printed Circuit

LARGE numbers of readers have expressed their interest in the printed circuit and suggest that this journal should sponsor a design incorporating it. I have no doubt that something will be done, but it would be impossible to produce a design which would satisfy the multifarious requirements of our readers. Some want a portable, others a radiogram, and so on. A start would have to be made with a simpler circuit.

Credits

A READER resident at Hawthorne Crescent, Slough, who signs his letter so illegibly that he does not wish me to know his name, refers to my comments on those lengthy credits given at the end of TV programmes. I said that these credits are meaningless, although they may flatter the vanity of some of the people responsible for either production of the film or acting in it. You will gather from this that I have a very poor opinion of actors and actresses generally, and I am not easily deluded by the ballyhoo and aura of publicity which surrounds their unoriginal work. For all acting is unoriginal. The words are written by the author, the dresses and sets are designed by other people, the gags are turned out on production line method, and the producer tells them how, when and where to place their feet. They are "empty shells from eight till ten filled with the wit of other men." You can always find a Hamlet, but you can't find a Shakespeare. I emphasise that the public does not care two hoots who produces the programme.

If credits are necessary, it should be a short list, with the author's name first, followed by the leading actors and the name of the producer. But to string out a long list of names, of those who merely have walking on parts, or a couple of lines to utter, is boring, meaningless, and merely flattering to the vanity of these people even if pleasing to their friends. It is one of the annoyances of the cinema that the list of credit titles occupies so long—a hefty list of names of no interest whatever to the audience—and names usually which cannot be pronounced and presumably must be sneezed. I do not wish to know, for example, the name of the man who cut the film, nor the man responsible for sound effects. I am not in the least interested who manufactures a pound of sausages, nor who weaves the cloth of the clothes I wear. I repeat that it is merely pandering to the vanity of the lank hair Chelsea types who surround the stage, the cinema and the entertaining professions generally.

BENDIX RECEIVER RA 10.

A 4 waveband superhet covering 150 kc/s-10 mc/s. Valves 6SK7 1st R.F. 6KB Mixer. 6SK7 1st and 2nd I.F. 6R7 2nd Det. 6C5 B.F.O. 6K6 output. Size 6 1/2 x 1 1/2 in. Easily converted to mains operation as described on page 453 of the September "Practical Wireless." £5/10/- Carr. 7/6.

GOODMAN'S OUTPUT TRANSFORMERS. Impedance 5,000 ohms to 3 ohms. 3 watt, suitable for 6V6's, 6BW6, etc., 4/6 each. P. & P. 1/2.

HIGH RESISTANCE HEADPHONES. 4,000 ohms. Brand new, 11/6 each. P. & P. 2/-.

INDICATOR UNIT SLC No. 5.

Ideal for conversion into an Oscilloscope using a 139A or ACR 10 tube. Unit consists of 2-VR65, 1-VR66, various resistors, condensers and pots. Size 11 x 6 x 3 in. Brand new, complete with modification circuit. 20/- P. & P. 3/- each.

COLVERN WIRE WOUND POTENTIOMETERS. 25 watts 50k and 100k. Price 6/- each.

LEAD ACID ACCUMULATORS (unspillable). 2 volts 16 A.H. Ideal for 6 volts and 12 volts supply. Brand new original cartons. Size 4in. x 7in. x 2in. 5/6 each. P. & P. 2/6. 3 for 15/- P. & P. 3/6. 6 for 27/6. P. & P. 5/-.

AMERICAN THROAT MICROPHONES. Type T.S. 30 3/- each. Post paid.

CONVERTERS. Easily the most useful units released by the Ministry. Within minutes you can extend the frequency of any receiver to cover the following:—

R.F.26. 50-65 Mc/s., 20/- each.
R.F.25. 40-50 Mc/s., 8/6 each.
R.F.24. Shop soiled, 7/6 each.
Complete with valves and circuit.

3/6 Postage on each.

PYE 45 mc/s. I.F. STRIPS. Complete with seven valves. 6-EF50, 1-VR92, 6 tunable I.F. transformers. 30/- Post paid.

DYNAMIC SOUND POWERED HEADPHONES. Type D.L.R. 5. 60 ohms. Individual earpieces can be used for room-to-room communication.

No Batteries required—just connect up. Can also be used as miniature speakers. ONLY 7/6 pair. P. & P. 2/6.

INFRA-RED MONOCULAR. Ideal for night viewing, etc. Complete with push button power unit and focus lenses.

Brand new in beautiful carrying case. Originally cost Govt. £40. Our Price, 25/- P. & P. 3/6.

AMERICAN MIDGET ACCUMULATORS. 36 volts, lead acid type. 2/6 ea. P. & P. 1/-.

VIBRATOR POWER PACK. Input 12 v., output 150 V., at 100 milliamps. 2 bias packs 50 V each.



Complete with screen lead for battery. Completely smoothed. Brand new. Price 20/- Postage and packing 3/6.

WALKIE/TALKIE SET

ONLY 60/- EACH



consisting of transceiver covering 7.4-9 Mc/s., range approx. 10 miles. complete with 5 valves, headphones, microphone, junction box, & 6ft. telescope aerial. Only requires 150 v. & 3 v. dry battery. These magnificent Walkie Talkie sets (as used by H.M. Forces) are ideal for any application and can be operated with ease by young and old alike. Only 60/- each. P. & P. 4/-.

SIGNAL GENERATOR AND WAVEMETER

Type W.1649. Frequency of Signal generator: 140 to 240 Mc/s. Accuracy +0.5 Mc/s. Frequency of Heterodyne Wavemeter: 155-255 Mc/s. Accuracy +0.2 Mc/s. Containing VR.135 and 4-VR91, 5 meg. crystal. Retractable aerial. Power requirements: 6.3 volts and 120 volts. Unit housed in copper lined wooden case. Size 15 1/2 in. x 13 in. x 14 1/2 in. 45/- Plus 10/-.

R.C.A. MAINS TRANSFORMERS

Input 110-240 v., output 345-0-345 at 150 mA. 6.4 v. at 4.5 amps. 5 v. at 2 amps. Brand new fully shrouded. Limited quantity. Write now. Only 35/- P. & P. 3/-.

COMMUNICATION RECEIVER R.1155

This magnificent 10 valve 5 wave band receiver gives world wide reception over a coverage of 75-200 Kc/s., 200-500 Kc/s., 600-1500 Kc/s., 3-7 Mc/s., 7.5-18.5 Mc/s. (4000-15 Metres) incorporating Medium, Long and Short wave bands. Requires 250 volts and 6 volts. Fully tested and dispatched in full working order, complete with Super slow motion drive, circuit and instruction book. Originally cost £70. Our Price only £8.10.0. Carr. 10/-.

POCKET VOLT TEST METER

Two D.C. ranges: 0-250 v. and 0-15 v. Complete with test prods. Brand New Very limited quantity. ONLY 10/6, p. & p. 1/6.

WIRELESS SET NO. 19 MK. II

As described and recommended for Amateur use in April and May issues of "Practical Wireless." This famous Transmitter-Receiver incorporates "A" Set—TX/RX covering 2-8 Mc/s. (37.5—150 metres). "B" Set—VHF TX/RX covering 230-240 Mc/s. (1.2-1.3 metres) and intercom amplifier. Complete with 15 valves, 500 microamp check and tuning meter, circuits and instruction book. (American manufacture) In magnificent condition, 60/- carr. 10/-.

ATTACHMENTS FOR ABOVE:

Variometers	20/-
Headphone and microphone assembly	13/6
Morse key assembly	4/6
12ft. aerial	7/6

Relda Radio Ltd.

(Dept. "P") 32A, Coptic Street, London, W.C.1. Phone: MUSEUM 9607. Tottenham Court Road Underground. Fourth turning on the left down New Oxford Street.

LOUD HAILER SPEAKERS

Sound powered with output transformer, impedance of speech coil 7 ohm, handling capacity 8 watts. Ideal for inter-communication. Complete with carrying strap. Price 20/- Packing and carriage 5/-.

WHEATSTONE BRIDGE.

Consisting of four stud switches: 0-10 ohms, 0-100 ohms, 0-IN/F. Galvanometer centre zero F.S.D. 2.5 mA. Ranges easily extended. Housed in oak cabinet 16 x 7 1/2 x 6 in. Complete with instructions, 40/- P. & P. 4/-.

MUIRHEAD VERNIER SLOW MOTION DRIVES. Scaled 0-180 deg. Ratio 25 to 1. 3in. dia. 10/6. P. & P. 1/6.

R.T.-7/APN-I ALTIMETER TRANSCEIVER. Brand new complete with 14 valves: 3-12S7, 4-12SH7, 2-12H6, 1-VR150, 2-9004, 2-955. Famous Wobblulator Unit, Dynamotor, Relays 3,500 ohms and 6,500 ohms. A.F. amplifier. Receiver section covers 400-450 mc/s. Transmitter sweeps 418 to 462 mc/s. Ideal for model control work, etc. Only 35/- carriage 10/-.

PUSH BUTTON COIL PACKS. 465 Kc/s. I.F. Gram. long, medium and 6 short wave-band spread. 8/6. Post 1/6.

RELAYS. 6,500 ohms and 3,500 ohms. 8/- pair. Post paid.

WAVEMETER TYPE W1433. Frequency 154-260 mc/s., with crystal check and calibration chart. Mains 50 cycle. 50/- Carriage 10/-.

BENDIX RECEIVER MN26.C. Covering 150-1,500 kc/s in 3 bands. Valves used 5-6K7, 2-6N7, 2-6J5, 1-6F6, 1-6L7. Complete with switching motor and dynamotor. This superb unit has been modified for 12 v. operation. Ideal car radio. With circuit. Only 80/- Carr. 8/6.

WESTON I Amp. H.F. METERS. 2in. circular. Brand new, 5/6. P. & P. 1/-.


ARMOUR RECORDING WIRE. U.S.A. top quality on original reels. Length 3,700 yds. 10/- P. & P. 1/6.

COMMAND RECEIVERS. 1.5-3 mc/s. fully valved, with circuit. 65/- P. & P. 3/6.

LUMINOUS MAGNETIC MARCHING COMPASS. Pocket size. Brand new with instructions. Only 12/6. P. & P. 1/-.

COMPLETE HEADPHONE AND MICROPHONE ASSEMBLY. A must for every Constructor and "Ham," consists of moving coil, padded headphones and "press to talk" microphone. 10/- P. & P. 3/6.

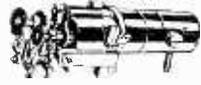
AMERICAN GEARED MOTOR. 24 v. D.C. with built-



in precision gearbox. No. 1 drive 24 R.P.M. No. 2 drive 6 R.P.M. On 12 v. No. 1 drive 16 R.P.M. No. 2 drive 4 R.P.M. Overall size of motor and gearbox, 7 1/2 in. x 3 1/2 in. x 3 in. Weight 1 lb. 14 ozs. Brand new. ONLY 17/6. P. & P. 3/-.

MAXI-Q INSULATORS

REGD.

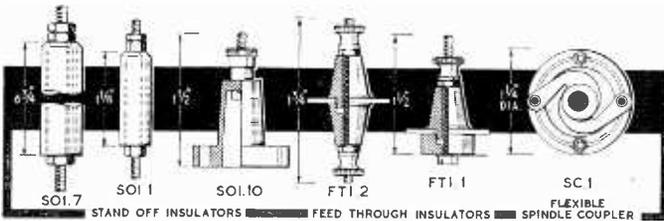

STAND OFF INSULATOR, SOI.10.
This insulator is completely moulded in polythene and fixing is by two 4BA holes on in. centres. Price 1/4.

FEED THROUGH INSULATORS, FTI.1 and FTI.2.
These moulded polythene components provide a sound means of feeding high voltage or r.f. leads through metal chassis, screens, etc., or, alternatively, are very suitable for use as a terminal where first class insulation is required. They are most suitable where rear of panel or under-chassis space is limited.
Moulded in the following colours: Red, Blue, Green, Black and Yellow. FTI.1 1/7, FTI.2 1/11.

FLEXIBLE SPINDLE COUPLER, SC.1.
The linking of components is made easy with these polythene insulated couplers. They are completely flexible, but entirely free from backlash. 1 1/2 in. dia. x 3/4 in. wide. The bushes are drilled for 1/4 in. dia. spindles. Price 2/6.

Send 1/- in Stamps for GENERAL CATALOGUE. Please send S.A.E. with all enquiries. Trading terms for direct Postal Orders, C.W.O. plus appropriate postal charges.

STAND OFF INSULATORS, SOI.1-7.
Produced from Polystyrene Rod. This range of Insulators has many uses in radio equipment, particularly for v.h.f. as the losses are negligible. One hole fixing is provided by a 6, 4 or 2BA threaded stud in the face of the insulator.

SOI.1 1 1/2 in. x 1/2 in. dia. 1/2. SOI.2 1 1/2 in. x 1/2 in. dia. 1/3. SOI.3 2 1/2 in. x 1/2 in. dia. 1/4. SOI.4 3 1/2 in. x 1/2 in. dia. 1/5. SOI.5 1 1/2 in. x 1/2 in. dia. 1/11. SOI.6 3 in. x 1/2 in. dia. 2/6. SOI.7 6 1/2 in. x 1/2 in. dia. 3/8.

The following Insulating Materials are available:
Polystyrene ROD 3 1/2 in. dia., 1 1/2 per foot; 1 in. dia. 1 1/4 15 1/2 in. dia., 1/9; 3/4 in. dia., 2 1/2; 1/2 in. dia., 3/8.
SHEET: 1/2 in. thick, 24 in. per square inch; 3/16 in., 1 1/4; 1/8 in., 2 1/2; 1/4 in., 3d.
Ebonite Rod: 1/2 in. dia., 1 - per foot; 3/4 in. dia., 1/9; 7/16 in. dia., 2/3; 1/2 in. dia., 3/8.
Ebonite Tube: 1/2 in. o.d. x 1/2 in. i.d. 1/3 per foot.
Paxolin Tube: Square 1/2 in. x 1/2 in. x 1/32 in. wall, 3 - per foot. Round 1/2 in. o.d. x 7/16 in. i.d. 1, 3 per foot; 1/2 in. o.d. x 1/2 in. i.d. 2, 7; 1/2 in. o.d. x 1/2 in. i.d. 1, 5; 1/2 in. o.d. x 1/2 in. i.d. 4, 3; 1/2 in. o.d. x 1/2 in. i.d. 3, 1/2 in. i.d. 4, 3; 1 1/2 in. o.d. x 1 1/2 in. i.d. 4, 6.
Paxolin Sheet: 1/32 in. thick, 4/3 per square foot; 1/16 in., 4 -; 3/32 in., 7/3; 1/8 in., 8, 3; 1/4 in., 15 -.
Pres-diana Sheet: 1/16 in. thick, 3/8 - per square foot.

DENCO (CLACTON) LTD. (Dept. P.W.), 357/9 Old Road, Clacton-on-Sea, Essex

Stop Press: MAXI-Q PRE-SET FM TUNER, completely assembled, £12. VARIABLE VERSION, £11. COMBINED POWER PACK AND AMPLIFIER, £5/10/- or in comprehensive kit form £5.

Tel.: Mitcham 6201
Open Daily to Callers

RST

All Valves Brand New
and Fully Guaranteed

211, STREATHAM ROAD, MITCHAM, SURREY

SPECIAL 24 HOUR EXPRESS MAIL ORDER SERVICE

Z4	5/9	612	5	7105	21/5	12S27	15/6	80	9	6/D63	6	EC881	6	EZ40	8	KT55	15	6	PEN44	11	6	TH41	23	6	UCH42	10	-		
1A7	12/6	6CH6	7	7106	21/5	12Z3	15/6	85A2	15	-D77	5	EC882	9	EZ41	10	6	KT61	15	6	PEN4BA		TH22	12	6	UCH41	11	6		
1D5	15/6	6E30T	10	-7108	21/5	1487	14/6	14147	7	6/D52	5	EC883	9	EZ80	8	-	KT63	10	11	6	TP25	23	6	UCH42	13	6			
1D6	10/6	6F1	19	7117	8	19A05	9/-	1054A	15/9	DAC32	9	EC884	10	EZ81	8	-	KT66	17	6	PEN46	6	-	TH4	13	6				
1H3	10/6	6F1	19	7117	8	19B56G	17	10B56G		H8TH	23	6	DAP91	9	EC885	10	6	KT66	12	6	PL23	8	6	TH4	11	6			
1N3	9/9	6F12	8	787	12/7			21/-	61BT	15/-	DAP96	6	EC891	7	EC2	14	6	KT66	12	6	PL28	23	6	U22	7	6			
1R3	8/9	6F13	18	6	784	7	2011	14	6	61SPT	15/-	DF33	9/9	ECF89	12	6	FC13	14	6	KT66	12	6	PL28	16	6				
1S3	8/9	6F14	23	6	8103	8	2012	23	-621T	25/-	DF91	6	ECF82	12	6	FC13	14	6	KT66	12	6	PL28	16	6					
1T4	8/-	6F15	15	6	903W	18/9	20F2	23	6	180BT	30/-	DP92	6	ECF81	21/-	FW4	30/6	14	6	KT66	12	6	PL28	16	6				
1U5	10/6	6H6	3	40C1	18	-	20L4	23	6	303	8	DP96	9	ECF42	9	6	KT66	12	6	PL28	21	-	U37	22	6				
3A3	12/6	6J5GT	6	6	10C2	18	6	20F4	23	6	304	8	DP97	9	ECF35	12	6	FW4	30/6	14	6	PM2A	10	-	U50	8			
3Q4	10/6	6J6	7	6	10P1	23	6	20F4	23	6	305	8	DP96	9	ECF35	12	6	FW4	30/6	14	6	PM2L	10	-	U52	8			
3Q5	9/9	6J7GT	10	-	10P3	21	-	20F5	21	-	328	9	DP76	8	ECF50	12	6	GZ32	11	6	MH4	12	6	U76	8				
3S4	8/-	6K7GT	10	-	10P9	12	6	35A91	18	6	329	9	DP77	7	ECF52	13	6	H39	4	9	MH4	8	6	PM2A	18	6			
3V4	8/6	6K8GT	12	3	10L11	15	6	35L6CT	9	-	AC3 PEN	14	DP7	10	6	EP9	21	-	H63	10	-	MH4	18	6	PM2M	11	6		
5V40	8/6	6K25	19	6	10P13	21	-	25Y3	10	6	-	DP79	11	6	EP97A	10	3	HL92	11	6	MH4	12	6	U132	19	6			
5Y3GT	8/6	6L1	17	6	10P14	18	6	25Z4	9	-	AC3 PEN	15/-	DP79	11	6	EP97	7	6	HL13DD	MKT4	6	PM202	15	6	U191	18	6		
5Z40	10/-	6L6	7	6	11D3	23	-	25Z5	10/-	6	-	DP92	11	6	EP40	15	-	11	6	-	PM20	15	6	U191	18	6			
6A7	13/6	6L18	12	4	11D5	23	-	25Z6	9/-	6	AC3 PEN	15/-	DP96	9	EP41	9	6	FW4	35/0	14	6	PM24	15	6	U281	18	6		
6A8	10/-	6L19	21	-	12A3	6	6	30C1	12	6	-	DP96	9	EP42	12	-	12	-	MH4	10	-	PM24	15	6	U282	20	6		
6AK5	6/6	6L30L2	13	-	12A4H	10	-	30F5	12	6	ACHT	29	6	EL35	13	6	EP50(A)	4	6	1W1	30/0	14	6	U31	18	6			
6AL5	6/6	6L32D9	15	3	12A76	8	9	30FL1	12	6	ACHT	11	6	EL35	13	6	EP80	8	6	-	N19	8	-	PM20	18	6			
6AM6	6/6	6N7GT	8	-	12A77	8	9	30L1	11	6	ACHT	11	6	EL35	13	6	EP80	8	6	-	N19	8	-	PM20	18	6			
6AN5	5/-	6P1	16	-	12A77	8	9	30F4	23	6	-	DP96	9	EP86	12	6	EP50	12	6	EP50	12	6	U31	18	6				
6AQ5	7/6	6P25	18	6	12A77	8	9	30F4	23	6	ACHT	29	6	EL35	13	6	EP80	8	6	-	N19	8	-	PM20	18	6			
6AT6	7/6	6P28	23	6	12B46	8	9	30F16	10	6	ACV1	23	6	EAC80	9	6	EP91	8	6	KL52	N42	6	SP4	15	6				
6AT6	15/6	6Q7GT	20	6	12B46	8	9	35A5	10	6	ACV1	23	6	EAC91	10	-	EP92	9	-	14	6	N53	11	3	SP41	3	10		
6B8	4/3	6SA7GT	8	6	12J3GT	7	-	35L6CT	10	-	AC3 PEN	14	DP92	11	6	EL32	5	6	KL25	10	6	N150	10	-	SP42	12	6		
6B46	8/6	6S47	8	6	12J7GT	10	-	35V4	8	-	-	EB41	10	6	EL33	3	6	KL25	10	6	SP41	12	6	U31	18	6			
6B26	8/3	6S47	8	6	12K7GT	8	6	35Z3	10	-	AC3 PEN	14	DP92	11	6	EL37	21	-	KL22	10	6	N108	16	6	TH4	21	6		
6B48	21	6S47	8	6	12K7GT	8	6	35Z4	9	6	14	23	6	EP80	12	6	EP88	23	6	KL22	10	6	PL28	12	6	TH4	21	6	
6B46	7/6	6S47	8	6	12K8GT	3	5	35Z5	10	6	14	23	6	EP80	12	6	EP88	23	6	KL22	10	6	PL28	12	6	TH4	21	6	
6B47	12/-	6S47GT	7	-	12L	12	3	35Z6	10	6	14	23	6	EP80	12	6	EP88	23	6	KL22	10	6	PL28	12	6	TH4	21	6	
6B46	8/6	6S47GT	8	6	12Q7GT	8	6	39C0D6	8	6	14	23	6	EP80	12	6	EP88	23	6	KL22	10	6	PL28	12	6	TH4	21	6	
6B47	8/6	6T4GT	11	6	12S47	8	6	37	6	16	6	14	23	6	EP80	12	6	EP88	23	6	KL22	10	6	PL28	12	6	TH4	21	6
6B46	8/6	6T4GT	11	6	12S47	8	6	37	6	16	6	14	23	6	EP80	12	6	EP88	23	6	KL22	10	6	PL28	12	6	TH4	21	6
6B46	8/6	6T4GT	11	6	12S47	8	6	37	6	16	6	14	23	6	EP80	12	6	EP88	23	6	KL22	10	6	PL28	12	6	TH4	21	6
6B46	8/6	6T4GT	11	6	12S47	8	6	37	6	16	6	14	23	6	EP80	12	6	EP88	23	6	KL22	10	6	PL28	12	6	TH4	21	6
6B46	8/6	6T4GT	11	6	12S47	8	6	37	6	16	6	14	23	6	EP80	12	6	EP88	23	6	KL22	10	6	PL28	12	6	TH4	21	6
6B46	8/6	6T4GT	11	6	12S47	8	6	37	6	16	6	14	23	6	EP80	12	6	EP88	23	6	KL22	10	6	PL28	12	6	TH4	21	6
6B46	8/6	6T4GT	11	6	12S47	8	6	37	6	16	6	14	23	6	EP80	12	6	EP88	23	6	KL22	10	6	PL28	12	6	TH4	21	6
6B46	8/6	6T4GT	11	6	12S47	8	6	37	6	16	6	14	23	6	EP80	12	6	EP88	23	6	KL22	10	6	PL28	12	6	TH4	21	6
6B46	8/6	6T4GT	11	6	12S47	8	6	37	6	16	6	14	23	6	EP80	12	6	EP88	23	6	KL22	10	6	PL28	12	6	TH4	21	6
6B46	8/6	6T4GT	11	6	12S47	8	6	37	6	16	6	14	23	6	EP80	12	6	EP88	23	6	KL22	10	6	PL28	12	6	TH4	21	6
6B46	8/6	6T4GT	11	6	12S47	8	6	37	6	16	6	14	23	6	EP80	12	6	EP88	23	6	KL22	10	6	PL28	12	6	TH4	21	6
6B46	8/6	6T4GT	11	6	12S47	8	6	37	6	16	6	14	23	6	EP80	12	6	EP88	23	6	KL22	10	6	PL28	12	6	TH4	21	6
6B46	8/6	6T4GT	11	6	12S47	8	6	37	6	16	6	14	23	6	EP80	12	6	EP88	23	6	KL22	10	6	PL28	12	6	TH4	21	6
6B46	8/6	6T4GT	11	6	12S47	8	6	37	6	16	6	14	23	6	EP80	12	6	EP88	23	6	KL22	10	6	PL28	12	6	TH4	21	6
6B46	8/6	6T4GT	11	6	12S47	8	6	37	6	16	6	14	23	6	EP80	12	6	EP88	23	6	KL22	10	6	PL28	12	6	TH4	21	6
6B46	8/6	6T4GT	11	6	12S47	8	6	37	6	16	6																		

TRANSISTORS

in Practice

6.—R.F. AMPLIFICATION

By R. Hindle

(Continued from page 120, April issue)

THE tap is assumed to be midway along the coil and the two capacitors are assumed equal. Therefore there is no signal between the two centre-taps, capacitor and inductive. As the inductive tap is at zero (earth) signal potential the capacitor centre-tap must also be at zero signal potential and so no signal is fed back.

In practice, the exact inter-electrode capacitance cannot be accurately forecast because besides the valve itself, the base and the wiring all add to the feedback strays, but by providing a variable neutralising capacitor the correct value can be chosen by adjustment whilst setting up the receiver. It is clear from this argument that in actual fact the tap on the inductance need not be in the centre so long as the capacitors are so arranged as to have a like proportion. Under these conditions also the bridge can be balanced.

A tapped anode coil is not an essential. Phase reversal can be obtained by means of a secondary winding connected in the appropriate sense so that the required phase relationships are provided. This method of neutralising is given in Fig. 34. The neutralising capacitor size will be determined by the ratio of the transformer—if this were 1 : 1, of course, C_n would have to equal C_{ag} .

Neutralising Transistors

The same arguments apply to transistor circuits, but with one difference—the feedback through the transistor is not purely capacitive but has a resistive component also. For perfect cancellation, therefore, the neutralising feedback loop should also consist of a resistance and a capacitance. The circuit is in Fig. 35 where the transistor internal feedback path is shown dotted and outside the transistor as C_{cb} and R_{cb} .

But of course, the practical man is not necessarily a perfectionist. All that he wants is to prevent instability and this he can do by feeding

back through the neutralising circuit a signal that is not necessarily exactly anti-phased to the feedback via the stray path internal to the transistor provided that it has a component that reduces the effective feedback to below the level of instability. The neutralising components, therefore, are not so critical as it seemed at first glance. It is quite common, in fact, for the resistive part of the feedback to be ignored and a capacitance only to be included in the neutralising circuit. Nor is the value of this component very critical under most circumstances. Some degree of positive feedback, so long as it is below the value that would cause instability or distortion does, in fact, increase the sensitivity of the circuit.

There are benefits to be derived from complete neutralisation (referred to as "unilateralisation" because by this means the transistor is made into a device that effectively conducts only in one direction). In particular, by eliminating the resistive feedback the interdependence of input and output resistances, a complicating factor in transistor design work, is avoided and the more highly developed theoretical considerations are similarly simplified. But to set up such a condition is not an easy matter for the home constructor to face and he will generally take the easier way out by selecting a feedback condition that prevents instability without aiming at theoretical perfection. Indeed, the internal feedback that causes this trouble, being a characteristic of the transistor itself, and transistor characteristic spreads being what they are, the circuit could be completely unilateralised for only one transistor, and a replacement transistor is unlikely to have the same constants.

In fact, in practice, transistors commonly used at present do not appear to be at all critical regarding the exact values of neutralising components used and commonly published designs for home construction specify fixed components rather than the variables that the experimenter in earlier valve days used to adjust with such care.

It should be pointed out that it is not sufficient just to avoid the point of instability. Before the circuit goes unstable there will be a degree of distortion and so some margin of safety should be allowed for.

At this point practical experience in transistor

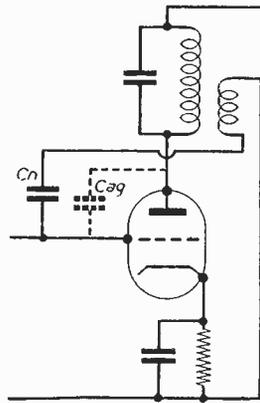


Fig. 34.—The transformer neutralising circuit.

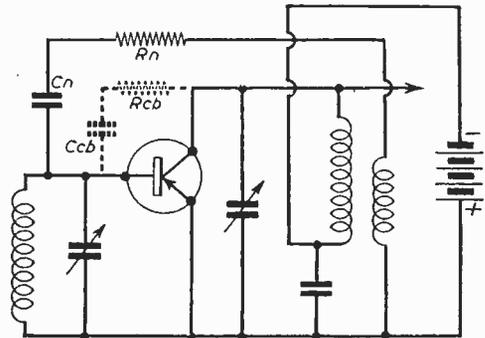



Fig. 35.—The neutralised transistor stage.

R.F. amplification is sought and so a stage of tuned R.F. will now be added to our experimental transistor receiver.

An R.F. Stage

Fig. 36 gives the circuit for the R.F. stage. L2 is the coil used previously for the regenerative stage but, as will be seen from the circuit, the secondary winding that was used previously for the regenerative feedback is now used for the neutralising feedback across the R.F. stage. The first move, therefore, is to disconnect the wiring previously going to this winding and to complete the collector wiring of the detector transistor without this winding as shown in Fig. 36. In effect connecting together the two points that previously were connected to the two ends of the feedback coil. Another change is to break the connection from the bottom end of the tuned winding of this coil, which was previously connected to earth, to connect C5 which is .01 μ F from this end of the coil to earth and also to connect the same end of this coil to the negative battery supply. The collector of the R.F. transistor will be connected to the upper end of the tuned winding of this coil in due course and will receive its current via the coil, which thus forms the collector load.

The R.F. stage is built up on a small aluminium sub-chassis cut from a piece of thin aluminium to the shape and dimensions given in Fig. 37. Before drilling this chassis it will be as well to check that the positions of the holes are right for the components to be used. The two holes marked "x" are intended to take small tag strips, each with one tag plus earth, and it is these that might vary because such tag strips do vary in size. When mounted, these strips should lie $\frac{1}{8}$ in. from the edges of the chassis, one along the inside top of the chassis and the other along the outside bottom of the chassis. The wiring diagram will clarify this instruction.

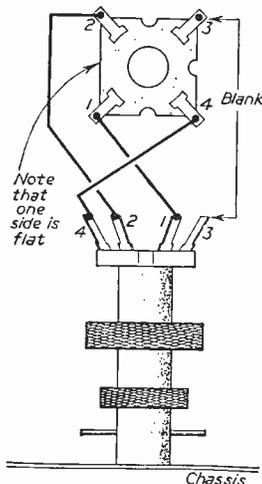

This additional illustration clarifies the connections to the coil shown in Fig. 29a of the March issue.

The chassis, which in the flat should look like the drawing in Fig. 37, should be folded so that the surface as drawn is inside and the corner along line "a" is square. The two fixing flanges at the bottom are then bent square with the walls of the chassis so that the shorter one on the $1\frac{1}{2}$ in. side bends outwards and the longer one ($1\frac{1}{2}$ in.) inwards as in Fig. 37 (b). This should now be placed on to the main chassis to occupy the corner between the front panel and the regenerative coil already mounted. This sub-chassis should fit flush with the front panel and should enclose the hole through which the lead from the half of the tuning capacitor not previously used passes. Holes are then marked and drilled in the main chassis to coincide with the holes on the R.F. sub-chassis. For this purpose the tuning capacitor should be disconnected and removed, and preferably it should be left off until later on when the sub-chassis is screwed on to the main chassis.

Having thus prepared the main chassis, the R.F. stage can be constructed and this is done before mounting the sub-chassis on to the main chassis. Up to now in this series the soldering in to the circuit of transistors has been avoided, but now with an R.F. stage liberties can no longer be taken or instability will result, so this is the point at which the soldering-in technique is to be adopted. The warnings previously given, however, with regard to the avoidance of damage to the transistors by the application of heat from the soldering iron has to be heeded and, in fact, the transistor is the last component to be wired to the sub-chassis. The two soldering tag strips are provided as convenient points to which the transistor leads can be soldered. The hole alongside the mounting hole for the tag strip at the top of the sub-chassis is to take the base lead to the circuit inside the sub-chassis.

The coil is mounted in the $5/16$ in. fixing hole, with the coil itself projecting into the inside of the chassis. The R.F. chassis thus forms the screen round this coil, which is also in this way mounted at right angles to the other coil, so

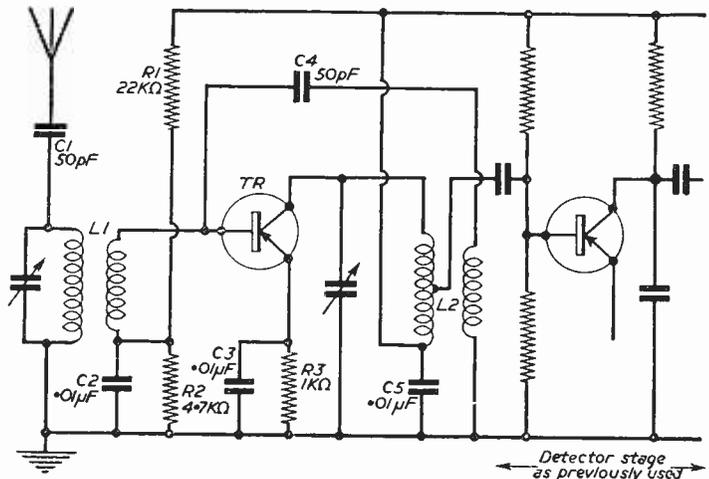


Fig. 36.—Circuit of the R.F. stage.

reducing coupling between coils to negligible proportions.

Wiring

The wiring of the sub-chassis can now proceed according to Fig. 38. The components mounted on the outside tag strip have to be so placed that they will fit into the space available underneath the coil on the main chassis and so, before doing this part of the wiring, it will be as well to try the sub-chassis in position so as to see what space is available. Miniature components must, of course, be used for a chassis of this size. Inside the sub-chassis the coil can be connected up. Four connections will be left for attention after the mounting of the sub-chassis, i.e., C1 to

again inside the sub-chassis area. A very convenient way, and that adopted on the prototype for first testing, was not to wire C1 on to the coil as shown in Fig. 38, but instead to solder it to the tag on the appropriate half of the tuning capacitor above the main chassis and to connect the aerial lead directly on to the other end of C1.

It is assumed that the tuning capacitor used is fitted with trimmers. If this is not so it will be necessary to mount two trimmers alongside the main tuning capacitor above the chassis. These are necessary, now that two stages are to be tuned, and the procedure is similar to that adopted when setting up a valve receiver, except that no

tuning scale has been used and so there is not the need to tune up to the calibrations determined by such a dial. A signal at the upper end of the tuning range is used first, and the coil cores adjusted for maximum signal; then a signal in the lower half of the wave-band is used and the trimmers adjusted for maximum signal. These two processes proceed alternately until satisfied that the best results are being obtained. It would be a useful refinement if one of the small reduction drive units were fitted to the tuning capacitor spindle to aid tuning. In the absence of signal in the earlier

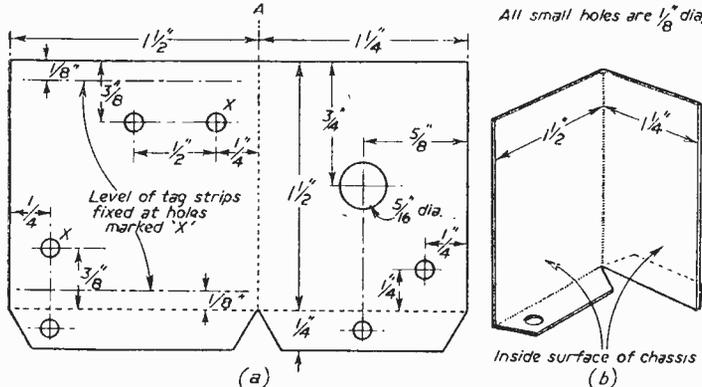


Fig. 37.—Details of the chassis for the R.F. stage.

the aerial input. C4 to the neutralising winding, the lead from the coil to the tuning capacitor and the lead from R1 to the battery negative lead tag. Finally the transistor itself can be fixed. This is held in place outside the sub-chassis by its wires and as these are soldered they must be held in the jaws of a pair of small pliers which will act as a heat shunt. The pliers must be in contact with the wires and not merely with sleeving, of course, but sleeving must be used, short enough to leave room for the pliers but yet in such a position to prevent short circuiting of the leads. The base lead passes through the hole in the sub-chassis to be soldered to the tag as shown in the wiring diagram, and this connection is first made. Then the emitter lead is soldered to the outside tag strip. The collector connection goes direct to the second coil, and so this connection has to be left until the sub-chassis is in position.

It will be unsatisfactory to take the aerial lead from inside the sub-chassis to the socket previously used for this purpose at the rear of the main chassis alongside the second coil. Consequently a separate socket should be mounted either on the front panel inside the sub-chassis area, or on a bracket placed at the side of the chassis,

stages it will be found that as the circuits come into tune there is a slight rushing noise in the earphones.

LIST OF PARTS FOR R.F. STAGE	
C1—50 pF	R1—22 K Ω
C2—.01 μ F	R2—4.7 K Ω
C3—.01 μ F	R3—1 K Ω
C4—50 pF	TR—Golpet V6/R8
C5—.01 μ F	L1—Osmor
	L2—Osmor (as used for regenerative Detector.)

Components unspecified are as used in earlier parts of the design.

(To be Continued)

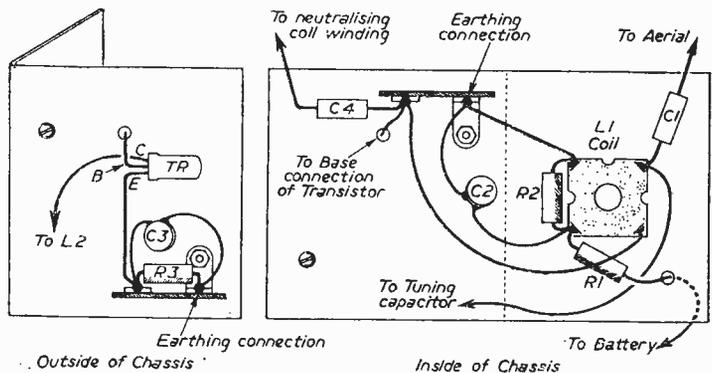


Fig. 38.—Wiring diagram of the R.F. stage.

Re-Converting the R.D.F.1

HOW TO MODIFY THIS POPULAR EX-GOVERNMENT RECEIVER FROM TV TO F.M. USE

By A. Sydenham

ANYONE who purchased the ex-Government R.D.F.1 unit for conversion to TV and who now has it lying idle will find that it is possible to modify the chassis as a F.M. receiver, complete with front end, four stagger-tuned I.F. stages (two of which may be limiters), two audio stages, power supply. By utilising

I.F. strip. Small modifications are required here which include building up the discriminator section.

The remainder of the diagram shows that part which must be built but as the power supply and audio sections—V10, V11, V12—occupy the

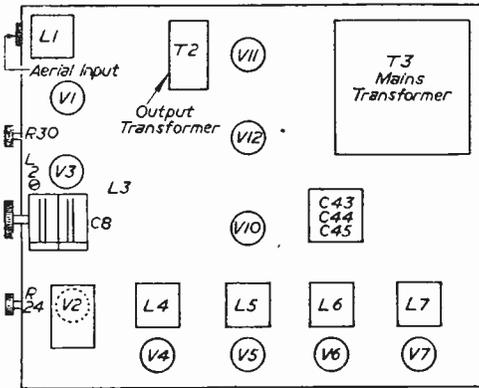


Fig. 2 (a).—Top of chassis layout.

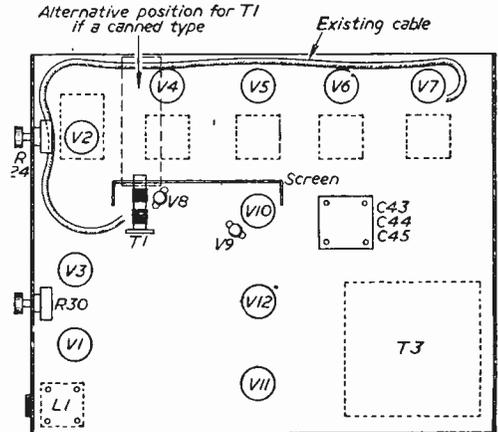


Fig. 2 (b).—Underside of chassis.

most of the original material, expense is kept small and a self-contained receiver results which works surprisingly well despite the fact that the first three valves are operating well above their recommended working frequencies.

The circuit is illustrated in Fig. 1, which, although looking forbidding at first, is not so, most of it being already in existence, the main section of the diagram comprising the original

positions occupied by the previous supply, plus the fact that the "front end"—V1, V2, V3—stands in front of it, there is little complication or need for drilling.

Modifications

First strip all components from the chassis except the actual I.F. strip and its wiring, which

LIST OF COMPONENTS

NOTE.—The majority of the components associated with valves 2, 4, 5, 6, 7, are already in position. Additional capacitors of some 500 pF might also be found connected across the screen decoupling capacitors and these may be left in place.

Capacitors

C1, C34—3 pF.
C2, C3, C5, C9, C16, C18, C20, C23, C28, C31, C32, C39, C40, C42—0.01 μ F.
C6, C12—100 pF.
C4, C7, C10, C13, C15, C17, C22, C27, C29, C30, C35—50 pF.
C8—20 pF. twin gang.
C11—1 pF.
C14—30 pF. trimmer.
C19, C21, C26—200 pF.
C24, C38—2,000 pF.

C25—500 pF.
C33—10 pF.
C36—4 μ F.
C37—300 pF.
C41—50 μ F.
C43, C44, C45— $8 \times 8 \times 8 \mu$ F.

Resistors

R1—2 K.
R2, R5, R21, R31—5 K Ω .
R3, R11, R13, R27—100 Ω .
R4, R6, R14—100 K Ω .
R7, R19—50 K Ω .
R8, R9, R12, R16, R17—1 K Ω .
R10, R18, R32—27 Ω .
R15, R20—47 K Ω .
R22—68 Ω .
R23—22 K Ω .

R24—1 M Ω pot.
R25—20 K Ω .
R26—3.3 M Ω .
R28—470 K Ω .
R29—270 Ω .
R30—50 K Ω pot.
R33—68 Ω , 5 watt.

Valves

V1-V7—SP61.
V8, V9—EA50.
V10—EC52.
V11—6V6.
V12—5V4.
T3—mains input. Output :
250-0-250 v. at 100 mA,
6.3 v. at 6 amps, 5 v. at
2 amps.
T2—To match 6V6 to LS.
LFC—10 Henries, 100 mA.

leave intact. Mount components as illustrated removing the EA50 diode valvholder at the rear of the chassis and re-fixing it underneath in front of the EC52 valvholder. (A position will be found where fixing holes already exist.)

Wind L1, L2, L3 and T1 as given in the table. (Note: A commercially made transformer may be used for T1 if desired, in which case it must be mounted horizontally across the I.F. strip—see diagram.) Mount these coils, then remove all I.F. transformer cans and strip off the windings, removing at the same time any parallel-connected damping resistors. The valve in the first can—the large one—becomes the mixer, but the coil former is not used. In can 2 remove the H.F. choke at the bottom. Solder an end of 36 s.w.g. d.s.c. wire to one of the tags previously associated with the choke, then wind 20 turns on to the coil former, soldering the end to the other tag from which the choke was freed. This coil is L4 (a). Cover winding with a single layer of tape then wind an identical coil on top, connecting its ends to the original coil tags. This is L4 (b). Wind 20 turns of the same wire on each of the remaining coil formers, connecting the ends to the respective tags. In can 4 cut the chassis return lead (black wire) and insert R14. C27. In can 5 remove the diode cathode and insert R19, C30. Connect a valve top-cap and lead to upper end of L7. Replace all cans.

Below chassis remove the 5,000 Ω potentiometer associated with the I.F. strip, also remove bias resistors from the first, fourth and fifth valvholders in the strip, connecting the freed pins to chassis.

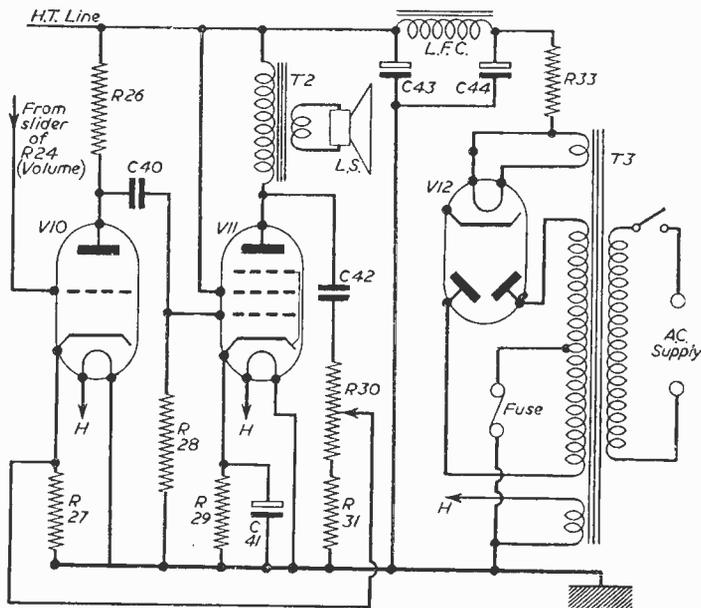


Fig. 1 (c).—Power and audio section.

Disconnect R15 (originally 2.2 K Ω) which lies across the underside of the can and solder in a new resistor of 47 K Ω . Solder the length of screened cable which runs at the side of the strip to pin 3, V7, at one end and to T1 at the other. Modify the screen and anode feeds to conform to those specified. Wire up remainder of circuit

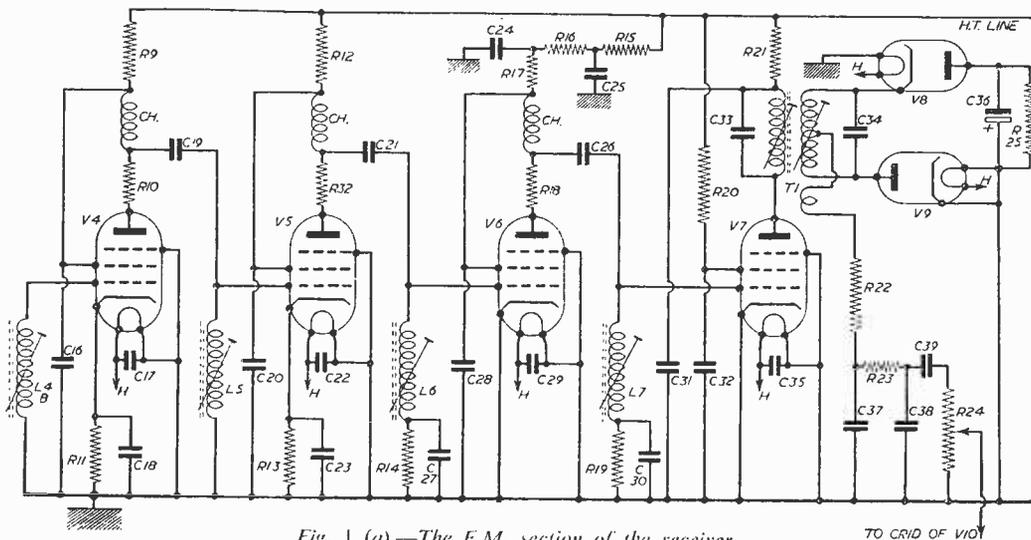


Fig. 1 (a).—The F.M. section of the receiver.

TO GRID OF V10

keeping all leads associated with valves 1, 2, 3 as short and direct as possible even at the expense of tidiness. Electrolytics C43, C44, C45 are parts of the existing block.

Testing the Set

This completes the receiver. Valves may now be inserted. routine tests made for H.T. shorts, etc., and the receiver switched on.

I.F. alignment should be carried out with a signal generator but subsequent "front end" alignment may be made on the signal and for

R.C.A. Junction Transistor

THE 2N404 is a junction transistor of the germanium p-n-p alloy type. It is specifically designed for use in switching circuits of compact, medium-speed military and industrial electronic computers. This transistor is also useful in other low-level, medium-speed "on-off" control circuits.

The 2N404 features a maximum collector-to-emitter saturation voltage of -150 millivolts at a current gain of 30, a maximum collector cut-off current of -5 ua at 25°C and -90 ua at 80°C, and a minimum alpha cut-off frequency of 4 megacycles per second. These features permit the design of electronic computers having exceptional stability over wide variations in temperature.

Careful control of the characteristics of this transistor with respect to saturation current, leakage current, breakdown voltage, and switching time contribute to the

dependable performance of the 2N404 in critical military and industrial computer applications.

The 2N404 is hermetically sealed in a metal case. Its maximum diameter is 0.360in. and its maximum body length is 0.250in.—R.C.A., Gt. Britain Ltd., Lincoln Way, Windmill Road, Sunbury-on-Thames, Middx.

COIL CHART

Coil	Turns	Wire (s.w.g.)	Former (dia. in.)	Remarks
L1	Primary 2 Secondary 4½	22 22 enam.	0.3 0.3	P.V.C. covered over sec. } Spaced wire thickness } canned
L2	4½	28 enam.	3/8	
L3	3½	28 enam.	3/8	Spaced twice wire thickness
L4-7	See Text			
T1	Primary 28 Secondary 15+15	28 enam. 28 enam.	0.3	Closewound Bifilar, spaced ⅛ in. from primary
	Tertiary 10 (see text)	28 enam.		Over primary—remotest end from sec.

this a dual tuning wand will be found a useful accessory.

Broader Tuning

In the I.F. strip, fixed resistors, value 6.8 to 10 KΩ may be connected across the coils to broaden the bandwidth if necessary.

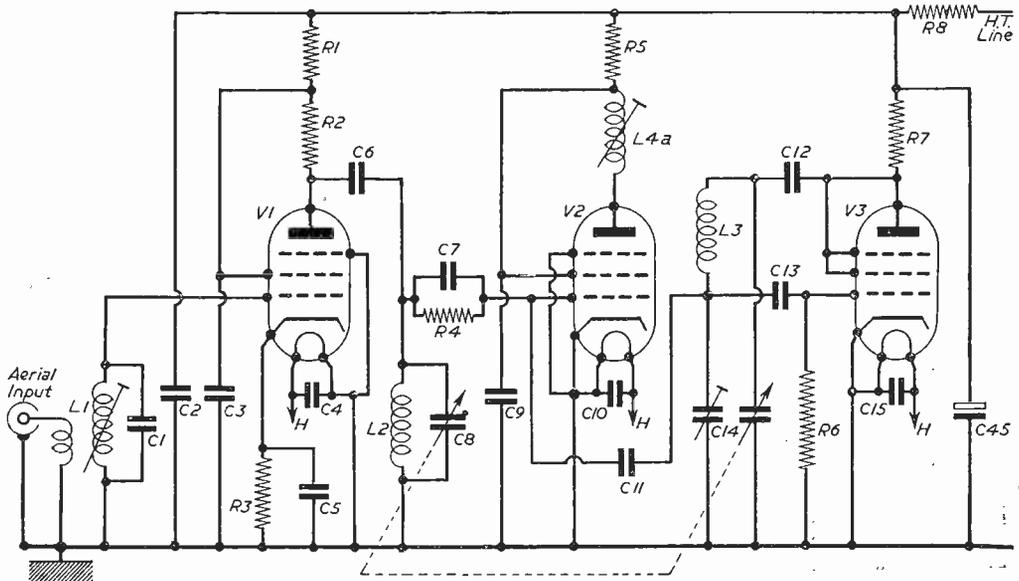


Fig. 1 (b).—The A.M. section of the converted R.D.F.1.

NEW 1958 EDITION

COLOSSAL VALUE!

OVER

2000 POPULAR MODELS

NEWNES

Radio and Television Servicing

Claim yours now

7 Days' FREE Examination

6 VOLUMES

OVER

3,600

CIRCUIT, COMPONENT & CHASSIS DIAGRAMS

3,500 PAGES

PLUS

2 YEARS' POSTAL ADVISORY SERVICE

★ **FREE** ★
Handy Enlarger

Just what you need to follow intricate circuits easily—magnifies small print, too. Sent boxed with lens polisher.

TELEVISION AND RADIOMEN— this is your opportunity to possess the biggest money-maker in radio. Here, ready for immediate use, are over 3,600 circuit, component and layout diagrams—TV receivers and converters from single-station sets to the latest 13-channel *printed-circuit* models: radios, radiograms, portables, car radios, record-reproducers, including transistor and VHF/FM models. And in addition—LARGE QUICK-REF FOLD-OUT CHARTS and Valve & Picture-Tube Data. It's yours FREE for 7 days—Hurry, send the coupon to-day!

TELEVISION SERVICING DATA for—

Acc. Alba, Ambassador, Argosy, Baird, Banner, Beethoven, Brayhead, Bush, Champion, Cossor, Decca, Defiant, Ekco, E.M.I., English Electric, Ferguson, Ferranti, G.E.C., H.M.V., Incivta, K-B, McCarthy, McMichael, Marconiphone, Masteradio, Murphy, Pam, Peto Scott, Philco, Philips, Pilot, Portadyne, Pye, Rainbow, Raymond, Regentone, R.G.D., Sobell, Spencer-West, Stella, Strad, Ultra, Valradio, Vidor, White-Ibbotson.

RADIO SERVICING DATA for—

Acc. Alba, Ambassador, Argosy, Armstrong, Banner, Beethoven, Berc, Bush, Champion, Cossor, Decca, Defiant, Eddystone, Ekco, Ever Ready, Ferguson, Ferranti, G.E.C., Grundig, H.M.V., Invicta, K-B, McCarthy, McMichael, Marconiphone, Masteradio, Motorola, Murphy, Pam, Peto Scott, Philco, Philips, Pilot, Portadyne, Pye, Pye Telecommunications, Radiomobile, Raymond, Regentone, R.G.D., Roberts' Radio, Sobell, Stella, Strad, Ultra, Vidor, Webcor.



"One glance only was enough to convince me of its worth" (J. F. B. Leicester).
"A boon and a must" (J. S. Manchester).
"Has more than repaid the cost in a short period" (E. J. S. Wolverote).

ACT NOW

George Newnes, Ltd., 66-69 Great Queen Street, London, W.C.99.
Send RADIO & T.V. SERVICING without obligation to purchase. I will return it in 8 days or send 10/- deposit 8 days after delivery, and you will then send the ENLARGER. Thereafter I will send twenty monthly subscriptions of 10/- paying £10 10s. 0d. in all. Cash price in 8 days £10.

NAME


ADDRESS

OCCUPATION

YOUR SIGNATURE (Or your Parent's Signature if under 21)

Place X where it applies
HouseOWNER
Householder
Living with Parents
Lodging Address

RV2

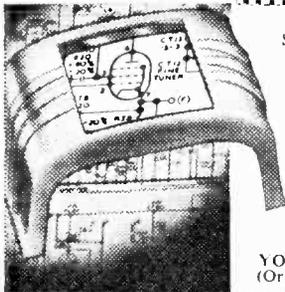

**LASKY'S
RADIO**



**COLLARO
4-SPEED MIXER AUTO-CHANGERS**

Incorporating auto and manual control. Complete with Studio crystal p.u. and sapphire stylus.

R.C. 456. List £13.17.0.

Lasky's Price **£7.19.6.**

Latest R.C. 457 (Continental), £8.19.6. Post on either of above, 3/6.

COLLARO 4-SPEED SINGLE PLAYERS

"Junior," Motor and separate crystal p.u., **92/6** Post Free.

Motor only, **59/6**, post 2/6.


Pick-up only, **29/6**, post 2/6.

4/564, 4-spd. Single Player Unit with Studio crystal p.u. **£6.19.6.** Carr. 5/-.

**GREATEST OFFER OF
4-SPEED MIXER AUTO-
CHANGERS EVER MADE!**

THE STARR GALAXY

**LISTED AT £12
LASKY'S PRICE 79/6**

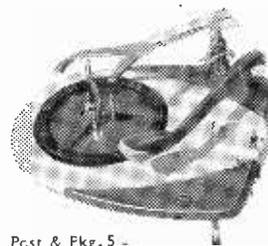

Post & Pkg. 5/-

Brand new and unused in makers' original cartons. Modern design, smart duo-tone finish, complete with crystal p.u. with styli. Incorporates auto and manual control. For A.C. 200-250 v. Send for this great bargain at **ONE THIRD LIST PRICE!**

AMAZING OFFER OF RECORDING TAPE

P.V.C. Magnetic Recording Tape on latest type plastic spools. Famous make, brand new, perfect and boxed. Will work with any Recorder. Limited quantity only. Send now. Satisfaction or Money Back Guaranteed.

LASKY'S PRICE

1,200ft. Standard on 7in. spool.	List 35/-	21/-
850ft. Standard on 5½in. Continental spool.	List 28/-	16/6
600ft. Standard on 5in. spool.	List 21/-	12/6
1,200ft. Long Play on 5½in. Continental spool.	List 35/-	22/6
850ft. Long Play on 5in. spool.	List 28/-	16/6

Post: 1 spool, 1/6. 3 or more post free.

LASKY'S (HARROW ROAD) LTD.

42, TOTTENHAM COURT ROAD, W.1.

Telephone: MUSEum 2605.

370, HARROW ROAD, PADDINGTON, W.9.

LAD 4075 and CUN 1979.

Open all day SATURDAY. Half-day Thursday.

PLEASE ADDRESS ALL MAIL ORDERS TO HARROW ROAD.

**Train for a wonderful future in
ELECTRONICS...**

Every day the demand for the expert in electronics grows. Radio, television, radar and the whole field of industrial automation are rapidly expanding and the trained specialist assures for himself a well-paid career in this quickly developing profession. Here is your opportunity to enter for:-

3 YEAR COURSE TELECOMMUNICATIONS - Entrance standard G.C.E. Ordinary level or equivalent. This course trains students to become Assistant Development Engineers. It covers the City and Guilds' Full Technological Certificate in Telecommunications Engineering. It also includes theoretical and practical instruction on Computers (Digital and Analogue), Process Control and Automation. Next course commences September 9th, 1958.

1 YEAR COURSE Full-time day course in the Principles and Practice of Radio and Television. Designed for the training of Radio and Television Servicing Engineers and others similarly engaged in the Electronics industry. Next course commences May 28th, 1958; others in September and January.

The E.M.I. College of Electronics, Dept. 32, 10 Pembridge Square, London, W.2. Telephone: Bayswater 5131.2
The College is part of E.M.I. Group... Britain's foremost electronic engineers... Pioneers of the world's first public Television Service.

**THE E.M.I. COLLEGE
OF ELECTRONICS**




Converting the 19 Set

HOW TO MODIFY THIS POPULAR EX-ARMY RECEIVER FOR AMATEUR USE

By K. E. Marcus

(Continued from page 105 April issue)

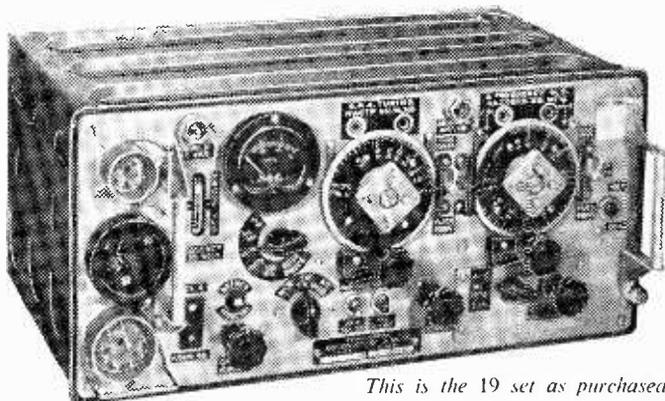

This is the 19 set as purchased.

CONTINUING the modification of range coverage, which is the eighth phase. (F) Reconnect C10E to tag 5 of L21 and C10F to tag 5 of L6 (refer to Fig. 1).

(G) Fix 50 pF trimmers to the following coils: (1) L22 instead of C10.1A (10 pF). (2) L7 between lug 5 (bottom lug leading to range switch S11A, segment 2) and earth. (3) L4 between lug 5 (bottom lug leading to range switch S11A, segment 4) and earth.

(H) From four-gang condenser remove in each section carefully six plates from the rotor and five plates of the stator. This reduces the maximum capacity from 470 pF to 253 pF. Thereafter, bring all the four trimmers on the gang to minimum capacity.

(I) Between range-switch S11A, segment 6 and the grid of the mixer, there is a capacitor C5A (0.1 μF) in parallel with a resistor R42A (10 KΩ). Remove these and join grid line and gang directly to segment 6.

The set should next be re-tested. It will cover now, on the low range 3.3—7.4 Mc/s, on the high range 7.0—15.5 Mc/s. But it is not time yet for realignment.

Ninth Phase (B.F.O. and Meter)

This part of the conversion concerns itself with the B.F.O. and the meter.

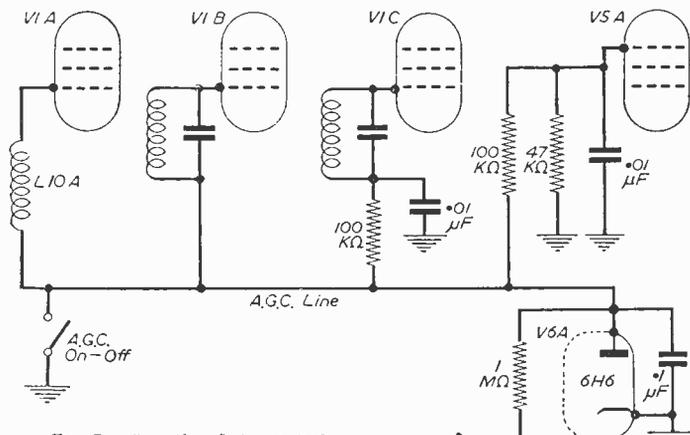


Fig. 7.—Details of the A.G.C. arrangements.

(A) Remove the B.F.O. coil from its can, unsolder all components and unwind the coil.

(B) Mount 4 Perspex 1/32in. thick washers 1in. dia. close fitting to the coil former, space them 1/4in. apart, thus creating 3 winding chambers, and fix them with dope.

(C) Wind 75 turns of the salvaged Litz wire into each chamber and connect up according to Fig. 8.

(D) Drill holes into the can for the leads to B.F.O. valve—grid (A) and to het. control (B). Mark connections C and D on the base plate of the coil unit and reassemble it into the can.

(E) Fit the B.F.O. assembly back into the set and finish wiring up the detector—B.F.O. valve according to Fig. 8.

(F) Use the old B-set tuning condenser as het. tone control. Bend one starter plate in such a way that it shorts to the rotor at full mesh. In this way the het. tone control works as a B.F.O. on/off switch when brought to full mesh.

(G) There was a lead running from the cathode of V1B (1st I.F. amplifier) to the meter switch. This lead is taken through a hole in the chassis to the meter, and connected to its positive terminal via a resistor 27KΩ, according to Fig. 9.

This meter will now give the tuning indication.

Final Remarks and Alignment

The conversion is now completed and it is advisable to go again round all parts of the set to remove all surplus wiring and components before alignment is begun.

As the set is highly sensitive an output meter and a signal generator are essential. The output meter is set to 600Ω

impedance and plugged into the 600Ω line jack. The injection of the generator signal is through a parallel combination of a resistor 100KΩ and a

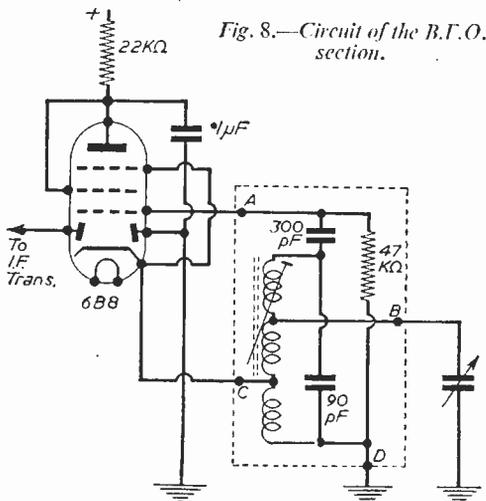


Fig. 8.—Circuit of the B.F.O. section.

capacitor 0.01μF into the grid of the valves, without taking off the grid leads. All screening cans should be in position.

The alignment is done with A.G.C. on, B.F.O. off, audio gain control full on, R.F. gain control full on.

The I.F. is 465 Kc/s. The sensitivity expected for 50 mW out is 50μV into the mixer grid. The I.F. curve should be checked for equal skirts at 6db down and 20db down. The bandwidth at 6db down should not be less than 6 Kc/s.

News from the Clubs

BURY RADIO SOCIETY

Hon. Sec.: Mr. L. Robinson, 56, Avondale Ave., Bury, Lanes. THE above society holds its meetings at the George Hotel, Kay Gardens, Bury, at 8 p.m. on the second Tuesday of each month.

Forthcoming meetings: April 8th, a lecture by Mr. H. Whalley (G2HW), subject to be announced later. May 13th, Technical Forum: "Aerials."

CRAY VALLEY RADIO CLUB

Hon. Sec.: S. W. Coursey (G3JJC), 49, Dulverton Road, New Eltham, London, S.E.9.

AT the meeting of the Cray Valley Radio Club, to be held at 8.0 p.m. Tuesday, April 22nd, 1958, at the Station Hotel, Sidecup, Kent, Mr. C. Burgess will give a talk entitled "Some Aspects of Directional Aerial Design." Visitors welcome.

SCIENCE MUSEUM RADIO SOCIETY

Hon. Sec.: G. C. Voller.

THE 1957-8 session of lectures comes to an end on April 15th, when the British Amateur Television Club will give a demonstration of Amateur Television. This meeting will be open to non members, who are requested to make prior arrangements with the Secretary, Mr. G. C. Voller. Ken: 6371, ex 237.

NORTHAMPTON SHORT WAVE RADIO CLUB (G3GW)

Hon. Sec.: S. J. Berridge (G3JTW), 20, Ethel Street Northampton.

THE Club now has 22 members, 11 of whom are licensed amateurs. At the close of the winter programme, which included five recorded lectures and two film shows, the committee would like to express its thanks in this column to those who gave so much assistance, particularly to Roy Goode (G3GJU),

After bringing back the signal generator to I.F.-middle the modulation should be switched off and the hct. tone control moved just out of

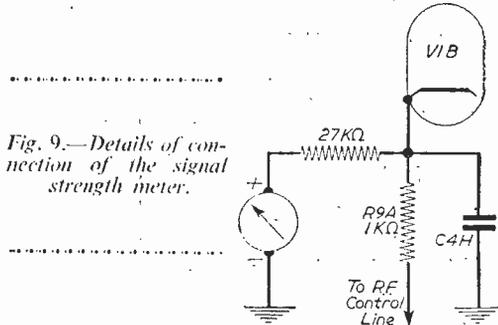


Fig. 9.—Details of connection of the signal strength meter.

mesh. The B.F.O. coil should now be aligned to zero beat, so that a further moving of the hct. control produces a rising beat note.

The oscillator tracking and the R.F.-alignment follows the usual practice. This will require some "wire pulling" at the low frequency end of each range. A "magic wand" (dust iron one end, brass the other) will prove useful for determining whether to "push" or to "pull." On the high frequency end of each range it is all trimming.

The lower range should be aligned first. Trimming to be done underneath the chassis. Only if one of these trimmers does not "reach" use should be made of the corresponding gang trimmer.

The sensitivity expected for 50 mW out is 3μV into the aerial on all frequencies. The R.F. alignment should be repeated if one end of the range is less sensitive than the other.

for the loan of his tape-recorder and to Jim Robinson (G3IAI) for the use of his services, films and projecting equipment. With the opening of the summer season prospective new members are invited to contact the Hon. Sec. at the above address for details of proposed Club activities which are now in process of being arranged.

LEICESTER RADIO SOCIETY

Hon. Sec.: P. G. Goadby (G3MCP), 535, Welford Road, Leicester.

THE following are fixtures for April:—

14th: Symposium on the "Cub" by G3MCP.

21st: Free night (work on new clubroom, etc.).

28th: Aerials by G2FCF.

The club meets every Monday at H.Q. as above at 7.30 p.m.

CLIFTON AMATEUR RADIO SOCIETY

Hon. Sec.: C. H. Bullivant G3DIC, 25, St. Fillans Road, Catford, S.E.6.

THE highlight of the February meetings was on Friday, February 21st, when members heard a most interesting talk by P. Horwood, G3FRB, on "Receiver Alignment." In covering R.F. and I.F. amplifiers, and crystal filters, Mr. Horwood gave many useful tips to improve the performance of communication receivers. A further talk has been promised when it is hoped to cover other stages of receivers and give details of "S" meter circuits.


Programme for April:

11th: "K.W. Products for the Amateur," by R. Shears, G8KW.

18th: Constructional Evening and Ragchew.

25th: "Direction Finding," by C. Hatfull, G3HZI.

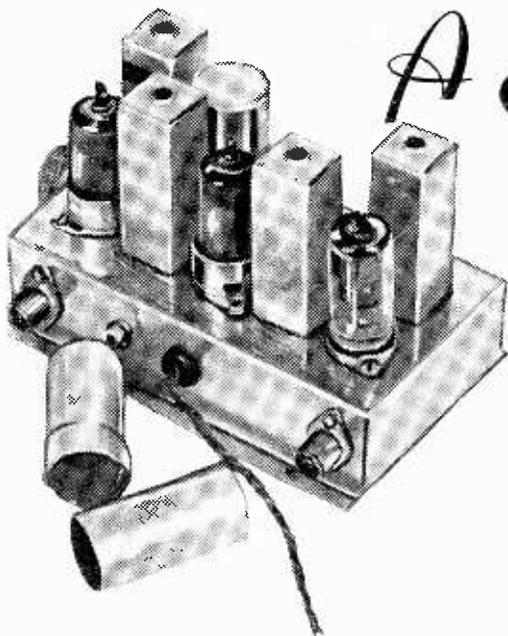Meetings are held every Friday at 7.30 p.m., at the clubrooms, 225, New Cross Road, London, S.E.14, when new members and visitors will receive a warm welcome.



A Switched FM Tuner

A HIGH-QUALITY TUNER WITH "DIOMATIC" FREQUENCY CONTROL
By P. Michael

Circuit Description

1. Earthed grid R.F. stage, V1A.

By using a triode in this position in place of the more usual pentode, a very much lower noise factor for the receiver has been obtained as well as a simplified circuit. There is, however, a disadvantage that modulation hum may appear unless heater chokes are used. These are rather bulky, so ferrite beads have been used with very great success in removing this bugbear of earthed grid circuits. The signal developed across L1 is injected into the cathode and appears at the anode after amplification. It is unnecessary to tune L1 accurately, as it is damped by the very low impedance of the cathode. L2, however, is not so damped and is consequently tuned to the centre station to ensure a similar level on all three stations.

2. The frequency changer, V1B.

Experience has shown that in general, conventional mixers are not so efficient at V.H.F. as self-mixing oscillators. The circuit is of an electron-coupled Hartley oscillator working as a multiplicative mixer. It is essential for correct oscillator operation that C4 is wired as shown.

3. The I.F. amplifier, V2A.

The cathode of this stage is directly earthed. Grid bias is produced by grid current flowing in the 470K ohm grid resistor. This provides a degree of A.G.C. which is not essential on V.H.F. receivers as the following stage provides complete limiting.

SEVERAL units for the reception of the V.H.F. transmission have been described in these pages, but so far none has the facility of station switching as opposed to station tuning with the aid of a magic eye or by ear.

The advantages of switching are obvious, but unfortunately it is impossible simply to substitute a switch for the tuning condenser, as the very real problem of oscillator drift raises its ugly head. To combat this problem a compensating device of one form or another has to be fitted. Usually this takes the form of a reactance valve such as has been described in these pages quite recently. By using the new circuitry of "Diomatic" frequency control, a control about ten times as effective as a reactance valve is possible.

As may be seen from the diagram the circuit is unusual but very simple, compactness having been obtained by employing double valves throughout and by using midget construction principles.

LIST OF COMPONENTS

R1—220Ω
R2—1.5 K.
R3—22 K.
R4—1.5 K.
R5—470 K.
R6—47 K.
R7—10 K. 1 W.
R8—47 K.
R9—47 K.
R10—10 K.)
R11—10 K.) } matched
R12—47 K.
R13—10 K.
R14—47 K.
V1—ECC81

V2) ECF80 or
V3) ECF82
Pair of matched diodes,
OA79 or GEX34
VR1—Variable 2 K.
C1—1,000 pF MC
C2—1,000 pF MC
C3—33 pF MC
C4—1,000 pF MC
C5—1,000 pF MC
C6—10,000 pF MC
C7—1,000 pF MC
C8—1,000 pF MC
C9—1,000 pF MC

C10—330 pF MC
C11—1,000 pF MC
C12—0.1 μF P
C13—330 pF MC
C14—330 pF MC
C15—8 μF E
C16—12 μF E
C17—12 μF E
C18—1,000 pF MC
C19—1,000 pF MC
C20—12 μF E
C21—3-5 pF MC
MC—Midget ceramic
P—Paper

E—Electrolytic
L1 and L2—See text
L3—Q PCM
L4—Q 1FM
L5—Q 1FM
L6—Q 1D } C. & G.
Kits, Ltd.
1 Chassis
3 Nylon loaded B9A
valve holders. (2 with
skirts and screens.)
1 Switch (1 pole 3 way)
2 Co-axial input sockets
1 Rubber grommet
3 Ferrocart heads

4. *The driver limiter, V3A.*

This stage is similar to the last stage, but working voltages are very much lower. Interference is completely eliminated by using this stage in conjunction with a ratio detector.

5. *Ratio detector Q.I.D.*

The operation of this form of detector will be found in text books on the subject and is too complex to describe here. For best interference limiting the voltage developed across C10 should be zero; on one side of this point it will be positive and on the other side negative.


6. *Cathode follower output stage.*

This is a straightforward design using a 10K ohm resistor in the cathode. It will be observed that there is no blocking condenser in the grid circuit. This has become redundant due to the "Dromatic" frequency control. The inclusion of this stage enables a long length of screened lead to be used between the amplifier and the tuner without fear of hum pick up or treble attenuation. This valve may be easily modified to a conventional amplifier giving very much higher gain. The anode provides a decoupled voltage source for the frequency control element.

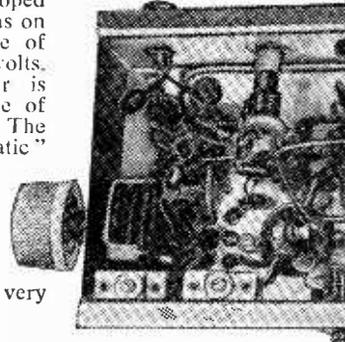7. *The "Dromatic" frequency control circuit.*

This is the most interesting feature of the unit. When incorrectly tuned, the voltage which is developed across C10 is amplified with a D.C.

amplifier V2B. This changes the bias on the junction diode connected across the oscillator coil. The diode is biased to cut-off and acts as voltage sensitive capacitor, changing the oscillator frequency which reduces the error signal developed across C10. The bias on the diode should be of the order of 10-20 volts. A variable resistor is used in the cathode of V2B for adjustment. The use of "Dromatic" frequency control also enables the oscillator voltage to be confined to the oscillator coil which helps to keep radiation to very small proportions.



Construction

An underside vi

It is essential to follow the layout very accurately especially with regard to earthing points. Tags should not be used but leads soldered direct to the chassis. It is preferable to use a supply with one side earthed, but a balanced supply may be used. Wire all leads carrying signals by as short leads as possible. Wire


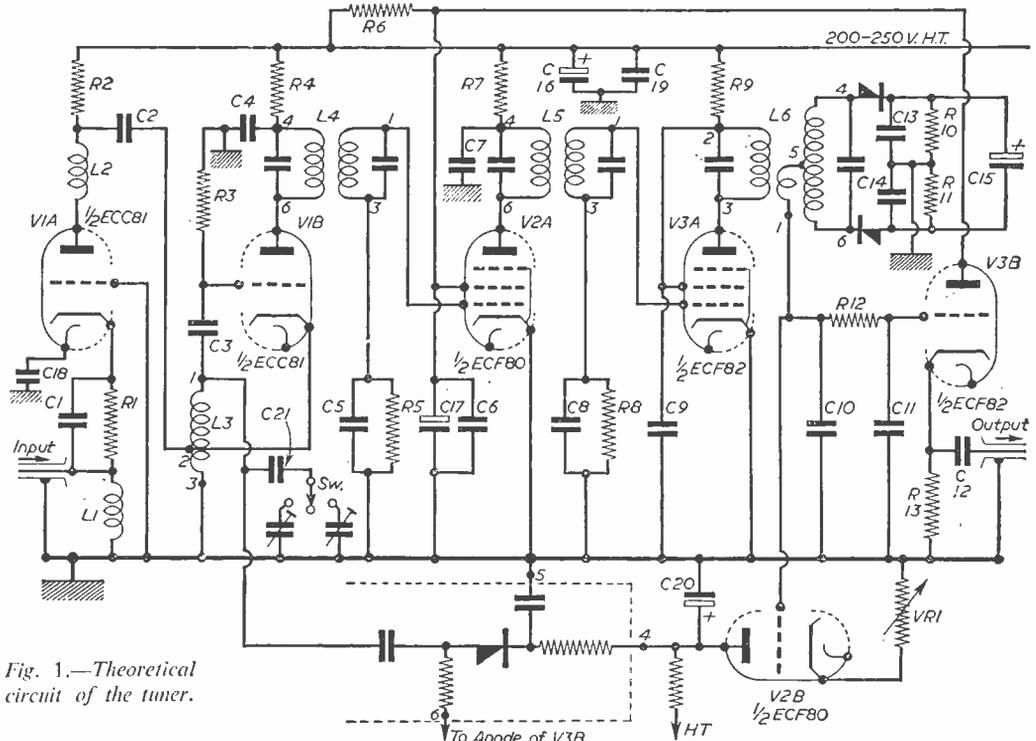


Fig. 1.—Theoretical circuit of the tuner.

the unit starting at V1 and finishing at Q.1D. The crystal diodes should be handled with care and soldered very quickly using a pair of pointed pliers and a heat shunt. Wire all H.T. dropping resistors vertically on short leads and connect them to a bus-bar after all else has been done. The bar should be thick copper wire connected at C16, taken direct to a tag on L2 and then bent at right angles and taken to the end of the chassis in line with the valves. V1 and V2 should be screened with a 2in. screening can. Check the wiring from Fig. 2.

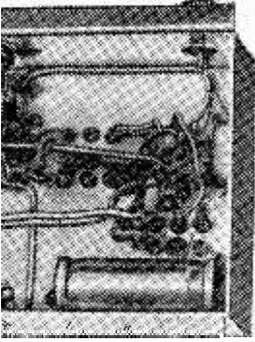

Alignment

Connect a high resistance D.C. voltmeter on its 100 volt range with the positive terminal on C17 and the negative on C20. Adjust VR1 for 15 volts. Connect meter across C15, and an

unmodulated signal generator tuned to 10.7 megacycles between the chassis and the grid of V3A (pin 2). Adjust the top core of Q.1D for maximum voltage. Transfer input to the oscillator coil (pin 1 Q PCM) and adjust both cores on L4 and L5 for maximum voltage, reducing the input so that the voltage never exceeds 5 volts. Leaving the input across the oscillator coil, transfer the meter to C10 and earth. Now adjust the bottom core of L6. When adjusted the reading will increase and then pass zero to the opposite direction, the correct point is as it passes through zero. Re-check all the coils as above, adjusting as necessary.

Tuning

Connect the aerial to the input socket and an amplifier to the output socket. A hissing should be heard in the loudspeaker. With the switch in the centre position adjust L3 with a plastic-bladed screwdriver until the Home Service is heard. There will probably be two tuning positions, one of which sounds distorted whilst the other clicks into tune. Now move the switch in one direction and adjust that trimmer for the Light programme and similarly for the Third in the other position. On the Third programme

of the tuner.

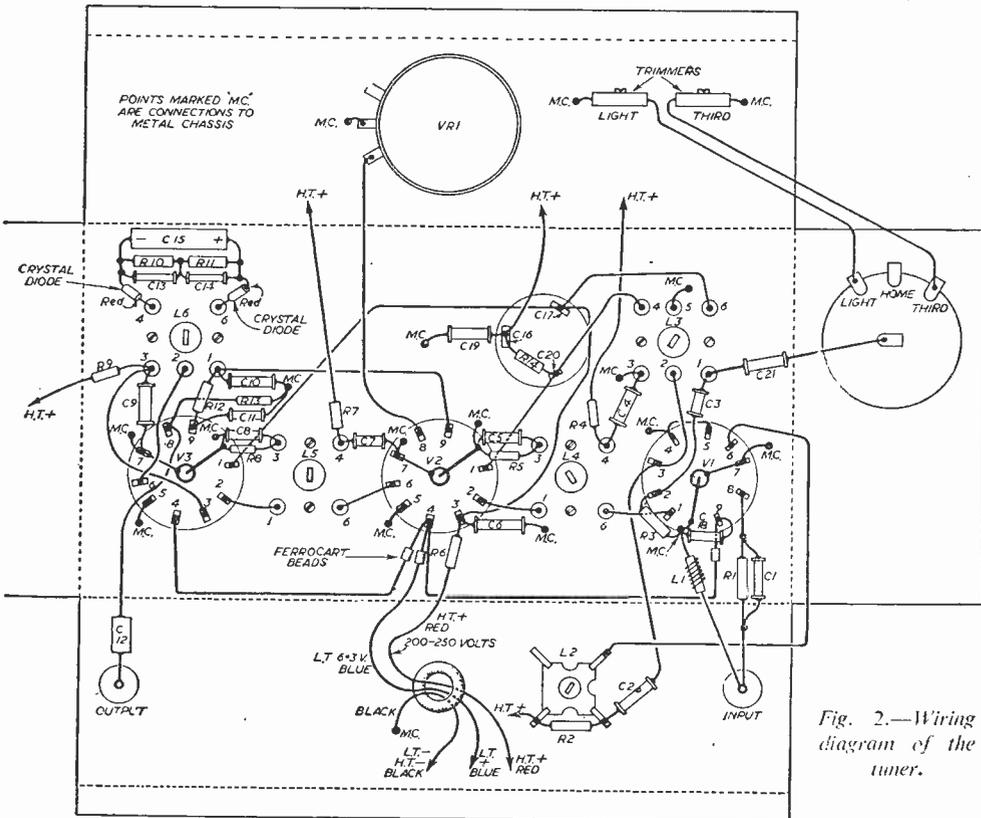


Fig. 2.—Wiring diagram of the tuner.

adjust L2 in conjunction with L3 for maximum voltage across C15. Retune the unit (L3 and trimmers) for zero voltage across C10.

- (2) Insert a 47K ohm resistor in series with the anode lead (pin 2).
- (3) Connect C12 to pin 1 instead of pin 8.

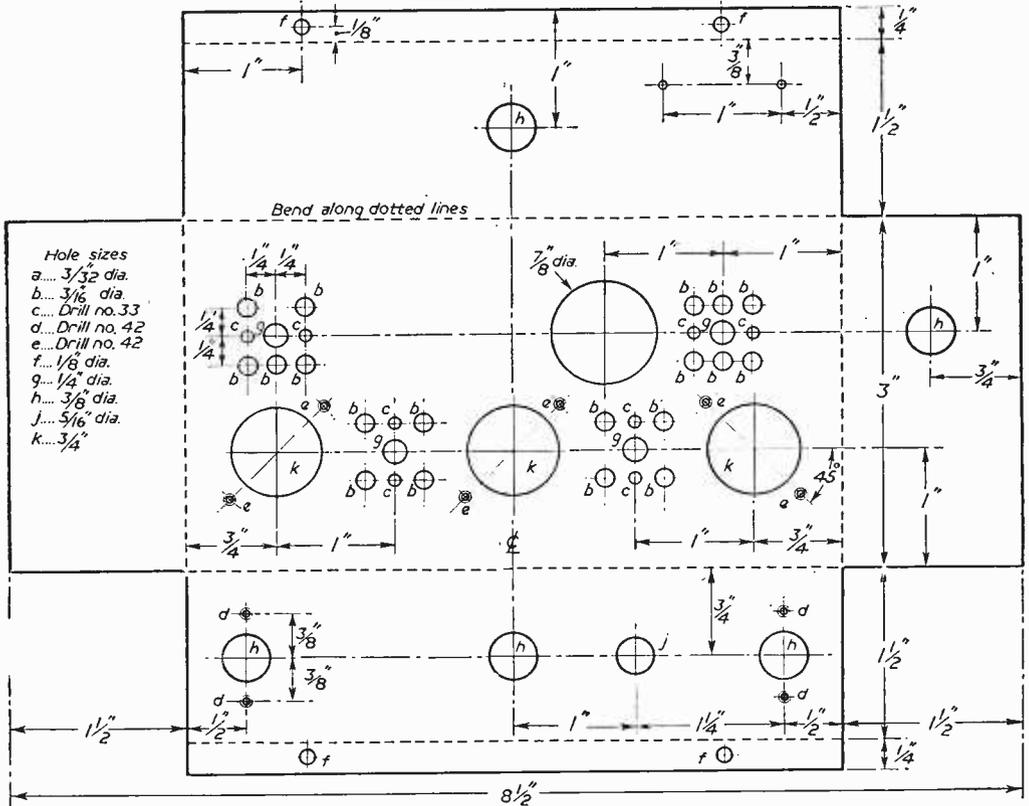


Fig. 3.—Full chassis data for constructing your own chassis.

Coils

L1 four turns of thin insulated wire on half a dust core.
 L2 six turns of 20 s.w.g. enamelled on 1/4 in. former with grey tuning core.

Aerials

If you are in the primary service of the transmitter the tuner will probably work on a simple Band II dipole. However, it is highly recommended that a loft mounted dipole is used. For longer distances a loft mounted, two or three element aerial may be required.

Pre-amplifier

The cathode follower low impedance output stage has a gain of slightly less than unity and from a suitable signal will deliver 0.5 volts into the amplifier. This should be suitable for nearly all types of medium and high gain amplifiers. In a case where the amplifier is insensitive, this stage may be into a conventional amplifier delivering 10 volts.

- (1) Replace R13 with a 1000 ohm resistor.

Power Supplies and Modulation Hum

The H.T. required is 200-250 volts at 30-40 mA. This must be adequately smoothed and decoupled. The L.T. of 6.3 volts at 1.2A should have one side earthed. If a centre tapped supply is used another decoupling capacitor at pins 4, 5 on V1, may be required to prevent modulation hum. A suitable component is a 1000 pF ceramic.

A NEW HANDBOOK

AMPLIFIERS: DESIGN & CONSTRUCTION

By F. J. CANN

17/6, Post 18/6

Containing Designs for Radio, Gramophone, Tape-Deck, P.A. Amplifiers, with a special chapter on D.C. Amplifiers.

From **GEORGE NEWNES, LTD.**
 Tower House, Southampton Street, Strand, W.C.2

Radio Component Show, 1958

GROSVENOR HOUSE, APRIL 14th TO APRIL 17th

THE following is a complete List of Exhibitors at this year's Radio Components Show, in Stand order. This is the fifteenth Annual

Private Exhibition of British Components, Valves and Test Gear for the Radio, Television, Electronic and Telecommunications Industries.

<i>Exhibitor</i>	<i>Stand No.</i>	<i>Exhibitor</i>	<i>Stand No.</i>
Standard Insulator Co., Ltd.	1	Telegraph Condenser Co., Ltd.	54
Wandleside Cable Works, Ltd.	2	Siemens Edison Swan, Ltd.	55
Geo. Salter & Co., Ltd.	3	London Electrical Manufacturing Co., Ltd.	56
Mullard, Ltd.	4	Reslosound, Ltd.	57
Diamond H. Switches, Ltd.	5	London Electric Wire Co. & Smiths, Ltd.	58
Zenith Electric Co., Ltd.	6	Egen Electric, Ltd.	59
Thermo-Plastics, Ltd.	7	James Neill & Co. (Sheffield), Ltd.	60
Cathodeon Crystals, Ltd.	8	Westinghouse Brake & Signal Co., Ltd.	61
Waveforms, Ltd.	9	Standard Telephones & Cables, Ltd.	62
Associated Electronic Engineers, Ltd.	10	Long & Hambly, Ltd.	63
Stratton & Co., Ltd.	11	Wingrove & Rogers, Ltd.	64
Suflex, Ltd.	12	Parmeko, Ltd.	65
Mica & Micanite Supplies, Ltd.	13	Permanoid, Ltd.	66
H. J. Enthoven & Sons, Ltd.	14	Ferranti, Ltd.	67
Taylor Electrical Instruments, Ltd.	15	Murex, Ltd.	68
Morganite Resistors, Ltd.	16	N.S.F., Ltd.	69
Alfred Imhof, Ltd.	17	Truvox, Ltd.	70
Radio Instruments, Ltd.	18	Measuring Instruments (Pullin), Ltd.	71
Belling & Lee, Ltd.	19	Telephone Manufacturing Co., Ltd.	72
Connollys (Blackley), Ltd.	20	Antiference, Ltd.	73
Mullard Overseas, Ltd.	21	McMurdo Instrument Co., Ltd.	74
Mullard, Ltd.	22	British Electric Resistance Co., Ltd.	75
Wego Condenser Co., Ltd.	23	Vactite Wire Co., Ltd.	76
Woden Transformer Co., Ltd.	24	Geo. Tucker Eyelet Co., Ltd.	77
Carr Fastener Co., Ltd.	25	Gresham Transformers, Ltd.	78
Duratube & Wire, Ltd.	26	Whiteley Electrical Radio Co., Ltd.	79
Colvern, Ltd.	27	Mycalex and T.I.M., Ltd.	80
Goldring Manufacturing Co. (Great Britain), Ltd.	28	Reliance Manufacturing Co. (Southwark), Ltd.	81
Erie Resistor, Ltd.	29	British Physical Laboratories, Ltd.	82
Cosmocord, Ltd.	30	J. Beam Aerials, Ltd.	83
British Insulated Callenders Cables, Ltd.	31	Thorn Electrical Industries, Ltd.	84
Reproducers and Amplifiers, Ltd.	32	Haddon Transformers, Ltd.	85
Dubilier Condenser Co. (1925), Ltd.	33	Walter Instruments, Ltd.	86
Weymouth Radio Manufacturing Co., Ltd.	34	Wimbledon Engineering Co., Ltd.	87
Collaro, Ltd.	35	Wolsey Electronics, Ltd.	88
Stability Capacitors, Ltd.	36	Electro Methods, Ltd.	89
Goodmans Industries, Ltd.	37	Langley London, Ltd.	90
Garrard Engineering & Mfg. Co., Ltd.	38	Spear Engineering Co., Ltd.	91
Jackson Bros. (London), Ltd.	39	Power Controls, Ltd.	92
Welwyn Electrical Laboratories, Ltd.	40	Magnetic Devices, Ltd.	93
Vitavox, Ltd.	41	Stocko (Metal Works), Ltd.	94
Painton & Co., Ltd.	42	Lustraphone, Ltd.	95
Rola Celestion, Ltd.	43	Oliver Pell Control, Ltd.	96
A.B. Metal Products, Ltd.	44	Minnesota Mining & Manufacturing Co., Ltd.	97
Steatite & Porcelain Products, Ltd.	45	A. K. Fans, Ltd.	98
Richard Allan Radio, Ltd.	46	Daly (Condensers), Ltd.	99
A. F. Bulgin & Co., Ltd.	47	Insulating Components & Materials, Ltd.	100
A. H. Hunt (Capacitors), Ltd.	48	Air Control Installations, Ltd.	101
Multicore Solders, Ltd.	49	Anglo-American Vulcanized Fibre Co., Ltd.	102
Partridge Transformers, Ltd.	50	Ross Courtney & Co., Ltd.	103
Electro Acoustic Industries, Ltd.	51	Technograph Electronic Products, Ltd.	104
Sydney S. Bird and Sons, Ltd.	52	Creators, Ltd.	105
Safford Electrical Instruments, Ltd.	53	Plannair, Ltd.	106
		Linton & Hirst, Ltd.	107

<i>Exhibitor</i>	<i>Stand No.</i>	<i>Exhibitor</i>	<i>Stand No.</i>
Electronic Components	108	Swift Levick & Sons, Ltd.	141
Geo. Bray & Co., Ltd.	109	Newmarket Transistor Co., Ltd.	142
H. D. Symons & Co., Ltd.	110	Ardente Acoustic Laboratories, Ltd.	143
Fine Wires, Ltd.	111	Henry & Thomas, Ltd.	144
H. Clarke and Co. (Manchester), Ltd.	112	British Communications & Electronics	145
Static Condenser Co., Ltd.	113	Ministry of Supply	146
Simon Equipment, Ltd.	114	Ministry of Supply	147
Mallory Batteries, Ltd.	115	Department of Scientific & Industrial Research	148
Guest, Keen & Nettlefolds (Midlands), Ltd....	116	Hinchley Engineering Co., Ltd.	149
Micanite & Insulators Co., Ltd.	117	M.O. Valve Co., Ltd.	150
Geo. L. Scott & Co., Ltd.	118	Ekco Plastics, Ltd.	151
Hellermann, Ltd.	119	E.M.I. Sales & Service, Ltd.	152
Electrothermal Engineering, Ltd.	120	Siemens Edison Swan Ltd. (Valve Division)	153
Harwin Engineers, Ltd....	121	Morgan Brothers (Publishers), Ltd.	154
Texas Instruments, Ltd.	122	Anderton Springs, Ltd.	155
Shell Chemical Co., Ltd.	123	Standard Telephones & Cables, Ltd. (Valve	
Formica, Ltd.	124	Division)	156
Marrison and Catherall, Ltd.	125	Plessey Company, Ltd.	157
Fortiphone, Ltd.	126	Plessey International, Ltd.	158
K.L.G. Sparking Plugs, Ltd.	127	Technical Ceramics, Ltd.	159
Darwins, Ltd.	128	Wireless Telephone Co., Ltd.	160
F. D. Sims, Ltd.	129	Telecon Magnetic Cores, Ltd.	161
Tufnol, Ltd.	130	Telegraph Construction & Maintenance Co.,	
Henry Wiggin & Co., Ltd.	131	Ltd.	162
Hassett & Harper, Ltd....	132	Magnetic & Electrical Alloys, Ltd.	163
Bakelite, Ltd.	133	Victoria Instruments, Ltd.	164
Enalon Plastics, Ltd.	134	Mansol (Great Britain), Ltd.	165
Aero Research, Ltd.	135	Associated Iliffe Press, Ltd.	166
Hallam, Sleight & Cheston, Ltd.	136	English Electric Co., Ltd.	167
Lion Electronic Developments, Ltd.	137	Instrument Review	168
Simmonds Aeroccessories, Ltd.	138	Brayhead (Ascot), Ltd.	169
W. T. Henley's Telegraph Works Co., Ltd. ...	139	Brayhead (Ascot), Ltd.	170
Ever Ready Co. (Great Britain), Ltd....	140	Brayhead Products, Ltd.	171

Northern Mobile Rally

Sunday, April 13th 1958, at Harewood House, Leeds.

BY kind permission of H.R.H. The Princess Royal, and the Earl and Countess of Harewood, Harewood House is to be the venue for the First Northern Mobile Rally. Organised by the Spen Valley Amateur Radio Society, in conjunction with the Leeds, Bradford and Leeds University Union Radio Societies, this first Annual Northern Mobile Rally will be held on Sunday, April 13th, 1958, from 12.15 p.m. to 6 p.m.

Rally Arrangements

Central stations will be sited at Harewood House, radiating on Top Bank, 80 metres and, it is hoped, 2 metres to guide visitors to Harewood from either Leeds or Harrogate. Fixed stations have undertaken to guide visitors into Leeds or Harrogate. Mobile stations are asked not to "call" the control stations until they are in Leeds or Harrogate.

On arrival, visitors will be directed to Reception, asked to leave their cards, sign in and receive a special Attendance Card. Car park is free (a special concession) and entrance fee to grounds, etc., is 1s. each.

Three judges will inspect the mobile equipment of those enlisting in the Concours D'Elegance, and

equipment will be judged for neatness, etc. A trophy, to be held for one year, has been donated and will be presented by Mr. J. R. Petty (G4JW), the Regional Representative of the R.S.G.B.

Various items of equipment have been donated by members of the Radio Industry and these will be raffled to defray the cost of the Rally.

Harewood House will be open to visitors (1s. 6d.) per head, and Hostesses will be in attendance to direct visitors to the House, Grounds, Farm and other attractions of this Royal Residence.

Meals

There is a pleasant up-to-date cafeteria and in addition, a private room has been made available to those making bookings in advance.

Specimen menus will be sent on request.

Intending visitors are asked to write to the Spen Valley Secretary, Mr. N. Pride, 100, Raikes Lane, Birstall, Nr. Leeds. Car stickers will be available on request.

A NEW HANDBOOK

RADIO CONTROLLED MODELS

By F. J. C.A.M.M

Price 12/6, by post 13/4d.

From

GEORGE NEWNES, LTD.,

Tower House, Southampton Street, Strand, W.C.2

TERMS AVAILABLE


RECTANGULAR T.V. TUBES

17in. £7. 10. 0.

14in. £5. 10. 0.

12 MONTHS' GUARANTEE

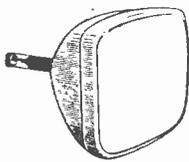6 months full replacement. 6 months progressive. We still retain our high quality. Ins. Carr. 15/6.
T.V. TUBES, 25. 14in., 15in., 16in. Why not convert your 9in., 10in., 12in. to these sizes. Full details in our catalogue on request.
12in. T.V. Tubes, £6. 3 months' guarantee. Ins. Carr. 15/6.
TUBES WITH BURNS, £1. Have one of these for stand-by or testing, while stocks last. Carr. included.




DENCO RADIOGRAM CHASSIS, 97/6

A.C./D.C. 4 w/band turret tuned s/het chassis with speaker. 5 valve international octal. Chassis size: 8 1/2in. x 10in. x 12in. Ins., Carr., 7/6.



SUPER CHASSIS, 99/6

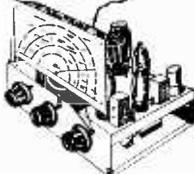5 valve (octal) s/het chassis, including 8in. speaker. 4 control knobs (Tone, Volume, Tuning, w/change sw.), 4 w/band with position for Gram P.U. and extension speaker. A.C. Ins., Carr., 5/6.



CONSTRUCTOR T.V. CHASSIS PRICES REDUCED TO CLEAR


TIME BASE, 4/9. Including scanning coil, focus unit, etc., less valves. FREE drawing. P. & P. 2/6.
SOUND & VISION STRIP, 3/6. Superhet. Complete vision strip, less valves. FREE drawing. P. & P. 2/6.
POWER PACK & AMPLIFIER, 19/6. O.P. stage 6V6 with O.P. trans; Smoothed H.T. 350v. 250 m.a., 6.3 v. 5 amp. 22v. 3 amp. 6.3v. 4 amp. and 4v. centre tapped. Less valves. FREE drawing. Carr. 5/6.

LOOK! COMPLETE T.V. CHASSIS, 49/6

Made by famous manufacturer. R.P. E.H.T. unit included. Drawing 2/6 or FREE with order. Chassis in 3 separate units (Power, s/vision, Timebase inter-connected). These chassis can easily be fitted into existing console cabinets. Less valves and tube. Channel 1-2, 3-5. Easily converted to I.T.A. Ins. Carr. 10/6.


HOME RADIO, 79/6

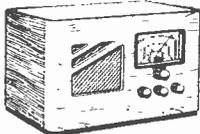A.C./D.C. Universal mains. 5 valve octal superhet. 3 w/band receiver. Can be adapted to gram P.U. In attractive wood cabinet. 18 1/2in. x 11in. x 8 1/2in. Ins., Carr., 7/6.



POPULAR RADIO OR RADIOGRAM CHASSIS, 39/6

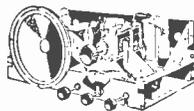3 w/band & gram. 5 valve s/het. International octal. Ideal table gram, but still giving high quality output. 4 knob control. 8in. P.M. speaker. 7/9 extra. Set of knobs, 2/. Chassis size: 12in. x 6in. x 9in. Less valves. Ins., Carr., 4/6.



ATTRACTIVE EXTENSION SPEAKER, 29/9


Complete, fitted with 8in. P.M. speaker "W.B." or "Goodmans" of the highest quality. Standard matching to any receiver (3-5 ohms) Plex & switch included. Money refunded if not completely satisfied. Ins., Carr., 3/6.

8in. P.M. SPEAKER, 8/9. Ideal for kitchen & bedroom extension. Let the lady of the house listen to that Radio or T.V. programme. Complete with O.P. trans., 10/. P. & P., 2/9.
P.M. SPEAKER, 12/9. 8in. Elac or Goodmans. High quality 2-5 ohms. Complete with O.P. trans., 14/. P. & P., 2/9.

Close! Thursdays, 1 p.m. Open all day Saturday. Send for FREE 1958 Catalogue. Liverpool St. to Manor Park Station—10 mins.
DUKE & CO. (Dept. 4), 621/3, ROMFORD ROAD, MANOR PARK, E.12. Tel.: ILF. 6001-3.

17in. T.V. CHASSIS, TUBE & SPEAKER £19.19.6

Latest improved circuits, higher E.H.T. (brilliant picture). Improved sensitivity (for greater range). Chassis easily adapted to any cabinet. 17in. Rectangular tube on adapted chassis. Channels 1-5. Less valves. With all-channel TURRET TUNER, 50/- extra. Chassis size: 14 1/2in. x 11 1/2in. deep. With 5 valves—6SN7GT, 6V6, EY51, 2-6D2's, £21.19.6. With all valves, including 6L18 EL38, 7-6P1's, £25.19.6. 12 months' guarantee on tube, 3 months on valves and chassis. State B.C. channel and I.T.A. if TURRET TUNER ordered. Ins. carr., 25/6.

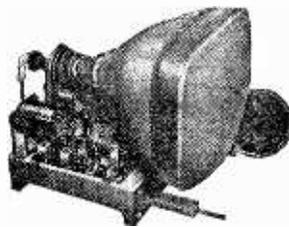

14in. T.V. CHASSIS, TUBE & SPEAKER £13.19.6

As above with 14in. round tube. Guaranteed 3 months. With 5 valves, £15.19.6. With all valves, £19.19.6. All-channel TURRET TUNER, 50/- extra. Ins. carr., 25/6.

T.V. AERIALS

25/6. For all I.T.A. channels. Outdoor or loft: 3-element. Famous manufacturer at half the normal price. Post 2/6.

15/9. B.B.C. indoor type. Folded dipole with 12ft. of co-axial cable fitted. Post 1/9.

7/9. Complete with co-axial cable. For all channels. This bargain aerial is for use indoor or loft. Extra co-axial at 6d. yard. Post 1/3.

WIRE AERIALS, 6/9. Whip antennae 50in. long. Collapsing to 11in. One-hole fixing. Post 1/-.

T.V. MASKS, 3/9. 12in. New. White rubber. Post 1/9.

T.V. MASKS, 7/9. 17in. Brand new. Grey plastic. Post 2/-.

T.V. MASKS, 10/9. 17in. Brand new. White plastic. Post 2/-.

T.V. MASKS, 14/9. 17in. Brand new. Halo lighting. Post 2/-.

T.V. WOODEN ENCLOSURES, 3/9. 9in. and 12in. wooden frames, fitted with toughened glass. Regret callers only.

R.F. E.H.T. COIL, 19/6. 6-10 kv. Uses 6V6 or P61 as osc. Data and drawing FREE with each order. Post 2/6.

Boxed VALVES 3 MONTHS' GUARANTEE

6L19	8/9	T41	8/9	SP61	3/9	EF37	4/9
6P28	10/9	6SG7	3/9	DF86	5/9	EP35	5/9
E240	8/9	77	3/9	EB34	1/9	PRN46	6/9
4D1	2/9	8D2	3/9	KTW61	6/9	E132	6/9
6B8	3/9	8D3	7/9	ECC81	8/9	EL91	3/9
6F12	7/9	12AU7	5/9	ECH42	8/9	PRN45	6/9
EF32	3/9	12BE6	6/9	EF39	6/9	TT11	6/9
6H6M	1/9	EAF42	8/9	EF41	8/9	451U	10/9
SP41	3/6	12S7	1/9	EF91	7/9	Z77	7/9

American Types. U.X. All at 1/9 each.

18	75	1D6	4C8
42	38	6D6	6A7

Barrettors 301

MAINS POWER TRANSFORMER, 9/9. 350-0-350 v. 250 m.a. 6 v. heater at 5 amp. 4 v. at 5 amp., 4 v. at 5 amp., isolated. Extra isolated winding for 2 v. or 4 v. tubes. Prim. 200-350 v. Drop through type. (41Hz. x 5in. x 5in.). Post 3/9.

HEATER TRANSFORMER, 12/9. 0-200-250 v. Prim. 12 v. Heater 1 amp. Post 1/9.

HEATER TRANSFORMER, 2/9. 2:1 ratio auto trans. For heater winding up to 6 v. Post 1/9.

HEADPHONES, 1/9. Single earphone and land C.L.R. Ideal for crystal sets, extension on radio, etc. Post 1/3.
CHASSIS, 1/- EACH. 6- or 8-valve. Latest type, midgeet valve design, for A.M. or P.M. Brand new, cadmium plated on heavy s.w.g. steel. Size: 12 1/2in. x 7 1/2in. x 2 1/2in. Post 1/9. 4 for 4/-, post 3/-, 12 for 10/-, carr. 5/-.

INSULATING TAPE, 1/6. Finest quality, 75 ft. x 1/2in. wide. Post 9d.

SELF-FEED SOLDERING TOOL, 19/6. 6-12 volt. 110-125 volt. Made for the American market. Car battery or mains. Export quality. Complete in light carrying case. Reel of solder and spare parts. Post 2/9. 200-240 volt adapter. 10/- extra.

CO-AX CABLE, 6d. YARD. Good quality. Cut to any length. 1 6 post on 20 yds., 45 - per 100 yds. post 3/6.

CHEAP, QUICK & EASY TO MAKE!



It's fun to build this "POCKETPAL" shoulder or pocket radio. So easy to build—it covers all the medium waveband with exceptional sensitivity and selectivity. Features a high efficiency pentode valve in well tested, powerful circuit. Personal phone ALLDAY battery operation (Batteries fit inside) slings over the shoulder—AERIAL INSIDE THE SLING LEAD!—or slips into pocket. Mini size 3" x 2" x 5". Build in about 90 minutes—WITHOUT ANY EXPERIENCE, using our "STEP-AND-CHECK" INSTRUCTION MANUAL WHERE EVERYTHING YOU DO IS SPELLED OUT FOR YOU IN PICTURES SO YOU CAN'T GO WRONG! This "POCKETPAL" radio can be built for only 37/6, including Case, Valve, Manual, Nuts, etc. Post & Packing is 2/- (C.O.D. 2/-). PARTS SOLD SEPARATELY—shopping list, etc. 1/6. EASY TO BUILD CERTAIN—DON'T PUT IT OFF—SEND NOW!



BUILD THIS FOR ONLY 35/-!

It's fascinating to build this "fantabulous" "TOM-TUM" transistors radio—only the size of a small cigarette packet, yet a marvel of clarity giving unexcelled transistor reception over all the medium waves. Personal phone circuitry gives loud and clear tone. Can be built by absolute novice in 30 minutes providing endless listening pleasure the moment building is completed. Uses only one small 8d. penlight battery lasting months. Absolute beginners are assured of error-free building because of our SPECIAL INSTRUCTION MANUAL—WHERE EVERYTHING IS SPELLED OUT FOR YOU IN PICTURES—SO YOU CAN'T GO WRONG! It costs only 35/- to build the "TOM-TUM" including Case, Transistors, Manual, Nuts, etc. Postage & packing amount to 2/- (C.O.D. 2/-). PARTS SOLD SEPARATELY—shopping list, etc. 1/6. EASY TO BUILD, THRILLING TO OWN—SEND AT ONCE!

BUILD THIS MAINS "FRYING-PAN" RADIO FOR ONLY 68/6!



Build this MAINS "FRYING-PAN" SPECIAL, uses highly sensitive twin-triode valve circuit and normal size speaker. Covers all Medium and Long Waves giving amazing performance and tone. Costs only 1d. for about 75 hours use! Excellent for KITCHEN, bedroom, garden hut, etc., etc. Robust design.

ANYONE CAN FOLLOW. Can be built for 68/6d, including valves, speaker, step-by-step plans, etc. Postage and packing 3/- (C.O.D. 2/-). PARTS SOLD SEPARATELY—shopping list, etc. 1/6. WILL PAY FOR ITSELF AGAIN AND AGAIN!—RUSH YOUR ORDER TODAY.

NOTE: Complete range of components stocked, regret no orders sent abroad, cheques gladly accepted. Sorry no callers at present.

MERLIN LABORATORIES (Dept. PW3), 167a PORTLAND ROAD, HOVE, SUSSEX

Best Buy at Britain's

AMERICAN MULTIMETERS, by Precision, U.S.A. 400 microamps basic. A.C. and D.C. volts to 6,000 D.C., milliamps to 600, Ohms to 5 megohms, 20 ranges in all. In polished wooden case, 7 1/2 x 7 1/2 x 5 1/2. Complete with leads, batteries and instructions. Tested and guaranteed. £8/19/6.

AVOMETERS—34 ranges Universal meter, for A.C. and D.C. volts, A.C. and D.C. current and Ohms. Large easy-to-read 5 in. mirror scale. B.S.I. standard. Complete with batteries and guaranteed in first-class working order. £8/19/6. P. & P. 4/-.

AVO BRIDGES—Measures capacity to 50 mfd., resistance to 50 megohms, meter indicates balance, and reads 0.1 to 15 v. as valve voltmeter. Leads, test and power factor scale. Full instructions. Tested and guaranteed. A.C. mains operation. £7/19/6.

MULLARD GM41401 C. & R. BRIDGES—0.1 Ohm to 10 Megohms in 4 ranges; 10 pFd. to 10 mFd. in 3 ranges. For 50 c/s A.C. mains. In perfect working order. £7/10/-, P. & P. 3/6.

WEE METERS—0 to 50 Megohms at 500 v. BRAND NEW in leather case. With leads and instructions. £12/10/-, Ditto, but 100 v., £8/10/-.

MINIATURE 373 I.F. STRIPS—For F.M. tuner described in April and May P.W. Complete with 3 of EF91, 2 of EF92 and EB91. A fresh release enables us to offer these once again. BRAND NEW, with circuit, 42/8. Or less valves. 12/6. Post either, 2/6.

SPEAKERS—3 Ohms, 6 1/2 in. diam. In grey wrinkled steel cabinet. 9 x 9 x 5 1/2 in. Complete with volume control and transformer for 600 Ohms line. Brand new. 27/6. P. & P. 3/6.

VIBRATOR PACK—Input 6 v. D.C. Output approx. 100 v. at 30 m/Amps. D.C. Fully smoothed and R.F. filtered. Size 6 1/2 x 5 x 2 1/2 in. Fitted with Mallory 629C vibrator. BRAND NEW. 12/6.

VIBRATOR PACK—Input 6 v. D.C. Output 200 v. D.C. 100 m/Amps Fully smoothed and R.F. filtered. Size 9 x 5 x 6 1/2 in. Complete with 0/4 and vibrator. Brand new. 27/6.

MAINS ISOLATING TRANSFORMERS (Vortexion).—For testing A.C./D.C. sets in safety. 230 v. input, output 230 v., 100 watts, 22/8. P. & P. 2/6.

MAINS TRANSFORMERS—Input 200-250 v. A.C. Outputs 275-0-275 v., 100 m/Amps, 6.3 v., 7 Amps, 5 v., 3 Amps. (Govt. ratings.) 4 x 4 1/2 x 4 1/2 in. high. Upright mtg. Brand new, 25/-, P. & P. 2/6.

R.C.A. OUTPUT TRANSFORMERS—Pri. push-pull 6L6s. Secs. 600 Ohms, tapped at 15, 7.5 and 5 Ohms. Tertiary winding for NFB. Handles 20 watts. Potted. Circuit of R.C.A. amplifier supplied FREE. Brand new. 27/6.

AVOMETER LEATHER CASES—Brand new, with strap, 7/6.

PLEASE ADD POSTAGE OR CARRIAGE ON ALL ITEMS
CHARLES BRITAIN (RADIO) LTD.
11 Upper Saint Martin's Lane, London, W.C.2

TEmpLe Bar 0545

Shop hours 9-6 p.m. (9-1 p.m. Thursday). Open All Day Saturday

REPANCO

HIGH GAIN TRANSISTOR COMPONENTS

STANDARD RANGE

Ferrite Slab Aerials Type FS2. Designed for Long and Medium Wave reception with transistor portable superhet. receivers. Slab size 5 1/2 in. x 3 1/2 in. x 5/32 in. Complete with fixing brackets, 13/6. **Combined Oscillator and 1st I.F. transformer Type OT1**. 1 3/16 in. sq. x 1 1/2 in. I.F. Frequency 315 Kc/s. 11/6. **2nd I.F. Transformer (315 Kc/s) Type TT2**, 5/-, **3rd I.F. Transformer (315 Kc/s) Type TT3**, 5/-, I.F. Transformers enclosed in iron dust pots with slug tuning. **Push Pull Interstage Transformer Type TT4**. Ratio 1 : 1 C.T. Stack size 1 1/2 in. x 1 1/16 in. x 7/16 in., 8/6. **Push Pull Output Transformer Type TT5**. Ratio 15 : 1 C.T. Size as TT4. Matched to 3 ohm speaker, 8/-.

MINIATURE RANGE.—For pocket receivers.


Ferrite Slab Aerial Type FS3. Medium Wave only. With fixing grommets. Size 3 in. x 1 1/2 in. x 5/32 in., 7/6. **Oscillator Coil Type XOB**. Medium Wave only. Overall size 1 in. dia x 1 in. Enclosed in Ferrite pots, 5/-, **I.F. Transformer Type XT6**. Suitable for 1st and 2nd I.F. 455 Kc/s. Size 1 in. sq. x 1 1/16 in., 10/-, **I.F. Transformer Type XT7**. Designed for 3rd I.F.T. or detector I.F.T. 455 Kc/s. Size as XT6, 10/-, **Push Pull Interstage Transformer Type TT9**. Ratio 1 : 1 C.T. Radiometal Core. Size 1 in. x 1 1/2 in. x 13/32 in., 12/6. **Push Pull Output Transformer Type TT10**. Ratio 8 : 1 C.T. Matched to 3 ohm speaker. Size as TT9, 12/6. Practical and Theoretical circuits enclosed with each Repanco Transistor Component.

JUST RELEASED. "THE MINI-7" a new personal portable transistor receiver. Size 5 1/2 in. x 3 1/2 in. x 1 1/2 in. Send 1/9 P.O. for instructions.

Mail Order and Trade:
RADIO EXPERIMENTAL PRODUCTS, LTD.
33 Much Park St.
COVENTRY
Tel.: 62572

Wholesale Enquiries and Export:
REPANCO, LTD.
O'Brien's Buildings
203-209 Foleshill Rd.
COVENTRY
Tel.: 40594

TRANSMITTING TOPICS

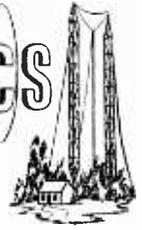

THE IMPORTANCE OF THE AERIAL

By O. J. Russell, B.Sc.(Hons.), G3BHJ

THE beginner, whether armed with the "simplest" crystal oscillator set, or with a more complex multiband outfit, or even a commercial manufactured transmitter, is faced with a multitude of aerial problems. In fact, if he takes too seriously all that has been written about amateur band aerials, he will find so many conflicting, or apparently conflicting statements, that he will be at a loss as to how to proceed. Generally he may adopt some "recommended"

seem safer. Gazing mournfully at his average size back garden, he is convinced that getting out a "good" signal in all directions is beyond his means.

The fact is, of course, that Fig. 1 is a snare and a delusion. It refers solely to the radiation of a dipole in free space. It also gives the "radiation pattern" at zero angle for a dipole mounted over the earth, where of course zero angle radiation is extremely small. For all other cases, the radiation pattern is strongly affected by ground reflections. Even in the absence of ground reflections, Fig. 2 shows that there is appreciable radiation "off the end" of the aerial at appreciable vertical angles. Fig. 3 illustrates the "effective polar diagram" of a dipole at vertical angles of, say, 30 degrees or more from the direction of horizontal radiation. Thus, for propagation in which radiation at appreciable vertical angles is effective, a horizontal half-wave dipole is effective in almost any direction. This explains why a southern station with a wire running north and south can work into Scotland with ease, despite the fact that the GM stations are right off the end direction of the aerial. Similarly, the typical "long wire" free space radiation pattern of Fig. 4 needs to be interpreted

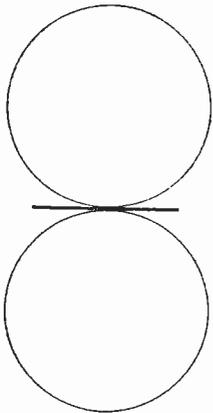


Fig. 1.—Diagrammatic representation of the polar diagram of a dipole in free space.

aerial, and operate with this for some time, but perhaps wondering if he is getting the best results, or indeed anywhere near the correct mode of operation. Coupled with the inevitable vagaries of propagation conditions, it is often difficult to come to any assessment of an aerial system without a considerable period of operating.

The examination of some of the fundamentals of aerials is clearly necessary, if only as an antidote to some of the bewildering statements often made. It should be noted that two dogmatic and apparently conflicting statements made about an aerial may both be true, provided that the conditions under which the statements apply are considered. A simple example of this is given by the half-wave dipole. The "radiation pattern" in a horizontal plane of a half-wave dipole is usually given as shown in Fig. 1, together with a few tips on aligning the direction of the aerial wire to guide the aspiring novice. Indeed the aspiring novice is then rapidly calculating that he will need at least a pair of dipoles per band to cover all directions, and that for good coverage in all directions three dipoles per band would

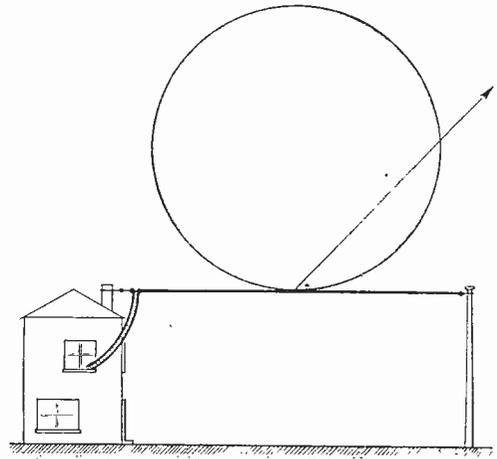


Fig. 2.—Neglecting ground reflections, it is clear that at high angles there is appreciable radiation "off the end" of a horizontal dipole. Only in a direct "end on" direction in the exact line of the wire itself is there zero radiation.

cautiously, as the sharp nulls may be blurred by ground reflection effects.

The effect of ground reflections also has another interesting effect. With horizontal aerials that are "close" to the ground, the effect of ground reflections is illustrated in Fig. 5. This shows that most of the energy is radiated skywards. Note that "close" indicates that the height of the aerial wire is a small fraction of a wavelength. Thus, on topband an aerial wire running 50ft. above ground is still rather close, as is a 30ft. high horizontal wire for 80 metres. Incidentally, two stations a few miles apart on

ings on topband are almost invariably affected mainly by ionospherically reflected energy.

Vertical Aerials

This points up the fact that a vertical radiator on topband with the enhanced low angle radiation may make a dramatic difference to signals within a 50 mile radius. It is easy to calculate that a topband station 30 miles away should produce an S9 signal by genuine ground wave. Usually on horizontal aerials signals may be quite weak in the S5 region. With vertical radiators a good local coverage should be achieved, and this points out the popularity of RAEN

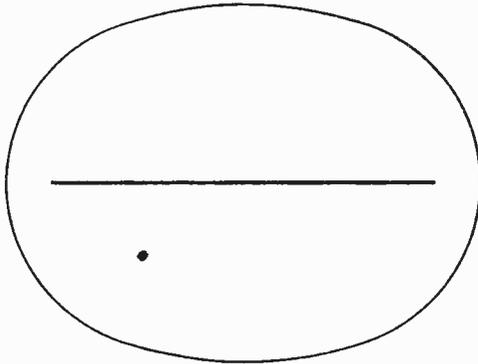


Fig. 3.—The polar diagram for a dipole that is not too high is similar to the above for propagation angles of thirty degrees or so to the vertical. This means that for European contacts up to about a thousand miles on the lower frequency bands, radiation is virtually omnidirectional.

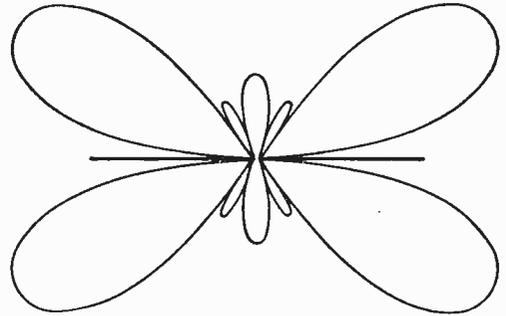


Fig. 4.—Schematic impression of a typical long wire radiation pattern. Ground reflection effects may in some cases tend to blur the sharpness of the null radiation directions.

80 or even 40 metres are, in effect, talking over some 120 miles of "airline." This is because most of the radiated energy goes straight up to the ionosphere, and is reflected down again on these low frequencies. However, with disturbed conditions, it is often possible to hear even a local topband, 80-metre or 40-metre station fading violently and sounding just like a DX signal, complete with sideband distortion. This is an unusual and dramatic proof that work-

emergency networks, who for mobile use obtain good results with short vertical aerials. It is fortunate that vertical aerials which are necessary for compact mounting on mobile RAEN stations operating from cars are also those which provide for reliable local coverage. For guidance, the radiation pattern of a short vertical antenna located over a good conduction soil is shown in Fig. 6.

It is hoped that the above has helped to clear up some of the aspects of radiation patterns, ground effects and so forth, which can be expected to worry some beginners. When we consider DX working on the higher frequency bands it may well be found that the radiation pattern begins to behave "more like" the textbook free space pattern suggests. The answer is found in Fig. 5. This shows that an aerial "close" to the ground radiates at high vertical angles. However, on the higher frequency bands, where the wavelength is shorter, the aerial is becoming less "close" to the ground. Thus, on 10 metres a dipole only 15ft. to 20ft. off the deck is no longer to be considered as "close" to ground. Moreover, on the higher frequencies, the lower angle radiation is mainly responsible for long distance communication. Thus, the height of the aerial is still important. This poses the question as to what height is "best" for the aerial system. In point of fact the higher the frequency the lower the angle of

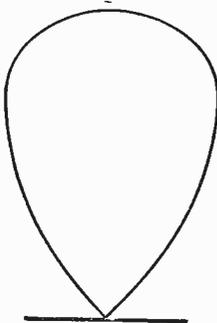


Fig. 5.—The effect of ground reflections on an aerial close to the ground is to concentrate energy skywards. This situation applies especially in topband and eighty metre working.

(Continued on page 217)

HOME RADIO OF MITCHAM


187 LONDON ROAD, MITCHAM, SURREY.

MIT 3282

London and Home Counties distributors for Panda Transmitters.

We are stockists for: EDDYSTONE, PANDA, DULCI, ARMSTRONG, DENCO, STENTORIAN, J.B., REPANCO, TELETRON, GOODMAN'S, WHARFEDALE, OSMOR, etc.

HERE IT IS! THE REPANCO "MINI-7"

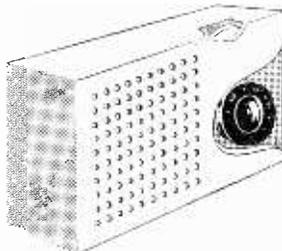

A 7 transistor superhet pocket portable with 2 1/2 in. loudspeaker that really gives guaranteed results on its internal ferrite rod aerial. Neat grey plastic case with scarlet knobs measuring approximately only 5 in. x 3 in. x 1 1/2 in., ideal for the pocket. Can be built in four

stages from easy point-to-point diagrams and instructions. This little set is a WINNER. Start building to-day and amaze your friends. Just the thing for the holidays. FULL CONSTRUCTIONAL DATA. PRICE LIST and PRIORITY ORDER FORM. PRICE 1.9 post paid. Total building cost £10.18.6.


ANOTHER DELIVERY OF GRAM PICK-UPS



If you were unlucky last time we now have a further supply of latest type lightweight crystal pick-up with turn-over cartridge and sapphire stylus for standard and long playing records. PRICE ONLY 37.6 (post 9d.).

SPECIAL NEWS. The well known firm of COSSOR famous for the pre-war "Melody Maker" kits comes back into the home constructor market with their No. 562K amplifier kit. This is the most complete kit ever offered, with such exact and complete instructions a child could do it. 3 valves, printed circuit type chassis, provide a compact and versatile amplifier suitable for radio, microphone, and gramophone inputs. Negative feedback and high quality output. Complete with main speaker and tweeter unit. PRICE ONLY £9.15.0, post paid.

DULCI CHASSIS

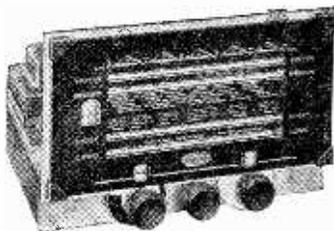

Model H.3. 5 valve AM, FM 3 waveband radio chassis, £20.17.0. Model H.4. 6 valve AM, FM 4 waveband radio chassis with magic eye, £24.6.6. Model H4T. 5 valve AM FM 4 waveband tuner chassis, self-powered, £20.17.0. Model H11. 6 valve plus rectifier and two diodes AM FM 4 waveband tuner with high quality audio pre-amplifier with bass and treble controls, equalisation, etc.,

£29.3.10. Model GA4. 4-watt quality amplifier with separate control panel, £9.9.0. Also 10 watt amplifier with pre-amp, £19.19.0, and new push-pull output radio chassis at £29.3.10. Full details on receipt of S.A.E.

BRENELL TAPE DECKS

We can now supply the Brenell tape deck from stock. A precision engineered unit with simplicity of design which gives that long term reliability so lacking in many mass produced articles. Three speeds, twin track, takes 7 in. spools, three motors, can be adapted for stereophonic. £24.12.0 with digital rev. counter. Also complete recorders in stock, £57.3.0

FULL RANGE OF RECORDING TAPES IN STOCK. BY RETURN C.O.D. SERVICE

E.H.T. TESTER




Don't guess E.H.T. - test it. 3 to 16 kV. A.C. and D.C. from transformer or fly-back source. An essential instrument for every engineer. Boxed with full instructions and guarantee. PRICE 52.6, post paid.

MULLARD '3-3' AMPLIFIER

We can now supply the famous Mullard 3 valve 3 watt quality amplifier complete and ready built with attractive front panel. Independent Bass and Treble controls and suitable for gramophone, radio, or microphone inputs. This little amplifier has shaken many Hi-Fi enthusiasts by its amazing performance. PRICE ONLY £8.8.0 (post 2.6).

W.B. STENTORIAN H.F.1012

The most popular Hi-Fi speaker on the market to-day. Top quality at realistic cost. 10 in. die-cast chassis with 12,000 gauss magnet. Response 30 to 14,000 c.p.s. 10 watts handling capacity and universal speech coil for 3, 7.5, and 15 ohms. PRICE £4.19.9 (post 2.-). For the Hi-Fi fanatic who wants the absolute best regardless of the cost the new W.B. H.F.1016 is the speaker to try. Delivery now from stock. £8.0.0. Also full range of W.B. speaker and equipment cabinets. S.A.E. for details.

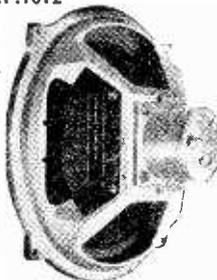

BARGAIN BASEMENT

Neon tester screwdrivers, 110 to 380 volts, 3.9, post 6d. (3 v. 3 A. pilot bulbs. 4 - dozen (post 6d.). 6 1/2 in. speakers, 17.6, post 2.-. 16 mfd. 350 v. T.C.C. condensers, 1.6 ea., or 6 for 7.6. Solon 625 instrument soldering iron with detachable bit, 22.6, post 9d., state voltage. High stability resistors 5% 1/2 watt all preferred values up to 1 meg, price 9d. each. (post 3d. on order.)


JASON F.M. TUNER KITS

If you are not yet enjoying the thrill of interference-free crystal-clear reception may we recommend the remarkable JASON F.M. tuner kits. Two versions available: Switch tuned with A.F.C. giving Home, Third, and Light spot on tune always. Complete kit, £10.10.0. Manual tuned with slide rule scale, the most popular kit ever produced. Complete kit, £7.7.6. Full constructional data of either of these kits price 2 - post 4d. Price lists of parts free on request.

FROM THE HOME OF HI-FI



High Fidelity at its finest

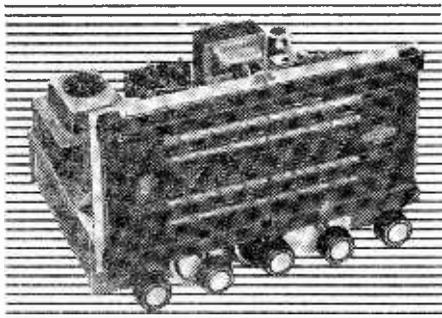

Model H3. Three waveband model (inc. VHF), 6 valves. For 3 ohm. speaker. Chassis immensely sensitive and stable, giving highest quality reproduction. Wide range Tone Control, with pick-up, extension speaker and gram motor sockets. **£20. 17. 0.** inc. P.T.

Model H4PP. (Illustrated) NEW! A complete Dulci High Fidelity radiogram chassis, combining sensitivity, selectivity and stability to delight the most discerning listener. Outstanding record and VHF reproduction, 4 wavebands. Ultra linear amplifier gives ample power output. Push-pull system, wide frequency response, bass and treble controls. Fits easily into any existing cabinet. The perfect chassis for modernising your radiogram.

AM/FM Model H4PP. Price **£29.3.10.** inc. P.T.

Model H4. AM/FM Radiogram chassis. 7 valve, 4 waveband superhet with FM (VHF). Magic eye tuning indicator. High sensitivity. Dial size 11½" x 5½". Sockets for speaker (3 and 15 ohm.) Mains sockets for motor. **£24. 6. 6.** inc. P.T.

Write for full details

DISTINCTLY



QUALITY PRODUCTS

THE DULCI COMPANY LTD. 97-99 VILLIERS ROAD LONDON N.W.2.

TELEPHONE: WILLESDEN 6678/9

VALVES AT BARGAIN PRICES

Guaranteed valves posted by return. 1 - post for 1 or 2; 1/6 for 3/4; 2 - for 6 or more.

1D3, 10 -; 1W4 350, 10 -; 1W4 500, 10 -; 2P, 17/6 -; 4XP, 25 -; 6A88, 10 -; 6AC7, 5/6 -; 6AL5, 5 -; 6D2, 5 -; 6K6GT G, 5/6 -; 6K7 G, 5 -; 6K25, 15 -; 6P28, 22/6 -; 6R7 G, 15 -; 6W2, 10 -; 7AN7, 10 -; 7B7, 7 -; 7S7, 7 -; 9A1, 5 -; 9D2, 4 -; 13VPA, 4 -; 40SUA, 10 -; 41STH, 14 -; 50C5, 7/7 -; 63SPT, 5 -; 3J2THA, 5 -; 354V, 5 -; 431U, 10 -; AC4Pen, 12/6 -; ACO42, 17/6 -; ACO41, 25 -; AC P4, 5 -; AC VPL, 5 -; AC VP2, 14 -; APP4E, 12/6 -; APV4, 10 -; B319, 10 -; D77, 5 -; D152, 5 -; DA30, 14 -; DD6, 5 -; DD41, 10 -; DH63, 7 -; DL63, 15 -; DO24, 10 -; EB91, 5 -; EBC33, 7 -; ECL80, 10 -; EF39, 5 -; EF50, 5 -; EM34, 8 -; EY51, 10 -; HL41DD, 10 -; HLI33DD, 10 -; KT55, 14 -; KTW63, 5 -; LN152, 10 -; LP4, 25 -; LZ319, 13 -; ME41, 14 -; MH4, 5 -; MH41, 6 -; MU14, 10 -; MVS PenB, 14 -; OM4, 7 -; P12/250, 25 -; P27 50, 10 -; P30 500, 14 -; P460, 25 -; PA20, 17/6 -; PCC84, 10 -; PCF80, 13 -; Pen45, 12/6 -; Pen48, 12/6 -; Pen383, 15 -; Pen453DD, 25 -; PP3 250, 25 -; PPS 400, 10 -; PX4, 25 -; PX25, 10 -; PX23A, 14 -; PX41, 25 -; R3, 10 -; R4A, 10 -; R12, 10 -; RZ, 10 -; SP41, 3 -; T41, 15 -; TH30, 5 -; TH30C, 5 -; TH41, 15 -; TH2321, 5 -; U151, 10 -; U301, 15 -; U4020, 10 -; URIC, 10 -; UUS, 10 -; UU6, 15 -; UU7, 12/6 -; V503, 14 -; VP4B, 14 -; VPI3R, 4 -; VPI3C, 4 -; VP41, 7 -; VPI322, 4 -; W42, 14 -; W63, 5 -; W149, 7 -; X41, 14 -; X64, 5 -; X81, 7 -; X81M, 7 -; X148, 7 -.

If any item is out of stock, we will supply the direct plug-in equivalent unless asked not to do so.

HIGH GAIN BAND 3 T.V. CONVERTERS

NO ALTERATIONS REQUIRED TO YOUR SET
RETURN OF POST SERVICE. All new goods.

Posted orders to Camberley, please. 3 - each extra post (4 - for 2), 2 - extra C.O.D.

Full instructions supplied. Can be fitted in 19 mins.; free from drift; fitted with co-axial plug; fully wired ready for use; with power pack, including metal rectifier; double wound transformer; 2 valves; mains on-off switch; fine tuner; B.B.C. to I.T.A. at turn of switch; 12 months' guarantee (B.V.A. valves 90 days). Terms available, one-third down and balance plus 7/6 in four equal monthly payments; postage with first payment. FOR ALL SETS EXCEPT EARLY PHILIPS.

AUTOMATIC RECORD

CHANGERS are in short supply. Collaro RC457 Studio turnover crystal pick-up, 4-speed mixer. A.C. mains 200-250 v., see illus. ALSO Collaro single player AC3/554, 3-speed, turnover crystal pick-up with "T" head. **£6 16 6** (3/6 p. & p.).



£8/16/6 (5/- p. & p.)


BATTERY ELIMINATOR FOR 4 LOW CONSUMPTION VALVES. 90 v., 20 mA. and 1.4 v., 250 mA., 35 - (2/6 p. & p.). 200-250 v. A.C. (size 3½ in. x 3½ in. x 2 in.).

GLADSTONE RADIO

82B, High Street, Camberley, Surrey. and 3, Church Road, Redfield, Bristol. Tel. 51297.

13 CHANNEL CONVERTER

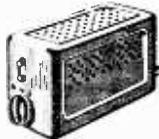Switch positions, off-I.T.A.-B.B.C. Valves PCF80 and PCC84. Moulded cabinet 8½ in. x 4½ in. x 6 in. Don't confuse with similar article being offered without power pack.



£5.5.0

Robust Band 3 AERIALS, for 1 in. to 2 in. diam. mast or, for loft, 3-element, 27 -; 5-element, 35 -; 9-element, 55 -; curr. paid.

radiation desirable. Also, for a given aerial height, the higher the frequency, the lower the angle of radiation will be for a horizontal dipole. Thus, a "reasonable" height will serve about equally well for all bands.

The novice, beginner or experienced amateur is earnestly counselled to take height considerations into account, preferably right at the start. A 60ft.

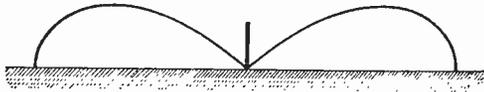


Fig. 6.—A short vertical aerial located over high conductivity soil has maximum radiation at low angles.

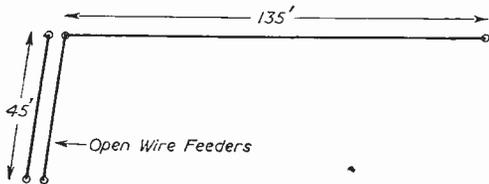


Fig. 7.—An end fed long wire aerial that makes a simple and highly effective system. It is a favourite aerial with a large number of leading DX operating stations. Many leading stations use long wires exclusively.

high aerial is definitely to be aimed at, even if this requires a little outlay and trouble in erecting a suitable mast. This, however, may be much less trouble than erecting a shorter mast, and then having to remove it and replace by a higher mast. Unfortunately, of course, costs rise steeply with increases of mast height. However, heights up to about 50ft. or so are feasible by bolting together two lightweight poles supported by simple guying systems. Greater heights involve more elaborate guying systems and some searching for suitable poles. Simple wooden towers may be made by the amateur, but steel towers and masts may involve heavy expenditure unless one is lucky with surplus purchases.

Unfortunately even 60ft. is not the ideal height. Certainly DX operators with 60ft. high aerials seem to outperform those with 40ft. high aerials. However, even 120ft. is not the "best height." A recent article analysing the problems in "getting out" of high power commercial short-wave stations using enormous rhombic aerials supported at the 100ft. mark has shown that a little more appreciation of communication problems would have resulted in an even higher choice of mast. In fact, somewhere around the 200ft. mark in height would enable more solid QSOs. or should we say "traffic handling," on the part of these commercial stations. Moreover, the increased height would enable communication to be maintained longer over a given path than with the lower aerial height. This increase in operating time over a DX path amounted to around an hour.

Height

The importance of getting a reasonable height for an aerial is certainly underlined by the above. The moral, then, for a beginner interested in horizontal aerials is to arrange for as high a mast as possible. Having decided to put up as high an aerial as one can conveniently manage, the question arises as to the sort of aerial one should use. Leaving out the question of further expenditure on beam arrays and automatic rotators for the moment, the "universal" long wire antenna of Fig. 7 is a simple multiband aerial that will enable one to work much DX in many directions. If this

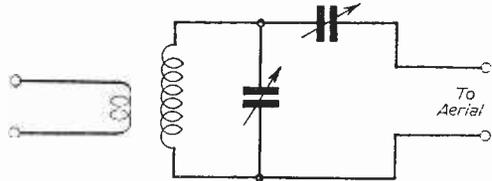


Fig. 8.—A universal aerial tuner, which will be found ideal for use with the aerial of Figure 6. It may be used for series and parallel tuning or a combination of both.

aerial is arranged to run approximately north and south, a glance at a Greatcircle map will show that it has, on the H.F. bands, four main lobes (Fig. 4) that will cover North America, South America, Africa and Australasia. Moreover, with odd lobes from the middle directions, it will be found that a good effective signal may be placed in almost any direction.

The SWL who is in process of becoming an amateur would do very well to erect now the sort of aerial he might be expected to employ when he gets his transmitting ticket. This may give a good angle on what directions he will expect to work.

PRACTICAL TELEVISION APRIL ISSUE NOW ON SALE PRICE 1s. 3d.

The current issue of our companion paper, PRACTICAL TELEVISION, which is now on sale, contains instructions for building a small unit which may be added to almost any meter to convert it into an E.H.T. meter. This particular device takes into account the very high voltage which exists at this part of a circuit, and enables a fairly high degree of accuracy to be obtained.

Another constructional feature deals with a Pattern Generator which is invaluable for testing television receivers, and also for test purposes there is described in this issue a Response Curve Generator. The latter, of course, is primarily of use for testing the tuning sections of a set, whilst the former enables all the more critical adjustments to be made.

Other articles deal with a Modified Scope Layout, Scanning and Synchronisation, Some Interesting Faults and Their Cure, Aerial Construction and Servicing the G.E.C. 1746.

The regular features are also included.

Servicing Transistor Receivers

CONSIDERATIONS IN THE HANDLING OF APPARATUS CONTAINING TRANSISTORS

By E. G. Bulley

WHEN servicing the conventional radio, it is common practice in the first place carefully to check the valves, but in transistorised circuitry it is advisable to adopt a different approach. The reason being that, although the transistor is mechanically sound and is considered to have indefinite life if it is operated correctly, it is susceptible to damage either electrically or through operating temperatures. Trouble from the latter can be caused to any transistor type radio if the receiver has been operated above or nearby a hot electric, gas or coal fire. Excessive heat affects transistors as is now well known, and such heat will be in excess of the manufacturers' storage temperature rating. If such is the case however, it is advisable to substitute the transistors in the circuit with some of the same type, and thus by elimination one is able to isolate the faulty transistor or transistors.

Nevertheless, assuming the receiver has been operated in a suitable position, it is advisable to remove the battery and measure the voltage at the battery terminals. A maximum permissible drop of battery voltage is approximately 40 per cent. of its original value, in which case, if the voltage has fallen to this value there is every likelihood that the receiver in question will become unstable as well as deliver a loss of volume.

Caution

It is as well to mention at this stage that on no account should connections be broken or made when the battery power is switched on, otherwise damage to transistors will result. Furthermore, when breaking or making a circuit, extreme care must be taken when soldering, otherwise, the transference of heat from the iron will likewise damage or destroy the transistor.

Practically all transistor receivers use miniature condensers for coupling and bypassing. Such condensers are either the electrolytic or tantalum anode type. These condensers have a fairly high capacitance for their physical size and should any of these become a dead short, leaky or open circuit, loss of gain or oscillatory effects will result. For example, a faulty bypass condenser used in the conventional bias arrangement of the emitter results in a loss of current flowing in the collector circuit, whereas a completely short-circuited condenser will result in the destruction of the transistor, as the full H.T. will be applied to the emitter and base connections.

Nevertheless, by inserting a suitable microammeter in the collector feed (with battery power off), the collector current can be checked when

the power is switched on. It may be as well to mention here that the D.C. bias voltage can also be measured by connecting a high resistance voltmeter across the collector and the base line.

Using Test Meters

Extreme care must be taken if using multi-range meters in servicing transistorised equipments as one must remember that when used as an ohmmeter, there is every possibility that the meter may inject a current into the circuit far in excess of that which the transistor will withstand. It is advisable therefore, when making continuity checks on transformers, etc., carefully to withdraw the transistors from the circuit unless you are certain what you are doing.

Individual checks on transistors can be carried out if one has a suitable multi-range meter and is sure that the current that will pass will not exceed that specified by the transistor manufacturer. A resistance check can be made on PNP types for emitter to base, and likewise collector to base. If such values obtained are far in excess, or alternatively well below, the value specified by the manufacturer, then it does indicate that the transistor is faulty.

Many circuits incorporate or adopt a push-pull output stage. Both these transistors, as in valve practice, are matched, and should one of these prove faulty it will be extremely difficult to obtain one to match the good one. It is therefore, necessary to replace both transistors with a matched pair. Failure to do so will result in distortion and poor quality reception. Likewise, faulty R.F. or I.F. amplifier transistors when replaced, may result in the circuit having to be realigned to obtain optimum results.

A Useful Test

An extremely useful test for transistors is that of gain, and can be considered as one of importance. Suitable transistor testers are or will be available in the near future, and such testers will be able to cater for the gain test. Such testers will undoubtedly be designed by experimenters and constructors and it will not be long before articles will be published describing their construction.

In conclusion, one must always bear in mind that great care must be taken when servicing such circuits as the receivers or equipments in question are usually small and compact. The compactness does not allow for probing or much disturbance of the wiring or components, otherwise, leads or components will touch and short circuit. Nevertheless, as time progresses, the constructor and experimenter will gain confidence as his predecessors did in the early valve days.



BAND 3 T/V CONVERTER—185 Mc/s - 199 Mc/s

Suitable for London, Birmingham, Northern and Scottish ITA Transmissions.

Mk. 2 Model as illustrated. Latest Cascade circuit using ECC84 and EF80 valves giving improved sensitivity (+ 18 db) over standard circuits. Built-in Power supply AC 200-250 v. Dimensions only 6 1/2 in. x 3 in. Ht. 4 in. Simple and easy to fit—only external plug in connections, wired, aligned and tested ready for use. State Channel required. Guar.

Bargain Offer—good results or full refund. only £3.19.6. Carr. & Pack. 2 6.

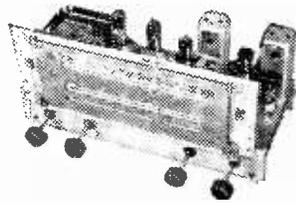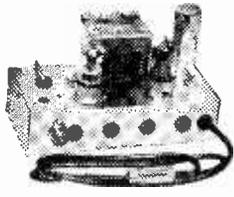CONVERTER ACCESSORIES
Band I-Band III Cross-over Lint, 7 6. Var. Attenuators 6db-36db, 6 9. BBC Pattern Filter, 8 6. Band III Aerials—outside Single Dipole with 4 yds. co-ax., etc., 13 9. 3 Element Beam, 27 6. 5 Element, 35 ., etc.



Volume Controls

Log. ratios, 10,000 ohms — 2 Megohms. Long spindles. 1 year guarantee. Midget EBR-kan type.
No Sw. R.P. Sw. D.P. Sw. 3- 4- 4- 4- 9
Linear Ratio, 10,000 ohms — 2 Megohms. Less switch, 3- each. Coax plugs, 1 2. Coax sockets, 1- Couplers, 1/3. Outlet boxes, 4/6. TWIN-FEEDER, 80 ohms, 6d. yd.; 300 ohms, 8d. yd. TWIN SCREEN FEEDER, 80 ohms, 1 3 yd. TRIMMERS, Ceramic, 4 pf.—70 pf., 9d.; 100 pf., 150 pf., 1 3; 250 pf., 1 8; 500 pf., 1 9. PHILIPS Beehive Type, 2 to 8 pf., or 3 to 30 pf., 1 2 each. RESISTORS. Pref. values 10 ohms 10 megohms.

80 ohm COAX

(CARL) STANBARD 1/2 in. diam. Polythene insulated. GRADE "A" ONLY.

8d. yd.

SPECIAL — Semi-air spaced polythene. 80 ohm Coax 1/2 in. diam. Standard conr. Losses cut 50%. Ideal Band 3. 9d. yd.

CARBON

20% Type, 1 w., 3d. 1 w., 5d.; 1 w., 6d. 2 w., 9d. 10% Type, 1 w., 8d. 5% Type, 1 w., 1 2. 1% Hi-Stab, 1 w., 2 2.

WIRE-WOUND

5 w. 25 ohms—1 3 10 w. 10,000 1 6 15 w. 10,000 2 2 5 w. 15,000—1 9 35,000 ohms 2 3

WIRE-WOUND POTS.

Preset Min. T.V. Type Knurled Slotted Knob. All values 25 ohms to 20 K., 3 — ea. 50 K., 4 — ea. 100 K., 4 — ea. Ditto Carbon Track, 50 K. to 2 Meg., 3 6. CONDENSERS.—Mica or S. Mica. All pref. values 3 pf. to 680 pf., 6d. ea. Ceramic types, 2 2 pf. 5,000 pf., 9d. each. Tubulars, 450 v., Hunts and T.C.C., 500, 1001, 3053, 101 and 1 250 v., 9d., 42, 60, 1200 v., Hunts T.C.C., 1 2, 25 Hunts, 1 6, 5 Hunts, 1 9. 1 2kV. T.C.C. (Simplex), 3 6. 501 6 kV. T.C.C., 5 6. 501 20 kV. T.C.C., 8 6.

LAB. COLVERN, etc.

Standard Size Pots, 2 1/2 in. Spindle. High Grade. All Values. 100 ohms to 50 K., 5/8; 100 K., 6/6. W/W EXT. SPEAKER CONTROL, 10 x 3/4-3/8.

SPEAKER FRET.

Expanded Bronze anodized metal 5 in. x 5 in., 2 3; 12 in. x 5 in., 2 3; 12 in. x 12 in., 4 8; 12 in. x 16 in., 6 2; 24 in. x 12 in., 9 — ea. TYGON FRET (Murphy pattern). 12 in. x 12 in., 2 3; 12 in. x 18 in., 3 —; 12 in. x 24 in., 4 —, etc.



RECORD PLAYER CABINETS

Contemporary style, veneer covered, 13 1/2 in. fronted lid with chrome interior, size 18 1/2 x 13 1/2 x 5 1/2 in., fitted with all accessories, including speaker baffle board and plastic fret. Space available for all modern amplifiers and autochangers, etc. Under record player mounting board 14 x 14 in.

Cabinet Price, £3. 3. 0. Carr. and ins., 3 6. 2 VALVE AMPLIFIER (to fit above cabinet), modern circuit with EL41 output, ready built, with 6 in. speaker and output transformer, £3.12.6. Carr. and ins., 2 6.

ALL-WAVE RADIOGRAM CHASSIS

3 WAVEBANDS 5 VALVES LATEST MIDGET M.W. 16 m. — 50 m. B.V.A. SERIES L.W. 200 m. — 500 m. B.V.A. SERIES 2,000 m. Brand new and guar. A.C. 200/250 v., 4 pos. W.C. Sw. Short-Medium-Long-Trim. P.L. socket. High Q. Ind. core coils. Latest circuit technique, delayed AVC and neg. feedback. OP 4 watts. Chassis size 13 1/2 x 2 1/2 in. Dial 10 in. x 4 1/2 in. Hor. or Vert. station names. Walnut or Ivory knobs to choice. Aligned and calibrated ready for use. Sensitivity and Quality at Low Cost. Chassis isolated from mains. BARGAIN 91 gns. Carr. and ins., 4 6. 8 or 10 in. speakers to match, 20/- and 25/-.

7 Valve De Luxe, push-pull EL41 version, 7 watt output, with H Duty Output Transformer, £12.10.0.

SINGLE PLAYERS RECORD PLAYER REDUCTIONS

4 sp. BSR (T10), 92 8. 4 sp. COLLARO JUNIOR, £4.10.0. 4 sp. GARRARD (4 S.P.), £7.15.0. Carr. & ins., 3 6. AUTO CHANGERS.—1 sp. BSR (TAS), £8.10.0. 4 sp. COLLARO, £8.15.0. 4 sp. GARRARD (R120/41/2), £10.0.0. Carr. & ins., 4 6. All above units are latest models and are fitted with modern styled lightweight Xtal. P.U. with turnover head and twin sapphire stylus.

SCOTCH BOY, EMITAPE, etc., 1,200ft., 27/- . Long playing, 1,900ft. reels, 45/- . Paper tape, good quality, 1,200ft., 12 6. Reels only, 3 in., 3 -; 5 in., 3 8; 3 1/2 in., 4 -; 7 in., 4 8.

SPECIAL OFFER

Recording tape by famous manufacturers, 1,200ft. on standard 7 in. plastic spool (exp. prior quality).

Special Price, 22/6 (normal price, 35/-)

NEW BOXED VALVES GUARANTEED

1R5	174	6	1P86	9-	1P41	10	6	1P82	10 6	
1R5	187	6	1R96	9-	1P80	10	6	1P83	12 6	
2B4	25	6	1D10	9-	1P88	12	6	1P11	12 6	
2Z4	9	6	2516	10	6	1P91	8	6	1P82	10-
6AT5	9	6	6AB6	9	6	1E41	10	6	1P83	11 6
6K7	8	6	6B91	6	6	1E84	11	6	1P80	9 6
6K8	8	6	6B41	10	6	1E85	11	6	1P81	9 6
6Q7	8	6	6B93	6	6	1E74	12	6	1P82	9 6
6N7	8	6	6C84	12	6	1E86	14	6	1P83	10 6
6S5	7	6	6CF80	12	6	1E210	8	6	1P22	8 6
6X4	7	6	6CF82	12	6	1E280	8	6	1P25	12 6
6X5	7	6	6CF42	10	6	1E281	8	6	1P11	10 6
7U5	9-	6	6H4	10	6	1M11	9	6	1P41	10-
7Y4	8	6	6E180	10	6	1P484	10	6	1P41	10 6
DA99	9-	6	6CL2	12	6	1P480	10	6	1P11	8 6

SPECIAL PRICE PER SET

1R5, 174, 185, 184 or 2B4 ... 27 6
1R5, 1P86, 1P96, DA99, 1P26 ... 35
6K8, 6K7, 9Q7, 6N6, 2Z4 or 6X5 ... 35

ELECTROLYTICS ALL TYPES NEW STOCK

Tubular Wire Ends	52	52	50 v. B.I.P.	5 6
25 25 v., 50 12 v.	1 9	52	250 v. Clips 3d.	ea.
50 50 v., 4 300 v.	2-	8	450 v.	2 6
100 25 v., 2 450 v.	2-	8	450 v. T.C.C.	4 6
8 450 v. B.E.C.	2 3	8	450 v. B.E.C.	5 6
8 500 v. Dub.	2 9	10	450 v. T.C.C.	5 6
8 450 v. Dub.	4 6	32	450 v. Dub.	4 6
8 250 v. T.C.C.	5	32	250 v. T.C.C.	6 6
16 450 v. B.E.C.	3 6	32	250 v. T.C.C.	6 6
16 500 v. Dub.	4	20	500 v. B.E.C.	8 6
16 16 450 v. T.C.C.	5 6	60	500 v. T.C.C.	6 6
16 250 v. Dub.	4	60	10 500 v.	11 6
32 500 v. Dub.	5	60	50 250 v.	12 6
50 50 500 v. B.E.C.	6 6	10	4 250 250 v.	12 6

Many other sizes 1s 10s stock.

TRANSISTOR—Midget Electrolytics.

2 mid., 4 mid., 8 mid., 15 v., 2 6. 6 mid., 10 mid., 16 mid., 15 v., 2 6. 12 mid., 15 v., 2 6.

SENTERCEL RECTIFIERS.

Back Voltages, K1 25 2 kV., 5 -; K2 10 25 kV., 6 9; K3 15 25 kV., 7 5; K4 25 25 kV., 8 6; K5 13 6. MAINS TYPES.—RM1 250 v., 60 mA., 4 0; RM2 125 v., 100 mA., 5 6; RM3 125 v., 120 mA., 7 6; RM4 250 v., 250 mA., 16 -; RM4B type 250 mA., 17 6; RM5 250 v., 200 mA., 21 -.

I.F. TRANSFORMER—465 kc.

Brand new ex-manufacture's midget I.F.T. type 2 1/2 in. x 1 1/2 in. dist. cone tubing, 1 1/2" wound coils, High Q. Bargain offer, 7 6 net.

MAINS TRANSFORMERS.


Made in our own Workshops to Top Grade spec. Fully insulated and impregnated. RADIO AND AMPLIFIER TYPE.—250 v., 60 mA. P.W. sec. 5 v. or 6 3 v., 1 2 net. 6 3 v., 20 a. set Htrs., 22 6 net. C.R.T. HTR. ISOLATION TYPE.—Low leakage with or without 25% sec. boost voltage. Ratio 1:1 or 1:1.25 2 1/2 v., 4 v., 6 v., 10 v., 10 6 ea. DITto with mains p.w. sec. 250 v., 12 6. SPECIALS to order.

L.F. CHOKES.—10 H. 65 mA., 5 -; 15 H. 100 mA., 10 6; 10 H. 120 mA., 10 6; 10 H. 150 mA., 15 6. OUTPUT TRANSY.—Standard pentode, 4 6; post-pull 12 watt, 13 6. Small pentode 3 9. Midget battery pentode (M4), etc., 4 6.

SPEAKERS.—PM-3 ohm, 2 1/2 in. dia., 16 6; 3 ohm, 10 6; 16 ohm, 15 in. R. & A., 17 6; 6 in. Celestion, 18 6; 7 x 4 in. Goodmans, 18 6; 8 in. Sov. R20, 20 6; 8 in. Special Cone G12ms, 21 6; 10 in. R. & A., 25 -.

Sin. P.M. SPEAKER (6 ohm)

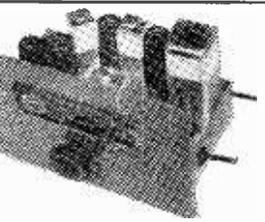Ex-Mfrs. units. Reels, W.B. Cells, etc. All reconditioned and guaranteed. Ideal ext. unit 7 6. J. & P. 1 6. Ditto with O.P.T. 9 6.



F.M. TUNER UNIT (87 mc s - 105 mc s) by Jason

As described in Radio Constructor. Designer Approved Kit of parts to build this modern highly successful unit, drilled chassis and superior type H.T. glass dial, only one coil of all quality components, etc. for only 5 Gns., post free. Set of 4 specified min. valves, 20 -, post free. Illustrated handbook, with full details, 2 - post free. 2-day alignment service now available, 7 6 plus P.A.T.

TRS RADIO COMPONENT SPECIALISTS (Est. 1946)

70 BRIGSTOCK ROAD, THORNTON HEATH, SURREY (THO 2188)


50 yards Thornton Heath Station. Listed above are only a few items from our very large stock. Hours: 9 a.m.—6 p.m. 1 p.m. Wed. Send 3d. stamp today for Complete Bargain List. OPEN ALL DAY SAT.



TRANSFORMER & COIL WINDING CAPACITY AVAILABLE FOR PROTOTYPES & SMALL RUNS.

Terms: C.W.O. or C.O.D. Retailer makes cheque, P.O.s, etc., payable to T.R.S. Post, Packing up to 3d. 7d. 11d. 1 1. 3d. 6. 5d. 7. 10d. 2 1.


SIGNAL GENERATORS

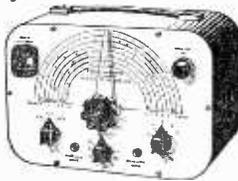

25/- deposit and 6 monthly payments of £1/6. Cash £8.19.6. Post and Packing 5/- extra. Coverage 100 Kc/s-100 Mc/s on fundamentals and 100 Mc/s to 200 Mc/s on harmonics. Metal case 10in. x 6 1/2in. x 5 1/2in. Grey hammer finish. Incorporating three miniature valves and Metal Rectifier. A.C. Mains 200-250 v. Internal Modulation of 400 c.p.s. to a depth of 30%. Modulated or unmodulated R.F. output continuously variable 100 millivolts. C.W. and mod. switch, variable A.F. output. Incorporating magic eye as output indicator. Accuracy plus or minus 2%.


25/- deposit plus P. & P. 5/- and 4 monthly payments of £1/6. Cash £4 19/6 plus P. & P. 5/-.

Coverage 123 Kc/s, 84 Mc/s. Metal case 10in. x 6 1/2in. x 4 1/2in. Size of scale. 6 1/2in. x 3 1/2in. 2 valves and rectifier. A.C. mains 200-250 v. Internal modulation of 400 c.p.s. to a depth of 30%. Modulated or unmodulated R.F. output continuously variable 100 millivolts. C.W. and mod. switch, variable A.F. output and moving coil output meter. Grey hammer finished case and white panel. Accuracy plus or minus 2%.

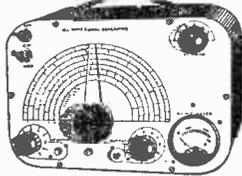


CONVERT TO I.T.A. FOR ONLY 25/- deposit plus P. & P. 5/- and 4 monthly payments of £1/5/6. Cash £5 17/- plus P. & P. 5/- ANY T.V. (except Philips, Bristol Area or Valley Area, Wales)

WITHIN 35 MILES OF I.T.A. TRANSMITTER. ALL CHANNELS NO ALTERATIONS TO SET. Complete with built-in power supply 200-250 v. A.C. mains. Crackle finish case 5 1/2in. long, 3 1/2in. wide, 4 1/2in. high, incorporating gain control and band switch. Plus, with cover removed. Complete installation comprises "Converter," Wolsey 3-element I.T.A. outside or loft aerial, 36ft. I.T.A. lead, two plugs. (Wolsey 5-element 10/- extra.)

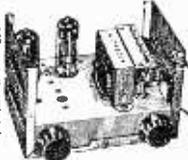

AC/DC POCKET MULTI-METER KIT

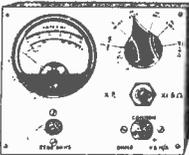

Comprising 2in. moving coil meter, scale calibrated in AC/DC volts, ohms and milliamps. Voltage range AC DC 0-50, 0-100, 0-250, 0-500, Milliamps 0-10, 0-100. Ohms range 0-10,000. Front panel, range switch, wire-wound pot. (for ohms zero setting), toggle switch, resistors and rectifier. In grey hammer finish case. **19/6** Plus Bullt and tested P. & P. 1/6. 7/6 extra.

Point to point wiring diagram 1 1/2", free with kit.

4-VALVE ALL - DRY SUPERHET PORTABLE KIT

Incorporating Ferrite rod aerial. Medium and long waves. In grey leatherette. Size 9in. x 7in. x 6in. Valve line-up : 1T4, 1R5, 1S5, 3V4. Complete kit of parts (less batteries).

£5. 19. 6 Plus Post & Packing 3/6.



COMPLETELY BUILT PORTABLE AMPLIFIER

approx. size 6 1/2in. x 2 1/2in., incorporating 2 valves, contact-cooled metal rectifier, 185 and 114le lit. crystals 4/6. Plus P. and double wound mains transformer 200-250 v. **59/6** & P. 3/6. 5" P.M. SPEAKER & O.P. TRANSFORMER, if purchased with the above, 18/6. Plus P. & P. 1/6.


COLLARO 4-SPEED AUTOMATIC CHANGER

Model 457 (suitable for use with above amplifier). A.C. mains. 200-250 v. turnover crystal head. Brand new, fully guaranteed. Plus 25/- deposit, plus P. & P. 5/-, and **£8. 19. 6** P. & P. 5/-. 7 monthly payments of £1/5/0.

RADIO & T.V. COMPONENTS (Acton) LTD.
23 HIGH STREET, ACTON, LONDON, W.3

All enquiries S.A.E. Goods not dispatched outside U.K.

"ASPDEN" TAPE RECORDER KITS

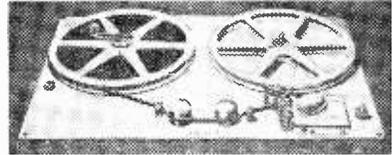

TAPE DECKS, 2-speed, twin track, easy to assemble kits with finest motor, Ferroxcube heads and full instructions.

MODEL 582 for 5in. spools, kit £8.5.0.

MODEL 782 for 7in. spools, kit £9.5.0.

Either model assembled and tested, 30/- extra.

AMPLIFIER kit, 2 1/2 watt, record/replay, 2 recording positions, neon indicator, etc., £5.18.0. Power pack kit for above, £2.18.6 (both without valves). Carr. and packing extra.

YOU CAN BUILD A QUALITY TAPE RECORDER

R.C.W. of Co. Durham writes :—

"... I have been using this equipment very successfully for some months now. Many people who have heard it have been staggered that such quality can be obtained for such a low price."

This tape deck and amplifier is being used in the Antarctic by an Expedition member.

Send stamp for full particulars to :—

W. S. ASPDEN Stanley Works, Back Clevedon Rd., BLACKPOOL, Lancs.

Train for a Wonderful future in RADIO & TELEVISION...

Radio and Television techniques are continually advancing and their applications ever increasing. These fields offer to the trained technician a career with an assured and remunerative future.

Here is your opportunity to enter for :—


1 YEAR COURSE Full-time day course in the Principles and Practice of Radio and Television. Designed for the training of Radio and Television Servicing Engineers and others similarly engaged in the Electronics Industry. Next course commences May 28th, 1958; others in September and January.

The E.M.I. College of Electronics, Dept. 32, 10, Pembroke Square, London, W.2. Telephone: BAYswater 5131/2.

The College is part of the E.M.I. Group... Britain's foremost electronic engineers... Pioneers of the world's first public television service.



Servicing Radio Receivers

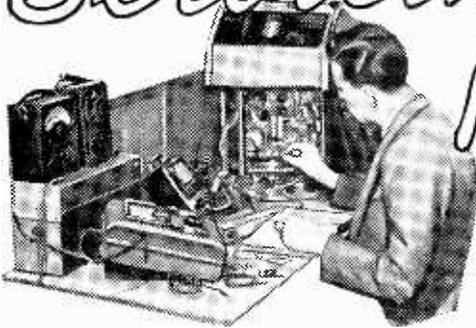

COSSOR A.M.-F.M. AUTORADIOGRAM
MODEL 529

By Gordon J. King, A.M.I.P.R.E.

The Cossor Model 529 is housed in a side-board style cabinet which is finished in a blond veneer; there is also space in the cabinet for record storage. Three loudspeakers, twin 8in. medium-frequency units, plus an elliptical 6in. X 4in. tweeter, are featured, connection being made to the output stage as shown in the inset at the top right-hand of the circuit in Fig. 3. The record player is a three-speed unit with a dual stylus crystal pick-up.

Cossor A.M.-F.M. Console Model 540

Using the same circuit and chassis assembly

is the Console Model 540. This, however, has two speakers only, a 10in. X 6in. elliptical unit for medium frequencies, plus a 6in X 4in. tweeter. Both models have provision for the connection of an extension 3 ohm loudspeaker. Switched pick-up sockets are available on the console for the connection of a record player with a high impedance or crystal pick-up.

A five-position band-selector switch provides for the switching of four bands (L.W., M.W., S.W. and V.H.F.-F.M.) and gram. The circuit, which consumes approximately 60 watts on radio, uses seven valves, including a full-wave rectifier and a magic-eye tuning indicator, is fully detailed in the accompanying circuits. There are two chassis sections, the main chassis and the F.M. chassis.

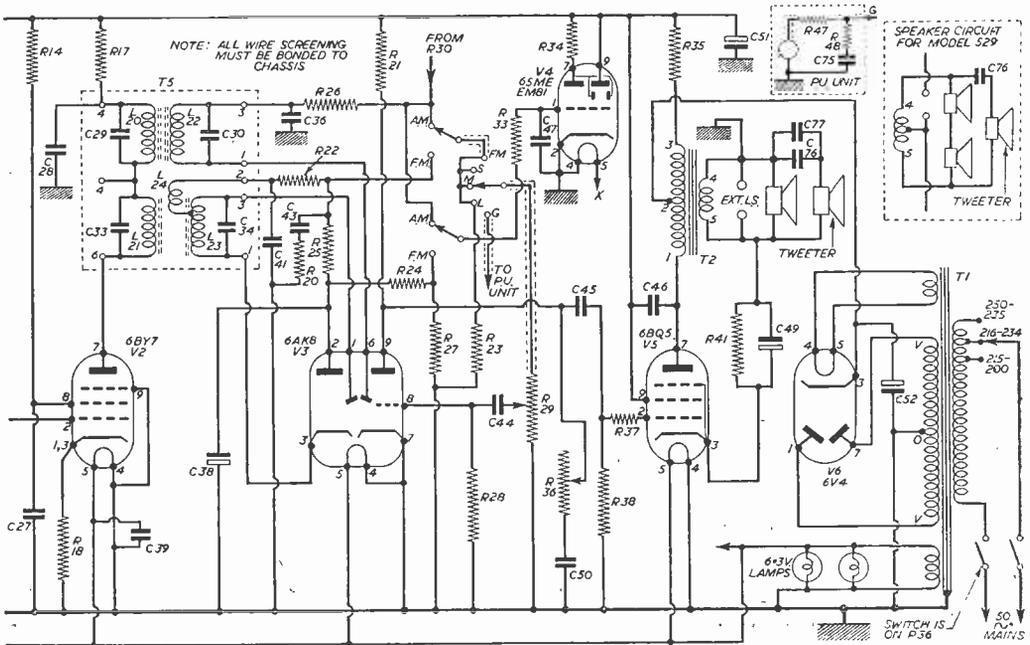


Fig. 3.—Output and power pack section of the Cossor receiver dealt with here.

Circuit Details

Valve V1 serves on A.M. as a conventional frequency changer, and on F.M. as an I.F. amplifier. The anode circuit of the mixer section is loaded into two series-connected I.F. transformers (housed in a common screening can and designated T4). L8/L10 being the A.M. I.F. tuned to 470 Kc/s, and L9/L11 being the F.M. I.F. tuned to 10.7 Mc/s. As a means of avoiding interference, the primary section of the transformer out of use is shorted out by reason of the associated F.M./A.M. changeover switch section.

A study of the circuits will reveal that there are several of these F.M./A.M. changeover sections in various parts of the receiver. The switch contacts are situated along a side-switch which extends the length of the chassis so as to keep each switch section close to its associated

circuit and avoid long connecting wires. The side-switch is mechanically ganged to the main band-selector switch and is actuated only when switching on or off the F.M. position.

The mixer section of V1 is thus responsive to signals at 470 Kc/s and 10.7 Mc/s. On A.M. the 470 Kc/s I.F. is produced in the ordinary way by the local oscillator (triode section of V1) signal heterodyning with the incoming signals. On F.M. the mixer section of V1 is supplied with 10.7 Mc/s signals from the F.M. tuner. In this connection H.T. is removed from the anode of the oscillator triode and applied to the F.M. tuner valve, while at the same time the grid circuit of the oscillator triode is connected to chassis. These functions account for two more F.M./A.M. changeover sections.

(Continued on page 225)

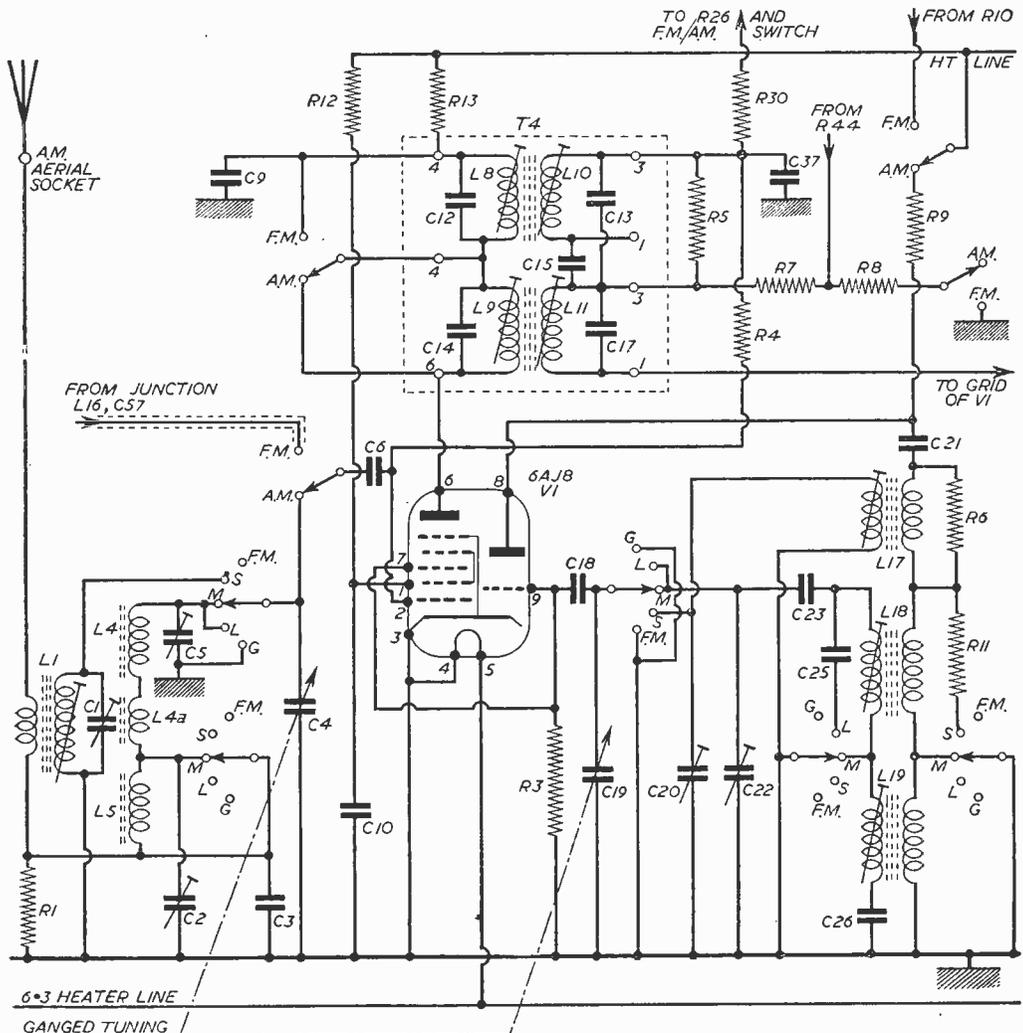


Fig. 2.—This is the A.M. Frequency changer and F.M. I.F.

RETURN-OF-POST SERVICE

JASON FM TUNER KIT

We can wholeheartedly recommend this tuner as being one of the most satisfactory of all the FM Kits. Construction is easy and results first class. Our Kit is really complete, the Instruction Book, all components, valves and small items such as wire, nuts, bolts and solder being included. Definitely nothing else to buy.

COMPLETE KIT, £6.19.6. Post free. Credit Terms. Deposit 19 6 and seven monthly payments of £1.0.0. All parts are available separately and our fully detailed list is available free upon request. Instruction Book can be supplied for 2 - plus 3d. postage.

AMPLIFIERS

MULLARD 510 and GEC 912 PLUS

We carry full stocks for all versions of these popular Amplifiers and our price lists are available free.

RECORDING TAPE

Full range of all the best tape and accessories in stock. Send stamp for list.

NEW MULLARD

2 VALVE PRE-AMPLIFIER

Constructional details for this appear in the March issue of Radio Constructor. We can supply all items, write for list.

GRAMOPHONE EQUIPMENT

BSR MONARCH RECORD CHANGER. Latest four-speed model, £8.12.6. Credit Terms. Deposit, £1.4.6 and seven monthly payments of £1.4.0.

RECORD CHANGERS. We have many types in stock—some at special prices. Send for list.

SINGLE RECORD PLAYERS

GARRARD 4SP. The latest Garrard four-speed player unit. Fitted with Garrard GC2 Crystal Pick-up, £8.1.9. Credit Terms. Deposit, £1.4.3 and seven monthly payments of £1.2.6.

COLLARO 4 564. Four-speed unit fitted with the well-known Studio Pick-up "O" or "P", £9.7.0. Credit Terms. Deposit, £1.9.4 and seven monthly payments of £1.5.6. Special Offer of the same unit fitted with "T" (High output) Pick-up only, £7.19.5. Credit Terms. Deposit, £1.5.6 and seven monthly payments of £1.2.0.

BSR T3. Four speed motor with separate Pick-up fitted with BSR T33 cartridge, £4.15.0. Credit Terms. Deposit, £1.5.0 and three monthly payments of £1.6.8.

COLLARO JUMPER. Four-speed motor with separate pick-up. The Pick-up is an ACOS model and is fitted with the HCP50 Cartridge, £4.13.6. Credit Terms. Deposit, £1.3.6 and three monthly payments of £1.6.8.

TRANSCRIPTION UNIT

COLLARO 4T 201. 4-speed with transcription pick-up, £19.10.0. Credit Terms. Deposit £2.18.0 and seven monthly payments of £2.12.0.

MULLARD TAPE AMPLIFIER TYPE "C"

THE MULLARD TAPE AMPLIFIER TYPE C is a new version of the Type B Amplifier. It comprises a recording amplifier and a play-back Pre-amplifier, and is intended to use an existing amplifier for play-back. It uses a Ferricycbe inductor in the treble boost circuit and has a switch for the speed equalising circuits in place of the plug-in unit on the Type B Amplifier. The circuit gives details for use with Brenell, Collaro, Truvox and Lane Tape Decks.

INSTRUCTION MANUAL is available from us free of charge. Please send 4d. in stamps to cover cost of postage. **COMPLETE KIT** containing all components, valves and sundries kit.

KIT A.—With alternative valves, £14.0.0.

KIT B.—With Mullard valves, £15.15.0.

All items available separately. Detailed list free

POWER PACK KIT, £4.0.0. Items available separately. Send for list.

CREDIT TERMS.—**KIT A.** Deposit £21.6 and seven monthly payments of £1.17.6. **KIT B.** Deposit £27.0 and seven monthly payments of £2.2.0.

NEW JASON "MERCURY" FM SWITCHED TUNER KIT

This fine new switched tuner provides all three BBC programmes at the turn of a switch. The front end unit is supplied ready wired and tested. See our advertisement in December PRACTICAL WIRELESS or send for full details. Instruction book 2/3 post free.

COMPLETE KIT, £9.19.0 POST FREE

CREDIT TERMS. Deposit £1.10.0 and seven monthly payments of £1.7.0.

LATEST AVO TEST METERS

AVO METER MODEL 8 MARK II

The latest version of this finest of all test meters is now available from stock. 50 microamp movement (20,000 ohms per volt). Eight DC Voltage, Seven DC Current, Seven AC Voltage, Four AC Current and three ohms ranges. Fully detailed literature available free. Price £23.10.0. Credit Terms. Deposit £3.9.0 and seven monthly payments of £3.3.0. Leather carrying case, £3.0.0.

AVO MULTIMINOR

A new and very attractive pocket size instrument at a modest price. Movement is 100 microamps (10,000 ohms per volt). Six DC Voltage, Five AC Voltage, Five DC Current and two ohms ranges. Descriptive leaflet available free upon request. Price £9.10.0 Credit Terms. Deposit £1.6.0 and seven monthly payments of £1.6.0. Leather carrying case, 32 6.

TRANSISTORS

SURPLUS TYPES

Special offer of the famous Red Spot, 76 each. Four for 27 6. RF Junction Type, Red/Yellow Spot, 21 - AP Junction Type, Yellow Green Spot. Pair in push-pull give 250 mW, 10" each.

MULLARD TYPES

OC70, 21 - OC71, 24 - OC72 Matched Pairs, 00 - All transistors post free.

CREDIT TERMS

Any of the above items can be supplied on Credit Terms. Details are as follows:—

SEVEN MONTHLY PAYMENTS. Deposit 3/- in the £ and balance plus a small service charge (10% of balance, but minimum charge 1d) payable in seven monthly payments.

THREE MONTHLY PAYMENTS. Deposit 6/- in the £ and balance plus a small service charge (5% of balance, but minimum charge 10/-) payable in three monthly payments.

TERMS OF BUSINESS.—Cash with order or C.O.D. Postage extra under £3. We charge C.O.D. orders as follows: Up to 10/- postage and C.O.D. fee, minimum 2/-; Over £3 and under £5, C.O.D. fee only 1/6. Over 15 no charge.


WATTS RADIO (MAIL ORDER) LTD.

54 CHURCH STREET, WEYBRIDGE, SURREY. Telephone: Weybridge 4556

PLEASE NOTE. POSTAL BUSINESS ONLY FROM THIS ADDRESS.

YOU can build any of these at Low Cost!

A MINI TRANSISTOR RADIO

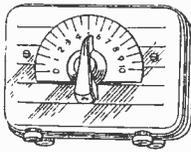

AN IDEAL PRESENT


A two-stage highly sensitive circuit uses a new super high gain transistor coil and mini tuning Total building cost
condenser. Gives remarkable performance. With step-by-step instructions. Beginners can't go wrong. Get your order in while prices are low. Send 2/- for wiring diagram and component price list.

37/6

Includes Plastic case, mini ear-pieces, Batteries etc. All parts sold separately.

Ideal for:
 1. Late night listening.
 2. Children's nursery, etc.

TRANSISTOR POCKET RADIO

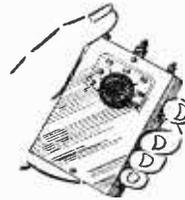


The ideal low cost transistor pocket radio for the beginner. The Two-Stage circuit utilises the new R.C.S. VARILoopstick transistor coil. A specially designed miniature .0005 tuning condenser permits the receiver to be in a case which fits in the palm of your hand. Works for months off small battery costing 7d. Can be built in 30 minutes. PRICE **30/-**
 All components are sold separately, full construction data, including plan to parts for 2/-.

WORLD WIDE SHORT-WAVE RADIO

EXPLORE THE WORLD ON SHORT WAVES!

Can be built from our list of components which can all be purchased separately, covers 10-100 metres and is capable of receiving speech and music from all over the world. Price includes the famous 954 acorn valve and one coil covering 40-100 metres. Provision is made to increase to two or three valves and all components are colour coded. Send 2/- for point to point wiring diagram, layout and price list.

30/-

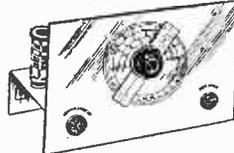

PERSONAL PORTABLE RADIO

THE SET FOR PERSONAL LISTENING


This little set was designed to give you a real personal portable radio that you can listen to anywhere without disturbing others. Use it on camping trips, in bed, in your office. Supplied with detachable rod aerial, it covers all the medium waves 200-500 metres. Average building time one hour. PRICE **30/-**
 Send 2/- for specification, point to point circuit and parts price list.



Post and packing: Under 10/- add 9d.; under 40/- add 1/6; over POST FREE.

R.C.S. PRODUCTS (RADIO) LTD., 11, OLIVER ROAD, LONDON, E.17. (Mail Order only)

CABINETS AND EQUIPMENT

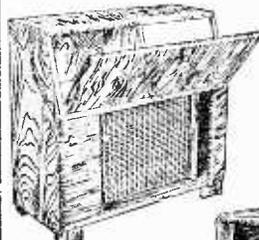


This popular Walnut Bureau Cabinet is veneered with the finest selected Walnut and beautifully polished. It is designed to accommodate any equipment with generous storage compartments.

Walnut £16-16-0
 Natural Oak £18-18-0

Veneered with finest selected walnut, beautifully polished to a medium shade; this attractive cabinet has generous storage space, with motor board sliding out smoothly on metal rollers.

"The Serenade"
 £12.19.6

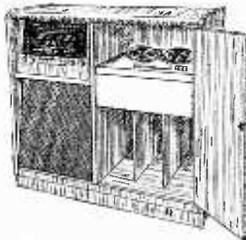We can supply and fit these or any cabinets with equipment. Fitting absolutely free.



Motek K9 Tape Deck £22. 1.0
 Truvon Mk. IV Tape Deck £30. 9.0
 4-speed B.S.H. Changer ... £8.15.0
 4-speed Colbaro Changer ... £9.19.6
 speakers ... from £1.12.0

- 5v. AM Chassis ... £14. 5.0
- 5v. FM Tuner ... £13.15.0
- 5v. Switched FM Tuner ... £15.12.9
- 6v. AM FM Chassis ... £29.17.0
- 7v. AM FM Chassis ... £24. 6.8
- 9v. AM FM Chassis ... £27. 6.0
- Motek KS Tape Deck ... £15. 0.0

Send for comprehensive illustrated catalogue of cabinets, auto-changers, speakers, etc., all available on easy H.P. terms.

LEWIS RADIO

120 (PWM), GREEN LANES, PALMERS GREEN, (N.R. Cock), LONDON, N.13. Tel. Bowes Park 1155/6.

EDDY'S (Nottm.) LTD.

Dept. P.W.

172 ALFRETON ROAD, NOTTINGHAM

This Month's Special Bargains

Midget Battery Eliminators to convert all types Battery Portables (please state Make and Model No.). 57/6. plus 2/6 Postage and Packing.

Single Piece Throat Mikes, 1/- each. Post 6d. Each Extra. Could be used for Electrifying Musical Instruments.

Germanium Diodes, 1/- Each. 10/- Dozen, Post, etc., 4d.

All New and Guaranteed.

Any Parcel insured against damage in transit. 6d. Extra. Surplus New and Guaranteed Valves. All tested before dispatch. Post. etc., 6d. per valve extra. Over £3 Free.

AZ1 12/11	GZ32 12/11	3V4 8/6	6SN7GT
EB91 6/6	KT33C 8/6	5U4G 6/6	10F1 15/11
EBC41 9/6	KT66 14/6	5Z4G 9/6	6BA6 6/6
EBF80 9/6	PCC84 9/6	6BA6 6/6	12A7 7/11
ECC81 8/11	PY80 8/6	6B8G 3/11	12AT6 9/11
ECC82 8/11	PY81 8/6	6B16 7/-	25Z4GT 9/-
ECC83 8/11	PY82 8/6	6F1 13/11	35AS 10/11
ECC84 10/6	U25 13/6	6F13 13/11	35W4 7/6
ECC85 9/6	UCH42 8/11	6F15 13/11	807 4/11
ECH42 9/11	UL41 9/6	6J5G 3/11	954 1/6
EF42 12/11	UY41 7/6	6K7G 2/11	955 3/11
EF80 8/11	1R5 7/11	6K8G 7/11	956 2/6
EF91 6/11	1S5 7/3	6SK7GT	958 3/11
EL84 9/11	1T4 7/3		

S.A.E. with all enquiries.

Tuning of the switched aerial circuits is performed by C4 section of the tuning gang, while the oscillator is tuned by section C19. The A.M. tuning is also ganged to the F.M. tuning, the latter being arranged by the controlled movement of dust-iron cores within the associated R.F. and oscillator coil formers.

The appropriate I.F. signal is applied to the control grip of the common I.F. amplifier valve V2 whose anode circuit is also loaded with transformer primaries tuned to 470 Kc/s and 10.7 Mc/s. Thus the I.F. signal appropriate to the service in use is developed either across L22 or L23 (I5). If the set is switched to the A.M. bands, the signal is developed across the secondary of the A.M. transformer (L22) and is passed to the third diode of the triple-diode-triode valve V3. This diode acts as the A.M. detector, and if the F.M./A.M. switching in this section is followed it will be seen that the volume control (R29) serves as the A.F. load of the detector circuit.

From the volume control, the A.F. signal is applied to the grid of V3 triode section, and an amplified A.F. signal is developed across the load resistor R21 in the anode circuit. From here the signal is conveyed to the control grid of the output valve (V5) through the coupling capacitor C45 and part of a potential-divider R37. The loudspeakers are driven from the anode circuit of V5 by way of a split primary output transformer, this serving to a large extent as a hum neutralising device.

A useful degree of negative feedback is obtained by passing the cathode circuit of the output valve through the secondary of the output transformer. A simple tone control system embraces the tone control itself (R36) and the associated capacitor C50, shunting the anode circuit of V3.

On F.M. the 10.7 Mc/s I.F. signal is developed across L23 (I5) and fed to the diodes of the ratio detector (part of V3). The remainder of the ratio detector comprises L24, the load resistors R24 and R27 in series, the stabilising capacitor C38 and capacitor C41. The A.F. component of the F.M. signal is developed across C41 and, as in the A.M. case, applied to the volume control through changeover switches. The required degree of de-emphasis is given by C43 and R20. From the volume control the A.F. circuits operate the same as for the A.M. case, already considered.

The F.M. Tuner

The double-triode valve (V7) serves both as an earthed-grid R.F. amplifier and a self-oscillating frequency changer. The grid of the R.F. section is "earthed" through C70 and the aerial signal is applied by way of a 70-80 ohm balanced feeder and the matching transformer L2/I3 to the cathode. The matching transformer is responsive over the whole of Band II, but the anode circuit comprising L7 and C68 is of greater "Q" and is variably tuned by means of a dust-iron core.

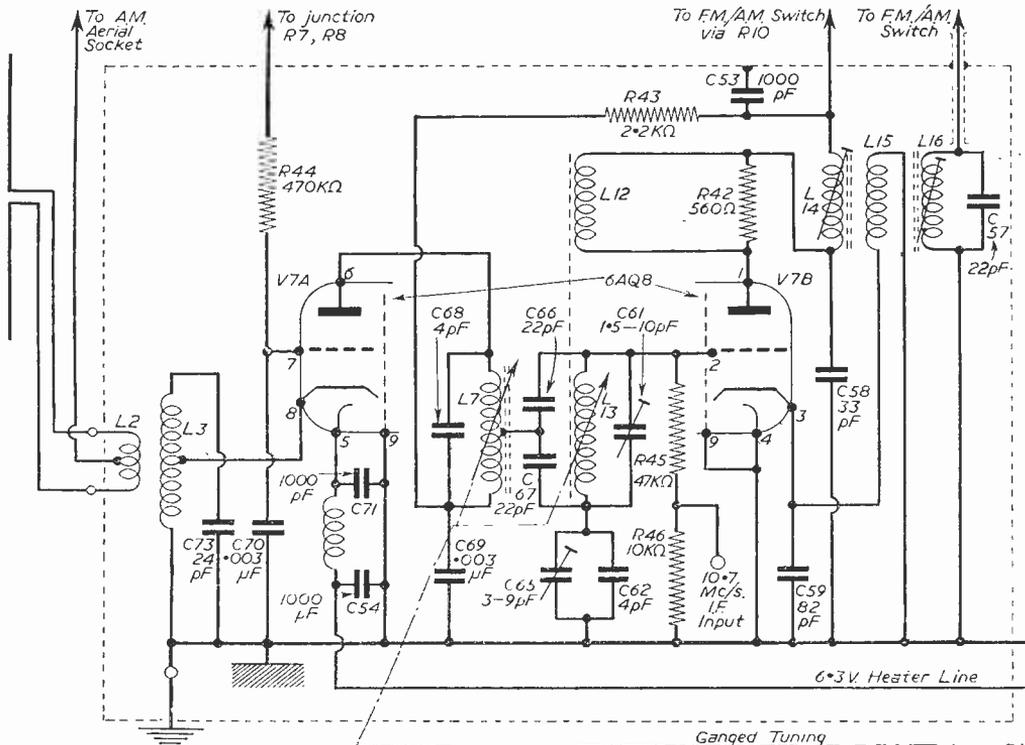


Fig. 1.—The tuner section of the receiver.

L13 and C61 form the oscillator tuned circuit, the core in L13 being ganged to that in L7. The R.F. signal is coupled from the R.F. stage from a point of optimum impedance on L7 to a point of zero oscillator voltage at the junction of C66 and C67. The idea of this is to prevent re-radiation of the oscillator signal through the

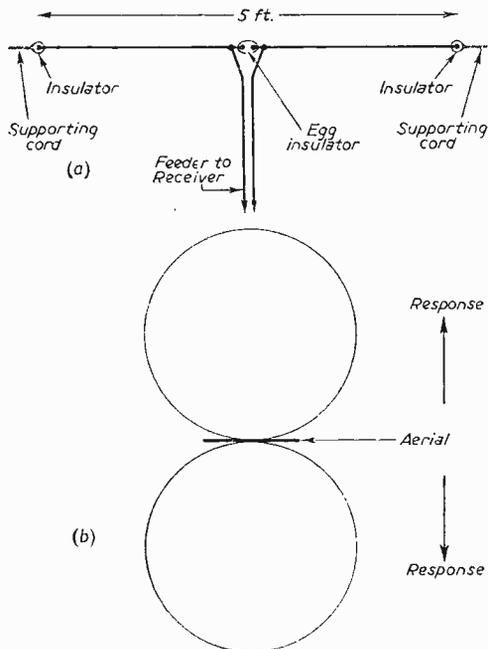


Fig. 4 (a and b).—A suitable aerial and its polar diagram.

aerial by way of the R.F. stage. In common with most F.M. tuners, a bridge circuit is formed by the capacitances of the oscillator valve, C66, C67 and C65, and provided the bridge is in reasonable balance zero oscillator voltage exists at C66/C67 junction. To facilitate adjustment of balance C65 is in the form of a trimmer which should be adjusted only when component changes are made, and then only very slightly for minimum oscillator signal at the aerial.

The Tuning Indicator

L14 forms the anode load of the frequency changer, and a small degree of positive feedback is given by the coupling L15. The 10.7 Mc/s I.F. signal is developed across L16 and is fed to the first F.M./A.M. changeover switch section through coaxial cable.

Signal for the tuning indicator is picked up from the A.G.C. line on A.M., and from across a portion of the ratio detector load resistor (R27) on F.M.

The power circuits are conventional. A fully isolated mains transformer drives a full-wave rectifier (V6) to give 285 volts D.C. at the cathode. The H.T. winding is rated at 250-0-250 volts, and two 6.3 volt L.T. windings supply the rectifier and valve heaters. The 6.5 volt 0.3 amp MES dial lamps are energised from the main heater line.

Servicing Notes

The centre-tap on the F.M. aerial coupling coil L2 enables the F.M. aerial to serve also on the A.M. bands by making the connection as shown on the circuit diagram. It is not necessary to remove this link when receiving F.M.

Internal aerials are contained within the cabinet for both services. However, to ensure interference-free reception for which F.M. is noted, an external horizontal dipole aerial is highly recommended in areas of doubtful signal strength and in locations which fall outside the 25 mile service zone. An elaborate array is called for only in fringe areas, and in most cases a simple attic-type system is adequately suitable. This can be made up with a 5ft. length of insulated wire cut in the centre and connected mechanically by means of an egg insulator. Similar insulators can be used either end to support the aerial in tension by means of cord attached to attic or roof-space beams. The twin feeder is connected to each section of the dipole across the insulator as shown in Fig. 4 (a). As a horizontally-mounted dipole possesses a figure-of-eight polar diagram (see Fig. 4 (b)), it must be orientated so that it is broadside to the transmitter.

For best results on F.M. the aerial signal should be large enough almost to close fully the magic-eye tuning indicator, or to produce, at least, 6 volts of A.G.C. as measured on a 20,000 ohms per volt meter on the 25 volts range across C38 (ratio detector stabilising capacitor).

Excessive distortion on F.M. (A.M. reception normal) accompanied by possible modulation hum and critical F.M. tuning, should lead to a substitution check of the 6AK8 (V3). If this valve is in good order, and the voltage across C38 (positive to chassis) rises on two definite peaks as the receiver is tuned over an F.M. signal.

Alignment

The complete alignment process, which is somewhat complex and requires the use of a wobblator and oscilloscope, need not be performed. Two resistors, each of 47,000 ohms, should be connected in series and then connected across C38. Between the junction of the resistors and point 2 (junction of C41 and R22) of T5 should be connected a 20,000 ohms per volt meter (25 volt range). A 10.7 Mc/s signal (unmodulated) is applied to the control grid of V2 (screen of signal lead to chassis) and the signal voltage raised until either a positive or negative indication is given on the meter. The core in L23 should then be adjusted for zero reading on the meter. After having checked with various levels of signal, the resistors and meter should be removed from the circuit.

Distortion on both A.M. and F.M. should first lead to a test of the voltage, relative to chassis, at the cathode of V5. If the voltage is considerably in excess of 7 volts, C45 should be replaced. It may also be found necessary to replace V5 in this case.

Tuning drift on F.M. is sometimes caused by a faulty 6AQ8 (V7); a substitution check is necessary to prove this possibility conclusively.



VALVES
Guaranteed
All Tested
Before
Dispatch

AC6PEN 6/6	ECF82 12/6	EM81 11/6	P61 3/6	U37 27/10	VU120A 3/6	5Y3G 8/-	6J5GT 5/6	7C6 8/-	20P1 27/10
AC/TH134/9	ECH21 24/4	EY51 13/6	PC884 10/-	U45 15/-	VU39 5Y3GT 8/-	6J5M 6/6	7H7 9/-	20P3 20/11	
ATP 3/6	ECH35 10/6	EY86 17/6	PCF80 13/6	U403 17/5	(MU12/14) 5Z4G 10/-	6J6 6/-	7Q7 9/-	20P5 20/11	
AZ31 17/5	ECH42 10/-	EZ40 9/-	PCF82 12/6	U404 11/10	8/9 6A7 13/-	6J7G 6/6	757 9/6	25A6G 20/12	
CB31 24/4	ECH81 9/-	EZ41 10/-	PCL82 14/6	U801 31/4	VU111 2/6	6A8G 10/-	7Y4 8/6	25L6GT 10/10	
CC33 20/2	ECL82 12/6	EZ80 8/9	PCL83 14/6	UABC80 10/6	W77 8/6	6AC7 6/6	6K6GT 7/6	25Y4 9/6	
CY31 17/5	EF22 8/6	EZ90 8/-	PL38 27/10	UAF42 10/6	W729 13/6	6AG5 5/6	6K7G 5/-	25Y5G 9/6	
DAF96 10/6	EF36 6/-	E1148 2/6	PL81 16/-	UAF42 10/6	X65 12/6	6AK5 6/6	6K7GT 7/6	25Z4 9/6	
DF96 10/6	EF37A 12/-	E232 12/-	PL82 9/6	UB41 9/6	X78 22/3	6AL5 6/6	6K7M 6/6	25Z5 10/-	
DK96 10/6	EF39 6/6	H30 5/-	PL83 11/6	UBC41 10/-	X79 11/6	6AM6 9/6	6K8G 8/6	25Z6 10/-	
DL96 10/6	EF40 13/6	HL23DD 8/6	PP225 3/11	UBF80 9/6	Y63 9/-	6AQ5 7/6	6K8GT 9/6	30F5 12/6	
DM70 8/6	EF41 9/9	HL29 12/6	PX25 12/6	UCC84 2/309	Z309 11/6	6AT6 8/6	6K25 20/11	30FL1 12/6	
EASO 1/6	EF42 14/-	K40N 9/-	PY80 9/-	20/11 2359	11/6	6AU6 10/6	6L6G 10/6	30P4 21/7	
EABC80 10/6	EF50 4/-	KF35 8/6	PY81 10/-	UCF80 23/-	Z759 11/6	6B4 5/-	6L7 7/6	30P12 12/6	
EAC91 7/6	EF54 6/-	KK32 23/-	PY82 8/6	UCH42 10/6	IA3 3/6	6B8G 4/-	6N7 7/6	35L6GT 9/6	
EAF42 10/6	EF55 10/-	KL32 8/6	PY83 10/-	UCH81 11/6	IA5GT 6/6	6BA6 7/6	6P25 13/6	25B6 10/-	
EB34 2/-	EF80 9/6	KT24 5/-	PE230 20/11	UCL82 23/-	IA7 12/6	6BE6 8/-	6P28 27/10	12BH7 11/6	
EB41 9/6	EF85 9/6	KT33C 10/-	PEN44 27/10	UC83 25/9	IC2 11/6	6BG6G 24/4	6Q7GT 9/-	12CB8GT 8/-	
EBC33 7/6	EF86 13/6	KT36 27/10	PEN45 27/10	UF41 10/6	IC5GT 12/6	6BH6 16/6	6A7GT 8/-	12D6GT 3/6	
EBC41 10/6	EF89 10/-	KT55 13/6	PEN46 27/10	UF85 10/6	ID6 12/6	6Bj6 9/6	6S7G 7/6	12J5GT 4/6	
EBF80 10/6	EK32 8/6	KT66 15/-	PEN47 27/10	UF89 10/6	IHSGT 10/6	6BR7 11/6	6H5H 6/6	12J7GT 10/6	
EBF89 18/1	EL32 5/6	KTV63 7/6	PEN48 27/10	UL41 10/6	IA4 6/6	6BW6 8/6	6S7 8/6	12K7GT 8/6	
EBL21 24/4	EL33 20/2	KTZ41 8/6	PEN49 27/10	UL46 24/4	IN5 10/6	6C4 7/6	6S7G 7/6	12K8GT 13/6	
EC32 6/6	EL38 27/10	ME41 7/6	PEN50 27/10	UL46 24/4	IR5 8/6	6CSGT 6/6	6S7GT 9/3	12Q7GT 8/6	
ECC40 12/6	EL42 12/6	MH41 7/9	TP25 27/10	VR116 4/3V4 9/6	6F13 14/6	6F5 14/6	6X5G 7/6	1986G 9002 5/6	
ECC84 10/3	EL84 10/6	N37 18/1	U10 10/6	VR150/30 4D1 3/6	6G6G 4/6	630L2 12/6	24/4 24/4	9003 5/6	
ECC85 9/6	EM34 10/6	N78 12/6	U22 8/-	5R4GY 9/6	6H6 2/6	7B7 8/6	20D1 14/6	9004 5/6	
ECF80 13/6	EM80 10/6	OZ4 5/6	U24 12/6	V570 3/6	6H6GT 2/6	7CS 8/6	20F2 27/10	9006 5/6	

HEATER TRANSFORMERS

230 v. Input 2 volt 3.5 amp.	5
230 v. Input 2 volt 3.4 amp.	8 3
230 v. Input 4 volt 1.5 amp.	5 6
230 v. Input 4 volt 3.0 amp.	10
230 v. Input 5 volt 2.0 amp.	10
230 v. Input 6.3 volt 1.5 amp.	6 6
230 v. Input 6.3 volt 1.5 amp.	6 9
230 v. Input 6.3 volt 3.0 amp.	10
230 v. Input 12 volt 1.5 amp.	5 9
Solid Dielectric Condensers.—0001, 0002, 3005, 3002, 3003	4 6
EMSO Type Tuning Indicators Escutcheon	2
Avo Minor Case with Carrying Strap	7 6
This Brayheal Turret Converter.—Complete installation instructions, plug-in facilities for over 100 popular models of T.V. sets of standard I.F. ranges	£27.0
Illustrated leaflets available. Adapters Price	7 6
Implosion Guards for 17in. tubes outside dimensions 17in. x 12in. Brown escutcheon	7 8
Postage	3

WB "Stentorian"

Model HF 812 Die cast chassis	84 6
.. HF 1012	89 6
Universal speech coils	9 6
Co-axial Cables, etc.	yd.
Aerolite Aerials 1397, semi-8 spaced	6d.
Ashton Coaxial cable solid	6d.
Ribbon feeder (Flat) 300 ohms	6d.
12 Yaxley Type Switches , Various Combinations. All brand new	doz.
Full Range Condensers available from stock. Cardboard covered wire-ended types.	9
.. 100 pfd. 450v.	1 11
.. 200 pfd. 450v.	2 9
.. 500 pfd. 450v.	4 2
.. 1000 pfd. 450v.	2 3
.. 16 x 16 mfd. 450v.	4 6
.. 32 mfd. 450v.	3 6
.. 32 x 32 mfd. 350v.	4 6
.. 16 x 16 mfd. 500v.	5 2
.. 8 x 8 mfd. 500v.	4 7
.. 16 x 8 mfd. 500v.	4 7

Standard Can Types:

2 1/2 x 2 1/2 x 16 mfd. 350v.	3 8
32 x 32 MA 450v.	6 8
60 x 60 mfd. 350v.	4 6

These are just a few of the types—good stocks of low voltage electrolytics, etc., etc.

CHASSIS

Aluminium Undrilled with Reinforced Corner. Available in the following sizes:—

6in. x 6in. x 2 1/2in.	4 6	12in. x 8in. x 2 1/2in.	8 6
8in. x 6in. x 2 1/2in.	6 3	14in. x 8in. x 2 1/2in.	8 6
10in. x 7in. x 2 1/2in.	7 3	14in. x 9in. x 2 1/2in.	12 6
12in. x 8in. x 2 1/2in.	6 9	16in. x 8in. x 2 1/2in.	8 6
12in. x 8in. x 2 1/2in.	6 9	16in. x 10in. x 2 1/2in.	14 6

All are torsion-ideal for radio receivers—amplifiers—power packs, etc.

PRE SET CONTROLS

Available wire wound 1K and 10K ohms, 2K ohms, 30K ohms. Available carbon track 50K, 100K, 1 Meg., 1 Meg., 2 Meg., 5K ohms, 1 Megohm.

VARIOUS MAKES and TYPES 150K ohms. All one price.—1,9 cu.

LOUDSPEAKER UNITS

Make	Type	Size	Price
Plessey	Square	3in.	19 6 each
Leetron, Plessey	Round	5in.	17 6 each
Goodmans, Plessey	Round	6 1/2in.	18 6 each
Goodmans, R. & A.	Round	10in.	19 6 each
Plessey, R. & A., Blue	Round	10in.	25 6 each
Blue	Elliptical	7in. x 4in.	19 6 each
Blue	Elliptical	10in. x 6in.	25 6 each

All the above are PM units with 2 to 3 ohms speech coils.

MTC 12in. heavy duty 20 watt model 12 ohms 17 6

Speech Coil 5 5 0

3in. Mains Energised Speaker £1 1 0

3in. Mains Energised Speaker £1 0 0

All have field coils of approx. 600 ohms.

SPECIAL OFFER

Just a few 3in. units by Goodmans and Leetron fitted with standard output transformer. £1 1 6 each

3in. P.M. Speaker Units with Output Transformer removed from equipment. 11 6 each

OUR 1958 ILLUSTRATED CATALOGUE is now available. Send 1/- in stamps for your copy.

MAINS TRANSFORMERS

3 Way Mounting Type.

MT1
Primary: 200-220-240 v. Secondaries: 250-0-250 v. 80 v. A 0-6.3 v. 4 amp. 0-4 v. 2 amp. Both tapped at 4 v. 21 9 each.

MT2
Primary: 200-220-240 v. Secondaries: 250-0-250 v. 80 v. A 0-6.3 v. 4 amp. 0.5 v. 2 amp. Both tapped at 4 v. 21 9 each.

MT3
Primary: 200-220-240 v. Secondary 20 v. 2 amp. Taps at 3 v., 4 v., 6 v., 8 v., 9 v., 10 v., 15 v., 18 v., 20 v., 24 v., 21 9 each. 3 way unit Packing please add 2/- per transformer.

ALPHA

RADIO SUPPLY CO.

103 LEEDS TERRACE
WINTON STREET
LEEDS 7

TERMS: Cash with order or C.O.D. Postage and Packing charges extra, as follows: Orders value 10/- add 1/-; 20/- add 1/6; 40/- add 2/-; £5 add 3/- unless otherwise stated. Minimum C.O.D. fee and postage 3/-. All single valves postage 6d. Personal Shoppers Monday-Friday 9 a.m. to 5 p.m. Saturday 10 a.m. to 1 p.m.

FREE TO AMBITIOUS ENGINEERS!

This 148-page Book



'ENGINEERING OPPORTUNITIES' is a highly informative guide to the best-paid Engineering posts. It tells you how you can quickly prepare at home on "NO PASS—NO FEE" terms for a recognised engineering qualification, outlines the widest range of modern Home-Study Courses in all branches of Engineering and explains the benefits of our Employment Dept. If you're earning less than £20 a week you cannot afford to miss reading this unique book. Send for your copy to-day—**FREE.**

--- FREE COUPON ---
Please send me your FREE 148-page "ENGINEERING OPPORTUNITIES"

NAME
ADDRESS
Subject or Exam.
that interests me.....
British Institute of Engineering Technology
409 B, College House, 29-31, Wright's Lane,
Kensington, W. 8.

WHICH IS YOUR PET SUBJECT ?

Mechanical Eng.
Electrical Eng.
Civil Engineering
Radio Engineering
Automobile Eng.
Aeronautical Eng.
Production Eng.
Building, Plastics,
Draughtsmanship,
Television, etc.

GET SOME LETTERS AFTER YOUR

NAME !
A.M.I.Mech.E.
A.M.I.C.E.
A.M.I.P.E.
A.M.I.M.I.
L.I.O.B.
A.F.R.Ac.S.
B.Sc.
A.M.Brit.R.E.
CITY & GUILDS
GEN. CERT.
OF EDUCATION
etc., etc.

G2AK This Month's Bargains

HI-FI EQUIPMENT

AVAILABLE FOR IMMEDIATE DELIVERY.

Amplifiers, speakers, pick-ups by
Gramplan Leak Quad
Rogers R.C.A. Spectone
W.B. Wharfedale. etc.

MULTI-WAY CABLE. 10-way (5 pairs). Screened and plastic covered. 2/- per yard. P. & P. 1/6.

100 Kc's XTALS. by famous American makers. 3-pin based holder. New condition. worth £3.10.0. Only 25/- post free.

PLUG IN NOISE LIMITERS. 3 Position Limiting. No Rewiring. Best with H.R. Phones. Only 8/6. P. & P. 1/6.

HEADPHONES. H.R. Type 4,000 ohms, very sensitive. Only 12/6 pr. Post 1/6. C.L.R. type (low res.) 8/6. Post 1/6.

SEMI-MIDGET COMBINED I.F. TRANSFORMERS. 10.7 Mc's and 465 kc's (can be used on 10.7 Mc's or 465 kc's only). 9/11 per pair, postage 9d.

CHOKES. 2.5 mH. 120 mH pie-wound R.F. chokes. 2/- each. 3 or more post free.

AERIAL WIRE. Copper. 7-25 stranded: 140ft., 10/-; 70ft., 5/-. Hard Drawn 14g.: 140ft., 17/-; 70ft., 8/6. P. & P. 2/.

RIBBED GLASS 3in. AERIAL INSULATORS. 1/6 ea., or 6 for 7/6. P. & P. 1/6.

CONDENSERS. 8 μ F 600 v. Trop. 750 v. normal condensers. NEW. ex W.D. stocks, 5/6. P. & P. 1/6.

ABSORPTION WAVEMETERS, 3 to 35 Mc's in 3 switched bands. Complete with indicator bulb. 17/6 post free.

No C.O.D. on orders under £1.

Please Print Your Name and Address.

CHAS. H. YOUNG LTD.

Dept. 'P' 110, Dale End, Birmingham, 4. (CEN. 1635)

BIET

ALFRED PADGETT

40, MEADOW LANE, LEEDS, 11
Tel.: CLECKHEATON 89

BRAND NEW WESTON U.S.A. MODEL 686 SOCKET SELECTOR.—Complete with Octal UX 4, 5, 6, 7, Local B.7G. Valve selectors and Valve data chart for more than 200 valves. If you have a meter it is a must. Price, 12/6. Post 2/6.

ONLY 300 TO OFFER PAPER CONDENSERS.—2 mfd. or 1 mfd. 450 volts working. 6d. each. Post 1/-, 4 mid., 1/-, post 1/3.

NEW METAL RECTIFIERS.—250 volts at 60 mills, 2/6. post 1/3. 150 volts at 40 mills, 1/-, post 1/3.

NEW EF50 VALVES.—Four on a strip with valve holders and locking rings, 10/- complete, post 2/-. With Ired Sylvania valves, 12/6, post 2/.

MIXED B.A. NUTS AND BOLTS.—1 1/2 half lb. 2/6 lb., post 1/6.

NEW 185V. 100W. HALF WATT RESISTORS.—Box of 50, 1 meg only. 7/6, post 9d.

CELLULOSE CEMENT.—Will soon fix that loose base, 1/6 bottle, post 1/3.

NEW HIGH-POWER TUBE 3845.—The cleaned up 1355, complete with 7 VR65 valve less 5U4 and 6X5, but otherwise complete. 12/6. Loss valves, 6/6. Carriage 8/-.

NEW POT METERS.—250 Kc. and 500 Kc. Good spindle length. 6d. each, post 9d.

NEW T.V. COAX. CABLE.—Any band. Worth 13 per yard. My price, 6d. per yd. post free. Also Mike Cable, 4d. per yard, post free.

NEW STOCK OF G.E.C. GERMANIUM DIODES.—9d. each, post 3d.

NEW VALVES, EX EQUIPMENT.—All at 1/- each, Post 9d. VR65, VR137, 802, (P222), VU111, VR6, 12SH7, 12SJ7, 11L510, 6X5, PT15 1908, 1/6.

All at 6d., post 9d. 6U6, VR62, VR54, 12116. All at 2/-, post 9d. 6J5, 606, 6K7.

G.E.C. 250 VOLT 15 AMP. BAKELITE FUSE HOLDERS. fitted with cartridge type fuse, 1/- each, post 3d.

Post orders of £1 or over send only 2/- post. Orders £2 or over post free.

RADIO-CONTROLLED MODELS

Contains both the radio and mechanical side of the equipment necessary and describes in detail a number of practical examples of the application of radio control.

By F. J. CAMM. Postage 6d.

PORTABLE TRANSISTOR RECEIVER. By S. W. Amos. 2/6. Postage 4d.

THE RADIO AMATEUR'S HANDBOOK. By A. R. R. L. 1958 ed. 32/6. Postage 1/9.

A BEGINNER'S GUIDE TO RADIO. by F. J. Camm. 7/6. Postage 6d.

LOW-COST HIGH-QUALITY AMPLIFIER. By P. J. Baxandall. 3/6. Postage 4d.

MAGNETIC RECORDING HANDBOOK. By R. E. B. Hickman. 21/-. Postage 1/.

RADIO DESIGNER'S HANDBOOK. By F. Langford-Smith. 42/-. Postage 1/9.

M. K. ELECTRONIC TUBE HANDBOOK. 5/-. Postage 1/-.

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS of British and American Technical Books

19-23 PRAED STREET, LONDON, W.2.


Complete catalogue 6d. Phone: PADDINGTON 4185. Open 6 days 9-6 p.m.

TELETRON TYPE FX.25



Self-tuned, Dual-wave Ferrite Rod Aerial, 15/- each.

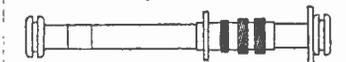Designed for use in pocket Transistor receivers. Descriptive folder with circuit-component layout, and wiring instructions for a three-Transistor regenerative receiver. Price 6d. NO aerial, earth or tuning condenser required. Operates speaker from 3 Penlight cells. All parts, including cabinet and chassis, available from component stockists.



Miniature Transistor H.T.s & Osc coil for 315 kc's, 6/6 ea. FRM 2 Transistor Ferrite Rod Aerial, 10/-.

Available from component stockists. Stamp for complete lists and circuits.



THE TELETRON Co. Ltd.
266 Nightingale Rd., London N.9

HOW 2527

Open to Discussion



The Editor does not necessarily agree with opinions expressed by his correspondents

A Condenser Tester

SIR.—I should like to thank you for the Condenser Tester Design published in the February issue. I made this up—a total of two evenings spare-time work and dug out all my old condensers. I found that at least 75 per cent. were worthless, or at least only fit for throwing away, and I am sure that others will find this of great value in saving time by using dud components or wasting time wiring them into sets only to have to throw them out afterwards.—H. YOUNG (Woking).

"Front to Back"

SIR.—I am ashamed to say that recently, during the alignment of a superhet. I placed the leading lady in the back row of the chorus. That is to say, I plugged a 6BE6 frequency changer into the output valve's holder, which was correctly wired for a 6AK6 output pentode. She performed with great volume and purity of tone in this unaccustomed position, and I was only apprised of my error by the low bias voltage on her cathode. I am glad to say that her vital statistics have not been affected by this indignity.—R. PAGE, LI. COL. R.A.E.C. (Singapore).

A Short-wave Hint

SIR.—Although I am not a transmitter I always read the Transmitting Topics article, and the recent details concerning aeriels have brought up a point which I should like to pass on. I am mostly interested in short waves and have tried everything in the way of an aerial, from a wire indoors across the ceiling, to a most elaborate long wire out in the garden. I have found however, that the best results were gained when I had a wire hanging from a bedroom window upstairs down to the room in which the set was placed. I have since found that most short-wave broadcasting stations abroad use a mast radiator and thus the vertical wire is most desirable. If therefore you find that your short waves are not coming in well, try a wire as mentioned above, but keep it at least 3 feet from the wall and insulate it very thoroughly at the top and bottom. The glass type of ex-government insulator is to be recommended.—G. R. JOHNS (Reading).

Wrong Speed Records

SIR.—Some time ago I became interested in hi-fi record reproduction and bought a most

expensive outfit. I have played many records but find that there is one most disturbing fault which I should very much like to overcome, and I wonder if one of your vast number of readers may have come up against the same problem and found a ready solution. My main interest is in organ music and I happen to own a small electronic organ which is in the same room as the record player. I find that with quite a number of organs, the speed of recording is such that the discs are not in tune. No doubt this also applies to many other vocal and orchestral records. I can play my organ with most broadcast items, except at certain times when a recorded item is relayed and this also suffers from the wrong speed. The problem is,

that the record player has fixed speeds of 33 $\frac{1}{3}$, 45 and 78, and no adjustment is available to these. It would appear that a very small variation each way would be all that is necessary but I cannot see any player on the market with this facility. I have tried small friction brakes and although they will slow up the record, I cannot speed them up, and one or two discs require a slightly higher speed to get them at the right pitch. Has any other reader met this difficulty and perhaps found a solution?—G. F. WATTS (Edgware).

Stereophonic Reproduction

SIR.—I notice that great strides are being made with stereo reproduction, including the development of gramophone records embracing this feature. It would appear that the means of obtaining this is, however, somewhat cumbersome and necessitates two amplifiers and two loudspeakers. If two loudspeakers are placed in a room as recommended, surely it is essential that you should sit exactly in the centre, and also how can the spacing of the speakers be decided? With stereoscopy the two pictures may be placed exactly the same width apart as the eyes, and then viewed through a suitable optical system. With the ears, however, there is quite a different effect, and many sounds we hear come from a single source. There is therefore no need for two speakers and the sound from a piano, say, played by stereophonic means from two speakers situated some feet apart would surely produce a wrong impression in the mind of a listener? Perhaps an orchestra

Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying commercial or surplus equipment. We cannot supply alternative details for receivers described in these pages. WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE. If a postal reply is required a stamped and addressed envelope must be enclosed with the coupon from page iii of cover.

might sound better for being produced from two sources, but vocalists, single instruments and speech surely should come from a single source only and our two ears supply the stereophonic effect.—R. WILLIAMS (Cardiff).

An Ancient Set

SIR.—I see that Thermion recently had the pleasure of hearing an old set (February issue) and was surprised at the results. I have a set still in use which was new many years before the war and apart from one valve replacement is still apparently as good as new. I believe that it has, in fact, deteriorated during the years, but so slightly as to be imperceptible, and it still brings in the foreigners. I use headphones, and can roam the world almost any night and apart from having to manipulate three controls I find the selectivity much better than most modern receivers. This is due, in the main, I think, to the use of variometer tuning and a remarkably smooth reaction control. The variometer is air-spaced and wound with fairly heavy gauge wire, whilst the reaction control is a combination of condenser and potentiometer. Batteries supply a quiet and steady power, and a pair of Brown's super headphones give crystal clear reception. I should like to see some of these older circuits brought out and modernised as I am sure they have good features.—B. BURTON (Leicester).

Echoes on Tape

SIR.—I have a tape recorder which has given many hours of pleasure, but I have come up against a snag. Many modern broadcasts owe their fine effects to a simple device known as "echo," and I believe this is put in either by a second mike placed at a distance, by a loudspeaker in a special room facing a mike, or by a special type of cable known as a "delay cable" in the circuit. None of these is practicable for recording at home, however, and I wonder if any one has found a simple way of producing an echo without using another recording head. I wish to record certain orchestral items from the radio, as well as my own piano playing, and I should like to put echo in some of those items which seem to sound "flat." There must surely be some fairly simple way in which this can be done, but so far have never seen anything published on the idea. What about it, fellow readers?—G. B. JAMES (N.W.).

Using Old Eliminators

SIR.—There must be many listeners, like myself, who are lumbered with an old type battery eliminator which they used when they first had mains facilities and wished to run their battery sets. These units delivered low H.T., round about 100 to 150 volts at about 30 or 40 mA, and in many cases contain also a trickle charger for keeping a 2-volt battery up to scratch. It seems a pity to throw these units away, and I wonder if any reader can suggest a really useful way of putting them into commission. It does not appear to me that there is anything in them which can have deteriorated and I am sure there must be some way of turning them to use.—H. YOUNG (Reading).

A Supersensitive Transistor Receiver

SIR.—I note that in the article in the March issue describing the above receiver the type of battery which was specified was given as Mallory RM250. I should like to point out that that should, in fact, have been quoted as RM625, and, as stated, is available from practically any Boots stores.—F. BRINTON (S.W.).

Transistors

SIR.—I have read several articles recently on transistors, and I note that these are easily damaged when soldering them into a receiver. Why do not the makers supply these in the form of plug-in units? Surely it would not be difficult for a manufacturer to provide them with a small paxolin or similar base and pins so that they could be inserted in small holders similar to miniature valves. This would also facilitate servicing, by enabling alternatives to be tried out easily, instead of having to unsolder three wires and solder up three new ones. Can there be any definite reason why a base is not fitted, or why they cannot be made "plug-in"? Perhaps the manufacturers will let us know.—F. R. EAMLS (Finchley).

Baby Alarms

SIR.—I built some time ago a small baby alarm and I know there are dozens of these in use. They are only small amplifiers which have a mike and they pick up the cry of a baby and superimpose it on the radio or television so that you can hear it. I do not know sufficient about the technical side but it appears to me that it would be much better if it could be arranged that, when the baby cried, when the cry reached a certain volume it could cut out the sound coming from our radio or TV and the cries only would be heard from the loudspeaker. Couldn't this be done, say, with a relay or something and an adjustment provided so that you could set it so that weak cries or murmurings had no effect, but when the baby really got going, then our radio cut out and only the cries come through the speaker? I should like to see something on these lines.—G. B. FAIRBAIRNS (Hove).

Novices' Band

SIR. I would like to say how much I agree with the idea of a novices' band. In my opinion a high frequency band should be used and a limited power of 20 watts on C.W. No phone to be used.

One more point which I would like to state is that I think a £1 per annum charge by the G.P.O. would ensure that no one who just wanted to make a nuisance of himself would come on to the band.—G. J. KNOCK (Tonbridge).

CALLING THE WIMBORNE CIRCUIT FANATIC.

Will the anonymous reader in the Wimborne area of Dorset who has been inundating us with circuits without a covering letter, please let us have his name and address.

NO EXPERIENCE NEEDED TO MAKE THESE CHEAP RADIOS!

LOOK!

BUILD THIS POCKET RADIO FOR ONLY 37/6




AT LAST! In response to many requests we now present the **HIGH EFFICIENCY PENTODE "SKYPOCKET,"** a beautifully designed precision **POCKET RADIO.** No radio knowledge needed!—**EVERY SINGLE PART TESTED BEFORE DESPATCH!**—our simple, pictorial plans take you step-by-step. This set has a remarkable sensitivity due to painstaking design. Covers all medium waves 200 to 550 Metres. Size only 5 1/2 in. x 3 in. x 2 in. in Strong, transparent case with panel, cover and ivoryine dial. A really personal phone, pocket-radio with **DETACHABLE ROD AERIAL.** Self-contained all-dry battery operation. Average building time 1 hour. **Total Building Cost—including Case, High Efficiency Pentode Valve, etc., in fact, everything down to the last nut and bolt—ONLY 37/6, with plans, Postage etc., 2/-.** C.O.D. 2/- extra. (Parts sold separately. Priced Parts List, etc., 1/6.) Demand is certain to be heavy—**SEND TODAY!**



47/6

Build this exceptionally sensitive high efficiency Pentode radio. Uses unique assembly system and can be built by anyone without any radio knowledge whatever in 45 minutes. Handsome black-crackle steel case with specially made black and gold dial with stations printed. Size of radio only 6 1/2 in. x 5 in. x 3 in. Covers all Medium and Long waves—uses only one all-dry battery. H.T. consumption only 1 to 1.5 mA. Uses personal phone. Ideal for Bedroom, Garden, Holiday, etc. Many unsolicited testimonials. **Mr. Norton, of Oxted writes: Yesterday evening on the Medium waveband, I counted 32 separate stations! I am very pleased with the set, which is well worth the money. BUILD THE "SKYRONA" NOW!** Total building cost—everything down to last nut and bolt—**47/6** (Postage, etc., 2/-) with full set of clear, easy-to-follow plans. (Parts sold separately. Priced Parts Lists, etc., 1/6.) C.O.D. 2/- EXTRA.

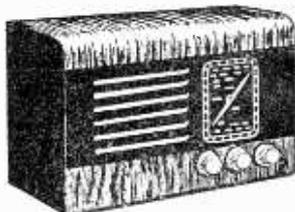

Total building cost including choice of beautiful walnut veneered cabinet or ivory or brown bakelite. This is the lowest possible price consistent with high quality. No radio knowledge whatever needed... can be built by anyone in 2-3 hours, using our very simple easy-to-follow diagrams. The terrific new circuit of the "OCEAN-HOPPER" covers all medium and long waves with optional negative feedback, has razor-edge selectivity, and exceptionally good tone. Price also includes ready drilled and punched chassis, set of simple easy-to-follow plans—in fact, everything! All parts sparkling brand new—no junk! Every single part tested before despatching. Uses standard octal-type valves (6XG high-frequency pentode feeding into 6J5G audio-bend detector triode, coupled to 6V6G powerful output beam-power tetrode, fed by robust rectifier. For A.C. Mains, 200-250 Volts (low running costs—approximately 18 Watts!) Size 12 in. x 6 in. x 5 in. **Build this four range powerful midset NOW.** All parts and set of plans, **£5.7.6.** (Post and packing 3/6.) Parts sold separately. Priced Parts List, 1/6. C.O.D. 2/- EXTRA.

107/6


Build This TRANSISTOR POCKET SET For Only 47/6!



FEW ONLY AT 95/-!

NEW in maker's sealed cartons—limited quantity of the famous 4-speed record player units, exceptionally easy to fix, with lightweight pick-up, incorporating "Acos" crystal turnover head and separate sapphire styl for Standard and Long-Playing. With full instructions and fixing plans. **Unbeatable price 95/-**, plus 3/6 Post, Packing, etc. C.O.D. 2/- extra. **RUSH YOUR ORDER NOW—BEFORE IT'S TOO LATE!**

WE'VE DONE IT AGAIN!... our design department in response to a great many requests have designed this "SKY PIXIE" **Vest-Pocket TRANSISTOR RADIO** which gives a superb performance. It is highly sensitive. Size only 4 1/2 in. x 3 in. x 1 1/2 in., the weight under 7 ozs.—yet it is a **TWO-STAGE** receiver covering all medium waves, working entirely off a tiny "pen-light" battery, which costs 6d.—fits inside the case—and lasts many months. Uses personal phone and has push-button **LUMINOUS** On/Off Switch. Every part tested before despatch! **SPECIAL STEP-BY-STEP PLANS** for **ABSOLUTE BEGINNERS.** Total building cost including case, transistors, etc.—everything down to the last nut and bolt—**ONLY 47/6** with plans, Postage, etc., 2/-. C.O.D. 2/- extra. (Parts sold separately. Priced parts list, etc., 1/6.) As the building cost is absolutely "rockbottom" (it might increase later) **DEMAND WILL BE VERY HEAVY—RUSH YOUR ORDER TO-DAY!**

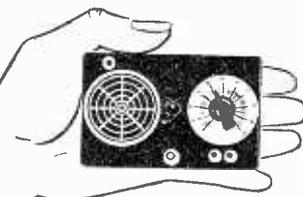

ONLY £8-10-0!

BRAND NEW—NOT SURPLUS! In maker's sealed cartons. Latest U88 "Monarch" 4-speed record player complete with High-fidelity "turnover" head. Type HGP 37-1. Capacity of 10 Records, plays 12 in., 10 in. and 7 in. intermixed in any order. 78, 45, 33 and 16 r.p.m. For A.C. mains 100 to 250 volts. Exclusive "mardisk" selector gives quickest and quietest change ever. With full instructions and fixing plans. **Limited Quantity at £8.10.0,** plus 4/6 Post, Packing, etc. **WHY PAY MORE! SEND NOW WHILE STOCKS LAST!**—modernise your radiogram and increase its value.

BUILD THIS TRANSISTOR SET FOR ONLY 35/-
VERY SPECIAL OFFER WHILE STOCK OF PARTS LASTS!—The "Sky Scout" Pocket two-stage transistor set, size only 4 in. x 3 1/2 in. x 4 in. Covers all medium waves and works entirely off tiny "pen-light" battery which costs 6d. and fits inside case. All parts tested before despatch. Can be built for 35/-, plus 2/- post and packing, including Case, Transistor, **STEP-BY-STEP PLANS FOR ABSOLUTE BEGINNERS,** nuts, bolts, etc. (C.O.D. 2/- extra.) Parts sold separately, priced parts list, etc., 1/6. **VERY SIMPLE TO BUILD.**



CONCORD ELECTRONICS

69, PRESTON STREET, BRIGHTON

Dept. PWU

Orders receive prompt attention. Cheques accepted. Cash on delivery 2/- extra. Please print name and address in block letters. Suppliers to Schools, Universities, Government and Research Establishments. Complete range of components and valves stocked. Regret no C.O.D. abroad.

LOOK!

Specially made for
YOUR Home Workshop . . .



New improved construction from one of the toughest imported hardwoods . . . top boards specially kiln-dried, joints through bolted. Top and bottom rails morticed into the legs and front legs let into front board provide absolute rigidity. 3-Way bench top by simple adjustment.



30 - DOWN or 40 - with vice

7-Wooden Woodworker's Quick Release Vice, illus. £3.10.0 ex. fitted free

Length 4' 6"
Width 2' 0"
Height 2' 9"

£7.10.0
incl. p.d.

To: J. POWELL & SON (Dept. C. TIMBER MERCHANTS, PENSNETT, BRIERLEY HILL, STAFFS.

Please forward fully comprehensive price lists, including full details of the bench illustrated and the model which incorporates drawer and cupboard.


NAME

ADDRESS



Years of experience and technical skill combined with many outstanding features including three speed control knob make this a truly fine deck.

Patents pending.
Details on request.

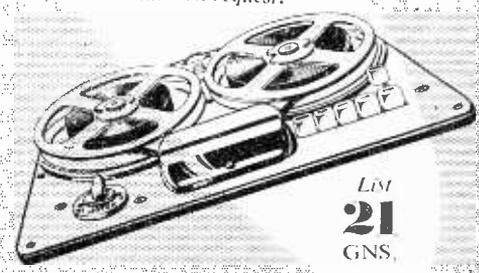

LIST 21 GNS.

MODERN TECHNIQUES

Wedmore Street, London, N.19. Tel: ARCHway 3114

NEW SURPLUS

MODULATOR TYPE 67. Contains complete A.C. mains power supply. Input 230 v. 50 c.s. (0 P 350 v. 120 m A trans. rated 200 m A). 6.3 v. 5 amps. heavy duty choke. 5Z4 and 11 other valves. Dozens of components, switches, pots., etc. BRAND NEW AND BOXED. only 45/- ea. 3 for £6. R107 UNITS. 1 R.F. front end for R.F. Mix. Osc. 3 bands 1.2-16 m c/s. with large h.t. moon calibrated dial and slave modulation driver. 2. Power pack for either 12 v. D.C. or A.C. mains. Both units BRAND NEW AND BOXED and only £3 the pair. less valves and vibrator. This is the basis of a really first class receiver.

WHIP AERIALS. 4 section screw-in. 12' 6" long (part of BC610 whip). 15' 6" ea.

COMMAND RECEIVERS BC454B. 3-6 mcs. New boxed with 6 valves. 45/- ea.

TRANSMITTER REG VALVES. 17 MK. 2. 44-61 mcs. Used good condition with valves. H.R. phones, mike and circuit. 45/- ea. or TWO for 79/6.

FEW ONLY RA10DB receivers. used good condition. 99/6 ea. with valves.

PERFORMANCE METERS. No. 2. 230 v. 50 c.s. input. Transformer 250 v. 30 m A. 6.3 v. 1 1/2 amps (60 m A H.T. can be taken safely). 20 H. choke. 5Z4. Y65 magic eye. 2. EF50. 1EC52. 1EA50. dozens of components all in smart grey lacquered case 10 x 9 x 9". Made by Parmeko. Only 32/6 ea. BRAND NEW AND BOXED. M.C. METERS. 21' rd. II. (2 dial) 0-500/amps. 17/6. 0-1 m A. 21' rd. II. 0-2 dial 0-30 m A. 0-200 m A. 0-500 m A. 0-2amps. 13/6 ea. 0-150 v. A.C. (1 m A base with rect.) 28/6 ea.

SPECIAL VALVE OFFER. 6J6. 6AG5. EL32. EF39. 6CG6. 2X2. 37 6 doz. 6BRG. 7FT11. EF50. 12SC7M. 21/- doz.

EL109A RECEIVERS. less valves. 35/- All goods carriage paid U.K. mainland S.A.E. enquiries.

JOHN ANGLIN

385, Cleethorpe Road, GRIMSBY, Lincs.

TEL. 56315

COPPER WIRE

ENAMELLED, TINNED, LITZ, COTTON AND SILK COVERED. RESISTANCE WIRES. 1 oz., 2 oz. & 4 oz. REELS. All gauges available.

B.A. SCREWS, NUTS, WASHERS, soldering tags, eyelets and rivets. EBONITE AND BAKELITE PANELS. TUFNOL ROD, PAXOLIN TYPE COIL FORMERS AND TUBES. ALL DIAMETERS.

Latest Radio Publications. SEND STAMP FOR LISTS.

SPECIAL OFFER

G.E.C., B.T.H. & WESTINGHOUSE GERMANIUM CRYSTAL DIODES

1/- each. Postage 3d.

Diagrams and three Crystal Set Circuits Free with each diode.

A large purchase of these fully GUARANTEED diodes from the manufacturers enables us to make this attractive offer.

CRYSTAL SET

INCORPORATING THE SILICON CRYSTAL VALVE

Adjustable Iron Cored Coil. RECEPTION GUARANTEED

Polished wood cabinet. 15/-, post 1/6 A REAL CRYSTAL SET, NOT A TOY

POST RADIO SUPPLIES

33 Bourne Gardens, London, E.4

FIRST-CLASS RADIO COURSES . . .

GET A CERTIFICATE!

QUALIFY AT HOME—IN SPARE TIME

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure your professional qualification. Prepare for YOUR share in the post-war boom in Radio. Let us show you how!

FREE GUIDE

The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success-compelling qualifications as A.M.Brit.I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs, Exams., Gen. Cert. of Educ., London B.Sc. (Eng.), A.M.I.P.E., A.M.I.Mech.E., Draughtsmanship (all branches), etc., together with particulars of our remarkable Guarantee of SUCCESS OR NO FEE

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER 150,000 SUCCESSSES

NATIONAL INSTITUTE OF ENGINEERING

(Dept. 461), 148, HOLBORN, LONDON, E.C.1.

Programme Pointers



AN original and refreshing play was "The Time of the Serpent," by Bruce Stewart, based on the Queensland legend of Mrs. Fraser, a widow. She was shipwrecked on its inhospitable coast some hundred years ago. Stumbling across the jungle she encounters Bracefell, an escaping convict from Botany Bay. He avers that he knows of a way through for both of them. When love rears its inevitable head Mrs. Fraser, whilst stalling off its more serious possibilities, decides to make every use of its conveniences. When civilisation is reached poor Bracefell is scarcely given a thank you. An encounter with aborigines on the way adds stimulant to the exciting story.

Joan Hart played Mrs. Fraser with just the right amount of feline self-interest, and Jack McGowran was excellent as the convict with the heart of gold though his soul seemed destroyed.

"The Donkey's Crusade," too, was original and interesting. One of the Monday series of plays specially written for radio, it told of the quest for Prester John to elicit his help in freeing the Holy places from the infidel. I particularly liked Elizabeth Poston's little bits of music for percussion, psaltery, treble recorder, oboe, cello and flute, all beautifully played. There was a very long cast in it.

The Weather

The weather forecasts, under the revised system, are as wearisome and repetitious as ever. The "general situation" gives so much detail that the "regional" forecasts, which follow immediately after, are often word for word the same. Also, the pinpointing of localities only a few miles apart for meticulously calculated details of wind, rainfall, temperature, etc., is in such a small country and such a notoriously unstable "island" climate as ours is, a great mistake. In spite of a liberal supply of "probablys," "likelyps" and "howevers," it is bound to lead to unnecessary errors and disappointments. To assert that the sunshine in Berkshire will last a little longer than in neighbouring Buckinghamshire, or that the rainfall "may" be rather heavier in Norfolk than in Suffolk, is, to say the least, assuming occult powers, unwarranted and "probably" unwanted!

Plays

Plays again seem the best things of the month, so I will mention one or two more. Rasputin! Monks and priests have frequently played large and sometimes decisive rôles in revolutions. Few have more sinister reputations than he who both gave his name to this piece and figured so largely in the Russian upheaval of 1917 and the immediately preceding years. This account of him,

Our Critic, Maurice Reeve, Reviews Some Recent Programmes

by Wm. Gerhardt, takes the opposite view to that generally held, and paints him in quite heroic colours.

Like all his tribe, Rasputin was a devil with the ladies and had those of the Russian Royal family eating out of his hand. But Sir Donald Wolfitt, in the title rôle, made him sound repugnant and revolting as well as rapscaillionish and rascally. Richard Hurdnall was excellent as the weak and ineffectual Nicholas II, Laidman Browne, too, as Baron Fredericks, and Joan Mathieson as the Tsaritsa. One noted that our Ambassador was addressed as the "English" instead of the "British."

Shaw Novels

Bernard Shaw wrote five novels before setting out on his career as a dramatist. They were never looked upon by him as anything but pot boilers: first attempts at earning money by his pen. I don't think any of them were accepted for publication, and probably didn't deserve to be. But the "Third" performed a service by giving a radio adaptation of one of them, "Love Among the Artists." For it showed unmistakably the buds which flowered so profusely later on. It contained many touches of Shavian wit and barb though they were, as yet, more or less in embryo.

Joan Hart was delightful as Mary Southerland, the girl who is told real truths about going on the stage. And Clifford Evans was equally good as Owen Jack, who tells them. The admirable cast was completed by Kenneth Connor, Denis Goacher, Jack Shaw, Patience Collier, Betty Hardy and Roger Snowdon. Adaptation by Edward Marsh. Narrator, Desmond Gordon. Production, Christopher Sykes.


Music

The first performance of Michael Tippett's Second Symphony by the BBC Symphony Orchestra, under its old chief, Sir Adrian Boult—and commissioned by the BBC—was marked by the unusual event of a breakdown shortly after the opening, and a return to the commencement. It was due to a false entry by the violins. By bringing the proceedings to this summary conclusion, Sir Adrian gallantly shouldered the responsibility. The work, by the way, is enormously difficult as well as pleasing and attractive.

News from the Trade

NEW HI-FI RECORD REPRODUCER

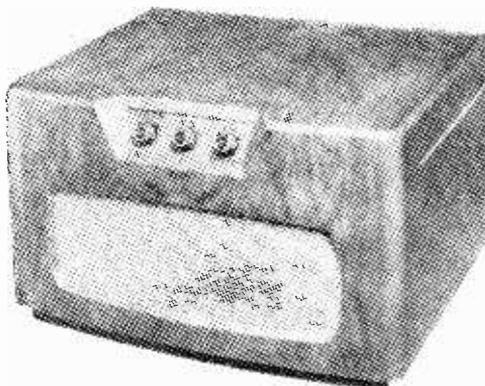THE "Cavalcade" Record Reproducer is the first instrument of its kind to be featured in the Dynatron range. This record reproducer provides reproduction from records which sets new standards for an instrument of its size. An outstanding specification includes the latest Garrard four-speed auto-changer or single record



The "Cavalcade" Record Reproducer.

player with plug-in high fidelity pick-up head, a five-stage, 8-w. push-pull amplifier with extension loudspeaker and radio/tape input sockets, separate bass and treble controls and a dual front facing high fidelity speaker system consisting of one 10in. elliptical and a 5in. high note, both with high flux magnets. The "Cavalcade" is designed for ease of operation, the fully illuminated control panel being situated at the front of the cabinet enabling volume, bass or treble adjustments to be made when it is closed for operation.

Superbly constructed, the acoustically balanced bow-fronted cabinet has, together with the attractive external control panel, a bronze finished speaker grille. The "Cavalcade" is available finished in a choice of light or medium walnut or mahogany high quality veneer.

Two optional extras are offered: a set of screw-in ebonised contemporary legs and an elegant bow-fronted table for the more traditional furnishings. The "Cavalcade" GR1 with auto-changer costs 49 gns. (including P.T.) and the "Cavalcade" GR2 with single player costs 46 gns.

E.M.I. PULSE GENERATOR

E. M. I. ELECTRONICS LTD. have developed this handy pulse generator for testing and demonstrating oscilloscopes and similar instruments. The pocket size instrument generates square and sawtooth waveforms simultaneously at amplitudes of 2.5, 5 or 7.5 v., and repetition rates of 100 c/s, 1 Kc/s or 50 Kc/s.

The top photograph shows an external view illustrating its compact size in comparison with a fountain pen and a three-penny piece. The lower

photograph is an interior view showing the compact transistorised circuit employed.

NEW MULLARD THYRATRON


A RECENT important advance in the design of larger types of rare-gas thyratrons is the use of the disc-seal construction technique usually associated with V.H.F. communications valves.

A new Xenon-filled triode thyatron, type XR1-6400A, using this technique has been introduced by Mullard Limited. It is rated at 6.4A average, 80A peak cathode current, with a maximum inverse anode voltage rating of 1500V. The control characteristic is negative over the working range. The valve is a plug-in replacement for the American type 6807.

As distinct from conventional designs, the grid structure of the XR1-6400A is at the centre of a large disc which is sealed into the glass envelope above the heater-cathode assembly and parallel with the base. The edge of the disc protrudes beyond the envelope, connection to the grid pin being made by a copper strip running externally down to the base. The anode—a dish-shaped electrode carrying the connecting cap—is sealed to the top of the envelope.

The advantages of this type of construction are several. In the first place, the grid is supported rigidly from the sides of the envelope and not from the foot as in conventional designs. This makes for greater mechanical strength and more consistent performance. Second, the entire

(Continued on page 237)

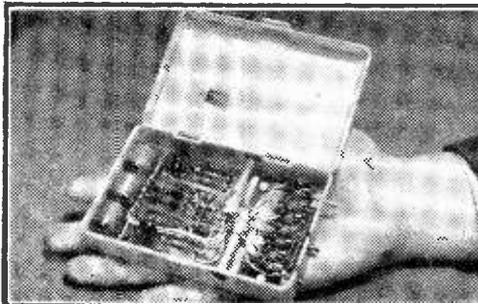

The E.M.I. Pulse Generator

C.R.T. ISOLATION TRANSFORMER

Type A. Low leakage windings. Ratio 1:1.25 giving a 25% boost on secondary. 2 v., 10/6; 4 v., 10/6; 6 v., 10/6; 10 v., 10/6; 13.3 v., 10/6. Ditto with main primaries. 12.6 each. Type B. Mains input 220-240 volts. Multi Output 2, 4, 6.3, 7.3, 10 and 13 volts. Input has two taps which increase output volts by 25% and 50% respectively. Low capacity suitable for most of the Ray Tubes, 21-. Ditto for 6.3 C.R. Tubes only. 17/6. Type C. Low capacity wound transformer for use with 2 volt Tubes with falling emission. Input 220-240 volts. Output 2-21-24-27-30 volts at 2 amps. With Tag Panel. 17/6 each. NOTE.—It is essential to use main primary types with T.V. receivers having series-connected heaters.

TRIMMERS, Ceramic. 30, 50, 70 pf., 9d.; 100 pf. 150 pf. 1/3; 250 pf. 1/6; 500 pf. 7/10 pf., 1/8. RESISTORS, Preferred values. 10 ohms to 10 meg., 1 w., 4d.; 1 w., 4d.; 1 w., 6d.; 1 w., 8d.; 2 w., 1/1-1/8. HIGH STABILITY. 1 w., 1/1-1/8. Preferred values 100 ohms to 10 meg. 1/10, 5/8, 9d. WIRE-WOUND RESISTORS. 5 watt (1) 25 ohms—10,000 ohms..... (1) 8 15 watt (2) 25 ohms—10,000 ohms..... (2) 15,000 ohms—50,000 ohms 5 w., 1/9; 10 w., 2/3.

12/6 PURETONE RECORDING TAPE


1,200 ft. on standard 7" metal reels. Spare Reels 7" plastic 4/3, 7" metal, 2/3. FERROVOCIE 1,200ft. Plastic Tapp 25/- on Plastic Reels.

O.P. TRANSFORMERS. Heavy Duty 50 mA., 4/6. Multitap, push-pull, 7/8. Miniature, 3/4, etc., 4/6. L.F. CHOKES. 100 H. 50 mA., 5/-; 19 H. 80 mA., 8/6; 19 H. 150 mA., 12/6. MAINS TRANS. 350-0-350, 80 mA., 6/2 w. tapped. 4 v. 4, 4 v. 5, tapped 1 v. 2 a., ditto 250-0-250, 22.6. Bargain 300-0-300 65 mA., 6 v. 4, 4 v. 2 a., 15/-. HEATER TRANS. Tapped prima. 200/250 v. 6.3 v. 11 amp., 7/6; tapped sec. 2, 4, 6, 8 v., 11 amp., 8/6; prim. 230 v. Sec. 6.3 v. 3 amp., 10/8.

ALADIN FORMERS and core, 4 in., 8d.; 5 in., 10/0. 0.3 in. FORMERS 5837/8 and Cans TV1/2. 2 in. sq. x 3 in. and 4 in. sq. x 1 in., 2/- ea., with cores. TYANA. 3-Mid. Sol. Soldering Iron. 200-250 v. or 230-250 v., 18/9. Solon Instrument Iron, 24/-. MAINS DROPPERS. 3 in. x 4 in. Adv. Siders. 6.3 amp. 750 ohms 4/3. 0.2 amp. 1,000 ohms, 4/3. LINECORD. 3 amp., 69 ohms per foot, 2 amp., 100 ohms per foot, 2 amp., 8d. per foot, 3-way, 7d. per foot. LOUDSPEAKER P.M. 3 OHM. 2 in. square, 17/6. 5 in. Goodman, 17/6. 7 in. x 4 in. Goodman, 21/- 3 in. square, Blac., 21/-. 1 in. Plesey, 19/6. 4 in. Goodman, 18/6. 10 in. R. & A., 30/-. TSW. Tweeter, LS473, 8/6. 250 Plesey, 30/0. 5 in. M.K. 4-5k. field, tapped O.P. transd. 24/6. 15 ohm Plesey 10 wt. 12 in. with Tweeter, 7/8. CRYSTAL DIODE G.C.M., 2/-, GEX34, 4/-.

HIGH RESISTANCE PHONES. 4,000 ohms, 16 p.p. MIKE TRANS. 30 V. 3.9 c/s., 100 H. Potol, 10/6. SWITCH CLEANER Fluid squirt, 4/3 tin. TWIN GANG TUNING CONDENSERS. 363 pf. miniature 1 in. x 1/2 in., 10/-, .0005 Standard with trimmers. 9/-; less trimmers, 8/-; midset, 7/6; SINGLE, 50 pf., 10/6; 100 pf., 150 pf., 8/6. Solid dielectric 100, 300 pf., 3/8. SPEAKER FRET. Expanded Metal Silver, 13 1/2 in. x 9 1/2 in., 2/- each. GOLD CLOTH. 17 in. x 25 in., 5/-; 25 in. x 35 in., 10/-. Tygan 10. 6 in. wide, 10/- ft.; 2 1/2 in. wide, 5/- ft.

Table with 4 columns: All Boxed Valves, New, and Guaranteed. Lists various valve types and their prices.

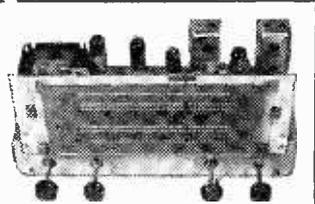

1958 RADIOGRAM CHASSIS

THREE WAVEBANDS. FIVE VALVES S.W. 16 m.—30 m. LATEST MULLARD M.W. 200 m.—550 m. ECH42, EF41, EB41, LW. 800 m.—2,000 m. EL41, EZ40 12-month guarantee. A.C. 200-250 v. 4-way switch; short-Medium-Long-Gram. A.V.C. and Negative feedback 4.2 watts. Chassis 13 1/2 x 5 1/2 x 2 1/2 in. Glass dial 10 x 4 1/2 in., horizontal or vertical available. 2 Pilot Lamps. Four Knobs, Walnut or Ivory. Aligned and calibrated. Chassis isolated from mains.

10 gns. Carr. & Ins. 4/6. TERMS: Deposit £5.50 and six monthly payments of £1. MATCHED SPEAKERS FOR ABOVE CHASSIS. 5 in., 17/6; 10 in., 25/-; 12 in., 30/-.

★ COLLARO ★ HIGH-FIDELITY AUTOCHANGER Mixer Model RC456 4-SPEEDS—10 RECORDS With Studio "O" pick-up BRAND NEW IN MAKER'S BOXES

OUR PRICE £9.15.0. post free TERMS: Deposit £5.50 and six monthly payments of £1. Suitable Player Cabinets, 49/6. Amplifier Player Cabinets, 63/-.

IMPORTANT NOTICE ALL THESE RECORD PLAYERS ARE FULLY GUARANTEED AND SPARES ARE AVAILABLE

GARRARD 4-SPEED SINGLE RECORD PLAYER 45P

AUDIO PERFECTION

Designed to play 16, 33, 45, 78 r.p.m. Records. 7 in., 10 in., 12 in. Lightweight Xtal pick-up. GC2 turnover head, two separate sapphire styli. OUR PRICE £8.0.0. each. Post Free. TERMS: Deposit £5 and 4 monthly payments of £1. Space required 14 in. x 12 in. Amplifier Player Cabinets, 45/-.

BUILD THIS REPRODUCER BARGAIN Special Single Player Kits. Famous maker's surplus stocks. 1-speed Collaro Junior Gram. pick-up unit, £4 12/6. Handsome portable case, 17 1/2 in. x 12 1/2 in., 12/6. £2 5/0. Rose and Cream Recline. Ready built 3-watt amplifier with valves and 7" elliptical loudspeaker, £3 12/6.

All available separately or if all purchased together. £9 15 0, "complete kit, post free. £3/5/0, extra with Garrard 4 sp.

ALUMINIUM CHASSIS. 18 s.w.g. un drilled. With 4 sides, riveted corners and lattice fixing holes. 2 1/2 in. sides, 7 x 4 in., 4/6; 9 x 7 in., 5/9; 11 x 7 in., 6/9; 13 x 9 in., 8/6; 14 x 11 in., 10/6; 15 x 14 in., 12/6; 18 x 16 x 3 in., 18/6.

TRANSISTORS. Audio, 10/-, R.F. 2/6 Me's, 21/-, Mullard GC71, 20/-.

HANDY VOLT METER. 2 1/2 in. Thin Range. 0-25 v. 0-250 v. D.C. with leads and leather case 12/6 complete.

CRYSTAL MIKE INSERT by Acos, precision engineered. Size only 1 1/4 in. x 3 1/4 in. Bargain Price 6/6. No transformer required.

TELETRON CRYSTAL SET KIT. Cabinet chassis components. Price 15/- with H.R. Phones, 30/-.

H.T.-GAIN BAND 3 PRE-AMP KIT. Case-constructed using valve ECC41. Price 27/6. With Power Pack, 49/6. Instructions only 1/-.

COSSOR COMPANION

SUPERBET MODEL 527-X FOR ALL-DRY BATTERY OPERATION S.W.1 13.6 to 43 metres, S.W.2 42.8 to 136 metres, Medium 187 to 575 metres. A line all-wave receiver giving world-wide reception on three wavebands. 6 in. speaker. The cabinet is maroon and beige with gold trimmings. Valves: DK92, DP96, DAF96, DL96. SIZE 9 1/2 in. x 6 1/2 in. x 4 1/2 in. Leadset S.A.F. (Battery 17/6 extra.) PRICE £6.15.0. Carr. & Ins. 4/6.

Volume Controls 80 ohm COAX Cable spaced. Semi-air spaced. These insulate. 1 in. dia. Stranded core. 9d. yd. Losses out 50%. Fringe Quality. 1/6 yd. Air Spaced.

COAX PLUGS ... 1/- DOUBLE SOCKET ... 1/3 SOCKETS ... 1/4 OUTLET BOXES ... 4/6 RACED TWIN FEEDER Yd. 9d. 300 ohms. DITTO SCREENED per yd. 1/- 80 ohms only. WIRE-WOUND POTS. 3 WATT. Pre-set Miut-T.V. Type. All values 25 ohms to 30 K., 3/- ca. 50 K. 4/-. (Carbon 50 K. to 2 m., 3/-) WIRE-WOUND 4 WATT. Pots 2 1/2 in. Spindle Values. 100 ohms to 50 K., 5/6; 100 K., 6/6. CONDENSERS. New Stock. 100 mfd. 7 kv. T.C.C. 5/6; Ditto, 20 kv., 9/6; 100 pf. to 500 pf. Micaf. 6d.; Tubular 500 v., 0.01 to .01 mfd., 9d.; .05, 1, 1.1, .25, 1.16; .5 350 v., 1/9; 1, 350 v., 9d.; .0325 500 v., 1/9; 1 mfd., 4, 2,000 volts, 2/8. CERAMIC COND. 500 v., 3 pf. to .01 mfd., 10d. SILVER MICA CONDENSERS. 10% 5 pf. to 500 pf., 1/-; 600 pf. to 3,000 pf., 1/3. Close tolerance (1 p.p.) 1.5 pf. to 47 pf., 1/6. Ditto 1/4, 50 pf. to 415 pf., 1/9; 1,000 pf. to 5,000 pf., 2/-.

I.F. TRANSFORMERS 7/6 pair. 465 Kc. Slog tuning Miniature Can. 2 1/2 in. x 1 in. x 1 in. High Q and good bandwidth. By Pye Radio. Data sheet supplied. Weatite M800 I.F. 465 Kc 12/6 per pair. Weatite 550 I.F. 465 Kc 12/6 per pair.

Table with 4 columns: NEW ELECTROLYTICS, FAMOUS MAKES, TUBULAR, TUBULAR, CAN TYPES. Lists various electrolytic capacitor types and prices.

SEMI-TERMINAL RECTIFIERS. E.H.T. TYPE FLY-BACK VOLTAGE. K325 2 kv., 5/-; K340 2 kv., 7/-; K345, 3 kv., 7/6; K350 4 kv., 8/6; K360 4 kv., 10/6. 50 kv. 50 kv. voltage, 30% of above. MAINS TYPE CONTACT COOLED 250 v., 50 mA., 8/6; 250 v., 85 mA., 9/6. Selenium 300 v., 85 mA., 7/6. COILS Weatite "P" type, 3/- each. Osamor Midget "Q" type nil. dust core, from 4/-, all ranges. TELETRON. L & Mod. T.V. with reaction, 3/6. FERRITE ROD AERIALS. M.W. 8/9; M.L., 12/6. T.R.F. COLLS A/HF 7/- pair. H.R. CHOKES, 2/6. FERRITE ROD 7 in. x 3 1/2 in. dia., 2/6.

JASON F.M. TUNER COIL SET. 28/-, H.F. coil, aerial coil, Oscillator coil, two I.F. transformers 10.7 Mc/s. Detector transformer and heater choke. Circuit book using four 6AM6, 2/-, J.B. chassis and Dial, 15/6. Complete Jason F.M. Kit, £5.15.0. With Jason superior calibrated dial, £6.15.0.

FULL WAVE BRIDGE SELENIUM RECTIFIERS. 6 v. 12 v. 11 amp. 9/2; 2 a., 11.2; 4 a., 8/2. CHARGER TRANSFORMERS. Tapped input 200/250 v. for charging at 2, 6 or 12 v., 11 amp., 15/6. 2 amp., 17/6; 4 amp., 22/6. Circuit included. VALVE and T.V. TUBE equivalent books, 5/-. TOGGLE SWITCHES. S.P.F. D.P. 3/6, D.P.F. D.T. 4/-. WAVELENGTH SWITCHES 5 p. 4-way 2 water long spindle ... 8/6 2 p. 2-way 3 p. 2-way short spindle ... 2/6 2 p. 6-way 4 p. 2-way 4 p. 3-way long spindle 3/6 3 p. 4-way, 1 p. 12-way long spindle ... 3/6 TELETRON HOLDERS. Pa. Int. Oct. 6d. P.F.50, E.A.9, 6d. B12A, CRT. 1B3. Eng. and Amer. 4, 5, 6, 7, and 9 pin, 1/-, MOULDED MAZDA and Int. Oct. 6d. B7C, 18A, B8C, B9A, 9d. B7E with can, 1/6. VCR97, 2/6, B95 with can, 2/6. CERAMIC EF90, B7C with can, 1/6. B7C with can, 1/9. BLACK CRACKLE PAINT, air drying, 3/- tin.

NEW AND ENLARGED SHOWROOMS NOW OPEN OUR WRITTEN GUARANTEE WITH EVERY PURCHASE. Please address all Mail Orders correctly as below RADIO COMPONENT SPECIALISTS 337 WHITEHORSE RD., WEST CROYDON OPEN ALL DAY—(Wed. 1 p.m.) Catalogue 6d. Te. THO 1665. Boxes 133 or 68 pass door. 48-hour postal service, P. & P. 1/-, over £2 post free. (Export Extra.) C.O.D. Service 1/6

THE SUPEREX "55"

BATTERY PORTABLE

BUILDING COST **£7.15.0**
Plus 5/- P.P.

- 4-VALVE SUPERHET.
- LONG MEDIUM WAVES.
- 7in. x 4in. SPEAKER.
- B7G 1.4 v. VALVES.
- SIMPLE CONSTRUCTION.

SEND 1/6 FOR BOOKLET.

CHASSIS ASSEMBLY

CONTAINING:
DRILLED CHASSIS AND
BACKPLATE. SIZE
12 x 7 x 9in., GLASS DIAL
L.M.S.G., DRIVE DRUM
AND SPINDLE, KNOBS.
PRICE 22/6 PLUS 2/6 P.P.

ALWAYS IN STOCK

RESISTORS, CONDENSERS, TRANSFORMERS, VALVES, AMPLIFIERS, AUTOCHANGERS, RADIO CHASSIS, SPEAKERS, CABINETS, PICK-UPS, SPEAKER FABRIC, RECORDING TAPE, MICROPHONES, ETC.

Shop Open : 9 a.m.—6 p.m. Early Closing : Thursday, 1 p.m.

SUPERIOR RADIO SUPPLIES LTD.

37, HILLSIDE, STONEBRIDGE N.W.10
PHONE : ELGAR 3644

VALVES • SAME DAY SERVICE

All Guaranteed New and Boxed

1.4v. midget, 1R5, 1S5, 1T4, 3S4, 3Q4, 3V1, DA901, DF91, DK91, DL92, DK92, DL91, ANY 4 for 27.6.

1A7GT	13/6	6L4GT	11/6	D77	6/-	EP50	22/6		
1C5GT	15/6	6V6G	7/-	DAC32	11/-	SYL 66	PL81	17/6	
1H5GT	11/-	6V6GT	7/6	DAF90	8/6	EP80	8/-	PL82	9/6
1N5GT	11/-	6X4	7/-	DF33	11/-	EP85	7/6	PL83	10/6
1R5	8/6	6X5GT	6/9	DF96	8/6	EP86	13/-	PL80	8/6
1S5	7/6	7B7	8/-	DH70	7/6	EP89	9/6	PL84	8/6
1T4	7/3	7C5	8/-	DH71	8/-	EP91	6/-	PY82	8/-
3A5	10/6	7G6	8/-	DK32	13/6	EP92	5/6	PY83	8/6
3Q4	8/-	7HT	8/-	DK92	8/6	EL33	16/9	PZ30	18/-
3Q5GT	9/6	7S7	9/-	DK96	9/6	EL38	22/6	R19	13/6
3A4	7/6	7Y4	8/-	DL33	9/6	EL41	9/9	SP41	3/6
3V1	8/6	12AHR	8/-	DL38	15/6	EL42	11/6	SP61	3/6
5U4G	8/-	12AT6	8/-	DL96	8/6	EL84	9/9	TH11	15/6
5V4G	11/9	12AT7	8/-	EABC80	7/9	EM80	10/-	U25	14/6
5Y3GT	7/6	12AU7	8/-	EAF32	10/6	EV51	11/6	U50	17/6
5Z4G	9/6	12AX7	8/-	EB91	6/6	EL41	15/-	U76	7/6
6AL5	6/-	12BA6	8/-	EB93	7/6	EZ40	7/9	U78	7/6
6AM5	5/-	12J6GT	10/6	PBC41	9/6	EZ41	9/6	UABC80	9/6
6AM6	6/-	12K7GT	7/6	EBF80	8/9	EZ80	7/6	UAF42	10/6
6AQ5	7/6	12K8GT	14/-	EBF89	9/-	EZ81	9/6	UBC41	8/6
6AT5	8/-	12Q7GT	7/6	EC81	8/-	FW4.500	9/-	U85	9/-
6BA6	7/6	12Z3	7/6	EC82	8/-	G232	11/6	UCC85	9/-
6BE6	7/6	14S7	12/-	EC83	8/-	KT33C	8/6	UCH42	9/-
6BH6	9/-	19AQ5	9/6	EC84	10/6	KT33C	8/6	UCH81	9/6
6BJ6	7/-	25A0G	13/6	EC85	9/6	KT63	6/6	UCL33	17/6
6BR7	8/6	25L6GT	9/6	ECF80	10/6	M14	6/6	UF4	8/-
6BW6	7/6	22Z4	9/6	ECF81	11/-	MU14	8/-	UF32	15/-
6BW7	7/6	35L6GT	9/6	ECH21	16/9	N18	8/-	UF80	10/6
6CD6G	27/6	35Z3	10/6	ECH35	10/-	PCB4	9/-	UL41	9/6
6F8C	6/6	35Z4CT	7/6	ECH42	9/6	PCF80	10/-	UY21	18/6
6F12	6/-	35Z5GT	9/6	ECH81	8/-	PCF82	10/9	UY41	7/6
6K7G	4/6	43	13/6	ECL80	10/-	PCL82	10/-	UY85	7/6
6K7GT	6/-	50CD6G	18/6	EF37A	8/6	PCL83	12/-	VP4B	14/6
6K8C	7/9	50L6GT	8/6	EF30	6/-	PENA4	14/6	VP41	7/-
6L18	12/6	AZ31	11/6	EF41	9/6	PEN36C	14/6	VP1321	21/-
6Q7GT	9/6	B38	18/6	EF42	11/6	PEN46	6/6	W76	7/6
6SLGT	7/6	CL33	16/9	EF36	15/-	W77	15/-	W78	5/6
6SN7GT	7/6					Z77			6/-

Postage 6d. per valve extra. Z77 6d. extra.

Any Parcel Insured Against Damage In Transit 6d. extra.

READERS' SERVICE

24, COLBERG PLACE, STAMFORD HILL,
LONDON, N.16 STA. 4587

BENSON'S BETTER BARGAINS

R1155B. Good condition, fully valued; tested with "N" drive; handbook supplied. £7 10/- (incl. 10/-). **TEST SET 127U** (1058). U.S.A. Micro-wave Frequency Meters: 375-725 mc s.; 3 valves, new, less bats. £7 10/- - **CR100**—brand new, power transformers, 30 - **POWER UNIT**, 200; the unit 200 250 v. Outputs: 250 v. 7.5 mA.; 21 v. 1 A. D.C. and 6.3 v. 3 A. A.C. New, sealed, with plugs 45/- (p.p. 3/6). **COMMAND RECEIVERS**, brand new, 6 valves, med. wave (0.52-1.5 mc s.). 97 6; used 82 8 (post 3/6). Conversion data & cims. to (CAR RAD10). 1 6. **1 P. STRIP 373**, new, with valves, 42 6. **RELAYS**, coaxial, "P" 12" 12 v. 10 -; set 3 plugs, 1 6. **RX78**, 2.4 12 mc s. with 5 valves, 100 kc/s. Xtal. Good cond., 35 - (p.p. 3/6) **BC1053**, 150 280 mc s. Receiver, valves 2 6/57, 1118stt, new, 15 - (p. 3/6). **VIBRAPAKS 6 v.** D.C. to 250 v., 20 mA., standard, cased, 22 8; Mallory 12 v. to 120 v., 40 mA., 5/6ch., 10 6 (post 2/6). **VIBRATORS**, Mallory G620" 12 v., 4-pin, 7 6. **BRAND NEW R.F. 2B, 25** - (post 5/-) **RF27**, good cond., 20 - **DYNAMOPHORS** (post 5/6): 12 v. to 250 v., 65 mA. and 6.3 v., 2.5 A., 11 8; 6 v. to 250 v., 80 mA., 12 6. 11 v. to 200 v., 50 mA. and 13 v. smoothed, filtered, cased, 15 -. **METAL RECTIFIERS**: 12 v. 1 A. bridge, 2 6; 250 v., 80 mA., 1W, 5/-; 240 v., 100 mA., 4/-; 250 v., 80 mA., 6/-; 12 v. 4 A. Bridge, 17 6; 210 v., 20 mA., 3 6; 1,000 v., 30 mA., 7 6. **R1155 S.M. DRIVES "N"** type, new 10 6. **TEST METERS**, New, 4 - 2 1/2 in. Read 1.5 and 5 v., 60 mA. and 5K Ω , 12 8. **TS347** contains 10 mA., 5 in. meter, res. etc., 9/8. **METERS**, contain 2 separate micro-amp movements and 2 neon, new, 7 6. Cross-over needle (L R), 100 μ A each section; good condition, 8/6 (post 2/-). **MOTORS**, enclosed, 3 1/2 in., 3 1/2 in. dia., D.E. 1/2 in. spindle, 200 250 v. (A.C. D.C.) Intermittent, 12 8 (post 3/-). **R.F. UNIT** with 2EF91, 3 EP92 motor (tuned, new, 30/- (p.p. 3/6). **METAL BOX**, 20 30 mc's. (1.E. 1 mc's.). Box with 6.3 v., 3 A. CT fil. trans., 4 panel fuses and 2 toggle, 10 6 (p.p. 3/6). **LST & ENQUIRIES**: S.A.E. please! Terms, C.W.O. Postage extra. Immediate despatch.

Call & post: W. A. BENSON (P.P.)
136 Rathbone Road, Liverpool, 15. *NEW*
Call & SUPERADIO (Whitechapel) LTD.
118 Whitechapel, Liverpool, 2. *ROY 1130*

TV SPARES

41, CADD LANE, LEEDS 1.

Tel. 28559.

We specialise in exact replacement components, e.g.

Mains Droppers for Ultra twin R6, 1,690 Ω + 1,450 Ω , 5/3; R7, 175 Ω + 340 Ω ; 410 Ω , 5/3. For Philips: R1, 150 Ω + 250 Ω + 170 Ω ; 100 Ω , 6/5. R3, 430 Ω ; 200 Ω ; 180 Ω , 4/10, etc.

Line Output Transformers: LOP4 fits Pye V4, VT4, V7, VT7, 55/2. LOP6 fits FV2, FV4, 50/9.

TSL HI-STAB 1/2 watt Resistors. 10 Ω to 10M Ω , 5d. each. 4/- per 12 mixed.

Crystal Diodes, 1/3. Red Spot Transistors, 7/6.

Service Sheets, 6 for 5/-, 12 for 9/-, P. & P. free. These are all mixed. No enquiries for sheets, they are sold just as they come.

New type AVO Multimeter, £9/10/-, P. & P. free by registered post.

Please enclose postage. No lists available yet.

W. B. SUPPLIES

Mail Order Dept.
22, Swan St., Manchester, 4
Terms Cash with order.

EX. W.D. MULTIRANGE TEST METERS

17/6

+ 1/6

postage.



17/6

+ 1/6

postage.

0-500, 0-5,000 Ω
0-1.5 volts, 0-300 volts.
0-60 mA.

Complete with instructions.

Book of 29 TV Circuits with service data 10/-, post paid. Comprising the following:
ALBA T301, AMBASSADOR TV7, BUSH TV22A, TV24A, FERRANTI 14T3, 17T3, 17K3, 14T3F, 17T3F, 17K3F, G.E.C. BT5146C, BT4543C, K8, HF60, MASTERADIO T917, MURPHY V210, V210C, PHILCO BT1753, BT1753C, PHILIPS 1101U, PILOT TV76, CV76, CV77, P.YE FV4C, FV4CDL, RAYMOND 14in., ULTRA VA72, VIDOR CN4216, WHITE-IBBOTSON 2015 Projection.

RED SPOT TRANSISTORS, SUPERIOR QUALITY, imported from Germany at SPECIAL LOW PRICE of 7/6 each, post paid. DON'T MISS THESE!

"AT A GLANCE" RESISTOR COLOUR CODE CHART, simplest ever invented, 1/9, post paid.

structure is extremely simple and therefore inherently more reliable.

Third, the grid forms an effective shield across the anode-cathode discharge gap and prevents spurious long-path voltage breakdown between cathode and anode, giving, consequently a greater margin of safety on voltage limits.

Fourth, since the entire upper surface of the anode and part of the grid are exposed to the air, cooling is greatly improved, grid emission current is reduced and so is the possibility of arc-back from the anode. Furthermore, the need for extra heat shields between anode and grid and grid and cathode is eliminated, thus further simplifying the structure of the valve.—Mullard Ltd., Mullard House, Torrington Place, London, W.C.1.

NEW ELECTRONIC FAULT-FINDER

DESIGNED to provide a quick, easy and effective method of overhauling transmission equipment not in service, a new portable percussion test amplifier has been recently introduced by the Automatic Telephone & Electric Company Limited.

Known as the Type M7A, it is a rectifier type test set designed primarily for testing audio or multi-channel carrier equipment. Advantages of this type of fault-detector over earlier instruments, are improved sensitivity and the reduction of tone level reaching the loudspeaker, rendering the detector easier to use for long periods.

The instrument operates on the following principle: when, in a circuit under test, a bad connection is disturbed, transient modulations occur in the current of the test tone. These transients are rectified, filtered and passed as an audio frequency into an L.F. amplifier, and are heard as clicks and crackles in the loudspeaker.

The manufacturers claim that even low-level disturbances in the circuit under test may be readily detected.—Automatic Telephone & Electric Co. Ltd., Strowger House, 8, Arundel Street, London, W.C.2.

COSSOR "DO-IT-YOURSELF" KIT

COSSOR RADIO & TELEVISION LIMITED have again entered the radio "do-it-yourself" market which they pioneered in 1927 with the famous "Melody Maker" radio kits. The new kit, now available, is for a high quality, 3 watt, twin speaker, audio amplifier.

The kit contains all the necessary components, including a printed circuit board with most of the components soldered into position, and 10in. elliptical and 4½in. tweeter loudspeakers. A sectional template is provided to facilitate mounting the amplifier and loudspeakers into an existing cabinet. An illustrated construction manual with circuit diagram and all necessary data is supplied with each kit, and model 562K provides a compact and versatile printed circuit amplifier suitable for operation from radio, microphone, gramophone and other audio sources. Retail price is £9 15s. inc. tax.

The 562K amplifier is the first of a series of "Do-it-Yourself" kits which will be marketed by Cossor Radio and Television Limited. Additions will be announced shortly. It is confidently



expected that these kits will prove as popular among home instructor enthusiasts as the kit oscilloscopes and valve voltmeter marketed by Cossor Instruments Limited.—Cossor Radio & Television Ltd., Cossor House, Highbury Grove, London, N.5.

"SIEMAX" BATTERIES PRICE REDUCTION

SIEMENS EDISON SWAN LTD., have pleasure in announcing that, consequent upon improved production facilities, etc., retail prices for most of the popular "Siemax" radio batteries are being reduced as follows:—

Type	Old price		New price	
	s.	d.	s.	d.
S.101	12	6	11	6
S.102	10	0	9	0
S.103	19	6	18	6
S.104	8	6	8	0
S.107	14	9	14	0
S.114	8	3	8	0
S.117	14	9	14	0
S.126	10	0	9	0
S.127	21	0	20	0
S.129	17	6	16	6
S.136	17	6	16	9
S.138	17	6	16	6
1340	11	0	10	6

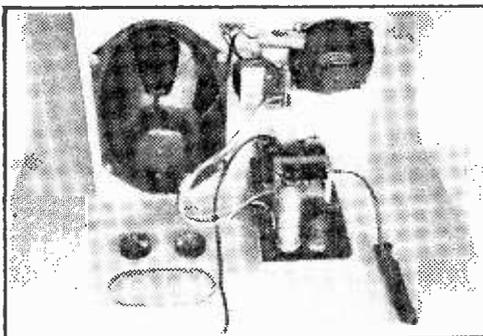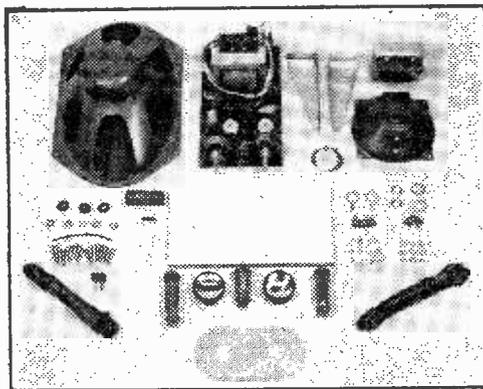The reduced prices were effective to the trade on and after 20th February, and to the public from 10th March.



The parts and an assembled amplifier by Cossor. This is a "Do-it-yourself" kit.

NEW! Taylor

POCKET SIZE UNIVERSAL METER MODEL 122A



A small 21-range instrument ideal for the enthusiastic amateur.
Sensitivity is 5,000 o.p.v. A.C. and D.C. Accuracy: 3% D.C. 4% A.C.
A high sensitivity moving coil centre pole type meter with 2 1/2" scale is fitted.

Size: 4 1/2" x 3 1/2" x 1 1/2".
Weight: 14 oz.

RANGES

Volts D.C.: 0-3-15-30-150-300-1,500.
Volts A.C.: 0-15-30-150-300-1,500.
Milliamperes D.C.: 0-15-30-150-300-1,500.
Amperes D.C.: 0-15. Resistance: 10 ohms-1 megohm.
Automatic overload protection fitted to meter movement.

PRICE: **£9.5.0** PROMPT DELIVERY

Or on Credit Sale Terms: 1st payment of £13.2 and 8 further monthly payments of £13.2.
ALL TAYLOR Instruments available on HIRE PURCHASE and 7 DAYS' APPROVAL.
Write for full details and Catalogue.

TAYLOR ELECTRICAL INSTRUMENTS LTD.

Montrose Avenue, Slough, Bucks


Telephone: Slough 21381—Cables: Taylins, Slough

TRANSISTORWISE

"RECO" ALL-WAVE 1 TRANSISTOR KIT


A low cost beginner's radio kit includes all parts, transistor, diode, and super sensitive. Phone for private listening, neat plastic case and 1.5V battery for months of dependable listening. Only 25/-.

Parts Price List, Wiring Diagram, 1/-.

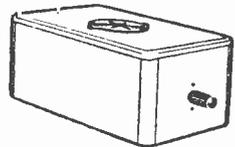

"RECO" TRANSISTOR 2 PORTABLE

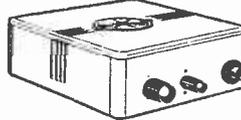
Receives home and Continental stations. Ferrite rod aerial. Attractive plastic case, 4 1/2" x 4 1/2" x 1 1/2" balanced armature output unit and all parts. 49/6 inc. 3 volt battery. Parts Price List, Wiring Diagram, etc., 1/3.



"RECO" PORTABLE TRANSISTOR 3

Similar specification to the "Reco" 2, but uses high gain frame aerial mounted on metal chassis. Has variable gain control. 65/- buys all parts, case and battery.

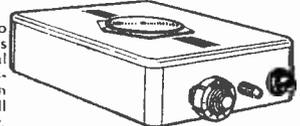Parts Price List, Wiring Diagram, etc., 1/3.



"RECO" MIDDY 3 PORTABLE

3 selected transistors. Specially designed high "Q" ferrite rod aerial. Unique tuning system covering medium waves and short-wave band. A super sensitive receiver in a vest pocket size case measuring 4 1/2" x 3 1/2" x 1 1/2". 55/- Personal pocket phone included free. Complete data and priced parts list, 1/3.

RADIO EXCHANGE CO.

(Dept. P.W.), 27A, HARPER STREET, BEDFORD

EVERYTHING in HI-FI

You can buy all your Hi-Fi and tape recording equipment by one of several easy methods of payment. Illustrated is a small selection of our vast stock of first-grade equipment. Many special offers to callers. If you cannot call, our Mail Order Department will give you efficient service.



QUAD II AMPLIFIER



QUAD II CONTROL UNIT



WB HF1012 SPEAKER

LONDON'S Hi-Fi SPECIALISTS



RADIO CENTRE Ltd.
33, Tottenham Court Rd., W.1
Tel.: MUSEum 6667

HOLE PUNCHES

ONE MINUTE TYPE

in. diameter	ca.
1/2	4.3
3/4	4.9
1	5.6

Postage and Packing 1/-

SCREW-UP TYPE


in. diameter	ca.
1/2	6.6
3/4	7-
1	7.6
1.1 16in.	8-
1 1/2	8.9
1 1/4	10-
1 3/4	11.3
1 1/2	12.6
1 3/4	13.9
1 1/2	14.6
1 3/4	15.3
2	16-
2.3 32in.	18-

Postage and Packing, 1/9
Special Chassis made to order.
Standard Chassis ex stock.

Oliver & Randall LIMITED

40 Perry Hill, London S.E.6

THE BARGAIN OF A LIFETIME

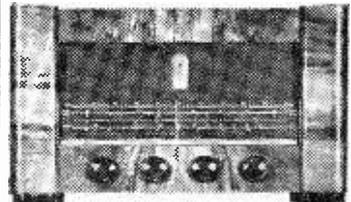

BEREC (EVER READY) SKYSCRAPER BATTERY RADIO

7 Mullard Valves
Latest Low Consumption Types

4 Wavebands	Walnut Cabinet
10 to 20.8 m.	44.5 to 100 m.
20.7 to 45 m.	190 to 545 m.
Ext. LS Sockets.	Gram PU Sockets.
Tuning Indicator	20" x 10" x 12"

BRAND NEW IN SEALED CARTONS BELOW COST, 9 gns.

While they last.

CASH ONLY. CARRIAGE PAID

Cancelled Export Order.

A MAGNIFICENT FACTORY BUILT SUPER SENSITIVE ALL DRY BATTERY RECEIVER

H.P. RADIO SERVICES LTD.,

51, County Road, Walton, Liverpool, 4.

Tel.: AINtree 1445. TELEX 62-244

Established 1935.

Wanted!

QUALIFIED MEN AND WOMEN

Industry and Commerce offer their best posts to those with the qualifications—appointments that will bring personal satisfaction, good money, status and security. As part of a modern industrial organisation, we have skilled knowledge of what is required and the best means of training personnel for present day and future requirements. We specialise also in teaching for hobbies, new interests or part-time occupations in any of the subjects listed here. Write to us to-day for further information. There is no obligation of any kind.

PERSONAL & INDIVIDUAL TRAINING IN —

- | | | | |
|---------------------------------------|----------------------------|-------------------------------|--------------------------------|
| Accountancy | Draughtsmanship | Mathematics | Sales Management |
| Advertising | Economics | M.C.A. Licences | Sanitary Engineering |
| Aeronautical Eng. | Electrical Eng. | Mechanical Eng. | Salesmanship |
| A.R.B. Licences | Electrical Instal. | Metallurgy | Secretaryship |
| Art (Fashion, Illustrating, Humorous) | Electronics | Motor Eng. | Servo Mechanisms |
| Automobile Eng. | Electronic Draughtsmanship | Painting & Decorating | Shorthand & Typing |
| Banking | Eng. Drawing | P.M.G. Certs. | Short Story Writing |
| Book-keeping | Export | Police Production Eng. | Short Wave Radio |
| Business Management | Gen. Cert. of Education | Production Eng. Planning | Sound Recording |
| Carpentry | Heat & Vent. Eng. | Radio Amateur (C & G) Licence | Television Communications |
| Chemistry | 'Hi-Fi' Equipment | Radio Engineering | Television Time & Motion Study |
| City & Guilds Exams | High Speed | Radio & Television Servicing | Tracing |
| Civil Service | Oil Engines | Refrigeration | Transistors |
| Commercial Subjects | Industrial Admin. | | Welding |
| Commercial Art | Jig & Tool Design | | Workshop Practice |
| Computers | Journalism | | Works Management etc., etc. |
| Customs Officer | Languages | | |
| | Management | | |
| | Maintenance Eng. | | |

Also courses for GENERAL CERTIFICATE OF EDUCATION, A.M.I.H.&V.E., A.M.S.E., A.M.Brit.I.R.E., A.M.I.Mech.E., A.M.I.E.D., A.M.I.M.I., A.F.R.Ae.S., A.M.I.P.E., A.M.I.I.A., A.C.C.A., A.C.I.S., A.C.C.S., A.C.W.A., City & Guilds Exams., R.T.E.B. Servicing Certificates, R.S.A. Certs., etc., etc. Moderate fees.



The E.M.I. Factories at Hayes, England.
 The only Home Study College operated by a world-wide manufacturing organisation

EMI
INSTITUTES

NEW! Courses with PRACTICAL EQUIPMENT

in RADIO · TELEVISION · MECHANICS
 CHEMISTRY · ELECTRICITY
 DRAUGHTSMANSHIP · PHOTOGRAPHY etc., etc.



POST THIS TODAY

To :- E.M.I. INSTITUTES, Dept. 32K, London, W.4.
 NAME _____ AGE _____
 (if under 21)
 ADDRESS _____

I am interested in the following subject(s) wish/without equipment

MAY 58 (We shall not worry you with personal visits)



BLOCK
 CAPS
 PLEASE

IC22

- part of 'His Master's Voice' Columbia, etc., etc.

RECEIVERS & COMPONENTS

TELEVISIONS, 12in. 5 channel. £14; 14in., £18; 17in., £27; Faulty Sets from £2. WILKINSON'S, 146, Goldhawk Rd., W.12. (SHE 4379.) Callers only.

MIDDLESBROUGH. Largest stocks on N-East coast. Radio, T.V. components. FM Kits. Gram. Cabinets. Tape Decks. Leak Amplifiers. Valves, etc. Callers only. PALMERS, 100, Newport Road. (Phone: 3096.)

TELEVISIONS NEEDING ATTENTION. 9in.-10in. models. £4/10/- each. 12in. models. £8/6/- each. 15in. models and Philips Projection models £11/10/- each; immediate despatch. carriage paid. BARKERS, 325, Brockley Road, S.E.4. (TID 6752.)

VALVES from 1/6. Radio, T.V. Components; low prices. Lists 3d. J. PALMER, 22, Neasden Lane, N.W.10.

T.V. TUBES, 30/-, with cathode heater shorts; 15/- with burn; carr. extra; ideal for testing; good picture. Please enquire for types and sizes required. DUKE & CO., 623, Romford Road, Manor Park, E.12. (BLE 6001.)

PHILIPS Mains Transformers, 200/250, 250-0-250, 80ma. 6.3V. 3A. 8/6, p. & p. 2/6. Philips Smoothing Chokes, 3/6, p. & p. 2/-. Philips Output Transformers, 3/6, p. & p. 2/-. ELECTROSURE, 118, Fore Street, Exeter. 56687.

F.M. AERIAL offers from manufacturers. Indoor Dipole, with mast and base. 12/6; "H" ditto, 22/6, post free. Send 1/- P.O. for our full T.V. Aerial Lists with illustrated parts catalogue and aerial data. Build your own aerials from our fully machined parts, and save money. SKYLINE WORKS, Barnsall Road, Coventry.

TELEVISIONS, 9in. models, £7/10/-; 12in. models, £13/10/-; 12in., 5-channel models, £18/10/- each; all working, carriage paid. Send for list. TOMLINS, 127, Brockley Rise, Forest Hill, S.E.23. (FOR 5497.)

HI-FI TEST TAPE. Check your recorder with the B.R. Test Tape Frequency response check, 50-10,000 cycles; transit and quality test, 600ft. reel recorded at 7 1/2 or 3 1/2 in. per sec.; 20/-, post free. BISPHAM RADIO LTD., 153, Red Bank Rd., Blackpool.

RADIO & TELEVISION COMPONENTS

of guaranteed performance and long life. We have a most extensive range to offer: Example: **ELLIPTICAL P.M. SPEAKER** 7in. x 4 1/2in. 6,000 line gauss flux density. Base resonance 100/10. 3-5 ohms, 17/6 each, post 2/-. **ACOS CRYSTAL MICROPHONE** 1 1/2in. DIAM. CONE. TYPE MC 6CX (1" NHOUSED). Ideal for tape recorders, amplifiers, etc. 10/6 each, post 1/-. Size 2 1/2in. x 2 1/2in. x 1 1/2in. **WESTINGHOUSE RECTIFIERS**. Mains input 240v. Output D.C. volts nominal 270 output current 300 m.A. 19/6 each, post 1/-. **V.H.F. TWIN GANG TUNING CONDENSERS**, 0 to 975 pF. Ball bearing drive. Size 2 1/2in. x 1 1/2in. x 1 1/2in. 5/6 each, post 1/6. The quality of our components cannot be exceeded. Send today 3d. stamp for complete lists of bargains.

J. E. SEXTON LTD.

162, GRAY'S INN RD., LONDON, W.C.1.
Tel.: TERminus 0228-9.

RATES: 5/6 per line or part thereof, average five words to line, minimum 2 lines. Box No. 1 - extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless," Tower House, Southampton St., Strand, London, W.C.2.

GUARANTEED TELEVISION, 12in. 5-Channel models, first-class picture, £26 each, carriage paid. T H E GRAMOPHONE SHOP, 19-21, Brockley Rise, London, S.E.23.

VALVES.—1L4 (1T4) at 2/6 each, or £11 per 100; carriage paid; 8in. Extension Speakers in polished wooden cabinets (used), but mechanically perfect, 15/6 each, plus 3/- carriage; 2-watt Amplifiers, complete with 8in. speaker in polished cabinet, ideal for use with record players, £4/19/6, plus 3/6 carriage; c.w.o. NORMAN H FIELD (ELECTRONICS), 20, Snow Hill, Birmingham, 4.

POWER IN PACKETS.—Hts. of all kinds, stamp for battery booklet. For those waiting for the 230v. Navy Oscilloscope as previously advertised, new lot just arrived and delivery your address imminent. Others requiring same, send for full mod. booklet, 6d. See Dec-Jan. advt. Price £5/15/- del. No more available after this lot definitely. A new buy. Files, money back guarantee, any doz. of your choosing, from 14in. to 8in. inc. Bastards, mill, breadnaughts, fine, etc., etc. 16/6 doz. delivered 3d. for list. DIGGINS, 129-133, Radnor St., Hulme, Manchester, 15 (MOS 2419.)

UNREPEATABLE OFFER.—12in., 5 Channel T.V. £15; 14in., £22, good working order. C. EDWARDS, 1070, Harrow Rd., London, N.W.10. (Phone: LADbroke 1734.)

T.V. FILTER of unique design, easily fitted. Stops wire netting or patterning on your picture. Only 10/6. LAVLO ELECTRICS, 8, Albert Terrace, Whitehaven, Cumb.

TRANSISTOR Hi Fi audio OP and interstage Transformers from 3/-; Television Booster Transformers, any voltage, 6/-; Hi Fi interleaved OP Transformer and matching KT33C, 5 watt, 12/6 pair; ditto with 6V6 valve 3/5 ohms, 12/6; Vibratorpack, 24-230v., 100 m/a, £1; 12 volt, 12 watt Amplifier, Mike, 500yd. Speaker, £6 complete. Lists. TRANSISTOR TECHNIQUES, 175, East Dulwich Grove, S.E.22. (CIP 1275.)

R.E.P. One valve chassis, 2/8. Coll. 4-3 Dial Plates, 2/3. 0003 Mid. tuning, 3/0. 0003, 3/10. Instructions, 9d. Chassis 3D Transistor, 3/-. Instructions, 9d. Seven Transistor superhet portable Instructions 1/6.

TRANSISTORS, Audio, 10/- R.F. 21/- **THREE** Waveband prealigned superhet coil pack, 26/-, plus P.T. 10/- **T.R.F.** coil set, 8/- Superhet coil, pair 3/- **ALL** coils complete with circuits, High Resistance earphones, 12/- **Resistors**, 6d. **TELETRON** pocket 3 TRANSISTOR "COMPANION". Complete Kit, 88/6, p.p. 1/6.

ELECTRADIO

18, Broadlands Avenue,
Keynsham, Som.

ANNAKIN

RECR. UNIT 1143A.—Has 1 EL32, 4 EF50 2 EF39, 1 EBC33, 1 EA50. Lots of Res., Cond. L.F.s, etc. O.K. for 2 metre conversion From new apparatus. 25/- ea., 3/6 post **MOVING COIL METERS**.—1 m.a. P.S. 10, 2/-, Calibrated -3 to +30. New, boxed, £1, post 1/3.

1143A EQUIPMENT, less valves and crystals: Receiver, No. 71, 3/6 ea., 3/6 post. Transmitter, No. 50, 2/6 ea., 3/6 post. Amplifier, No. 165, 3/- ea., 3/- post.

W.W. POTMS, 500 ohm, knob, case, etc. New, 1/- ea., 1/3 post. **TRANN RA.12.G.**, 25/- carr. 15/- **RECV. R26 ARC.5**, 45/- ea., carr. 15/- **WAVEMETER C.R.1**, 25/5/- carr. 15/- **1109 RECR.**, less valves, vib., 35/- carr. 8/6 **RECR. UNIT R9.B.A.P.N.4**, 45/- carr. 8/6 **MODULATOR 67**, 39/- ea., carr. 7/6 **A.F. TRANSF.**, 1/-, post 9d. Above prices England and Wales only. All enquiries, requests for Lists, S.A.E. only. Money Back Guarantee. Fast Service. **25, ASHFIELD PLACE, OTLEY, YORKS**

"OSMOR NEWS". Fit an Osmor Band I III Equaliser Tunable Receiver. Components lists for "P.W.", "Consul Car Radio", "P.W.", "The Chorister" and "R. Constructor" "Beginner's 8 Wave 1 Valve" on request. OSMOR, 418, Brighton Rd., S. Croydon. (CRO 5148.)

SPECIAL OFFER. Hi-Fi HGP 59 Turnover Pick-ups, complete, only 28/6. Latest BSR TU.9 Gram. Units. High Fidelity Turnover Pick-up, 99/6. Denco fringe FM Tuners, £11; self-powered, £13. All goods brand new. C.w.o., carriage paid or c.o.d. Credit terms available. RICHARDS, Dunderdell, Carveza Road, Truro, Cornwall.

FM-AM CHASSIS

PUSH-PULL OUTPUT — 7 VALVES
HIGH SENSITIVITY — GRAM INPUT
7 x 5" FULL VIEW SCALE
AFC-AVC
ONLY 18/

BEL SOUND PRODUCTS CO.
Marborough Yard, N.18 Tel.: ARC 5078
20 mins. West End

AMAZING OFFER.—Originally £40-£100 each. Ecco, Pye, H.M.V., Marconi, Philips, Murphy, etc., 9-10in. Televisions, complete, not working, 50/- each; carriage paid; immediate dispatch; 12in., £5/5/-; 15in., £9/-; Philips 17in. Projection Televisions, £9/15/-; TOMLINS, 127, Brockley Rise, London, S.E.23.

LOUDSPEAKERS repaired promptly. MODEL LOUDSPEAKER SERVICE, Bullington Rd., Oxford.

SERVICE SHEETS

SERVICE SHEETS for sale and hire. Radio T.V. S.A.E. enquiries, J. PALMER, 32, Neasden Lane, N.W.10.

SERVICE MANUALS SHEETS, Tel. Radio for hire, sale and wanted. Mixed Manuals and Sheets, 12 for 10/-; s.a.e. enquiries, W. J. GILBERT (P.W.), 24, Frithville Gdns., London, W.12.

SERVICE SHEETS. Radio/Television Sale and Hire; s.a.e. with inquiry. SULTAN RADIO (P.W.), 11, Old Bond St., London, W.1.

(Continued on page 241)

SITUATIONS VACANT

THERE IS a national shortage of Mercantile Radio Officers. Why not make Communications your career? You can be assured of a sea-going appointment after qualifying at The School of Marine Radio and Radar (A.S.T.), Hamble, Southampton. For details, apply Commandant, quoting A.12.

RADIO (METEOROLOGICAL) TECHNICIANS required by Meteorological Office. Qualifications. Basic knowledge of radio and radar and experience in maintenance/operation of radar equipment including oscilloscopes. Successful applicants serve in United Kingdom and overseas. Commencing London salary £600 at age 25 or over, rising annually to £705 subject to deductions for each year below age 25. Provincial salary £28 to £30 lower. Overtime, night duty allowance, etc. Apply at any **EMPLOYMENT EXCHANGE**, quoting King's Cross 2458/036/99.

EDUCATIONAL

FREE! Brochure giving details of Home Study Training in Radio, Television, and all branches of Electronics. Courses for the Hobby Enthusiast or for those aiming at the A.M.Brit.I.R.E., City and Guilds, R.T.E.B., and other Professional Examinations. Train with the college operated by Britain's largest Electronics organisation. Moderate fees. Write to: **E.M.I. INSTITUTES**, Dept. PW28, London, W.4.

THERE IS a national shortage of Mercantile Radio Officers. Why not make Communications your career? You can be assured of a sea-going appointment after qualifying at The School of Marine Radio and Radar (A.S.T.), Hamble, Southampton. For details, apply Commandant, quoting A.12.

ELECTRADIX FOR BARGAINS

A.C. MOTORS 230 volts 50 c/s, 1 h.p., capacitor start, brand new, 4-hole mounting, 95/-, carr. 5/-.

VACUUM PUMPS, 7 cu. ft. per min. rolbs. per sq. inch at 1,200 r.p.m. Rotary vane type, 30/-, post 2/9.

SYNCHRONOUS MOTOR, 200/250 volts 50 c/s 1 r.p.m., clockwise rotation; totally enclosed, with spindle 3" long by 3/4" dia. 40/-, post 1/9.

MINIATURE MOTORS for model work, 4 1/2 v 6 volts D.C., weight 1 oz., size 1/2" x 1/2" thick. Ideal for up to 18" motor boats, model aircraft or remote control. 10/9, post free.

D.C. DYNAMOS, 14/32 volts, 9 amps. Shunt wound, 2,500 r.p.m., foot mounting. £7/10/-, Control Panel, 65/-, 12 volt, 5 amp. high-speed, with 70/1 reduction gear to 60 r.p.m. With smoothing unit, totally enclosed. 35/-, carr. 5/-.

PARALEX HOLE CUTTERS. Capacity 1-4", 32/6; 1 1/2-6 1/2", 35/-; 2-10 1/2", 95/-; 2-12 1/2", 105/-, Morse Taper shank; brand new—write for special Leaflet.

ELECTRADIX RADIOS

Dept. P. 214, Queenstown Road, Battersea, S.W.8. MACaulay 3159

11 + EXAMINATION

Write for **FREE 24-page GUIDE** and Test, sitting age of child, to: **THE REGISTRAR** (Dept. M8, Mercer's Correspondence College, 69, Wimpole St., London, W.1).

LEARN IT AS YOU DO IT—we provide practical equipment combined with instruction in Radio, Television, Electricity, Mechanics, Chemistry, Photography, etc. Write for full details to: **E.M.I. INSTITUTES**, Dept. PW47, London, W.4.

A.M.I.P.R.E.—For details of suitable study courses (only a limited number of students accepted) send for free Syllabus of Instructional Text, I.P.R.E. Conditions of Membership Booklet, 1/-; "The Practical Radio Engineer" Journal, sample copy, 2/3; 6,000 Alignment Peaks for Piperechts, 5/- All post free from **SECRETARY, I.P.R.E.**, 20, Fairfield Rd., London, N.8.

A.M.I.Mech.E., A.M.Brit.I.R.E., City and Guilds, etc., on "no pass—no fee" terms; over 95% successes. For details of exams, and courses in all branches of engineering, building, etc., write for 144-page handbook, free. **B.I.E.T.** (Dept. 242B), 29, Wright's Lane, London, W.8.

CITY AND GUILDS (Electrical, etc.) on "no pass—no fee" terms. Over 95% successes. For full details of modern courses in all branches of Electrical Technology send for our 144-page handbook free and post free. **B.I.E.T.** (Dept. 242A), 29, Wright's Lane, London, W.8.

T/V and RADIO,—**A.M.Brit.I.R.E.**, City and Guilds, R.T.E.B. Cert., etc., on "no pass—no fee" terms. Over 95% successes. Details of exams, and home training courses in all branches of radio and T.V. write for 144-page handbook free. **B.I.E.T.** (Dept. 242G), 29, Wright's Lane, London, W.8.

WIRELESS. See the world as a Radio Officer in the Merchant Navy; short training period; low fees; scholarships, etc., available. Boarding and Day students. Stamp for prospectus. **WIRELESS COLLEGE**, Colwyn Bay.

MAINS MIDGET TRANSFORMER.—200/250 v. A.C. output; 500 v. 25 m.A. 6.3 v. 1 amp. 10/6.

CHARGERS.—6 12 v. 2 amp., 45/-.

CHARGER TRANS.—200 250 v. A.C.; tapped sec. for 2, 6 and 12 v. 1 amp. 12/6; 2 amp. 15/-; 4 amp. 17/6.

CHARGER RECTIFIERS.—2, 6 and 12 v. 1 amp. 7/6; 2 amp. 11/-; 4 amp. 17/6.

PICK-UP with crystal turnover cartridge for L.P. & 78; special purchase 35/-.

COILS TRF.—m/1 wave with circuit, 7/6.

AERIALS.—Band II FM dipole, 7/6; Band III Dipole, 7/6; 3-element array, 25/-.

HEADPHONES.—HR 4,000 ohms, 16/-.

VIBRATORS.—4 pin, 6 or 12 v. 10/6.

SPEAKERS.—P.M. 3 ohms, 2 1/2 in., 17/6; 5 in., 17/6; 7 x 4 in., 19/6; 6 in., 18/6; 10 x 6 in., 27/6.

CHOKES.—New boxed, 65 m.A. 5/6; 85 m.A. 7/6; 150 m.A. 12/6.

VALVES, new boxed: 5U4G, 5Z1G, 6X8G; 6QT6; 12X7GT; 35L6GT; 35Z4GT; 25Z5; 6X4; 6X5; 6X6; 6X99; 6X100.

Postage on all orders, trade and mail order.

OSMABET LTD.

14, Hillside Road, Tottenham, London, N.15.

MISCELLANEOUS

THE TAPE RECORDER SPECIALISTS offer wonderful bargains in Tape. Famous British make. 7in., 1,200ft., 22/6; 5 1/2in., 1,200ft. (L.P.), 22/6; 5 1/2in., 850ft., 19/6; 5 1/2in., 850ft. (L.P.), 19/6; 5 1/2in., 600ft., 14/6; each plus p. & p. 1/6. Send now, only 500 recls. available. Tape Recorders bought for cash; all makes stocked; no interest terms; free offers; specialise repair service. **E. C. KINGSLEY & CO. (G.)**, 132, Tottenham Court Road, London, W.1. (EUSON 6590.)

WANTED

GLASGOW. Cameras bought for cash or taken part exchange for Tape Recorders, Players, or Amplifiers. **VICTOR MORRIS**, 405, Argyle St., Glasgow, C.2.

WANTED VALVES

All types for prompt cash. Must be new. State quantity.

WILLIAM CARVIS LTD.

103, North Street, Leeds, 7.

VALVES WANTED. ECL80, EY51, EY86, PL81, PCF80, and all Miniature Types. U25, 10C1, 10C2, 10F1, etc., 5Z4G, 6K8G, 6V6G. Brand new only. Prompt cash by return. **R.H.S.**, 155, Swan Arcade, Bradford, 1.

WANTED, Transmitter T.59, Trans-receivers TR.1520, 1934, 1935, 1936, 1987, Receivers BC.312 and type 103, P.S.U. type 301, Dynamotors DM.21 and DM.28, GILFILLAN, 7, High St., Worthing, (Tel. 8719.)

(Continued overleaf)



GP35/A EQUIPMENT CABINET

3 ft. wide, 17 in. x 14 in. Motor Board. Supplied in Oak, Walnut or Mahogany veneers finished to shade required.

Alternative Interior. Motor Board 35 in. x 14 in. and Control Panel omitted.

Price £16.10.9 OR 47/- Deposit and 9 Monthly Payments of 33/9 Delivery 12/6

Write for Catalogue of Cabinets for Equipment Records and Speakers.

A. L. STAMFORD (Dept. T29) Correspondence: 20, College Parade, Salisbury Rd., London, N.W.6 Showroom; 98, Weymouth Terrace, London, E.2. Phone SHO 5003

FOR SALE

MINIFON POCKET WIRE RECORDER with foot controls. £63 o.n.p.; Swan London. Box 7, c/o PRACTICAL WIRELESS.

TAN IN 24 HOURS.—Super-tonic Sunray Lamps. Ultra-violet Infra-red combined; automatic exposure; controlled emission; all mains. Listed £7 10/- our price, 80/-. S.A.E. illustrated brochure. Dept 100. SCIENTIFIC PRODUCTS, Cleveleys, Lancs.

EVERYTHING FOR THE AMATEUR. Write for our new List catering for home engineers, Hi-Fi Fans, Tape Recording Fans, etc., etc. Probably the most comprehensive in the trade. Price 1/-. R.H.S., 155, Swan Arcade, Bradford 1.

F M TUNER: I F 373 conversion in April '57 P.W. Complete kit. £5. Box 6, c/o PRACTICAL WIRELESS.

PRACTICAL Informative Booklets, e.g., Electronics for Boys; 208 Special; Fault Finding; Electronic Novelties; Amplifiers, 1/6 each, post. 3d. Many others. Components, Kits; mail order only; s.a.e. enquiries. ELEKTRO RADIO, 8, Myers Rd. West, Liverpool, 23.

VALVE CARTONS.—We can supply from 12 to 100,000 off the shelf Plain white or printed. Miniatures, 10; "G.T.s." 12; "Gs." 14—per 100, plus 2/- postage. Also printing done to your special requirements; quotations gladly given. J. & A. BOX-MAKERS, 75a, Goodwin St., Bradford, 1.

HIGH GAIN Short Wave Converters, from £2 5/-; s.a.e. details. G.P.X.B. 86, Cross Rd., Southwick, Sussex.

300-WATT TRANSMITTER FOR ONLY £15 DOWN

and 8 monthly payments of £14.0.0.
Delivery after first payment. Cash price £120.0.0.

LOOK AT THE SPECIFICATION !!!

Power Output—300 watts all services.
Power Input—180/250 volt 50 cycle A.C. Mains.

Hand or High Speed Keying.
Crystal or MO Control with temperature compensated MO circuit.

Types of wave—C.W., M.C.W., and R.I.
Frequency Range—1.5 Mc/s to 20 Mc/s.
Modulation—100 per cent.

Output Impedance—50 Ohms coaxial Feeder.

Audio Input Impedance—600 Ohms.
Remote Control facilities if desired.

ALSO:—Hallicrafters S-27 Communication Receivers.

Wireless Sets 62—14 to 16 Mc/s
Send and Receive.

Wireless Sets 88 Walkie-Talkies
40 to 42 Mc/s.

Wireless Sets 19 with all operating equipment.

Collins T.C.S. Sets complete 11-12 Mc/s with Power Supply Units for 12 volt, 24 volt or Mains Supply.

H.P. or Credit Facilities on all goods.

R. GILFILLAN & CO., LTD.

7, High Street, Worthing, Sussex.
Tel.: Worthing 8719 or 30181.

FOR IMMEDIATE DISPOSAL!

Non-Auto Collaro Junior 4-speed A.C. Motors with separate dual hi-fi pick-up. New. Maker's cartons. 70/-. Baseboard cut-out 15in. x 13in. (if required), 5/-.

New Continental Type Star "Galaxy" 4-speed Multi-mixer Autochange Unit. A.C. mains. Maker's cartons. £4.0.0. Baseboard cut-out 18in. x 16in. (if required), 10/-.

Collaro RC54 3-speed Auto-Mixer Unit. Complete, but 110 volts A.C. 50 cycles. Maker's carton. £5.

Vidor "Hornet" Cycle Hooters. List 7/6. Fully complete, 2/6. (Can be used as buzzers, etc.)

Hi-Fidelity Midget 2-Stage A.C. 4 Watt Amplifier (transformer job). With valves ECL82 and 6X4 (less speaker). New. Maker's carton. 70/-.

Roll Films. Ensign 620 (outdated), Panchromatic EFP62, fine grain. Tin, 1/-.

Isophon Type STHB7 Electrostatic Speaker. With circuits, etc. New. 5/-.

9in. Mazda S.H. (Reception Tested) Television Tubes. Type CRM92A. 20/-.

Television Co-axial Cable. Band 1/III (brown). Yard 6d.

Cash with order.

Please allow for Post and Packing on all goods.

MAZEL RADIO

(Dept. P.W.)

124/136 London Road,
Manchester, 1, Lancs.


Phone: Ardwick 3505

SPECIAL OFFER of TRANSMITTER-RECEIVERS

Type 38 Mk. II (WALKIE TALKIE)
A recent direct Large Purchase of this well-known Tx-R enables us to make this

VERY SPECIAL OFFER

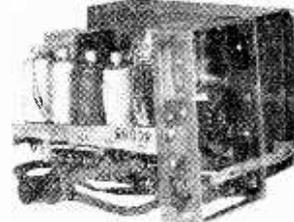Type "38" Mk. II complete in Metal Carrying Case. 9 x 6 1/2 in. x 4 in. Weight 6 lbs. Frequency 7.3 to 9 Mcs. Five valves. £17/6, post paid.



These Tx-Rs are in NEW CONDITION, but owing to demand they are not tested by us and carry no guarantee, but should prove SERVICEABLE.

ATTACHMENTS for Type "38" Trans-receivers, ALL BRAND NEW: Headphones 15/6; Throat Microphones, 4/6; Junction Boxes, 2/6; Aerials, No. 1, 2/6; No. 2, 5/-; Webbing, 4/-; Haversacks, 5/-; Valves—A.R.P.12, 4/6, A.T.P.4, 3/6; Set of FIVE VALVES, 19/- the set.

OFFER No. 2:

"38", as above, complete with set of external attachments, 42/6, post paid.

OFFER No. 3:

Transmitter-Receiver "38" Mk. II Brand New with complete set of external attachments and complete set of spares, including Webbing, Haversacks and Valves, 57/6, post paid.

TRANS RECEIVERS. Type "18" Mark III, Two Units (Receiver and Sender). Six Valves, Micro-ammeter, etc. in Metal Case. Untested, without guarantee but COMPLETE. £2/18/6.

ATTACHMENTS for "18" Trans-receivers, ALL BRAND NEW, Headphones, 15/6; Hand Microphone, 12/6; Aerials, 5/-; Set of 6 Valves, 30/-.

R.109 RECEIVERS S.W. Receiver in Case, eight valves. Speaker and 6-v. vib. Pack. Untested, no guarantee but COMPLETE. £2/18/6.

RESISTANCES. 100 Assorted useful values. New wire end. 12/6.

CONDENSERS. 100 Assorted Mica; Tubular; etc., 15/-.

BOMBSIGHT COMPUTERS. Ex-R.A.F. NEW. Hundreds of Components, Gears, etc. Ideal for Experimenters, £3.

LUBBRA HOLE CUTTERS. Adjustable 3/4 in. to 3 1/2 in. For Metal, Plastic, etc., 7/-.

QUARTZ CRYSTALS. Types F.T.241 and F.T.243. 2-Pin, 3/4 in. Spacing. Frequencies between 5,675 kcs. and 8,650 kcs. (F.T.243).

20 Mcs. and 38.8 Mcs. (F.T.241. 54th Harmonic), 4/- each. ALL BRAND NEW.

TWELVE ASSORTED CRYSTALS, 45/-.

Holders for both types 1/- each. Customers ordering 12 crystals can be supplied with lists of Frequencies available for their choice.

MORSE TAPPERS. Standard 3/6; Extra Heavy on Base, 5/6.

TRANSPARENT MAP CASES. Plastic 14in. x 10 1/2 in. Ideal for Maps, Display, etc. 5/6

STAR IDENTIFIERS. Type I A-N Covers both Hemispheres, 5/6.

CONTACTOR TIME SWITCHES. 2 impulses per sec. in case, 11/6.

Post or carr. extra. Full list Radio, Books, etc., 3d.

SOUTHERN RADIO SUPPLY, LTD.

11, LITTLE NEWPORT STREET,
LONDON, W.C.2. GERard 6653

REPANCO HIGH GAIN COILS

Dual Range Crystal Set Coil, Type DRX1	...	2 6
Dual Range Coil with Reaction, Type DRR2	...	4/-
Matched Pair Dual Range T.R.F. Coils, Type DRM3 pair	...	8/-
Pair Dual Range Superhet Coils, Type SH4, pair	...	8/-
Miniature Iron Dust Cored Coils, Type "R" :-		
Range Aerial	H.F. Osc.	
800-2,000m. RA1	RHF1 RO1	
190- 550m. RA2	RHF2 RO2	each 3 3
70- 230m. RA3	RHF3 RO3	
15- 50m. RA4	RHF4 RO4	
Ferrite Rod Aerial, Dual Range Type FR1	...	12 6
Miniature I.F. Transformers, Type MSE (465 Kc s), pair		12 6
Standard I.F. Transformers, Type TCG (465 Kc s), pair		13 6

EASY-TO-BUILD TRANSISTOR RECEIVERS

Repanco "Three Dee."—A new dual range radio with band pass tuning using a crystal diode and 3 transistors. Easy wiring plans and instructions. 1/- post free.

Repanco "Transeven."—Latest portable superhet 7 transistor receiver with preset tuning for 4 stations. Easy wiring plans and instructions. 1 9 (post free).


Repanco "Mini-7." The amazing new Pocket Transistor Radio. Size only 3 1/2 in. x 3 1/2 in. x 2 1/2 in. A seven transistor Superhet circuit fully tunable over medium wave. Uses 3 White Spot and 4 Red Spot transistors. Attractively housed in a plastic case. Comprehensive plans and component price list 1 9 (post free).

RADIO EXPERIMENTAL PRODUCTS LTD.

33 MUGH PARK ST., COVENTRY

Tel. 62572.

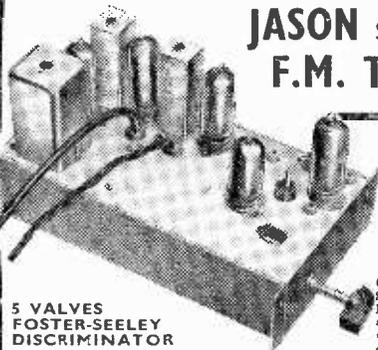BUILD THIS AUTHENTIC JASON SWITCHED F.M. TUNER



JASON MERCURY

5 VALVES FOSTER-SEELEY DISCRIMINATOR

This British-designed F.M. Tuner provides choice of the three B.B.C. programmes at the turn of a switch, with a fourth position for "OFF." It is a stable unit, free from drift and of high quality. The Switch Tuned Front End is supplied wired, tested and aligned, complete with 2 valves and station-indicating plate. Chassis ready punched. In conformity with all Jason F.M. Units, this model is completely stable and offers the highest possible standards of reproduction.

CONSTRUCTOR'S SWITCH-TUNED MODEL with assembled Front End with two valves and all parts as specified come to **£9.0 0**

SWITCH-TUNED FRONT END with two valves, complete.

£6.5 0

(Incl. £1.15 O.P. Tax)

Data Publication Book of the Tuner (Post Paid) **2/-**

JASON POWER PACK **£2.1 9**

Paris come to

FROM LEADING STOCKISTS, or in cases of difficulty: **THE JASON MOTOR & ELECTRONIC CO.**

3-4 Gt. Chapel Street, Oxford Street, London, W.1

"D I Y"

Yes! YOU can DO IT YOURSELF with the aid of our RADIO HOME CONSTRUCTOR'S HANDBOOK. Over 100,000 enthusiasts already have earlier issues of this famous publication which gives full parts lists, circuits, etc., of many receivers, tape recorder, oscilloscope, feeder units, communications set, hi-fi amplifiers, power pack, crystal set, etc. (Incl. "P.W." Coronets). It is also packed with data, construction, soldering and servicing hints, facts, formulae, colour code, etc. Our latest "Easy-as-A.B.C." FULL SIZED P-P. Construction sheets are available FREE with orders so that even the beginner gets professional results first time! This claim is confirmed by many hundreds of genuine testimonials received. Send 3/- to-day for your copy. (Worth much more!)

NOWHERE IS THERE A BOOK SO VALUABLE TO THE NOVICE CONSTRUCTOR AND EXPERT!

RODING LABORATORIES

Hurn Airport, Christchurch, Hants

TECHNICAL TRADING CO.

1 SPEED CHANGERS LATEST MK. II STAAR GALAXY

With "hi-fi" Power Point lightweight sapphire turnover head, plays 10 records, highest quality and finish (listed £12/16/-).

Brand new in Manufacturer's Boxes **£3-19-6!!**

TRULY THE OFFER OF THE YEAR Post 3/- ALSO Limited Quantity as above, but with latest "hi-fi" Acos turnover needle pick-up, £4/10/6.

S.A.E. NEW LIST 500 AMAZING SNIPDS INCLUDING: 12 Volt 3-4 amps charging packs, 3/6, 10in. quality speakers, 19/-, Octal valveholders, 2/6 doz., meter pots, 12 switch, 3/- spindle, 3/6, Midget 465 Kcs J.F.S., 5/- pair, Dubilier 16+16 350 v.w., 3/-, 89A Amphenol valveholders, w/screen, 1/-, Germanium xtal diodes, 9d. ea., 8/- doz., TRANSISTORS, Red Spot, L.F., 7/-, White Spot, R.F., 14/-.

S.A.E. FOR TRULY LOW-COST LIST 100 VALVES:

5U4G 6/6 | 6C4 4/8 | ECC82 6/6 | 6X4 6/- | 5Z4G 9/-
 6F50 2/6 | 6F91 7/6 | 6V6GT 6/6 | 6J5G 3/- | 6K7G 4/6

10,000 OTHER BARGAINS AND TELEVISION SETS AT --

350/352 FRATTON ROAD, PORTSMOUTH

TRANSISTORS ARE OUR SPECIALITY

ALL PRICES ARE POST PAID

Red Spot, 7/6, Red/Yellow, 21/-, White Spot, 12/6, Green/Yellow, 10/-, Also, Mullard & Mazda Types, Crystal Diodes, 1/3.

The New "Mini-Seven" Circuit, 1/6. "Transeven" Portable Circuit, 1/6 (Kit now ONLY £10.12.6.) 3-Transistor Radio Circuit, 11d. HEADPHONES.—Low Res. Ex-W.D., 8/11.

ELECTROLYTICS—GUARANTEED 16 mfd. 450 v. 150 mA. 1 1/2" x 1", 2/4 each. 8-8 mfd. 450 v. 10" mA. 1 1/2" x 1", 2/9. 8-16 mfd. 450 v. 100 mA. 1 1/2" x 1", 2/9. 50 mfd. 50 v., 1/6. 25 mfd. 25 v., 1/8. Resistors: All Values 10%, 1 watt, 6d. ea. TERMS: C.W.O. or C.O.D. (over £2). FULL COMPONENT LIST, 6d.

OAKFIELD RADIO

44 OAKFIELD ROAD, STOCKPORT

T.V. Servicing, Vol. I by Patchett, 5/-, postage 0d.

Tape Recorders and Tape Recording, by Weller, 23/-, postage 1/-.

The A.R.R.L. Handbook 1958, 32 6, postage 1/9.

Model Boat Radio Control by Casebrock, M. A. P., 6/-, postage 8d.

Portable Transistor Receiver by Amos, reprint W.W., 2/6, postage 6d.

Quality Amplifiers Data Book No. II, 4/6, postage 6d.

Radio Controlled Models by Camm, 12 6, postage 1/-.

We also have a full range of Slide Rules and Drawing Instrument Sets. Send for list.

UNIVERSAL BOOK CO.

12 Little Newport Street, London, W.C.2

(adjoining Lisle Street)

1% AC/DC Multimeter Kit 27/6

A new kit for your 1 mA meter (any resistance). Ranges 2.5, 10, 100, 250, 500 Volts DC; 10, 100, 250, 500 Volts A.C.; 10, 100 mA, 1 amp.; Ohms range. Kit comprises 1% High Stab. multipliers, 1% shunts, GEC instrument rectifier, W.W. pot., two switches, current, instructions, 27 6, post free. Circuit and instructions only, 9d. 5 mA meters are cheap! Build yourself an eight range AC/DC Voltmeter with reliable 1% Wirewound resistors. Set of 8 resistors, for 10, 100, 250, 500 Volts AC and DC, with circuit, 16/-.

SPECIAL OFFER: for one month only. Set of 18 Wirewound resistors, 1% accuracy, to make Wheatstone Bridge for measurement of resistance (0.1 ohm to 1 Megohm. With circuit and notes, 19/6.

New list now available, send 3d. stamp.


PLANET INSTRUMENT CO.

25, DOMINION AVE., LEEDS 7.

ELGE RADIO PEN

Versatile pocket
Fault
Finder

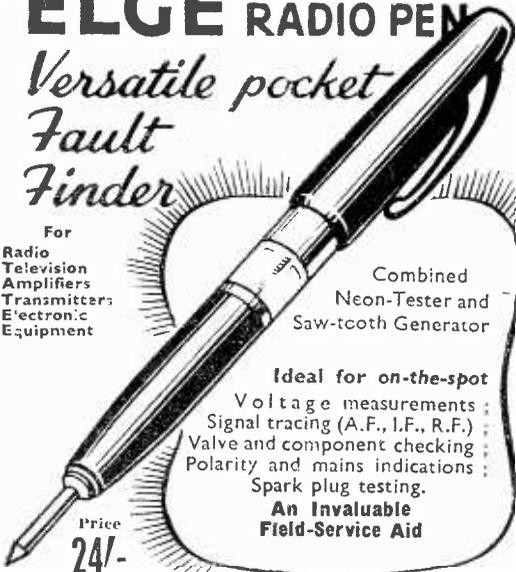For
Radio
Television
Amplifiers
Transmitters
Electronic
Equipment



Combined
Neon-Tester and
Saw-tooth Generator

Ideal for on-the-spot
Voltage measurements
Signal tracing (A.F., I.F., R.F.)
Valve and component checking
Polarity and mains indications
Spark plug testing.

An Invaluable
Field-Service Aid

Price
24/-

MERCIA ENTERPRISES LIMITED

Godiva House, Allesley Old Road, Coventry

S.A.E. for illustrated leaflet. Trade Enquiries invited.

COVENTRY RADIO

Component Specialists since 1925

We have now trebled the size of our premises in order to supply a larger range of Components, Amplifiers and Hi-Fi Equipment.

Send your enquiries to :

189-191 Dunstable Road, Luton, Beds.
New Telephone No. : LUTON 7388-9

HANNEY

offers

COSSOR 3 VALVE 3 WATT
HI-FI AMPLIFIER KITS,

£9 - 15 - 0

CARRIAGE PAID

AVO MULTIMINOR

£9 - 10 - 0

Components for

OSRAM 912 PLUS AMPLIFIER
OSRAM 912 PASSIVE UNIT
OSRAM 912 PRE-AMPLIFIER
OSRAM F.M. PLUS TUNER
MULLARD 510 AMPLIFIER
MULLARD 510 "A" PRE-AMPLIFIER
MULLARD 510 "B" PRE-AMPLIFIER
MULLARD 3/3 AMPLIFIER
MULLARD F.M. TUNER UNIT
DENCO MAXI-Q F.M. TUNER UNIT

Manuals available :
912 PLUS AMPLIFIER—4/- ; OSRAM F.M. PLUS TUNER—
2/6 ; MULLARD HIGH QUALITY AMPLIFIER MANUAL
(contains F.M. details)—3/6 ; DENCO F.M. TUNER—1/6.
Send 3d. postage, stating lists required. General Components
list also available.

L. F. HANNEY

77, Lower Bristol Road
Bath

AMOS (ELECTRONICS) LTD. BLETCHLEY, BUCKS

COILS FOR RADIO & TELEVISION

R.F. E.H.T. Coil giving up to 7 Kv at 1 m.a. (As described in *Practical Television*, April 1957.)

I.F. COILS

465 and 470 Kc's Coils in miniature can, screw core, 10.7 Mc's coils.

AERIAL COILS TAPE-DECK OSCILLATOR COILS
WAVEOUND CHOKES PRE-TUNED COIL PACKS

R.F. E.H.T. GENERATOR COILS

Write for details and prices.

B.B.C.-I.T.V.-F.M. AERIALS

Band 1 (B.B.C.) Telescopic
Loft, 19 6. External
S Dipole, 23 3.
Band 3 (I.T.V.) 3 element
loft array, 24 -. 5 element
32 3. External wall mounting
3 element, 33 9. 5
element, 41 6. Combined
(B.B.C.-I.T.V.) loft 1 3
element, 41 3. 1 5
element, 43 9. External
wall mounting, 1 3
element, 56 3. 1 5 element,
12 9. Room aerial,
56 3. P.P. 2 6. Co-axial 8d. yd. Co-axial
plugs, 1 2. State channel when ordering.
C.W.O. or C.O.D. S.A.E. for price list.

K.V.A. ELECTRONICS (Dept. 11)
189, Kent House Road, Beckenham,
Kent, S.Y.D. 2483.

TELEVISION

The advance of Radio Technique will offer unlimited opportunities of high pay and secure posts for those Radio Engineers who have had the foresight to become technically qualified. How you can do this quickly and easily in your spare time is fully explained in our unique handbook. Full details are given of A.M.Brit.I.R.E., City & Guilds Exams., and particulars of up-to-date courses in Wireless Engineering, Radio Servicing, Short Waves, Television, Mathematics, etc., etc. We guarantee "NO PASS—NO FEE." Prepare for to-morrow's opportunities and future competition by sending for this very informative 14-page guide NOW—FREE and without obligation.

BRITISH INSTITUTE OF
ENGINEERING TECHNOLOGY
(Dept. 242), COLLEGE HOUSE,
29-31, Wright's Lane, Kensington, W.8

VALVES—Guaranteed


EA50	2-1VR65	3 6SB6	7-6U7	5-
EB41	7 6 VR65A	3 6BH6	5/-7B6	8-
EB91	7-1VR91	4-6BW6	6 8 7D3	7 6
ECC33	8 6 VR137	4-6CSM	6-3D2	4 6
EF36	4 6 VT29	3 6 3D2	7-3D2	5-
EP37	7 6 VT51	4-6R6	7-3D2	5-
EP39	5 6 VT51	4-6R13	11 6 9D6	5-
EP59	5-1VU11	2 6 6J5	6-12BA6	7 6
EP83	8 6 W77	5-6J6	6-12BE6	6-
EP32	5-0Z4	5-6KTG	4 6 12A7	8 6
PS1	5-2Z52	8 6 6KT7M	5 8 12K7	8-
PY31	9 0 1D5	8 6 6SA7	8-15D2	6-
PY81	10-11N5	6-6SN7GT	18	7 6
SP41	4-4D1	4-	8 6 20D1	12-
SP61	6-6AKC	7 6 6U5	7 6 35V1	7 6
TT11	3 6 8A15	7-8UUX	50C5	8 6
VR21	4-8B8	6-	7 6 78	7 6

Postage 6d. per valve, orders over £1 post free. (Also all components) TV Tubes, Perfect Condition (callers only) MW22 16, MW 22 1B, £4.0.0 each. Also all Transistor Components.

TELEKIT SUPPLY

101 High Street, Beckenham, Kent.
Phone : BEC 6729

Armstrong AM/FM RADIOGRAM CHASSIS

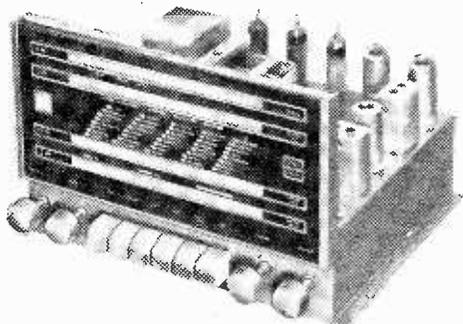

MODEL PB 409 (illustrated) 28 Gns.

A high quality Radiogram Replacement Unit

- ★ 9 valves ★ 6 watts Push-Pull output ★ Negative Feedback
- ★ 4 wavebands including VHF ★ Quick action Piano Key Selectors
- ★ Separate Bass and Treble controls ★ Magic Eye.

MODEL AF 105 £37

AM and FM Tuners and High Fidelity Amplifier on one compact chassis

- ★ 10 valves ★ 10 watts Push-Pull output ★ 20 dB Negative Feedback
- ★ 5 wavebands including VHF ★ Independent wide range Bass and Treble controls with visual indicators ★ Magic Eye.

Whether you replace the "works" in your radio or radiogram...

Whether you build a new radiogram that is all your own work...

Whether you can't be bothered with the woodwork and just put it on a shelf...

AN ARMSTRONG IS THE ANSWER

Post this coupon or write for descriptive literature and details of Home Trial facilities, Credit terms and Guarantee to Armstrong Wireless and Television Co. Ltd., Warklers Rd., Holloway, N.7. Tel.: NOR 3213. BLOCK CAPITALS PLEASE.

NAME
ADDRESS

Demonstrations at our Holloway Showroom 9-6 Weekdays and Saturdays. PMY

RES/CAP. BRIDGE 35/-
p. & p. 2/-
Checks all types of resistors and condensers.
Easy to Build Up Easy to Use
READY CALIBRATED
Stamp for details of this and other kits.
RADIO MAIL (Dept. P)
Raleigh Mews, Raleigh Street, Nottingham

1-Finger Pianists
Build your own electronic keyboard and play everything! Send for free leaflet. Guitar, cello, flute and trumpet are all easy. Write now...
C & S, 10 Duke St., Darlington, Co. Durham

LYONS RADIO
LTD.
Dept. M.P., 3 GOLDHAWK ROAD
SHEPHERDS BUSH, LONDON, W.12
Telephone: SHEpherds Bush 1729

RECEIVERS TYPE R.1155N. One of the best known and most popular of ex-Government communications receivers. This model embodies the extended frequency range to include the Shipping and Trawler Band and is fitted with the latest type of improved slow-motion drive. The frequency range in 5 switched bands is 500 to 200 Kc. (600 to 1,500 metres) and 600 Kc. to 18 Mc. (17 to 500 metres). Power requirements are H.T. approx. 250 v. smoothed D.C. and L.T. 6.3 v. A.C. Supplied in good condition and working order together with circuit diagram and instruction leaflet which includes power pack constructional data. **PRICE ONLY £10.10.0.** carriage 10/-.

HEADPHONES. Brand new ex-Gov. by Ericssons with metal headband and long connecting cord, resistance 4,000 ohms. **PRICE ONLY 10/6.** post 1/6.

POWER UNITS TYPE 325. As fitted in many types of Marconi/Ecco Test Instruments. Exceptionally well finished chassis 7 1/2 in. long x 4 1/2 in. wide extends from back of front panel which is 10 in. x 5 in. Input 200-250 v. 50 cps. A.C. mains. Output approx. 250 D.C. (Unsmoothed) at 75 mA., 6.3 v. A.C. at 3 A. and 4 v. at 2 A. Mains input interference suppressor unit is incorporated. In absolutely mint condition and supplied with a most useful transit case 11 in. long x 6 1/2 in. wide x 10 in. deep with leather carrying strap. **PRICE ONLY 35/-.** post 3/6.

TEST SET TYPE 48. Comprises an R.F. oscillator having a frequency of 350 Mc. employing valve RL18 with a switched 750 cps. modulation, valve VR118 being employed in this circuit. The radiator is a wave vertical rod. Operates from 6 v. L.T. and 120 v. H.T. Housed in Teak instrument cases, with space for batteries, 15 x 10 x 8 1/2 in. In good condition. **PRICE ONLY 30/-.** carriage 4/6.


Solder with
PERMATIP
AND
PERMABIT
INSTRUMENTS
FOR
**GREATER
SOLDERING
EFFICIENCY**

The soldering bit which maintains its face indefinitely without attention. 25 models available for mains or low voltage supply. Bit sizes 3/32 to 3/8 inch. Full details in booklet S.P.10 from sole manufacturers :-
LIGHT SOLDERING DEVELOPMENTS LTD.,
106, GEORGE STREET, CROYDON, SURREY. Tel. CR0ydon 9589.

THE WAVEMASTER
TRANSISTOR PORTABLE

AN OLYMPIC WINNER
Pick of the World's Stations at your finger-tips.
Long and Medium Wavebands.
Comprehensive assembly data and Components Lists, 1/6.
Complete Receivers Available.
OLYMPIC RADIO COMPONENTS, LTD.
224, Hornsey Road, Holloway, N.7.

P.C.M. SUPERB RECEPTION OF V.H.F.

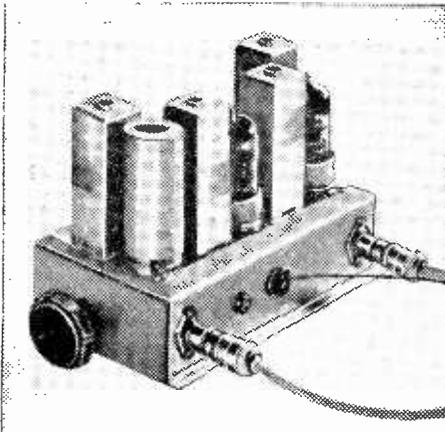

This **SWITCHED** Tuner is a sensitive and entirely drift free unit fitted with the new **DIOMATIC FREQUENCY CONTROL** which is 10 times as effective as a conventional reactance valve. **DOUBLE VALVES** are used throughout, enabling a **SIX VALVE** circuit to be constructed on a chassis 3in. x 5½in. An included **PRE-AMPLIFIER** gives 10 volts output. All Parts and Valves, **£7.19.6**. Instructions 2/- from **C. & G. KITS**, Dept. F.M., 285, Lower Addiscombe Rd., Croydon, Surrey.

INFRA-RED VIEWING EQUIPMENT

See in the dark with equipment specially developed for night driving, reconnaissance, sniping, etc.

MONOCULAR £1.0.0. Carriage paid

Sealed unit incorporating push button operated zamboni pile. Focusing eyepiece. Brand new in stout hide (binocular type) case.

MONOCULAR £1.10.0. Carriage paid

Larger, all plastic model, with bigger caesium cell. Brand new in superb hide shoulder strap carrying case.

VIEWING LAMP 17/6 Carriage paid

Weatherproof car spotlight providing a powerful source of infra-red rays through easily removable filter. Takes standard 12 v. bulb. Swivelling single-point bumper fitting. Brand new.

12 VOLT SOLENOID

Powerful solenoid with lever mechanism giving mechanical advantage of approx. 4:1 (½in. travel ¾in. arm). Consumption 350 mA. Ideal for remote controls, model railways and mechanical indicators. Bargain offer—3 for 10/-, p.p.

PROOPS BROS. LTD.

Dept. P. 52 Tottenham Court Road, London, W.1
Tel.: LANGHAM 0141. Shop hours: 9-6. Thurs. 9-1

TRANSISTOR SUPPLIES

TRANSISTORS. L.F., 7 8; R.F., 13 6 and 18 -; Mullard OC71, 24 -; OC72, 30 -; Matched pairs OC22, 23. Diodes, 1 6; Mullard, 5 -; Brimar, 7 6. **MORCO TRANSISTOR** and Diode Coil for transistor and diode circuits, 3 -; **TRANSISTOR TRANSFORMERS**, interstage, 8 8; Driver Push-Pull, 8 6; Push-Pull output, 8 8. **ELECTROLYTICS** for transistor circuits, 8 0F, 2 -; 15 0F, 2 -; 50 0F, 1 6. **FERRITE ROD ASSEMBLY**, long, medium wave and coupling coil for MORCO CIRCUIT, 19 6. **Loud SPEAKER**, sensitive P.M. 5in., 18 6; output transformer for same, 5 -. **HEADPHONES**, L.R., 8 6; H.R. (4,000 ohms), 17 6. **TRANSFORMERS**, MULLARD CIRCUIT, 20 -; Bargain Lines—Balanced inserts (as miniature speakers), 5 -; Trimmers 100, 250, 750H., 1 9; Var Condenser, Air 0003 3 -; 8ins. speakers with output trans., 16 6; Sub-Miniature Transistor Transformers, 8 6; Super Coax, semi-air, 1 -; 3d; ordinary coax 6d. yd.; Crystal Inserts, 4 6; Two High Resistance Earpieces, Band and Flex to assemble own H.R. Phones, 9 -; Limited Stocks, Morse Keys, 2 6. Terms: C.W.O. postage extra. Eyes refused. Send 3d. stamps for transistor circuits and list.

MORCO EXPERIMENTAL SUPPLIES

(Props.: Moores (Sheffield), Ltd.)

8 & 10, GRANVILLE ST., SHEFFIELD, 2
Tel.: 27461.

Morse Code operating as a PROFESSION

45 years of teaching Morse Code is proof of the efficiency of the Candler System.

Send 3d. stamp for Payment Plan and full details of all Courses.


CANDLER SYSTEM CO., Dept. 51.0
52b, Abingdon Road, London, W.8.
Candler System Co., Denver, Colorado, U.S.A.

HERTFORDSHIRE WE'RE HERE!

Ex-Government Radio Equipment and Surplus Components. At Lowest London prices

E.M.A.

41 Cowbridge, Hertford

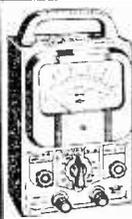

PULLIN SERIES
100 HIGH RESISTANCE TEST METER

A.C./D.C.
10,000 ohms/volt
21 RANGES
100 microamps to 1000 v.

Complete in die-cast case with test leads, clips & prods.
FULLY GUARANTEED

CASH PRICE or Deposit £2-10-0 & nine further monthly payments of £1-4-6.

Illustrated brochure free on request

FRITH RADIOCRAFT LTD
69-71 CHURCH GATE LEICESTER
& 28 HIGH ST. NEWPORT PAGNELL Bucks

RECORD PLAYERS



COLLARO AC.3/554. Three-speed, single player for A.C. mains 200/250 v., cream finish, complete with turnover crystal pick-up, "T" type head. Strictly limited quantity at **£8.19.6**, plus 5/6 carr.

CRYSTAL PICK-UPS fitted Acus HG377 cartridge. Ultra lightweight. Our price **£7.6**, plus 2/6 carr. **3-SPEED RECORD PLAYERS**, fitted with Acus turntable HGP59 pick-ups with twin sapphire styli, rexine case with lid, fitted clasp and handle. Worth 10 gns. Our price **£7.15.6**, plus 6/6 carr.

3-SPEED GRAM MOTORS, complete with crystal pick-up. Our Price **79/6**, plus 5/6 carriage.

REXINE COVERED CABINETS, single player size, suitable most non-auto units, including transcription motors. (Motor board uncut). Our price **£6.6**, plus 5/6 carriage.

PORTABLE RECORD PLAYER CABINETS to house Monarch, Collaro or Garrard 120 Changers, with space for Amplifier and Speaker. Rexine finish in attractive colours, fitted catches and handles. Our price **£8.5.0**, plus 5/6 carriage. Send stamp for complete bargain lists.

RONALD WILSON & CO.

(DEPT. P.W.), 12 BRIDGE STREET, WORCESTER

Forrest

Transistor Transformers for Quality Equipment

H. W. FORREST (Transformers) Ltd.

349, Haslucks Green Road, Shirley, Solihull, Warwicks. Tel.: Shirley 2483.

All material offered below guaranteed new and perfect. Money refunded if dissatisfied.

METERS.—5 amp. D.C. M.I. 2 1/2 in. Pl. Rnd. 11/6. 7 1/2 amp. D.C. M.I. 3 1/2 in. Rnd. Pr. 12/6. 1 mA. M.C. 2 1/2 in. Pl. Rnd. 22/6. 200 mA. M.C. 2 1/2 in. Pl. Rnd. 9/6. 25 v. D.C. M.C. 2 1/2 in. Pl. Rnd. 7/6. 300 v. A.C. M.C. 2 1/2 in. Pl. Rnd., 22/6. P. & P. on all meters 1/6 each.

VERNER REVOLUTION COUNTER. 6 columns, fixed reduction drive, built inside small unit. New. 9/6 each. P. & P. 2/-.

U.S.A. RELAYS. 27 volt miniature, 4 pole change over, 5/6 each. P. & P. 6d.

MURHEAD PRECISION ROTARY SWITCH SWITCHES. 4 banks, each bank 24 position, heavy duty contact, 17/6 each. P. & P. 1/6.

HIGHEST QUALITY DIAMOND REPLACEMENT STYLUS with 6 months guarantee. Please specify type of your record player. £3.0.0 each, including P. Tax and postage.

SLIDER RESISTANCE HEAVY DUTY. 79 ohms, 2 barrels with lead drive 2.9 amp. Price 22/6. P. & P. 3/6.

PHOTO MULTIPLIER. Type 561A, for Alfa counter, film scanning, spectrography, etc. £25/- each. P. & P. 1/-.

TELEPHONE HANDSETS, sound power, pair will work by simple connection without batteries. 22/6 each. P. & P. 1/9.

TELEPHONE HANDSETS, U.S.A. Similar to G.P.O., with switch, on 6 hooks, each. 12/6 each. P. & P. 1/6.

ARMOUR RECORDING WIRE. U.S.A. Top quality on original reels, length 8,700 yards 17/6. P. & P. 1/6.

HEADPHONES. 4,000 ohms, imported, 15/-, L.R. M.C. 8/6. Brown, 12/-, H.S.30 L.R. U.S.A. mit. ear pads, 15/-, P. & P. on above 1/6 each.

MICROPHONES. Throat, British, magnetic, 4/6. Throat, carbon, U.S.A., 3/6. No. 8 carbon, with switch, 7/6. Type 48, ex. ovy. mark. 3/6. P. & P. on above 1/- each.

AUTO. TRANSFORMER, step up, step down, 110 v.-200-220-240 v. Fully shrouded, 300 watt type, 22/2 each. P. & P. 4/6. 500 watt type, 23/3 each. P. & P. 1/6. 1,000 watt type, 24/4 each. P. & P. 1/6.

200-250 v. A.C. MOTORS. New 180 h.p.m., 2 drives, direct 6,000 r.p.m., reduction 3,000 r.p.m. 22/6 each. P. & P. 2/6.

MORSE PRACTICE SET. Wooden base, upper, adjustable luzzers, battery clips and terminals, 8/6 each. P. & P. 2/-.

MORSE KEYS. 5-ampere Service unit, 2/6 each. P. & P. 1/-.

NEON LIGHT, 250 v. A.C. M.B.A. (Clear), 1/9 each. P. & P. 6d.

NEON PANEL MOUNTING INDICATOR LIGHTS, with flying leads, chrome bezel, 200-250 v. Rnd., clear and green, 3/9 each. P. & P. 6d.

ULTRA VIOLET BULB, A.C. D.C., 12 v. 36 watt, 5/6 each. P. & P. 6d.

RADIAL STUD SWITCH, 20 sizes, 1/2 in. sq. Complete with handle and housing, 5/- each. P. & P. 2/-.

CONTACTOR TIME SWITCH, two impulses per second. In sound-proof box, 11/6 each. P. & P. 3/-.

MURHEAD Verner Drive. Scaled 0/180 deg. ratio 21/1, drive shaft fitted to RF-22. Fully. Complete with handholder. In manufacturers' original packing, 8/6 each. P. & P. 1/6.

INFRA-RED TELESCOPE, complete with insert in Zamboni pile, image converter tube and full optical system. Brass box, complete with lens carrying case, 17/3 each. P. & P. 2/6.

HIGH-SPEED RELAY. Siemens, 2 bobins, 1,000 ohms each, 10/6 each. P. & P. 1/-.

WHEATSTONE BRIDGE UNIT. 4 start switches, 6-10, 10-100 ohms, 250-volts centre zero, P.S.D., 2 1/2 in. A. In rack carrying case 16 x 7 1/2 x 4 in. 40/- each. P. & P. 2/6.

MINIATURE 24 v. D.C. REVERSIBLE RECORDER MOTORS, fitted governor and right angle gear drive, 300 x 150 x 1 1/2 in. 12/6 each. P. & P. 2/-.

EVERSHED AND WIGMORES Circuit Testing Units. Meter, pattern "S", complete testing posts, instruction book, etc., two ranges 3 and 30 ohms, 14/7 6 each. P. & P. 2/6.

"SCOTCH BOY" 1,200 ft. plastic tape on plastic spool, 25/-, P. 1/6.

SIEMENS CONTACT COOLED RECTIFIERS. H.W. 125 v., 50 mA., 4/3. 250 v., 30 mA., 7/-, 250 v., 50 mA., 8/6. Bridge 250 v., 75 mA., 11/-, 250 v., 150 mA., 17/8. P. 1/6.

TOGGLE SWITCHES on off S.P., 1/9; change-over 2/6. D.P.S.T. 3/9. P. 1/6.

COLLARO Crystal Microphones, 37/6. P. & P. 1/-.

SERVICE TRADING CO.

Personal callers: 9 LITTLE NEWPORT STREET, LONDON, W.C.2.

All mail orders: Dept. P., 47 HIGH STREET, KINGSTON-ON-THAMES.

Build your own POCKET RADIO

ALL PARTS NECESSARY TO BUILD YOURSELF A COMPLETE 5-TRANSISTOR POCKET RADIO (Size less than 5 1/2" x 3 1/2" x 1 1/2") CAN BE SUPPLIED FOR AS LITTLE AS £9.18.2. (MEDIUM WAVE) or £10.6.8. (LONG AND MEDIUM WAVES). Send now for free price list and/or 3/- for instruction booklet.

- Components available include:
- Miniature 30 ohms. Loudspeaker 27/6.
 - Johnson O.O. Twin Gang with intersection screen ... 10/8.
 - Oscillator and I.F. Coils ... 8/-.
 - Output transformers matching single OC72 to 3 ohms ... 10/-.
 - Battery packs to give 9 volts from 1 1/2 slim-pen-light cells 5/-.
- (Also available to give 3, 6 or 12 volts.)
- Resistors ... from 4d.
 - Capacitors ... from 6d.
- Special Offer—Transistor Radio Batteries (1.5 v.) Size 1 1/2" x 1 3/16". 3d. each.

S. E. C. Ltd.,
9-11 Monmouth St., London, W.C.2.

An essential book for the connoisseur and enthusiast, for the engineer and dealer



Gen. Ed.: E. MOLLOY
Introduction by:
H. J. LEAK, M.Brit.I.R.E.

HIGH FIDELITY SOUND REPRODUCTION

Deals with the principles of electro-acoustics, including the forms of DISTORTION, room ACOUSTICS and STEREOPHONIC sound. Explains the units making up a complete high-fidelity installation: AMPLIFIERS and PRE-AMPLIFIER control units, dynamic LOUSPEAKERS, loudspeaker enclosures and the recently developed wide-range ELECTRO-STATIC LOUSPEAKERS. Also Record Reproduction, TAPE RECORDINGS, etc.

212 pages · only 20s. net
151 illustrations

FROM ALL BOOKSELLERS
... or in case of difficulty 21s. 3d. from
GEORGE NEWNES LTD., Tower House,
Southampton St., London, W.C.2.

ASTRAL RADIO PRODUCTS

- 'HOME RADIO,' 32-page illustrated booklet. Simple wiring instructions for Crystal Set, 1, 2, 3 Valves, 2/-, post 3d.
- TRIP COILS, Specified for 'Push-button 4', 'All Dry 3 Band, 3' 'Push-button 4', etc. 7/- pr. post 6d.
- Push-button Unit with modification data 1/6.
- DUAL WAVE HF Coil, Specified for 'Summer All Dry Portable', 'Modern 1 Valve', 'Modern 2 Valves', 'A.C. Double Triode 1', etc. 4/6, post 3d.
- IFT's Miniature, 1" x 1 1/2" x 2 1/2" in cans. Extra high 'Q'. Special offer, 9/- pr. post 6d.
- K COILS. 'A.C.' B pass 3, 3/3 each, post 3d.
- FRAME AERIALS. M.W., 5/-, post 4d.
- COIL PACKS. L.M.S., 30/-, post 1/6.
- Crystal Set Coils. L. & M.W., 2/6, post 3d.
- 82, Centurion Road, Brighton.

ILLUSTRATED CATALOGUE No. 11. 9d. POST FREE
(British Isles & H.M. Forces)

56 pages with 108 photographic illustrations on art paper. Over 2,000 new and guaranteed lines by the leading makers. No junk or ex-Govt. goods.


Special components for the short wave listener and amateur transmitter. VHF and transistor components. Special features for the service engineer and the constructor.

All orders dealt with by return.

SOUTHERN RADIO & ELECTRICAL SUPPLIES
SO-RAD WORKS
REDLYNCH, SALISBURY

Fidelia HAND BUILT

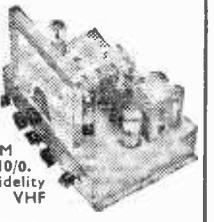Fidelia genuine hand built real high fidelity equipment for those people who desire the finest.



Major AM/FM 12 valves, £44.
De-Luxe AM/FM 11 valves, £34/10/0.
Imperial, high fidelity amplifier and VHF tuner, £34.
Full details willingly but 6d. in stamps is appreciated.

ELECTRO ACOUSTIC DEVELOPMENTS
2, Amhurst Road, Telscombe Cliffs, Sussex.

Practical Wireless BLUEPRINT SERVICE

PRACTICAL WIRELESS

No. of
Blueprint

CRYSTAL SETS

2/- each	
1937 Crystal Receiver ...	PW71*
The "Junior" Crystal Set	PW94*
2/6 each	
Dual - Wave "Crystal Diode"	PW95*

STRAIGHT SETS

Battery Operated

One-valve : 2/6 each	
The "Pyramid" One-valver (HF Pen) ...	PW93*
The Modern One-valver	PW96*
Two-valve : 2/6 each	
The Signet Two (D & LF)	PW76*
3/6 each	
Modern Two-valver (two band receiver) ...	PW98*
Three-valve : 2/6 each	
Summit Three (HF, Pen, D, Pen)	PW37*
The "Rapide" Straight 3 (D, 2 LF (RC & Trans))	PW82*
F. J. Camm's "Sprite" Three (HF, Pen, D, Tet)	PW87*
3/6 each	
The All-dry Three ...	PW97*
Four-valve : 2/6 each	
Fury Four Super (SG, SG, D, Pen)	PW34C*

Mains Operated

Two-valve : 2/6 each	
Selectone A.C. Radio-gram Two (D, Pow) ...	PW19*
Three-valve : 4/- each	
A.C. Band-Pass 3 ...	PW99*
Four-valve : 2/6 each	
A.C. Fury Four (SG, SG, D, Pen)	PW20*
A.C. Hall-Mark (HF, Pen, D, Push Pull) ...	PW45*

SUPERHETS

Battery Sets : 2/6 each	
F. J. Camm's 2-valve Superhet	PW52*
Mains Operated : 4/- each	
"Coronet" A.C.4 ...	PW100*
AC/DC "Coronet" Four	PW101*

No. of
Blueprint

SHORT-WAVE SETS

Battery Operated

One-valve : 2/6 each	
Simple S.W. One-valver	PW88*
Two-valve : 2/6 each	
Midget Short-wave Two (D, Pen)	PW38A*
Three-valve : 2/6 each	
Experimenter's Short-wave Three (SG, D, Pow)	PW30A*
The Prefect 3 (D, 2 LF (RC and Trans)) ...	PW63*
The Band-spread S.W. Three (HF, Pen, D (Pen), Pen)	PW68*

MISCELLANEOUS

2/6 each	
S.W. Converter-Adapter (1 valve)	PW48A*
The P.W. 3-speed Auto-gram (2 sheets), 8/-	
The P.W. Monophonic Electronic Organ (2 sheets), 8/-	

TELEVISION

The "Argus" (6in. C.R. Tube), 3/-	
The "Simplex"	3/6*
The P.T. Band III Converter	1/6*

All the following blueprints, as well as the PRACTICAL WIRELESS numbers below '94, are pre-war designs, kept in circulation for those amateurs who wish to utilise old components which they may have in their spares box. The majority of the components for these receivers are no longer stocked by retailers.

AMATEUR WIRELESS AND WIRELESS MAGAZINE STRAIGHT SETS

Battery Operated

One-valve : 2/6	
B.B.C. Special One-valver	AW387*

Mains Operated

Two-valve : 2/6 each	
Consoelectric Two (D, Pen), A.C.	AW403

SPECIAL NOTE

THESE blueprints are drawn full size. The issues containing descriptions of these sets are now out of print, but an asterisk denotes that constructional details are available, free with the blueprint.

The index letters which precede the Blueprint Number indicate the periodical in which the description appears. Thus P.W. refers to PRACTICAL WIRELESS, A.W. to Amateur Wireless, W.M. to Wireless Magazine.

Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to PRACTICAL WIRELESS, Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

No. of
Blueprint

SHORT-WAVE SETS

Battery Operated

One-valve : 2/6 each	
S.W. One-valver for American	AW429*
Two-valve : 2/6 each	
Ultra-short Battery Two (SG, det Pen)	WM402*
Four-valve : 3/6 each	
A.W. Short Wave World-beater (HF, Pen, D, RC, Trans)	AW436*
Standard Four-valver Short-waver (SG, D, LF, P)	WM383*

Mains Operated

Four-valve : 3/6	
Standard Four-valve A.C. Short-waver (SG, D, RC, Trans)	WM391*

MISCELLANEOUS

Enthusiast's Power Amplifier (10 Watts) (3/6)	WM387*
Listener's 5-watt A.C. Amplifier (3/6)	WM392*
De Luxe Concert A.C. Electrogram (2/6) ...	WM403*

QUERY COUPON

This coupon is available until May 6th, 1958, and must accompany all Queries sent in accord with the notice on our "Open to Discussion" page. PRACTICAL WIRELESS, MAY 1958


SPUTNIK-SPECIAL**SHORT-WAVE RECEIVER 10-60 MC/S (5-30 Metres) RECEPTION SET TYPE 208**

Complete with 6 valves, 2-6K8G, 2-EF39, 6Q7G and 6V6G. Internal mains power pack and 6 v. vibrator pack. Built-in 6 in. speaker. Muirhead slow-motion drive. B.F.O. and R.F. stage. I.F. freq. 2 Mc/s. Provision for phones and micing and 600 ohms. Dual input 100/250 v. A.C. and 6 v. D.C. All sets in new condition and air tested. £6.19.6. Carr. 15/6.

BE PREPARED TO LISTEN TO THE SATELLITES.

"EAVESDROPPER" THREE TRANSISTOR POCKET RADIO

(No Aerial or Earth required)
Variable tuning on medium waves. Total cost as specified, including Transistors, Transformers, Coils, Condensers and Battery, etc., with circuit and plastic case. All items sold separately. Full practical layout diagrams. 77/6 post free. With balanced armature earpiece. 81/- With Min. Hearing Aid, 90/-.

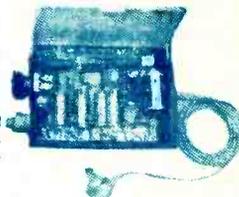**"HOMELIGHT" TWO TRANSISTOR PERSONAL PORTABLE**

Variable tuning. We can supply all components, including two Transistors, Diode-Resistors, Condensers and Miniature Hearing Aid and plastic case, size 4½ x 2½ x 1½ in. and 1½-volt battery for 52/6. Practical layout.

All items sold separately.

"TRANSISTOR-8"


Push-Pull Portable Superhet CAN BE BUILT FOR £11.10.
This Portable 8 Transistor Superhet is tunable for both Medium and Long Waves and is comparable in performance to any equivalent Commercial Transistor Set. Simplified construction enables this set to be built easily and quickly into an attractive lightweight cabinet supplied.

TEN STAR FEATURES

- ★ 8 Specially selected Transistors.
 - ★ 250 Milliwatts Output Push Pull.
 - ★ Medium and Long Waves.
 - ★ Internal Ferrite Rod Aerial.
 - ★ 7 x 4 Elliptical Speaker.
 - ★ Drilled Plastic Chassis 8½ x 2½ in.
 - ★ Point-to-Point Wiring and Practical Layout.
 - ★ Economical. Powered by 7½ v. battery.
 - ★ Highly sensitive.
 - ★ Attractive lightweight contemporary case.
- N.B.—Pair of XC101's supplied at additional cost of 40/-.
Call and hear demonstration model. Further details in the August issue of "Radio Constructor."

We can supply all these items including Cabinet for £11.10. All parts sold separately.

Send for circuit diagrams, assembly data, illustrations and instructions, and full shopping list FREE.

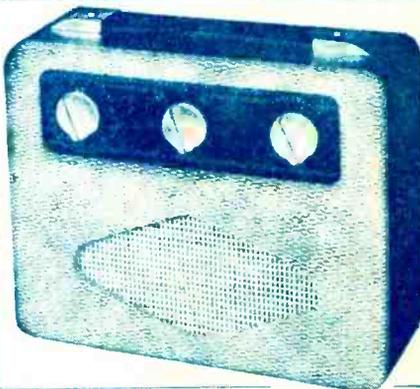**REPANCO MINI-7 POCKET TRANSISTOR RECEIVER**

We can supply all components for building this miniature receiver complete with plastic case. Send for full particulars.

TRANSISTOR SIGNAL TRACER


Complete Kit with 2 Transistors, components, phones, with circuit and plastic case. 42/6.

TRANSISTORS SQUARE WAVE GENERATOR

Complete Kit with 2 Transistors, components, circuit and plastic case. 25/-.

U.S.A. TESTMETER TYPE "934-S"**A.C./D.C. 15 RANGES**

Complete in wooden carrying case with leads and internal batteries. A.C./D.C. Volts 12/60/370/600 v. 1,200/6,000 v. Milliamps 1.2/12/60/600 m/a. Ohms 0-5000/5 meg. F.S.D. 1,000 o.p.v. £6.19.6

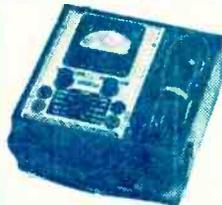**"373" MINIATURE 9.72 MC/S I.F. STRIP**

The ideal F.M. Conversion Unit as described in P.W. April/May 1957. Complete with 6 valves: 3-EF91, 2-EF92 and EB91. I.F.T.s., etc., in absolutely new condition. With circuit and conversion data.

12/6 (less valves). 42/6 (with valves)
Postage 2/6 on either type.

HENRY'S (RADIO) LTD.
5, HARROW ROAD, EDGWARE ROAD, PADDINGTON, LONDON, W.2.

Opposite Edgware Road Station
OPEN MONDAY to SAT. 9-6.

PADDINGTON 1008/9
THURS. 1 o'clock

TRANSISTORS**JUNCTION TYPE P-N-P. (British Manufacture.)**

Red-Spot, 800 Kc/s Audio Frequency ... 10/-
Blue-Spot, 1.6 Mc/s Mixer and Frequency Changer... 15/-
White-Spot, 2.5 Mc/s R.F. and I.F. Amp. ... 20/-

MINI-TWO TRANSISTOR MINIATURE POCKET RADIO

The smallest Transistor set offered on the market. Variable tuning. Drilled chassis, plastic case 3 x 2 x ½ in., Miniature Hearing Aid, 2 Transistors and all components including 12 volt battery, circuits and full practical layout diagrams. All components sold separately. Total cost 49/6 complete.



15 ranges
1,000 ohm
per volt

**TRIPLETT A.C./D.C. POCKET TEST-METER TYPE 666H**

In new condition with Prods and Internal battery.
A.C./D.C. 10/50/250/1,000/5,000 volts.

Milliamps 0-10/100/500.
Ohms 0-300/250,000 ohms.
£5.10.0

HUNDREDS OF BARGAINS AVAILABLE IN TRANSISTOR COMPONENTS, VALVES, ETC. SEND 6d. for 28-PAGE CATALOGUE.

718