

THE BEGINNERS' TEST METER

PRACTICAL 1/3 WIRELESS

JULY
1959



Contents

- A MIXER PRE-AMP UNIT
SERVICING RADIO RECEIVERS
- IMPROVING RECEIVER
SELECTIVITY
- A TWIN SPEAKER BASS
REFLEX CABINET
- EXPERIMENTAL PRINTED
CIRCUIT AMPLIFIER

U.S.A. HIGH-FIDELITY COAXIAL SPEAKERS

Recognised as the finest Hi-Fi speakers produced today! Imported by us from U.S.A. to bring you the best quality at the lowest prices ever!



15" Coaxial Speaker

The woofer uses 6.8 oz. Alnico 5 magnet. Has 5in. tweeter and an electronic crossover network to separate the speaker functions. Frequency response: 40-17,000 cycles, output 15 watts, input to system 8 ohms. Sturdy frame.
ONLY 160/- P. & P. 4/-

12" Coaxial Speaker

This American-made speaker is ideal for low cost improvement of your Radio, T.V. or gramophone. Woofer uses 6.8 oz. of Alnico 5. Includes 8in. tweeter and crossover network. Handles 12 watts. Impedance 8 ohms.
ONLY 120/- P. & P. 4/-

8" Coaxial Speaker

A pleasant surprise is in store for you when you hear this speaker with 2 1/2in. tweeter, 8in. woofer with 3.16 oz. Alnico 5, and built-in crossover network. Handles 8-10 watts. Impedance 8 ohms. Are you price conscious?
ONLY 90/- P. & P. 4/-

U.S.A. DYNAMOTORS manufactured by EICOR.



as above, output 250 v. at 100 mA., size 5 1/2 in. x 3 1/2 in. x 3 1/2 in.

VIBRATOR PACKS. 12 volt input, 300 volts output at 150 mA. Fully smoothed. **ONLY 25/-, carr. 7/6.** Also 6 v. input, 230 v. output at 100 mA. Fully smoothed. **25/- each, P. & P. 3/6.**

PYE 10in. HIGH QUALITY SPEAKER. Supplied in magnificent cabinet complete with 30ft. of lead and plug. Ideal for Hi-Fi and Stereo. Brand New in original packing. **45/- each, carriage 5/-**

AERIAL VARIOMETERS. These magnificent instruments will enable you to receive maximum signal strength on all S.W. receivers. Precision calibrated control. Complete with connection details. **12/6. P. & P. 2/6.**

HEADPHONES - BRAND NEW. American chamois padded, moving coil, 100 ohms, 25-ohm dynamic D.L.R.5. 8/6. Low resistance 120 ohms. **6/6. P. & P. 1/6** on each.

WALKI/TALKIE SET. Consisting of transmitter covering 7-9 Mc/s, range up to 10 miles, complete with 5 valves, headphones, microphone, junction box, aerial and circuit. **ONLY 60/- each, P. & P. 4/-.** Two for **£6.** Post Free.


H.R.O. SENIOR RECEIVERS. 50 kc/s-30 Mc/s. Complete with all valves, 4 frequency coil sets, "S" meter, crystal gate, matched mains, power pack. Fully independent and supplied ready for immediate operation. **ONLY £16.19.6, Carr. 20/6.**

PORTABLE 6 V. ACCUMULATORS. Brand new fully portable 6v. 40 A.H. accumulator's complete in steel carrying case with handle and output terminal. Size 10in. high by 9in. wide by 5in. deep. **ONLY 45/-, Carr. 7/6.**

U.S.A. W.P. AERIALS. 12ft., 12/6. P. & P. 2/6.

COMPLETE HEADPHONE & MICROPHONE ASSEMBLY. A must for every Constructor and "Ham," consists of moving coil, padded headphones and microphone. **press to talk microphone. 10/-, P. & P. 3/6.**

WIRELESS SET NO. 19 MK. II

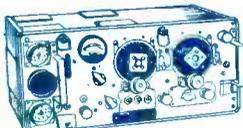

Incorporates "A" Set - TNRX covering 2-8 Mc/s (37.5-150 metres). "B" Set - VHF TX/RX covering 230-240 Mc/s (1.2-1.3 metres) and intercom. amplifier. Complete with 15 valves, 500 microamp check and tuning meter, circuit and instruction book. (American manufacture.) In magnificent condition. **60/-, Carr. 10/-.**

GEIGER COUNTERS

Designed to detect and measure variations in gamma-ray intensity. I.E. emissions of radio active potassium, minute traces of uranium and thorium, etc., in ordinary soil and rock. The readings being measured on a 50 microamp meter, working battery life is approx. 2,000 hours. Instrument housed in tough plastic case, hermetically sealed. All components I.S.C. Tech. C. approved. Size 8 1/2 x 8 x 3 1/2 in., weight 6 1/2 lbs. Supplied with canvas carrying case. Fully guaranteed. **£7.10.0. P. & P. 7/6.**



WALKI/TALKIE INTERCOM



Boys! They're terrific! Two "space styled" hand telephone units in beautiful two-tone finish. No batteries or soldering required, simply connect twin wire between the two units and talk into microphone or listen on one and listen to speaker or talk on the other. Ideal for intercom from house to house, room to room, tent to tent, etc., operates anywhere even up to 200 yards. Brand New! Complete with 25ft. of wire. **ONLY 6/6 Per Set. P. & P. 1/-.**

PORTABLE TRANS/RECEIVER No. 18

A self-contained Trans/Receiver for Telephone and C.W. Range approx 10 miles. Freq.: 6-9 Mc/s (50-33.3 metres). Valve line-up: 3 ARF-12, 2 AR-8, 1 ATP4. Complete with aerial, H.T. and L.T. meter. Weight 20 lbs. Size 8 x 10 x 1 7/8 in. **ONLY 60/-, Carr. 10/-**



AMERICAN LIGHT-WEIGHT HEADSET



They're High and Low Impedance! These H.S.30 phones are the finest used by the U.S. Air Force. 250Ω imp. using soft rubber miniature ear moulds for maximum music and voice reproduction of the finest quality. Supplied free is a small transformer unit with cord and plug which steps impedance up to 4,000Ω. **ONLY 15/- P. & P. 2/6.**

CONTROL BOX - B.C. 602.



Complete push-button control box. 4 position and on/off. 21 break with dual coloured indicators for instant channel check. In black crackle case 5 1/2 in. x 3 1/2 in. x 1 1/2 in. Bargain price. **5/- each, P. & P. 1/6.** Two for **8/-, P. & P. 2/6.**

BARGAIN OFFER. Relay package containing one 6.12 and 24 volt stepping relay giving 4 two miniature 12 and 24 volt coils with one make position, one 12 and 24 volt heavy duty relay with 2 make and break and 1 break positions, one miniature gate switch double pole press to make 1 amp. 250 volts. Made by leading American manufacturers, all for **only 8/-, P. & P. 2/-.**

TELEPHONE HANDSET. Brand new. **12/6. P. & P. 1/-.**

RECTIFIER BARGAINS. Mains (doubler) 300 volts per section at 120 mA., 5/- each. P. & P. 1/6. Two (full wave) for 8/-, P. & P. 2/-.

PICTURE FRAME AERIAL. Incorporates MW and LW aerial with provision for tuning out unwanted signals, noise, etc. Size 8 1/2 x 1 1/2 x 1 1/2 in. Magnificent appearance. Brand new with full instructions. **12/6. P. & P. 2/6.**

WESTINGHOUSE .150 PENCIL RECTIFIERS. 500 v. 5 mA., 3/6. P. & P. 1/-.

SOLDERING IRON. Instrument type 230 to 250 volt A.C. 25 w. with neon indicator. **ONLY 16/6. P. & P. 1/6.**

MICROPHONES - BRAND NEW. Throat magnetic, 4/6; No. 8 carbon with switch, 6/6; No. 7 moving coil, 8/6.

HOOVER ROTARY TRANSFORMERS. 12 v. input. 500 v. output at 65 mA., or 6 v. input. 250 v. output at 75 mA. **ONLY 10/6 each, P. & P. 2/6.**

TRANSFORMER B.C. 625. Covers 100-156 Mc/s, will deliver 15 watts, consists of seven valves (2-832). 3 for modulation, 4 for R.F. Complete with operating details and circuits. **ONLY 25/-, P. & P. 5/-.**

ACCUMULATORS. 2 volts 16 A.H. (unspliable). Ideal for 6 and 12 volts supply, etc. Brand new. Original cartons. Size 4 in. x 7 1/2 in. x 2 1/2 in., 5/6 each. P. & P. 1/6. 3 for 15/-, P. & P. 3/6. 6 for 27/6. P. & P. 5/6.



Callers: 87, TOTTENHAM CT. RD., LONDON, W.1.
Mail orders: (DEPT. P), 32a, COPTIC STREET, LONDON, W.C.1.
Telephone: MUSeum 9607.

WOT! You don't own a Relda catalogue! It's terrific and fully illus. Only 1/3.

THE BEST VALUE ON THE MARKET

Stern's "fidelity" TAPE RECORDER

DIRECT—MANUFACTURER to USER

NO "MIDDLEMAN'S" DISCOUNT IS INCLUDED IN OUR PRICES.


IT INCORPORATES

- The latest COLLARO TRANSCRIPTOR TAPE DECK.
- The model HF/TR3 "fidelity" AMPLIFIER. (Described below).
- Matching elliptical 7in. x 4in. P.M. Speaker.
- 1,200 reef HIGH QUALITY EMITAPE.
- ACOS Crystal Microphone.

BEFORE CHOOSING YOUR TAPE RECORDER YOU SHOULD HEAR THIS MODEL—TRULY "HI-FI" RECORDINGS ARE OBTAINABLE and it is comparable to much higher-priced Recorders.

Alternately send S.A.E. for ILLUSTRATED LEAFLET.

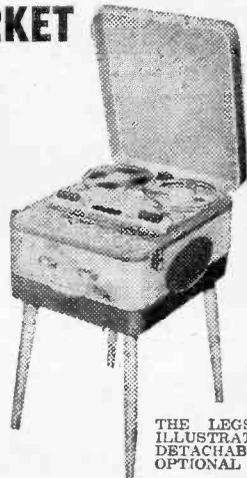(Plus £1.10.0 Carriage and Insurance, of which £1 is refunded on return of Packing Case.)



PRICE
£49.10.0

Terms: Dep. £9.18.0 and 12 monthly payments of £3.12.7 or Dep. £16.10.0 and 12 monthly payments of £3.0.6.

THE LEGS SHOWN IN THE ILLUSTRATION ARE READILY DETACHABLE, AND ARE AN OPTIONAL EXTRA AT £12.6.


THE MODEL HF/TR3 TAPE AMPLIFIER

INCORPORATING

3-SPEED TREBLE EQUALISATION by means of the latest FERROXCUBE POT CORE INDUCTOR.

PRICE FOR COMPLETE KIT OF PARTS **£12.15.0**

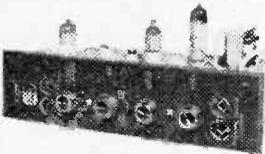PRICE FULLY ASSEMBLED & TESTED **£16.10.0**



HIRE PURCHASE. Deposit £3.6.0 and 12 monthly payments of £1.4.2. A very high-quality Amplifier based on the very successful TYPE "A" design completed in the MULLARD LABORATORIES. ONLY NEW HIGH-GRADE COMPONENTS are incorporated including MULLARD VALVES and a GILSON OUTPUT TRANSFORMER—other features are—Magic Eye Recording hand indicator—Effective Tone Control—Monitoring and Extension Speaker Sockets—Has own Power Supply and can be used as independent Amplifier for direct reproduction of Gram Records or from Radio Tuner. Overall size 11in. x 6in. x 4in. Can be supplied for use with Truvox—Collaro—Lane—Brenell or Mot'k Decks. Please specify which.

Send S.A.E. For leaflet or 2/6 for the complete Assembly Manual.

STERN'S—MULLARD TYPE "C" TAPE PRE-AMPLIFIER-ERASE UNIT

INCORPORATING THE NEW FERROXCUBE POT CORE PUSH-PULL OSCILLATOR and 3-SPEED TREBLE EQUALISATION by means of the latest FERROXCUBE POT CORE INDUCTOR.

PRICES... INCLUDING SEPARATE SMALL POWER SUPPLY

COMPLETE KIT OF PARTS **£14.0.0**

ASSEMBLED AND TESTED **£17.0.0**

Deposit £3.8.0 and 12 months of £1.4.11.



ALSO AVAILABLE EXCLUDING POWER SUPPLY UNIT FOR £11.15.0 and £14.10.0 respectively. (Carriage and Insurance is 5/- extra.)

WHEN ORDERING PLEASE STATE MAKE OF TAPE DECK TO BE USED. We present this "HI-FI" Pre-amplifier strictly to Mullard's specification incorporating ONLY NEW HIGH-GRADE COMPONENTS and the SPECIFIED NEW MULLARD VALVES. It comprises a COMPLETELY SELF-CONTAINED UNIT, all components and valves being contained in a well-ventilated Box-Chassis neatly finished in Hammered Gold with a very attractively engraved PERSPEX FRONT PANEL.



HOME CONSTRUCTORS

YOU CAN BUILD THIS PORTABLE TAPE RECORDER from £39.15.0

TO ADD FULL TAPE RECORDING FACILITIES

WE OFFER YOU THIS SELECTION

- (a) THE PORTABLE CASE illustrated here **£5.0.0**. 1,200ft. E.M.I. TAPE (£1.15.0). ACOS CRYSTAL MIKE (£1.15.0). ROLA 10in. x 6in. LOUD-SPEAKER (£1.10.0). ALL FOR **£9.0.0**

AVAILABLE ON HIRE PURCHASE WITH (b) or (d) below.
(b) THE COLLARO MK. IV TAPE DECK (£25.0.0) and the HF TR3 AMPLIFIER Assembled and Tested. FOR **£34.10.0**

H.P. Deposit £6.18.0 and 12 months of £2.10.8.
(c) As in (b) above, but HF/TR3 supplied as COMPLETE KIT OF PARTS. **£30.15.0**

(d) THE MK IV TRUVOX TAPE DECK WITH the assembled and tested HF/TR3 AMPLIFIER H.P. Deposit **£8.6.0** and 12 months **£3.0.10**

(e) As in (d) above but the HF/TR3 supplied as COMPLETE KIT OF PARTS. **£38.0.0**

(Carriage and Insurance on above quotes 10/- extra.)
NOTE: Messrs. Collaro when supplying the MK. IV Deck do not wire up the Deck Switches. We will do this at charge of £1.0.0. or supply a Wiring Diagram to the Home Constructor.

Please send S.A.E. with all correspondence.

To any modern "HI-FI" AUDIO AMPLIFIER (such as our Mullard 5-10" and 2" valve Pre-amplifier) ALL YOU NEED IS "THE TYPE "C" PRE-AMPLIFIER and a TAPE DECK... WE OFFER—

(a) THE COLLARO MK. IV TAPE DECK and the MULLARD TYPE "C" PRE-AMPLIFIER with Power Unit **£35.0.0** Assembled and Tested
H.P. Deposit £7.0.0 and 12 months of £2.11.4.

(b) As in (a) above but the Type "C" supplied as COMPLETE KIT OF PARTS. **£32.0.0**

(c) THE TRUVOX MK. IV TAPE DECK with the assembled and tested TYPE "C" PRE-AMPLIFIER and POWER UNIT **£42.10.0** H.P. Deposit **£8.10.0**. 12 months **£3.2.4**.

(d) As above but the TYPE "C" UNIT supplied as COMPLETE KIT OF PARTS. **£39.10.0**

(Carriage and Insurance on above quotes 10/- extra.)

STERN RADIO LTD.
109 & 115 FLEET ST., LONDON, E.C.4
Telephone: FLEET STREET 5812/3/4

**AMPLIFIERS
PRE-AMPLIFIERS
FOR THE "HI-FI" ENTHUSIAST**

**MULLARD DESIGNS FOR
THE
HOME CONSTRUCTOR**

MODEL 510/M

**THE VERY
POPULAR
MULLARD
"5-10" MAIN
AMPLIFIER**




**MULLARD'S
NEW 2-STAGE
PRE-AMPLIFIER
TONE CONTROL**



MODEL 3-3/M

**THE NEW
MULLARD 3-3
MAIN
AMPLIFIER**

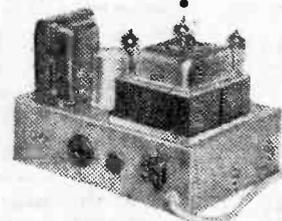


Please enclose S.A.E. if ILLUSTRATED and DESCRIPTIVE LEAFLETS are required; the ASSEMBLY MANUALS, containing Practical Drawings, etc., are available at 1/6 each.

SPECIAL PRICE REDUCTIONS . . .

- (a) The COMPLETE KIT OF PARTS to build both the "3-3" MAIN AMPLIFIER and the 2-STAGE PRE-AMPLIFIER-CONTROL UNIT **£12.10.0**
 - (b) The COMPLETE KIT OF PARTS to build the "5-10" MAIN AMPLIFIER and the 2-STAGE PRE-AMPLIFIER-CONTROL UNIT **£15.15.0**
- PRICES FOR THE "5-10" ARE SUBJECT TO £1.5.0 EXTRA IF THE PARTRIDGE TRANSFORMER IS REQUIRED.


MODEL 510/R

**THE NEW
COMPLETE
MULLARD 5-10
AMPLIFIER**

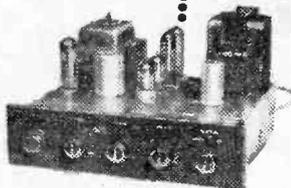

MODEL 3-3/R

**THE NEW
COMPLETE
MULLARD 3-3**

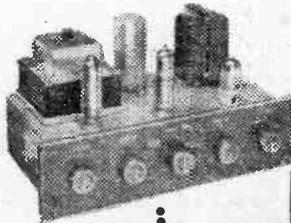

Undoubtedly the most successful amplifier yet designed, and used in conjunction with the new Mullard Pre-amplifier, an undistorted power output of up to 10 watts is obtained. Thoroughly recommended to the "Hi-Fi" enthusiast who contemplates a very high quality home installation. In addition the versatility of the equipment makes it quite suitable for use in small halls, etc. We supply complete to MULLARD'S Specification with specified valves and components and including the latest PARMEKO Ultra-linear Output Transformer and the PARMEKO Mains Transformer which has power available to drive Radio Tuning Unit.

COMPLETE KIT **£10.0.0** Alternatively we supply ASSEMBLED & TESTED **£11.10.0** OF PARTS (Carriage & Insurance 5/- extra.)

THIS "5-10" with the latest PARTRIDGE £1.6.0 extra ULTRA-LINEAR OUTPUT TRANSFORMER for

A completely new design employing two EFB8 valves, and in particular designed to operate with the Mullard range of Power Amplifiers, but also perfectly suitable for other makes, etc. Briefly it incorporates:

- Equalisation for the latest R.I.A.A. characteristics.
- Input for variable reluctance. ● Magnetic Pickups.
- Input for Crystal Pickups. ● Input for Tape replay.

- (a) Direct from High Impedance Tape Head.
- (b) From a Tape Amplifier or Pre-amplifier.
- Sensitive Microphone Channel.
- Wide range Bass and TREBLE Controls.
- Attractive Perspex front control panel.
- Our Kit is strictly to MULLARD'S SPECIFICATION.

COMPLETE KIT OF **£6.6.0** Alternatively we supply ASSEMBLED & TESTED **£8.0.0** PARTS (Carriage & Insurance 5/- extra.)

Based entirely on the present very popular "3-3" model and designed to operate in conjunction with the new 2-stage PRE-AMPLIFIER (shown left) thus providing all the facilities associated with the more expensive "Hi-Fi" equipment. We recommend it as the IDEAL HOME INSTALLATION where very high quality is desired at the lower volume level (up to 3 watts). We supply complete to MULLARD'S SPECIFICATION including the latest PARMEKO Output Transformer, specified Valves and Components. Has power available to drive a Radio Tuning Unit.

COMPLETE KIT OF **£7.0.0** Alternatively we supply ASSEMBLED & TESTED **£8.0.0** PARTS (Carriage & Insurance 5/- extra.)

- Only NEW HIGH GRADE Components
- and MULLARD VALVES are supplied
- with these KITS.

(a) The "3-3" and the 2-STAGE PRE-AMPLIFIER **£15.0.0** both ASSEMBLED and TESTED

H.P. : DEPOSIT £3.0.0 and 12 Monthly Payments of £1.2.0.

(b) The "5-10" and the 2-STAGE PRE-AMPLIFIER both ASSEMBLED and TESTED **£18.18.0**

H.P. : DEPOSIT £3.16.0 and 12 Monthly Payments of £1.7.8. When ordering include an extra 7/6 to cover Carriage and Insurance

Designed for a simple domestic installation with Genuine High Quality reproduction up to a maximum of 10 watts. Separate BASS and TREBLE Controls are incorporated with switched inputs for 78 and L.P. Records plus Radio Tuning Unit. We incorporate SPECIFIED COMPONENTS and NEW MULLARD VALVES. We also give the purchaser the choice of two of the best ULTRA-LINEAR OUTPUT TRANSFORMERS made—first the latest by PARMEKO, LTD., and also the latest by PARTRIDGE (£1.6.0 extra). We also supply the PARMEKO MAINS TRANSFORMER, and this has extra power available to supply a Radio Tuning Unit. The Control Unit can easily be detached from the Amplifier Chassis for use in a remote position. COMPLETE KIT OF PARTS **£11.10.0** Alternatively we supply ASSEMBLED and TESTED **£13.10.0** (PARMEKO Transformer)

H.P. Terms : Dep. £2.14.0 and 12 Monthly Payments of 19/10. Send S.A.E. for ILLUSTRATED LEAFLET or 1/6 for the ASSEMBLY MANUAL.

THE IDEAL AMPLIFIER FOR A SMALL HIGH QUALITY INSTALLATION

COMPLETE KIT **£7.10.0** Alternatively supplied ASSEMBLED OF PARTS and FULLY TESTED **£8.19.6** (plus 6/6 coverage and insurance)

H.P. Terms : Dep. £2.0.0 and 8 Months of £1.0.0. Developed from the very popular 3-valve 3-watt Amplifier designed in the Mullard Laboratories. Our Kit is complete to MULLARD'S SPECIFICATION including supply of specified components, Mullard valves and a PARMEKO OUTPUT TRANSFORMER. Send S.A.E. for leaflet or 1/6 for ASSEMBLY MANUAL.

STERN RADIO LTD.

"MODERNISE YOUR OLD RADIOGRAM"

IT IS CHEAPER AND BETTER VALUE TO REPLACE YOUR OLD CHASSIS AND GRAM UNIT

!! RADIOGRAM CHASSIS !!

ARMSTRONG "STEREO TWELVE" £37.6.0

The most complete unit yet produced for Stereo, giving 6 watts high-fidelity push-pull output on each channel, 12 watts for monaural. Full VHF band, medium and long wavebands. Stereo and monaural inputs or records, tape and radio, and a tape output for stereo and monaural tape recording. Comprehensive matching for all types of crystal pick-ups. The perfect basis for a complete monaural reproducing system or for a complete stereophonic system now or later.

ARMSTRONG "JUBILEE" £29.8.0

An AM/FM chassis with nine valves and two diodes and with push-pull output stage providing 6 watts. Full VHF, medium and long wavebands with automatic frequency control on FM and ferrite aerial on AM. Tape record and playback facilities. Can be adapted for stereo at any time by the addition of our compact, easy-to-fit converter amplifier.

ARMSTRONG "STEREO 44" £28.7.0

Provision is made for Stereo and monaural playback from pick-up or tape. Outputs provided for Stereo or Monaural tape recordings. Alternative inputs enable the use of most crystal pick-ups, together with tape recorders or tape pre-amplifiers (such as our type "C" unit). 8 Watts output. Radio covers med. waveband and the complete VHF/FM transmissions 87-108 Mc/s.

DULCI "HAPP" £27.16.6

An eight-valve AM/FM 4 waveband chassis giving 6 watts ultra linear output. Covers short, long, medium wavebands plus the VHF/FM band and has internal aerial on the medium and long wavebands. Tape outlet incorporated and suitable for 3 to 15 ohm loudspeakers.

DULCI "H3" £19.17.6

A 6-valve AM/FM chassis giving 4 watts output. Covers medium and long wavebands, on which an internal aerial operates, plus the VHF/FM band. Full AVC on all wavebands and Tape outlet incorporated.

AM/FM RADIO TUNING UNITS

Containing our Power Supply Units.

ARMSTRONG "S.T.3" £27.6.0

A self-powered high-fidelity tuner covering full VHF, medium, and long wavebands with automatic frequency control on VHF.

DULCI "H4/T" £23.15.8

A 4 waveband self-powered high-fidelity tuner covering the VHF/FM transmissions plus the long, medium and short wavebands. **NEW HIRE PURCHASE TERMS** are available on all above. Illustrated leaflets available—send S.A.E.

STERN'S FOR STEREO OUR POPULAR MULLARD MAIN AMPLIFIERS ARE RECOMMENDED FOR USE WITH THE DULCI STEREO PRE-AMPLIFIERS

WE OFFER PRE-AMPLIFIER and AMPLIFIER AT SPECIALLY REDUCED PRICES

Send S.A.E. for full details.

A SPECIAL CASH ONLY OFFER !!

This very attractive **PORTABLE AMPLIFIER CASE** together with a good quality **GRAM AMPLIFIER** and a matched **P.M. SPEAKER**.


ALL for ONLY **£8.7.6** (Plus 7/6 Carr. & Ins.)

The Amplifier consists of a 2-stage design incorporating 3 modern B.V.A. valves and has separate **BASS** and **TREBLE CONTROLS**. The Portable Case will also accommodate almost any make of Autochanger and is attractively finished in Maroon and Grey Rexine.

WE ALSO SUPPLY SEPARATELY—
(a) The 2-stage (plus Rectifier) **AMPLIFIER £4.2.6**

(b) The **PORTABLE CARRYING CASE £3.17.6**

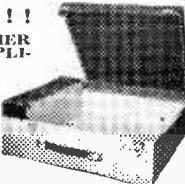(c) **P.M. SPEAKER 18/9** Carriage and Insurance 4/- extra.



STERN'S 12 VOLT CAR RADIO

Incorporating **PRINTED CIRCUIT** and **POWER TRANSISTOR**

A versatile design covering both **LONG** and **MEDIUM WAVEBANDS**, incorporating **Transistor Output**, thus having **operated direct off 12 volt Car Battery**

We offer it on the **UNIT ASSEMBLY BASIS**, consisting of **THREE SEPARATE FULLY WIRED, ALIGNED and TESTED UNITS**, plus the complete **loudspeaker assembly**. All for **£15.0.0**

Only 12 solder joints are required to finish the complete receiver. Send 1/6 for Manual containing complete data.



!! RECORD PLAYERS !!

THE LATEST MODELS ARE IN STOCK

MANY AT REDUCED PRICES!!!
SEND S.A.E. FOR ILLUSTRATED LEAFLET
A FEW CASH BARGAINS

B.S.R. MONARCH
UA8 4-speed mixer
Autochanger with
Crystal Pick-up



£6.12.6

The **COLLARO "CONQUEST" 4-speed Autochanger, Studio Pick-up £7.10.0**

The latest **COLLARO "CONTINENTAL" 4-speed MIXER Autochanger, Studio "O" Pick-up £8.10.0**

The **COLLARO 4-speed Single Record Player, Studio Pick-up £6.6.0**

THE NEW B.S.R. Model UA12 is in Stock. A 4" "SPEED" MIXER AUTOCHANGER £8.7.6

UA12 also available incorporating the B.S.R. STEREO Pick-up, plays L.P. and 78 Records £10.10.0

B.S.R. MODEL TU9 4-speed Single Record Player, complete with separate Crystal Pick-up £4.5.0

(This high output Pick-up is available separately for £1/12/8.) Carriage and Insurance on each above 5/- extra.

HIGH-FIDELITY UNITS ARE ALSO IN STOCK

as follows:
GARRARD MODEL 301 . . . 4HF . . . TA/Mk11 . . . RC98 . . . RC121/4 . . . T.P.A.12 PICK-UP . . . etc

Send S.A.E. For Leaflet.

NEW HIRE PURCHASE TERMS ARE AVAILABLE ON ALL EQUIPMENT VALUE £9.0.0 AND OVER.

SPECIAL CASH ONLY BARGAIN

A bulk purchase enables us to offer this very useful

INTERCOM SET OR BABY ALARM for only **£5.5.0.**



Consists of **MASTER UNIT** (Illustrated) and one **EXTENSION** providing **2-way TALKING** facility. Complete in polished wood cases, size of each only **7 1/4 x 4 1/2 x 6 in.** high.

STERN'S MK. II fidelity F.M. TUNING UNIT PRICE

(Plus 5/- Carr. **£14.5.0**

and Ins.)

HIRE PURCHASE: Deposit **£2.0.0** and 12 Monthly Payments of **£1.0.9.**

Incorporates the latest **MULLARD PERMEABILITY TUNING HEART** and the corresponding **MULLARD VALVE LINE-UP** comprising **EC85, 2 type EF85s (or EF89s) EM84 Tuning Indicator, plus 2 type O.A.79s Germanium Diodes.** A really first-class Tuner, very attractively presented and comparable to many offered at much higher prices. Power consumption is only 1.5 amps at 6.3 volts and 25 mA at 250 volts.

HOME CONSTRUCTORS! YOU CAN BUILD THIS TUNING UNIT FOR ONLY £10.10.0 (Plus 5/- Carr. & Ins.) Please send S.A.E. for fully descriptive leaflet, or the Assembly Manual is available for 1/6.

HOME CONSTRUCTORS

A RANGE OF "EASY TO ASSEMBLE" **PREFABRICATED CABINETS**

Designed by the W.B. "STENTORIAN" COMPANY for "H-FI" Loudspeaker systems or to accommodate high-quality equipment. The acoustically designed **Bass Reflex Cabinets** containing the very successful "Stentorian" Speakers give really first-class reproduction and are well recommended. Models are also available to accommodate high-quality



Amplifiers, Pre-amplifiers, Tuning Units, Record Players; etc. All models are very easily assembled, in fact, only a screwdriver is required. Fully illustrated leaflets are available, including complete specifications of the various **STENTORIAN LOUDSPEAKERS. PLEASE ENCLOSE S.A.E. WITH ALL CORRESPONDENCE.**

109 & 115 FLEET ST., LONDON, E.C.4
Telephone: **FLEET STREET 5812/3/4**

BENTLEY ACUSTIC CORPORATION LTD.

THE VALVE SPECIALISTS. 38 CHALCOT ROAD, LONDON, N.W.1. Telephone: PRIMROSE 9090.

EXPRESS SERVICE! C.O.D. ORDERS RECEIVED BY 3.30 P.M., EITHER BY LETTER, PHONE OR WIRE, DESPATCHED THE SAME AFTERNOON, ALL ORDERS RECEIVED BY FIRST POST DESPATCHED SAME DAY.

ANY ORDER UP TO £10 INSURED AGAINST DAMAGE IN TRANSIT FOR ONLY 6d. EXTRA. ORDERS OVER £10 INSURED FREE.


0B2	17/6	6C5G	6/6	6U7G	8/6	18	23/3	5763	12/6	DK96	10/-	EF91	7/6	KTW61	8/-	PY80	8/-	UBL21	23/3
0Z4	6/-	6C6	6/6	6V6G	7/-	19AQ5	11/-	7193	5/-	DL33	9/6	EF92	5/6	KTW62	8/-	PY81	9/-	UCC84	19/11
1A3	3/-	6C8	12/6	6V6GTG	8/-	19BHG6G	23/3	7475	7/6	DL66	15/-	EK32	8/6	KTW63	8/-	PY82	9/-	UCC85	10/6
1A5	6/-	6C9	12/6	6X4	7/-	19H1	10/-	9002	5/6	DL68	15/-	EL32	5/6	KTZ41	8/-	PY83	9/6	UCF80	21/11
1A7GT21	11/6	6C10	12/6	6X5GT	6/6	20D1	15/3	9006	6/-	DL92	7/6	EL33	12/6	KTZ63	10/6	PZ30	19/11	UCH21	23/3
1C5	12/6	6CD6G	6/30L2	10/-	20F2	26/6	AC/PEN			DL94	7/6	EL34	17/6	L63	6/-	QP21	7/-	UCH42	9/6
1D6	10/6		29/10	7A7	12/6	20L1	26/6	(5 or 7 pin)		DL96	10/-	EL38	26/6	LN152	12/6	QP25	15/-	UCH81	11/6
1H5GT	11/6	6CH6	12/6	7B6	19/3	20P1	26/6		23/3	DL510	10/6	EL41	11/-	LZ319	9/-	QS150/15		UCL82	15/6
1L4	6/6	6D3	19/11	7B7	8/6	20P3	23/3	AC2PEN		DM70	8/6	EL42	11/6	MH4	7/-			UCL83	24/7
1LD5	5/-	6D6	6/6	7C5	8/6	20P4	26/6		23/3	EA50	2/-	EL81	15/-	MHL4	7/6	R12	10/6	UF41	9/6
1LN5	5/-	6E5	12/6	7C6	8/6	20P5	23/3	AC2PEN		EA76	9/6	EL84	10/6	MHL6	12/6	R18	17/6	UF42	18/7
1NSGT	11/6	6F1	26/6	7D5	23/3	25A6G	19/3	DD	26/6	EABC80	9/-	EL91	5/-	ML4	12/6	R19	19/11	UF80	10/6
1R5	7/6	6F6G	7/-	7H7	8/6	25L6GT	10/-	AC4PEN		EAC91	7/6	EL95	10/6	ML6	6/6	SD6	12/-	UF85	10/6
1S4	9/6	6F6GTG	8/-	7R7	12/6	25Y5	10/6		26/6	EAF42	10/6	EM34	10/6	MPT4	(5 or	SPA(7)	15/-	UF86	23/3
1S5	7/6	6F8	12/6	7S7	10/6	25Y5G	10/-	AC5PEN		EB34	2/6	EM71	23/3	7 pin	23/3	SP41	3/6	UF89	10/6
1T4	6/6	6F11	17/3	7V7	8/6	25Z5	10/6		23/3	EB41	8/6	EM80	10/6	MU14	10/6	SP42	12/6	UL41	10/6
1U5	10/6	6F12	7/6	7Y4	8/6	25Z4G	10/-	AC6PEN	7/6	EB91	6/6	EM81	10/6	MX40	26/6	SP61	3/6	UL44	26/6
2A7	10/6	6F13	12/6	8D2	3/6	25Z6G	10/-	AC/HL		EBC33	7/6	EN31	37/3	N37	19/11	SU25	26/6	UL46	15/6
2C26	4/-	6F14	26/6	8D3	7/6	25Z6GT	17/6	DDD	15/-	EBC41	10/-	EY51	10/6	N78	19/11	SU61	10/6	UL94	11/6
2D13C	7/6	6F15	15/3	9D2	4/-	27S U	19/11	AC/P4	8/-	EBC81	13/11	EY83	16/7	N108	18/7	T41	23/3	UM4	17/3
2P	26/6	6F16	9/6	9B6W	15/3	28D7	7/-	AC/TP	33/2	EBF80	10/-	EY86	14/6	N308	20/7	TDD4	24/7	URIC	16/7
2X2	4/6	6F17	12/6	10C1	15/-	30C1	9/-	AC/VP1	15/-	EBF89	9/6	EZ35	6/6	N329	26/6	TH4B	26/6	UO6	19/11
3A4	7/-	6F30	10/6	10C2	26/6	30F5	8/-	AC/VP2	23/3	EBL21	23/3	EZ40	8/-	OA70	5/-	TH41	26/6	UUB	26/6
3A5	12/6	6F33	7/6	10D2	12/-	30FL1	10/-	ATP4	5/-	EBL31	23/3	EZ41	10/-	OA71/81	6/-	TH333	33/2	UVIN	16/7
3B7	12/6	6G6	6/6	10F1	19/6	30L1	9/-	AZ1	16/7	ECS2	5/6	EZ80	9/6	OC72	30/-	TY2321	20/-	UY21	16/6
3D6	5/-	6H6GTG	3/-	10F9	11/6	30P12	12/6	AZ31	10/-	ECS4	6/6	EZ81	9/-	P61	3/6	TY22	15/-	UY41	8/6
3Q4	7/6	6H6GTG	3/6	10LD3	10/-	30P16	6/6	AZ41	13/11	EC70	12/6	FC2A	24/7	PABC80	15/-	TP2620	33/2	VMP4G	15/6
3Q5GT	9/6	6J5G	5/-	10LD11	15/11	31	7/6	BL63	24/7	ECC31	15/-	FC4	26/6	PCC8	9/6	TP25	19/6	UY85	10/6
3S4	7/6	6J5GTG	5/6					BL63	7/6	ECC32	10/6	FC13	26/6	PCC89	29/10	TY86F	19/11	VP2(7)	12/6
3V4	7/6	6J5GTG	6/-					C1	12/6	ECC33	8/6	FC24	26/6	PCC89	29/10	TY86F	19/11	VP4(7)	15/-
3R4G	17/6	6J6	5/6	10P13	17/6	33A/158M		C1	12/6	ECC34	24/7	FV4/500	10/6	PCF80	9/-	U1/12	12/-	VP4B	23/3
3U4G	8/6	6J7G	6/6	10P14	19/6	35/1	12/6	CBL1	26/6	ECC35	8/6		10/-	PCF82	12/6	U18/20	10/-	VP13C	7/-
3V4G	11/6	6J7GT	6/6	10P15	19/6	35/2	12/6	CBL2	26/6	ECC36	8/6		10/-	PCF82	12/6	U22	8/-	VP23	6/6
3Y4G	12/6	6K6GT	8/-	12AC6	15/3	35L6GT	9/6	CBL3	23/3	ECC40	23/3	FV4/800	10/6	PCF83	12/6	U24	29/10	VP41	6/6
3Y3G	8/-	6K7G	5/-	12AD6	17/3	35W4	8/6	CK506	6/6	ECC82	7/6	GZ30	10/6	PCL84	21/11	U25	17/11	VR150/309	-
3Y3GT	8/6	6K7GT	4/-	12AE6	13/11	35Z3	10/6	CL33	19/3	ECC83	10/-	GZ32	12/6	PEN4DD		U26	12/6	VR150/309	-
3Y4	12/6	6K8G	8/-	12AH7	8/-	35Z4	7/6	CV63	10/6	ECC84	10/-	GZ34	14/-		26/6	U31	10/6	VT61A	5/-
3Z3	12/6	6K8GTG	G	12A8H	10/6	35Z5GT	9/-	CV85	12/6	ECC85	9/6	H30	5/-	PEN25	20/-	U33	26/6	VT501	5/-
3Z4G	10/6	12/6	12/6	12AT6	10/6	41MTL	8/-	CV271	10/6	ECC91	5/6	H63	12/6	PEN36C	10/6	U35	26/6	W61M	26/6
3Z4GT	12/6	6K25	19/11	12AT7	8/-	42	23/3	CV428	30/-	ECC80	13/6	HABC8013	6/6	PEN40DD		U37	26/6	W76	7/6
6A7	26/6	6L1	23/3	12A16	23/6	43	23/3	CY1	16/7	ECC82	13/6	HL133DD			25/-	U43	10/6	W81M	6/6
6A8	10/-	6L6G	9/6	12A17	7/6	50C5	12/6	CY31	16/7	ECH3	26/6		12/6	PEN44	26/6	U45	10/6	W107	12/6
6AB7	8/-	6L7GT	12/6	12A18	10/6	50CD6G		D1	16/7	ECH21	23/3	HL23	10/6	PEN45	19/6	U50	8/-	W729	18/7
6AB8	12/6	6L18	13/-	12BA6	9/-		29/10	D15	10/6	ECH35	9/6	HL23DD		PEN45DD		U52	8/6	X31	26/6
6AC7	6/6	6L19	23/3	12BE6	10/-	50L6GT	9/6	D42	10/6	ECH42	9/6		16/7		26/6	U56	7/6	X41	26/6
6AG5	6/6	6LD20	15/11	12BH7	21/3	53KU	19/11	D63	5/-	ECH81	9/-	HL41	12/6	PEN46	7/6	U78	7/-	X42	26/6
6AK5	8/-	6N7	8/-	12C8	15/-	72	4/6	D77	6/6	ECL80	12/6	HL41DD		PEN383	23/3	U107	16/7	X61	26/6
6AL5	6/6	6P1	19/1	12E1	30/-	75	24/7	DAC32	11/-	ECL82	12/6		19/3	PEN453DD		U191	16/7	X61M	26/6
6AM6	7/6	6P25	12/6	12J5GT	4/6	77	8/-	DAF91	7/6	ECL83	24/7	HL42DD			33/2	U251	15/-	X63	10/6
6AQ5	8/6	6P28	26/6	12J7GT	10/6	78	8/6	DAF96	10/-	EF9	23/3		19/3	PEN/DD		U281	19/11	X65	12/6
6AT6	8/6	6Q7G	10/-	12K5	17/11	80	9/-	DD41	13/11	EF22	14/-	HN309	24/7	4020	33/2	U282	22/7	X66	12/6
6AU6	10/6	6Q7GT	11/-	12K7GT	7/6	83	15/-	DDT4	24/7	EF36	6/-	HVR2	20/-	PL33	19/3	U301	23/3	X76M	14/-
6B7	10/6	6R7G	10/-	12K8GT	14/-	83V	12/6	DF33	11/-	EF37A	8/-	HVR2A	6/-	PL36	15/-	U329	15/-	X78	21/3
6BBG	4/6	6SA7GT	8/6	12Q7GT	7/6	85A2	15/-	DF91	6/6	EF39	6/-	KF35	8/6	PL38	26/6	U339	16/7	X79	21/3
6BBGTM	5/-	6SC7	10/6	12SA7	8/6	150B2	15/-	DF96	10/-	EF40	15/-	KL32	21/11	PL81	13/6	U403	16/7	X109	17/3
6BA6	7/6	6SGYGT	8/-	12SC7	8/6	185B7	33/2	DH63	10/-	EF41	9/6	KL35	8/6	PL82	8/6	U404	10/6	XG(1.5)	6/6
6BE6	7/6	6SH7	8/-	12SG7	8/6	185BTA	33/2	DH63(M)		EF42	12/6	KLL32	24/7	PL83	11/6	U801	29/10	XD1	18/-
6BBG6	23/3	6S17	8/-	12SH7	8/6	203THA	26/6		17/6	EF50(A)	7/-	KT2	5/-	PM2B	12/6	U4020	16/7	XH(1.5)	6/6
6BH6	9/-	6SK7GT	8/-	12SJ7	8/6	220TH	24/7	DH76	7/6	EF50(E)	5/-	KT33C	10/-	PM12	6/6	UABC80106	XSG(1.5)	6/6	
6BJ6	7/6	6SL7GT	8/-	12SK7	8/6	305	10/6	DH107	8/6	EF54	5/-	KT36	29/10	PM12M	6/6	UAF42	10/6	Y63	7/6
6BR7	23/3	6SN7GT	7/6	12SQ7	12/6	402PEN		DH107	13/11	EF73	10/6	KT41	26/6	PM24M	21/3	UB41	12/6	Y63	10/6
6BW6	9/6	6SQ7GT	9/-	12SR7	8/6		23/3	DK32	21/11	EF80	8/-	KT44	15/-	PX4	33/2	UBC41	10/-	Z66	20/-
6BW7	8/-	6SS7	8/-	12Y4	10/6	807	7/6	DK40	21/3	EF85	7/6	KT61	12/6	PX25	59/8	UCB81	13/11	Z77	7/6
6BX6	8/-	6U4GT	12/6	14S7	23/3	956	3/6	DK91	7/6	EF86	14/-	KT63	7/6	PY31	16/7	UBF80	9/6	Z719	8/-
6C4	7/-	6U5G	7/6	15D1	26/6	1821	16/7	DK92	10/6	EF89	10/-	KT66	15/-	PY32	19/11	UBF89	10/6	Z729	14/-

NEW METAL RECTIFIERS—FULLY GUARANTEED

DRM-1B	15/4	RM-2	9/-	WX3	3/6	14A100	27/-	14R4	1-2-8-2	19/-	16R6	2-1-8-1	8/6
DRM-2B	16/2	RM-3	9/6	WX4	3/6	14A124	28/-	14R4	1-2-8-3	23/6	16R4	1-1-8-1	4/6
DRM-3B	23/3	RM-4	18/-	WX6	3/6	14A163	38/-	14R4	2-1-16-1	21/-	16R4	1-1-16-1	6/6
LW7	22/6	RM-5	24/-	14A86	18/-	14B130	35/-	16R4	1-1-16-1	8/6	16R4	1-2-8-1	11/-
RM-0	7/11	W4	3/6	14A97	25/-	14B261	11/6	16RD	2-2-8-1	12/-	16RD	2-2-8-	

QUICK, EFFICIENT UP-TO-DATE COMPONENT SERVICE!

TWO-TRANSISTOR POCKET SET

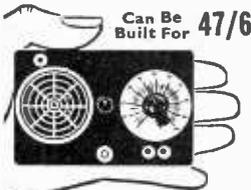

Can Be Built For **47/6**

BUILD THE "SKY PIXIE" VEST-POCKET TWO-TRANSISTOR PLUS DIODE RADIO which gives a superb performance and is highly sensitive. Size only 4 1/4 in. x 3 1/4 in. x 1 1/4 in., weight under 7oz.—yet it is a **THREE-STAGE** receiver covering all medium waves, working entirely off a tiny "pen-light" battery. Every part tested before despatch! **SPECIAL STEP-BY-STEP PLANS FOR ABSOLUTE BEGINNERS.** Total building cost including case, transistors, etc.—**ONLY 47/6** with plans. Postage, etc. 2/-. C.O.D. 2/- extra. (Parts sold separately. Priced parts list and plans 1/6.) **RUSH YOUR ORDER TODAY!**

everything down to the last nut and bolt—**ONLY 47/6** with plans. Postage, etc. 2/-. C.O.D. 2/- extra. (Parts sold separately. Priced parts list and plans 1/6.) **RUSH YOUR ORDER TODAY!**

POCKET VALVE RADIO

Can Be Built For **39/6**

Anyone Can Build This Beautiful Precision Pocket Radio in an hour or two. No knowledge whatever needed, our Simple, Pictorial Plans take you step by step! Remarkably sensitive—covers all medium waves, incl. Luxembourg, Home, Light. Size only 2 1/2 in. x 3 in. x 5 1/2 in. Not a Top! But a Real Valve Radio! Uses self-contained battery and is a really personal-phone, pocket radio with Detachable Aerial. **IDEAL FOR BEDROOM, GARDEN, etc.** We supply ALL parts necessary together with plans, etc.—for the Special Price of 39/6 (Plus 2/6 post, etc.). **BUILD YOURS NOW!** (All parts sold separately.) Priced parts list, etc. 1/9. Big demand certain—Send Today! C.O.D. 2/- extra.




RECORD CHANGER AND PLAYER BARGAINS!

E.S.E. MONARCH, 4-speed, mixer auto-changer unit, model U.A.S. Fully complete with crystal pickup, etc. Brand new—Limited Stocks Only. **GIFT 58/19/6.** (Plus post and packing, 5/-) **LATEST "COLLARO"** 4-speed auto-changer, with Hi-Fi pickup. Complete in maker's sealed cartons. **BARGAIN 47/19/6.** (Plus test and packing 4/6.) **"COLLARO" JUNIOR**, 4-speed, single player, with crystal pickup, using HGP59 cartridge. **OUR PRICE 92/6.** (Plus 4/- post and packing.)

Choice of beautiful walnut veneered cabinet or ivory or brown bakelite. This is the lowest possible price consistent with high quality. No radio knowledge whatever needed... can be built by anyone in 2-3 hours, using our very simple easy-to-follow diagrams. The terrific new circuit of the **"OCEAN-HOPPER"** covers all medium and long waves, has razor-edge selectivity and exceptionally good tone. Price also includes ready drilled and punched chassis, set of simple easy-to-follow plans—in fact, everything! **Parts tested before despatch!** Uses standard octal-base valves. For A.C. mains 200-250 volts (low running costs—approximately 18 watts!). Size 12 in. x 8 in. x 5 in. Build this long-range powerful midset NOW. **TOTAL BUILDING COST INCLUDING PLANS, ETC., 55/7/6.** (Post and packing 3/6.) Parts sold separately. Priced parts list and plans 1/9. C.O.D. 2/- extra.

Can Be Built For **107/6**

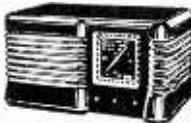

COMPONENT BARGAINS!

Red-Spot Transistors, tested, 8/6. White-Spot Transistors, tested, 15/-. Also all Mullard and standard types stocked. Moving Coil P.M. Speakers. 2 1/2 in. 17/6; 3 1/2 in. 19/6; 5 in. 17/6; 8 in. 19/6. **ALL TYPES OF COMPONENTS STOCKED AT COMPETITION PRICES**

PRINTED CIRCUIT POCKET SET

BUILD THIS 3 TRANSISTOR POCKET RADIO... PRINTED CIRCUIT VERSION! The "Companion" is comparable in sensitivity to a three-valve battery set, it is exceptionally small in size (4 1/4 in. x 3 1/4 in. x 1 1/4 in.) and is a self-contained pocket radio that does not need aerial or earth. It has built-in speaker and covers medium and long waves. This unique little set **CAN BE BUILT FOR ONLY 97/6.** **EVERYTHING INCLUDED!** (Plus post and packing 2/6.) All parts sold separately. Price list, etc., 6d. C.O.D. 2/- extra.

PRINTED CIRCUIT POCKET SUPERHET

BUILD THIS PROFESSIONAL-LOOKING, FIRST-CLASS 6 TRANSISTOR POCKET SUPERHET THE "TRANSIDYNE." Size only 6 1/2 in. x 3 1/2 in. x 1 1/2 in. Beautiful red and cream plastic case with engraved dial. Set weighs only 20oz. with batteries! Covers medium and long waves. Works off two No. 8 batteries. The second I.F. Stage is reflexed to give additional audio gain. In-built ferrite rod aerial and 2 1/2 in. P.M. speaker. This **TRANSIDYNE** is probably the best of its kind, it is simple to build and really sensitive. **ALL COMPONENTS INCLUDING CABINET, PRINTED CIRCUIT, TRANSISTORS—IN FACT EVERYTHING CAN BE SUPPLIED FOR 111/15/-.** (Plus post and packing 2/6.) (All parts sold separately. Price list, circuit, etc., 9d.) C.O.D. 2/- extra.

CAN BE BUILT FOR

47/6

Build this exceptionally sensitive high efficiency Pentode radio. Uses unique assembly system and can be built by anyone without any radio knowledge whatever in 45 minutes. Handsome black-crackle steel case with specially made black and gold dial with stations printed. Size of radio only 6 1/4 in. x 5 in. x 3 in. Covers all Medium and Long waves—uses only one all-day battery. H.T. consumption only 1 to 1.5 mA. Use personal phone. Ideal for Bedroom, Garden, Holiday, etc. **BUILD THE "SKYROMA" NOW!** Total building cost—everything down to last nut and bolt—47/6 (Postage etc., 2/-)—with full set of clear, easy-to-follow plans. (Parts sold separately. Priced Parts Lists & Plans 1/6d.) C.O.D. 2/- extra.

READ WHAT OTHERS SAY!

- I WAS SURPRISED AT THE NUMBER OF STATIONS—**
L. D. C., of Worcester, writes, "—Just a few lines to let you know how pleased I am with the midget portable radio. I was surprised at the number of stations I could get, with a clear performance. The price was a real bargain. Have you lists of other bargains? If so, please send them—"
- I MUST SAY I AM VERY PLEASED—**
J. W. S., of Scarborough, Yorks, writes, "—I feel I must say I am very pleased in the way you do business and if at any time I require anything, or can recommend you to anyone, I will not hesitate to help you—"
- I'VE HEARD MUCH PRAISE OF THEM—**
J. E. O'Hilton, Mr. Derby, writes, "—I would like one of your portable radio kits as I've heard much praise of them—"
- THIRTY-TWO STATIONS RECEIVED—**
J. N., of Oxford, writes, "—Yesterday evening on the Medium Wave-band, between 10 p.m. and 10.30 p.m., I counted 32 distinguishable stations! I am very pleased with the set, which is well worth the money—"
- MY DEEPEST ADMIRATION—**
J. R., of North Shields, Northumberland, writes, "—The honest and direct dealing of your firm has earned from me my deepest admiration—"
- ITS PERFORMANCE IS ALMOST UNBELIEVABLE—**
E. F., of Ipswich, writes, "—For so small a set I think it is a wonderful station getter with ample volume on all. Its performance is almost unbelievable, and it's a very convenient little set giving me stations I've never been able to get on a larger set—"

THIS TRANSISTOR SET

CAN BE BUILT FOR ONLY

29/6

VERY SPECIAL OFFER WHILE STOCK OF POCKET LASTS!—The "Sky-Scout" Pocket two-stage transistor set, size only 5 1/2 in. x 3 1/2 in. x 4 1/4 in. Covers all medium waves and works entirely off tiny "penlight" battery which costs 6d. and fits inside case. All parts tested before despatch. Can be built for 29/6, plus 2/- post and packing, including Case, Transistor. **STEP-BY-STEP PLANS FOR ABSOLUTE BEGINNERS,** nuts, bolts, etc. (C.O.D. 2/- extra). Parts sold separately, priced parts list & Plans, 1/6. **VERY SIMPLE TO BUILD.**



CONCORD ELECTRONICS

69, PRESTON STREET, BRIGHTON.

Dept. PW9

Orders receive prompt attention. Cheques accepted. Cash on delivery 2/- extra. Please print name and address in block letters. Suppliers to Schools, Universities, Government and Research Establishments. Complete range of components and valves stocked. Reorder no C.O.D. abroad. Money refunded if parts returned intact within 7 days.

R.S.C. HI-FI TAPE RECORDER

REALISM AT INCREDIBLY LOW COST


The Recorder incorporates the Latest Collaro Mark IV Tape Transcriber. The Linear L.T45 High Quality Tape Amplifier, High Flux P.M. Speaker, empty Tape Spool, and a Reel of Best Quality L.P. Tape (850ft.) are included. A Collaro Studio Microphone can be supplied with the recorder only at a special price of 37/6. **39 1/2 GNS.** H.P. TERMS. Deposit 3 Gns. and 12 monthly Carr. 15/-. payments £3.10.6.

R.S.C. A8 HIGH FIDELITY 12 WATT AMPLIFIER

Ultra Linear Push-Pull Amplifier with "Built-in" Tone Control. Pre-amp stages, high sensitivity. Includes 5 valves (807 outputs). High Quality sectionally wound output transformer, specially designed for Ultra Linear operation, and reliable small condensers of current manufacture. **INDIVIDUAL CONTROLS FOR BASS AND TREBLE** "Lift" and "Cut." Frequency response +3 db. 30-30,000 c/s. Six negative feedback loops. Hum level 71 db. down. ONLY 70 millivolts INPUT required for FULL OUTPUT. Suitable for use with all makes and types of pick-ups and practically all microphones. Comparable with the very best designs.

£7-15-0
For STANDING or LONG PLAYING RECORDS. For MUSICAL INSTRUMENTS such as STRING BASS, GUITARS, etc. OUTPUT SOCKET with plug provides 300 v. 30 mA. and 6.3 v. 1.5A. For supply of a RADIO FEELDER UNIT. Size approx. 12-9-7in. For A.C. mains 200-230-250 v. 50 c/s. Outputs for 3 and 15 ohm speakers. Kit is complete to last nut. Chassis is fully punched. Full instructions, points-to-point wiring diagrams supplied. Unapproachable value, at £7/15-0 or factory built 45/- extra. Carriage 10/-.

If required louvred metal cover with 2

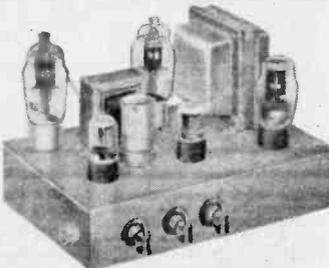

carrying handles can be supplied for 18/9. Additional input sockets, with associate Vol. control so that two different inputs such as Gram and "Mike" or Tape and Radio can be mixed, can be provided for 13/- extra. Guaranteed 12 months. TERMS on assembled two input model: DEPOSIT 18/9 and 12 monthly payments 18/9. HIGH FIDELITY MICROPHONES and SPEAKERS in stock. Keep cash prices or credit terms if supplied with amplifier.

HI-FI 8 WATT AMPLIFIER

Special Purchase due to Cancelled Export Order. For 200-250 v. A.C. A limited number is available of these highly sensitive Push Pull units guaranteed brand new and in working order and with separately controlled inputs for "mike" and gram, etc. LATEST B.V.A. VALVES. Excellent performance. **£4-19-9** Carr. 7/6.

STAAR GALAXY 4-SPEED MIXER AUTO-CHANGERS

Brand new, cartoned. Turnover sapphire stylus. Many exclusive features. Unique design motor virtually free from "wow". For 200-250 v. A.C. mains. Only **£5.19.6.** while stocks last or fitted Acoos turnover head for 78 r.p.m. L.P. or Stereo records. **£3.19.6.** Carr. 3/9 extra.

PORTABLE CABINETS. High Quality Finish. Revolving covers. Attractive design. Inside measurements 7 1/2 in. x 12 1/2 in. x 8 1/2 in. high. Clearance above base-board 1 1/2 in. Below 2 1/2 in. 69/9 each. Or size 14 1/2 in. x 13 1/2 in. x 6 1/2 in., only 47/9.

SPECIAL OFFER. Above cabinet, LG3 Amplifier, Staar, Changer and 6 1/2 in. P.M. Speaker 11 Gns. Carr. 10/-.

THE SKYFOUR T.R.F. RECEIVER.

A design of a 3-valve Long and Medium wave 200-250 v. A.C. Mains receiver with selenium rectifier, High gain H.F. stage and low distortion audio band detector. Power pentode output. Valve line-up 6K7, 5P6i, 6V6G. Selectivity and quality are well up to standard, an simplicity of construction is a special feature. Point-to-point wiring diagrams, instructions and parts list, 1/8. Maximum building costs **£4.19.6.** Inc. attractive Brown or Cream Bakelite or Walnut veneered wood cabinet 12 x 6 1/2 x 5 1/2 in.

ACOS CRYSTAL "MIKE" INSERTS. Approx. 1 1/2 in. square. Fly lead connections. Only 5/11 each. Brand New. Round type approx. 1 1/2 in. diam. Equipment tested, 4/11 each.

PICK-UP ARMS complete with Hi-Fi turnover crystal head. Acos GP54. Limited number brand new, perfect, at approx. half price. Only 35/9.

ACOS CRYSTAL MICROPHONES. Type 33-1, hand or desk. List price 50/- Brand new, cartoned. 29/6.

EXTENSION SPEAKERS

Ready for use in walnut veneered cabinet.

- 6 1/2 in. 2-3 ohms, 29/11.
 - 8 in. 2-3 ohms, 35/9.
 - 1 1/2 in. 2-3 ohms, 56/9.
- Very limited number



14 WATT AMPLIFIERS. Unused and in good order but store soiled. For 200-250 v. A.C. mains input. Outputs for 3 and 15 ohm speaker. Inputs for "mike" and Gram. Limited number, complete with valves. Only 6 Gns., carr. 5/-.

R.S.C. MAINS TRANSFORMERS (FULLY GUARANTEED)

Interleaved and Impregnated. Primaries 200-230-250 v. 50 c/s. Screened. **TOP SHROUDED DROP THROUGH**
250-0-250 v. 200 mA. 6.3 v. 2 a. 16/9
350-0-350 v. 80 mA. 6.3 v. 2 a. 5 v. 2 a. 18/9
250-0-250 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. 23/9
300-0-300 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. 23/9
350-0-350 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. 23/9
350-0-350 v. 100 mA. 6.3 v. 4 a. 4 a. C.T.
0.4-5 v. 3 a. ... 23/9
350-0-350 v. 150 mA. 6.3 v. 4 a. 5 v. 3 a. 29/9

FULLY SHROUDED UPRIGHT
250-0-250 v. 60 mA. 6.3 v. 2 a. 5 v. 2 a. ... 17/6
Midjet type 21-3-3in. ... 17/6
250-0-250 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. 26/9
300-0-300 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. 26/9
350-0-350 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. 26/9
300-0-300 v. 130 mA. 6.3 v. 4 a. 6.3 v. 1 a. for Mullard 150 Amplifier ... 35/9
350-0-350 v. 150 mA. 6.3 v. 4 a. 5 v. 3 a. 33/9
350-0-350 v. 150 mA. 6.3 v. 2 a. 6.3 v. 2 a. 5 v. 3 a. ... 35/9
425-0-425 v. 200 mA. 6.3 v. 4 a. C.T. 6.3 v. 4 a. C.T., 5 v. 3 a. Suitable Williamson Amplifier. etc. ... 48/9



A SIX TRANSISTOR "POCKET" SUPERHET RADIO

All parts including Transistors Printed Circuit. Attractive Cream or Coloured Plastic case. Ferrite aerial. 2 1/2 in. P.M. Speaker, etc., etc. and full instruction booklet. Size 5 1/2 x 3 1/2 x 1 1/2 in. completed Long and Medium Wavebands 250 M.W. push-pull output. Demonstrated at our counter premises. **£9.19.6** Carr. 3/6 extra.

R.S.C. BATTERY TO MAINS CONVERSION UNITS

Type BM1. An all-dry battery eliminator. Size 5 1/2 x 4 1/2 x 2 1/2 in. approx. Completely replaces battery supplying 1.4 v. and 90 v. where A.C. mains 200-250 v. 50 c/s is available. Suitable for all battery portable receivers requiring 1.4 v. and 90 v. This includes latest low consumption types. Complete kit with diagrams, 39/9. or ready to use, 46/9.



Type BM2. Size 8 x 5 1/2 x 2 1/2 in. Supplies 120v. 90 v. and 60 v., 40 mA. and 2 v. 0.4 a. to 1 amp. fully smoothed. Thereby completely replacing both I.T. batteries and L.T. 2 v. accumulators. When connected to A.C. mains supply 200-250 v. 50 c/s. **SUITABLE FOR ALL BATTERY RECEIVERS** normally using 2 v. accumulator. Complete kit of parts with diagrams and instructions. 49/8. or ready for use, 59/6.

ELIMINATOR TRANSFORMERS

Primaries 200-250 v. 50 c/s.
120 v. 40 mA. 5-0-5 v. 1 a. ... 15/9
90 v. 15 mA. 4-0-5 v. 200 mA. ... 9/8

SMOOTHING CHOKES

150 mA. 710 H 250 ohms ... 11/9
100 mA. 10 H 200 ohms ... 8/9
80 mA. 10 H 350 ohms ... 5/9
60 mA. 10 H 400 ohms ... 4/11

CHARGER TRANSFORMERS

All with 200-230-250 v. 50 c/s Primaries:
0.9-15 v. 11 a. 11/9. 0.9-15 v. 3 a. 18/9
0.9-15 v. 5 a. 19/9. 0.9-15 v. 6 a. 23/9.

COLLARO R054 3-SPEED AUTO-CHANGERS

with Studio pick-up. Brand new. For 110 v. 50 c.p.s. A.C. mains. Price with 110 v. to 220-250 v. Auto Trans. only **£5.19.6.** Carr. 5/6.

COLLARO CONQUEST 4-SPEED AUTO-CHANGER

with high speed Studio pick-up. Latest model. Brand new. Cartoned. For 200-250 v. 50 c.p.s. A.C. mains. Our price **£7.19.8.** Carr. 5/6.

COLLARO 4-SPEED SINGLE PLAYER

with separate pick-up, GP54 with sapphire stylus. For 200-250 v. A.C. mains. **£4.10.0.**

ELIMINATOR TRANSFORMERS

Primaries 200-250 v. 50 c/s.
120 v. 40 mA. 5-0-5 v. 1 a. ... 15/9
90 v. 15 mA. 4-0-5 v. 200 mA. ... 9/8

SMOOTHING CHOKES

150 mA. 710 H 250 ohms ... 11/9
100 mA. 10 H 200 ohms ... 8/9
80 mA. 10 H 350 ohms ... 5/9
60 mA. 10 H 400 ohms ... 4/11

CHARGER TRANSFORMERS

All with 200-230-250 v. 50 c/s Primaries:
0.9-15 v. 11 a. 11/9. 0.9-15 v. 3 a. 18/9
0.9-15 v. 5 a. 19/9. 0.9-15 v. 6 a. 23/9.

COLLARO R054 3-SPEED AUTO-CHANGERS

with Studio pick-up. Brand new. For 110 v. 50 c.p.s. A.C. mains. Price with 110 v. to 220-250 v. Auto Trans. only **£5.19.6.** Carr. 5/6.

COLLARO CONQUEST 4-SPEED AUTO-CHANGER

with high speed Studio pick-up. Latest model. Brand new. Cartoned. For 200-250 v. 50 c.p.s. A.C. mains. Our price **£7.19.8.** Carr. 5/6.

COLLARO 4-SPEED SINGLE PLAYER

with separate pick-up, GP54 with sapphire stylus. For 200-250 v. A.C. mains. **£4.10.0.**

R.S.C. A12 STEREOPHONIC AMPLIFIER KIT

A complete set of parts to construct a Stereo amplifier with an undistorted output total 6 watts (3 watts each channel). For A.C. mains input of 200-250 v. Outputs for matched 2-3 ohm speakers. Sensitivity 130 m.v. Ganged Vol. and Tone Controls. Preset balance control. Full instructions and point to point wiring diagrams Carr. and pkg. 5/- supplied. Only good quality components and latest high grade valves used. Exceptionally realistic reproduction can be obtained at ample volume for the home, as can be demonstrated in typical surroundings at our County Arcade premises. A really sensational offer.

£3-19-6

STEREO EQUIPMENT OFFER.
Comprising A12 Kit, 2 matched 8in. L/Speakers, and Acos T/O Stereo head suitable most pick-ups. Carr. 7/6

£6-19-6

LINEAR LT45 HIGH QUALITY TAPE DECK AMPLIFIER. With "built in" Power pack and oscillator stage. For Tape Decks with High or Low Impedance. Playback and Erase Heads. such as Lane. Carr. 7/6

12 GNS.

etc. For A.C. Mains 200-250 v. 50 c/s. Linear frequency response of +3 db. 50-11,000 c/s. Negative feedback equalisation. Output 4 watts. Send S.A.E. for leaflet.

R.S.C. 30 WATT ULTRA LINEAR HIGH FIDELITY AMPLIFIER A10

A highly sensitive Push-Pull high output unit with self-contained Pre-amp. Tone Control Stages. Certified performance figures compare equally with most expensive amplifiers available. Hum level 70 db. down. Frequency response +3 db. 30-30,000 c/s. A specially designed sectionally wound ultra linear output transformer is used with 807 output valves. All components are chosen for reliability. Six valves are used, EF86, EF86, ECC83, 807, 807, CZ33. Separate Bass and Treble Controls are provided. Minimum input required for full output is only 12 millivolts so that ANY KIND OF MICROPHONE OR PICK-UP IS SUITABLE. The unit is designed for CLUBS, SCHOOLS, THEATRES, DANCE HALLS or OUTDOOR FUNCTIONS, etc. For use with Electronic ORGAN, GUITAR, STRING BASS, etc. For standard or long-playing records. OUTPUT SOCKET PROVIDES L.T. and H.T. for a RADIO FEEDER UNIT. An extra input with associated vol. control is provided so that two separate inputs such as Gram and 'Mike' can be mixed. Amplifier operates on 200-250 v. 50 c/s. A.C. Mains and has output for 3 and 15 ohm speakers. Complete kit of 3 and 15 ohm parts with fully punched chassis and point-to-point wiring diagrams and instructions. Carr. 10/-

11 GNS.

as for A8 can be supplied for 18/-. The amplifier can be supplied, factory built with 12 months' guarantee, for £13.19.6. TERMS: DEPOSIT 2/9 and 12 monthly payments of 2/9.

LINEAR 'DIATONIC' 10-14 WATT HIGH FIDELITY PUSH-PULL ULTRA LINEAR AMPLIFIER. For 200-250 v. A.C. mains. Valves EC83, ECC83, EL84, EL84 miniature Mullard. Self-contained Pre-amp. Tone Control stage and separate Bass and Treble Controls. Independent 'Mike' and Gram input sockets are provided. Output Matchings for 3 and 15 ohm speakers. Only 12 GNS. or Deposit 2/9 plus 10 carr. and 12 monthly payments of 2/9. Send S.A.E. for leaflet.

LINEAR L10 HI-FI 10 watt Amplifier and separate Pre-amplifier. 15 GNS. Complete. Send S.A.E. for leaflet.

LINEAR L50 50 WATT P.A. AMPLIFIER. High quality and sensitivity. 19 GNS. Send S.A.E. for leaflet.


D.C. SUPPLY KIT. 12 v. 1 a. consisting of partially drilled metal case, mains trans., F.W. Bridge Rectifier, 2 fuseholders and fuses. Change Direction switch, variable speed regulator and circuit. For 200-250 v. A.C. mains. Suitable Electric Trains, etc. Limited number available at 29/9.

BUILD A HIGH QUALITY 29 1/2 GNS. TAPE RECORDER FOR Carr. 12/6

Kit consists of latest Collaro Tape Transcripator Mark IV listed £25. Linear LT45 complete Tape Amplifier listed 12 Gns. Acos 33-1 microphone listed 50/-, Reel of recording tape listed 28/6. 6in. x 4in. or 6in. loudspeaker listed 29/6. and wiring diagrams.

AM/FM RADIOGRAM CHASSIS HIGH QUALITY 6-8 WATT PUSH-PULL OUTPUT

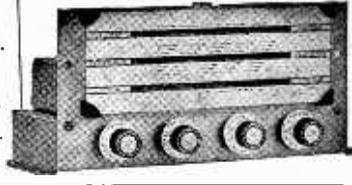For 200-250 v. Mains. Long wave, Medium, F.M. and Gram. Complete with 8 B.V.A. valves. Guaranteed 12 months. Only 22 GNS. Or Deposit £2.12.0 and 9 monthly payments of £2.12.0.



R.S.C. 45 WATT A5 HIGH-GAIN AMPLIFIER

A highly-sensitive 4-valve amplifier for the home, small club, etc. Only 50 millivolts input is required for full output so that it is suitable for use with the latest high fidelity pick-up heads, in addition to all other types of pick-ups and practically all 'mikes'. Separate Bass and Treble Controls are provided. These give full long-playing record equalisation. Hum level is negligible being 71db. down, 15 db. of negative feedback is used. H.T. of 300 v. 25 mA. and L.T. of 6.3 v. 1.5 a. is available for the supply of a Radio Feeder Unit, or Tape-Deck pre-amplifier. For A.C. mains input of 200-230-250 v. 50 c/s. Output for 2-3 ohm speaker. Chassis is not suitable for use with any other type of baseplate with Blue hammer finish and point-to-point wiring diagrams and instructions. Exceptional value at only £4/15/-, or assembled ready for use 25/- extra, plus 3/6 carr. ; or Deposit 22/6 and 5 monthly payments of 22/6 for assembled unit.

R.S.C. 3-4 WATT A7 HIGH-GAIN AMPLIFIER

For 200/250 v. 50 c/s. Mains input. Appearance and Specification, with exception of output wattage, as A5. Complete Kit with diagrams, £3.15.0. Carr. 3/6.

LINEAR STEREOPHONIC L3/3 3+3 WATT QUALITY AMPLIFIER

Output 6 watts when not used with stereo head. For 200-250 v. 50 c.p.s. A.C. mains. Ganged controls, Volume and Tone. Outputs matched by preset balance control. For use with 2 matched 3 ohm speakers. Only requires connecting to Pick-up speakers and mains point. Sensitivity 150 m.v. Supplied with guarantee and instructions. Send S.A.E. for leaflet. Terms available.

7 GNS.

LINEAR L45 MINIATURE 4/5 WATT QUALITY AMPLIFIER. Suitable for use with Collaro, B.S.R. or any other record playing unit, and most microphones. Negative feed-back 12 db. Separate Bass and Treble Controls. For A.C. mains input of 200-250 v. 50 c/s. Output for 2-3 ohm speaker. Three miniature Mullard valves used. Size of unit only 6-5-4in. high. Output for 2-3 ohm speaker. Guaranteed for 12 months. Only £5/19/6. Send S.A.E. for illustrated leaflet. Credit Terms. Deposit 22/6 and 5 monthly payments of 22/6.

12in. 10 WATT HIGH QUALITY LOUD-SPEAKERS IN POLISHED WALNUT FINISHED CABINET

Gauss 12,000 lines. Speech coil 1 ohms or 15 ohms. Only £4.19.6 Carr. 5/- Terms: Deposit 11/- and 5 monthly payments of 11/-

Terms: C.W.O. or C.O.D. No C.O.D. under £1. Post 19/9 extra under 22; 2/9 extra under 55. All goods supplied subject to terms and guarantee as detailed in current catalogue. Open 9 to 6; Weds. until 1 p.m. Catalogue 6d. Trade supplied. S.A.E. with all enquiries.

PLESSEY DUAL CONCENTRIC 12in. 15 ohms HIGH FIDELITY SPEAKER (12,000 lines) with built-in tweeter (completely separate elliptical speaker with choke, condensers, etc.), providing extraordinarily realistic reproduction when used with our A8 or similar amplifier. Rated 10 watts. Price only £5/17/6.

ACOS HI-FI Crystal Cartridges. (Turn-over type with sapphire stylus.) HGP59. Standard replacement for Garrard and B.S.R. Only 17/9. Stereo Type or 7B, L.P. and Stereo records. Will fit B.S.R., Collaro, Garrard, and Galaxy changers. 52/6.

COLLARO Mk. III 3-SPEED TAPE TRANSCRIBERS Carr. 7/6
Brand New Carboxed & Limited Number.

SPEAKERS. 10in. W.B. "Stentorian" 3 or 15 ohms type HF1012 10 watts, hi-fidelity type. Recommended for use with our A8 amplifier. £4/10/9. 12in. Plessey 3 ohms 10 watts (12,000 lines). 59/6.

LG8 MINIATURE 2-3 WATT GRAM AMPLIFIER. For use with above or any other single or auto-change units. Output for 2-3 ohm speaker. For 200-250 v. 50 c.p.s. A.C. mains. Over-all size 6 1/2 x 4 1/2 in. Controls: Vol. and Tone with switch. Guaranteed 12 months. Only 55/9.

SUPERHET FEEDER UNIT. Design of a high quality Radio Tuner Unit (specially suitable for use with any of our Amplifiers). Delayed A.V.C. employed. Tuning W.C. Sw. incorporates Gram position. Controls are Tuning, W.Ch. and Vol. only 250 v. 15 mA. H.T. and L.T. of 6.3 v. 1 amp. required from amplifier. Size of unit approx. 9-6-7in. high. Simple alignment procedure. Point-to-Point wiring diagrams, instructions and priced parts list with illustration, 2/6. Total building cost £4/15/- For descriptive leaflet send S.A.E.


COLLARO ACA/564 4-SPEED SINGLE RECORD PLAYER UNIT. With Turnover crystal head 26/9/6. carr. 3/6.

COLLARO 4T/200 TRANSCRIPTION UNITS. With Transcription Pick-up. Mounted in attractively reline covered carrying case. Only 19 GNS.

R.S.C. (Leeds) MANCHESTER and LEEDS Ltd.

Mail Orders to 29-31 Moorfield Rd., Leeds 12. Callers to 5 and 7 County (Mecca) Arcade, Briggate, Leeds 1. and Universal Bazaars Ltd., 8-10 Brown St. (Market St.), Manchester 2.

LASKY'S RADIO

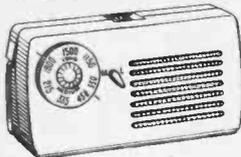

You can build this 6 TRANSISTOR POCKET RADIO

for £9/19/6 plus 3/6 post.
Printed Circuit construction. A FULL medium and long wave superhet, using very latest components including 6 transistors, 2 1/2 in. moving coil speaker and Ferrite aerial. Cream or coloured plastic case, 5 1/2 x 3 1/2 x 1 1/2 in., weight 12 ozs. Full assembly instructions supplied. Instruction Book 3/6, post free, returnable or deductible.
Demonstrated at either address.

LASKY'S F.M. TUNER

Printed Circuit version of the G.E.C. 912 "F.M.Plus." Can be built for £7/19/6 plus 3/6 post.

"Easy-to-Build" Radios

Complete Parcels. All components available separately. **CIRCUIT DIAGRAM & BUILDING INSTRUCTIONS FOR ANY OF THESE, 1/6 each, post free.**

CAR RADIO!


Do you know that you can build a car Radio with all these star features?

- ★ 12 v operation.
- ★ New hybrid circuit.
- ★ Transistor output.
- ★ New type Brimar valves.
- ★ No vibrator. 12 volt H.T. and L.T.
- ★ T.C.C. Printed Circuit and condensers.
- ★ Tuned R.F. stage.
- ★ Med. and long waves.
- ★ Permeability tuning.
- ★ Small size. Fits any car.

CAN BE BUILT FOR
£12.19.6

using all brand new components.

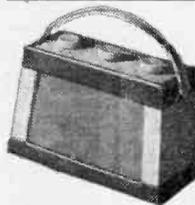Call and see it working in a car. Send 1/6 for Instruction Booklet, giving full details, illustrations, etc.



4-VALVE S/HET PORTABLE

Med. & long wave. BATTERY version can be built for 7 Gns. plus 3/6 post (only batteries extra).

MAINS/BATTERY version can be built complete for 9 Gns. plus 3/6 post.

BUILD A 6v. TRANSISTOR PORTABLE RECORD PLAYER FOR 10 GNS.

4 Transistor 200/250 milliwatts Amplifier Kit, £3/19/6.

Star of Garrard 45 r.p.m. Player and p.u., £4/19/6.

7 in. x 4 in. Ellip. Speaker, 14/6.

Case, 12 in. wide, 8 in. deep, 6 in. high, £2/5/-.
Total £11/18/6. Special Price for the Parcel. 10 Gns., post free.

MAIL ORDERS TO HARROW ROAD. PLEASE

LASKY'S (HARROW RD.) LTD.

42, TOTTENHAM COURT ROAD, W.1.

Telephone: MUSEum 2605.

370, HARROW ROAD, PADDINGTON, W.9.
LADbroke 4075 and CUNningham 1979.

Open all day SATURDAY. Half day Thursday.

Training in Radio and Television Servicing

The Pembridge College of Electronics provides a full-time One Year course in the basic principles of Radio and Television for prospective servicing engineers. It is also suitable for those wishing to become proficient in the maintenance of all types of industrial electronic equipment.

The next course commences on 8th September, 1959 and enrolments are now being accepted. The following course will commence on 5th January, 1960.

Home-study courses in Radio and Television are at present under preparation by our experienced staff and will be available soon.

For details of the One Year and other courses, write for prospectus and admission forms to:

The Principal, Dept. P10

THE PEMBRIDGE COLLEGE OF ELECTRONICS
34a Hereford Road, London, W.2. Telephone: BAYswater 9117

FOR VALVES AND SERVICE SPARES BY RETURN POST SERVICE



H30 5/-	PEN46 7/-	UF89 10/6	ILDS 3/6	6C6 5/-	6X5G 7/6	12SQ7 8/6
HL23DD 8/6	PEN220A 4/-	UL41 10/6	INS 10/6	6D6 5/-	6X5GT 7/6	14S7 17/6
HL41 3/6	PEN4A 15/-	UL84 11/6	IRS 8/6	6F6G 7/6	6/30L2 12/6	15D2 7/9
K40N 9/-	QP21 7/6	UJ6 19/11	IS4 10/6	6F6M 7/6	7B7 8/6	19AQ5 9/9
KF35 8/6	R16 26/6	UJ8 26/6	IS5 7/6	6F1 14/-	7B8 6/-	20D1 16/-
KK32 21/11	R19 19/11	UY1N 12/6	IT4 7/6	6F14 17/6	7C5 8/-	20F2 17/6
KL132 8/6	SP4 (5 pin) 10/6	UY41 8/6	IU5 7/6	6F15 14/-	7D6 13/6	20P1 26/6
KT2 5/-	SP4 (7 pin) 10/6	UY85 10/-	2C26 1/6	6H6 2/6	7H7 9/-	20P5 11/6
KT33C 10/-	SP41 10/6	UYZ1 12/6	2X2 4/6	6H6GT 2/6	7Q7 9/-	25A6G 15/-
KT55 11/6	SP61 3/-	VP13C 3/6	3A4 7/-	6J5M 6/6	7S7 9/6	25L6GT 10/-
KT61 14/-	SP61 3/-	VR22 3/6	3A4 7/-	3D6 5/-	7Y4 8/6	25Y5G 9/9
KT66 17/6	T41 23/3	(PM2A) 3/-	3Q4 9/-	6J7G 6/6	8D2 2/9	25Z4 9/6
KTW61 6/6	PT22 8/-	VP23 6/6	3K5GT 9/6	6J7M 9/6	9D2 3/6	25Z5 9/6
KTW63 7/6	PT25 26/6	VP41 8/6	354 8/-	6K7G 5/9	10C1 17/6	25Z6 10/6
KTZ41 5/6	UI0 10/6	VR105/30	3V4 9/-	6K7GT 5/9	10C2 17/6	30F1 10/6
MH41 7/9	U22 8/-	VR116 4/-	4D1 3/-	6K7M 6/6	10F1 (sur-	30F1A 10/6
ML4 8/6	U25 15/-	VR150/30	5R4GY 9/6	6K8G 8/6	15C (plus) 15/-	30P4 7/6
MSP4/5 10/6	U26 12/6	VR150/30	5U4G 8/-	6K8GT 10/-	12A6 6/6	30P12 12/6
MSP4/7 10/6	U37 26/6	VU120A 3/6	5V4 12/-	6K25 19/11	12A8 10/6	30PL1 12/6
N78 19/11	U45 15/-	VU39 (MU12/14)	5Y3G 8/-	6L6G 8/-	12A7 10/6	35L6GT 9/6
OZ4 5/6	U50 8/-	VU111 2/6	5Y3GT 8/-	6LM 9/-	12A7 9/-	25Y5 9/6
P61 3/6	UI91 11/6	W77 8/6	5Z4G 10/-	6L7 7/6	12A6 10/6	35W4 8/6
PC88 10/-	U339 12/-	W79 10/6	6A7 13/-	6L18 13/6	12A7 8/-	35Z4GT 8/6
PCF80 13/6	U404 11/4	X65 11/6	6A8G 10/-	6N7 7/6	12A7 9/-	42 8/-
PCF82 12/6	U801 29/10	X78 16/-	6AC7 6/6	6Q7G 9/-	12A6 9/-	35Z5GT 9/6
PCL82 13/6	UAB80 10/6	Y63 9/-	6AGS 5/6	6Q7GT 9/-	12B6 10/-	50C5 11/6
PCL83 17/6	UAF42 9/6	Z309 9/6	6AK5 6/6	6R7 9/-	12C8 9/-	50L6GT 8/6
PL36 17/6	UAF42 9/6	Z359 9/6	6AL5 6/6	6S47GT 8/-	12H6GT 3/-	75 11/6
PL38 20/6	YB41 12/-	Z579 9/6	6AM6 7/6	6SG7 7/6	12J5GT 3/-	77 7/6
PL81 16/-	UBC41 10/-	IC2 11/6	6AQ5 7/6	6SH7 6/6	12K7GT 10/6	80 8/6
PL82 9/6	UBF80 9/6	IC5GT 12/6	6AT6 9/-	6S17 8/-	12J7GT 7/6	142BT 3/6
PL83 11/6	UCC84 19/11	ID5 12/6	6AU6 10/-	6SK7 7/-	12K8GT 13/6	210DDT 4/6
PX25 12/6	UCC85 12/-	ID6 12/6	6B8G 4/6	6SL7GT 8/-	12Q7GT 7/6	807 6/6
PY80 9/-	UCC80 21/11	IHS5GT 10/6	6BA6 7/-	6SN7GT 9/6	12S7G 7/6	954 2/-
PY81 10/-	UCH42 10/6	IL4 6/6	6BE6 8/6	6U4GT 12/-	12S7H 6/9	955 4/-
PY82 9/6	UCH81 11/6	IL4 6/6	6B6 10/-	6USG 8/6	12S17 8/-	956 3/6
PY83 10/-	UCL82 21/11	IL4 6/6	6BH6 10/-	6U7G 8/6	12SK7 6/-	9001 5/6
PZ30 19/11	UCL83 17/-	IL4 6/6	6B16 9/-	6V6G 7/6	12SL7 8/-	9002 5/6
PEN4VA 15/-	UF41 10/6	IL4 6/6	6BW 10/-	6V6GT 7/6	12SN7GT 17/6	9004 5/6
PEN25 6/-	UF85 10/6		6CSGT 6/6	6X4 7/6		9006 5/6

AMPLIFIERS

3-3 amplifier, built to Mullard's exact specification, with 3 Mullard valves EL84, EF86, EZ81, complete with front panel, £8.2.6. Packing and post 3/6.

"Tru-Sound" Stereo Amplifier, suitable for use in conjunction with any standard or stereo record player. Twin amplifiers delivering a total of app. 7 watts. Output to match 3 ohm loudspeakers. Overall size 9 x 6 x 5 in. OUR PRICE £8.10.0. Post and packing 3/6.

EX GOVERNMENT HEADPHONE AND HAND MICROPHONE
Microphone No. 7 with press to speak switch in handle. Headphones with padded earpieces, moving coil. 8/6 complete. Post 1/9.

AUTOMATIC RECORD CHANGERS
B.S.R. UA8, 4-speed Mixer Automatic changer, manual and auto-control complete with latest B.S.R. "ful-fi" pickup. Carriage and packing 3/6. OUR PRICE £6.19.6.

The new B.S.R. Model UA12, 4-speed Mixer Automatic record changer, fitted with latest type turnover cartridge. OUR PRICE £8.17.6. Carriage 3/6.

The latest Collaro Conquest, 4-speed auto-changer, in cream with Studio 'O' insert.

Brand new, fully guaranteed, £7.19.6. plus packing and post 3/6.

Garrard 4 SP. This famous single record 4-speed unit complete with GC2 turnover crystal head and sapphire styli available in limited quantity, brand new and fully guaranteed. OUR PRICE £6.19.6. Post and packing 3/6.

NEW RELEASE CANADIAN WIRELESS REMOTE CONTROL UNIT No. 1
Consists of Hand Generator, Morse Key, Bell, Buzzer and indicator lamp. Housed in Portable Transit Case 12in. x 9in. x 7 1/2 in., 15/- each. Postage 4/6.

TAPE DECKS
Truvox Tape Deck Mark III. New and unused in maker's carton, 2-speed, 3 1/2 and 7 1/2, takes standard 7in. spools, twin track, high impedance heads, response 50-10,000 c.p.s. £14.19.6. Carriage & insurance 10/6. Full instruction and circuit diagram included with each Deck.

Collaro Mark IV Tape Transcriber, 3-speeds, 3 1/2, 7 1/2 and 15in. per sec. 4 heads, two "Record/Play-back" and two "Erase" heads are sited on two different levels and head wear thus halved for any given length of track. Frequency range 30 to 10,000 c.p.s. £15.15.0. Carriage & insurance 10/6.

PUBLICATIONS

Radio Valve Data (Sixth Edition), compiled by Wireless World. Characterisation of 3,000 valves, Transistors, Rectifiers and Cathode ray tubes. 5/-, post 4d.

"Wireless World" Guide to Broadcasting Stations, L. & M. wave European Stations, V.H.F. Sound Transmitters in the U.K., Short-wave Stations of the World. Price 2/6, post 4d.

SPECIAL OFFER I.T.V. AERIAL
4 element I.T.V. Outdoor aerial by well-known manufacturer, suitable for Channels 8, 9 and 10. Array only 19/6, cranked arm available, 6/6 extra. Carriage and packing 4/6.

ACOS MICROPHONES

Acos Mic 39-1. Crystal Stick Microphone for use as a hand desk stand or floor stand unit for high quality recording, broadcasting and public address work. LIST PRICE £5.5.0. OUR PRICE 39/6. With Stand, 47/6. Postage 1/6.

Acos Mis Type 33-1. Crystal hand or table microphone. Flat response for 7,000 c.p.s. Omni-directional. Suitable for tape recording, etc. Dark brown plastic case. Brand new in maker's cartons. List 50/- OUR PRICE 29/6. Postage 1/6.

TERMS: Cash with order or C.O.D. Postage and Packing charges extra, as follows: Orders value 10/- add 1/-; 20/- add 1/6; 40/- add 2/-; £5 add 3/- unless otherwise stated. Minimum C.O.D. fee and postage 3/-. For full terms of business see inside cover of our catalogue. Personal shoppers 9 a.m. to 5 p.m. Mon. to Friday. Saturday 10 a.m. to 1 p.m.



103 LEEDS TERRACE
WINTOUN STREET
LEEDS 7

Visit the City's new acoustically designed
HI-FI Centre

COME AND HEAR THE LEADING MAKES IN AMPLIFIERS AND TUNERS

AMPLIFIERS BY VERDIK ARMSTRONG ROGERS DULCI	GOODSELL QUAD LEAK W.B., etc.	V.H.F. TUNERS BY ARMSTRONG LEAK QUAD ROGERS, etc.	T.S.L. DULCI GOODSELL	HI-FI SPEAKERS BY GOODMAN PLESSEY WHARFEDALE LORENZ, etc.	W.B. T.S.L. G.E.C.
--	---	--	------------------------------------	--	---------------------------------

LIMITED NUMBER ONLY AT THIS AMAZING PRICE

Easy to build 6 transistor and diode pocket superhet. Long and med. wavebands; printed circuit; matched Mullard transistors; built-in HiQ Ferrite Aerial; P/pull output; circuit and point-to-point layout diagrams. Circuit Line Up: Mixer stage, 2-I.F. stages, Germanium detector, A.F. driver and p/pull output stages, 3 in. loudspeaker.

ALL COMPONENTS COMPLETE LESS CABINET AND BATTERIES AT THE SPECIAL PRICE OF £7.19.6

Post & Pkg. 2/6.
 All parts sold separately.

THREE ASTOUNDING T.V. TUBE OFFERS

All brand new in famous maker's cartons.

(1) 17 in. rectangular aluminised 6.3 HTRS .3A. current; max. anode voltage 16 kV. Usual price £17.5.0. **OUR PRICE £9.19.6.** Crating & carr. 15/-.



(2) Ferranti T12/44 and T12/54G 12 in. magnetic white fluorescence; 4 v. heater; max. anode 10 kV. As used in many T.V. receivers. Original price £17.5.0. Our price **£4.19.6.** Crating & Carr. 12/6.

(3) Ferranti 9in. Tube round white fluorescence, 4 v. heater, max anode voltage 7 kV. Our price **£2.19.6.** Crating & carr. 11/6.

A FEW ONLY

Brand new Goldring Bantam Magnetic light-weight pick-up. 9/6. Post & pkg. 2/6.

Electronics (FLEET ST.) Ltd

Dept. E, 152/3, FLEET STREET, LONDON, E.C.4.
 Business Hours: Weekdays 9-6. Saturdays 9-1. Tel.: FLEet 2833

Now... in your own home, LEARN

RADIO - TELEVISION - ELECTRONICS

NO PREVIOUS TECHNICAL EXPERIENCE NEEDED!
PRACTICAL EQUIPMENT (INCLUDING TOOLS) GIVES YOU A REAL LABORATORY TRAINING

"The trained electronics engineer has a great career ahead of him."

Valuable **FREE** Book shows how E.M.I. Institutes School of Electronics can train you for today's wonderful opportunities.

Radio, Television and Electronics provide an exciting field for the trained man—high pay, a prosperous future—or if you prefer it—independence in your own business. If you are trained at home by E.M.I. you will be in the hands of *specialists* who know the quickest way to prepare you for one of the fine jobs open to trained electronics-men. Whether you are a beginner or an advanced student with an examination in mind, E.M.I. Institutes School of Electronics has a Course exactly suited to your needs—with or without practical equipment—from electricity and magnetism to automation techniques.

- Practical Radio
- Radio & Television Servicing
- Practical Electronics
- Electronics Engineering Automation
- Basic Practical and Theoretic Courses for beginners in Radio, T.V., Electronics, Etc.
- A.M. Brit. I.R.E., City & Guilds Radio Amateurs Exam.
- R.T.E.B. Certificate
- P.M.G. Certificate
- "NO PASS—NO FEE"

We Definitely Guarantee "NO PASS—NO FEE"

Full details of the Courses, Practical Equipment, convenient monthly payments, our Employment and Advisory Depts., and much other helpful information is given in our Guide to Careers in Electronics. Write for your copy today. There is no obligation and the book will be sent to you quite free of charge.

FREE BOOK - POST NOW!

Please send me a free copy of your Guide to Careers in Electronics.

NAME

ADDRESS

Subject or Exam



E.M.I. INSTITUTES

SCHOOL OF ELECTRONICS

The Specialist Electronics Division of the British Institute of Engineering Technology.
 (DEPT. SE/21), COLLEGE HOUSE, 29-31, WRIGHT'S LANE, KENSINGTON, LONDON, W.8.

Brand new, individually checked and guaranteed

VALVES

AC/DD	2/6	DET20	2/6	EL32	3/9
AC/HL	2/6	DH76	4/9	EL41	8/3
AC/P	2/6	DLS10	4/6	EL84	8/6
AC/PI	2/6	E1148	2/-	EL91	7/6
AC6/PEN	5/-	EA50	1/6	EY91	4/6
AC/SP3	4/6	EAC91	4/6	EZ40	7/6
AR6	2/6	EB34	1/6	EZ80	7/-
AR8	5/-	EBC33	6/-	FA15	4/-
ARDD5	2/-	EC52	3/9	FW4/500	8/-
ARP3	3/-	EC54	3/6	H30	3/6
ARP4	3/6	ECC32	4/-	H63	5/-
ARP12	2/9	ECC81	5/10	HP4101	6/-
ARP21	5/6	ECC82	6/9	KBC32	5/-
ARP24	3/6	ECC83	6/9	KF35	5/-
ARP34	4/6	ECC84	7/9	KT30	7/-
ATP4	2/9	ECC91	4/-	KT31	8/-
ATP7	5/6	ECL80	10/3	KT33C	7/-
B30	3/6	EF8	6/-	KT241	9/-
BL63	6/-	EF22	7/3	KTW63	6/6
D41	3/3	EF36	3/6	L30	4/-
D42	4/-	EF39	4/9	MH4	4/-
D77	4/3	EF50	3/-	MH40	6/6
DA30	20/-	EF55	6/-	MH41	6/6
DD41	4/6	EF80	6/9	MHLD6	4/6
DD620	4/6	EF85	6/10	ML4	4/6
DETS	20/-	EF89	8/9	ML6	6/-
DET18	30/-	EF91	4/10	MS/PEN	6/-
DET19	2/6	EF92	5/-	MS/PENB	6/-

N34	8/-	SP41	2/9	4A1	4/6	6L6GA	6/6	35Z4GT	7/-	930	8/-
NR15A	3/-	SP61	2/9	4D1	2/6	6L34	4/6	39/44	6/-	554	2/-
NR61	7/-	SU2150A	4/9	5U4G	6/-	6N7GT	7/-	41FP	1/9	956	2/9
NT37		TT11	3/-	5Y3GT	6/9	6Q7G	6/3	524G	8/-	1619	6/-
(4033A)	14/-	U18	6/-	5Z3	8/6	6SA7	6/9	53A	3/-	1625	6/-
OD3	6/-	UU4	4/6	5Z4G	8/-	6SC7GT	7/-	58	6/-	1626	4/6
OZ4	5/-	V2D33B	8/-	6A6	5/-	6SG7	5/-	59	6/-	1629	4/6
OZ4A	5/-	VP23	5/-	6AB7	5/-	6SH7	5/-	71A	4/6	4242A	6/-
P61	2/6	VR99	8/-	6AC7	5/-	6SJ7	6/9	77	6/-	7193	1/9
PCC84	8/-	VR150/30	6/-	6AG5	4/6	6SK7	5/6	82	8/-	7475	5/-
PCC85	8/-	VS110	4/-	6AK6	7/6	6SL7GT	6/9	83	12/-	8010AR	22/6
PEN25	4/6	VT25	8/6	6AM5	5/-	6SN7GT	4/6	83V	12/-	8020	6/-
PEN46	5/9	W31	7/-	6AM6	6/3	6SQ7	6/6	84	12/6	9001	5/-
PEN141	4/-	W42	7/-	6B4G	4/6	6SS7	8/-	89	6/-	9003	5/6
PEN220A		Y66	8/-	6B8	5/6	6V6G	5/6	210LF	3/-	9004	4/-
	3/-	Z31	6/-	6B8G	2/6	6X5GT	5/6	210VPT	3/-	9006	4/-
PEN1340		IA3	3/6	6C4	4/-	6D2	2/6	217C	17/6		
	6/-	IA5GT	5/-	6C5	6/-	9D2	3/-	220VSG	3/-		
PENDU/		IB23	11/-	6C6	4/6	12A6	5/-	350B	8/-		
1360	9/6	IB24	11/-	6C8G	5/-	12AH7	7/-	446A	14/-		
PL82	8/3	IB26	11/-	6F6	7/-	12C8	7/6	446B	14/-	3BP1	25/-
PL83	9/-	IB32	10/-	6FBG	6/6	12E1	22/6	705A	17/6	5CP1	42/6
PM4DX	3/-	ID8GT	6/-	6F12	5/-	12H6	2/6	715B	97/6	5FP7	45/-
PT25H	7/6	IL4	4/-	6G6G	3/-	12J5GT	3/6	717A	8/6	VCR517	10/-
PY82	8/-	ILD5	3/6	6H6M	2/3	12S7G	6/6	801	6/-		
QP21	6/-	IR5	6/9	6H6GT	1/9	12SH7	4/9	803	22/6		
QP25	5/3	IS5	6/-	6J5	3/6	12SJ7	6/-	805	30/-		
RG1-240a		IT4	4/-	6J6	4/3	12SK7	5/-	807AMER			
	17/6	2A3	8/-	6K6GT	6/6	12SL7	7/-		5/3		
RG3-250		2A6	7/-	6K7G	2/3	12SR7	6/-	807BR	3/9		
	17/6	2C34	2/6	6K7GT	5/3	15D2	6/-	813	70/-		
RG4-1250		2D4A	4/-	6K8G	6/6	15E	8/-	815	80/-	723AB	52/6
		2X2	4/-	6K8GT	8/-	15R	7/6	833A	£17.10	726A	27/6
RK34	2/6	3A4	6/6	6L5G	6/-	19E2	5/-	843	7/6	VX7110	15/-
SP4B	7/6	3E29	3/-	6L6	10/-	28D7	8/-	866A	10/-	WL417A	15/-
SP13C	4/6	(829B)	75/-	6L6G	6/6	35T	30/-	872A	35/-	WL417A	15/-

All U.K. Orders below 10/-. P. & P. 1/-; over 10/-. 1/6; Orders over £2 P. & P. free. Overseas Postage extra at cost.

Brand new original spare parts for AR88 Receivers. Please see advert. Dec. issue.

High Resistance Headphones. 4,000 ohms. Brand new, ex W.D. boxed. 10/6 per pair. P. & P. 1/-.

Low Resistance Headphones, brand new, type CLR, 5/-.

Microphone Transformers. Balanced input 30 or 250 ohms. U.S.A. manufacture, 7/6. P. & P. 1/6.

Projection Lamps, Osram. 250 v. 500 w. meas. of glass bulb dia. 2 1/2 in., length 4 in., 7/6 P. & P. 2/-.

813, Ceramic Valveholders, 3/- each. P. & P. 1/6.

Marconi Signal Generator. TFI44G: 85 kc/s, 25 mc/s. Made up to new standard, £70, delivered free.

Vacuum Condenser 32,000 V. 50 pF 25/-.

Telephone Handset, Standard G.P.O. type. New, 10/-. P. & P. 1/-.

Transceivers Type 68T. 3-5 mc/s. together with aerial rods, microphones, H.R. headphones, key. In full working order. £6.15.0. P. & P. 5/-.

Johnson's Transmitting Variable Condensers. 500 pF. 2,000 v., 17/6. 501 pF. 3,500 v., 22/6. Both brand new. P. & P. 2/-.

Modulation Transformers (U.S.A. Collins), primary imp. 6,000 ohms. C.T., secondary 6,000 ohms, 20 W., 9/6 each. Post free.

Carbon Inset Microphone, G.P.O. Type, 2/6. P. & P. 1/-.

Complete Installation ILS. Consist^o of transmitter, receiver, control unit, aerial, plugs, etc., £22.10.0 post free.

Loud Hailer. Heavy duty. 20 w. 15 ohms, completely covered for outside use. 1 1/2 in. dia. £5.15.0. P. & P. 7/6.

Accumulators. 6 v. 100/125 amp-hours in steel cases. Brand new, £5. P. & P. 15/-.

Telescopic Aerial Masts. 7 sections, total 11 yards. Immediate erection. £4.10.0 each or £8 per pair. Post free.

Light Headgear Assembly. Ideal for mobile use. Headphones 600 ohms carbon microphone. 18/-. P. & P. 3/-.

Signal Generator Type TS. I4/AP. 3,200-3,370 mc/s. Fully guaranteed. £85.

Output Power Metre Type TS. 118 R.F. Frequency 20-75 mc/s., Power 5,500 w. Full working—with manual, £45.

Miniature Lead Acid Accumulator, 2 v., 1.5 amp. 1 Hour at the 10 Hour Rate, size 4 in. x 1 1/2 in. Price 6/- P. & P. 2/-.

P. C. RADIO LTD.
170 GOLDHAWK RD.,
W.12 SHEPHERDS BUSH 4946

PERSONAL CALLERS WELCOME

PETHERICK'S RADIO SUPPLIES
Radio Component Specialist,
22, HIGH STREET, BIDEFORD, NORTH DEVON

TRANSISTORS from 6/9.
Red Spot, 6/9; Yellow/Green, 6/9; White Spot, 10/6; Red/Yellow, 14/-; V6/R2 Gold Top, 18/-

EDISWAY TRANSISTORS, X.A.104, 18/-; X.A.103, 15/-; X.B.104, 10/-.

CRYSTAL SET COIL, M. & L. with circuit, 2/6 each.

DIRR2 DUAL RANGE COIL with reaction winding, boxed with circuits, 4/-.

CRYSTAL DIODES, 1/- each; 10/- doz.

REACTION CONDENSERS. .0003 or .0005, 4/- each.

MINIATURE .0005 reaction or tuning, 4/- each.

2 mfd. 150 v. electrolytics, 1/6 each.

VARI-LOOPSTICK M.W. COIL with TRANSISTOR SET CIRCUIT, 4/6 each.

HEADPHONES, designed for crystal or transistor set use, 14/- pair.

All sent Post Free in U.K.

The A.R.R.L. Radio Amateurs' Handbook, 1959, 32/6. Postage 1/9.

Practical Radio Inside Out, by Easterling, 3/6. Postage 6d.

T.V. Servicing, Vol. 4, by Patchett, 7/6. Postage 6d.

British Transistor Manual, by Bradley, 12/6. Postage 1/-.

Jason F.M. Tuners, by Blundell, 2/6. Postage 6d.

Practical Transistor Receivers, Book I, by Sinclair, 5/- Postage 6d.

T.V. Fault Finding, by Radio Constructor, 5/- Postage 6d.

Radio Circuits, 4th Edition, by Miller, 15/- Postage 1/-.

Guide to Broadcasting Stations, 1959, 2/6. Postage 6d.

UNIVERSAL BOOK CO.
12 Little Newport Street, London, W.C.2
(adjoining Lisle Street)

SHORT WAVE KITS

H.A.C. were the original suppliers of SHORT-WAVE RECEIVER KITS for the amateur. Over 10,000 satisfied customers.

PRICES FROM 25/- TO 77/-.


POST THIS COUPON NOW!
To:- H. A. C. Short-Wave Products, 11, Old Bond Street, London, W.1.
Please send me FREE and without obligation your 1959 literature.

NAME

ADDRESS

Hi-Fi Snip
Infinite Wall Baffle

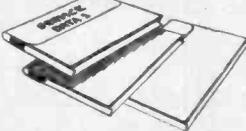Nicely veneered and polished. Corner fitting (attaches to picture rail). Takes up no floor space. Gives really fantastic results with only low-priced 8in. speaker. **File-thing for tweeter.** Only 45/- each. carriage and insurance 3/6.



T.V. Service Sheets

200 sheets covering most popular post-war televisions by leading makers—Cossor, Ekco, Ferguson, Pye, etc. £2 post free. **PREVIOUS PURCHASERS OF THESE SHEETS PLEASE NOTE: WE CAN SUPPLY SHEETS Nos. 100-200, £1, or 150-200, 10/-.**

Tube Tester and Re-Activator

We can supply all the main components for making this unit which will not only test Cathode Ray Tubes but also will re-activate them, supplied complete with full instructions. Price £3, plus 2/6 post and ins.

Miniature Microphone

American made. Dynamic type. real bargain at 2/6, plus 6d. postage.



Speaker Bargain



12in. Hi-Fidelity loudspeaker. High flux. Permanent magnet type with standard 3 ohm speech coil. Will handle up to 12 watts. Brand new by famous maker. Price 32/6, plus 3/6 post and insurance.

Don't Stumble in the Dark



Install 2-way switches. Our outfit comprises: 30 yds. Multi-core cable, two 2-way switches, two wood blocks. Full instructions, 9/6 each, post and insurance 2/6.

Assure your future

The ownership of a good instrument has been the turning point in many a famous career. You can own the latest Pullin Series 100 Test Set which is undoubtedly a most useful instrument by a firm long famous for fine instruments, entirely redesigned it has a square movement with diacon plastic cover, this makes for a brighter, more readable scale, extra scale length and wider angle of vision. With the test set is included a pair of combined test prods and crocodile clips also a stand for inclining the meter at the best reading positions. **Ranges A.C. Volts: 0-10, 0-25, 0-100, 0-250, 0-500, 0-1,000, ditto D.C. A.C. current 0-100 mA. D.C. Current 0-25, 0-10, 0-100, 0-500 mA. Resistance: 0-1 M and 0-10 K. All at 10,000 ohms per volts. Price £12, 7/6 or 10/- deposit and 21 fortnightly payments of 10/-.** (This figure includes insurance for 12 months.) **Non-callers add 5/- carr. and insurance. FREE GIFT.**—All purchasers of the above item this month will receive Range Extender scale and data which add capacity 2Pf-1mFd., in two ranges. Inductance 0-100 henrys, etc., etc.



Unique Opportunity to build Fine Transistor Set

Constructor's parcel: to build Pocket 6 Transistor Set as currently being sold at £17.10. Parcel comprises Motified two-tone cabinet as illustrated, tuning dial, two gang tuning condenser, combined bakelite chassis/printed circuit and easy to follow circuit. Costing value 57/6—offered while supplies last at only 25/6, plus 2/6 post. Suitable for your own circuit or to build original circuit. All parts available at highly competitive prices. Do not miss the tremendous bargain.




Special introductory offer



Introducing our new 40" fluorescent white enamel. Suitable for chain slipping or direct fixing, uses fully compounded choke ballast and radio suppressed starter. Offered at a special price this month to introduce it, namely 39/6, complete with tube. Carriage up to 150 miles 5/6; up to 250 miles, 7/6.

Dulci AM/FM Radiogram Chassis

Chassis Model H.3. This has three wavebands, F.M. 87-101 Mc/s., Medium Wave 187-540 metres and Long Wave 1,000-2,000 metres, uses 7 of the latest miniature valves and built-in ferrite aerial. "Why not modernise your Radiogram, get the best from modern records with this hi-fi 4 watt output chassis." Price, £19.17.6 or £2 down and 20 fortnightly payments of £1.0.6. Hi-Fi Model H4 PP. £27.16.6 or £2.16.6 down and 26 fortnightly payments of £1.2.0. (Note: Hire-purchase figures include insurance for 12 months.)

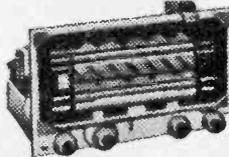

B.B.C. Television Transistor Set. All parts available—total cost, including two transistors, with copy of circuit diagram and instructions. Postage 2/- extra.

FOR ADDRESS SEE NEXT PAGE

Band III Converters



fine tuner, contrast control, condensers and resistors. (Metal case available as an extra). Price only 19/6, plus 2/6 post and insurance. Data free with parts or available separately. 1/6. Please send two more kits, the one you sent last week is performing magnificently. We receive this sort of letter every day of the week, so if you have hesitated because you thought our kits too cheap you need hesitate no longer.

Cabinet Snip



This fine cabinet as illustrated but less control knobs is available this month at a special snip price of 12/6, plus 3/6 post and insurance. Size is 13 1/2in. x 8in. x 4in. and it is nicely covered in two-tone I.C.I. fabric.


RI155 for Spares




These are less values but otherwise reasonably complete—ideal for spares prices £2 to £4 depending on condition—carriage 7/6.

Morganite Potentiometers

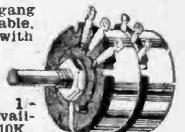Single and 2-gang types available, standard size with good length spindle, all boxed. Single types 1- each, values available: 5K., 10K., 25K., 50K1., 100K., 250K., 1 meg., 2 meg. Gang type 3/- each—values available: 5K. + 5K., 100K. + 100K., 1 meg. + 1 meg., 2 meg. + 2 meg.



LAST FEW

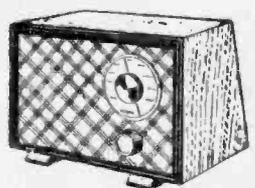

The Skysearcher

This is a 2-valve plus-metal receiver set useful as an educational set for beginners, also makes a fine second set for the bedroom, workshop, etc. All parts, less cabinet, chassis and speaker 19/6. Post and ins. 2/6. Data free with parts or available separately. 1/6. 3 valve battery version also available at the same price.

Bargains

Install those extra points.—3.029 twin flat T.R.S. cable. Big purchase enables us to sell this at 45/- per 100 yds., carriage 3/6.

Low Resistance Head Phones. Ideal crystal sets, etc., 7/6, plus 2/6.

Goodmans Multi-Ratio Output Transformer. 6 watt, 6 ratios : from 12-1 to 72-1. Centre tapped for push/pull, 7/6, plus 1/-.

Ditto, unbranded. 6/6, post 1/-.

Cold Cathode Valve CV413. Voltage regulator or trigger switch—unused but ex-equipment, 2/- each.

Tak Panels. Ideal for constructors, experimental circuits, etc., 3 of each of 12 different types, 5/-, post 1/6.

Slidlok Panel Mounting Fuses with Carrier. 5 amp 2/- each, 15 amp 2/6 each.

Belling Lee 2BA fully insulated terminals for mounting through metal panels, 2/- each.

Terminal Heads, insulated 4BA, 2/- doz.

Twin Twisted V.L.R. Flex, 7/-, .006 (14/36 equiv.), 17/6 100 yd. coil.

Mains Lead. 4 core rubber insulated and circular, 12/- doz.

Has prepared ends suitable converter or similar. 6 ft. long 9d. each, 7/6 doz.

Metal Rectifier. Equivalent of RM5-250 mA., 250 v., 12/6.

Welding Transformer. 12v-50 amp continuous rating — intermittent rating for spot welding—exceeds 2,000 amps. 45/-, carriage and packing 5/-.

6ft. Unbreakable Mains Lead. Type of lead fitted to electric razors, makes fine lead for test meters and any other devices where subject to continuous bending. Twin figure eight construction, soft cream P.V.C. covered. Normally costs 2/- per yard—we offer three leads for 2/-, 1 mfd 350 v. Small tubular metal cased condensers made by Dubilier, 2/6 doz.

50 Assorted Resistors. Well mixed and useful values 1 and 1/2 watt, 5/- for 50.

Ditto, but 1 watt, 6/6 for 50.

Mains Transformer. Standard 230 v., input 250-0-250 at 80 mA., 6.3 v. at 5 A., 12/6.

Toggle Switch. Standard metal body, type with round dolly, fixing ring and on/off indicating plate, 1/3 or 12/- doz.

Metal Rectifier. 250 v. 60-80 milliamps. ideal for mains set or instrument or to replace that expensive valve, 4/6.

Screened Cable. Rubber covered flexible with metal braiding, ideal for microphone or gramophone extensions. 4d. per yard, 30/- per 100 yds.

Neon Lamps. midget wire ended. Ideal for making mains tester or for any of the dozen-and-one applications to which a neon can be put. New 2/-, Ex-equipment, 1/6.

Instrument Transformer. Input 200-230 v., output 6.3 v. at 3/4 amps, and two separate 85 v. 10 milliamp windings which can be joined in series or parallel, 8/6, plus 1/6 post & packing.

3in. Meter Moving Coil, flush mounting, really beautifully made by G.C.E. Two types available 500-0-500 microamp and 1 milliamp f.s.d. 37/6, plus 2/- p. & i.

Winking Eye, telephone or circuit indicator, 5/-.

Parneko (Neptune Series) "C" Core Transformers (potted).—Model No. 6000/53 15 watt output transformer 6,500 ohms centre tapped, primary, secondary 2.4 ohms centre tapped. Price 27/6.

Model No. 6000/85—mains transformer, primary standard 50 cycle mains 200-240 volt (5 volt tapping) and 115 volt.

Secondary 325-0-325 at 250 mA., 335-0-335 at 180 mA. Price 25 each.

**Virtually A Transcription Unit
Philips AG2009 Record Player**

Philips AG2009 Record Player, a modestly priced 4-speed unit with many outstanding features, is ideal for the enthusiast who is assembling his own equipment or modernising an older installation. The pick-up arm is wired for stereo and the Philips stereo head is available as an optional extra.

Eddy Current Brake gives 2% fine adjustment on all four speeds. Continuously variable pick-up playing weight (2-12 gms.).

Supplied with Philips Hi-Fi crystal head type AG3019, for microgroove and 78 r.p.m.

Frequency response 30-15,000 c/s.

Auto-stop and automatic release of idler wheel.

Pick-up lifting and lowering device.

Individually balanced heavy turntable.

Wow and rumble of a low order.

Muting switch fitted.

Can be used with any amplifier or radio set.

Mains voltage range : 110-127 v. and 200-240 v., A.C.—50 cycles.

Complete with monaural pick-up, £10.0.0., or £1 deposit and 22 fortnightly payments of 10/-, carriage, etc., 5/-.

Available also with stereo head, diamond or sapphire stylus. Prices on request.




**Navigation
Compass**

In carrying case but less fluid, may be slightly damaged. 4/6, plus 2/6.



Suppressor Condenser

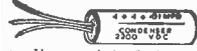
Stop your rill or other appliances interfering with your or your neighbours' radio or television. Simple instructions given. 1/6 each. 12/- dozen.



TV Masks

Latest type grey crystallate
14in., 10/-; 17in., 12/-
Plus 1/- post.

Rectifier Bargains

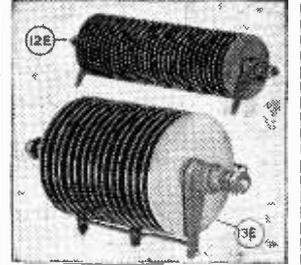

Selenium rectifier type 12, 500 v. 1 A. half-wave, easily rebuilt into full wave or multiple type, contains 30 35 mm. discs. Price 8/6, plus 1/6 post. Type 13, 36 volt 3 amp easily rebuilt into six full wave charger rectifiers suitable for 6 or 12 volt batteries at 3 amps, contains 24 84 mm. discs. Real bargain at 19/6, plus 1/6 post.

Electrical Accessories

We carry good stocks of most accessories at competitive prices.

**5 Amp. Wall
Switches**




By Hicraft, bakelite, positive action, oblong brown 1 way or 2 way, 1/- each.

Sockets Hicraft

Flush type for skirting, 5 amp, 3-pin shuttered, 1/3 each; ditto with switch, 2/3 each.



This Month's Snip

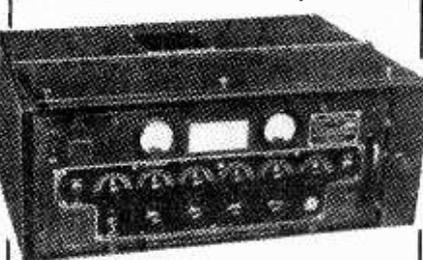

American Receiver C64608

This is a 12-valve receiver originally designed for military operation on the 60-80 mc band. One stage of R.F. and three stages of I.F. with additional stages for noise suppression and A.V.C. make this an extremely versatile receiver, also crystal in oscillator provides highest stability. On the front panel are all controls and moving coil input and output meters. Complete with its own power supplies, these, however, are intended to operate on American voltage 115. So with each receiver we supply a step down transformer. A limited quantity only of these offered at the extremely low price of £6.10.0 plus 12/6 carriage and packing. Size approx. 26in. x 9in. x 17in. Note: these sets are unused but have been in store for some years and may therefore require servicing before being put into operation. At the low price charged we cannot test these nor do we give any guarantee. Complete with valves and one crystal. Circuit diagram and technical notes free with equipment or separately price 2/6.

All items advertised can be obtained from the following Companies. If ordering by post, address your order to the Company nearest to you and please include postage.

Instrument Co.
6, High Street,
Thame, Oxon.
Phone : THAME 182.

Electronics (Ruislip), Ltd.
42-46, Windmill Hill,
Ruislip, Middx.
Phone : RUISLIP 5780.
Half day Wednesday.

Electronics (Croydon), Ltd.
268, London Road,
Croydon.
Phone : CRO 6558.
Half day Wednesday

Electronics (Finsbury Park), Ltd.
29, Stroud Green Rd.,
Finsbury Park, N.4.
Phone : ARCHWAY 1049.
Half day Thursday.




EASY TO BUY . . . (delivered to your door . . . post free). **FASCINATING AND SO SIMPLE TO BUILD** (even for beginners). **PROFESSIONAL IN PERFORMANCE AND APPEARANCE** . . . **MILLIONS OF HEATHKIT** "build-it-yourself" models are in regular use throughout the world because they are so good and such value for money. **THEY'LL SAVE YOU POUNDS!**



MODEL UXR-1

MODEL UXR-1 TRANSISTOR PORTABLE . . . £16.18.6

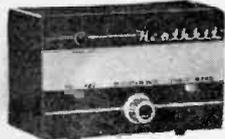This Dual-wave, 6 transistor portable radio, strikingly styled in handsome solid leather case, is universally admired. The tone is rich and brilliant and it performs well everywhere, including in a car. Easily built in 6 hours.



MODEL USP-1

MODEL C-3U R/C BRIDGE £7.19.6

Measures Capacitance, 10 pF (0.00001 μ F) to 1,000 μ F; Power Factor; Resistance, 100 Ω to 5 M Ω , and indicates leakage. Automatic Discharge Safety-Switch.

MODEL AG-9U AUDIO SIGNAL GENERATOR £19.3.0

10 c/s to 100 kc/s. Sine-Wave output 10 V f.s.d. down to 3 mV. f.s.d. Less than 0.1% distortion (20 c/s to 20 kc/s). Decade frequency selection. Decibel ranges, -60 to +22. 1% precision resistors.

MODEL USP-1 HI-FI STEREO BOOSTER . . . £5.19.6

Enables low-output pick-ups (e.g., Decca fess) tape heads and microphones to load fully amplifiers of medium sensitivity.



MODEL S-33

MODEL O-12U 5in. OSCILLOSCOPE £34.15.0

This fine general purpose 'scope has "Y" sensitivity of 10 mV/cm and covers 3 c/s to over 5 Mc/s. Rise time is 0.08 μ secs. or less. Timebase 10 c/s to 500 Kc/s in 5 steps. Electronically stabilised. Voltage calibrator.

MODEL S-33 HI-FI 6 W. STEREO AMPLIFIER £11.8.0

World's best value in low-price Stereo. 0.3% distortion at 2.5 W./chnl. Ideal for average room.



MODEL S-88

MODEL S-88 HI-FI 16W. STEREO AMPLIFIER £25.5.6

World's finest 16 Watt Stereo amplifier regardless of price. 0.1% dist. at 6 W./chnl. The attractively styled S-88 has many excellent features.

MODEL V-7A VALVE VOLTMETER £13

World's most popular VVM. Measures volts, ohms and decibels. Sensitivity 7,333,333 ohms per Volt.



MODEL UJR-1

MODEL SSU-1 HI-FI SPEAKER SYSTEM . . . £10.5.6

Legs £1.7.0 extra. Ideal for Stereo in average living-room where cost must be low. Twin speakers.

MODEL DX-40U "HAM" TRANSMITTER . £29.10.0

40 Watts to aerial. 75 W. C.W. 60 W. pk. C.C. 'phone. Provision for VFO. Designed by "Hams" for "Hams."



MODEL SSU-1

MODEL UJR-1 TRANSISTOR RADIO £2.16.6


Ideal for youngsters. Novel circuit gets lots of stations. Additional amplifier stage, 16/6 extra.



MODEL C-3U



MODEL AG-9U

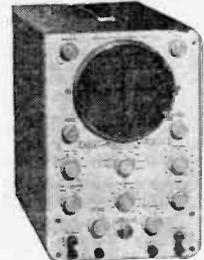

MODEL O-12U



MODEL V-7A



MODEL DX-40U

ALL PRICES INCLUDE FREE DELIVERY IN THE U.K. (AND ANY P.T.). DEFERRED TERMS ARE AVAILABLE

★ IF YOU ARE NOT ALREADY ON OUR MAILING LIST, WHY NOT SEND FOR OUR FREE CATALOGUE . . . NOW?

Without obligation please send me FREE CATALOGUE (Tick here)

Full details of model(s)

NAME.....
(BLOCK CAPITALS)
ADDRESS.....
.....

DAYSTROM LTD., DEPT. PW. 7, GLOUCESTER, ENGLAND
A member of the Daystrom Group, manufacturers of THE LARGEST-SELLING ELECTRONIC KITS IN THE WORLD.

PRACTICAL WIRELESS

27th YEAR
OF ISSUE

EVERY MONTH
VOL. XXXV, No. 631, JULY 1959
COMMENTS OF THE MONTH

BY THE EDITOR

NATIONAL RADIO SHOW

THIS year's National Radio and Television Exhibition will be held at Earls Court from August 26th to September 5th. The newly-formed Radio Industry Exhibitions Company is organising the event, with the aid of a reconstituted organising committee. H.M. The Queen has again honoured the radio industry by becoming Patron of the Exhibition.

The ground floor arrangements will be much the same as last year, with the large commercial stands in the well of the Hall and the offices and demonstration rooms around the perimeter. The Audio Hall will be on the first floor in the Philbeach wing. It will be considerably larger than it was last year.

Normally, it is impossible to demonstrate portable radio receivers at the Exhibition by virtue of the construction of the Earls Court building, but if there is sufficient demand, the organisers will arrange for the installation of a cable system carrying amplified radio signals of suitable wavelengths. A wire loop at Stands requiring the service would provide radiation adequate for good reception. TV signals will be piped to Stands as before, and demonstrations of record-players, tape-recorders, etc., will be permitted, provided that they are not an annoyance to neighbouring stands.

In view of the popularity of the Radio Show with the trade, the amateur and the public alike, we think that the organisers of smaller exhibitions should consider making their shows part of the National Show. After all, hotels are not really the best places for serious demonstrations.

A BEGINNERS' TEST-METER

IN the centre pages of this issue will be found the first article of a series describing the building of a multi-range test-meter. In this issue, the meter movement is discussed and a simple 0-10V range is wired. In the next article, parts will be added to make a multi-range D.C. voltmeter reading from 0 to 1,000V. In subsequent articles, the instrument will be progressively increased in scope until it may be used on A.C. as well as D.C. and also for resistance measurements.

The illustration on the cover shows the meter in three of the stages of construction; in the foreground, wiring of the multi-range D.C. voltmeter is being completed. Behind this, on the left, all the D.C. ranges have been incorporated and the meter reads 0-1,000V and 0-1A. On the right, the meter is shown with A.C. and resistance ranges added to complete the construction. The graph on the side of the stand is for resistance readings.

The series is intended for the beginner and, accordingly, very little knowledge is assumed. The construction proceeds in simple stages and each of these is explained with clear text and suitable illustrations. However, the meter is suitable not only for the beginner, but also for the more experienced constructor who is in need of less detail than is given and who must, perforce, bear with the writer if the explanations seem somewhat laboured or unnecessary.

Our next issue, dated August, will be published on July 7th

Editorial and Advertisement Offices :
PRACTICAL WIRELESS
George Newnes, Ltd., Tower House,
Southampton Street, Strand, W.C.2.

© George Newnes Ltd., 1959.

Phone : Temple Bar 4363.
Telegrams : Newnes, Rand, London.
Registered at the G.P.O. for trans-
mission by Canadian Magazine Post.

SUBSCRIPTION RATES

including postage for one year

Inland - - - 19s. per annum
Abroad - - - 17s. 6d. per annum
Canada - - - 16s. per annum


CONTENTS :

	Page
Editorial	371
Round the World of Wireless	372
A Twin Speaker Bass Reflex Cabinet	374
A Mixer Pre-Amp Unit	377
Basic Theory for the Constructor	379
Servicing Radio Receivers	381
On Your Wavelength	387
Improving Receiver Selectivity (Short Wave Section)	388
A Master Relay Unit	390
Crystal Heterodyne Frequency Meter	395
A Beginners' Test-meter	398
Resistor Wattages	402
Becoming an "Amateur"	405
An Experimental "Printed Circuit" Amplifier	409
News from the Clubs	413
An Intercom Amplifier	414
The "Gramdeck" Tape Recorder	418
News from the Trade	421
Open to Discussion	426

The Editor will be pleased to consider articles of a practical nature. Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed: The Editor PRACTICAL WIRELESS, George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Owing to the rapid progress in the design of wireless apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in PRACTICAL WIRELESS is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. PRACTICAL WIRELESS incorporates "Amateur Wireless."

ROUND THE WORLD OF WIRELESS

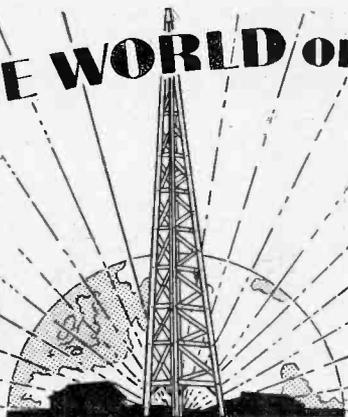

By "QUESTOR"

Broadcast Receiving Licences

THE following statement shows the approximate number of Broadcast Receiving Licences in force at the end of March, 1959, in respect of receiving stations situated within the various Postal Regions of England, Wales, Scotland and Northern Ireland. The numbers include licences issued to blind persons without payment.

Region	Total
London Postal...	905,526
Home Counties ...	896,057
Midland... ..	659,039
North Eastern ...	788,924
North Western...	619,316
South Western...	539,062
Wales and Border Counties...	332,161
Total England and Wales ...	4,740,085
Scotland	579,014
Northern Ireland ...	161,892
Grand Total	5,480,991

1959 Radio Hobbies Exhibition

THIS year's International Radio Hobbies Exhibition will open at the Royal Horticultural Society's Old Hall, Westminster, on Wednesday, 25th November and will close on Saturday, 28th November.

This year's show, which as always is organised for the R.S.G.B., will have "communications receivers of the world" as its main feature. Amateur television features will be well to the fore and kits for radio, television, etc., for the home constructor will be seen, many being shown for the first time.

A silver trophy will again be awarded for the most outstanding item of home constructed amateur equipment, and for the first time a silver trophy will be awarded for the outstanding piece of equipment manufactured industrially for radio amateur use on show at the exhibition.

New Managing Director for Marconi (South Africa) Ltd.

MR. HERMAN BAKER, for the past six years Far East Regional Manager for Marconi's Wireless Telegraph Company, has been appointed

tract for the Belgian Congo installations is valued at £60,000.

SHF Multichannel Link for Finland

THE Posts and Telegraphs Administration of Finland has placed a contract with Marconi's Wireless Telegraph Company for the supply of SHF multichannel radio equipment for the establishment of a two-way radio telephone link between Pori and Tampere, a distance of 104 km. Included in the order are aerials, feeders and spares.

The Finnish authorities decided in favour of multichannel radio equipment because of the mountainous nature of the terrain and the arctic conditions experienced. Under such circumstances, multichannel radio offers not only a large saving in initial outlay but also consider-


Managing Director of Marconi (South Africa) Ltd. He has been with Marconi's since 1930.

Pye I.L.S. for the Congo

IN view of the recent controversy about the relative merits of British and American Instrument Landing Systems it is interesting to note that the Government of the Belgian Congo have decided that Pye Instrument Landing Systems should be installed at both Elisabethville and Leopoldville airports.

Pye Telecommunications Ltd. of Cambridge have previously installed Instrument Landing Systems at Geneva International Airport, and at Prague and Moscow Airports and the Indian Air Force are at present installing their first Pye I.L.S. system.

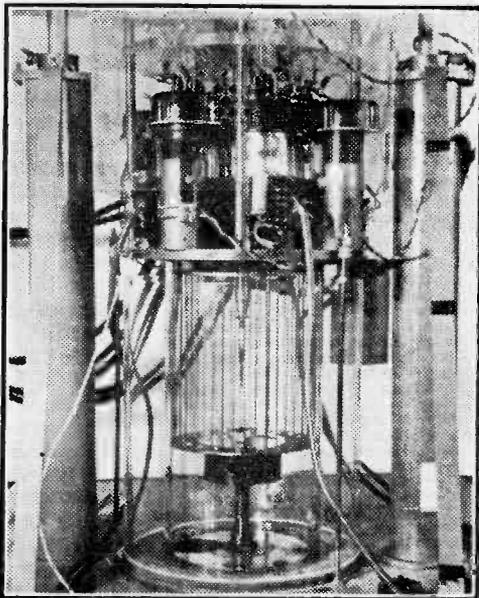One of the features of Pye I.L.S. most appreciated by airport administrators is the ease with which ground installation can be erected so that no expensive fitting parties from England are needed. The con-



This furnace for pulling crystals of silicon used in transistor manufacture was exhibited by A.E.I., Ltd., at the recent International Transistor Convention.

ably reduced maintenance costs.

The 104 km. between Pori and Tampere will be bridged by repeater stations at Kokemaki and Nohkuu.

Extension to Laboratories

TWO new laboratory blocks are being built on a site adjacent to the existing buildings of Mullard Research Laboratories at Salfords, Nr. Redhill, Surrey.

An extra 45,000 sq. ft. of floor space will be provided by the new buildings, which will consist of a three and a four storey block. They will house the electronics, telecommunications, transistor applications and television laboratories which have been built up during recent years, and parts of which have hitherto been operating in temporary buildings. It will also improve the facilities for the valve, semi-conductor and materials research activities.

BBC Engineering Appointment

THE BBC announces the appointment of Mr. E. W. Hayes, M.I.E.E., as Head of Planning and Installation Department in succession to Mr. A. N. Thomas, A.M.I.E.E., who has retired after 33 years service.

Mr. Hayes joined the Corporation in 1933 as an Assistant Maintenance Engineer and, after service at the Daventry transmitting station, where he became a Senior Maintenance Engineer and was engaged in development work on short-wave transmitting aerials, he was appointed Assistant Engineer-in-Charge of the Rampisham short-wave transmitting station in 1940 and of the Skelton transmitting station in 1942. In 1948 Mr. Hayes was appointed Resident Engineer, British Far Eastern Broadcasting Service, Singapore, where he was responsible for the building and later the operation of the high-power short-wave transmitting station at Tebrau. On his return to the United Kingdom in 1951 he was appointed Head of the Transmitter Equipment Section of the Planning and Installation Department.


More Radio Channels for Private Mobiles

DOUBLE the number of radio channels will become avail-

able for private mobile services as a result of approval by the Postmaster - General of the recommendations in the Third report of the Mobile Radio Committee. This committee advises him on matters affecting

been introduced by the Electronics Department of Ferranti Ltd.

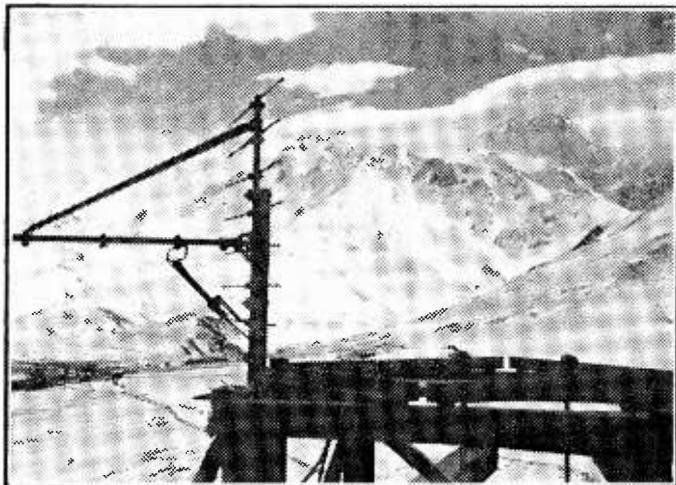These tubes, known as the CL60 and CL70 series, light up all over simultaneously in contrast to the behaviour of the normal cathode-ray tube.



View from the aerial tower at Kuhe Sefid which shows the mountains crossed by the chain of radio repeater stations. (See "Iranian Oil Pipeline Radio System.")

the users of V.H.F. mobile radio services.

This increase in radio channels in the lower V.H.F. band will be obtained by introducing equipment capable of operating on channels 25 kc/s wide instead of 50 kc/s. The use of narrower channels has been made possible by advances in equipment design by British manufacturers.

The new channel-spacing comes into force on June 1st, 1959. Thereafter, all new land-mobile schemes in the V.H.F. low band will have to use equipment meeting the 25 kc/s specification. With few exceptions, the new equipment standard will also apply to additions or replacements for existing systems. There is a "Five Year Plan" for the change-over of existing services to 25 kc/s equipment to be completed by June 1st, 1964.

New High-speed Flash Tube

A NEW range of high-speed cathode-ray flash tubes which produce a flash of the same order of intensity as a gas-filled electronic flash tube, such as is used in photography, has

Iranian Oil Pipeline Radio System

A FURTHER contract to the approximate value of £84,000 has been received by Marconi's Wireless Telegraph Co. Ltd. for the supply and installation of V.H.F. multi-channel radio equipment for the National Iranian Oil Company. In 1956 the oil company awarded a £350,000 contract to Marconi's for the supply and construction of a complete V.H.F. multi-channel radio system along the length of their 600 mile oil pipeline from Abadan to Teheran. The original scheme has now been working for some time and the new order represents an extension to the system.

The tower system is becoming very popular, as the structures do not require frequent overhaul, as do poles, nor do extremes of temperature affect them.

Westinghouse Appointment

WESTINGHOUSE BRAKE AND SIGNAL COMPANY LTD. announce that Mr. George William Dunkley, O.B.E., has been appointed a Director.


A Twin Speaker

BASS

Reflex Cabinet

IMPROVE RESULTS FROM YOUR AMPLIFIER WITH THIS
LOUDSPEAKER ENCLOSURE

By L. F. G. Burrell

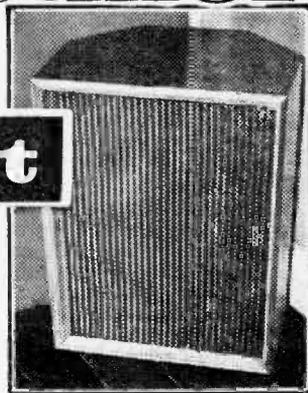

As the number of hi-fi enthusiasts increases, many will be constructing their own equipment and will find, as I did, a lack of information on a simple and efficient loudspeaker cabinet which is also a pleasing item of furniture. The design given here is of the bass reflex type and is a modified version of an American model. This cabinet can also be used for a 10in. "Woofer" plus a "Tweeter" or 12in. or 10in. single speakers, and for those of limited means, the "Tweeter" could be provided for, and the hole blocked internally, with a thick piece of ply, purchasing it when finances allow. If only a single speaker is to be used, the hole in the baffle board could be centralised horizontally.

Materials and First Steps

The main carcass needs solid, rigid timber, and the best for this is 15 mm. (12 ply) which is approximately 9/16in. thick. Other than that, only 3/4in. block board, or solid timber at least 1/2in thick will do. Any thinner material will not allow the speakers to give of their best and may lead to distortion and unwelcome vibrations at certain frequencies. Depending on the finish

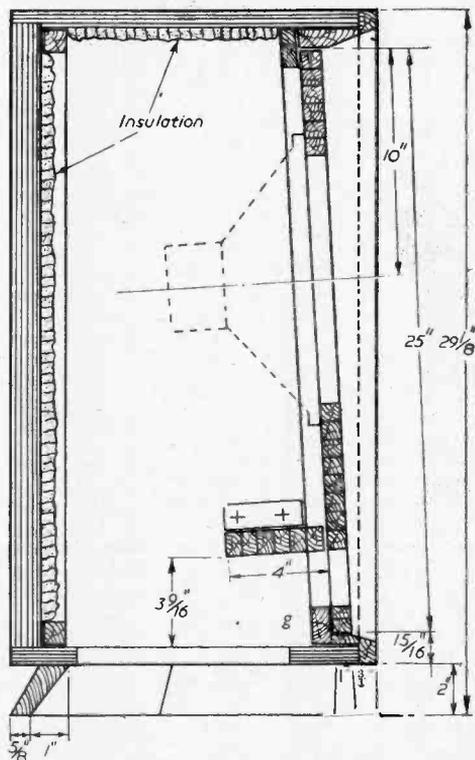
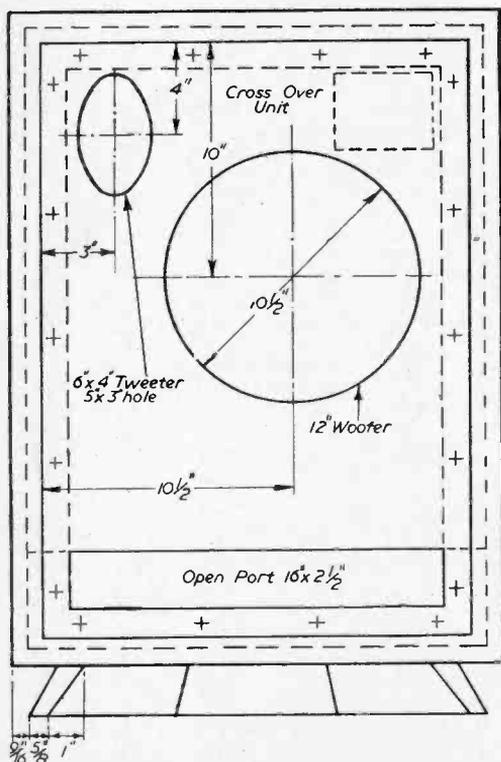


Fig. 1a (Left)—Front elevation of the cabinet. Fig. 1b (Right)—Side elevation.

required and money available 15 mm. ply could be obtained faced one side with a wood veneer.

By a careful layout and a little delicate work with a hand saw (Fig. 2), the size of the piece of ply required can be reduced down to 42in. X 48in. or 14 sq. ft., or smaller still if back and bottom are made from slightly less expensive 3/4 in. block board.

Laid out thus, the resulting grain pattern with

MATERIALS

- 42in. x 48in. oak-faced plywood (15mm. thickness).
- 3 3/4 sq. ft. of 3/4 in. block board for deflector and baffle.
- 20ft. of battening.
- 3ft. 2 1/2 in. x 1 1/4 in. hardwood for feet.
- 8ft. x 1 in. x 3/4 in. hardwood for framing.
- 8ft. x 3 1/2 in. x 3/4 in. oak.
- 2ft. 6in. x 2ft. Tygan mesh.
- 1 gross assorted screws.
- Glue and wadding as required.

faced ply is rather pleasing. To make the baffle board, I chose 3/4 in. block board. It is very rigid and slightly cheaper than 15 mm. ply. As it is covered with mesh afterward, faced ply would be a waste of money.

A piece of Tygan mesh 24in. X 30in. with the pattern running the longest way is required. Silk could be used but has a muffling effect. The other alternative is expanded alloy mesh, but this can be very expensive and does not give quite the professional finish of Tygan.

Other materials required are some lengths of hardboard for feet and battens and odd offcuts for a mitre block which is used to make the feet. Brass screws (a must if battens and feet are of oak), glue, tacks, polish and a couple of packets of wadding (for acoustical damping) are also needed. A pound or so can be saved by using second-hand hardwood for the battens. (Breaking up an old piece of furniture can yield some very useful timber.)

Construction (base)

The following point must be borne in mind while construction proceeds. Airtight joints should be made wherever possible if the best is to be got from the speakers. This may sound absurd when there are holes in front and the bottom, but losses in quality will occur if sound can leak through cracks in the cabinet sides.

Also ensure that everything inside is tight and cannot rattle. Loose screws, threads of hardened

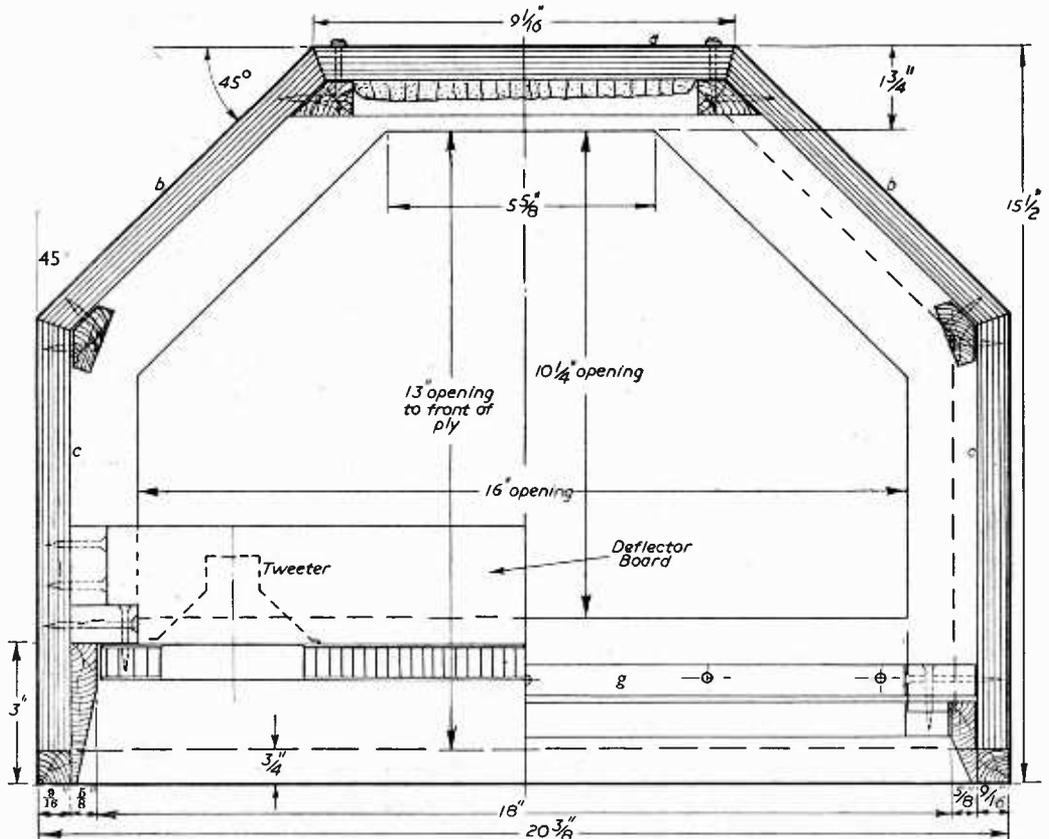


Fig. 1c.—Plan view at top and bottom of baffle board. (Note: The thickness of the bevelled edge at the front of the cabinet is 3/8 in.)

glue, etc., can cause peculiar noises to be heard at certain frequencies.

Having studied Fig. 1 set out the parts on the faced side of the ply sheet (Fig. 2). Choose one edge as a straight edge and true if necessary. If possible, use a tee-square and set-square, but, failing this, a large try square will be second best. Draw plan of base first and measure off widths of sides and back from this. Allow $\frac{1}{4}$ in. on each dimension on the drawing for planing and joint-

materials available. Square and screw the mitre block up carefully. Mark the angles of cut with a level square and square up from the bottom of the block on the inside. (The bevel square is one tool you must have for this job.) Saw down dead on line with a tenon saw, and the block is ready to cut the feet.

Making the Feet

Prepare the timber for the feet and plane the top and bottom to angle first, using a full sized section drawn on scrapwood as a profile. Working from one face edge, either top or bottom, cut the feet to angle, using the full sized plan to ascertain lengths. Draw the inside line of the feet on the underside of the base "e" and temporarily pin the feet in position from the underside. Turn the base over and drill and screw the feet in place with $1\frac{1}{4}$ in. No. 8 countersunk screws. Remove, glue up and rescrew in position, taking care not to forget to glue the mitred joints and fill any holes or cracks with glue also. Clean off the bottom of the feet to form level floor contact, chamfer the outer edge to avoid splintering and glasspaper to a smooth finish.

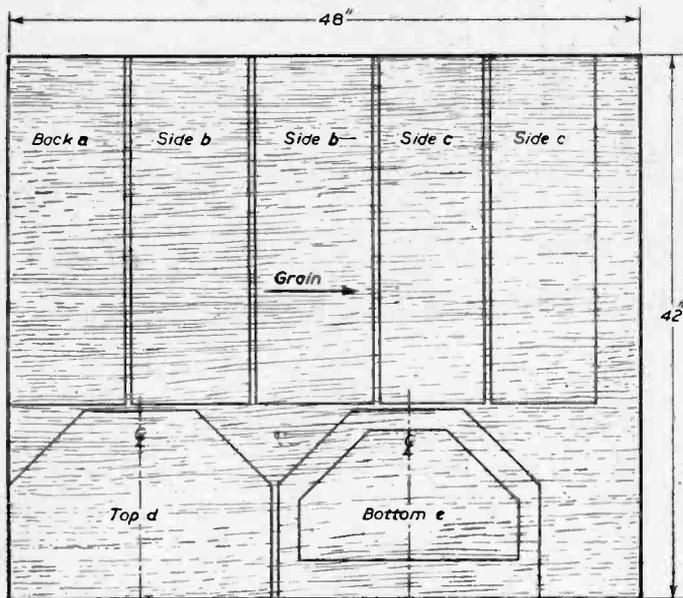


Fig. 2.—The marking out of the ply sheet.

ing. Saw on the waste side of the lines, checking the sizes of each piece before sawing. Saw the hole in the base "a" with a bow or pad saw. Alternatively, drill round the inside of the hole with brace and bit, link holes with a pad saw, and finish off with a rasp and sandpaper. For this operation and holes in baffle board, a power drill would save a great deal of work.

Drawing

A full size drawing, on a piece of hardboard, of the base plan is useful in checking shape of base and angles of cut of the feet. Check all the edges of the base after trueing up, for squareness, as the more near square they are the stronger will be the glued joint.

The feet are cut from hardwood $2\frac{3}{4}$ in. \times $1\frac{1}{2}$ in. and mitred together using a special mitre block made from 4 in. \times 1 in. hardboard or 15 mm. ply offcuts (Fig 3). The dimensions shown are arbitrary and can be varied to suit personal taste and


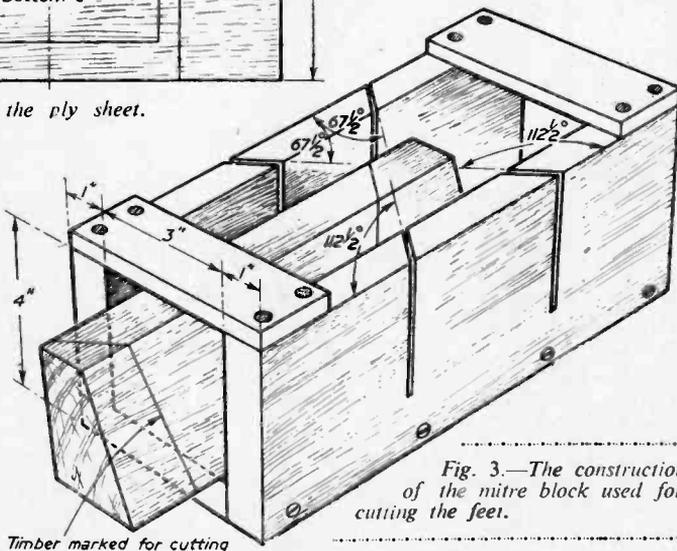


Fig. 3.—The construction of the mitre block used for cutting the feet.

Main Carcass

The baffle board fixing batten "g" is required next. Size $1\frac{1}{2}$ in. \times $\frac{3}{4}$ in. with bottom slightly bevelled to allow for the slope of the baffle. This batten extends the full width of the base and is set back 1 in. from the front edge. Drill it for screwing to the baffle board. Cramp in correct (Continued on page 410)

THIS unit was originally designed for use with a gramophone amplifier. The prototype was required to mix up to four inputs and boost the resultant signal to a suitable level for fully loading the main amplifier. Each input had its own gain control so that it could be adjusted to give any desired balance between the four. If only two inputs are required it is quite in order to omit one of the 6SN7's completely. On the other hand if six inputs are required another 6SN7 may be added, but it should be remembered that each additional valve requires about another 10mA of H.T.

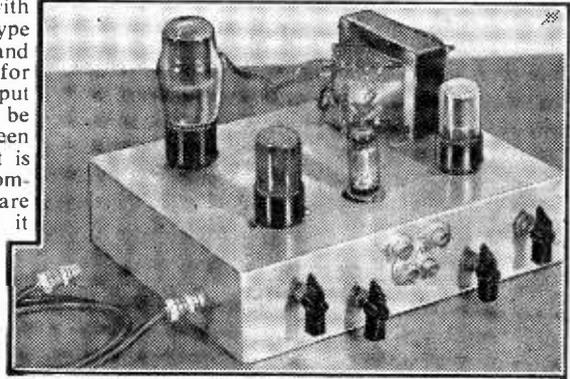

A Mixer

Pre-amp Unit

Circuit

The circuit is straightforward, having two double triodes (6SN7's) as the mixers, which feed the mixed signal to a high gain pentode (EF86) in a voltage amplifier circuit. The output from the EF86 is fed via a .01 μ F coupling condenser to the output socket. The output is at high impedance and can be fed directly into any amplifier having a high input impedance. The prototype had its own power unit built in as it requires just over 20mA of H.T., which would have put an excessive load on the power unit of the main amplifier. There is no reason why

FOUR INPUTS ARE PROVIDED EACH WITH ITS OWN VOLUME CONTROL

By J. A. Scuffam

power should not be taken from an external source. Before taking power from any other equipment it is well to make sure that the necessary current is available. If it is desired to build the power unit, a suitable circuit is shown in Fig. 2.

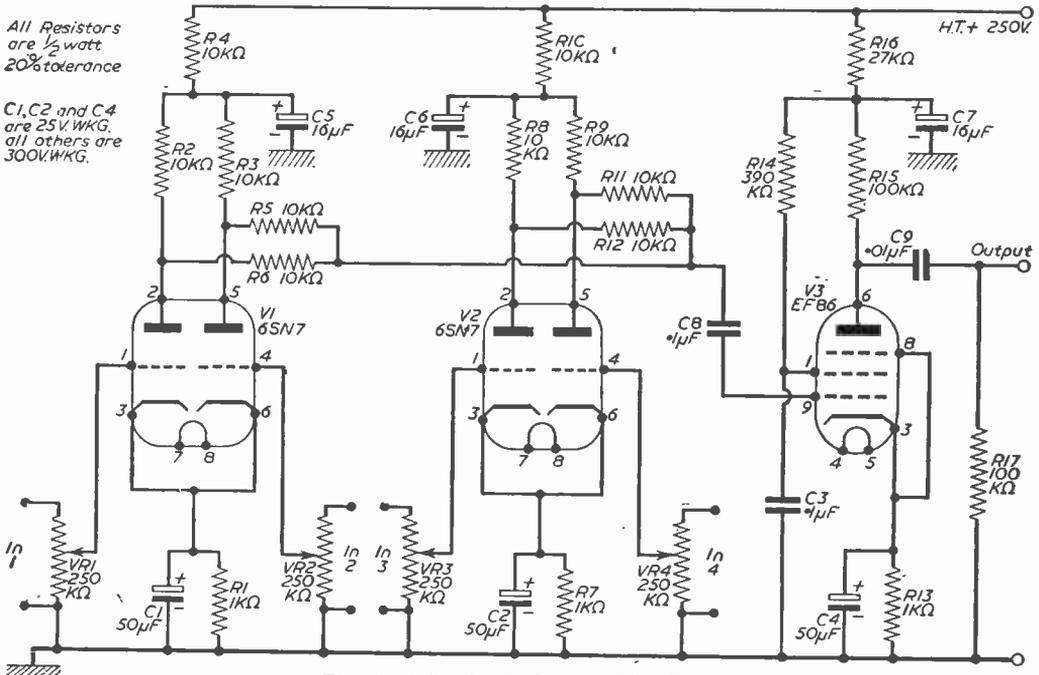


Fig. 1.—The circuit diagram (for four inputs).

Each stage is adequately decoupled and this contributes to the high stability of the unit. It also helps to keep the hum level down, but screened cable must be used in all the grid circuits. In addition to this, pins 3 and 7 on

tap on the heater supply this should be connected to the chassis instead of one side of the supply.

Screened Wiring

The next step is the screened wiring in the grid circuits. Care must be taken here as it is most important that all these leads are well screened. The cases of the potentiometers should be connected to earth. When soldering to coaxial sockets the lead should be trimmed first and the joint made quickly with a hot iron. This

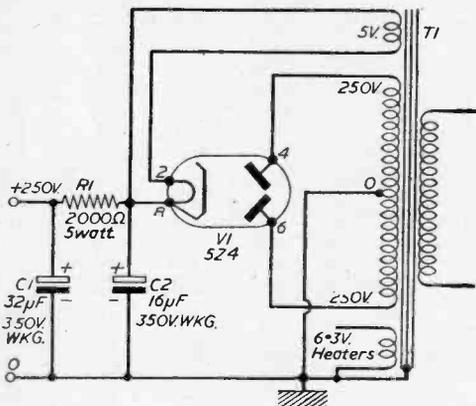


Fig. 2.—A suitable power-pack.

the EF86 should be earthed as these are connected to the internal screening of the valve.

Construction

The original was built on a chassis 11in. × 8in. × 2½in. which gave sufficient room for the power unit. If the power unit is to be omitted the chassis size may be reduced to 11in. × 5in. × 2½in. The layout was as shown in Fig. 3. The gain controls were staggered as they were somewhat larger than average. The front panel can be redesigned as required, the layout not being critical. Full use of chassis room should be made and all components well spaced.

Wiring should begin with the power unit and all heater leads, the latter running close to the chassis and being well twisted together. One side of the heater supply should be connected to the chassis but if the mains transformer has a centre

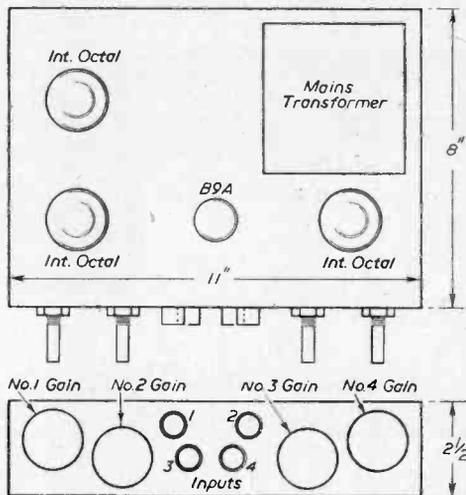


Fig. 3.—Layout of the chassis and control panel.

avoids unnecessary melting of the polythene insert.


The rest of the wiring may now be carried out. Although a tag board was used, this was only intended for anchoring the heavier components. Much of the wiring is self-supporting and all resistors leading to valveholder tags should be soldered direct to them whenever possible.

Operation

It will be found on using this unit that the settings of gain controls become much more critical. This is due to the high gain of the EF86 which may tend to overload the main amplifier. If your main amplifier has its gain control in the grid circuit of its first valve, the best results are obtained by reducing the gain of the main amplifier as much as possible to give the maximum output required for the lowest available input. All control of volume should then be confined to the gain controls on the mixer pre-amp. unit.

When using a gramophone or similar equipment which has a relatively high output it may be found that the gain control can

(Continued on page 384)

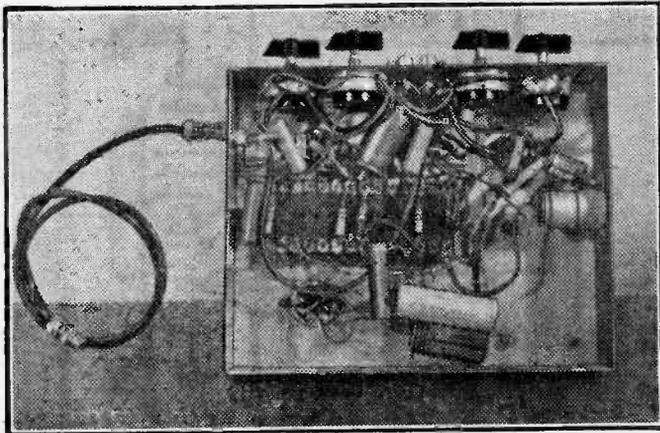

Underchassis view of the unit.

Basic Theory for the Constructor

No. 5.—ALTERATIONS TO SERIES HEATER CIRCUITS

By G. Palmer

THERE may well arise an occasion where an experimenter has available a valve which would be suitable as a replacement for a defective one in a series-connected heater chain were it not for the difference in heater current.

In the previous article in this series we discovered that a valve with a heater current rating less than the heater chain current would be over-run owing to the resulting increase in volts drop across the heater when introduced in a constant current circuit, and that conversely a valve with a heater current rating greater than the heater chain current would be under-run. It was also shown that the heater voltage rating is of little moment in relation to the current rating in a series-connected heater chain.

Modification

During the war it was often found necessary to modify series-connected heaters circuits to cater for a valve with a heater current different from the chain current. These days such a modification is considerably less likely to be warranted since most A.C./D.C. type valves, even those dating back before the war, are not unduly difficult to obtain.

Nevertheless, certain valves of this nature are in short supply, and it often happens that a valve from the "junk box" could be put to good use

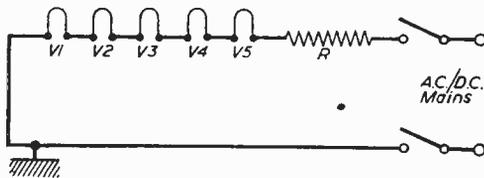


Fig. 1.—Simple series-connected heater circuit.

in an A.C./D.C. type receiver which is so old that it is uneconomical to employ a new replacement, bearing in mind that old type valves are often costly and carry a high rate of tax.

By-passing the Surplus Current

A typical series-connected heater circuit is shown in Fig. 1. Three of these valves may have 12.6 v. heaters and the remaining two 25 v. heaters, giving a total of almost 88 v. If the supply is 230 v., then the ballast resistor R is called upon to drop the difference between 230 v. and 88 v., which is 142 v. If the heaters are rated at 0.3A, which is most probable with this range

of voltages, from Ohm's law ($R=E/I$) we find that R has to have a value of 473 ohms.

We have already delved into such simple problems in previous articles, but I^2R (the power formula) indicates that R will be called upon to dissipate about 42.5 w. ($0.3^2 \times 473 = 0.09 \times 473 = 42.57$ w.). A 50 w. resistor would almost certainly be used here.

Now let us suppose that V4 is a 25L6GT (25 v. 0.3A heater) and that a replacement is not readily available, but we have in hand a 35L6GT. The 35L6GT has characteristics almost identical to the 25L6GT, apart from the heater rating, which is 35 v. 0.15A.

Over-running

If this substitution was made without any alteration to the circuit, the set would undoubtedly work for a short while, but the 35L6GT heater would have about 70 v. developed across it; it would thus glow very brightly and soon burn out. Moreover, A.F. distortion would be likely to result from over-heating of the valve.

However, a simple resistor can be arranged to bypass the surplus current from the 0.15A heater of the 35L6GT, as is shown in Fig. 2. Thus, the value of R_s is adjusted so that in relation to the voltage across it, it passes 0.15A.

Calculating R_s

We must, of course, ensure that the 35L6GT has a full 35 v., no less and no more. The Ohm's law formula is again brought into action. Hence, $R_s = E/I$, where E is the heater voltage of the valve (35 v. in our case) and I is the difference between the heater chain current 0.3A and the replacement valve heater current 0.15A ($0.3 - 0.15 = 0.15$). This method of working should be followed irrespective of the heater rating of the replacement valve and the heater chain current. It can thus be adopted to suit any case which may arise.

We now discover that $R_s = 35/0.15$, which works out to some 233 ohms. This means that provided the heater chain is passing 0.3A, the voltage developed across V4 heater in parallel with R_s is 35 v., and that V4 heater is passing only 0.15A, the resistor passing the surplus 0.15A. All very straightforward.

Theoretically, though, the overall volts drop across the series-connected heaters has risen because the circuit, in relation to R, was designed originally for a drop of 88 v. That was when V4

had a 25 v. heater, but since the modification it represents a 35 v. heater.

Chain Current

Roughly speaking, this means that the chain current will be a little less than the optimum 0.3A. There will, for example, be 98 v. developed across the whole of the heaters in series, instead of the original 88 v. If the supply is still 230 v., then the ballast resistor R will be required to drop 132 v., instead of the original 142 v. This means that the heater current will now equal $132/473$ ($I=E/R$), which works out to be a little less than 0.28A.

The difference, even though only very small as worked out above, may be less than that com-

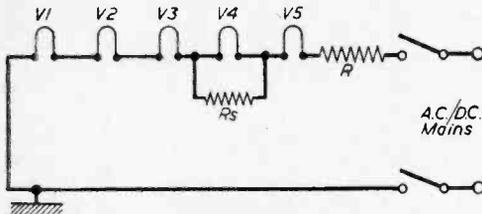


Fig. 2.—A valve of heater current less than the chain current could be employed in the chain, provided it is shunted with a resistor (R_s) of a suitable value to bypass the surplus current.

puted owing to the slight increase in resistance of the valve heaters as the result of their very slightly reduced operating temperature owing to the current reduction. In other words, there occurs a kind of compensating balance in the heater chain.

Checking the Current

In practice, an alteration to the value of R to compensate more fully would hardly be warranted, but after such a modification it may well be of interest to check the chain current if a fairly accurate A.C. ammeter is available. The instrument could be inserted almost anywhere in the chain, provided H.T. current is not inadvertently measured along with the heater current. Probably, the best thing to do would be to break a link between two of the valves, say, V2 and V3, and connect the meter in place of the link, as shown in Fig. 3.

If the meter was inserted in series with the mains supply proper, H.T. current would also be measured, and a reading in excess of normal would be obtained, thereby giving rise to some bewilderment. Of course, if the set is operated on D.C. mains, then a D.C. ammeter would be suitable.

If the current is low and R is adjustable, it would pay to use a voltage tapping on R which provides the correct heater chain current, but if the current is well out after the modification, check the accuracy of the ammeter, particularly if the valve heaters appear to be lighting at normal brilliance.

Power Rating of R_s

So far nothing has been said about the power rating of R_s . A resistor of small rating would

quickly burn out in this position and V4 would be left with 0.3A in its 0.15A heater.

There are two ways of finding the power rating. One is by using the $W=I^2R$ formula, where I is the current and R the value of R_s . Since the current has to be worked in amps., this formula introduces a lot of decimals, and the alternative $W=E \times I$ formula is best. E is the voltage across V4 heater (which is the same as across R_s) and I is the current in the resistor. This gives $W=35 \times 0.15$, which works out to about 5.25 w. A 6 w. resistor, wire-wound type, should thus be used.

Pilot Lamp Shunt

The idea can be extended to any other element in a series-connected circuit. For example, a shunt is often advantageous across the pilot lamp in an A.C./D.C. type receiver, not only to prevent frequent replacements but also to prevent the set from ceasing to function in the event of bulb failure.

Bulbs normally used in such positions are invariably rated at 6 v. 0.3A, or 6 v. 0.15A, to match the heater current of the valves. Owing to their very nature they inevitably represent the weakest link in the series chain, and a failure usually open-circuits the chain and causes the valve heaters to go out. The inclusion of a resistor, R_s in Fig. 4, maintains continuity in such an event, but in addition it means that the bulb is not run to its limit.

Bulb Life

Let us suppose that the pilot lamp is, in fact, rated at 6 v. 0.3A, and to safeguard its future it is decided to run it at a lower voltage, say, 4.5 v. Now, if at 4.5 v. the bulb current drops to 0.2A, which is a likely value, then R_s should be made to equal $4.5/0.1$ ($R_s=E/I$, where E is the voltage

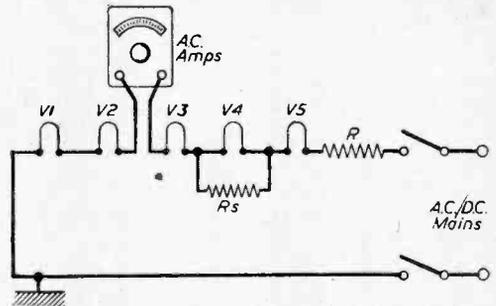


Fig. 3.—Heater chain current can be measured by introducing an ammeter in a suitable position in the chain, as shown.


required across the bulb and I is the difference between the heater chain current and the bulb current), which is 45 ohms.

Wattage of Shunt

Under this condition the resistor will dissipate 4.5×0.1 w., so a 1 w. resistor would serve quite well. However, if the bulb should fail, the resistor will pass the full 0.3 A of the heater chain.

(Continued on page 413)

Servicing Radio Receivers

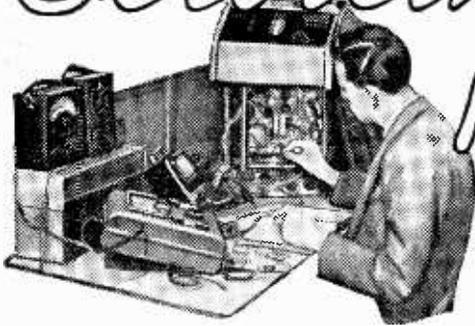

THE PILOT "CLIPPER" F.M./A.M. RECEIVER

By Gordon J. King, A.M.I.P.R.E.

volts. It contains six valves, including a half-wave rectifier, the complete circuit being given in Fig. 1.

THE Pilot "Clipper" is a table model having a V.H.F.-F.M. band in addition to the M.W. and L.W. bands. It features a built-in compressed dipole for V.H.F., an internal ferrite rod aerial for the A.M. bands, a reduction drive to facilitate accurate tuning and a full length illuminated station scale.


There is also a large loudspeaker which is driven from a single pentode output stage having negative feedback. Sockets for external aerials, gram, pick-up and extension loudspeaker are also incorporated. The chassis is of the A.C./D.C. type and operates within the range of 200-250

Valve Line-up

V1 (UCC85) is concerned solely with the V.H.F. section, it being arranged in the form of an earthed grid R.F. amplifier (V1A) and a self-oscillating frequency changer (V1B). V2 (UCH81) is the A.M. frequency changer, but when the receiver is switched to the V.H.F. band the local oscillator triode section is switched off and the heptode section serves as an extra I.F. amplifier, it picking up its signals from the V.H.F. tuner.

V3 (UF89) is the I.F. amplifier for both A.M. and F.M., its anode and control grid circuits, as

Fig. 1. — Circuit diagram for the Pilot "Clipper." (See also overleaf.)

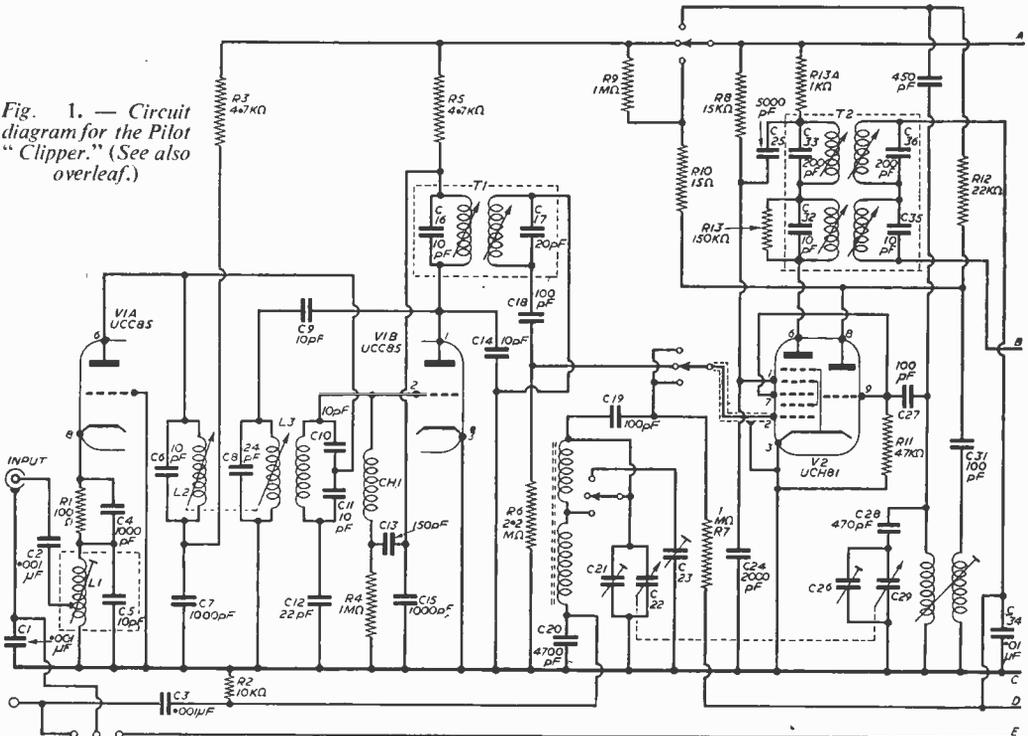

with the anode of V2 heptode, being loaded with two I.F. transformer windings in series—the windings actually connected to the valve electrodes are concerned with the F.M. intermediate-frequency, this being standard practice.

V4 (UABC80) is really three valves in one envelope working from two cathodes. There is a single diode, a double diode and a triode. The single diode has its own cathode, while the double diode and the triode share the other cathode. This arrangement allows the valve to operate in three different modes, which are (1) ratio detector for F.M., using the single diode and one of the double diodes; (2) A.M. detector, using one of the double diodes and (3) A.F. voltage amplifier, the triode being used for this operation.

V5 (UL84) is simply the output valve on both services, it being biased by the volts drop across the 270-ohm cathode resistor.

V6 (UY85) supplies H.T. voltage to the receiver. It being the rectifier. Its anode is energised direct from the power supply, via the 82-ohm surge limiting resistor (R30).

Heater Circuit

The heaters of all the valves are rated at 0.1 amp. and are connected in series as is normal A.C./D.C. practice. It will be seen that the chassis of the set is connected to one side of the mains power supply by way of the on/off switch. Thus, to the chassis is connected one side of V4 heater, the other side of the heater to V1 heater and so on through the chain to V6. Chain continuity is maintained first through the pilot lamps, B1 and B2, through the thermistor

M2. the volts dropper resistor R29 and the surge limiting resistor R30, and back to the other side of the mains power supply.

It will be realised, therefore, that failure of any valve heater or component in the heater chain will result in all valve heaters going out. This will not apply to failure of a pilot bulb, since both bulbs are shunted with thermistor M1. In the event of bulb failure, this thermistor will quickly heat up and its resulting reduction in resistance will tend to balance the heater chain.

With A.C./D.C. type of receivers, it is always desirable to ensure that the power lead which is in connection with the chassis, through the switch, is plugged into the mains neutral socket. Failure to observe this precaution may result in the receiver chassis being at mains potential with respect to earth, and a serious electric shock may result on touching the chassis when the set is connected to the mains.

Circuit Notes

The anode of the tuner R.F. amplifier valve section is coupled to the frequency changer valve section at a point of minimum oscillator signal, this being at the junction of C10 and C11. The oscillator circuit, in conjunction with the capacitors mentioned and C12, forms a balanced bridge circuit so that undue oscillator signal is not radiated by the aerial system.

The oscillator signal coupling to the R.F. stage will increase if the "bridge" balance is disturbed due to alteration in value of one of the capacitors. If the balance is considerably upset for any reason, apart from the above effect, the V.H.F.

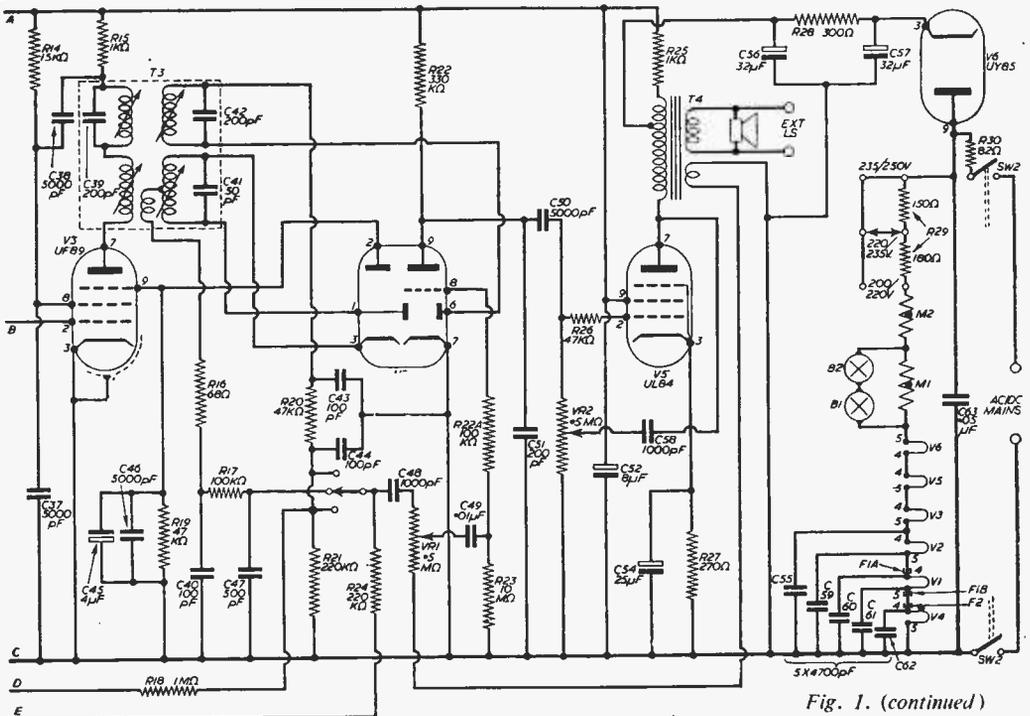


Fig. 1. (continued)

tuner will fail to track correctly over the V.H.F. band.

The V.H.F.-F.M. intermediate-frequency is 10.7 Mc/s, this being developed in the first instance across the tuner I.F. transformer, T1. When the set is switched to "V.H.F.", the signal from this transformer is conveyed to the signal grid of V2 heptode and the oscillator is cut out. After its passage through the I.F. amplifier, the F.M. I.F. signal appears considerably magnified across the ratio detector transformer in T3 (the transformer whose windings are connected to pin 7 of V3 and pins 1 and 3 of V4).


The demodulated F.M. signal appears across C40 and is applied to the top of the volume

The output transformer, T4, appears to be rather complex. The primary winding is tapped and H.T. is applied to the tap in such a way that the winding serves as a hum neutralising device, it being seen that H.T. for the rest of the set is obtained from the top of the winding, through R25. The smoothing capacitors are C52 and C56, while the electrolytic C57 is the reservoir. Resistor R28 also helps reduce the hum level, it being the filter resistor, used instead of a choke, which is common practice these days.

The ratio detector load resistor proper is R19, it being shunted with the stabilising capacitor C45, the two together forming a time-constant of optimum value for the suppression of A.M. interference. An interesting point is the application of the negative potential appearing across the ratio detector load resistor to the suppressor grid of the I.F. amplifier valve, V3. This provides an A.G.C. control, it being remembered that the stronger the F.M. signal the greater the negative voltage across the load, and the greater the voltage applied to V3 suppressor, the less the gain of the valve.

-When the set is switched to the A.M. bands, R20 and R21 comprise the A.M. detector filter and load resistors, filtering also being assisted by C44. The direction of the A.F. signal is the same as detailed above, but on A.M. the D.C. voltage, negative to chassis, which is present across R21 in magnitude dependent on the signal strength, is applied to V2 and V3 as an A.G.C. (automatic gain control) bias.

There are two negative feedback loops in the A.F. stages. One working in relation to the tone control, VR2, this being frequency selective by virtue of C58. Negative voltage feedback is also applied over stages V4 and V5 from the voltage induced in the small feedback winding on the output transformer, T4. One side of this winding is connected to receiver chassis, while the other side is connected to the grid circuit of V4 triode.

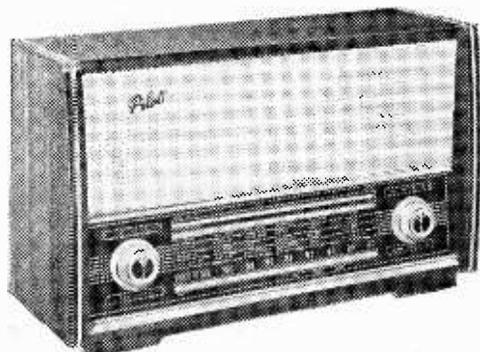

The Pilot "Clipper" F.M./A.M. radio.

control, VR1, by way of the de-emphasis network, R17 and C47, and C48 A.F. coupling capacitor. From the slider of the control, the signal is carried to the grid of V4 triode through C49 and R22A. The A.F. signal appears considerably magnified across the load resistor, R22, in the anode circuit of V4 triode. From here it is coupled to the signal grid of V5, through C50 and R26.


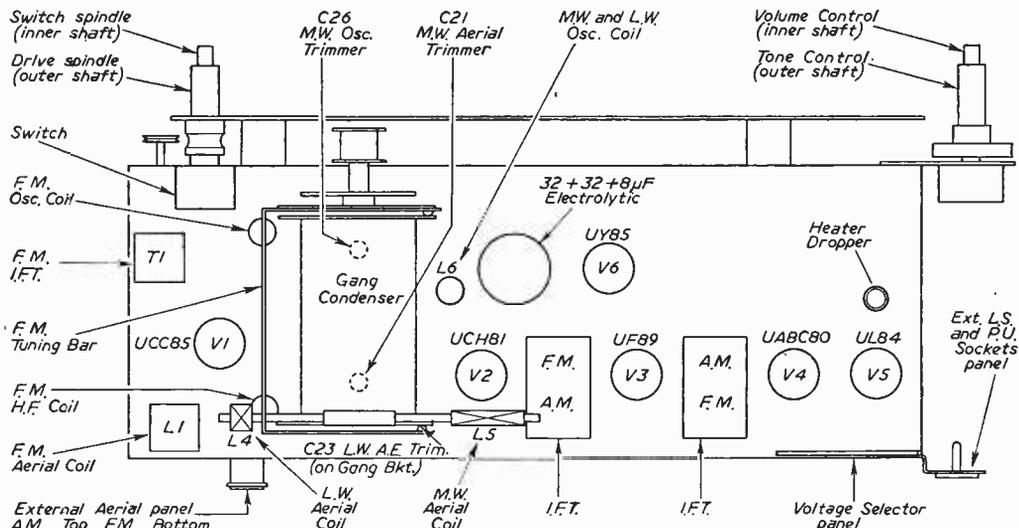


Fig. 2.—Top view of the chassis, showing tuning cores and trimmers

Nores on Alignment

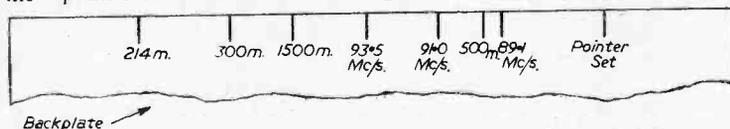In Fig. 2 is depicted a top view of the chassis, revealing the position of the trimmers and transformers. Fig. 3 serves to identify the indents in the top of the receiver backplate. Before the alignment process is commenced the tuning pointer should be carefully set to coincide with the "pointer set" indent on the backplate. Care



should also be taken to ensure that the correct tuning cores are identified before making any adjustment.

A.M. Intermediate-frequency

Switch receiver to M.W. and set the tuning gang to the fully closed position. Inject a 470kc/s 30 per cent. modulated signal into pin 2 of V2 through an 0.1 μ F capacitor. Adjust T3 and T2 top and bottom cores for maximum audio output.

Medium and Long Waves


Couple the signal generator to the ferrite rod aerial by way of a coupling coil positioned, at least, 6in. from the aerial. Trim at 1,400kc/s C25 and C20. Pad at 600kc/s L6. Tune the receiver and generator to 200kc/s and trim C22.

F.M. Intermediate-frequency

Connect an oscilloscope to the junction of R17 and C45. Inject a 10.7 Mc/s plus and minus 100 kc/s frequency modulated signal into pin 6 of V1 through an 0.1 μ F capacitor. Adjust T3, T2, T1 top and bottom cores for maximum output on the oscilloscope with minimum distortion.

Fig. 3. (Left)—The tuning points on the backplate.

Fig. 4. (Below)—Details of tuning cord drive.

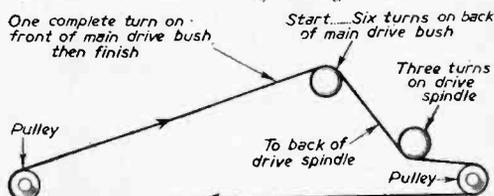

Drive cord viewed from front of chassis with gang shut

F.M. R.F. Section

Tune the receiver to 91 Mc/s. Inject a 91 Mc/s plus and minus 100 kc/s frequency modulated signal into the F.M. aerial socket and adjust L3, L2 and L1 for maximum output on the oscilloscope.

Tuning Drive

Full details for replacing the cord of the tuning drive are given in Fig. 4.

1959 National Radio Control Championship

Rules.—MYA/IRCMS Provisional Rules.

Date.—August 29th/30th, 1959.

Place.—Poole Park, Dorset.

Programme.—The event will be sailed over a triangular course using the MYA Tournament system of sailing.

Class.—Yachts holding a current "A" Class certificate measurer with or without radio equipment and ex-"A" Class yachts similarly measured.

Entrance fee.—10s. per boat.

Frequencies.—27 Mc/s and 465 Mc/s.

Equipment.—Any type of control equipment is allowed provided it complies with the Rules and does not cause interference to other competitors in either of the above bands. This will necessitate the use of crystal control and superhets unless group system is entered, details of which must be approved by the Poole MYC before entry. Early notification of crystal frequencies is essential so that the position may be studied.

Closing date.—August 8th, 1959.

Entry forms.—MYA entry forms will be used by all entrants. IRCMS members to forward all forms to Mr. Carrington-Wood together with entry fees not later than July 30th, 1959.

Entrants.—Members of clubs affiliated to the MYA or IRCMS.

Sailing Committee.—Messrs. Miller, Dehon, Cobb, Brooks and Allan-Drake.

Further details.—Site facilities and other ancillary details will be published by the Poole MYC as soon as possible.

Further details may be obtained from T. Brook, 12, Gorse Hill Road, Poole. (See also page 413.)

A MIXER PRE-AMP UNIT

(Continued from page 378)

only be used over a small part of its track otherwise the unit is overloaded. In this case the trouble can be overcome by using a pre-set potentiometer (mounted on the gram unit and well screened.) This should be set to give the output required, and locked in position.

Gain Controls

The gain controls in the original design were 250k Ω potentiometers, which matched the microphones and inputs that were used. Most crystal microphones would be better matched into 1M Ω or more, depending on the maker's instructions.

Providing that extreme mismatch is avoided, the 250k Ω potentiometers will work perfectly well in general use, but it is advised that the reader matches his potentiometers as nearly as possible to the impedance of the microphone, etc., used. This only applies to inputs of a higher impedance than 250k Ω . Low impedance inputs should be matched through a suitable transformer.

NEW!

DO-IT-YOURSELF TRAINING TECHNIQUE in RADIO & ELECTRONICS

You LEARN while you BUILD...

SIMPLE...PRACTICAL...FASCINATING...

ANNOUNCING—after many years of highly successful operation in the U.S.A. and in Europe—the latest system in home training in electronics is now introduced by an entirely new British training organisation.

AT LAST—a comprehensive and simple way of learning—by practical means—the basic principles of radio and electronics, with a minimum of theory.

YOU LEARN BY BUILDING actual equipment with the components and parts which we send you. You advance by simple steps using high quality equipment and performing a whole series of interesting and instructive experiments. No mathematics!

INSTRUCTION MANUALS and our teaching staff employ the latest techniques for showing clearly how radio works in a practical and interesting manner. You really have fun whilst learning! And you end by possessing a first rate piece of home equipment with the full knowledge of how it operates and—very important—how to service and maintain it afterwards. A full library of magnificent illustrated textbooks are included with the Courses.

IN FACT for the "Do-it-Yourself" enthusiast, the hobbyist, or those wanting help with their radio career training, or to set up their own full or part-time servicing business—then this new and exciting instructional system is exactly what is needed and it can all be provided at very moderate cost. Easy payments available. Post the coupon now, for full details. There is no obligation of any kind.

BUILD YOUR OWN: ● RADIO EQUIPMENT ● HI-FI INSTALLATION ● TEST GEAR—
AND LEARN AS YOU DO IT!

FREE-POST TODAY

RADIOSTRUCTOR

BRITAIN'S LEADING RADIO TRAINING ORGANISATION

LOTS OF INSTRUCTIVE EXPERIMENTS AT HOME!

Power supply circuits

Test equipment supplied

Amplifier, oscillator and detector circuits

Basic 1st stage receiver

Servicing of commercial receivers

No Mathematics!

To RADIOSTRUCTOR (Dept. G30)
46 MARKET PLACE, READING, BERKS.

Please send full details of your Radio Equipment Courses without any obligation to:

Name

Address


BLOCK CAPS PLEASE

801 We do not employ representatives. 7-59

WEYRAD

COILS AND TRANSFORMERS FOR A 2-WAVE TRANSISTOR SUPERHET WITH PRINTED CIRCUIT AND FERRITE ROD AERIAL

- LONG AND MEDIUM WAVE AERIAL—RA2W
On 6in. rod, 7/16in. diameter, flying lead connections, 208 pF tuning 12/6
- OSCILLATOR COIL—P50/1AC
Medium wave in screening can. For 176 pF tuning condenser 5/4
- 1st AND 2nd I.F. TRANSFORMERS—P50/2CC
470 Kc/s operation with 250 pF tuning in cans. 11/16in. diameter by 3/4in. high 5/7
- 3rd I.F. TRANSFORMER—P50/3CC
Last stage transformer to feed diode detector. Size as P50/2 6/-
- DRIVER TRANSFORMER—LFD T1
Fully enclosed with six connecting tags—case 11/16in. square by 1 1/2in. high 17/6
- PRINTED CIRCUIT—PCAI
Size 2 1/2in. x 8 1/2in. Ready drilled and printed with component positions 9/6

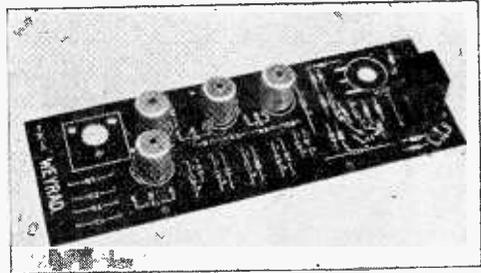

THESE COMPONENTS ARE APPROVED BY TRANSISTOR MAKERS AND PERFORMANCE IS GUARANTEED.

Constructor's Booklet with full details, 2/-.

WEYMOUTH RADIO MANUFACTURING CO., LTD.
CRESCENT STREET, WEYMOUTH, DORSET

(DEPT. WY)
PP COMPONENTS LTD.

AMATEURS' MUSTS

- MAINS POWER TRANS.**, 12/6. 350-0-350 v. at 250 m/a., 22 v. 3a., 4 v. 3a., 6.3 v. 4a., 6.3 v. 4a., 4 v. centre-tapped. Prim. 200/250 v. Drop thro' type. P. & P. 3/9.
- MAINS POWER TRANS.**, 12/6. 350-0-350 v. 250 m/a., 6.3 v. 5a., 4 v. 4a., 4 v. 7a., 4 v. centre-tapped. Drop thro' type. Prim. 200/250 v. P. & P. 3/9.
- HEATER TRANS.**, 1/9. 4 volt-6 volt at 3 amp. Ideal auto trans. P. & P. 1/-.
- O.P. TRANS.**, 1/3. Std. size. 2.5 Ω. P. & P. 1/-, 20 for £1. Carr. 5/6.
- 2 GANG CONDS.** Miniature 2/6. 500+500 and 30+30. P. & P. 1/3.
- TUNING CONDS.**, 2/6. Regentone. New, std. size. 500+400. P. & P. 1/3.
- 2 GANG CONDS.**, 2/6. Plessey. A.M./F.M. Std. size. P. & P. 1/3.
- VISCONAL CONDENSERS.** 5/9. 0.1 μF at kV. working and 0.001 μF at 12.5 kV. working. Post 1/-.
- VICINROLS.** 2/6 doz. Assorted volume and tone controls stripped from working chassis. Post 2/-.
- INSULATING TAPE.** 1/6. Finest quality tape. 75ft. x 1/2in. wide. In sealed metal tins. Post on 1 tin 9d., on 6 tins 2/-.
- FOCUS MAGNETS.** 8/9. Brand new, 38 mm. Incorporating picture shift controls. P. & P. 1/3.
- FOCUS MAGNETS.** 12/9. Elac. New. 35-38 mm. P. & P. 1/3.
- FOCUS MAGNETS.** 3/9. Plessey. 35 mm. Permanent magnet. Salvage. P. & P. 1/9.
- SCANNING COILS.** 10/6. Low impedance. 38 mm. Brand new. P. & P. 1/3.
- T.V. SLIDER CONTROLS.** 5/- for panel of 5 sliders. 1 K., 5 K., 10 K. and 2 at 50 K. ohms. Complete with knobs, P. & P. 1/-.
- 17in. T.V. MASKS.** 7/8. Brand new. Good quality. Grey or white plastic. P. & P. 2/3.
- 12in. T.V. MASKS.** 1/9. White rubber. Slightly soiled. Easily cleaned. P. & P. 2/3.
- CO-AX. CABLE.** 6d. yd. Good quality. Cut to any length. Post on 20 yds. 1/6. 45/- per 100 yds. P. & P. 3/6.
- RECTIFIERS.** 2/9. Westinghouse. 250 v. 100 m/a. Full or half-wave. Salvage guaranteed. P. & P. 1/3.
- SPEAKERS** 8in. P. 31. 5/9. Limited quantity of these modern type speakers. All tested and "money back guarantee." They have a slight come fault that is repaired. Not affecting the quality. Post on 1. 2/6; 2. 3/6.
- 6in. SPEAKER.** 12/6. Standard matching to any receiver. 2-5 ohms. P. & P. 2/6.
- ELLIPTICAL SPEAKER.** 19/6. New. 4in. x 7in. P. & P. 2/6.

219, ILFORD LANE, ILFORD, ESSEX.

Tel.: ILF 0295


Stamp for FREE CATALOGUE. U.K. only.

SUMMER ATTRACTIONS

- E.M.I. 4-SPEED BATTERY RECORD PLAYER.** 6 or 9 v., 99/6. P. & P. 4/6.
- VALVE BATTERY AMPLIFIER.** 1 1/2 v. l.t. 60 or 90 v. h.t., 39/6. P. & P. 3/6.
- 3 TRANSISTOR AMPLIFIER.** 1 control, 9 v., 79/6. P. & P. 3/6.

VALVES

1/9	3/9	Z77	6K7	10/6
6H6M	3D6		6L25	6CD6
ARP18	6B9	6,9	6P25	6F28
D1	8D2		6S7	10F1
EA50	11E3	6X5	6V8	45IU =
EB34	CV73	9D2 =	6X4	FW4500
KT24	EF39	VR106	12A6	EL94
LP220	EF92	11D3	12AT7	U22
PEN220A	W81	12BE6	12K7	UUB
PM22		15D2 =	35L6	
VR21	4/9	DH81	807 = 12V	
VR35	EF37A	EBC33	1025 = 607	
VR37	EL32 =	PEN45	DK36	
VW36	VT52	PEN46	EAF42	
	VT501	P61	ECC81	
			ECH42	
			ECL80	1D6
			EF80	6A7
			EF85	8C6
			EZ40	6D6
			EZ80	18
			KT81	42
			N77	75
			PL83	77
			PY80	78
			Y82	80
			T41	83
			UBC41	
			UF41	
			W76 =	
			12K7	P. & P. 9d.
			X81	on 1-2-6
				on 1 doz.

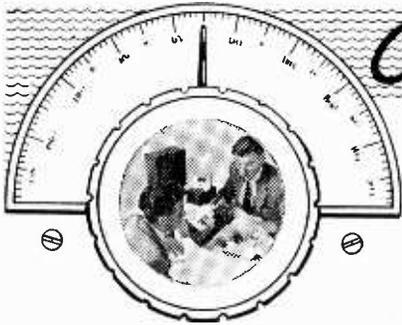

On Your Wavelength

BY THERMION

"Mad Dogs . . ."

THE warm weather is with us again, bringing with it the temporary decline in the practice of indoor hobbies including radio. Experimental gear is put on one side in the workshop or in a box on top of the wardrobe to collect dust and lie forgotten until the evenings are once again cold and dark. What a pity this all is! I don't suggest that the radio enthusiast should spend hot summer evenings indoors toiling away at some intricate piece of constructional work but there are many aspects of radio which can be enjoyed in the summer months; new aerials can be built and tried out by both listeners and transmitters, while the opportunity can be taken of building a shack for all the gear that the family tell you is a lot of junk.

One keen experimenter who I know does no constructional work at this time of year but in odd moments of spare time, after a game of tennis, for instance, he sits in a deck-chair in the garden or in one of the cooler rooms of his house, depending on his mood, and designs various pieces of gear to construct during the winter months. It is a revelation to see him manipulate his slide-rule and estimate the performance of the finished unit. As he says, it's useful practice in radio theory and half the enjoyment proceeds from finding how far the practical results differ from the theoretical, predicted, results.

Of course, few of us have the knowledge or inclination to go to this extreme, but I seriously suggest that we do waste a great deal of time in the summer months which could be employed for the furtherance of our hobby. Those who intend to become amateur transmitters could study a little of the theory which they will require for the R.A.E. A few evenings thus spent would be very valuable later when the real hard effort started.

Turning a Deaf Ear

TALKING of warm summer evenings, picture the following scene. Low evening sunshine, a pleasant garden, a young radio enthusiast in a deck-chair underneath the apple tree (swotting for the R.A.E.) and suddenly a voice floating across on the breeze—"Use Y's soap powder." This invasion of privacy is becoming more common than ever before and I cannot see any cure for it. Nearly everyone now possesses some elec-

tronic gadget whether record-player, radio or "idiot's lantern," and with the high volume output stages now fitted it is almost impossible to sit in the garden of an evening and not hear at least one radio or TV programme right through or the current "top ten." Why, some unintelligent and selfish folk even take their record-player or portable radio out in the garden with them and annoy the neighbours over quite a large area.

As I said before, I cannot see any cure for this state of affairs. Even the tactful appeals by the radio and TV announcers have little effect other than perhaps causing an increase in the volume of the offending apparatus. The worst part is that one never hears anything one enjoys: for example, I always manage to hear the latest popular records of which regular readers of this page will know I am not over-fond.

I should be very interested to hear from anyone who has found a (peaceful) remedy. Please do not suggest that I should sit in a sound-proof room!

The Show

THE Radio Show will be held this year at Earls Court as usual. The dates are August 26th to September 5th. The mixture will be much "as before" but nevertheless I am sure that its popularity will be just as great as in previous years. On the whole, amateurs are the most enthusiastic visitors, even if they cannot afford to buy much of the equipment.

The BBC exhibit will be housed in the West End fly-over as usual but the sound theatre will be on the Brompton side near the TV Celebrity Dais. An exhibit for the independent television companies will be organised by the I.T.A. and will be on the first floor. The stands manned by the Services will be in the Brompton wing.

The Audio Hall which was introduced last year will be enlarged this time, as the innovation was popular and more and more interest is being shown in this side of the radio industry.


Stereo

FOR my own part, I think that stereo sound reproduction has a long way to go before it surpasses the mono reproduction in all respects. Stereo can give wonderful effects, I agree, but so far very little is known about the theoretical aspects of the subject. The findings of the recent two-day I.E.E. Stereo Convention illustrate my viewpoint. The views expressed showed that much of the present theory is subjective and empirical and has little scientific basis. Various experts put forward differing views as to the mechanism of sound source location, and until some theory is found which fits all aspects of this complex subject I think that stereo progress will be slow.

SHORT-WAVE SECTION

IMPROVING RECEIVER SELECTIVITY

By J. B. Dance, M.Sc.

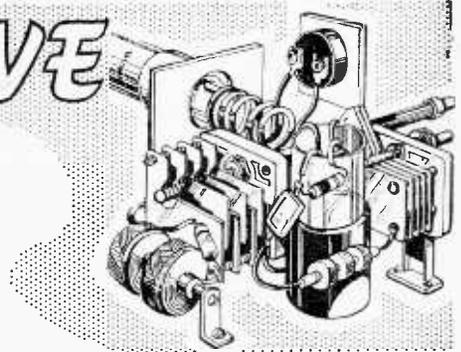

THE short-wave listener who requires a better performance from his receiver must adopt some method of obtaining increased selectivity. The two methods most frequently employed are the use of crystal filters and conversion to a double superheterodyne.

The double superhet operates, as its name suggests, by converting the incoming signals first to an intermediate frequency which is fairly high (often 1.6 Mc/s or possibly 465 kc/s) and then converting the frequency to a very low intermediate frequency (probably between 50 and 100 kc/s). The rejection of image interference is good because of the fairly high first intermediate frequency. The selectivity can be made excellent because of the low second intermediate frequency.


Practical Details

A single superhet receiver can be converted into a double superhet using the circuit in Fig. 1 as an add-on unit.

The input to this unit should be taken from the anode of the last intermediate frequency amplifier of the receiver via a small condenser, C1. Valve V1 is a 6K8 frequency changer, but any other suitable frequency changer could be used with appropriate circuit modifications. V2 is an amplifier operating at the second intermediate frequency and may be a 6K7 or EF39 or, if a single-ended valve is preferred, V2 could be a 6BA6 (miniature) or 6SK7 (octal). V3 is a cathode follower detector (also known as an infinite impedance detector) and any small triode (or triode connected pentode) such as a 6J5 or 6C4 can be used.

Choice of Second I.F.

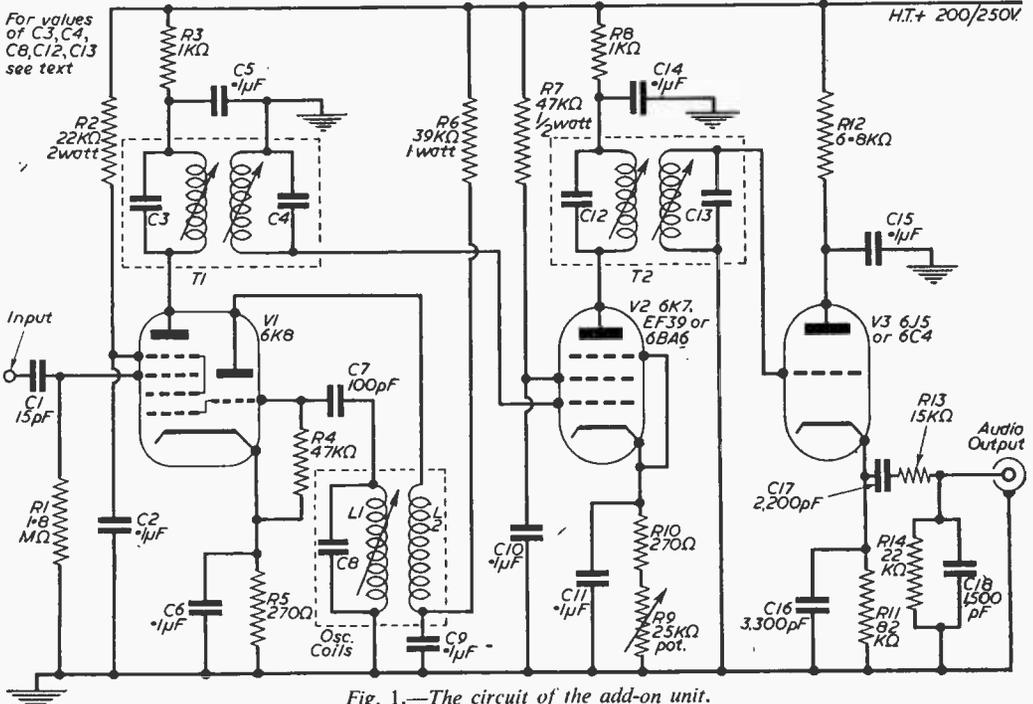The individual constructor must decide what second intermediate frequency he wishes to use. Generally any frequency between 50 and 120 kc/s



is perfectly satisfactory, but the lower frequencies give rather more selectivity. 85 kc/s transformers (T1 and T2 of Fig. 1) may be purchased or obtained from surplus BC453 units. The frequency may be lowered somewhat if desired by using a larger parallel condenser with each coil. Alternatively, suitable transformers may be constructed quite easily. Some unwanted transformers were bought on the "surplus" market and the cans were used to construct the transformers shown diagrammatically in Fig. 2. It is desirable that they should be permeability tuned (i.e., there should be an iron dust core in the centre of each coil for the purpose of altering its

WINDING DATA FOR COIL L1				
1st I.F. (kc/s)	2nd I.F. (kc/s)	C8 (pF)	Number of turns on L1 with dust core	Number of turns on L1 without dust core
1,600	85	150	64	73
1,600	85	100	76	87
1,600	50	100	74	85
465	85	200	228	254
465	50	250	174	202

inductance). The coils made by the author consist of 1,000 turns of 38 s.w.g. single silk enamelled copper wire wound on a half inch diameter former. The coils should be held in position by coating them with a suitable cement—preferably polystyrene. It is convenient to wind the coils between cardboard cheeks which are removed when the cement has partly set. The wire should be wound in a random manner and during the actual winding the cardboard cheeks should be supported with plasticine or another suitable material. The spacing between the centres of the two coils of each transformer should be about 1.2in. The cans used were about 1.4in. square. When a 220pF condenser was placed in parallel with one of these coils, the tuned circuit was found to resonate at about 85 kc/s ($Q=75$), but the capacitance could be increased to 680pF giving a resonant frequency of about 50 kc/s ($Q=60$). The second intermediate frequency can therefore be varied somewhat as desired. The inside connection from each coil should be connected to earth or H.T. + and the outside connection to grid or anode of the valve. The amount of selectivity obtained depends on the design of transformers T1 and T2 and the size of wire used for the coils of these transformers is important.

Oscillator Coil.

The oscillator coil may also be conveniently placed in an old transformer can for screening purposes. The number of turns on the tuned coil (L1 in Fig. 1) depends on both the first and second intermediate frequencies and on the value of C8. Typical values for the number of turns required on L1 are shown in the table above for a coil 0.2in. long on a former 0.5in. in diameter; values are quoted both when L1 contains an iron dust core and when no core is used. These values are correct to within a few turns, but provision must be made for varying the oscillator frequency either by iron dust core tuning of L1 or by using

a fixed condenser in parallel with a small trimmer for C8. The coupling coil, L2, should consist of about half the number of turns on the tuned coil. Silk covered copper wire, 30 to 38 s.w.g., is suitable for both oscillator coils. It is extremely important that all components of the oscillator should be rigidly fixed to the chassis. If this is not done, the oscillator frequency may alter and throw the unit out of alignment.

The coupling coil must be connected the correct way round or the oscillator will not work. The cathode end of the 47kΩ grid resistor should be disconnected and an 0-1mA meter inserted between the free end of this resistor and the cathode as shown in Fig. 3. If the oscillator is working the meter will probably read between 25 and 500μA. If no reading is obtained, reverse the connections of the coupling coil, L2, and if it is still impossible to obtain a reading, the number of turns on the coupling coil may be increased and it may be moved nearer to L1. The spacing between the two coils should be of the order of a quarter of an inch. The spacing of the coils and/or the number of turns on the coupling coil should then be altered until the meter reads $140 \pm 10\mu A$. The oscillator is then operating at the correct voltage of about 7 volts. The meter should then be removed and the end of the 47kΩ resistor reconnected. It is worthwhile checking the meter reading when the alignment of the oscillator has been completed.

Decoupling

The intermediate frequency amplifier (V2) is of conventional design and requires little comment. R9 controls the amplification of the unit and

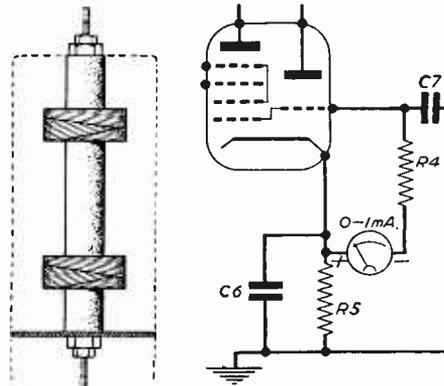



Fig. 2 (Left).—The low-frequency I.F. transformers (T1 and T2).

Fig. 3 (Right).—Using a 0-1mA meter for checking the oscillator voltage of the 6K8 frequency changer valve.

could be omitted if desired. It is important to use a reasonably large value for the decoupling condensers (because of the low intermediate frequency); 0.1μF should be regarded as the minimum value for these condensers.

A cathode follower detector is recommended because this type of detector does not impose any
(Continued on page 418)

A MASTER RELAY UNIT

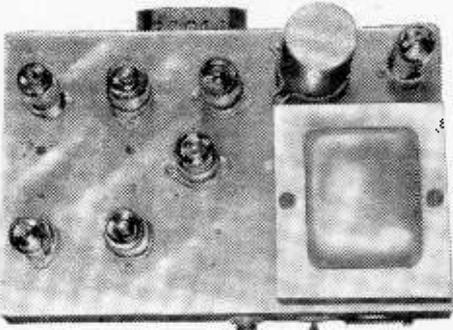

THE DIMENSIONS AND CONSTRUCTIONAL DETAILS OF THE CHASSIS By Hugh Guy

(Continued from page 242 of the May issue)

AS mentioned in the previous article, if loudspeakers are to be used instead of headphones, then power tetrodes capable of delivering sufficient power for the number of speakers used must be substituted for the cathode follower stages. The power pack must be able to

give sufficient current and a suitable supply together with one power output stage is shown in Fig. 3.

The successful distribution of signal power to drive a loudspeaker system requires a more careful layout than that for a headphone system if excessive power losses and the generation of crosstalk are both to be avoided. As a result the terminations at each listening point should be matched resulting in a slightly greater complexity of circuitry associated with each loudspeaker.

However, the distribution systems required for both headphone and loudspeaker reception are discussed later after the constructional details of the headphone relay unit have been described.


Constructional Details

The chassis is made from 18 s.w.g. aluminium sheet. All the marking out and drilling information is given in Figs. 4 and 7 from which it can be seen that an open-ended construction is used.

It is important that the R.F. section of the combined receiver be carefully screened. This is essential if R.F. instability is to be avoided. The two screens are made from 18 s.w.g. material and differ slightly in the way they are bent, as the separate drawings of each show—Figs. 5 and 6.

Two 1/2 in. struts in 1/4 in. material serve a double purpose. The first is to strengthen the assembly when they are fitted after the wiring is complete and the second is to provide a means of fixing the unit to its cabinet. These will be illustrated next month.

A simple front panel completes the metal work required. This panel is designed to be mounted directly on to the chassis, and countersunk fixing

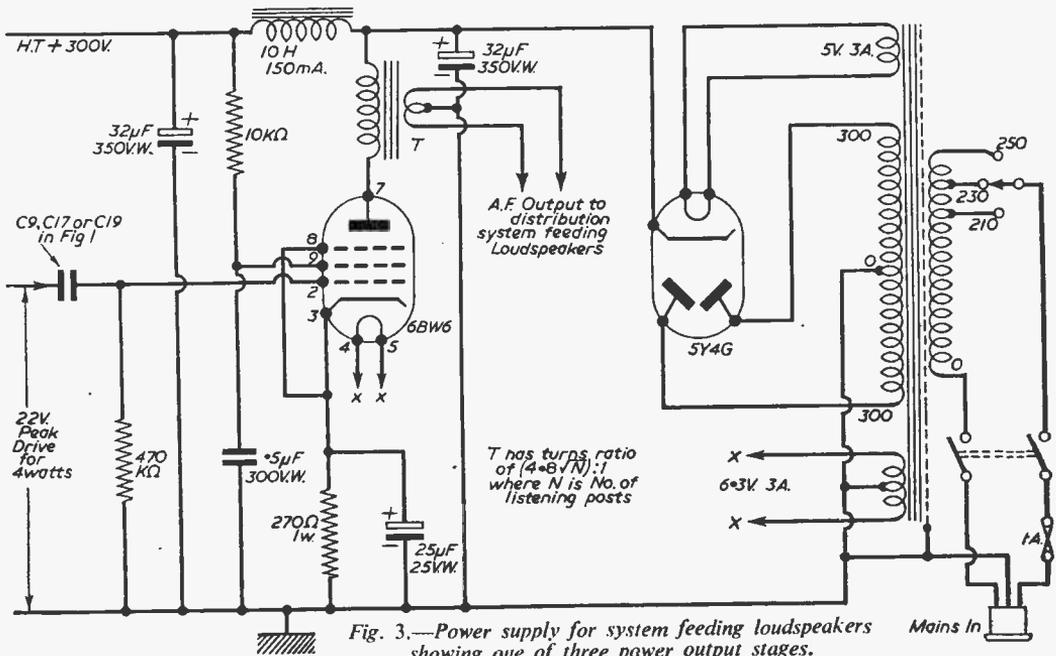

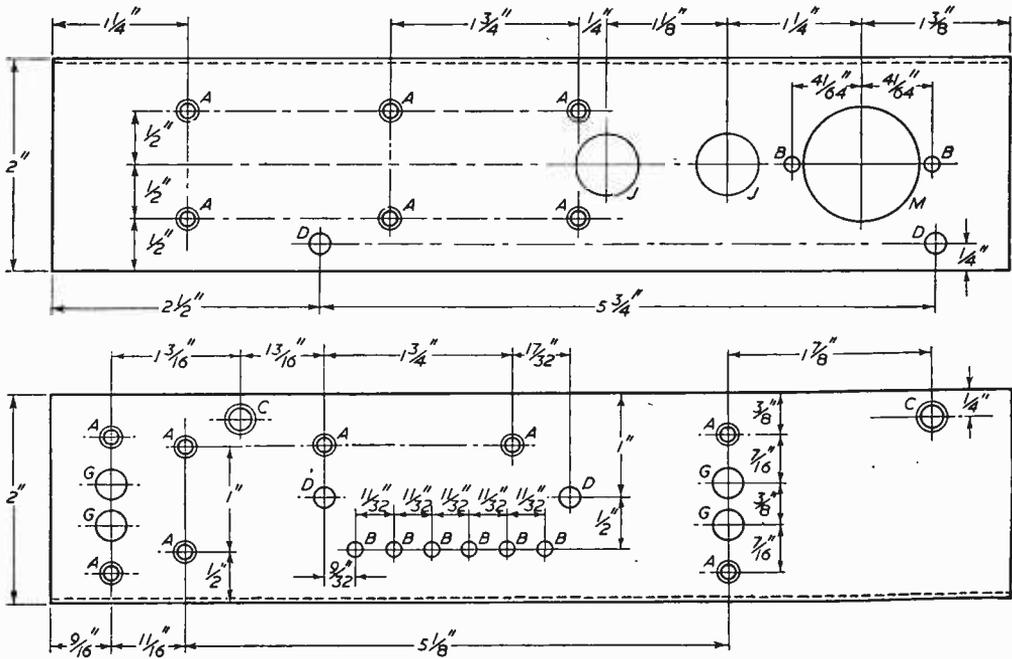


Fig. 4.—Drilling details of the front and rear chassis runners.

holes at the top and bottom of the panel provide a means for attaching whatever is used as a of the latter are left to readers, some of whom may want to incorporate the unit in the record player from which the third programme is obtained, while others will want to construct the device as a separate assembly.

The cabinet used in the models designed for hairdressing salon applications, is made of aluminium and stove enamelled white, with louvres at the top and sides for ventilation purposes.

Assembly

First screw the screening plates into position. Mount the valve holders, chassis sockets and terminal block, followed by the mains transformer and power supply electrolytic condenser. Leave the mains supply fittings until later as these have to be mounted through the corresponding holes on the front panel.

The underchassis view indicates where solder tags are required for earthing purposes

and in addition shows a five-way tag strip for distributing the H.T. supply.

Finally, before commencing the wiring fit the coils. The recommended variety manufactured by Messrs. Weymouth Radio Mfg. Co. Ltd. If the Light and Home programmes are both to be received on the medium wave-band then the types required are KA3 and KH3, aerial and H.F. coils respectively. Two of each kind will be needed. For long-wave reception of the Light

HOLE SIZES FOR FIGS 4 and 7

A	6BA C'sk (No. 31 Drill)	G	5/16 in. dia.
B	6BA (No. 31 Drill)	J	1/2 in. dia.
C	4BA C'sk (No. 26 Drill)	K	3/8 in. dia.
D	4BA (No. 26 Drill)	L	3/4 in. dia.
E	1/8 in. dia.	M	1 1/8 in. dia.
F	2BA (No. 12 Drill)		

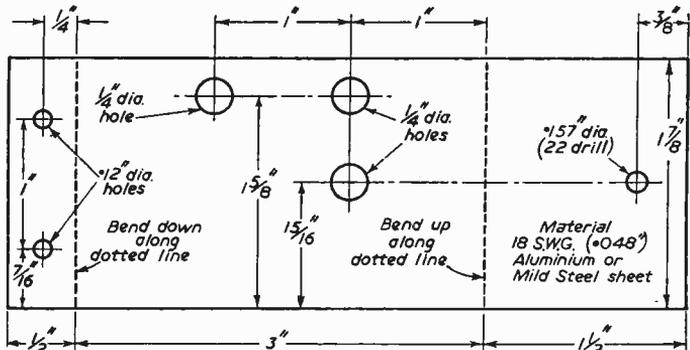


Fig. 5.—First screen for the R.F. section.

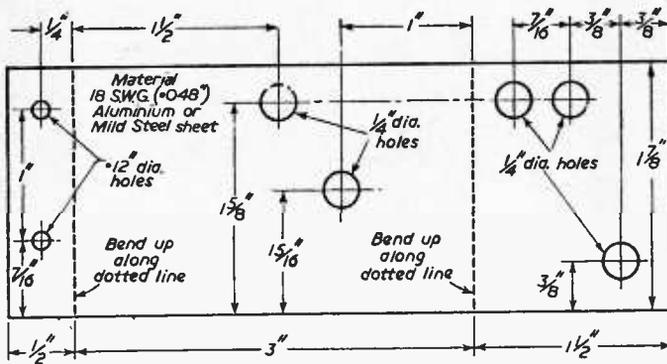


Fig. 6.—Second screen for the R.F. section.

programme, the appropriate coils are types KA1 and KH1.

Wire the heaters to the valves first using twisted pairs of wire to minimise hum radiation. The coils may now be wired. Do not apply too much heat to the connecting tags as wax pours everywhere making further soldering very difficult. The coils should be carefully orientated so that the shortest possible leads may be used. Next wire the resistors to the various stages. Finally, solder the condensers in place except for those tuning the coils. Some selection of values may be required for the latter on test. One important point to note is that, as far as possible, the earthed connections are returned to one common point on the chassis for each stage.

The Input Connection

The amplifier input connection is taken via a short length of screened lead to the grid point to prevent hum pick-up. If the input is provided by a fairly low impedance source then the screened lead may be dispensed with provided that the input connection is kept clear of the heater leads. Therefore all leads should be kept as short as possible for this reason and, as the underchassis view shows, as many components as can be are mounted directly between the valve pins that they link. For this reason, miniature components have been used as far as possible.

The front panel is now fixed and the mains plug, switch and fuse are fitted and wired. The unit is then ready for preliminary testing.

Testing

To facilitate testing, one receiver station is required. This should comprise essentially a three-position single pole switch, each of the three poles of which is connected to one of the programme, and with a pick-up connected to the wiper of which should be connected to one terminal of a headset. The other terminal of the latter is returned to the common earth point.

(To be continued)

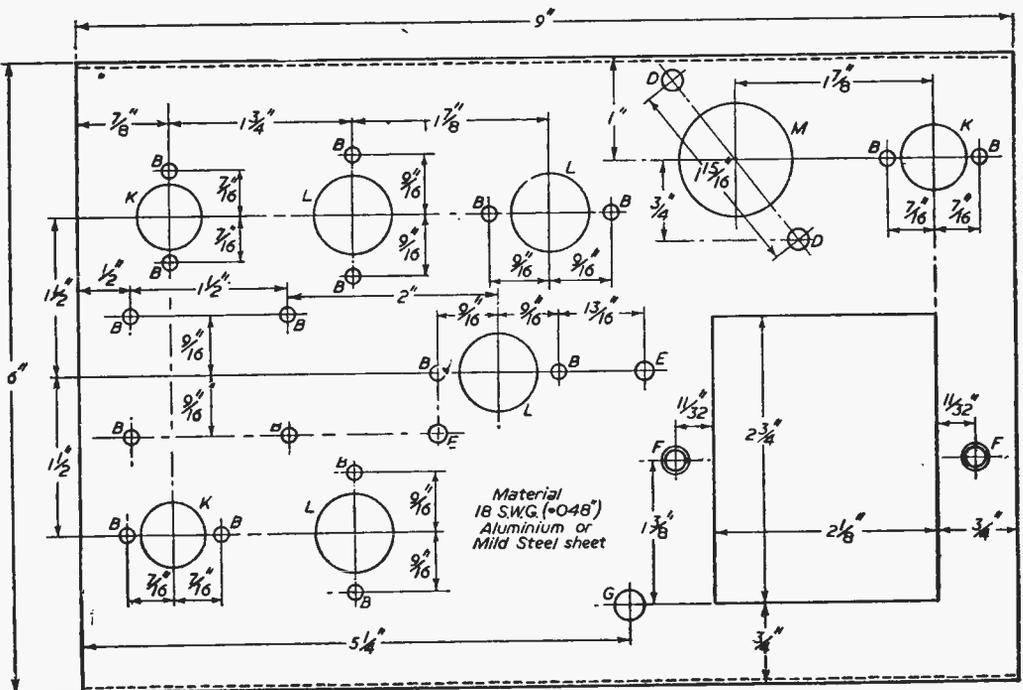


Fig. 7.—Details of the chassis.

C.R.T. ISOLATION TRANSFORMERS

TAPPED MAINS PRIMARIES
TYPE A. OPTIONAL 25% and 50% BOOST.
 2 V. OF 4 V. OR 6.3 V. OR 10.0 V. OR
 13.3 V. 12/6.

OUR LATEST SUPERIOR PRODUCT
TYPE A2. HIGH QUALITY, LOW CAPACITANCE,
 10/15 PF. OPTIONAL BOOST 25%, 50%,
 75%, 10/6 EACH.

TYPE B. MAINS INPUT, MULTI OUTPUT 2,
 4, 6.3, 7.3, 10 AND 13 VOLTS. BOOST 25%
 AND 50%. LOW CAPACITY. 21/-.

TRIMMERS, Ceramic, 30, 50, 70 pf., 8d.; 100 pf.,
 150 pf., 1/3; 250 pf., 1/6; 500 pf., 750 pf., 1/6.
 RESISTORS, Preferred values, 10 ohms to 10 meg.,
 1 w., 4d.; 1 w., 4d.; 1 w., 6d.; 1 1/2 w., 8d.; 2 w., 1/-
HIGH STABILITY. 1/2 w., 1/2, 2/- Preferred values,
 100Ω to 10 meg. 10/10, 5/-, 100Ω to 10 meg. D. 9d.,
 5 watt) **WIRE-WOUND RESISTORS** { 1/3
 10 watt) 25 ohms-10,000 ohms { 1/6
 15 watt) { 2/-
 15,000 ohms-50,000 ohms. 5 w., 1/9; 10 w., 2/3.

GEVART GEVASONOR

50% extra long lay plastic tape, 1,700 ft. 7in.
 Reel, 35/-; 850ft. 5in. reel, 21/-.

SUPERIOR 1,200 ft. Plastic Tape on 7" Plastic
 Reels. Quality Guaranteed, 21/-.

SPARE REELS, ALL SIZES, 3/-.

"Instant" Bulk Tape Eraser, 200/250 v. A.C.
 for any make of size of tape, 27/6.

O.P. TRANSFORMERS. Heavy Duty 50 mA., 4/6.
 Multiratio, push-pull, 7/6. Miniature, 3/4, etc.; 10 H.
 L.F. CHOKES 15/10 H. 60/65 mA., 5/-; 40 H.
 85 mA., 10/6; 10 H. 150 mA., 14/-.

MAINS TRANSFORMERS 200/250 v. A.C.
 STANDARD, 250-0-250, 80 mA., 1.3 v. 3.5 a.
 tapped 4 v., 4 Rectifier 6.3 v. 6.3 v. 2 a.
 2 a. or 4 v. 2 a. Ditto, 330-0-330 22/6
 MINATURE, 200 v. 20 mA., 6.3 v. 1 a. 10/6
 MIDGET, 220 v. 45 mA., 6.3 v. 2 a. 15/6
 SMALL, 250-0-250, 100 mA., 6.3 v. 3 a. 19/6
 STANDARD, 250-0-250, 65 mA., 6.3 v. 3 a.
 3.5 a. 17/6
 HEATER TRANS. 6.3 v. 1 1/2 amp. 7/6
 Ditto, tapped sec. 2, 4, 6.3 v., 1 1/2 amp. 8/6
 Ditto, sec. 6.3 v. 3 amp. 10/6

ALADDIN FORMERS and core. 4in. 8d.; 4in. 10d.
 3in. FORMERS 5937/8 and Cas TV12, 1in. sq. x
 2 1/2in. and 1in. sq. x 1 1/2in. 2/- each, with cores.
 TYANA—Midget Soldering Iron, 40 w., 16/9.

REMPLOY Instrument Iron, 25 w., 17/6.
MAINS DROPPERS. 3in. x 1 1/4in. Adj. Sliders,
 0.3 amp., 750 ohms, 4/2. 0.2 amp., 1,000 ohms, 4/3.
LINE CORD. 3 amp., 60 ohms per foot, 2 amp., 100
 ohms per foot, 2 way, 6d. per foot, 3 way, 7d. per ft.

LOUDSPEAKER P.M. 3 O.E.M. 2 1/2in. & 3in. 17/6.
 1in. Plessey, 19/6. 6in. x 4in. Rola, 18/-, 6 1/2in. R.A.
 18/6, 8 x 5in., 21/-, 10 x 6in., 27/6. 10in. Rola, 30/-.
 Hi-Fi Tweeter, 25/-, 12in. R.A., 38/-, 12in. 15 ohm
 10 v. Plessey, 45/-.

SPENFORIAN HELIOT 10in. 3 to 15ohm 10 w., 99/6.
 12in. Baker 15 watt 3 ohms, or 15 ohms, 105/-.
CRYSTAL DIODE (G.E.C.) 2/-, GEX34, 4/-.

HIGH RESISTANCE PHONES. 4,000 ohms, 16/8 pr.
MIKE TRANS. 5/1, 3/9 etc.; 100Ω, Potted, 10/6.
SWITCH CLEANER. Plug socket, sheet, 4/3 1/2in.


TWIN GANG TUNING CONDENSERS. 3x5 pf.
 miniature 1in. x 1 1/2in. 10/-, .0005 Standard
 with trimmers, 9/-; less trimmers, 8/-; midget, 7/6.
SINGLE. 50 pF., 2/6; 80 pF., 1/0 PF., 160 pF., 7/-.
 801Ω dielectric 100, 300, 500 pf. 3/6.

SPEAKER FEET. Expanded Metal Sliver, 15 1/2in. x
 9 1/2in. 2/- each. **GOLD CLOTH.** 7in. x 25in., 5/-;
 25in. x 30in., 10/-, Tylan 4d. 6in. wide, 10/-; 2ft.
 3in. wide, 5/- Samples, 8 A.E.

New and boxed **VALVES** 90-day Guarantee.

1R5	8/6	6K8G	8/6	EAB30	HAB30
1R5	8/6	6L0G	10/6		10/6
1T4	8/6	6N7	7/6	EB4	6/6
2X2	3/6	6Q7G	10/6	EB33	8/6
384	8/6	68A7	7/6	EB41	6/6
3V4	8/6	68J7M	10/6	EB80	12/6
5U4	8/6	68N7	8/6	EB34	12/6
5Y3	8/6	6V0G	7/6	EC70	11/6
6Z4	10/6	6E6	7/6	EC12	6/6
6AM6	8/6	6X5	7/6	EC12	12/6
6B8	5/6	12A7	9/6	EF30	7/6
6BE6	7/6	12A7	9/6	EF41	10/6
6BH6	10/6		9/6	EF50	5/6
6BW6	10/6	12BE6	10/6	EF80	10/6
6D6	7/6	12K7	8/6	EF91	8/6
6FG6	7/6	12Q7	8/6	EF92	5/6
6HG	3/6	35L6	8/6	EL32	5/6
6J5	6/6	65Z4	9/6	EL34	10/6
6J6	7/6	69	10/6	EM81	12/6
6J7	8/6	807	6/6	EZ40	10/6
6K6GT	8/6	954	1/6	EZ80	9/6
6K7G	5/6	EA50	1/6	EL145	1/6

FINEST VALUE

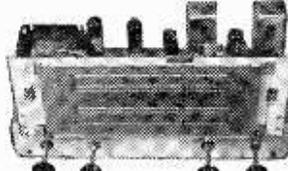

1959 RADIOGRAM CHASSIS

THREE WAVEBANDS FIVE VALVES
 S.W. 16 m.—50 m. LATEST MULLARD
 M.W. 200 m.—650 m. ECH42, EF41, EBC41,
 L.W. 800 m.—2,000 m. EL41, EZ40,
 12-month guarantee.

A.C. 200/250 v. 4-way Switch; short-Medium-
 Long-Gram. A.V.C. and Negative feedback
 4.2 watts. Chassis 1 1/2 x 6 1/2 x 2 1/2in. Glass dia
 12 1/2in. x 5 1/2in. horizontal or vertical 10in. x 4 1/2in.
 2 Pilot Lamps. Four Knobs Walnut or Ivory.
 Aligned and calibrated. Isolated Chassis.

£9.10.0 Carr. & Ins. 4/6.

TERMS: Dep. £5.0.0 and five monthly of £1.
MATCHED SPEAKERS FOR ABOVE CHASSIS.
 8in., 17/6; 10in., 25/-; 12in., 30/-.



UA8 World's Finest 4-Speed Autochanger

OUR PRICE £6.19.6

TERMS: Dep. £3.10.0 and four monthly of £1.
 Stereo Model UA8 £9.19.6; UA12 £11.17.6.

COLLARO LATEST MODEL

HIGH-FIDELITY AUTOCHANGER

4-SPEEDS-10 RECORDS

With Studio "O" pick-up

BRAND NEW IN MAKER'S BOXES

OUR PRICE £7.19.6 post free.

BUILD THIS REPRODUCER
BARGAIN SINGLE PLAYER KIT
 Ready for immediate assembly.

4-speed Collaro "Junior" Unit £4 12 6
 Handsome case, 17 1/2 x 13 x 7 1/2in.,
 with room to play 12in. records £2 5 0
 Ready-built 3-watt amplifier with
 two valves and loudspeaker £3 12 6

or **£9.15.0** complete kit post free.

ALUMINUM CHASSIS. 18 s.w.g. undrilled.
 With 4 sides, riveted corners and lattice fixing
 holes, 2 1/2in. sides, 7 x 4in., 4/6; 9 x 7in., 5/9;
 11 x 7in., 6/9; 13 x 9in., 8/6; 14 x 11in., 10/6;
 15 x 14in., 12/6; 18 x 16 in., 16/6.

TRANSISTORS, GENUINE PVE GOLTOP.
 Audio, 10/-, R.F. (3 Mc/s average), 18/-.
 Power, 20/-, Complete data sheets supplied.

CRYSTAL MIKE insert by Acos, precision
 engineering. Size only 1in. x 3 1/2in., 6/6.

HI-GAIN BAND 3 I.T.A. PRE-AMP KIT.
 Cascode circuit with valve EOC34. Price 29/6.
 With Power Pack, 48/6. Plans only 6d.
 Band 1 B.B.C. version same prices.

TELETRON "TRANSIDNEY"
MIDGET SUPERHET PORTABLE 6" x 4" x 1 1/2"
 6 transistors, printed circuit, Ferrite aerial.
 All parts and cabinet, £11.9.6. Plans 9d.
 We include 6 Goltop or Mullard Transistors
 for maximum performance.

BBC T.V. TRANSISTOR RADIO. Complete kit
 32 G. phones 7.8 extra. Deaf Aid Ear-
 piece 12.6. Special Lead 2.6.

GARRARD 45P. SINGLE PLAYER

AUDIO PERFECTION

Designed to play 16, 33, 45, 78 r.p.m. Records
 7in., 10in., 12in. Lightweight Xtal pick-up.
 GC2 turnover head, two separate sapphire styli.

OUR PRICE £8.0.0 each. Post Free.

De luxe cabinet, quality amplifier and 6 1/2 in.
 speaker, £6.15.0 or complete kit, £14.10.0.

Volume Controls 80 ohm CABLE COAX

Long spindles. Guaranteed 1 year. Midget
 5K ohms to 2 Meg. Losses cut 50%.

No Sw. D.P.S.W. Stranded core, 9d. yd.
 3/- 4/6 Fringe quality 1/6 yd.
 Linear or Log Tracks. Air Spaced.

COAX PLUGS... 1/- **DOUBLE SOCKET** ...1/3
SOCKETS ... 1/- **OUTLET BOXES** ...4/6
BALANCED TWIN FEEDER yd. 6d. 80 or 300 ohms.
DITTO SCREENED per yd. 1/6. 80 ohms only
WIRE-WOUND POTS, 3 WATT. Pre-set Min.
 T.V. Type. All values 25 ohms 25 K., 3/-
 30 K., 50 K., 4/-, (Carbon 30 K., 2 meg., 3/-).

WIRE-WOUND 4 WATT. Pots 2 1/2in. Spindle
 Values, 100 ohms to 50 K., 6/8; 100 K., 7/6.

CONDENSERS. New Stock. .001 mfd. 7 kV.
 T.T.C. 5/6; 10/10, 20 kV., 9/6; 100 pf. to 500 pf.
 Micas, 6d. Tubular 500 .001 to .01 mfd., 9d.;
 .05 .1, 1/-; .25, 1/6; .5/350 v., 1/9; 1/350 v., 9d.;
 .01/2,000 v., 1/8; .1 mfd., 2,000 volts, 3/6.

CERAMIC CONDS. 500 v., .3 pf. to .01 mfd., 9d.
SILVER MICA CONDENSERS. .01 mfd. to 500
 pf., 1/-; 600 pf. to 1,000 pf., 1/3 (both tolerances
 ± 1 pF.) 1.5 pf. to 47 pf., 1/8. Ditto 15, 50
 to 815 pf., 1/8; 1,000 pf. to 5,000 pf., 2/-.

I.F. TRANSFORMERS 7/6 pair.

465 Kc/s Slus Tuning Miniature Can, 2 1/2in. x
 1 in. Rich and good bandwidth.
 By Re Radio. Data sheet supplied.

Wearite M800 I.F. 465 Kc/s, 12/6 per pair.

Wearite 550 I.F. 465 Kc/s, 12/6 per pair.

NEW ELECTROLYTICS. FAMOUS MAKES

TUBULAR TUBULAR CAN TYPES

1/350 v. 2/- 64/350v. 5/8 8/500v. 3/-
 2/450 v. 2/3 100/25v. 2/- 13/600v. 4/-
 4/450 v. 2/3 250/25v. 2/8 32/350v. 4/-
 8/450 v. 2/3 500/12v. 3/- 100/270v. 5/6
 8/500 v. 2/9 8+8/450v. 4/6 2,500/3v. 4/6
 16/450v. 3/6 8+8/500v. 5/6 6,000/6v. 5/-
 16/500v. 4/- 8+8/16/500v. 5/6 50+50/350v. 4/6
 32/450v. 5/6 8+8/15/500v. 5/6 50+50/350v. 7/-
 25/25v. 1/9 16+16/450v. 5/6 64+120/270v. 7/6
 60/25v. 2/- 32+32/350v. 4/6 64+120/350v. 11/6
 50/50v. 2/- 32+32/500v. 7/6 100+200/275v. 12/6

**SEMTECEL RECTIFIERS. E.H.T. TYPE FLY-
 BACK VOLTAGE.** K325 2 kV., 5/-; K3/40 3.2
 kV., 7/-; K3/45 3.6 kV., 7/8; K3/50 4 kV., 8/-;
 K3/100 8 kV., 14/6; 50 c.p.s. voltage, 20% of above.

MAINS TYPE SELENIUM 300 v. 85 mA., 7/6.
CONTACT COOLED 250 v. 50 mA., 7/6; 60 mA., 8/6;
 85 mA., 9/6; 200 mA., 21/-; 300 mA., 27/6.

COILS Warranted "P" type, 300 Ohm. Midget
 "Q" type, add cost, 2/- core from 4/-. All ranges.

TELETRON L. & Med. T.R.F. with reaction, 3/6.
FERRET ROD AERIALS. M.W. 8/8; M & L, 12/6.
F.R.P. COILS A/H/F. 7/- pair. H.F. CHOKES, 2/6.
TERRISTOR. 7in. x 3/8in. dia., 2/6.

JASON E.M. TUNER COIL SET, 26/-. H.F. coil,
 aerial coil, oscillator coil, two I.F. trans.
 10.7 Mc/s. Ratio Detector and heater choke.

Complete kit book using our book, 2/6.
COMPLETE JASON E.M. KIT WITH VALVES,
 £8.15.0. Fringe area kit, 22/6 extra.

MULLARD 3-8 AMPIFIER READY BUILT.
 Spare Power for Tuner, etc., 27.1.6.

FULL WAVE BRIDGE SELENIUM RECTIFIERS:
 2, 6 or 12 v. 1 1/2 amp., 8/9; 2 a., 11/3; 4 a., 17/6.
CHARGER TRANSFORMERS. Tapped input 200/
 v. for charging at 2, 6 or 12 v., 1 1/2 amp., 15/6.
 2 amp., 17/6; 4 amp., 22/6. Circuit included.

VALVE and T.V. Tube equivalent books, 5/-.
TOGGLE SWITCHES. S.P. 2/-, D.P. 3/6, D.P.D.T. 4/-.
WAVECHANGING SWITCHES

5 p. 4-way, 2 water long spindle ... 6/6
 2 p. 2-way, or 3 p. 2-way short spindle ... 2/6
 2 p. 6-way, 4 p. 2-way, 4 p. 3-way long spindle ... 3/6
 3 p. 4-way, or 1 p. 12-way long spindle ... 3/6


VALVE-OLDERS. Pax. Int. Oct. 4d. EF50, EA50,
 6d., B12A, CRT, 13/-, Eng. and Amer. 4, 5, 6, and
 7 pin. 1.1. MOULDED M.D. and Int. Oct., 8d.
 B7C, B8A, B8C, B9A, 8d. B7C with can, 1/6.
 B9A with can, 1/9. CERAMIC EF50, B7C, B8A,
 Int. Oct., 1/-, B7C with can, 1/8.

RADIO COMPONENT SPECIALISTS

OUR ONLY ADDRESS
 337 WHITEHORSE RD.,
 WEST CROYDON

Postal service. 1/-, over 12 free. (Export Extra.) C.O.D. 1/6. (Wed. 1 p.m.) Catalogue 1/6. THO 1665. Buses 133 or 68

● **new and enlarged edition NOW READY**

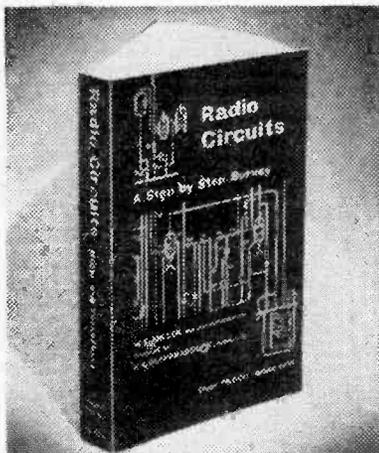

RADIO CIRCUITS

by *W. E. Miller, M.A. (Cantab), M.Brit.I.R.E., revised by E. A. W. Spreadbury, M.Brit.I.R.E., associate editor of "Wireless & Electrical Trader"*

This standard introduction to superheterodyne receiver circuits has been greatly extended and brought completely up-to-date. The whole text has been revised in the light of the latest developments, and new chapters have been added on transistors, car radio and F.M. receivers. Although virtually a new book, it is still written in the same simple, non-mathematical style that has received such widespread acclaim.

over 75,000 copies of previous editions sold

15s. net by post 15s. 10d. 172 pp. Illustrated

obtainable from leading booksellers *Published by*
Iiffe & Sons, Ltd. Dorset House, Stamford Street, London S.E.1

62AK : This Month's Bargains

SPECIAL OFFER ROTARY CONVERTERS

6 v. input, 250 v., 125 mA. output. Excellent machines. 5½ in. x 3 in. x 3 in. ONLY 17/6 each. P. & P. 3/-
12 v. Miniature Rotary Converters. Only 4½ in. x 2½ in. Output 360 v., 30 mA. or 310 v. 70 mA. NEW LOW PRICE 12/6 ea. or 22/6 pr., p. & p. 1/6.

VOLTMETERS. Dual range 0-5 v. and 0-100 v. voltmeters, M.C. 1,000 Ω/v. Ranges easily extended. With test prods and leads. Complete in solid leather carrying case, 6½ in. x 5 in. x 2½ in. A gift at 25/- post free.

HEADPHONES. H.R. Type 4,000 ohms, very sensitive. Only 12/6 pr. Post 1/6. C.L.R. type (low res.), 8/6. Post 1/6.

SHADED POLE MOTORS for Tape decks or gram. units, 3-hole fixing. Twin Coil closed field type; 200/240 v. 50 c/s, 15/- ea. or 27/6 for 2, p. & p. 2/-.

AERIAL WIRE. Copper, 7.25 stranded; 140ft., 10/-; 70ft., 5/-, Hard Drawn 14g.; 140ft., 17/-, 70ft., 8/6. P & P. 2/-.

GLASS AERIAL INSULATORS, 3in., 1/6 ea., or 6 for 7/6. P. & P. 1/6. Also **CERAMIC "T"** pieces for centre of dipoles. 1/6 each.

CONDENSERS. 8 μF 600 v. Trop. 750 v. normal condensers. NEW, ex W.D. stocks, 5/6. P. & P. 1/6.

ABSORPTION WAVEMETERS, 3 to 35 Mc/s in 3 switched bands. Complete with indicator bulb. 17/6 post free.

Send for our NEW 53-page
ILLUSTRATED CATALOGUE
P.O. or stamps, 1/3.

CHAS. H. YOUNG LTD.

Dept. 'P', 110, Dale End, Birmingham, 4. (CEN 1635)

No C.O.D. on orders under £1.

Please Print Your Name and Address

TRANSISTOR

PRICES SLASHED

RED SPOT, 7/-. **WHITE SPOT, 10/-.**

GREEN/YELLOW, 7/6. RED/YELLOW, 15/-.

EDISWAN (See P.W. March for full details, page 87).

NB 104, 10/-; XA 104, 18/-; XA 103, 15/-.

ALL MULLARD, BRIMAR, NEWMARKET, and EDISWAN/MAZDA TRANSISTORS SUPPLIED

CRYSTAL DIODES. STILL ONLY 1/- each.

TRANSISTOR CIRCUITS

Maxi "Q" (6 transistor), 8d. Three Dee (3 transistor), 11d. Major-7 (uses 7in. x 4in. speaker), 1.61 Mini-7 Mk. II, 1/6. R.E.P. Car Radio (7 transistor 2 watt output), 2/-.

1 Valve Battery Circuit (beginners), 11d.

TRANSISTOR HOLDERS, 1/3.

COILS.—Type DRR/2, 4/-; Type DRX/1, 2/6.

TUNING CONDENSER 500 pF (.0005 mfd.) Variable. Solid Dielectric, 4/- each.
Trial Packet **ERSEN MULTICORE SOLDER**, enough for 200 joints, 9d.

BATTERIES. EVER READY transistor Type PP-4, 2/3.

HEADPHONES.—Ex W.D. but brand new. Special Bargain Price, 8/11 per pair. Hurry...

B9A Valve Holders. Screening can and spring, complete, ONLY 1/6.

MICROPHONES.—Acos Type 39-2. Usual Price 55/-. OUR PRICE 30/6.

RECORDING TAPE.—Standard P.V.C. 600ft. on 5in. spool. 13/6.

FERRITE ROD. 1in. dia. x 8in. long, 2/6.

Three Dee, 3 Transistor Kit, 75/-; Circuit, etc., 11d.

RESISTORS, all Values, 10%, ± watt, 6d. each.

ELECTROLYTICS (CAN TYPE). 32-32/450 v., 6 6; 50-50/400 v., 7/-; 100-200/275 v., 8/9; 60-250/275 v., 8/9;

64-120/350 v., 9/6; 24-24/350 v., 4 6 each.

TUBULAR, (wire ended) 16 mfd./450 v., 2/4; 16-16/450 v., 4/-; 8-8/450 v., 2/9; 8-16/450 v., 2/9; 50/50 v., 1/6; 25/25 v., 1/6.

TERMS: Cash with Order, or C.O.D. (Orders over £2 only).

ALL OUR PRICES ARE POST PAID.

OAKFIELD RADIO

THE TRANSISTOR PEOPLE

44 Oakfield Road,

Stockport, Cheshire.


YOU CAN SAVE 1/- in every £1. Send 1/6 for our 56-page Catalogue and receive your order number for the Amazing Credit Coupon Scheme, Free Lists, Bargain Offers, Latest News, etc., etc. **ORDER NOW.** Don't Delay.

Crystal Heterodyne Frequency Meter


A USEFUL ACCESSORY FOR
THE AMATEUR TRANSMITTER
WHICH MAY BE ADAPTED
ALSO FOR SERVICING

By A. G. Barnsley

AT one time or another most of us have had need for some means of measuring frequency to a reasonable degree of accuracy. The Heterodyne Frequency Meter is the instrument usually employed for such measurements. It is in any case an essential piece of equipment for any enthusiast to build. Indeed, if the reader is an amateur using a variable frequency oscillator (V.F.O.) to drive his transmitter, the G.P.O. will insist on his being able to measure his frequency to an accuracy of 0.1 per cent. The instrument to be described will easily measure to this accuracy. Furthermore, if a modulator is included, its use is

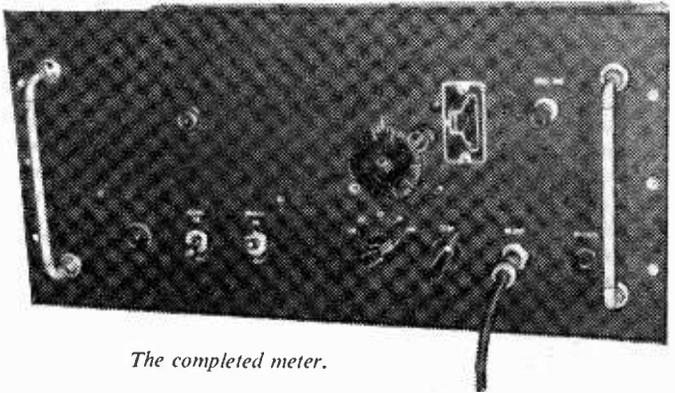

The completed meter.

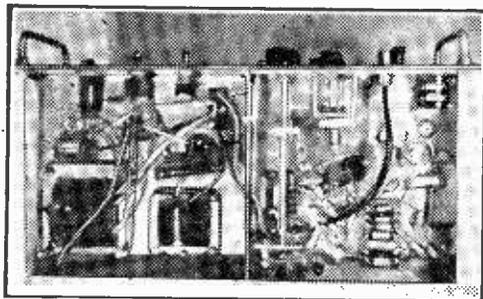

View of the underside of the meter.

extended to cover radio servicing. It was felt necessary to keep the cost of the unit as low as possible, and in fact, the majority of the components will probably be at hand already.

Principles of Operation

The arrangement, as shown in Fig. 1, is the basic system of the Heterodyne Frequency Meter. The variable oscillator, which is abundant in harmonics, is usually designed to cover the lowest frequency expected to be used. Measure-


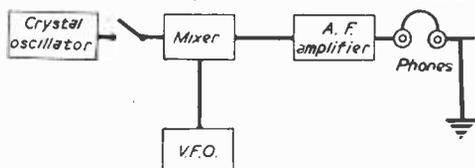


Fig. 1.—A block diagram of the basic system of the meter.

ments of the higher frequencies can be effected by using the harmonics of the V.F.O.

The crystal oscillator operates at a frequency of 100 kc/s and is the frequency standard of the instrument. The output of this oscillator together with that from the V.F.O. is fed to a mixer valve, and, as a result, beats will be heard between harmonics of the V.F.O. and harmonics of the crystal oscillator. The resultant audio frequency is amplified by V4 and can be heard in the 'phones. The frequency of the V.F.O. may be checked every 100 kc/s and any discrepancy may be tuned out by the "zero" control, C1.

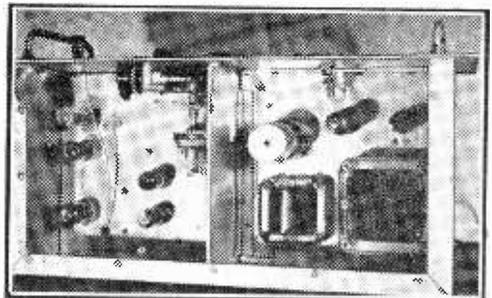We now have a variable source of R.F. accurately checked to as high a frequency as the maximum harmonic frequency of the V.F.O., and to help in this direction a separate amplifier is used with its anode circuit broadly tuned by means of switched coils resonating with the stray circuit capacitances at 144.50 and 28 Mc/s. (The information for winding these coils is given



Plan view showing the layout.

in the table.) A radio frequency choke is connected to the fourth position and gives ample strength at the lower frequencies.

The Circuit

The circuit, which is shown in Fig. 2, uses a crystal oscillator of fairly conventional form,

with provisions for switching it off when the V.F.O. only is used. This circuit has the advantage that no tuning coil is required and will oscillate readily with crystals widely differing in frequency, amplitude of oscillation being adjusted by C10.

The V.F.O. uses a Z77 in an E.C.O. circuit, tuning from 3.5 Mc/s to 4.0 Mc/s, and is quite stable in operation provided good quality components are used. One half of a 12AX7 acts as a mixer for calibration purposes and the other half as an A.F. amplifier. If a pair of phones are plugged into the jack, the instrument becomes a satisfactory monitor, R.F. being picked up by means of a short wire connected to the "crystal out" terminal. In order to obtain the utmost stability from the V.F.O., a neon stabiliser is used to supply H.T. to the screen grids of both the V.F.O. and harmonic amplifier and also to the crystal oscillator.

Calibration

Switch the instrument on for about 15 minutes to allow it to warm up. Then, if it is thought necessary to check the accuracy of the crystal, this can be accomplished by running a short lead from the "crystal out" terminal near to the aerial input of a receiver that will cover the range required, and, by tuning the receiver to one of the National Physical Laboratories

COMPONENTS LIST

CH1—15 H., 60 mA.
 T1—250-0-250v., 60 mA : 6.3v., 3.0 A.
 LP1—6.3v. M.E.S. indicator bulb.
 S1—S.P.S.T. xtal on/off.
 S2—5 way single pole Yaxley.
 S3—D.P.D.T. mains on/off.

RESISTORS AND CAPACITORS

R1, 7, 10, 11—100K.	C3—360pF.
R2, 5, 13—470K.	C4, 6, 8, 11—100pF.
R3—470Ω	C5, 9, 12, 17, 18—.01μF.
R4—15K.	350 v.w.
R6—10K.	C7, 14—.01μF, 350 v.w.
R8—30 or 33K.	C10—75pF. trimmer.
R9—15K.	C13—10pF.
R12—2.7K.	C15—47pF.
C1—3.50pF.	C16—470pF.
C2—5-150pF.	C19, 20—16μF., 350 v.w.

standard frequencies transmissions on, say, 2.5 Mc/s or 5 Mc/s and with the crystal switched in, zero beat, or a very low audio frequency should be heard.

The receiver may also be used to check provisionally the fundamental frequency range of the V.F.O. which should be from 3.5 Mc/s to 4.0 Mc/s: If the low end is not correct, the frequency may be increased by reducing C3, or vice versa. Having obtained the right limits for the

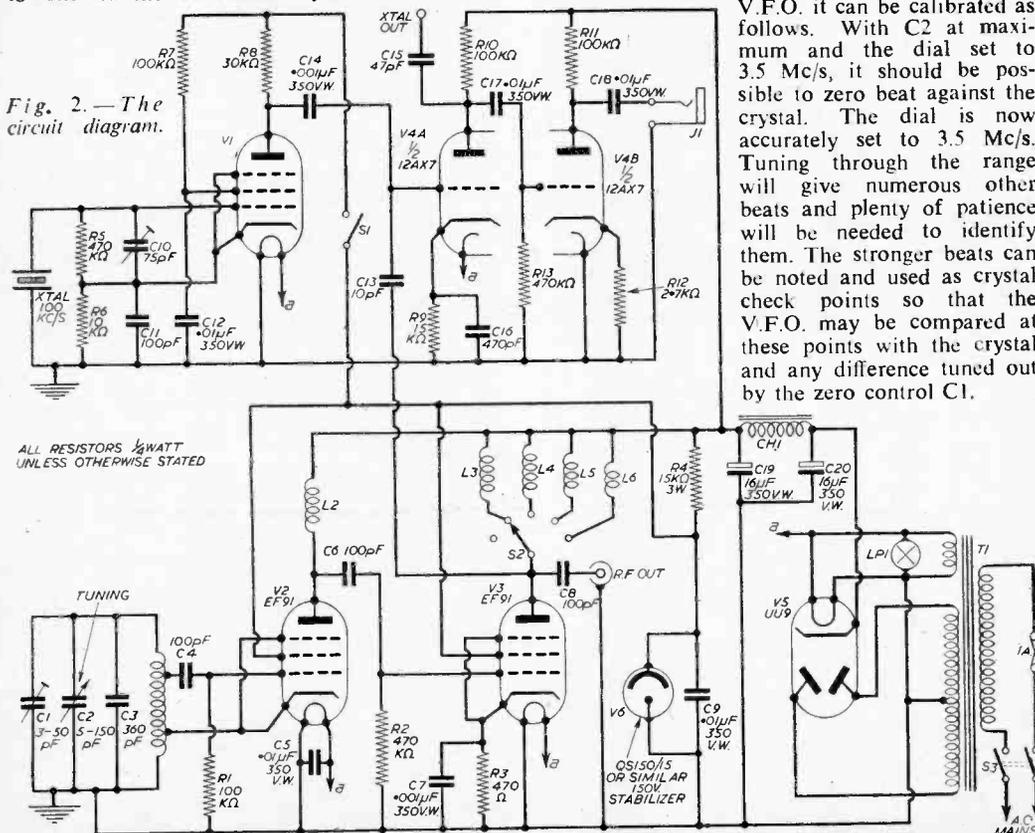



Fig. 2.—The circuit diagram.

ALL RESISTORS 1/2WATT UNLESS OTHERWISE STATED

V.F.O. it can be calibrated as follows. With C2 at maximum and the dial set to 3.5 Mc/s, it should be possible to zero beat against the crystal. The dial is now accurately set to 3.5 Mc/s. Tuning through the range will give numerous other beats and plenty of patience will be needed to identify them. The stronger beats can be noted and used as crystal check points so that the V.F.O. may be compared at these points with the crystal and any difference tuned out by the zero control C1.

Fourth Harmonic

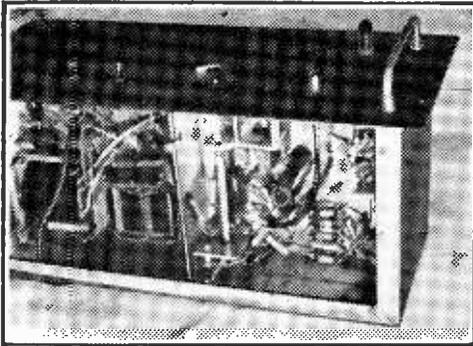Again, the receiver can be used as an auxiliary. For example, if the receiver is adjusted to pick up the fourth harmonic of the V.F.O. (14 Mc/s to 16 Mc/s), and this harmonic beats against the crystal, the 100 kc/s intervals on that range will give 25 kc/s intervals on the fundamental. A number of such points can be obtained and plotted on graph paper, or better still, five



Another view of the underside of the meter.

separate graphs with 100 kc/s coverage on each graph and at least one crystal check point.

Provided care is taken to keep the wiring short and rigid a stable instrument should result.

COIL WINDING DATA

Coil	No. of turns	Wire gauge	Former diameter	Comments
L4 ...	24	19 s.w.g. enamel	$\frac{1}{4}$ in.	Close wound
L5 ...	11	19 s.w.g. enamel	$\frac{1}{4}$ in.	Close wound
L6 ...	2	18 s.w.g. enamel	$\frac{1}{4}$ in.	Spaced to be $\frac{1}{2}$ in. long

L1 : 18 turns of 20 s.w.g. enamelled wire wound on a $\frac{1}{4}$ in. diameter paxolin former tapped at 6 and 15 turns from earthy end.

L2 L3 : 2.5 mH. chokes.

Large diameter wire (16 s.w.g.) is recommended for all leads associated with the tuned circuits, and should run as directly as possible. The variable capacitors should be firmly mounted, and all the other components should be wired on tag boards or straight across the pins of their respective valveholders. A solidly made cabinet is also desirable to house the instrument.

New RCA Transistors

RCA-2N649 is a new alloy-junction transistor of the germanium n-p-n type. It is designed for use along with its p-n-p counterpart, RCA-2N408, in class B complementary-symmetry power output stages of compact, transformerless battery-operated portable radio receivers, record-players, and audio amplifiers operating at battery-supply voltages up to 9 volts. In such equipment, the 2N649 ensures good frequency response and relatively high power output at low cost. This transistor may also be used in conventional class B push-pull and in class A audio amplifier circuits.

In a typical class B complementary-symmetry circuit, a 2N649 (n-p-n type) and a 2N408 (p-n-p type) used together in the output stage and driven by a 2N408 as a class A driver are capable of providing a power output of approximately 100 milliwatts at a power gain of 54dB.

In a typical push-pull circuit, two 2N649's used in the output stage and driven by another 2N649 as a class A driver are capable of providing a power output of approximately 100 milliwatts at a power gain of 66dB.

The 2N649 has a D.C. current gain which is essentially constant over the operating current range to insure circuit linearity, a collector cut-off current of only 14 microamperes to ensure stable performance under varying ambient temperature, and excellent uniformity of characteristics to provide unit-to-unit interchangeability.

The 2N649 has flexible leads and is hermetically sealed in a metal case.

Drift Transistors


RCA also announce three new drift transistors of the germanium p-n-p type. These transistors are designed specifically for A.M. Broadcast Band applications in car receivers—the 2N640 for radio-frequency amplifier service, the 2N641 for 262.5 kc/s or 455 kc/s intermediate-frequency amplifier service, and the 2N642 for converter service. These transistors provide the equipment designer with a transistor complement which makes practicable quantity-produced 5-transistor car receivers utilising an audio driver stage and a single-ended output stage, and featuring high signal-to-noise ratios, high gain per stage, and good A.G.C. characteristics.

The 2N640 in an unneutralised circuit is capable of providing a power gain of 28dB at 1.5 Mc/s; the 2N641, in a neutralised circuit, power gains of 41dB at 262.5 kc/s. and 40dB at 455 kc/s; and the 2N642, a useful conversion power gain of 40dB at 1 Mc/s.

These drift transistors have excellent uniformity of characteristics, exceptional stability, and low feedback capacitance made possible by their unique design. Furthermore, close manufacturing controls for the small-signal parameters insure optimum performance in car receivers operating over the frequency range of 535 kc/s to 1,640 kc/s.

The 2N640, 2N641 and 2N642 utilise flexible leads and are hermetically sealed.

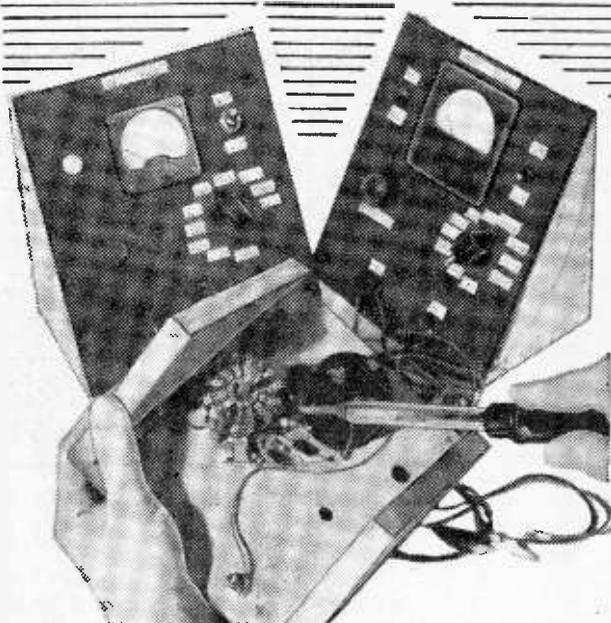Additional information on these components may be obtained from: RCA Great Britain Limited, Windmill Rd., Sunbury, Middx.



A Beginner

THIS NEW SERIES OF CONSTRUCTION
OF THE POPULAR "BEE"

too much current from the circuit being tested and thus give a false reading unless a battery or other large source is being tested. What is required is a sensitive meter which will take a very small current, but at the same time will stand up to a fair amount of mechanical mishandling (e.g., being pulled off the bench) and electrical overloading (e.g., putting the meter on 100V when it is set for 10V). With this in mind the basic movement is a one milliamp moving-coil meter.

Any size will do; the larger it is the better and more accurate the finished instrument. A small 2½ in. instrument with a flange fitting is very suitable.

Construction

It is proposed to make the meter in three stages, each one leaving the meter in working order for testing and practice in the art of trouble locating using the ranges so far completed. The first stage consists of making a multi-range D.C. voltmeter to read 0 to 10V; 0 to 100V; 0 to 250V; 0 to 500V; and 0 to 1,000V.

Purchasing the Parts

Do not buy any other type of meter but a moving-coil with one milliamp

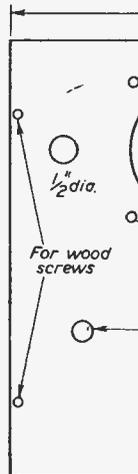


Fig. 1 (a), (b)

MANY beginners find difficulties when they have wired up some apparatus and it does not work. If they had at their command a simple multimeter, sensitive but not necessarily very accurate, they would in most cases be able to sort out the fault very quickly.

Accuracy

The meter proposed by the author will be quite accurate (within 5 per cent.) on all D.C. voltage ranges, rather more accurate on current ranges, especially the lower ones, but on A.C. the accuracy will not be so great, probably about 10 per cent. depending on the components used. Thus the meter is not intended for the laboratory technician, but for the amateur radio enthusiast.

There are many types of basic meter, some are on the market as voltmeters for a few shillings, but few are worth buying as they draw

PARTS TO BUY FIRST :


- 1 in. ply or hardboard, 7 in. by 8 in.
- 1/2 in. softwood, 8 in. by 8 1/2 in.
- One milliampere moving-coil movement, any size, the bigger the better, resistance unimportant unless a very accurate instrument is required.
- One toggle switch, one-pole, one-way.
- One range switch, two banks of one-pole, 11-way. Pointer knob to suit.
- Two terminals or wander plug sockets, preferably red and black. Insulated types are most suitable.
- Red and black plastic multi strand flex.
- Crocodile clips.
- 1/2 or 1 watt, gold line resistors (silver line or ordinary resistors will do for less accurate results) as follows : R5, 10kΩ ; R4, 100kΩ ; R3, 250kΩ ; R2, 500kΩ ; R1, 1MΩ.

PARTS REQUIRED TO COMPLETE THE METER :

- Wire for shunts, 26 s.w.g. Eureka or Constantan wire (about a yard only is required) ; 600 watt electric fire element wire would do.
- 38 to 42 s.w.g. Eureka or Constantan wire (about 4yd. will allow for errors and breakages) or use an old 25 or 50kΩ wire-wound pot. obtainable at any servicing depot.
- One toggle switch ; two-pole, two-way.
- One 4 1/2 v. torch battery.
- One 1mA meter rectifier (you may care to wait before you buy this as you can use germanium diodes which are obtainable for a few pence. Details will be given later.)
- One 3.3kΩ silver line resistor (R10.)
- One 1kΩ potentiometer, round knob to suit.

Test-Meter

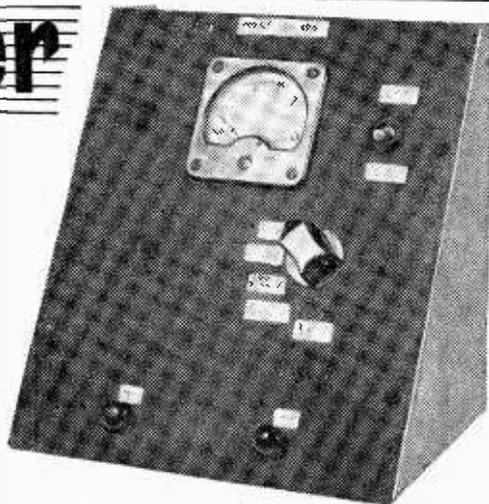ALL ARTICLES IS BY E. V. KING, THE AUTHOR OF "THE CONSTRUCTIONAL COURSE"



The multi-range D.C. voltmeter.

ruined in this fashion. Be patient and satisfied at first with a thorough examination externally. If you have an old meter (or one you have burnt out!) by all means open it up and examine the working parts. Do not do this with a new one unless you are a watch-maker or other fine instrument maker. Notice that the needle may be set accurately at zero by means of the little screw head about $\frac{1}{16}$ in. below the pivot point of the needle. This screw controls the hairspring. When the meter is mounted in its working position this screw is adjusted to give a perfect zero when viewed from directly over the needle. Oblique viewing will introduce an error. Out of interest try looking at the meter from a point 1 ft. to the left and then 1 ft. to the right. Different readings will appear, neither being correct. Good meters have a mirror above and behind the scale and you have to view so that the needle and the image of the needle are superimposed.

Gently turn the zero screw. If it has been waxed it will help to gently warm the outside of the case. The screw will turn right round indefinitely (it is not really a screw inside) and the needle will then move either side of zero. Set the meter to zero again after experiment with the screw.

Replacing the Case

If you ever have the front off a meter the zero screw can easily be broken on the inside when replacing the

full scale deflection or the resistors will all be of the wrong value. Make sure the needle is free when you gently shake the meter and ask the seller to show you that it works by putting it in series with his own meter on resistance range. If the needle shows the slightest tendency to stick, reject it. If the needle is bent at the tip the meter has been overloaded at some time and should be rejected.


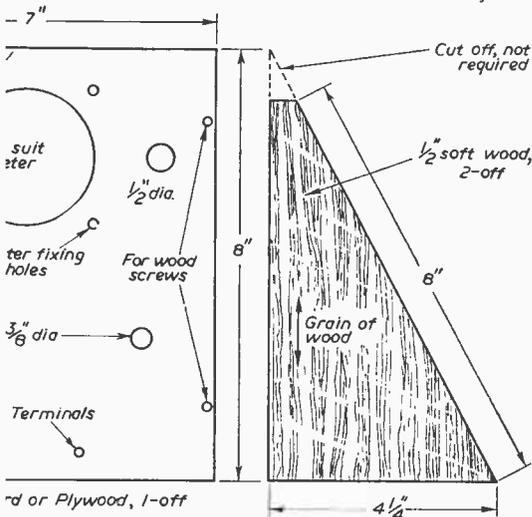


Fig. 1 (c) (Below, right).—The construction of the meter panel and stand.

The scale reading should be from 0 to 10, or multiples thereof. Some meters are calibrated for a specific purpose (e.g., 0 to 6) and these should be cheaper. It is not an easy job to make and fit another graph, but it could be done. or a conversion graph could be made up. A meter with this type of "odd" scale is not recommended for multi-meter purposes. Most meters have an internal resistance of 100 ohms, but for the accuracy required of this multi-meter it will not matter, almost any internal resistance will suit.

Examining the Meter

Do not be tempted to try out the meter on a torch battery. Many a meter must have been

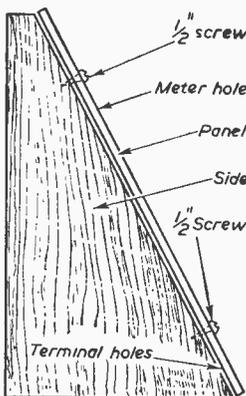

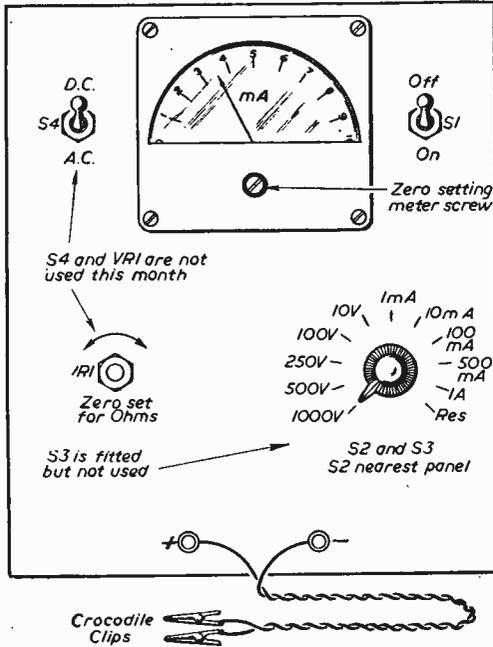


Fig. 2.—The meter panel (when completed).

front in position. Examine the mechanism very carefully and make sure the little "pip" on the inside is located in the long groove on the hair spring adjuster before turning the screw. If it is incorrectly replaced and then adjusted, the "screw" will fracture, and your instrument will not be suitable for very accurate work. It could be set at zero inside and then left, but it would be inaccurate after some use, or in different temperatures (when the hairspring expands or contracts).

If there is no information supplied to the contrary with the meter, it may be assumed that it will work in any position, horizontal or vertical. To be "on the safe side" this meter is mounted at an angle somewhere between the two. On some meters designed specifically for horizontal or vertical operation this might introduce a small error (not to be worried about in this instrument) so the reader may care to make the panel as shown, but mount it in some other way—for instance in a box.

Making the Panel and Stand

In the interests of safety it is best to cut the panel and all holes before anything else is done. The panel may be mounted on the stand, but it will probably help to leave it off until all the

wiring is finished. If the left-hand part of the stand is attached to the panel it will leave the side with the complicated wiring (to the 11-way switches) with easy access.

The panel and associated parts are shown in Fig. 1 (a), (b) and (c). The panel is cut to the size shown and the various holes cut out. The larger ones can be cut with a fretsaw. The material may be plywood, or hardboard. Iron or any magnetic metal must not be used as it may affect the meter, but brass or aluminium could be used. Chances of short circuits are reduced by using wooden panels.

The stand consists of two triangles of wood with the points sawn off as shown in Fig. 1 (b). When mounting the switches in the holes shown at the side of the meter allow room for the triangles to be screwed alongside. There is plenty of room if the triangles are of 1/4 in. wood. Make sure the grain is along the height of the triangles or they will break as you cut them or when you screw on the panel.

Make sure the meter stand does rest firm and level when made. If it does not, rub the base down with sandpaper until it is square and flush with the bench. If the meter is to be used for servicing receivers in the living-room, stick felt to the bottom of the stand.

Drilling

When drilling hardboard always drill from both sides or the result will be very rough indeed, and it helps future work on the front panel (i.e., blacking and marking figures in white) if the high gloss is gently removed with sandpaper too.

When finished the panel can be painted with black Indian ink. This may be rubbed a bit before the meter is finally finished, but it may be redone finally when the A.C. switch has been fitted.

Fit S1 as shown in Fig. 2, also the two terminals. These could be plugs and can be coloured or otherwise and in any event should be of such a type that they are insulated on top. Metal terminals are not suitable. Plugs have the

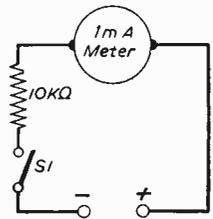
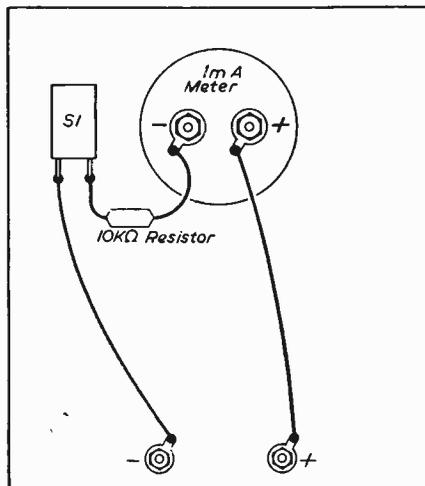


Fig. 3 (a) (Left).—Making a trial 10V meter.

Fig. 3 (b) (Above).—Circuit diagram for the 10V meter.

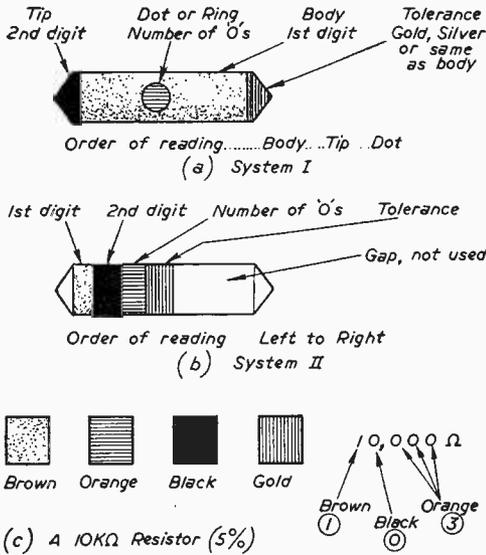


Fig. 4.—Reading the resistor colour code.

advantage that they are easily removed to use on some other gear, but suffer the disadvantage that they often give erratic connections, especially when old. Then mount the meter itself. You may need some small nuts and bolts (1/4 in. Whit. from the ironmonger would do) or the screwed rods may have been pressed into the plastic case in which event you must be very careful to do the nuts up tight, but no more.

The 10V Range

First, it is proposed to make the simple 0 to 10V meter shown in Fig. 3. The reader will note how simple the theoretical diagram is and will no doubt be able to follow it in the practical one.

Ignoring the resistance of the meter the 10kΩ resistance will restrict the current from a 10V. battery applied to the plus and minus terminals to one milliamp (1mA). Thus, the meter needle goes right over and points to 1mA, but we read it as 10 volts. When it points to 0.45mA, as it would on a flat type torch battery, we read 4.5V.

Having mounted the components and made sure the switch S1 is on when it is down by using a torch battery and bulb, proceed as follows. Wire soldering tag on negative terminal to one tag of S1. Other tag of S1 via a 10kΩ 5 per cent resistor (be very careful indeed that you really have this value or your meter may be damaged beyond repair).

Test Leads

Attach two crocodile clips carefully to the ends of some red and black plastic-covered multistranded wire. The other ends are attached to the terminals About 2ft. or 2ft. 6in. of wire is ideal. The author likes to make a small loop of wire round a nail a little bigger than the terminal to be used. This loop is then run over with solder to make a neat permanent loop for attachment to the terminal.

Colour Code Chart

Black.....	0	*
Brown.....	1	*
Red.....	2	*
Orange.....	3	*
Yellow.....	4	*
Green.....	5	*
Blue.....	6	
Violet.....	7	*
Grey.....	8	
White.....	9	
Silver.....	10%	
Gold.....	5%	

* The beginner should learn these by heart

Test this simple meter out on various torch batteries, none of which will be over 10V. Remember that each dry cell gives 1 1/2V. If the meter does not work, then either one of the components is faulty (test by substitution) or you have wired up incorrectly. This can usually be diagnosed as the needle tries to move backwards, but can only do so for 1/4 in. or so. You could make quite a good test on a car battery by attaching the negative clip to the small lug and working upwards cell by cell, remembering to scrape the lead connectors each time you need a contact. You should not test all the cells of a 12V battery, although it would probably do no harm, as these meters are fairly robust. Lead acid cells are not exactly 2V each. This is only a mean figure depending on the state of charge.

Reasons for Inaccuracy

If you buy a new flat torch battery which contains three cells in series, the needle should go fairly accurately over to 0.45mA. The reasons for errors are as follows in order of importance:

1. The resistor may not be exactly 10kΩ but could be 9,500 or 10,500 ohms.
2. We have, in stating 10kΩ, ignored the resistance of the meter; if this is 100Ω then strictly speaking we should use a 9.9kΩ resistor. Such a resistor is not made as standard. A special one of high accuracy would have to be purchased.
3. Small errors in the meter and the battery voltage.

The Colour Code

Refer to Fig. 4 and to the resistors which you have purchased in order to make the meter. If these are of the 5 per cent. type which is recommended, then they may have a gold band on them. This means that they are within 5 per cent. of the specified value. You could use 10 per cent. ones which have a silver band or 20 per cent. ones which have no metallic colour on them. The accuracy of the meter would suffer with the latter unless you are able to get a friend to select values "spot on" with a bridge. This is the best way of all. Values of resistor a little too low may be increased by carefully filing away with a nail file. Do not join resistors in series as you may have shorts, etc., develop in the meter which will often be moved about.

The chart with Fig. 4 gives complete details of what each colour stands for, those with the asterisk are very common ones and should be learnt by heart as soon as possible.

In the next article, the author explains in detail the two systems of colour codes used for resistors and goes on to deal with the working of the range switch and the construction of a multi-range D.C. voltmeter.

(To be continued)

RESISTOR WATTAGES

HOW TO CALCULATE THE RATINGS FOR VARIOUS RESISTORS

By F. G. Rayer

IN circuits of receivers, amplifiers and other equipment, the resistance values are specified, so that the constructor can wire in suitable components. Quite frequently the wattages are not shown, and this may cause some doubt as to best wattage to use. This problem can also arise when replacing a defective resistor.

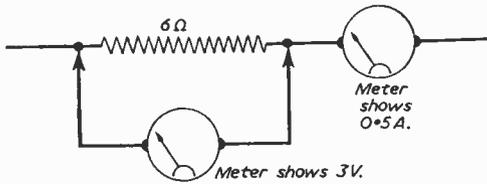


Fig. 1.—A current of 0.5 amps flows through a resistor of 6 when the P.D. across it is 3 v.

Calculation

Difficulties of this kind are easily overcome when the methods of calculating wattage are known. There are three methods, each of a simple nature, and that chosen for a particular calculation usually depends upon the factors known. These factors are voltage, current and resistance, and wattage may be determined by any of the following methods: (Voltage \times Current) or $\frac{(\text{Voltage})^2}{\text{Resistance}}$ or $(\text{Current})^2 \times \text{Resistance}$.

A simple example will show how these calculations are worked in practice. In Fig. 1, 3 v. are applied to a 6-ohm resistor so that .5 amp. flows. Using each of the methods in turn gives the following results:

$$(\text{Voltage}) \times (\text{Current}) : 3 \times 0.5 = 1.5 \text{ W.}$$

$$\frac{(\text{Voltage})^2}{\text{Resistance}} : \frac{3 \times 3}{6} = \frac{9}{6} = 1.5 \text{ W.}$$

$$(\text{Current})^2 \times \text{Resistance} : 0.5 \times 0.5 \times 6 = .25 \times 6 = 1.5 \text{ W.}$$

It will thus be seen that if any two of the factors (voltage, current, resistance) are known, the wattage can be found. It will also be clear that the factors must be expressed in volts,

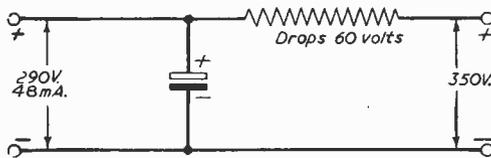


Fig. 4.—H.T. dropper resistor.

amps. and ohms, and this must always be remembered when dealing with resistor values indicated as kilohms, or currents of low value given in milliamps. Before working, these can be converted. 1 k = 1,000 ohms, and 1 amp. = 1,000 mA.

Circuit Resistors

It is usual to indicate voltage by V, current by I, and resistance by R. Fig. 2 shows a valve with anode and screen grid resistors. Any of the methods listed will indicate the wattage dissipated.

Assume that 100 v. are dropped in the resistor, which is 50 k.

$$\frac{V^2}{R} = \frac{100 \times 100}{50,000} = 0.2 \text{ W.}$$

Assume a meter shows 2 mA to flow, with 100 v. dropped. Then VI or $100 \times 0.002 = .2 \text{ W.}$

If measurement of the valve data show 2 mA to flow, with the 50 k resistor, then $I^2 \times R = .002^2 \times 50,000 = 0.2 \text{ W.}$

The smallest rating which may be employed would thus be 0.2 W., or 1/5th watt, but a 1/4-watt resistor would usually be fitted, because the next larger generally available wattage is suitable. If 1/4-watt or 1-watt resistors were to hand they would be equally suitable, unless space is so limited that they cannot be accommodated.

When larger currents are encountered, resistors of fractional wattage rating may be too small. In Fig. 3, anode and screen grid currents total 49.5 mA. An average cathode current of 50 mA may thus be assumed, to simplify calculation. Resistance and current being known, $I^2 \times R$ gives the wattage. That is, $.05 \times .05 \times 250 = .625 \text{ W.}$ A 1-watt resistor is too small, so a 1-watt resistor can be used here.

H.T. Dropper

In Fig. 4, a 350 v. H.T. supply is dropped to 290 v., and 48 mA flows. The resistor thus drops 60 v. at 48 mA. Therefore, $V \times I$, or $60 \times .048 = 2.88 \text{ W.}$ As the next larger manufactured value has to be selected, a 3-watt resistor would be used.

In some circuit positions, especially A.V.C. circuits and grid circuits, exceedingly small currents will flow, so that calculation shows the power dissipated to be small fractions of a watt. Small resistors, such as those of 1/4-watt rating or less can be employed uniformly here.

(Continued on page 429)

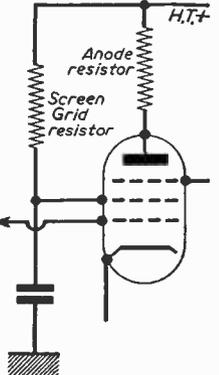


Fig. 2.—Anode and screen-grid resistors.

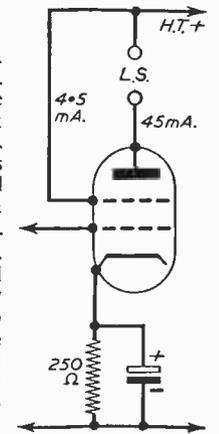


Fig. 3.—Cathode bias resistor.

R.S.C. (Leeds) MANCHESTER Ltd. and LEEDS

Mail Orders to 29-31 Moorfield Rd., Leeds 12.
Callers to 5 and 7 County (Mecca) Arcade, Briggate, Leeds 1,
and Universal Bazaars Ltd., 8-10 Brown St. (Market St.),
Manchester 2.

Terms C.W.O. or C.O.D. No C.O.D. under £1. Post 1/9 under £2, 2/9 under £5.

EX. GOVT. MAINS TRANSFORMERS

Primaries 200-250 v. 50 c.p.s. A.C.	
275-0-275 v. 190 m.a. 6.3 v. 7 a. 5 v. 3 a.	21/9
250-0-250 v. 150 m.a. 5 v. 3 a.	16/9
350-0-350 v. 160 m.a. 6.3 v. 5 a. 5 v. 3 a.	27/9
450-0-450 v. 250 m.a. 6.3 v. 3 a., 6.3 v. 1 a.	
5 v. 6 a.	49/9
12.5 v. 3 a., 5 v. 3 a.	12/9

SELENIUM RECTIFIERS

F. W. BRIDGE	L.T. Types H.W.
6-12 v. 1 a.....	3/11
6-12 v. 2 a.....	6/11
6-12 v. 3 a.....	9/9
6-12 v. 4 a.....	12/3
6-12 v. 6 a.....	15/3
6-12 v. 10 a.....	25/9
6-12 v. 15 a.....	35/9
24 v. 2 a.....	14/9
2-6 v. 1 a.....	2/11
6-12 v. 1 a.....	1/9
11 v. 40 m.a.....	3/9
250 v. 50 m.a.....	3/11
250 v. 60 m.a.....	4/11
250 v. 80 m.a.....	5/11
250 v. 250 m.a.	12/9

SPECIAL OFFER OF BRAND NEW EX. GOVT. SELENIUM RECTIFIERS TELEVISION TYPE HEAVY DUTY TYPE

250 v. 200 m.a.....6/9
24 v. 15 amp. F.W. Bridge, with large square aluminium coolers—27/9 ea

R.S.C. BATTERY CHARGING EQUIPMENT

All for A.C. Mains 200-250 v., 50 ccs. Guaranteed 12 months.

ASSEMBLED CHARGERS

6 v. 1 amp.....	19/9
6 v. or 12 v. 1 amp.....	27/9
6 v. 2 amps.....	29/9
6 v. or 12 v. 2 amps.....	38/9
6 v. or 12 v. 4 amps.....	56/9

Above ready for use. With mains and output leads. Carr. 3/6.



Assembled 6 v. or 12 v. 4 amps.
Fitted Ammeter and variable charge rate selector. Also selector plug for 6 v. or 12 v. charging. Louvred steel case with stoved blue hammer finished. Fused at 75/- use with Carr. 4/6 mains and output leads. Credit Terms: Deposit 14/11 and 5 monthly payments 14/11.

ASSEMBLED CHARGER
6 v. or 12 v. 2 amps.
Fitted Ammeter and selector plug for 6 v. or 12 v. Louvred metal case, finished attractive hammer blue. Ready for use. With mains and output leads. Double Fused. Only Carr. 3/9 **49/9**

BATTERY CHARGER KITS
Consisting of Mains Transformer, F.W. Bridge, Metal Rectifier, well ventilated steel case. Fuses, Fuse-holders, Grommets, panels and circuit. Carr. 3/6 extra.
6 v. or 12 v. 1 amp..... 29/9
As above, with Ammeter..... 32/9
6 v. 2 amps..... 25/9
6 v. or 12 v. 2 amps..... 31/6
6 v. or 12 v. 4 amps..... 41/6
6 v. or 12 v. 4 amps. incl. BATTERY CHARGER KIT
6/12 v. 6 amp. consisting of F.W. Bridge Rectifier, Mains Trans. and Ammeter, 40/9. Post and packing 4/6.

EX. GOVT. SMOOTHING CHOKES

60 m.a. 5-10 h. 250 ohms.....	2/9
80 m.a. 20 h. 900 ohms.....	5/11
100 m.a. 5 h. 100 ohms.....	3/11
120 m.a. 12 h. 100 ohms.....	8/9
150 m.a. 10 h. 100 ohms.....	10/9
200 m.a. 3-5 h. 100 ohms.....	8/9
250 m.a. 20 h. 200 ohms.....	19/9

EX-GOVT. CASES. Size 14-10-8 1/2 in. high. Well ventilated, black crackle finished, undrilled cover. IDEAL FOR BATTERY CHARGER OR INSTRUMENT CASE, OR COVER COULD BE USED FOR AMPLIFIER. Only 9/9, plus 2/9 postage. 2 v. 16 a.h. EX-GOVT. ACCUMULATORS. New, boxed. Only 5/6 each, 3 for 15/-, post 2/6. 6 for 27/6, carr. 3/6.

RE-ENTRANT SPEAKERS. Tannoy, 8 watt, 7.5 ohms. Only 19/6 each.
5 CORED FLEX. Rubber insulated. 14.36, 1 3/4 yd., 50/- 50 yds., 24 per 100 yds.
STANDARD JACK PLUGS. With 4ft. screened lead, 1/11 ea.
STANDARD MOULDED JACK SOCKETS. 2/9 ea.
TRANSISTORS. Audio Type, 7/6; R.F. 15/-.

PHILCO V.H.F. F.M. RADIO TUNERS with self-contained Power Pack. For 110-200/250 v. A.C. mains. Inc. 6 valves (Magic eye tuning indicator). Housed in beautiful polished walnut veneered cabinet. List price £20. Limited stocks, brand new. 12/6 gns., carr. 7/6, or on H.P. terms.

VOLUME CONTROLS with long (1 1/2 in. diam.) spindles all values less switch, 2/9, with switch, 3/9.
R3693 UNITS. Comprising chassis with strong cover 17 in. x 10 in. x 8 in. Over 70 resistors (many high stability) and condensers. Valveholders, I.F.T.'s co-ax. sockets, controls, fuseholders, tagboards, etc. etc. Except value at only 15/-, carr. paid.

CO-AXIAL CABLE. 75 ohm. 1/2 in., 8d. yd. Twin-Screened Feeder 11d. yd.

GRAM MOTORS with 10 in. Turntable. Centre Drive. Variable speed 6-78 r.p.m. Made by Collaro. Few only 59/6, or less Turntable 49/6. For 200-250 v. A.C. mains. EN-FO (Ford) CAR RADIOS. For 6 v. supply but we can supply dropper for connection to 12 v. If required. Limited number at fraction of list price. Only 15 kms. Brand new, cartoned and complete with aerial. Carr. 7/6.

COLLARO 3-SPEED TAPE TRANSCRIPTORS Mk. III. Few only brand new cartoned at only 15 kms. Carr. 7/6.
TURNOVER STEREO/MONORAL PICK-UP HEADS. by Acos. Suitable for normal 78, 45, or 33 1/3 r.p.m. records or for stereo type. Sapphire Stylus. Will fit Garrard, B.S.R. Collaro and Starr Galaxy Record Changers. Only 49/9.

Fully guaranteed and tested before despatch VALVES

1AB6 6/9	6C9 11/9	6X5 5.11	53KU 10/9	DL93 7/9	EL90 9/9	N727 9/9	U78 9/9
1AH5 6/9	6C9D6G 7/9	7CN7 7/9	54KU 11/9	DL94 8/9	EL91 4/9	OA81 4/9	U139 9/9
1AJ4 6/9	6D1 1/9	7C5 7/9	62DDT 9/9	DL96 8/9	EM90 9/9	OC72 25/-	U142 9/9
1CLEM 6/9	6D2 6/9	7C6 7/9	62VP 9/9	EA50 8/9	EM91 11/9	OM4 6/9	U151 8/9
1C3 6/9	6D6 5/9	7S7 7/9	63ME 6/9	EABCB0 9/9	EY31 13/9	P61 2/9	U152 9/9
1L4 5/11	6F1 11/9	7Y4 7/9	65ME 8/9	EAF42 8/9	EZ35 9/9	PCF80 12/3	U153 9/9
1FD1 6/9	6F12 6/9	8D2 3/3	141TH 8/9	EB34 2/3	EZ80 8/9	PCF82 9/9	U154 9/9
1FD9 6/9	6F13 11/9	8D3 6/9	17LDDP 8/9	EB41 7/8	EZ81 8/11	PCL82 12/6	U281 9/9
1F1 6/9	6F14 11/9	8D7 7/6	311SU 8/9	EB81 5/9	EZ90 6/9	PCL84 8/9	U282 9/9
1F2 6/9	6F15 11/9	9D2 3/9	411U 9/9	EBC33 6/9	GZ40/500 9/9	PEN46 6/9	U319 9/9
1F3 5/11	6H6 2/3	9U8 6/9	451PT 7/9	EBC41 9/9	GW30 9/9	PEN383 8/9	U381 9/9
1P1 6/9	6J5 4/9	954 1/9	AC6PEN 5/9	EBC90 11/9	GZ32 11/9	PL33 9/9	U403 9/9
1P10 6/9	6J5G 4/6	10C1 13/9	AC/HL 5/9	EBF80 9/9	GZ33 10/9	PL38 16/9	UAOC80 10/6
1P11 8/9	6J6 4/6	10F1 17/9	EB35 8/9	EBF85 9/6	GZ34 13/9	PL81 13/9	UAF42 10/6
1R5 7/9	6J7G 5/9	10LD3 15/9	B65 7/3	ECC35 2/9	GZ37 9/9	PL82 9/9	UAF43 11/9
1S5 7/9	6K7G 4/9	10LD12 7/9	B152 8/9	ECC81 7/9	HLA1D 9/9	PL83 10/9	UBC41 8/9
1T4 5/11	6K7MET 5/9	10LD14 15/9	B309 8/9	ECC82 7/3		PY31 11/9	UBF80 8/6
3A4 8/9	6K8G 8/9	10P18 9/9	B319 8/9	ECC83 9/9	IW4/350 9/9	PY80 7/9	UCC85 10/6
6C4 6/9	6K25 8/6	12A5 5/9	B329 8/9	ECC84 8/9	IW432 9/9	PY81 8/9	UCH43 10/9
3S4 6/9	6L3D 8/9	12A7 7/9	B338 9/9	ECC85 9/9	KT32 9/9	PY82 8/9	UCL82 14/9
3V4 8/9	6LD12 9/9	12AU6 7/9	B719 8/9	ECC91 4/9	KT33 9/9	PY83 9/9	UF42 8/9
4D1 5/9	6LD20 8/9	12AU7 9/9	CCH35 7/9	ECF80 12/9	KT36 9/9	PZ30 16/9	UF89 9/9
5U4G 6/9	6L12 8/9	12AX7 9/9	DI 2/3	ECF82 12/9	KT44 14/9	R2 9/9	UL41 9/9
5Y3G 7/9	6L18 11/9	12SN7GT 6/9	DAF91 7/9	ECH81 8/9	KT45 9/9	R3 9/9	UL46 14/9
5Z4G 8/9	6L6G 8/11		DAF96 9/9	ECH80 8/9	KT61 11/9	R12 11/9	UL84 9/9
6AB8 12/9	6L19 11/9	12SPA 3/3	DF91 7/9	ECL82 11/9	KTW83 4/9	SD61 1/9	UL93 9/9
6AC7 5/9	6M1 6/9	13VPA 3/9	DF92 9/9	EF39 5/9	KT241 7/9	SP6 6/9	U04 9/9
6AG6G 11/9	6N8 8/9	15A6 7/9	DF96 9/9	EF41 8/11	L63 4/9	SP42 11/9	U05 9/9
6A78 8/9	6P25 11/9	16A5 6/9	D63 2/3	EF50 4/9	LN152 9/9	SP61 2/9	UY41 7/9
6AK3 8/9	6P28 9/9	16A8 7/9	D77 5/11	EF54 5/11	MH4 5/9	SP64 8/9	UY85 10/6
6AL5 5/9	6Q7G 8/9	17Z3 9/9	D152 8/9	EF85 7/9	MU12 9/9	SU61 9/9	VP1322 3/9
6AM5 4/9	6S67 6/9	19X3 9/9	DD6 11/9	EF86 7/9	MU14 9/9	T81 16/9	VS110 3/9
6AM6 6/9	6SK7 8/9	19Y3 9/9	DD41 8/9	EF86 16/9	N17 7/3	U18-20 3/9	VU120A 3/9
6AQ5 7/9	6SL7GT 7/9	20D1 14/9	DH83 6/9	EF89 9/9	N19 9/9	U22 7/9	W17 5.11
6AQ8 7/9	6SN7GT 7/3	20F2 8/9	DH77 11/9	EF91 5/9	N37 18/9	U24 7/9	W47 5.9
6AT6 7/9	6U4GT 12/9	20L1 9/9	DH109 10/6	EF93 9/9	N42 9/9	U25 7/9	W150 9/9
6B8 3/11	6U6G 8/9	20P1 12/9	DH142 8/9	EF96 11/9	N43 9/9	U31 9/9	W179 9/9
6BE6 9/9	6U8 8/9	21A6 8/9	DH147 6/9	EL32 9/9	N144 4/9	U35 9/9	W197 9/9
6BG6G 16/9	6V4 8/9	25L6 9/9	DH150 8/9	EL33 11/9	N148 7/9	U43 9/9	WD142 9/9
6BQ5 9/9	6V6GT 7/9	30L1 8/9	DH719 8/9	EL34 16/9	N152 9/9	U46 9/9	WD709 9/9
6BX6 8/6	6V8G 6/9	30P16 9/9	DK91 7/9	EL38 19/9	N154 9/9	U50 8/9	X17 9/9
6BY5 9/9	6X2 8/9	35Z4 6/9	DK36 9/9	EL41 10/9	N329 9/9	U52 6/9	X78 10.6
6BX7 7/9	6X5 8/9	41MHL 6/9	DL32 7/3	EL84 9/9	N709 9/9	U54 10/9	X142 9/9

BUILD AN INSTRUMENT YOU WILL BE PROUD TO OWN!


Two more **MAGNIFICENT**
ELECTRONIC ORGANS in Kit
form for the Home Constructor.

Everything supplied. No specialised knowledge required to build using our easy-to-read layout diagrams. Send stamped-addressed envelope (8" x 6") for beautifully illustrated Brochure giving details of our range of four polyphonic electronic organs specially designed for the home constructor.

HIRE PURCHASE TERMS WITH LOW DEPOSITS AND UP TO 3 YEARS TO PAY are available, and details are included with brochure.

Available only from:—

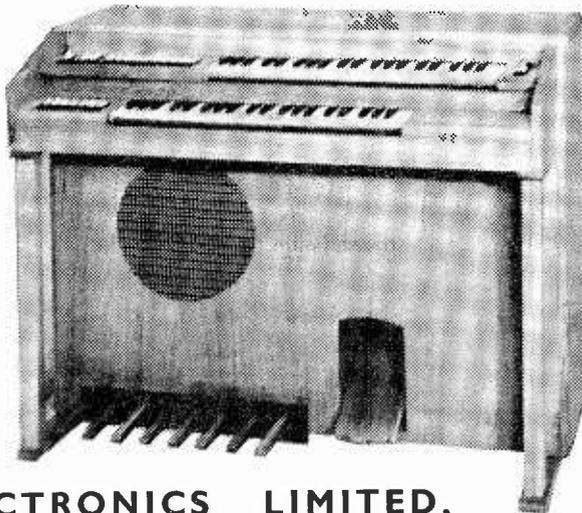BURGE ELECTRONICS LIMITED,
MAPLE CROSS INDUSTRIAL ESTATE, RICKMANSWORTH, HERTFORDSHIRE.



ADCOLA

PRODUCTS LIMITED
(Regd. Trade Mark)

SOLDERING EQUIPMENT


ILLUSTRATED

**3/8" Detachable
bit type (List
No. 64)**

**Protective Shield
(List No. 68)**

**Catalogues sent
FREE**

Telephones :
**MACaulay 4272
& 3101**

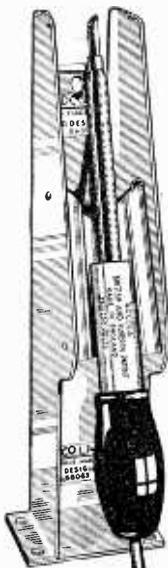

British and
Foreign Pats.

Reg. Designs,
etc.

Head Office, Sales :

**ADCOLA
PRODUCTS
LTD.**

**Gauden Road,
Clapham High
St., London,
S.W.4**

REPANCO

HIGH GAIN TRANSISTOR COMPONENTS

Ferrite Slab Aerial Type FS3. Medium Wave only. With fixing grommets. Size 3in. x 3/4in. x 5/32in., 7/6.

Long Wave Loading Coil for the FS3 Type XL1. 3/6.

Oscillator Coil Type X08 for 176 pF gang. Ferrite core. Size 3/4in. sq. x 11/16in., 5/-.

Oscillator Coil Type X015 for 365 pF gang. Ferrite core. Size 3/4in. sq. x 11/16in., 5/-.

I.F. Transformer Type XT6. Suitable for 1st and 2nd I.F. 455 Kc/s. Size 3/4in. sq. x 11/16in. 10/-.

I.F. Transformer Type XT7. Designed for 3rd I.F.T. or detector I.F.T. 455 Kc/s. Size as XT6, 10/-.

Push Pull Interstage Transformer Type TT9. Ratio 1 : 1 C.T. Radiometal Core. Size 3/4in. x 3/4in. x 13/32in., 12/6.

Push Pull Output Transformer Type TT10. Ratio 8 : 1 C.T. Matched to 3 ohm speaker. Size as TT9, 12/6.

Practical and Theoretical circuits enclosed with each Repanco Transistor Component.

REPANCO EASY-TO-BUILD RECEIVERS

Mini-7. 7 Transistor pocket receiver. Size 5 1/2in. x 3 1/2in. x 1 1/16in. Long and medium wave Envelope, 1/6.

Major-7. New Portable 7 transistor receiver. 9in. x 7in. x 4in. Long and medium wave. Envelope, 1/6.

Car Radio Receiver. 7 transistors. Long and medium wave. 2 watt output. R.F. stage. A.G.C. and auxiliary A.G.C. circuits. 12 volt or 6 volt. Envelope, 2/-.

Mail Order and Trade :
**RADIO EXPERIMENTAL
PRODUCTS, LTD.**
33 Much Park St.
COVENTRY
Tel. : 62572

Wholesale Enquiries and Export :
REPANCO, LTD.
O'Brien's Buildings,
203-269 Foleshill Rd.,
COVENTRY
Tel. : 40594

Becoming an "Amateur"

AMATEUR RADIO FOR BEGINNERS—No. 1

By J. D. Pearson, G3KOC

THIS series of articles is intended to put the raw beginner on the right road to a transmitting licence, and to assist with some of the problems he will meet on the way.

The Law

To-day it is illegal in the United Kingdom to operate any type of transmitting equipment without a licence to do so. The sole authority for the issue of licences in this country is the Postmaster-General. Anyone wishing to engage in the hobby of radio transmission for experimental, self-educational or entertainment reasons on the amateur bands must be in possession of a licence. This is known as the Amateur (Sound) Licence.

The Amateur (Sound) Licence

This licence costs £2 per annum and owing to the fact that it permits unrestricted operation on a wide band of frequencies with equipment which may be home-constructed the P.M.G. insists that all intending licensees shall be capable of correctly installing and operating such equipment. This entails a certain standard of theoretical knowledge on the part of the licensee. The standard required is the minimum necessary to ensure complete capability of the operator and, contrary to a certain school of thought, is not designed expressly to limit application for licences.

The reader's main concern at this stage no doubt is the exact standard required and how best to obtain it. The City and Guilds of London Institute holds a yearly examination known as the Radio Amateurs' Examination. A pass-slip for this is accepted by the Post Office as sufficient indication of the applicant's theoretical qualifications. Arrangements to take the R.A.E. must be made through the reader's local technical college or evening school. The C. and G. will not accept applications direct from persons wishing to take the examination, which is held each May, and applications must be in before the end of the previous February. For less than half-a-crown the City and Guilds will supply a syllabus which details precisely the standard of knowledge required for the R.A.E. They will also supply copies of past years' examination papers at 6d. per copy, together with a list of recommended books for study. The address is: City and Guilds of London Institute, 76. Portland Place, London, W.1. It is essential to quote "Subject No. 55, Radio Amateurs' Examination" when writing.

Exemption from the R.A.E.

It should be mentioned here that certain people who possess higher qualifications may be granted

exemption from the R.A.E. (e.g., university graduates who have taken certain radio subjects); certain Service trades are also exempt, provided application is made within a certain time of service completion, but, generally speaking, the reader, if he is a beginner, will certainly have to take the R.A.E. A full and complete list of these exemptions can be obtained from the following address: Headquarters, G.P.O., Radio and Accommodation Branch, St. Martin's-le-Grand, London, E.C.1. Together with this list the G.P.O. will supply a considerable amount of useful information regarding licencing conditions.

The Next Step

Having gone so far the reader will now have some idea of what amateur radio is, and the knowledge required to obtain a licence. The next question he asks is: "How and where can I obtain this knowledge?" followed closely by: "How long will it take to acquire?"

There are three methods of study: (a) technical college or evening institute; (b) correspondence course; (c) self-tuition at home. The first method is the most efficient as the student can usually ask questions concerning difficult points and receive immediate verbal replies, whereas with the other two methods he is apt to become discouraged when stuck on some theoretical problem. The reader is advised first to ascertain whether a course of instruction is available at his local evening school, stressing that he wishes to study for the R.A.E., and not some other branch of radio for which a course may be in progress. If a course is not available it should be borne in mind that most of these evening institutes are prepared to inaugurate particular courses if there is sufficient demand. Fees are quite moderate and courses usually run from September or October until April or May.

If, owing to distance, etc., attendance at an evening school is impossible then method (b) should be considered. Here financial considerations will usually be the deciding factor. Again, when making enquiries, ensure that you mention the R.A.E.

Studying at Home

Finally, we come to method (c). There will be many readers who, for various reasons, will favour this method which, incidentally, was the one used by the writer. There are a large number of people who, although wishing to adopt this method, feel it to be an almost impossible task to undertake. The writer regarded the situation in just this way some years ago, and whilst not wishing in any way to minimise the effort involved, it may be

The first of a new series written especially to aid the newcomer to the field of amateur radio transmission. This month's article explains the procedure to be followed to obtain a transmitting licence.

stated here that any person of average intelligence can undertake the necessary self-tuition with a reasonable chance of ultimate success, given one other essential quality—enthusiasm! Without it discouragement comes quickly.

The next consideration is the time-factor. Purely as a guide, the reader may find the following information useful. The writer studied theory for some six months before taking the R.A.E. At the beginning of the period of study absolutely nothing was known of the subject. Four or five nights a week were occupied with theory, the remainder being given over to short-wave listening and other interests. Prior to commencing serious

test has to be taken again! This is not to say that some form of regular morse instruction and practice should not be initiated almost immediately one has decided that the Amateur (Sound) Licence is the final objective.

The G.P.O. Test

The Post Office hold their own R.A.E. yearly, every October. This is held at certain large cities, and all details will be supplied from Post Office Headquarters on request, at the address given previously. Taking this examination usually necessitates travelling a long distance, but if you happen to live in one of the few large cities where it is held and feel qualified to take the R.A.E., a long wait until the following May can be avoided.

The Radio Amateur's Certificate

This is an attractive, well-printed parchment suitable for framing. It is issued automatically by the G.P.O. to all applicants for an Amateur (Sound) Licence who has passed the R.A.E. and the Morse Test. It is not issued to anyone who, whilst they may be eligible for a licence, claim exemption from the R.A.E. or the Morse Test.


The holder of this certificate is allowed to operate a station owned by another licensee, provided the said licensee is present and that an entry is made in his log-book accordingly. The reason for this is as follows: a person may, for various reasons, not wish to take out an Amateur (Sound) Licence immediately, although he has passed both the R.A.E. and the Morse Test. He can, however, operate a station owned, for instance, by a friend.

If a licence is not taken out within two years of the issue of a Radio Amateur's Certificate then the Morse Test must be taken again before a licence can be issued.

Further Steps

The reader will by now have a fairly clear idea of what he must do to obtain a transmitting licence. Further progress is now dependent on the individual, but the writer will be pleased to deal with queries arising from a study of theory as the basis for future articles. All queries should be forwarded to the Editor in the usual manner with the query coupon from the current issue.

(To be continued)

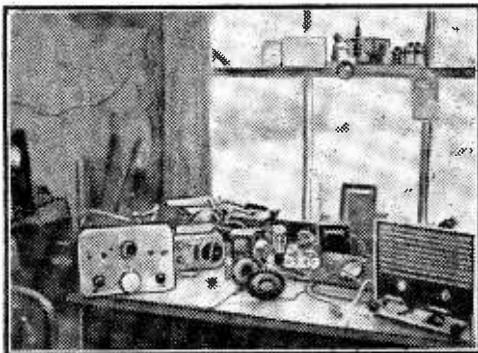

The den of Mr. R. Bulbert of Co. Tipp., Eire.

study, three years were spent as a short-wave listener.

Mathematics

Several correspondents have raised this subject and all were doubtful as to whether their standard was sufficient to get them through the R.A.E. There is no reason for anxiety on this point. If the reader can add, subtract, multiply and divide simple fractions and decimals, and extract a square root this is all he will require. A knowledge of logarithms and the ability to use indices is extremely useful, but not absolutely essential. It should be borne in mind that the R.A.E. is not designed to discover the candidate's mathematical ability, but to ensure that he is qualified to be let loose on the air with a hundred and fifty watts at his finger tips.

The Morse Test

Apart from the theoretical qualification, the Postmaster-General also requires that all applicants for an Amateur (Sound) Licence shall be capable of sending and receiving morse at 12 words per minute. The test is held at various centres throughout the country, and the Post Office is very obliging regarding the arrangement of dates and times to suit individual applicants for this test.


The reader should forget all about the actual morse test until he has passed the R.A.E. If the R.A.E. is not taken and passed within twelve months of passing the morse test then the morse

JOIN THE PRACTICAL GROUP

PRACTICAL TELEVISION	1/3
PRACTICAL HOUSEHOLDER	1/3
PRACTICAL MECHANICS	1/3
PRACTICAL MOTORIST & MOTOR CYCLIST	1/3

They are all published monthly

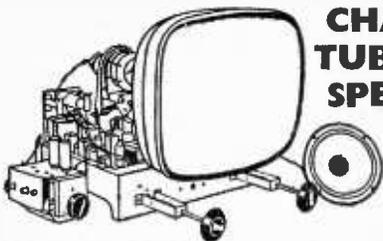★ **17in T.V. CHASSIS, TUBE and SPEAKER**
16 GNS.



17in. Rectangular Tube on modified chassis. Supplied as single channel chassis covering B.B.C. channels 1-5, or, incorporating Turret Tuner at 50/- extra (chassis purchasers only) giving choice of any 2 channels (B.B.C. and I.T.A.). Extra channels can be supplied at 7/6 each. Chassis size 12 x 14½ x 1 in. With tube and speaker (less valves), 16 guineas. Complete and working with valves and Turret Tuner 24 guineas. 12 months' guarantee on the Tubes. 3 months' guarantee on the valves and chassis. Ins., carr. (incl. Tube) 25/-.

14in. T.V. CHASSIS, TUBE & SPEAKER 11 GNS.
As above with 14in. Rectangular Tube. 12 months' guarantee on Tube. 3 months' guarantee on chassis and valves. Chassis with Tube and speaker (less valves), 11 guineas. Complete and working with valves and Turret Tuner, 19 guineas. Ins., carr. (incl. Tube) 25/-.

★ **T.V. CHASSIS AT CLEARANCE PRICES ★**
The Popular 12in. Plessey Chassis 19/6
A bargain for anyone wanting to make up their own T.V. at a very low cost. A chassis in one unit less valves and tube. 1.Fs 10.5-14 Mc/s. Can be adapted for a 12 channel Turret Tuner and modified to take a larger tube. Carr. & Ins. 10/6.



REPLACEMENT REBUILT T.V. TUBES

£8.10.0 carr. & ins. 15/6.
12 Months' Full Guarantee

All sizes and types except 10in. Rebuilt to the high standard required to give long picture life, quality and value. We are also able to offer attractive terms on the above as follows: 8/6 initial payment and 19 wkly. repayments of 8/6.


SOUND/VISION & I.F. STRIP 5/9
Salvaged. Complete sound and vision strip. 8 valveholders. Less valves. I.Fs 16-19.5 Mc/s. Size 8½ x 4½ x 4½ in. Drawings free with order. P. & P. 2/6.

TIME BASE 4/9
Containing scanning coils, focus unit, line transformer, etc. Less valves. Drawings free with order. P. & P. 2/6.

POWER PACK & AMPLIFIER 19/6
Output stage 6V6 with O.P. Trans. (3 Ω) choke. Smoothed H.T. 350 v. at 250 mA., 6.3 v. at 5 A., 22 v. at 3 A., 6.3 v. at 4 A., & 4 v. centre tapped. Valve line-up as follows: UU6, 6P25 & P61 (not included), carr. & ins. 5/6.

SUPER CHASSIS, 79/6

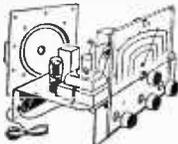5 valve superhet chassis including 8in. P.M. speaker and valves. Four control knobs (tone, volume, tuning, w/change switch). Four w/bands with position for gram. p.u. and extension speaker. Ins., carr. 5/6.




FAMILY RADIO £6.10.0
5 valve (octal) superhet. A.C. 3 waveband and gram. position, 4 controls. Modern attractive cabinet size 15½ x 18 x 10½ in. in cream and brown. Carr. & ins. 8/6.

CONTEMPORARY EXTENSION SPEAKER 19/6
18 x 7 x 15in. Dark veneered walnut cabinet. Attractive speaker fret. High quality 8in. P.M. speaker. On and off switch and volume control. P. & P. 3/6.

SOLO SOLDERING TOOL, 12/6

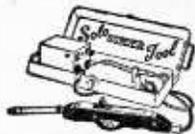110v. 6v. or 12v. (special adaptor for 200/240v., 10/- extra). Automatic solder feed including a 20ft. reel of Ersin 60/40 solder and spare parts. It is a tool for electronic soldering or car wiring. Revolutionary in design. Instantly ready for use and cannot burn. In light metal case with full instructions for use. Post 2/9.



BAKELITE CABINETS 5/9
Brand new. Colour brown. Attractive design. Size 12 x 7 x 5½ in. Ideal for small receivers, converters, etc. P. & P. 3/9.

★ **HERE IS UNREPEATABLE VALUE!**

RECORD PLAYER CABINET R.P.6.



29/6 Elegant cabinet, cloth covered in grey or red with sunken control panel and speaker fret. Size 13 x 17 x 8in. deep. Takes B.S.R. Monarch 4-speed Autochanger: 7 x 4in. Elliptical speaker and most of the modern portable amplifiers. Carr. & Ins. 4/6.

★ **WORLD'S FINEST AUTOCHANGER**



UA8 B.S.R. MONARCH 4-SPD. AUTOCHANGER £6.19.6

Collaro Conquest 4-spd. Autochanger, £6.19.6.
U.A.12. Latest B.S.R. Monarch 4-spd. Mixer, £8.9.6.
T.U.9. B.S.R. 4-speed Single Player, 89/6.
B.S.R. Monarch 4-spd. Stereo Autochanger, £9.19.6.
Collaro Conquest Stereo Autochanger, 11 guineas.
P. & P. on autochangers 5/6.

PORTABLE AMPLIFIER MK. D.1 59/6
12 Months' Guarantee


Brand new. Latest design with printed circuit. Dimensions 7 x 2½ x 5in. A.C. only. Mains isolated. 2-3 watts output. Incorporating EL84 as high gain output valve. Volume and tone controls. Knobs 2/6 extra. P. & P. 3/6.

PORTABLE AMPLIFIER MK. D.4 49/6

Brand new. By famous manufacturer. Especially built for portable record players. Dimensions 4½ x 3½ x 4in. A.C. only. 2 valves: EL84 as high gain output valve. E280 as rectifier. Volume and tone controls. Knobs, 2/6 extra. P. & P. 3/6.

EXTENSION SPEAKERS, 19/9

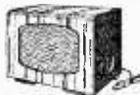Polished oak cabinet of attractive appearance. Fitted with 8in. P.M. speaker W.B. or Goodmans of the highest quality. Standard matching to any receiver (2-5 ohms). Switch and flex included. Ins., carr. 3/6.



★ **IDEAL FOR STEREOPHONIC SOUND!**
8in. P.M. Speakers, 8/9. With O.P. transformer fitted, 10/-.
6in. P.M. Speakers, 12/6. 4 x 7in. and 8 x 5in. Elliptical speakers, 19/6. Post 2/9.

DUKE & CO.

(Dept. D.7)

621/3, ROMFORD ROAD, MANOR PARK, E.12.
DEFERRED TERMS TO SUIT ALL POCKETS.

Monthly credit terms or weekly easy payments—
Details on request.

Send for FREE Catalogue. **ILF 6001/3**

CONSTRUCTORS CORNER


ENSURE SUCCESS WITH R.C.S.

Explore the world on short-wave radio (10-100 m)
FOR ONLY **35/-**

BUILD THIS AMAZING RADIO

POWERFUL! PERSONAL! PORTABLE!

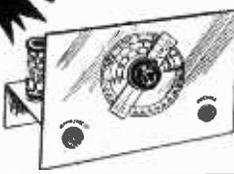Construction price includes valve and one coil covering 40-100 m.
● Can be converted to 2v. or 3v
● Receives speech and music clearly from all over the world.
Send 2/- for diagram and price list.



TRANSISTOR POCKET RADIO


- Two-stage circuit using variloopstick coil.
- Ideal for the beginner.
 - Can be built in 30 minutes.
 - Works for months off 7d. battery.
 - Fits into palm of your hand.

CRYSTAL RECEIVER

Covers M/W Band
All components including case for **10/6**
Ideal for the Beginner.

- ★ Sturdy metal case.
- ★ No holes to drill.
- ★ Detachable rod aerial.
- ★ All batteries self contained.
- ★ Can be built in 1 hour.
- ★ Covers medium waves.
- ★ Loud clear tone.
- ★ Selective tuning.
- ★ All parts are sold separately.

FOR ONLY **35/-**

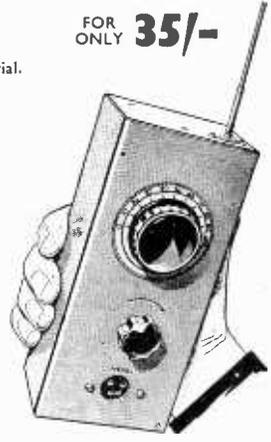

This delightful set is designed to give you a completely personal portable radio. Bronze-finished case. Ideal for the beach, the bedroom, the office—in fact, anywhere.
Send 2/- for wiring diagram and component price list.


The ideal low-cost transistor pocket radio for the beginner.
Send 2/- for data and list of components.

ONLY **30/-**

Trade Enquiries Welcomed **R.C.S. PRODUCTS (RADIO) LTD. 11, OLIVER RD., LONDON, E.17.** Mail Order Only

Build your own HI-FI!

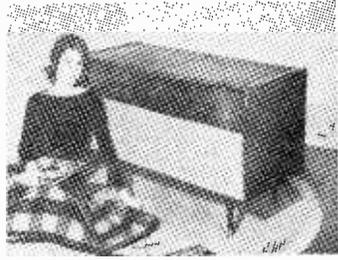At last! A specially selected and designed HI-FI Sound Installation for your home at really reasonable cost!



You save because you assemble everything yourself following our step by step instructions. You gain because you learn about the equipment as you build and are able to service and maintain it afterwards. Best of all—you'll have fun building it and be thrilled with the finished instrument which will bring you an entirely new experience in the enjoyment of sound. No previous skill or experience is needed. Post coupon now for full details, without any obligation. Easy terms available.

Equipment includes: Luxury Cabinets - Top Quality Amplifier suitable for stereo or non-stereo reproduction - VHF/FM Radio Units - Record Player - Tape Recorder - Hi-Fi Speaker system.

Best Buy at Britain's

FERRANTI TESTMETER TYPE Q. An extremely compact self-contained multimeter. Volts 0 to 30, 150, 600 AC/DC, with additional 0-3 v. DC, and 0-15 v. AC ranges; milliamps 0 to 7.5, 30, 150 and 750 DC; ohms 0-25 K ohms. Accuracy BSS first grade, 500 ohms per volt. Knife-edge pointer and clearly calibrated 2 1/2 in. scale. Complete with leads, probe, battery and instructions. In fitted velvet-lined 4 x 7 x 3 in. case. Brand new condition, perfect working order, 72/6, post 2/6.
R.F. UNITS. R.F.24. 12/6; R.F.26. 17/6; R.F.27. 22/6; Condition as new. Post each, 3/6.
CR100 COMMUNICATIONS RECEIVERS. Covers 60 kc/s—30 Mc/s in 6 bands, 11 valves, 2 R.F. and 3 I.F. stages. Crystal gate, BFO, etc. Ready for 200-250 v. A.C. mains. 21 watts output for 3 ohms speaker. SUPERB CONDITION AND OUTSTANDING PERFORMANCE for ONLY £21. S.A.E. for illustrated details.
CR100 SPARES KITS. 15 valves, 2 of U50, Dh53, KT63, X66 and 7 KTW61. Output transformer, resistors, condensers, electrolytics, lamps. ALL BRAND NEW. 50/6, post 4/6.
HIRO COMMUNICATIONS RECEIVERS. complete with 9 coils. From 18 gns. S.A.E. for full particulars.
R1155B. with latest drive, first-class condition, £7.19.6. R1155L. £12.19.6. S.A.E. for full particulars.
MINING COIL PHONES.—Finest quality Canadian, with Chamois ear-muffs and leather covered headband. With lead and jack plus. Noise excluding, supremely comfortable. 19/6, post 2/6.
INVICTA LOUDSPEAKERS.—Good quality 10 in. unit (impedance 3 ohms) in wooden cabinet 17 x 17 x 6 in. Complete with 50 ft. lead and jack plug. BRAND NEW. 39/6, carr. 5/6.
WENTON F772 ANALYSERS.—Multimeter. Current, 0 to 100 microamps 1, 10, 50, 100, 500 mA. D.C. 0 to 1, 1.5 Amps. A.C. volts, 0 to 2.5, 10, 50, 250, 1,000, D.C. and A.C. Resistance 0 to 100, 1,000, 100 K., 10 Megohms. Complete in "Rexine" covered carrying case, with leads and battery. Guaranteed, £5.19.6, carr. 4/6.
AMERICAN MULTIMETERS. by Precision, U.S.A. 400 microamps basic. A.C. and D.C. volts to 6,000 D.C., milliamps to 600, Ohms to 5 Megs., 20 ranges in all. In polished wooden case, 7 1/2 x 5 1/2. Complete with leads, batteries and instructions. Tested and guaranteed, £5.19.6, post 3/6.
TRANSFORMER BARGAIN.—Input 0-200/250 tapped. Outputs 250-0-250 v., 30 mAmps.; 5 v. 2 Amps.; 6.3 v. 4.5 Amps. Upright mtg. BRAND NEW. Boxed. Ex-Admiralty, made 1952. A fine 50 cfs. mains tranny for ONLY 16/6. Post FREE.
PLEASE ADD POSTAGE OR CARRIAGE ON ALL ITEMS

FREE BROCHURE - POST TODAY

Radiostructor, (Dept. H34), 46 Market Place, Reading, Berks.
Please send Brochure without obligation to:

Name **BLOCK CAPS PLEASE**

Address..... **PLEASE**

309 We do not employ representatives 759

CHARLES BRITAIN (RADIO) LTD.
11 Upper Saint Martin's Lane, London, W.C.2
TEmple Bar 0545
Shop Hours 9-6 p.m. (9-1 p.m. Thursday). Open All Day Saturday

RADIOSTRUCTOR

BRITAIN'S LEADING RADIO TRAINING ORGANISATION

AN EXPERIMENTAL "PRINTED" CIRCUIT AMPLIFIER

THE WIRING IS MADE FROM METALLIC CONDUCTING FOIL GLUED TO A HARDBOARD CHASSIS
By S. Woods

WHILE this amplifier is not a true printed circuit design it will nevertheless enable the amateur to obtain some experience in the practical applications of this method of wiring.

First, cut a piece of hardboard $\frac{1}{8}$ in. thick and 7 in. X 5 in. Lay out the components and mark round them as in Fig. 2. The valvholders should be pressed down so that the tags are spread out slightly. These should lay flat on the chassis. Make a

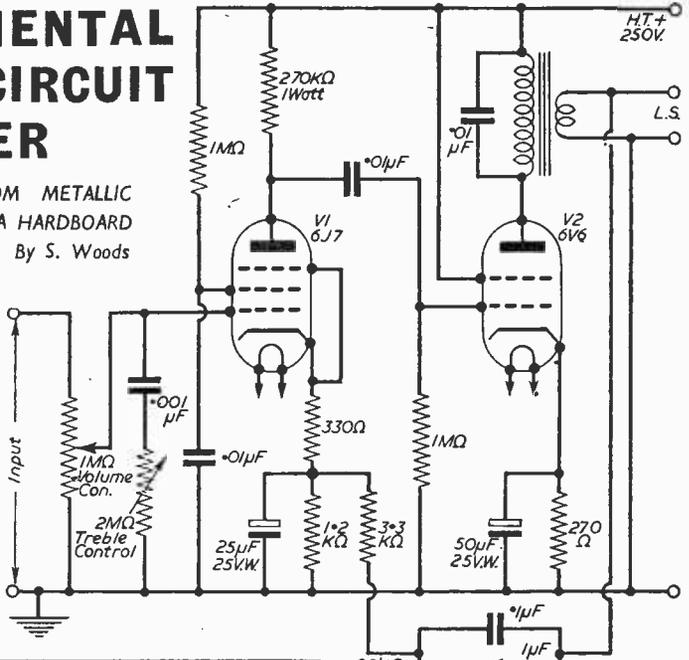


Fig. 1 (Above). — The circuit diagram.

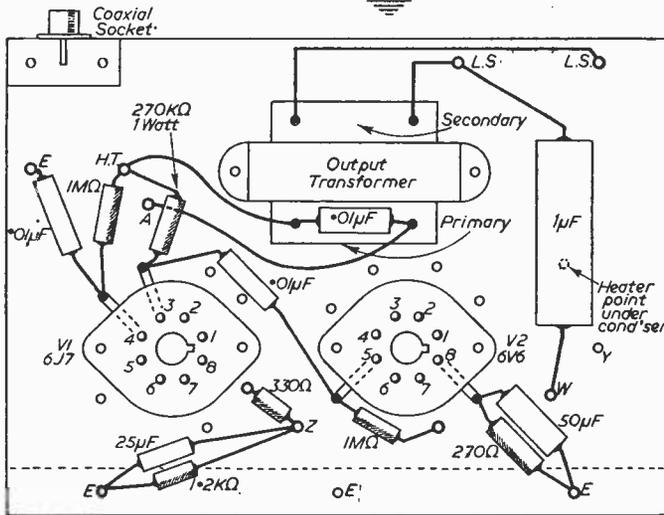


Fig. 2 (Above). — Layout of the parts.


Fig. 3 (Below, right). — Mounting the controls on the panel.

pencil dot on the chassis through the holes in the tags.

The Conducting Foil

Drill holes 6 B.A. to correspond with the valvholder tags that are to contact the "printing," i.e., tags 1, 2, 5, 7 and 8 on valve one; and 1, 2, 3, 4 and 7 on valve two.

Next cut a piece of foil the

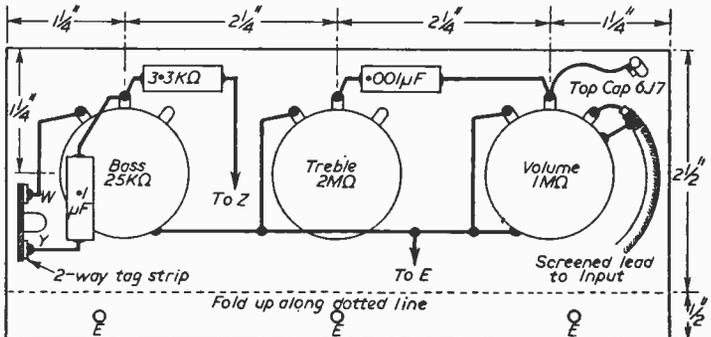

same size. (Foil obtainable from empty tea chests.) Stick this on the underside of the hardboard, i.e., the rough side, with suitable adhesive. Before this is quite set, cut away the shaded part as shown. The holes that have been drilled will show up in outline through the foil.

Next put the 6 B.A. screws through the holes with a washer under the head and nut. These screws should be just long enough to go through the hardboard. If longer, cut off the surplus and file flat to the nut. Tin the screw heads and nuts

RETURN-OF-POST SERVICE

ILLUSTRATED LISTS. We now have available separate illustrated lists on all of the following:—

GRAMOPHONE EQUIPMENT.—This list details no less than 14 different items including Record Changers, Single Record Players and Transcription Units. Some at special prices.

READY BUILT AMPLIFIERS.—Hi-Fi and less expensive popular types.

TEST GEAR.—Test Meters, Signal Generators, etc., by AVO, Pullin and Taylor.

LOUDSPEAKERS.—Full details of Goodmans, Whiteley, Wharfedale, GEC and Elac types which we stock.

TAPE DECKS.—All the popular makes including a special offer.

RECORDING TAPES.—We have a very wide range of tape and accessories by all the well-known makers. Any of these lists will be sent free upon request.

JASON FM TUNER KITS

There are no less than five different Jason FM Tuner Kits now available to the Home Constructor. Brief details are given here and individual lists on any are available free.

MOST IMPORTANT. We take great pains to see that the kits we supply are absolutely complete in every detail and also that all components supplied are entirely suitable in every way. This accounts for differences in price you may notice between our prices and those of some of our competitors. THIS SHOULD BE BORNE IN MIND WHEN COMPARING PRICES.

STANDARD TUNERS

STANDARD TUNER. The very popular tuner which is supplied with a chassis assembly fitted with a gold hammer finish front panel and glass dial. Employs four EF91 valves. External power supply is required. Complete kit **£6.19.6**. Power pack kit, 39/-.

STANDARD TUNER IN SHELF MOUNTING CASE. This is a new version of the above tuner. The circuit has been brought up to date and is built into the very attractive shelf mounting case of the new Fringe Tuner mentioned below. The circuit uses four EF90 valves and the power supply can be built into the case if desired. Complete kit **£7.19.6** without power supply components. **£9.19.0** with power supply.

MERCURY SWITCHED TUNER. This is a tuner in chassis form which has a three position switch for the three BBC programmes. Uses one ECF90 and four EF90 valves. External power supply is required. Complete kit **£9.19.0**. Power Pack Kit, 39/-.

FRINGE TUNERS

NEW FRINGE TUNER IN SHELF MOUNTING CASE. This is an entirely new Fringe Tuner and is supplied complete with a very attractive green shelf mounting case with Perspex dial. The tuner is fitted with variable AFC. Internal power supply if desired. Valves used are one ECC81 and five EF90. Complete kit **£10.5.0** without power supply components. **£12.3.6** with power supply.

TV SOUND/FM SWITCHED TUNER

This tuner, also supplied in an attractive shelf mounting case, has a TV type Coll Turret fitted to provide TV sound from any BBC or ITV Sound channel as well as the three BBC/FM programmes. Fitted with internal power supply. Valves: one ECC84, one ECF90, one EF90, one EF90, one EM91 and one EZ90. Complete kit **£15.15.0**.

INSTRUCTION MANUALS

All our kits include the appropriate instruction manual. All available separately as follows:— Manual covers both Standard Tuners and the new Fringe Area model, 2/10; Mercury 2/3; TV Sound/FM, 3/-, All post free.

LATEST TEST METERS

	Cash Price	Deposit	Hire Mthly.	Purchase Fmts.
AVO Model 8	£23.10.0	£4.14.0	12 of	£1.14.6
AVO Model 8 with leather case	£26.10.0	£5. 6.0	12 of	£1.18.10
AVO Model 7	£19.10.0	£3.18.0	12 of	£1. 8.8
AVO Model 7 with leather case	£22.10.0	£4.10.0	12 of	£1.13.0
AVO Multiminor	£9. 10.0	£1.18.0	12 of	12 of 1/4
AVO Multiminor with case	£11. 2.6	£2. 4.6	12 of	12 of 16/6
TAYLOR Model 71A	£12.10.0	£2.10.0	12 of	12 of 18/4
PULLIN Series 100	£12. 7.6	£2. 9.6	12 of	12 of 18/2
TAYLOR MONTROSE	£3.10.0	£1. 0.0	3 of	£1. 0.0
PIFCO All-in-One	£1. 12.6			

HIRE PURCHASE

H.P. Terms are available on any item. Repayments may be spread over 3, 6 or 12 months. Details as follows: Three months: Deposit 6/- in the £. Service charge 5% but minimum charge 10/-. Six and Twelve months: Deposit 4/- in the £. Service charge 10%, but minimum charge 20/-.

Terms of Business.—Cash with order or C.O.D. Postage extra under £3. We charge C.O.D. orders as follows. Up to £3. postage and C.O.D. fee minimum 2/8. Over £3 and under £5. C.O.D. fee only 1/6. Over £5 no charge.

AMPLIFIER KITS

MULLARD 510 AND GEC 912 PLUS
We carry full stocks for all versions of these popular Amplifiers and our price lists are available free.

MULLARD 2 VALVE PIPE-AMPLIFIER
Latest Mullard circuit for use with the 510 Amplifier. Booklet giving full details now available 1/3 post free. Complete Kit, including drilled chassis and control panel, **£6.12.0**. H.P. Terms. Deposit **£1.6.0** and six monthly payments of **£1.1.0**.

JASON STEREO

We stock the "Jupiter" and J.S.A.2 Kits. Fully detailed lists available.

GRAMOPHONE EQUIPMENT

	Cash Price	Deposit	Hire Mthly.	Purchase Fmts.
RECORD CHANGERS				
COLLARO. Conquest	£7.19.8	£1.12.0	6 of	£1. 4.7
GARRARD. RC121/4	£10. 2.6	£2. 0.8	12 of	15/2
GARRARD. RC88/4	£14. 3.0	£2.16.0	12 of	£1.0.10
BSR UA8 Monarch	£6.19.8	£1. 7.6	6 of	£1. 2.0
BSR UA12 Monarch	£9.19.6	£1.19.6	12 of	15/-
SINGLE RECORD PLAYERS				
GARRARD TA Mk. 2	£9. 6.6	£1.17.0	12 of	14/1
GARRARD 45P	£7.10.0	£1.10.0	6 of	£1. 3.4
BSR TU9	£4.10.0	£1. 5.0	3 of	£1. 5.0

TRANSCRIPTION UNITS

COLLARO. 4T/200 with PU	£18.12.0	£3.14.0	12 of	£1. 7.4
COLLARO. 4TR 200 Motor	£13.17.6	£2.15.6	12 of	£1. 0.4
GARRARD. 4HF	£18. 9.8	£3.19.8	12 of	£1. 6.7
GARRARD. 301 Motor	£25. 4.5	£5. 1.5	12 of	£1.16.11

All the above are fitted with Monaural cartridges. Some can be supplied with Stereo inserts and details are given in our illustrated list of Gramophone Equipment.

DOUBLE PLAY TAPE

Double Play Tape uses a new plastic base which is half the thickness of standard tape. Any reel will thus hold twice the length of Double Play Tape compared to Standard Tape. Owners of Recorders which take 5in. or smaller reels will find this tape of particular interest as the playing time can be considerably increased.

IASF. 300ft. (3in.), 14/-, 600ft. (4in.), 25/-, 1,200ft. (5in.), 42/-, 1,600ft. (5in.), 52/6, 2,400ft. (7in.), 77/6.

TELEFUNKEN. 1,200ft. (5in.), 35/-, 2,400ft. (7in.), 72/6.

All post free. New list of Standard and L.P. Tapes and Accessories free upon request.

MULLARD TAPE "C" PRE-AMPLIFIER

A booklet giving full technical details and constructional information is now available. Price 2/10, post free. COMPLETE KIT containing every item needed right down to the last nut and bolt. First-class items only are included. Ready drilled chassis and gold finished front panel. Price **£14.10.0**. H.P. Terms. Deposit **£2.16.0** and six monthly payments of **£2.3.0**. POWER PACK KIT, **£4.0.0**. All components are available separately and our detailed list is available free. CONVERSION KIT to convert original version to the new model, instruction manual included, **52/6**, post free.

TRANSISTORS

AUDIO. BTH Red Spot. Latest type. 7.6: GEC Yellow/Green, 10/-; Brimar TS9, 13/6; Ediswan XB102, 10/-, XB104, 10/-; Goldtop V10/15A, 15/-; Mullard OC70, 21/-, OC71, 24/-.

AUDIO OUTPUT. Mullard OC72 Matched pair, 60/-; Ediswan XC101 Matched pair, 60/-; R.F. GEC Yellow/Red, 17/6; Ediswan XA101, 35/-; XA102, 40/-; XA103, 15/-; XA104, 18/-; Goldtop V6/R2, 24/-; Mullard OC35, 35/-.

All transistors post free.


WATTS RADIO (MAIL ORDER) LTD.

54 CHURCH STREET, WEYBRIDGE, SURREY. Telephone: Weybridge 4556

PLEASE NOTE: POSTAL BUSINESS ONLY FROM THIS ADDRESS.


CLOSED FOR ANNUAL HOLIDAYS AUGUST 8TH TO 22ND.

Fully Guaranteed Components

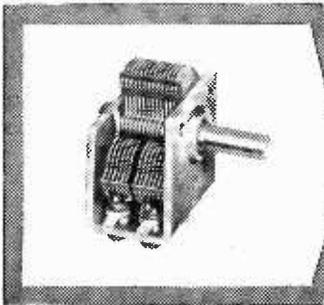


"00" TWIN CONDENSER

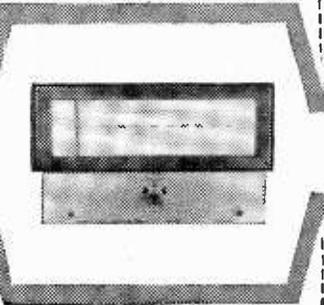Designed for use in miniature transistor receivers. The front (aerial) section is 208 pf. to provide coverage for medium waves, and the rear section is 176 pf., which may be padded to match the oscillator—very robust yet light weight. Front area 1 1/4 in. x 1 17/32 in. x 1 1/32 in. deep, price 9s. 6d.



S.L. 16 DRIVE

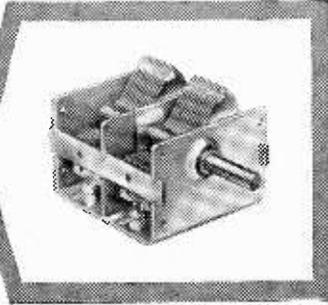A general purpose slide rule Drive for F.M./V.H.F. Units, short-wave converters, etc. Printed in two colours on aluminium, with a 0-100 scale and provision is made for individual calibrations. Complete with bronze escutcheon and glass. Price 13s. 9d.



F. GANG CONDENSER

A good general purpose gang Robust but small in size. "E" law to match our S.L.8 Full Vision, Square Plane and Air Plane Drives. Size 2 1/4 in. x 1 21/32 in. x 2 9/16 in. long (3 gang 3 11/16 in.). Price for 2 Gang, 13s. 3d. 3 Gang, 17s. 6d. Complete with trimmers.


JACKSON BROS.
(London) Ltd.

PRECISION BUILT COMPONENTS
KINGSWAY · WADDON · SURREY

Telephone: Croydon 2754/5



Five stars to guide you ...

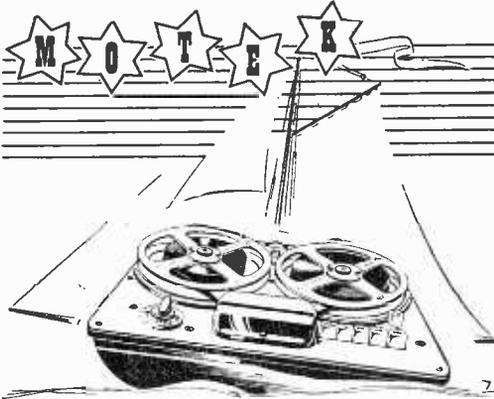

The deck of the "Five Star" is always ship-shape and Motek fashion—for it has been designed for the absolute minimum of maintenance. From port to starboard the super-structure has five perfect points which make Motek the finest of the line.

Push Button Operation makes for ease of control, the Counter gives you dead reckoning, the Safety Erase Button prevents errors in erasing, the Pause Control functions easily and Three Speeds adapt the machine to the fidelity required. Keep your tapes on Motek Five Star.

Details on request.
Patents Pending.

List **21** GNS.

MODERN TECHNIQUES

Wedmore Street, London, N.19. Tel.: ARCHway 3114
DHB 6613

FREE TO AMBITIOUS ENGINEERS!

The latest edition of "Engineering Opportunities"



Have you sent for your copy?

'ENGINEERING OPPORTUNITIES'

is a highly informative guide to the best-paid Engineering posts. It tells you how you can quickly prepare at home on "NO PASS—NO FEE" terms for a recognised engineering qualification, outlines the widest range of modern Home-Study Courses in all branches of Engineering and explains the benefits of our Employment Dept. If you're earning less than £20 a week you cannot afford to miss reading this unique book. Send for your copy to-day—FREE.

WHICH IS YOUR PET SUBJECT ?

- Mechanical Eng.
- Electrical Eng.
- Civil Engineering
- Radio Engineering
- Automobile Eng.
- Aeronautical Eng.
- Production Eng.
- Building, Plastics, Draughtsmanship, Television, etc.

GET SOME LETTERS AFTER YOUR NAME!

- A.M.I.Mech.E.
- A.M.I.C.E.
- A.M.I.P.E.
- A.M.I.M.I.
- L.I.O.B.
- A.F.R.Ae.S.
- B.Sc.
- A.M.Bric.I.R.E.
- CITY & GUILDS GEN. CERT.
- OF EDUCATION etc., etc.

--- FREE COUPON ---
Please send me your FREE 148-page "ENGINEERING OPPORTUNITIES"

NAME

ADDRESS

Subject or Exam. that interests me.....

British Institute of Engineering Technology
409B, College House, 29-31, Wright's Lane,
Kensington, W.8.

BIET

NEWS FROM THE CLUBS

HALIFAX AND DISTRICT AMATEUR RADIO SOCIETY
Hon. Sec. : A. Robinson (G3MDW), Candy Cabin, Ogdén, Halifax.

THE monthly meeting of the Halifax and District Amateur Radio Society, held at the Sportsman Inn, Ogdén, on May 5th, was in the form of a sale of "junk" from which the club benefited by over £6. Most of the gear was given by Mr. J. H. Bateman, G6BX. The chairman, Mr. Makin, presided. Meetings of the Society are held on the first and third Tuesdays of each month.

Future meetings :
June 16th, Ragchew.
July 7th, Open.
July 21st, Social.

INTERNATIONAL RADIO CONTROLLED MODELS SOCIETY

THE Annual Contest for Model Boats, Cars, etc., will be held this year on August Bank Holiday Sunday and Monday, (2nd and 3rd) in East Park, Kingston-upon-Hull. The contest is open to all radio-control modellers, whether or not they are members of the Society and, of course, visitors will be very welcome. Anyone interested is advised to make early application to participate. Entry forms, copies of Rules and any further information will be sent, on request to the Honorary Competition Secretary, B. E. Veal, 33, Steynburg Street, Newbridge Road, Kingston-upon-Hull, Yorks. (See also page 384.)

LIVERPOOL AND DISTRICT AMATEUR RADIO SOCIETY
Hon. Sec. : H. James, G3MCN, 448, East Prescott Road, Knotty Ash, Liverpool, 14.

MEETINGS are held every Tuesday, at 8 p.m., at the Gladstone Mission Hall, Queens Drive, Childwall, Liverpool (opposite the Signal House T.A. Centre).

As Mr. W. D. Wardle (G3EWZ) is leaving the city, he has had to resign as Hon. Sec. and his place has been taken by Mr. H. James (G3MCN).

The society has a very full programme ahead as apart from the normal Tuesday evening programme, visits to establishments of interest have been arranged.

An amateur station using the call G3AHD will be in operation on all bands during the Liverpool Show, July 16th to 18th.

Anyone wishing to join the Society will be most welcome, as will any visitors to Liverpool.

Future events :
June 9th, Open discussion on NFD.

OVERSTONE AMATEUR RADIO SOCIETY
Hon. Sec. : P. Crane, 120, The Drive, Northampton.

AT the Annual General Meeting on April 8th, the following officers were elected : Chairman, A. Hazelwood ; Treasurer, M. Bateman ; Secretary, P. Crane ; and Committee Members, P. Lea, D. Crane and "Bert."

The Club meets every Wednesday evening, and the subscription is 7s. per week. At present, at least half an hour each week is devoted to Morse practice.

The meeting on April 15th was held at the home of Cyril Wileman (G2HDK), where the Club went "on the air." Several very interesting visits have been made to the Northampton Short Wave Radio Club. We are always pleased to see new members—further details are available on application from the Hon. Secretary.

PORTSMOUTH AND DISTRICT RADIO SOCIETY
(Affiliated R.S.G.B.)

Hon. Sec. : A. C. Cake (G3CNO), 7, Wheatstone Road, Southsea, Hants.

THE Society holds its meetings every Tuesday evening at 7.30 p.m., over "Scarrs (Drapers) Ltd." in Albert Road, Southsea. New members are always very welcome. Morse instruction classes are held before meetings by special arrangement.

National Field Day plans are the main topic at present. At a meeting held recently, a site for operation was agreed upon—an open space off Eastern Road, Portsmouth. All members and friends are cordially invited to be present and we are particularly hoping to see as many former members of the Society as possible.

SLADE RADIO SOCIETY

Hon. Sec. : C. N. Smart, 110, Woolmore Road, Erdington, Birmingham, 23.

THE Club Station (G3JBN) at The Church House, High Street, Erdington, Birmingham, 23, is available for the use of members for constructional purposes. Instructional morse classes are held every Wednesday, at 7.45 p.m. Slow morse transmissions are radiated on the air each Tuesday evening from Station G3AYJ on 1.9 Mc/s, at 8 p.m.

Visitors to the Society's meetings, which commence at 7.45 p.m., prompt, and to the Club Station, are cordially welcome. Full particulars of the Society are obtainable from the Hon. Sec.

Forthcoming events :

June 19th.—"The Design of Direction Finding Receivers." A talk by Messrs. G. Nicholson, G3HKC, and C. N. Smart ; to be followed by a discussion.

June 28th.—RSGB D/F Contest Preliminary—High Wycombe.

WORTHING AND DISTRICT AMATEUR RADIO CLUB
(Affiliated R.S.G.B.)

Hon. Sec. : J. R. Tootill, 113, Kings Road, Lancing, Sussex.

THE Club continues to meet regularly at 8 p.m. on the second Monday of each month except August, at the Adult Education Centre, Worthing, which is almost opposite the Police Station in Union Place. There is a varied programme of lectures and talks, and new members are always welcome. The annual "Bucket and Spade Party" is being held on Sunday, June 28th on the raised promenade and, as usual, will be quite informal. All interested in Amateur Radio are cordially invited to come along with their families and friends, and full details can be obtained from the Honorary Secretary.

BASIC THEORY FOR THE CONSTRUCTOR

(Continued from page 380)

and since its value is 45 ohms, it will dissipate $0.09 \times 45 \text{ W}$ (i.e., $W=I^2R$), or 4.05 W. Thus, it would possibly pay to use a 5 W wire-wound resistor.

A small thermistor could be used in this position. With such a component, bulb failure would simply result in the thermistor increasing in

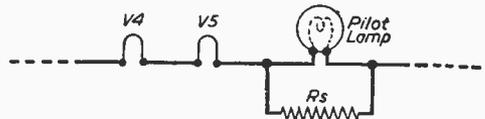


Fig. 4.—A reduction in bulb voltage can be secured by the shunt resistor R_s .

temperature and decreasing in resistance, thereby maintaining almost perfect chain balance. With an ordinary resistor, the chain current will be reduced slightly, as already described, when the bulb fails.

A Difficulty

It will now be apparent that substituting in a series chain a valve of which the heater is rated above the chain current is not a simple matter. Indeed, it would hardly be worth the trouble, since the whole of the chain, apart from the substituted valve, would have to be raised in current to suit that of the new valve. This may well mean the replacement of the ballast resistor.

(To be continued)

An Intercom Amplifier

IMPROVE RESULTS FROM SIMPLE HOME TELEPHONE CIRCUITS WITH THIS ONE-TRANSISTOR UNIT

By G. R. Francis

HOME telephone circuits, for amusement or communication between one room and another, usually have no means of amplification incorporated. They are sometimes termed "sound powered" and in the simplest possible form consist of two earphone or similar units, wired together as in Fig. 1. Additions may be present, such as a bell ringing circuit, or a buzzer, and two units may be employed at each end of

4½V dry battery, will give a worthwhile improvement in volume, so that conversation can be carried on easily, results being more nearly like those from a G.P.O. telephone.

Fig. 2 shows a simplified circuit without switching, so that the method of working can be readily understood. Here, it is assumed that unit "A" is acting as microphone. The signal from it is amplified by the transistor, so that unit "B," acting as receiver, works at much increased volume. The 100kΩ (100,000 ohm) resistor is of the small carbon type, as used in radio sets. The coupling condenser may be .5μF to 16μF capacity. About 2μF to 8μF is most satisfactory. It may be a "paper" condenser, bias condenser, smoothing condenser, or miniature transistor coupling condenser, as all give similar results.



Fig. 1.—Simple intercom circuit.

the line, one as microphone, and one as receiver. However, it is only with the actual telephone part of the circuit that the amplifier is concerned, not with the bells or buzzers, which can remain unchanged.

Volume

Though workable, an arrangement like that in Fig. 1 suffers from rather poor volume. Words spoken near unit "A" generate a current, operating unit "B." To reverse conversation, "B" is used as a microphone, and "A" as receiver. Losses, and the absence of any amplification make reproduction somewhat weak. This difficulty is increased if two units are used at each end of the line, as microphone and receiver, because the output of one unit is then distributed among the other three.

With magnetic units of this kind, a microphone step-up transformer cannot be used, while a valve amplifier would require H.T. and L.T. batteries, if it were not mains operated. All these difficulties may be overcome by using a transistor amplifier. A single transistor, with a 1½, 3, or

"Speak" and "Listen" Switch

To avoid the need for two complete amplifiers,

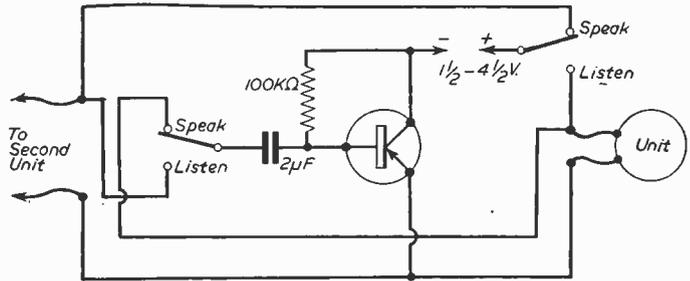


Fig. 3.—Amplifier circuit with "Speak/Listen" switch.

a change-over switch, wired as in Fig. 3, allows either unit to be used as microphone in turn. To simplify switching, the battery has been transferred to the other side of the unit circuit.

When changing from speaking to listening, the switch has to be operated. This resembles the method of working adopted with simple loud-speaker communication systems. The amplifier thus needs to be within reach of one unit, or built into a case in which the unit can be fitted. The switch has an "off" position to put the amplifier out of action.

When the buzzer or bell circuit gives warning, the user turns the switch to "speak" and answers, afterwards turning the switch to "listen." Two units, wired in series, can be used at each end of the line, to avoid the inconvenience occasioned by a single unit. When conversation has ended, the switch is returned to "off." If the person at the amplifier end is making the call, he operates the bell or buzzer push, turns the switch to "listen" and waits until the second person speaks.

(Continued on page 417)

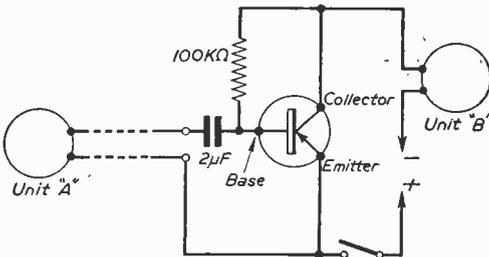


Fig. 2.—Amplifier circuit.



8-WATT PUSH-PULL AMPLIFIER

COMPLETE WITH CRYSTAL MIKE AND 8in. LOUDSPEAKER

A.C. mains 100-250 v. Size 10 1/2 in. x 6 1/2 in. x 2 1/2 in. Incorporating 6 valves, H.F. pen., 2 triodes, 2 output pens and rectifier. For use with all makes and types of pick-up and mike. Negative feed back. Two inputs, mike and gram., and controls for same. Separate controls for Bass and Treble lift. For use with Std. or L.P. records, musical instruments such as Guitars, etc.

£4.19.6 Plus P. & P. 7/6. Or 35/- deposit Plus P. & P. 7/6, and 3 monthly payments of 25/-.

6-WATT PUSH-PULL AMPLIFIER

A.C. Mains 200/250 v., incorporating 4 valves and metal rectifier, 2 inputs, high and low, and controls for same. Separate controls for Bass and Treble lift. Size of chassis 11 in. x 4 1/2 in. x 2 in.

59/6 Plus P. & P. 5/-.

PORTABLE AMPLIFIER


Size 6 1/2 in. long, 5 in. high, 2 1/2 in. deep. Will suit any type of crystal pick-up. Output approx. 2 watts. Incorporating ECC83 double triode. Cossor 142BT output pentode and contact-cooled rectifier. Fully isolated mains transformer for 230/250 A.C. mains. Base, treble and volume controls.

49/6 Plus P. & P. 3/6.

5in. SPEAKER with O.P. TRANSFORMER, purchased with the above, 18/6, plus P. & P. 1/6.



AC/DC POCKET MULTI-METER KIT

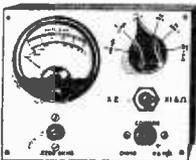

Comprising 2in. moving coil meter, scale calibrated in AC/DC volts, ohms and milliamps. Voltage range AC/DC 0-50, 0-100, 0-250, 0-500. Milliamps 0-10, 0-100. Ohms range 0-10,000. Front panel, range switch, wire-wound pot (for ohms zero setting), toggle switch, resistor and rectifier. In grey hammer finish case.

19/6 Plus P. & P. 1/6. Built and tested 7/6 extra.

Point to point wiring diagram 1/-, free with kit.

MAINS TRANSFORMERS

All with tapped primaries. 200-250 volts. 0-180, 180, 200 v., 60 ma., 6.3 v. 2 amps. 10/6. 320-0-320 v. 75 ma., 6.3 v., 2.5 amp., 5 v., 2 amp., 10/6. 350-0-350 v. 250 ma., 6.3 v. 7 amp., 5 v. 2 amp., 19/6. Postage and packing on the above 3/-.

F.M. TUNER UNIT

Permeability tuned, by famous German Manufacturer. Coverage 68-100 Kc/s. Complete with ECC85. Size 4" x 2" x 2".

25/- Plus P. & P. 1.6.

IMITATION LOG FIRE EFFECT

Size 14 inches x 11 inches


19/6 Plus P. & P. 2.6.

13 CHANNEL TUNER

34 to 38 Mc/s. complete with PCF80 and PCC84. These have been removed from chassis. 23/- Complete with knobs. P. & P. 3/6 extra.

as above, 16-19 Mc/s. complete with knobs less valves. 13/- Plus P. & P. 2.6.

SIGNAL GENERATORS

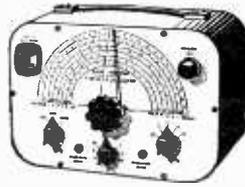


Cash £6.19.6 or 25/- deposit and 6 monthly payments of 21.6. Post and Packing 5/- extra.

Coverage 100 Kc/s-100 Mc/s on fundamentals and 100 Mc/s to 200 Mc/s on harmonics. Metal case 10in. x 6 1/2 in. x 5 1/2 in., grey hammer finish. Incorporating three miniature valves and Metal Rectifier. A.C. Mains 200/250 v. Internal Modulation of 400 c.p.s. to a depth of 30%; Modulated or unmodulated R.F. output continuously variable 100 millivolts. C.W. and mod. switch, variable A.F. output. Incorporating magic eye as output indicator. Accuracy plus or minus 2%.

unmodulated R.F. output continuously variable 100 millivolts. C.W. and mod. switch, variable A.F. output. Incorporating magic eye as output indicator. Accuracy plus or minus 2%.

Cash £4.19.6 or 25/- deposit and 4 monthly payments of 21/6. Plus Postage and Packing, 5/-.


Coverage 120 Kc/s-84 Mc/s. Metal case 10in. x 6 1/2 in. x 4 1/2 in. Size of scale, 6 1/2 in. x 3 1/2 in. 2 valves and rectifier. A.C. mains 230-250 v. Internal modulation of 400 c.p.s. to a depth of 30%, modulated or unmodulated R.F. output continuously variable 100 millivolts. C.W. and mod. switch variable A.F. output and moving coil output meter. Grey hammer finished case and white panel. Accuracy plus or minus 2%.

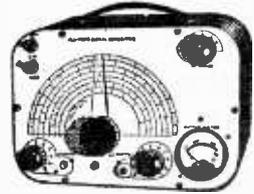

4-WAVE BAND COIL UNIT

Complete with tuning condenser. Separate sections for Short Wave. Coverage 10-21 m. 21-45 m., 44-100 m. and 190-545 m. I.F. 470 Kc. BRAND NEW, by famous manufacturer. Completely assembled on sub-chassis. With circuit diagram.

19/6 Plus P. & P. 3/6.

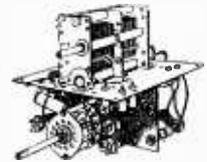

B.S.R. MONARCH UA8



4-speed, plays 10 records 12in., 10in. or 7in. at 33, 45 or 78 r.p.m. Intermixes 7in., 10in. and 12in. records of the same speed. Has manual play position; colour brown. Dimensions: 12 1/2 in. x 10 1/2 in. Space required above baseboard 4 1/2 in., below baseboard 2 1/2 in. Fitted with Full-FI turnover crystal head.

£6.19.6 Plus 5/- Postage & Packing.

CONSTRUCTORS' PORTABLE PARCEL



Comprising case, chassis, top plate, scale, 5in. P.M. speaker with O.P. trans., twin gang, 2 470 Kc/s. I.F.s. trimmers, 2 470 Kc/s. wave holders, wave-change switch and volume control with switch.

39/6 Plus 3/6 Postage & Packing.

RADIO & T.V. COMPONENTS (Acton) LTD.


23 HIGH STREET, ACTON, LONDON, W.3.

All enquiries S.A.E. Goods not dispatched outside U.K.

Treco Scope

The **TRECOSCOPE**, designed around a most modern 3" cathode ray tube and new type valves, meets all the requirements for a high performance and versatile general purpose oscilloscope. Its overall size is 7" x 8½" x 11" and the specification, too comprehensive to be fully given here, is contained in our illustrated brochure, a copy of which will gladly be sent on receipt of S.A.E.

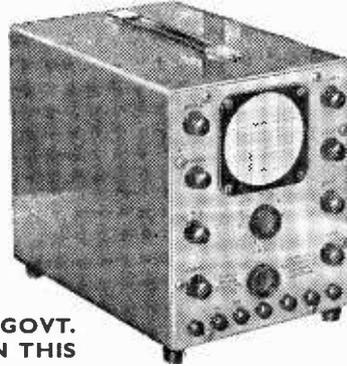*** NOT A SINGLE ITEM OF GOVT. SURPLUS STOCK IS USED IN THIS INSTRUMENT.**



CONTROLS : brilliance, focus, X shift, Y shift, coarse time base, fine time base, synchronisation, Y amplitude, X amplitude, Y input selector switch.

FACILITIES : Y plates via (1) high gain amplifier, (2) low gain negative feedback amplifier, (3) isolating condenser, (4) isolating condenser and attenuator. Hard valve time base covering 5 c.p.s., to 150 kc/s. X plate deflection from external source via X amplifier. Synchronisation via sync., amplifier at Y or other frequencies. 50 c.p.s., calibrating voltage. Brilliance modulation. Flyback suppression.

The Treco scope is guaranteed for 12 months.

PRICE : £17.17.0 or £22.0 down and 12 monthly payments of £1.9.7.
Postage and packing 6/-.

THE RANGE ELECTRONICS COMPANY

CORMORANT WORKS, LETT ROAD, LONDON, E.15

Phone : MARYland 5266.

Get these



CIRCUITS & WIRING DIAGRAMS

T.R.F. Circuits
Battery Circuits
Portable Circuits
S'het Circuits
Mains Circuits
Filter Circuits
F.M. Tuner

T.V. Converter Circuits, etc.

Send Postage 1/- (stamps)

OSMOR COILS are regularly used and recommended by designers writing in "Practical Wireless," "Wireless World" and "Radio Constructor." Why not follow the experts ?

"Q Coils" All ranges
Potted Coils
F.M. COILS Speaker Cross-over Coils
TAPE COILS ROD AERIALS
Coils and I.F.s for Transistor Circuits
SUB-MINIATURE COILS
Midget I.F. Trans. With ferrite cores



418 Brighton Road,
South Croydon.
Telephone : CRO 5143/9

RST

MAIL ORDER DEPARTMENT

211 Streatham Road, Mitcham, Surrey.

ALL VALVES LISTED ARE NEW STOCK

• Terms C.W.O. or C.O.D. Postage 3d. per valve.

MITCHAM 6201.

AZ31 10/8	EF92 5/3	PCF82	UY85 8/-	6K8G 7/6
B65 8/6	ET42 10/-		VP4B 17/6	6K8GT
DAF91 8/6	ET54 9/6	PCL82	W81M 5/9	6L1 12/6
DAF96 8/6	EL90 8/6		W142 9/-	6L6G 7/6
DF91 5/-	EM80 10/-	PCL83	W719 7/6	6L18 12/6
DH719 7/6	EM81 10/-		W727 7/6	6L19 21/-
DK91 9/-	EY81 10/6	PEN44	X78 21/-	6N7G/GT 7/6
EABC80 9/6	EY84 10/6		X79 21/-	6SL7GT 7/6
	EY86 14/-	PEN4VA	Z21 12/6	6SN7GT 7/6
EAF42 7/6	EY91 9/-		Z27 5/6	
EB91 6/-	EZ35 7/-		Z152 7/6	
EB41 9/6	EZ40 8/-	PL81 14/9	Z179 7/6	
EBF80 9/6	EZ41 8/6	PL82 10/-	1R5 9/-	
EBF89 9/6	EZ80 8/-	PL83 11/6	5U4G 7/6	6V6G 6/6
EC91 9/6	EZ81 8/-		5V4G 9/6	6X5GT 5/6
ECC33 8/-	EY32 21/-	PY80 8/6	5Y81 9/-	7S7 10/6
ECC81 8/6	FC4 17/6	PY82 8/-	5Y3GT 8/6	7Y4 7/6
ECC83 9/6	FC13 17/6	PY83 8/6	5Z4G 10/-	8D3 5/6
ECC84 9/6	FC13C 21/-	R10 21/-	6A8GT	10LD11
ECC85 9/6	GZ32 11/6	R19 19/6		
ECF80 12/6	H30 5/6	TDD4 17/6	6AL5 10/-	12A8H 10/-
	H83 9/6	TP22 17/6	6AM6 5/6	12AT6 9/-
ECF82 12/6	HB90 9/6	U142 8/-	6AN5 7/6	12AT7 7/9
	HL82 6/6	U147 7/-	6AQ5 8/3	12AU7 9/6
ECH35 9/-	ILL33D	U153 9/-	6BA6 7/6	12AX7 9/6
ECH42 10/-		UABC80	6BE9 7/6	12BA6 9/6
ECH81 9/-	KT33C 10/-	UAF42 9/-	6B76 7/6	12BE6 9/6
ECL80 12/6	KT66 17/6	UBC41 9/6	6BR7 15/-	12BH7 17/6
	LZ319 12/6	UBF80 9/6	6BW6 8/6	12J7G/GT 9/6
ECL82 12/6	MKT4(5)	UBW7 7/-	6BX6 7/6	12K7GT
	(or 7) 17/6	UCH42	6D2 6/-	12K8GT 8/6
EF37A 8/6	ML4 15/-	UCH81 10/-	6F1 15/6	12L6GT 12/6
EF40 15/-	MSP4 17/6	UCH83 10/-	6F12 5/6	12Q7 8/6
EF41 9/3	MU14 9/-		6F13 17/6	12Q7GT
EF42 12/6	MX40 17/6	UF41 9/-	6J5G 4/6	
EF50(A) 4/6	N142 9/6	UF49 9/-	6J7GT 9/6	35Z4GT 9/6
EF80 7/6	N153 11/6	UF89 9/-	6K7 4/6	
EF85 7/9	PCC84 9/6	UL41 9/6	6K7G 4/-	50L6GT 7/6
EF86 13/6	PCF80	UL84 9/6	6K7GT	
EF89 10/-		UY41 8/-		813 50/-
EF91 6/6				

SEND FOR LISTS.

Quotations given for any types not listed. Obsolete and old types a speciality.

It should be noted that the amplifier works best with units of reasonably high impedance, and many balanced armature and-diaphragm type earpieces are of this kind. Low impedance units, such as ex-service moving-coil phones, or low impedance balanced armature units, will prevent the transistor amplifier operating properly, unless a matching or coupling transformer is added to the circuit of each unit.

Wiring Details

The parts may be assembled on a small insulated panel, as in Fig. 4. With the inexpensive "Red Spot" type of transistor, the red spot indicates the collector, marked "C" in Fig. 4. Here, "B" indicates base, and "E" is the emitter connection. If another type of transistor is used, the maker's connecting data must be followed, because there is no standard method of showing leads, and wrong connections can easily damage the transistor. Any small low-frequency or audio-frequency type of transistor is satisfactory.

A 1½V dry cell is shown, but a 3V or 4½V battery can be used if the extra volume is wanted. The battery *must* be wired in in the correct polarity, negative (or zinc case) going to the collector. Reversing the battery may destroy the transistor.

A small rotary switch is suitable for change-over. With this type of switch, one position is used as "off" so that a two-pole, three-way switch is required. If a two-pole, two-way switch without off position is to hand, it can be used if an on/off switch is added in series with one battery lead. In the circuit diagram (Fig. 3) the switch is shown, for simplicity, as a two-pole two-way.

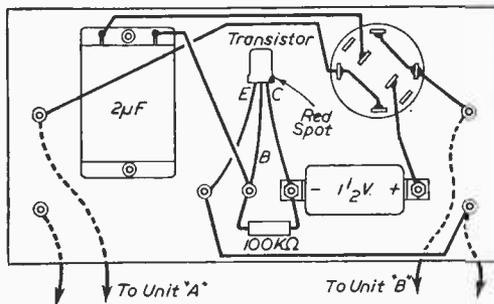


Fig. 4.—Wiring diagram.

However, in the wiring diagram (Fig. 4) a two-pole, three-way switch is shown, in which the position between "speak" and "listen" is used as the "off" position.

Condensers

Paper condensers can be wired in either way, but electrolytic or polarised condensers will have positive and negative markings. The *positive* tag or lead must then go to the switch, with the *negative* tag or lead to the base of the transistor.


The transistor leads can be taken to small bolts, which serve as junction points for other wiring. Four small terminals provide connections for the two sets of units. At the amplifier end, two or three feet of twin flex will be sufficient. For the second unit, or combined microphone and receiver, a long line of thin twin flex will be required. This will already be present if a circuit such as that in Fig. 1 has been used.

MULLARD SOUTHAMPTON WORKS

WORK on the second stage of the central Mullard semiconductor plant at Southampton has now been completed. The new section adds approximately 50,000 square feet of floor space to the plant's manufacturing capacity, and is already in production.

Silicon Transistors

Much of the space arising from the new

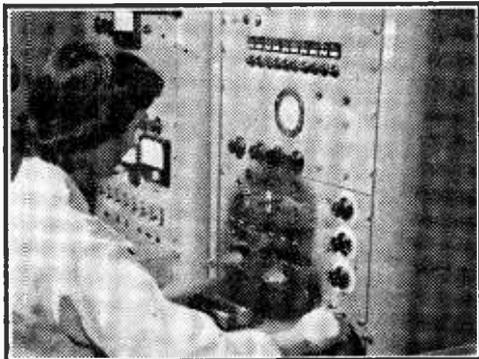

Final testing of germanium audio frequency transistors using semi-automatic equipment.

section is given over to the large-scale production of silicon transistors and diodes. The demand for silicon devices, which can operate at much higher temperatures than their germanium counterparts, is growing rapidly for industrial and military purposes, and an increasing amount of the plant's resources is being devoted to manufacturing them. It is expected that by 1960 silicon devices will account for a significant proportion of the total output.

Future Development

The next stage in the development of the Southampton plant is the construction of a 30,000 square foot administration wing, scheduled for completion early in 1960. This will release for manufacturing purposes a further area of factory floor space now being used for offices. Following this a further large section is to be added to the main factory building.

When completed, the Southampton plant will employ between 2,000 and 2,500 people. Its payroll at present numbers 1,000, of whom no fewer than 70 are graduate scientists and engineers working in the plant's research and development laboratories. The total number employed on transistor production throughout the Mullard organisation is at present 1,500.

The "Gramdeck" Tape-Recorder

A TAPE TRANSPORT MECHANISM WHICH CAN BE DRIVEN FROM AN ORDINARY
GRAMOPHONE TURNTABLE

THE "Gramdeck" is a cleverly designed unit for converting a gramophone into a tape-recorder. It consists of a diamond-shaped base plate in the centre of which is the tape drive capstan. A 5in. diameter plate is attached to the underside of the capstan and supports the whole unit on the turntable, as can be seen in the illustration. A slot is cut in one corner of the base plate and engages with a metal pillar fixed to the motor board, thus preventing rotation with the turntable. The unit is otherwise completely free to move, allowing for a turntable or drive plate which is out of true, thereby removing the possibility of wow.

Operation

The spindle of the take-up spool is driven by a plastic belt from the capstan and the slipping drive required is provided by friction between the spool, a felt washer and the rotating spindle. For rewinding, friction is increased by a weight, supplied with the unit.


In use, the tape passes from the feed spool over either of two guides, one of which contains a permanent magnet for erasing, to a tape head which records on half the tape width with the standard track sense. It then passes into a groove in the capstan and is held in place by a spring loaded roller. This roller locks in the open position by means of a catch with a push-button release.

Pre-amplifier

The head is of the high-impedance type and the output can be fed to a suitable audio amplifier or to the pre-amplifier supplied in the "Gramdeck" equipment. This amplifier, battery-powered, and measuring approximately $7\frac{1}{2}$ in. \times $4\frac{1}{2}$ in. \times $3\frac{1}{2}$ in., uses two transistors, one as the playback or

microphone amplifier and one as a 40kc/s recording bias oscillator. The battery used has an operating life of between 600 and 800 hours, and the output from the unit is about 250mV peak.

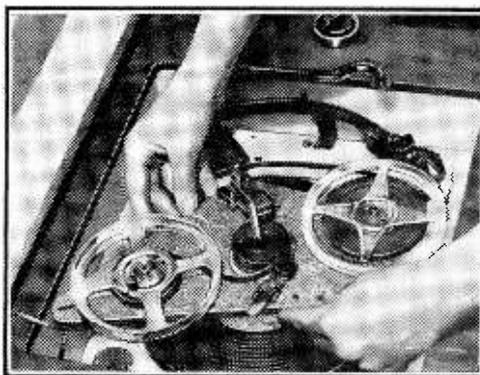The frequency response is good, even at the



The "Gramdeck."

slower gramophone speeds; at 78 rev./min. the tape speed is the standard $7\frac{1}{2}$ in./s., but at other gramophone speeds the tape speed is not standard. No wow, other than that already present in the gramophone unit, was detected during our tests. The unit performs very well, providing care is taken to set it up correctly. The threading of the tape can be a tricky operation, but becomes easier with practice.

The "Gramdeck" itself costs £7 10s. and the transistorised control unit £5 12s. 6d. Further details can be obtained from the suppliers, Messrs. Andrew Merryfield, Ltd., "Gramdeck," 29, Wright's Lane, Kensington, London. W.8.

SHORT WAVE SECTION

(Continued from page 389)

appreciable load on the I.F. transformer feeding it. A diode detector would reduce the selectivity obtainable because it would load the last transformer of the unit (T2). Capacitors C16 and C18 by-pass the I.F. signals but not the audio signals. The I.F. used is not very much above the highest audio frequencies and its complete removal is not easy. A small coupling condenser, C17, is used to introduce bass cut.

Alignment

The alignment of the unit is relatively simple. C1 should be connected to the receiver from which the signals are taken and, with V1 working, the last intermediate frequency transformer of the receiver supplying the signals to the unit should be re-trimmed, as the extra capacitance of C1

will have thrown it slightly off tune. Resistor R9 should be set for minimum resistance, i.e., maximum gain, and the value of either L1 or C8 should be altered until a signal is received at the output of V3 which should be connected to an audio amplifier. The audio amplifier of the receiver could be utilised if the signal is fed back from the second I.F. amplifier into the receiver. If no signal can be obtained, another condenser either slightly higher or slightly lower in value should be substituted for C8 until one is obtained. The cores of T1 and T2 should then all be set for maximum signal strength. This can be done much more accurately if a 0-1mA meter is placed in the anode lead of V3 and the cores of the two transformers are adjusted for maximum reading on this meter. A fairly strong signal is required to give a meter reading, but the meter reading then increases rapidly with increasing signal strength. The unit is then fully aligned.

TUBES

FACTORY REVAQUUMED. ALL GUARANTEED 3 MONTHS. Carriage and insurance 12/6 extra. Enquiries welcomed for any types not listed. Due to the high quality of our tubes and low number of returns, we are able to maintain the following unusually low prices.

- 6S01, 6S04, 6S05, CRM91, CRM92, MW22-7, MW22-14, MW22-14C, **£2/15/-**
- MW22-17, MW22-18, **£2/15/-**
- C12FM, CRM121, CRM121A, CRM122, MW31-7, MW31-14C, MW31-17 **£3/5/-**
- MW31-19, T12/54, **£3/5/-**
- 3/16, 2/31, 14KP4, 14KP4A, 106K, 121K, 141K, 7201A, 7202A, 7203A, AW36-21, C14FM, CRM141, CRM142, MW31-16, MW31-7A, **£3/15/-**
- ME36-24, MW36-44, T12-549, **£3/15/-**
- 17AR24, 17AS24, 6706A, C17FM, CRM171, CRM172, MW43-43, **£4/10/-**
- MW43-44, 7401A, **£4/10/-**
- 3/8A, 4/15, 6901A, C14BM, C17BM, CRM151, CRM152A, CRM152B, CRM153, MW41-1, MW43-50, TA15, **£5/5/-**
- TX14-2, MW43-49, **£5/5/-**
- C21HM, C21NM, CRM211, CRM212, **£6/15/-**
- MW53-20, MW53-80.

REGUNNED TV TUBES

- ALL GUARANTEED 12 MONTHS.** Excellent workmanship. Carr. & insa. 12/6.
- MW31/16, MW31/74, **£5/10/-**
- 121K, 121P **£5/10/-**
- MW36-24, AW36-21, 141K, 14KP4, CRM141, CRM142, **£5/15/-**
- CRM152A, CRM152B, CRM153, CRM171, MW43/64, 171K, 17AS24, **£6/15/-**
- 171K, 17AS24, **£6/15/-**
- MW53-20, MW53-80, **£9/10/-**
- CRM211, CRM212.

NEW TV TUBES

- Subject to Manufacturers Guarantee. Carriage and insurance 12/6 extra. All standard types available including Cosor, G.E.C., Emitron, Emitrace, e.g.
- MW6-2, 28.
 - MW31-74, AW36-21, AW36-80, **£10/10/-**
 - MW36-24, MW36-44, **£10/10/-**
 - C14FM, C14BM, £11.15.
 - MW43-50, MW43-54, **£12/-/-**
 - MW43-69, MW43-80, **£12/-/-**
 - MW41-1, CRM141, CRM142, £12.15.0.
 - CRM121, CRM123, £13.0.0.
 - CRM171, CRM172, CRM173, **£13/10/-**
 - C17BM, C17FM, **£13/10/-**
 - CRM152, £15.15.0, CRM152B, £16.15.0.
 - AW53-80, MW53-20, MW53-80, £18.0.0.

VALVES

GUARANTEED 3 MONTHS. 24 HOUR SERVICE FREE TRANSIT INSURANCE. All valves are new or of fully guaranteed ex-Government or ex-military origin. Satisfaction or Money Back Guarantee on goods if returned unused within 14 days.

10% DISCOUNT SPECIAL OFFER TO PURCHASERS of any SIX VALVES marked in black type (15% in dozens). Post: 1 valve, 6d.; 2-11, 1/-.

1A3	2/6	5V30T	9/6	6BX6	5/6	6J6	2/6	787	7/7	12Q7GT	6/6	2050	3/6	6BC91	9/-	EP86	14/6	KTW11	6/6	RP4H	9/-	UCH81	10/6
1A7	14/6	5Z41	9/6	6C4	6/6	6J7M	5/7	8K7	7/6	12N37	7/6	5753	9/6	6BF90	9/6	EPF8	9/6	KTZ63	5/6	SP41	3/-	UCL82	14/6
13G0T	11/6	5Z40T	11/6	6V3GT	5/6	6J7M	5/7	8K7GT	7/6	12A435	9/6	AZ31	9/6	EP89	9/6	EP90	9/6	6L59	3/6	6L81	3/6	UCL88	15/-
1K6	6/-	5AN1	9/6	6C8	4/6	6K6GT	7/6	10C1	9/6	20D1	9/6	6B88	9/6	6BL31	23/6	EP91	4/6	LN152	9/6	6NU2150A4	6/6	UF41	9/6
105	15/-	6AB8A	9/6	6C9	9/6	6K7G	2/3	10X2	12/6	20L1	14/6	6CH35	8/6	6E52	4/6	EP95	5/6	MU14	8/6	6TH30C	12/6	UP80	10/-
115G1	10/6	6AC7	5/6	6C10	9/6	6K7GT	5/6	6V61	8/6	20P1	14/6	6L38	8/6	6E91	4/6	EP97	4/6	X37	9/6	6U18	9/6	UP86	10/-
1185	7/6	6AK5	5/6	6V3	6/6	6K25	9/6	6V6GT	8/6	20P3	15/6	6Y31	7/6	6E93	11/6	EP98	9/6	6N78	11/6	1222	8/6	UP88	16/-
124	3/6	6AG7	5/6	6C8	11/6	6K9G	9/6	6X3	5/6	20P4	27/10	6B3	4/6	6E92	9/6	EP98	9/6	6N08	9/6	6U24	7/6	UP89	10/-
13G1	10/6	6AJ7	5/6	6C12	4/6	6K8GT	10/6	6X3GT	5/6	25A84	8/6	6D77	4/6	6E93	7/6	EP11	4/6	EP41	4/6	6U25	13/6	UP91	8/6
185	6/6	6AK5	5/6	6V3	6/6	6K25	9/6	6X3GT	5/6	25L64	6/6	6D152	5/6	6E93A	9/6	EP12	4/6	EP81	2/6	6U26	13/6	UP94	13/-
185	6/6	6AK5	5/6	6V3	6/6	6K25	9/6	787	7/6	25L6GT	9/6	6D3C32	10/6	6E93B	7/6	EP14	10/6	6Y84	8/6	6U31	5/6	UP96	14/6
185	6/6	6AK5	5/6	6V3	6/6	6K25	9/6	787	7/6	25Y5G	9/6	6D4F96	9/6	6E93C	8/6	EP14	4/6	PC989	19/6	6U33	6/6	UP96	10/6
185	6/6	6AK5	5/6	6V3	6/6	6K25	9/6	787	7/6	25Z26	9/6	6D1D41	4/6	6E93A	9/6	EP15	9/6	PC980	9/6	6U35	6/6	UP98	10/6
1T4	5/6	6AAM6	4/6	6P1	9/6	6L16G	13/6	787	7/6	278U	10/6	6D3F33	10/6	6E93E	9/6	EP14	6/6	PC982	11/6	6U32	7/6	UP97	9/6
2A7	8/6	6AT8	7/6	6P6G	7/6	6L17	9/6	787	7/6	30C1	9/6	6D3F81	6/6	6E93F	10/6	EP16	10/6	PC984	10/6	6U32	11/6	UP98	27/10
2D21	4/6	6B89G	4/6	6P12	4/6	6L19	11/6	787	7/6	30P1	9/6	6E96	9/6	6E93G	12/6	EP16	10/6	PC983	12/6	6U31	9/6	UP99	7/6
3Q5GT	9/6	6BA6	6/6	6P13	9/6	6L20	9/6	787	7/6	30L4	9/6	6E96	9/6	6E93H	9/6	EP17	7/6	PC984	10/6	6U31	9/6	UP99	7/6
384	7/6	6B89G	6/6	6P14	9/6	6P25	9/6	10C1	9/6	35L6GT	9/6	6D9H77	7/6	6E93I	7/6	EP18	7/6	6E935	6/6	6U31	9/6	UP99	7/6
3V4	8/6	6B89G	9/6	6P15	9/6	6P25	9/6	10X2	12/6	35W4	6/6	6D9K91	7/6	6E93J	7/6	EP19	7/6	6E936	6/6	6U31	9/6	UP99	7/6
4D1	2/6	6EJ6	7/6	6P23	6/6	6P27	9/6	10Y1	9/6	35Z46T	6/6	6D9K92	10/6	6E93K	10/6	EP19	7/6	6E937	13/6	6U31	9/6	UP99	7/6
5A4GT	11/6	6BH6	8/6	6P19M	2/6	6P28	9/6	10P9	10/6	35Z5GT	6/6	6D9L96	9/6	6E93L	9/6	EP20	7/6	6E938	9/6	6U31	9/6	UP99	7/6
5U4G	7/6	6BR7	11/6	6P25	5/6	6P29GT	10/6	10L11	12/6	49	7/6	6D123	11/6	6E93M	9/6	EP21	9/6	6E939	9/6	6U31	9/6	UP99	7/6
6V4G	9/6	6B89G	6/6	6P25G	9/6	6P29	9/6	10L13	12/6	49	7/6	6D123	11/6	6E93N	9/6	EP21	9/6	6E940	9/6	6U31	9/6	UP99	7/6
5Y3G	6/6	6B89G	6/6	6P25GT	4/6	6P29GT	10/6	10L14	12/6	50L6GT	9/6	6D1D94	4/6	6E93P	7/6	EP22	9/6	6E941	9/6	6U31	9/6	UP99	7/6
								12A7E	9/6	59K1	11/6	6D196	9/6	6E93Q	5/6	EP22	9/6	6E942	9/6	6U31	9/6	UP99	7/6
								12A7F	7/6	54K1	11/6	6E90	9/6	6E93R	14/6	EP23	12/6	6E943	12/6	6U31	9/6	UP99	7/6
								12A7G	7/6	618T	9/6	6E9C90	9/6	6E93S	9/6	EP24	9/6	6E944	10/6	6U31	9/6	UP99	7/6
								12A7H	5/6	618T	11/6	6E9C91	9/6	6E93T	9/6	EP24	9/6	6E945	9/6	6U31	9/6	UP99	7/6
								12B6A	6/6	80	7/6	6E9F42	9/6	-Brit.	1/6	KT36C	6/6	EP21	8/6	6U31	9/6	UP99	7/6
								12B6B	9/6	83	7/6	6E9B34	1/6	-Brit.	2/6	KT36	6/6	EP22	8/6	6U31	9/6	UP99	7/6
								12B6C	9/6	83	7/6	6E9B34	1/6	-Brit.	2/6	KT36	6/6	EP22	8/6	6U31	9/6	UP99	7/6
								12B6D	9/6	83	7/6	6E9B34	1/6	-Brit.	2/6	KT36	6/6	EP22	8/6	6U31	9/6	UP99	7/6
								12B6E	9/6	83	7/6	6E9B34	1/6	-Brit.	2/6	KT36	6/6	EP22	8/6	6U31	9/6	UP99	7/6
								12B6F	9/6	83	7/6	6E9B34	1/6	-Brit.	2/6	KT36	6/6	EP22	8/6	6U31	9/6	UP99	7/6
								12B6G	9/6	83	7/6	6E9B34	1/6	-Brit.	2/6	KT36	6/6	EP22	8/6	6U31	9/6	UP99	7/6
								12B6H	9/6	83	7/6	6E9B34	1/6	-Brit.	2/6	KT36	6/6	EP22	8/6	6U31	9/6	UP99	7/6
								12B6I	9/6	83	7/6	6E9B34	1/6	-Brit.	2/6	KT36	6/6	EP22	8/6	6U31	9/6	UP99	7/6
								12B6J	9/6	83	7/6	6E9B34	1/6	-Brit.	2/6	KT36	6/6	EP22	8/6	6U31	9/6	UP99	7/6
								12B6K	9/6	83	7/6	6E9B34	1/6	-Brit.	2/6	KT36	6/6	EP22	8/6	6U31	9/6	UP99	7/6
								12B6L	9/6	83	7/6	6E9B34	1/6	-Brit.	2/6	KT36	6/6	EP22	8/6	6U31	9/6	UP99	7/6
								12B6M	9/6	83	7/6	6E9B34	1/6	-Brit.	2/6	KT36	6/6	EP22	8/6	6U31	9/6	UP99	7/6
								12B6N	9/6	83	7/6	6E9B34	1/6	-Brit.	2/6	KT36	6/6	EP22	8/6	6U31	9/6	UP99	7/6
								12B6O	9/6	83	7/6	6E9B34	1/6	-Brit.	2/6	KT36	6/6	EP22	8/6	6U31	9/6	UP99	7/6
								12B6P	9/6	83	7/6	6E9B34	1/6	-Brit.	2/6	KT36	6/6	EP22	8/6	6U31	9/6	UP99	7/6
								12B6Q	9/6	83	7/6	6E9B34	1/6	-Brit.	2/6	KT36	6/6	EP22	8/6	6U31	9/6	UP99	7/6
								12B6R	9/6	83	7/6	6E9B34	1/6	-Brit.	2/6	KT36	6/6	EP22	8/6	6U31	9/6	UP99	7/6
								12B6S	9/6	83	7/6	6E9B34	1/6	-Brit.	2/6	KT36	6/6	EP22	8/6	6U31	9/6	UP99	7/6
								12B6T	9/6	83	7/6	6E9B34	1/6	-Brit.	2/6	KT36	6/6	EP22	8/6	6U31	9/6	UP99	7/6
								12B6U	9/6	83	7/6	6E9B34	1/6	-Brit.	2/6	KT36	6/6	EP22	8/6	6U31	9/6	UP99	7/6
								12B6V	9/6	83	7/6	6E9B34	1/6	-Brit.	2/6	KT36	6/6	EP22	8/6	6U31	9/6	UP99	7/6
								12B6W	9/6	83	7/6	6E9B34	1/6	-Brit.	2/6	KT36	6/6	EP22	8/6	6U31	9/6	UP99	7/6
								12B6X	9/6	83	7/6	6E9B34	1/6	-Brit.	2/6	KT36	6/6	EP22	8/6	6U31	9/6	UP99	7/6
								12B6Y	9/6	83	7/6	6E9B34	1/6	-Brit.	2/6	KT36	6/6	EP22	8/6	6U31	9/6	UP99	7/6
								12B6Z	9/6	83	7/6	6E9B34	1/6	-Brit.	2/6	KT36	6/6	EP22	8/6	6U31	9/6	UP99	7/6

Post: 2 lbs. 1/6, 4 lbs. 2/-, 7 lbs. 2/9, 15 lbs. 3/6. No C.O.D. Callers always welcomed. (E. C. Weds.) ALL ITEMS LESS 5% AND POST FREE IN DOZENS.

TECHNICAL TRADING CO. 350-352, FRATTON ROAD, PORTSMOUTH.

SPECIAL OFFERS

4-SPEED RECORD PLAYERS. Latest B.S.R


KINGSMERE SUPPLIES LIMITED

MAIL ORDER HOUSE

TERMS: Remit with Order or C.O.D.

All Goods Post Free. (Export extra.)

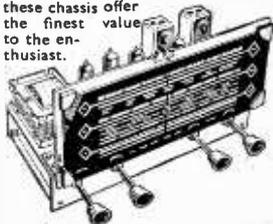Built to the highest specifications, these chassis offer the finest value to the enthusiast.



ALL BRITISH RADIOGRAM CHASSIS. 3 WAVEBANDS 5 MULLARD VALVES

ECH42, EF41, EBG41, EL41, EZ40. Brand new and guar. A.C. 200/250 v. Short-Medium-Long-Gram. P.U. High Q. dust core coils. Latest circuit technique. AVC and neg. feedback. 4 watts. Chassis size-13½ x 6 x 8in. high. Aligned and calibrated ready for use. Quality at Low Cost. Chassis isolated. H. P. Dep. £5 and five monthly of £1.

OUR PRICE £9-9-0

Matched Speakers, 5in., 6in. x 4in., 6½in., 8in. 17/6 ea. 10in. 25/-


BRAND NEW AND BOXED
OUR PRICE £6-19-6

LIST PRICE £9-15-0

U.A.S. WORLD'S FINEST 4-SPEED AUTOCHANGER
 IDEAL FOR USE WITH OUR CHASSIS
 H. P. Dep. £3-10 and four monthly of £1.

THE KINGSMERE POCKET MULTITESTER

Size 5½ x 3½ x 1½in.

300 microamp F.S.D. 3in. Scale.

17 Ranges. 3,330 ohms per volt.

A.C. Volts. 0 to 1,200 v. in 5 ranges.

D.C. Volts. 0 to 1,200 v. in 5 ranges.

D.C. Current. 0 to 300 m.a. in 3 ranges.

Resistance. 0 to 20 K and 0 to 2 meg.

Decibels. -20 to +23 db. and +20 to +37 db.

Complete with leads and prods. Uses No. 8 battery.

Made in Belgium.

BARGAIN PRICE £6-19-6
FOAMCOURT WAYE, FERRING, WORTHING, SUSSEX

SPECIAL PURCHASE
FINEST QUALITY WORLD FAMOUS
"GEVAERT GEVASONOR"

LONG PLAY PLASTIC RECORDING TAPE

On universal fitting plastic spools, for all recorders—single and double track. 50% extra at standard prices.
 7in. spool 1,700ft. tape ... our price 35/- (List 50/-)
 5in. spool 850ft. tape ... our price 21/- (List 28/-)

Satisfaction guaranteed or cash refunded.

SOLDERING EQUIPMENT

BY



PRECISION SOLDERING INSTRUMENTS
for the ELECTRONICS INDUSTRY

- Comprehensive range
- Robust & Reliable
- Light weight
- Rapid heating
- Bit sizes 3/32in. to 3/8in.
- 'Permabit' or Copper bits
- All voltage ranges 6/7v. to 230/250 v.
- Prices from 19/6

Illustrated is the 25w. 3/16in. replaceable bit model with safety shield.

British and Foreign Patents. Registered designs. Suppliers to H.M. and Foreign Governments. Agents throughout the world.

Brochure No. S.10 sent free on request.

Sole proprietors and manufacturers:

LIGHT SOLDERING DEVELOPMENTS LIMITED

106 George Street, Croydon, Surrey.

Phone: CROydon 8589 Grams: Litesold Croydon



A television course for you to study at home

Entirely new! Practical!
Bang up to date!

THE FAMOUS BENNETT COLLEGE OFFERS YOU THIS

An entirely new course of study based upon up-to-date techniques has now been prepared by The Bennett College.

The course is non-mathematical, and contains clear diagrams, starting from the very beginning (even including the basic principles of sound radio receivers, if desired) and covering all that you need to know!

This is what you've been looking for! A home-study course includes: production

of the signal, scanning and reproduction of picture from signal. Aerials, types and purpose. The cathode-ray tube. Time-base oscillators, and output circuits. Synchronisation. Video frequency amplifiers. The TV tuner, turret, incremental, etc. Television test gear. Television faults.

For more details, fill in the coupon below. Your studies cost little, the book you need is included in the cost.

-To THE BENNETT COLLEGE (Dept. G 104TV, Sheffield)

Please send me details of the new
 TELEVISION SERVICING COURSE

NAME _____

ADDRESS _____

AGE _____


NEWS FROM THE TRADE

LATEST DEVELOPMENTS
IN RECEIVERS AND
COMPONENTS

TRANSISTOR PORTABLE

A PORTABLE transistorised radio has been added to the "Dansette" range of J. and A. Margolin, 112-116, Old Street, London, E.C.1. The receiver has a socket for a car aerial. The case is covered with hard-wearing plastic and there is a choice of colours: off-white, red or pastel green.

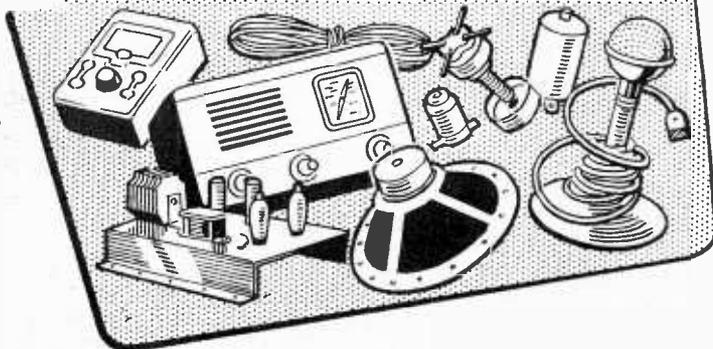The overall size is 8½ in. × 5½ in. × 3 in. and the set weighs 3lb. 4oz. including the battery which



microphones. Details from Dynatron Radio Ltd., Maidenhead, Berks.


PRICE REDUCTION

WESTINGHOUSE BRAKE AND SIGNAL COMPANY LTD. have recently announced readjustments in the prices of their range of germanium power rectifier units resulting in reductions of up to 33 per cent. on some types. These reductions are made possible by improvements in manufacturing technique and increased production capacity.

Simultaneously with the introduction of the revised prices a new publication (Technical Publication 601) has been issued, in which are contained full details of the existing range of germanium rectifier units.

TAPE HEAD DEMAGNETISER

RESIDUAL magnetism in tape recorder heads can cause unwanted hiss and background noise, degrading both recording and playback. This can be avoided by periodically demagnetising the heads. Cinesmith Products, Britannic Works, Regent Street, Barnsley, has produced the "Cinesmith Depolariser" for this operation. The device is housed in a plastic moulding with press switch at one end and operative pole pieces at the other. The "toe" of the pole piece is designed

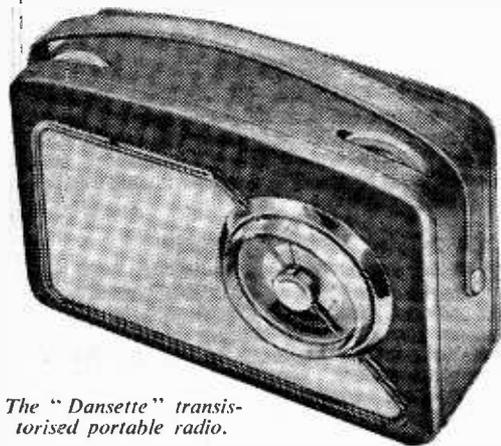

The "Dansette" transistorised portable radio.

has a life of some 130 hours. The retail price is 19 guineas, including purchase tax.

NEW POWER AMPLIFIER

DYNATRON RADIO'S new audio amplifier type LF20 provides 20 watts of audio output power with negligible distortion. In physical construction, the equipment is robust and engineered to a high standard. The chassis contains a power supply for the pre-amplifier (normally the TC20) and radio feeder completely separate from the main power pack to ensure amplifier stability.

The circuit consists of a low-noise pentode directly coupled to two high-gain triodes, functioning as a cathode-coupled phase inverter stage which drives the push-pull output valves operating in an ultra-linear circuit.

The preamplifier for use with the LF20 is the Controller Mixer Unit TC20. This unit is a low-noise high-gain pre-amplifier with mixing circuits for four channels and a comprehensive control system. Various inputs are provided for all types of pick-up, radio tuner units, tape recorders and




Dynatron power amplifier LF20.

so that the recorder heads can be reached easily without any dismantling. The price is 34s. from dealers or post free from the manufacturers.

STEREO CHASSIS

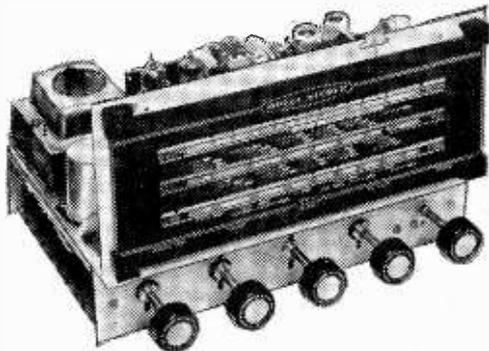A CHASSIS which is suitable for converting older types of radiogram to give reproduction of stereo records has been marketed recently. When switched to radio, the output is 8 watts and




The Dulci stereogram chassis.

in the 'gram position, 4 watts per channel. This chassis, known as the H3S Stereogram, is £27 16s. 6d., including tax. Descriptive literature is available from the manufacturers, Dulci Co., Ltd., 97-99, Villiers Road, London, N.W.2.

PICKUP ARM AND HEAD

PHILIPS ELECTRICAL LTD., Shaftesbury Avenue, London, W.C.2, have introduced a Transcription pickup arm (Type NG.5400/S) fitted with a head (Type AG.3060) which is designed for reproduction of stereophonic as well as monophonic long playing records. Arm and head complete sell as £15 15s.

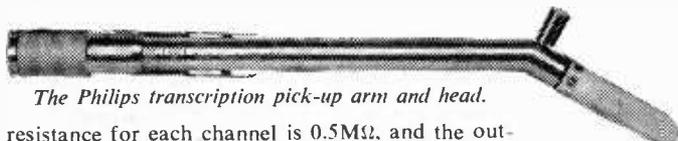The arm is professional in appearance, with a durable satin chrome finish. It is equipped with a playing weight adjustment and the arm pedestal and rest are adjustable in height. The crystal pickup head has a diamond stylus and a frequency response of 30-12,000 c/s. The recommended load



The Philips transcription pick-up arm and head.


resistance for each channel is 0.5M Ω , and the output is approximately 0.5V for each channel. The suggested playing weight is 4-6 grams.

HOLLOW SPINDLE POTENTIOMETER

A NEW approach to spindle-controlled variable components by The Plessey Company Limited, Ilford, Essex, has resulted in the production of a triangular-spindled potentiometer in which the spindle is formed from flat brass strip.

The design of the spindle is such that the need for machining special flats and knob fixings, etc., has been obviated, all locations and fixings being achieved by bending or forming the hollow brass

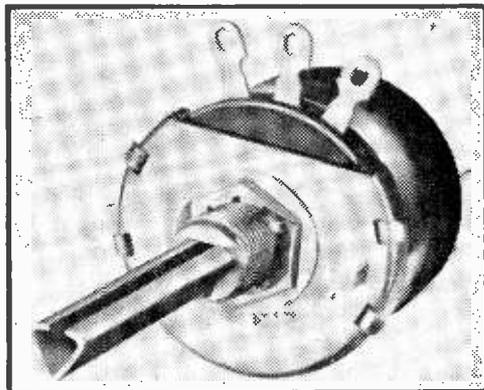spindle to accommodate a polystyrene ring which, in turn, holds the brush gear. The limit stop and switch operating lug are also incorporated in the polystyrene ring.



The Plessey triangular-spindled potentiometer.

CHANGE OF ADDRESS

MESSRS. WILSON, 48, Cathay, Bristol, 1, inform us that they are moving to more suitable premises at 213, Stapleton Road, Bristol, 5 (Tel.: 57819 and 51850). By moving to this new address they hope to give a full retail and mail order service.

LEARNING ABOUT RADIO

A NEW postal teaching service has been started under the name of "Radiostructor" by Educational Technical Developments Ltd. At present there are five courses ranging from one suitable for the beginner to one for the more advanced student. Every main fact is shown in a picture-strip technique and none of the courses is mathematical.

With each course, parts are supplied for the building of at least one piece of high grade equipment and this provides a valuable means of practical instruction. Emphasis is also placed on the use of measuring instruments. Although no

previous knowledge or experience is required, any student who possesses such knowledge will find that the material makes an interesting way of revising old facts and, perhaps, of learning new ones. Full details can be

obtained from "Radiostructor," 46, Market Place, Reading, Berks.

STABILISED POWER SUPPLY UNIT

THE "Advance" stabilised power supply Type 1L101 is a special-purpose instrument providing a constant voltage source of 600 volts positive and two stabilised 150 volts negative D.C. supplies, one of which is a variable line having a high impedance source. Two stabilised 6.3 volts A.C. heater supplies are also provided. Further details can be obtained on application to the manufacturers, Advance Components Ltd., Roebuck Road, Hainault, Ilford, Essex.

...and NOW THE TOURIST PORTABLE

4 valve, 2 waveband (Med. and L.W.) Lightweight Battery Radio. Wt. 3 1/2 lbs., incl. Battery.

Complete Receiver Component Kit ... 57/6 P. & P. 1/6
 Set 4 miniature valves (96 series) ... 35/- P. & P. 9d.
 5in. Speaker & Output Trans. ... 21/- P. & P. 1/6
 Cabinet, Dial & Knobs, etc. ... 22/6 P. & P. 2/-
 Parts List and Instruction Booklet, 1/6. (Free with Kit)


Latest circuitry, delayed AVC & A.F. Neg. feedback.

Sensitive Ferrite Rod Internal Aerial. Contemporary style 11" weight Cabinet. Operates from B114 Battery, 69 v. + 1 1/2 v. (8/- extra)

MAINS UNIT KIT Available shortly Only 45/-

Terrific performance — Remarkable size — Staggering value

Size only Bin. x 5 1/2 in. x 4 in.

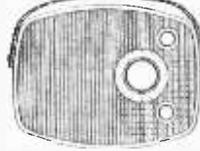

Complete Kit post free **£6.10.0**

G.R.T. Heater Isolation Transformers

New improved types—mains prim. 200/250 v. tapped.
 All Isolation Transformers now supplied with alternative no boost plus 25%, and plus 50% boost taps, at no extra charge.
 2V. 2A type 12/6 (P. & P. 1/6)
 6.3V. .5A .. 12/6 ..
 10.5V. .3A .. 12/6 ..
 13V. .3A .. 12/6 ..
 Other voltages available—no extra cost.
 Small size and tag terminated for easy fitting.

RE-GUNNED TV TUBES

New Reduced Budget Prices
 New Heater, Cathode and Gun Assembly fitted to all tubes. Reconditioned virtually as new. Full 6 months' guarantee to highest standards—as used by our own Service Dept.
 12in. £6. 14in. £7. 17in. £8.10.0.
 Most Mullard & Mazda types ex-stock. Carr. & ins. 10/-
 10/- Part Exchange allowance on your old tube.

COAX 80 OHM CABLE

Stand 1/2" diam.
 Low Loss Semi-Air Spaced AERAXIAL. SPECIAL REDUCED PRICES
 20 yds. 12/6. 40 yds. 22/6. 60 yds. 32/6.
 P. & P. 1/6. P. & P. 3/-. P. & P. 3/-.
 All other lengths 8d. per yd.
 Coax Plugs, 1/-. Sockets, 1/-. Couplers, 1/6.
 Cable End Sockets, 1/6. Outlet Boxes, 4/6.

VOLUME CONTROLS

10,000 ohms—2 Megohms. All long spindles. Morganite Midget type. 1 1/2 in. diameter. Guar. 1 year. Log. or Lin. Ratios. Less Sw. 3/-. 1 P. 8w. 4/9. Twin Gauged Controls, 1 Meg. 1 Meg., less Sw., each 5/9.

CONDENSERS—Silver Mica. All Prof. values. 2 pl. to 1000 pl. 6d. each. Dkto ceramic, 9d. each. Tubulars 450v. T.C.C.'s, etc., .001 mfd.—60 and 1/350 v., 9d. each. 1.02-1/500 v. 1/- each. 55 Hmms, 1/6. 8 T.C.C. 1/9. .001 60v. 5/6. .001 200v. 9/6.
RESISTORS—FULL RANGE 10 ohms—10 megohms 20% ± w. 3d.; ± w. 5d.; 1 w. 6d.; 2 w. 9d. 10% Hi-Stab., ± w. 5d.; ± w. 7d.; 5% ± w. 9d.
HI-SWAPS, ± w. 1/6 (10-100 ohms, 2/-).
PRE-SET W/W POTS, 7/V Type. 25-ohms—30K ohms, 3/-.
50K—2 Megs. (Carbon Track), 3/-.
SPEAKERS—FRET—Expanded Bronze sandcast metal 8 x 6in. 2/6; 12 x 6in., 3/-; 12 x 12in., 4/6; 12 x 15in., 6/-; 24 x 12in., 8/-, etc.
TYGAN FRET (Contemporary pattern) 12 x 12in., 2/-; 12 x 18in., 3/-; 12 x 24in., 4/-, etc.
SPEAKERS P.M. 3 ohm 2 1/2 in. Elac, 10/6, 3 1/2 in. Goodman, 16/6. Bin. 3. & A. 17/6. 6in. Celestion, 18/6. 7 x 4 in. Goodman, 18/6. 8in. Rola, 20/-, 8in. Special Cone G'snna, 21/6. 10in. R. & A. 25/-.

Listed above are only a few items from our very large stock. Send 3d. stamp today for Complete Bargain List.

Terms: C.W.O. or C.O.D. Kindly make cheques, P.O.s, etc., payable to T.R.S. Post/Packing up to 1/6 7d., 1lb. 1/1, 3lb. 1/6, 5lb. 2/-, 10lb. 5/9. Hours: 9 a.m.—6 p.m. 1 p.m. Wed. Open all day Saturday.

NEW VALVES GUARANTEED ALL

1R5, 1T4 7/6	DF96	9/-	EP80	10/6	PCP82	10/6	
1R5	7/6	DK96	9/-	EP86	14/6	PCL83	12/6
3R4, 3V4	8/-	DL96	9/-	EP91	8/6	PL81	14/6
5Z4	9/6	35L6	10/6	EL41	10/6	PL82	10/6
6K7	6/6	EA8C9	9/6	EL64	11/6	PL83	11/6
6K8	6/6	EBC41	10/6	EM85	11/6	PY80	9/6
6Q7	8/6	BCX83	9/6	EY51	12/6	PY81	9/6
6N7	8/6	BCX84	12/6	EY86	14/6	PY82	8/6
6AV6	7/6	BCP80	12/6	EZ80	8/6	PY83	10/6
6X4	7/6	BCF82	12/6	EZ91	8/6	U25	18/6
7C5	9/-	ECH81	10/6	ME14	9/6	U191	13/6
7Y4	8/6	ECL80	12/6	PCCR4	10/6	UCH42	10/6
DAF96	9/-	ECL82	12/6	PCP80	10/6	UF41	10/-

and many others too numerous to mention.
SPECIAL PRICE PER SET
 1R5, 1T4, 1R5, 3R4, or 3V4 ... 27/6
 DK96, DF96, DAF96, DL96 ... 35/-
 6K8, 6K7, 6Q7, 6V6, 5Z4 or 6X5 ... 35/-

MULLARD "3-3" AMPLIFIER

Quality built to Mullard's specification, with special sectionalised O/P Trans.
 Complete kit with front panel only **£6.19.6**, p. & p. 3/6.

JASON FM TUNER UNITS (87-105 Mc/s)

Designer-approved kits of parts for these quality and highly popular tuners available as follows.
STANDARD MODEL (FMT1)—as previously extensively advertised.
 COMPLETE KIT, 5 gns., post free.
 Set of 4 spec. valves, 30/-, post free.
LATEST MODEL (FMT2)—attractively presented shelf mounting unit in enclosed Metal Cabinet with Built-in Power Supply.
 COMPLETE KIT, £7. p. & p. 3/6.
 Set of 5 spec. valves, 39/6.
NEW JASON COMPREHENSIVE F.M. HANDBOOK, 2/6 post free.
 48 hr. Alignment Service, 7/6. p. & p. 2/6.

PERDIO POCKET TRANSISTOR "6"

(as extensively advertised)
 Med. & L.W. TRANSISTOR PORTABLE.
 Modern sensitive superbet circuit—4 Transistors and 1 Xtal Diode. Lightweight and compact, only 5 1/2 in. x 3 1/2 in. x 1 1/2 in. Weight 14 ozs. **£9.19.6**, P. & P. 2/6.

ELECTROLYTICS ALL TYPES NEW STOCK

Tubular Wire Ends	32 & 32/350 v. B.E.C.	5/6
25/25 v.	50/12 v. 1/8 Can. Types, Clips 3d. ea.	1/6
50/50 v.	4/500 v. 2/-	8/500 v. Dub. 3/-
8/450 v. T.C.C.	2/8	16/450 v. Hunts 5/6
8 & 16/450 v. T.C.C.	5/-	32/350 v. B.E.C. 4/6
16/450 v. B.E.C.	3/6	32 & 32/275 v. Hunts 4/6
16 & 16/450 v. T.C.C.	5/6	60 & 100/350 v. B.E.C. 11/6
32/350 v. B.E.C.	4/6	60 & 250/275 v. B.E.C. 12/6
50 & 50, 350 v. B.E.C.	6/6	100 & 200/275 v. B.E.C. 12/6

MAINS TRANSFORMER WINDING CAPACITY AVAILABLE FOR PROTOTYPES & SMALL RUNS

TRANSISTOR 'ONE-WATT' AMPLIFIER 6 v. Battery Operated

Latest Push-Pull, 4 Transistor circuit giving full 1 watt Output into standard 8 ohm speaker. Good sensitivity and improved freq. response. Neg. feedback, Var. Tone and Volume Controls. (Chassis Size 6 1/2 in. x 3 1/2 in. x 1 1/2 in. Current consumption 10 mA (maximum)—250 mA at 1 watt.
 2 matched GEC GET15 Transistors 42/- pr.
 2 GEC GET3 Transistors 21/- pr.
 Driver Trans. 8/6
 Output Trans. (to 3 ohms) 10/6
 Complete Kit of Parts incl. circuit, etc., less speaker.
ONLY 99/6 p. & p. 2/6.
 Circuit and instruction booklet 1/6 post free.

STAAR 45 r.p.m. SINGLE RECORD PLAYER 6 v. Battery Operated.

LT weight Xtal Pick-up with Twin Sapphire Stylus (one spare). Auto Stop. Mounting 7 1/2 in. x 6 in. Attractive Continental styling, ideal companion Unit to above Transistor Amplifier.
RECOMMENDED BARGAIN
ONLY 92/6 P. & P. 3/6.
 Suitable Cabinet 8 1/2 in. x 3 1/2 in. to house above units and 7 in. x 4 in. Speaker. Available shortly.

RECORD PLAYER BARGAINS

SINGLE PLAYERS 4-speed BSR (TU9), £4.10.0; 4-speed COLLARO (4/564), 6 GME.; 4-speed GARRARD (4 M.P.), £7.10.0. GARRARD (TA Mk. II), £8.19.6. Carr. and Ins. 3/6.
AUTOCHANGERS 4-speed BSR (UA8), £6.19.6; 4-speed COLLARO, £7.18.6; GARRARD (RC121/D Mk. II) Plug-in head, stereo adapted, 10 gns. BSR UA12 latest Stereo and Monaural model, 10 gns. Carr. and ins. 4/6. All above units are latest 4-speed models, fitted lightweight crystal pick-up and twin sapphire styl. Complete and ready to use.
FINEST SELECTION AVAILABLE—ALL BRAND NEW AND GUAR.

RECORD PLAYER CABINETS

Contemporary style, rexine Cabinet covered cabinet Price in red with white polka dot relief, cream interior. Carr. and Size 18 1/2 x 13 1/2 x 11 1/2 in. 3/6. Ht. 8 1/2 in., fitted with all accessories, including baffle board and anodised metal fret Space available for all modern amplifiers and tone changers, etc. Uncut record player mounting board 14 x 13 in. supplied.
2-valve AMPLIFIER Mk. 2
 Latest developed circuit giving a higher fidelity response and greater output (2-3 watts) using twin stage valve ECL82 and neg. feedback Tone Control. Complete with knobs wired and tested with 6in. Speaker, etc., ready to fit in above cabinet. Only **£3.19.6**. Carr. 2/6.



RADIO COMPONENT SPECIALISTS (Est. 1946)

70 BRIGSTOCK ROAD, THORNTON HEATH, SURREY (THO 2189)
 50 yards Thornton Heath Station.

Buses: 130A, 133, 159, 166 and 190

ADVISORY SERVICE

We offer a complete before and after sales service. Our advice is ALWAYS available and freely given, BUYING or NOT! Whether expert or novice, let our extensive experience ensure your success.

AERIALS

An even wider range. We select the ever-popular I.T.V. add-ons to illustrate our bargains.
5 ELEMENT. Complete with universal clamp and stand-off arm. Still unbeatable, 39/6. Also at 45/-.
8 ELEMENT. As above. 51/6. Also at 62/6.
Easifix. All aerials pre-assembled and collapsed for transit.
Easimod. All single aerials can be modified to "double" arrays if desired.
Tokiteasi! DO be careful on the roof. DON'T wear crêpe soles in wet weather. (Better still, wait for good weather.)
NOTE.—Efficiency and gain of aerials depends on number of elements, spacing, siting, etc., and hardly varies with PRICE which concerns finish, long-term durability and patent assembly methods. DO write us for aerial advice if in doubt.

CABLE & ACCESSORIES

CO-AXIAL. Hi-grade, low loss, suitable all normal purposes Expanded polythene type. 8d. per yd. any length.
SEMI-AIRSPACED. A "must" for long runs in fringe areas ("Don't spoil the ship," etc.) 1/6 per yd. any length.
DIPLEXERS (junction boxes). Indoor type, 10/3. Outdoor type, 13/-.
IF-IN-DOUBT. Use a separate download for I.T.V. with a skirting board "diplexer" if necessary.

I.T.V. CONVERTERS

WE ARE CONVERSION SPECIALISTS. Our supplementary advice ensures success. Many appreciative letters from all parts.
 Still available: CYLDON, BRAYHEAD and CHANNEL converters and turret-tuners at VERY FAVOURABLE PRICES
 Write for advice and quote, giving make, model no. and local channels.

BARGAIN OF THE MONTH

VALVES: Types PCC84, PCF80, ECC84, ECF80. Per pair, new, boxed, Mullard or Brimar, £1 post free.

C.R.T. "RE-NU" KITS

Give that ageing tube a new lease of life! Reactivate as per our simple advice.
 Booster available but not always needed.
 18 months of good extra viewing quite common.
 Complete kit, with reactivation advice and multi-purpose transformer, leads, etc., 37/6, pkg./postage 2/6.
BETTER THAN BRUTE-FORCE BOOSTING!

RADIO KITS (F.M./V.H.F.)

Our DO-IT-YOURSELF radio. Again, after many tests, we have selected the famous Cossor 701K.
 Everything except the cabinet for a 6-valve V.H.F./F.M. radio. Pre-aligned R.F. and I.F. stages. (Expensive test gear not required).
 10in. Elliptical loudspeaker.
 Illustrated construction manual plus our Supplementary Advice. £15.15.0 tax paid.

VALVE KITS FOR YOUR TV

Save hours of fault-finding. Clear 90% faults. One off, each type. Guaranteed valves, tested prior to despatch and very carefully packed.
 Complete with TV Fault-finding Guide and advice on your TV. Standard Kits: £5.0.0 post free. (If non-standard, favourable quote by return.) Why pay repair bills? (State make and model number.)

TERMS OF BUSINESS

Cash with order or C.O.D. (2/6 extra).
 Extended credit on more expensive items. Write to us in confidence.
 Packing and carriage 1/6. Above £5 free, except aerials (5eL, 2/6; 8eL, 3/6; Others, 5/-).
 If in doubt or if needing advice WRITE US FIRST.
 (Our catalogue now available—6d. stamp.)

WILSON

213 STAPLETON ROAD, BRISTOL 5
 TEL. 58150 (day), 57819 (night)

AVOMETER MODEL 40

Just purchased from the Ministry of Supply, these famous A.C./D.C. Test Meters are a "snip" for anyone requiring a First Grade instrument. The overall size is 7 1/2 in. x 5 1/2 in. x 3 1/2 in., indication being given on a 5 in. Mirror Scale. Thoroughly overhauled, and complete with heavy Leather Carrying Case. Batteries and Instructions. Provides 40 Ranges of Current. Voltage and Resistance, as follows:

D.C. Voltage	A.C. Voltage	D.C. Current	A.C. Current
60 mV	5 V	3 mA	6 mA
120 mV	1 V	12 mA	12 mA
600 mV	60 V	12 mA	60 mA
1.2 V	120 V	60 mA	120 mA
6 V	240 V	120 mA	600 mA
12 V	480 V	600 mA	1.2 A
60 V	600 V	1.2 A	6 A
120 V	1,200 V	6 A	12 A
240 V		12 A	
480 V			Resistance
600 V			1,000 Ohms
1,200 V			10,000 Ohms
			100,000 Ohms

ONLY £10.19.6 (Carriage, etc., 5/6.)

COMMUNICATIONS RECEIVER R1155

The famous Bomber Command receiver known the world over to be supreme in its class. Covers 5 wave ranges 18.5 to 7.5 Mc/s. 7.5 to 3 Mc/s. 1,500 to 600 kc/s. 500 to 200 kc/s. and 200 to 75 kc/s. and is easily and simply adapted for normal mains use. Full details being supplied. All sets thoroughly tested and in perfect working order before dispatch, and on demonstration to callers. Fitted latest type super slow-motion tuning assembly. Have had some use but in excellent condition. ONLY £7/19/6.
A.C. MAINS POWER PACK OUTPUT STA6G. In black crackle case to match, enabling it to be operated immediately, by just plugging in, without any modification. With built-in 6 1/2 in. P.M. speaker, £5/10/-, or de-luxe with 8 in. speaker, £6/10/-.
DEDUCT 10/- IF PURCHASING RECEIVER AND POWER PACK TOGETHER.
 Send S.A.E. for illustrated leaflet, or 1/3 for 14-page booklet which gives technical information, circuits, etc., and is supplied free with each receiver. Add carriage 10/6 for Receiver, 5/- for Power Unit.

AMPLIFIER N24

Manufactured for the Admiralty in 1952 by Burndepct. this utilises 4 valves, 1 each 5Z4C - 6V6G - 6J6G - 6J5G, and high quality components such as "C" Core-Transformers and Block Paper Smoothing Condensers. Has A.C. Mains Pack for nominal 110/230 volts. Provision for 600 ohms or High Impedance Input, and has Output to 600 Ohms Line. For normal use only requires changing Output Transformer. Can be used for speech or Music. 50Watts High Quality Reproduction. Output approximately 4 watts. Enclosed in metal case, and designed for Standard 19 in. Rack Mounting, having grey front panel, size 19 in x 7 in. with Chromium Handles. All connections to rear panel, front having On/Off Switch, Gain Control, Indicator Light, Fuses and Valve Inspection Panel. BRAND NEW IN MAKER'S PACKING. ONLY £4/9/6 (carriage 10/6).

HRO MAINS POWER UNITS. Input 115/230 volts A.C./D.C. output (fully smoothed) 230 volts 75 mA., and 6.2 volts 3.5 amps. Complete in black crackle case. ONLY 60/-.
POWER UNITS TYPE 231. Primary input 200/250 v. 50 cycles. Outputs of 250 v, 100 mA. and 6.3 v. 4 amps. Fitted double smoothing. For normal rack mounting (or bench use) having grey front panel size 19 in. x 7 in. BRAND NEW. ONLY 59/6 (carriage, etc., 7/6).
12 VOLTS AMERICAN DYNAMOTOR. Delivers 220 volts at 100 milli. Ideal for running Car Radio or Electric Shaver, etc., from Car Battery. ONLY 32/6.
6 v. VIBRATOR PACKS. Output approx. 130 v. at 30 mA., fully filtered and smoothed. COME BRAND NEW. ONLY 12/6.
R1155 SUPER SLOW-MOTION TUNING ASSEMBLY. As used on all late model R1155s. Easily fitted to "A" sets. etc. BRAND NEW. ONLY 12/6.

EHT TRANSFORMERS. 5.5 kV. (Rect.) with 2 v. 1 a., 79/6. 7 kV. (Rect.) with 2 v. 1 a., 89/6. 2.5 kV. (Rect.) with 2-0-2 v. 1.1 a., 2-0-2 v. 2 a. (for VCR97 tube, etc.). 42/6 (postage 2/- per trans.).

FWKET VOLTMETERS. Read 0-15 volts and 0-300 volts A.C. or D.C. BRAND NEW AND UNUSED. ONLY 18/6.
CRYSTALS. British Standards 2-pin 500 kc/s., 15/-; Miniature 200 kc/s., 10/-.

ROLA 6 1/2 in. P.M. SPEAKER. Mounted in grey cracked metal cabinet 9 in. x 9 in. x 4 1/2 in., with volume-control. Ideal for use with receiver, or as extension. BRAND NEW. ONLY 27/6. (Post 2/6).

MAINS ISOLATING TRANSFORMER. Manufactured by Vortexion. Fully shrouded. Will provide true 1:1 ratio from nominal 230 v. Primary. Rated at 100 watts. BRAND NEW. ONLY 22/6. (Post 2/6).

SPRAGUE CONDENSERS. Metal cased, wire ends. New .01 mfd. 1,000 volt, and .1 mfd. 500 volt, 7/6 per dozen. Special quotes for quantities.

HARRIS ELECTRONICS

(LONDON) LTD.

138 Gray's Inn Road, London, W.C.1.

(Phone TERminus 7937)

Please include carriage costs on All items.

(Open until 1 p.m. Saturdays. We are 2 mins. from High Holborn (Chancery Lane Station) and 5 mins. by bus from King's Cross.)

ZENER DIODES

EXAMPLES OF THE USE OF THESE DEVICES IN VOLTAGE STABILISATION.

By E. G. Bulley

THESE units belong to the semi-conductor category and can be classified as silicon diodes. When the zener diode is wired into D.C. circuitry, it is connected with reverse polarity.

The conventional silicon diode has a high reverse resistance together with a low forward resistance, but in the zener diode, this reverse resistance is broken down at what is known as the zener voltage. This voltage is the reverse voltage specified by the manufacturer.

Voltage Stabilising

In such diodes, however, the reverse voltage is related to the reverse current, and this current value is more or less zero for all values of reverse voltage until the zener value is reached when breakdown occurs and the reverse current increases. The reverse voltage in this region is then more or less independent of the current passing through the device, in which case, the voltage can be said to be constant.

One must, however, bear in mind that the upper reverse current range is limited by the permissible dissipation of the diode and furthermore, the lower limit is governed by the slope or reverse resistance.

It is this constant voltage characteristic that lends the device to voltage regulation applications.

Such applications will have advantages over many of the conventional methods now in use

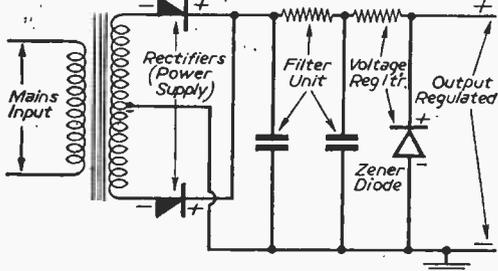


Fig. 1.—Circuit using a Zener diode to obtain a stabilised output from a power supply.

including small physical size and extremely long life, both important factors.

High Voltages

It is recommended by the manufacturers that several of these devices should be connected in series if it is required to regulate several hundreds of volts rather than using an individual diode of much larger breakdown voltage. The reason is that the heat dissipation is spread over many diodes instead of one single unit.

Basic circuits showing these devices connected

as voltage regulators are shown in Figs. 1 and 2.

New applications for zener diodes will no doubt be developed more fully this year, and will undoubtedly include such applications as wave-

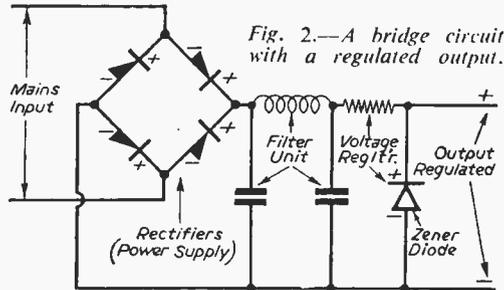


Fig. 2.—A bridge circuit with a regulated output.

form clipping and reference circuits.

These devices lend themselves to the experimenter and constructor and will prove interesting to those who like to develop new circuits and applications.

Books Received

THE PRACTICAL HI-FI HANDBOOK. By G. J. King. Published by Odhams Press, Ltd., 96, Long Acre, London, W.C.2. 224 pages. Price 30s.


This profusely illustrated book, as its name implies, covers the subject of high fidelity equipment, and has been written with the aim of providing practical and up-to-date information on the various kinds of hi-fi equipment and their choice, operation and servicing. It deals with pre-amplifiers, loudspeakers, enclosures, pickups, record players, microphones and mixers and has a chapter devoted to stereophony.

RADIO CIRCUITS : A STEP-BY-STEP SURVEY. Fourth Edition. By W. E. Miller, M.A.(Cantab.), M.Brit.I.R.E. Published by Iliffe and Sons, Ltd., Dorset House, Stamford Street, London, S.E.1. Price 15s. net (by post 15s. 10d.). Size 8½in. x 5½in. 172 pages, including 84 diagrams in the text, and two fold-outs.

This popular book explains in simple language and in easy stages all the varieties of circuits that are found in radio receivers of the kind that are used for broadcast reception. It does this by taking separately each stage of the receiver, item by item, and explaining it without the complication of all the associated circuits round it.

In this way every detail can be absorbed easily by the reader, who is not obliged to cope with more than he can assimilate at any one time. As he acquires familiarity with several parts, however, he is introduced to their association with one another, and he is finally led to an understanding of the complete circuit of a receiver.

Open to Discussion

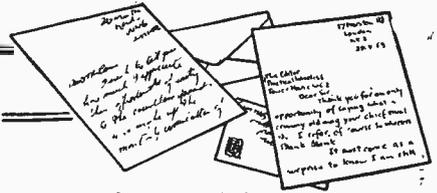

The Editor does not necessarily agree with opinions expressed by his correspondents.

Transistors v. Valves

SIR.—As a member of the younger generation to which G. Plachey refers (May issue, "Open to Discussion"), I would like to answer his points in support of valves.

One very important factor in support of the transistor is its size and it seems obvious to me that, as TV sets (and for that matter radio sets) become more and more complicated in the search for better quality and more sensitivity, the only way to keep them down to a reasonable size will be to use transistors.

As for the small home radio, why the need for two sets, home and portable? The transistor set can compete on equal terms with the mains set where economy is concerned. With transistors a set with enough power and quality for a home radio can easily be made light enough to be taken out on a picnic or holiday as a portable, as indeed has been done by a prominent manufacturer.—MARTIN ROBINSON (13) (A.H.G.S. Grammar School, York).

Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying commercial or surplus equipment. We cannot supply alternative details for receivers described in these pages. WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE. If a postal reply is required a stamped and addressed envelope must be enclosed with the coupon from page iii of cover.

selves together" and take stock. The irrefutable fact is that the days of the valve in common application are severely limited. Unfortunately this country has lagged behind in industrial production of semi-conductors, America and Western Germany being well ahead. However, the last twelve months have seen giant strides and several new factories have come into production.

Transistors have many advantages—they don't wear out and, in spite of popular belief, the associated circuitry is simpler and involves fewer components. For example, take the crystal diode (a semi-conductor) which replaced the valve in many makes of domestic superhet years ago—and simplified the circuit. Transistors will be considerably cheaper to produce; we have seen retail price reductions in recent months.

To older readers, I would say, "One is as young as one's mental approach."—VINCENT EVANS (Parbold, Lancs).

Cabinets

SIR.—I wonder if anyone can solve a problem that many a constructor has to face—that of acquiring a smart cabinet to house his newly built chassis; after all, our hobby is wireless, not carpentry, and the trouble about purchasing a cabinet by post is the cost of carriage. It would help if a cabinet firm could supply a set of, say, five cabinets of such sizes that they would fit into each other (like a nest of tables) for ease of transport and storage. The sizes of the cabinets should also be such that each would suit a standard size of chassis. Perhaps one or two new standard sizes of chassis would have to be created and the writers of constructional articles would be recommended to use one of the standard chassis where possible.—T. G. BELL (Manchester, 20).


Meter Shunts and Multipliers

SIR.—Recent issues have dealt with the conversion of milliammeters to voltmeters, which can be done merely by putting in series with the milliammeter a multiplier resistance R_1 given by $R_1 = V/I - R_m$ where V is the required voltage range, R_m is the meter's resistance and I is the FSD current of the meter. Two am-

(Continued on page 429)

SIR.—I sympathise with the nostalgic feelings of your two correspondents (May and June "Open to Discussion") for the thermionic valve, but like all of us older folk brought up on cathodes, grids and anodes we must "pull our-

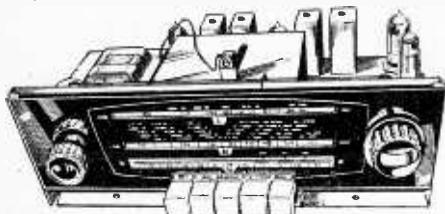WONDERFUL OFFER OF A.M.-F.M. CHASSIS AT £13.6.8. (P. & P. 10/-)



Why buy a F.M. Tuner at the same price?
Tapped input 220-225 v. and 226-250 v. A.C. ONLY.
Chassis size 15" x 6 3/4" x 5 1/4" high. New manufacture.
Dial 14 1/2" x 4" in gold, red and deep brown.
Pick-up, Extension Speaker, Ae., E. and Dipole sockets.
Five "piano" push buttons—OFF, L.W., M.W., F.M. and Gram. Aligned and tested. With all valves & O.P. Transformer.
Covers 1,000-1,900 M.; 200-500 M.; 88-99 Mc/s.
Valves EZ80 rect., ECH81, EF89, EABC80, EL84, ECC85.
Speaker & Cabinet to fit, polished, with back, 67/6.
10" x 6" ELLIPTICAL SPEAKER, 20/- Tone Control fitted.
TERMS:—(Chassis) £4.16.8 down + 10/- carr. and 6 Monthly Payments of 30/-, or with Cabinet & Speaker £5.9.2 down + 10/- carr. and 7 Monthly Payments of 35/-.


"READY TO USE" I.T.A. CONVERTER

I.T.A. high gain converter. ALL CHANNELS—ALL AREAS—ALL SETS. Direct switching (I.T.A. to B.B.C.); internal power pack: valves PCF80 and PCC84; moulded cabinet 8 1/2" x 4" x 6". No alteration to your set; fitted in 10 mins. 12 months' guarantee. For Philips' sets using Twin Feeder Specify "Twin Feeder."
£5.5.0 p. & p. 3/-




AUTOMATIC RECORD CHANGERS COLLAR CONQUEST

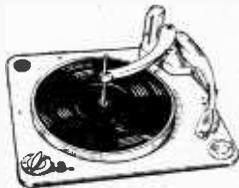with manual play also. Turnover crystal pick-up, 4-speed, A.C. mains 200-250 v., see illus. Buy for your friends as well. Box of 4 B.S.R. Monarch for only £26 (carr. £1).



£7.17.6 (5/- p. & p.)

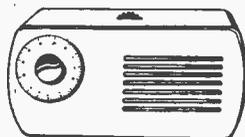

10 GUINEAS
(Reg. Post 2/6 extra)


Fully transistorized completely built printed circuit Radio, M.W. only. Originally nearly twice the price. Uses Ever Ready 9 v. PP4 battery.

Weights only 16 ozs. Unbreakable plastic case, cream, red or blue. 6" x 3 1/4" x 1 1/4". We have received more than 20 Stations at loudspeaker strength.

SIX TRANSISTOR SUPERHET KIT £9.19.6
Med. and L.W.; Printed Circuit; Instruction Book. Internal aerial. Details as for 10 Gn. Set above. All items supplied separately. Write for price list.

BATTERY CHARGER KITS with mains leads, and clips. 6 v. and 12 v. in one case. (P. & P. 3/-) 1 amp 21/-; 2 amp. 30/-, (or assembled 5/- each extra).

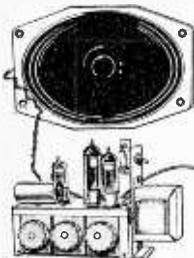AERIALS. F.M. Aerials single dipole room mtg., 17/6; ditto loft mtg., 20/-; "H" with chimney lashings, 65/- Co-axial low loss cable 8d. yard or 20 yds. 12/6, all these items carriage paid.



3-VALVE AMPLIFIER (INCL. RECT.). Capable of giving 6 watts. 8" x 5" Speaker wired-in. Mains and output transformers. Valves ECC81, EL84 and Rect. 3 Controls, volume, bass and treble. On/Off switch. Fully guaranteed. Chassis size 6 1/2" x 3" x 2 1/4".

67/- (3/- p. & p.)

Large selection of complete Radiograms, ready built in cabinets, with 4-speed Autochanger. Write for details, giving approximate size required. Price from £25 for A.M. only, or £30 for A.M./F.M.

GLADSTONE RADIO—25, Wordsworth Road, Worthing, Sussex, Tel.: 235; 58A, High Street, Camberley, Surrey, Tel.: 2633; 3, Church Road, Redfield, Bristol, 5, Tel.: 51207.

GRAMOPHONE AMPLIFIER with 5in. SPEAKER. On Fabric covered Baffle 12 1/2" x 5". Mains and Output Transformers. Metal Rectifier. ECL82 Valve. Tone and Volume Controls. On/Off switch. Plenty of Volume. Fully Guaranteed. Two Knobs supplied. Ready to play. ONLY 57/- (post 3/-). Useful for Stereo.



BEREC "PIONEER" RADIO IN MAKER'S CARTON. Valves DK96, DF96, DAF96, DL96. Berec Ever-Ready Battery B103, 20/- extra. Two Short Wavebands 2.5 to 7 Mc/s and 6.5 to 17 Mc/s. Cabinet, 12" x 7 1/2" x 6". In kit form with instructions and fully wired coil pack. Two Short Wavebands £3.10.0. One M.W. and S.W. £3.17.6. Plus 2/6 p. & p. Separate items supplied.



ONLY £4.15.0 (5/- p. & p.)

BATTERY ELIMINATOR. Converts your Battery Set to Mains. For 4 Low Consumption Valves (DK96 range). 90 v. 15 ma. and 1.4 v. 125 ma., 42/6 (2/6 post). 200-250 v. A.C. Size 5 1/2" x 3 1/2" x 2". Also for 250 ma. 1.4 v. and 90 v. 15 ma. at same price. Specify which.

LOUDSPEAKERS—Rola 10,000 line (2-3 ohm), 3 1/2" square, 15/- (1/-); 8" x 5" Celestion elliptical 20/- (1/6); 6 1/2" circ. 14/6 (1/6); all 2-3 ohm. (p. & p. in brackets).

50 SILVERED MICA AND CERAMIC CONDENSERS. 10/-, post paid.

Send 6d. (stamps will do) for our illustrated catalogue of the above items and others. All New Goods. Posted Orders to Worthing, please. Delivery by return. Terms:—One-third down and balance plus 7/6 in four equal monthly payments. Postage with down payment. (C.O.D. 2/- extra.)

SEE SPECIAL TERMS FOR A.M./F.M. CHASSIS.

SKILLED MEN!

USE YOUR KNOWLEDGE IN A WORTHWHILE JOB

VACANCIES
FOR
LINEMEN
DRIVERS
DISPATCH RIDERS
DRAUGHTSMEN
DRIVER
ELECTRICIANS
RADIO
MECHANICS
TECHNICAL
STOREMEN
TELEGRAPH
MECHANICS
OPERATORS
in
**THE ROYAL
SIGNALS**

*Up to £25 tax-free Bonus
plus first-rate wages for
two weeks of your time*

ARE you in a skilled trade? Then you can probably add a tidy sum to your income by joining the Army Emergency Reserve. For one thing, you get pay and allowances at full Regular Army rates whilst in camp. And the more your skill's worth in civilian work, the higher your Army rank and pay. Better still, you also get £9-£25 bonus tax-free.

For this you just spend 14 days a year at a camp, working on your own speciality. And money's not the only profit you get from that. You get a grand refresher course, giving you a lot of new ideas, and putting you right in touch with the latest Army developments. And you

get a welcome break from the usual routine, with sports, games and a great social life. For the place is full of people with the same interests as yourself. Don't miss this chance! Send off the coupon now to: H.Q. A.E.R. (R. Sigs.), Blacon Camp, Chester.

POST THIS OFF RIGHT AWAY!

*Please send me—without obligation—the illustrated booklet telling me
all about the Army Emergency Reserve.*

NAME

ADDRESS

TRADE (PW/AER)

culties arise; first, R1 usually comes to a number which is not available as a preferred value, and secondly, the resistor must be accurate, with a tolerance of only a few per cent., instead of 20 per cent. as with the usual resistors.

Initially, use for the multiplier a 20 per cent. resistor of the nearest preferred value above R1, and call this one R2. This will make the voltmeter read low. To find out how low, use the voltmeter in its present state to measure a known voltage, such as a battery that is new or has been checked with a standard voltmeter, and obtain the ratio $x = \text{actual voltage}/\text{reading shown}$. x will therefore be just greater than one. Then obtain a resistance $R3 = x.R1/x - 1$ and put this in parallel with R2.

As an example, with a meter $I = 1\text{mA}$ and $Rm = 100\Omega$ to read to 5 volts.
 $R1 = (5/0.001) - 100 = 4,900\Omega$.

Therefore $R2 = 5,600\Omega$, being the nearest preferred value above. Then, allowing for R2 being 20 per cent. tolerance, let us assume that a 3-volt battery gave a reading of 2.7V. Then the term

$\frac{x}{x-1}$ becomes 10, and $R3$ is 49Ω , and for this a 47k resistor can be used, which again need only be of 20 per cent. tolerance, though 10 per cent. could be used as these are normally the same price.

Not only does this method give a multiplier of the required value, but although neither resistor is an accurate one, the error is only 1 per cent. if $R3$ is a 10 per cent resistor, because $R3$ is so much greater than $R2$.—J. C. ALLDRED (Romsey, Hants).

SIR,—Mr. Berry, in the May issue, claims that his method of calculating shunt values is simpler than the formula given in the April issue, but is it?

The formula $R_s = \frac{I_m R_m}{I - I_m}$ consists of one multiplication, one subtraction, and one division. Mr. Berry's method adds to that number to the tune of one multiplication and one division.

My own method, and I use it daily, is as follows.

Taking Mr. Berry's example, subtract the meter current, 1mA, from the total current, 1A, leaving 999mA, which is the current in the shunt. The shunt current is 999 times as great as the meter current, so the shunt resistance required is 999 times smaller than the meter resistance. Divide 999 into 100 ohms, therefore, which gives the answer, 1.001 ohms. If the reader will compare this method with the formula he will see that it is exactly the same, but done in three logical steps.—R. MASSEY (Leeds, 7).

"Arrangements"

SIR,—With reference to Mr. W. J. Nye's letter in the June issue of PRACTICAL WIRELESS, I should like to point out that, while not denying that certain classical composers use themes from works of other composers, at least they openly admit that they "borrow," as shown in the titles. Examples which spring to mind include Rachmaninov's "Rhapsody on a Theme of

Paganini" and Benjamin Britten's "Variations and Fugue on a Theme of Purcell."

With regard to Dvořák's "New World Symphony," I would point out that, though negro spirituals inspired him to write this symphony during a visit to America, the various movements were not derived directly from them.—M. HUTCHINSON (Petts Wood, Kent).

SIR.—I have been reading with considerable interest the correspondence in your columns on the above subject, and find myself in complete agreement with "Thermion." I am firmly of the opinion that no one has the right to "arrange" a composer's work, for the composer, and he alone, knows just how he intends the music to be performed. It appears to be nothing but sheer laziness and cheating on the part of a few so-called "musicians" who would prefer to monkey about with someone else's tunes rather than coin their own. Outrageous misquotations from poetry and plays generally bring forth a spate of indignation. Why then is this not the case with music?—S. LEWIS (London, S.E.).

Correspondents Wanted

SIR.—I am 16 years of age and very interested in amateur radio. I shall soon be taking up radio and television as a career, and would like to correspond with any amateur radio listeners of my own age.

I would also like to know if anyone could tell me the frequency and time at which Radio Budapest comes on the air for the radio amateurs' programme.—G. CUNDY (6, Oswald Crescent, Park Estate, Ashbourne, Derbyshire).

SIR.—I am 15 years of age and very interested in amateur radio. I hope to be a radio amateur in the near future, and would, therefore, like to correspond with any boys of my age who are interested in radio. I should like to say that I enjoyed very much reading your series "Printed Circuits." I found it very interesting.—J.v.d. HOVENS (98, Twin Street, Rustenburg, Transvaal, South Africa).

RESISTOR WATTAGES

(Continued from page 402)

Resistors will often withstand some over-running without breaking down, but this is not wise. Instead, when appreciable power is dissipated, it is better to use a resistor with a generous wattage rating, as a precaution against early failure.

Mains Droppers

With resistors of high wattage, such as mains droppers and line cords, it is usual to rate the component or cord in terms of the current it is designed to carry. This will usually be .15A, .2A, or .3A. Provided the dropper or cord has the appropriate current rating, the wattage need not be known. It will, however, be large. For example, a .3A dropper used with a 80V heater chain, with 240V mains, would drop 160V. From this, $160V \times .3A = 48$ watts.

RECEIVERS & COMPONENTS

SPEAKER REPAIRS, Cones/Fields fitted. Clock Coils Wound. L.S. REPAIRS. Pluckley. Ashford, Kent.

MIDDLESBROUGH. Largest stocks on N.-East coast. Radio, TV components, FM Kits. Gram. Cabinets. Tape Decks. Leak Amplifiers, Valves, etc. Callers only. PALMERS, 106, Newport Road. (Phone: 3096.)

LOUDSPEAKERS

ELAC 5in. P.M. 3 ohms 9,700 gauss. Our Price 15/6, post 1/6.

AXIOM 150 Mk II Double Cone 12in., 15 watts, 15 ohms. Fully dustproof. Our Price £7.19.6, post 7/6.

PYE 10in. Portable, 3 ohms, complete with flex and plug, 50/-, cge. 7/6.

L. WILKINSON (CROYDON) LTD.

9 LANSDOWNE RD. CROYDON SURREY
Phone: CRO 1274 Cables: WELCO CROYDON

THOUSANDS OF SPARES. Transformers, Coils, Valves, Tubes cheap, from dismantled radio, television sets, 1938-1958. We may have what you need. 9in.-10in. Projection Tubes. 30/-; 12in.-14in., £3/10/-; 17in., £5. All picture tested! EF80, EF91, EB91, 3/6. Obsolete Sets our speciality. Write, phone, call: "ST. JOHN'S RADIO," 156 St. John's Hill, S.W.11. (BATTERSEA 9838.)

CALLING 9IN. TELEVISION OWNERS.—Brand new factory fresh 9in. Ferranti Tubes, originally £14/10/-, will replace Mazda, Brimar, G.E.C., etc., £4/10/- each; 6 months' guarantee. TOMLINS, 127, Brockley Rise, Forest Hill, S.E.23.

ALUMINIUM CHASSIS, 5 different types, 720 standard sizes. Write for catalogue. 25, Leach St., Prestwich, Manchester.

Collaro 4 Speed Single Players, £6.15.0. P. & P. 3/6.
Collaro Conquest 4 Speed Autochangers, £7.19.6. P. & P. 3/6.
Garrard 4 Speed Autochangers, £9.17.6. P. & P. 3/6.
3 watt Amplifiers, £3.12.6; 5 watt with full tone control, £5.5.0; 12 watt P.P. HI-FI with built-in pre-amp., £14.10.0. P. & P. 2/6.
Isolating Transformers, 230 v. primary, 250 v. secondary at 80 mA. 6.3 v. 1.5 a., 10/-; P. & P. 2/-.
Vacuum Impregnated Transformers, 250-0-250 v. 80 mA., 4 v. 4 a., 6.3 v. 3.5 a., 0-4.5 v. 2 a., 6.3 v. 1 a. ES screen chassis mounting, 22/6. P. & P. 2/6.
Batteries (Charging Transformers, 2, 6, 12v. 1amp., 10/6; 2amp. 13/6; 4amp. 17/6. P. & P. 2/-.
Phillips Type Transformers, 250-0-250 v. 80 mA., 6.3 v. 3 a., 7/6. P. & P. 2/-, Chokes, 20 h., 100 mA., 3/-, P. & P. 1/6.
Output Transformers with Humbuck and feed back windings, 2/6. P. & P. 1/6.
Battery Charging Rectifiers, 12 v. D.C. Output Maximum 1 a., 7/6; 2 a., 10/-; 4 a., 20/-; 6 a., 27/-, P. & P. 1/3.
Miniature Pots, Log, 250 k., 500 k., 1 meg., 1.5, 4/6; ditto, WS, 5/6. P. & P. 6d.
Pots, WW 10 ohm, 50 ohm, 100 ohm, 1 k., 2 k., 2.5 k., 3 k., 5 k., 10 k., 25 k., 50 k., 1/6. P. & P. 6d.
Condensators, 2 µF. 800 v. D.C. wkg. chassis mounting, 3/6; 4+2 mfd. 350 v. D.C. wkg. 4/-; 2 mfd. 350 v. D.C. wkg., 1/6. P. & P. 6d.
Terms C.W.O., or C.O.D. over £2. Immediate Despatch.

ELECTROSURE

118, Fore Street, Exeter. Phone: 56667.

RATES: 5/6 per line or part thereof, average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless," Tower House, Southampton St., Strand, London, W.C.2.

RECEIVERS & COMPONENTS

(Continued)

SUPERHET PERFORMANCE WITH ONLY ONE TRANSISTOR

COMPLETE KIT FOR MEDIUM WAVE RECEIVER ... 45/-
EXTRA ITEMS FOR LONG WAVE 6/8 CIRCUIT & ASSEMBLY GEN. ... 3/-
Will Receive Home and Continental Stations and is Selective. Suitable as Radio Feeder Unit.

"WEYRAD" TRANSISTOR RECEIVER

COMPLETE KIT—LONG & MEDIUM-WAVE. PUSH-PULL O.P. ... £9/12/6
CONSTRUCTOR'S BOOKLET ... 2/-
Send S.A.E. for Shopping List

WESTHAM RADIO SUPPLIES
Rear of 176, Abbotsbury Road
WEYMOUTH, DORSET

TRANSISTORS, R.F. type 9-6. Acos 39-1 stickmike, 49/6, list 5 gns.; Walkie Talkie 38, new, tested, 45/-; 1988 VHF RX + TV £6/10/-; 26 Converter, new, 15/-; Vibro Pack, 6v. with OZ4, 250v. at 100 ma., 17/6; Camera Control, type 35-20, Timer, 25/- (p.p. extra). CARTER (RADIO), 347, Ladypool Rd., Birmingham, 12.

RESISTORS.—100 new, wire ended, assorted, all types 7/6 box, post free. COOK'S OF BEDFORD, 29, St. Mary's St., Bedford.

H.M.V. 15IN., English Electric 15in. Ultra, etc. Televisions, not working, originally £175 each. £5/10/- TOMLINS, 127, Brockley Rise, Forest Hill, S.E.23.

AMERICAN 5in. P.M. LOUD SPEAKERS.—Hi-flux magnets in circular metal cases, 6in. dia. x 3in. ideal for car radio, 20/- (3/6). 75FI, PLYWOOD MASTS, —9in. dia. with all fittings take any aerial strain, £35 (cost). MOBILE DISC RECORDERS for 12 v. input precision B.B.C. type, complete units in three portable cases, £25 (20/-). THERMIONIC SOUND MIRROR TAPE RECORDERS, as new, £20 (10/-). WIDE BAND AERIAL ALPHAS, six outputs from one aerial rack mounting, mains input, £9/10 (10/-). 25 foot SELF-SUPPORTING TRIPOD BASE AERIAL MASTS, plywood tube, 2in. to 4in. dia., complete, 95/- (10/-). MILLIAMETERS, 24in. dia., M. 0/7, 20/- (2/6). 0/30 and 0/100, 12/6 (2/6). AR-88 PATTERN CABINETS, 70/- (10/-). 6FI, BENDIX TRANSMITTER CABINETS, £6 (20/-). 6FI, PLESSEY ditto, £5 (20/-). P.O. R.A.C.K.S.—Heavy de luxe 3ft. high, 50 (10/-). 6ft. 6in. high, 100/- (15/-). CHOKES, —Wooden 20 H. 400 mA., 25/- (5/-). TBS TRANSMITTERS, 60/80.—New, less valves and crystal, 80/- (30/-). TBS RECEIVERS, —New, less valves, 90/- (30/-). 30F. ONE-PIECE WOOD POLES—4in. dia. hollow, light, strong, 35/- (special). ET-4332 MODULATION DRIVER TRANSFORMERS, 15/- (3/6). 50-WATT MODULATION TRANSFORMER—Pri. and Sec. 15/15 (3/6). 65 watt, 40/- (5/-), 200 watt, 65/- (10/-).
Amounts in brackets are carriage England and Wales *includes wood case. We have lots of 'ft bits and pieces'. Send your requirements, all enquiries answered. Lists of over 1,000 different items! available.

P. HARRIS, ORGANFORD, DORSET.

RECEIVERS & COMPONENTS

(Continued)

FM-AM STEREO

Radiogram chassis-CB8

Paired output 6 watts
Plain or Stereo Records.
A hand-built quality unit
ONLY £20.

BEL SOUND PRODUCTS CO.,
Marlborough Yard, London, N.19.
ARC. 5078.

POWER IN PACKETS.—Brand new and beautifully crated with internal spring suspension. CV1397 CRTs. identical to VC97 in voltage and colour but having slightly longer persistence; crated and delivered for 11/6, repeat 11/6. Clarke's Eliminators, 240v. to 120v. at 30 mA. fully smoothed, internally soiled but O.K., 15/6 each. Brand new 5CP1 CRTs, 25/- each, delivered. Now compare prices with others. 60-yr. coils of 5-core Cable on steel drums, 22/6.—delivered. Stamp for super list of Grindstones, all sizes, i.e., 4in., 4/3, up to 16in. at 27/6. DIGGINS, 129-133, Radnor St., Hulme, Manchester. 15.

FIX IT YOURSELF AERIALS! Pre-Assembled Ready for Fixing. No "Tech. Gen." required. Loft 3EL 2A/-, Wall 5EL 32/6. Clip On 5EL 28/-, 8EL 40/-, Indoor B.B.C./I.T.V., 16/6. Dipole +6EL + Chimney Kit, 73/-, Double 5 array, 72/6. Fringe Area Super Low Loss Co-axial, 1/3. Standard Low Loss, 7d. 7d. Diplexers 12/6. BRAYHEAD TURRET TUNER for any area. Will convert over 600 models, 137/6. Plug In Adaptor, 3/- extra. State model + Channel. ALL ITEMS CARRIAGE PAID C.W.O. S.A.E. for Aerial List. Enquiries invited for full range of T.V., Radio, Valves and Spares.
HASE SUPPLIES, 34, PRINCE ST., BRISTOL (Dept. P.W.).

WE HAVE large stocks of pretty well all TV Components, Valves and Tubes at much lower than standard prices, especially for old type receivers. CINTRISS LIMITED, Birmingham, 1.

ANNAKIN

The Fame 12in. Speaker. Please see previous adverts., or send for free leaflet. Only £9 each. Carriage paid in U.K.

Receiver No. 1. F9/110DB/226. U.S.A. made. Centimetre unit having two T2A13 Klavions, 1-6S1, 70T, 3-6AK5, 2-6J6, 1-1N21. Midret relay inchoing relay. Waveguides. New. Only 50/- ea., carr. 5/-.

Receiver R3683 with 14 valves and 50 cycle Power Pack. New. 55/- ea., carr. 7/6.

Dinghy Distress Unit T3180. With CV93 valve, dipole, battery case, 7ft. 5in. mast (collapsible). Best battery, 6/- ea., post 1/3.

Nife Cells, 1.2 v. 5 AH. New. 3/-, post 1/3.

Block Condensers, 1 mfd., 600 v., 6d., post 9d., 10 mfd., 250 v., 2/- ea., post 1/6.

1 mfd., 5 kV., 1/- ea., 1/9 post.

Electromagnetic Mikes. Used. 2/6 ea., post 9d.

Carbon Mikes. Metal case. New. 3/-, post 1/6.

Single Phone and headband. 2/-, post 1/3.

Disc Magnets, 1in. D. x 1in. 2/6 doz., post 6d.

New APN-13 Spares
Relay 8,000 ohm, 1 M., 3/6, post 10d., 30 Mo. IPT, 6d., L.T. hash Chokes, 6d., AF transformers 35T-140T, 6d., 7+15 ohm W.W. 20 W., 1/-, 15+29 ohm W.W. 20 W., 1/-, AF transt., 1040T-3220T, 1/-, Trimmer tool, 6d., Allen Key No. 8, 3d.

Stamped addressed envelope for list. Mainland only. No Export.

25 ASHFIELD PLACE, OTLEY, YORKS

SOUND RECORDING

TAPE/DISC/TAPE TRANSFER. 1,800 ft. L.P. new Tape. 37/6. UNIMIXER Units for quality work. SOUND NEWS, 10, Clifford St., London, W.1.

WANTED

A PROMPT CASH OFFER for your surplus Brand New Valves, Speakers, Components, Test Instruments, etc. R.H.S., 155, Swan Arcade, Bradford, 1.

URGENTLY REQUIRED, new Radio, Television or Industrial Valves. Also old and obsolete types. Cash prices offered for any quantity. Write, call or phone: MIT 6202, 201, Streatham Rd., Mitcham, Surrey.

ALL TYPES of Valves wanted. PL81, ECL80, EY51, U25, PCP80, PZ30, U801, etc., etc., best cash price by return. STAN WILLETTTS, 43, Spon, Lane, West Bromwich, Staffs. (Tel.: WES 2392.)

URGENTLY NEEDED as gift. Radio. WAR DISABLED, Red Cross, Caer-narvon.

WANTED VALVES

All types for prompt cash. Must be new. State quantity.

WILLIAM CARVIS LTD.
103, North Street, Leeds, 7.

FOR SALE

A.C. METER, 4 1/2 x 4 1/2, 5in. scale, 6" calibrated scales, 1ma, F.S.D. 100 ohms, with circuit, £47/7.6. A.C.2 Meter, 3 1/2 diameter, as above, calibrated, ohms and volts, £22/2/6. Suitable circuits included with all meters, which are tested with sub-standard. MACLACHLAN & CO., 11, Riverside Drive, Stirling.

THE TAPE KING scoops again with a new low-priced tape bargain! 7in. L.P. 1,800ft. "Agfa" (list 50/-) 32/6, p. and p. 1/6; 5 1/2in. L.P. "Agfa" (list 35/-), 22/6, p. and p. 1/6; 3in. L.P. "Agfa" (list 9/6) 5/6, p. and p. 6d. Also 7in. L.P. by various leading British and Continental makers at up to 30% cheaper than list. 7in. 1,200ft. "Ferrotape" (X.M.O.S.) (list 45/-), 25/-, p. and p. 1/6. Secondhand latest Philips AG8108G (list 62 gns.) 49 gns., or terms; secondhand Grundig TK9, 37 gns., or terms; secondhand Quad II, complete, £32/10/-, or terms. 20 secondhand Recorders, Amplifiers, Pickups, etc. Send for list. E. C. F. KINGSLEY & CO., "Always first for tape," 132, Tottenham Court Rd. (corner of Warren St.) London, W.1. (EUS 6500.)

CABINETS, EQUIPMENT & SPEAKERS

Write for CATALOGUE.
A. L. STAMFORD
-Dept. G29,
84 Weymouth Terrace,
London, E.2.



FOR SALE (Continued)

ASTOUNDING VALUE.—9in. Televisions 45/-, 12in. Televisions 70/-, 14in. £9/10/-, 15in. £5/10/-, 17in. £14. Complete but not guaranteed working, as received in part exchange. TOMLINS, 127, Brockley Rise, Forest Hill, London, S.E.23. All famous makes available, carriage 7/6.

AMERICAN MAGAZINES.—Year's subscription, "Popular Electronics," 35/6; "Radio Electronics," 35/6; "Audio," 35/-, Specimens, 4/- each. Full catalogue free. WILLEN LTD. (Dept. 40), 9, Drapers Gdns., London, E.C.2.

MULLARD 510, Osram 912, Mains Trans., fully shrouded, 39/6, p. free; U/Linear output trans. to match; Mullard 36/6, Osram (12w.), 49/6; Mullard 3-3, Mains Trans., 24/6; Resistors, individually carded, 1w. 4d., 1/2w. 5d., 1w. 7d., 5w. 1/2; Decamatic ECL82 Amplifiers with speakers, knobs and circuit, £42/6; Collaro 3-speed single Players with "T" turnover cartridge, £5/19/6; Service Sheets, 3/3, S.A.E. enquiries, please LINE ELECTRIC, 76a, Gladstone St., Hyson Green, Nottingham.

100 BAYS of brand new adjustable steel Shelving, 72in. high x 34in. wide x 12in. deep; stove enamelled, dark green; sent unassembled; 6-shelf Bay, £3/15/-; sample delivered free; quantity discounts. N. C. BROWN, LTD., Eagle Steelworks, Heywood, Lancs. (Tel.: 69018.)

SATISFACTION ASSURED.—12in. Televisions £9/10/-, 14in. £16, 17in. £19/10/-. Write for quotation, stating requirements. We guarantee satisfaction. TOMLINS, 127, Brockley Rise, Forest Hill, S.E.23.

SCANNING COILS, 15 9. Wide angle 90 deg. 38mm. Low impedance. P. & P. 1/3.

FOCUS MAGNET, 9/9. Brand New. 38mm. Incorporating picture shift control. P. & P. 1/3.

CLYVERN PRESET POTENTIOMETERS 9/9. Brand New. 200 ohms 10 K. & 20 K. P. & P. 6d.

DUKE & CO. (Dept. D.7)

621-3, Romford Road, Manor Park, E.12. Tel.: HF 6001-3

TEST EQUIPMENT BARGAINS.—45A and 45B Taylor Valve Testers, with modern adaptors and valve charts, £8 and £11 respectively. American Genometer, model TV50 Signal Generator (110v. A.C.), £10. 77A Taylor Multimeter, 20,000 o.p.v., in new condition, £9. 88A Taylor Universal Multimeter, 20,000 o.p.v., in new condition, £12/10/-. G.E.C. Frequency Meter (0-75 kc/s), £6. 260A Taylor TV Wobbulator combined with scope, practically new, £18/10/-. 120A Taylor Multimeter, £4/10/-. All instruments in perfect working condition, supplied with instruction manuals. E. STRAUSS, 9, Keble Rd., Maidenhead, Berkshire.

SUB-MINIATURE SOLDERING IRONS

New Ultra Lightweight—Designed for all Radio work, Essential for Transistors. Printed Circuits, etc. Weight 1 oz. & 9 walt, 10/6 post free. Or with isolating transformer for A.C. Mains, 13/6, plus 1/- postage.

KENNETT & CO.
23 LEYLANDS GROVE, BRADFORD 9

FOR SALE (Continued)

SPECIAL OFFER.—Famous Pye Invicta 12in., 13 channel, Televisions (without tubes or valves), £2/15/-; otherwise complete. Each one with walnut cabinet, and Pye 13-channel turret. TOMLINS, 127, Brockley Rise, Forest Hill, S.E.23.

CRYSTALS, brand new, 6815 k/cs, 2 pin, 2/9 post free. WALLACE, 18, Caledonian Cres., Annan, Dumfriesshire.

EDUCATIONAL

INCORPORATED Practical Radio Engineers home study courses of radio and TV engineering are recognised by the trade as outstanding and authoritative. Moderate fees to a limited number of students only. Syllabus of Instructional Text is free. The "Practical Radio Engineer" journal, sample copy 2/-, 6,000 Alignment Peaks for Superhets, 5/9. Membership and Entry Conditions booklet, 1/-, all post free from the SECRETARY, I.P.R.E., 20, Fairfield Road, London, N.8.

WIRELESS. See the world as a Radio Officer in the Merchant Navy; short training period; low fees; scholarships, etc., available. Boarding and Day students. Stamp for prospectus. WIRELESS COLLEGE, Colwyn Bay.

BRADFORD INSTITUTE OF TECHNOLOGY

Principal : E. G. Edwards, Ph.D., B.Sc., F.R.C.

A Sandwich Course for —
DIPLOMA IN TECHNOLOGY
IN
ELECTRICAL ENGINEERING
will commence
in January, 1960.

(Arrangements will be made to accept students for industrial training in September, 1959).

Further details and application forms for the course may be obtained from the Registrar, Bradford Institute of Technology, Bradford, 7. Telephone No. 28637.

EASY MATHEMATICS COURSE for Radio/TV. Write: TUTORIALS, 200, Buchanan St., Glasgow, C.1.

AT LAST—at a reasonable cost—quality Hi-Fi in your home by building it yourself under our new system. Free brochure from: Dept. PW2, RADIOSTRUCTOR, 46, Market Place, Reading, Berks.

LEARN RADIO AND ELECTRONICS the new practical way! Hosts of absorbing experiments carried out at home under expert guidance to teach you radio in a new, enjoyable and interesting way. Construction, servicing and fault-finding on equipment made easy for the first time! No previous experience needed. No mathematics used. Free brochure from: Dept. PW11, RADIO-STRUCTOR, 46, Market Place, Reading, Berks.

II+ EXAMINATION

Time is vital to your child. Write NOW for FREE 24-page GUIDE and Test stating age of child to (Dept. M.8),
MERCER'S
CORRESPONDENCE COLLEGE,
69 Wimpole Street, London, W.1

(Continued overleaf)

SITUATIONS VACANT

Following the recent Government White Paper we are proceeding with the development of **BLUE STREAK** (The British Long-range Ballistic Missile)

Expansion is demanding additional personnel for this absorbing and vital project. Immediate vacancies exist for:—

ELECTRICAL FITTERS

Applicants must have experience of assembling and wiring electronic equipment of a wide and varied nature, coupled with the ability to work to electronic circuit diagrams.

ELECTRONIC WIREMEN

Experience of assembly work and wiring to point-to-point wiring diagrams is essential.

TRANSFORMERS AND ARMATURE WINDERS

Preference will be given to applicants who have experience of windings of a small nature consistent with the radio trade.

INSTRUMENT MAKERS (ELECTRICAL)

Applicants must be capable of calibrating, adjusting and repairing electrical measuring instruments, and also have the ability to check, build, and calibrate electronic test gear.

COIL WINDERS

These positions cover a wide and interesting field and are for our Hatfield establishment, situated 18 miles from Central London in the Hertfordshire countryside.

Single accommodation can easily be arranged.

For further particulars or an Application Form please write to:—



The Personnel Manager (REF. 303)

DE HAVILLAND PROPELLERS, LTD.

HATFIELD, HERTS

CITY AND GUILDS (Electrical, etc.) on "No pass—no fee" terms. Over 95% successes. For details of Electrical Engineering, Applied Electronics, Automation, etc., send for our 148-page handbook, free and post free. B.I.E.T. (Dept. 242a), 29, Wright's Lane, London, W.8.

A.M.I.Mech.E., A.M.Brit.I.R.E., City and Guilds, G.C.E., etc., bring high pay and security. "No pass—no fee" terms. Over 95% successes. For details of exams and courses in all branches of Engineering, Building, Electronics, etc., write for 148-page handbook, free. B.I.E.T. (Dept. 242B), London, W.8.

RADIO/TELEVISION SERVICEMAN required in Nigeria to service domestic radio/television receivers and tape recorders sold by a large retail organisation. Must be capable of controlling a workshop and supervising and training local mechanics. Contract of 24 months at a salary of £1,250 p.a. with possibility of further contracts. Free passages, free fully-furnished accommodation and family allowances with gratuity on satisfactory completion of contract.

Apply stating age, qualifications and experience to: Box 18, c/o PRACTICAL WIRELESS.

T.V AND RADIO, A.M.Brit.I.R.E., City and Guilds, R.T.E.B., Cert., etc. on "No pass—no fee" terms. Over 95% successes. For details of Exams and Courses (including practical apparatus) in all branches of radio, T/V and Electronics, write for 148-page handbook, free. B.I.E.T. (Dept. 242G), 29, Wright's Lane, London, W.8.

PUBLIC APPOINTMENTS

RADIO TECHNICIANS (METEOROLOGICAL) Meteorological Office. Qualifications: Basic knowledge of radio and radar and experience in maintenance/operation of radar equipment including oscilloscopes. Successful applicants serve in United Kingdom and overseas. Commencing London salary £635 at age 25 or over rising annually to £740 subject to deductions for each year below age 25, provincial salary £30 to £40 lower. Overtime, night duty allowance, etc. Applications should be sent to Meteorological Office (M.O. 10 R/M/T.), Victory House, London, W.C.2.

Telecommunications

CAMBRIDGE ENGLAND



require

TESTERS

at

HAVERHILL in SUFFOLK

The Company is engaged in manufacturing a wide range of electronic equipments.

Applicants should have had a minimum of three years' practical experience in industry or have served in H.M. Forces as Wireless/Radar mechanics.

The Factory is a modern one in a rapidly expanding market town. HOUSES are available for suitable applicants.

Applications, giving full particulars of past experience, should be made in writing to:— THE PERSONNEL MANAGER,

PYE TELECOMMUNICATIONS LTD.
Newmarket Road, Cambridge

SERVICE SHEETS

SERVICE SHEETS, Radio/TV for sale from 1/- each. List free. J. PALMER, 32, Neasden Lane, N.W.10.

TELEVISION SERVICE SHEETS.—Over 100 Sheets covering 330 popular models, 18/6, post free. Send for full details. All types of Service Sheets for sale and hire. Radio, Television, Electronics Books, Radio Servicing, 4/-; Television Servicing, 5/-. List free. HAMILTON RADIO, BCM/DATA2, London, W.C.1.

SERVICE SHEETS.—We have the largest stock of Radio and T.V. Service Sheets in the country for sale at 4/- each. Why tolerate delay in obtaining Service Sheets when we will despatch by return? Also Fault-finders, 2/- each. List 1/-; s.a.e. with enquiries, please. S.P. DISTRIBUTORS, 11, Old Bond St., London, W.1.

SERVICE SHEETS

RADIO and Television

Over 100,000. S.A.E for List.

JOHN GILBERT RADIO,

20, Extension

Shepherds Bush Market, London, W.12

SHE 3052

SERVICE SHEETS for sale, TV 4/-, Radio 3/-; immediate delivery. S.A.E. with inquiry. SULTAN RADIO, 23b, Albert St., Tunbridge Wells, Kent.

SERVICE SHEETS, Radio, T.V. 5,000 models. Lists 1/-. S.A.E. enquiries. TELRAY, 11, Maudland Bk., Preston.

SERVICE SHEETS AND MANUALS for sale from 1/- ea.; Radio and Television List, 1/-; s.a.e. with enquiries, please. GLOBE SUPPLIES, BCM/Electrique, London, W.C.1.

MISCELLANEOUS

MAKING YOUR OWN TELESCOPES, Enlargers, Projectors, Viewers, Microscopes, Episcopes, etc. then our booklets "How to Use Ex-Gov Lenses and Prisms" Nos. 1 and 2 at 2/6 ea., will show you easily and quickly how to achieve the finest possible results at lowest possible cost. The most comprehensive lists of optical and scientific equipment in the British Isles is free for s.a.e. H. W. ENGLISH, Rayleigh Rd., Hutton, Brentwood, Essex.

AUDIOPHILES

Building for Hi-Fi? Then this is for you. Small compact F.M. front end, 85-102 mc/s. output 10.7 mc/s. Tucks in anywhere. Highly sensitive. Single valve (ECC85). Price including circuit and data, but excluding valve, £2/12/3, plus 2/- postage. Delivery ex stock.

(Department E/2), **ROTOPONS LTD.,** 54, Beddington Lane, Croydon, Surrey

New Hi-Fi Publications

- JASON VARIABLE TUNERS 2s. 6d.
- MERCURY SWITCHED TUNER 2s. 0d.
- MULLARD AMPLIFIER MANUAL 8s. 6d.
- MULLARD TAPE PRE-AMP. C 2s. 6d.
- QUALITY AMPLIFIERS B designs 4s. 6d.

All components in stock.

Separate price lists available on request to **J. T. FILMER** 82, DARTFORD ROAD, DARTFORD, KENT.

Tel. Dartford 4057.

CECO

THE NEW IDEA in SOLDERING IRONS



QUICKLY HEATS— NEVER OVERHEATS

Thermostatically controlled, the Ceco soldering iron is maintained within -15°C. of the temperature set by simple Allen-key adjustment. With no overheating, elements have a far longer life, there is no oxidation, or alloying, and the bit never needs filing. Rated at 70 watts, the element quickly replaces lost heat, heats up from cold in 1 1/2 minutes. Spares are quickly obtainable and interchangeable. Insulation tested to 1,000 volts, all components are guaranteed for 3 months. And the price is only 79/6. For quick, professional soldering on the most intricate work, you need a CECO instrument soldering iron, made for the electronics industry—now available to you.

Free literature from

CARDROSS ENGINEERING CO. LTD.

Woodyard Road, Dumbarton, Scotland



TRANSISTOR

AUDIO AMPLIFIERS

250 mW Class B push-pull using GET114 transistors, operating from a 6V supply. Class B single-ended push-pull (Transformerless) using GET114 transistors, operating from a 9V supply.

500 mW Class B push-pull using GET114 transistors operating from a 6V supply. Class B single-ended push-pull (transformerless) using GET114 transistors, operating from a 9V supply.

1 W Class B push-pull using GET114 transistors, operating from a 6V supply. Class B single-ended push-pull (transformerless) using GET114 transistors, operating from a 12V supply.

2 W Class B push-pull using GET116 transistors, operating from a 12V supply.

3 W Class B single-ended push-pull (transformerless) using GET115 transistors (mounted on 3" x 3" fins) operating from a 12V supply.

These are a selection from the range of audio amplifier circuits using G.E.C. transistors. For details of any of these circuits or information on the wide range of G.E.C. transistors, please write to :

G.E.C. SEMICONDUCTOR DIVISION

School Street, Hazel Grove,

STOCKPORT, CHESHIRE.

FIRST-CLASS RADIO COURSES . . .

GET A CERTIFICATE !

QUALIFY AT HOME—IN SPARE TIME

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure your professional qualification. Prepare for YOUR share in the post-war boom in Radio. Let us show you how !

—FREE GUIDE—

The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success-compelling qualifications as A.M.Brit.I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs, Exams, Gen. Cert. of Educ., London B.Sc. (Eng.), A. M. I. P. E., A.M.I.Mech.E., Draughtsmanship (all branches) etc., together with particulars of our remarkable Guarantee of **SUCCESS OR NO FEE**

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.


FOUNDED 1885—OVER 150,000 SUCCESSES.

NATIONAL INSTITUTE OF ENGINEERING

(Dept. 461), 148, HOLBORN, LONDON, E.C.1.
S. Africa : P.O. Box 8417, Jo'burg.
Australia : P.O. Box 4570, Melbourne

Build your own TAPE RECORDER "ASPDEN"

Tape Deck and Amplifier Kits

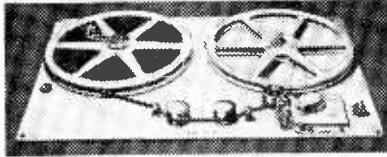

TAPE DECKS. 2-speed, twin track, easy to assemble kits with finest motor. Ferroxcube heads and full instructions. Model 582 for 5in. spools, kit £8.5.0. Model 782 for 7in. spools, kit £9.5.0. Either model assembled and tested, 30/- extra.

AMPLIFIER kit, 2½ watt, record/replay, 2 recording positions, neon indicator, etc., £5.18.0. Power Pack kit for above, £2.18.6 (both without valves). Carr. and packing extra.

Mr. R. White of Omagh, N. Ireland, writes: "The performance of the recorder is very good, and I recommend it to all those who wish to get first class performance at approx. half the cost."

NEW:—"STANLEY" Tape Position Indicator, large clock type, easy to fit, £2.5.0.

Send STAMP for full particulars to:—
W. S. ASPDEN Stanley Works, Clevedon Road, Blackpool, Lancs.

EXPRESS ELECTRONICS ROSEDEEN LABORATORIES KINGSWOOD WAY, SELSDON, SURREY

VALVES NEW, TESTED AND GUARANTEED				
1AC8 9/-	6BA6 7/-	12K7GT 6/9	EB91 5/8	N18 8/-
1C1 7/6	6BE6 7/-	12K8GT 12/6	EBC41 10/-	N19 8/-
1C2 9/-	6BR7 10/8	12Q7GT 7/6	EBF80 9/6	PC84 9/-
1C3 8/6	6BW6 7/6	16A5 7/-	ECC81 7/6	PCF80 9/-
1F1 8/6	6BW7 7/-	25A6G 10/6	ECC82 7/6	PCF82 10/6
1F3 7/6	6C10 9/-	25L6GT 7/6	ECC83 7/6	PL38 22/6
1FD1 8/6	6D2 6/6	25Z4G 9/-	ECC84 9/6	PL81 13/6
1FD9 7/6	6P12 5/6	35L6GT 9/-	ECF80 10/6	PL82 9/-
1L4 6/6	6J7GT 8/6	35W4 8/6	ECF82 10/6	PY81 8/6
1P1 8/6	6K7G 2/6	35Z4GT 8/-	ECH42 9/-	PY82 7/6
1P10 7/6	6K7GT 5/6	5763 10/6	ECH81 10/6	U52 6/6
1P11 8/-	6K8G 7/6	DAP91 7/6	ECL80 11/6	U76 7/6
1R5 7/6	6L6G 10/6	DAP96 8/6	EF41 9/-	U78 7/-
1R5 7/6	6Q7GT 3/6	DP91 7/6	EF80 8/6	UBC41 8/6
1T4 7/6	6N1GT 7/6	DP96 8/6	EF86 12/-	UCH42 9/6
1U5 6/-	6SN7GT 8/-	DH76 7/6	EP91 6/6	UF41 8/6
3A5 10/8	6Y6G 7/6	DH77 7/-	EP92 5/6	UL41 10/-
3Q4 8/-	6X4 7/-	DH142 8/6	EL38 22/6	UY41 7/6
3R4 7/6	6X5GT 8/-	DH150 10/-	EL41 10/-	W76 6/6
3V3 8/-	6D3 6/6	DK91 7/6	EL84 8/6	W142 8/6
5U4G 6/6	12A6H 10/6	DK92 9/-	EV41 10/6	X17 7/6
5Z4G 9/6	12A76 8/6	DK96 8/6	EZ40 7/6	X18 9/-
6AK6 6/6	12A77 7/6	DL82 7/6	EZ80 8/-	X142 9/-
6AL5 5/6	12A7U 7/6	DL94 8/6	EZ81 8/-	X150 9/-
6AM6 6/6	12AX7 7/6	DL96 8/6	KT65 11/6	Z77 7/6
6AT6 7/-	12J7GT 10/-	EABCB80 8/6	N17 7/6	ZD17 6/6

VOLUME CONTROLS MIDGET SIZE LONG SPINDLE h.p. switch, 3/9; S.P., 3/3; Less switch, 2/6. Values 10K to 2M. Pre set 2/6.

MATCHED PAIRS	
EL84 21/-, 6V6G 17/-, KT66 27/6, 6BW6 18/- per pair.	Push Pull O.P.
Transformers for above 3-15Ω 14/6, 12" P.M. Speakers 3Ω 24/6.	
SETS OF VALVES	
DK91, DP91, DAP91, DL92 or DL94.....	27/6 1/2
DK96, DP96, DAP96, DL96.....	35/-
1C3, 1F1, 1FD1, 1P1.....	35/-
1R5, 1T4, 1R5, 3R4 or 3V4.....	27/6
6K8, 6K7, 6Q7, 6V6, 5Z4G or 6X5G.....	27/6

Postage and packing 6d. Over £1 post free. C.O.D. 2/6.

ALFRED PADGETT


40, MEADOW LANE, LEEDS, 11
Tel.: CLECKHEATON 2886

Canadian Telephone Sets, Brand New Portable Telephones, complete with hand generator, ringing device, Morse key, buzzer lamp, etc., less phones, 12/6. carr. 5/-, Two Sets, 30/-, carr. free.
Tube Unit. Complete with 8 EF50 valves. VCR37 tube, etc., 25/-, carr. 7/6.
T.V. Sets. In good working order. Tubes not Boosted. Elco, Pye, Bush, Ultra, Ferguson, 12in. £6/10/-, 14in. £10/10/-. These sets will tune to all B.B.C. stations. Carriage on set (tube sent in separate carton), 17/-.
Other Sets. B.B.C. and I.T.V. for Sale, 12-14in. T.V. Chassis, 12 INCH TUBE Model. Complete. Less valves and tube, 15/-, carr. 5/-.
Brand New 6in. C.R.T. Tube CV1397. 6/6, post 3/6.
New Co-ax Cable. Top Grade, multi-strand, 6d. per yard, post free. Any length cut.
New American Motor. 27 volts in. out. 285 volts at 75 mills. 6/6, post 3/-.
Small Mag-Slip Repeater Motor. 1/6, post 2/6.

SPECIAL OFFER!
Brand New, Boxed. All U.S.A., J.A.N. All Post Free.
6KTG. 2/6; 6K7M. 4/6; 6J7M. 4/-; 6J5M. 4/6; 6K8C. 6/-; 6AG5. 2/6; 6C4. 2/6; 6J6. 2/6; 6ACTM. 4/6; 6H6M. 2/-; 6AKS. 3/-; 954. 1/9; 955. 3/-; 12S7M. 2/-; 12SH7M. 2/-; 12H6M. 1/6; 12A6M. 5/-; 9001. 9004. 9006. all at 1/3.

EQUAL TO NEW T.V. VALVES
3 Months' Guarantee. Post Free.
Marconi Z77, X78, D77, DH77, Z63, all at 3/-, Marconi B36, KT33C, KT36, U35, U31, all at 5/-, Mazda 10F1, 20D1, 6F1, 6P15, 10P13, 20F2, 6L18, 6P25, 20P1, all at 5/-, Mullard EF80, EF91, EB91, all at 3/-, ECL80, P230, 5/-.

THE WAVEMASTER TRANSISTOR PORTABLE

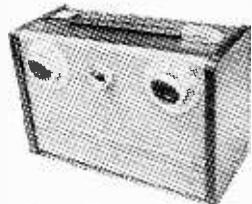

'AN OLYMPIC MINISTER
Pick of the World's Stations at your finger-tips.
Long and Medium Wavebands. Comprehensive assembly data and Components Lists, 1/6.
Complete Receivers Available.
OLYMPIC RADIO COMPONENTS, LTD.
224, Hornsey Road, Holloway, N.7.

ASTRAL RADIO PRODUCTS

COIL PACKS. L/M/S. 36/-, post 1/-
HOME RADIO. 32-page illustrated booklet. Simple wiring instructions for Crystal Set, 1, 2, 3 Valves. 2/-, post 3d.
TRF COILS. 7/-, pr., post 6d.
DUAL WAVE. HF Coil with REACTION. Specified for 'Summer All Dry Portable', 'A.C. Double Triode 1', etc., 4/6, post 3d.
IFT'S Miniature. 1" x 1 1/2" x 2 1/2" in cans. Extra high 'Q'. Special offer, 9/-, pr., post 6d.
Crystal Set Coils. L & M.W. 2/6, post 3d.
82 Centurion Road, Brighton

WIRING ACCESSORIES

Return of Post Service. Lowest possible prices consistent with high quality. Money back guarantee.

PVC Cable Flat Twin Twin with E. 3 Core			
1.044	£2. 1. 8	£2.15. 1	£2.19. 4
3.029	£2.14. 2	£3. 8. 11	£3.19. 0
3.036	£3.16. 5	£4.10. 9	£5.10. 10
7.029	£4.19. 11	£6. 1. 11	£6.18. 3

TRS CABLE			
1.044	£2. 3. 5	£2.13. 11	£3. 0. 10
3.029	£2.15. 9	£3. 6. 10	£4. 5. 4
3.036	£3.15. 2	£4. 6. 5	£5. 8. 2
7.029	£4.13. 10	£5.18. 2	£6.16. 7

Prices per 100 yds. All sizes stocked. Supplied in 25, 50, 75 or 100 yd. lengths. 7.029 and above cut to length—no cutting charge. Carriage paid on all orders over £2. Full range of accessories available. Send for complete lists.

F. HUNT & CO.
STEPCOTE HILL, EXETER.
Phone: Exeter 56687.

1-Finger Pianist

Build your own electronic keyboard and play everything! Send for free leaflet. Guitar, cello, flute and trumpet are all easy. Write now...

C & S, 20 Maude Street, Darlington, Co. Durham.

HOME RADIO OF MITCHAM

(Dept. P), 187 LONDON ROAD, MITCHAM, SURREY. MIT 3282

Shop Hours: 9 a.m.—6.30 p.m. Wednesday 9 a.m.—1 p.m.

We are stockists for—
EDDYSTONE

short wave receivers and components.



New **JASON FMT2** F.M. Tuner. Crystal clear Hi-Fi reception at all times. Modern slide-rule scale, easy tuning, neat case. Full data book, 2/9 post paid. Complete kit with Power Unit £9.8.0.




Mullard versatile 2-valve audio pre-amplifier. Bass, Treble, Volume and selector switch. Full data book, 1/3 post paid. Complete kit £6.5.0.



Philips AG-2009 4-speed transcription record unit. Solid accurately machined turntable with speed control. Hi-Fi crystal pick-up for standard and L.P. records. Many novel features. Leaflet on request. PRICE £10, plus 2/- post.

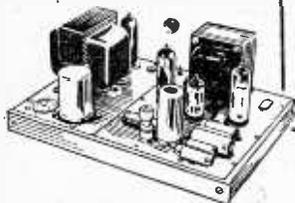BUILD YOUR OWN COMPLETE SUPER HI-FI SYSTEM FOR LESS THAN £50



The famous **MULLARD 510** main amplifier now available on printed circuit giving perfect results every time. Very easy to build and smart professional appearance. Full constructional data 1/6 Complete kit £13.12.6.

Stentorian CX3000 cross-over unit gives smooth division of output between the two speakers. PRICE 30/-, plus 1/- post.



Stentorian T359 tweeter for tingling realism and frequency response up to 17,000 c.p.s. Brings the programme to LIFE! PRICE 35/-, plus 1/- post.

Bakers (Selhurst) Stalwart 12 in. speaker. Foam suspension gives clean smooth bass response. Dust-proof, tropicalised, and precision built by craftsmen. Frequency range 40 to 13,500 cycles. PRICE £6.15.0 plus 3/6 post.



Q-MAX CHASSIS CUTTERS

1/2 in. 12/9, 3/4 in. 13/9, 1 in. 13/9, plus 1/- key.
1 in., 1 1/4 in., 1 1/2 in., all at 16/-, plus 1/4 key.
1 3/4 in. 20/6, 1 in. square 25/6, plus 1/4 key.
Please add 9d. post.

MULLARD TAPE PRE-AMPLIFIER

Type C.



The finest home constructor tape pre-amplifier kit to date. Designed by Mullard's laboratories and incorporating latest facilities and refinements and ideal for feeding into Hi-Fi amplifiers, etc. Full constructional data, 2/9 post paid. Complete kit £13.15.0.


CONDENSERS

SPECIAL OFFER of new 16 mfd. 350 v. condensers. Size 2 in. x 1 in.

ONLY 1/- each or 6 for 5/-. Please add 6d. post to order.



BATTERY SHORT WAVERS

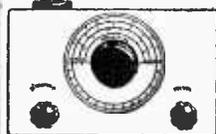

We now stock parts for the RCS short wave and personal portable battery sets.

MODEL SW1.

1 valve short wave set with coil for 20 to 40 metres. Can be increased to 2 or 3 valves and additional coils available from 10 to 400 metres. Parts for 1 valve set cost 35/-. Parts for two valve set cost 42/6.

MODEL PP2. 2 valve personal portable with rod aerial. Medium waves. All-dry battery operation. Parts cost 41/-. Data sheets on either of these sets 2/-, post paid.

MINI-7 TRANSISTOR POCKET PORTABLE

Last opportunity to obtain the parts for this 7 transistor pocket portable with 2 1/2 in. speaker at our Holiday Bargain price of **ONLY £8.17.6**. Full constructional Data with point to point diagrams, etc., 1/6, post paid.

We can also offer the following special transistor components for constructors using their own circuits: Grey plastic pocket portable case, group board to fit, ferrite aerial, R.F./Osc. coil, 3-L.F. transformers, Jackson "00" midget 2-gang, Push-pull driver and output transformer. Data. Bargain parcel TC.1. PRICE **ONLY £3.3.0**.

NEW EDDYSTONE DIAL



PRICE 58/-

A high grade dial assembly for short wave receivers, convertors, test-gear, etc. Gear driven with 110 to 1 reduction ratio. Vernier scale. Cat. No. 858. Send 6d. stamp for catalogue of Eddystone components.



The "Ariel" PORTABLE

MAY BE BUILT FOR

£7.7.0

Plus p. & p. 3/-.

BATTERIES EXTRA. H.T. 10/- (Type B126) or equivalent. L.T. 1/6 (Type AD35) or equivalent.

★ Size only 8in. x 8in. x 4½in.

★ Instruction book 1/6

BATTERY ELIMINATOR, housed in two containers which are approx. the same size as AD35 and B126 batteries. 37/6, plus 2/- p. & p. **MAY BE CONSTRUCTED.**

THE BEREC

The 'Berec' Battery Receiver for only **£4.19.6**, plus 5/- pkg. and postage, or **£1.0.0** deposit and 5 monthly payments of 19/-. This receiver is ideally suitable for use in the home or where normal electricity supply is not available, remarkable reception on both medium and short wavebands, incorporating the following latest type miniature Battery Valves: DK92, DF96, DAF96, DL96 and operates on an external B.103 Battery or equivalent. The receiver is housed in an attractive two-tone metal case. Size 11½ x 7½ x 5½in. **BATTERY EXTRA, 18/6.**



THE "MID-FI"

A NEW DESIGN 4½ WATT AMPLIFIER KIT

A new circuit for the home constructor **May Be Built For** requiring a good quality medium powered Amplifier for reproduction of Records **95/-** plus 3/- p. & p. or F.M. Broadcasts. The use of a high gain, low noise pentode (EF86) feeding the high-slope EL84 Output Valve ensures adequate output even when used in conjunction with modern low-output Pick-ups. The separate wide range, bass and treble controls give sufficient control to compensate for variations in recordings and associated equipment. For use with Loudspeakers of 3 or 15 ohms impedance. Technical Specifications: separate bass and treble controls. Valve line-up EF86, EL84, EZ80. Voltage adjustment for A.C. mains from 200-250 volt, 3 or 15 ohms impedance. Negative feedback. Size 7 x 5 x 2in., overall height 5 in. Silver hammered finished Chassis.



2-BAND TRF RECEIVER

MAY BE BUILT FOR £5.10.0 plus 3/- packing and postage. This receiver uses the latest type circuitry and supplied complete with easy to follow point-to-point wiring diagrams, suitable for use on A.C. mains 200/250 v. When constructed the Receiver is housed in an attractive walnut finished Bakelite Cabinet or, if required, Wooden Walnut Cabinet. Overall dimensions 12 x 6½ x 5½in. Instruction Books available separately. **PRICE 1/-.**

B.S.R. MONARCH UA8 4-SPEED AUTOCHANGER, £6.19.6.
COLLAR CONQUEST 4-speed AUTOCHANGER, £7.19.6.
GARRARD R.C120 MARK II 4-SPEED AUTOCHANGER, £9.19.6. Postage and Packing on the above units 5/- each item
★ **ALL ITEMS ADVERTISED CAN BE DESPATCHED FROM STOCK WITHIN 24 HOURS.**

DUVIDAL TRADING COMPANY

6-12 TUDOR PLACE, TOTTENHAM COURT RD., W.1.

Museum 0216/1043

TELETRON MINIATURE TRANSISTOR SUPERHET COIL KIT,



42/-

470 k/c.

I.F. Transformers & Osc. coil, in screening cans ¾in. x ¾in. dia. Dual wave Ferrite rod aerial 5½in. x 5/16in. dia. For the TRANSIDYNE printed circuit Superhet. ★ 6 Transistors. ★ P.P. output. ★ A.G.C. ★ Reflex. Full constructional folder, 9d. All component parts available from advertisers.

Push-pull and single ended Tape oscillator coils available for most decks at 8/6 each. Bias rejector coils and top lift Inductors. Dual range and Xtal diode coils, etc. Lists, 6d.

**THE
TELETRON CO. LTD.,
112B, Station Rd., London, E.4.**
Phone: SIL. 0836.

TRANSISTORS

Brand New & Guaranteed.

Not Surplus or Rejects.

LOOK AT THESE PRICES

RF/IF: Red/Yellow, 13/6; White Spot, 9/6. Audio: Yellow/Green, 7/- (Pair in P.P. 280 M/W matched pair, 15/-). Red Spot, 7/-.

Miniature 3-stage 4 Transistor amplifier P.P. output 280 M/W. 2-3 ohm speaker output for gram, radio, mike, baby alarm, etc. High gain, excellent quality, low consumption from small 6 v. Dry battery. Easy assembly. Full kit, matched transistors, base panel, complete instructions, 59/6. Post 1/6. Circuit diagram, layout, parts list, 2/6.

SUB.MIN. Electrolytics: 2, 4, 8, 25, 50, 100 MFD 15 V.W., 2/9 each.

MIDGET RESISTORS. ½ watt. All values 10 ohm to 12 meg. ohm. 3½d. each.

MIDGET VOLUME CONTROLS. L/S. 5K to 2 megs, 2/10 each. 5 in. P.M. speakers, new, 15/6.

MIDGET Valve/Transistor Hybrid Set. Amazing results on 3 ft. aerial. Med. wave B.B.C. and Continentals. Circuit diagram, layout, parts list, 2/-.

FULL RANGE OF NEW COMPONENTS. TRANSISTOR COILS, TRANSFORMERS, CERAMIC & MICA CAPACITORS, DIALS, TRANSISTOR BATTERIES, Etc. Send 3d. stamp for Full List.

BURLAND RADIO ACCESSORIES

Est. 1947

G3JE

G3JZ

**ANN'S PLACE, SOUTHWICK,
SUSSEX**

LYONS RADIO LTD.

Dept. M.P., 3, GOLDHAWK ROAD,
SHEPHERDS BUSH, LONDON, W.12

Telephone: SHEpherds Bush 1729

TRANSFORMER BARGAINS. Primary tapped 210/230/250 v. 50 cps. Secondary: 350/0/350 v. at 75 mA., 6.3 v. tapped at 4 v. at 3 A. and 6.3 v. at 1 A. Made by R.I., Ltd., a manufacturer's surplus stock in good unused condition. Can be mounted upright or sideways. Size 3½ x 3½ x 2½in. **PRICE ONLY 12/6**, post 1/6. **E.H.T. Type Primary 230 v. 50 cps. ; secondary 3,500 v. at 10 mA.** Overall size 8in. high x 4½in. sq. Ex-Govt., as new. **PRICE ONLY 29/6**, post 2/6.

TYGAN SPEAKER MESH.—Plastic, non-creasing, washable, fadeless and easily fitted. Any size cut. Send S.A.E. for samples and quotation for size needed.

HEADPHONES.—Type DLR3 — low resistance, fitted with metal headband, connecting cord and earpieces with felt faced rubber ear cushions. **PRICE ONLY 6/6** pair. Balanced armature types: — with canvas headband and connecting cord. Special type of construction enables them to match either high or low impedance output. Extra sensitive, can be used for transistor or crystal sets. Standard size — type DLR5. **PRICE ONLY 7/6** pair. Small light-weight type 1 Mk. 2. **PRICE ONLY 8/6** pair. **POSTAGE**, all types, 1/6.

MORE METER BARGAINS.—Moving coil types, flush panel mounting. D.C. **AMMETERS**, 2in. dia., 0/15A., 0/20A., 0/40A., all at 6/6 each. **VOLTMETER**, 2in. dia., 0/25v. D.C. at 7/6, 24in. dia. 0/100 **MICRO-AMMETERS** at 35/- or with blank scale at 25/-. All post free.

VALVES SAME DAY SERVICE

NEW! TESTED! GUARANTEED!

SETS 1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DK92, DL92, DL94 any 4 for 27/6
 1A1F96, DF96, DK96, DL96 4 for 32/6
 8K7G, 6K8G, 6Q7G, 6V6G, 6X5G or 5Y3G 5 for 27/-

1A7GT 14/6	6Q7G 8/-	30L1 9/7	EBF98 8/9	FW4500 9/6	U25 13/3
1D5 8/6	6Q7GT 9/6	35L6GT 10/-	EP421 20/6	G232 9/-	U26 12/6
1H5GT 10/-	6SL7GT 7/6	35Z4GT 6/6	ECC81 8/-	KT33C 9/-	U50 7/6
1N5GT 10/-	6SN7GT 6/6	35Z5GT 8/6	ECC82 7/6	KT41 14/6	U52 6/6
1R5 1R5	6U4GT 11/-	43 12/6	ECC83 8/-	KT63 6/6	U76 6/6
1S4 8/6	6V6G 8/-	50CD6G 26/9	ECC84 9/6	KT61 10/-	U78 6/9
1S5 7/6	6V6GT 7/6	50L6GT 9/9	ECC85 9/6	KT71 12/6	UABC80 9/-
1T4 6/3	6X4 6/9	AZ31 9/6	ECC86 11/6	KTW61 6/-	UA42 9/6
1U5 6/6	6X5G 6/-	B36 15/6	ECC87 11/6	MH4 6/-	UBC41 8/6
3A5 10/6	6X5GT 6/-	CL33 15/9	ECH21 17/6	MU14 9/-	UBF80 9/6
3Q4 8/6	7B7 8/-	CY31 14/6	ECH32 6/9	MX40 12/6	UBF89 9/6
3S4 7/6	7C8 8/-	D77 5/6	ECH45 9/6	N18 8/6	UBL21 20/6
3V4 6/-	7C8 8/-	DAC32 10/-	ECH81 8/6	N152 12/6	UC84 17/-
5V4G 6/6	7H7 8/-	DAF91 7/6	ECL80 10/6	PCC84 8/-	UCC85 9/6
5V4G 11/-	7S7 9/9	DAF96 8/6	ECL82 11/6	PCC89 17/6	UCF80 18/6
5Y3GT 7/6	7Y4 8/-	DCC90 10/6	EF39 5/6	PCF80 8/-	UCH21 20/6
5Z4G 9/6	10C1 14/6	DF33 10/-	EF41 9/6	PCF82 10/6	UCH42 9/6
8A15 5/6	10C2 17/6	DF91 8/3	EF42 11/6	PCL22 10/6	UCH81 9/6
8A15 5/6	10F1 17/6	DF96 8/8	EF80 6/6	PCL83 12/6	UCL82 13/6
8A16 6/6	10F9 10/6	DH76 6/6	EF98 11/6	PCL84 15/-	UCL83 14/3
8A16 6/6	10P13 15/9	DH77 7/3	EF99 9/6	PENA4 11/-	UF41 9/3
8A16 7/3	12A1T 8/-	DK32 14/6	EF91 6/3	PEN36C 9/6	UF89 9/6
8BA6 7/6	12A1T 7/6	DK40 16/-	EF92 5/-	PEN45 12/6	UL41 8/-
8BE6 7/6	12A1T 8/-	DK91 7/6	EF93 5/6	PEN46 9/-	UL42 21/9
8BH6 8/-	12BA6 8/-	DK92 8/6	EL38 21/6	PL36 14/-	UL44 8/6
8BJ6 7/6	12K7GT 6/6	DK96 8/6	EL41 9/-	PL38 21/6	URIC 9/6
8BW7 7/-	12K8GT 12/6	DL33 9/-	EL42 10/6	PL81 12/6	U6 10/6
8D6G 26/9	12Q7GT 6/6	DL35 12/3	EL44 8/9	PL82 8/6	UY1N 12/6
8F1 14/6	17Z3 7/6	DL92 7/6	EM30 9/6	PL83 9/6	UY21 14/-
8F6G 8/8	19AQ5 7/6	DL94 8/-	EM81 9/6	PY32 16/-	UY41 7/-
8F13 12/6	20F2 17/6	DLC6 8/6	EM84 13/6	PY80 8/-	UY85 7/6
8F14 17/6	20L1 17/6	EABC80 7/9	EY51 10/6	PY81 7/6	VP4B 9/6
8K7G 3/9	21A6 13/6	EAF42 9/6	EY96 11/6	PY82 8/6	VP41 6/6
8K7GT 6/-	25AG 11/-	EB91 5/6	EY40 8/6	PY83 8/6	W76 6/6
8K8G 6/9	25ZAG 9/-	EB33 7/-	EZ41 9/6	PZ30 17/-	W77 5/-
8L1 16/9	25Z6GT 9/6	EB41 9/6	EZ80 7/9	SP61 3/6	Z77 6/3
8L18 12/3	30C1 8/-	EBF80 8/9	EZ81 8/6		

READERS RADIO

24, COLBERG PLACE, STAMFORD HILL, LONDON, N.16. STRA. 4587

Postage 6d. per valve extra.
 Any Parcel insured Against Damage in Transit 6d. extra.
 Any C.O.D. Parcel 2/6 extra.

CABINETS & HI-FI EQUIPMENT

We can supply any Cabinet to your own specification.



"The Contemporary" £11. 15. 0

This beautifully made cabinet is oak veneered with mahogany interior and is waxed finished. Available in any shade to order at slightly extra cost. We can also supply and fit this or any cabinet with the latest Hi-Fi amplifiers, tuners, Transcription units, record changers, speakers, etc.

Write for our NEW 24-page fully illustrated catalogue of cabinets and details of our complete range of chassis, autochangers, speakers, tape decks, etc., all available on easy terms.

LEWIS RADIO

120 (PW79) Green Lanes, Palmers Green London, N.13. BOWES Park 1155/6 (Nr. The Cock Tavern)

B.B.C. - I.T.V. - F.M. AERIALS



B.B.C. (BAND 1). Telescopic loft, 19/6. External, S/D, 26/3.
I.T.V. (BAND 3). 3 Element loft array, 24/- 5 Element, 32/6. Wall mounting, 3 Element, 33/9. 5 Element, 41/3.
COMBINED B.B.C. + I.T.V. Loft 1+3 Element, 41/3. 1+5 Element, 48/9. Wall mounting, 1+3 Element, 56/3. 1+5 Element 63/9. Chimney and mast mounting units also available.
F.M. (BAND 2). Loft "H" 28/- 3 Element loft, 52/6. S/D loft, 12/6. External S/D 26/3. State channel when ordering. C.W.O. or C.O.D. P.P. 2/6. Coaxial cable, 8d. yd. Coaxial plugs, 1/3. Send 6d. stamps for illustrated lists.
K.V.A. ELECTRONICS (Dept. P.W.)
 3B, Godstone Road, Kenley Surrey

EXTRA RANGES - REDUCED PRICE

15 RANGE A.C./D.C. MULTIMETER KIT.—1,800 o.p.v. A.C. and D.C. Ranges 3, 15, 60, 150, 300, 600 v. D.C. ; 15, 60, 150, 300, 600 v. A.C. ; 6, 60, 600 mA. ; Ohms to 2 M. Kit comprises : all 15 High Stability multipliers, ready adjusted 1%. Shunts, 0-500 uA meter scaled 0-15 and 0-600, switches, pot. and Salford Instrument Rectifier. With circuit and instructions, 45/-, post free. No adjustments to make.
INSTRUMENT RECTIFIERS. New Salford Bridge type 1 mA., 7/6 ; 5 mA., 7/6. Ex-Govt. M3 Westinghouse Bridge 5-50 mA., 4/6. 250 v. 50 mA. Selenium 6/9.
PRECISION WIREWOUND RESISTORS. 1 watt, 1 to 1,000 ohms, 1%, 2/9 ; 0.2%, 4/3 ; 1 K. to 5 K., 1%, 3/3 ; 0.2%, 4/8. 5 K. to 20 K., 1%, 4/- ; 0.2%, 6/- ; 20 K. to 50 K., 1%, 4/3. Your value wound to order.
PLANET INSTRUMENT CO.
 25, DOMINION AVE., LEEDS, 7

be TRANSISTORWISE! be POCKET-WISE!



"RECO" MIDDY TRANSISTOR ONE KIT

(Med. and Long or Med. and Short Waves). Size: 4 1/2" x 3 1/2" x 1 1/2". Variable sensitivity control. High gain

Vari Q ferrite rod aerial. "Sonotone" dynamic min. earpiece. Mths. of listening pleasure from pencil battery. 37/6, p.p. 2/-.

"RECO" PUSH-PULL FIVE. M/L. Waves. Indoors or outdoors this brilliant radio with Celestion 2 1/2in. M/C spkr. brings Light, Home and Continental stations to your finger tips. 5 transistors including Mullard OC45 R.F. stage and push-pull output for tone and punch. Pale blue case with grille in red. Complete kit, £6.7.6, p.p. 2/6. Data Only 2/6. Size 6 1/2in. x 4 1/2in.

"RECO" TRANSGEN THREE KIT (Med. & Long Waves or Med. & Trawler Band). Size:



6 1/2" x 4 1/2" x 1 1/2". Entirely self contained (no external aerial req.). R.F. stage with Mullard OC 45 transistor followed by two high gain transistor stages. On test tuned in Third, Home, Light, Radio Luxembourg after dark and many others at good listening level. The receiver was tested at approx. 50 miles from nearest transmitter. Complete kit with easy build practical wiring diagrams, "Sonotone" super dynamic min. earphone with insert or bal. arm. reproducer. Pencil battery for months of listening pleasure. 75/-, p.p. 2/6.

"RECO" SUPER SPECIAL THREE KIT (Med., Long or Med. & Short Wave). Bal. arm.



reproducer which in areas of good signal reception may be mounted under red contrasting grille. Sensitivity control for distant stations. A fine kit, complete with pencil and easy build diagrams. 65/-, p.p. 2/6.

"RECO" PUSH-PULL FOUR KIT

As above, but with push-pull output stage and 2 1/2 in. moving coil speaker which fits under red contrasting grille. Gleaming pale blue polystyrene case. Size: 6 1/2in. x 4 1/2in. x 1 1/2in. Complete with data. 99/6, p.p. 2/6. Practical wiring diagrams, parts price list, circuits, 1/6 each.

AFTER SALES SERVICE

RADIO EXCHANGE CO.

27 HARPUR ST., BEDFORD Telephone 2367. Closed 1 o/c Saturdays.

EDDY'S (Nottm.) LTD.

(Dept. P.W.)

**172 ALFRETON ROAD,
NOTTINGHAM.**

ACOS CRYSTAL TURNOVER PICK-UP (2 sapphire stylis), 29/11. Post, etc., 2/6. **NIFE ACCUMULATORS MIDGET.** Single Unit size 3 x 2 1/2 in., 1/11. Post 1/6. **MORSE TAPPERS.** Plated Contacts. Adjustable Gaps, Heavy Duty. Good Quality, 3/6. Post 9d.

CONDENSERS TUBULAR WIRE END (Not Ex-Govt.). 8 mfd. 450 v., 1/9 ; 8-8 mfd. 450 v., 2/9 ; 16 mfd. 450 v., 2/9 ; 16 x 16 450 v., 3/9 ; 16 x 8 450 v., 4/- ; 32 mfd. 450 v., 3/9 ; 32 x 32 450 v., 4/-.

THROAT MIKES, 1/-. Post 6d. Can be used for electrifying musical instruments. **TRANSISTORS.** Yellow/Green Spot, 6/11. R.F. Yellow/Red Spot, 13/11. Post 4d. **TRANSISTOR CONDENSERS.** Sub Miniature. 1.6 mfd., 5 mfd., 8 mfd., 16 mfd., 25 mfd., 32 mfd., 2/6. P. & P. 6d.

NEON MAINS TESTER SCREWDRIVERS, 4/6 each. Post 6d. **GERMANIUM DIODES, 1/-** each., 10/- doz. Post 4d. **MINIMOTORS.** Lightweight, High Speed, 1 1/2 v. to 6 v., 8/6. Post 1/6.

MIDGET CONDENSERS. 25 x 25 mfd. Size 1 in., 1/3. Post 6d. **ELECTROLYTIC CONDENSERS.** Standard Can. 50 x 50 mfd. 400 v.d.c., 5/11. 100 x 200 mfd. 275 v.d.c., 9/6. Post 1/6.

JACK PLUGS. Standard Types, 1/11 each. Post 6d. **GIUITAR PICK-UP "THE PLECTRO."** Super Hi-Fi, Non-Acoustical Universal fitting. 3 x 1 1/2 in. High output. Complete with lead and plug. Full and easy instructions. 39/11. Post 1/6.

DYNAMOTORS. 200 volts D.C. to 12 volts D.C. Ideal for train sets for D.C. mains, 19/11. Post 2/6. **RECTIFIERS.** Contact cooled 250 v 60 mA., 8/6 ; RML, 4/9 ; RM3, 7/6 ; RM4, 15/6 ; RM5, 19/6. Post 1/6.

DIMMER SWITCHES. Ideal for Train Speed Regulators, 1/11. Post 6d. **All above are new and guaranteed.**

Surplus New and Guaranteed Valves.		
IA7GT	14/6	6P28 11/-
IC5GT	11/6	6SA7M 7/-
IDS	9/6	6SG7M 7/-
IHS5GT	10/6	6SH7M 7/-
INSGT	10/6	6SN7GT 7/-
IRS	7/6	6V6G 5/11
ISS	7/6	6V6GT 6/6
IT4	5/11	6XS6T 5/11
3Q5GT	9/6	6Z4/84 11/6
354	7/6	10F1 9/6
3V4	8/6	10F9 10/6
6AG5	4/6	12AH7 5/11
6B8G	2/11	12AH8 9/6
6BA6	6/-	12AT6 9/6
6B8J	7/-	25A6G 9/6
6C4	3/-	25L6G 9/6
6C6	4/6	25Z4G 8/6
6CH6	10/6	35L6GT 9/6
6D6	5/-	35W4 7/6
6F1	9/-	35Z4 7/6
6F6MET	7/6	42 42 7/6
6F13	9/-	80 6/6
6F15	9/-	90AV 7/6
6F33	6/6	807(B) 3/9
6H6MET	2/6	807(USA)
6J5G	2/11	5/6
6J5GT	3/11	1/6
6J5MET	4/6	955 3/11
6K7	2/6	956 2/11
6K8G	6/11	9001 4/6
		9004 4/-
		9006 4/-
		AZ1 12/6
		AZ31 9/-
		DAF96 8/6
		DAF96 8/6
		DK96 8/6
		DL96 8/6
		DM70 7/6
		EB34 1/6
		EB91 4/6
		EBF80 9/-
		EC81 6/6
		EC82 7/6
		ECF80 12/6
		EF36 3/6
		EF37 4/6
		EF41 9/-
		EF50 2/9
		EF50(R) 4/-
		EF80 7/6
		EF85 7/6
		EF86 13/6
		EF91 5/-
		EF92 5/-
		GTIC 7/6
		PZ30 9/6
		UY41 8/-
		Z63 5/-
		Z66 9/6

ALL TESTED BEFORE DESPATCH
Any parcel insured against damage in transit for only 6d. extra per order. All uninsured parcels at customer's risk. C.O.D. or C.W.O. only. S.A.E. with all enquiries. Postage and Packing 6d. per valve extra. Trade enquiries invited.

**BENSON'S
LETTER
BARGAINS**

F.M. Discriminator Transformers, with 185 valve, new, 12/6. BOX with 4 3,000 type relays, twin 500Ω coils, plat. and tungsten contacts, 18/6. CONDENSERS, elec., 200 mfd., 275 v.w., 3/8 ; 16750 v.w., 4/6. TRANSFORMERS, vibrator, 11 v. to 265 v., potted, 10/6. MORSE KEY with cover and jackplug, 5/8. HAND-SETS, G.P.O. type, new, 10/6. CR100 Noise Limiter assemblies, with valve, 3/6 ; CR100 Power Trans., 30/-, BC434A Control boxes, 7/8. NEW M.C. METERS, 3 1/2 in. round flush, 50 μA., 70/- ; 100 μA., 65/- ; 1 mA., 55/- ; 2 mA. (rectified), 45/- ; 2 1/2 in. 500 μA., 27/6 ; 1 mA., 22/6 ; 5 mA., 7/8. 2 1/2 in. 100 mA., 200 mA., 300 mA., each 8/6. 2 1/2 in. 20 v. A.C., 8/6 ; 2 in. 40 v., 8/8 ; 300 v. A.C. 2 1/2 in., 15/-.

Crossover needle type 2 x 1 mA., 8/6. Indicator, coils, 400 μA. and 600 μA. (cz) movements and 2 neons, 8/6. 2 1/2 in. square, 150-0-150 A. (less shunt) 5 mA., 7/8. COMMAND RECEIVERS, brand new, 6 valves, med. wave (0.52-1.5 Mc/s), 97/8 ; used 82/6 (post 3/6). Conversion data and circ. to CAR RADIO, 1/6. I.F. STRIP 373, new, with valves, 37/8. VIBRATORS, Mallory G634C 12 v. 4-pin, 7/8. R.F. 26, R.F. 27, good cond., 18/- (p.p. 3/6). DYNAMOTORS (post 5/0) : 12 v. to 250 v. 60 mA. and 6.3 v. 11.6 A., 11/6. 6 v. to 250 v. 60 mA., 12/6. TYPE 2A, 12 v. to 300 v. 240 mA., 150 v. 10 mA., and 6.3 v. 5 A., smoothed, filtered, cased, 25/-.

R1155B, new condition, tested, with handbook, 27/10 (Rail 10/-). SCES22 Modulation or Driver Trans., either 7/6. INDICATORS with C.R.T.s VCR517 and VCR-139A, 5 valves, etc., 50/- (rail 8/6). Single 6 1/2 in. C.R.T., 10 valves 30/- (rail 7/6). CONVERTERS (ROTARY), 24 v. D.C. to 50 v. A.C., 4 A., 40/- (rail 7/6). MORSE TRAINER SET with buzz and key wired for 4 1/2 v. battery, 8/6. DRIVES : slow-motion Admiralty 200:1 ratio, sealed 0-100, 5/8. R1155 S.M. "N" type, new, 10/6. VIBRAPAK, 8 v. D.C. to 250 v. 60 mA., smoothed, cased, 22/6. 12 v. to 250 v. 100 mA., 17/6 (p.p. 8/6). LIST AND ENQUIRIES, S.A.E. please! Terms, C.W.O. Postage extra. Immediate despatch.

Callers and Post W. A. BENSON (PW)
138, Rathbone Road, Liverpool, 15. NEP 6853
Callers SUPERADIO (Whitechapel) LTD.
116 Whitechapel, Liverpool, 2. ROY 1130

**COVENTRY RADIO
LTD.**

189/191, Dunstable Rd., Luton

If you are unable to visit us at Luton, why not send for one of our "HI-FI" CATALOGUES? Price 1/-, plus 6d. postage. 70 pages and listing over 300 items.

Also now on sale: "THE GRUNDIG BOOK." Price 12/6, plus 1/- postage. The owner of any make of tape recorder will find this book an essential for successful recording.

LUTON'S HI-FI CENTRE
Telephone : Luton 7388/9.

**H.A.C. SHORT-WAVE
EQUIPMENT**

Noted for over 25 years for S.W. Receivers and Kits of Quality. Improved designs with Demco coils as supplied to Technical Colleges, etc. One-Valve Kit, Model "C", Price 25/- Two-Valve Kit, Model "E", Price 50/- New Addition: "Model "K" Super sensitive "All Dry" Receiver. Special incl. price. Complete Kit, 77/-.

All kits complete with all components, accessories and full instructions. Before ordering call and inspect a demonstration receiver. Or send stamped, addressed envelope for descriptive catalogue and order form. "H.A.C." SHORT-WAVE PRODUCTS (Dept. TH), 11, Old Bond Street, London, W.1.

TRANSISTOR SUPPLIES

Red Spots, 7/- ; White Spots, 10/- ; Yell./Green, 7/3 ; Yell./Red, 15/- ; Ediswan XA102 (8 M/cs), 40/- ; XA104 (6 M/cs), 18/- ; XA103 (4 M/cs), 15/- ; XB104, 10/- ; Mullard OC71, 24/- ; OC72, 30/- (Matched Pairs, 6/-) ; OC45, 35/- ; OC44 (12 M/cs), 40/- ; Newmarket V1510P, 20/- ; V1520P, 39/- ; V1530P, 48/- ; V15201P, 25/-.

ELECTROLYTICS. Sub-Min., 3/- each (15 volt), 2, 5, 8, 25, 50μF. Ardente Trans., D239 and D240, 8/6 ; T1079, 12/- ; D131 and D132, 12/9. T.V. Receiver Circuit—DRR2 coils, 4/- each.

BARGAIN LINES (Post Free)—Moving Coil (L.R.) Headphones and Mike, 10/6 ; Power Hand Mikes, 6/6 ; Super Co-ax, 8d. yard ; Var. Condensers, 003 AIR, 4/- ; Morse Keys, 3/3.

TERMS—Cash with order. Post Extra. Morco Reflex Circuit—Best 2 Transistor. Send 8d. stamps for our Notes.

MORCO EXPERIMENTAL SUPPLIES
8 & 10, Granville St., Sheffield, 2
Tel. : 27461.

RADIO CIRCUITS

A STEP BY STEP SURVEY
For its Fourth Edition this standard introduction to super-heterodyne receiver circuits, has been greatly extended and brought completely up to date. The whole text has been revised in the light of the latest developments, and new chapters have been added on transistors, car radio, and FM receivers. Although virtually a new book, it is written in the same simple, non-mathematical style intended for the student of radio, servicing apprentice and amateur enthusiast. By W. E. Miller & E. A. W. Spreadbury. 15/-. Postage 10d.

BRITISH TRANSISTOR MANUAL. By E. N. Bradley. 12/6. Postage 9d.

THE RIGHT WAY TO TAPE RECORD. By L. Mallory. 7/6. Postage 6d.

PRINCIPLES OF TRANSISTOR CIRCUITS. By S. W. Amos. 21/-. Postage 1/6.

ELEMENTARY TELECOMMUNICATIONS EXAMINATION GUIDE. By W. T. Perkins. 17/6. Postage 1/6.

RADIO VALVE DATA. 6th Ed. Compiled by "WW." 5/-. Post 9d.

BASIC PULSES. By I. Gottlieb. 27/-. Postage 1/6.

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS of British and American Technical Books
**19-23, PRAED STREET,
LONDON, W.2.**
Phone : PADdington 4185.
Open 6 days 9-6 p.m.

Why save up for a test set?



-you can have one NOW

Don't be at a loss waiting for a test set until you have sufficient money saved to buy one. You can have one of the well-known M.I.P. Series 100 Multi-Range test sets sent to you almost at once. A deposit of 47/6 secures. Balance payable over 6 or 12 months. Cash price £12.7.6.

Extended Terms

Deposit 47/6 and 6 monthly payments of £1.15.0

or

Deposit 47/6 and 12 monthly payments of 17/11

★ 21 SELF-CONTAINED RANGES ★

10-1,000 d.c. volts. 10-1,000 a.c. volts. 100 Microamps to 500 Milliamps d.c. 100 Microamps a.c. 0 to 1 Megohm. 8 to 10,000 ohms.

All voltage measurements a.c. and d.c. are at 10,000 ohms per volt.



MULTI-RANGE TEST SET - SERIES 100

MEASURING INSTRUMENTS (PULLIN) LTD.
Electrin Works, Winchester St., Acton, London, W.3.
Please send illustrated leaflet of the Series 100 Test Set with details of new easy payments scheme

NAME

ADDRESS

E759

GD.23

POST COUPON FOR FULL DETAILS

REPANCO EASY TO BUILD RECEIVERS

Repanco One Valve (Beginners set)	Instructions	1/-	post free
The Highwayman (Battery Portable)	..	1/9
Three Dee (Three transistor set)	..	1/-
Transeven (Transistor portable—preset)	..	1/9
Major 7 (Transistor portable—turntable)	..	1/9
Mini 7 (7 Transistor pocket set)	..	1/9
Repanco Car Radio (all Transistor)	..	2/6
FM Tuner Unit	..	1/9

All instructions with easy point to point wiring and assembly plans.

RADIO EXPERIMENTAL PRODUCTS LTD.

33, Much Park Street, Coventry. Tel: 62572.

SOUTHERN RADIO'S WIRELESS BARGAINS

QUARTZ CRYSTALS. Types F.T.241 and F.T.243, 2-pin, 3" Spacing. Frequencies between 5,675 Kc/s and 8,650 Kc/s. (F.T.243) 20 Mc/s. and 38.8 Mc/s. (F.T.24), 54th Harmonic, 4/- each. ALL BRAND NEW. TWELVE ASSORTED CRYSTALS, 45/-. Holders for both types, 1/- each. Customers ordering 12 crystals can be supplied with lists of frequencies available for their choice.

TRANSPARENT MAP CASES, Plastic. 14" x 10 1/2". Ideal for Maps, Display, etc..... 5/6

STAR IDENTIFIERS. Type I A-N Covers both Hemispheres. 5/6

CONTACTOR TIME SWITCHES. 2 Impulses per sec., in case 11/6

REMOTE CONTACTOR. For use with above..... 7/6

TRANSRECEIVERS. Type " 38 " (Walkie-Talkie) complete with 5 valves, etc. New condition, untested by us, but serviceable no guarantee. 22/6 each.

ATTACHMENTS for Type " 38 " Transreceivers. ALL BRAND NEW. PHONES, 15/6; THROAT MICROPHONES, 4/6; JUNCTION BOXES, 2/6; AERIALS, No. 1, 2/6; No. 2, 5/-; WEBBING, 4/-; HAVERSACKS, 5/-; VALVES, A.R.P.12, 4/6; A.T.P.4, 3/6. Set of FIVE VALVES, 19/- the set.

RESISTANCES. 100 Assorted useful values. New wire end, 12/6

CONDENSERS. 100 Assorted. Mica, Tubular, etc. NEW. 15/-

LUFBRA HOLE CUTTERS. Adjustable 4" to 3 1/2". For Metal, Plastic, etc. 7/-

MORSE TAPPERS. Midget Type, 2/9. Standard, 3/6. Heavy Type on Base, 5/6. ALL BRAND NEW.

MORSE PRACTICE SET. TAPPER with BUZZER on Base. Complete with Battery. BRAND NEW..... 12/6

MAGNETS. Strong Bar Type. 2" x 1 1/2". 1/6 each.

TRANSRECEIVERS. Type " 18 " Mark III. Two Units (Receiver and Sender). Six Valves, Micrometer, etc. Metal Case. Un-tested. No guarantee, but COMPLETE..... 22 18s. 6d.

ATTACHMENTS for " 18 " Transreceivers. ALL BRAND NEW. HEADPHONES, 15/6; HAND MICROPHONE, 12/6; AERIALS, 5/-; SET OF 6 VALVES, 30/-.

PACKARD-BELL AMPLIFIERS. Complete BRAND NEW with Valves; Relay, etc. etc. 17/6 each.

SPECIAL OFFER. 12 ASSORTED METERS. Slightly damaged. Mainly broken cases (perfect movements). Including 3 Brand New Aircraft Instruments. 12 for 45/-.

POST OR CARRIAGE EXTRA. FULL LIST OF RADIO BOOKS, ETC., 3d.

SOUTHERN RADIO SUPPLY LTD.
11, LITTLE NEWPORT ST., LONDON, W.C.2. GER. 6653.

The "TYANA"

Standard Soldering Iron



- 40 Watt economy Consumption

16/8. Replacement Elements and Bits always available.

- Adjustable Bit.
- Weight approx. 4oz.
- Heating Time 3 min.
- Standard Voltage Ranges.



"DIPLOMA" HEADPHONES

Lightweight High Resistance (4,000 ohms). Complete with cord. 17/6. Ideal for CRYSTAL SETS and also for use with TAPE RECORDERS.


KENROY LIMITED, 152/297 UPPER ST., ISLINGTON, LONDON, N.1
Telephone: Canonbury 4905-4663

MAXI-Q

REGD.

"WE COULD BLIND YOU WITH SCIENCE"
 on the technical superiority of our coils but
 are sure you would prefer us just to say
"WE GUARANTEE THEM"!

Coverage from 3.8 to 2,000 metres in 7 ranges—
 Each coil is packed in an aluminium container
 which may be used as a screening can for the
 coil itself—Brass threaded adjustable iron
 cores—Colour coded moulded polystyrene
 formers—Chassis/Plug-in Technical Bulletin
 DTB.1 1/6—Dual Purpose Technical Bulletin,
 DTB.4 1/6—Colour Code Identified Coils;
 BLUE Signal Grid Coil with Aerial Coupling
 winding—YELLOW Signal Grid Coil with
 intervalve coupling winding—GREEN Grid Coil
 with reaction and coupling windings—RED
 Superhet Oscillator for I.F. of 465 Kc/s—WHITE
 Superhet Oscillator for 1.6 Mc/s. Prices range
 from 4/1 to 4/9 each. Five Colour Glass Scale,
 Back Plate, Pointer, Pulleys and Cord for use
 with 315 pF tuning condensers. Coverage (1)
 150-400 Kc/s; (2) 530-1600 Kc/s; (3) 1.5-4 Mc/s;
 (4) 4-12 Mc/s; (5) 10-30 Mc/s; Price 15/-.

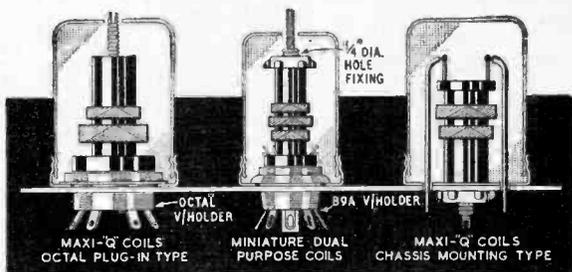

FOR GENERAL CATALOGUE covering full range of components send 1 Ad. in stamps or P.O. PLEASE SEND S.A.E. WITH ALL ENQUIRIES.

DENCO (CLACTON) LTD. (Dept. P.W.), 357/9 Old Road, Clacton-on-Sea, Essex

STOP PRESS: TREBLE LIFT INDUCTOR FOR THE MULLARD TYPE "C" TAPE PRE-AMPLIFIER. Wound in ferroxcube pot. core assembly. Price 22/6 each. Chassis. 32/6. Power Pack Chassis, 11/6. Front Panel with EM81 cut-out, hammered gold with neat control markings. 8/-.

EX-GOV'T SURPLUS POWER PACKS



Power supply units, vibrator type, 8 volt D.C., 300 VOLTS, 90 millamps, brand new, originally used with Communication General Purpose Receiver, model AR88, 77 & 77E. Complete with vibrator, tube, cable, adaptor, instruction pamphlet. F. & P. 3/6. **19/6**

RADIO CONTROL BOXES

Brand new, BC/802 B Complete with A, B, C D and off push button switches and five 24 volt electric bulbs, ideal for radio control, electric trains, etc. **4/6**

Carriage paid.

Money refund Guarantee.

S. & G. Stores, 40 High St., Scunthorpe.

Morse Code operating . . . as a PROFESSION

45 years of teaching Morse Code is proof of the efficiency of the Candler system.

Send 3d. stamp for Payment Plans and full details of all Courses.

CANDLER SYSTEM CO. Dept. SLO
52b, Abingdon Road, London, W.8.
Candler System Co., Denver, Colorado, U.S.A.

VALVES

6AM6, 6/-; 6BA6, 6/6; 6BE6, 6/6; 6AL5, 5/-; 6J6, 4/6; 6BV6, 8/6; 6CM6, 10/-; 6F33, 7/-; 6X4, 6/-; 6C4, 4/-; 12AT7, 6/-; 12AU7, 6/6; 12AX7, 8/-; 85A2, 12/6; 2D21, 10/-; EF86, 12/6; EY51, 9/-; EL91, 4/6.

SKILLMAN,

79A, FRANCHISE ST., WEYMOUTH

"GLOBE-KING"

WORLD-FAMOUS KITS AND RECEIVERS for the Radio Amateur and S.W. Listener. Catalogue Free, enclose stamp for Postage. Kits from 79/6 at your dealers, or direct from sole manufacturers:

JOHNSONS RADIO
St. Martins Gate, Worcester

TRANSFORMERS

Suppliers to B.B.C., I.T.A. and leading radio manufacturers, single or long runs, prompt delivery home and export.

Rewinds to all makes.

H. W. FORREST (Transformers) Ltd.
Shirley, Solihull, Warwickshire.
Tel.: SHirley 2483.

SPARKS' DATA SHEETS

Designs for Short-Waves & Trailers, etc. 10 to 220 Metres.

"**KESTREL**" Mk. II. Batt. Op. 3-Valver. H.F. Stage. Simplicity with Efficiency.
 "COXON" A.C. D.C. 2-Valver. Rect. Range and Power. An Outstanding design. Data Sheets with Detailed Instructions, etc. for the above. 3/3 each.

"**TIE**" 331 "A.C. TIE" 3-Valver. Rect. Widely Praised. Data Sheet. 3/6.
L. ORMOND SPARKES (P.)
 Valley Road, Corfe Castle, Dorset.

RES/CAP. BRIDGE 37/-

p. & p. 2/-
Checks all types of resistors, condensers 6 RANGES

Built in 1 hour. Direct reading
READY CALIBRATED

Stamp for details of this and other kits.

RADIO MAIL (Dept. PP)

Raleigh Mews, Raleigh Street, Nottingham

CHASSIS

18 swg Aluminium. Strengthened corners.
 6" x 4" x 2 1/2" 4- 11 1/2" x 7 1/2" x 2 1/2" 7/6
 7 1/2" x 5 1/2" x 2 1/2" 5/6 12" x 8" x 2 1/2" 8/-
 10" x 7 1/2" x 2 1/2" 6/8 14" x 9" x 2 1/2" 11/-
 Prompt service. Add 1/- post & pack. Orders over £1 post free. Moderate charges for punching and drilling to your requirements. Chassis for all Mullard circuits available.

Sweetnam & Bradley Ltd. Dept. AX
BRISTOL ROAD, MALMESBURY, WILTS.

GUARANTEED CAPACITORS

Hi-K Disc. : 500 v. d.c. wkg. 470 pF., .001 μ F., .002 μ F., .003 μ F., .005 μ F. 9d. each.
 Tubular : 500 v. d.c. wkg., 1, 1.5, 2, 3 pF. 1/- each; 5, 7.5, 10, 15, 20, 25, 30, 40, 47, 50, 60, 75, 100 pF. 10d. each; 150, 200, 250, 300, 350, 400, 500 pF., 1/2 each. Hi-K midge tubular, 500 v. d.c. wkg., 500 pF., .001 μ F., .002 μ F., .003 μ F., 10d. each; .005 μ F., .01 μ F. 1/- each.

Close Tolerance Silver Mica. Plus or Minus 1 pF. : 1.5, 2, 2.2, 3.9, 4.7, 5, 5.6, 8.2, 10, 15, 20, 25, 30, 40 pF. 11d. each. 1% : 47, 50, 56, 60, 68, 75, 80, 100 pF., 1/4 each.

Minimum postage 9d. on orders under £3. Please note we do not supply overseas except to H.M. Forces.

56-page illustrated catalogue No. 11 9d., post free.

SOUTHERN RADIO & ELECTRICAL SUPPLIES
SORAD WORKS
REDLYNCH, SALISBURY

Practical Wireless BLUEPRINT SERVICE

PRACTICAL WIRELESS

	<i>No. of Blueprint</i>
CRYSTAL SETS	
2/- each	
Crystal Receiver ...	PW71*
The "Junior" Crystal Set ...	PW94*
2/6 each	
Dual - Wave "Crystal Diode" ...	PW95*

STRAIGHT SETS

	<i>No. of Blueprint</i>
Battery Operated	
One-valve : 2/6 each	
The "Pyramid" One-valver (HF Pen) ...	PW93*
The Modern One-valver ...	PW96*
Two-valve : 2/6 each	
The Signet Two (D & LF) ...	PW76*
3/6 each	
Modern Two-valver (two band receiver) ...	PW98*
Three-valve : 2/6 each	
Summit Three (HF, Pen, D, Pen) ...	PW37*
The "Rapid" Straight 3 (D, 2 LF (RC & Trans) ...	PW82*
F. J. Camm's "Sprite" Three (HF, Pen, D, Tet) ...	PW87*
3/6 each	
The All-dry Three ...	PW97*
Four-valve : 2/6 each	
Fury Four Super (SG, SG, D, Pen) ...	PW34C*
Mains Operated	
Two-valve : 2/6 each	
Selectone A.C. Radiogram Two (D, Pow) ...	PW19*
Three-valve : 4/- each	
A.C. Band-Pass 3 ...	PW99*
Four-valve : 2/6 each	
A.C. Fury Four (SG, SG, D, Pen) ...	PW20*
A.C. Hall - Mark (HF, Pen, D, Push Pull) ...	PW45*

SUPERHETS

Battery Sets : 2/6 each	
F. J. Camm's 2-valve Superhet ...	PW52*
Mains Operated : 4/- each	
"Coronet" A.C.4 ...	PW100*
AC/DC "Coronet" Four ...	PW101*

*No. of
Blueprint*

SHORT-WAVE SETS

Battery Operated	
One-valve : 2/6 each	
Simple S.W. One-valver ...	PW88*
Two-valve : 2/6 each	
Midget Short-wave Two (D, Pen) ...	PW38A*
Three-valve : 2/6 each	
Experimenter's Short-wave Three (SG, D, Pow) ...	PW30A*
The Prefect 3 (D, 2 LF (RC and Trans) ...	PW63*
The Band-spread S.W. Three (HF, Pen, D (Pen), Pen) ...	PW68*

MISCELLANEOUS

2/6 each	
S.W. Converter-Adapter (1 valve) ...	PW48A*
The P.W. 3-speed Autogram ... (2 sheets), 8/-*	
The P.W. Monophonic Electronic Organ (2 sheets), 8/-*	
TELEVISION	
The "Argus" (6in. C.R. Tube) 3 -*	
The "Simplex" ... 3/6*	
The P.T. Band III Converter 1/6*	

All the following blueprints, as well as the PRACTICAL WIRELESS numbers below 94, are pre-war designs, kept in circulation for those amateurs who wish to utilise old components which they may have in their spares box. The majority of the components for these receivers are no longer stocked by retailers.

AMATEUR WIRELESS AND WIRELESS MAGAZINE

STRAIGHT SETS

Battery Operated	
One-valve : 2/6	
B.B.C. Special One-valver ...	AW387*
Mains Operated	
Two-valve : 2/6 each	
Consoelectric Two (D, Pen), A.C. ...	AW430

SPECIAL NOTE

THESE blueprints are drawn full size. The issues containing descriptions of these sets are now out of print, but an asterisk denotes that constructional details are available, free with the blueprint.

The index letters which precede the Blueprint Number indicate the periodical in which the description appears. Thus P.W. refers to PRACTICAL WIRELESS, A.W. to Amateur Wireless, W.M. to Wireless Magazine.

Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to PRACTICAL WIRELESS, Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

*No. of
Blueprint*

SHORT-WAVE SETS

Battery Operated	
One-valve : 2/6 each	
S.W. One-valver for American ...	AW429*
Two-valve : 2/6 each	
Ultra-short Battery Two (SG, det Pen) ...	WM402*
Four-valve : 3/6 each	
A.W. Short Wave World-beater (HF, Pen, D, RC, Trans) ...	AW436*
Standard Four-valver Short-waver (SG, D, LF, P) ...	WM383*
Mains Operated	
Four-valve : 3/6	
Standard Four-valve A.C. Short-waver (SG, D, RC, Trans) ...	WM391*

MISCELLANEOUS

Enthusiast's Power Amplifier (10 Watts) (3/6) ...	WM387*
Listener's 5-watt A.C. Amplifier (3/6) ...	WM392*
De Luxe Concert A.C. Electrogram (2/6) ...	WM403*

QUERY COUPON

This coupon is available until July 6th 1959, and must accompany all Queries sent in accord with the notice on our "Open to Discussion" page, PRACTICAL WIRELESS, JULY, 1959.

DO IT YOURSELF! NO EXTRAS TO BUY, EVERYTHING SUPPLIED FREE LISTS SENT ON ANY MODEL

All Components and Transistors Guaranteed

MAJOR—2

(Two-transistor Pocket Radio)



- ★ 4-stage reflex!
- ★ Medium wave; tunable!
- ★ Very sensitive!
- ★ No aerial or earth!
- ★ Complete layout!
- ★ Over 6 months on one battery!
- ★ 4½ x 3 x 1½ in.
- ★ Weight only 4 ozs.

Complete set of components with EDISWAN transistors, 72/6, post free. All components sold separately.

EXCEEDS ALL EXPECTATIONS!

"373" MINIATURE I.F. STRIP 9.72 MC/S



The ideal F.M. conversion unit as described in "P.W." April/May, 1957. Complete with 6 valves, three EF91s, two EF92s and one EB91 I.F.T.'s, etc., in absolutely new condition. With circuit and conversion data.

12/6 (less valves) 37/6 (with valves)

Postage and packing 2/6 (either type) FM AT ITS CHEAPEST!

LARGEST RANGE IN COUNTRY OF QUARTZ CRYSTALS AND VALVES. SEND FOR FREE LISTS.

SPEAKS FOR ITSELF! "THE TRANSISTOR—8"

Combined Portable/Car Radio

Push-Pull Portable Superhet

- ★ Tunable over medium and long wavebands.
- ★ 250 mW output push-pull.
- ★ Internal Ferrite aerial.
- ★ Highly sensitive and selective.
- ★ 7 x 4 in. large magnet speaker.
- ★ All components identified and carded.
- ★ EDISWAN transistors throughout.
- ★ Easy-to-follow layout diagrams.

Car radio components, 8/-; A.V.C., 4/3; 325 mW version, £13.10.0. P. & P. 2/6.

CAR RADIO 2-watt Amplifier

A permanent power transistor stage complete with 7 x 4 in. speaker. May be used with any battery portable using a 3 ohm speaker.

Complete set of parts ... 65/- P.P. 2/6 SEND FOR
Unit built up and tested ... 77/6 P.P. 2/6 FREE LISTS.

Complete set of parts including cabinet and all components.

£11.10.0.

P. & P. 2/6.

All parts sold separately. FREE BOOKLET



Size 9 x 7 x 3½ in. Weight 4 lbs.

TRANSISTORS

JUNCTION TYPE P.N.P.

EDISWAN XA104 6 Mc/s osc./mixer, r.f. amplifier ...	18/-
EDISWAN XA103 4 Mc/s i.f. and r.f. amplifier ...	15/-
EDISWAN XB104 1 Mc/s audio output and driver ...	10/-
(A pair in push-pull will give up to 250 mW audio output)	
Continental OC44 12 Mc/s osc./mixer, r.f. amp. ...	30/-
Continental OC45 6 Mc/s i.f. and r.f. amp. ...	25/-
Continental OC72 325 mW in push-pull ...	20/-
Red Spot 800 kc/s audio amplifier ...	7/6
White Spot 2 to 5 Mc/s r.f. and i.f. amp. ...	12/6
Green/Yellow 600 kc/s audio amplifier ...	7/6
Red/Yellow 1.5 to 8 Mc/s r.f. and i.f. amp. ...	15/-

OTHER EDISWAN AND MULLARD TRANSISTORS;
NEWMARKET POWER TRANSISTORS IN STOCK.
FREE DATA AND EQUIVALENTS LISTS SENT ON REQUEST.

NEW BARGAIN PARCEL

Perdio style cabinet with gold trimmings, 12/6 ★
Screened 208 and 176 pF Tuner, 10/- 2½ in. Speaker to fit, 21/6 ★
20:1 Single ended Transformer 3 £ 10/- ★
5-Transistor printed circuit board, 5/6 ★ Circuit diagram 1/- ★
Complete components as above, Special Price, 55/- P.P. 2/-

TELETRON ABOVE TRANSIDYNE

6-TRANSISTOR MEDIUM AND LONG-WAVE POCKET
RADIO USING LATEST EDISWAN TRANSISTORS. 150 mW.
PRINTED CIRCUIT, ETC. £11.19.6. P. & P. 2/6. LIST FREE.

LARGEST RANGE OF TRANSISTOR COMPONENTS
FOR THE HOME CONSTRUCTOR IN THE COUNTRY
FREE LISTS BY RETURN POST.

HENRY'S (RADIO) LTD. (Dept. P.W.JY). 5, HARROW ROAD, EDGWARE ROAD,
Opposite Edgware Road Tube Station. PADDINGTON 1008/9. PADDINGTON, LONDON, W.2.
OPEN MONDAY to SAT. 9-6, THURS. 1 o'clock.

718