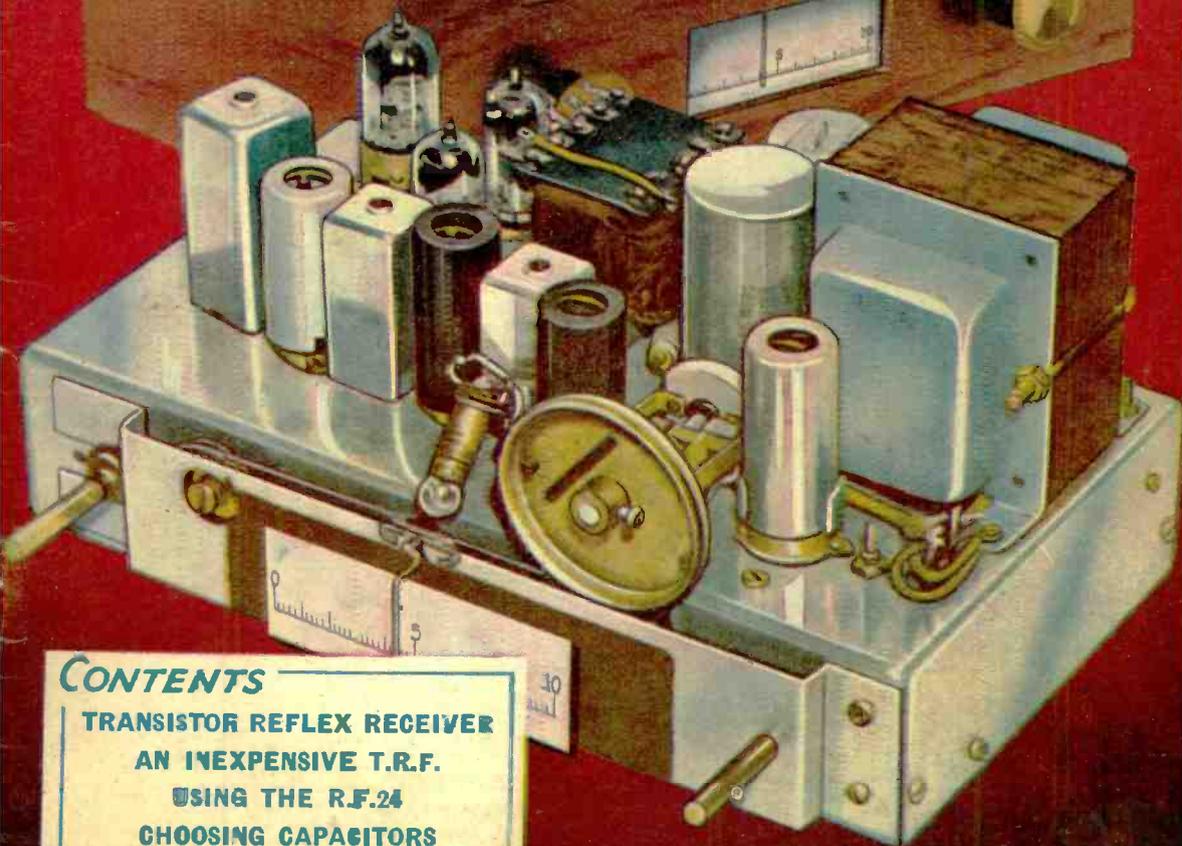


A QUALITY F.M. RECEIVER

PRACTICAL ^{1/6} WIRELESS

JANUARY

1960



CONTENTS

TRANSISTOR REFLEX RECEIVER

AN INEXPENSIVE T.R.F.

USING THE R.F.24

CHOOSING CAPACITORS

THREE-WAVEBAND SUPERHET

ETC. ETC. ETC.


COLLINS T.C.S. TRANSMITTERS & RECEIVERS



If both units purchased together. £17.0.0, carr. 25

T.C.S. TRANSMITTER. Designed for Mains and Mobile operation covering 1.5-12 Mc/s. (160-90-40 metre bands) consists of V.F.O., buffer, doubler, P.A. with internal push-pull modulator, provision for V.F.O. or crystal control on 4 channels. Output 25 watts phone. 50 watts C.W. Complete with aerial current meter scaled 0-3 amps. R.F. and plate current meter scaled 0-200 M.A., for phone and C.W. Panel controls: Aerial coupling, plate tuning, aerial selector, aerial loading unit, band selector, oscillator selector emission switch, power switch, geared and calibrated tuning drive, microphone and key inputs. Offered in used condition complete with full details. **£9.10.0** carr. 15/-

T.C.S. RECEIVER. 1.5 - 12 Mc/s. 7 valve superhet, built like a dream. 12SK7-RF. 12SA7 mixer, 12A6 oscillator, 12Q7 detector. AVC-BFO-1st Af. 12SK7-1.Fs. The 12A6 final puts 1.4 watts into 500 ohms with an input modulated only 30%. Panel controls: R.F. Gain, A.F. Gain, C.W. Pitch, bandswitch, mod. C.W. switch, power switch, ground and aerial posts, M.O. or crystal frequency switch, speaker jack, card holder to log 30 stations, hand vernier tuning knob turning a large etched calibrated plate behind hair lined window w. anti-backlash gears used. Used condition. **£8.10.0** carr. 15/-

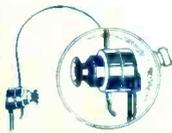

LIGHT-WEIGHT HEADSET. These H.S. 30 phones are the smallest used by the U.S. Air Force. 250Ω imp.

using soft rubber miniature ear moulds for maximum music and voice reproduction of the finest quality. Supplied free is a small transformer unit with cord and plug which steps impedance up to 4,000Ω. **ONLY 15/-.** P. & P. 2/6.

U.S.A. WHIP AERIALS. 12ft., 12/6. P. & P. 2/6.




WALK-TALK-INTERCOM. Two "space styled" telephone units in beautiful two-tone finish. No batteries or soldering required. Simply connect a wire between the two units and talk into microphone or listen on one and listen to speaker or talk on the other. Ideal for intercom from house to house, room to room, tent to tent, etc., operates anywhere even up to 200 yards. Brand new! Complete with 25ft. of wire. **ONLY 6/6 Per Set.** P. & P. 1/-

BUILD AN F.M. TUNER with this miniature 9.72 Mc/s I.F. Strip. Has 6 modern mini-



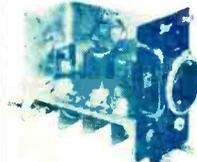ature valves, I.F.T.'s, etc., supplied with full F.M. Tuner conversion details. Hailed by all our previous purchasers as a wonderful F.M. Tuner. Brand new, only **40/-.** P. & P. 3/6.




CONVERT TO V.H.F.


Within minutes you can extend the frequency of your receiver to cover V.H.F. by using our brand new V.H.F. Converter. R.F. 26 covers 50-65 Mc/s. vernier calibrated tuning. 20- R.F. 25 covers 40-50 Mc/s. Switched tuning, 9/6. Circuits supplied. P. & P. 3/6 on each.

COMPLETE MORSE TRAINING UNIT

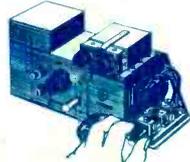Complete Code Set contains key, buzzer, headphones, pitch control, operating internal battery, housed in portable wooden case. Brand new, only 12/6. carr. 5/-, battery 1/6 extra.



WIRELESS SET NO. 19 MK.II

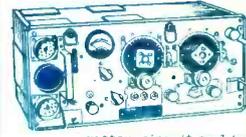


Incorporates "A" Set -TX RX covering 2-8 Mc/s (37.5-150 metres). "B" Set -V.H.F. TX RX covering 230-240 Mc/s. (1.2-1.3 metres) and intercom amplifier. Complete with 15 valves, 500 microamp check and tuning meter, circuit and instruction book. (American manufacture.) in used condition. 65/-, carr. 10/-.

POCKET MULTIMETER



2,500 o.p.v. Multi range 6/30 120 300 1,200 v. A.C. ditto D.C. 0-1 K. 0-1 megohm 400 MicroA. 12 mA., 300 mA. -0 to +64 D.B. 5 ranges: 3in. x 4 1/2in. x 1 1/2in. Large clear dial. Leads supplied.

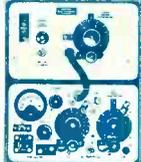List Price £6.19.6. **OUR PRICE** £4.7.6. Saving you £2.12.0. P. & P. 2/6.



PORTABLE TRANS/RECEIVER No. 18

A self-contained Trans Receiver for Telephone and C.W. Range approx. 10 miles. Freq. 6-9 Mc/s. (50-33.3 metres). Valve line-up: 3 ARP-12, 2 AR 8, 1 ATP 4. Complete with aerial, H.T. and L.T. meter and all accessories. Weight 20 lbs. Size 8 x 10 x 1 1/2in. **BRAND NEW ONLY 80/-** Carr. 10/-

CONTROL BOX—B.C.602



Complete push-button control box. 4 position and on/off, with dual coloured indicators for instant channel check. In black crackle case 5 1/2in. x 3 1/2in. x 1 1/2in. Bargain price. 5/- each. P. & P. 1/6. Two for 8/- P. & P. 2/6.

D.M.34. America's finest little dynamotor offering 12 v. in with 220 v. out at 80 mA. With suppression and smoothing mounting base. Size 4 1/2 x 2 1/2 x 2 1/2in. Original packing. **ONLY 35/-.** P. & P. 3/6.

1 mA METER 2in. round. 17/6. P. & P. 1/6.



HI-FI CO-AXIAL SPEAKERS BRAND NEW—U.S.A. MADE 12 1/2in. Co-axial Speaker. The woofer uses 6.8 oz. Alnico 5 magnet. Has 3in. tweeter and an electronic crossover network to separate the speaker functions. Frequency response: 40-17,000 cycles. Output 12 watts, impedance 8 ohms. **ONLY 160/-.** 8in. 2 1/2in. tweeter, 10 watts, etc., 90/- P. & P. 4/- on each.

VERDICK HI-FI AMPLIFIER. 10-watt push-pull ultra-linear feedback. Beautifully styled in green stove enamel. Provision for tuner, bass and treble, 5-position selector for radio, mike, tape, L.P. and std. records. List price 20 gns. **OUR PRICE £13.19.6.** P. & P. 7/6.

ACCUMULATORS. 2 volts 16 A.H. (unspillable). Ideal for 6 and 12 volts supply, etc. Brand new. Original cartons. Size 4in. x 7in. x 2in. 5/6 each. P. & P. 1/6. 3 for 15/- P. & P. 3/6. 6 for 27/6. P. & P. 5/-

ETCH YOUR OWN PRINTED CIRCUITS

You can now make your own printed circuits in the comfort of your own home. Etch-your-own kits do not require any skill or additional equipment, errors can be corrected at any stage, and can be completed within 1 hour. Each kit contains more than 60 square inches of laminated board and sufficient chemicals to make dozens of printed circuits. Highest quality materials and completely safe to handle. Absolutely any schematic can be made to printed circuit. This kit opens a whole new field for the radio constructor, hobbyist, etc., no matter how limited his skill. Complete kit with comprehensive manual containing advice and illustrated examples on translating **ONLY 19/6** P. & P. 1/6.



SPECIALY DESIGNED MINIATURE KITS FOR OUR ETCH-YOUR-OWN PRINTED CIRCUIT KIT
 1 Transistor diode pocket radio 24/6. p.p. 1/6
 2 valve 3 watt mains amplifier 49/6. p.p. 2/6
 3 Transistor Super Pocket Radio 72/6. p.p. 2/6
 All kits supplied entirely complete with full wiring and assembly details. Fully guaranteed.




Callers: 87, Tottenham Court Road, London, W.1.
 Mail orders: (Dept. P), 32a, Coptic Street, London, W.C.1.
 Telephone: MUSEUM 9607

See top of opposite page for another Relda Special!

IT'S NEW!

**INSTANT MULTI-PURPOSE
VALVE FILAMENT TESTER**

Pocket Size! Battery Operated!

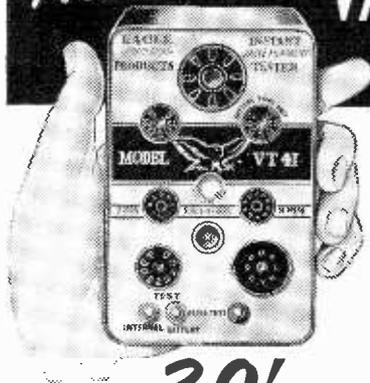

GIVES INSTANT CHECK OF:-

- All Receiver Valves.
- All Television Valves.
- All TV and Radio Fuses.
- All Pilot Lamps.
- Circuit Continuity.
- Built-in 7 and 9 pin Valve straighteners.
- Built-in Battery Test.

It is a well-known fact that 80% of Radio and Television faults are caused by Valves and Fuses which are the first components tested by a Service Engineer when examining a faulty set. Now, with this completely new and revolutionary precision instrument, you are your own Service Engineer and can test your own Valves, Fuses, Continuity and a large range of other radio parts.

Each component tested is shown "Good" or "Faulty" by a panel light.

By owning an Instant Tester Model VT41 you will be able to repair all your own sets and save the expense of calling in radio repair man.

**30%
POST AND
PACKING 2/6**

Finished in black hammer case with gold front panel. Complete with internal batteries and ready for immediate use.
GUARANTEED 12 MONTHS

★ Manufactured by Eagle Products, one of Britain's leading Test Equipment Specialists.

We consider this instrument so unparalleled for quality and value that we will refund your money if not entirely satisfied.

Relda Radio

Callers : 87, Tottenham Court Road, London, W.1.
Mail orders : (Dept. P), 32a, Coptic Street, London, W.C.1.
Telephone : MUSEum 9607

Now... in your own home. LEARN

RADIO - TELEVISION - ELECTRONICS

NO PREVIOUS TECHNICAL EXPERIENCE NEEDED!
PRACTICAL EQUIPMENT (INCLUDING TOOLS) GIVES YOU A REAL LABORATORY TRAINING

"The trained electronics engineer has a great career ahead of him."

Valuable FREE Book shows how E.M.I. Institutes School of Electronics can train you for today's wonderful opportunities.

Radio, Television and Electronics provide an exciting field for the trained man—high pay, a prosperous future—or if you prefer it—independence in your own business. If you are trained at home by E.M.I. Institutes you will be in the hands of specialists who know the quickest way to prepare you for one of the fine jobs open to trained electronics-men. Whether you are a beginner or an advanced student with an examination in mind, E.M.I. Institutes School of Electronics has a Course exactly suited to your needs—with or without practical equipment—from electricity and magnetism to automation techniques.

Practical Radio
Radio & Television Servicing
Practical Electronics
Electronics Engineering
Automation
Basic Practical and Theoretic Courses for beginners in Radio, T.V., Electronics, Etc.
A.M. Brit. I.R.E.,
City & Guilds Radio
Amateurs' Exam.
R.T.E.B. Certificate
P.M.G. Certificate
"NO PASS—NO FEE"

We Definitely Guarantee "NO PASS—NO FEE"
Full details of the Courses, Practical Equipment, convenient monthly payments, our Employment and Advisory Depts., and much other helpful information is given in our Guide to Careers in Electronics. Write for your copy today. There is no obligation and the book will be sent to you quite free of charge.

FREE BOOK - POST NOW!

■ Please send me a free copy of your Guide to Careers in Electronics.

■ NAME

■ ADDRESS

■ Subject or Exam



E.M.I. INSTITUTES

SCHOOL OF ELECTRONICS

The Specialist Electronics Division of the British Institute of Engineering Technology.

(DEPT. SE/20), COLLEGE HOUSE, 29-31, WRIGHT'S LANE, KENSINGTON, LONDON, W.8.

BENTLEY ACOUSTIC CORPORATION LTD.

THE VALVE SPECIALISTS. 38 CHALCOT ROAD, LONDON, N.W.1. Telephone: PRIMROSE 9090

EXPRESS POSTAL SERVICE! ALL ORDERS DESPATCHED SAME DAY AS RECEIVED. FOR ONLY 2/- EXTRA TELEPHONE FOR THAT URGENT ORDER TO BE DESPATCHED IMMEDIATELY BY OUR SPECIAL C.O.-DELIVERY.

ANY ORDER INSURED AGAINST DAMAGE IN TRANSIT FOR ONLY 6d. EXTRA.																				
0B2	17/6	6C8	12/6	6X4	6/6	19H1	10/-	AC/PEN	DL94	7/6	EL33	12/6	KTZ63	10/6	QP25	15/-	UCH81	9/6		
0Z4	6/-	6C9	12/6	6X5GT	6/6	20D1	15/3	5-pin 23/3	DL96	9/-	EL34	15/-	L63	6/-	Q150/15	10/6	UCL82	11/6		
1A3	3/-	6C10	10/6	6J30L2	10/-	20F2	26/6	7-pin 15/-	DL510	10/6	EL38	26/6	LN152	10/6		10/6	UCL83	19/3		
1A5	6/-	6CD6G	7/6	7A7	12/6	20L1	26/6	AC2PEN	DM70	7/6	EL41	9/-	MH4(C)	7/-	R12	9/6	UFL1	9/-		
1A7GT			36/6	7B6	21/3	20P1	26/6		EASO	2/-	EL42	13/11	MHL4	7/6	R18	14/-	UF42	12/6		
	21/11	6CH6	12/6	7B7	8/6	20P3	23/3	AC2PEN	EABC80	9/-	EL45	12/6	MHLD6	12/6	R19	19/11	UFL0	10/6		
1C5	12/6	6D3	19/11	7C5	8/-	20P5	23/3	DD	EAC91	7/6	EL84	8/6	ML4	12/6	SD6	12/-	UF85	10/6		
ID6	10/6	6D6	6/6	7C6	8/-	25A6G	11/-	AC/PEN	EAF42	9/6	EL85	13/11	MU14	9/-	SP4(7)	15/-	UF86	17/11		
IHSGT	11/-	6E5	12/6	7D8	23/3	25L6GT	10/-		EB34	2/6	EL91	5/-	MX40	15/-	SP41	3/6	UF89	9/-		
1L4	6/-	6F1	26/6	7H7	8/-	25U4	16/7	AC5PEN	EB41	8/6	EL95	10/6	N37	19/11	SP42	12/6	UL41	9/-		
1LD5	5/-	6F6G	7/-	7R7	12/6	25Y5	10/6		EB91	5/6	EM34	10/6	N78	19/11	SP61	3/6	UL44	26/6		
1LNS	5/-	6F6GT	8/-	757	10/6	25Y5G	10/-	AC6PEN 7/6	EB33	23/3	EM71	23/3	N108	19/11	SU25	26/6	UL46	14/6		
IN5GT	11/-	6F8	12/6	7Y7	8/6	25Z4G	9/6	AC/P4	EB33	7/-	EM80	9/6	N308	20/7	T41	9/6	UL94	8/6		
1RS	7/6	6F11	17/3	7Y8	8/-	25Z5	10/6	AC/SJ 23/3	EB34	8/6	EM81	9/6	N339	29/10	T41	23/3	UM4	17/3		
IS4	9/-	6F12	5/6	7Z4	18/7	25Z6GT	10/6	AC/TP 33/2	EB38	8/6	EM84	10/6	OA70	4/-	TH48	15/-	U06	19/11		
IS5	7/6	6F13	11/6	8D2	3/6	25Z6GT	10/6	AC/VP1	EBF80	10/-	EN31	37/6	OA71/81	4/-	TH48	15/-	U06	19/11		
IT4	6/-	6F14	26/6	8D3	5/6		16/7	7-pin 15/-	EBF83	13/11	EY51	9/6	OC72	7/6	TH41	26/6	U07	16/7		
1U5	10/-	6F15	15/3	9BW6	15/3	27SU	19/11	AC/VP2 23/3	EBF89	9/6	EY83	16/7	P6	3/6	TH233	33/2	U08	26/6		
2A7	10/6	6F16	9/6	9D2	4/-	28D7	7/-	ATP4	5/-	EBL21	23/3	EY84	14/6	PABC80		TH2321	20/-	U09	7/6	
2P	26/6	6F17	12/6	10C1	12/-	30C1	8/-	AZ1	18/7	EBL31	23/3	EY86	10/-		13/11	TP22	15/-	UY1N	18/7	
2X2	4/6	6F32	10/6	10C2	26/6	30F5	7/-	AZ21	10/-	EC52	5/6	EZ35	6/-	PCC84	8/-	TP25	19/6	UY21	16/6	
3A4	7/-	6F33	7/6	10D2	12/-	30FL1	10/-	AZ41	13/11	EC54	6/-	EZ40	7/6	PCC85	9/6	TP2620	33/2	UY41	7/6	
3A5	10/6	6G6	6/6	10F1	17/6	30L1	8/-	B36	24/7	EC70	12/6	EZ41	7/6	PCC88 23/11	TY86F	13/3	UY85	7/6		
3B7	12/6	6H6GTG	3/-	10F9	17/6	30P12	8/-	BL63	7/6	EC92	13/3	EZ80	7/6	PCC89	14/-	UI2/14	12/-	VMS48	23/3	
3D4	5/-	6H6GTM	3/-	10LD3	8/6	30P16	8/-	CI	12/6	ECC32	10/6	EZ81	7/6	PCC88	8/-	UI6	12/-	VP2(7)	12/6	
3Q6	9/6	6H6GTG	5/6	10LD11	11/6	31	7/6	CBL1	26/6	ECC34	24/7	FC4	15/-	PCL82	11/6	UI28	8/-	VP4(7)	15/-	
3Q5GT	7/6	6H6GTM	6/-	10P13	15/6	33A/158M		CBL31	23/3	ECC35	8/6	FC13	26/6	PCL83	11/6	U24	29/10	VP4B	23/3	
3S4	7/6	6H6GTG	5/6	10P14	19/3		30/6	CH35	23/3	ECC40	23/3	FC13C	26/6	PCL84	12/6	U25	13/6	VP13C	7/6	
3V4	7/6	6H6GTG	5/6	10P14	19/3		30/6	CH35	23/3	ECC40	23/3	FC13C	26/6	PCL84	12/6	U25	13/6	VP13C	7/6	
3R4GY	17/6	6I7G	6/-	11D3	24/7	35/51	12/6	CK506	6/6	ECC81	8/-	FW4/500		PEN4DD	U26	10/-	VP23	6/6		
5U4G	8/6	6I7GT	10/6	12A6	6/6	35A5	21/3	CL33	19/3	ECC82	7/6			PEN25	19/11	U33	26/6	VR75/30		
5V4G	11/-	6K6GT	8/-	12AC6	15/3	35L6GT	9/6	CV63	10/6	ECC83	8/6	FW4/800		PEN25	19/11	U33	26/6	VR105/30		
5X4G	12/6	6K7G	5/-	12AD6	17/3	35WV4	7/6	CV271	10/6	ECC84	9/6			PEN36C	U35	26/6			17/6	
5Y3G	8/-	6K7GT	6/-	12AE6	13/11	35Z3	10/6	CY428	30/-	ECC85	8/6	GZ30	10/6		10/6	U37	26/6	VR105/30		
5Y3GT	7/6	6K8G	8/-	12AH7	8/-	35Z4	6/6	CV1	18/7	ECC91	5/6	GZ32	12/6	PEN40DD	U43	9/6			9/-	
5Y4	12/6	6K8GTG	12/6	12AH8	12/6	35Z52G	9/-	CY31	16/7	ECCF80	11/6	GZ34	14/-		25/45	U45	9/6	VR150/30		
5Z3	12/6		12/6	12AT6	7/6	41MTL	8/-	DI	3/6	ECF82	10/6	H30	5/-	PEN44	26/6	U50	8/-		9/-	
5Z4G	10/6	6K25	19/11	12AT7	8/-	42	23/3	D15	10/6	ECH3	26/6	H63	12/6	PEN45	19/6	U52	8/6	VT61A	5/-	
5Z4GT	12/6	6L1	23/3	12AU6	23/3	43	12/6	D63	5/6	ECH21	23/3	HABC80		PEN45DD	U54	19/11	VT501	5/-		
6A7	26/6	6L6G	9/6	12AU7	7/6	50C5	12/6	D77	5/6	ECH35	9/6				26/6	U76	6/6	W61M	26/6	
6A8	10/-	6L6M	12/6	12AV6	12/7	50CD6G		DAC32	11/6	ECH42	10/6	HL23	10/6	PEN46	7/6	U78	6/6	W76	6/6	
6AB7	8/-	6L7GT	12/6	12AX7	8/-		36/6	DAF91	7/6	ECH81	9/-	HL23DD		PEN383 23/3	U107	16/7	W81M	6/6		
6AB8	10/6	6L18	13/-	12BA6	8/-	50L6GT	9/6	DAF96	9/6	ECH83	13/11			PEN453DD	U191	16/7	W107	15/3		
6AC7	6/6	6L19	23/3	12BB6	10/-	53KU	19/11	DC90	13/11	ECL80	10/6	HL41	12/6		33/2	U201	16/7	W229	18/7	
6AG5	6/6	6LD3	8/6	12BH7	21/3	72	4/6	DD41	13/11	ECL82	10/6	HL41DD		PEN/DD	U251	14/-	X24M	24/7		
6AK5	8/-	6LD20	15/11	12E1	30/7	75	24/7	DDT4	24/7	ECL83	19/3				4020	33/2	U281	19/11	X31	26/6
6AL5	5/6	6N7	8/-	12J5GT	4/6	77	8/-	DF33	11/6	EF9	23/3	HL42DD			PL33	19/3	U282	22/7	X41	15/-
6AM6	5/6	6P1	19/3	12J7GT	10/6	78	8/6	DF66	15/-	EF22	14/-				PL36	14/-	U301	23/3	X42	12/6
6AQ5	8/6	6P25	12/6	12K5	17/11	80	9/-	DF70	15/-	EF36	6/-	HN309	24/7	PL38	26/6	U329	16/7	X61(C)	12/6	
6AT6	8/6	6P28	26/6	12K7GT	6/6	83	15/-	DF91	6/-	EF37A	8/-	HVR2	20/-	PL81	12/6	U339	16/7	X61M	26/6	
6AU6	10/6	6Q7G	8/-	12K8GT	14/-	83V	12/6	DF96	9/-	EF39	5/6	HVR2A	6/-	PL82	8/-	U403	16/7	X63	10/6	
6AV6	12/7	6Q7GT	11/-	12Q7GT	6/6	85A2	15/-	DF97	9/-	EF40	15/-	KF35	8/6	PL84	9/-	U404	8/6	X65	12/6	
6B7	10/6	6R7G	10/-	12SA7	8/6	85B2	15/-	DH63	8/-	EF41	9/6	KL32	21/11	PL84	12/6	U801	29/10	X66	12/6	
6BBG	4/6	6SA7G	8/6	12SC7	8/6	185BT	33/2	DH63(Mec)	EF42	11/6	KL35	8/6	PL820	18/7	U4020	16/7	X76M	14/6		
6BBGT	5/-	6SC7	10/6	12SG7	8/6	185BTA	33/2		EF50(A)	7/6	KL32	24/7	PM28	12/6	UABC80	9/-	X78	21/3		
6BA6	7/6	6SG7GT	8/-	12SH7	8/6	304	10/6	DH76	6/6	EF50(E)	5/-	KT2	5/-	PM12	6/6	UAF42	9/6	X79	21/3	
6BE6	7/6	6SH7GT	8/-	12SI7	8/6	305	10/6	DH77	8/6	EF54	5/-	KT33C	10/6	PM12M	6/6	UB41	12/-	X101	33/2	
6BG6G	23/3	6S7GT	8/-	12SK7	8/6	402Pn/A		DH101	28/6	EF73	10/6	KT36	29/10	PM24M	21/3	UB41	8/6	X109	17/3	
6BH6	9/-	6SK7GT	8/-	12SQ7	12/6		23/3	DH107	13/11	EF80	7/-	KT41	26/6	PX4	10/6	UBC81	11/4	XD(1.5)	6/6	
6B16	7/6	6SL7GT	8/-	12SR7	8/6	807	7/6	DK32	21/11	EF85	7/-	KT44	15/-	PX25	59/8	UBF80	9/-	XFG1	18/-	
6BQ7A	15/-	6NS7GT	6/6	12Y4	10/6	956	3/-	DK40	21/3	EF86	12/6	KT61	12/6	PY31	16/7	UBF89	9/6	XFY34	17/6	
6BR7	23/3	6OS7GT	9/-	14Y7	23/3	1821	16/7	DK91	7/6	EF89	9/-	KT63	7/-	PY32	17/11	UBL21	23/3	XH(1.5)	6/6	
6BV6	10/6	6S7GT	9/-	14Y7	23/3	1821	16/7	DK92	10/6	EF91	5/6	KT66	15/-	PY80	7/6	UBL21	23/3	XSG(1.5)	6/6	
6BW7	7/-	6US7	12/6	15D1	26/6	5763	12/6	DK96	9/-	EF92	5/6	KT88	22/6	PY81	9/-	UCB84	14/7		6/6	
6BX6	7/-	6US7	7/6	18	23/3	7193	5/-	DL33	9/6	EF97	13/3	KTW61	8/-	PY82	7/-	UCC85	9/-	Y63	7/6	
6C4	7/-	6U7G	8/6	19AQ5	10/6	7475	7/6	DL66	15/-	EF98	13/3	KTW62	8/-	PY83	9/6	UCC80	16/7	Z63	10/6	
6C5G	4/6	6V6G	7/-	19BG6G		9002	5/6	DL68	15/-	EL32	8/6	KTW63	8/-	PZ30	19/11	UCH21	23/3	Z66	20/-	
6C6	6/6	6V6GTG	8/-		23/3	9006	6/6	DL92	7/6	EL32	5/6	KTZ41	8/-	PZ31	7/-	UCH42	9/6	Z77	5/6	

NEW METAL RECTIFIERS—FULLY GUARANTEED

DRM-1B	15/4	RM-2	7/6	WX3	3/6	14A100	25/-	14RA 1-2-8-2	19/-	16RE 2-1-8-1	8/6
DRM-2B	16/2	RM-3	9/6	WX4	3/6	14A124	28/-	14RA 1-2-8-3	23/6	18RA 1-1-8-1	4/6
DRM-3B	23/3	RM-4	16/-	WX6	3/6	14A163	38/-	14RA 1-1-16-1	21/-	18RA 1	

Stern's "fidelity" TAPE EQUIPMENT

YOU CAN BUILD A COMPLETE TAPE RECORDER

for **£36.0.0**

A SELECTION OF HIGH FIDELITY PORTABLE TAPE PREAMPLIFIERS

Adds "Hi-Fi" TAPE RECORDING TO YOUR EXISTING AUDIO INSTALLATION

IN ALL MODELS WE INCORPORATE THE TYPE "C" PREAMPLIFIER

AND OFFER IT COMPLETE IN CASE WITH . . .

- (a) The new COLLARO "STUDIO" 3 Speed Deck H.P. Deposit. **£7.6.0.** 12 months **£213.6.** **£36.10.0**
- (b) The COLLARO Mk. IV "Transcripitor" 3 Speed Deck H.P. Deposit. **£8.6.0.** 12 months **£3.0.11.** **£41.10.0**
- (c) The New TRUVOX Mk. VI. Tape Deck H.P. Deposit. **£8.14.0.** 12 months **£3.3.10.** **£43.10.0**
- (d) The BRENNEL Mk. V 3 Speed Deck H.P. Deposit **£10.6.0.** 12 months **£3.15.7.** **£51.10.0**
- (e) The WEARITE MODEL 4A Tape Deck Deposit. **£12.4.0.** 12 months **£4.9.5.** **£61.0.0**

STERN'S MULLARD TYPE "C" TAPE PREAMPLIFIER-ERASE UNIT

INCORPORATING THE NEW FERROXUCUBE POT CORE PUSH-PULL OSCILLATOR and 3-SPEED TREBLE EQUALISATION by means of the latest FERROXUCUBE POT CORE INDUCTOR. FITTED . . . INCLUDING SEPARATE SMALL POWER SUPPLY COMPLETE KIT OF PARTS **£14.0.0**
ASSEMBLED AND TESTED **£17.0.0**

Dep. **£3.5.0** and 12 of **£14.1.11.**
ALSO AVAILABLE EXCLUDING POWER SUPPLY UNIT FOR **£11.15.0** and **£14.10.0** respectively.

WHEN ORDERING PLEASE STATE MAKE OF TAPE DECK TO BE USED. We present this "Hi-Fi" Preamplifier strictly to Mullard's specification incorporating ONLY NEW HIGH-GRADE COMPONENTS and the SPECIFIED NEW MULLARD VALVES. It comprises a COMPLETELY SELF-CONTAINED UNIT, neatly finished in Hammered Gold with a very attractively engraved PERSPEX FRONT PANEL.

FOR PERMANENT HIGH QUALITY INSTALLATIONS WE ALSO OFFER (excluding case)

- (a) The COLLARO "STUDIO" TAPE DECK and our Mullard Type "C" PREAMPLIFIER and Power Unit Assembled and Tested. **£32.10.0**
H.P. Deposit **£8.10.0.** and 12 months **£2.7.8.**
- (b) As above but TYPE "C" PREAMPLIFIER supplied as complete KIT OF PARTS. **£29.0.0**
- (c) The COLLARO Mk. IV TAPE DECK and the MULLARD TYPE "C" PREAMPLIFIER & Power Unit assembled, tested. **£35.0.0**
H.P. Deposit **£7** and 12 months **£2.11.4.**
- (d) As (c) but Type "C" as COMPLETE KIT OF PARTS. **£32.0.0**
- (e) The TRUVOX Mk. VI DECK and the assembled Type "C" Preamplifier and Power Unit. **£40.0.0**
H.P. Deposit **£8.0.0.** and 12 months **£2.18.3.**
- (f) As above but Type "C" as complete KIT OF PARTS. **£36.10.0**
- (g) The BRENNEL Mk. V DECK and the assembled Type "C" PREAMPLIFIER and POWER UNIT. **£46.0.0**
H.P. Deposit **£9.4.0.** and 12 months **£3.7.6.**
- (h) As (g) but Type "C" as complete KIT OF PARTS. **£43.0.0**
- (i) The WEARITE 4A DECK with TYPE "C" assembled and tested. **£45.0.0**
H.P. Deposit. **£11.4.0** and 12 months **£4.2.1.**
(Carriage and Insurance on above quotes 10% extra.)

PLEASE ENCLOSE S.A.E. WITH ALL CORRESPONDENCE.

STERN RADIO LTD.

109 & 115 FLEET ST., LONDON, E.C.4

Telephone: FLEET STREET 5812/3/4



H.P. TERMS Deposit **£7.4.0.**
12 months **£2.12.10.**

FOR THIS WE SUPPLY:

- ★ COMPLETE KIT OF PARTS TO BUILD THE HF/TR3 TAPE AMPLIFIER.
- ★ NEW COLLARO "STUDIO" TAPE DECK
- ★ PORTABLE CARRYING CASE (as illustrated).
- ★ ROLA CELESTION 10in. x 6in. P.M. LOUDSPEAKER.
- ★ ACOS CRYSTAL MICROPHONE, 1.200ft. SPOOL E.M.I. TAPE. For those who prefer another type of TAPE DECK we will supply precisely as

above—but IN PLACE of the COLLARO "STUDIO" DECK—WE INCLUDE:


- (a) The Mk. IV COLLARO "TRANSCRIPTOR" DECK H.P. Deposit **£8.0.0** and 12 months **£2.18.2.** (£1 extra if we are required to wire up the Transcripitor Switch Banks.) **£39.15.0**
- (b) The New TRUVOX Mk. IV DECK H.P. Deposit **£9.0.0.** and 12 months **£3.6.0.** (Carriage and Insurance on all above is 12/6 extra.) For Constructors with their own Cabinet WE OFFER: (a) COMPLETE KIT to build the HF/TR3 Amplifier together with the COLLARO "STUDIO" DECK... **£28.0.0**
- (b) As above but with HF TR3 supplied ASSEMBLED and TESTED **£31.10.0**
H.P. Deposit **£6.6.0.** and 12 months **£2.6.0.**
- (c) COMPLETE KIT to build the HF/TR3 together with the Mk. IV COLLARO "TRANSCRIPTOR" TAPE DECK (21 extra if we are required to wire up Deck Switch Banks.) **£30.15.0**
- (d) As above but HF, TR3 supplied ASSEMBLED and TESTED **£34.10.0**
(£1 extra if we are to wire up Deck Switch Banks.)
- (e) COMPLETE KIT to build the HF/TR3, together with the NEW TRUVOX Mk. VI TAPE DECK... **£36.0.0**
- (f) As above but HF/TR3 supplied ASSEMBLED and TESTED **£39.10.0**
H.P. Deposit **£7.10.0.** and 12 months **£2.17.11.**
- (g) COMPLETE KIT to build the HF/TR3 AMPLIFIER with the BRENNEL Mk. V TAPE DECK... **£41.10.0**
- (h) As above but HF/TR3 supplied ASSEMBLED and TESTED **£45.0.0**
H.P. Deposit **£9.0.0.** and 12 months **£3.6.0.**
Carriage and Insurance on each above is 10/- extra.

Attractive PORTABLE CASE is available to accommodate the TRUVOX or COLLARO TAPE DECKS and we offer it, together with ROLA CELESTION 10in. x 6in. LOUDSPEAKER—ACOS CRYSTAL MICROPHONE—and 1,200 ft. SPOOL E.M.I. TAPE—ALL FOR **£9.0.0.** Carriage and Insurance 6/- extra.

WE HAVE THE NEW 2 SPEED TWIN TRACK TRUVOX Mk VI TAPE DECK IN STOCK £26.5.0
DEPOSIT : **£5.5.0** and 12 MONTHS : **£1.18.6**

THE MODEL HF/TR3 TAPE AMPLIFIER

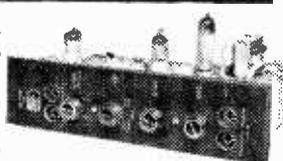INCORPORATING 3-SPEED TREBLE EQUALISATION by means of the latest FERROXUCUBE POT CORE INDUCTOR.
PRICE for COMPLETE KIT OF PARTS **£12.15.0**
PRICE FULLY ASSEMBLED & TESTED **£16.10.0**



HIRE PURCHASE. Deposit **£3.6.6** and 12 monthly payments of **£1.4.2.** A very high-quality Amplifier based on the very successful TYPE "A" design completed in the MULLARD LABORATORIES. ONLY NEW HIGH-GRADE COMPONENTS are incorporated including MULLARD VALVES and a GILSON OUTPUT TRANSFORMER. . . other features are—Magic Eye Recording hand indicator—Effective Tone Control—Monitoring and Extension Speaker Sockets—Has own Power Supply and can be used as independent Amplifier for direct reproduction of Gram Records or from Radio Tuner. Overall size 11in. x 6in. x 6in. Can be supplied for use with Truvox—Collaro—Lane—Brenell or Motok Decks. Please specify which. Send S.A.E. for leaflet or 2/6 for complete Assembly Manual.


MULLARD DESIGNS

*Still by far the
finest value*

Designed by MULLARD—presented by STERNS strictly to specification.
COMPLETE KIT OF PARTS—

MULLARD "5-10" MAIN AMPLIFIER

For use with the MULLARD 2-stage pre-amplifier (described below) with which an undistorted power output of up to 10 watts is obtained. This combination is thoroughly recommended to "Hi-Fi" enthusiasts who contemplate a versatile and very high quality home installation. We supply SPECIFIED COMPONENTS and NEW MULLARD VALVES, including PARMEKO MAINS TRANSFORMER (which has extra Power available to drive Radio Tuner) and the choice of the latest Ultra-Linear PARMEKO or the PARTRIDGE Output Transformer.

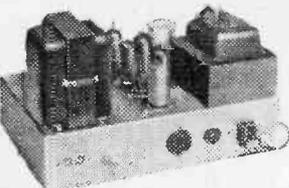

PRICE COMPLETE KIT (PARMEKO) **£10.00** Alternatively we supply ASSEMBLED and TESTED, **£11.10.0**. ABOVE INCORPORATING PARTRIDGE OUTPUT TRANSFORMER, **£16.0** EXTRA.

MULLARD'S PRE-AMPLIFIER TONE CONTROL UNIT



Employing two EF95 valves, and designed to operate with the MULLARD 3-3 and 5-10 MAIN AMPLIFIERS, also perfectly suitable for other makes.


PRICE, COMPLETE KIT OF PARTS, **£6.6.0** Alternatively we supply ASSEMBLED AND TESTED **£8.0.0** (Carriage & Insurance, 5/- extra.)

Our kit is strictly to MULLARD'S SPECIFICATION and incorporates:

- Equalisation for the latest R.I.A.A. characteristics;
- Input for Crystal Pick-ups, and variable reluctance magnetic types.
- Input. (a) Direct from High Imp. Tape Head. (b) From a Tape Amplifier or Pre-amplifier.
- Sensitive Microphone Channel.
- Wide range BASS and TREBLE Controls.

COMPLETE MULLARD 5-10

The popular and very successful complete "5-10" incorporating Control Unit providing up to 10 watts high quality reproduction. Input channels for high output pick-ups and all modern Radio Tuning Units only Specified Components and new MULLARD VALVES are supplied, including PARMEKO MAINS TRANSFORMER and choice of the latest PARMEKO or PARTRIDGE ULTRA-Linear Output Transformers. Adequate power available to drive Radio Tuner.

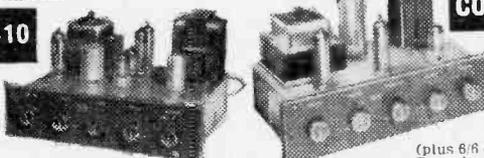

£11.10.0

Alternatively we supply ASSEMBLED and TESTED **£13.10.0**

HIRE PURCHASE (Assembled Amp. only) DEPOSIT : **£2.14.0**.
12 MONTHS : **19/10**.
ABOVE incorporating PARTRIDGE OUTPUT TRANS.. **£16.0** extra.

SPECIAL PRICE REDUCTIONS

(a) The COMPLETE KIT OF PARTS to build both the "3-3" MAIN AMPLIFIER and the 2-STAGE PRE-AMPLIFIER-CONTROL UNIT **£12.10.0**

(b) The COMPLETE KIT OF PARTS to build the "5-10" MAIN AMPLIFIER and the 2-STAGE PRE-AMPLIFIER-CONTROL UNIT **£15.15.0**

(a) The "3-3" and the 2-STAGE PRE-AMPLIFIER both ASSEMBLED and TESTED **£15.0.0**

I.P.P. : DEPOSIT **£3.0.0** and 12 Monthly Payments of **£1.2.0**.

(b) The "5-10" and the 2-STAGE PRE-AMPLIFIER both ASSEMBLED and TESTED **£18.18.0**

I.P.P. : DEPOSIT **£3.16.0** and 12 Monthly Payments of **£1.7.8**. When

ordering include an extra 7/6 to cover Carriage and Insurance.

PRICES FOR THE "5-10" ARE SUBJECT TO **£16.0** EXTRA IF THE PARTRIDGE TRANSFORMER IS REQUIRED.

COMPLETE MULLARD 3-3

THE IDEAL AMPLIFIER FOR A SMALL HIGH QUALITY INSTALLATION

COMPLETE KIT OF PARTS **£7.10.0**

Alternatively supplied ASSEMBLED and FULLY TESTED **£8.19.6**

(plus 6/6 coverage and insurance) H.P. Terms : Deposit **£2.0.0** and 8 Months at **£1.0.0**. Developed from the very popular 3-valve 3-watt design. Complete to MULLARD'S SPECIFICATION including Mullard valves and a PARMEKO OUTPUT TRANSFORMER.

Only new HIGH GRADE Specified Components and MULLARD VALVES are supplied.


MULLARD — STERN STEREO DESIGNS

DUAL "3-3" MAIN AMPLIFIER

Comprises two "3-3" MAIN AMPLIFIERS (described above) on one chassis and is designed to operate with our DUAL CHANNEL PRE-AMPLIFIER for both STEREOPHONIC or MONAURAL operation.

PRICE : COMPLETE KIT OF PARTS **£10.0.0**

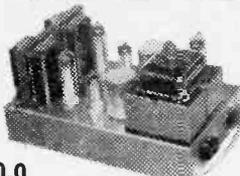Alternatively ASSEMBLED AND TESTED **£11.15.0** H.P. Terms: Deposit **£2-7-0** & 12 months at **17/4**. Its output power is 6 watts (3 watts per channel) and together with our PRE-AMPLIFIER provides a very acceptable STEREO installation.



DUAL CHANNEL PRE-AMPLIFIER

This model incorporates two 2-valve Pre-Amplifiers (described above) combined into a Single Unit, enabling it to be used for both STEREOPHONIC or MONAURAL operation. It is designed primarily to operate with our range of MULLARD MAIN AMPLIFIERS but will also operate equally well with any make of Amplifiers requiring an input of 250 mv/ohms.

COMPLETE KIT OF PARTS **£12.10.0** ASSEMBLED AND TESTED **£15.0.0**

It will operate equally well for MONAURAL only operation with one "3-3" or one "5-10" Main Amplifier to which the second Main Amplifier can at any time be added, thus very easily providing for both STEREO or MONAURAL reproduction. Recommended combinations for STEREO operation:

- The DUAL CHANNEL PRE-AMPLIFIER together with the Dual "3-3" MAIN AMPLIFIER
 - The DUAL CHANNEL PRE-AMPLIFIER together with two "5-10" MAIN AMPLIFIERS.
- THE ASSEMBLY MANUAL is available for 2/6.




COMPLETE STEREO AMPLIFIER

A thoroughly recommended design that very effectively meets the many requests for a low-priced but good quality DUAL CHANNEL STEREOPHONIC AMPLIFIER. PRICE : COMPLETE KIT OF PARTS **£8.10.0**

ALTERNATIVELY ASSEMBLED AND TESTED **£10.10.0**

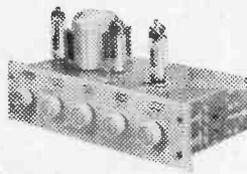Two MULLARD ECL82 Triode Pentode Valves are incorporated in the design; they form a "CLASS A" single-ended output stage in each channel. The input sensitivity is 90 mv/ohms, therefore when used with most STEREO Crystal Pick-Ups, or Radio Tuning Units, an output of 2 watts per channel is achieved, or similarly when switched to MONAURAL Pick-Up position a combined output of 4 watts is produced.



Please enclose S.A.E. if ILLUSTRATED and DESCRIPTIVE LEAFLETS are required... alternatively the COMPLETE ASSEMBLY MANUALS are available at 1/6 each.

STERN RADIO LTD.

Stern's "fidelity" TAPE RECORDERS

BEFORE YOU BUY—YOU SHOULD HEAR THESE RECORDERS. THEY ARE COMPARABLE TO THE MUCH HIGHER PRICED MODELS

- MODEL CR3/S.** Incorporates the New COLLARO "STUDIO" TWIN TRACK 3-Speed Deck H.P. Terms: Deposit £8.4.0 and 12 months of £3.0.2. **£41.0.0**
- MODEL CR3/T.** Incorporates the very popular 3-Speed COLLARO Mk. IV "TRANSCRIPTOR" Deck which has both upper and lower tape tracks..... **£49.10.0**
H.P. Terms: Deposit £9.18.0 and 12 months of £3.12.7.
- MODEL TR3/Mk. VI.** Incorporates the New TRUVOX Mk. VI TWINTRACK 2-Speed Tape Deck **£49.10.0**
H.P. Terms: Deposit £9.18.0 and 12 months of £3.12.7.



Each Model incorporates the highly successful HF/TRJ Amplifier (described opposite) thus ensuring truly "Hi-Fi" record and playback facilities.

All prices quoted provide for the COMPLETE RECORDER including CRYSTAL MICROPHONE and 1,200 ft. Spool of Tape.

There are no better value for money Tape Recorders on the market—if you can't call and hear them, send S.A.E. for fully descriptive leaflets.

!! RADIOGRAM CHASSIS !!

- ARMSTRONG MODEL AF/208**..... **£23.2.0**
7 valve AM/FM Chassis producing Max. 5 watts output.
- ARMSTRONG "STEREO TWELVE"**..... **£37.16.0**
The most complete AM FM unit yet produced for Stereo, giving 6 watts high-fidelity push-pull output on each channel. 12 watts for monaural.
- ARMSTRONG "JUBILEE"**..... **£29.8.0**
An AM/FM chassis with nine valves and with push-pull output stage providing 6 watts.
- ARMSTRONG AM/FM "STEREO 44"**..... **£28.7.0**
Provision is made for Stereo and monaural playback from pick-up or tape. Outputs provided for Stereo or Monaural tape recordings.

RADIO TUNING UNITS

- DULCI MODEL FMT/2**..... **£19.17.6**
A complete self-powered F.M. Tuner incorporating automatic frequency control.
 - ARMSTRONG "S.T.3" AM/FM UNITS**..... **£27.6.0**
A self-powered high-fidelity Tuner covering full VHF, medium, and long wavebands with automatic frequency control on VHF.
 - DULCI "H4/T" AM/FM UNIT**..... **£23.15.8**
A 4 waveband self-powered high-fidelity tuner covering the VHF/FM trans-missions plus the long, medium and short wavebands.
- NEW HIRE PURCHASE TERMS** are available on all above. Illustrated leaflets available—send S.A.E. (Carr. and Ins. 5/- extra.)

A SPECIAL CASH ONLY OFFER !!

This very attractive **PORTABLE AMPLIFIER CASE** together with a good quality **GRAM AMPLIFIER** and a matched **P.M. SPEAKER**.
ALL for ONLY **£8.7.6** (Plus 7/6 Carr. & Ins.)
The Amplifier consists of a 2-stage design incorporating 3 modern B.V.A. valves and has separate **BASS** and **TREBLE CONTROLS**. The Portable Case will also accommodate almost any make of Autochanger and is attractively finished in Mushroom Grey Rexine. **WE ALSO SUPPLY SEPARATELY**:
(a) The 2-stage (plus Rectifier) **AMPLIFIER** **£4.2.6** (b) **THE PORTABLE CARRYING CASE** **£3.17.6**
(c) **P.M. SPEAKER 18/9** Carriage and Insurance 4/- extra.




— SPECIAL CASH ONLY BARGAIN —

A bulk purchase enables us to offer a very useful **INTERCOM SET OR BABY ALARM** for only **£5.5.0** (Plus 5/- carriage & Insurance).
Consists of **MASTER UNIT** and one **EXTENSION**, providing 2-way **TALK-LISTEN** facility. Complete in polished wood cases, size of each only 7 1/2 x 4 1/2 x 6 in. high.


STERN'S MK. II "fidelity" F.M. TUNING UNIT

PRICE £14.5.0 (Plus 5/- Carr. and Ins.)
HIRE PURCHASE: Deposit £2.17.0 and 12 Monthly Payments of £1.0.11
Incorporates the latest **MULLARD PERMEABILITY TUNING HEART** and the corresponding **MULLARD VALVE LINE-UP**. A really first-class Tuner, very attractively presented and comparable to many offered at much higher prices. Power consumption is only 15 amps. at 6.3 volts and 25 m/a at 250 volts.
HOME CONSTRUCTORS! YOU CAN BUILD THIS TUNING UNIT FOR ONLY £10.10.0 (Plus 5/- Carr. & Ins.) Please send S.A.E. for fully descriptive leaflet, or the Assembly Manual is available for 1/6.

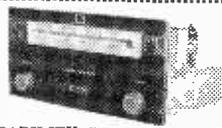

!! RECORD PLAYERS !! THE LATEST MODELS ARE IN STOCK MANY AT REDUCED PRICES !!

- SEND S.A.E. FOR ILLUSTRATED LEAFLET
B.S.R. MONARCH UA8 4-speed mixer Autochanger with Crystal Pick-up..... **£6.12.6**
- The **NEW COLLARO MODEL RP594** 4-speed Single Record Player. Studio Cartridge **£9.18.9**
- The **COLLARO "CONQUEST"** 1-speed Autochanger, Studio Pick-up..... **£7.10.0**
- The latest **COLLARO "CONTINENTAL"** 4-speed MIXER Autochanger Studio "O" Pick-up..... **£8.10.0**
- The **COLLARO** 4-speed Single Record Player, Studio Pick-up..... **£6.6.0**
- THE NEW B.S.R. Model UA12** is in Stock. A 4" **"SPEED" MIXER AUTOCHANGER**..... **£8.7.6**
UA12 also available incorporating the **B.S.R. STEREO** Pick-up, plays L.P. and 78 Records..... **£10.10.0**
- B.S.R. MODEL TU9** 4-speed Single Record Player, complete with separate Crystal Pick-up..... **£4.4.0**
- GARRARD MODEL TA/Mk. 11** 4 Speed Player fitted high output Crystal Pick-up..... **£8.10.0**
- GARRARD MODEL RC/121/4**. Autochanger 4 speeds. High Output. Crystal Pick-up..... **£10.0.0**
Carriage and Insurance on each above. 5/- extra.

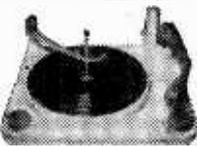

"Hi-Fi" LOUDSPEAKERS WE HAVE IN STOCK A COMPLETE RANGE BY GOODMANS—WHARFDALE—W.B.

- And will be pleased to send you Illustrated and Priced Leaflets. Recommended Types are:
- GOODMANS "AXIOM 300"**. The Best 12in. Seller. 15 ohms V/Coil..... **£11.5.9**
 - GOODMANS "AXLETTE"** 8in. 3 or 15 ohms..... **£6.12.0**
 - W.B. "STENTORIAN" H.F. 816**. 8in. 3 or 15 ohms..... **£6.10.6**
 - W.B. "STENTORIAN" H.F. 1016**. 10in. 3 or 15 ohms..... **£7.12.3**
 - W.B. "STENTORIAN" H.F.1214**. 12in. 15ohms..... **£9.15.6**
 - WHARFDALE "SUPER 8 FS/A1"**. 8 in. 3 or 15 ohms..... **£6.19.11**
 - WHARFDALE "GOLDEN FSB"**. 10in. 3 or 15 ohms. Voice Coil..... **£7.13.3**
 - WHARFDALE "W12/Fs"**. 12in. 15 ohms. Voice Coil..... **£10.5.0**
 - WHARFDALE "SUPER 12/Fs/AL"**. 12in. 15 ohms. Voice Coil..... **£17.10.0**
- LOUDSPEAKER ENCLOSURES, TWEETER UNITS, CROSSOVER UNITS** are also available.

HOME CONSTRUCTOR

A RANGE OF "EASY TO ASSEMBLE" PREFABRICATED CABINETS. Designed by the **W.B. "STENTORIAN" COMPANY** for "Hi-Fi" Loudspeaker systems or to accommodate high-quality equipment. The acoustically designed **Bass Reflex Cabinets** containing the very successful "Stentorian" Speakers give really first-class reproduction and are well recommended. Models are also available to accommodate high-quality Amplifiers, Pre-amplifiers, Tuning Units, Record Players, etc. All models are very easily assembled, in fact, only a screwdriver is required. Fully illustrated leaflets are available, including complete specifications of the various **STENTORIAN LOUDSPEAKERS**.

109 & 115 FLEET ST., LONDON, E.C.4
Telephone: FLEET STREET 5812/3/4
PLEASE ENCLOSE S.A.E. WITH ALL ENQUIRIES.

Let I.C.S. train YOU!



COURSES ON:—

- RADIO and TELEVISION
- SERVICING ELECTRONICS

EXAMINATION COURSES FOR:—

- C. & G. Radio Servicing Certificate (R.T.E.B.)
- C. & G. Radio Amateurs' Exam. (Amateurs' Transmitting Licence)
- British Institution of Radio Engrs., etc. C. & G. Telecom Technicians.


Whether you plan to have your own business, to become an electronics engineer or to take up a career in industry, an I.C.S. Course will help you to succeed. You learn at home in your own time, under expert tuition. Moderate fees include all books.

LEARN - AS - YOU - BUILD


Practical Radio Course

A basic course in radio, electronic and electrical theory backed by thorough practical training. You build a 4-valve T.R.F. and a 5-valve superhet radio receiver, signal generator and multi-tester.

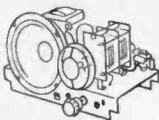Other Learn-as-you-Build radio courses are available



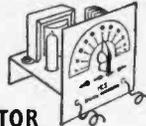MULTI-TESTER
(Sensitivity 1,000 ohms per volt)



- 5-VALVE SUPERHET RECEIVER
- RF/AF SIGNAL GENERATOR

Post this Coupon TODAY! for FREE book on careers in Radio, etc., and full details of I.C.S. Courses.

INTERNATIONAL CORRESPONDENCE SCHOOLS

(Dept. 171J), Intertext House, Parkgate Road, London, S.W.11.

Name..... Age.....
(Block Letters please)


Address.....

Occupation..... I-60

INTERNATIONAL CORRESPONDENCE SCHOOLS

Build your own TAPE RECORDER "ASPDEN"

Tape Deck and Amplifier Kits

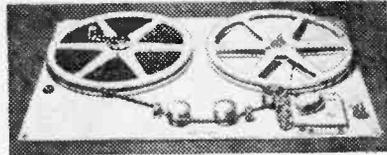

TAPE DECKS. 2-speed, twin track, easy to assemble kits with finest motor. Ferroxcube heads and full instructions.

- Model 582 for 5in. spools, kit £9.5.0
- Model 782 for 7in. spools, kit £9.5.0
- Either model assembled and tested, 30/- extra.

AMPLIFIER kit. 2½ watt. record/replay, 2 recording positions, neon indicator, etc., £5.18.0. Power Pack kit for above. £2.18.6 (both without valves). Carr. and packing extra.

Mr. R. White of Omagh, N. Ireland, writes: "The performance of the recorder is very good, and I recommend it to all those who wish to get first class performance at approx. half the cost."

Send STAMP for full particulars to:—

W. S. ASPDEN Stanley Works, Clevedon Road, Blackpool, Lancs.

SOUTHERN RADIO'S WIRELESS BARGAINS

- ATTACHMENTS for "18" Transreceivers. ALL BRAND NEW. HEADPHONES, 15/6; HAND MICROPHONE, 12/6; AERIALS, 5/-; SET OF 6 VALVES, 30/-.
- CONDENSERS. 100 Assorted. Mica, Tubular, etc. NEW, 15/-.
- CONTACTOR TIME SWITCHES. 2 impulses per sec., in case 11/6
- REMOTE CONTACTOR. For use with above. 7/6
- LUBBRA HOLE CUTTERS. Adjustable 2" to 3½". For Metal, Plastic, etc. 7/-
- MAGNETS. Strong Bar Type. 2" x 1½". 1/6 each.
- MORSE PRACTICE SET. TAPPER with BUZZER on Base. Complete with Battery. BRAND NEW 12/6
- MORSE TAPPERS. Midget Type, 2/9. Standard, 3/6. Heavy Type on Base, 5/6. ALL BRAND NEW.
- PACKARD-BELL AMPLIFIERS. Complete BRAND NEW with Valves; Relay, etc., etc. 17/6 each.
- QUARTZ CRYSTALS. Types F.T.241 and F.T.243, 2-pin. ½ Spacing. Frequencies between 5,675 Kc/s and 8,650 Kc/s. (F.T. 243) 20 Mc/s. and 38.8 Mc/s. (F.T.241) 54th Harmonic, 4/- each. ALL BRAND NEW. TWELVE ASSORTED CRYSTALS, 45/-.
- HOLDERS for both types, 1/- each. Customers ordering 12 crystals can be supplied with lists of frequencies available for their choice.
- RECORDING BLANKS. New "Emidisc," ready for use. 13" 6/- each. Quantity of 15 in metal case £4.
- RESISTANCES. 100 Assorted useful values. New wire end, 12/6.
- SPECIAL OFFER. 12 ASSORTED METERS. Slightly damaged. Mainly broken cases (perfect movements). Including 3 Brand New Aircraft Instruments. 12 for 45/-.
- STAR IDENTIFIERS. Type I A-N Covers both Hemispheres. 5/6.
- TI154 TRANSMITTERS. Complete, NEW condition, in Transit case. £2.5.0
- TRANSPARENT MAP CASES, Plastic. 14" x 10½". Ideal for Maps, Display, etc. 5/6
- TRANSRECEIVERS. Type "38" complete with 5 valves, etc. New condition, untested by us, but serviceable, no guarantee. 22/6 each.
- ATTACHMENTS for Type "38" Transreceivers. ALL BRAND NEW. PHONES, 15/6; THROAT MICROPHONES, 4/6; JUNCTION BOXES, 2/6; AERIALS, No. 1, 2/6; No. 2, 5/-; WEBBING, 4/-; HAVERSACKS, 5/-; VALVES, A.R.P.12, 4/6; A.T.P.4, 3/6. Set of FIVE VALVES, 19/- the set.
- POST OR CARRIAGE EXTRA. FULL LIST OF RADIO BOOKS, etc. 3d.

SOUTHERN RADIO SUPPLY LTD.

11, LITTLE NEWPORT ST., LONDON, W.C.2. GER. 6653

guaranteed Tubes

REGUNNED NEW

THAT SECOND SET? MOST MAKES IN STOCK

ALL GUARANTEED 12 MONTHS

CRM92, MW22-7, MW22-14, MW22-14C, MW22-18, CRM121, CRM121A, CRM122, MW31-14C, MW31-17, MW31-18, 121K, 141K, AW38-21, C14FM, CRM141, CRM142, MW31-18, MW31-74, ME36-24, MW36-44, C17FM, CRM171, CRM172, MW43-84, MW43-89, C14BM, C17BM, CRM151, CRM152A, CRM152B, CRM153, MW43-50, MW41-1, MW53-20, MW53-50	£2/15/-	£3/5/-	£3/15/-	£4/10/-	£5/5/-	£6/15/-
	£5/10/-	£7/19/-	£8/19/-	£9/10/-		

12" — £3.19.

14" — £7.10.

CARRIAGE FREE

BUT

AT CUSTOMER'S RISK

NEW TV TUBE : SPECIAL OFFER 108K : £2/19/-

100 CONDENSERS 10s.

A must for your spare box. A well-balanced assortment of miniature silver mica and ceramic condensers. 3-10,000 pF. List value over £5.

GUARANTEED P.M. SPEAKERS.
Standard 3 ohms, ex-equipment, tested top notes, performance guaranteed.

4 1/2" 7/- 5 1/2" 11/- 10 1/2" 13/-
8 1/2" 7X 10X6

EXTERNAL I.T.V. CONVERTERS WITH INTERNAL POWER PACK.

Well-known make at a very competitive price, completely enclosed. Finished in hammered gold. Very compact. Can be put into practically all T.V.s. Galn and Trimming controls. Listed at £7.7.0. Our Price, Carr. 2/6. **£3/10/-**

FAMOUS MAKE KITS

AMPLIFIER, £5.15.0. F/M £5.19.0.

LINE OUTPUT TRANSFORMERS

Most types ex-equipment. From 10/-.

TUNING CONDENSERS .005 twin gang, 4/-.

INFRA RED HEATERS

1,300 w. : 2ft. 9in. long..... £3. 5
2,000 w. : 2ft. 9in. long..... £3.15
3/- carriage & packing.

100 RESISTORS 7s. 6d.
A WELL-BALANCED SELECTION—A MUST

H.T. RECTIFIERS

280LUT79A (240 v. 80 mA.), 5/-, R.M1, 6/-, R.M2, 6/6, R.M3, 9/-, R.M4 (ER.4), 15/6, R.M5 (ER.5), 21/-, 14A86, 17/-, 14A97, 23/-, 14A100, 25/-, 18RA, 1-1-16-1, 7/9, 14RA 1-2-8-2, 18/-, 18R1, 2-2-8-1, 14/-, 14RA 1-2-8-3, 22/-.

BURWELL T.V. AERIALS. Complete Illustrated Price List of 1 to 12 element Band I and III aerials at amazing competitive prices (3d. stamp).

TRANSISTORS AND DIODES

RED SPOT. Transistors for I.P., L.P. and Output up to 800 kc/s, 5/- ea. (4/3 each in dozens). **WHITE SPOT.** R.F. and I.P. 2.5 Mc/s, 7/6 (7/- each in dozens). **KA103, 15/-; KA104, 17/6; XB104, 10/-; GEX15, 25/-; V15/10P "GOLTOP" 15/-.**

GERMANIUM DIODES. General purpose famous make. 8d., 8/- doz.

DIODES. Equivalent to GEX44, 3/9.

B.S.R. MONARCH UA8

4-speed mixer Autochanger..... **£7.19.6**

COLLARO "CONQUEST"

Hi-Fi 4-speed, 10 record Autochanger. Brand new, unused. **£6/19/6** Limited Quantity

or Carlon containing **£13/-/-**
2 Players

STEREO :

Famous make single player. Stereo equipped. Unrepeatable at **£6/19/-** Carr. 3/-

4-SPEED RECORD PLAYERS

Latest Turntable, together with lightweight Star Galaxy dual sapphire crystal turnover pick-up head. Truly amazing value. **£3/10/-** Carr. 3/-

A RADIO SET, complete 29/-

6KT, 6K9, 6Q7, 6V6 with Speaker plus 5/- and 6-volt vibrator pack. Suitable for carriage, adaptation as car radio.

TRANSMITTER POWER PACKS.

230V. A.C. 2 separate smoothed outputs 375, 550 or 620 v. 200/250 mA., 6.3 v. 5 a. Boxed. 4 5U4G, £7/10/-, Less valves £6/10/-.

VALVES ALL GUARANTEED 3 MONTHS SOLED, AMAZING PL81 VALUE AT ONLY 7/-

EY51 SHORT ENDS 7/- U25 SHORT 7/- ENDS

PICK-UP CARTRIDGE

ACOS. 22/6. POWER POINT, 18/6.
STEG and REUTER, 15/-, SONOTONE, 17/6

CO-AXIAL CABLE

Semi-Air-Spaced low loss. 1-19 yds., 7d. per yd., p. & p. 1/3. 20-30 yds., 6d. per yd., p. & p. 1/9

50 YARD DRUMS 22/6. P. & P. 2/-
100 YARD DRUMS 40/- P. & P. 3/-

PRICES REDUCED

GUARANTEED 3 MONTHS. 24 HOUR SERVICE
FREE TRANSIT INSURANCE. All valves are new or fully guaranteed ex-Government or ex-equipment origin. Satisfaction or Money Back Guarantee on goods if returned unused within 14 days. S.A.E. FOR LIST OF 800 TYPES.

10% DISCOUNT SPECIAL OFFER

TO PURCHASERS of any SIX VALVES marked in black type (15% in dozens). Post : 1 valve, 6d., 2-11, 1/-.

EF91	4/-	KT263	5/-	ISU2150A	UF85	9/6	
EF92	4/9	L63	2/9		UF86	18/-	
EF95	6/6	LN152	8/6	T41	7/6	UF89	8/6
EL32	9/-	LN300	11/6	U15	9/-	UL41	7/6
EL33	9/-	LZ319	7/9	U22	6/6	UL44	12/6
EL38	12/6	MU14	8/-	U24	7/6	UL46	9/6
EL41	9/6	N37	11/-	U25	12/-	UL54	8/6
EL42	9/6	N78	15/-	U26	12/-	UM80	9/6
EL43	8/3	N108	11/-	U31	7/9	UU6	9/6
EL45	11/-	P41	4/6	X33	11/-	UU7	9/6
EL49	4/9	P81	2/3	U35	8/6	UU8	16/6
EL55	9/6	PC84	7/9	U50	6/-	UU9	7/-
EM34	9/3	PC85	9/6	U52	6/3	UY41	6/6
EM80	9/3	PC89	18/-	U78	6/-	UY85	7/3
EM81	9/3	PCF80	7/9	U191	9/6	VR150/30	
EM84	10/6	PCF82	9/9	U201	9/6		7/-
EM85	10/6	PC82	10/-	U231	9/6	W91	9/6
EN31	18/-	PL183	11/6	U301	9/6	W61M	9/6
EY51	9/6	PL84	12/6	U310	7/6	W76	6/6
		Small	9/6	PN25	5/-	U329	12/6
				PN45	7/6	U339	9/6
				PN46	8/6	U403	9/6
				PN47	8/6	U408	9/6
				PN48	8/6	U409	9/6
				PN49	8/6	U410	9/6
				PN50	8/6	U411	9/6
				PN51	8/6	U412	9/6
				PN52	8/6	U413	9/6
				PN53	8/6	U414	9/6
				PN54	8/6	U415	9/6
				PN55	8/6	U416	9/6
				PN56	8/6	U417	9/6
				PN57	8/6	U418	9/6
				PN58	8/6	U419	9/6
				PN59	8/6	U420	9/6
				PN60	8/6	U421	9/6
				PN61	8/6	U422	9/6
				PN62	8/6	U423	9/6
				PN63	8/6	U424	9/6
				PN64	8/6	U425	9/6
				PN65	8/6	U426	9/6
				PN66	8/6	U427	9/6
				PN67	8/6	U428	9/6
				PN68	8/6	U429	9/6
				PN69	8/6	U430	9/6
				PN70	8/6	U431	9/6
				PN71	8/6	U432	9/6
				PN72	8/6	U433	9/6
				PN73	8/6	U434	9/6
				PN74	8/6	U435	9/6
				PN75	8/6	U436	9/6
				PN76	8/6	U437	9/6
				PN77	8/6	U438	9/6
				PN78	8/6	U439	9/6
				PN79	8/6	U440	9/6
				PN80	8/6	U441	9/6
				PN81	8/6	U442	9/6
				PN82	8/6	U443	9/6
				PN83	8/6	U444	9/6
				PN84	8/6	U445	9/6
				PN85	8/6	U446	9/6
				PN86	8/6	U447	9/6
				PN87	8/6	U448	9/6
				PN88	8/6	U449	9/6
				PN89	8/6	U450	9/6
				PN90	8/6	U451	9/6
				PN91	8/6	U452	9/6
				PN92	8/6	U453	9/6
				PN93	8/6	U454	9/6
				PN94	8/6	U455	9/6
				PN95	8/6	U456	9/6
				PN96	8/6	U457	9/6
				PN97	8/6	U458	9/6
				PN98	8/6	U459	9/6
				PN99	8/6	U460	9/6
				PN100	8/6	U461	9/6


VALUES

Post : 2 lbs., 1/6. 4 lbs. 2/-, 7 lbs. 2/9, 15 lbs. 3/6.

No C.O.D. Callers always welcome (E.C. Weds.)
ALL ITEMS LESS 5% AND POST FREE IN DOZENS.

TECHNICAL TRADING CO. P.O. BOX 21(P), 350-352, FRATTON ROAD, PORTSMOUTH

NEW! EASY-TO-BUILD AND

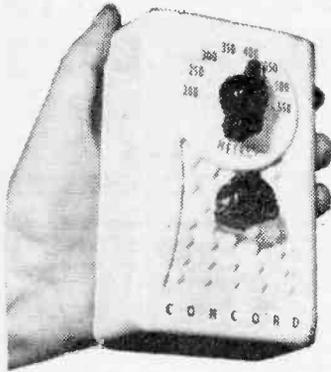

The new, exciting De Luxe "Gold Star" Pocket Radio in beautiful moulded plastic case—choice of four lovely colours, Red, Green, Blue and Pink. This model is a highly sensitive, self-contained set covering all medium waves. Uses modern miniature "button-base" valve and specially designed high efficiency coil. Exceptionally easy to build from our step-by-step plans—the case is supplied ready drilled! Size of radio only 4in. x 2½in. x 1½in. —and batteries fit inside. We can supply all parts including case, detachable aerial, instruction book, screws, wire, etc., for only 48/- plus 2/- Post and Packing. C.O.D. 2/- extra. (Parts sold separately, priced parts list 1/9.)



Our engineers have designed a novel Wrist-Watch Radio using latest Transistor Techniques. Size only 1½in. x 1in. x ½in. !!!—"Feather-weight"—yet gives clear, crisp, personal-phone reception over all medium waves. Tiny battery inside lasts months—costs 5d. No Snags, anyone can build it in an hour or two using our pictorial step-by-step simple plans. All parts supplied (including case and strap) for only 29/6 (add 2/6 Post, etc.). C.O.D. 2/- extra. (All parts sold separately, priced parts list 1/6.) Send Now!


Choice of beautiful walnut veneered cabinet or ivory bakelite. This is the lowest possible price consistent with high quality. No radio knowledge whatever needed



... can be built by anyone in 2-3 hours, using our very simple, easy-to-follow diagrams. The terrific new circuit of the "Ocean-Hopper" covers all medium and long waves, has razor-edge selectivity and exceptionally good tone. Price also includes ready drilled and punched chassis, set of simple-to-follow plans—in fact everything! Parts tested before despatch! Uses standard octal-base valves. (Low running costs—approximately 18 watts.) Size 12in. x 6in. x 5in. Build this long-range powerful midget NOW. TOTAL BUILDING COST INCLUDING PLANS, ETC. 45/7.6. (Post and Packing 3/6.) Parts sold separately. Priced parts list and plans, 1/9. C.O.D. 2/- extra.



This amazing "Tiny-Tim" model—no larger than a matchbox—costs nothing to run—ever! No batteries! No Valves! No electricity! Will never run down or burn out. Uses the latest TRANSISTOR TYPE GERMANIUM DIODE, receives local stations anywhere—without extra aerial. Clear, Crisp Tone. No snags, anyone can build it within an hour using our step-by-step instruction book, etc., for only 17/6, plus 1/6 Post and Packing (C.O.D. 2/- extra). (Parts sold separately, priced parts list 1/9.)

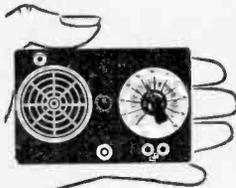

THIS TRANSISTOR SET Can Be Built For Only 29/6. The "Sky-Scout" Pocket two-stage transistor set, size only 1in. x 3½in. x 4½in. Covers all medium waves and works entirely off tiny "penlight" battery which costs 6d. and fits inside case. All parts tested before despatch. Can be built for 29/6, plus 2/- Post and Packing, INCLUDING CASE, TRANSISTOR, STEP-BY-STEP


PLANS FOR ABSOLUTE BEGINNERS, nuts, bolts, etc. (C.O.D. 2/- extra.) Parts sold separately, priced parts list and plans, 1/6. VERY SIMPLE TO BUILD.



Learn Electricity by building a low cost Concord Model! Concord models include the latest electronic advances and are constantly being modernised by Concord's own research department. Concord designs are years ahead. Every latest advance finds its way into the educational and highly practical Concord Models. Special instruction books describe minutely every step in the assembly. Build, Learn from AND USE Concord Designs. TRADE ENQUIRIES INVITED. WE BULK PURCHASE ELECTRONIC COMPONENTS AND EQUIPMENT.

ADDRESS ON OPPOSITE PAGE →

FUN-TO-MAKE CONCORD RADIOS

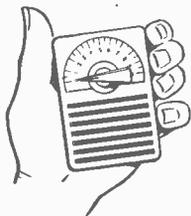

Postage, etc., 2/- (C.O.D. 2/- extra.) (Parts sold separately. Priced parts list and plans 1/6.) RUSH YOUR ORDER TODAY!

TWO-TRANSISTOR POCKET SET. Can Be Built for 45/-. BUILD THE "SKYGNOME" VEST-POCKET TWO TRANSISTOR RADIO which gives a superb performance and is highly sensitive. Weight under 7 ozs.—yet it is a THREE-STAGE receiver covering all medium waves, working entirely off a "penlight" battery. Every part tested before despatch! SPECIAL STEP-BY-STEP PLANS FOR ABSOLUTE BEGINNERS. Total building cost including case, transistors, etc.—everything down to the last nut and bolt—ONLY 45/- with plans.

BUILD THIS POCKET RADIO

Can Be Built for 39/6.

Anyone can build this beautiful precision Pocket Radio in an hour or two. No knowledge whatever needed. Our simple pictorial plans take you step-by-step! Remarkably sensitive—covers all medium waves, inc. Luxembourg, Home, Light. Size only 2in. x 3in. x 5 1/2in.—Not a Toy! But a Real, Personal-phone, Valve Radio With Detachable Aerial! IDEAL FOR BEDROOM, GARDEN, etc. We supply ALL parts necessary, together with plans, etc., for the special price of 39/6, plus 2/6 post and packing. (C.O.D. 2/- extra.) BUILD YOURS NOW! (All parts sold separately, priced parts list 1/9.) Send Today! Money refunded if parts returned intact within 7 days.



The "COMPANION" PRINTED CIRCUIT POCKET SET.

BUILD THIS 3 TRANSISTOR POCKET RADIO... PRINTED CIRCUIT VERSION! The "Companion" is comparable in sensitivity to a three-valve battery set. It is exceptionally small in size (4 1/2in. x 3in. x 1 1/2in.) and is a self-contained pocket radio that does not need aerial or earth. It has built-in speaker and covers medium and long waves. This unique little set can be built FOR ONLY 97/6. EVERYTHING INCLUDED! (Plus post and packing 2/6.) All parts sold separately, price list, etc. 6d. C.O.D. 2/- extra.

LIMITED QUANTITY ONLY!

Never before such amazing value! A high grade universal testmeter. Large scale (3 1/2in.), highly sensitive movement (500 MicroAmps!) Measures A.C. Volts, D.C. Volts, D.C. Current, Ohms, Decibels, Inductance and Capacitance! Ranges: D.C. Volts—0-10 v., 50 v., 250 v., 500 v., 1,000 v. A.C. Volts—0-10 v., 50 v., 250 v., 500 v., 1,000 v. D.C. Current—0-500 MicroAmps, 25 MilliAmps, 250 MilliAmps. Resistance—0-10 K ohms and 1 Megohm. Decibels—20 dB. to + 22 dB. and - 20 dB. to - 36 dB. Capacitance—100 pfd. to 0.6 mfd. Inductance—10 to 1,000 Henries (also with external D.C. voltage will measure to 100,000,000 ohms!). A beautiful, strongly-made instrument. Brand New, not a kit, at only 97/6, including test prods, instruction book and internal batteries (replacements cost only 6d. each). Plus 2/6 Post and Packing. (C.O.D. 2 - extra.)




Can Be Built for 47/6. Build this exceptionally sensitive high efficiency personal phone radio. Uses unique assembly system and can be built by anyone without any radio knowledge whatever in 45 minutes. Handsome black-crackle steel case with specially made

black and gold dial with stations printed. Size of radio only 6 1/2in. x 5in. x 3in. Covers all medium and long waves. H.T. consumption only 1 to 1.5 mA. Ideal for Bedroom, Garden, Holiday, etc. BUILD THE "SKYROMA" NOW! Total building cost—everything down to the last nut and bolt, 47/6 (Postage, etc., 2/-)—with full set of clear, easy-to-follow plans. (Parts sold separately. Priced parts list and plans 1/6.) C.O.D. 2/- extra.



The sensational "Silvertone" model! A highly compact self-contained miniature "button-base" valve pocket radio at absolute "rockbottom" build-

ing cost! Covers all the medium waves with the very latest circuitry bringing in stations from all over Europe—without fuss. Easy as A.B.C. to assemble, using our step-by-step instruction manual. Size only 4 1/2in. x 2 1/2in. x 1 1/2in.—a fascinating little pocket radio. We can supply all the parts including beautiful two-tone case, detachable aerial, instruction book, screws, wire, etc., for only 29/6 (plus 2/- post and packing). C.O.D. 2/- extra. (Parts sold separately, priced parts list 1/9.)

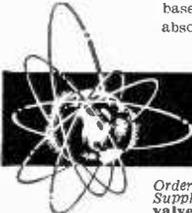

CONCORD ELECTRONICS

210, Church Road, Hove, Sussex

Dept. PW14

Orders receive prompt attention. Cheques accepted, Cash on delivery 2/- extra. Please print name and address in block letters. Suppliers to Schools, Universities, Government and Research Establishments. Complete range of components and valves stocked. Regret no C.O.D. abroad.

RETURN-OF-POST SERVICE

NEW ILLUSTRATED LISTS

New illustrated lists are available on all the following. Any will be sent free upon request.

GRAMOPHONE EQUIPMENT. Details of many types of Auto Changers, Single Record Players and Transcription Units including all the latest models. Many at special prices.

TEST GEAR. Test meters, Signal Generators, etc., by AVO, Jason, Pullin and Taylor.

LOUDSPEAKERS. Full details of Goodmans, Whiteley, Wharfedale and Elac types.

TAPE DECKS. All popular makes with a special offer.

RECORDING TAPES. A very wide range of all tapes and accessories.

LATEST AVO TEST METERS



AVOMETER MODEL 8. The finest multi-range meter available. 20,000 ohms per volt on D.C. ranges. Eight D.C. Voltage ranges 2.5 v. to 2,500 v. Seven D.C. current ranges 50 microamps, to 10 amps. Seven A.C. Voltage ranges 2.5 v. to 2,500 v. Four current ranges 100 mA. to 10 amps. Three resistance ranges. Fully detailed leaflet available. Price £23.10.0. H.P. Deposit £4.14.0 and 12 monthly payments of £1.14.6. Price with leather carrying case. £27.8.0. H.P. Deposit £5.8.0 and 12 payments of £2.0.4.

Other AVO Meters available include the Model 7, £19.10.0. H.P. Deposit £3.18.0 and 12

Multimor price £9.10.0. H.P. Deposit £1.18.0 and 12 monthly payments of 14'4.

TRANSISTORS

All at the new reduced prices.

AUDIO. B.T.H. Red Spot 7/6. G.E.C. Yellow/Green. 7/6. BRIMAR. TSI. 10'-. TS2. 21'-. TS3. 13/6.

EDISWAN. XB102. 10'-. XB104. 10'-. MULLARD. OC70. 14'-. OC71. 14'-. GOLDTOP. V10/15A. 15'-. AUDIO OUTPUT. Matched Pairs. Mullard OC72. 34'-. Ediswan XC101. 32'-. R.F. G.E.C. Yellow/Red. 15'-. EDISWAN. XA101. 23'-. XA102. 26'-. XA103. 15'-. XA104. 18'-. MULLARD. OC44. 28'-. OC45. 23'-. All transistors post free.

OUTPUT TRANSFORMERS

We can supply a wide range of High Quality Output Transformers and full details are given below. All are fitted with sectionalised secondaries and can be connected for either 3 or 15 ohm speakers.

PARTRIDGE

P3591A. Ultra Linear. Push Pull EL84. 20% Taps. 7,000 ohm load. Specified for GEC 912. 99'-. P5202. Ultra Linear. Push Pull EL84. 43% Taps. 7,000-9,000 ohm load. Suitable for the Mullard 510. 95'-. P5203. Ultra Linear. Push Pull EL84. 20% Taps. 5,000-7,000 ohm load. Suitable for the G.E.C. 912. 95'-. P4014. "C" Core. Push Pull Ultra Linear EL84. 8,000 ohm load. 43% Taps. Specified for the Mullard 510. 98/6. P4131. Push Pull Ultra Linear EL84. 43% Taps. 8,000 ohm load. Specified for the Mullard 510. 60'-. P3667. Push Pull EL84. 8,000 ohm primary tapped at 6,000 ohms. Specified for the Mullard 510. 52/6.

GISSON

W0562A. Push Pull EL84. Load 8,000 ohms. Specified for the Mullard 510. 50/6. W0696B. Push Pull EL84. Load 6,000 ohms. Specified for the Mullard 510. 50/6. W0710. Push Pull Ultra Linear EL84. Load 7,000 ohms. 20% Taps. Specified for the G.E.C. 912. 55/8. W0710/8K. Push Pull Ultra Linear EL84. Load 8,000 ohms. 43% Taps. Specified for the Mullard 510. 55/6. W0682. Push Pull Ultra Linear EL84. Load 8,000 ohms. 43% Taps. Specified for the Mullard 510. 62/6.

ELSTONE

OT/ML. Push Pull Ultra Linear EL84. 8,000 ohm load. 43% Taps. 45'-. OT/3. Single EL84. 5,000 ohm load. Specified for Mullard 3-3. 25'-. PARMERKO P2641. Single EL84. Load 5,000 ohms. Potted. Specified for the Mullard 3-3. 27'-. PARMERKO

W0696B. Push Pull EL84. Load 6,000 ohms. Specified for the Mullard 510. 50/6.

W0710. Push Pull Ultra Linear EL84. Load 7,000 ohms. 20% Taps. Specified for the G.E.C. 912. 55/8.

W0710/8K. Push Pull Ultra Linear EL84. Load 8,000 ohms. 43% Taps. Specified for the Mullard 510. 55/6.

W0682. Push Pull Ultra Linear EL84. Load 8,000 ohms. 43% Taps. Specified for the Mullard 510. 62/6.

OT/ML. Push Pull Ultra Linear EL84. 8,000 ohm load. 43% Taps. 45'-. OT/3. Single EL84. 5,000 ohm load. Specified for Mullard 3-3. 25'-. PARMERKO

P2641. Single EL84. Load 5,000 ohms. Potted. Specified for the Mullard 3-3. 27'-. PARMERKO

W0696B. Push Pull EL84. Load 6,000 ohms. Specified for the Mullard 510. 50/6.

W0710. Push Pull Ultra Linear EL84. Load 7,000 ohms. 20% Taps. Specified for the G.E.C. 912. 55/8.

W0710/8K. Push Pull Ultra Linear EL84. Load 8,000 ohms. 43% Taps. Specified for the Mullard 510. 55/6.

W0682. Push Pull Ultra Linear EL84. Load 8,000 ohms. 43% Taps. Specified for the Mullard 510. 62/6.

OT/ML. Push Pull Ultra Linear EL84. 8,000 ohm load. 43% Taps. 45'-. OT/3. Single EL84. 5,000 ohm load. Specified for Mullard 3-3. 25'-. PARMERKO


P2641. Single EL84. Load 5,000 ohms. Potted. Specified for the Mullard 3-3. 27'-. PARMERKO

TRANSISTORISE YOUR CRYSTAL SET

A kit to construct a single transistor amplifier for any Crystal Set. Increases the volume many times. No soldering required and full instructions supplied. Complete kit with brand new Transistor. 21/6. Post free.

JASON FM TUNER

FMT1

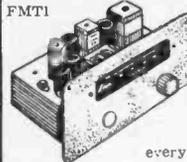

There are no less than four different Jason FM Tuner Kits now available to the Home Constructor. Brief details are given here and individual lists on any are available free.

MOST IMPORTANT. We take great pains to see that the kits we supply are absolutely complete in every detail and also that all components

supplied are entirely suitable in every way. This accounts for differences in price you may notice between our prices and those of some of our competitors. **THIS SHOULD BE BORNE IN MIND WHEN COMPARING PRICES.**

Hire Purchase Terms available. FMT2 & 3

STANDARD TUNERS

STANDARD TUNER, FMT1. The very popular tuner which is supplied with a chassis assembly fitted with a gold hammer finish front panel and glass dial. Employs four EF81 valves. External power supply is required. Complete kit £6.19.6. Power pack kit. 39'-. **STANDARD TUNER IN SHELF MOUNTING CASE, FMT2.** This is a new version of the above tuner. The circuit has been brought up to date and is built into the very attractive five shelf mounting case of the new Fringe Tuner mentioned below. The circuit uses four EF80 valves and the power supply can be built into the case if desired. Complete Kit £7.17.6 without power supply components. £9.16.0. with power supply.

MERCURY SWITCHED TUNER. This is a tuner in chassis form which has a three position switch for the three BBC programmes. Uses one ECC80 and four EF80 valves. External power supply is required. Complete Kit £9.19.0. Power Pack Kit 39'-. **FRINGE TUNERS**

NEW FRINGE TUNER IN SHELF MOUNTING CASE, FMT3. This is an entirely new Fringe Tuner and is supplied complete with a very attractive green shelf mounting case with Perspex dial. The tuner is fitted with variable AFC. Internal power supply if desired. Valves used are one ECC81 and five EF80. Complete Kit £9.19.6 without power supply components. £11.18.0 with power supply.

INSTRUCTION MANUALS

All our kits include the appropriate instruction manual. All available separately as follows:— Manual covering both Standard Tuners and the new Fringe Area model. 2/10; "Mercury." 2/3; All post free.

MULLARD TAPE PRE-AMPLIFIER

This unit is intended for use with an existing amplifier and provides all the circuits necessary for tape recordings and playback. Instruction manual, giving full constructional information is available price. 2/10, post free.

COMPLETE KIT containing every item required down to the last nut and bolt. First-class items only included. £14.7.0. H.P. Deposit £2.17.0 and six monthly payments of £2.2.6. Kit less valves. £10.19.6. H.P. Deposit. £1.19.6 and six payments of £1.13.4. Power Unit kit. £3.19.6.

AMPLIFIER KITS

We carry in stock all the items needed for the following amplifiers. Fully detailed lists are available.

MULLARD 3-3 and 510 Amplifiers. Two- and Three-valve Pre-Amplifiers. Four Channel Mixer Unit. 912 Plus Amplifier.

G.E.C. Jupiter and JSA2 Stereo Amplifiers. Publications giving full details of the above are available as follows: Mullard "Circuits for Audio Amplifiers." 9/4; G.E.C. 912. 4/6; Jason Jupiter. 2/10; Jason JSA2. 2/4. All post free.

WATTS RADIO (MAIL ORDER) LTD.

We offer a really efficient Mail Order Service on all items stocked. All cash orders are dealt with on the day of receipt. Hire Purchase orders are subject to slight delay but this is kept to the absolute minimum.

MAINS TRANSFORMERS

All the following are suitable for High Quality Amplifiers. Normal Primaries for 200-250 volts 50 cycles are fitted in all cases.

PARTRIDGE

H300/100. 300-0-300 volts. 110 ma. 6.3 v. 2.5 a. 6.3 v. 2 a. tapped at 5 a. Specified for Mullard 510 and GEC 912. 72/-.

GILSON

W0741A. 300-0-300 v. 150 ma. 6.3 v. 5 a. 6.3 v. 1 a. tapped 5 v. 2 a. Specified for Mullard 510 and GEC 912. 63/-.

FLSTONE

MT510. 300-0-300 v. 100 ma. 6.3 v. 2 a. 6.3 v. 2 a. tapped 5 v. Specified for Mullard 510. 42/-.

MT/MU. 300-0-300 v. 120 ma. 6.3 v. 2 a. Twice. 6.3 v. 1 a. Specified for Mullard 510. 45/-.

MT/M. 300-0-300 v. 80 ma. 6.2 v. 2 a. 6.3 v. 1 a. Specified for the Mullard 3-3. 35/-.

MT/912. 300-0-300 v. 120 ma. 6.3 v. 2.5 a. 6.3 v. 1 a. Specified for the GEC 912. 44/-.

PARMEKO

P2831. Potted. 300-0-300 v. 60 ma. 6.3 v. 2 a. 6.3 v. 1 a. Specified for the Mullard 3-3. 32/3.

GRAMPHONE EQUIPMENT

ALL LATEST MODELS Hire Purchase Cash Price Deposit Mthly. Pmts.

RECORD CHANGERS

COLLARO Conquest (Studio O PU) ... £7.19. 6 £1.12. 0 6 of £1. 4.7

GARRARD RC121 (GC8 PU) ... £9.19. 6 £1.19. 6 12 of 15/-

GARRARD RC88 (GC8 PU) ... £16. 8. 0 £3. 6. 0 12 of £1. 4. 0

GARRARD RC98 (GC8 PU) ... £18.12. 8 £3.15. 8 12 of £1. 7. 3

B.S.R. U48 Monarch (TC8 PU) ... £7. 5. 0 £1. 9. 0 6 of £1. 2. 8

BSR UA12 Monarch (TC8 PU) ... £9.19. 6 £1.19. 6 12 of 15/-

BSR UA12 Monarch (TC8S Stereo PU) ... £10.17. 6 £2. 3. 6 12 of 16/2

SINGLE RECORD PLAYERS

GARRARD TA (GC8 PU) ... £8.10. 0 £1.14. 0 12 of 13/-

BSR TU9 (TC8 PU) ... £4.10. 0 £1. 5. 0 3 of £1. 5. 0

COLLARO RP584 (O, P or T PU) ... £8.18.11 £1.15.11 12 of 13/7

COLLARO RP594 (O, P or T PU) ... £9.18. 9 £1.18. 9 12 of 15/-

TRANSCRIPTION UNITS

COLLARO 4T/200 (TX88 PU) ... £18.13. 0 £3.15. 0 12 of £1. 7. 4

COLLARO 4TR/200 Motor only ... £13.18. 3 £2.15. 3 12 of £1. 0. 5

GARRARD 4HP (GC8 PU) ... £18. 9. 9 £3.15. 9 12 of £1. 7. 0

Many of the above can be supplied for stereo working. See our Gramophone Equipment List for details.

LOUDSPEAKERS

Cash Price Deposit Mthly. Pmts.

WHITLEY HF1016 10" ... £7.12.3 £1.10.3 6 of £1.3.8

HF1012 10" ... £4.15.0 £1.10.0 3 of £1.5.0

HF818 8" ... £6.10.6 £1. 6. 6 6 of £1.0.8

HF817 8" ... £10.16.8 £2. 3. 8 12 of 16.1

TS15 Cone Tweeter ... £6. 3. 9 £2. 3. 9 6 of £1.0.0

T10 Tweeter ... £6. 4. 0 £1. 4. 0 3 of £1.3.4

T359 Cone Tweeter ... £1.13.3 — — —

Crossover CX3000 ... £1.10.0 — — —

Crossover CX1500 ... £1.18.3 — — —

Other Whitley Speakers available, also full ranges of Goodman and Wharfedale.

CATHODE-RAY TUBES

BRAND NEW STOCK. NOT REBUILDS.

12 MONTHS' GUARANTEE

We can supply all BVA branded tubes at the new reduced prices. This includes Brimar, Cosor, Emiscope, Emitron, Ferranti, G.E.C., Mazda and Mullard. Full list of all available types sent on request.

MULLARD. 12in. and 14in. types. £10.10.0. H.P. Deposit £2.2.0 and 12 monthly payments of 15/8. 17in. Types (except MW4343) £12.0.0. H.P. Deposit £2.2.0 and 12 payments of 17/8. 17in. MW4343 £14.0.0. H.P. Deposit £2.16.0 and 12 payments of £1.0.8. 21in. Types £16.0.0. H.P. Deposit £3.4.0 and 12 payments of £1.3.5.

All tubes sent carriage free and safe delivery guaranteed.

LATEST CABY TEST METERS

Now in stock. CABY SUPREME MULTI-RANGE METERS. Made abroad. We can confidently recommend these meters as being accurate, well made and very good value for money.

MODEL A-10. Sensitivity 2,000 ohms per volt A.C. and D.C. Five voltage ranges 10-1,000 volts A.C. and D.C. Three D.C. current ranges .5-250 ma. Two resistance ranges. Size 5 1/2 x 3 1/2 in. Price, £4.17.6. H.P. Deposit £1.7.6 and three monthly payments of £1.6.8.

MODEL B-20. Sensitivity 4,000 ohms per volt A.C. and D.C. Voltage ranges—Five D.C. 10-1,000 volts. Four A.C. 10-1,000 volts. Four D.C. current ranges. .5-250 ma. Four resistance ranges. Price £6.10.0. H.P. Deposit £2 and three monthly payments of £1.13.4.



Illustrated leaflet giving full details of both models free upon request.

RECORDING TAPE

DOUBLE PLAY

BASE. 300ft. (3in.) 14/-; 600ft. (4in.) 25/-; 1,200ft. (5in.) 42/-; 1,800ft. (5 1/2in.) 52/6; 2,400ft. (7in.) 77/6.

SCOTCH BOY 200. 400ft. (3 1/2in.) 17/-; 1,200ft. (5in.) 45/-; 2,400ft. (7in.) 80/-.

TELEFUNKEN. 1,200ft. (5in.) In plastic container, 40/-; 2,400ft. (7in.) 75/-.

LONG PLAY

BASE. 210ft. (3in.) 9/-; 850ft. (5in.) 28/-; 1,200ft. (5 1/2in.) 35/-; 1,800ft. (7in.) 50/-.

EMITAPE 99. 50ft. (3in.) 9/6; 850ft. (5in.) 28/-; In Emicase, 30/6. 1,200ft. (5 1/2in.) 35/-; In Emicase, 37/6. 1,800ft. (7in.) 50/-; In Emicase, 52/6. 2,400ft. (8in.) 72/6.

GRUNDIG. 1,200ft. (5 1/2in.) 35/-; 1,800ft. (7in.) 50/-; 2,400ft. (7 1/2in.) 60/-; 4,600ft. (14 1/8; 5 1/2in.) 28/-; 1,200ft. (5 1/2in.) 35/-; 1,800ft. (7in.) 50/-; 2,400ft. (8 1/2in.) 70/-; PHILIPS. 850ft. (5in.) In plastic container, 28/-; 1,800ft. (7in.) 50/-.

SCOTCH BOY 150. 300ft. (3 1/2in.) 9/6; 900 ft. (5in.) 28/-; 1,275ft. (5 1/2in.) 35/-; 1,800ft. (7in.) 50/-.

SPECIAL OFFER. 1,200ft. Standard Tape. Brand new. Famous maker. Fully guaranteed. 25/- Four for 95/-.

Full range of standard tape and accessories also stocked. Send for list. All tape post free.

TRIPLE TONE AMPLIFIERS

We particularly recommend the Tripletone ready-built Amplifiers. The performance is very good, construction excellent and they represent excellent value for money.

HI-FI MAJOR. Push-Pull stage gives 12 watt output. Separate tone controls for Treble, Middle and Bass. Input for Microphone. Frequency response 15-20,000 cycles.

Price £15.18.9d. H.P. Deposit £3.3.9 and 12 monthly payments of £1.3.5.

POPULAR. Three valve amplifier giving three watts output. Separate time controls for Bass, Middle and Top.

Price, £6.18.6. H.P. Deposit £1.0.6 and six monthly payments of £1.3.2.

STEREO PICK-UP CARTRIDGES

RONETTE DC284. For all Collaro Models to replace the Studio Cartridge. Turn-over for 78/LP/Stereo. £3.18.6.

B.S.R. TC88. Will replace the TC8H or TC8M in any Monarch Changer. Plays 78/LP/Stereo records. £3.6.0.

HIRE PURCHASE

H.P. Terms are available on any item. Repayments may be spread over 3, 6 or 12 months. Details as follows: Three months: Deposit 6/- in the £. Service charge 5% but minimum charge 10/-.

Six and Twelve months: Deposit 4/- in the £. Service charge 10%, but minimum charge 20/-.

Terms of Business.—Cash with order or C.O.D. Postage extra under £3. We charge C.O.D. orders as follows. Up to £3, postage and C.O.D. fee minimum 2/8. Over £3 and under £5, C.O.D. fee only 1/6. Over £5 no charge.

54 CHURCH STREET, WEYBRIDGE, SURREY. Telephone: Weybridge 4556

PLEASE NOTE: POSTAL BUSINESS ONLY FROM THIS ADDRESS.

Brand new, individually checked and guaranteed
VALVES

AC/DD 2/6	E1148 2/-	EZ80 7/6
AC/P 4/6	EAS0 1/6	FA15 4/-
AC/PI 2/6	EAC91 4/6	FW4/500 8/-
AC6/PEN5/-	EB34 2/-	H30 5/-
AC/SP3 4/6	EBC33 6/-	H63 3/6
AL60 2/6	EC52 3/9	HP4101 6/-
AR6 2/6	EC54 3/6	KBC32 5/-
AR8 5/-	ECC32 4/-	KF35 5/-
ARDD5 2/-	ECC81 6/6	KT31 8/-
ARP3 3/-	ECC82 6/9	KT33C 7/-
ARP4 3/6	ECC83 7/-	KT66 7/6
ARP12 2/9	ECC84 7/9	KT241 9/-
ARP24 3/6	ECC91 4/-	KTW63 6/6
ARP31 5/6	ECL80 7/6	L30 4/-
SRP34 4/6	EF22 7/3	MH4 4/-
STP4 2/9	EF32 5/-	MH40 6/6
ATP7 5/6	EF36 3/6	MH41 6/6
AU1 5/-	EF39 4/6	ML4 4/-
AVW3 4/-	EF50 2/6	ML6 6/-
B30 3/6	EF52 5/-	MC/PEN 6/-
BL63 6/-	EF54 3/6	MC/PENB6/-
D41 3/3	EF55 6/-	MS/PEN/T 7/-
D42 4/-	EF70 4/-	N34 8/-
D77 4/3	EF80 6/9	NR15A 3/-
DA30 12/6	EF85 6/10	NR61 7/-
DD41 4/6	EF89 8/9	MT37 7/-
DD620 4/6	EF91 4/10	(4033A) 14/-
DETS 20/-	EF92 5/-	OD3 6/-
DET18 30/-	EL41 3/9	OZ4 5/-
DET19 2/6	EL4 8/3	OZ4A 5/-
DET20 2/6	EL8 7/6	161 4/6
DH76 4/9	FY91 3/6	PCC84 8/-
DSL10 4/6	EZ40 7/-	PCC85 8/-

PEN25 4/6	UL84 8/6	3Q5GT 9/-	6Q7G 6/3	35T 30/-	954 2/-
PEN46 5/6	UU4 4/6	4A1 4/6	6SC7G 5/6	35Z3GT 7/-	956 2/9
PEN65 6/6	UY85 7/-	4D1 2/6	6SC7GT 6/-	39/44 6/-	1619 6/6
PEN141 4/-	V2D33B 8/-	5U4G 5/-	6SG7 5/-	41FP 1/9	1625 6/6
PEN220A 3/-	VP23 5/-	5V4 7/-	6SH7 5/-	524G 8/-	1626 3/6
PEN1340 6/-	VR78 4/-	5Y3GT 6/9	6S17 6/9	53A 3/-	1629 4/6
PENDD/1360 9/6	VR99 8/-	5Z3 8/6	6S17G 6/6	58 6/-	4242A 6/6
PL81 11/-	VR105/30 7/6	5Z4G 8/-	6SK7 5/6	59 6/-	7193 1/9
PL82 8/-	VR150/30 4/3	6A6 5/-	6SL7GT 6/9	71A 4/6	7475 5/-
PL83 9/-	VR150/30 6/-	6AB7 5/3	6SN7GT 4/6	77 6/-	8010AR 12/6
PM4DX 3/-	VS110 4/-	6AC7 4/3	6SQ7 6/6	80 6/3	8020 6/-
PT25H 7/6	VT25 8/6	6AG5 4/6	6SR7 6/6	82 8/-	9001 5/-
PY82 8/-	VU111 3/-	6AG7 10/-	6SST 6/6	83 9/6	9003 5/6
QY21 6/-	VU120 3/-	6AK6 7/6	6V6G 5/6	83V 12/-	9004 4/-
OP25 5/3	VU133A 3/6	6AK7 10/-	6V6GT 6/-	84 12/6	9006 4/-
OS75/20 6/9	W31 7/-	6AM5 5/-	6XSGT 6/6	89 6/-	
OS95/10 6/9	W42 7/-	6AM6 6/3	6XSGT 6/6	210LF 3/-	Cathode Ray Tubes
QS108/45 6/9	Y66 8/-	6B64 4/6	7SAZ 6/9	210VPT 3/-	3BP1 25/-
QSI05/15 6/9	Z31 6/-	6C4 4/-	8D2 2/6	212VC 17/6	SCP1 42/6
	IA3 3/6	6C5 6/6	9D2 3/-	220VSG 3/-	5FP7 45/-
	IA5GT 5/-	6C6 4/6	12A6 5/-	350B 8/-	PG7/5 15/-
	IB23 11/-	6CBG 5/-	12A7 7/6	393A 25/-	VCR517 19/-
	IB24 11/-	6F6 7/-	12A7 6/6	446A 14/-	VCRX258
	IB26 11/-	6FBH 6/6	12AX7 7/9	446B 14/-	(with scanning coil)
	IB32 10/-	6F12 4/6	12CB 7/6	705A 17/6	45/-
	ID8GT 6/-	6GG6 3/-	12E1 22/6	715B 97/6	
	IL4 3/9	6H6M 2/3	12H6 2/6	717A 8/6	
	ILD5 3/6	6H6GT 1/9	12IGT 3/6	801 6/-	Special Valves
	IR5 6/9	6J5 3/6	12SC7 4/6	803 22/6	2J31 45/-
	IS5 6/-	6J6 6/6	12SG7 6/6	805 30/-	3A/1481 45/-
	IT4 4/-	6K6GT 6/6	12SH7 4/9	807AMER 807	3/1170/E £35
	IA3 3/6	6K7G 2/3	12SJ7 6/9	813 70/-	3/1192/E
	IA3 3/6	6K7G 2/3	12SK7 5/3	815 80/-	£37.10
	IA3 3/6	6K8G 6/6	12SL7 7/-	816 30/-	723AB 52/6
	IA3 3/6	6L5G 6/-	12SR7 6/-	829A 30/-	726N 27/6
	IA3 3/6	6L6 10/-	15D2 6/-	832A £14	ACT25 40/6
	IA3 3/6	6L6G 6/6	15E 8/-	843 7/6	CV691 60/-
	IA3 3/6	6L6GA 6/6	15R 7/6	866A 10/-	KR3 45/-
	IA3 3/6	3E29 6/6	19E2 5/-	827A 35/-	VX7110 15/-
	IA3 3/6	3E29 6/6	6N7GT 7/-	930 8/-	WL417A15/-

AND MANY OTHERS IN STOCK

Brand new original spare parts for AR88 Receivers.

Tuning Mechanism (gear), £2/10/-, post free.

Please write your other requirements.

Low Resistance Headphones, brand new, type CLR, 5/-.

Balanced Armature, 7/6. P. & P. 1/-.

Microphone Transformers. Balanced input 30 or 250 ohms. U.S.A. manufacture 7/6. P. & P. 1/6.

813 Ceramic Valveholders, 3/- each. P. & P. 1/6.

Vacuum Condenser 32,000 V. 50 pF 15/-.

Post free.

Modulation Transformers (U.S.A. Collins), primary imp. 6,000 ohms. C.T., secondary 6,000 ohms, 20 W., 9/6 each. Post free.

Carbon Inset Microphone G.P.O. Type 2/6. P. & P. 1/-.

Telescopic Aerial Masts. 7 sections, total 11 yards. Immediate erection. £4/10/- each or £8 per pair. Post free.

Light Headgear Assembly. Ideal for mobile use. Headphones 600 ohms carbon microphone, 18/-.

P. & P. 3/-.

Signal Generator Type TS. 14/AP. 3,200-3,370 mc/s. Fully guaranteed, £85.

Rotary Transformer. 171 W 12v input, 1,600 v 100 mA output, 30/-.

P. & P. 7/6.

R109 Receiver. Covering 2-8 mc/s 6 v. D.C. New and Tested, £4/5/-.

Carriage paid.

R109A Receiver. Covering 2-12 mc/s 6 v. D.C. New and Tested, £5/5/-.

Carriage paid.

URGENTLY WANTED
SPEECH AMPLIFIERS
BC 614 E or H £17-10-0
or JUNCTION BOXES
J.B.70 £10-0-0

Filament Transformers. Primary 0-190-210-230-250 v., 50 C. Sec. 1 2.5 v. C.T. at 10 amps.; 2 2.5 v. C.T. at 10 amps.; 3 10.5 v. C.T. at 11 amps., 4,000 v. insulation. Price £2.19.0. P. & P. 5/-.

Primary 0-190-210-230-250 v., 50 C. Sec. 1 10 v. C.T. at 4.5 amps.; 2 10 v. C.T. at 4.5 amps, 4,000 v. insulation. £1.16.0. P. & P. 5/-.

Primary 230 v. 50/60 c 67 v. amps. Sec. 1 6.3 v. 1-6 amps.; 2 6.3 v. C.T. 3 amps.; 3 6.3 v. C.T. 3 amps.; 3 6.3 v. C.T. 3 amps.; 4 6.3 v. C.T. 3 amps. £1.12.0. P. & P. 5/-.

P. C. RADIO LTD.
170 GOLDHAWK RD., W.12
SHepherds Bush 4946

Driver Transformers. Primary 500 ohms imp. Sec. to match two 805 in push pull. £1.7.6. P. & P. 5/-.

Transformers. Relay supply. Primary 230 v. Sec. 0-27-28-31 v. at 0.5 amps. 15/-.

P. & P. 5/-.

I.F. TRANSFORMERS 4.5 mc/s, American Made in black crackle finish housing. 6/-.

P. & P. 1/-.

SCR.522 Receivers (BC624), 100-156 mc/s, including all valves, 25/-.

P. & P. 5/-.

Vibrator Unit. 12 v./180 v. 60 mA. Exceedingly well filtered and smoothed, excellent for car radios. New, including one OZ4 valve and vibrator, 12/6.

P. & P. 5/-.

Famous U.S.A. Field Telephones in canvas or leather case, type EEB, £9 per pair. Post free.

Transreceivers. 68T. 325 mc/s together with aerial rods, microphone, H.R. headphones. Key in full working order. £6/15/-.

P. & P. 5/-.

Marconi Signal Generator. TF144C; 85 kc/s, 25 Mc/s. Made up to new standard, £70, delivered free.

Complete Set of Strong Aerial Rods (American). Screw-in type MP49, 50, 41, 52, 53, total length 15ft. 10in., top diameter 0.615in., bottom diameter 0.185in., together with matched aerial base. MP37 with ceramic insulator, ideal for car or roof insulation, £2/10/-, post free

AR88D and L.F. Receivers, completely overhauled and tuned, £60 and £57/10/- respectively. Completely rebuilt with P.V.C. wiring, £85.

HRO Mains power pack, input 115/250 v. A.C.; output 250 v. .75 mA. and 6.3 v. 3.5 amps. £3, inc. carr.

PERSONAL CALLERS WELCOME

D.C. OSCILLOSCOPE

A.C. MAINS 200-250 VOLTS

SIMPLIFIED SERVICING PROBLEMS WHEN USING THE

'TESTGEAR' SCOPE
3in. D.C. OSCILLOSCOPE



Engineered to precision standards, this high-grade instrument is made available at the lowest possible price, incorporating the essential features usually associated with luxury instruments.

This "SCOPE" will appeal particularly to Service Engineers and Amateurs. A high gain, extremely stable differential

Y-amplifier (30 mV/C.M.). Provides ample sensitivity with A.C. or D.C. inputs. Especially suitable for measurement of transistor operating conditions where maintenance of D.C. levels is of paramount importance. Push-pull X amplifier; Fly-back suppression; Internal Time-base Scan Waveform available for external use; pulse output available for checking T.V. Line O/P Transformers, etc.; Provision for external X I/P and CRT. Brightness Modulation. Size 10in. high, 6in. wide, 9in. deep. Wgt. 11 lb. £15.15.0. plus P. & P. 7/6. or 30/- deposit, plus P. & P. 7/6 and 12 monthly payments of 28/6.

FULL 12 MONTHS GUARANTEE INCLUDING VALVES AND TUBE.



8-WATT PUSH-PULL AMPLIFIER

COMPLETE WITH CRYSTAL MIKE AND 8in. LOUDSPEAKER

A.C. mains 200-250 v. Size 10 1/2 in. x 6 1/2 in. x 2 1/2 in. Incorporating 6 valves, H.F. pen., 2 triodes, 2 output pens and rectifier. For use with all makes and type of pick-up and mike. Negative feedback. Two inputs, mike and gram., and controls for same. Separate controls for Bass and Treble lift. Response flat from 40 cycles to 15 Kcs..


± 2 dB : 4 db down to 20 Kcs. Output 8 watts at 5% total distortion. Noise level 40 db down all hum. Output transformer tapped for 3 and 15 ohm speech coils. For use with Std. or L.P. records, musical instruments such as £4.19.6 Plus Guitars, etc. P. & P. 7/6. Or 20/- deposit Plus P. & P. 7/6. and 4 monthly payments of 23/-.

2-TRANSISTOR POCKET RADIO

Plus Germanium diode, fully tuneable over medium and long waves. Size 3 1/2 in. x 4 1/2 in. x 1 in. Complete set of components including case, 2 transistors and earpiece (less batteries).

19/6 Plus P. & P. 1/6.

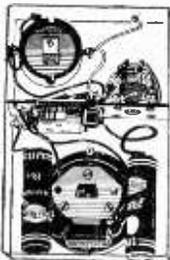Point to point wiring diagram 1/6 free with kit




PUSH-PULL OUTPUT STAGE

Inclusive of transistors with input and output transformers to match 3 ohm speech coil, suitable for use with the above kit. Complete kit of parts including transistors.

19/6 Plus P. & P. 1/6.

Point to point wiring diagram 1/6 free with kit

AC/DC POCKET MULTI-METER KIT

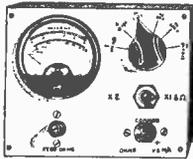


Comprising 2in. moving coil meter, scale calibrated in AC/DC volts, ohms and milliamperes. Voltage range AC/DC 0-50, 0-100, 0-250, 0-500. Milliamps 0-10, 0-100. Ohms range 0-10,000. Front panel, range switch, wire-wound pot (for ohms zero setting), toggle switch, resistor and rectifier. In grey hammer finish case.

19/6 Plus Built and tested P. & P. 1/6 7/6 extra.

Point to point wiring diagram 1/-, free with kit.

SIGNAL GENERATORS

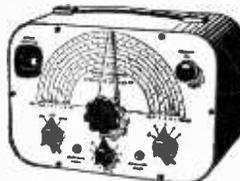


Cash £6.19.6 or 25/- deposit and 6 monthly payments of 21/6. Post and Packing 5/- extra.

Coverage 100 Kc/s-100 Mc/s on fundamentals and 100Mc/s to 200 Mc/s on harmonics. Metal case 10in. x 6 1/2 in. x 5 1/2 in. grey hammer finish. Incorporating three miniature valves and Metal Rectifier. A.C. Mains 200/250 v. Internal Modulation of 400 c.p.s. to a depth of 30%; Modulated or unmodulated R.F. output continuously variable 100 millivolts. C.W. and mod. switch, variable A.F. output. Incorporating magic eye as output indicator. Accuracy plus or minus 2%.

Cash £4.19.6 or 25/- deposit and 4 monthly payments of 21/6. Plus Postage and Packing, 5/-.

Coverage 120 Kc/s-84 Mc/s. Metal case 10in. x 6 1/2 in. x 4 1/2 in. Size of scale, 6 1/2 in. x 3 1/2 in. 2 valves and rectifier. A.C. mains 230-250 v. Internal modulation of 400 c.p.s. to a depth of 30%. modulated or unmodulated R.F. output continuously variable 100 millivolts. C.W. and mod. switch variable A.D. output and moving coil output meter. Grey hammer finished case and white panel. Accuracy plus or minus 2%.

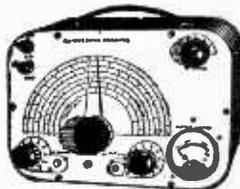

B.S.R. MONARCH UA8 WITH STEREO HEAD



4-speed plays 10 records 12in., 10in or 7in. at 33, 45 or 78 r.p.m. Inter-mixes 7in., 10in, and 12in. records of the same speed. Has manual play position; colour brown. Dimensions: 12in. x 10in. Space required above baseboard 4 1/2 in., below baseboard 2 1/2 in. Fitted with Full-FI turnover crystal head.

£7.19.6 Plus 5/- Postage & Packing. With standard head £6.19.6. plus 5/- P. & P.

PLAYER CABINET

Finished in 2-tone leatherette, will take B.S.R. UA8, with room for amplifier and 7in. x 4in. speaker. Overall size, 15 1/2 in. x 13 1/2 in. x 9 1/2 in.

39/6 Plus 5/- P. & P.

Similar to the above in POLISHED WALNUT will take Collaro 39/6 Plus 5/- P. & P.

MAINS TRANSFORMERS

All with tapped primaries, 200-250 volts, 0-160, 180, 200 v., 60 ma., 6.3 v. 2 amps, 10.8, 320-0-320 v. 75 ma. 6.3 v., 2.5 amp., 5 v., 2 amp., 10/6. 280-0-280, 80 ma, 6.3 v. 2 amp., 6.3 v. 1 amp., 10/6. Postage and packing on the above 3/-.

F.M. TUNER UNIT

Permeability tuned, by famous German Manufacturer. Coverage 88-100 Mc/s. Complete with ECC85. Size 4in. x 2in. x 2in.

25/- Plus P. & P. 1/6.

Circuit diagram 1/-, free with unit.

IMITATION LOG FIRE EFFECT

Size 14 inches x 11 inches 19/6 Plus P. & P. 2/6.

RADIO CHASSIS

A.C. MAINS 200/250 v. Medium & Long Wave Suberhet.

4 valve and rectifier. Complete with 8in. P.M. speaker. Valve line-up 6K8, 6K7, 6Q7, EL32 and rectifier. These have been used but fully serviced with new Electrolytics and valves. FULLY GUARANTEED.

42/6 Plus 7/6 P. & P.

RADIO & T.V. COMPONENTS (Acton) LTD.

23 HIGH STREET, ACTON, LONDON, W.3.

All enquiries S.A.E.

Goods not dispatched outside U.K.

Components Would Cost More



Car Battery Charger—ready-made high output battery charger in stove enamelled sheet steel louvered case. New, complete and ready to work. Rated at 12 v. 4 amps. and variable rate selector for trickle charging, also a meter to show charging rate. Suitable for 230/250 A.C. mains. Special snip price of 55/-, plus 3/6 post and insurance.

Building A Scope ?




9in. oscilloscope tube American made Type No. 3FP7. Octal base 6.3 v. 6 amp heater, electrostatic deflection. Brand new and guaranteed. 15/- each, plus 1/6 post and insurance. Complete with circuit diagram.

Multi-Purpose Mains Transformer

Heavy duty construction, must have cost at least £3 to make. Offered at a snip price of 14/6.

Specification:—
 Primary Standard 230 v.
 Secondary 1. 660 v.-200 mA. centre tapped.
 Secondary 2. 80 v.-100 mA.
 Secondary 3. 23 v.-750 mA.
 Secondary 4. 7 v.-5 amp. centre tapped.
 Secondary 5. 5 v.-3 amp.
 In addition there is a window space for extra L.T. windings, winding ratio is 21 turns per volt. Weight of transformer is 12 lb., size approximately 6in. x 4in. x 4in. Connections all brought out to terminals on bakelite panel. We have only 500 of these, so order at once to avoid disappointment. Non-callers add 3/6 postage please.

Fluorescents

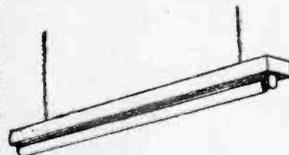

All complete with polyester filled choke and interference suppressor starters.
 5 ft. 80 watt, 39/6 plus 5/- carr. & ins.
 4 ft. 40 watt, 32/6 plus 4/6 carr. & ins.
 Or complete with tube, 39/6 plus 5/6 carr. & ins.
 3 ft. 40 watt, 31/6 plus 3/6 carr. & ins.
 Or complete with tube, 39/6 plus 4/6 carr. & ins.
 2 ft. 20 watt, 29/6 plus 3/6 carr. & ins.
 Circular 40 watt, 49/6 plus 3/6 carr. & ins.
 Or complete with tube, 87/- plus 4/6 carr. & ins.

Miniature Microphone

American made. Dynamic type, real bargain at 2/6, plus 8d. postage.



Assure Your Future

The ownership of a good instrument has been the turning point in many a famous career. You can own the latest Pullin Series 100 Test Set which is undoubtedly a most useful instrument by a firm long famous for fine instruments. Entirely redesigned, it has a square movement with diacron plastic cover. This makes for a brighter, more readable scale, extra scale length and wider angle of vision. With the test set is included a pair of combined test prods and crocodile clips also a stand for inclining the meter at the best reading positions. Ranges A.C. Volts: 0-10, 0-25, 0-100, 0-250, 0-500, 0-1,000 ditto D.C. A.C. Current 0-100 mA. D.C. Current 0-2.5, 0-10, 0-100, 0-500 mA. Resistance: 0-1M and 0-10K. All at 10,000 ohms per volt. Price £127/8 or £14/- deposit and 26 fortnightly payments of 10/-, non callers add 5/- carr. and insurance.



FREE GIFT.—All purchasers of the above item this month will receive Range Extender scale and data which add capacity 20E—1mPd. in two ranges. Inductance 0-100 henrys, etc., etc.

Six Useful Articles

Our 1960 catalogue now ready gives constructional hints and circuits for the following items:
 Moisture operated switch.
 Simple but clever signal tracer.
 Versatile power pack costing only 10/-.
 Instantaneous heater for workshop or den.
 Six transistor pocket superhet.
 Photo-flood controller.
 Send for this catalogue to-day, price 2/6 refundable from purchases.


Towards Hi-Fi Perfection

The revolutionary B.J. tweeter unit stands on top of the cabinet, and with it the best in the loudspeaker is brought out by top "C" positive and controllable. Frequency response 2,000 to 18,000 c.p.s. effective acoustic spread 360 deg.—dimensions 6" x 5" diameter—weight 1 1/2 lbs. approximately, finished in sapele mahogany veneer. Price £4.15/1, plus 3/6 carriage & insurance. Fuller technical details available on request.



For Cycles and Scooters

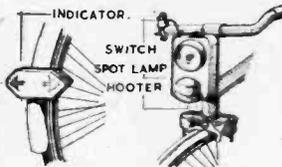This three part outfit comprises combined head lamp with built-in hooter and a rear fitting direction indicator and a well made outfit which will make cycling safer. 15/6 complete plus 2/6 post and packing.



Avo Proclips

The advantage of these test prods is that by pressing the trigger at the side they become crocodile clips and this is a great time saver when servicing. Price 15/- Pair.



**FOR ADDRESS
SEE OPPOSITE PAGE**

RI155 for Spares



These are less valves but otherwise very reasonable reasons—complete spares—prices £2 to £4 depending on condition—carriage 7/6.

Radio Stethoscope

This can be slipped into the pocket rather like a fountain pen. With it in most districts a receiver can be checked from the grid of the first valve right through to the output without a signal generator, the stethoscope will operate in both L.F. and R.F. circuits without alteration. It is a complete, fault-finder. All the necessary parts to make this tracer 9/6, post 1/-.



Tube Tester and Reactivator

We can supply all the main components for making this unit which will not only test Cathode Ray Tubes but also will reactivate them supplied complete with full instructions. Price £3, plus 2/6 post and ins.

Super Sensitive (2,000 O.P.V.) Multimeter Kit

17 ranges including D.C. volts to 1,000 v. A.C. volts to 1,000 v. D.C. milliamperes to 500 ohms, to 2 meg. All the essential parts, including metal case, selected resistors, wire for shunts, selected switches, calibrated scales and instructions, 32/6, plus 2/6 post and insurance.

Transistor Set Parcel

Cabinet as illustrated—with handle and motifs—2 ranges tuning condenser—printed circuit—tuning scale—full circuit diagram showing other necessary parts—separate value £3—will all be sent for 29/6, plus 2/6 post and insurance.



Battery Charging Rectifier—Selenium 12-15 v. full wave 5 amp. 9/6, plus 1/6 carriage.

Metal Chassis—Punched for Mullard 510 amplifier—complete with inner screening sections and stove enamelled. 12/6, plus 2/6.

Geiger Counter Tubes—20th Century type. Type No. G24—complete with circuit or geiger counter. 29/6, plus 2/6.

Heavy Duty Test Prods—Red and black with plug-in lead attachments 8/6 pair, plus 1/-.

Speaker Bargain



12in. Hi-fidelity loudspeaker. High flux. Permanent magnet type with standard 3 ohm speech coil. Will handle up to 12 watts. Brand new by famous maker. Price 32/6, plus 3/6 post and insurance.

Hi-Fi Snip Infinite Wall Baffle



Nicely veneered and polished. Corner fitting (attaches to picture rail). Takes up no floor space. Gives really fantastic results with only low-priced 8 in. speaker. Fitting for tweeter. Only 45/- each, carriage and insurance 3/6.

BEGINNER'S SUPERHET



All the components including metal chassis, valves, metal rectifier, coil, tuning condenser, etc., required to build the "Beginner's Superhet" as described in the January, 1958, issue, are available as a parcel. Price £3, plus 3/- post and insurance.

W.D. Circuit Details

Diagrams and other information extracted from official manuals. All 1/6 per copy, 12 for 15/-.


A-134 R-102
 BC-348 HRO Receiver
 BC-312 R28/ARC5
 R-103A R1116 A
 BC-342 RA-1B
 RA-1B AN APA-1
 R-208 78
 R-1155 76
 R-1121A R.T.18
 R-1132A/R-1481 CAY-46-AAM-
 R-1147 RADAR
 R-1124A A.S.B.-3
 R-1082 Indicator 62A
 R-1355 Indicator A.S.B.3
 B.C.1206-A/B Indicator 62
 B-455-A (or-B) Indicator 6K
 B-454-A (or-B) Indicator 6K
 B-456-M-A (or-B) R.F. unit 24
 Transmitter T1154 R.F. unit 25
 Fifty-eight walkie R.F. unit 26
 talkie R.F. unit 27
 Frequency meter R.F. unit 27
 B.C. 221 Wireless set No. 19
 Demobbed valves

CONNECTING WIRE



P.V.C. covered in 100ft. coils—2/9 a coil or four coils different colours, 10/-, post free.

Philips AG2009 Transcription Unit

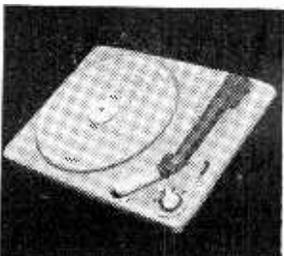

Philips AG2009 Record Player, a modestly priced 4-speed unit with many outstanding features, is ideal for the enthusiast who is assembling his own equipment or modernising an older installation. The pick-up arm is wired for stereo and the Philips stereo head is available as an optional extra. Eddy Current Brake gives $\pm 2\%$ fine adjustment on all four speeds. Continuously variable pick-up playing weight (2-12 grms.). Supplied with Philips Hi-Fi crystal head, type AG3019 for microgroove and 78 r.p.m. Frequency response 30-15,000 c/s. Pick-up lifting and lowering device. Individually balanced heavy turntable. Muting switch fitted. Can be used with any amplifier or radio set. Complete with monaural pick-up, £10.10.0. or £1 deposit and 21 fortnightly payments of 10/- Available also with stereo head, diamond or sapphire stylus. Prices on request.

Component Storage Drawers



Stout board construction these drawers are ideal for small parts. Supplied complete with simple erection instructions—1/6 each or 12 drawers each 6 x 2 1/2 x 6 1/2 in., 13/6, post 2/-.

THIS MONTH'S SNIP



5 valve F.M. receiver kit. Note: this is not just a tuner but a complete receiver with power supplies—made by the famous Cossor Company. Until very recently this cost £15.15.0, but due to a large purchase we are able to offer this at


the remarkably low price of £8.18.6, plus 3/6 post and insurance. Complete with full constructional details. The circuit uses 5 B9A valves and special features are the cascade R.F. stage and the Foster Seeley discriminator. All valves and components, printed circuit, printed dial, 10in. x 6in. elliptical speaker, in fact everything except the cabinet is supplied. Do not miss this wonderful bargain!

CABINET SNIP



Extremely well made portable amplifier case finished in two-tone and very modern in appearance. Large enough for stereo outfit with tape deck or auto-changer. Snip price 59/6, plus 3/6 carriage and insurance.

Thermostats

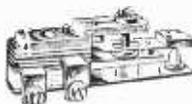

Useful for the control of appliances such as convector gluepots, vulcanisers, hot plates, etc. Adjustable to operate over temperature range 50-550 deg. F., fitted with heavy silver contacts. 8/6. Other types: 11 amp, 3/6; 5 amp, 8/6; 2 amp, QMB, 5/6; 15 amp, QMB, 15/-; 15 amp, encased wall mounting type, 29/6.

Band III Converters



Suitable Wales, London, Midlands, North, Scotland, etc. All the parts including 2 BF80 valves, coils, fine tuner, contrast control, condensers and resistors. (Metal case available as an extra.) Price only 19/6, plus 2/6 post and insurance. Data free with parts or available separately, 1/6. Please send two more kits, the one you sent last week is performing magnificently. We receive this sort of letter every day of the week, so if you have hesitated because you thought our kits too cheap you need hesitate no longer.

A.C./D.C. Multimeter Kit



Ranges: D.C. volts 0-5, 0-50, 0-100, 0-500, 0-1000. A.C. volts 0-5, 0-50, 0-100, 0-500, 0-1000. D.C. milliamps 0-5, 0-100, 0-500. Ohms 0-50,000 with internal batteries. 0-500,000 with external batteries. Measures A.C./D.C. volts, D.C. current and ohms. All the essential parts including metal case, 2in. moving coil meter, selected resistors, wire for shunts, range selector, switches, calibrated scale and full instructions, price 19/6, plus 2/6 post and insurance.

Cabinet Snip



This fine cabinet as illustrated but less control knobs is available this month at a special snip price of 12/6, plus 3/6 post and insurance. Size is 13 1/2 in. x 9 in. x 4 in. and it is nicely covered in two tone I.C.I. fabric.

All items advertised can be obtained from the following Companies.

If ordering by post, address your order to the Company nearest to you and please include postage.

Electronics (Ruislip) Ltd. 42-46, Windmill Hill, Ruislip, Middx. Phone: RUISLIP 5780. Half day Wednesday.	Electronics (Croydon) Ltd. 286, London Road, Croydon. Phone: CRO 6559. Half day Wednesday.	Electronics (Finsbury Park) Ltd. 29, Stroud Green Rd., Finsbury Park, N.4. Phone: ARCHWAY 1049. Half day Thursday.	Electronics (Manor Park) Ltd. 520, High St. North, Manor Park, E.12.
---	--	--	--

R.S.C. HI-FI TAPE RECORDER KIT

REALISM AT INCREDIBLY LOW COST. CAN BE ASSEMBLED IN 1 HOUR
The Recorder incorporates the Latest Collaro Mark IV Tape Transcriber listed £25. The Linear LT45 High Quality Tape Amplifier listed £12.10. High Flux P.M. Speaker listed 30/-, empty Tape Spool, a Reel of Best Quality Tape listed 22/6, and a Handsome Portable carrying Cabinet finished in veneered walnut, size 18in. x 13in. x 9in. high, listed £4 10/0 and circuit. Total cost if purchased individually approx. £45. Performance equal to units in the £50-£80 class. Send S.A.E. for leaflet.

29 1/2


GNS. H.P. TERMS. Deposit 3 gns. and 12 monthly Carr. payments 53/9. Cas 17/6. price if settled in 3 mths.

HI-FI 8 WATT AMPLIFIER

Special Purchase due to Cancelled Export Order. **£4-19-9** Carr. 7/6.
For 200-250 v. A.C.
A limited number is available of these highly sensitive Push Pull units guaranteed brand new and in working order and with separately controlled inputs for 'mike' and gram. etc., LATEST B.V.A. VALVES. Excellent performance.

R.S.C. A8 HIGH FIDELITY 12 WATT AMPLIFIER

Ultra Linear Push-Pull Amplifier with "Built-in" Tone Control. Pre-amp stages, high sensitivity, includes 5 valves (807 outputs). High Quality sectionally wound output transformer, specially designed for Ultra Linear operation, and reliable small condensers of current manufacture. **INDIVIDUAL CONTROLS FOR BASS AND TREBLE** "Lift" and "Cut". Frequency response ± 3 db. 30-30,000 c/s. Six negative feedback loops. Hum level 71 db. down. **ONLY 70 millivolts INPUT** required for **FULL OUTPUT**. Suitable for use with all makes and types of pick-ups and practically all microphones. Comparable with the very best designs.

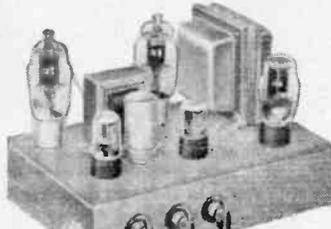

For STANDING or LONG PLAYING RECORDS. For **MUSICAL INSTRUMENTS** such as **STRING BASS, GUITARS, etc.** **OUTPUT SOCKET** with plug provides 300 v. 30 mA. and 6.3 v. 1.5a. For supply of a **RADIO FEEDER UNIT**. Size approx. 12-9/7in. For A.C. mains 200-230-250 v. 50 c/s. Outputs for 3 and 15 ohm speaker. Kit is complete to last out. Chassis is fully punched. Full instructions and point-to-point wiring diagrams supplied. Unapproachable value. At **£7/15/0** or factory built 45/- extra. Carriage 10/- if required louvered metal cover with 2

£7-15-0

carrying handles can be supplied for 18/9. Additional input sockets, with appropriate Vol. control so that two different inputs such as Gram and 'Mike' or Tape and Radio can be mixed, can be provided for 12/- extra. Guaranteed 12 months. **TERMS** on assembled two input model: **DEPOSIT 18/9** and 12 monthly payments 18/9. **HIGH FIDELITY MICROPHONES and SPEAKERS** in stock. Ready cash prices or credit terms if supplied with amplifier.

STAAR GALAXY 4-SPEED MIXER AUTO-CHANGERS
Brand new, cartoned. Turnover sapphire styl. Many exclusive features. Unique design motor virtually free from rumble. For 200-250 v. A.C. mains. Only **£5.18.6**.

PORTABLE CABINETS
Full range of attractive designs from **15/9**

SPECIAL OFFER. Two tone Portable cabinet, Gram amplifier, Staar Changer and 7in. x 4in. P.M. Speaker, 10 gns. Carr. 10/- or with B.S.R. UAS. 12 gns.

THE SKYFOUR T.R.F. RECEIVER. A design of a 3-valve Long and Medium wave 200-250 v. A.C. Mains receiver with selenium rectifier, High gain H.F. stage and low distortion detector. Power pentode output. Valve line-up 6K7, 6X4, 6V6G. Selectivity and quality are well up to standard, and simplicity of construction is a special feature. Point-to-Point wiring diagrams, instructions and parts list 1/9. Maximum buildings costs **£4.19.6**, inc. attractive Walnut veneered wood cabinet 12in. x 6in. x 5in.

R.S.C. PORTABLE TAPE RECORDER

A completely assembled unit in attractive two-tone rexine covered carrying case. Excellent frequency response. Auto-erase. Fast rewind. Takes up to 5 1/2 in. tape spools. High Flux speaker. 3 watts output. Inputs for Radio Gram and 'Mike'. For 200-250 v. 50 c.p.s. A.C. mains. Sensational value! Price, including 'Mike' Reel of best quality tape and empty spool. Usual 12 months' guarantee. H.P. Terms: Deposit 44/- and 12 monthly payments of 33/4. **19 GNS.**

PICK-UP ARMS complete with Hi-Fi turnover crystal head. Acos GP41. Limited number brand new, perfect, at approx. half price. Only 29 11/.

ACOS CRYSTAL MICROPHONES. Mic 40 hand or desk. Listed 45/- Only 29/9. Type 39-1, hand or desk. List price 50/- Brand new, cartoned, 35/9. 39-1 Stick type, list price 5 gns. Brand new. 39/6.

COSSOR VHF/FM RADIO RECEIVER KITS

Including 6 valves, Printed Circuit and Goodman's 10" x 6" Elliptical Speaker. Limited to retail at 15 GNS. Make **£8-19-6** number at

EXTENSION SPEAKERS

Ready for use in walnut veneered cabinet.
6in. 2-3 ohms. 29/11.
8in. 2-3 ohms. 35/9.
10in. 2-3 ohms. 58/9.
Very limited number.



10 WATT AMPLIFIERS. Unused and in good order but slightly store soiled. For 200-250 v. A.C. mains input. Output for 15 ohm speaker. Inputs for 'mike' and Gram. Limited number, complete with Mullard valves. Only **£6.15.0** carr. 5/-.

R.S.C. BATTERY TO MAINS CONVERSION UNITS

Type BML. All-dry battery eliminator. Size 5 1/2 x 4 1/2 x 2 1/2 in. approx. Completely replaces battery supplying 1.4 v. and 90 v. where A.C. mains 200-250 v. 50 c/s is available. Suitable for all battery portable receivers requiring 1.4 v. and 90 v. This includes latest low consumption types. Complete kit with diagrams. 39/9. or ready to use. 48/9.



Type BM2. Size 9 x 5 1/2 x 2 1/2 in. Supplies 120v. 90 v. and 60 v. 50 mA. and 2 v. 0.4 a. Fully smoothed. Thereby completely replacing both H.T. batteries and L.T. 2 v. accumulators when connected to A.C. mains supply 200-250 v. 50 c/s. **SUITABLE FOR ALL BATTERY RECEIVERS** normally using 2 v. accumulator. Complete kit of parts with diagrams and instructions. 49/9. or ready for use. 59/6.

R.S.C. MAINS TRANSFORMERS (FULLY GUARANTEED)

Interleaved and Impregnated. Primaries 200-230-250 v. 50 c/s. Screened. **TOP SHROUDED DROP THROUGH**
250-0-250 v. 70 mA. 6.3 v. 2 a. 5 v. 2 a. ... 16/9
350-0-350 v. 80 mA. 6.3 v. 2 a. 5 v. 2 a. ... 18/9
250-0-250 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. ... 23/9
300-0-300 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. ... 23/9
350-0-350 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. ... 23/9
350-0-350 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. ... 23/9
6.4 v. 3 a. ... 23/9
350-0-350 v. 150 mA. 6.3 v. 4 a. 5 v. 3 a. ... 26/9
FULLY SHROUDED UPRIGHT
250-0-250 v. 60 mA. 6.3 v. 2 a. 5 v. 2 a. ... 17/6
Midjet type 21-3-3in. ... 17/6
250-0-250 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. ... 26/9
300-0-300 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. ... 26/9
350-0-350 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. ... 26/9
300-0-300 v. 130 mA. 6.3 v. 4 a. 6.3 v. 1 a. ... 35/9
For Mullard 510 Amplifier ... 35/9
350-0-350 v. 150 mA. 6.3 v. 4 a. 5 v. 3 a. ... 33/9
350-0-350 v. 150 mA. 6.3 v. 2 a. 6.3 v. 2 a. 5 v. 3 a. ... 35/9
425-0-425 v. 200 mA. 6.3 v. 4 a. C.T. 6.3 v. 4 a. C.T. 5 v. 3 a. Suitable Williamson Amplifier. etc. ... 49/9

FILAMENT TRANSFORMERS
All with 200-250 v. 50 c/s, primaries 6.3 v. 1.5 a. 5/9; 6.3 v. 2 a. 7/6; 0-4-6.3 v. 2 a. 7/9; 12 v. 1 a. 7/11; 6.3 v. 3 a. 8/11; 6.3 v. 6 a. 17/6; 12 v. 3 a. or 24 v. 1.5 a. 17/6.
OUTPUT TRANSFORMERS
Midjet Battery Pentode 66:1 for 354. etc. ... 3/9
Small Pentode, 5000Ω to 3Ω ... 3/9
Small Pentode 78,000Ω to 3Ω ... 3/9
Standard Pentode, 5,000Ω to 3Ω ... 5/6
Standard Pentode, 78,000Ω to 3Ω ... 5/6
10,000 to 3Ω ... 5/6
Push-Pull 10-12 watts 6V6 to 3Ω or 15Ω ... 16/9
Push-Pull 10-12 watts to match 6V6 to 3-5-8 or 15Ω ... 18/9
Push-Pull EL84 to 3 or 15Ω ... 16/9
Push-Pull 15-18 watts. 6L6, KT88 ... 22/9
Push-Pull for Mullard 510 Ultra Linear ... 29/9
Push-Pull 20 watts, sectionally wound 6L6, KT88, etc., to 3 to 15Ω ... 47/9

ELIMINATOR TRANSFORMERS
Primaries 200-250 v. 50 c/s.
120 v. 40 mA. 5-0-5 v. 1 a. ... 15/9
90 v. 15 mA. 4-0-4 v. 500 mA. ... 9/9
SMOOTHING CHOKES
150 mA. 7-10 H 250 ohms ... 11/3
100 mA. 10 H 200 ohms ... 8/9
80 mA. 10 H 350 ohms ... 5/9
60 mA. 10 H 400 ohms ... 4/11
CHARGER TRANSFORMERS
All with 200-250 v. 50 c/s Primaries:
0-9-15 v. 1 a. 11/9; 0-9-15 v. 3 a. 16/9;
0-3-15 v. 5 a. 19/9; 0-9-15 v. 6 a. 23/9.

AUTO TRANSFORMERS. 50 watt
0-110-115-230/250 v. 8/11 each.

COLLARO CONQUEST 4-SPEED AUTO-CHANGER with high fidelity Studio pick-up. Latest model. Brand new. Cartoned. For 200-250 v. 50 c.p.s. A.C. mains. Our price **£7.19.6**. Carr. 5/6.
COLLARO 4-SPEED SINGLE PLAYER UNITS. Type AC/4564 with turnover crystal head. **£6.12.6**. Carr. 4/6.

R.S.C. A12 STEREOPHONIC AMPLIFIER KIT

A complete set of parts to construct a Stereo amplifier with an undistorted output total 6 watts. For A.C. mains input of 200-250 v. Outputs for matched 2-3 ohm speakers. Sensitivity 130 m.v. Ganged Vol. and Tone Controls. Preset balance control. Full instructions and point-to-point wiring diagrams supplied. Only good quality Carr. and pkg. 5/- components and latest high grade valves used. Exceptionally realistic reproduction can be obtained at ample volume for the home, as can be demonstrated in typical surroundings at our County Arcade premises. A really sensational offer.

£3-19-6

STEREO EQUIPMENT OFFER. Comprising A12 Kit, 2 matched 8in. L/Speakers, and Acos T/O Stereo head with diamond stylus suitable most pick-ups.

£6-19-6
Carr. 7/6

LINEAR L745 HIGH QUALITY TAPE DECK AMPLIFIER. With "built in" power pack and oscillator stage. For Tape Decks with High or Low Impedance. Playback and Ease Heads, such as Lane, Truvox, Coilaro, Brennel, Carr. 7/6 etc. For A.C. Mains 230-250 v. 50 c/s. Linear Frequency Response ± 3 db. 50-11,000 c/s. Switched negative feedback equalisation for 31, 74 and 151n. per sec. Output 4 watts. Send S.A.E. for leaflet.

Ready for Use, ONLY 12 GNS.

R.S.C. 30 WATT ULTRA LINEAR HIGH FIDELITY AMPLIFIER A10

A highly sensitive Push-Pull high output unit with self-contained Pre-amp. Tone Control Stages. Certified performance figures compare equally with most expensive amplifiers available. Hum level 70 db. down. Frequency response ± 3 db. 30-30,000 c/s. A specially designed sectionally wound ultra linear output transformer is used with 807 output valves. All components are chosen for reliability. Six valves are used, EF86, EF86, EC83, 807, 807, CZ33. Separate Bass and Treble Controls are provided. Minimum input required for full output is only 12 millivolts so that ANY KIND OF MICROPHONE OR PICK-UP IS SUITABLE. The unit is designed for CLUBS, SCHOOLS, THEATRES, DANCE HALLS or OUTDOOR ENTERTAINMENTS, etc. For use with Electronic ORGAN, GUITAR, STRING BASS, etc. For standard or long-playing records. OUTPUT SOCKET PROVIDES L.T. and H.T. for a RADIO FEEDER UNIT. An extra input with associated vol. control is provided so that two separate inputs such as Gram and 'Mike' can be mixed. Amplifier operates on 200-250 v. 50 c/s. A.C. Mains and has output for 3 and 15 ohm speakers. Complete kit of parts with fully punched chassis and point-to-point wiring diagrams and instructions. If required cover as for A8 can be supplied for 18/9. The amplifier can be supplied, factory built with 12 months' guarantee, for £13.19.6. TERMS: DEPOSIT 24/6 and 12 monthly payments of 24/9.

11 GNS.

Carr. 10/-

LINEAR 'DIATONIC' 10-14 WATT HIGH FIDELITY PUSH-PULL ULTRA LINEAR AMPLIFIER. For 200-250 v. A.C. mains. Valves EC83, EC83, EL84, EL84, E281. Self-contained Pre-amp Tone Control stage. Separate Bass and Treble Controls Independent 'Mike' and Gram input sockets. Outputs for 3 and 15 ohm speakers. Only 12 GNS.; or Deposit 22/3 plus 10/- carr. and 12 monthly payments of 22.3. Send S.A.E. for leaflet.

LINEAR L50 50 WATT P.A. AMPLIFIER. High quality and sensitivity. 19 GNS. Send S.A.E. for leaflet.

GARRARD 4-SPEED AUTO-CHANGERS. Type RC120H. Very limited number at only £9.19.6. Carr. 5/6.


R.S.C. 3-4 WATT AT HIGH-GAIN AMPLIFIER

For 200/250 v. 50 c/s. Mains input. Appearance and Specification, with exception of output wattage, as A5 amplifier. Complete Kit with diagrams. £3.15.0. Carr. 3/6.

R.S.C. BRADFORD, MANCHESTER and LEEDS
(Leeds) Ltd.

AM/FM RADIOGRAM CHASSIS HIGH QUALITY 6-8 WATT PUSH-PULL OUTPUT

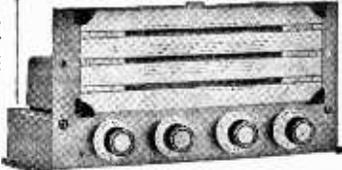For 200-250 v. Mains. Long wave, Medium, F.M. and Gram. Complete with 8 B.V.A. valves. Guaranteed 12 months. Only 22 GNS. Or Deposit £2.12.0 and 9 monthly payments of £2.12.0.



LINEAR L45 MINIATURE 4 1/2 WATT QUALITY AMPLIFIER. Suitable for use with any record playing unit, and most microphones. Negative feedback 12 db. Separate Bass and Treble Controls. For A.C. mains input of 200-250 v. 50 c/s. Output for 2-3 ohm speaker. Three miniature Mullard valves used. Size of unit only 6-5-5 1/2 in. high. Guaranteed for 12 months. Only £5/19/6. Send S.A.E. for illustrated leaflet. Terms: Deposit 22/6 and 5 monthly payments of 22/6.

R.S.C. 4-5 WATT A5 HIGH-GAIN AMPLIFIER

A highly-sensitive 4-valve quality amplifier for the home, small club, etc. Only 50 millivolts input is required for full output so that it is suitable for use with the latest high fidelity pick-up heads, in addition to all other types of pick-ups and practically all 'mikes'. Separate Bass and Treble Controls are provided. These give full long-playing record equalisation. Hum level is negligible being 71db. down, 15 db. of negative feedback is used. H.T. of 300 v. 25 mA. and L.T. of 6.3 v. 1.5 a. is available for the supply of a Radio Feeder Unit, or Tape-Deck pre-amplifier. For A.C. mains input of 200-230-250 v. 50 c/s. Output for 2-3 ohm speaker. Kit is complete in every detail and includes fully punched chassis (with baseplate) with Blue hammer finish and point-to-point wiring diagrams and instructions. Exceptional value at only 24/15/-, or assembled ready for use 25/- extra, plus 3/6 carr. or Deposit 22/6 and 5 monthly payments of 22/6 for assembled unit.



R.S.C. PORTABLE GUITAR AMPLIFIERS

Junior 5 watts High quality output. Separate Bass and Treble 'Cut' and 'Boost' controls. Sensitivity 15 m.v. Twin inputs. High Flux 8in. Loudspeaker 'built-in'. Handsome, strongly made Cabinet (size approx. 14 x 14 x 7in.) finished in satin walnut, and fitted carrying handle. H.P. Terms. Deposit £1 and 9 monthly payments of £1.


£8-19-6

Carr. 7/6

Senior 10 watts High Fidelity output. Separate Bass and Treble 'Cut' and 'Boost' controls. Twin separately controlled high gain input, so that two instruments such as Guitar and String Bass can be used at the same time. Two loudspeakers are incorporated. A high Flux 12 in. for Bass notes and a 7 x 4 in. elliptical for Treble. Cabinet is made and finished satin walnut. Size approx. 18 x 18 x 8 in. H.P. Terms. Deposit 23/6 and 12 monthly payments of 23/6. Both models for 200-250 v. A.C. Both models for 200-250 v. A.C. Carr. 10/-

13 GNS.

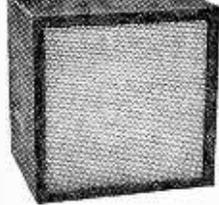12in. 10 WATT HIGH QUALITY LOUD-SPEAKERS IN POLISHED WALNUT FINISHED CABINET



Gauss 12,000 lines. Speech coil 3 ohms or 15 ohms. Only £4.19.6 Carr. 5/- Terms: Deposit 11/- and 9 monthly payments of 11/-

12 in. 20 WATT HI-FI LOUD-SPEAKERS IN CABINETS. Size 18 x 18 x 8 in. Finish as above. Terms: Deposit 13/10 and 12 monthly payments of 13/10. Only £7.19.6. Carr. 8/6.

COLLARO 4-SPEED SINGLE PLAYER. Separate pick-up (GP54). Only £3.15.0. Twin sapphire stylus. 200-250 v. A.C. mains.

TERMS: C.W.O. or C.O.D. No C.O.D. under £1. Post 1/9 extra under £5. 2/9 extra under £5.5. Wed. until 1 p.m. Trade supplied. S.A.E. with enquiries.

PLESSEY DUAL CONCENTRIC 12in. 15 ohms HIGH FIDELITY SPEAKER (12,000 lines) with built-in tweeter (completely separate elliptical speaker with choke, condensers, etc.), providing extraordinarily realistic reproduction when used with our A8 or similar amplifier. Rated 10 watts. Price only £5/17/6.

HI-FI CRYSTAL PICK-UP HEADS. (Turnover type with sapphire stylus). HGP59. Standard replacement for Garrard and B.S.R. B.S.R. Ful-1, Garrard C62, 19/9.

POWER PACK KIT. Output 250 v. 50 mA. fully smoothed and 6.3 v. 1.5 a. Consisting of Mains Trans., Selenium Rectifier, Smoothing Choke, Double Electrolytic Condenser. Chassis 6in. x 3 1/2 in. and Circuit. Only 18/9.

P.M. SPEAKERS. 2-3 ohm. 2 1/2 in. Perdio 21/9. 5in., 17/9. 6in., 16/9. 8in., 19/9. 8 x 5in. 25/9. 10in. 26/9. 10 x 6in. 29/9. 12in. 29/11. 6in. W.V. Selenotorial 3 or 15 ohms type HF1012 10 watts, hi-fidelity type. Recommended for use with our A8 Amplifier. £4.10.9. 12in. Plessey 3 ohms 10 watts (12,000 lines). 59/6.

TWEETERS. Plessey 3 ohms 19/9. Rola-Celestion 7.5 ohms 25/9.


L63 MINIATURE 2-3 WATT GRAM AMPLIFIER. For use with any single or auto-change unit. Output for 2-3 ohm speaker. For 200-250 v. 50 c.p.s. A.C. mains. Over-all size 6 1/2 x 4 1/2 x 2 1/2 in. Controls: Vol. and Tone with switch. Guaranteed 12 months. Only 57/9.

SUPERHET FEEDER UNIT. Design of a high quality Radio Tuner Unit (specially suitable for use with any of our Amplifiers). Delayed A.V.C. employed. The W.Ch. Sw. incorporates Gram position. Controls are Tuning, W.Ch. and Vol. only 250 v. 15 mA. H.T. and L.T. of 6.3 v. 1 amp. required from amplifier. Size of unit approx. 9-6-7in. high. Simple alignment procedure. Point-to-Point wiring diagrams, instructions and priced parts list with illustration, 2/6. Total building cost £4/15/-. For descriptive leaflet send S.A.E.

E.M.I. 4-SPEED SINGLE RECORD PLAYER UNITS with turn-over crystal head for Stereo and Monoaural. Only £7/15/-, Carr. 4/6.

Mail Orders to 29-31 Moorfield Rd., Leeds 12. Callers to 5 and 7 County (Mecca) Arcade, Briggate, Leeds 1, and 8-10 Brown St. (Market St.), Manchester 2, or 56, Morley Street, (Next to Majestic Ballroom) Bradford.

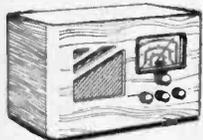**ALL OUR GOODS ARE AVAILABLE ON INTEREST-FREE
CREDIT TERMS— ★ SOME EXAMPLES: ★**



HOME RADIO
Cash Price 79/6

★ **5/1 1st WEEK
BALANCE AT ONLY
3/11 PER WEEK!**

A.C./D.C. Universal mains 5 valve octal superhet 3 waveband receiver can be adapted to gram p.u. In attractive wooden cabinet. 9½ x 18½ x 11½ in. Ins. carr. 4/6.

★ **Just 1/8 DEPOSIT—**
Balance at 10d. per week.

**PHOTOGRAPHIC
SLIDE CASE—**

17/6 Cash Price. P. & P. 2/6




XMAS MEMORIES CAPTURED ON FILM

Keep these pictures safe in one of our slide cases. Size 8 x 12½ x 2½ in. deep. Will hold 150 of those expensive coloured transparencies in separated partitions.

BAKELITE CABINETS

5/9

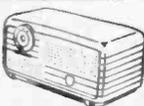Brand new. Colour brown. Attractive design. Size 12 x 7 x 5½ in. Ideal for small receivers, converters, etc. P. & P. 3/9.



T.V. AERIALS 23/6

For all I.T.A. channels. Outdoor or loft. 3 elements. P. & P. 2/6.

AERIALS 15/6

B.B.C. indoor type. Folded dipole with 12ft. co-ax cable fitted. Post 1/9.

T.V. AERIALS 7/9

For all channels. Complete with co-ax cable. For use indoors or in the loft. Post 1/3.

CO-AX CABLE 6d. yd.

Any length cut. Good quality. 1/6 postage on 20 yds.

IDEAL RADIO CHASSIS

5 volt superhet A.C. radio or radiogram 39/6

chassis. 3 waveband and gram switched Bin. P.M. speaker included. Valve line-up: 6K8, 6K7; 6Q7; 6V6; 5Z4 (not included). Chassis size 19½ x 7½ x 9 in. Knobs 2/- extra. Set of valves 45/9 extra. Complete set £4.5.0. Ins. carr. 5/6.

**RECORD PLAYER
CABINET R.P.6.**



★ **2/7**

initial deposit.

Balance payable at
1/5 per week.

Elegant cabinet, cloth covered in grey or red with sunken control panel and speaker fret. Size 13 x 17 x 8 in. deep. Takes a B.S.R. Monarch 4 speed autochanger; 7 x 4 in. elliptical speaker and most of the modern portable amplifiers. Carr. & Ins. 4/6.


Cash price 29/6

RECORD PLAYER CABINET

★ **6/1**

DEPOSIT

Balance at 4/11
a week.

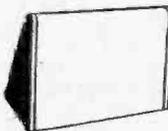

S.T.I.

99/6

Cash

Price

Continental style cabinet including extra clip on speaker cabinet. 15½ x 10½ x 24½ in. deep. Takes B.S.R. 4 speed stereo autochanger. Printed circuit amplifier. Two Bin. speakers. Carr. & Ins. 12/6.

STEREOPHONIC AMPLIFIER

★ **9/1 1st week. Balance at 7/11 a week.**

12 MONTHS GUARANTEE

Beautifully made for portable stereophonic record players. Latest design with printed circuit. Dimensions 3 x 5½ x 9½ in. A.C. only. Mains isolated. Twin amplifiers each side giving 3-4 watts output. Incorporating ECL82 triode pentode valve. Full tone, volume and balance controls. Complete and ready to fit. Knobs 3/6 per set extra. Carr. & Ins. 3/6. Cash price £7.19.6

**DUKE
& CO.**

★ **4/7 DEPOSIT—**
Balance at 3/5 per week.

A beautifully styled cabinet. Made by a famous manufacturer. In polka dot cloth with clipped lid and carrying handle. Size 16 x 14½ x 8½ in. deep. Will take B.S.R. Monarch 4 speed Autochanger and 7 x 4 in. elliptical speaker and most of the modern portable amplifiers. Carr. & Ins. 4/6.



CASH
PRICE
69/6

TRANSFORMERS:—

MAINS TRANSFORMER 5/9

Primary 200-250. Secondary 0-100-250. 150 mA. Suitable for small amplifier with J series valves. 2½ x 1½ in. P. & P. 1/9.

**OUTPUT TRANSFORMER
& SMOOTHING CHOKE
COMBINED** 4/9

2½ x 1½ in. Suitable for EL84s in single or push pull output. P. & P. 1/9.

MAINS TRANSFORMER 7/9

Primary 200-250. Secondary 300-0-300. 6 v. 3.3 amps. P. & P. 1/9.

MAINS TRANSFORMER 3/9

Primary 200-250. Secondary 250-0-250. 6.3 at 3 amps. 5 volts at 2 amps P. & P. 2/3.

**FRAME OUTPUT
TRANSFORMER** 1/9

500 ohms primary. 18 ohms secondary. P. & P. 1/6.

SMOOTHING CHOKE 5/9

250 mA
2nd. 40 ohms. D.C. Res. New. P. & P. 1/6.



**RECORD PLAYER
CABINET R.P.2.**

CARRIAGE AND INSURANCE MUST BE SENT WITH INITIAL PAYMENTS. TERMS ON THESE EXAMPLES ★ ARE FOR A PERIOD OF 20 WEEKS.

SOLO SOLDERING TOOL

12/6

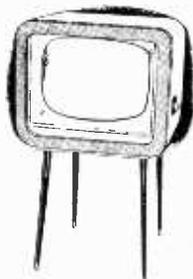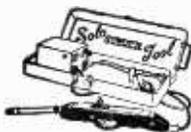110 v. 6 v. 12 v. (special adaptor for 200/250 v., 10/- extra). Automatic solder feed including a 20ft. reel of Ersin 60/40 solder and spare parts. It is a tool for electronic soldering or car wiring. Revolutionary in design. Instantly ready for use and cannot burn. In light metal case with full instructions for use. Post 3/6.



**★ 17" T.V.
19 GNS.**

CASH PRICE

OR 20/7 initial payment & 19 weekly payments of 19/11.

OR 11/1 initial payment & 35 weekly payments of 11/1.

(4 weekly payments required in advance before despatch—plus ins. carr. 30/-)

FEATURES

Beautiful latest finish cabinet in contemporary style covered and washable.

★ Polished legs 18in. optional extra for 25/-.

★ 17in. Rectangular Tube. Guaranteed fully for 12 months.

★ 12 channels "Turret Tuned"—ITV/B.B.C. (Extra coils at only 7/6 a pair with order.)

★ Chassis: 14 B.V.A. Valves—Salvaged but reconditioned and guaranteed 3 months.

Due to overwhelming demands, some delay may occur. Please enquire when ordering.

T.V. Chassis at clearance prices.

The popular 12in. Plessey chassis

9/6

A bargain for anyone wanting to make up their own T.V. at a very low cost. A chassis in one unit. Less valves and tube. Chassis size 12 x 14 1/2 x 11in. I.F.'s 10.5-14 Mc/s. Can be adapted for a 12 channel Turret tuner and modified to take a larger tube. Carr. & ins. 10/6.

SOUND/VISION & I.F. STRIP

7/9

Plessey. I.F. 10.5 Mc/s sound. 14 Mc/s vision. 8 valve holders. Less valves. Size 8 1/2 x 5 x 4 1/2in. Circuit incl. The tuner unit plugs directly into this chassis. P. & P. 2/6.

TIMEBASE

2/9

Containing scanning coils, line transformer, etc. less valves. Drawings free with order. P. & P. 2/6.

POWER PACK & AMPLIFIER

12/6

Output stage 6V6 with O.P. trans. 3 ohms choke smoothed H.T. 350 v. at 250 mA 6.3 v. at 5 amp 22 v. at 3 amp. 6.3 v. at 4 amp and 4 v. centre tapped. Less valves Ins. carr. 5/6.

13 CHANNEL TURRET TUNER

65/-

Brand new. Well-known manufacturer. 38 Mc/s. Complete with valves PCF80 and PCC84. 3 series line up and channel coils covering channels 1, 2, 3, 4, 5, 8 and 9. Carr. & ins. 3/6.

FAMILY RADIO

99/6

5 valve (octal) superhet. A.C. 3 waveband and gram. position. 4 controls. Modern attractive cabinet size 15 1/2 x 18 x 10 1/2in. In cream and brown. Carr. & ins. 8/6.

SUPER SUPERIOR RADIO


89/6

4 waveband. 5 valve superhet radio. 2 tone covered metal cabinet. Size 24 1/2 x 12 x 10in. deep. 4 control knobs. Position for gram p.u. and extension speaker. A.C. only. Ins. carr. 8/6.



SUPER CHASSIS 79/6

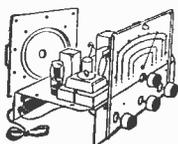5 valve superhet chassis including 8in. P.M. speaker and valves. Four control knobs (tone, volume, tuning w/change switch). Four w/bands with position for gram. p.u. and extension speaker. A.C. Ins. carr. 5/6.



**REPLACEMENT
RE-BUILT
T/V TUBES**



CASH PRICE **£8.10.0**

12 months' full guarantee.

All sizes except 10in. Completely rebuilt gun assembly new cathode, heaters, etc., giving the high standard required for long picture life, quality and value. Carr. & ins. 15/6.

OR Yours for 8/6 initial payment (plus carr. & ins.) and 19 weekly payments of 8/6.



**FROM OUR NEW RANGE OF
CONTINENTAL TYPE RECORD
PLAYER CABINETS**

In gay two-tone colours.

T.W.1 CABINET

79/6

Size 15 1/2 x 19 1/2 x 10 1/2in. Takes B.S.R. U.A.8 4-speed auto-changer, twin speakers. 3 control amplifier. Carr. & ins. 4/6.

**World's Finest
AUTOCHANGERS**

**U.A.8. B.S.R.
MONARCH 4-SPEED
AUTOCHANGER
£6.19.6**



COLLARO CONQUEST 4 SPEED AUTOCHANGER 28.19.6.

U.A.12 LATEST B.S.R. MONARCH 4 SPEED MIXER 28.9.6.

COLLARO CONQUEST STEREO AUTOCHANGERS 11 gns

P. & P. on all the above 5/6.

PORTABLE AMPLIFIER MK. D.3

89/6

De luxe model. Printed circuit. Latest design. Dimensions 7 x 2 1/2 x 5in. A.C. only. Mains isolated. 3-4 watts output. Incorporating the latest ECL82 triode pentode output valve giving higher undistorted output. Volume, treble & bass control. Knobs 3/6 extra. P. & P. 3/6.

EXTENSION SPEAKERS

19/9



Polished oak cabinet of attractive appearance. Fitted with 8in. P.M. speaker W.B. or Goodmans of the highest quality. Standard matching to any receiver (2-5 ohms). Switch and flex included. Ins. carr. 3/9

IDEAL FOR STEREOPHONIC SOUND

8in. P.M. Speakers, 8/9. With O.P. trans fitted, 10/-. Post 2/6. 7 x 4in. Elliptical speakers, 19/6. 9 1/2 x 4 1/2in. Elliptical speakers, 22/6. Post 2/9.

DUKE & CO.

(Dept. D.1),

621/3, ROMFORD ROAD, MANOR PARK, E.12.

Tel.: ILF. 6001/3

DEFERRED TERMS TO SUIT ALL POCKETS.


MONTHLY CREDIT TERMS OR WEEKLY EASY PAYMENTS—
DETAILS ON REQUEST.

Here are some new models



F.M. TUNER
£13.12.6

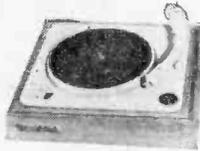R.F. TUNING UNIT and I.F. AMPLIFIER AVAILABLE SEPARATELY



RP-1U
£12.10.0

“PACKAGED DEALS”

The above models and others, can be obtained as parts of “packaged deals” of **MATCHED STEREO HI-FI EQUIPMENT**, thereby saving you additional money.

FREE DELIVERY IN U.K.
DEFERRED TERMS AVAILABLE OVER £10.

TRANSCRIPTION RECORD PLAYER. Embodies new Collaro RP594 unit with the Ronette Stereo Pick-up. Gives excellent results on stereo or mono. (33, 45 L.P. or 78 r.p.m.) discs. Detachable head and supplied with wooden plinth.

THE ‘COTSWOLD.’ An acoustically designed 3-unit Speaker System capable of doing justice to finest programme sources. Range 30-20,000 c/s. All parts left “in the white” for finish to personal taste.

THE “GLOUCESTER” cabinet has been specially designed to meet the varying needs of different homes. Mk. I houses Record Player Stereo Amplifier, F.M. Tuner and records, etc. The Mk. II will house a Tape Deck in addition.



THE “COTSWOLD”
£19.18.6



THE “GLOUCESTER”
Mk. I £15.18.6
Mk. II £17.8.6

Why not send for Free Catalogue !

Other models include

TRANSISTOR PORTABLE model UXR-1. This dual-wave, 6 transistor portable radio, strikingly styled in handsome solid leather case, is universally admired. The tone is rich and brilliant and it performs well everywhere, including in a car. Easily built in 6 hours..... **£15.18.6**

TRANSISTOR JUNIOR RADIO model UJR-1. Ideal for youngsters. Novel circuit gets lots of stations..... **£2.16.6**
(Additional amplifier stage, 16/6 extra)

HI-FI 16 W. STEREO AMPLIFIER model S-88. World's finest 16 Watt Stereo amplifier regardless of price. 0.1% distn. at 6 W./chnl. The attractively styled S-88 has many excellent features **£25. 5.6**

HI-FI 6 W. STEREO AMPLIFIER model S-33. World's best value in low-price Stereo. 0.3% distortion at 2.5 W./chnl. Ideal for average room..... **£11. 8.0**

HI-FI SPEAKER SYSTEM model SSU-1. Ideal for Stereo in average living-room where cost must be low. Two speakers in the enclosure..... **£10. 5.6**
(Legs, £17.0 extra)

R/C BRIDGE model C-3U. Measures Capacitance, 10 pF (0.00001 μF) to 1,000 μF; Power Factor; Resistance, 100 Ω to 5 M Ω and indicates leakage. Automatic Discharge Safety-Switch **£7.19.6**

AUDIO SIGNAL GENERATOR model AG-9U. 10 c/s to 100 Kc/s. Sine-wave output 10 V. f.s.d. down to 3 mV. f.s.d. Less than 0.1% distortion (20 c/s to 20 Kc/s). Decade frequency selection. Decibel ranges, -60 to +22. 1% precision resistors **£19. 3.0**

VALVE VOLTMETER model V-7A. World's most popular VVM. Measures volts, ohms and decibels. D.C. sensitivity 7,333,333 ohms per Volt **£13. 0.0**

5 in. OSCILLOSCOPE model O-12U. This fine general-purpose 'scope has “Y” sensitivity of 10 mV/cm, and covers 3 c/s to over 5 Mc/s. Rise time is 0.08 μ secs or less. Timebase 10 c/s to 500 Kc/s in 5 steps. Electronically stabilised. Voltage calibrator **£34.15.0**

DIRECT READING CAPACITANCE METER model CM-1U. 4 1/2 in. meter scale calibrated in μF and pF. Full scale deflection 100 micro-microfarads, 1,000 micro-microfarad, 0.01 microfarad, 0.1 microfarad **£14.10.0**

DX-100U AMATEUR TRANSMITTER. The most popular Amateur transmitter in the world. 100-140 watts output. 160, 80, 40, 20, 15 or 10 metres..... **£78.10.0**

DX-40U AMATEUR TRANSMITTER. 40 Watts to aerial. 75 W. C.W., 60 W. pk. C.C. 'phone. Provision for V.F.O. Designed by “Hams” for “Hams” **£29.10.0**

Without obligation please send me **FREE CATALOGUE** (Yes/No).....

Full details of model(s)..... **Deferred Payments** (Yes/No).....

NAME
(BLOCK CAPITALS).....

ADDRESS.....

DAYSTROM LTD., DEPT. PW. I,
GLOUCESTER, ENGLAND

A member of the Daystrom Group, manufacturers of
THE LARGEST-SELLING ELECTRONIC KITS IN THE WORLD.

Practical Wireless

VOL. XXXV, No. 635, JANUARY 1960

Editorial and Advertisement

Offices :

PRACTICAL WIRELESS

George Newnes, Ltd., Tower House,
Southampton Street, Strand, W.C.2.

©George Newnes Ltd., 1960.

Phone : Temple Bar 4363.

Telegrams: Newnes, Rand, London.

Registered at the G.P.O. for trans-
mission by Canadian Magazine Post.

SUBSCRIPTION RATES

including postage for one year

Inland - - - - - £1.3.0 per annum

Abroad - - - - - £1.1.6 per annum

Canada - - - - - 19s per annum

Contents

	Page
Editorial	733
Round the World of Wireless	736
Using the R.F.24	736
Becoming an Amateur	739
Preventing I.F. Breakthrough	742
A Transistor Reflex Receiver	743
Beginners' Test Meter	747
On Your Wavelength... ..	750
Three-Waveband Superhet	751
An Inexpensive T.R.F.	757
A Quality V.H.F./F.M. Receiver	760
Choosing Capacitors	764
A Transistorised Mixer Unit	765
Improving Amplifier Quality	769
A.C. Pre-tuned Superhet	773
Calculating Resistor Values... ..	777
A Crystall Receiver and Ampli- fier	781
News from the Clubs	786
News from the Trade... ..	789
Open to Discussion	793

The Editor will be pleased to consider articles of a practical nature. Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed: The Editor PRACTICAL WIRELESS, George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Owing to the rapid progress in the design of wireless apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in PRACTICAL WIRELESS is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. PRACTICAL WIRELESS incorporates "Amateur Wireless."

IMPORT CONTROLS

IN a written reply to a Parliamentary Question, the President of the Board of Trade, Mr. Reginald Maudling, announced that most of the remaining controls on imports from the Dollar Area, Western Europe, and a number of other countries were to be removed with effect from Monday, November 9th. The continuing strength of the £ and of the balance of payments position of the United Kingdom has enabled more progress to be made in freeing trade.

From our point of view the most interesting part of the announcement is that electrical equipment and apparatus is included in the list of freed goods. This heading includes valves but not transistors, although the reason for the omission of transistors is not clear. It seems to us that relaxation of import control of transistors would be of benefit both to industry and to the home constructor.

CLUB REPORTS

WE are always pleased to print reports of club activities whether past, present or future, and such insertions are free. As we have previously pointed out, to assist us in the preparation of "News from the Clubs," club reports should be sent, whenever possible, in the style in which we print them. The title of the club should be given first, followed by the meeting place, the name and address of the secretary, reports of past activities, and finally, future events. We adopt this method of presentation because it is easy to follow and because the reports tend to be uninteresting to readers unless there is some uniformity.

Reports should reach us well in advance; on or before the first of the month preceding the issue in which the report is to appear. Any "future events" listed should, of course, occur after the issue concerned is published and, in general, reports should include information of interest to readers who are not members of the club.

CONTRIBUTIONS

THOSE of our readers who wish to submit articles should send them direct to the Editor at the address given on this page. Manuscripts should be typewritten with double spacing although legible hand-written articles are also acceptable. Articles should be between 1,000 and 2,000 words in length, be written on one side of the paper only, and deal with the home construction of items of radio and electronic equipment. We do not require articles of a theoretical nature unless these are written expressly for the amateur constructor. Clear drawings of the apparatus should be included with the article and need only be sufficient for our draughtsmen to prepare suitable illustrations. We also like to include with articles photographic illustrations. Large clear prints, or preferably negatives, should be sent if possible but we are prepared to take the necessary photographs ourselves if the apparatus can be sent to us for inspection. An illustrated article is always of more appeal as the methods of construction are shown more clearly.

Our next issue, dated February, will be published on January 7th

Round the World of Wireless

POTENTIAL AND CURRENT NEWS

Broadcast Receiving Licences

THE following statement shows the approximate number of Broadcast Receiving Licences in force at the end of September, 1959, in respect of wireless receiving stations situated within the various Postal Regions of England, Wales, Scotland and Northern Ireland. The numbers include Licences issued to blind persons without payment.


Region	Total
London Postal	869,184
Home Counties	857,971
Midland	636,090
North Eastern	726,396
North Western	585,002
South Western	511,480
Wales and Border Counties	315,813
Total England and Wales ...	4,501,936
Scotland	542,662
Northern Ireland	154,823
Grand Total	5,199,421

Commonwealth Cable Order

AN order has been placed by Cable & Wireless Ltd. for 1,635 nautical miles of light-weight, co-axial, deep-sea cable for the first section of the Commonwealth round-the-world telephone cable at a cost of £2,300,000. The cable will be laid between Scotland and Newfoundland in the summer of 1961, and will be made by Submarine Cables Ltd., of London, at their Greenwich factory. The estimated total cost of the trans-Atlantic section of the cable, which will carry 60 simultaneous telephone conversations, is £6,000,000. It is being jointly financed by Cable & Wireless Ltd. and the Canadian Overseas Telecommunication Corporation.

Technical articles

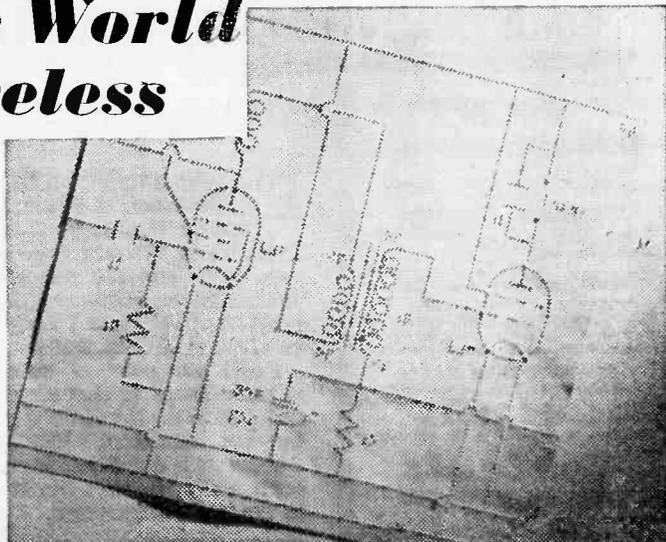THE scheme for awarding annual premiums for articles on electronics, organised in the past by the Radio Industry Council (London) is now under the joint sponsorship of the Council and of the Electronic Engineering Association. Articles published during 1959 will be considered by the panel



The Royal National Institute for the Blind is aware of the interest taken by its readers in technical literature and the illustration above shows part of one of the many embossed diagrams in a recently brailled book on radio engineering.

of judges early in the New Year, and explanatory leaflets can be obtained from the Electronic Engineering Association, 11, Green Street, London, W.1, to whom also eligible articles should be submitted before the end of the year.

Six premiums of 25 guineas are offered to writers not earning their living wholly or mainly by writing. The judges, headed by Professor H. E. M. Barlow, Professor of Electrical Engineering, University College, London, are given the greatest possible freedom in allocating awards, but main factors taken into consideration are:—

The value of the article in making known British achievements in radio and electronics; originality of the subject; technical interest; and presentation and clarity.

Articles published abroad as well as in the United Kingdom are eligible as are articles in journals serving the many fields in which electronic methods of control and production are being increasingly used.

Equipment for India

AN agreement has been concluded between Marconi's Wireless Telegraph Company and the Government of India

(Ministry of Defence) for the manufacture under licence in India of Marconi V.H.F. multi-channel radio terminals and repeaters, and ancillary equipment. The Marconi V.H.F. multi-channel radio equipments to be manufactured in India are the HM 100 series, used by telecommunications authorities in many parts of the world, including India, where they are used on the railway network. This series was developed by Marconi's for use in terrain unsuitable for the construction of line or cable routes. They are designed to carry up to 48 telephone channels, any of which may be sub-divided to give either 18 or 24 telegraph channels.

New British Standard

THIS standard deals with Fixed carbon resistors for use in telecommunication and allied electronic equipment—Part 1: general requirements and tests. B.S. 2112: Part 1: 1959 applies to fixed carbon resistors having a dissipation not exceeding 3watts at 70 deg. C. and a rated resistance value of not less than 10ohms and not greater than 10megohms. The resistors to which this standard applies are intended for use over the

ambient temperature range—40 deg. C. to + 100 deg. C. in one of the humidity classes (H1, H2, H3 or H3A) of B.S.2011. "Basic climatic and durability tests for components for use in radio and allied electronic equipment."

The new publication specifies *general requirements and tests*. Part 2, which is to follow, will give a list of standard sizes, ratings, etc.. of resistors.

The standard colour code for the indication of resistance value, tolerance, and, in certain instances the grade of resistors, is described in an Appendix to Part 1.

Copies of this standard may be obtained from the British Standards Institution, Sales Branch, 2, Park Street, London, W.1. Price 10s. (Postage will be charged extra to non-subscribers.)

Philips S.W. Headquarters

PHILIPS ELECTRICAL LTD. has recently opened a new and enlarged headquarters for their South West region at 51, Victoria Street, Bristol. The new building covers an area of over 17,000sq. ft. and occupies an island site bounded by St. Thomas Street, St. Thomas Street East, Long Row and Victoria Street. It has four storeys which house offices, stores, a trade counter, a modern public showroom for the display of the firm's products and various other departments.

A special feature of the showroom, designed by J. Lohman, is that many of the items on show are mounted on movable stands. This allows for greater flexibility of layout and also permits the showroom to be converted into a lecture room. A section devoted to electrical appliances has full demonstration facilities, and the lighting section includes a selection of lamps for all purposes, and a display of fittings. A sales and service centre to cover the whole of Wales and the West is situated on the top floor and also the drawing offices of the Lighting Design Service. The building also has a Hearing Aid Centre. Equipped with the very latest apparatus for conducting hearing tests, it is staffed by fully-qualified audiometricians.

New Branch

A NEW branch office at 247, Western Road, Leicester, has recently been acquired by Siemens Edison Swan Ltd. for their customers in Leicestershire, Northants and Rutland. Easier access for lorries and vans and car parking facilities for customers are two immediate advantages over the old premises in Leicester's congested High-cross Street. Additionally, new buildings to be erected will mean better service facilities.


"Talking" Books

"IT would be difficult to express the amount of sheer bliss the talking book library affords one." So writes one of the 5,500 "readers" of the unique library

said amateur radio and sound recording enthusiasts throughout the country who render us such magnificent help in servicing the machines. Their generosity in giving so freely of their time and skill not only frequently reduces the period during which a faulty instrument may be out of use, but also relieves the owner of the cost of the necessary repairs."

Radar Installation for

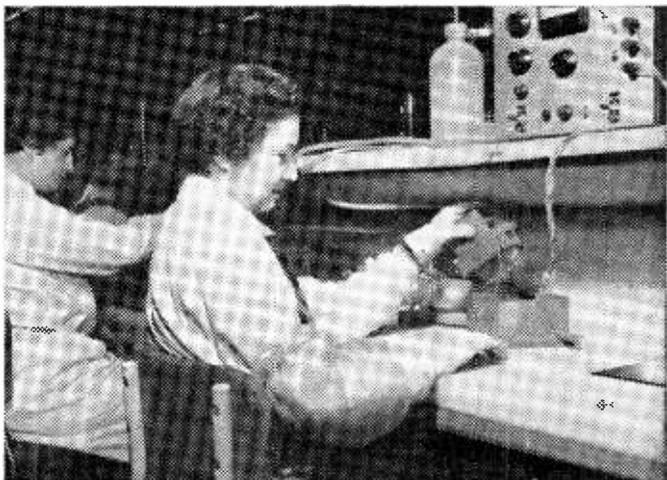Wellington (N.Z.) Airport
WELLINGTON AIRPORT, which has just been officially opened, is the first airport in the world to have a high-power (500kW) 50cm radar installation. This has been supplied and installed by



The recently built Mullard Semiconductor Plant at Southampton is one of the most advanced in the country and work is proceeding to enable transistors to be mass-produced. Here, a batch of silicon alloy transistors is about to be finally etched to attain the desired characteristic.

of long-playing gramophone records which provides so much companionship and entertainment to the elderly and the house-bound blind.

The care taken to select for recording only the best examples of books from a wide range of categories is reflected in the continued steady increase in reading by individual members.

In the latest report of the executive council, the R.N.I.B. states:


"It is with sincere pleasure that we record the grateful thanks, not only of ourselves but of our members to the two thou-

Marconi's who were awarded the contract after an exhaustive independent evaluation of other radars available in Europe and the U.S.A. The equipment supplied is the Marconi Type S264A, with a dual transmitter/receiver installation, either unit of which can be switched to a common radar aerial. Two-way microwave radio links are provided, over which the radar signals are passed to displays at the airport and the airways control centre four miles away; the links also provide a path for the remote control of the radar head.

Using the RF24

THIS EX-GOVERNMENT UNIT CAN BE USED WITH MANY RECEIVERS

By D. Noble and D. Pratt

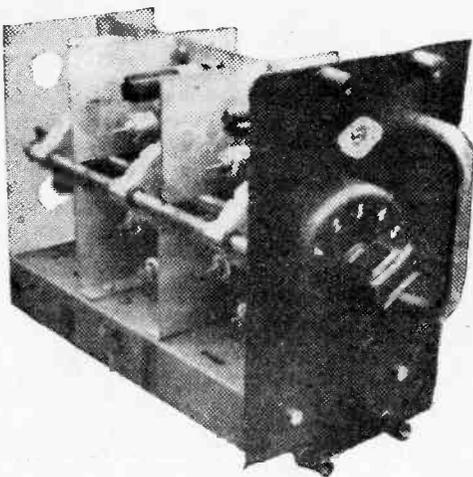

MANY receivers have a maximum frequency range such that they are unable to receive transmissions on the 14, 21 and 28Mc/s amateur bands. Many people are, therefore, faced with the problem of how the frequency range of their receiver may be extended without too much trouble.

Crystal Control

The cheaply-obtainable R.F.24 unit, is, in its original condition, very suitable for use as a converter for 21 and 28Mc/s. It has, however, certain drawbacks. The oscillator tends to drift, and thus it cannot be accurately calibrated. By using a crystal oscillator circuit in place of the original variable local oscillator, however, and if the

receiver dial at 6Mc/s. and 30Mc/s will be on 8Mc/s, and the intermediate frequencies pro-rata.

By careful selection of a local oscillator crystal, it can be arranged that either the fundamental or the second or third harmonics will give approximately the same I.F. output frequency for each of the 14, 21 and 28Mc/s amateur bands. A different crystal may be used for each band, of course, but then the cost may become prohibitive, while if a crystal is chosen so that the I.F. frequencies corresponding to the three bands differ widely from each other, it will be necessary to add another switch wafer to retune the I.F. coil of the converter to the appropriate frequency for each band.

TABLE I

Switch position	R.F. paddler	Mixer paddler
1	82 pF (C43)	150 pF (C46)
2	15 pF (C44)	47 pF (C47)
3	15 pF (C45)	47 pF (C48)
4	not required	not required
5	not required	not required

receiver with which the converter is used is suitably calibrated, there will be no need to calibrate further. Say we had a local oscillator frequency on 22Mc/s, then 28Mc/s will appear on the

"Birdies"

If crystals of certain frequencies are chosen it will be found that as the receiver is tuned over the I.F. frequencies concerned a number of apparent carriers will be heard. These are not a

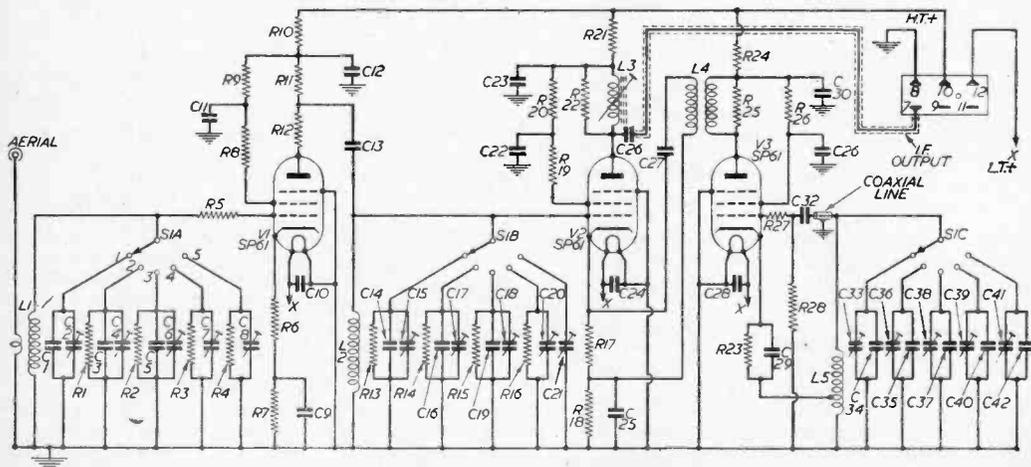


Fig. 1.—The original circuit diagram.

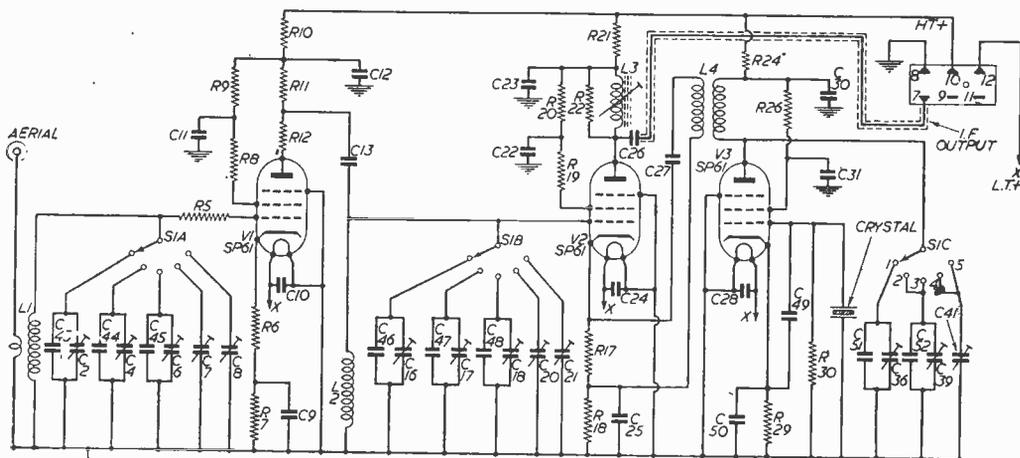


Fig. 2.—The modified circuit diagram.


number of thoughtless people who have left their transmitters running by mistake, but they are what are known as "birdies." These are caused when the I.F. tuning range is extended over the local oscillator harmonics and fundamental frequency. If a 7.5Mc/s crystal is employed, then, apart from the harmonics of the receiver local oscillator appearing on the converter input frequency range, the only "birdy" caused by the converter itself will be on the fourth harmonic of the crystal on 30Mc/s and can be put to good use as a band edge marker (see Table II).

Before commencing modification, the R.F.4 converter should be tested in its original form so that if it is faulty, it can be ascertained that any fault is not due to the modifications. After connecting up as indicated in Fig. 1, with a short aerial, signals should be received when the main receiver is tuned around the I.F. frequency of about 7.5Mc/s.

Procedure

The first stage in the modifications is to remove all the padding condensers and damping resistors connected in parallel with the concentric trimmers. The wiring of the oscillator stage above the chassis should be stripped, and the oscillator

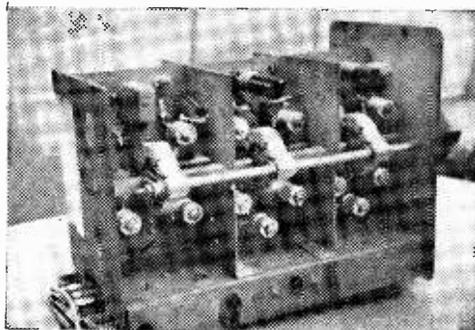trimmers for ranges 1 and 3 removed. The coaxial line fastened to the dividing screen should be taken out as should also the oscillator grid coil. There should now be sufficient space avail-



able in which to fit the 7.5Mc/s crystal and its holder, and the crystal oscillator can be wired up according to Fig. 2.

Padding condensers should be fitted across the trimmers of the R.F. and mixer stages, and are given in Table I.

The damping resistor across the oscillator anode coil is not necessary, and may be removed. Also, so as to enable the oscillator anode coil to tune on each

Switch position	Converter freq. range	Local oscillator harmonic used	I.F. tuning range	Tune R.F. and mixer stages on :
1	Mc/s 14.0-14.35	Mc/s 7.5	Mc/s 6.5-6.85	Mc/s 14.2
2	21.0-21.2	15	6.0-6.2	21.1
3	21.2-21.45	15	6.2-6.45	21.3
4	28.0-29.0	22.5	5.5-6.5	28.5
5	29.0-30.0	22.5	6.5-7.5	29.5

band, five turns should be taken off its winding.

Alignment

The converter is now ready for testing. It should be connected to a suitable power supply, and its output fed into a receiver. The converter is switched to each position in turn, and the receiver tuned to a signal at about the centre

COMPONENTS LIST


C1, C42, C44, C45, C49	15pF
C2, C4, C6, C7, C8, C15, C17, C18, C20, C21, C33, C36, C38, C39, C41	3-30pF trimmers
C3, C19, C26	10pF
C5	5pF
C9, C11	0.001 μ F
C10, C12, C22, C23, C24, C25, C28, C29, C30, C31	300pF
C13	100pF
C14	40pF
C16, C37	25pF
C27, C32	50pF
C34	35pF
C35	30pF
C40	20pF
C43	82pF
C46	150pF
C47, C48, C50	47pF
C51	680pF
C52	22pF
R1	3,900 ohms
R2	4,700 ohms
R3	6,200 ohms
R4	6,800 ohms
R15, R17, R27	47 ohms
R6	27 ohms
R7, R19	100 ohms
R8	12 ohms
R9, R16, R22, R26, R28	10,000 ohms
R10, R14, R21, R24	2,200 ohms
R11	3,000 ohms
R12	22 ohms
R13	1,500 ohms
R15	3,600 ohms
R18, R25	1,000 ohms
R20	100,000 ohms
R25	2,400 ohms
R29	270 ohms
R30	68,000 ohms
V1, V2, V3	Mazda SP61 (VR65)
S1	3-bank, 3-pole, 5-way ceramic switch
Xtal	7.5 Mc/s quartz crystal

COMPONENTS REMOVED DURING MODIFICATION :

C1, C3, C5, C14, C16, C19, C29, C33, C34, C35, C37, C38, C40, C42, R1, R2, R3, R4, R13, R14, R15, R16, R23, R27, R28.

COMPONENTS ADDED DURING MODIFICATION :

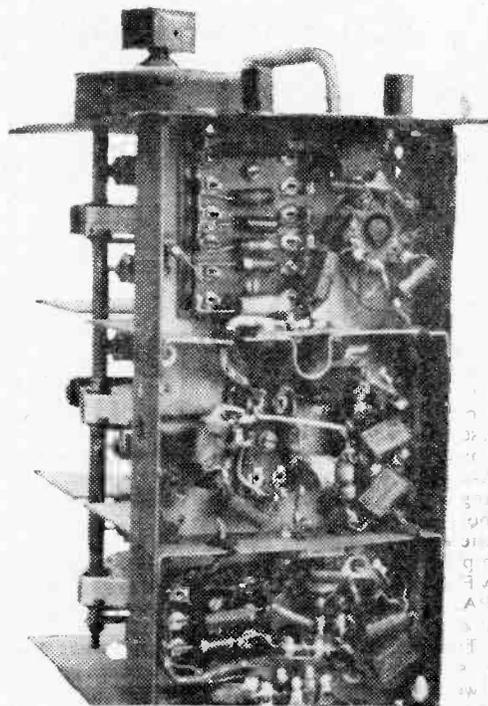C43, C44, C45, C46, C47, C48, C49, C50, C51, C52, R29, R30, 7.5 Mc/s crystal.



modified to crystal control has the advantage that the frequency is accurately known, and it is, therefore, more suitable for serious amateur radio listening.

Books Received

Principles of Frequency Modulation

THIS book is intended primarily for students, radio engineers and radio amateurs. In concise form and logical sequence it gives a comprehensive account of the fundamentals of frequency modulation and its application. This book is published by Illiffe & Sons Ltd., Dorset House, Stamford Street, London, S.E.1, and costs 21s., postage 10d. extra. It consists of 147 pages and 87 diagrams. The size of the book is 8 $\frac{1}{2}$ in. X 5 $\frac{1}{2}$ in. The contents include Basic Principles of Frequency Modulation, Theory of Frequency Modulation, Frequency Modulation and Interference, F.M. Receivers, etc. Now that the incorporation of V.H.F. in broadcast receivers is standard practice this book is of great value for all radio technicians and students.

The Television Annual for 1960

THIS year's edition of the Television Annual includes many interesting articles by television personalities including Tommy Steele, Charlie Drake, Dr. Bronowski, Sir Kenneth Clark, Peter Scott, Max Jaffa, Perry Como and Gilbert Harding. It is published by Odhams Press Ltd., 96, Long Acre, London, W.C.2, and costs 10s. 6d. It consists of 158 pages and many photographs of television actors, actresses and personalities.

frequency of the range given in Table II, column 4. The corresponding trimmers in each stage should then be tuned for maximum response either aurally, or by the deflection of the S-meter if the receiver has one fitted.

Many amateur stations use the R.F.24 both as modified and in its original form: but the unit

Becoming an Amateur

No. 5.—AMATEUR ABBREVIATIONS AND MORE RADIO THEORY

By J. D. Pearson, G3KOC

MANY beginners are discouraged when first tuning the amateur bands by the apparent gibberish spoken between licensed stations. This is due to the use on phone (telephony) of certain abbreviations and slang terms designed originally for use on C.W. (telegraphy), in order to speed up communication. Some of these words are obvious contractions, such as "condx" for "conditions," "XYL" for "wife" (ex-young lady), and so on. Others are pure slang derivations, i.e., "cans" for "headphones," "bottles" for "valves." Another practice, hastened no doubt by war-time brevity, is to use simply the initial letters of words, as with "VFO" for variable frequency oscillator, and "PA" for power amplifier. A full and complete list of the abbreviations in current usage is given in Table I. With this by his side the newcomer to short-wave listening can follow contacts between amateurs with interest, and when licensed will find this list absolutely essential. In order to develop familiarity with these terms they will be used where necessary throughout the remainder of this series.


Circuit Diagrams

Before attempting construction of any type of radio or electronic gear the beginner must be able to "read" a circuit-diagram. This consists of a composition of various printed signs and symbols, each of which represents a particular component; it shows also the quantity and value of individual components, and their electrical disposition. A circuit-diagram should not be confused with a wiring diagram, which shows the physical disposition of various components which go to make up a completed piece of equipment. It is the practice of this magazine to give both circuit and wiring diagrams, except in the case of extremely simple circuits.

A working knowledge of the various signs and symbols used in radio circuitry, and the units used to express capacity, inductance and resistance can be gained by reference to the publications mentioned in previous articles.

Ohm's Law

This is a simple law dealing with the relationship between current, voltage and resistance which states that if any two of the quantities are known the third can be calculated. No apology is made for dealing with so basic a principle here as correspondence shows that several readers, when seeing the question on calculation of power input and R.F. output in copies of past R.A.E. examination papers, have expressed inability to tackle

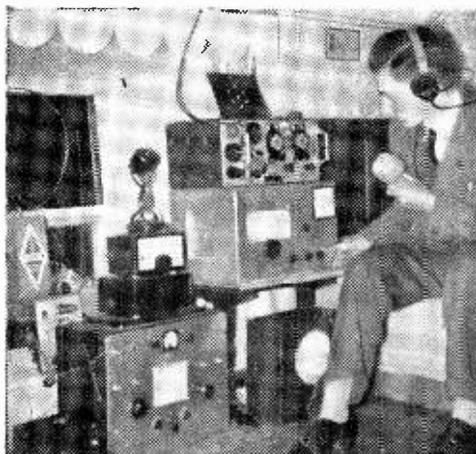

D. W. Dillon of Ballycastle in his den.

the question. They are either not familiar with Ohm's Law, or have failed to appreciate that the question is designed to test the candidate's knowledge of this law.

In the following formulae the letter "E" represents voltage, "I" current and "R" resistance. Ohm's Law states that:—

$$E=I \times R, I=\frac{E}{R} \quad R=\frac{E}{I}$$

It will be seen that two of the equations involve division, whilst the first requires multiplication. An aid to memory is the fact that in the equation involving multiplication the addition of an "e" would cause it to read the name of the Irish Republic—"EIRE." And if one remembers also that in the two equations involving division the "E" is always at the "top," a second's thought will always produce the required formula.

Analogy

When dealing with calculations involving Ohm's Law, the beginner may obtain assistance from a useful analogy: A large-bore horizontal pipe filled with water, such as a water main, is connected at one end to a water pump. When the pump is started the "pressure" behind the resultant flow represents the voltage; the "rate-of flow" past a given point on the pipe represents the current; and the inside diameter, or "bore" of the pipe represents resistance.

Consideration of the above analogy will reveal what occurs in a comparative circuit containing direct current, voltage and resistance. Circuits involving A.C. will be dealt with at a later stage when discussing A.C. theory.

Current and voltages are always referred to in whole numbers, or fractional parts of amps or volts. Resistance is measured in "ohms," after the scientist who established the theory which bears his name. The circuit symbol for ohms is the Greek letter Omega, thus: Ω .

Several prefixes are in common use in connection with electrical quantities; these are given in Table II. It is essential when using Ohm's Law to ensure that all quantities are expressed

as whole or fractional parts of the *basic* unit before multiplication or division takes place. For instance, multiplying 250mA by 100 ohms directly will result in the completely erroneous figure of 25,000 volts. The calculation should, of course, be set down as 0.25amps \times 100ohms, which gives the correct result as 25V. This is an elementary mistake, but one often made on R.A.E. examination papers.

Watts

There are two further simple formulae with which the beginner must become thoroughly conversant. These state respectively that:—

$$W = E \times I \text{ and also } W = I^2 \times R$$

where $W = \text{Watts}$.

To illustrate the use of these two formulae it is proposed to examine in detail a typical question from an R.A.E. examination paper. The following information is usually given in the question:—

The D.C. input to the final anode of the power-amplifier stage of a transmitter is 1,000V at 100mA. The measured R.F. current in the aerial, which has a radiation resistance of 75 ohms, is 1 amp. State:—

- The power input.
- The power output.
- The anode dissipation.
- The stage efficiency.

A compound question of this nature usually carries 15 marks. The reader should be able to answer parts (a) and (b) confidently, using the basic formulae already given. If he feels he cannot do so he should turn back to the heading "Ohm's Law" and study the formulae again. A little intelligent detective work should reveal the answer to part (c) although admittedly this has not yet been discussed. Part (d) will be obvious only if the first three parts have been answered correctly.

Calculation

Let us first examine part (a) more fully. The question asks for an expression of power. Power is expressed in watts, and we have seen that W can equal volts \times amps, or alternatively, amps squared \times resistance. The first equation would seem more suited to our immediate needs because the question gives us circuit values which will fit the formulae. By substitution, therefore, we have:—

$W = E \times I$ (or $W = A \times V$) = 1,000V \times 0.1A (remembering that we must convert 100mA into 0.1A, as required by Ohm's Law) = 100W. This is the power input.

Using exactly the same procedure we can determine the power output, but this time we find the wattage formulae we require is $I^2 \times R$. At this stage we may not be quite sure as to what is meant by the term "radiation resistance," but let us rest content that we have found a value for substitution in our equation. We have now then:— $W = I^2 \times R = 1\text{amp} \times 1\text{amp} \times 75\text{ohms} = 75\text{watts}$. This is the power output.

Anode Dissipation

Unless any piece of radio or electrical equipment is 100 per cent. efficient (which it never is) the power output must be less than the power input. This power-loss occurs by way of heat losses in the form of radiation primarily, but there are other factors involved.

In the final power-amplifier stage of a transmitter power is lost chiefly by way of heat dissipation. A badly designed P.A. coil and poorly insulated tuning condensers will also contribute to lowered efficiency.

It will be seen, therefore, that anode dissipation equals power input minus power output, the case under discussion being 100W - 75W = 25W. This is a realistic figure, and a transmitter providing these figures which represent an efficiency of

TABLE 1.—SOME OF THE COMMONER ABBREVIATIONS USED BY AMATEURS.

abt	—about	gb	—goodbye	sigs	—signals
agn	—again	ge	—good evening	SWL	—Short Wave Listener
ani	—any	gld	—glad	tk	—thanks
ant	—antenna	gnd	—ground	tnx	—thanks
BC	—broadcast	gud	—good	tu	—thank you
BCL	—broadcast listener	hi	—laughter	tx	—transmitter
BCI	—broadcast interference	hpe	—hope	tvi	—Television interference
cct	—circuit	hr	—here	u	—you
clg	—calling	hrd	—heard	ur	—your, you're
CO	—crystal oscillator	hve	—have	vfo	—Variable Frequency Oscillator
cpse	—counterpoise	kes	—kilocycles	vy	—very
CQ	—Require qso	mni	—Many	WX	—weather
condx	—conditions	mcs	—Megacycles	wid	—with
cul	—see you later	nw	—now	wkd	—worked
de	—from	ob	—old boy	wl	—will
dx	—long distance	om	—old man	wud	—would
ECO	—Electron coupled oscillator	op	—operator	xmtr	—transmitter
ere	—here	pa	—Power Amplifier	Xtal	—crystal
es	—and	pse	—please	XYL	—wife (ex young lady)
fb	—fine business	R	—all received	YL	—young lady
fer	—for	rppt	—report	73	—Best regards
fone	—telephony	rx	—receiver	88	—Love and kisses
		sa	—say		
		sed	—said		

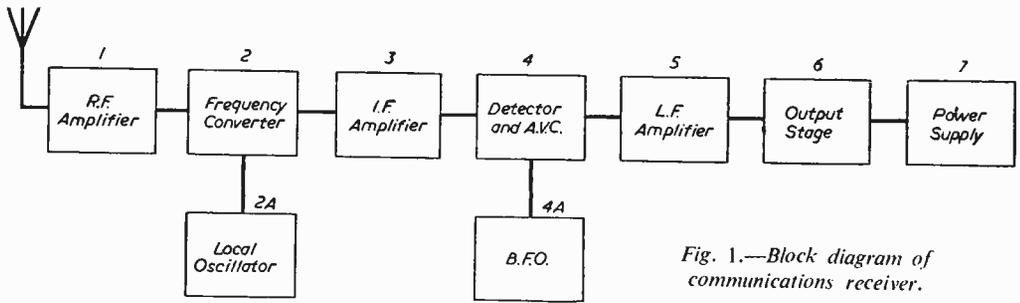


Fig. 1.—Block diagram of communications receiver.

75 per cent. would be considered quite satisfactory.

Stage Efficiency

The efficiency of any device, whether mechanical, electrical, electronic or hydraulic is usually expressed as the ratio of input to output, in terms of a percentage. This is the case with the problem under analysis, and we find that a simple formula can be derived which will cover all similar problems:—

$$\text{Stage efficiency (\%)} = \frac{\text{Power output (W)}}{\text{Power input (W)}} \times 100.$$

Calculation Practice

The beginner should now be in a position to set himself various problems involving Ohm's Law and obtain the right answer every time.

PREFIXES		
Sign	Expression	Explanation
k	kilo 10 ³	X 1,000
m	milli 10 ⁻³	one thousandth part of
M	Mega 10 ⁶	x 1,000,000
μ	micro 10 ⁻⁶	one millionth part of
p	pico 10 ⁻¹²	one millionth part of

Table II.—The above prefixes are commonly used in connection with electrical and radio units and quantities.

Eventually he will be able to do all calculation (excepting that which is really unwieldy), mentally. It is useful to remember that 100mA is 0.1A. and that 50mA is 0.05A.

Basic Receiver Principles

There are two main methods employed in the detection and amplification of a radio signal. Both must be fully understood for R.A.E. purposes. A third system, detection of frequency-modulated signals, cannot be dealt with at this stage.

The first system, known as "tuned radio frequency" reception (usually abbreviated to T.R.F.) and even more commonly as "straight" reception, is one with which many older readers will be familiar. This method involves the detection and amplification of a radio signal on the same frequency as it is received.

The second system is a little more complicated. The incoming signal is first "mixed" or hetero-

dyned with another signal which is generated in the receiver by the "local oscillator." This locally generated signal is different in frequency to the incoming signal by only a few hundred kc/s (usually 465kc/s). The result of "mixing" the two signals produces, at the anode of the frequency-changer valve (sometimes known as the "mixer"), several different frequencies. One of these, 465kc/s. say, is passed on for further amplification before detection; or to use the correct term, demodulation.

It will be appreciated that as any succeeding stages of amplification following the frequency-changer have to deal with only one frequency, they can be designed to operate with maximum efficiency at that particular frequency. This has the effect of increasing selectivity far in excess of that obtainable with a "straight" receiver. There are other advantages with this second system of reception, which is known as the "superheterodyne" principle, usually abbreviated "superhet," but the object at the moment is simply to impress upon the beginner the basic essential differences between the two modes of reception.

It should be noted that the frequency chosen for amplification in the superhet is known as the I.F., or intermediate frequency; and that although 465kc/s has been quoted almost any frequency may be used. Many TV receivers use an I.F. of 10Mc/s; the "surplus" receiver R1155 uses an I.F. of 560kc/s.

Theory Required

For the Radio Amateur's Examination the candidate must be capable of discussing intelligently the merits and faults of both superhet and T.R.F. receivers; he may be required to draw a circuit of a 3-stage "straight" receiver, but it is unlikely he will be asked to draw a complete circuit of a superhet. He should be in a position, however, to draw a "block" diagram of a superhet, showing the various functional stages. Such a diagram is shown in Fig. 1. It is sufficient for the moment that the reader understands the points outlined, however; greater attention can be given to this subject in a future article when the beginner fully understands the operation of the tuned circuit.

As stated in a previous article it is almost essential that the newcomer to amateur radio spends a period as a short-wave listener before becoming licensed.

(To be continued)

Preventing I.F. Breakthrough

FEW EXTRA COMPONENTS ARE REQUIRED

By J. B. Dance, M.Sc.

IT is sometimes found that a certain unwanted signal interferes with many wanted programmes from a receiver and that this interference is not removed by alteration of the tuning, although a large tuning alteration may reduce its strength. The trouble—which may be present on more than one waveband—is caused by a signal of approximately the same frequency as the I.F. of the receiver finding its way into the I.F. chain. It will then be amplified and detected together with the wanted signal. As far as

signal near the I.F. is picked up by the aerial and passes with the wanted signal to the frequency changer grid. It is then amplified by the frequency changer and passed to the I.F. amplifier without its frequency being altered. Whilst passing from the aerial to the frequency changer, however, it has to pass through the R.F. tuned circuits which are resonant at a different frequency to the interference (namely the signal frequency); the interfering signal must therefore be fairly strong at the aerial or the attenuation of the R.F. tuned circuits would render it inaudible. For a certain setting of the receiver gain, this type of interference will probably be worst when the wanted signal frequency is fairly close to the I.F., as the attenuating effect of the signal frequency tuned circuits will then be less. The greater the R.F. selectivity, the better will be the rejection of I.F. interference picked up in the aerial. The trouble is most likely to occur when no R.F. stage is used, as the interfering signal will then normally have to force its way through only one tuned circuit resonant at the frequency of the wanted signal.

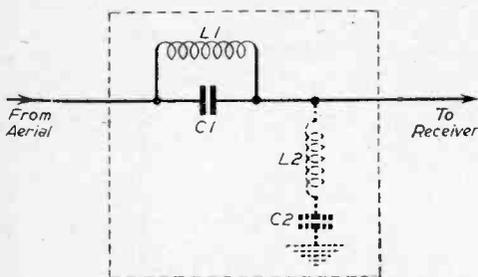


Fig. 1.—Using a filter circuit in the aerial lead.

possible, receiver designers avoid the trouble by choosing the receiver I.F. so that it is unlikely that a powerful signal will be picked up on the frequency. Frequencies within the medium wave band are therefore avoided for I.F.s. It is possible that interference may come from coastal navigational stations, especially if one lives near to them.

First I.F. Stage

Occasionally the interfering signal of the I.F. frequency is picked up between the anode of the frequency changer and the grid of the first I.F. amplifier. Any signal picked up after the first I.F. amplifier will not be amplified enough to cause appreciable interference. Interference which is picked up after the frequency changer will be present on all wavebands and, providing the receiver gain is constant (no A.G.C. used), it will not vary in strength as the tuning is altered. The interference will still be heard if the frequency changer grid is earthed. Suitable screening from the frequency changer anode to the first I.F. amplifier grid will provide a complete cure for this type of I.F. pick-up; screened leads (preferably coaxial) may be used for connections between the frequency changer and the first I.F. valve, but the first transformer must then be realigned.

Breakthrough from the Aerial

A more common form of I.F. breakthrough occurs when a fairly strong

When the interference is picked up by the aerial, it may be possible to get rid of it by improving the selectivity of the R.F. tuned circuits, i.e., by using coils of a higher "Q" or by using more tuned R.F. circuits (possibly with the addition of an R.F. amplifier). This is not always practicable, however, and other methods have to be found.

Aerial Filters

One of the best solutions is the use of a tuned circuit resonant at the receiver I.F. which is placed in the aerial lead as shown in Fig. 1. Normally either the parallel rejector circuit (L1C1) or the series acceptor circuit (L2C2, shown dotted) is adequate, but one of these circuits may give somewhat better results than the other and the

(Continued on page 759)

Table 1.—Number of turns required on a coil to make it resonate at certain commonly used I.F.s when used with the capacitance shown.

I.F. (kc/s)	C (pF)	Former Diameter (in.)	Winding length (in.)	NUMBER OF TURNS	
				Without dust core.	With dust core.
455-470	120	0.4	0.5	455	415
455-470	150	0.4	0.5	410	375
1600	100	0.4	0.4	128	116
560	120	0.4	0.5	375	340
(As in the 1155 receiver)					

The other components have their normal function as in an orthodox reflex set. The tuned circuit feeds the amplified signal to the detector. The residual R.F. is removed by C5 and the audio fraction passed via the blocking condenser C6 back to the base of the transistor. It is then amplified again, passes through the tuning coil, and is R-C coupled to the second transistor. This is a normal audio stage and may be followed by a similar third stage if more volume is required.

Layout

The components may be mounted in any convenient way. The author used a 3/8 in. thick baseboard with a plywood panel fixed to its edge at right-angles. On the panels were mounted C1, R5 and S together with the ferrite rod. All other parts were fixed on the baseboard which had two parallel brass strips attached by wood-screws to act as negative and positive bars. The bars were separated by 3 in. and this proved quite adequate for miniature components.

For each transistor, three tag-washers with the tags bent at right-angles, were arranged in a line, 1/2 in. apart, and fixed by round-headed wood-screws to the board. The pigtailed of the transistors were clamped firmly under these washers after all wiring-up was completed, thus avoiding all the risks of soldering these components.

Coil

The success of this rather unusual circuit depends on the development of a very sharply peaked resonance in L1. In order to ensure this, a pot-core assembly, Neosid D.10, obtainable from Denco, Ltd., is used. These pot-cores, which provide a completely closed magnetic circuit, permit a Q-factor of 200 or more to be achieved, and in addition make coil-winding a very simple matter indeed.

If the reader has not had any previous experience of pot cores, he should, on obtaining one, take it carefully to pieces to see how it is constructed. Proceed as follows:—

First undo the slotted plastic screw on the top of the pot, and lift off the upper ferrite cup. Take out the small polystyrene hobbin and notice that it has three annular slots to accommodate three separate coils. We shall only be using the middle one. Take the rest of the pot apart and notice that each cup has two semi-circular grooves, one each side. These must coincide when the pot is reassembled to provide two circular holes for the coil lead-in wires.

In the construction of this receiver two strips of brass are laid on the base to serve as positive and negative bars; that in the prototype is 3/8 in. x 1/16 in., a gauge readily obtainable from hardware shops.

The two rails, after cleaning with fine emery paper, are drilled at each end and screwed down parallel, and 3 in. to 4 in. apart. Round-headed brass wood-screws are used on a wooden base-board; on a plastic base (which saves weight and some space), 6B.A. round-headed brass bolts, 3/8 in. long, are ideal.

You should now obtain 19 tag-washers, size 6B.A., and bend up all the tags through almost a

right angle. These provide all the anchoring points needed. Four of them go under the heads of the screws at the ends of the two bars, the other fifteen being arranged in the pattern shown.

The various basic components can now be fitted on, using the component wires themselves to provide conductors. It is best to connect up without soldering until all the conductors are in position. Simply pass each wire through the appropriate tag-hole, bend round to secure, then snip off the surplus wire. Leave the transistors and diodes on one side until all the soldering (including the few connecting wires needed) has been completed. At the last moment you can loosen a little the nine screws concerned, and clamp the transistor and diode wires firmly under the washers. Provided the wires and washers are quite clean, the contacts so made are perfectly good, and the four semi-conductors can suffer no damage by overheating.

Wires

The few insulated connecting wires used should be kept as short as possible. The six fly-leads shown can be allowed a little more length and may be twisted into "flex" for convenience and neatness. If you do this, be careful with the battery fly-lead and use two different colours of wire so as to make no mistakes of polarity.

The ferrite rod (actually three thin 6 in. rods, bound together) was fixed high up behind the front panel. In this position L1 and L2 are far enough apart not to interact, their axes being at right-angles to each other, anyway. Note also the plastic extension to the shaft of the tuning condenser to remove hand-capacity effects.

(To be continued.)

SET ANALYSER

IN the article on the Set Analyser given in the June, 1959, issue, double-pole, changeover switches were specified, but several readers have informed us that they are experiencing difficulty in obtaining this type of switch. Double-pole, double-throw switches are, however, more readily available and a wiring diagram is given below so that a pair of such switches may be used in the Analyser.


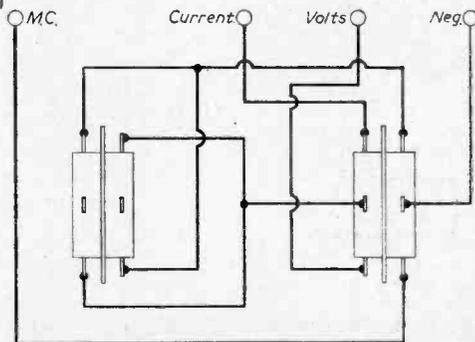


Fig. 1.—Wiring of DPDT switches.

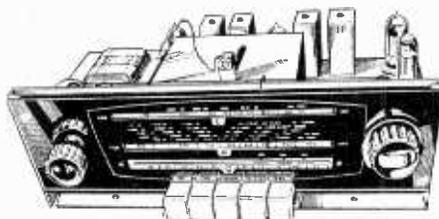BRAND NEW AM/FM (V.H.F.) RADIOGRAM CHASSIS AT £13.68. (P. & P. 10/-)



Why buy a F.M. Tuner at the same price?
Tapped input 220-225 v. and 226-250 v. A.C. ONLY.
Chassis size 15" x 6 1/2" x 5 1/2" high. New manufacture.
Dial 14 1/2" x 4" in gold and black.
Pick-up. Extension Speaker, Ae., E., and Dipole sockets. Five " piano " push buttons—OFF, L.W., M.W., F.M. and Gram. Aligned and tested.
With all valves & O.P. Transformer. Tone Control Fitted.
Covers 1,000-1,900 M.; 200-500 M.; 88-99 Mc/s.
Valves EZ80 rect., ECH81, EF89, EABC80, EL84, ECC85. Speaker & Cabinet to fit chassis, 47/6.
10" x 6" ELLIPTICAL SPEAKER, 20/-.

TERMS:—(Chassis) £4.16.8 down + 10/- carr. and 6 Monthly Payments of 30/-, or with Cabinet & Speaker £5.9.2 down and 7 Monthly Payments of 32/-.

"READY TO USE" I.T.A. CONVERTER

I.T.A. high gain converter. ALL CHANNELS—ALI, AREAS—ALL SETS. Direct switching (I.T.A. to B.B.C.); internal power pack; valves PC70 and FCC84; moulded cabinet 8 1/2" x 4" x 6". No alteration to your set; fitted in 10 mins. 12 months' guarantee.

£5.5.0 p. & p.
3.-



AUTOMATIC RECORD CHANGERS COLLARO CONQUEST with manual play also. Turnover crystal pick-up. 4-speed, A.C. mains 200-250 v., see illus.

£7.10.0 (5/- p. & p.)


B.S.R. 4-SPEED AUTO-CHANGER UAS only **£6.12.6** (5/- carr.)



COMPLETE RADIO FOR ONLY £10.10.0 carr. pd.

Size 19" x 13" x 7 1/2" or Chassis and dial for £8 (carr. pd.). Chassis Size 15" x 6 1/2" x 5 1/2"; 1,000-2,000 M.; 200-550 and 16-54 M. Mains (200-250 v. A.C.) and O.P. Trans. (3 ohm); Gram., Aer. E., Ext. L.S. Sockets; New Mullard Valves ECH42, EF41, EBC41, EL41, EZ40 and Magic Eye EM81. Dial 15" x 3". Fully aligned. Fantastic value for money.

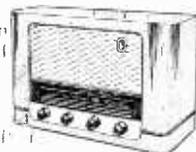6 1/2" or 6" x 4" speaker fitted to cabinet.



GRAMOPHONE AMPLIFIER with 5 in. SPEAKER. On Fabric-covered Baffle 12 1/2" x 5". Mains and Output Transformers. Metal Rectifier. ECL82 Valve. Tone and Volume Controls. Fully Guaranteed. Two Knobs supplied. Ready to play. Useful for Stereo.


ONLY 57/- post 2/.

BATTERY ELIMINATOR. Converts your Battery Set to Mains. For 4 Low Consumption Valves (DK range). 90 v. 15 ma. and 1.4 v. 125 ma.. 42/6 (2/6 post). 200-250 v. A.C. Size 5 1/2" x 3 1/2" x 2". Also for 250 ma. 1.4 v. and 90 v. 15 ma. at same price. Specify which.

TELEFECTION. "Twenty-20" adjustable set top or table for Bands 1, 2 and 3. "Gold" finished rods and mounting. List Price 42/- . Our price 30/- (carr. paid).

AERIALS F.M. Aerials single dipole room mtg., 17/6; ditto loft mtg., 20/-; "H" with chimney lashings, 65/- . Co-axial low loss cable 8d. yard or 20 yds. 12/6, all these items carriage paid.

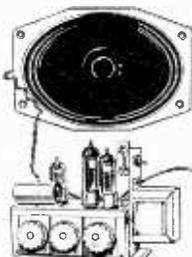50 SILVERED MICA AND CERAMIC CONDENSERS, 10-. 50 RESISTORS. 5/-. ALL DIFFERENT VALUES.



3-VALVE AMPLIFIER (INCL. RECT.). Capable of giving 6 watts. 8" x 5" Speaker wired-in. Mains and output transformers. Valves ECC81, EL84 and Rect. 3 Controls, volume, bass and treble. On/Off switch. Fully guaranteed. Chassis size 6 1/2" x 3" x 2 1/2". 67/- (3/- p. & p.).

BEREC "PIONEER" RADIO IN MAKER'S CARTON.


Valves DK96, DF96, DAF96, DL96. Berec Ever-Ready Battery B103, 18/6 extra. Two Short Wavebands 2.5 to 7 Mc/s and 6.5 to 17 Mc/s. Cabinet, 12" x 7 1/2" x 6". **ONLY £4.10.0** (2/6 p. & p.) (MW and SW £4.15.0 plus 2/6 p. & p.). In kit form with instructions and fully wired coil pack. Two Short Wavebands £4. One M.W. and S.W. £4.5.0. Plus 2/6 p. & p. Separate items supplied.

YOU CAN HAVE the sprayed case (grey and blue), back, chassis. (without components or coil pack), bracketry, dial cover for dial, and speaker baffle for only 15/- carr. pd. Illust. as above.

TAKE A CHANCE. We have surplus to present manufacturing requirements tens of thousands of resistors, silvered mica, tubulars, volume controls, electrolytics, valve holders, etc. **SEND US 20/-** for a bargain parcel of new goods. Our good name is your guarantee. Money back if not satisfied. State preference of types of goods.

SIX TRANSISTOR SUPERBET KIT £8.19.6

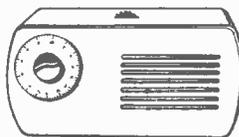Med. and L.W.; Printed Circuit; Instruction Book. Internal aerial. All items supplied separately. Write for price list. Battery, 9 v., PP4, 2/6.



Send 6d. (stamps will do) for our illustrated catalogue of the above items and others. All New Goods. Delivery by return. Terms—One-third down and balance plus 7/6 in four equal monthly payments. Postage with down payment. (C.O.D. 2/- extra.)

SEE SPECIAL TERMS FOR A.M./F.M. CHASSIS.

Large selection of complete Radiograms, ready built in cabinets, with 4-speed Autochanger. Write for details, giving approximate size required. Price from **£25** for A.M. only, or **£36** for A.M./F.M.

GLADSTONE RADIO—58A, HIGH STREET, CAMBERLEY, SURREY. Tel. 22791


Armstrong

AF208

VHF/MW RADIOGRAM CHASSIS

A new economically priced chassis
of traditional Armstrong quality
price 22 gns

Full VHF band (87-108 mc/s) and medium waveband.
● 5 watts output. ● Frequency Response 30-22,000
c.p.s. \pm 2 dB. ● Negative Feedback 15 dB. ● Harmonic
Distortion 0.5%. ● Hum Level 60 dB down.
● Separate wide range bass and treble controls. ● Output
for tape recording. ● Tape playback input for use with
separate recorder or tape deck with tape pre-amplifier. ● Two
compensated pick-up inputs (switched, to allow two
separate pick-ups to be connected). ● Continental
reception of good programme value. ● Absolute freedom
from drift on VHF. ● Satinised brass dial surround
and veneered fascia board available. ● Dimensions 12in.
 \times 8in. \times 7in. high.

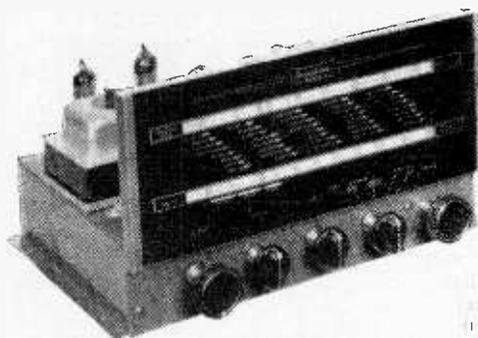

Other models in our range of radiogram chassis

STEREO-TWELVE	36 GNS
STEREO 44	27 GNS
JUBILEE	28 GNS

The name ARMSTRONG is the registered trade mark of
ARMSTRONG WIRELESS & TELEVISION CO. LTD.
WALTERS RD., LONDON N.7. TEL. NORTH 3231

Post this coupon or write for descriptive literature or call at our
Holloway Showroom for full unhurried demonstration and
professional advice on your installation. Open 9-6 Weekdays,
and 9-5 Sats.

NAME

ADDRESS

PJ8

ADCOLA

REGD. TRADE MARK
(Regd. Trade Mark)

SOLDERING EQUIPMENT

ILLUSTRATED

$\frac{3}{16}$ " Detachable
bit type (List
No. 64)

Protective Shield
(List No. 68)

Catalogues sent
FREE

Telephones:
MACaulay 4272
& 3101



British and
Foreign Pats.

Reg. Designs,
etc.

Head Office, Sales:

**ADCOLA
PRODUCTS
LTD.**

Gauden Road,
Clapham High
St., London,
S.W.4

GENUINE GUARANTEED BRITISH TRANSISTORS

FAMOUS MAKES... LOWEST PRICES EVER
"TRI." L.F./I.F./General purpose 800 k/c. 4/6.

RED SPOT.—L.F./I.F. General Purpose 900 k/c.s., 5/-.

WHITE SPOT.—R.F. Osc./I.F. 3-4 mcs., 6/3.

Green/Yellow.—Audio/Output 125 mW., 7/6.

TS3.—Special Offer, a few only, 12/6.

EDISWAN.—XA104, 18/-; XB102, 10/-; XB104, 10/-; XA103.

15/- EDISWAN.—Set of Seven Transistors, XA102, two XA101.

XB102, XB103, two XC101. ONLY 60/6 PER SET.

MULLARD.—OC16, 54/-; OC44, 26/-; OC45, 23/-; OC65, 22 8/8
OC66, 25/-; OCT0, 14/-; OCT1, 14/-; OCT2, 17/-; 2/OCT2 (Matched
Pair), 34/-.

ANY TYPE OF TRANSISTOR CAN BE SUPPLIED.

TRANSISTOR HOLDERS, 1/3. ARDENTE sub-miniature, 1 9/.

CRYSTAL DIODES, 1/-. GEX34, 4/-; Mullard OA81, 4/-.

FERRITE ROD.—3in. \times tin., 2/6; 6in. \times tin., 2/8; 3in. \times 5.16in.

1/6.

COILS.—Repanco DRR2, 4/-; DRX1, 2 6; Teletron HAX, 3-

All complete with circuits.

TUNING CONDENSERS.—Solid, dielectric, 500 pF (.0005 mfd.).

4/-; 300 pF, 3/8; 100 pF, 3/-; MINIATURE, 500 pF, 5/-.

TRANSISTOR CIRCUITS.—MINI 3, 1/3; Mini 7, 1/6; Major, 7

1/6; MAXI "Q", 6 11d; Teletron Transidyne, 11d (Full Kit,

£11/17/6); Three Dec, 11d (Full Kit, 67/6).

BEGINNERS 1 VALVE.—Circuit and plans, 11d. Kit, 37 6.

RESISTORS.—All values 10% \pm w. 6d., 1 watt, 9d.

CONDENSERS.—Miniature, .001 mfd., .002 mfd./100 v., 8d.;

.01/100 v., 10d.; 1 mfd./100 v., 12/-; .005/200 v., 10d.; Standard size,

.01/1,000 v., 8d.; 1,350 v., 9d.; 1,500 v., 10d.; 5,350 v., 11/0.

ELECTROLYTICS.—(Can type) 32-32/450 v., 8/6; 100-200/275 v.,

8/9; 60-250/275 v., 8/9; 64-120/350 v., 9/6; 60-100/275 v., 7/-; 24-24/

350 v., 4 6; 100-100/200/275 v., 13/-; 60-50-50/350 v., 9/10; Wire

ended, 16 mfd./450 v., 2/4; 16-16/450 v., 4/-; 8-8/450 v., 2/8; 8-16-450

v., 2/9; 50 mfd./50 v., 1/6; 25 mfd./25 v., 1/9; 100 mfd./6 v., 2 3/

Miniature, 25 mfd., 2 6; 50 mfd., 2 3/8; 8 mfd., 2 9. SUB MINI-

TURE; 25 mfd., 8 mfd., 16 mfd., 4 mfd., 2 mfd., 3 6; 100 mfd., 2 9;

1 mfd., TCC, 4/-.

TERMS: Cash with Order

(or C.O.D. on orders over £2).

ALL OUR PRICES ARE

POST PAID.

OAKFIELD RADIO

THE TRANSISTOR PEOPLE

Mail Order Only

44 Oakfield Road,

Stockport, Cheshire.

YOU CAN SAVE 1/- in every
£1. Send 1/6 for our 56-page
Catalogue and receive your
order number for the Amazing
Credit Coupon Scheme. Free
Lists, Bargain Offers, Latest
News, etc., etc. ORDER NOW.
Don't Delay.

Beginners' Test-Meter

No. 6.—ADDING THE RESISTANCE RANGE TO THE MULTI-METER


By E. V. King

IN the previous two articles the wiring for the current ranges was added to the meter and the shunts were constructed. The wiring of the multi-meter should now be as shown in Figs. 14 and 17 (which were given on pages 572 and 573 of the November 1959 issue). Before proceeding further you should make sure that your meter operates perfectly on all the ranges so far completed. The method of testing the various ranges was given in the previous article (in the December issue).

Resistance Range

The resistance range to be added to the meter can be used to read resistance values from about 200ohms to 0.5megohms, the accuracy being greatest around readings of 3,000 to 5,000ohms. Although the meter will not be as accurate as a resistance bridge, it will suffice for most tests needed in servicing that will be encountered by the beginner or even by those with more experience. In most radio receivers and in most electronic equipment, resistor values are not particularly critical and a really accurate resistance meter is, therefore, unnecessary.

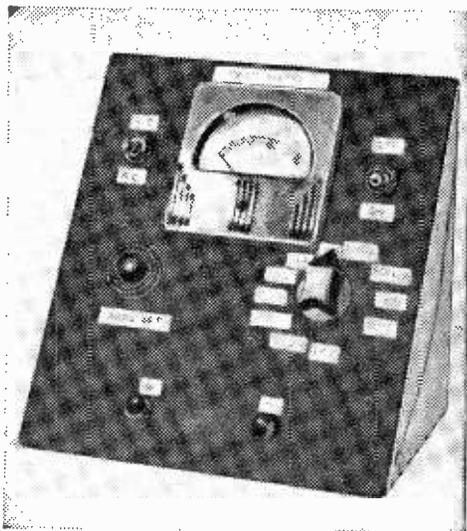The additional parts required for the resistance range are VRI, a battery, and R10. Resistor R10 has a value of 3.3k (3,300ohms) and is in series



The completed meter.

with VRI which has a value of 1k. This latter variable resistor is inserted to compensate for the changes in battery voltage which occur at the end of its life. The 3.3k resistor limits the current through the meter and when you choose this resistor make sure that you read the colour code correctly as the insertion of an incorrect value could cause the meter to be burnt out.

Variable resistor VRI is mounted in the only spare hole in the panel (which has been shown in many diagrams). It is fitted with a small knob which need not be of the pointer type.

Wiring

Refer to Fig. 26 and compare it with Figs. 27 and 28 (a). At first sight, these diagrams may appear rather confusing to the beginner but all will become clear later. Meanwhile note that no wires already in position have to be altered. Three wires are needed in addition to R10, VRI and the battery (4½V, "flat").

Solder two 6in. leads on to the battery tags and take the positive lead (the one from the shorter tag) to one of the outside tags of VRI. Take the other lead to the "bus-bar" which joins all the voltage resistors together. R4 and R5 being shown in Fig. 26. Join the centre

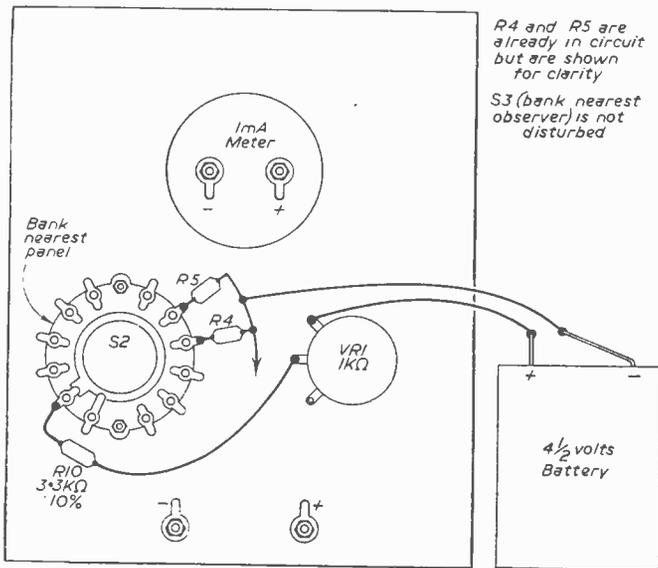


Fig. 26.—Extra wiring for the resistance range.

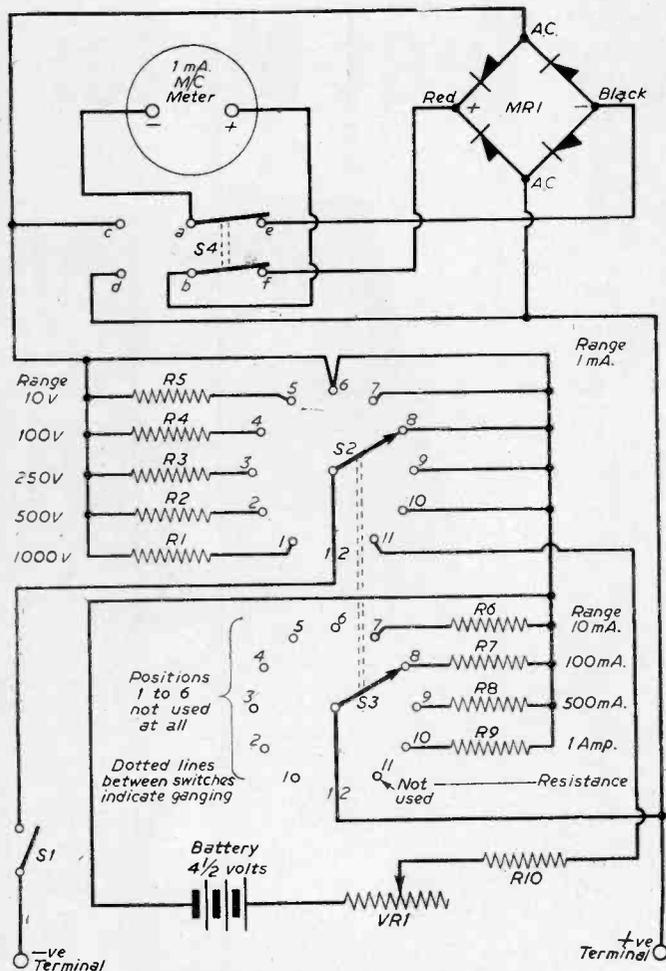


Fig. 27.—The final circuit diagram of the multimeter.

tag of the potentiometer to tag 11 on S2 via the 3.3k resistor. Mount this on a short lead on the switch tag. Note that S2 is being used and is the wafer nearer to the panel. Now verify that all the tags of S2 are in use and that the first six of S3 are not used.

Testing the Resistance Range

As always when testing, do not put S1 on until you are ready. Clip the test leads to a resistor of between 5k and 20k and make sure that good contact is made. Switch on S1 with the range switch pointing to resistance (see Fig. 12). The meter should move but should not go over beyond 0.7 on the scale. If it does then R10 is probably faulty. If the movement is not too great, then all is well. Take the resistor off and clip the test leads together. The pointer will now move right across the scale to show 'zero' resistance. Now carefully set the zero setting control VR1 so that the needle shows 1mA exactly. The zero control is then left in this position and normally will not

need further adjustment for a long time. Eventually the zeroing control will be unable to compensate for the low battery voltage and a new battery will have to be fitted.

Explanation of the Circuit

In Fig. 28(a) is shown the resistance range of the meter in simple form. Electrons leave the negative pole of the battery being repelled by the 4½V of the battery through the meter, the resistance being tested, the variable resistance, and the 3.3k resistor until eventually they arrive at the positive pole of the battery. When the resistance under test is a straight wire of no resistance the current through the circuit is exactly 1mA. Readers can refer to any text book on electricity to gain a knowledge of Ohm's Law.

If we now insert a resistance of about 4,500ohms in circuit in place of the wire the battery voltage will not force 1mA through, but only ½mA. This is the calibration point for 4.5k. Thus the higher the resistor placed in the circuit the less the current and the less the deflection of the needle. Values below about 500ohms give such a large current (almost 1mA) that it is difficult to read accurately. The same applies to values of over 0.5M. However, a 1M resistor will just show a needle movement if it is all right.

Now refer to Fig. 27. The switch S4 has not yet been added to the circuit, but in the D.C. position the tag c is joined (via S4) to meter minus and tag d to meter plus. Thus for the moment we may consider c and d as meter terminals.

Starting with battery minus follow the circuit through as follows (remember, the switch is on No 11 range):—

1. Battery minus to "c", i.e., meter.
2. Through meter to the plus terminal of the meter, i.e., "d."
3. From "d" to the plus terminal of the multimeter and through the test lead.
4. From the test lead through the resistance to be tested to the other lead and the negative

PARTS REQUIRED

- R10, 3.3 k., ¼W. resistor, 10 per cent. tolerance (silver line).
- Two-pole two-way, toggle switch.
- Meter rectifier, 1 mA. (or use diodes as suggested in text).
- 4½V. flat torch battery.
- Tin plate (from cocoa tin, etc.), screws, etc

terminal of the multi-meter.

5. Then through S1 (if it is on).

6. From S1 to the slider of S2 which is connecting with tag 11.

7. Tag 11 leads the current through the 3.3k resistor and the variable resistance VR1 and so back to the other side of the battery.

The beginner should follow the above circuit through on the diagrams and on his meter so that he is quite sure how it all works.

Calibration

The author has already mentioned that the beginner is to be cautioned against taking the meter to pieces as he is very likely to damage it in some way. However, it is quite possible to do so, especially if the operator is able to control his fingers within fine limits as in watch repairing. In that case, a new scale may be added with black or white Indian ink so that a kilohms scale can be directly read off. This could be done using good resistors, but can be done fairly accurately by using the chart given below. These figures are affected by your value for the 3.3k, your battery voltage and the meter resistance. The figures are within 10 per cent. accurate.

Another method which the author favours for beginners is to obtain at the stationers some graph paper, standard 1/2 in. squares will do, but you could use a sheet from a "radio diary."

A suitable layout for the graphs is shown in Fig. 29. The milliamps shown by the needle are down the left-hand side and along the bottom are the kilohms which will cause such a deflection. The graphs may be plotted using the points given

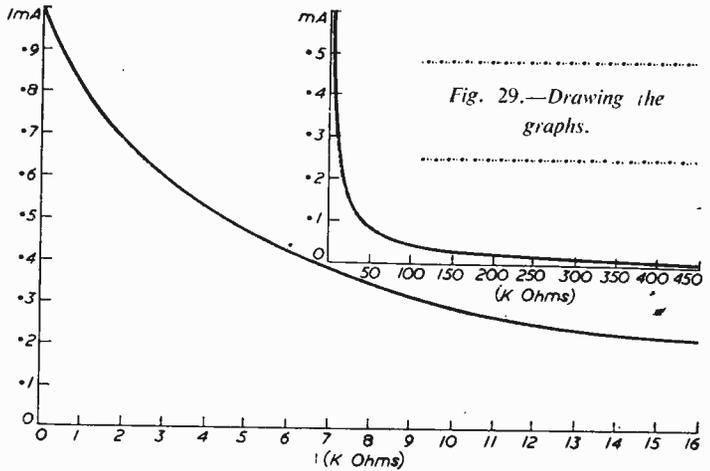


Fig. 29.—Drawing the graphs.

in the chart or may be copied from Fig. 29. An example of how to find a plotting point is taken; a 1k resistor causes a deflection of 0.8mA. A dot is made at the intersection of the 1k line upwards with the 0.8mA line horizontally. When all the dots are marked in, the smooth line may be carefully drawn in.

In Fig. 29 you will notice a smaller graph in the top right-hand corner, this could, of course, be on another piece of paper. The kilohms scale is different, so that you can read off high resistor values with more accuracy. Suitable scales are given here:—

Low Kilohms

Milliamps: 0.1 milliamp to each 1/2 in., starting at 0.3milliamps along the bottom from the right angle to the front panel finishing, of course, with 1milliamp.

Kilohms: 1k to each 1/2 in., starting at zero at the right angle, upwards along the back to 10k. This will be about 1in. from the top of the side.

High Kilohms

Milliamps: 0.1 milliamps to each 1/2 in., starting at zero along the bottom from the right angle to the front panel finish with 0.6mA.

Kilohms: 50k to each 1/2 in., starting at zero at the right angle and working upwards along the back to 500k (0.5M), which will be about 1/2 in. from the top of the side.

Chart for Resistance Calibration (or the Graph)

Meter reading	Resistance (approx.)
Zero	Very high or infinite resistance
0.1	40,000ohms.
0.2	18,000ohms.
0.3	10,500ohms.
0.4	6,750ohms.
0.5	4,500ohms.
0.6	3,000ohms.
0.7	2,000ohms.
0.8	1,000ohms.
0.9	500ohms
1.0	Very low or no resistance

(To be continued)


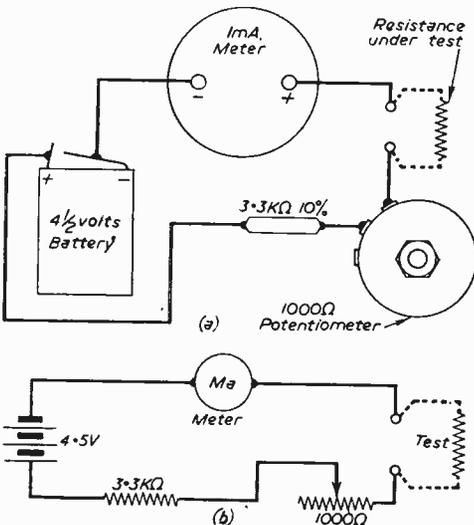


Fig. 28.—The circuit of the resistance range.

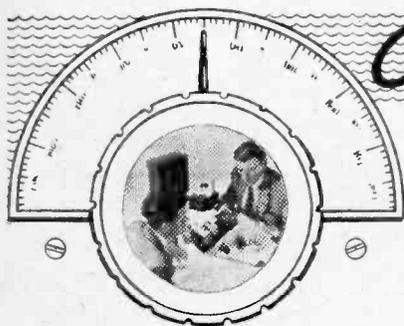

On Your Wavelength

BY THERMION

CONSEQUENT upon my assessment of the present state of Amateur Radio in my article last month, I have received a number of letters; all of them have proved most interesting reading. The majority express agreement with my views, especially those from older readers who remember the thrills of the early days of our hobby. Younger readers tend to be in disagreement with me.

Mr. Graham S. H. Stubbs, of Hitchin, does not hold my views and his letter contains some interesting guesses concerning my character and knowledge which would amuse my friends. Mr. Stubbs said:

"Thermion's latest assessment of amateur radio is the greatest example of his own ignorance he has yet offered.

"He states in the December, 1959, issue; 'Nowadays everything is over; there is nothing left to discover.' Nothing could be further from the truth; there is so much work yet to be done by the radio amateur that the real problem is to know where to begin.

"Much work in the field of radio communication can only be carried out by the radio amateur who has the experience, patience and enthusiasm to develop ideas which might be rejected by the professional engineer as economically unworthy of development. The professional left it to the radio amateur to open up the higher frequency bands before the war, and on these same bands the modern radio amateur can make new developments and discoveries; as yet very little work has been done on the higher frequencies using transistors entirely in place of thermionic valves. This is but one example of a field in which the radio amateur has a big part to play."

Mr. Stubbs says, "Much work in the field of radio communication can only be carried out by the radio amateur who has the experience, patience and enthusiasm to develop ideas which might be rejected by the professional engineer as economically unworthy of development." While the first part of this statement may have been true in the very early days of radio communication, it certainly no longer applies. Mr. Stubbs seems to revere the word "amateur" and seems to think only those who can be called amateurs are capable of possessing any of the three qualities—experience, patience and enthusiasm—which he lists. These are qualities of the professional as well as the amateur, although they are often more marked in the

amateur, but only because he does not make his living by the application of electronics. In these days, any professional is bound to have more experience than the amateur—by "professional" I mean someone who spends his time on research into radio subjects, not a radio serviceman. As for patience, this is a quality possessed by everyone to some degree, from farmers to pharmacists and is certainly not unique to the radio fraternity. Enthusiasm, too, is a quality which depends upon whether one is interested in one's work, and not on what work one does.

Facilities

It is obvious that the professional has the advantage of better facilities. Few amateurs have access to a laboratory, to precision instruments, or to sufficient money for their optimistically-named "research schemes." Nowadays, it is a mistaken belief that the amateur has much to offer to the development of radio: this sentiment is purely wishful thinking. It appeals to the whimsically minded to convince themselves and say that with all the much-vaunted facilities of the professional research worker, it takes an amateur, struggling in some cold, dark, dingy shed at the bottom of his garden, to solve a problem which has been baffling the professional for months. Nothing could be further from the truth and any clear-thinking person will agree with me.

As I said previously, it may have been true that, in the past, many far-reaching discoveries were made by amateurs, but I maintain that this state of affairs no longer exists. It is true that there is much to occupy the amateur, but this is mainly in the nature of testing or confirming the results obtained by the professional and not in branching out into some hitherto uncharted field of development. The amateur has neither the time, money, experience and, very often, ability for detailed scientific research work. Even the results he does manage to obtain are qualitative rather than quantitative.


No, the days of the amateur radio as an instrument of research are wellnigh over; it is only the monetarily and mentally gifted amateur who stands a chance. The advantages of the professional are overwhelming and it is best to consider amateur radio purely as an interesting, absorbing, and exceedingly instructive hobby.

**Don't forget the
P.W. AND P.T. FILM SHOW
Caxton Hall, Westminster, London**
January 22nd, at 7.30 p.m.

Applications for tickets should be made now. Please mark your envelopes "Caxton Hall" in the top left-hand corner and enclose a stamped, addressed envelope.

Three-waveband Superhet

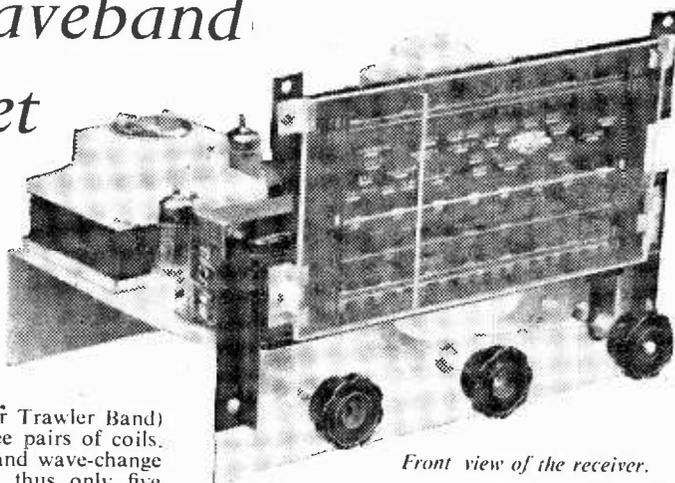EASILY CONSTRUCTED
AND ALIGNED
By R. MORGAN



Front view of the receiver.

THE construction and wiring of a receiver of this type is much simplified by using a ready-made coilpack. The one fitted allows long, medium and short waves (or Trawler Band) to be tuned and contains the three pairs of coils, six associated trimmers, padders and wave-change switch, ready wired. There are thus only five connections from the pack, in addition to the mounting bush, and this should be particularly appreciated by the constructor who feels that the wiring of individual coils, trimmers, padders and switch may be too difficult.

Size

As miniature construction also tends to introduce difficulties, the receiver is of fairly large size and this makes wiring and soldering less awkward. It also allows a large attractive tuning dial, with vertical pointer, to be fitted, which gives clear indications of wavelengths and stations for the long and medium wavebands and shows wavelengths and short wavebands on the S.W. portion of the scale.

The receiver circuit is shown in Fig. 1, the numbered points connecting up to the tags on the coilpack. A receiver of this kind can give very good results, with ample volume from a large

number of M.W. stations and a lively performance on S.W. Automatic volume control is provided in the usual way, to counteract fading. The two 200pF condensers and 10k resistor (or R.F. choke) form a modulation hum filter, designed to cut out the tunable hum which may in some circumstances otherwise be troublesome.

Readings

It should be noted that if accurate dial readings are to be expected on all bands, it is necessary to use the specified coilpack, tuning condenser and dial. These are intended to work together. Miniature I.F. transformers can be fitted, if desired, provided they are for 465kc/s and are efficient. Some transformers have coloured leads, while others have projecting tags and it is important that the transformers are wired correctly.

This is shown in Fig. 2, which also indicates


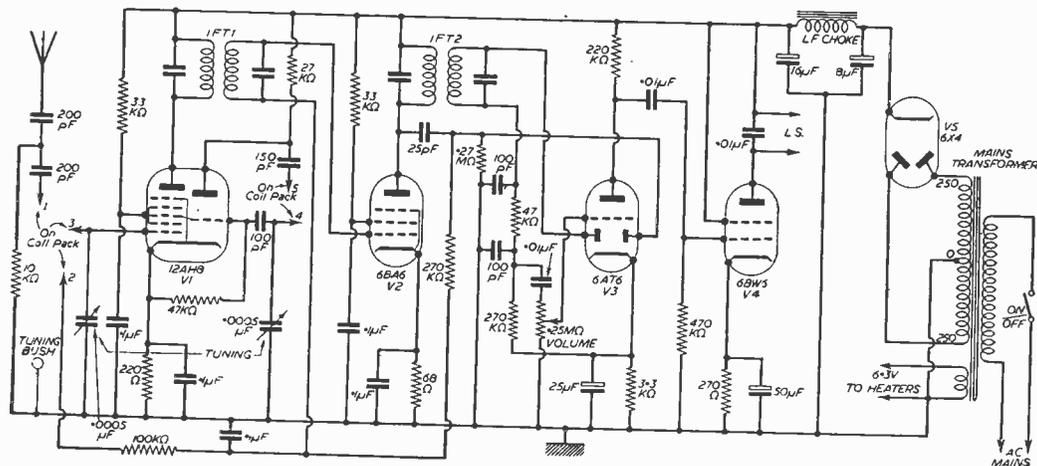


Fig. 1.—The circuit diagram.

where the valves should be inserted, when the receiver is completed. Construction is much simplified by using a ready-drilled chassis, as there is then no need to cut valvholder holes, or an aperture for the mains transformer.

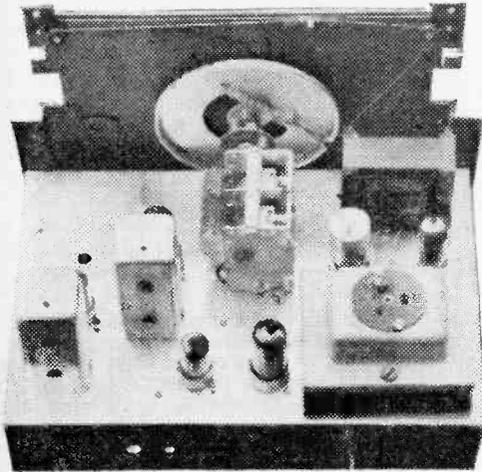The dial and 2-gang condenser should be located so that the spindles come in line, so that the flexible coupler fits easily and no excessive friction is caused. This is most easily assured by lining up the spindles with the coupler removed.



Rear view of the receiver.

When the gang condenser has been bolted in place, the dial can be removed until front wiring is completed. The bolts holding the front fixing feet of the condenser should be inserted from below. If inserted from above, they may foul the coilpack.

Valvholders

When bolting down the valvholders, position them so that the sockets come approximately as shown in Fig. 3. Note that the 6BW6 and 12AH8 valves use 9-pin holders and that the latter has two heater tags joined, as this is necessary when running the 12AH8 from a 6.3V heater circuit.

The layout of components below the chassis will be seen from Fig. 3. There is no need to position resistors and condensers exactly as shown, provided all connections are reasonably short and direct. In the actual receiver, some parts will tend to overlap others, but they should not touch each other, or other leads, or the chassis.

Wiring

All connections in the receiver are shown in Fig. 3. Two leads pass from the positive tags of the 8 plus 16 μ F condenser to the smoothing choke. Lead "X" goes from tag 4 of the pack, to the rear

set of fixed plates on the gang condenser. Lead "Y" passes from tag 3 to the front set of fixed plates.

Four small tag strips are used to anchor various points. Strip "A" has one tag joined to the chassis and holds the modulation hum filter components. About 6ft. of thin flex is soldered to the free tag, as shown, to provide an aerial. A longer indoor or outdoor aerial may be joined to this, if desired.

Tag strip "B" has two free tags and one joined to the chassis and provides connecting points for the two 100pF condensers, 47k resistor, and other leads.

Strip "C" has three free tags, two of which are joined to allow various resistors and other leads in the H.T. positive circuit to be wired up easily. The 33k resistor is also joined on here, the left-hand tag forming the screen grid connecting point for the I.F. stage.

Strip "D" has two free tags, these forming junction points for the A.V.C. line and 0.01 μ F condenser. Here, as elsewhere in Fig. 3, all points marked "E" should be joined to the chassis. This is best done by soldering the leads to 6 B.A. tags held with short 6 B.A. bolts.

With the first I.F. transformer, "A" indicates the anode lead or tag and "H.T." the high tension positive connection. The primary of the second I.F. transformer is wired in the same way, "A" to anode and "H.T." to H.T. line. With the first transformer, the secondary connection "G" goes to the I.F. valve grid, while the lead marked "A.V.C." is taken to the A.V.C. line. With the second transformer, "D" goes to diode and "D.L." to diode load components. All these connections are shown in Fig. 3. The colour coding or numbering given by the transformer maker should be followed, so that these components are correctly wired in.

Condensers

With the 8 plus 16 μ F condenser, the negative connection is made by the mounting bracket

(Continued on page 755)

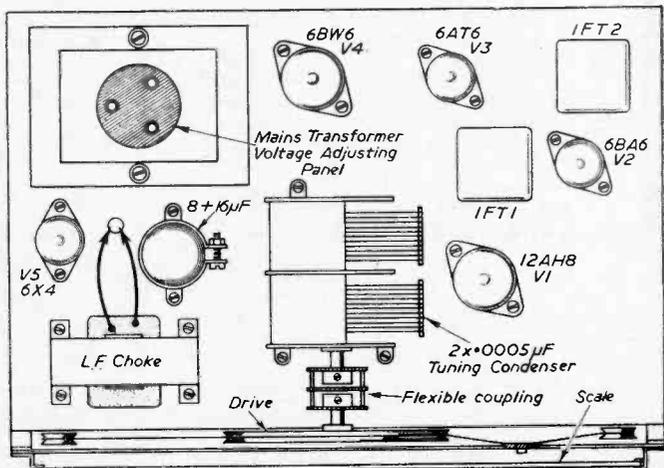


Fig. 2.—Chassis layout.

The decision is YOURS. To be a success in your chosen career; to qualify for the highest paid job . . . to control a profitable business of your own. ICS home-study courses put your plans on a practical basis; teach you theory and practice; give you the knowledge and experience to take you, at your own pace, to the top.

Technical Training in Radio, Television and Electronics Engineering with

Choose the *RIGHT* course :

- RADIO & TELEVISION ENGINEERING
- INDUSTRIAL TELEVISION
- RADIO & TELEVISION SERVICING
- RADIO SERVICE AND SALES
- VHF/FM ENGINEERING : ELECTRONICS
- COMPUTERS & PROGRAMMING


ICS provides thorough coaching for professional examinations:

- Brit. I.R.E., City and Guilds Telecommunication C. & G. Tech.,
- Radio Servicing (R.T.E.B.); C. & G.
- Radio Amateurs C. & G.

LEARN AS YOU BUILD

Practical Radio Courses

Gain a sound up-to-professional-standards knowledge of Radio and Television as you build **YOUR OWN** 4-valve T.R.F. and 5-valve superhet radio receiver, Signal Generator and High-quality Multi-tester. At the end of the course you have three pieces of permanent and practical equipment and a fund of personal knowledge and skill. ICS Practical Radio courses open a new world to the keen Radio amateur.

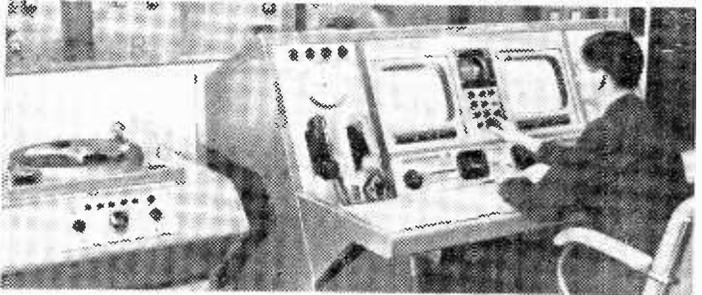

THERE ARE ICS COURSES TO MEET YOUR NEEDS AT EVERY STAGE OF YOUR CAREER. FILL IN AND POST THIS COUPON TODAY.

You will receive the FREE 60 page ICS Prospectus listing examinations and ICS technical courses in radio, television and electronics PLUS details of over 150 specialised subjects.

- Other ICS courses include :
- MECHANICAL, MOTOR, FIRE, CHEMICAL & ELECTRICAL ENGINEERING.
- FARMING, GARDENING, ARCHITECTURE & WOODWORKING.
- SELLING & MANAGEMENT.
- ART, PHOTOGRAPHY, etc., etc.

A WHOLE WORLD OF SKILL AND KNOWLEDGE FOR THE KEEN STUDENT.



INTERNATIONAL CORRESPONDENCE SCHOOLS
 (DEPT. 170 L), INTERTEXT HOUSE, PARKGATE RD., LONDON, SW11

PLEASE SEND FREE BOOK ON

NAME

ADDRESS

.....


OCCUPATION AGE.....

1.60

TSL—LORENZ SUB-MINIATURE SPEAKERS FOR TRANSISTOR SETS


The application of transistors to small radio receiver design brings with it the need for miniature loudspeakers of good performance with "transistor characteristics" in order to take full advantage of transistor outputs. The two presented here will be found to conform ideally with the requirements involved.

MODEL LP. 70

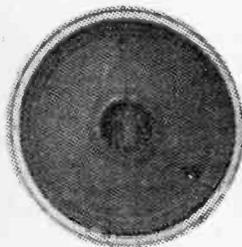

2 3/4 in. diam. x 1 1/4 in. deep. Will convert as little as 4 milliwatts loading into a loud, clearly audible signal. Special cone suspension ensures wide range response from 120 to 14,000 c.p.s. Impedance 10 ohms. Very small receivers with 1/2 watt class B output become a practical proposition with this unit. **25/-**
Inc. P/tax

MODEL LP. 31

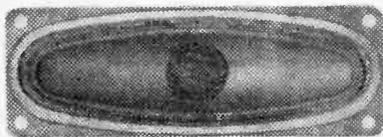

High quality elliptical speaker 4 in. x 1 1/4 in. x 1 in. overall. Response 120-14,000 c.p.s. Impedance 3 ohms. Loading 4 to 500 milliwatts. Enables a battery radiogram to be built only 2 in. in depth. The cone is specially suspended within a chassis of specially robust construction, and as such the LP.31 may also be used to advantage in larger instruments. Price, inc. P/tax **24/-**

From your usual equipment stockist. Leaflet together with latest catalogue of constructors' handbooks free on request.

TECHNICAL SUPPLIERS LTD

Hudson House 63 Goldhawk Rd. London W12

Telephone: SHEpherds Bush 2581 and 4794



Solve
that
Circuit
trouble!

PIFCO
Radiometer


Not only circuit tests but everything electrical can be tested with this handy compact meter. Tests H.T. & L.T., Valves, components, electrical appliances and car lighting systems, etc. May be used on A.C. & D.C. mains.

See the Radiometer at your dealer or write for illustrated leaflet to :-

only
32/6
complete

PIFCO LTD.
WATLING STREET · MANCHESTER · 4.

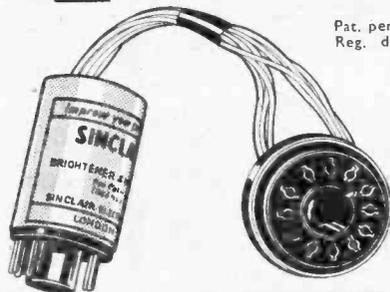IS YOUR T.V. TUBE DIMMING? YOU CAN EXTEND THE LIFE OF THAT TUBE AND IMPROVE THE PICTURE



Pat. pending.
Reg. design.

PRICE **30/-**

Package & Postage 2/6.
(Postal Orders,
C.W.O. C.O.D.)

- NO SOLDERING
- NO WIRING
- JUST PLUG IN
- IT'S AUTOMATIC
- IT'S GUARANTEED!

One of the most common T.V. Tube faults is low emission, resulting in loss of brightness, contrast, definition and focus. The Sinclair Unit restores the cathode emission and corrects the above faults for a very low cost. Applicable to all sets operating off A.C. mains.
IMPORTANT. State make and model No. of set and tube in block capitals, please. If not satisfied money refunded if returned within 7 days.

SINCLAIR ELECTRONICS,

Dept. P.W., 33, BERWICK ST., W.1.

CALLERS WELCOME—TRADE ENQUIRIES INVITED.

bolted to the chassis. Card condensers, or condensers with isolated cans, will have a negative tag or lead, which must be wired to the chassis.

The tags marked "H" are wired together and the 6.3V secondary of the mains transformer. If wiring is systematically checked against Fig. 3, the receiver should be expected to work properly as soon as completed. A suitable length of good twin flex should be used for the mains leads.

When wiring in the coil pack, follow Fig. 3, and note that the tags are not numbered consecutively from right to left, as the actual numbering agrees with Fig. 1.

Operational Details

Best results cannot be expected until the circuits have been aligned, but this is not difficult. When the coilpack and transformers are fitted, alignment will not be exact, but it should not be so in error that no signals can be heard at all. It is thus best not to begin adjusting the trimmers or cores until reasonable reception shows that the set is correctly wired and otherwise in order.

It is essential that a matching transformer be used between the receiver and speaker. The optimum load for the output valve is $5k\Omega$. With a 2 to 3 ohm speaker, a transformer with a ratio of approximately 45 : 1 will thus be necessary. For a 15 ohm speaker, the transformer should be approximately 18 : 1.

I.F. Alignment

The I.F. transformers should be aligned first. If a signal generator is available, adjust this to

nected from A.V.C. line to chassis. Alignment will then be for maximum A.V.C. voltage, as shown by the meter. Positive is taken to chassis and the 10V or 25V range will suffice. A further method is temporarily to disconnect the H.T. lead to the second I.F. transformer and to insert

COMPONENTS LIST			
Fixed Condensers		Resistors : ($\frac{1}{2}$ watt)	
1—25pF	3—.01 μ F	1—68 ohm	2—47k
3—100pF	5—.1 μ F	1—220 ohm	1—100k
1—150 pF	1—8-16 μ F	1—3k	2—220k
	350 v.		
2—200pF	1—25 μ F 25V.	1—10k	3—270k
	1—50 μ F 25V.	1—27k	
	or 50 v.	2—33k	1—470k
		1—270 ohm	—(1 W.)
		1—250k potentiometer	with switch.
3-Band Superhet Coilpack (Osmor).			
2-gang 500pF, tuning condenser with drive.			
Dial assembly.			
60 mA smoothing choke.			
250-0-250V., 60 mA, 6, 3V, 3A mains transformer.			
3 x B7G valveholders, 2 x 9-pin B9A valveholders.			
Valves : 12AH8 ; 6BA6 ; 6AT6 ; 6BW6 and 6X4.			
Chassis approx. 11 $\frac{1}{2}$ in. x 7 $\frac{1}{2}$ in. x 2 $\frac{1}{2}$ in.			
2 x 465 kc/s I.F.T.'s.			
5in. to 8 in. P.M. speaker with transformer as specified.			

a 10mA or similar meter here, with a 0.1μ F bypass condenser in parallel. Alignment is then for minimum reading on this meter.

The use of some form of meter more easily gives an exact indication, but satisfactory alignment is readily achieved by ear alone.

If no signal generator is available, tune in the local station and adjust the I.F. transformer cores for best reception. No core should be at the limit of its travel in either direction. If it is, re-adjust the three other cores, retune with the control knob, and again peak all cores for best results. A more exact, final adjustment will be possible with a weak station, but the transmission chosen should not be subjected to fading.


Once the I.F. transformers have been adjusted for better results they should not be touched again.

Coil Alignment

When aligning the coilpack, it is best to do the M.W. band first. It should be remembered that there are two cores and two trimmers for each waveband. When one band has been dealt with, leave the cores and trimmers for this band untouched when aligning the other bands. Never adjust cores and trimmers together.

The drive coupler should be securely locked, so that the pointer travels from minimum reading with the condenser fully open. Fig. 3 shows the positions of the various trimmers and cores:

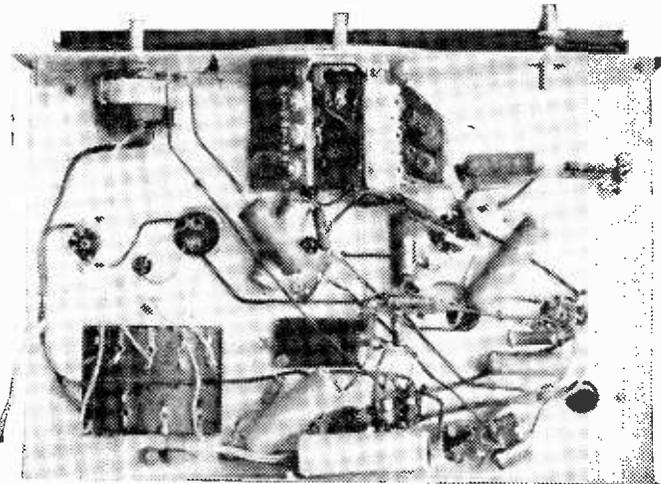To deal with the M.W. band, tune in a station fairly low on the scale (say, below 250m) and adjust the M.W. trimmers for best volume, or



The wiring of the receiver.

give a 465kc/s output and inject this via a very small capacitor at tag 3 of the pack. (In most cases clipping the lead on to the insulation of lead Y will suffice.) The I.F. cores are then adjusted for maximum response. This can be done by ear, or by using an output meter. With these methods, temporarily shorting the A.V.C. line to the chassis will give a sharper indication. If a $10k\Omega/V$ meter is to hand, this may be con-

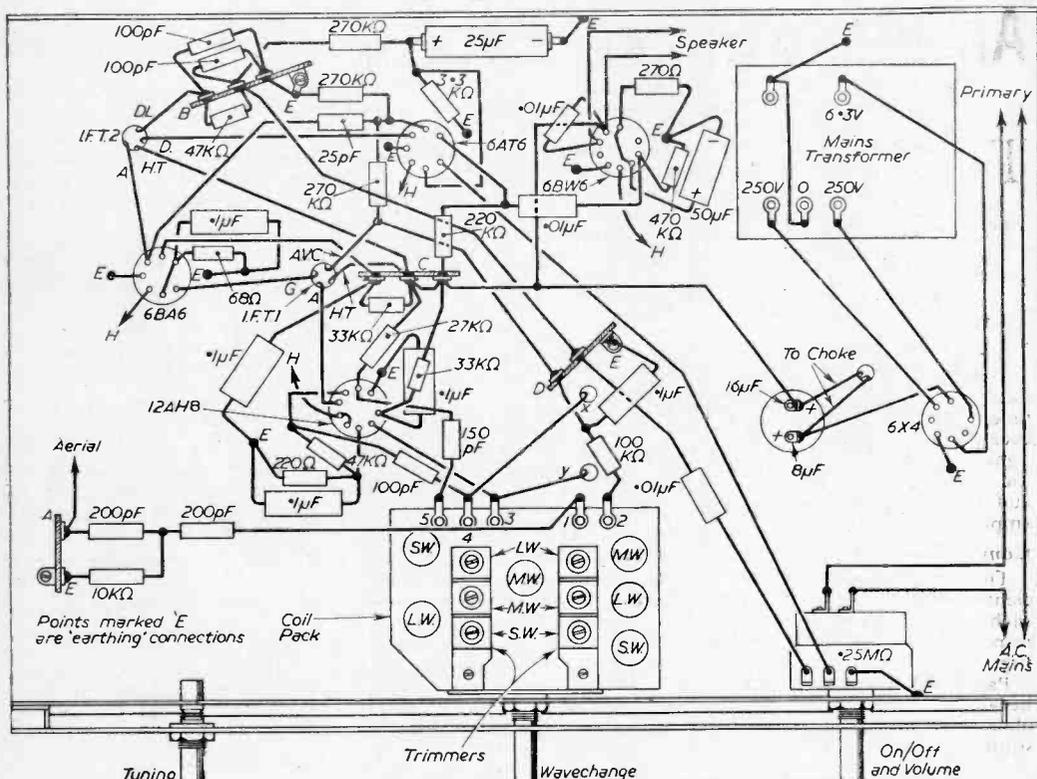


Fig. 3.—Underchassis wiring diagram.

maximum response as shown by the meter. Then tune to a station of fairly high wavelength (say, around 500m) and adjust the M.W. cores for best results. Return to a low wavelength station and make careful trimming adjustments again. Then retune to a high wavelength station and make any further, final adjustment which may be needed to the cores, for best volume.

The wavechange switch control knob is then turned to L.W. and the procedure repeated, the L.W. trimmers and cores being adjusted.

Finally, the S.W. band is similarly dealt with. Here, it will be found that adjustments are quite critical. After initial alignment has provided good volume throughout the S.W. band, final adjustments can be made with stations of known wavelength, or by means of the 20m and 40m amateur bands.

In all cases a metal screwdriver may be used for the first, rough adjustments only. For final adjustments, a tool with an insulated blade is essential and this can be fashioned from a length

of ebonite rod, or any similar strong, insulated material. A screwdriver with an insulated handle only is not satisfactory, because the presence of the metal blade in the coils will change their inductance and thus upset alignment.

The scales can be illuminated by fitting a 6.3V dial lamp at each end of the plate. The mains transformer should be adjusted to the correct mains voltage, before using the set. If the exact figure is not provided, select the next highest figure on the transformer (e.g., the 230V) for 220V mains, and so on.

With the circuit as shown, hum is at a low level. If it is desired to reduce this further, especially for a large speaker with good bass response, then a 47k resistor may be added between the 6AT6 220k anode load resistor and H.T. line. A 8μF or similar condenser is wired from the junction of 47k and 220k resistors to chassis, the latter being negative. It is also possible to screen the leads from the 0.25m potentiometer and 0.01μF coupling condenser.

The Entirely New 13th Edition of The Famous Standard Work

THE PRACTICAL WIRELESS ENCYCLOPEDIA

By F. J. CANN

Considerably enlarged, amplified and entirely re-written and re-illustrated. Complete Television Section, with theoretical and constructional data.

All the facts, figures, and constructional data of Radio and Television—Definition. Terms—Units—Principles, Circuits, etc. Over 300,000 copies sold. Price 21/- or 22/6 by post from:

GEORGE NEWNES, LTD., Tower House, Southampton Street, Strand, W.C.2.

The components do not have to be arranged exactly as shown, but it is desirable that L1 and L2 are kept reasonably apart, otherwise instability will occur. The output valve V3 and its transformer should be situated as far as possible from V1 and its associated components, for the same reasons. (See Fig. 4.)

Chassis measuring 12in. X 6in. with three holes, for I.O. valve holders, are usually stocked by most radio dealers. It does not matter if the chassis has numerous other holes in it, because some of these can be used for mounting the components. In most cases, though, all the necessary holes will have to be drilled.

Wiring

The components under the chassis must be wired before the above-chassis components are mounted, so that the chassis can be placed flat on a table and the wiring done comfortably.

First wire the valve heaters by connecting pin 7 of all three valveholders together. Connect a 6in. length of wire to pin 7 of V3; this will go to the heater transformer when it is mounted. Next earth pin 2 of each valve holder. This will complete the heater circuit, because one side of the secondary of the transformer will also be earthed to chassis.

The valve-holders are of the I.O. type and when they are inserted, earth tags should be affixed under the nuts. The securing nut of V2 should hold a seven-way tag strip, as shown in Fig. 3. The valveholders are then wired with their various components.

It is a good idea to wire in all the resistors first and then the condensers, so as to avoid confusion. All the component leads should be covered with sleeving, and care must be taken

when soldering the crystal diode into position. The heat can be shunted away by holding the connecting lead with a pair of pliers when the iron is applied.

To prevent chafing of the insulation of wires that pass through holes in the chassis, rubber grommets should be used. Alternatively, the wires could have a length of insulation tape wound round them at the point where they pass through the holes.

The H.F.C. recommended is a midget type, which can be secured to the underneath of the chassis. If a top-mounting choke is used it must be screened.

Now that the underneath part is wired, the chassis should be turned over and the top components mounted with nuts and bolts. The wiring of these components is then completed.

If there is a twin tuning condenser at hand without trimmers, do not discard it, because trimmers can be purchased very cheaply and are easily soldered into position, on the top of the tuning condenser.

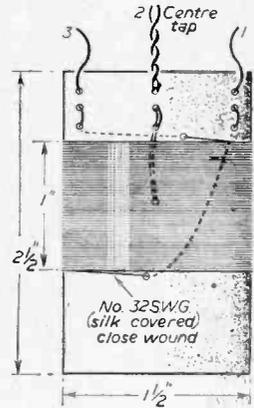


Fig. 2.—Coil winding.

Testing

When everything is connected, check the wiring very carefully before switching on. Ensure also

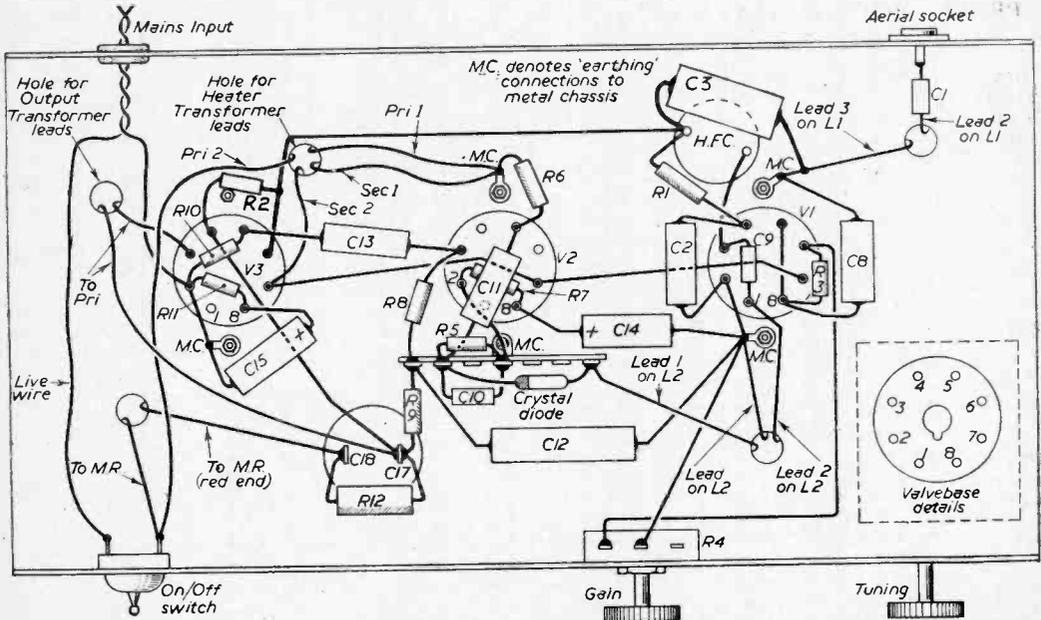


Fig. 3.—Wiring diagram.

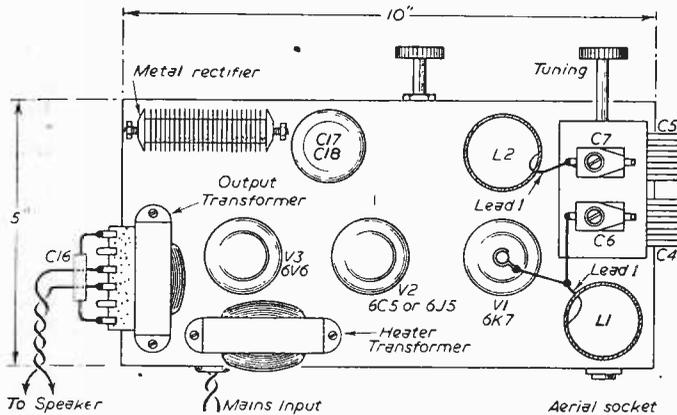


Fig. 4.—Above-chassis layout.

that the black lead (neutral) of the mains flex is the one that is connected to the chassis, and that this lead is also connected to the neutral pin of the mains plug, which should be the non-reversible type. This point cannot be emphasised enough, because there is a danger of electric shock when the leads are connected the wrong way round.

With a good aerial plugged in, switch on and allow the valves two or three minutes to "warm up" properly. When this is done, set the aerial condenser trimmer, C6, to about half way, then tune in to a low wavelength. (The more the condenser is open the lower will be the wavelength received.) Turn down the volume control

until the station is just audible and then adjust the other trimmer, C7, for maximum volume. If it is found that the trimmer is at the limit of its travel either way, the aerial trimmer should be readjusted to compensate. If instability should occur, earth one of the speaker transformer secondary leads. If instability still persists, though the wiring has been properly done, the lead to the top cap of V1 should be screened.

In some cases, modulation hum may be present. A cure is nearly always effected by wiring a 0.01 μ F (1000V D.C.) from the live mains leads to chassis.

(If the trimmers (C6 and C7) are not connected to the body of the tuning condenser they should be connected to chassis at a convenient point.)

be connected to

Selectivity

If the selectivity is found to be rather poor, particularly after dark when hundreds of stations start to transmit, the aerial coupling condenser should be substituted for a 50pF preset condenser. This condenser is then adjusted for a compromise between selectivity and sensitivity. It will be found that as the selectivity is increased—by decreasing the aerial coupling—the sensitivity will fall. When this aerial trimmer is adjusted the tuning condenser will have to be adjusted accordingly. It may also be found necessary to readjust the trimmer, C7, afterwards.

PREVENTING I.F. BREAKTHROUGH

(Continued from 742)

same condenser and coil can be tried in each position. In an extremely difficult case both the parallel and series circuits could be used to obtain very great attenuation of the interfering signal, but the two tuned circuits should then be separately screened. It must be possible to tune the circuits either by using a coil with an adjustable dust core or by using a variable capacitor for a portion of C1 (and C2, if used) in the resonant circuit of Fig. 1. The components may be placed on the receiver chassis, but careful screening is necessary to prevent pick up of signals radiated from the I.F. stages. Alternatively the filter may be placed in a separate box in the aerial lead.

Coils

If half a spare I.F. transformer of the same frequency as the receiver I.F. is available, the condenser and coil in it will be of the correct values for use in the Fig. 1 circuit. The transformer can will also be useful for screening. In case any readers do not have a spare I.F. transformer of the correct frequency available. Table 1 shows the number of turns which should be placed on a coil of the dimensions given in order to make it resonate at the typical I.F.s shown when

the capacitor value used is as stated. Single silk-covered enamelled copper wire (30s.w.g.) is suitable for a coil to resonate at 1.6Mc/s. but somewhat thinner wire is better for lower frequencies. When the circuit has been fitted into the aerial lead, the tuning of the filter should be altered until the interference disappears or at least becomes a minimum.

It must be emphasised that an aerial filter cannot reduce any interference which is picked up at any point other than the aerial.

I.F. breakthrough may also be very much reduced by altering the tuning of all the I.F. transformers slightly so that no strong signal of the same frequency as the I.F. is present at the receiver. This method is applicable to I.F. signals picked up at any point, but will necessitate re-aligning the receiver if the tracking is to be kept perfect. Generally the interference can be eliminated more easily by the other methods given.

TRADE NEWS

TO coincide with expected record sales of tape recorders and magnetic tape this Christmas, "Scotch" Brand are marketing their new Accessory Kit gift wrapped in a gay "to-and-from" Christmas sleeve. This will prove a most acceptable gift both for the recorder enthusiast and the beginner. The sleeve can be easily removed after the Festive season is over, preventing dealers' stock becoming out-dated.

A QUALITY

THIS SET CONTAINS ITS

programme is received at once, clear of noticeable distortion and extraneous noise, provided of course, that the set was left tuned to the station when last switched off.

Circuit

Referring to the circuit diagram (Fig. 1) it will be seen that the signal from the aerial is applied to the grid of V1 via the coil L1, which is slug tuned to the centre of the three stations it is desired to receive

No separate tuning capacitance is required, the self capacitance of the coil plus the input capacitance of V1 being sufficient. V1 functions as an R.F. amplifier and in addition to providing worthwhile gain, effectively prevents any appreciable oscillator radiation from the aerial. This latter function is important since


This design resulted from the author's requirement for a compact receiver giving good quality reproduction for use in a position where the level of electrical interference was high. V.H.F. reception is the only adequate remedy for interference and was accordingly decided upon, while for the double advantage of minimum heat generation in the receiver and economy in cost of components, the power requirement was kept to a minimum. The degree of success achieved in this direction may be judged from the fact that the receiver requires only 52mA at 250V and 3A at 6.3V and includes a 4W push-pull output stage.

Sections

The set will be described in two sections, the V.H.F. receiver and the A.F. amplifier. It may be constructed complete, or as an F.M. tuner, self-powered or otherwise, for use with an existing amplifier. For housing the complete receiver, a description will also be given of an easily made cabinet of professional appearance which will avoid domestic criticism and which requires only simple tools and the expenditure of a few shillings.

The V.H.F. Receiver

This is largely conventional though a little unusual in that it employs both a limiter valve and a balanced ratio detector for the elimination of interference. This feature, combined with a stable form of oscillator, results in the complete elimination of impulsive interference and a minimum of inter-station noise and is well worth the cost of the few extra components required. Further, when the receiver is slightly off-tune, as it will be when first switched on from cold, the

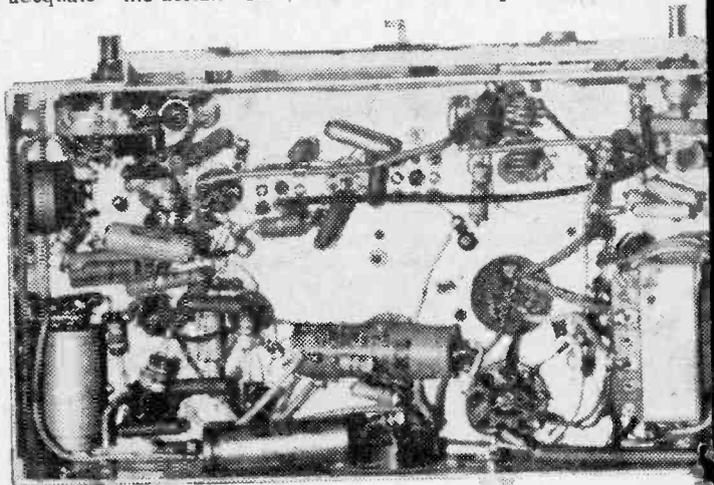

View of the wiring.


the second harmonic of the oscillator frequency falls within television Band III. The amplified signal appears at the anode of V1 and is transferred to the grid of V2.

V2 is an additive frequency changer. It oscillates at a frequency determined by the inductance L2 connected to the screen grid, this frequency being combined within the valve with the signal at the control grid, to produce in the anode circuit the intermediate frequency of 10.7Mc/s. To ensure stability, no capacity other than the 2-gang tuning condenser is placed across L2 and L3. R5

TYPICAL V.H.F./F.M. RECEIVER

OWN POWER PACK AND PUSH-PULL OUTPUT STAGE

By V. E. Holley

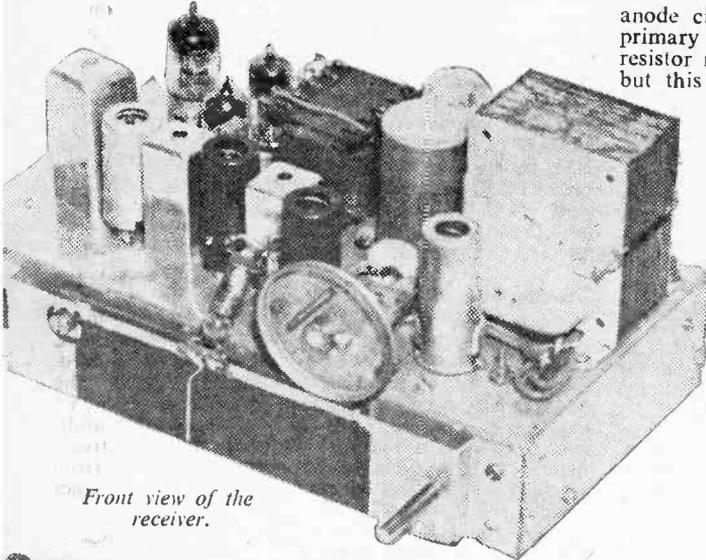

Front view of the receiver.

anode circuit has a 47k resistor, R9 across the primary to flatten the response curve. A similar resistor may be used across the primary of IFT, but this was not found necessary in the prototype. The signal is next presented to the grid of V4, the noise limiter. Because of its low anode and screen voltages, this valve is in a saturated condition and amplitude changes (impulsive interference) present at the grid are not reproduced to any extent in the anode circuit. This action is assisted by the network C15, R11 in the grid circuit, which generates bias and reduces the anode current to a very low value. The anode of V4 is loaded by the ratio detector transformer (RDT) which may be regarded as a conventional I.F. transformer with an additional winding known as a tertiary winding.

Diodes 1 and 2 are so connected that they conduct on the same half cycle of applied voltage and when a signal is applied to the transformer, a rectified current flows around the series

is connected across C8 as shown, for the same reason.

I.F. Amplification

The signal at intermediate frequency is next dealt with by V3 which is arranged as a conventional I.F. amplifier. The transformer in its

circuit Diode 1—R14—VR1—R15—Diode 2. This current is "smoothed" by the "reservoir" action of the capacitors C21 and C22 and a steady potential is built up across the diodes. The capacity of C21 and C22 is such that this voltage remains constant at a level related to the average value of the incoming signal, even upon the receipt of a large interference pulse. Such inter-

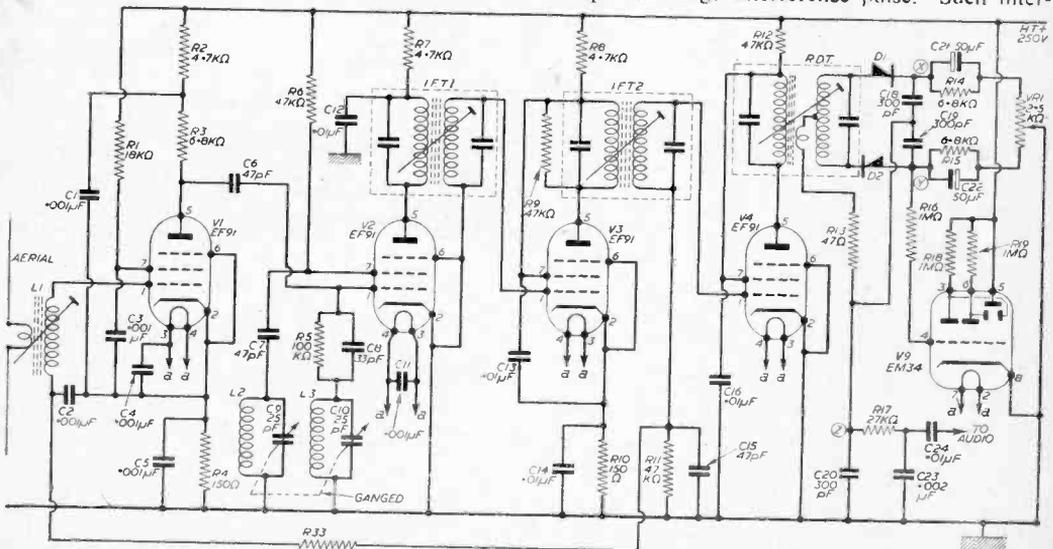


Fig. 1.—The circuit diagram of the V.H.F. section. (There is no C17.)

prolonged if the target voltage is limited to about 220 by means of a suitable series resistor.

Construction

Those who wish to build a tuner with self-contained power supply will probably find it convenient to use the chassis designed for the complete receiver (Fig. 2). If a power supply is not being included then the front half only of this chassis will be suitable. The prototype

a small soldering iron of the instrument type is required. Too much heat must not be applied in making connections and with delicate components, such as the crystal diodes, the wire ends should be held with a small pair of pliers acting as a heat shunt while the iron is applied.

The constructor may be assured, however, that if this receiver is built to specification it will be entirely free from the faults mentioned.

The positioning of the components is not unduly critical, but the constructor is advised to copy faithfully the lay-out of the R.F. and frequency changer stages (Fig. 3(a)).

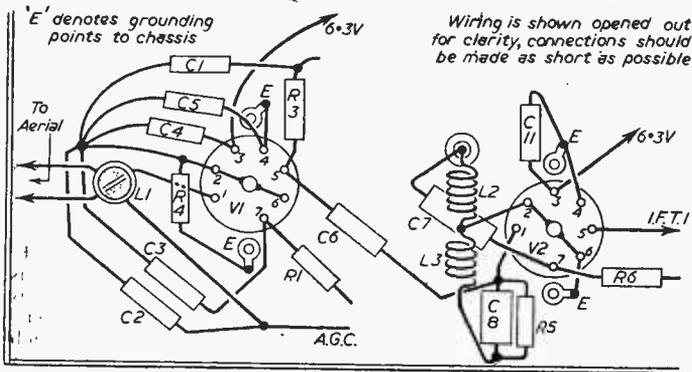


Fig. 3(a).—Wiring of the R.F. and frequency changer stages.

receiver was built on a chassis 10in. X 5in. which was to hand, but this led to some inconvenient congestion at one end, as will be seen from the illustration, and the size recommended is 11in. X 5½in. X 2in.; 16s.w.g. aluminium is suitable material.

To those with no previous experience of V.H.F. apparatus let it be said that the construction is no more difficult than that of a conventional A.M. receiver. Alignment is, if anything, easier, because all the circuits are broadly tuned and therefore more easily brought into line; oscillator tracking presents no difficulty. It is necessary, though, that the technique and principles of this kind of construction should be understood.

Instability must be avoided at all costs, since even a trace will result in a asymmetrical response curve and consequent audio frequency distortion. Reception will be spoiled, too, if harmonics of the intermediate frequency are allowed to appear in the R.F. and frequency changer stages. This latter fault produces what appear to be strong unmodulated carriers which can be seen on the tuning indicator at tuning positions coincident with harmonics of the frequency to which the I.F. circuits are tuned.

Wiring

The requirement, therefore, is for efficient bypassing and decoupling and minimum radiation from wiring and components. It must be remembered that even short lengths of wire have considerable inductance at very high frequencies and that radiation may be picked up by a near-by conductor and conveyed to another part of the chassis. Symmetrical and orderly lay-out must be abandoned in favour of connections as short and direct as possible. Miniature components help greatly, especially ceramic condensers, and

Coils

The aerial coil, L1, consists of 3½ turns of 20 gauge tinned copper wire on a ¼in. former having a ¼in. adjustable dust core. The winding should commence about ¼in. from the open end of the former, the turns being spaced a little more than one wire diameter. If the wire is first wound on a 5/16in. former, removed and slipped over the ¼in. former, it will be a tight spring fit. The aerial coupling

coil of one complete turn should then be added and both windings secured in position with cellulose cement. The arrangement of the windings will be clear from Fig. 3(b).

The R.F. anode and oscillator coils are wound as one self supporting unit with 16s.w.g. tinned copper wire in a clockwise direction on a 5/16in. former. The turns should be close wound with a space of ¼in. between the two coils. Five turns are required for L2 and four for L3. The former should then be removed and the coils opened out evenly to overall lengths of 13/32in. (L2) and 21/64in. (L3). The ends should, of

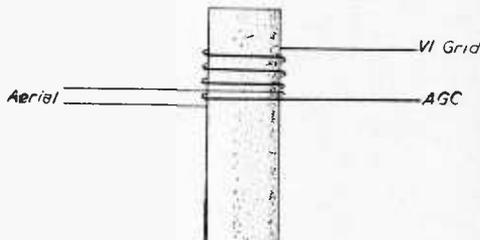


Fig. 3(b).—Construction of the coil L1.

course, be left long enough to pass through the chassis to connect with the tuning condenser. The coils should be mounted about ¼in. below the chassis so that C7 can be fitted diagonally underneath them (when viewed from below chassis). The Jackson U101 is a suitable tuning condenser, but any surplus 2-gang component can be pressed into service provided it is of suitable physical size and the rotor is earthed. The maximum capacity should be reduced if necessary by removing plates from the rotor—three plates in

(Continued on page 785)

Choosing Capacitors

PROPERTIES OF THE VARIOUS TYPES

By J. Ball

ALMOST all constructors appreciate the importance of choosing a capacitor of suitable value and of adequate voltage rating for the circuit in which it is to be used, but the particular uses of the very wide range of capacitors now available is not so well known. Only the most commonly used types of small capacitors will be discussed here.

Electrolytics

Electrolytics are useful because it is possible to obtain very large values in comparatively small containers. It should be noted, however, that they can only be used when connected the correct way round with a suitable D.C. voltage across them. The considerable leakage current which occurs with all electrolytics and their large power factor (about 0.2) renders them unsuitable for many purposes. After the D.C. working voltage has been applied for three minutes, the leakage current is normally of the order of 0.15CV amps where C is the capacitance in Farads and V is the applied voltage. The leakage current is much higher immediately after the D.C. voltage has first been applied. Electrolytics present a fairly high impedance at radio frequencies and are therefore not very satisfactory for R.F. decoupling.

The maximum working voltage of a single electrolytic capacitor is about 600V. If two (or more) are connected in series, the safe working voltage is increased by a factor of about 1.7; no potential dividing resistors should be placed in parallel with each electrolytic when in series, as when no resistors are used, the leakage current allows a lower voltage to be developed across the weaker electrolytic.

Electrolytics are especially suitable for mains frequency smoothing and audio decoupling when large values are required. They are almost the only reasonably small type of condenser which can be made in values of a few thousand microfarads rated at voltages which are quite small.

Ceramics

There is a very large variety of modern ceramic condensers, many of them being suitable for miniature equipment.

The Hi-K (high permittivity) ceramic condensers have a poor power factor (about 0.025) and a rather indeterminate temperature coefficient. They enable a condenser of several thousand pF to be put in a narrow tube less than 1in. long and are usually rated at only 300V D.C. They are more satisfactory in low frequency circuits than at high radio frequencies. Such condensers are almost invariably marked "Hi-K."

The common type of tubular ceramic condenser (other than Hi-K) usually has a power factor comparable to mica condensers (about 0.003) and is therefore suitable for use at high frequencies.

The stability (about 10 per cent.) is much less than that of mica, however, so that this type is not suitable for tuned circuits in which a high stability is required. Ceramic condensers can be obtained with either a positive or negative temperature coefficient and are therefore useful in circuits in which it is desired to minimise thermal drift. Typical values of temperature coefficients are $(+100 \pm 60) \times 10^{-6}$ and $(-750 \pm 80) \times 10^{-6}$ per degree centigrade. Such capacitors would be marked P 100 or N 750, the P and N standing for positive and negative respectively. These small tubular ceramics are not normally used when values much above 1,000pF are required, but values down to 1pF are common. The D.C. working voltage is usually 500 and the insulation resistance about 10,000M, so that the leakage is low.

Ceramic condensers are also available in "feed through" types which are mounted in a hole in

Table showing advantages which certain types of condensers can have.

	Paper	Mica	Hi-K Ceramic	Ordinary Ceramic	Electrolytic
Small size			★		★
Large values... ..	★				★
High Stability		★			
Low Power Factor		★		★	
High Leakage Resistance		★		★	
Negative Temp. Coefficients				★	
Small Temperature Coefficients		★		★	
High working voltage	★				

the chassis or screening and are extremely useful for decoupling at high radio frequencies where the absolute minimum of inductance is required. The values normally range from about 100pF to 500 or 1,000pF. The power factor and working voltage are similar to ordinary ceramic condensers.

Small ceramic capacitors are also made with the very small power factor of 0.0005 for use at several kilovolts D.C. or A.C. with high R.F. currents passing through them.

(Continued on page 790)

Transistorised Mixer Unit

AN IDEAL CIRCUIT FOR STAGE EFFECTS

By A. M. Shafford

THERE are many occasions when it is desirable to mix two or more separate inputs into a common audio amplifier system. In dance-band work two or three microphones are needed to give overall coverage and in studio applications it is frequently necessary to combine speech with a musical background or to fade in sound effects. The mixer unit described will perform all these functions and is a valuable accessory to a tape-recorder.

Gain Controls

An audio mixer accepts two or more separate inputs and combines them into a single output for amplification. Gain controls are provided on


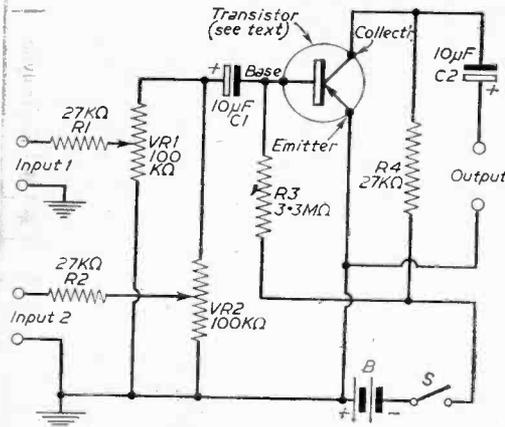


Fig. 1.—A two-channel mixer.

each channel to enable the individual levels to be set up to the required amount. In more ambitious designs, the variation of gain on one channel has no appreciable effect on the level of other channels. This simplified mixer is not entirely free from interaction between gain controls but the effect is so small that it does not represent a serious disadvantage. This is especially true when the mixer is used in a "dynamic" role to fade up one channel whilst simultaneously fading down another.

Self-contained Unit

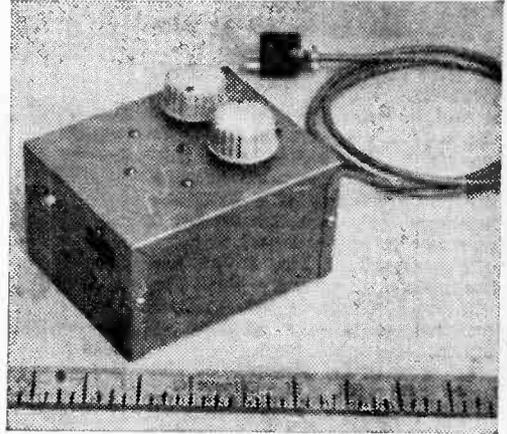The illustration shows a two-channel form of the mixer, although it can be constructed to accommodate three or even four separate inputs.



A completed two-channel mixer.

The unit is cheap, small in size and requires no external power supplies, having its own internal battery made up of two pen-light cells.

In the photograph the two control knobs, one for each channel, which adjust the gain are clearly shown, and the channel input sockets are visible at the end of the box. In the model shown, different types of input socket are used for each channel, but this is simply to suit the writer's particular requirements. Any input socket can be used, and similarly, the cable connecting the mixer to the amplifier can be terminated with any suitable plug. This cable is shown in the illustration in a coil at the rear of the unit.

Components Not Critical

Fig. 1 shows the circuit of a two-channel mixer and lists the component values, none of which is critical. The transistor can be a red-spot type or an OC71, both of which are readily available at a low price. The unit operates on two pen-light cells in series (total 3V) held in a clip designed for this purpose which is available from radio parts dealers. Alternatively the cells can be soldered directly into circuit since the drain on them is so low that a battery life of several hundred hours can be expected.

COMPONENTS FOR FIG. 1

- R1, R2—27k ½-watt.
- R3—4.3 M ½-watt.
- R4—27k ½-watt.
- VR1, VR2—100k potentiometers.
- C1, C2—10μF 25V.W. electrolytic.
- S—Single-pole on/off switch.
- B—2 penlight cells (two 1½V).

COMPONENTS FOR FIG. 2

- R—27k ½-watt.
- VR—100k potentiometer.
- R3—3.3M ½-watt.
- R4—27k ½-watt.
- C1, C2—10μF 25V.W. electrolytic.

Use as a Pre-amplifier

With both knobs set at mid-scale the output is shared more or less equally between both channels. With a little practice it will be found possible to fade the channels up and down quite smoothly. By setting one gain control at zero, the other channel can be used singly as a transistor pre-amplifier which makes for a very useful and compact unit.

The circuit of Fig. 2 indicates the method of adding a third and additional channels when it is required to mix a number of inputs.

It is a useful feature of this unit that since it uses no A.C. power supplies it is hum-free, an important point for high quality reproduction.


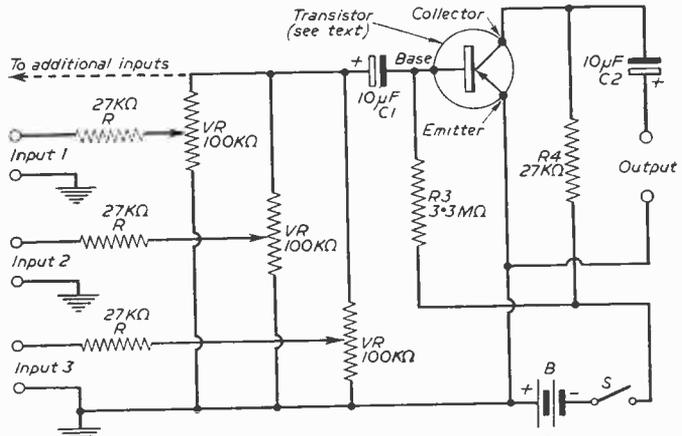


Fig. 2.—Method of adding a third and additional channels.

Wireless Set No. 19 Mk. II

NOTES ON THIS EX-GOVERNMENT RECEIVER

By R. G. Fenby

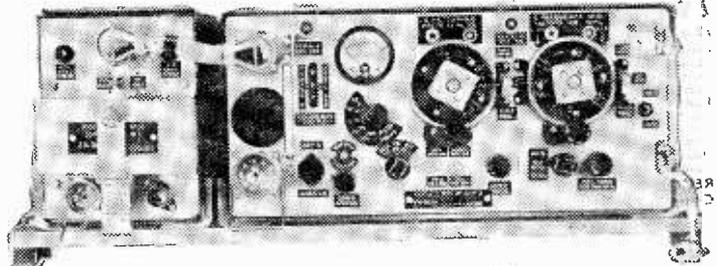


The No. 19 set and power pack.

THE following points on the Wireless Set No. 19 might be of interest to owners of this transceiver of which many thousands were recently released by the Ministry of Supply.

In the H.F. receiver 2Mc/s. one disadvantage that is often talked about is lack of selectivity in the I.F. amplifiers. When newly produced, the I.F. response curve was about 8kc/s wide, and over the years the sets have aged so much that many of them in amateur use now have very broad selectivity curves.

This broad selectivity of 8kc/s was produced purposely by the designers, and reference to a circuit diagram will show that across each I.F. transformer primary coil there is a resistor to 100k. The function of this is to broaden the selectivity curve artificially, which is not required for amateur use.

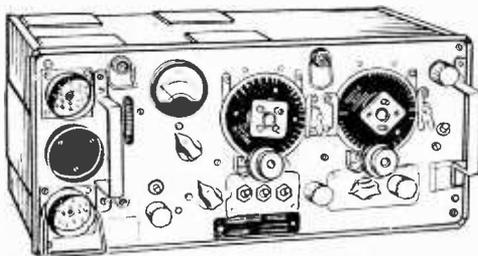The original reason for a broad I.F. was that



Another view of the No. 19 set.

Army stations always operated on "nets" of several stations, using one frequency. Unfortunately, owing to the rough conditions in which they were used, the sets used to drift off frequency and so all the stations on one net were usually covering several kc/s at the end of an hour or so. Thus the I.F. response had to be broad.

The remedy is obviously to remove these resistors, and such action will sharpen the selectivity appreciably. Since the majority of the Mark 2 sets in current release were made in Canada in the Second World War, they are now almost 20 years old and, consequently, the tuning capacitors of the I.F. transformers will almost certainly be "leaky." This will tend to give the same effect reported above, so it is worthwhile replacing all these capacitors and retrimming the transformers using the meter switched to "AVC." tuning for maximum dip, using a steady signal.

In the same way the AVC smoothing condensers will also be leaky and should be replaced. Proof of this is available by examining the drop in "AVC" reading on the meter when tuning into a strong station. There should be a dip of 50 per cent. for an S9 signal. No dip or a very small dip, signifies leaks in the AVC capacitors.

Lastly, it is very strongly advised that you use the correct variometer between aerial and input of the set. By simply connecting the aerial to the aerial socket on the receiver, the signal-to-noise ratio will decrease, and there will be more second channel interference.

RECORD PLAYER BARGAIN OFFER

A self-contained Portable unit comprising the latest Collaro 4-speed Auto Changer Record Player, incorporating the famous High Fidelity Studio "O" Xtal Pick-up with Turnover Cartridge, and fitted with L.P. and 78 Sapphire stylii. An internal 2 valve amplifier of modern design with variable tone and volume controls is fitted. This, together with a quality 6in. P.M. speaker, ensures a high standard of reproduction. The whole is housed in a high standard of reproduction. The whole is housed in a robust wooden cabinet attractively styled in a maroon contemporary leather cloth with contrasting polka dot relief. A fortunate buyer purchase enables us to offer this commercially styled Player at the following attractive breakdown Unit prices:



TRS

- Collaro 4-speed autochanger, £6.19.6 + 4/6 carr.
- 2-valve, 2-stage amplifier, ready wired, complete with speaker, etc., £3. 7.6 + 2/6 carr.
- Cabinet with mounting board, etc. Size 18 1/2 in. x 13 1/2 in. x Ht. 8 1/2 in. £2.12.6 + 3/6 carr.

This complete 3 unit "Do-it-yourself" Record Player Kit offered at amazing bargain price of

£12.19.6

carriage free.

This is a recommended bargain buy and when present stock is exhausted cannot be repeated. Originally built to be sold at 17 gns.

2 Waveband Car Radio Kit

12 v. operation Med. & Long Waves Development of the famous Brimar Hybrid vibratorless Car Radio Circuit. 5 latest type low voltage valves and Power Transistor. R.F. stage and permeability pre-aligned Cyclon Tuner Unit provide extremely good sensitivity and Signal/Noise ratio. Printed circuit and 7in. x 4in. Speaker. Self-contained in neat Metal Cabinet 8in. x 7in. x 2 1/2in. with attractive dial. Speaker and Power Transistor stage mounted separately, approx. 8in. x 5in. x 3in.

RECOMMENDED BUY Complete Kit £12.19.6

Complete "Bargain Price" £12.19.6
F. & P. 3/6.
Instruction Booklet and Parts List available shortly 2/3 post free.

NEW BOXED VALVES	NEW REDUCED PRICES		
1R5, 1T4 7/8	1D96 9/-	1E90 9/6	1PCF82 10/6
1R5 7/6	1DK99 8/-	1EP86 13/6	1PL33 12/6
2R4, 3V1 8/6	1DL86 9/-	1EP91 8/6	1PL31 12/6
5Z4 9/6	135L6 9/6	1EL41 10/6	1PL82 7/6
6K7 5/6	1EAC80 9/6	1EL41 9/6	1PL83 11/6
6K8 8/6	1EBC41 9/6	1EM45 10/6	1PY80 9/6
6X4 7/6	1ECC83 9/6	1EY51 10/6	1PY81 9/6
6X7 8/6	1EYX4 10/6	1EY56 10/6	1PY82 9/6
6V6 4/6	1EYF80 11/6	1EY80 7/6	1PY83 10/6
6X4 7/6	1EYF82 11/6	1EY81 7/6	1U25 12/6
7C4 9/6	1EYH81 10/6	1MU14 9/6	1U191 12/6
7Y4 9/6	1EYH82 11/6	1PC84 10/6	1UCH42 10/6
1DAP96 9/6	1ECL82 11/6	1PCF80 10/6	1UP41 10/6

Sold for List.

SPECIAL PRICE PER SET
1R5, 1T4, 1R5, 2R4 or 3V4 ... 27/6
1DK96, 1D96, 1DAP96, 1L86 ... 35/-
6K8, 6K7, 6Q7, 6V6, 5Z4 or 6X5 ... 35/-

SPECIAL OFFER

Superior type Art leather covered Portable case. Well-known Manufacturer's surplus, in attractive tan colour with non-tarnish gilt fittings.
Size: 16in. x 11 1/2in. x 5 1/2in.

Knockout price 15/6 Post & Pack. 2/6

ALTERNATIVE OFFER

Above case fitted with latest BSR 4-speed T19 Record Player Unit, Pul-Fi Xtal pick-up. Ready mounted and wired. Complete with mains lead and detachable screened pick-up lead. An ideal portable record player unit for tape or amplifier use.

Bargain 5 gns. Post & Pack. 4/6.

7-VALVE AM/FM RADIOGRAM CHASSIS

Surplus Bargain Offer



Valve Line up: 6C85, ECH81, EF89, EABC80, EL84, EM81, EZ80.
3 waveband and switched gram positions. Med. 200 m.-500 m., Long 1,000-2,000 m., VHF/FM 89-95 Mc/s.
4 Controls. Vol., On-off, Tone, Tuning, Wavechange. P.U., Ae. and E.U., and speaker sockets. Magic eye tuning. Philips continental tuning insert with permeability tuning on FM, and combined AM/FM IF transformers, 460 Kc/s and 10.7 Mc/s. Dust core tuning all coils. Latest circuitry, including AVC and Neg. Feedback. 3 watt output. Sensitivity and reproduction of a very high standard. Chassis size 13 1/2in. x 6 1/2in. Height 7 1/2in. Edge illuminated glass dial 1 1/2in. x 3 1/2in. Vertical pointer, Horizontal station names, gold on brown background. A.C. 200/250 v. operation.

£13. 10. 0

Carr. and ins. 5/-.

Complete with 4 knobs—walnut or ivory to choice.

RE-GUNNED TV TUBES

New Reduced Budget Prices

New Heater, Cathode and Gun Assembly fitted to all tubes. Reconditioned virtually as new. Now 12 months' guarantee to highest standards—as used by our own Service Dept.

- 12in. £6. 14in. £7. 17in. £8.10.0.
- Most Mullard & Mazda types ex-stock Carr. a ins. 10/-.
- 10/- Part Exchange allowance on your old tube.

RECORD PLAYER BARGAINS

NEW RELEASE by E.M.I.—4-speed Single Player Unit fitted with latest stereo and monaural Xtal cartridge and dual sapphire stylii. Auto stop and start. A fidelity unit and bargain buy at only **£8.19.6**.
BSR—UAS Model, 4-speed autochanger with crystal turnover cartridge, etc., wired for stereo, Bargain, **£6.19.6**.
Garrard—Latest BC191 D.Mk 2—fitted with G.S. Xtal cartridge, plug-in monaural head. Auto/manual selector, etc. The connoisseur's choice for audio perfection. Bargain 10 gns.
Plug-in stereo head G.S.10 £2 extra.
All above are brand new, fully guaranteed models. Carr. and ins. 4/6.
Comprehensive bargain range of Collaro, BSR and Garrard Units in stock. Send for comprehensive bargain lists.

COAX 80 OHM CABLE

Stand 1/2in. diam.

Low Loss Semi-rigid spaced AERIAL polythene ins. **SPECIAL REDUCED PRICES**. 20 yds., 12/6. 40 yds., 22/6. 60 yds., 32/6 P. & P. 1/6. F. & P. 2/-. P. & P. 3/-. All other lengths 5d. per yd.
Coax Plugs, 1/-; Sockets, 1/-; Couplers, 1/3; Cable End Sockets, 1/6. Outlet Boxes, 4/6.

JASON FM TUNER UNITS

(87-105 Mc s)

Designer-approved kits of parts for these quality and highly popular tuners available as follows.

STANDARD MODEL (FMT)—as previously extensively advertised.

COMPLETE KIT, 5 gns., post free.

Set of 4 spec. valves, 39/6, post free.

LATEST MODEL (FMT2)—attractively presented shelf mounting unit in enclosed Metal Cabinet with Built-in Power Supply.

COMPLETE KIT, 27. p. & p. 3/6.

Set of 5 spec. valves, 39/6.

NEW JASON COMPREHENSIVE F.M. HANDBOOK

48 hr. Alignment Service, 7.6 p. & p. 2/6.



Listed above are only a few items from our very large stock. Send 3d. stamp today for Complete Bargain List.

Terms: C.W.O. or C.O.D. Kindly make cheques, P.O.s, etc., payable to T.R.S. Post/Packing up to 11s 7d., 11s. 1/1, 31s. 1/4, 51s. 2/1, 101s. 2/6.

Hours: 9 a.m.-6 p.m. 1 p.m. Wed. Open all day Saturday.

TRS

70 BRIGSTOCK ROAD, THORNTON HEATH, SURREY (THO 2188)

50 yards Thornton Heath Station.

Buses: 130A, 133, 159, 166 and 190

CIRCUITS FOR AUDIO AMPLIFIERS

-a book every enthusiast will want!

This new Mullard publication is a practical manual for every audio enthusiast. In addition to describing twelve of the most popular Mullard circuits, it has introductory chapters on many of the theoretical and practical aspects of high quality sound reproduction.

Whether you are interested in disc or tape, monaural or stereo, you will find that "Circuits for Audio Amplifiers" gives just the sort of information you need.

This informative book costs only 8/6. The demand for it is high, so get your copy now from your local radio dealer.




Mullard

MULLARD LIMITED • MULLARD HOUSE • TORRINGTON PLACE

LONDON W.C.1
MYM423A

CONSTRUCTORS CORNER

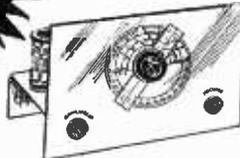Construction price includes valve and one coil covering 40-100 m.
 ● Can be converted to 2v. or 3v.
 ● Receives speech and music clearly from all over the world.
 Send 2/- for diagram and price list.



Explore the world on short-wave radio (10-100 m)

FOR ONLY **35/-**

TRANSISTOR POCKET RADIO

Two-stage circuit using variloopstick coil.

- Ideal for the beginner.
- Can be built in 30 minutes.
- Works for months off 7d. battery.
- Fits into palm of your hand.



The ideal low-cost transistor pocket radio for the beginner.
 Send 2/- for data and list of components.

ONLY **30/-**

CRYSTAL RECEIVER

Covers M/W Band

All components including case for **10/6**
 Ideal for the beginner

ENSURE SUCCESS WITH R.C.S.

SENSATIONAL RESULTS WITH 2 TRANSISTORS

- ★ No aerial or earth.
- ★ Dial tuning with mini .0005.
- ★ Drilled chassis, colour coded, components, simple layout for beginners.
- ★ Special small case fits shirt pocket.
- ★ Soldering iron and pliers are only tools needed.



Finest results ever obtained with 2 transistors and diode layout. The ideal radio to carry with you everywhere. PARTS PRICE LIST & EASY LAYOUT PLANS, 2/-.
 Total building cost, including transistors, wire, etc., **62/6**

BUILD THIS AMAZING RADIO

POWERFUL! PERSONAL! PORTABLE!

- ★ Sturdy metal case.
 - ★ No holes to drill.
 - ★ Detachable rod aerial.
 - ★ All batteries self contained.
 - ★ Can be built in 1 hour.
 - ★ Covers medium waves.
 - ★ Loud clear tone.
 - ★ Selective tuning.
 - ★ All parts are sold separately.
- This delightful set is designed to give you a completely personal portable radio. Bronze-finished case. Ideal for the beach, the bedroom, the office—in fact, anywhere.
 Send 2/- for wiring diagram and component price list.

FOR ONLY **35/-**




Post and packing: Under 10/- add 9d.; under 40/- add 1/6; over POST FREE

Trade Enquiries
 Welcomed

R.C.S. PRODUCTS (RADIO) LTD. 11, OLIVER RD., LONDON, E.17.

Mail Order
 Only

Improving Amplifier Quality

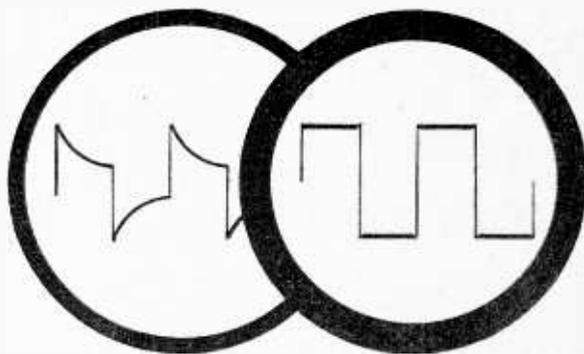

USING NEGATIVE FEEDBACK TO REDUCE DISTORTION

By C. Stone

THE quality of reproduction obtained from inexpensive and simple amplifiers can usually be improved considerably by making small circuit changes, such as adding negative feedback. Or it may be feasible to enlarge the amplifier, possibly replacing a single output valve by means of a push-pull stage, or by adding a pre-amplifier to compensate for the reduced gain arising from the use of feedback.

Lower Gain

Negative feedback always reduces amplification over that part of the amplifier to which it is applied. The gain with feedback is:

$$\frac{A}{1 + Ab}$$

where A is the original gain of the amplifier before feedback was used, and b is the fraction of voltage

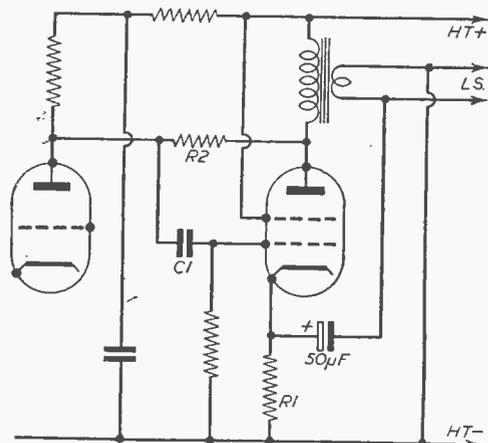


Fig. 1.—Applying negative feedback to the output stage.

fed back. For example, assume the amplifier originally had a gain of 500, and the fraction fed back is 1/200th, or 0.005. Gain with feedback is:

$$\frac{500}{1 + (500 \times .005)} = \frac{500}{3.5} = 143 \text{ approx.}$$

At first sight this reduction may seem rather severe. However, it is seldom necessary to have the gain or volume control at maximum. If it is, the reduction in

volume may not be too great, because the human ear does not convey a sensation of volume directly proportional to power, instead having increased sensitivity at lower volumes. If volume *does* become insufficient, it can in any case be restored by adding a small triode, current for which will usually be available without overloading the existing power pack.

Reduced Distortion

The improvement in quality, with feedback, can be approximately calculated from the following:

$$\frac{d}{1 + Ab}$$

where d was the distortion without feedback, A the amplifier gain, and b the fraction fed back. Assume the amplifier gave 4 per cent. distortion. With the proportion of feedback previously mentioned this becomes:

$$\frac{4 \text{ per cent.}}{1 + (500 \times .005)} = \frac{4}{3.5} = 1.1 \text{ per cent. approx.}$$

This is a considerable reduction in distortion. If feedback is increased, distortion falls. For example, with 5 per cent. feedback, the figure becomes approximately 0.15 per cent. Amplification is also reduced as feedback is increased.

If the feedback is positive, instead of negative, the amplifier will give very distorted results, or oscillate. This is usually corrected by reversing connections to the output transformer secondary, which is usually included in the feedback circuit.

Applying Feedback

Two very simple methods of applying feedback to an output stage are shown in Fig. 1. The cathode by-pass condenser circuit is completed through the output transformer secondary, so that feedback is applied directly to the cathode. If oscillation arises the transformer connections must be reversed. This applies to other circuits where feedback is taken from the secondary.

R2 also applies feedback to the output valve grid, and helps to compensate for the falling bass characteristic of C1. That is, C1 passes high frequencies most readily. These frequencies therefore appear most strongly at the output valve anode, and are applied through R2 to the input. R2 is of high value (say 0.5 to 1M) and has little effect on the anode load of the triode.

With most simple two or three valve amplifiers, feedback can be applied to the cathode of an early

valve, as in Fig. 2. Values are for the valves indicated, but the same circuit can, of course, be used with other valves.

The amount of feedback can be increased by reducing the value of R1. Initially, 4.7k can be used, but the best value depends on the extent to which amplification can be reduced. With such a circuit

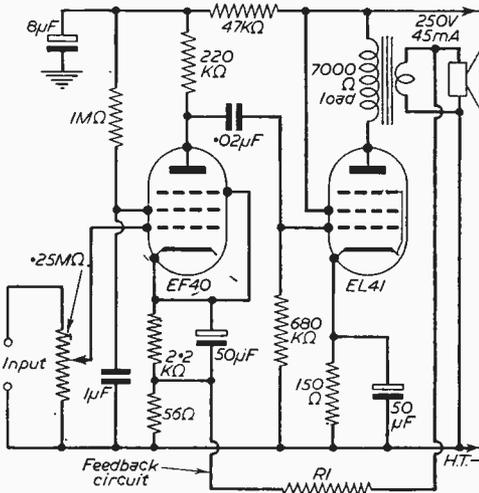


Fig. 2.—Addition of negative feedback to a simple amplifier.

employing only two valves, there is little gain to spare with small inputs, but plenty to spare with large inputs, such as from a valve radio feeder.

When adding feedback to powerful amplifiers, do not allow oscillation to build up or reach maximum or persist, but switch off and reverse connections as explained. Nor should feedback be applied over parts of the circuit in which tone controls exist though it can be used over all stages after the tone control circuits.

Triode Operation

A very simple means of reducing harmonic distortion in an output stage employing a pentode or tetrode is to re-wire the holder for triode operation. To do this, join screen grid and anode, as in Fig. 3. It is usually best to remove any by-pass condenser across the output transformer, at the same time, as it is no longer needed.

This modification is almost always possible, the exception being with very small valves where the maximum screen grid voltage is lower than the anode voltage actually present. Triode running will somewhat reduce gain in this stage.

This simple modification is particularly useful when no feedback is applied and the harmonic distortion of the output stage is felt to be rather high. For example, a pair of 6V6 valves in push-pull would normally have a harmonic distortion of about 3.5 per cent., but this falls to about 0.5 per cent. with triode operation. The power output from the stage is also reduced, and this must not be overlooked if the amplifier is used for public-address or other purposes where maximum output is necessary.

Changing to triode operation somewhat reduces the optimum load. For example, the optimum load

for two 6V6 valves, tetrode operated, with a 285V. supply, is 8,000 ohms. This falls to 4,500 ohms for triode operation. The output transformer need not necessarily be changed, however, because triodes work well with somewhat higher loads than optimum. This means that an improvement is still possible with the same transformer. But if the transformer has windings enabling a lower ratio to be selected, these should be chosen.

Transformer Ratio

Distortion can easily arise from the wrong output transformer ratio. The correct ratio can be found from the following:

$$\sqrt{\frac{\text{Optimum Load}}{\text{Speaker Impedance}}}$$

For example, assume the output stage optimum load is 8,000 ohms, and a 5 ohm speaker is used. Transformer ratio equals:

$$\sqrt{\frac{8,000}{5}} = \sqrt{1,600} = 40.$$

A transformer of approximately 40 : 1 ratio should thus be fitted.

When feedback is applied, the effective output impedance falls. With triodes, this is not usually very critical, because a slightly higher impedance than that actually required is not important. But for best possible results, or when using tetrodes or pentodes, the transformer ratio can be modified.

The approximate effective output impedance, with feedback, may be calculated from the following:

$$\frac{r_a}{1 + \mu b}$$

where r_a is the anode impedance of the output valve, and μ its amplification factor, b being the fraction of output voltage fed back. For example, assume the amplification factor is 20, and anode impedance 10,000 ohms. The effective output impedance, with 0.005 (or 1/200th) feedback is:

$$\frac{10,000}{1 + (20 \times 0.005)} = \frac{10,000}{1.1} = 9,090 \text{ ohms approx.}$$

In the event of the amplification factor of the valve not being listed, it can be found by multiplying the Mutual Conductance in mA/V by the anode impedance in kilohms. For example, anode impedance 10,000 ohms or 10k, Mutual Conductance 2mA/V, so amplification factor = $10 \times 2 = 20$.

When negative feedback is used the characteristics of the output transformer become particularly important, and for the best possible results a transformer of sound design is necessary. With very small, cheap transformers internal capacity or other defects may cause phase shift at some frequencies, so that the feedback is no longer even approximately 180deg. out of phase with the input to the amplifier.

(To be continued)

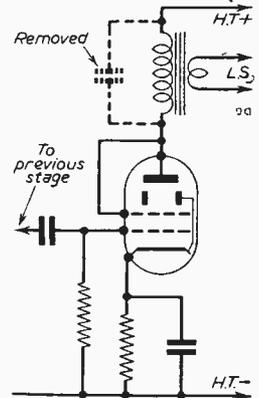



Fig. 3.—Triode operation of pentodes and tetrodes.



FOR VALVES - TUBES AND COMPONENTS - BY RETURN POST SERVICE

AC/P 7/6	ECH81 9/-	GZ32 12/-	PL84 12/7	UCL83 14/-	2C26 1/6	6F15 14/-	7D6 13/6	30P12 12/6
AC6PEN 6/6	ECH83 13/11	H30 5/-	PL820 18/7	UF41 9/-	2X2 4/6	6F18 15/3	7H7 9/-	30P16 9/6
ACVP1/5	ECL80 10/-	H63 10/-	PX25 12/6	UF80 13/11	3A4 7/-	6F23 18/7	7Q7 9/-	30PL1 12/6
10/-	ECL82 12/6	HL23DD 8/6	PY32 17/11	UF89 9/-	3A8GT 6/-	6F33 9/-	757 9/6	35L6GT 10/-
ATP4 3/6	ECL83 19/3	HL41 3/6	PY80 7/6	UL41 10/-	3D6 5/-	6H6 2/6	7Y4 8/6	25Y5 9/9
AZ1 10/-	EF22 8/6	K40N 9/-	PY81 8/6	UL84 9/-	3Q5GT 9/6	6H6GT 2/6	8D2 2/9	35W4 7/6
AZ31 10/-	EF36 5/-	KF35 8/6	PY82 7/6	UYIN 12/6	3S4 7/6	6J5M 7/6	9D2 3/6	35Z4GT 8/-
AZ41 13/11	EF37A 15/-	KF35 8/6	PY83 8/6	UY41 7/6	4D1 3/-	6J7 6/6	10C1 17/3	42 8/-
B36 15/-	EF39 5/9	KT2 5/-	PZ30 19/11	UY85 7/6	4D1 3/-	6J7M 6/6	10D2 12/-	35Z5GT 9/-
CL4 12/6	EF40 14/6	KT24 5/-	PEN4VA 15/-	VP13C 3/6	5R4G 9/6	6K7M 6/6	10F1 15/-	50C5 11/6
CL33 19/3	EF41 9/9	KT33C 8/6	PEN25 6/-	VP23 6/6	5U4G 6/6	6K7M 6/9	12A6 6/6	50L6GT 8/6
CY31 16/7	EF42 11/-	KT55 11/6	PEN46 7/-	VP41 8/6	5V4 11/6	6K6GT 7/6	12A7 7/6	75 11/6
CY1 18/7	EF50 4/-	KT61 13/6	PEN220A 4/-	VP133 15/-	5Y3G 8/-	6K6GT 7/6	12A7 7/6	80 8/6
DAF96 8/9	EF50SYL 7/-	KT63 7/6	PENA4 15/-	VR22 5/6	5Y3GT 8/-	6K7GT 5/9	12A7 7/6	80 8/6
DF96 8/9	EF54 6/-	KT66 17/6	PM12M 8/-	VR150/30 3/-	5Z4G 9/-	6K8GT 10/-	12A7 7/6	80 8/6
DH63 9/-	EF55 10/-	KT88 22/6	QP21 5/-	VR105/30 8/-	5Z4M 10/-	6K8GT 10/-	12A7 7/6	80 8/6
DK96 8/9	EF80 7/6	KTW61 6/6	SP41 3/-	VR116 4/-	6A7 11/6	6K25 19/11	12BA6 9/-	83 10/-
DL96 8/9	EF85 7/6	KTW63 7/6	SP61 3/-	VR150/30 7/6	6A8G 9/-	6L6G 8/-	12BE6 9/-	83 10/-
DM70 7/6	EF86 13/-	KTW41 3/6	SP45 10/6	VU120A 3/6	6AC7 6/6	6L6M 9/6	12C8 9/-	302 10/6
EASO 1/6	EF89 8/9	MLH41 7/9	SP47 10/6	VU39 7/6	6AG5 5/6	6L7G 7/6	12H6 3/6	304 10/6
EABC80 9/6	EF91 5/9	M44 8/6	TDD13C 7/6	VU39 7/6	6AL5 5/6	6N7GT 7/6	12J5GT 3/-	305 10/6
EAF42 10/6	EF91(BVA) 9/-	MSP4/5 7/6	U10 10/6	(MU12/14) 8/9	6AM5 12/6	6P28 26/6	12K7GT 10/6	306 10/6
EB34 2/-	EF97 13/3	MSP4/7 7/6	U14 8/6	W76 7/6	6AM6 6/6	6Q7G 9/6	12K8GT 7/6	807 16/6
EB41 8/6	EF98 13/3	MVS/PEN 10/-	U22 8/-	W77 8/6	6AQ5 7/6	6Q7G 9/6	12K8GT 7/6	954 2/-
EB91 6/6	EL32 5/6	OZ4 5/6	U25 14/-	W79 10/6	6AT6 8/6	6SA7GT 8/6	12Q7GT 7/6	956 3/6
EBC33 6/9	EL33 13/-	P61 3/6	U40 8/-	X78 16/-	6AU6 10/6	6SG7 7/6	12S47 6/6	5763 9/6
EBC41 9/6	EL34 15/-	PABC80 13/11	U45 15/-	Y63 9/-	6B8G 4/6	6SH7 6/6	12S47 6/6	9002 5/6
EBC81 11/4	EL38 26/6	PCC84 9/-	U50 8/-	Z309 7/6	6BA6 7/6	6S17 8/6	12S7 6/6	9004 5/6
EBC90 12/7	EL41 10/6	PCF80 9/6	U76 8/-	Z359 7/6	6BE6 8/-	6SK7 6/-	12S7 6/6	9006 5/6
EBF80 9/9	EL42 10/6	PCF82 12/6	U91 11/6	I3 3/6	6BH6 9/-	6SL7GT 8/-	12SN7GT 8/-	9006 5/6
EBF89 9/6	EL81 16/7	PCF84 16/7	U91 11/6	I3 3/6	6B8 9/-	6SN7GT 7/6	12SN7GT 8/-	9006 5/6
EC31 7/6	EL84 9/-	PCL82 12/-	U91 11/6	I3 3/6	6BR7 12/6	6S07 9/3	12SN7GT 8/-	9006 5/6
EC81 8/-	EM34 9/6	PCL83 14/6	U91 11/6	I3 3/6	6BV6 9/-	6UAGT 12/-	12S7 8/6	9006 5/6
EC82 7/6	EM80 10/-	PL38 17/6	U91 11/6	I3 3/6	6BW7 8/6	6U5G 8/6	12S7 8/6	9006 5/6
EC83 9/-	EM81 10/6	PL36 15/-	U91 11/6	I3 3/6	6C4 6/6	6U7G 8/6	12S7 8/6	9006 5/6
EC84 10/6	EY51 10/6	PL81 12/6	U91 11/6	I3 3/6	6C5GT 12/6	6V6G 6/6	12S7 8/6	9006 5/6
EC85 9/6	EY81 13/3	PL82 8/6	U91 11/6	I3 3/6	6C6 5/-	6V6GT 7/9	12S7 8/6	9006 5/6
ECF80 12/-	EY86 10/-	PL83 10/-	U91 11/6	I3 3/6	6C31 7/6	6X4 7/6	12S7 8/6	9006 5/6
ECF82 13/-	EZ40 7/6	UCL82 16/7	U91 11/6	I3 3/6	6CD6G 6/6	6X5G 7/-	12S7 8/6	9006 5/6
ECH42 9/6	EZ41 7/6	UCL82 16/7	U91 11/6	I3 3/6	6D6 5/-	6X5GT 7/6	12S7 8/6	9006 5/6

RECORD PLAYER UNITS
 BSR Monarch Model UA8, 4 speed, 10 record capacity, Full-Fi turnover crystal cartridge, £6.19.6.
 Collaro Conquest, fully mixing changer on 7", 10" and 12" records fitted with Studio "O" Crystal Cartridge, £7.19.6.
 Garrard RC120/D/11, 4 speed automatic unit, manual control to enable records to be played singly.
 Collaro AC4/564, 4 speed single player, with automatic stop, fitted Studio "O" Crystal Cartridge.
 Pifco All-in-One Radiometer, for all practical testing, 32/6.
 Tyana Soldering Irons, 40 watt, 16/9 each.
 Headphones, Low Resistance, 120 ohms, 7/6 pair.
 Headphones, High Resistance, 4,000 ohms, 13/6 pair.

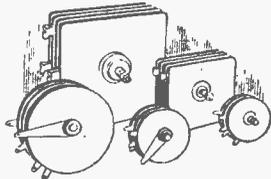

ACOS MICROPHONES
 Acos Mic 39-1. Crystal Stick Microphone for use as a hand, desk or floor stand unit for high quality recording, broadcasting and public address work. LIST PRICE £5.50. OUR PRICE, 39/6. With stand, 47/6. With Floor Stand adaptor, 52/6. Postage 1/6. MIC 40, as supplied with most modern tape recorders, listed at 35/-. OUR PRICE, 25/-. With folding rest and 8 ft. lead, 40/-. 6,000 c.p.s.

RECTIFIERS FOR BATTERY CHARGERS
 12 v. 1 amp. ... 4/3
 12 v. 2 amp. ... 7/-
 12 v. 3 amp. ... 10/-
 12 v. 4 amp. ... 12/-
 12 v. 5 amp. ... 14/6

LOUDSPEAKER UNITS
 All Brand New. Note the Special Prices. All Permanent Magnet 3 ohms Impedance.
 2" Square Celestion ... 18/6
 3" Square Celestion ... 18/6
 3" Square Elac ... 19/6
 5" Round, Goodman, Celestion & Plessey ... 16/6
 6" Round Celestion ... 17/6
 10" Round Elac & Celestion ... 22/6
 12" Round Plessey ... 32/6
 6" x 4" Plessey ... 19/6
 7" x 4" Plessey & Goodman ... 19/6
 8" x 5" Allen (Golden) ... 25/6
 10" x 6" Goodman & Celestion ... 25/6
 Special Offer 8" Golden Eight, 15 ohms Speech coil, 42/6

TELEVISION BAND III CONVERTORS
 INVICTOR Model 245. Self-contained own power unit. Bands 6 to 10. Listed £9.19.6. OUR PRICE, £4.10.0.
 INVICTOR 13 Channel Adaptor, for Models 118, 119, 120. Listed £7.19.6. OUR PRICE, 59/6.
 WOLSEY TC 165 Converter Aerial Converter. Listed £9.19.6. OUR PRICE, £4.10.0.

CATALOGUE
 Our 1960 catalogue is now available, please send 1/- in stamps for your copy. Trade Catalogues also available, please attach your Business Letter Heading.


ALPHA
 RADIO SUPPLY CO.
 103 LEEDS TERRACE
 WINTOUN STREET
 LEEDS 7

TERMS: Cash with order or C.O.D. Postage and Packing charges extra, as follows: Orders value 10/- add 1/-; 20/- add 1/6; 40/- add 2/-; £5 add 3/- unless otherwise stated. Minimum C.O.D. fee and postage 3/-. For full terms of business see inside cover of our catalogue. Personal Shoppers 9 a.m. to 5 p.m. Mon. to Friday, Saturday 9 a.m. to 1 p.m.

**New! A TRULY REMARKABLE
BRITISH INVENTION!**

Gramdeck

GRAMOPHONE TAPE RECORDER

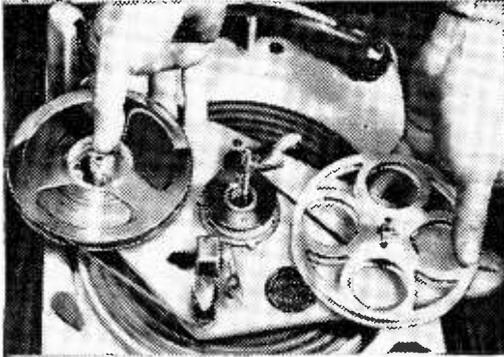

**Turns any gramophone into
a superb TAPE RECORDER!
and back into a record-player in a moment!**

- ★ Uses standard tapes.
- ★ Plays at 7 1/2 per sec. or 3 other speeds.
- ★ Records direct from radio or microphone.
- ★ Erase and fast rewind.

£13. 12s.

Special moving-coil microphone and tape extra.

EASY TERMS

Gramdeck is an ingenious invention that instantly turns your gramophone into a tape-recorder and back into a gramophone at will! You simply slip it on to your turntable and you are ready to record direct-from-radio or microphone... the voices of your family... radio programmes... your favourite music—and you can instantly play it back through your own gramophone or radio with *Lifelike Fidelity*. Made by the people who make radar instruments for Viscounts and Britannias, the amazing Gramdeck now brings full tape-recording facilities to every gramophone owner at little extra cost.

AS EASY AS PUTTING ON A RECORD
“Real hi-fi results.” “Better than many so-called hi-fi recorders...” These are typical comments of famous technical journals. Gramdeck enables any gramophone owner to add superbly good tape-recording facilities to existing equipment, at a fraction of the usual cost. Full details, photos, specifications, Easy Terms, etc., are given in the Gramdeck Book. Send for your FREE copy today.

Free!



FREE BOOK—POST NOW!

Please send me the Gramdeck Book—FREE and without obligation.

NAME

ADDRESS

Gramdeck

GRAMOPHONE TAPE RECORDER
(Dept. PA/804), 29-31, WRIGHT'S LANE, LONDON, W.8.

GRAMDECK TURNS A TURNTABLE INTO A TAPE RECORDER

**Get these
FREE
CIRCUITS
&
WIRING DIAGRAMS**

T.R.F. Circuits
Battery Circuits
Portable Circuits
Shet Circuits
Mains Circuits
Filter Circuits
F.M. Tuner

T.V. Converter Circuits, etc.
etc.

Send Postage 1/- (stamps)

OSMOR COILS are regularly used and recommended by designers writing in “Practical Wireless,” “Wireless World” and “Radio Constructor.” Why not follow the experts?

“Q Coils”
All ranges
Potted Coils
F.M. COILS
Speaker Cross-over Coils
Tape Coils
ROD AERIALS
Coils and I.F.s for Transistor Circuits
SUB-MINIATURE COILS
Midget I.F. Trans.
With ferrite cores



418 Brighton Road,
South Croydon.
Telephone: CRO 5148/9

SOLDERING EQUIPMENT

BY **LITESOLD**
1950 TRADE MARK

**PRECISION
SOLDERING
INSTRUMENTS
for the ELECTRONICS
INDUSTRY**

- Comprehensive range
- Robust & Reliable
- Light weight
- Rapid heating
- Bit sizes 3/32in. to 3/8in.
- ‘Permabit’ or Copper bits
- All voltage ranges 6/7v. to 230/250v.
- Prices from 19/6

Illustrated is the 25w. 3/16in. replaceable bit model with safety shield.


British and Foreign Patents. Registered designs. Suppliers to H.M. and Foreign Governments. Agents throughout the world.

Brochure No. S.10 sent free on request. Sole proprietors and manufacturers:

**LIGHT SOLDERING DEVELOPMENTS
LIMITED**

28, Sydenham Road, Croydon, Surrey.

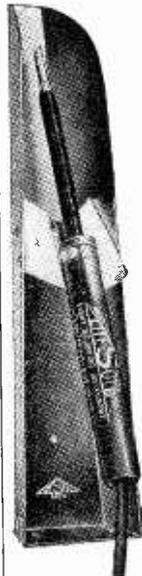Phone: CROydon 8589 Grams: Litesold Croydon



A.C. Pre-tuned Superhet

ALTERNATIVE SWITCHING FOR PRE-SET STATIONS

IN the A.C. Pre-Tuned Superhet (December, 1958, issue) a 5-pole 5-way switch was used. In some circumstances a simpler type of switch may be used instead.

Original Circuit

The original circuit is shown in Fig. 2 and is followed by I.F. detector and output stages of ordinary type. With the 5-pole switch in one position, the L.W. aerial and oscillator coils are in use, a pair of pre-sets tuning-in the 1,500m transmitter. For the other four positions, the M.W. coils are in circuit, four pairs of pre-sets furnishing four pre-tuned stations. In one position, a standard 2-gang condenser may be switched in, giving manual tuning.

New switches with this number of separate poles are quite expensive. Ex-service or surplus switches can be obtained from time to time, or made up by including separate switch wafers on a common spindle. A surplus switch with one wafer for each pole is easiest to use, but switches having two or more poles on each wafer are equally suitable. The number of "ways" is also unimportant, provided one position is available for each station. For example, a 3-way switch

would give pre-set tuning for three stations; alternatively, it could provide manual tuning, with two pre-selected stations.

M.W. Only

In some areas the Light Programme is satisfactorily received on the M.W. band. There is then no need to fit long-wave coils and a switch with only two poles is required, wired as shown in Fig. 2. Such switches can be readily obtained at low cost, as surplus, or purchased new.

A compact rotary switch suitable for this

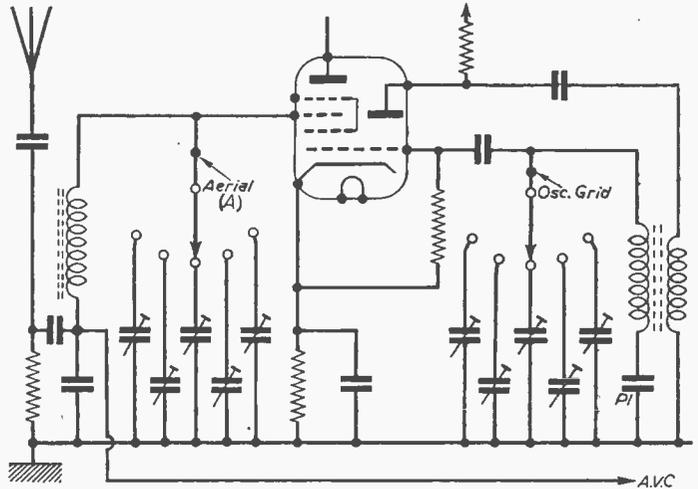


Fig. 1.—The new frequency changer circuit.

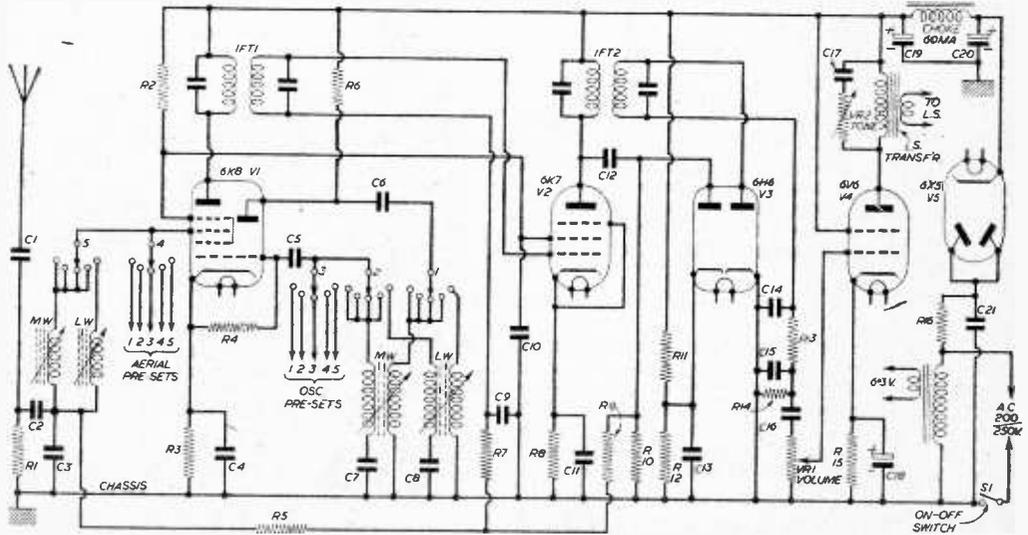


Fig. 2.—The original circuit of the receiver.

circuit is a 2-pole 9-way model. Wiring for this switch is given in Fig. 3. The extra tags may be left unused, or may be wired to further pairs of pre-sets, thereby giving more pre-selected stations. Or one set of tags may bring in the usual gang condenser for manual tuning, in addition to the pre-set stations. Because of its simplicity, the circuit in Fig. 1 is recommended when a long-wave range is not needed.

3-pole L.W. Working

With some modification to the circuit, a 3-pole, 6-way switch can provide one L.W. station, with up to five pre-set M.W. stations (or four, with manual tuning).

For this circuit, the aerial portion of the frequency changer is wired as in Fig. 1, two poles of the switch being used for this purpose. In the oscillator section, the M.W. oscillator coil is permanently wired, as in Fig. 2, but the padder, P1, is omitted. It is now possible to adjust one pre-set to 665kc/s, thereby giving reception of the 200kc/s (1.500m) transmitter, with the M.W. oscillator coil.

Efficiency will be a little reduced, compared with that achieved with a separate L.W. coil, but

will normally be good enough for adequate volume from the 1.500m Light Programme transmitter. If a manual tuning control is provided, the padder must be added in series with the gang condenser fixed plates. The oscillator coil core

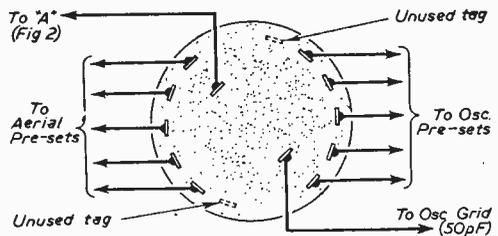


Fig. 3.—Wiring of the switch.

will need to be well in, to secure sufficient inductance and a 500pF trimmer will be necessary for the L.W. station. For other pre-set stations, in the M.W. band, rather low settings will be necessary, as all the trimmers have to be reduced in value to compensate for the loss of the oscillator coil padder. This can be done by removing one or more plates, if necessary.

NUVISTOR VALVES

THE constant attention of electronic engineers concerned with the design and manufacture of receiving valves is towards providing improved performance, quality and reliability, and with the advent and growth of the transistor the question of size is now of paramount importance.

From recent research work, RCA engineers have presented the "Nuvistor," which is now in the advanced stages of development. Many factors were considered in the design of the Nuvistor, including planar structures, cylindrical structures, metal-to-glass seals and metal-to-ceramic seals. For example, ease of assembly led to research in using planar tube elements, but any advantage to be gained by this was offset by disadvantages in electrical and thermal characteristics. In contrast, cylindrical tube elements offered electrical and thermal stability and efficiency, and at the same time could be easy and economical to manufacture. The new design employs concentric cylinders supported in an open-ended cantilever construction, together with a combination of new materials, processes and manufacturing techniques.

Construction

For ruggedness a strong ceramic base-wafer is used as a platform on which is erected an array of valve electrodes, each solidly held in place by a tripod-like structure. The electrodes are thus strongly supported in an open-ended cantilever construction. These electrodes are small, light cylinders which, because of their form and low mass, are able to withstand a high degree of shock or vibration.

There are no micas to fray under vibration or

to interfere with high-temperature exhaust processing of the tube. There is no glass to limit the processing temperature or to break under mechanical or thermal shock.

All joints in the valve are brazed together in one simple operation at high temperatures, and thus the parts are joined in a strain-free assembly. Because the valve elements are accurately secured in their original strain-free position, the possibility of shorts developing in the valve during operation is remote.

Comparison With Competitive Devices

Some of the more significant advantages of electron valves, and in particular the Nuvistor, over competitive devices can be summarised as follows:


1. In a valve the electrode spacing can be 50 times larger than the electrode spacing in a transistor intended for comparable performance. Valve spacings and the associated tolerances can, therefore, be more easily controlled in manufacturing operations.
2. The valve is economical in initial cost, has high impedance and gain, and generally requires less expensive associated circuit components.
3. At high frequencies the noise factor and the gain of the valve are superior.
4. The valve has a high uniformity of initial characteristics and does not require a costly selection process.
5. The valve is capable of handling momentary overloads.
6. The valve is inherently less susceptible to radiation damage.
7. Valves, and particularly the Nuvistor design, maintain their characteristics over a wide range of ambient temperatures.

HOME RADIO OF MITCHAM

(Dept. P), 187 LONDON ROAD, MITCHAM, SURREY. MIT 3282

Shop Hours: 9 a.m.—6.30 p.m. Wednesday 9 a.m.—1 p.m.

An Exciting Gift for any Youngster.

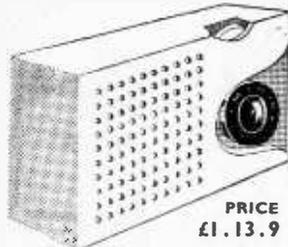


PRICE
£1.13.9

THE "KIDSET"

Ready built and tested. Crystal diode plus one transistor. Medium and long wavebands. Pen-light battery gives many months use. Permeability tuning and attractive case. For use with high-impedance phones or deaf-aid earpiece. Requires aerial and earth. PRICE £1.13.9, including battery and post. Headphones or ear-piece, 15/- extra.

"THE BEST WINTER HOBBY OF ALL"

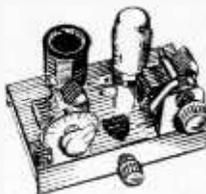


"GLOBE-KING"

SHORT-WAVE RADIO

Explore the world from your own fireside, news from America, music from Hawaii, sport from Australia, and all the amateurs in every corner. Real long-distance reception at minimum cost. Complete kit with three 'matched coils, £3.19.6. Send for leaflet and full details.

DULCI H3S STEREO-GRAM CHASSIS

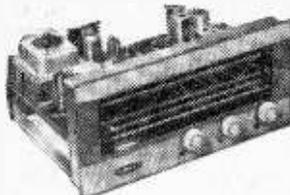

carriage. All other Dulci chassis and equipment in stock and

Long, medium, and FM/VHF radio plus incomparable reproduction of standard, long-playing, and stereophonic records. Simple and convenient to install into any cabinet and workmanship and materials of the highest standard. 8 valves, 8 watts output. PRICE

£27.16.6, plus 3/6 part

Latest Mullard Book

"DESIGNS FOR AUDIO AMPLIFIERS"

Every keen constructor should have a copy of this exciting new book on audio amplifiers. 136 pages on art paper with technical data and constructional plans for over twelve different designs, including amplifiers, pre-amplifiers, tape amplifiers and pre-amplifiers, 4 channel mixers, stereo pre-amps and amplifiers, A.C./D.C. amplifier, etc., etc. Keep up-to-date with audio design by having this reference book to hand always.

PRICE 8/6, plus 1/- post.

We can also supply all the parts to build these circuits including ready-punched chassis, ganged controls, Bulgin components, special switches, Elcom and Painton plugs and sockets. Detailed price lists 6d. for post.

"INSTANT" BULK TAPE ERASER



Enables a complete reel of magnetic recording tape to be erased of all traces of recorded matter in a few seconds. Eliminates background noise and leaves tape as new. Also can be used as a defluxer to remove residual magnetism in heads and give high quality recordings. Leaflet available.

PRICE 27/6, plus 1/6 post.

BARGAIN OFFER RECORDING TAPES

A fortunate purchase enables us to offer the following high quality recording tapes at below wholesale price while stocks last:—

LONG-PLAY TAPES

3in. 250ft., 7/-; 5in. 850ft., 19/6; 5 1/2in. 1,200ft., 25/-; 7in., 1,700ft., 32/6. Also 7in. 1,200ft. standard tape, 22/6. Please add 1/- post to order.

UNIVERSAL SOUND MIXER

An essential accessory for all Tape Recorders, audio amplifiers, cine sound equipment, etc. Permits controlled fading in or out of up to three separate signal sources. Laboratory designed and robustly built in attractive case with channels clearly marked. S.A.E. for leaflet.



PRICE £2.2.0, plus 1/- post.



JASON FM/VHF TUNER

Are you enjoying the crystal-tingling realism that is now available on FM/VHF. These high quality transmissions make ordinary radio sound like the old horn gramophone. The Jason kit is recognised as the finest home constructor design ever produced and the latest

version has greater sensitivity, sleek modern case and scale, and provision for built-in power supply if required. Don't put up with the crackles and whistles any longer. Send for full constructional data TODAY!

Data with price list, 2/9, post paid.

Set of parts with cabinet and including power unit components, £9.8.0, plus 1/- post.

PHILIPS AG2009

Transcription Player Unit

Without question this Philips record player represents the best value today in a transcription quality unit. Heavy accurately machined turntable ensures steady speed and freedom from rumble, flutter, or wow. 4 speed with additional variation on each speed. Hi-Fi crystal pick-up for standard and L.P. records. PRICE £10.10.0, plus 2/- post. Stereo plug-in head available, 30/- extra.



LINEAR L3/3 STEREO AMPLIFIER



Wonderful value and excellent results. Full twin channel stereo amplifier with 3 watts each channel. Volume, Tone, and Balance controls. 3 ohms output. S.A.E. for leaflet. PRICE £7.7.0, plus 2/6 carriage.

"SHORT-WAVE RECEIVERS FOR BEGINNERS"

This new book contains constructional data for six different simple receivers for battery and mains operation. PRICE 6/- post 9d

Still the most popular Hi-Fi speaker for either monaural or stereo equipment. The HF1012 Stentorian is a 10in. unit with die-cast chassis and has a level response from 30 to 14,000 cycles. Universal speech coil for 3, 7 1/2 and 15 ohms. PRICE DOWN TO £4.15.0, plus 2/- post.



WE ARE STOCKISTS OF ALL THE WELL-KNOWN JASON KITS FOR TUNERS, AMPLIFIERS, TRANSISTOR RECEIVERS, TEST GEAR, etc. Entirely British in design and material, they represent the finest value in constructional equipment today.

CADENZA CRYSTAL MICROPHONE

This is the most up-to-date and elegant crystal microphone on the market today. High quality Acos crystal insert housed in modern case complete with attractive desk stand and supplied with lead. PRICE £3.13.6, post 1/-. Leaflet on request. Also available crystal microphone inserts, 7/6, post 6d.


KINGSMERE SUPPLIES LIMITED

Insured Post 1/-, over £2 Free. (Export extra.)

MAIL ORDER HOUSE

TERMS: Remit with Order or C.O.D.

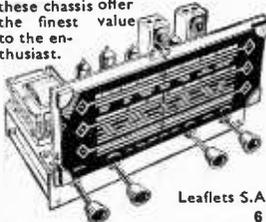Built to the highest specifications, these chassis offer the finest value to the enthusiasts.



Leafless S.A.E.

ALL BRITISH RADIOGRAM CHASSIS. 3 WAVEBANDS 5 MULLARD VALVES
ECH81, EF89, EBC81, EL84, EZ80
 Brand new and guar. A.C. 200/250 v. Short-Medium-Long-Gram. P.U. High Q dust core coils. Latest circuit technique. AVC and neg. feedback. 4 watts. Chassis size 13½ x 6 x 7in. high. Aligned and calibrated ready for use. **Quality at Low Cost.** Chassis isolated. H.P. Dep. £5 and five monthly of £1.

OUR PRICE £9-9-0

6 VALVE AM-FM MODEL £18-18-0

Matched Speakers, 5in., 6½in., 8in. 17/6 ea. 10in. 25/-.



The Artlessly Successful

BRAND NEW AND BOXED

OUR PRICE

£6-19-6

U.A.S. WORLD'S FINEST 4-SPEED AUTOCHANGER

IDEAL FOR USE WITH OUR CHASSIS H.P. Dep. £3.10.0 and four monthly of £1.

Stereo-monoaural model £1 extra

90-DAY GUARANTEE VALVES		ALL BRAND NEW	
6/6	7/6	1/6	5/6
5U4	6Q7G	954	155
6K8G	12AX7	EA50	1T4
6N7M	EF41	E1148	6K6GT
6V6G	EL41	6H6GT	807
6X5G	EL84	2/6	SP61
6AM6	EZ40	6K7G	6AC7M

SPECIAL PRICE PER SET

6K8G, 6K7G, 6Q7G, 6V6G, 6X5G ... 27/6

1R5, 1T4, 155, 3V4 or 354 ... 27/6

Matched Pairs 6V6G, 15/-, EL84, 17/6

Valve Boxes, All Sizes ... 2/- doz.

Carbon Pots, 5K to 2M, 2/6; DP, 4/-.

BSR 4-SPEED SINGLE PLAYER Model TU9. Our bargain price, 90/-.

Cut out board, 12½in. x 16½in., 5/-.

ALFA MULTIMETER

Pocket size 5½ x 3½ x 1½in.

300 microamp F.S.D. 3in. Scale.

17 Ranges. 3,330 ohms per volt.

A.C. Volts. 0 to 1,200 v. in 5 ranges.

D.C. Volts. 0 to 1,200 v. in 5 ranges.

D.C. Current. 0 to 300 m.a. in 3 ranges.

Resistance. 0 to 20 K and 0 to 2 meg.

Decibels. -20 to +23 db. and +20 to +37 db.

Complete with leads and prods. Uses

No. 8 battery. Fully Guaranteed.

REDUCED PRICE £5-19-6

FAMOUS MAKE LONG PLAY PLASTIC RECORDING TAPE

On universal fitting plastic spools, for all recorders single and double track. 50% extra play at standard prices. 7in. spool 1,700ft. tape, our price 35/- 5½ in. spool 1,200ft. tape, our price 28/- 5in. spool 850ft. tape, our price 21/- MSS 3in. spool 225ft. price 7/6

STANDARD PLASTIC TAPE

7in. spool 1,200ft. tape, 24/-

5in. spool 600ft. tape, 15/-

Satisfaction guaranteed or cash refunded.

FOAMCOURT WAYE, FERRING, WORTHING, SUSSEX

FIRST-CLASS RADIO COURSES ...

GET A CERTIFICATE!

QUALIFY AT HOME—IN SPARE TIME

After brief, intensely interesting study—undertaken at home in your spare time—**YOU** can secure your professional qualification. Prepare for **YOUR** share in the post-war boom in Radio. Let us show you how!

—FREE GUIDE—

The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success-compelling qualifications as **A.M.Brit.I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs, Exams., Gen. Cert. of Educ., London B.Sc. (Eng.), A. M. I. P. E., A.M.I.Mech.E., Draughtsmanship** (all branches) etc., together with particulars of our remarkable Guarantee of

SUCCESS OR NO FEE

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER 150,000 SUCCESSES.

NATIONAL INSTITUTE OF ENGINEERING
 (Dept. 461), 148, HOLBORN, LONDON, E.C.1.

S. Africa: P.O. Box 8417, Jo'burg.
 Australia: P.O. Box 4570, Melbourne

PRINTED CIRCUITS

This is a book on the "How-to-do-it" of printed circuits and miniature equipment and has been written especially for the radio ham. TV and radio service technicians, and garage and basement experimenter. Practical techniques and methods have been presented wherever possible.

By H. Moses.

23/-.

Postage 1/-.

MODEL RADIO-CONTROL. By

E. L. Safford. 21/-, Postage 1/-.

A BEGINNER'S GUIDE TO RADIO. By F. J. Camm. 7/6.

Postage 6d.

SERVICING TRANSISTOR RADIOS. By L. D'Airo. 23/-, Postage 1/-.

HOW TO GET THE BEST OUT OF YOUR TAPE RECORDER. By P. J. Guy. 8/6. Postage 8d.

RADIO VALVE DATA. 6th Edition. Compiled by "WW." 5/-, Postage 9d.

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS of British and American Technical Books

19-23 PRAED STREET, LONDON, W.2.

Complete catalogue 6d

Phone: PADDINGTON 4185.

Open 6 days 9-6 p.m.

THE PUNCH YOU NEED!

HOLE PUNCHES

One Minute Type

3/8" diameter	...	4/9 ea.
1/2" "	...	5/6 "

Screw-up Type

1/8" diameter	...	6/- ea.
3/8" " B7G	...	6/6 "
3/8" " B8A, B9A	...	7/- "
1/2" " "	...	7/3 "
1" " "	...	7/6 "

Postage and packing 1/-

1 1/16" diameter	...	8/- ea.
1 1/8" " Int. Octal	...	8/9 "
1 1/4" " "	...	10/- "
1 3/8" " "	...	11/3 "
1 1/2" " B9G...	...	12/6 "
2 3/32" " Meter	...	18/- "
2 1/16" " Meter	...	45/- "

Postage and packing 1/9

Oliver & Randall Ltd.

Dept. P.W.,

40, Perry Hill, London, S.E.6.

Tel.: FORest Hill 8424

Calculating Resistor Values

THE PROCEDURE EXPLAINED

By J. Golding

WHEN repairing or modifying a receiver it may be necessary to find resistor values to suit changed valves or conditions, or to replace damaged resistors with obliterated markings. Calculations of this kind usually prove to be quite straightforward, because when any two of the three terms voltage, current, or resistance are known, the remaining term can be found. To find a resistance value, the calculation is:

$$\text{Resistance} = \frac{\text{Voltage}}{\text{Current}}$$

When it is necessary to know what voltage is dropped by a resistor, the calculation is:

$$\text{Voltage} = \text{Current} \times \text{Resistance}$$

It may also be necessary to know what current flows in a circuit where voltage and resistance are known, and this can be found from the calculation:

$$\text{Current} = \frac{\text{Voltage}}{\text{Resistance}}$$

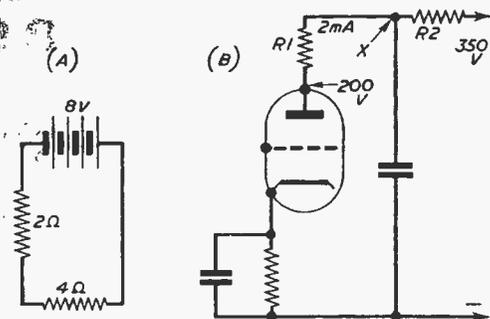


Fig. 2.—Circuits with resistors in series.

A few simple examples will show how these methods of calculating resistance, voltage and current are applied, and how circuits with more than one resistor can be dealt with.

Single Series Resistor

Fig. 1 shows a simple example, and a case which could arise if a small battery set were to be run from a 3V dry battery, instead of 2V accumulator.

At "A" voltage and resistance are known, so the current flowing can be found from

$$\frac{\text{Voltage}}{\text{Resistance}}$$

That is,

$$\frac{4}{2} = 2A$$

With "B" the valves are in parallel, and thus take .3 ampere. They require 2V, but the battery is 3V. R1 must therefore drop 1V. The resistance required is thus:

$$\frac{1}{0.3} = 3\frac{1}{3} \text{ ohms}$$

With any simple series resistor circuit this same calculation is used. That is:

$$\frac{\text{Voltage to be dropped}}{\text{Current flowing}} = \text{Resistance required.}$$

Resistors in Series

When resistors are in series, their values are added. At "A" in Fig. 2, the total resistance is 6 ohms.

$$\text{Current flowing} = \frac{8}{6} = 1\frac{1}{3}A$$

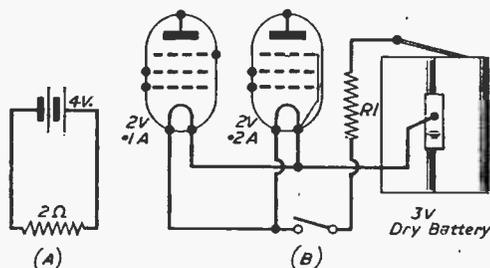


Fig. 1.—Series resistor circuits.

At "B" an audio-frequency triode is shown needing 200V at its anode and operated in such a way that 2mA anode current is taken. Assuming that R1 has to be 50k, because this is the optimum load for the valve, the decoupling and dropping resistor R2 has to be chosen so that the anode voltage is correct.

With small currents it is important to remember that

$$1A = 1,000mA$$

The voltage drop in R1 can then be found from

$$\text{Current} \times \text{Resistance} = \text{Voltage}$$

That is,

$$0.002 \times 50,000 = 100V$$

A potential of 300V will thus be needed at the point "X" so that 50V must be dropped in R2, which draws current from the 350V H.T. line.

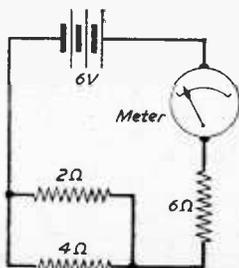


Fig. 3 (a).—Circuit involving resistors in series and in parallel.

The resistance required can be found from:

$$\frac{\text{Voltage}}{\text{Current}} = \frac{50}{0.002} = 25,000 \text{ ohms}$$

Series and Parallel

When resistors are in series, their values are simply added. But with two resistors in parallel, the value is shown by:

$$\text{Total resistance} = \frac{R1 \times R2}{R1 + R2}$$

It is thus easy to calculate the current which the meter at "A" in Fig. 3 would indicate. First,

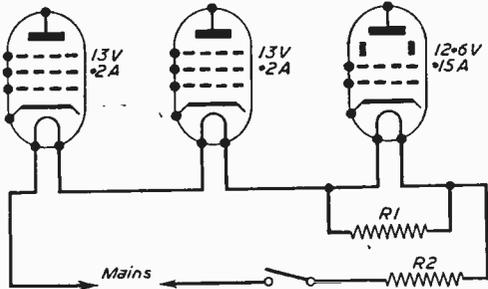


Fig. 3.—Valve circuit with resistors in series.

the overall value of 2 ohm and 4 ohm resistors in parallel will be:

$$\frac{2 \times 4}{2 + 4} = \frac{8}{6} = 1\frac{1}{3} \text{ ohm}$$

The 6 ohm resistor is in series, so the total resistance is $7\frac{1}{3}$ ohms.

$$\text{Current} = \frac{6}{7\frac{1}{3}} = \frac{6}{1} \div \frac{22}{3} = \frac{6}{1} \times \frac{3}{22} = \frac{9}{11} \text{ A.}$$

At "B" in Fig. 3 a 3-valve mains' receiver using two 13V 0.2A valves and one 12.6V 0.15A valve is to be run from 230/240V mains. R1 has to be of such a value that the heater of the 0.15A valve is not over-run. It will be seen that the circuit will be passing 0.2A but that only 0.15A must flow through the 12.6V valve. The surplus 0.05A must thus flow through R1. As 12.6V will be applied to this resistor, its value will be:

$$\frac{12.6}{0.05} = 252 \text{ ohms}$$

The mains dropper or line cord R2 can now be calculated. The three valves require 38.6V together. Taking this from 240V shows that 201.4V must be dropped in R2. R2 therefore equals:

$$\frac{201.4}{0.2} = 1007 \text{ ohms}$$

In practice, a 1000 ohm 0.2A dropper would be suitable for 230/250V mains.

Potential Dividers

When the current flowing is stable, a lower voltage can be obtained by using a series resistor, as already explained. But if the current is subjected to fluctuation a potential divider will furnish a more stable source of voltage. In Fig. 4, 100V will be required for the screen grid of an automatic volume controlled stage with a nominal S.G. current of approximately 2mA. Assuming that R1 and R2, in parallel with the

H.T. supply, must not pass more than 10mA, in order that a small safety margin shall exist, the value of R1 can easily be found, since

$$\text{Resistance} = \frac{\text{Voltage}}{\text{Current}}$$

$$R1 = \frac{100}{0.01} = 10,000 \text{ ohms}$$

In the case of R2, the 2mA S.G. current must be added to the 10mA flowing through R1, and R2 must drop 150V at 12mA.

$$R2 = \frac{150}{0.012} = 12,500 \text{ ohms}$$

As the current consumption equals the current through R2, and is 12mA, this is well within the 15mA maximum which could be drawn from the H.T. circuit without overloading.

At "B" in Fig. 4 it is assumed that an "all dry" receiver taking 10mA at 90V is to be run from a power pack normally supplying 240V at 40mA. R3 can thus pass 30mA. Its value is

$$\frac{90}{0.03} = 3,000 \text{ ohms}$$

R4 must drop 240-90, or 150V, with 40mA flowing. It is thus

$$\frac{150}{0.04} = 3,750 \text{ ohms}$$

When calculating a resistor value it is nearly always possible to deal with one resistor at a time, as indicated, and this greatly simplifies

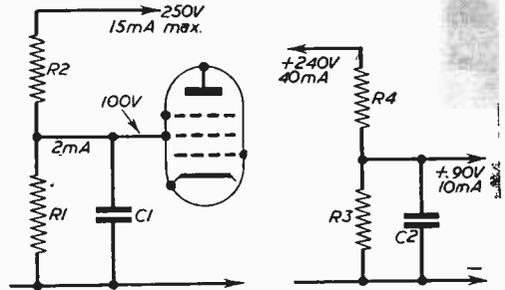


Fig. 4.—Potential divider circuits.

working. If there are two or more resistors, or different currents in various parts of the circuit, as in Figs. 3 and 4, the same solution can be reached by various methods.

When moderately high currents or fairly large voltages are encountered, the minimum resistor wattage should be calculated.

$$\text{Wattage} = \text{Voltage} \times \text{Current}$$


The wattage can be found easily, and the rating of the resistor should be equal to this; or larger. In practice, it is usual to select a resistor of standard value and ample rating. Referring to Fig. 4

- for R1: $100 \times .01 = 1\text{W}$,
- for R2: $150 \times .012 = 1.8\text{W}$,
- so a 2W resistor could be used,
- for R3: $90 \times 0.03 = 2.7\text{W}$,
- so a 3W resistor could be fitted,
- for R4: $150 \times 0.04 = 6\text{W}$

For long periods of running, or when ventilation is not very good, the resistors can best be of generous size. For example, a 5W component could be used for R3, and a 8W resistor for R4.

LEARN Train at home in your spare time
RADIO & T.V. SERVICING
 this new, easy, practical way!

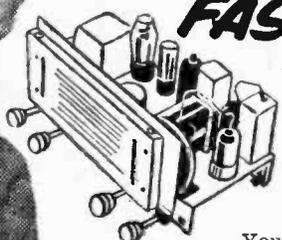
**YOUR OWN... BUSINESS...
 CAREER... OR
 FASCINATING HOBBY**



*Electronics is rapidly becoming a great new industry with far reaching applications into every field of modern activity.
 You can learn all the essentials of this new science at home in your spare time and turn your knowledge to good purpose!
 Now is your chance to set up your own business and be your own boss!*

**RADIOSTRUCTOR EQUIPMENT COURSES
 MAKE LEARNING SO SIMPLE**

You learn by building actual equipment with the big kits of components and parts which we send you. You advance by simple steps using high quality equipment and performing a whole series of interesting and instructive experiments—there are no complicated mathematics! Instruction manuals and our teaching staff employ the latest techniques for showing clearly how radio works in a practical and interesting manner; in fact, you really have fun whilst learning! And you end by possessing a first-rate piece of home equipment with the full knowledge of how it operates, and how to maintain it afterwards. In fact, for those wanting help with their radio career training, to set up their own full or part-time servicing business, or the hobbyist, this new and instructional system is exactly what is needed, and it can be provided at very moderate cost with payments available. Post the coupon now, for full details. There is no obligation of any kind.

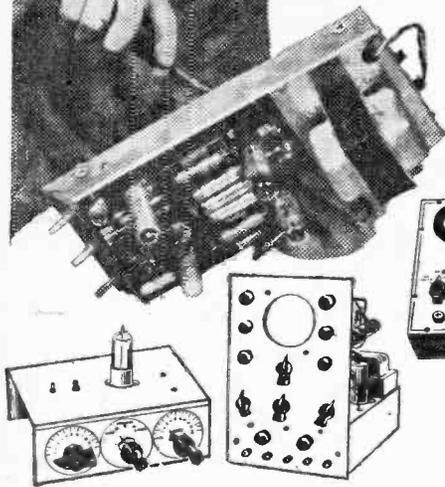

- NO MATHEMATICS
- EASY TERMS AVAILABLE
- ALL TEST EQUIPMENT SUPPLIED
- PERSONAL TUITION
- FINEST EQUIPMENT

POST TODAY FOR FREE brochure

To RADIOSTRUCTOR (Dept. G82)
 46 MARKET PLACE, READING, BERKS.
 Please send Brochure without obligation to:

Name _____

Address _____

BLOCK
 CAPS
 PLEASE

(827) We do not employ representatives 1-60



RADIOSTRUCTOR

BRITAIN'S LEADING RADIO TRAINING ORGANISATION

Crystal Receiver and Amplifier

A CONSTRUCTIONAL ARTICLE INTENDED FOR THE BEGINNER
By James Saunders

FROM the circuit diagram (Fig. 1) it will be seen that there are two diodes, one in the earth lead and the other in the aerial lead, so that there is full-wave rectification of the radio frequencies. The diodes are of the inexpensive type sold for a shilling or so as no considerable difference was noticed when better quality diodes were tried. These diodes should both be connected the same way round, that is with the red end away from the coils.

Notice the 0.0003 μ F fixed condenser across the variable condensers; this couples the two tuned

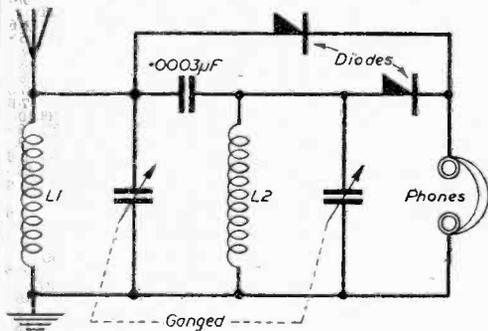


Fig. 2.—The circuit redrawn to show the capacitive coupling between L1 and L2.

circuits together and so improves selectivity. Fig. 2 is the same circuit drawn another way and shows this more clearly.

Coils

The coils are wound on 1 $\frac{1}{4}$ in. formers, 3 $\frac{1}{2}$ in. long, using 94 turns of No. 24s.w.g. enamelled wire. If cardboard formers are used they must be varnished before the coils are wound.

Begin the construction with the baseboard. The components can be held in place with $\frac{1}{2}$ in. woodscrews. So that the screws holding the coils can be reached, holes large enough for a slim screwdriver are made at each end of the coil. Stick a piece of insulation tape on the tuning condenser before fixing in the coil L1 to prevent the coil touching. Also, stick some thin paper on this coil to prevent the back of the set from chafing the winding.

Layout

When all the components are screwed in place, solder the leads to their connections as shown in

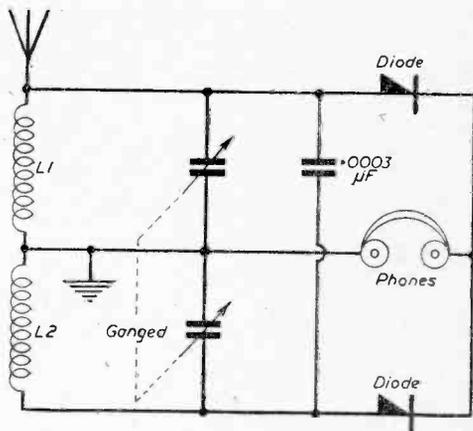


Fig. 1.—The circuit diagram.

the layout diagram (Fig. 3). If you are unused to making soldered joints, then a word about it may not be out of place here.

Use a multi-cored solder as this contains several cores of flux so there is no need to apply a flux to the joint. But make sure the components are clean. The solder and the iron should be applied simultaneously. Do not melt the solder on to the iron and then carry it to the joint—the proper way is to apply the solder to the component, then place the bit on top so that the solder is fused to the joint. This way, you can make a tidy join using the minimum amount of solder.

Cabinet

For the cabinet, ordinary deal is strong enough, but for a really strong job $\frac{1}{2}$ in. oak would be best. The back and front are cut from $\frac{1}{2}$ in. hardboard. To find the right position for the hole through which the condenser spindle protrudes, put a small drop of ink on the end of the spindle then line up the front panel with the cabinet and press it lightly against the spindle. The ink will

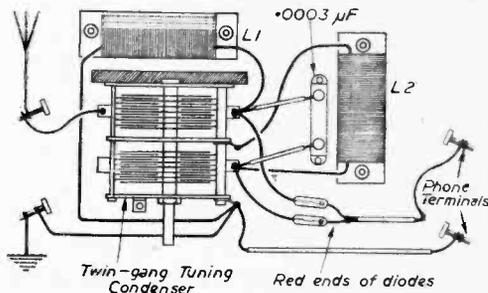


Fig. 3.—Wiring diagram.

leave a mark enabling a $\frac{1}{4}$ in. hole to be bored in the right position. Either $\frac{1}{2}$ in. woodscrews or panel pins may be used to hold the cabinet together.

A good finish can be obtained by sandpapering the wood to a smooth surface then varnishing. I used some passe-partout (sold at 1s. 3d. for a

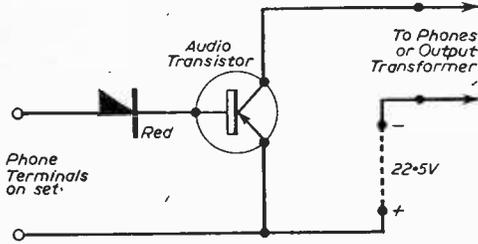


Fig. 4.—The circuit of the transistor amplifier.

fair-sized roll). This was stuck to the top and sides and given a coat of varnish. To finish off, the whole cabinet should be given two or three coats of varnish. Before varnishing the back and front, rub in linseed oil which helps to preserve

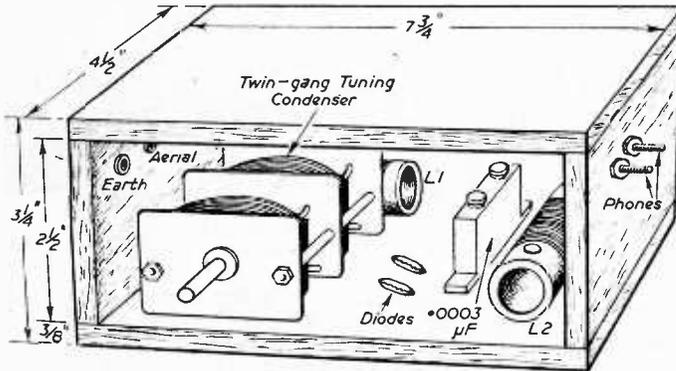


Fig. 6.—Layout of the parts.

the material, cleans away any natural oils, and helps the varnish to take more easily.

Amplifier

If the set is to operate a loudspeaker, then a single transistor will provide ample volume for bedside listening. The circuit for a small amplifier is shown in Fig. 4 and the diode in series with the base is to replace the earphones in the crystal circuit—without it the tuning is so affected that stations spread right across the tuning range.

The amplifier is so small that it can be housed

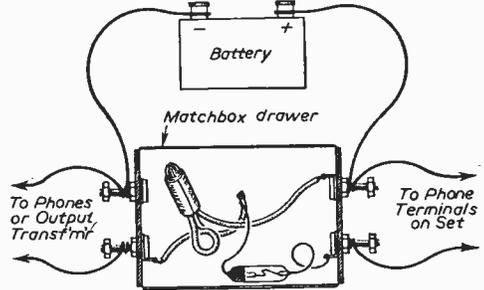


Fig. 5.—Wiring the amplifier.

in a matchbox which may be covered with passe-partout the same as the cabinet.

An audio transistor is required here, such as an XFT2 (Hivac) or a yellow/green spot. To protect the leads of the transistor so that they will not snap off, obtain a length of flex and push each lead into about 1 1/2 in. of the wire, as shown in Fig. 5; then wind a piece of insulation tape close to the transistor to hold the wires together.

If a layer-type hearing aid battery is used it can be attached to the matchbox with elastic bands. There is only one soldered connection in the amplifier where the diode joins the base of the transistor but when applying the solder make the joint quickly because too much heat can damage both the diode and the transistor.

Aerial

The higher the aerial, the more effective will it be. Adding a few feet to the height is as good as adding another valve or transistor to the set. But where it is impracticable to erect an outside aerial, a length of wire can be stretched out in a loft. This set will give good results with an indoor aerial provided the wire is kept clear of the walls and is about 50ft. long.

Aerial wire for use out of doors is mostly sold with a strong protective covering to guard against the harmful effects of rain and snow, etc., but for an indoor aerial either cotton-covered or enamelled wire will suffice provided a fairly stout gauge of wire is used, say, 22 to 26s.w.g. In a bedroom an aerial wound round the window frame gives a good reception and in some cases will be found to be more selective than an outside aerial.

Earth

A good earth is as essential as a good aerial so try to keep the lead-in as short as possible. The wire can be taken to a cold water pipe—or to a metal stake, about two feet long, driven into the earth if the room overlooks a garden. If it is impossible to obtain a good earth without using

(Continued on page 785)


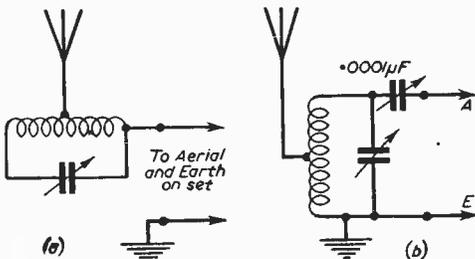


Fig. 7(a and b).—Two methods of improving selectivity.

Touch-down!

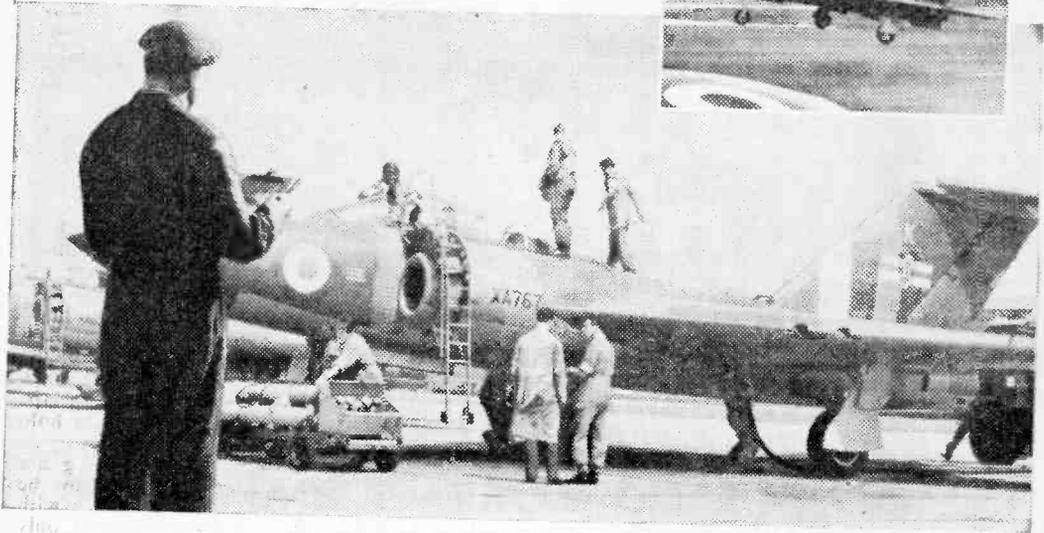

7 minutes to go!

Their sortie completed—two Javelins return—only two aircraft—only four men—but it takes a large team of technicians to get them back into the air without delay.

A Javelin's ground crew works at top speed. They can rearm and refuel the aircraft and have it back on the runway fully serviced in seven minutes. Here, the Master Radar Station takes over. Once again a technical team . . . air operations staff, teleprinter operators, radar specialists. In the R.A.F., every man counts.

You'll get more out of life in the

R.A.F.

The R.A.F. will train you for a key post and a planned career in electronics, radio, radar or one of many other trades. For full details, post this coupon today.

To: Royal Air Force Central Recruiting Office (PW18),
Victory House, Kingsway, London WC2

NAME DATE OF BIRTH

STATE TRADE PREFERENCE

ADDRESS



AS PART OF THEIR SERVICING, re-charged batteries are hoisted into the Javelin's fuselage. These provide a reserve source of electric power.




IN SEVEN MINUTES, two more Javelins are ready on the runway. From the Control Tower, it's . . . 'All clear for take-off'.

WEYRAD

COILS AND TRANSFORMERS FOR A 2-WAVE TRANSISTOR SUPERHET WITH PRINTED CIRCUIT AND FERRITE ROD AERIAL

LONG AND MEDIUM WAVE AERIAL—RA2W
 On 6in. rod, 7/16in. diameter, flying lead connections, 208 pF tuning 12/6
 OSCILLATOR COIL—P50/1AC
 Medium wave in screening can. For 176 pF tuning condenser 5/4
 1st AND 2nd I.F. TRANSFORMERS—P50/2CC
 470 Kc/s operation with 250 pF tuning in cans. 11/16in. diameter by 3/4in. high 5/7
 3rd I.F. TRANSFORMER—P50/3CC
 Last stage transformer to feed diode detector. Size as P50/2 6/-
 DRIVER TRANSFORMER—LFDT2
 Upright mounting with six connecting tags—1 1/8 in. x 3/8 in. x 1 1/4 in. 9/6

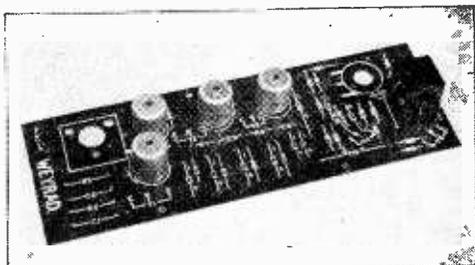

PRINTED CIRCUIT—PCAI


Size 2 3/4 in. x 8 1/2 in. Ready drilled and printed with component positions 9/6

THESE COMPONENTS ARE APPROVED BY TRANSISTOR MAKERS AND PERFORMANCE IS GUARANTEED.

Constructor's Booklet with full details, 2/-.

WEYMOUTH RADIO MANUFACTURING CO., LTD.
 CRESCENT STREET, WEYMOUTH, DORSET

BUILD YOUR OWN

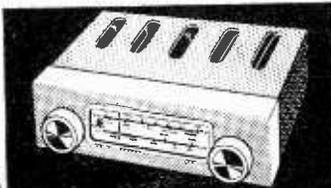

MAYKIT TRANSISTORISED CAR RADIO

- EASY TO BUILD ON PRINTED CIRCUIT.
- 5-VALVE SUPERHET WITH TRANSISTOR.
- STANDARD 7 x 2" for 12 VOLT BATTERY.

First tested Do-it-Yourself Car Radio, acclaimed by the Press. Uses low voltage valves and printed circuit. Negligible "fade," no buzz, only 1.5 amp. consumption. Complete with full instructions, diagrams, etc. Servicing and free advice on request. Also Jason Car Radios. Send 3/6 for Car Radio booklet.

Can be built for **£13.10.0** plus 5/- post./ins. and pack. Cash with order or BUY-AS-YOU-BUILD details and leaflet.

Dept. N., **MAYRA ELECTRONICS LTD.**
 118 Brighton Rd., Purley, Surrey. Tel. : EYW 1263.

GOVERNMENT SURPLUS AND MANUFACTURERS CLEARANCE

METERS, 500-0-500 Microamp. 3 1/2 in. dia. 37/6 ea. Dual Range 0-5 v. 0-100 v. FSD 1 m/a. 20/- ea. 0-1 m/a 2 1/2 in. dia. 20/-
 I.T.A. AERIALS. New 3 element 22/6. 5 element 27/6
 CO-AX CABLE 6d. yd. AIR SPACED 9d. DIPLEXERS 12/-
 GERMAN MIDDLES 1/- 10/- doz. TRANSISTORS from 6/-
 VOLUME CONTROLS. Long Spindle Midget. 10 K-2 Meg. Less Switch. 3/- D.P. switch 4/6
 CONDENSERS. Twin Gang .0005 Standard 5/6. Midget 6/6
 VENER SYN. MTRS. 200/250 v. with gear train driving. 5 dials, 110-1,000 hrs. 25/- ea.
 REL. RECS. 12 v. 1 amp. 5/- 2 amp. 11/6. 4 amp. 15/- 500 v. 1 amp. containing 30/35 m.m. discs. 10/- ea.
 12 WAY P.V.C. Cable. Screened & P.V.C. cov. 2/6 vd.
 ELECTROLYTICS. Canned. 20+20 mid. 450 v. 2/6 ea. 25/- doz.
 VAR. SLIDERS. 10 ohm 30 w. for chargers, trains. 3/- ea.
 FERRITE Rod Aerials. Med. & Long Wave. 10/- ea.
 CONNECTING WIRE. P.V.C. 100 ft. 2/6. various cols.
 373 I.F. Strip. NEW. with valves. 9.72 m.c/s.. £2.
 REPLAYS. Large stocks. assorted sizes, from 2/6 ea.
 MICROPHONES. Carbon 5/6. Inserts 2/6. Tammy 7/- Throat 4/6. Buttons 2/- Trans. 4/6. Acos. Crv. 33/1 28/6.

VALVES TESTED ON MULLARDS ELECTRONIC TESTER.

1L4	5/-	6D2	6/-	6X3	7/-	EA50	1/6	EY51	5/-
1T4	6/6	6E1	7/6	6X5	7/-	EABC80		EY51	8/-
1U4	6/-	6E6	7/-	8D2	4/6			P61	4/-
324	6/-	6F13	7/6	9D2	5/-	EB41	7/6	PEN45	7/6
34A	9/-	6J5	6/-	10F1	7/6	EB91	5/6	PEN46	7/-
4D1	4/-	6J6	6/-	12A6	7/8	ECH42	3/-	SP41	4/-
6AG5	5/-	6J7	6/-	12AH8	8/-	ECL80	9/-	SP61	4/-
6AL5	5/-	6K7	4/6	12AT7	6/-	EF36	5/-	VR150/30	
6AM5	5/-	6L6	6/6	12AU7	7/-	EF37	9/-	UL84	5/-
6AM6	6/-	6SA7	6/-	12AX7	7/-	EF39	5/6	VC97	9/-
6AQ5	6/-	6SC7	4/6	12BH7	10/-	EF50	3/6		
6AY6	7/-	6SK7	5/-	12SH7	5/-	EF50	5/-		
6BE6	3/-	6SK7	5/-	12SJ7	6/6	EF80	3/-		15/-
6BH6	5/6	6SL7	6/-	12SK7	5/-	EF91	6/-	VC138A	25/-
6BD6	5/6	6SN7	7/-	15D2	6/-	EF92	7/-	VC139A	25/-
6DW6	6/6	6U5	6/6	50C5	10/-	EL32	5/-		
6C4	5/-	6V6	6/6	807	6/-	EL91	5/6		

SECONDHAND VALVES. YOUR CHOICE £1.0.0 for EIGHT. ECL80. 6C4. 6AM6. 6AG5. 6J6. EF50. 6BE6. 3A4. EF80. SP61. P61. 6E6. P30. P32. 7Z7. 6AL5. 6K7. 6SJ7. EL32. EF42. 6D2. 20P1. 6F13. SP41. EY51. EB91. EF91. EF39.

HUGGETT'S LIMITED

2-4 PAWSONS ROAD, WEST CROYDON

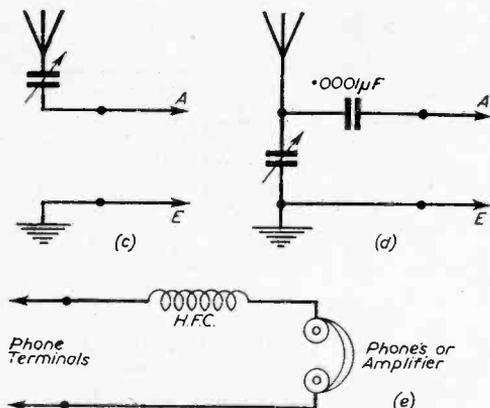


Fig. 7(c, d and e).—Three more circuit modifications.

a long wire try attaching the wire to the springs of a bed for this can be quite effective.

Should the selectivity be poor, then there are a few methods you can try with the crystal set to prevent the stations overlapping each other. Fig. 7(a) shows a wave-trap which is much used by some constructors to tune out a station that

persists in crowding out all other stations. The coil for this is a medium-wave coil wound the same as the coils in the set, that is, 94 turns on 1½ in. diameter former. The coil is tapped half-way down as this further increases the selectivity. In Fig. 7 (b) another tuned circuit is connected across the aerial and earth terminals with a 0.0001μF preset condenser to couple the circuit to the tuned circuits in the set. You could go on adding tuned circuits, but with too much selectivity the quality of reproduction is so affected that voices and music sound tinny.

Series Condenser

Sometimes a simple arrangement, such as a variable or preset condenser in series with the aerial Fig. 7(c) will be effective. An arrangement that is particularly good when the aerial is about 50 to 53ft. long is as in Fig. 7(d) where the aerial, earth and 0.0005μF variable condenser are treated as a tuned circuit. Another method is to put an H.F. choke in series with the phones (Fig. 7 (e)).

However, constructors will most probably find the set will bring in enough stations for comfortable listening without any outside attachments.

If the amplifier is intended to be a permanent part of the set, it can be fixed inside the cabinet over the coil, L2.

A QUALITY V.H.F./F.M. RECEIVER

(Continued from page 763)

each section will generally provide sufficient capacity.

Layout

No attempt should be made at neat and tidy lay-out, the aim being to make all connections as short and direct as possible without regard to appearance, especially in the "hot" parts of the circuit.

As a precaution against I.F. harmonic feedback along the heater line, decoupling is provided at V1 and V2 and the heater supply, one side of which should be earthed, is fed in at both ends of the tuner, so that there is no direct connection between V2 and V3.

Alignment

Alignment instructions will now be given for the benefit of those readers who wish to build the tuner only. If the complete receiver is being built, alignment should be deferred until it is complete.

The ideal method requires the use of a frequency-modulated signal generator and an oscilloscope. Those fortunate enough to possess these instruments will be well acquainted with their use and no more need be said about this method. Equally good results can be obtained with a little care, using an amplitude modulated generator and a value voltmeter or a high resistance multimeter (20,000ΩV for preference). It is also possible to align this receiver satisfactorily without any instruments at all, especially if pre-tuned I.F. transformers are used.

If instruments are available, connect the meter on the 10V D.C. range between points X and Y

on the circuit diagram and inject an unmodulated signal at 10.7Mc/s at V4 grid. Adjust the primary of the detector transformer (top core) for maximum reading. If no response can be obtained, try injecting the signal at V3 grid. Next, with injection at V3 grid, adjust both cores of the second I.F. transformer, reducing the output of the signal generator progressively so that the meter reading does not exceed about 5 volts. Transfer the generator to the grid of V2 and adjust the cores of the first I.F. transformer. Now connect the meter between earth and point Z and adjust the bottom core of the detector transformer for zero reading. The acceptance bandwidth of the tuner should now be checked by moving the generator slowly over the range 10.4 to 11Mc/s. The meter should indicate a maximum voltage at about 10.6, zero at 10.7 and a reverse maximum at 10.8. The two maxima should be of equal magnitude and equidistant from the zero. Since the various adjustments are to a certain extent inter-dependent, it is now advisable to repeat the whole operation as a check.

The tuner should now be connected to an audio amplifier and an amplitude modulated signal at 10.7Mc/s injected into the grid of V4 at sufficient strength to be heard in the speaker. VR1 is then adjusted for minimum response. This adjustment will probably affect the bottom core of the detector transformer which should be re-adjusted.

Connect an aerial and if the tuning capacity is about right, transmissions will be heard somewhere in the first 90 deg. of rotation of the tuning condenser. Stations will also probably be heard at near minimum capacity, but the lower oscillator frequency is the one to be used and the rotation of the condenser should be limited by suitable stops to restrict tuning to the desired range.

(To be continued)

Club News

REPORTS OF CURRENT ACTIVITIES

BRADFORD AMATEUR RADIO SOCIETY

Cambridge House, 66, Little Horton Lane, Bradford 5.
Hon. Sec.: D. M. Pratt (G3KEP), "Glenluce," Lyndale Road, Eldwick, Bingley, Yorkshire.

THREE very interesting lectures have been given recently: on September 8th J. Davidson (G3JKD) gave a lecture with numerous practical demonstrations on "Television Tuners and Printed Circuitry." This was followed on the 22nd by H. D. Kitchen's lecture on "The Interpretation of Valve Data," and on October 20th M. Firth (G3MMK) lectured on the "K.W. Vanguard Transmitter and Z-match Tuner." The annual Mullard film meeting was held at St. George's Hall on October 6th.

Copies of the new syllabus are available from the secretary and except where otherwise stated meetings are held at 7.30 p.m. Morse classes are held by arrangement before meetings to which all interested in radio and television are invited. Transport arrangement for visits, etc., are made at the meeting prior to each visit.

Future events:

December 8th.—Annual social evening at the Mechanics' Institute Cafe.
December 29th.—Film show.

1960

January 12th.—"Colour Photography," by A. R. Baily, M.Sc. (G3IBN).
January 26th.—Display of members' gear.
February 9th.—"Inexpensive Sound Fidelity," by G. M. Pratt (G3KEP).

THE BRITISH INSTITUTION OF RADIO ENGINEERS

9, Bedford Square, London, W.C.1.

Meetings for December, 1959

London Section.—Meetings are held at the London School of Hygiene and Tropical Medicine, Keppel Street, Gower Street, W.C.1.

December 10th at 6.30 p.m.—Computer group meeting. "The Simulation of Nuclear Reactors and Power Plants," by W. J. G. Cox and J. Dowsing.

December 15th at 3 p.m. and 6 p.m.—Half-day symposium on "Magnetic Recording Techniques."

"Magnetic Recording Heads."—M. B. Martin.
"Some Engineering Aspects of Magnetic Tape System Design."—D. W. Willis and P. Skinner.
"Magnetic Head Whose Output Signal is Independent of Tape Speed over a Wide Range."—D. Kerr and E. J. M. Quirk.
"Assessment of Reliability of Magnetic Tape for Data Processing."—R. Noble, B.Sc.

"Instrumentation Magnetic Recording."—Dr. P. E. Axon, O.B.E.

"A Fast Start/Stop Magnetic Tape Transport Mechanism."—W. C. R. Withers.

"The Development of a High Performance Tape Handler."—H. M. Harrison.

"Data Recording in Nuclear Instrumentation."—F. H. Wells.
December 16th at 6.30 p.m.—Medical electronics group meeting.
"Measurements in the Presence of Noise," by Dr. D. A. Bell, M.A., and Dr. G. D. Dawson.

Birmingham, West Midland Section.—Meetings are held at the Matthew Boulton Technical College, Suffolk Street.

December 8th at 7.15 p.m.—"The Development of High Frequency Tape Recording," by P. J. Guy.

Bristol, South-western Section.—Meetings are held at the School of Management Studies, Unity Street.

December 17th at 7 p.m.—"The Transistor and its Use in Communication and Control Equipment," by E. Wolfendale, B.Sc.

Edinburgh, Scottish Section.—Meetings are held at the Department of Natural Philosophy, The University, Drummond Street.

December 18th at 7 p.m.—"The Digital Voltmeter," by J. A. Irvine and D. A. Pucknell.

Glasgow, Scottish Section.—Meetings are held at the Institution of Engineers and Shipbuilders, 39, Elmbank Crescent.

December 17th at 7 p.m.—"The Digital Voltmeter," by J. A. Irvine and D. A. Pucknell.

Manchester, North-western Section.—Meetings are held at Reynolds Hall, College of Technology, Sackville Street.

December 10th at 6.30 p.m.—"Learning Machines," by P. Huggins (associate member).

Newcastle-upon-Tyne, North-eastern Section.—Meetings are held at the Institution of Mining and Mechanical Engineers, Neville Hall, Westgate Rd.

December 9th at 6 p.m.—"Micro Miniaturisation," by H. G. Manfield.

MIDLAND AMATEUR RADIO SOCIETY

The Birmingham Midland Institute, Paradise Street, Birmingham.
Hon. Sec.: Mr. C. Haycock (G3JDJ).

FUTURE events:

December 15th, at 7 p.m.—"Do and be done by night". An auction for the benefit of the Society when all members bring their "spare" components and items for disposal.

1960

January 7th at 7 p.m.—Talk by Mr. Ron Rew on construction of a complete 70 cm. Transmitter.

January 19th, at 7 p.m.—Talk by Mr. H. Buckley, of Bradmac. The talk will probably be on high quality recording and reproduction.

February 16th, at 7 p.m.—Talk by Mr. R. Roberts of the BBC on "1 SW in 50 countries."

DERBY AND DISTRICT AMATEUR RADIO SOCIETY

Room No. 4, 119, Green Lane, Derby.
Hon. Sec.: F. C. Ward (G2CVV), 5, Uplands Avenue, Littleover, Derby.

Future events:

December 9th at 7.30 p.m.—Open evening in sub-basement rooms.

December 11th at 7.30 p.m.—Christmas party.

December 16th at 7.30 p.m.—Electronic gadgets for amusement from the junk box.

December 23rd and 30th.—Club rooms closed. Top band net will operate Christmas Eve and New Year's Eve for exchange of greetings.

1960:

January 6th at 7.30 p.m.—Open evening: collection of 1960 subscriptions. Seniors 5s. Juniors 2s. 6d.

RAVENSBOROUGH AMATEUR RADIO CLUB

Hon. Sec.: J. Wilshaw (G3MPX), 4, Station Road, Bromley, Kent.

CLUB meetings at Downham have been cancelled and it is proposed to hold monthly meetings elsewhere. Details can be obtained from the Secretary. The club transmitter (G3HEV) will still be active in contests and field days.

READING AMATEUR RADIO CLUB

Hon. Sec.: R. J. Nash (G3EJA), "Peacehaven" 9, Holybrook Road, Reading, Berkshire.

THE October meeting was well attended when G3DXJ concluded his lectures on "SSB for the Ham." A party of members went along to the Newbury Hamfest and had a good time. The November meeting was held at 7 p.m. at Palmer Hall, West Street, Reading, when a talk was given on aials. A junk sale and rag chew followed.

All subscriptions become due on January 1st, 1960, and it is hoped that those members who do not attend the December meeting will send their subscriptions to the treasurer G3GKH.

We are finishing the year 1959 in a much stronger position; membership has trebled and attendance at meetings has increased both of which give encouragement for the future.

Future event:

December 19th.—"Home-built communication receivers." This talk will be given by G3LLK and based on the receiver which he has recently constructed and should be of great interest to those short wave listeners about to embark on similar subjects.

December 19th.—"Home-built communication receivers."

This talk will be given by G3LLK and based on the receiver which he has recently constructed and should be of great interest to those short wave listeners about to embark on similar subjects.

December 19th.—"Home-built communication receivers."

This talk will be given by G3LLK and based on the receiver which he has recently constructed and should be of great interest to those short wave listeners about to embark on similar subjects.

December 19th.—"Home-built communication receivers."

This talk will be given by G3LLK and based on the receiver which he has recently constructed and should be of great interest to those short wave listeners about to embark on similar subjects.

December 19th.—"Home-built communication receivers."

This talk will be given by G3LLK and based on the receiver which he has recently constructed and should be of great interest to those short wave listeners about to embark on similar subjects.

December 19th.—"Home-built communication receivers."

This talk will be given by G3LLK and based on the receiver which he has recently constructed and should be of great interest to those short wave listeners about to embark on similar subjects.

December 19th.—"Home-built communication receivers."

This talk will be given by G3LLK and based on the receiver which he has recently constructed and should be of great interest to those short wave listeners about to embark on similar subjects.

December 19th.—"Home-built communication receivers."

This talk will be given by G3LLK and based on the receiver which he has recently constructed and should be of great interest to those short wave listeners about to embark on similar subjects.

December 19th.—"Home-built communication receivers."

This talk will be given by G3LLK and based on the receiver which he has recently constructed and should be of great interest to those short wave listeners about to embark on similar subjects.

December 19th.—"Home-built communication receivers."

This talk will be given by G3LLK and based on the receiver which he has recently constructed and should be of great interest to those short wave listeners about to embark on similar subjects.

Catalogue Received

Home Radio (Mitcham) Ltd.

THE 1960 edition of Home Radio's catalogue is now available from them price 2/-. This catalogue consists of 127 pages of information and is of great interest to all radio enthusiasts. It is produced on art paper and contains a three-page index and a page of useful formulae. Many of the items in the catalogue are depicted by half-tone illustrations. The catalogue lists almost every component on the market and contains a handy bookmark with a list of abbreviations used throughout the catalogue. When sending to Home Radio for the catalogue please enclose 9d. in stamps for postage and packing.

C.R.T. ISOLATION TRANSFORMERS
 TYPE A. OPTIONAL 25% and 50% BOOST.
 5 V. OR 4 V. OR 6.3 V. OR 10.8 V. OR
 13.3 V. 12/6. MAINS INPUT.
 OUR LATEST SUPERIOR PRODUCT
 TYPE A2. HIGH QUALITY, LOW CAPACITY.
 10.15 PF. OPTIMUM BOOST 25%, 50%,
 75%. 16/8 EACH. MAINS INPUT.
 TYPE B. MAINS INPUT. MULTI OUTPUT 2.
 4, 6.3, 7.5, 10 AND 13 VOLTS. BOOST 25%
 AND 50%. LOW CAPACITY. 21/-.

TRIMMERS. Ceramic. 30, 50, 70 p.f., 94, 100 p.f.,
 150 p.f., 1/2; 250 p.f., 1/8; 500 p.f., 750 p.f., 1/9.
RESISTORS. Preferred values. 10 ohms to 10 meg.
 1/4 w., 4d.; 1/2 w., 4d.; 1 w., 6d.; 1 1/2 w., 8d.; 2 w., 1/-
HIGH STABILITY. 1/2 w., 1% 2/-, Preferred values.
 100 Ω to 10 meg. Dkto. 5%, 100 Ω to 5 meg. 1/2 9d.
3 watt WIRE-WOUND RESISTORS 1/3
 10 watt 25 ohms-10,000 ohms 1/6
 15 watt 15,000 ohms-50,000 ohms 5 w., 1/9; 10 w., 2/3.

GEVAERT GEVASOR
 Long play plastic tape. 1,700 ft. 7in. reel. 75/-;
 850ft. 5in. reel, 21/-; M.8.S. 220ft. 3in. reel. 3/6.
SUPERIOR 1,200 ft. Plastic Tape on 7" Plastic
Reels 24/-. 600ft. 5in. reel, 15/- Long play
 7,200 ft. 5in. reel, 28/-.
SPARE REELS. ALL SIZES. 3/-.


"Instant" Bulk Tape Eraser and Head De-
 tuser. 200/250 v. A.C., 27/6. Leaflet, S.A.E.
O.P. TRANSFORMERS. Heavy Duty 30 mA., 4/6.
 Multitrate, push-pull, 7/6. Miniature. 384, etc., 4/6.
L.F. CHOKES 15/10 H. 60/65 mA., 5/-; 10 H.
 85 mA., 10/6; 10 H. 150 mA., 14/-.

MAINS TRANSFORMERS 200/250 v. A.C.
STANDARD. 250-0-250, 80 mA. 6.3 v. 3.5 a.
 tapped 4 v., 4 a. Rectifier 0.3 v., 1 a. 5 v.
 2 v. or 4 v. 2 a. d.k. 0.350-0.350 22/8
MINIATURE. 200 v. 20 mA. 6.3 v. 1 a. 10/6
MIDGET. 220 v. 45 mA., 6.3 v. 2 a. 15/6
SMALL. 250-0-250, 100 mA. 6.3 v. 3.5 a. 19/6
STANDARD. 250-0-250, 65 mA., 6.3 v.
 3.5 a. 17/6
HEATER TRANS. 6.3 v. 14 amp. 17/6
 Ditto, tapped sec. 2, 4, 6.3 v., 11 amp. 8/6
 Ditto, sec. 6.3 v. 3 amp. 10/6

ALADDIN FORMERS and core. 4in., 8in., 10d.,
 3in. FORMERS 5937/8 and Caps TV12, 3in. sq. x
 2 1/2in. and 3in. sq. x 1 1/2in. 2/- ea., with cores.
TYANA. -Midget Soldering Iron, 230 v. 40 w., 16/9.
REMPLOY Instrument Iron, 230 v. 25 w., 17/8.
MAINS DROPPERS. 3in. x 1 1/2in. 4d. 4diders.
 8.5 amp., 750 ohms, 4/3. 0.2 amp., 1,000 ohms, 4/3.
LIME CORD. 3 amp., 60 ohms per foot, 2 amp., 100
 ohms per foot, 3-way, 6d. per foot, 3-way, 7d. per ft.
LOUDSPEAKER P.M. 3 OHM. 5in. Rols. 17/8.
 5in. Plessey, 19/6. 6in. x 3in. Rols. 26/-, 4in. Rols.
 18/8. 8 x 3in., 21/- x 6in., 27/6. 10in. Rols. 30/-
 15" Tweeter, 25/-, 12in. R.A. 30/-.
SENTORIAN HF1012 10in. 3 to 15mhz 10 w., 95/-.
 15in. Baker 15 watt, 3 ohms, 0.15 ohms, 105/-.
12in. BAKER FOAM SUSPENSION 11 ohm, 8/8.
CRYSTAL DIODE G.E.C., 2/-. GEX34, 4/-.
HIGH RESISTANCE PHONES. 4,000 ohms, 16/8 per
 pair. **MIKE TRANSF.** 50:1, 3/8 ea., 100:1, Potted, 10/6.
SWITCH CLEANER. Fluid squirt atomizer, 3/6 p.f.
TWIN GANG TUNING CONDENSER 4/3 tin.
 miniature 1in. x 1 1/2in., 10/-, .0005 Standard
 with trimmers, 9/-; less trimmers, 8/-; midget, 7/6.
SINGLE. 50 pF., 2/6; 80 pF., 100 pF., 160 pF., 7/-.
 solid dielectric 100, 200, 500 pF., 3/6.
SPEAKER FREE. OLD CLOTH. 17in. x 25in., 5/-.
 25in. x 35in., 10/-, Tyxan 4d. 6in. wide, 10/-; 2 1/2in.
 3in. wide, 5/- ft. SAMPLES S.A.E.

New and Boxed VALVES 90-day Guarantee.

1R5	8/6	6K8G	8/6	EABC80	10/6	HABC80	
1R5	8/6	6L6G	10/6		10/6		10/6
1T4	8/6	6N7M	7/6	EB91	8/6	HV20A	7/6
3X2	3/6	6Q7G	10/6	ECB3	8/6	MU14	7/6
3X4	8/6	6X5	7/6	EB41	10/6		8/6
3V4	8/6	6S7M	10/6	EP80	10/6	PCCR4	8/6
5U1	8/6	6S7N	8/6	EC84	12/6	PCP80	11/6
5Y3	8/6	6V6G	7/6	ECF90	11/6	PCL82	10/6
5Z4	10/6	6X4	7/6	ECH42	10/6	PEN35	8/6
6AM6	8/6	6X5	7/6	EC82	12/6	PL2	10/6
6B8	5/6	12AT7	9/6	EP39	7/6	PY80	8/6
6BE6	7/6	12AU7	9/6	EP41	10/6	PY81	10/6
6BE6	10/6	12AX7	9/6	EP50	5/6	PY82	8/6
6BW6	10/6	12BE6	10/6	EP80	10/6	SP61	5/6
6D4	7/6	12CT7	8/6	EC41	10/6	UC41	10/6
6PG6	7/6	12Q7	8/6	EP92	5/6	UC42	10/6
6HG	3/6	35L6	9/6	EF12	5/6	UF41	10/6
6J5	6/6	35Z4	8/6	EL84	10/6	UL41	10/6
6J6	7/6	80	10/6	EM81	12/6	UY41	8/6
6J7G	8/6	12X7	8/6	EC40	8/6	UZ22	10/6
6K6GT	6/6	854	1/6	EZ80	8/6	VR105	8/6
6K7G	5/6	EAS0	1/6	EL148	1/6	VR150	8/6

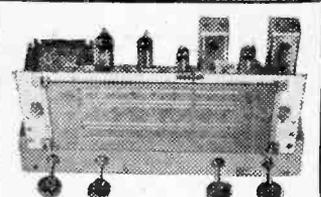

1960 RADIOGRAM CHASSIS
THREE WAVEBANDS. FIVE VALVES
 N.W. 16 in.-50 m. LATEST MULLARD
 M.W. 200 m.-550 m. EBH1, EP80, EB381,
 L.W. 800 m.-2,000 m. EL94, EZ80,
 12-month guarantee.
 A.C. 200/250 v. 4-way Switch; Short-Medium-
 Long-Range. A.V.C. and Negative feedback
 4.2 watts. Chassis 12 1/2 x 5 1/2 x 2 1/2in. Glass shield
 horizontal or vertical size 10in. x 4in.
 Aligned and calibrated. Isolated Chassis.

£9.10.0 Carr. & Ins. 4/6.
 TERMS: Dep. £5.5.6 and five monthly of £1.
MATCHED SPEAKERS FOR ABOVE CHASSIS.
 5in., 17/8; 10in., 25/-; 12in., 30/-

NEW AM-FM MODEL
 6 Valves **£18.19.6** Leaflet, S.A.E.



£6.19.6 *World's Best Sound Assurance*
 TERMS: Dep. £3.10.0 and four monthly of £1.
 Stereo Model U48 £7.19.6; UA12 £10.10.0.

COLLARO LATEST MODEL
HIGH-FIDELITY AUTOCHANGER
4-SPEEDS-10 RECORDS
 With Studio "O" pick-up
BRAND NEW IN MAKER'S BOXES
OUR PRICE £7.19.6 post free.

BUILD THIS REPRODUCER
BARGAIN SINGLE PLAYER KIT
 Ready for immediate assembly.
 4-speed Collaro "Junior" Unit £4 12 6
 Handmade case, 17 1/2 x 13 1/2 x 7 1/2in. £2 5 0
 With room to play 12in. records £2 5 0
 Ready-built 3-watt amplifier with
 two valves and loudspeaker £3 12 6
or £9.15.0 complete kit post free.

STEREO E.M.I 4-SPEED SINGLE RECORD
PLAYER. Acos 73 hi-fi stereo and normal vital
 pick-up. Silent motor heavy turntable.
 Special Offer £8.18.6. Post 3/6.

ALUMINIUM CHASSIS. 18 s.w.g. unshielded.
 With 4 sides, riveted corners and lattice fixing
 holes. 2 1/2in. sides, 7 x 4in., 4/8; 5 x 7in., 5/8;
 11 x 7in., 6/8; 13 x 9in., 8/6; 14 x 11in., 10/6;
 15 x 14in., 12/6; 18 x 16 x 5in., 16/6.

TRANSISTORS, GENUINE EDISWAN
 R.F. 4 Mc/s, 18/-; 2 Mc/s, 15/-, Audio, 10/-.
 Complete data sheets supplied.

CRYSTAL MIKE INSERT by Acos, precision
 engineered. Size only 1in. x 3/16in., 6/8.

HI-GAIN BAND 3 I.T.A. PRE-AMP KIT.
 Cascode circuit with valve EC84. Price 22/6.
 With Power Pack, 49/6. Plans only 6d.
 Band 1 B.B.C. version same prices.

BBC TRANSISTOR RADIO. M. & L. valve.
 Complete kit 32/6, phones 7/6 extra. Deaf Aid
 Earpiece 12/8. Special Lead 2/6. Details 6d.

GARRARD 45P. SINGLE PLAYER
AUDIO PERFECTION

Designed to play 16, 33, 45, 78 r.p.m. Records
 7in., 10in., 12in. Lightweight Xtal pick-up.
 GC2 turnover head, two separate sapphire styl.
OUR PRICE £7.10.0 each. Post Free
 Model TA Mk II £8-10-0. Model 4HF 218-0-0.
 With Plug-in Normal Heads.
 (Stereo heads £2 extra). Leaflets, S.A.E.

Volume Controls 80 ohm COAX
 Long spindles. Guaranteed 1 year. Midget
 5K ohms to 2 Meg. No Sw. D.P.S. 8.
 3/- 4/9
 Linear or Log Tracks. Air Spaced. 1/- yd.

COAX PLUGS 1/- LEAD SOCKET 2/-
PANEL SOCKETS 1/- OUTLET BOXES. 4/6
BALANCED TWIN FEEDER yd. 6d. 80 or 300 ohms.
DITTO SCREENED yd. 1/6. 80 ohms only.
WIRE-WOUND POTS, 3 WATT. Pre-set Min.
 T.V. Type. All values 25 ohms to 25 K. 3/- ea.
 30 K, 50 K, 4/- (Carbon 30 K, 2 to meg., 3/-).
WIRE-WOUND 4 WATT Pots. Long Spindle.
 Values, 100 ohms to 50 K. 6/6; 100 K, 7/6.
CONDENSERS. New Stock. .001 mid. 7 kV.
 T.C.C. 5/6; Ditto, 20 kV., 9/6; .1mf. 7 kV., 9/6;
 Tubular 500 v. .001 to .05 mf., 9d.; 1.1/-, 25, 1/6;
 5/350 v., 1/9; 1.350 v., 9d.; 1/1000 v., 1/9
 10/2,000 v., 1/9; .1mf., 2,000 volts, 3/6.
CERAMIC COND. 500 v., 3 pf. to .01 mf., 9d.
SILVER MICA CONDENSERS. 10% 5 pf. to 500
 pf., 1/-; 600 pf. to 3,000 pf., 1/3. Close tolerance
 (± 1 p.f.) 1.5 p.f. to 47 p.f., 1/6. Ditto 1% 50 p.f.
 to 815 p.f., 1/9; 1,000 p.f. to 6,000 p.f., 2/-.

I.F. TRANSFORMERS 7/6 pair.
 465 Kcs Sing Tuning Miniature Can, 2 1/2in. x
 1in. x 1in. E3H Q and good bandwidth.
 By Pye Radio. Data sheet supplied.
 Wearite M800 I.F. 465 Kcs, 12/6 per pair.
 Wearite 550 I.F. 465 Kcs, 12/6 per pair.

NEW ELECTROLYTICS. FAMOUS MAKES

TUBULAR	TUBULAR	CAN TYPES	
1/350v. 2/3	64/300v. 5/8	8/500v. 3/-	
2/450v. 2/3	100/25v. 2/-	16/500v. 4/-	
2/450v. 2/3	250/25v. 2/6	32/350v. 4/6	
8/450v. 2/3	500/12v. 2/6	100/270v. 5/6	
8/500v. 2/9	8-8/450v. 4/6	250/35v. 4/6	
18/450v. 3/6	8-8/500v. 5/-	32+32/350v. 4/6	
18/500v. 4/6	8-16/450v. 5/-	32+32/450v. 6/6	
22/25v. 1/9	8-16/500v. 5/6	50+50/350v. 7/6	
50/25v. 2/-	16+16/450v. 5/6	64+120/350v. 11/6	
50/50v. 2/-	32+32/350v. 4/6	100+200/270v. 12/6	

SELENIUM RECTIFIER. 300 v. 85 mA., 7/6.
CONTACT COOLED 250 v. 50 mA., 7/6; 60 mA., 8/6;
 85 mA., 9/8; 200 mA., 21/-; 300 mA., 27/6.
COILS Wearite "P" type, 3/- each. Osmor Midget
 2" type adj. dist. type 4/-, 4" P. R.F. with reaction, 3/6.
TELETRON L & M. P. R.F. with reaction, 3/6.
FERRITE ROD AERIALS. M.W. 8/9; M. L. 12/6.
T.R.F. COILS A.H.F. 7/- pair. H.F. CHOKES, 2/6.
FERRITE ROD. Tin x 3/8in. dia., 2/6.

JASON F.M. TUNER COIL SET. 26/-, H.F.
 coil, aerial coil, Oscillator coil, 20 I.F. Irons
 10.7 Mc/s. Ratio Detector and better choice.
 Circuit book using 40AM6, 2/6.
COMPLETE JASON F.M. KIT WITH VALVES.
 £6.15.0. Fringe area kit, 22/8 extra.

FULL WAVE BRIDGE SELENIUM RECTIFIERS -
 2, 6 or 12 v. 1 1/2 amp. 8/8; 2 a., 11/2; 4 a., 17/6.
CHARGER TRANSFORMERS. Tapped input 200/
 250 v. for charging at 2, 6 or 12 v., 1 1/2 amp., 15/6.
 2" type, 17/6; 4" type, 22/8. Circuit included.

VALVE and T.V. TUBE equivalent books, 9/6.
TOGGLE SWITCHES. S.P. 2/-, D.P. 3/6. D.T. 4/-.
WAVECRANE SWITCHES
 5 p. 4-way 2 waffer long spindle 6/8
 2 p. 3-way, or 3 p. 2-way short spindle 2/6
 2 p. 6-way, 4 p. 2-way, 4 p. 3-way long spindle 3/6
 3 p. 4-way, or 1 p. 12-way long spindle 3/6
VALVEHOUSES. Pax. Int. Oct., 4d. EP50, EA50,
 6d. B12A, CRT. 1/3. Rmc. and Amer. 4, 5, 6, and
 7 pin. 1/2. Moulded MAZDA and Int. Oct., 6d.
 BTG. BBA, BSG, B9A, 9d. B7G with can., 1/8.
 B9A with can., 1/8. CERAMIC EF50, B7G, B9A,
 Int. Oct., 1/8. 8-Caus. B7G, B1A, 1/8.
COSSOR MAINS-BATTERY POWER PACK 90 v.
 R.D. 1 1/2 v. L.T. Same size as BATTERY B126
 and RD 35. List 65/-, our price 59/6.

NEW! TAYLORMETER Model 127A

20,000 o.p.v. POCKET SIZE!

Performance equal to a high priced instrument

OUTSTANDING FEATURES:

- ★ Sensitivity 20,000 o.p.v. D.C. 1,000 o.p.v. A.C.
- ★ 20 Ranges.
- ★ D.C. Current 50 μ A, to 1 Amp.
- ★ D.C. Volts 0.3 v. to 1,000 v. (25 kV by probe).
- ★ A.C. Volts 10 v. to 1,000 v.
- ★ 3 Resistance Ranges from 0-20 megohms (self-contained).
- ★ Meter 40 μ A 3 $\frac{1}{2}$ " arc. Accuracy D.C. 3%, A.C. 4%, Ohms 5%.
- ★ Dimensions 5 $\frac{1}{2}$ " x 3 $\frac{1}{2}$ " x 1 $\frac{1}{2}$ ".
- ★ Weight 140z.


Price: £10.0.0

Credit Sale Terms available
9 monthly instalments of
£1.4.4.

Complete with Instruction Manual
and interchangeable test
prods and clips.
High quality leather case, if required,
£1.12.0.
H.V. Probe for 25 kV £4.15.0.

Write for full details
and catalogue.

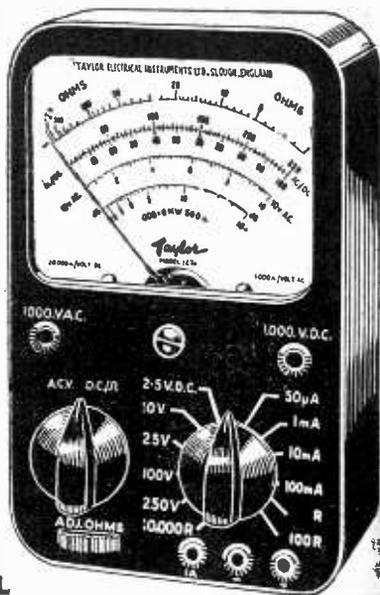**TAYLOR ELECTRICAL
INSTRUMENTS LIMITED**
MONTROSE AVENUE, SLOUGH, BUCKS.



Telephone: Slough 21381-7
Cables: Taylins, Slough.



AMPLIFIER IN CABINET



82/6
(3/- P. & P.)

Beautifully finished wood cabinet with "gold" and brown dividing strip and "gold" finished fabric front. Size 13" x 7 $\frac{3}{4}$ " front to back 4 $\frac{1}{2}$ ". 5" P.M. speaker. ECL82 valve with metal rectifier. Vol. tone, on-off. 82/6 (3/- p. & p.). Cabinet only 20/-, plus 2/- post.

COILPACK



I.F. 465-470 kc/s.; complete with two-gang tuner; fully aligned and tested.

Type 1. For 41M-120M, and 16-49 M. Price 20/-.
Type 2. For 25-75 M. and 200-550 M. (22/6.) BOTH POST PAID

COMPLETE V.H.F./A.M. RADIO FOR £12.12.



Brand new set, in superb walnut cabinet (size 19" x 8 $\frac{1}{2}$ " x 14 $\frac{1}{2}$ " high). Covering 80-100 Mc/s, 16-49 M., 200-500 M. and 1,200-2,000 M. Mains trans. 200-250 v. with 3 tapings. Ferrite rod aerial for A.M. Controls: volume on/off, tone, tuning, w/change. Gram and ext. speaker position provided. Fully

guaranteed. Post and packing 10/- extra. Terms: £3.12.0 down (inc. carr.) and 5 monthly payments of £2. Indoor V.H.F. aerial 10/- extra, cash.

UNIC SHAVERS LTD.,
25, Wordsworth Road, Worthing, Sussex.

REPANCO

HIGH GAIN TRANSISTOR COMPONENT

Ferrite Slab Aerial Type FS3. Medium Wave only. With fixing grommets. Size 3in. x 3in. x 5/32in., 7/6.

Long Wave Loading Coil for the FS3 Type XL1. 3/6.

Oscillator Coil Type X08 for 176 pF gang. Ferrite core. Size 3in. sq. x 11/16in., 5/-.
Oscillator Coil Type X015 for 365 pF gang. Ferrite core. Size 3in. sq. x 11/16in., 5/-.

I.F. Transformer Type XT6. Suitable for 1st and 2nd I.F. 455 Kc/s. Size 3in. sq. x 11/16in. 10/-.

I.F. Transformer Type XT7. Designed for 3rd I.F.T. or detector I.F.T. 455 Kc/s. Size as XT6, 10/-.

Push Pull Interstage Transformer Type TT9. Ratio 1 : 1 C.T. Radiometal Core. Size 3in. x 3in. x 13/32in., 12/6.

Push Pull Output Transformer Type TT10. Ratio 8 : 1 C.T. Matched to 3 ohm speaker. Size as TT9, 12/6.

Practical and Theoretical circuits enclosed with each Repanco Transistor Component.

REPANCO EASY-TO-BUILD RECEIVERS

Mini-7. 7 Transistor pocket receiver. Size 53in. x 33in. x 11/16in. Long and medium wave Envelope, 1/6.

Major-7. New Portable 7 transistor receiver. 9in. x 7in. x 4in. Long and medium wave. Envelope, 1/6.

Car Radio Receiver. 7 transistors. Long and medium wave. 2 watt output. R.F. stage. A.G.C. and auxiliary A.G.C. circuits. 12 volt or 6 volt. Envelope, 2/-.

Mail Order and Trade:
**RADIO EXPERIMENTAL
PRODUCTS, LTD.**
33 Much Park St.
COVENTRY
Tel.: 62572



Wholesale Enquiries and Export:
REPANCO, LTD.
O'Brien's Buildings,
203-269 Foleshill Rd.,
COVENTRY
Tel.: 40594

NEWS FROM THE TRADE

LATEST DEVELOPMENTS
IN RECEIVERS AND
COMPONENTS

TAPE DECK

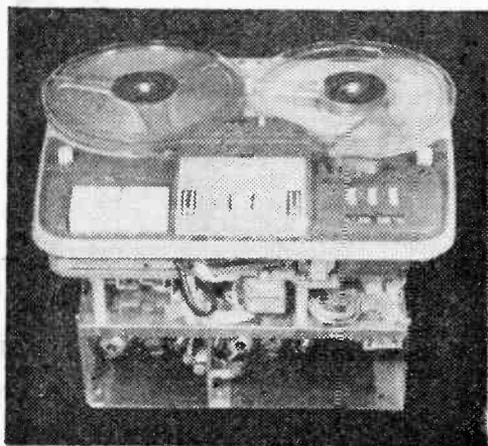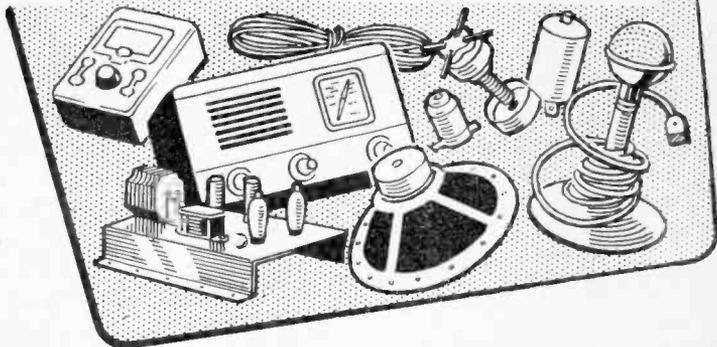THE TM 60, the tape deck of the TK 60 stereophonic and monophonic tape recorder released by Grundig (Great Britain) Limited is now available. The deck itself is identical with that of the TK 60 and contains the whole electronic equipment of the TK 60



The Grundig TM60 tape-deck.

other than power amplifiers and speakers. A separate box attached to the main unit by a connecting lead contains three sockets for microphone inputs. Although designed primarily for use with the Grundig Gainsborough Radiogram, the TM 60 can be used with any good amplifier or stereo amplifier, radio or radiogram. The price, including 1,800ft. of long play tape, is 90 guineas.

NEW KITS

IT is announced by Daystrom Ltd., of Gloucester, that a direct reading capacitor meter and an electronic switch for oscilloscopes are to be added to their range of "Heathkits." The capacitor meter which weighs 7lb. has four ranges with full scale deflections of a 100pF, 1,000pF, 0.01 μ F and 0.1 μ F. The unit is powered from 200-250V A.C. mains and has an accuracy of 1


per cent. on the 100 and 1,000pF ranges and 2 per cent. on the 0.01 and 0.1 μ F ranges. The unit is approximately 7in. \times 5in. \times 4in.

The oscilloscope trace doubler has switching rates of approximately 150, 500, 1,500, 5,000 and 15,000c/s and the frequency response is \pm 1dB over the range 0-100kc/s. The valves used are two ECC83s, three ECC82s, one EC90 and one EZ81. The unit weighs 8lb and is approximately 9 $\frac{1}{2}$ in. \times 6 $\frac{1}{2}$ in. \times 5in.

Further details can be obtained from Daystrom Ltd., Glevum Hall, Southgate Street, Gloucester.

STEREOPHONIC AMPLIFIERS

AFTER a period of more than a year during which many improvements have been incorporated in the Whiteley stereophonic amplifiers, the WB Stentorian equipment now covers the wide range of apparatus suitable for stereophonic sound reproduction. The Whiteley stereophonic amplifier consists of two sections, a control unit and the power amplifier. The control unit has provision for radio and tape input as well as for crystal and low output magnetic pick-ups. Full bass and treble controls are provided together

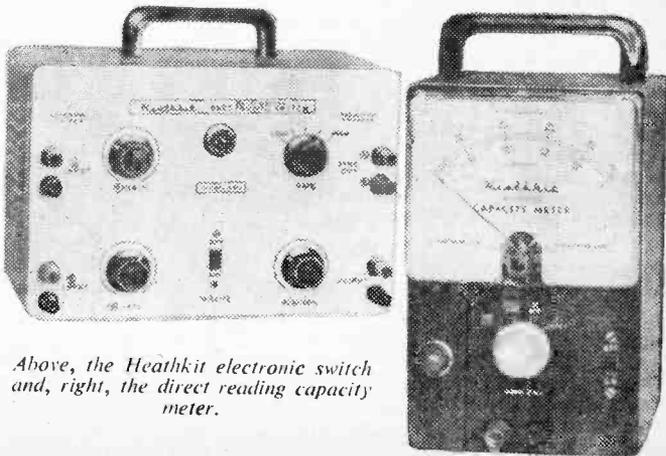

Above, the Heathkit electronic switch and, right, the direct reading capacity meter.


with a balance control and a stereo/mono-phonetic switch. The unit may be used in conjunction with two W.B.12 main amplifiers or with a single W.B. stereophonic power amplifier. This consists of two 8W output channels and a common power supply mounted on a single chassis. A low value of distortion is obtained and the two units form a compact medium power high quality system suitable for most domestic requirements.

DULCI PRODUCTS

IN announcing that they have taken over the Dulci Company, Messrs. Lee Products (Gt. Britain) Ltd. add still further to the range of products they manufacture and distribute throughout the radio and electrical industries. It is understood that the Dulci factory at Willesden, N.W. London, is included in the deal and it is the new owner's intention to continue to produce existing Dulci lines. Furthermore, plans are well advanced for extending and improving the range, at the same time maintaining the very high standards of design and manufacture so closely associated with the products of both companies.

CATALOGUE

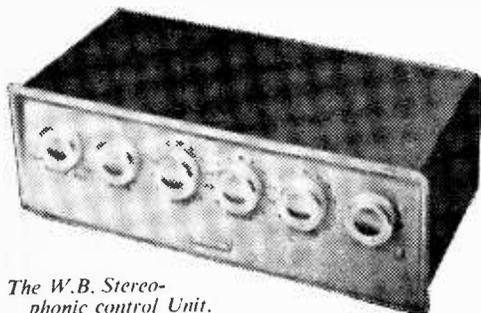A NEW catalogue entitled "Hi-Fi, Stereo and Tape Recorder" is now available from City Sale and Exchange Ltd., 93-4, Fleet Street,




*The W.B. Stereo-
phonic control Unit.*

London, E.C.4. This catalogue includes all the latest type of hi-fidelity equipment which many people are having built into their own fixtures at home. With stereo to-day these units can be very compact and will not take up a lot of room. The catalogue includes details of most of the latest recorders, business dictating machines, tuners, tape decks, etc., found on the market to-day. A copy of this may be obtained free from the above firm. When writing, please send in stamps for necessary postage.

PRICE REDUCTION

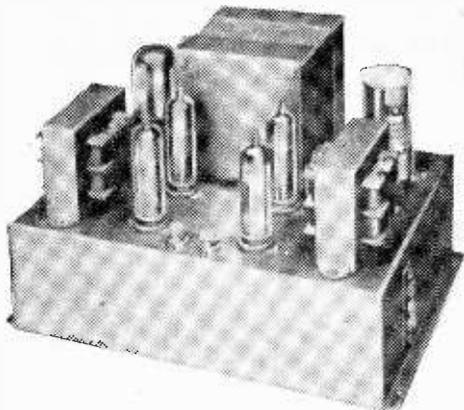OWING to the increasing demand for the "Thoroughbred" tape recorder manufactured by Winston Electronics Limited, Shepperton, Middlesex, it has been reduced in price from 69 guineas to 59 guineas. The de luxe model of the "Thoroughbred" is also being reduced in price from 79 guineas to 69 guineas. The prices include the microphone and 1,800ft. of tape.



The W.B.8S Stereophonic power amplifier.

CHOOSING CAPACITORS

(Continued from page 764)

Mica Condensers

Mica condensers are the most suitable for use when very high stability is required. Ordinary mica condensers have a stability of about 1 per cent. and a power factor of about 0.003 at 1Mc/s. Although the insulation resistance of mica condensers is high (about 10,000M), it is important to remember that the working voltage of small mica condensers is normally only 350 D.C. They have the small temperature coefficient of about 50×10^{-6} per degree centigrade. Whilst mica condensers are made in values larger than 0.1 μ F and working voltages which may be very high, such condensers are always comparatively large.

Paper Condensers

Paper condensers are comparatively cheap and are normally manufactured in a range of values varying from about 500pF to about 50 μ F. The stability is of the order of 15 per cent. The working voltages vary widely according to the type and thickness of the paper. Metallised foil paper condensers are usually smaller but the working voltages and insulation resistance are normally lower than the normal type of paper condenser. The insulation resistance of paper condensers is normally lower than that of good quality ceramic or mica components and the power factor (about 0.015) is about five times that of mica or ceramic.

Paper condensers are very suitable for decoupling at normal radio frequencies and for coupling and decoupling in audio amplifiers.

The table shows the types of capacitors which possess the advantages mentioned.

**REMEMBER TO BUY
OUR COMPANION JOURNAL
PRACTICAL TELEVISION
1/6 Every Month**

R.S.C. MANCHESTER BRADFORD & LEEDS

(Leeds) LTD.

Terms C.W.O. or C.O.D. No C.O.D. under £1. Post 1/9 under £2. 2/9 under £5.

EX. GOVT. MAINS TRANSFORMERS

Primaries 200-250 v. 50 c.p.s. A.C.	
250 v. 60 m.a., 6.3 v. 2 a.	10/11
275-0-275 v. 100 m.a., 6.3 v. 2 a., 5 v. 3 a.	21/9
300-0-300 v. 60 m.a., 6.3 v. 2 a.	11/9
300-0-300 v. 100 m.a., 6.3 v. 2 a., 5 v. 3 a.	27/9
350-0-350 v. 100 m.a., 6.3 v. 2 a., 5 v. 3 a.	27/9
450-0-450 v. 250 m.a., 6.3 v. 3 a., 6.3 v. 1 a.	
5 v. 6 a.	40/9

SELENIUM RECTIFIERS		H.T. Types H.W.	
F. W. BRIDGE		150 v. 40 m.a.	3/9
6/12 v. 1 a.	3/11	250 v. 50 m.a.	3/11
6/12 v. 2 a.	6/11	250 v. 60 m.a.	4/11
6/12 v. 3 a.	9/9	250 v. 80 m.a.	5/11
6/12 v. 4 a.	12/3	250 v. 250 m.a.	12/9
6/12 v. 6 a.	15/3		
6/12 v. 10 a.	25/9		
6/12 v. 15 a.	35/9		
24 v. 2 a.	14/9		

SPECIAL OFFER OF BRAND NEW

EX. GOVT. SELENIUM RECTIFIERS TELEVISION TYPE
 250 v. 200 m.a. 6/9

HEAVY DUTY TYPE
 24 v. 15 amp. F.W. Bridge, with large square aluminium coolers—27/9 ea

R.S.C. BATTERY CHARGING EQUIPMENT

All for A.C. Mains 200-250 v., 50 cc.

ASSEMBLED CHARGERS

6 v. 1 amp.	19/9
6 v. or 12 v. 1 amp.	27/9
6 v. 2 amps.	29/9
6 v. or 12 v. 2 amps.	38/9
6 v. or 12 v. 3 amps. with ammeter	59/9

Above ready for use. With mains and output leads. Carr. 9/6.



Assembled 6 v. or 12 v. 4 amps.

Fitted Ammeter and variable charge rate selector. Also selector plug for 6 v. or 12 v. charging. Louvred steel case with stoved blue hammer finish. Fused 69/9

Use with Carr. 5-mains and output leads. Terms: Deposit 13/3 and 5 monthly payments 13/3.

ASSEMBLED CHARGER

6 v. or 12 v. 2 amps.

Fitted Ammeter and selector plug for 6 v. or 12 v. Louvred metal case, finished attractive hammer blue. Ready lead for use. With mains and output leads. Double Fused. Only Carr. 3/9. **49/9**

Guaranteed 12 months. BATTERY CHARGER KITS

Consisting of Mains Transformer, F.W. Bridge, Metal Rectifier, well ventilated steel case, Fuses, Fuse-holders, Grammetts, panels and circuit. Carr. 3/6 extra.

6 v. or 12 v. 1 amp. 22/9
 As above, with Ammeter... 25/9
 6 v. 2 amps. 25/9
 6 v. or 12 v. 2 amps. 31/6
 6 v. or 12 v. 2 amps. inclusive of Ammeter... 42/9
 6 v. or 12 v. 4 amps. 53/9
 6 v. or 12 v. 4 amps. with Ammeter and variable charge rate selector. 59/9.

CHARGER METERS.
 0-1.5 a., 0-3 a., 0-4 a., 0-7 a., 0-25 a., 0-60 a., 8/9.

HEAVY DUTY CHARGER KIT.

6/12 v. 6 amps. variable output. Consisting of Mains Transformer 0-200-250 v., F.W. (Bridge) Selenium Rectifier; Ammeter, Multi Position Switch with Knob; Panels, Plugs, Fuses, Fuseholder, and circuit. 59/9. Carr. 4/6.

EX-GOVT. CASES. Size 14-10-8 1/2 in. high. Well ventilated, black crackle finished, un-drilled cover. IDEAL FOR BATTERY CHARGER OR INSTRUMENT CASE OR COVER COULD BE USED FOR AMPLIFIER. Only 9/9, plus 2/9 postage. 2 v. 16 a. EX-GOVT. ACCUMULATORS. New, boxed. Only 5/6 each, 3 for 15/-, post 2/6. 6 for 27/6. carr. 3/6.

PHILCO V.H.F. M. RADIO TUNERS with self-contained Power Pack. For 110-200/250 v. A.C. mains. Inc. 6 valves (Magic eye tuning indicator). Housed in beautiful polished walnut veneered cabinet. List price £20. Limited stocks, brand new. 12/- each, carr. 7/6, or on H.P. terms. Deposit 22/6 and 12 monthly of 22/6.

D.C. SUPPLY KIT. 12 v. 1 a. consisting of partially drilled metal case, mains transformer, F.W. Bridge Rectifier, 2 fuseholders and fuses, Change Direction switch, variable Speed regulator and circuit. For 200-250 v. A.C. mains. Suitable for Electric Trains, etc. Limited number available at 29/9.

RE-ENTRANT SPEAKERS. Tannoy. 8 watt, 7.5 ohms. Only 19/6 each. Or 35/- per pair.

LITTLE STAAR BATTERY-OPERATED RECORD-PLAYING UNITS COMPLETE WITH PICK-UP To take 45 r.p.m. records. As used by leading manufacturers in Transistorised Standard players. Brand new. £3.19.6 only.

STANDARD JACK SOCKETS. With 4ft. screened lead. 1/11 ea.

5 CORED FLEX. Rubber insulated. 14/36. 1 1/2 yd. 50 v. TRANSISTORS. Audio Type. 6/6. R.F. 12/6. Power type. X2104. 10/- Most types at bargain prices. Diodes 0A81, GD3, 3/8. **REPAIR CO. CONSTRUCTIONAL ENVELOPES AND PARTS IN STOCK.** Parts for 3 Dec 3 Transistor Radio, £3-6-6. Hi-wayman Portable. £7-15-/. Mini-Seven 7 Transistor Pocket Portable. 10 Gu.

AKDENITE DEAF AID EARPIECES. Brand new complete with ear insert and only 15/6 each.

TURNOVER STEREO MONO. PICK-UP HEADS. by Acos. Suitable for normal 78, 45, or 33 r.p.m. records or for stereo type. Sapphire Stylus. Will fit Garrard B.S.R., Collaro and Staap Galaxy Record Changers. Only 49/9.

Fully guaranteed and tested before despatch

VALVES

Postage 6d up to 3 valves, 9d 4 to 6. Above six subject to our usual terms.

1AB6 9/9	8D2 6/9	7C5 7/9	65ME 8/9	EB91 5/9	FW4500 9/9	PEN46 6/9	UAF42 10/6
1AH5 9/9	6D6 5/9	7C6 7/9	141TH 8/9	EBC33 6/9	GZ30 9/9	PL33 9/9	UB41 9/9
1A4J 6/9	6F1 11/9	7S7 7/9	171DDP 8/9	EBC41 9/9	GZ32 11/9	PL81 13/9	UB61 9/9
1CIEM 6/9	6F12 6/9	8D2 3/3	318U 8/9	EBC90 11/9	GZ33 10/9	PL82 9/9	UBF80 9/9
1C3 9/9	6F13 11/9	8D3 6/9	441U 9/9	EBC90 11/9	GZ34 13/9	PL83 10/9	UCC85 10/6
11L 5/11	6F14 11/9	307 7/6	451PT 7/9	EBF89 9/9	GZ37 9/9	PY31 7/9	UCH42 10/9
1FD1 9/9	6F15 11/9	3D2 3/9	AC6PEN 5/9	ECC35 7/6	HL41DD 11/9	PY80 9/9	UCL82 14/9
1FD9 6/9	6H6 2/3	9U8 6/9	AC/HL 5/9	ECC81 7/9	IW4350 9/9	PY81 9/9	UF42 8/9
1F1 6/9	6J5 4/9	954 1/9	B38 8/9	ECC82 7/3	IW4500 9/9	PY82 8/9	UF89 14/9
1F2 6/9	6J5G 4/6	10F1 17/9	B65 7/3	ECC83 9/9	KT32 9/9	PY83 8/9	UL41 9/9
1F3 5/11	6J6 4/9	10LD3 7/9	B152 8/9	ECC84 9/9	KT33 9/9	PZ30 16/9	UL46 14/9
1F1 6/9	6J7C 5/9	10LD12 15/9	B309 8/9	ECC85 9/6	KT36 9/9	R2 9/9	UL84 9/9
1P10 6/9	6K7C 4/9	10LD14 15/9	B339 8/9	ECC91 4/9	KT45 14/9	R3 9/9	UT3 9/9
1P11 8/9	6KM7M5T 5/9	10P1 9/9	B339 8/9	ECC91 4/9	KT45 9/9	R12 11/9	UU4 9/9
1R5 7/9	6K9G 8/9	10P18 9/9	B339 8/9	ECC91 4/9	KT45 9/9	SD61 1/9	UU5 7/9
1S5 7/9	6L1 9/9	12A6 5/9	B719 8/9	ECL80 10/9	KT263 4/9	SP4 8/6	UY41 7/9
1T4 5/11	6L3 8/9	12AT7 7/9	DI 2/3	ECL82 11/9	L63 4/9	SP61 11/9	UY85 10/6
3A4 6/9	6LD12 8/9	12AU6 7/9	DAF96 9/9	EF9 5/9	LN152 9/9	SP64 8/9	VP1322 3/9
3C4 6/9	6LD20 8/9	12AU7 7/9	DAF96 9/9	EF42 8/11	LN309 16/9	SU61 11/9	VS110 3/9
3S4 7/3	6L12 8/9	12AX7 9/9	DF91 7/9	EF42 9/9	M12 5/9	TA1 16/9	WU120A 3/9
3V1 6/9	6L18 11/9	12SN7GT 8/9	DF92 9/9	EF42 9/9	MUI2 9/9	UB220 9/9	W17 5/11
3V4 5/9	6L19 11/9	12SP4 3/3	DF96 9/9	EF42 9/9	MUI4 9/9	U22 13/9	W147 5/9
514G 6/9	6L8C 9/9	13Y7A 3/9	D63 2/3	EF45 4/9	N17 7/3	U25 13/9	W150 5/9
5Y3G 7/9	6L19 11/9	18A6 10/9	D77 5/11	EF50 4/9	N19 9/9	U31 9/9	W179 9/9
5Z4G 9/9	6M1 6/9	16A5 9/9	D152 8/9	EF80 7/9	N37 4/9	U35 9/9	W227 9/9
6AB8 12/9	6N8 8/9	16A8 7/9	DD6 11/9	EF85 7/3	N19 9/9	U35 9/9	WD142 9/9
6AC7 5/9	6P25 11/9	17Z3 9/9	DH83 6/9	EF86 16/9	N19 9/9	U35 9/9	WD709 9/9
6AC6G 6/9	6P28 9/9	18X3 9/9	DH77 11/9	EF89 9/9	N142 9/9	U46 11/9	XD19 9/9
6AJ8 8/9	6Q7G 9/9	19Y3 9/9	DH109 10/6	EF91 5/9	N144 4/9	U46 11/9	X17 9/9
6AK8 8/9	6S7G 6/9	20D1 14/9	DH142 8/9	EF93 9/9	N148 4/9	U50 8/9	X142 9/9
6AL5 5/9	6S7K 6/9	20L1 9/9	DH147 6/9	EK90 12/9	N152 13/9	U52 6/9	X279 5/9
6AM5 4/9	6S7VGT 7/9	20P1 12/9	DH150 8/9	EL32 4/9	N154 9/9	U54 10/9	X727 9/9
6AN6 6/9	6S7VGT 7/9	20P1 12/9	DH150 8/9	EL33 11/9	N154 9/9	U78 9/9	Y83 5/9
6AQ5 7/9	6U1GT 12/9	21A6 13/9	DH179 8/9	EL34 16/9	N329 9/9	U78 9/9	Z63 9/9
6AO8 7/9	6U5G 6/9	25L6 9/9	DK91 7/9	EL38 19/9	N709 9/9	U84 9/9	Z77 7/6
6AT6 7/9	6U8 6/9	30L1 8/9	DK96 9/9	EL41 10/9	N727 9/9	U139 9/9	Z87 9/9
6BB 3/11	6V4 8/9	30P16 9/9	DL83 7/3	EL84 9/9	OM4 6/9	U142 9/9	Z77 7/6
6BE6 9/9	6V6GT 7/9	35Z4 6/9	DL83 7/3	EL80 9/9	P61 2/9	U151 11/9	Z142 9/9
6BBG 18/9	6V8G 6/9	41MHL 6/9	DL96 9/9	EL91 4/9	PC84 9/9	U152 9/9	Z145 9/9
6BQ5 9/9	6V8G 6/9	53KU 10/9	EA50 1/9	EM80 9/9	PCF80 12/3	U153 9/9	Z150 9/9
6BK6 6/6	6X2 11/9	54KU 11/9	EAB80 9/9	EY51 11/4	PCF82 10/3	U154 9/9	Z152 5/9
6BY5 9/9	6X4 6/9	62DDT 8/9	EAF42 8/9	EY96 12/9	PCF82 10/3	U154 9/9	Z152 5/9
6BY7 7/9	6X5 5/11	62V7 7/9	EB34 2/3	EZ35 9/9	PCF82 10/3	U154 9/9	Z152 5/9
6C9 11/9	7AN7 8/9	63ME 6/9	EB41 7/6	EZ80 8/9	PCL83 16/9	U881 8/9	Z719 18/9
6D1 1/9	7B7 9/9			EZ81 8/11	PCL84 8/9	U403 8/9	ZD152 5/9
				EZ90 6/9	PEN45 7/9	UAC80 10/6	

A.M./F.M. RECEIVER


In beautiful Walnut Cabinet, 5 valves, internal Ferrite Aerial, Long, Medium and Short Wave, and F.M. Wave Bands. Price

£12.12.0. p. & p. 5/-




COSSOR MELODY MINOR MODEL 565

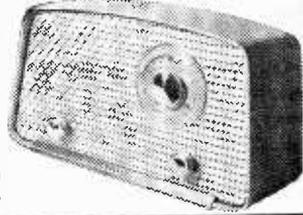A transportable Model of Ultra Lightweight design for use on 200/250 v. Mains D.C. or A.C., 40/100 c/s. Using 4 valves UCH81, UBF89, UY85 and Internal Ferrite Aerial. LIST PRICE 14½ gns.



OUR PRICE **£8-17-6** p. & p. 2/6

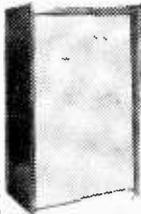

BASS REFLEX CABINET

for your Hi-Fi or Stereo Equipment. Size 13½" x 8" x 23". A beautiful walnut finish cabinet strongly built, using a 12in. P.M. Speaker and 4in. Tweeter.

LIST PRICE 9 gns. OUR PRICE **£5.19.6** p. & p. 2/6




Convert your Battery Set to Mains with a COSSOR BATTERY ELIMINATOR

MU2. For operation on 200/250 v. 50 c/s A.C. mains. Output: L.T., 1.5 v. 125 mA.; H.T., 90 v. 10 mA.

LIST PRICE 3 gns. OUR PRICE **37/6** p. & p. 2/6

AMPLIFIER AND CABINET

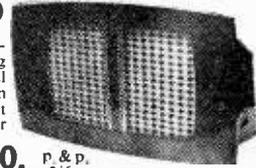3-watt Amplifier, using an ECL82 Valve and Metal Rectifier, housed in a modern attractive styled walnut cabinet with 5" P/M Speaker and on/off and tone controls.



£4.5.0. p. & p. 3/6. Can be sold for

RECORD CHANGERS

Collaro Conquest: 4-speed Auto Changers, turn over still, £7.19.6. Collaro AC4564: Rim drive 4-speed player, turn over still, £6.9.6. Collaro Junior: 4-speed Single Player, Separate Pick-up, £3.15.0. B.S.R.: UA8 4-speed Auto Changer, Manual and Auto Control Dual turnover still, £6.19.6 Garrard RC120/D Mark 2, 4-speed Auto and Manual Controls, using GC2 Cartridge, price £9.9.0. Post and Packing 3/6.

WIRECOMP ELECTRONICS

378 HARROW ROAD, LONDON, W.9. Tel.: CUNNINGHAM 9530
Hours of business: 9 a.m.-6 p.m. Open all day Saturday.

FREE TO AMBITIOUS ENGINEERS!

The latest edition of "Engineering Opportunities"

Have you sent for your copy?



'ENGINEERING OPPORTUNITIES'

is a highly informative guide to the best-paid Engineering posts. It tells you how you can quickly prepare at home on "NO PASS-NO FEE" terms for a recognised engineering qualification, outlines the widest range of modern Home-Study Courses in all branches of Engineering and explains the benefits of our Employment Dept. If you're earning less than £20 a week you cannot afford to miss reading this unique book. Send for your copy to-day—FREE.

FREE COUPON— Please send me your FREE 148-page "ENGINEERING OPPORTUNITIES"

NAME
ADDRESS
Subject or Exam that interests me
British Institute of Engineering Technology
409 B, College House, 29-31, Wright's Lane,
Kensington, W.8.

WHICH IS YOUR PET SUBJECT?

Mechanical Eng.
Electrical Eng.
Civil Engineering
Radio Engineering
Automobile Eng.
Aeronautical Eng.
Production Eng.
Building, Plastics, Draughtsmanship, Television, etc.

GET SOME LETTERS AFTER YOUR NAME!

A.M.I.Mech.E.
A.M.I.C.E.
A.M.I.P.E.
A.M.I.M.I.
L.I.O.B.
A.F.R.Ae.S.
B.Sc.
A.M.Brit.I.R.E.
CITY & GUILDS
GEN. CERT.
OF EDUCATION
etc., etc.

For Safety's Sake use AVO Prodclips



Safety first every time with these patented spring-loaded AVO Prodclips.

Cleverly designed for use as insulated prods, they are invaluable for reaching and holding test points which are difficult of access.

Post Free **15/-** per pair.

AVO LTD · AVOCET HOUSE,
92-96 VAUXHALL BRIDGE ROAD, LONDON, S.W.1.
Victoria 3404 (12 lines)
A MEMBER OF THE METAL INDUSTRIES GROUP OF COMPANIES.

Open to Discussion



The Editor does not necessarily agree with opinions expressed by his correspondents.

Radio Pick-up

SIR—In reply to Mr. Trueman's problem of radio pick-up (November issue), may I suggest that he earths the co-axial cable at the recorder end only and if the recorder has a two-pin plug (I believe that most, if not all, have co-axial plugs) he checks that the outer of the co-axial is connected to the earthed or earthy side of the input.

With reference to Mr. Kingdon's letter on earth and mains connections I would like first to stress his point about the correct connection of mains plugs. There is at least one maker who fits three-core mains leads but they also provide an earth socket in the usual manner, perhaps one of your readers could say why two earthing connections are provided.—**J. DIXON** (Portishead).

Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying commercial or surplus equipment. We cannot supply alternative details for receivers described in these pages. WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE. If a postal reply is required a stamped and addressed envelope must be enclosed with the coupon from page iii of cover.

SIR—In reply to Mr. Trueman in the November issue, may I offer to help him by passing on some information derived from experience and also from manufacturers of tape recorders. May I begin by assuming that he is using a high impedance mike such as a condenser or crystal, and that the trouble mainly occurs on "record." Firstly he should try the effect of shunting the grid leak resistor with a capacitor of around 22pF. If this does not cure the trouble, a small choke can be wired in the live lead of the mike. Also if he is using a high impedance mike on a long run, the loss will be very high indeed and I would advise a low impedance mike and matching transformer with twin screened mike cable.

If the trouble manifests itself on playback, a 50pF capacitor can be wired directly across the head which should cure the trouble. I hope these little pointers may be of service.—**C. BRADDOCK** (266, Waterloo Road, Blackpool).

SIR—With reference to Mr. Trueman's letter on radio pick-up, the trouble can be due to one of three things. (1) Detection is taking place at the crystal microphone (assuming it is crystal), the co-axial cable outer acting as the "aerial," the audio being fed to the grid circuit in the conventional way. (2) The first and second amplifier stages are oscillating somewhere well above audibility due to accidental positive feedback in the circuit, and this oscillation, or one of its harmonics, is beating with some short wave station(s) at the amplifier input and rectification

(detection) owing to the anode bend effect is taking place. (3) In a sensitive amplifier, minute signal voltages picked up on the input lead are detected by a poorly soldered joint or "dirty" plug connection. A few ohms D.C. resistance along its length can produce sufficient R.F. pick-up owing to the "earthing" impedance of the lead being high from an R.F. viewpoint.

The cure for (1) and (3) is simple and consists of inserting extra components in the grid circuit of the input stage. A resistor of 22k is wired in series with the lead to the grid of the valve and a condenser of 50pF is wired from the grid to earth. The normal grid leak is wired to the other end of the 22k resistor and a capacitor of 50pF is also connected from this point to earth.

To remedy (2) the self-oscillation must be stopped, and the usual remedies such as screening of input from output, etc., tried. For extra protection the components given above may also be fitted to a circuit even after the self-oscillation has been cured.

Incidentally it will be found very handy on tape recorder inputs, etc., operating very near amateur radio transmitters, and has been loosely called a "CQ 40" chopper circuit.—**B. PHILLIPS** (Preston).

Becoming an Amateur

SIR—I have thought for some time about becoming a "ham" and your new course about how to become an amateur has prompted me to start a class at school with the object of teaching some of the pupils and myself the necessary theory to sit for the R.A.E.

I have two or three books from which I am obtaining my information for teaching the class, but, unfortunately, they do not describe the necessary theory about control of a transmitter. As I am not able to purchase, or borrow for a sufficient length of time from the public libraries, books explaining the above theory, perhaps it is possible that you could reintroduce "Transmitting Topics" and "Short Wave Section." I am sure, also, that the items would be of great value to others in similar predicaments to my society.—**A. T. ROBINSON** (Chairman of Westcliff High School for Boys Amateur Radio Society).

[Further articles in the series mentioned are planned for future issues.—Ed.]

Transistors v. Valves

SIR.—The Editorial in your November issue proved a little disappointing to me. I am interested in all branches of electronics and have been building valve sets for twenty-five years, but what a welcome change the transistor has made.

There are many applications of the thermionic valve that cannot yet be matched or even performed by the transistor but it is a definite advantage to have a receiver small enough to be slipped into a "vest pocket," which weighs only ounces instead of pounds and which will work for many months on a single $1\frac{1}{2}$ V cell. Judging by the ever-increasing number of advertisers in your journal who feature transistors and sub-miniature components there is a great deal of interest in this aspect of amateur electronics.

Let us by all means continue with articles on valve sets, but please publish new circuits, new applications and every bit of additional information that you can glean about the transistor (my own tastes run to reflex and super-regenerative receivers).—L. F. GRAY (W.7.).

[A reflexed transistor receiver is described on page 743.—Ed.]

SIR.—I would like to say a word on the side of the transistor which has been criticised so much in your columns. I am surprised that the critics do not appear to realise that valves can be damaged just as easily as transistors. A transistor set can be operated much easier than a valve set as there is no reaction to tune in and they take no time to "warm up." I will agree that for the moment we cannot altogether dispense with the services of the valve although there are some jobs which a transistor can do just as effectively and cheaper. For example, I have a two-transistor set on which I have heard eleven recognisable stations, and not all of them English, by any means. I get 150 hours of listening from a two-shilling battery, a PP4. The set can be left on for days without any ill effects. If this happened to a valve set a new H.T. and L.T. battery would be needed very frequently.—D. A. PRICKEIT (Bury).

Transistors on Mains

SIR.—Perhaps other readers would be interested in a battery eliminator for a transistor set which is used frequently by myself.

Transistors may, of course, use the mains supply the same as valves. Since the current consumption is extremely small a rectifier with cooling fins is unnecessary and a crystal diode may be used.

Either a 100ohm resistance or a choke will suffice for smoothing with two $25\mu\text{F}$, 25V.W. condensers, although I find that one condenser is sufficient. If a transformer giving a higher voltage is used (up to say 45V) then two diodes should be used in series.—J. SAUNDERS (Cardiff).

Transistor Signal Tracer

SIR.—I have made up the transistor signal tracer (see Sept./Oct. issue), using transformer coupling, as I had one to hand, and I have found it has many more applications, as an amplifier

and preceded by a coil and condenser it makes a stand-by radio. It will take the mike or a pick-up and the output can be fed into a push-pull output stage for a loudspeaker.—S. J. REECE (Ashford).

Rectification

SIR.—Replying to G. R. E. (Bristol) in the December issue, I would like to say that I have also received stations when using an audio amplifier with no detector at all. My explanation is that the anode current/grid volts curve of the first valve at the point of working is not quite straight and there is a slight anode-bend detection taking place. I am interested to know that others have met this.

I enjoy listening to classical LP records on a Hi-Fi gramophone but I find one fault standing out above any other. Sometimes on a long note the pitch slowly rises and falls most unpleasantly as the record revolves. I have found that it is due to the hole in the record being slightly larger than the spindle on the turntable, and the record is not quite in the middle. The effect is only noticeable on a sustained note, but it sounds awful to a musical ear. Is this fault peculiar to my own gramophone, or have other readers noticed this effect?—G. BRIAN JAMES (Grasmere).

[We have found that many instances of radio reception on tape recorders, etc., have been due to induction from a neighbour's receiver.—Ed.]

Miniature Mains Receiver

SIR.—I am one of the younger readers of your fascinating magazine, and am naturally very glad to see simple and inexpensive sets described in your pages. I enclose a photograph of the miniature mains set as described in the June edition. It gives excellent reception of Medium Wave stations with a 5ft. aerial. As regards the transistor v. valve dispute, I think both have their place.—J. BELL (Aberdeen).

[We were interested to see Mr. Bell's receiver which is well constructed in a small cabinet.—Ed.]

LAST-MINUTE CHRISTMAS GIFTS

No need to rush out to the shops. Here's one you can arrange now . . . in a few moments . . . in the comfort of your own armchair. A year's subscription for PRACTICAL WIRELESS is the ideal gift for friends who are radio enthusiasts.

But hurry! You must send now to make sure that first copies arrive in time for Christmas. Simply send your friends' names and addresses, together with your own and remittance* to cover each subscription, to The Subscription Manager (G.3), Practical Wireless, Tower House, Southampton Street, London, W.C.2. An attractive Christmas Greetings Card will be sent in your name to announce each gift.

* RATES (INCLUDING POSTAGE) FOR ONE YEAR (12 ISSUES):—U.K. £1.3.0, OVERSEAS £1.1.6, CANADA £0.19.0, U.S.A. \$3.

SKILLED MEN!

USE YOUR KNOWLEDGE IN A WORTHWHILE JOB

VACANCIES
FOR
**LINEMEN
DRIVERS
DISPATCH RIDERS
DRAUGHTSMEN
DRIVER
ELECTRICIANS
RADIO
MECHANICS
TECHNICAL
STOREMEN
TELEGRAPH
MECHANICS
OPERATORS**
in
**THE ROYAL
SIGNALS**

*Up to £25 tax-free Bonus
plus first-rate wages for
two weeks of your time*

ARE you in a skilled trade? Then you can probably add a tidy sum to your income by joining the Army Emergency Reserve. For one thing, you get pay and allowances at full Regular Army rates whilst in camp. And the more your skill's worth in civilian work, the higher your Army rank and pay. Better still, you also get £9-£25 bonus tax-free.

For this you just spend 14 days a year at a camp, working on your own speciality. And money's not the only profit you get from that. You get a grand refresher course, giving you a lot of new ideas, and putting you right in touch with the latest Army developments. And you

get a welcome break from the usual routine, with sports, games and a great social life. For the place is full of people with the same interests as yourself. Don't miss this chance! Send off the coupon now to: H.Q. A.E.R. (R. Sigs.), Blacon Camp, Chester.

POST THIS OFF RIGHT AWAY!

*Please send me—without obligation—the illustrated booklet telling me
all about the Army Emergency Reserve.*

NAME _____

ADDRESS _____

TRADE _____ (PW/AER)

RECEIVERS & COMPONENTS

VALVES, new and used. from 1/6 each, all guaranteed. All types Radio, Television Components. Lists free. **HAMILTON RADIO**, 237, Sedlescombe Rd. N., Hastings.

CALLING 9IN. TELEVISION OWNERS.—Brand new factory fresh 9in. Ferranti Tubes, originally £14/10/-, will replace Mazda, Brimar, G.E.C. etc., £4/10/- each; 6 months guarantee. **TOMLINS**, 127, Brockley Rise, Forest Hill, S.E.23.

FIX IT YOURSELF! Pre-assembled ready for instant fitting. Clip-on 5BL 30/-; 8EL, 42/6. **FRINGE AREA MODELS** for high gain. Double 5 Array, 72/6; Double 8 Array, 100/-. Fringe area super low-loss Coaxial, 1/3 yd. Standard low-loss, 1d. yd. **NEW T.V. TUBES**—2 YEARS' GUARANTEE. Suitable 'Plug-in' replacement for Mullard, Mazda, etc. 14in. all types, £10/10/0; 17in. all types (except CRM), £12; 17in. CRM types, £11/0/0. S.A.E. for CRT and Aerial List. Satisfaction or money refunded within 10 days. All items carriage paid C.W.O.

HASE SUPPLIES

34, Prince St., Bristol (Dept. P.W.)

H.M.V. 15IN., English Electric 15in., Ultra, etc., Televisions, not working, originally £175 each. £5/10/-. **TOMLINS**, 127, Brockley Rise, Forest Hill, S.E.23.

SPEAKER REPAIRS, Cones/Fields fitted. Clock Coils Wound. **L.S. REPAIRS**, Pluckley, Ashford, Kent.

TURRET TUNERS, "Brayhead" made, £6/15/- post free; few only; state model. **A. RADIO COMPONENTS**, 14, The Borough, Canterbury.

AMAZING OFFERS BY ELECTRADIX

to celebrate their fortieth year of trading.

TRANSAIR. Super sensitive **TRANSISTOR RADIO** can be built by anyone in 45 minutes following the simple pictorial plans and full instructions everything supplied to the last nut and bolt. Picks up local stations anywhere and many foreign stations. Fully guaranteed. Free service information to all. **SEE FOR YOURSELF** send for the KIT complete with **WATCH RECEIVER**, 29/6. Not obtainable elsewhere. Parts sold separately. Priced parts list and plans, 1/6.

THE LESDIX ELECTROTOR. The lightest and most efficient miniature motor made. 4 1/2 volts D.C. Weight 1/2 oz. Ideal for toy and model makers. Will drive model boats up to 18in. Brand New, 6/6, post 6d.

Do your own Nickel Electro-Plating with the **VICTRIX** miniature plating plant. Results to full commercial standards. Tank 10in. x 8in. Cleaning chemical, Nickel chemical, 99.9% pure anodes, rods and spacers and U2 dry cell which give 12/15 hours of plating. Full instruction manual, all for 90/- plus 5/- postage and packing.

ELECTRADIX RADIOS

(Dept. P), 214, Queenstown Road, Battersea, S.W.8.
MACaulay 2159.

RATES: 5/6 per line or part thereof, average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless," Tower House, Southampton St., Strand, London, W.C.2.

"WEYRAD" TRANSISTOR RECEIVER

COMPLETE KIT—LONG & MEDIUM-WAVE, PUSH-PULL O.P. ... £9/12/6
CONSTRUCTORS BOOKLET ... 2/-
Send S.A.E. for Shopping List.

WESTHAM RADIO SUPPLIES
Rear of 176, Abbotsbury Road
WEYMOUTH, DORSET

RESISTORS.—100 new, wire ended, assorted, all types 7/6 box, post free. **COOK'S OF BEDFORD**, 29, St. Mary's St., Bedford.

RECLAIMED VALVES, tested and perfect; huge stocks; all one price, 5/-, plus 6d. postage each. Delivery by return. **LEWIS**, 57, Chalford Walk, Woodford Green, Essex.

FM-AM STEREO**Radiogram chassis-CBB**

Paired output 6 watts Plain or Stereo Records. A hand-built quality unit with two speakers
ONLY £20.

BEL SOUND PRODUCTS CO.
Marlborough Yard, London, N.19.
ARC. 5078.

MIDGET OUTPUT TRANSFORMERS, 5000ohms to 30hms for 6V, etc., 5/9 each, post free. **AJAX ELECTRONIC PRODUCTS**, 85, Felsham Road, S.W.15.

TRANSISTORS, OC71, 6/6 each; OC44, 10/6. Superb Instrument Cases, 1 1/4 x 7 1/4 x 6, new, 7/6. **B.S.R.** 4-spd. TU9 single players, 67/6, plus 3/6 p.p. **D. B. CARTER**, 347, Ladypool Road, Birmingham, 11.

40in. American Stainless Steel Whip Aerials, one piece with mountings and special loading coil in base in effect increasing height to 12 feet. 30" (5/-), 250 Watt U.S.A. R.F. Amplifiers, raises output of small transmitter to 250 watts. Includes 28 HK—257 valves in push pull. Weight 88 lbs. New in case, £8/10/- (15/-). Inter-
phone Amplifiers, 4 valves, 28 v. D.C. input, easily convertible, 25/- with valves (5/-). **Kurman Plate Relays**, 7,000 ohms S.P.D.T., 12/6 (2/6). **Boeing Beehive Insulators**, white, 3 1/2in. x 1 1/2in. Ideal for H.F. 1/- (6d.). **Microswitches**, S.P.S.T., 1/6 (6d.). S.P.D.T., 2/- (6d.). **Chokes**, Freed 9 H. 270 m/a, 88 ohms, 10 lbs., 12/6 (3/-). 15 H. 60 m/a, 260 ohms, 8/- (2/-). **Chicago** 5/25H, 200 m/a, 7 lbs., 10/6 (2/6). 5/20 H.

4-page list of over 100 different items available

300 m/a, 14 lbs., 20/- (4/-). **Germanium Rectifiers**, IN-52, 2/- (6d.). **Klixon Circuit Breakers**, give automatic protection. 35 amps, break, simply push to re-set, 5/- (1/-). **Deck Insulators**, heavy, 10in. dia., 6 1/2in. feed through, 15/- (3/6). **Eimac VT-127A Valves**, 5 v. 10 amp, 100 watts, 300 mc/s, 25/- (3/-). **Plywood 25ft. Tripod Base, self-supporting Aerial Masts**, 95" (20/-). 60 to 110 Mc/s Adjustable Calibrated 3 Element Beams Arrays, on adjustable boom for 2in. dia. mast with 100 feet, 1in. Co-Ax. 1 lead in, 90/- (5/-). We have lots of "bits and pieces"—please send your requirements—we can probably help. All enquiries answered. Amounts in brackets are carriage England and Wales.

P. HARRIS
ORGANFORD, DORSET

KINGSLAND ELECTRONIC COMPONENTS**Stupendous Offer**

FREE: Set of 13 drills from 1/16in. to 1in. or Set of two-way screwdrivers in plastic cases. With bargain pack consisting of:—One pair throat microphones, 50 assorted resistors, approx. 150 assorted screws, one dial pointer 2ft. 2in. screened lead with sockets, one 5 Henry 200 mA. choke, two electrolytic condensers, radio knobs, toggle switches, Octal valve bases, vibrators, one pair M.C. earphones, one waveband switch, four Co-Ax. plugs, one box of assorted coils, cartridge fuses, three potentiometers, one WW multiplier, 24 assorted condensers, one Festoon lamp and holder, one coil PVC wiring-up wire.
All this for 35/-, p.p. 4/6.

A RADIO CHASSIS WITH OVER 200 USEFUL PARTS, consisting of condensers, resistances, valve holders, chokes, switches, coils, nuts and bolts, etc., 10/6 p.p. 4/6.

100 ASSORTED RESISTANCES, including W.W., 10/-, p.p. 1/9.
50 ASSORTED CONDENSERS, 10/-, p.p. 1/9.
ONE 5 HENRY CHOKE, 2 amp. Ideal for radio or TV smoothing, 5/6, p.p. 1/6.

SIX ASSORTED POTENTIOMETERS, 5/-, p.p. 1/6.
Open Saturday until one o'clock. Personal callers welcome.

182, KINGSLAND RD., SHOREDITCH, E.2. Tel.: SHO 6572. Sorry U.K. only.

POWER IN PACKETS.—Another good buy enables us to offer 162 x 12 x 3v. (18 set H.T.), 87 x 64 x 4 1/2v. 90 x 14v. heavy duty H.T., all at 10/9 each. 80 x 7 1/2v. at 5/-. 14v. Heavy Duty, 1/6 ea., 3 for 4/-. All inc. p. and p. Another good buy, more beautifully crated CV 1397 C.R.T.s available, bought at the right price enables us to offer these at the reduced price of 10/-, delivered (same as '97 but slightly longer persistence). **R. J. DIGGINS**, 129/133, Radnor St., Hulme, Manchester, 15.

VALVES FOR SALE, all tested on Mullard Valve Tester: 6P12, 6D2, 6F80, 10F1, 6F1, PY82, 20L1, 6V6, 6P25, 6P13, 6F14, 6F15, 20D1, ECC81, ECC82, 5/- each, plus 1/- p. and p. on orders of less than 6. **J. R. CALVERLEY & CO. LTD.**, 130, Water Stn., Radcliffe, Lancs.

The Famous Telephone type F in excellent condition. Works up to 3 miles with any twin wire. 60/- each, carr. etc., 10/-.

10 Line UC exchanges for use with any buzzer or magneto calling phones, £5, carr. 1/-.

Sets of 120 new American crystals from 5675 Kc to 8850 Kc in steps of 25 Kc except for 5725 and 5950. Must have cost £300. Offered at £5, plus p. & 5/-.

30 watt pressure type loudspeaker units. Unused, £3, plus carr. etc., 5/-.

4 of any of the following valves for 10/-: EB91, EF91, EF92, 6K7, KT61, 210SP1, 210VPT, 210DDT, Post 1/-.

PO Relays 2,000 ohm coil, 2 make, 1 break. New, 5/-, p. & p. 1/-.

Vibrator Power packs. New, fully smoothed in black crackle case with croc. clips, etc. 6 v. input, output 160 v., 40 mA, 25/-, p. & p. 3/6.

Brand New Creed Repetitors with tools and instruction book, etc. £9, inc. carr. U.K. Brand New Teleprinter. Page printers in sealed cases £25.

ELECTROSURE 118, FORE STREET, EXETER

Phone: Exeter 56687

RECEIVERS & COMPONENTS
(Continued)

SAVE ON REPAIRS. — 100.000 Salvaged Radio and TV spares. Valves. Tubes for practically any set made since 1936 c. Prices from: Lot. 17/6; P.O.T. 7/6; Osc. Tr. 6/-; Sound, 2/6; Mains, 10/-; E.H.T. Mains, 50/-; Def. Coils, 12/6; Speakers, 5/-; Tubes, Mullard, Mazda, etc., 9-10in., 30/-; 12-14in., £2/19/6; 17in., £3/19/6; all picture tested, fitted free or sent subject to 14 days money-back guarantee; Mullard 6 months' guarantee. Valves: 1,000 types from 1/6; EF91, EB91, 6J5, 2/6; EF90, UF42, 10F1, 6F1, 6SN7, 3/6. We can save you pounds! Send s.a.e. with enquiries or for complete list. **ST. JOHN'S RADIO**, 156, St. John's Hill, S.W.11. (Bat 9838.)

ANNAKIN

Pamphonic No. 1004 Hi-Fi Amplifiers. — New, boxed. Complete with valves. Only £15.15.0. Post free. **3-5-6-8-3-10.** Fane and Wharfedale Speakers.—List prices. **I.F. Strips No. 476.** —9.72 mc/s with 3-EF92, 1-DF91, 1-EB91, 1-EAC91. Similar to No. 373 strip. New. Only 32/6 each. Post 1/9. **Receiver Strips No. 114.** —124-156 mc/s. No dials, with 3-EF91, 2-EL91, 5-gang tune cond. New. Only 25/- each. Post 1/9. **Moving Coil Phones (double) and Moving Coil Mike.** cord, plug. 12/6 each. Post 2/- **Heater Transformers.** —230-250 v. mains. 6.3 v. 1.75 A. output. New, boxed. 6/6. Post 1/6. **Stepdown Transformers.** —200-240 v. mains. 30 v. 2 A. output. Tapped at 3, 5, 6, 8, 3, 10, 12, 15, 18, 20, 24 and 30 v. New, boxed. 25/- each. Post 2/6. **Small Electric Motors.** —4.6 v. D.C. 1 1/2 oz. New, boxed. 6/- each. Post 7d. **Mike Transf.** —100-1, small. New. 2/6 each. Post 9d. **Granophone Amplifiers.** —With EL84 valve, 230 v. mains trans. volume and tone controls. Chassis 8 3/16in. x 2 1/2in. x 1 13/16in. New. 57/- Post 2/3. **Nickel Soldering Irons.** —6 v. only. Weight 1 oz. Works off mains transformer (not supplied). New. 10/9 each. Post free. **Volume Controls.** —1 meg. switch. Long shaft. New. 4/- **Mainland only. No Export. C.W.O. only.** Send stamped, addressed envelope for Lists. **25, Ashfield Place, Otley, Yorks.**

NEW MINIATURE PRINTED RECEPTORS. 6d. RAY, 4, Dalton Ave., Whitefield, Manchester.

AUDIO TRANSISTORS 5/-

Red spot, 6/-; White spot, 8/-; Yellow/Green, 6/8; Red/Yellow, 12/6. **Miniature Electrolytics,** 2/9 each. All transistor components supplied. **Earphones** 14/- per pair. Post paid in U.K. S.A.E. enquiries please.

KIRK GATE RADIO,
82, KIRK GATE, HUDDERSFIELD

SPEAKERS. —Elac. 3 ohms P.M., 5in., 9/6, £5 doz.; 6 1/2, 8in., 11/6; P. and p. 1/9 all sizes. C.W.O. to B. & E., 47, Middle Hillgate, Stockport.

Well known FM Tuner Kits. Complete kit ready to assemble, less valves... £3.15.0. Complete with valves... £5. 5.0. Easy to follow Building Plans and Instructions ... 3s. 6d. **Few Only:** Sets of PM Coils, I.F.s R/Def., etc., with circuit, and instructions £1. 0.0. S.A.E. for enquiries.

R.C.R. 89, DERLEY ROAD, SOUTHALL, MIDD.X.
Callers at R.T.S. Goldhawk Rd., Seven Stars, London, W.12.

FOR SALE

COMPONENT STORAGE DRAWERS. Of stout cardboard, 5 1/2in. x 2 1/2in. x 6 1/2in.; sample, 1/9; 13/6 dozen. postage 2/3. **A.1 RADIO COMPONENTS**, 14, The Borough, Canterbury, Kent.

BENDIX RECEIVERS, RA-10, 4-band, superhet 150 kc/s-10 mc/s. Valves: 6SK7, RF, 6K8, F/C, two 6SK7 IF, 6R7 second det, 6C5 BFO, 6K6 OP, 6H6 diode. Built-in PU 24v., D.C., size 6 1/2in. x 15 1/2in., easily converted to mains as described on Page 453 of mains as described on Page 453 of Sept., 1957. P.W. £4 plus p.p. 10/- **American Beacon Tx-Rx RT37/PPN-2** brand new, composed of transmitter-receiver with 9 valves (5-3A5, 3-155, 1-1R5), built-in 2v. vibrator pack, spare vibrator, headset, connector leads and 10ft. collapsible aerial. frequency 214/238 mc/s, £3/15/-, plus p.p. 7/6. **E.W.S. CO.**, 69, Church Rd., Moseley, Birmingham, 13.

SATISFACTION ASSURED. — 12in. Televisions £9/10/-, 14in. £16, 17in. £19/10/- Write for quotation, stating requirements. We guarantee satisfaction. **TOMLINS**, 127, Brockley Rise, Forest Hill, S.E.23.

AMAZING VALUE. Philco Shortwave Car Radio Converters, originally £10, fit to any existing car radio and add six extra wavebands, 16-19-25-31-49 metre bands, also standard broadcast, 6/12 volts; compact under dash counting; chromium control panel with six press-buttons. Complete all fittings and instructions, easily fitted, 45/- post free. Each instrument brand new with Mullard valves. **TOMLINS**, 127, Brockley Rise, Forest Hill, S.E.23.

SAVE 30%. —The Tape King makes possible the impossible once more. **Agfa-Wolfen Tape**, 1,800ft. L.P. on 7in. spools, would be 50/-, only 35/-; limited quantity; also Tape barrens in sizes from 3in. to 8 1/2in.; many secondhand recorders: all new makes. S.A.E. for list. Once again a few only of the famous **E.M.I. Professional Tape Deck** at a fractional cost, 7 1/2in. per sec. 7in. spool; same price as before only 22 Gns. or terms. **E. C. F. KINGSLEY & CO.**, 132, Tottenham Court Rd., London, W.1. (EUS 6500.)

ASTOUNDING VALUE. —9in. Televisions 45/-, 12in. Televisions 70/-, 14in. £9/10/-, 15in. £5/10/-, 17in. £14. Complete but not guaranteed wiring, as received in part exchange. **TOMLINS**, 127, Brockley Rise, Forest Hill, London, S.E.23. All famous makes available, carriage 7/6.

CABINETS, ENCLOSURES AND EQUIPMENT By STAMFORD

EQUIPMENT CABINET 3ft. wide, choice of veneers. Motor Board 18in. x 14in. Control Panel. Amplifier Compartment and Record Storage.



GP57

	Cash Price		Hire Purchase	
	£	s. d.	Deposit	18 Months
SPEAKERS				
Axiote	6	12 1	20/-	7/2
W.B. HF1012	4	15 0	14/3	5/2
Golden 10in. FS8	8	6 7	25/-	9/-
Axiom 300	11	5 9	34/-	12/3
TUNERS & CHASSIS				
Armstrong ST3 AM/FM	27	6 0	81/9	29/8
... Jubilee	29	8 0	88/6	31/11
Duke H42 Powered	33	15 8	71/-	25/11
Chapman FM85	29	0 0	57/-	31/6
AMPLIFIERS				
Rogers Cadet & Control	17	10 0	52/6	19/1
CQ Twin Four	22	1 0	66/-	24/-
Leak TL12 & Vistalope III	34	13 0	104/-	37/9
MOTORS				
Garrard TA MK. II	8	10 0	25/6	9/3
... 4HF	18	9 9	55/6	20/1
Collaro 4T/200	18	13 0	54/9	20/4

Write for Lists for Cabinets, Equipment and Completed Systems.
A. L. STAMFORD LTD. (Dept. K29).
Showrooms: 84/86/98, Weymouth Terrace, Hackney Road, London, E.2. No. 6 bus from Liverpool Street, book to Odeon, Hackney Road and walk back two turnings.

AMERICAN MAGAZINES. — Year's subscription: "Popular Electronics" 35/6; "Radio Electronics" 35/6; "Audio" 35/-. Specimens, 4/- each. Full catalogue free. **WILLEN LTD.** (Dept. 40), 9, Drapers Gdns., London, E.C.2.

12 NEW ELECTROLYTICS, 5/-; 50 Resistors, 5/-; 25 Condensers, 5/-; Metal Rectifiers, 250v. 60mA, 4/6; P.M. Loudspeakers (used), 7/6; Valves from 1/6; Complete Kits, Crystal Set, 7/9; Pocket Transistor Radio, 27/9; Valve Radio, 36/- All guaranteed. Postage extra. Lists free. **HAMILTON RADIO (W)**, 237, Sedlescombe Rd., N. Hastings.

NEW CONDENSERS. Resistors. Switches. Transformers. Cable Plugs, etc. S.A.E. lists. 448, East Prescott Rd., Liverpool.

PERSONAL MOBILE RECEIVER. — Coils as specified at 4/- each plus 6d. postage. **AJAX ELECTRONIC PRODUCTS**, 85, Felsham Rd., London, S.W.15.

SUB-MINIATURE SOLDERING INSTRUMENTS

Ultra-lightweight—only 1 oz.! The most efficient tool for all Transistor and other delicate soldering. 6 volt 9 watt. 10/9 Post free. Or with isolating transformer for A.C. Mains. 14/6 plus 1/3 p. & p.

KENNETT & COMPANY,
Doe Park, Denholme, Yorks.
Trade enquiries invited.

100 BAYS of brand new adjustable steel Shelving, 72in. high x 34in. wide x 12in. deep; stove enamelled. Light green; sent unassembled. 6-shelf Bay, £3/15/-; sample delivered free; quantity discounts. **N. C. BROWN, LTD.**, Eagle Steelworks, Heywood, Lancs. (Tel.: 69018.)

STAMP COLLECTIONS

STAMP COLLECTIONS or accumulations valued and purchased at highest prices. Send to **JOHN LISTER LTD.**, 186/8, Shaftesbury Ave., London, W.C.2.

SOUND RECORDING

TAPE DISC/TAPE transfer, 1,800ft. new L.P. Tape. 32/6. Unimixer Mixing Units for quality. **SOUND NEWS**, 10, Clifford St., London, W.1.

WANTED

ALL TYPES of Valves wanted. PL81, ECL80, EY51, U25, PCF80, PZ30, U801, etc., etc., best cash price by return. **STAN WILLETTS**, 43, Spon Lane, West Bromwich, Staffs. (Tel.: WEST 2392.)

A PROMPT CASH OFFER for your surplus Brand New Valves, Speakers, Components, Test Instruments, etc. **R.H.S.**, 155, Swan Arcade, Bradford, 1.

URGENTLY REQUIRED, new Radio, Television or Industrial Valves. Also old and obsolete types. Cash prices offered for any quantity. Write, call or phone: **MIT 6202**, 201, Streatham Rd., Mitcham, Surrey.

WANTED VALVES

All types for prompt cash. Must be new. State quantity.

WILLIAM CARVIS LTD.
103, North Street, Leeds, 7.

SERVICE SHEETS

SERVICE SHEETS.—Radio and TV, 2/6 ea. List 1/-. S.A.E. with enquiries, please. **GLOBE SUPPLIES**, BCM/Electrique, Monomark House, London, W.C.1.

FAULTFINDER FILES (TV), showing common faults that each receiver is prone to, and other useful servicing information. 2/- ea. List 9d., plus postage. **S. P. DISTRIBUTORS**, 11, Old Bond St., London, W.1.

SERVICE SHEETS for sale, TV 4/-, Radio 3/-; immediate delivery. S.A.E. with enquiries. Callers welcomed. **SULTAN RADIO**, 6, Mt. Ephraim Rd., Tunbridge Wells, Kent. (Phone: 22710.)

SERVICE SHEETS, Radio, T.V., 5,000 models. Lists 1/-. S.A.E. enquiries. **TELRAY**, 11, Maudland Bk., Preston.

SERVICE SHEETS for sale, all types, from 1/- each. Also Radio, Television Books. Lists free. 100 Television Service Sheets, covering 330 popular models, 18/6. **HAMILTON RADIO**, 237, Sedlescombe Rd. N., Hastings.

SERVICE SHEETS.—We have the largest stock of Radio and TV Service Sheets in the country for sale at 4/- ea. and for hire. Why tolerate delay in obtaining Service Sheets when we will despatch by return? List 1/-. S.A.E. with enquiries, please. **S. P. DISTRIBUTORS**, 11, Old Bond St., London, W.1.

SERVICE SHEETS

RADIO and Television
Over 100,000. S.A.E. for List.
Large stock of obsolete Radio and Television Valves.

JOHN GILBERT RADIO,
20, Extension
Shepherd's Bush Market, London, W.12
SHE 3052

SITUATIONS VACANT**BRITISH RELAY WIRELESS LTD.**

Due to rapid continuing expansion in the field of sound and television relay the services of competent **ENGINEERS** are required for varied and interesting work, comprising:

TEST, ALIGNMENT, CALIBRATION AND MAINTENANCE

of a wide range of equipment for **TELEVISION TRANSMISSION** and **DISTRIBUTION**

Opportunities are offered for employment on experimental work.

Applicants who should be competent in the use of electronic measuring instruments are invited to write, stating age, experience and qualifications to:

B.R.W. LTD.

1-7, Croft St., Bermondsey, S.E.8.

CITY AND GUILDS (Electrical, etc.), on "No pass—no fee" terms. Over 95% successes. For details of Electrical Engineering, Applied Electronics, Automation, etc., send for our 148-page handbook, free and post free. **B.I.E.T.** (Dept. 242a), 29, Wright's Lane, London, W.8.

A.M.I.Mech.E., A.M.Brit.I.R.E., City and Guilds, G.C.E., etc., bring high pay and security. "No pass—no fee" terms. Over 95% successes. For details of exams and courses in all branches of Engineering, Building, Electronics, etc., write for 148-page handbook, free. **B.I.E.T.** (Dept. 242B), London, W.8.

THERE IS A NATIONAL SHORTAGE of Mercantile Radio Officers. Why not make Communications your career? You can be assured of a sea-going appointment after qualifying at the School of Marine Radio and Radar (A.S.T.), Hamble, Southampton. For details apply to the **COMMANDANT**.

T/V AND RADIO, A.M.Brit.I.R.E., City and Guilds, R.T.E.B., Cert., etc. on "No pass—no fee" terms. Over 95% successes. For details of Exams and Courses (including practical apparatus) in all branches of Radio, T/V and Electronics, write for 148-page handbook, free. **B.I.E.T.** (Dept. 242G), 29, Wright's Lane, London, W.8.

RADIO

AT LAST VHF/FM/AM for the family man. Astonishing De Luxe VHF/FM Radio offer. Merging of world famous Co., enables us to offer £28 DE LUXE VHF/FM/AM Radios for £15.10.0. Factory Fresh, Maker's Guarantee, extra thrilling quality. All features including Ferrite aeriels. Our satisfaction guarantee or purchase price refunded. **AC/DC 200/250v.** Smaller radio with VHF/FM/AM, £13.10.0 originally £21, or Miniature Superhet two-wave model £8.10.0.

TOMLIN ELECTRICAL,
127, Brockley Rise, London, S.E.23



The Royal Air Force

PILOTS, NAVIGATORS AND AIR ELECTRONICS OFFICERS COMMISSIONS IN THE GENERAL DUTIES BRANCH

Vacancies now exist for fit young men of character and good education and who are capable of taking responsibility, to train as pilots, navigators or air electronics officers in the general duties branch of the Royal Air Force.

Methods of Entry

University Entry—University graduates may enter on permanent or four-year short-service commissions. Permanent commissions carry an ante-date. University students may be accepted subject to graduation. Maximum age limit 25.

Direct Commissions—The direct commission scheme offers the choice of a permanent career leading to a pension, or a twelve-year commission with the option of leaving after eight years. Age limits: 17½ to 25.

Short-Service Commissions—The short-service commission is for

five years and there are opportunities for transfer to either form of direct commission. Age limits: 17½ to 21.

Pay and Gratuities—Pay is high and terminal gratuities are generous. For example, a Flight Lieutenant of 25 can earn, with full allowances, nearly £1,700 a year. The tax-free gratuity paid at the end of a twelve-year commission is £4,000.

Write for further details, stating age and education, and the method of entry in which you are interested, to the Air Ministry (PW562b), Adastral House, London, W.C.1.

EDUCATIONAL

WIRELESS. See the world as a Radio Officer in the Merchant Navy; short training period; low fees; scholarships, etc., available. Boarding and Day students. Stamp for prospectus. **WIRELESS COLLEGE,** Colwyn Bay.

**Bristol Education Committee
THE COLLEGE OF
TECHNOLOGY**

School of Marine Radio and Radar

The above Radio School, formerly the Hamble School of Marine Radio and Radar, will open at the College of Technology in May, 1960, and will offer

Courses leading to the 1st and 2nd Class P.M.G. Certificates for Marine Radio Officers, Radar Maintenance Courses and Pre-Sea courses for qualified officers.

Further details may be obtained from the Registrar, College of Technology, Ashley Down, Bristol, 7.

THERE IS A NATIONAL SHORTAGE of Mercantile Radio Officers. Why not make Communications your career? You can be assured of a sea-going appointment after qualifying at the School of Marine Radio and Radar (A.S.T.). Hamble, Southampton. For details apply to the **COMMANDANT.**

MATHEMATICS FOR G.C.E. Year's course 5/- per lesson. Key to Radio/TV. 12/6. Write: **TUTORIALS,** 220, Buchanan St., Glasgow.

INCORPORATED Practical Radio Engineers home study courses of radio and TV engineering are recognised by the trade as outstanding and authoritative. Moderate fees to a limited number of students only. Syllabus of Instructional Text is free. The "Practical Radio Engineer" journal, sample copy 2/-. 6,000 Alignment Peaks for Superhets, 5/9. Membership and Entry Conditions booklet 1/-, all post free from the **SECRETARY, P.R.E.,** 20, Fairfield Road, London, N.8.

★ **LEARN** ★
**RADIO & TV
SERVICING**
for your OWN
BUSINESS/HOBBY

● by a new exciting no-maths system, using practical equipment, recently introduced to this country.

FREE Brochure from:—

RADIOSTRUCTOR
DEPT. G77, 46, MARKET PLACE,
READING, BERKS. 1/60

BOOKS & PUBLICATIONS

BOOKS for C. and G. exams: Tels. Principles A and B, 9/6; Tels. (Principles), 1 and 2, 10/6; Maths for Tels., 1, 7/-; Maths for Tels., 2, 5/-, all post free. **RIDDIFORD,** 384, Tilehurst Rd., Reading.

MISCELLANEOUS

PHOTOELECTRIC PARKING LIGHT SWITCH will switch your lights on at dusk, off at dawn, automatically, while you are at work, in bed, or away from home. Controlled by light. Transistorised. Negligible consumption (.008amp.). Protect your car at night. Avoid accidents. fines. Save your battery. Kit of parts, 52/6; built and tested. 57/6; instructions only, 1/-, Pat. applied for. "ST. JOHN'S RADIO." 156, St. John's Hill, S.W.11. (BAT 9838.)

MAKING YOUR OWN TELESCOPES. Enlargers. Projectors. Viewers. Microscopes. Episcopes, etc. then your booklets "How to Use Ex-Gov. Lenses and Prisms," Nos. 1 and 2 at 2/6 ea., will show you easily and quickly how to achieve the finest possible results at lowest possible cost. The most comprehensive lists of optical and scientific equipment in the British Isles is free for s.a.e. **H. W. ENGLISH,** Rayleigh Rd., Hutton, Brentwood, Essex.

LOUDSPEAKERS, Electric Clocks and Shavers repaired promptly. **MCDL LOUDSPEAKER SERVICE,** Sipton on Cherwell, Oxford.

1-Finger Pianist

Build your own electronic keyboard and play everything! Send for free leaflet. Guitar, cello, flute and trumpet are all easy. Write now.

**C & S, 20 Maude Street,
Darlington, Co. Durham.**

New HI-FI Publications

JASON FM TUNERS 2s. 6d.
MULLARD AMPLIFIER MANUAL 8s. 6d.
MULLARD TAPE PRE-AMP. C 2s. 6d.
QUALITY AMPLIFIERS 7 designs 4s. 6d.

52-page Catalogue available on request.

J. T. FILMER 82, DARTFORD ROAD
DARTFORD, KENT.

Tel. Dartford 4057

TRANSISTOR SUPPLIES

Teletron Transidyne Pocket Transistor Set. All parts £11/- (Post 2/6)
Mini 7 Transistor Pocket Receiver. Complete kit, £9/2/6 (post 2/6).

Red Spots, 5/-; White Spots, 7/6; Green/Yell., 5/9; Ediswan XB104, 8/6; XA104, 16/-; OC70, 14/-; OC71, 14/-; OC72, 17/-; OC44, 26/-.

Moving Coil Earpiece (use as miniature speaker), 5/-.

Super Coax, 6d. yard. Var. Air Condenser, 365 pf. 3/- Subminiature Electrolytics (15 vol.), 2, 5, 8, 25, 50 μ f., 3/- Submin. Transformer Interstage, 5-1, 8-1, 7/6.

Power Packs: 200/250 v. in.; 300 v. 200 mA. and 12 v. A.C. out., 50/- (carr. 7/6). 6 v. D.C. in., 120 v. 60 mA. (vibrator) out., 17/6 (carr. 5/-). Receiver 78, 35/- (carr. 5/-).

TERMS.—Cash with order. Post extra. **Morco Reflex Circuit**—Best 2 Transistor. Send 8d. stamps for our Notes.

**MORCO EXPERIMENTAL
SUPPLIES**

8 & 10, Granville Street, Sheffield, 2
Tel.: 27461

EDDY'S (Nottm.) LTD.
172 ALFRETON ROAD,
NOTTINGHAM

NIFE ACCUMULATORS. Midget Single Unit Size 3 x 2 1/2 x 1/2 in., 7 am. hrs., 1/11. Post 1/6.

LUXEMBOURG EXPANDING AERIALS. Compact and easy to fit. No technical knowledge required. Greatly improves reception. 3/11. Post 6d.

ACOS CRYSTAL PICK-UPS. Turnover head (2 sapphire styli). 29/11. Post 2/6.

HEADPHONE CORDS. High Quality 6ft., 1/11 pair. Post 6d.

SPEAKER GOLD GRILLE. 6 1/2 in. x 4 in., 1/- each. Post 6d.

VIBRATORS. 12 v. 4 pin, 4/11 each. Post 1/-.

MORSE TAPPERS. Plated Contacts. Adjustable gaps. Heavy Duty. 3/6. Post 9d.

DIMMER SWITCHES. Ideal for train speed regulators. 1/11. Post 9d.

SPECIAL OFFER

GRAM AMPLIFIERS. High Sensitivity 3 watts output. Separate volume and tone controls. Printed Circuit. 59/11. Post 4/- Fully Guaranteed. Size 8 x 2 1/2 in. Max. Height, 5 in.

MINIMOTORS. For model makers. High Speed 1 1/2 volts to 6 volts. 8/6. Post 1/-.

THROAT MIKES. 1/- Post 6d. Could be used for electrifying musical instruments, etc.

NEON MAINSTESTER / SCREW-DRIVERS. 3/11 each. Post 9d.

GERMANIUM DIODES. 1/- each; 9/6 doz. Post 4d.

DYNAMOTORS. 200VDC to 12VDC. Ideal for train sets, etc. 19/11. Post 2/6.

ACOS CRYSTAL MIKES. Type MIC/35 1 25/11. Post and Packing 2/6.

CRYSTAL SETS. Complete 2-wave bands. High gain. Good quality. 19/11. Post and Packing 2/-.

CONDENSERS. Tubular Wire End. (Not ex-Govt.) 8 mfd. 450 v., 1/9; 8-8 mfd. 450 v., 2/6; 16 mfd. 450 v., 2/9; 16-8 mfd. 450 v., 4/-; 16-16 mfd. 450 v., 3/9; 32-32 mfd. 350 v., 4/-; post 1/-.

TRANSISTORS SUB MINATURE CONDENSERS. 1.6 mfd., 5 mfd., 8 mfd., 10 mfd., 16 mfd., 25 mfd., 32 mfd. 2/3 each Post 6d.

RECTIFIERS FOR BATTERY CHARGERS. 12 v. 1 amp. 4/3; 12 v. 2 amp., 7/-; 12 v. 4 amp., 12/- Post and Packing 1/6.

ALL ABOVE ARE NEW AND GUARANTEED

SURPLUS NEW AND GUARANTEED VALVES. ALL TESTED BEFORE DESPATCH.

AZ1	12/6	U31	7/9	6V6GT	6/6
DAF96	8/6	U35	9/6	6X4	6/-
DF96	8/6	UBC41	8/3	6X5GT	6/6
HD63	7/6	IDS	9/6	7C5	7/6
DK96	8/6	IL4	3/9	7C6	7/6
DL96	8/6	IS5	6/6	7S7	9/6
DM70	7/6	IT4	4/9	7Y4	7/6
EB91	4/-	5Z4G	9/-	10F1	9/6
ECC81	6/-	6AG5	5/-	12A6	6/6
ECC84	9/-	6BB8	2/11	12AH7	5/6
ECC85	8/6	6BA6	6/6	25A6G	8/-
ECL82	11/-	6BJ6	6/6	25L6GT	9/-
EF36	2/6	6C4	3/6	25Z4G	7/9
EF37	4/-	6F33	5/6	35W4	6/9
EF42	8/6	6J5G	2/6	807(B)	3/9
EF50	1/11	6J5GT	3/6	954	1/6
EF91	4/-	6J5M	4/3	955	3/11
EL84	8/3	6K7G	2/3	956	2/11
GTIC	7/6	6K8G	6/6	9001	4/6
KTW61	5/6	6P28	9/6	9004	4/6
PY31	8/6	6SN7GT	4/9	9006	4/-
PY80	7/-				


Any parcel insured against damage in transit for only 6d. extra per order. All uninsured parcels at customer's risk. Postage and Packing 6d. per valve. Over £3 Free. C.O.D. Charge 3/- extra. S.A.E. with enquiries. C.O.D. or C.W.O. only

The Heart of a good tape recorder is its DECK!

For the enthusiast who loves to experiment — who wishes to build up his own tape recording unit—to construct into his own furniture or to add to existing hi-fi equipment, the Brenell Mk. 5 Deck presents truly remarkable value. Its versatility of application has firmly established the Brenell in the hi-fi market as a general purpose deck with immense advantages. Superbly made, it is conclusive evidence of the skillful design for which Brenell are noted.

Brenell

Performance is true-to-life performance

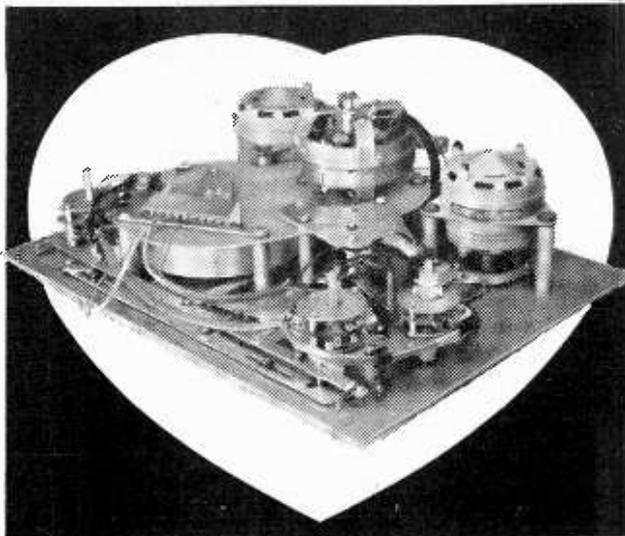

Four recording speeds: $1\frac{1}{2}$, $3\frac{1}{2}$, $7\frac{1}{2}$ and 15 i.p.s. Permits use of 8 $\frac{1}{2}$ in. reels (3,600ft. of D.P. tape at $1\frac{1}{2}$ i.p.s. plays over 12 hours); three independent motors (B.T.H.). Special foolproof interlocking controls. Instant stop without spillage. Pause control. Digital rev. counter. Fast rewind (1,200ft. in 45 secs.). Tape Deck with provision for extra heads. 28 Gns. Extra erase heads, £2.4.0. inc. pressure pads. Extra rec./playback heads (upper or lower track), £2.4.0. inc. pressure pads. Stacked stereo rec./playback heads, £10 inc. pressure pads. Also rec./playback amplifier with power unit, £24.

BRENELL ENGINEERING CO. LTD., 1a, Doughty Street, London, W.C.1. Tel. CHA 5809, HOL 7358.

H.A.C. SHORT-WAVE EQUIPMENT AND SHORT WAVE KITS

Famous for over 25 years for S.W. Receivers and Kits of Quality.

H.A.C. were the original suppliers of SHORT-WAVE RECEIVER KITS for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, Hams, etc.

Improved designs with Denco coils:
One-valve Kit, Model "C", Price 25/-
Two-valve Kit, Model "E", Price 50/-
New Addition: Model "K" Receiver.
Super sensitive "All Dry" Receiver.
Special incl. price. Complete Kit, 77/-

All kits complete with all components, accessories and full instructions. Before ordering, call and inspect a demonstration receiver, or send for descriptive catalogue and order form.

POST THIS COUPON NOW!

"H.A.C." SHORT-WAVE PRODUCTS

(Dept. TH), 11, Old Bond Street, London, W.1.

Please send me FREE and without obligation your 1960 literature.

NAME _____

ADDRESS _____

REDUCED PRICES HIGH GAIN TRANSISTORS

BRAND NEW AND GUARANTEED

Red/Yell. (6 mc/s), 8/6. White Spt. (4 mc/s), 7/6. Yell./Grn., 6/6 (Matched pr. 250 mW), 13/6. Red Spt., 6/6.

MINIATURE AMPLIFIER

3-stage 4 TRANSISTORS, p.p. output, 250 mW, for 2-3 ohm speaker. Ideal for Gram., Radio, etc. High gain. Excellent quality, uses small 6 v. batt. Easy assembly. Full kit, matched Ediswan Transistors, complete instructions. Brand New Components, 59/6, p. & p. 1/6. Circuit diagram assembly details, 2/6.

SUB-MIN. ELECTROLYTICS, 2, 4, 8, 25, 50, 100 mfd., 15 v.w., 2/9.

MIDGET RESISTORS. $\frac{1}{2}$ wt. Approved values, 3 1/2.

MIDGET VOL. CONTROLS. Standard values, 2/10.

MIDGET ACCUMULATORS. About $1\frac{1}{2}$ in. x $\frac{1}{2}$ in. x $\frac{1}{2}$ in., 2 v. .27 amp./hrs. Ideal for radio, models, etc. 3/-.

PLASTIC BOXES with hinged lids: $4\frac{1}{2}$ in. x 3 in. x $1\frac{1}{2}$ in., 2/6, p.p. 1/-; 5 1/2 in. x 3 1/2 in. x $1\frac{1}{2}$ in., 3/3, p.p. 1/-; $7\frac{1}{2}$ in. x 3 1/2 in. x $1\frac{1}{2}$ in., 4/9, p.p. 1/3.


PERSPEX. 6 in. x 3 in. x $\frac{1}{2}$ in. Ivory, 1/-, p.p. 6d.

Please include sufficient postage when ordering. Send 3d. stamp for list of New Components.

BURLAND RADIO ACCESSORIES
G3IRE Est. 1947 G3JZ
ANN'S PLACE, SOUTHWICK, SUSSEX

CABINETS & HI-FI EQUIPMENT

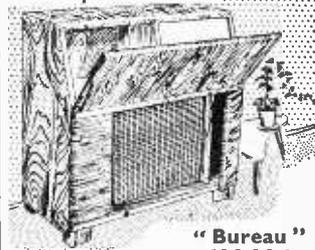We can supply any Cabinet to your own specification.



"Bureau"
£16.16.0

This is only one example taken from our extensive range of stock cabinets. Write for our NEW 24 page fully illustrated catalogue on: THE LARGEST RANGE OF CABINETS IN THE COUNTRY.

Equipment is also our speciality and we now offer, in a novel book form: A NEW EQUIPMENT COMPARATOR illustrating our range of radio chassis, speakers, tape decks, single players and autochangers. SEND TODAY for a copy of these two books, which are absolutely FREE.


LEWIS RADIO

120 (PW160) Green Lanes, Palmers Green
London, N.13. BOWes Park 1155/6
(Nr. The Cock Tavern)

MAXI-Q
REGD.

"WE COULD BLIND YOU WITH SCIENCE"
on the technical superiority of our coils but
are sure you would prefer us just to say
"WE GUARANTEE THEM"!

Coverage from 3.8 to 2,000 metres in 7 ranges—Each coil is packed in an aluminium container which may be used as a screening can for the coil itself—Brass threaded adjustable iron cores—Colour coded moulded polystyrene formers—Chassis/Plug-in Technical Bulletin, DTB.1 1/6—Dual Purpose Technical Bulletin, DTB.4 1/6—Colour Code Identified Coils: BLUE Signal Grid Coil with Aerial Coupling winding—YELLOW Signal Grid Coil with intervalve coupling winding—GREEN Grid Coil with reaction and coupling windings—RED Superhet Oscillator for I.F. of 465 Kc/s—White Superhet Oscillator for 1.6 Mc/s. Prices range from 4/1 to 4/9 each. Five Colour Glass Scale, Back Plate, Pointer, Pulleys and Cord for use with 315/pF tuning condensers. Coverage (1) 150-400 Kc/s.; (2) 530-1,600 Kc/s.; (3) 1.5-4 Mc/s.; (4) 4-12 Mc/s.; (5) 10-30 Mc/s.; Price 15/-.

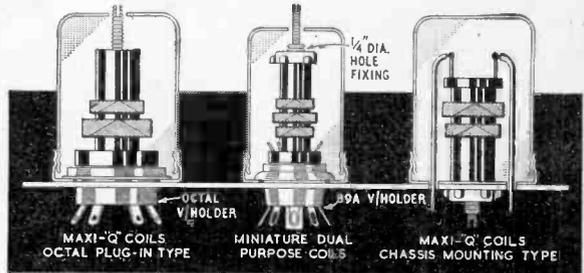

GENERAL CATALOGUE covering full range of components send 1/4d. in stamps or P.O. PLEASE SEND S.A.E. WITH ALL ENQUIRIES

DENCO (CLACTON) LTD. (Dept. P.W.), 357/9 Old Road, Clacton-on-Sea, Essex

LYONS RADIO LTD.

Dept. M.P., 3, GOLDHAWK ROAD, SHEPHERD'S BUSH, LONDON, W.12

Telephone: SHEpherd's Bush 1729

BEAT FREQUENCY OSCILLATORS.—These instruments by Purzehill Laboratories have a continuously variable frequency range from 0/10 Kc/s. with separate 50 cycle check and set zero control. Output impedance 10 and 600 ohms monitored by a two range (0.5 v. and 0/50 v.) meter. Operate from 100/120 v. or 200/250 v. A.C. mains. In good condition and working order. PRICE ONLY £9.10.0. carriage 10/-.

EARPHONE-INTERCOM.—Single earphones which also serve as microphones. Two connected together make an amazingly simple but efficient means of two-way communication. Self energising, no batteries required. Dozens of uses in the Home, Factory, Office, etc. and provide hours of fun for the youngsters. Ideal gift. Supplied ready for use connected with 36ft. twin flex (extra flex plus 3rd. yard) ready for immediate use. PRICE ONLY 9/6. post 1/6.

COMBINED AUDIO AMPLIFIERS AND SPEAKER.—Polished in attractive case with finely polished veneer front with decorative grille. Fitted with tone control and combined volume control on/off switch. Suitable for either magnetic or crystal type pick-up. Output 2.3 watts. For 220/240 v. A.C. mains. ready to switch on. PRICE ONLY £5.10.0. post 3/6.

EXTENSION SPEAKERS.—Few only 5in. dia. m/c. speakers fitted in handsome cabinet with polished walnut veneer. PRICE ONLY 2/6. post 2/6.

VALVE BARGAINS.—A/C/P. ARP12, EC54. all at 3/6 each. 1L4, 6C5, 6AC7. all at 4/- each. FX25, 9/6 each matched pair. 18-, EF50-Red 3 for 7/6, Sylvania 3 for 9/-. Post 6d. per valve.

VALVES

SAME DAY SERVICE

NEW! TESTED! GUARANTEED!

SETS 1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DK92, DL92, DL94, any 4 for 25/-, DAF96, DF96, DK96, DL96 4 for 32/6, 6K7G, 6K8G, 6Q7G, 6V6G, 6X5G or 5Y3G 5 for 27/-

1A7GT 12-	6L18 12/3	2526GT 9/6	EBF89 8/9	EZ80 6/3	TH41 16/6
1D5 9/6	6P25 9-	30C1 7/8	EBL21 20/6	EZ81 7/6	U25 11/6
1H5GT 10/-	6Q7G 7/6	30P1 7/9	ECB1 7/6	FW41500 9/6	U29 12/6
1N5GT 10/-	6Q7GT 9/6	35L8GT 10-	ECC82 6/6	GZ32 9/-	U60 7/6
1R5 6/9	6SL7GT 7/-	35Z4GT 6/6	ECC83 7/-	KT33C 7/-	U52 5/6
1S5 9-	6SN7GT 5/8	35Z5GT 8/6	ECC84 8/9	KT41 14/6	U76 6/6
1T4 5/3	6U4GT 11/-	43 12/6	ECC85 9/6	KT61 10/-	U78 6/6
1U5 6/6	6V6GT 7/6	50CD6G 28/9	ECF80 11/6	KT73 6/6	UABC90 8/9
3A5 10/6	6X4 6/9	50L6GT 9/9	ECF82 10-	KT71 12/6	UAF42 9/6
3Q4 8/6	6X5GT 6/-	AZ31 9/6	ECH21 20/6	NH4 6/-	UBC41 8/6
3S4 6/9	7B7 8/-	B36 15/6	ECH35 6/9	MU14 9/-	UBF80 9/6
3V4 7/6	7C5 8/-	CL33 13/6	ECH42 9/6	MX40 12/6	UBF89 8/6
5U4G 5/3	7C6 8/-	DAC32 10-	ECH81 8/6	N15 8/6	UBL21 20/6
5V4G 10/6	7H7 8/-	DAF91 8/3	ECL80 8/6	N152 10/6	UCB94 12/9
5Y3GT 7/3	7S7 8/9	DAF96 8/6	ECL82 10-	PCC84 7/9	UC85 8/6
5Z4G 9/6	7Y4 8/6	DC90 10/6	EF39 5/6	PCC89 14/-	UC89 14/-
6A15 3/9	10C1 14/6	DF31 10/-	EF41 8/6	PCF80 7/3	UCH21 20/6
6AM5 5/-	10C2 17/6	DF91 5/8	EF42 11/6	PCF82 9/3	UCH32 9/6
6AM6 3/9	10P1 15/6	DF96 8/6	EF50 6/6	ECL82 9/3	UCH81 9/6
6AQ5 7/9	10F9 10/6	DH76 6/6	EF85 7/6	PCL83 12/6	UCL82 11/6
6A76 7/3	10P13 21/-	DH77 7/3	EF86 11/6	PCL84 7/9	UCL83 14/3
6BA6 6/-	12A18 10/6	DK32 12/-	EF89 8/-	PENA4 11/-	UF41 9/3
6BE6 6/-	12A77 7/6	DK40 14/-	EF91 3/9	PEN36C 9/6	UF42 8/6
6BH6 6/9	12A77 7/6	DK92 12/6	EF92 4/6	PEN45 8/-	UF89 7/6
6B/6 6/-	12A77 7/6	DK96 8/6	EL30 10-	PEN46 5/6	UL1 8/-
6BR7 10/6	12A77 7/6	DL33 10-	EL41 9/-	PL36 13/-	UL45 21/6
6B/7 6/6	12BA6 8/-	DL35 12/3	EL42 10/6	PL38 14/6	UL84 8/-
6CD6G 26/9	12K7GT 6/6	DL32 12/6	EL43 10/6	PL81 10/-	URIC 8/-
6F1 14/6	12K8GT 12/6	DL32 12/6	EL82 8/6	PL82 8/6	UY1N 12/6
6FG9 6/6	12Q7GT 6/6	DL94 9/6	EM34 8/6	PL83 8/6	UY21 14/-
6F13 12/6	1223 7/6	DL96 8/6	EM80 9/6	PY32 11/6	UY41 7/-
6F14 17/6	1457 16/9	EAB80 7/9	EM81 9/-	PY80 7/6	UY85 6/9
6K7C 3/9	18AQ5 7/6	EAF42 9/6	EM84 10/-	PY81 6/9	VP4B 9/6
6K7GT 6/-	20P2 17/6	EBC31 3/9	EY51 9/6	PY82 7/-	VP41 6/6
6K8G 6/9	20L1 17/6	EBC33 7/-	EY86 9/-	PY83 8/-	W76 6/6
6L1 16/9	25A6G 11/-	EBC41 8/6	EZ40 7/6	PZ30 17/-	W77 4/6
	25Z4G 9/-	EBF80 8/-	EZ41 7/6	SP61 3/6	Z77 3/9

READERS RADIO
24, COLBERG PLACE, STAMFORD HILL,
LONDON, N.16. STA. 4587

Post 6d. per valve extra.
Any Parcel insured Against Damage in Transit.
Any C.O.D. Parcel 2/6 extra.

Visit the City's popular acoustically designed

HI-FI Centre

COME AND HEAR THE LEADING MAKES IN
AMPLIFIERS AND TUNERS

AMPLIFIERS BY	V.H.F. TUNERS	HI-FI SPEAKERS
VERDIK	BY	BY
ARMSTRONG	ARMSTRONG	GOODMANS
ROGERS	LEAK	PLESSEY
DULCI	QUAD	WHARDEDALE
GOODSELL	T.S.L.	W.B.
QUAD	DULCI	T.S.L.
LEAK	GOODSELL	G.E.C.
W.B., etc.	ROGERS, etc.	LORENZ, etc.

LOOK AT THIS AMAZING OFFER
IDEAL AS XMAS GIFT

THE POCKET TRANSISTOR SET THAT IS PROVING
A REAL WINNER

6 Transistor Plus Diode Pocket Superhet Radio

Easy to build, using 6 Mullard transistors: OC44, OC45(2), OC71, matched pair OC72, OA70. Medium and long wave bands. Printed circuit. Built-in HiQ Ferrite Aerial Push-pull output. 150 ohms 3in. loud-speaker. Circuit and layout diagram. Low consumption. Power output 150 M.W. Sensitivity—1MV for 50 MV output. Circuit line up: mixer stage, 2 I.F. stages, Germanium detector, AF driver stage and push-pull output.

ALL COMPONENTS COMPLETE LESS CABINET AND
BATTERIES AT THE SPECIAL PRICE OF
£7-19-6

Post and packing 2/6. Cabinet available in parts to be assembled, comprising cabinet, tuning knob, switch knob, escutcheon, coloured Rexine, aerial and battery bkts. and battery. Price 18/6. Post & Pkg. 1/6.



ANOTHER SNIP OFFER

SLIGHTLY SOILED
AT THE
LOW PRICE
29/6

and 4/-
post and packing.

Surplus to manufacturer's requirements, well made 2-tone colour portable player cabinets, will take non-auto player, Amplifier and 4in. or 5in. speaker. The above portable cabinet,

B.S.R. 4-speed player and Acos t/over r/up, 2-watt amplifier and 6 x 4 elliptical speaker making an ideal portable player at the special price of £8/5/- plus 7/6 Post & Pkg.

EVERYBODY IS CLAMOURING FOR
THE 2 COSSOR KIT BARGAINS

The new Cossor 6 valve FM receiver kit comprising all components including 6 valves, Goodmans 10 x 6 speaker, printed circuit chassis, easy to follow instructions. Even to nuts and bolts. Manufacturer's price 15 gns. Our price £8/19/6 complete. P. & P. 2/6. Cossor 3-watt printed circuit amplifier. All components mounted on printed circuit chassis. 3 Cossor valves, 10 x 6 speaker, 4in. tweeter, and all components including easy to follow instructions. Cossor's price £9/15/-. Our price complete, £5/19/6. P. & P. 3/6.

Electronics Ltd

(FLEET ST.)

Dept. B.

152/3 Fleet St., London, E.C.4. Tel. FLE 2833
Business Hours: Weekdays, 9-6. Saturdays, 9-1.

Special Bargain Offers

FERRANTI TESTMETER TYPE D. An extremely compact self-contained multimeter. Volts 0 to 30, 150, 600 AC/DC, with additional 0.3 v. DC, and 0-15 v. AC ranges; milliamps 0 to 7.5, 30, 150 and 750 DC; ohms 0-25 K Ω . Accuracy BSS first grade. Knife-edge pointer and clearly calibrated 2 1/2 in. scale. 500 Ω /volt. With leads, prods, battery and instructions. In fitted velvet-lined 4 x 7 x 3 in. case. Brand new condition, perfect working order. 52/6. post 2/6.

GRAMOPHONE MOTORS. A.C. mains. Garrard AC-6, 78 r.p.m. For replacements, BRAND NEW. Boxed, 35/-, Post 2/6.
VITAVOX PRESSURE UNITS, TYPE N. 20 watts. P.M. Heavy duty. BRAND NEW. Boxed, 89/6, carr. 5/6.
Q5'er. (BC-453 Command Receiver). Covers 190-550 Kc/s (IF 85 Kc/s). Ideal for double superhet conversion, etc. Supplied BRAND NEW in original cartons, with all 6 valves and circuit. 89/6. Post 3/6.
R-109 RECEIVERS. 8 valve superhet using 5 ARF12's and 3 ARB's. 1.8-8.5 Mc/s (34-108 m). Internal 3 1/2 in. speaker and 6 v. vibrator pack (takes 11 amps). In metal case 13 x 12 x 1 1/2 in. Aerial tested. Good condition. Circuit supplied. 79/6. carr. 7/6.
R-1155-B. with latest drive, first-class condition. 27.19.6.
R-1155-L. £12.19.6. Power Packs, 26.10.0. S.A.E. details.
CR100 COMMUNICATION RECEIVERS. Covers 60 kc/s—30 Mc/s in 6 bands, 11 valves, 2 R.F. and 3 I.F. stages. Crystal gate. BFO, etc. Ready for 200-250 v. A.C. mains 2 1/2 watts output for 3 ohms speaker. SUPERB CONDITION AND OUTSTANDING PERFORMANCE for ONLY £21. S.A.E. for illustrated details.
HRO COMMUNICATION RECEIVERS. complete with 9 coils. From 18 gns. S.A.E. for full particulars.

RCA AR-88 SPEAKERS. 3 Ω 8in. P.M. speaker in heavy gauge black cracked steel cabinet 11 x 10 x 6in., with rubber feet. A SUPER QUALITY unit. BRAND NEW, for ONLY 45/-, Post 3/6.

MINIATURE 373 I.F. STRIPS.—For P.M. tuner described in P.W. With 3 of EF91, 2 of EF92 and EB91. A fresh release enables us to offer these once again. BRAND NEW with circuit and full P.W. Reprint, 35/-, OR less valves, 12/6. Post 6/6. 2/6.
MOVING COIL PHONES.—Finest quality Canadian, with Chamois ear-muffs and leather-covered headband. With lead and jack plug. Noise excluding, supremely comfortable. 19/6, post 1/6.
R.F. UNITS. R.F.25, 17/6; R.F.27, 22/6. Good condition. Post each, 3/6.

PLEASE ADD POSTAGE OR CARRIAGE ON ALL ITEMS

CHARLES BRITAIN (RADIO) LTD.

11 Upper Saint Martin's Lane, London, W.C.2

TEmpLe Bar 0545

Shop Hours 9-6 p.m., (9-1 p.m. Thursday). Open All Day Saturday

A television course for you to study at home

Entirely new! Practical!
Bang up to date!

THE FAMOUS BENNETT COLLEGE OFFERS YOU THIS

An entirely new course of study based upon up-to-date techniques has now been prepared by The Bennett College.

The course is non-mathematical, and contains clear diagrams, starting from the very beginning (even including the basic principles of sound radio receivers, if desired) and covering all that you need to know!

This is what you've been looking for! A home-study course includes: production

of the signal, scanning and reproduction of picture from signal. Aerials, types and purpose. The cathode-ray tube. Time-base oscillators, and output circuits. Synchronisation. Video frequency amplifiers. The TV tuner, turret, incremental, etc. Television test gear. Television faults.

For more details, fill in the coupon below. Your studies cost little, the book you need is included in the cost.

-To THE BENNETT COLLEGE (Dept. A104/TV Sheffield)

Please send me details of the new
TELEVISION SERVICING COURSE

NAME _____

ADDRESS _____

AGE _____

G2AK: This Month's Bargains

VARIABLE CONDENSERS

All Brass with Ceramic End Plates and Ball Race Bearings. 50 pf., 5/9; 100 pf., 6/6; 160 pf., 7/6; 250 pf., 8/6; and 300 pf., 9/6. P. & P. 1/6. Designed for the S.W. constructor.

REPANCO MINIATURE COMPONENTS

Full Range in Stock.

VOLTMETERS. Dual range 0-5 V. and 0-100 V. M.C. 1,000 o.p.v. Ranges easily extended. With test probes and leads. Complete in carrying case, 6 1/2 in. x 5 in. x 2 1/2 in. **A GIFT at 25/- post free.**

HEADPHONES H.R. TYPE. 4,000 ohms., very sensitive. **ONLY 12/6** pr. P. & P. 1/6. C.L.R. Type (low res.), 8/6. P. & P. 1/6.

Absorption Wavemeters. 3.00 to 35.00 Mc/s in 3 switched bands, marked on scale. Complete with indicator bulb. **A MUST** for any Ham shack. **ONLY 17/6**, post free.

Rotary Converters. 6 v. input, 250 v., 125 mA. output. **ONLY 17/6**. P. & P. 3/-.

2 METER 5 ELEMENT BEAM. W.S. Yagi, complete in box with lin.-2 1/2 in. Masthead Bracket. **PRICE 49/-**, p. & p. 3/6.

SUPER LOW LOSS AERAXIAL CABLE, 1/8 per yd., p. & p. 1/6.

CHAS. H. YOUNG LTD.

THE COMPONENT SPECIALISTS

Dept. "P" 110, Dale End, Birmingham, 4. (CEN 1635)

(No C.O.D. under £1 please)

(By return Service)

12-VOLT RATCHET MOTORS (Impulse Motors), 5.75 ohms coil. 3 6 each, p.p. 1/-.

BZZERS. Model T Mk 1, 4/6 each, p.p. 1/6.

TR-1520 TRANSMITTER STRIPS. 115-145 mc/s, consisting of 4.86 mc/s auxiliary crystal oscillator CV-136. Balanced Modulator (mixing crystal channel frequency with 4.86 mc/s)—two CV-138. Doubler CV-136. Amplifier QV04-7. Power Amplifier TT-15, complete with valves, crystal and circuit diagram. 52/6, p.p. 3/6.

DFTFO. less valves, 7/6, p.p. 2/6.

VHF RECEIVER CHASSIS BC-624 (Part of SCR-522). Four crystal channel 100-156 mc/s, valves: RF stage 9003, Mixer 9003, three IF stages 12SG7, Det/AVC/Audio 12C8. 2nd Audio 12J5GT. Oscillator 12AH7GT, Harmonic Generator 9002. Harmonic Amplifier 9003, Audio Squelch—other section of 12AH7GT. High and Low Impedance Output. **PRICE** complete with valves and circuit, but without squelch relay, 25/-, p.p. 5/-.

PRICE, chassis only, less valves, 7/6, p.p. 3/6.

VHF TRANSMITTER CHASSIS BC-625. Speech Amplifier 6SS7, Push-pull Modulator 12A6, Oscillator 6G6G, 1st Harmonic Amplifier 12A6, 2nd Harmonic Amplifier 832, Power Amplifier 832, Power output 8 watts.

PRICE, complete with valves and circuit, 22/6, p.p. 5/-.

PRICE, chassis only, less valves, 7/6, p.p. 3/6.

CHOKES. PARMECO 5H .06A, 5/8; 2H .15A, 5/-; 1H .030A, 5/-; BENDIX 1.2H .45 ADC, 15 ohms, 5/6; p.p. 2/- per choke.

"C" SHAPED MAGNETS. 700 Gauss, Pole Faces 1 in. x 1 in., 10/6, p.p. 1/6.

POWER UNITS TYPE 234A. Input 230 v. AC mains. Output fully smoothed 180 to 270 v. DC at 80 mA. and 6.3 v. 4 A. A.C. Brand new. 59/6, pp. 10/-.

Z & I AERO SERVICES LTD.,

Callers only: 85 Tottenham Court Road, W.1 (near Goadge Street Station). Tel. LANGHAM 8403. Mail orders and all correspondence to: 14 South Wharf Road, London, W.2. Tel.: AMBASSADOR 0151/2.

be TRANSISTOR - WISE! be POCKET - WISE!

"RECO" MIDDY ONE TRANSISTOR KIT



(Medium and Long Waves or Medium and Short Waves). Size 4 1/2 x 3 1/2 x 1 1/2 in. Variable sensitivity control. High gain Vari Q Ferrite Rod Aerial. "Sonotone" Dynamic Earpiece. Months of listening pleasure from 1 1/2 volt pencil. Complete Kit with EDISWAN TRANSISTOR and easy build plans, 39/6 post free.

"RECO" SUPER SPECIAL THREE TRANSISTOR KIT

(Medium and Long Waves with two Short Wave Coils FREE).


Ferrite Rod Aerial. Variable Bias Sensitivity Control. B.A. Reproducer can be used for group listening in good reception areas, also makes a Super Personal Phone for Private Listening. Complete Kit with 3 EDISWAN TRANSISTORS and 4 1/2 volt Flashlamp battery, 67/6, p.p. 2/6.



"RECO" PUSH - PULL FOUR TRANSISTOR KIT

(Medium and Long Waves with two Short Wave Coils FREE).

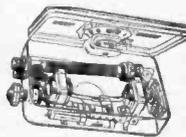(Case size, 6 1/2 x 4 1/2 x 1 1/2 in.) New improved circuit. 3 in. High Grade Moving Coil Speaker. Bias sensitivity volume control. Ferrite Rod Aerial. Gleaming Pale Blue Polystyrene Case with Contrasting Speaker Grille in Red. Complete Kit with 4, 1st grade EDISWAN TRANSISTORS and 3 volt battery, 45.3.6, p.p. 2/6.



"RECO" PUSH - PULL FIVE TRANSISTOR KIT

(Size 6 1/2 x 4 1/2 x 1 1/2 in.) Medium, Long Waves and Trawler Band. Indoors or outdoors this brilliant radio brings Home and Continental Stations to your finger tips. High Grade 3 in. Moving Coil Speaker. Regenerative receiver with Mullard OC45 R.F. Transistor and 4 EDISWAN TRANSISTORS. Push-Pull Output Stage. High Gain Ferrite Rod Aerial. Gleaming Pale Blue Polystyrene Case with Contrasting Speaker Grille in Red. Complete Kit with Pencil battery and easy build diagrams, etc., £6.9.6, p.p. 2/6.

A customer in Dorset writes—"Makes fine car radio."

"RECO" TRANSIGEN THREE TRANSISTOR KIT

(Case as PPS). (Medium, Long Waves and Trawler Band). Entirely self-contained no external aerial required. Fitted Super High Gain Ferrite Rod Aerial. R.F. Stage with Mullard OC45 Transistor followed by 2, 1st grade EDISWAN TRANSISTORS. On test: tuned in Home, Light, Third, Radio Luxembourg, A.F.N. and many others at good listening level. The Prototype was tested at approximately 50 miles from nearest transmitter. Complete Kit with Super B.A. Reproducer and 4 1/2 volt battery, 75/-, p.p. 2/6.



"RECO" TRANSIGEN TWO TRANSISTOR KIT

(Medium and Long Waves.) Regenerative circuit with Ferrite Rod Aerial. For good reception areas. Complete Kit with Personal Phone, EDISWAN TRANSISTORS and 3 volt battery, 59/6, p.p. 2/6.

AFTER SALES SERVICE.

Circuits and price list for the above kits, 2/6.

RADIO EXCHANGE CO.
27 HARPUR ST., BEDFORD Telephone 2367.

Closed 1 o/c Saturdays.

LASKY'S RADIO

Now Ready! The Finest Components Catalogue

for the home constructor.
100 pages, 8 1/2 x 5 1/2 in.,
copiously illustrated.

PRICE 2/- Post 6d.
With free Bargain Bulletin.

TAPE DECK OFFERS

Latest B.S.R. "MONARDECK", Single speed.
3 1/2 i.p.s. Takes 5 1/2 in. spools. Simple controls.
LASKY'S PRICE £9.19.6.

Latest COLLARO Studio Tape Transcriber, 3-spd.,
1 1/2, 3 1/2, 7 1/2 i.p.s. Fitted digital counter. Takes 7 in.
spools. Push-button controls. £15.19.6.


COLLARO MK. 4 Tape Transcriber, fitted digital
counter. Few only. £17.19.6.
Carriage and Insurance all Tape Decks, 12/6.

SPECIAL OFFER OF RECORDING TAPE
Famous make. P.V.C. base on latest type plastic spools.
Brand new, perfect and guaranteed. 1,200ft. on 7 in.
spool, 21/-.

GEVAERT L.P. PLASTIC TAPE, 1,700 ft. (7 in.
spool), 35/-; 850 ft. (5 in.), 18/6; 210 ft. (3 in.), 6/6;
Post on all above. 1 Spool 1/6. Orders over 60/- post
free.

4-SPEED MIXER AUTO-CHANGERS

Brand New
in makers'
cartons

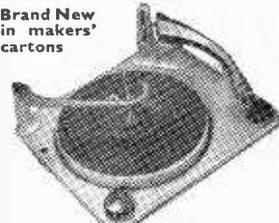

B.S.R. type UA8, complete with
latest "full-f" pick-up. £6.19.6.
Post 5/-.

Ditto. wired for STEREO and complete
with stereo cartridge, £7.19.6.

B.S.R. latest type UA12, wired for
STEREO and complete with stereo
cartridge. £8.19.6. Post 5/-.

Ditto, monaural cartridge, £7.19.6.

COLLARO, complete with Studio
crystal pick-up and sapphire stylus.
£7.19.6. Post 3/6.

GARRARD 4-spd. Auto-changers,
monaural, from £9.19.6.

Wired for STEREO and complete
with stereo cartridge, from £11.19.6.

A TRANSISTORISED RADIO WHICH CAN BE BUILT FOR

The remarkable "DIDEON"—a high
efficiency 2-stage receiver using crystal diode
detector and transistor in cascade. Covers
200-500 metres (medium wave). High gain
tuning coil gives great sensitivity. Novel
chassis shows pictorially all components and
connections. Price of complete parcel, including two U16
batteries, 25/10, post free.

EARPHONES. High Imp., 14/6. Low Imp., 7/6. Post 1/6.

ONLY
25/10

SINGLE PLAYERS

E.M.I. 4-spd., wired for
STEREO and fitted Apos
stereo t.o. cartridge.

£6.19.6.
Post 5/-.

COLLARO Junior 4-
spd. Motor and separate
pick-ups.

75/- Post free.

AN IDEAL GIFT FOR A BOY!

LASKY'S (HARROW ROAD) LTD.

Open all day Saturday. Early Closing Thurs. Mail Orders to Edgware Road, please.
42, TOTENTHAM COURT ROAD, W.1. 207, EDGWARE ROAD, LONDON. W.2.
Telephone: MUSeum 2605. PADdington 32712.

ALFRED PADGETT

40, MEADOW LANE, LEEDS, 11

Tel.: CLECKHEATON 2866

**SPECIAL OFFER OF RECONDITIONED
ULTRA TV SETS, MODEL \$15, A 14 in.
TV for all B.B.C. and I.T.V. Stations.**
Perfect results and sold with a money-back
guarantee. For £12 only. Tube in separate
carton. Carriage per B.R.S., 17/-.

RECEIVER TYPE 3645. The cleaned up
1355. Complete with 7 VR65, 1 VR91 valves.
With valves, 12/- Less valves, 6/- Carriage
per B.R.S., 7/6.

BUSH TV 24C 12 in. TV, B.B.C. and I.T.V.
Perfect pictures, £9, Carr., 17/-.

BUSH-PYE-ULTRA, 12 in. B.B.C. only.
Perfect pictures, £6, Carr., 17/-.

TWELVE INCH TV CHASSIS, complete
with L.O.T. focus coils, less valves, 15/-
Pye, Ultra, Plessey, Banner, Ekco, Marconi,
etc. Carriage per B.R.S., 5/- Chassis less
L.O.T. and focus coils, 5/- Carr. 4/-

SPEAKERS FROM TV SETS. All Perfect
-7 x 4, 10" : 8 in., 6/6 : 8 in., 6/6. Post 2/6.

KEY SWITCHES. 13. Post 1/3. 15/- per
doz., post free.

NEW CO-AX. T.V. CABLE. 6d. per yd.
20-50 yds. All post free.

RELAYS. 3000 Type, 2/- Post 1/3. 20/-
per doz., post free.

MAINS TRANSFORMER. Ex-R.A.F.
250 x 250 volts at 30 mA., £3 at 15 amp.
5 volts at 2 amp. 230 volt Prim. 6/6. Post 2/6.

NEW VALVES, POST FREE. U50, 6/-
U14, 5/-; DLS10, 1/8; KT63, 5/-; DH63, 5/-;
6K8, 5/-; 6C4, 2/6; 6J6, 2/6; 6AG5, 2/6
6AC7M, 2/-; 95S, 2/6; 9001, 1/3; 12SH7M,
2/-; 12S7M, 2/-; 12A6M, 4/-; 12H6M, 1/3;
2X2, 1/8.

EQUAL TO NEW TV VALVES. Three
Months' Guarantee. Post free. 10F1, 5/-
6P1, 3/-; 6AM6, 3/-; EF90, 3/- S.A.E. for
valve list.

TELETRON TAPEJAK



The first Transistorised Radio
Tuner, specially
designed for use
with Tape Rec-
orders. Con-
verts your Re-
corder to a high
quality Radio re-
ceiver. Direct
Recording on
Tape.

5" x 3 1/2" x 1 1/2"

- ★ High sensitivity.
- ★ Twin Tuned Circuits.
- ★ Pre-setting for M.W. Programmes.
- ★ Fixed Tuned for 1,500 M.
- ★ Switched programme selector.
- ★ Self powered.

Tested and ready for use.

£5.9.0. BATTERY EXTRA.

THE
TELETRON CO. LTD.,
112B, Station Rd., London, E.4
Phone: SIL. 0836.

BENSON'S BETTER BARGAINS

RELAYS. 2 heavy makes; 12 v. or 24 v. or
either 3/6 0 v. 2 breaks, 1/8; 2 makes, 2/6;
TX 1134 multi c/o. heavy contacts, 5/6; **DYNA-
MOTORS** : D.C. 6 v. to 250 v., 60 mA. 11/8
12 v. to 250 v., 60 mA. and 6 3/4 x 2.5 A. 11/8
(post 5/6); miniature 11 v. to 310/300 v. 40/30
mA. 10/8; **INDICATORS**, type 277, with 1 in.
C.R.F., 4/VR91, 2/VR92, 3/76 (p.p. 3/6);
Type 101, with VR330 (4 in. Blue, magnetic, Octal
base) and 9/VR91, 2/VR10; new cond.,
30/- (Post 3/6); Type 1, with VCRX263, 2/VR92,
-636, 1/VR96, 1/VEY1, 2/VE91, 3/VE91; with
RF EHT Generator and 28 kc/s. xtal. 5/-
(Rail 2/6); Type 97 with VCR517, 10 valves, 30/-
(Rail 7/6); CR100 Noise limiter assemblies, with
valve, 3/6; **NEW M.C. METERS**, 3 1/2 in. round
dial, 200 A., 70/-; 1000 A., 65/-; 1 mA., 55/-
- mA. (rectified), 45/-; 2 1/2 in., 1 mA., 22/6; 3 in.
100 mA., 200 mA., 300 mA., each, 8/8, 2 1/2 in. 20
v. A.C., 8/6; 3 in. 40 v. 8/6; 300 v. A.C. 2 1/2 in.,
15/-; **VIBRATORS**, Mallory 6534C 12 v.
4-pin, 7/6; 6 pin (5343), reversible, 7/8.
EL155B, good condit., tested, with handbook,
£7/10; (Rail 10/-) **SCR522** Modulation or Driver
Trans., either 7/8. **MORSE TRAINER SET** with
luzzer and key wired for 44 v. battery, 8/8.
DRIVES : slow-motion Admiralty 200; 1 ratio,
scaled 0-100, 5/6. **EL155 S.M.** N type, new,
20/8. **DYNAMOTORS** Type 2 A. Input 12 v.
Outputs 300 v., 230 mA., 150 v., 10 mA., 0 v. 5 A.
filtered, cased, 25/-; **TRANSFORMERS**, vibrator,
11 v. to 265 v., 7/8. **Morse Key**, covered with
luzzer, 5/8. **Potentiometers**, miniature wirewound,
6 1/2, 100 0, 300 0, 1k or 2k, each 1/4. **CHOKES**,
1P 10H 140 mA., 8/8; Potted 10H 100 mA., 7/8;
"C" 5H 400 mA., 10/8. **Mic. inserts**, G.P.O.
carbon, 2/6. **Bal. armature** type, 2/8. **ACCUMU-
LATORS**, 2 v. 4AH 21 x 13 x 3 1/2 in., 7/8. **TX**,
FAR. CONDENSERS, 36K, test; 50 or 100 pF,
each, 7/8. **MONITOR** Type 55 (2 units oscilloscope
and power mit), £8/10; (Rail 20/-).

LIST AND ENQUIRIES : S.A.E. please. Terms.
C.W.O. Postage extra. Immediate despatch.

Callers and Post : W. A. BENSON (P/W), 136
Rathbone Road, Liverpool, 15. SEP 6853
Callers : SUPERADIO (Whitechapel), LTD., 116,
Whitechapel, Liverpool, 2. RTF 1180

SAVE MONEY IN 1960!

STEREO BY "PERTH" EXCEPTIONAL NEW YEAR OFFER RECORD PLAYER CABINET



99/6

Portable 1960 "Perth" show model, in two-tone colours. Extension speaker cabinet secured in lid. (Arrow indicates position when fixed.) Size: 18 x 14 x 8 in. high. This Stereophonic player complete, retails at 35 gns. In the shops to-day. A must for all teenagers, and an essential for the enthusiast. Carr. & Ins. 5/6.

SPARES FOR ALL



EXTENSION SPEAKERS. 19/6.

Ideal for Stereophonic sound. Attractive polished cabinet fitted with 8 in. P.M. speaker Std., matching to any receiver. 2-5 ohms. Switch and flex. P. & P. 3/6.

8 in. P.M. SPEAKER. 5/9. Had a slight cone repair, not affecting the quality. Tested and guaranteed. Limited quantity 2/9.

8 in. P.M. SPEAKERS. 8/9. Good quality 2-5 ohms. P. & 2/9.

6 in. P.M. SPEAKERS. 12/6. Std. 2-5 ohms. P. & P. 2/6.

ELLIPTICAL SPEAKERS. 19/6. Size 10 x 4 1/2 in. Ideal for record players. P. & P. 2/6.

VOLUME CONTROLS. 2/6 doz. : mixed parcel of volume and tone controls taken from working chassis. P. & P. 2/-.

FOCUS MAGNETS. 9/9. Brand new, 38 mm. Incorporate picture shift control. Post 1/3.

ELAC FOCUS MAGNET. 12/6. Brand new, 35 3/8 mm. P. & P. 1/3.



DEPT. I.

PP COMPONENTS LTD.

219, ILFORD LANE, ILFORD, ESSEX.

STAMP for CATALOGUE

ILF. 0295.

★ TRANSFORMERS ★

REVISED LIST

MAINS AUTO. 8/9. 0-205-225-245 volts at 300 m.a. Isolated windings 6.3 v., 6.3 v. and 2 v. P. & P. 3/9.

MAINS TRANS. 5/9. 200-250 v. at 150 m.a. Sec. 0-100-250. Suitable small amplifiers. 2 1/2 x 1 1/2 in. P. & P. 1/9.

MAINS TRANS. 7/9. 300-0-300 v. Prim. 200-250. 6.3 v. at 3 amp. P. & P. 2/9.

MAINS TRANS. 6/9. 300-0-300 v. at 80 m.a. Prim. 200-250 v. 6.3 at 3 amp. 5 v. at 2 amp. P. & P. 2/9.

O.P. TRANS. & SMOOTHING CHOKES. 4/9. Suitable for EL84, single or P Pull output. P. & P. 1/9.

O.P. TRANS. 1/3. Std. size. 2-5 ohms. P. & P. 1/20 for 2 1/2. Carr. 5/6.


FRAME O.P. TRANS. 1/9. 500 ohms. Prim. Sec. 18 ohms. P. & P. 1/6.

HEATER TRANS. 3/9. 2-1 ratio. Auto trans. 2 v. to 4 v. 3 watts. Post 1/9.

HEATER TRANS. 12/9. 12 v. at 1 amp. Prim. 0-200-250 v. P. & P. 1/9.

EY51 ISOLATION TRANS. 5/9. 7 kV. 1-1 ratio. P. & P. 1/9.

RECORD OR TAPE GIFT CASE

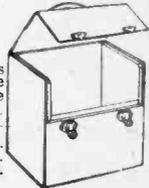

Beautifully made in various colours, covered in washable leatherette. Strong modern case and carry handle, hinged top, plated clip fasteners. P. & P. 2/6.

To hold 30 E.P. 7 in. records 21/9.

To hold 40 E.P. 7 in. records 23/9.

To hold 20 10 in. or 12 in. records 22/6.

To hold 50 10 in. records 24/6.

Also hold 10 large tapes.

WIRING ACCESSORIES

Return of Post Service. Lowest Possible prices consistent with high quality. Money back guarantee.

PVC Cable Flat Twin with E. 3 Core

1.044	£2. 1. 8	£2.15. 1	£2.19. 1
3.029	£2.14. 2	£3. 8.11	£3.19. 0
3.036	£3.18. 5	£4.10. 9	£5.10.10
7.029	£4.19.11	£6. 1.11	£8.18. 3

TRS CABLE

1.044	£2. 3. 5	£2.13.11	£3. 0.10
3.029	£2.15. 9	£3. 6.10	£4. 5. 4
3.036	£3.15. 2	£4. 6. 5	£5. 8. 7
7.029	£4.13.10	£5.18. 2	£8.18. 7

Prices per 100 yds. All sizes stocked. Supplied in 25, 50, 75 or 100 yd. lengths. 7.029 and above cut to length—no cutting charge. Carriage paid on all orders over £2. Full range of accessories available. Send for complete lists.

ELECTROSURE
118, FORE STREET, EXETER
Phone: Exeter 56687.

GUARANTEED CAPACITORS

Hi-K Disc. : 500 v. d.c. wkg., 470 pF, .001 uF, .002 uF, .003 uF, .005 uF, 9d. each.
Tubular : 500 v. d.c. wkg., 1, 1.5, 2, 3 pF. 1/4 each; 5, 7.5, 10, 15, 20, 25, 30, 40, 47, 50, 60, 75, 100 pF, 10/d. each; 150, 200, 250, 300, 350, 400, 500 pF, 1/2 each. Hi-K midget tubular, 500 v. d.c. wkg.; 500 pF, .001 uF, .002 uF, .003 uF, 10/d. each; .005 uF, 101 uF, 1/- each.

Close Tolerance Silver Mica. Plus or Minus 1 pF: 1.5, 2, 2.2, 2.9, 4.7, 5, 5.6, 8.2, 10, 15, 20, 25, 30, 40 pF, 11d. each. 1% : 47, 50, 56, 60, 68, 75, 80, 100 pF, 1/- each.

Minimum postage 9d. on orders under £3.

Please note we do not supply overseas except to H.M. Forces.

SOUTHERN RADIO & ELECTRICAL SUPPLIES
SORAD WORKS
REDLYNCH, SALISBURY

Morse Code operating . . . as a PROFESSION

45 years of teaching Morse Code is proof of the efficiency of the Candler system.

Send 3d. stamp for Payment Plans and full details of all Courses.

CANDLER SYSTEM CO. Dept. 510
52b, Abingdon Road, London, W.7.
Candler System Co., Denver, Colorado, U.S.A.

12 v. D.C. MAGNETIC SWITCH. Cuts out on 2 a. overload or dead short. 13/6.
12 in. SPEAKER and separate 1" tweeter in floor stand walnut cabinet 22 1/2 x 8 x 13 in. at less than half price. £6/15/-.

COSSOR V.H.F. F.M. KIT. Model 701K. £8/19/6. List Price 15 gns.

LIGHTWEIGHT PENCIL BIT SOLDERING IRON. 200/240 v. 25 w. Indicator light in handle (list price 24/6). Price 16/6.

SCOOTER BATTERIES. 6 v. 10 A.H. Hard rubber case 5 x 5 x 1 1/2 ins. Weight 3 lb. 15/- . Also ideal for model use.

NEW BOXED COLLARO CONQUEST 4-SPEED AT TOCHANGERS. 200/250 v. A.C. £8/19/6. Carriage 5/-.

OUR FAMOUS TRANSFORMERS. Input 200/250. Output tapped 3 to 30 v. 2 a. or 5, 11, 17 v. 5 a. Each 24/6.

F.V. METAL RECTIFIERS. 12/6 volt. 1 a., 7/6; 3 a., 13/6; 4 a., 17/6; 6 a., 27/6. **STUDIO "O" PU CARTRIDGES.** 21/-.

FLAT TYPE H.W. RECTIFIERS. 250 v. 25 m.a. 7/6. 60 m.a., 7/6. 300 m.a. 24/- . All P.P. Most other types stocked.

TOGGLE SWITCHES. DPDT. 3/6.
MICRO SWITCHES. Make & Break. 5/8.
MAINS TRANSFORM. & RECTIFIER. 12 v. 1 a. D.C. 19/6.

NICKEL NIFE BATTERIES. 1.2 v. 2.5 a. Size 3 x 2 1/2 x 1 in. 6/- or 3 for 16/-.

ARMY MORSE KEYS. 3/- . P.P.
LIGHT WEIGHT H.R. PHONES. 17/6.

RELAYS. We hold large stocks. Any contact combination and operating coil voltage supplied from 3/-.

KEY SWITCHES from 3/-.

U.S. TWIST DRILLS. Set 7. 1/16"-1". 4/-.

All items new, guaranteed & post free except where stated.

Lists sent on request. Post orders only to
THE RADIO & ELECTRICAL MART
29 STATION APPROACH, SUDBURY TOWN, WEMBLEY, MIDD.


"GLOBE-KING"
WORLD-FAMOUS KITS AND RECEIVERS for the Radio Amateur and S.W. Listener. Catalogue Free, enclose stamp for Postage. Kits from 79/6 at your dealers, or direct from
JOHNSONS (RADIO)
8T, MARTINS GATE, WORCESTER

MOTEK

THREE SPEED TAPE-DECK

The Motek tape deck is both the heart and backbone of a multitude of recording machines. Confidence in Motek, felt by manufacturers and enthusiasts alike, grows with the technical excellence of Motek equipment.

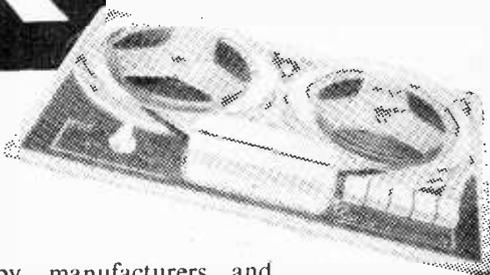Three speeds, pause control, push button operation, accidental erasure prevention, positioning counter . . . these are a few of the outward signs of internal quality. **List 21 gns.**



Patents Pending.
Details on Request.

MODERN TECHNIQUES

Wedmore Street, London, N.19.
Tel.: Archway 3114.

PETHERICK'S RADIO SUPPLIES

22, High St., Bideford, N. Devon.

5/- TRANSISTORS 5/-

Red Spor. 5/- each; Yellow/Green. 5/6 each; White Spots. 6/6. Red/Yellow. 12/6. Vari-Loopstick M.W. Coils, with Transistor Circuit, 4/6. DRR2 Coils with transistor and Valve Circuits, 4/- each. Crystal Set Coil M.L. with Circuit, 2/6. Crystal Diodes, 1/- G.E.X.34. 4/-. Reaction Condensers .0001, 3/-. .0003, 3/9; .0005, 4/-. Miniature, .0005, 4/-.

NEON MAINS TESTERS, 3/9 each. 2 mfd. 150 volt Electrolytics, 1/6. Miniature 15 volt Electrolytics in 2 mfd., 5 mfd., 8 mfd., 25 mfd., 50 mfd. or 100 mfd. All at 3/- each.

Postage FREE in U.K.

ASTRAL RADIO PRODUCTS

'HOME RADIO,' 32-page illustrated booklet. Simple wiring instructions for Crystal Set, 1, 2, 3 Valves, 2/-, post 3d. TRF COILS, 7/-, post 6d. **DUAL WAVE HF Coil with REACTION.** Specified for 'Summer All Dry Portable.' 'A.C.' Double Triode 1/- etc., 4/6, post 3d. 'FT's' Miniature, 1" x 1 1/2" x 2 1/2" in cans, Extra high 'Q.' Special offer, 9/-, post 6d. Crystal Set Coils, L. & M.W. 2/6, post 3d.

82 Centurion Road, Brighton

RES/CAP BRIDGE 37/-

p. & p. 2/-
Checks all types of resistors, condensers
6 RANGES

Built in 1 hour. Direct reading
READY CALIBRATED
Stamp for details of this and other kits.

RADIO MAIL (Dept. PU)
Raleigh Mews, Raleigh Street, Nottingham

RESISTORS

Fully insulated carbon composition. $\pm 10\%$ tolerance. Full range of standard values. 10 ohms to 10 megohms.

1 watt. length 1/2 in., 5d. each.
1 watt. length 3/4 in., 6d. each.
2 watt. length 1 in., 9d. each.

High stability cracked carbon. Fully insulated. $\pm 5\%$ tolerance. Standard values 100 ohms to 1 megohm.

1 watt. length 1 in., 9d. each.

Cash with order please! Postage extra. Up to 5/- add 6d., 10/- add 1/-, 20/- add 1/6, over 20/- post free.

Sandmar Electronic Products,
68, Nina Drive, New Moston,
Manchester 10, Lancs.

A 3d. stamp will bring you a copy
of our latest

RADIO & TELEVISION COMPONENT Catalogue

JAMES H. MARTIN & CO.
FINSTHWAITE, NEWBY BRIDGE,
ULVERSTON, LANCs.

B.B.C. - I.T.V. - F.M. AERIALS



B.B.C. (BAND 1). Telescope loft, 19/6. External, S/D. 26/3.

I.T.V. (BAND 3). 3 Element loft array, 24/-, 5 Element, 32/6. Wall mounting, 3 Element, 33/9. 5 Element, 41/3.

COMBINED B.B.C. + I.T.V. Loft 1+3 Element, 41/3. 1+5 Element, 43/9. Wall mounting, 1+3 Element, 56/3. 1+5 Element, 63/9. Chimney and mast

mounting units also available. **F.M. (BAND 2).** Loft "H," 28/-, 3 Element S/D 26/3. S/D loft, 12/6. External S/D 26/3. State channel when ordering. C.W.O. or C.O.D. P.P. 2/6. Coaxial cable, 8d. yd. Coaxial plugs, 1/3. Send 6d. stamps for illustrated lists.

K.V.A. ELECTRONICS (Dept. P.W.)
3B, Godstone Road, Kenley, Surrey

TRANSISTOR TEST SET

Directly calibrated in Gain (0.50 and 0.125). Also measures Base current (0.50 μ A) and Collector current (0.25 mA). Works from 9 v. G.B. Battery (not supplied). Accurate, complete, brand new, with operating instructions. 35/-, p. & p. 1/6.

Rectifiers. All Full-wave bridge. New Salford 1 or 1/2 mA., 7/6; 5 mA., 7/6. New Westinghouse. 250 μ A, 1, 5 or 10 mA., 14/6; 100 μ A, 17/4. Ex-Govt. M3, 5-50 mA., 3/6. All post 6d.

0-1 mA. Meter. 2 1/2 in. scale, flush fitting, scaled A.C./D.C. multimeter, with free circuit, 32/6, p. & p. 1/6.

Precision Wirewound Resistors. Wound to your value, 1 ohm to 1 K. 1%, 2/9; to 5 K., 3/3; to 20 K., 4/-; to 50 K., 4/3; to 100 K., 4/6.

Leather Meter Cases, with shoulder strap, 6 in. x 4 1/2 in. x 2 in. int. with partition, 5/-, p. & p. 1/-.

Special Offer. Salford 1 mA. Rec. with 1% multipliers for 10, 100, 250 and 500 v. A.C., 12/6, post free.

PLANET INSTRUMENT CO.,
25, DOMINION AVENUE, LEEDS, 7


Premier RADIO

23, TOTTENHAM COURT ROAD, LONDON, W.1.

TEL.: MUSEUM 3451/2

Visit our New Branch at: 309, EDGWARE ROAD, LONDON, W.2.

TEL.: PAD 6963

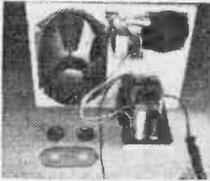

The Famous Cossor 3 watt
AUDIO AMPLIFIER KIT 562K
Original Price £9.15.0.

OUR PRICE £5.19.6, p. & p. 2/6


This Kit assembled will provide a compact versatile Amplifier which incorporates the most up-to-date pre-assembled printed circuit and is suitable for operation from Radio, Microphone or Gramophone. The circuit design includes negative feedback, valve line-up 6V4, 6BQ5, EF86. Two Loudspeakers are used, i.e., 10in. x 6in. Elliptical and 4in. Treble, ensuring high quality output, suitable for use on 200/250 v. A.C. mains. All items are supplied, including Loudspeakers, Knobs and Escutcheon, with full assembly instructions and in maker's original cartons.

The Cossor Printed Circuit
Model 701K VHF/FM Radio Receiver Kit

Original Price 15 gns.

OUR PRICE £8.19.6, p.p. 2/6

This Kit is easily assembled and will provide a complete Radio Receiver for reception of VHF/FM transmission. The Receiver utilises the latest type printed circuit, for use on A.C. or D.C. mains, incorporating UCC85, UF89, UF89, UABC80, UL84, UY85 Valves. All components are supplied including a Goodmans 10in. x 6in. Elliptical Speaker, full assembly instructions and presented in manufacturer's original cartons.

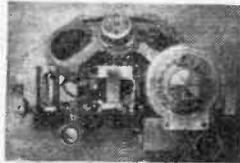

THE BEREC

The 'Berec' Battery Receiver for only £4.19.6, plus 5/- p. & p. or £10.0 dep. and 5 mthly pymts of 17/-. Suitable for use in the home or where normal electricity supply is not available, remarkable reception on med. and short wavebands, using DK92, DF92, DAF96, DL96, latest type min. Battery Valves: operates on an external B.103 Battery or equiv. Housed in an attractive, two-tone metal case. Size 11½ x 7½ x 5½in. **BATTERY EXTRA 18/6.**



Quality at low cost!

A well designed Amplifier using latest type printed circuit, two ECL82 Valves, Metal Rectifier, ganged volume and tone controls and separate balancing control, output 3 watts per channel and suitable for 3½ Speakers. Housed in black metal cabinet 10½ x 7½ x 4½in. with Engraved Front Panel. Price £8.19.6, plus p. & p. 5/-.



Convert your Battery Portable to A.C. mains operation with the Cossor MU2 Battery Eliminator.

This unit is assembled and supplied with 4ft. of Mains Lead and unit Torpedo type of On/Off Switch. Housed in 2 metal containers approximately the same size as the AD.35 and B.126 batteries and suitable for Receivers using 1.4 volt L.T. and 90 volt H.T.

ORIGINAL PRICE 3 gns.

OUR PRICE for a limited period, 37/6, plus 2/- p. & p.

★ **GENEROUS H.P. TERMS AVAILABLE** ★

EXPRESS ELECTRONICS

ROSEDEEN LABORATORIES
KINGSWOOD WAY, SELSDON, SURREY

VALVES NEW, TESTED AND GUARANTEED
REDUCED PRICES

1C1	7/6	6BR7	10/6	12Q7GT	7/6	EB91	5/6	N17	7/6
1C3	8/-	6BW6	7/6	16A5	9/6	EB41	10/-	N18	9/-
1P1	8/-	6BW7	7/-	25A6G	10/6	EBF90	6/6	N19	7/6
1P3	7/6	6C10	9/-	25L6GT	9/-	ECC81	7/6	PCF84	9/-
1PD1	8/-	6I12	8/6	25Z4G	9/-	ECC82	7/6	PCF90	9/-
1PD9	7/6	6F12	8/6	30C1	8/-	ECC83	7/6	PCF92	10/6
1L4	6/9	6T7GT	8/6	30L1	8/-	ECC84	8/6	PCL92	10/6
1P1	8/-	6K7G	5/6	35L6GT	9/-	ECF90	10/6	PL38	22/6
1P10	7/6	6K8G	7/6	35W4	8/6	ECP92	10/6	PL81	12/-
1P11	7/6	6L9G	10/6	35Z4GT	8/-	ECH42	9/-	PL82	9/-
1B5	7/6	6Q7G	7/6	33KU	11/6	ECH81	10/-	PY81	8/6
1B5	7/6	6R17GT	7/6	37G3	10/6	ECL80	10/6	PY92	7/6
1J4	7/6	68N7GT	5/-	DAF91	7/6	EP41	9/-	U52	7/6
1E5	6/-	6V6G	7/6	DAF96	8/6	EP80	8/6	U78	7/6
3A5	10/6	6X4	7/-	DF91	7/6	EP86	11/-	U78	7/-
3Q4	8/-	6X5GT	6/-	DP96	8/-	EP91	4/6	Y8C41	8/6
3B4	7/6	6D3	4/6	DH76	8/6	EP92	5/6	UGH42	8/6
3V4	7/6	12A88	10/6	DH77	7/-	EL38	22/6	UF41	8/6
5U4G	7/6	12AT6	8/6	DH142	8/6	EL41	9/6	UL41	8/6
5Y3GT	7/6	12AT7	7/6	DH150	10/6	EL84	8/6	UY41	7/6
5Z4G	9/6	12A07	7/6	DK91	7/6	EY51	10/6	W78	6/9
6AK6	6/6	12AX7	7/6	DK92	9/-	EZ40	7/6	W142	8/6
6AL5	5/6	12BH7	14/6	DK96	8/-	EZ80	7/-	X17	7/6
6AM6	4/6	12J7GT	10/-	DL92	7/6	EZ80	7/-	X142	9/-
6AT6	7/6	12K7GT	6/9	DL94	7/6	EZ81	8/-	X150	9/-
6BA6	7/-	12K8GT	7/6	DL96	8/-	KT33C	9/6	Z77	4/6
6BE6	7/-	12L8	12/6	EABC80	8/6	KT66	11/6	ZD17	7/6

VOLUME CONTROLS MIDGET SIZE LONG SPINDLES D.P. switch, 3/9, 8.P., 3/3; Less switch, 2/6. Values 10K to 2M. Pre set 2/6.

MATCHED PAIRS


EL84 21/-, 6V6G 17/-, KT66 27/6, 6BW6 18/- per pair. Push Pull O.P. Transformers for above 3-15Ω 14/6. 15" P.M. Speakers 3Ω 24/6.

SETS OF VALVES

DK91, DF91, DAF91, DL92 or DL94	27/6
DK96, DF96, DAF92, DL96	32/-
1C3, 1P1, 1PD1, 1P1	32/-
1E5, 1J4, 1B5, 3B4, or 3V4	27/6
6K5, 6K7, 6Q2, 6V6, 2Z4G or 6X5G	27/6

Postage and packing 6d. Over £1 post free. C.O.D. 2/6.

Fully Guaranteed Components

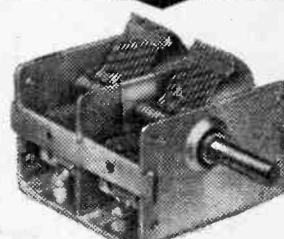

F. GANG CONDENSER

A good general purpose gang. Robust but small in size. "E" law to match our S.L.8 Full Vision, Square Plane and Air Plane Drives. Size 2½in. x 1 21/32in. x 2 9/16in. long (3 gang 3 11/16in.). Price for 2 Gang, 13s. 3d. 3 Gang, 17s. 6d. Complete with trimmers.

JACKSON BROS. (London) Ltd.
PRECISION BUILT COMPONENTS
KINGSWAY · WADDON · SURREY



Telephone: Croydon 2754/5

FREE LISTS

BY RETURN

SHORT-WAVE TRANSISTORS

SB078 20 Mc/s 6 mW	10/-
SB305 25 Mc/s 10 mW	15/-
SB231 30 Mc/s 10 mW	22/6
SB231R 50 Mc/s 10 mW	30/-
OC170 70 Mc/s 70 mW	35/-

FREE LIST AND DATA.

TRANSISTOR CRYSTAL OSCILLATOR (3 to 12 Mc/s)

With new 25 Mc/s Transistor. Use any quartz crystal from 3 to 12 Mc/s.

- ★ Ideal Frequency Check.
 - ★ Short Range Transmitter.
- All Components less crystal 22/6 P.P. 1/-.
SEE SEPARATE LIST FOR FREQUENCIES.

LIGHT-OPERATED SWITCH

Two-transistor including Photo-Transistor and Relay. Overall size 2in. x 3in. x 8in.

- ★ Switch Car Lights, etc., on and off automatically.
- All Components 27/6 P.P. 1/-.
FREE LIST AND DIAGRAM.

TRANSISTOR CAR RADIO 2-WATT AMPLIFIER

A permanent power transistor stage complete with 7 x 4in. speaker. May be used with any battery portable using a 3-ohm or 15-ohm speaker. Use it with the "8." Complete Set of Parts ... 65/- P.P. 2/6
Unit built up and tested ... 77/6 P.P. 2/6
(See "RC," December, 1959)

SEND FOR FREE LIST.

R.F., I.F. GENERATOR

Pocket size Test Unit. Harmonic output 450 kc/s to 2 Mc/s. Ideal for aligning all Receivers. Size 2 1/2 x 1 1/2 x 1in. All Components ... 25/- P.P. 1/-
SEND FOR FREE LIST AND DIAGRAM.

TOP BAND TRANSISTOR TRANSMITTER

Pocket size 150 to 160 metre Transistor Transmitter. Range up to 100ft. on 3ft. aerial. Ideal for Short Range Communication, Car to Car, etc. Microphone input. Complete Set of Parts ... 57/6 P.P. 1/6
SEND FOR FREE CIRCUIT AND LIST.
(See "RC," January, 1960)

SELECTION FROM OUR VALVE LIST:

0Z4	5/-	607G	7/6	35L6	10/-
1C5	10/-	65L7	6/-	35Z4	8/6
1R5	7/-	65N7	6/-	CV188	6/-
1S4	7/-	6V6G	6/-	DAF91	7/-
1S5	6/6	6V6GT	7/6	DAF96	9/-
1T4	6/-	6X4	6/-	DF91	9/-
3A5	9/-	6X5GT	5/-	DF96	9/-
3Q5	9/-	7C5	9/-	DK91	7/-
3S4	7/-	7C6	7/6	DL91	7/-
3V4	7/6	7C7	8/6	DK96	9/-
5U4	6/-	7Y4	7/-	DL33	9/-
5Y3GT	8/6	7Z4	7/-	DL35	10/-
5Z4	8/6	9D6	5/-	D92	7/-
6A7	9/-	12A7	8/-	DL94	7/6
6ABGT	9/-	12AU7	7/6	DL96	9/6
6AC7	5/-	12AR6	10/-	DM70	8/6
6AL5	5/-	12K8M	10/-	EB91	5/-
6AM6	5/-	12SL7	10/-	EB41	9/6
6BA6	8/6	12SN7	10/-	EBF80	9/6
6C4	5/-	12SQ7	8/6	EBF89	9/6
6F12	5/-	14S7	14/-	ECC81	8/6
6L6G	8/-	25L6	10/-	ECC82	7/6
6L6M	10/-	25Z4	9/-	ECC85	9/6

LARGE RANGE OF VALVES, TUBES, QUARTZ CRYSTALS, METERS, TRANSISTORS, MINIATURE COMPONENTS, SUGGESTED CIRCUITS.



R.C.A. VALVE-VOLTMETER

Type 165-A

D.C. ELECTRONIC VOLTMETER

6-Ranges 0-1,000 volts
Input Res. 11,000,000 ohms.
Sensitivity 3,666,666 o.p.v. on 3 v. scale.

A.C. VOLTMETER

5-Ranges 0-1,000 volts
Sensitivity 1,000 o.p.v.

ELECTRONIC OHMMETER

6-Ranges from 0.1 ohms to 1,000 Megohms.
Movement 200 Microamperes D.C.
Accuracy $\pm 2\%$.
110/250 v. A.C. input.

BRAND NEW

With Instruction Book and Test Prods.

£12.10.0 P.P. 3/6

INVALUABLE TO EXPERIMENTER AND SERVICE MAN.

LIMITED STOCKS—BUY NOW

SHORT-WAVE RADIO

650 kc/s to 27 Mc/s (10 to 500 metres)


- ★ 3 WAVEBANDS (Med. and 2 Short).
- ★ SLOW MOTION TUNING: A.C./D.C. MAINS.
- ★ 5 MARCONI VALVES (SUPERHET).
- ★ 7 x 4in. SPEAKER : FRAME AERIAL.

ONLY £7.12.6 P.P. 5/6


NOW—INCLUSIVE OF CABINET.

Includes Gram. Input. CHASSIS SIZE 10 x 10 x 4in.

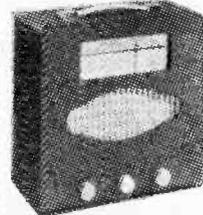- ★ ALTERNATIVE MODEL (MED., LONG AND SHORT)
- ★ SHORT-WAVE RECEPTION MUST BE HEARD TO BE BELIEVED.



POCKET MULTIMETER

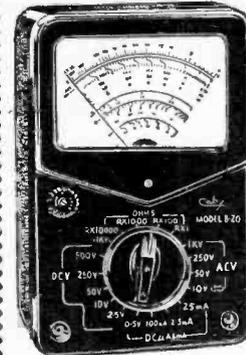

Size 5 1/2 x 3 1/2 x 1 1/2 in.
Weight 17 ozs.

MODEL A10 : 500 Microamp Movement.

★ A.C./D.C. voltages 2,000 ohms per volt : 10, 50, 250, 500 and 1,000 volts. ★ Resistance 10kohms and 1 Megohm.
★ D.C. current 0.5 mA ; 25 mA ; 250 mA. ★ Decibel range. ★ D.C. $\pm 2\%$ accuracy ; A.C. $\pm 3\%$.

INCLUSIVE OF TEST PRODS. ILLUSTRATION BOOK AND BATTERIES.

£4.17.6 P.P.

BRAND NEW AND GUARANTEED

Free Leaflet by return

TRANSMITTER/RECEIVER

Army Type 17 Mk. II.

Complete with Valves, High Resistance Headphones, Hand Mike, Instruction Book and Circuit. Frequency Range 44.0 to 61 Mc/s. Range approximately 3 to 8 miles. Power requirements: Standard 120 v. H.T. and 2 v. L.T. Ideal for Civil Defence and communications.

BRAND NEW 45/- P.P. 5/-

44-61 Mc/s calibrated wavemeter for same, 10/- extra.

TYPE 38 TRANSMITTER/RECEIVER

Complete with 5 valves. In new condition. These sets are sold without guarantee, but are serviceable.

7 to 9 Mc/s 22/6 P.P. 2/6

Headphones 7/6 pair. Junction Box 2/6. Throat Mike 4/6. Canvas Bag 4/- Aerial Rod 2/6.

HENRY'S (RADIO) LTD.

Opposite Edgware Road Tube Station. PADdington 1008/9.

5, HARROW ROAD, EDGWARE ROAD, PADDINGTON, LONDON, W.2.
OPEN MONDAY TO SAT. 9-6. THURS. 10'clock.

SEE BACK PAGE

Practical Wireless

BLUEPRINT

SERVICE

ALL OF these blueprints are drawn full-size and although the issues containing descriptions of these sets are now out of print, an asterisk in the list below denotes that constructional details are available free with the blueprint.

The index letters which precede the Blueprint Number indicate the periodical in which the description appeared. Thus PW refers to PRACTICAL WIRELESS; AW to *Amateur Wireless* and WM to *Wireless Magazine*.

Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to

PRACTICAL WIRELESS, Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

SPECIAL NOTE

THE following blueprints include some pre-war designs and are kept in circulation for those constructors who wish to make use of old components which they may have in their spares box. The majority of the components for these receivers are no longer stocked by retailers.

Title	Number	Price	Title	Number	Price
CRYSTAL SETS			A.C. Fury Four	PW20*	2/6
Junior Crystal Set	PW94*	2/-	Experimenter's Short Wave ...	PW30a*	2/6
Dual-wave Crystal Diode ...	PW95*	2/6	Midget Short Wave Two	PW38a*	2/6
STRAIGHT SETS			Band-Spread Three (Battery) ...	PW68*	2/6
Battery Operated			Crystal Receiver	PW71*	2/-
Modern One-valver	PW96*	2/6	Signet Two (Battery)	PW76*	2/6
All-dry Three	PW97*	3/6	Simple S.W. One-valver	PW88*	2/6
Modern Two-valver	PW98*	3/6	Pyramid One-valver	PW93*	2/6
SUPERHETS			BBC Special One-valver	AW387*	2/6
Mains Operated			Short-Wave Two	AW429*	2/6
A.C. Band-pass Three	PW99*	4/-	Short-Wave World Beater	AW436*	3/6
A.C. Coronet-4	PW100*	4/-	Standard Four Valve S.W.	WM383*	3/6
A.C./D.C. Coronet	PW101*	4/-	Enthusiast's Power Amplifier ...	WM387*	3/6
MISCELLANEOUS			Standard Four Valve	WM391*	3/6
The PW 3-speed Autogram ... *		8/-	Listener's 5-Watt Amplifier	WM392*	3/6
The PW Monophonic Electronic Organ		8/-	TELEVISION		
TELEVISION			Argus Television Receiver	—*	3/-
The PT Band II Converter		1/6	Simplex Television Receiver	—*	3/6

QUERY COUPON

This coupon is available until 6th January, 1960 and must accompany all queries in accordance with the notice on our "Open to Discussion" page.

PRACTICAL WIRELESS, JANUARY, 1960

Published on the 7th of each month by GEORGE NEWNES, LIMITED, Tower House, Southampton Street, Strand, London, W.C.2, and printed in England by W. SPEAIGHT & SONS, Exmoor Street, London, W.10. Sole Agents for Australia and New Zealand: GORDON & GOTCH (A/sia), LTD. South Africa and Rhodesia: CENTRAL NEWS AGENCY, LTD. Subscription rate including postage for one year: Inland £1.3.0, Abroad £1.1.6 (Canada 19s.). Registered at the General Post Office for the Canadian Magazine Post.

ANNOUNCING AN ENTIRELY NEW COMBINED TRANSISTOR PORTABLE/CAR RADIO CONTINENTAL—6 (SUPERSEDING THE TRANSISTOR "8") SIX TRANSISTOR PORTABLE SUPERHET MEDIUM AND LONG WAVE


SPECIFICATIONS

- ★ New Type Printed Circuit with all components marked. Just plug-in and solder.
- ★ 6 Ediswan selected transistors plus two diodes.
- ★ Slow Motion tuning.
- ★ Full A.V.C. and Car-Radio.
- ★ 400 M/W Push-Pull Output.
- ★ High fidelity speaker.
- ★ 6 Months' battery life.

TOTAL COST OF ALL SPECIFIED COMPONENTS INCLUDING CABINET AND BATTERY ONLY
£11.10.0 P.P. 3/6

ALL COMPONENTS AVAILABLE SEPARATELY. SEND FOR DESCRIPTIVE LEAFLET AND PRICES.

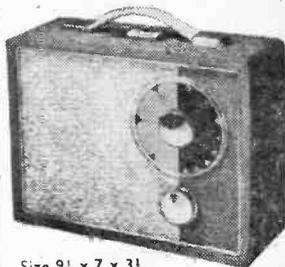BRILLIANT ENGINEERING HAS PRODUCED THIS HIGHLY SENSITIVE AND SELECTIVE SET, WHICH WILL PERFORM EQUALLY WELL AS A CAR RADIO. ITS GOOD LOOKS COUPLED WITH EASE OF CONSTRUCTION—QUALITY—PERFORMANCE—AND LOW RUNNING COSTS—EQUALLING ANY COMMERCIAL SET IN THE 20-GUINEA CLASS.



Size 9½ x 7 x 3½.
Weight 4 lbs.

MAJOR—2

(Two-transistor Pocket Radio)



69/6 TOTAL COST
P.P. 1/6.

NEW BOOKLET FREE: All components sold separately.

GOOD RECEPTION ANYWHERE!

- ★ 4-stage reflex!
- ★ Medium wave: tunable!
- ★ Very sensitive!
- ★ No aerial or earth!
- ★ Complete layout!
- ★ Over 6 months on one battery.
- ★ 4½ x 3 x 1½ in.
- ★ Weight only 4 ozs.
- ★ Personal 'phone.

RED-SPOT TRANSISTORS


5/- EACH

WHITE-SPOT

7/6

FREE LIST ON REQUEST

MAJOR—3

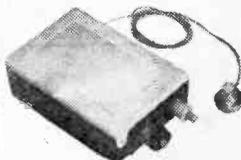

(AS DESCRIBED IN "R.C." SEPT. '59)


TOTAL COST **87/6** P.P. 1/6 FREE BOOKLET

FANTASTIC OUTPUT, TERRIFIC RECEPTION. GUARANTEED ANYWHERE

- ★ 5-stage Reflex Circuit.
- ★ No Aerial or Earth.
- ★ Min. Volume Control.
- ★ 3 Ediswan Transistors.
- ★ Medium Wave Tuning.
- ★ Size 4½ x 3 x 1½ in.
- ★ Personal 'phone.

SUPER 6

SIX TRANSISTOR MEDIUM AND LONG WAVES

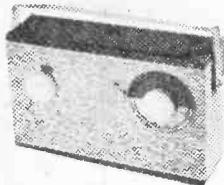

- ★ Plessey Printed Circuit
- ★ Mullard Transistors
- ★ 3-inch Speaker
- ★ Full Medium & Long Waves
- ★ Size 7 x 4½ x 2 in.

Recommended by us as being the easiest to build 6-Transistor printed circuit superhet receiver ever offered.

TOTAL COST OF ALL COMPONENTS, INCLUDING CABINET AND BATTERY.

ONLY

£9.10.0 P.P. 2/6

All parts sold separately.

NEW "ADDON" STAGE

- ★ 2 Ediswan Transistors
- ★ Push-Pull up to 250 mW
- ★ 3 inch ELAC Speaker
- ★ Cabinet 5½ x 3½ x 1½ in.

A unit for use with major 2 and 3 or any earpiece pocket-portable to give full speaker output; complete set of parts with cabinet.

59/6 P.P. 1/6

FREE LIST AND DIAGRAM

LIMITED QUANTITY ONLY FREE LIST ON REQUEST

AUDIO GENERATOR


- ★ XB104 Transistor
 - ★ Size 2½ x 1! x 1 in.
 - ★ Ideal modulator
- 25/-** P.P. 1/6

Complete with all parts.

SEE OTHER ADVT. INSIDE

Ideal pocket Tester. Free Circuit.

THE MINOR

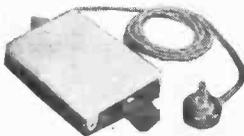

TOTAL COST WITH CASE AND MINIATURE EAR-PIECE **49/6** P.P. 1/6

All parts sold separately. Diagram and List Free.

- ★ 3 x 2 x ¾ in.
- ★ Medium wave
- ★ 3-stage reflex
- ★ Internal aerial
- ★ Smallest yet

SIGNAL TRACER

- R.F., I.F. and Audio
- ★ 2-XB104 Transistors
- ★ Headphone output
- ★ Easy to Build
- ★ Simple to use

All parts. 37/6, P.P. 1/6. Free Diagram.

HENRY'S (RADIO) LTD. (Dept. P.W.D.) 5, HARROW ROAD, EDGWARE ROAD, PADDINGTON, LONDON W.2.
Opposite Edgware Road Tube Station. PADDington 1008/9 OPEN MONDAY to SAT. 9-6, THURS. 1 o'clock.

Practical Wireless

BLUEPRINT

SERVICE

ALL OF these blueprints are drawn full-size and although the issues containing descriptions of these sets are now out of print, an asterisk in the list below denotes that constructional details are available free with the blueprint.

The index letters which precede the Blueprint Number indicate the periodical in which the description appeared. Thus PW refers to PRACTICAL WIRELESS; AW to *Amateur Wireless* and WM to *Wireless Magazine*.

Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to

PRACTICAL WIRELESS, Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

SPECIAL NOTE

THE following blueprints include some pre-war designs and are kept in circulation for those constructors who wish to make use of old components which they may have in their spares box. The majority of the components for these receivers are no longer stocked by retailers.

Title	Number	Price
-------	--------	-------

CRYSTAL SETS

Junior Crystal Set	PW94*	2/-
Dual-wave Crystal Diode	PW95*	2/6

STRAIGHT SETS

Battery Operated

Modern One-valver	PW96*	2/6
All-dry Three	PW97*	3/6
Modern Two-valver	PW98*	3/6

SUPERHETS

Mains Operated

A.C. Band-pass Three	PW99*	4/-
A.C. Coronet-4	PW100*	4/-
A.C./D.C. Coronet	PW101*	4/-

MISCELLANEOUS

The PW 3-speed Autogram	—*	8/-
The PW Monophonic Electronic Organ	—	8/-

TELEVISION

The PT Band II Converter	—*	1/6
--------------------------	----	-----

Title	Number	Price
-------	--------	-------

A.C. Fury Four	PW20*	2/6
Experimenter's Short Wave	PW30a*	2/6
Midget Short Wave Two	PW38a*	2/6
Band-Spread Three (Battery)	PW68*	2/6
Crystal Receiver	PW71*	2/-
Signet Two (Battery)	PW76*	2/6
Simple S.W. One-valver	PW88*	2/6
Pyramid One-valver	PW93*	2/6

BBC Special One-valver	AW387*	2/6
Short-Wave Two	AW429*	2/6
Short-Wave World Beater	AW436*	3/6

Standard Four Valve S.W.	WM383*	3/6
Enthusiast's Power Amplifier	WM387*	3/6
Standard Four Valve	WM391*	3/6
Listener's 5-Watt Amplifier	WM392*	3/6

TELEVISION

Argus Television Receiver	—*	3/-
Simplex Television Receiver	—*	3/6

QUERY COUPON

This coupon is available until 6th January, 1960 and must accompany all queries in accordance with the notice on our "Open to Discussion" page.

PRACTICAL WIRELESS, JANUARY, 1960

ANNOUNCING AN ENTIRELY NEW COMBINED TRANSISTOR PORTABLE/CAR RADIO CONTINENTAL—6 (SUPERSEDING THE TRANSISTOR "8") SIX TRANSISTOR PORTABLE SUPERHET MEDIUM AND LONG WAVE

SPECIFICATIONS

- ★ New Type Printed Circuit with all components marked. Just plug-in and solder.
- ★ 6 Ediswan selected transistors plus two diodes.
- ★ Slow Motion tuning.
- ★ Full A.V.C. and Car-Radio.
- ★ 400 M/W Push-Pull Output.
- ★ High fidelity speaker.
- ★ 6 Months' battery life.

TOTAL COST OF ALL SPECIFIED COMPONENTS INCLUDING CABINET AND BATTERY ONLY
£11.10.0 P.P. 3/6

ALL COMPONENTS AVAILABLE SEPARATELY. SEND FOR DESCRIPTIVE LEAFLET AND PRICES.



Size 9½ x 7 x 3½.
Weight 4 lbs.

BRILLIANT ENGINEERING HAS PRODUCED THIS HIGHLY SENSITIVE AND SELECTIVE SET, WHICH WILL PERFORM EQUALLY WELL AS A CAR RADIO. ITS GOOD LOOKS COUPLED WITH—EASE OF CONSTRUCTION—QUALITY—PERFORMANCE—AND LOW RUNNING COSTS—EQUALLING ANY COMMERCIAL SET IN THE 20-GUINEA CLASS.

MAJOR—2

(Two-transistor Pocket Radio)



69/6 TOTAL COST
P.P. 1/6.

- ★ 4-stage reflex!
- ★ Medium wave : tunable!
- ★ Very sensitive!
- ★ No aerial or earth!
- ★ Complete layout!
- ★ Over 6 months on one battery.
- ★ 4½ x 3 x 1½ in.
- ★ Weight only 4 ozs.
- ★ Personal 'phone.

RED-SPOT TRANSISTORS

5/- EACH

WHITE-SPOT 7/6

FREE LIST ON REQUEST

MAJOR—3



(AS DESCRIBED IN "R.C." SEPT. '59)

- ★ 5-stage Reflex Circuit.
- ★ No Aerial or Earth.
- ★ Min. Volume Control.
- ★ 3 Ediswan Transistors.
- ★ Medium Wave Tuning.
- ★ Size 4½ x 3 x 1½ in.
- ★ Personal 'phone.

TOTAL COST **87/6** P.P. 1/6 FREE BOOKLET


FANTASTIC OUTPUT, TERRIFIC RECEPTION. GUARANTEED ANYWHERE

NEW BOOKLET FREE: All components sold separately.

GOOD RECEPTION ANYWHERE!

SUPER 6

SIX TRANSISTOR MEDIUM AND LONG WAVES

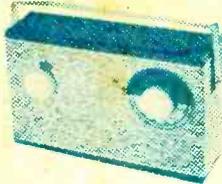

- ★ Plessey Printed Circuit
- ★ Mullard Transistors
- ★ 3-inch Speaker
- ★ Full Medium & Long Waves
- ★ Size 7 x 4½ x 2 in.

Recommended by us as being the easiest to build 6-Transistor printed circuit superhet receiver ever offered.

TOTAL COST OF ALL COMPONENTS, INCLUDING CABINET AND BATTERY. ONLY

£9.10.0 P.P. 2/6
All parts sold separately.

NEW "ADDON" STAGE

- ★ 2 Ediswan Transistors
- ★ Push-Pull up to 250 mW
- ★ 3 inch ELAC Speaker
- ★ Cabinet 5½ x 3½ x 1½ in.

A unit for use with major 2 and 3 or any earpiece pocket-portable to give full speaker output; complete set of parts with cabinet.

59/6 P.P. 1/6

FREE LIST AND DIAGRAM

LIMITED QUANTITY ONLY FREE LIST ON REQUEST

AUDIO GENERATOR


- ★ XB104 Transistor
 - ★ Size 2½ x 1½ x 1 in.
 - ★ Ideal modulator
- 25/-** P.P. 1/6

Complete with all parts.

SEE OTHER ADVT. INSIDE

Ideal pocket Tester. Free Circuit.

THE MINOR

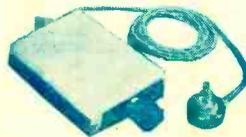

TOTAL COST WITH CASE AND MINIATURE EAR-PIECE **49/6** P.P. 1/6

All parts sold separately. Diagram and List Free.

- ★ 3 x 2 x 1½ in.
- ★ Medium wave
- ★ 3-stage reflex
- ★ Internal aerial
- ★ Smallest yet

SIGNAL TRACER

- R.F., I.F. and Audio
- ★ 2-XB104 Transistors
- ★ Headphone output
- ★ Easy to Build
- ★ Simple to use

All parts. **37/6**, P.P. 1/6. Free Diagram.

HENRY'S (RADIO) LTD. (Dept. P.W.D.) 5, HARROW ROAD, EDGWARE ROAD, PADDINGTON, LONDON W.2.
Opposite Edgware Road Tube Station. PADDington 1008/9 OPEN MONDAY to SAT. 9-6, THURS. 1 o'clock.