

JANUARY  
1962

# Practical 2- WIRELESS

**Experimenter's  
Power Pack**



**P.W. MINUETTE**

**- a pocket portable  
with four transistors**

# CLYNE RADIO LTD. THE COMPONENT SPECIALISTS



18 TOTTENHAM COURT ROAD, W.1 MUSEum 5929/0095  
 162 HOLLOWAY ROAD, LONDON N.E.7 NORTH 6295/6/7  
 9 CAMBERWELL CHURCH STREET, S.E.5 RODney 2875

**OPEN:** Tottenham Court Rd., 9 a.m. to 6 p.m. Mon. to Fri., Sat. 1 p.m. Holloway Rd. and Camberwell: 9 a.m. to 6 p.m. daily. Thurs. 1 p.m. Sat. 5.30 p.m. Our Advantageous H.P. and Credit Sale Terms are available on any single item over £5. Your enquiries invited. Please print your name and address.

All post orders and correspondence to 162 HOLLOWAY ROAD, LONDON N.7

## NEW! NEW! THE "CLYMAX"

At last a 6-transistor pocket size superhet for Medium and Long Wave at a price you can afford. All required components



**ONLY £6.16.6** *Nothing more to buy!*

Plus 2/6 P. & P.

- ★ Completely self contained. No external aerial or earth required.
- ★ Full medium wave coverage, plus switched Light programme on Long Wave
- ★ Push pull output—250 milliwatts
- ★ Matched set of latest type Mullard transistors
- ★ Genuine 3in. P.M. Speaker.
- ★ High-Q Coils.
- ★ Ferrite rod aerial with low selectivity.
- ★ Size: 5 1/2 x 3 1/2 x 1 1/2 in. Two tone cabinet.
- ★ Precision etched printed circuit with components references clearly marked.
- ★ Alignment service available. All parts available separately. Full assembly instructions and individually priced parts list. 2/- post free.

## The "HIGHWAYMAN"

At last a quality Car Radio to build yourself, at an economical price.



All parts available separately, but if purchased at one time, the whole will be supplied at a special inclusive price of only **£10.19.6** Plus 4/- P. & P

Parts list and comprehensive instruction booklet 2/6 post free. (Deducted from cost if complete parcel purchased later)

Look at these features.—

- ★ Attractive styling
- ★ Push pull output
- ★ 3 latest Mullard transistors plus valves type EBF 83 and ECH 83.
- ★ No Buzz High Output and sensitivity.
- ★ Printed circuit (newest type)
- ★ 4" High flux p.m. speaker
- ★ FULL Medium and Long Wave Coverage
- ★ Push Buttons for fingertip control.
- ★ Extremely low Battery consumption (less than 1 amp)
- ★ Easy to fit—any make car (Positive earth type)
- ★ 12 volt operation.
- ★ Compact size measures only 7" x 7" x 2" deep.
- ★ Easy assembly, supplied with dial and drive already mounted.



Full range of competitively priced new speakers in stock. Ask for list

## EXTENSION SPEAKER CABINETS

New design in light oak. Two sizes available. For 6" or 8" speaker at 22/6. For 10" speaker at 25/- only.

Each plus 2/6 P. & P. Suitable reconditioned 8" P.M. unit at 13/6 only, plus 1/6 P. & P.

## OUTSTANDING METER IMPORT!

20,000 ohms per volt!  
 MODEL 200H. Volt-ohm-Millimeter



Ranges: A.C. Voltage: 10, 50, 100, 500, and 1000 volts (10,000 ohms per volt) D.C. Voltage: 5-25, 50, 250, 500, and 2.5k (20,000 ohms per volt) D.C. Current: 0-50 microamps 0-2.5 m/a 0-250 m/a Resistance: 0-6k, 0-6 meg (300 ohm and 30k at centre scale) Capacitance: 10 pF to .001 mfd, .001 mfd to 1 mfd Decibels —20 to +22 dB

A fully guaranteed pocket size meter (actual size 4 1/2 x 3 1/2 x 1 1/2) knife edge pointer, top quality supplied complete with test probes and full operating instructions at **£6.19.6 ONLY**. Post Free Optional extra: Attractive carrying case 15/- only. (Bonus trade enquiries invited) Leaflet available. **JUST ARRIVED!** MODEL TE10. Identical in appearance and size with rotary type switch but 10,000 Ω/v. Ranges: D.C. Voltage: 0-6-30-120-600-1200 volts (10,000 ohms per volt) A.C. voltage: 0-6-30-120-600-1200 volts (10,000 ohms per volt) D.C. Current: 0-120 microamp. 0-3-300mA. Resistance: 0-30k. 0-3 Meg. (150 ohm and 15k at centre scale). Capacitance: 50 pF to 0.01 mfd, 0.001 mfd to 0.15 mfd. Decibels: —20 to +63 dB in 5 ranges **PRICE £5.19.6**. Post Free.

## "P.W. TUTOR"

COMPLETE KIT AS SPECIFIED. Stages 1-4, 65/-, plus 2/- P. & P. All parts available separately. Send stamp for list.

## THE "WAVEMASTER" 7-TRANSISTOR LUXURY PORTABLE NEW LOW PRICE £9.19.6

400 Milliwatt Output

To build yourself. Medium and Long Waves—Push-Pull Superhet A. V. C. Perfect Car Radio reception. Size 10in. x 6in. x 4 1/2in. at base tapering to 4in. at top. Very attractive two-tone grey Vyndic covered cabinet with black and gold printed escutcheon plate, cream and gold knobs, handle and cabinet fittings. ★ Weight—with long-life 7 1/2 v. battery—3 1/2 lb. ★ Mullard high-grade transistors throughout. ★ High-Flux 7in. x 4in. Elliptical Speaker. ★ Slow motion tuning. ★ Co-axial socket at rear for direct connection to Car Radio Aerial. ★ Improved reception by use of five-section telescopic aerial disappearing into cabinet when closed. 3 1/2in. above Cabinet when fully extended. Construction simplified by Bakelite chassis board with the following components already mounted: I.F. Transformer (3), Oscillator Coil, Trimmer Bank, Output Transformer, Interstage Transformer, Aerial Brackets and Earth Bar. **SPECIAL INCLUSIVE PRICE** for all required components. Full assembly instructions—nothing more to buy—**£9.19.6**, plus 3/6 P. & P. Alignment service available. Full assembly instructions and individually priced parts list, all of which are available separately. 2/6. Post Free.



## "POPULAR FOUR"



## IMPROVED APPEARANCE AND PERFORMANCE

A new three valve plus miniature contact-cooled rectifier mains T.R.F. Receiver is now available. New De Luxe Cabinet polished walnut finish, cream trim, attractive horizontal dial (as illustrated) Quality 5in. P.M. speaker. Special wound high gain super-sensitive Denco coils. Medium and Long Wavebands. Excellent Continental reception! Overall dimensions: 12in. x 6in. x 5in. A.C. 200/250 v. Simple construction with guaranteed results. Easy to follow practical and theoretical diagrams supplied. All necessary components, down to the last nut and bolt, are offered at a **SPECIAL INCLUSIVE PRICE OF £5.5.0**, plus 3/6 P. & P. Instruction book available separately 1/6 post free. The same circuit is available in attractive White or Brown Bakelite Cabinet with rectangular dial at **97/6 ONLY**, plus 3/6 P. & P. **ALL PARTS AVAILABLE SEPARATELY.**

**STOP PRESS!** The well known Brayhead Tonic "SUPER 60" Radio Kit. A complete kit to make your own transistorised Transmitter and Receiver. No soldering reqd. 7 different circuits to build. Ideal Xmas Gift—in original manufacturer's coloured box with instructions. (As nationally advertised at £5.48) Few only at 49/6. P. & P. 4/-

## THE "CITIZEN" NEW LOW PRICE 85/-

Our Sensitive 5Stage (transistor plus diode) pocket transistor receiver, for full medium wave reception with the following outstanding features:



- ★ Completely self-contained—No external aerial or earth required
- ★ Genuine 2 1/2in. High Flux P.M. Speaker
- ★ Push-pull Output—250 milliwatts
- ★ Genuine Mullard transistors
- ★ Socket provided for personal listening
- ★ Socket provided for connection to Car Aerial
- ★ Volume Control with on/off switch—Condenser tuning
- ★ Easy assembly on pre-tagged circuit board
- ★ Attractive red polystyrene cabinet measures 5 1/2 x 3 x 1 1/2 in. chrome handle, attractive dial. All required components including full instructions, included at special inclusive price of only **85/-**. (Yes, Eighty-Five Shillings Only!) Plus 2/6 P. & P. Nothing more to spend. Suitable crystal dead-air type miniature earpiece fitted with miniature jack plus at 7/6 extra only! If req. All parts available separately—itemised list and full assembly instructions, sent for 1/6 post free. Hear this amazing little receiver working, at any of our branches.

Tel: Mitcham 6201

Open Daily to Callers

# R S T

All Valves Brand New  
and Fully Guaranteed

211 STREATHAM ROAD, MITCHAM, SURREY

Special 24 Hour Express Mail Order Service

AC2PEN 21/-	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	SZ4GT 12/6	6LD20 14/-	12C8 8/6
AC2PEN DD 32/-	ECCF80 8/6	EZ40 7/-	PCF82 7/-	U14 9/-	VMS4B 12/6	6A7 9/-	6P25 10/6	12J5GT 4/-
ACTP 21/-	ECCF82 8/6	EZ41 7/-	PCF84 16/-	U22 8/-	VP4 15/6	6A8G 8/6	6P28 17/6	12J7GT 8/6
ACVP1 17/6	ECH3 21/-	EZ80 7/-	PCF86 15/-	U24 21/-	VP4A 17/6	6A8GT 13/6	6Q7 6/6	12K7GT 5/-
AZ1 15/-	ECH21 22/-	EZ81 7/-	PCL82 9/6	U25 12/6	VP4B 17/6	6A8B 9/-	6Q7GT 8/6	12K8GT 10/-
AZ31 10/-	ECH42 9/6	EZ90 7/-	PCL83 12/6	U26 10/-	VR10530 7/-	6A9B 9/6	6SA7 7/-	12Q7GT 6/6
B36 10/-	ECH35 10/6	E1148 2/-	CPL84 10/6	U27 8/-	VR15030 7/-	6AK5 5/-	6S67 7/-	12SA7 8/6
C1C 12/6	ECH81 8/-	FC2 21/-	PCL85 16/-	U31 9/-	VU39 9/-	6AK8 7/6	6SH7 6/-	12SK7 6/-
CBL31 21/6	ECH83 8/6	FC2A 21/-	PENA4 17/6	U35 17/6	VU111 2/6	6AL5 6/-	6SJ7 6/6	12SQ7 8/6
CCH35 12/6	ECL80 9/-	FC4 15/-	PENB4 17/6	U37 17/6	VU120 2/6	6AM5 5/-	6SK7 5/6	12SL7 10/-
CL33 18/6	ECL81 10/-	FC13 21/-	PEN4DD 25/-	U43 8/6	W61 11/-	6AM6 4/-	6SL7GT 6/-	12SN7 8/-
CY1 15/-	ECL82 9/6	FC13C 21/-	PEN4VA 17/6	U45 10/-	W76 5/-	6AN5 7/6	6SN7GT 5/6	13D3 12/6
CY31 15/9	ECL83 12/-	FW4/500 9/-	PEN45 10/-	U47 12/6	W77 4/-	6AQ8 9/6	6U4GT 7/6	14H7 10/-
D77 4/-	EF6 21/-	FW4/800 9/-	PEN36C 21/-	U50 7/6	W81 6/-	6A6T6 6/-	6U6G 7/6	14S7 15/-
DAC32 9/6	EF9 21/-	GZ30 10/6	PEN45 10/-	U52 4/-	W81M 6/-	6A6T6 6/-	6V6G 4/6	19A9S 8/-
DAF91 7/6	EF22 14/-	GZ32 10/6	PEN45 10/-	U76 7/6	X17 8/6	6A6T6 6/-	6V6G 4/6	19B6G 21/-
DAF96 8/6	EF37 8/-	GZ33 13/6	PEN45 10/-	U78 4/6	X18 9/-	6B8G 3/-	6V6GT 8/-	20D1 10/-
DCC90 14/9	EF37A 8/-	GZ37 19/3	PEN45 10/-	U81 15/-	X41 15/-	6B8G 3/-	6V6GT 8/-	20F2 17/6
DF33 10/-	EF40 15/-	H41DD 8/6	PEN45 10/-	U82 19/6	X61 12/6	6BE6 6/-	6X4 4/6	20L1 17/6
DF91 4/-	EF41 8/-	HL92 8/6	PEN45 10/-	U301 22/6	X65 12/6	6B8G 8/-	6X6 15/-	20P1 25/-
DF92 7/6	EF42 10/-	HLI33DD 25/-	PEN45 10/-	U329 12/6	X76 12/6	6B8G 8/-	6X6 15/-	20P3 25/-
DF96 8/6	EF50A 4/-	HN309 20/-	PEN45 10/-	U339 15/-	X78 21/-	6B8G 8/-	6X6 15/-	20P4 22/-
DF97 9/6	EF50E 3/6	IV4/350 10/-	PEN45 10/-	U403 10/-	X79 21/-	6B8V7 12/6	6X6 15/-	20P5 25/-
DH63 6/6	EF80 5/-	IV4/350 10/-	PEN45 10/-	U404 10/-	Y61 10/-	6B8V7 12/6	6X6 15/-	21B6 12/-
DH77 7/6	EF85 5/-	IV4/350 10/-	PEN45 10/-	U801 29/-	Y66 9/6	6B8V7 12/6	6X6 15/-	25A6 8/-
DK32 11/6	EF86 10/6	KT33C 8/-	PEN45 10/-	PL82 8/-	Z63 7/6	6B8V7 12/6	6X6 15/-	25L6 8/-
DK91 8/6	EF89 9/-	KT36 17/6	PEN45 10/-	PL83 10/6	Z66 10/-	6B8V7 12/6	6X6 15/-	25S5 8/-
DK92 8/6	EF91 4/-	KT55 17/6	PEN45 10/-	PL84 9/-	Z77 4/-	6C4 3/6	6X6 15/-	25Z4 7/6
DK96 8/6	EF92 4/-	KT61 9/6	PEN45 10/-	PL820 18/-	Z152 5/-	6C5GT 8/-	6X6 15/-	25Z5 8/-
DL33 8/6	EF95 7/6	KT66 15/6	PEN45 10/-	PM24M 13/6	ZD17 8/-	6C6 6/6	6X6 15/-	25Z6 8/-
DL35 10/6	EF97 12/6	KT76 10/-	PEN45 10/-	PX4 15/-	ZD152 8/6	6C9 12/6	6X6 15/-	27SU 17/6
DL92 7/6	EF98 10/-	KT81 15/-	PEN45 10/-	PX25 25/-	ZD6G 32/-	6CD6G 32/-	6X6 15/-	30C1 9/6
DL93 7/6	EF183 18/-	KT88 21/-	PEN45 10/-	PY31 15/-	6CH6 10/-	6CH6 10/-	6X6 15/-	30F1 10/6
DL94 8/6	EF184 14/-	L63 5/-	PEN45 10/-	PY32 12/6	6D2 4/-	6D2 4/-	6X6 15/-	30FL1 10/6
DL96 8/6	EFK32 8/6	LN152 9/-	PEN45 10/-	PY80 7/6	6E5 5/6	6E5 5/6	6X6 15/-	30L1 9/6
EA50 2/-	EL2 21/-	LN309 12/6	PEN45 10/-	PY81 7/6	6E5 10/-	6E5 10/-	6X6 15/-	30L15 11/6
EABC80 6/-	EL3 21/-	LZ319 12/6	PEN45 10/-	PY82 7/6	6F1 10/6	6F1 10/6	6X6 15/-	30P4 21/-
EAC91 4/-	EL6 21/-	MKT4 17/6	PEN45 10/-	PY83 8/6	6F6 6/6	6F6 6/6	6X6 15/-	30P12 10/-
EAF42 9/6	EL32 4/6	MS4B 17/6	PEN45 10/-	PZ30 18/6	6F12 4/-	6F12 4/-	6X6 15/-	30P16 4/-
EB34 2/6	EL33 10/-	MVSPEN 17/6	PEN45 10/-	QS9510 10/-	6F12 4/-	6F12 4/-	6X6 15/-	30P16 4/-
EB41 7/6	EL34 15/-	MVSPENB 17/6	PEN45 10/-	R2 10/-	6F13 10/-	6F13 10/-	6X6 15/-	30P16 4/-
EB91 4/-	EL35 10/-	MU14 17/6	PEN45 10/-	R3 10/-	6F14 10/-	6F14 10/-	6X6 15/-	30P16 4/-
EBC31 21/-	EL37 17/6	MX40 15/-	PEN45 10/-	R12 8/6	6F15 12/6	6F15 12/6	6X6 15/-	30P16 4/-
EBC33 4/6	EL38 21/-	N18 8/-	PEN45 10/-	R16 17/6	6F19 12/6	6F19 12/6	6X6 15/-	30P16 4/-
EBC41 9/6	EL41 10/-	N37 14/-	PEN45 10/-	R19 19/-	6F23 10/6	6F23 10/6	6X6 15/-	30P16 4/-
EBC81 10/-	EL42 10/-	N78 17/6	PEN45 10/-	R20 19/-	6F33 5/6	6F33 5/6	6X6 15/-	30P16 4/-
EBF80 8/6	EL81 12/6	N108 18/6	PEN45 10/-	R19 19/-	6G6 2/-	6G6 2/-	6X6 15/-	30P16 4/-
EBF83 8/6	EL84 6/9	N108 18/6	PEN45 10/-	R20 19/-	6H6 2/-	6H6 2/-	6X6 15/-	30P16 4/-
EBF89 8/6	EL85 10/-	N108 18/6	PEN45 10/-	S130 7/6	6I4 6/5	6I4 6/5	6X6 15/-	30P16 4/-
EBL21 22/-	EL90 8/6	N308 20/-	PEN45 10/-	SP41 3/6	6J5 4/6	6J5 4/6	6X6 15/-	30P16 4/-
EBL31 21/6	EL91 4/-	N339 15/-	PEN45 10/-	SP61 3/6	6J5 4/6	6J5 4/6	6X6 15/-	30P16 4/-
ECC34 15/-	EL95 10/6	N369 10/6	PEN45 10/-	SU2150 25/-	6K7 2/6	6K7 2/6	6X6 15/-	30P16 4/-
ECC35 8/6	EM80 8/6	OD3 5/-	PEN45 10/-	SU2150A 25/-	6K7GT 7/6	6K7GT 7/6	6X6 15/-	30P16 4/-
ECC40 21/-	EM81 8/6	OZ4 5/-	PEN45 10/-	UL85 7/6	6K8 8/6	6K8 8/6	6X6 15/-	30P16 4/-
ECC81 5/9	EM84 9/6	P2 10/-	PEN45 10/-	UL85 7/6	6K8 8/6	6K8 8/6	6X6 15/-	30P16 4/-
ECC82 8/6	EM85 10/-	PABC80 13/-	PEN45 10/-	UM80 10/6	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
ECC83 7/6	EY51 8/6	PCC84 9/-	PEN45 10/-	UR1C 15/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
ECC84 8/6	EY81 8/6	PCC85 9/-	PEN45 10/-	U4 15/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
ECC85 8/-	EY83 15/-	PCC88 15/-	PEN45 10/-	U6 19/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
ECC88 17/6	EY86 8/6	PCC89 9/6	PEN45 10/-	U8 21/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
			PEN45 10/-	U9 7/6	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
			PEN45 10/-	U10 9/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
			PEN45 10/-	U11 9/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
			PEN45 10/-	U12 9/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
			PEN45 10/-	U13 9/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
			PEN45 10/-	U14 9/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
			PEN45 10/-	U15 9/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
			PEN45 10/-	U16 9/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
			PEN45 10/-	U17 9/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
			PEN45 10/-	U18 9/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
			PEN45 10/-	U19 9/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
			PEN45 10/-	U20 9/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
			PEN45 10/-	U21 9/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
			PEN45 10/-	U22 9/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
			PEN45 10/-	U23 9/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
			PEN45 10/-	U24 9/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
			PEN45 10/-	U25 9/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
			PEN45 10/-	U26 9/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
			PEN45 10/-	U27 9/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
			PEN45 10/-	U28 9/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
			PEN45 10/-	U29 9/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
			PEN45 10/-	U30 9/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
			PEN45 10/-	U31 9/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
			PEN45 10/-	U32 9/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
			PEN45 10/-	U33 9/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
			PEN45 10/-	U34 9/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
			PEN45 10/-	U35 9/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
			PEN45 10/-	U36 9/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
			PEN45 10/-	U37 9/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
			PEN45 10/-	U38 9/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
			PEN45 10/-	U39 9/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
			PEN45 10/-	U40 9/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
			PEN45 10/-	U41 9/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
			PEN45 10/-	U42 9/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
			PEN45 10/-	U43 9/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
			PEN45 10/-	U44 9/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
			PEN45 10/-	U45 9/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
			PEN45 10/-	U46 9/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
			PEN45 10/-	U47 9/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
			PEN45 10/-	U48 9/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
			PEN45 10/-	U49 9/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
			PEN45 10/-	U50 9/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	30P16 4/-
			PEN45 10/-	U51 9/-	6K8GT 9/6	6K8GT 9/6	6X6 15/-	


## R.S.C. HI-FI TAPE RECORDER KIT

**REALISM AT INCREDIBLY LOW COST, CAN BE ASSEMBLED IN HALF AN HOUR**  
 The Recorder Incorporates the Latest Collo Studio Tape Transcriber. The Linear LT45X High Quality Tape Amplifier listed £12.12.0 High Flux P.M. Speaker listed 30/-, empty Tape Spool, a Reel of Best quality Tape listed 22/6, and a Handsome Portable carrying Cabinet with latest attractive two-tone polychrome finish, size 18 x 13 x 9in. high, listed £4.10.0, and circuit. Total cost if purchased individually approximately £40. Performance equal to units in the £80-£90 class. S.A.E. for leaflet.

## HIGH FIDELITY 12-14 WATT AMPLIFIER TYPE A11
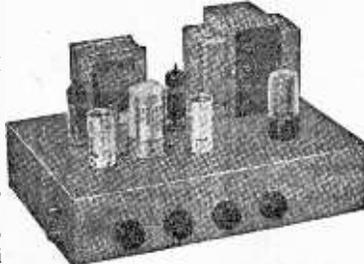
### PUSH-PULL ULTRA LINEAR OUTPUT "BUILT-IN" TONE CONTROL PRE-AMP STAGES

Two input sockets with associated controls allow mixing of "mike" and gram, as in A10. 'High sensitivity'. Includes 5 valves, ECC83, ECC83, EL84, EL84, 5Y3. High quality sectionally wound output transformer specially designed for Ultra Linear operation and reliable small condensers of current manufacture. INDIVIDUAL CONTROLS FOR BASS AND TREBLE "LIFT" and "CUT". Frequency response + 3 D.B. 30-30,000 c/s. Six negative feedback loops. Hum level 60 D.B. down. ONLY 23 millivolts INPUT required for FULL OUTPUT. Suitable for use with all makes and types of pick-ups and microphones. Comparable with the very best designs. For STANDARD or LONG PLAYING RECORDS For MUSICAL INSTRUMENTS such as STRING BASS, VIOLINS, etc. OUTPUT SOCKET with plug provides 300 v. 30 mA. and 6.3 v. 1.5 a. For supply of a RADIO FEEDER UNIT. Size approx. 12-9-7in. For A.C. mains 200-250 v. 50 c.p.s. Output for 3 and 15 ohms speakers. Kit is complete to last nut. Chassis is fully punched. Full instructions and point-to-point wiring diagrams supplied. Only **8 Gns.** Carr. 10/- (Or factory built 5/- extra). If required lowered metal cover with 2 carrying handles can be supplied for 18/9. TERMS ON ASSEMBLED UNITS. DEPOSIT 24/9, and 8 monthly payments of 24/9. Send S.A.E. for illustrated leaflet detailing Ready-to-assemble Cabinets, Speakers, Microphones etc. with cash and credit terms.



**25 1/2 GNS.**

Carr. 17/6

**H.P. TERMS, Deposit £5.7.6 and 12 monthly payments of 2 gns. Cash price if settled in 3 months.**

**TELEVISION RECTIFIERS 250 v. 200 mA. small size. Only 6/9 each.**

**COLLARO CONQUEST 4-SPEED AUTO-CHANGER**, with high fidelity Studio pick-up. Latest model. For 200-250 v. 50 c.p.s. A.C. mains. Our price £6.19.6. Carr. 5/6.

**COLLARO RC 457 4 SPEED MIXER AUTO-CHANGERS**, Turnover Studio Pick-up head, for 200-250 v. A.C. £7.19.6. Carr. 4/6.

**THE SKYFOUR T.R.F. RECEIVER.** A design of a 3 valve long and medium wave 200-250 v. A.C. Mains receiver with selenium rectifier, High gain H.F. stage and low distortion detector. Valve line-up 6KT, SP61, 6V6G. Selectivity and quality excellent. Simple to construct. Point-to-Point wiring diagrams, instructions and parts list. 1/9, maximum building costs £4.19.6, inc. attractive Walnut veneered wood cabinet 12 x 9 1/2 x 5 1/2 in.

**GL3A MINIATURE 2-3 WATT GRAM AMPLIFIER.** For use with any single or auto-change unit. Output for 2-3 ohm speaker. For 200-250 v. A.C. mains. Size 11 x 2 1/2 x 2 1/2 in. Controls: Vol. and Tone with switch. Only 5/6.

## R.S.C. STEREO/TEN HIGH QUALITY AMPLIFIER



A complete set of parts for the construction of a stereophonic amplifier giving 5 watts high quality output on each channel (total 10 watts). Sensitivity is 50 millivolts, suitable for all crystal stereo heads. Ganged Bass and Treble Controls give equal variation of "lift" and "cut". Provision is made for use as straight (monaural) 10 watt amplifier. Valve line-up ECC83, ECC83, EL84, EZ81. Outputs for 2-3 ohm speakers. Point-to-Point wiring diagrams and in- **8 Gns.** Full instructions supplied. Send S.A.E. for leaflet. Full constructional details and price list 2/6. Carr. 10/- Kit can be supplied assembled, ready for use, for 59/6 extra.

## R.S.C. BATTERY CHARGING EQUIPMENT

All for A.C. Mains 200-250v., 50c/s. Guaranteed 12 months.

**HEAVY DUTY CHARGER KIT** 6/12 v. 8 amps, variable output. Consisting of Mains Transformer, 0-200-230-250 v. 50 W. (Bridge) Selenium Rectifier; Ammeter, Variable Charge Rate Selector Panels, Plugs, Fuses, Fuseholder and circuit. 59/9, Carr. 4/6.



**Assembled 6 v. or 12 v. 4 amps.** Fitted Ammeter and variable charge rate selector. Also selector plug for 6 v. or 12 v. charging. Louvered steel case with stoved blue hammer finished. Fused 69/6 and ready for use with Carr. 5/- mains and output leads. Terms: Deposit 13/3 and 5 monthly payments 13/3. 6/12 v. 3a., all facilities as above. Only 59/9, carr. 3/9.

**ASSEMBLED CHARGERS** 6 v. or 12 v. 2 amps. Fitted Ammeter and selector plug for 6 v. or 12 v. Louvered metal case finished attractive hammer blue. Ready for use with mains and output leads. Double Fused. Carr. 3/9 **49/9**

**BATTERY CHARGER KITS** Consisting of Mains Transformer, F.W. Bridge, Metal Rectifier, well ventilated steel case. Fuses. Fuse-holders. Grommets, panels and circuit. Carr. 3/6 extra. 6v. or 12v. 1 amp. .... 24/9 As above, with Ammeters 32/9 6 v. 2 amps. .... 25/9 6v. or 12v. 2 amps. .... 31/6 6 v. or 12 v. 2 amps. inclusive of Ammeter. .... 42/9 6v. or 12 v. 4 amps. .... 49/9 6 v. or 12 v. 4 amps. with Ammeter and variable charge rate selector. .... 59/9 **CHARGER AMMETERS.** 0-15 a., 0-3 a., 0-4 a., 0-7 a., 0-25 a., 0-60 a. 8/9.

**DEAF AID EARPIECES.** Low Impedance with lead, 8/8. High Impedance Crystal 8/9.

**MICROPHONE INSERTS.** Crystal type 8/9.

**SOLDERING IRONS.** 230-250 v. 30 watts. First quality. For Radio work. 19/9. Spare elements and bits available.

## R.S.C. MAINS TRANSFORMERS

Interleaved and Impregnated. Primaries 200-230-250 v. 50 c/s. Screened TOP SHROUDED DROP THROUGH  
 250-0-250 v. 10 mA. 6.3 v. 2 a. 5 v. 2 a. 17/9  
 350-0-350 v. 80 mA. 6.3 v. 2 a. 5 v. 2 a. 18/9  
 250-0-250 v. 100 mA. 6.3 v. 2 a. 6.3 v. 1 a. 21/9  
 250-0-250 v. 100 mA. 6.3 v. 3.5 a. C.T. ... 19/9  
 250-0-250 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. 25/9  
 300-0-300 v. 130 mA. 6.3 v. 4 a. 6.3 v. 1 a. for Mullard 510 Amplifier ... 29/9  
 300-0-300 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. 28/9  
 350-0-350 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. 26/9  
 350-0-350 v. 100 mA. 6.3 v. 4 v. 4 a. C.T. 0-5 v. 3 a. 28/9  
 350-0-350 v. 150 mA. 6.3 v. 4 a. 5 v. 3 a. 29/9  
**FULLY SHROUDED UPRIGHT** 250-0-250 v. 60 mA. 6.3 v. 2 a. 5 v. 2 a. Midret type 24-3-3in. ... 17/11  
 250-0-250 v. 100 mA. 6.3 v. 2 a. 5 v. 3 a. 27/9  
 300-0-300 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. 27/11  
 350-0-350 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. 27/11  
 350-0-350 v. 150 mA. 6.3 v. 4 a. 5 v. 3 a. 35/9  
 425-0-425 v. 230 mA. 6.3 v. 4 a. C.T. 6.3 v. 4 a. C.T. 5 v. 3 a. ... 49/9

## FILAMENT TRANSFORMERS (FULLY GUARANTEED)

All with 200-250 v. 50 c/s. primaries 6.3 v. 1.5 a. 5/9; 6.3 v. 2 a. 7/9; 0-4-6.3 v. 2 a. 7/9; 12 v. 1 a. 7/11; 6.3 v. 3 a. 8/11; 6.3 v. 6 a. 17/9; 12 v. 1.5 a. twice, 17/6.  
**OUTPUT TRANSFORMERS**  
 Midret Battery Pentode 66:1 for 354, etc. ... 3/9  
 Small Pentode, 500Ω to 3Ω ... 3/9  
 Small Pentode 7/8,000Ω to 3Ω ... 3/9  
 Standard Pentode 5,000Ω to 3Ω ... 5/9  
 Standard Pentode 7/8,000Ω to 3Ω ... 5/9  
 10,000Ω to 3Ω ... 5/9  
 Push-Pull 4 watts, EL84, or 6V6 to 3% or matched to 15Ω ... 9/9  
 Push-Pull 10-12 watts to match 6V6 or EL84 to 3-5-8 or 15% ... 19/9  
 Following types for 3 and 15Ω speakers:  
 Push-Pull 10-12 watts 6V6 or EL84 ... 13/9  
 Push-Pull 15-18 watts, 6L6, KT66 ... 22/9  
 Push-Pull for Mullard 510 Ultra Linear ... 29/9  
 Push-Pull 20 watts, sectionally wound, 6L6, KT66, etc. ... 49/9

**MIDGET MAINS** Primaries 200-250 v. 50 c/s. 250 v. 60 mA. 6.3 v. 2 a. ... 11/9  
 250-0-250 v. 60 mA. 6.3 v. 2 a. ... 12/9  
 Both above size 2 1/2 x 2 1/2 in.  
**SMOOTHING CHOKES** 150 mA, 7-10H 250 ohms ... 11/9  
 100 mA, 10 H 200 ohms ... 8/9  
 80 mA, 10 H 350 ohms ... 5/9  
 60 mA, 10 H 400 ohms ... 4/11  
**PARMEKO POTTED TYPES** 200 mA, 12 H 200 ohms ... 18/9  
 120 mA, 30 H 200 ohms ... 16/9  
 120 mA, 8 H 50 ohms ... 13/9  
**CHARGER TRANSFORMERS** All with 200-230-250 v. 50 c/s Primaries: 0-9-15 v. 1 1/2 a. 11/9; 0-9-15 v. 2 a. 14/9; 0-9-15 v. 3 a. 16/9; 0-9-15 v. 5 a. 19/9; 0-9-15 v. 6 a. 23/9; 0-9-15 v. 8 a. 25/9.  
**AUTO (Step-up/Step down) TRANS.** 0-110/120-230/250 v. 50-80 watts, 13/8; 150 watts, 27/9. 250 watts 39/9.  
**MICROPHONE TRANSFORMERS** 120:1 high grade, clamped, 6/9; 120:1 Potted, Mu-metal screened, 9/9.

**R.S.C. (Manchester) Ltd. LIVERPOOL, LEEDS, BRADFORD, MANCHESTER**

**R.S.C. A12 STEREOPHONIC AMPLIFIER KIT WITH TWIN SPEAKERS**

A complete set of parts to construct a good quality Stereo amplifier with an undistorted output total 6 watts. For A.C. mains input of 200-250 v. Outputs for matched 2-3 ohm speakers. Sensitivity 130 m.v. Ganged Vol. and Tone Controls. Preset balance control. Full instructions and point-to-point wiring diagrams supplied.

**STEREO EQUIPMENT OFFER-**  
Comprising A12 Kit, 2 matched 8in. 1 1/2" speakers, and Acos T10 Stereo head suitable most pickups. **£6.19.6** Carr. 7/6.

**PICK-UP ARMS** complete with Hi-Fi turnover crystal head. Acos GP54. Limited number brand new, perfect at approx. half price. Only 29/11.

**ACOS CRYSTAL MICROPHONES.** M140 stand or desk. Listed 35/- Only 27/9. 39-1 Stick type. Listed 3 gns. Only 35/6.

**R.S.C. 30 WATT ULTRA LINE HIGH FIDELITY AMPLIFIER A10**  
A highly sensitive Push-Pull high output unit with self-contained Pre-amp. Tone Control Stages. Certified performance figures compare equally with most expensive amplifiers available. Hum level 70 db. down. Frequency response ± 3 db 30-30,000 c/s. A specially designed sectionally wound ultra linear output transformer is used with 807 output valves. All components are chosen for reliability. Six valves are used: EF86, EF86, ECC83, 807, 807, G233. Separate Bass and Treble Controls are provided. Minimum input required for full output is 12 millivolts so that ANY KIND OF MICROPHONE OR PICK-UP IS SUITABLE. The unit is designed for CLUBS, SCHOOLS, THEATRES, DANCE HALLS or OUTDOOR FUNCTIONS, etc. For use with Electronic ORGAN, GUITAR, STRING BASS, etc. For standard or long-playing records, OUTPUT SOCKET PROVIDES L.T. and H.T. for a RADIO FEEDER UNIT. An extra input with associated vol. control is provided so that two separate inputs such as Gram, and 'Mike' can be mixed. Amplifier operates on 200-250 v. 50 c/s. A.C. Mains and has output for 3 and 15 ohm speakers. Complete kit of parts with fully punched chassis and point-to-point wiring diagrams and instructions. If required perforated cover with carrying handles can be supplied for 19/9. The amplifier can be supplied, factory built with EL34 output valves and 12 months guarantee for 4 Gns.

**TERMS: DEPOSIT 33/9** and 9 monthly payments of 33/9. Suitable microphones and speakers available at competitive prices.

**FULL RANGE OF LINEAR AMPLIFIERS ALWAYS IN STOCK.**

**COLLARO JUNIOR** 4-speed single player units and Hi-Fi crystal pick-up with turn-over head, £3.19.6.

**B.S.R. UAS 4-SPEED AUTO-CHANGERS** with Hi-Fi turnover pick-up head, £6.19.6. Carr. 5/-.

**4 Gns.**

Carr. and pkg. 5/-

**Jason FM/IT V.H.F./FM Radio Tuner design.** Total cost of parts including valves, Tuning dial, Escutcheon, etc. £6.19.6.

**LINEAR L45 MINIATURE 4 1/2 WATT QUALITY AMPLIFIER.** Suitable for use with any record playing unit, and most microphones. Negative feed-back 12db. Separate Bass and Treble Controls. For A.C. mains input of 200-250 v. 50 c/s. Output for 2-3 ohm speaker. Three miniature Mullard valves used. Size of unit only 7-5 1/2in. high. Guaranteed for 12 months. Only £5.19.6. Send S.A.E. for illustrated leaflet. Terms: Deposit 22/6 and 5 monthly payments of 22/6.

**12in. 10 WATT HIGH QUALITY LOUD-SPEAKER IN POLISHED WALNUT FINISHED CABINET**



Gauss 12,000 lines. Speech coil 3 ohms or 15 ohms. Only £4.19.6 Carr. 5/-. Terms: Deposit 11/3 and 8 monthly payments of 11/3. **12in. 20 WATT HI-FI LOUD-SPEAKERS IN CABINETS.** Size 18 x 18 x 10in. Finish as above. Terms: Deposit 17/9 and 3 monthly payments of 17/9. Only £7.19.6. Carr. 5/6.

**R.S.C. 4.5 WATT A5 HIGH-GAIN AMPLIFIER**



A highly sensitive 4-valve quality amplifier for the home, small club, etc. so that it is suitable for use with the latest high fidelity pick-up heads, in addition to all other types of pick-ups and practically all 'mikes'. Separate Bass and Treble Controls are provided. These give full tone-playing record equalization. Hum level is negligible being 71db. down 15db. of Negative feedback is used. H.T. or 300 v. 25 mA. and L.T. or 6.3 v. 1.5 A. is available for the supply of a Radio Feeder Unit, or Tape-Deck pre-amplifier. For A.C. mains input of 200-250 v. 50 c/s. Output for 2-3 ohm speaker. Chassis is complete in every detail and includes fully punched chassis (with base plate) with blue hamer finish and point-to-point wiring diagrams and instructions. Exceptional value at only £4.15.0, or assembled ready for use 25/- extra. plus 3/6 carr.; or Deposit 22/6 and 5 monthly payments of 22/6 for assembled unit.

**R.S.C. PORTABLE GUITAR AMPLIFIERS.** (For 200-250v. A.C. Mains) Junior 5 watts High Quality output. Separate Bass and Treble "Cut" and "Boost" controls. Sensitivity 15 m.v. Twin inputs. High Flux 8in. Loudspeaker "built-in". Handsome, strongly made Cabinet (size approx. 14 x 14 x 7in.) finished in attractive and durable polycrome, and fitted carrying handle. Terms: Deposit £1 and 9 monthly payments of £1.

**Senior 10 watts High Fidelity Output** Separate Bass and Treble "Cut" and "Boost" controls. Twin separately controlled high gain inputs so that two instruments such as Guitar and String Bass can be used at the same time. Two loudspeakers are incorporated, a high Flux 12in. for Bass notes and a 7 x 4 m. elliptical for Treble. Cabinet is well made and finished as Junior model. Size approx. 18 x 18 x 9in. H.P. Terms. Deposit 34/9 and 9 monthly payments of 34/9. Carr. 10/-.

**Super Hi-Fi 15 Watt.** All facilities as 10 watt. Cabinet size 18 x 18 x 10ins. Terms: Deposit £2.11.6, and nine monthly payments of 51/6. Cash 22 gns. Carr. 12/6. **£8.19.6**

**R.S.C. BASS REFLEX CABINETS, JUNIOR MODEL.** Specially designed for W.B. HF1012 Speaker, but suitable for any good quality 10in. speaker. Acoustically lined and ported. Polished walnut veneer finish. Size 18 x 12 x 10in. Handsome appearance. Ensure superb reproduction for only £3.19.6.

**STANDARD MODEL** As above but for 12in. speakers. Size 20 x 15 x 13in. Especially recommended for Plessey Dual Concentric Speaker, £5.19.6. Suitable for sets of 4, legs with brass ferrules, 25/- per set of 4.

**PLESSEY DUAL CONCENTRIC 12in. 15 ohms HIGH FIDELITY SPEAKER** (12,000 lines) with built-in tweeter (completely separate elliptical speaker with choke, condensers, etc.) providing extraordinarily realistic reproduction when used with our All or similar amplifier. Rated 10 watts. Price only £5.19.6.


**P.M. SPEAKERS.** 2-3 ohm, 2 1/2in. Perdio 21/9. 5in. 17/9. 6in. 21/9. 8in. 19/9. 8 x 5in. 25/9. 10in. 29/9. 10 x 6in. 29/9. 12in. 29/11. 10in. W.B. "Stentorian" 3 or 15 ohms type HF1012 10 watts. hi-fidelity type. Recommended for use with our All Amplifier. £4.12.9. 12in. R.A. 3 ohms 10 watts (12,000 lines). 59/6.

**TWEETERS.** Plessey 30 19/9. 15 5 25/9. **HI-FI CRYSTAL PICK-UP HEADS.** (Turnover type with sapphire stylus.) Acos. Standard replacement for Garrard and B.S.R. B.S.R. Ful-n. Garrard GC2, 19/9. Acos. Stereo-Monaural 49/9.

**R.S.C. EQUIPMENT CABINET.** Dimensions and outer appearance identical with Standard Bass Reflex Cabinet. Top hinge and Bass board adjustable. Will take Tape Deck or Player Unit, and Amplifier plus F.M. or A.M./F.M. Unit. Only 6 gns. **SUPERBET FEEDER UNIT.** Design of a high quality Radio Tuner Unit (especially suitable for use with any of our Amplifiers). Delayed A.V.C. Controls are Tuning, W/Ch. and Vol. Only 25v. 15 mA. H.T. and L.T. of 6.3 v. 1 amp. required from amplifier. Size of unit approx. 9-6 7/8in. high. Simple alignment procedure. Point-to-Point wiring diagrams. Instructions and priced parts list with illustration. 2/6. Total building cost £4.15.0. For leaflet send S.A.E.

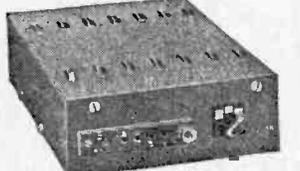**R.S.C. BATTERY TO MAINS CONVERSION UNITS**

Type BM1. All-dry battery eliminator. Size 5 1/4 x 4 1/4 x 2 1/2in. approx. Completely replaces battery supplying 1.4 v. and 90 v. where A.C. mains 200-250v. 50 c/s is available. Suitable for all battery portable receivers requiring 1.4 v. and 90 v. This includes latest low consumption types. Complete kit with diagrams, 39/9, or ready to use, 46/9.



Type BM2. Size 9 x 5 1/2 x 2 1/2in. Supplies 120 v. 90 v. and 60 v. 40 mA. and 2 v. 0.4 a. to 1 amp. fully smoothed. Thereby completely replacing both H.T. batteries and L.T. 2 v. accumulators when connected to mains supply 200-250 v. 50 c/s. **SUITABLE FOR ALL BATTERY RECEIVERS** normally using 2 v. accumulator. Complete kit of parts with diagrams and instructions. 49/9, or ready for use, 59/6.

**LINEAR TAPE PRE-AMPLIFIER TYPE LP/1.** Switched Negative feedback equalization. Positions for Record (in. 3in., 7in. and Playback), EM54 Record Level indicator. Designed primarily as the link between a Collaro Tape Transcriber and a high fidelity amplifier, but suitable for almost any Tape Deck. Only 9 gns. S.A.E. for leaflet.

**TERMS: C.W.O. or C.O.D. No G.O.D. under £1.** Post 1/9 extra under £2. 3/3 extra under £5. Open 9 to 6. Weds. until 1 p.m., except Manchester open all week. Trade supplied. S.A.E. with all enquiries.

**R.S.C. (Manchester) Ltd.**

Mail Orders to 29-31 Moorfield Road, Leeds 12. Personal shoppers to any of branches below—  
73 Dale Street, Liverpool 2 | 5-7 County (Mecca) Arcade, Briggate, Leeds 1 | 8-10 Brown St. (Market St.), Manchester 2. | 56 Morley Street, (Above Alhambra Theatre), Bradford

# BENTLEY ACOUSTIC CORPORATION LTD.

38 CHALCOT ROAD, CHALK FARM, LONDON, N.W.1.

Telephone: PRIMROSE 9090

EXPRESS POSTAL SERVICE. ALL ORDERS DESPATCHED SAME DAY AS RECEIVED. TELEPHONE AND TELEGRAM ORDERS FOR CASH ON DELIVERY SERVICE ACCEPTED UP TO 3.30 P.M.

OA2	17/6	6F1	27/2	12AC6	15/8	77	8/1	DL68	15/-	EF50(A)	7/-	HVR2	20/-	PX4	10/6	UBF80	9/-	Z66	17/6
OB2	17/6	6F6G	7/-	12AD6	17/8	78	6/6	DL72	15/-	EF50(E)	5/-	HVK2A	6/-	PY31	10/6	UBF89	9/6	Z77	4/6
OZ4	5/-	6F12	4/6	12AE6	14/3	80	9/-	DL92	7/-	EF54	5/-	KF35	8/6	PY32	12/6	UBL21	23/10	Transistors	
IA5	6/-	6F13	11/6	12AH7	8/-	83	15/-	DL94	7/6	EF73	10/6	KL35	8/6	PY80	7/6	UCC84	14/11	and diodes	
IA7GT	12/-	6F23	10/6	12AH8	12/6	85A2	16/-	DL96	8/6	EF80	6/-	KLL32	25/2	PY81	8/6	UCC85	9/-	CG1C	3/-
IC5	12/6	6F24	12/6	12A16	7/6	90AG	67/6	DM70	7/6	EF85	6/-	KT2	5/-	PY82	7/6	UCC89	17/-	CG4E	3/-
ID6	10/6	6F33	7/6	12A7	6/-	90AV	67/6	EB0F	30/-	EF86	10/6	KT33C	10/-	PY83	8/6	UCH21	23/10	CG6E	3/-
IG6	17/6	6H6	3/-	12AU7	6/6	90C1	16/-	EB0F	30/-	EF89	9/-	KT36	30/7	PY88	13/6	UCH42	9/6	CG7E	7/6
IHSGT	10/6	6J5	5/-	12AX7	7/6	90CC	37/6	E180F	34/6	EF91	4/6	KT41	23/10	PZ30	20/5	UCH81	9/6	CG10E	3/-
IL4	3/6	6J6	5/6	12BA6	8/1	101	13/6	EAS0	27/6	EF92	4/6	KT44	12/6	QP21	7/-	UCL82	11/6	CG12E	3/-
ILD5	5/-	6J7G	6/-	12BE6	9/-	150B2	18/-	EAT6	9/6	EF97	13/7	KT61	12/6	QP25	14/6	UCL83	19/9	GD3	4, 5
ILN5	5/-	6J7GT	10/6	12BH7	21/9	185B7	34/-	EARC80	9/-	EF98	13/7	KT63	7/6	QS150/15	UF41	9/-	6, 8	4/-	
INSGT	10/6	6K7G	5/-	12J5GT	4/6	304	10/6	EAC91	4/6	EF183	19/1	KT66	15/-		UF42	12/6	OA70	3/-	
IR5	6/6	6K7GT	6/-	12J7GT	9/6	305	10/6	EAF42	9/-	EF184	12/6	KT88	24/-	R12	10/6	UF80	10/6	OA73	3/-
IS4	9/-	6K8GT	10/6	12K5	18/4	807	7/6	EB34	2/6	EK32	8/6	KTW61	6/6	R18	11/6	UF89	9/6	OA79	3/-
IS5	6/-	6K8G	6/6	12K7GT	5/6	956	3/-	EB41	8/6	EL32	5/-	KTW62	7/6	R19	20/5	UF89	18/4	OA81	3/-
IT4	3/6	6K25	20/5	12K8GT	14/-	1821	17/6	EB41	8/6	EL33	12/6	KTW63	6/6	RG1/240A	UF89	9/-	OA86	4/-	
I05	6/-	6L1	23/10	12Q7GT	5/-	4033L	12/6	EB3C	23/10	EL34	15/-	KTZ41	8/-		UL41	9/-	OA91	3/6	
2P	27/2	6L6G	6/6	12S2A7	8/6	5763	12/6	EB3C	5/-	EL38	27/2	KTZ63	7/6	RK34	54/-	UL44	27/2	OA95	3/6
3A4	4/6	6L6M	9/6	12S2C7	8/6	7193	5/-	EB4C1	8/6	EL41	9/-	L63	6/6	SP4(7)	14/6	UL46	14/6	OA210	11/-
3A5	10/6	6L7GT	7/6	12S2G7	7/-	7475	7/6	EB4C1	8/6	EL42	10/6	MHL4	7/6	SP41	3/6	UL84	8/6	OA211	20/-
3B7	12/6	6L18	13/-	12S2H7	8/6	9002	5/6	EBF80	9/-	EL81	17/-	MHLD6	12/6	SP42	12/6	UM4	17/8	OC16	48/-
3D6	5/-	6L20	16/4	12S2J7	8/6	AC/PCN		EBF83	14/3	EL83	20/5	ML4	8/6	SP61	3/6	UM34	17/8	OC19	48/-
3Q4	7/6	6N7	8/-	12S2K7	6/-	5-pin	23/10	EBF89	9/6	EL84	7/6	MS4B	23/10	SU25	27/2	UM80	15/8	OC22	28/-
3Q5GT	9/6	6P28	27/2	12S2L7	11/6	7-pin	15/10	EBL1	30/6	EL85	14/3	MU12/14	8/-	T41	9/-	UR1C	19/1	OC23	87/-
3S4	7/-	6Q7G	6/6	12S2R7	8/6	AC2/PCN		EBL2	23/10	EL86	17/8	N37	23/10	TD4	12/6	U06	20/5	OC26	25/-
3V4	7/6	6Q7GT	11/-	12Y4	10/6	DD	12/6	EBL31	23/10	EL91	5/-	N78	20/5	TH41	27/2	U08	27/2	OC28	25/-
5R4Y	17/6	6R7G	10/-	19AQ5	10/6	AC/PCN		EC52	5/6	EL95	10/6	N108	23/10	TP22	15/-	UY1N	19/1	OC35	25/6
5U4G	6/6	6S7GT	8/6	19H1	10/-	AC/CTP	34/-	EC54	6/-	EL820	19/1	N308	21/11	TP25	15/-	UY21	17/1	OC44	11/-
5V4G	10/-	6SCT	7/6	20D1	15/8	ATP4	5/-	EC70	12/6	EL821	27/2	N339	15/-	TP2620	34/-	UY41	7/6	OC45	10/-
5Y3	6/6	6S7GT	8/-	20F2	27/2	AZ1	19/1	EC81	27/6	EL822	19/6	P61	3/6	TY867	13/7	UY85	7/6	OC65	22/6
5Z3	20/5	6S7GT	8/-	20L1	27/2	AZ31	10/-	EC92	13/7	EM34	9/6	PABC80	14/3	UI2/14	8/6	VMP4A	15/-	OC66	25/-
5Z4G	9/-	6S7GT	8/-	20P1	27/2	AZ41	14/3	ECC32	5/6	EM71	23/10	PCC84	8/6	UI6	10/6	VMS4B	15/-	OC70	6/6
6A7	10/6	6S7GT	6/-	20P3	23/10	B36	15/-	ECC33	8/6	EM80	9/-	PCC85	9/6	UI9	48/6	VP2	12/6	OC71	6/6
6A8	9/-	6S7GT	6/6	20P4	27/2	BL63	7/6	ECC34	25/2	EM81	9/-	PCC88	18/6	U22	8/6	VP4	15/-	OC72	8/-
6A7	4/-	6S7GT	5/6	20P5	23/10	C1	12/6	ECC35	8/6	EM84	10/6	PCC89	11/6	U24	30/7	VP2B	14/6	OC73	16/-
6AG5	5/6	6S7GT	9/-	25A6G	10/6	CIC	12/6	ECC40	23/10	EM85	17/8	PCC80	8/-	U25	18/5	VP4B	23/10	OC75	8/-
6AG7	7/6	6S7GT	8/-	25L6GT	10/-	CB11	27/2	ECC81	6/-	EN31	53/-	PCF82	10/6	U26	10/-	VP13C	7/1	OC77	15/-
6AK5	8/6	6U4GT	12/6	25Y5G	10/-	CB31	23/10	ECC82	6/6	EY51	9/-	PCF84	17/6	U31	9/6	VP23	6/6	OC78	8/-
6AL5	4/-	6U5G	7/6	25Z4G	9/6	CCH35	23/10	ECC83	7/6	EY83	17/6	PCF86	15/-	U33	27/2	VP41	6/6	OC81	8/-
6AM6	4/6	6U7G	8/6	25Z5	9/6	CK506	6/6	ECC85	6/6	EY84	14/-	PCL82	10/6	U35	27/2	VR105	8/1	OC139	24/-
6AQ5	7/6	6V6G	7/1	25Z6G	10/-	CL33	19/9	ECC85	8/6	EY86	9/-	PCL83	10/6	U37	27/2	VR150	7/6	OC170	13/6
6AT6	7/-	6V6GTG	8/-	25J1	20/5	CV63	10/6	ECC88	18/6	EZ35	6/-	PCL84	12/6	U45	13/6	VT61A	5/-	OC171	14/6
6AU6	10/-	6X4	5/-	28D7	7/1	CY1	19/1	ECF80	10/6	E240	6/-	PCL85	17/6	U50	6/6	VT501	5/-	OC200	16/6
6B8	5/-	6XS7G	6/-	30C1	8/-	CY31	11/-	ECF82	10/6	E241	7/-	PCL86	17/6	U52	6/6	W76	5/6	OC203	24/-
6BA6	7/6	6/30L2	10/-	30F5	6/-	D15	10/6	ECF86	20/5	E280	7/-	PENA4	23/10	U54	20/5	WM18	6/-	OCP71	29/6
6BE6	6/-	7B7	8/6	30FL1	10/-	DAC32	10/6	ECH3	27/2	E281	7/-	PEN4DD	U76	6/-	WI07	19/1	TJ1	40/-	
6BGG23/10	7C5	8/-	30L1	8/-	DAF91	6/6	ECH21	23/10	FC4	15/-			U191	17/-	WT29	20/5	TJ2	45/-	
6BH6	8/-	7C6	8/-	30L15	11/6	DAF96	8/6	ECH35	6/6	FW4/500	8/6	PEN25	4/6	U201	17/-	X41	15/-	TJ3	50/-
6B16	6/-	7H7	8/-	30P4	12/6	DD41	14/3	ECH42	9/-	FW4/800	8/6	PEN45	19/6	U251	14/-	X61(C)	12/6	TP1	40/-
6BQ7A	15/-	7R7	12/6	30P12	7/6	DET25	7/6	ECH81	9/-	GU50	41/6	PEN46	7/6	U281	20/5	X63	9/-	TP2	40/-
6BR7	12/6	757	9/6	30PL1	10/6	DF33	10/6	ECH83	14/3	G330	9/-	PEN383	U282	23/2	X65	12/6	TS1	10/-	
6BR8	19/1	7V7	8/6	30PL13	13/6	DF66	15/-	ECL80	9/-	GZ32	10/-		23/10	U301	23/10	X66	12/6	TS2	12/6
6BW6	8/6	7Y4	7/6	35A5	21/9	DF91	3/6	ECL82	10/6	GZ33	20/5	PEN/DD	U329	14/-	X76M	14/-	TS3	15/-	
6BW7	6/-	8D2	3/6	35L6GT	9/6	DF96	8/6	ECL83	19/9	GZ34	14/-	4020	34/-	U339	17/-	X78	23/10	TS4	24/-
6C4	5/-	9BWW6	15/8	35VW4	7/6	DF97	9/6	ECL86	17/-	GZ37	20/5	PL33	19/9	U403	17/-	X79	23/10	V30/10P	28/6
6C5	6/6	9D2	4/-	35Z3	19/1	DH63	6/6	EF9	23/10	HABC80		PL36	12/6	U404	8/6	X109	17/8	XA101	9/-
6C6	6/6	10C1	13/-	35Z4GT	6/-	DH76	5/-	EF22	14/-			PL38	27/2	U801	30/7	XD(1.5)	6/6	XA102	10/-
6C9	13/6	10C2	27/2	35Z5GT	9/-	DK32	12/6	EF36	4/-	HL2	7/6	PL81	10/6	U4020	19/1	XFG1	18/5	XA103	15/-
6C10	9/-	10F1	27/2	43	10/-	DK91	6/6	EF37A	8/-	HL23	15/8	PL82	7/6	UABC80	9/6	YF12	9/6	XA104	18/-
6CD6G	37/5	10LD11	16/4	50C5	10/-	DK92	9/-	EF39	5/6	HL23DD	7/6	PL83	9/-	UAF42	9/6	YF34	18/-	XB102	6/6
6CH6	9/-	10P13	15/-	50CD6G		DK96	8/6	EF40	15/-	HL42DD		PL84	13/-	UBA41	12/-	XH(1.5)	6/6	XB103	6/6
6D6	6/6	10P14	19/9			DL33	9/6	EF41	9/-		19/9	PL80	19/1	UBC41	8/6	YSG(1.5)6/6	XB104	7/6	
6E5	12/6	12A6	5/-	50L6GT	9/6	DL66	17/6	EF42	10/6	HN309	25/2	PM84	17/8	UBC81	11/6	Y63	7/6	XC101	6/6

PLEASE NOTE THAT WE DO NOT SELL SECONDHAND GOODS OR MANUFACTURERS' REJECTS

### LINE OUTPUT TRANSFORMERS, SCAN AND DEFLECTOR COILS

Available for Ace, Alba, Ambassador, Argosy, Armstrong, Baird, Banner, Beechoven, Bush, Champion, Columbia, Corsor, Decca, Defiant, Dynatron, Ekco, English Electric, Etronic, Ferguson, Ferranti, G.E.C., H.M.V., Invicta, K.B., Marconi, Masteraudio, McCarthey, McMichael, Mullard, Murphy, Pam, Peto Scott, Philco, Philips, Pilot, Portadyne, Pye, Raymond, Regentone, R.G.D., Sobell, Stella, Ultra, Vidor, etc. Prices from 39/6. Please quote full details of model number. Quotation on receipt of S.A.E. or order C.O.D.

### ALL GOODS BRAND NEW, SUBJECT TO FULL MAKERS' GUARANTEE, AND ACTUALLY IN STOCK.


<b>VOLUME CONTROLS</b>	DRM1B	13/-	RM-1	5/3	14A86	17/6	14B130	35/-	14RA	1-2-83	21/-	18RA	1-1-16-1	4/6	
Less switch 3/- each.	DRM2B	15/6	RM-2	7/1	14A97	25/-	14B261	11/6	(FC31)				(FC116)		
With D.P. switch 4/6 each.	DRM3B	15/6	RM-3	7/9	14A100	27/-	14RA	1-2-82	17/6	16RD	2-2-81	12/-	18RD	1-2-8-1	11/-
10 K 25 K 50 K 100 K	LW7	21/-	RM-4	14/-	14A124	28/-	(FC101)			16RE	2-1-8-1	8/6	18RD	2-3-8-1	15/-
‡ mg. † mg. ‡ meg. † meg.	RM-0	7/11	RM-												

# STERN'S MULLARD DESIGNS

Designed by MULLARD—presented by STERN's strictly to specification
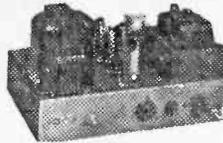
## COMPLETE KIT OF PARTS MULLARD "5-10" MAIN AMPLIFIER

For use with the MULLARD 2-valve pre-amplifier with which undistorted power output of up to 10 watts is obtained. We supply SPECIFIED COMPONENTS AND NEW MULLARD VALVES. Including PARMKO MAINS TRANSFORMER and choice of the latest Ultra-Linear PARMKO or the PARTRIDGE Output Transformer. COMPLETE KIT OF PARTS (PARMEKO Output Trans.) **£10.00**



Alternatively we supply **ASSEMBLED AND TESTED. £11.10.0** INCORPORATING PARTRIDGE OUTPUT TRANSFORMER. £1.6.0 EXTRA.

## MULLARD'S PRE-AMPLIFIER TONE CONTROL UNIT

Employing two EF86 valves, and designed to operate with the MULLARD MAIN AMPLIFIERS, but also perfectly suitable for other makes.



PRICE COMPLETE **£6.6.0** ASSEMBLED AND TESTED **£8.0.0**

- KITS OF PARTS Supplied strictly to MULLARD'S SPECIFICATION and incorporating:
- Equalisation for the latest R.I.A. characteristics.
  - Input for Crystal Pick-ups, and variable reluctance magnetic types.
  - Input (a) Direct from High Imp. Tape Head. (b) From a Tape Amplifier or Pre-amplifier.
  - Sensitive Microphone Channel. • Wide range BASS and TREBLE Controls.

## COMPLETE MULLARD "5-10" AMPLIFIER

The popular and very successful complete "5-10" Incorporating Control Unit providing up to 10 watts high quality reproduction. Only Specified Components and new MULLARD VALVES are supplied including PARMKO MAINS TRANSFORMERS and choice of the latest PARMKO or PARTRIDGE ULTRA-Linear Output Transformers.



KIT OF PARTS **£11.10.0** OR ASSEMBLED **£13.10.0**

DEPOSIT **£2.14.0** 12 months at 19/10. ABOVE incorporating PARTRIDGE OUTPUT TRANS. £1.6. extra.



## COMPLETE MULLARD "3-3"

THE IDEAL AMPLIFIER FOR A SMALL HIGH QUALITY INSTALLATION PROVIDING EXCELLENT REPRODUCTION OF UP TO 3 WATTS OUTPUT


COMPLETE KIT **£7.10.0** OR ASSEMBLED **£8.19.6**

(plus 6/6 carriage and insurance) H.P. Terms: Deposit £2.0.0 and 8 Months at £1.0.0. Complete to MULLARD'S SPECIFICATION including Mullard valves and a PARMKO Output Transformer.
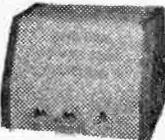
## STERN'S INTER-COMM BABY ALARM

A small versatile Unit employing the new MULLARD ECL86 valve and designed to provide two (or three) way conversation up to extreme distances. Operates from A.C. mains 200 to 250 Volts.

PRICES . . . MASTER UNIT and ONE EXTENSION



KIT OF PARTS **£6.17.6** ASSEMBLED AND TESTED **£8.0.0**

Consists of a MASTER UNIT, size only 8 1/2 x 5 1/2 x 6 in. and ONE EXTENSION (a second extension may be added to any time). The Master Unit incorporates switching and power supply and with the chassis completely isolated from the mains is operated in absolute safety. Cases covered in quality leatherette.

## A BULK PURCHASE OF MARCONIPHONE TAPE RECORDING EQUIPMENT ENABLES US TO OFFER The Model MTR/1 PORTABLE TAPE RECORDER FOR ONLY **£25.0.0** (Carr. & Ins. 10/- extra)



Deposit **£5.0.0**, 12 months of £1.16.8  
The list price of the MTR/1 is £44/2/0. It is a 3-Speed Twin Track Recorder incorporating the latest Collaro "Studio" Tape Deck and operates at 1 1/2, 3 1/2 and 7 1/2 in./sec. Speeds. It incorporates a "Pause" Control, a safety interlock device which ensures that a recorded tape cannot be accidentally erased and a low level output socket so that the output may be fed into an external high fidelity amplifier for monitoring purposes or for high quality reproduction on playback.

## COMBINED ORDER PRICE REDUCTIONS

(a) The KIT OF PARTS to build both the "5-10" Main Amplifier and the 2-valve PRE-AMP CONTROL UNIT. . . . . **£15.15.0**

(b) The "5-10" and the 2-stage PRE-AMP both ASSEMBLED and TESTED H.P. Dep. £3.16.0 and 12 months of £1.7.5. . . . . **£18.18.0**

## RECORD PLAYERS

The Latest Models are in stock, many at reduced prices.

Send S.A.E. For Illustrated Leaflet, THE NEW GARRARD "AUTO-SLIM" 4-speed Autochanger with Crystal Pick-up **£8.10.0**

COLLARO "JUNIOR" 4 SPEED SINGLE RECORD PLAY-ER with separate Crystal Pick-up. Carriage and Insurance 5/- Above Pick-up separately for £1.6.8 **£3.15.0**

THE NEW COLLARO C60 4-speed Autochanger unit with Studio "O" Pick-up. . . . . **£7.19.6**

The E.M.I. 4-speed Single Record Player with crystal Pick-up. . . . . **£6.9.6**

B.S.R. MODEL UA14. A 4-speed mixer Autochanger with Crystal Pick-up. . . . . **£7.10.0**

Available incorporating the B.S.R. STEREO Pick-up, plays L.P. and 78 Records. **£8.13.10**

GARRARD MODEL TA/MKH 4-speed Player fitted high output Crystal Pick-up. . . . . **£8.10.0**

GARRARD MODEL RC210. Autochanger. 4-speeds. High output. Crystal Pick-up. . . . . **£10.10.0**

Carriage and Insurance on each above 5/- extra.

## SPECIAL CASH OFFER

This very attractive PORTABLE AMPLIFIER CASE together with a good quality GRAM AMPLIFIER and a matched P.M. SPEAKER.



ALL for ONLY **£8.7.6** (Plus 7/6 Carr. & Ins.)

The Amplifier consists of a 2-stage design incorporating 3 modern B.V.A. valves and has separate BASS and TREBLE CONTROLS.

The Portable Case will also accommodate almost any make of Autochanger and is attractively finished in Mushroom Grey Rexine.

WE ALSO SUPPLY SEPARATELY: (a) The 2-stage (plus Rectifier) AMPLIFIER **£4.2.6**

(b) THE PORTABLE CARRYING CASE **£3.17.6**

(c) 6in. P.M. SPEAKER 18/9 Carriage and Insurance 4/- extra.

## MULLARD FOUR CHANNEL MIXER UNIT

Self powered with Cathode follower output. Incorporates Two inputs for MICROPHONES



One for CRYSTAL PICK UP and a fourth for RADIO or TAPE Complete Kit of Parts **£8.8.0**

Assembled and Tested **£10.0.0**

TERMS: Deposit £2 and 12 months at 15/-

MODEL L.I.L. one microphone input matched for moving coil or Ribbon Mike. £1.17.0 extra.

## WE CAN ALSO SUPPLY The MTR/1 and LOUDSPEAKER

With the COLLARO "STUDIO" TAPE DECK all assembled on top board. TESTED AND READY FOR USE. (Carr. & Ins. 10/- extra). Deposit **£4.0.0**, 12 months **£1.9.4**.

# STERN RADIO LTD.

Dept. P.W. 109 FLEET ST., LONDON, E.C.4

Telephone: FLEET STREET 5812/3/4



# Stern's "Fidelity" TAPE RECORDERS

For truly "Hi-Fi" Recordings

**MODEL CR3/S** Incorporates the COLLARO "STUDIO" TWIN TRACK 3-speed Deck, operating at 1 1/2-in., 3 1/2-in. and 7 1/2-in. speeds ..... **£39.10.0**  
 H.P. Terms: Deposit £7.18.0 and 12 months of £2.17.11.

**MODEL TR3/Mk.VI** Incorporates the New TRUVOX Mk. VI TWIN TRACK 2-speed Tape Deck operating at 3 1/2-in. and 7 1/2-in. speeds ..... **£44.0.0**  
 H.P. Terms: Deposit £8.18 and 12 months of £3.4.7

**The MODEL HFG/2R PORTABLE TAPE RECORDER**  
 (Original Price £33.0.0)  
**FOR ONLY 22 gns**

H.P. Dep. £4.14.0. 12 months £1.13.9. (Carr. and ins. 10/- extra). Incorporates THE LATEST GARRARD "MAGAZINE" TAPE DECK and a HIGH QUALITY AMPLIFIER which is entirely based on the very successful MULLARD

developed to operate the GARRARD TAPE DECK. Price includes SUPPLY OF THE GARRARD TAPE MAGAZINE and 4in. SPOOL OF DOUBLE PLAY TAPE. Comprises a Twin Track Recorder operating at 3 1/2-in. speed and providing up to 1 hour 10 mins. playing time. Truly "Portable", weighs only 22 lbs. Outstanding features are excellent performance and simplicity of operation.

**ADD "HI-FI" TAPE RECORDING TO YOUR EXISTING AUDIO INSTALLATION WITH MULLARD TYPE "C" TAPE PRE-AMPLIFIER—ERASE UNIT**

The "HI-FI" link to add full tape recording facilities to High Fidelity home installations. Incorporates FEROXUCUBE POT CORE PUSH PULL OSCILLATOR and 3-speed treble equalisation by FEROXUCUBE POT CORE INDUCTOR FOR WEARITE-COLLARO-TRUVOX OR BRENNELL TAPE DECKS. Includes separate power supply unit.  
**KIT OF PARTS £14.0.0** H.P. £3.8.0 Deposit and 12 months £1.4.11 **£17.0.0**  
 (Excluding power unit £1.15.0 and £14.1.0 respectively).

**"SPECIAL COMBINED ORDER" PRICES**

- (a) The COLLARO "Studio" Deck with the Model "C" Preamplifier and POWER SUPPLY UNIT ASSEMBLED AND TESTED ..... **£29.10.0**  
 Deposit £5.18.0. 12 monthly payments of £2.3.3
- (b) As above but the TYPK "C" Unit and POWER UNIT supplied as COMPLETE KIT OF PARTS. . . . . **£26.10.0**  
 Deposit £5.6.0. 12 monthly payments of £1.18.10
- (c) The TRUVOX MkVI Deck (incorporating Pause Control and Rev. Counter) with the Model "C" PREAMPLIFIER and POWER UNIT ASSEMBLED AND TESTED ..... **£35.0.0**  
 Deposit £7.0.0 and 12 months at £2.11.4
- (d) As above but the Model "C" PREAMPLIFIER and POWER UNIT supplied as a COMPLETE KIT OF PARTS ..... **£31.10.0**  
 Deposit £6.6.0. 12 monthly payments of £2.6.2
- (e) The BRENNELL MkV Deck with the Model "C" PREAMPLIFIER and POWER UNIT ASSEMBLED AND TESTED ..... **£46.0.0**  
 Deposit £9.4.0 and 12 months at £3.7.6
- (f) As above but the Model "C" PREAMPLIFIER and POWER UNIT supplied as a COMPLETE KIT OF PARTS ..... **£43.0.0**  
 Deposit £8.12.0. 12 monthly payments of £3.3.1
- (g) The WEARITE MODEL "4" DECK with ASSEMBLED AND TESTED Model "C" PREAMPLIFIER AND POWER UNIT incorporating WEARITE HEADLIFT TRANSFORMER, Etc. .... **£56.0.0**  
 Deposit £11.4.0 and 12 months at £4.2.1.  
 (Carriage and Insurance on above is 10/- extra).

**HF/TR3 MK.II TAPE AMPLIFIER**

(Mullard Type "A" design) A very high quality Amplifier incorporating 3-speed treble equalisation, by the latest FEROXUCUBE POT CORE INDUCTOR, FOR COLLARO-TRUVOX-BRENNELL WEARITE Tape Decks, has GILSEN Output Transformer. Includes separate Power Supply Unit.



EACH MODEL INCORPORATES THE MODEL HF/TR3 MK.II TAPE AMPLIFIER (Described below)

Each price quoted provide for the COMPLETE RECORDER including CRYSTAL MICROPHONE and 1,200ft. Spool of Tape.



**THE "ADD-A-DECK"**

Incorporating GARRARD "MAGAZINE" TAPE and the MATCHED MODEL HF/G2P PRE-AMPLIFIER Supplied on ONE CHASSIS (as illustrated) **READY FOR USE 18 Gns.**  
 (Carr. & Ins. 10/- extra).  
 Price includes Garrard Magazine and a 4in. Spool Double Play Tape

H.P. Deposit £3.18.0, and 12 months of £1.7.9. Provides complete tape recording facilities and designed to operate through the pick-up sockets of the standard type of RADIO RECEIVER, or an AMPLIFIER, from which really first class reproduction is obtained. It consists of a Twin Track Deck connected to the Pre-amplifier and operates at 3 1/2-in. speed providing up to 1 hr. 10 mins. playing time.

## BUILD A HIGH FIDELITY TAPE RECORDER



◀ LIKE THIS for **£35.0.0**

Deposit £7.0.0. 12 months at £2.11.4.

**FOR THIS WE SUPPLY**

- ★ Complete Kit of Parts to Build the HF/TR3 Tape Amplifier
- ★ The New Collaro "Studio" Tape Deck.
- ★ Portable Carrying Case (as illustrated).
- ★ Roll/Collection on 10 x 6in. p.m. Loudspeaker.

★ ACOS Crystal Microphone and 1,200ft. Spool E.M.I. Tape. Alternatively for those who prefer another make of Tape Deck—we will supply precisely as above—but in place of the Collaro "studio" Deck. We will include:

- The Truvox MK VI Deck ..... **£40.10.0**  
 Deposit £7.0.0. 12 months at £2.19.5.
- (a) For Constructors with their own cabinet—WE OFFER—COMPLETE KIT to build the HF/TR3 Amplifier together with the COLLARO "STUDIO" DECK. . . . . **£26.0.0**  
 Deposit £5.4.0. 12 monthly payments of £1.18.2
- (b) As above but with the HF/TR3 supplied ASSEMBLED AND TESTED. . . . . **£29.10.0**  
 Deposit £5.18.0. 12 monthly payments of £2.3.4.
- (c) COMPLETE KIT to build the HF/TR3 together with the TRUVOX Mk. VI TAPE DECK. . . . . **£31.10.0**  
 Deposit £8.6.0. 12 monthly payments of £2.6.2.
- (d) As above but with HF/TR3 supplied ASSEMBLED AND TESTED. . . . . **£35.0.0**  
 Deposit £7.0.0. 12 monthly payments of £2.11.4.
- (e) COMPLETE KIT to build the HF/TR3 AMPLIFIER with the BRENNELL Mk.V. TAPE DECK. . . . . **£42.0.0**  
 Deposit £8.8.0. 12 monthly payments of £3.1.7.
- (f) As above but with HF/TR3 supplied ASSEMBLED AND TESTED. . . . . **£45.10.0**  
 Deposit £9.2.0. 12 monthly payments of £3.6.9.
- (g) THE ASSEMBLED and TESTED HF/TR3 AMPLIFIER with the WEARITE MODEL 4A DECK, incorporates Wearite Head Lift Transformer etc. Deposit £11.4.0. 12 monthly payments of £4.2.1.  
 Carriage and Insurance on each above is 10/- extra.

KIT OF PARTS **£13.13.0** H.P. Deposit £3.8.0 and 12 months at £1.4.11. OR ASSEMBLED **£17**

# STERN RADIO LTD.

# Stereophonic Sound by Stern's


## THE "STP-1" STEREO TAPE PREAMPLIFIER DESIGNED TO OPERATE WITH

● TRUVOX MKVI TAPE DECK incorporating the latest 4-TRACK MINIFLUX TAPE HEADS.

● BRENNELL MkV TAPE DECK incorporating similar 4-TRACK MINIFLUX TAPE HEADS.

● COLLARO "STUDIO" TAPE DECK incorporating the latest 4-TRACK REUTER TAPE HEADS.

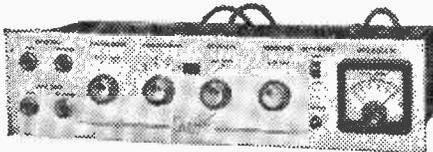- PUSH PULL OSCILLATOR CIRCUIT
- 4-SPEED EQUALISATION
- FERROXUBE OSCILLATOR TRANSFORMER
- SENSITIVE METER FOR SIGNAL LEVEL
- SEPARATE GAIN CONTROLS IN EACH CHANNEL
- MULLARD VALVES INCORPORATED



OVERALL SIZE CASE 13½ x 3in. FRONT PANEL (Choice of Black or White) 14 x 3in.

PRICE  
**£26.0.0**

Including separate Power Supply Unit.  
Deposit £5.4.0, 12 months £11.8.2.

### COMBINED PRICE SCHEDULE

#### THE "STP-1" PREAMPLIFIER is offered

- WITH TAPE DECKS AS FOLLOWS:
- TRUVOX MKVI 4-TRACK MODEL..... **£47.0.0**  
Deposit £8.8.0, 12 months £3.8.11.
  - BRENNELL MkV 4-TRACK MODEL..... **£65.0.0**  
Deposit £13.0.0, 12 months £4.15.4.
  - COLLARO "STUDIO" 4-TRACK MODEL..... **£41.10.0**  
Deposit £8.6.0, 12 months £3.0.11.

#### THE MULLARD "10+10" STEREO AMPLIFIER

(described below) with the "STP-1" PREAMPLIFIER and one of the TAPE DECKS provide a COMPLETE STEREOPHONIC INSTALLATION. WE OFFER

- "10+10" AMPLIFIER, "STP-1" PREAMPLIFIER and the TRUVOX MK.VI DECK..... **£67.0.0**  
Deposit £13.8.0, 12 months £4.18.3.
- As above with BRENNELL MK.V DECK..... **£85.0.0**  
Deposit £17.0.0, 12 months £6.4.8.
- As above with COLLARO "STUDIO" DECK..... **£61.10.0**  
Deposit £12.6.0, 12 months £4.10.2.

Please enclose S.A.E. with all enquiries.

**STEREOPHONIC RECORD PLAYER UNITS  
MICROPHONES & TWIN LOUSPEAKERS  
ARE AVAILABLE FROM STOCK**

## MULLARD'S "10 PLUS 10"

### STEREO POWER AMPLIFIER

A high fidelity design based on the famous Mullard "5-10". Provides up to 10 watts (per channel) Superb reproduction. Frequency response flat to within 3 db from c/s. To 80 Kc/s at 50 Mw.



Total Harmonic Distortion at 10 watts 0.1%.  
(a) ASSEMBLED COMPLETE AMPLIFIER, including CONTROL UNIT (as illustrated).  
Deposit £4.4.0, 12 months of £1.10.10. **PRICE: £21.0.0**

(b) A complete KIT of PARTS..... **£18.10.0**

Built to the very highest technical standards and presented strictly to MULLARD'S specification. Incorporates complete Mullard valve line-up including two of the new valves, type ECL86, in each channel. Two specially designed GILSON OUTPUT TRANSFORMERS with 20% taps are used for ultra linear operation. The matching CONTROL UNIT is designed to be either attached to the Amplifier (as illustrated) or can be detached for separate mounting on a Cabinet panel. Provides inputs for CRYSTAL PICK UPS, RADIO TUNING UNIT, and TAPE RELAY.

AS AUDIO SPECIALISTS WE CONFIDENTLY RECOMMEND THIS DESIGN IS A MUST to the serious minded sound enthusiast.

We can also supply the assembled MAIN AMPLIFIER only (excludes control unit) for operation with our DUAL CHANNEL PREAMPLIFIER, this provides for a more versatile or elaborate installation and would be essential if a low output Magnetic Pick Up, such as the Decca, is to be used.

(a) THE ASSEMBLED MAIN AMPLIFIER with the ASSEMBLED DUAL CHANNEL PREAMPLIFIER..... **PRICE: £30.0.0**  
Deposit £6.0.0, 12 months of £2.4.0.

(b) A complete KIT of PARTS for both Units..... **£26.0.0**

**!! A BARGAIN !!** We are able to offer BRAND NEW and FULLY GUARANTEED—TRUVOX MK. VI TAPE DECKS. List Price **£18.18.0** £28.5.0 for ..... Deposit £3.16.0 and 12 months at £1.7.8. (Carr. & Ins. 7/6 extra) A twin track model operating on 31 and 7 1/2 in./sec. speeds and incorporating pause Control and Rev. Counter. THE ABOVE INCORPORATING THE LATEST 4-TRACK MINIFLUX HEADS FOR STEREO OPERATION IS AVAILABLE FOR..... **£21.10.0** (Carr. & Ins. 7/6 extra). Deposit £4.6.0, 12 months of £1.11.7.

## DUAL CHANNEL PREAMPLIFIER

Incorporates two Mullard 2-valve Triode Amplifiers combined into a Single unit enabling it to be used for both STEREOPHONIC or MONAURAL operation. It is designed primarily to operate with our range of MULLARD MAIN AMPLIFIERS but will also operate equally well with any make of Amplifiers requiring an input of 250 m/volts. COMPLETE KIT **£12.10.0** ASSEMBLED AND TESTED **£15.0.0** OF PARTS H.P. £3 Dep. and 12 mths. at £1.2.0



## STEREO "TWIN THREE" AMPLIFIER with specially designed PORTABLE CASE

A most compact portable design consisting of TWIN CHANNEL AMPLIFIER based on the latest design by MULLARD LTD. incorporating top grade Output Transformers, and the new audio Triode-Pentode Valves Mullard E.C.L.86. Separate Bass and Treble controls. Suitable for use with Crystal Pick Ups, and capable of genuine high quality reproduction up to 3 Watts per channel. An attractive and contemporary portable Case in two tone colours. The unique feature of the design is the loudspeaker mounting. Two 8 x 5in. p.m. elliptical loudspeakers are separately baffled and mounted in the lid, which is detachable, allowing for each speaker to be individually positioned. A very versatile stereo arrangement tested and guaranteed which can be assembled in the minimum of time.



PRICE for the ASSEMBLED AMPLIFIER, Two 8 x 5in. ROLA SPEAKERS and PORTABLE CASE **£14.0.0**  
Deposit £2.16.0, 12 months of £1.0.6.

ASSEMBLED AMPLIFIER supplied for..... **£7.15.0**  
8 x 5in. ROLA LOUSPEAKERS (3 ohms) each. **£1.1.0**

PORTABLE CASE..... **£5.0.0**  
A CHOICE OF SINGLE RECORD PLAYERS and AUTOCHANGERS is available from Stock (Send S.A.E. for details)

Dept. P.W. **109 FLEET ST., LONDON, E.C.4**

Telephone: **FLEET STREET 5812/3/4**

Illustrated and Descriptive Brochures available. Please enclose S.A.E.



# VALVES BY RETURN OF POST



## THE MOST COMPREHENSIVE COMPETITIVE VALVE LIST IN THE COUNTRY

**10% DISCOUNT** SPECIAL OFFER TO PURCHASERS in black type (35% in dozen). Post: 1 valve, 6d., 2-11, 1/-.

**NEW LOW PRICES GUARANTEED 3 MONTHS**

**FREE TRANSIT INSURANCE.** All valves are new or fully guaranteed ex-works or ex-equipment origin. Satisfaction or Money back Guarantee on goods if returned unsworn within 14 days.

074	5/-	6AB8	7/-	6F23	8/6	6040GT	10/6	12B17	10/6	30P16	6/6	1D77	3/6	EC91	4/6	EL33	8/-	MU14	8/-	SP41	2/6	UCH41	8/6
1A3GT	5/6	6AC7	4/3	6F33	6/6	605G	6/3	12C8	6/6	30P11	9/6	1D52	5/6	EC93	9/6	EL35	7/-	N7	17/6	SP61	2/6	UCL8	13/6
1A7GT	11/3	6AG5	3/6	6H3	2/6	6V6GT	5/6	12E1	13/6	35L6GT	6/6	DA30	12/6	EC92	4/-	EL37	11/6	N78	15/6	SP150A	4/6	UF41	8/6
1G5GT	8/6	6A17	7/-	6J5	4/3	6V6GT	8/-	12J5GT	3/6	35W4	6/6	DA90	2/6	EC93	4/6	EL38	12/6	N108	16/-		4/6	UF42	5/6
113	8/3	6AK5	5/-	6J5G	2/9	6X2	6/6	12K7GT	4/9	35Z4GT	5/3	DA91	3/6	EC94	9/-	EL41	8/-	N152	8/9	T41	7/-	UF80	2/6
106	9/9	6AL5	3/6	6J3GT	3/9	6X4	5/-	12K8	12/-	35Z6GT	7/6	DAC32	3/6	EC95	6/-	EL42	9/-	P41	4/6	TD44	7/6	UF85	8/6
1H5GT	9/9	6AM6	3/-	6J6	4/-	6X5GT	5/-	12K9GT	11/-	42	7/6	DAF96	7/6	EC91	6/6	EL94	7/-	P61	2/8	U14	8/-	UF86	14/6
114	3/6	6AQ5	6/-	6J7	7/9	6X5GT	5/6	12S47	6/-	43	7/6	DF33	9/9	EC92	6/-	EL91	4/6	PABC8011	U18	8/6	UF89	7/-	
1LD5	3/6	6AT8	5/-	6J7G	5/-	6X6G	7/9	12T7GT	5/-	50C5	7/6	DF91	3/6	EC93	6/6	EM34	8/6	PC84	7/-	U22	6/9	UL41	7/-
1LNS	8/6	6AU6	7/6	6J7GT	7/6	7B6	9/-	12S47	6/-	50L6GT	9/-	DF96	7/3	EC94	7/-	EM80	7/9	PC85	7/3	U24	16/-	UL44	11/-
1N5GT	9/9	6B7	8/6	6J8	8/6	7B7	7/3	12S47	5/6	52K10	10/6	DH63	6/3	EC95	7/9	EM81	8/9	PC88	19/-	U25	12/6	UL46	9/6
1R5	8/-	6B4G	3/6	6K6GT	6/6	7C5	7/6	12S47	4/-	53K10	10/6	DH75	5/6	EC90	8/6	EM84	6/9	PC89	13/6	U26	9/6	UL47	7/6
1R1	8/-	6BA8	9/-	6K8	5/9	7C8	7/3	12SNGT	7/3	54K10	11/3	DH85	5/6	EC91	8/6	EM85	10/6	PCF90	13/6	U27	9/6	UM80	9/6
1R3	4/9	6B6G	5/6	6K7G	2/3	7H7	7/3	12SNGT	8/-	61S1PT	11/-	DK91	5/6	EC82	12/6	EN31	16/-	PCF82	7/3	U35	11/-	UU6	19/-
1T4	3/9	6B9G	12/6	6K7GT	4/9	7K7	9/6	12G5	9/-	75	8/-	DK92	7/6	EC85	9/6	EY51		PCL82	7/3	U37	26/-	UU7	9/6
2A8	7/9	6B16	6/-	6K8GT	8/9	7Q7	7/6	1487	22/6	77	6/6	DK93	7/3	EC82	14/6	Small	8/-	PCL83	10/6	U38	8/-	UU8	17/-
212L	4/9	6B16	6/-	6L1	12/6	7S7	9/-	194A3	7/6	78	6/6	DL33	8/6	EC83	7/9	Small	8/-	PCL84	7/6	U39	11/-	UY18	11/-
3A4	4/9	6B17	9/6	6L6	9/9	7V7	6/-	194A3	7/6	80	5/3	DL33	8/6	EC80	7/-	EZ35	6/6	PC85	6/6	U52	4/6	UY21	11/-
3A5	9/-	6B8W	7/6	6L6G	6/9	7Y4	6/3	20D1	8/6	83	9/6	DL82	9/-	EC82	8/6	EZ40	6/6	PC85	7/6	U58	5/6	UY41	6/-
3D6	4/6	6B9V7	5/9	6L18	8/6	7Y4	6/6	20E2	8/6	145B7	13/-	DL91	8/-	EC83	12/-	EZ41	7/-	PC86	5/3	U78	5/6	UY85	6/6
3Q4	7/-	6B8X	4/9	6L19	12/6	8D3	3/-	20L1	18/-	807(A)	5/6	DL92	6/-	EC87(A)	5/6	EZ90	6/-	PL83	8/3	U91	11/-	VR105/30	
3Q5GT	9/6	8C4	3/6	6L19	8/-	10C1	11/-	20P1	9/6	807(B)	5/9	DL84	6/-	EC87	6/3	EZ91	6/6	PL85	10/6	U92	9/6		
3B1	8/6	8C5	5/6	6L13	8/6	10D1	11/3	20P2	9/6	809	5/6	DL84	6/-	EC87	6/3	EZ91	6/6	PL85	10/6	U92	9/6		
3B4	9/6	8C8	4/9	6LD20	8/6	10P1	9/6	20P4	17/-	964	2/-	EA50	9/6	EF40	13/6	HL14DD79	PL81	8/-	U309	7/7	W01M	11/-	
6L4G	9/6	6C9	9/6	6N7	6/6	10L14	7/9	20P5	15/-	955	3/9	EABC80	7/6	EF41	8/-	HVR2	7/6	PL82	6/9	U329	11/-	W78	11/-
6T4	8/9	6C9G	21/-	6P1	14/-	10L13	7/9	25A6G	8/-	956	2/6	EAC91	4/6	EF42	7/6	KL35	7/6	PL83	6/9	U349	11/-	W81	7/6
6U4G	4/9	6C8H	8/3	6P25	8/6	10L11	13/6	26L8G	9/9	9763	10/6	EAP42	3/6	EF50-BA	2/-	KT38	4/9	PM84	14/-	U81	20/-	X61M	11/-
5V4G	9/6	6D1	9/6	6P28	12/6	10L12	8/6	25L6GT	9/-	9601	4/-	EB34	1/6	EF50-USA	2/-	KT38	4/9	PM84	14/-	U81	20/-	X61M	11/-
5Y3G	9/6	6D2	3/6	6Q7G	6/6	10P13	7/6	25Y3G	9/-	9002	4/6	EB41	7/6	EF50-USA	2/-	KT38	4/9	PM84	14/-	U81	20/-	X61M	11/-
5Y3GT	9/-	6D3	12/6	6Q7GT	8/9	10P14	9/-	25Z4G	7/9	9003	4/3	EB91	3/3	KT44	6/3	PT31	7/9	UF42	8/-	X65	6/3		
5Y4G	11/-	6D4	4/9	6K7G	6/6	10L18	7/6	25Z5	8/-	ATP4	2/9	EC93	9/6	EF54	3/3	KT45	6/3	PT32	10/-	UB41	7/6	X66	11/-
5Z3	3/3	6F1	4/9	6S47	4/9	12A5	5/-	25Z6	8/-	AZ31	8/6	EB33	4/9	EF50	4/9	KT61	8/6	PT60	7/6	UC61	7/9	X75	22/-
624G	9/6	6F6M	7/-	6S47	4/9	12A18	9/9	30C1	7/6	B65	4/6	EB81	7/9	EF85	6/6	KT63	6/3	PT81	6/6	UB81	10/-	X79	16/8
64GT	11/-	6F6G	6/3	6S37	4/6	12A17	7/6	30P5	6/6	CL3	6/6	EBF80	7/9	EF89	6/9	KTW61	5/9	PT83	7/6	UCB21	14/6	Y63	6/6
60L1	8/6	6F12	3/6	6S8K7	5/3	12A17	5/6	30P11	9/6	CBL31	21/-	EBF89	8/6	EF91	3/6	KTW63	5/9	PT80	7/6	UCB24	14/6	Z68	5/-
6A8	7/6	6F13	6/9	6S17GT	6/-	12A17	5/6	30L1	12/6	CH33	14/-	EBC33	4/9	EF92	4/6	KTW65	6/6	R18	13/-	UCB5	7/6	Z68	9/6
6A7	15/-	6F14	9/6	6S17GT	4/9	12AX7	6/9	30L15	5/-	CL33	11/9	EBC11	21/-	EF95	6/6	L63	5/6	R19	11/-	UCF80	16/-	Z77	3/-
6A8G	9/6	6F15	9/6	6S2T	6/-	12B47	6/-	30P4	12/6	CY31	7/6	EC52	3/6	EK52	7/6	LN152	7/-	SD6	8/6	UCH21	12/6	Z158	4/9
6A8GT	13/-	6F16	8/6	6S87	4/6	12B6G	8/6	30P12	8/-	D63	1/6	EC90	3/6	EL32	3/9	LN319	7/-	SP8	3/6	UCH42	7/6	Z719	4/9

**TRANSISTORS**  
 Red Spot 3/8 each; White Spot 4/6 each; Yellow Spot 2/9 each; Green Spot 2/6 each.  
**GERMANIUM DIODES**, general purpose, 9d. each, 8/- doz.  
**PORTABLE TAPE-RECORDER CASES**  
 10 1/2 x 14 1/2 x 5 1/2 .. 14/-  
 16 x 12 x 7 .. 20/-  
 Covered Attractive Resine. P. & P. 3/-.

**Tubes** HIGHEST QUALITY—COMPARE OUR PRICES  
 Carr. 6/-  
 Ina. 12/6.

	6 Months	12 Months	NEW TYPES
12in.	£2-0-0	£3-5-0	£4-0-0
14in.	£2-10-0	£3-15-0	£5-0-0
15/17in.	£3-5-0	£4-10-0	
21in.	£3-15-0	£5-15-0	£6-0-0

**MOST MULLARD, MAZDA, COSSOR, EMITRON, EMISCOPE, BRIMAR, FERRANTI TYPES, PROCESSED IN OUR OWN FACTORY.**

**PORTABLE RECORD PLAYERS**  
 Takes all sizes, all Speeds, Records, Autochange Unit. Complete in attractive Two-tone Cabinet. Makes Gift. **£14.15.0**  
**13 CHANNEL TVs**  
 Table Models. Complete with Valves and Tube. They are untested, not guaranteed to be in working order. 12in. £21.9.0 (P. & P. 12/6). 14in. £41.9.0 (P. & P. 16/-).

**COMPLETE RECORD PLAYERS**  
 B.S.R. UA8, 4 Speed Autochanger .. 26 15 0  
 B.S.R. UA14, 4 Speed Autochanger .. 27 19 0  
 B.S.R. UA20, 4 Speed Autochanger .. 28 19 0  
 Garrard 809/810 .. 29 19 0  
 EMI 4 Speed Single Player .. 24 12 0  
 P. & P. on above 4/-.

**4-SPD. RECORD PLAYERS**  
**4-SPD. RECORD PLAYERS**  
 Latest B.S.R. TU9 Turntable, together with light-weight Starr Galaxy dust cap, sapphire crystal pick-up head. Truly amazing value at **£3.10.0** Carr. 3/-.

**RENEW YOUR PICK-UP.** Cartridges only. Acoz 22/6; Monotone 17/-; Steag and Reuter 15/-; Power Point 17/-. Complete with tone arm, 3/- extra.

**MAINS AMPLIFIERS**  
 3 valves (10P3, 10P14, UU9), 3 watt, 8in. loud-speaker, in two-tone cases with controls. Ideal for record players. **19/6** P. & P. 6/-.

**CO-AX** standard and low loss, 25 yds., 12/6, 50 yds., 22/6, 100 yds., 42/6. Co-ax. Plugs 1/2. Wall outlet boxes 3/6.

**CONNECTING WIRE**  
 Either solid or flex, 1/- 25 ft. coil, 5 coils different colours, 4/-.

**EXTENSION LOUDSPEAKERS**  
 Covered in attractive Resine, Gold Metal 21/6  
 Pret. Complete, size 8 x 6 x 3 1/2 in.  
 Baffle type, polished wood front, with Gold Metal Pret. Snaped. Size 11 1/2 x 7 x 3 1/2 in. P. & P. 2/-.

**CONDENSERS**  
 25 Mixed, Electrolytic. Many popular sizes. List value 25. OUR PRICE **10/-** P.P.

**FERRITE RODS AND SLABS**  
 6 x 1/2 in., 8 x 1/2 in., 8 x 3/4 in., 2 1/2 each; 4 x 1 in., 1/3; 6 x 1 in., 1/8; 8 x 1 in., 1/8.

**CAR RADIO AERIALS**  
 "Galaxy" make, Extend to **22/6** ONLY 48in. Plated. P. & P. 2/-.

**TOOLS**  
 11 piece Socket Wrench, Electro-plated. 18/-  
 7 1/2 to 1 1/2 in. Excellent value. P. & P. 1/6.

**POWER CABLE**  
 7/099, 15 amp. 2 core, power cable, 1/- yd.; 3 core, 1/6 yd.; 4 amp. P/C Twin Flex, 4d. yd. 100-yd. drum. 30/-, plus postage.

**YOUR ENQUIRIES GLADY ANSWERED. S.A.E.**

**100 RESISTORS 6/6**  
**100 CONDENSERS 10/-**  
 Miniature Ceramic and Silver Mica Condensers 3 pF to 10,000 pF. LIST VALUE OVER 25.

**SILICONE DIODES**  
 125 v., 500 mA., 2 in series make superior replacement for R.M.4 and R.M.5, etc., 8/- each.

**LOUDSPEAKERS**  
**TOP MAKES—MANUFACTURER FRESH**  
 2 1/2in. 18/-; 3in. 18/-; 3 1/2in. 18/-; 5in. 16/-; 8in. 19/-; 10in. 22/6; 7 1/2in. elliptical 19/-; 8 x 8in. elliptical 22/6; 10 x 8in. elliptical 22/6; 8 x 13in. Speakers 29/-.

**PM SPEAKERS**  
 3 ohms, top makes, performance guaranteed:  
 8in. 8/-      5in. 11/-      10in. 13/-  
 6 1/2in. 8/-      7 x 4 1/2 11/-      10 x 6

**UNIVERSAL VOLT OHM MULTIMETER**  
 Reads A.C. and D.C. volts to 1000, 6 ranges at 1000 ohms per volt resistance reading to 200k in 2 ranges. Complete with prods, 59/6. P. & P. 1/6.

**EY51 SHORT ENDS 4/6 U25 SHORT ENDS 8/-**  
**HEADPHONES**  
 Ex-Govt. Quality, with Jack Plug **7/6** pr. P. & P. 1/6

Post: 2 lbs. 2/-, 4 lbs. 3/-, 7 lbs. 3/6, 15 lbs. 4/-, etc. No C.O.D. ALL ITEMS 5% & POST FREE IN DOZENS (Callers-always welcome) LIST OF 1000 SNIPDS 6d. P.O. BOX (21) W 350-352 FRATTON ROAD, PORTSMOUTH.

The decision is YOURS. To be a success in your chosen career; to qualify for the highest paid job . . . to control a profitable business of your own. ICS home-study courses put your plans on a practical basis; teach you theory and practice; give you the knowledge and experience to take you, at your own pace, to the top.

*Choose the RIGHT course*

RADIO & TELEVISION ENGINEERING  
INDUSTRIAL TELEVISION

RADIO & TELEVISION SERVICING  
RADIO SERVICE AND SALES

VHF/FM ENGINEERING : ELECTRONIC  
COMPUTERS & PROGRAMMING

ICS provides thorough coaching  
for professional examinations:


Brit. I.R.E., City and Guilds Tele-  
communication Technicians, C. & G.  
Radio & TV Servicing (R.T.E.B.);  
C. & G. Radio Amateurs.

**LEARN AS YOU BUILD**

*Practical Radio Courses*

Gain a sound up-to-professional-standards knowledge of Radio and Television as you build **YOUR OWN** 4-valve T.R.F. and 5-valve superhet radio receiver, Signal Generator and High-quality Multi-meter. At the end of the course you have three pieces of permanent and practical equipment and a fund of personal knowledge and skill. ICS Practical Radio courses open a new world to the keen Radio amateur.

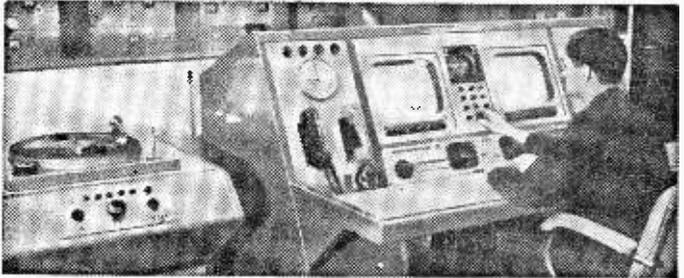*Technical  
Training  
in Radio,  
Television  
and  
Electronics  
Engineering  
with*



**THERE ARE ICS COURSES TO MEET YOUR NEEDS AT EVERY STAGE OF YOUR CAREER. FILL IN AND POST THIS COUPON TODAY.**

You will receive the FREE 60 page ICS Prospectus listing examinations and ICS technical courses in radio, television and electronics PLUS details of over 150 specialised subjects.

Other ICS courses include: MECHANICAL, MOTOR, FIRE, ELECTRICAL & CHEMICAL ENGINEERING. FARMING, GARDENING. ARCHITECTURE & WOODWORKING. SELLING & MANAGEMENT. ART, PHOTOGRAPHY, etc., etc.

**PLEASE STATE ON COUPON SUBJECT YOU ARE INTERESTED IN . . .**

**INTERNATIONAL CORRESPONDENCE SCHOOLS**  
 (DEPT. 170) INTERTEXT HOUSE, PARKGATE RD., LONDON, SW11

PLEASE SEND FREE BOOK ON.....

NAME .....

ADDRESS .....


.....

OCCUPATION..... AGE.....

1.62

**COMPLETE V.H.F./A.M. RADIO FOR £12.10.0**

(carr. paid)

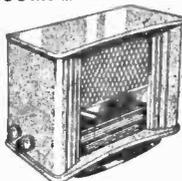


Brand new set, in superb walnut cabinet (size 19 x 8 1/2 x 14 1/2 in. high). Covering 80-100 Mc/s. 16-49 M., and 200-500 M. Mains trans. 200-250 v. with 2 tappings. Ferrite rod aerial for A.M. Controls: volume on/off, tone, tuning, w/charge. Gram and ext. speaker position provided. Valves 12AT7, 12AF8, 6BJ6, EABC80 6BW6 and metal rectifier. Fully guaranteed. Today's Value £20.

**BUILD YOUR OWN RECORD PLAYER FOR £12.0.0**


2v. amp 57/-; B.S.R. UA14 4-sp. autochanger £7.10.0; case 20 x 16 x 9 1/2 ins. black and cream 45/-; carr. 7/6 on any two items or the lot for £12.0.0—carr. paid. Assembled in 15 mins. Extra for 3 v. amp, 10/-.

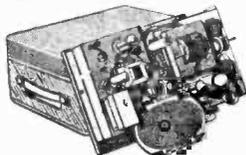**TAPE RECORDER FOR ONLY £17.17.0 (10/- carr.)**

**A QUALITY ARTICLE.** Valves E280, ECC83, ECL82, DM70. Acos Crystal "mike", 850ft. Tape and extra spool. 3 1/2 in./sec. Mike and Radio inputs. Vol. on/off tone. Ext. L.S. and Monitor. Fast forward and reverse. Cannot be accidentally erased. Magic Eye Indicator. 6 x 4 in. Speaker. Cabinet 14x11x7 in. Supplied completely built and in cabinet.




**SELF-POWERED VHF TUNER CHASSIS.** Covering 88-95 Mc/s. Mullard permeability tuner. Dims. 10 1/2 x 4 1/2 x 5 1/2 in. high ECC85, EF91, EF91 and 2 diodes. Metal Rectifier. Mains transformer. Fully wired and tested. Only £7.14.0 (carr. pd.). Room dipole 10'—300 ohm twin feeder. 6d. yd. Tuner without power pack £6.14.0 (carr. paid).

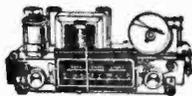**LISTEN****WITHOUT INTERFERENCE**

Fully built V.H.F./F.M. Set for £8.12.0 (carr. pd.). Covers 88/95 Mc/sec. Wired, aligned and tested. Mullard permeability tuner and 4 valves (ECC85, ECL82 and two EF91). 2 diodes. Cheap room dipole, 10'—300 ohm twin feeder, or co-axial cable. 6d. yd.

**PUSH-PULL AMPLIFIER £4.15.0**

(4/- Carr.)

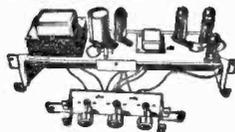


Brand new 200-240 A.C. mains. Bass, treble and vol. controls. With valves E280, ECC83 and 2-EL84 giving full 8 w. Chassis 12 x 3 1/2 x 3 1/2 in. With o.p. trans. for 2-3 ohm speaker.

Front panel (normally screwed to chassis) may be removed and used as "flying panel".

**3-VALVE AMPLIFIER (INC. RECT.).** 4 watts. Valves ECC83, EL84 and #Z80. Controls, volume, bass and treble. On/off switch. (Chassis size 6 1/2 x 3 x 2 1/2 in.) Round or 7 x 4 in. elliptical speaker. Not suitable for microphone input. A.C. only. 67/- P. & P. 3/-




**REREC BATTERY RADIO IN MAKERS' CARTON.** Valves DK96, DF96, DA96, DL96. Two Short Wavebands 2 to 7 Mc/s and 6.5 to 17 Mc/s. Cabinet 12 x 7 1/2 x 6 in. ONLY £5 (2/6 p. & p.); MW and SW £5.4.0 (plus 2/6 p. & p.).

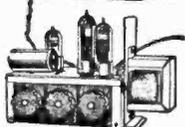
**STEREO AMPLIFIER £4.15.0**

(4/- p. &amp; p.)

Brand new. 200-250 A.C. Tone and volume controls each channel. E280, ECC83; and 2-EL84; giving 2 x 4W. Size 12 x 3 1/2 x 3 1/2 ins. O.P. Trans. for 2-3 ohm speaker. Separate on/off switch to allow balancing to remain set.

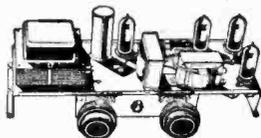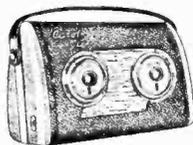**IN TIME FOR CHRISTMAS!**

A really elegant 6-transistor radio covered in sponge clean Duracour fabric, in latest two tone shades. M.W. and L.W., ferrite rod, provision for car aerial. 2-colour scale. With PP9 battery giving 300 hours use. Weighs under 4lbs. With carrying handle. 12 x 7 1/2 in. high x 4 1/2 in. at base tapering to 2 1/2 in. at top. Brand new, fully guaranteed, £10.0.0. Carr. paid. Worth £16.



**SAVE 10/-.** Swiss made Unic Shaver operating from 1.5 v. battery, usual price 59/8. Our price 50/- with battery. Takes U2 battery. Not a toy, but a shaver (carr. paid).

**GARRARD SINGLE 4-SPEED RECORD PLAYER. TA Mark II.** £9.10.0, carriage paid.

**SUPERIOR GRAMOPHONE AMPLIFIER 3 valves, 4 watt**


13 1/2 x 7 1/2 in. (2 1/2 in. front to back). 3 front controls, bass, treble, vol. on-off. 6 in. circ. or 8 x 5 in. speaker; UY85, UF80 and UL84. Mains trans. 200-240ac; "gold" fret front. ONLY 70/- (p.p. 3/6).

**NEW LOUDSPEAKER BARGAINS. Good Makes.**

2-3 ohm. 13 x 8 1/2 in. 35/- (4/-); 7 x 4 in. 14/8 (2/-); 6 1/2 x 4 1/2 in. 12/6 (2/-); 10 x 6 in. 25/- (3/-); 5 in. 12/- (2/-); 4 in. tweeter 7/6 (2/-); 7 x 5 1/2 in. 17/6 (2/-); 9 x 6 in. 22/- (2/6); Postal charges bracketed.

**MAINS OPERATED RADIO CHASSIS AND AMPLIFIER OF FAMOUS MANUFACTURE**

Chassis 10 x 5 1/2 x 4 1/2 in. front to back. Valves: UBC41, UCH41, UF89, UL84 with metal rectifier, 5 in. speaker. Ferrite rod aerial. Tone, vol. and gram. position. Covers L. and M. waves. Limited quantity at only £6 (5/- carr.) complete with small dial. Unused and in working order.

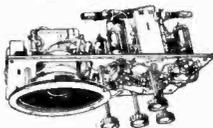**UNREPEATABLE OFFER OF AM-FM CHASSIS AT ONLY £9.9.0 carr. pd.**

A small quantity of Printed Circuit chassis by famous manufacturer. Valves UY85, UCH81, UF89, UABC80, UL84 and UCC85. O.p. trans. for 2-3 ohm speaker. Chassis 14 x 7 x 7 in. Front controls concentric, left—Vol. and Tone; right—W/c and Tuning. "Gold" centre knobs provided. 2-dial bulbs. Sockets, AE; E; Ext. sp.; 2 U. Mains isolating transformer free. Covers Long, Med., VHF (87-101 Mc/s). Unused slightly tarnished, but not dirty; New Mullard Valves; not our manufacture, so no guarantee. Dial in gold and brown, size 13 x 3 1/2 in.

**SPECIAL OFFER OF GOODMAN 10 x 6 in. SPEAKER** high gauss, with doped cone specially suitable for high fidelity work. Price 27/6 (post 2/6).


**CRYSTAL MICROPHONES.** TSL stick mike 25/-; small hand mike made by "Acos", 18/6. Both post paid.

**BATTERY ELIMINATOR.** For 4 Low Consumption Valves (96 range), 90 v. 15mA and 1.4 v. 125 mA. 42/6 (2/6 post). 200-250 v. A.C. Size 6 1/2 x 3 1/2 x 2 in. Also for 250 mA, 1.4 v. and 90 v. 15 mA at same price.

**AUTOMATIC RECORD CHANGERS. ALL 4-SPEED WITH TURN-OVER CRYSTAL CARTRIDGE** (carr. 5/- extra). Latest UA14. £7.10.0. Collaro C.60 Studio model, plays any records, 7-12 in. Only £7.15.0. Motor board for UA8, UA14 or Collaro 3/6 (post 1/6). Both UA14 and C.60 fitted monaural cartridge but wired for stereo.

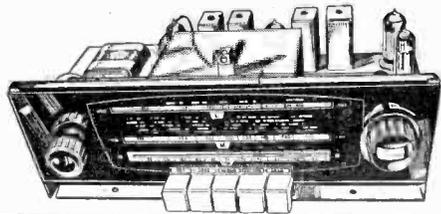
# BRAND NEW AM/FM (V.H.F.) RADIOGRAM CHASSIS AT £14 (Carriage Paid)

Tapped input 200-225 v. and 226-250 v. A.C. ONLY.  
 Chassis size 15 x 6 1/2 x 5 1/2 in. high. New manufacture. 12 m'ths guarantee.  
 Dial 1 1/4 x 4 in. in black and gold.  
 Pick-up. Extension Speaker. Ae., E., hd Dipole Sockets. Five "piano" push buttons—OFF L.W., M.W., F.M. and Gram. Aligned and tested with all valves and O.P. transformer. Tone Control Fitted.  
 Covers 1.5M—1.500 M., 200-500 M., 39-39 Mc/s.  
 Valves EZ80 rect., ECH81, EF89, EABC80, EL84, ECC85.  
 Speaker and Cabinet to fit chassis (table model), 47/6 (post 2/6).  
 10 x 6 in. **ELECTRICAL SPEAKER 20/-**, to purchasers of this chassis.  
**TERMS**—(Chassis) £5 down and 5 Monthly Payments of £2, or with Cabinet and Speaker £5.10.0 down and 6 Monthly Payments of £2. Cheap Room Dipole 10/-, Feeder 6d. yard.



This chassis is an ideal partner for the radiogram cabinet appearing on this page.
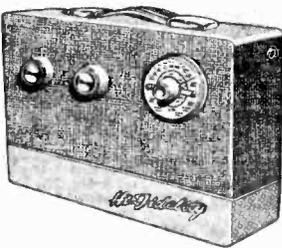
## THE "CANTATA" 6-TRANSISTOR AND DIODE PORTABLE



COMPLETE KIT FOR ONLY  
**£7.19.6**  
 (post 3/6)

- ★ 500mW push-pull output.
- ★ Ferrite rod aerial.
- ★ Car aerial socket and coil.
- ★ M.W. and L.W. full coverage.
- ★ Operates on two 4.5v cells.
- ★ Printed circuit board 8 1/2 x 2 1/2 in.
- ★ All holes drilled and component positions marked on reverse side of board.
- ★ Booklet of full instructions 2/6 for 16p. (refunded on purchase of kit).
- ★ Size 9 x 3 1/2 x 7 in.
- ★ 8 x 2 1/2 in. P.M. high quality speaker.
- ★ Two batteries Vinair covered cabinet, two tone.
- ★ High Sensitivity.
- ★ Good selectivity.
- ★ Mullard transistors OC44, 2 x OC45, OC81D, and 2x OC81.
- ★ Top grade Weymouth Radio coils and transformers.
- ★ Alignment service if required 17/6 (inc. post).
- ★ Write for list of prices.
- ★ All parts supplied separately.
- ★ Note the total cost—no extras at all.
- ★ Built in two hours.

**MINIATURISED COMPONENTS FOR TRANSISTOR SET.**  
 3 I.F. trans. 7/16in. sq. x 9/16in.; 2-gang 165pF valve 65pF; 1 x 1 x 1/2 in. input and output trans. each 9/16in. cube; osc. coil. THE LOT for 34/- (post 2/-).

**TRANSISTORS, Top Grade.** Two matched OC78: 1—OC78D; 1—OC44 (yellow); 2—OC45 (orange and blue). THE LOT of 6 for 37/6 (registered 1/- extra).

### AERIALS

**Combined B.B.C. (Single Dipole) and Band 3 I.T.A. (5-Element) Aerial** with chimney lashings and Stand-off Arm £3.15.0.  
**I.T.A. (Band 3) Aerials**, for clipping to existing mast of diameter 1in. to 2in. Alternatively with wall-fixing plate at same price: 3 element £1.2.0, 5 element £1.10.0, 8 element £2.10.0, 11 element £3.2.6. Chimney lashings and Stand-off Arm 20/- extra for each of above.

**Lot Mounting I.T.A. Aerials**, 3 element 20/-, 5 element 26/-, Larger aerials for I.T.A. and B.B.C. can be supplied to special order.


**Double 6 Element I.T.A. Plus B.B.C. "H" Aerial** with 10ft. pole and double chimney lashings. £8.10.0.

*All the above aerials are carriage paid.*  
**An I.T.A. Table Top Aerial** with amazing performance. The Wolsey Hi-Q at 19/6 (2/6 post). Good reception up to 20 miles. Cross-over unit in base with socket for B.B.C. aerial. Slightly tarnished at 12/6 (2/6 postage).

**PERSPEX**, 15 x 12 x 1/2 in., tinted blue/grey, 6/6; 12 x 9 1/2 x 1/2 in., Clear, 5/-; 16 x 14 x 3/16ins., Clear 7/6. Postage 2/- on 1; 3/- on 2 or more; 6 post paid.

Send 6d. (stamps will do) for 20 page illustrated catalogue. All New Goods. Delivered by return. Terms: One-third down and balance plus 12/6 in four equal monthly payments. Postage with down payment (C.O.D. 2/- extra). See Special Terms for A.M./F.M. Chassis  
**ALL ITEMS GUARANTEED 12 MONTHS—B.V.A. VALVES 3 MONTHS.**

## SUPERB CONTEMPORARY CABINET

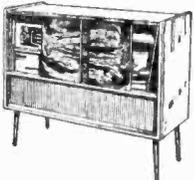

Fitted with 3 sliding doors providing room for Radio Autochanger, speakers, and record storage. Size 38 x 24in. high (plus legs 8in.) x 16in. Polished walnut.

PRICE 15 Gns.

Free delivery in London area, 35/- carriage elsewhere.

## THE "CABY" TEST METERS

Prices include Test Prods, Batteries, Instruction Book. Also measure dB. Accuracy: A.C. 3 per cent, D.C. 2 per cent.

A-10 **£4.17.6** B-20 **£6.10.0**

A.10—2K ohms/v. on A.C. and D.C. volts (10, 50, 250, 500 and 1000 v.); 10K and 1M ohms; 1mA, 25 mA and 250 mA. D.C. Size, 5 1/2 x 3 1/2 x 1 1/2 in. Weight 17 oz.

B.20—10K ohms/v. on 0.5 v. and 2.5 v.; 4K ohms/v. on 10, 50, 250, 500 and 1000 v.; A.C. and D.C. Resistance, 2K, 200K, 2M and 20M ohms; D.C. current, 100 microA, 2.5 mA, 25 mA, 250 mA. Size 5 1/2 x 3 1/2 x 2 1/2 in. Weight 24 oz.




## GRAMOPHONE AMPLIFIER

With 5in. SPEAKER. Baffle 12 1/2 x 6in. EZ40 and EL41, Tone and Volume On/Off switch. Two Knobs. Ready to play. Useful for Stereo. ONLY 57/-, post 3/-.


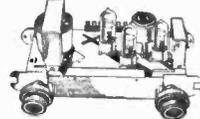
## 3-VALVE AMPLIFIER (INC. RECT.)

21 watts. ECC83, ECL82 and EZ80. Controls, volume bass and treble. On/off switch. Overall size 12 x 4 x 4 1/2 in. over valves. Mains and O.P. trans. and 6 1/2 x 4 1/2 in. Celestion speaker. Suitable for microphone input and for guitar amplifier. A.C. only.



70/- P. & P. 4/-.

## "READY TO USE" ITA CONVERTER

Direct switching ITA to BBC, metal rectifier, co-axial plug. Can be fitted in 5-10 mins., and needs no alteration to your set. ALL AREAS. ALL SETS. ALL CHANNELS. 12 months' guarantee (3 months on valves). Separate gain controls. Valves ECF80 and ECC84. Switch positions OFF—ITA—BBC. Bakelite moulded cabinet, 8 1/2 x 4 x 6 in. 70/- (3/- P. & P.).



## PANEL OF 7 POTS.

10 x 1 1/2 in. 4 x 1M; 3 x 2M. 4/- (post 1/-).



6 DIFFERENT PRE-SET POTS. 2K to 500K. 3/- (post 1/3).

SIEMENS-HALSKE RECTIFIERS. 250 v. 50 mA. 1/2 wave, 6/6, post paid.

# GLADSTONE RADIO "SCALA", CAMP ROAD, FARNBOROUGH, HANTS.

Also at 347 New Road, Portsmouth, Hants, and 56 Stokes Croft, Bristol 1.  
 Farnborough closed Saturdays, Portsmouth and Bristol closed Wednesday.  
 Posted Orders to Farnborough Please.



# Valves by return post

AZ1	10/-	EC91	15/11
AZ31	10/-	ECC81	8/-
DAF96	8/-	ECC82	7/6
D96	8/-	ECC83	9/-
DK9	8/-	ECC84	10/-
DL96	8/-	ECC85	9/6
EABC80	9/-	EL91	4/6
EAF42	9/6	EFC82	10/6
EB91	4/6	ECH42	9/6
ECB33	6/9	ECH81	9/-
EBC41	8/9	ECL80	9/6
EBC90	8/6	ECL82	10/6
EBF80	9/9	EF36	3/6
EBF83	13/11	EF41	9/6
EBF89	9/6	EF50	5/-
EBL21	23/3	EF50SYL	7/-
EBL31	23/3	EF80	7/-
EC90	4/6	EF85	7/-

EF86	12/6	GZ32	11/6
EF89	8/9	HL23DD	8/6
EF91	5/9	HL42DD	10/-
EF91(BVA)			
EF92	6/-	KT2	5/-
EF183	15/-	KT33C	6/-
EF184	15/-	KT61	10/-
EF185	15/-	KTW61	6/6
EF186	15/-	MX40	12/6
EF187	15/-	OZ4	4/6
EF188	15/-	PCC84	12/-
EF189	15/-	PCC85	8/6
EF190	15/-	PCF80	8/9
EF191	15/-	PCF82	11/6
EF192	15/-	PCL83	13/6
EF193	15/-	PCL84	10/-
EF194	15/-	PL36	13/6
EF195	15/-	PL81	11/-
EF196	15/-	PL82	8/6
EF197	15/-	PL83	9/6
EF198	15/-	PL84	9/6
EF199	15/-	PKX25	12/6
EF200	15/-	PF80	7/6
EF201	15/-	PF81	7/6
EF202	15/-	PF82	7/6
EF203	15/-	PF83	7/6
EF204	15/-	PF84	7/6
EF205	15/-	PF85	7/6
EF206	15/-	PF86	7/6
EF207	15/-	PF87	7/6
EF208	15/-	PF88	7/6
EF209	15/-	PF89	7/6
EF210	15/-	PF90	7/6

UL84	9/-	5R4GY	9/6
UU6	19/3	SU4G	5/-
UY1N	12/6	SV4	11/6
UY41	6/6	SY3G	8/-
UY85	7/-	SY3GT	7/6
Y23	5/-	SZ4G	9/-
VRI05/30	8/-	6A7	10/-
VRI50/30	7/6	6AB8	9/-
VU39(MU)	6/6	6AK5	5/-
6AL5	4/-	6K8GT	10/-
6AM5	7/6	6L6G	8/-
6AM6	4/-	6L6M	9/6
6AQ5	7/6	6L8	11/6
6AT5	8/6	6N7GT	7/6
6BA6	7/-	6Q7G	7/6
6BE6	7/6	6Q7GT	9/6
6BH6	7/6	6SK7	6/-
6B16	6/6	6SL7GT	8/-
6B6W	9/-	6SN7GT	7/6
6C4	6/6	6SQ7	9/3
6C5GT	6/6	6U4GT	12/-
6C6	5/-	6V6	5/-
6C6H	5/-	6V6GT	7/6
6CH6	7/6	6X4	7/6
6F6G	7/-	6X5G	7/-

Expanded Metal, 12 x 12in. 5/- each.  
 B.S.R. Monarch UA14 Record Changer. £6.19.6.  
 Collaro Studio Tape Deck. £10.19.6.  
 Tygan, 4/- square foot. 10 patterns available, send 1/- stamps.  
 Aerialite Golden Wand Room Aerial 17/6  
 12ft x 2in. Alloy Mast for aerials, 20/- each, Callers only.  
 Pre-set Potentiometers 2.5K, 50K, 100K, 1 Meg, each. 1/9 each.  
 Cabinet Lid Stays. 6d. each.  
 Assorted Knobs, various colours. 2/- doz.  
 Dial Bulbs, 6.3v. MES, 4/- doz. Box of 50, 12/6.  
 Potentiometers Single Pole Switch, 2 Meg, 100K, 500K, 1 Meg, each. 1/- each.  
 Assorted Mains Dropping Resistances, 6 for 3/6.  
 Pneumatic Lid Stays, 2/6 each.  
 Spade Terminals, white and black, 1/6 doz.  
 Cabinet Lid Hinges, Bronze, 1/9 doz.  
 Insulated Sleeving, 2/6 bundle.  
 Toggle Switches, D.P.D.T. and S.P.D.T., 1/9 each.  
 Flash Lamp Bulbs, 2.5v, 12/6 per 100.  
 Semi-airspaced Co-axial Cable, Brown or Cream, 6d. yd.  
 British 4-pin Paxolin Valveholders, 2/- doz.  
 4-valve B7G Portable Angle Chassis, ready drilled, 1/6 each.  
 Switch, 3 pole, 3 way, 3 bank, 2/3 each.  
 Microphone Inserts, 1 1/2in. diam., 7/6 each.  
 Transistors, OC169, 10/6; OC77, 10/-; OC201, 12/6.  
 Ferrite Rod Aerial and Coil, 3/6 each.  
 Solid Dielectric Condensers, 0.0001mF, 0.0003mF, 0.0005mF, 4/9 each.  
 Acos Microphone, MIC 45, 25/6; MIC 40, 19/6.  
 B.S.R. Turnover Cartridges, TC8M and TC8H, 29/9 each.  
 T.S.L. Speaker Units, LPH70 25/- each and LPH45 25/- each.  
 Repanco, XT6 10/-, XT7 10/-, TT9 12/6, TT10 12/6.  
 Crystal Set Coil, Type DRX1, 2/6 each.  
 Dual Range High Gain Coil, 4/- each.  
 Wavechange Switches, 3P 3W, 4P 3W, 3P, 4W, 2P 6V, 1P 12W, 3/- each.  
 Panel Paint, Black, 3/- tin.

All parts for "Practical Wireless" Mini-amplifier available from stock.  
 Transistors, V6/R2 9/3, OC71 6/6, OC72 8/-, OC75 8/- each.  
 Ardenite Transformers, D240 10/-, D1001 12/-.  
 Garrard Cartridge, GC2/PA, 15/6 each.  
 Stylus Pressure Gauge by Garrard, 20/3 each.  
 Battery Charger Transformer for 2, 6 and 12 volt batteries, 4 amp, 21/-.  
 Output Transformer, 5000/3 ohms. 60mA, 5/9 each.  
 L.T. Metal Rectifiers for Battery Chargers 2amp 7/-, 3amp 10/-, 4amp 12/6, 5amp 14/6  
 Plessey 10 x 6in. PM Speaker Unit, 21/-.  
 Crystal Microphone, Type BM3 for hand, desk or floor stand use, 45/- each.  
 B.S.R. AF333 Pick-up Matching Transformer, 36/-.  
 High Resistance Headphones, 4000 ohms 13/6 pair.  
 CCIR Calibration and Test Tape, 49/6 reel.  
 Diodes, OA70 3/-, OA5 3/-, OA10 4/-, OA81 3/-.  
 Set of Transistors comprising 1 OC44, 2 OC45, 1 OC81D, 2 OC81, 37/6 set.  
 Silicone Rectifier, Type 1WVPS, 125 v. RMS, 2 connected in series in half-wave circuit, output current 500mA, 16/6 pair.  
 Empty Tape Spools, 3in. 1/6, 5in. 2/1, 7in. 3/- each.  
 Continental Screened Jack Plug, 3/6 ea.  
 Solon Instrument Iron, 25 watts, 24/- ea.  
 Litesold Soldering Iron, 240 v. 10 watts, 3/32in. Permabit, 2/16 each.  
 Steadfast 6 in one File Set. An ideal tool for model makers, radio constructors, etc. 10/6 each.  
 Repanco One Valve Receiver, complete in every detail, 45/-.  
 Collaro Studio C60, 4-speed Automatic Record Changer. £7.19.6.  
 PIFCO Radio Meter, 32/6.  
 Midget I.F. Transformers, 465 kc/s, 9/- pair.  
 4-Pin Vibrators, 6 v., 8/6 ea.; 12 v., 2/6 ea.  
 Tubular Copper Rods, 12in. long, 4/- doz.  
 Solder, 1 lb. reel, 7/6.  
 2-Gang Condensers, 500pF, Standard 7/6, Midget 7/6.

Paxolin Sheet, 1/4in. thick, 6 x 6in. 1/- 12 x 6in. 2/-, 12 x 12in. 4/-.  
 Grelco 10-way Connector Strip, 1/- each.  
 Garrard TA Mark II 4-speed Single Player, £8.10.0.  
 Heater Transformer, 6.3 v. 1 1/2 amps, 6/9 each.  
 Rectifiers, 14A86 17/6, 14A97 21/-, 14A100 21/-.  
 Loudspeaker Unit, 7 x 4in. Goodmans, 15/6 each.  
 Collaro Junior 4-speed Turntable and Pick-up, 75/-.  
 Acos Crystal Stick Microphone, MIC 39/1, 3/6 each.  
 B.S.R. Monarch GU6, 4-speed Gramophone Unit on Motorboard, 11 x 8 1/2in., £4.19.6.  
 Telefunken Stereo High Fidelity Amplifier, £8.8.0.  
 BIB Recording Tape Slicer, 18/6.  
 P.W. Transistor "Six", printed circuit version, £8.15.0.  
 "Wireless World" Radio Valve Data, 7th edition, 6/-.  
 Transistor, 1 watt Amp., ready built, 72/6.  
 Sub-miniature 2-way Jack Plug and Socket, 2/6 pair.  
 Personal Earphones, Crystal High Imp. 8/-, Magnetic Low Imp. 8/-.  
 J.B. "00" Twin Condenser, 12/6 each.  
 Hunts W99 Condensers, 0.001mF, 0.01mF, 0.02mF, 0.04mF, 9d. each.  
 Signal Lamp Fittings, MES Holder available with Red, Green, Clear and Amber Glass, 2/3 each.  
 Aluminium Chassis, 6 x 4 x 2 1/2in. 4/6 each; 12 x 5 x 2 1/2in. 6/9 each.  
 Standard Can Condenser, 32 x 32 x 32mF, 350 v., 2/9 each.  
 Aerialite Video "V", All Stations TV FM Indoor Aerial, 23/6.

**CATALOGUE IS NOW AVAILABLE. PLEASE SEND 1/- IN STAMPS FOR YOUR COPY. TRADE CATALOGUE ALSO AVAILABLE. FOR WHICH PLEASE ATTACH YOUR BUSINESS LETTER HEADING.**

**TERMS:** Cash with Order or C.O.D. Postage and Packing Charges extra. Single valves 9d., Minimum Parcel Post charges 2/-. Please include sufficient postage with your order. Minimum C.O.D. fees and postage 3/6. These Postal Rates apply to U.K. only. For full terms of business see inside cover of catalogue. Personal Shoppers 9 a.m. to 5 p.m. Mon. to Friday, Saturday 10 a.m. to 1 p.m.




103 LEEDS TERRACE  
 WINTON STREET  
 LEEDS 7

# HARVERSON SURPLUS CO. LTD. PLEASE TURN OVER FOR ADDRESS AND MORE BARGAINS
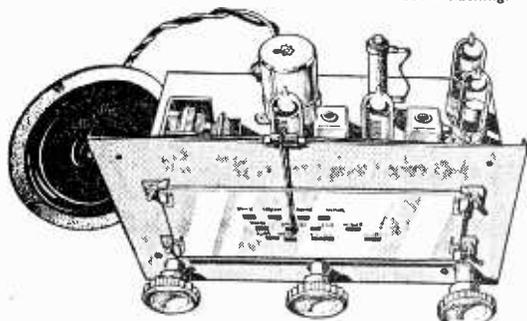
## 2 BAND SUPERHET CHASSIS with Speaker

**ONLY £4.19.6**  
Plus 6/6 Post & Packing.




A quality 4 valve AC/DC superhet chassis made by a world famous manufacturer. Long and Medium wave coverage. Fitted with a cord and drum reduction tuning drive and attractive illuminated glass dial (size 6½ x 2½in.). Controls: Volume on/off, tuning and wave change. The receiver is self-powered, employing a mains dropper and a valve rectifier. Chassis dimensions 6½ x 9 x 5½in. high. Supplied complete with a good quality 5-inch loudspeaker, valves (UCH42, UAF42, UL41, UY41), AC/DC mains input lead, ivory knobs, etc.

**DON'T HESITATE, ORDER NOW!** This unbeatable bargain is bound to sell out quickly at only £4.19.6, plus 6/6 post and packing.

## 4 STATION PRESET CHASSIS with Speaker


**ONLY £4.17.6**

Plus 6/6 P. & P.

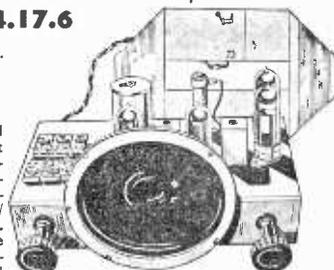


A compact, 4 station preset mains transportable receiver for operation from AC/DC mains. Two simple controls, volume on/off and 4 position station selector. The latter is set to Light Programme (Long Wave), Third Programme, Home Service and Light Programme (Medium Wave), but may of course be adjusted to alternative selections if required. A frame aerial with throw-out extension is supplied, making this receiver ideal as a general purpose transportable set for the home. A fully smoothed power supply is provided from AC/DC mains input by a mains dropper and a valve rectifier. The good tone qualities are assisted by the provision of a quality 5in. speaker, which is ready-mounted on the chassis (this is easily detachable if alternative positioning is required). Valve line up, UCH42, UAF42, UL41, UY41. This chassis (size 9 x 6½ x 5½in. high) is supplied complete with valves, knobs, mains lead, aerial, etc. It is beautifully made by a famous maker, and is a first-class buy at the rock bottom price of only £4.17.6, plus 6/6 post and packing.

## A.M. RADIOGRAM CHASSIS

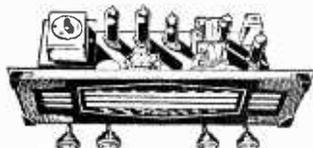

A chassis of distinction, by a famous maker. Covering Long, Med. and Short Waves, plus gram position, this chassis (size 15½ x 7 x 6½in. high) incorporates the latest circuitry, using fully delayed A.V.C., and negative feedback. Controls: Tone, Vol. On/Off, W/Change (L.M.S. and Gram), Tuning. Tapped input 200-250 v. A.C. only. An attractive brown and gold illuminated dial with matching knobs, make this one of the most handsome, in addition to being one of the best performing chassis yet offered. Complete with valves (ECH81, EF89, EBC81, EL84, EZ81), knobs, output transformer, leads, etc. **OUR PRICE ONLY £9.19.6** plus 4/6 post & packing.

## HARVERSONS' F.M. TUNER

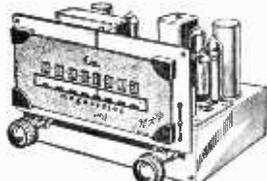


At last a quality F.M. Tuner Kit at a price you can afford. Just look at these fine features which are usually associated with equipment at twice the price.

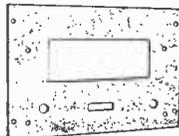
### NOW AVAILABLE

A robust cabinet made from heavy gauge metal which has been specially designed to house the above F.M. Tuner. Beautifully finished in a choice of glossy hammer green, or hammer grey enamel, or black crackle. The front panel (illustrated) has holes for control spindles, and apertures for tuning dial and magic eye. **PRICE 25/-** P. & P. 1/9. (Front panel only 10/6, P.P. 9d.).

- ★ F.M. Tuning Head by famous maker.
  - ★ Guaranteed Non-drift.
  - ★ Permeability Tuning.
  - ★ Frequency coverage 88-100 Mc/s.
  - ★ OAB1 Balanced Diode Output.
  - ★ Two I.F. Stages and Discriminator.
  - ★ Attractive maroon and gold dial (7 x 3in. glass).
  - ★ Self powered, using a good quality mains transformer and valve rectifier.
  - ★ Valves used ECC85, two EF80's, and EZ80 (rectifier).
  - ★ Fully drilled chassis.
  - ★ Everything supplied, down to the last nut and bolt.
  - ★ Size of completed tuner 8 x 6 x 5½in.
  - ★ All parts sold separately.
- Plus 8/6 P.P. and Ins. **£4.19.6**  
Circuit diagram and illustrations, 1/6, post free.


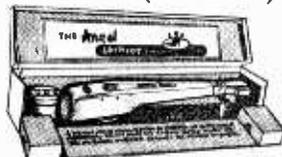
## THE WORLD FAMOUS E.M.I. ANGEL TRANSCRIPTION P.U. (Model 17A)



A Pick-up for the connoisseur originally priced at £17.10.0. The last remaining few offered at £5.15.0, plus P. & P. 5/-.


## MAINS PORTABLE SOLDERING IRON

Probably one of the most outstanding soldering instruments yet produced, this iron has a detachable handle which can be placed over the bit and barrel, enabling it to be carried in complete safety even when hot. The provision of an extremely stable 30w element makes this ideal for transistor and all similar lightweight applications. Brand new in P.V.C. bag, with lead and plug. **ONLY 18/9**, plus 1/3 P. & P.

## MINIATURE EARPHONE WITH CORD SUB-MINIATURE PLUG AND SOCKET

A deaf aid type earpiece of top grade quality. Gives an exceptionally crisp reproduction of both speech and music. Brand new and fully guaranteed. Two types available. CR-5 high impedance crystal, MR-4 low impedance magnetic. **ONLY 7/6** Plus 1/- P. & P.

## F.M. TUNER HEAD

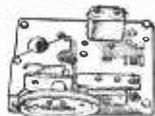


A permeability tuned tuner head by a famous maker, supplied without valve (ECC85) 18/6 plus 1/9 P. & P. Valve 8/6 extra.

# HARVERSON SURPLUS CO. LTD.

## Introducing HARVERSON'S Monaural Amplifier Kit

**39/6**

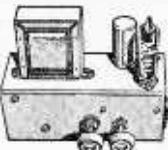

In response to numerous requests from delighted purchasers of our "SUPER STEREO KIT" we have produced a "MONAURAL AMPLIFIER" on similar lines.

★ A 2JCL 82 valve provides a triode amplifying stage, and a pentode output stage (3 watts), enabling good amplification and sparkling reproduction to be combined with physical compactness (amplifier size, 7 x 3½ x 6½in. high).

★ Modern circuitry design, good quality O.P. transformer (to match 3Ω) keep hum and distortion to a low level.


★ The controls, volume on/off, and tone, are complete with attractive cream and gold knobs.

★ The amplifier has a built-in fully smoothed power supply, using a good quality mains transformer (A.C. mains only) and metal rectifier.

★ All you need is supplied including easy to follow instructions which guarantee good results for the beginner and expert. All components, leads, chassis, valve, knobs, etc., are first grade items by prominent manufacturers.

OUR PRICE **39/6**  
Plus 4/6 Post and Packing

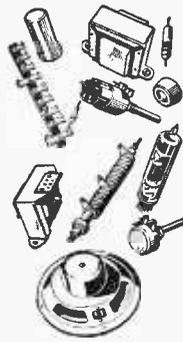5in. LOUDSPEAKER TO SUIT 14/6 EXTRA  
ALL PARTS SOLD SEPARATELY



## THE HARVERSON 6 TRANSISTOR & DIODE SUPERHET KIT

A first class 2 wave band transistor superhet in kit form.

- ★ Printed circuit panel (size 8½ x 2½ins.)
- ★ 3 Pre-aligned I.F. Transformers.
- ★ Output Transformer.
- ★ 5 inch 5 Ω Speaker.
- ★ High gain Ferrite rod aerial.
- ★ First grade G.E.C. transistors.
- ★ Car aerial socket.
- ★ Push/Pull output.

All parts down to the minutest item with simple instructions. ONLY

**£6.19.6** Plus 2/6 P. & P.

Cabinet to Suit (if available) 15/- extra.



## BARGAIN MONTH FOR TRANSISTORS

POWER			
OC36 ... ..	10/-	GET15 ... ..	9/-
OC44 ... ..	9/-	GET15 (matched pr.) ...	16/6
OC45 ... ..	8/-	GET102... ..	7/6
OC71 ... ..	5/-	XAI103 ... ..	8/6
OC75 ... ..	6/6	PXA101 ... ..	9/6
OC76 ... ..	6/6	PXA102 ... ..	9/6
OC78 ... ..	6/6		
OC78D ... ..	6/6		

### DIODE

OAB1 ... .. 3/-

Please add 6d. postage for each transistor.

### TRANSISTOR SPEAKER

Western Electric 3Ω or 80Ω speaker. Size 2½ x 1½in. deep. 12/6 p.p. 1/-.

### SUPERHET CHASSIS—less Valves & Cabinet

Modern AC/DC chassis with printed circuit and ferrite rod aerial. Although not completely built, the main components are mounted. L & M. wave coverage. 4 valves (UBF89, UCL83, UCH81, UY85). Everything supplied except valves and cabinet. With speaker and simple instructions. **£3.6.6** plus 3/6 P. & P.

### COIL and TRANSFORMER SET FOR TRANSISTOR SUPERHET

3 I.F. Transformers, one oscillator coil, one driver transformer, and wound ferrite aerial (Med., Long and aerial coupling) 28/6 complete, post 1/-. 6 transistor printed circuit board to match 8/6, post 9d Circuit diagram 1/6 extra.

### CONDENSER/RESISTOR PARCEL

50 mixed P.F. Condensers and 50 mixed Resistors. An assortment of useful values. All popular sizes—all new—a must for the serviceman and constructor **10/-** P. & P. 1/-.


## THE HARVERSON COMPLETE F.M./V.H.F. RECEIVER KIT **£6.19.6**

AT LAST—A COMPLETE F.M. RECEIVER IN KIT FORM!

Specially designed with the home constructor in mind, this kit enables the construction of a completely self-contained V.H.F. receiver, at fraction of the normal cost of comparable equipment. This is basically a quality self-powered F.M. tuner plus 2 separate audio amplifier stages, and output transformer and speaker.

- ★ F.M. Tuning Head by famous maker.
- ★ Guaranteed Non-drift.
- ★ Permeability Tuning.
- ★ Frequency coverage 88-100 Mc/s.
- ★ OAB1 Balanced Diode Output.
- ★ Two I.F. Stage and Discriminator.
- ★ Self powered using a good quality mains transformer and valve rectifier.
- ★ Valves used ECC85, two EF80's, ECL82 and EZ80 (rectifier).
- ★ Fully drilled chassis.
- ★ Good quality speaker.
- ★ Well designed output transformer.
- ★ Attractive maroon and gold glass dial.
- ★ Two output stages (using ECL82).
- ★ Everything supplied, down to the last nut and bolt.
- ★ Compact size.
- ★ All parts sold separately.


OUR PRICE **£6.19.6** Plus 4/6 P. & P.

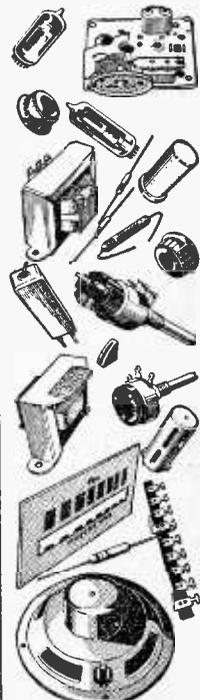

# 83 HIGH STREET, MERTON, S.W.19

CHerrywood 3985/6

## 14 WATT HI-FI AMPLIFIER KIT

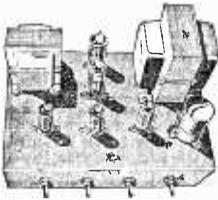


A kit designed to meet the exacting requirements of the audio enthusiast, yet remain within the price range of the average constructor. A stylishly finished monaural amplifier with an output of 14 Watts from 2 EL84's in push pull. Super reproduction of both music and speech

(Frequency response  $\pm 3\text{dB}$  c/s-60 Kc/s with negligible hum.) Separate inputs for mike and gram allow records and announcements to follow each other and make this amplifier ideal for small halls, youth clubs, etc. Fully shrouded Linear output transformer (to match 3-15 $\Omega$  speaker), and fully shrouded mains transformer (these alone are worth over £3.10.0). 2 independent volume controls, and separate Bass and Treble controls are provided, giving good lift and cut. Valve line up 2 EL84's, ECC83, EF86 and EZ80 rectifier. All parts down to the last nut and bolt, including valves, knobs, heavy gauge metal chassis finished in glossy hammer green enamel mains and output transformers finished to match.  
P. & P. 6/6 (simple instruction booklet 1/6, free with kit).

ONLY **£6.19.6**


## QUALITY RECORD PLAYER AMPLIFIER KIT

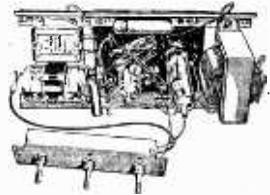

A top quality record player amplifier in kit form. This amplifier (which is used in a 29-gn. record player) has a printed circuit and has an internal fully smoothed power supply (input AC/DC Mains) using a mains dropper and contact cooled rectifier. A flying panel is supplied accommodating BASS, TREBLE AND VOLUME — ON/OFF controls. 2 valves (UL84 and UF89) and linear output transformer give crisp reproduction from all records at 4 watts. Our price for the complete kit of parts (including valves) ONLY **59/6** plus P. & P. 6/6. Simple instructions 1/6. (Free with kit).
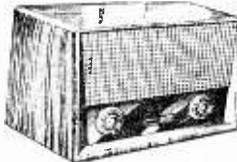
## SUPER TABLE RADIO CABINET

A very fortunate purchase allows us to offer this quality table radio cabinet for only 18/6 (this cabinet cost the manufacturers 35/- each to make). The positions of the controls make it ideal for housing our 6 TRANSISTOR SUPERHET KIT described opposite. Beautifully finished in walnut and tegan.




OUR PRICE **18/6** Plus 1/6 P. & P. ins.  
ONLY


## SUPER STEREO KIT MK. II

A kit of ready-built units only requiring interconnection. Comprising two midget 3W amplifiers, push button switch, transformer, control unit (bass, treble and vol.), power pack, two speakers, indicator light valves (ECL82, EZ80 range), and comprehensive instructions.

**£3.19.6** Plus 6/6 P. & P.

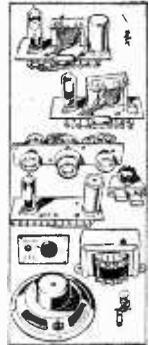

## E.M.I. 4-speed Player and P.U.

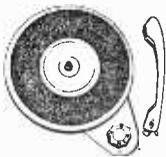

Heavy 8 3/4 in. metal turntable. Low flutter performance 200/250V shaded motor with tap at 80V for amplifier valve filament if required. Turnover LP/78 head.

PRICE 89/6 Plus 4/6 P. & P.

**VALVES** WE HAVE 20,000 IN STOCK—ALL AT BARGAIN PRICES. See our list in December "Practical Wireless", write, phone or call for your requirements

## SPECIAL OFFER... 6 TRANSISTOR RADIO IN KIT FORM

Special offer. Limited quantity only of new ex-manufacturers' parts to make a 6 transistor 2 wave band superhet chassis. Ideal for portable or table radio. All parts including transistors, ferrite aerial, printed circuit, etc., but EXCLUDING speaker and cabinet. P. & P. 2/6  
Few Only. **£4.19.6**  
Simple instructions 1/6 (Free with kit).

**SPECIAL OFFER**  
**54-in. LOUDSPEAKER SILKS**  
Heavily woven in ivory and gold. Original price 35/- per yard length. OUR SPECIAL PRICE, 13/6 per yard length. P. & P. 1/6.

## TAPE DECKS

B.S.R. Monardeck (single speed) 3 1/2 in. per sec., simple control, uses 5 1/2 in. spools. £7.5.0, plus 5/6 carr. and ins. (tapes extra).  
COLLARO STUDIO DECK £10, plus 5/6 carriage and ins. (tapes extra).

## CRYSTAL MIKES

T.S.L. Stick Mike.....22/6  
ACOS (latest model).....18/6

## PLESSEY SPEAKER

8 x 5 inch 3 $\Omega$  Speaker.  
Large Pot. .... 12/6, P.P. 1/6

## HI-FI STEREO

**MONAURAL AMPLIFIER**  
A 5 valve HI/FI amplifier with switched stereo/monaural operation. Output 3 watts per channel, provision for bass and treble speakers on each. Volume and tone controls fitted both channels. All housed in stylish blue/grey metal case, with gold finished knobs and trimmings. **£9.19.6** Plus 4/6 P. & P.

## PUSH-BUTTON TRANSISTOR SWITCH

A 3 push-button switch, specially designed for transistor radios. Button functions provided are on-off, long and medium wave. The back of switch is also equipped with a rack for mounting a Ferrite Aerial. Easily worth 15/-.  
OUR PRICE ONLY **5/6** P. & P. 1/-.

# RELDA OFFERS THE GREATEST VALUE IN MINIATURE COMPONENTS FOR THE 'KIT FAN'

**MINIATURE DP/DT SLIDE WAVE-CHANGE SWITCH**  
2/6 each.

**MAINS 3 AMP. DP/DT TOGGLE SWITCH** with on/off plate. 4/- each.

**TRANSISTOR SPECIAL!**  
**5K. EDGEWISE MINIATURE VOLUME CONTROL MODEL K2.** 16, with switch and ivory knob. As used in all miniature transistor radios. 4/6 each.

**LAPEL MICROPHONE M178**  
Precision engineered Crystal Microphone—for lapel or hand use. Only 1 1/2 in. diameter. Exceptionally sensitive. Chrome plated case and clip includes 5ft. shielded cable. Only 17/6.

**CRYSTAL MICROPHONE INSERTS MODEL MC.1.** Precision disc type crystal microphone cartridge. Output:—53dB. Response: 100—6,000 c.p.s. PRICE 6/6.

**SPARE VALVE KIT**  
Here's a gift for all 39 and 18 Set owners! Case contains 4 AEP2 & 1 A T P 4 valves. Only 10/- P. & P. 2/6

**AERIAL VARIOMETERS**  
These magnificent instruments will enable you to receive maximum signal strength on all S.W. receivers. Precision, calibrated control 12/6. P. & P. 2/6.

### SUB-MINIATURE TRANSFORMERS

Here is outstanding value in transistor transformers consisting of one Driver Transformer and one Output Transformer. Ideal pair for miniature transistor portables, etc.  
**Driver Model LT44:** Primary: 20k. Secondary: 1k. Centre Tapped. Ratio: 5 : 1.  
**Output Model LT700:** Primary: 1.2K. Centre Tapped. Output: 3.2 ohms. Ratio: 2 : 1. Complete with detailed instructions. Only 9/6 per pair. P. & P. 1/6.



### MINIATURE EARPHONE

A really sensitive dynamic earphone of exceptionally fine quality. Provides clear reproduction of music as well as speech. Fully Guaranteed and complete with transparent ear insert, 3 feet cord, sub-miniature plug and socket.  
CR-5 High imp. crystal 8/- Each  
MR-4 Low imp. magnetic 8/- Post 1/-

**JUST ARRIVED!**  
**A "MUST" FOR EVERY TRANSISTOR SET OWNER!**  
**9V. BATTERY CHARGER AND A.C. ELIMINATOR MODEL LA.6P**

Save those batteries during the winter by running your transistor set direct from A.C. Mains. Reactivate all your old 9V batteries.

Unit contains neon indicator and standard battery connections with nearly 2 yards of mains lead and plus. Also snap cord for connection to set.

LIMITED QUANTITY OFFERED FOR THE FIRST TIME IN THIS COUNTRY! **29/6** P. & P. 1/6

**ONLY 60/- Per Set**  
P. & P. 4/-

**PORTABLE TRANS/RECEIVER SETS**  
Consisting of transreceiver covering 7.4-9 Mc/s range up to 10 miles, complete with 5 valve headphones, microphone, junction box and 6ft. telescopic aerial. Only reqs 120 v. and 3 v. dry battery.  
**TWO FOR £8.** Post Free.  
**SPECIAL 135 V. H.T. BATTERIES.** Ideal for above. 12/6 each.

### PS.35. SUB-MINIATURE PLUG AND SOCKET



Two-way bakelite barrel Jack plug only 1 1/2 in. long. Socket only 1 1/2 in. long. 3/6 per pair. Post paid.

### CH.305 CHROME MINIATURE PLUGS AND SOCKETS

Size: plug barrel 1", socket 1". These will give your equipment that expert finish! 3/6 Per Set.

### S L I M RADIO PLUGS AND SOCKETS

**SOCKETS.** Two-way, black bakelite solder terminal PLUG and STURDY standard SOCKET. 5/6 per pair. Post Paid. Panel mounting, neat finish.

### P217A. MINIATURE 2in. SPEAKER

A miniature HI-FI speaker that outperforms all others. Designed to meet today's requirements for transistor, miniature and sub-miniature applications. Size 2 1/2 in. x 1 1/2 in. deep. Voice coil impedance: 8 ohms. Power range: 150-5000 c/s. Power: 200mW. 18/6.

**HOOVER ROTARY TRANSFORMERS**  
12 v. input, 500 v. output at 85 mA. or 6v. input 250 output at 75 mA.  
Only 10/6 each. P. & P. 2/-



**No. 7 MOVING COIL MICROPHONE INSERTS.** Ultra sensitive. As used in many Govt. Microphones! Size 1 1/2 in. dia. x 1 1/2" deep. Brand new and guaranteed. 6/6 each.

## All Transistor 2-STATION INTERCOM and Baby Alarm

**MODEL T1.302**

**12 Gns.**

Complete with battery and 60 ft. of wire.



Here is an Intercom system for both calling and conversing which uses the highest quality transistors and is operated from a single battery. May be used for multi-purpose applications especially where there is no local electrical supply and also where voltage fluctuations are severe. Specially suited for use in offices manufacturing plants, hotels, restaurants, residences and wherever conversation is required between two or more locations. Ideal Baby Alarm. Brief Spec: 3 transistors, 200 mW output, 9 v. battery, built-in 2 1/2 in. speakers. The Master station incorporates individual volume control to ensure perfect speech reproduction. The Sub-station incorporates a unique "buzzing" call system which ensures maximum efficiency. S.A.E. for further details.


## PYE COMMUNICATION RECEIVERS

World coverage on these famous Communication Receivers. They are the simplest type to use yet bring in stations that will amaze you. The ideal domestic receiver for medium wave during the day with Amateur stations at night. All have been converted to 230 v. A.C. mains and are guaranteed to work immediately. Incorporate Wave Switch. Audio gain aerial trimmer, high and low tone control, station locking device, aerial and earth inputs, speaker output sockets, etc. Size 17 x 8 x 9 1/2 in. Black crackle finish front panel. On demonstration at 87 Tottenham Court Road.

**P.C.R.2.** Medium and long waves and 6-23 Mc/s. Less speaker.  
**P.C.R.** Medium and long waves and 6-18 Mc/s. With speaker.  
(All the above P.C.R. Receivers have been completely reconditioned).

**ONLY £8.19.6**  
EACH TYPE

Plus **Order Early!**  
Callers 10/6

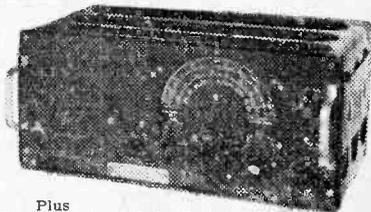


MAIL ORDERS TO  
(DEPT. P.), 32a COPTIC STREET,  
LONDON, W.C.1



CALLERS WELCOME AT  
87 TOTTENHAM COURT ROAD,  
LONDON, W.1 MUS 9606
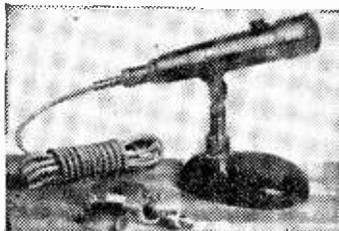
# PROVED to be the BEST BUY in the Country!



## 3-WAY SLIM CRYSTAL MICROPHONE

May be hand-held, stand mounted (either floor stand or desk stand) or suspended by lavalier cord. Response 60-10,000 Cps. Built in on/off switch. Output level—52db. Omni-directional head. Clips on or off standard stand adaptor permitting tilting for multi-angle use. Satin chrome finish.

## MODEL 100C

Supplied complete with 7ft. of shielded cable, lavalier cord and desk stand.

**ONLY 48/-**

## TUBULAR BAFFLE EXTENSION SPEAKER MODEL TS.30

Mounts vertically—mounts horizontally—mounts on wall—sits on desk! Designed for use with transistor radios, valve radios, car radios, amplifiers, auxiliary speakers in Hi-Fi and numerous other applications where quality reproduction of sound is required.

The cabinet is finished in beige leather, with contemporary gold baffles at each end. Complete with 12 ft. extension cord fitted with miniature plugs, individually cartoned and guaranteed.

**57/6**


P. & P. 2/6.

Model TS.30 will give your transistor set "Big Set" reproduction. Simply plug into earpiece socket and you will be amazed at the results!



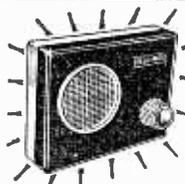**V. H. F. MOBILE AERIAL** and base, with PYE connections, 27in. overall, as used by Taxis, Police, etc., 7/6.

**U.S.A. WHIP AERIALS** 12ft. 10/- COMPLETE HEADPHONE AND MICROPHONE ASSEMBLY 10/- P. & P. 3/6.



**SUPER TRANSISTOR RADIO** With Miniature Speaker. Simple instructions enable anyone to build this miniature radio. Gives reception over the entire broadcast band. Each kit is supplied with all latest miniature parts including:

- ★ two transistors ★ ferrite rod
- ★ speaker ★ coloured plastic case
- ★ step by step illustrated instructions. Size 4 x 3 x 1in.

**ONLY 27/6** P. & P. 1/6. Battery 1/- ex.

★ Made available owing to public demand! ★

**ACCUMULATORS.** 2 volts 16 A.H. (unavailable). Ideal for 6 and 12 volts supply, etc. Brand new. Original cartons. Size 4in. x 7in. x 2in. 5/6 each. P. & P. 1/6. 3 for 15/- P. & P. 3/8. 6 for 27/6. P. & P. 5/-.



**RAM TAPE RECORDERS.** As previously advertised. Few available at £11.19.6. P. & P. 3/6.



## THE GREATEST MULTI-METER VALUE AVAILABLE TODAY!

**10,000 o.p.v. ON BOTH A.C. & D.C.**

A complete wired and tested instrument (not a kit) incorporating extra large 9in. meter face and unique slide range switch. Can be conveniently carried in the pocket and features unusually sensitive 10,000 ohms per volt AC-DC meter. 1 per cent precision resistors, and largest meter ever placed on an instrument this size. Single, easy to use range selector switch, can be appreciated by the novice and engineer alike. Complete with colour coded test leads and battery.

Size: 4 1/2 x 3 1/2 x 1 1/2 in. Model EP-10K **ONLY £5.19.6**

**FULL SCALE RANGES:**  
 D.C. VOLTAGE: 0-6-30-120-600-1200v. (10,000 o.p.v.)  
 A.C. VOLTAGE: 0-6-30-120-600-1200v. (10,000 o.p.v.)  
 D.C. CURRENT: 0-120 uA, 0-12-300mA  
 RESISTANCE: 0-20K, 0-2 Meg. (150 ohm, 15K at centre scale).  
 CAPACITANCE: 0.005 to 0.15 uF (at A.C. 6v.).  
 DECIBELS: -20 to +63db. (600 ohm, 1mW, 0dbm = 0.755 v.).  
 ACCURACY: D.C. Voltage and Current +2% i.s. A.C. Voltage +4% i.s. Resistance ±3% of total scale length.

## MINIATURE PANEL METERS

Precision built clear plastic miniature panel meters. Featuring d'arsonval movements, jewelled bearings, silvered dials with black numerals and pointers. Accuracy 2% of full scale. 1.21/32in. square fronts, 1 1/2in. overall front to back. Require 1 1/2in. diameter round hole in panel. All have clear plastic fronts with zero adjustment screws.



**"S" METER MODEL SR. 2P.** Standard "Ham" Signal strength indicator. Calibrated in "S" units from 0-9 with scale terminating in +10 to +30 db calibrations. Additional full scale calibrations of 0-5 + 0-10 in linear scale divisions. A "must" for radio amateurs for conversion of any Communication Receivers with A.V.C. action to give calibrated signal strength action. 35/-


**DC MICROAMMETERS**  
 Model MR.25 0 to 50 uA 39/6  
 Model MR.250 0 to 500 uA. 32/6

**DC MILLIAMMETER**  
 Model MR.21 0 to 1mA. 27/6.  
 All models individually Boxed and Fully Guaranteed. P. & P. 2/6 each.

**VU METER MODEL VR. 1P.** Calibrated and damped in accordance with standard VU Meter Practice. Upper scale reads -20 to +3VU. Lower scale 0-100% modulation. Uses precision carbon film multiplier resistor and full wave rectifier. 42/6.
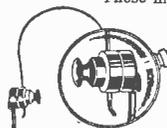
## HI-FI HEADPHONES

These miniature Hi-Fi phones use high quality permanent magnetic speakers with regulated voice coil.



The soft rubber ear moulds give correct spacing for optimum acoustic load. Each unit has a built-in miniature Hi-Fi transformer to ensure the finest music and voice reproduction. Supplied free is a small transformer unit which steps impedance up to 4000 ohms. Only 15/- P. & P. 2/6.

MAIL ORDERS TO  
 (DEPT. P.) 32a COPTIC STREET,  
 LONDON, W.C.1




CALLERS WELCOME AT  
 87 TOTTENHAM COURT ROAD,  
 LONDON, W.1 MUS 9606

**Speaker Bargain**

12in. Hi-fidelity loudspeaker. High flux, permanent magnet type with standard 3 ohm speech coil. Will handle up to 12 watts. Brand new by famous maker. Price 39/6, plus 3/6 post and insurance.

**Miniature Microphone**

American made. Dynamic type, real bargain at 2/6, plus 6d. postage.

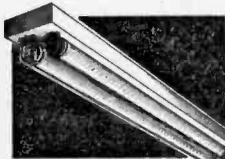**Fluorescent Lighting**

Complete lighting fittings. Built-in ballast and starters—stove enamelled white and ready to work. Ideal kitchen, workshop—anywhere.

**Twin 20** approximately 27in. long complete with two 20W tubes. 49/6.

**Single 40** approximately 4ft. long complete with one 40W tube. 39/6.

**Inductor 80** approximately 5ft. long complete with one 80W tube. 49/6. Carriage and insurance up to 150 miles 7/6, up to 250 miles 8/6.

**2 1/2in. Miniature** complete with 13 watt tube. Ideal for showcase or position where miniature fitting is required. Complete with latest fin. diameter tube. 49/6 each.

**Circular.** Complete with 40 watt tube. 44.19.6.

Carriage and ins. 7/6 any type.

**750mW TRANSISTOR AMPLIFIER**

4 transistors including two in push-pull input for crystal or magnetic microphone for pick-up—feed back loops—sensitivity 5 m/v—output 1 watt peak into 35 ohm speaker. Speakers available. Price 52/6. Postage and insurance 2/6.

**Building A Scope?**

3in. oscilloscope tube. American made type No. 3PP7, 6.3 v. 0.6 amp. heater, electrostatic deflection, brand new and guaranteed with circuit diagram of scope. 15/- each, plus 1/6 post and insurance.

**BATTERY CHARGER BARGAIN****Components Would Cost More**



Car Battery Charger—ready-made high output battery charger in stove enamelled sheet steel louvered case. New, complete and ready to work. Rated at 12 v. 5 amps. and variable rate selector for trickle charging, also a meter to show charging rate. Suitable for 230/250 A.C. mains. Special snip price of 65/-, plus 3/6 post and ins.

**MOTOR SNIP**


Miniature motor 2 1/2in. long x 1 1/2in. diameter, laminated poles and armature, separate windings for reversing. Operates off 20-30 v. D.C. or off A.C. mains through stepdown transformer. Original cost at least £3 each. Snip price for one month only 8/6, plus 1/6 postage and insurance.

**Component Storage Drawers**

Stout board construction these drawers are ideal for small parts. Suitable complete with simple erection instructions—1/6 each or 12 drawers each 6 x 2 1/2 x 6 1/2in. 18/6, post 2/-.

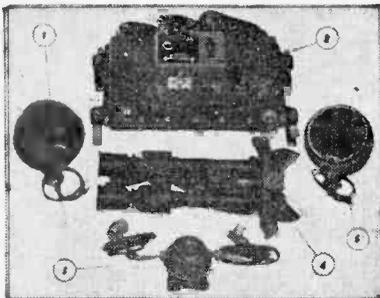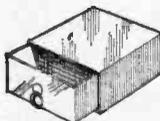**TABBY EQUIPMENT COMPLETE**


Complete equipment for seeing in the dark, as fitted to Army vehicles for night driving, etc. Complete working equipment comprises: 2 Infra Red Radiators, adjustable binoculars, power pack for 6 or 12 volts, control units and inter-connection cables. Original cost probably around £100. Unused and in perfect order—£6.19.6 or 10/- deposit and 15 fortnightly payments of 10/-.

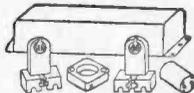**FLUORESCENT LIGHT BARGAIN**

Kit of Parts comprising: choke, two lamp holders, starter holder and starter. 40 watt, 19/6; 80 watt, 23/6. Plus 2/- post and insurance.

**INFRA-RED HEATERS**

Make up one of these latest type heaters ideal for bathroom, kitchen, bedroom, etc. They are simple to make from our easy to follow instructions—uses silica enclosed elements designed for the correct infra-red wavelength (3 microns). Price for 750 watt element and instructions 15/6, plus 2/6 post and insurance.

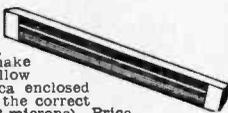**LIMITED QUANTITY ONLY!**

**Waterproof heater wire.** 16 yds. length. 70 watts. Self regulating temperature control. 10/-. Post Free.

**SUB-MINIATURE COMPONENTS**

1. Ferrite aerial with Long and Medium Wave Coils. 4 1/2in. long, for pocket superhet, complete with circuit showing component values, etc., 7/6.
2. Ferrite aerial, as above, but 1 1/2in. diameter, 3in. long, for table model receiver or portable. 10/6.
3. Three I.F. Transformers with oscillator coil and circuit details to work with item 1. 19/6.
4. Three I.F. Coils and oscillator to work with item 2. 23/6.
5. Smallest possible electrolytics. 1MFD, 2MFD, 5MFD, 50MFD, 8MFD, 10MFD, 20MFD, 30MFD, 50MFD, 100MFD, 200MFD, all 1/9 each.
6. Smallest 1 watt resistors, all 10 per cent values. 5d. each.
7. Miniature condensers, 1. 1/-; 0.5, .04, .02, .01, all 8d. values, below this 7d.
8. Miniature slide switch double pole change over, 2/6.
9. Edge-wise volume controls. 2K, 5K, 10K and 20K, 2/6 each.
10. Small edge-wise controls with switch, 2K, 5K, 10K and 20K, 4/9 each.
11. Red Spot Transistors, tested and suitable all A.F. applications, 2/6.
12. White Spot Transistors tested and suitable as I.F. or mixer, 3/6.
13. Set of six Mullard transistors for superhet in original packets, fully guaranteed, comprising OC44, OC45, OC81D and matched pair OC81. 22 the set.
14. Special 500 sub-miniature diodes, 1/6 each.
15. Surface Barrier transistors. 5-10 Mc/s, 6/8 each; 10-15 Mc/s, 8/- each; 20-30 Mc/s, 9/- each; 40-50 Mc/s, 15/- each.
16. Push-Pull Driver and Push-Pull output transformers for pocket superhets. 150 mW, 10/- pair; 400mW, 15/- pair; 750 mW (driver only, no o.t. needed), 8/6, all complete with circuit details.
17. Smallest Tuning Condenser, size approx. 1 1/2in. sq., 165pF and 85pF, with trimmers, 17/6 each.
18. Oscillator coil to suit the above. 6/-.
19. Three I.F.s, 455 k/c sub-miniature to suit items 17 and 18. 18/- the set.
20. Jackson 00 2-gang tuning condensers, 208pF plus 175 pm, spindle tapped 6BA, with trimmers. 10/6, less trimmers 9/6.
21. Tuning condensers for items 1 and 3. 9/6.
22. Tuning condensers for items 2 and 4. 10/6.
23. Printed circuit for items 1 and 3. 6/6.
24. Printed circuit for items 2 and 4. 7/6.
25. 2 1/2in. speaker, 3ohm. 19/6; 80 ohm. 19/6.
26. 3in. speaker, 3 ohm. 18/6; 80 ohm. 18/6.
27. 5in. speaker, 3 ohm. 18/6; 35 ohm Hi flux. 19/6; 35 ohm Super Hi flux. 22/6.
28. Elliptical speaker, 7 x 4. 3 ohm. 19/6; 35 ohm. 19/6.
29. Battery connectors, large. 1/- pair; miniature, 1/- pair.

**Connecting Wire**

P.V.C. covered in 100ft. coils—2/9 a coil or four coils different colours, 10/- post free.

## MULTI-METER BARGAINS!

**MODEL 200H** (illus. on right). 20,000 ohms per volt, 20 ranges comprising AC volts, 5 ranges up to 1,000V DC volts, 6 ranges up to 2.5KV, DC current, 3 ranges up to 28 ohms, resistance, 2 ranges up to 6 meg, capacity 2 ranges up to .1 decibels—20 to +22. Scale cornwise to the equivalent of 4in. movement is a pocket size instrument measuring 4 1/2 x 3 1/2 in. Complete with test prods, battery and operating instructions, price £6.19.3, post free.


**MODEL TE10**. Similar in size and appearance to 200H except that this is 10,000 ohms per volt and maximum DC volts 1,200 instead of 2.5K, also no capacity range. Price £5.19.6. Post free.



**MODEL TPS5**, (illus. on left). 20,000 ohms per volt, DC volts, 5 ranges up to 1,000 AC volts, 5 ranges up to 1,000, resistance, 2 ranges up to 10 meg., capacity 2 ranges up to .1 decibels—20 to +26. One switch control, really beautifully made precision instrument, size only 3 1/2 x 5 1/2 in., price only £5.19.6. Post free.

**MODEL TP10**. Similar in size and appearance to TPS5, but sensitivity 2,000 ohms per volt, price £3.19.6. Post free.

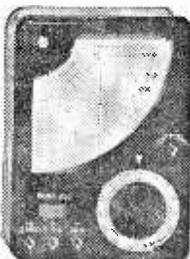**MODEL UI**. A robust instrument of 1,000 ohms per volt sensitivity, AC/DC volts up to 1,000. DC current up to 500, resistance up to 200K, size 5 1/2 x 3 1/2 x 2 1/2 ins. complete with test prods, single switch control, large easily read scale, price only £2.19.6. Post free.




## MOST AMAZING BARGAIN!

All components for a  
**5 Transistor Radio**  
that really works!

ONLY  
**69/6**

Postage and insurance 2/6  
Battery 2/-

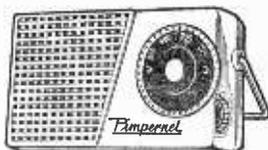

This remarkable little receiver uses 5 transistors and 2 diodes, 3in. Moving Coil Speaker, Tuning Condenser, Volume Control with On/Off switch, latest type circuitry giving excellent station separation and ample volume at good tone. Push-pull output circuit ensures long life from PP4 battery.

All components included for Medium Wave operation in handsome plastic case with carrying handle as illustrated.

**Demonstrations at all branches**


Circuit diagram FREE with parts or 2/- separately.

### OPTIONAL EXTRAS


Fully punched printed circuit board .. .. 6/6  
All components and switch for Long Waves .. .. 8/6  
Motif "Pimpernel" .. .. .. 2/-
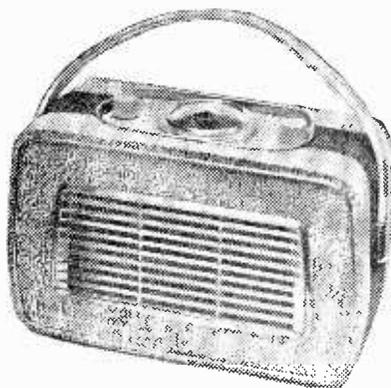
## A proved success . . . The "GOOD COMPANION" CAR RADIO & PORTABLE

One of the finest of its kind available. The design is the combined efforts of our technicians and of those of several of the leading manufacturers in the country, and the resulting set has a performance as good as if not superior to those selling at £20 and more. It has the eight transistor set performance.



Alternative Cabinet 20/- extra.

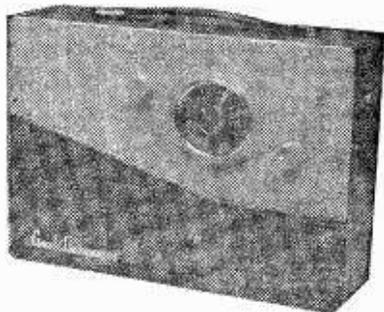

Features include American Philco R.F. transistors and Mullard A.F. transistors—Q.P.P. output giving 750 mW—full coverage on Medium and Long—very fine tuning arrangement—excellent reception of difficult stations like 208—variable feed-back control—full tonal qualities—really superior looking cabinet size 11 x 8 x 3in. approximately—car aerial attachment—several months' operation from battery costing only 3/6.

Circuit employs six transistors and two diodes, it incorporates all latest refinements, and oscillator I.F. Transformers are pre-aligned so no instruments are necessary. Anyone who can solder competently can make this set. The instructions are fully comprehensive with plenty of illustrations. Service is available in the unlikely event of your getting into difficulties. All components fully guaranteed. Price of all components and cabinet to make set as illustrated

**£9.19.6**

Post and insurance 5/-  
Battery 3/6 extra.

### POCKET COMPANION

should now be ready for constructors. Constructional details 2/6, or all parts complete

**£6.15.0** Post & Insurance 2/6.

## ELECTRONIC PRECISION EQUIPMENT LTD.

post orders are dealt with from Eastbourne, so for prompt attention please post your orders to 66 Grove Road, Eastbourne, marked Department 7. Callers may use any one of the Companies below.

266 London Road,  
Croydon.  
Phone: CRO 6558  
Half day Wednesday

29 Stroud Green Rd.,  
Finchley Park, N.4.  
Phone: ARChway 1049  
Half day Thursday

520 High Street North  
Manor Park, E.12.  
Phone: ILFord 1011  
Half day Thursday

42-46 Windmill Hill,  
Ruislip, Middx.  
Phone: RUislip 5780  
Half day Wednesday

246 High Street,  
Harlesden, N.W.10.  
Phone: ELGar 4444  
Half day Thursday

Brand new, individually checked and guaranteed

**VALVES**

ACSPENDD	EAC91	4/6	EL91	7/6	
AL60	4/-	EB34	1/6	EM80	8/-
AP4	4/-	EB91	3/9	EN31	22/6
ARR8	5/-	EBC21	8/-	EP72	5/6
ARDD5	2/-	EBC90	5/-	ESU208	8/-
ARP3	4/-	EBC91	3/9	EY51	8/-
ARPA	3/6	EC52	8/-	EY86	8/-
ARP12	2/9	EC90	10/-	EY91	3/6
ARP21	4/6	EC90	10/-	EZ40	7/-
ARP24	4/6	ECC81	5/6	EZ41	6/9
ARP34	5/6	ECC82	6/6	EZ80	6/6
ARTH2	7/-	ECC83	7/-	EZ81	6/9
ATP4	2/9	ECC84	7/-	GL450	10/-
AU1	5/-	ECC85	7/9	GL464A	10/-
AU4	5/-	ECC91	4/-	GZ32	9/-
AVW4	4/-	ECH82	8/6	HL23	8/-
AZ31	8/-	ECH42	7/6	HL23DD	8/-
BL63	6/-	ECH81	7/9	HVR2	12/6
BS4A	5/6	ECL80	8/-	KF35	5/-
BT45	40/-	ECL82	9/-	KRN2A	19/-
BT83	22/6	EF22	7/3	KT31	8/-
BT98	25/-	EF32	5/-	KT32	8/-
CV54	5/-	EF36	3/6	KT33C	4/9
CV264	35/-	EF37A	8/-	KT44	6/3
CY31	7/6	EF39	4/3	KTW62	7/6
D41	3/3	EF50	2/6	KTW63	6/6
D77	4/3	EF54	3/3	MH4	4/6
DA30	12/6	EF55	6/-	MH41	5/-
DAF86	8/-	EF70	4/-	ML4	4/-
DAF91	6/-	EF73	6/-	ML6	6/-
DETS	15/-	EF80	5/6	MS/PEN	6/-
DF72	7/6	EF85	6/10	NJ37	6/-
DF91	3/3	EF86	9/-	(4033A)	10/-
DK96	7/3	EF89	7/9	NU12	5/-
DF96	8/-	EF91	3/6	OB3	7/-
DL92	6/-	EF92	4/6	OC3	5/-
DL94	6/-	EF95	7/6	OD3	5/-
DL96	8/-	EK32	7/-	OZ4	5/-
DX25	9/-	EL32	3/9	PCC84	7/-
E1232	5/6	EL33	8/-	PCC85	8/3
E1323	25/-	EL35	8/3	PCF80	7/-
E1436	3/6	EL41	8/3	PCF82	8/-
E1524	6/6	EL42	9/-	PCL82	8/6
EA50	1/6	EL84	7/6	PEN25	4/6
EABC80	7/3	EL85	10/-	PEN46	5/-

PEN65	6/6	UL85	7/-	6AB7	4/-
PEN220A	3/-	UU9	5/6	6AC7	3/-
PENDD/		UY41	6/-	6AG5	3/6
1360	9/6	UY85	6/6	6AG7	6/-
PL81	9/-	VP23	3/6	6AJ7	4/3
PL82	8/-	VP41	5/6	6AK5	5/-
PL83	7/9	VR78	4/-	6AK7	8/-
PT15	10/-	VR99	8/-	6AM6	6/3
PT25H	7/6	VR105/307/6	6AT6	5/-	
PVD7	7/6	VR150/307/3	6AQ5	7/-	
PX4	19/-	VT4C	25/-	6BA6	6/-
PX25	10/3	VU39	6/-	6BB	5/6
PY83	7/3	VU111	3/3	6BBG	2/6
PY80	6/9	VX3138	12/-	6C4	3/6
PY81	7/-	W31	7/-	6C5	6/-
PY82	8/-	Y63	5/-	6C6G	4/3
QP21	6/-	Y66	8/-	6C8G	5/-
QP25	5/3	Z31	6/-	6D6	4/6
QS75	20	IA3	3/-	6F6	7/6
QS95	10	IA5GT	5/-	6F6G	4/6
QS108/456/9	ICSGT	7/6	6F8G	6/6	
QV04/7	12/6	ID8GT	6/-	6F12	4/6
QV05-25	5/-	IE7G	7/6	6F17	7/6
R3	8/-	IG6GT	12/-	6G6G	3/-
R3/10	4/-	ILD5	3/6	6H6M	2/-
R10	12/6	ILN5	4/9	6J5	3/6
REL21	25/-	IR5	6/-	6J5G	3/-
RK34	2/6	IS5	5/9	6J6	4/3
RX235	10/-	IT4	4/-	6J7G	5/-
SP2	4/-	IW4	6/-	6K6GT	2/6
SP13C	4/6	2A3	8/-	6K7G	2/3
SP41	2/6	2A5	8/-	6K7GT	4/9
SP61	2/-	2A6	7/-	6K8G	5/9
STV280/80		2034	2/6	6K8GT	8/3
		2D21	6/-	6K8M	6/-
		2D4A	4/-	6L5G	6/-
SU2150A	4/9	2X2	4/-	6L6	6/6
T41	7/-	3A4	5/-	6L6G	9/6
T41	8/-	3A4	5/-	6L3A	4/6
TP25	15/-	3B7	5/-	6N7G	5/9
TT11	3/-	3B2A	8/-	6N7GT	6/-
TZ20	16/-	3E89		6Q7G	6/-
U17	5/-	(889B)	60/-	6R7	8/-
U18	5/-	3Q5GT	9/-	6S47	6/-
U27	8/-	3S4	5/-	6SC7G	5/6
U52	5/-	3V4	6/-	6SG7	5/-
UBC41	7/6	5T4	9/-	6SG7GT	6/-
UCH42	7/6	5U4G	5/-	6SH7	5/-
UL11	5/-	5V4G	8/-	6SH	5/-
UL12	5/-	5Y3GT	6/-	6SH7	4/6
UL41	7/-	5Z3	8/6	6S17GT	5/9
UL84	7/6	5Z4G	8/-	6SK7	5/3

6SL7GT	6/6	38	4/-	6064	10/-
6SN7GT	4/6	58	6/-	7193	1/9
6SQ7	6/-	59	6/-	6475	5/-
6S57	6/-	57	8/-	8013A	25/-
6V6G	5/6	76	5/-	8020	6/-
6V6GT	6/-	77	6/-	9001	4/6
6X4	5/7	78	7/-	9002	5/6
6X5GT	6/6	80	6/3	9003	6/-
6Y6G	6/-	81	80	9004	4/-
		81	8/3	9006	4/-
		82	8/4		
		83	12/-		
		84	8/-		
		85A3	15/-		
		7C7	7/-		
		7D7	6/6		
		7H7	7/3		
		7Q7	7/-		
		7V7	5/-		
		7Y4	6/-		
		7Z4	6/6		
		8D2	2/6		
		9D2	3/-		
		12A6	5/-		
		12AH7	7/-		
		12A7H	5/6		
		12AU6	9/-		
		12AU7	6/-		
		12AX7	7/-		
		12CB	3/-		
		12E1	22/6		
		12H6	2/-		
		12J5GT	6/6		
		12K7GT	4/6		
		12K8M	9/3		
		12SA7	7/6		
		12SC7	4/6		
		12SG7	6/6		
		12SH7	3/-		
		12S7	6/-		
		12SK7	4/-		
		12SL7	7/-		
		12SN7	8/-		
		12Q7GT	4/6		
		12SR7	6/-		
		15D2	6/-		
		15R	5/-		
		20A2	7/6		
		21B6	9/-		
		30	5/-		
		35L6GT	8/-		
		35T	30/-		
		35Z4GT	7/-		
		37	4/-		
		807AMER	6/-		
		807BR	5/-		
		808	8/-		
		813	6/16		
		815	40/-		
		816	30/-		
		826	10/-		
		829A	30/-		
		832A	15/-		
		832A	35/-		
		843	7/6		
		866A	12/6		
		920A	35/-		
		973A	6/-		
		954	2/-		
		956	2/-		
		958A	5/-		
		1616	3/-		
		1629	5/-		
		1626	4/6		
		1629	4/6		
		4120	4/-		
		807AMER	6/-		
		807BR	5/-		
		808	8/-		
		813	6/16		
		815	40/-		
		816	30/-		
		826	10/-		
		829A	30/-		
		832A	15/-		
		832A	35/-		
		843	7/6		
		866A	12/6		
		920A	35/-		
		973A	6/-		
		954	2/-		
		956	2/-		
		958A	5/-		
		1616	3/-		
		1629	5/-		
		1626	4/6		
		1629	4/6		
		4120	4/-		
		807AMER	6/-		
		807BR	5/-		
		808	8/-		
		813	6/16		
		815	40/-		
		816	30/-		
		826	10/-		
		829A	30/-		
		832A	15/-		
		832A	35/-		
		843	7/6		
		866A	12/6		
		920A	35/-		
		973A	6/-		
		954	2/-		
		956	2/-		
		958A	5/-		
		1616	3/-		
		1629	5/-		
		1626	4/6		
		1629	4/6		
		4120	4/-		

AND MANY OTHERS IN STOCK, INCLUDING CATHODE RAY TUBES AND SPECIAL VALVES. All U.K. Orders below 10/-, 2/- P. & P. 2/6 over 10/-. Orders over £3, P. & P. free. C.O.D. 2/6 extra Overseas Postage extra at cost.

**FREQUENCY METRE BC221 TECHNICAL MANUAL 22/6.**

**FIELD TELEPHONE TYPE "L"**  
Excellent guaranteed condition, £5.50 per pair, carriage paid.

**B.P.5 TRANSRECEIVERS.** Specially built for Parachutists during the war. Receiver superhet Transmitter crystal controlled. C.W., and phone. 2-8 Mc/s. 829 valve as output. 60 w. on C.W. 15 w. on microphone together with mains power pack 120/220 v. Two rotary converters to work from 12 v. battery, microphone, key and dipole aerial. Price £15. Carriage 30/-.

**RECEIVER TYPE BC342.** 110 v. A.C. 1.5-18 Mc/s. £22.10.0, carriage 30/-.

**RECEIVER TYPE BC312.** As above but 12 volt battery. £22.10.0, carriage 30/-.

**R109 RECEIVER.** Covering 2-8 Mc/s 6 v. D.C. with set of spare valves and carrier. Brand new in original packing case, £6.18.0, including delivery in U.K.

**VIBRATOR UNIT.** 12 v./160 v. 35 mA. Exceedingly well filtered

**TRANSISTORISED**

**PRINTED CIRCUIT**


# **P.W. POCKET SET**

Modified boosted version

**NEW ATTRACTIVE CONTEMPORARY CASE**

**WITH BUILT-IN DIAL ASSEMBLY**

(Illustration free on request)

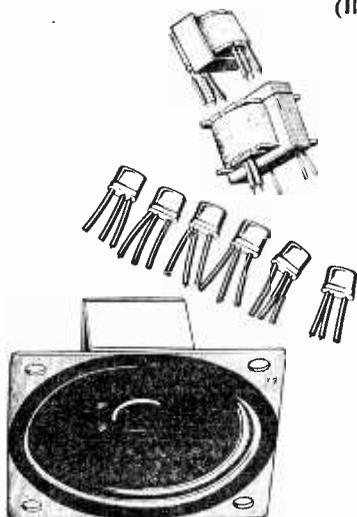

## **ALL GUARANTEED COMPONENTS**

INCLUDING:—

**Specially designed push-pull transformers**

**HIGH Q OSMOR SUBMINIATURE COILS**

**EFFICIENT FERRITE ROD AERIAL**

**Six transistors selected and recommended  
by makers specially for OSMOR matched speaker**

**Sub-miniature resistors and capacitors**

**Printed circuit board ensuring easy construction**

**Blown-up diagram of printed board to double check**

## **ALIGNMENT & FAULT-FINDING SERVICE**

DETAILS ON REQUEST


**A-Z CONSTRUCTIONAL BOOKLET**  
**1/6 EACH**

*from your usual Dealer or Direct*

**Osmor**

**418 BRIGHTON ROAD, SOUTH CROYDON. CRO 5148/9**

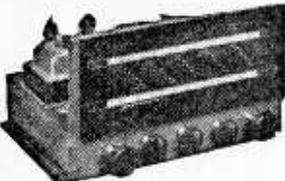**ARMSTRONG AF208 AM/FM RADIOGRAM CHASSIS**



★ Full VHF Band (87-108 Mc/s) and Medium Band, 187-570M) ★ 7 Valves ★ 5 Watts Output ★ 15db Negative Feedback ★ Separate wide range Bass and Treble Controls ★ 2 Compensated Pick-up Inputs ★ Frequency Response 30-22,000 C.P.S. ★ 2db ★ Tape Record and Playback Facilities ★ Continental Reception of Good Programme Value ★ For 3, 7½ and 15 ohm speakers. Send S.A.E. for leaflet.

PRICE 22 GUINEAS **Carr. Free**

**LATEST "E.M.I." 4 SPEED SINGLE RECORD PLAYER**

Acops Hi-Fi Pick-up for LP, and/or 78, 7, 10 and 12in. records. Silent motor, heavy turntable, auto stop.

Special offer **£6.5.0** post free. Stereo/Monaural **£8.10.6**

**SINGLE-PLAYER BARGAIN**

Ready-built, complete with BSR TU9 4-speed gram pick-up unit. Handsome portable case. 3-watt amplifier with 2 valves and speaker. List price £12.10.0. OUR PRICE **£9.9.0**. Post 4/- Fully guaranteed in manufacturer's sealed cartons.

**New Boxed Valves 90-day Guarantee**

1R5	7/6	6K80	7/6	EA50	1/8	EB20	7/6
1R5	7/6	6L90	10/6	EA80	8/6	EL18	1/6
1T4	6/-	6NTM	6/6	EB30	6/-	HAB30	6/6
2X3	3/6	6Q70	8/6	EB33	8/6		12/6
3V4	7/6	6SA7	6/-	EB41	8/6	HVR2A	6/6
384	7/6	6M7M	6/6	EBF80	10/-	MU14	9/-
5U4	7/6	6SN7	6/6	EC34	8/6	PC34	8/6
5Y3	7/6	6V93	6/6	ECF90	8/6	PCF90	8/6
5Z4	9/6	6X4	7/6	ECH42	10/6	PC182	11/6
6AM6	5/-	6X5	8/6	ECL80	10/6	PCN25	6/6
6B5	5/-	12A6	7/6	ECL82	10/6	PL81	12/6
6B96	7/6	12AT7	8/-	EP30	5/6	PL32	10/6
6B96	9/6	12AX7	8/-	EP41	9/6	PY80	7/6
6B96	9/6	12AX7	8/-	EP50	5/6	PY81	9/6
6D8	6/-	12BE6	8/6	EP80	8/-	PY82	7/6
6F5	7/6	12K7	6/6	EP86	12/6	SP61	3/6
6H6	3/6	12Q7	6/6	EP92	5/6	UBC41	9/6
6J5	5/6	35L6	9/6	EL33	5/6	UC142	9/6
6J6	5/6	35Z4	7/6	EL11	9/6	UF41	9/6
6J70	6/6	50	9/6	EL34	3/6	UL41	9/6
6K6GT	6/6	807	5/6	EY61	9/6	UY41	8/-
6K7G	5/-	194	1/6	EZ40	7/6	UZ2	8/-

DK96, DF96, DAF96, DL96, 8/6 each or 30/- set.

NEW ELECTROLYTICS		FAMOUS CAN TYPES	
TUBULAR	TUBULAR		
1/350V	2/-	50/350V	5/6
2/350V	2/3	100/25V	3/-
4/450V	2/3	250/25V	3/-
8/450V	2/3	500/12V	3/-
6/500V	2/3	8 + 8/450V	8/6
16/450V	3/-	8 + 8/500V	5/-
16/500V	4/-	8 + 16/450V	3/9
22/450V	3/9	8 + 16/500V	5/6
25/25V	1/10	16 + 16/450V	4/5
50/25V	2/-	16 + 16/500V	6/-
50/50V	2/-	32 + 120/250V	11/6
50/50V	2/-	32 + 22/250V	4/6

**C.R.T. BOOSTER TRANSFORMERS**

For Cathode Ray Tubes having heater cathode short circuit and for C.R. Tubes with falling emission. Full instructions supplied.

Type A. Optional 25% and 50% Boost. 2V or 4V or 6.3V or 10.8V or 13.3V. Mains input. 12/6

Type A2. High quality, low capacity. 10/15pF. Optional boost 25%, 50%, 75%. Mains input. 16/6

Type B. Mains input. Low capacity. Multi output 2, 4, 6.3, 10 and 13V. Boost 25% and 50%. This transformer is suitable for all TV tubes. £1/- each.

**COMPLETE RADIO £4.19.6 post free**



4 Mullard valves, 5in. speakers, frame aerial, 4 pre-set stations. 1 long, 3 med. wave. Superhet Circuit. Size 9 x 6 x 5 1/2 in. High. Tested ready for use. 200/250 v. A.C.—D.C. Mains.

Post 2/- each.

<b>MAINS TRANSFORMERS 200/250 v. A.C. STANDARD.</b>	
250-0-250, 80 mA, 6.3 v. 3.5 a.	29/6
tapped 4 v. 4 a. Rectifier 1.3 v. 1 a. 5 v. 2 a. or 4 v. 2 a., 22/6; ditto, 350-0-350	10/6
MINIATURE 200 v. 20 mA, 6.3 v. 1 a.	15/6
MIDGET, 220 v. 45 mA, 6.3 v. 2 a.	17/6
SMALL, 220-0-220, 50 mA, 6.3 v. 2 a.	17/6
STD., 250-0-250, 85 mA, 6.3 v. 3.5 a.	7/6
HEATER TRANS, 6.3 v. 1 1/2 amp.	10/6
Ditto, tapped sec. 2, 4, 6.3 v., 1 1/2 amp.	10/6
Ditto, sec. 6.3 v. 3 amp.	10/6
<b>GENERAL PURPOSE LOW VOLTAGE, Ea.</b>	
3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24, 30 v.	22/6
AUTO TRANS. 0110, 240 v. 150 w.	22/6
Ditto, 500 w.	22/6

O.P. TRANSFORMERS. Heavy Duty 50 mA, 4/6. Multiratio, push-pull, 7/6. Ditto, 10 w., 15/6. Miniature, 384m etc., 4/6. L.F. CHOKES 15/10E, 60/95 mA, 5/-; 10 H. 85 mA, 10/6; 10 H. 180 mA, 14/-.

**TELEVISION REPLACEMENT Line Output Transformers from 45/- each, New Stock**

and other timebase components. Most makes available. S.A.E. with all enquiries.

FULL WAVE BRIDGE SELENIUM RECTIFIER: 2, 4 or 12 v. 1 1/2 amp. 9/6; 2 a., 11/3; 4 a., 17/6. CHARGER TRANSFORMERS. Tapped input 200/250 v. for charging at 2, 6 or 12 v., 1 1/2 amps., 15/6. 2 amps., 17/6; 4 amps., 22/6. Circuit included. 4 AMP CAR BATTERY CHARGER with amp meter Leads, Fuse Case, etc., for 6 v. or 12 v., 69/6.

**BOOKS**

40 Circuits for Germanium Diodes 3/- "W.W." Radio Valve Data, 6/- High Fidelity Speaker Enclosure, 5/- Valve and TV Tube Equivalents, 9/6 TV Fault Finding, 5/- Quality Amplifiers, 4/6 Radio Valve Guide. Books 1, 2, 3 or 4, 5/- each. Transistor Superhet Receivers, 7/6.

**CRYSTAL MIKE INSERT by ACOS 9/6**  
Precision engineered. Size only 1 1/2 in. dia. x 1 1/2 in.  
ACOS CRYSTAL MIKE 40 .. 25/-  
DE LUXE STICK MIKE .. 35/-

LOUDSPEAKER F.M. 8 OHM, 2 1/2, 3, 4in. 19/6, 5in. Rois, 17/6; 5in. Plessey, 19/6, 7in. x 4in. Plessey, 19/-; 6in. Rois, 18/6, 10 x 6in. 27/6, 10in. Rois, 30/-; 4in. Treeter, 25/-; 12in. EA. 30/-; 1 1/2 x 8in. 45/-; STENTORIAN HF1012. 10in. 3-15 ohms, 10 w., 95/-

**BAKER SELHURST LOUDSPEAKERS**

12in. Baker 15w. Stalwart 3 or 15 ohms, 45-13,000 c.p.s. .. 10m  
12in. Baker ditto, foam suspension, 15 ohms, 40-13,000 c.p.s. .. 26  
12in. Stereo, 15 w., 25-15,000 c.p.s. .. 28  
12in. Baker Ultra Treble, 20 c.p.s. to 25 kofa. £17.10  
15in. Bass Auditorium Mk.II, 25 w. .. 51s



CRYSTAL DIODE G.E.C. 2/- GEX34, 4/- HIGH RESISTANCE PHONES, 4,000 ohms, 15/- pr. MIKE TRANSF. 50: 1, 3/9 ea.; 100: 1, Posted, 10/6. SWITCH CLEANER. Fluid squirt spot, 4/8 tin. TWIN GANG TUNING CONDENSERS. 365 pF. miniature lin. x 1 1/2 in. x 1 1/2 in., 10/-, 500pF Standard with trimmers, 9/-; midget, 7/6; with trimmer, 9/- SINGLE, 50 pF 2/6; 75 pF, 100 pF, 150 pF, 5/6. Solid dielectric 100, 500 pF, 8/6. CONDENSERS. New Stock. 0.001 mfd. 7 kV. T.C.C., 5/6; Ditto, 10 kV., 9/6; 0.1 mfd. 7 kV., 9/6. Tubiar 500 v. 0.001 to 0.05 mfd., 9d., 0.1, 1/- 0.25, 1/8; 0.5/500 v., 1/8; 0.1/350 v., 9d.; 0.01/2,000 v. 0.1/1,000 v., 1/8; 0.1 mfd., 2,000 volts, 3/6. CERAMIC COND., 500 v., 0.5 pF to 0.1 mfd. ad. SILVER MICA CONDENSERS. 10w. 5 pF to 500 pF, 1/-; 500 pF to 3,000 pF, 1/8. Close tolerance. (± 1 pF) 1.5 pF to 47 pF, 1/8. Ditto 1% 50 pF to 815 pF, 1/8; 1,000 pF to 5,000 pF, 2/-.

465 kc/s SIGNAL GENERATOR Total cost 15/- Uses B.F.O. Unit. ZA 30038 ready made. POCKET SIZE 2 1/2 x 4 1/2 in. Slight modifications required (full instructions supplied). Battery 7/6 extra 80V +14V. Details S.A.E.

Wavechange Switches. 2 p. 2-way. 3 p. 2-way, short spindle, 2/6; 5 p. 4-way. 2 wafers, long spindle, 6/6; 2 p. 6-way. 4 p. 2-way, 4 p. 3-way, long spindle, 3/6; 6 p. 4-way, 1 p. 2-way, long spindle, 3/6

Wavechange "MAKITS". Wafers available: 1 p. 12 wafers, 2 p. 6 wafers, 3 p. 4 wafers, 4 p. 3 wafers, 5 p. 2 wafers, 1 wafers, 8/6; 2 wafers, 12/6; 3 wafers, 16/6; additional wafers up to 14, 3/6 each extra.

Toggle Switches, s.p., 2/-; d.p., 3/6; d.p.d.t., 4/-.

JASON FM TUNER COIL SET, 25/- H.F. coil, aerial coil, oscillator coil, two i.f. transformers 10.7 Mc/s, detector transformer and heater choke. Circuit and component book using four 6AM6, 2/6. Complete Jason FM.T.I. Kit. Jason chassis with calibrated dial, components and 4 valves. £6.5.0.

Valveholders. Pax. int. oct., 4d. EA50. 6d. B12A, CRT, 1/3, Eng. and Amer. 4, 5, 6, and 7 pin. 1/- MOULDED Magda and int. oct., 6d.; B7C, EA, E8G, B9A, 9d. B7C with can, 1/8. B9A with can, 1/8. Ceramic, EF50, B7G, B9A, int. oct., 1/- B7G, B9A caps, 1/- each.

**"A MERRY CHRISTMAS TO ALL"**

**RADIO COMPONENT**

Our written guarantee with every purchase. Bus 133 or 68 pass door S.R. Station Selhurst

**Volume Controls** 80 ohm CABLE COAX  
Semi-air spaced tin. Stranded core. 6d. yd.  
40 yds. 17/8.  
50 yds. 25/-  
D.P. Sw. 3/-  
4/6  
Fringe quality 1/- yd.  
Air Spaced.

**TRIPLEXERS** Bands I, II, III .. 12/6  
**COAX PLUG** 1/- **LEAD SOCKET** 2/-  
**PANEL SOCKETS** 1/- **OUTLET BOXES** 4/8  
**BALANCED TWIN FEEDER** yd. 8d. 80 or 300 ohms.  
**DITTO SCREENED** per yd. 1/6. 80 ohms only.  
**WIRE-WOUND POTS, 3 WATT.** Pre-set Min. TV Type. All values 10 ohms to 25 K. 3/- ca. 30 K., 50 K., 4/- (Carbon 30 K., to 2 meg., 3/-).  
**WIRE-WOUND 4 WATT Pots.** Long spindle. Values, 50 ohms to 50 K.; 6/8; 100 K.; 7/6.

**TRIMMERS.** Ceramic. 80, 50, 70 pF., 9d.; 100 pF., 150 pF., 1/3; 250 pF., 1/6; 500 pF., 75d. pF., 1/9.  
**RESISTORS.** Preferred values. 10 ohms to 10 meg., 1 w., 4d.; 1/2 w., 4d.; 1 w., 8d.; 1 1/2 w., 8d.; 2 w., 1/-.  
**HIGH STABILITY.** 1 w., 1/6; 2 w., 2/-. Preferred values. 10  $\Omega$  to 10 meg. Ditto 5% 100  $\Omega$  to 5 meg., 9d.  
5 watt **WIRE-WOUND RESISTORS** 1/3  
10 watt 25 ohms-10,000 ohms 2/-  
15 watt 100 ohms-10,000 ohms 1/6  
12.5K to 50K 10w .. .. . 3/-

**AMERICAN "BRAND FIVE" PLASTIC RECORDING TAPE**

Double Play 7in. reel, 2,400ft	60/-	Spare Plastic Reels	1/8
5in. reel, 1,200ft	37/6	4in. 2 1/2	2/-
Long Play 7in. reel, 1,800ft	35/-	5in. 2 1/2	2/-
5in. reel, 1,200ft	23/6	5in. 2 1/2	2/-
5in. reel, 900ft	19/6	7in. 2 1/2	6/-
Standard 7in. reel, 1,200ft	25/-		
5in. reel, 600ft	16/-		

"Instant" Bulk Tape Eraser and Head Detuxer, 200/250 v. A.C. 27/6. Leaflet, S.A.E.

Neon Mains Tester Screwdriver, 5/-  
Solder Radlograde, 4d. yd., 1lb. 5/-  
Black Crackle Paint. Air drying, 3/- tin.

**HIGH GAIN TV PRE-AMPLIFIERS BAND I H.C.**  
Tunable channels 1 to 5. Gain 18db. ECC84 valve. Kit price 29/6 or 49/6 with power cable. Details 6d. (ECC84 valves if preferred.)  
**BAND III L.C.A.**—Same prices. Tunable channels 8 to 13. Gain 17db.

Faxolin Panels, 10 x 8in., 1/6.  
Miniature Contact Cooled Rectifiers. 250V 50mA, 7/8; 250V 80mA, 8/8; 250V 85mA, 9/8; 300mA, 21/-; 300mA, 27/6.  
Selenium Rect. 300V 85mA, 7/6.  
Coils. Wairite "P" type, 3/- each. Osrom Midret "Q" type, adj. dust core, from 4/- each. All ranges.  
Teleton D.W.R. L. and Med. T.R.F. with reaction, 3/6.  
Ferrite Rod Aerials. M.W., 8/9; M. and L., 12/6.  
Osrom Ferrite Rod Aerials. L. and M. for transistor circuits, 10/- each.  
Ferrite Rods, 8 x 1in., 2/6.  
H.F. Chokes, 2/6.  
T.R.F. Coils, A/HF, 7/- pair; HAX, 3/- DRR2, 4/-.

Aluminium Chassis, 18 s.w.g. Plain, undrilled, 4 sides, riveted corners, lattice fixing holes, 2 1/2in. sides, 7 x 4in., 4/6; 9 x 7in., 5/9; 11 x 7in., 6/9; 13 x 9in., 8/6; 14 x 11in., 10/6; 15 x 14in., 12/6; 18 x 15 x 3in., 16/6.  
Aluminium Panels, 18 s.w.g., 12 x 12in., 4/8; 14 x 9in., 4/-; 12 x 9in., 3/-; 10 x 7in., 2/8.

**AUTOCHANGER ACCESSORIES**  
Suitable player cabinets (except 4 H.F.) .. 49/6  
Amplifier player cabinets (except 4 H.F.) .. 63/-  
2-valve amplifier and 6in. speaker 35/-  
3-valve amplifier and 6in. speaker 105/-  
Wired and tested ready for use with above.

**QUALITY 2-STAGE HI-FI AMPLIFIER.** A.C. only 200-250V. Valves ECL82 and EZ80. 3 watt quality output. Mullard tone circuits, bass boost, treble and volume controls. Separate engraved Perspex front-panel with deluxe finish. Heavy duty output transformer 3 ohm. Shrouded mains transformer. Stove enamelled chassis size 6 x 5 x 3in. Bargain price £41.00. Circuit supplied.

**JACKS.** English open circuit, 2/6. Closed circuit, 4/3. Grundig type, 3 pin, 1/3.  
**JACK PLUGS.** English, 3/-; Grundig, 3 pin, 3/6.  
**Wirewound Ext. Speaker Control, 100, 3/-.**

**ALADDIN FORMERS** and cores. 1in., 8d.; 2in., 10d.  
**0.3in. FORMERS** 5837 or 8 and cans TV1 or 2, tin. sq. x 2in. or tin. sq. x 1 1/2in., 2/- with cores.

**SLOW MOTION DRIVES.** Epicyclic ratio 6-1, 2, 3.  
**SOLENOID IRON.** 25W, 200V or 230V, 24/-.  
**MAINS DROPPER.** 3 x 1 1/2in. With adjustable sliders. 0.3A, 1,000 ohms, 4/3; 0.2A, 1,000 ohms, 4/3.  
**LINE CORD.** 0.3A 60 ohms per foot, 0.2A 100 ohms per foot, 2-way, 1/- per foot; 3-way 1 1/2 per foot.  
**MIKE TRANS.** 50-1, 3/9; 100:1, potted, 10/6  
H.C. Coils, AWire, 3 colours, single or stranded, 2d. yd. Sleeveings, 1.2mm, 2d.; 4mm, 3d.; 6mm, 5d. yd.  
Speaker Fret. Gold cloth, 17 x 25in., 5/-; 25 x 35in., 10/-; Tygan, 52in. wide, 10/-; 26in. wide, 5/- ft. Samples, S.A.E.  
Expanded Metal, Gold, 12 x 12in., 6/-.

**I.F. TRANSFORMERS 7/6 pair**  
465 kc/s tuning miniature can 1 1/2 x 1/2 x 1/4in. High Q and good band width. Data sheet supplied.

**"REGENT" 4 VALVE**

"96" RANGE VALVES KIT PRICE £6. 6. 0. carr. 4/-



**PRINTED CIRCUIT BATTERY PORTABLE KIT**

Medium and long wave. Powerful 7 x 4in. high Flux Speaker. T.C.C. Printed Circuit and condensers. Components of finest quality clearly identified with assembly instructions. Osrom Ferrite Aerial Coils. Rexine covered attache case cabinet. Size 12in. x 8in. x 4in. Batteries used B126 (L5512) and AD35 (L5040), 10/- extra. Instructions 9d. (free with kit). Mains Unit ready made for above 39/6. Sold separately. Details free.

**MONARCH RECORD PLAYER**



**BUILD IT YOURSELF** using 4-SPEED BSR MONARCH AUTOCHANGER  
READY BUILT 3W. AMPLIFIER, HANDSOME PORTABLE CASE, HIGH FLUX LOUD-SPEAKER. FULL INSTRUCTIONS SUPPLIED.  
Total Price **£12.10.0**  
Carr. and ins. 5/-.

**RECORD PLAYER BARGAINS**  
Post 2/- each.  
4 Speed Autochangers:  
4 Speed U.A.14 .. .. . 27.10.0  
Collaro Autochanger .. .. . 27.19.8  
Garrard "Slimline" .. .. . 23.17.6  
Garrard RC209 .. .. . 29. 9.0  
Garrard RC210 .. .. . 29.10.0  
4 speed Single Players:  
Garrard TA Mk. II .. .. . 28. 8.0  
Model 45P .. .. . 26.17.6  
Garrard 4 HF Transcription 27.19.8  
Garrard Stereo Heads 2 extra.  
All Sapphire Stylus available from 6/-.

**ARDENTE TRANSISTOR TRANSFORMERS**

Type D3035, 7.3 CT: Push Pull to 3 ohms for OC72, etc., 1 x 1 x 1in., 9/6.  
Type D3034, 1.75: 1 CT, Push Pull Driver for OC72, etc., 1 x 1 x 1in., 9/6.  
Type D3058, 11.5:1 Output to 3 ohms for OC72, etc., 1 x 1 x 1in., 9/6.  
Type D167, 18.2:1 Output to 3 ohms for OC72, etc., 1 x 1 x 1in., 12/-.  
Type D236, 4.5:1 Driver Transformer, 1 x 1 x 1in., 10/-.  
Type D240, 8.5:1 Driver Transformer, 1 x 1 x 1in., 10/-.

**ARDENTE TRANSISTOR VOLUME CONTROLS**

Type VC1545, 5K with switch, dia. 0.9in., 8/-  
Type VC1760, 5K with switch, dia. 0.7in., 10/6  
Deaf aid ear piece xtal or magnetic 7/6.

**WEYRAD**

**COILS AND TRANSFORMERS FOR A 2-WAVE TRANSISTOR SUPERHETERODYNE PRINTED CIRCUIT AND FERRITE ROD AERIAL**  
Long and Medium Wave Aerial—RA2W. On 6in. rod, 7/16in. diameter, 208pF tuning, 12/6.  
Oscillator Coil P50/1AC, Medium wave. For 176pF tuning, 5/4.  
1st and 2nd I.F. Transformers—P50/2CC, 470 kc/s, 1/16in. diameter by tin. high, 5/7.  
3rd I.F. Transformers—P50/3CC, to feed diode detector, 6/-.  
Driver Transformer—LFD/T2. 1 5/16 x 1 x 1 1/2in., 9/6.  
Printed Circuit—PCA1. Size 2 1/2 x 8in. Ready drilled and printed with component positions, 9/6.  
7 x 4in., 35 ohm Speaker, 25/-.  
These components are approved by transistor makers and performance is guaranteed.  
Constructor's Booklet 2/-.

**NEW MULLARD TRANSISTORS**  
Audio OC71 6/- R.F. OC44 10/8  
OC72 7/6 OC45 9/6  
Sub-miniature Electrolytics (15V). 100uF, 2uF, 4uF, 5uF, 8uF, 25uF, 50uF, 100uF, 2/6. Diodes OA71, OA81, 3/- GEX 34, 4/-.

B.B.C. Pocket 2 Transistor. M.W. and L.W. Radio Kit, 32/6. Phones 7/6 or deaf aid earpiece, 7/6.

"P.V." POCKET 6 TRANSISTOR KIT MK.II WITH LATEST OSMOR MODIFICATIONS. A.L. PARTS, PRINTED CIRCUIT AND CABINET. OSMOR DESIGNED KIT. 28.15.0.

**READERS OF PRACTICAL WIRELESS" 337 WHITEHORSE ROAD WEST CROYDON Telephone: THO 1665**  
**SPECIALISTS**  
P. and P. charge 1/-, over £3 post free. C.O.D. 2/-.  
(Export welcome. Send remittance and extra postage.)

## Easy-to-build kit-sets of



## highest quality at lowest cost

**THE "MOHICAN" GENERAL COVERAGE RECEIVER Model GC-1U** Fully transistorised, 4 piezo-electric transistors. Excellent portable or Fixed Station receiver for the amateur and short-wave listener. £38.15.0

### SHORT-WAVE TRANSISTOR PORTABLE

**Model RSW-1** Extending aerial, leather case, four band (2 short-wave, Trawler and Medium). £22.10.0

### 6-TRANSISTOR PORTABLE Model UXR-1

Pre-aligned I.F. transformers printed circuit, 7 x 4in. high-flux speaker. Real hide case. £14.18.6

### DUAL-WAVE TRANSISTOR RADIO UJR-1

This sensitive headphone set is a fine introduction to electronics for any youngster. £2.16.6

### HI-FI F.M. TUNER Tuning range 88-108 Mc/s.

For your convenience this is available in two units sold separately: Tuning Unit (FMT-4U) with 10.7 Mc/s. I.F. output £3.5.0 (inc. P.T.). I.F. Amplifier (FMA-4U) complete with cabinet and valves £14.16.0 (£11.11.0).

### HI-FI 16W STEREO AMPLIFIER Model S-88

20mV. basic sensitivity (4 mV. available, 7/16 extra.) Ganged controls. Stereo-Monaural gram. radio and tape recorder input. Push-button selection. £26.12.6

### 6W STEREO AMPLIFIER Model S-33 3 watts

per channel, 0.3% distortion at 2.5 w/chn 20dB N.F.B. Inputs for Radio (or Tape) and Gram. Stereo or Monaural, ganged controls. Sensitivity 200 mV. £12.8.6

### TRANSCRIPTION RECORD PLAYER, GL-58

Goldring—Lenco four speed unit. G.60 pick-up arm and infinitely variable speed adjustment between 33 $\frac{1}{3}$  and 80 r.p.m. with fixed speed at 16 r.p.m. Balanced turntable (3 $\frac{1}{2}$  lb.). Stereo. £20.12.2

### HI-FI SPEAKER SYSTEM Model SSU-1

Ducted-port bass reflex cabinet "in the white". Twin speakers. With legs, £11.18.6

### "COTSWOLD" HI-FI SPEAKER SYSTEM KIT

Acoustically designed enclosure "in the white" 26 x 23 x 15 $\frac{1}{2}$ in., housing a 12in. bass speaker with 2in. speech coil, elliptical middle speaker and pressure unit to cover the full frequency range of 30-20,000 c/s. Complete with speakers, cross-over unit, level control, etc. £21.19.0

### COMPLETE MATCHED STEREO OUTFIT

includes record player, amplifier and twin speaker systems (pedestal speaker legs optional £2.2.0 extra). £44.9.4

### STEREO CONTROL UNIT USC-1

Luxury model with press-button inputs to suit any pick-up or tuner and most tape-heads. Output 1.3 v. R.M.S. per channel. Printed circuit construction. £18.18.6

### MULTIMETER Model MM-1U

Measures wide range of voltage, current resistance and dB in over 20 ranges. Sensitivity 20,000 ohms/volt D.C. and 5,000 ohms/volt A.C. 0-1.5, 1,500 volts A.C. and D.C. 0-150 $\mu$ A, 15 A D.C. Resistance 0.2 $\Omega$  to 20M $\Omega$ . 4 $\frac{1}{2}$ in. meter, 50  $\mu$ A f.s.d. £11.18.6



F.M. TUNER



S.33



S.88



DX-40



UXR-1



OS-1



SSU-1



AG.9U



GC.1U

### AMATEUR TRANSMITTER Model DX-100U

Covers all amateur bands from 160-10 metres. 150 watts D.C. input. Self-contained including Power Supply Modulator V.F.O. £81.10.0

### AMATEUR TRANSMITTER Model DX-40U

From 80-10 m. Power input 75 w. C.V.V., 60 w. peak C.C. phone, Output 40 w. to aerial. Compact and self-contained. Prov. for V.F.O. £32.10.0

### VAR. FREQ. OSCILLATOR VF-1U

Calibrated 160-10 m. Fundamentals on 160 & 40 m. Ideal for our DX-40U and similar transmitters. £11.2.0

### R.F. SIGNAL GENERATOR Model RF-1U

Up to 100 Mc/s fundamental and 200 Mc/s on harmonics and up to 100 mV. output on all bands. £11.8.0

### AUDIO SIGNAL GENERATOR Model AG-9U

10 c/s to 100 kc/s, switch selected. Distortion less than 0.1% 10 v. sine wave output metered in volts and dB's. £19.19.6

### VALVE VOLTMETER Model V-7A

Measures volts to 1,500 (D.C. and R.M.S.) and 4,000 pk. to pk. Res. 0.1  $\Omega$  to 1,000 M  $\Omega$ . D.C. input impd. 11M $\Omega$ . Complete with test prods leads and standardising battery. £13.0.0

### Portable 2 $\frac{3}{4}$ in. SERVICE 'Scope Model OS-1

Compact portable scope ideal for servicing and general work. Y amplifier sensitivity 10 mV/cm; response  $\pm$  3 dB 10 c/s-2.5 Mc/s. Time base 15 c/s-150 kc/s. Printed circuit. Case 7 $\frac{1}{2}$  x 4 $\frac{1}{2}$  x 12 $\frac{1}{2}$ in. Vt. only 10 $\frac{1}{2}$ lb. £19.10.0

### 5 in OSCILLOSCOPE Model O-12U

Wide-band amplifiers, essential for TV servicing. F.M. alignment, ecc. Vertical freq. response 3 c/s. to over 5 Mc/s. without extra switching. T/B covers 10 c/s to 500 kc/s. in 5 ranges. £36.10.0

### RES.-CAP BRIDGE Model C-3U

Measures resistance 100 $\Omega$  to 5M $\Omega$ , capacity 10pF to 1000 $\mu$ F, and power factor. Test voltages 5-450 v. £8.6.6 with automatic safety switch.

### SINGLE CHANNEL AMPLIFIER, MA-12

10-12 watt Hi-Fi amplifier, low distortion and wide frequency range. £10.19.6

### HI-FI EQUIPMENT CABINETS

Range of cabinets available with at least one to suit your particular needs. From small to large, housing Tape Deck, Record Player and full equipment. In the white for finishing to personal taste.

From £11.5.6 to £17.18.6

### GRID DIP METER Model GD-1U

Coverage from 1.8 Mc/s to 250 Mc/s. Complete set of plug-in coils provided. £10.9.6

### TAPE RECORDING/PLAYBACK

#### AMPLIFIER Model TA-1

Monaural (TA-1M) £18.2.6. Conversion unit, £23.6.0

to Stereo £6.10.0. Stereo (TA-1S), £23.6.0

#### 'PACKAGED DEALS' of Hi-Fi

Equipment including TAPE DECKS, RECORD PLAYERS and DECCA His PICK-UPS. Write in to see how these deals save you further money.

All prices include free delivery to UK

Deferred Terms

available on orders over £10

Please send me FREE CATALOGUE (Yes/No) \_\_\_\_\_

Full details of model(s) \_\_\_\_\_

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

PW1

# DAYSTROM LTD.

Dept. P.W.1, GLOUCESTER, ENGLAND

A member of the Daystrom Group, manufacturers of the  
WORLD'S LARGEST-SELLING ELECTRONIC KITS

# Practical Wireless

Vol. XXXVII No. 659 JANUARY, 1962.

Editorial and Advertisement  
Offices:

**PRACTICAL WIRELESS**

George Newnes, Ltd., Tower House,  
Southampton Street, W.C.2.

© George Newnes Ltd., 1962

Phone: Temple Bar 4363

Telegrams: Newnes, Rand, London,  
Registered at the G.P.O. for trans-  
mission by Canadian Magazine Post.

## SUBSCRIPTION RATES

including postage for one year

Inland - - - £1.9.0 per annum  
Abroad - - - £1.7.6 per annum  
Canada - - - £1.5.0 per annum

## Contents

	Page
Editorial . . . . .	793
Round the World of Wireless P.W. "Minuettes" . . . . .	794
High Sensitivity Bridge . . . . .	796
All About Cathode-Follower Circuits . . . . .	801
Power for Transistors . . . . .	804
Transmitting Topics . . . . .	807
Short-wave Listeners' Log . . . . .	808
How Transistors Work . . . . .	809
On Your Wavelength . . . . .	812
The P.W. "Citizen" . . . . .	815
Improving the All-band TRF . . . . .	818
Recording Level Indicators . . . . .	819
Experimenter's Power Pack . . . . .	820
Faults in VHF/F.M. Receivers Short-wave Section . . . . .	829
Universal Shunts . . . . .	834
Improving Broadcast Receivers Trade News . . . . .	837
The Bass Reflex Cabinet . . . . .	841
Letters to the Editor . . . . .	845
Club News . . . . .	853
Understanding Power Supplies	854
	857

The Editor will be pleased to consider articles of a practical nature. Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed: The Editor, PRACTICAL WIRELESS, George Newnes, Ltd., Tower House, Southampton Street, London, W.C.2. Owing to the rapid progress in the designs of wireless apparatus and to our efforts to keep readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in PRACTICAL WIRELESS is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. PRACTICAL WIRELESS incorporates "Amateur Wireless."

## RADIO AS A HOBBY

IT is not so many years ago that the man who had a radio set was regarded by his neighbours as a "scientific genius", and was able to entertain, as well as mystify, by demonstrating his apparatus. Many converts were made for the hobby and, when broadcasting started, the number of radio hobbyists grew until it assumed such proportions that it almost rivalled photography. As it grew, periodicals appeared devoted to the hobby and at one time there were a dozen of these, and it was noteworthy that the majority of constructors were middle-aged. Youth at the time was unable to take part in view of the expense and lack of knowledge or interest and the subject appeared too technical to follow. As time went on, the hobby began to die, and one by one the periodicals and magazines disappeared from the market, whilst the number of stores dealing in radio components also gradually reduced. After the war, however, there was a marked revival, not only on account of the many radio "experts" who left the armed forces, but because of the many valuable items of ex-government equipment which were released for general sale. The hobby again took on a healthy outlook and, although the technique was more involved, schools began to devote classes and instruction to certain aspects and thus the younger generation became interested.

Today, radio construction as a hobby is probably in as good a position as it was before the decrease just prior to the war. Transistors have come into such wide use that many schoolboys now have their own pocket portables which they have made up and carry about with them, and on the Christmas market will be found constructional toys which embrace not only simple transistor equipment but also various types of electronic equipment. The attendance at the recent Radio Hobbies Exhibition last month (November) showed an interest even greater than before, and it was interesting to note the age-groups and how they have changed from pre-war days.

Our recent "Tutor" series has been started up in a number of schools and the many letters which we have received show that there is a very great development of interest in radio and its associated fields. Broadcasting and television are no longer regarded as scientific marvels but are part of everyday life, and the forthcoming year should see even greater developments, as the growing field of enthusiasts must lead to new ideas.

## A FILM SHOW

ANOTHER film show has been arranged in collaboration with Mullard Ltd. It will be held at Caxton Hall, Westminster, and readers are invited to send for their free tickets which are now available from these offices. The films will be shown on Friday, February 2nd, 1962, and the programme will begin at 7.30 p.m. When applying for tickets, enclose a stamped and addressed envelope (at least 3½ in. x 6 in.). Mark your envelope "Caxton Hall" in the top left-hand corner.

The films to be shown are *Special Quality Valves*, which deals with valves made to withstand vibration and shock, and *Transistors*, which deals with the "everyday" uses of transistors.

Our next issue dated February, will be published on January 5th

# Round the World of Wireless

## POTENTIAL AND CURRENT NEWS

### Broadcast Receiving Licences

THE following statement shows the approximate number of Broadcast Receiving Licences in force at the end of September, 1961, in respect of wireless receiving stations situated within the various Postal Regions of England, Wales, Scotland and Northern Ireland. The numbers include Licences issued to blind persons without payment.

Region	Total
London .. .. .	683,155
Home Counties .. .. .	640,703
Midland .. .. .	468,163
North Eastern .. .. .	500,260
North Western .. .. .	430,938
South Western .. .. .	378,859
Wales and Border Counties .. .. .	221,640
<b>Total England and Wales .. .. .</b>	<b>3,323,393</b>
Scotland .. .. .	367,644
Northern Ireland .. .. .	115,449
<b>Grand Total .. .. .</b>	<b>3,806,486</b>


### The Indian Industries Fair

THE Indian Industries Fair which opened in New Delhi on 14th November will last for six weeks.

AEI's contribution both to the Indian industrial revolution and to power developments throughout the world form the main theme of their stand which takes up 2,000sq. ft.

Working models, photographs, films and other devices will be used to show some of the 3,500 types of equipment which AEI makes and supplies to all parts of the world. Dominating the central section, which deals with the part AEI is playing in the Indian industrial revolution, is a large map giving the location of eight main projects with which the company has been concerned. One of these is the giant heavy electrical plant being built in Bhopal by the Indian Government. Stress here is laid on the special training scheme which AEI is establishing for this project, which enables 3,000 men to be trained at a time. Other important schemes are the Durgapur Steel Works, where AEI as a member of the British Consortium known as ISCON has supplied five 90MW generator sets; and electric railway and traction developments including those in Bombay and Calcutta.

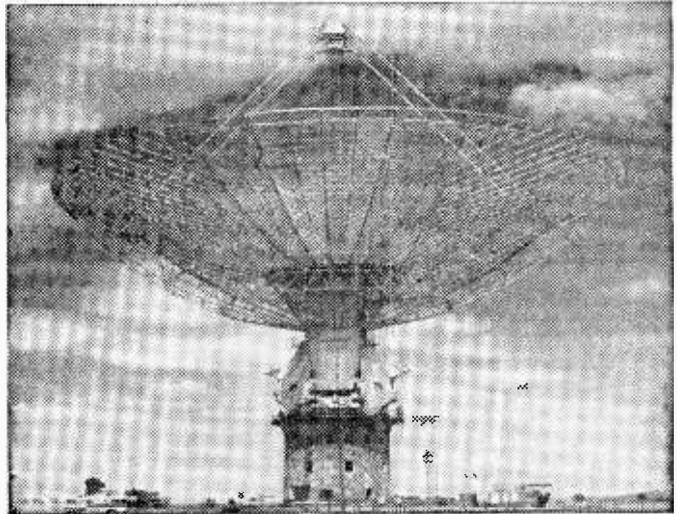Surrounding the Indian section is a perimeter display giving a



This new radio telescope is in New South Wales, Australia. Although slightly smaller than the Jodrell Bank telescope, it is expected to give better performance.

comprehensive guide to AEI activities throughout the world. An illuminated map pin-points the company's 70 factories and four research laboratories in the United Kingdom and a rotating drum, with the flags of the nations to which equipment has been supplied, gives details of work in five continents. Turbo-generator sets up to 550MW supplied for British power stations; electric units for British Railways and London's Underground; turbo-electric propulsion for British ships and power stations for Spain are some European examples.

Asian work shown includes generating equipment and electric trains for India; a gas turbine power station for Iran; synchronous condensers for Ceylon and generator sets for Burma, Singapore and Hong Kong. African work is represented by electric locomotives and mine winders for South Africa; water wheel alternators for Uganda, and generating and distribution equipment for the Kariba Dam in Rhodesia. Work carried out in Australasia which will be shown are circuit breakers, power transformers and electric locomotives supplied to New South Wales and New Zealand. For the Americas

there are switchgear, transformers and generators for the Argentine, turbo-generators and telephone cables for Canada and railway electrification and electric trains for Brazil.

### Radio Telescope in Australia

THE new Radio Telescope at Parkes, New South Wales, 240 miles West of Sydney, Australia, was opened on 31st October. The picture on this page shows the "dish" in the parked position which will be necessary when winds are over 25m.p.h. The "dish" is 210ft in diameter and although this is 40ft less than the Jodrell Bank telescope, the Australian telescope is expected to give a better performance, as the "hydrogen line" had not been discovered at the time the British instrument was being designed. It cannot therefore, like the Australian one, be used at full aperture down to a wavelength of 21cm., but the new telescope is designed to have a surface accuracy of  $\pm \frac{1}{16}$  in. under all temperature variations and winds up to 10m.p.h. It can be steered to an accuracy of one minute of arc. The tower is 39ft in diameter, 42ft high and the total weight on the foundations is 1,750 tons. The actual reflect-

tive surface is made of 1,300 small mesh panels on the face of the "dish". The cost of the telescope was shared between the Australian Government, the Carnegie Corporation, the Rockefeller Foundation of New York and private Australian subscribers.

#### **Multichannel Radio System for Ghana**

**A** CONTRACT by the Ghana Posts and Telegraphs authorities for the supply and installation of a twin-path VHF multichannel radio telephone system to link the Volta River dam area with Accra, the capital, has been awarded to Marconi's Wireless Telegraph Company Ltd.

The route, which was surveyed by Marconi's under a separate contract, will run from Accra to Tema and then to Akosombo, where the dam is being built.

Between Accra and Tema a super-high-frequency (7,000Mc/s) link will be built which will have a maximum telephone capacity of 300 channels. The route from Tema to Akosombo will be via a repeater station at Ningo Hill and will have a maximum capacity of 48 telephone channels, although initially 12 channels will be used along the whole route, with full facilities for telephone, telegraph and teletypewriter services. The Ningo Hill repeater will be unattended, with duplicate diesel-electric power supplies and automatic changeover in the event of failure.

At Akosombo a mobile radio system is to be provided under the contract to enable engineers working on the dam to effect communication into the radio link. In addition a telephone subscriber network is to be supplied and installed in the Akosombo area and this will be connected to the main radio link and also the mobile radio system. Full channel access will be provided at Tema and telephone exchanges are to be supplied for this station and also for the Accra terminal.

#### **Also in Ghana**

**O**N October 27th, President Nkrumah performed the ceremonial opening of Ghana's new external broadcasting station—the most modern short wave broadcasting system on the African Continent—which with its four 100kW transmitters, is capable of world coverage.

The entire project—the spec-

ially-designed station buildings, the transmitters and ancillary equipment, the masts, aerial and feeder systems and the complete studio link equipment—was the responsibility of Marconi's Wireless Telegraph Company Ltd., who were awarded the contract by the Ghana Government.

The station, which is at Tema, near Accra, is built in the form of a hollow square, with a spacious rectangular courtyard occupying the enclosed area. The buildings have been specially designed to cope with earthquake shocks and the effects of solar heat and salt-laden air. A microwave radio link connects the studios at Accra with the transmitters at Tema.

Marconi's are also supplying technical staff for the supervision and maintenance of the station for a period of four years and


are also training personnel of the Ghana Broadcasting System both at the station and at the Company's Chelmsford Works.

#### **Electronic Telephone Exchange for Hull Docks**

**A** 20-line electronic exchange for the British Transport Dock Department in their grain silo at Hull is to be installed by Pye Telecommunications.

The exchange is to be installed in a location where high dust levels make electronic switching particularly suitable. Special T.M.C. heavy-duty telephones will also be used in the silo to minimise the effect of dust.

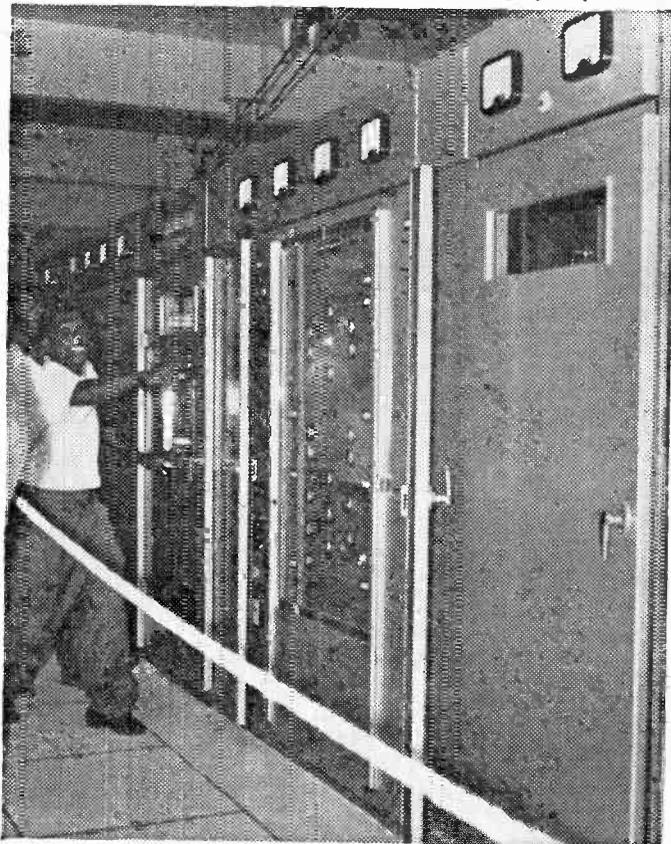
Pye mobile radio equipment has also been supplied for communication between the grain silo office and the floating elevators at work discharging ships.



*On October 27th President Nkrumah officially opened Ghana's new high power short wave broadcasting station, at Tema, near Accra.*

*The station, which comprises four 100kW transmitters, is the most modern broadcasting system in Africa and capable of world-wide coverage. This picture shows a view of part of the Transmitting Hall.*

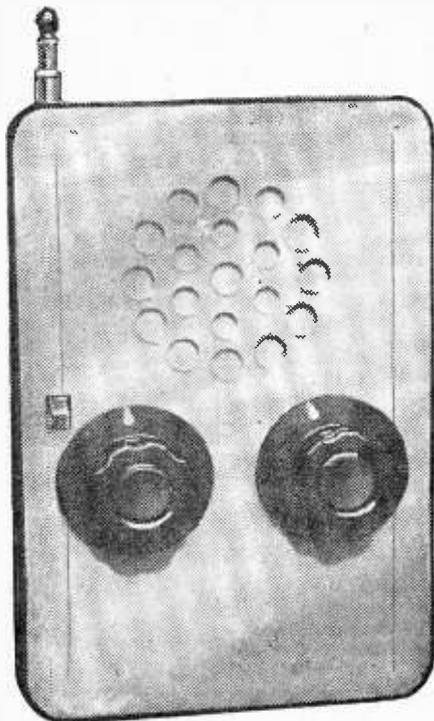A TRF  
POCKET PORTABLE RECEIVER  
WITH  
FOUR TRANSISTORS



**T**HE TRF type of receiver is much easier to construct than a superhet, and does not require any form of trimming or alignment whatsoever. It is thus particularly suitable for use when a straightforward circuit giving reception of local stations only is required. The circuit shown in Fig. 1 has four transistors, and gives very good speaker results, in these circumstances.

#### Circuit

The first transistor operates as detector, with regeneration, which considerably increases sensitivity. It is followed by a driver and push-pull output stages, with 2½in. speaker. It was found that sufficient volume was often obtained with the ferrite slab internal aerial only. However, to permit more distant reception, a telescopic chrome aerial is incorporated. This is about 6in. long when closed, and extends to about 36in. The receiver is so made that it can stand upright, with the aerial vertical.

When the extended aerial is not in use, the receiver can be placed flat, or upright, and should be turned for maximum signal pick-up in the usual way. If preferred, the extending aerial may be omitted. It is also in order to use a few feet of thin insulated flex for an aerial instead, when the ferrite slab gives insufficient volume. It should generally be possible to obtain sufficient volume without extending the rod, or using an external aerial, except in areas where signal strength is poor.

#### Ferrite Slab

This is shown in Fig. 2, and is approximately 3in. x ½in. x ½in. The larger winding has 52 turns, with tapping 2 made 11 turns from end 3. A space of ¼in. is left, and six further turns are wound on in the same direction. Both windings are of 28s.w.g. DCC wire, which is easy to use. The tapping is made by baring the wire, and soldering on a lead. A small piece of insulating material under this joint will prevent any possible shorts to adjacent turns. The ends of the windings can be secured with adhesive, or tape. The windings should not be painted, waxed, or covered with adhesive.

A ferrite rod or slab with a ready-made Litz medium wave winding could be used instead. The small additional winding can be of any wire of about 32s.w.g. to 24s.w.g. Enamelled wire should be wound on a layer of paper.

Two mounts are cut from ebonite or similar material, and slotted to take the slab. These

P. W.

MINUETTE

By F. G. Rayer

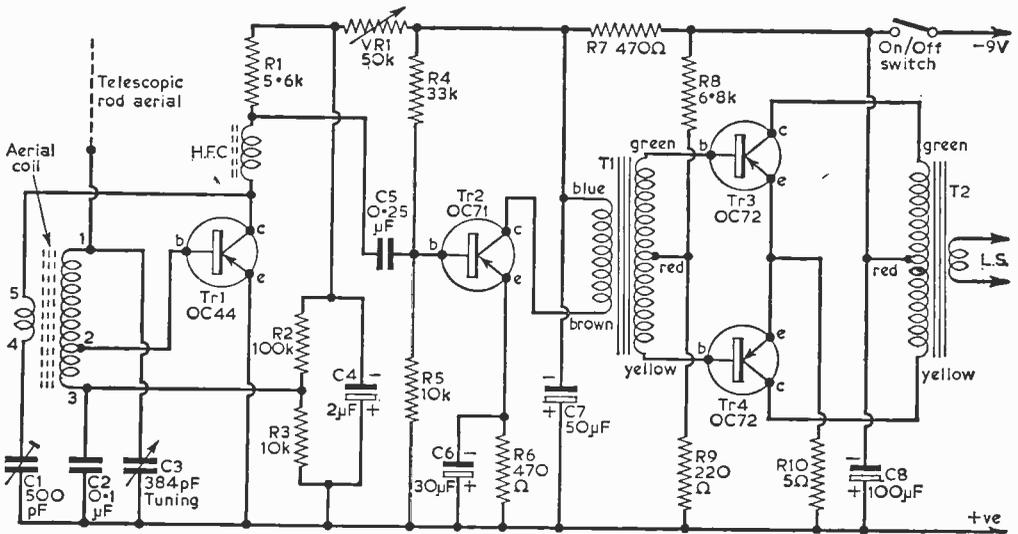


Fig. 1—The circuit of the receiver.


mounts are secured to the panel with countersunk screws, which can be self-tapping into holes in the mounts. Adhesive is placed on the slab and mounts, and the slab inserted in the slots.

**Receiver Case**

This is easily obtainable and is a popular plastic "lunch box" approximately 4½ in. x 6¾ in. x 1½ in.

The case should be supported upon a block of wood while drilling. The drills should be sharp, and only light pressure should be used. Holes about ⅜ in. in diameter are then drilled for the controls, and the slot is made for the switch. This can be done by drilling one or two small holes, and squaring up with a small file.

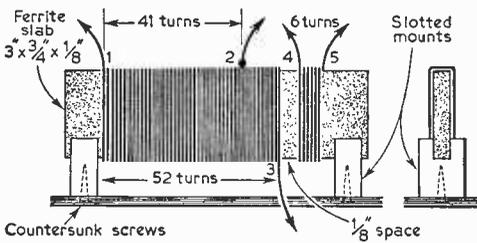After removing any fragments, paint the case on the inside with the desired colour. A quick-



All coils wound with 28swg. D.C.C. copper wire

Fig. 2 (above)—The construction of the ferrite slab aerial.

There is enough free space to make construction easy, and to allow alternative components to be used.

The case is drilled to form a speaker fret, as shown in Fig. 3. Two circles are drawn, one of ½ in. radius, and one of 1 in. radius. The small circle is divided into six, and the large circle into twelve. This can be done with compasses. Small pilot holes are then drilled, being positioned as accurately as possible. Six holes about ⅜ in. in diameter are then drilled, and thirteen holes about ⅜ in. in diameter.

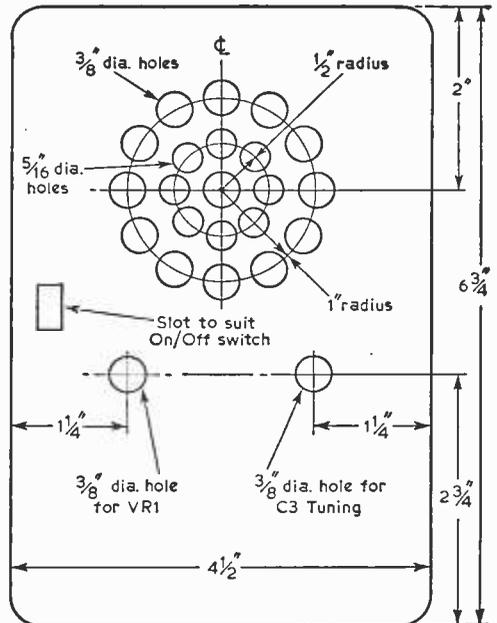


Fig. 3 (right)—The drilling details of the case.

drying enamel or paint will be most suitable.

When the receiver is finished the back is held on by a single screw, near the centre, which enters a threaded bush screwed to the receiver panel. Removing this single screw allows the back to be taken off to change the battery.

### Receiver Panel

The receiver is constructed on a paxolin panel  $4\frac{1}{2}$  in. x  $6\frac{1}{2}$  in., and can be tested complete, with speaker, before inserting it in the case. When inserted, it is held in by the nut on the bush of the 50k potentiometer, and by a small bolt near the tuning condenser spindle hole.

Fig. 4 shows the receiver panel inside the case. It is, of course, only inserted when finished and tested.

The tuning condenser is a 2-gang air-spaced miniature type, as this is readily available for transistor receivers. Both sections are in parallel, making a total of about 384pF. This condenser is held to the panel by three short 4B.A. countersunk screws. Subsequently, one screw is removed, and passes through a hole in the case, to hold the receiver, as described. Care is necessary that these screws are not too long, or they will short circuit the condenser, or bend its plates. A 500pF solid dielectric may be used instead, with a small reduction in efficiency. If so, the fixing nuts of the 50k potentiometer and 500pF condenser will secure the receiver in its case.

The speaker is secured with countersunk 6B.A. bolts. Extra nuts, or spacing sleeves, are used with two bolts, so that the 5-tag strip shown in Fig. 4 can be fixed in position.

(To be continued)

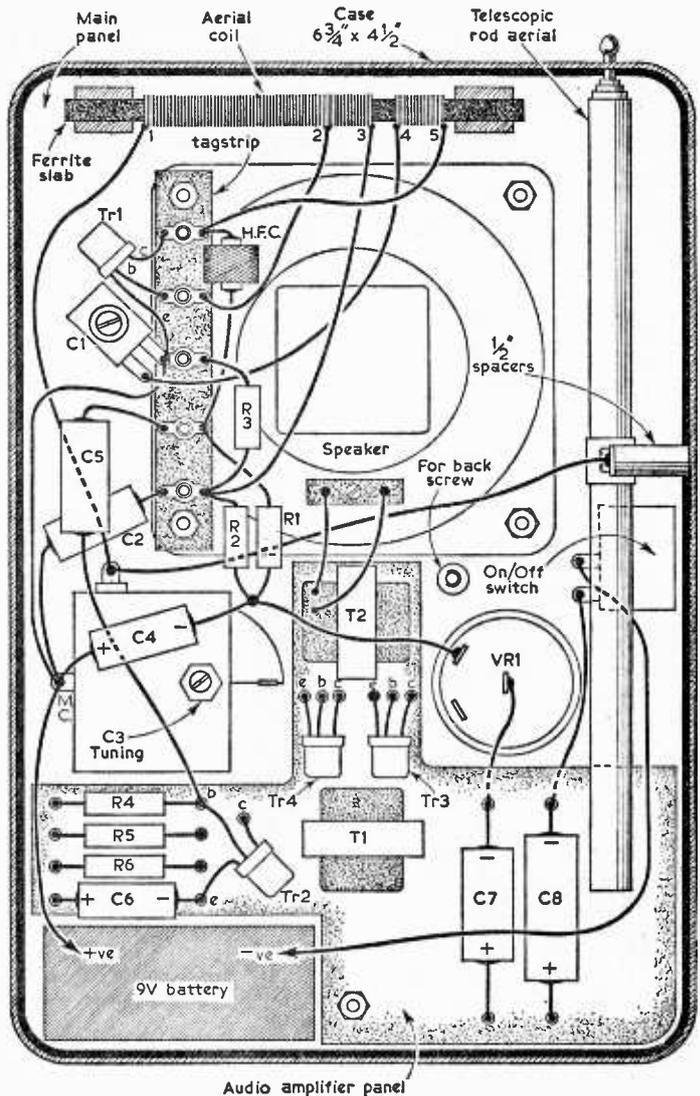


Fig. 4—The internal layout of components.

### COMPONENT LIST

#### Resistors

R1 5.6k	R6 470 Ω
R2 100k	R7 470 Ω
R3 10k	R8 6.8k
R4 33k	R9 220 Ω
R5 10k	R10 5 Ω

#### Capacitors

C1 500pF trimmer	C3 384pF tuning
C2 0.1 µF	C4 2 µF elec.

C3 is a 2-gang condenser (J.B.)

C5 0.25 µF	C7 50 µF elec.
C6 30 µF elec.	C8 100 µF elec.
VR1 50k	
Tr1 OC44	Tr2 OC71
T1 Driver transformer PW/DT (Osmor)	Tr3,4 OC72
T2 Output transformer PW/OT (Osmor)	

On/off switch, 2½ in. loudspeaker, whip aerial, case, knobs, etc.

# High Sensitivity Bridge

## A CIRCUIT WITH AMPLIFIED NULL INDICATOR

By M. A. Harris

(Continued from page 737 of the December issue)

**L**AST month it was decided that calibration could be executed easily with the use of little more than a protractor and a slide rule. The protractor should be a large one—which gives greater accuracy—the 6in. diameter type gives graduations every half degree. A 360° protractor is advantageous, although a 180° type will do.

The slide rule is for division and multiplication. Log. tables will suffice although this will take a longer time. If the constructor possesses neither of these, the required calculations can be carried out by hand, and it is here where the most patience is required.

The first thing to do is to find the total angle of travel of the pointer on the balance knob. In the prototype this was 310° (see Fig. 7). This angle will be designated  $\theta$  (theta) since different potentiometers have different total angles of travel. When the resistance (or capacitance) to be measured is equal to the standard employed, the balance point will be when the pointer is at an angle of  $\theta/2$  from the zero or datum line (in a clockwise direction). If the test resistance is  $\frac{1}{10}$ th of the standard, the balance point will be when the angle is

$$\frac{(1/10)/(1+1/10) \times \theta^\circ}{=1/11\theta^\circ}$$

Similarly when the test resistance is 10 times that of the standard the balance will be  $10/11\theta^\circ$ .

Cut out a piece of paper 10in. in diameter, and mark on it the datum line,  $1/11\theta$ ,  $\theta/2$ ,  $10/11\theta$  and  $\theta$ . The calculations can be done by slide rule (the quickest), log tables or by long-hand.

Let, for sake of argument, the standard be 100Ω. Then the balance point when 10Ω is across the test terminals will be  $1/11\theta$ .

For 20Ω, the balance point will be

$$\frac{20}{20 + 100} \theta = \frac{2}{11}\theta$$

For 30Ω, the balance point will be

$$\frac{30}{30 + 100} \theta \text{ and so on.}$$

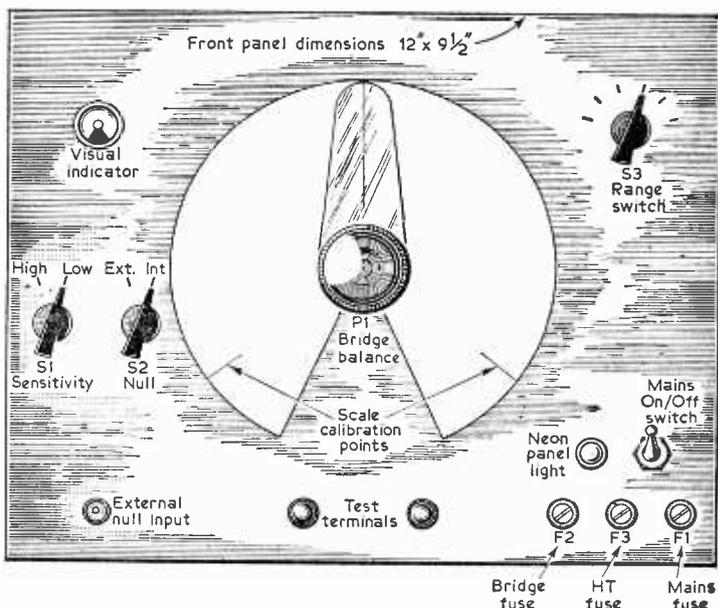


Fig. 5—The layout of the front panel.

For 200Ω, the balance point will be

$$\frac{200}{200 + 100} \theta = \frac{2}{3}\theta$$

For 300Ω, the balance point will be

$$\frac{300}{300 + 100} \theta \text{ and so on.}$$

The values at which these calculations are made are as follows:—

8Ω	} overlap.	60Ω	400Ω
9Ω		70Ω	500Ω
10Ω		80Ω	600Ω
15Ω		90Ω	700Ω
20Ω		100Ω	800Ω
30Ω		150Ω	900Ω
40Ω		200Ω	1kΩ
50Ω		300Ω	1.5kΩ
			2kΩ

The other resistance ranges will be 1k—100k and 100k—10M.

The overlap is provided at each end to facilitate readings of resistance at the extreme ends of the scale. When all these angles have been worked out, they are then transferred to the scale. The scale markings should, if reasonable care has been taken, be accurate, and for greater accuracy, intermediate values can be worked out and drawn in.

**Reciprocal Scale**

For the capacitance ranges, the values of C are the exact reciprocals of R.

e.g. if balance with a standard R of 100Ω were 10Ω, the same balance with a standard C of 100pF would be 1000pF. In other words, if, with a standard R a balance point R1 were obtained, with a standard C, the same balance point would represent a capacity of C×R/R1.

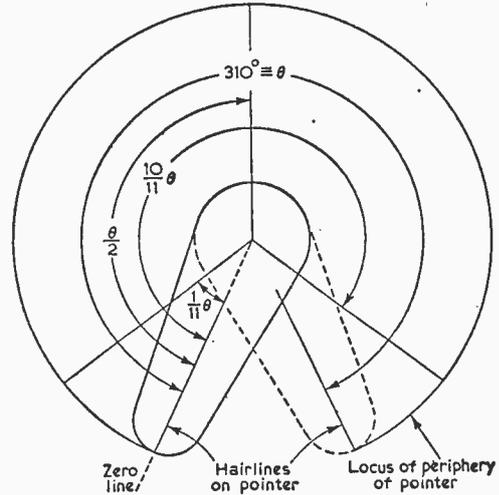


Fig. 7—The method of marking the scale.

continue trying different 1μF condensers until one is obtained that is under 1μF. From simple subtraction, the value of the condenser to be placed in parallel with it is obtained, so making the value exactly 1μF. (Condensers in parallel add up.) If desired, the balance point can be set (i.e., what it should be) and a trimmer placed across the nominally 1μF condenser, and this trimmer adjusted until the magic eye shows a balance (i.e., eye fully open).

The instrument is now complete and ready for use. It is a good idea to use a 3ft piece of twin flex with crocodile clips on the end, so that rapid measurements are obtained. One word of warning, however, on the low capacitance range, the self-capacitance of the flex will have to be taken into account. This is easily done by leaving the crocodile clips unconnected and taking a balance reading. Then from whatever value of balance is obtained when measuring a condenser, this value obtained for the self-capacitance is simply subtracted.

**Conclusion**

This instrument has been in use for the last six months and has proved reliable, and repaid for itself many times over, in the time saved by its use.

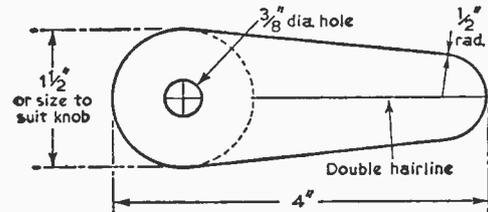


Fig. 6—The dimensions of the cursor.

So for all the values of R plotted, the values of C are equal to 1/R. A good idea is to mark the C scale in a different colour from the R scale. The scale card should be carefully placed over the balance potentiometer spindle, and glued into position. A coat of clear varnish will prevent dirty fingermarks appearing.

**To obtain an accurate 1μF capacitor**

Switch to the 1μF range. Select any 1μF condenser and measure its value on the 1μF range (near the right-hand end). Switch to the 10,000pF range and measure its value again (near the left-hand end). This answer will be the accurate one. Consequently the actual value of the nominal 1μF condenser can be calculated.

Let the true value of the 0.1μF capacitor (as measured on 10,000pF range)=C.

Let the apparent value of the 0.1μF capacitor, as measured on the 1μF range be C1.

Then the true value of the nominally 1μF condenser is

$$(C/C1 \times 1)\mu F$$

If the true value of this nominally 1μF condenser is under 1μF, all very well and good, otherwise

**JOIN THE PRACTICAL GROUP**

<b>PRACTICAL TELEVISION</b> ... ..	<b>1/9</b>
Every Month	
<b>PRACTICAL MECHANICS</b> ... ..	<b>1/6</b>
Every Month	
Devoted to Mechanics, Science and Invention	
<b>PRACTICAL MOTORIST</b> ... ..	<b>1/6</b>
Every Month	
<b>PRACTICAL HOUSEHOLDER</b> ... ..	<b>1/3</b>
Every Month	

# All about CATHODE-FOLLOWER circuits

By E. McLoughlin

## PRINCIPLES AND USES OF THIS TYPE OF CIRCUIT

ALMOST every experimenter who is not a complete newcomer to radio will have heard of, and doubtless even used, cathode-follower circuits. He will have some idea of their purpose and their principle. He will probably know that a cathode-follower circuit delivers an output voltage approximately equal to the input voltage, but at a much lower impedance level, so that more current and power can be drawn at the output without the voltage collapsing. He will very likely have heard that "the output impedance is the reciprocal of the mutual conductance of the valve", yet he may have been puzzled by the fact that output cathode resistors used (see Fig. 1, a typical basic cathode-follower) normally need to be several thousand ohms, which is much greater than the reciprocal of the mutual conductance of a modern valve which is about 5mA/V for a triode, giving only 200Ω as the reciprocal; naturally, we must express the reciprocal in Volts/Amps, not V/mA, to obtain a result in Ohms! Now all these facts mentioned are perfectly true; the difficulty lies in their proper understanding, i.e. *exactly* what is meant, how the facts fit in with each other, and how practical use may be made of them.

The author must apologise now for having to use some mathematics at this stage, but it will be kept as brief and simple as possible. It is absolutely necessary to understand the processes involved in a cathode-follower clearly, before being able to grasp its practical applications to full advantage.

### Basic Circuit and Principles

We will, for the moment, ignore the question of the correct D.C. conditions for maintaining the proper or desired operating point. We assume that somehow this is realised, and leave its discussion for later in this article. The voltages  $V_{in}$  (input at the grid, between grid and chassis, as usual) and  $V_{out}$  (between chassis and cathode, output voltage) in Fig. 1 are supposed to be r.m.s. A.C. voltages applied, which represent the active signal interesting us. For the purposes of the following simple mathematics, they may be treated as if they were D.C. voltage differences, and thus the familiar versions of Ohm's Law may be used freely.

If  $V_{in}$  is made more positive (taking now a small part of a cycle of the A.C. waveform), valve current will increase, and thus the cathode voltage, i.e.  $V_{out}$ , will also follow in that it goes more positive, too, and, vice versa, on the negative half

cycles. Thus, the input and output voltages are in phase; they follow each other; hence the name. As far as grid and cathode are concerned, it is the *difference* of the input and output voltages which is actually operative as the input signal to the valve. It is quite obvious from a glance at Fig. 1, that input and output voltages are in *series opposition* between grid and cathode of the valve.

We thus have the signal ( $V_{in}-V_{out}$ ) as input to the valve between grid and cathode.

Let  $g_m$  be the mutual conductance of the valve. Then, by the definition of mutual conductance, this input signal will cause an anode current signal equal to,

$$(V_{in}-V_{out}) g_m$$

which must flow through the cathode resistor  $R_K$ , across which it thus causes a signal voltage drop, given simply by Ohm's Law, as

$$R_K(V_{in}-V_{out})g_m$$

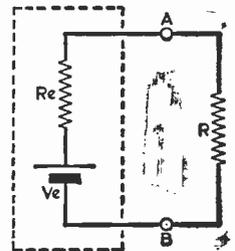
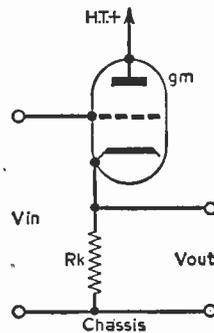


Fig. 1 (left)—The basic cathode-follower circuit.

Fig. 2 (right)—A diagram to explain the internal impedance of the cathode-follower.

But this voltage drop is the output signal,  $V_{out}$ , to which we may equate it, and thus arrive at the fundamental cathode-follower equation:—

$$V_{out} = R_K g_m (V_{in} - V_{out})$$

Simply rearranging this to a more useful form, we obtain

$$V_{out} = V_{in} \left\{ \frac{g_m R_K}{1 + g_m R_K} \right\}$$

Now  $R_K$  is typically 10k, and  $g_m$  is typically 5mA/V. This makes the factor

$$\frac{g_m R_K}{1 + g_m R_K} = \frac{50}{51}$$



consider the *matched condition*. As explained above, the load voltage is then half of the EMF, i.e.  $V_{out}$  is then only equal to *half* of  $V_{in}$ , because the value of  $R_k$  has been reduced drastically until it is equal to the internal impedance  $Z$ .

Taking again the basic cathode follower equation which we found,

$$V_{out} = V_{in} \left\{ \frac{gm \cdot R_k}{1 + gm \cdot R_k} \right\}$$

we now find for the present condition, putting  $R_k = Z$  and putting  $V_{out} = \text{half of } V_{in}$ :—

$$\frac{1}{2} V_{in} = V_{in} \left\{ \frac{gm \cdot Z}{1 + gm \cdot Z} \right\}, \text{ giving } 1 + gm \cdot Z = 2gm \cdot Z$$

i.e.  $gm \cdot Z = 1$                       i.e.  $Z = 1/gm$

It is thus apparent now exactly what is meant by the familiar statement that "the output impedance

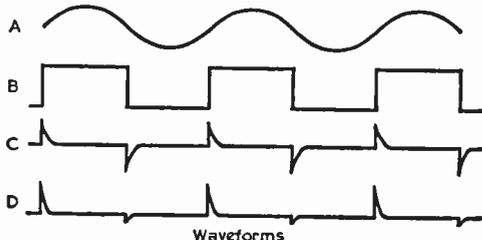


Fig. 5—Waveforms of the circuit in Fig. 4.

of a cathode-follower is equal to the reciprocal of the mutual conductance of the valve used." It means that we can reduce the value of the cathode resistance  $R_k$  in Fig. 1, which represents the external *output load*, down to the reciprocal of the mutual conductance of the valve used before 50% of the input voltage is lost. Naturally, if we are interested in maintaining as near 100% of the voltage as possible, the load resistor  $R_k$  must be very much larger, as it normally is. This is the usual application of the cathode-follower. But if we are interested in obtaining as much *power output* as possible, then the very much smaller value for  $R_k$ , equal to the reciprocal of the mutual conductance of the valve, must be used.

It is thus necessary to divide the following survey of the practical applications of the cathode-follower into two distinct categories:—

**(1) 1:1 voltage transfer:  $R_k$  much greater than  $1/gm$**

Under these conditions the benefit derived from the circuit is simply that the output voltage is to a large degree independent of the load, i.e. the output voltage remains virtually constant and equal to the input voltage, regardless of large fluctuations in the load resistance. The power output is very small, and not of interest for such applications.

**(2) Maximum power output at low impedance without the use of a transformer:  $R_k$  equal to  $1/gm$**

It must be mentioned that, in case (1), by making the value of  $R_k$  suitably large, and using a sufficiently high H.T. voltage, the signal amplitude which can be handled is very great indeed. This is because the input and output voltages are almost equal, the difference being very small, yet this alone represents the actual signal reaching the grid-cathode path of the valve. It is a good "rule-of-thumb" that the maximum peak-to-peak signal

amplitude capable of being handled is equal to half the H.T. voltage used, provided that the output load resistance is not less than some 50 times the reciprocal of the mutual conductance of the valve used.

**High Amplitude Signal Cathode-Followers**

We will now consider typical uses of high-amplitude cathode-followers, handling signal inputs of some 150V. (Note that it is necessary to ensure operation within the heater-cathode voltage rating of the valve used, when building such a circuit.) Fig. 3a shows a typical circuit, with component values. The D.C. operation point must now be considered. In the circuit shown, this is quite close to cut-off, because only a small anode current can flow before a high effective bias is developed across  $R_k$  functioning in the usual way as cathode bias resistor. With this circuit as it stands, a negligibly small negative-going input signal suffices to cut the valve off, giving a negative output signal equal at the most to the grid-base of the valve. However, a positive-going input signal gives correspondingly great positive output signals. The circuit is thus selective of polarity, which simply means that it rectifies, and it may be familiar as the "infinite impedance detector". An infinite impedance detector circuit can handle very large signal amplitudes if necessary, yet causes virtually no damping on the tuned circuit from which it receives its input because it does not run into grid-current. Hence the name "infinite impedance", this referring to the *input*. The output impedance is, of course, of the usual low nature typical of the cathode-follower.

**Triggering**

Apart from use as an R.F. detector in radios and tuners, the infinite impedance detector circuit of Fig. 3(b) has other uses which emphasize its signal-handling capabilities more strongly. In television timebases, oscilloscope timebases, radar timebases, and a host of other pulse-circuits, it is often required to trigger off a sawtooth oscillator, or other pulse-circuit at definite times. For this, voltage

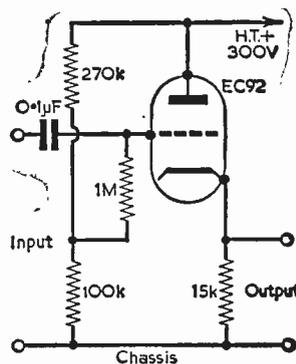


Fig. 6—A cathode-follower circuit, capable of handling peak 75V signals (positive or negative).

"kicks" of high amplitude (some 100V or more), usually positive, are required for the synchronisation process. Very often these kicks are obtained from the mains frequency or from the sync pulses from a television video waveform. Let us suppose, for example, that they originate from the mains sine wave of 50c/s. The sine wave is first squared, by driving a pentode very hard with it (see Fig. 4), and then "differentiated" by

(Continued on page 808)

# POWER for Transistors

By J. Anderson

## A WORKSHOP POWER PACK OR MAINS CONVERTER FOR TRANSISTORISED EQUIPMENT

**M**ANY constructors must at times, like the author, feel a pang of despair when looking at the many batteries and mercury cells which have been used in order to supply experimental transistor units for short periods. The unit about to be described was made to give any voltage from 0 to 12, or 0 to 20, depending on the transformer used, at up to 100mA, free from hum, and it was

power such as the relay-operating circuits in many transmitters, these giving a steady 12V at high current; alternatively, although it will limit the power of the unit somewhat, as well as its range, the unit can be supplied from the heater circuit of an existing set, providing that the circuit is able to supply the current needed.

The main component in the unit is the transformer—if a small heater transformer is all that is available, then it can be used, but this will probably limit the maximum output of the supply unit to 6.3V (or to the output of the transformer). The serious constructor may well consider it worth while to wind his own 20V-0-20V centre-tapped transformer, but in the author's case a small domestic electric bell transformer was found, giving about 24V output from the secondary with a good current rating, and, incidentally, it was inexpensive.

Rectification of the output from the transformer is accomplished by two diodes, the type used in this case being GJ-7M, although any small rectifier rated at about 30V 250mA will fulfil the purpose admirably.

### Size

Owing to the low voltage of the output, miniature transistor components can be used for R1, C1 and C2. The majority of the

*(Continued on page 824)*

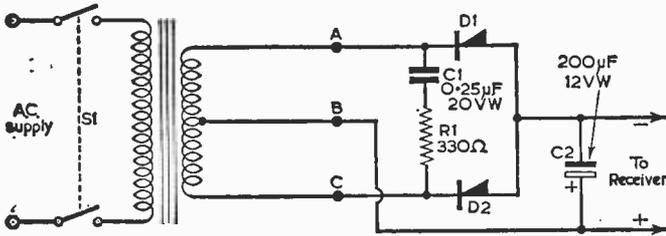


Fig. 1—This circuit is suitable for running a transistor portable receiver from the mains supply (see text).

designed to be sufficiently flexible to be used in the workshop or used as a mains converter when a portable set was being used at home for any length of time.

### Power Source

The power for the unit can be derived from the mains supply, or from some suitable source of

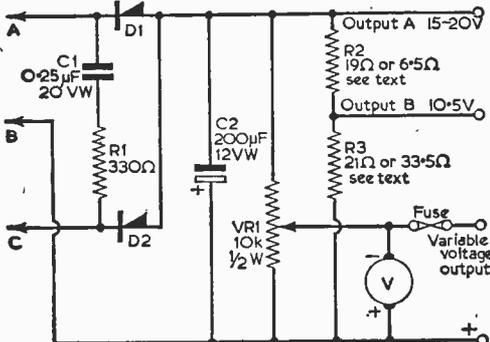


Fig. 2—A workshop supply unit with variable outputs.

### COMPONENTS LIST

#### Resistors:

- R1 330 Ω ½W
- R2 19 Ω for 20V transformer
- R3 6.5 Ω for 12V transformer
- R3 21 Ω for 20V transformer
- R3 33.5 Ω for 12V transformer
- VR1 10k ½W

#### Capacitors:

- C1 0.25 µF 20VW (minimum)
- C2 200 µF 12VW electrolytic

#### Rectifiers:

- D1 and D2 GJ-7M

#### Meter:

- V 25V FSD DC meter

#### Switch:

- S1 DPST, mains on/off switch

#### Transformer:

- Mains primary; secondary centre-tapped (20V-0-20V etc.—see text)


# THIS MONTH ONLY!

"SONOTONE" MIN. EARPIECE free with all parts totalling £4.10.0 or over

## TRANSONA-6

(6 Transistors plus 2 Diodes)

M/L & T. BAND

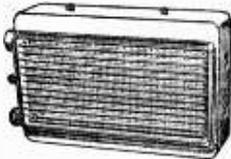

350 Mw XC101's push-pull output Transistors. Powerful magnet 3in. high grade speaker. Push-pull transformers. This is a top performing receiver. Nearly 30 stations listed in one evening including Luxembourg loud and clear. A pleasure to listen to. **FERRITE ROD AERIAL.** All parts sold separately, including pale blue gleaming polystyrene case with duo-diffusion grilles in red. Uses 9 volt battery. Sockets for car aerial.


Total building cost **£5.19.6** P.P. 3/-. Size 6½ x 4½ x 1½in.

"Agreeably surprised with Trawler Band reception. Luxembourg as loud as local. Your easy build diagram helped a lot... my first attempt."—H.S., Penzance, Cornwall (poor reception area).
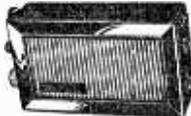
## TRANSONA-4

(4 Transistors, plus 2 Diodes)

Miniature speaker. **FERRITE ROD AERIAL.** MW/LW and Trawler Band coverage down to 80 metres. On test tuned in nearly 30 stations inc. Luxembourg. Easy-build plans 1/3. Handsome pocket case.



May be built for **52/6** P.P. 3/-.

"Best transistor set I have ever built—dozens of stations."—A.G.H., Deal, Kent.

## BEGINNERS PUSH-PULL FIVE

(5 Transistors, plus Diode)



- ★ 2½in. M/C Speaker
- ★ Ferrite rod aerial
- ★ Tuning condenser
- ★ Volume/oscillator control
- ★ Case with speaker grille in red.
- ★ Fully tunable over med/long waves
- ★ Simple assembly diagrams
- ★ 250 Milliwatts output stage


★ Can be built for **59/6** P.P. 3/- With 3" speaker 68/- post free

**POCKET 5 TRANSISTOR RADIO** Still Available Uses 5 transistors plus 2 diodes & 3in. speaker **£3.19.6.** P.P. 3/-

## TRANSONA-5

(MW/LW and TRAWLER BAND)

(5 Transistors plus 2 Diodes)

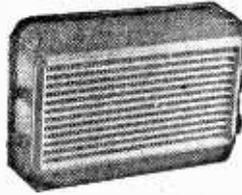

No aerial required  
3in. SPEAKER

Nearly 30 stations inc. Lux. 250mW output in push/pull for superb tonal quality. 2 R.F. stages for sensitivity. **FERRITE ROD AERIAL.** Pale blue polystyrene case with speaker grilles in red. Volume/sensitivity control.

Total building cost **£4.15.0** P.P. 3/-  
**ALL PARTS SOLD SEPARATELY**

## NOW THE SUPER SEVEN 4-WAVEBAND RADIO

(7 Transistors plus 2 Diodes)

- ★ 3 R.F. STAGES
- ★ Mullard and Surface Barrier Transistors
- ★ Coverage of Medium, Long Waves, Trawler Band and approximately 20-60 metres short wave
- ★ Use as domestic radio, car radio or fit with strap (not supplied) for carry-about.
- ★ No aerial required except for use as car radio and for short waves
- ★ 3-inch speaker but will drive a larger speaker
- ★ Performance comparable to many receivers costing treble
- ★ 400 milliwatts output stage
- ★ Minimum of 30 stations tuned in excluding S.W.



May be built for **£6.19.6** plus 3/6 post, etc.  
**PARTS PRICE LIST AND EASY BUILD PLANS 1/3**

## NEW SUPER SIX DESIGN

MED/LONG WAVES, TRAWLER BAND AND S.W. TO APPROX. 40 METRES



- ★ 6 1st grade Transistors (inc. Mullard and Surface Barrier) plus 2 DIODES.
- ★ Top grade 3in. L/speaker.
- ★ 2 R.F. Stages for extra boost.
- ★ High Q 7in. Ferrite Rod Aerial
- ★ Easy-build diagrams
- ★ No aerial or earth required (except as car radio)
- ★ Attractive pale blue case with speaker grilles in red.
- ★ 350 Milliwatts output stage
- ★ Sockets for car radio
- ★ Test receiver tuned in over 30 stations (inc. Luxembourg loud and clear.)

THIS FINE RECEIVER MAY BE BUILT FOR **£6.9.6** Plus 3/- P.P.

**DATA SHEETS AND PARTS PRICE LIST FOR THE ABOVE 1/3 EACH**

ALL PARTS SOLD SEPARATELY

**AFTER SALES SERVICE YOUR PROTECTION**

# RADIO EXCHANGE COMPANY


27 HARPUR STREET, BEDFORD

PHONE 2367

(Opposite Co-op)

10 a.m. to 1 p.m. SAT.
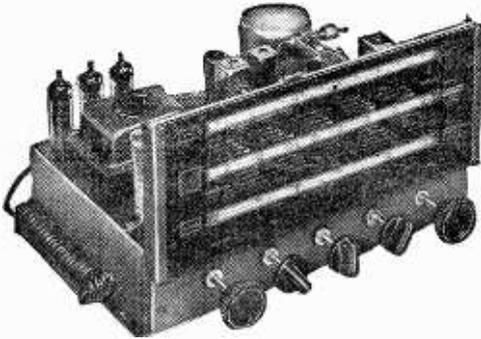
# For Radio . . . For Records . . . For Tape an *Armstrong* Chassis



An Armstrong chassis is more than just a radio-gram chassis. It is a carefully designed combination of tuner, control unit and amplifier in one compact unit which can be used as the basis of a complete high fidelity system. A system which can include tape recording and playback as well as AM and FM radio and record reproduction. All Armstrong chassis are suitable for use with a complete tape recorder or with a tape deck and its associated tape pre-amplifier. Where a tape deck is used we recommend the Armstrong Pabo-3 tape pre-amplifier.

**JUBILEE Mk. 2** (illustrated) £31.150  
VHF, with automatic frequency control. Medium and long wavebands with ferrite aerial and magic eye tuning. Separate tone controls. Tape record and playback inputs. 8 watts push-pull output.

**AF208** £23.150  
An AM/FM chassis of 5 watts output covering the VHF and Medium bands. Although economically priced, this has the same superior finish and components as our more expensive models.

*AM/FM Stereo Chassis are also available.*

**ARMSTRONG WIRELESS & TELEVISION Co. Ltd.**  
WALTERS ROAD, LONDON N.7. Tel.: NOR 3213

Post this coupon or write for catalogue or call at our Showroom for full demonstration and professional advice on your installation. Open 9-5 including Saturdays.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

PJC

ALL TAPE SENT BY RETURN OF POST



### DON'T MISS THIS SUPER QUALITY HI-FI AMERICAN "CBS" TAPE

BRAND NEW AND GUARANTEED

CIP-6	600ft. 5in.	Standard Play	13/-
LP-9	900ft. 5in.	Long Play	17/6
CMXP-12	1,200ft. 5in.	Double Play	32/-
CIP-9	900ft. 5 1/2 in.	Standard Play	15/-
LP-12	1,200ft. 5 1/2 in.	Long Play	19/6
CMXP-18	1,800ft. 5 1/2 in.	Double Play	37/-
CIP-18	1,200ft. 7in.	Standard Play	21/-
LP-18	1,800ft. 7in.	Long Play	28/8
CMXP-24	2,400ft. 7in.	Double Play	47/-

SPECIAL XMAS OFFERS! 1,200ft. 5 1/2 in. P.V.C. D.C. current: 250µA/10 mA/250 mA.

Guaranteed first quality 15/-, P. & P. 1/- Ditto, 7in. cassette 17/6 P. & P. 1/- (2 or more sent post paid). Many other types available including "Scotch," "EMI," "Triton," "Syncretape," B.A.S.F., etc. Send s.a.e. for our huge money-saving literature on Tapes and Accessories.

### POCKET TEST METER MODEL "CASSIE H.20"

(4,000 O.P.V.) FOR ONLY £4 POST FREE

A pocket size individual circuit tester with bakelite panel and metal cabinet. Complete with test leads. Ranges: D.C. Volts: 10-50-250-1,000 v. A.C. Volts: 10-50-250-1,000 v. (2,000 o.p.v.). D.C. Current: 250µA/10 mA/250 mA. Resistance: 0-10 K ohms/0-1 M ohms (by 3V internal battery). Decibels: -20 to + 22db (0dB -0.775v. -900 ohms). Size: 4 1/4 in. x 3 1/4 in. x 1 1/2 in.



Also available: MODEL TK.50

1,000 o.p.v. Ranges: D.C. mA: 1-250 mA., D.C. and A.C. Volts: 10-250-500-1,000 v. Ohms: 0-10K ohms 0-100 K ohms, £3.7.6.



**SUPER QUALITY TEST LEAD KIT No. 520**  
10/-  
Post Paid

Comprises leads and prods, English and Continental type plugs, splice terminals and crocodile clips. Complete in attractive case.

### WAVEMETER CLASS D

Freq. band 1,900 Kc/s. to 8,000 Kc/s. (158-37.5 metres) in two ranges. 1,900 Kc/s.-4,000 Kc/s., also 4,000 Kc/s.-8,000 Kc/s. Supply 6 v. D.C. input. Complete with twin crystal, spare vibrator, head phones, original instruction manual and transit case. As new £5.50.

### TELEFUNKEN STEREO HI-FI AMPLIFIER

110/250 v. A.C. input. 5 watt undistorted output (10 watts nominal) size 12 x 9 x 2 1/2 in., weight 9lb. Illustrated lead available, our price £9/15/-, carr. 5/-.


### AVO MODEL 7

Latest Ministry release of this well-known test instrument. Supplying 50 ranges of current, voltage and resistance tests. Complete with leads and batteries. Ready for use. Perfect condition. £11/10/-, Carr 5/-.

### BRAND NEW CRYSTAL CALIBRATOR No. 10

(Battery powered 1.4 v. valves). Complete with full working instructions, circuit diagram, carrying haversack, connecting lead and spare valves. Frequency range: 1.5 to 10 Mc/s. (nominal) but can actually be used up to 30 Mc/s. Weight 5lb. Size 7 x 7 1/2 x 4 in. As fully described in "Practical Wireless" Dec. 1960 issue, pages 691-693. ONLY £4.17.6. P. & P. 2/6.
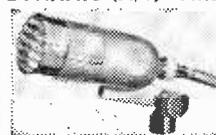
### SUPER QUALITY HI-FI DYNAMIC (M/C) MIKE



with built-in Transformer 200 ohm or 50 k. impedance. Complete with screened lead. OUTSTANDING VALUE MODEL £4.15.0 (State M.D.180 Imp. reqd.) Post Free

### CRYSTAL MICROPHONE MODEL BM.3

Three-way mike for hand, desk or floor stand use. Response 100-8,000 c/s. Sensitivity -62dB. Length 7in. Head dia. 1 1/2 in. Supplied with neckband. Terrific performance! Outstanding value at ONLY 39/8. P. & P. 2/-

Also Available: MD.170. Similar in design to BM.3 but moving coil with built-in transformer. Guaranteed. Outstanding value. £4.7.6 Post Free.

**TELESCOPIC FLOOR STD.** HEAVY 9in. dome chromium base, chromium stand with screw top. Extends to approx. 6ft. Suitable for above mikes, etc., £2.10.0, Carr. 5/-

## GEE BROS. (RADIO) LTD

15 LITTLE NEWPORT STREET, LONDON W.C.2.  
Telephone: GERard 6794/1453

Adjoining Leicester Square Tube Station Open 9-6 Mon.-Fri. 9-1 Sat.

# TRANSMITTING TOPICS



## A "SENTRY" UNIT

By J. Brown

**T**HIS small unit was primarily designed for R.F. indication. For field strength indication it is usual to have a circuit similar to Fig. 1, but this becomes more of a hindrance than a help to the enthusiast with a multiband transmitter, as coils have to be changed for each band.

### The Choke Method

After various experiments, it was found that a normal 2.5 $\mu$ H choke of the R.F. type would suffice for all bands. This meant that a readable indication was obtainable without having to change any coils, etc., or even having to tune for the maximum reading.

The purpose of this unit is not to obtain actual measurement of R.F., only to give some indication. It was found that the choke method was sufficient for 160m to 30Mc/s; to achieve a higher reading it is only necessary to couple the unit more tightly to the source of R.F., or have a longer pick-up wire connected to the junction of RFC1/D1 (Fig. 5).

With this arrangement any changes in R.F. were made visible e.g. increase or decrease of the R.F. could be seen when any component or valve changes were made. Also the effect of the drive to the final P.A. was obvious, and exact tuning was possible when using a  $\pi$  output. Beam and other aerials could also be adjusted for maximum output.

A further modification of this instrument was to use a pair of headphones in place of the meter, thus making the unit a "phone monitor". A switch arrangement was used to change from meter to audio (Fig. 3). On trial it was found the audio was very pronounced and so a carbon potentiometer was added to control the amount of rectified R.F. to either the phones or the meter.

This was a very useful addition as faults in the modulator/speech amplifier, such as hum, etc., could be found very simply, and even effects of component changes could be heard.

This unit was found of great use when TVI (audio breakthrough) was experienced. It was found to be mains-borne, by investigation with the pick-up wire on the monitor unit (running it along the electrical system of the house). The transmitter was set up for normal use, the modulator switched on with the microphone connected and stood near a clock. The R.F. was then modulated by the ticking. When the pick-up wire of the unit was placed near the house wiring, the ticking was heard, so, obviously, the TVI was mains-borne. Chokes with their associated condensers (ceramic type) in the modulator and the P.A. mains transformer leads removed the TVI.

Another version of the unit is given in Fig. 4. This is very useful for many purposes, Parasitic oscillations can be found: these appear on the

(Continued on page 854)



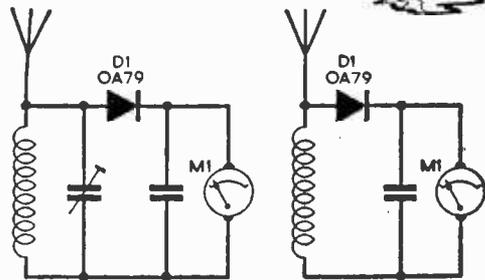


Fig. 1 (above left)—A field strength indicator circuit. Fig. 2 (above right)—A modified circuit. Fig. 3 (below)—A "phone monitor" circuit.

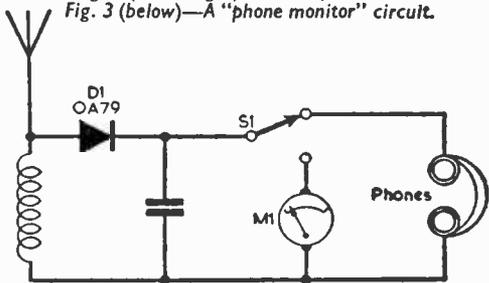

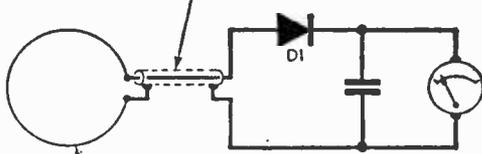
Note: The "Loop" is joined to the circuit by a length of coaxial cable



Loop...3 turns 2" diam. of PVC. covered wire

Fig. 4 (above)—Another version of the unit this is useful for picking up parasitic oscillations. Fig. 5 (below)—The circuit of the final design.

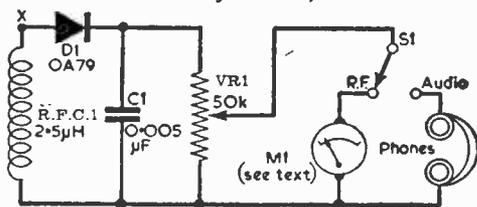At point "X" an 8" length of wire is enough for monitoring, otherwise use a piece of flex (sufficient to obtain a reading on meter)



# Short-wave Listeners' Log

**M**OST interest on the short wave bands is probably in Dx (long distance) reception. For best results, it is necessary to keep in mind which bands are most likely to provide signals from various remote parts of the world, or to listen on wavelengths which have been chosen according to the time of day.

It will be found that it is almost always possible to tune in some Dx signals of interest, at nearly any hour. But if reception of very distant stations in some particular area is in view, it will usually be necessary to choose a time and band to suit.

Enthusiastic S.W. listeners who intend to receive as many countries as possible make a point of switching on to certain bands, so as to make the best use of conditions. An example is the reception of Australian stations. In the early morning, some will generally be audible, and when conditions are good, even a one- or two-valver can be sufficient to pick them up. But at other times of day reception from this area will generally be impossible.

As the list of times to be given covers 24 hours, it is worth noting that amateur band activity is usually at its highest at weekends, and some listening periods should often be possible then.

The times given are GMT, and there is easily a latitude of half an hour to an hour either way, according to conditions. But, on the whole, it will usually be most satisfactory to tune to the bands indicated, at the times given. The choice of bands is for Dx reception, not for European and other near stations.

**06.00-08.30:** 1.8Mc/s and 3.5Mc/s bands: North America and Canada (unusual for these bands). 7Mc/s band: North America to Pacific coast. 14Mc/s band: world wide, including Australia, New Zealand and remote Pacific Dx. 21Mc/s band: Australia, Far East, South Africa.

**08.00-10.30:** 14Mc/s: Pacific islands, but Australian area probably fading out. 21Mc/s: Panama area, South America, South Africa, and still possibly world wide reception.

**10.00-Noon:** 21/14Mc/s: Still active, with Pacific area and Far East when conditions are good. Also Africa and occasional Central and South Americas.

**Noon-14.30:** 14Mc/s: Relatively inactive, but North America may begin coming in towards the end of the period. 21Mc/s: North America, Canada, Greenland, and occasional South Africa and other Dx.

**14.00-18.00:** 14Mc/s: Near East beginning to fade out, or completely gone. Many stations from North American area beginning to come up. 21Mc/s: Occasional good reception from many parts of the world, but American stations most likely.

**17.30-20.00:** 14Mc/s: Good for world wide reception, but often congested with American transmissions, which make reception of more remote stations difficult. Should easily provide dozens of new countries for beginning a log. 21Mc/s band: Interesting scattered Dx sometimes, but often high noise level.

**20.00-Midnight:** 14Mc/s band: Central and South America, and beginning to extend into the Pacific area.

21Mc/s: similar, but often less trouble from North American interference.

**Midnight-04.00:** 14Mc/s: Beginning to open out for world wide reception, and giving improved reception from South America, and South Pacific area, extending out towards the New Zealand area. South America may become audible on 7Mc/s, while towards the end of this period North America may become audible on the 3.5Mc/s band.

**04.00-06.30:** 14Mc/s: Reception extending to include Australia and New Zealand, but world wide reception possible. 21Mc/s: Australia and Far East areas beginning to come in, and occasional long distance reception on 3.5Mc/s and even 1.8Mc/s beginning to arise.

It will be seen that for general Dx listening, the 14Mc/s and 21Mc/s bands will usually be of interest. When Dx stations are to be logged on the broadcast bands, somewhat similar results will be obtained. For example, the 19m and 17m bands are very near the 20m (14Mc/s) amateur band, and propagation is similar. The 25m band is also very useful for long distance results. The 31m and 41m bands will become very active towards nightfall, and during the hours of darkness until midnight, and the 25m band will begin to open out towards the Australian region with early morning. 

## All about CATHODE-FOLLOWER circuits

(Continued from page 803)

using a very small coupling condenser to the next stage. The result is a series of negative and positive kicks, alternately, one pair for each original sine wave cycle. We do not want the negative ones, and these are automatically rejected by the cathode-follower (see Fig. 5) as explained above. The positive ones appear at the cathode output with full amplitude, and can trigger the timebase, as desired. The very low output impedance of the cathode-follower effectively decouples the subsequent proceedings in the timebase from the foregoing circuitry.

If we desire to pass on both negative and positive signals through the cathode-follower, giving preference to neither, being interested solely in the high signal amplitude handling capacity and low output impedance, then we must use a D.C. operating point of the circuit which lies more positive than in Fig. 3a. The necessary modification is shown in Fig. 6. Here the grid leak of the cathode-follower is taken on to an H.T. bleeder to a point positive with respect to chassis by an amount somewhat greater than the maximum amplitude of negative signals with which it is desired to cope. The positive signals will then take care of themselves automatically, provided the sum of maximum positive and negative amplitudes does not exceed about half the H.T. voltage. If it does exceed this, then a higher H.T. voltage must be used, if the valve is rated to withstand it.

(To be continued)

# How Transistors Work

By B. N. Rolfe

## A BASIC, NON-MATHEMATICAL EXPLANATION

**T**HERE is no reason whatsoever why a transistor circuit should cause confusion. Theoretically, a transistor is considerably less complex than a valve. Indeed, it has only three elements while even the simplest of valves—the triode—has four elements, namely, the anode, grid, cathode and heater. A transistor has no heater, but it has elements (or electrodes) which are much related to the triode valve. It has a base instead of a grid, an emitter instead of a cathode, and a collector instead of an anode. There are transistors which have four elements, rather like the four essential elements of a tetrode valve, but to date these are few and far between and need not be considered.

are many good books on the theory of semi-conductors.

### Two Diodes

If we had no previous knowledge of transistors and were given a three-wire device and told that it was a transistor, and we were also handed an ohmmeter and told to find out as much as possible about the transistor by making resistance checks, it would not take us very long to discover that within a transistor exist two diodes, or rectifiers. We would also eventually discover that the diodes are connected in series opposition. If we were to draw a diagram of our findings it would look like Fig. 1.

We know, of course, that an ohmmeter is nothing more than a voltmeter connected in series with a battery, and that when the two terminals are connected together the voltmeter is effectively connected across the battery. Full deflection is given on a dial scaled in "ohms" by adjusting a variable resistor labelled "set zero". Thus, when a resistor is connected across the terminals, the pointer reads something less than full-scale (because of the voltage dropped across the resistor) which is read off the "ohms" calibration as some definite value.

### Polarity of Terminals

The ohmmeter terminals are polarised by the battery (positive and negative), so the ohmmeter therefore provides a source of voltage as well as resistance measurement. This is exactly what is required for examining semiconductors, which are designed to have a low resistance to current passing in the "forward" direction and a high resistance to current passing in the "reverse" direction. It should be noted, however, that the "positive", or red, terminal on some multimeters when set to "ohms" may not be connected to the positive side of the internal battery. It is as well to check this before becoming involved in resistance checks on semiconductors.

To return to Fig. 1. With the positive terminal of the ohmmeter connected to wire A and the negative terminal to wire B there is a "low resistance" reading, as shown by Test 1. This indicates that current from the ohmmeter battery is flowing through the diode in the forward direction, and this is indicated by the direction of the "arrow" on the diode (or rectifier) symbol. Current in this context is the *conventional* flow from positive to negative and *not* electron flow, which is from negative to positive.

### Diodes

When the ohmmeter connections are reversed, then we obtain a high resistance reading, as shown

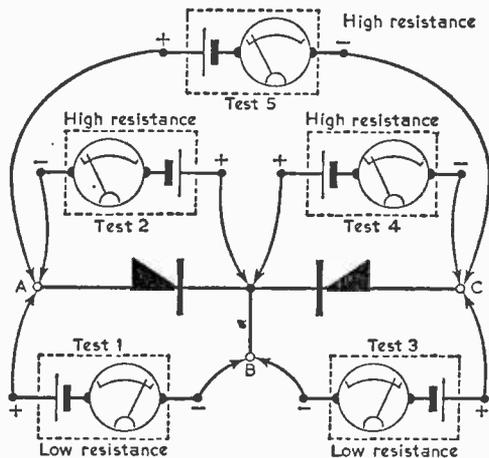


Fig. 1—How a series of ohmmeter tests indicates that a transistor contains two diodes connected in series opposition. (Test 6 is the same as Test 5, but with the ohmmeter leads transposed.)

### Theory

We are left, therefore, with the semiconductor equivalent of a triode valve, so, no matter how technical the circuit, it always revolves around a simple three-element device. It is not intended in this series of articles to delve into the basic theory of transistors. The conception of positive and negative current carriers and the like is adequately dealt with in other literature, and there

by Test 2. This indicates that current from the ohmmeter battery is flowing through the diode in the reverse direction, where it comes up against opposition. (Of course, in a perfect diode or rectifier there would be zero resistance to current in the forward direction and infinite resistance to current in the reverse direction, but as no diode is perfect, there will always be a low, but definite resistance to forward current and a large, but not infinite, resistance to reverse current, depending on the type of semiconductor. The ratio of reverse to forward resistance can be used as a measure to assess the quality of a semiconductor—as we shall see later.)

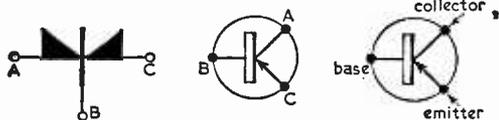


Fig. 2 (left)—Although there are two junctions in a transistor, it has one element which is common to both of them (shown at B).

Fig. 3 (centre)—The conventional transistor symbol using "A", "B" and "C", as in Figs. 1 and 2.

Fig. 4 (right)—The conventional symbol with the elements identified.

We discover the other diode section by connecting the ohmmeter between wires B and C, first to give the resistance to forward current (Test 3) and then to give the resistance to the reverse current (Test 4). We see from the forward current tests (Tests 1 and 3) that there is no need to remove the negative ohmmeter connection from wire B, and that forward resistance is given on each diode section simply by changing the ohmmeter positive from wire A to wire C. This in itself reveals that the two diodes must be connected in opposition.

Further proof of this is given, however, by Tests 5 and 6, for whichever way round the ohmmeter is connected across wires A and C there is always a high resistance, indicating that reverse current flows when the battery is connected in both polarities. This could only happen with diodes connected in opposition.

### Transistor Make-up

We have so far proved that a transistor contains two diode sections, and it is unlikely whether we would find out much more about a transistor given just a transistor and an ohmmeter. It is possible to find out more with this simple instrument, but assuming that we knew nothing at all about a transistor when we started, additional information would be found more by luck than by technical ability.

### Common Electrode

It is true that a transistor has two diode sections connected in opposition, but one "electrode" is common to both diodes, and the common electrode is that connected to wire B, as would be expected. We may thus redraw the circuit of Fig. 1 as shown in Fig. 2, which shows clearly the common electrode on wire B.

For reasons unknown to the author, the transistor symbol took on a slightly different form from that in Fig. 2, and this is shown in Fig. 3. Here the common element is at B and the two "outside" elements at A and C. One of the "outside" elements is given an arrow head simply to distinguish it from the other one. To be symbolically accurate, of course, each outside element should be given an arrow-head to conform with the build-up from the symbol in Fig. 2, but, since each "diode junction" has a different function, it is essential to be able to differentiate one from the other, and the use of a single arrow-head permits this.

### Transistor Elements

We must now abandon our earlier A B C identification and instead use the correct terms for the transistor elements. We have done this in Fig. 4, which reveals that the common element is called the "base", the element with the arrow-head the "emitter" and the element without the arrow-head the "collector".

### Transistor Biasing Arrangements

In practical transistor circuits, the base is biased negatively with respect to the emitter, as shown in Fig. 5. It will be seen, therefore, that the base-emitter diode junction is polarised for forward current. This means that the circuit is now equivalent to a low resistance and, as a consequence, passes a current (from the battery) of a value limited by the base-emitter junction resistance, any resistance in the external circuit and the battery voltage.

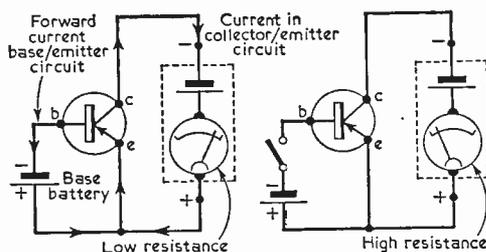


Fig. 5 (left)—The action of forward current in the base-emitter circuit gives a reduction in the apparent resistance between the collector and emitter.

Fig. 6 (right)—When the base current in Fig. 5 is switched off, the resistance between the collector and emitter increases. (This was also shown in Test 5 of Fig. 1).

Furthermore, the collector is also connected to a negative voltage with respect to the emitter. It will be recalled that our previous ohmmeter tests between the two "outside" elements (now called collector and emitter) showed that no matter which way round the voltage source was connected there was always a high resistance between them. However, owing to the forward current in the base-emitter circuit, the conditions between the collector and emitter are now severely modified, for instead of there being a high resistance between them, an

ohmmeter connected negative to collector and positive to emitter would register a relatively low resistance, as shown in Fig. 5.

**Change in Resistance**

By keeping the ohmmeter connected and switching off the base-emitter forward current, the ohmmeter would change from a low to a high reading, as shown in Fig. 6. Indeed, the apparent resistance as registered on the ohmmeter would alter depending on the actual base-emitter current. Within limits, the greater the current the smaller the apparent resistance—maximum base voltage gives maximum collector current and zero base voltage gives zero collector current (or nearly so as there is always some leakage in semiconductors).

In a transistor, therefore, a change in collector current is promoted by a change in base current (or voltage, since a voltage change gives a current change in the base circuit). This is rather like a valve, where a change in control grid voltage causes a change in anode current. It is because of this similarity that the base of a transistor is sometimes likened to the grid of a triode valve and the collector to the anode. Similarly, the emitter corresponds to the cathode.

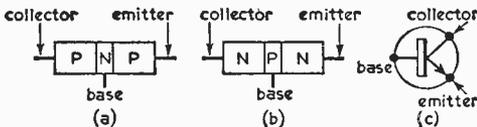


Fig. 7—The basic physical construction of (a) a pnp transistor, and (b) an npn transistor. In (c) is given the symbol for an npn transistor—the emitter arrow points in the opposite direction to the arrow in the symbol for a pnp transistor.

**Basic Concept**

A good book on semiconductor theory will reveal why collector current is promoted by the current in the base-emitter junction. One would learn that “holes” flowing from emitter to base diffuse through the base, and when they arrive in proximity to the collector are attracted into the collector by its negative voltage, thereby giving collector current.

condition is purposely arranged in p-type semiconducting materials. The “hole” or positive charge is then available for conduction.

This happens when the “hole” is filled by a “free” electron from an adjacent atom which, when it fills the hole, leaves another hole behind it. This hole in turn is filled by another electron from another atom, again leaving a corresponding hole, and so the process continues.

It will be understood from this brief description that the series of holes appears to be moving in a direction opposite to that of the electrons. Transistors are made of two types of semiconducting material, a material which uses holes to give a mobile positive flow called “p” (for positive) type, and a material which uses electrons for negative conduction called “n” (for negative type). Either a wafer of n-type material in sandwiched between two pieces of p-type material to make a pnp transistor or a wafer of p-type material is sandwiched between two pieces of n-type material to make an npn transistor as shown in Fig. 7.

The majority of transistors used at present in this country are of the pnp variety. Transistors of the npn variety are used in certain switching applications, though there is reason to believe that they may also be used more extensively in domestic equipment in the future, as they are already used in America.

**How npn Transistors Differ in Circuit**

Transistors of the npn type differ basically from pnp types by being connected to the supply voltages the other way round, with the base and collector being connected to a positive source with respect to emitter, instead of a negative source, as is required with pnp types.

Transistors of the npn type are symbolised by the arrow on the emitter pointing away from the base, as shown in Fig. 7(c).

**A Further Ohmmeter Test**

If we reproduce Test 5 of Fig. 1 on a transistor, as shown in Fig. 8, we would again prove that a high resistance exists between collector and emitter whichever way round the meter is connected, though we may find that the resistance is slightly greater when the negative of the meter is connected to the collector than when the positive of the meter is connected to it. However, if we set the arrangement with the negative of the meter to the collector and the positive to the emitter the resistance should be very high.

Now, if we connect a resistor between the collector and base, as shown in Fig. 9, the resistance should fall to a relatively low value, provided the transistor is in good order. Indeed, this represents a very good resistance test since, in effect, the ratio of resistance change corresponds to the D.C. gain of the transistor. The resistor effectively applies a negative bias to the base with respect to the emitter and thus causes conduction to take place between the emitter and collector. For most small transistors a resistor of about 33,000Ω (33k) is suitable, but it is not desirable for this or other transistor resistance measurements to be undertaken if the ohmmeter contains a battery in excess of 1.5V. A higher voltage may result in excessive current through the diode junctions which could cause a breakdown.

(To be continued)


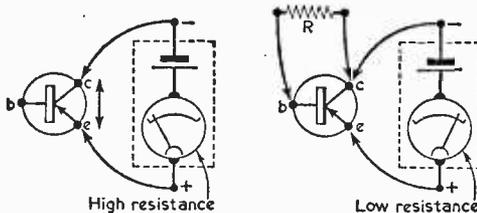


Fig. 8 (left)—Transistor leakage test.

Fig. 9 (right)—Using an ohmmeter and a resistor to check effective D.C. gain.

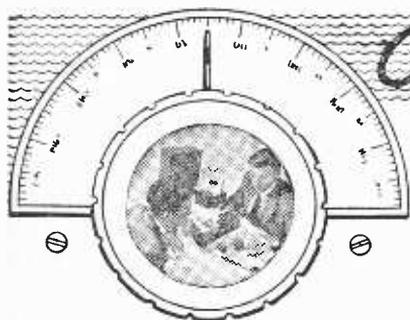The term “hole” is a convenient way of expressing a positive charge as distinct from the negative charge of an electron. A “hole” is said to be produced when an atom of the semiconducting material is short of a “free” electron, and this



# On Your Wavelength

## BY THERMION

I MUST thank the very many readers who wrote to me recently, after I had mentioned a "well-known reverend gentleman" who was responsible for some unorthodox circuits in the very early days of radio. I am indeed most pleased to hear that he is still alive and well and is living happily in retirement in the country. Many of these readers had used the circuit which I referred to, built around two audio transformers, and substantiated the very many claims which were made at the time—mainly in regard to the response to low organ notes.

The gentleman in question is still regarded as a foremost authority on the organ and Mr. Lucas of Tachbrook tells me that letters from him still appear at intervals in various organ periodicals. What a pity that we do not still have experimenters of this calibre still with us—or is there now no need for these experimental hook-ups?

Many readers, presumably of the older school, still state that they preferred the early days because of the scope which was afforded for experimental work, and although we have recently seen the introduction of the transistor, I feel that the opinions of a large number are to be respected—there is not so much scope with this particular component, at least not in the pure radio field.

In the field of computers and similar equipment, no doubt there is a vast territory still to be explored and perhaps many will find their hobby will offer fruitful experiments along these lines.

### Test Gear

What is the minimum which could be used to furnish a radio experimenter's workshop? I am tempted to ask this as I have had one or two letters asking me to make my recommendations on this question, each of the readers making some proviso regarding expense. This is a very difficult thing to decide—leaving out for the moment the question of money. One might say, providing no quantitative analyses and so on are to be made, a really reliable all-purpose testmeter would be sufficient. Others would hold, however, that a bridge or a tester for capacities and resistances is a must, and no really reliable experiments could be carried out without first making certain that components being used are the correct values.

In this connection one reader tells me that he uses a home-made neon tester and a £75 tester (the property of his employer). When he first started testing components he dug out 42 condensers from

his spares box and only three were fit to use! He says he had also found that the colour code on resistors appears to be what he calls "a practical joke".

He instances a case where he bought six 47k components (with a silver band) which, when bridged, measured between 62k and 80k. He says he has lost all faith in colour codes. I do not feel that this is general and it is certainly not my experience, and I do test all such items before I make up experimental lay-outs. But I do agree that if you want to be sure of success when making experimental equipment, it is best to make sure that every item is sound and its value is as marked, before using it. In this way, you save disappointment and limit the amount of checking which has to be done if the item fails to function as specified or as one desires.

### Peculiar Faults

I have before mentioned some of the weird faults which are experienced from time-to-time in both radio and television equipment, but I was very interested to hear the other day of a new one—experienced in a service laboratory by a skilled engineer. He was actually servicing a television receiver at the time and noted that he was repeatedly feeling the effects of a mild electric shock, although not using any screwdriver etc., at the time. When he approached the C.R. tube the usual symptoms of entering a strong electrostatic field were noted, and although he kept his hands in his pockets the trouble still persisted. I had heard previously where a bunch of keys in a pocket had been sufficient to pick up a stray field and in this case a very similar arrangement was responsible for the symptoms which were experienced. The engineer was wearing a tie which had a metallic thread running through it as part of the pattern and when he leant towards the set, these threads became charged and produced the effects which he had noticed. Had he been wearing rubber soled shoes no doubt nothing would have been noted, but in this particular case the usual unforeseen chain of circumstances came into play. He was not wearing rubber soles, and the lino in the workshop had been taken up for replacement; as a friend said, when told of the occurrence, with radio "You never can tell"! I should be glad to hear of similar unexplained or unexplainable instances.

## PRACTICAL WIRELESS CIRCUITS

17th Edition

By F. J. CAMM

17/6 by post 18/7

from

**GEORGE NEWNES, LTD.,**

Tower House, Southampton Street, London W.C.2.

# RETURN-OF-POST SERVICE

We offer a really efficient Mail Order Service on all items stocked. All cash orders are dealt with on the day of receipt.

★ Hire purchase orders are subject to slight delay but this is kept to the absolute minimum

## ● LOUDSPEAKERS

**GOODMANS:** Axiom 110 10in. £25.20; Axiom 112 10in. £21.40; Axiotele Bin. £215.00; Axiom 300 12in. £11.50; Axiom 400 12in. £161.00; Autumn 60 Bass, 12in. £212.90; Trebax Tweeter £24.00; CX 500 Cross-over unit £11.80.  
**WHITELEY:** HF 1016 10in. £24.00; HF 1012 10in. £25.20; HF816 Bin. £7.00; T816 Bin. £26.10; T10 Tweeter £4.80; T359 Tweeter £11.15; CX3000 Cross-over unit £11.10; CX1500 Cross-over unit £2.00. H.P. Terms available.

## ● SPECIAL OFFER OF TAPE HEADS

Bradmatic Tape Recording head as fitted to Collaro Studio Deck. Erase and record playback. 32/6 per pair. Post Free.

## ● TRANSISTORS

MULLARD. Reduced prices. Current production types, not rejects. All in makers' boxes.  
 OC44, 11/-; OC45, 10/-; OC70 and OC71, 6/8; OC72, 8/-; OC72 Matched Pairs 16/-; OC78, 8/-; OC81, 8/-; OC170, 13/6; OC171, 14/6. Postage 3d. on each transistor.

## ● AMPLIFIER KITS

We have full stocks of all components for the Mullard 510, Mullard 3-3, Mullard 2 and 3 Valve Pre-amp, Mullard Stereo, Mullard Mixer, GEC 912 Plus. Fully detailed list on any of these sent upon request.

Instruction Manuals; All Mullard Audio Circuits in "Circuits for Audio Amplifiers", 9/5. GEC 912, 4/6. All post free.

## ● STEREO COMPONENTS

Morganite ganged potentiometers as specified for the Mullard circuits. ● Log/Anti-Log, 500K, 1 meg, 2 meg. ● Log/Log, 50K, 250K, 1 meg, 2 meg. ● Lin/Lin, 250K, 500K, 1 meg. All 10/6 each. Pick-up cartridges, B.S.R. TC8S £2.50. Turn-over type for Stereo. L.P. and 78 records. List of all components for Mullard Stereo Designs is available.

## ● "P.W. TUTOR"

Everything in stock. Stage 1 including brand new light-weight headphones, 39/6. Less headphones, 23/6. Stage 2 19/-; Stage 3 21/6. Stage 4 11/6. All Stages 1 to 4 £4.80. Less headphones 23/13.6. All post free. Please note that the hardware, wood, Terry Clips and cement not included. All items available separately—send for list.

## ● "P.W. MINI-AMP"

Complete kit for amplifier £4.2.6. Whiteley Speaker P2.585, £1.4.0. Greengate Gramophone Unit £5.8.0. All parts available separately. send for list.

## ● "P.W. TUNER UNIT"

Send for parts list.

## ● GRAMPHONE EQUIPMENT

ALL LATEST MODELS Hire Purchase  
 ALL POST FREE Cash Price Deposit Mthly/Pmts.

**GARRARD AUTOSLIM RECORD CHANGERS**  
 (GC8 FU) ... £8.50 £11.30 12 of 13/-  
**COLLARO C60 (GP87 PU)** ... £8.50 £11.30 12 of 13/-  
**GARRARD RC210 (GC8 PU)** £10. 6.0 £2. 2.0 12 of 15/4  
**B.S.R. UA14 (TC8 PU)** ... £7.19.6 £11.2.6 12 of 12/3  
**B.S.R. UA14 Monarch** ... £8.19.6 £11.6.6 12 of 13/7  
 (TC8S Stereo/LP78)

**SINGLE RECORD PLAYERS**  
**GARRARD TA (GC8 PU)** ... £8.10.0 £11.4.0 12 of 13/-  
**B.S.R. T8 (TC8 PU)** ... £4.12.6 £1. 6.6 3 of £15.4  
**E.M.I. (Acos Stereo/Mono PU)** £26.15.0 £1. 7.0 12 of 10/6

**TRANSCRIPTION UNITS**  
**GARRARD 41F (GC8 PU)** £18.18.0 £3.16.0 12 of £11.7.8  
**PHILIPS AG1016** ... £14. 3.8 £2.17.8 12 of £10.9  
 Many of the above can be supplied for stereo working. See our Gramophone Equipment List for details.

## ● MAINS TRANSFORMERS

**GILSON:** W0741AB, 63/-, post free; W0839, 48/9, post 2/6;  
**PARTRIDGE:** P300/110, 77/8, post free; P4132, 78/6, post free;  
**P377, 69, post free; P4013, 69/-, post free.**  
**ELSTONE:** MT/MU, 45/-, post 3/3; MT3/M, 35/-, post 3/-;  
**PARMEKO:** P2831, 32/3, post 2/6.

## ● OUTPUT TRANSFORMERS

**GILSON:** W0896A, W0895B, 50/6, post 2/6; W0710, W0710/8K, 55/6, post 2/6; W0892, 62/3, post free; W0767, 27/-, post 1/6.  
**PARTRIDGE:** P3667, 52/6, post 2/6; P4014, 98/6, post free; P4131, 60/-, post free; P3591A, 99/-, post free; P5202, P5203, 95/-, post free.  
**PARMEKO:** P2841, 28/-, post 2/-.

**TERMS OF BUSINESS:**  
 Cash with order or C.O.D. We charge C.O.D. orders as follows. Up to £3, minimum of 3/2. Over £3 and under £5, 1/6. Over £5 and under £10, 1/8. Over £10, no charge. Postage extra on CASH orders under £3 except where stated. Postage extra on Overseas orders irrespective of price.

## ● JASON FM TUNER KITS

We supply kits for all the Jason FM Tuners. Fully detailed lists available. Kits are complete with all valves and instruction manuals—definitely noting else to buy.  
**FMT1 Standard Tuner** with ext. power supply, £28.19.6. Power pack kit, £22.12.6 extra. **FMT2 Standard Tuner** with internal power supply, £10.9.6. Less power supply, £8.9.6. **FMT3 Fringe Tuner** with internal power supply, £12.7.6. Less power supply, £10.9.6. **Mercury 2 FM/TV Sound Switched Tuner.** External power supply, £11.7.6. Power pack kit, £22.12.6 extra. **JTV2 FM/TV Sound Switched Tuner.** Internal Power supply, £15.17.6. **IMPORTANT—**Please state TV Channels required when ordering Mercury and JTV Kits.  
**INSTRUCTION MANUALS.** Booklet for FMT1, 2 and 3, 2/10. Mercury 2, 3/10. JTV2 3/10. All post free. **HIRE PURCHASE** terms available on any kit.

## ● TRANSISTORISE YOUR CRYSTAL SET

We have two new designs for Transistor amplifiers which can be used to greatly improve the signal from any crystal set. Leaflet available.

**RLD4 Kit.** One stage 19/- post free.  
**RLD5 Kit.** Two stage 21/- post free.  
 The kits are easy to build and very detailed instructions are supplied.

## ● MULLARD CATHODE RAY TUBES

ALL AT THE NEW REDUCED PRICES  
 We supply both Mullard Radiant Screen (Brand new factory fresh) and Mullard Lumener (Re-builds by Mullard with re-gained colour parts brand new). List of types available with prices and hire purchase terms.

## ● LATEST TEST METERS

	Cash Price	Deposit	Mthly/Pmts.	Hire Purchase
AVO Model 8 Mark II	£24. 0.0	£4.16.0	12 of	£1.15. 8
AVO Model 8 with leather carrying case	£27.18.0	£5.12.0	12 of	£2. 0.11
AVO Model 7 Mark II	£21. 0.0	£2. 4.0	12 of	£1.10.10
AVO Multiminor	£29.10.0	£1.18.0	12 of	14/4
AVO Multiminor with leather carrying case	£11. 9.0	£2. 5.0	12 of	17/-
TAYLOR MODEL 127A	£10. 0.0	£2. 0.0	12 of	15/-
CABY A10	£11. 7.6	£1. 7.6	3 of	£1. 6.8
CABY B20	£26.10.0	£2. 0.0	3 of	£1.13.4

Full details of any of the above supplied free on request. The AVO Models 7 and 8 are both latest models from current production—not to be confused with Government Surplus.

## ● ILLUSTRATED LISTS

Illustrated lists are available on LOUDSPEAKERS, TAPE RECORDERS, TEST EQUIPMENT, RECORDING TAPES, GRAMPHONE EQUIPMENT, AMPLIFIERS. Any will be sent free upon request.

## ● "BRAND FIVE" RECORDING TAPE

Standard Play: 600ft. (5") 16/-; 1,200ft. (7") 25/-.  
 Long Play: 900ft. (5"), 18/6; 1,200ft. (6"), 23/6; 1,800ft. (7"), 35/-.  
 Double Play: 1,200ft. (5"), 37/6; 2,400ft. (7"), 60/- (All Post Free.)

## ● B.A.S.F. RECORDING TAPE

Long Play: 210ft (3"), 9/-; 900ft (5"), 28/-; 1,200ft (6"), 35/-; 1,800ft (7"), 50/-.  
 Double Play: 900ft (3"), 14/-; 800ft (4"), 25/-; 1,200ft (5"), 42/-; 1,800ft (6"), 56/-; 2,400ft (7"), 77/6. All post free.

## ● TAPE RECORDING EQUIPMENT

	Cash Price	Deposit	Mthly/Pmts.	Hire Purchase
ALL CARRIAGE FREE				
B.S.R. TD2	£28.19.6	£1.18.6	12 of	13/7
COLLARO Studio	£12.19.6	£2.12.6	12 of	19/-

**TAPE AMPLIFIERS**  
 We now stock the Martin Recorder Kits. These are partly assembled kits for complete tape recorders. The Amplifier Printed Circuit panels are completely wired, but the assembly of this and external components is left to the constructor. Very complete instructions are supplied. Send for leaflet.  
**MODEL C** for Collaro Studio Deck £11.11.0  
**MODEL B** for BSR TD2 Deck, £8.8.0.  
**CARRIAGE CASES.** Smart carrying cases are available to take the above amplifiers and decks. Fitted with speaker. For Model C Amplifier and Collaro Deck, £5.5.0.  
 For Model B Amplifier and BSR Deck, £4.4.0.  
 H.P. Terms available for amplifiers, cases and decks.

## ● TAPE PRE-AMPLIFIERS

**ARMSTRONG PAB10-3.** This is a ready made version of the Mullard Tube C Pre-amplifier. Price £13.8.0. Hire Purchase: Deposit £3.8.0, and 12 monthly payments of £1.4.7.  
**MULLARD TAP C PRE-AMPLIFIER.** We stock complete kits and all components. Send for list.  
**MARTIN Kit** for Collaro Studio Deck £8.8.0.

**HIRE PURCHASE TERMS:**  
 are available on any item. Repayments may be spread over 3, 6 or 12 months. Details as follows: Three months: Deposit 6/- in the £. Service charge 5 per cent but minimum charge of 10/- Six and Twelve months: Deposit 4/- in the £. Service charge 10 per cent, but minimum charge 20/-.

**WATTS RADIO**  
 (MAIL ORDER) LTD.

54 CHURCH STREET, WEYBRIDGE, SURREY

Telephone: Weybridge 4556

Please note: Postal business only from this address

# NEW! DO-IT-YOURSELF TRAINING TECHNIQUE in RADIO & ELECTRONICS

You LEARN while you BUILD...

SIMPLE...PRACTICAL...FASCINATING... 1st stage receiver


ANNOUNCING—after many years of highly successful operation in the U.S.A. and in Europe—the latest system in home training in electronics is now introduced by an entirely new British training organisation. AT LAST—a comprehensive and simple way of learning—by practical means—the basic principles of radio and electronics, with a minimum of theory. YOU LEARN BY BUILDING actual equipment with the components and parts which we send you. You advance by simple steps using high quality equipment and performing a whole series of interesting and instructive experiments. No mathematics! INSTRUCTION MANUALS and our teaching staff employ the latest techniques for showing clearly how radio works in a practical and interesting manner. You really have fun whilst learning! And you end by possessing a first rate piece of home equipment with the full knowledge of how it operates and—very important—how to service and maintain it afterwards. A full library of magnificent illustrated textbooks are included with the Courses. IN FACT for the 'Do-it-Yourself' enthusiasts, the hobbyist, or those wanting help with their radio career training, or to set up their own full or part-time servicing business—then this new and exciting instructional system is exactly what is needed and it can all be provided at very moderate cost. Easy payments available. Post the coupon now, for full details. There is no obligation.

BUILD YOUR OWN • RADIO EQUIPMENT • TEST GEAR  
• HI-FI INSTALLATION—AND LEARN AS YOU DO IT

## RADIOSTRUCTOR

BRITAIN'S LEADING RADIO TRAINING ORGANISATION

**FREE**  
POST TODAY

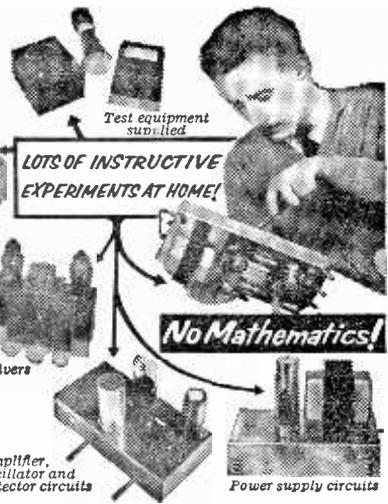

To: RADIOSTRUCTOR (Dept. G107),  
Reading, Berks.


Name..... } BLOCK  
Address..... } CAPS  
..... } PLEASE  
(821) We do not employ representatives 1-62

# Premier RADIO

23 TOTTENHAM COURT ROAD, LONDON W.1  
and at 309 EDGWARE ROAD, LONDON W.2

Tel: MUSEUM 3451/2  
Tel: PADDINGTON 6963

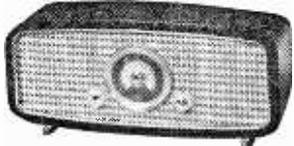The  
**SUPER 60**  
6-Transistor  
Battery Receiver  
May be Built for  
**£9.15.0**  
Plus 5/- P. & P.  
Ever-Ready PP10  
Battery Extra 11/-



**STAR FEATURES—**  
★ Six 1st grade Mullard Transistors and one Diode.  
★ Internal Ferrite Rod Aerial.  
★ 7in. x 4in. Elliptical Speaker.  
★ Printed Circuit.  
★ 500mW Push-Pull Output.  
The Receiver is housed in an attractive cabinet trimmed with gilt, supported by gilt stands. The receiver will operate for months on one 9-volt long-life battery. Instruction Book separately at 2/6 p.p.

- ★ Full medium and long waveband coverage.
- ★ Calibrated Direct Drive Dial Drive Assembly.
- ★ Full point-to-point instructions supplied.
- ★ Dimensions 18in. x 7 1/2in. x 5 1/2in.

## THE LECO 6 TRANSISTOR POCKET RECEIVER

This well designed transistor Receiver is ideally suited for the pocket or handbag being only 4 1/2 x 2 1/2 x 1 1/2in. in size and 7 oz. in weight, it has full medium wave coverage and incorporates 6 high grade transistors and 1 diode in a superhet circuit. Available in black, grey, green or cream.

Complete with Earpiece and Plastic Case.  
**£8.19.6**  
p. & p. 2/-  
PP3 Battery extra 2/6



## OUTSTANDING STEREO OFFER!

THE TELEFUNKEN STEREO HI-FI AMPLIFIER



Original Price 16 gns.  
NOW ONLY **£7.19.6**  
P. & P. 5/-.

- BRIEF SPECIFICATIONS:**
- ★ Piano key selecting.
  - ★ Preselected tone control.
  - ★ Size: 12in. wide x 9in. deep x 2in. high.
  - ★ Weighs 9lbs.
  - ★ Finish: Hammered enamel in grey/green with gold trimmings. Controls and press buttons in cream with black, blue and red lettering.

- ★ Power Output 5 watts total (2 1/2 watts per channel).
- ★ Total harmonic distortion less than 1% at 1 watt output.
- ★ Frequency Response: 30 c/s to 40 Kc/s 2dB 45 c/s to 30 Kc/s 1dB
- ★ Sensitivity sufficient for all normal inputs from Tape Recorders, Pick-ups, Microphones, Radios.
- ★ Power requirements 110, 125, 150, 220, 240 volts A.C.

Why not convert your battery portable to mains operation with the **COSSOR MU2 BATTERY ELIMINATOR!** This Eliminator is completely assembled and supplied with 4ft of Mains Lead and Torpedo Type of On/Off Switch. It is housed in 2 Metal Containers approximately the same size as the AD35 and B126 Batteries, and suitable for receivers using DK96 range valves for use on 200-250V A.C. mains. Size: L.T. Unit 3in. x 2 1/2in. x 1 1/2in. H.T. Unit 4in. x 2 1/2in. x 2in. Original price 3 gns. **39/6** plus 2/- P. & P.

Front, back and side of lid  $\frac{3}{8}$ " softwood  
 Top of lid  $\frac{1}{8}$ " hardboard

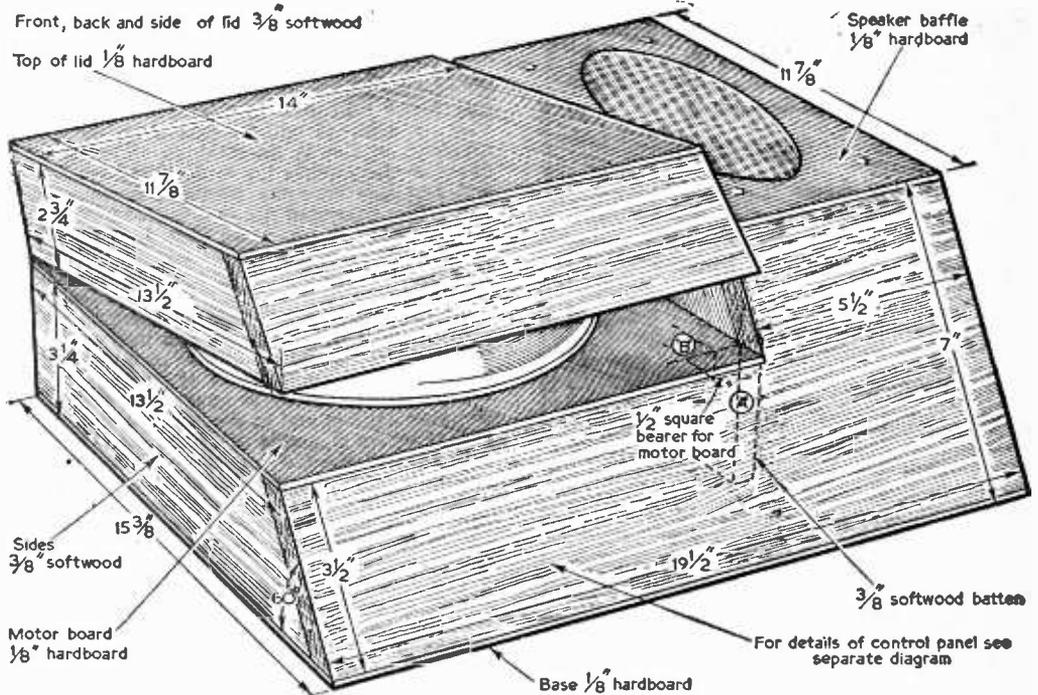


Fig. 20—General dimensions of the cabinet.

# A cabinet for the CITIZEN

(Continued from page 720 of the December issue)

**T**HE two sections of the "Citizen"—the I.F. amplifier and the oscillator—when correctly connected, form a superhet tuner which may be used with any suitable amplifier as a superhet receiver. Such an amplifier is the "Mini-Amp", a unit constructed on the same lines as the two "Citizen" units, and described in the November issue of P.W. [Details for connecting the three units will be given next month.—Ed.]

When the constructor has all three units built, one thing further remains to be done before he may congratulate himself on his success with this new receiver. A cabinet must be built to house the "Citizen", the amplifier, loudspeaker, the batteries and all the other various switches and controls.

Some readers may be individualists and will therefore want to make a cabinet to suit their own tastes and requirements. But for those to whom originality in design comes with difficulty, we

recommend them to follow the instructions given in this article, which will result in each becoming the proud possessor of a cabinet, which although simple in construction is, we consider, modern in appearance.

The reader will note that our design incorporates a record deck, which is connected to the audio amplifier section of the receiver. This feature alters the title of the complete set from "radio" to "portable radiogram", which is an instrument not met with very often, even on the commercial market.

### Construction

Most of the material to be used in the construction of the cabinet is  $\frac{3}{8}$  in. thick softwood; which is readily obtainable from any wood merchant. It is sold in standard widths, but as there is no piece of exactly the same dimensions as any other, there is little point in demanding wood of any particular width. Indeed it will be

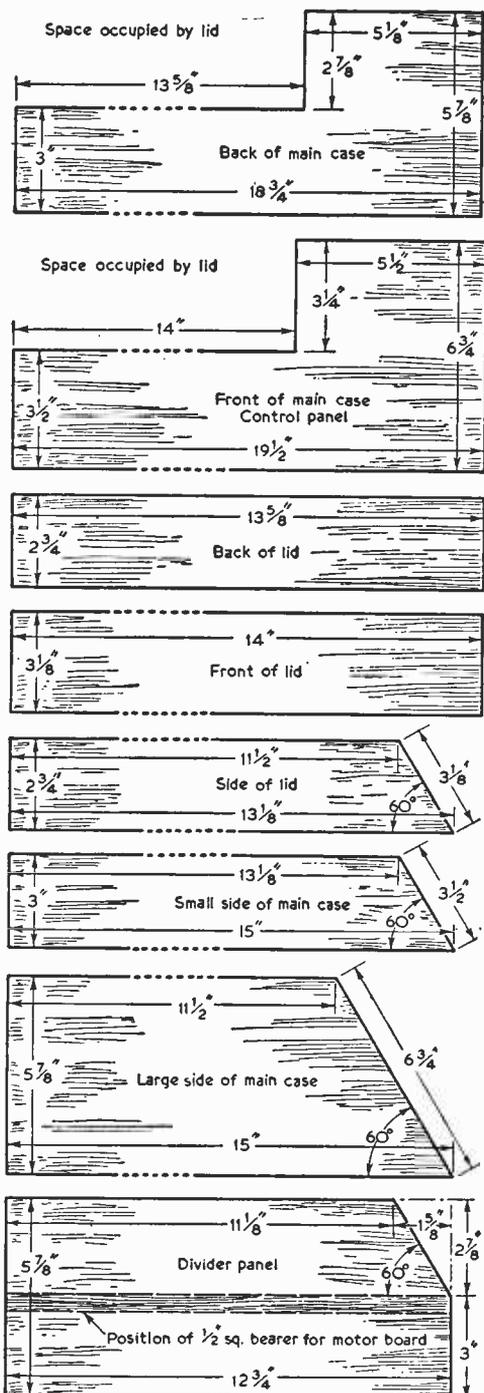


Fig. 21—Dimensions of the softwood sections of the cabinet. (Note: the lid requires only three sides—see Fig. 20.)

found less troublesome and less expensive to ask for off-cuts of softwood.

Fig. 20 is fairly self-explanatory so far as the dimensions of the parts are concerned. The control panel will have to be cut from a piece  $19\frac{1}{2}$ in. x  $6\frac{3}{4}$ in. It will be seen from the diagram that part of this is cut away to allow the motor board to drop below the level of the loudspeaker, and that this cut-away portion measures 14in. x  $3\frac{1}{2}$ in. This part need not be discarded as waste, as it only needs an  $\frac{1}{8}$ in. to be planed off for it to be used as the front portion of the lid. (The  $\frac{1}{8}$ in. is the allowance required by the thickness of the motor board.) When cutting the back—which has similar, but not identical dimensions to the control panel—the cut-away portion may be used for the back of the lid in a similar fashion to that used when making the front of the lid.

Fig. 20 only gives general dimensions of the complete cabinet and so the reader should refer to Fig. 21 where diagrams of all the individual pieces of softwood needed are given with their exact measurements. It must be noted, that the upper and lower edges of the control panel and the front part of the lid, have to be planed to an angle of  $60^\circ$  to the vertical to allow for the slope of the front panel.

The "divider", which is shown in detail in Fig. 21, separates the section of the cabinet which contains the loudspeaker from the record-deck section, and it also gives added strength to the whole construction as it will, at a later stage, be joined to the back, front and base of the cabinet. The divider is shown in Fig. 20 by dotted lines, and is labelled 'A' and referred to as " $\frac{1}{4}$ in. softwood batten". To this divider, a batten of  $\frac{1}{4}$ in. square wood is glued to support the motor board ('B' in Fig. 20; this runs the complete length of 'A' in the position shown. It will be seen from the diagram, that 'A' is not sawn to follow the slope of the control panel: this is to allow room for the component group-board which will eventually be positioned there (see Fig. 22).

The motor board is a rectangular piece of  $\frac{1}{4}$ in. hardboard, 14in. x  $13\frac{1}{2}$ in. A hole will have to be cut to suit the motor and speed control of the record deck. A smaller hole will also have to be drilled to take the support of the pick-up (Fig. 23).

The loudspeaker baffle is also of  $\frac{1}{4}$ in. hardboard and measures  $11\frac{1}{2}$ in. x  $5\frac{1}{2}$ in., and has an aperture cut to suit the loudspeaker (we suggest that for best performance with consideration to the design of the cabinet, an elliptical speaker is to be preferred). Expanded aluminium may be used to cover the aperture, and a convenient method of mounting the loudspeaker, is to sandwich the aluminium between the baffle and speaker when bolting the latter piece of equipment to the hardboard. It is also advisable to insert a strip of foam rubber or similar substance between the loudspeaker and the aluminium and to tighten the nuts and bolts holding it as far as possible. This will prevent cabinet vibration and acoustic feedback from becoming annoying. The reader will appreciate, from inspection of Fig. 23, that the motor board and loudspeaker baffle may be conveniently cut from one piece of hardboard.

The top of the lid and the base are cut from the same thickness of hardboard as the preceding two parts, and measure 14in. x  $11\frac{1}{2}$ in. and  $19\frac{1}{2}$ in. x  $1\frac{1}{2}$ in. respectively.

All parts of the cabinet should now be planed and sandpapered so that, when they are assembled and held with a few panel pins, they meet one another without any overlapping.

The sides, front and back of the cabinet may at this point, be finally assembled. A satisfactory way of joining the parts, is to glue them with one of the modern contact adhesives now on the market. A few panel pins may be used as well to give added strength, if the constructor thinks it necessary. The divider may now be "dropped" into position between the control panel and the back and glued there.

The lid is assembled in a similar fashion to the main cabinet, but it is at this point that the question of hinging the lid must be dealt with. A "hidden" hinge is the obvious solution, but if the constructor considers this beyond his ability, a hinge, simply screwed on to the back of the cabinet and the back of the lid, will not necessarily spoil the appearance of the finished case, being to the rear of the instrument.

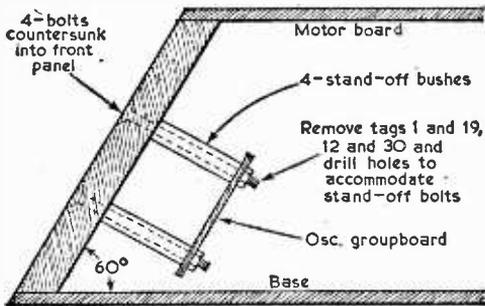


Fig. 22—The method of mounting the oscillator group board on the front panel of the cabinet.

**MATERIALS REQUIRED**

Approximately 7ft. of softwood, 7in. wide (or an equivalent length in off-cuts).

Four pieces of 1/8 in. hardboard :- 19 1/2 in. x 15 3/8 in., 14 in. x 13 1/2 in., 14 in. x 11 7/8 in. and 11 7/8 in. x 5 1/2 in. EMI 985 record player deck (battery operated version) and pick-up to match.

Elliptical Loudspeaker

PP9 batteries.

Control knobs, hinges, loudspeaker grille, etc.

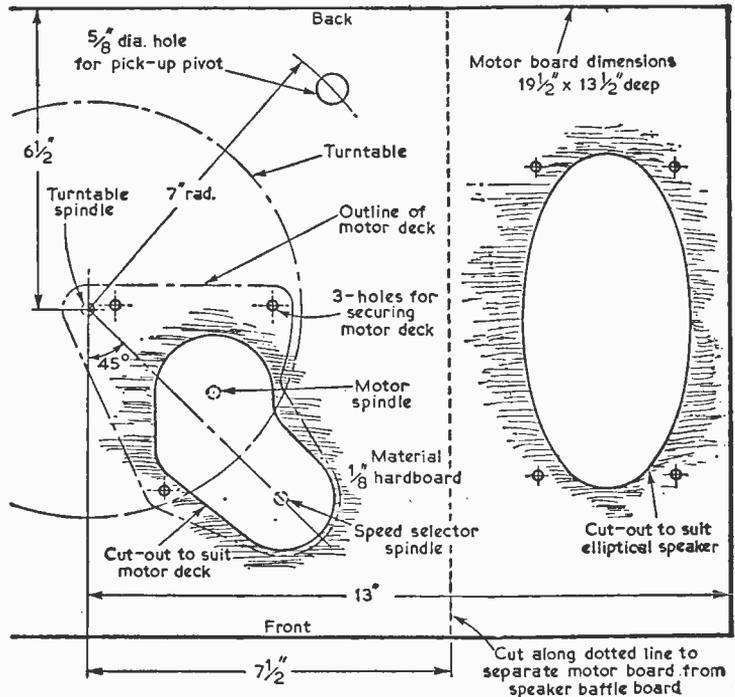


Fig. 23—Dimensions of the motor board and its cut-outs.

Three wood screws secure the motor unit to the motor board and the pick-up is held by a nut which is supplied with it, to suit the thread on the supporting column. The "arm rest", which is also supplied with the pick-up, is fixed to the motor board in any convenient position. It is not necessary, at this juncture, to place the turntable on its spindle, and as it is easier to handle the motor board without it, it is best secured at a later stage. The motor board should now be glued in position.

The speaker baffle, with the loudspeaker and the grille already in place, is now pinned and glued to the cabinet.

The lid should be fitted at this stage so that it will protect the motor and pick-up when the whole cabinet is turned over when wiring begins.

(To be continued)

FRIDAY, FEBRUARY 2nd, 1962

**A FILM SHOW**

(In collaboration with Mullard Ltd.)  
CAXTON HALL, WESTMINSTER  
at 7.30 p.m.

Send for your free tickets now marking your envelope "Caxton Hall" in the top, left-hand corner and enclosing a stamped addressed envelope (at least 3 1/2 in. x 6 in.) for the tickets.

The films to be shown are listed on the Editorial page (793).

The demand for tickets will be great; order yours NOW.

# Improving the All-band TRF

## ADDING AN R.F. STAGE

By J. L. Wain

(Continued from page 715 of the December issue)

**I**NSTRUCTIONS on mounting C8 to the front panel concluded the article last month. The band-spread condenser (C8) is fitted with a slow-motion drive and, for appearance sake, the pointer is placed behind the panel and viewed through an aperture. A piece of  $\frac{1}{8}$ in. Perspex is used to cover the aperture in the front panel. This was marked

out with a scribe and compasses and cut out with the aid of a coping saw, but a fret saw will probably do the job just as well. The edges can be bevelled with a file and draw-filed, then finished with fine emery paper, to give a professional effect.

Another piece of aluminium  $7\frac{1}{2}$ in. x 6in. was next cut to shape and fitted behind the aperture so that a suitable dial could be affixed. A short length of heavy gauge wire is painted red to act as a pointer. It should be suitably bent so it can be fixed to the slow-motion drive, and have a clearance of about  $\frac{1}{16}$ in. from the front panel.

### Coils

The detector coil switching is straightforward (see Fig. 1). Three short-wave coils were used and one medium.

The detector coils are wound on  $1\frac{1}{2}$ in. formers and are as follows: for 18m to 30m, 11 turns of 22s.w.g. enamelled copper wire occupying  $1\frac{1}{2}$ in. with the cathode tap half a turn from the earthed end, and six turns for the primary.

The 30m to 60m coil is wound with 20 turns of 22s.w.g. wire occupying  $1\frac{1}{2}$ in. with the tapping three-quarters of a turn from earthed end and with 16 turns for the primary.

For 60m to 100m, 35 turns of 24s.w.g. are used, with the tap  $1\frac{1}{2}$  turns from the earthed end, and with 20 turns for the primary.

The medium wave coil is wound with 93 turns of 32s.w.g. wire with the tap three turns from the earthed end and with 50 turns for the primary.

The primaries of all the coils can be wound with 26-30s.w.g. wire, and about  $\frac{1}{2}$ in. should be left between this winding and the earthed end of the tuned section.

The short-wave aerial coils are wound on  $\frac{1}{2}$ in. formers with dust cores: for 18m to 30m, 20 turns of 24s.w.g.; 30m to 60m, 30 turns of 26s.w.g.; 60m to 100m, 50 turns of 26s.w.g.

The medium wave aerial coil was made from a small I.F. transformer.

### Finishing the Set

The front panel was given a black crackle finish and transfers were used to put the necessary wording under each control. Ordinary clear Perspex protractors, with a piece of white paper behind them were used as dials, for the band-set and aerial coil tuning. The completed receiver was installed in an aluminium case with power pack, L.S. and amplifier sockets mounted at the side. If desired, there is ample room to instal a small speaker at the side of the receiver.

To operate the set, turn the aerial switch to R3 position, and advance the reaction control so that the set is just on the point of oscillation. Tuning is carried out by the 15pF condenser and the 100pF bandset condenser can be moved ten degrees at a time, breaking each waveband into smaller wavebands, which are covered with the 10pF condenser. ■

### COMPONENTS LIST

#### Resistors ( $\frac{1}{2}$ W, 10%)

R1	22k	R2	2.2M
R3	470k	R4	100 $\Omega$
R5, R6	100k	R7	22k
R8, R9	47k	R10	270k
R11	270 $\Omega$	R12	3.3k
VR1	100k pot.—R.F. gain		
VR2	50k pot.—Reaction.		
VR3	500k pot.—Volume		
VR4	25k pot.—Top cut		

#### Condensers:

C1	50pF variable condenser (with isolated spindle if an aluminium panel is being used)
C2	300pF variable condenser
C3, C4, C5	0.1 $\mu$ F
C7	100pF
C8	10pF
C6	50pF
C9	500pF
C10, C13	0.01 $\mu$ F
C11	16 $\mu$ F 350VW
C12	8 $\mu$ F 350VW
C14, C15	25 $\mu$ F, 25VW
C16	2000pF
C17	0.05 $\mu$ F
C18	0.1 $\mu$ F
C19	16 $\mu$ F 350VW
C20	8 $\mu$ F 350VW
C21	0.1 $\mu$ F 350VW

#### LF smoothing choke

Output transformer to suit loudspeaker

Mains transformer 5V 2A, 6.3V 2A, 250V 60mA

S1A, S1B 2-pole, 5-way wave-change switch

S2 3-pole, 4-way wave-change switch

S3 S.P.S.T. switch (mains off-on)

S4, S5 S.P.S.T. switches

Valves EF39, 6J7, 6S5, 6V6, 5Z4

# RECORDING LEVEL INDICATORS

## MONITORING MODULATION DEPTH

By J. Smith

**T**HE most well-known type of recording level indicator is the "magic eye" which makes use of a cathode ray tuning indicator. The magic eye will close or open with an increase of grid voltage; some of the modern types open with an increase in voltage whilst others, of the older variety, close. Amongst those most often used are the 6E5, 6U5/6G5, EM34 and the more recently developed EM80, EM81, UM80 and the DM70. The latter has a 1.4V filament and lends itself to use in battery-operated recorders.

In the magic eye system, two types of circuit are probably the most common. Fig. 1 shows the circuit where the grid of the magic eye is connected to an audio connection in the recorder.

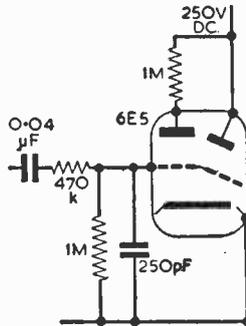


Fig. 1—In this circuit, the grid of the magic eye is connected to an audio connection in the recorder.

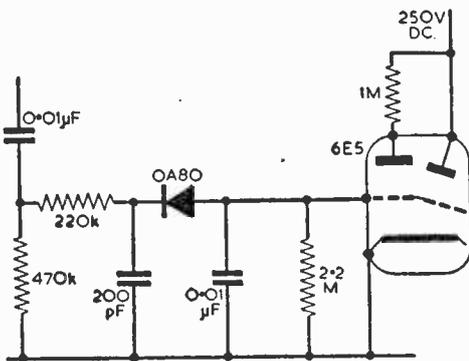


Fig. 2—This circuit is usually connected to the recording output.

recorder. The circuit of Fig. 2 is generally found connected to the recording output valve; the diode (OA80) is to remove the H.F. bias supply and give a slight delay to the magic eye shadow. The audio passes to the grid of the eye and the effect of the audio (without the bias) is seen on the magic eye. The values given are to be taken as approximate — they depend on the type of circuits used in the recorder. The diode used should have a high reverse resis-

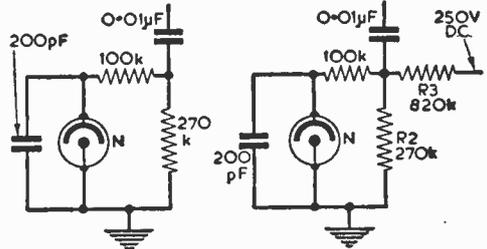


Fig. 3—A simple indicator circuit using a neon.  
Fig. 4—A neon indicator circuit with bias.

tance. It should also be noted that the fluctuations in modulation shown with the circuit of Fig. 2 will not be so obvious as with the circuit of Fig. 1. The valve shown is the 6E5 or equivalent; other valves will work excellently, but the EM34 would require more components than the 6E5 since it is a "clover

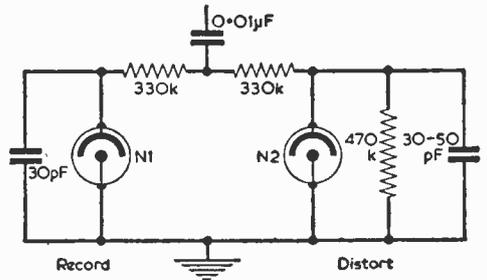



Fig. 5—A circuit using two neons; one for record and one for over-record.

leaf" type having more segments to the indication.

Another type of level indicator uses neons. Here, a simple neon is connected in the circuit and flashes according to the audio level. Fig. 3 shows a simple circuit. This is connected to the audio valve feeding the recording head and the neon chosen has a much lower extinction voltage than firing voltage. If the audio is not sufficient to ignite the neon, bias can be introduced by a D.C. voltage (see Fig. 4). Another version uses two neons, one for record and one for "over-record". Sometimes, these are known as "Record" and "Distort" neons, one neon lighting on peaks corresponding to correct modulation level and the other lighting on levels which would result in over-recording. In Fig. 5, N1 is the "record neon", which flashes only on peaks, and N2 is the "over-record" or "distort" neon. In this circuit, N2 requires a much higher audio voltage than N1 before it flashes. ■

By M. L. Michaelis

# POWER-P

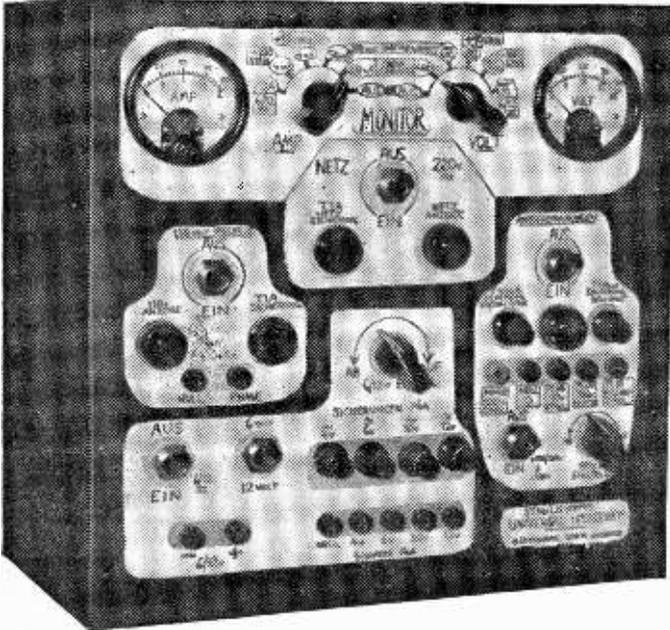

The author's unit

**T**HIS design uses, as a starting point, the excellent stabilised power supply described in the August 1961 issue by J. W. Adams.

### Modifications and Additions to Basic Circuit

The stabilised H.T. power supply in the August 1961 issue contains all the essentials for an effective and efficient unit, but no more than that. In a more advanced unit, which is the subject of this article, the following points should receive consideration:—

(a) The power supply will be used for experimental work, to feed power to "breadboard" circuits under test. Under such circumstances short-circuits can often occur, and some measure of protection against these is desirable.

Upon shorting the output of Mr Adams's circuit, several hundred milliamperes were found to flow, which could rapidly damage the valves. Fuses in the output would give some measure of protection, but the difference between rated current and immediate fusing current is too great, so that a fuse does not give sufficient protection against partial short-circuits. Apart from this, there is the trouble and expense of repeatedly renewing blown fuses.

The author's aim in the present circuit was to make the unit electronically self-limiting, so that

A UNIT FOR THE ADVANCED CONSTRUCTION IS TO BE DESCRIBED OF THE THEORETICAL DEVELOPMENT

the short-circuit output current is little more than the maximum rated current, and thus shorting the output terminals for even considerable periods can do no damage. This aim has been achieved.

(b) The present circuit has been devised for using only a single series valve, an EL34, instead of two 6L6 valves in parallel. The valve rectifier has been replaced by small flat metal rectifiers. These measures reduce heating and save considerable space, so that the new circuit items could be added, and their heat-dissipation tolerated, without undue increase in size of the whole apparatus.

(c) The circuit has been trimmed to give adequate voltage and current output for all normal purposes, yet use a normal 350-0-350V H.T. winding on the transformer, which is easily obtainable.

(d) A stabilised negative grid-bias output of approximately 100V has been added.

(e) A separate extra H.T. output of approximately 300V at 50mA has also been added. This is not stabilised, and serves to feed all parts of apparatus not requiring stabilised H.T. The stabilised output is therefore fully decoupled from other parts of the circuit, and is not loaded higher than is really necessary. This makes the whole power supply even more versatile for the experimental workshop.

(f) Not only have A.C. 6.3V heaters been catered for, but A.C. outputs of a number of other common heater voltages are provided. Also a smoothed D.C. heater output is supplied.

### Modified Stabilised H.T. Supply

The circuit of Fig. 1 was connected up experimentally. The two 6L6 valves of Mr. Adams have been replaced by a single EL34, and his EF80 is replaced by one half of an ECC83, the other half of which is to be used later for the short-circuit limiting function. In this circuit, the stabilisation is good up to 75mA to 100mA at all output voltages from 150 to 300. The internal impedance of 1150Ω, which the transformer, rectifier and smoothing alone had, has been reduced to about 50Ω, representing a stabilisation factor of about 23 (ratio of internal impedance of power supply before stabilisation to that after stabilisation). This is adequate for the normal experimenter.



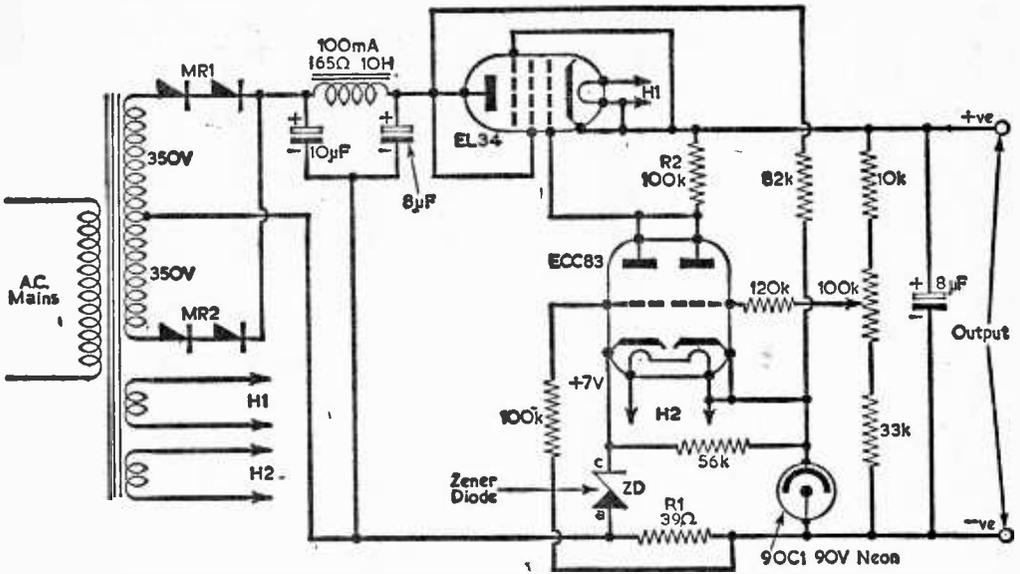


Fig. 2—The basic circuit with the addition of a current limiting device (which proved unsuccessful—see text).

The performance of this circuit is shown in Fig. 4, and is very pleasing indeed. Within the rated output current range for all voltages from 150 to 300 the stabilisation is good, representing an internal impedance of about 40Ω. As soon as the rated current of 100mA is exceeded, the internal impedance rises to 12,500Ω, and limits the short-circuit current to a mere 120mA under all circumstances, which is still within the peak rating of all components.

The two neons N2 and N3 supply two voltages negative to chassis, of about 90 and 108 volts respectively. The smaller is fed to the cathode and the larger to the grid of the limiter-half of the ECC83, thus normally cutting it off.

The output current flows through R1, causing a voltage drop across it which raises the grid voltage of the limiter-half of the ECC83. The value of R1 is so chosen that at about 100mA output current the limiter valve just reaches cut-on.

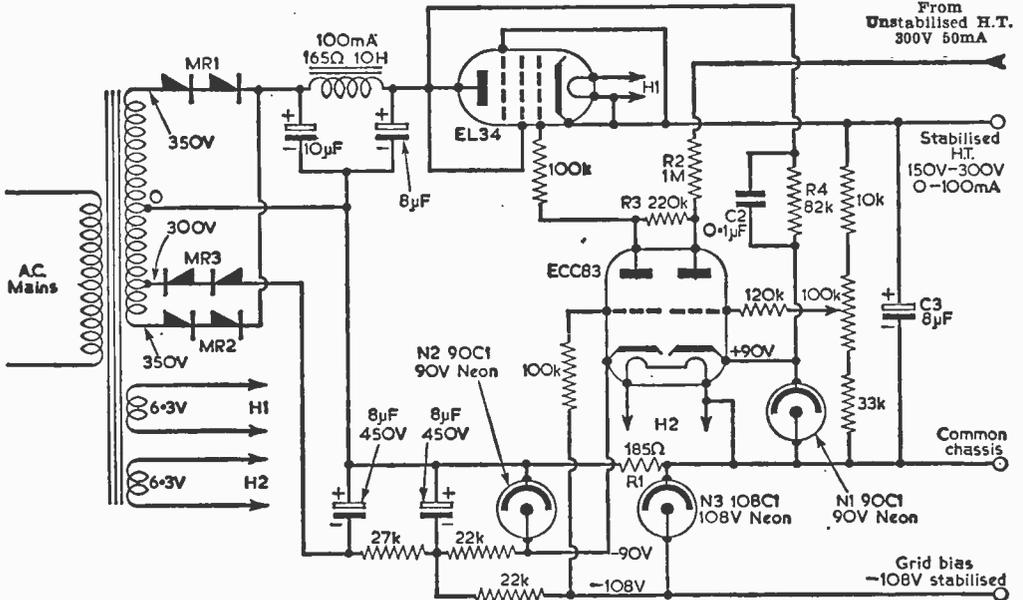


Fig. 3—The advanced stabilising circuit with the addition of an effective current limiting circuit.

At 120mA output current, the limiter valve anode current has risen sufficiently to drive the anode about 14V negative to chassis, which is the bias required to limit the EL34 to 120mA. This represents the short-circuit current, which can never be exceeded.

The very large value for R2 was found to be essential for two reasons. Firstly, the voltage at the anode of the limiter triode section in the limiting condition is very low and thus only small anode current can flow. But this small anode current must cause a drop across R2 right from plus 350V down to minus 14V. Thus, R2 must be very large. Secondly, for the lower output voltages, the right-hand anode of the ECC83 must go down below such output voltages, and this is

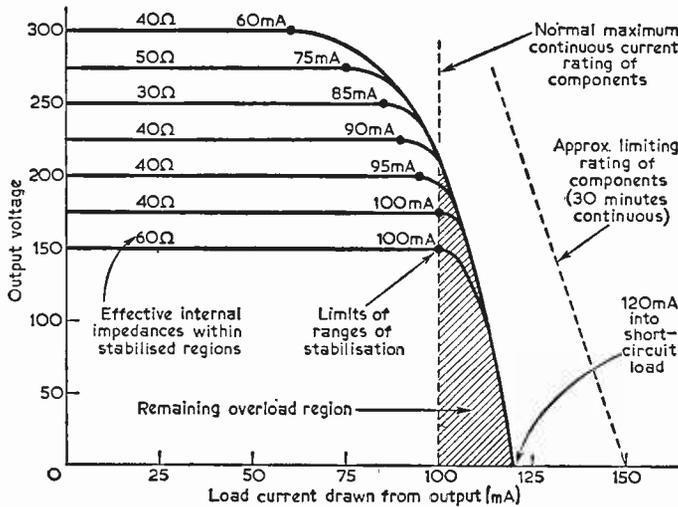


Fig. 4—Performance graph of the circuit of Fig. 3 with R1 having a value of 185Ω. (When R1 was made 150Ω, merely the overload region was increased, so that the short circuit current was 147mA; when R1 was made 200Ω, the overload region was entirely removed, and the short circuit current was only 110mA, or less. However, cut-off then encroaches on the available stabilised region. It may thus be seen that R1 is critical and that 185Ω is the optimum value.)

The 50c/s ripple of the output was 0.25% r.m.s. approximately, regardless of the voltage or loading.

required to be achieved for small anode current, so that the right-hand grid of the ECC83 may still be sufficiently negative to prevent grid current, which would otherwise disturb the voltage-comparison, and thus destroy the voltage-regulation at the lower voltages. Again, the requirement is that R2 be large. The value of 1M, shown in Fig. 3, was found to be optimum.

**Independent Supply**

It is seen that the already mentioned further output, the unstabilised 300V H.T. output, has been used to feed the ECC83 as well. This ensures that the ECC83 always has a high and independent H.T. supply, even when the stabilised H.T. output is low; thus the ECC83 can always amplify well, which very considerably improved the stabilisation of the lower stabilised output voltages.

A separate small mains transformer is used in the final circuit, to be given next month, and contributes to the high decoupling, so that really sensitive apparatus may be fed from the two supplies simultaneously without interference. The assortment of heater windings present on the two transformers enables the provision of the already mentioned generous range of heater voltages to be made.

Some slight tendency to indefinite instability was present until R3 was inserted. There remained a definite oscillation at 10kc/s over certain ranges of output current, and this was traced with the oscilloscope, and found to be a sawtooth of small amplitude between R4, the neon, N1, and the stray capacities. It was found that C2 shunted across R4 removed all inclination for such oscillation. It was not found necessary to shunt such condensers across the feed resistors of the other neons, but in the final circuit to be described in the second part of this article, they will be included for safety.

**Measurement of Characteristics of Final Circuit**

Fig. 4 shows the static D.C. performance of the final circuit graphically. There are, however, other features apart from the static D.C. performance, which are of vital importance in deciding the ultimate value of a power supply. The chief of these is the dynamic internal impedance, which determines the r.m.s. output voltage ripple caused when fluctuating (A.C.) current is drawn, e.g. the anode current of a valve heavily driven with a sine wave at the grid. This just mentioned example provides the simplest way of measuring this dynamic internal impedance of a power supply, as shown in Fig. 5. R5 is chosen to be approximately equal to the expected dynamic impedance, R. The 6V6 valve is fed with a sine wave from a signal generator, of amplitude within the undistorted range of amplification. Via a suitable condenser, an oscilloscope is connected first between A and chassis, then between B and chassis, and the ratio of the heights of the two waveforms is observed. The ratio A divided by B is clearly equal to the ratio (R plus R5) divided by R, so that the dynamic internal impedance of the power supply, R, is easily calculated to be

$$R5 \text{ divided by } \frac{A}{B} - 1 \text{ ohms.}$$

The dynamic impedance is not necessarily equal to the static D.C. internal impedance, since the power supply contains not only resistors but also condensers and inductances, which make the A.C. behaviour in general different from the D.C. behaviour. Too large a value for C3 in Fig. 3

can give the voltage-stabilisation too large a time-constant, so that in fact the low-frequency performance may suffer. On the other hand, too small a value of C3 will block even the higher frequencies inadequately. Thus there is a definite optimum value for C3, which one may consider that one has reached when the low-frequency dynamic impedance is equal approximately to the static D.C. internal impedance, and when this dynamic impedance falls steadily, without a maximum at any frequency, as the frequency is increased. The value shown for C3,  $8\mu\text{F}$ , was found to be optimum with the components used. If there is a maximum in the dynamic impedance at a certain frequency, due to incorrect choice of C3, then it is under certain circumstances possible

extent of stabilisation against mains voltage fluctuation. With the circuit of Fig. 3 it was found that 25% fluctuation of mains voltage, even rapidly, or very slowly, produced no output fluctuations exceeding about 2%, for any set output voltage or current within the rated ranges. There is thus a stabilisation factor of 25 divided by 2, i.e. about 12, present with respect to mains voltage fluctuation. For smaller mains voltage fluctuations, the output fluctuations were even smaller. A 10% mains voltage fluctuation produced only  $\frac{1}{3}\%$  output fluctuation in most cases, representing a stabilisation factor of 30.

### Ripple

A final important characteristic is the remaining mains ripple. It is not possible to make measurements here on a breadboard lash-up, as hum is there introduced on to the grids of the ECC83 regulator valve, which could well be less in a final layout. But, as a matter of interest, the r.m.s. ripple in the experimental circuit was found to be 0.25% at all output voltages and currents. This is easily measured with a calibrated oscilloscope connected in parallel with the output terminals.

(To be continued)

## POWER FOR TRANSISTORS

(Continued from page 804)

components, therefore, are small, and, as the unit will not have to handle any excessive current, it may be fitted into a small box without much fear of overheating. In the original, the unit was housed in a small metal box obtained from a tobacconist (it was originally a lighter fuel tube container which was not only small but had sufficient strength to withstand the average workshop accident, and would fit into the battery space in most portable receivers with little trouble). The container should be metal, otherwise if it were placed in a receiver, the hum from the transformer would be collected by the receiver and appear in the A.F. output. If it is wished to make an existing transistor portable receiver into a mains-operated set, then the circuit shown in Fig. 1 is advisable, but if the unit is to be used for experimental purposes, then the circuit of Fig. 2 is advisable, and a voltmeter can be connected into it, as well as a milliammeter if desired, either in the case or by means of wander-plug sockets.

The output of the unit can be derived through a potential divider network, as shown, or through a suitable variable resistance, but it is advisable to connect either a current-operated fuse or a meter overload-trip into the unit so that only the current needed and no more can be drawn, in order to protect the transistors.

The output allows for permanent sockets for 1.5V and 10.5V, as these are needed by several of the currently popular transistor testers.

It is most important that the output voltage of the unit should be adjusted to suit the transistor set with which it is to be used. It would be as well to monitor the output voltage on load with a suitable meter.

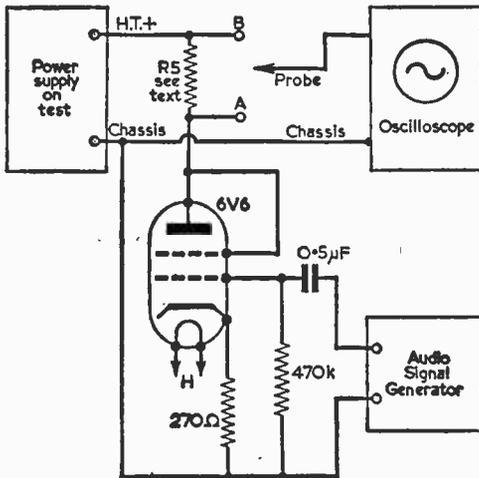


Fig. 5—Method of measuring dynamic internal impedance.

that instability could be caused at that frequency. This instability could manifest itself merely as undue distortion of waves containing that frequency, in an amplifier fed from the power supply, which could prove very puzzling if one were not aware of this point.

### Variation of conditions

The circuit of Fig. 3 was found to have the same value of about  $40\Omega$ , for the dynamic internal impedance, as was found for the D.C. static internal impedance, for all frequencies up to about  $1\text{kc/s}$ , and for all frequencies above  $2\text{kc/s}$  it was well under  $20\Omega$ .

It is the dynamic internal impedance which is finally decisive for the degree of non-interference of various items of apparatus fed simultaneously from the power supply. It represents the remaining common coupling resistance between the various circuits fed. Thus it is desirable that it be made as small as possible.

The static D.C. internal impedance is simply given at all times for any range of output current as voltage fall over the range (volts) divided by length of the range (mA), multiplied by a thousand. The result is in ohms.

A further characteristic of importance is the

# FAULTS IN VHF/F.M. RECEIVERS

## 3—The Final Stages

By G. J. King

(Continued from page 729 of the December issue)

**I**N last month's instalment we considered the I.F. stages. We now come to the final stages of the combined A.M./F.M. receiver, namely the detector, A.F. amplifier, output and rectifier. These stages are given in the circuit in Fig. 9. Valve V4 (EABC80) is a multi-electrode device developed specially for combined A.M./F.M. receivers. As in the circuit, it is usually employed as A.M. detector AGC ratio detector for F.M. and A.F. amplifier for both services.

The EL84, V5, is a high-slope output valve, the EZ80, V7, is the H.T. rectifier and the EM34, V6, is the magic-eye tuning indicator.

### Two I.F. Transformers

The second I.F. transformer (IFT2) is a composite component which carries both the ratio detector windings for F.M. and the ordinary A.M. windings for feeding the diode detector. When the set is switched to A.M. the ratio detector primary (L27) offers a low impedance to the A.M. I.F. signals which are thus developed across

the primary of the A.M. I.F. transformer (L25) and induced into the secondary (L26). The A.M. I.F. signals thus arrive at the A.M. detector diode, which is on pin 6 of V4.

The A.M. detector load is R27 and the associated reservoir capacitor is C56. It is across this load that the A.M. A.F. is developed, and this is conveyed via switch S1b, the bass control and the volume control to the grid of the triode section of V4. The signals are amplified by that valve and reappear across the anode load R24.

### A.M. AGC

Some of the I.F. signal at the primary of the A.M. I.F. transformer (L25) is fed through C50 to the rectifier WX6. A D.C. voltage is developed across the rectifier load R19, the value of which is proportional to the signal strength. This voltage is negative with respect to chassis and is filtered by R18 and applied as a control bias to the AGC controlled valves.

Moreover, the D.C. component of the detected signal across the detector load R27 is conveyed to the grid of the magic-eye through R29 and R40. This causes the "eye" to close when the set is properly on tune. C66 is simply a decoupling or filter capacitor to remove any I.F. signal that may be present at the grid of the "eye."

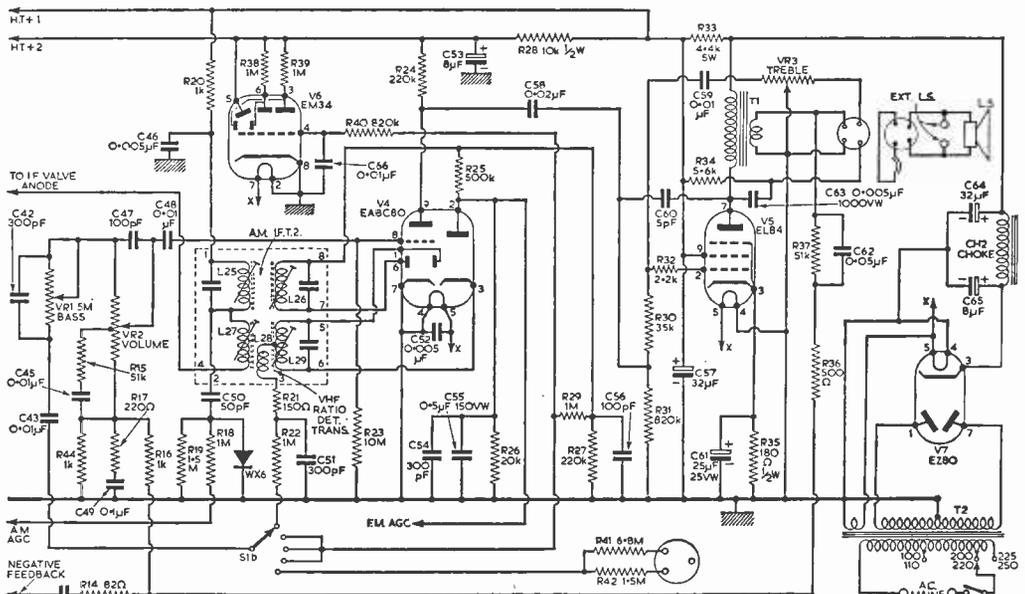


Fig. 9—The circuit diagram of the detector, AGC, A.F., output and rectifier stages of a combined A.M./F.M. receiver.

### The Ratio Detector

When the set is switched to F.M., the A.M. I.F. transformer primary (L25) offers a low impedance to the F.M. I.F. signal which is thus developed across the ratio detector transformer primary (L27) and induced into L28 and L29. The F.M. I.F. signal is applied across the cathode and anode of two separate diode sections in accordance with normal ratio detector practice, and to facilitate the description of this section of the circuit the ratio detector has been extracted from Fig. 9 and redrawn in Fig. 10 with the same component references.

From this it is easy to see how the ratio detector is derived. L28 is the ordinary tertiary winding in the ratio detector transformer, while R26 is the ratio detector D.C. load. C55 is the time-constant capacitor, while C54 in parallel eliminates unwanted I.F. signal. The detected F.M. signal is developed across C51, in series with the tertiary winding, and this is fed through the filter R22, switch S1b, the bass control and the volume control to the grid of the triode section in V4, the same as with the detected A.M. signal. Switch S1b is ganged with the A.M./F.M. changeover switch, of course, and simply selects the output from the detector which is in use. The required de-emphasis is given by the time-constant of C51 and R22 in the A.F. feed circuit.

### F.M. AGC

The voltage across the ratio detector D.C. load resistor R26 is used, relative to chassis, as an F.M. AGC potential. This voltage is negative with respect to chassis and is at a maximum when the F.M. signal is correctly tuned.

A fraction of the same voltage is taken through R25, R29 and R40 to operate the magic-eye tuning indicator on F.M.

### A.F. Circuits

From the foregoing description it will be understood that so far as the triode A.F. amplifier stage is concerned this receives the detected audio whether it be A.M. or F.M. derived. The amplified A.F. is developed across the triode anode load R24 in each case and from there is fed to the control grid of the output valve through C58, R30 and R32.

A small amount of negative feedback is provided by the anode to grid coupling capacitor C60. As this feedback occurs mostly at high audio frequencies, the arrangement gives a degree of tone compensation. The high-frequency speaker is energised from the anode of the output valve through C63 and the power here is controlled by VR3 which is in fact the treble control. A full negative feedback loop is also provided from the secondary of the speaker transformer to the grid of the A.F. triode via R36, R37 and C62.

### Power Supply

In this particular set, a double-wound mains transformer provides complete mains isolation and full-wave rectification is employed. C65 is the rectifier reservoir capacitor and smoothing is accomplished by the choke CH2 and the smoothing electrolytic C64. To remove all traces of hum and

to provide the required H.T. distribution, additional filter circuits are incorporated, such as R33 and C57 and R28 and C53.

The heaters of all the valves, including the rectifier, are energised from a 6.3V winding on the mains transformer. One side of this power source is connected to chassis while the other side is common to all heaters.

### No Signals

Complete failure of both services is sometimes caused by trouble in the EL84. This is immediately indicated by the magic-eye tuning indicator operating normally when the set is tuned over either A.M. or F.M. stations. Such a symptom would, of course, indicate that all stages prior to the A.F. amplifier, including the detectors, are working correctly. Since the detectors are working it is unusual for the triode A.F. amplifier to be at fault, so the most likely cause of the trouble is the output valve or associated components, such as the speaker transformer.

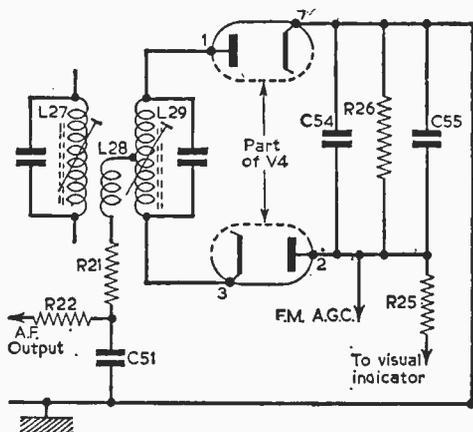


Fig. 10—The ratio detector section from the receiver shown in Fig. 9 with the same component references.

### Low Sensitivity

One receiver brought in for service with "low sensitivity" was subjected to the usual tests and very little could be found wrong. The emission of the valves was slightly below normal, but replacements did not help matters. It was later observed that the I.F. valve appeared to be hotter than normal. The bias was checked and the control grid was found to be slightly positive with respect to the cathode. A check on the AGC line eventually brought to light a leak in the capacitor coupling the AGC rectifier to the I.F. signal source. In Fig. 9 this would be C50, and as it is connected to a point of H.T. positive, as well as signal, a leak would reflect a positive voltage on the AGC line and thus on to the control grids of the controlled valves. The action of the rectifier prevented a high rise in positive voltage, but that which found its way to the valve grids was sufficient to destroy the normal sensitivity.

(To be continued)


# TEST METERS FOR EVERY PURPOSE & POCKET



**1,000 O.P.V. Model U.I.** Reads A.C. & D.C. Volts up to 1,000; D.C. Current to 500 mA; Resistance to 200K. Basic movement 300µA. Easy to read open scale. Size 5 1/2 in. x 3 1/2 in. x 2 1/2 in. **£2.19.6**



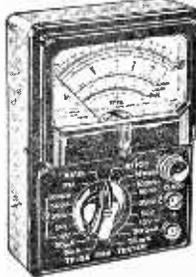**2,000 O.P.V. Model TP-10.** Reads A.C. & D.C. Volts up to 1,000; D.C. Current to 500mA; Resistance to 1 Meg; Capacitance to 1µF; Decibels from -20 to +36; Output jack for Audio Measurements. Size 3 1/2 in. x 5 x 1 1/2 in. **£3.19.6**



**20,000 O.P.V. Model TP-5S.** Reads voltages up to 1,000 D.C. at 20,000 Ohms per volt and A.C. at 10,000 o.p.v.; D.C. Current to 500mA; Resistance to 10 Megs; Capacitance to 0.1µF; Decibels from -20 to +36. Size 3 1/2 in. x 5 1/2 in. x 1 1/2 in. **£5.19.6**



**30,000 O.P.V. Model 500.** Volts to 1,000 D.C. at 30,000 O.P.V. A.C. at 20,000; 12 Amps D.C. Current; 20 Megs Resistance; -20 to +56 Dbs; Internal buzzer short circuit warning. Size 3 5/16 in. x 6 5/16 in. x 2 1/2 in. **£8.19.6**

All Brand New stock, with test leads, prods. and internal batteries. Fully guaranteed. S.A.E. further details.

**CRYSTAL CALIBRATOR No. 10.** A superb Crystal Controlled Wavemeter just released by the Ministry of Supply. Has directly calibrated dial for nominal coverage of 5-10.0 Mc/s. but may actually be used from 500 Kc/s. up to 30 Mc/s. Complete with 500 Kc/s. Crystal 2 valves type 1T4, 1 or 1R5 and 1 of CV286 (Neon Stabiliser), and Instruction Book. Size 7 in. x 7 1/2 in. x 4 in., weight 5 lbs. Used but in first class condition. **ONLY £2.19.6.** Carr. 3/6.

**B.C. 221 FREQUENCY METERS.** The famous American crystal controlled, portable frequency measuring standard. Coverage 125 kc/s-30 Mc/s. With original calibration book. Perfect order. Illustrated details on request. **ONLY £16.**

**10/- CONSTRUCTION PARCEL.** 10 yards each of 6 colours wiring wire, solder, 24 each assorted Resistors and Condensers.


**RESISTORS.** 100 assorted values. **NEW 10/-**  
**CONDENSERS.** 100 assorted mica and silvermica. **NEW 12/6.**  
**SPRAGUE CONDENSERS.** Metal cased, wire ends. New 0.01 mfd. 1,000 volt, and 0.1 mfd. 500 volt, 7/6 per dozen. Special quotes for quantities.

**MINIATURE MOTORS.** Ideal for models. Operates on 3-6 v. D.C. Size 1 1/2 x 1 x 1 1/2 in. plus tin spindle. **BRAND NEW 5/-.**


**PCR COMMUNICATIONS RECEIVERS**

Manufactured by **Pye & Philips.** One of the Army's most versatile and sensitive sets. RF stage and 2 of I.F., using 6 British I.F. type valves. Large 180 degrees illuminated and Calibrated Dial. Flywheel Tuning with locking device. Aerial Trimmer, Tone and Vol. Controls. Band switch front panel jacks for speaker or phones. In black metal case, size 17 in. L x 8 in. H. x 1 1/2 in. D. Model PCR covers 6-18 Mc/s, 200-550 metres and 850-2,000 metres, and has internal 5 in. speaker. REME reconditioned. **AS NEW £6.19.6.** Model PCR has similar L & M waveband coverage. Short wave 8-22Mc/s, but no speaker. Used, but excellent condition **£5.19.6.** Every receiver aerial tested before despatch. Add 10/6 carr. all models. Designed to operate from bulky EXTERNAL power supply, but any set can be fitted with BRAND NEW COMPONENTS INTERNAL PACK for 200/250 v. A.C. at an extra cost of **£2.** S.A.E. FOR ILLUSTRATED LEAFLET

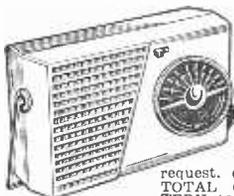**"P.W." 6 TRANSISTOR PERSONAL RECEIVER**



Designed by the technical staff of *Practical Wireless*; easy to build, using printed circuit and 1st Grade Matched Transistors and Diode. Full Medium and Long Wave coverage to internal speakers. All parts sold separately (new components only) enabling you to buy as required, and full detailed price list will be sent on request. Constructional details 1/6. **TOTAL COST INCLUDING BATTERY AND CABINET £8.19.6.**

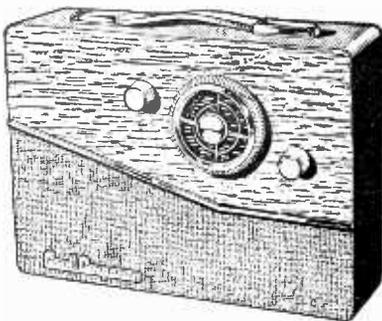

**"THE GOOD COMPANION"**

**THE FINEST COMBINED PORTABLE & CAR RADIO YET DESIGNED FOR THE HOME CONSTRUCTOR**

- ★ 750 mW output.
- ★ 6 transistors and 2 diodes.
- ★ Full Medium and Long Wave coverage.
- ★ Quality speaker.
- ★ Pre-aligned I.F.T.'s.
- ★ Brilliantly styled 2 tone cabinet, size 11 x 8 x 3 ins.
- ★ Very fine tuning with calibrated dial.
- ★ Latest Printed circuit.
- ★ Internal high gain aerial, with car aerial socket.
- ★ Easy to follow construction data (available separately 3/6.)

All parts sold separately and full illustrated details will be sent on request.


Total cost **£9.19.6** plus 5/- post and ins. (Battery 3/6 extra.)

**"POCKET 4" TRANSISTOR RECEIVER**

Attractive cabinet as illustrated for "P.W. 6". Uses miniature speaker, proper tuning condenser, and volume control. Built-in aerial makes unit efficient and portable. Ideal for the beginner. Full medium wave coverage. All components for only 42/6 (p. & p. 2/6). Ten-page constructional book free with parts or separately 1/6. S.A.E. for parts price list.

**HARRIS ELECTRONICS** 138 Gray's Inn Road, London, W.C.1  
(LONDON) LTD (Phone TERMINUS 7937)

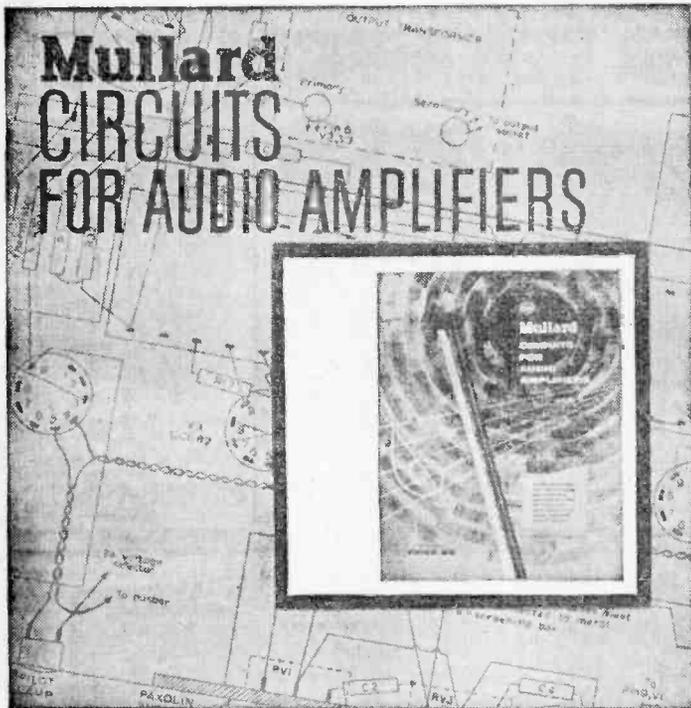Please include carriage costs on All items (Open until 1 p.m. Saturdays). We are 2 mins. from High Holborn (Chancery Lane Station) and 5 mins. by bus from King's Cross.



**A BOOK EVERY ENTHUSIAST WILL WANT!**

This Mullard publication is a practical manual for every audio enthusiast. In addition to describing twelve of the most popular Mullard circuits, it has introductory chapters on many of the theoretical and practical aspects of high quality sound reproduction. Whether you are interested in disc or tape, monaural or stereo, you will find that "Circuits for Audio Amplifiers" gives you just the sort of information you need. This informative book costs only 8/6 (U.K. price). The demand for it is high, so get your copy now from your radio dealer, or order direct from Mullard Ltd. (postage and packing 1s. 0d. extra in U.K.).

MULLARD LIMITED · MULLARD HOUSE  
TORRINGTON PLACE · LONDON W.C.1


MVM4005

**JACKSON**

the big name in PRECISION components

Precision built radio components are an important contribution to the radio and communications industry.

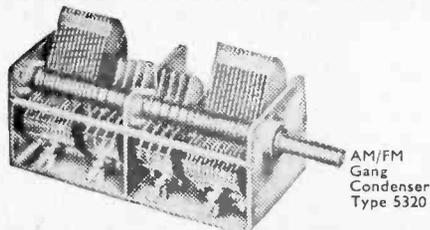Be sure of the best and buy Jackson Precision Built Components.



AM/FM  
Gang  
Condenser  
Type 5320

**JACKSON BROS. (LONDON) LTD.**  
KINGSWAY-WADDON, SURREY  
Phone: Croydon 2754-5 Grams: Walfico, Souphone, London

**SPECIAL FOR THE "HAMS" RADIO STATION**

*Illustrated*


1/8 inch detachable bit  
soldering instrument  
List No. 70

Combined Protective Unit  
with Wiper/Abrasion Pad  
and Solder Reel  
List No. 700

Apply **SALES & SERVICE**

**ADCOLA**  
REGISTERED TRADE MARK  
(Regd. Trade Mark)

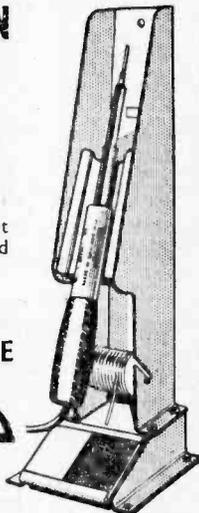**ADCOLA HOUSE  
GAUDEN ROAD  
LONDON, S.W.4**



British & Foreign  
Patents, Registered  
Designs, etc.


Telephones:  
MACaulay 3272-3101

Telegrams:  
"SOLJOINT, LONDON, S.W.4."

# SHORT-WAVE SECTION

A PRACTICAL  
PRE-SELECTOR

By A. Sydenham

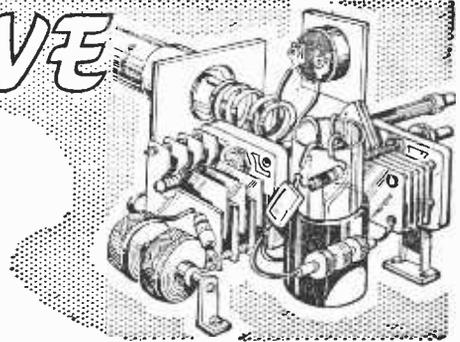

FOR reasons of economy, pre-mixer R.F. amplifying stages are often omitted from superhets of comparatively simple design. TRF receivers often have only one such stage preceding the detector and because of this sensitivity is frequently of a low order.

### Effects

The benefits that result from the inclusion of a tuned R.F. stage are well known, the addition being particularly desirable in the case of a superheterodyne where the first valve operates as a frequency changer, since not only is sensitivity increased enormously but also interference forms common to this type of receiver are minimised.

Many constructors and SWL's acknowledge the need for a tuned R.F. stage in their equipment but realise that, from a practical viewpoint, the

inclusion is not easy since a complete rebuild might be necessitated.

A simpler method of obtaining the R.F. gain desired is to use a pre-selector, the additional controls of which add little complication to tuning.

### Requirements

The following features are desirable in a pre-selector:

- (1) It should be capable of providing adequate R.F. gain.
- (2) The gain it provides should be controllable.
- (3) It should be stable in operation.
- (4) Differing aerial constants should not affect the calibration of its scale.
- (5) The output impedance should be of a value suitable for feeding into the aerial/earth sockets of the receiver with which it is to be used.

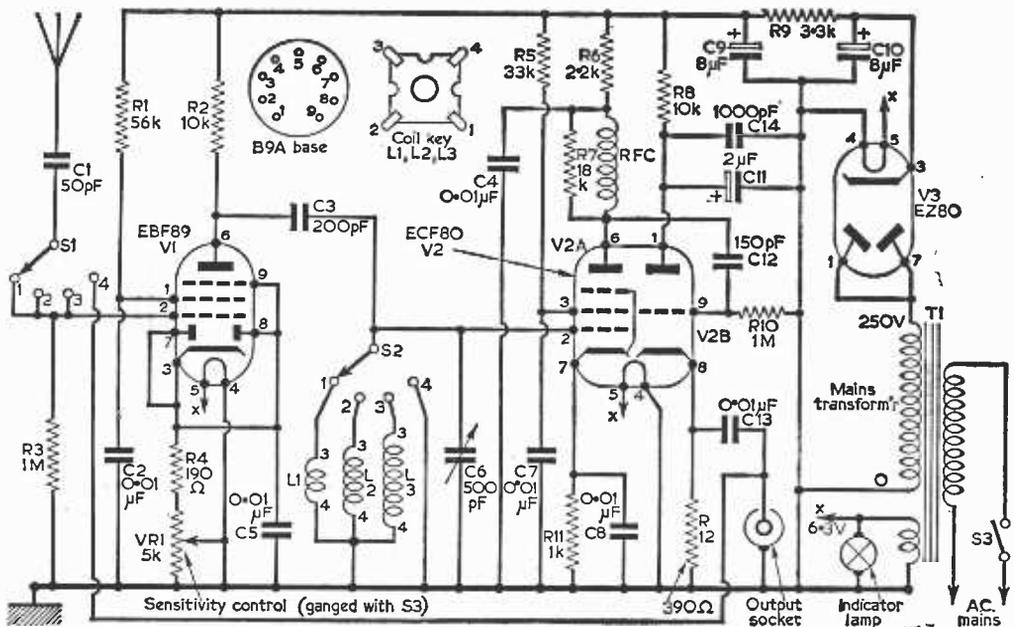


Fig. 1—The complete circuit.

(6) It should be entirely independent of the main receiver and facilities for completely switching it out of circuit should be included.

A unit meeting the above requirements is presented here and the circuit may be seen in Fig. 1.

Fig. 2a—The above-chassis layout.

The heart of the pre-selector is V2A and its associated circuitry which is sandwiched between an input and an output stage. The input stage, V1, provides a certain small amount of gain, but its main function it to act as a buffer in addition to providing variable gain facilities. Tuned circuits are associated with the grid circuit of V2A, C6 tuning the particular coil selected by S2. V2B is merely a cathode-follower stage that makes available an output impedance suitable for feeding to



#### The pre-selector unit

the receiver with which the unit is to be used.

#### Band Selection

For band selection purposes a 2-pole, 4-way rotary switch, S1, S2, is fitted, this being built from a "Makit" assembly comprising wafer, spacers, shafting etc. A less expensive method, but one

(Continued on page 833)

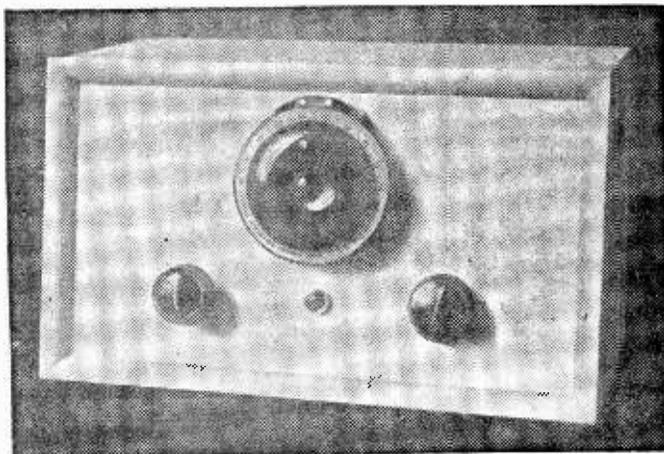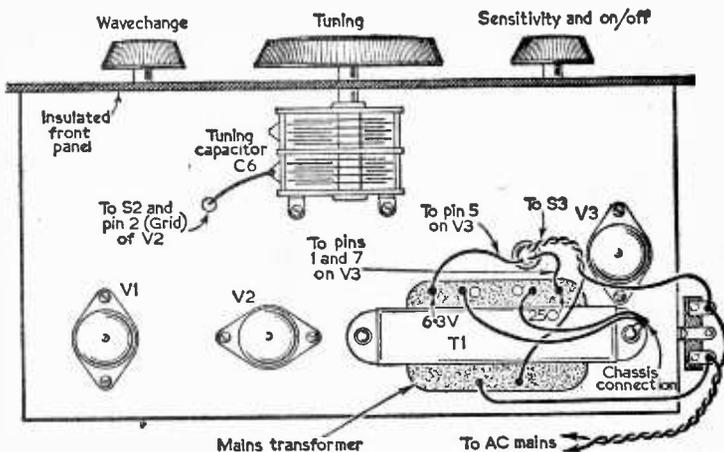

#### COMPONENTS LIST

Resistors:  $\frac{1}{2}$ W except where stated

R1 56k	R8 10k 1W
R2 10k	R9 3.3k 1W
R3 1M	R10 1M
R4 190 $\Omega$	R11 1k
R5 33k	R12 390 $\Omega$
R6 2.2k	VR1 5k pot and switch
R7 18k	

#### Condensers

C1 50pF mica
C2, C7, C8 0.01 $\mu$ F ceramic or paper
C3 200pF mica
C4 0.01 $\mu$ F ceramic or paper
C5 0.01 $\mu$ F ceramic or paper
C6 500pF (nominal)
C9 8 $\mu$ F 350W electrolytic
C10 8 $\mu$ F 350VW electrolytic
C11 2 $\mu$ F 275VW electrolytic
C12 150pF ceramic or mica
C13 0.01 $\mu$ F ceramic or paper
C14 1.000 pF ceramic

#### Coils

L1 Osmor QA1
L2 Osmor QA3
L3 Osmor QA4

#### Valves

V1 EBF89	V2 ECF80	V3 EZ80
----------	----------	---------

Mains Transformer: Mains input. Output: 0-250V 25mA, 6.3V 1A

R.F. Choke: QCI (Osmor)


Wavechange switch: S1 and S2 (see text)

Chassis: 8in x 4in. x 2in.

#### Miscellaneous:

- Lens and bush—1 hole fixing,  $\frac{3}{8}$ in. dia. (Bulgin D190)
- Panel light holder and bulb—6.3V, 0.15A
- Valve bases (3) B9A
- Dial and drive—see text
- Aerial/earth socket strip
- Coaxial plug and flush mounting socket
- Aerial/earth plugs; Spire clips (3)
- Material for cabinet, solder, tags, wire, etc.
- Tag strips—one 8-way, one 3-way

# CHECK with these

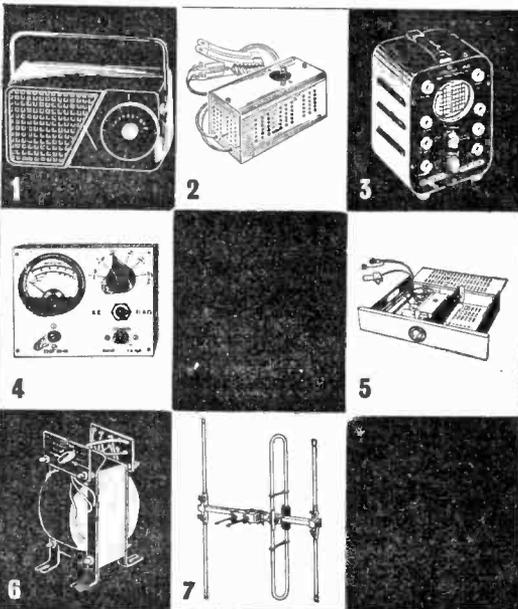

10. **SIGNAL GENERATORS.** Cash \$4.19.6. P. & P. 5/6. Coverage 120 kc/s to 84 Mc/s. Case 10 x 6 1/2 x 4 1/2 in. Size of scale 6 1/2 x 3 1/2 in. 2 valves and rectifier. A.C. mains 230-250 v. Internal modulation of 400 c.p.s. to a depth of 30 per cent, modulated or unmodulated R.F. output continuously variable 100 millivolts. C.W. and mod. switch variable A.F. output and moving coil output meter. Accuracy  $\pm$  2 per cent.

11. **BATTERY RECORD PLAYER AND AMPLIFIER.** 45 r.p.m. "Star" motor "Acos" crystal pick-up, 3 transistor push-pull amplifier complete with transistors. Output 500 milliwatts, 49/6, P. & P. 4/4.

12. **8-watt PUSH-PULL 5 VALVE AMPLIFIER.** A.C. mains 250-250 v. Size 10 1/2 x 6 1/2 x 2 1/2 in. 5 valves. For use with all makes and type of pick-up and mike. Negative feed back. Two inputs, mike and gram. and controls for same. Separate controls for Bass and Treble lift. Response flat from 40 cycles to 15 kc/s,  $\pm$  2 db; 4 db down to 20 kc/s. Output 8 watts at 5 per cent total distortion. Noise level 40 db down all hum. Output transformer tapped for 3 and 15 ohms speech coils. For use with Std. or L.P. records, musical instruments such as guitars, etc. Suitable for small halls, £3.19.6 P. & P. 6/5. Crystal mike to suit 15/-, P. & P. 2/-, 5in. P.M. Speaker to suit 12/6, P. & P. 2/-.

13. **B.S.R. MONARCH UAS WITH PUL-FI HEAD.** 4-speed, plays 30 records, 12in., 10in., or 7in. at 16, 33, 45 or 78 r.p.m. Intermixes 7in., 10in. and 12in. records of the same speed. Has manual play position; colour, brown. Dimensions: 12 1/2 x 10 1/2 in. Space required above baseboard 4 1/2 in. below baseboard 2 1/2 in. Fitted with Pul-Fi turnover crystal head, £6.19.6, P. & P. 5/6 With Stereo Head £7.19.6, P. & P. 5/6.

14. **TRANSISTOR TESTER.** For both P.N.P. and N.P.N. transistors incorporating moving coil meter. In metal case, size 4 1/2 x 3 1/2 x 1 1/2 in. Scale marked in gain and leakage. 19/6, P. & P. 3/-.

15. **PUSH-PULL OUTPUT STAGE** inclusive of transistors with input and output transformers to match 3 ohms speech coil, suitable for use with the POCKET RADIO. Kit of parts, including transistors. 19/6, P. & P. 2/-, Wiring diagram 1/6, free with kit.

16. **PORTABLE AMPLIFIER.** On printed circuit for A.C. Mains 200/250 v. Size 4 x 3 in. with tone and volume control. Complete with Valves: ECL82 and E280. Output 2 watts. 39/6, P. & P. 3/-.

# BARGAINS

1. **3-TRANSISTOR POCKET RADIO** with MINIATURE SPEAKER, FERRITE ROD, and 2 GERMANIUM DIODES. The only 3 transistor radio available at the price. Build it in 1 evening! Tunable over M/L waves. Complete with easy-to-follow instructions and all components (less batteries obtainable anywhere 1/3). 27/6. P. & P. 2/6. (All parts available separately.)

2. **NO MORE FLAT BATTERIES.** Charge your own battery overnight with this wonderful little charger. Output 6 and 12 volts, 2 amps. Input 200-250v A.C. mains. Mains fuse incorporated. Attractive silver hammer finished case, 6 x 3 x 3 ins. Complete with leads and battery clips only 21/-. P.P. 3/6.

3. **OSCILLOSCOPE** for D.C. and A.C. APPLICATIONS. A high gain, extremely stable differential Y-amplifier (30 mV/C.M.). Provide ample sensitivity with A.C. or D.C. inputs. Especially suitable for measurements of transistor operating conditions where maintenance of D.C. levels is of paramount importance. Push-pull X amplifier; Fly-back suppression; Internal Time-base Scan Waveform available for external use; pulse output available for checking TV line O/P Transformers, etc. Provision for external—1/P and C.R.T. Brightness Modulation. A.C. mains 200/250 v. £15.15.0, P. & P. 8/- or 30/- deposit, plus P. & P. 8/- and 12 monthly payments of 26/6. FULL 12 MONTHS' GUARANTEE INCLUDING VALVES and TUBE.


4. **A.C./D.C. POCKET MULTI-METER KIT.** 2in. moving coil meter, scale calibrated in A.C./D.C. volts, ohms and milliamps. Voltage range A.C./D.C. 0-50, 0-100, 0-250, 0-500. Milliamps 0-10, 0-100. Ohms range 0-10,000. Front panel, range switch, wirewound pot (for ohms zero setting), toggle switch, resistor and rectifier. 19/6. P. & P. 2/-, Wiring diagram 1/-, free with kit.

5. **CHANNEL TUNER.** Will tune to all Band I and Band III stations. Complete with P.C.C.84 and P.C.F.80 valves (in series) I.F. 16-19 or 33-38. Can be modified as an aerial converter (instructions supplied). 32/6, plus 4/- P. & P. HEATER TRANSFORMER to suit above, 200-250 v., 6/-, plus 2/- P. & P.

6. **MAINS TRANSFORMERS.** All with tapped primaries, 250-500 v. 70 mA, 6.3 v. 2 amp, 10/6, P. & P. 3/-, 280-0-280v. 70mA 5.3v. 2A, 6.3v. 1A 10/6, P. & P. 3/-, 280-0-280 120mA 6.3v. 2A, 6.3v. 3A, 17/6, P. & P. 3/6.

7. **WOLSEY 3-ELEMENT FOLDED DIPOLE.** I.T.V. Aerial less mounting bracket for external use, complete with 12 yds. of coaxial cable, 15/- P. & P. 4/-.

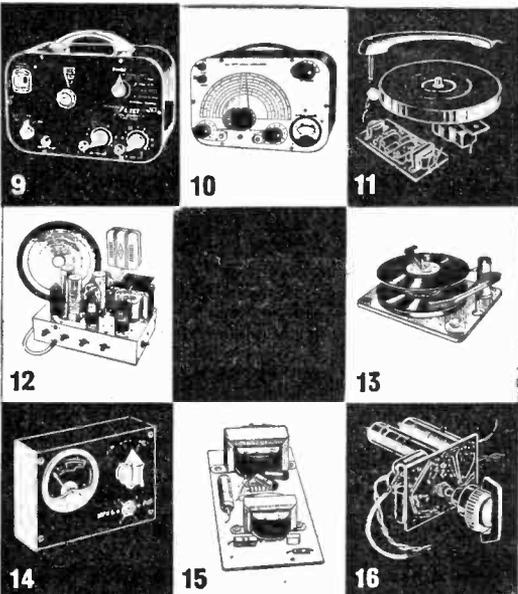9. **SIGNAL GENERATORS.** Cash £6.19.6 or 25/- deposit and 6 monthly payments of 21/6, P. & P. 5/6. Coverage 100 kc/s to 100 Mc/s on fundamentals and 100 Mc/s to 200 Mc/s on harmonics. Case 10 x 6 1/2 x 4 1/2 in. Three miniature valves and Metal Rectifier. A.C. mains 200/250 v. Internal modulation of 400 c.p.s. to a depth of 30 per cent. Modulated or unmodulated R.F. output continuously variable 100 millivolts. C.W. and mod. switch, variable A.F. output. Magic eye as output indicator. Accuracy  $\pm$  2 per cent.



**RADIO & T.V. COMPONENTS**  
(Acton) LTD.

**23B HIGH STREET, ACTON, LONDON, W.3.**

ALL ENQUIRIES S.A.E.  
GOODS NOT DISPATCHED OUTSIDE U.K.

# TECHNICAL TRAINING in radio television and electronics

Whether you plan to have your own business, to become an electronics engineer, to take up a career in industry, or to brush-up your knowledge and study new developments, transistors, etc., an I.C.S. Course will help you to success. You learn at home in your own time, under expert tuition. Moderate fees include all books.

## EXAMINATION COURSES FOR:—

**C. & G. Radio and TV Servicing Certificate**  
(R.T.E.B.)

**C. & G. Radio Amateurs' Exam.**  
(Amateurs' Transmitting Licence)

British Institution of Radio Engineers, etc.  
C. & G. Telecom. Technician's Cert.

## LEARN AS YOU BUILD

### Practical Radio Servicing Course

A basic course in radio electronic and electrical theory backed by thorough practical training. You build radio receivers, signal generator and multimeter.



**Post this Coupon TODAY!** for FREE book on careers in Radio, and full details of other I.C.S. Courses

**INTERNATIONAL CORRESPONDENCE SCHOOLS**  
(Dept. 171), Intertext House, Parkgate Road, London, S.W.11.

Please send book on \_\_\_\_\_

Name \_\_\_\_\_ Age \_\_\_\_\_  
(Block Letters Please)

Address \_\_\_\_\_

Occupation \_\_\_\_\_ I.62

**INTERNATIONAL CORRESPONDENCE SCHOOLS**

## D. & B. TELEVISION

Phone: Cherrywood 3955  
Dept. A1 131 & 131a KINGSTON ROAD  
SOUTH WIMBLEDON, LONDON, S.W.19

"Compare our prices with any others"  
For the **FINEST, FASTEST SERVICE** in the COUNTRY  
We are open from 10 a.m. Until Midnight. (1 p.m. Wednesday.)  
For any information or problems you have, Call or Phone, we are always pleased to help.

**NEW!**  
SEND FOR OUR COMPREHENSIVE L.O.P.T. Scan Coil L.B.O., F.B.O., F.O.P.T. LIST. Prices of nearly all makes and models, 2/6, post 6d. Invaluable as a service aid. The finest list ever compiled.

**HUGE PURCHASE ENABLES US TO SELL TRANSISTORS AT THIS ASTONISHING PRICE**  
Mullard: OC44, 9/-; OC45, 8/-; OC70, 6/-; OC71, 5/-; \*OC72, 6/-; OC76, 7/-; OC78, 7/-; \*OC81, 7/-; OC8ID, 6/-; G.E.C.: GE874, 8/-; \*GET873, 7/6; \*GET114, 5/-.  
\* Available in matched pairs at 1/- extra.  
Mullard Diodes: OA70, 2/9; OA79, 2/9; OA81, 2/9; OA91, 3/6. G.E.C.: GEX34, 3/3.  
TURRET TUNERS, Various Makes: 10, 16, 38 Mc/s, 40/-

**EXAMPLE OF TRANSFORMER LIST**

	L.O.T.	SCAN COILS
FERGUSON:	(New)	(Used)
103T, 105T ...	69/9	35/-
992/4/6/8 ...	69/9	35/-
PYE:	(New)	(Used)
V4, VT4, V7 ...	52/6	35/-
V77, CTM4 ...	52/6	35/-
MURPHY:	(New)	(Used)
V214, V240, V250 ...	60/6	35/-

**REGUNDED CATHODE RAY TUBES**  
all with 12 months' Guarantee  
ALL MAKES: 12in., £3.15.0; 14in., £4.5.0; 17in., £4.15.0.  
ADD: 10/- for 90°, 15/- for 90°, 5/- for Electrostatic Types.  
SECONDS, with 12-month Guarantee—ALL MAKES: 12in., £2.15.0; 14in., £3.5.0; 17in., £3.15.0.  
SECONDS, No Guarantee—ALL MAKES: 12in., £1.5.0; 14in., £1.15.0; 17in., £2.15.0.  
10/- allowance on old tube if in good condition.

**HUGE PURCHASE! Again passed on to you**  
T/V or coffee tables, veneered in walnut. Complete with 4 screw-on legs. Many other uses. Size: 15 x 18 1/2 in. Amazing offer at only 14/6. P.P. 3/.

SPECIALLY made cabinets for the REPANCO JOURNEY-MAN KIT, complete with 3 ohm speaker, dial and knobs. Well made in wood and covered in Vynidex. Colours: Yellow, White, Red, State second choice. 30/- each. P.P. 3/-.  
**HURRY WHILE STOCKS LAST!**

### ALL VALVES ARE SOLD SUBJECT TO FULL GUARANTEE

**CURRENT VALVE LIST**

AZ31	8/6	EC084	6/0	6L30	6/-	6L8	10/0	6U4	10/9	6U4	10/9
B36	5/6	EC085	7/6	KT36	8/0	8F41	2/3	UL84	7/8	7C6	6/0
CBLS1	19/6	EC121	12/8	KT61	8/8	8F61	2/3	UO8	14/6	7C6	7/0
COH33	12/6	EC135	9/-	KT63	6/3	9U2	0/8	UO9	6/8	787	8/0
CL33	10/6	EC142	7/6	KT61	5/9	9U4	10/0	UY41	6/-	7Y4	6/0
D77	8/6	EC181	7/6	KT63	5/9	9U5	12/0	UY56	6/6	10F1	4/6
DAF91	4/6	EC180	6/9	L63	2/9	9U6	9/9	W77	4/-	10C1	10/0
DAF96	6/6	EC182	9/8	PCC84	7/0	U31	7/-	Z77	3/-	10C2	13/0
DF91	3/8	ECL35	11/9	PCF89	8/0	U37	18/9	5U4	4/8	10F13	8/9
DF96	8/8	EF39	4/8	PCF80	7/0	U50	9/8	5V4	8/9	10P14	8/9
DI63	6/6	EF50	1/8	PCF82	7/9	U52	6/-	5Y3	5/9	12AT7	7/8
DH77	4/8	EF80	4/6	PCF86	14/6	U191	9/-	5Z4	10/-	12AT7	4/8
DK91	6/6	EF91	8/-	PCL82	7/0	U281	9/-	6AL5	8/-	12AU7	5/8
DK92	7/-	EF92	4/-	PCL83	9/9	U282	14/6	6AM6	8/-	12AX7	6/8
DK96	6/8	EF85	6/3	PCL84	7/0	U301	17/6	6AT5	15/6	193G6	14/6
DL31	7/8	EF86	8/9	PC155	15/-	U801	9/0	6B5	12/-	20F2	8/6
DL82	9/6	EF86	6/6	PL33	8/-	UAB080/8/6	6B/6	7/6	20L1	12/6	12/6
DL84	6/6	EL33	7/6	PL36	9/9	UBA42	8/-	6C02	25/6	20P1	9/6
DL86	6/6	EL38	12/-	PL38	14/6	UBA1	7/8	6D2	3/-	20P3	12/6
EABC80	7/8	EL41	7/9	PL81	8/6	UBC41	7/8	6F1	4/6	20P4	16/6
EA42	7/8	EL84	6/9	PL82	6/6	UBC49	7/8	6F12	3/-	20P5	14/6
EB41	6/6	ELM80	8/6	PL83	6/6	UBC54	12/6	6F13	6/6	27U5	14/6
EB91	3/6	GM81	8/6	PL84	8/0	UC055	7/8	6F14	9/-	30C1	7/8
EBU33	4/6	EM84	9/6	PY31	7/0	UCP80	14/6	6F15	9/-	30FL1	9/8
EBU41	7/8	EY51	7/9	PY32	10/-	UCB21	12/6	6F33	9/8	30L1	7/8
EBP80	7/6	EY86	7/6	PY80	8/0	UC42	2/0	6B5	12/0	80L1	10/0
EBF89	8/3	EZ40	6/3	PY81	6/0	UBA11	8/3	6L8	9/9	80P19	7/6
EBL31	20/-	EZ41	6/9	PY82	8/-	UCL38	18/6	6V6	5/-	82KU	10/0
EOC81	4/6	EZ80	6/0	PY83	8/-	UF42	8/9	6L18	8/0	83KU	10/0
EOC82	6/8	GZ24	8/9	PY88	12/-	UL41	7/-	6L19	12/0	84KU	8/8
EOC83	6/8	GZ34	12/6	EZ80	8/0	UL46	7/0	6N7	4/8	188BT	14/6

These are only examples of our valves; if you do not see what you require send stamped addressed envelope for special quotation.

We pride ourselves that we can obtain and supply any TV spare, **OUR GIGANTIC STOCKS INCLUDE:** Line, Frame and Sound Output, Line and Frame Blocking, Osc., Trans., and Scan Coils for any make or model Television. Please ask us for ANY components you require we are almost certain to have them. TERMS: S.A.E. all enquiries. C.W.O. or C.O.D. 3/- extra. Postage on Valves, 6d. each. C.R.T.s 12/6 inc. insurance. **SATISFACTION ASSURED. RETURN POST SERVICE.**

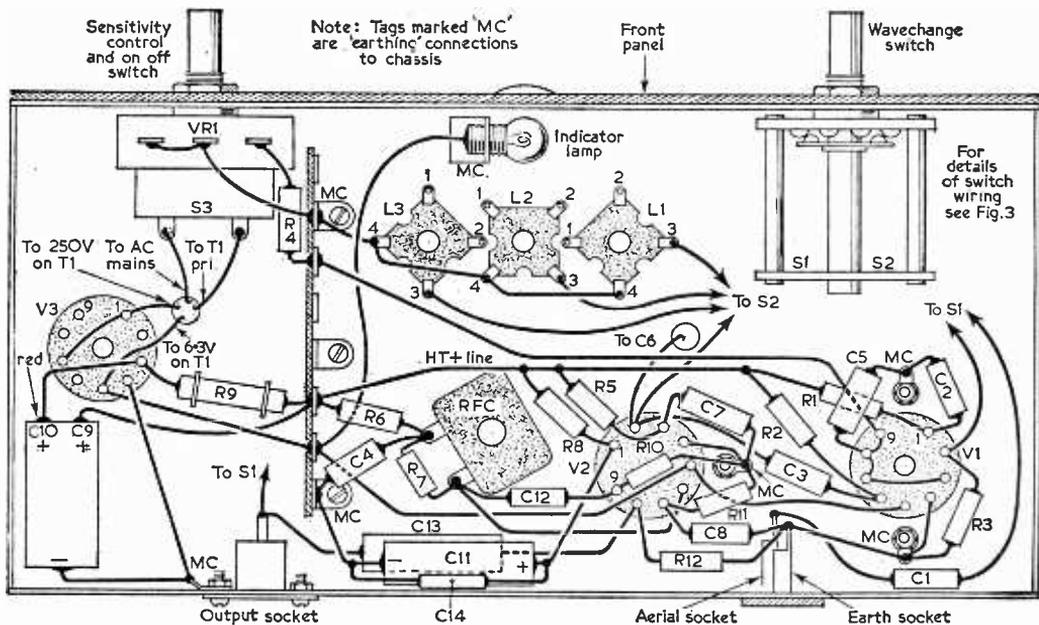


Fig. 2b—The under-chassis layout and wiring diagram.

(Continued from page 830)

that limits the number of "ways" available is to use a miniature rotary switch and the manner in which a conventional 3-pole, 4-way type of this pattern can be used is shown in Fig. 3. In the prototype, S2 selects from three coils in the short wavebands, the fourth position being used in conjunction with S1 to mute the unit and simultaneously connect the aerial direct to the main receiver.

Suitable coils of the type used in the prototype may be selected to suit individual requirements. Alternatively, home-wound coils may be used since no ganging problems arise. More than three coils may be accommodated by using a switch with sufficient "ways" after allowing for one to be used for muting, etc.

**Tuning Mechanism**

A slow motion drive is used to facilitate ease of tuning and no bandspread condenser is fitted. The tuning mechanism used in the prototype was taken from an RF27 unit of ex-Service origin, but a Jackson 4489 or Eddystone 843 could also be employed, these having reduction ratios of approximately 6:1 and 10:1 respectively. A twin gang tuning condenser is fitted, one section being left disconnected.

**The Power Supply Section**

This is quite simple, V3 being used as a half-wave rectifier in association with a mains isolating transformer T1, which makes the chassis safe to handle. No fuses are fitted to the prototype, but it might be beneficial to wire a 2.5V torch bulb in series with the secondary winding of T1 at the "earthy" end to protect the apparatus somewhat should a fault occur such as a heater/cathode short circuit in V3 which would cause an excessive current flow. Filtering and smoothing are given by R9, C9 and C10.

**Layout**

Both above and below chassis layout are given in Figs. 2a and b respectively, and as may be

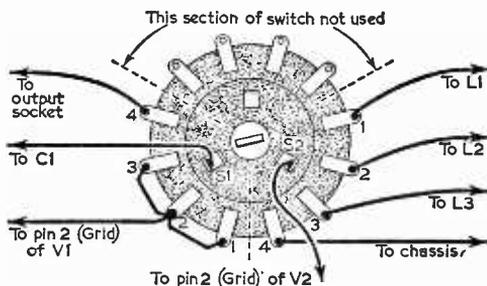


Fig. 3—Utilising a 3-pole, 4-way, rotary switch for band selection.

seen the amount of above-chassis wiring is very small. To minimise self pick-up the coils and switching are contained beneath the chassis where they are automatically screened by the chassis "box".

**Constructional Notes**

In the wiring diagrams, the positions of minor components might be seen to differ slightly from those shown in the illustrations, the reason being that it would not otherwise be possible to show the precise location with the wiring on a single diagram. Slight rearrangements are not important provided that leads associated with the anode circuit of V2A are not allowed to come too close to those of the grid circuit or unwanted oscillations might result.

(To be continued)

# universal SHUNTS

A SIMPLE UNIT WHICH MAY BE USED TO EXTEND THE RANGE OF MULTIMETERS

By R. Traynor

**M**ANY articles have been published recently on the construction of multimeters, all of which require the purchase or construction of shunts. If the constructor wishes to use a meter having a resistance or full scale deflection other than that specified, then new values must be calculated, and since these shunts are often of very low value and each one must be calculated with a fair degree of accuracy, this can become quite tedious.

The connections are shown in Fig. 1, which shows the values of typical resistors and the multiplying power at each switch position. In the example shown, the total resistance across the meter is 10,000Ω, which has negligible shunting effect. If we assume a meter having an f.s.d. of 100μA, then, in switch position 1, with no shunting effect, the meter reads 100μA. In switch position 10 the meter is out of circuit. The other switch positions will read as shown in Table 1.

Table 1

Switch Position	Multiplying Factor	f.s.d.
1	1	100 μA
2	5	500 μA
3	10	1mA
4	50	5mA
5	100	10mA
6	500	50mA
7	1000	100mA
8	5000	0.5A
9	10,000	1A

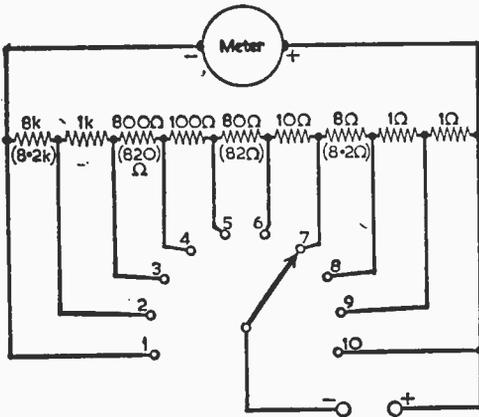


Fig. 1—A circuit of a switched universal shunt. The figures in brackets are preferred values of components which may be used if extreme accuracy is not essential.

If extreme accuracy is not required, the constructor may use preferred value components of say 5% as shown in Fig. 1. This will still give an accuracy of better than 1%, which is quite good enough for most applications.

☆ ☆ ☆ ☆ ☆ ☆ ☆ ☆ ☆ ☆ ☆

☆ **LAST-MINUTE CHRISTMAS GIFTS** ☆

☆ *No need to rush out to the shops. Here's one you can arrange now... in a few moments... in the comfort of your own armchair. A year's subscription for PRACTICAL WIRELESS is the ideal gift for friends who are radio enthusiasts.* ☆

☆ *But hurry! You must send now to make sure that first copies arrive in time for Christmas. Simply send your friends' names and addresses, together with your own, and remittance\* to cover each subscription, to The Subscription Manager (G.3), Practical Wireless, Tower House, Southampton Street, London, W.C.2. An attractive Christmas Greetings Card will be sent in your name to announce each gift.* ☆

☆ **\* RATES (INCLUDING POSTAGE) FOR ONE YEAR (12 ISSUES):—U.K. £1.9.0, OVERSEAS £1.7.6, CANADA £1.5.0.** ☆

☆ ☆ ☆ ☆ ☆ ☆ ☆ ☆ ☆ ☆ ☆

A simple method of avoiding these calculations and of cutting the cost by using standard components is by means of the universal shunt, an arrangement used in many commercial multimeters.

This shunt consists of a number of fixed resistors of different value joined in series and the whole connected across the meter terminals. By means of a selector switch any value of resistance can be selected, thus varying the multiplying power. One of the advantages of this arrangement is that there need be no relationship between the values of the resistors and the meter resistance. The multiplying power of a shunt is given by

$$n = \frac{\text{Meter resistance} + \text{Shunt resistance}}{\text{Shunt resistance}}$$

With the universal shunt the sum (M + S) is a constant, therefore the multiplying power of the shunt is inversely proportional to the shunt resistance and

$$n = \left( \frac{\text{Shunt resistance}}{\text{Multiplying resistance}} \right) + 1$$

There's **NO BETTER WAY** than  
**THE "PICTURE BOOK"** way  
*of learning*

**ELECTRICITY & ELECTRONICS**

(as 1000's have already discovered from)

THE ILLUSTRATED COURSES of ELEMENTARY TECHNICIAN TRAINING

Published by THE TECHNICAL PRESS LTD.

**BASIC ELECTRICITY (5 PARTS)**

**BASIC ELECTRONICS (6 PARTS)**

**BASIC SYNCHROS & SERVOS (2 PARTS)**



*In preparation* BASIC RADAR, BASIC ELECTRONIC CIRCUITS

"... there can be no better gift from father to son..."—*Hobbies Weekly*



So why not THE "PICTURE BOOK" way  
 for CHRISTMAS?

**COUPON - SEND NOW!**

To THE TECHNICAL PRESS LTD.

112 Westbourne Grove, London, W.2.

Please send me your FREE prospectus,  
 describing 'BASIC ELECTRICITY' 'BASIC  
 ELECTRONICS' and 'BASIC SYNCHROS  
 and SERVOMECHANISMS'

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

PW

THE WORD **MAXI-Q** IS THE REGISTERED  
TRADE MARK  
OF Denco (Clacton) Limited  
IT IS ALSO A GUARANTEE OF  
WORKMANSHIP & TECHNICAL PERFORMANCE

OUR RANGE OF PRODUCTS IS SO GREAT THAT WE NOW HAVE TO REQUEST THE AMOUNT OF 1/6d FOR OUR GENERAL CATALOGUE AND TO SAVE YOU POSTAL ORDER POUNDAGE CHARGE WE REQUEST SEND 1/6d IN STAMPS.

COMPONENTS FOR USE WITH THE "PRACTICAL WIRELESS"

## AN AMATEUR COMMUNICATIONS RECEIVER

(PUBLISHED JULY/AUGUST 1961)

### COIL TURRET—CT7/B

This turret is the basic portion of the CT7. It comprises cadmium plated steel frame (size  $5\frac{1}{2}$ " deep x  $4\frac{1}{2}$ " high x  $3\frac{1}{2}$ " wide), silver plated contacts, polystyrene insulation and a rotary turret movement incorporating Aerial, Mixer and Oscillator coils for the three bands 1.5-4 Mc/s, 4-12 Mc/s and 10-30 Mc/s. **PRICE 75/-**

Coil strips for the long and medium wavebands may be purchased separately for incorporation in the turret. **PRICE 10/6 each**

The turret requires a 315pF tuning capacitor. A suitable 3-gang component with ceramic insulation is available. **PRICE 19/-**

Air spaced concentric trimmers, 3/30pF, **PRICE 3/6 each**

### SCALE ASSEMBLY—S1

Comprising basic 5 waveband glass scale for use with 315pF tuning condenser, back plate, pulleys, rubber scale mounts, pointer, cord, drum, spring, drive spindle, screws, nuts and spacers. **PRICE 19/-**

### BEAT FREQUENCY OSCILLATOR COIL—BFO.2/465/kcs.

A compact coil wound on a bakelite former and enclosed in an aluminium screened can **PRICE 5/-**

### I.F. TRANSFORMER—IFT.11/465 kc/s (Four required)

A miniature I.F. Transformer for 465 kc/s. Permeability tuned, litz wound coils, enclosed in an aluminium screening can  $1\frac{1}{2}$ " high x  $\frac{3}{4}$ " square. **PRICE 6/6 each**

PLEASE SEND S.A.E. WITH ALL ENQUIRIES

**DENCO (CLACTON) LTD.,** (Dept. P.W.) 357/9 Old Road, Clacton-on-Sea, Essex

## Well paid to see the world

A really interesting and worthwhile job as a Radio Officer in the Merchant Navy awaits you if you are the holder of a current P.M.G. certificate. Salary and allowances are good from the start, rising by regular increments to well over the four figure mark with all found. Your job can take you all over the world, and you get generous annual leave besides off-duty time in foreign ports. Sea service offers ample opportunity to study for further technical qualifications and many well-paid shore appointments are open to you later on.

## A tradition second to none

Marconi Marine Radio Officers have a long and proud tradition of service extending back to the early years of this century. Among them are to be found names hallowed in the history of the sea. Moreover, many men in the highest public and administrative positions today began their careers as Radio Officers in the Marconi Marine Company.

Write for particulars to: F. E. ASH, Esq.

**THE MARCONI INTERNATIONAL  
MARINE COMMUNICATION CO.  
LTD.**

English Electric House, Strand, London. W.C.2

## For Safety's Sake use AVO Prodclips



Safety first every time with these patented spring-loaded AVO Prodclips.

Cleverly designed for use as insulated prods, they are invaluable for reaching and holding test points which are difficult of access.

Suitable for use with AvoMeter, Multimeter and Avo Electronic Test Meter Leads.

Post Free  
15/-  
per pair.

**AVO LTD** . AVOCET HOUSE,  
92-96 VAUXHALL BRIDGE ROAD, LONDON, S.W.1.  
VICtoria 3404 (12 lines)

A MEMBER OF THE METAL INDUSTRIES GROUP OF COMPANIES

# Improving Broadcast Receivers

By K. Berry

A SMALL INVESTMENT IN A FEW NEW COMPONENTS WILL REJUVENATE AN OLD SET


**M**ANY radio enthusiasts use standard broadcast receivers for their own or their families' entertainment. The purpose of this article is to show a few simple ways in which the performance of ordinary broadcast receivers can easily be improved. Some or all of these ideas can save money, since they will enable an old and "tired" set to give a performance comparable with that of a new receiver.

The application of one or more of these modifications will give you a receiver that is better than anything you could buy these days for £20 or so. If you decide to incorporate one or more of these ideas, do not stop there; when you have completed your electrical improvements, spend a little time (and perhaps money!) on cleaning and renovating

give the family visible evidence that the radio really is better! But seriously, do not spend three or four hours working on the inside of the receiver and then completely neglect the external appearance.

### Increased Sensitivity

A frequently felt need is the desire for a more sensitive receiver. There are two ways of achieving this. One is to add gain before the frequency changer (R.F. gain) by means of an R.F. stage, the other is to add gain after the frequency changer (I.F. gain) by means of an additional I.F. amplifier

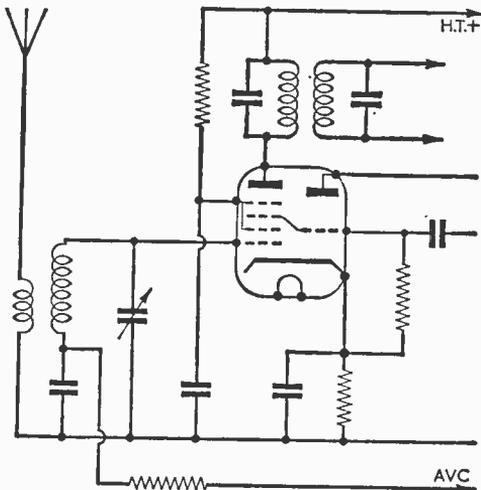

[Fig. 1—A typical receiver input circuit.

the appearance of the set. If one or more dial lights are defective, then replace them. If the loud-speaker aperture covering material is soiled, replace it—perhaps with gilt anodised aluminium. Do consider fitting a fresh set of knobs—the addition of a modern style of knob can do wonders to the appearance of a set. Finally give the case a good clean and polish it. Attentions such as these will

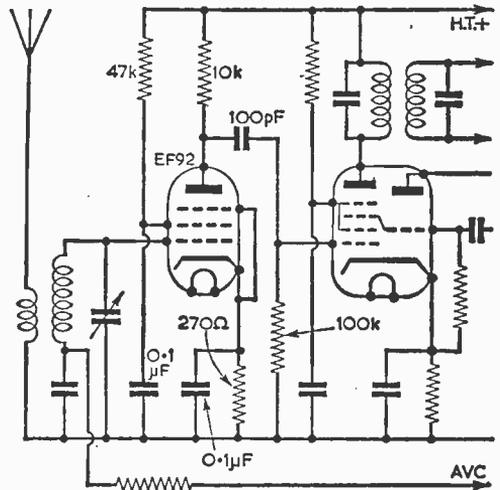


Fig. 2—The circuit of Fig. 1 with an R.F. stage added.

stage. There are advantages and disadvantages to each method, and these are tabulated on page 838. The best compromise is, perhaps, to add both. It should be noted that the added R.F. stage will be of the "aperiodic" or untuned variety. This is of necessity since the addition of a tuned R.F. stage would involve replacement of the existing tuning capacitor by one with an extra section and fitting extra coils and their associated bandswitching—altogether too complicated a job.

It is probably worthwhile to amplify the comments in the table regarding the selectivity question. The I.F. selectivity of receivers varies from make to make and model to model. Some receivers have, by design, a fairly wide I.F., whilst others are designed to have as narrow an I.F. as can be tolerated. Furthermore, some listeners live

Fig. 3 (right)—Another improvement to the circuit; this time the R.F. stage is before the original tuning coils.

in areas of good reception where there is little adjacent channel interference to BBC stations, thus permitting the use of a wide I.F. passband, whereas other, less fortunate listeners live in areas wherein reception of BBC stations is spoilt by strong adjacent signals, or they often listen to foreign broadcasting stations, in which case a narrow I.F. passband is essential. Thus, for some people, a decrease in I.F. passband would be an advantage—whilst for others it could be a little disadvantageous  
(Continued on page 853)

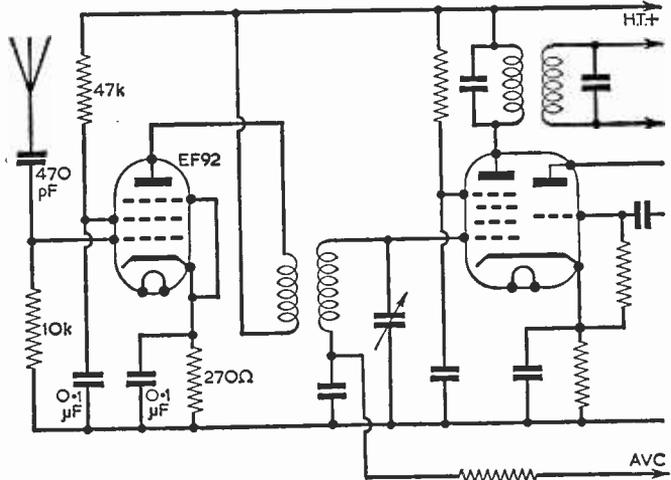


Table I

Untuned R.F. Stage	Tuned I.F. Stage
Extra gain.	Tuned amplifier gives more gain.
Improvement in Signal/Noise ratio.	Signal/Noise ratio very slightly worsened.
No increase in selectivity with its attendant side-band cutting.	May cause side-band cutting due to increase in selectivity.
Few components required.	More components required.
No additional selectivity	Increase in selectivity gives better separation of stations.
Normally no instability problems.	Possibility of I.F. instability due to large increase in I.F. gain.

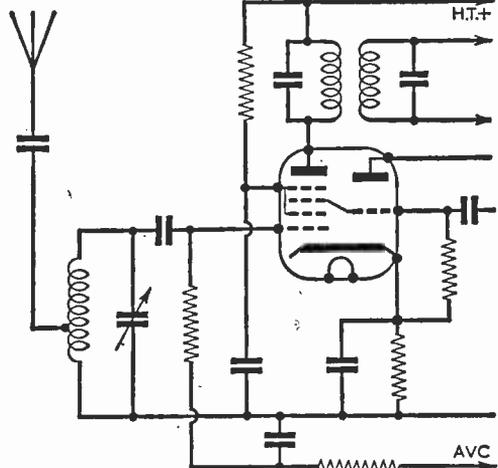


Fig. 4 (above)—A typical receiver input circuit which does not employ an aerial coupling coil.


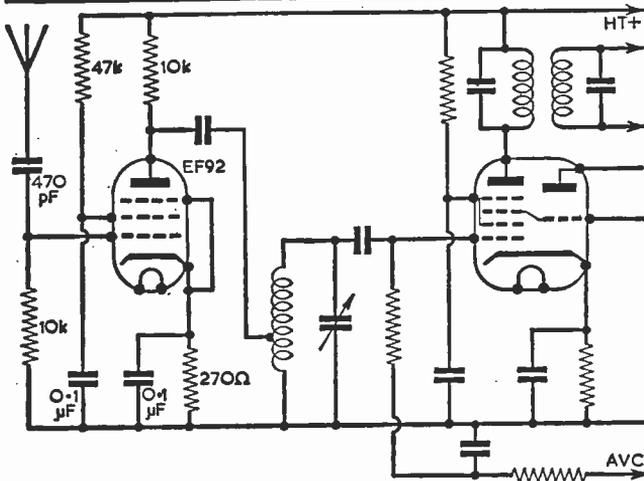


Fig. 5 (left)—A suitable improvement for the circuit of Fig. 4.

Fig. 6 (right)—A method of applying AVC.

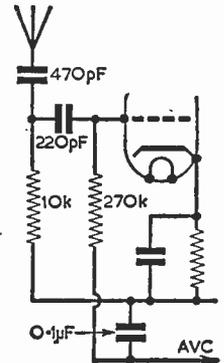

## SPECIAL BARGAIN OFFER—RECORD PLAYER KITS

**AUTO CHANGER KIT**—Comprising three Units. Contemporary styled Cabinet—2 valve, 2 watt amp. and 7 x 4in. quality speaker. Variable tone and Volume controls with feedback circuit and B.S.R. 4-speed 12 Record Mixer, Auto Changer Unit.

**BARGAIN PRICE, £12.10s.** only. Cabinet Size: 17 x 14½ x 8½ins. Carr. 7/6.

**SINGLE PLAYER KIT**—Similar spec. to Auto Changer Kit except Player is 4-speed B.S.R. T.U.S. Single Record Player Unit. Attractive Contemporary Styled Cabinet. Size: 13½ x 13 x 6ins. with splendid volume and reproduction.

**BARGAIN PRICE £8.19.6** only. Carr. 5/-.

**ALL UNITS READY WIRED, SIMPLE SCREWDRIVER ASSEMBLY ONLY FULL SALES ACTION—REFUND GUARANTEE**

Send for leaflet. Full details—3d. stamp.

## 7 VALVE AM/FM RADIOGRAM CHASSIS

Valve Line-up: ECC85 ECC81 F89 EABC80 EL84 EM81 EZ80.

Three Waveband and Switched Gram position. Med. 200-500 m., Long 1,000-2,000 m., VHF/FM 88-108 Mc/s. Philips Continental Tuning insert with permeability tuning on FM and combined AM/FM I.F. transformers, 460 Kc/s and 10.7 Mc/s. Duet core tuning all coils. Latest circuitry including AVC and Neg. Feedback. Three watt output. Sensitivity and reproduction are of a very high standard. Chassis size 13½ x 6ins. Height 7½ins. Edge illuminated glass dial 11¼ x 3½ins. Vertical pointer. Horizontal station names. Gold on brown background. A.C. 200/250 v. operation.



Aligned and tested ready for use **£13.10.0** Carr. & ins. 5/-.

Complete with 4 Knobs—walnut or ivory to choice. Indoor FM Aerial, 3/6 extra. Three ohm P.M. speaker only required. Recommended quality speakers.

10in. Rola (Heavy Duty)... 30/-.  
8in. Rola or Elac (heavy duty)... 28/-, p. & p. 2/-.

## BARGAINS 4-SPEED PLAYER UNITS

Single Players	Carr. 3/6	Auto-Changers	Carr. 5/-
Garrard 4 S.P.	£6.19.6	Garrard RC210	£10.10.0
Garrard TA Mk.2	7/- 9/6	Collaro 'C' 808	£7.15.0
Collaro 'Junior'	7/5-8	B.S.R. (UAB)	£6.19.6
B.S.R. (TU9)	7/9/6	B.S.R. (UAB Stereo)	£7.10.0
E.M.I. Junior	8/9/6	B.S.R. (UA14)	£7.15.0

## TURRET TUNER—BAND

VBAND 3. Ex. mfrs. current production offer—std. type 13-channel unit. 35-38 Mc/s I.F. Complete with PCC24 and PCF80 Valves and coils for channels 1-3-9. No knobs or circuit diagram, but connection data supplied. Clearcance Bargain Only 32/6. Carr. 2/6. Worth 5 gns.

**ENAMELLED COPPER WIRE**—4lb. reels. 14g-20g. 2/6; 22g-28g. 3/-; 30g-40g. 3/8. Other gauges quoted for.

**PVC CONNECTING WIRE**—19 colours (for chassis wiring, etc.)—Single or stranded conductor, per yd., 2d.

**RECORDING TAPE—SPECIAL BARGAIN OFFER**  
Famous American Columbia (CBS) Premier Quality Tape at NEW REDUCED PRICES. A genuine recommended Quality Tape—TRY IT! Brand new, boxed and fully guaranteed. Fitted with leader and stop foils.

	Standard	Long Play	Double Play
5in.	600ft. 15/-	900ft. 18/8	1,200ft. 31/6
5½in.	900ft. 19/6	1,200ft. 22/6	1,800ft. 39/6
7in.	1,200ft. 21/-	1,800ft. 32/6	2,400ft. 47/6

Post and Packing, per reel, 1/-, plus 6d. each for additional reels.  
**SPECIAL OFFER**—3in. mfrs. surplus tape, 225ft. 5/6. P. & P. per reel 6d. Plastic Tape Reels, 3in. 2/6, 5in. 3/-; 5½in. 3/3, 7in. 3/6.

**METAL RECTIFIERS, STC**  
Types—RM1, 4/9; RM2, 5/1; RM3, 7/6; RM4, 16/-; RM5, 25/-; RM4B, 17/6.

**SIEMENS TYPES**—Contact Cooled: 250V, 50mA, 7/6; 250V, 85mA, 10/-; 250V, 125mA, 15/-; 250V, 300mA, 26/6.

**KNOBBS—Modern Continental types:** Brown or Ivory with Gold Ring, 1in. dia., 9d. each; 1½in., 1/- each; Brown or Ivory with Gold Centre, 1in. dia., 10d. each; 1½in., 1/3 each. **LARGE SELECTION** available, TYGAN PHET (contemp. pat.), 12 x 12in. 2/-, 12 x 18in. 3/6, 12 x 24in. 4/-, 18 x 24in. 6/-, etc.

## NEW BOXED VALVES

Boxed	Valves	Guaranteed	All
174	6/- ECC85	8/6 PCC84	9/6
185	7/6 ECC82	9/6 PCF80	9/6
185	7/6 ECC80	10/6 PCL38	12/6
384	7/6 EBF82	8/6 PCL34	12/6
374	7/6 EBF82	12/6 PL81	12/6
DAF96	9/- EL84	8/6 PL82	9/6
DF96	9/- EY81	8/6 PL83	10/6
DK96	9/- EY86	10/- PY82	12/6
DL96	9/- EZ81	7/6 P81	9/6
ECC81	8/- GZ32	12/6 PY89	7/6
ECC82	8/- EM81	9/6 U25	12/6

## TRANSISTOR COMPONENTS

Midget I.F.'s—465 Kc/s, 9/16in. dia.  
Osc. Coil—M/W, 9/16in. dia. 5/3  
Osc. Coil—M. & L.W. 5/3  
Midget Drive Trans. 3.5:1 6/9  
Midget O/P Trans. P.P. to 3 ohms 8/9.  
Ferrite Aerial M. & L.W., Car aerial coil, 9/3.  
Elect. Condensers—Midget Type 1 2in-50mfd, ea. 1/9. 100 mfd. 2in-60/12V wks. 3/6.  
Condensers—.01mfd, .03mfd, .05mfd, .1mfd, 1/-; .25mfd, 1/3; .5mfd, 1/6.  
Vol. Controls—Midget Type with edge Control Knob. 47K, 1 M/ohm, ea. 2/6.  
Speakers P.M.—2in. E.M.L. 3 ohms 17/6. 7 x 4in. Plessey 35 ohms 23/6.  
Ear Plug Phones—Min. Continental type, 3ft. lead, jack plug and socket, High Imp. 8/-. Low Imp. 7/6.

## TRANSISTOR BARGAINS

Brand	New-BVA	1st Grade
OC44	10/8	8/3
OC45	9/6	GET114 9/6
OC81	9/6	OC72 7/6
2/OC81	15/8	OC70 5/6
XA102	10/-	OC71 6/9
XA101	9/6	GEX34 2/9
X3103	7/6	OA70 2/9
XC101	8/6	AS 2/9
874	9/6	GD17 2/9
SE305	Surface Barrier Type	9/6 each.

All Post Free!

**Speaker Fret**—Expanded bronze anodised metal 8 x 8in. 2/3, 12 x 8in. 3/-, 12 x 12in. 4/6, 12 x 16in. 6/-, 24 x 12in. 9/-, 36 x 12in. 13/6, etc. etc.

## Electrolytics All Types New Stock

TUBULAR	CAN TYPES
2525V 1/9	8-8440V 4/6
50/12V 1/9	8-16460V 5/-
50/50V 2/-	32+32275V 4/6
100/25V 2/6	50+50/350V 6/6
8440V 2/8	80+250/ 27/6
19440V 3/6	100+200/ 12/6
16+16/450V 5/6	32+32/450V 6/6
32+32/450V 6/6	27/6 12/6

Erns Multicoore Solder 80/20 3d. per yard. 1lb. 2/6, etc.

## SLEEVING—Various Colours

1mm, 2mm, 2½, 3mm, 4mm, 5d. yd., 6mm, 6d. yd.

## CRT ITR INSULATION TRANSFORMERS

New improved types, low capacity small size and tag terminated a.c. 200/250V. Secondaries 11:1 +25% +50% BOOST for 2V, 4V, 6.3V, 10.5V, 12V or 13V tubes. Each type 12/6 each. P. & P. 1/6.

**TRIMMERS, Ceramic** (Ceramic Control Type)—30mF, 70mF, 9d.; 150mF, 150mF, 1/3; 250mF, 1/6; 600mF, 1/8.

**PHILIPS, Bee Hive Type** (Conc. Air Spaced)—2-8pF, 1/-; 3-30pF, 1/-.

**TUNING COND.—Twin Gang** by J.B., etc. 365pF Midget, 8/6; 0.005 mfd Midget, 7/6. Transistor Type, J. Bros. 0d. Midget Twin Gang 208pF+176pF, 9/-.

**SINGLE TUNING COND.—Reaction Type, Mica Dielectric, 0.005 mfd., 0.0003 mfd., 0.006 mfd., 3/6 each.**

**Wavechange SWITCHES** Midget Type—2 pole 2 way, 1 pole 2 way, 2/6 each; 1 pole 12 way, 2 pole 6 way, 3 pole 4 way, 4 pole 2 way, 4 pole 3 way, 3/6 each.

**SINGLE SCREENED LEAD:** Standard size 8d. yd.; Ditto Lightweight for Fiosup, etc. 7d. yd.; ditto lightweight PVC sheathed, 9d. yd.; Twin screened sheathed, 1/- yd.

**Volume Controls**—5K-2 Meg. ohms. 5in. Spindles Morganite Midget Type, 1½in. diam. Gur. 1 year. LOG or LIN ratios less Sw. 3/-. DP. Sw. 4/8. Twin Stereo less Sw. 6/6. D.P. Sw. 8/-.  
**COAX 90 OHM CABLE** High grade low loss Cellular air spaced Polythene—¼in. diameter. Stranded cond. Famous mfrs. Now only 6d. per yard. Bargain Prices—Special lengths—20 yds. 9/-, P. & P. 1/6. 40 yds. 17/6, P. & P. 2/-. 60 yds. 25/-, P. & P. 3/-. Coax Plugs 1/-, Sockets 1/-. Couplers 1/3, Outlet Boxes 4/6

**Condensers—Silver Mica.** All values, 2pF to 1,000pF, 6d. each. Ditto, Ceramics 9d. Tub. 450V T.C.C., etc., 0.001 mfd., 0.01 and 0.1/350V, 9d., 0.02, 0.1/500V, 1/-. 0.25 Hunts 1/6. 0.5 T.C.C. 1/6, etc., etc. Close Tol. 8/Micas—10% 5pF-500pF 6d., 600-5,000pF 1/-, 5% 2pF-100pF 9d., 100pF-500pF 11d., 675pF-5,000pF 1/6. Resistors—Full Range 10 ohms-10 meg. ohms 20% ± and 1W 3d., 1W 5d. (Midget type modern rating) 1W 6d., 2W 9d., 1½W 10% 1W 5d., 1W 7d., 5% 1W 9d., 1% 1W 1/6. 1W Resistors 25 ohms to 10K, 5W 1/3, 10W 1/16, 15W 2/-. Preset T/P Pots, W/W 25 ohms —50 K 3/-, 50K-2 Meg. (Carbon) 3/-.

## JASON FM TUNER UNITS

Designer-approved kits of parts.  
FMT1, 5 gns. 4 valves, 20/-.  
FMT2, 27. 5 valves, 37/6.  
JTY MERCURY 10 gns.  
JTY2 £13.19.6. 4 valves, 32/6.

**NEW JASON FM HANDBOOK, 2/6.** 48 hr. Alignment Service 7/6. P. & P. 2/6.

**Speakers P.M.—3 ohms 2½in.** Elac 17/6. 3½in. Goodmans 18/6. 5in. Rola 17/6. 6in. Elac 19/6. 7 x 4in. Goodmans 18/6. 8in. Rola 20/-, 10in. R. X. A. 25/-, 10 x 6in. Goodmans 25/-. E.M.L. Tweeter 29/6.

## TAPE RECORDER KIT

**Special Offer.** Latest 5 valve circuit based on Mullard's design. Magic eye and tone controls. Printed circuit already wired. A sensitive quality recorder I.S.R. Amp Kit 95/-. B.S.R. Tape Deck 29.10.0. Collaro Amp. Kit 28.5.6. Collaro Tape Deck 212.10.0. Set of 5 valves 45/-. Special Unit Kit Prices—Send stamp for detailed list. Construction and circuit details 2/6. Bargain Complete B.S.R. Kit £16.10.0. Carr. 4/6.




Send for detailed bargain lists, 3d. stamp.  
We manufacture all types Radio Mains Transf. Chokes, Quality O/P Trans., etc. Enquiries invited for Specials, Prototypes for small production runs. Quotation by return.

## RADIO COMPONENT SPECIALISTS

70 Bricktort Rd., Thornton Heath, Surrey.  
Tel: 2188. Terms: C. P.O. or C.O.D. Post and Packing up to 1lb., 7d.; 1lb. 1½; 5lb. 24s. 2/-; 10lb., 2/6.  
Hours: 9 a.m.-6 p.m., 1 p.m. Wed. Hours: 9 a.m.-6 p.m., 1 p.m. Wed. Hours: 9 a.m.-6 p.m., 1 p.m. Wed.

**TAPE RECORDER AMPLIFIERS**

£7.19.6.

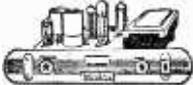

Compact, well designed 5 valve amplifier. Output 3.5W. Input for Microphone, Radio and Gram. Size 8½ x 3 x 4½ in. Ins. Carr. 5/- 12 months' guarantee. Terms available. Extras: Dial plate, including sockets and superimpose switch, 3/6. Knobs 2/6.

£9.15.6.

By famous manufacturer. Superb 4-valve amplifier. Two controls and superimpose switch. Sockets for Mike and Gram. Size 11 x 4 x 6in. Drawings FREE with order. Ins., Carr. 5/-.

**RECORD PLAYER AMPLIFIER**

79/6 MK. D.2




Latest design incorporating negative feedback, giving 4 watts undistorted output. Valves: ECL82, and metal rectifier. Tone and volume control panel on flying leads. P. & P. 4/-.

**5¼ in. SCOTCH BOY TAPE 19/9**  
Limited Quantity. Post Free.

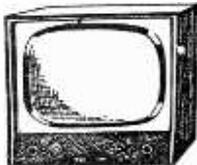**LOOK — EX-RENTAL SETS**

17 INCH £11.10.0

Excellent Table models. ITA/BBC. Famous manufacturer. 12 months' guarantee on Tube, 3 months on chassis and valves. Personal collection advised. Despatch in 3 parcels for easy assembly. Carr. 25/-. (Regret some delay).



14 INCH £7.10.0

ITA/BBC. Identical to 17in. TV. Ideal for Caravans, Weekend Bungalows, Chalets, etc. Carriage 20/-.

**TV TUBES**

12 MONTHS' GUARANTEE



21in. - 99/6

17in. - - - - 90/-

15, 14, 12in. - - - - 70/-

★ Insurance and carriage 15/6.

£1 extra without old bowl, refundable if same received within 14 days.

14in. TV TUBES 35/-  
14KP4 Due to purchase of rental replacement stocks. Carr. 5/6. 36/24

**TRANSISTORS**

Per Set 47/6 Post Free

Mullard

1 OC81D 6/9, 2 OC81 6/9,  
1 OC44 9/9, 2 OC45 8/9,  
Diode 1/9

GEC  
114 6/9  
873 8/9  
2-874 9/9

Ediswan  
XC121 8/9  
XB113 8/9

**DUKE & CO.**

(LONDON) LTD.  
621/3 Romford Road,  
MANOR PARK, E.12.  
ILF 6001/3

9 a.m.—6 p.m.  
Half Day Thursday.

STAMP FOR FREE LIST

**—AVO UNIVERSAL IMPEDANCE BRIDGE No. 2—**

Resistance 0.5Ω-55MΩ. Capacity 5pFd-55mFd. Inductance 50mH-550H. Leakage at 25, 50, 150, 250, 350 and 450 volts. Power factor. A.C. mains operation. Brand new with manual. £20, carr. 7/6.

**MULTIMETERS.** 1000Ω/volt. A.C. and D.C. volts, 0-10, 50, 250, 500 & 1000 D.C. current 0-10, 100mA. Resistance 0-2KΩ and 0-200KΩ Bakelite case, complete with test leads. BRAND NEW 59/6.

**BC 221.** The most accurate precision portable heterodyne frequency meter 125Kcs to 20Mc/s. Complete with original individual calibration book. Guaranteed perfect £16.

**CRYSTAL CALIBRATION No. 10.** Good condition, tested, with instruction manual. ONLY 59/6 or AS NEW with three spare valves, leads, etc. £4.10.0. P. & P. 3/6.

**PCR COMMUNICATIONS RECEIVER**

**Type PCR.** Has self-contained speaker. Covers 850-2000, 200-550 and 16-50 metres.

**AS NEW CONDITION.** £8.19.6

**Type PCR-2.** Requires external speaker. Covers 850-2000, 200-500 and 13-50 metres.

**USED (Good condition.)** £5.19.6

**Carriage (any type) 10/6.** Full details S.A.E. Any model fitted with BRAND NEW INTERNAL POWER SUPPLY, guaranteed ready for use on A.C. mains £2 extra.

**Moving Coil Phones.** Finest quality Canadian, with Chamois ear-muffs and leather-covered headband. With lead and jack plug. Noise excluding supremely comfortable, 19/6, post 1/6.

**GIANT COMPONENT PARCEL.** Contains 100 ½ and 1 watt resistors, 50 HI Stab resistors, W/W resistors, carbon and W/W pots, 100 capacitors (mica, paper, Sprague bias, variable, etc.), valveholders, tag strips, metal rectifiers, sleeving, etc. All components are unused. **GUARANTEE VALUE, 25/-,** plus 2/6 post.

**TRANSISTOR SETS**

We now stock The Pocket 4, a neat little job which can be made for 42/6. (Printed Circuit Version 52/6), and The Good Companion (a super job equal to the best). Easily constructed for only £9.19.6. Gladly demonstrated to callers.

**CHARLES BRITAIN (RADIO) LTD.**

11 Upper Saint Martins Lane, London, W.C.2

TEMPle Bar 0545

Shop Hours 9-6 p.m. (9-1 p.m. Thursday)  
Open all day Saturday.

**DOWN TO EARTH**

BOOKS

by

**Gordon J. King** for  
(Enterprises) Limited

- Constructors
- Experimenters
- Home Repairs
- Students
- Service Technicians

Technical Publications Division Tel.: Brixham 2304

★ **CIRCUIT AND DATA SERVICE**—circuits of all radio and television sets.  
★ **ADVISORY SERVICE**—free on all orders over £3. Post Coupon for full details and specially developed fault diagnosis **QUESTIONNAIRE FORM.**

★ **DEFERRED TERMS**—on all orders over £3. Post coupon for details.

★ **ALL BRITISH BOOKS AVAILABLE**, including those by Newnes, Odhams, Fountain, McGraw-Hill, Iliffe, Price, Bernard, Technical Press, etc.

1 **TELEVISION SERVICING HANDBOOK**—80/-

● All sound and vision faults fully described. ● Fault-finding and repairs.

● Useful procedure charts detail ALL major faults. ● How to repair and boost worn tubes. ● All about TV aerials. ● How to convert for ITA, etc., etc.

2 **PRACTICAL HI-FI HANDBOOK**, 25/-

● How to set-up and operate equipment for the best results. Record players.

● Tape recorders and recording. ● All about STEREO. ● Fault finding and repairs. ● Control units and power amplifiers. ● Room acoustics. ● Speakers and enclosures. ● The art of hi-fi, etc., etc.

3 **FM RADIO SERVICING HANDBOOK**, 25/-

● Full PRACTICAL description of the FM system. ● How to repair and adjust FM/AM sets. ● FM tuners. ● FM aerials. ● Complete fault-finding and servicing guide, including alignment techniques, etc., etc.

4 **ESSENTIAL SERVICING DATA VOL 1—TV SETS—10/6.**

5 **ESSENTIAL SERVICING DATA VOL 2—RADIOS AND GRAMS—13/6.**

● All essential items of hundreds of sets detailed, including: ● Valve line-ups.

● Electrolytics. ● All controls. ● TV pre-sets. ● Mains droppers. ● Line-cords. ● I.F.'s. ● FM and ITA converters. ● Tubes. ● Thermistors. ● Pilot lamps. ● Fuses. ● Surge limiters. ● EHT also. ● SERVICING NOTES.

A truly indispensable book for ALL.

6 **POINTS ON PICK-UPS**—7/6 paper, 10/- stiff-bound. ● Illustrates and details almost all pick-up cartridges, heads and stylis both mono and stereo. Gives:

● Colour-codes. ● Replacement stylis type No's. ● Price and tax. ● A NEW fourth edition. ● A MUST for all interested in records.

**GORDON J. KING (ENTERPRISES) LIMITED**  
"Kingsford", South Fazeham Road, BRIKHAM, Devon

Please send me (tick where applicable) BOOKS  1  2  3  4  5  6 for which I enclose £ s. d. (please add 1/3 postage under £3, 2/- over £3). **BOOK CATALOGUE**  **CIRCUIT LISTS**  (please send 1/3). Details of (please send S.A.E.): **ADVISORY SERVICE**  **DEFERRED TERMS**  **CIRCUIT SERVICE**

Name \_\_\_\_\_  
Address \_\_\_\_\_

My special interest is \_\_\_\_\_

# T rade N ews


## NEW RADIO FOR THE U.K.

SIX new models have been added recently to the 1961/62 range of Zenith radios now available in this country.

The Royal 500H de Luxe pocket transistor has eight plug-in transistors and employs a 5in. x 3in. speaker, powered by a new ceramic magnet.

The Royal 500 H is housed in a nylon case of modern design with a gold front. It is available in three colours—ebony, white and two-tone grey—and costs £33 13s. 6d., plus £11 17s. 9d. purchase tax.

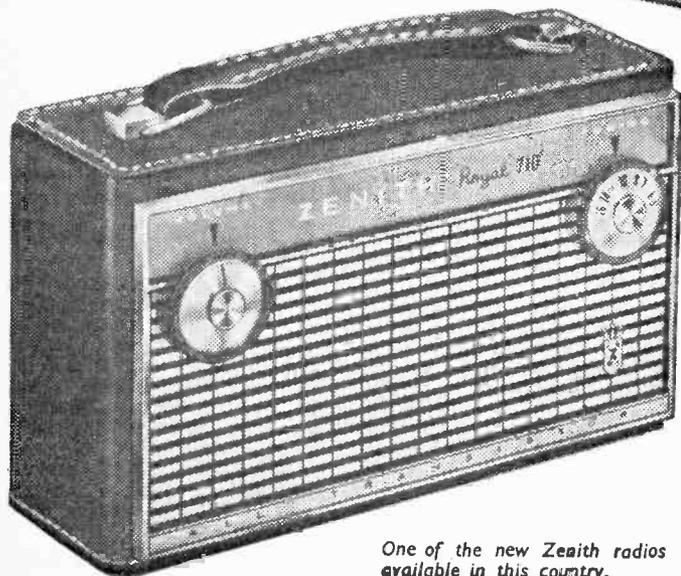Another new addition is the Royal 400, a seven transistor



One of the new Zenith radios available in this country.

pocket radio, which has the same 5in. x 3in. speaker and maximum audio output of 200mW. It is available in several colours and costs £28 8s. 10d., plus £8 19s. 6d. purchase tax.

Another newcomer, the Royal 710LG, has 500mW of undistorted audio output. Using seven transistors, it is powered with torch batteries, providing up to 350 hours of operation. It has a 4in. loudspeaker and costs £32 13s. 8d., plus £11 10s. 9d. purchase tax.

These and other Zenith radios are distributed in this country by *United Mercantile Co. Ltd., 13-14 Queen Street, Mayfair, London.*

## RADIO SIGNAL PROBE

A NEW 'Lab-Craft' radio signal has been designed for fault tracing and functions as a wide-band modulated signal generator.



(Above)—The Lab-Craft radio signal probe—Model 704.

Two outputs are provided; a direct output at the sockets and a radiated signal from a plug-in ferrite rod aerial.

The amplitude of the direct output is controlled by an attenuator so that relative stage gains can be determined.

The model 704 is one of the range of service equipment manufactured by *Lab-Craft Ltd., 38 Ilford Lane, Ilford, Essex.*

## RECHARGEABLE BATTERY

A NEW rechargeable battery, manufactured by Electronics and Automation (London) Ltd., is being marketed. It is the size of two U2 standard cells, is charged by removing a cap, which


simultaneously switches in the internal rectifier and also completely isolates the battery electrically. The two 5A pins revealed are then plugged directly into a mains socket.

Being completely self-contained, no connections, wires, trickle-chargers or other equipment are required. The battery is guaranteed by the makers for one year.

The Etromat is encased in a very robust plastic. It may be left for months in a torch-case. There is no corrosion, because the storage section is completely, hermetically sealed and contains no chemicals to corrode the metal contact base.

Since the battery is constructed for recharging from 110V to 250V supplies, it may be used anywhere. The life of one recharge is the same as that of the replaceable type of battery. The charging time at 250V is 14 hours and at 110V 20 hours.

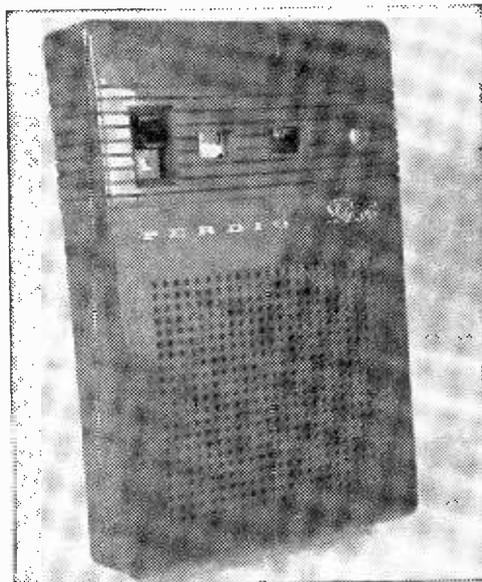No matter the voltage (from 2.5V to 6V) or the type, the battery is always the same size. *Electronics and Automation (London) Ltd., Maxwell House, Arundel Street, London, W.C.2.*



This is one of the latest Perdio transistor receivers. Presented in a two-tone plastic case, it covers long and medium wavebands. The "Mini Six", as this receiver is known, uses a 9V battery and as an audio output 200mW. It is completely portable and employs six transistors.

The model number is PR24, and the set is made by Perdio Ltd., Perdio House, Bonhill Street, London, E.C.2.

#### A NEW TRANSISTOR RECEIVER

THE "Sky Prince" receiver employs six transistors, and an 8in. x 5in. elliptical speaker gives one watt output. Up to 400 service hours can be expected from the one battery.

An important feature of the Sky Prince is that it can be carried easily from room to room as there are no leads and plugs to disconnect.

Full coverage of long and medium waves is afforded, plus external aerial socket and external speaker socket. The Sky Prince cost 18½ guineas and is made by *The Ever Ready Company Limited, Hercules Place, Holloway, London, N.7.*

#### NEW RANGE OF MINIATURE SOLDERING INSTRUMENTS


THE Oryx range of soldering instruments has recently been extended to include instruments with voltages up to 230/250. A variety of tips are available with 6 to 20W output. Replaceable tips are available and the heavy duty elements quickly provide a tip temperature up to 932°F, depending on the model.

The sole distributors of Oryx products are *W. Greenwood Electronics Limited, of 667 Finchley Road, London, N.W.2.*



(Above)—The Etromat rechargeable torch battery.

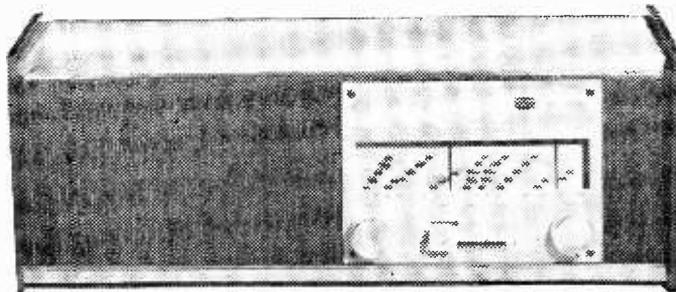(Below)—The Sky Prince transistor radio made by Ever Ready Limited.



# SURBITON PARK RADIO LTD

## for POST HASTE—POST FREE SERVICE

### F.M. TUNERS

**JASON F.M. TUNER KITS** We are the Authorised Jason Dealer and the whole kit is as supplied by them. You can therefore safely return to Jason for alignment without them rejecting it for non-standard components. We can also align for the standard charge.

<b>FMT1</b> Is the standard variable tuner for cabinet mounting, un-powered. Supplied complete with four EF91 valves.....	£11.3
Hire purchase deposit £1.76 and 6 monthly.....	£2.12.8
<b>FMT1</b> Power pack ready drilled chassis complete.....	
<b>FMT2</b> Is a new tuner in a modern case, green, which can be used for shelf or cabinet mounting, and has the space for power supplies if required. Supplied complete with four EF80 valves.....	£7.17.6
Hire purchase deposit £1.11.6 and 6 monthly.....	£1.4.4
<b>FMT2</b> With power. Complete kit.....	£9.15.0
Hire purchase deposit £1.19.0 and 6 monthly.....	£1.9.4
<b>FMT3</b> Is the fringe version and should be used when farther than 70 miles from the transmitter. Supplied complete with 6 valves.....	£9.12.6
Hire purchase deposit £1.18.6 and 6 monthly.....	£1.9.0
<b>FMT3</b> With power. Complete kit.....	£12.0.0
Hire purchase deposit £2.8.0 and 8 monthly.....	£1.6.8
The instruction book is included in all kits, but otherwise 2/6.	

### JASON SWITCHED TUNERS

The JTV/2 and Mercury 2 are both of the pre-set station type with the addition of BBC and ITA sound. They use the latest "Fireball" turret and the A.F.C. ensures freedom from drift. The Mercury 2 is for cabinet mounting with external power, the JTV/2 has the same tuning heart, with power supplies mounted in a case, and can be used for shelf or cabinet.

JTV/2 Complete with valves and book.....	£115.0
Hire purchase deposit £3.0.0 and 12 monthly.....	£11.6
Mercury 2 complete with valves and book.....	£10.15.0
Hire purchase deposit £2.3.0 and 8 monthly.....	£1.4.0
Power pack kit for Mercury 2 ready drilled chassis.....	£2.12.8
Instruction book for switched tuners 4/-.	

**REQUIRED CHANNELS MUST BE SPECIFIED FOR SWITCHED TUNERS**  
A more detailed list can be sent upon request.  
**ALL JASON TUNERS ARE ON DEMONSTRATION, AND ALWAYS IN STOCK.**

### READY BUILT TUNER

F.M. Tuner Aligned and assembled, using Philips tuning head with EC85, EF85, EF85, EZ81 and EM81, with 2 diodes. **SELF POWERED.** In enamelled metal case. **UNREPEATABLE BARGAIN.**.....CASH **£8.8.0**

### JASON ARGUS

Transistor 2 wave band A.M. Tuner in attractive wooden case.....KIA **£7.10.0**

## MARTIN RECORDAKITS

We are able to offer for the first time, a proprietary range of Recorders in kit or assembled form. This enables you to take advantage of mass production techniques and prices, should you wish to assemble yourself. The components having all the improvements B.S.R. and Collaro make from time to time, heads, etc. The amplifiers are packed in special cartons with instructions which enable anyone to build. We are confident you will find these Recorders very good value, they have been built up to a standard and not down to a price.

<b>B.S.R. TD8</b> Monardeck, latest model 5 1/2 in. spools.....	CASH	£9.9.0
Hire purchase deposit £1.19.0 and 6 monthly.....		£1.8.4
<b>Tape Amplifier</b> for B.S.R. deck, printed circuit ready wired, with EC85, EC82, EM85 and EZ81. Complete with all plugs, sockets, panels, knobs, etc. The whole amplifier mounts on to the deck, making a self contained unit.....	CASH PRICE	£3.8.0
Hire purchase deposit £1.14.0 and 6 monthly.....		£1.5.8
<b>Cabinet</b> for above including 7 x 4 in. speaker.....	CASH	£4.4.0
Total kit as above.....	CASH	£22.0.0
Hire purchase deposit £4.19.0 and 12 monthly.....		£1.12.1
The above recorder can be supplied complete with Mic: tape assembled and tested for.....	CASH PRICE	£25.0.0
Hire purchase deposit £5.0.0 and 12 monthly.....		£1.16.8
<b>Collaro</b> Studio Deck. Very latest model 3 speeds.....	CASH	£12.10.0
Hire purchase deposit £2.10.0 and 6 monthly.....		£1.7.6
<b>Tape Amplifier</b> for Studio Deck, with ready wired printed circuit, control and input panels, mains and output trans., complete with knobs, plans, screws, etc., EF86, EC83, EM84, EZ81, OA81 and 2 EL84, 3 waste output. Magic eye, Radio and Mic. inputs. EX L/8 socket, Tone control. Can be used as an amplifier. <b>COMPLETE CASH</b> .....	£11.11.0	
Hire purchase deposit £2.7.0 and 8 monthly.....		£1.5.6

<b>Cabinet</b> for above including 9 x 5 in. speaker.....	CASH	£5.5.0
Total kit as above.....	CASH	£29.0.0
Hire purchase deposit £6.0.0 and 12 monthly.....		£2.2.8

We can supply the above recorder, complete with tape and Mic., in a DE LUXE cabinet, assembled for.....**£35.0.0**

**THIS MACHINE IS LISTED £41.0.0 BY MAKERS AND IS A VERY GOOD BUY.**

Hire purchase deposit £7.0.0 and 12 monthly.....	£2.11.4
--	---------

<b>Tape</b> Pre-amplifier, for recording and playback, as above less output stage, with power supplies.....	£8.8.0
Hire purchase deposit £1.14.0 and 6 monthly.....	£1.8.8

**Microphone** for the above recorders, Acoas MIC 40, 25/-, 5/C plug 4/6.

<b>Synchrotape</b> 5 in. 600ft. 15/-	5 in. 900ft. 19/6
Finest 6 1/2 in. 850ft. 19/6	5 1/2 in. 1200ft. 22/6
Boxed 7 in. 1200ft. 22/6	7 in. 1800ft. 32/6

<b>Tape Recorder</b> Speaker Cabinet, corner, 20 x 10 in. High class finish in two-tone Grey "Vynair".....	£2.15.0
With 9 x 5 in. high flux speaker.....	£4.0.0

### GRAMOPHONE EQUIPMENT

<b>B.S.R. UA14</b> TC8/H cartridge.....	£7.15.0
Hire purchase deposit £1.11.0 and 6 monthly.....	£1.4.0
<b>Collaro</b> O60 Autochanger "O" cartridge.....	£3.15.0
Hire purchase deposit £1.15.0 and 6 monthly.....	£1.6.8
<b>Garrard</b> 'Autoslim' 67/3 cartridge.....	£9.3.4
Hire purchase deposit £1.17.4 and 6 monthly.....	£1.7.8

**MINI AMP** P/W November issue, Resistors 6/-, V/C 6/-, Condensers 9/-, Transistors 7/6, 9/-, OC71 6/6, OC72 9/-, T/T3 13/-, T/T2 8/6, PP9 3/6, Press studs 1/-, Speaker 7 x 4 in. 17/6, Group/B 2/6. All the above, if ordered at one time, £4.15.0. Diagram may be obtained from "Practical Wireless", 5/-.

### TRANSISTORS

MULLARD HAVE REDUCED THE PRICE OF MANY TYPES TO OC44 11/-, OC45 10/-, OC70 6/6, OC71 6/6, OC72 8/-, OC73 8/-, OC78 8/-, OC81 9/-, ABOVE ARE THEIR NEW LIST PRICES. WHY BUY SURPLUS?  
**MATCHED PAIRS ONLY.** Mullard OC72 at 16/- pair.

### — TRANSISTOR SUPERHET KITS —

#### "PRACTICAL WIRELESS" POCKET SUPERHET

OSMOR printed circuit version. Osmor Rod Aerial 10/-. L.F.T.s and Osc. Coils, 22/6. Osmor Driver, 11/6. Osmor Output, 10/6. Set MULLARD transistors, 53/6, OA81 Diode, 3/-, J.B. Gang, 11/-. Trimmers, 2/8 pr. Set Condensers, 15/-, Set Resistors, 6/6. Ardente Vol. Control, 3/-, Ardente W/C, 3/6. Speaker, 19/10. Hardware, 4/6. Printed Circuit, 9/-, Case and Knob, 7/6. Dial, 6d. Battery PP4, 2/-, Leadlit giving full illustrated details, 1/9. All the above components if purchased at one time £9.9.0. OSMOR undertake to align this receiver for a charge of 10/-. Modification Kit, 10/-.

#### "WEYRAD"

WEYMOUTH RADIO 6 Transistor Superhet using the P50 coils, as they advertise in this journal. P50/LAC Osc. Coil, 5/4. P50/20C 1st and 2nd L.F.T.s, 6/7 ea. P50/30C 3rd L.F.T., 8/-. RASW Rod Aerial, 12/6. LFY22 Driver, 9/6. PCA1/PRINTED Circuit, 9/6. Instruction Book, 2/-, Set Resistors, 7/6. Vol. Control D.P.F., 5/6. Set Condensers, 20/-, J.B. Gang, 11/-, Beehive Trimmers, 1/3 ea. W/C, 3/6. Dial and Knob, 3/6. Battery PP11, 5/6. OA81, 3/-, Set MULLARD transistors, 53/6. 35 ohm 5 in. round L/8, 14/-, Car Aerial Coupling Coil, 1/-.

## 43 SURBITON ROAD, KINGSTON-UPON-THAMES, SURREY

Established over 30 years Telephone KIN 5549

We pay all postage and insurance. All orders despatched same day. Money refund guarantee. Hours: 9 a.m.—6 p.m. (1 p.m. Wednesday) We do not close for lunch. Open all day Saturday.

# HOME RADIO OF MITCHAM

(Dept. P), 187 London Road, Mitcham, Surrey.  
MIT 3282  
Shop hours 9 a.m. to 6.30 p.m. Wed. 9 a.m. to 1 p.m.

## WE ARE ACTUAL STOCKISTS FOR HEATHKITS

INCLUDING the wonderful new EW-1 electronic workshop.

20 exciting experiments with this one kit, transistor radios, intercom. sets, burglar alarms, electric eye, TV silencer, etc. No soldering! No tools required! Wonderful and instructive gift for any youngster (and Dad). Learn basic principles of radio and electronics this easy and absorbing way. Kit complete with circuit boards, transistors, speakers, earphone, photo-cell, relay, resistors, condensers, and comprehensive instruction manual. PRICE £7.18.0, post paid.

## IMPORTANT


Closed all day  
**MONDAY, JAN. 1**  
for Stocktaking

## SUPER CATALOGUE

- 170 PAGES
- 600 PICTURES
- 5000 ITEMS

2/- PLUS 1/- POST

## NEW—JASON ARGUS A.M. TUNER

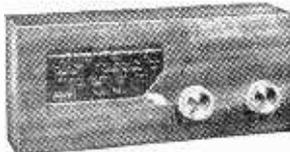

Entirely new three-transistor Superhet AM Tuner for Medium and Long waves. Self contained high efficiency ferrite rod aerial gives good reception of main Continental stations. Complete with neat

polished case size 9 x 4 x 2½ in. Ideal for tape-recording or in conjunction with FM tuner. PRICE of KIT £7.10.0, post 1/6d. MERCURY 11. Switched Tuner, covering Home, Third and Light on VHF, plus ITV and BBC television sound. Full constructional data PRICE 3/6d., post 6d. PRICE of KIT £12.0.0 FMT/2 TUNER. Enjoy crystal clear Hi-Fi reception with a Jason FM/VHF tuner. Manual tuned version in neat shelf mounting case with own power unit. Constructional data 2/6d., post 6d. PRICE of KIT £11.7.6.



## AVO MULTIMINOR

A well designed, simple to use, rectifier moving coil Test Meter of pocket size and sturdy construction, complete with rubber moulded test leads and clips. 19 different ranges covering AC and DC voltage, DC current, and resistance up to 2 megohms. PRICE £9.10.0, post 1/6.

## CELESTION P44 12" SPEAKER

This popular High Fidelity Speaker is now available again in 3 and 15 ohms. 12in. unit with heavy duty magnet, and suitable for high quality domestic use or for public address and dance halls, etc.

PRICE £3.15.0, post 2/6.

## STILL THE BEST SHORT-WAVE GLOBE-KING 100/A



Explore the world from your own armchair. Build this truly amazing little one-valver which gives really long distance at minimum cost. Learn Morse and listen in to shipping and amateurs, etc. Extra stage can be added later. 100/A kit with three coils covering 10 to 100 metres, PRICE £3.19.6, post 1/6. WONDERFUL GIFT FOR A YOUNGSTER.

We carry full range **EDDYSTONE** RECEIVERS & COMPONENTS

## completely revised new edition

## Radio and Electronic Laboratory Handbook

M. G. SCROGGIE, B.Sc., M.I.E.E.

This well-known practical handbook has been completely revised and now covers techniques applicable to many fields beyond that of radio. The extensive revision necessary was due primarily to the growing use of semi-conductor devices, including transistors. Electronic instruments have increased in number, cost and complexity and in this handbook amateur and professional technicians will find invaluable guidance.

55s. net, by post 57s. 3d. 537 pp. 7th edition

from leading booksellers

Published for "Wireless World" by

ILIFFE BOOKS Ltd.

Dorset House • Stamford Street • London S.E.1

# FIVE-TRANSISTOR POCKET RADIO

COMPLETELY PORTABLE,  
NO AERIAL OR EARTH REQUIRED

- ★ Size 4¾x3¼x1½ in.
- ★ Output 200mW
- ★ 5 First quality transistors
- ★ Push-pull output
- ★ Fitted 2¼ in. high-flux moving coil speaker



- ★ Medium and long wave
- ★ Internal high gain ferrox aerial
- ★ Twin coloured case in red and black
- ★ All parts available separately
- ★ Circuit-diagram 1/6. Free with kit.

PRICE ONLY **£2/19/6** plus 3/6 post and packing

RADIO & TV LTD. (Dept. 5T)  
23 High Street, Acton, London, W.3.

# The

# BASS

# Reflex

# Cabinet

## THEORY AND PRACTICAL DESIGN

By J. B. Dance

ONE of the most difficult problems encountered in the design of "Hi-Fi" equipment is that of obtaining a level and undistorted bass response. For this reason the design of the loudspeaker cabinet should be undertaken most carefully.

### Unmounted Loudspeaker

The vibrating cone of a moving coil loudspeaker is small compared with the wavelength of low frequency sounds in air. If a loudspeaker is used at low frequencies without any baffle whatsoever, the air which is pushed forward by the loudspeaker cone will merely pass around the outside of the loudspeaker to fill the partial vacuum created at the rear of the cone. Similarly when the cone moves backwards, air will pass from the rear to the front of the loudspeaker.

The loudspeaker cone is intended to set the whole of the air in the room in vibration, but if no baffle is used, the air slips around the edges of the loudspeaker at low frequencies and the effect on the air in the room is very small indeed. The air currents (i.e. the sounds) are thus short circuited. The use of a baffle will prevent this short circuiting of the air currents provided that the baffle is not so small that the air can pass easily around the outside of it from the front to the back of the loudspeaker and vice-versa at the frequency in question.

### High Frequencies

At high frequencies, however, the movements of the cone are so rapid that there is not enough time for the air to move between the back and front of the loudspeaker and so to equalise completely the pressures before the direction of movement of the loudspeaker cone has been reversed.

One has only to compare the sound from an unmounted loudspeaker with the sound from a properly mounted loudspeaker to appreciate that the unmounted loudspeaker produces almost negligible sound when the input frequency is low. The volume of the middle frequencies is also much less than that from a correctly mounted loudspeaker. This effect is very prominent with a large unmounted loudspeaker, but is even worse with a small unmounted loudspeaker, as the air can pass from the back to the front of the cone much more easily and quickly than in the case of a large loudspeaker.

### Loudspeaker Resonance

The resonance curve of a typical loudspeaker of nominal impedance  $15\Omega$  is shown in Fig. 1. In this

graph the actual impedance of the loudspeaker in ohms is plotted against the input frequency. The graph covers only bass frequencies; the impedance rises somewhat at high frequencies. The peak, in the case shown at 65c/s, is at the natural resonant frequency of the loudspeaker; that is, at the frequency at which the loudspeaker cone vibrates if the cone is gently tapped with the finger. The loudspeaker cone will vibrate with a very large amplitude if quite a small input of this particular frequency is applied to the loudspeaker terminals.

### Bass Reflex

A simple system which gives an equally satisfactory performance consists of a plain, closed, cabinet with an opening at the front; the volume of the cabinet and opening are so calculated that the air inside the cabinet resonates with the air in the vent at the same frequency as that of the fundamental resonance of the loudspeaker used. The sound emerging from the vent is in phase with that from the loudspeaker cone. Hence the bass reflex cabinet is also known as the acoustical phase inverter.

The size of the loudspeaker cabinet required for this arrangement can be appreciably reduced by fitting a pipe or wooden column which projects back into the cabinet from the opening at the front as shown in Fig. 2. The opening below the loudspeaker opening is known as the vent.

### Design

The first problem one meets when designing a bass reflex cabinet is that of calculating the size of the enclosure and vent which will enable the cabinet to resonate at the same frequency as the loudspeaker. In order to do this, one must know the fundamental resonant frequency of the loudspeaker. The manufacturers of all good loudspeakers supply a nominal value for the resonant frequency. However, this frequency usually decreases by about 10% to 15% after the loudspeaker has been in use for some hours. This decrease occurs because the suspension becomes weaker after a few hours of use.

It is therefore best to measure the resonant frequency of the loudspeaker experimentally if possible, not when the loudspeaker is quite new, but when it has been used for about twenty hours or so fastened to a temporary mounting and used at reasonably high power. The value obtained can then be used in the calculation. If for any reason the frequency is not measured experimentally, the manufacturer's figure may be used, but it is wise to reduce this figure by up to 10% to allow for the suspension becoming slightly weaker with use.

### Experimental Determination

The fundamental resonant frequency of the loudspeaker may be determined experimentally in the following way. An audio signal generator should be used to feed an audio power amplifier connected to the unmounted loudspeaker under test. An A.C. ammeter should be placed in one of the leads to the loudspeaker as shown in Fig. 3. The input power from the amplifier to the loudspeaker should not exceed a small fraction of a watt and therefore a reasonably sensitive ammeter should be used, say 0-½A. The amplitude of the cone movement should be checked (by touching the cone) to make sure that it is not too large.

As the signal generator is tuned and its output kept fairly constant, the current passing through the loudspeaker and indicated by the ammeter will be found to have a definite minimum value at the loudspeaker resonant frequency. This frequency can then be read from the scale of the audio generator.

### The Helmholtz Resonator

The cabinet resonates in the same way as a Helmholtz resonator. (If one blows across the top of a suitable bottle, a similar resonance effect can be noticed.) The theory of the Helmholtz resonator has been worked out in detail and it can be shown that the resonant frequency is determined by the volume of the enclosure itself and by the dimensions of the opening or vent. The air in the enclosure acts in a way similar to that of a condenser in an electrical resonant circuit and the air in the vent resembles an inductance. In the same way that various combinations of inductance and capacitance can resonate at the same frequency, it is found that Helmholtz resonators or loudspeaker cabinets can be designed to operate at the

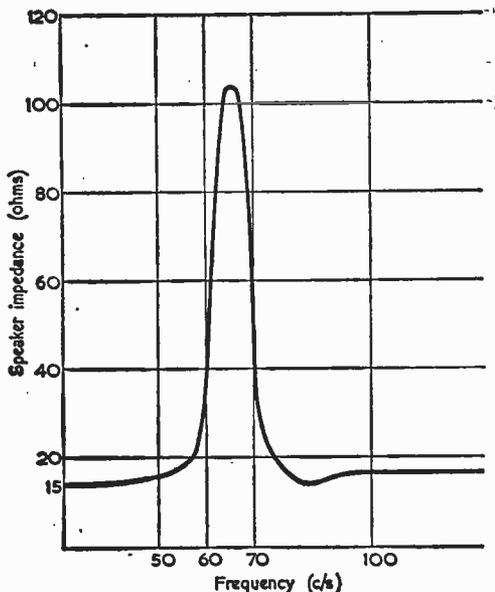


Fig. 1—A typical resonance curve for a 15Ω speaker with a 65c/s resonance.

same frequency and yet have different vent sizes and internal volumes. Once the vent size is chosen, however, there is only one particular volume which the interior of the cabinet can have if it is to resonate at the same frequency as that of the loudspeaker cone.

### Formula

According to Rayleigh, the resonant frequency of a Helmholtz resonator is

$$f = \frac{v}{2\pi} \sqrt{\left\{ \frac{A}{C(L + \frac{1}{2}\sqrt{\pi A})} \right\}}$$

where  $v$  = the speed of sound in inches per second.  
 $\pi$  = 3.142.

$A$  = Cross sectional area of vent in square inches.

$C$  = Volume of air in the cabinet in cubic inches.

$L$  = Length of vent in inches (including thickness of front panel).

This equation can be squared all through and transposed to enable us to obtain the cabinet volume.

$$C = \frac{V^2 A}{4\pi^2 f^2 (L + \frac{1}{2}\sqrt{\pi A})}$$

Substituting for the value for the velocity of sound (13,500 inches per sec.) and for  $\pi$

$$C = \frac{4,614,000A}{f^2 (L + 0.886\sqrt{A})}$$

### The Vent

Before the calculation can be continued, the dimensions of the vent must be decided. Opinions differ somewhat as to the most satisfactory values for these. It is generally agreed that the vent should not extend too far into the cabinet, and that the length of the vent tunnel should not be greater than about one twelfth of the wavelength of the resonant frequency of the loudspeaker cone; neither should the length of the vent be so great that it extends more than half way between the front and back of the loudspeaker. It is not even necessary to make a vent tunnel at all, for if one merely cuts a hole in the front panel, one will have a vent of a length equal to the thickness of the front panel. If this course is adopted, however, the cabinet will have to be considerably larger than is necessary if it is to resonate at the desired frequency. Wood is expensive and space in a room is scarce, so a vent tunnel is usually employed. It can be seen from the equations that a long vent will enable a smaller cabinet to be used.

The size of the vent hole is also important; i.e. its cross sectional area,  $A$ . Some experts advise that the area of the vent should be equal to the area of the effective part of the loudspeaker cone at low frequencies, whilst others think that any reasonable area (say between one half and double the effective loudspeaker cone area) will give satisfactory results. The effective cone area is the area of the sides of the cone (not including the corrugated suspension at the edge) projected on to an imaginary circle at the front of the loudspeaker.

The area of the vent appears in both the numerator and denominator of the above equations, but the term in the numerator is most important; the use of a small vent area will therefore

(Continued on page 849)

**NOW!**  
**YOU can MASTER ELECTRONICS!**

**BRITAIN'S MOST COMPREHENSIVE PRACTICAL COURSE IN RADIO • ELECTRONICS TELEVISION!**


**THESE SPECIAL TRAINING KITS — YOURS TO KEEP**



**Multi-Range TEST METER**



**CATHODE RAY OSCILLOSCOPE**

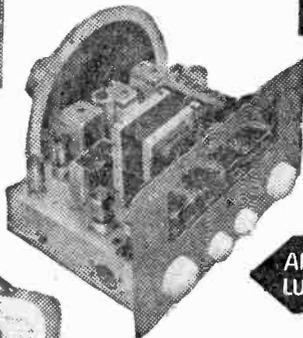

**AM and VHF/FM LUXURY RECEIVER**



**SIGNAL GENERATOR**




**Complete set of Picture Way books and Experimental Manuals**

**LEARN BY BUILDING NOW** for your **CAREER • HOBBY OWN BUSINESS**

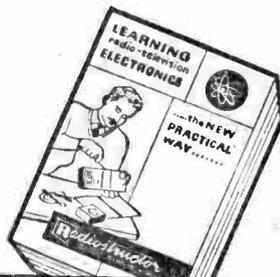**YOU RECEIVE**

- Complete kits of equipment as illustrated.
- Complete set of experimental manuals.
- Complete set of "picture-way" theory books.
- Modern test-yourself examination sheets.
- Study programme.
- Unlimited consultation with Tutors.



**FREE BROCHURE**  
**POST NOW**

**RADIOSTRUCTOR**

TO RADIOSTRUCTOR (DEPT. M.82) READING, BERKS.

Name \_\_\_\_\_ **BLOCK**

Address \_\_\_\_\_ **CAPS**

\_\_\_\_\_ **PLEASE**

(We do not employ representatives)

1/62


# CODAR "CLIPPER" ALL BAND RECEIVERS 10-2000 METRES

LISTEN TO AMATEURS, AIRCRAFT, SHIPPING, SHORT, MEDIUM, LONG WAVE BROADCAST STATIONS THROUGHOUT THE WORLD.

## THE MINI-CLIPPER

The miniature valve radio with the BIG SET features. Covers all Short, Medium, Long waves 10-2000 metres (5 coils). Smart all satin silver ali. front panel with engraved dials, etc. Ball bearing, air spaced variables. Size only 6½ x 3½ x 4in. Battery lasts months. No drilling. Total building cost including punched chassis, valve, front panel, one coil for 20-60 metres, nuts, bolts, wire, Step-by-step pictorial plans, 39/6. P. & P. 2/-. Additional coils and electrical bandsread optional extras. Parts sold separately. Full plans, parts list, 2/-.

39/6

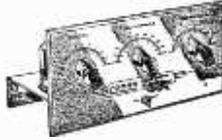

## THE SUPER CLIPPER 88/6

This world-famous hybrid receiver has achieved remarkable success. Tremendous performance with Hi-gain valve detector PLUS two Ediswan transistor amplifiers which are supplied assembled, only 3 wires to connect. Large precision dial, 7 x 4in., with 2 pointers, bandset and bandsread, dual slow-motion drivers, air spaced variables. Punched chassis 8 x 5½in. Batteries last months. Covers 10-2000 metres (5 coils). Total building cost including chassis, valve, 2 transistor stages, 2 coils 20-60 and 55-190 metres. Step-by-step pictorial plans, nuts, bolts, wire 88/6. P. & P. 2/6. Plans only, 2/6. **THE CLIPPER.** As above but one transistor stage, 79/6. P. & P. 2/6. Optional Front Panel, Silver Hammer finish, all holes, 6/9.



## THE CLIPPER CR 45

£6.17.6




This A.C. Mains receiver is the latest model in the famous CLIPPER Series and combines really top performance with superb professional finish. It is the finest ALL BAND receiver at the price with a new high gain circuit using ECC81 double triode, EL84 output, EZ80 full wave rectifier. Power output 3½ watts for 2/3 ohm speaker. Covers 10-2000 metres (5 coils). World-wide reception. Outstanding features include 3 planetary slow motion drives, separate electrical bandsread, air spaced low loss variables, satin silver dials, silver hammer front panel. Total building cost, including 10 x 5½in. punched chassis, valves, front panel, 2 coils 20-60 and 55-190 metres, nuts, bolts, wire, etc., 10 pages pictorial plans, £6.17.6. P. & P. 3/6. Optional extra. Modern styled Cabinet, rear panel, silver hammer finish, 27/6. Parts sold separately Full plans, parts list, 10 pages, 3/6 post free.

No technical knowledge is required to build these fine receivers. Send 3d. stamp for leaflets. Details now available for the new 1962 CR66 AC Communication Superhet. We wish all P.W. readers a Happy Xmas and prosperous New Year. 73's from G3IRE and G3IPA.

**CODAR RADIO COMPANY, COLEBROOK ROAD, SOUTHWICK, SUSSEX**

## INSTALLING HI-FI?

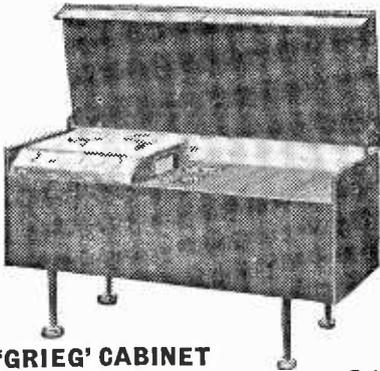

### THE 'GRIEG' CABINET HOUSES IT ALL HANDSOMELY: 24 gns.

The newest and largest of our wide range of hi-fi furniture. The Grieg can house your tape-deck, turntable, pre-amp, amplifier, tuner; takes a Ferrograph tape recorder, complete in its case.

Finishes: medium walnut or mahogany. Overall Size: 48in. long, 21in. deep, 18in. high plus 9in. legs. Mounting boards: 20in. x 19in. and 26in. x 19in.

Write today for details of full range and nearest stockists.

**RECORD HOUSING** (DEPT. PW162)  
BROOK ROAD, LONDON N.22

Please state location of convenient shopping centres.

## SOUTHERN RADIO'S WIRELESS BARGAINS

**PORTABLE TEST METERS.** (As featured in March issue, pages 1005 to 1010) 0-5000 ohms; 0-60 mA; 0-15 v., 0-3 v., 12/6 each.

**TRANSMITTER RECEIVERS.** "Type 38" with 5 valves. New but untested. No guarantee, 25/- each. Post paid.

**ATTACHMENTS FOR "38" TRANSMITTER-RECEIVER;** Headphones, 15/6; Throat Microphones, 4/6; Junction Boxes, 2/6; Aerials, No. 1, 2/9, No. 2, 5/3; Webbing, 4/-; Haversacks, 5/6; Valves—A.R.P.12 4/6. A.T.P.4, 3/6. Set of five valves, 19/-. Postage on each item 1/6 extra (except valves).

**ATTACHMENTS FOR "18" TRANSRECEIVER.** Headphones, 15/6; Microphone 4s, 12/6; Aerials, 5/-; Morse Key, 6/6; Valves—A.R.P.12, 4/6, A.T.P.4, 3/6, A.R.8, 7/6; Set of six valves, 25/- Official booklet "18" T-R Circuits, etc., 6/6 post paid. Postage extra (except valves) 1/6 each item.

**QUARTZ CRYSTALS.** Types F.T.241/F.T.243 2 pin ½in. spacing. F.T.241 20 to 38.9 Mc/s (54th and 72nd Harmonic). F.T.243 5700 to 8650 kc/s (Fundamental), 4/6 each. Lists of available frequencies on request. Crystal Holders for F.T.241/243, 1/3. F.T.241/243 Crystals. New but not guaranteed (ideal for using the case or regrounding). 12/6 per dozen. Post paid.

**RECORDING BLANKS.** New 13in., 6/- each or 15 complete in Tin, £4.

**BOMBSIGHT COMPUTERS.** Ex-R.A.F. Wealth of gears, motors, blowers, etc. Ideal for experimenters, £3.12.6, carr. paid.

**RESISTANCES.** 100 Ass'd. Useful values, new, 12/6 per 100.

**CONDENSERS.** 100 Ass. Mica Elec., Tub., etc. New 15/- per 100.

**MORSE PRACTICE SETS.** Key with Buzzer on Base, with battery, 12/6, postage 2/-.

**LUFBRA HOLE CUTTERS.** Adjustable. ½in. to 3½in., 7/3.

**STAR IDENTIFIERS.** I-AN. Covers both hemispheres, 5/6.

**VISUAL INDICATORS (10Q4).** Type 3 with 2 meter movements, 2 neons. New 12/-.

**MAGNETS.** Strong Bar, 2in. x ½in. 1/6 each.

**COMMAND RECEIVERS B.C. 454** 3-6 Mc/s, B.C. 455 6-9 Mc/s. Complete with 6 valves, 47/6 each.


POST OR CARRIAGE EXTRA, FULL LIST OF RADIO BOOKS, ETC., 3d.

**SOUTHERN RADIO SUPPLY LTD.**

11 LITTLE NEWPORT ST., LONDON W.C.2. GER. 6653

(Continued from page 846)

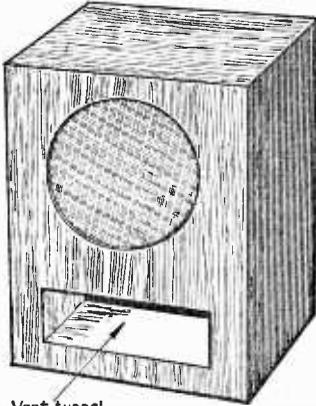enable a smaller cabinet to be used than the use of a large vent, other things being equal. The vent can be of any shape, but will normally be of rectangular cross section to simplify construction of the tunnel. Circular vents are sometimes used.



Vent tunnel

Fig. 2—A bass reflex cabinet showing the rectangular vent and tunnel beneath the speaker.

**Design Example**

Let us suppose that we wish to design a bass reflex cabinet for use with a loudspeaker of a nominal diameter of 10in. which has a fundamental resonant frequency, measured as described, of 65c/s.

It is first necessary to insert values for the length and cross sectional area of the vent in the equation in order to try to design a cabinet of suitable dimensions.

Let us assume that the vent is to be 5in. long and that the cross sectional area of the vent opening is to be equal to the area of the effective part of the loudspeaker cone. The average 10in. loudspeaker will have an effective cone diameter of about 8.5in. and an effective cone radius of half this value, i.e. 4.25in. The area of the vent will equal  $\pi r^2$ ; where  $r=4.25$  and  $\pi=3.142$ ; the area= $56.75\text{sq. in.}$

**Calculation**

Putting these values into the last equation:—  

$$C = \frac{4,614,000 \times 56.75}{(65)^2(5 + 0.886\sqrt{[56.75]})}$$

$$C = \frac{61,980}{(5 + 6.67)} = 531\text{cu. in.}$$

This is the volume of air which should be enclosed in the cabinet and does not include the volume of air and wood in the vent. In order to obtain a value for the total volume of the inside of the cabinet, it is necessary to add to the above figure the following quantities:—

(1) The volume of the vent (i.e. the external volume of the vent as seen from inside the cabinet including the volume of air and the wood from which the vent is made).

(2) The volume of the loudspeaker. The presence of the loudspeaker reduces the volume of air in the cabinet. If the volume of the loudspeaker is quoted by the makers, this figure should be used. Otherwise the approximate volume of the loudspeaker can be obtained from the data given in Table 1.

(3) The estimated volume of any wooden struts which are to be used to strengthen the cabinet.

About 100cu. in. may be allowed for a fairly small cabinet and more for a large one.

(4) As it is much easier to reduce the volume of the completed cabinet by fastening a block of wood in it than it is to raise the frequency by extending the vent inwards, it is wise to add an additional hundred cubic inches or so which can be kept in reserve. In the design being considered, the volume of air in the vent tunnel is  $56.75 \times 4.25$  which is about 241cu.in. if the wood is to be  $\frac{1}{2}$ in. thick. About 80cu.in. may be allowed for the wood of the vent tunnel. From Table 1, the volume of the 10in. loudspeaker will be approximately 400cu.in.

Adding these quantities to the 531cu.in. obtained above, we find that the total internal volume of the cabinet should be approximately 6232cu.in.

**Possible Shapes**

A number of different shapes of cabinet can be used to satisfy the condition that the total internal volume must be approximately 6232cu.in. The vertical height of the cabinet must be great enough to accommodate the loudspeaker and vent above one another. It is therefore wise to start by estimating the approximate minimum height. For this purpose let us assume that the vent area of  $56.75\text{sq.in.}$  is to be obtained by making a hole 6in. in vertical height and 9.46in. in length in the front of the cabinet. Allow minimum dimensions of:—

- top of the cabinet to top of the loudspeaker 1in.
  - distance across loudspeaker, allowing space for fixing ... .. 11in.
  - distance from the bottom of the loudspeaker to the top of the vent ... .. 2in.
  - distance across vent ... .. 6in.
  - distance between bottom of vent and bottom of cabinet ... .. 2in.
- Therefore, the total minimum height of the cabinet is 22in.

Nominal Diameter of Loudspeaker (Inches)	Approximate volume of air displaced by speaker (Cubic Inches)
6	150
8	250
10	400
12	630
15	1350
18	2400

Table 1—The average volume of air displaced by typical loudspeakers of various sizes.

The vertical height must therefore be at least 22in. Similarly the breadth should be at least 12in. to accommodate the loudspeaker and vent easily. The depth of the cabinet must be at least 10in. or the requirement that the vent tunnel length must

not exceed half the length of the cabinet will not be met.

Three lengths must now be chosen which are possible values for the length, width and height. These values must be compatible with the foregoing requirements and when all three lengths, expressed in inches, are multiplied together the result must be approximately 6232cu.in. Some examples of the possible dimensions are:—

$$\begin{aligned} 29\frac{1}{2} \times 15 \times 14 &= 6205\text{cu.in.} \\ 26 \times 16 \times 15 &= 6240\text{cu.in.} \\ 24 \times 20 \times 13 &= 6240\text{cu.in.} \\ 25 \times 18 \times 14 &= 6300\text{cu.in.} \end{aligned}$$

There are, of course, many other possibilities and the constructor must now make his own choice from the possible dimensions. As the tunnel will not extend half way through the cabinet, the calculation could be carried out again with a longer tunnel length to obtain the smallest possible cabinet size.

#### Without Tunnel

It is interesting to compare the above results with the dimensions which would have been necessary if no tunnel had been employed. The length of the vent would then have been equal to the thickness of the wood used for the front panel, say  $\frac{1}{2}$ in. The equation would then be:—

$$C = \frac{61,980}{(0.75 + 6.67)} = 8354\text{cu. in.}$$

The volume of the vent is now zero. Adding the volume of the loudspeaker, the estimated volume of the supporting struts and the reserve volume to the 8354cu.in. obtained above, we find the total internal cabinet volume to be 8954cu.in.

Thus, the omission of the internal vent tunnel requires the volume to be increased from some 6200cu.in. to some 8954cu.in. One of the sets of possible cabinet dimensions with a 5in. vent tunnel was 29 $\frac{1}{2}$ in. x 15in. x 14in.; without the tunnel this would have to be increased to 42 $\frac{1}{2}$ in. x 15in. x 14in. or to some similar dimensions. Thus much more wood would be required and the cost of the cabinet might easily be increased by 50%.

It must be emphasised that the dimensions quoted above are all internal dimensions. The external dimensions of the cabinet will be larger than the internal dimensions by the thickness of the wood used.

#### Other Loudspeakers

The results obtained above apply to a loudspeaker with a resonant frequency of 65c/s. If a loudspeaker with a fundamental resonant frequency of half this value were used, namely one resonating at 32.5c/s, the volume of air enclosed in the cabinet should be four times as great. Thus the cabinet will be very much larger; it will also require much more support or the use of thicker wood if undesirable vibrations are not going to take place. Thus the cost of the cabinet is increased enormously, but a much better bass response should be obtained.

If the loudspeaker had a resonant frequency of

32.5c/s and all other factors were as stated in the previous example a typical size for the cabinet would be 40in. x 30in. x 21in. with a 5in. tunnel fitted to the vent. At this stage, it would be well worth while performing the calculation again with a longer tunnel in order to reduce the size of the cabinet. One cannot choose a suitable value for the vent until the calculation has been completed and one knows the cabinet depth; it is therefore necessary to insert an estimate for the length of the vent in order to find the approximate cabinet dimensions. The calculation can then be repeated when the exact vent length has been chosen.

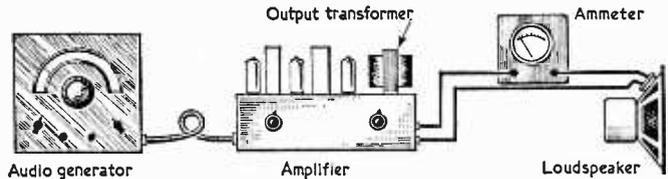


Fig. 3—Determining the fundamental resonant frequency of a loudspeaker.

#### Construction

Cabinets are normally made of wood, but brick and concrete can be used very successfully. Assuming wood is to be used, it should be quite thick—at least half an inch for the smaller cabinets, but a thickness of an inch is desirable for the larger ones. Cabinets are made in which the walls consist of a double thickness of wood, the space between the inner and outer walls being filled with sand. Such cabinets are extremely heavy but comparatively cheap to build and certainly very effective.

It is desirable to fix adjoining pieces of wood together with glue and also with screws placed three or four inches apart. A hundred or so screws at least will be required. Countersunk screws should be employed, as they can then be fitted with their heads below the surface of the wood. Plastic wood can be used to cover the heads of the screws. The plastic wood used should be chosen to match the colour of the other wood as closely as possible and it should be applied layer by layer, allowing each layer to set before the next one is applied. The plastic wood should finally protrude slightly above the level of the cabinet before it is rubbed down with fine sandpaper. The back of the cabinet should be screwed in position using sufficient screws, but it should not be glued or it will not be easy to make any necessary adjustments.

#### Strengthening

It is most important that the panels be strengthened with an adequate number of supporting strips of thick wood. Many poorly constructed cabinets are almost useless owing to wall vibration at large inputs. The amount of supporting struts required varies greatly with the size of the cabinet, thickness of the wood used, etc. and no definite guide can be given.

(To be continued)

# WEYRAD

IMPROVED COMPONENTS FOR THE 6-TRANSISTOR  
2-WAVE SUPERHET RECEIVER

NEW ROD AERIAL AND DRIVER TRANSFORMER FOR SIMPLER ASSEMBLY  
AND HIGHER PERFORMANCE

**ROD AERIAL—RA2W**

6 in. long, 3/8 in. diameter. connections to tags  
on Coils. For 208 pF tuning capacity ... .. 12/8  
Car Aerial coupling Coil ... .. 1/-

**OSCILLATOR COIL—P50/1AC**

M.W. covered with 176 pF tuning capacity.  
L.W. by extra padder ... .. 5/4

**I.F. TRANSFORMERS**

1st and 2nd Stage—P50/2CC ... .. 5/7  
3rd Stage—P50/3CC ... .. (2 required) 6/-

**DRIVER TRANSFORMER—LFD4T**

redesigned to reduce size and improve perform-  
ance. Six spills for mounting and connections 9/8

**PRINTED CIRCUIT—PCAT**


Size 2 3/4 in. x 8 1/4 in. Ready drilled and printed with component positions ... .. 9/6

WE CAN NOW OFFER A CIRCULAR TUNING SCALE PRINTED IN BLACK ON GOLD FOIL,  
CALIBRATED WITH WAVE-LENGTHS AND STATION NAMES ... .. PRICE 6d.

CONSTRUCTOR'S BOOKLET WITH FULL DETAILS AND FREE SCALE ... .. 2/-

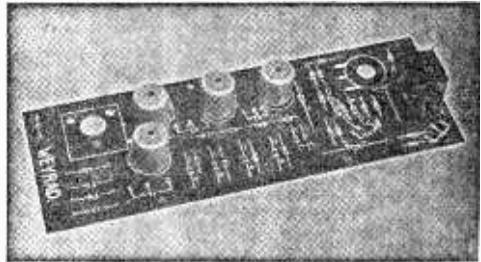**WEYMOUTH RADIO MANUFACTURING CO., LTD.**

REGENT FACTORY, SCHOOL STREET,  
WEYMOUTH, DORSET



**EXPRESS ELECTRONICS**  
ROSEDENE LABORATORIES  
KINGSWOOD WAY, SELSDON, SURREY

**VALVES** NEW TESTED AND GUARANTEED  
FOR THREE MONTHS

1C1	7/8	6BA8	3/4	6D5	4/-	DF96	8/-	EE41	9/-	PCL84	7/-
1C3	6/-	6BE6	7/-	12AH8	10/-	DH76	7/8	EF80	8/-	PL81	12/8
1F1	8/-	6BH6	5/9	12AT7	6/-	DH77	6/-	EF86	9/-	PL82	7/-
1F3	7/8	6BJ6	5/9	12AU7	5/8	DH142	8/6	EF91	4/-	PL83	7/8
1FD1	8/-	6BR7	8/9	12AX7	6/-	DH150	10/-	EF92	5/8	PY81	6/8
1FD9	7/8	6BR7	10/8	12B26	8/8	DK91	7/8	EL41	9/8	PY82	7/8
1L4	6/8	6BW6	7/8	12BH7	10/8	DK92	7/8	EL94	7/-	PY83	7/8
1F1	8/-	6BW7	7/-	12K80T1L	-	DK96	8/-	EM84	10/-	R19	11/8
1P10	7/8	6C10	9/-	12Q7GT	7/8	DL92	7/8	EM85	10/-	U26	9/8
1P11	7/8	6D2	4/-	16A5	9/-	DL84	6/6	EY81	7/8	U52	7/8
1R5	6/-	6F12	4/-	25A6G	8/8	DL86	8/-	EY81	10/-	U76	7/8
1R3	6/-	6H6GT	8/-	25L6GT	7/8	EB91	4/-	EZ40	7/8	U78	5/-
1T4	7/8	6J7GT	7/8	25Z4G	9/-	EBC41	10/-	EZ80	6/-	UBC41	8/8
1U5	5/8	6K7Q	5/8	30C1	6/8	EBF80	8/6	EZ81	6/8	UCH42	8/8
3Q4	8/-	6K9G	6/-	30L1	7/-	ECC81	6/-	ET38C	6/-	UP41	8/8
3R4	7/8	6Q7G	5/8	35L6GT	5/-	ECC82	6/8	RT86	11/8	UL41	8/8
3V4	6/8	6SL7GT	6/-	35W4	8/8	ECC83	6/-	N17	7/8	UY41	7/8
5U4G	7/8	6SN7GT	6/-	35Z4GT	8/-	ECC84	7/8	N18	8/-	W76	6/8
5Y3GT	5/-	6V6G	7/8	53K10	10/8	ECP80	8/8	N19	7/8	W142	8/8
5Z42	8/8	6X4	6/-	57B5	7/8	ECP82	8/-	N709	7/-	X17	7/8
6AK5	6/8	6X5G	5/-	90	9/-	ECH42	9/-	PC084	6/8	X142	9/-
6AL5	4/-	6X5GT	6/-	DAP91	7/8	ECH81	10/-	PCF80	6/8	X150	9/-
6AM6	4/-	7B7	7/8	DAP96	8/-	ECL80	8/8	PCF82	7/-	Z77	4/-
6AT6	6/-	787	9/8	DF91	7/8	ECL82	9/-	PCL82	8/-	ZD17	7/8

High Stability Resistors 1W 5% 50 Ω to 1M, 9d. Midget Ceramics 500 v. 9d.  
Coat. Super quality 1in. 6d. v. 1in. 9d. Scotch 9d. Silicon H.T. Resist.  
250v. 300 MA lin. x 1in. 17/6. Contact Cooled 250v. 50 MA 8/6. 85 MA 8/6.

**VALVES MATCHED IN PAIRS**

EL84 17/-, N709 17/-, 6V6 18/-, 6BW6 18/- per pair. Push Pull O.P.  
Transformers for above 3-15 Ω 14/6, P. & P. 1/6, 12in. P.M. Speakers  
3 Ω 94/8, Baker's "Bethurst" 12in. 15 Ω 15W, 90/-, 12in. Stereo Model,  
57,7,0.

**SETS OF VALVES**

DK01, DF91, DAF91, DL92 or DL84 ... .. 11/6  
DK96, DF96, DAF96, DL96 ... .. 27/6  
1C3, 1F1, 1FD1, 1P1 ... .. 27/6  
1R5, 1T4, 1R5, 3R4, or 3V4 ... .. 19/6  
Postage and packing 6d. Over £1 post free. C.O.D. 9/8.

## SOLDERING EQUIPMENT

by



**PRECISION SOLDERING**  
for the  
**ELECTRONICS INDUSTRY**

Comprehensive range—Robust & Reliable  
- Lightweight - Rapid heating - Bit sizes  
3/32in. to 3/8in. - 'Permabit' or Copper  
bits - All voltage ranges 67v. to 230/  
250v. - Prices from 19/6.

Also

- Plastic Cable Strippers
- Miniature Solder Pots
- Heat Guards
- Long Life Bits

Illustrated is the 25w. 3/16in. replaceable  
bit model with safety shield.

**ADAMIN**—the new range of precision  
micro-soldering instruments—  
Have you had details?

Brochure No. S10 sent free on request.  
Sole proprietors and manufacturers:  
**LIGHTSOLDERING DEVELOPMENTS LTD.**  
28 Sydenham Road, Croydon, Surrey  
Phone: CROYdon 8589 Grams: Litesold Croydon



**TESTED AND GUARANTEED VALVES**

New Valve Price List Available

0A2	8/-					EL91	4/8
0A3	10/-					EY51	9/-
0B2	6/-					EY56	8/-
0B3	8/-					EY91	3/-
0C3	5/6					EZ90	9/-
0D3	5/6					EZ91	9/-
0Z4A	5/6					PC13	15/-
1L4	3/8					KTS	27/6
1LD5	6/-	6C5	8/-	12K8	8/-	AC/HL	5/-
1LW5	5/-	6CH6	8/-	128A7	7/-	AR.P12	2/9
1B4	6/-	6D8	4/-	128H7	3/-	ARTH2	7/-
1R5	6/-	6E8	5/-	128L7	5/-	APTA	4/-
1S4	6/-	6F8G	6/8	128LGT/G	6/-	CIC	10/-
1S5	6/-	6F83	7/-	128R7	5/-	CCSL	4/-
1T4	4/-	6GG6	2/6	12Y4	2/6	CL33	9/-
1U5	6/-	6H6	1/6	25L6GT/G	6/-	CV31	9/-
1V4	4/-	6J5	4/-	807	8/-	DAF91	6/-
1Z2	17/6	6J6	3/8	35L6GT	9/-	DAF98	7/6
2C26A	4/-	6K7	4/-	35Z4GT	8/-	DC090	5/-
2C34	4/-	6K6	9/-	35Z6GT	9/-	DF91	5/-
2D21	6/-	6L6G	7/-	39F44	3/-	DF92	3/6
2E25	20/-	6L7	5/-	42Z4	2/-	DF96	7/6
2X2	4/-	6L18	8/-	50L6GT	7/-	DK63	6/-
3A4	5/-	6N7	6/-	63KU	9/-	DK92	9/-
3A5	5/-	68A7	7/-	7E	5/-	DK98	7/6
3D6	4/-	68H7	3/-	88	10/-	DL33	7/-
3Q4	7/-	68J7	5/-	26V	9/-	DL66	7/6
3S4	5/-	68K7	5/-	85A1	9/-	DL810	4/-
3V4	6/-	68L7GT	6/6	85A2	7/6	DM70	3/6
4X150A.50	6/-	68N7GT	4/-	71A	80/-	E88C0	10/-
6U4G	6/-	6887	3/-	71T4	4/-	E180F	20/-
6V4E	10/-	6V6GT	5/6	807	6/8	EA3080	5/-
Y3G	5/8	6X4	5/-	814	85/-	EAC91	4/-
E23	7/-	6X5GT	6/-	815	40/-	EC90	2/6
E24	9/-	6Y6G	6/-	832	15/-	EC91	3/-
6Z4G	7/-	6Z4	8/-	86GA	10/-	ECC32	4/-
6AB7	4/-	7AG7	5/-	87Z4	20/-	ECC84	8/-
6AG5	3/-	7B7	5/8	95A	3/-	ECC85	8/-
6AG7	7/8	7N7	5/8	20S1	7/8	ECP80	10/8
6AK5	5/-	7Q7	7/-	5070	10/-	ECP82	10/8
6AK6	7/-	7Z4	4/-	6678	8/-	ECP85	8/-
6AL5	4/-	1E3	17/8	6702	15/-	ECL80	10/-
6AM5	4/6	12A6	2/-	5763	10/-	EF22	3/-
6AM6	4/-	12AT7	6/-	6005	10/-	EF37A	8/-
6AQ5	7/-	12AU7	6/-	6080	30/-	EF40	10/-
6AT6	6/-	12AX7	7/-	6148	25/-	EF50	1/6
6AU6	7/-	12AY7	7/8	7133	2/-	EF55	5/-
6B4G	10/-	12BA6	5/-	7475	4/-	EF80	6/-
6B8	6/-	12BE6	8/-	9002	5/8	EF88	7/-
6BA6	6/-	12C3	3/-	9003	8/-	EP91	4/-
6BE6	8/-	12E1	20/-	9004	5/8	EP92	3/8
6C4	2/6	12F6GT	3/6	9008	5/6	EL84	7/-

We Buy Special VALVES and TUBES, KLYSTRONS, MAGNETRONS, etc., and High-class TEST EQUIPMENT and COMMUNICATION RECEIVERS

**Z & I AERO SERVICES LTD**

Retail Shop; 85 TOTTENHAM CT. ROAD, W.1. Tel. LANGHAM 8403

Head Office and Warehouse: 14 SOUTH WHARF ROAD, W.2. Tel. AMB 0151/2, 0677. Please send all correspondence and Mail Orders to the Head Office.

**CV428 MODERN MINIATURE 807 VALVE Guaranteed at 30/-**

**RELAYS**  
Second hand, guaranteed  
S.T.C. MIDGET RELAYS:  
1 M. Contact at 5A, 250Q Coil.  
Operating 40mA. Release 15mA ... 6/6  
2 C.O. Bifurcated Contacts at 500mA, 700Q Coil; operating 10mA; release 5mA ... 7/6  
SIGMA TYPE 4C1 or ALLIED TYPE "qg"  
HIGH speed, 1B contact, 5000Q coil; current 4mA ± 5mA. Will operate with change of current of 0.2mA ... 5/6  
SIEMENS HIGH SPEED SEALED 1 C.O. contact at 500mA. 7-pin coil 2 x 140Q; operating 15mA with coils in series, 30mA with coils parallel ... 5/-  
POST OFFICE RELAYS  
Type 600, 600 Q coil, 2 C.O. contacts 6/8  
Type 3000, 500 Q coil, 2 C.O. contacts 7/6  
Type 3000, 100 Q coil, 4M-4B contacts, break before make. Operating 50mA. Release 20mA ... 7/6  
A102817 MIDGET RELAY  
1M 2 Amps, 12V 76Q coil, dim. 1 1/2 x 1 1/2 ... 1/6  
D168816 WESTINGHOUSE POLARIZED RELAY  
1 C.O. twin 1450Q coil and soaking winding of 90Q. Speed of operation 500 or more per second. Complete with nine pins ... 20/-  
Post and packing 9d. per relay.

**VENNER TIME SWITCHES**  
Eight-day clockwork type. One make and one break every 24 hours. 1 amp. 250V contacts. Dial graduated in hours. Second hand, guaranteed, complete 27/6 p. & p. with key.

**HEADSETS**  
DLR-5 ... .. 10/-  
HS-30/U ... .. 15/-  
Post and packing 1/9 per headset.  
**MAINS ENERGED LOUDSPEAKERS (new)**  
6in., 1000Q Fd., 3Q Sp. Coil ... 9/-  
6in., 68Q Fd., 5Q Sp. Coil ... 8/-  
10in., 68Q Fd., 5Q Sp. Coil ... 12/6  
Packing and postage 2/6 per speaker.  
**MAINS TRANSFORMERS**  
Input 120V, output 6.3V at 5A, 7.5A and 0.5A. new ... 12/6  
Input 120V, output 6.3V at 10A, 0.5A and 0.3A and 5V at 4A. new ... 15/-  
Input 100/250V, output 275-0-275V at 80mA, 6.3V at 2.5A, and 0.6A ... 15/-  
Input 200-250V, Gardiner or Parmeko, output 350-0-350V at 70mA D.C., and 6.3V at 2X1A and 2X3A, new 25/-  
Postage and packing 3/6 per transformer.  
**AVOMETER MODEL 7**  
Fully overhauled and guaranteed £12.10.0  
Leads, per pair ... 15/-  
Packing and postage, 10/-.  
T36EH745 Tubular, screw terminals, 1220V rms at 2mA, new ... 7/6  
3E8HT45, as above, but solder tag terminals ... 5/-  
Germanium Power Rectifier GJ6M, 300 p.p.v. at 550mA D.C. ... 10/6  
Postage and packing 9d. per rectifier.  
**COMMUNICATION RECEIVERS**

**FREE TO AMBITIOUS ENGINEERS**  
— THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

**Have you sent for your copy?**  
ENGINEERING OPPORTUNITIES is a highly informative 156-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronics Courses, administered by our Specialist Electronics Training Division—the B.J.E.T. School of Electronics, explains the benefits of our Employment Dept. and shows you how to qualify for five years promotion in one year.

**We definitely Guarantee "NO PASS—NO FEE"**  
Whatever your age or experience, you cannot afford to miss reading this famous book. If you are earning less than £25 a week, send for your copy of "ENGINEERING OPPORTUNITIES" today—FREE

**WHICH IS YOUR PET SUBJECT?**  
Mechanical Eng.,  
Electrical Eng.,  
Civil Engineering,  
Radio Engineering,  
Automobile Eng.,  
Aeronautical Eng.,  
Production Eng.,  
Building, Plastics,  
Draughtsmanship,  
Television, etc.

**GET SOME LETTERS AFTER YOUR NAME!**  
A.M.I. Mech. E.  
A.M.I.C.E.  
A.M.I. Prod. E.  
A.M.I.M.I.  
A.I.O.B.  
A.F.R. Ae.S.  
B.Sc.  
A.M. Brit. I.R.E.  
City & Guilds  
Gen. Cert. of Education  
Etc. etc.

**PRACTICAL EQUIPMENT**  
Basic Practical and Theoretical Courses for beginners in Radio, T.V., Electronics Etc., A.M. Brit. I.R.E. City & Guilds Radio Amateurs' Exam. R.T.E.B. Certificate P.M.G. Certificate Practical Radio  
Radio & Television Servicing Practical Electronics Electronics Engineering Automation

**INCLUDING TOOLS!**  
The specialist Electronics Division of B.I.E.T. (Incorporating E.M.I. Institutes) NOW offers you a real laboratory training at home with practical equipment. Ask for details.  
**B.I.E.T. SCHOOL OF ELECTRONICS**



**POST COUPON NOW!**

Please send me your FREE 156-page "ENGINEERING OPPORTUNITIES"  
 (Write if you prefer not to cut page)  
 NAME.....  
 ADDRESS.....  
 SUBJECT OR EXAM THAT INTERESTS ME..... (SE/21)

**BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY (Incorporating E.M.I. Institutes) (Dept. SE/21), 29 Wright's Lane, London, W.8**

**THE B.I.E.T. IS THE LEADING ORGANISATION OF ITS KIND IN THE WORLD**

# Letters to the Editor

The Editor does not necessarily agree with the opinions expressed by his correspondents

Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying commercial or surplus equipment. We cannot supply alternative details for receivers described in these pages. **WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE.** If a postal reply is required a stamped and addressed envelope must be enclosed with the coupon from page iii of cover.

## F. M. QUALITY

SIR,—I wonder if any of your readers feel, as I do, that the quality of the received VHF/F.M. transmissions of the BBC is somewhat lacking? It seems to me that the lower frequencies are thinned out in some way so that the roundness of tone is missing. I had the opportunity of checking a good Continental receiver the other day, which had the facilities of separate A.M. and F.M. tuners, with a piano-key type switch, so that, for instance, the Home Service could be set up on both M.W. A.M. and VHF/F.M. and the switch could select either almost instantaneously. As might be expected, the direct comparison gave a much extended clean top on the VHF section, but when this good top was reduced (with a top-cutting tone control) to about the level of the A.M. response, the thinness of the lower frequencies was very marked. BBC TV A.M. sound does not seem to suffer in this way, so I have a feeling that the ratio detector system in common use is falling down on the job somewhere—what do other readers think?—B. D. VAN DER SYDE (Parkstone).

## METAL CABINETS

SIR,—I am an ardent reader of your excellent magazine, as like many amateurs I have constructed various pieces of test equipment as described in your pages. However, I find in the trade sections a distinct lack of any metal cabinets—an essential for signal oscillators, etc.—and month after month I scan through the adverts hoping to see a selection of these cabinets being offered in various shapes, sizes and finishes, but to no avail. Isn't it apparent to the suppliers, that a real need is set up by every amateur who strongly desires to build equipment equivalent or sometimes superior in performance to that of commercial offerings and yet still possessing a professional finish?—T. H. HUGHES (Rhonda).

## SEMI-CONDUCTOR RATING

SIR,—Owing to the increasing use of semi-conductor rectifiers in power supply units, I feel that the warning should again be sounded concerning PIV (peak inverse voltage) ratings. A very common mistake is to reckon that, under "surge" conditions, i.e. should the load be accidentally disconnected the PIV across the rectifier would only rise to 1.414 times the r.m.s. out-

put of the secondary (or, in the case of a full-wave rectifier, of the half-secondary) of the mains transformer. Actually, of course, reckoning the negative peak voltage the PIV rises to 2.828 times the output of the transformer so that in practice the minimum PIV rating to be chosen would be for safety three times the output of the secondary (or half secondary as the case may be) of the mains transformer. To give an example, using two rectifiers in a full wave circuit and a transformer secondary giving 350-0-350V, the PIV across each rectifier could rise to no less than  $50 \times 2.828 = 989.8V$  and in the half-wave condition using a small 250V transformer the PIV could, if the load were momentarily disconnected, rise to the high figure of  $250 \times 2.828 = 707V$ . I feel that this warning should be kept in mind to avoid expensive breakdowns and even, under certain circumstances, serious danger. — A. T. FARRER (Newcastle-upon-Tyne).

## IMPROVING BROADCAST RECEIVERS

(Continued from page 838)

in that it would lead to a reduction in the highest audio (modulation) frequency which can be received. This little exposition on I.F. passband may be a little confusing to some, so it is best summarised by saying that for most purposes any reduction in I.F. passband is very acceptable these days in view of the overcrowded state of the medium waveband whilst additional gain is always welcome.

### Increased R.F. Gain by Untuned R.F. Amplifier

A typical receiver input circuit is shown in Fig. 1. This is shown again in Fig. 2 with the addition of an R.F. stage between the original signal tuned circuit and the mixer, whilst in Fig. 3, the R.F. stage is placed before the original tuning coils, the former aerial coupling coil now being connected into the anode circuit of the R.F. amplifier. There is little to choose between the two methods. The first method is perhaps neater, but the second method may be easier to achieve—particularly from the layout point of view.

### R.C. Amplifier

In Fig. 4 is shown a receiver input circuit which does not employ an aerial coupling coil; for this type of circuit the additional amplifier must be added as in Figs. 2 or 5. Note that the method shown in Fig. 5 may equally well be used with a receiver which does have an aerial coupling coil. It is in fact just a R.C. amplifier with a low load resistor to give a good H.F. response, i.e. it is virtually a video amplifier.

(To be continued)

# Club News

## REPORTS OF CURRENT ACTIVITIES

### BRADFORD RADIO SOCIETY

Hon. Sec.: M. T. Powell, G3NNO, 28 Gledhow Avenue, Roundhay, Leeds 8.

"Modern Methods of communication", by E. M. Price was the subject of the meeting for November 15th. A "junk" sale was held on the 28th of the same month.

#### Future Events:

December 12th—"The development of time measurement", given by W. Barton.

January 2nd—D. M. Pratt talks on "Amateur receiver construction."

January 16th—"Electronic Organs", by A. R. Bailey.

### BURLEAM AMATEUR RADIO CLUB

Hon. Sec.: W. Luscott, 36 Rothsay Avenue, Sneyd Green, Hanley, Stoke-on-Trent.

On October 1st, twenty club members enjoyed a tour of the BBC's television station at Sutton Coldfield. On October 18th, A. J. Hodgkinson gave a demonstration and lecture on the G2 D.A.F. 55B receiver.

"Aerials and Propagation" was the subject of the lecture of the November meeting and was given by Peter Jones.

#### Future Event:

December 20th—"Silvered mica capacitors", by H. D. Hemmer.

### BURTON-UPON-TRENT AND DISTRICT RADIO SOCIETY

Hon. Sec.: J. Adkin, 25 Huntingdon Road, Stapenhill, Burton-upon-Trent, Staffordshire.

R. Harrison gave a talk on "Constrictors and inductance" on October 11th; and on November 8th, the club held its annual dinner at the Midland Hotel.

#### Future Events:

December 13th—J. Elliott talks on valves and how they work.

January 10th—W. Hazeldeau will give a talk on aerials for receiving and transmitting.

### DERBY AND DISTRICT AMATEUR RADIO SOCIETY

Hon. Sec.: F. C. Ward, G2CVV, 5 Uplands Avenue, Littleover, Derby.

Members had a busy November this year, starting with a surplus sale on the 1st. On the 15th, G. Morgan gave a lecture entitled, "Electronics as applied to telecommunications". A stereophonic tape demonstration was given for members on the 22nd November, and on the 25th, the annual trip to the International Hobbies Exhibition was held. The month ended with "Open evening" at the society's club rooms.

For the first meeting in December, another surplus sale held on the 6th.

#### Future Event:

December 13th—Open Night.

### MITCHAM AND DISTRICT RADIO SOCIETY

Hon. Sec.: M. Pharaoh, G3LCH, 1 Madeira Road, Mitcham. The society's transmitter, which took part in the Boy Scouts' International Jamboree-on-the-Air, was operated from the headquarters of the 3rd Mitcham, Woodland Way, Mitcham.

"The manufacture and development of capacitors" was the title of the talk given by A. E. Lesse, on October 20th, and on Friday, November 3rd, R. C. Hills talked on "Aerials".

### PETERBOROUGH AND DISTRICT RADIO SOCIETY

Hon. Sec.: D. Byrne, G3KPO, Jersey House, Eye, Peterborough.

At the first meeting of the winter session, Mr. R. Houlby spoke on direction finding, and the construction of special top-band portable receivers for competing in D.F. contests.

The annual general meeting was held on November 3rd, and the Christmas party on December 1st.

#### Future Event:

January 5th—A talk on aerials.

### ROTHERHAM RADIO CLUB

Hon. Sec.: S. J. Scarbrough, 25 Crawshaw Avenue, Sheffield 8

The winter programme began on October 4th, with an interesting and informative talk given by R. Moore, on transistors and transistorised equipment.

### SLADE RADIO SOCIETY

Hon. Sec.: C. N. Smart, 110 Woolmore Road, Erdington, Birmingham 23.

Recently, members have enjoyed two demonstrations of high-fidelity stereophonic sound, one in October and the other in November. Mr. K. Gunary gave a talk on October 20th, called "Rectifier locomotives for industrial frequency A.C. railway traction".

The annual general meeting was held on November 17th, and on December 1st members heard a lecture on D.F. developments.

### SPEN VALLEY AMATEUR RADIO SOCIETY

Hon. Sec.: N. Pride, 100 Raikes Lane, Birstall, Nr. Leeds.

"Amateur radio receiver alignment" was discussed by H. A. Mathias at the meeting on October 11th. On November 8th members met the zonal representative of the R.S.G.B. "Interference problems" was the subject of J. C. Belcher's lecture on November 22nd.

#### Future Events:

December 20th—Brains Trust.

January 3rd—Rag Chew.

## TRANSMITTING TOPICS

(Continued from page 807)

meter as small readings and sometimes the needle kicks up and down. The effects of neutralising a P.A. stage can also be seen simply by slipping the loop over the P.A. valve (with the H.T. off, of course), and tuning the P.A. The oscillations will show up on the meter and the neutralising can be carried out in the usual way—adding a capacity from anode to grid (to overcome the "Miller" effect). Although neutralising is usually carried out by watching the grid drive meter, a finer degree of control can be obtained by using the simple unit in Fig. 4.

If the loop coil is applied to a circuit which is in an oscillatory state, the meter will read, providing it is not coupled so as to stop the actual oscillation. The final design (see Fig. 5) was built up in a Bakelite case, but could be well built up in a "tin". Fig. 5 gives the final circuit which is simple to construct, requires no calibration and no tuning. The circuit is simple and untuned (RFC1 and D1); C1 removes any R.F. content in the rectified R.F. and the output is fed to VR1, a carbon

potentiometer which controls the output to both meter and to the phones (this was found a great asset and can be adjusted to a particular reading on the scale, for adjustment changes to be seen easily).

To use for R.F. indications it is only necessary to place the pick-up wire near the feeder system—even inches away—until a favourable reading is obtained on the meter scale, adjusting VRI if necessary. Any change in the actual R.F. output is clearly seen by a change in the reading. To use the unit as a monitor for 'phone working, set it up as above and adjust VRI with the switch set to the audio position and the gain adjusted for comfortable listening. For use as a field strength comparator, sometimes the pick-wire has to be replaced by a longer wire or even by a short aerial.

For the meter, a 1mA movement is preferred but other meters of lower or higher sensitivities may be used. Obviously, the lower the f.s.d. of the meter, the further away from the R.F. source can it be used. R.F. meters with the thermocouple removed would be suitable, but the sensitivity would be less as these generally have an f.s.d. of about 2mA.

# SOUND REPRODUCERS (LONDON) LTD.

The Transistor Component Specialists  
 Dept. P.W. 15, 7 Jepson Road, Forest Gate,  
 London E7. (Mail Order Only)



Our well-known Traveller is now supplied with printed circuit, 3 top quality transistors, 2 diodes in latest circuitry.

## AGENTS REQUIRED

### INTRODUCING... THE ROVER

The second of our Transistor Radio designs. 4 Mullard transistors in a circuit specially designed around the new AF117 diffused alloy R.F. transistor. OC81D-20C81. Push-pull output on printed circuit. Sensitivity approx. 1 mV per metre. Air-spaced tuner. Luxembourg guaranteed at excellent volume (if normally receivable).

Both sets of components have following outstanding features. Supplied complete with full Easy-to-follow Instructions. Physical layout and theoretical circuits. 3in. Moving Coil Speaker. Fully tunable on Medium Waves. Ferrite Rod Aerial. Solenoid Wound Coils. Plug in 9 v. Battery. Fully portable. No Aerial or Earth required. All components tested and guaranteed 12 months. Complete satisfaction or money refunded. All components supplied separately. Instruction Book 1/6 post free. Supplied free with set of components.

TRAVELLER **£3.17.6** TRADE SUPPLIED ROVER **£4.19.6**

ALL PARTS and BLUE PLASTIC CASE AS ILLUSTRATED. Post and packing 3/6. "Hook On" personal earpiece with instructions 9/-. Battery extra. P. & P. 3/6.

#### SNIPS

XA101, 6/-; SB078, 8/-; XB102, 9/-; AF117, 12/6; OC81D-20C81, 22/6; 6in. Ferrite Rod, 1/2 or 3/4 in., 1/9; Litz wire, 3d. yard We can supply components for "P.W." Tutor and Mini-Amp. Send for List. 3d. Stamp for Catalogue.

**"There is no Virtue without Courage— No Reward without Labour"**

Not simply a school motto but at B.N.R.S. a creed and a way of life. We owe to it all we have and are. If you are prepared to make it your motto and live up to it, we can help you to get to the top. It will take time, it will take effort, it will take courage, and on top of all this you will actually be charged fees.

If we haven't succeeded in putting you off, write for details, today, to:

**Mr. J. SYKES**  
 (M.I.E.E., M. Brit. I.R.E., M.I.N.)

Principal:

**BRITISH NATIONAL RADIO SCHOOL**  
 Red Lion Court, Stalbridge, Dorset

Britain's premier Radio Correspondence School specialising in City and Guilds examinations.



## RS12/DD

This fine 12 in. loudspeaker employs a new type of double diaphragm assembly (patent application No. 40667/60). The main cone is moulded from a specially formulated soft pulp which reduces break-up effects to a minimum. Higher frequencies are radiated by a one-piece tweeter cone with its edge supported on foam plastic to avoid resonance.

The moving assembly is supported by a roll surround, formed from resin impregnated cloth permanently moulded under heat and pressure. Together with the high grade synthetic centring device this roll surround permits very large cone and coil excursions with minimum distortion.

The magnet system is a highly efficient Feroba II assembly, giving outstanding performance with reduced depth and weight. Furthermore, these new magnets are very stable and almost impossible to demagnetise.

This loudspeaker covers a very wide frequency range and the roll surround permits the use of enclosures down to 1 1/4 cu. ft. with good L.F. performance, provided the acoustic requirements are met. Constructional details of several specially designed cabinets are supplied with each unit.

#### Some important features of the RS12/DD:

Very low bass resonance—Synthetic Centring device—Ceramic Magnet—Die-cast chassis—Foam edge damping—One-piece HF flare and dome—Soft, heavy main cone with wool fibres—Airtight impregnated roll surround.

#### RS12/DD Specification :

Fundamental Resonance	25-32 c/s
Frequency Range	30 c/s-15 Kc/s
Flux Density	14,000 gauss
Total Flux	156,000 maxwells
1 1/2 in. dia. Centre Pole	
Aluminium Voice Coil	12-15 ohms only
Impedance	15 watts r.m.s.
Max. Input	30 watts peak

**£11.10.0 Tax Free**

Descriptive literature and cabinet construction sheet free on request—



**IDLE, BRADFORD, Yorkshire**  
 Telephone Idle 1235/6  
 Grams: 'Wharfedel' Idle, Bradford



# MODEL 127A MULTI-METER

## 20,000 o.p.v. POCKET-SIZE


Performance equal to a high priced instrument

### OUTSTANDING FEATURES:

- ★ Sensitivity 20,000 o.p.v. D.C. 1,000 o.p.v. A.C.
- ★ 20 Ranges.
- ★ D.C. Current 50 ΩA, to 1 Amp.
- ★ D.C. Volts 0.3 v. to 1,000 v. (25 kV by probe.)
- ★ A.C. Volts 10 v. to 1,000 v.
- ★ 3 Resistance Ranges from 0-20 megohms (self-contained).
- ★ Meter 40 ΩA 3½ in. arc.
- ★ Accuracy D.C. 3%, A.C. 4%.
- ★ Dimensions 5½ x 3½ x 1½ in.

PRICE: £10.0.0.

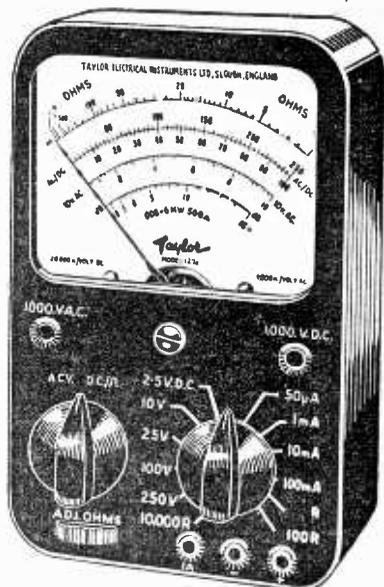Complete with instruction Manual and interchangeable test prods and clips. High quality leather case, if required, £1.12.0.  
H.V. Probe for 25 kV ... £4.15.0



Write for  
fullest  
details to:


**TAYLOR ELECTRICAL INSTRUMENTS LIMITED**  
MONTROSE AVENUE, SLOUGH Telephone: Slough 21381 Cables: TAYLINS Slough

METAL INDUSTRIES GROUP


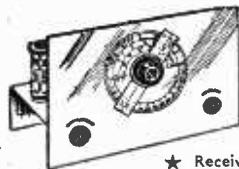
## "BUILD IT YOURSELF" THIS XMAS

EXPLORE THE WORLD ON THIS  
1-VALVE SHORT-WAVE RADIO



Total  
Building  
Costs  
**35/-**  
P. & P.  
2/-

★ Receives speech and music from all over the world. Construction price includes valve and one coil covering 40-100 metres. Can be extended to cover 10-100 metres. Can be converted to 2 or 3 valve. Send 2/- for wiring diagram and components price list.

PUT YOUR FAVOURITE PROGRAMME ON TAPE with the R.C.S. TAPE TUNER



Will operate on all types of Recorder. High impedance output. Variable Medium wave tuning. Triple wound Super Hi-Q coil. Chassis and components colour coded. Easily constructed from full instruction data and layout diagrams. Size 3½ x 1½ x 1½ in.

Total build-**30/-** P.P.  
ing costs 1/6


Send 1/6 for wiring diagram and components price list.

5 STAGE SUPER SENSITIVE

TRANSISTOR PORTABLE

THE  
"BOBETTE"

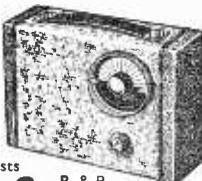- Simple to Build
- All First Grade Components



Total  
Building Costs  
**£5.26**  
P. & P.  
2/6

A truly portable transistor radio giving full medium wave reception. Incorporates 5in. High Flux Speaker, push pull output, first grade transistors, High-Q ferrite aerial, socket for car aerial, pre-tagged circuit board for easy construction. Attractive two-tone case.

ALL PARTS SOLD SEPARATELY.

Send 1/6 for itemised price list and full assembly instructions (Free with order).

EASY TO BUILD  
TWO STAGE TRANSISTOR SET

THE  
"BIJOU"

The set that looks like a Radio Set.



- Attractive Case.
- Mini .005 Tuner.
- High Q Litz Coil.
- Works for months off No. 8 Battery.
- Simple to construct in 15 min.

Total  
Building Costs **25/-** P. & P.  
2/-

You can't go wrong. We guarantee good results.

Components Price List, Layout Plans 1/6 (free with order).

### CRYSTAL RECEIVER

Covering Medium Wave Band  
IDEAL FOR THE BEGINNER!

All components including case for only 12/6. P. & P. 1/6.

Easily converted to 1-transistor or 2-stage transistor receiver. Send 1/6 for construction details and component price list.

R.C.S. PRODUCTS (RADIO) LTD.

11 OLIVER ROAD, LONDON, E.17  
Mail Order only. Trade Enquiries welcomed.

# Understanding POWER Supplies

## THE FULL-WAVE RECTIFIER CIRCUIT

(Continued from page 712 of the December issue)

By A. Foord

**L**AST month the diode valve and the half-wave rectifier circuit were considered.

### The Full Wave Rectifier Circuit

The half wave circuit suffers from the following disadvantages: It only charges the reservoir capacitor during every positive wave. If the full wave circuit—as shown in Fig 9—is used, the operation is very similar.

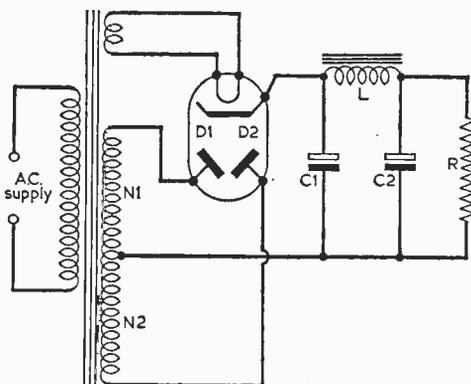


Fig. 9—A complete H.T. full-wave rectifier circuit.

The circuit can be regarded as two separate diodes—D1 and D2—fed from their own windings—N1 and N2—but having a common load R, and components C1, C2 and L. Alternate half waves are rectified in turn as each becomes positive to the centre tap. Fig 10 shows the output voltage without the output reservoir capacitor C1. Fig. 11 shows the output voltage with a reservoir capacitor. In this case the action of the components is similar to the half wave circuit, but now they are more effective because the principal hum component is now 100c/s instead of 50c/s. Consequently L and C2 do not have to be so large for the same ripple voltage as they were in the previous circuit.

Most mains transformers are fitted with an earthed copper screen between primary and secondary. Its purpose is to prevent radio frequency signals being passed on from the mains and, although the ends of the screen may overlap, they

should not touch, or the screen will consist of a shorted turn, and the transformer will overheat.

### The Full Wave Bridge Circuit

The full wave bridge circuit is shown in Fig. 12. Although valves can be used in this circuit, metal rectifiers are normally employed, thus overcoming the difficulty of separate heater supplies. Figs. 13a and b show that whatever the polarity of the supply the voltage across the load is always the same. In the absence of any reservoir capacitor the average output voltage is 0.636 of the peak input voltage. This circuit is commonly used for instruments as well as for H.T. supplies, as it gives full wave rectification without the use of a centre-tapped transformer, and therefore saves turns and space on the transformer.

### The Voltage Doubler Circuit

The action is again evident by considering the paths of alternate half waves. It can be seen that both capacitors are being charged in the same direction to the full peak voltage of the supply. (This is shown in Fig. 14.) It will also be seen that the capacitors are connected in series with the load.

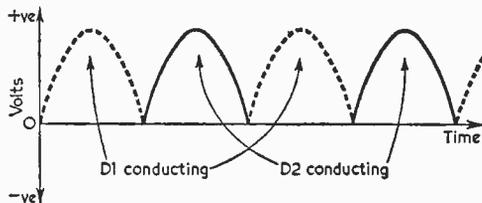


Fig. 10—This represents the output voltage from a full-wave supply, without a reservoir capacitor or smoothing components.

To indicate the advantage of the voltage doubler circuit, an A.C. input of 125V would probably give a D.C. output of 300V on load. With a bridge circuit, the input voltage would have to be about 300V root mean square (r.m.s.) while for the same output (300V), a full wave C.T. circuit would have to provide about 600V r.m.s. overall. (Of course, the power taken from the supply would be the same, it is only the current that alters.)

When using the voltage doubler, the transformer windings must be thicker to carry the extra current,

but this would be more than compensated by the reduced number of turns.

**Metal Rectifiers**

Metal rectifiers can be used instead of valves in all the circuits shown here. Indeed, their use is almost essential in some of the circuits. They have several advantages, of which the most important is that they have no heater supply. They can therefore be connected anywhere in a circuit without heater insulation difficulties. In addition they have an infinite life unless overloaded. They can be manufactured in very small sizes and have a high efficiency (about 80%). Metal rectifiers

**Conclusions**

It is possible, when working out power supply voltages, to make accurate calculations for the effects of reservoir and smoothing components on output voltage and hum; but it is usually better for the home constructor to work more by trial and error. By increasing the reservoir capacitor, the H.T. is raised, while by increasing the inductance or the smoothing capacitor, the hum is reduced. If the reservoir capacitor is increased in value, make sure that it is not more than the


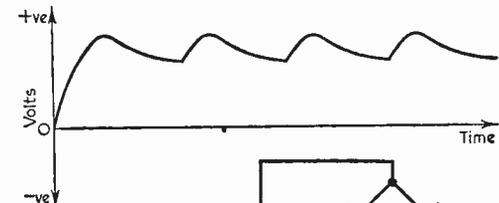


Fig. 11 (above)—The output voltage from a full-wave circuit with a reservoir capacitor.

Fig. 12 (right)—A full-wave bridge circuit.

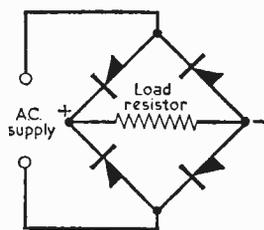

have an oxide coating, and it is this oxide that has a high resistance one way and a low one the other. In this way they rectify; but their action is not perfect, since they have a small reverse current. The rectifier has a maximum reverse voltage which it will withstand, but if this is exceeded the oxide film breaks down; but a number of elements can be connected in series to withstand any high voltage.

There are three types of metal rectifiers used in power supplies, copper, selenium and silicon.

**The Copper Oxide Rectifier**

This type has a disc of copper as the element. One side only has an oxide coating and contact is made with this oxide by means of a lead disc. Electrons flow best from the copper into the oxide.

**The Selenium Rectifier**

The metal used in this type, instead of copper, is an aluminium or nickel-plated steel disc, which is plated on one side with a thin layer of selenium. In this case the current flows easily from the aluminium or steel into the selenium.

**The Silicon Rectifier**

This is a development of the study of semi-conductors, and uses silicon in its construction. Because of the nature of its construction it has a very low forward resistance. It is therefore able to rectify a large current without dissipating much heat, or dropping much voltage. This forms an extremely efficient and compact rectifier, and unlike the other types of rectifier no cooling fins are required.

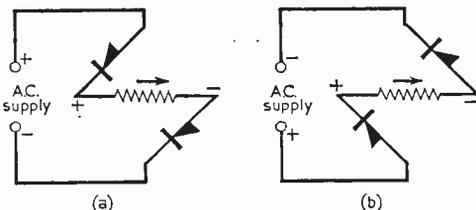


Fig. 13 (above)—These diagrams represent the actions of the bridge circuit of Fig. 12. Whatever the supply polarity, the load current is always in the same direction.

maximum permitted by the valve or rectifier manufacturer and that an adequate series resistance is in circuit with the rectifier. (This is to prevent large surges which could damage the valve or rectifier.)

In general, for a given r.m.s. input of  $xV$ , the bridge fullwave and halfwave circuits, give about  $xV$  D.C. output; while the voltage doubler gives about  $2xV$  D.C. output. This is only approximate, but gives an approximation of the output which may be expected from power supply.

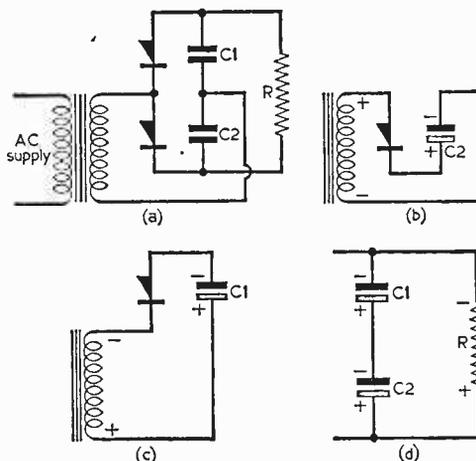


Fig. 14 (a)—The complete voltage doubler circuit. (b)—When the supply voltage is as shown in the diagram, C2 is charged. (c)—When the supply is reversed, C1 is charged as shown. (d)—This shows that the charges on C1 and C2 are in series and discharge through the load resistor R.

# LASKY'S RADIO

## TELEFUNKEN STEREO HI-FI AMPLIFIER At BIG REDUCTION!



### The "CLARION" Transistor Battery Tape Recorder

Capstan drive, push-button controls. Speed 3 1/2 i.p.s. Uses 3 1/2 in. spools. High impact plastic case with transparent upper. Size: 9 1/2 x 5 x 3 1/2 in. LIST 25 Gns. LASKY'S PRICE, with Mike and Tape. **16 1/2 Gns.** Carr. 7/6.

A complete stereo amplifier of unsurpassed quality, with inputs for radio, tape recorder, F.M. tuner etc., either monaural or stereo. For A.C. mains 110, 125, 150, 220, 240 v. Freq. response: 30 c/s to 40 Kc/s. Output: 5 watts (21 each channel), but actual power fed to speakers equals a normal 10-watt amplifier. Bass and treble controls, etc. Size: 12 x 9 x 2 1/2 in. Green/grey hammered enamel with gold trim. New in maker's cartons, guaranteed.

LISTED AT 16 GNS. **£7.19.6** Post 8/6.  
LASKY'S PRICE

### TRANSISTOR RECORD PLAYER

CAN BE BUILT FOR

**£9.19.6** Carr. free.

6 v. operation. For all L.P. and standard records. All components available separately.

**AMPLIFIER.** 300 milliwatts push-pull output using two OC71 and two OC72 transistors. Fully assembled. 69/6. Knobs, 5/6 extra. P. & P. 2/6.

**LOUDSPEAKER.** 30 ohms, 7 x 4 in. elliptical, matched to Amplifier. 25/-.


**3-SPEED TUNTABLE.** 6 v., complete with t.f. crystal cartridge and two sapphire styl. 79/6. P. & P. 3/6.

**CARRYING CASE.** smart two-tone finish. 17 x 14 x 5 1/2 in. High 49/6. P. & P. 7/6. Batteries extra.

### TRANSISTOR POCKET RADIOS
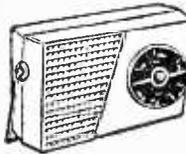
#### THE "TORONTO 3"

Size 5 1/2 x 3 x 1 1/2 in. Uses 3 transistors plus germanium diode, ferrite rod aerial. Tunable over med. and long waves. Can be built for 32/6. Post 3/-. All components available separately.



**32/6** Post 3/6

#### THE NEW "ALBERTA 5"

Push-pull. 200 milliwatts output. Five transistors and one diode. 2 1/2 in. moving coil speaker, ferrite rod aerial. Med. and long wave. Smart plastic case 4 1/2 x 3 1/2 x 1 1/2 in. overall. CAN BE BUILT FOR 59/6. Post 3/-. All components available separately. Full details, circuit diagram 1/6 post free. Battery PP3. 2/6 extra.



**59/6** Post 3/6

207 EDGWARE ROAD, LONDON, W.2.

Near Praed St. PADDINGTON 3271/2

33 TOTTENHAM COURT, ROAD, W.1.

Nearest Stn. Goudge St. MUSEUM 2605

BOTH OPEN ALL DAY SAT. Early Closing Thurs. Mail Orders to Dept. P.W., Edgware Road.

### SOLDERING IRON 18/9 CARR. FREE

For lightweight applications. High stable heat characteristics assure long life and safety in use. Features a removable handle that may be used to cover the tip and barrel to permit the iron to be carried safely even while hot. Complete with vinyl bag, mains lead and plug. Total overall length 10 1/2" (6 1/2" when not in use)

**15/- TUBES**  
**12"** 31/74, 124, 153  
EX-RENTAL **15"**  
WORKING and GUARANTEED  
CARR. 5/-.

**35/-** 36/24, 14KP4.  
Wonderful Offer.  
Working & Guaranteed.  
CARR. 5/-.

### P.P. COMPONENTS LTD.

c/o 623 Romford Road, Manor Park, London, E.12.  
STAMP FOR FREE LIST. Regret Mail Order Only.

### SURPLUS RADIO SUPPLIES

2 LAING'S CORNER, MITCHAM SURREY

SEND TO-DAY FOR OUR CATALOGUE

## 400 BARGAINS

At prices below manufacturing cost. Price 1/6, post paid.

Crystal Deaf Aid Earpieces. Suitable for Crystal Sets, 5/-. Complete with Jack Plug and Socket, 7/6. 1/6 Postage.

## Become a Television expert this easy way

The Bennett College offers you a complete course

THE Bennett College offers you personal tuition in a course that's non-mathematical and particularly easy to follow. It contains clear diagrams which cover everything you want to know from beginning to end (and even includes the basic principles of sound radio if you wish).

The complete home-study course covers everything: Production of the signal, scanning and reproduction of picture from signals. Aerials, types and purpose. The cathode-ray tube. Time-base oscillators, and output circuits. Synchronisation. Video frequency amplifiers. The TV tuner, turret incremental, etc. Television test gear. Television faults.

For more details, please fill in the coupon below. Your studies cost very little and the book you need is included in the cost.

To THE BENNETT COLLEGE (Dept. A 104NTY, Sheffield)  
Please send me details of the new  
TELEVISION SERVICING COURSE

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

AGE \_\_\_\_\_

**RECEIVERS & COMPONENTS**

**COMPONENTS, VALVES.** Tubes, etc. Write or phone for free list. ARION TELEVISION, 4 Maxted Road, Peckham, S.E.15 (New X 7152).

"HEATHKITS" can now be seen in London and purchased on easy terms. Free brochure. DIRECT TV REPLACEMENTS LTD., Dept. PW/7/12, 138 Lewisham Way, S.E.14, Tideway 6666.

**A.1. BARGAINS,** all post free. Table/Hand crystal mikes, brand new 19/6. Reclaimed valves all tested. 6D2, EF50, SP61, P61 1/3, EF80 1/6, 6F13, 6P25, Z77, PEN45 1/9, 10P13, B36, L63 3/3, PY31, PY81, PY82, PL33, PL81, PL83, PL82, ECL30 4/3, PZ30, ZBF90, 4/3, 10% reduction on dozens. Few of last month's bargains available. C.W.O. A.1. RADIO COMPONENTS, 14 The Borough, Canterbury, Kent.

**CRYSTAL SETS,** sensitive, selective, in luxury REXINE covered case, 18/6 complete, p and p 1/-, RADMORE, 11a Westmorland Street, Wakefield, Yorks.

**SPEAKER REPAIRS.** Cones/Fields fitted. Clock Coils Wound, L. S. REPAIRS, Pluckley, Ashford, Kent.

**TRANSISTOR SETS.** OC44, 20C45, OC81D, 20C81 35/6, OC44 9/-, OC45 8/8, OC71 6/3, XA102 9/-, XA101 8/8, XB103 6/3, Red Spot 3/6, White Spot 4/-, Diodes General 1/-, OA79 3/-, OA70 3/-, OA71 2/9, OA81 2/9, GEX34 2/9. Ear Pieces complete with plug and jacks 100, 250 and high Z 7/9 each. Min. Caps 1 to 32MFD 1/9 each. P. and P. paid by CHAPPLE RADIO, 107 Neasden Lane, N.W.10.

**TUBES—VALVES—SPARES**

**TUBES 6 mod. Guar. FITTED FREE** 9-10-12in. 30/-, 14in. 40/-, 17in. 50/-  
**VALVES, 50,000 in stock, 1,000 types.** Most tested before despatch. Examples:  
5UA 4/6 EBC41 6/- N37 4/6  
5V4 4/6 EBC90 4/6 N108 10/-  
5Z4 4/6 EBF80 6/- PCC84 4/6  
6AU6 4/6 EBL31 12/6 PCF30 4/6  
6BE5 4/6 EBL31 12/6 PCL82 4/6  
6BA6 4/6 ECC82 3/- PenA4 5/-  
6BE6 4/6 ECC83 3/- PL38 10/-  
6BG6 10/- ECC84 4/6 PL81 4/6  
6BW6 4/6 ECC85 4/6 PL82 4/6  
6CH6 17/6 EBC91 4/6 PL83 4/6  
6CH6 4/6 ECH35 6/- PY31 4/6  
6C9 6/- ECH42 6/- PY80 4/6  
6K25 4/6 ECF80 4/6 PY81 4/6  
6L18 4/6 ECL30 4/6 PY82 4/6  
6P25 4/- ECL82 6/- PZ30 4/6  
6V6 4/6 EF80 2/- R19 7/6  
6X4 4/6 EFB6 4/6 MU14 5/-  
7S7 4/6 EFB2 4/6 T41 2/-  
7Y4 4/6 EL58 4/6 U22 4/6  
10C2 6/- EL41 4/6 U24 7/6  
10P1 3/- EL90 4/6 U25 10/-  
10P13 6/- EY51 4/6 U37 12/6  
12BH7 6/- EY81 4/6 U31 4/6  
12DL1 6/- EY86 4/6 U35 4/6  
20B1 4/6 FC4 4/6 U191 4/6  
20P3 6/- KT36 4/6 U281 6/-  
185BT 12/6 KT66 7/6 U801 12/6  
B35 4/6 KT81 4/6 UL41 4/6  
DIT4 5/- KT83 7/6 UL44 6/-

Most Pre-war 4, 5, 7 and 9 pin valves of British, European and American manufacture, 5/- each. Postage and packing 6d. per valve. Orders over £1-free.  
**NEW TRANSISTOR SETS.** Red Spot 2/6, OC45, OC72, OC76, 7/6, OC35 11-watt, OC201 (Silicon) 20/-, Postage 3d. each.  
**SPEAKERS:** 6in. 5/-. Postage 2/-.  
**LINE OUTPUT TRANSF.** for 20/-.  
**CONSTRUCTORS' PARTS:** 2lbs. assorted components from TV Sets, resistors, condensers, pots, electrolytics, valve-holders, etc., 7/6. Postage 2/6.  
**VALVE PARCEL.** 12 valves, all different, as taken out of TV sets, ideal spares, 9/6. Post and Packing 1/6.  
Send stamp with enquiries or for full list of 1000 valves, tubes, transistors, etc. to: "ST. JOHN'S RADIO", 3 Jews Row, London SW18. Phone: VAN 8922

**RATES:** 6/6 per line or part thereof, average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless", Tower House, Southampton St., London W.C.2.

**TELEVISION TUBE SHOP**

now stock

**Tubes for every make of set OVER 600 TUBES IN STOCK**

12 inch Mullard type ...	£4. 5.0
12 inch Mazda type ...	£4.15.0
14 inch Mullard type ...	£5. 5.0
14 inch Mazda type ...	£5.10.0
15 inch Mullard type ...	£5.15.0
16 inch G.E.C. & Mullard type	£6.12.6
17 inch Mazda & Mullard type	£6.10.0
17 inch G.E.C. & Brimar type	£6.15.0
21 inch Mullard type ...	£8. 0.0

Add 10/- for insured carriage to your door within 48 hours, or 5/- via B.R.S. Terms £2 down (plus carriage). All tubes tested before despatch and guaranteed for 12 months. Guarantee cards enclosed with each tube. **Special Purchase of 110", 17 inch tubes—** Slight mark, Guaranteed for 12 months. Mazda CME 1703 replace AW43-88, GEC 7405A £6. **Shop Soiled Tubes.** (Slight scratches or marks) Guaranteed 12 months. Ideal for second set. 12in. 3/18, 31-34 5/6, MW31-74 50/-, 14in. MW 36-44 27/6, CRM141 55/-, 17in. CRM171, MW 43-64 60/-.

Others available from time to time. Please enquire. **Service Engineers** Our Rebate Scheme shows real savings—send for details.

**Television Tube Shop**

48 Battersea Bridge Road, S.W.11  
BAT 6859  
Just South of the Bridge. Open Saturdays until 4 p.m.

**Variable Condensers,** transmitting types 2000 v. spacing, 7, 40, 60, 100 or 150 mmf. or 2 x 2 x 40 mmf. All 7/6 each (1/6). **Electrotype Type 600** moving coil microphones with push to talk switch and cord 70/- (3/6). T-17 microphones with switch and cord 20/- (2/6). Post Office Table type carbon microphones, 12/6 (2/6). Meters 6 4in. flush 0/1 ma calibrated 0/30, 30/- (2/6). Miniature 1 1/2in. dia. flush 0/1 ma calibrated 30 divisions 0/60, 30/- (1/6). Helical Potentiometers, 5000 ohms 8 turns 12/6 (1/6). Miniature sealed Relays 1700 + 1700; 700; 145 + 145 or 2.5 ohms all 7/6 each (1/6). TA-12 Transmitters £5 (10/-). AM-36/AC American Amplifiers with 4 valves and dynamotor for 28 v. 5 watts output, 25/- (5/-).

40 PAGE LIST OF OVER 1,000 ITEMS IN STOCK AVAILABLE—KEEP ONE BY YOU

24 v. 1A Smooth D.C. Supply. Comprising transformer, metal rectifier, choke, condenser input 200/250 v. A.C., the four 27/6 (3/6). **Audio Transformers,** Bendix, R.C.A. or G.E.C. Mike 7/6 (1/6). Interstage 7/6 (1/6). ET-4336 Drive 15/- (3/6). 50 watts Bendix 15/- (3/6). 85 watts Woden 40/- (7/6). 200 watts G.E.C. 65/- (7/6). P.O. Raeks 5ft. high, 19in. wide 55/- (10/-). Rectifier sets 200/250V. A.C. to 110 v. 750 ma or 50 v. 1A in metal cabinets, 59/6 each (7/6). Chokes, high quality, guaranteed plus 50% continuous rated 11H. 270 ma 15/- (3/6). 20H 400 ma 20/0 (5/-). Morse Keys American J-47, 5/- (1/6). British enclosed 7/6 (2/6).

We have large quantities of "bits and pieces" we cannot list—and invite your enquiries—we can probably help—every one answered.  
Amount in brackets are carriage England and Wales.  
**P. HARRIS, ORGANFORD, DORSET.**

**RECEIVERS & COMPONENTS (continued)**

**KINGSLAND ELECTRONIC COMPONENTS Stupendous Offers**

5in. Speaker, new, 3 ohms, 15/9. High gain Transistors and Ferrite Aerials 3/9 each. Diodes, 1/9. All with circuits. XA116 Transistors. Ideal I.F. amp, 45s k/cos, or L.F. driver, gain 12.5, 5/6 each. New, lightweight Headphones, 2000 ohms. General use, adjustable ready for use, 14/6. Driver and Output Transformers, sub-miniature, 10/6 pair. Volume controls, edgewise movement with switch 5K, 20K, 1meg., miniature, 8/6 each. Earpieces, crystal, 9/6. Magnetic, 9/-, complete with sub-miniature Jack and Socket or Jack and Socket, only 3/6. P.W. Pocket 6 Transistor Kit. Complete with printed circuit, cabinet, transistors and speaker. Osborn designed kit and full instructions, all parts guaranteed new. This is the Kit for the Ambitious constructor. £9.10.0. Try our surprise pack of accessories, if not satisfied return within seven days and money will be refunded. 7/6, p. & p. 2/6. 6 assorted voltage droppers, 5/-, p. & p. 1/6. 100 assorted condensers, 6/-, p. & p. 1/9. 6 volt or 12 volt vibrators, 3/6 each p. & p. 1/6. Mike and pick-up transformers ideal for baby alarms, 4/6, p. & p. 1/9. 6 assorted potentiometers, 5/-, p. & p. 1/9. 50 assorted resistances and condensers, 6 miniature valve holders, 2 tag strips, 40 separate contacts each 4/8, p. & p. 1/9.

182 KINGSLAND RD., SHOREDITCH, E.2. Tel: SHO 6572. Sorvvi U.K. only.

**NEW AND Surplus Valves,** fully guaranteed. S.A.E. for List. Also Reclaimed Valves, perfect, 5/- maximum. Genuine bargains, valves bought, LEWIS, 46 Woodford Avenue, 11ford, Essex.

**In Scotland . . . . .**

**RENVUE for Better Value**

**COMPLETELY REPROCESSED TUBE (NEW GUN, SCREENED, ALUMINISED)**

12.6v. and 6.3v., 0.3 amp.,	...
17 and 15in. Types ...	£6.10.0
12.6v. and 6.3v., 0.3 amp.,	...
14in. Types ...	£6. 0.0
12v., 15in. Types ...	£7. 0.0
2v., 12 and 15in. Types ...	£6. 0.0

Electrostatic 90 degree and 110 degree tubes 10/- extra. Carr. paid.

17in. BBC and STV Receivers ... £19.0  
**COMPLETELY OVERHAULD AND FITTED WITH PROCESSED TUBE**  
STV and BBC 14in. Receivers ... £2.10  
**COMPLETE WITH VALVES AND TUBE. CALLERS ONLY. CARRIAGE EXTRA.**  
OPEN SATURDAY AFTERNOON

**Renfrew Electronics Ltd. Anderson Drive Renfrew : Scotland**  
Tel.: Renfrew 2642

**RECEIVERS & COMPONENTS**  
(continued)

**LEADER RADIO**

**REPAICO MINI-7**

The amazing new transistor set for the home constructor. Seven transistors, superhet circuit, fully tunable over long and medium wave. Equal to any manufactured set. Kit complete with instruction data (excluding battery).....£10.00

**REPAICO MINI-4**

The popular pocket four transistor superhet. Size 5 1/2 x 3 1/2 in. with pre-aligned coils and transformers. 2 1/2 in. hgh flux speaker, ferric slab aerial. Easy to build. Kit complete with instruction data, less battery.....£6.19.6

**CLARION TRANSLISTOR TAPE RECORDER**

Amazing reproduction. Push button controls. Speed 3 1/2 l.p.s. Uses 60. spools. Size 9 1/2 x 3 1/2 in. Powered by U2 batteries. Complete with mike and tape. Only 16 1/2 lbs., including carr.

**COLLARO STUDIO TAPE DECK.** 3 motors, 3 speed, only £17.6. S.A.E. with enquiries.

**THE TELETRON TAPEJACK** (Transistorised tuner) Converts your tape recorder into a high quality Radio Receiver. Recording of Radio Programmes directly on tape. High sensitivity. £6.9.0. excluding P4 battery. Carr. 3/6.

**73 VISTA WAY KENTON HARROW, MIDD.**  
Phone WOB 4312.

**KITS BUILT.** tested details S.A.E. "Good Companion" ready built £11/18/6. Mains Transformers size J. KINDER, 6 Hooker Road, Heartsease, Norwich, Norfolk.

**FOR SALE**

ASK your dealer for American Ferro-dynamics. "Brand Five" Recording Tapes—the best tape value!

**100 MICRO-AMP METERS**, brand new and boxed, manufactured by well-known maker. 4 1/2 in. x 2 1/2 in. — 350 ohms Internal Resistance. Scaled as follows: 0-30 MW., 0-1 Watts, 0-20 Watts, 0-12 Volts, 0-200 Volts, 0-100 Micro-amp. A first class instrument at 38/6. Limited supply only. 100 Micro-amp Meters 2 1/2 in. round — 620 Ohms Internal Resistance. Few only at 22/6. Mains Transformers, size 2 1/2 in. x 2 1/2 in. Input 0-200-220-240 volt. Output 250-0-250 volt, 25ma, 0-6.3 volt, 1 amp 8/6. Orders over £1 post free—under add 1/-. **BOLD & BURROWS LTD.**, Verulam Road, St. Albans, Herts. Telephone St. Albans 50717. Personal callers welcome.

**5IN. ELAC 3 ohm Speaker 7/6.** 4 amp Cartridge Puses 5/- 100. Resistors 5/- 100. Condensers 5/- 100. 5k Pots WW 1/-. Small Transmitter Chassis, less valves 2/6. All post free. **E. R. NICHOLLS**, 33-35 Carrington Field Street, Higher Hillgate, Stockport.

**FOR SALE (continued)**

**12 CHANNEL 17in. Television Receivers** in 6000 order £45 each. C.W.O., carriage 20/-. **S. BURNS**, 1 Harewood Drive, Ilford, Essex.

**SOUND VISION**

**BARGAIN PARCEL**

Electrolytic Condensers, Volume Controls, assorted Condensers, etc. £2 value for 5/-. P. & P 6d.

Red Spot, 3/-; White, 3/9; Yellow (6 volt), 2/3; Yellow/Green, 3/9; Red/Yellow, 5/-; STC/TS1 (OC71), 4/3; TS17 (OC72), 6/- each; XA101, 102, XB102, 103, 8/-; OC81D 6/6; OC81, 7/6; OC170, 10/6. P. & P. 6d.

**E.M.I. 4-SPEED PLAYER and P.U.**, 89/6. P. & P. 2/6.

**"VERDIK QUALITY TEN"**

10 watt, push-pull ultra linear Hi-Fi amplifier with pre-amp control. **OUR PRICE £14 19s. 6d.** P. & P. 7/6.

**MARTIN RECORDER KITS**

Model 'C' for Collaro Deck, £11 11s. 0d. P. & P. 2/6.

Collaro Studio 3-speed Deck, £11 15s. 0d. P. & P. 5/-.  
Dynamic Mic. DM-175, 49/6. P. & P. 2/6.

**JASON F.M. TUNER KITS**

F.M.T.1 with valves ... .. £6.10.0  
F.M.T.2 with valves ... .. £7.17.6  
F.M.T.3 with valves, powered ... .. £12.0.0

**PRINTED BOARDS**

Mullard 3-3 ... ..	£	s.	d.
Mullard 5-10 ... ..	11	9	6
Mullard Stereo 5-10 ... ..	1	3	6
Mullard 5-20 ... ..	11	9	6

} P. & P. 6d.

Illustrated Catalogue 1/-.  
**137 MOULSHAM STREET**  
**CHELMSFORD, ESSEX**  
Phone 56815

**AMERICAN MAGAZINES.** Year's subscription Electronics World 43/-; Radio Electronics 49/6; Audio 35/-; Specimens 5/- each. Full catalogue free. **WILLEEN LTD.** (Dept. 40), 9 Drapers Gardens, London, E.C.2

**VHF UNIT.** Ready built Front End F.M. unit. Coverage 85-100Mc/s. I.F. 10.7Mc/s. Single valve (ECC85). Price including circuit and data but without valve, £2/12/3, plus 2/- postage.

**VHF TUNER UNIT**, ready built without dial and valves. Price including circuit and data, £6/16/0, plus 3/6 postage. Delivery ex stock.

(DEPARTMENT 2)  
**ROTOPONS LIMITED,**  
54 BEDDINGTON LANE, CROYDON, SURREY.

**FOR SALE (continued)**

**100 BAYS** of Brand New adjustable Steel Shelving. 72in. high by 34in. wide by 12in. deep, stove enamelled dark green. Sent unassembled. Six Shelf Bay—£3/15/-. Sample delivered free. Quantity discounts. **N. C. BROWN LTD.**, Eagle Steelworks, Heywood, Lancs. Tel: 69018.

**MAKERS' SEALED CARTONS**

GARRARD R.C. 210 ... .. £9. 8.6

NEW GARRARD "AUTOSLIM" 4-SPEED CHANGER ... .. £8. 5.0

B.S.R. UA14 ... .. £7.15.0

B.S.R. TU9 ... .. £4. 5.6

B.S.R. Tape Deck ... .. £7.10.0

COLLARO Tape Deck ... .. £8.10.0

Valves, Transistors, Condensers, Etc., Etc.

**AUTUMN LIST NOW READY**

**H. F. JAMES**

21 Claremont Road, Twickenham, Middlesex.  
Tel. POPesgrove 3579.

**CAR CIGARETTE LIGHTERS 6 or 12V 8/6.** WHITSAM ELECTRICAL, 18 Woodrow Close, Perivale, Middx.

**WANTED**

**WANTED. TEST GEAR,** Meters, Valves, Components, Communication sets, Amplifiers. **HUGGETTS LTD.**, 2-4 Pawson's Road, West Croydon, Surrey.

**WANTED NEW valves and transistors,** any quantity. **S. N. WILLETS,** 43 Spod Lane, West Bromwich, Staffs. Tel: WES 2392.

**WANTED VALVES**

All types for prompt cash. Must be new. State quantity.

**WILLIAM CARVIS LTD.**

103 North Street, Leeds 7

**NEW VALVES** buying, state price. **A. D. A. MANUFACTURING CO.,** 172 Alfreton Road, Nottingham.

**NEW VALVES WANTED**

Any type, any quantity


**CASH PAID**

**R.S.T. 211 Streamham Road,** Mitcham, Surrey.  
**Telephone: MITCHAM 6201**

**HANDICRAFTS**

**JEWELLERY** Simply made. Brooches, Rings, Marcasites. List Free. **WEBBS,** 46 Burnway, Hornchurch, Essex.

(Continued on next page)

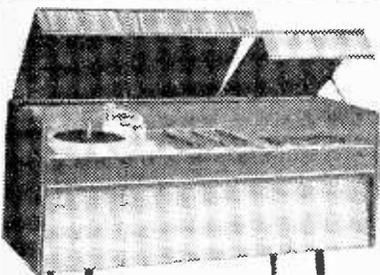

**GP76—FOR STEREO OR MONAURAL**  
4 1/2 in. wide, record storage. Control Panel. Desk 17 1/2 x 16 in. Tygan grille. Cash Price £22.10.0 or £4.10.0 dep. and 18 payments of 21/6 monthly. Delivery 15/- Write for Catalogue.

**CABINETS, ENCLOSURES and EQUIPMENT by STAMFORD**

	Cash	Hire P'chase
		Dpct. 18mths.
<b>SPEAKERS</b>		
Axiotele ..	£8.15.4	27/8
Axiom 110 ..	£5. 2.5	20/8
Axiom 300 ..	£11. 5.9	45/2
WB HF 1012 ..	£5. 2.8	20/6
10in. Golden FSB	£8.10.8	34/2
		8/2
<b>MOTORS</b>		
Garrd 210 Mono	£13. 7.2	53/6
Garrd 4 HF Mono	£19.15.2	79/8
Garrd TA Mk. II, Mono ..	£8. 3.8	36/9
		8/11
<b>CHASSIS</b>		
Armstrong 208 ..	£23.15.0	95/-
Armstrong Jubilee	£31.15.0	127/-
Armat's Stereo 55	£33.15.0	135/-
Armat's Stereo 12	£44.15.0	179/-
		42/9
<b>TUNERS</b>		
Armstrong SP3 ..	£28.10.0	114/-
Roters Switched	£18. 7.3	65/9
Roters Variable	£28. 9.6	108/-
		25/4

**A. L. STAMFORD** Dept. R 39  
84/86/88 WYMOUTH TERRACE  
HACKNEY ROAD, LONDON, E.2.

## MISCELLANEOUS

DIAMOND  STYLUS

## FOR DIAMONDS

Manufacturer's offer to users—send us your old stylus arm and we will retip with finest Transcription quality Diamond.  
To ensure best production every Diamond is inspected for finish and radius with 500 magnification.

**FOR £1.0.0 ONLY**

Or we will supply complete with any stylus arm for £1 5s. 0d. Tax Paid and will despatch within 48 hours of receipt, post free.

**All Diamonds are Guaranteed for One Year.**

(Sapphires also supplied 4/6 Tax Paid)

Mail Orders to:—Dasco, Frith Park, Tadworth, Surrey.

## ELECTRONIC MUSIC ?

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes. It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swing.  
Write NOW for free leaflet and further details to C. & S., 20 Maude Street, Darlington, Durham.

## BOOKS &amp; PUBLICATIONS

**FIND TV SET TROUBLES IN MINUTES** from that great book 'The Principles of TV Receiver Servicing' 10/6 all book houses and radio wholesalers. If not in stock, from Secretary, I.P.R.E., 20 Fairfield Road, London, N.8.

## SERVICE SHEETS

**SERVICE SHEETS** for all makes of radio and TV, 1930-1962. Prices from 1/-, with free fault-finding guide. Catalogue of 6,000 models 1/6. 125 Radio/TV sheets covering 370 popular models 20/-. S.A.E. inquiries HAMILTON RADIO, Western Road, St Leonards, Sussex.

38 SET WALKIE TALKIE  
CIRCUIT INFORMATION

Alignment procedure. Faults. Components. Diagrams etc. P.O. 5/-.  
18 SET TRANSMITTER RECEIVER

## CIRCUIT INFORMATION

Description. Operation. Values. Diagrams. Tests, etc., P.O. 5/-. Your address in block capitals, please.

## CAMPBELL

Everland Road, Hungerford, Berks.

**SERVICE SHEETS.** Radio and Television 4/- each, list 1/-. All old and modern receiver sheets available. Faultfinder files 2/- each. List now available 1/-. KAYBRO PUBLICATIONS, 44 Old Bond Street, London W.1.

**SERVICE SHEETS.** Radio and TV 4/- each. List 1/-. All orders despatched on day received. Also manuals for sale and hire. S.A.E. please. SULTAN RADIO, 29 Church Road, Tunbridge Wells, Kent.

**SERVICE SHEETS,** Radio, TV, 5,000 models. List 1/-. S.A.E. enquiries: TELRAY, 11 Maudland Bk., Preston.

## SITUATIONS VACANT

# Training for engineers in the Electricity Supply Industry

The Electricity Supply Industry employs 18,000 electrical and mechanical engineers in all parts of England and Wales. They are responsible for generating electricity in the power stations, transmitting it over the Grid, and distributing it throughout the country. To keep this key force up to strength as older staff retire and sales of power rise, the industry needs each year to recruit several hundred young men to its technical training schemes.

Five-year apprenticeships are available to school-leavers who hold either a good Ordinary level G.C.E. including maths, English and science, or two Advanced level passes in maths and physics, plus a good G.C.E. at "O" level. Training is by means of planned practical experience, combined with day or "sandwich" release leading to an engineering qualification.

Two-year traineeships are offered to graduates holding a degree in electrical or mechanical engineering from a British university. Training provides extensive and varied practical experience and satisfies the requirement of the professional institutions.

Traineeships are also offered to holders of an engineering diploma, and their training will be planned to take into account their previous practical experience.

On satisfactory completion of training, all apprentices and trainees are guaranteed employment in this essential and expanding industry. A wide range of careers is available, in many types of engineering, including research and commercial development.

For further information write to:

The Education and Training Officer,  
The Electricity Council, 155 Winsley Street, London, W.1

## SITUATIONS VACANT

(continued)

**CITY AND GUILDS** (Electrical, etc.) on "No pass—no fee" terms. Over 95% successes. For details of Electrical Engineering, Applied Electronics, Automation etc., send for our 148-page handbook, free and post free. B.I.E.T. (Dept. 242A), 29 Wright's Lane, London, W.8.

**TV AND RADIO, A.M.Brit.I.R.E.,** City and Guilds, R.T.E.B. Cert., etc. on "No pass—no fee" terms. Over 95% successes. For details of exams and courses (including practical apparatus) in all branches of Radio, TV and Electronics, write for 148-page handbook, free. B.I.E.T. (Dept. 242G), 29 Wright's Lane, London, W.3.

**A.M.I. Mech E., A.M.Brit.I.R.E.,** City and Guilds G.C.E., etc. brings high pay and security. "No pass — no pay" terms. Over 95% successes. For details of exams and courses in all branches of Engineering, Building, Electronics, etc., write for 148-page handbook, free. B.I.E.T. (Dept. 242B), London W.8.



*Servicing electronic computer for Comet simulator*

# Make your hobby your career

In today's R.A.F. you can work on some of the most sensitive electronic equipment ever made

The man in this photograph is an instrument fitter at work. At least, it's called work, but to him it has the fascination of a hobby—a paid hobby at that. Still, he's an enthusiast; anything to do with electronics and he's not happy until he's ferreted out all the secrets. And there are plenty of secrets in the R.A.F. In fact, you don't really know what advanced equipment is until you've handled some of the R.A.F. stuff.

If you have the flair that makes the born electronics man, the R.A.F. offers you a satisfying career. You will get a skilled training that is yours for life. You get paid well, you live well—and you may travel anywhere in the world. There's no doubt about it, —the R.A.F. gives you a secure career—and an adventurous one.

**THE FUTURE IS WITH THE R.A.F.**

**The Royal Air Force**

.....

● Fill in this coupon and you will be sent, without obligation, a free copy of "The Man on the Ground", an illustrated booklet giving details of all R.A.F. trades.

● **NAME** \_\_\_\_\_

● **ADDRESS** \_\_\_\_\_

● \_\_\_\_\_

● **DATE OF BIRTH** \_\_\_\_\_

● *Send the completed coupon to:*

● **R.A.F. Careers Information Centre (PW 116C),**

● **Victory House, Kingsway, London, W.C.2.**

● .....

## SITUATIONS VACANT

(continued)

### PHILIPS ELECTRICAL LIMITED

45 Nightingale Lane, Balham, S.W.12

#### ELECTRONIC ENGINEERS

required for our Medical X-Ray service and installation department. TV radio or radar engineers would be considered. Applications to the Personnel Officer at the above address, or telephone Kelvin 7766 for appointment.

## EDUCATIONAL

### LEARN RADIO AND ELECTRONICS

the new and practical way! Hosts of absorbing experiments carried out at home under expert guidance to teach you Radio in a new, enjoyable and interesting way. Construction, servicing and fault-finding on equipment made easy for the first time! No previous experience needed. No mathematics used. Free brochure from: Dept. 11 P.W., RADIO-STRUCTUR, Reading.

**WIRELESS.** See the world as a Radio Officer in the Merchant Navy; short training period; low fees; scholarships, etc., available. Boarding and Day students. Stamp for prospectus. **WIRELESS COLLEGE,** Colwyn Bay.

**"HOW AND WHY"** of Radio and Electronics made easy by a new, non-maths practical way. Postal instruction based on host of experiments and equipment building carried out at home. New courses bring enjoyment as well as knowledge of this fascinating subject. **FREE** brochure from: Dept. P.W., 12 RADIOSTRUCTOR, Reading.

**TRAINING** in Radio and Television Servicing. Next full-time One Year course commences on 3rd January. Recognised by R.T.E.B. for new Radio and Television Servicing Certificate examinations. Details from: **THE PEMBRIDGE COLLEGE OF ELECTRONICS,** 34a Hereford Road, London, W.2.

$$X = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

**DON'T FUMBLE** with Formulae. Master Mathematics quickly and easily the Understandable Way.

**1st lesson and details FREE**

The Dryden School of UNDERSTANDABLE MATHEMATICS

■ 11F Dryden Chambers, Oxford St. ■  
 ■ London, W.1. ■

■ Name \_\_\_\_\_ ■

■ Address \_\_\_\_\_ ■

■ \_\_\_\_\_ ■

■ \_\_\_\_\_ ■

(Continued on next page)

**EDUCATIONAL (continued)**

**RADIO & TELEVISION SERVICING.** Home-study courses with special schemes of practical work are available from the Pembridge College.

- (1) Introductory course for beginners.
- (2) More advanced courses covering new R.T.E.B. Intermediate Certificate.

Retails from: **THE PEMBRIDGE COLLEGE OF ELECTRONICS**, 34a Hereford Road, London W.2.

**Radio Television & Electronics**

Learn at home with the world's largest home study organisation, Brit.I.R.E.; City & Guilds; R.T.E.B., etc. Also Practical Courses with equipment. No books to buy.

Write for **FREE prospectus** stating subject to

**I.C.S.**

(Dept. 541), Intertext House, Parkgate Road, London, S.W.11

**THE Incorporated Practitioners in Radio and Electronics (I.P.R.E.) Ltd.**, Membership Conditions booklet 1/-, Sample copy of I.P.R.E. Official Journal 2/-, post free. Secretary, 20 Fairfield Road, London, N.8.

**ELECTRONICS**

Key to YOUR future?

An exciting career - A new Hobby -

Your own spare or full-time BUSINESS!



New experimental course includes big kits for building test gear and a complete AM/VHF receiver.



FREE brochure from

**RADIOSTRUCTOR**

DEPT. E77, READING, BERKS.

**SOUND RECORDINGS**

**RECORDING TAPE**, save up to 30% send for list; also 50 second-hand recorders in stock.—E. C. KINGSLEY & CO., 132 Tottenham Court Road, London, W.1. EUS 6500.

**THE FAMOUS "TELEFUNKEN" TAPE HEADS.** 30/20 Kcs. TWIN TRACK. RECORD/REPLAY AND ERASE. BRAND NEW 30/- The Pair. LIST 5 Gns.

A. Fanthorpe Ltd., 6-8 Hepworth's Arcade, Hull, Yorkshire.

**EDDY'S (NOTTM) LTD.**

172 Alfreton Road  
Nottingham

New or Surplus VALVES  
Guaranteed and Tested by Return Post.

AC2/ PENDD	EZ40 EZ41	6/3 7/-	6F13 6F15	6/11 8/6
CIC	HL23DD	7/6	6F33	6/6
CY31	MU14	7/11	6J5G	2/9
DAF91	KT33C	6/6	6J5GT	3/9
DAF96	OZ4	5/-	6J7G	5/-
DF91	PEN36C	8/-	6K7G	1/11
DF96	PCL84	9/6	6K8G	5/6
DL96	PZ30	9/6	6Q7G	5/9
DL93	SP6	2/6	6SG7M	4/9
EAF42	TDD4	7/6	6S17M	5/9
ECC81	UCH42	7/6	6SN7GT	4/3
ECC82	UF41	7/9	6V6G	4/9
ECC85	VP23	6/6	6V6GT	6/-
EB41	ID5	7/6	6X5G	5/6
EB91	IL4	3/6	6X5GT	6/6
ECH42	IR5	5/6	7C5	6/11
ECL82	IS5	4/9	10F1	6/6
EF36	IT4	3/6	10P13	9/6
EF37	3S4	5/11	12A6	5/3
EF39	SU4G	4/9	12A6	5/3
EF41	SZ4G	7/6	12AT6	7/6
EF42	6A7	10/6	12K7	5/3
EF50	6AG5	3/6	12Q7	5/3
EF80	6AC7	4/-	20P1	9/6
EF86	6B8G	2/11	25A6G	8/-
EF91	6B16	6/11	25L6GT	8/6
EF92	6C5	4/9	35L6GT	8/11
EL41	6CH6	9/6	35W4	6/9
EL91	6BW7	6/11	3S24	5/3
EY86	6C4	3/6	954	1/6
			955	3/6
			956	2/6

**BUILD YOUR OWN CAR RADIO!**



7 Transistors Long and Medium Waves. Two watts output RF stage and automatic gain control. (6 or 8)

12 volts, please state). full instructions at Size: 7 1/2 x 7 1/2 x 2 1/2 in. Speaker 17/11 extra (7 x 4 ellipt.) if required. Postage and packing 5/- extra per kit.

**10 1/2 Gns.**

**CRYSTAL SETS.** Complete 2 wave bands high gain, 17/11, also with transistor amplifier extra, 9/11, P. & P. 2/6.

**HEADPHONES.** High res. to suit above crystal set. Good quality, 13/11, P. & P. 1/6.

**NIFE ACCUMULATORS.** 1.25 v. size 3 x 2 1/2 x 3/4 in. 7 amp. hrs., weight 13ozs., 2/6 each. P. & P. 2/-, one only add 9d. per cell.

**THROAT MIKES.** 2/- ea., P. 8d. Could be used for electrifying musical inst. etc.

**DIMMER SWITCHES.** Ideal for train speed regulators, 1/11, Post 1/3.

**GERMANIUM DIODES.** 9d. each. 7/- dozen. Post 6d.

**VIBRATORS.** 12 volt, 4 pin, 4/11. 6 volt, 4 pin, 8/11. Post 1/6.

**POCKET RADIO.** 2 transistor with miniature speaker. Complete with all parts, wiring diagram and full instructions, 27/6. Batteries 1/-, P. & P. 2/-.

**LUXEMBOURG AERIALS.** Complete and easy to fit. No technical knowledge required, 3/11, Post 6d.

**V.H.F. AERIALS.** 6/11, Post 10d.

All Above are New and Guaranteed.

Any parcel insured against damage in transit for only 6d. extra per order. All uninsured parcels at customers risk. Post and Packing 6d. per valve extra. C.W.O. or C.O.D. only. C.O.D. charge 3/- extra, S.A.E. with enquiries.

**THE PUNCH YOU NEED!**

**HOLE PUNCHES**

<b>Instant Type</b>	...	...	5/6 ea.
3/4" diameter	...	...	5/6 ea.
<b>Screw-up Type</b>	...	...	6/8 ea.
1 1/2" diameter	...	...	6/8 ea.
1 1/2" "	B7G	...	7/2 "
1 1/2" "	B8A, B9A	...	7/8 "
1 1/2" "	...	...	8/3 "
1 1/2" "	...	...	8/7 "
1 1/2" "	...	...	9/6 "
1 1/2" "	...	...	10/11 ea.
1 1/2" "	...	...	13/3 "
1 1/2" "	...	...	15/6 "
1 1/2" "	B9G	...	17/11 "
1 1/2" "	...	...	20/4 "
2 3/32" "	Meter	...	27/8 "

Postage and packing 1/11

Postage and packing 2/3

Complete set including postage and packing £7.10.0d.

**OLIVER & RANDALL LTD**

Dept. 7.

40 Perry Hill, London, S.E.6

Tel.: BECKenham 8262

**Lyons Radio Ltd.**

Telephone: SHEpherds Bush 1729

3 Goldhawk Road, Shepherds Bush, London W.12

**ROTARY TRANSFORMERS.** Size of both 6in. long x 3in. dia. Type 31—input 12v. D.C. Output 250v. D.C. at 125mA. PRICE ONLY 12/6. Type 32—input 12v. D.C. Output 500v. D.C. at 65mA. PRICE ONLY 7/6. Post either type 3/11.

**TUBULAR EXTENSION SPEAKERS.** Brilliant new design for use with transistor valve and car radios, amplifiers, auxiliary speakers in Hi-Fi, etc. Frequency response 65-7000 cps, rated at 1.5 watts. Size 9 1/2 in. x 3 1/2 in. dia. Mounts horizontally, vertically on wall or sits on desk. PRICE ONLY 57/6, post 2/- send S.A.E. for illustrated leaflet.

**SUPPLY UNITS W/S. No. 19. Mk.3.** Rotary transformer units in metal cases, 10 x 8 x 6ins. Input 12v. D.C. Output approx. 220v. D.C. at 125mA and 450v. D.C. at 65mA. PRICE ONLY 21/-, carriage 5/6.

**I.F.F. UNITS.** Contain a wealth of useful components including relays, 10 valves (6-8SH7, 2-1930, 2-8H6) and a rotary converter rated at 18v. D.C. input. Using only 12v. input the output obtainable is of the order of 250v. D.C. at 80mA. One end of converter is fitted with blower fan, the other with a gear box. Both can easily be removed. The converter can also be operated from 6v. D.C. Two driving shafts protrude from the gear box and rotate at approx. 4 and 16rpm for 12v. input and about half this speed for 6v. input. Offer good value and usefulness for experimenter and handyman. PRICE ONLY 25/-, carriage 6/6.

**SLYDOK FUSEHOLDERS.** 15 amp. size, 19/8 doz., 6 for 11/8; 3 for 6/3. Reduced prices for larger quantities.

## COYNE'S NEW PIN-POINT TV TROUBLES

**TAKES HEADACHES OUT OF  
ALL SERVICING PROBLEMS**



Your most useful on-the-job "tool"! Quickly and easily pin-points the exact trouble in any TV set. Covers 78 symptoms, 700 trouble spots. Over 340 cross-indexed pages; 50 time-saving Check-Charts; 280 diagrams and photos; explanation of circuits and designs.  
**SIMPLE CHECK-CHART SYSTEM SAVES TIME!**

This amazingly practical handbook shows you how to find the trouble in any TV circuit **FAST!** Simple cross-index tells you in what section you'll find cause of trouble. Handy Check-Charts then help you accurately locate the **EXACT** trouble spot. Cut waste time, eliminate hours of aggravation, get right to the heart of the trouble in minutes.

**USE THIS BOOK RIGHT ON THE JOB—NO NEED TO MEMORIZE!**

This Pin-Point Book was designed especially for on-the-job trouble-shooting. You simply turn to the indexed section, locate the circuit description and Check Chart, and in minutes you have the trouble spot located and ready for repair. No complicated theory or mathematics. Down-to-earth, practical circuit description, service methods and trouble-shooting techniques. Published by the famous Coyne Electrical School and approved by leading authorities in the field.

**J. E. C. Grover of Breatham says:**  
"Immediately I glanced through this book I was convinced that your claim concerning the merits of this work were justified, for it is, without a doubt, the finest book of its kind that I have ever come across. It is not only unique in its presentation but it is also superbly produced."

**G. Axam of London, S.E.3. says:**  
"I have spent nearly £50 on technical books over the past 5 years all of which I feel has now been wasted as your book is the best I have yet had the pleasure of examining, it is practical to the point, with just the right amount of technical information needed, covering almost every aspect of TV servicing."

### FREE TRIAL OFFER!

Mail Coupon now for fast return service! To **BIM-TECH TECHNICAL BOOKS**, Dept. A-6, Gater's Mill, West End, Southampton, Hants.

**RUSH TV Troubles** for free seven day trial. If not satisfied I may return book and owe nothing. If I keep the book I will send full amount of 22/- including postage within 7 days, OR two payments of 11/- within 30 days.

**SAVE!** Send only 31/6 if paying cash with order. (We pay postage). Same 7-day-money-back guarantee.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

County \_\_\_\_\_

# RADIO CLEARANCE LTD.

The oldest Component Specialists in the Trade  
27 TOTTENHAM COURT ROAD, LONDON, W.1.

Telephone: MUSEUM 9188

TRADE ENQUIRIES INVITED

EST. 30 YRS.

IN THE HOME, IN THE CAR, BY THE SEA, IN FIELDS AFAR, THE

## "CONTESSA" IS VOTED BEST OF ALL

A really remarkable 2-Band 6-Transistor Superhet Kit—25,000 satisfied customers and still in huge demand.

The Contessa is the professional looking set with the professional performance.

Study these brilliant features which cannot be found in any other kit—



- Waveband coverage of 530 kc/s to 1,620 kc/s and 160 kc/s to 270 kc/s.
- Assured reception of at least a dozen stations in daylight!
- Large clearly-calibrated station-named dial.
- Internal high-gain, Ferrox aerial.
- 5:1 ratio slow motion tuning.
- Fitted with the latest 12,000-line high flux loudspeaker.
- Power of 410 milliwatts from the single-ended push-pull final stage.
- Specially designed aerial matching coil for use in a CAR.
- Only first-grade fully guaranteed matched transistors and diodes are used.
- Double tuned IF transformers for maximum gain and knife-edged selectivity.
- Fully drilled printed circuit panel marked with component numbers.
- The two-colour case measures 10 x 7 1/2 x 3 1/2 in. and weighs approx. 4 lbs. when assembled.
- Battery lasts 4 months with normal usage.
- Book supplied with detailed assembly instructions, diagrams and circuitry.
- Anyone can build this set—everything supplied just a soldering iron required.

Inclusive price for all associated components, cabinet and battery, complete in every detail, or our **BUY AS YOU BUILD SCHEME**, any parts sold separately. Send for comprehensive descriptive Manual and Parts List, 3/6 post free  
Plus 3/6 P. & Pkg. **£10.19.6**

And now this is what you have been eagerly waiting for—

## THE "CAPRI"

A miniature pocket transistor kit that **REALLY** works, retaining the most attractive features of the famous "Contessa". SIX first-grade Mullard transistors and diode are employed in a highly sensitive superhet MW and preset LW circuit embodying the most modern design practice. A special 2 1/2 in. high gauss loudspeaker provides surprising volume and a personal earpiece socket is also available. An attractive two-tone plastic case is supplied in two colours. Ivory/Red or Ivory/Blue, the full constructional details being given with each set of parts. The total measurements of the "Capri" are 4 1/2 x 2 1/2 x 1 1/2 in. **SEE AND HEAR A WORKING MODEL TODAY.**



Inclusive price for all associated components, case and battery, complete in every detail on our **BUY AS YOU BUILD SCHEME**. ANY PARTS SOLD SEPARATELY.

**£7.10.0**  
plus 2/- P. & Pkg.

STAMPED and ADDRESSED ENVELOPE with any enquiry please. But regret no lists or catalogues—our stocks move too quickly!

PLEASE ALLOW **FULL POSTAGE AND PACKING CHARGES**

Terms of Business:  
**CASH WITH ORDER OR C.O.D. ON ORDERS OVER 10/-**

**D.C. SUPPLY KIT.** 12 v. 1 a. consisting of a partially drilled metal case, mains trans., F.W. Bridge Rectifier, 2 fuseholders and fuses. Change Direction switch, variable Speed regulator and circuit. For 200-250 v. A.C. mains. Suitable for Electric Trains. Limited number available at 33/9.

**SELENIUM RECTIFIERS**  
 F.W. BRIDGE H.T. Types H.W.  
 6/12v. 1 a. .3/11 150 v. 40 m.a. ... 3/9  
 9/12v. 2 a. .6/11 250 v. 50 m.a. ... 4/11  
 6/12v. 3 a. .9/9 250 v. 60 m.a. ... 4/11  
 6/12v. 4 a. .12/3 250 v. 80 m.a. ... 5/11  
 6/12v. 6 a. .15/3 250 v. 250 m.a. ... 11/9  
 6/12v. 10 a. .25/9 **CONTACT COOLED**  
 250 v. 80 m.a. H.W.  
 6/11. 250 v. 50 m.a.  
 2x v. 2 a. .15/9 F.W. (Bridger) 8/11

**B.S.R. MONARDECK TAPEDECKS.** Speed 31in. per sec. High quality recording heads. 25/19.6. Carr. 5/6.

**SPECIAL OFFER OF BRAND NEW BRIMAR TRANSISTORS.** TS1 Audio lots of three. 8/11; TS7 R.F. three for 14/9.

**EX. GOVT. CASES.** Size 14-10Hn. high. Well ventilated. Black crackle finished. Unrilled cover. IDEAL FOR BATTERY CHARGER OR INSTRUMENT CASE OR COVER COULD BE USED FOR AMPLIFIER. Only 9/9, plus 2/- postage.

**LINEAR TREMOLO/PRE-AMP UNIT** Type TP/U/L with 3 controls, volume, amplitude and frequency. Inputs for guitar and microphone. Requires power supply of 250 v. 10 m.a. and 6.3 v. 1 a. available from any R.S.C. or LINEAR amplifier. The unit is merely connected to normal input socket of hi-fi amplifier or Guitar amplifier. Only 5 gns.

**R.S.C. BRADFORD MANCHESTER and LEEDS**  
 (Manchester) Ltd.

**R.S.C. GRAM AMPLIFIER KIT.** 3 watts output. Negative feedback. Controls Vol. Tone and Switch. Mains operation 200-250 v. A.C. Fully isolated chassis. Circuit etc. supplied. Only 39/9. Carr. 3/9.

**HI-FI 10 WATT AMPLIFIERS**  
 Brand new. Manufacturer's discontinued line. Fitted latest Mullard valves. Dual inputs for "trikes" and gram., etc. Bass and Treble Controls. High sensitivity and quality. Output for 3 ohm or 15 ohm speaker. For 230-250 v. A.C. **£7.19.6** Carriage 7/6.

**PORTABLE TRANSISTOR RADIO DESIGN** with 7 x 4in. loudspeaker and Car Aerial Socket. Attractively designed and covered cabinet size 8 x 10 x 3in. Gold dials with revolving perspex. Controls. M. and L. wavebands. Six first grade Brimar Transistors and Printed circuit. Easy to follow instructions and diagrams. 2/6. Total cost of parts only 29.19.6, carr. 3/9. Demonstration models at all branches.

**R.S.C. TRANSISTORISED GRAM AMPLIFIER.** Output 1 watt, for 3 ohm speaker. Transistors XB113, XB113, XC101A, XC101A. Suitable for any normal crystal pick-up. Only 69/9.

**MULTI-METERS.**  
**CARY A10.** Basic Meter sensitivity 155 micro-amps. A.C. and D.C. ranges £4.17.6.  
**CARY B20.** Sensitivity up to 10,000 ohms per volt. A.C. and D.C. £6.10.0.  
 S.A.E. will bring leaflets on A10 or B20.

**RELAYS.** Carpenters' Type. Polarised 2 times 9,500 turns at 1.685 ohms, 13/9. Miniature Type C.G.E. 670 Sealed, wire ends. 4 covers. platinum MX855. 12/8.

**SPECIAL OFFER EX. GOVERNMENT SELENIUM RECTIFIERS.** 12 v. 15 amp. with large square cooling fins. 19/9 each.

**EX. GOVT. SMOOTHING CHOKES.** 200 mA, 3.5 H, 50 ohms; Parmeko 8/9; 100 mA, 5 H, 100 ohms 3/11; 150 mA, 10 H, 50 ohms 9/8; 80 mA, 20 H, 900 ohms 5/8; 120 mA, 12 H, 100 ohms 8/8; 50 mA, 50 H, 1,000 ohms 6/8; 100 mA, 10 H, 100 ohms 6/8; 60 mA, 5-10 H, 250 ohms 2/11.

**EX. GOVT. MAINS TRANSFORMERS**  
 Primaries 200-250 v. 50 c.p.s. A.C.  
 250v. 60mA 3.3v. 2a. ... 11/9  
 250-0-250v. 60mA 6.3v. 2a. ... 12/9  
 270-0-275v. 100mA 6.3v. 7a. 5v. 3a. ... 22/9  
 300-0-300v. 60mA 6.3v. 2a. ... 12/11  
 300-0-300v. 100mA 6.3v. 2a. 5v. 2a. ... 15/9  
 3,500v. 5mA 2v. 2a. ... 3/9  
 0-35-0-45-50v. 300mA 6.3v. 3a. ... 17/9  
 12v. 20a. (carr. 7/6) ... 49/9

**2 VOLT ACCUMULATORS**  
 Varleys small size 4 x 3 x 1 1/2 v. 14 A.H., brand new. 6/9 ea., 3 for 15/6.

**R.S.C. BABY ALARM or INTER-COMM. KIT.** Complete set of parts with diagrams, etc. Master Unit housed in veneered walnut cabinet. High sensitivity. For 200-250v. A.C. mains. Fully isolated. Only 79/6. Carr. 5/-. Or assembled ready for use £5.15.0.

**TERMS: C.W.O. or C.O.D. No C.O.D. under 1st. Post 19/9 extra under 22. 2/9 extra under 25. Open 9 to 6. Weds. until 1 p.m., except Manchester open all week. Trade supplied. S.A.E. with all enquiries.**

**Mail Orders to 29-31 Moorfield Road, Leeds 12.**  
**5 and 7 County (Mecca) Arcade, Briggate, Leeds 1.**  
**8-10 Brown Street (Market Street), Manchester 2.**  
**56 Morley Street (next to Majestic Ballroom), Bradford.**  
**73 Dale Street, Liverpool 2.**

**VALVES SAME DAY SERVICE! STOP! LOOK! FREE POSTAGE**

**SETS** 1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL94 ... Set 4 for 19/8  
 DAF96, DF96, DK96, DL96 ... Set 4 for 27/6

1A7GT 11/-	6L19 12/-	30C15 13/6	EBF80 8/-	EZ80 6/3	U52 4/6
1D5 8/-	6LD20 8/-	30PL1 10/-	EBF89 8/9	EZ81 8/-	U78 4/6
1H5GT 9/-	6P1 10/-	30L15 11/-	EBL2 15/6	K73C 7/-	U81 14/6
1NSGT 9/-	6P2 8/6	30L16 10/-	EC040 15/6	K741 11/6	U125 12/-
1B 8/-	6Q7G 8/-	30PL13 11/9	EC081 5/-	K744 5/8	U281 17/-
1S4 8/-	6Q7GT 8/6	30P12 7/6	EC082 6/3	K761 9/-	U291 18/6
1S5 5/3	6SL7GT 4/9	35A5 14/3	EC083 7/7	K763 6/8	U301 18/9
1T4 3/8	6SN7GT 5/8	35L6GT 8/6	EC084 8/3	M114 9/6	UAB30 6/6
1U5 6/9	6U4GT 9/8	35Z4GT 8/3	EC085 7/9	MX40 9/6	UAF42 8/3
3A5 9/6	6V8G 8/6	35Z5GT 8/3	EC090 7/6	N18 7/-	UB41 8/6
3Q4 7/-	6V8GT 6/6	50L6GT 8/6	ECF82 8/6	PC85 10/-	UBC41 7/8
3S4 7/-	6X4 4/6	AC/TH1 18/9	ECH21 13/6	PC84 7/6	UBF89 8/3
3V4 7/-	6X5GT 4/8	AZ31 9/6	ECH35 15/6	PC88 9/3	UC81 7/1
5V4G 4/6	6X5L2 9/9	E36 8/6	ECH42 8/9	PCF80 7/8	UCC84 13/3
5V4G 7/6	7B1 9/-	CL33 12/3	ECH81 7/9	PCF82 8/-	UCC85 7/-
5Y3GT 6/-	7B7 7/6	DAC32 9/6	ECL80 7/6	PCF86 14/-	UCF39 14/6
5Z4G 7/9	7C5 7/6	DAF91 5/3	ECL82 9/-	PCL82 9/-	UCH21 13/6
6A1S 3/9	7C8 7/8	DAF96 7/6	EF8 7/8	PCL83 11/6	UCH42 8/-
6A1MS 3/6	7H7 7/6	DCC90 9/-	EF40 12/6	PCL84 10/-	UCH81 7/6
6A2S 6/-	7S7 8/-	DF33 9/6	EF41 7/9	PCL85 13/6	UCL82 9/9
6A7S 9/9	7Y4 7/-	DF91 3/6	EF80 4/9	PEN44 11/-	UCL83 13/3
6BA6 5/9	10C2 17/-	DF96 7/6	EF85 4/9	PEN36C 8/-	UF41 7/-
6BE6 5/9	10P13 14/6	DH76 4/9	EF86 8/9	PL36 11/6	UF42 5/6
6BH7 5/9	12A7G 5/-	DH77 6/9	EF88 7/-	PL11 9/6	UF85 7/-
6B9 5/9	12A7T 5/-	DK32 11/-	EF91 3/6	PL82 7/-	UF89 7/-
6BR7 12/6	12AUT 6/3	DK91 6/-	EF92 3/6	PL83 7/6	UL41 8/-
6BW6 7/-	12AX7 7/-	DK92 7/6	EL33 9/-	PL84 8/6	UL84 6/6
6CD6G 27/3	12K7GT 4/9	DK96 7/6	EL41 6/6	PL85 11/6	UM4 14/-
6F1 10/-	12K8GT 9/6	DL33 9/-	EL42 9/6	PY40 7/6	UR1C 8/-
6F1G 9/6	12Q7GT 8/6	DL35 9/6	EL43 9/6	PY41 7/-	UU6 13/6
6F13 10/-	12Z3 7/6	DL92 6/-	EM34 6/6	PY42 6/6	UY21 13/6
6F14 10/-	14S7 19/6	DL94 7/6	EM80 8/-	Y33 7/9	UY41 8/6
6F23 10/-	20F2 17/6	DL96 7/6	EM81 9/-	Y41 7/9	UY85 6/6
6K7G 11/1	20F1 17/6	EABC90 5/6	EM84 8/-	U1 9/6	VP4B 9/6
6KTGT 5/-	20P4 20/-	EAF42 8/6	EY51 7/6	U24 17/6	VP41 5/-
6K8G 5/-	25AG9 8/-	EB91 3/9	EY88 7/9	U25 12/9	W76 4/9
6K8GT 9/-	25L6GT 7/9	EB33 5/-	EZ40 8/9	U26 10/-	W77 3/9
6L18 10/-	25Z4G 7/3	EB41 8/-	EZ41 7/-	U50 6/-	Z77 3/8

**MULLARD TRANSISTORS, OC71 6/6, OC72 8/-, Matched Pairs 16/-, OC78, 8/-, OC81 8/-, OC45 10/-, OC44 11/-, OC170 13/6, OC171 14/6.**

**TRANSISTORS from 2/6**  
**YELLOW SPOT A.F. 6 volt, 2/6.**  
**RED SPOTS 3/- each, 3 for 8/6.**  
**WHITESPOT TRANSISTORS, 3/- each.**  
**YELLOW/GREEN 3/3 each, 3 for 9/-.**  
**RED/YELLOW R.F. Type, 5/- each.**  
**GERMANIUM DIODES, 1/- 3 for 2/6.**  
**MULLARD DIODES, OA70, OA79, OA81, 3/- each. OA91 or OA95, 3/6 each.**  
**TRANSISTOR HOLDERS, 1/3 each 3 for 3/6.**

**MINIATURE TRANSISTOR TRANSFORMERS, P-P Driver 4.5 : 1 P-P Output 20 : 1. Boxed with Spec., 9/6 pair.**  
**CRYSTAL EARPIECES with Lead and Plug 8/6. LOW IMP EARPIECES, 8/6.**  
**REPANCO DRX1 CRYSTAL SET COILS M & L, 2/6.**  
**REPANCO DRR2 Dual Range Coils, 4/-.**  
**REACTION CONDENSERS, .0001, 3/-, .0003, 3/9, .0005, 4/-. Miniature .0005, 4/-.**  
**LIGHTWEIGHT HEADPHONES, 2000 ohm, 14/-, 4000 ohm, 15/9.**

**ALL SENT POST FREE IN U.K. by**

**PETHERICK'S RADIO SUPPLIES**  
 22 High Street, Bideford, N. Devon  
 Tel.: Bideford 1217

**S.A.E. WITH INQUIRIES PLEASE**

**READERS RADIO**  
 24, COLBERG PLACE, STAMFORD HILL,  
 LONDON, N.16 **STA. 4587**

Post 6d. per valve extra.  
 Any Parcel Insured Against Damage in Transit 6d. extra.  
 Any C.O.D. Parcel 3/- extra.



## GRAB! This Month's Bargains

### SCREENED CABLES

Screened Microphone Cable, 1st Grade, 9d. yd. 12-Core  
Screened Cable, 2/- yd. 10-Core (5 Pairs) Screened Cable,  
1/8 yd. All plus 2/- P. & P.

### AERIAL EQUIPMENT

**TWIN FEEDER.** 300 ohm twin ribbon feeder, similar K25, 6d. per yard. K35B Telcon (round) 1/6 per yard. Post on above feeder and cable 1/6 any length.  
**COPPER WIRE.** 14 G., H/D 140ft. 17/-; 70ft. 8/6. P. & P. 2/-.  
Other lengths *pro rata*.

**RIBBED GLASS.** 3in. aerial insulators, 1/9 each. P. & P. 1/6. up to 12.

**CERAMIC FEEDER SPREADERS.** 6in. type F.S. 10d. each P. & P. 2/-.

**CERAMIC "T" PIECES.** Type A.T. for centre of dipoles, 1/6 each. P. & P. 1/-.

**2 METRE BEAM 5 ELEMENT W.S. YAGI.** Complete in box with 1 x 25in. mast head bracket. **PRICE 49/-.** P. & P. 3/6.  
**SUPER AERAXIAL CABLE.** 75 ohm, 300 watts, very low loss, 1/8 per yard. P. & P. 2/-, 50 ohm, 300 watt coax, very low loss, 1/9 yd. P. & P. 2/-.

**ABSORPTION WAVEMETERS.** 3.00 to 35.00 Mc/s in 3 switched bands, 3.5, 7, 14, 21 and 28 Mc/s. Ham Bands marked on scale. Complete with indicator bulb. **A MUST** for any Ham shack. 22/6 post free.

**VARIABLE CONDENSERS.** All brass with ceramic end plates and ball race bearings. 50 pF, 5/9, 100 pF, 6/6, 160 pF, 7/6, 240 pF, 8/6, and 300 pF, 9/6. All fitted with rear extension for ganging. P. & P. 1/-. Also Flexible Couplers, 1/- each. B.I. 8 MFD. 1,200 v. D.C. Wkg. Capacitors, 12/6 each. P. & P. 2/-.


## CHAS. H. YOUNG LTD.

THE COMPONENT SPECIALISTS

Dept. "P", 110 Dale End, Birmingham 4. (CEN 1635)  
(No C.O.D. under £1 please.) (By return service.)

## NEW MODIFIED VERSION!

★ 'PW' 6-TRANSISTOR ★

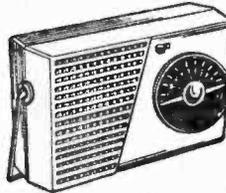

MEDIUM AND LONG WAVE

**POCKET SUPERHET**  
The latest version of this fine performer incorporates improvements giving even greater sensitivity and all round performance.

★ 150 mW Push-Pull Output on 2 1/2in. P.M. Speaker.

★ Guaranteed first grade Matched Transistors.

★ High Q Internal Ferrite Rod Aerial.

★ Printed Circuit and full instructions

All parts required

**£8.19.6**

Every item down to the last nut and bolt is supplied together with easy to follow, step by step instructions—no extras to buy.

**NORCOL LTD.** Castle Road, Camberley, Surrey.

Phone: Camberley 22760.

## REPANCO NEW RANGE OF SHORT WAVE COILS FOR TRANSISTOR RECEIVERS

Range 1	Range 2	Range 3
85 to 200 metres XTA 31 Aerial Coil XTF 32 H.F. Coil XOT 33 Oscillator Coil	35 to 85 metres XSA 34 Aerial Coil XSF 35 H.F. Coil XOS 36 Oscillator Coil	16 to 43 metres XSA 37 Aerial Coil XSF 38 H.F. Coil

By using the 1st harmonic of the XOS 36 coil a separate oscillator coil is not necessary for Range 3.

All coils are miniature using special High Frequency ferrite pots and cores and enclosed in screening cans 3in. square x 1 1/2in.

Boxed complete with circuits—10/- each coil.  
Set of Three 465 k/s I.F. Transformers (Two Type XT28; One Type XT27) for use with the above coils—18/- per set.

**RADIO EXPERIMENTAL PRODUCTS LIMITED**  
33 MUCH PARK STREET, COVENTRY  
Telephone 27114

## CABINETS & HI-FI EQUIPMENT

We can supply any Cabinet to your own specification



"Grosvenor" £22.1.0

This is only one example taken from our extensive range of stock cabinets. Write for our NEW 24 page fully illustrated catalogue on:

**THE LARGEST RANGE OF CABINETS IN THE COUNTRY**

Equipment is also our speciality and we now offer, in a novel book form, A NEW EQUIPMENT COMPARATOR illustrating our range of radio chassis, speakers, tape decks, single players and autochangers.

SEND TODAY for a copy of these two books! which are absolutely FREE.

**LEWIS radio**

100 (P111) Chase Side, Southgate, London, N.14. Pal 3733/9666

## 18,000 O.P.V. MULTIMETER KIT

Ranges 0-0.25 and 2.5 V DC; 10, 25, 100, 250, 500, 1000 V A.C. DC, and output volts; Ohms 100 ohms to 10 Meg. (two ranges); 0.25, 2.5, 25, 250 mA DC (2.5A range 4/- extra). Kit comprises new 3 x 2 1/2in. Weston 0-50 microamps m.c. meter, all 1% multipliers, 1% ready adjusted shunts, padding resistor adjusted for each meter, 3 other resistors, 1 condenser, meter rec., knobs, switches, sockets, pots, circuit, instructions, wiring diag. scale (ohms, dB, uF, mA & V, 10V A.C. scales, i.e. everything except case and battery. Details of 200 pF—0.5uF range. Price 69/11. post free. Circuit, scale etc. 9d. free with kit. 0-50uA meter as above, with circuit, etc. 22/6, post 1/6.

1% High Stability Resistors. Surplus and new list available.

## PLANET INSTRUMENT CO.

25 DOMINION AVE., LEEDS, 7.

### GENUINE BRITISH TRANSISTORS

RED SPOT, 3/-; WHITE SPOT, 3/-; XA102, 9/-; OC44, 11/-; OC45, 10/-; OCTO, 6/6; OCT1, 6/6; OCT2, 8/- (16/- pr.), all other types at list price.

Crystal Diodes Still Only 1/- Resistors: All Values 10% 1 watt, 6d. ea.

**MIN. CONDENSERS FOR ALL TRANSISTOR SETS:** .1 mfd., 1/3; .01 mfd., 11d.; .001 mfd., 1d.; .04 mfd., 1/-

**WIRE:** 6 yds. asstd. 1/8, 12 yds. 2/6.

**JOURNEYMAN "6":** Long and M.W. fully tunable, large PRINTED CIRCUIT (no cramped components) uses 7" x 4" speaker. Pre-aligned I.F.'s. Car aerial socket, everything supplied, including battery and solder, all you need is a soldering iron. SWITCH ON AND IT WORKS. Circuit and plans 1/7. KIT £9.15.0. Send S.A.E. for full details and parts list.

### OAKFIELD RADIO

121 MACCLESFIELD ROAD,  
HAZEL GROVE, STOCKPORT, CHESHIRE

MAIL ORDER ONLY

## FIELD'S RADIOCENTRE

PRINTED CIRCUIT BOARD. 12 x 5 1/2in. 2/6, p. & p. 9d.; 18 x 9in. 7/-, p. & p. 1/3.

**TRANSFORMERS.** Standard size half shrouded, tapped primary, brand new 250-0-250 150 mA., 6 volts at 24 amps., 2 volts at 6 amps. 12/6 each, p. & p. 3/6. Another 215-0-215V at 100mA. 6.3 at 1 amp, 6.3 at 2 amps. 10/- each, p. & p. 3/6.

**MEDIUM SIZED OUTPUT TRANSFORMERS.** Push-pull 15 ohms, suitable for 6V6 or E.L.84, 5/- each, p. & p. 2/-.

**P.C.B. Vibrator Power Packs.** Complete with spare vibrators, bulbs, fuses, all leads 12V, input 230V, 100mA output. Brand new in original carton. Price £1 each, p. & p. 5/-.

**CARBON HAND MIKES.** With pressel switch. Price 5/- each, p. & p. 2/-.

**5in. ELAC LOUDSPEAKERS.** 3 ohms. Brand new. 12/6 each, p. & p. 1/6.

**BUILD YOUR OWN BATTERY CHARGER.** 8 or 12V 1 1/2 amp. transformer and rectifier, complete with circuit. 12/-, plus 2/6 p.p.

**PORTABLE AERIAL.** Ex Radio Sonde. Spring base, 2 section flick action, makes good car aerial. 3/6, plus 1/6 p.p.

**SMOOTHING CHOKES.** Complete with circuit. 8/6, plus 1/6 p.p.

**TANNOY No. 1 LOUDSPEAKER DIAPHRAGMS.** Brand new in maker's tins. 15 ohms. 8/-, plus 1/- p.p.

**MICROPHONE FLOOR STANDS.** Two section telescopic. Fits most types of mike. Heavy Chrome finish. £2.2.9, plus 3/- p.p.

**150mA. Fully shrouded.** 5/-, plus 2/- p.p.


**HEADPHONES.** Ex. Govt. Brand new D.L.R. No. 1. Very sensitive. 8/6, plus 2/- p.p.

**TUNING CONDENSERS. AIR SPACED.** 0.0003 and 0.0005 twin gang slow motion gear drive, beautifully made. 3/6, plus 1/- p.p.

**SHORT WAVE CONDENSERS.** Ex. R.F. unit No. 26 and 27. Brand new 75 plus 75 p.p. silver plated. 2/6, plus 1/- p.p.

**67 LONDON ROAD, CROYDON, Surrey**  
(Croydon 1512)

# KITS THAT 'BUILD THEMSELVES'

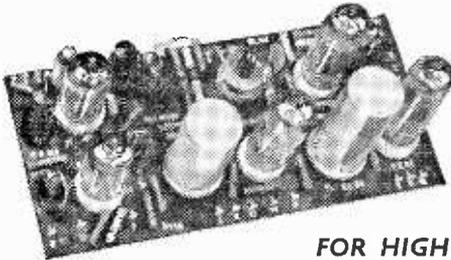

- HI-FI quality printed-circuit amplifiers, supplied checked and assembled
- Complete with valves, transformers and everything down to wire cut to length.

Produced by the makers of amplifiers for some of today's best known recorders and backed by years of experience in audio design. The specially designed kits offered here set entirely new standards of performance and finish for the home constructor. Amplifier available separately or with case and speaker and deck. **EASY TO FOLLOW INSTRUCTIONS.** All equipment complete and guaranteed.

From radio dealers, or in cases of difficulty please write direct

## FOR HIGH QUALITY TWO & FOUR TRACK TAPE RECORDERS

- AMPLIFIER 'C' for Collaro Studio Deck (illustrated above). 11 gns. Case and Speaker for above. 5 gns.
- AMPLIFIER 'A' (4-TRACK) for BSR Monardeck 9 gns.
- AMPLIFIER 'B' (TWO TRACK) for BSR Monardeck 8 gns. Two-tone covered wooden case with speaker for above. 4 gns.
- KIT 'A' with Deck, Case and Speaker. 24 gns.
- KIT 'B' with Deck, Case and Speaker. 21 gns.
- KIT 'C' with Case, Speaker and Deck (as illustrated). 28½ gns.

All amplifiers supplied assembled on printed circuit boards with valves.



MODEL C

# MARTIN RECORDAKITS

Leaflet free on request. Set of full instructions for any one model 2/6d. post free. (Allowable on purchasing kit).

COUPON BRINGS DETAILS →

MARTIN ELECTRONICS LIMITED,  
155 HIGH ST., BRENTFORD, MIDDIX.

Leaflet on Martin Recordakits please.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

(In Block Letters.)

P.W.I.

## NEW VALVES!

Guaranteed Set Tested  
24-HOUR SERVICE

1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL94, SET of 4, 18/6.

DAF96, DF96, DK96, DL96, SET of 4 20/-.

1D5	7/-	DL92	5/11	PCP80	7/9
1R5	6/-	DL94	6/9	PCP82	7/6
1S5	4/6	DL96	6/9	PCL82	8/3
1T4	3/3	EB91	3/-	PCL83	11/6
3S4	5/11	EBC41	7/6	PCL84	9/9
3V4	6/9	EBF90	7/9	PL36	10/9
5Y4G	4/3	EBL21	12/6	PL81	8/6
6Y3GT	5/6	ECC40	14/6	PL82	6/6
5Z4C	7/3	ECC81	4/9	PL83	6/6
6AM6	2/9	ECC82	5/9	PL84	8/-
6K7G	1/9	ECC83	6/3	PY32	11/-
6K9G	4/9	ECC84	8/-	PY80	7/-
6Q7G	5/6	ECC85	7/6	PY81	7/-
6V6G	4/-	ECP80	7/3	PY82	6/-
6V8GT	6/6	ECP82	8/3	PY83	7/3
6X5GT	4/3	ECH21	12/6	U25	11/6
12K7GT	4/3	ECH42	7/9	UABC80	6/-
12B3GT	9/-	ECL80	6/9	UAF42	8/-
12Q7GT	4/6	EF40	12/3	UBC41	7/-
35Z6GT	8/-	EF41	7/6	UBF80	8/-
35Z4GT	5/9	EF80	4/3	UCB85	6/6
AZ31	8/9	EF85	4/6	UCH21	12/6
CL35	11/9	EF86	8/9	UCH42	7/6
DAC32	8/6	EF89	8/6	UCH81	7/-
DAF91	4/6	EF91	2/9	UCL82	9/3
DAF96	6/9	EL41	9/-	UCL83	13/-
DF33	8/6	EL84	6/3	UF41	6/6
DF91	3/3	EY51	7/3	UF85	6/6
DF96	6/9	EY88	7/3	UF89	6/9
DH77	6/-	EZ40	6/-	UL41	7/-
DK32	10/6	EZ41	6/9	UL84	6/6
DK33	9/-	EZ30	5/9	UY21	13/-
DK96	7/3	EZ61	6/-	UY41	5/6
DL33	7/3	MU14	6/-	UY85	6/3
DL35	7/6	PCC84	6/9	VP4B	8/6
		PCC89	9/-	Z77	2/9

Postage 6d. per valve extra. Any Parcel Insured Against Damage in Transit 6d. extra. Any C.O.D. Parcel 3/- extra. Office address, no callers.

**GERALD BERNARD**  
(Note new address—formerly of Leeds)  
83 OSBALDESTON ROAD,  
STOKE NEWINGTON, LONDON, N.16

## FIRST-CLASS RADIO COURSES . . .

GET A CERTIFICATE!

QUALIFY AT HOME—IN SPARE TIME

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure your professional qualification or learn Service and Theory. Let us show you how.

**'FREE GUIDE'**  
The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success-compelling qualifications as A.M.Brit.I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs' Exams, Gen. Cert. of Educ. London B.Sc. (Eng.), A.M.I.P.E. A.M.I.Mech.E., Draughtsmanship (all branches) etc., together with particulars of our remarkable Guarantee of

**SUCCESS OR NO FEE**

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career

**FOUNDED 1885—OVER 150,000 SUCCESSSES**

**NATIONAL INSTITUTE OF ENGINEERING**  
(Dept. 461), 148 HOLBORN LONDON, E.C.1

S. Africa: P.O. Box 8417, Jo'burg.  
Australia: P.O. Box 4570, Melbourne.

## Mullard MAINTENANCE MANUAL

This is a completely new and up-to-date edition including all current replacement types. It contains valuable new material and is an essential source of reference for every Service Engineer. 16/- Postage 1/-.

**RADIO CONTROL MANUAL** by E. L. Safford Jr., 25/-. Postage 1/-.

**BASIC PRINCIPLES OF ELECTRONICS & TELECOMMUNICATIONS** by M. D. Armitage, 22/6. Postage 1/3.

**RECORDS & GRAMOPHONE EQUIPMENT** by E. N. Bradley, 8/6. Postage 6d.

**TRANSISTORS. How to Test Them.** Gernsbach Lib. 16/-. Postage 9d.

**RADIO VALVE DATA** by "WW" 7th ed. 6/-. Postage 10d.

**GUIDE TO BROADCASTING STATIONS** 13th Ed. Compiled by "WW" 3/6. Postage 6d.

**LOUDSPEAKERS** by G. A. Briggs, 19/6. Postage 1/-.

**INTRODUCTION TO HI FI** by C. Brown, 21/-. Postage 1/-.

**COMPLETE CATALOGUE** 1/-.

## THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS of British and American Technical Books  
19-21 PRAED STREET LONDON, W.2  
Phone: PADdington 4185  
Open 6 days 9-6 p.m.

# RADIO BOOKS

**NEW PICTORIAL APPROACH TO LEARNING**  
**BASIC ELECTRICITY, 5 parts.**  
**BASIC ELECTRONICS, 4 parts.**  
 The Complete Set sent on payment of first instalment.  
**LEARN WHILE YOU PAY**  
**FOR ONLY 2/6 PER WEEK**  
 Write for FREE Illustrated Prospectus giving details of instalment plan.

**EXTRA EQUIPMENT FOR YOUR TAPE RECORDER.** Describes Mixer-amplifier, Monitor-amplifier, Programme meter etc. 6/6.

**PRACTICAL TRANSISTOR AUDIO AMPLIFIERS** for home constructor. 4/-  
**HI-FI TRANSISTOR FM TUNER** for home constructor. 4/-

**TRANSISTOR CIRCUITS** for Radio Co. 3/-  
**AMPLIFIED MODELS**, Howard Boys. 8/-  
**SUPER SENSITIVE TRANSISTORISED POCKET RADIO.** 4/-  
**INTERNATIONAL RADIO STATION LIST** 3/-

**TRANSISTOR CIRCUITS Nos. 1, 2, 3, 4, 3/-** each. Each book gives instruction for building ten different Transistor Units.  
**COIL DESIGN AND CONSTRUCTION MANUAL.** 5/6

**HI-FI TAPE RECORDER** 3/-  
**ONE VALVE RECEIVERS, TWO VALVE RECEIVERS, THREE VALVE RECEIVERS, FOUR VALVE RECEIVERS.** 1/9 each. Each book gives full comprehensive instructions, diagrams, etc.

**BOY'S BOOK OF CRYSTAL SETS, 12** different circuits fully illustrated. 3/-  
**HOW TO GET THE BEST OUT OF YOUR TAPE RECORDER.** By Guy 9/-  
**HIGH FIDELITY LOUDSPEAKER ENCLOSURES.** 5/6

**TRANSISTOR SUPERHET RECEIVERS** 3/-  
 Includes circuit diagrams of 50 different Receivers.

**40 CIRCUITS USING GERMANIUM DIODES.** 3/6  
**RADIO VALVE DATA** (Wireless World) 7th edition. 7/-  
**BRIMAR VALVE MANUAL No. 8.** 7/-

**GUIDE TO BROADCASTING STATIONS** (Wireless World) 12th edition. 4/-  
**MULLARD REFERENCE MANUAL OF TRANSISTOR CIRCUITS.** 13/6

**ELECTRONIC NOVELTIES.** Bradley 5/6  
**ELECTRONIC GADGETS.** Bradley 4/-  
**RADIO CONTROL OF MODELS.** By Sommerhoff 5/6

**SERVICING TRANSISTOR RECEIVERS.** Pettit. 6/6  
**USING AN OSCILLOSCOPE.** Easterling. 7/-

**BEGINNERS GUIDE TO RADIO.** Camm. New and Revised Edition. 8/6  
**DICTIONARY OF MATHEMATICAL DATA.** 2/3

**RADIO TEST EQUIPMENT MANUAL** 3/-  
**HI-FI STEREO GRAMOPHONE FOR CONSTRUCTOR.** Easterling 5/6

All above titles include postage.

SEND STAMP FOR LISTS

**SLRAY BOOK CO.**

30 HAYES HILL, HAYES, BROMLEY KENT. Tel. HURSTWAY 1818

# 2 METRES!

The thrills of 144 Mc/s can now be yours for only 99/6, complete kit! Tunable range 150-100 Mc/s, simplified construction, etc., write today for descriptive literature, also if a newcomer-beginner to Amateur Radio, ask for free copy of the world-famous "Globe-King" kits and receivers—stamp to cover postage costs appreciated. Write now to makers:

**JOHNSONS (Radio)**  
 8t. Martins Gate, Worcester

# PADGETTS RADIO STORE

40 MEADOW LANE, LEEDS 11  
 Phone: Cleckheaton 2866.

**SCR532, RX and TX.** Less valves and crystals, otherwise complete. 15/-, carriage 7/6. Receiver only 7/6, carriage 5/-.  
**Complete TV CHASSIS.** For spares less chassis, four for 10/-, carriage 5/-. 14in. chassis, four for 15/-, carriage 7/6.

**TV Tubes Returned.** 12 months guarantee. Old glass not required. 12, 14, 15, 16 and 17in. Any make all one price, £3.15.0. Carr. & Ins. 7/6.

**Perfect Reclaimed Tubes.** Six months guarantee. 12in. 17/-, 14in. Mullard only £1.10.0. carriage and insurance 7/6.

**P.M. Speakers.** All perfect, removed from TV sets. 3ohms coil. Goodman, Phillips, Rola, R. and A. etc. 5in. 6/6. 6in. 4/-, 6 x 4in. 5/-, 7 x 4 6/-, 8in. 6/-. Post 2/6 extra.

**Crystal Diodes.** Now only 6d. post 3d. 5/- doz. post free.

**NEW VALVES, Ex-units.** All post free. 6K7 2/-, 6X5 4/-, 6V6 3/-, 6V6GT 4/-, 6AQ5 3/6, 6C4 2/-, KT63 4/-, DH33 4/-, EF91 1/6, EL61 1/6, EF92 1/6, EF90 1/6, 8/- doz. VR150/30 4/-, IS4 2/-, 5U4 4/6, 8S4 1/6, 9001 9d., 5/- doz. DLS10 1/-, 6/- doz. VR50/VR92 6d., 4/6 doz.

Valves removed from TV sets. Tested on a Mullard Valve Tester, and are 100% as new. They carry a 3 months' unconditional guarantee.

EF90 1/6, 10/- per doz. EF90, Grade 2, 6d, 4/- per doz.

ECL80	4/6	6G6	2/8	U25	5/-
ECC82	5/-	6V6	2/-	U281	5/-
EL38	4/6	6LD20	5/-	U329	5/-
EY51	4/-	6SN7	2/9	KT36	5/-
EFB80	4/6	10C2	2/-	PL81	5/-
EB91	1/-	10F1	2/-	PY81	5/-
EF91	1/-	or 15/- doz.		PL82	5/-
EL81	1/-	10P30	5/-	PY30	5/-
6P25	4/-	10P13	5/-	PL38	5/-
6P28	5/-	20D1	3/-	PZ30	5/-
6F1	2/-	20P1	5/-	B36	4/6
6F13	2/-	20L1	5/-	N37	5/-
6F14	5/-	20L1	5/-	N37	5/-
6S87	2/-	185BT	8/6	L63	3/-

**TV Converters** less valves and knobs. Coils fitted 2 and 10. Ekco, Ultra, Marconi. ETC. 2/6, 2/- post.

**Cydon Converters.** Complete with valves and knobs. 25/-, post 2/-. Coils fitted 2 and 10.

**Tube Unit** with 3in. tube, valves and A.C. mains transformer, this will make a good scope. These units are not new but condition good. £2.5.0. Carriage 8/6.

**Small Speaker Transformer** ex TX chassis. 1/6. Post 1/3. Doz. lots 15/-, post free.

# 3-TRANSISTOR POCKET RADIO

WITH MINIATURE LOUDSPEAKER  
 ABSOLUTELY NO SOLDERING REQUIRED  
 UNIQUE DESIGN



Or the more powerful SAVOY SUPER 3. Three transistors and 2 diodes in a 5 stage reflex circuit. Dimensions as above. No aerial required.

ALL PARTS SOLD SEPARATELY  
 Battery 1/- extra. P. & P. 2/-.

**SAVOY ELECTRONICS LTD.**  
 15 Maiden Lane, Strand, London W.C.2.  
 (Back of Adelphi Theatre)

# The NEW 'SAVOY'

# 4-TRANSISTOR SELF-CONTAINED POCKET RADIO

WITH MOVING COIL SPEAKER

ABSOLUTELY NO SOLDERING NO DRILLING


4-Transistors and 2 diodes; 5-stage reflex circuit; push-pull output; size 5 1/2 x 3 x 1 1/2 in.; full medium wave; simple instructions and assembly tool provided.

**95/-** Plus battery 2/- extra  
 Postage and packing 3/-  
 All parts sold separately

**(PW) SAVOY ELECTRONICS LTD'**

15 Maiden Lane, Strand, London W.C.2  
 (Back of Adelphi Theatre)

# BBC - ITV - F.M. AERIALS

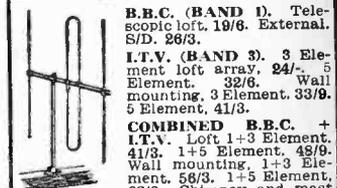

**B.B.C. (BAND D).** Telescopic lot, 19/6. External. S/D. 28/3.  
**I.T.V. (BAND 3).** 3 Element lot array, 24/-, 5 Element. 32/6. Wall mounting, 3 Element. 33/6. 5 Element, 41/3.  
**COMBINED B.B.C. + I.T.V.** Lot 1-3 Element, 41/3. 1+5 Element, 43/6. Wall mounting, 1+3 Element, 56/3. 1+5 Element, 63/9. Chimney and mast mounting units also available.

**F.M. (BAND 2).** Lot "H" 28/-, 3 Element lot, 52/6. S/D lot, 12/8. External S/D. 26/3. Gate channel when ordering. C.W.O. or C.O.D. P.P. 2/6. Coaxial cable, 8d. yd. Coaxial plugs, 1/3. Send 6d. stamps for illustrated lists.

**K.V.A. ELECTRONICS (Dept.P.W.)**  
 38, Godstone Road, Kenley, Surrey.

# JAMES H. MARTIN & CO.

Radio & Television Component Service

Finsthwaite, Newby Bridge

Ulverston, Lancs.

Lists available. Inland 3d. stamp only

Overseas, airmail 5/- refundable.

# BENSON'S BETTER BARGAINS

UNTIL FURTHER NOTICE THIS BUSINESS

WILL BE FOR

"CALLERS ONLY"

Operated from

SUPERADIO only


W. A. BENSON (P.W.), 138 Rathbone Road, Liverpool, 15. S.F.F. 0868. **Guitars: SUPERADIO** (Whitechapel), Ltd., 116 Whitechapel, Liverpool R.O.F 1130

# SENSATIONAL NEW 1961 DESIGNS—BY CONCORD

## LOW PRICES ★ PICTORIAL STEP-BY-STEP PLANS ★ EASY AS A.B.C.
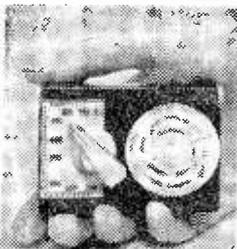
### THE NEW "LISBON" TRANSISTOR SET


This is a pocket 2-stage transistor set not much larger than a matchbox. Excellent clear reception covering all medium waves, works for months off a tiny 1½ or 3 volt battery costing only 3½d. Easy to build and an excellent introduction to transistor circuitry. Everything can be supplied down to the last nut and bolt incl. **SIMPLE PICTORIAL STEP-BY-STEP PLANS FOR ONLY 19/6**, plus post and packing 1/6. (C.O.D. 2/- extra). Parts sold separately, priced parts list 1/-.



### THE NEW "FLORIDA" VALVE RADIO

This sensational "FLORIDA" model is one of our most sensitive valve radios. It is a highly compact, self-contained miniature push button base, valve pocket radio at absolutely rock bottom building cost. Covers all medium waves with very latest circuitry bringing in stations from all over Europe without fuss. Size only 4½ x 2½ x 1½in. A fascinating pocket radio. We can supply all the parts including beautiful 2-tone case and **SIMPLE AS ABC PICTORIAL STEP-BY-STEP PLANS**, screws, wire, etc. Can be built for the exceptionally **LOW PRICE OF 27/6**, plus post and packing 1/6 (C.O.D. 2/- extra). Parts sold separately, priced parts list 1/-.


27/6

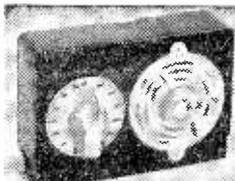

### OUR NEW 4 STAGE "MINUETTE"

Build this newly-designed "MINUETTE" 4-STAGE transistor set in very strong ready drilled **ULTRA-MODERN CASE**, size only 5 x 3½ x 1½in. Uses three transistors and diode and **SELF-CONTAINED LOUD SPEAKER**. Very sensitive, ideal for office, bedroom, holidays, etc. Months and months of listening off an 8d. battery. Can be built **FOR ONLY 39/6**, including **PROPER CASE**, miniature speaker, etc. **SIMPLE AS ABC PICTORIAL STEP-BY-STEP PLANS** etc., plus post and packing 1/6 (C.O.D. 2/- extra). Parts sold separately, priced parts list 1/-.

39/6

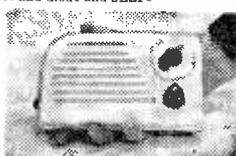

### THE NEW "SAN REMO" ONLY 32/6

This All Transistor Speaker Radio—The "San Remo"—covers all medium waves including "Home," "Light," etc. Reliable and lightweight—Slips easily into the Pocket or Handbag—size only 4½ x 2½ x 1½in. Works for Months off 8d. Battery! Ideal for holidays, Camping, Bedroom, etc. Anyone can assemble it in an hour or two with our simple-as-ABC PLANS! Complete set of parts including miniature speaker—everything—only 32/6, plus 2/6 P. & P. (C.O.D. 2/- extra.) Parts can be bought separately.



**CONCORD ELECTRONICS Dept. PW38**  
210, Church Road, Hove, Sussex

Cheques accepted. Cash on delivery 2/- extra. Please print name and address in block letters. Suppliers to Schools, Universities, Government and Research Establishments. Complete range of components and valves stocked. Regret no C.O.D. abroad. DEMONSTRATIONS DAILY AT WORKS.

### RADIO VALVE DATA

by W. W. new 7th Ed. 6/- Postage 9d.  
Mullard Maintenance Manual, new 2nd edition, 16/-, postage 1/-.  
Practical Transistor Audio Amplifiers, for Home Constructor, 3/6, postage 6d.  
Radio Amateurs Examination Manual by R.S.G.B., 5/-, postage 8d.  
Brimar Valve and Tele Tube Manual, new No. 9 edition, 6/-, postage 9d.  
Transistor Circuits for Radio Controlled Models by Howard Boys, 7/6, postage 6d.  
Surplus Radio Conversion Manuals, Volumes 1, 2 and 3, each 24/-, postage 1/- each  
Junction Transistors in Pulse Circuits by Neesoon, 28/6, postage 1/-.  
The Oscilloscope Book by Bradley, 5/-, postage 6d.

### UNIVERSAL BOOK CO.

12 Little Newport Street, London, W.C.2 (adjoining Lisie Street)

### TV TUBE RESTORER

EXTRA LIFE, EXTRA BRILLIANCE

PLUGS ON TO YOUR

TV TUBE

ANY SIZE

PATENTED

Important! State Make, Model No. Name and Address in Block Letters Please.

STANDARD MODEL .. 22/6  
DE LUXE MODEL .. 30/-  
Postage 2/6 either model.

**SINCLAIR ELECTRONICS** Dept. P.W.4  
18 Newport Court Charing X Rd. WC2  
Terms: C.W.O., C.O.D.

### RES/CAP. BRIDGE 38/-

p. & p. 2/6

Checks all types of resistors, condensers 6 RANGES

Built in 1 hour. Direct reading.

READY CALIBRATED

Stamp for details of this and other kits.

RADIO MAIL (DEPT. TP)

Raleigh Mews, Raleigh Street, Nottingham

### POCKET RADIO

ASTOUNDING RESULTS

Covers medium and long waves.

No aerial or earth required.

Very compact; personal earphone.

ALL PARTS 59/6, plus post 2/-.

Write for details (3d. stamp) before you buy elsewhere.

Red Spot Transistors 2/3, White Spots 2/3; Bargain set, 6 Ediswan Transistors (1-XA102, 2-XA101, 1-XB103, 2-XC101) and Diode for Superhet, 39/6. All parts "P.W." Pocket Superhet (Mullard transistors), £8.5.0; Sub-min. Electrolytics 2, 4, 8, 10, 16mfd, 2/-; 50, 100mfd, 2/9. M.C. Earpiece (used as speaker), 5/-; Balance Inserts (as earpiece or speaker), 3/6. Silicon Rectifier bargain 70 p.i.v. ½ amp., 3/3; Westalite Contact Rectifier 250 v., 60 mA, 7/6; Packard 250-0-250 v., 6 v. and 5 v., 15/-; Packard Bell Amplifiers, new 12/6; Garrard Portable Record Player, cabinet, battery turntable 45 r.p.m. and P.U.; takes trans. amplifier, £3.10.0, plus carr. 3/3. Real bargain. Limited quantity.

TERMS.—C.W.O. Post extra, excess refunded. Our Reflex Rx., best 2-transistor Receiver. Send 10d. stamps for notes. **MOORE'S EXPERIMENTAL SUPPLIES** 8 & 10 Granville Street, Sheffield 2 Tel.: 27461

## H.A.C. SHORT-WAVE EQUIPMENT AND SHORT-WAVE KITS

Famous for over 25 years for ... S.W. Receivers and Kits of Quality.

H.A.C. were the original suppliers of SHORT-WAVE RECEIVER KITS for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, Hams, etc.

Improved designs with Denco coils: One-valve Kit, Model "C", Price 25/-; Two-valve Kit, Model "B", Price 50/-; New Addition: Model "K", Price 50/-; Super sensitive "All Dry" Receiver. Special inc. price. Complete Kit, 77/-.

All kits complete with all components, accessories and full instructions. Before ordering one and inspect a demonstration receiver, or send for descriptive catalogue and order form.

### POST THIS COUPON NOW!

"H.A.C." SHORT-WAVE PRODUCTS


(Dept. TB), 44 Old Bond Street, London W.1

Please send me FREE and without obligation your 1962 literature.

NAME .....

ADDRESS .....

**FIDELITY "CORONET"**

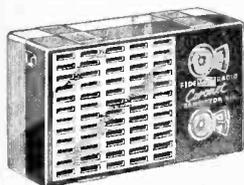

Inc. Battery

**£9.19.6** Reg. Post 2/6

**6-TRANSISTOR MEDIUM & LONG WAVE POCKET RADIO**

- Size 2½ x 4½ x 1½ in.
- Quality Push-Pull Speaker Output
- Guaranteed for 12 months.
- Phone and Tape Sockets
- Carrying Case

**ALL BRITISH DESIGN AND CONSTRUCTION**

Attractive Two-tone Moulded Cabinet. Very sensitive. Ideal present for any occasion. **Built and Ready to Use.**

**AVO-7 MULTIMETER**



Famous AVO Multimeter. Reconditioned and fully Guaranteed.

Supplied with batteries, test leads, instructions. At the **NEW LOW PRICE**

**£11.10.0**

Reg. Post 5/-

**FULLY GUARANTEED**



**CRYSTAL LAPEL MICROPHONE**  
Ideal for portable tape recording, etc.  
17/6 P.P. 1/-



**4000 Ohm Headphones**  
Lightweight very sensitive.  
12/6 P.P. 1/-

**RECORD PLAYER AMPLIFIER**

- 2-watt output.
- Ready built with Valves and 8 x 5 Speaker, Tone and Volume controls. Printed circuit.

**75/-** P.P. 2/-

Ideal for Portable Record Player.  
● UA8 4-speed Record Changer, ideal for above. £6.19.6. P.P. 3/6.

**STEREO AMPLIFIER**

**BARGAIN OFFER**

- 2 watts per channel.
- Full tone, balance and volume controls.
- Complete with sockets, dials, etc.

**97/6** P.P. 2/6.

Suitable Speakers, 9 x 5 in., 49/6 pair. UA14 Stereo Deck, £8.19.6. P.P. 3/6. **READY BUILT AND TESTED.**

**POCKET TESTER MODEL TE10**

Volt-Ohm-Milliammeter ★ Size 4½ x 3½ x 1½ in. Over 20 Scales

**10,000 ohms/volt**

Price, inclusive of Test Prods, Battery and instructions

£5.19.6 P.P. 1/6

**Top Quality Meter—Fully Guaranteed.**



Also Model 200H, 20,000 ohms/volt. size £6.19.6. P.P. 1/6. Same

**POCKET IRON**

★ Pocket Soldering Iron. 220/250 v. A.C./D.C. 30 watts, complete with mains plug, case, etc. Handle unscrews to cover element, enabling iron to be carried in pocket. 18/6. P.P. 1/-.

**Telephone Adaptor**

★ Ideal for recording telephone conversations. Supplied with screened cable. Fitted rubber sucker. 14/- P.P. 9d.




**CRYSTAL MICROPHONE FULLY GUARANTEED**

**ACOS 39-1.** Stick Microphone with screened cable and stand (list 5 gns.), 39/6, P.P. 1/6.

**ACOS 40 Desk Microphone** with screened cable and built-in stand (list 50/-), 19/6, P.P. 1/6.

**ACOS 45 Hand Microphone** with screened lead, very sensitive, 29/6, P.P. 1/6.

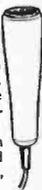**100 C Stick Microphone** with muting switch and screened cable, detachable desk stand, cord, etc. 39/6, P.P. 1/6.



**EXTENSION SPEAKER UNIT**

Tubular Unit. To give Big Set Performance from any Commercial Transistor Pocket Radio. Supplied with Plugs to fit most radios. Just plug in and hear the difference. 57/6 (incl. P. Tax)

**3-TRANSISTOR AND DIODE PERSONAL POCKET RADIO**

Quality Output on Personal Earphone. A simple to build local station radio with personal earphone output. Built-in Ferrite Aerial and Battery lasting 9 months. Size 4½ x 3 x 1½ in.



ALL PARTS 37/6 P.P. 1/6

**BABY SITTER**



**ALL TRANSISTOR BABY OR INVALID ALARM**

NOW HOUSED IN ATTRACTIVE GOLD HAMMER FINISH PORTABLE CABINET Battery operated, push-pull, 400mW output. Low impedance microphone enables unit to be used up to 200 yards. Output on quality speaker.


★ **GUARANTEED FOR 12 MONTHS** and 100% SAFE.

★ Microphone is placed within 6ft. of baby; twin flex is taken to amplifier unit and placed in any room required. **COMPLETELY BUILT & TESTED.**

£5.10.0 P.P. 2/6.

★ **Used All Night, Every Night.** Battery Life 3 to 4 months.

**Transistor 2-Way Intercomm**

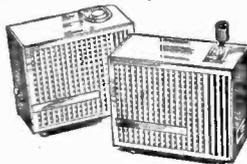

**10 Gns.**

Unit Sizes 3½ x 1½ x 3½ in. (Approx.)

- 2-way Talking.
  - Internal Buzzing System
  - Full Volume Control
  - Long Life Built-in Battery
- Built-in 2½ in. Speakers housed in attractive moulded cabinets. Supplied in presentation carton. Complete with Battery and 60 ft. wire.
- **Fully Guaranteed and Tested**

**SPECIAL OFFER**

COMPLETE SET OF PARTS FOR "P.W." CITIZEN AS PER DEC./JAN. EDITIONS OF "PRACTICAL WIRELESS."

**79/6** P.P. 1/6.

**TRANSISTORS**

We Stock Transistors FROM and Components for Every Purpose. Enquiries Welcomed **3/6**

**1st GRADE—FULLY GUARANTEED** SEND FOR LATEST PRICE LISTS



COMPLETE SET OF PARTS FOR "P.W." MINI-AMP AS PER NOVEMBER EDITION OF "PRACTICAL WIRELESS" **65/-** P.P. 1/6

★ Suitable Battery Record Player 79/6. P.P. 1/6.

**OUR SPECIALITIES** Transistors, Valves, Quartz, Crystals, Components at Competitive Prices. Let us quote for your circuit.

**Henry's Radio Ltd**

5 HARROW ROAD - LONDON W.2

Opposite Edgware Road Tube Station OPEN MON. to SAT 9.6. THURS. 1 o'clock Telephone PADdington 1008/9.

**PLEASE TURN TO BACK PAGE**

# Practical Wireless

## BLUEPRINT

## SERVICE

ALL OF these blueprints are drawn full-size and although the issues containing descriptions of these sets are now out of print, constructional details are available free with each blueprint except for the PW Monophonic Electronic Organ and the PW Roadfarer.

The Index letters which precede the Blueprint Number indicate the periodical in which the description appeared. Thus PW refers to PRACTICAL WIRELESS; AW to *Amateur Wireless* and WM to *Wireless Magazine*.

Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to

PRACTICAL WIRELESS, Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, London, W.C.2

### SPECIAL NOTE

THE following blueprints include some pre-war designs and are kept in circulation for those constructors who wish to make use of old components which they may have in their spares box. The majority of the components for these receivers are no longer stocked by retailers.

Title	Number	Price	Title	Number	Price
<b>CRYSTAL SETS</b>					
Junior Crystal Set . . . . .	PW94	2/-	A.C. Fury Four . . . . .	PW20	2/6
Dual-wave Crystal Diode . . . . .	PW95	2/6	Experimenter's Short Wave . . . . .	PW30a	2/6
<b>STRAIGHT SETS</b>					
<b>Battery Operated</b>					
Modern One-valver . . . . .	PW95	2/6	Midget Short Wave Two . . . . .	PW38a	2/6
All-dry Three . . . . .	PW97	3/6	Band-Spread Three (Battery) . . . . .	PW68	2/6
Modern Two-valver . . . . .	PW98	3/6	Crystal Receiver . . . . .	PW71	2/-
<b>SUPERHETS</b>					
A.C. Band-pass Three . . . . .	PW99	4/-	Signet Two (Battery) . . . . .	PW76	2/6
A.C. Coronet-4 . . . . .	PW100	4/-	Simple S.W. One-valver . . . . .	PW88	2/6
A.C./D.C. Coronet . . . . .	PW101	4/-	Pyramid One-valver . . . . .	PW93	2/6
The PW Pocket Superhet . . . . .	—	5/-	<hr/>		
<b>MISCELLANEOUS</b>					
The PW 3-speed Autogram . . . . .	—	8/-	BBC Special One-valver . . . . .	AW387	2/6
The PW Monophonic Electronic Organ . . . . .	—	8/-	Short-Wave Two . . . . .	AW429	2/6
<i>(No constructional details are available with this blueprint)</i>			Short-Wave World Beater . . . . .	AW436	3/6
The PW Roadfarer . . . . .	—	5/-	<hr/>		
<i>(No constructional details are available with this blueprint)</i>			Standard Four Valve S.W. . . . .	WM383	3/6
<b>TELEVISION</b>					
The PT Band III converter . . . . .	—	1/6	Enthusiast's Power Amplifier . . . . .	WM387	3/6
			Standard Four Valve . . . . .	WM391	3/6
			Listener's 5-Watt Amplifier . . . . .	WM392	3/6

### QUERY COUPON

This coupon is available until 5th January, 1962, and must accompany all queries in accordance with the notice on our "Letters to the Editor" page.

PRACTICAL WIRELESS, JANUARY, 1962

Published on the 7th of each month by GEORGE NEWNES, LIMITED, Tower House, Southampton Street, London, W.C.2, and printed in England by WATMOUGHS LIMITED, Idle, Bradford; and London. Sole Agents for Australia and New Zealand; GORDON & GOTCH (A/asia), Ltd., South Africa and Rhodesia; CENTRAL NEWS AGENCY, LTD. Subscription rate including postage for one year: Inland £1.9.0. Abroad £1.7.6 (Canada £1.5.0.). Registered at the General Post Office for the Canadian Magazine Post.

**ANNOUNCING ANOTHER COMPLETELY NEW 6-TRANSISTOR POCKET RADIO**

**THE "CAPRI" POCKET SIX**

TOTAL COST OF ALL PARTS  
**£7.10.0** P.P. 2/-



- 6-TRANSISTOR SUPERHET
- Push-Pull Output.
- 6 Mullard Transistors.
- Printed Circuit.
- Illustrated Building Instructions.
- Amazing Sensitivity.
- Housed in attractive two-tone moulded cabinet with mesh grill.

ALL OUR UNITS ARE COVERED BY AFTER SALES SERVICE AND GUARANTEE

● SEND FOR DETAILS OF COMPLETE RANGE ●

IDEAL PRESENTS FOR CHRISTMAS

Please turn to the next page for more items.

REALLY POCKET SIZE!  
Full Descriptive Leaflet and Details on Request.

● ALL PARTS SOLD SEPARATELY

● Size 4½ x 2½ x 1½ ins.

**"TRANSFIVE" PORTABLE MEDIUM AND LONG WAVE PORTABLE RADIO**



- 325mW Push-Pull Output on 5-inch Speaker.
- Pictorial Building Plans.
- Easy to Build Printed Circuit.
- Carded Components.
- 5 Mullard Transistors.

**AFTER SALES SERVICE and FULLY GUARANTEED**

TOTAL COST OF ALL PARTS  
**£6.19.6** P.P. 2/6  
NO EXTRAS TO BUY

Size 8½ x 6½ x 3½ in.

● Full coverage on Medium and Long wavebands. Excellent quality with full station separation. Car aerial socket.

**"QUINET" MEDIUM AND LONG WAVE POCKET LOUDSPEAKER RADIO**



- 250mW Push-Pull Output.
- Plainly marked Printed Circuit Board and Carded Components.
- 5 Mullard Transistors.
- Illustrated Plans.

A new printed circuit design fully tunable on both wavebands. Guaranteed reception of Continental and local stations including Luxembourg, anywhere with full station separation. Fitted Car Aerial and Earpiece Sockets.

Size 5½ x 3 x 1½ in.

TOTAL COST OF ALL PARTS  
**£5.10.0** P.P. 2/6  
NO EXTRAS TO BUY

VERY EASY TO BUILD AND USE. After Sales Service and Guarantee. All Parts Sold Separately FREE ON REQUEST ●

● BUILDING PLANS & PRICES FREE ON REQUEST ●

**RANGER 3 NO EXTERNAL AERIAL OR EARTH—3-TRANSISTOR and 2 DIODES**



Personal Pocket Radio with 5 stages giving clear reception on medium wave, amateur top band and shipping.

Size 4½ x 3 x 1½ in.


All Components

**79/6** P.P. 1/6  
Everything Supplied

● Easy to follow instructions with pictorial layout free on request.

● Reception of Radio Luxembourg guaranteed.

**3/4 WATT 4 TRANSISTOR AMPLIFIER**

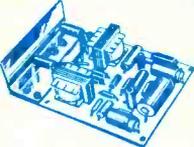

- 1 watt peak output.
- ± 3db 70c/s to 12 kc/s.
- Output to 3 ohm speaker
- 9 volt operated.

Built and Tested  
**69/6** P. & P. 1/6

Details on request

A printed circuit high gain amplifier size 4 x 2½ x 2½ in. using Mullard OC71/OC81D and 2-OC81 Transistors. Ideal for Inter-comm., Record Player, Tuner Amplifier or any application requiring a quality and reliable amplifier.

**Henry's Radio Ltd**

PADDINGTON 1008/9

5 HARROW ROAD, LONDON W2

Open Monday to Sat. 9-6, Thurs. 1 o'clock

Send 1/- Stamp For New

Illustrated Price Lists

PLEASE TURN PAGE

**CONTESSA 6 TRANSISTOR MEDIUM AND LONG WAVE SUPERHET**



**COMBINED PORTABLE AND CAR RADIO**

- High "Q" Internal Ferrite Aerial.
- Car Radio Adaptation and AVC.
- "Hi-Fi" Quality Speaker.
- Slow Motion Fingercip Tuning with Station names clearly marked.
- 425mW Push-Pull Output.
- 6 "Top-Grade" Ediswan Transistors.
- New Type Printed Circuit with all components marked.
- Full Medium and Long Wave Tuning.

TOTAL COST OF ALL PARTS  
**£10.19.6** P.P. 3/6  
● NO EXTRAS TO BUY ●

● Attractive Rexine Covered Cabinet Red/White or Blue/White. 10 x 7½ x 3½ in.

UNBEATABLE IN PERFORMANCE AND APPEARANCE

Employs the latest techniques. Double tuned IF's, AVC and first-grade components are standard features. Excellent tone, sensitivity and selectivity on both wavebands guaranteed.

Descriptive Leaflet on request.

**RANGER 2**

All Parts  
**59/6**  
P.P. 1/6



**PERSONAL POCKET RADIO**

● Two Transistor Two Diode fully tunable over medium waves. Good reception of Radio Luxembourg. Size 4½ x 3 x 1½ in. No extras to buy

● PICTORIAL PLANS AND DETAILS FREE ON REQUEST

**TRANSISTOR PORTABLE TAPE RECORDER**

Size  
6 x 8½ x 2½ in.

**12**  
Gns.



- Over 1 hour play/record.
- Quality Re-production on Built-in Speaker.
- Fast Rewind—Full Volume Control.

SUPPLIED COMPLETE WITH MICROPHONE, BATTERIES, PERSONAL PHONE AND TAPE.

**1 WATT TRANSISTOR AMPLIFIER**

● EMI 4-Transistor Amplifier with speaker, tone and volume controls. Ready assembled for use with crystal pick-ups. 7½ x 9 volt operated. 89/6 P.P. 1/6.

**BATTERY RECORD PLAYER**

● 6—7½ volt Garrard Turntable with crystal pick-up. Plays 45 r.p.m. Ideal for above amplifier. 79/6 P.P. 1/6.

710