

AUGUST  
1963

# *Practical* 2/- **WIRELESS**



**NEW**  
**Power Transistor**  
**DESIGN**

THE *Kenilworth* PORTABLE PA AMPLIFIER



**SOLDERING INSTRUMENTS AND EQUIPMENT**

**DESIGNED FOR THE AMATEUR'S RADIO STATION**

**ILLUSTRATED**

List No. 70.  $\frac{1}{8}$ " BIT IN PROTECTIVE SHIELD  
List No. 68



APPLY DIRECT FOR CATALOGUE TO  
Sales and Service Dept.

**ADCOLA PRODUCTS LTD**


**ADCOLA HOUSE GAUDEN ROAD,**

**LONDON, S.W.4**

Telephones  
MACaulay 4272 & 3101

Telegrams  
SOLJOINT LONDON SW4

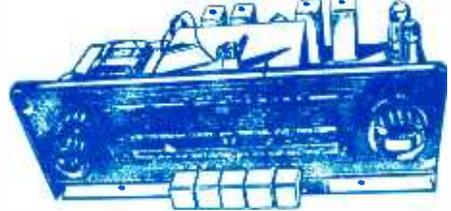**BRAND NEW AM/FM (V.H.F.) RADIOGRAM CHASSIS AT £12.12.0 (Carriage Paid)**




A.C. ONLY. Chassis size 15 x 6 $\frac{1}{2}$  x 3 $\frac{1}{2}$ in. high. New manufacture. Dial 14 $\frac{1}{2}$  x 4in. in 2 colours, predominantly gold.  
Pick-up Ext. Speaker. Ae. E., and Dipole Sockets. Five push buttons—OFF, L.W., M.W., F.M. and Gram. Aligned and tested. O.P. Transformer. Tone Control. 1000-1900 M.C.: 200-500 M.C.: 88-98 Mc/a. Valves E280 rect.; ECH81, EF89, EABC80, EL84, ECC85. Negative feed-back circuit. Speaker and Cabinet to fit chassis (table model). 47/8 (post 5/-).  
9 x 6in. ELLIPTICAL SPEAKER. 20/-, to purchasers of this chassis.  
TERMS: (Chassis) £3.10.0 down and 5 monthly payments of £2.  
Cheap Room Dipole for V.H.F., 12/6. Feeder 6d. yd. Circuit diagram 2/6.

**THE "VERONA" SPEAKER CABINET ONLY £5.9.6. (carr. 7/6)**

Beautifully finished in semi-matt medium wainut. 23 $\frac{1}{2}$ in. high x 11 $\frac{1}{2}$ in. x 13 $\frac{1}{2}$ in. Takes 8in. speaker with room below (11 $\frac{1}{2}$  x 10in.) for amplifier, if desired, (our 5 w. amplifier price 60/-, post paid, suite).  
Speakers from 18/6 to £4. SPECIAL OFFER of 18/6 Speaker, Cabinet and Amplifier for only £9 carriage paid.




**PUSH-PULL AMPLIFIER £5.5.0**

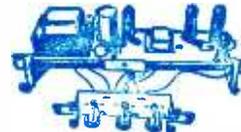

(5/- Carr.)  
Brand new 200/240 A.C. mains. Bass, treble and vol. controls. With valves E280, ECC83 and 2-EL84 giving full 8 w. Chassis 12 x 3 $\frac{1}{2}$  x 3 $\frac{1}{2}$ in. With o.p. trans. for 3-ohm speaker. Front panel (normally screwed to chassis) may be removed and used as "flying panel". Stereo version 2 x 4 w., same price. Fixed panel. Tone & Vol. Controls.

**TAPE RECORDER AMPLIFIER**

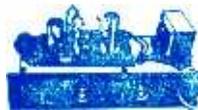

Type TR3. Fully built, high gain, low noise, printed circuit. Attractive grey and gold front panel. 13 x 1 $\frac{1}{2}$ in. Height 5 $\frac{1}{2}$ in. overall. Front to back 5 $\frac{1}{2}$ in. Vol. and on-off tone. Mike, radio and ext. speaker jacks. Valves magic eye, ECC83, ECL82, E280. Mains trans. Ready to bolt to B.S.R. Deck. Complete with switch wafer wired. Our Price ONLY £6.15.0 (6/- Packing and Carr.). Also available for Collard Deck at 5/- extra.

**6-TRANSISTOR KITS AND SETS**

All brand new parts. Rexine and Vynair Cabinets. Different colours. All holes drilled in printed circuit boards. Full M.W. and L.W. coverage. Car aerial socket. Alignment service, 17/6, inc. return post. All parts supplied separately. built in 2/3 hours. 600 mW. output. Booklet 2/6, refunded on purchase of kit.

**THE "SCALA"**



"Scala" Kit £4.19.6. (Post 3/-). Size 8 $\frac{1}{2}$  x 2 x 5 $\frac{1}{2}$ in. high and 3 $\frac{1}{2}$ in. speaker; or fully built £7.10.6.

**THE "MILAN"**



"Milan" Kit £5.17.6. (Post 3/6). Size 9 x 3 $\frac{1}{2}$  x 7 $\frac{1}{2}$ in., 8 x 2 $\frac{1}{2}$ in. speaker.

**ALL ITEMS ARE NEW AND FULLY BUILT UNLESS OTHERWISE STATED. TESTED BEFORE DESPATCH.**

Terms Available on Items over £5. Send 6d. (stamps will do) for 20-page illustrated catalogue. Delivery by return C.O.D. 2/- extra.

**ALL ITEMS GUARANTEED 12 MONTHS VALVES 3 MONTHS**

**GLADSTONE RADIO**

**"SCALA", CAMP RD., FARNBOROUGH, Hants.**

Farnborough 3371

FARNBOROUGH CLOSED SATS.

# R.S.T. VALVE MAIL ORDER CO.

Tel: MITcham 6202  
Open Daily to Callers

## 211a STREATHAM ROAD, MITCHAM, SURREY.

All Valves Brand New and Fully Guaranteed — Obsolete valves a speciality.  
Quotations given on any type not listed. Send S.A.E.

### Special 24 Hour Express Mail Order Service

AC2/PEN 12/6	ECC85 12/6	EY83 12/6	PCC85 9/6	TDD4 12/6	UU6 17/6	6A8GT 13/6	6P25 10/6	12Q7GT 6/6
AC2/PEN DD 21/-	ECC83 12/6	EY86 7/-	PCC88 12/6	TDD13C 17/6	UU8 15/-	6AC7 6/-	6P28 12/6	12SA7 8/6
AC/TP 29/-	ECC91 3/-	EY91 3/-	PCC89 8/6	TH41 20/-	UU9 7/6	6AK5 5/-	6Q7 9/6	12S17 8/6
AC/VP1-5-7	ECF80 7/6	EZ35 6/-	PCF80 9/-	TY86F 12/6	UY1N 12/6	6AL5 14/-	6Q7G 6/6	12SK7 6/6
AZ1 15/-	ECF82 8/6	EZ40 7/-	PCF82 7/-	U10 9/-	UY21 15/6	6AM5 5/-	6Q7GT 8/6	12SL7 8/6
AZ31 9/6	ECH21 21/-	EZ80 6/-	PCF84 12/6	U12 9/-	UY41 7/6	6AM6 4/-	6SA7 7/-	12SN7 10/-
B35 9/-	ECH35 10/-	EZ81 6/-	PCF86 12/6	U14 9/-	UY85 6/6	6AQ5 6/6	6SC7 8/6	12SQ7 12/-
C1C 10/-	ECH83 8/6	EZ90 5/-	PCL82 9/-	U19 11/-	VMS4B 12/6	6AT6 6/-	6SF5 10/-	14H7 10/-
CCH35 20/-	ECH88 8/6	E1148 2/-	PCL83 10/-	U22 8/-	VP4 15/-	6AU6 9/-	6SG7 7/-	14K7 10/-
CL33 12/6	ECL80 7/6	FC2 15/-	PCL84 7/-	U24 21/-	VP4A 15/-	6B8G 3/-	6SH7 6/-	14S7 10/-
CY1 15/-	ECL81 10/-	FC2A 15/-	PCL85 5/-	U25 11/-	VP4B 15/-	6BA6 6/-	6S17 6/6	19AQ5 8/6
CY31 10/-	ECL82 9/6	FW4/500 9/-	PCL86 12/6	U26 10/-	VR150/307 7/-	6BE6 6/-	6SK7 5/6	19BQ6G 15/-
D77 4/-	ECL83 10/6	FW4/800 9/-	PEN44 17/6	U31 9/-	VR150/307 7/-	6BG6G 15/-	6SL7GT 6/-	20D1 10/-
DAC32 9/6	ECL86 9/6	GZ30 10/6	PEN44D 22/6	U35 17/6	W61 11/-	6B16 6/-	6SN7GT 5/6	20D2 21/-
DAF91 5/6	EF6 21/-	GZ32 10/6	PEN4VA 17/6	U37 17/6	W76 5/6	6B07A 12/6	6USG 8/6	20F2 17/6
DAF96 7/6	EF9 21/-	GZ33 19/3	PEN36C 20/-	U47 11/-	W77 4/-	6BR7 10/6	6U4GT 10/-	20L1 22/6
DCC00 12/6	EF22 14/-	GZ34 13/6	PEN45 10/6	U50 7/-	W81 6/-	6BS7 12/6	6V6G 4/6	20P1 15/-
DF33 9/6	EF36 4/-	GZ37 19/3	PEN45DD 25/-	U52 4/-	W8M 6/-	6BV6 8/-	6V6GT 8/-	20P2 24/-
DF91 7/-	EF37A 8/-	HABCB010 10/-	PEN46 20/-	U76 7/6	X41 22/6	6BV7 8/-	6X4 4/6	20P5 20/-
DF92 7/-	EF39 4/-	HL41 8/-	PEN45DD 25/-	U78 4/6	X61M 10/-	6C4 3/6	6X5G 6/-	25A6 8/6
DF96 7/6	EF40 15/-	HL41DD 8/6	PEN46 20/-	U145 10/6	X65 12/6	6C5GT 8/-	6X5GT 8/6	25L6 8/6
DH63 6/6	EF41 8/-	HL92 8/6	PEN45DD 20/-	U191 13/6	X76 12/6	6C6 6/6	6X6GT 8/6	25L7 8/6
DH77 7/-	EF42 10/6	HL92 8/6	PEN45DD 20/-	U251 15/-	X76M 12/6	6C9 12/6	6Y3L2 10/-	25V5 8/6
DK32 11/-	EF50A 3/6	HL92 8/6	PEN45DD 20/-	U281 15/-	X78 26/-	6CD6G 27/6	7B5 12/6	25Y5G 8/6
DK91 6/6	EF50E 3/6	HN309 25/-	PENDD4020 20/-	U282 19/6	X79 40/6	6CH6 10/-	7B6 10/-	25Z4 7/6
DK92 7/6	EF80 2/-	IW4/350 10/-	PL33 15/-	U301 17/-	X81 10/-	6CW4 16/-	7B7 8/6	25Z5 8/6
DK96 7/6	EF85 5/-	IW4/500 10/-	PL36 12/6	U329 15/-	Y61 10/-	6D2 4/6	7C5 8/6	25Z6 8/6
DL33 0/6	EF86 8/-	KT33C 8/-	PL38 12/6	U403 10/-	Y63 10/-	6D6 5/6	7C6 8/6	27SU 19/6
DL35 10/-	EF89 9/-	KT36 17/6	PL38 21/-	U404 10/-	Z66 10/-	6E5 10/-	7D5 15/-	30C1 9/6
DL91 8/6	EF91 4/-	KT66 9/6	PL81 9/-	U801 19/6	Z77 4/-	6F1 10/6	7D8 15/-	30C15 12/6
DL92 6/6	EF92 4/-	KT66 15/-	PL82 8/6	UABC80 7/-	Z152 5/6	6F6 6/9	7H7 6/-	30F5 10/-
DL93 7/-	EF95 5/-	KT76 10/-	PL83 7/6	UB41 7/6	OZ4 5/6	6F12 4/-	7H7 6/-	30FL1 10/6
DL94 7/6	EF98 10/6	KTW61 8/-	PL84 0/6	UBC41 8/6	IA7 11/-	6F13 10/-	7R7 10/-	30L1 8/6
DL96 7/6	EF183 10/6	LN3 5/-	PL820 13/6	UBC81 10/-	IC5 10/-	6F14 10/-	7S7 10/-	30L15 11/-
EA50 2/6	EF184 10/6	LN152 8/-	PBM24M 18/-	UBF80 8/6	ID5 8/6	6F15 12/6	7Y4 6/6	30P4 18/-
EABCB0 5/-	EK32 8/6	LN309 11/6	PX4 25/-	UBF89 7/6	ID6 10/-	6F19 12/6	8D3 4/-	30P12 10/6
EAC91 4/-	EL3 21/6	LZ319 12/6	PX25 25/-	UBL21 20/-	IH5 9/6	6F23 10/6	9BW6 12/6	30P16 9/6
EAF42 9/6	EL32 4/6	MKT4 17/6	PY31 12/6	UCB84 11/6	IL4 5/6	6F25 16/6	10C1 12/6	30P19 17/6
EB34 2/6	EL33 10/6	MS4B 17/6	PY32 15/6	UCC85 7/6	IN5 9/6	6F26 13/6	10C2 17/6	30PL1 11/6
EB41 5/-	EL34 14/-	MVS/PEN 17/6	PY33 10/6	UCF80 12/6	IR5 6/-	6F33 5/6	10F1 10/-	30PL13 11/6
EB91 4/-	EL35 10/-	MVS/PEN 17/6	PY80 7/6	UCH21 20/-	IS4 8/-	6H6 2/-	10F9 12/6	30PL14 16/6
EBC3 21/-	EL37 17/6	MVS/PEN 17/6	PY81 7/6	UCH42 8/6	IS5 5/6	6I5 5/6	10LD11 15/-	35A5 15/-
EBC33 4/6	EL38 17/6	MU14 9/-	PY82 6/9	UCL82 9/6	IT4 4/-	6I5GT 5/6	10PI3 15/-	35L6GT 8/6
EBC41 8/6	EL41 9/6	MX40 15/-	PY83 8/-	UCL83 12/6	IUS 5/9	6I7 7/6	10PI4 19/-	35W4 7/6
EBF80 8/-	EL42 5/6	N18 8/-	PY88 10/-	UF41 7/6	2P 22/6	6I7G 5/-	11D5 23/6	35Z3 15/-
EBF83 8/-	EL84 6/9	N37 14/-	PY800 10/-	UF42 7/6	3A4 5/-	6K7 7/6	12A8H 9/-	35Z4 7/6
EBF89 8/-	EL85 10/-	N78 22/6	PZ30 15/-	UF80 7/-	3A5 10/-	6K7G 2/-	12AT7 5/-	42 12/6
EBL1 21/-	EL90 8/6	N108 15/6	QS95/10 10/-	UF85 7/6	3Q5 9/-	6K7GT 7/6	12AU6 17/6	50C5 10/-
ECC35 8/-	EL95 10/6	N339 18/-	QS150/15 10/-	UF86 12/6	3V4 7/-	6K8 9/6	12AU7 5/-	50CD6G 30/-
ECC40 15/-	EM30 2/6	N369 10/6	R2 10/-	UF89 6/6	SU4 4/-	6K8GT 9/6	12BA6 7/6	50L6 8/6
ECC81 5/-	EM81 2/6	OD3 5/6	R16 17/6	UL41 8/-	5V4G 7/9	6K25 17/6	12BE6 7/6	75 7/6
ECC82 5/-	EM84 9/6	OZ2 5/6	R19 16/-	UL44 20/-	5Y3G 5/6	6L1 10/-	12BH7 10/-	78 9/6
ECC83 7/-	EM85 10/6	P2 10/-	R20 16/-	UL46 14/6	5Y3GT 6/6	6L6 7/6	12C8 8/6	80 8/6
ECC84 8/6	EY81 8/6	PBCB0 13/-	SP41 3/6	UL84 6/6	5Z4G 9/6	6L7 10/-	12IGT 4/6	85A2 12/6
		PCC84 8/6	SP61 3/6	UL85 7/6	5Z4GT 12/6	6L8 10/-	12JGT 8/6	185BT 30/-
			T41 15/-	UR18 10/6	6A7 9/-	6L9 15/-	12KGT 5/-	807A 6/6
				UR1C 15/-	6A8G 8/6	6N7GT 9/6	12K8GT 10/-	807B 6/-

## COMPLETE VALVE LIST FREE WITH ORDER

### METAL RECTIFIERS

RM1 7/6	14A86 23/-	16RD 2-2-8-1	12/-	(FC142)
RM2 8/-	14A97 26/-	16RE 2-1-8-1	10/-	
RM3 10/-	14A100 28/-	18RA 1-1-8-1	5/-	
RM4 17/6	14RA 1-2-8-2	18RA 1-1-16-1	7/-	(FC116)
RM5 19/6	14RA 1-2-8-3	18RA 2N-1-8-1	12/-	(FC31)
	16RC 1-1-16-1	18RD 2-2-8-1	16/-	(FC124)

### BRAND NEW TRANSISTORS

OC44 6/-	OC74 8/-	OC81D 8/-
OC45 7/-	OC75 6/-	OC82 8/-
OC71 5/-	OC77 6/-	OC82D 6/-
OC72 8/-	OC81 6/-	

### SILICON RECTIFIERS

400 volts 350 mA ... .. 8/- each


### SETS OF VALVES

1R5, 1S5, 1T4, 354, 3V4 ... .. Set of 4, 19/-  
 DAF91, DF91, DK91, DL92, DL94 ... .. Set of 4, 19/-  
 DAF96, DF96, DK96, DL96 ... .. Set of 4, 26/6

TERMS OF BUSINESS C.W.O. or C.O.D.  
 4/2 PACKING CHARGE ON ALL C.O.D.  
 ORDERS. POSTAGE 6d. per VALVE

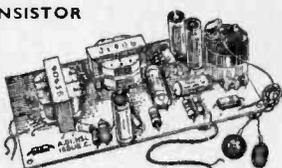**HIGH GAIN 4-TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT Type TA1**


● Peak output in excess of 15 watts. ● All standard British components. ● Built on printed circuit panel, size 6 x 3in. ● Generous size Driver and Output Transformers. ● Output transformer tapped for 9 ohm and 15 ohm speakers. ● Transistors (GRT114 or 81 Mullard OC81D and matched pair of OC81 o/p). ● 9 volt operation. ● Everything supplied, wire, battery clips, solder, etc. ● Comprehensive easy to follow instructions and circuit diagram 1/6 (Free with Kit). All parts sold separately. P. & P. 2/6.



**SPECIAL PRICE 45/- P. & P. 2/6.**

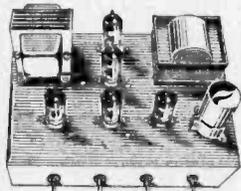**10/14 WATT HI-FI AMPLIFIER KIT**

A stylishly finished hi-fi amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and E280 rectifier. Simple instruction booklet 1/6. (Free with parts). All parts sold separately.



**ONLY £6.19.6 P. & P. 6/6.**

**AMPLIFIER ON PRINTED CIRCUIT BOARD**

Two valve. U785, U184 O.P. frame, use with 50 volt tap off motor. 39/6. P.P. 2/6 on above. Dropper res. for filaments if required. 2/6.

**B.S.R. AUTO UNITS** 150 v. Suitable for use with above. (Slightly soiled.) £4.0.0.

**LARGE CABINET** Suitable for above two items. Complete with 3 ohm speaker. £3.9.6. Carr. 5/-.

**Superior CABINET** Similar to above to take 8 x 5in. speaker, with motor board, will accommodate BSR UA14 or UA18. £3.9.6. Carr. 5/6. Speaker 16/- extra. P. & P. 1/6 extra.

**UNREPEATABLE OFFER! BRAND NEW 8 x 5 3 OHM SPEAKERS**  
By well known maker 10/6 each.  
P. & P. 1/6 per speaker  
A pair of these are ideal for Stereo

**BRAND NEW 3 OHM LOUDSPEAKERS**

- 2 1/2in. 12/6; 5in. 12/6; 6 1/2in. 15/-;
- 8in. 21/-; 10in. 25/-; 12in. 27/6.
- Goodmans 5in. tweeter .. 10/6
- E.M.I. 2 1/2in. tweeter .. 10/6
- E.M.I. 10in. x 6in. ceramic magnet .. 25/-
- E.M.I. 1 1/2in. x 8 1/2in. high flux 32/6
- Kola Celestion approx. 9in. x 6in. middle register speaker 10/6
- Also 15 ohm 12 inch, 30/-
- P. & P. up to 6in. 1/6; over 6in. 2/6 per speaker.

**RECORDING TAPE**

P.V.C. base, full frequency L.P. tape. 7in. 1800ft. (normally 50/-) 27/6; 6in., 1,200 ft. (normally 36/-) 18/6; 5in., 900ft. (normally 28/-) 15/-; P. & P. 1/- per spool. Ideal for 2 or 4 track recorder.

**TAPE DECKS**  
**COLLARO STUDIO DECK** £10.10.0, plus 5/6 carr. and insa. B.S.R. MONARDECK (Single speed) 31in. per sec., simple control, uses 5 1/2in. spools, £6.15.0 plus 5/6 carr. and insa. (Tapes extra on both).

**SPECIAL BARGAIN OFFERS!**

- MAINS TRANSFORMERS.** Tapped Primary. 1/2 wave or Bridge Rectifier. Secondary 250 v. at 75 mA 6.3 volts at 2 amps. 10/6 each. P. & P. 3/-.
- TWO GANG .0005 TUNING CONDENSER.** Geared precision reduction drive. Size 2 1/2in. x 2 1/2in. Brand new and unused. 3/6 each. P. & P. 1/-.
- MAINS TRANSFORMER.** Impregnated and fully shrouded. Size 4 1/2 x 3 1/2 x 2 1/2in. Weight 6 lbs. Tapped primary 205, 225, 245v. Electrostatic screen. Output 360-0-360 v. at 120 mA D.C. plus 1050 v. half wave at 3 mA D.C. 6.3 v. at 3.5 amps, centre tapped 5 v. at 2 1/2 amps and 6.3 v. at .5 amps. PRICE ONLY 21/- each. P. & P. 0/-.
- CARBON MIKE INSERTS.** Brand new, 2 1/2in. dia., 3/6. P. & P. 9d.
- ELECTROSTATIC H.F. TWEETERS.** Type L.S.H. 75. Size 3 x 3in., 2/6 each, plus 5d. P. & P.
- MIDRANGE 2/GANG CONDENSERS.** Capacity 195 and 100 pF. Polystyrene case with built-in trimmers. Size 1 x 1 1/2in. Not used but removed from P/O Boards. Two for 9/- plus 1/- P. & P.
- ACOS CRYSTAL MIKES.** High imp. For desk or hand use. High sensitivity. 18/6. P. & P. 1/6.
- TSL CRYSTAL STICK MIKE.** Listed at 45/-. Our price 18/6. P. & P. 1/6.
- TRANSISTOR DRIVER and O/P TRANSFORMERS.** (Tapped 3 ohms and 15 ohms output), plus 4 suitable Transistors giving approx. 1 watt output. 30/-. P. & P. 2/-.
- 3 PUSH-BUTTON TRANSISTOR SWITCH D.P.—D.T.** Each switch 6/6 and 1/- P. & P.


**FURTHER HUGE PURCHASE**

**TELEFUNKEN HI-FI STEREO AMPLIFIER.** Model 892 with BALANCE CONTROL 110/250 v. A.C. input. 5 watt undistorted output (10 watts nominal). Size 12 x 9 x 2in. Weight 9 lb. Complete with spec. and instructions. Now only 25.19.6 Carr. 7/-.

**SPECIAL PURCHASE! TURRET TUNERS**

by famous-maker Brand new and unused. Complete with PCC34 and PCC80 valves, 34-38 Mc/s I.F. Hicuts for Channels 1 to 5 and 8 and 9. Circuit diagram supplied. ONLY 25/- each. P.P. 2/6.

**F.M. TUNER HEAD**

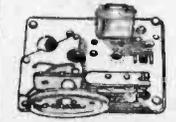


A permeability tuned tuner head by a famous maker, supplied without valve (ECC85) and drum and spindle. 18/6, plus 1/9 P. & P. Valve 8/6 extra. Drum and spindle 3/6 extra.

**GÖRLER F.M. TUNER HEADS**

10.7 Mc/s I.F., 15/-, plus 1/9 P. & P. (ECC85 valve. 8/6 extra.)

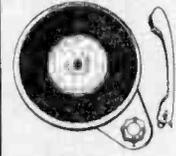**E.M.I. 4-speed Player and P.U.**

FURTHER HUGE PURCHASE enables us to offer these 67/6 P. & P. at 4/8.



Heavy 8 1/2in. metal turntable. Low flutter performance 200/250V shaded motor with tap at 45 V for amplifier valve filament if required. Turnover LP7/8 head.

**RECORD PLAYER AMPLIFIER**

2 valve (E280, EC182). A.C. mains. 3 watts output, ready built, tested and complete with valves and output transformer. Size 7in. w. x 2 1/2in. d. x 5 1/2in. h. 65/-, P. & P. 3/-. Suitable speakers: 6in. 15/- P. & P. 1/6. 10 x 6in. 25/-, P. & P. 1/6.

**4-SPEED PLAYER UNIT BARGAINS**


**SINGLE PLAYERS**  
TU12 £3.10.0. Carr. 3/6.  
**AUTO CHANGERS**  
B.S.R. UA14. £6.2.8.  
Latest B.S.R. UA16. £7.2.8.  
Latest Garrard 'Auto-Slim' £5.17.0. Carr. 5/- on each.

**SPEAKER & CABINET FABRICS**

Oatmeal fabric for speaker or cabinet or Red rexine for cabinet 5 1/2in. wide 13/6 per yard length. (Minimum order). P. & P. 1/6.

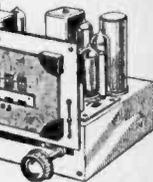**HARVERSON'S F.M. TUNER Mk.1**

● F.M. tuning head by famous-maker. ● Guaranteed non-drift. ● Permeability tuning. ● Frequency coverage 88-100 Mc/s. ● O.A.M. balanced diode output. ● Two I.F. stages and discriminator. ● Attractive maroon and gold dial (7 x 3in. glass). ● Self powered using a good quality mains transformer and valve rectifier. ● Valves used ECC85, two EF86s, and E280 (rectifier). ● Fully drilled chassis. ● Size of completed tuner 8 x 6 x 5 1/2in. ● All parts sold separately. Set of parts if purchased at one time 25.19.6, plus 8/6 P.P. and insa. Circuit diagram and instructions 1/6 post free. Mark II Version as above but complete with magic eye, front panel and brackets, £6.12.6. P. & P. 8/6.



Mark III Version as Mark I but with output stage (ECL82) and tone control. £7.7.0. P. & P. 8/6. Handsome Metal Cabinets. Choice of Gray, Black or Green. To fit Mark I, 25/-, P. & P. 2/6. To fit Mark II, 17/6, P. & P. 2/6.

**6 TRANSISTOR AND DIODE SUPERHET**

A first-class 2 waveband transistor superhet. ● Printed circuit panel (size 8 1/2 x 2 1/2in.) ● 3 pre-aligned I.F. transformers. ● High-gain Ferrite rod aerial. ● All First-grade transistors. ● Car aerial winding. ● Push-pull output. ● All parts supplied with simple instructions. All parts sold separately. Set of parts if purchased at one time.



**ONLY £4.5.0 P. & P. 2/6**

**35 OHM SPEAKERS**

Suitable for use with above. 2in. Goodmans. Ideal replacement for most pocket portables 8/6; 2 1/2in. 10/6; 3 1/2in. 12/6; 5in. 17/6; 7 x 4in. 21/-; P. & P. 1/6 per speaker.



**Portable CABINET**

Size approx. 9 1/2 x 6 1/2 x 3 1/2in. Suitable for above using 3 1/2in. speaker. 25/-, P. & P. 2/6.



**COIL AND TRANSFORMER SET FOR TRANSISTOR SUPERHET**

3 I.F. transformers, one oscillator coil, one driver transformer and wound Ferrite aerial (med., long and aerial coupling), 25/6 complete post 1/6 and volume control. On/off control. 8/6, post 9d. Circuit diagram 1/6 extra.

**QUALITY RECORD PLAYER AMPLIFIER**

A top-quality record player amplifier. This amplifier (which is used in a 25 gm record player) employs ECC83, EL84, E280 valves. Bass, treble and volume control. On/off control.

**PRICE 69/6, P. & P. 3/6**  
DITTO. Mounted on board with output transformer and 6in. speaker.  
Complete at 89/6, P. & P. 4/6.

**TRANSISTORS**

- GAT 15 (Matched Pair) 15/-
  - OC71 .. .. 5/- P.XA101 .. 6/6
  - OC72 .. .. 6/- XA102 .. 6/6
  - OC73 .. .. 8/- V15/100 .. 12/6
  - OC74 .. .. 8/- V15/100 .. 12/6
- Set of Mullard 6 transistors OC44, 2-OC45, OC81D, matched pair OC81. 25/-, All Post Free.

**HARVERSON SURPLUS CO. LTD.**

170 HIGH ST., MERTON, S.W.19. CHERRYWOOD 3985/6

Open all day Saturday. Early closing Wed., 1 p.m.  
A few minutes from South Wimbledon Tube Station. (Please write clearly)  
Please Note: P. & P. charges quoted apply to U.K. only. P. & P. on overseas orders charged extra. (S.A.E. all enquiries).

**UNIVERSAL AVOMETERS**



Guaranteed perfect working order. Supplied complete with leads, batteries and instructions.  
**Model "D" 34 range £8.19.6**  
**Model "7" 50 range £11.0.0**  
 Registered Post 5/- extra.

**MICROAMMETERS**

0-500 microamps. 2 1/2 in. circular flush panel mounting. Dials engraved 0-15, 0-600 volts. **BRAND NEW. BOXED. 15/-.** P.P. 1/6.

**7.5 K.V.A. AUTO TRANSFORMERS**

0-115-230 volts. Brand new boxed. **£15.** Carriage 10/-.

**230/250 VOLT A.C. MOTORS**  
 44 x 3 in. dia., 90 watts, 5,000 r.p.m. 1/2 in. spindle. **22/6.** P.P. 1/6.

**1 K.V.A. ISOLATION TRANSFORMERS**

230 v. P.T. 1, 230 v. Sec. Boxed, **£5** each. Carriage 10/-.

**VARIAC TRANSFORMERS**  
 24 amp., 230 volt primary, 185 to 250 volt output, **£12.10.0.** Carriage 10/-.

**TELEPHONES TYPE "H"**  
 Sound powered, generator bell ringing, 2 line connection. Fully tested. **£4.19.6** pair. Carr. 5/-.

**MINIFLUX HI-FI TAPE HEADS**  
 Set of three, record, playback, erase. Only **29/6** set. P.P. 9d.

**3000 WATT AUTO TRANSFORMERS**

0-115-230 volts, step-up or step-down. Brand new, boxed ex-U.S.A. **£7.10.0** each. Carr. 10/-.

**PANEL METERS**

100µA	2 1/2" F.M.	D.C.	42/6
100µA	3 1/2" F.M.	D.C.	62/6
1 mA	2 1/2" F.M.	D.C.	25/-
30/10/30 mA	2 1/2" F.M.	D.C.	9/8
350 mA	2 1/2" F.M.	D.C.	10/6
300 v.	2 1/2" Proj.	A.C.	19/6
300 v.	2 1/2" F.M.	A.C.	25/-
300 v.	2 1/2" F.M.	A.C.	25/-
120 v.	3 1/2" F.M.	D.C.	32/6

Postage Extra.

**FIELD TELEPHONES TYPE "F"**

Suitable for many applications. Generator bell ringing, 2 line connection. With batteries and wooden carrying case, fully tested. **£4.19.6** per pair. Carr. 5/-.

**SUB-STANDARD D.C. AMMETERS**  
 9 ranges, 150mA, 1.5A, 3A, 7.5A, 15A, 30A, 80A, 300A, and 450A. Housed in teak portable case, 6 in. mirror scale. Supplied brand new with all shunts and leather carrying case. **£15** each. P.P. 10/-.


**P.C.R.2 RECEIVERS**

800-2,000 metres, 190-550 metres 6-22 Mc/s. output for phones or 3 Ω speaker. As new **£5.19.6.** Carr. 10/6. P.C.R.2 as PCR2 but covers 130/550 metres, 2-7 Mc/s. 7-22 Mc/s. including top band. As new **£8.8.0.** Carr. 10/6. All above models can be supplied with internal power unit to operate on 200/250 v. A.C. at 39/6 extra or alternatively plug-in external power units are 35/-.

**AVO WIDE RANGE SIGNAL GENERATORS**

Frequency coverage 50 Kc/s to 80 Mc/s in six turret operated ranges. For use on standard A.C. mains. Packed in original transit cases with accessories. Supplied in as new condition, fully checked before despatch, **£15.** Carriage 10/-.

**NATIONAL H.R.O. RECEIVERS**

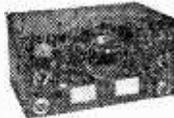

**SENIOR MODEL.** Supplied complete with full set of 9 coils covering 50 kc/s. to 30 Mc/s. Each receiver thoroughly checked and available as follows:  
**TABLE MODEL.** As new condition **£25.**  
**TABLE MODEL.** Extremely good used condition **£19.19.0.**  
**RACK MODEL.** Extremely good used condition **£18.19.0.** Carriage **£1** extra.

200/250 volt A.C. power packs for above receiver, also sold separately, **59/6.** Carr. 5/-.

**PRECISION COMBINATION VOLTMEETER/AMMETER FOR A.C. AND D.C.**

Two separate instruments housed in polished wood case. 6 in. scales with knife edge pointers.

Ranges:  
 Volts A.C. and D.C. 160-300-600 v.  
 Amps. A.C. and D.C. 25-50-150-200 A.  
 Supplied complete with all current shunts, leads and leather carrying case. Manufactured by Elliott Bros. Supplied brand new. **£9.19.6** each. Carriage 7/6.

**HALLICRAFTER S-36 V.H.F. RECEIVERS**

F.M./A.M. 27-143 Mc/s. .110 volt A.C. (transformer supplied for 230 v. A.C.) Improved version of S-27. Tested before despatch. Brand new boxed with instruction manual. **£40** each. Carr. **£2**

**MINE DETECTOR No. 4A**

Will detect all types of metal. Fully portable. Complete equipment supplied tested with instructions, **39/6.** Carriage, 10/6. Battery 8/6 extra.

**COLLARO STUDIO TAPE TRANSCRIBOR**

Brand new 1962 model, 3 speeds, 3 motors, digital counter, etc. With latest Bradmatic heads and interlock button. Supplied with spare spool. Instructions, fixings, 10 kms. each. Carr. paid.

**FABULOUS TAPE OFFER**

Famous American Brand Tapes. Brand new, fully guaranteed. 5in.—600ft., 10/6, 5in.—900ft., 13/6, 5in.—1200ft., 17/-, 7in.—1200ft., 13/6, 7in.—1800ft., 18/6, 7in.—2400ft., 27/6, P. & P. extra. S.A.E. for full tape list.

**MULTIMETERS BRAND NEW—FULLY GUARANTEED—LOWEST EVER PRICES**

Supplied with Leads, Batteries and Instructions.

1,000 Ω/VOLT	20,000 Ω/VOLT
0/15/150/1,000 v. A.C. and D.C.	0/10/50/250/500/1,000 v. A.C. and D.C.
0/150 mA D.C.	0/50µA/10/250 mA D.C.
0/100 K Ω etc.	0/50K/100K/1 meg. etc. 97/6.
39/6. P. & P. 1/6.	P. & P. 2/6.

30,000 Ω/VOLT	50,000 Ω/VOLT
0/1/1/10/50/250/500/1,000 v. D.C.	0/10/50/250/500 v. A.C.
0/10/50/250/500 v. A.C.	0/50µA/10/10/250 mA D.C.
0/10K/1 meg./10 meg. etc. £5.10.0.	P.P. 2/6.
30,000 Ω/VOLT	0/1/1/2/10/25/100/250/500/1,000 v. D.C. and A.C.
0/50µA/5/50/500 mA/10/12 amp. D.C.	0/60 K Ω to meg. 160 meg. etc. £8.17.6.
0/60 K Ω to meg. 160 meg. etc. £8.17.6.	Post paid.

50,000 Ω/VOLT	100,000 Ω/VOLT
0/10/50/250/500/1,000 v. D.C. and A.C.	2.5/10/50/250/1,000 v. A.C.
0/25µA/2.5/25/250 mA D.C.	10/250µA/2.5/25/250 mA/10 amp. D.C.
0/50K/100K/1 meg./10 meg. etc. £7.10.0.	P.P. 2/6.
100,000 Ω/VOLT	5/2.5/10/50/250/500/1,000 v. D.C.
2.5/10/50/250/1,000 v. A.C.	10/250µA/2.5/25/250 mA/10 amp. D.C.
20K/250K/2 meg./20 meg. ohm. etc.,	£6.19.6 post paid.

Hours of Business: 3 LISLE STREET, 9 a.m.—6 p.m. Half Day Saturday  
 34 LISLE STREET, 9 a.m.—6 p.m. Half Day Thursday

**MARCONI CRI00/8 RECEIVERS BRAND NEW**

Packed in original transit cases and complete with handbook/manual. 60 Kc/s to 30 Mc/s. 200/250 volt A.C. operation. Tested before despatch.

**£35** Carriage **£2.**

**DOUBLE BEAM OSCILLOSCOPES**

Erskine Type 13A. £27.10.0. Carr. £1. Cossor Type 1035. £45. Carr. 30/-. All fully checked perfect equipment. Other types in stock.

**L.T. METAL RECTIFIERS**

All full wave, bridge connected. Brand new.  
 12/18v.1.5A. 3/9 24/36v. 4A. 22/6  
 12/18v.2.5A. 6/3 24/36v. 6A. 27/6  
 12/18v. 4A. 8/3 24/36v. 15A. 45/-  
 12/18v. 6A. 12/3 36/48v. 2A. 19/6  
 12/18v. 10A. 22/6 36/48v. 4A. 29/6  
 12/18v. 15A. 37/6 36/48v. 6A. 32/6  
 24/36v. 1A. 7/3 48/60v. 2A. 21/-  
 24/36v. 2A. 13/6 48/60v.10A. 82/6  
 Please add postage.

**L.T. TRANSFORMERS**

All primaries tapped 200/250 volts 1 Battery Charging, 3.5, 9 or 17 volt, 1 amp., 9/8. Ditto 2 amp., 14/3. Ditto 4 amp., 16/6. 9 or 17 volt, 6 amp., 22/6.  
 2 Model Type 3, 4, 5, 6, 8, 10, 12, 15, 18, 20, 24 or 30 volt, 2 amp., 18/6. Ditto 4 amp., 30/-. Ditto 5 amp., 37/6. Add Postage.

**MINIATURE MODEL ACCUMULATORS**

Lead Acid. BRAND NEW. 2v. 1.5 A.H., 4 x 1 1/4 x 1 in. 1lb., 5/6. P.P. 1/3. 12v. 0.75 A.H., 4 x 3 x 1 1/2 in. 2lb., 15/6. P.P. 1/6.

**R.C.A. PLATE TRANSFORMERS**

Pri. 200/250 v. sec., 2,000-0-2,000 v. 500 mA, tapped 1,500 v. New. Boxed, **£6.10.0.** Carriage 15/-.

**DUMONT K1051PI DOUBLE BEAM C.R.T.**

Twin Gun. Brand new, boxed. 59/6, P.P. 3/6.

**1.2 Ohm 12 Amp RHEOSTAT**  
 Chmed slider type, new boxed. 15/8 each. P.P. 3/6.

**MARCONI TF-885 VIDEO OSCILLATORS**

25c/s-5Mc/s. Supplied in guaranteed as new condition. **£90** each.

**H.R.O. DIALS**

Brand new, 27/6. P.P. 2/6.

**MINIATURE PANEL METERS**

For 1 1/2 in. dia. panel hole.  
 0-50 µA 89/6 0-300 v. D.C. 27/6  
 0-500 µA 28/6 "50" meter 25/6  
 0-1 mA 27/6 "VU" meter 42/6  
 0-5 mA 27/6

**CONSTANT VOLTAGE TRANSFORMERS**

95-130v. Input. 115v. Output. 500 Watts. Can be used in series for 230v. **£4** each. Carr. 10/-.

**WESTON MICROAMMETER MOVING COIL RELAYS.** Brand new boxed, fully guaranteed. 42/6 each, P.P. 2/-.

Send S.A.E. For Bargain Lists

**G.W. SMITH & CO (RADIO) LIMITED**  
 Phone: GERRARD 8204/9155  
 Cables: SMITHEX LESQUARE  
 3-34 LISLE STREET, LONDON, W.C.2

*Stern's*

# MULLARD DESIGNS

COMPLETE KITS OF PARTS

## MULLARD 3-VALVE PRE-AMPLIFIER TONE CONTROL UNIT

Designed mainly for Mullard Range of Amplifiers, also suitable for any Amplifiers requiring input up to 250mV. Incorporates 5 input Channels, including for Tape and Magnetic Pickups. Separate Bass and Treble controls. High pass filter 20 to 160 c/s, low pass filter 5-9 Kc/s. Totally enclosed in case size 11 1/2" x 4 1/2" x 4".



KIT OF PARTS **£10.00** ASSEMBLED & TESTED **£13.13.0**  
(Carr. & Ins. 5/-).

## MULLARD "5-10" MAIN AMPLIFIER



For use with MULLARD 2 or 3 valve pre-amplifiers with which an undistorted power output of up to 10 watts is obtained. SPECIFIED COMPONENTS AND MULLARD VALVES including PARMEKO MAINS TRANSFORMER and choice of PARMEKO or PARTRIDGE Output Transformer.

COMPLETE KIT (Parmeko Output Trans.) **£10.00**  
ASSEMBLED AND TESTED **£13.10.0**

(Carr. & Ins. 6/6).

ABOVE incorporating PARTRIDGE OUTPUT TRANS. **£1.6.0 extra.**

## THE MULLARD 510/RC AMPLIFIER

The popular complete "5-10" incorporating Passive Control Unit providing up to 10 watts high quality reproduction with input of 800 mV. Specified components and new MULLARD VALVES. Includes PARMEKO MAINS TRANSFORMERS and choice of PARMEKO or PARTRIDGE Output Transformers. Surplus Power available for Tuner.




COMPLETE KIT **£12.00**  
ASSEMBLED AND TESTED **£16.00** With PARTRIDGE OUTPUT TRANS. **£1.6.0 ex.**  
(Carr. & Ins. 7/6).

## THE MULLARD 33/RC

A HIGH QUALITY AMPLIFIER DEVELOPED FROM THE VERY POPULAR 3-WATT MULLARD "3-3" DESIGN.

KIT OF PARTS **£8.8.0**  
ASSEMBLED AND TESTED **£11.10.0**

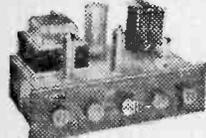Complete to the MULLARD specification including PARMEKO OUTPUT TRANSFORMER. Switched inputs for 78 and 100. Extra power to drive a Radio Tuning Unit is also available. (Carr. & Ins. 6/6). Please state L.S. Impedance.



L.P. records plus a Radio position. (Carr. & Ins. 6/6). Please state L.S. Impedance.

## THE "MONO-GRAM"

A small Amplifier of genuine high quality performance. Incorporates MULLARD ECL86 Valve, separate BASS and TREBLE controls and produces up to 3 watts undistorted output. (Carr. & Ins. 3/6).

KIT OF PARTS **£4.10.0** Assembled and Tested **£6.0.0**



Perfectly suited for Portable installations for which purpose we offer PORTABLE CASE (£3.10.0), the AMPLIFIER (KIT) and 8" x 5" SPEAKER (£1.0.0). All for **£9.0.0** Alternatively with ASSEMBLED AMPLIFIER **£10.0.0**  
(Carr. & Ins. 3/6).

The Case quoted above will accommodate some 4-speed Single Record Units. A larger model is available for extra 10/-. With this Equipment a COMPLETE PORTABLE RECORD PLAYER can be built for **£14.0.0**



## MULLARD FOUR CHANNEL MIXING UNIT

Self powered Cathode follower output. Incorporates two inputs for CRYSTAL MICROPHONES, one for CRYSTAL PICK-UPS and a fourth for Radio or Tape.

KIT OF PARTS **£8.8.0** ASSEMBLED AND TESTED **£11.10.0** (Carr. & Ins. 5/-).  
Alternative Model I/L provides for one input matched for moving coil or ribbon mike **£1.17.0 extra.**



## ARMSTRONG RADIOGRAM CHASSIS

We have the full range in stock. Prices range from £20.10.0. Full details are readily available.



Send S.A.E. for fully descriptive technical leaflets, or call at our showrooms and hear the equipment on demonstration.

## MULLARD 2-VALVE PRE-AMPLIFIER TONE CONTROL UNIT

Employing two EF36 valves and designed to operate with the Mullard AMPLIFIERS but also perfectly suitable for other makes with input up to 250 mV.



- ★ Equalisation for the latest R.I.A.A. characteristics.
- ★ Input for Crystal Pick-ups and variable reluctance magnetic types
- ★ Input (a) Direct from High Imp. Tape Head. (b) From a Tape Amplifier or Pre-Amplifier.
- ★ Sensitive Microphone Channel. ★ Wide range BASS and TREBLE Controls.

KIT OF PARTS **£6.6.0** ASSEMBLED AND TESTED **£9.10.0** (Carr. & Ins. 5/-).

### PRICE REDUCTIONS

- (a) THE KIT OF PARTS to build both the "5-10" Amplifier and the 2-Valve Pre-Amplifier **£15.15.0** (Carr. & Ins. 8/6).
- (a) Assembled and Tested **£21.10.0**
- (b) THE KIT OF PARTS to build both the "5-10" Amplifier and the 3-Valve Pre-Amplifier **£19.10.0** (Carr. & Ins. 10/-).
- (b) Assembled and Tested **£25.10.0**
- With PARTRIDGE OUTPUT TRANSFORMER **£1.6.0 extra.**

## HIGH FIDELITY LOUDSPEAKERS

WE STOCK THE COMPLETE RANGE BY GOODMAN'S, WHARFEDALE and W.B. STENTORIAN A few recommended examples

- 8 INCH TYPES
  - GOODMANS "AXIETTE" **£5.5.7**
  - W.B. HF 816 **£5.19.6**
  - WHARFEDALE "SUPER 8RS/DD" **£6.14.2**
  - 10 INCH TYPES
  - GOODMANS "AXIOM 10" **£8.5.11**
  - W.B. MODEL HF 1016 **£7.0.0**
  - WHARFEDALE "GOLDEN 10RS/DD" **£7.17.5**
  - 12 INCH TYPES
  - GOODMANS "AXIOM 20" 15 watts **£10.7.0**
  - GOODMANS "AXIOM 30" 20 watts **£14.10.0**
  - W.B. MODEL HF 1214 15 watts **£10.5.8**
  - WHARFEDALE "W12/RS" **£10.15.0**
  - WHARFEDALE "Super 12RS/DD" **£17.10.0**
- Carr. & Ins. on above 5/6 each.

We are pleased to announce that all Stern's products are now available from

**CLYNE RADIO LTD.**  
12 SUFFOLK HOUSE  
GEORGE STREET, CROYDON  
Telephone: MUN 3250

## RECORD PLAYERS

- THE COLLARO "JUNIOR" 4-speed single player with separate crystal pick-up **£3.10.0**
- THE NEW GARRARD "AUTOSLIM" 4-speed autochanger with crystal pick-up **£6.10.0**
- GARRARD "AUTOSLIM DE LUXE" 4-speed autochanger. Incorporates transcription pick-up arm **£11.8.0**
- THE COLLARO "C8" 4-speed autochanger unit with Studio "O" pick-up **£6.19.6**
- K.S.R. Model UA14. 4-speed mixer autochanger with crystal pick-up **£5.19.6**
- The new GARRARD Model 4111 High Quality Single Record Player fitted with the latest T.P.A. 12 pick-up arm and G.C.B. crystal Cartridge **£16.17.6**
- GARRARD Model S.R.P. 10 single record player fitted with high output crystal pick-up PH 11's Model A.G.116. 4-speed player can be operated both manually and automatically. Suitable for Mono or Stereo operation **£59.1**
- Carr. and Ins. on each above 5/6 extra. **£12.12.0**

## Mk. 11 "Fidelity" FM TUNING UNIT

- An attractively presented Unit incorporating the TYPE OF EQUIPMENT TO USE—OUR WIDELY EXPERIENCED TECHNICAL STAFF WILL WITH PLEASURE PUT FORWARD RECOMMENDATIONS—STATE TYPE OF INSTALLATION CONTEMPLATED AND APPROX. PRICE LEVEL. CREDIT SALE TERMS are available on all Equipment over £10.0.0. FULLY DESCRIPTIVE LEAFLETS are readily available—please advise items of interest and enclose S.A.E.
- KIT OF PARTS **£10.10.0**
- ASSEMBLED AND TESTED **£14.5.0** Carr. & Ins. 9/-.

IF YOU ARE PLANNING TO INSTALL "HI-FI" and UNCERTAIN OF THE TYPE OF EQUIPMENT TO USE—OUR WIDELY EXPERIENCED TECHNICAL STAFF WILL WITH PLEASURE PUT FORWARD RECOMMENDATIONS—STATE TYPE OF INSTALLATION CONTEMPLATED AND APPROX. PRICE LEVEL. CREDIT SALE TERMS are available on all Equipment over £10.0.0. FULLY DESCRIPTIVE LEAFLETS are readily available—please advise items of interest and enclose S.A.E.

*Stern's*

**SPECIALISTS IN SOUND EQUIPMENT FOR OVER 25 YEARS**

**MULLARD "10+10" STEREO AMPLIFIER**

A high fidelity design providing up to 10 watts (per channel). Superb reproduction frequency response flat to within 3db from 3 c/s to 60 Kc/s at 50mW Total Harmonic Distortion at 10 watts 0.1%.



- (a) THE ASSEMBLED MAIN AMPLIFIER AND ASSEMBLED DUAL CHANNEL PRE-AMP..... **£34.0.0**
- (b) KIT OF PARTS..... **£27.0.0**

**MODEL CR3/S TAPE RECORDER**

MODEL CR3/S Incorporates the HF/TR3 Mk. II Tape Amplifier (described below) and the Collaro "Studio" Twin Track 3-speed Deck operating at 1 1/2in., 3 1/2in., and 7 1/2in. speeds. Complete with microphone and 1,200ft. tape.

- KIT OF PARTS **£33.8.0**
- ASSEMBLED **£43.0.0**
- AND TESTED (Carr. & Ins. 15/- extra).



**MULLARD DUAL-CHANNEL PRE-AMPLIFIER**

A four Valve design for both STEREO-PHONIC and MONOPHONIC operation. Operates equally well with any make of Amplifier requiring an input of up to 250 mV.



- PARTS **£12.10.0**
- ASSEMBLED AND TESTED **£15.0.0**
- (Carr. & Ins. 5/-)

**STEREO TAPE PRE-AMPLIFIER**



MODEL STP-1. For use with current TRUVOX, BRENNELL, or COLLARO "STUDIO" 1 and 1/2 track Stereo Decks. Incorporates Ferroxcube Oscillator, 4 speed Equalisation Signal Level Meter and separate Gain Controls. Includes separate Power Unit.

- KIT OF PARTS **£22.0.0**
- INS. 8/6.
- ASSEMBLED **£28.0.0**

**TAPE PRE-AMPLIFIER MULLARD Type "C"**

Suitable for most 1/2 track, Mono Tape Decks. Incorporates Ferroxcube Push Pull Oscillator, Treble Inductor and 3-speed Equalisation. Includes Separate Power Unit.



- KIT OF PARTS **£14.0.0**
- ASSEMBLED **£19.10.0**
- (Carr. & Ins. 7/6)

**MULLARD TAPE AMPLIFIER**

Based on Mullard's Type "A" design and suitable for most 1/2 track Mono Tape Decks. Incorporates Ferroxcube Treble Inductor, Gilson Output Transformer, and 3-speed Equalisation. Includes separate Power Unit.



- MODEL HF/TR3 MK. II
- ASSEMBLED **£19.0.0**

**STERN'S "ADD-A-DECK"**

A self contained Unit consisting of Garrard Deck and matched Pre-amplifier on one chassis. Provides full tape recording facilities and replays through Pick Up Sockets of standard Radio receiver or Amplifier.



- PRICE includes complete Tape Magazine. **£18.18.0**
- (Carr. & Ins. 10/-)


**COMBINED PRICE OFFERS !!!**

- Includes small charge for special testing and PRECISE MATCHING of the ASSEMBLED PRE-AMPLIFIER (or Amplifier) to TAPE DECK
- STP-1 (Kit) and "STUDIO" Deck **£39.0.0** Assembled **£46.0.0**
- STP-1 (Kit) and Brenell Deck .. **£66.0.0** Assembled **£75.0.0**
- STP-1 (Kit) and Truvox Deck .. **£51.0.0** Assembled **£59.0.0**
- TYPE "C" (Kit) and "STUDIO" Deck .. **£26.10.0** Assembled **£33.0.0**
- TYPE "C" (Kit) and BRENNELL Deck .. **£43.0.0** Assembled **£50.0.0**
- TYPE "C" Assembled and Wearite Deck **£70.0.0** Inc. Head Lift Trans.
- HF/TR3 (Kit) and "STUDIO" Deck **£26.0.0** Assembled **£33.0.0**
- HF/TR3 (Kit) and BRENNELL Deck **£43.0.0** Assembled **£59.0.0**
- HF/TR3 Assembled and Wearite Deck .. **£70.0.0** Inc. Head Lift Trans.

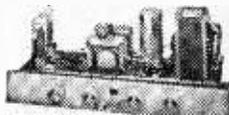**THE "TWIN THREE" STEREO AMPLIFIER**

ASSEMBLED AND TESTED

- £9.0.0** (Carriage and Insurance 5/- extra)



Based on a recent design by MULLARD LTD., is ideally suited for use in Portable RECORD PLAYERS for which purpose we offer a specially designed Case: incorporates MULLARD ECL 86 Valves, separate BASS and TREBLE CONTROLS and produces up to 3 watts per channel. Frequency response 40 c/s to 35 Kc/s, size is only 1 1/2in. x 3in. x 5in. To construct a STEREO PORTABLE RECORD PLAYER we offer: ASSEMBLED AMPLIFIER with two ROLA 8in. x 5in. **£16.10.0** Carr. & LOUSPEAKERS and PORTABLE CASE for.... **£16.10.0** Ins. 10/-

**THE "TUDOR" STEREO AMPLIFIER**


- PRICE **£15.0.0** (Packing & Carr. 7/6)



A self-contained Shelf-mounting Amplifier designed to provide high quality stereophonic and monophonic reproduction. Each channel provides a rated output of 6 watts and for monophonic operation approx. 12 watts is produced. Separate BASS and TREBLE CONTROLS. The Cabinet is finished in Black Crackle. Size 14 x 8 x 4in. Send for full specification.

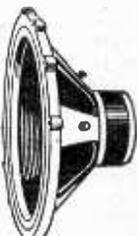**PLESSEY 15in. P.M. LOUSPEAKER**

- Ex B.B.C.
- A high quality 15in. loudspeaker, handling 20 watts of audio. Suitable for use in public address systems where considerable power is handled, or as a bass reproducer in dual or triple loudspeaker systems where full use can be made of the low fundamental resonance and smooth response.
- Impedance .. .. . 15 ohms at 400 c/s.
- Dia. of pole piece .. .. . 2 inches
- Power rating .. .. . 20 watts
- Flux density .. .. . 12,000 lines
- Total flux .. .. . 185,000 Maxwells
- Bass resonance .. .. . 25 C.P.S.
- Frequency range .. .. . 20 C.P.C. to 5 Kc/s.
- Nett weight .. .. . 25lb oz.



- PRICE **12 gns.** Carr. & Ins. 10/6 extra

Our Technical dept. will be happy to advise on the choice of matching PICK-UPS, Microphones, Loudspeakers.

**Send for current price list of all leading recording tapes and accessories**

WHEN ORDERING OR WRITING FOR LEAFLETS PLEASE STATE DEPT. P.W.

<p><b>POSTAL ENQUIRIES and MAIL ORDERS TO . . .</b></p> <p><b>STERN RADIO LTD.</b></p> <p>6-12, TUDOR PLACE, TOTTENHAM COURT RD. LONDON, W1. TEL. MUSEUM 6128/9</p>	<p><b>DEMONSTRATION and SHOWROOMS AT . . .</b></p> <p><b>STERN RADIO LTD.</b></p> <p>109, FLEET ST. LONDON, EC4</p> <p>TEL. FLEET ST. 5812/3</p> <p>OPEN... 9 a.m. to 6 p.m. SAT. close 1 p.m.</p>	<p><b>PREMIER RADIO</b></p> <p>23, TOTTENHAM COURT RD. LONDON, W1. TEL. MUSEUM 6128/9</p> <p>OPEN... 9 a.m. to 6 p.m. THURS. close 1 p.m.</p>
---	--	---

Brand new individually checked and guaranteed

VALVES

AC/HL 4/8	EABC80 6/3	EL91 4/6	FOC84 6/6	U27 8/-	2X2 3/-	6F7 5/-	7H7 7/3	59 6/-	7475 3/-
AC/P4 4/8	EAC91 3/6	EL95 4/6	FOC85 7/6	U32 5/-	3A4 4/-	6F8 5/-	7Q7 7/-	73 5/6	8013A 25/-
AC/CPEN	EH34 1/6	EM80 7/6	FOC89 10/6	U601 20/-	3A/167M	6F12 4/6	7V7 5/-	78 5/-	8001 3/-
ARR 5/-	EHC33 6/-	EN31 10/6	FOC92 6/8	UHC41 7/-	3B7 2/-	6F13 5/-	7Z4 4/8	77 4/-	8002 4/6
ARP3 3/-	EBCA1 7/9	EYU308 6/-	PCL82 9/-	UBF89 8/-	3B24 5/-	6F22 4/-	8D2 2/6	79 5/-	9003 6/-
ARP4 3/6	EC90 5/6	EU151 8/-	PCL83 9/-	UBF89 7/6	3B28 15/-	6F23 3/6	9D2 3/-	80 5/6	9004 2/6
ARP12 2/6	EHF50 7/6	EY86 7/-	PCL84 7/-	UCH43 7/6	3E29 50/-	6H1 6/-	11E3 17/6	81 6/-	9006 2/6
ARP21 7/6	EHF89 7/9	EY91 3/-	PCL96 10/6	UCH81 8/-	3Q4 6/-	6H5M 1/6	12A17 5/-	82 8/-	
ARP24 3/6	EC90 20/-	EZ40 6/6	PEX26 6/6	UC82 9/-	3S4 6/-	6J4 9/-	12A19 11/-	83A2 7/6	C.R. Tubes
ARI34 4/-	EC91 3/-	EZ41 6/6	PEX46 4/-	UC83 11/-	3V4 6/-	6J5 3/6	12AT7 4/6	89 6/-	ACR8 20/-
ARTP1 6/-	EC081 4/6	EZ80 6/-	PEN20A	UL41 2/-	6A173G 5/-	6J5G 3/6	12A06 9/-	90C1 8/-	CV195 15/-
ATP4 2/3	EC082 4/6	EZ81 6/-	PL36 3/-	UL42 7/-	6A174G 5/-	6L8 8/6	12A07 5/-	90C1 8/-	CV1500 60/-
ATP7 6/6	EC083 6/-	F0057 5/-	PL37 3/-	UL43 7/-	5B/25M	6K7G 5/-	12A07 10/-	90C1 8/-	CV1596 5/-
A17 50/-	EC084 7/-	F0691 3/-	PL38 6/6	UY41 8/-	19/-	6K7GT 5/-	12C2 3/-	90C1 8/-	109J1 5/-
A231 7/-	EC085 8/-	F0693 4/-	PL39 6/6	UY45 8/-	5R4GY 9/-	6K7G 2/-	12C8 3/-	90C1 8/-	E4103/B4 25/-
B844 4/6	EC091 4/-	PW43006/6	PL40 6/6	V1924 20/-	5T4 8/-	6K7GT 4/6	12E1 17/-	90C1 8/-	309A 5/-
BT45 15/-	ECF80 7/9	Q12894 9/-	PL41 7/3	VMP4G 12/-	5U4G 5/-	6K90 9/-	12E6 9/-	90C1 8/-	E4304/B/16 30/-
BT9B 20/-	ECF82 7/9	Q232 9/-	PL42 10/6	VP23 3/-	5X4G 8/6	6K90T 8/3	12E5GT 2/6	90C1 8/-	309A 15/-
BT83 35/-	ECF84 9/6	Q383 7/6	PL43 6/6	VR195/30	6Y8G 8/6	6K9M 8/6	12E6 9/-	90C1 8/-	309A 15/-
CC34 2/-	ECH81 7/-	HK54 22/6	PL44 6/6	VR150/30	5Y3G 3/-	6K25 12/-	12K8M 7/6	713B 60/-	VCR128 28/-
CIC 5/-	ECL80 6/8	HL2K 2/6	PL45 6/6	VR150/30	5Y3GT 6/-	6L5G 6/-	12Q7GT 4/6	801 6/-	VCR139A 30/-
CV71 3/-	ECL82 8/-	HL23 6/-	PL46 6/6	VX32 9/6	5Z4 8/6	6L8 9/-	12S47 7/-	803 22/6	309A 15/-
CV109 1/3	ELC83 10/-	HL23DD 6/-	PL47 6/6	VX32 9/6	5Z4G 7/6	6L8 9/-	12S47 7/-	803 22/6	309A 15/-
CV284 12/6	ELC84 11/-	HL24 6/-	PL48 6/6	VX39 6/-	6A167 4/-	6L8 9/-	12S47 7/-	803 22/6	309A 15/-
CV4014 7/-	EP30 4/6	HV2 9/-	PL49 6/6	VX39 6/-	6A167 4/-	6L8 9/-	12S47 7/-	803 22/6	309A 15/-
CV4015 5/-	EP39 4/6	K3A 10/-	PL50 6/6	VX32G 4/-	6A05 3/-	6L19 6/6	12S47 7/-	803 22/6	309A 15/-
CV4025 10/-	EP41 8/-	KT32 8/-	PL51 6/6	VX32G 4/-	6A05 3/-	6L19 6/6	12S47 7/-	803 22/6	309A 15/-
CV4048 40/-	EP50 1/6	KT39C 4/-	PL52 6/6	VX32G 4/-	6A05 3/-	6L19 6/6	12S47 7/-	803 22/6	309A 15/-
CV31 6/-	EP54 3/3	K744 5/6	PL53 6/6	VX32G 4/-	6A05 3/-	6L19 6/6	12S47 7/-	803 22/6	309A 15/-
D1 3/6	EP55 4/6	K758 4/-	PL54 6/6	VX32G 4/-	6A05 3/-	6L19 6/6	12S47 7/-	803 22/6	309A 15/-
D41 3/3	EP70 4/-	K766 1/6	PL55 6/6	VX32G 4/-	6A05 3/-	6L19 6/6	12S47 7/-	803 22/6	309A 15/-
D77 4/3	EP73 6/-	K767 15/-	PL56 6/6	VX32G 4/-	6A05 3/-	6L19 6/6	12S47 7/-	803 22/6	309A 15/-
DA30 12/6	EP74 7/-	K776 8/6	PL57 6/6	VX32G 4/-	6A05 3/-	6L19 6/6	12S47 7/-	803 22/6	309A 15/-
DA96 7/-	EP80 5/6	K781 6/6	PL58 6/6	VX32G 4/-	6A05 3/-	6L19 6/6	12S47 7/-	803 22/6	309A 15/-
DD41 4/-	EP85 6/-	K782 6/6	PL59 6/6	VX32G 4/-	6A05 3/-	6L19 6/6	12S47 7/-	803 22/6	309A 15/-
DET20 2/-	EP86 6/-	K784 6/6	PL60 6/6	VX32G 4/-	6A05 3/-	6L19 6/6	12S47 7/-	803 22/6	309A 15/-
DE72 5/-	EP89 6/-	K783 6/6	PL61 6/6	VX32G 4/-	6A05 3/-	6L19 6/6	12S47 7/-	803 22/6	309A 15/-
DE91 3/-	EP91 2/6	LP2 10/-	PL62 6/6	VX32G 4/-	6A05 3/-	6L19 6/6	12S47 7/-	803 22/6	309A 15/-
DE96 7/-	EP92 3/-	MS12 12/-	PL63 6/6	VX32G 4/-	6A05 3/-	6L19 6/6	12S47 7/-	803 22/6	309A 15/-
DK98 7/3	EP93 3/-	MH 3/6	PL64 6/6	VX32G 4/-	6A05 3/-	6L19 6/6	12S47 7/-	803 22/6	309A 15/-
DL92 5/-	EP183 9/-	M14 4/6	PL65 6/6	VX32G 4/-	6A05 3/-	6L19 6/6	12S47 7/-	803 22/6	309A 15/-
DL93 3/-	EP184 9/-	M16 6/-	PL66 6/6	VX32G 4/-	6A05 3/-	6L19 6/6	12S47 7/-	803 22/6	309A 15/-
DL94 6/-	EL32 3/6	MN/PEN 6/-	PL67 6/6	VX32G 4/-	6A05 3/-	6L19 6/6	12S47 7/-	803 22/6	309A 15/-
DL96 7/-	E134 12/-	N78 10/-	PL68 6/6	VX32G 4/-	6A05 3/-	6L19 6/6	12S47 7/-	803 22/6	309A 15/-
DL819 15/-	E135 5/-	OB3 7/6	PL69 6/6	VX32G 4/-	6A05 3/-	6L19 6/6	12S47 7/-	803 22/6	309A 15/-
E1415 30/-	E141 8/-	OC3 5/6	PL70 6/6	VX32G 4/-	6A05 3/-	6L19 6/6	12S47 7/-	803 22/6	309A 15/-
E1234 16/-	E142 8/-	OD3 6/-	PL71 6/6	VX32G 4/-	6A05 3/-	6L19 6/6	12S47 7/-	803 22/6	309A 15/-
E450 1/6	E184 6/3	OZ4 4/-	PL72 6/6	VX32G 4/-	6A05 3/-	6L19 6/6	12S47 7/-	803 22/6	309A 15/-

MANY OTHERS IN STOCK include: Cathode Ray Tubes and Special Valves. U.K. orders below £1 P. & P. 1/-; over £1 2/-; over £5, P. & P. free C.O.D. 2/6 extra. Overseas Postage extra at cost.

MARCONI COMMUNICATION RECEIVERS. CR.150.

Frequency coverage 2-60 Mc/s in 5 bands. Two I.F.s. 1st 1,600 kc/s, 2nd 463 kc/s. Image signal protecting over 40 dB up to 30 Mc/s and 20-40 dB from 30-60 Mc/s. Self checking calibration (built in calibrator). Stabilisation of supply and temperature compensation. Electrical and mechanical bandspread. Metering and visual tuning indicator. Bandpass from 100c/s to 10kc in 5 stages. Acoustic filter associated with 100c/s. Bandpass position for CW reception. Facilities for diversity reception. In as new guaranteed condition with original mains power supply unit £70 or without power supply unit £60. Carriage 30/-.

P.C. RADIO'S mains power supply unit for above, 90/-.

CR.150/2. Frequency coverage 1.5-22 Mc/s in 4 bands, all other features as in CR.150. Price £35. Carriage 30/-.

P.C. RADIO'S mains power supply unit for above, 90/-.

CR.150/3. Same as CR.150 with additional separate antenna trimmer on front panel, crystal controlled 1st oscillator for fixed frequency reception, muting switch (during transmission), wide bandpass extended to 13 kc/s. In as new guaranteed condition with original mains power supply unit £75 or without power supply unit £65. Carriage 30/-.

P.C. RADIO'S mains power supply unit for above, 90/-.

H.R.O. Senior. Table Model. In excellent, fully checked, and tested condition (without coils and power pack), £15.10.0. As above but rack mounted model, £14.10.0.

Individual frequency coils for above £1 each set or set of 9 £8. Either mode, carriage £1.10.0.

Original mains power pack for H.R.O. 110/220 v. A.C. Brand new in original packing, 45/-, P. & P. 4/-.

"CONNECT AND FORGET" - "CANNOT OVERCHARGE" - "ESS-TRON" MARK I AUTOMATIC BATTERY CHARGER. Initial charging rate 6-7 amps. The charging rate automatically adjusts itself to the charge in the battery. Automatic current and voltage control. Patented application of magnetic amplification to battery charging. Indicator lights show battery fully charged, receiving charge, incorrectly connected or faulty cells. Mains voltage 200/250 v. Built for 6 or 12 v. batteries. Measurements 7 x 5 x 5 1/2 in. Weight 8 1/2 lb. Price £7.19.6. P. & P. 3/6.

CHR HIGH RESISTANCE HEAD- PHONES. New, 16/-. P. & P. 1/6.

TELEPHONE HANDSET. Standard G.P.O. type. New 12/-. P. & P. 2/-.

R.109 RECEIVER. Covering 2.8 Mc/s. 6 v. D.C. £6.18.0 including delivery in U.K.

CONNECTORS FOR TCS RECEIVER, TRANSMITTER AND REMOTE CONTROL, with original plugs of both ends. New £1.17.6 each. P. & P. 2/6.

U.H.F. SIGNAL GENERATOR TYPE TS14. 3,200-3,370 mc/s., power measuring range 20-200 mW., R.F. output power range 20 to 100 dbm below 1 mW. Power supply 115 v. A.C. Price £7.10.0. Carriage 15/-.

R.209 RECEPTION SET. A 10-valve high-grade Superhet Receiver with facilities for receiving R/T (A.M. or F.M.), and C.W. frequency 1 Mc/s-20 Mc/s. Hermetically sealed. Built on miniature valves and incorporating its own vibrator power supply unit driven by a 6 v. battery (2 point connector included). The set provides for reception from rod, open-wire or dipole aerial with built-in loudspeaker or phone output. Dimensions: Length 12 in., width 8 in., depth 9 in. Weight 23 lb. In as new, tested and guaranteed condition. £23.10.0, including special headphone and supply leads. Carr. £1.

COMPLETE SET OF STRONG AERIAL RODS (American). Screw-in type MP49, 50, 51, 52, 53, total length 15ft. 10in. Top diameter 0.185in. Bottom diameter 0.61in., together with matched aerial base. MP37 with ceramic insulator. Ideal for car or roof insulation, £2.10.0. Post free.

CHOKE SMOOTHING 8H. 10mA D.C. resistance 200 ohms, 15/-, P. & P. 2/-.

MICROPHONE TRANSFORMERS. Primary 75 ohm, Secondary 125,000 ohms. Centre tapped 20W. 150-5,000 c/sec ± 1 dB, 9/6, P. & P. 2/-.

OUTPUT TRANSFORMERS. Primary 7,500 ohm, Secondary 500 ohm. Centre tapped 2.5W. 200-5,000 c/sec ± 1 dB, 12/6, P. & P. 2/-.

MODULATION TRANSFORMERS. Primary 6,000 ohm. Centre tapped 200 ohm. D.C. resistance. Secondary 6,000 ohm. 20W, 200-5,000 c/sec ± 1 dB. Interwinding screening, 17/6, P. & P. 4/-.

All four above items fully shrouded, chassis mounting. Ex-equipment but in excellent and fully tested condition.

CARBON INSET MICROPHONE. G.P.O. type 2/6, P. & P. 1/6.

**P. C. RADIO LTD**  
170 GOLDHAWK ROAD, W.12  
Shepherd's Bush 4946

# EVEN

# BETTER PERFORMANCE

# PARISIENNE!!

## THE "TEN STAR" TRANSISTOR POCKET RADIO

### With the NEW MARK 8



# NOW ONLY 69/6

Price reduction made possible by huge demand.

- ★ No external aerial or earth required.
- ★ Free 9-volt long life battery.
- ★ Handsome black and gold tuning dial graduated for long and medium waves.
- ★ 3-inch moving coil speaker gives loud and clear reception on both long and medium waves even in your car and guarantees your favourite Luxembourg, AF.N. and Light programmes.
- ★ Printed circuit for easy assembly including high "Q" ferrite rod aerial.
- ★ Carrying handle fitted to distinctive satin cream Polystyrene case, size 5½ x 3 x 2in.
- ★ All new components including the highest gain transistors available.
- ★ Valuable illustrated instruction and reference booklet, 2/9. No experience necessary.
- ★ Hundreds of letters from satisfied customers (which may be inspected) underline the "Parisiennne" success story and pay tribute to the unique after sales service.

*All components supplied separately if required.*

★ ALSO SUPPLIED BUILT AND READY FOR USE £3.19.6

PLEASE SEND FOLLOWING ITEMS  
TICK BOX BELOW AS REQUIRED

- FULL SET OF PARISIENNE COMPONENTS 69/6
- READY BUILT PARISIENNE £3.19.6
- BOOKLET 2/9 POST FREE

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_

I ENCLOSE CHEQUE P.O. MONEY ORDER INCLUDING  
2/6 P. & P. FOR £.            s.    d.

# WOLVERHAMPTON RADIO AND TV SUPPLIES

42, DARLINGTON STREET, WOLVERHAMPTON  
Telephone No. 20315

P.W.2.

# POST NOW!

# SURBITON PARK RADIO LTD.

FOR POST HASTE—POST FREE SERVICE

## MARTIN RECORDAKITS

### HALF TRACK

B.S.R. TD2 Monardeck, latest model 8 1/2 in. spool	£9.90
Deposit £1.0.0 and 9 monthly	£1.1.0
Tape Amplifier for B.S.R. deck, printed circuit wired, with ECC83, ECC82, EM55 and E251. Complete with all plugs, sockets, panels, knobs, etc. The whole amplifier mounts on to the deck, making a self-contained unit	£8.8.0
Deposit £1.0.0 and 8 monthly	£1.1.0
Case with 7in. x 4in. speaker in two tone grey	£4.4.0
Complete Kit as above	£22.0.0
Deposit £2.4.0 and 12 monthly	£1.16.8
The above recorder can be supplied assembled, tested and complete with tape and microphone for	£25.0.0
Deposit £2.10.0 and 12 monthly	£2.1.6
Collaro Studio Deck, Very latest model 3 speeds 7in. spools	£12.10.0
Deposit £1.5.0 and 12 monthly	£1.0.8
Tape Amplifier for studio deck, with ready wired printed circuit control and input panels, mains and output transformers. Complete with valves, knobs, plans, screws, etc. EF96, ECC83, EM54, E251, OA81 and 2 E254, 3 wate output. Magic eye, radio and mic. inputs, EX L/S socket, tone and monitor controls. Can be used as an amplifier	£11.11.0
Deposit £1.4.0 and 12 monthly	19/-
Case for above including 9in. x 6in. speaker	£5.5.0
Total Kit as above	£29.0.0
Deposit £2.18.0 and 12 monthly	£2.8.2
We can offer the above recorder, complete with tape and microphone, in a De Luxe two tone grey cabinet, assembled for	£35.0.0
Deposit £3.10.0 and 12 monthly	£2.18.2
This Machine is listed at 39 £ns. by makers and is a very good buy. Building Instructions available at 2/6 each kit (retuned if kit bought)	

### QUARTER TRACK

B.S.R. TD2	£11.11.0
Deposit £1.4.0 and 12 monthly	19/-
Tape Amplifier as above, but quarter track	£9.9.0
Deposit £1.0.0 and 9 monthly	£1.1.0
Case, two tone grey, with speaker	£4.4.0
Complete Kit as above	£25.0.0
Deposit £2.10.0 and 12 monthly	£2.1.6
Collaro Studio Deck, 4 track	£17.17.0
Deposit £1.17.5 and 12 monthly	£1.9.5
Tape Amplifier, as above, but 4 track	£12.12.0
Deposit £1.7.0 and 12 monthly	£1.0.8
Case with 9in. x 6in. speaker	£5.5.0
Complete Kit 4 track Collaro	£35.0.0
Deposit £3.10.0 and 12 monthly	£2.18.2
Tape Pre-amplifier for Collaro deck, with power supplies, ECC83, ECC82, E280 and EM55. Radio and Mic. sockets, gives an equalised output of 400 m/Volts.	
Half Track	£8.8.0
Deposit £1.0.0 and 8 monthly	£1.1.0
Quarter Track	£9.9.0
Deposit £1.0.0 and 8 monthly	£1.1.0
Bradmatic R/P/B and Erase on Collaro bracket 1/2 track	£11.9.6
Bradmatic R/P/B (deci 3rd head Collaro deck 1/2 track	£11.2.6
Pressure pad (Studio Deck only)	4/0
Brenell Mk.5 deck, 1/2 track, 4 speeds	£28.8.0
Deposit £3.1.6 and 12 monthly	£2.8.2
Brenell Mk.5 Amplifier, with power	£24.0.0
Deposit £2.8.0 and 12 monthly	£1.19.10

### JASON F.M. TUNERS

FMT1, complete with valves	£6.17.8
Deposit £1.1.0 and 6 monthly	£1.2.9
FMT2, complete with valves, Less Power	£7.17.8
Deposit £1.0.0 and 7 monthly	£1.2.8
FMT2, complete with valves, Self powered	£9.15.0
Deposit £1.0.0 and 9 monthly	£1.1.8
FMT3, complete with valves, Less power	£9.12.6
Deposit £1.0.8 and 9 monthly	£1.1.4
FMT3, complete with valves, Self powered	£12.0.0
Deposit £1.4.0 and 12 monthly	19/10
Power pack kit ready drilled chassis for FMT1, etc. The instruction books are included in all kits but are otherwise 8/6.	£2.12.6
JTV2, switched F.M. and T.V. Sound self powered. All valves	£14.15.0
Deposit £1.9.6 and 12 monthly	£1.4.5
Mercury 2 as JTV2 but less power, with all valves	£10.18.0
Deposit £1.1.8 and 12 monthly	17/10
The instruction book is again included but is otherwise 3/6.	
All the above units are available ready built and aligned. Price on request.	

### AMPLIFIERS (MONO)

Linear L45 Three valve amplifier	£5.19.6
Linear Distonic Five valve, push pull	£12.12.0
Deposit £1.7.0 and 12 monthly	£1.0.8
Linear Concord 30 watt with case	£18.0.0
Deposit £1.16.0 and 12 monthly	£1.9.10
Tripletone Hi Fi Major, with Pre-amp	£16.18.9
Deposit £1.15.3 and 12 monthly	£1.6.1
Pye Mozart, including Pre-amp, 10 watt	£25.4.0
Deposit £2.10.8 and 12 monthly	£2.1.11
Leak TL 12. Main amp, only 10 watt	£18.18.0
Deposit £2.0.8 and 12 monthly	£1.11.5
Leak Variolope 111 Pre-amplifier	£16.15.0
Deposit £1.11.6 and 12 monthly	£1.6.1
Quad Main amp, only 15 watt	£22.10.0
Deposit £2.5.0 and 12 monthly	£1.17.4

### AMPLIFIERS (STEREO)

Dulci AC202, Integrated	£12.12.0
Deposit £1.7.0 and 12 monthly	£1.0.8
Dulci GA505, Integrated	£18.18.0
Deposit £2.0.8 and 12 monthly	£1.11.1
Rogers Cadet Mk2, with Pre-amplifier	£26.15.0
Deposit £2.13.8 and 12 monthly	£2.4.5
Leak Stereo 20 Main amplifier	£30.9.0
Deposit £3.4.8 and 12 monthly	£2.10.3
Leak Variolope 111 Stereo Pre-amplifier	£25.0.0
Deposit £2.10.0 and 12 monthly	£2.1.6
Quad 22 Stereo Control unit, Pre-amplifier	£26.0.0
Deposit £2.10.0 and 12 monthly	£2.1.6

### RADIO TUNERS

Armstrong TM C. V.H.F. Tuner self powered	£17.19.0
Deposit £1.19.8 and 12 monthly	£1.9.5
Armstrong S73 Mk2, AM/FM self powered	£26.12.0
Deposit £2.13.0 and 12 monthly	£2.4
Armstrong AP208 AM/FM Radio chassis, Base and Treble controls, P.U. controls etc.	£21.4.0
Deposit £2.0.0 and 12 monthly	£1.14.10
Armstrong Jubilee Mk2, AM/FM Push Pull Output stage, Base and Treble	£38.5.0
Deposit £2.16.8 and 12 monthly	£2.6.11
Armstrong Stereo 55, AM/FM Radio chassis, with stereo gram. Base and Treble etc.	£29.18.0
Deposit £2.8.8 and 12 monthly	£2.9.5
Armstrong Stereo 12 Mk2, AM/FM Radio chassis, Stereo gram. Push pull output	£40.5.0
Deposit £4.0.8 and 12 monthly	£3.6.11
Brass enclosure for AP208 and Jub. Mk2	7/6
Pye HFT109, FM tuner self powered	£23.12.6
Deposit £2.9.8 and 12 monthly	£1.19.0
Pye HFT113, AM/FM Tuner self powered	£28.7.0
Deposit £2.18.8 and 12 monthly	£2.6.11
Quad F.M. Tuner self-powered	£24.18.9
Deposit £2.13.3 and 12 monthly	£2.1.1

### GRAMOPHONE UNITS

Garrard SRP10, with G.C.S Mono Cartridge	£5.9.11
B.S.R. UA14 TC8 cartridge	£6.19.6
Deposit £1.0.0 and 6 monthly	£1.8.2
Garrard Autolom Mono cartridge	£7.17.0
Deposit £1.0.0 and 7 monthly	£1.2.6
Garrard Autolom De Luxe Mono cartridge	£11.9.0
Deposit £1.8.8 and 8 monthly	£1.4.9
Phillips AG1016 with stereo cartridge	£12.12.0
Deposit £1.7.0 and 12 monthly	£1.0.8
Decca Deram Arm only	£5.5.0
Decca Deram Transcription cartridge	£4.14.6
Decca Deram Auto cartridge	£3.13.8
Goldring GL53, with arm, less cartridge	£15.19.8
Deposit £1.12.0 and 12 monthly	£1.6.6
Goldring 438 Transcription, no pick up	£17.14.0
Deposit £1.18.0 and 12 monthly	£1.5.0
Goldring GL55X as GL53 but less P.U. arm	£13.17.0
Deposit £1.7.7 and 12 monthly	£1.1.0
Garrard 4HF with Mono cartridge	£17.0.0
Deposit £1.14.0 and 12 monthly	£1.8.2
Garrard Lab. Type 101, Auto-changer, Mono	£19.14.9
Deposit £1.19.8 and 12 monthly	£1.12.9
Garrard 301	£20.12.2
Deposit £2.3.2 and 12 monthly	£1.14.0
Garrard 301 Strobe	£22.0.0
Deposit £2.4.0 and 12 monthly	£1.16.8

### LOUDSPEAKERS

Goodmans Axiote 8	£5.5.7
Goodmans Axiom 10	£6.5.11
Goodmans Axiom 201	£10.7.0
Deposit £1.1.0 and 8 monthly	£1.5.9
Goodmans 5H/20/XL Tweeter with cross over	£7.0.0
Wharfedale RS12/DD 12in. full range	£11.10.0
Deposit £1.7.6 and 9 monthly	£1.4.9
Whiteley Electrical W.B. H.F. 1012 10in.	£4.7.6

## 48 SURBITON ROAD, KINGSTON UPON THAMES, SURREY

Established over 30 years

Telephone KIN 5549

We pay all postage and insurance. All orders despatched same day. Money refund guarantee.

Hours: 9 a.m.—6 p.m. (1 p.m. Wednesday). We do not close for lunch. Open all day Saturday.

# THE R.S.C. BASS-MAJOR 30 WATT GUITAR AMPLIFIER


A MULTI-PURPOSE HIGH FIDELITY, HIGH OUTPUT UNIT FOR VOCAL AND INSTRUMENTALIST GROUPS

Eminently suitable for bass guitar and all other musical instruments

- ★ Incorporating two 12in. heavy duty 25-watt high flux (17,000 lines) loudspeakers with 2in. diameter speech coils. Designed for efficiently handling full output of amplifier at frequencies down to 25 c.t.s.
- ★ Dual Cone in second speaker reproduces frequencies up to 17,000 c.p.s.
- ★ Heavily made cabinet of convenient size 24 x 21 x 14in. has an exceptionally attractive covering in two contrasting tones of Vynair.
- ★ For 200-250 v. to 50 c.p.s. A.C. mains operation.
- ★ Four jack socket inputs and two independent vol. controls for simultaneous connection of up to four instrument pick-ups or microphones.
- ★ Separate bass and treble controls providing more than adequate "Boost" or "Cut".
- ★ LEVEL frequency response throughout the audible range.
- ★ SUPERIOR TO UNITS AT TWICE THE COST.

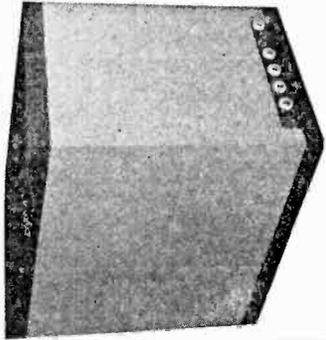**39<sup>1</sup>/<sub>2</sub> Gns.**

Send S.A.E. for leaflet.  
OR DEPOSIT of £4.3.0 and 12 monthly payments of £3.9.11. Carr. 17/6.



**R.S.C. JUNIOR GUITAR AMPLIFIER**  
5-watt high quality output. Separate bass and treble "cut" and "boost" controls. Sensitivity 15 m.v. Two high impedance inputs. 10in. loudspeaker. Handsome, strongly made cabinet (Size 14 x 14 x 7in. approx.) finished in attractive and durable polychrome. 200-250 A.C. mains operation.  
**£8.19.6** OR DEPOSIT £1 and 9 monthly payments of £1. Carr. 7/6.

**LINEAR TREMOLO/PREAMP. UNIT**  
Designed for introducing the Tremolo effect to any amplifier which is fitted with a reserve power supply point for smoothed H.T. and 6.3 v. A.C. L.T. This applies to practically all amplifiers of our manufacture, and to those of several other manufacturers. The unit plugs into power supply point and any input socket of amplifier. Controls are Speed (frequency of interruptions). Depth (for heavy or light effect). Volume and Switch. Three sockets are for two inputs and Foot Switch.  
**ONLY 4 Gns.**

## LEICESTER BRANCH NOW OPEN

**TRANSISTOR SALE.** Mullard OC71 3/9, OC45 4/11, OC44 4/11, OC72 4/9, OC81 4/11, OC171 6/9, Ediswan XA101 3/8, XB102 3/8, XA112 3/9, XB113 3/9, XB104 3/9, XC101A 3/9. Postage 6d. for up to 3 Transistors.

**D.C. SUPPLY KIT, 12 v. 1 a.** consisting of a partially drilled metal case, mains trans., F.W. Bridge Rectifier, 2 fuseholders and fuses. Change Direction switch, variable Speed regulator and circuit. For 200-250 v. A.C. mains. Suitable for Electric Trains. Limited number available at 29/11.

### SELENIUM RECTIFIERS

F.W. BRIDGE 24 v. 2 amp. . . 14/9  
6/12 v. 1 a. . . 9/11 24 v. 20 amp. . . 69/9  
6/12 v. 2 a. . . 6/11 H.T. TYPES II v.  
6/12 v. 3 a. . . 9/9 150 v. 40 mA . . . 3/9  
6/12 v. 4 a. . . 12/3 250 v. 60 mA . . . 3/11  
6/12 v. 6 a. . . 15/3 250 v. 80 mA . . . 4/11  
6/12 v. 10 a. . . 28/9 250 v. 80 mA . . . 5/11  
6/12 v. 15 a. . . 35/9 250 v. 250 mA . . . 11/9  
**CONTACT COOLED.** 250 v. 75 mA. F.W. (Bridge). 10/11. 250 v. 50 mA. F.W. (Bridge). 8/11. H.W. 250 v. 60 mA. 5/11.

**LINEAR TAPE PRE-AMPLIFIER**  
Type LP/1, Switched Negative feedback equalisation Positions for Record (1in. 3in., 7in. and Playback. EM84 Recording Level Indicator. Designed primarily as the link between a Colortape Transcriber and a high fidelity amplifier, but suitable for almost any Tape Deck. Only 9 gns. S.A.E. for leaflet.

**HUGE PURCHASE OF BRAND NEW 24 v. 20 Amp. F.W. (BRIDGE) SELENIUM RECTIFIERS.**

**49/9**

**R.S.C. SENIOR Guitar Amplifier**  
14 watt high-fidelity push-pull output.

Separate bass and treble "cut" and "boost" controls. Twin separately controlled inputs so that two instruments or "mike" and pick-up can be used at the same time. Two loudspeakers are incorporated, a 12in. high flux 14 watt bass unit, and a 6 x 4in. elliptical for treble. Cabinet is well made and finished as Junior Model. Size approx. 18 x 18 x 8in.  
**Only 16 Gns.** Carr. 10/-

Send S.A.E. for leaflet. OR DEPOSIT 37/- and nine monthly payments of 37/-.

**HEAVY DUTY LOUSPEAKERS IN SUBSTANTIAL REXINE COVERED CABINETS.** Type BGL. Suitable for Bass Guitar. Speak Unit 15in. High Flux. 15 Ohms, 25 watts. Cabinet size approx. 24 x 21 x 13in. Only 194 gns. Or Deposit 42/- and 12 monthly payments of 34/9. Type BG2. Suitable for Bass Guitar. Super Sensitive, 15in. 15 ohms high flux speaker. Cabinet size approx. 30 x 21 x 14in. Attractive covering of two contrasting tones of Rexine and Vynair. Rating 50 watts. Only 29 gns. Or Deposit £3.7.6 and 12 monthly payments of 50/-.


Type BG3/2. Suitable for Bass and Lead Guitar. Two 12in. high flux 15 ohm 25 watt speakers, one with aluminium speech coil and dual cone to provide smooth frequency response from 25 to 17,000 c.p.s. Cabinet size approx. 30 x 21 x 14in. Covered in two contrasting tones of grey Vynair and Rexine. Rating 50 watts. Only 29 gns. Or Deposit £3.7.6 and 12 monthly payments of 50/-.

**LARGE REXINE COVERED SPEAKER CABINETS.** Heavy block-board construction. Very attractive tone covering of Rexine and Vynair. Size 30 x 21 x 16in. cut for 15in. or 18in. speaker or for two 12in. 11 gns. or Deposit 25/9 and nine monthly payments 25/9. Size 30 x 30 x 16in. cut for 15in. or 18in. speaker 13 gns. or Deposit 30/4 and nine monthly payments 30/4. Suitable speakers available.

**FAVE ACOUSTICS 15in. HEAVY DUTY LOUSPEAKER.** High flux. 15 ohm 25 watt. Total flux 186,000 lines. Cast chassis. Suitable for Bass Guitar. Only 13 gns. or Deposit 31/6 and nine monthly payments 31/6.

**EXTRA HEAVY DUTY 15in. Type 152.** 40 watts. Total flux 375,000 lines. Extremely high sensitivity. 15 ohm voice coil. Only 18 gns. or Deposit 35/- and 12 monthly payments 35/-.
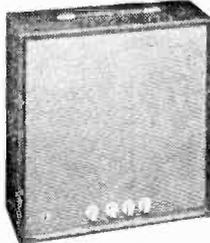
## ANNOUNCING THE R.S.C. B20 BASS GUITAR AMPLIFIER



A highly efficient unit incorporating a massive 15in. high flux loudspeaker specially constructed to withstand heaviest load conditions. Rating 25 watts. Individual bass and treble controls give ample "boost" and "cut". Two high impedance jack socket inputs are separately controlled. All controls are conveniently positioned in a recess on top of the cabinet. Cabinet is of substantial construction and attractively finished in two contrasting tones of Rexine and Vynair. Size approx. 24 x 21 x 13in. Operation from 200-250 v. 50 c.p.s. A.C. mains.  
Send S.A.E. for leaflet.

**29<sup>1</sup>/<sub>2</sub> Gns** Or Deposit £3.2.0 and 12 monthly payments of 56/10. Carr. 17/6.


**EX. GOVERNMENT ACCUMULATORS.** Size 7 1/4 x 4 x 2 1/2 in. 2 v. 16 A.H. brand new. 6/9 each. 3 for 15/6.

**EX. GOVT. SMOOTHING CHOKES.** 20 mA 3-5 H. 50 ohms. Farmto 8/9; 150 mA. 10 H. 50 ohms 9/9; 80 mA. 20 H. 900 ohms 5/9; 120 mA. 12 H. 100 ohms 8/9; 50 mA. 50 H. 1,000 ohms 6/9; 100 mA. 40 H. 100 ohms 6/9; 60 mA. 5-10 H. 250 ohms 2/11.

**COMPLETE POWER PACK, 39/9 KIT, 19/11**  
Consisting of Mains Trans., Metal Rectifier, Double electrolytic smoothing chokes chassis and circuit. For 200-250 v. A.C. mains. Outputs 250 v., 60 mA. 6.3 v. 2 a.

**R.S.C. POWER PACK, 39/9.** Louvred metal case only 8 x 5 1/2 x 2 1/2ins. Stove enamelled. For 200-250 v. A.C. mains Output at a pin plug and socket 250 v. 60 mA. fully smoothed and 6.3 v. 2 a. Suitable for power requirements of almost any Pre-amp or Radio Tuner.

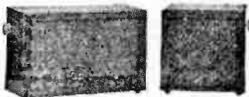**R.S.C. BABY ALARM or INTERCOMM. KIT.** Complete set of parts with diagrams, etc. Housed in two polished walnut finished cabinets of pleasing design. High sensitivity. For 200-250 v. A.C. mains. Fully isolated. Controllable at both units. An Intercomm. of this class would normally cost £20-£30. Only 79/6. carr. 5/- or assembled ready for use £5.15.0.



**EX. GOVT. SELENIUM RECTIFIERS 12v 15 AMP (BRIDGE) F.W. ONLY 19/9**

## R.S.C. (Manchester) Ltd.

MAIL ORDERS to 5 County Arcade, Leeds 1. Terms: C.W.O. or C.O.D. No C.O.D. under £1. Postage 2/9 extra under £2. 4/6 extra under £5. Trade Supplied. S.A.E. with all enquiries please.

<b>LEICESTER:</b> BIRMINGHAM: 32 High St. Half-day Thursday	<b>SHEFFIELD:</b> 6 Gt. Western Arcade Birmingham No half-day	<b>HULL:</b> 13 Exchange St. Castle Market Bldgs. Sheffield Half-day Thursday	<b>LIVERPOOL:</b> 51 Savile St., Hull Half-day Wednesday	<b>BRADFORD:</b> 73 Dale St. Liverpool 2 Half-day Wednesday	<b>MANCHESTER:</b> 56 Morley St. (above Alhambra Theatre) Bradford No half-day	<b>LEEDS:</b> 8-10 Brown St. (Market St.) Manchester 2 No half-day	<b>LEEDS:</b> 5-7 County (Mecca) Arcade Briggate, Leeds No half-day
---	--	---	--	--	--	--	--

**R.S.C.**

(Manchester) Ltd.  
 LEICESTER: 32 High St.  
 Half-day Thursday

MAIL ORDERS to 5 County Arcade, Leeds 1. Terms: C.W.O. or C.O.D. No C.O.D. under £1.  
 Postage 2/9 extra under £2. 4/6 extra under £5. Trade Supplied. S.A.E. with all enquiries please.  
 SHEFFIELD: 13 Exchange St.  
 Castle Market Bldgs. Sheffield  
 Half-day Thursday

HULL: 51 Savile St., Hull  
 Half-day Thursday

LIVERPOOL: 73 Dale St., Liverpool 2  
 Half-day Wednesday

BRADFORD: 56 Morley St. (above Alhambra Theatre) Bradford  
 Half-day Wednesday

MANCHESTER: 8-10 Brown St. (Market St.) Manchester 2  
 No half-day

LEEDS: 5-7 County (Mecca) Arcade, Briggate, Leeds.  
 No Half-day

**SENSATIONAL STEREO OFFER**

A complete set of parts to construct a good quality Stereo amplifier with an undistorted output total of 6 watts. For A.C. mains input of 230-250 v. Sensitivity 130 m.v. Ganged Vol. and Tone Controls. Preset balance control. Full instructions and wiring diagrams supplied. Stereo Pickup Head 19/9 extra with above only.

**R.S.C. 30-WATT ULTRA LINEAR HIGH FIDELITY AMPLIFIER A10**

A highly sensitive Push-Pull high output unit with self-contained Pre-amp. Tone Control Stages. Certified performance figures compare equally with most expensive amplifiers available. Hum level 70 db down. Frequency response ±3 db. 30-30,000 c/s. A specially designed sectionally wound ultra linear output transformer is used with 307 output valves. All components are chosen for reliability. Six valves are used EF86, EF98, ECC83, 6X7, 6Z7. Separate Bass and Treble Controls are provided. Minimum input required or full output is only 12 millivolts so that ANY KIND OF MICROPHONE OR PICK-UP IS SUITABLE. The unit is designed for CLUBS, SCHOOLS, THEATRES, DANCE HALLS or OUTDOOR FUNCTIONS, etc. For use with Electronic ORGAN, GUITAR, STRING BASS, etc. For standard or long-playing records OUTPUT SOCKET PROVIDES L.T. and H.T. for a RADIO FEEDER UNIT. An extra input with associated vol. control is provided so that two separate inputs such as Gram and "Mike" can be mixed. Amplifier operates on 200-250 v. 50 c/s. A.C. Mains and has output for 3 and 15 ohm speakers. Complete Kit of parts with fully punched chassis and point-to-point wiring diagrams and instructions. If required perforated cover with carrying handles can be supplied for 19/9. The amplifier can be supplied, factory built with EL34 output valves and 12 months guarantee for 14 gns. Send S.A.E. for leaflet.

**11 Gns.** Carr. 10/-  
 Suitable microphones and speakers available at competitive prices.

**WE STOCK ARMSTRONG, DULCI LINEAR and JASON EQUIPMENT GOODMANS W.B. AND FANE SPEAKERS GARRARD and GOLDRING T/TABLES**

**SUPERHET FEEDER UNIT.** Design of a high quality Radio Tuner (specially suitable for use with our Amplifiers). Delayed A.V.C. Controls are Tuning W/Ch. and Vol. Only 250 v. 50 mA. H.T. and L.T. of 6.3 v. 1 amp. required from amplifier. Size approx. 9 x 6 x 7 in. High. Simple alignment procedure. Point-to-point wiring diagrams, instructions and priced parts list supplied. S.A.E. for leaflet. Total building cost £4.15.0. S.A.E. for leaflet.

**R.S.C. BATTERY TO MAINS CONVERSION UNITS**

Type BM1. An all-dry battery eliminator. Size 5 1/2 x 4 x 2 1/2 in. approx. Completely replaces battery supply in 1.4 v. and 90 v. where A.C. mains 200-250 v. 50c/s is available. Suitable for all battery portable receivers requiring 1.4 and 90 v. This includes low consumption types. Complete kit with diagrams, 39/9, or ready to use, 46/6.



Type BM2. Size 8 x 5 1/2 x 2 1/2 in. Supplies 120 v. 90 v. and 60 v. 40 mA and 2 v. 0.4 a. to 1 amp. fully smoothed. Thereby completely replacing both H.T. batteries and L.T. 2 v. accumulators when connected to A.C. mains supply 200-250 v. 50 c/s. **SUITABLE FOR ALL BATTERY RECEIVERS** normally using 2 v. accumulators. Complete kit of parts with diagrams and instructions. 49/9, or ready for use, 59/6.

**P.M. SPEAKERS.** 10 in. W.B. "Stentorian" 3 or 15 ohms type HF 1312 10 watts, hi-fidelity type. Recommended for use with our "All American" £47.6. 12 in. H.A. 10 ohms 10 watts (12,000 lines). 59/6.

**TWEETERS.** Plessey 3Ω 19/9, 15Ω 25/9.

Jason FMT1 V.H.F./F.M. Radio Tuner design. Total costs of parts including valves, Tuning dial, Escutcheon, etc., £6.19.9. Other Jason equipment in stock.

**LINEAR 145 MINIATURE 4/5 WATT QUALITY AMPLIFIER.** Suitable for any record playing unit, and most microphones. Negative feedback 12 db. Separate Bass and Treble Control. For mains 200-250 v. 50 c/s. Output for 2-3 ohm speaker. Mullard valves E280, ECC83, EL84. Size only 7-5-5 in. high. Guaranteed 12 months. Only £5.18.6. Send S.A.E. for leaflet. Terms: Deposit 22/6 and 5 monthly payments of 22/6.

**R.S.C. 4-5 WATT AS HIGH-GAIN AMPLIFIER**

A highly-sensitive 4-valve quality amplifier for the home, small c.u.b. etc. Only 50 millivolts input is required for full output so that it is suitable for use with the latest high fidelity pick-up heads, in addition to all other types or pick-ups and practically all "mikes". Separate Bass and Treble Controls are provided. These give full long-playing record equalisation. Hum level is negligible being 71 db. down 15 db. of Negative feedback is used. H.T. of 300 v. 25 mA and L.T. of 6.3 v. 1.5 a. is suitable for the supply of a Radio Feeder Unit, or Tape-Deck pre-amplifier. For A.C. mains input of 200-250 v. 50 c/s. Output for 2-3 ohm speaker. Chassis is not alive. Kit is complete in every detail and includes full punched chassis (with baseplate) with Blue Hammer finish and point-to-point wiring diagrams and instructions. Exceptional value at only £4.15.0 or assembled ready for use 25/9 extra. Plus 3/6 carr., or deposit £2/6 and 5 monthly payments of 22/6 for assembled unit.

**NOW OPEN AT LEICESTER**

**R.S.C. GRAM AMPLIFIER KIT.** 3 watts output. Negative feedback. Controls Vol. Tone and Switch. Mains operation 200-250 v. A.C. Fully isolated chassis. Circuit, etc., supplied. Only 39/9. Carr. 3/9.  
**THE SKYFOUR I.R.F. RECEIVER** A design of a 3 valve long and medium wave 200-250 v. A.C. Mains receiver with selenium rectifier. High gain H.F. stage and low distortion detector. Valve line-up 6K7, 6SP1, 6V6G. Selectivity and quality excellent. Simple to construct. Point-to-point wiring diagrams, instructions and parts list 1/9. maximum building costs £4.19.6. inc. attractive walnut veneered wood cabinet 12 x 6 1/2 x 5 1/2 in.

**MULTI-METERS.** CARY III. Sensitivity 2,000 ohms per volt. A.C. and D.C. 54/-, A.10. Basic Meter sensitivity 155 micro-amps A.C. and D.C. ranges £4.17.6. B.30. Sensitivity up to 10,000 ohms per volt A.C. and D.C. £6.10.0. 30,000 ohms per volt £8.18.8.

**R.S.C. JUNIOR HI-FI REPRODUCER.** The very latest Goodmans Axiote 8 High Fidelity loudspeaker (retailing at approx. 5 gns.) fitted in a specially designed Bass Reflex cabinet size 12 in. x 18 in. x 10 in. Acoustically lined and ported and finished in polished walnut veneer. Matching impedance 15 ohms. Frequency range 40-15,000 c.p.s. Power handling 6 watts nominal. Ideal for Stereo. Limited number. Carr. 4/6

**8 Gns.**

**12 in. 10 WATT HIGH QUALITY LOUDSPEAKER**



In walnut veneered cabinet. Gauss 12,000 lines. Speech coil 3 ohms or 15 ohms. Only £4.19.6 Carr. 5/-. Terms: Deposit 11/3 and 9 monthly payments of 11/3.  
**12 in. 20 WATT HI-FI LOUD-SPEAKERS IN CABINETS.** Size 18 x 18 x 10 in. Finish as above. Terms: Deposit 17/9 and 5 monthly payments of 17/9. Only £7.19.6. Carr. 8/8. For larger types see page 297.

**R.A. 12 in. DUAL CONE 3 ohm 8 watt Speakers.** Ideal for Stereo. Only 39/9 ea.

**R.S.C. 4-5 WATT AS HIGH-GAIN AMPLIFIER**


A highly-sensitive 4-valve quality amplifier for the home, small c.u.b. etc. Only 50 millivolts input is required for full output so that it is suitable for use with the latest high fidelity pick-up heads, in addition to all other types or pick-ups and practically all "mikes". Separate Bass and Treble Controls are provided. These give full long-playing record equalisation. Hum level is negligible being 71 db. down 15 db. of Negative feedback is used. H.T. of 300 v. 25 mA and L.T. of 6.3 v. 1.5 a. is suitable for the supply of a Radio Feeder Unit, or Tape-Deck pre-amplifier. For A.C. mains input of 200-250 v. 50 c/s. Output for 2-3 ohm speaker. Chassis is not alive. Kit is complete in every detail and includes full punched chassis (with baseplate) with Blue Hammer finish and point-to-point wiring diagrams and instructions. Exceptional value at only £4.15.0 or assembled ready for use 25/9 extra. Plus 3/6 carr., or deposit £2/6 and 5 monthly payments of 22/6 for assembled unit.

**R.S.C. BASS REFLEX CABINETS, JUNIOR MODEL.** Specially designed for W.B. HF1012 Speaker, but suitable for any good quality 10 in. speaker. Acoustically lined and ported. Polished walnut veneer finish. Size 12 x 12 x 10 in. Handsome appearance. Ensure superb reproduction for only £3.19.6.

**STANDARD MODEL.** As above but for 12 in. speakers. Size 20 x 15 x 13 in. For vertical or horizontal use. £5.16.6. Suitable legs with brass ferrules, 19/6 per set of 4.

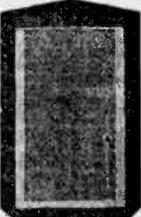**R.S.C. CORNER CONSOLE CABINETS**

Polished walnut veneer finish. Pleasing design. **JUNIOR MODEL.** Size 20 x 15 x 8 in. for 8 x 5 in. or 10 x 8 in. speakers, £2.9.9. **STANDARD MODEL.** Size 27 x 18 x 12 in. for 8 or 10 in. speakers, £4.11.9. **SENIOR MODEL.** Size 30 x 20 x 15 in. for 12 in. Speaker Suitable. Ensure superb reproduction for only 7 gns.



**AUDIOTONE HI-FI SPEAKER SYSTEMS.** Consisting of matched 12 in. 12,000 line, 15 ohm high quality speaker; cross-over unit (consisting of choke, condenser, etc.) and Tweeter. The smooth response and extended frequency range ensure surprisingly realistic reproduction. Standard 10 watt rating £4.19.9. Carr. 5/-. Or Senior 15 watt, 7 gns. Carr. 7/6.

**AUDIOTONE EQUIPMENT CABINETS**

Size 36 x 15 x 18 in. Beautiful walnut veneer finish. Elegant contemporary design. Robust construction. Uncut removable baseboard. Depth above baseboard 5 1/2 in. Only 121 gns. Carr. 15/-  
 Terms: Dep. 29/9, and 9 mthly. pymts. 29/9



# AUDIOTRON HI-FI TAPE RECORDER KIT 25<sup>1</sup>/<sub>2</sub> GNS. Carr. 17/6.

REALISM AT INCREDIBLY LOW COST, CAN BE ASSEMBLED IN AN HOUR

Incorporating the latest Collaro Studio Tape Transcriber. The audiorone High Quality Tape Amplifier with negative feedback circuit for each of 3 speeds. High Flux P.M. Speaker, empty Tape Spool, a Reel of Best Quality Tape and a Handsome Portable carrying Cabinet with latest attractive two-tone polychrome finish, size 14 1/2 x 15 x 8 1/2 in. high and circuit. Total cost if purchased individually approximately £40. Performance equal to units in the £60-£80 class. S.A.E. for leaflets. TERMS. Deposit £2.13.9 and 12 monthly payments of 44/-... Cash price if settled in 3 months.




ONLY 3 PAIRS OF SOLDERED JOINTS PLUS MAINS

**SPECIAL NOTE.** The Tape Decks we supply are latest models. Where customers already have a Deck or wish to use one of those being offered cheaply we can supply Kit less Deck at 13 gns. carr. 10/-. Or deposit 2 gns. and 12 monthly payments 23/9. Also if required we can supply in lieu of portable cabinet and 7 x 4 1/2 in. speaker the Equipment Cabinet illustrated at foot of opp. page and a high flux 81 x 5 1/2 in. speaker for 81 gns. extra.
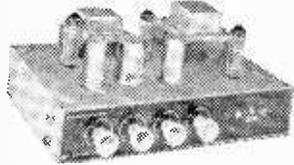
## HIGH FIDELITY 12-14 WATT AMPLIFIER TYPE A11

PUSH-PULL ULTRA LINEAR OUTPUT "BUILT-IN" TONE CONTROL PRE-AMP STAGES



Two input sockets with associated controls allow mixing of "mlke" and gram. as in A.10. High sensitivity. Includes 5 valves, ECC83, ECC83, EL84, EL84, E281. High Quality sectionally wound output transformer specially designed for Ultra Linear operation and reliable small condensers of current manufacture. INDIVIDUAL CONTROLS FOR BASS AND TREBLE "Lift" and "Cut". Frequency response  $\pm 3$  D.B. 30-30,000 c/s. Six negative feedback loops. Hum level 60 D.B. down. ONLY 22 millivolt INPUT required for FULL OUTPUT. Suitable for use with all makes and types of pick-ups and microphones. Comparable with the very best designs. For STANDARD or LONG PLAYING RECORDS. For MUSICAL INSTRUMENTS such as STRING, BASS, LEAD or RHYTHM GUITARS, etc.

OUTPUT SOCKET with plus provides 300 v. 30 mA. and 6.3 v. 1.5 a. For supply of a RADIO PEEK C.N.T. Size approx. 12-9-7in. For A.C. mains 200-250 v. 50 c.p.s. Output for 3 and 15 ohms speakers. Kit is complete to last nut. Chassis is fully punched. Full instructions and point-to-point wiring diagrams supplied. Only **8 Gns. Carr.** (Or factory built 51/- extra.) If required loured metal cover with 2 carrying handles can be supplied for 18/9. TERMS ON ASSEMBLY UNIT. DEPOSIT 24/9 and 9 monthly payments of 24/9. Send S.A.E. for illustrated leaflet detailing ready-to-assemble Cabinets. Speaker. Microphones, etc., with cash and credit terms.

**B.S.R. MONARDEK TAPEDECKS.** Speed 3in. per sec. With high quality recording heads. £6.19.6. Carr. 5/- Cabinets to take Deck and amplifier 38/6.

**R.S.C. TRANSFORMER GRAM AMPLIFIER.** Output 1 watt. for 3ohm speaker. Transformers Mullard OC71, OC81D, OC81, OC81. Fitted Vol. Control with switch. Assembled and tested. Suitable for any normal crystal pick-up. Only 59/9.

## R.S.C. STEREO/TEN HIGH QUALITY AMPLIFIER



A complete set of parts for the construction of a stereo-ophone amplifier giving 5 watts high quality output on each channel (total 10 watts). Sensitivity is 50 millivolts, suitable for all crystal stereo heads. Ganged Bass and Treble Control give equal variation of "lift" and "cut". Provision is made for use as straight (monaural) 10-watt amplifier. Valve line-up ECC83, ECC83, EL84, EL84, E281. Outputs for 2-3 ohm speakers. Point-to-Point wiring diagrams and instructions supplied. Send S.A.E. for leaflet. Full constructional details and price list 2/6. Carr. 10/-. **8 Gns.**

Kit can be supplied assembled ready to use for 59/6 extra.

## R.S.C. BATTERY CHARGING EQUIPMENT

### HEAVY DUTY CHARGER KIT

212 v. 6 amp. variable output. Consisting of Mains Transformer 0-200-250 v.: F.W. (Bridge) Selenium Rectifier; Ammeter, Variable Charge Rate Selector Panels, Fuses, Fuses, Fuseholder and circuit. 59/9. Carr. 4/6.

### CHARGER KIT, 12v. 14 AMP

or 24v. 7 amp. Consisting of mains trans. 200-250 v. F.W. (Bridge) selenium Rectifier, F. Ammeter, Fuses, Variable Resistor and Circuit. Only 6 gns. Carr. 15/- Please state if 12v. or 24v. kit required.

### SOLDERING IRONS.

230-250 v. or 30 watts. First quality. For Radio work. 18/9. Spare elements and bits available.



### Assembled 4-5 amps 6/12 v.

Fitted Ammeter and variable charge rate selector. Also selector plug for 6 v. or 12 v. charging. Loured steel case with stoved blue hammer finished. Fused and ready for use with mains and output leads. Carr. 5/-. Terms: Deposit 13/3 and 5 monthly payments 13/3. 6/12 v. 3a., all facilities as above. Only 59/9, carr. 3/9.

**ASSEMBLED 12v. 10 Amp** with variable charge rate adjustment, ammeter and strong loured, stove enamelled case. Ready for use. Only 7 gns. Carr. 10/- or in Kit Form 5 gns.

### ASSEMBLED 6/12 v. 2 amps.

Fitted Ammeter and selector plug for 6 v. or 12 v. Loured metal case finished attractive hammer blue. Fused, ready for use with mains and output leads. Carr. 3/9.

### 49/9

6/12v. 1 amp. 2/9 Less meter.

All for A.C. Mains 200-250v., 50 c/s. Guaranteed 12 months.

### BATTERY CHARGER KITS

Consisting of Mains Transformer, F.W. Bridge, Metal Rectifier, vent ventilated steel case. Fuses. Fuse-holders. Grommets, panels, Heavy Duty C.I.B.s. circuit. Carr. 3/6 extra 6v. or 12v. amp. .... 22/9 As above, with Ammeter 23/9 6 v. 2 amps. .... 19/9 6v. or 12v. 2 amps. .... 25/9 6 v. or 12 v. 2 amps. inclusive of Ammeter. .... 35/9 6 v. or 12 v. 4 amps. .... 45/9 6 v. or 12 v. 4 amps. with Ammeter and variable charge rate selector. .... 52/9

### CHARGER AMMETERS

0-1.5 a., 0-3 a., 0-4 a., 0-7 a., 0-60 a., 8/9.

## R.S.C. MAINS TRANSFORMERS (FULLY GUARANTEED)

Interleaved and Impregnated. Primaries 200-250 v. variable output. **TOP SHROUDED DROP THROUGH** 250-0-250v. 70mA. 6.3v. 2a. 0-5-6.3v. 2a/17/9 350-0-350v. 80mA. 6.3v. 2a. 5v. 2a. .... 18/9 250-0-250v. 100mA. 6.3v. 2a. 6.3v. 1a. .... 21/9 250-0-250v. 100mA. 6.3v. 3.5a. C.T. .... 19/9 250-0-250v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a 29/9 300-0-300v. 130mA. 6.3v. 4a. 6.3v. 1a. for Mullard 510 Amplifier. .... 29/9 300-0-300v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a 26/9 350-0-350v. 150mA. 6.3v. 4a. 0-5-6.3v. 3a 29/9 425-0-425v. 200mA. 6.3v. 4a. 5v. 3a. .... 49/9 **FULLY SHROUDED UPRIGHT** 250-0-250v. 60mA. 6.3v. 2a. 0-5-6.3v. 2a. .... 17/11 Midget type 21-3-3in. .... 17/11 250-0-250v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a 27/9 300-0-300v. 100mA. 6.3v. 4a. 5v. 3a. .... 27/11 300-0-300v. 130mA. 6.3v. 4a. C.T. 6.3v. 1a. for Mullard Amplifier .... 33/9 350-0-350v. 100mA. 6.3v. 4a. 5v. 3a .... 27/11 350-0-350v. 150mA. 6.3v. 4a. 5v. 3a .... 35/9

**FULLY SHROUDED (continued)**— 425-0-425v. 200mA. 6.3v. 4a. C.T. 5v. 3a 55/- 425-0-425v. 200mA. 6.3v. 4a. C.T. 6.3v. 4a. C.T. 5v. 3a. .... 59/9 450-0-450v. 250mA. 6.3v. 4a. C.T. 5v. 3a 69/9 **OUTPUT TRANSFORMERS** Midget Battery Pentode 66 : 1 for 354. etc. .... 4/6 Small Pentode, 5000Ω to 3Ω .... 4/6 Small Pentode 778,000Ω to 3Ω .... 4/6 Standard Pentode 5,000Ω to 3Ω .... 5/9 Standard Pentode 7,000Ω to 3Ω .... 5/9 10,000Ω to 3Ω .... 5/9 Push-Pull 8 watts. EL84, or 6V6 to 3Ω or matched to 15Ω .... 9/9 Push-Pull 10-12 watts to match 6V6 or EL84 to 3-5-9Ω to 15Ω .... 19/9 Following types for 3 and 15 ohm speakers: Push-Pull 10-12 watts 6V6 or EL84 .... 18/9 Push-Pull 15-18 watts. 6L6, KT66 .... 22/9 Push-Pull Mullard 510 Ultra Linear .... 29/9 Push-Pull 20 watts, sectionally wound. 6L6, KT66, EL34, etc. .... 49/9

### MIDGET MAINS Primaries 200-250 v

50 c/s. 250 v. 60 mA. 6.3 v. 2a. .... 11/9 250-0-250 v. 60 mA. 6.3 v. 2a. .... 12/11 Both above size 21 x 21 x 2 1/2 in. **FILAMENT TRANSFORMERS** All with 200-250 v. 50 c/s. primaries 6.3 v. 1.5a. 5/9; 6.3 v. 2a. 7/6; 0-4-6.3 v. 2a. 7/9. 12 v. 1 a. 7/11; 6.3 v. 3 a. 8/11; 6.3 v. 6a.: 17/6; 12 v. 1.5 a. twice 7/6. **SMOOTHING CAPACITORS** 150 mA. 7-10 H H 250 ohms .... 11/9 100 mA. 10 H 200 ohms .... 8/9 80 mA. 10 H 350 ohms .... 5/9 60 mA. 10 H 400 ohms .... 4/11 **LARGER TRANSFORMERS** All with 200-250 v. 50 c/s Primaries; 0-9-15 v. 1 1/2 a. 12/9; 0-9-15 v. 2a. 14/9; 0-9-15 v. 3 a. 16/9; 0-9-15 v. 5a. 18/9; 0-9-15 v. 6 a. 23/9; 0-9-15 v. 8a. 28/9; **WOUND (step up) TRANS.** 0-110/120-230/250 v. 50-80 watts. 13/9; 250 watts. 39/9; 150 watts. 27/9. **MICROPHONE TRANSFORMERS** 120 : 1 high grade, clamped, 6/9; 120 : 1 Potted. Mu-metal screened. 9/9.

# BENTLEY ACUSTIC CORPORATION LTD.

THE VALVE SPECIALISTS 38 CHALCOT ROAD, LONDON, N.W.1 Telephone: PRIMROSE 9090  
NEAREST UNDERGROUND: CHALK FARM. ALL GOODS LISTED BELOW ACTUALLY IN STOCK

ALL GOODS ARE NEW, BEST QUALITY BRANDS ONLY, AND SUBJECT TO MAKERS' FULL GUARANTEE. PLEASE NOTE THAT WE DO NOT SELL ITEMS FROM DISMANTLED EQUIPMENT NOR MANUFACTURERS' SECONDS & REJECTS, WHICH ARE OFTEN DESCRIBED AS "NEW AND TESTED," BUT HAVE A SHORT AND UNRELIABLE LIFE

0A2	5/-	8BR7	8/6	6U7G	9/6	25A6	7/8	AC/PEN	EA091	3/6	EL37	2/7	KTW63	5/9	Q725	5/-	U37	22/3	AF114	11/-	
0B2	17/8	8BR8	9/3	6V6G	4/-	25A6GT	7/-	AC/PEN	EA092	6/8	EL38	12/8	KTZ41	6/-	Q8150/16	10/-	U41	19/6	AF115	10/6	
0ZAGT	4/3	8H87	25/-	6V6GT	6/-	25A6GT1612	7/-	AC/PEN	EA093	1/8	EL41	7/8	LK73	3/-		10/-	U43	6/8	AF116	10/6	
1A3	3/-	6B16V	6/-	6X4	4/3	25Y5	8/-	17/-	EB41	4/9	EL42	9/-	LN309	8/9	R10	15/-	U45	15/6	AF117	9/6	
1A3	5/-	6B17V	5/-	6X3	4/8	25Y5G	8/-	AC/8G	EB81	3/-	EL43	8/9	LP2	9/8	R12	12/6	U47	10/6	AF118	20/-	
1A7	9/6	6B18V	4/3	6Y6	6/-	25Z4G	7/-	AC/8G/V	EB83	20/8	EL43	7/8	ME41	18/10	R16	12/6	U53	5/3	AF127	12/-	
1C1	5/-	6C4	2/3	7B6	9/-	30Z5	8/-	AC/18	EB84	7/8	EL44	5/6	ME91	12/6	R17	17/6	U52	4/8	GET103	6/-	
1C2	7/8	6C5	4/-	7B7	7/8	32Z6GT	8/-	AC/18	EB85	9/8	EL45	9/8	M14	8/8	R18	14/-	U78	5/8	GET104/10	10/6	
1C5	6/9	6C6	3/-	7C5	10/6	37A4	23/8	AC/TP	EB89	5/-	EL46	7/8	M114	6/8	R19	7/-	U78	4/3	GET106/17/6	8/6	
1C6	7/8	6C8	3/-	7C6	7/8	38D7	7/-	AC/VP1	EB91	5/8	EL47	2/8	M114	7/8	R22	9/-	U84	4/7	GET113	8/6	
1C8	10/6	6C9	11/-	7D3	21/-	30C1	6/8	AC/VP2	EB92	7/8	EL48	6/3	M14D12/8	6/8	R21/24A	10/1	U91	19/6	GET114	6/6	
1D6	7/8	6C10	8/-	7D5	16/-	30C15	10/6	AC/TP4	EB93	8/-	EL49	27/11	M14	4/-		54/-	U107	17/6	GET127/10/6	10/6	
1D6	9/8	6C12	7/8	7D6	18/6	30C3	6/8	AC/18	EB99	7/8	EL50	12/8	M22	15/-	RK34	7/8	U191	11/6	GET129/10/6	10/6	
1F1	6/8	6D1	13/6	7D6	15/-	30FL1	9/8	AZ31	7/8	ELB21	9/8	ELB22	19/8	M84B	22/8	S130	22/8	U201	7/6	GET174	9/6
1F2	3/-	6D6G	32/-	7H7	5/9	30FL12	12/8	AZ41	12/3	EC52	4/6	ELL80	25/8	MP4	12/-	U261	9/6	GRX13	3/8		
1F3	2/6	6C16	6/-	7H7	15/-	30L1	6/3	R36	5/6	EC53	12/6	E34	17/9	M12/14/5/6	8/8	RP13C	12/8	GRX35	1/6		
1F7	15/-	6C17	23/-	7Y4	5/-	30L15	10/3	BL63	10/6	EC54	6/8	EM34	10/6	MX40	15/-	U281	14/6	GRX36	10/6		
1FD9	4/3	6D1	1/6	8D2	7/6	30P4	12/8	C12	12/8	EC70	12/8	EM40	15/8	PC88	11/8	S49	12/8	GRX45	6/8		
1G6	6/8	6D3	12/6	8D3	3/6	30P12	7/8	C1C	12/8	EC81	27/8	EM71	22/8	N78	26/2	SP61	2/-	GRX46	11/6		
1H8GT	8/9	6D5	3/-	8P16V	13/6	30P16	6/8	CB11	27/8	EC90	2/8	EM80	6/9	N108	26/2	U299	9/6	GRX66	15/6		
1L4	3/-	6D8	15/-	8D2	3/-	30P19	12/6	CCX35	22/8	EC91	3/8	EM81	8/8	N119	22/8	SU61	6/9	MAT100	7/8		
1L46	16/10	6E5	6/-	8D7	13/7	30P11	10/6	CCX56	6/8	EC92	11/8	EM84	8/8	N151	9/-	U403	16/2	MAT101	8/8		
1L46	4/3	6E1	9/8	10C1	10/-	30P13	9/8	CL4	23/10	EC93	7/8	EM85	9/8	N308	12/8	U404	8/6	MAT120	7/8		
1L6	4/6	6E6	5/8	10C2	12/8	30P14	19/3	CV6	2/6	EC93A	23/11	EM87	13/2	Q39	15/-	TD14	8/8	MAT121	8/8		
1NGST	8/9	6E8G	4/-	10D1	7/-	35A5	20/-	CV63	10/6	EC95	5/9	EN91	15/-	N369	7/8	TH21C	14/6	OA10	8/8		
1P1	6/9	6E8GT	7/8	10D2	11/3	35A5	20/-	CV27	12/6	EC96	8/8	EY51	6/9	PAB	2/9	TH30C	14/6	OA10	8/8		
1P10	4/9	6E8	5/-	10F1	10/6	35A5	20/-	CY1	18/2	EC98	4/6	EY81	8/8	PC88	11/8	TH41	17/8	OA10	8/8		
1P11	6/9	6E11	17/9	10F6	10/6	35Z4GT	8/-	CY1	18/2	EC98	4/6	EY81	8/8	PC88	11/8	TH41	17/8	OA10	8/8		
1R5	5/6	6E12	3/6	10F8	18/6	35Z4GT	8/-	CY91	6/9	EC98A	4/6	EY84	14/8	PC95	15/8	TP25	6/-	OA10	8/8		
184	5/-	6E13	10/6	10D3	7/-	35Z4GT	8/-	D1	1/6	EC98B	6/8	EY86	6/3	PC97	9/-	TP26	20/2	OA10	8/8		
185	4/3	6E14	25/11	10D11	11/3	35Z4GT	8/-	D15	13/6	EC98C	7/3	EY81	3/8	PC98	9/3	TY66F	13/-	OA10	8/8		
1T2	25/11	6E15	9/6	10P13	13/6	41B25/11/2	11/2	D41	3/8	EC98D	11/6	EZ35	4/6	PC98S	7/9	UAB30	9/6	OA10	8/8		
1T4	2/9	6E16	7/8	10P14	12/-	42	5/8	D43	10/6	EC98E	22/8	EZ41	6/8	PC98S	7/9	UAB31	2/8	OA10	8/8		
1U5	5/3	6E17	12/6	11E1	15/-	43	10/6	D63	5/8	EC98F	22/8	EZ41	6/8	PC98S	7/9	UAB32	11/8	OA10	8/8		
2A7	10/6	6E19	6/9	12A6	2/3	60A5	21/10	D77	3/8	EC98G	8/8	EZ81	5/8	PCF96	13/8	UBC41	7/8	OA10	8/8		
2C26	3/-	6E20	9/8	12A8	16/6	60B5	7/8	DAF91	4/3	EC98H	19/6	EZ90	4/3	PCF96	6/8	UBC42	7/8	OA10	8/8		
2D13C	7/-	6E24	11/6	12A06	13/6	60C5	32/8	DAF96	9/8	EC98I	20/8	EZ90	4/3	PCF96	6/8	UBC43	7/8	OA10	8/8		
2D21	15/-	6E24	4/3	12A06	13/6	60D6G	32/8	DAF96	9/8	EC98J	20/8	EZ90	4/3	PCF96	6/8	UBC44	7/8	OA10	8/8		
2F	29/3	6E25	3/6	12A06	13/6	60L6GT	7/8	DD4	12/8	EC98K	22/8	EW4	5/6	PCF96	6/8	UBC45	7/8	OA10	8/8		
2X2	3/-	6E6	2/8	12A8	7/8	68K	14/6	DD4	12/8	EC98L	11/8	FC13	14/8	PCF96	6/8	UBC46	7/8	OA10	8/8		
2X4	4/-	6H6	1/6	12A8H	9/8	73	6/8	DD4	12/8	EC98M	11/8	FC13	14/8	PCF96	6/8	UBC47	7/8	OA10	8/8		
2A3	7/-	6J5G	3/-	12A76	5/8	73	6/8	DDT4	7/8	EC98N	7/8	FC13	14/8	PCF96	6/8	UBC48	7/8	OA10	8/8		
2B7	5/-	6J5GT	4/3	12A77	4/6	73	6/8	DDT5	7/8	EC98O	7/8	FC13	14/8	PCF96	6/8	UBC49	7/8	OA10	8/8		
2D6	4/-	6J6	3/-	12A76	6/8	73	6/8	DDT6	7/8	EC98P	7/8	FC13	14/8	PCF96	6/8	UBC50	7/8	OA10	8/8		
2E4	6/8	6A4G	4/9	12A7	6/8	77	9/8	DDF6	15/-	EC98Q	8/8	GZ30	7/8	PCN48	19/3	UCH81	7/3	OA10	8/8		
2X5	7/3	6J7GT	7/-	12A7	6/8	77	9/8	DDF7	30/-	EC98R	14/7	GZ32	7/8	PCN48	19/3	UCH82	7/3	OA10	8/8		
2S4	4/9	6J8	12/6	12A7	4/9	90	5/8	DDF9	2/9	EC98S	6/3	GZ33	17/8	PCN48	19/3	UCH83	7/3	OA10	8/8		
2Y4	6/-	6K6	8/8	12B4A	6/8	83	13/8	DDF6	6/9	EC98T	8/8	GZ34	11/8	PCN48	19/3	UCH84	7/3	OA10	8/8		
4D1	4/-	6K7G	1/8	12B6	5/8	83	13/8	DDF7	6/9	EC98U	8/8	GZ35	11/8	PCN48	19/3	UCH85	7/3	OA10	8/8		
BRAGY	9/-	6K7GT	1/8	12B6	5/8	83	13/8	DDF8	6/9	EC98V	8/8	GZ36	11/8	PCN48	19/3	UCH86	7/3	OA10	8/8		
5T4	8/-	6K4G	4/6	12E1	17/-	85A2	12/8	DDH3	5/6	EC98W	6/8	H30	5/-	PCN48	19/3	UCH87	7/3	OA10	8/8		
5U4G	4/6	6K8GT	8/-	12H6	1/6	90A4	6/8	DDH6	4/6	EC98X	6/8	H30	5/-	PCN48	19/3	UCH88	7/3	OA10	8/8		
5V4G	7/6	6K25	13/6	12J6GT	2/8	90A4	6/8	DH77	5/-	EC98Y	21/-	HAB08	10/-	PCN48	19/3	UCH89	7/3	OA10	8/8		
5Y3GT	5/3	6L1	9/8	12J7GT	7/8	90C4	12/8	DH81	25/11	EC98Z	3/3	H12	7/6	PCN48	19/3	UCH90	7/3	OA10	8/8		
6Y4	9/6	6L3G	6/8	12K1	7/8	90C4	12/8	DH82	25/11	EC98A	3/3	H12	7/6	PCN48	19/3	UCH91	7/3	OA10	8/8		
6Z3	19/6	6L6M	9/-	12K7GT	4/3	90C1	12/8	DH107	15/9	EC98B	4/6	H123	14/11	PCN48	19/3	UCH92	7/3	OA10	8/8		
6Z4G	7/-	6L7GT	4/6	12K8GT	9/-	10B3	18/8	DK32	9/8	EC98C	10/6	H123D	5/-	PCN48	19/3	UCH93	7/3	OA10	8/8		
6J9012	9/-	6L17	12/6	12Q7GT	4/6	1590Z	8/8	DK40	18/8	EC98D	10/6	H141	8/8	PCN48	19/3	UCH94	7/3	OA10	8/8		
6A7	9/-	6L18	7/8	12K47	7/-	181	13/8	DK91	5/-	EC98E	6/8	H133D	5/-	PCN48	19/3	UCH95	7/3	OA10	8/8		
6A8G	7/6	6L19	6/8	12K57	4/6	18B2T	34/11	DK92	5/-	EC98F	6/8	H133D	5/-	PCN48	19/3	UCH96	7/3	OA10	8/8		
6A8T	4/-	6L03	7/-	12K07	3/-	2158G	6/8	DK95	6/8	Bat. 1	1/6	HN309	26/2	PCN48	19/3	UCH97	7/3	OA10	8/8		
6A07	3/-	6L1D3	7/-	12K17	3/-	220B	10/6	DL33	7/3	Amer. 2/3	1/6	HV22	9/-	PCN48	19/3	UCH98	7/3	OA10	8/8		
6A05	2/9	6L1D2	15/7	12K27	5/8	301	20/8	DL35	7/3	EF54	3/8	IV3	5/8	PCN48	19/3	UCH99	7/3	OA10	8/8		
6A97	8/-	6N7GT	5/-	12K37	3/8	304	18/8	DL63	6/8	EF73	5/8	IV3	5/8	PCN48	19/3	UCH100	7/3	OA10	8/8		
6A15	8/8	6N19	18/9	12K47	8/-	305	13/8	DL68	17/8	EF90	4/3	IV4/500	5/8	PCN48	19/3	UCH101	7/3	OA10	8/8		
6A15	8/8	6N19	18/9	12K47	8/-	304	13/8	DL68	17/8												

EASY TO BUILD




AMATEUR RADIO EQUIPMENT

**CR 66 COMMUNICATIONS RECEIVER** ★ **A CODAR KIT TRIUMPH**

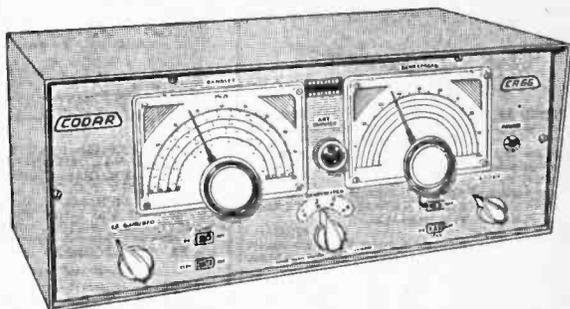**NOW... THE FINEST KIT EVER OFFERED!**


*This completely new Communications Receiver with its many design features and handsome styling offers more in performance and quality than many higher priced units.*



Frequency Range 540 Kc/s to 30 Mc/s in four Band-switched ranges. Separate Main Tuning and Electrical Bands spread. Entirely new design High "Q" ferrite cored Coils. Oscillator Coils fitted temperature compensated trimmers for stability. Coil Unit is wired and assembled, and with the I.F. Transformers is supplied factory aligned and tested. Low loss Trolax glass alkyl switch wafers. Controlled regenerative I.F. amp. for maximum gain and B.F.O. Panel Ant. Trimmer. Delayed A.V.C. Cathode follower output for tape recorder, etc. 3 watts output for external 2/3 ohm speaker. For panel slider switches. On-Off/Standby-Receiver/A.V.C. On-Off/Speaker On-Off Front Panel Silver and Black, control knobs Grey with Silver trim. Provision for EM 84 Signal strength indicator. Panel phone jack. Heavy gauge steel chassis, cadmium plated. Valve line-up: ECH81/EBF89/ECC81/EL84/EZ80. Instruction Manual, 17 pages. Cabinet size 16 x 6 1/2 x 8 3/4 ins. Silver Grey. For AC 200-250 volts. (Export and Marine Model 115 volts). Total cost of complete Kit, **£16.10.0** carr. 6/7. CR 66 Cabinet **£1.15.0** Signal strength indicator with EM84 **17/6** less Cabinet and Indicator

H. P. Terms available. Details on request.

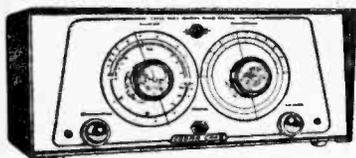**THE NEW CR 45** ★ **NEW STYLING TOP PERFORMANCE**



- ★ Tunes 10-2000 metres (5 Coils).
- ★ Separate electrical bands spread.
- ★ Three slow motion vernier drives.
- ★ Low loss polystyrene plug-in coils, factory aligned.
- ★ Dials calibrated in frequencies and degrees.
- ★ Power output 3 watts for 2/3 ohm speaker.
- ★ Valve line-up: ECC81/EL84/EZ80.
- ★ Front Panel Silver and Black, control knobs Grey.
- ★ Provision for panel phone jack.

Superb styling. World-wide reception. Total building cost, with 2 Coils, 25-75 and 60-175 metres. Instruction Manual 11 pages, less Cabinet

**£6.19.6** carr. 3/6.

CR 45 Cabinet Silver Grey, 12 x 5 1/2 x 7 in. sliding door for easy coil changing **27/6** Extra coils, all ranges **4/9** each.

ALL PARTS AVAILABLE SEPARATELY

★ **THE MINI-CLIPPER** ★

- ★ Tunes 10-2000 metres (5 coils).
- ★ Miniature 1 valve, all band receiver.
- ★ Low loss polystyrene plug-in coils, factory aligned.
- ★ Air spaced ball bearing condensers.
- ★ Provision to add two-transistor amplifier.
- ★ Battery lasts months.

**36/6**



Can be built in an evening, will receive Amateur and Broadcast stations from all parts of the world. Total building cost with one coil 25-75 metres, Instruction Manual 4 pages, 36/6, carr. 2/6. Extra coils, all ranges, 4/9 each. Electrical bands spread available. All parts available separately.

★ **THE SUPER CLIPPER** ★

- ★ Tunes 10-2000 metres (5 coils).
- ★ Large precision dial, dual slow motion drives.
- ★ Bands spread on all Bands.
- ★ High gain valve/transistor hybrid circuit.
- ★ 2 Mullard transistor amplifiers, pre-ass embled and tested.
- ★ Low loss polystyrene plug-in coils, factory aligned.
- ★ Batteries last months.

**88/6**



Easy to assemble, this top performing All Band Receiver brings a new world of listening pleasure to your finger-tips at low cost. Total building cost with 2 Coils, 20-60 and 55-190 metres, Instruction Manual 7 pages, 88/6, carr. 2/6. Extra Coils, all ranges, 4/9 each. Front Panel, Silver Grey, 10 x 7 1/2 in. 6/9.

Please note NEW address. We have now acquired new modern premises, combining all depts., offices and laboratories. New equipment under development will be announced in due course. Now available P.R.30 R.F. Preselector 1.5/30 Mc/s., greatly improves performance of any superhet receiver. CODAR Equipment is famous for Top Quality, Peak Performance and Easy-to-Follow Instructions—no guesswork. 6d. in stamps brings illustrated leaflets. Coming shortly, 70 watt 5 Band Transmitter Model No. CT80.

**CODAR RADIO COMPANY**

BANK HOUSE, SOUTHWICK SQUARE, SOUTHWICK, SUSSEX

G31RE

Canadian Distributors: JAYCO ELECTRONICS, TWED, ONT.

G31PA



**Volume Controls 80 ohm COAX**

Linear of Log Tracks Semi-air spaced (in.)  
Long spindles. Midget Stranded core  
3 K ohms to 2 Meg. 40 yds. 17/8 6d.yd.  
L.S. 3/-; D.P. 4/6; 60 yds. 25/-  
Stereo L/S 10/0; D.P. 14/6 Fringe Quality  
All spaced 1/yd.

**TELESCOPI CHROME AERIALS.** 13in. extending to 43in. 3/8 ea. Coax Adaptor Plug 1/8 extra.  
**TRIPLETERS** Bands I, II, III  
**COAX PLUGS.** 1/2. **OUTLET SOCKETS.** 2/-  
**PANEL SOCKETS.** 1/- **OUTLET BOXES.** 4/-  
**BALANCED TWIN FEEDER** yd. 6d. 80 or 300 ohms.  
**DITTO SCREENED** per yd. 1/6. 80 ohms only.  
**Wirewound Em. Speaker Control.** 10D 3/-, 25D 6/6.  
**WIRE-WOUND POTS.** 3 WATT. Pre-set Min. TV Types. All values to 10 ohms to 25 K., 3/- ea. 30 K., 60 K., 4/-; (Carbon 30 K. to 2 meg., 3/-).  
**WIRE-WOUND 4 WATTS Pots.** Long spindle. Value, 50 ohms to 50 K., 6/8; 100 K., 7/6.  
**PHILIPS TRIMMERS.** 0-10 pF. 3-30 pF. 1/2.  
**TRIMMERS.** Coramino, 30, 50, 70 pF., 9d.; 100 pF., 150 pF., 1/2; 250 pF., 1/8; 500 pF., 7/30 pF., 1/9.  
**IV etc. TRIMMER** 1000 pF. with knobs. 2/-.  
**RESISTORS.** Preferred values, 10 ohms to 10 meg., 1/2, 1/4, 1/8, 1/16, 1/32, 1/64, 1/128, 1/256, 1/512, 1/1024, 1/2048, 1/4096, 1/8192, 1/16384, 1/32768, 1/65536, 1/131072, 1/262144, 1/524288, 1/1048576, 1/2097152, 1/4194304, 1/8388608, 1/16777216, 1/33554432, 1/67108864, 1/134217728, 1/268435456, 1/536870912, 1/1073741824, 1/2147483648, 1/4294967296, 1/8589934592, 1/17179869184, 1/34359738368, 1/68719476736, 1/137438953472, 1/274877906944, 1/549755813888, 1/1099511627776, 1/2199023255552, 1/4398046511104, 1/8796093022208, 1/17592186044416, 1/35184372088832, 1/70368744177664, 1/140737488355328, 1/281474976710656, 1/562949953421312, 1/1125899906842624, 1/2251799813685248, 1/4503599627370496, 1/9007199254740992, 1/18014398509481984, 1/36028797018963968, 1/72057594037927936, 1/144115188075855872, 1/288230376151711744, 1/576460752303423488, 1/1152921504606846976, 1/2305843009213693952, 1/4611686018427387904, 1/9223372036854775808, 1/18446744073709551616, 1/36893488147419103232, 1/73786976294838206464, 1/147573952589676412928, 1/295147905179352825856, 1/590295810358705651712, 1/1180591620717411303424, 1/2361183241434822606848, 1/4722366482869645213696, 1/9444732965739290427392, 1/18889465931478580854784, 1/37778931862957161709568, 1/755578637259143234191136, 1/151115727451828468382272, 1/302231454903656936764544, 1/604462909807313873529088, 1/1208925819614627747057936, 1/24178516392292554941155712, 1/48357032784585109882311424, 1/96714065569170219764622848, 1/19342813113834043952924576, 1/38685626227668087905849152, 1/7737125245533617581169830304, 1/15474250491067235723396660608, 1/30948500982134471446793321216, 1/61897001964268942893486642432, 1/123794003928537885789737284864, 1/247588007857075771579474569728, 1/495176015714151543158949115456, 1/99035203142830308631791982291136, 1/1980704062856606172739596452224, 1/3961408125713212344467911044448, 1/7922816251442424688935822088896, 1/15845632502884849778671654477792, 1/31691265005769699557343113555584, 1/6338253001153391911467270271111136, 1/1267650600226678382293454442222272, 1/253530120045335676458688868444444448, 1/507060240090671352917377736888888896, 1/1014120480181342705834755555555552, 1/20282409603626854116707111111111104, 1/40564819207253708333414222222222208, 1/811296384145075166668844444444444448, 1/16225927682905133333768888888888896, 1/32451855365810266667537777777777792, 1/6490371072116205333351155555555555552, 1/1298074214432401066610222222222222208, 1/259614842886480213332044444444444448, 1/51922968577296042664088888888888896, 1/10384593715593608528177777777777792, 1/2076918743118721705635555555555555552, 1/415383748623744341127111111111111104, 1/830767497247488682244222222222222208, 1/166153499449497364488844444444444448, 1/3323069988989947289777777777777792, 1/664613997797989457955555555555555552, 1/132922799559597911911111111111111104, 1/26584559911919582222222222222222208, 1/53169119823839164444444444444444448, 1/10633823964767832888888888888888896, 1/2126764792953566577777777777777792, 1/425352958590713311555555555555555552, 1/85070591718142662222222222222222208, 1/17014118343628524444444444444444448, 1/34028236687257048888888888888888896, 1/6805647337451409777777777777777792, 1/136112946749028195555555555555555552, 1/272225893480563391111111111111111104, 1/54445178696112678222222222222222208, 1/10889035392224535444444444444444448, 1/21778070784449070888888888888888896, 1/4355614156889814177777777777777792, 1/871122831377962835555555555555555552, 1/174224562755932571111111111111111104, 1/34844912551186514222222222222222208, 1/69689825103573028444444444444444448, 1/13937965020714605688888888888888896, 1/2787593004142811377777777777777792, 1/557518600828562275555555555555555552, 1/111503720165712453111111111111111104, 1/22300744033142485222222222222222208, 1/44601488066284970444444444444444448, 1/89202976132569940888888888888888896, 1/1784059526513918177777777777777792, 1/356811905302783635555555555555555552, 1/713623810605567271111111111111111104, 1/14272476211131345444444444444444448, 1/28544952422262690888888888888888896, 1/5708990484452538177777777777777792, 1/114179808889050763555555555555555552, 1/228359617780101527111111111111111104, 1/45671923561621045444444444444444448, 1/913438471232244109088888888888888896, 1/18268768246448821817777777777777792, 1/365375364928976363555555555555555552, 1/730750729857952727111111111111111104, 1/14615014597159445444444444444444448, 1/29230029191518890888888888888888896, 1/5846005838303778177777777777777792, 1/116920116766615556355555555555555552, 1/233840233533211112711111111111111104, 1/46768046706642222444444444444444448, 1/93536093413284444888888888888888896, 1/1870721868265688977777777777777792, 1/3741443736531377777777777777777792, 1/748288747306275555555555555555555552, 1/149657749461251111111111111111111104, 1/29931549892250222222222222222222208, 1/59863099784500444444444444444444448, 1/11972619956900088888888888888888896, 1/2394523991380017777777777777777792, 1/478904798276003555555555555555555552, 1/95780959655200711111111111111111104, 1/19156191310400142222222222222222208, 1/38312382620800284444444444444444448, 1/76624765241600568888888888888888896, 1/1532495304320011377777777777777792, 1/306499060864002275555555555555555552, 1/612998121728004551111111111111111104, 1/12259962355600910222222222222222208, 1/24519924711200184444444444444444448, 1/49039849422400368888888888888888896, 1/980796988448007377777777777777792, 1/196159397689601475555555555555555552, 1/392318795379202951111111111111111104, 1/78463759075840590222222222222222208, 1/15692758151680118444444444444444448, 1/31385516303360236888888888888888896, 1/6277103260672047377777777777777792, 1/125542065213440955555555555555555552, 1/251084130426881911111111111111111104, 1/50216826085376382222222222222222208, 1/10043365170754276444444444444444448, 1/20086730341508552888888888888888896, 1/4017346068301711377777777777777792, 1/803469213660342275555555555555555552, 1/160693842721284545111111111111111104, 1/32138768544256909022222222222222208, 1/64277537088513818044444444444444448, 1/128555074171276360888888888888888896, 1/2571101483425527217777777777777792, 1/514220296684545445555555555555555552, 1/102844059336909109111111111111111104, 1/20568811867381818222222222222222208, 1/41137623734763636444444444444444448, 1/82275247469527272888888888888888896, 1/1645504949390545457777777777777792, 1/329100989878109091555555555555555552, 1/658201979756218183111111111111111104, 1/13164039595243636622222222222222208, 1/26328079190487273244444444444444448, 1/52656158380974546488888888888888896, 1/1053123167619409091777777777777792, 1/210624633523881818355555555555555552, 1/421249267047763636711111111111111104, 1/84249853409552727344444444444444448, 1/168499706819145454888888888888888896, 1/3369994136382909091777777777777792, 1/673998827276581818355555555555555552, 1/134799765455303636711111111111111104, 1/26959953091067272734444444444444448, 1/539199061821345454888888888888888896, 1/1078398123642909091777777777777792, 1/215679624728581818355555555555555552, 1/431359249457163636711111111111111104, 1/86271849891437272734444444444444448, 1/172543697828745454888888888888888896, 1/3450873956574909091777777777777792, 1/690174791314981818355555555555555552, 1/138034952262993636711111111111111104, 1/276069904525987272734444444444444448, 1/552139809051974545888888888888888896, 1/11042796180394909091777777777777792, 1/220855923607891818355555555555555552, 1/441711847215783636711111111111111104, 1/883423694431567272734444444444444448, 1/17668473888631345454888888888888888896, 1/3533694777726270909091777777777792, 1/706738955545254090915555555555555552, 1/141347791090508181831111111111111104, 1/28269558218101636366222222222222208, 1/56539116436203272734444444444444448, 1/1130782327324065454888888888888888896, 1/2261564654648130909091777777777792, 1/452312930929626181835555555555555552, 1/904625861859252363671111111111111104, 1/18092517237185272734444444444444448, 1/3618503447437054548888888888888888896, 1/723700689487410909091777777777792, 1/144740137897421818355555555555555552, 1/289480275794843636711111111111111104, 1/578960551589687272734444444444444448, 1/11579211031779365454888888888888888896, 1/2315842203359773090909177777777792, 1/463168440671954618183555555555555552, 1/92633688134391636366222222222222208, 1/185267376343783272734444444444444448, 1/3705347526875665454888888888888888896, 1/7410695053751330909091777777777792, 1/148213901150266181835555555555555552, 1/296427802300532363671111111111111104, 1/5928556046010647272734444444444444448, 1/11857112092021294545888888888888888896, 1/2371422418404258909091777777777792, 1/474284483680851781835555555555555552, 1/94856896736170356366222222222222208, 1/189713793473407137272734444444444444448, 1/379427586946814274545888888888888888896, 1/7588551738936364909091777777777792, 1/151771037787727381835555555555555552, 1/30354207557545467272734444444444444448, 1/60708415115090914545888888888888888896, 1/121416830230181835555555555555555552, 1/242833660460363667111111111111111104, 1/48566732092072734444444444444444448, 1/97133464184145467272734444444444444448, 1/1942669236829090917777777777777792, 1/388533847365818183555555555555555552, 1/77706769473163636622222222222222208, 1/155413538743267272734444444444444448, 1/3108270774865345458888888888888888896, 1/621654154973130909091777777777792, 1/124330830954261818355555555555555552, 1/248661661908523636671111111111111104, 1/4973233238170545458888888888888888896, 1/99464664763410909091777777777792, 1/198929329526818183555555555555555552, 1/39785865905363636622222222222222208, 1/79571731810727273444444444444444448, 1/1591434636214454548888888888888888896, 1/3182869272428909091777777777792, 1/636573854485781818355555555555555552, 1/12731477089715636366222222222222208, 1/25462954179151272734444444444444448, 1/5092590835830254545888888888888888896, 1/101851817182604909091777777777792, 1/203703634365209818183555555555555552, 1/40740726873041976366222222222222208, 1/8148145374608395272734444444444444448, 1/16296290749167804545888888888888888896, 1/3259258149833560909091777777777792, 1/651851629966712181835555555555555552, 1/13037032599334236366222222222222208, 1/2607406519866847272734444444444444448, 1/5214813039733694545888888888888888896, 1/1042962607967378909091777777777792, 1/208592521593475781835555555555555552, 1/41718504319687556366222222222222208, 1/8343700863937514545888888888888888896, 1/166874017277502909091777777777792, 1/333748034555005818183555555555555552, 1/667496069110011636366222222222222208, 1/133499213820023272734444444444444448, 1/26699842764004654545888888888888888896, 1/5339968552800930909091777777777792, 1/106799371056018618183555555555555552, 1/213598742112037236366222222222222208, 1/4271974842240745458888888888888888896, 1/85439496844814909091777777777792, 1/170878993696298181835555555555555552, 1/34175798739259636366222222222222208, 1/68351597478519272734444444444444448, 1/13670319497003854545888888888888888896, 1/2734063899400770909091777777777792, 1/546812779880154181835555555555555552, 1/109362559976030836366222222222222208, 1/21872511995206167272734444444444444448, 1/43745023990412324545888888888888888896, 1/8749004798082464909091777777777792, 1/174980095816492818183555555555555552, 1/349960191632985636366222222222222208, 1/699920383265971272734444444444444448, 1/13998407665319424545888888888888888896, 1/2799681533063884909091777777777792, 1/559936306612767818183555555555555552, 1/1119872633225555636366222222222222208, 1/2239745266451111272734444444444444448, 1/4479490532902222454588888888888888889

**FREE** THIS BOOK WILL INTEREST YOU!

LEARNING the PRACTICAL WAY

**A NEW-PRACTICAL WAY of UNDERSTANDING**

**Radiostructor**  
EQUIPMENT-COURSES

## Radio - Television - Electronics

Including: Transistors; VHF/FM, Hi-Fi equipment; Computers; Servo-mechs; Test Instruments; Photo-electrics; Nucleonics, etc.

**FOR ...Your Career...Your Own Business...An absorbing Hobby**

Radiostructor—an organisation specialising in electronic training systems offers a new self-instructional method using specially designed equipment on a "do-it-yourself" basis.

You learn by building actual equipment with the big kits of components which we send you. You advance by simple steps, performing a whole series of interesting and instructive experiments—with no complicated mathematics! Instructional manuals employ the latest techniques for showing the full story of electronics in a practical and interesting way—in fact—you really have fun whilst learning! Post the coupon below, now, for full details.—

**RADIOSTRUCTOR**  
**LEADS THE WORLD**  
**IN ELECTRONICS TRAINING**

**POST NOW**

To RADIOSTRUCTOR (Dept. G82)  
READING, BERKS.

Please send brochure, without obligation, to:—

★ Name \_\_\_\_\_

Address \_\_\_\_\_

8/63

★ BLOCK CAPITALS PLEASE  
(We do not employ representatives)

# Practical Wireless

Vol. XXXIX No. 678 AUGUST, 1963

Editorial and Advertisement  
Offices:

**PRACTICAL WIRELESS**

George Newnes Ltd., Tower House,  
Southampton Street, W.C.2.

© George Newnes Ltd., 1963

Phone: Temple Bar 4363

Telegrams: Newnes, Rand, London,  
Registered at the G.P.O. for trans-  
mission by Canadian Magazine Post.

## SUBSCRIPTION RATES

including postage for one year

To any part of the world £12.0

## Contents

	Page
Editorial ... ..	305
Round the World of Wireless ...	306
The Photophone ... ..	308
Signal Strength Comparator ...	312
The Kenilworth Public Address Amplifier ... ..	314
A Top Band R.T. Transmitter ...	322
7 Valve Stereogram ... ..	327
Transistorised Striplights ...	332
Test Gear Techniques ... ..	336
The Malvern Tape Recorder ...	342
On Your Wavelength ... ..	350
Semiconductors ... ..	353
Club News ... ..	358
Trade News ... ..	361
Letters to the Editor ... ..	362

The Editor will be pleased to consider articles of a practical nature. Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed to The Editor, PRACTICAL WIRELESS, George Newnes, Ltd., Tower House, Southampton Street, London, W.C.2. Owing to the rapid progress in the designs of wireless apparatus and to our efforts to keep readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in PRACTICAL WIRELESS is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. PRACTICAL WIRELESS incorporates "Amateur Wireless."

## The Bright Side

**I**N the July Editorial we briefly discussed some of the keys to successful construction. As a corollary it might be useful to consider some aspects of failure.

The average piece of equipment built by the average constructor (assuming that either of these really exist!) generally functions satisfactorily; if not at first, at least after eliminating initial troubles. But there are also the failures.

Among these are some that can never hope to be converted into workable apparatus. These are often experimental hook-ups in which the chances of complete success was a calculated risk. But there are also efforts so poorly constructed that the only real hope lies in complete reconstruction.

Readers with little experience or knowledge can take heart that even the most advanced enthusiast cannot deny his quota of monumental flops! It is understandably frustrating when the result of hours of work culminates in an infuriating collection of components that steadfastly refuse to co-operate and do the job they were assigned. But there is, strangely, a bright side to all this.

Just as troubles are said to be sent to try us, so it might be claimed that unsuccessful home-built equipment is sent to teach us. For no piece of apparatus fails to work for any sinister motive. There must be a logical reason. And the enthusiast who adopts a philosophical attitude, refuses to be flustered and is willing to probe, has the key to future success in his hands.

Most failures are a potential source of valuable information. In the case of the experimenter, he will have learned a good deal about the type of circuitry he has been trying out, and can either redesign and reconstruct on the lines suggested by the behaviour of his hook-up, or he can abandon the idea as impracticable. In either case he adds to his store of knowledge.

If a beginner has failed to build a piece of equipment from an already proven design he should think hard before considering stripping it down. Possible reasons are legion—dry joints, incorrect wiring, poor layout, faulty or inefficient components, etc.

In exploring the possibilities, a basic theoretical knowledge is obviously helpful, and for those likely to build more than an occasional item, a basic test meter and at least a rudimentary knowledge of its applications is essential.

It may be little consolation at the time, but when faced with a piece of equipment that refuses to work properly it is worth bearing in mind that although *everyone* makes mistakes, the range and extent of successful construction and design will be enhanced by learning the nature of these mistakes and not making the same ones twice!

Our next issue dated September will be published on August 7th



## NEWS AT HOME AND ABROAD

### Transatlantic Telephone Cable

THE first 600 nautical miles of the first direct submarine telephone cable between the U.S.A. and Britain is being laid by the G.P.O. cable ship HMTS Alert. Previous transatlantic cables have been made via Newfoundland, but this project (named TAT-3) joins Tuckerton, New Jersey and Widemouth, Cornwall, by a single cable link of 3,600 nautical miles—making it the longest in the world.

The cable for the TAT-3 project is being made by Standard Telephones and Cables Limited at Southampton. The cable will be laid by HMTS Alert and the American cable ship "Long Lines".

The TAT-3 cable system was designed in the Bell Telephone Laboratories and will provide 128 transatlantic voice circuits.

### BRITISH EQUIPMENT AT POLISH TRADE FAIR

FIFTY-SEVEN British firms exhibited at the 32nd International Trade Fair held recently at Poznan, Poland, and among the exhibits, EMI Electronics Ltd. had on show their instrumentation tape deck type TD4 which processes and stores information in analogue and digital forms. Another exhibit was the EMIac II analogue computer and a range of specialised valves and tubes was shown along with much tape and audio equipment.

## WAVELENGTH SELECTION FOR H.F. RADIO

THE Canadian firm of EMI-Cossor Electronics Ltd. have developed equipment to determine rapidly the optimum wavelength for long range h.f. radio communication. Previously, lengthy trial and error methods only were available to forecast the results to be expected on any particular short wave band, which are so much influenced by the structure of the ionosphere. The new device (Ionosonde model 8000) is designed for use with existing transmitter/receivers.

In use, one Ionosonde at one point commences pulse transmissions, the frequency of which is rapidly changed in a series of 128 logarithmic steps to cover the band from 1.8 to 28.8Mc/s. At another point a second Ionosonde has a receiver which similarly steps and tunes through the same frequency steps in synchronisation with the first equipment. In this fashion the entire band is covered in just two seconds.

Pulses received at the second equipment are shown on the face of a long persistence screen c.r.t. by one or more dots appearing on vertical lines. Reception will be best at frequencies where just a single dot occurs—indicating no multipath.

## Radio and Radar for New Airport

CONSTRUCTION on Kuwait's new International Airport has already begun eight miles from the city of Kuwait. As the airport will be capable of handling the latest jet aircraft, extensive radio and radar installations have been ordered. The contract for this equipment has been placed with a consortium formed by Marconi's Wireless Telegraph Company Limited and N. V. Philips Telecommunicatie Industrie.

This contract covers overall responsibility for the supply, installation and full commissioning of all radar, radio navigational aids and telecommunications equipment, together with the maintenance of the equipment during the first year of operation.

Equipment to be supplied by the Marconi Company includes airways surveillance and long range height-finder radars, together with display facilities for each. A Marconi v.h.f. direction finder will also be installed at the airfield. N. V. Philips Telecommunicatie Industrie are to supply h.t. transmitters and receivers, m.f. locator beacons, short range radio telephone system, mast, feeders and aerials, etc.

The total value of the contract exceeds £2½ million.

## CAMBRIDGE'S NEW RADIO TELESCOPE


A NEW radio telescope will shortly be in operation at the Mullard Radio Astronomy Observatory at Cambridge, adding greatly to the research being done by Professor Ryle and his colleagues of Cambridge University.

One movable and two fixed installations form the aerial system of the new telescope which has been financed by a grant of £542,000 by the Department of Scientific and Industrial Research. The three paraboloid aerials are mounted

in line, on an E-W axis, the two outermost aerials being separated by a maximum distance of one mile. The dish of each aerial is 60ft in diameter and can be steered individually, although normally all three will be controlled in unison from a central control.

When in use, the signals received by the three aerials will be recorded and then combined in an electronic computer at the University. The results obtained will provide information about the Universe which would require an aerial with a dish of about one mile in diameter, if a single installation were employed. Professor Ryle's three aerial system, however, obtains these results more economically and without the very exacting engineering problems that would arise with a single paraboloid. Nevertheless, the accuracies called for in the construction of the new telescope were of a very high order, and the half-mile railway track of the movable aerial, for example, has been levelled to an accuracy of  $\frac{1}{8}$  in.!

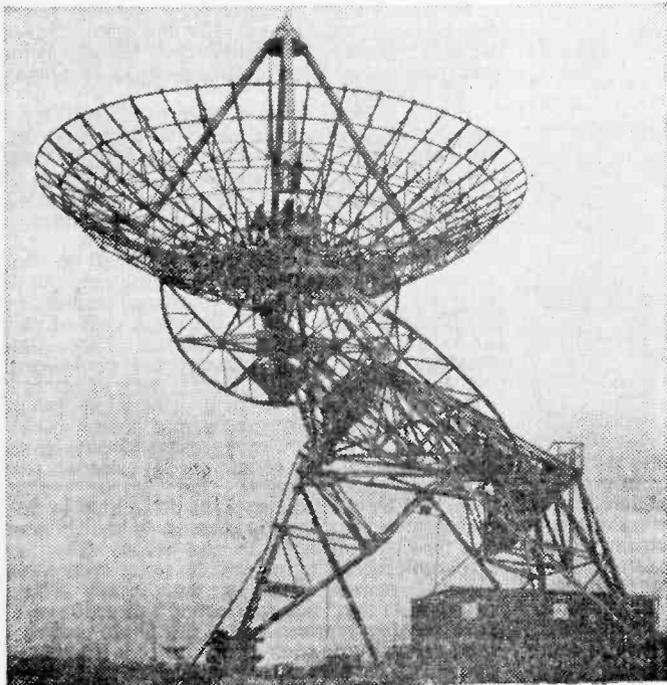The receivers and data recording equipment will be constructed by Cambridge University.



*This illustration shows the central, fixed aerial of the new radio telescope at Cambridge. Underneath this aerial is its control building and just visible above the skyline is the movable aerial.*

## NEW COPPER MICROWIRE IS GLASS INSULATED!

INSULATED copper "microwire", 50 times thinner than a human hair, is now being produced in this country and is finding many uses wherever micro-miniaturisation is necessary. The insulation used is a glass sheath around the wire, and this has been made possible by research into new techniques made by Glass Developments Ltd.

Some of the gauges of wire produced are so fine that they cannot be seen by the naked eye and a 100-mile length would weigh only 1lb. So flexible is the wire that it is possible to coil it round a pin without damaging the glass cover.

Quantities of the wire are being exported to the U.S.A. where earlier attempts to produce a similar wire proved unsatisfactory.

## Radar for Swedish Ships

RADAR equipments for four new vessels being built for a Swedish shipping firm, will be supplied by Associated Electrical Industries Ltd. Each ship will be fitted with two types of radar equipments, both designed and manufactured by the Electronic Apparatus Division of AEL.

## Stereophonic Transmissions

ALTHOUGH the BBC recently concluded the second series of field trials of the Zenith-G.E. pilot-tone stereophonic system, using the Wrotham Third Programme transmitter, test transmissions continue on Wednesdays, with programme transmissions from 11 a.m. to 11.30 a.m. and tone test transmissions from 12 p.m. to 12.30 p.m.

The fortnightly experimental stereophonic transmissions on alternate Saturday mornings using the television sound channel and the v.h.f. and medium wave band Network Three frequencies are also continuing.

# The PHOTOPHONE

By M. L. Michaelis

Experiments with  
light waves - a new  
interest for the amateur  
electronics enthusiast.

**L**IGHT is a form of electromagnetic radiation, in no way whatsoever different from ordinary wireless waves except for a difference of wavelength and frequency. Thus, whereas ordinary wireless waves occupy a spectrum from a fraction of a metre to some thousands of metres, representing frequencies from a few kc/s to some thousands of Mc/s, visible light occupies altogether higher frequency bands and much shorter wavelengths. Thus yellow light has a frequency of some 600 million Mc/s ( $6 \times 10^{14}$  c/s) and a wavelength of about half a millionth of a metre.

It is easy to understand why the wavelengths of visible light must be so short, once it is appreciated that the "transmitting aerials" are the tiny atoms themselves. The "receiving aerials" are, again atoms, normally special arrangements of these at the back of the human eye, which convert the energy of the incident light to corresponding *electric* signals going down the optic nerves to the brain.

This conversion of the energy of light, an electromagnetic radiation, into energy of electric currents in a receiving circuit is not only analogous to, but in fact *fully identical* to the function of a conventional wireless receiver.

Apart from the biological example of eyes, there exist purely electronic devices which "receive" light in this way, and these are called "photoelectric devices" or "photocells".

For various reasons beyond the scope of this article it is generally not practicable to frequency-modulate a beam of light for the purposes of transmitting intelligence along it in the usual manner, yet ordinary amplitude modulation is very easy indeed, even with the simplest mechanical or electromechanical devices.

All photocells give primarily a *d.c. output* which is a direct or logarithmic measure of the incident light intensity, this output therefore corresponding in every way to rectified carrier voltage at the detector-stage of an ordinary wireless set. In addition to this, all photocells give a greater or lesser *a.c. output* voltage corresponding to any amplitude modulation (intensity modulation) which the received light possessed.

## Types of Photoelectric Devices

Photocells may be divided, very roughly, into two major groups of types. The first group includes virtually all semiconductor devices (*all* diodes and transistors, in addition to those specifically intended as photo-elements).

If the barrier layer of any semiconductor is illuminated, a voltage is generated across the barrier, and the resistance of the barrier in the "non-conducting" direction is reduced. Both effects are always present *together* in any semiconductor, and either may be used for providing signals into the subsequent registering circuitry.


However, both effects may be small in those devices not intended for photoelectric use, and are fully removed in ordinary transistors and diodes, rectifiers, etc. by virtue of the black coat of paint or other opaque exterior coating. Those semiconductors specifically intended for photoelectric use are manufactured in such a way as either to enhance the barrier-voltage generation (photo-elements) or the barrier-resistance change (photo-resistors). Thus ordinary conventional photographic exposure meters use special selenium rectifiers as photo-elements, the barrier voltage generated by the incident light being able to drive sufficient current directly through a built-in sensitive moving coil meter to give usable deflections. A photo-resistor is operated in series with a high external resistor from a *d.c.* supply voltage polarised in the "non-conducting" direction of the pure rectifier represented by the photo-resistor in total darkness. As soon as the device is illuminated, the resistance falls correspondingly, and a current flows to give a voltage drop across the external resistance, giving a measure of the incident light intensity. Both photo-elements and photo-resistors may be built directly as transistors, giving amplified effects in the collector current.

A feature which all these semiconductor devices have in common, apart from excellent sensitivity at (relatively) low impedance—i.e. good *power* output—is their relative sluggishness. Thus, if the incident light is amplitude-modulated, an *a.c.* output at usable effective sensitivity is generally limited to the lower audio frequencies. This is connected with the time needed for the barrier-effects to take place, and is also due to the high capacity represented by the barriers in many devices. However, more recent research has produced some semiconductor photo-devices capable of operating at much higher frequencies.

The second major group of photoelectric devices is given by the true "photo-cells", which are vacuum or gas-filled cold-cathode diode valves.

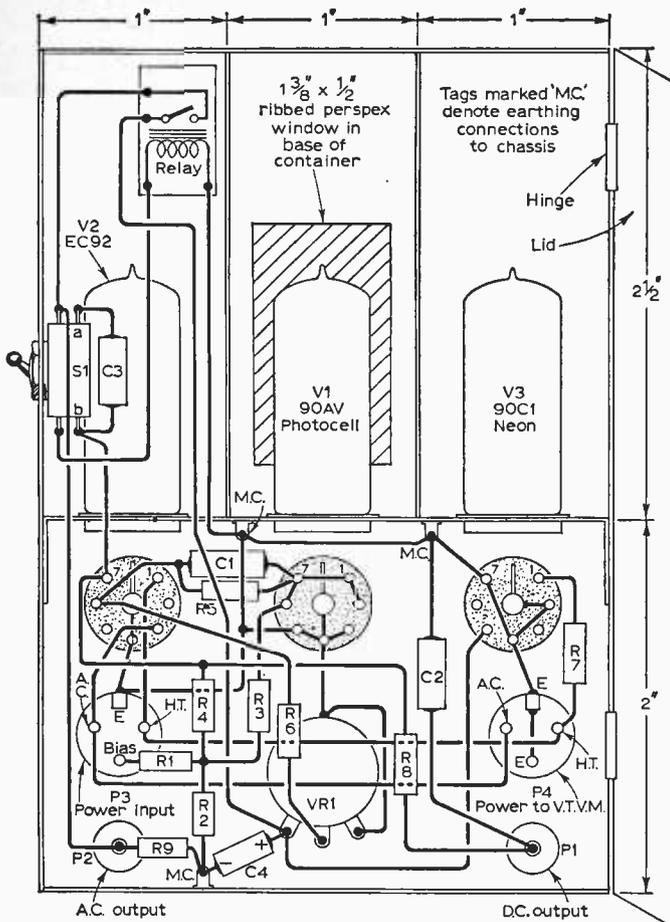The gas-filled types again have a limited frequency response, on account of times needed for ionisation and de-ionisation effects in the gas filling, yet they usually cover at least the full hi-fi audio-spectrum. However, due to secondary effects





Chassis dimensions  $4\frac{1}{2}$ " high x 3" wide x  $2\frac{1}{4}$ " deep. Material.....Tinplate  
 Fig. 2: The complete wiring diagram (valve bases shown 'detached' for clarity).

sufficient for this purpose, as shown in the practical circuit now to be described. This circuit is concerned with the vacuum tube photocell type 90AV, which is a small device of the usual shape and size of a miniature valve, on a B7G base, with the light-sensitive cathode vertical and so orientated that pin 4 of the base must face the incoming light.

#### Requirements for a Universal Circuit

From the above discussion of general practical principles, those design-features which would lead to a reasonably universal unit are already clear.

A unit for as many of the applications possible in general with photoelectric devices should be able to give d.c. and a.c. outputs over as high a range as possible, have excellent sensitivity, and it should have a linear light intensity/output voltage characteristic. It should be able to give d.c. outputs to a meter, for monitoring light intensity in the usual foot-candle units, also it should give an audio output for any ordinary audio amplifier-speaker unit, for uses in experiments with modulated-light transmissions. Finally, it should provide pulse

outputs for a digital counter, for counting light flashes, or for counting the number of times a steady beam of light is interrupted by passing objects (e.g. counting articles on a conveyor-belt).

A suitable circuit employing a vacuum photocell tube and a cathode follower power amplifier is both simple and cheap, and satisfies all of these requirements. Fig. 1 shows the theoretical circuit and Fig. 2 the wiring details and dimensions. It is seen that the whole unit, although being, together with its neon stabiliser, a three-valve circuit, can be built to a size little greater than a clenched fist. This unit has been, very aptly, called the "photophone".

#### Description of Circuit Function

The power supplies required for the photophone are fed in at P3, a four-pole (three-pole and casing as earth) socket such as found on the connection boards of Grundig (and some other makes) of tape recorders. These supplies are of the standard form: 6.3V a.c. heaters; 200-300V h.t.; and minus 100V bias.

The anode of the photocell, V1, is earthed direct to chassis, and the cathode fed negative from the bias supply. This gives a positive-going output voltage from R3, with a negative bias. The stabiliser neon V3, together with VR1, give a corresponding adjustable positive voltage. V1, V3; R5, R6 thus form a d.c. bridge circuit, those out-of-balance voltage is the signal applied to the grid of V2, the cathode follower power amplifier.

This bridge may be balanced under any conditions of illumination or darkness of V1, for various purposes as will become clear in the course of further discussion below, by means of suitable adjustment of VR1. The range of control of VR1 is definitely sufficient for enabling balance to be established for any intensity illumination of V1. The condition of balance (considering, for the present, S1 switched such as to make contact "a" and break "b", the condition labelled "Audio") is represented by grid pin 6 of V2 resting at chassis potential, zero, because the voltage selected at the slider of VR1 is of equal magnitude but opposite polarity to the voltage existing across V1. Under these conditions, the voltage drops across R5 and R6 always being equal, the centre point, to which the grid of V2 is connected, must be resting at zero potential. Apart from the slight difference caused by the grid base of V2, a sensitive moving coil meter or valve voltmeter connected to the d.c. output socket, P1 should read zero at the balanced condition. If a moving coil meter is used, then this should be a

### COMPONENTS LIST

#### Resistors:

R1	10k $\Omega$	R6	10M $\Omega$
R2	100k $\Omega$	R7	68k $\Omega$
R3	2.7M $\Omega$	R8	47k $\Omega$
R4	56k $\Omega$	R9	1M $\Omega$
R5	10M $\Omega$		
All $\pm$ 20%, 1W carbon.			
VRI 1M $\Omega$ carbon potentiometer linear.			

#### Capacitors:

C1	0.082 $\mu$ F paper 500V
C2	0.068 $\mu$ F paper 500V
C3	0.022 $\mu$ F paper 500V
C4	8 $\mu$ F electrolytic 350V

#### Miscellaneous:

V1	90AV photocell
V2	EC92 (6AB4)
V3	90CI neon
P1, 2	Miniature coaxial sockets
P3, 4	4-pole sockets
S1	Toggle switch, 1 pole on/off
Midget relay 3,000 $\Omega$ 10mA. Pointer knob.	
Tin box 3 x 4 $\frac{1}{2}$ x 2 $\frac{1}{4}$ in. approx. Three ceramic B7G holders.	

microammeter of about 250 or 500 $\mu$ A f.s.d. A centre-zero type should be used, or a reversing switch used. R8 automatically converts this meter into a suitable voltmeter. C2 smooths the d.c. output.

Greater sensitivity is obtained if a valve voltmeter is connected to P1. The output voltage is some 15V at P1 (positive) if the bridge was balanced with V1 dark, and an average pocket torch shone into V1 then at close range.

A valve voltmeter should have two ranges giving, when connected to the photophone at P1, a f.s.d. at 2.5V and at 25V. A suitable design for such an instrument will be included in the second part of this article.

#### Sensitivities

Using the dimensions shown in Fig. 2, with the specified components and voltages, and using all bright metal construction internally and the Perspex window, of the stipulated dimensions, ribbed but clear (i.e. not milky), half a volt of output voltage at P1 represents one foot-candle, to a good approximation.

If greater accuracy is required, calibration by comparison with a standard foot-candle meter is required. On a moving coil meter connected to P1, each 10 $\mu$ A deflection represents (approximately) one foot-candle illumination intensity reaching the window area of V1. The response is primarily to the blue component of the incident light, which is deliberate in the choice of valve type for V1, to match the response of photographic enlarging papers—as one of the primary uses for this function of the unit will doubtless be as a darkroom exposure meter for making photographic enlargements.

As will be familiar to photo enthusiasts, the sensitivity of a conventional exposure meter is seldom sufficient for such purposes, and the accuracy also often insufficient. Whilst photo-

graphically minded readers are reminded of the ultimate need to perfect final calibrations by means of trial exposures when first putting the unit into operation, some indication of the approximate conversion factors is here nevertheless useful. Thus an illumination of about one foot-candle on to many ordinary types of enlarging paper calls for an exposure time of about quarter of a second. Regarding films, if a scene is illuminated at intensity one foot-candle, the correct exposure on a film of 40 ASA speed will come out at about 2 to 3 seconds at stop f8. For other intensities, film speeds, stops, etc., the usual photographic conversion rules apply, so that no more need be said here.

#### Light Beam Interruption Counting

The second most important group of uses to which the average reader may wish to put a photoelectric head unit concern counting the number of times a beam of light is switched on or off, or causing any desired functions of switching or mechanical nature to be performed when a beam of light is interrupted.

A typical application is the counting of articles on a conveyor belt as they interrupt a beam of light by passing between the lamp and photocell. Here we require a voltage pulse output from the photoelectric head, of suitable character for operating a digital counter of the type, for instance, as published in PRACTICAL WIRELESS, February, 1962, and following issues.

On the other hand, the switching functions require a relay to operate in response to the changes of photoelectric current. For example, the relay can operate a motor to open a door when a person approaches and interrupts the beam of light across a passageway. However, we shall shortly see that the requirements for counting functions and operative mechanical functions turn out to be identical, both cases needing, primarily, a relay, it then being a matter of mere detail whether a digital counter or any other electro-mechanical device is operated by the relay.

TO BE CONTINUED

### HELP FOR HOME BUYERS

When you are buying or selling property it is vitally important to know where you stand as far as the law is concerned. Ignorance or carelessness might cost you hundreds of pounds. There's sure to be a big welcome, then, for the new FREE LEGAL ADVICE SERVICE just announced by Newnes *Property Advertiser and Holiday Guide*. Every week, from now on, this paper will carry questions and answers on such topics as mortgages, insurance, surveying and general legal points. In addition any reader may have his own particular questions answered by a panel of experts simply by filling in a Query Coupon on the Legal Advice Page. Newnes *Property Advertiser and Holiday Guide*, which contains details of thousands of houses, flats, shops, business and holiday addresses, is on sale every Friday, price 4d.

# SIGNAL STRENGTH COMPARATOR

*An S-Meter and Tuning Indicator*

BY J. LONGRISE

**E**XPENSIVE communication type receivers often feature an S-meter on the front panel, to provide an indication of the strength of the carrier of the transmission to which the receiver is tuned. This can be extremely useful for comparing the signal strength of one transmission with that of another and for observing how the strength of a particular signal varies throughout the day and night.

S-meters are used extensively by transmitting amateurs so that details of the received signal strength, of a station being worked, may be recorded and transmitted back to the operator in "standard" terms. Listeners on the short wave and amateur bands also find such meters useful for, apart from giving relative signal strengths, they can be employed for facilitating the adjustment and orientation of an aerial for optimum pick-up at one particular frequency or band of frequencies.

## Tuning Indicators

Ordinary receivers in the domestic class rarely provide a definite means of indicating signal strength. Early models sometimes have embodied a so-called tuning indicator. This may be a simple milliammeter which operates across an uncalibrated scale, the idea being to tune the set for maximum deflection.

More recent models have a magic-eye tuning indicator in which a fluorescent glow within the eye alters in width or shape depending upon the tuning of the station. In the past there have also been other forms of tuning indicators, some of which use ordinary low-voltage lamps or neon tubes for providing the indication in terms of light intensity.

All these methods, including the S-meter, have much in common, and that is they invariably work from the receiver's automatic gain-control (a.g.c.) line.

All modern receivers incorporate a.g.c., and there are two main ways of achieving this. The circuit in Fig. 1 shows the usual arrangement, where one of the two diodes in a double-diode-triode valve is employed exclusively for the production of a.g.c. bias.

Diode A is the ordinary detector diode, while diode B is the a.g.c. diode. To the latter is applied some of the i.f. signal from the anode circuit of the final i.f. amplifier valve V1, via a small coupling capacitor C1. This diode rectifies the signal and produces across its load resistor, R1, a d.c. voltage whose value is proportional to the amplitude of the i.f. carrier—the stronger the signal, the greater the voltage across R1.

Now, since the load is connected direct to the diode itself, the voltage developed is *negative* with

respect to the chassis side of R1. A negative bias is thus produced which goes more negative with increase in signal strength. The voltage is fed through the filter comprising R2 and C2—which eliminates residual i.f. signal no longer required—to the controlled valves in the receiver.

In Fig. 2 is shown the other method sometimes used to produce an a.g.c. bias. Here only one diode is used, and in the case of a double-diode-triode valve, the redundant diode is connected to chassis out of the way. However, there may be only a single diode in the valve (such as a diode-pentode) or a germanium crystal diode may be used.

The i.f. signal at the secondary of the i.f. transformer is fed direct to the diode (diode A) and voltage due to the rectified signal appears across R1 and R2 in series. These are really the detector load resistors, and the audio signal is filtered through the coupling capacitor C1 to the volume control—this capacitor isolating the d.c. component, of course.

The d.c. voltage across R2 is fed to the controlled valves through the filter made up of R3 and C2, as in the former example. There are various arrangements of these circuits, but the basic ideas given in the foregoing rarely differ in practice to any large extent.

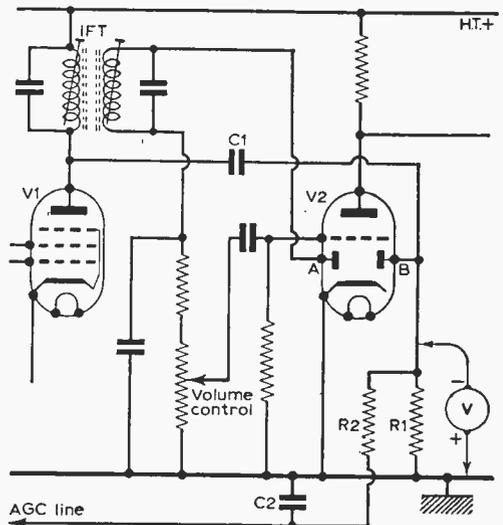


Fig. 1: In this circuit a separate diode (diode B) is employed for the production of an a.g.c. bias. Diode A is the ordinary detector diode.



# The KENILWORTH Public Address Amplifier

★ 10 Watt Output

★ 12 Volt Operation

BY S. GIBSON

★ 5 Transistor Circuit

**T**HIS 10W amplifier has been designed to obtain the highest performance from a transistorised circuit. The unit lends itself particularly to outdoor power amplifier use where a car battery is available. It should have particular appeal for organisers of fetes, garden parties, outdoor sports, political meetings and so on.

The electrical performance of the amplifier is good and there is no apparent distortion at full power—and, of course, there would be no mains hum when driven from a d.c. source. The unit can be made at a very reasonable cost and, as will be seen from the layout, it is of the simplest design from the constructional point of view. Indeed it would be possible for anybody with little or no previous experience of electronics to put this together. It is reasonably light to carry yet of a robust construction. Having transistors instead of valves, it should prove less prone to damage.

Before going on to a detailed construction

procedure the following is a stage-by-stage description of the circuit.

The amplifier requires a 12-14V d.c. supply. This input is controlled by the on/off switch S1, connected in the negative lead.


### First Amplifier Stage

The input signal is applied to the amplifier via a jack plug JK1 to one end of the gain control VR1. A simple potentiometer was chosen here because it was envisaged that a pre-amplifier would be designed later which could incorporate tone correcting network and matching circuits for various types of microphone or gramophone pick-up.

The signal from the gain control VR1 is passed via R1 and C1 to the base of Tr1, which is OC71. This transistor is used in a conventional amplifier circuit. Adequate decoupling from the next stage is obtained by R3 and C2.

Negative feedback from the secondary of the

Fig. 1: The circuit diagram.

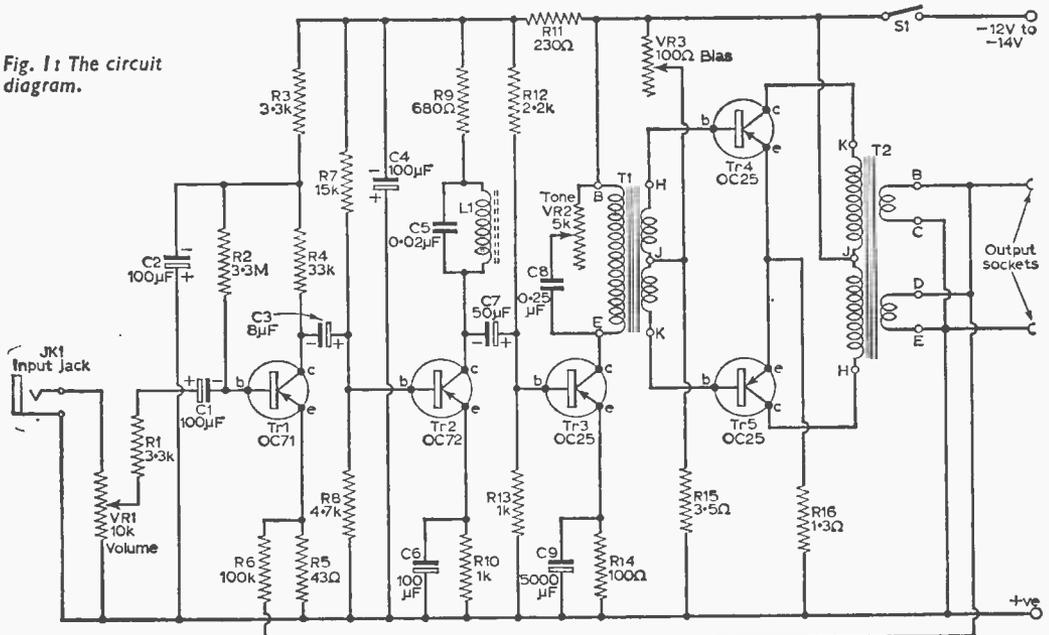

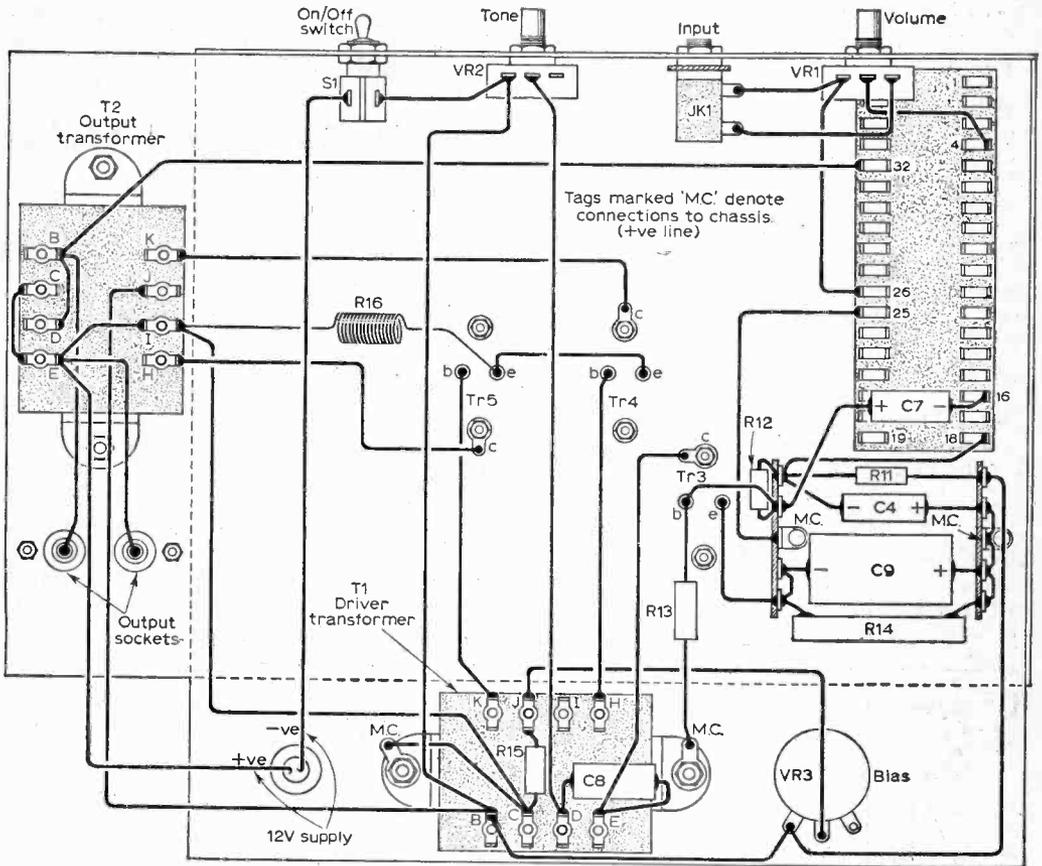


Fig. 2: The underchassis wiring diagram.

output transformer T2 is fed back to this stage via R6 and developed across R5. The values of these two resistors were determined by balancing the gain required and overall response of the amplifier. More negative feedback would in theory have given a better frequency response curve, but at the expense of gain.


**Second Amplifier Stage**

The second transistor Tr2 is an OC72 which acts as a pre-driver stage to boost the signal to the power transistors. R7 and R8 are the biasing resistors for Tr2. The emitter bias resistor R10 is bypassed by C6.

High frequency tone correction is provided in the collector load by the circuit consisting of a 10mH ferrite-cored L1 and the 0.02μF capacitor C5.

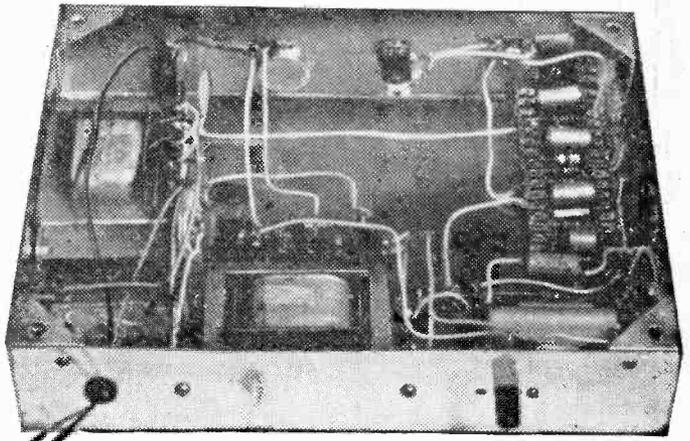**First Power Stage**

The first power stage employs an OC25, Tr3. The output from this stage drives the final push-pull output stage.



Right—This illustration gives an idea of the layout of the amplifier.



**RADIO-AMATEUR GEAR  
EDUCATIONAL KITS**



**TEST INSTRUMENTS  
HI-FI EQUIPMENT**

*With the clearly-written instruction manuals,  
anyone can build any of our models—  
and save money!*



**AMATEUR BANDS RECEIVER. Model RA-1.** Covers all Amateur Bands from 160 to 10m. Special features incl. half lattice crystal filter, 8 valves, signal strength "S" meter, tuned R.F. amplifier stage ... .. £39.6.6

**NEW!**



**"OXFORD" LUXURY TRANSISTOR PORTABLE. Model UXR-2.** The ideal domestic, car, or personal portable receiver. 10 Semi-conductors. Send for full details. £14.18.0

**NEW! 5W HI-FI MONO AMPLIFIER. Model MA-5.** A low-priced amplifier based on the S-33. Printed circuit construction makes it easy to build ... .. £10.19.6

**TAPE RECORDING/PLAYBACK AMPLIFIER. Stereo (TA-IS) £24.10.0** Monaural (TA-IM) ... .. £19.2.6

**STEREO CONTROL UNIT. USC-1.** Luxury model with inputs to suit any pick-up or tuner ... .. £19.10.0

**6W DE LUXE AMPLIFIER. Model S-33H.** An inexpensive Stereo-Mono amplifier, with high sensitivity. Suitable for Decca Deram cartridge ... .. £15.17.6

**6 TRANSISTOR PORTABLE. Model UXR-1.** Preamplified I.F. transformers, Printed circuit, 7 x 4in. high flux speaker. Real hide case ... .. £12.11.0

**SHORTWAVE TRANSISTOR PORTABLE. Model RSW-1** Two short bands, trawler and medium ... .. £19.17.6



**"MOHICAN" GENERAL COVERAGE RECEIVER. Model GC-U.** Fully Transistorised. Excellent portable or general purpose receiver for amateur or shortwave listening. See full spec. leaflet. £39.17.6.



**HI-FI F.M. TUNER.** Tuning range 88-108 Mc/s. Tuning unit (FMT-4U) with 10.7 Mc/s. I.F. output (£2.15.0 inc. P.T.). I.F. Amp. (FMA-4U) complete with cabinet and valves. (£12.6.0). Total ... .. £15.1.0

Assembled models also available, prices on request — Deferred terms available over £10. Free Delivery U.K.

**SEND FOR FREE BRITISH CATALOGUE — OVER 50 MODELS TO CHOOSE FROM**

**AVAILABLE SHORTLY!**

**MONO CONTROL UNIT. Model UMC-1.** Suitable for cabinet mounting or free-standing. Ideal for use with MA-12 or similar amplifier requiring 0.25 v. or less for full output ... .. £8.12.6



S-33

**HI-FI EQUIPMENT CABINETS.** Large range, in kit form or assembled and finished, available to meet various needs. Details on request ... .. from £6.19.6 to £29.8.0

**PORTABLE SERVICE OSCILLOSCOPE. Model OS-1.** Compact portable scope, ideal for servicing and general work. Printed circ. Case 7 3/4 x 4 1/2 x 12 1/2 in. long. Wt. only 10 1/2 lb. £19.19.0

**5in. OSCILLOSCOPE. Model O-12U.** Wide band amplifiers essential for TV servicing, F.M. alignment, etc. T/B covers 10 c/s-500 kc/s in 5 ranges ... .. £38.10.0

**VALVE VOLTMETER. Model V7A.** Measures up to 1,500 volts (D.C. and R.M.S.) and 4,000 pk. to pk. Res. 0.152-1,000MΩ £13.18.6

**6 W STEREO AMPLIFIER. Model S-33/3** w/chl. Inputs for radio-tape-gram. Stereo. Mono ganged controls. Sensitivity 200 mV. £13.7.6

**HI-FI 18 W STEREO AMPLIFIER. Model S-99.** Ganged controls. Stereo/Mono model, radio and tape recorder inputs. P/B selection. £27.19.6

**HI-FI A.M./F.M. TUNER.** Covers F.M. 88-108 Mc/s. A.M. 16-50, 200-550, 900-2,000 m. Tuning heart (£4.13.6 inc. P.T.) and I.F. Amp. (£20.13.0). Printed circuit board. Total ... .. £25.6.6

**HI-FI SPEAKER SYSTEM. Model SS-U.** Two speakers in ducted port bass reflex cabinet. Bookcase model £10.17.6. Legs 1 1/2 extra.

**MULTIMETER. Model MM-1U.** Ranges: 0-1.5 v. to 1,500 v. A.C. and D.C. 150 μA—15A D.C. 0.2Ω to 20MΩ. 4 1/2in. 50μA meter ... .. £12.10.0

**R.F. SIGNAL GENERATOR. Model RF-1U.** Up to 100 Mc/s fundamental, 200 Mc/s on harmonics. Up to 100 mV output all bands ... .. £12.15.6



DX-40U


**250**

**AMERICAN HEATHKIT MODELS**

Full details of direct Mail Order Scheme and catalogue can be obtained from us for 1/- post paid. (FREE to Service Departments.)

**AMATEUR TRANSMITTER. Model DX-40U.** Self-contained. 80-10 m. Power input 75 w. CVV., 60 w. peak C.C. phone. Output 40 w. to aerial. Provision for V.F.O. ... .. £33.19.0

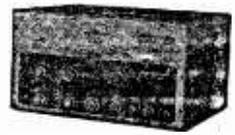**AMATEUR TRANSMITTER. Model DX-100U.** Covers all amateur bands, 160-10 m. 150 w. D.C. input, self contained with power supply. Modulator, V.F.O. £74.19.0



DX-100U

**DAYSTROM LTD.**

Dept. P.W.8, GLOUCESTER, ENGLAND.

A member of the Daystrom Group, manufacturers of the  
WORLD'S LARGEST-SELLING ELECTRONIC KITS

Send me **FREE BRITISH CATALOGUE** (Yes/No)

Full details of model(s) \_\_\_\_\_

NAME \_\_\_\_\_


ADDRESS \_\_\_\_\_

PV8

**INEXPENSIVE  
BASIS OF  
A COMPLETE  
HI-FI SYSTEM  
OR TOP QUALITY  
RADIOGRAM**


*Armstrong*

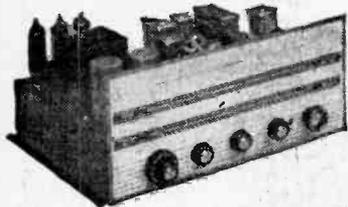**STEREO 55  
TUNER AMPLIFIER  
CHASSIS**



One compact chassis combines AM and FM tuners, Stereo Control Unit and two High Fidelity Amplifiers. For mono reproduction the two amplifiers are used together so that up to 10 watts output is available. Provision for tape recording and play back is made with a choice of inputs for crystal or ceramic pick-ups including the Decca Deram. The facilities are also available for use with a tape deck and its associated pre-amplifier.

PRICE ..... £29.18.0

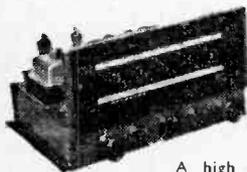

**AF 208 AM/FM  
CHASSIS**

A high quality tuner amplifier chassis which can be used for the conversion of an existing radiogram or as the basis for building a new radiogram or reproducing system. A system which can include tape recording and play back as well as the normal AM and FM radio and record reproduction.

PRICE ..... £21.4.0

Write for descriptive literature to

**ARMSTRONG** (Dept. PAC.)  
Warlters Road, London, N.7. Tel: NORth 3213

**ADAMIN—  
by LITESOLD**



These new ADAMIN micro soldering instruments supplement the well-known LITESOLD models for special applications and still further extend our very comprehensive range of specialised soldering equipment. Bit sizes now  $\frac{1}{16}$  in. to  $\frac{1}{4}$  in.

**A NEW ADAMIN MAINS MODEL**

The C10L (shown on bench stand) is probably the smallest mains voltage model in the world. Bit dia.  $\frac{3}{32}$  in., length 7 in., weight 1oz. (less flex). Heats in 30 secs.

Brochure No. S10 sent free on request.

Sole proprietors and manufacturers:  
**LIGHT SOLDERING DEVELOPMENTS LTD**  
28 Sydenham Road, Croydon, Surrey

Phone: CROydon 8589

Grams: Litesold Croydon

*OSMOR*

**PRICE LISTS & INFORMATION ON  
Various Designs in**

Practical | Radio | Wireless | R.S.G.B.  
Wireless | Constructor | World | Bulletin

SEND 6d. POSTAGE FOR



**CIRCUITS**

**OSMOR LTD**

418 BRIGHTON ROAD  
S. CROYDON SURREY  
Telephone CRO 5148

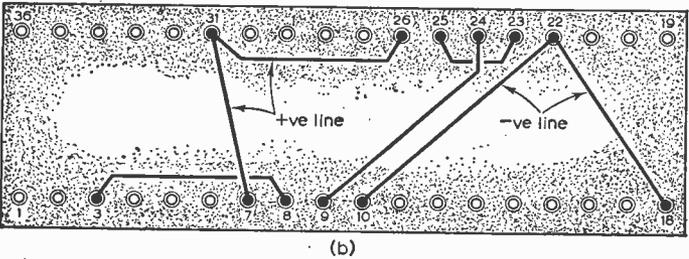
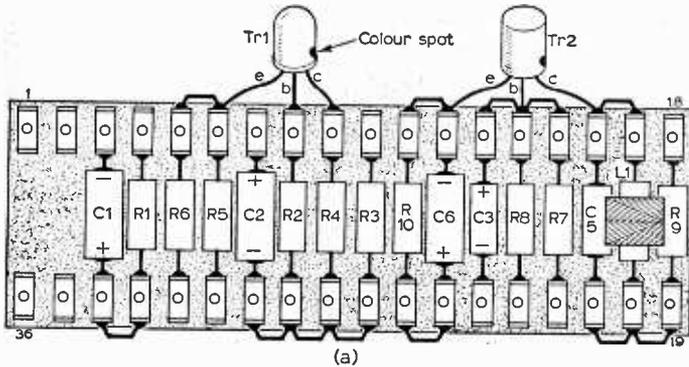


Fig. 4: Above and below views of the tag panel.

and two 6B.A. holes. The on/off switch requires a  $\frac{1}{2}$  in. hole. Otherwise all holes are 6B.A. or 4B.A. clearance.

The dimensioning of the three power transistors calls for some comment.

On the drawing (Fig. 3) the makers exact measurements have been used, but these are in millimetres. Similarly the size of all the holes marked C is given as 4mm. Conversion of course is easily done as 25.4mm equals 1 in. A  $\frac{3}{16}$  in. or a 4B.A. clearance drill may be used for the holes marked C.

**Step II—Wiring up Tag Panel**

The main 18-way tag panel carries most of the components for the first two transistor stages. Fig. 4(a) shows the layout on the top of the tag panel, and Fig. 4(b) the underside wiring connections. This should present no difficulties if this layout is followed carefully. There is an exception here, in as much as R9 should only be soldered to one tag until the tag strip has been mounted on the chassis. This is necessary in order to get at the nut securing the tag strip in position on the chassis.

Care should be taken in soldering the transistor leads. P.V.C. sleeving about  $\frac{1}{4}$  in. long should be pushed on each transistor lead. The leads should not be shortened but soldered in as they are. A pair of pliers should be used to grip the leads between the soldering iron and the transistors. Soldering should be done as quickly as possible. The pliers will carry the heat away and the procedure will tend to protect the transistors OC71 and OC72.

Fig. 4(b) shows the underside wiring. This is in

fact best done first using 22s.w.g. tinned copper wire and 1mm sleeving.

**Step III—Assembly of Parts to Chassis**

Method of assembly of the parts on the chassis allows for individual preference, but the following is a pretty logical sequence.

First, the power transistors Tr3, Tr4 and Tr5. Fig. 6(a) gives the connections to the OC25, power output transistors. Two stiff leads project through the mounting base. These can be identified as the base and emitter connections by reference to Fig. 6. The collector is electrically connected to the mounting base. Collector connection later is made to a tag which is held in contact with the top of the mounting base by one of the mounting nuts. Each OC25 transistor is insulated electrically from the chassis by a mica washer and two bushes. The chassis acts as a heat sink and the mica washer is so thin that it gives minimum thermal insulation. Two 6B.A.  $\frac{1}{4}$  in. or  $\frac{1}{2}$  in. screws and nuts are used to clamp the transistors using the insulating bushes.

The 18-way tag panel which was assembled under Step II can next be assembled to the chassis. It is held by two 6B.A. screws with

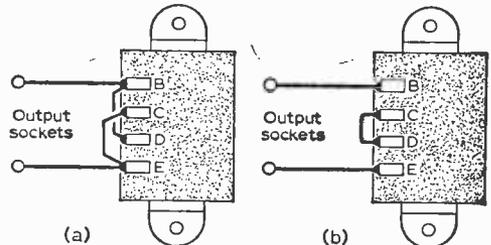


Fig. 5: Output transformer connections for (a) a 3Ω loudspeaker, (b) a 15Ω loudspeaker.

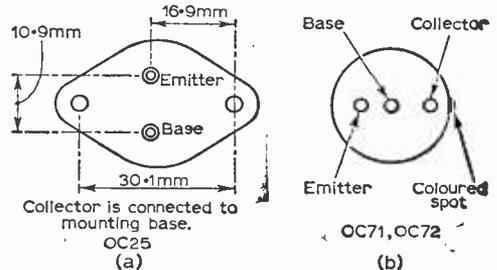


Fig. 6: Transistor connection details.

two ¼ in. spacers or two 6B.A. nuts to keep it away from the chassis.

The three potentiometers, VR1, VR2 and VR3, on/off switches, input jack JK1 and the output sockets can now be assembled to the chassis. The rubber grommet carrying the supply lead into the chassis is fixed in the appropriate ¼ in. hole.

Next the two 5-way panels carrying in due course R11, C4, C9, R14 and R12 can be screwed to chassis by one 4B.A. screw and nut each.

Finally, the two transformers can be bolted to the chassis by the four 4B.A. screws and nuts with a 4B.A. solder tag under each nut in the case of T1.

#### Step IV—Wiring the Circuit

The 18-way tag panel was wired up in Step II except that R9 was only soldered to one tag

#### COMPONENTS LIST

##### Resistors:

R1	3.3kΩ	R9	680Ω
R2	3.3MΩ	R10	1kΩ
R3	3.3kΩ	R11	230Ω
R4	33kΩ	R12	2.2kΩ
R5	43Ω	R13	1kΩ
R6	100kΩ	R14	100Ω 3W w-w
R7	15kΩ	R15	3.5Ω 3W w-w
R8	4.7kΩ	R16	1.3Ω 3W w-w

All 10% 5W carbon, unless otherwise stated.

VR1	10kΩ carbon potentiometer
VR2	5kΩ carbon potentiometer
VR3	100kΩ wire-wound potentiometer

##### Capacitors:

C1	100μF electrolytic 12V
C2	100μF electrolytic 12V
C3	8μF electrolytic 12V
C4	100μF electrolytic 12V
C5	0.02μF paper
C6	100μF electrolytic 12V
C7	50μF electrolytic 12V
C8	0.25μF paper
C9	5,000μF electrolytic 6V

##### Transformers:

T1	Driver transformer (Repanco TT23)
T2	Output transformer (Repanco TT24)

##### Transistors:

Tr1	OC71	Tr4	OC25
Tr2	OC72	Tr5	OC25
Tr3	OC25		

##### Other Circuit Components:

L1	10mH choke (Repanco CH2)
JK1	Jack socket (Radiospares)
S1	On/off toggle switch s.p.d.t.

##### Miscellaneous:

Two-way output socket panel. Two control knobs. Three mica washers (Mullard 56201B) and six insulated bushes (Mullard 56201A). One eighteen-way miniature tag panel. Two 5-way tag strips. Chassis 10in. x 7½ in. x 2¼ in. Quantity of 4 or 6 B.A. screws, nuts and solder tags.

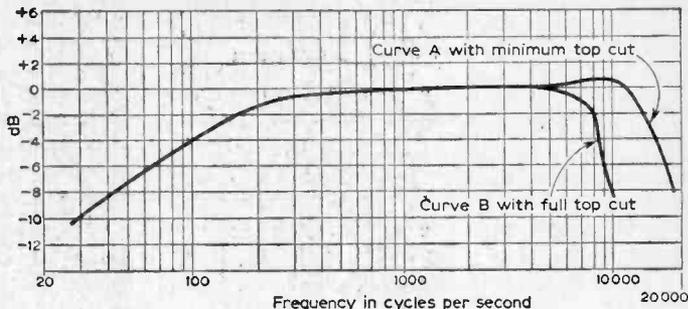


Fig. 7: Response curves.

until after assembly to the chassis; the other lead of R9 can now be soldered to the tag.

The input jack is wired to the volume control potentiometer VR1 and connections made to the appropriate points on the tag panel as shown on the wiring diagram.

Wiring of the power stages according to the wiring diagram and layout diagram should present no difficulties. Care should be taken to solder the leads to the base and emitter tags of Tr3, Tr4 and Tr5 as quickly as possible. This will avoid damaging the transistors.

Connection of the output transformer T2 (Repanco TT24) will vary according to whether a 3Ω or 15Ω loudspeaker is being used. Fig. 5 shows the connections for both these impedances. For a 3Ω loudspeaker the split windings of the secondary are connected in parallel, that is E and C are connected and the loudspeaker is connected across B and E.

For 15Ω output C is connected to D and the loudspeaker is across B and E.

R16 is given as 1.3Ω wire-wound. This resistor acts as a stopper or protection device for the OC25's to prevent thermal runaway. The value was set at 1.3Ω as that which would cause the circuit to operate in Class A condition. Probably the easiest way to obtain the 1.3Ω is to wind it if there is a meter for measuring resistance available. The value is not too critical say within 0.3Ω. Two 3Ω resistors in parallel would also be satisfactory.

#### Operating Conditions

As has been explained this amplifier has been set to operate in Class A, since this gives the best possibility of reducing any distortion. However this does mean that there is a high quiescent current. The quiescent current of the amplifier under Class A conditions is 600mA, and VR3 was adjusted to obtain this figure. This control can also be adjusted to give a condition approaching Class B with the current in the quiescent conditions between 250 to 375mA. This, of course, means that there is less drain on the d.c. supply.

Under the Class A condition the quiescent current is 600mA as stated and the current for full power output is 1.2A. Current to the final stage is 100-150mA for each OC25 of the output stage.

The supply required is 12V d.c. and mains operated supply units to give this voltage at 1.2A are available, although it is envisaged that a unit

of this kind to go with this amplifier will be designed in due course. As stated previously, an ordinary car battery gives this order of current without difficulty for a long time and the amplifier was designed with this fact in mind. Where complete portability is required away from a mains unit (if available) or from a car battery, it would be possible to operate the amplifier for a short time from lantern batteries. In this case when not in use the amplifier should be switched off to allow the batteries to recover. According to the state of charge of a car battery, the voltage may vary up to 14V and the amplifier will accept this input.

### Performance

As has been explained the negative feedback has been adjusted to give a balance between gain and performance, and Class A conditions for the amplifier should bring operation under best conditions from the point of view of distortion.

The variable resistor VR2 provides a tone control adjustment by giving a varying degree of top cut. The effect of this is shown on the approximate response curves in Fig. 7 which give an indication of the response with the top cut at a minimum (curve A) and with full top cut in operation (curve B).

The -3dB points with no top cut are approximately 150c/s and 14,000c/s; with all the top cut in circuit the -3dB points are approximately 150c/s and 8,000c/s. These figures are approximate but give an indication of the

performance. For public address systems the frequency response of 150c/s to about 8,000c/s is in fact a desirable range of frequency reproduction.

Response figures apart, the proof of the amplifier is in the listening, and all those who have listened to this amplifier have found it very acceptable.

### Conclusion

Having completed the amplifier and adjusted it to obtain the required conditions, the remaining operation in the design as it stands is to make the bottom cover. This cover consists of a piece of 18 gauge aluminium sheet cut to approximately 7½ in. x 10 in. A piece of insulating paper is glued on the aluminium sheet on the side facing into the chassis to prevent any possibility of touching the tags on the driver and output transformers; this insulating paper should be approximately 5½ in. x 8 in. in size.

This bottom plate is fixed in position by four plastic-headed fixing buttons. These fixing buttons are not easy to obtain but are often held in stock by motor dealers because they are widely used for attaching panels and the like in motor cars. A quarter-inch hole is drilled through the corner supports on the chassis and a similar hole in each corner of the bottom plate. These fixing buttons can be levered out with a screwdriver and being very springy will click into position again very easily.

With the completion of this bottom plate the amplifier is finished and ready for use. ■

## Signal Strength Comparator

—continued from page 313

plastic case, such as one of these sold by popular stores as sandwich containers. A metal case should not be employed on account of the danger that may arise when used with a "live" chassis type of receiver.

The circuit is perfectly straightforward, and a Mullard OC71 transistor is connected in the "earthed-emitter" mode. The collector load is formed by R3, R4 and R5 in conjunction with a milliammeter of 1mA f.s.d. The emitter is connected to battery positive through a 470Ω resistor which provides stabilisation, and the instrument is operated from a 3V battery, such as two 1.5V cells in series.

The a.g.c. line voltage is applied to the base through the sensitivity control R1, and C1 clears all traces of residual i.f. signal from the base circuit.

With the instrument connected to the a.g.c. line of a receiver and with the instrument and receiver switched on (the latter with the aerial disconnected) the milliammeter should be set to zero current by adjusting the "set zero" control R3.

The aerial should then be connected to the receiver and the strongest possible signal tuned in. This will cause the milliammeter to deflect, and the extent of deflection can be controlled by the "sensitivity" control R1. This should be adjusted to give almost full-scale deflection.

Thus, relative to zero and f.s.d., the milliammeter can be calibrated as required in terms of signal strength units or decibels. ■

## Handbooks for Enthusiasts!

GET  
YOUR  
TODAY




Practical!  
Authoritative!

- ★ **TRANSISTOR RADIO CIRCUITS.** Constructional details of receivers, basic principles and servicing.
- ★ **TEST GEAR FOR AMATEURS.** Constructional details of many signal generators and other test instruments.

3/6 EACH

FROM NEWSAGENTS AND BOOKSTALLS

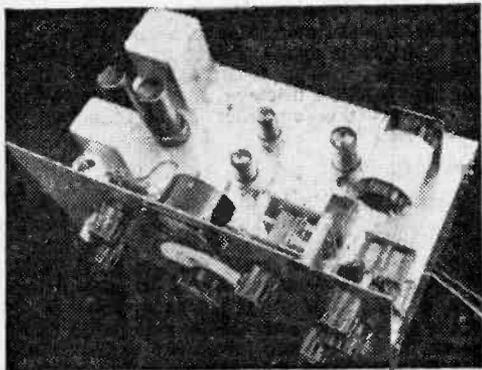

# A Top Band R.T. Transmitter

By G3OGR

**T**HIS transmitter is intended for use in the 1.8-2Mc/s band, and can be operated by a licensed amateur at the full permitted input of 10 watts. A push-pull modulator is incorporated, designed for use with a crystal microphone, and this gives very satisfactory modulation and speech quality. The transmitter is controlled by a variable frequency oscillator (v.f.o.) so that it can be operated anywhere in the band, and no frequency crystals, as required for a crystal-controlled transmitter, are necessary. A separate power pack is used.

### The R.F. Section

Fig. 1 shows the complete r.f. section of the transmitter. V1 is the v.f.o. tunable from 1.8—2Mc/s. This stage employs series tuning, with a high slope pentode, and if construction is rigid, sufficient frequency stability is obtained. VC1 is the v.f.o. tuning capacitor.

V2 is a pentode buffer, and VR1 allows the output of this stage to be adjusted, to secure correct grid drive to the power amplifier. No tuned circuits are used between V1 and V2, and the anode circuit of V2 is broadly resonant at about 1.9Mc/s. This arrangement avoids any need for tuning the buffer stage, and 4mA p.a. grid current, which is more than adequate can be obtained throughout 1.8—2Mc/s.

For the power amplifier, a 6BW6 is used. In

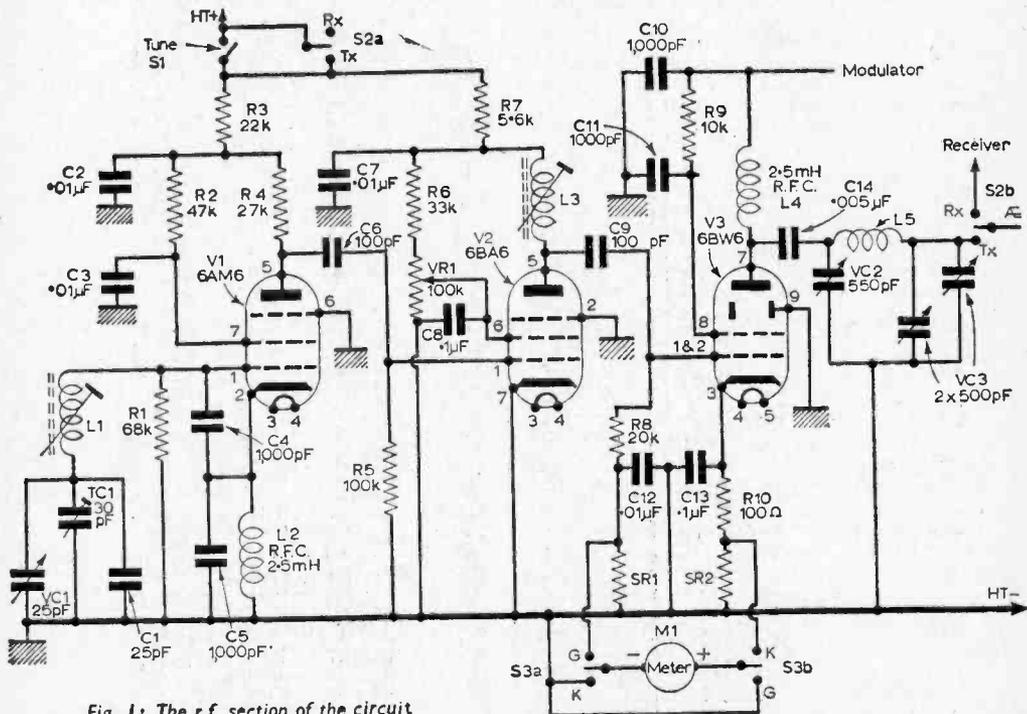


Fig. 1: The r.f. section of the circuit

such equipment, a 5763 is often fitted, but the 6BW6 was found satisfactory, and can easily be loaded up to full input. Should a 5763 be to hand, it may be used by wiring the holder to suit. Operating bias is obtained in the usual way by voltage drop across the grid resistor. The 100 ohm cathode resistor furnishes protective bias, limiting anode current in the absence of grid drive, or when the stage is off tune.

The popular type of  $\pi$  output circuit allows the transmitter to operate into many kinds of end-fed aerials. For other aerials, a small aerial tuner can be used as a separate unit.

When the "Tune" switch is closed only the v.f.o. and buffer stages are operating. This allows the v.f.o. to be adjusted to the required frequency by

corresponds to about 40V bias across the 20k $\Omega$  grid resistor.

With the meter switched to show cathode current, aerial loading is adjusted, as explained later, to obtain a reading of about 40mA, with a 250V h.t. supply. This indicates  $250 \times 0.04$ , or 10 watts. As the meter reads the combined cathode current, there is a slight safety margin against exceeding the 10W limit.

**Modulator**

Fig. 2 shows the modulator circuit. V4 is a double triode, with an r.f. filter in the microphone circuit (R11 and C15). With the crystal microphone used, adequate modulation was obtained, so the cathode by-pass capacitor was omitted from

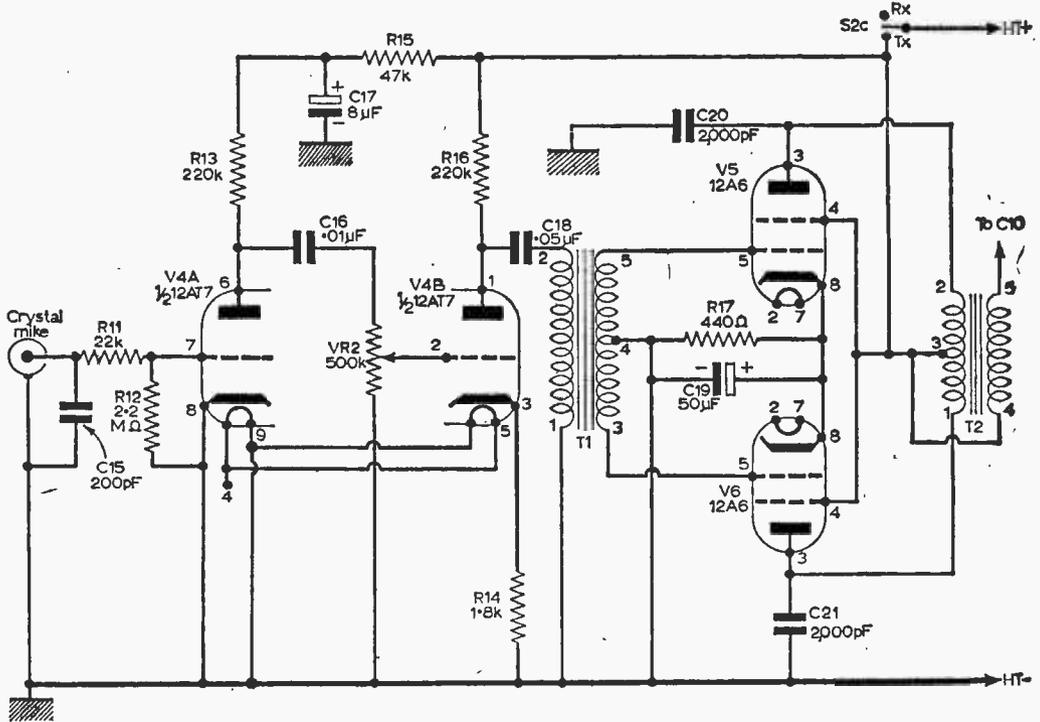


Fig. 2: The modulator stage of the circuit.

listening for the carrier on the station receiver. The p.a. grid drive may also be adjusted by VR1, if necessary.

The "Transmit-Receive" switch S2 controls the transmitter, switches the aerial from receiver to transmitter, and also silences the receiver loud-speaker, if necessary. When working, this gives single knob control of the station, for easy changing from transmit to receive.

A single meter M1, with switch S3, reads grid and cathode current. R.F. output is not much influenced by quite large changes in grid current, but begins to fall off with less than 1mA. VR1 is thus adjusted to obtain between 1.5mA and 2.5mA grid current, as shown by the meter. Here, 2mA

the second triode. If more gain is required, for a microphone with a lower output, a 25 $\mu$ F capacitor may be wired in parallel with R14.

Two 12A6's are used in the modulator, as these are easy to obtain and inexpensive, and originally employed in equipment using the surplus modulation transformer. These valves have 12.6V heaters, so they are run from a small 12.6V heater transformer.

Other small output pentodes or tetrodes, able to deliver some 5 watts or so in push-pull, would be satisfactory. The modulating impedance of the p.a. (V3) is approximately 6,200 ohms. The optimum load for various output valves other than the 12A6's may be found from valve data,

## COMPONENTS LIST

## Resistors:

R1	68k $\Omega$	R10	100 $\Omega$
R2	47k $\Omega$	R11	22k $\Omega$
R3	22k $\Omega$	R12	2.2M $\Omega$
R4	27k $\Omega$	R13	220k $\Omega$
R5	100k $\Omega$	R14	1.8k $\Omega$
R6	33k $\Omega$	R15	47k $\Omega$
R7	5.6k $\Omega$	R16	220k $\Omega$
R8	20k $\Omega$	R17	440 $\Omega$
R9	10k $\Omega$		
SR1 and SR2	shunts		
VR1	100k pot.	VR2	500k pot.

## Capacitors:

C1	25pF	C12	0.01 $\mu$ F
C2	0.01 $\mu$ F	C13	0.1 $\mu$ F
C3	0.01 $\mu$ F	C14	0.005 $\mu$ F 1000V mica
C4	1,000pF	C15	200pF
C5	1,000pF	C16	0.01 $\mu$ F
C6	100pF	C17	8 $\mu$ F 350V
C7	0.01 $\mu$ F	C18	0.05 $\mu$ F
C8	0.1 $\mu$ F	C19	50 $\mu$ F 25V
C9	100pF	C20	2,000pF
C10	1,000pF	C21	2,000pF
C11	1,000pF		
TC1	30pF trimmer		
VC1	25pF miniature variable		
VC2	250-500pF	VC3	2x500pF

## Valves:

V1	6AM6	V4	12AT7
V2	6BA6	V5	12A6
V3	6BW6	V6	12A6

## Transformers:

T1	Push-pull input transformer, surplus SCR522, 1:2 ratio or similar
T2	Modulation transformer, surplus SCR522, ratio 2:1, or similar

## Inductors:

L1	See text
L2	R.F. choke 2.5mH 100mA
L3	See text
L4	R.F. choke 2.5mH 100mA
L5	See text

## Switches:

S1	On/off toggle switch
S2	4-pole, 2-way rotary switch
S3	2-pole, 2-way rotary switch

## Meter:

M1	0-1mA meter
----	-------------

## Miscellaneous

Two B9A holders. Two B7G holders. B9A screen. Two octal holders. Four-sided chassis 12 x 7 x 3 and 12 x 7 panel (Home Radio, Mitcham). Knobs, etc.

and the ratio of the modulation transformer T2 can thus be calculated in the usual way, if necessary. New multi-ratio modulation transformers are obtainable, allowing correct matching of any output stage.

Both the r.f. and the modulator sections are built on a common chassis, with meter and all controls except the power pack on/off switch.

## Chassis

This is 12in. x 7in. x 3in. deep, so that the v.f.o. may be constructed underneath. A four-sided chassis is required, for rigidity, and a 12in. x 7in. panel is held in place by the component nuts. The positions of the valveholders and other items will be seen from Fig. 3.

TO BE CONTINUED


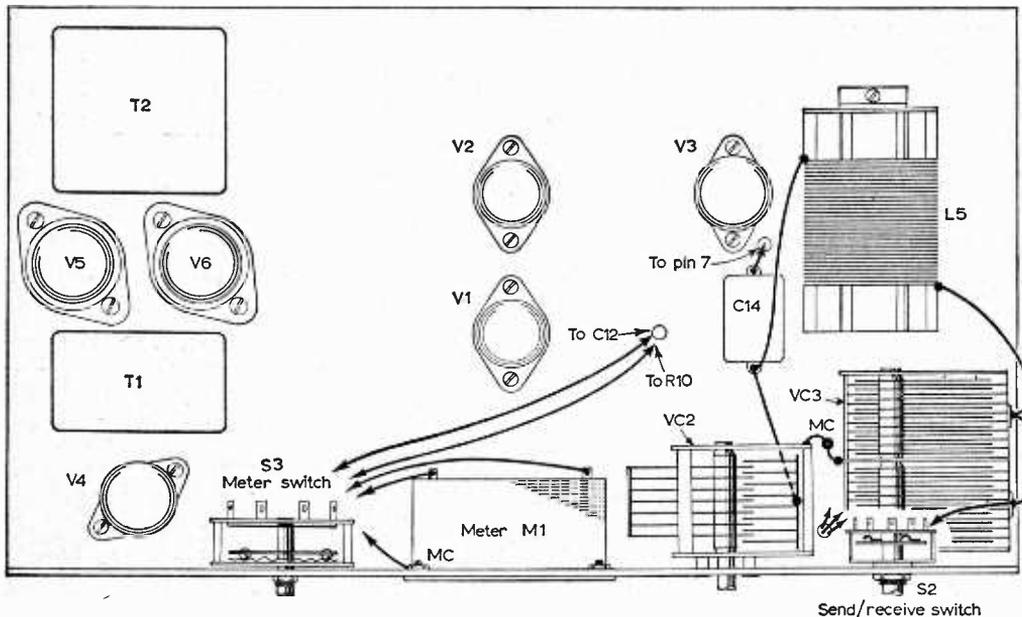


Fig. 3: The above-chassis layout of components.

# Just a few of our BARGAINS

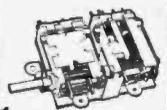

1



2



3



4




5




6



7

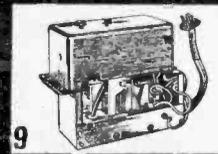


9

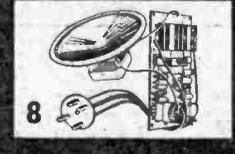

8




10

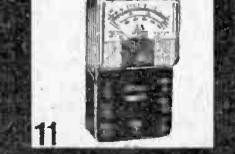


11



12

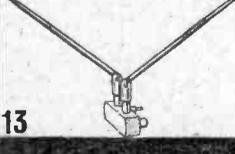

13

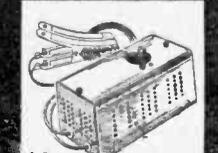

14

**RADIO & T. V.  
COMPONENTS  
[ACTON]  
LIMITED**

- 1. A.M. F.M. PERMEABILITY TUNER FOR ALL TRANSISTOR OPERATION.** Size  $2\frac{1}{2} \times 2\frac{1}{2}$  in. approx. By famous manufacturer. A.M.-I.F. 470Kc/s. F.M.-I.F. 10.7Mc/s. A.M. coverage from 1,620 Kc/s-525Kc/s. F.M. coverage 108Mc/s-88Mc/s. Circuit diagram 2/6, FREE with Tuner. 25/-, plus 1/- P. & P.
- 2. TRANSISTORISED POCKET RADIO** with printed circuit, mini-tube, high gain ferrox slab aerial. No aerial or earth required. To build yourself for completely personal listening.  $4\frac{1}{2} \times 3\frac{1}{2} \times 1\frac{1}{2}$  in. Luxembourg in favourable areas. Only 21/-. P. & P. 2/6. All parts available separately.
- 3. A.C./D.C. POCKET MULTI-METER KIT.** 2in. moving coil meter scale calibrated in A.C./D.C. volts, ohms and milliamps. Voltage range A.C./D.C. 0-50, 0-100, 0-250, 0-500. Milliamps 0-10, 0-1000 Ohms ranges 0-1,000, 0-100,000, 19/6. P. & P. 3/-. Wiring diagram 1/-, free with parts.
- 4. SIGNAL GENERATORS:** Cash 57.5.0, or 30/- deposit and 6 monthly payments of 21/6. P. & P. 6/6. Coverage 100 kc/s to 100 Mc/s on fundamentals and 100 Mc/s to 200 Mc/s on harmonics. Case  $10 \times 6\frac{1}{2} \times 5\frac{1}{2}$  in. Three miniature valves and Metal Rectifier. A.C. mains 200/250v. Internal modulation of 400 c.p.s. to a depth of 30 per cent. Modulated or unmodulated R.F. output continuously variable 100 millivolts. C.W. and mod. switch, variable A.F. output. Magic eye as output indicator. Accuracy 2 per cent.
- 5. SIGNAL GENERATORS.** Cash 55.5.0. P. & P. 6/6. Coverage 120 kc/s to 84 Mc/s. Case  $10 \times 6\frac{1}{2} \times 4\frac{1}{2}$  in. Size of scale  $6\frac{1}{2} \times 3\frac{1}{2}$  in. 2 valves and rectifier. A.C. mains 230-250v. Internal modulation of 400 c.p.s. to a depth of 30 per cent, modulated or unmodulated R.F. output continuously variable 100 millivolts. C.W. and mod. switch variable A.F. output and moving coil output meter. Accuracy  $\pm 2$  per cent.
- 6. STAAR 45, 9 v. BATTERY RECORD PLAYER** complete with pick-up and deck. A completely portable player. Head protected by plastic dome with a brush which cleans the stylus as it rises into playing position. 45 r.p.m. Auto on-off switch governed motor, attractive two-tone grey finish, 22.9.6. P. & P. 2/-.  
**7. CARRYING CASE** for STAAR 45 or **COMPLETE KIT** beautifully styled in two tone with record compartment. Specially designed to take player and amplifier. Just screw in and connect up. All parts available separately. Case only 22/6. P. & P. 9/-. Complete kit, 25.10.0. P. & P. 5/-.
- 8. TRANSISTORISED AMPLIFIER,** suitable STAAR 45. Output 1 watt. Size  $4\frac{1}{2} \times 2\frac{1}{2}$  in. Printed circuit, tone/volume controls plus 4 transistors. Push-pull output complete with 3in. moving coil speaker. Built and tested, 40/6. P. & P. 2/-.
- 9. CHANNEL TUNER I.F.** 16-19 Mc/s. Continuously tunable from 174-216 Mc/s. Valves required—PCP80 and PC084 (in series). Cover BBC and ITA ranges. Also Police, Fire and Taxic, etc. Brand new by famous maker, 10/-. P. & P. 3/-.
- 10. B.S.R. MONARCH UA4 WITH FUL-FI HEAD.** 4-speed, plays 10 records, 12in., 10in. or 7in. at 16, 33, 45 or 78 r.p.m. Internals 7in., 10in. and 12in. records of the same speed. Has manual play position: colour brown. Dimensions:  $12\frac{1}{2} \times 10\frac{1}{2}$  in. Space required above baseboard 4in., below baseboard 2in. Fitted with Ful-Fi turnover crystal head, 25.19.6. P. & P. 6/6.
- 11. POCKET MULTI-METER.** Size  $3\frac{1}{2} \times 2\frac{1}{2} \times 1\frac{1}{2}$  in. Meter size  $2\frac{1}{2} \times 1\frac{1}{2}$  in. Sensitivity 1,000 O.F.V. on both A.C. and D.C. A.C. and D.C. volts 0-15, 0-150, 0-1,000. D.C. current 0-150 mA. Resistance 0-100K  $\Omega$ . Complete with test leads, battery and full instructions, 35/-. Plus 1/6 P. & P.
- 12. 8-watt PUSH-PULL 4 VALVE AMPLIFIER** plus **METAL RECTIFIER.** A.C. mains 200-250 v. Size  $10\frac{1}{2} \times 6\frac{1}{2} \times 2\frac{1}{2}$  in. 5 valves. For use with all mikes and types of pick-up and mike. Negative feed back. Two input, mike and gram, and controls for same. Separate controls for Bass and Treble lift. Response flat from 40 cycles to 15 kc/s. 2 dB down to 20 kc/s. Output 8 watts at 5 per cent total distortion. Noise level 40 dB down all hum. Output transformer tapped for 3 and 16 ohms speech coils. For use with Std. or L.P. records, musical instruments such as guitars, etc. Suitable for small halls, 23.19.6. P. & P. 6/-. Crystal mike to suit 15/-. P. & P. 2/-. 8in. P.M. Speaker to suit, 12/6. P. & P. 2/-.
- 13. INDOOR AERIAL** for ITV/BBO/FM. Complete with standard co-axial plug. Heavy chrome extending dipoles—7ft. fully extended. Flings straight into TV or VHF Tuner. Fully directional, 10/6. P. & P. 1/6.
- 14. NO MORE FLAT BATTERIES.** Charge your own battery overnight with this wonderful little charger. Output 6 and 12 volts, 2 amp. Input 200-250 v. A.C. mains. Mains fuse incorporated. Attractive silver hammer finished case, 6 x 3 x 3 in. Complete with leads and battery clips only 21/-. P. & P. 3/6.


**21b HIGH STREET  
ACTON, LONDON, W.3.**

ALL ENQUIRIES S.A.E.  
GOODS NOT DESPATCHED OUTSIDE U.K.



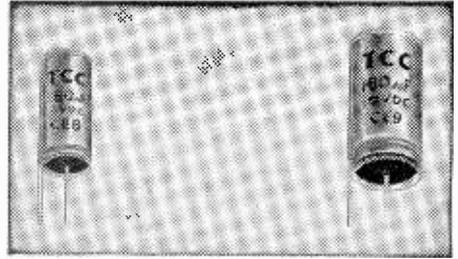
## SUB-MINIATURE ELECTROLYTICS FOR TRANSISTOR CIRCUITS

These capacitors are ideal for miniaturised transistor circuits such as in pocket radios. Each is available with wires at opposite ends for horizontal mounting ("H"), or at one end for vertical mounting ("V"). Connection wires are welded for low resistance contact and solder coated for ease of assembly. The standard length is  $1\frac{1}{2}$ " for the horizontal range, cropped to  $\frac{3}{8}$ " for the vertical range.



The capacitors are in insulated seamless aluminium cases and sealed with a synthetic rubber bung. **Capacitance and Tolerance** Standard tolerance is  $-20\% + 100\%$  of the rated capacitance. **Operating Temperature Range:**  $-20^{\circ}\text{C}$  to  $+60^{\circ}\text{C}$ .

T.C.C. TYPE	CASE SIZE IN INCHES			MAXIMUM D.C. WKG. VOLTAGES AND CAPACITANCE ( $\mu\text{F}$ )					
	D	L	C	3V.	6V.	10V.	15V.	25V.	50V.
CE.8 ..	$\frac{1}{4}$	$\frac{3}{8}$	0.14	100	80	60	40	25	8
CE.9 ..	$\frac{1}{8}$	$\frac{3}{8}$	0.2	250	200	160	100	60	20

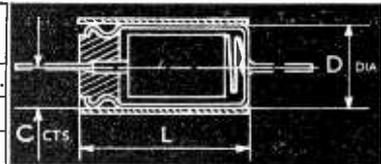

**THE TELEGRAPH CONDENSER CO. LTD.**  
RADIO DIVISION • NORTH ACTON • LONDON • W.3 • Tel: ACOrn 0061

**FREE** THIS BOOK WILL INTEREST YOU!

LEARNING the PRACTICAL WAY

**RADIOSTRUCTOR EQUIPMENT-COURSES**

FOR .. Your Career  
.. Your Own Business  
.. An Absorbing Hobby

## A NEW-PRACTICAL WAY of UNDERSTANDING Radio : Television Electronics

including: Transistors; VHF/FM; Hi-Fi equipment; Computers; Servo-mechs; Test instruments; Photo-electrics; Nucleonics, etc.

Radiostructor—an organisation specialising in electronic training systems—offers a new self-instructional method using specially designed equipment on a "do-it-yourself" basis. You learn by building actual equipment with the big kits of components which we send you.

You advance by simple steps, performing a whole series of interesting and instructive experiments—with no complicated mathematics! Instructional manuals employ the latest techniques for showing the full story of electronics in a practical and interesting way—in fact, you really have fun whilst learning! Fill in the coupon below for full particulars.

**POST NOW**

TO RADIOSTRUCTOR (DEPT. G107)  
READING, BERKS.

Please send brochure, without obligation to:

★Name ..... } ★BLOCK  
Address ..... } CAPS  
..... } PLEASE  
(We do not employ representatives) 8/63

**RADIOSTRUCTOR**  
LEADS THE WORLD  
IN ELECTRONICS TRAINING

# 7 VALVE STEREOGRAM

CONTINUED FROM PAGE 243 OF THE JULY ISSUE

By J. B. Willmott

To commence wiring-up, first prepare the four-way power supply cable; this may conveniently comprise a suitable length (according to the dimensions of cabinet in which the receiver is to be housed) of twisted twin red/black flex (for the h.t. supply), and twisted twin plain flex (for the heater supply). One end of the cable should be terminated with an octal plug. Wire the red lead to pin 6, the black lead to pin 1, and the plain leads to pins 2 and 7, the pin numbers being numbered from below the plug, in the same manner as an octal valveholder (into which, of course, it is to be plugged on the power supply chassis when the latter is constructed). Thread the other ends of the four-way cable through the  $\frac{1}{2}$ in. grommets hole in the top left hand corner of the main chassis (Fig. 2), and anchor the ends beneath the chassis as follows: the red wire (which is h.t. positive), leave free for the moment (later this will be soldered to the h.t. connection on the 5-way tagboard); the black lead to the solder tag mounted on V4 valveholder; the twisted plain leads to pins 7 and 8 of this same valveholder (these being the heater tags for a 6SL7 valve), and at the same time, earth pin 8 to the nearby solder tag. Note that this is the only point at which the heater supply is earthed. Now carry out the wiring to all other valve heaters, using twisted plastic flex, starting from pins 7 and 8 of V4 just mentioned to include pins 2 and 7 of every other valveholder. Keep this wiring pressed down close

to the chassis. Also wire in the clip-on pilot bulb-holders (which must be of the two-pole "isolated" type) mounted on the tuning dial assembly.

Wiring of this receiver is greatly simplified by the use of two tagboards for supporting many of the resistors and capacitors, and the preparation of these should next be undertaken. Figs. 3(a) and 3(b) clearly show what is required, and if care is taken when mounting and interconnecting the various components, no trouble should arise. Observe carefully the polarity of the electrolytic capacitors. Short lengths of wire, about 4in. long, can be attached to the lower tags where shown, in readiness for connecting into the circuit when the tagboards are mounted in position, when these leads can be trimmed down to the requisite lengths.

### Screened Leads

It is not proposed to give detailed point-to-point wiring instructions—any constructor of average experience should be able to carry out wiring satisfactorily by reference to the theoretical diagram (Fig. 1), in conjunction with Figs. 3, 4 and 5. The only "tricky" parts are possibly the connections to the wavechange switch, and to the dual-gang potentiometers, but a

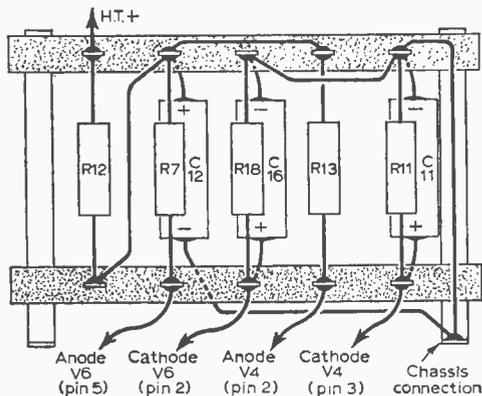


Fig. 3(a): Showing the connections of the anode and cathode components of V4 and V6.


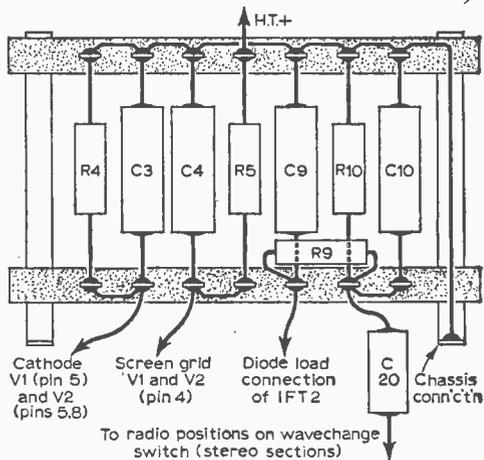


Fig. 3(b): The connections of the screen grid and cathode components of V1 and V2 and the diode load filter.

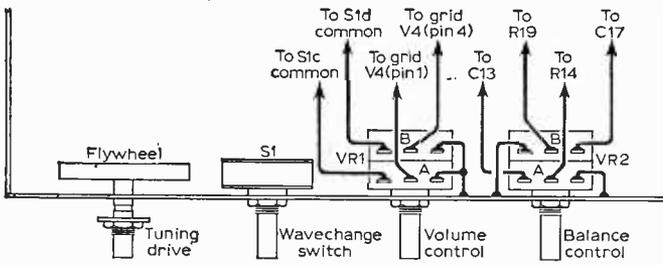

**Initial Tests**


Make sure that a suitable loudspeaker (3Ω impedance) is connected to each of the output sockets, and insert the octal power plug into the socket provided on the power supply chassis. Set the volume control to minimum, the balance control to mid-way, and the wavechange switch to the "gram" position (fully clockwise). Slowly turn up the volume control, and at maximum setting a faint hum should be audible from each speaker. Place the blade of a screwdriver on each of the "live" pick-up sockets in turn, when a loud hum should be heard from first one loudspeaker, then the other. Keep the screwdriver blade on one of the pick-up sockets, and try the effect of rotat-

Fig. 4: The wiring of the dual volume and balance potentiometers.

methodical approach, taking each tag in turn, should obviate errors. The following connections should be carried out in screened wire, the outer screening being earthed to any convenient earth

from C20 to the wavechange switch; from the "live" pick-up sockets to the wavechange switch; from the wavechange switch to the "top" of each section of the dual-gang volume control: from the "slider" of each volume control to the control grids of V4 and V6; from C13 and C17 to the "end" tags of the balance control, and finally from the "centre" tags of the balance control to the top cap connections of V5 and V7. Note that a grid stopper resistor (R14 and R19) is mounted as close as possible to the top-cap grid connection of V5 and V7.

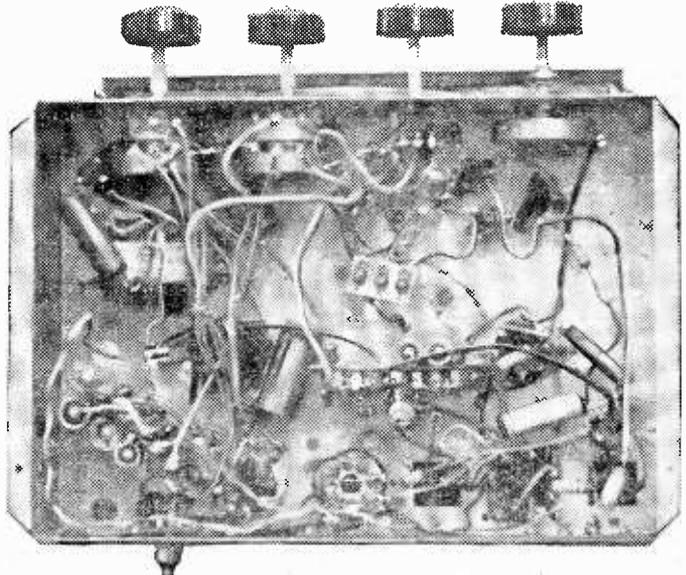When wiring up the r.f. and i.f. circuits, short, neat wiring is particularly important, otherwise uncontrollable oscillation, or at the very least, a disappointing standard of sensitivity on radio signals, will result. Check over all wiring carefully.



A view of the underside of the receiver chassis.

**The Power Supply Unit**

Construction of this unit is very straightforward, and practically all the necessary information can be gleaned from Figs. 6 and 7. The chassis used in the prototype measured 11½in. x 6in. x 2½in., but as the layout is in no way critical, practically any type of chassis will serve, so long as the components can be accommodated. Drilling dimensions applicable to the prototype are given; if a different make of mains transformer and smoothing choke are used, the actual components should be used as marking templates.

Note that rubber grommets should be provided in all holes through which leads pass between components above the chassis and those below.

Do not test the power supply unit without any "load" connected, as the high voltages produced may cause breakdown of the electrolytic capacitor C21.


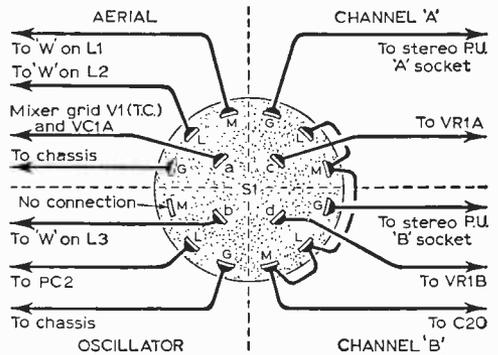


Fig. 5: The wiring of the wave-change/gram switch.

ing the balance control; this should be found to vary the output of the two channels, one increasing as the other decreases and vice-versa when the blade is transferred to the other pick-up socket.

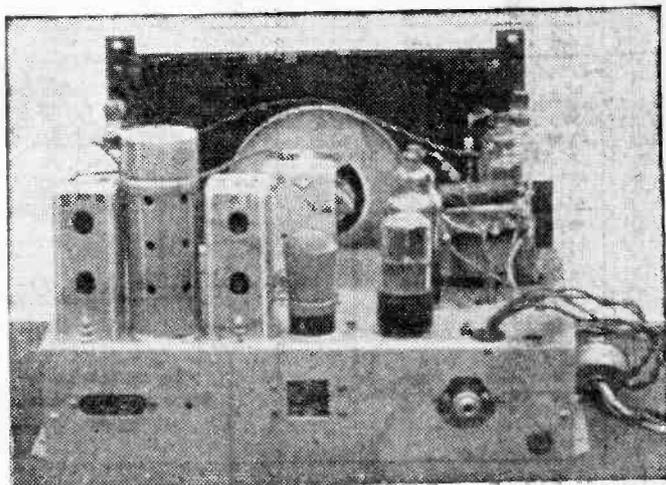**Receiver Alignment**

Set the signal generator to provide a modulated output of 465kc/s, switch it on and allow some five minutes for it to warm up. Meanwhile, remove the top cap connection to V1, and temporarily wire in (using crocodile clips) a 100kΩ resistor between the top cap and chassis. Using the "direct" output leads from the signal generator, connect them to the top cap of V1 and to chassis. Make sure that the wavechange switch is set either to the long or medium wave position (i.e. not to "gram" as the r.f. and oscillator circuits would be rendered totally inoperative). With the volume control at maximum, turn up the generator output until the note is heard in the loudspeakers. Now, using the sharpened end of a plastic knitting needle (or a proper trimming tool if you possess one), adjust the cores of the i.f. transformers in turn, begin-



A rear view of the main chassis.

sockets of the receiver. Remove the temporary 100kΩ resistor from the top cap of V1, and replace the cap and lead going to the fixed plates of the mixer tuning section of the 2-gang capacitor. Set the wavechange switch to medium waves (fully anti-clockwise), and the dial pointer to the 200m mark. Set the generator to 1,500 kc/s, and adjust the output until a signal is audible, if necessary slightly rocking the tuning control of the receiver. Now adjust TC3 and TC1 for maximum response with the dial pointer correctly indicating 200m: again, keep the output from the generator to lowest level possible. Now turn the receiver dial to 500m and the generator to 600kc/s, and adjust the cores of L3 and L1 for maximum response. Repeat these adjustments at 200m (1,500 kc/s) and 500m (600kc/s) several times until no improvement can be heard.

The only station likely to be required on the long waveband is the BBC Light Programme, and this adjustment is best carried out on the actual signal. Turn the wavechange switch to the long wave position, and search for the programme in the vicinity of 1500m on the dial. As soon as it is located, try to bring it into tune by adjustment of TC2 and the core of L2, but on no account touch TC3 or L3 in the oscillator section, as this would, of course, completely upset the medium wave alignment previously carried out. If it is found that the BBC Light Programme "peaks" at a point removed from the 1500m mark on the dial, some slight adjustment of the long wave oscillator padder PC2 is called for. Try the effect of connecting a small capacitor, say 50pF, in parallel, and if this brings the point of resonance nearer to the correct point on the dial, try varying values of parallel capacity (it is unlikely that more than 50pF will be required) until the desired setting is obtained. If addition of capacity only drives the point of resonance further from the desired setting, a reduction in value of PC2 is called for, and a component of slightly lower value (by some 20pF or so) should be tried.

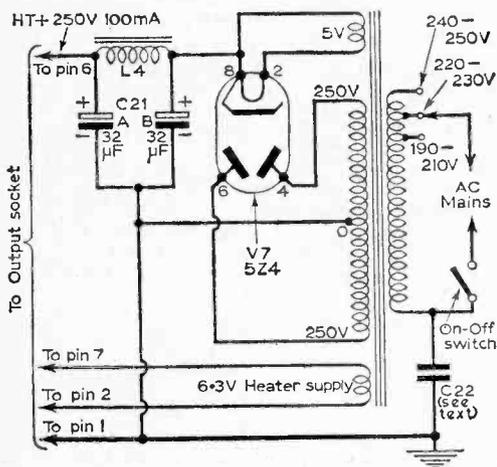


Fig. 6: The circuit of the power supply.

ning with the secondary of IFT2, following with the primary of IFT2, the secondary of IFT1, and finally the primary of IFT1. Repeat the process, and as the circuits come into tune, reduce the output from the signal generator to the lowest possible level consistent with an audible output from the loudspeakers.

Next replace the "direct" output leads of the signal generator with the "dummy aerial," and connect them between the aerial and earth

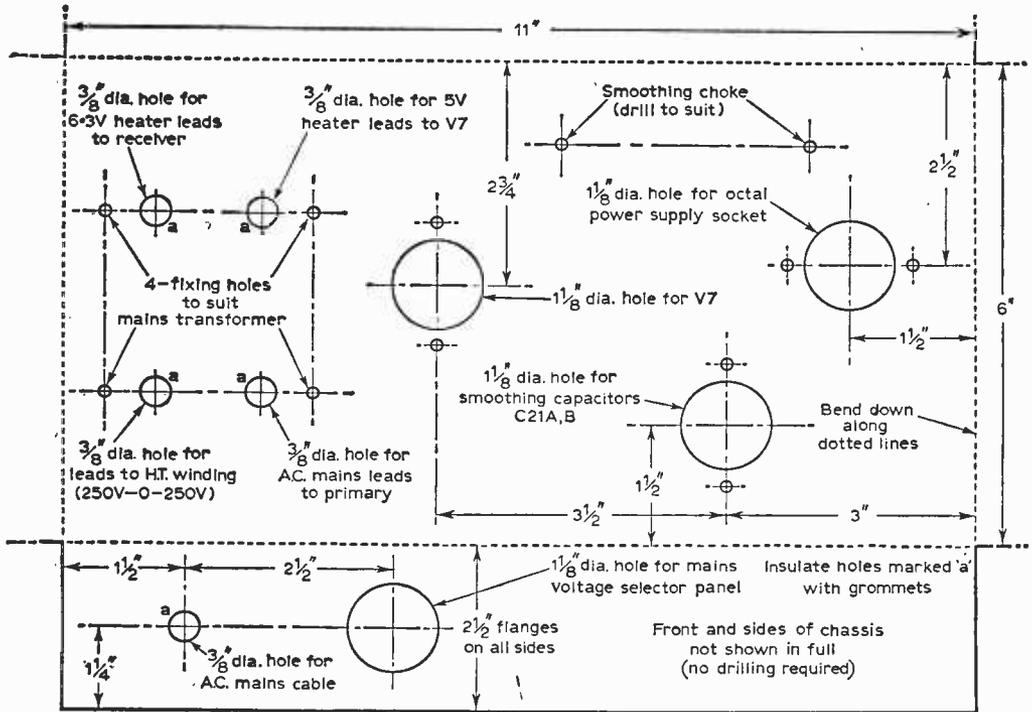


Fig. 7: The dimensions of the power supply chassis.


In the prototype, the value of 390pF was found to give correct alignment.

#### Setting Up and Installation

Having completed the alignment of the radio section, attention may now be turned to the setting up of the audio section for correct stereo operation. It is essential that the two loudspeakers employed be of identical characteristics. It will be found that with the simple audio circuits

employed, perfectly adequate results will be obtained from loudspeakers in the lower price range, although it is recommended that these should preferably be of not less than 8in. diameter.

Some thought should be given to the ultimate method of housing the various units, and there are various possibilities, using the range of cabinets offered by advertisers in this magazine. The simplest method is to mount all the equipment in a single console cabinet of the "wide" pattern, which allows the loudspeakers to be mounted at opposite ends and give reasonable separation. Alternatively, the receiver and power supply unit, together with one loudspeaker, may be mounted in the main console, and the second loudspeaker in a separate free-standing cabinet. Yet a third possibility is to mount the receiver and power supply in a compact "control console", with the two loudspeakers as separate free standing units, possibly of the vertical column type. This latter method offers considerable flexibility, and is often the most suited to living rooms of modest dimensions. For the initial tests, however, it will suffice if the loudspeakers are placed in some form of temporary mounting,

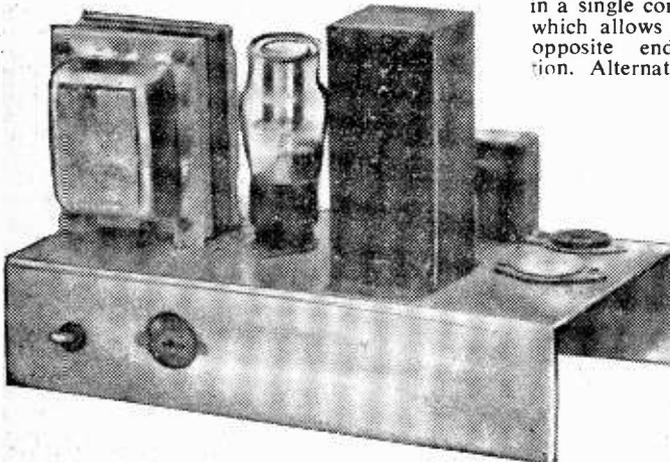

The power supply.

## COMPONENTS LIST

## Resistors:

R1	10k $\Omega$	R11	3.3k $\Omega$
R2	100k $\Omega$	R12	22k $\Omega$
R3	1M	R13	270k $\Omega$
R4	220 $\Omega$	R14	100k $\Omega$
R5	27k $\Omega$ 2W	R15	470 $\Omega$
R6	47k $\Omega$	R16	22k $\Omega$
R7	47k $\Omega$ 1W	R17	270k $\Omega$
R8	1M	R18	3.3k $\Omega$
R9	47k $\Omega$	R19	100k $\Omega$
R10	220k $\Omega$	R20	470 $\Omega$
		R21	22k $\Omega$

All 10%,  $\frac{1}{2}$ W carbon, unless otherwise stated.

VR1a, b 1M $\Omega$  + 1M $\Omega$  dual-ganged potentiometer, log/log.

VR2a, b 500k $\Omega$  + 500k $\Omega$  dual-ganged potentiometer, log/antalog.

## Capacitors:

C1	0.01 $\mu$ F paper 450V
C2	2,500pF 5% silver mica
C3	0.1 $\mu$ F paper 350V
C4	0.1 $\mu$ F paper 350V
C5	100pF mica or ceramic
C6	100pF mica or ceramic
C7	50pF mica or ceramic
C8	0.1 $\mu$ F paper 350V
C9	100pF mica or ceramic
C10	100pF mica or ceramic
C11	25 $\mu$ F electrolytic 25V
C12	8 $\mu$ F electrolytic 350V
C13	0.01 $\mu$ F paper 450V
C14	25 $\mu$ F electrolytic 25V
C15	0.05 $\mu$ F paper 450V
C16	25 $\mu$ F electrolytic 25V
C17	0.01 $\mu$ F paper 450V
C18	0.05 $\mu$ F paper 450V
C19	25 $\mu$ F electrolytic 25V
C20	0.01 $\mu$ F paper 450V
C21	32 $\mu$ F
C22	32 $\mu$ F
PCI	470pF 5% (or better) silver mica.
PC2	390pF 5% (or better) silver mica.

} dual electrolytic 450V

## Variable Capacitors:

VC1a, b	500pF + 500pF twin-gang tuner.
TC1	50pF compression type trimmer.
TC2	50pF compression type trimmer.
TC3	50pF compression type trimmer.

## Inductors:

L1	Medium wave aerial coil (Weymouth HA3).
L2	Long wave aerial coil (Weymouth HA1).
L3	Oscillator coil (Weymouth HO3).
L4	Smoothing choke 100mA.

## Transformers:

IFT1, 2	Standard size 465 kc/s i.f. transformer.
T1, 2	Pentode output transformer, 8,000 $\Omega$ primary, 3 $\Omega$ secondary.
T3	Mains transformer. Tapped primary. Secondaries: 250-0-250V. 100mA; 6.3V 4A; 5V 2A.

## Switches:

S1	4-pole, 3-way single wafer.
S2	Toggle type s.p. s.t.

## Valves:

V1	ECH35 (6K8)	V4	ECC35 (6SL7)
V2	EF39 (6K7)	V5	EL32
V3	EB34 (6H6)	V6	E632
		V7	GZ30 (5Z4)

## Miscellaneous:

Two 8in. diameter 3 $\Omega$  loudspeakers. Two 6.5V 0.3A diameters and holders (twin tag type). Eight I.O. valve holders. One I.O. plug (discarded valve base). Aerial and earth socket strip. Loudspeaker socket strip, 4-way. 3-pin plug and socket (for pick-up). Two 2-way tag strips. One 5-way group board. One 7-way group board. Four I.O. valve top cap clips. Four control knobs. One spin wheel drive assembly (Jackson SL8). Receiver chassis 12 x 9 x 2 $\frac{1}{2}$ in. Power supply chassis 11 x 6 x 2 $\frac{1}{2}$ in. Connecting wire, insulated sleeving, screened wire, 4 B.A. and 6 B.A. nuts, bolts, washers and solder tags. Rubber grommets.

such as a plywood baffle board. For best results they should be placed about eight to twelve feet apart, facing towards the normal listening position.


## Gram Testing

It is assumed that a suitable record playing unit, together with the necessary stereo head, has already been obtained, with the necessary length of two-way screened lead. A three-pin plug, to match the socket provided on the rear chassis panel, is fitted to the pick-up lead, the two inner leads to the outside pins, and the screening to the centre (earth) pin. Insert the plug into the pick-up socket, and for the first trial, place an ordinary (mono) L.P. record on the turntable, and with volume at a suitable level, play the record. By careful adjustment of the balance control, a setting should be reached where the sound appears to come from a point midway between the two speakers. If this cannot be realised, the reason is probably that the speakers are not correctly phased, i.e., the cones of the two speakers, instead of moving inwards and outwards in unison, are moving in opposite directions at any given time.

To correct this, reverse the plugs of one of the speakers, and try again. Once the correct phasing has been found, it is a good plan to mark the speaker plugs in some manner, together with their sockets, so that if at anytime they have to be disconnected, they can be reinserted correctly without further trials.

Having achieved a satisfactory balance, the "mono" record can be exchanged for a "stereo" one, preferably one of the special "Test and Demonstration" records which are ideal for setting up purposes. Listen carefully, and first of all make sure that the "right hand" and "left hand" channels are being reproduced by the correct speaker, either from the spoken commentary of the test record, or as a rough guide, it is general practice in orchestral and dance band records for the bass instruments, saxophones, etc., to predominate in the right-hand channel, and the strings and other higher pitched instruments in the left hand channel, whilst a vocal solo will appear to come from the mid-point. If the reproduction appears to be reversed, change over the connections of the loudspeakers, i.e. exchange the right- and left-hand channel connections.

# Transisto

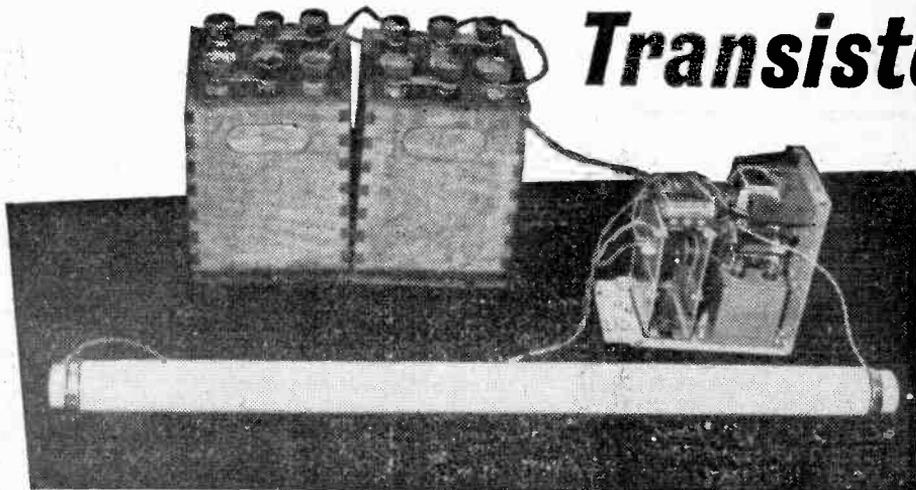

**I**T is always difficult to provide adequate means of lighting once one is away from the usual mains electricity supply. One way of overcoming this obstacle is to make fuller use of battery-operated fluorescent strip lighting.

This lighting is ideal for seaside chalets, caravans, vans and boats, and for emergency lighting in homes, hospitals or at the site of road accidents or breakdowns. Unfortunately, at these times, there is generally only low voltage d.c. current available from accumulators. In order to overcome this difficulty a transistor converter can be connected between the available batteries and the striplight: this produces the high voltage a.c. power with which to operate the light.

It is even possible to use dry-cell batteries for small striplights. For example, four bicycle lamp batteries will run a miniature 6in. fluorescent striplight for several hours. For use with larger striplights, however, it is necessary to use correspondingly larger batteries. It is advantageous to use accumulators rather than dry-cell batteries in this case.

Striplights are economical to use in that although they may cost considerably more than an ordinary lamp they have about five times the working life. They also have the advantage of being "shadowless" and there is a choice of several colours available.

A transistor inverter, suitable for supplying a small fluorescent striplight with power, can alternatively be used to supply the necessary power for a photographic electronic flash.

## Striplights

A fluorescent striplight contains a low-pressure gas through which an electric current is induced to pass. The passage of the current produces ultra-violet light which is in turn used to activate a fluorescent coating on the inside of the tube. The composition of the coating determines the colour of the light produced.

Alternatively the striplight may be constructed from uncoated Wood's glass, which permits the free passage of the ultra-violet light, allowing it to be used in various ways; e.g., suitable materials or paints can be made to fluoresce, it is used as a sterilising agent, killing bacteria or it can even be used for acquiring a suntan.

In order to obtain the passage of a current through the tube at a reasonable voltage, heated cathodes are fitted at each end to provide electron emission for tube starting. Once the tube has struck (i.e. a current has started to flow) the heating current to the cathodes may be reduced or removed and the cathode temperature is then maintained by ionic bombardment from the gas particles in the tube.

The electrical characteristic of the working tube is such that the discharge exhibits the property of negative resistance, i.e. an increase in current through the tube is associated with a decrease in the voltage across it.

This characteristic necessitates the employment of control equipment, termed "ballast", with these tubes, in order to limit the discharge current to the desired level. The ballast may be inductive, capacitive or resistive.

# ised STRIPLIGHTS

## AN INVERTER FOR SUPPLYING FLUORESCENT TUBES FROM LOW VOLTAGE D.C. SUPPLIES

The inductive ballast is generally preferred as the resistive ballast is wasteful in power and the capacitive ballast produces an undesirable current waveform in some circumstances.

The inductive and capacitive ballasts are, however, only suitable for use on an alternating current supply. The shape of the waveform of the a.c. supply is not restricted, although much may be said in favour of the sinewave.

### The Inverter

Modern striplights are designed to operate from a 210-250V 50c/s a.c. supply via their own associated control equipment. It can be shown, however, that an increase in the efficiency of the lamp can be obtained by using a supply of higher frequency. The use of a higher frequency also implies a reduction in the size of inductive components.

It was decided that the output of the inverter in this example should be 250V, for easy lamp starting, and at 6,500c/s to facilitate easy construction of the inductive components required. The choice of a lower frequency would have meant more larger windings on the transformer and choke, while the choice of a higher frequency would have precluded the use of certain moderately priced power transistors of low cut-off frequency.

The comparatively high working frequency does, however, necessitate the use of ferrite transformer and choke cores rather than the usual laminated iron or steel. The choice of mica capacitors, for low losses in the secondary circuit, would also be necessary.

### The Circuit

The circuit of the inverter is a single-stage, push-pull sinewave transistor oscillator. The frequency of oscillation is set by a resonant tuned secondary of the feedback transformer. This winding also supplies the h.t. output to the striplight. Further windings on the transformer provide the currents for cathode heating.

Feedback signals are provided by the cross-coupled windings on the transformer between the collectors and bases of the transistors. Small reverse bias to drive the transistors into class "C" operation is provided by the transistor base currents and the capacitor connected in parallel with the drive control resistor.

In class "C" operation each transistor conducts for less than half of each cycle, which aids economical operation. Forward bias for starting is provided from the h.t. rail via R1. The bias components R2/C2 form a compromise between

efficiency, easy starting and good waveform. A capacitor C1 connected between the two collectors suppresses switching transients.

The discharge circuit is fed from the resonant transformer secondary via a series inductance to limit the discharge current as previously described. For example, a 6in., 4W lamp requires approximately 150mA at 30V during discharge and the series inductance is used to set this value. To obtain 150mA with the 6,500c/s 230V source an inductance of 40mH is required.

A suitable core on which such a choke might be wound can be made up of Mullard Ferroxcube pieces FX1036, "U" Core, and FX1067, "I" Core.

With the specified cores, the number of turns required is 158. The two halves of the core should be firmly butted together and clamped. The wire used should be enamelled copper, not less than 30s.w.g., to handle the current.

If this unit, however, is to be used with a selection of different wattage striplights, it is suggested that the choke be wound with 300 turns of wire and the inductance adjusted later to the requisite value by the introduction of a suitable air gap in the core.

### The Transformer

To produce a sinewave in a simple circuit a tuned resonant element is required. This may be most conveniently incorporated in the transformer. If the resonant circuit has reasonable "Q" the reflected e.m.f.s of the circulating currents can be used to reduce the number of turns per volt necessary in the transformer from what would have been required in a conventional transformer, providing the same voltage and current output.

The one remaining consideration is the provision of adequate coupling between the windings. In order to prevent undue voltage excursions of the primary windings during the cut-off intervals of transistor operation, the two halves of the primary must be closely magnetically coupled. This may be most conveniently achieved by bifilar winding.

In order to prevent parasitic oscillation of the circuit during use, the leakage inductance of the transformer should be kept as low as possible. This is achieved by keeping the primary to secondary coupling high by sandwiching the secondaries between two electrically identical primary windings connected in parallel.

### Transformer Construction

First construct a cardboard bobbin on to which the windings will be wound. Ensure that the centre spool is a loose fit on the ferrite cores (see Fig. 3).

The bobbin should be dried in an oven and shellaced against damp. The centre of the bobbin should be well bound with Sellotape.

Take 2yd of 21s.w.g. enamelled wire and fold it into a double 1yd length, ensuring that the two wires are not twisted together. Puncture two holes through the side of the bobbin near the centre, marking this side of the bobbin "Start". Thread the two strands of wire through the holes from the outside, leaving a 6in. loop on the outside for connecting purposes.

Holding the two strands together and avoiding twists, wind nine turns of the double wire and pass the ends through two holes punctured on the other side of the former. Mark this side of the former "Finish". Well tape the winding into position with Sellotape to provide insulation and prevent vibration.

The resonant high-tension secondary winding is wound next. The 250 turns are wound in even layers, one thickness of Sellotape between each layer. When the winding is complete it, too, should be tightly bound with several layers of Sellotape.

Two separate windings of 11 turns each are now wound to provide current to pre-heat the tube cathodes. They are well insulated from one another and from the remaining transformer windings by layers of Sellotape.

The bifilar secondary winding of four turns of double 21s.w.g. enamelled wire is now constructed similarly to the first winding and well taped. Finally the remainder of the primary winding is bifilar wound, similarly to the first winding, except that, due to the increase in diameter, a rather longer length of wire will be required. All windings should be wound in the same direction.

Taking in turn the inner primary, feedback, and outer primary windings, cut the loop where the wire has been doubled, bare the ends, and with a continuity tester identify the ends of each part of the winding. Connect the halves of the bifilar winding in series (the "Start" end of one half to the "Finish" end of the other). Connect the inner and outer primary windings in parallel (see Fig. 1).

The wires may be trimmed and connected to a small tag-strip, marked to identify connection.

**Other Components**

The transistors should be mounted on suitable cooling fins, 3in. x 3in. 18s.w.g. aluminium being suitable where the unit is to be run at low wattages.

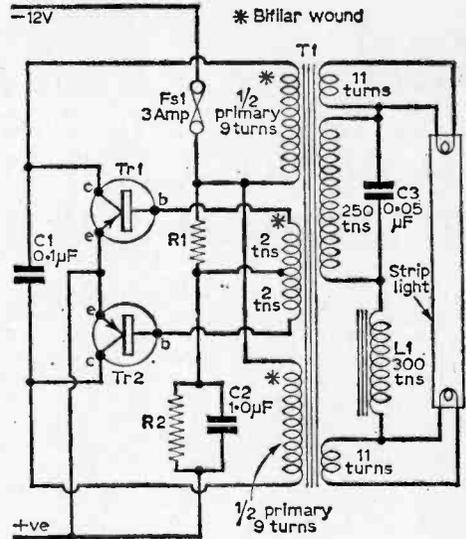


Fig. 1 The inverter circuit

and 9in. x 9in. 16s.w.g. for maximum ratings. The cooling fins may be folded into more compact shapes as long as free air circulation is not impeded, and the effective areas thereby reduced. The plates are drilled to take the transistor connections and mounting bolts, and the areas of contact of transistor and plate smeared with silicone grease before assembly.

During operation the cooling fins are "live" to collector potentials and should therefore be electrically insulated from the supports and chassis. During connection of the transistors, the customary "heat shunt" must be used for soldering.

As previously mentioned, the tuned secondary winding requires a mica capacitor for tuning (C3). Values of mica capacitor in excess of 0.01μF are not plentiful and it will be found that a bank of mica capacitors of this value, connected in parallel, give a ready solution to this difficulty.

Low value, high wattage, resistors may be simply constructed from measured lengths of electric fire replacement elements of the coil type. A complete 1kW, 240V electric fire element has a resistance of

**COMPONENTS LIST**

Ref.	(4 watt tube)	(20 watt tube)
Tr1, Tr2	Transistors V30/10P	Transistors V30/10P
C1	Capacitor 0.1μF paper	Capacitor 0.1μF paper
C2	Capacitor 1μF paper	Capacitor 1μF paper
C3	Capacitor 0.05μF mica (see text)	Capacitor 0.05μF mica (see text)
R1	Resistor 1.5kΩ 1/2W	Resistor 100Ω 1W
R2	Resistor 30Ω 1/2W	Resistor 2Ω w.w. (see text)
FS1	Fuse <3.0 A	Fuse 3.0 A
T1	Transformer (see text)	Transformer (see text)
L1	Choke (see text)	Choke (see text)

approximately 60Ω and may be sub-divided with the aid of a ruler.

**Setting up**

A length of thin wire should be taped along the length of the striplight bulb and one end connected to a pin of the lamp. This assists in the initial striking of the lamp.

When the unit has been assembled and checked for correct wiring, power should be cautiously applied. Audible oscillation should be at once apparent although the striplight may not appear to be fully lit. If oscillation does not commence at once and all else is in order, the fault is probably a reversal of either the feedback winding of the transformer or one half of the primary winding. The effect of reversing each of these windings in turn should be tried at once.

If this should fail the cause will be probably due to transistors of low β gain, requiring more bias. The value of R1 should be reduced by 10%—20%. Once oscillation has been established the frequency and current are adjusted. The frequency is controlled by inserting pieces of paper between the halves of the transformer core to produce a suitable length gap. The sound required is one octave above the sound of the highest black key on a piano.

The current is adjusted by inserting thicknesses of paper between the two halves of the choke core, until the requisite current flows through the striplight. This may be assessed either by means of a suitable meter (a surplus r.f. milliammeter is adequate) or by comparing the brightness of the striplight on a photographic exposure meter with one operating from an orthodox source of power.

As the flow of secondary current effects the operating frequency it is likely that a second adjustment of the transformer core gap may be required when the tube current has been set. Once satisfactory gaps have been established the choke

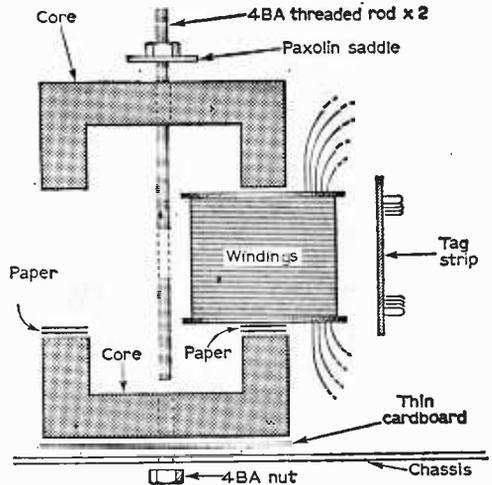


Fig. 3: Assembling the transformer.

and transformer should be firmly clamped in position. The drain from the battery will be about 0.7A for a 4W lamp to about 2.5A when using a 20W lamp.

During the initial run the transistors should be checked to ensure that neither is overheating. If they both become too warm for comfortable contact with the back of the hand, the bias and/or drive are too high and the resistors R1 and R2 should be proportionately increased. One transistor, only, overheating indicates that either the transistors are not a matched pair, or that there are short circuited turns in one side of the transformer.

If it is required to operate the unit from a high impedance source, or if two or more such units are to be operated from the same power supply, a capacitor of 100μF should be connected across the input to the unit.

**Alternative Striplights**

Any standard type striplamp between four and 20W may be used with this converter as long as the drive and core gaps are set up to suit the particular tube. The drive is increased by decreasing the values of R1 and R2, but only up to the point where it is just possible to obtain the necessary tube current by adjustment of the choke and transformer core gaps. If, however, any difficulty in starting is experienced, a little extra drive should then be applied.

**Alternative Transistors**

Any power transistors of more than 3A, 25V capacity may be used in the converter if the drive resistors are adjusted to suit. The resistors R1 and R2 should be increased in proportion to the transistor gain. If it is found that the β gain falls off excessively at 6,500c/s the working frequency may be dropped slightly by reducing the transformer core gap which will, in turn, necessitate a reduction of the choke core gap.

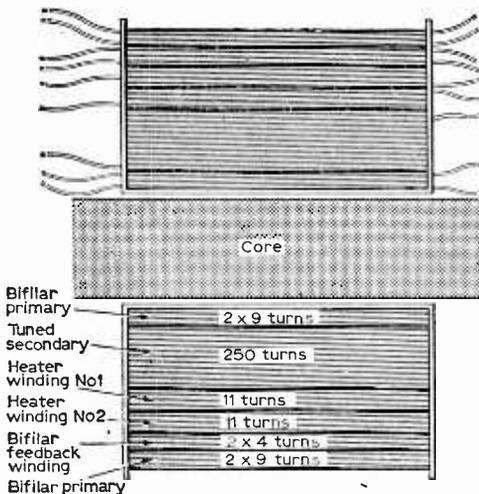


Fig. 2: A section through the transformer windings.

# TEST GEAR techniques

## PART 6 - THE OSCILLOSCOPE

H. W. Hellyer

PERHAPS the most useful yet, paradoxically, least-used instrument in the average radio and television service department is the oscilloscope. There are many applications in which this device is the only possible means of making a satisfactory test. But there are also a great number of alternative techniques where the oscilloscope can reduce fault-finding time, confirm a tentative diagnosis, increase the test range and provide an instant, observable answer to an obscure problem. It finds its value not only in the observation of waveforms but in the measurement of a.c. and d.c. voltage, with negligible load upon the circuit, as a signal tracer, a hum detector, a response measurement instrument and a frequency comparator.

Provided the oscilloscope has a Y amplifier with a sensitivity of at least 100mV/cm and a frequency response which is flat within 3dB from about 20c/s (or, preferably, zero frequency) up to 4 or 5Mc/s, plus a timebase which covers the frequency range 10c/s to 100kc/s (or up to half a megacycle if there is no trace expansion), most workshop tests can be carried out effectively.

These are not unreasonable standards as we shall see. In fact some instruments that have been constructed and described in these pages possess much more rigorous specifications and have a wide range of facilities. Take, for example, the M. L. Michaelis design, the Auditron, which has been fully described in previous issues of PRACTICAL WIRELESS with a wealth of incidental detail on oscilloscope design. Readers who wish to brush up on their basic information on the oscilloscope would be advised to turn up these back issues from September, 1962, to April, 1963, even if they have no intention of setting about the construction of this comprehensive instrument.

It is not proposed to cover the same ground in these articles; this must be stressed, for already there have been instances of readers requesting

specific constructional data on some of the instruments described in these articles. The author's purpose is merely to present a review of the types of instrument in modern use with a few comments on their employment.

### Fundamental Sections

Any oscilloscope must have certain fundamental sections and the wide differences in price that will be noted from a quick flick through the catalogues usually refers to the fine limits to which these sections are built, plus some extra facilities for special purposes.

Basically we have a cathode ray tube and a power supply, a vertical deflection amplifier, a horizontal timebase and, in many instruments, a horizontal deflection amplifier. The trace is displayed on the face of the c.r.t. by feeding a signal to the vertical deflection plates of the electrostatic tube while the internal timebase of the instrument drives the spot across the face of the tube by the sawtooth voltage applied to the X plates (horizontal deflection). See Fig. 1.

It is important that the sawtooth waveform be true in order to obtain a linear movement of the spot across the screen, and the speed of this movement must be such that the waveform applied to the Y plates will trace a small enough number of cycles to make an observable pattern. Thus, if a sample of mains frequency is to be checked, a 50-cycle supply is fed to the Y plates and the X timebase is adjusted to scan the width of the screen 50 times a second, and the result is the display of a complete single cycle. See Fig. 2.

This display will only be a steady trace if the speed of the timebase is synchronised with the frequency of the input—that is if the timebase is "triggered" by the signal. But this term "triggering" is used to apply to a special function and can be misleading here.

Normal procedure for simple scope construction is an X timebase that is controlled to run at just less than the input frequency, which then forces the display into synchronisation by feedback of a part of the Y signal to the X timebase. Triggering, however, refers to the principle of forcing the timebase into single responses so that the horizontal trace only occurs in step with each impulse from the Y signal.

The normal procedure is for the synchronising terminal on the oscilloscope control panel to be connected to the timebase via a potentiometer which reduces the Y input to prevent distortion. But it may be unnecessary where a "sync switch" is incorporated, for these instruments have an internal connection and an alternative external route to the X timebase, and the refinement of a "sync selector" completes the facilities and allows triggering. In addition to this, an X amplifier can

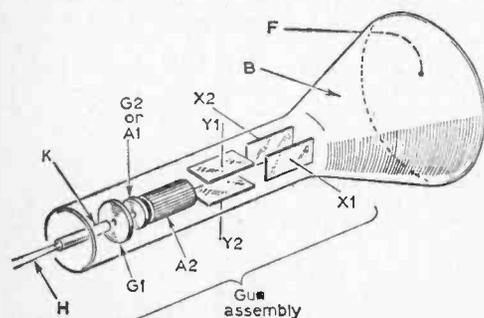


Fig. 1: Schematic view of electrostatically focused c.r.t.

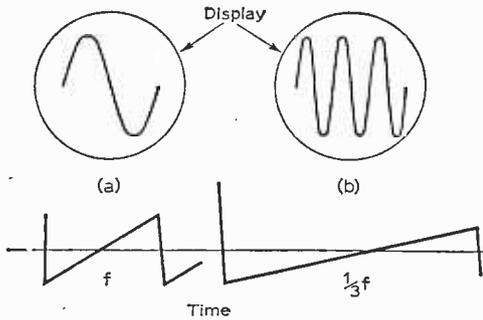


Fig. 2: Sawtooth timebase and sine wave input signal. (a) time of sweep duration approximates time of complete cycle of signal, (b) timebase running at one-third signal frequency.

be used to provide trace expansion, which allows a portion of the scanned waveform to be inspected.

**Trace Expansion**

As an example of the above facility of "trace expansion" an amplifier connected between the timebase and the X plates of the tube may have a gain which provides a linear expansion of ten times. The effective sweep length can be expanded from six to 60 centimetres and a portion of a waveform which would otherwise be too cramped for comfortable observation is displayed on the whole face of the small tube.

So we now have at least three controls for the X timebase: a coarse frequency control, giving typical ranges from 10c/s to 5 kc/s; a fine

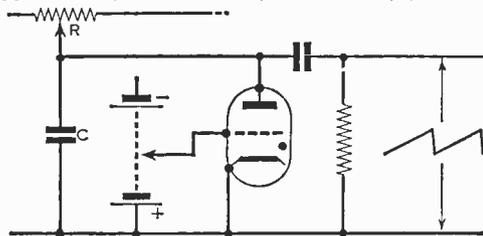


Fig. 3(a): Thyatron timebase.

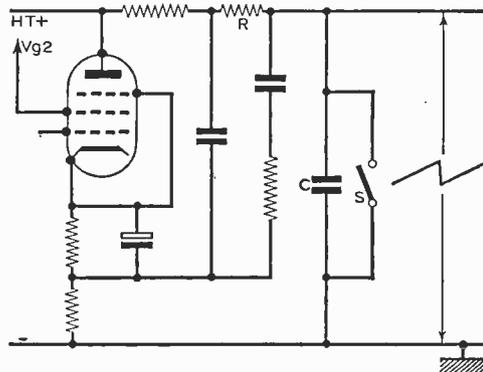


Fig. 3(c): Cathode follower, basic circuit.

Fig. 3(d) (right): Pentode as charge resistor.

frequency control which covers the intermediate frequencies of oscillation between the switched steps and a gain control which provides sweep expansion. Collectively these may be referred to as "sweep controls" and the typical specification denotes the time per sweep length as in milliseconds per centimetre. The range may be from 500msec to 1μsec per centimetre. This should not be confused with the frequency range of the oscilloscope, which refers to the coverage of the Y amplifier.

The generation of an accurate sawtooth voltage is an important part of oscilloscope design. A number of ingenious circuits have evolved both for the basic oscillator and for associated amplifiers. Some representative circuits are shown in Fig. 3 and the choice of an ultimate design depends largely upon the current requirements, the timebase frequency coverage, the c.r.t. characteristics and the general design of the rest of the instrument.

**Timebases**

Basically this part of the circuit consists of a means of charging and discharging a capacitor through a resistor. For this reason these components are marked C and R in the diagrams. Choice of components is made to ensure that the sweep speed allows the rise-time of the Y signal to be displayed over about one-tenth of the screen; that the flyback time should be as short as possible; and a blanking pulse is then applied to the c.r.t. to avoid the confusion of misleading traces and that synchronisation of the timebase with the Y signal is made possible.

There are various advantages and defects of


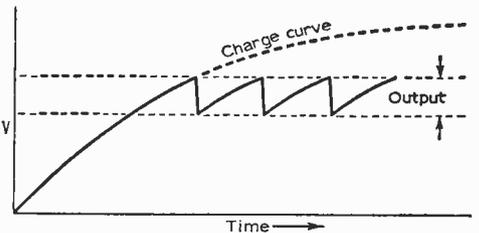


Fig. 3(b): Choice of CR combination affects position of sawtooth on charge curve.

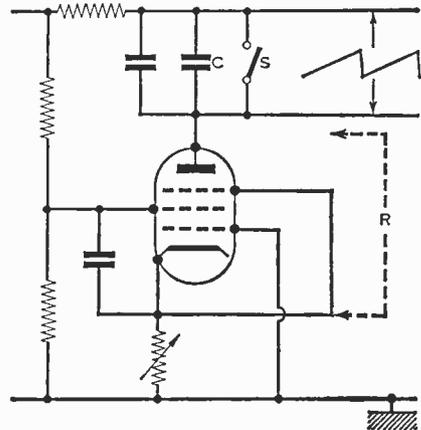

alternative circuits, but this is not the place to enter into a discussion—even a controversy—about oscillator design. Perhaps the most popular method of obtaining a “linear” sawtooth of sufficient output, with short flyback, is the Miller Transitron and this will be discussed at greater length.

Many of the older instruments employed a thyratron timebase such as illustrated in Fig. 3(a). Here the capacitor is charged to a determined voltage, but only partially discharged, and the output is a direct voltage on which the sawtooth is superimposed as in Fig. 3(b). The d.c. component is filtered out before application to the deflecting plates of the tube. But the introduction of a coupling circuit and, indeed, the necessary inclusion of some form of amplifier, affects the charge rate. Some velocity distortion may also be apparent by alteration of timebase frequency.

The amplifier can be designed within very accurate limits, but in this work it must be con-

sidered as part of the whole timebase and there are several considerations that apply. The time constants of the coupling components must be sufficiently high to avoid distortion of the transferred voltage and the output should be in phase with the input. A two-stage amplifier is therefore needed for a 180° phase shift.

Of course this phase shift can be obtained by other means, as demonstrated in the circuit of Fig. 3(c), where a cathode follower is shown. The switch S is the discharge device and, as we shall see, is part of the electronic circuitry, not a mechanical switch.

**Constant Current Device**

In another theoretical configuration, Fig. 3(d), the charge resistor R is replaced by a pentode valve, taking advantage of the fact that the anode current of a pentode is largely constant over a great part of the  $I_a/V_a$  characteristic as depicted in Fig. 3(e). The curvature of the characteristic can

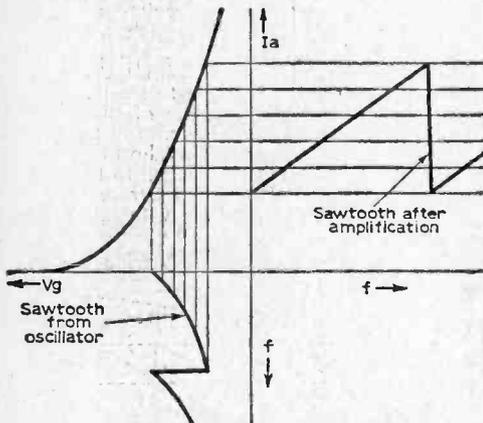


Fig. 3(e): Curvature of amplifier  $I_a/V_g$  characteristic can be used to correct distortion in exponential applied signal.

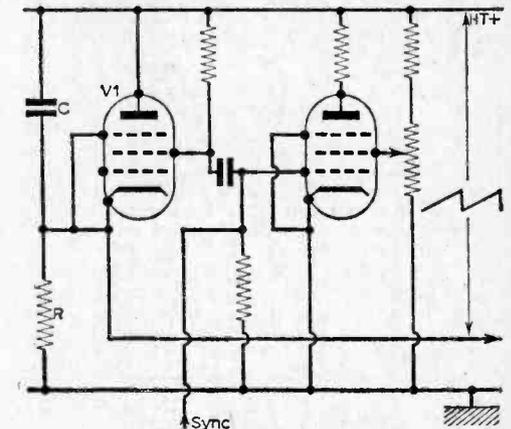


Fig. 3(f): Two-valve timebase with one pentode as feedback element and the other as switch.

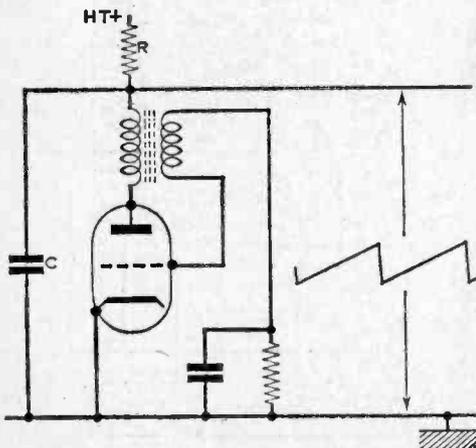


Fig. 3(g): Blocking oscillator timebase.

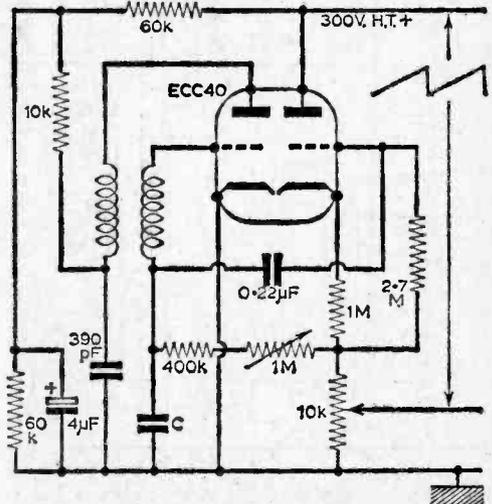




Fig. 3(h): Squugging oscillator timebase.

# THE WHARFEDALE Super Range

Each loudspeaker in this range is fitted with roll surround for low resonance and double diaphragm assembly for extended HF response.
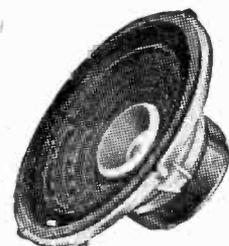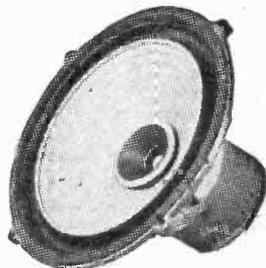
## SUPER 10/RS/DD

Impedance 10/15 ohms.  
Flux density 16,000 oersteds.  
Max. input 10 watts rms  
or 20 watts peak.  
Frequency range 30-20,000 c/s.  
Aluminium Voice Coil.  
Roll surround and double  
diaphragm.  
Bass resonance 38/43 c/s.  
Price: 218/8 inc. P.T.



## SUPER 8/RS/DD

Impedance 10/15 ohms.  
Ceramic Magnet.  
Flux density 14,500 oersteds.  
Total flux 60,000 maxwells.  
Aluminium Voice Coil.  
Max. input 6 watts rms  
or 12 watts peak.  
Frequency range 40-20,000 c/s.  
Bass resonance 50/60 c/s.  
Price: 134/2 inc. P.T.

## SUPER 12/RS/DD

Impedance 12/15 ohms.  
Flux density 17,000 oersteds.  
Total flux 190,000 maxwells.  
Aluminium Voice Coil.  
Max. input 20 watts rms  
or 40 watts peak.  
Frequency range 25-20,000 c/s.  
Bass resonance 26/32 c/s.  
Price: 350/- (no tax).



Write for information and fully illustrated 12 page booklet

# Wharfedale

WHARFEDALE WIRELESS WORKS LTD  
IDLE, BRADFORD, YORKSHIRE


Telephone: Idle 1235/6.

Telegrams: 'Wharfedel' Idle, Bradford.

# WEYRAD

## 6-TRANSISTOR 2-WAVE SUPERHET RECEIVER MODIFICATIONS NOW AVAILABLE FOR 500mW OUTPUT

<b>ROD AERIAL—RA2W</b>	
6 in. long, 3/8 in. diameter, connections to tags on Coils. For 208pF tuning capacity. Complete with Car Aerial Coil ... .. 12/8	
<b>OSCILLATOR COIL—P50/1AC</b>	
M.W. covered with 176pF tuning capacity, L.W. by extra padder ... .. 5/4	
<b>I.F. TRANSFORMERS</b>	
1st and 2nd Stage—P50/2CC ... .. 5/7	(2 required)
3rd Stage—P50/3CC ... .. 6/-	
<b>DRIVER TRANSFORMER—LFDT4</b> ... .. 9/8	
<b>OUTPUT TRANSFORMER—OPT1</b> ... .. 10/6	
<b>PRINTED CIRCUIT—PCA1</b> ... .. 9/6	

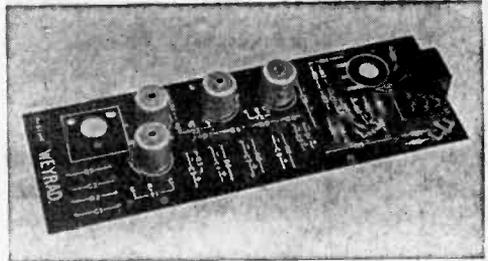

In response to many requests we have redesigned the output stages to give 500mW and to enable a standard 3 ohm Speaker to be used. Full details of the simple changes are given on a separate leaflet available on receipt of stamp.

<b>CONSTRUCTOR'S BOOKLET WITH FULL DETAILS</b> ... .. 2/-
<b>TRANSISTOR A.F. AMPLIFIER TYPE A.F.1—LOW IMPEDANCE INPUT, 3-TRANSISTOR, 500mW OUTPUT, FULLY ASSEMBLED WITH VOLUME CONTROL</b> ... .. 63/6

**WEYMOUTH RADIO MANUFACTURING CO., LTD.**  
REGENT FACTORY, SCHOOL STREET,  
WEYMOUTH, DORSET



of this famous Catalogue  
**NOW READY!**

This is the 4th Edition and 8th Re-printing of our Catalogue. In addition to enlarging it we have re-arranged many sections for easier reference. Customers who purchased earlier editions will need no encouragement to obtain this one. To new customers we would point out that of 5,000 items listed all but 14 are actually in stock, and that this unique catalogue is backed by a Mail Order Service second to none!

**OBTAINABLE ONLY  
FROM  
HOME RADIO  
OF MITCHAM**

**ONLY  
2'6  
PLUS 1/- POST  
AND PACKING**

**POST COUPON TODAY**  
Write CATALOGUE on top left of envelope

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_

Enclose P.O. 3/6

Home Radio Ltd. (PW), 187 London Road, Mitcham, Surrey

be used to provide compensation for an exponential waveform, as this diagram shows, and this design is the fundamental stepping point for the practical techniques that follow.

Our next circuit, Fig. 3(f), shows the connection of two pentodes with one acting as the switch part of the circuit and the other as the feedback element. A double triode can be used — and has been in many simple instruments for home constructors—but the higher input capacitance of the triode has its effect on the flyback ratio. In the arrangement of Fig. 3(f) no coupling capacitor is needed between the second anode and first grid, and the amplitude of the sawtooth is less dependent on frequency. A potentiometer control in the screen grid of the second pentode allows amplitude variation, controlling the anode current, and thus the V1 grid voltage and the anode voltage, consequently, at which V1 commences conducting.

This multivibrator circuit has its disadvantages: the cathode of V1, for example, is at a fairly high potential, and it is necessary to avoid high heater-cathode stresses by feeding the heaters from a separate power pack winding.

**Blocking and Squegging Oscillators**

A simple alternative, using a single valve, is the familiar blocking oscillator shown in Fig. 3(g).

This type of circuit will not often be used except for special applications, for its fundamental advantage, stability and high output at its resonant frequency, is also its basic drawback; less flexibility for frequency control over the wide range necessary for a "general purpose" instrument.

A more practical circuit, which can be built around the windings of a 470kc/s i.f. coil for experimental work, is the squegging oscillator of Fig. 3(h). By making C a series of switched capacitors between 150 and 50,000pF, and other components as shown, a timebase frequency of 20c/s to 20kc/s can be achieved with an amplitude of 54 to 42V peak to peak, a flyback ratio of 1:40

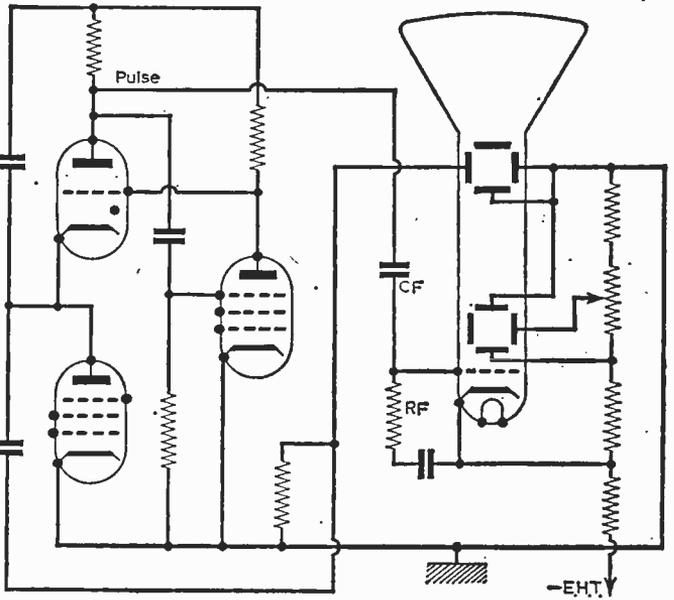


Fig. 4(a): Puckle timebase with blanking pulse applied to c.r.t. grid.

to 1:12, depending on the charge resistor setting, and a velocity error of -8.8 to -5.4%. This interesting circuit derives from the Philips Technical Library publication, "An Introduction to the Cathode Ray Oscilloscope", by Harley Carter, A.M.I.E.E.

**Eliminating Flyback**

Blanking circuits are deceptively simple. On many television receivers, for example, the "frame flyback" components consist of no more than a capacitor and resistor taken from a convenient point in the frame oscillator/output. A similar principle is used for some oscilloscope timebases as in the case of the Puckle timebase shown in Fig. 4(a). The need for a flyback eliminator becomes apparent as the frequency of the signal under inspection is raised. Fig. 4(b) shows the sort of trace one would expect from a 1Mc/s timebase and a signal of a frequency that provides about three complete cycles of trace. The outward trace has a 3μs duration and the flyback pulse 2μs. The result is that for three cycles of our required signal we obtain also two cycles of a flyback signal. Suppression of the flyback provides us with a clear trace as in Fig. 4(c). This is done by applying a negative pulse to the grid of the tube with a high-rated capacitor and a suppression resistor connected from a convenient circuit point.

This is not always so simple as it appears: there is a risk of cross-modulation and parasitic oscillation at the higher timebase frequencies, which is just when the flyback elimination is most needed. Moreover the connection of the blanking circuit to the oscillator may affect its stability and there may not be a convenient point to extract a negative pulse. It is for this reason that we sometimes come across an additional stage; a positive pulse is taken and a phase inverter added.

**PART 7 APPEARS NEXT MONTH.**


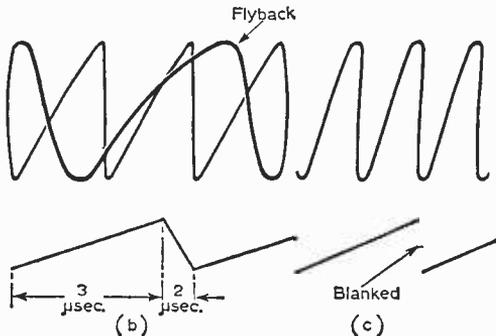


Fig. 4(b): Display showing three cycles with flyback; (c): Display showing same trace with flyback blanked.

# THE MALVERN TAPE RECORDER

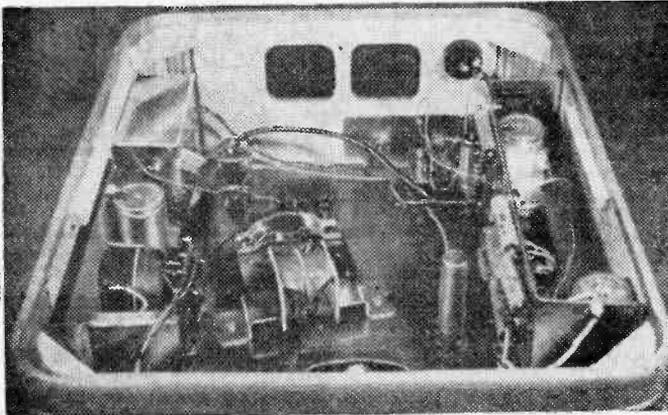

By  
T. Snowball

CONTINUED FROM PAGE 219 OF THE JULY ISSUE

**T**HE output transistors are fed from Tr4 the OC71 driver, the collector load of which is somewhat more complicated than usual; the load resistor being the 1.8k $\Omega$  resistor R21 and the diode OA10.

A small d.c. voltage is developed across this diode due to the collector current, but of course no signals are developed across the diode, because of its low a.c. resistance. The small d.c. voltage developed this way is used to stabilise the quiescent current in the output transistors. The diode voltage changes with temperature and so controls the base voltages on the output transistors and keeps their current steady with variation in temperature.

The 100 $\mu$ F capacitor C16 feeds the audio signals on to the top of the 1.8k $\Omega$  resistor R21, so allowing larger drive signals to the output transistors during large volume peaks. Negative feedback comes via the 33k $\Omega$  resistor (R18) to the base of the driver transistor Tr4. If the centre point of the output stage tends to move, current is fed back through the 33k $\Omega$  resistor, which tends to cancel the original change; this works for both d.c. to counteract temperature changes, and for a.c. to reduce distortion and to lower the output impedance.

The output driver stage is fed from Tr3 with the treble boost circuit as the coupling network.

#### Treble Boost Amplifier

Tr3 (OC71) is a rather more normal stage with some negative feedback due to the 22 $\Omega$  resistor R13 in its emitter lead. The 1k $\Omega$  collector load

R12 feeds the treble boost circuit, which consists of a series resonant circuit L1, C11 shunted by a resistor (R16) and capacitor (C12). Without the shunt resistor, signals could only go through at the resonant frequency, thus the boost of high frequencies would be considered to be very large. But with the shunt resistor, the gain at other frequencies can be set by this resistor. With the value used the resistor cuts the gain by 6dB and when the coil resonates the signals go straight through. The sharpness of the peak depends on the "Q" of the tuned circuit and the value of the shunt capacitor, because this starts to feed the high frequencies through before the inductor resonates. This was shown in Fig. 2, last month.

The volume control VR1 precedes this stage and controls the amount of output applied from the feedback pair in the pre-amplifier stage.

#### Pre-amplifier

On record, the pre-amplifier consists of two transistors Tr1 and Tr2, GET106 (OC45) and OC71. These transistors are d.c. coupled in a temperature stabilised circuit, whose response is uniform from 50c/s to 5kc/s.

The first transistor is a GET106, which is used at a very low collector current of 400 $\mu$ A, to provide a low noise performance. The 200 $\mu$ F capacitor C6 decouples the feedback path to a.c., while the 4.7k $\Omega$  resistor R4 sets the current in the first transistor, by feeding in the voltage existing at the junction of the two 220 $\Omega$  resistors R6, R7.

Of course, as this is a feedback circuit the

# RADIO CLEARANCE LIMITED

27 TOTTENHAM COURT ROAD, LONDON W.1

THE OLDEST COMPONENT SPECIALISTS IN THE TRADE

TRADE ENQUIRIES INVITED

Telephone: MUSEUM 9188

EST. 35 YRS.

## AGAIN CRASHING THE SOUND BARRIER!

Enormous purchases of Brand New and Guaranteed Plessey loudspeakers enable us to offer these units at THE LOWEST PRICES EVER! Don't miss this golden opportunity to obtain a first-grade permanent-magnet LOUDSPEAKER off the production line at LESS THAN THE MANUFACTURER'S COST! Read carefully the prepared list below and choose just the right speaker for the job—COMPARE THE PRICES ANYWHERE!

### SCHEDULE OF LOUDSPEAKERS AVAILABLE

Diameter in inches	Gauss in lines	Imped. in ohms	Price	Diameter in inches	Gauss in lines	Imped. in ohms	Price	Diameter in inches	Gauss in lines	Imped. in ohms	Price	Diameter in inches	Gauss in lines	Imped. in ohms	Price
2	7000	80	8/-	4	9500	3	8/6	5	4000	3	8/-	5	6000	25	10/6
2 1/2	7000	35	8/6	4	9500	5	9/8	5	6000	5	8/-	5	6000	30	10/6
2 1/2	7000	50	8/6	4	6000	25	10/8	5	7000	3	8/8	5	9500	25	11/6
2 1/2	7000	80	8/-	4	7000	25	11/8	5	7000	5	8/8	5	9500	35	11/8
3	8500 (E.M.L.)	3	8/6	4	8000	35	10/8	5	7500	3	9/-	5	10000	25	18/-
3 1/2	7000	35	8/6	4	7000	35	11/-	5	8500	5	9/8	6 1/2	7000	5	11/-
3 1/2	9500	50	10/8	4	9500	35	11/6	5	9500	3	10/8	6 1/2	8500	3	11/8
4	6000	3	7/6	4 tweeter	6000	3	7/8	5	3500	5	10/8	8	7000	3	12/-
4	6000	3	8/-	4 "	7000	5	8/-	5	10000	3	11/8	8	8500	3	12/6

Elliptical Size	Gauss in lines	Imped. in ohms	Price	Elliptical Size	Gauss in lines	Imped. in ohms	Price	Elliptical Size	Gauss in lines	Imped. in ohms	Price	Elliptical Size	Gauss in lines	Imped. in ohms	Price
5 x 3	6000	3	7/8	6 x 4	8500	3	9/6	7 x 4	9500	50	11/6	8 x 2 1/2	9500	5	10/-
5 x 3	7000	3	8/-	6 x 4	9500	3	10/-	7 x 4	10000	15	13/6	8 x 2 1/2	10000	5	10/8
5 x 3	9000	3	8/6	6 x 4	9500	5	10/-	7 x 4	9500	3	13/8	8 x 5	8000	3	9/8
5 x 3	9000	4	8/8	7 x 3 1/2	9500	3	10/8	8 x 3 1/2	6000	3	8/8	8 x 5	7000	3	9/-
5 x 3	9500	5	8/8	7 x 4	7000	3	10/-	8 x 3 1/2	7000	3	9/-	8 x 5	8500	3	9/8
5 x 3	6000	25	9/8	7 x 4	7000	5	10/-	8 x 3 1/2	7000	5	9/-	8 x 5	9500	3	10/-
5 x 3	7000	25	10/-	7 x 4	8000	3	10/8	8 x 2 1/2	6000	6	8/8	8 x 5	9500	15	12/8
5 x 3	9000	25	11/-	7 x 4	9500	3	11/-	8 x 2 1/2	6000	30	9/8	8 x 5	10000	3	10/8
5 x 3	9000	35	11/-	7 x 4	9500	4	11/-	8 x 2 1/2	8500	5	9/8	8 x 5	12000	3	11/-
6 x 4	6000	3	8/8	7 x 4	9500	5	11/-	8 x 2 1/2	9500	3	10/-	8 x 5	12000	15	14/8
6 x 4	7000	3	9/-	7 x 4	9500	30	11/8	8 x 2 1/2	9500	4	10/-				

ALLOW 2/- each speaker for postage and packing, and please specify the exact requirements—the nearest available will be sent.

## OVER 50,000 SOLD & STILL THE DEMAND CONTINUES FOR OUR 'HEAVENLY TWINS'

Ask for a demonstration in the shop.

### "CAPRI"

Sensitive!  
Super-selective!  
Superb Speaker!  
New Price  
NOW ONLY  
**79/6**



(2/- p. & pkg.)  
Pocket Super-het MW and Drottwich  
Size 4 1/2 x 2 1/2 x 1 1/2 in.  
Constructional data 1/9  
Post Free.

The best and easiest transistor build-yourself sets available.

Send S.A.E. for FREE PARTS LIST

6 First Grade MULLARD Transistors, Diode(s) and all components BRAND NEW and GUARANTEED

Choice of a dozen stations in daylight . . .


"CONTESSA Mk III" 'QUEEN OF THEM ALL'

ONLY **£9.19.6**

(3/6 p. & pkg.)

PORTABLE CAR RADIO  
2 WAVEBAND SUPER-HET

Construction manual 2/10 Post Free.

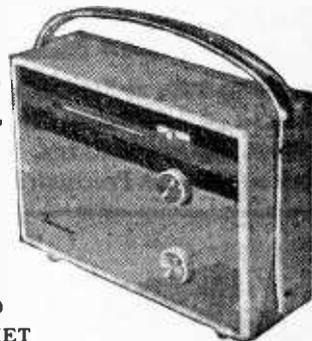

Inclusive price for all associated components, case, battery and instruction Book complete in every detail.  
ANY PARTS SOLD SEPARATELY ON THE BUILD-AS-YOU-BUY SCHEME

CONTESSA III **£9.19.6**  
CAPRI **79/6**

(plus 3/6)  
(plus 2/-)

### SELECTED GUARANTEED BARGAINS—BRAND NEW

Beautifully geared AM/FM 2 Gang Condensers, 4/6; AM/FM IFT's 465kc/s and 10.7 Mc/s, 4/6 pair; Magnavox Crystal Tape Recorder Mike, 12/8; Double-tuned Transistor tetrox IFT's Q120, 470 kc/s, 5/6 pr.; 3 matched IFT's and oscillator coil for Mullard transistor circuit, 10/6 the set; Plessey-Bry head turret tuners 34/38 Mc/s, valved 8/6 each; 3 watt Stereo Amplifiers, complete, ready to switch on 79/6; Sentercell rectifiers R32D-D3-2-1Y, 2/6 each. GERMANIUM DIODES—0A70, 0A79, 0A81, 0A90, CG46H, 2/- each. TRANSISTORS: Set of 6 (RF and LF) including 1 watt matched pair, heat sink and diode, 13/8 the set; OC44 (or equiv.), 6/9, OC45 4/6, OC81 5/6; matched pair 12/-, PXC 101A 4/6, matched pair 9/6, PXA 101 3/9, AF 115 4/6, SB 305 2/-, Submin. Germanium diode 1/3. Please send STAMPED and ADDRESSED envelope with any enquiry. We regret no catalogues—our stocks move too quickly! Kindly make provision for additional postage and packing charges to avoid delay.

TERMS: CASH WITH ORDER or C.O.D. ON ORDERS OVER 10/-.

TEST METERS



**20,000 OHMS PER VOLT MODEL TP-6S** (illustrated). Reads voltages up to 1,000 D.C. at 20,000 ohms per volt and A.C. at 10,000 o.p.v.; D.C. current to 200 mA; Resistance to 10 Mega. Capacitance to 0.1  $\mu$ F; Decibels from -20 to +36. Size 3 1/2 x 5 1/2 x 1 1/2 in. £5.19.6.

**2000 OHMS PER VOLT MODEL TP-10.** Reads A.C. and D.C. volts up to 1,000; D.C. current to 500 mA; Resistance to 1 Meg.; Capacitance to 1  $\mu$ F; Decibels from -20 to +36; Output Jack for Audio measurements. Size 3 1/2 x 5 x 1 1/2 in. £3.19.6.

**50,000 OHMS PER VOLT MODEL 500.** Reads voltages up to 1,000 D.C. at 50,000 ohms per volt, and A.C. at 15,000 o.p.v.; D.C. current to 12 amps.; Resistance to 50 Mega; Decibels from -20 to +56. Size 3 3/16 x 6 7/16 x 2 1/2 in. £3.19.6.

**LAYOUE UHF WAVEMETER MODEL 105.** Coverage 375/725 Mc/s. Complete with correct Calibration Chart. First-class condition. Battery operated and portable, size 11 x 8 x 7 1/2 in. ONLY £3.19.6 (carriage 7/6).

**HRO SENIOR TABLE MODEL RECEIVERS.** Complete with 9 coils sets covering 50 Kc/s to 30 Mc/s. Used, very good condition, aerial tested. A few rare Model 5T with I.O. valves, £29.10.0 (carriage 30/-)

**DOUBLE BEAM OSCILLOSCOPE TUBES.** Another purchase of Type CY 1390, equivalent to Cosmor 09D as used in Oscilloscopes by Cosmor (339 series) and Hartley & Erskine (13 series). Listed £12 Brand new in maker's crates 25/- (car. 5/-)

**CRYSTAL DESK MIKE** with screened lead and built-in stand. ONLY 18/6. (Post 1/6)

**COSMOR TYPE 1035 DOUBLE BEAM OSCILLOSCOPES.** A few only of these modern scopes, overhauled and in perfect order ONLY 44s. Further details on request.

**AMERICAN DESK TELEPHONE,** complete with handset. Non-dial type, but has internal bell. Ideal for extension or inter-com. BRAND NEW. ONLY 30/- (Post 4/-).

**ACOG 39/1 STICK MIKE** with screened lead and table stand. ONLY 39/6. (Post 1/6.)


FOR COMMUNICATION RECEIVERS

Manufactured by Pye and Philips. One of the Army's most versatile and sensitive sets. RF stage and 2 of IF, using 6 British I.O. type valves. Large 180 degrees Illuminated and Calibrated Dial. Flywheel tuning with locking device. Aerial trimmer. Tone and volume controls. Band switch from panel jacks for speaker or phones. In black metal case, size 17 1/2 x 8 1/2 x 10 1/2. Model PCB covers 6-18 Mc/s, 200-650 metres and 850-2,000 metres and has internal 5in. speaker, £6.19.6. Model PCB2 has similar L & M waveband coverage. Short wave 6-22 Mc/s. but no speaker. Used but excellent condition, £5.19.6. Model PCB3. As PCB2 but has 2 Short Wave Bands, 2.0-7.0 Mc/s and 7.0-23.0 Mc/s. and Medium Wave Band 190-530 metres. ONLY £6.9.0. Every receiver aerial tested before despatch. Add 10% carr. all models. Designed to operate from bulky external power supply, but any set can be fitted with BRAND NEW COMPONENTS INTERNAL PACK for 200/250 v. A.C. at extra cost of 8s. S.A.E. for illustrated leaflet.

THE "GOOD COMPANION" Mk. II

Using transfilters, the latest manufacturing technique to save alignment difficulty. The finest combined portable and car radio yet designed for the home constructor.

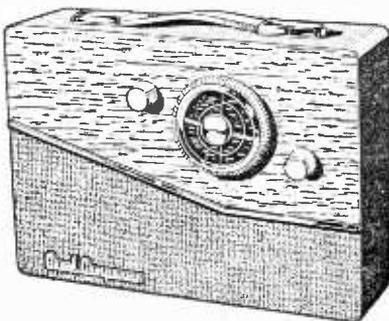- ★ 750mW output.
- ★ 6 transistors and diode.
- ★ Full Medium and Long Wave coverage.
- ★ Quality speaker.
- ★ Brilliantly styled 2-tone cabinet, size 11 x 8 x 3 in.
- ★ Very fine tuning with calibrated dial.
- ★ Latest printed circuit.
- ★ Internal high gain aerial with car aerial socket.
- ★ Easy to follow construction data (available separately 3/6).



Total cost **£9.19.6**

All parts sold separately and full illustrated details will be sent on request. With alternative luxury cabinet using 7 x 4in. speaker, £10.19.6. Either type, plus 3/- post and ins. (Battery 3/6 extra).

"Practical Wireless" 6 transistor Personal Receiver. 2 band printed circuit, etc. Building cost £7.19.6. "Pocket 4" Transistor Personal. Ideal for beginner. Building cost 42/6. All components sold separately, price lists for either of above S.A.E.

**MINIATURE MOTORS.** Ideal for models. Operates on 3-6 volts D.C. Size 1 1/2 x 1 x 1 1/2 in. plus pin spindle. BRAND NEW 5/- or 6 for 25/-. 20/- CONSTRUCTOR'S PARCEL. Assorted colours wiring wire, solder, resistors, condensers, volume controls tag panel. ALL NEW (Post 2/6). **RESISTORS.** 100 assorted values our choice. NEW 10/-. **CONDENSERS.** 100 assorted mica and altermica. NEW 12/6.

HARRIS ELECTRONICS (LONDON) LTD.

139 GRAY'S INN ROAD, LONDON, W.C.1 Telephone TERMINUS 7937 Please include carriage costs on ALL items. Open until 1 p.m. Saturdays. We are 2 mins from High Holborn (Chancery Lane Sta.) and 5 mins. bus from Kings Cross.

**JACKSON** the big name in PRECISION components


Precision built radio components are an important contribution to the radio and communications industry. Be sure of the best and buy Jackson Precision Built Components.

**"00" Twin Condenser**

Designed for use in miniature transistor receivers. The front (aerial) section is 208 pF to provide coverage for medium waves, and the rear section is 176 pF, which may be padded to match the oscillator—very robust yet lightweight. Front area 1 1/2 in. x 1 1/2 in. x 1 1/2 in. deep.

**JACKSON BROS. (LONDON) LTD.**  
(Dept. P.W.) KINGSWAY-WADDON,  
CROYDON, SURREY  
Phone: Croydon 2754-5. Grams: Walfico, Souphone, London

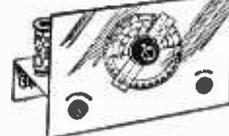LISTEN TO THE WORLD on TELSTAR our I-VALVE SHORT WAVE RADIO



Receives speech and music from all over the world. Price includes valve and one coil covering 40-100 metres. Can be extended to cover 10-100 metres. Can be converted to 2 or 3 valve and all-aims speaker use. Total Building Costs 35/- P. & P. 2/-.

THE R.C.S. PERSONAL SET

For Private Listening  
An amazing little set, with built-in ferrite rod aerial bringing in medium wave at wonderful volume. Sturdy case. Size only 2 1/2 x 3 1/2 x 1 in. Fits into the palm of the hand. Drilled chassis colour coded for easy assembly. Total Building Costs (including earpiece) 30/- P. & P. 2/-.

AMAZING RESULTS from OUR LATEST

5-STAGE TRANSISTOR RECEIVER

A highly sensitive receiver using top grade transistors and components. Fully tunable over medium wave. ★ Can be built in 1 hour. ★ High flux moving coil speaker. ★ Built-in ferrite rod aerial. ★ Specially designed coils for maximum signal strength. ★ Volume on/off control. ★ Etched circuit board. ★ Easy to follow building plan.



Total Building Cost P. & P. 50/- 2/6.

R.S.C. CRYSTAL RECEIVER

Covering medium wave band, ideal for the beginner! All components in- 8/6 P. & P. cluding case. 1/6. (Suitable headphones 8/6). Easily converted to 1-transistor or 2-stage transistor receiver.



All parts available separately. Send S.A.E. for free layout plans and parts lists on any of the above sets.

**R.C.S. PRODUCTS (RADIO) LTD.**  
11 OLIVER ROAD, LONDON, E.17  
(Mail Order Only)

characteristics of the transistors are largely taken out by the negative feedback; but unusual transistors may cause variations which cannot be taken care of by the feedback.

If any trouble is experienced, the best way of checking the circuit is to measure the supply at the circuit, while on record—which is the condition which gives the lowest voltage. Assume this measures 10V, then as the emitter of Tr2 should be at 0.3V, it is obvious that the collector of Tr2 should be between 3.5V and 6V in order to allow large voltage swings before cut-off or bottoming.

So with the h.t. supply of 10V and collector load of 8.2kΩ the current should be between 0.5mA and 0.8mA, which of course is the easiest to measure, unless a high resistance testmeter is available.

**Input Conditions**

The input to the pre-amplifier is fed in through series resistors of 1.5MΩ (R1) and 100kΩ (R2) in order to accommodate various amplitudes of input signals. As a guide, crystal microphones and magnetic pick-ups will be best connected via the 100kΩ resistor and high impedance outputs from radio tuners and crystal pick-ups through the 1.5MΩ resistor.

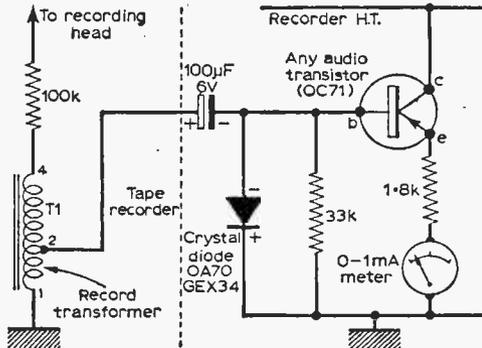


Fig. 4: A suggested recording level monitor.

**THE PLAYBACK CIRCUIT**

When used on playback the erase oscillator is switched off by the record/playback switch and the output stage remains as for "record", with the exception that the loudspeaker is joined directly across the output.

The treble boost circuit is removed from the collector or Tr3, and an RC circuit is inserted in its place. This gives a gradual rise of up to 3 or 4dB at 4kc/s in order to compensate for tape and head losses as already mentioned.

The characteristics of the feedback pre-amplifier are considerably changed by the removal of the 200µF capacitor C6.

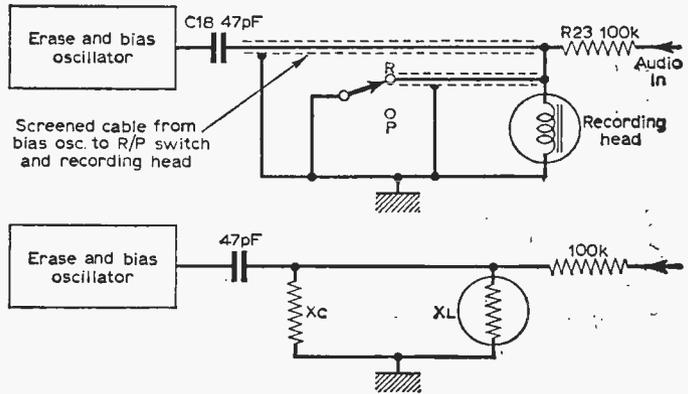


Fig. 5: Illustrating the effect of a long cable on bias power. Ordinary screened cable has a capacity of about 50pF/ft. If one foot of such cable is used at 60kc/s then Xc=50kΩ and XL=60kΩ, thus half the bias power will flow through the cable.

The pre-amplifier now becomes an LR integrator, with the head inductance and the 4.7kΩ resistor R4 as the active elements. This provides a characteristic falling at 6dB octave that would be correct for an ideal head and tape. But as was shown earlier the output has to stop falling and remain roughly constant up to 4 or 5 kc/s. This is achieved by the 0.5µF capacitor C5 which removes the feedback at 1kc/s and above.

The overall frequency response was shown in Fig. 3 in which it can be seen that it is not linear at the low frequency end; this is due to the resistance of the head, but with the characteristic as shown it is matched to the system.

**ADDITIONAL FACILITIES AND IMPROVEMENTS**

So now, as in Fig. 1 is a tape recorder with facilities for monitoring the output as recording is in progress, switching to external loudspeakers, and also the possibility of some extra facilities by the addition of simple switches.

**Straight-forward Amplifier**

For instance, the motor switch S3 stops the motor when the recorder is required as an amplifier for records or radio. All that is required to perform this function is to put the record/play switch at record.

This switch is, of course, spring-loaded and should not be held in position by the tape deck control while the motor is not running; otherwise indentations may be made on the pinch roller. The solution here is to prepare a small block of wood which can be dropped in and so hold the record/play switch at record. Also when the motor is stopped, the switch cuts out the series resistor in the loudspeaker circuit, and also stops the erase oscillator by breaking the earth lead from chassis. This is a precaution to avoid overheating of the erase head if left on for long periods; or to prevent erasure of a small portion of tape near the head.

**Extending the Frequency Response**

If the constructor includes in his specification a larger loudspeaker housed in a separate cabinet, he

no doubt would like to improve the recorder in order to take advantage of the better quality available.

The frequency response can be extended to at least 6kc/s by means of tuning the treble boost inductor to 6kc/s and increasing the amount of boost to 12dB. This is done by changing C11 to 2,000pF, R16 to 5.6kΩ and C12 to 0.003μF at the expense of 6dB in signal to noise ratio.

**Minimising Distortion**

In order to minimise distortion, a check in bias level is useful.

There is an optimum value of bias which gives less distortion but needs more h.f. boost to be applied during recording. The lower ranges of bias give more output from the tape on playback, but more distortion.

If the constructor wishes to check the bias current, a 50Ω resistor should be inserted in the earthy end of the recording head, and of course with 1mA r.m.s. bias current, there should be 50mV r.m.s. across the resistor. This can be adjusted by varying the value of the capacitor C18.

The measurement demands an oscilloscope or valve voltmeter because of the low levels.

The correct bias current for any particular tape is arrived at by recording a sine wave at 400c/s and increasing the bias in known steps from 0.4mA to 1.2mA. Then, when playing back, the output will be found to increase at first and then decrease; when it has dropped by about 2dB, this is the bias level for minimum distortion.

**Recording Level Meter**

The use of a recording level meter will mean that when recording large ranges of signal levels, such as orchestral items, it will be easier to make sure that the loud passages do not overload, and the quiet passages do not get lost in noise and hum. As the output stage is of very low output impedance it is easy to drive a cheap 1mA meter using a circuit as given in Fig. 4.

A simple transistor amplifier is used to drive the meter, since this was considered cheaper than using a more sensitive meter, such as 100 or 200μA movement. The circuit consists of a shunt diode rectifier and an emitter follower to provide a low drain on the rectifier, and also to supply the current for the meter. The 1.8kΩ resistor sets the meter reading and will give half-scale reading for the normal recording peaks, that is 150mA. The 33kΩ sets the amount by which the meter is slugged. These values may be adjusted as found necessary.

**CONSTRUCTION**

Plugs and sockets can be used to connect the deck to the circuits, but inevitably they add quite a lot of capacity to the head wiring, thus endangering the h.t. response and of course shunting the h.f. bias. This can be seen in Fig. 5 in which the cable from the bias feed point on the oscillator can be seen as a shunt capacitor to the h.f. bias, so indicating the need for as short a lead as possible.

**Three Sub-Units**

Bearing these points in mind, this tape recorder is built in three sections.

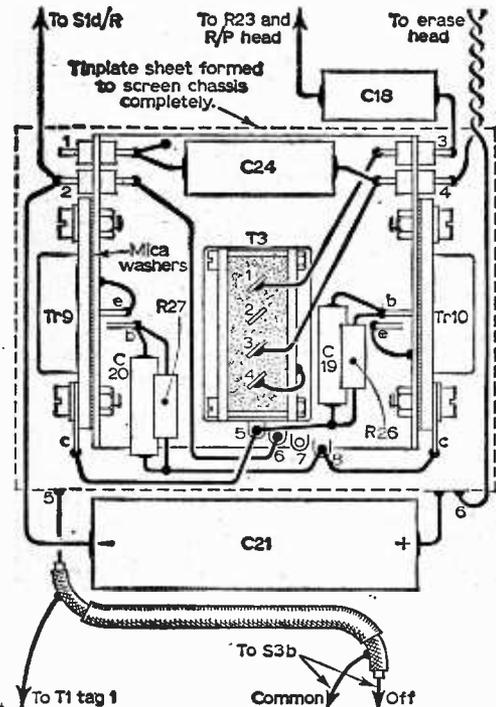


Fig. 6: Layout of the erase oscillator.

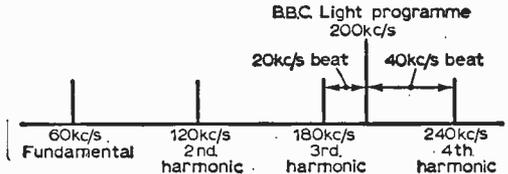


Fig. 7: Relationship between the frequencies of the bias oscillator and the broadcast station.

The three sections are easily seen in the illustrations and consist of (1) record/playback amplifier, (2) erase oscillator, and (3) power unit. Actually the head transformer is mounted separately on the tape-deck chassis, in order to get short leads to the erase chassis and to record/playback switch.

The erase oscillator should be reasonably well screened, as previously mentioned, in order to avoid pick-up in the amplifier; and also in this respect the lead from the bias output to the record/play switch and head transformer should be screened, short coaxial cable is best but ordinary screened cable will do if kept short.

**Erase Oscillator**

A sketch is shown in Fig. 6 giving details of how the erase oscillator was built. A screening can was made from thin tin, bent to shape and soldered to the chassis in two or three places after checking the operation of the circuit.

The chassis acts as a heat sink for the transistors but of course they must be electrically insulated from the chassis by thin mica washers. Suitable washers are usually supplied with the transistors. Remove all the sharp edges from the mounting

# PORTABLE TRANSISTOR RADIOS

## BACKED BY SUPER AFTER SALES SERVICE

### ROAMER SEVEN

● 9 stages—7 transistors and 2 diodes.

Covers Medium and Long Waves, Trawler Band and two Short Waves to approx. 17 metres. Push-pull output for room filling volume from rich toned heavy duty 5in. speaker. Ferrite rod aerial for M & L waves and telescopic aerial for S Waves. Air spaced ganged tuning condenser ensures wonderful station selection. Simulated hide case with gilt trim and shoulder and hand straps. Size 9 x 7 x 4in. approx. **The perfect portable and the ideal car radio.** (Uses PP9 battery available anywhere.)


### 5 WAVEBAND PORTABLE OR CAR RADIO

Amazing performance and specification

Total cost of all parts

**£7.9.6.**

P. & P. 5/6.

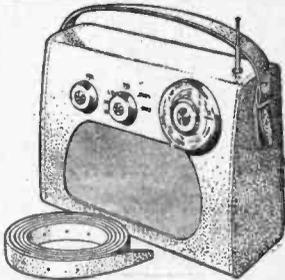Parts Price List and easy build plans 3/-.  


### MELODY SIX NEW!



● 8 stages—6 transistors and 2 diodes.

Our latest completely portable transistor radio covering medium and long waves. Incorporates pre-tagged circuit board, 3in. heavy duty speaker, top grade transistors, volume control, tuning condenser, wave change slide switch, sensitive 6in. ferrite rod aerial. Push pull output.

Wonderful reception of B.B.C. Home and Light, 208, and many continental stations. Handsome leather look pocket size case, only 6½ x 3½ x 1½in. approx., with gilt speaker grille and supplied with hand and shoulder straps.

Total cost of all parts **£4.9.6** P. & P. 3/-. Parts Price List and easy build plans 2/-.

### POCKET FIVE

● 7 stages—5 transistors and 2 diodes.


Covers Medium and Long Waves and Trawler Band, a feature usually found in only the most expensive radios. On test Home, Light, Luxembourg and many Continental stations were received loud and clear. Designed round supersensitive Ferrite Rod Aerial and fine tone 3in. moving coil speaker, built into attractive black case with red speaker grille. Size 5½ x 1½ x 3½in. (Uses PP4 battery available anywhere.)



Total cost of all parts **59/6**

P. & P. 3/-.  
 Parts Price List and easy build plans 1/6.

### SUPER SEVEN

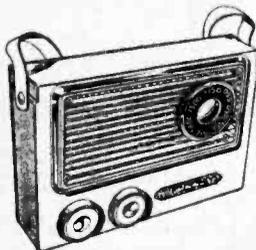

● 9 stages—7 transistors and 2 diodes.

Covers Medium and Long Waves and Trawler band. The ideal radio for home, car or can be fitted with carrying strap for outdoor use. Completely portable—has built in aerial for wonderful reception. Special circuit incorporating 2 R.F. stages, push pull output, 3in. speaker (will drive larger speaker). Size 7½ x 5½ x 1½in. (Uses PP9 battery available anywhere.)

Total cost of all parts

**£4.19.6** P. & P. 3/6.

Parts Price List and easy build plans 2/-.


### TRANSONA FIVE

● 7 stages—5 transistors and 2 diodes.

Fully tunable over medium and Long Waves and Trawler Band. Incorporates Ferrite rod aerial tuning condenser, volume control, 3in. super tone speaker, etc. Attractive case. Size 6½ x 4½ x 1½in. with red speaker grille and carrying handle. (Uses PP4 battery available anywhere.)


Total cost of all parts **59/6**

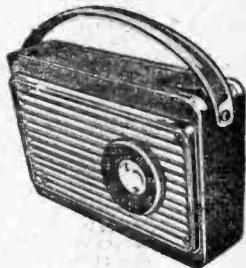P. & P. 3/-.  
 Parts Price List and easy build plans 2/-.



"Home, Light, A.F.N., Lux., all at good volume."  
 G.P., Durkoin.

### ROAMER SIX

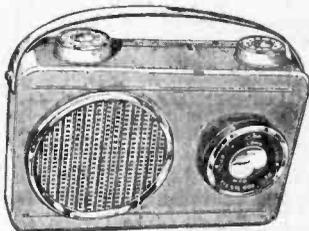

● 8 stages 6 transistors and 2 diodes.

Listen to stations half a world away with this 5 waveband portable. Tunable on Medium and Long waves, Trawler Band and two Short waves. Sensitive ferrite rod aerial and telescopic aerial for short waves. Top grade transistors, 3-inch speaker, handsome case with gilt fittings. Size 6½ x 4½ x 1½in.

Total cost of all parts

**£5.9.6** P. & P. 3/6

Parts Price List and easy build plans 3/-

All components used in our receivers may be purchased separately if desired. Parts price lists and easy build plans supplied free with sets of parts or available separately at prices stated.

## Radio Exchange Co.

27 HARPUR STREET, BEDFORD

Phone 2367 ● Opposite Co-Op. ● 10-1 p.m. Sats.

# FEATURED IN

## THE Radio Constructor


### JULY

**Converting Battery Portables to Transistor Operation by T. Snowball.**  
A practical method of modernising your old set, whilst retaining most of the original components.


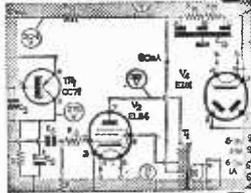
### AUGUST

**Low Cost Hi-Fi Amplifier by G. A. Stevens.** A design using the minimum number of components consistent with obtaining Hi-Fi performance.



### AUGUST

**Inexpensive Medium and Short Wave Receiver by Ian McDonald.** An easy-to-build 3-valve "straight" mains operated receiver.



## THE Radio Constructor

PUBLISHED ON THE 1st OF EACH MONTH, PRICE TWO SHILLINGS, BY DATA PUBLICATIONS LTD., 57 MAIDA VALE, LONDON W.9.

### ANOTHER TAPE RECORDER BARGAIN

Mfrs. end of production  
Surplus Offer



A 24 gns. Tape Recorder offered at the bargain price of only 15 gns. plus 10/- carr. Supplied in 3 Units already wired and tested. A modern Circuit for quality recording from Mike, Gram or Radio, using latest B.S.R. Twin Track Monardeck Type TD2 Valve line up 6F86, ECL82, EM84, EZ280 and Silicon Diode.

- 2 tone Cabinet and 8" x 5" Speaker. Size 14" x 10 1/2" x 7 1/2"
- Wired Amplifier complete with 4 Valves, front Panel, Knobs, etc.
- B.S.R. Monardeck Type T.D.2

**£3.10.0** +5/- Carr.

**£5.12.6** +3/6 Carr.

**£7.7.0** +4/6 Carr.

**£1.0.0** +2/- Carr.

**15 gns.** +10/- Carr.

BARGAIN PRICE

Items above

### RECORDING TAPE—Reduced Prices

Famous American Columbia (CBS) Premier Quality Tape at NEW REDUCED PRICES. A genuine recommended Quality Tape—TRY IT! Brand new, boxed and fully guaranteed. Fitted with leader and stop foils.

	Standard	Long Play	Double Play
5in.	800ft. 13/-	900ft. 17/6	1,200ft. 31/6
5 1/2in.	900ft. 16/-	1,200ft. 19/6	1,800ft. 37/6
7in.	1,200ft. 21/-	1,800ft. 28/6	2,400ft. 47/6

P. & P. per reel 1/- 6d. on each additional reel.

**SPECIAL BARGAIN.** 3in. Message Tape, 150ft., 3/9. P. & P. 6d. 3in. L.P. 225ft. 4/8. 3in. D.P. 30ft. 6/6.  
Plastic Tape Reels . . . . .3in., 1/3. 5in., 2/-, 5 1/2in., 2/-, 7in., 2/3  
Plastic Spool Containers . . . . .3in., 1/6. 5 1/2in., 2/-, 7in., 2/3

### JASON FM TUNER UNITS

Postmer-approved kits:  
FMT1 5 gns. 4 valves, 20/-  
FMT2, £7. 5 valves, 37/6.  
JTV MERCURY 10 gns.  
JTV2 £13.19.6 4 valves 32/6.  
**NEW JASON FM HANDBOOK,** 2/6. 48 hr. Alignment Service 7/6. P. & P. 2/6.

### Electrolytics All Types New Stock

TUBULAR	CAN TYPES
25/25V. 50/12V 1/9	8+8/450V 4/8
50/50V, 100/25V 2/6	8+16/450V 5/-
8/450V	2/3 32+32/275V 4/8
16/450V	3/8 50+50/350V 6/8
16+16/45V	5/6 60+250V 12/8
32+32/450V	6/8 100+200V 12/6

**RESISTORS—**Modern ratings full range 10 ohms to 10 megohms. 20% 1 1/2 w. 8d. ca. ditto 1w 8d. ca., 2 w. 9d. ca. 10% 1 1/2 w. 4d. ca. 5% Hi-stab. 1 1/2 w. 8d. ca. (below 100 ohms and over 1 meg. 9d. ca.). 1% Hi-stab. 1 w. 1/6d. ca. (below 100 ohms 2/- ca.). **WIREWOUND,** 25 ohms to 10K. 5 w. 1/3. 10 w. 1/6. 15 w. 2/-

**TYGAN FRET** (contemp. pat.)  
12 x 12in. 2/-, 12 x 18in. 3/-  
12 x 24in. 4/-, 18 x 24in. 6/- etc.

**EXPANDED ANODISED METAL.** Attractive gilt finish 1/2 x 1in. diamond mesh. 4/6 sq.ft. Multiples of 6in. cut. Max. size 4 ft. x 3 ft., 47/6.

**ENAMELLED COPPER WIRE—**1lb. reels. 14g-20g, 2/6; 22g-28g, 3/-; 30g-40g, 3/9; 36g-38g, 4/3; 38g-40g, 4/6, etc. etc.

**Volume Controls—**SK-2 Meg-ohms, 3in. Spindles Morganite Midget Type 1 1/2in. diam. Guar. 1 Year. LOG or LIN ratios less Sw. 3/-, DF Sw. 4/6. Twin Stereo less Sw. 6/6. DF Sw. 8/-.

### RECORD PLAYER CABINETS

Cabinet Price **£3.3.0** Carr. & Ins. 5/-  
Attractive, contemporary two tone. Size 18 1/2 x 13 1/2 x ht. 8 1/2in., fitted all accessories.

**2-VALVE 2-WATT AMPLIFIER.** Twin stage ECL82 with vol. and neg. feedback Tone control. A.C. 200/250 V. with Knobs, etc., ready wired to fit above cabinet inc. 6in. speaker, etc. £3.19.6 Carr. 2/6.  
Complete Kit, including either B.S.R. UA14 Unit or Garard "Autosim" as ill. New reduced price £12.10.0. Carr. 7/6.



Only a few items are listed from our comprehensive stock. Write now for full bargain lists, 3d.

Terms: C.W.O. or C.O.D., post and packing 1/6. 9d., 1/6, 1/3, 3/6. 2/3, 5/6. 2/9, 10/6. 3/9, etc.



## RADIO COMPONENT SPECIALISTS

Established 1946

70 BRIGSTOCK RD., THORNTON HEATH, SURREY  
Tel. THO 2188; Hours: 9 a.m.—6 p.m. 1 p.m. Wednesday.


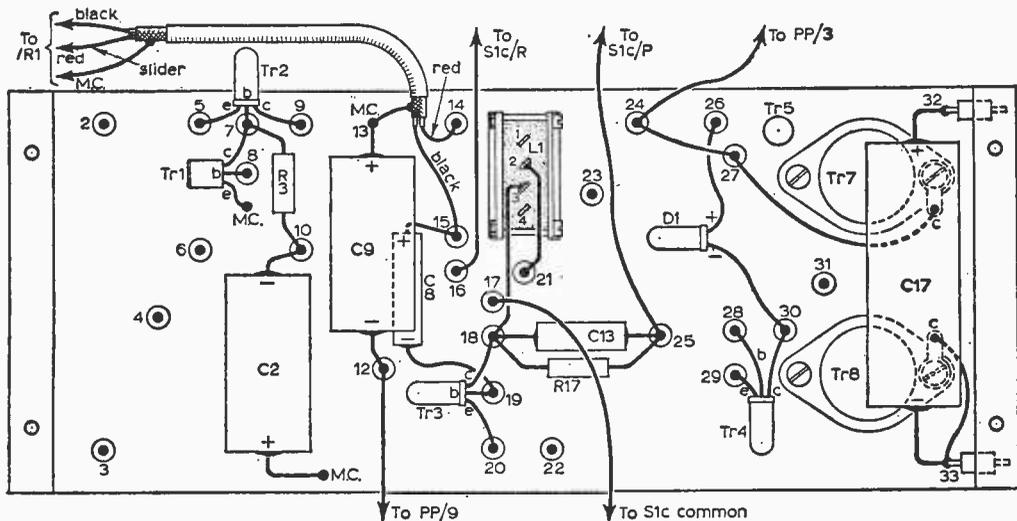


Fig. 8a (above): The top of the record/playback chassis and b (below)—the below-chassis view.

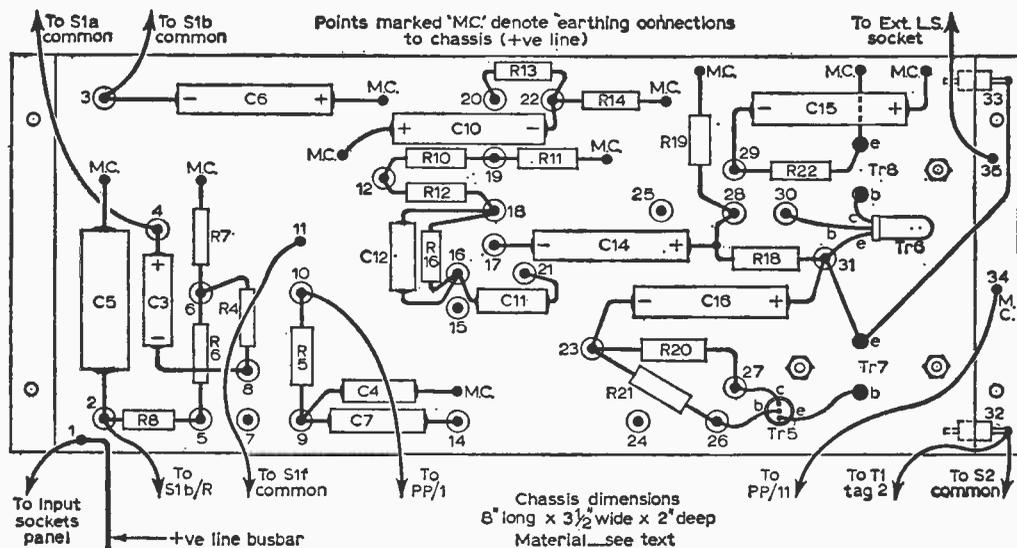

Chassis dimensions  
8" long x 3 1/2" wide x 2" deep  
Material—see text

holes in order to avoid puncturing the mica washers when bolting down the transistors.

One point about the oscillator is that when a radio is used near, or inside, the recorder a beat between the station and an oscillator harmonic may cause a bad whistle. This can be cured by moving the oscillator frequency in order to make the beat inaudible. In Fig. 7 is shown the oscillator 3rd and 4th harmonics at 180 and 240kc/s if the fundamental is 60kc/s. This of course will cause no interference with the Light Programme on 200kc/s because the beat frequencies are 20kc/s and 40kc/s. But had the oscillator fundamental been 66kc/s, the 3rd harmonic would have been 198kc/s and the result would be objectional inter-


ference at 2kc/s on top of the station.

Changing the oscillator frequency is best performed by adding a small capacitor across C24. Use a small value as is necessary, in order to avoid changing the oscillator frequency too drastically

**The Record/Playback Amplifier**

The layout of the record/playback amplifier is sketched in Fig. 8 and the chassis can be made from tinplate for ease of making earth connections. Push-through tags were used in the prototype, but these are rather expensive and stand-off insulators or small tagstrips are equally suitable for anchoring the components.

TO BE CONTINUED

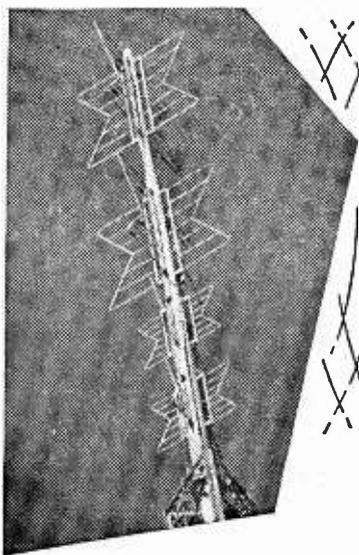

# On Your Wavelength

By THERMION

COMPARED with the glamour that has been bestowed upon the transistor the modern dry battery has received scant attention. Yet the unique features of the transistor could not have been fully exploited in the production of small portable apparatus without the availability of compact, highly reliable and efficient sources of h.t. current.

The advent of the layer type of battery represented the first major change in the methods of dry battery construction. This type battery is built up from a number of flat, rectangular units stacked together; the electrodes are flat plates and these provide a more efficient arrangement than the conventional Leclanche-type dry cell employing a cylindrical case and carbon rod.

## Looking Back

It is interesting to reflect how the humble dry battery has regained or possibly surpassed its former pre-eminence of the early days of radio. Some of my older readers will surely recall the rows of 3V pocket torch batteries arranged alongside that masterpiece in a mahogany case and black ebonite panel. Then eventually, in response to the growing demand, the manufacturers produced the multicell package to supply our h.t. needs, and so the jungle of inter-connecting clips and leads disappeared. Next followed what may, I suppose, be described as the heyday of the old-style dry batteries (yes, accumulators as well!). Soon the widespread availability of a.c. mains supplies encouraged us to try the mains-operated battery "eliminator" for a while, until finally the all-mains valves came on the scene. From then until round about 1945 the radio battery had but a modest role to perform, mainly in battery portables, and these sets were comparatively rare—unlike the ubiquitous transistor radio of today!

The layer-type battery was originally developed and put into production to meet the requirements of

the Services. In the post-war era this battery (like many other new developments) became available for general commercial use.

In its modern form, the dry battery has rebounded back into general use and indeed in so many of our activities and pastimes we have become dependent upon this miniature store of energy to power electronic equipment of some kind or other.

## Is Recharging Practical?

I have often been asked whether it is possible to recharge a dry cell or battery. In theory primary cells (such as these) are not rechargeable.

However, it is no secret that in practice a certain amount of rejuvenation is possible in the case of the conventional round-cell battery, provided the cell has not been more than about half exhausted. Care is necessary since charging at an excessive rate will cause damage. It must be emphasised that this recharging treatment should not be attempted with layer-type batteries. Due to the compact nature of the cell units, gassing can easily occur if current is passed through them and the battery will be permanently ruined.

Bearing in mind the reasonable prices of present-day batteries and the low current taken by transistors, I cannot believe that it is really worth while to build mains-operated rejuvenators.

## Twiddlers

Variable controls are irresistible! If you don't believe me just place a radio receiver, test instrument or any odd chassis (with knobs on) in front of someone who happens to be around. In no time he will be twiddling—and, more likely than not, doing this quite unconsciously. This habit is often harmless enough where operating controls are concerned, but there is the danger that a certain important preset control will next receive attention.

Some individuals are indeed a positive menace if let loose among exposed equipment. Be especially on your guard for the character armed with a newly acquired screwdriver or trimming tool which needs must be tested.

Apart from trouble and inconvenience caused by disturbed settings, the iron-dust cores of r.f. and i.f. coils are particularly susceptible to actual material damage should an oversize trimming tool be pushed into the slot, since this action may cause the core to fracture and become jammed in the former. It is usual for makers of miniature permeability tuned components to supply a suitable tool with each order. Keep this tool in some safe place, otherwise the occasion may arise when you will be tempted to carry out alignment with the wrong tool.

# POST FREE MAIL ORDER SERVICE

**SP-20 RADIO EARPHONES.** Hi-impedance-2,000 ohm general use headset. Black and Ivory plastic cased electro-magnetic units with adjustable headband for comfortable fit. Individual listening for all types of applications. Individually packed, with flexible cord attached, 14/6.



**ELRS HEADPHONES.** Moving coil, low resistance. Velvet padded ear cushions for maximum comfort. Extremely high sensitivity, ideal for communication receivers, tape recorders, etc. PRICE 12/6.



All goods sent by return

## PORTABLE MAINS SOLDERING IRON SP.1

30 watts. Features removable handle that covers tip and barrel. Complete for 18/9.



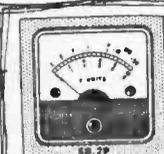
## SIGNAL INJECTION PROBE IT.1.



Push button operation. Ideal for making rapid checks on radios, TV, Amps, tuners, etc. Price 42/6.

Full range of Eagle Products always in stock




## "KEW" PANEL METERS

"g" Meter, 35/-; DC Microammeters, 5 mA, 27/6; 300  $\mu$ ., 27/6; 0-50  $\mu$ A, 38/6; 0-500  $\mu$ A, 32/6; DC Milliammeter, 0-1mA, 27/6. Available in Clear Plastic or Black Bakelite. Will fit 1 1/2 in. dia. cut out. State choice when ordering. All models individually boxed and fully guaranteed.

**MULTI-METER MODEL TK 20A, 1,000 O.P.V. ON A.C. & D.C.**  
RANGES: D.C. voltage: 0-15-150-1,000 V. (1,000 O.P.V.). A.C. voltage: 0-15-150-1,000 V. (1,000 O.P.V.). D.C. current: 0-100 mA. Resistance: 0-100K. Size: 3 1/2 in. x 2 1/2 in. x 1 in. Complete with battery, test leads and instructions, fully guaranteed. Price 49/6.

All goods available as previously advertised

## No. 19. 2-8 Mc/s TRANSMITTER RECEIVER

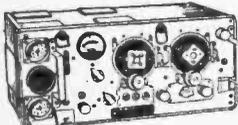


This most famous Army Transf Receiver covers 2-8 Mc/s. (150-37 metres in two bands). Has an intercom. amplifier. Designed for 12 and 24 volt operation but supplied with "P.W." Mains conversion details. Uses a 6 valve superhet receiver, I.F. being transmitter designed for voice and C.W. operations. Incorporates test and tuning meter for voltages, serial loading and current tests. P.A. tuning, gain control, MCW, CW, R/T switch. Het-tone setting. On-on Quench aerial, AVC LT-HT —Drives tests. Supplied complete with instructions book. Only 75/-

12ft. WHIP AERIAL (U.S.A.), 10/-.
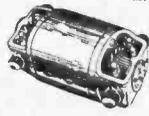
## LEAD ACID ACCUMULATORS (unspillable),

8 volts 16 A.H. Brand new. Size 4 1/2 in. x 7 1/2 in. x 2 1/2 in. Six for 20/- (min), 12/6 each for callers).



## HOOVER ROTARY TRANSFORMERS

12v. input, 500 v. output at 65 mA. or 6 v. input, 250 output at 75 mA. Only 12/6 Each.

VISIT OUR HI-FI SHOWROOM AT 87, TOTTENHAM CT. RD., W.I

## REIDA EXCLUSIVE!!

100,000 O.P.V. MULTI-TESTER MODEL EP.100K. A handy size high sensitivity multi-tester with a shock-proof meter of 9.5  $\mu$ A. Incorporates three germanium diodes and simplified meter scale for easy reading.

RANGES:  
D.C. Volts: 0.5V, 2.5V, 10V, 50V, 250V (100,000 ohm/V), 500V, 1,000V (35,000 ohm/V). A.C. Volts: 2.5V, 10V, 50V, 250V, 1,000V (12,500 ohm/V).  
D.C. Amps: 10  $\mu$ A, 250  $\mu$ A, 2.5mA, 25mA, 250mA.  
Ohms: 0-20K ohm, 0-200K ohm, 0-2M ohm, 0-20M ohm. Centre—100 ohm, 1.6K ohm, 16K ohm, 160K ohm. L.L.: 18  $\mu$ A, 180  $\mu$ A, 1.8mA, 18mA.  
L.V.: 2V.  
Decibels: minus 20db—plus 62db. Size: 5 1/2 in. x 3 1/2 in. x 2 1/2 in.

ORIGINALLY £14.14.0.

OUR PRICE £6.19.6 COMPLETE



## A MINIATURE TAPE RECORDER IN KIT FORM ONLY £4.19.6



Exclusively offered complete with all accessories. No extras to buy. Consisting of three transistor amplifier, record-play, volume control, miniature speaker, forward-stop-rewind switch, reel of tape and spare reel, motor, attractive coloured case, Mic. and earphone sockets, pick-up coil, mike, earphone and carrying handle supplied. Standard battery operated. Simple to put together in less than one hour. Brand new and guaranteed.

## PORTABLE RADIO PHONE

Consisting of trans-receiver covering 7.4-9 Mc/s. Range up to 6 miles, depending upon obstructions and elevation. On test the receiver astounded us for we heard 65 short wave stations—one as far away as Russia. Complete with 5 valves, headphones, microphone, junction box and fit, telescopic aerial. Operates from standard 120 v. and 3 v. dry batteries.

ONLY 85/- EACH  
TWO FOR £8  
(Batteries 20/- per set extra.)



**Reida Radio Ltd.**

MAIL ORDERS TO: DEPT. P 32A, COPTIC STREET, LONDON, W.C.1 Tel: MUScum 9606

# THE LINEAR L1/10

A 10-WATT HIGH FIDELITY ULTRA LINEAR AMPLIFIER WITH INTEGRAL PRE-AMP

Full advantage has been taken of latest component miniaturisation developments to produce a 10-watt Hi-Fi push-pull amplifier incorporating tone control pre-amplifier stages within the measurements of 9 x 7 x 5ins. In addition two high impedance input sockets are provided for microphone and gram., etc. With selector switch and vol. control, five B.V.A. valves are employed ECC83, ECC83, EL84, EL84, EZ81, H.T. and L.T. power supply point is included for a radio tuner.

#### FREQUENCY RESPONSE

±1 d.b., 30-20,000 c.p.s.

#### MAXIMUM POWER OUTPUT

In excess of 14 watts.

#### SENSITIVITY

L.P. 220 m.v. for 10 watts. 78 r.p.m. 220

m.v. for 10 watts. Radio/Microphone 40

m.v. for 10 watts.

#### TREBLE LIFT CONTROL

+ 10 d.b. to -22 d.b. at 12,000 c.p.s.

#### BASS CONTROL

+ 14 d.b. to -10 d.b. at 50 c.p.s.

#### HUM LEVEL

Referred to maximum output and including integral pre-amp.—70 d.b.

#### NEGATIVE FEEDBACK

21 d.b. in main loop.



**HARMONIC DISTORTION** Less than 0.1% measured at 8 watts at 1000 c.p.s. Weight 10 lbs. Power consumption 90 watts. For 200-230-250 v. 50 c.p.s. A.C. mains. Outputs for 3- and 15-ohm speakers. Chassis finish stoved Gold hammer.

**HIGHEST QUALITY** Retail Price

**MAXIMUM RELIABILITY** AT A PRICE YOU CAN AFFORD **13**

**MAXIMUM RELIABILITY** AT A PRICE YOU CAN AFFORD **6NS.**

Send S.A.E. for descriptive literature

TRADE ENQUIRIES to

Also Available—THE L.45.A compact High Quality 4-5 watt amplifier. Size approx. 7-5-5 1/2 in. high. Sensitivity is 28 millivolts so that the input socket can be used for either microphone or gram., tape, radio tuner etc. B.V.A. valves used are ECC83 EL84, EZ80. Controls are: Vol. Treble and Bass with mains switch. The Tone controls provide full compensation for long playing records. Output matching for 3 ohm loudspeaker. Retail price £5.19.6.

**THE L745 TAPE DECK AMPLIFIER.** A complete unit (power pack and oscillator incorporated) ready for connection to A.C. mains. 3 ohm loudspeaker and practically any make of deck. Negative feedback equalisation adjustment by multi-position switch for 1 1/2, 3 1/2 and 7 1/2 in. per second. Retail price 12 gns.

**DIATONIC 10-14 WATT.** High Fidelity amplifier with integral pre-amplifier. Retail 12 gns.

**CONCHORD 30 WATT.** Hi-Fi amplifier with two separately controlled inputs. Retail 16 gns.

**L50 50 WATT AMPLIFIER.** Size approximately 14 x 10 x 8 in. Sensitivity 25 mV. Output for 3 and 15 Ω speakers. Retail price 22 gns.

**L5/5 STEREO AMPLIFIER** 5 x 5 watt 12 gns.


**LINEAR PRODUCTS LTD.**

**ELECTRON WORKS, ARMLEY LEEDS**
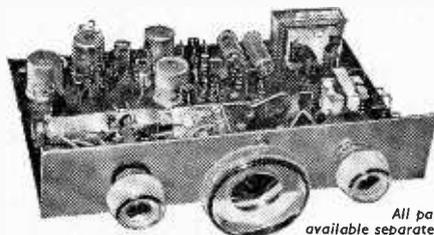
## "NORCOL NOMAD"

SEVEN TRANSISTOR TWO WAVEBAND SUPERHET RADIO UNIT  
BRAND NEW DESIGN FOR CAR RADIO AND GENERAL PURPOSE GIVING  
ONE WATT OUTPUT WHEN CONNECTED TO ANY STANDARD 3 ohm SPEAKER

This versatile unit has been designed to fit into a variety of cases and all components, down to control knobs and battery clips, are supplied together with clear illustrated plans. It gives a superb performance with dozens of stations including Luxembourg when connected to a 9 volt battery and speaker.



Size: 7 x 5 x 1 1/2 in. Building Plans 2/6 (Free with kit).

All parts available separately.

- FEATURES**
- NEW PRINTED CIRCUIT OF OUR OWN DESIGN
  - LARGE OUTPUT TRANSFORMER
  - SEVEN FIRST GRADE TRANSISTORS
  - INTERNAL HIGH "Q" FERRITE AERIAL
  - CAR AERIAL COUPLING COIL

We are offering the above for **THE AMAZING PRICE OF £6.19.6** P.P. 2/- or at NO EXTRA COST in 3 Stages (A, B and C) of 46/6 each plus P.P. 1/6.

#### ALIGNMENT SERVICE:

This unit is covered by our Test and Alignment Service which also handles the PW-6 Pocket Superhet and Mercury-6 Mk. II, for which we stock all components. The charge is 12/6 plus P.P. for Test and Alignment and where fault finding and broken component replacement is required a small service charge is added. (Cases and Speakers should not be included.)

**P.W. SPINETTE** R/Player.  
**P.W. CELESTE** Radio.  
**P.W. MERCURY** Radio.  
**P.W.-6** Pocket Superhet.  
S.A.E. FOR PRICE LISTS.

**NORCOL LTD.** 147 LONDON ROAD, YORKTOWN,  
ELECTRONIC COMPONENTS CAMBERLEY, SURREY Phone: CAMBERLEY 3743

by G.M. and E.C.D.

# semiconductors

## TALKING POINTS ON CIRCUIT PRACTICE

### No. 7—Transistor Characteristic Curves

Continued from page 232 of the July issue

IT has been suggested that as the characteristic curves published for transistors differ considerably from those published for valves, now that we have dealt with some of the fundamental aspects of transistors themselves, a few words on these curves and how to use them might be helpful.

There is quite a considerable number of curves published for transistors. The amateur is likely to be interested in only one or two of them. Basically the "Output-Characteristic" is likely to concern him most because by means of this curve he can judge what he can put into his transistor in the way of input, what he can take out of it without overloading it, what values of base bias he should use and what values of collector load.

The difficulty is that some readers may already understand the use of these characteristic curves and others may not. In keeping with the policy followed throughout these articles, therefore, we had better start with first things and explain just what these curves mean and how they are compiled.

### "OUTPUT CHARACTERISTIC"

The "Output Characteristic" curve as published for transistors is obtained by fixing the base at a definite value of bias and then plotting a curve for output current with varying values of output volts, i.e. collector volts. This on the face of it may seem to be a queer method when what we really want to know is output values for various values of input. But let us examine it.

Let us fix the base bias at, say, to choose an arbitrary figure merely for the purpose of explanation,  $40\mu\text{A}$ , sticking to bias in terms of current rather than volts as before. Let us then increase the voltage on the collector by gradual stages from, say, no volts to a maximum of 12V negative, and let us read the changing values of output current (by putting a meter in the collector or emitter lead) for each change of collector volts. We shall obtain a curve like the one marked " $40\mu\text{A}$ " on Fig. 1.

Now let us repeat the process at a different value of base-bias, say,  $20\mu\text{A}$ , and draw the curve corresponding to that value of bias. Repeating the procedure until we have a whole "family" of

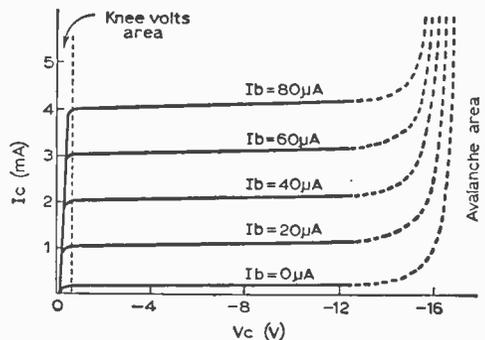


Fig. 1: Family of output-characteristic curves.

curves drawn on the same graph—each individual curve relating to one definite value of bias on the base (assuming common-emitter configuration as before).

Now let us look at these imaginary curves of Fig. 1. Each one of these curves, taken at different values of bias on the base, exhibits similar characteristics. The first thing we notice is that with  $V_c=0$  volts collector current is substantially zero. As we increase  $V_c$  there is a sharp rise in current over the first tenth or so of a volt until, at a defined value of  $V_c$ —something less than 1V—the current reaches its maximum value, after which no matter how much we increase the voltage on the collector it rises no more, right up to the maximum value shown, 12V negative.

This restates in graphical form what we have said more than once in this series of articles, namely that collector current, with transistors, is independent of collector voltage; unlike valve technique where the anode current is determined largely by the anode voltage and varies as the anode voltage varies quite apart from variations due to variation of grid bias. This is one of the large differences between transistors and valves. Output current in transistors does *not* depend upon output voltage. They are controlled, as regards current, solely by the bias on the base.

Having made that statement we must now say that it is not entirely true. Obviously over the first few tenths of a volt  $V_c$  the current depends

very much on collector voltage; it is only after that that the curve levels out and it ceases to be influenced by changing collector volts. It would also cease to be true were we to go on increasing the collector voltage beyond the value of 12V shown . . . we would reach a value at which the current would start to rise again very sharply and we would get the curves shown dotted in Fig. 1 and the transistor would be destroyed.

But what is true is that over the range of normal operation, that is from a few tenths of a volt  $V_c$  (known as the knee voltage) up to the critical voltage at which the "avalanche effect" commences, collector current is not influenced by collector voltage. It is no part of our purpose to consider avalanche effects here since these lie beyond the voltages at which the normal user is likely to operate a transistor.

The knee-voltage, however, we must consider, for this represents the minimum voltage which we must use on the collector to achieve linear transfer (input/output). This differs from transistor to transistor and, as a glance at the figure shows, it increases slightly as the value of base bias is increased, but is still only a few tenths of a volt.

Another point which is shown in these curves is the fact that with even no base bias at all, i.e., with base open circuit, a definite collector current . . . very small but nevertheless there . . . still flows. This is the leakage current and may average round about  $100\mu A$ .

These curves, therefore, give a complete picture of what happens to collector current at various values of base-bias, at any collector potential from no volts to  $-12V$ .

### PRACTICAL APPLICATION

Having understood this, then, now for the practical use of these curves. Let us use a battery voltage of  $4V$  for our collector supply.  $V_c$  will then be  $-4V$ . Let us place a standing base-bias on the transistor of  $40\mu A$ . Looking at the  $40\mu A$  curve in Fig. 1 we see that at this collector voltage the collector current will be  $2mA$ .

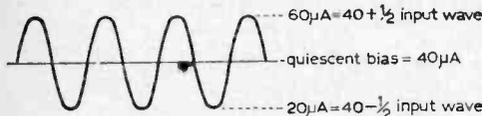


Fig. 2: A sine wave input signal.

Suppose now a sinewave of sufficient amplitude be fed on to the base to move the base-bias up to  $60\mu A$  and down to  $20\mu A$  as the signal changes (Fig. 2). We will not worry at the moment about what the r.m.s. voltage of the sinewave would have to be, we will simply assume that it is sufficient to increase the current passed through the base/emitter path of the transistor from  $40\mu A$  to  $60\mu A$  on the negative half of the wave, and sufficient to decrease it to  $20\mu A$  on the positive half of the wave.

It will be obvious then that the characteristic of the transistor output will travel upwards from the  $40\mu A$  curve to the  $60\mu A$  curve, and corre-

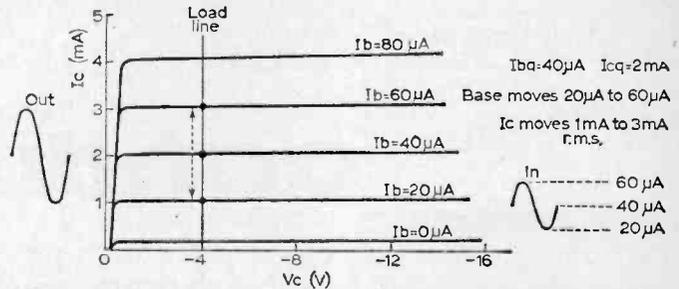


Fig. 3: This shows how a magnified version of the input current waveform appears in the collector circuit.

spondingly down to the  $20\mu A$  curve. It will move above and below the standing ( $40\mu A$ ) bias—from one curve to the other.

The collector voltage remains that of the supply,  $4V$ , therefore if we draw a vertical "loadline" at the  $4V$  point on the horizontal axis, passing through the three curves (Fig. 3), the output will swing, as shown by the arrow; the variation in output current according to input signal will be between  $1mA$  and  $3mA$ , about a standing value (with no signal) of  $2mA$ .

If we increased the value of the incoming wave then the output would swing further up and down the loadline . . . say from  $0mA$  up to  $4mA$ .

Reducing the amplitude of the signal would have the reverse effect.  $I_c$  might swing only between  $1.5mA$  and  $2.5mA$ , but it would still swing up and down the loadline we have drawn; collector volts would not change, only collector current.

It is seen, then, that the transistor is a current amplifying device—changes in current passing via the base are reflected in (amplified) changes in current via the collector. The amplification factor or "gain" of the transistor is a pure ratio: of input current/output current.

If  $100\mu A$  input produces  $1,000\mu A$  output, then the gain of the transistor is 10—remembering the point brought out in earlier articles that the gain of a transistor is not constant . . . suppose it be 10 at a certain value of base current (small signal conditions), it may have a different value at large values of base current (large signal conditions). We have already dealt with this point in past articles and cannot go into it again here.

So far, so good. If we have understood how these curves are drawn, and how to use them, we

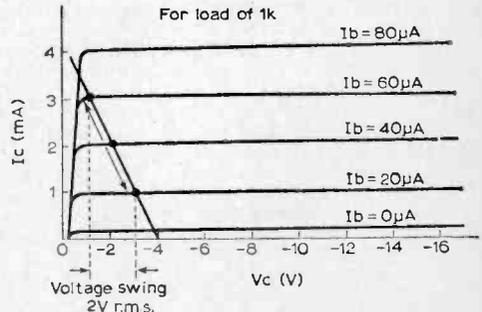


Fig. 4: Loadline for collector load of  $1k\Omega$ .

# CLYNE RADIO LTD.



18 TOTENHAM COURT ROAD, W.1  
162 HOLLOWAY ROAD, LONDON N.7  
9 CAMBERWELL CHURCH STREET, S.E.5  
12 SUFFOLK HOUSE, GEORGE ST., CROYDON MUN 3250  
10 WITTHY GROVE, MANCHESTER, 4 Blackfriars 5379

All post orders, etc. to 162 HOLLOWAY ROAD, LONDON, N.7

## THE COMPONENT SPECIALISTS

MUSEum 5929/0095  
NORTH 6295/677  
RODnes 2875  
CROYDON MUN 3250  
Blackfriars 5379

## TAPE RECORDER CONSTRUCTORS

**LATEST COLLARO STUDIO TAPE TRANSCRIBTOR.** Latest type incorporating Record, Interlock, Lever, Button, 3 motors 3 speeds, 11, 31, 74 I.P.S., takes 7in. spools. Push-button controls. **NEW! LOW PRICE!** OF £10.10.0 ONLY! plus 7/6 P. & P. Usual H.P. facilities.

**NEW TAPE RECORDER AMPLIFIER TYPE 831-V.** Sub-assembled—anyone can build! Printed Circuit, all components mounted and dip soldered. Already tested. Each



lead cut to length. All that is required to complete the tape recorder is for a few components to be mounted in the cabinet and the free ends of the leads soldered to terminals which are clearly marked, everything supplied, all you need is solder iron, pliers and screwdriver. Valve line-up: EP86, ECC83, 2x EL84, EZ81 and EM84 magic eye. Monitoring facilities, output socket for feeding to high quality amplifier, can be used as "straight" amplifier for record reproduction. **EQUALISING ON TWO SPEEDS. OUTSTANDING VALUE AT £11.11.0 plus 2/6 P. & P.** including all necessary instructions.

**ATTRACTIVE TWO-TONE PORTABLE CARRYING CASE.** Suitable for above amplifier and Collaro Studio deck. Fitted with 9in. x 5in. High Flux P.M. speaker for high quality reproduction. Inclusive price £5.5.0 plus 5/- P. & P. Full list of competitively priced mics (and stands on request) The above 3 items purchased at one time, SUPPLIED CARR. PAID.

**NOW AVAILABLE! FOUR TRACK STUDIO DECK AS ABOVE, FITTED WITH HIGH-FI FOUR-TRACK HEADS. PRICE £13.12.6 plus 7/6 P. & P.** Four track heads supplied separately, complete with mounting bracket for Studio Deck at 92/6 pair, plus 2/6 P. & P.

**TAPE RECORDER AMPLIFIER 831-V.** Exactly as 831-V but four track. Suitable for the above high-fi four-track heads. Price £12.12.0 plus 2/6 P. & P.

**PRE-AMPLIFIER KIT TYPE 8312-CP.** Complete high quality pre-amplifier kit for use with Collaro Studio Deck. Price £8.8.0 plus 2/6 P. & P.

**N.B.** Four-track deck and amplifier fit the above case without any modification whatsoever.

**TELEPHONE PICK-UP COIL.** Designed to feed into the microphone input of either a tape recorder or any high gain amplifier. Easily attached to telephone by rubber suction attachment. The coil is electrostatically shielded to minimise hum pick-up. When positioned on telephone, this model is more than adequate for a fully modulated tape recording. Brand new complete with 5 ft. shielded cable. **ONLY 14/-**. Post free.

## TAPE ! TAPE !

For the first time in this country Canada's Hi Fi Magnetic Recording Tape. Made by "Bel-Cleer" of Canada.



Following sizes available, others to follow. Brand New, NOT sub-standard. High grade Acetate base, attractively boxed, fitted leaders, fully guaranteed.

5in., 600 ft., 12/6; 5in., 900 ft., 15/-; 5 1/2in., 1,200 ft., 18/6; 7in., 1,200 ft., 18/6; 7in., 1,800 ft., 25/-; 7 1/2in., 600 ft., 9/- per spool, 3 or more post free. (Bona fide trade inquiries invited.)

**PLASTIC SPOOL CONTAINERS** for spool sizes 5in. 1/6; 5 1/2in. 2/1; 7in. 2/3.

**PLASTIC TAPE SPOOLS.** Best quality. 3in., 12, 4in., 2/-; 5in., 2/-; 5 1/2in., 2/3; 7in., 2/6. P. & P. 6d. per item. Others over 1/- post free.

## NEW BRANCH CROYDON

NOW OPEN AT  
12 SUFFOLK HOUSE, GEORGE ST.  
Municipal 3250  
(One minute from East Croydon Station)  
OPEN ALL DAY SATURDAY

### MODEL TK.20A

Size 3 1/2" x 2 1/2" x 1 1/2". Meter size 2 1/2" x 1 1/2". Sensitivity 1000 o.p.v. on both A.C. and D.C. volts, 0/15, 0/150, 0/1000 volts. D.C. Current, 0/150 mA. Resistance, 0/100K. Complete with test prods, battery and full instructions. **OUTSTANDING VALUE AT**


**42/-** Plus 1/6 P. & P.



### MODEL TK.50

Size 5" x 3 1/2" x 1 1/2" 1000 ohms per volt AC/DC. DC Current 1-250 mA DC and AC volts, 10, 250-500 and 1000 v. Resistance 0-10K, 0-100K. Complete with test prods, battery and full instructions. Outstanding buy at

**57/6** Plus 2/6 P. & P.

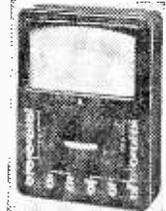

## The SINCLAIR SLIMLINE

A new miniature 2 TRANSISTOR printed circuit pocket radio. Completely portable and the smallest of them all—only 2 1/2" x 1 1/2" x 1 1/2". Uses latest Micro Alloy Transistors and with built in ferrite aerial will receive all stations on Medium Wave—B.B.C., 208, etc. Easy to assemble—no alignment problems. All required components, including earpiece **ONLY 49/6** P. & P. 1/6

All parts sold separately.

## AN ALL BRITISH. PRECISION TEST METER (To build yourself)




Designed for Test bench and produced for us by one of Britain's leading technical training organisations this instrument covers the following nineteen basic ranges: D.C. Voltage 0-2.5, 0-10, 0-50, 0-100, 0-500, 0-1000. (All ranges 5000 ohms per volt). A.C. Voltage 0-10, 0-50, 0-100, 0-500, 0-1000. (All ranges 5000 ohms per volt). D.C. current 0-200 microamps, 0-10 ma., 0-100 ma., 0-250 ma., 0-500 ma., A.C. current, 0-200 microamps, Resistance, 0-200,000 ohms. (Easily extendible to 2 megohms.) Accuracy, 3% of F.S.D. on D.C. ranges, 4% on A.C. ranges, any frequency between 15-20,000 C.P.S. (Sine wave) 5% on resistance range. Positive Range selection by means of plug and socket. Easily constructed, full instructions being given with each assembly. All necessary components offered at the **ABSURDLY LOW PRICE OF 59/6**, P. & P. 2/6. Strictly limited quantity!

0-500 ma., A.C. current, 0-200 microamps, Resistance, 0-200,000 ohms. (Easily extendible to 2 megohms.) Accuracy, 3% of F.S.D. on D.C. ranges, 4% on A.C. ranges, any frequency between 15-20,000 C.P.S. (Sine wave) 5% on resistance range. Positive Range selection by means of plug and socket. Easily constructed, full instructions being given with each assembly. All necessary components offered at the **ABSURDLY LOW PRICE OF 59/6**, P. & P. 2/6. Strictly limited quantity!

## The "AIR KING"

Our new highly successful Six transistor luxury portable with the "SLIM LINE" look. To build yourself, with printed circuit chassis for reliability and simplicity in construction. May be used as Car Radio, with full MEDIUM wave and LONG wave coverage.

Look at these features:

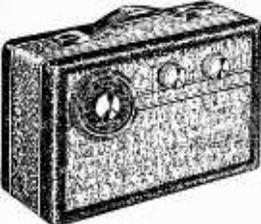

- \* 500 milliwatt output to high flux 7 x 3in. high fidelity loudspeaker.
- \* Six selected Mullard Transistors in latest super sensitive circuit, plus germanium diode. \* Compact size—only 9 1/2 x 3 1/2 x 6 1/2in. (high).
- \* Attractive three-tone cabinet. Black, Dark Grey, and Silver Grey, with gilt control knobs and all gilt fittings.
- \* Coax socket for car aerial. \* Brand new guaranteed components. \* Push pull output. \* Automatic volume control. \* Long life battery. \* Super sensitive internal ferrite rod aerial. \* Nothing more to buy. Cabinet included.


Special inclusive price for the 19.6. All required components. **£7.19.6**

Plus P. & P. 4/- Alignment service available. Full assembly details and individually priced parts list, all of which are available separately, price 1/6 post free.
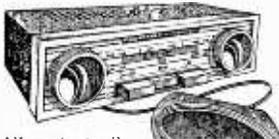
## The "HIGHWAYMAN"

At last a quality Car Radio to build yourself, at an economical price. Look at these features:—

- \* Attractive styling. \* Push-pull output. \* 3 latest Mullard transistors plus valves type EBF83 and ECH83.
- \* No Buzz. High Output and sensitivity. \* Printed circuit (newest type). 7 x 4" High flux p.m. speaker.
- \* Medium and Long Waves. \* Push Buttons for fingertip control. \* Extremely low Battery consumption (less than 1 amp.) \* Easy to fit any make car (Positive earth only). \* 12 volt operation. \* Compact size measures only 7" x 2" deep. \* Easy assembly. Supplied with dial and drive already mounted.



All parts available separately but if purchased at one time, the whole will be supplied at a special inclusive price of only **£10.19.6** Plus 4/- P. & P. Parts list and comprehensive instruction booklet 2/6, post free. (Deduct from cost if complete parcel purchased later.)

## RETURN-OF-POST SERVICE

ON CASH OR C.O.D. ORDERS

### P.W. CELESTE

All parts stocked, send for list.

### LATEST TEST METERS

	Cash Price	Deposit	Mthly/Pmts.	Hire Purchase
AVO Model 8 Mark II	£24.00	£4.16	12 of £1.15	2
AVO Model 7 Mark II	£21.00	£4.40	12 of £1.10	10
AVO Multimeter Mark 4	£9.10	£1.80	12 of	14/4
T.M.K. TP19	£3.19.6	£1.3.6	3 of	£1.2.0
T.M.K. TP55	£5.19.6	£1.15.0	3 of	£1.11.4
T.M.K. Model 500	£5.19.6	£1.15.0	12 of	13/8
TAYLOR MODEL 127A	£10.10.0	£2.2.0	12 of	15/8

Full details of any of the above supplied free on request.  
The AVO models 7 and 8 are both latest models from current production—not to be confused with Government Surplus.

### GRAMOPHONE EQUIPMENT

ALL LATEST MODELS  
ALL POST FREE

	Cash Price	Deposit	Mthly/Pmts.	Hire Purchase
<b>RECORD CHANGERS</b>				
GARRARD AUTOSLIM (Mono PU)	£7.2.6	£1.8.6	12 of	11/2
GARRARD AUTOSLIM De-luxe AT6 (Mono PU)	£11.9.0	£2.6.0	12 of	16/11
GARRARD AUTOSLIM De-luxe AT6 (S/M PU)	£12.5.4	£2.9.4	12 of	18/-
B.S.R. UA14 (TC8 Mono PU)	£6.19.6	£1.7.6	12 of	11/-
B.S.R. UA14 Monarch (TC8 Stereo/LP/78)	£7.19.6	£1.11.6	12 of	12/4
B.S.R. UA16 (TC8 Mono PU)	£7.19.6	£1.11.6	12 of	12/4
B.S.R. UA16 (TC8 Stereo/LP/78)	£8.19.6	£1.15.6	12 of	13/8
<b>SINGLE RECORD PLAYERS</b>				
B.S.R. TU12 (TC8 Mono PU)	£3.17.8	£1.4.6	3 of	£1.1.0
B.S.R. GU7 (TC8 Mono PU)	£4.18.8	£1.8.8	3 of	£1.6.8
GARRARD SRP10 (Mono PU)	£5.9.11	£1.12.11	3 of	£1.9.0
<b>TRANSCRIPTION UNITS</b>				
GARRARD 4HF (GC8 PU)	£16.12.6	£3.6.6	12 of	£14.5
PHILIPS AG1016 (S/M PU)	£12.12.0	£2.10.0	12 of	18/8

Many of the above can be supplied for stereo working. See our Gramophone Equipment List for details.

### TAPE RECORDING EQUIPMENT

	Cash Price	Deposit	Mthly/Pmts.	Hire Purchase
<b>TAPE DECKS</b>				
ALL CARRIAGE FREE				
COLLAIO STUDIO, Latest model. Two track. Bradmatic Heads	£10.19.6	£2.3.6	12 of	16/4
Four Track. Marriott Heads	£17.17.0	£3.12.0	12 of	26/2
<b>MARTIN TAPE AMPLIFIER KITS</b>				
Tape Amplifiers				
For Collario 8311-V 2-Track	£11.11.0		8311-4-V 4-Track	£12.12.0
<b>Tape Pre-Amplifiers</b>				
For Collario 8312-CP 2-Track	£8.8.0		8312-4-CP 4-Track	£9.9.0
Drop through assembly for mounting 8312 Pre-Amp under Collario Deck. £11.1.6.				
Carrying Cases with speaker. For Collario Deck and 8311 Amplifier. £5.5.0.				

H.P. TERMS available on decks, amp. and cases. Ask for quote.

### JASON F.M. TUNER KITS

Kits supplied complete with every item needed including instruction manuals. Fully detailed list available. Separate items supplied, ask for price list. H.P. Terms available on any kit.

FMT1, £6.12.6; FMT2 (less power), £7.15.0.  
FMT2 (with power), £9.12.6; FMT3 (less power), £9.9.6.  
FM T3 (with power), £11.7.6; Mercury 2, £10.14.6.  
JTV2, £14.12.6.

### AMPLIFIER KITS

We have full stocks of all components for the Mullard 510. Mullard 2-3, Mullard 2 and 3 Valve Pre-amp, Mullard Stereo, Mullard Mixer, GEC 912 Plus. Fully detailed list on any of these sent upon request. Instruction Manuals: All Mullard Audio Circuits in "Circuits for Audio Amplifiers", 9/5. GEC 912. 4/6. All post free.

### ILLUSTRATED LISTS

Illustrated lists are available on LOUDSPEAKERS, TAPE DECKS, TEST GEAR, GRAMOPHONE EQUIPMENT, AMPLIFIERS. Any will be sent free upon request.

## WATTS RADIO (Mail Order) LTD

54 CHURCH STREET, WEYBRIDGE, SURREY  
Telephone Weybridge 47556

Please note: Postal business only from this address.  
Callers welcome by appointment.

### \* TERMS OF BUSINESS

Cash with order or C.O.D. We charge C.O.D. orders as follows: Up to £3, minimum of 4/2. Over £3 and under 5, 2/8. Over 5 and under 10, 2/8. Over 10, no charge. Postage extra on CASH orders under £3 except where stated. Postage extra on overseas orders irrespective of price.

**HIRE PURCHASE TERMS** available on many items. Send for quotation.

CLOSED FOR ANNUAL HOLIDAYS AUGUST 7th to 24th

## NOMBREX Instrumentation

### TRANSISTORISED WIDE-RANGE C.R. BRIDGE

6 Ranges

MODEL 62

1Ω to 100MΩ


1pF to 100MFds

Power Factor Check  
Leakage Test

Visual Null Indicator

Internal 9v. Battery

Compact and light

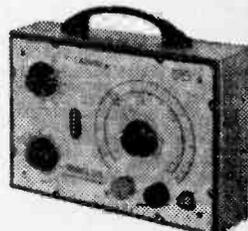

Battery 2/3  
Post & Pkg. 3/6

Price £7.0.0

Cash with Order. Regret no C.O.D.

**NOW IN QUANTITY PRODUCTION**  
Orders in strict rotation  
TRADE AND EXPORT INQUIRIES INVITED  
S.A.E. for full technical leaflet

## NOMBREX LTD. (Instruments Division 59)

Estuary House, Camperdown Terrace, Exmouth, Devon  
England. Tel. 3515

## SPECIAL OFFER!

OBTAINABLE ONLY FROM R. & T.V.  
THE

*Elegant Seven*

COMBINED  
PORTABLE  
AND  
CAR  
RADIO

THE RADIO WITH  
THE STAR FEATURES



★ 7-transistor superhet. Output 300 mW. ★ Two-tone grey wooden cabinet, fitted handle with silver coloured fittings. Size 11 1/2 x 8 1/2 x 3 1/2 in. ★ Horizontal tuning scale, size 1 1/2 x 2 1/2 in. In silver with black lettering. ★ All stations clearly marked. ★ Ferrite-rod internal aerial. ★ IF 470 Kc/s. ★ Operated from PP9 battery. ★ Full comprehensive instructions and point-to-point wiring diagram. ★ Printed circuit board, back-printed with all component values. ★ Fully tunable over medium and long wavelength. ★ Car aerial socket. ★ Full after sale service.

PARTS LIST AND CIRCUIT DIAGRAM 2/6. FREE with parts.  
**ONLY £5.9.6** PLUS 5/6  
POSTAGE & PACKING

Goods not despatched outside U.K.  
All enquiries S.A.E. Terms C.W.O.  
**RADIO & T.V. COMPONENTS LTD.**  
21c HIGH STREET, ACTON, LONDON, W.3.

must now realise that the output curves as published refer to the performance of the transistor *with no load in the collector circuit*—a condition impossible to obtain in practice.

Let us assume now, then, that we have a resistive load of 1k ohms in the collector (emitter) circuit. Any load in the emitter is also in the collector, of course, as well as in the base circuit. Keeping the same quiescent bias on the base, namely 40µA, the current as before will be 2mA (from the 40µA curve). But now the 2mA passes through the 1kΩ load, which drops 2V, so that the actual voltage on the collector under quiescent conditions is now 2V.

We must now plot a fresh loadline (Fig. 4). The transistor is now seated at  $I_c=2mA$   $V_c=2V$  in quiescent conditions. The incoming signal on the base, moving the base as before, swings the output current between 1mA and 3mA, over the standing value of 2mA, as before. But at the maximum  $I_c$  of 3mA the 1k ohm load drops 3V (Fig. 4). At the minimum value of  $I_c$  the load drops 1V. Joining on the graph the point 3mA-1V (4V-3V) and 1mA-3V (4V-1V) we get a new loadline as shown. The characteristic now travels as shown by the arrow in Fig. 4.

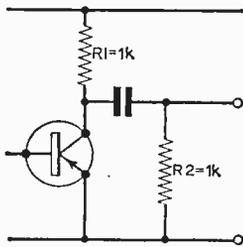


Fig. 5: R.C. interstage coupling.

It will be seen that the current changes in the output are the same as before, for the same changes in input (namely the gain of the transistor), but there are now voltage changes in the output also, developed across the load. And the slope of the loadline is different.

The current swing in the output, therefore, is independent of the load, but by introducing a load we have achieved voltage swing as well as current swing, the voltage swing depending upon the value of the load.

Now take another and very practical set-up. Let us suppose that we are going to connect our transistor to a following stage through a normal RC coupling such as Fig. 5. Let the value of the capacitor be sufficiently large to have negligible reactance so that we can ignore it as far as signal a.c. is concerned. Let the value of  $R_2$  be another 1k ohm (for simplicity).

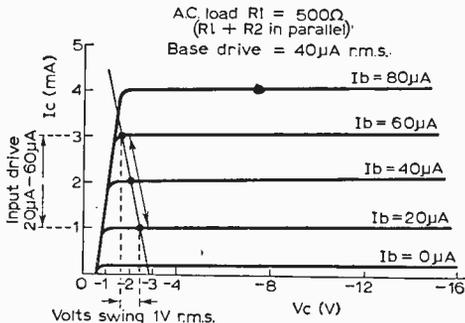


Fig. 6: The graph modified for an effective load of 500Ω.

Now let us draw a loadline for the new set of conditions (Fig. 6).

So far as the standing d.c. is concerned the capacitor isolates the collector of the first transistor. Taking the same standing base-bias, 40µA, therefore,  $I_c$  will be 2mA (d.c.) at any value of collector volts . . . but we have 1k ohms in the collector circuit, which drops 2V at 2mA; the transistor therefore is seated d.c.-wise at the same point as before, namely 2mA-2V (4V-2V). Now let the d.c. signal come on to the base, moving it as before so that the output current  $I_c$  moves between 1mA and 3mA. At a.c. the capacitor no longer isolates the collector from the following stage but can be considered as virtually a short-circuit. Therefore, as explained in previous articles, we have  $R_2$ , the resistive factor in the RC coupler, as far as a.c. is concerned, in parallel with  $R_1$ , reducing the total value of the load in the collector circuit from 1kΩ to 500Ω (to a.c.).

As  $I_c$  rises to 3mA on signal, 3mA drops 1.5V through 500 ohms, but the transistor is already seated (d.c.-wise) at 2V with 2mA flowing.  $I_c$  increases by 1mA (to 3mA) on signal and decreases by 1mA (to 1mA) on signal. These changes are at a.c. frequency, half being developed over the collector load  $R_1$  and half over the coupling resistor  $R_2$ . The characteristic, therefore, now travels as shown by the arrow (Fig. 6), the 1mA swing on either side of the standing value producing only 0.5V on each side of the standing value.

As before, current swing is unchanged but voltage swing, dependent upon the load, is now reduced, because by introducing the RC coupling we have effectively reduced the value of the load (to a.c.) by half.

It is obvious, therefore, that if we are going to use RC coupling to the next stage the loadline we drew previously, which did not take into account this RC coupling, is useless. We would in practice be getting far less gain (volt-wise) from our stage than we had calculated on getting.

How we overcome this difficulty by shifting the loadline will be dealt with in the next article.

**SERIES CONTINUED NEXT MONTH**

**THE PRACTICAL WAY . . .**

. . . to make sure of your regular copy of PRACTICAL WIRELESS is to place an order with your newsagent. Do it now! The order form below is included for your convenience. Simply complete it and hand it to your newsagent next time you call.

**ORDER FORM**

To \_\_\_\_\_  
(Name of newsagent).

Please send/reserve PRACTICAL WIRELESS (2/-) every month, commencing with the next issue.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

**DETACH AND HAND TO YOUR NEWSAGENT**

# CLUB

## AMATEUR RADIO MOBILE SOCIETY

Hon. Sec.: G3FPK, 79 Murchison Road, London, E.10.

The fourth International Mobile Rally organised by this Society was held successfully on June 16th at the United States Air Force base, Barford St. John, Oxfordshire. As in previous years, mobile amateurs gathered from all parts of the country and from abroad to join in this stupendous occasion.

The main attraction for visitors, many of whom made a weekend of it by camping out on the previous night, was the appearance of the United States Third Air Force band. Many other attractions and events made the rally really enjoyable for all who attended and especially so for those who took home the many prizes which were won.

## BRADFORD RADIO SOCIETY

Hon. Sec.: E. G. Barker, G3OTO, 63 Woodcot Avenue, Baildon, Shipley, Yorkshire.

"Adjustment of Linear Amplifiers" was the topic for A. W. Walsley's lecture which he gave on June 11th. On 25th June members paid a visit to the C.E.G.B. power station at Canal Road, Bradford.

## DERBY AND DISTRICT AMATEUR RADIO SOCIETY

Hon. Sec.: F. C. Ward, G2CVV, 5 Uplands Avenue, Littleover, Derby.

This Society operated two stations from Glebe Farm, Littleover, in participating in N.F.D. this year.

The "open evening" meeting of June 19th was followed a week later by the third d.f. practice run. The R.S.G.B. d.f. qualifying event held at Derby on June 30th was organised by members A. Hitchcock and F. Allsopp.

## EAST WORCESTERSHIRE GROUP

Hon. Sec.: L. Hickingbotham, G3HZG, 95 Oakenshaw Road, Redditch, Worcestershire.

This group meets on the second Thursday of each month at the Old Peoples Centre, Park Road, Redditch, and at the June meeting a number of members described their stations and operating activity.

## FLINTSHIRE RADIO SOCIETY

Hon. Sec.: Alan Antley, Fairholme, Fairfield Avenue, Rhyl, Flintshire.

As usual, unlicensed members were able to get in some more practice before the main meeting for June began. This was followed by another lecture from L. W. Barnes on "Simple Hints and Kinks", and arrangements for v.h.f. field day took up the remainder of the evening.

## LOTHIANS RADIO SOCIETY

Hon. Sec.: W. T. Sutherland, GM3JWS, 47 Great King Street, Edinburgh 3.

Although the most important meeting in June was the Annual General Meeting, a good deal of interest was raised by a Constructional Competition for members which was held earlier in the month on June 13th.

## MID-WARWICKSHIRE AMATEUR RADIO SOCIETY

Hon. Sec.: T. Inkester, 13 Dormer Place, Leamington Spa, Warwickshire.

As the Whitsun holiday coincided with the first meeting date of June, no meeting was held on the 3rd. However, on June 17th, members assembled at the Leamington Boys Club to hear a lecture on "Microphones."

At the July meeting held on the 1st, "Transistors" was the subject under discussion.

## NORTHERN HEIGHTS AMATEUR RADIO SOCIETY

Hon. Sec.: A. Robinson, G3MDW, Candy Cabin, Ogden, Halifax, Yorkshire.

The meeting for June 19th was the usual ragchew, with anything and everything being discussed informally. Earlier in the month, however, members manned a demonstration station at the Halifax Fete, under the call sign G3MDV/A. This is the first of four such demonstration stations which this Society has undertaken to provide this year.


On July 3rd, the Society visited the local C.E.G.B. power station at Elland which is near Halifax itself.

## READING AMATEUR RADIO CLUB

Hon. Sec.: R. G. Nash, G3EJA, "Peacehaven", 9 Holybrook Road, Reading, Berkshire.

On June 29th the Club met to hear a discussion by Mr. Shears on a range of gear which is available to amateurs today.

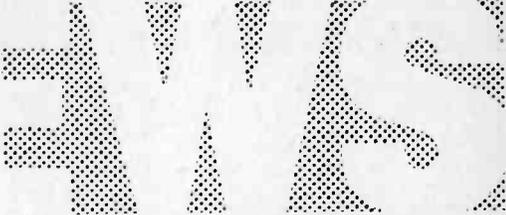If there are enough interested members, the Club is hoping that the Reading Technical College will arrange a course of lectures covering the R.A.E.



## SHEFFIELD AMATEUR RADIO CLUB

Hon. Sec.: D. A. Justice, G3PYL, 9 Leslie Road, Sheffield 6.

The Meeting for June, which fell on the 14th, was mainly devoted to a demonstration by G3LLV of "Radio Teletype."

## SLADE RADIO SOCIETY

Hon. Sec.: D. D. S. Williams, 117 The Boulevard, Wyld Green, Sutton Coldfield, Warwickshire.

Some of the Society's newly licensed members gave accounts of their experiences prior to and during the R.A.E., at the meeting for June 14th.

On June 28th, Mr. J. E. Smith continued his series of lectures on "Radio Fundamentals."

The one d.f. event for June was the Harcourt Trophy test, which was run on the 16th.

## SOUTH SHIELDS AND DISTRICT AMATEUR RADIO CLUB

Hon. Sec.: Derek Forster, G3KZZ, 41 Marlborough Street, South Shields, Co. Durham.

This Club is to hold its 5th Mobile Rally on Sunday, July 7th at Bents Park Recreation Ground, Coast Road, South Shields. The control station—G3D11—will be operating on 160m.

## SOUTH YORKSHIRE AMATEUR RADIO SOCIETY

Hon. Sec.: V. J. Ludlow, 50 Wellington Road, Lindholme, Hatfield, Doncaster, Yorkshire.

Formal meetings, which are now held fortnightly, alternate with constructional evenings when the club transmitter is in operation.

Members are building a 14Mc/s phone transmitter to supplement the 160m rig already operating under the Club call sign.

## SPEN VALLEY AMATEUR RADIO SOCIETY

Hon. Sec.: L. A. Metcalfe, 1a Moorlands Road, Birkenshaw, Bradford, Yorkshire.

On June 15th F. L. Allen gave a lecture entitled "Oscilloscope Patterns."

The meeting on June 27th was the last of the Society's meetings for the year 1962/63, before the Annual General Meeting to be held on July 11th.

## STOURBRIDGE AND DISTRICT AMATEUR RADIO SOCIETY

Hon. Sec.: R. A. G. MacIntosh, 50 Field Lane, Oldswinford, near Stourbridge, Worcestershire.

The Society was represented at an exhibition staged at the Town Hall, Stourbridge, during June, and in conjunction with this exhibition, a working station was set up by members in a local park.

On July 2nd, Mr. T. R. Smith (G3BMN) delivered a lecture with the title "Mobile."

## WESSEX AMATEUR RADIO GROUP

Hon. Sec.: G. K. Fowle, 138 Surrey Road, Branksome, Poole, Dorset.

This Group reports a steadily increasing membership and a number of these members faced the Southampton R.S.G.B. Group in an amateur radio quiz held on 10th June. This quiz, which was a return match, was followed by a talk on "Radio Controlled Boats" by G. Wood.

Mr. Simmonds (G8VB) was the judge of the constructional contest open to all members and held on 1st July.

## WEST KENT AMATEUR RADIO SOCIETY

R. Trevitt, 28 Delves Avenue, Tunbridge Wells, Kent.

W. H. Allen's lecture given on June 14th was on the subject of "2m Convertors." On June 28th, G4IB gave a talk on "Modulators."

## WIRRAL AMATEUR RADIO SOCIETY

Hon. Sec.: A. Seed, G3FOO, 31 Withert Avenue, Bebington, Wirral, Cheshire.

On 19th June the Society conducted an inquest into their participation of N.F.D.

On the agenda for July 3rd was a talk by L. Flint entitled "Metals."

## WOLVERHAMPTON AMATEUR RADIO SOCIETY

Hon. Sec.: J. Rickwood, 738 Stafford Road, Wolverhampton, Staffordshire.

On June 15th, this Society organised a mobile rally to run in conjunction with a local sports day and gala. Many prizes were awarded to mobile visitors and the numerous other attractions made the occasion enjoyable for all those who attended.

R.S.G.B. Contests for July. Second 144 Mc/s Portable Contest (July 6th to 9th) and D/F Qualifying Event (July 21st).

# CRYSTALS & COMPONENTS LTD

TEL: TEM.1189 2.4. EARLHAM STREET W.C.2.

Near Cambridge Circus. A few minutes' walk from Leicester Square or Tottenham Court Road Underground Stations  
 HOURS OF BUSINESS: 9 to 6. Saturdays 9 to 1. OPEN ALL DAY THURSDAY

### TYPE 38 TRANS/RECEIVERS

Brand new. Operating on 7.4 to 9 Mc/s. Trans/Receivers. Complete with headphones, throat microphone, junction box and aerial rods. Operate on 150 volts HT & 3 volts LT dry batteries. Complete less batteries and not tested. 42/6 per set plus 6/6 post. Or £4 per pair plus 10/- post and packing.



### VIBRATOR POWER SUPPLY UNIT

6 volts D.C. input. 230 volts 100 mA A.C. output and 6 V. L.T. out. Fully smoothed, with O24 rectifier valve. Brand new in steel case with pilot light, on/off switch and Silydok fuse on front panel. Measures 8 1/2 x 6 x 5 1/2 in. 39/6 plus 6/6 post and packing.

### SILICON RECTIFIERS

Westinghouse 1,000 P.I.V. 500 mA, 9/- each. 800 P.I.V. 500 mA, 7/6 each. 400 P.I.V. 200 mA, 3/6 each.

### SELENIUM F.W. HIGH CURRENT BRIDGE RECTIFIERS

18 v. 8 amps. 4 1/2 in. sq. Price	19/6
18 v. 18 amps. 7 1/2 in. sq. Price	39/6
18 v. 36 amps. 7 1/2 in. sq. Price	79/6
18 v. 54 amps. 7 1/2 in. sq. Price	117/6
36 v. 8 amps. 4 1/2 in. sq. Price	39/6
36 v. 18 amps. 7 1/2 in. sq. Price	79/6
36 v. 36 amps. 7 1/2 in. sq. Price	119/6
36 v. 54 amps. 7 1/2 in. sq. Price	235/-
54 v. 8 amps. 4 1/2 in. sq. Price	59/6
54 v. 18 amps. 7 1/2 in. sq. Price	117/6
54 v. 36 amps. 7 1/2 in. sq. Price	235/-

Volts/amps indicated are maximum input volts and amps. are max. current out. Supplied brand new and guaranteed. Not government surplus.

### FIELD STRENGTH METERS

100-150 Mc/s. Contains 0-1 mA meter. IS5 valve, chrome telescopic aerial, etc. New condition in black crackle case. Operates on 1.5 V. and 90 V. batteries. Dimensions: 7 x 7 x 7 1/2 in. 45/-. P. & P. 2/9.

### 20-0-20 AMMETER

2 in. flush mounting. D.C. Brand new. 11/6 each. post 1/6.

### A GEARED ELECTRIC MOTOR


FOR ONLY 9/6. Post and Packing 2/6. Due to bulk purchase we are able to offer these 24 V. Rotary Convertors at this fantastic price. Easily modified for mains operation (full-simple conversion details supplied). Complete with 400 to 1 reduction gearbox.

### AR 88 LF RECEIVERS

75-550 Kc/s and 1.5 to 30 Mc/s. 110/240 v. A.C. input. In as new condition and fully tested £30. Carriage and packing 25/-.
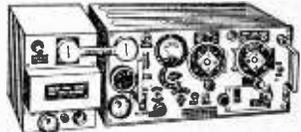
### WIRELESS SET NO. 17

Complete with original power supply unit for 12 volts input. Transmitter/Receiver covering 2-8 Mc/s and V.H.F. 240 Mc/s. 6 valve superhet receiver and 6 valves in Transmitter. Using I.F. of 465 Kc/s. For voice and C.W. In good condition not tested. £4.17.6. Plus £1 packing and carriage. Microphone and headset for this set 17/6 plus 2/6 post and packing. 19 Set Variometers, 17/6 plus 2/6 post and packing. Control box for 19 set, 10/- plus 2/- post and packing.



### SPECIAL OFFER OF 6in. METRO-VIC TEST METERS

ALL AT ONE PRICE 25/- FOR CALLERS ONLY

including  
 0/20/50 mA, 0/100 mA, 0/15 mA, 0/500 mA, 0/50 mA, 0/300 volts D.C., 0/30 volts D.C., 0/50 volts, 0/100 volts, 0/5 Kv, 0/500 volts, and many others. All in perfect condition (surface mounting).

### ON VIEW IN OUR SHOP FOR CALLERS ONLY. VERY LARGE RANGE OF TEST GEAR including

Signal generators, Decade resistance boxes, Pen recording Voltmeters and thermometers, Electronic Tuning Forks, etc.

### L.T. TRANSFORMERS

Pri.: 240 volts. Output 6.3 volts 5 amps. 9/6, post 2/6. Pri.: 240 volts. Output 17 volts 1 amp., 9/6, post 2/-.

### H.T. TRANSFORMERS

Type (350/120) Tapped 200/250 V. Input 350/0/350 v. 120 mA. 6.3 V. 31 amp. 5 v. at 2 amps., 18/6. P. & P. 3/6. Type 5K Pri. 200/250 V. Output 350/0/350 V. 350 mA. 5 v. 3 amps. Tapped 4 v. 2 v. 2 amps. 10 kv. ins. 20 v. 1 amp. 7.5 v. 1 amp. 5 kv. 5 mA. Price 25/- Post & Packing 6/-.

### SPECIAL H.D.

50 volts 10 amps. transformers. 250 volts input. Brand new and boxed. Conservatively rated. 55/- each. Carriage 7/6.

### ASSORTED PACKETS OF 100 BRAND NEW RESISTORS

Including miniature and high stab., 12/6 post paid all useful values.

### CONDENSERS 100 ASSORTED

Including mica, ceramic, metal tubular etc. 15/- post free.

### VARIABLE AIR-SPACED CONDENSERS

150 pFd with lin. spindle, 4/8 each. 75+75 pFd with lin. spindle, 4/8 each. 100 pFd with lin. spindle, 2/6 each. 100 pFd pre-set, 2/- each. 50 pFd pre-set, 1/6 each.

### TERMS OF BUSINESS

CASH WITH ORDER. Handling charge of 1/6 on all orders under 20/- where P.P. is not otherwise stated.

### TYPE 68 TRANS/RECEIVER

3 to 5.2 Mc/s. Portable station with range up to 10 miles under good conditions. In very good condition, complete with valves hand mike and aerial rods. 70/- plus 9/6 carriage and packing. Require 150 V. H.T. 3 V. L.T. and 9 V. G.B.

### B.C. 221 FREQUENCY METERS

Every one tested and working in perfect order. Exterior slightly soiled. From £12.10.0. Packings and carriage 17/6.

### MORSE KEYS

Ex R.A.F. strap-on type. Perfect condition. 2/6 each, post paid.

### CRYSTALS !!!

LARGE RANGE OF 10X, 10XJ, FT243, FT241 CRYSTALS ALWAYS IN STOCK.

Send stamped and addressed envelope for our free, comprehensive list.

### WOBBULATOR FREQUENCY MULTIPLIER

Band 1. Channels 1-13, with 50 micro/ammeter and 0-80 dB attenuator. £9. P. & P. 10/-.

### DECCA X.M.S. L.P. PICK-UP HEADS

Brand New. 8/6. P. & P. 1/-.

### TF.144G STANDARD SIGNAL GENERATOR

85 Kc/s to 25 Mc/s. Fully serviced and in perfect condition. £36 post paid.

### DOUGLAS AUTO TRANSFORMERS

Auto 115-200-230-250v. 300w. 45/-, P.P. 5/-, Auto 110-120-200-240v. 75w. 18/-, P.P. 3/6, Auto 115-200-230-250v. 900w. 78/6, P.P. 5/-, Auto 115-200-230-240v. 1kw. 118/-, P.P. 6/6.

### MOTORS 200v-230v 50c

Shaded pole. Made by Hoover for washing machines. Brand New. 30/- each, P. & P. 7/6 Also 115v. A.C. 22/8 each. P. & P. 7/6.

### E.H.T. TRANSFORMERS


E.H.T.1. Input 200/250 volts 50 C/s. Output 2kV. 10 M/a 4 v. 1A. 0-2-4V. 1.5A., 22/6. P. & P. 5/-.  
 E.H.T.2. Input 200/250 volts 50 C/s. Output 2.5 kV. 10 M/a. 6.3 v. 3A. 2 v. 1.5A. 3.5 kv. D.C. Wks. 22/8. P. & P. 5/-.  
 E.H.T.4. Input 200/250 volts 50 C/s. Output 2,000 v. 15 M/a. 4 v. 1.5A. 0-2-4 v. 2A., 29/6. P. & P. 5/-.

# LASKY'S RADIO

The finest range of Transistor Receivers available for home construction
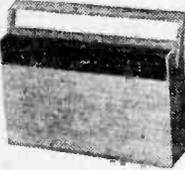
## "COROVER" 'SIX'

★ A6-transistor plus 2-diode superhet receiver using the latest circuitry. ★ Three Mullard AF117 alloy diffused transistors are used with OA79 and OA91 diodes followed by OC81D and two OC81's in push-pull. ★



I.F. frequency 470 Kc/s. ★ Covers the full medium and long wavebands. ★ Sockets provided for personal earpiece or tape recorder, and car radio aerial. ★ Laffe internal ferrite rod aerial gives high sensitivity. ★ Uses four 1.5 v. pen torch batteries. ★ All components mounted on a single printed circuit. Simple stage by stage instructions. ★ Cabinet size 6 1/2 x 4 x 1 1/2 in. With carrying handle. ★ All coils and I.F.'s ready wound.

ALL COMPONENTS AVAILABLE SEPARATELY. Data and instructions separately 2/6. Refunded if you purchase the parcel.

CAN BE BUILT FOR **£5.7.6** P. & P. 4/- ex. Batteries 1/4.

## "SPRITE"

Inclusive price of

**79/6**

P. & P. 3/6 extra.




★ Six-Transistor Superhet Miniature Personal Pocket Radio. ★ Tunable over Long and Medium wavebands. ★ Uses PP3 battery, Ferrite Rod aerial. ★ I.F. Frequency 470 Kc/s. Transistors: 3 Philco 2087's, 2 Mullard OC81 M OC81 DM and OA90 diode. ★ 3 inch speaker. ★ Printed circuit 2 1/2 x 2 1/2 in. ★ Slow Motion Drive. ★ In Plastic Case. Size 4 x 2 1/2 x 1 1/2 in.

In order to ensure perfect results, the SPRITE is supplied to you with R.F. and I.F. stages, Driver and Output stages ready built with all components ready mounted on the printed circuit. To complete assembly you only have to fit the wavechange switch, tuning condenser and drive, volume control, earphone socket and aerial rod, the remaining components all having been pre-fitted at the factory for you. The SPRITE is offered as above, pre-assembled, plus cabinet, speaker and all components for final construction, at the inclusive price of 79/6. Postage and packing 3/6 extra. Data and instructions separately. 2/6. Refunded if parcel is purchased. Real calf leather case, wrist-strap, personal earphone and case for earphone and battery 12/8 the lot extra. Make no mistake this is a SUPERHET receiver of genuine commercial quality. It is not a regenerative circuit.
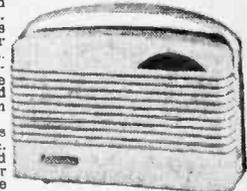
## "REALISTIC" 'SEVEN'

STAR FEATURES ★★★★★

- ★ 7 Transistor Superhet. 350 Milliwatt output into 4-inch high flux speaker.
- ★ All components mounted on a single printed circuit board, size 5 1/2 x 5 1/2 in. in one complete assembly.
- ★ Plastic cabinet, with carrying handle, size 7 x 10 x 3 1/2 in. in choice of colours: Red/Grey, Blue/Grey, all Grey.
- ★ Easy to read Dial.
- ★ External Socket for car aerial.
- ★ I.F. frequency 470 Kc/s.
- ★ Ferrite rod (int'l) aerial.
- ★ Operates from PP3 or similar batt.
- ★ Full comprehensive data supplied with each Receiver.
- ★ All coils and I.F.'s etc. fully wound ready for immediate assembly.



An Outstanding Receiver. Lasky's Price for the complete parcel including Transistors, Cabinet, Speaker, etc., and Full Construction Data: **£5.19.6**  
P. & P. 4/8.  
PP3 Battery 3/9. Data and instructions separately 2/6. Refunded if you purchase the parcel.

207 EDGWARE ROAD, LONDON, W.2.  
Near Praed St. PADDINGTON 3271/2

33 TOTTENHAM COURT ROAD, W.1.  
Nearest Stn., Goodge St. MUSEUM 2605

152/3 FLEET STREET, LONDON, E.C.4.  
Telephone: Fleet Street 2833.  
Open all day Thursday. Early closing Sat.

THE  
PEMBRIDGE  
COLLEGE  
OF ELECTRONICS  
PROVIDES TRAINING  
IN RADIO  
AND TELEVISION

### ATTENDING COURSE

Full-time One-Year Course in Radio and Television. College course in basic principles for prospective servicing engineers. Next course commences 3rd September, 1963. This course is recognised by the Radio Trades Examination Board (R.T.E.B.) for the Radio and Television Servicing Certificate examinations. Provides excellent practical experience on valve and transistor radio receivers and all well-known makes of television receivers.

To:

The Pembridge College of Electronics (Dept. P11)  
34a, Hereford Road, London, W.2

Please send, without obligation, details of the One-Year Course.

Name \_\_\_\_\_


Address \_\_\_\_\_

# T rade N ews
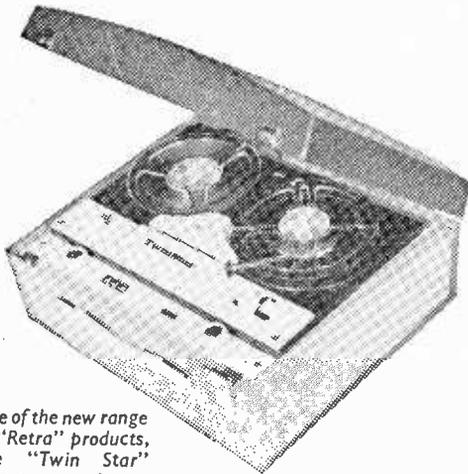
## Morse Trainer

A COMPREHENSIVE morse training instrument has just been announced by Aero Electronics Limited. Mains or battery operated versions of this unit (the SCOPA T/20) are available, and each trainer can provide for 20 headsets and keys.

The SCOPA T/20, which features a fully transistorised circuit, is manufactured by *Aero Electronics Limited, Gatwick House, Horley, Surrey.*



One of the new range of "Retra" products, the "Twin Star" tape recorder.

## New Brand of Electrical Merchandise

A COMPLETELY new brand of electrical merchandise has been introduced recently under the trade name of "Retra". These goods will be exclusive to Radio and Television Retailers Association (R.T.R.A.) member shops, and will be quality controlled by a committee of the R.T.R.A.


The twin-track tape recorder illustrated above, is one of the new "Retra" products. Called the "Twin Star" it costs only 22 guineas. *R.T.R.A., 19-21 Conway Street, Fitzroy Square, London W1.*

## Four Waveband Portable

A NEW four waveband, portable receiver has been added to the range of radios made by the Standard Corporation of Japan and stocked, in the U.K., by their agents Denham and Morley Limited.

This new model—the SR-J802FL—covers long, medium and short waves, and also a v.h.f. band. It is powered by four torch batteries and employs a ten transistor circuit.

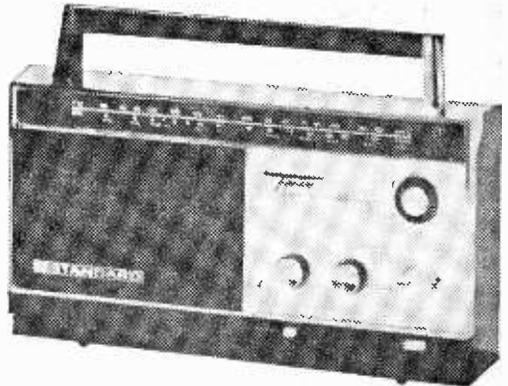The price of the SR-J802FL is 32 guineas and is available from *Denham and Morley Limited, Denmore House, 172-175 Cleveland Street, London W1.*




This Standard portable receiver is stocked in the U.K. by Denham and Morley Ltd.
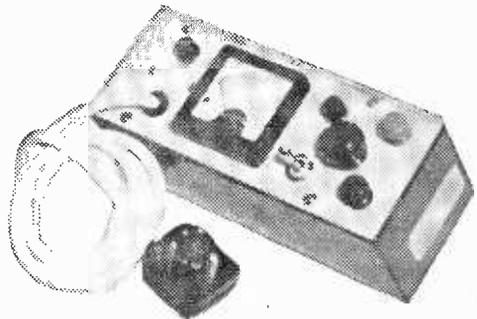
## Low Voltage Power Supply

A LOW voltage power supply is an essential for anyone proposing to service transistor equipment and for this purpose, Anagraph Precision have brought out the type V.P.10 unit which provides a d.c. output continuously variable from 0.1 to 10V. The output is controlled by a single knob and currents between 0 and 250mA can be obtained.

The unit is housed in a steel box, 3in. x 3in. x 8in. and costs £14 10s. The manufacturers are *Anagraph Precision, 31 Charlton Road, Two Mile Hill, Kingswood, Bristol.*



This low voltage power supply unit is made by Anagraph Precision.

# LETTERS TO THE EDITOR

## Novice Licences

**SIR**,—I think that the enclosed article I submitted to our School Magazine and which was duly published, will be of interest to all your readers.

*"Past and present members of the School Radio Society mourn with me the passing of an era. You who enjoyed the thrill of speaking into the microphone of the Society's transmitter . . . with the blessing of the representatives of the powers that be—mourn with me the death of an institution."*

*"For eight years . . . we have enjoyed contacts with old and new friends over the air. Now, however, the blow has fallen. Red-tape, bureaucracy, pomposity, or call it what you will, has decreed that if a boy speaks into the microphone, by the same token he is operating the transmitter, and this he cannot do unless he has taken the necessary Amateur Examination and shown a proficiency in sending and receiving Morse. By the same token, if a boy coughs, laughs, slams a door or hammers a nail into a piece of wood, he modulates the transmitter and is committing the crime of "operating" the set. Hence, at all times in the future when the only authorised operator is transmitting, a deathly hush will be over all in the shack, Big Brother Monitor will be listening somewhere in England for the slightest wheeze, cough snuffle or crackle."*

This will indicate to all those who hopefully seek a novice licence the amount of sympathy they can expect from official circles!—E. T. WARD (G3JWC, Burton-on-Trent, Staffordshire).

## TRADE NEWS

—continued from previous page

### Oil Applicator

A NEW Swiss-made device for lubricating switch contacts occurring in radio equipment is available in Britain under the trade name of "Lubristyl". It is constructed in the form of a pen so that oil may be applied accurately by placing the nozzle on the point to be lubricated and pressing down slightly, which opens a valve and allows a small amount of oil to flow.

The Lubristyl oil applicator is available from the U.K. distributors (Haymor Ltd.) on their receipt of a remittance of 12s. 6d. (the retail price). The sole distributors in this country are Haymor Ltd., 167 Greyhound Road, London W6.

### Preselector

THE new model PR.30 preselector from the Codar Radio Company, covers a frequency range of 1.5 to 30Mc/s. Used with any superhet receiver it will provide up to 20dB gain together

Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying commercial or surplus equipment. We cannot supply alternative details for receivers described in these pages. **WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE.** If a postal reply is required a stamped and addressed envelope must be enclosed with the coupon from page iii of the cover.

The Editor does not necessarily agree with the opinions expressed by his correspondents

## No Justification Necessary

**SIR**,—With reference to "Amateur Ambassador" on the Club News page of the July issue, I would like to comment that the Ham fraternity are always defending and justifying themselves; to prove that they are entitled to wavelength allocations because of their usefulness to society. That they do serve a useful purpose I do not dispute, but why this attitude?

Are we only allowed to operate because we are useful to the community? Is the G.P.O. waiting to grab our bands unless we can prove this?


We all know that there are many demands on the radio space—that powerful interests may dominate and gradually steal our allotted bands, but will cringing to authority get us anywhere? After all this is a democracy and we a free people, thus the ether is common property and every individual has a right to use it. The duty of authority is to safeguard these rights by allowing everyone a fair and equal share, not by allowing strong influences to dominate over the weak. I can see the heads shaking as these words are read and the reader saying to himself "this chap is living in a dream world".

Well, maybe so. As individuals we submit to examinations and inspection because we understand that this is necessary, but I see no reason to have to justify amateur operation further.

This letter is not an attack on the G.P.O. for I have always found them most helpful and I think they would respect us more if we stopped making excuses.—H. COLE (Workington).

with substantial image rejection and improved signal/noise ratio.

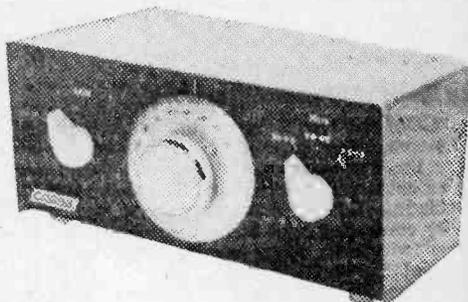The price of the PR.30 is £4 17s. 6d. and it is obtainable from Codar Radio Company, Bank House, Southwick Square, Southwick, Sussex.




Codar's new model PR.30 preselector.

# ACCLAIMED THE MOST AMAZING RECEIVER EVER


You've never seen or heard transistor set design like this before. Small enough to conceal in one hand, the Sinclair "Slimline" gives choice of British and European programmes with staggeringly good quality from its own internal ferrite rod aerial. With its entirely new R.F. Reflex Circuit, superhet selectivity is achieved without any of the latter's problems of alignment. And it's so easy to build with its neat printed circuit board and well illustrated and presented instructions. Success is assured before you begin to build even if you are new to receiver construction.

*Such dramatic new standards within even smaller dimensions are made possible through the wonderful new MAT Transistors in circuitry developed exclusively to exploit their amazing characteristics—yet it costs so little to build this minute receiver with its giant performance—so send for yours NOW!*

**THE PERFECT SET FOR YOUR HOLIDAY!**

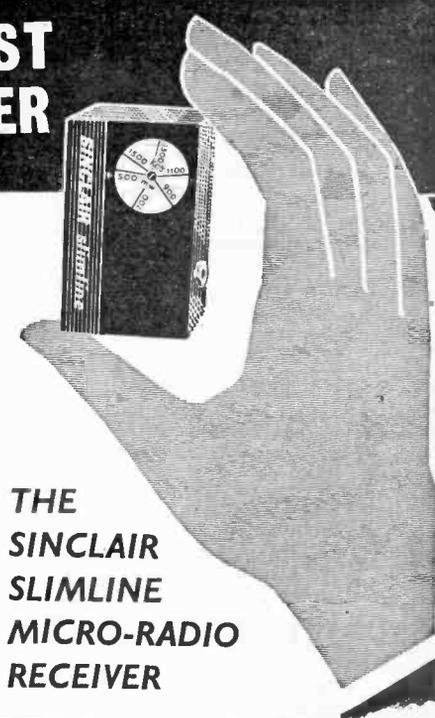
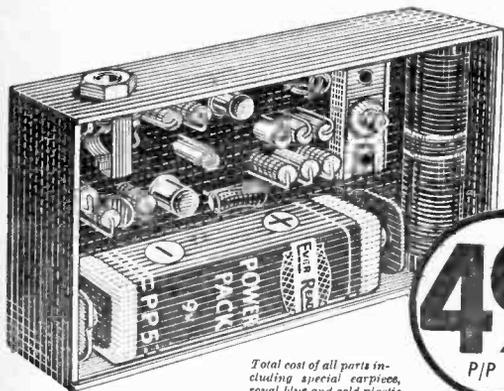
## THE SINCLAIR SLIMLINE MICRO-RADIO RECEIVER



*Total cost of all parts including special earpiece, royal blue and gold plastic case and instructions.*

**49'6**  
P/P 1/6

**BUILT IN A COUPLE OF HOURS** **2 3/4" x 1 5/8" x 5/8"**  
**COMPLETELY SELF-CONTAINED**

**RECEIVES HOME, LIGHT, THIRD AND COUNTLESS EUROPEAN STATIONS WITH FANTASTIC EASE AND QUALITY**

### MAT TRANSISTORS

**MAKE THIS WONDERFUL PERFORMANCE POSSIBLE**



These amazing new Micro Alloy Transistors take transistor performance into entirely new fields by their coverage of A.F., I.F., R.F., and V.H.F. frequency bands. They provide far greater gain for less power consumption so that two MAT Transistors can do the work of three ordinary types with considerable saving in space, components and cost. Each one is carefully tested before leaving the factory. For full description, send for our book "22 TESTED CIRCUITS USING MICRO-ALLOY TRANSISTORS", price 5s. 9d. inc. postage.

Gold-plated leads assure perfect contact.

MAT 100 **7/9** each      MAT 101 **8/6** each  
MAT 120                      MAT 121

Comprises brand new sub-miniature components, genuine MAT TRANSISTORS, elegantly designed plastic case and calibrated tuning control with high quality featherweight earpiece; also thoughtfully presented step-by-step instructions.

Enthusiastic testimonials continue to pour in. Here are more typical examples.

"A most ingenious set. Having built it for amusement, I find myself using it for serious listening more and more, it is so reliable."  
J.A., Wakefield.

"Would never have thought such performance possible from such a tiny set. Log Rome, Moscow, Brussels and many more stations with ease, as well as B.B.C. and Luxembourg." F.G.M., Lewes.

"Wonderfully easy to build. Please send two more for the rest of the family who are quite converted to this 'new way of listening.'"  
C.H.L., Norwich.

To **SINCLAIR RADIONICS LTD., 69 Histon Rd, Cambridge**

Please send Parts for building SINCLAIR "SLIMLINE" RECEIVER...

"22 Tested Circuits Using Micro Alloy Transistors"  
.... MAT 100: .... MAT 120: .... MAT 101: .... MAT 121 Transistors  
for which I enclose Cash/ Cheque/ Money Order  
for £..... Mark off items required

NAME .....

ADDRESS .....

BLOCK LETTERS PLEASE. PWS

**SINCLAIR radionics LTD.**  
**69 HISTON ROAD, CAMBRIDGE**

## RECEIVERS &amp; COMPONENTS

**EXCEPTIONAL VALUE:** Picture Tubes, brand new, Mazda 19in. CME190L, Mullard 19in. AW47-90/91, £4/10/-; Mullard 23in., AW59/90, £8/10/-; carriage (insured) paid, 12 months' guarantee. Note: All brand new. We also supply most other sizes completely regunned at £4/17/6, guaranteed 12 months. TOMLINS, 156 Lewisham Way, New Cross. SE14. TD 3857.

**THE FINEST READY TO OPERATE COMMUNICATIONS RECEIVER EVER OFFERED TO THE SHORT WAVE ENTHUSIAST**

SEND S.A.E. NOW FOR DETAILED LEAFLET OR ENCLOSE 5/- FOR HANDBOOK

**f9**

COMPLETE, AND CARRIAGE PAID

ANADIAN MARCONI 52 RECEIVERS

Set is complete with Power Unit Z.E. 12, and connecting cable, ready to operate from 230/240 v. A.C. Mains, or 12 v. Battery. Ample Spare Valves stocked. Suitable Headphones 12/6 extra.

**G.W.M. RADIO LTD.**  
40/42 Portland Rd WORTHING

**SPEAKER REPAIRS.** Cones/Fields fitted. Clock coils wound. L. S. REPAIRS, Pluckley, Ashford, Kent.

## Glasgow Electronic Services

21 OLD DUMBARTON ROAD, GLASGOW, CB  
Telephone WEST 2642

**"FOR THE COMMUNICATIONS RECEIVER MAN"**

**GANG TUNING CAPACITORS:** 2, 3 or 4 gang, max. capacity 210 or 487pF ceramic insulated condensers, 14/9, 19/3 and 26/3 respectively, either capacity. **BANDSPREAD TUNING CAPACITORS:** 2, 3 or 4 gang; 2 gang available 10 or 27pF max. at 11/3, 3 gang 15pF max. at 19/3, 4 gang 15pF at 27/6. **"WAVEMASTER"** S.W. VARIABLES: A range of single, ceramic insulated, brass vanes, tuning capacitors. Can be ganged to form a low loss tuning or bandspread condenser. Available 15pF at 4/8, 25pF at 4/8, 40pF at 4/8, 60pF at 4/8, 60pF at 5/3, 75pF at 5/8, 100pF at 5/9, 100pF at 8/-, 200pF at 7/6. **B.F.O. TRANSFORMERS:** 85 kc/s, 465 kc/s or 1.8 Mc/s nominal frequencies. **FORMERS:** 465 kc/s, 1.8 Mc/s or 10.7 Mc/s nominal frequency, litz wound, permeability tuned, highly efficient transformers, min. size 6/8 each. **DOUBLE SUPERHET TRANSFORMERS:** Narrow band 85 kc/s or 100 kc/s transformers. Iron dust tuning. 16/- each. **TUNING COILS:** Full range of Denno Maxi-Q coils covering from 150 kc/s to 78 Mc/s. Mixer B.F., Osc., plug-in or chassis mounting, from 4/1 each. Full technical information, circuits, etc., in Bulletin DTB4, 8/- post paid. **SCREENED VALVE-HOLDERS:** Low loss B7G or B9A screened valveholders, ideal for 8W construction, 1/10 each.

Plus, of course, our large range of accessories for receiver construction—R.F. Chokes, Chassis, Tagboards, group panels, B.W. Transistor coils, capacitors of all types, etc., etc. Send for our latest list, 6d. post free.

Terms of business: Cash with Order; C.O.D. 3/- extra. Postage extra under £3 total value.

**RATES:** 7/3 per line or part thereof, average five words to line, minimum 2 lines, Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless", Tower House, Southampton St., London W.C.2.

## RECEIVERS &amp; COMPONENTS


(continued)

**CLOSING DOWN SALE.** Thousands of Radio and TV Components at giveaway prices. Constructor's parcel of condensers, transformers, resistors, pots, valves, etc., only 19/6, pp. 2/6. M. SEED 4 Heather Grove, Ribbleson, Preston, Lancs.

**A1 POST-FREE BARGAINS.** Guaranteed set Tested Valves: EF80, EB91, 10P1 9d. each, 3 for 1/6; L63, 2/-; EOL80, 2/6, 3 for 6/-; PZ30, PY81, EL38, PL33, 3/6; PL83, PL82, PY80, PY82, PCF80, 4/-; KT36, N37, B36, PY31, U281, U282, 20P1, 27SU 4/6; EB41, EBC41, EOC81, EOC82, EL42, PL81, U31, UY41, UP41, UF42, UL41, UL44, UL46, UY41, 6C13, 10C2, 6LD20, 20L1, 5/-; 30P4, 53KU, EL33, PL36, U07, 7/-.

Thousands of valves in stock, including obsolete types. Exchange, reclaimed and all-new B.V.A. types and makes. **A1 RADIO COMPONENTS,** 14 The Borough, Canterbury, Kent.

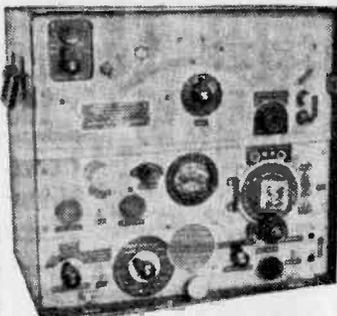**MARCONI CANADIAN RECEIVER No. 52**  
(Brand New)



**AMATEUR SHIPPING BROADCAST**

Magnificent 10 valve receiver in 3 wavebands covering 1.75-16Mc/s (19-170 metres), plus 3 valve crystal calibrator employing dual 100/1000kc crystal to provide marker check at 10-100-1000kc/s. 1 RF and 2 IF stages. Other refinements include valve check meter, internal 3in. speaker, RF-AF gain, Noise Limiter, BFO, Heterodyne Pitch, Wide/Narrow Bandwidth, Speaker or Phones, Man or AVC on CW and RT, Fast/Slow tuning with additional Osc. for fine adjustment. Power required: HT 160v, 60mA, LT 12v. 1½. Circuit supplied. SIZE 15" x 12" x 15".

**BRAND NEW.** Complete with Power Pack for 115/230v AC mains and 12v DC., £12.19.6. carr. 20/-.

Many other surplus bargains with **PERSONAL SERVICE.** Lists 6d. S.A.E. inquiries.

**A. J. THOMPSON**  
"EILING LODGE"  
CODICOTE, HITCHIN, HERTS.  
Phone: Codicote 242.

## RECEIVERS &amp; COMPONENTS

(continued)

**ALL TYPES LINE OUTPUT TRANSFORMERS SUPPLIED (RETAIL AND TRADE).** Finest service in the country. Send S.A.E. for return of post service. Terms C.W.O. or C.O.D. Trade enquiries invited. **D AND B TELEVISION (WIMBLEDON) LTD.,** 131 Kingston Road, Wimbeldon, SW19. CHERRYWOOD 3955.

"**HEATHKITS**" can now be seen in London and purchased on easy terms. Free brochure. **DIRECT TV REPLACEMENTS LTD.,** Dept. P.W.7/9, 126 Hamilton Road, West Norwood, S.E.27. GIPSY HILL 6166.

## NEW VALVES! GUARANTEED!

EBF80	7/6	EL84	6/6	PCL84	6/6
EBF89	8/9	EY51	7/6	PCL85	8/6
ECC81	4/6	EY81	7/6	PL6	8/6
ECC82	4/6	EZ40	6/6	PY33	11/-
ECC83	6/3	EZ80	6/3	PY81	7/-
ECL90	5/9	PC84	6/9	PY82	6/6
ECL82	9/-	PC89	8/9	U25	11/6
EF80	4/9	PCF80	7/9	UC88	7/6
EF85	5/9	PCF82	7/-	UCH42	7/6
EF86	8/9	PL82	9/-	6BW6	7/6

Postage 6d. per valve extra.

S.A.E. for full lists and discounts


**LEWIS ELECTRONICS**

16 GLENWOOD GARDENS, GANTS HILL, ILFORD, ESSEX.  
Telephone: Crescent 5485

**DIRECT TV REPLACEMENTS LTD.,** largest stockists of TV Components in the U.K. Line Output Transformers, Frame Output Transformers, Deflector Coils for most makes. Official sole suppliers for many set makers. Same Day Dispatch Service. Terms C.O.D. or C.W.O. Send S.A.E. for quotes. Day and Night Telephone GIPSY HILL 6166. 126 Hamilton Road, West Norwood, S.E.27.

**DATA TRANSISTOR POCKET KITS**  
NO SOLDERING OR DRILLING, COMPLETELY SELF CONTAINED

NO AERIAL REQUIRED - MEDIUM & LONG WAVE - ASSEMBLY TOOL PROVIDED - CAN BE BUILT BY ANYONE

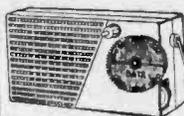

**DATA 55**  
5 85MI-CONDUCTORS  
5 STAGES  
MOVING COIL SPEAKER  
**50/-** P.P. 2/9 extra.  
Battery 2/3 extra.

5½ x 3 x 1½in.

**DATA 427, 4 TRANSISTORS, 2 DIODES, 7 STAGES, MOVING COIL SPEAKER** **65/-** extra.  
Battery 2/3 extra. P.P. 2/9 extra.



**DATA 326**  
3 TRANSISTORS  
2 DIODES  
6 STAGES  
PERSONAL EARPIECE  
**40/-** P.P. 2/- extra.  
Batt. 1/- extra.

4½ x 2½ x 1½in.

All Parts Supplied Separately

**DATA ELECTRONICS LTD.**

6 HILLSIDE GDNS., EDGWARE, Middlesex

**RECEIVERS & COMPONENTS**

(continued)

**HALF PRICE** Transistors. Mullard OC44, OC45, OC81, OC81D, OC170, OC171, all 4/6 each, min. 4 doz. lots: OC26, OC36, 12/6 each. Post 9d. C.W.O. **RADIOMEX**, 184 Kingston Road, Portsmouth.

**CONDENSERS.** Fantastic Bargain! 500,000 Miniature Condensers, 1in. long, 1in. diameter. Tested 750V. Capacity .0001 to .04uF, 7/6 per 100, post free. Ideal for transistor sets. **MILWARD**, 17 Peel Close, Drayton Bassett, Staffordshire.

**FOR SALE**

**ETCHING PRINTED CIRCUIT KIT**

Consists of Plastic Bath and Case. Size 9 x 5 x 2 in. Contents: Solvent, Etchant, Resist, 100 sq. in. Copper Laminate Board. Comprehensive book gives examples and circuit layouts. 18/6 inc. post.

**RADIOCENTRE**

94 Hurst Street, Birmingham. Dept. P

**240watt ELECTRIC POWER ANYWHERE**  
**ANYTIME!** from 12 watt CAR BATTERY  
 THE AMERICAN DYNAMOTOR UNIT  
 Input 12v. output 200/250v at 150 to 220 watts.  
 Perfect for TELEVISION. POWER TOOLS and all  
 universal AC/DC ELECTRICAL EQUIPMENT, plus  
 wonderful results. Price only £8. - incl. carriage.  
 Best transport unit for full technical details  
 W. SCIENTIFIC PRODUCTS, CLEVELAND, U.S.A.



**Corvair 6-Transistor Pocket Radios** with all accessories, only 95/- each. **Spl Mains Soldering Irons**, 15/- each. **Low Imp Earpieces**, 3/6 each. **High**, 4/9 each.

**BUMPER BARGAIN PARCELS**

All Brand New. Not Ex-Gov. Contents plus many more items: 100 mixed resistors, 100 mixed condensers, volume controls, pre-set pots, tag strips, etc. This is a must, only 20/- post free.

**100% Tested and Fully Guaranteed Transistors** by Mullard and Mazda. All Brand New and these are not seconds.

OC44, OC45, OC81, OC81D, 3/6 each; OC170, OC171, 4/- each; OC26, 12/- each; Red Spots, 1/3 each; XB103, XA102, 2/3 each; XC141, 6/6 each; XD210 Sub. Min. Diodes, 9d. each, 6/- doz.

S.A.E. FOR FREE BARGAIN LISTS

**B. W. CURSONS**

78 BROAD STREET  
 CANTERBURY, KENT


**FOR SALE**

(continued)

**EXCEPTIONAL** Transistor Portable Tape Recorder, value £6/19/6, complete with crystal microphone, earphone, spools, tape, batteries, instructions, presentation box (extra tapes 100ft 4/6). Ideal gift, £6/19/6. Satisfaction guaranteed. Postage, packing 2/6. **TOMLINS**, 156 Lewisham Way, New Cross, SE14.

**AMATEUR LICENCE** Morse Course. The new Rhythm Method of teaching takes the drudgery out of learning Morse and is the quickest known! For full explanatory booklet: 6d. Stamp G3CHS, 45 Green Lane, Furley, Surrey.

**GUITAR AMPLIFIERS WITH TREMOLO**

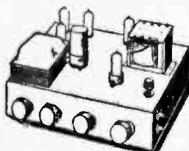

Hi Fi 15 watts. Valves ECC83, ECC83, ECC82, EL84, EL84, EZ81. Four jack inputs. Six controls: two volume, bass, treble, tremolo speed, depth. Remote plug, 3 and 15 ohm outputs. Real value. Ready built, £11. Similar 30 watt. Valves ECC83, ECC83, ECF82, EL84, EL84, EZ81, £14. Amplifiers as prev. advert. 15 watt (illust.) Kit, £6.10.0, ready built £9. 30 watt, Kit £9.10.0, ready built £12. Add carr. 7/6 any amplifier. Send for free leaflet.

**STROUD AUDIO**

Bath Road, Stroud, Glos.  
 Tel. Stroud 783.

**COMPLETE TELEVISION SETS.**

Untested, 12in. 15/-, 14in. 25/-, 14in. 13-Channel £2. Carriage on any set 10/-. Insurance against damage 8/6 extra. 4 h.p. 220-250V. Motors (second hand), all tested and in good working order, 30/-. Post and packing 8/-. Orders to **MODERN ELECTRICS (BFD.) LTD.**, 89 Holroyd Hill, Wibsey, Bradford, Yorkshire. Tel.: 76924.

**E. R. NICHOLLS**

**No. 1 BUMPER PARCEL**

- 100 Assorted Resistors.
- 50 Assorted Condensers.
- 15in. 3 ohm Elac Speaker.
- 1 Isolating Transformer.
- 4 Terminal Blocks.
- 2 Rotary Toggle Switches.
- 1 Small Chassis containing 60 components.
- 2 Westectors.
- 2 Thermistors.
- 100 Cartridge Fuses.

**No. 2 BUMPER PARCEL**

- 1 Pair Test Prods, retractable with leads and spades.
- 17 x 4in. 3 ohm Speaker.
- 6 Assorted Valves.
- 6 Assorted Potentiometers.
- 6 Assorted Valve Bases.
- 25-Way Plugs and Sockets with leads.
- 4 Mixed Plugs or Sockets.
- 100 Cartridge Fuses.
- 1 Inductance Variometer.

One for 20/- Post Free, or any two parcels 35/- Post Free.

20ft. Steel Telescopic Mast, 50/- High Stub Resistors 6d. each. List now ready for **Paper Block Condensers, Valves, Oscillators, Test Sets.** S.A.E. Please.

Mail Order and Retail Shop:  
 46 Lowfield Road, off Shaw Heath, Stockport, Cheshire.

**AERIALS**

**140ft. AERIAL INSTALLATIONS**

First Government release of these brand new Marconi coil Aerial tuning systems, enabling operators to work their Receivers or Transmitters to their best efficiency. Containing a drum of 140ft. Copper aerial wire with insulators, etc., feeding into the matching unit, size 13in. x 8 1/2in. x 9 1/2in., with slow motion tuning using Nos. 0-999. Originally intended for the 52TX-RX, a must for any poor reception areas and serious operators.

300 ONLY, 35/-  
 Post 5/-, two post free.

**Dept. N., J. T. SUPPLY**

309 Meanwood Road, Leeds 7

**SERVICE SHEETS**

**SERVICE SHEETS** for all makes of radio and TV 1925-1963. Prices from 1/- with free fault-finding guide. S.A.E. enquiries. Catalogue of 6,000 models 1/6. 125 Radio/TV Sheets covering many popular models 21/- Valves, modern and obsolete. Radio/TV books. S.A.E. lists. **HAMILTON RADIO**, Western Road, St Leonards, Sussex.

**WHY TOLERATE DELAY** when we can supply your Radio or TV Service Sheet by return of post at 4/- each plus postage. List 1/-. Also Manuals for sale and hire. List 1/-. S.A.E. with inquiries, please. Mail orders only to S.P. DISTRIBUTORS, 44 Old Bond Street, London W1.

**TRADE SERVICE SHEETS** offered by retired engineer. If I haven't got it you won't get it. All 4/- each by return. Please include large S.A.E. Mail orders only: **ETIZIONI**, 80 Merrion Avenue, Stanmore, Middx.

**FAULT-FINDING FILES** showing common faults that each receiver is prone to and other useful servicing information 2/- each. List 9d. plus postage. Mail orders only. S.P. DISTRIBUTORS, 44 Old Bond Street, London W1.

**SERVICE SHEETS:** Radio, TV, 5,000 models. List 1/-. S.A.E. enquiries: **TELRAY**, 11 Maudland Bank, Preston.

**SERVICE SHEETS,** Radio and TV, 4/- each. List 1/-. All orders dispatched on day received. Also Manuals for sale and hire. List 1/-. S.A.E., please: **SULTAN RADIO**, 29 Church Road, Tunbridge Wells, Kent.

**SERVICE SHEETS,** Radio and TV, 4/- each post free. All types. Send S.A.E. for inquiries. **D. AND B. TELEVISION (WIMBLEDON) LTD.**, 131, Kingston Road, Wimbeldon, SW19. CHE 3955.

**SERVICE SHEETS,** also Current and Obsolete Valves for sale. **JOHN GILBERT TELEVISION**, 1b Shepherd's Bush Road, London W2. Phone: SHE 8441.

(continued overleaf)

## WANTED

**A PROMPT CASH OFFER** for your surplus brand new Valves and Transistors, R.H.S., Beverley House, Mannville Terrace, Bradford 7.

**ABSOLUTE TOP PRICE** paid for Valves, Transistors, Components, etc., in quantity. Try us first. Cash by return. **WOLVERHAMPTON RADIO AND TV SUPPLIES**, 42 Darlington Street, Wolverhampton. Tel.: 20315.

## WANTED VALVES ONLY

Must be new and boxed  
Payment by return.

**WILLIAM CARVIS LTD.**  
103 North Street, Leeds 7

**WANTED: TEST GEAR**, Meters, Valves, Components, Communication Sets, Amplifiers. Letters only. **HUGGETT'S LTD.**, 2-4 Pawson's Road, West Croydon, Surrey.

**WANTED: NEW Valves and Transistors**, any quantity. **S. N. WILLETS**, 43 Spon Lane, West Bromwich, Staffs. Tel.: WES 2392.

**WANTED: Electronic Organ.** Any make, cheap. Box No. 47.

## NEW VALVES WANTED

Any type, any quantity

### CASH PAID

**R.S.T. Valve Mail Order Co.**,  
211A Streatham Road  
Mitcham, Surrey  
Telephone: MITCHAM 6202

## EDUCATIONAL

**BECOME "TECHNICALLY QUALIFIED"** in your spare time. Guaranteed Diploma and Exam., Home-study Courses in Radio, TV Servicing and Maintenance, R.T.E.B., City and Guilds, etc. Highly informative 120-page Guide—**FREE!** N.I.E. (Dept. 363), 148 Holborn, London EC1.

**"HOW AND WHY"** of Radio and Electronics made easy by a new, non-maths., practical way. Postal instruction based on hosts of experiments and equipment building carried out at home. New courses bring enjoyment as well as knowledge of this fascinating subject. Free brochure from: Dept. P.W.12, **RADIOSTRUCTOR**, Reading.

$$X = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

**DON'T FUMBLE** with Formulae. Master Mathematics quickly and easily the Understandable Way.

1st lesson  
and details  
**FREE**

The Dryden School of  
**UNDERSTANDABLE MATHEMATICS**

11F8 Dryden Chambers, Oxford  
St., London, W.1.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
\_\_\_\_\_

**LEARN RADIO AND ELECTRONICS** the new and practical way. Hosts of absorbing experiments carried out at home under expert guidance to teach you Radio in a new, enjoyable and interesting way. Construction, servicing and fault-finding on equipment made easy for the first time! No previous experience needed. No mathematics used. Free brochure from: Dept. 11, P.W., **RADIOSTRUCTOR**, Reading.

## EDUCATIONAL

(continued)

**THE MORSE CODE** can be memorised in less than one hour by the Coros System, 3/9 post free. **COROS**, 20 St. Mary Street, Bridgwater.

**THE Incorporated Practitioners in Radio and Electronics (I.P.R.E.) Ltd.** Membership Conditions booklet 1/-. Sample copy of I.P.R.E. Official Journal 2/- post free. Secretary, 32 Kidmore Road, Caversham, Reading, Berks.

## Radio Television & Electronics

Learn at home with the world's largest home study organisation, Brit.I.R.E.; City & Guilds; P.M.G.'s certs., etc. Also Practical Courses with equipment.

All books supplied.  
Write for **FREE** prospectus  
stating subjects to

**I.C.S.**

(Dept 541), Intertext House,  
Parkgate Road, London, S.W.11

**RADIO OFFICERS** see the world. Immediate sea-going appointments. Our many recent successes provide additional trainee vacancies during 1963. Day and boarding students. Grants and Scholarships available. Stamp for prospectus. **WIRELESS COLLEGE**, Colwyn Bay.

## EDUCATIONAL COURSES

COUNTY BOROUGH OF SOUTHAMPTON EDUCATION COMMITTEE

### SOUTHAMPTON COLLEGE OF TECHNOLOGY

(Incorporating Southampton Technical College)

Places are now being allocated in Full-Time Courses, beginning September 1963, in

## COMMUNICATION ENGINEERING AND ELECTRONICS

Three years' course leading to College Diploma and exemption from Graduate examination of British Institute of Radio Engineers. Minimum age 17 years.

## MARINE RADIO AND RADAR

Two years' course leading to P.M.G. 1st class Certificate for Radio Officers and M.O.T. Certificate in Radar Maintenance, qualifying for employment as Radio and Radar Officers in Mercantile Marine. Minimum age 16 years.

Full information and application forms obtainable from the Registrar, College of Technology, St. Mary Street, Southampton.



By repairing Radio and TV Sets as a job or as a spare time business. Our practical course will show you the way. No previous experience is required.

**SEND FOR FREE BOOK TODAY!**

## RADIOSTRUCTOR

Dept. G77

READING, BERKS

### BOOKS & PUBLICATIONS

**FIND TV SET TROUBLES IN MINUTES** from that great book "The Principles of TV Receiver Servicing", 10/6 all book houses and radio wholesalers. If not in stock from Secretary, I.P.R.E., 32 Kidmore Rd., Caversham, Reading, Berks.

**PIN-POINT TV TROUBLES IN TEN MINUTES.** The title can be imitated but the contents never! The book that really tells you how to fix televisions. Over 340 cross-indexed pages. MUST be able to earn you more than its cost within two weeks or your money refunded. Price 33/- incl. postage. Write for free trial to **SIM-TECH BOOKS**, West End, Southampton, Hants.

**METAL WORK**

**METALWORK.** All types cabinets, chassis, racks, etc. to your specifications. **PHILPOIT'S METALWORKS LTD.**, Chapman St., Loughborough.

**SITUATIONS VACANT**

**CITY AND GUILDS** (Electrical, etc.) on "no pass—no fee" terms. Over 95% successes. For details of Electrical Engineering, Applied Electronics, Automation, etc., send for our 148-page handbook, free and post free. **B.I.E.T.** (Dept. 242A), 29 Wright's Lane, London W8.

**PUBLIC SCHOOL** leaver required as an Electronic and/or Electro-Mechanical Trainee to assist in the design and construction of industrial controls for use in the manufacture of glass fibre products. Starting salary £728. Write giving details of education and interests to Fibrelite Industries, Trafford Hall, Chester.

**A.M.I.Mech.E., A.M.Brit.I.R.E.,** City and Guilds, G.O.E., etc., brings high pay and security. "No pass—no pay" terms. Over 95% successes. For details of exams and courses in all branches of Engineering, Building, Electronics, etc., write for 148-page handbook, free. **B.I.E.T.** (Dept. 242B), 29 Wright's Lane, London W8.

**RADIO TECHNICIANS** required for Ocean Weather Ships with a sound knowledge of at least three of the following types of equipment: Single Side-band Transmitter, Radar Navigational Radar Height-Finding Echo Sounders and Radio Receivers, Automatic DF v.h.f. and MF, Low Voltage Servo Recorders, Digital Telemetering Equipment. Salary scale £636-1,036 per annum plus £120 per annum overtime allowance. Free food and accommodation provided on board ship. Applicants must be natural born British subjects. Full details from Shore Captain, Ocean Weather Ship Base, Great Harbour, Greenock. Tel.: Greenock 24291.

**TV AND RADIO.** **A.M.Brit.I.R.E.,** City and Guilds, R.T.E.B. Cert., etc., on "no pass—no fee" terms. Over 95% successes. For details of exams and courses (including practical apparatus) in all branches of Radio, TV and Electronics write for 148-page handbook, free. **B.I.E.T.** (Dept. 242G), 29 Wright's Lane, London W8.

**MISCELLANEOUS**

Cases, Chassis, Frames, etc., anything in metal. Send your drawing for quotation. 'One off's' with pleasure.

Stove enamelled any professional finish. Steel Shelving, Drawer Units, etc.

**Moss Watson**

40 MOUNT PLEASANT STREET  
OLDHAM, LANCs. MAIN 9400

**ELECTRONIC MUSIC?**

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes! It has 5 octaves, 2 manuals and pedals with 24 stops—uses 4 valves. With its variable attack you can play Classics and Swing.  
**Write NOW** for free leaflet and further details to **C. & B.**, 20 Maudslayi Street, Darlington, Durham. Send 2d. Stamp.

**SOUND RECORDINGS**

**A UNIQUE BUY!** Recording tape top brand 5in. 1,200ft 19/6; 7in. 2,400ft 13/6 28/6. P. and p. 1/6 per spool. Bargains in all sizes. **S.A.E.** for list. **E. C. KINGSLEY AND CO.**, 132 Tottenham Court Road, London W1. EUSTON 6500.

**A.R.R.L. RADIO AMATEURS HANDBOOK 1963**

New edition 38/-. Postage 2/3.  
**The Amateur Radio Handbook**, by R.S.G.B., 34/-, postage 2/3.  
**British Semiconductor Survey**, by Sinclair 15/-, postage 1/-.  
**Hi-Fi Year Book 1963**, new edition, 10/6, postage 1/-.  
**Radio and Line Transmission, Vol. 1**, by Danielson, 21/-, postage 1/3.  
**More about Loudspeakers**, by Briggs, 8/6, postage 1/-.  
**British Transistor Directory**, by Bradley, 8/6, postage 9d.  
**Radio Control for Models**, new edition by Judd, 15/-, postage 1/-.  
**The Oculostope Book**, by Bradley, 5/-, postage 6d.

**UNIVERSAL BOOK CO.**

12 Little Newport Street, London, W.C.2 (adjoining Lisie Street)

**D. & B. TELEVISION (Wimbledon) LIMITED**

131 & 131a, Kingston Road, South Wimbledon, London, S.W.19

Phone: CHERrywood 3955  
OPEN  
Monday to Saturday, 10 a.m. to 7 p.m. (Except Wednesday, 1 p.m.)

Nearest Tube: South Wimbledon (Northern Line)

**COMPARE OUR PRICES**  
For the Finest in the Country  
YOUR PROBLEMS ARE OUR BUSINESS  
MOST LINE-OUTPUT TRANSFORMERS IN STOCK

Surplus or Ex-Equipment Valves  
Guaranteed 3 Months, New Low Prices

EB91	2/6	PCL82	5/-	UAF1	17/6
EF80	5/6	PCL83	5/6	UBA42	5/6
ECC81	4/-	PCL84	7/-	UBC41	5/6
ECC82	4/-	PL33	7/6	UCB84	8/6
ECC83	4/6	PL36	7/6	UCF80	8/6
ECL80	4/6	PL38	12/-	UF42	3/-
ECL82	6/6	PL81	6/6	6F1	3/6
EF80	2/6	PL82	5/-	6F12	2/6
EF85	5/-	PL83	5/6	6F13	5/6
EF91	2/-	PL84	5/-	6F15	5/6
EL33	5/6	PY31	7/-	6L1	7/6
EL84	5/-	PY32	8/-	6L18	6/6
EY51	3/6	PY80	4/-	6P25	8/6
EY86	5/-	PY81	4/-	6P28	8/6
EZ80	4/6	PY82	4/-	10F1	3/6
EZ81	5/-	PY83	6/6	10P13	7/-
GZ32	5/6	PZ30	7/6	10P14	6/9
GZ34	8/-			20D1	5/6
KT33c	4/-	U24	8/-	20F2	6/6
KT36	8/-	U25	7/6	20L1	9/9
KT61	6/9	U26	6/6	20P1	7/6
KT63	5/-	U31	7/-	20P3	8/-
PCB84	5/-	U52	4/6	20P4	12/6
PCF80	5/-	U191	7/9	20P5	8/-
PCF86	7/-	U301	10/-	30P4	7/6

We pride ourselves that we can obtain and supply any TV spare. Please ask us for ANY components you may require we are almost certain to have them.

TERMS: S.A.E. all inquiries. C.W.O. C.O.D. 5/- extra. Postage on Valves 6d. each. C.R.T.s 12/6 inc. Insurance.

Satisfaction assured. Return Post Service

**ULTRA VIOLET BULBS**

Easy to use source of UV for dozens of practical and experimental uses.  
12 volt 36 watt AC/DC SBC 0/6. P. & P. 1/-  
12 volt 60 watt AC/DC SBC 8/6. P. & P. 1/-  
Trans former to suit the above: Input 200-240 A.C. Output 12 Vol. A.C. 36 watt, 18/6. P. & P. 2/6. Input 200-240 A.C. 12 volt A.C. 66 watt, 22/6. P. & P. 3/6.

Set of 4 colours **FLUORESCENT PAINT**, Red, Orange, Green and Blue in 1 oz. tins. Ideal for use with the above Ultra Violet Bulbs, 9/6. P. & P. 1/6.

**BUILD AN EFFICIENT STROBE UNIT FOR ONLY 37/6**

The ideal instrument for workshop, lab. or factory. This wonderful device enables you to "freeze" motion and examine moving parts as stationary. We supply a simple circuit diagram and 11 electrical parts including the NSF7 Strobe tube which will enable you to easily and quickly construct a unit for infinite variety of speeds, from 1 flash in several seconds to several thousands per minute. New modified circuits bring price down to 37/6 plus 3/- P. & P.  
**NSP2 (V236 STROBOTHON FLASH-TUBE)** made by Ferranti, brand new, I.O. base. Price 15/- P. & P. 1/-.

**MAGNETIC COUNTERS 10 IMPULSES PER SECOND**

Very latest High Speed type ex. P.O. guaranteed perfect, type No. 10CB, coil 2,300 ohms, for 48 volt D.C. operation (will work on 26 volt), overall size 4 x 1 x 1 in. Also available, type 10A which can be used as an interesting accessory with our Strobe unit. Either type price 15/- P. & P. 1/6.



**Variable Voltage Transformer**

Input 230 v. A.C. Output 0-280 v. at 2.5 amp. Fully shrouded. New, £5.19.6. inc. carriage. Also available 1rm. storage, 6, 8, 10 and 20 amp. Write for details.

4,000 Ohm Headphones, brand new (imported). 12/6 each pair. P. & P. 1/6.  
**SIEMENS H.S. RELAY.** Very latest type sealed. H96E, 1,700 ohms plus 1,700 ohms, single C/O contacts. Price 16/6 each, plus 1/- P. & P.

**VOLT 40 A.H. ACCUMULATOR**, in metal case with leather carrying handle. New. Price 27/6, carriage 8/-.

**500 MICROAMP SUB-MINIATURE M/M METER.** 1 1/4 in. diameter, flush mounting, single hole fixing. Scaled 0-1 mA. Supplied with resistor for use as IMA if required 9/6 plus 1/- P. & P.

**230 VOLT A.C. GEARED MOTORS**  
Type B16G 90 r.p.m., 26 lb. inch, £1.18.6. P.P. 2/-.  
Type D16G 6 r.p.m., 1.7 lb. inch, £2.9.6. P.P. 2/6.  
Type D16G, 13 r.p.m., 1.4 lb. inch, £2.12.6. P.P. 2/6.

**LIGHT SENSITIVE SWITCH.** Complete kit of parts, including ORP-12 Cadmium Sulphide Photo-Relay, Transistor and Circuit, etc. price 25/- plus 2/6 P. & P. Additional ORP-12, 8/6 each plus 1/- P. & P. (Reset not supplied separately).

**AVO METER MODEL 7.** Individually tested on all ranges and guaranteed. Inclusive of Test Leads, £11.0.0 each. P. & P. 5/-, Case 20/-

**MINIATURE LEAD ACID ACCUMULATORS.** (Brand New). 2V, 1.5 A.H. Size 4 x 1 x 1 1/2 in. Wt. approx. 1 lb, 16/6 for 3 P. & P. 1/6. 12V, 0.75 A.H. Size 4 x 3 x 1 1/2 in. Wt. approx. 2 lb. (can be used as double 6V 15/6 each. P. & P. 1/6).

**TRANSISTORS**

OC30	10/-	OC75	7/-	Get 114	5/-	
OC41	7/-	OC78	6/-	Get 573	12/6	
OC45	8/-	OC77	9/-	Get 573	25/-	
OC45	9/-	OC139	12/-	M/Pair		
		OC170	9/6	1N155A	4/-	
OC71	5/-	OC171	10/6	2N458	20/-	
OC72	7/-	OC200	10/6	2S005	30/-	
OC73	14/-	OC201	21/-	2S013	100/-	
		Q	104	6/-	SB945	7/6
OC73	6/-	Get 105	10/-	TK20B	4/-	

**SERVICE TRADING CO.**

All Mail Orders also callers.  
47-49 High Street, Kingston on Thamer  
Tel: KINGSTON 9460

Personal callers only  
9 Little Newport Street, London W.C.2 (off Leicester Square)  
Tel: GERrard 0876.



## VALVES — SUMMER SEASON PRICES

DAF96	7/-	EFC80	10/-	EL41	8/-	PL36	12/6
DF96	7/-	ECH42	8/-	EL84	7/6	PL81	9/6
DL96	7/-	ECH81	8/-	EY51	8/-	PL82	7/6
EBC33	5/6	ECL80	8/-	PCC84	7/6	PY32	12/6
ECC81	5/6	ECL82	8/6	PCF80	7/6	PY81	7/6
ECC82	5/6	EF80	6/-	PCL82	10/-	U25	10/-
ECC83	6/-	EF86	10/-	PCL83	10/6	UCL83	10/-

## CHASSIS

Aluminium Undrilled with Reinforced Corner, available in the following sizes:

6in. x 4in. x 2½in. ...	4/6 each
8in. x 6in. x 2½in. ...	6/3 each
10in. x 7in. x 2½in. ...	7/3 each
12in. x 3in. x 2½in. ...	5/9 each
12in. x 5in. x 2½in. ...	6/9 each
12in. x 8in. x 2½in. ...	8/6 each
14in. x 3in. x 2½in. ...	6/- each
14in. x 9in. x 2½in. ...	12/- each
16in. x 6in. x 2½in. ...	9/3 each
16in. x 10in. x 2½in. ...	14/- each

All are four-sided—ideal for radio receivers, amplifiers, power packs, etc.

## MTP 3, E.K.E. 9 V. POWER UNIT

A 9 V. power supply unit to operate any transistor equipment from A.C. mains 235/245 V. 50 a.p.s. Specification: Full wave bridge, contact cooled rectifier; Zener stabilised and transistor regulated D.C. output. Less than 2 V. variation from no load to 30 mA. consumption. Fully safeguarded against all accidental shorts or overloads, with no fuses to replace. Maximum continuous rating 50 mA. at 50 deg. C. ambient. Nylon bobbin, impregnated transformer. The whole mounted on plated sub-chassis with 2 fixing holes. Size: 4 x 2 x 3in. 45/- ea.

**TERMS:** Cash with Order or C.O.D. Postage and Packing Charges extra. Single valves 9d., Minimum Parcel Post charges 2/-.

Please include sufficient postage with your order. Minimum C.O.D. fee and postage 3/6.

**ALPHA RADIO SUPPLY CO., 103 Leeds Terrace, Wintoun Street, LEEDS 7**

**AMATEUR RADIO**  
**CHAS. H. YOUNG LTD.**

Come and See Our  
**NEW SUPER STORE**

The Finest in the  
**MIDLANDS**

All the usual lines  
& **MANY NEW ONES**

Eddystone, Armstrong,  
Quad, Leak, etc.  
**Ex Stock.**

**170-172 CORPORATION ST.**  
**BIRMINGHAM 4**

Telephone as before: **CEN 1635**

## REPANCO

**TRANSFORMERS FOR 10 WATT  
TRANSISTOR AMPLIFIERS**

TT23 Interstage Transformer **22/6** (P.P. 1/6)

TT24 Output Transformer **22/6** (P.P. 1/6)

Send 3d. stamp for latest catalogue of REPANCO components  
Mail order and trade:

**Radio Experimental Products Ltd.**  
33 Much Park St., Coventry

Wholesale and Export:

**REPANCO Ltd.**  
O'Briens Buildings, 203-269 Foleshill Road  
Coventry.

Now in a new 3rd edition . . .

## A BEGINNER'S GUIDE TO TELEVISION

The modern miracle of television is here explained in a series of seventeen lessons. Written in non-technical language which the veriest beginner can understand, the reader is taken by easy stages through every aspect of TV transmission and reception. A further lesson has been added on the conversion of 405 to 625 line pictures. It is a companion volume to the "Beginner's Guide to Radio", a best seller which has already sold over 75,000 copies.

Only 8s. 6d. from all booksellers

... or, in case of difficulty, 9s. 6d. by post from George Newnes Ltd.,  
Tower House, Southampton St., London, W.C.2.

**NEWNES**

# READY BUILT - READY TO GO

Listen in comfort to your favourite programmes, without annoying others with the "PORTO-BELLO"


Our Personal Transistor Pocket Radio designed exclusively for personal use.

Works anywhere, any time—our special circuit with built-in ferrite rod aerial ensures wonderful reception over the full medium wave band, B.B.C. Home, Light, Luxembourg and many Continental stations. Completely portable, compact size, only 2 1/2 x 3 1/2 in., slips into pocket. NO EXTERNAL AERIAL OR BATTERY REQUIRED. Condenser tuning and with "exclusive" separate fine tuning control for "spot on" station selection. Complete station separation makes this ideal for use as Tape Jack for recording or turner unit for amplifier.



37/6 P.P.2-

Earpiece 5/- extra. Battery 2/6 extra.

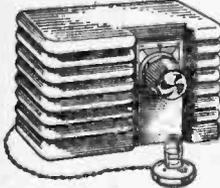

## COMMANDER IV CRYSTAL SET

Covers the full medium wave band and is ideal for use in Bedroom, etc. Requires NO batteries—works for ever. Operates with miniature personal earpiece. Attractive case and dial—a Radio set in miniature.

PRICE 10/- P. & P. 2/-

Earpiece 5/- extra. Both fully guaranteed.

*Transradio*

11, OLIVER ROAD, LONDON, E.17

## EXPRESS ELECTRONICS

32 SOUTH END CROYDON SURREY TEL. CRO. 9186

VALVES NEW TESTED AND GUARANTEED FOR THREE MONTHS

1C1	7/8	6BE6	7/-	12AU7	6/9	6D7	7/6	EF80	6/-	PL82	7/-
1C2	7/6	6BH6	5/9	12AX7	6/8	6D7	7/6	EF91	4/-	PL83	7/9
1C3	8/-	6BJ6	5/8	12BE6	6/8	6D7	7/6	EF92	6/8	PY91	6/9
1F1	8/-	6BK7	8/9	12BH7	10/6	6D110	10/-	E141	9/8	PY92	7/6
1F3	7/6	6BW6	6/6	12K8GT11	DK91	7/6	EL24	7/-	PY93	7/8	
1FD1	8/-	6BW7	7/-	12Q1GT	7/8	DK96	8/-	EM84	10/-	R19	10/3
1FD9	7/6	6D12	4/-	12SN7	6/-	DL92	5/8	EM85	10/-	36A1	9/8
1F11	8/1	6F12	7/-	16A3	9/-	DL94	6/1	EL31	7/8	U52	7/6
1P10	7/6	6H8GT	2/-	18AQ5	5/8	DL96	8/-	EY81	10/1	U76	7/6
1P11	7/6	6J7GT	7/8	28A60	7/6	EB91	4/-	EZ40	7/1	U78	6/-
1L5	6/-	6K7Q	5/8	25L6GT	7/8	EBC41	10/-	EZ80	6/-	U142	7/8
1L5	6/-	6K8Q	6/-	25Z4G	9/-	EBF80	8/8	EZ81	6/9	UBC41	8/8
1T4	5/8	6Q7G	5/8	30C1	7/8	EUC81	6/-	HVR2	9/8	UCH42	8/6
1U5	5/8	6SL7GT	6/-	30L1	7/8	EUC82	6/9	NTS8C	6/-	UY41	8/6
3Q4	8/-	68N7GT	6/-	35L1GT	7/8	ECC83	6/8	N17	5/9	UY41	8/6
384	6/9	6V6G	7/8	35V4	8/6	ECC84	7/8	N18	8/-	UY41	7/8
3V4	6/8	6X4	5/-	35Z4GT	8/-	ECC80	8/8	N19	7/6	W17	7/6
4V3GT	5/-	6X5G	5/9	37G3	7/8	ECC85	8/-	N709	7/-	W78	4/8
5Z4G	7/8	747	9/8	6W	6/8	ECH42	9/-	PCC84	7/6	W142	8/8
6AK6	6/8	6D3	4/-	DAF91	7/8	ECH81	10/-	PCF80	7/6	X17	7/8
6AL5	4/-	9D7	9/8	DAF96	8/-	ECL80	8/6	PCF82	7/8	X142	9/-
6AM6	4/-	12AD6	11/8	DCC90	12/6	ECL82	8/-	PCL82	8/-	X150	9/-
6AT5	6/-	12A78	10/4	D91	11/8	EF41	9/-	PCL84	9/-	X77	4/-
6BA8	5/-	12AT7	6/-	DF96	8/-	EF80	8/-	PL81	12/6	ZD17	7/8

ASK FOR RESISTOR AND CAPACITOR COLOUR CODE. FREE WITH EVERY PURCHASE

High Stability Resistors 1W 5% 50 Ω to 1M, 9d. Midget Ceramics 500 v. 9d. Cond. Super quality 1in. 6d. 7d. Plugs 9d. Sockets 9d. Silicon H.T. Rects. 250v. 300 MA 4in. 4in. 9/6. Contact Gooled 850v. 50 MA 6/6. 35 MA 6/6. NEW TRANSISTORS BY MULLARD. OC19. OC26. OC68. OC69. 25/- OC44. OC43. 9/-; OC70. OC71. 6/-; OC72. 7/6; OC72 matched in pra. 16/-; OC74. OC75. OC78. OC81. 7/8; OC82. OC170. 9/6.

### VALVES MATCHED IN PAIRS

EL34 27/8, EL84 15/-, N709 15/-, 6V6G 15/-, 6BW6 14/- per pair. Push Pull P.P. Transformer for above 3 15 Ω 14/6. P. & P. 1/6. 12in. P.M. Speakers 3 Ω 24/6. Baker's "Bethurst" 12in. 15 Ω 15W, 80/- 12in. Stereo Model 86.15.0.

### SETS OF VALVES

DK91, DP91, DAF91, DL92 or DL94. 19/6  
 DK96, DP96, DAF96, DL96..... 27/8  
 1C3, 1F1, 1FD1, 1P1..... 27/8  
 1E5, 1T4, 1E5, 384, or 3V4..... 19/6  
 Postage and packing 6d. Over 61 post free. C.O.D. 4/-.

# TECHNICAL TRAINING in radio television and electronics

Whether you plan to have your own business, to become an electronics engineer, to take up a career in industry, or to brush-up your knowledge and study new developments, transistors, etc., an I.C.S. Course will help you to success. You learn at home in your own time, under expert tuition. Moderate fees include all books.

## EXAMINATION COURSES FOR:-

- C. & G. Radio and TV Servicing Certificate (R.T.E.B.)
- C. & G. Radio Amateurs' Exam. (Amateurs' Transmitting Licence)
- P.M.G. Certificates in Radiotelegraphy

British Institution of Radio Engineers, C. & G. Telecom. Technician's Cert. Gen. Cert. of Education etc.

## LEARN AS YOU BUILD

### Practical Radio Servicing Course



A basic course in radio electronic and electrical theory backed by thorough practical training. You build radio receivers, signal generators and multimeter.

Post this Coupon TODAY! for FREE book on careers in Radio, and full details of other I.C.S. Courses Member of the Association of British Correspondence Colleges

### INTERNATIONAL CORRESPONDENCE SCHOOLS

(Dept. 171), Intertext House, Parkgate Road, London, S.W.11.

Please send book on \_\_\_\_\_

Name \_\_\_\_\_ Age \_\_\_\_\_

(Block Letters Please)

Address \_\_\_\_\_

Occupation \_\_\_\_\_ 8.63

## INTERNATIONAL CORRESPONDENCE SCHOOLS

**COMMUNICATION RECEIVERS**

**CR100/8MOD.** Covers 60 kc/s-30 Mc/s in 6 bands. 11 valves. 2 R.F., and 3 I.F. stages. Crystal gate. B.F.O., etc. Ready for 200/250 volt a.c. mains. 2 watts output for 8 Ω speaker. BRAND NEW in original packing. £35, carr. £2. S.A.E. for illustrated details.

**HRO SENIOR RECEIVERS.** Complete with 9 coils, £17.10.0. S.A.E. for full details.

**PCR-3 RECEIVERS.** 3-wave bands, medium wave and 2 short wave, from 120-13 metres. Good condition, tested, 8 gns. Carr. 10/- . A.C. mains internal power supply £2 extra.

**SILICON RECTIFIERS.** Type 1EA2 (4 x 1in.) will handle 250 volts at up to 500mA. Replaces any TV metal rectifier. 7/6.

**MOVING COIL PHONES.** Finest quality Canadian with Chamolite ear muffs and leather-covered headband. With lead and jack plug. Noise excluding, supremely comfortable. BRAND NEW ..... 22/6, post 1/6.

**AVOL C & R BRIDGE.** Capacity 5 pF to 50 mF. Resistance 5 Ω to 50 Ω. Inductance can be measured against external standard. Balance is indicated on a meter which can be used as a valve voltmeter from 0.1 to 15 v. Leakage test and Power Factor scale. A.C. mains operation. Tested and guaranteed and in superlative condition. £9.10.0, plus 7/6 & P.

**AVO WIDE RANGE SIGNAL GENERATORS.** Six turret operated range covering 50 Kc/s to 80 Mc/s. For use on standard A.C. mains. Packed in original transit cases with accessories. Post-war type in new condition. £15. Carriage 10/- . REAL BARGAIN.

**AR-88 SPARE VALVES.** Complete set of BRAND NEW individually boxed original valves (14). 50/- . P. & P. 2/6.

**RCA AR-88 SPEAKERS.** 3 Ω 8in. P.M. speaker in heavy gauge black cracked steel cabinet 11 x 10 x 6in., with rubber feet. A SUPER QUALITY unit. BRAND NEW, for ONLY 65/- . P. & P. 5/-.

**AR-88 VIBRATOR PACKS.** For 6 v. operation. Complete with vibrator and OZ4 rectifier. BRAND NEW in original cartons. 17/6. P. & P. 5/-.

**AERIAL KITS.** Comprising seven 4ft. aerial rods making a 16ft. and a 12ft. aerial. There is also an aerial base with a ground spike. All in a steel carrying tube with web strap. 22/6, carr. 4/-.

**MULTIMETER SPECIAL. MODEL CT-500.** 20,000 Ω/v. DC volts: 0 to 2.5-10-50-250-500-5,000 (20K Ω/v). AC volts: 0 to 10-50-250-500-1,000 (10K Ω/v). DC Current: 0 to 50 μA, 5 mA, 50mA, 500mA. RESISTANCE: 0 to 12K Ω, 120K Ω, 1.2M Ω, 12M Ω. Mid scale 60, 600, 6K, 60K ohms. Decimals .20 to +62. In neat moulded case 5 1/2 x 4 1/2 x 1 1/2in., with leather carrying handle, complete with batteries, leads and instructions. BRAND NEW. Fully guaranteed. 95/- . P. & P. 2/6.

CHARLES BRITAIN (RADIO) LTD.

11 UPPER SAINT MARTINS LANE, LONDON, W.C.2  
 Temple Bar 0545 Shop Hours 9-6 p.m. (9-1 p.m. Thursday).  
 Open all day Saturday.

Stamp for FREE LIST DUKE & CO. (LONDON) LTD. 621/3 Romford Road, Manor Park, E.12 Liverpool St.—Manor Pk.—10 mins. Phone ILFord 6001/2/3



**SPEAKERS 7/9 EACH**  
 P.P. 2/3.

6in. 8in. 7in. x 4in. Money back guaranteed. Enquire for other sizes. Ex. mid. salvage.

**TAPE CABINETS 20/-**  
 To fit B.S.R. and Collaro Studio Decks. Carriage 5/-.

**Condensers. 100, 10/-, New.** Assorted electrolytics & Pfs.

**Resistances. 100—5/-.** Assorted sizes, watts, grades.

**Variable Pots. 40, 10/-, New.** TV or Radio. Assorted P.P. 2/6.

**TELEPHONE HANDSETS 15/6** per pair. P.&P. 4/6. G.P.O. standard pattern. House to Workshop, garage, inter-office, etc. Works off any small battery.

**Reguned TV TUBES** 21in., 99/6 17in., 79/6 15, 14, 12in., 59/6

**Guaranteed One Year** Ins. and Carr., 10/- . Add 10% refundable on OLD TUBE. 110° Tubes in Stock.

**Ex-Rentals** 121, 31/74, 36/24, 141, 14KP4 and others. Set tested. Carr. 5/-.

**15/-**

**VALVES 9d. Each** 1000's available. Most types. Post & Packing 1d. each. Minimum 6d.

**COMPLETE**

14 INCH £7.10.0

100% Guaranteed.

12 months' Full Written Guarantee.

Shown working all channels in Shop.



**TELEVISIONS**

17 INCH £11.10.0

Legs—39/6 per set

Part exchange allowance on ANYTHING USEFUL

Personal collection advised, or insured Carr. 14in. 20/-, 17in. 30/-.

**VALVES SAME DAY SERVICE**  
 NEW! TESTED! GUARANTEED!

**SETS** 1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL94 .. Set of 4 for 17/- DAF96, DF96, DK96, DL96 .. 4 for 25/6

1A7GT 9/-	6SN7GT 4/9	18B5T 19/6	ECC84 7/8	KT81 7/6	U78 4/3
1D5 7/6	6U4CT 9/6	AC/CTH1 18/6	ECC85 7/8	MT14 8/1	U91 11/1
1B5GT 8/6	6V6G 3/11	AZ1 12/6	ECC86 7/8	MX40 13/6	U981 9/6
1N5GT 8/9	6V6GT 6/6	CB1 12/-	ECC87 7/9	N18 7/-	U282 14/6
1R5 5/-	6X4 4/3	CCH35 13/6	ECH35 6/6	N37 10/-	U291 11/-
184 7/6	6X5GT 8/9	CL33 9/6	ECH42 8/3	PC85 9/6	U301 12/9
1T5 4/6	6Y0L2 8/6	CY1 12/6	ECH81 6/9	PC92 9/8	U31 18/-
1T4 3/-	7B7 8/6	CY31 5/8	ECL30 9/3	PC84 8/8	UABC80 5/9
3A5 6/9	7C5 7/9	DAC32 8/6	ECL82 7/9	PCC85 7/6	UAF42 9/-
3Q4 5/9	7C6 7/6	DAF91 4/-	ECL86 9/-	PCC89 8/6	UBC41 6/11
3S4 5/-	7H7 5/9	DAF96 6/6	EF37A 6/-	PCP80 6/3	UBF80 7/6
3V4 5/9	7S7 9/6	DCO30 6/9	EF39 3/9	PCP82 8/3	UBP89 7/3
6U4G 4/6	7Y4 6/-	DF33 8/9	EF40 11/9	PCP86 8/6	UBL21 13/6
6V4G 8/-	10C1 9/6	DF91 3/-	EF41 7/3	PCL82 7/3	UC82 7/6
5Y3GT 5/-	10C2 13/-	DF96 6/6	EF42 6/3	PCL83 9/-	UCC84 11/3
5Z4G 8/9	10LD11 10/9	DH76 4/3	EF80 4/3	PCPL84 5/9	UCC85 6/8
6AL5 2/6	12AT7 4/9	DH77 4/6	EF85 5/6	PCL85 8/6	UCR90 10/9
6AM6 3/3	12AT7 4/9	DK32 9/6	EF98 6/9	PEN44 11/6	UCH21 13/6
6AQ5 6/-	12AU7 4/9	DK91 5/-	EF99 5/-	PEN36C 8/3	UCH42 7/6
6AT6 4/9	12AX7 4/9	EK92 6/9	EF91 3/3	PL36 9/3	UCH81 7/6
6BA6 5/3	12K7GT 4/3	EK96 3/6	EF92 2/6	PL81 7/9	UCL82 8/9
6BE6 5/3	12K9GT 9/6	EL37 7/6	EF184 8/9	PL82 5/9	UCL83 10/9
6BR6G 13/6	12Q7GT 4/3	EL35 9/6	EL33 7/6	PL83 5/9	UF41 7/3
6BB6 5/9	12Z3 8/6	DL92 5/-	EL41 7/9	PL84 7/6	UF89 6/3
8E36 5/6	1487 14/6	DL94 5/9	EL42 8/6	PX4 9/6	UL41 7/9
8CD9G 26/6	19SG6G 13/6	EL96 6/6	EL34 6/-	PX25 8/3	UL44 10/6
6F1 9/6	20P4 15/11	EACB30 8/-	EM34 7/3	PY32 9/3	UL46 9/6
6F14 9/6	20P5 14/9	EB91 2/6	EM80 7/3	PY33 10/3	UL84 6/3
6K7G 1/11	25L6GT 6/-	EBC33 5/-	EM81 8/6	PY80 6/-	URIC 7/3
6K7GT 4/3	27S4 17/6	EBC37 7/3	EM84 8/3	PY81 6/6	UU7 9/6
6K8G 4/3	30L15 10/3	EBF80 7/3	EM93 9/3	PY92 6/6	UL44 11/-
6K8GT 7/9	30P19 13/-	EBF89 7/6	EY51 6/6	PY83 6/6	UY41 5/9
6L6G 6/6	30PL13 11/-	EBL21 13/6	EY85 6/6	R16 17/6	UY85 5/9
6L19 10/-	35A5 14/-	EEL31 17/-	EZ40 7/6	TH21C 15/-	VP4B 9/6
6LD20 5/6	35L6GT 7/9	ECC40 8/6	EZ41 7/6	U2 15/-	VP41 5/-
6P25 8/6	38L6GT 4/11	ECC81 4/3	EZ80 5/6	U26 8/3	W76 4/6
6O7G 4/9	50L24GT 7/9	ECC82 4/9	EZ81 5/-	U47 9/9	W77 2/6
6O7GT 7/9	50L24GT 4/11	ECC83 4/9	GZ32 8/6	U50 4/6	W729 14/-
6SL7GT 5/9	58L6GT 7/-	ECC84 7/3	KT72 6/6	U52 4/3	Z77 3/3

**UNDERSTANDING AMATEUR RADIO PRINCIPLES-CONSTRUCTION OPERATION**

A New A.R.R.L. Publication

18/- Postage 1/3

**SEMICONDUCTOR CIRCUIT DESIGN**, by R. V. Leedham. 7/6. Postage 1/-.

**HI-FI YEAR BOOK 1963 Edn.** 10/6. Postage 1/-.

**LEARN ELECTRONICS BY BUILDING EASY-TO-BUILD PROJECTS**, by J. Schroeder. 27/- . Postage 1/-.

**BASIC TRANSISTOR COURSE**, by P. R. Kenian. 30/- . Postage 1/-.

**ELECTRONIC ORGAN HANDBOOK 1963 Edn.**, by A.R.R.L. 36/- . Postage 2/6.

**RADIO VALVE DATA**, compiled by Wireless World. 6/- . Postage 10d.

**COMPLETE CATALOGUE** 1/-

**THE MODERN BOOK CO.**

BRITAIN'S LARGEST STOCKISTS of British and American Technical Books

19-21 PRÆD STREET LONDON, W.2

Phone: PADDington 4185

Open 6 days 9-6 p.m.

**READERS RADIO**


24 COLBERG PLACE, STAMFORD HILL LONDON N.16 STA. 4587

Post 6d. per valve extra. Any Parcel Insured Against Damage in Transit 6d. extra. Any C.O.D. Parcel 4/3 extra.

**LOOK AT OUR NEW PRICES! BUILD IT - TODAY!**

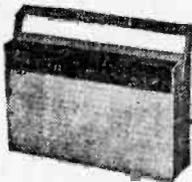**THE COROVER '6'**


This superhet receiver uses the very latest circuitry, 6 transistors and two diodes and is fully tunable over both medium and long wavebands. First stages uses three Mullard AF117 alloy diffused transistors with OC81D and two OC81's in push-pull. I.F. frequency 470 Kc/s. Large internal ferrite rod aerial gives excellent reception over all ranges. 3 inch high flux speaker has a maximum output of 30mW. Operates on four 1.5 v. pen torch batteries. All components are mounted on a single printed circuit board. Attractive plastic case with carrying handle—fitted sockets for personal earpieces, tape recorder and car aerial. Size 6½ x 4 x 1½ in.



**MAY BE BUILT FOR £5.7.6** All parts sold separately.  
P. & P. 4/- extra. (Data and instructions 2/6, free if all parts bought.)

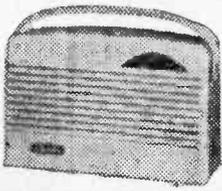**THE 'REALISTIC 7'**

A fully transistorised Portable Receiver made to the highest professional standards—is now available to the home constructor. Comprises 7 Mullard Trans. OC44, 2 OC45's, OC71, OC81D, and 2 OC81's plus OA70 Crystal Diode. Delivers 350 milliwatt output to 4in. high flux speaker—I.F. frequency 470 Kc/s.—fully tunable over medium and long wavebands. All components mounted on single printed circuit board, size 6½ x 6½ in. Attractive two-tone plastic cabinet with carrying handle—size 7 x 10 x 3½ in. with easy to read dial and socket for car aerial, choice of Red/Grey, Blue/Grey or all Grey. Complete with full instructions. All parts sold separately.



**WIRECOMP'S PRICE ONLY £5.19.6** Battery 3/9 extra.  
P. & P. 4/6 extra. (Circuit diagram 2/6, free if all parts bought.)

**The SPRITE**



A unique Wirecomp offer. The Sprite is a six transistor superhet Miniature Pocket Radio of Commercial Quality—offered to you in three main pre-assembled units—which together with simple wiring—enable you to build it in only one hour!

Fully tunable over Long and Medium wavebands. Uses printed circuit and High sensitivity internal ferrite rod aerial. I.F. frequency 470 Kc/s. Transistors: 3 Philco 2067's, 2 Mullard OC81M's, OC81DM and OA90 diode. 3 inch speaker. Works on single PP3 battery. Supplied with the complete R.F. and I.F. stages. Driver and Output stages, ready built and mounted on the printed circuit; for final assembly you only have to fit the wave-change switch, tuning condenser and drive, volume control, earphone socket and aerial rod. In very attractive plastic case, size 4 x 2½ x 1½ in. All parts sold separately.

**WIRECOMP'S BARGAIN PRICE 79/6**

Real Calf Leather Case, wrist strap and Personal Earphone with case and Battery, 12/6 extra.

P. & P. 3/6 extra. (Data and instructions 2/6, free if all parts bought.)

**WIRECOMP ELECTRONICS**  
378 HARROW ROAD, LONDON, W9.

TEL: CUNNINGHAM 9530

Hours of business: 9 a.m. to 6 p.m. Open all day Saturday. Opposite Paddington General Hospital. Buses 181 and 36 pass the door.

Announcing the opening of

**BERWICK ELECTRONICS LTD**

The newest and most exciting COMPONENT SHOPS

For the service man, enthusiast, novice or experienced old hand there is always something new at Berwick!

NO LISTS READY YET BUT WE ARE READY AND OPEN FOR CUSTOMERS. MAKE A POINT OF VISITING BERWICK ELECTRONICS

Everything electronic from Car Aerials to Signal Generators—from Amplifiers to Rectifiers—Tygan, Aluminium Chassis, Mains transformers, Test meters, F.H.P. Motors & literally thousands of small components.

Hours: 9 a.m. to 6 p.m. (Sat. to 1 p.m.)


**BERWICK ELECTRONICS LTD**

70 BERWICK STREET, LONDON, W.1

Telephone GERrard 8152

and 100 TIB STREET, MANCHESTER

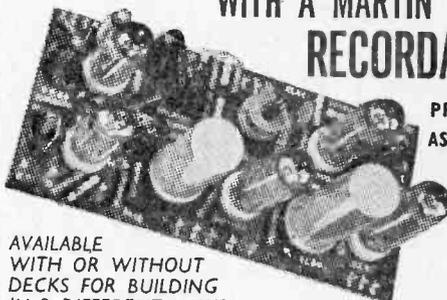**ADD TAPE TO YOUR HI-FI WITH A MARTIN RECORDAKIT**



PRE-AMP ASSEMBLY

AVAILABLE WITH OR WITHOUT DECKS FOR BUILDING IN 3 DIFFERENT WAYS

MARTIN RECORDAKIT PRE-AMP ASSEMBLIES are available for 2 or 4 track use with Collaro Studio Deck or B.S.R. Monardeck. Amplifying portions are supplied assembled with valves on printed circuit boards. Kits may be bought for pre-amp alone, with deck for mounting into existing cabinet, or with deck and modern polished wood cabinet. Whichever way suits you, these Recordakits provide a wonderful way to add tape to existing installations for very little expense, and give wonderful quality.

Money Saving too!

- 2 Track Pre-Amp Kit alone 8 gns
- 4 Track Pre-Amp Kit alone 9 gns
- Kit with polished wood Cabinet and Deck from 17 gns

**MARTIN RECORDAKITS**

From Radio Stockists or direct in cases of difficulty write or phone  
15Leworth 5885/1161

MARTIN ELECTRONICS LTD.  
155 High St., Brentford, Middx.  
Latest Recordakits leaflets please!

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
PP8 \_\_\_\_\_

**MICRO-MINIATURE TRANSISTOR AMPLIFIERS**

Brilliantly constructed with incredibly minute yet robust components and providing ideal packaged units for probes, electronic stethoscopes, signal tracers, listening devices, telephone amplifiers, etc. Each has an overall gain of about 40 db. and a substantially flat response over the range 500-3,000 c/s. Each type can be operated from a tiny Mullorj cell size only  $\frac{1}{2}$  in. diam. x  $\frac{1}{4}$  in. thick.

**TYPE 2** Three transistor, completely encapsulated, rectangular pattern, size  $\frac{1}{2}$  x  $\frac{1}{2}$  x  $\frac{1}{4}$  in. thick. Input impedance 300-350 ohms. Output impedance 100 ohms. **30/- P. & P. 1/-.**

**TYPE 3** Three-transistor type mounted on open circuit board and complete with built-in miniature volume control. Size: 2in. long x  $\frac{1}{2}$  in. wide (tapering to  $\frac{1}{4}$  in.) x  $\frac{3}{16}$  in. thick. Input and output impedances 2,000 ohms. **30/- P. & P. 1/-.**

**TYPE 4** Three transistor type mounted on open circuit board and complete with built-in miniature volume control. Size:  $1\frac{1}{2}$  x  $\frac{1}{2}$  x  $\frac{1}{4}$  in. high. Input impedance 2,500 ohms. Output impedance 600 ohms. **20/- P. & P. 1/-.** Each type supplied complete with wiring diagram.

**MINIATURE DYNAMIC MICROPHONES**

**4/- P. & P. 1/-**

Low impedance. Totally enclosed in metal case, size only  $\frac{1}{2}$  x  $\frac{1}{2}$  x  $\frac{3}{16}$  in.

**MINIATURE EARPIECES**

High impedance **10/-**

Low impedance **9/- P. & P. 1/-.**

Transistor radio types with long lead and miniature plug and socket.

**MINIATURE VOLUME CONTROLS**

Totally enclosed black bakelite, rim operated type, size only  $\frac{1}{2}$  in. diam. x  $\frac{3}{16}$  in. thick. Can be supplied with or without ON/OFF switch. Values available 5K and 20K with switch, 5K without switch. **2 for 3/- Post free**

**POCKET MULTIMETER**



for home use

**49/6 P. & P. 2/-**

A really handy, robustly made multimeter that makes an ideal tool for the home electrician, car owner, and Radio/TV fixer. Measures AC or DC

voltages in four complete full scale ranges of 6, 30, 150 and 600 volts; direct current up to 150 milliamperes; and resistance up to 100,000 ohms. Suitable for measurement and continuity and leakage testing. Size only  $3\frac{1}{2}$  x  $2\frac{1}{2}$  x  $1\frac{1}{2}$  in. deep. In black crackle metal case with tough plastic faceplate, and complete with battery and red and black test leads.

**Etch your own PRINTED CIRCUIT KIT**

Each contains over 50 sq. in. of laminated board and sufficient chemicals to make dozens of printed circuits, plus comprehensive instruction book giving advice and examples on translating theoretical circuits into layouts ready for etching. High quality materials—completely safe to handle—carefully prepared to ensure fine definition and uniform results without laboratory control. **21/- Post free**

**PROOPS BROS. LTD.**

Dept. P.W. 52, Tottenham Court Road, London, W.1. Tel: LAN 0141

**TRANSISTORS FROM 1/3**

**GREEN SPOT A.F. 3 volt. ONLY 1/3.**  
**YELLOW SPOT A.F. 6 volt 1/6.**  
**RED SPOTS. Now ONLY 1/9 each.**  
**WHITE SPOTS. ONLY 2/6 each.**

**MICRO-ALLOY TRANSISTORS**

MAT100 7/9, MAT101 8/6, MAT120 7/9, MAT121 8/6. 22 Tested Circuits using Micro-Alloy Transistors 5/-.

**MULLARD TRANSISTORS**

OC70 6/6, OC71 6/6, OC72 8/-, Matched Pr 161/-, OC81 8/-, Matched Pr 161/-, OC78 8/-, OC44 9/3, OC45 9/-, OC170 9/6, OC171 10/6, AF102 27/6, AF114 11/-, AF115 10/6, AF116 10/-, AF117 9/6, AF124 11/-, AF125 10/6, AF126 10/-, AF127 9/6.

**DIODES** OA70, OA79, OA81, OA90, OA91 all 3/- each. BY100 13/-.

**SURPLUS DIODES** CG3E 1/6.

Miniature Type 3 for 2/-, 7/- doz.

**TRANSISTOR HOLDERS** 3 or 5 pin 1/-.

**REPANCO COMPONENTS**

**TRANSISTOR TRANSFORMERS**

TT49 Interstage, TT45 Driver, TT46 Output, TT47 Driver. All 5/- each.

FR2 Ferrite Rod Aerial 12/6.

DRX1 Crystal Set Coil M. & L. 3/-.

DRR2 Dual Range Coils 4/6.

CHI Miniature R.F. Chokes 2/6.

**THE HIKER**, 4 Transistor Portable. Step-by-Step Instructions 1/6.

ALL SENT POST FREE IN U.K. by

**PETHERICK'S RADIO SUPPLIES**

22 High Street, Bideford, N. Devon

Tel.: Bideford 1217

S.A.E. with ALL enquiries please.

**NEW VALVES!**

Guaranteed Set Tested

**24-HOUR SERVICE**

1R5	1S5	1T4	3S4	3V4	DAF91	DF91
DK91	DL92	DL94	SET of 4, 10/9.			
1A4F36	DF96	DK96	DL96	SET of 4, 25/-		
OA2	5/-	DL33	7/3	PCF80	6/-	
1D5	6/9	DL35	7/3	PCF82	6/6	
1R5	4/9	DL92	4/9	PCL82	7/-	
1S5	3/9	DL94	5/6	PCL83	8/9	
1T4	2/11	DL96	6/3	PCL84	5/6	
3S4	4/9	EB91	2/3	PL88	9/-	
3V4	5/6	EB41	7/-	PL81	7/6	
5U4G	4/3	EBF80	7/-	PL82	5/6	
5Y3GT	5/-	EBL21	9/-	PL83	5/6	
5Z4G	8/-	ECC40	4/6	PL84	7/-	
6K7G	1/9	ECC81	4/-	PY31	7/6	
6K9G	4/-	ECC82	4/6	PY32	9/-	
6Q7G	4/6	ECC83	5/9	PY30	5/9	
6V6G	3/9	ECC84	6/6	PY81	5/9	
6X5GT	5/6	ECC85	7/6	PY82	5/3	
12AT6GT	3/11	ECP86	6/9	PY83	6/3	
12K85GT	9/11	ECP82	7/6			
12Q7GT	3/11	ECH42	7/9	U25	9/-	
12SN7GT	5/6	ECL80	6/3	U26	8/-	
14S7	14/-	EF41	7/-	UAF42	5/6	
35L6GT	7/6	EF80	4/1	UBC41	6/9	
39Z4GT	4/9	EF85	5/-	UBC41	6/9	
85A2	6/6	EF86	6/6	UBF80	7/6	
A/C/T/P	21/-	EF89	4/9	UCC85	6/6	
CL33	8/6	EF91	2/9	UCH81	7/3	
DA3C2	8/3	EL41	7/6	UCL82	8/6	
DAF91	3/9	EL94	5/9	UCL83	10/6	
DAF96	6/3	EY51	6/3	UF41	6/9	
DF33	8/6	EY96	6/3	UF89	6/3	
DF91	2/11	EZ40	5/9	UL41	7/6	
DF96	6/3	EZ80	5/3	UL84	6/3	
DH7	4/6	EZ81	4/6	UO82	7/3	
DK32	8/9	KTW61	5/3	UO8	12/6	
DK91	4/9	MU14	5/9	UY21	9/-	
DK92	6/9	PCC84	6/-	UY41	5/6	
DK96	6/9	PCC89	7/9	UY85	5/6	

Postage 6d. per valve extra. Any Parcel Insured Against Damage in Transit 6d. extra Any C.O.D. Parcel 4/3 extra. Office address, no callers.

**GERALD BERNARD**

83 OSBALDESTON ROAD, STOKE NEWINGTON, LONDON, N.16

**Lewis have the Cabinet for you**


We can supply any cabinet to your own specification

This is only one example of—**THE LARGEST RANGE OF CABINETS IN THE COUNTRY**

Equipment is also our speciality.



The Grosvenor Price 15 gns.

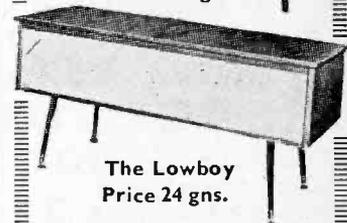

The Lowboy Price 24 gns.

**LEWIS radio**

100(P83) Chase Side, Southgate, London, N.14. Pal 3733/9666

**Send today for the two new Lewis Catalogues**

Designed to assist your choice of cabinet and equipment.

THE New Lewis Radio Cabinet Catalogue—the most comprehensive ever prepared. THE unique 64 page equipment catalogue.

Please send your two new catalogues enclosed in P.O. for 3/6 which will be credited against any purchase 1 make.

Name \_\_\_\_\_

Address \_\_\_\_\_

BLOCK CAPITALS PLEASE

# FREE TO AMBITIOUS ENGINEERS

— THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

## Have you sent for your copy?

ENGINEERING OPPORTUNITIES is a highly informative 156-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronics Courses, administered by our Specialist Electronics Training Division—the B.I.E.T. School of Electronics, explains the benefits of our Employment Dept. and shows you how to qualify for five years promotion in one year.

## We definitely Guarantee "NO PASS—NO FEE"

Whatever your age or experience, you cannot afford to miss reading this famous book. If you are earning less than £25 a week, send for your copy of "ENGINEERING OPPORTUNITIES" today—FREE.

**BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY** (Incorporating E.M.I. Institutes)  
(Dept. SE/21), 29 Wright's Lane, London, W.8

### WHICH IS YOUR PET SUBJECT?

Mechanical Eng.,  
Electrical Eng.,  
Civil Engineering,  
Radio Engineering,  
Automobile Eng.,  
Aeronautical Eng.,  
Production Eng.,  
Building, Plastics,  
Draughtsmanship,  
Television, etc.

### GET SOME LETTERS AFTER YOUR NAME!

A.M.I. Mech. E.  
A.M.I.C.E.  
A.M.I. Prod. E.  
A.M.I.M.I.  
A.I.O.B.  
A.F.R.Ae.S.  
B.Sc.  
A.M.Brit.I.R.E.  
City & Guilds  
Gen. Cert. of Education  
Etc., etc.

### PRACTICAL EQUIPMENT

Basic Practical and Theoretical Courses for beginners in Radio, T.V., Electronics, Etc., A.M. Brit. I.R.E. City & Guilds Radio Amateurs' Exam. R.T.E.B. Certificate P.M.G. Certificate Practical Radio Radio & Television Servicing Practical Electronics Electronics Engineering Automation

### INCLUDING TOOLS!

The specialist Electronics Division of B.I.E.T. (Incorporating E.M.I. Institutes) NOW offers you a real laboratory training at home with practical equipment. Ask for details.

### B.I.E.T. SCHOOL OF ELECTRONICS



### POST COUPON NOW!

Please send me your FREE 156-page "ENGINEERING OPPORTUNITIES" (Write if you prefer not to cut page)

NAME .....

ADDRESS .....

SUBJECT OR EXAM THAT INTERESTS ME .....

SE/21

## THE B.I.E.T. IS THE LEADING ORGANISATION OF ITS KIND IN THE WORLD

## RADIO BOOKS BASIC ELECTRICITY ELECTRONICS

In Simple straight-forward words and Clear Explanatory Pictures. The Reader is taken Step by Step from picture to picture. Officially used by the ARMY, NAVY and AIR FORCE, used by Trainees in the Radio and Electronic Industry.

Write for Illustrated Prospectus giving details of our 7 DAYS FREE TRIAL SCHEME.

BRITISH Semi-conductor Survey 1963 16/-

HOW TO RECEIVE Foreign T.V. programmes on your T.V. set by simple modifications 5/6

22 TESTED Circuits using Micro Alloy Transistors 5/6

BRITISH Transistor Directory (Bradley) 9/-

OSCILLOSCOPE Book USING an Oscilloscope 5/6

OSCILLOSCOPE Equipment 5/6

MULLARD Transistor Radios 5/6

MULLARD Ref. Transistor Circuits, EXTRA Equipment Tape Recorder 13/6

COIL Design and Construction 6/6

TRANSISTOR Audio Amplifiers 5/6

TRANSISTOR Circuits for Radio Control of Models 8/-

RADIO Servicing Instruments 5/6

HIGH Fidelity L/Speaker Enclosures 5/6

BOY'S Book of Crystal Sets 3/-

SERVICING Transistor Receivers 8/-

ELECTRONIC Novelties 5/6

RADIO Valve Data "Wireless World" 7/-

BEGINNERS' Guide to Radio 8/6

MODERN Transistor Circuits for Beginners 9/-

TRANSISTOR Test Equipment 4/-

MAGNETIC Recording Wire and Tape 5/-

RADIO Engineers' Pocket Book 11/6

TRANSISTOR Circuits for the Constructor (Bradley) Nos. 1, 2, 3 and 4 4/- each

SEND STAMP FOR LISTS

**SELRAY BOOK CO.**

60 HAYES HILL, HAYES, BROMLEY KENT. TEL HURSTWAY 1818

## H.A.C. SHORT-WAVE EQUIPMENT

AND

## SHORT-WAVE KITS

Famous for over 25 years for . . . S.W. Receivers and Kits of Quality.

H.A.C. were the original suppliers of SHORT-WAVE RECEIVER KITS for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, Hams, etc.

Improved designs with Denco coils: One-valve Kit, Model "C", Price 25/-; Two-valve Kit, Model "E", Price 50/-; New Addition: Model "K". Super sensitive "All Dry" Receiver. Special inc. price. Complete Kit, 77/-.

All kits complete with all components, accessories and full instructions. Before ordering call and inspect a demonstration receiver, or send for descriptive catalogue and order form.

### POST THIS COUPON NOW!

"H.A.C." SHORT-WAVE PRODUCTS (Dept. TH), 44 Old Bond Street, London, W.1

Please send me FREE and without obligation your 1963 literature.

NAME .....

ADDRESS .....

Multimeter Kit. Our 18,000 o.p.v., 25 range kit, with Weston 50 microamp meter now only 65/- post paid. Send stamp only for full circuit, and details of other multimeters.

WHITE SPOT TRANSISTORS 1/9 Min. Rotary Switches 1p 12w, 2p 6w, 3p 4w, 4p 3w, 4p 2w, 3/8 each, post 9d.

WW pots. 3W. Min. pre-set TV type with moulded knob, all values 25 $\Omega$  to 25k, carbon 30K-2M, 3/-, post 9d.

WW pots. 200 5k, 1.5k, 1/8 ea., post 9d.

Meter Rectifiers, Westinghouse 0.25, 1.5 or 10mA, 14/6, post 6d.

Precision Wirewound Resistors, 1W, 1 $\Omega$  to 1k, 1%, 2/9; to 5k, 3/3; to 20k, 4/-; 1% add 3d. Your value wound to order.

High Stab. Resistors, 1W, 1%, 2/-; 1W, 1%, 2/9; 1W, 10%, 6d.; full range, list available.

Special, 1W, 1%, 100, 10K, 100K, 1/6.

Surplus High Stab. Resistors, 1-2W, 1-5%, list available. Assorted 1%, 3/-; 2%, 2/-; 5%, 1/3 doz., post 1/-

Neon Indicators, Red, amber, clear, single hole fixing, mains volts, 3/6, post 9d.

2W Resistors, 100 assd., 7/6, post 2/-.

## PLANET INSTRUMENT CO., 25, DOMINION AVENUE, LEEDS 7

### BBC - ITV - F.M. AERIALS



B.B.C. (BAND 1), Telescope loft, 21/-, External S/D 30/-.

I.T.V. (BAND 3), 3 Element, loft array, 25/-, 5 Element, 35/-, Wall mounting, 3 Element, 35/-, 5 Element, 45/-.

COMBINED B.B.C./I.T.V. Loft 1+3, 41/3; 1+5, 48/9. Wall mounting 1+3, 56/3; 1+5, 63/9. Chimney 1+3, 63/9; 1+5, 71/3.

F.M. (BAND 3), Loft S/D, 12/6; "H", 30/-, 3 Element, 52/6. External units available. Coax cable 6d., yd. Coax, plus 1/3. C.W.D. or C.O.D. P.P. 3/-.

Send 6d. stamps for illustrated lists. Band IV 625 line Aerials also available.

**K.V.A ELECTRONICS** (Dept. P.W.) 3B, Godstone Road, Kenley, Surrey.

# NOW TWO LOW COST COURSES TO HELP YOU BECOME AN EXPERT IN RADIO OR ELECTRONICS

Our now famous Electronics Course won instant acclaim when offered just over one year ago.

**NOW WE ARE PROUD TO BE ABLE TO OFFER A NEW COMPANION RADIO COURSE FOR THE SAME REASONABLE COST.**

The lessons are crystal clear, practical, easy to master and use. Early lessons make fundamentals clear even to the beginner, while other lessons will give you the practical "know-how" of an expert!

These are real home-study courses that have been printed in large volume and bound into one giant 8x11in. manual to reduce cost. Compares favourably with some courses costing ten times as much. By receiving all lessons at one time you save letter writing, additional postage, and other expenses.

Everyone can benefit from these practical courses. No old fashioned ideas used here. Just straightforward easy to understand explanations to help you get ahead in radio or electronics.

Modern wireless sets use complex circuits, but their function is based on surprisingly few principles. These principles can easily be mastered when explained clearly. That is the object of these courses. Soon you will be well on your way to becoming a first class radio or electronics technician.

More and more people are needed every day to repair wireless sets, amplifiers, VHF/FM radios and electronic gadgets. Are you prepared to get your share of the money to be earned?

Just clip the coupon indicating the course required. You must be convinced that this is the best value you have ever seen in electronic and radio training otherwise you can return the manual (or have your money refunded if sent with order) after you have examined it in your own home for a period of seven full days.

The price? Only 36/- per course, plus postage.

**YOU CAN QUALIFY FOR A CERTIFICATE.** Details sent with each course ordered.

**FREE DATA HANDBOOK WITH EVERY ORDER**

## FREE TRIAL OFFER

TERMS ONLY 5/- PER WEEK!

To SIM-TECH TECHNICAL BOOKS, Dept. WA1, Gater's Mill, West End, Southampton, Hants.

Send ELECTRONICS COURSE  RADIO COURSE

for a full seven days' free trial. If not delighted I may return the course post paid without further obligation on my part. Otherwise I will pay cash or 6/- weekly until paid.

Tick here if enclosing full price (we pay postage). Same 7 day money-back guarantee. Postage charges 1/6 per course. Overseas customers please send full amount (including Ireland).

Name .....

Address .....

City..... County.....

## PADGETTS RADIO STORES

OLD TOWN HALL,  
KNOWLER HILL,  
LIVERSEDGE, YORKS.

Telephone: Cleckheaton 2866

**COMPLETE TV SETS UNTESTED**  
Bush 12in. 13 channels, TV 24C ... 30/-  
Bush 14in. 13 channels, TV43 ... 70/-  
Bush 14in. 13 channels, TV53 ... 75/-  
Pye 14in. 13 channels, V14C console ... 50/-  
Pye 14in. 13 channels, VT4 ... 50/-  
We have 17in. TV Sets with rough cabinets, coils fitted 2 and 10, at 50/-. Carriage on any TV Set 10/- per B.R.S. Well packed but sent at owner's risk.

**Valves Removed from TV Sets.** Tested on Mullard Valve Tester and are 100% as new. Three months unconditional guarantee. POST FREE.

ECL80	4/-	10C2	5/-	PY80	5/-
ECC82	5/-	10F1	1/-	PY81	1/-
EY51	2/6	10P13	5/-	PY82	5/-
EBF90	4/6	10P14	5/-	PZ30	4/-
EB9	9d.	20D1	3/-	PCF80	4/6
EF91	9d.	20P1	5/-	PCC84	4/6
6SN7	2/9	20L1	5/-	PCL85	6/-
696	2/-	185BT	8/6	PL83	5/-
6F1	1/-	U281	5/-	PL33	4/-
6F13	3/-	U282	5/-	B38	4/-
6F14	5/-	U329	5/-	N37	5/-
6F15	5/-	KT36	5/-	6J5	3/-
6LD20	5/-	PL81	5/-	2T5U	5/-
PCL82	6/-	PL82	5/-	U12	4/-

EF80 1/6 or 10/- per doz. Grade 2 EF90 for test purposes, 60Z.

**New Valves Ex Units.** POST FREE.  
AR12 1/6, 6 for 5/6, box of 50 20/-, IT4 2/6,  
AR8 2/-, AHTP2 2/-, APT4 2/-, AFP37 2/-,  
6K7 2/-, 6K8 4/-, 6V6 3/-, 6VGGT 4/6, VR150/30  
2/6, 6C4 2/-, EL91 1/9, EF91 1/9, EF50 1/-,  
6/- doz., 6F6 2/6, 5Z4 5/6, 6X5 4/6.

**P.M. Speakers.** Removed from TV Sets. All perfect condition. Rola and Plessey, 6 x 4in., 5/-; Goodman and R. and A., 7 x 4in., 9/-; Rola and R. and A., 6in. round, 3/6; 6in. Dish, round, 5/-; 8in. round, 6/-. Post on any speaker, 2/-.

**TV Tubes Picture Tested.** Reclaimed from TV Sets, 12in. 17-, 14in. 30/-, Carriage 6 months unconditional guarantee.  
**NEW BOXED UNITS.** Type 230. Complete with 5Z4, Y63, magic eye, four EF50 and complete A.C. 230 volt Power Pack, 25/-.

**Carriage 7/6.**

**Motors Removed from Washing Machines.** 1 hp. 230-250 volts. Tested, 25/-, Carriage 5/-.

**Special Offer.** Grade 1 Transistors, XA101, (OC45), 2/6. Personal earphone, 3/9. Post free.

**T.V. Chassis for Spares.** 56 lbs. weight, 7/6. Carriage 10/-.

## RES/CAP. BRIDGE 39/6 p. & p. 2/6

Checks all types of resistors, condensers 6 RANGES

Built in 1 hour. Direct reading. **READY CALIBRATED**


Stamp for details of this and other kits. Please write to:

**RADIO MAIL (Dept. PO)**  
Raleigh Mews, Raleigh Street, Nottingham
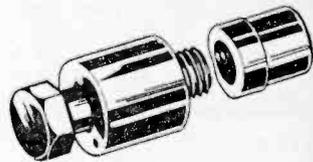
## 2 METRES 4

The thrills of VHF Amateur Radio can now be yours for as low as 39/6—complete kit; by post 2/6 extra—tunable range 70-150 Mc/s. Write today for interesting literature, s.a.e. please. If a newcomer to Short-Wave Radio, ask for free copy of the world-famous "Globe-King" Short-Wave kits and other receivers—stamp for post please, not s.a.e.

**JOHNSONS (Radio)**  
St. Martins Gate, Worcester



The PUNCH you need!

### HOLE PUNCHES

Instant Type	3" diameter ...	6/10 ea.
Screw-up Type	3" diameter ...	8/6 "
	" B7G ...	9/- "
	" B8A, B9A ...	9/6 "
	" ...	10/2 "
	" ...	10/8 "
	" ...	11/8 "
	1 1/2" diameter Int. Octal ...	13/4 "
	" ...	16/2 "
	" ...	18/10 "
	" B9G ...	21/8 "
	" ...	24/4 "
	2 1/2" " Meter ...	33/2 "

Complete Set £8.15.0.

All the above prices include postage and packing.

## Oliver & Randall Ltd

Dept. 7

40 PERRY HILL, LONDON, S.E.6  
Tel.: Forest Hill 3415



After brief, intensely interesting study — undertaken at home in your spare time — YOU can secure a recognised qualification or extend your knowledge of Radio and TV. Let us show you how.

**FREE GUIDE**

The New Free Guide contains 120 pages of information of the greatest importance to both the amateur and the man employed in the Radio industry. Chambers College provides first-rate postal courses for Radio Amateurs' Exam., R.T.E.B. Servicing Cert., C. & G. Telecoms, Grad. Brit. I.R.E. Guide also gives details of range of diploma courses in Radio/TV Servicing, Electronics and other branches of engineering, together with particulars of our remarkable Guarantee of

**SUCCESS OR NO FEE**

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

**FOUNDED 1885—OVER 150,000 SUCCESSSES**

**CHAMBERS COLLEGE**  
(Incorp. National Institute of Engineering)  
(Dept. 461), 148 HOLBORN  
LONDON, E.C.1

# Tubes

Carr. & Ins. 12/6.

HIGHEST QUALITY—  
COMPARE OUR PRICES

6 Months 12 Months NEW TYPES

MOST MULLARD, MAZDA, COSSOR, EMITRON, EMI- SCOPE, BRIMAR, FERRANTI TYPES.	12in. £2. 0.0 £3. 0.0	MW 31/74
PROCESSED IN OUR OWN FACTORY	14in. £2.10.0 £3.10.0	MW 36/24
	15-17in. £3. 5.0 £4. 5.0	ORM 172
	21in. £3.15.0 £5.15.0	MW 43/64 £6.0.0

**SPECIAL TEMPORARY OFFER**  
Due to huge Buik Special Purchase we are offering MW 31-74 Tubes at the unrepeatable price of 29/-, MW 36/24 ditto, 39/-, P. 12/6. The above are guaranteed for 6 months.

### TRANSISTOR RADIO

Zephyr 6 transistor midget de luxe, superbet 180-550 metres with leather case few only **£4.10.0**

P.M. SPEAKERS. 3Ω Top Makes.  
6In. **7/6**  
5In. **8/6**  
7 x 4In. **8/6**

**100 RESISTORS 6/6**  
Excellent. Sizes 1/4-3 watt.

**10 CONDENSERS 10/-**  
Miniature Ceramic and Silver Mica Condensers, 3 pF to 5,000 pF. LIST VALUE OVER £5.

12 POTS. Popular values. 5K to 2 Meg. Unused, mixed, pre-set, long sp. switched, etc. **4/6**  
CONDENSERS. 25 Mixed, Electrolytic. Many popular sizes. List Value £5. Our Price **10/-**

### SILICON RECTS.

250V 500mA standard TV replacement. Top quality 8/6 (3 for 24/-)

### 3 VALVE AMPLIFIERS

Kit of new parts, consisting chassis mains and output transformers, valves (6F1, 6X6, 6X5) and all components. With full instructions for making high gain amplifier with separate base and treble controls, negative feed-back, etc. Truly unusual value **29/-**


**VALUE!**  
**4 watt AMPLIFIERS**  
excellent amplifier with high gain preamp stage, 10F3 driving 10F1 output stage, complete with bin. speaker. In attractive 2-tone case. Tone control, negative feed-back, ready for immediate use. Individually tested. Amazing volume and clarity. Ideal for guitars, record players, h.a. in small halls, baby alarms etc. Easily won't stock last. Carr. **45/-** Packing, etc. 7/6.

CO-AX. low loss, 6d. vd., 25 yds., 11/6. 50 yds., 22/-, 100 yds., 42/6. Coax Plugs. 1/3. Wall outlet boxes 3/6.

# ALL WAVE RADIOS

**VERDI 55. MAINS 5 VALVE SUPER-SENSITIVE SUPERHET.** Really attractive high quality modernistic pastel and gold cabinet. Very compact. Wavebands 18-500-180-5500m, 700-3000m, ferrite aerial and throat aerial. Smooth slow motion tuning. High dux 4in. speaker. **AMAZING S.W. PERFORMANCE, CLARITY, VOLUME.** Standard miniature valves. Easily serviced, standard layout. Truly unusual value and UNRIVALLED absolutely complete with guarantee and circuit. Tax paid.

Guaranteed 3 Months

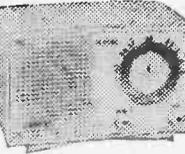

**VERDI 54.** As above but medium and long wave only. **6 Gns.** each

### BBC/ITA 14in. TVs.

With CRM 141 Tubes. Absolutely complete, tested for raster. Famous make, large purchase enables us to offer them at **£4.19.0** Carr. 12/6.

### P.V.C. CONNECTING WIRE

100 yd. 30 mlli: Special Price 7/6.  
200 yd. 30 mlli: Special Price 12/6.  
25ft. Coil, 1/-, 5 Coils different colours. 4/-, Connecting Res. Prices as above.

### AM/FM RADIOS

Fantastic offer. 7 valves plus 2 diodes. Contemporary Cabinet. Top quality and finish. A.P.C. A.V.C. Absolutely complete. Guaranteed 3 months. **£11**

### PORTABLE RECORD PLAYERS.

Take all sizes Records, all speeds, amplifier, auto-changer, Garrard new "Silhouette" Gram. In two-tone case. **13 gns.** All absolutely new.

### PORTABLE RADIOGRAMS.

As above with 3 valve superbet radio. Med. and Long wave. Fantastic value. 17 gns.

TELEPHONE C.O.D. ORDERS  
DISPATCHED THE SAME DAY.

### TRANSISTORS

Guaranteed Top Quality  
Huge reductions. Red Spot standard L.F. type now only 1/8; White Spot R.A. 2/1; Mullard Matched Output Kits (OC81 and 2-OC81) 12/6. Receiver Kits. (OC44, OC45(2), OC81D. 24/- OC81(2), six transistors. **24/-**

AF114 8/- OC28 12/6 OC81 5/6  
AF115 7/6 OC38 14/- OC81D 5/6  
AF118 7/6 OC44 5/6 OC170 8/6  
AF117 7/- OC43 8/6 OC171 8/6  
AF127 9/6 OC72 5/6 XB104 5/6

ENQUIRIES WELCOMED  
Quantity Prices or Quotes for items not listed, particularly rare values.

# ★ GUARANTEED VALVES ★

by return of post  
**THE MOST ATTRACTIVE COMPETITIVE VALVE LIST IN THE COUNTRY**


All valves are new and unused unless otherwise advised.

POST	3 MONTHS GUARANTEE	FREE TRANSIT INSURANCE. Satisfaction or Money back Guarantee on Goods if returned within 14 days.
1 Valve 6d., 2-11, 1/-	In writing with every valve.	

024	4/6	6K7	5/9	20D1	8/8	DL32	9/-	EZ40	6/8	U18	7/6
1A7GT	9/6	6K7G	2/-	20F2	6/6	DL32	9/-	EZ41	6/9	U22	6/9
1C5GT	7/6	6K7GT	9/-	20L1	16/6	DL34	8/6	EZ42	5/8	U34	12/6
1D5	7/-	6K8G	5/-	20P1	8/6	DL96	7/6	EZ43	6/-	U25	10/6
1D6	9/6	6K8GT	8/3	20P3	12/6	EAS0	1/3	FW4/500	7/6	U26	8/6
1H5GT	8/0	3K25	8/6	30P4	17/6	EA50	6/0	GTIC	12/6	U31	7/-
1L4	3/-	6L1	9/6	20P5	15/-	EA091	4/-	GZ32	7/6	U33	14/-
1L25	4/6	6L10	7/6	25AG6	5/-	EA742	8/3	GZ34	11/6	U35	12/6
1N5	4/6	4L8G	6/6	25L6G	7/6	EB34	1/6	HL390	9/6	U37	26/-
1N6GT	8/6	6L13	7/6	25V5G	6/-	EB41	5/-	HL41DD	8/6	U50	4/9
1R5	6/6	6L18	12/6	25Z4G	7/-	EB91	3/3	HN309	19/-	U52	4/9
1U5	6/6	6L20	7/6	25Z5	3/-	EB303	4/9	HVR2	9/-	U78	5/6
1S4	4/6	6P1	9/6	27Z6G	6/-	EB41	7/6	KT32	6/9	U78	4/8
1S5	4/6	6P1	9/6	27Z6G	17/6	EB301	7/6	KT30	4/-	U107	12/6
174	3/-	6P25	8/6	30C1	6/6	EBF90	7/6	KT38	14/-	U191	11/6
2D21	5/6	6P23	9/6	30C15	11/6	EBF83	9/6	KT44	6/-	U281	9/6
3A3	4/-	3Q7G	5/6	30P5	6/-	EBF89	7/6	KT45	8/6	U282	15/-
3A5	8/6	3Q7G	9/6	30L1	9/6	EBL21	9/6	KT61	8/6	U301	12/6
3D3	4/-	3R7G	9/-	30C1	9/6	EB90	11/6	KT62	8/6	U302	6/6
3Q4	7/-	6S47	5/9	30L15	8/6	EC52	4/6	KT68	13/6	U329	9/6
334	5/-	6S47	4/9	30P4	9/6	EC01	4/6	KT78	8/6	U339	11/6
3V4	6/6	6S67	4/9	30P12	6/6	EC02	8/6	KT88	19/-	U404	8/6
6A3GT	9/6	6S47	5/6	30P13	5/6	EC031	7/6	KT91	5/9	U501	19/-
5T4	8/-	6S7	6/-	30P1	9/6	EC03	4/6	KT92	6/6	U502	7/6
5U4G	4/9	6S67	5/-	30P13	9/6	EC033	4/6	KT93	5/9	U503	7/6
5V4G	7/6	6S7GT	5/9	35C5	8/6	EC034	9/-	KT263	11/6	U4M4	7/6
5Y3G	4/6	6S87GT	4/9	35L6GT	8/-	EC035	5/9	L83	3/-	UB41	7/6
6A3GT	5/6	6S7GT	5/9	35V4	6/-	EC040	9/6	LN162	6/6	UB01	7/6
5Y4G	9/6	6S87	5/6	35Z4G	6/6	EC042	9/6	LN174	6/6	UB02	7/6
5Z4	9/-	6U4GT	9/6	35Z3GT	7/-	EC082	4/9	N37	10/6	UF99	7/6
5Z4G	7/-	6V8G	4/6	41	6/6	EC083	6/-	N78	18/-	UBL21	12/-
5Z4GT	9/6	6V8GT	6/-	42	6/6	EC084	7/6	N108	13/-	UC02	8/6
6A3GT	8/6	6X4	4/6	50B5	5/6	EC085	7/6	N152	8/3	UC034	12/-
6A7	3/6	6X5G	5/-	50C5	9/6	EC088	11/6	PC72	3/6	UC035	7/3
6A7	9/-	6X5GT	5/6	50L6GT	7/6	ECF30	8/3	P81	2/9	UCF90	13/3
6A8G	7/9	7B8	9/-	63K0	9/6	ECF32	8/3	PAC80	8/-	UCF91	9/6
6A8GT	12/6	7B7	7/6	61BT	17/6	ECG01	11/6	PC86	11/6	UCF42	7/6
6A9G	11/6	7C7	7/6	61PT	11/6	ECH35	7/6	PC87	9/6	UCF81	7/3
6A9GT	2/9	7C8	7/6	62BT	13/6	ECH42	9/6	PC89	6/6	UL32	8/6
6AG7	6/9	7A7	7/3	75	5/6	ECH81	7/-	PC85	7/9	UL33	12/-
6AK5	5/-	7A7	15/-	78	5/6	ECH83	8/6	PC088	11/6	UF41	7/6
6AL5	3/3	757	8/3	30	5/6	ECLO8	6/6	PC089	8/6	UF42	5/6
6AM5	6/-	734	4/6	83	9/6	EC132	9/6	PC189	13/6	UF90	7/6
6AQ5	6/-	724	5/-	185BT	19/6	EC183	10/6	PC183	10/6	UF92	8/6
6AT6	5/-	8D3	3/-	185BTA	19/6	EC186	10/3	PCF82	7/-	UF86	14/6
6A8U	7/-	10C1	11/6	307(A)	5/6	EF2	7/-	PCF84	12/-	UF89	7/6
6A8V	5/6	10C2	14/6	307E	4/9	EP38	3/3	PCF86	11/-	UL41	7/6
6B6G	8/6	10F1	7/6	313	6/6	EP74	7/-	PCF87	7/3	UL44	14/-
6B8G	3/-	10F9	10/6	832	14/-	EP30	4/6	PCF88	9/6	UL46	9/6
6B8A	5/6	10F13	10/-	866A	12/6	EP40	11/-	PL84	7/3	UL94	7/6
6B8E	5/6	10L1D11	14/6	954	3/9	EP41	8/-	PL85	10/-	UM80	9/6
6B8GT	15/-	10P13	8/6	955	2/3	EP42	6/9	PL86	10/6	URIC	7/6
6B9G	6/6	10P17	9/6	956	4/6	EP43	6/6	PL87	8/6	UR14	3/6
6B16	5/6	10P18	7/-	1025	5/6	EP5(A)	2/6	PL88	6/6	UR15	6/6
6B27	8/6	12A5	2/3	5763	7/6	EP50	3/3	PL89	4/6	UR16	13/6
6B28	9/6	12A5	9/6	9001	3/6	EP84	4/6	PL33	9/6	UY11	11/6
6B29	6/6	12A5	6/6	9002	4/9	EP86	6/-	PL36	9/6	UY21	9/6
6B2W	5/-	12A7	7/6	9005	5/6	EP88	7/6	PL38	17/6	UY41	6/-
6C4	2/3	12A7G	9/-	ATP4	2/6	EP89	6/6	PL81	8/3	UY85	6/6
6C5	5/6	12A7G	6/-	AZ31	7/6	EP91	3/-	PL82	6/6	VP4B	8/6
6C6	3/6	12A7V	6/6	AZ41	7/-	EP92	3/-	PL83	6/6	VP23	2/9
6C7	11/6	12C7	6/6	636	6/6	EP132	9/6	PL84	7/6	VP41	5/6
6CDDG	17/6	12BA6	6/-	61C	8/6	EP183	9/6	PL85	6/6	VR105	5/6
6C6H	6/6	12BE6	6/6	6CH35	13/6	EC32	7/6	PM84	9/6	VR150	5/6
6D2	3/3	12BH7	8/6	6CL33	9/6	EL32	3/9	PX4	12/6	W76	4/9
6D3	9/6	12C8	5/6	6Y31	7/6	EL33	7/-	PX25	8/6	W81	7/3
6D4	3/-	12E1	17/6	6D3	3/6	EL34	11/6	PX31	8/-	X81	11/6
6F1	4/9	12H6	1/9	D30	11/6	EL60	11/6	PL88	11/6	X83	8/6
6F6	7/6	12J5GT	3/3	DAC32	9/6	EL33	12/6	PY33	11/-	X85	11/6
6F8G	4/6	12J7GT	6/-	DAF91	4/6	EL41	8/-	PY80	6/6	X86	7/9
6E13	4/6	12K7GT	4/6	DAF96	7/6	EL42	7/9	PY81	6/6	X76	11/6
6E14	9/6	12K7GT	9/6	DF33	8/-	EL81	8/9	PY82	8/6	X78	21/6
6F15	9/6	12K3GT	4/6	DF91	6/-	EL84	6/6	PY83	6/6	X79	21/6
6F19	6/-	12Q7GT	4/6	DF96	7/6	EL85	8/9	PY88	9/-	X81	9/-
6F32	4/9	12S47	7/-	DF97	7/6	EL91	3/9	PY80	9/-	Y83	6/6
6F33	4/9	12S67	4/6	DH63	5/6	EL95	6/6	PZ30	9/6	Z83	4/9
6F34	9/6	12S7	8/6	DL33	4/6	EM34	4/6	EM34	9/6	Z86	8/6
6J5	4/3	12S7	5/6	DK32	9/6	EM80	9/6	RL18	17/6		
6J5G	3/-	12S7K	4/6	DK91	5/6	EM81	8/6	SP41	2/3		
6J6GT	4/3	12S7GT	8/9	DK92	7/-	EM84	8/6	SP61	2/3		
6K6	8/6	12S7	8/6	DK95	7/6	EM85	9/6	SU25	16/-		
6K7	8/6	13D3	5/6	DL33	6/6	EM81	16/6	TD150	4/6		
6K7G	4/9	14S7	14/6	DL35	7/6	EM51	7/6	T4	6/9		
6K7GT	7/6	19A45	9/6	DL63	8/-	EY88	7/6	TDD4	8/6		
6K6GT	6/-	19B6G	14/-	DL75	6/-</						

**FROM STOCK** We can supply a complete range of Valves, Crystals, Transistors, Diodes, Miniature and Standard Components. The largest range of Components and Equipment in the Country.  
Latest 68 page Illustrated Catalogue 2/- post free. Includes new HI-FI Section.
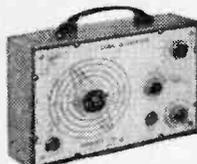
### NEW MODEL TRANSISTOR PORTABLE SIGNAL GENERATOR



PRICE  
**£7.18.6**

With battery and test probe.  
P.P. 2/-.  
A 1st class Signal Generator covering 149 Kc/s to 35 Mc/s in 8 ranges. Radio broadcasts and I.F., Amateur, VHF, Shipping, TV, etc. R.F., I.F., A.F., modulated R.F. outputs. Easy to read and use with full details. Within 2% accuracy. Size 6½ x 4½ x 2in.

**12 MONTH'S GUARANTEE**  
Leaflet on Request.

#### SUBSTITUTION BOXES

- Capacitor Box. Provides 9 standard values from 0.001 to 0.22 mfd at 600 volt working, 29/6.
- Resistor Box. Provides 24 standard values at 1 watt. 15 ohms to 10 meg., 37/6.

Each box fully calibrated with insulated leads. Invaluable for service and design.

#### FIELD STRENGTH METER

Five channels cover 1 Mc/s to 200 Mc/s. Fitted 200 microamp meter for CW or R.F. Indication and Earphone for A.F. monitoring. Designed for checking all types of transmitters. Size 4x2½x2½in. Complete. Ready to Use, with instructions and telescopic aerial, 69/6. Post Free.

½ Track Record/Playback Tape Heads.  
2 KΩ impedance, 15/-.

#### SILICON RECTIFIERS 500mA

100 PIV	3/-	1000 PIV	10/-
200 PIV	3/6	100 PIV 1 amp	4/6
300 PIV	4/6	200 PIV 6 amp	12/6
400 PIV	5/-		


Complete list free on request

#### 100 Kc/s QUARTZ CRYSTALS

2 Pin: OCTAL or RCA	15/- ea.
500 Kc/s 2 Pin	15/-
455 Kc/s (AR88)	12/6
5000 Kc/s 2 Pin	10/-
10 Mc/s 2 Pin	15/-

Complete list free on request

#### ¾ WATT 4 TRANSISTOR AMPLIFIER

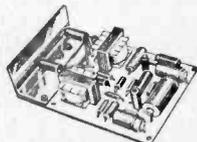

- Improved Version

1½ watt peak output.  
± 3dB 70c/s to 12 Kc/s.  
Output to 3 ohm speaker  
9 volt operated.

Details on request.

Built and Tested  
**59/6** OR **52/6**  
P.P. 1/6 P.P. 1/6

- ★ 4-Transistor PK543. Printed circuit amplifier as previously advertised. Ready to use with full details. 49/6. P. & P. 1/6.
- ★ Crystal Guitar or Contact Microphone, 12/6.
- ★ Telephone Coil for any amplifier or recorder, 12/6.

#### TRANSISTOR BABY ALARM

As previously advertised.  
**£5.10.0**

#### TELEPHONE AMPLIFIER

Speaker output from G.P.O. phone  
**£5.10.0**

#### POCKET RADIO BOOSTER

Tubular unit which plugs into earphone socket of any transistor radio. Performance increase is fantastic. Ideal for home or car. 8 x 2½in. diameter, 22/6. P.P. 1/-, 9½ x 3½in. diameter, 27/6. P.P. 1/-.

#### TYPE 38, TRANSMITTER RECEIVER

Complete with 5 valves. In new condition. These sets are sold without guarantee but are serviceable. **22/6** P.P. 7/4 to 9 Mc/s. 2/6  
Headphones 7/6 pair. Junction Box 2/6. Throat Mike 4/6. Aerial Rod 2/6.

#### DEAC RECHARGEABLE BATTERIES

- (a) 18 volt 100mA/H 4 x 1in. diameter. Brand new sleeved, 30/-.
  - (b) As above but 150mA/H, 35/-.
- Both types easily split into any multiple of 1.2 volt. Brand new.

#### RUN YOUR RADIO OR AMPLIFIER FROM MAINS. BATTERY ELIMINATORS AND CHARGERS

1. For PP3 or equivalent 9 volt Pocket Radio Battery, 18/6. P.P. 1/-.
2. For PP4, PP7, PP9, PP10, 9 volt Portable Radio and Equipment Supplies up to 300 mA. 49/6. P.P. 2/-.
3. De Luxe version of No. 1 also charges PP3 type batteries. 24/-, P.P. 1/-.
4. Rechargeable PP3 battery. Runs as long as 100 batteries. Complete with charger unit, 25/-, P.P. 1/-.

#### LIGHTWEIGHT HEADPHONES



- 2,000 OHMS 12/6
- 4,000 OHMS 14/6

HIGH EFFICIENCY

#### METER BARGAINS

- 50 Microamp 2in. square MC ... 35/-
- 1 mA 2in. square MC ... 25/-
- 1 mA 2½in. Flush Round ... 30/-
- 2½in. Moving Coil double range Voltmeter centre zero. 30-0-30 and 3-0-3 volts. Ideal for transistor tester or voltage measurements, 12/6. Post Free.
- 0/500µA 2in. .... 15/-
- 0/500µA 2½in., flush-mounting, D.C. 20/-
- 0/2½-0-2½mA, 2½in. flush D.C. ... 12/6
- 0/40/120mA 2in. D.C. ... 10/-
- 0/15 volt M.I. 2½in. FR. A.C. ... 8/6

#### Miniature Panel Meters

- \*0/50µA (D.C.) 39/6 \*0/5mA (D.C.) 27/6
  - \*0/500µA (D.C.) 32/6 \*0/300V (D.C.) 27/6
  - \*0/1mA (D.C.) 27/6 Vu Meter 42/6
  - \*5" Meter 35/- All Brand New Boxed.
- \* Available Clear Plastic Front or Black Moulded. State which.

D.C. to A.C. CONVERTER. Converts 12 volts D.C. i.e. Car Battery, up to 230 volts A.C. 15 watts. Uses 2 power transistors in special circuit. Kit 57/6 P.P. 1/6.

## Henry's Radio Ltd

PADdington 1008/9

303 EDGWARE RD., LONDON W.2  
Open Monday to Sat. 9-6. Thurs. 1 o'clock

PLEASE TURN TO BACK PAGE

#### MULTI-METERS



PT34. 1000Ω/V.  
0/10/50/250/500/1,000 volts A.C./D.C.  
0/1/100/500 mA, D.C.  
0/100k etc.  
Size 3½ x 2½ x 1½in.

**45/-**

P.P. 1/6.

All meters supplied complete with batteries, test leads and instructions. See latest catalogue for full details.

#### THL33. 2000Ω/V.

(Illustrated.)  
0/10/50/250/500/1,000 volts A.C. and D.C.  
0/500µA/10/250 mA, D.C.  
0/10k/1000k/1 meg. etc., etc.  
Size 5 x 3½ x 1½in.

**75/-**

P.P. 1/6.

#### ITI-. 20,000Ω/V.

0/5/25/250/500/2,500 volts A.C./D.C.  
0/50µA. 0/2½/250 mA, D.C.  
0/6k/6 meg. etc.  
Size 4½ x 3½ x 1½in.

**5 gns.**

P.P. 1/6.

#### TP55. 20,000Ω/V.

0/10/50/250/500/1,000 volts A.C./D.C.  
0/50µA/0/5/50/500 mA, D.C.  
0/10k/100k/1 meg./10 meg. etc.  
Size 5½ x 3½ x 1½in.

**£5.19.6**

P.P. 1/6.

#### EPIOK. 10,000Ω/V.

0/5/25/100/500/1,000 volts A.C. and D.C.  
0/100µA/250 mA, D.C.  
0/30k/3 meg., etc.  
Size 3½ x 4½ x 1in.

**89/6**

P.P. 1/6.

#### EP30K. 30,000Ω/V.

0/½/1/10/50/250/500/1,000 volts A.C. and D.C.  
0/50µA/10 mA./250 mA, D.C.  
0/10k/1 meg./10 meg. etc.  
Size 4½ x 3½ x 1½in.

**£6.19.6**

P.P. 1/6.

#### EP50K. 50,000Ω/V.

0/10/50/250/500/1,000 volts A.C. and D.C.  
0/25µA. 2½/25/250 mA, D.C.  
0/10k/100k/1 meg./10 meg. etc.  
Size 6½ x 4½ x 2½in.

**£9.19.6**

P.P. 2/-.

#### 500. 30,000Ω/V.

0/½/1/2½/10/25/100/250/500/1,000 volts A.C. and D.C.  
0/150µA/15/50/500 mA. 0/12 amps: short test etc.  
0/60k/6 meg./60 meg. etc.  
Size 6½ x 4½ x 2½in.

**£8.19.6**

P.P. 2/-.

Brand New  
Fully Guaranteed

## TRANSISTOR TAPE RECORDER

The best obtainable

#### WELL KNOWN "MINY" TWO TRACK RECORDER.

Features 4-Transistor push-button amplifier, 2 motors, single switch operation, pause, speed, wind/rewind, record/playback. Can be used horizontally, vertically, carried or table top. Take it anywhere.

Reduced from 12 gns. NOW **£8.19.6**. P. & P. 2/6. Fully guaranteed—complete with microphone, tape, batteries and fully detailed booklet.

# Practical Wireless

# BLUEPRINT SERVICE

**A**LL of these blueprints are drawn full-size and although the issues containing descriptions of these sets are now out of print, constructional details are available free with each blueprint except for those marked thus (\*).

Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to PRACTICAL WIRELESS, Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, London W.C.2.

## DOUBLE-SIDED BLUEPRINTS

Each blueprint in this series contains details of two separate instruments or items of equipment.

The Strand Amplifier ... ..	}	*	5/-
The PW Signal Generator ... ..			
The Savoy VHF Tuner ... ..	}	*	5/-
The Mayfair Pre-amplifier ... ..			
The Berkeley Loudspeaker Enclosure	}	*	5/-
The Luxembourg Tuner ... ..			
The PW Troubadour ... ..	}		7/6
The PW Everest Tuner ... ..			
The PW Britannic Two ... ..	}	*	6/-
The PW Mercury Six ... ..			
The PW Regency ... ..	}	*	5/-
The PW International Short Wave Two			

## RECEIVERS

The Tutor * ... ..	3/-
The Citizen * ... ..	5/-
Junior Crystal Set ... ..	PW94 2/-
Dual-wave Crystal Diode ... ..	PW95 2/6
Modern One-valver ... ..	PW96 2/6
All-dry Three ... ..	PW97 3/6
Modern Two-valver ... ..	PW98 3/6
A.C. Band-pass Three ... ..	PW99 4/-
A.C. Coronet-4 ... ..	PW100 4/-
A.C./D.C. Coronet ... ..	PW101 4/-
The PW Pocket Superhet ... ..	5/-

## MISCELLANEOUS

The PW 3-speed Autogram ... ..	8/-
The PW Monophonic Electric Organ ... ..	8/-
The PW Roadfarer * ... ..	5/-
The PT Band III TV converter ... ..	1/6
The Mini-amp * ... ..	5/-
The PT Olympic * ... ..	7/6
The PT Multimeter * ... ..	5/-

## SOME EARLIER DESIGNS

**T**HE following blueprints include some pre-war designs and are kept in circulation for those constructors who wish to make use of old components which they may have in their spares box. The majority of the components for these receivers are no longer stocked by retailers.

Experimenter's Short Wave ... ..	PW30a	2/6
Midget Short Wave Two ... ..	PW38a	2/6
Simple S.W. One-valver ... ..	PW88	2/6
Pyramid One-valver ... ..	PW93	2/6
BBC Special One-valver ... ..	AW387	2/6
A One-valver for America ... ..	AW429	2/6
Short-Wave World Beater ... ..	AW436	3/6
Standard Four Valve S.W. ... ..	WM383	3/6
Enthusiast's Power Amplifier ... ..	WM387	3/6
Standard Four Valve ... ..	WM391	3/6
Listener's 5-Watt Amplifier ... ..	WM392	3/6

## QUERY COUPON

This coupon is available until 7th August, 1963, and must accompany all queries in accordance with the notice on our "Letters to the Editor" page.

PRACTICAL WIRELESS, AUGUST, 1963.

