

# PRACTICAL WIRELESS

MARCH 1964

2<sup>1</sup>/<sub>2</sub>



THE "7-20"  
STEREO  
AMPLIFIER

USING THE NEW ECLL 700 AUDIO VALVE



**SOLDERING EQUIPMENT**

for


**TOTAL PERFORMANCE**

**A COMPLETE RANGE OF EQUIPMENT FOR THE RADIO AMATEUR**

**ILLUSTRATED**

- List 64.  $\frac{3}{16}$ " DETACHABLE BIT IN PROTECTIVE SHIELD
- List 700

BRIT. & FOR. PATS.

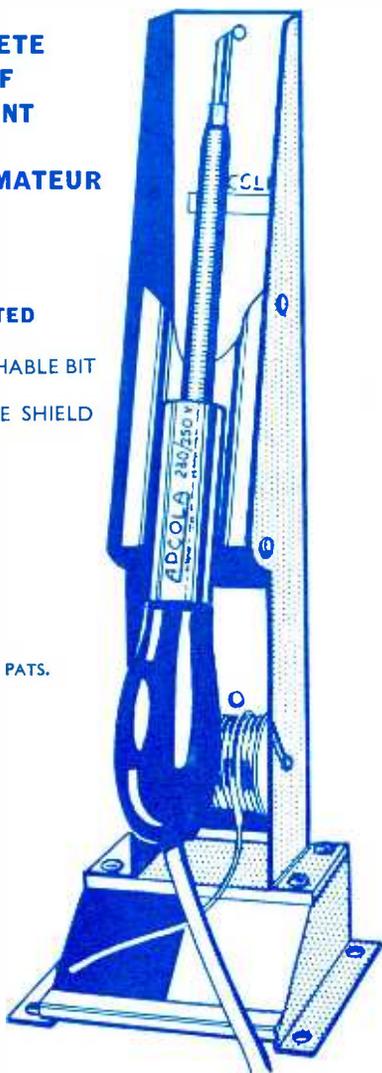

**Sales & Service**


APPLY DIRECT FOR CATALOGUE TO

**ADCOLA PRODUCTS LTD.,  
ADCOLA HOUSE,  
GAUDEN ROAD, LONDON, S.W.4**

Telephones MACaulay 4272 & 3101      Telegrams SOLJOINT LONDON SW4



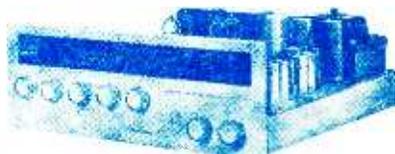A NEW range of Tuner-Amplifiers with all the performance capabilities of separate tuners and amplifiers, superseding the Stereo 12 and Jubilee models.



**227 AM-FM STEREO TUNER-AMPLIFIER**

20 watts power output. Covering the full FM and medium wavebands. Inputs for any ceramic or crystal pick-up and tape playback, also outputs for tape recording. Exceptional sensitivity and stability on FM, the Foster Seeley Discriminator being preceded by two IF Stages and a limiter stage. Medium waveband featuring automatic variable selectivity and heterodyne rejection filter provides Continental reception of good programme value

PRICE **£48.15.0**

**227 M. AM-FM TUNER-AMPLIFIER**

This is the mono version of the 227 above and is identical in performance and specification except that a single channel control unit is incorporated with only one amplifier. Stinking is also similar to the 227.

PRICE **£33.18.0**



**STEREO 55 TUNER-AMPLIFIER CHASSIS**

One compact chassis combines AM and FM tuners. Stereo Control Unit and two power amplifiers. For mono reproduction the two amplifiers are used together so that up to 10 watts output is available. Provision for tape recording and playback is made with a choice of inputs for crystal or ceramic pick-ups including the Decca Deram.

PRICE: **£29.18.0**

**AF 208 AM-FM CHASSIS**

A high quality tuner amplifier chassis which can be used for the conversion of an existing radiogram or as the basis for building a new radiogram or reproducing system.

PRICE: **£21.4.0**

Full descriptive literature available from Dept. No. PMT.

**ARMSTRONG AUDIO LTD.**  
WALTERS RD., LONDON, N.7. Tel: North 3213

# ★ GUARANTEED VALVES ★

by return of post

**THE MOST ATTRACTIVE COMPETITIVE VALVE LIST IN THE COUNTRY**

**All valves are new and unused unless otherwise advised**

| POST  | 3 MONTHS  | FREE TRANSIT IN-  |
|---|---|---|
| 1 Valve 6d. 2-11. 1/-<br>FREE for 12 or more<br>valves. | <b>GUARANTEE</b><br>in writing with<br>every valve. | <b>SURANCE.</b> Satisfaction<br>or Money back Guarantees<br>on Goods if returned<br>within 14 days. |

|        |      |         |      |        |       |           |       |        |      |        |      |
|--------|------|---------|------|--------|-------|-----------|-------|--------|------|--------|------|
| 02A    | 4/6  | 6K7G    | 2/-  | 20D1   | 8/9   | DL75      | 6/-   | EY51   | 7/-  | 8U25   | 1/6  |
| 1A7GT  | 9/6  | 6K7GT   | 4/6  | 20P2   | 9/6   | DL82      | 9/6   | EY56   | 5/6  | 8U2150 | 4/6  |
| 1C5GT  | 7/6  | 6K8G    | 5/-  | 20L1   | 15/-  | DL92      | 3/-   | EY58   | 9/6  | T41    | 6/8  |
| 1D5    | 7/-  | 6K9GT   | 8/6  | 20P1   | 9/6   | DL94      | 6/6   | EY59   | 5/6  | TDD4   | 8/8  |
| 1D6    | 9/6  | 6K25    | 8/6  | 20P3   | 6/6   | DL96      | 6/6   | EZ41   | 6/6  | U14    | 2/6  |
| 1H5GT  | 8/9  | 3L1     | 9/6  | 20P4   | 1/5   | EA50      | 1/5   | EZ80   | 5/6  | U18    | 7/6  |
| 1L4    | 3/-  | 6L6     | 7/6  | 20P5   | 12/6  | EAC80     | 6/-   | EZ81   | 4/6  | U22    | 9/6  |
| 1L5    | 4/6  | 6L9     | 8/6  | 25A9G  | 8/-   | EAC91     | 4/-   | FC4    | 9/6  | U24    | 12/6 |
| 1L6    | 4/6  | 6L19    | 7/6  | 25L6GT | 6/-   | EAF41     | 6/6   | FW4500 | 7/-  | U25    | 11/- |
| 1N5GT  | 8/9  | 3L19    | 12/6 | 25Y5G  | 8/-   | EAF42     | 8/3   | GTIC   | 12/6 | U26    | 9/6  |
| 1R5    | 6/6  | 3LD20   | 7/9  | 25Z4   | 7/-   | EB84      | 1/3   | GZ22   | 10/- | U31    | 7/-  |
| 1U5    | 6/-  | 6N7     | 7/6  | 25Z5   | 8/-   | EB41      | 5/-   | GZ24   | 10/- | U33    | 14/- |
| 1T4    | 7/6  | 6P1     | 9/6  | 25Z6G  | 8/-   | EB91      | 3/3   | HK90   | 9/6  | U35    | 28/6 |
| 1R5    | 4/6  | 6P25    | 4/6  | 25Z7U  | 9/6   | ECC38     | 4/9   | ELD11  | 6/6  | U37    | 28/6 |
| 1R4    | 3/-  | 6P28    | 9/6  | 30C1   | 6/6   | EBC41     | 6/6   | EN808  | 19/- | U38    | 4/9  |
| 2D21   | 5/6  | 6Q7G    | 5/6  | 30C15  | 6/6   | EBC81     | 6/-   | HV22   | 9/-  | U52    | 4/9  |
| 3A4    | 4/-  | 6Q7GT   | 8/-  | 30F5   | 10/6  | EBF80     | 6/6   | KT32   | 6/9  | U76    | 5/6  |
| 3A5    | 7/-  | 6R7G    | 9/-  | 30FL1  | 10/6  | EBF88     | 7/6   | KT33   | 4/-  | U78    | 4/6  |
| 4S4    | 4/6  | 6S2     | 5/6  | 30L1   | 6/6   | ECC38     | 4/9   | KT36   | 14/- | U107   | 12/6 |
| 3Q4    | 7/-  | 6SC7    | 4/9  | 30L15  | 12/6  | EEL21     | 11/-  | KT44   | 6/-  | U134   | 9/6  |
| 3S4    | 5/-  | 6SG7    | 4/9  | 30P4   | 9/6   | EEL31     | 17/6  | KT55   | 17/6 | U281   | 9/-  |
| 3V4    | 6/6  | 6SH7    | 3/-  | 30P12  | 9/6   | ECS2      | 4/9   | KT61   | 8/6  | U282   | 14/- |
| 5R4GT  | 9/6  | 6S7     | 5/-  | 30P19  | 14/-  | EC91      | 4/6   | KT63   | 4/6  | U301   | 12/6 |
| 5R5    | 7/-  | 6S7     | 5/-  | 30R2   | 10/6  | ECS2      | 8/6   | KT66   | 13/6 | U309   | 9/6  |
| 5U4G   | 4/9  | 6SL7GT  | 5/9  | 30FL13 | 12/6  | ECC31     | 7/6   | KT76   | 6/6  | U309   | 9/6  |
| 5V4G   | 7/6  | 6SN7GT  | 4/6  | 30FL14 | 12/6  | ECC32     | 4/-   | KT88   | 19/- | U339   | 11/6 |
| 5Y3G   | 4/9  | 6S4T    | 5/9  | 35C5   | 8/6   | ECC33     | 4/6   | KTW61  | 5/9  | U404   | 6/6  |
| 5Y3GT  | 5/6  | 6S5T    | 3/6  | 35L9GT | 7/-   | EC94      | 9/-   | KTW62  | 6/6  | U401   | 17/6 |
| Y4G    | 4/6  | 6T4GT   | 5/6  | 35R7   | 4/6   | EC95      | 6/6   | KTW63  | 5/9  | U43C80 | 5/6  |
| 5Z4    | 9/-  | 6V8G    | 6/-  | 35Z4GT | 6/-   | EC90      | 9/6   | KTW68  | 11/- | U4743  | 9/6  |
| 5Z4G   | 7/-  | 6V8GT   | 6/-  | 35Z5GT | 6/-   | EC91      | 4/9   | L63    | 3/-  | UB41   | 7/6  |
| 5Z4GT  | 9/6  | 6X4     | 4/6  | 41     | 6/6   | EC92      | 4/9   | LN158  | 6/6  | UB41   | 6/6  |
| 6/30L2 | 9/-  | 6X5G    | 5/6  | 42     | 8/6   | EC93      | 6/-   | MU14   | 7/-  | UBC81  | 7/6  |
| 6A5    | 8/9  | 6S5GT   | 7/6  | 40B5   | 7/9   | EC94      | 6/6   | N57    | 10/6 | UBF80  | 6/6  |
| 6A7    | 9/-  | 7B6     | 9/-  | 50C5   | 8/6   | EC95      | 6/6   | N78    | 13/- | UBF89  | 7/6  |
| 6A9G   | 7/9  | 7B7     | 7/9  | 50L8GT | 8/-   | EC98      | 11/6  | N108   | 13/- | UBE11  | 11/6 |
| 6A9GT  | 12/6 | 7C5     | 7/2  | 55KX   | 9/6   | ECF80     | 7/6   | N153   | 8/3  | UC92   | 8/6  |
| 6A7    | 3/-  | 7C6     | 7/6  | 61BT   | 17/6  | ECF82     | 7/-   | P41    | 3/6  | UC94   | 9/6  |
| 6A8    | 9/6  | 7B7     | 5/-  | 61PT   | 11/-  | EC91      | 11/-  | P61    | 5/6  | UC95   | 9/6  |
| 6A7    | 6/9  | 7B7     | 15/- | 2BT    | 13/6  | ECH35     | 7/6   | PAB30  | 7/6  | UCF80  | 9/6  |
| 6AK5   | 5/-  | 787     | 8/9  | 75     | 5/6   | ECH42     | 8/-   | PC86   | 11/6 | UCF81  | 8/6  |
| 6AL5   | 3/8  | 774     | 5/-  | 78     | 5/6   | ECH31     | 6/-   | PC97   | 8/6  | UCF82  | 7/6  |
| 6AM5   | 8/-  | 724     | 5/6  | 80     | 6/6   | ECH33     | 7/6   | PC94   | 6/6  | UCF81  | 7/6  |
| 6AQ5   | 6/-  | 8D8     | 11/6 | 83     | 9/6   | ECL30     | 7/6   | PC94   | 7/6  | UL48   | 9/6  |
| 6AT6   | 5/-  | 10C1    | 11/6 | 185BT  | 19/6  | ECL82     | 7/6   | PC98   | 11/9 | UL83   | 30/- |
| 6A7    | 6/6  | 7/1     | 10C2 | 11/6   | 185BT | 19/6      | ECL83 | 10/-   | PC98 | 10/-   |      |
| 6AV6   | 8/9  | 10F1    | 7/6  | 807A   | 10/6  | ECL86     | 10/-  | PC918  | 13/6 | UF42   | 7/6  |
| 6B7    | 3/6  | 10F9    | 7/6  | 808    | 4/9   | EF32      | 3/6   | PCF30  | 5/6  | UF80   | 6/6  |
| 6B9G   | 3/-  | 10F18   | 10/- | 813    | 4/9   | EF32      | 3/6   | PCF32  | 6/6  | UF85   | 5/6  |
| 6BA6   | 4/9  | 10LD11  | 14/6 | 832    | 14/-  | EF37A     | 7/6   | PCF84  | 10/- | UF86   | 12/6 |
| 6B2E   | 5/-  | 10F13   | 12/6 | 866A   | 12/6  | EF39      | 4/6   | PCF86  | 8/-  | UF89   | 6/6  |
| 6B6G   | 15/- | 10F14   | 9/6  | 954    | 3/9   | EF40      | 4/6   | PCL32  | 6/6  | UL41   | 7/6  |
| 6B18   | 7/-  | 10P18   | 7/6  | 885    | 2/3   | EF41      | 6/6   | PCL33  | 3/3  | UL44   | 14/9 |
| 6B16   | 8/-  | 12A6    | 2/3  | 886    | 2/6   | EF42      | 6/6   | PCL34  | 7/6  | UL48   | 7/6  |
| 6BR7   | 8/6  | 12A65   | 9/-  | 1825   | 5/6   | EF50-BR16 | 6/6   | PCL55  | 7/6  | UL84   | 7/6  |
| 6B8E   | 9/6  | 12A28   | 11/- | 5763   | 7/6   | EF50A     | 2/6   | PCL38  | 8/-  | UM80   | 9/6  |
| 6B9E   | 9/-  | 12AT    | 6/6  | 8901   | 2/6   | EF54      | 3/3   | PN23   | 3/9  | UR1C   | 7/6  |
| 6B9T   | 6/-  | 12AT7   | 7/6  | 8902   | 4/9   | EF90      | 5/-   | PN45   | 6/6  | UT7    | 9/6  |
| 6C4    | 2/8  | 12A06   | 9/-  | 9008   | 5/6   | EF95      | 6/6   | PN46   | 4/6  | UT7    | 9/6  |
| 6C5    | 10/6 | 12A07   | 6/-  | ATP4   | 2/6   | EF96      | 6/-   | PL33   | 9/6  | UY9    | 13/6 |
| 6C8    | 3/6  | 12A08   | 9/6  | AZ21   | 8/-   | EF99      | 4/6   | PL36   | 8/-  | UY11   | 11/- |
| 6C9    | 11/- | 12A07   | 9/6  | AZ41   | 7/-   | EF91      | 8/-   | PL38   | 16/- | UY21   | 8/6  |
| 6C6G   | 3/6  | 12B6    | 7/6  | 806    | 6/6   | EF92      | 6/6   | PL31   | 10/- | UY41   | 9/6  |
| 6C6E   | 6/6  | 12B6E   | 6/6  | C1C    | 9/-   | EF183     | 8/-   | PL85   | 5/6  | UY55   | 9/6  |
| 6D2    | 8/3  | 12B7    | 9/9  | COH35  | 13/6  | EF184     | 8/-   | PL88   | 6/-  | VP48   | 9/6  |
| 6D8    | 9/6  | 12C3    | 6/6  | CL33   | 9/-   | EK32      | 3/6   | PL84   | 6/6  | VP23   | 2/6  |
| 6T4    | 3/6  | 12E1    | 17/6 | FD31   | 7/6   | EL32      | 3/9   | PL89   | 8/3  | VP41   | 5/6  |
| 6F1    | 4/9  | 12E5    | 6/6  | DE79   | 8/6   | EL33      | 7/6   | PMA    | 9/6  | VR105  | 6/6  |
| 6F6    | 7/6  | 12J5GT  | 3/3  | DA80   | 11/6  | EL34      | 10/-  | PX4    | 12/6 | VR160  | 6/6  |
| 6F9G   | 4/8  | 12J7GT  | 3/-  | DAC32  | 9/9   | EL35      | 6/-   | PX25   | 9/-  | W78    | 4/9  |
| 6F13   | 4/9  | 12K7GT  | 4/6  | DAP91  | 4/6   | EL38      | 12/6  | PY31   | 8/-  | W81    | 7/6  |
| 6F14   | 9/6  | 12K7    | 8/6  | DAP96  | 6/-   | EL41      | 7/3   | PY32   | 10/- | X63    | 8/6  |
| 6F15   | 9/6  | 12K8GT  | 8/6  | DF33   | 8/6   | EL42      | 8/6   | PY33   | 10/- | X65    | 11/6 |
| 6F19   | 6/-  | 12Q7GT  | 4/6  | DF91   | 3/6   | EL51      | 8/9   | PY80   | 6/6  | X69    | 9/6  |
| 6F22   | 4/9  | 128A7   | 7/-  | DF96   | 6/-   | EL84      | 5/-   | PY81   | 6/6  | X81M   | 9/-  |
| 6F23   | 4/9  | 128G7   | 4/6  | DF97   | 7/6   | EL85      | 9/9   | PY82   | 5/-  | Y68    | 6/6  |
| 6F24   | 1/6  | 128H7   | 3/6  | DH63   | 3/6   | EL86      | 7/6   | PY83   | 6/-  | Z63    | 4/9  |
| 6J5    | 4/3  | 128J7   | 6/6  | DE79   | 8/6   | EL81      | 4/6   | EL13   | 8/6  | Z66    | 8/6  |
| 6J5G   | 3/-  | 128K7   | 4/6  | DK32   | 9/6   | EL85      | 9/-   | PY80   | 6/6  |        |      |
| 6J5GT  | 4/3  | 128N7GT | 6/9  | DE91   | 6/6   | EM34      | 8/9   | PY801  | 6/6  |        |      |
| 6J6    | 3/6  | 128Q7   | 8/6  | DK98   | 6/6   | EM80      | 6/6   | PZ80   | 9/6  |        |      |
| 6J7    | 5/6  | 128R7   | 6/6  | DH63   | 6/6   | EM91      | 7/6   | R10    | 9/6  |        |      |
| 6J7G   | 4/9  | 1487    | 14/6 | DL83   | 7/6   | EM84      | 8/-   | EL13   | 11/6 |        |      |
| 6J7GT  | 7/6  | 19A4G5  | 7/9  | DL35   | 7/6   | EM85      | 9/-   | SP41   | 2/3  |        |      |
| 6K9GT  | 6/-  | 19B6G   | 14/- | DL63   | 9/-   | EN31      | 16/-  | SP61   | 2/3  |        |      |
| 6K7    | 5/8  |         |      |        |       |           |       |        |      |        |      |

**8K00 L.O.P.T.** Unused replacements for Permaplast based 1954/7 models, complete with E.H.T. rect. **39/-** unreplaceable.

**00-AX** low loss, 6d. yds., 25 yds., 11/6, 50 yds., 22/-, 100 yds., 42/6, Co-ax plugs, 1/8. Wall-out letter boxes 3/6.

**SPECIAL C.E.T. OFFER**  
Due to huge Bulk Special Purchase we are offering MW 31-74 Tubes at the unreplaceable price of 29/-, MW 36/24 ditto 39/-, P.P. 12/6. The above are guaranteed for 6 months.

**LOUDSPEAKERS.** 3Ω Top Makes. 6 1/2 in. 5in. 8/6 7 x 4in. 8/6

**CONNECTING WIRE**  
P.V.C. Bright colours. Five 4/- 25ft. coils only

**3 VALVE AMPLIFIERS**  
Kit of new parts, consisting chassis, mains and output transformers, valves (P61, 6X6G, 6X5G) and all components. With full instructions for making high gain amplifier with separate base and treble controls, negative feedback, etc. Truly unobtainable **29/-**

**MAINS TRANSFORMERS**  
Excellent Quality Guaranteed. Upright mounting 250-0-250 V 60ma, 6.3 V 3 A (80ma 12/6) 9/6 Ditto semi-shrouded 9/6.

## TRANSISTORS

**GUARANTEED TOP QUALITY**  
Huge reduction. Red Spot standard L.F. type now only **1/6** White Spot **2/6**

|   |      |       |     |
|---|------|-------|-----|
| <b>Mullard Matched Output Kits</b> (OC81D and 2-OC81E) R.F. Kits (OC44, OC45 (2), 3 transistors.) |      |       |     |
| AF114   | 8/-  | OC44  | 5/6 |
| AF115   | 7/6  | OC45  | 5/6 |
| AF116   | 7/6  | OC72  | 5/6 |
| AF117   | 7/-  | OC81  | 5/6 |
| AF127   | 9/6  | OC81D | 5/6 |
| OC82  | 12/6 | OC82  | 6/6 |
| OC88  | 14/- | OC170 | 8/6 |
|   |      | OC171 | 8/6 |

**GERMANIUM DIODES**  
General Purpose miniature detector, A.V.C., etc. or 6/6 doz. **8d.**

Gold bonded single quality. Individually tested. **1/9** doz.

**SILICON RECTIFIERS**  
Guaranteed performance. Top Make. Tested 250V working. 100mA 3/9 250mA (3 for 9/6) 3/9 (3 for 19/6) 7/6

# NEW SHOP SOUTHAMPTON

OPENING IN LARGE PREMISES

WE LOOK FORWARD TO OFFERING YOU A FIRST CLASS SERVICE FROM 18th JAN. 1964 at:

## 72, EAST STREET (TEL. 25851)

With widest Stocks, Keenest Prices: T.V., Radios, Valves, Transistors, Hi-Fi Equipment, Loudspeakers, Autochangers, Cables, Components etc.

**★ BULK BARGAINS ★**  
12 POTS. Popular values. 5K to 2 MΩ. Unused, mixed, pre-CONDENSERS, 25 Mixed, Electrolytic. Many popular sizes. List Value £5. Our Price **10/-**

**100 RESISTORS 6/6**  
Excellent. Sizes 1-3 watt.

**100 CONDENSERS 9/6**  
Miniature Ceramic and Silver Mica Condensers, 3 pF to 5,000 pF. LIST VALUE OVER £5.

**25 TAG STRIPS 4/-**  
2, 4, 6, 8 way etc. Unused.

**100 HI STABS 9/6**  
1% to 5% 100Ω to 5MΩ.

**4 watt AMPLIFIERS**  
excellent amplifier with high gain preamp stage, 10F8 driving 10P14 output stage, complete with 8in. speaker. In attractive 2-tone case. Tone control, negative feedback, ready for immediate use, individual test points, amazing volume and clarity, ideal for guitars, record players, p.a. in small halls, baby alarms, etc. Easily worth £5. Our price whilst stocks last. **45/-** Carr. Packing, etc.


**ENQUIRIES WELCOMED**  
Quantity Prices or Quotes for items not listed. Particularly rare values  
**TELEPHONE C.O.D. ORDERS DISPATCHED THE SAME DAY.**

## Tubes

Carr. & Ins. 12/6

|  |  |                 |                  |  |       |          |                 |       |          |                 |          |         |                 |
|--|--|-----------------|------------------|--|-------|----------|-----------------|-------|----------|-----------------|----------|---------|-----------------|
|  | <b>HIGHEST QUALITY—COMPARE OUR PRICES</b>  |                 |                  |  |       |          |                 |       |          |                 |          |         |                 |
|  | <b>GUARANTEED</b>  |                 |                  |  |       |          |                 |       |          |                 |          |         |                 |
|  | 6 Months    12 Months  |                 |                  |  |       |          |                 |       |          |                 |          |         |                 |
| <p><b>MOST MULLARD, MAZDA, COSSOR, EMITRON, EMISCOPE, BRIMAR, FERRENTI TYPES, PROCESSED IN OUR OWN FACTORY</b></p> | <table style="width: 100%; border-collapse: collapse;"> <tr> <td style="width: 30%;"></td> <td style="width: 30%; text-align: center;"><b>NEW TYPES</b></td> <td style="width: 40%;"></td> </tr> <tr> <td style="font-weight: bold;">12in.</td> <td style="text-align: center;">MW 31/74</td> <td style="text-align: right;"><b>£3.15.00</b></td> </tr> <tr> <td style="font-weight: bold;">14in.</td> <td style="text-align: center;">MW 38/94</td> <td style="text-align: right;"><b>£4.15.00</b></td> </tr> <tr> <td style="font-weight: bold;">15-17in.</td> <td style="text-align: center;">CRM 172</td> <td style="text-align: right;"><b>£5.10.00</b></td> </tr> <tr> </tr></table> |                 | <b>NEW TYPES</b> |  | 12in. | MW 31/74 | <b>£3.15.00</b> | 14in. | MW 38/94 | <b>£4.15.00</b> | 15-17in. | CRM 172 | <b>£5.10.00</b> |
|  | <b>NEW TYPES</b>   |                 |                  |  |       |          |                 |       |          |                 |          |         |                 |
| 12in.  | MW 31/74   | <b>£3.15.00</b> |                  |  |       |          |                 |       |          |                 |          |         |                 |
| 14in.  | MW 38/94   | <b>£4.15.00</b> |                  |  |       |          |                 |       |          |                 |          |         |                 |
| 15-17in.   | CRM 172  | <b>£5.10.00</b> |                  |  |       |          |                 |       |          |                 |          |         |                 |
|  |  |                 |                  |  |       |          |                 |       |          |                 |          |         |                 |

# THE SMALLEST

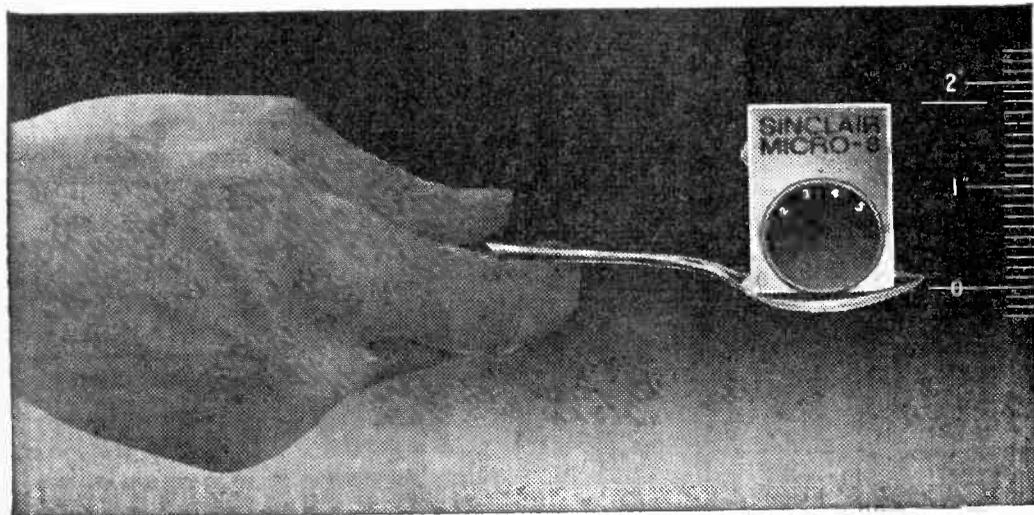

*A teaspoonful of power!*



## TECHNICAL SPECIFICATION

The Sinclair Micro-Six comprise two stages of R.F. amplification with double diode detector. These are followed by three stages of audio amplification. The application of negative feedback to all three A.F. stages ensures ultra-linear amplification, while amplified A.G.C. applied to the first R.F. stage provides fade-free reception from distant stations such as Luxembourg. Sensitivity is actually superior to that of conventional radios many times larger. The Micro-Six tunes over the entire medium waveband with increased coverage at the high frequency end to provide improved separation of Continental stations. The set switches on automatically when the high-impedance featherweight earpiece is plugged into the specially designed micro socket. Quality of reproduction is exceptionally good.

### POWER REQUIREMENTS

A Mallory Mercury Cell Type ZM.312, the world's smallest battery, will give approximately 6 months' life, costs 1s. 11d. and is readily available. Two can be accommodated for still greater power and sensitivity if desired.

**CHASSIS VIEW  
GREATLY  
ENLARGED**

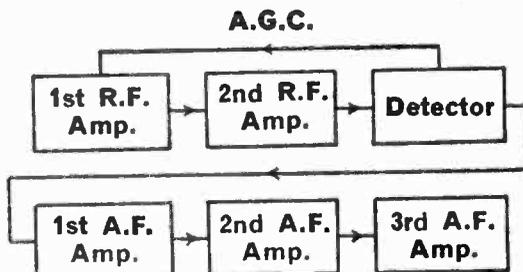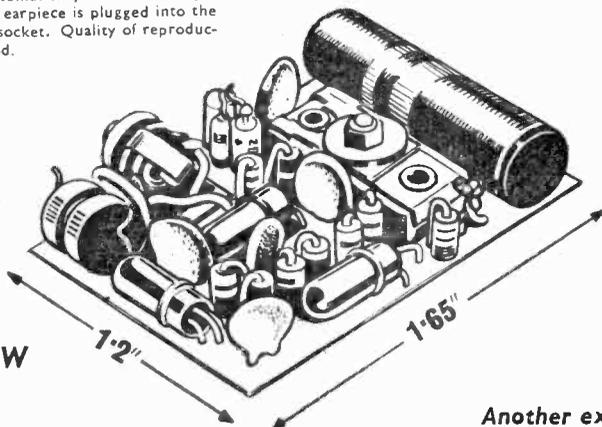

Block diagram of Sinclair Micro-Six

6-STAGE SENSITIVITY BETTER THAN MANY SUPERHETS

UNIQUE CIRCUITRY GIVES IMMENSE POWER AND QUALITY

PLAYS IN CAR, BUS, TRAIN, PLANE

CHOICE OF MANY STATIONS

BATTERIES AND AERIAL COMPLETELY SELF-CONTAINED

*Another exclusive Sinclair design*

# SET IN THE WORLD

## A fantastic advance in micro-miniaturisation

Just look at the remarkable specification of this latest Sinclair micro-electronic design—and then look at its size— $1\frac{1}{2}$  x  $1\frac{3}{10}$  x  $\frac{1}{2}$  in. It is almost unbelievable that a set with these tested and proven standards of performance can be contained within a case considerably smaller than a matchbox. Yet it gives superb results from stations all over the medium waveband with a power and sensitivity placing it years ahead of anything even the Japanese have produced. This is a professionally styled set brilliantly designed by the Sinclair research team to incorporate all the important circuit features of a de-luxe receiver. You will find building the Micro-Six the most absorbing experience you have ever had in electronics. So send for your Micro-Six today, and you will have for your pride and pleasure the smallest and most efficient receiver of its kind in the world.

### SINCLAIR GUARANTEE


Should you not be completely satisfied with your purchase (although we are confident that you will be delighted) the full purchase price will be refunded instantly without question.

FULL SERVICE FACILITIES AVAILABLE TO ALL SINCLAIR CUSTOMERS
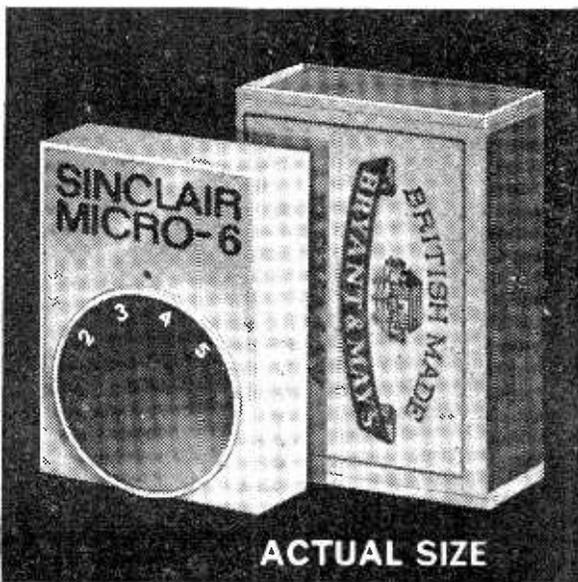
# SINCLAIR MICRO-6

★ MORE SINCLAIR DESIGNS ON NEXT PAGE  
**SINCLAIR RADIONICS LTD.**  
 69, HISTON ROAD, CAMBRIDGE

If you do not wish to cut this page, please mention "Practical Wireless" (March) when ordering.



ACTUAL SIZE

ONLY  $1\frac{1}{2}$ " x  $1\frac{3}{10}$ " x  $\frac{1}{2}$ "

## ALL YOU WANT TO BUILD THE SINCLAIR MICRO-6

All parts necessary to build this wonderful receiver, including MAT transistors, diodes, micro-miniature components, printed circuit board, special ferrite-rod aerial, elegant case and knurled dial and featherweight hi-fi quality earpiece together with well presented instructions come only to

**59/6**

Mallory Mercury Cell, Type ZM.312, 1s. 11d. each

### IMPORTANT NOTICE

The Sinclair Micro-6 is an ultra-small precision designed instrument. As such, previous experience in transistor building will be found helpful. It is imperative that a modern miniature soldering iron be used when building the set.

To Sinclair Radionics Ltd., 69 Histon Rd., Cambridge

Please send parts for building.....Micro-6 Receiver(s) and.....Mallory Cells, Type ZM.312 at 1s. 11d. ea. for which I enclose £.....s.....d.

NAME .....

ADDRESS .....

PW.3 .....


# MORE SINCLAIR DESIGNS FOR THE TRANSISTOR ENTHUSIAST

## THE Sinclair "SLIMLINE" THE EASY-TO-BUILD MICRO-RECEIVER THAT GIVES YOU EUROPE in the PALM of YOUR HAND

Here's the set to start you in micro-electronic building. For POWER, SELECTIVITY and QUALITY, it is unsurpassed in its class, yet it is actually smaller than a standard packet of 20 cigarettes! Such exciting standards are due entirely to exclusively developed Sinclair circuitry—yet it costs so very little to build this wonderful receiver. It gives you Home, Light and Third Programmes and other stations with amazing ease, playing even in cars and trains. For a brand new concept in radio listening, BUILD A SLIMLINE NOW—it's fascinatingly easy even if you have never built a set before in your life. Size 2½ x 1½ x ¾ in.

With MAT transistors, featherweight hi-hi quality earpiece, all parts, royal blue and gold case and instructions, it costs only

**49/6**

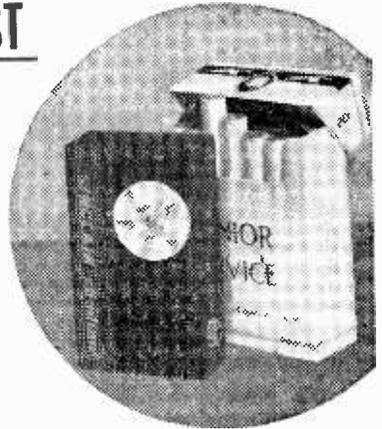

### SMALLER THAN A 3d. PIECE SINCLAIR MICRO-AMP




Build it for only

**28/6**

The Sinclair Micro-amp is now widely used throughout the Electronics Industry.


### BOOKS FOR BUILDERS

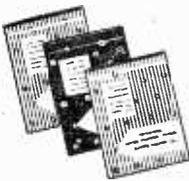

- GENERAL "22 Tested Circuits using Micro-Alloy Transistors" Post free 5/6
- SHORT WAVES "Tested Short Wave Receivers Using MATs." Post free 5/6
- S.W. & COMMUNICATIONS "Tested Superhet Circuits for Shortwave and Communication Receivers, using MATs." Post free 6/6
- SPECIAL PRICE FOR 3 TOGETHER..... 16/-

### SINCLAIR QUALITY TRANSISTORS

|  |      |
|--|------|
| MAT 100 High gain low level .....  | 7/9  |
| MAT 101 Extra high gain, low level .....   | 8/6  |
| MAT 120 High gain, medium and high level .....   | 7/9  |
| MAT 121 Extra high gain, medium and high level .....   | 8/8  |
| ADT.140 FOR V.H.F. and U.H.F. Suitable for F.M., T.V., V.H.F. and U.H.F. frequencies Typical alpha cut-off of 400 Mc/s ..... | 15/- |

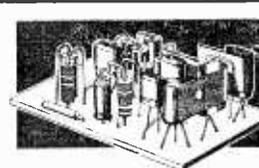

### SINCLAIR TR.5 VERSATILE 1/2 WATT AMP WITH PRE-AMP STAGE


For a perfectly clean half watt of audio power even from very low output tape heads, pick-ups and microphones. Ready built with instructions and unconditionally guaranteed.

POWER GAIN—90 dB (100 million times)  
FREQUENCY—50 c/s to 20 kc/s ± 3 dB.  
SIZE 2½ x 1½ x ¾ in.  
POWER REQUIREMENTS —9V.  
READY BUILT AND TESTED **59/6**

CIRCUIT—5 matched transistors and temperature compensating diode in a transformerless complementary-symmetry configuration.  
POWER OUTPUT—500 mW into 15 ohms.  
SENSITIVITY—0.5 mV.
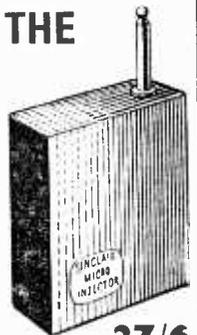
### FAULT TRACING THE MODERN WAY

Here is the modern and efficient way to trace faults in valve and transistor audio and radio equipment of all kinds. This precision sub-miniature instrument generates and injects a signal into any part of the equipment to be tested at a frequency from 1 Kc/s to 30 Mc/s. The 6d. standard battery which it uses will last for about 3 months. Building is extremely easy with the help of the instructions provided. With neat, well-made plastic case and all parts except battery. 1½ in. x 1½ in. x ¾ in. plus probe ¾ in. long.



### BUILD YOUR OWN SINCLAIR MICRO-INJECTOR AND SAVE POUNDS

Also available ready built and tested. 32/6.

**27/6**

### SINCLAIR MICRO-6—See preceding 2 pages

- ALL ITEMS FULLY GUARANTEED
- FULL SERVICE FACILITIES AVAILABLE
- PROMPT ATTENTION TO ALL ORDERS

## SINCLAIR RADIONICS LTD 69 HISTON ROAD, CAMBRIDGE

If you do not wish to cut this page, please mention "Practical Wireless" March, when ordering.

Sinclair Radionics Ltd., 69 Histon Rd., Cambridge

Please send .....

..... For which I enclose £.....s.....d.

NAME .....

ADDRESS .....

PW.3 .....

# THE R.S.C. BASS-MAJOR 30 WATT GUITAR AMPLIFIER

A MULTI-PURPOSE HIGH FIDELITY, HIGH OUTPUT UNIT FOR VOCAL AND INSTRUMENTALIST GROUPS

*Eminently suitable for bass, lead or rhythm guitar and all other musical instruments*

- ★ Incorporating two 12in. heavy duty 25-watt high flux (17,000 lines) loudspeakers with 2in. diameter speech coils. Designed for efficiently handling full output of amplifier at frequencies down to 25 c.p.s.
- ★ Dual Cone in second speaker reproduces frequencies up to 17,000 c.p.s.
- ★ Heavily made cabinet of convenient size 24 x 21 x 14in. has an exceptionally attractive covering in two contrasting tones of Vynair.
- ★ For 200-250 v. to 50 c.p.s. A.C. mains operation.
- ★ Four jack socket inputs and two independent vol. controls for simultaneous connection of up to four instrument pick-ups or microphones.
- ★ Separate bass and treble controls providing more than adequate "Boost" or "Cut".
- ★ LEVEL frequency response throughout the audible range.
- ★ SUPERIOR TO UNITS AT TWICE THE COST.

**39<sup>1</sup>/<sub>2</sub> Gns.**

Send S.A.E. for leaflet.  
OR DEPOSIT of £43.0 and 12 monthly payments of £3.8.11. Carr. 17/6.



**R.S.C. JUNIOR GUITAR AMPLIFIER**  
5-watt high quality output. Separate bass and treble "cut" and "boost" controls. Sensitivity 15 m.v. Two high impedance inputs. 10in. loudspeaker. Handsome, strongly made cabinet (size 14 x 14 x 7in. approx.) finished in complementary shades of Rexine/Tygan. 200-250 A.C. mains.  
**£8.19.6** Or DEPOSIT £1 and 9 monthly payments of £1. Carr. 7/6.

**LINEAR TREMOLO/PREAMP. UNIT**  
Designed for introducing the Tremolo effect to any amplifier which is fitted with a reserve power supply point for smoothed H.T. and 6.3 v. A.C. L.T. This applies to practically all amplifiers of our manufacture, and to those of several other manufacturers. The unit plugs into power supply point and any input socket or amplifier. Controls are Speed (frequency of interruptions), Depth (for heavy or light effect), Volume and Switch. Three sockets are for two inputs and Foot Switch. **4 Gns.** ONLY

## R.S.C. SENIOR 15 WATT LEAD or RHYTHM GUITAR AMPLIFIER

High-fidelity push-pull output. Separate bass and treble "cut" and "boost" controls. Twin separately controlled inputs so that two instruments or "mike" and pick-up can be used at the same time. Loudspeaker is a heavy duty high flux 12in. 20 watt model with cast chassis. Cabinet is well made and finished as Junior Model. Size approx. 18 x 18 x 8in.

Only **18 Gns.** Carr. 10/-

Send S.A.E. for leaflet, OR DEPOSIT 35/- and twelve monthly payments of 35/-.

## R.S.C. B20 BASS GUITAR AMPLIFIER

A highly efficient unit incorporating a massive 15in. high flux loudspeaker specially constructed to withstand heaviest load conditions. Rating 25 watts. Individual bass and treble controls give ample "boost" and "cut". Two high impedance jack socket inputs are separately controlled. All controls are conveniently positioned in a recess on top of the cabinet. Cabinet is of substantial construction and attractively finished in two contrasting tones of Rexine and Vynair. Size approx. 24 x 21 x 13in. Operation from 200-250 v. 50 c.p.s. A.C. mains.



Send S.A.E. for leaflet.  
**29<sup>1</sup>/<sub>2</sub> Gns.** Or Deposit £23.0 and 12 monthly payments of 56/10. Carr. 17/6.

## GLASGOW — LONDON — EDINBURGH

326 ARGYLE STREET 238 EDGWARE ROAD 133 LEITH STREET  
Three new branches opening early March

**TRANSISTOR SALE.** Mullard OC71 3/9, OC45 4/11, OC44 4/11, OC72 4/9, OC81 4/11, OC171 8/9, Ediswan XA101 3/9, XB102 3/9, XA112 3/9, XB113 3/9, XB104 3/9, XC101A 3/9. Postage 6d. for up to 3 Transistors.

**D.C. SUPPLY KIT.** 12 v. 1 a. consisting of a partially drilled metal case, mains trans., F.W. Bridge Rectifier, 2 fuseholders and fuses, Change Direction switch, variable Speed regulator and circuit. For 200-250 v. A.C. mains. Suitable for Electric Trains. Limited number available at 29/11.

**SELENIUM RECTIFIERS**  
F.W. BRIDGE 24 v. 2 amp. .. 14/9  
6/12 v. 1 a. .. 3/11 24 v. 20 amp. .. 89/9  
6/12 v. 2 a. .. 6/11 H.T. TYPES H.W.  
6/12 v. 3 a. .. 9/9 150 v. 40 mA .. 3/9  
6/12 v. 4 a. .. 12/3 250 v. 50 mA .. 3/11  
6/12 v. 8 a. .. 15/3 250 v. 60 mA .. 4/11  
6/12 v. 10 a. .. 26/9 250 v. 80 mA .. 5/11  
6/12 v. 15 a. .. 35/9 250 v. 250 mA .. 11/9  
**CONTACT COOLED.** 250 v. 75 mA. F.W. (Bridge) 10/11. 250 v. 50 mA. F.W. (Bridge) 8/11. H.W. 250 v. 60 mA. 5/11.

**HI-FI 10-WATT AMPLIFIERS.**  
Brand New Complete **£7.19.9** Carr. 5/6  
Units.  
Manufacturers' discontinued Model. Full output. Latest high efficiency valves. Dual separately controlled inputs for "Mike". Separate Bass and Treble Controls. High sensitivity. Output for 3 or 15 ohm speaker. Guaranteed tested and in perfect working order.

**HEAVY DUTY LOUDSPEAKERS IN CABINET.** Type B21. Suitable for Bass Guitar. Speaker Unit 15in. High Flux. 15 ohms, 30 watts. Cabinet size approx. 24 x 21 x 13in. Only 18/9 Gns. Or Deposit 37/6 and 12 monthly payments of 37/6.  
Type B22. Suitable Bass and Lead Guitar. Two 12in. high flux 15 ohm 25 watt speakers, one with aluminium speech coil and dual cone to provide smooth frequency response from 25 to 17,000 c.p.s. Cabinet size approx. 30 x 21 x 14in. Covered in two contrasting tones of grey Vynair and Rexine. Rating 50 watts. Only 29 Gns. Or Deposit £3.7.6 and 12 monthly payments of 50/-.

**LARGE REXINE COVERED SPEAKER CABINETS.** Heavy blackboard construction. Very attractive two tone covering output for 15in. or 18in. speaker or for two 12in. 11 Gns. or Deposit 25/9 and 9 monthly payments 25/9. Size 30 x 30 x 16in. cut for 15in. or 18in. speaker 13 Gns. or Deposit 30/4 and 9 monthly payments 30/4. Suitable speakers available.

**FANE EXTRA HEAVY DUTY LOUDSPEAKER 15in. TYPE 153.** 40 watts. Total flux 375,000 lines. Extremely high sensitivity. 15 ohm voice coil. Only 18 Gns. or Deposit 35/- and 12 monthly payments 35/-.

**FANE EXTRA HEAVY L/SPEAKER 183.** 18in., 15 ohms, 60 watts, 3in. diam. Speech Coil. Total Flux 375,000 lines. High sensitivity. ONLY 24 Gns. or Deposit 51/- and 12 monthly payments of 42/9. Send S.A.E. for leaflet on 153 and 183.

**EX. GOVT. SMOOTHING CHOKES.**  
200 mA, 3-5 H., 50 ohms. Farmeko 8/9.  
150 mA, 10 H., 50 ohms 9/9; 80 mA, 20 H., 900 ohms 5/9; 120 mA, 12 H., 100 ohms 8/9; 50 mA, 50 H., 1,000 ohms 6/9; 100 mA, 10 H., 100 ohms 6/9; 60 mA, 5-10 H., 250 ohms 2/11.

**COMPLETE POWER PACK KIT, 19/11**  
Consisting of Mains Trans., Metal Rectifier, Double electrolytic, smoothing choke chassis and circuit. For 200-250 v. A.C. mains. Output 250 v., 60 mA, 6.3 v., 2 a.

**R.S.C. POWER PACK, 39/9.** Louvred metal case only 8 x 5 1/4 x 2 1/4in. Stove enamelled. For 200-250 v. A.C. mains. Output at 4 pin plug and socket 250 v., 60 mA, fully smoothed and 6.3 v., 2 a. Suitable for power requirements of almost any Pre-amp. or Radio Tuner.

**R.S.C. BABY ALARM or INTER-COMM. KIT.** Complete set of parts with diagrams, etc. Housed in two polished walnut finished cabinets of pleasing design. High sensitivity. For 200-250 v. A.C. mains. Fully isolated. Controllable at both units. An intercomm. of this class would normally cost £20-£30. Only 89/6, carr. 5/- or assembled ready for use 6 Gns.



**EX. GOVT. SELENIUM RECTIFIERS 12v. 15 AMP 19/9 (BRIDGE) F.W. ONLY**

## DERBY

Now open at  
26 Osmaston Road  
The Spot

## R.S.C. (Manchester) Ltd.

MAIL ORDERS to 5 County Arcade, Leeds 1. Terms: C.W.O. or C.O.D. No C.O.D. under £1. Postage 2/9 extra under £2. 4/6 extra under £5. Trade Supplied. S.A.E. with all enquiries please.

**LEICESTER** 32 High St.  
**BIRMINGHAM** 6 Gt. Western Arcade, Opp. Snow Hill Station  
Half-day Thursday  
No half-day

**SHEFFIELD** 13 Exchange St. (Castle Market Bldgs.) Sheffield  
Half-day Thursday

**HULL** 51 Savile St., Hull

**LIVERPOOL** 73 Dale St. Liverpool 2  
Half-day Wednesday

**BRADFORD** 56 Morley St. (above Alhambra Theatre) Bradford

**MANCHESTER** 8-10 Brown St. (Market Street) Manchester 2  
No half-day

**LEEDS** 5-7 County (Mecca) Arcade Briggate, Leeds  
No half-day

**R.S.C.** (Manchester) Ltd. MAIL ORDERS to 5 County Arcade, Leeds 1. Terms: C.W.O. or C.O.D. No C.O.D. under £1. Postage 21/9 extra under £2. 4/6 extra under £5. Trade Supplied. S.A.E. with all enquiries please.

|   |  |  |   |  |   |   |  |
|---|--|--|---|--|---|---|--|
| <b>LEICESTER</b><br>32 High St.<br>Half-day<br>Thursday | <b>BIRMINGHAM</b><br>6 Gt. Western<br>Arcade, Opp.<br>Snow Hill Station<br>No half-day | <b>SHEFFIELD</b><br>13 Exchange St.<br>(Castle Market<br>Bldgs.) Sheffield<br>Half-day | <b>HULL</b><br>51 Savile<br>St., Hull<br>Thursday | <b>LIVERPOOL</b><br>73 Dale St.<br>Liverpool 2<br>Half-day | <b>BRADFORD</b><br>56 Morley St.<br>(above Alhambra<br>Theatre) Bradford<br>Wednesday | <b>MANCHESTER</b><br>8-10 Brown St.<br>(Market Street)<br>Manchester 2<br>No half-day | <b>LEEDS</b><br>5-7 County<br>(Mecca) Arcade<br>Briggate, Leeds<br>No half-day |
|---|--|--|---|--|---|---|--|

**DERBY 26** Osaston Road  
**THE SPOT**

**FANE HEAVY DUTY HI-FI SPEAKERS**

12in. 15 ohms. Cast chassis. Exceptionally robust 2in. diam. Voice Coil Assemblies. 12/10 20watt, 8 gns. 12/20/10A 20watt, 8 gns. 12/21/20watt, 8 gns. 12/12A 20watt, £7.19.8. 12/21/4 22watt, 11 gns. 12/14A 22watt, 10 gns. 12/17 25watt, 11 gns. 12/17A 25watt, 12 gns. 15in. 15 ohms. Cast chassis. Exceptionally robust 2in. diam. Voice Coil Assemblies. 15/12 20watt, 12 gns. 15/12A 20watt, 13 gns. 15/14 27watt, 14 gns. 15/14A 27watt, 15 gns. 15/17 35watt, 16 gns. 15/17A 35watt, 17 gns. "A" indicates dual cone type, 30/17/00 c.p.s. Send S.A.E. for leaflets. Terms available.

**R.S.C. 30-WATT ULTRA LINEAR HIGH FIDELITY AMPLIFIER A10**

A highly sensitive Push-Pull high output unit with self-contained Pre-amp. Tone Control Stages. Certified performance figures compare equally with most expensive amplifiers available. Hum level 70 dB down. Frequency response +3 dB 30-30,000 c/s. A specially designed sectionally wound ultra linear output transformer is used with 800 output valves. All components are chosen for reliability. Six valves are used EF86, EF86, ECC83, 807, 807, GZ31. Separate Bass and Treble Controls are provided. Minimum input required for full output is only 12 millivolts so that ANY KIND OF MICROPHONE OR PICK-UP IS SUITABLE. The unit is designed for CLUBS, SCHOOLS, THEATRES, DANCE HALLS or OUTDOOR FUNCTIONS, etc. For use with ELECTRONIC ORGAN, GUITAR, STRING BASS, etc. For standard or long-playing records. OUTPUT SOCKET PROVIDES L.F. and H.T. for RADIO FEEDER UNIT. An extra input with separate input control is provided so that two separate inputs such as Gram and "Mike" can be mixed. Amplifier operates on 200-250 v. 50 c/s. A.C. Mains and has output for 15 and 15 ohm speakers. Complete kit of parts with fully punched chassis and point-to-point wiring diagrams and full instructions. If required perforated cover with carry handles can be supplied Carr. 10/- for 19/9. The amplifier can be supplied, factory built with EL34 output valves and 12 months' guarantee, for 14 gns. Send S.A.E. for leaflet.

**TERMS: DEPOSIT 33/9 and 9 monthly payments of 33/9.**

Suitable microphones and speakers available at competitive prices.

**ARMSTRONG, DULCI, LINEAR, ROGERS, LEAK and JASON EQUIPMENT, GOODMAN'S, W.B. and FANE SPEAKERS, GARRARD AND GOLDRING T/ABLES CASH or H.P.**

**SUPERHET FEEDER UNIT.** Design of a high quality Radio Tuner specially suitable for use with our Amplifiers. Delayed A.V.C. Controls are Tuning, W/Ch. and Vol. Only 250 v. 15 mA. H.T. and L.T. of 3 v. an.p. required from amplifier. Size approx. 9 x 6 x 7in. High. Simple alignment procedure. Point-to-Point wiring diagrams, instructions and priced parts list with illustrations. 2/6. Total building cost £4.15.0. S.A.E. for leaflet.

**R.S.C. BATTERY TO MAINS CONVERSION UNITS**

Type BM2. Size 8 x 5 1/2 x 2 1/2in. Supplies 120 v. 90 v. and 60 v. 40 mA and 2 v. 0.4 a. to 1 amp. fully smoothed. Thereby completely replacing both H.T. batteries and 2 v. accumulators when connected to A.C. mains supply 200/500 v. 50 c/s SUITABLE FOR ALL BATTERY RECEIVERS normally using 2 v. accumulators. Complete kit of parts with diagrams and instructions. 4/9/9, or ready for use, 5/9/6



Kit of parts with diagrams and instructions. 4/9/9, or ready for use, 5/9/6

P.M. SPEAKERS. 10in. W.B. "Stentorian" 30 or 15 ohms type 1F 1012 10 watts hi-fidelity type. Recommended for use with our All Amplifier. £4.7.8. 12in. R.A. 3 ohms 10 watts (12,000 lines). 5/9/8.

TWEETERS. R.A. 3ohm, 19/11; 15 ohm. 25/9

R.A. 12in. DUAL CONE 3 ohm x watt Speakers. Ideal for Stereo. Only 39/9 ea.

JASON FATTI V.H.F./M. Radio Tuner design. Total cost of parts including valves, Tuning dial, Escutcheon, etc., £8.19.6.

**LINEAR 1.45 MINIATURE 4/5 WATT QUALITY AMPLIFIER.** Suitable for any record playing unit and most microphones. Negative feed-back 12 dB. Separate Bass and Treble Controls. For mains 200-250 v. 50 c/s. Output for 2-3 ohm speaker. Mullard valves EZ80, ECC83, EL84. Size only 17 x 5 x 5 1/2in. high. Guaranteed 12 months. Only £5.19.6. Send S.A.E. for leaflet. Terms: Deposit 22/6 and 5 monthly payments of 22/6.

**R.S.C. 4.5 WATT A5 HIGH-GAIN AMPLIFIER**



A highly-sensitive 4-valve quality amplifier for the home, small club, etc. Only 50 millivolts input is required for full output so that it is suitable for use with the latest hi-fidelity pick-ups and leads, in addition to all other types of pick-ups and practically all "mikes". Separate Bass and Treble Controls are provided. These give full long-playing record equalisation. Hum level is negligible being 71 dB down, 15 dB of Negative feedback is used. H.T. of 300 v. 35 mA and L.T. of 6.3 v. 1.5 a. is available for the supply of a Radio Feeder Unit, or Tape-Deck pre-amplifier. For A.C. mains input of 200-250 v. 50 c/s. Output for 2-3 ohm speaker. Chassis is fully punched with baseplate (included) with Blue Hammer finish and point-to-point wiring diagrams and instructions. Exceptional value at only £4.15.0, or assembled ready for use 25/- extra. Plus 3/6 carr., or deposit 22/6 and 5 monthly payments of 22/6 for assembled unit.

**GLASGOW — LONDON — EDINBURGH**

326 ARGYLE STREET 28 EDGWARE ROAD 133 LEITH STREET  
Three new branches opening early March

**THE SKYFOUR T.R.F. RECEIVER.** A design for a 3 valve long and medium wave 200-250 v. A.C. Mains receiver with selenium rectifier. High gain H.F. stage and low distortion detector. Valve line-up 6K7, SP61, 6V6G. Selectivity and quality excellent. Simple to construct. Point-to-point wiring diagrams, instructions and parts list 1/9, maximum build-up costs £4.19.6, inc. attractive walnut veneered wood cabinet 12 x 6 1/2 x 5 1/2in.

**R.S.C. BASS REFLEX CABINETS, JUNIOR MODEL.** Specially designed for W.B. HF1012 Speaker, but suitable for any good quality 10in. speaker. Acoustically lined and ported. Polished walnut veneer finish. Size 18 x 12 x 10in. Handsome appearance. Ensure superb reproduction for only £3.19.6.

**STANDARD MODEL.** As above but for 12in. speakers. Size 20 x 15 x 13in. Acoustically lined and ported. £5.19.6. Set of legs with brass ferrules, 1/9/6.

**R.S.C. JUNIOR HI-FI REPRODUCER.** The very latest Goodman Axiette 8 High Fidelity loudspeaker (retailing at approx. 5 gns.) fitted in a specially designed Bass Reflex cabinet size 12 x 18 x 10in. Acoustically lined and ported and finished in polished walnut veneer. Matching impedance 15 ohms. Frequency range 40-15,000 c.p.s. Power handling 6 watts nominal. 8 Gns. Carr. 4/6.

**2in. 10 WATT HIGH QUALITY LOUDSPEAKER**



In walnut veneered cabinet. Gauss 12,000 lines. Speech coil 3 ohms or 15 ohms. Only £4.19.6 Carr. 5/-. Terms: Deposit 11/3 and 9 monthly payments of 11/3.

**12in. 30 WATT HI-FI LOUDSPEAKERS.** Size 18 x 18 x 10in. Finish as above. Terms: Deposit 17/9 and 9 monthly payments of 17/9. Only £7.19.6. Carr. 8/6. For larger types see preceding page.

**LINEAR 1G34 GRAM AMPLIFIER.** High quality. Separate Bass and Treble controls. Handsome appearance. Completely enclosed. Black/Gold Frontplate 5 gns.

**MULTI-METER, CABY M1.** Sensitivity 2,000 ohms per volt. A.C. and D.C. 54/- A.10. Basic Meter sensitivity 155 microamps A.C. and D.C. ranges £4.17.6. B.30. Sensitivity up to 10,000 ohms per volt. A.C. and D.C. £8.10.0. 30,000 ohms per volt. with overload buzzer. £8.19.6.

**R.S.C. CORNER CONSOLE CABINETS**

Polished walnut veneer finish. Pleasing design. **JUNIOR MODEL.** Size 20 x 11 x 8in. for 8 x 5in. or 10 x 6in. speakers. £2.9.9.



**STANDARD MODEL.** Size 27 x 18 x 12in. for 8 or 10in. speakers. £4.11.6. **SENIOR MODEL.** Size 30 x 20 x 15in. for 12in. Speaker. Suitable Speaker systems below. Only 7 gns.

**AUDIOTRINE HI-FI SPEAKER SYSTEMS.** Consisting of matched 12,000 line 15 ohm high quality speaker; cross-over unit (consisting of choke, condenser, etc.) and Tweeter. The smooth response and extended frequency range ensure surprisingly realistic reproduction. Standard 10 watt rating £4.19.9. Carr. 5/-. Or Senior 15 watt. £8.19.9. Carr. 7/6.

**AUDIOTRINE EQUIPMENT CABINETS.**

Size 36 x 15 x 18in. Beautiful walnut veneer finish. Elegant contemporary design. Robust construction. Uncut, removable baseboard. Depth above baseboard 29in. Carr. 15/-. Terms: Dep. 25/9, and 9 monthly pmts 29/9



# AUDIOTRINE HI-FI TAPE RECORDER KIT 25½


GNS. Carr. 17/6.

**REALISM AT INCREDIBLY LOW COST, CAN BE ASSEMBLED IN AN HOUR.** Incorporating the latest Collaro Studio Tape Transcriber. The Audiotrine High Quality Tape Amplifier with negative feedback equalisation for each of 3 speeds. High Flux P.M. Speaker, empty Tape Spool, a Reel of Best Quality Tape and a Handsome Portable Carrying Cabinet with latest attractive two-tone polychrome finish, size 14½ x 15 x 4½ in. high and circuit. Total cost if purchased individually approximately £40. Performance equal to units in the £60-£80 class. S.A.E. for leaflets. **TERMS.** Deposit £2.13.9 and 12 monthly payments of 44/-. Cash price if settled in 3 months.

## HIGH FIDELITY 12-14 WATT AMPLIFIER TYPE A11

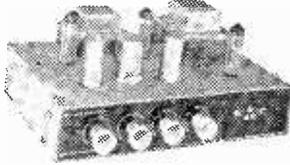**PUSH-PULL ULTRA LINEAR OUTPUT 'BUILT-IN' TONE CONTROL PRE-AMP STAGES**

Two input sockets with associated controls allow mixing of "mike" and gram., as in A10. High sensitivity. Includes 5 valves, ECC83, ECC83, EL84, EL84, E281. High Quality sectionally wound output transformer specially designed for Ultra Linear operation and reliable small condensers of current manufacture. **INDIVIDUAL CONTROLS FOR BASS AND TREBLE "Lift" and "Cut".** Frequency response ± 3 db 30-30,000 c/s. Six negative feedback loops. Hum level 60 db down. **ONLY 23 millivolts INPUT required for FULL OUTPUT.** Suitable for use with all makes and types of pick-ups and microphones. Comparable with the very best designs for **STANDARD or LONG PLAYING RECORDS.** For **MUSICAL INSTRUMENTS** such as **STEELING BASS, LEAD OR RHYTHM GUITARS,** etc. **OUTPUT SOCKET** with plug provides 300 v. 30 mA. and 6.3 v. 1.5 a. For supply of a **RADIO FEEDER UNIT.** Size approx. 12 x 9 x 7 in. For A.C. mains 200-250 v. 50 c.p.s. Output for 3 and 15 ohms speakers. Kit is complete to last nut. Chassis is fully punched. Full instructions and point-to-point wiring diagrams supplied. **Only 8 Gns. Carr. 10/-.** (Or factory built 5/11 extra.)



If required louvred metal cover with 2 carrying handles can be supplied for 18/9. **TERMS ON ASSEMBLED UNITS.** DEPOSIT 24/9 and 9 monthly payments of 24/9. Send S.A.E. for illustrated leaflet detailing Cabinets, Speakers, Microphones, etc., with cash and credit terms.

**LINEAR TAPE PRE-AMPLIFIER.** Type LP1, Switched Negative feedback equalisation. Positions for Record 11in., 3½in., 7½in. and Playback. EM84 Recording Level Indicator. Designed primarily as the link between a Collaro Tape Transcriber and a high fidelity amplifier, but suitable for almost any Tape Deck. **Only 9 gns. S.A.E. for leaflet.**

## R.S.C. STEREO/TEN HIGH QUALITY AMPLIFIER



A complete set of parts for the construction of a stereophonic amplifier giving 5 watts high quality output on each channel (total 10 watts). Sensitivity is 50 millivolts. Suitable for all crystal stereo heads. Ganged Bass and Treble Control give equal variation of "lift" and "cut". Provision is made for use as straight (monaural) 10-watt amplifier. Valve line-up ECC83, ECC83, EL84, EL84, E281. Outputs for 2-3 ohm speakers. Point-to-point wiring diagrams and in-structions supplied. Send S.A.E. for leaflet. Full constructional details and price list 2/6. Carr. 10/-.

Kit can be supplied assembled and ready to use for 59/6 extra.


## SENSATIONAL STEREO OFFER

A complete set of parts to construct a good quality Stereo amplifier with an undistorted output total 8 watts. For A.C. mains input of 200-250 v. Sensitivity 130 m.v. Ganged Vol. and Tone Controls. Preset balance control. Full instructions and wiring diagrams supplied. Stereo Pick-up Head 19/9 extra with above only.

**HEAVY DUTY CHARGER KIT.** 6/12 v. 6 amps., variable output. 250-0-250v. 100mA. 6.3v. 2a. Mains Transformer 0-200-230-250 v. F.W. Bridge, Selenium Rectifier, Ammeter, Variable Charge Rate Selector Panels, Plugs, Fuses. Fuseholder and circuit. 59/9. Carr. 4/6.

## R.S.C. BATTERY CHARGING EQUIPMENT

Guaranteed 12 months.

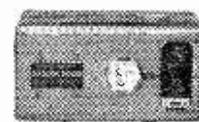

charging. Louvred steel case with stoved grey hammer finish. Fused and ready for use with mains and output 59/9 leads and battery clips. Carr. 4/6.

All for A.C. Mains 200-250 v., 50 c/s.

**ASSEMBLED 4 amps 6/12 v., 6/12 v. 2 amps. 6/12 v. 2 amps. 6/12 v. 2 amps.** Fused, ready for use with mains and output leads. Carr. 39/9. Less meter. 6/12v. 1 amp. 27/9.

**ASSEMBLED 6/12 v. 2 amps.** Fused, ready for use with mains and output leads. Carr. 39/9. Less meter. 6/12v. 1 amp. 27/9.

**CHARGER KIT, 12 v. 14 AMP or 24 v. 7 AMP** Consisting of mains trans. 200-230-250 v. F.W. (Bridge) selenium Rectifier, Ammeter, Fuses, Variable Resistor, Heavy Steel Stove enamelled case and Circuit. **Only £9.19.6.** Carr. 15/-. Please state if 12 v. or 24 v. kit required.

**BATTERY CHARGER KITS** Consisting of Mains Transformer, F.W. Bridge, Metal Rectifier, well ventilated steel case. Fuses. Fuse-holder. Chromes, panels, Heavy Duty Clip, circuit. Carr. 3/6 extra.  
6v. or 12v. 1 amp. .... 22/9  
As above, with Ammeter. . . 28/9  
6 v. 2 amps. .... 19/9  
6 v. or 12 v. 2 amps. .... 25/9  
6 v. or 12 v. 2 amps. including Ammeter. .... 35/9  
6 v. or 12 v. 4 amps. with Ammeter and variable charge rate selector. .... 52/9

**CHARGER AMMETERS** 0-1.5 a., 0-4 a., 0-7 a. 8/9 ea.

**CHARGER KIT, 12v. 10 Amp.** with variable charge rate adjustment and ammeter. 24.19.6. Carr. 10/-.

## R.S.C. MAINS TRANSFORMERS (FULLY GUARANTEED)

Interleaved and Impregnated. Primaries 200-230-250 v. 50 c/s. Screened

**TOP SHROUDED DROP THROUGH**  
250-0-250v. 70mA. 6.3v. 2a. 0.5-6.3v. 2a. 17/9  
350-0-350v. 80mA. 6.3v. 2a. 0.5-6.3v. 2a. 18/9  
250-0-250v. 100mA. 6.3v. 2a. 6.3v. 1a. 21/9  
250-0-250v. 100mA. 6.3v. 4a. C.T. 5v. 3a. 19/9  
250-0-250v. 100mA. 6.3v. 4a. 0.5-6.3v. 3a. 25/9  
300-0-300v. 130mA. 6.3v. 4a. 6.3v. 1a. (or Mullard 510 Amplifier) 29/9  
300-0-300v. 100mA. 6.3v. 4a. 0.5-6.3v. 3a. 26/9  
350-0-350v. 100mA. 6.3v. 4a. 0.5-6.3v. 3a. 26/9  
350-0-350v. 150mA. 6.3v. 4a. 0.5-6.3v. 3a. 29/9

**FULLY SHROUDED UPRIGHT**  
250-0-250v. 60mA. 6.3v. 2a. 0.5-6.3v. 2a. 17/11  
Midget type 2½ x 3 3in. 27/9  
250-0-250v. 100mA. 6.3v. 4a. 0.5-6.3v. 3a. 27/9  
300-0-300v. 100mA. 6.3v. 4a. C.T. 5v. 3a. 27/9  
300-0-300v. 130mA. 6.3v. 4a. C.T. 5v. 3a. 27/9  
1a. for Mullard Amplifier 33/9  
350-0-350v. 100mA. 6.3v. 4a. 0.5-6.3v. 3a. 27/11  
350-0-350v. 150mA. 6.3v. 4a. 0.5-6.3v. 3a. 35/9

**MIDGET MAINS Primaries 200-250 v.**  
50 c/s. 250v. 60mA. 6.3v. 2a. . . . 11/9  
250-0-250v. 60mA. 6.3v. 2a. . . . 12/11  
Both above size 2½ x 2½ x 2½ in.

**FILAMENT TRANSFORMERS**  
All with 200-250v. 50 c/s primaries 6.3v.  
1.5a., 5/9; 6.3v. 2a., 7/6; 0-4-6.3v. 2a. 7/9;  
12v. 1a., 7/11; 6.3v. 3a. 8/11; 6.3v. 6a. 17/6;  
12v. 1.5a. twice. 13/6.

**SMOOTHING CHOKES**  
150mA. 7-10 H. 250 ohms. . . . 11/9  
100mA. 10H. 200 ohms . . . . 5/9  
80mA. 10H. 350 ohms . . . . 8/9  
60mA. 10H. 400 ohms . . . . 4/11

**CHARGER TRANSFORMERS**  
All with 200-230-250v. 50 c/s Primaries:  
0-9-15v. 1½, 12/9; 0-9-15v. 2a. 14/9; 0-9-15v. 3a. 16/9; 0-9-15v. 5a. 19/9; 0-9-15v. 6a. 23/9; 0-9-15v. 8a. 28/9.

**AUTO (Step up/Step down) TRANS.**  
0-110-120-230-250v. 50 c/s. 12v. 1a. 19/9; 250 watts. 39/9; 150 watts. 27/9.

**MICROPHONE TRANSFORMERS**  
120: 1 high grade, clamped, 8/9.

# BERNARDS BOOKS

**FOR CONSTRUCTORS FROM  
BEGINNERS TO EXPERTS**

*Hundreds of designs to choose from,  
and we stock all the parts required*

## SOME RECOMMENDED TITLES

| No. | TITLE  | PRICE<br>Post Free |
|-----|--|--------------------|
| 100 | Comprehensive Radio Valve Guide, Book 1. Covers all valves issued up to 1951, clearly classified, with connection and base diagrams. Includes many special types | 5/-                |
| 121 | Comprehensive Radio Valve Guide, Book 2, covers all valves between 1951-1954   | 5/-                |
| 138 | How to make Aerials for TV & VHF/FM Transmissions. Size 10 1/4 x 7 1/4 in.   | 2/6                |
| 143 | Comprehensive Radio Valve Guide, Book 3, covers all valves between 1954-1956   | 5/-                |
| 151 | Transistor Superhet Receivers. Over 50 complete circuit diagrams, servicing hints, technical specifications and equivalents list, etc.                           | 7/6                |
| 155 | Portable Transistor Radio and Radiogram. How to build one in an attractive cabinet.  | 2/6                |
| 156 | Transistor Circuits, Manual No. 1. How to build various radios, phone amplifier, etc.  | 2/6                |
| 157 | Comprehensive Radio Valve Guide, Book 4, covers all valves issued since 1956   | 5/-                |
| 163 | Transistor Circuits Manual No. 2. For more advanced equipment  | 2/6                |
| 167 | Transistor Circuits Manual No. 3   | 2/6                |
| 168 | Transistor Circuits Manual No. 4   | 2/6                |
| 170 | Transistor Circuits for Radio Controlled Models  | 7/6                |
| 171 | Super-sensitive Transistor Pocket Radio  | 3/6                |
| 172 | International Radio Stations List  | 2/6                |
| 173 | Practical Transistor Audio Amplifier, Book 1   | 3/6                |
| 174 | Transistor Subminiature Receivers  | 5/-                |
| 175 | Transistor Test Equipment and Servicing Manual   | 3/6                |
| 176 | Manual of Transistor Audio Amplifiers from 50 microwatt to 75 watt types   | 6/-                |
| 178 | Comprehensive Radio Valve Guide, Book 5 Covers all valves since 1960   | 6/-                |

(Note—the entire series includes TV and CR tubes, thyristor and other specials, and have about 900 illustrations per volume).

179 Transistor Circuits Manual No. 5. Contains many advanced designs 5/-  
 182 At-a-Glance Radio Valve & TV Tube Equivalents Manual. Over 8,000 types, cross-indexed 3/6  
 183 How to Receive Foreign TV Programmes on Your Set by Simple Modifications 5/-

All these books are expertly presented, well illustrated and generously provided with circuits and instructions where appropriate.

**SEND 6d.** for 16-page Catalogue of all Bernards Publications. Full range always in stock.  
**ALL BOOKS POST FREE - SEE ALSO PAGE 1034**

Orders by post to Mail Order Division.

# BEAR HUDSON LTD


63 GOLDHAWK RD., SHEPHERDS BUSH  
LONDON W.12

Next to Goldhawk Rd. Station, Met. Phone SHE 2581 and 4794  
 also at 11 JERDAN PLACE, FULHAM, LONDON S.W.6  
 (Fulham Broadway) Phone FUL. 3405

## HARVERSON SURPLUS CO. LTD.

For address see  
opposite page

### OUR LATEST BULK PURCHASE!

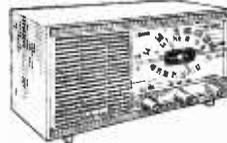

**BRAND NEW A.C. MAINS  
6 VALVE SUPERHET  
RADIO RECEIVER**  
 Housed in beautifully styled cabinets offering terrific performance and very high quality reproduction. Built-in ferrite rod aerial for reception of all your favourite programmes. Fully guaranteed.  
**MODEL 55** (as illus.). Covers Medium, Long and Short waves. Size 8 1/2 in. w. 3 1/2 in. d. x 4 1/2 in. h. **PRICE ONLY £7,17.8.**  
 P. & P. 5/6.

**MODEL 36.** Similar circuitry to above but covers Medium wave only. Size 7 1/2 in. w. x 3 1/2 in. d. x 4 1/2 in. h. **PRICE ONLY £4,14.8.** P. & P. 5/6.  
 Either of the above can be easily adapted for use as A.M. Feeder unit.

### 3-VALVE AUDIO AMPLIFIER. MODEL HA34



Designed for Hi-Fi reproduction of records A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2 in. w. x 4 1/2 in. d. Incorporates ECL82, EL54, EZ80 valves, heavy duty double wound mains transformer and output transformer matched for 8 ohm speaker, separate Bass, Treble and volume controls. Negative feedback line. Output 44 watts. Front panel can be detached and leads extended for remote mounting of controls.

The HA34 has been specially designed for us and our quantity order enables us to offer them complete with knobs valves, etc., wired and tested for only **£45.0** P. & P. 4/-  
**TWO VALVE AMPLIFIER** similar to above but using ECL82 and EZ80 with tone and volume controls. Output 3 watts. **PRICE 76/-.** P. & P. 4/-

### SPECIAL OFFER!

**MARCONI QUARTZ  
CRYSTALS TYPES ZHB**  
 Glass encapsulated, 2 wire lead out. Size 1 1/2 in. high x 1/2 in. dia. Following frequencies (Kcs) only available  
 13021, 13085, 13049, 13706  
 13771, 13838, 13905, 13908  
 14021, 14088, 14146, 14208  
 14271, 14338, 14396, 14459  
 6/- each. P. & P. 1/- per crystal, 3 or more Post Free.

### 4-SPEED PLAYER UNIT BARGAINS

All Brand New in Makers' Original Packing  
**SINGLE PLAYERS**  
 TU/12 £3.10.0 Carr. 3/6  
**AUTO CHANGERS**  
 B.S.R. CA14 £8.2.0  
 Latest B.S.R. CA16 £7.2.0  
**LATEST GARRARD AUTO-SLIM**  
 with heavy-duty 4-pole motor.  
**FEW ONLY £77.0** (standard Auto-Slim £6.17.8). Carr. 5/- on each.

### SPECIAL TRANSISTOR BARGAINS

**ALL BRAND NEW  
GET 15 (Matched Pair) 16/-**  
 OC71 .. 8/- PXA101 6/6  
 OC72 .. 6/- XA109 6/6  
 OC76 .. 6/- V15/10p 13/6  
 Set of Mullard 6 transistors, OC44, 2—OC45, OC81d matched pair OC81, 25/-  
**EDISWAN MAZDA**  
 R.F.1 Pack: 2—PXA102 Mixer; 2—PXA101 I.F. Amp.; (Equiv. OC44 and OC45) .. 10/6  
 R.F.2 Pack: 2—PXA101 I.F.; PXA102 Osc.; 1—PXA102 Mixer .. 12/6  
 L.F.6 Pack: Consisting of PXB113 Driver. Matched pair PXC171, mounted complete with heat sinks (Equiv. OC81d and OC81) .. 12/6  
**ALL TRANSISTORS POST FREE**

### CARTRIDGE BARGAINS!

**B.S.R. T088** High output compatible Stereo Cartridge. Brand New. Complete with Stereo/LE/78 capsule styl and universal mounting bracket. Original list price £4/11.0. **OUR PRICE 22/6.** P. & P. 1/-

### COLLARO HI-FI STEREO T/O CARTRIDGE


Type "G". Complete with universal bracket and styl for Stereo, LP and 78. Original list price 59/6. **OUR PRICE 26/-.** P. & P. 1/-

**ACOS GP80/1 T/O MONO CRYSTAL CARTRIDGE.** Comp. with suitable styl and mounting bracket. Limited number only at 12/6. P. & P. 1/-

### MARTIN RECORDAKITS

**Tape Amplifier for B.S.R. £8.8.0**  
 Deck. P. & P. 3/6  
 Cabinet with 7 x 4 in. speaker for above £4.4.0. Carr. and Ins. 5/-  
**Tape Amplifier for Collaro Studio Deck £11.1.0.** P. & P. 3/6.  
 Cabinets with 9 x 5 in. speaker for above, £6.5.0. Carr. and Ins. 5/-  
**Tape Pre-Amplifier for Collaro Studio deck, complete with power supplies, £2.8.0.** P. & P. 3/6. Full easy-to-follow instructions supplied.  
 Send S.A.E. for leaflet. Full range of Microphones and Tape always in stock.

FEW ONLY

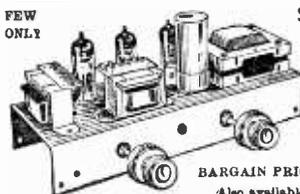

### STEREO AMPLIFIER

Incorporating 2 ECL82s and 1 EZ80, heavy duty, double wound mains transformer. Output 4 watts per channel. Full tone and volume controls. Absolutely complete.

**BARGAIN PRICE 89/6** P. & P. 5/-

Also available complete with two 8 x 5 in. Speakers for only £5.10.6. P. & P. 6/6.





# Service in Great Britain CONSTRUCTORS' BARGAINS

## LASKY'S NEW SCOOP The "Sixteen" Multirange METER KIT

This outstanding meter was featured by *Practical Wireless* in the Jan. '64 issue. Lasky's are now able to offer the complete kit of parts as specified by the designer. The "Sixteen" Multirange offers the home constructor and serviceman an instrument that will meet most of his requirements for voltage, current and resistance measurement. There are 16 switched ranges: 9 for voltage measurement, 4 current ranges and 3 resistance ranges. All British components are used throughout. The instrument case is supplied with the meter movement built-in. The two scales are clearly printed in black on white and are very easy to read.



This offer is exclusive to Lasky's Radio.

**LASKY'S PRICE**  
**£5.19.6** P. & P. 5/-

**RANGE SPECIFICATION:** D.C. volts: 0-2.5-25-50-250-500 at 20,000 Ω/V. A.C. volts: 0-25-50-250-500 at 1,000 Ω/V. D.C. current: 0-50 μA, 0-2.5-50-250 mA. Resistance: 0-2,000 Ω, 0-200 k Ω, 0-20 M Ω. Basic movement: 40 μA f.s.d. moving coil. With universal shunt full scale deflection current is 50 μA. Size/finish: Black plastic case, 3 1/2 x 5 1/2 x 1 1/2 in. Controls: 12 position range switch; separate slide switch for A.C. volts—D.C. ohms; ohms zero adjustment pot. meter; meter zero. External connections: Two 4mm. sockets for test lead plugs. Power requirements: One 15V. and one 1.5V. batteries. Complete with all parts and full construction details.

Data and circuit available separately 5/- refunded if all parts bought.

### TAPE DECK MOTORS



Motors for the Collaro Studio Deck—new and unused. 200-250 v. A.C. Take-up, rewinding and capstan. Listed at £2.5.0 each. **LASKY'S PRICE 14/11** each. P. & P. 2/6. Set of 3 35/-, P. & P. 6/-.

### U.H.F. TUNERS

Only a few available. Complete with PC36 and PC33 valves. We regret no circuit or data is available. **LASKY'S PRICE 59/6**. P. & P. 2/6.



# LASKY'S RADIO



### MAKERS SURPLUS FM TUNER CHASSIS

A factory built FM Tuner using the Gorrler front end unit and I.F.S. Freq. range: 88-108 Mc/s. Valve line-up: 6AL5, 3 x 6AU6, ECC85. Fully assembled on printed circuit. Illuminated glass dial. Overall size 12 x 5 x 3 in. Unpowered—requires 6.3 v. L.T. and 200 v. at 40 mA H.T. Full circuit data included.

**LASKY'S PRICE £5.19.6** P. & P. 6/-

### 4-SPEED AUTO CHANGERS

- B.S.R. Type UA14/UA20..... £5 19 6
  - COLLARO Studio C80 wired for stereo with Monaural..... £6 19 6
  - MAGNAVOX-COLLARO latest model, 4-speed Stereo Autochanger. Fitted diamond stylus and record dust cleaning attachment Stereo..... £7 19 6
  - GARRARD Auto-Slim Mono..... £6 10 0
  - Auto-Slim Stereo..... £7 10 0
  - Auto-Slim Mono Plug-in-head..... £7 7 0
  - Auto-Slim De Luxe Mono AT6..... £11 9 0
  - Auto-Slim De Luxe Stereo AT6..... £12 5 0
  - Lab. Model "A" Mono..... £18 14 0
  - Lab. Model "A" Stereo..... £20 10 0
- Postage on all above 5/-.

**H.M.V. 45 P.P.M. AUTOMATIC RECORD PLAYER.** Designed to take only 45 p.p.m. 7in. discs. Will play up to 8 automatically. Fitted with lightweight pick-up and crystal cartridge, mounted on a plinth. For 200/250 v. A.C. mains. Size approx. 10 x 10 x 3 in. **LASKY'S PRICE 69/6**. Post and packing 3/6 extra.

See opposite page for addresses

## The AMATEUR RADIO HANDBOOK

Third Edition

Contents include Fundamentals, Valves, Semi-conductors, H.F. Receivers, V.H.F./U.H.F. Receivers, H.F. Transmitters, V.H.F./U.H.F. Transmitters, Keying and Break-in, Modulation, Single Sideband, Frequency Modulation Propagation, H.F. Aerials, V.H.F. Aerials, Noise, Mobile Equipment, Power Supplies, Interference, Measurements, Operating Technique and Station Layout, the R.S.G.B. and General Data.

Bound in maroon linson buckram - - 544 pages  
700 diagrams and 100 half-tones

**PRICE 34/-** (Postage and packing 2/6)  
(£5.50 post paid U.S.A. and Canada)

Obtainable from leading booksellers or

(Dept. P.W.3)

## RADIO SOCIETY OF GREAT BRITAIN

28 Little Russell Street, London, W.C.1

## BARGAIN OFFER!

**AMPLIFIER.** 3 watts, 2 valves, 6X4, ECL82. AC Mains. Mounted on board with 8in. speaker, Pilot light and Tone Control. **£3.10.0** complete. Post 4/6.

**CONNECTING WIRE.** Stranded or Single. Various colours, our selection, 100ft., 4/-.

**ELECTROSTATIC Tweeter LSH75** with diagram, only 2/6 each.

**SPEAKER CABINET.** THE HAYDON (17 x 15 x 8in.). Designed to take a 12in. heavy duty speaker. Made of 3in. wood. Ideal for bass guitar. Covered with Vynide and Vynair in contrasting colours. With strong carrying handle, 60/-, post 7/6 extra.

**SPEAKER** suitable for above cabinet. R.T.C. 15 ohm 15 watts. Heavy duty 12in., £5, post 4/-.

**STEREO** Ronette S106, 25/-.

**CARTRIDGES.** Monaural. Acos GP59-5 high output, 15/-; Acos GP65-1G medium output, 15/-, to fit most Garrard, Collaro or B.S.R. pick-ups.

**EARPIECES** with cord and 3.5 mm. plug. Crystal, 4/-; 180 ohms magnetic, 6/6; 80 ohm 2.5 plug, 4/-.

**HIGH RESISTANCE PHONES:** 4,000 ohms. Chinese, 11/6 pair.

**TRANSISTOR ELECTROLYTICS:** 1uF, 2uF, 4uF, 5uF, 8uF, 16uF, 32uF, 50uF, 100uF, all 15 volt, 1/3 each.

**BARGAINS IN TRANSISTORS.** The latest Mullard M Series. OC44M, two OC45M, OC81DM. Two OC81M matched pair; OA30 diode. Complete set, 22/6. OC44, 3/6; OC45, 3/-; OC71, 2/6; OC72, 3/-; OA81, 2/3; GEC SE Good AF General Purpose, 2/-; GET873 RF, 2/3.

**McMICHAEL TELESCOPIC TV AERIAL.** 23" extending to 45". Fitted with coaxial plug. Will suit any set. **ONLY 7/6.**

**MAKE** your own light-sensitive switch: for parking lights, burglar alarms, model railways, door bells, window lights, etc., etc. The Circuit. Mullard ORP12 Light Cell, two transistors and resistors, 25/- the Set.


TERMS: C.W.O.

## BROADWAY ELECTRONICS

92 MITCHAM ROAD, TOOTING, S.W.17.

(four minutes from Tooting Broadway Underground Station)

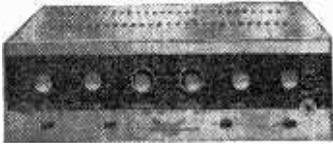**INTEGRATED STEREO AMPLIFIER**  
Model SA.300



Engineered for the professional... designed for the home. A completely new dual 15 watt stereo amplifier for professional quality reproduction, remarkable versatility, and new distinctive styling—worthy of a place in the finest stereo Hi-Fi system. A full range of front panel controls and switches permit adjusting volume, balance and tonal characteristics through every delicate shading of the entire audio range. Supplied complete with installation and operation manual. PRICE £29.10.0. S.A.E. for further details.

**CT.10 HORN TWEETER**



For true high fidelity reproduction of the upper, middle and top frequency ranges in multi-unit speaker installations. Pressure unit type utilizing a spun aluminium diaphragm. Output 10 watts. Frequency response 1500-1800 c.p.s. Impedance 16 ohm.

Finished in matt black, flanged and drilled for baffle mounting. PRICE 29/6

**HT.20 HORN TWEETER**

Designed for 2- and 3-way speaker systems, for smooth high-quality reproduction of the critical upper, middle and top frequencies. The operating system used is a pressure unit utilising a plastic domed voice coil wound with aluminium wire operating in a magnetic gap of high-flux density. Finished in stove enamelled gold with adjustable chrome base to permit mounting inside or on top of enclosures. Output: 20 watts. Response: 1500-18,000 c.p.s. Impedance: 16 ohm. Mounting: 4in. x 1 1/2in.



PRICE 69/6

**SF.20 RADIO EARPHONES**



Hi-impedance 2,000 ohms general use headset. Black and ivory plastic cased electro-magnetic units with adjustable headband for comfortable fit. Individual listening for all types of applications. Individually packed, with flexible cord attached.

PRICE 12/-

**MM.71. MINIATURE DESK OR HAND MAGNETIC MICROPHONE.**



Ideal for Tape Recorders, Intercoms, Amplifiers, Transmitters etc., where high quality at low cost is required. Complete with support and lead.

PRICE 12/6

**DM.614. 50K DYNAMIC SUPER SENSITIVE DESK OR NECK MICROPHONE.**

Never before such high quality at such low price. Complete with lavalier cord and desk stand. Lightweight. PRICE 45/-. Complete in presentation pack.



**MINIATURE PORTABLE TAPE RECORDER MODEL TC.601**

- ★ Fully transistorised.
- ★ Dual track.




- ★ Combined microphone/speaker.
- ★ Size only 10 1/2" x 3 1/2" x 2 1/2".

Completely portable, self-contained, full function miniature tape recorder utilising advanced transistor circuitry with 4-transistor push-pull output stage to give you quality reproduction you would only expect from units three times the price. Simple control for rewind/stop/playback/record, and variable volume control. Attractive tan and gold high impact poly-vinyl case with transparent snap-on plexiglass top enabling unit to be operated with top in position. Complete with dual purpose microphone/speaker. 200 ft. of tape, batteries and instruction book.

PRICE £8.19.6

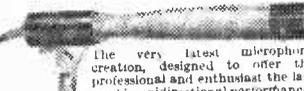**UD.19HL UNIDIRECTIONAL DYNAMIC MICROPHONE**



The very latest microphone creation, designed to offer the professional and enthusiast the last word in unidirectional performance.

Designed to provide the speed component from the periphery, thus eliminating all previous common unidirectional design defects. Exclusive features include high sensitivity and excellent frequency characteristics achieved by use of an aluminium wire voice coil. High stability by use of polyester film for the diaphragm. Extremely effective in minimising feedback problems. Dual high and low impedance, swivel adaptor and shielded cable. PRICE £14.14.0.

**DS.1 MICROPHONE DESK STAND**

5 in. dia., grey plastic base. 3 1/2 x 1/2 in. dia. rod (27 thread).

PRICE 10/6



**AMT.31 3-TRANSISTOR SUB-MINIATURE AM TUNER**

Covers full broadcast band. 4 transformers—2 1F and 1 0.5c. Ferrite rod aerial. Completely wired superhet circuit on printed circuit board. Complete with instructions. PRICE 64/1.

**MINIATURE EARPHONES**

Fully guaranteed and complete with 3 feet cord, sub-miniature plug and socket, CB-9 High Imp. crystal or MB-4 Low Imp. magnetic.

ONLY 4/6 each. Post Paid.



**TAPE SPLICER AND CUTTER MODEL T.635**



Cuts 2 rounded indentations in the tape splice leaving the edges of the tape which contact parts of the recorder entirely free of adhesive. As little as 1/16 in. tape need be removed. Complete with instructions. PRICE 15/-


**SIGNAL INJECTION PROBE IT.1**

Push button operation ideal for making rapid checks on radios, TV, Amps, tuners, etc. PRICE 39/6



**4-TRANSISTOR PUSH-PULL AUDIO AMPLIFIER**

Model EG.2004

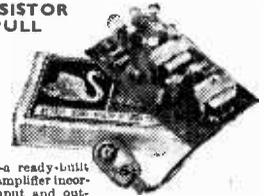

Not a kit—a ready-built miniature amplifier incorporating input and output transformers, 4 transistors, 9 volt battery snap cord (for Power), speaker and volume control connection leads. The most useful amplifier ever produced. Complete with full instructions and circuit diagram. Ideal for making professional tape recorders, baby alarm record players, intercoms etc. Must be heard to be appreciated.

ONLY 42/6

**MM.4 4-CHANNEL TRANSISTORISED MICROPHONE MIXER**



Add musical highlights and additional sound effects to your recordings. The MM-4 permits mixing of four signals such as microphone, records, tuner, etc. into a single output. Inputs and output take standard plugs. Fully transistorised and self-contained in handsome case.

PRICE ONLY 59/6


**8" DOUBLE CONE HI-FI SPEAKER Model 8A7**



Frequency range 50-16,000 c/s. Lowest resonance 60 + 15 e/s. Sensitivity 98dB. Programme source input 8 watts. Voice coil impedance 16 ohms. Nett weight 870 grammes. BRAND NEW AND GUARANTEED.

PRICE 78/6

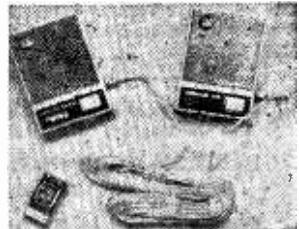**HANDY TWO-STATION TRANSISTORISED INTERCOM AND BABY ALARM MODEL TI.206**



89/6 Fully Guaranteed. Fantastic Value.

Complete with battery and 50ft. of wire. An intercom system for both calling and conversing operated from a single battery. Ideal Baby Alarm. S.A.E. for further details.



The Leading Mail Order House for Quality Electronic Products



**NOW ONLY 24/6**

With the **R330 RADIO AMPLIFIER**

Designed for use with transistor radios, valve radios, car radios, amplifiers, where quality reproduction of sound is required. Plugs into earpiece output socket of nearly all miniature sets. The cabinet is finished in beige leather with contemporary gold baffles at each end. Complete with 12ft. extension cord fitted with miniature plugs, individually cartoned and guaranteed. Size: 9 1/2 in. x 3 1/4 in. diameter.

**9V BATTERY CHARGER AND AC ELIMINATOR MODEL LA.6P**

A "REU" for every transistor set owner! Save these batteries by running your transistor set directly from A.C. mains. Reactivate all your old PP3 batteries. Unit contains neop indicator and standard battery connections with nearly 2 yards of mains leads and plug. Also snap cord for connection to set.

**NOW ONLY 24/6**



**MT.1000 TAPE RECORDER**

The smoothest performing battery model available, uses 4 transistor plus diode push-pull amplifier with built in speaker stop/record/playback/rewind switch, volume control, speed control, pause switch. Size only 7 1/2 x 6 1/2 x 3 1/2 in. Attractive two-tone case. Complete with mike, earphone, batteries, tape and instruction manual. **NOW ONLY 28.10.6.**

Complete with mike, earphone, batteries, tape and instruction manual. **NOW ONLY 28.10.6.**

**TD.79. TAPE HEAD DEMAGNETIZER**

The TD.79 is a compact easy to handle, truly professional quality tape head demagnetizer to completely remove magnetism from tape heads, permitting improved tape recordings and through frequent use reduces harmonic distortion and noise level. 250 v. AC complete with instructions. **PRICE 29/6.**

**3-WAY SLIM CRYSTAL MICROPHONE**

**MODEL 100C.** May be hand-held, floor stand or desk stand mounted or suspended by lanyard cord. Response 50-10,000 cps. Built in on/off switch. Output level—20dB. Omni-directional head. Clips on or off standard stand adaptor permitting tilting for multi-angle use. Beads chrome finish. Supplied complete with 100C stand, cable and lanyard cord. **PRICE 48/6.**

**FE.3. TELESCOPIC FLOOR STAND.** 3 section chrome plated with heavy base. **27/6.**

**10,000 O.P.V. MULTI-METER IN SEMI-ASSEMBLED KIT FORM**



**ONLY 69/6**  
**RANGES:** D.C. voltage 0-6-30-120-600-1,000 v. (10,000 o.p.v.). A.C. voltage: 0-6-30-120-600-1,200 v. (10,000 o.p.v.). D.C. Current: 0-120μA, 0-12-300 mA Resistance: 0-20K, 0-2 Meg. (100 ohm, 15K at centre scale). Decibels: -50 to +63dB (600 ohms 1 mW, odBm=0.775 v.). Accuracy: D.C. voltage and current ±2% f.s. A.C. voltage ±4% f.s.

Resistance ±3% of total scale length. Size: 4 1/2 in. x 3 1/2 in. x 1 in. Complete with test leads, battery and instructions.

**MODEL TK20A 1,000 O.P.V. ON AC and DC**



Extremely compact wide range multi-tester. A most useful instrument for hobbyists, experimenters and technicians who require a reliable tester at a budget price. Operation is extremely easy: simply plug leads into desired scale and you are ready to go. **RANGES:** D.C. voltages: 0-15-150-1,000 v. (1,000 o.p.v.). A.C. voltage: 0-15-150-1,000 v. (1,000 o.p.v.). D.C. current: 0-150 mA. Resistance: 0-100K. Size: 2 1/2 x 2 1/2 x 1 in.

Complete with battery, test leads and instructions, fully guaranteed. **49/6.**

**SUBSTITUTION BOXES**

Fully calibrated complete with insulated leads **Model O.M.G. RESISTANCE BOX.** Provides 24 standard values at 1 watt, 15 ohms to 10 meg. **Price 37/6.** **Model O.M.B. CAPACITANCE BOX.** Provides 9 standard values from 0.001 to 0.22 mfd at 500 volt working. **Price 29/6.**

**AR.13 UNIVERSAL TEST LEAD KIT IN PLASTIC CASE**




Consists of 4 1/2 in. long x 3/16 in. dia. red and black plastic handle pin leads with heavy duty 57in. rubber leads with 3,000 v. breakdown insulation terminating 2 1/2 in. long x 3/16 in. dia. plastic grip banana plugs. 3 sets of interchangeable terminals are included (spade lugs, phone tips, alligator clips), all slip directly on to banana plugs. **PRICE 9/6.**

**R.F. FIELD INDICATOR**




**RF.40.** Designed for checking the radiation from a transmitting antenna. The sensitivity can be controlled by adjustment of panel control, the antenna length or by increasing distance from the radiator. **Freq. range 1-250 Mc/s. 200μA D.C. Meter.** Complete as illustrated with instructions. **PRICE 69/6.**

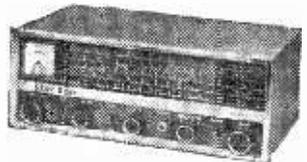**EAGLE DE-LUXE 4 BAND SHORT WAVE COMMUNICATION RECEIVER RX.60.**



4 band power-packed Superheterodyne circuit. Covers Broadcast Band (560-1600 Kc/s) and Short Wave from 1.4-30 Mc/s in 3 bands. Electrical Bandspread. Built-in "R" meter, A.V.C., noise limiter, B.F.O. Phone Jack. Built-in 50 speaker. Never before such fantastic value in Short Wave receivers, beautifully styled, features a precision electrical Bandspread dial, 0-100 logging scale for easy self calibration. Separate handspired tuning condenser and calibrated "R" meter for accurate tuning. Sensitive circuit features A.V.C. to minimize blasting and/or fade out. A.N.L., to reduce annoying interference. **PRICE 224.10.0.** Send S.A.E. for further details.

**6 PIECE SCREWDRIVER SET MODEL 3360.**

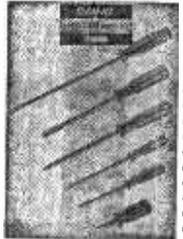

Consisting of mechanics, electricians, Phillips, midget and stubby types. Magnetised blades of tempered, hardened tool steel. Unbreakable, flameproof and shockproof plastic handles. Display bagged. **ONLY 7/-.**

**THIS MONTH'S SPECIAL OFFERS!**

**AERIAL VARIOMETERS**

These magnificent instruments will enable you to receive maximum signal strength on all H.W. receivers. Precision calibrated control. Used condition.



**SNIP PRICE 10/-** post paid.

**TRANSMITTER SNIP!**

**12 VOLT DYNAMOTORS.** 400 v. output at 150 mA.

**ONLY 25/-** post paid.

**STANDING WAVE RATIO METER**

"L" Hand standing wave measuring test set. Complete set in fitted wood carrying case includes: Bolometer assembly, power cable operates from 115 volts A.C. 50-1,000 cycles, junction box assembly, probe cable, slotted line assembly, flexible line, flexible line coupler and a number of connections and adaptors, fuses, wrenches. Slotted line approx. 6in. long.

**ONLY 60/-** cart. paid

MAIL ORDERS TO: (DEPT. P), 32a COPTIC STREET, LONDON W.C.1.

CALLERS WELCOME AT: 87 TOTTENHAM COURT RD, LONDON W.1. MUS 9606



# POST HASTE FROM SURBITON

ALL ORDERS DESPATCHED SAME DAY ● WE PAY POSTAGE and INSURANCE ● ALL TRANSACTIONS receive PERSONAL ATTENTION and PROTECTION from our MONEY BACK GUARANTEE

## ★ MARTIN RECORDAKITS ★

### For HALF TRACK

Table Amplifier for Studio Deck with ready wired printed circuit, control and input panels, mains and output transformers, knobs, plans, screws, etc. EF86, ECC83, EZ80, EM85 and 2 EL84. 3 watts output. Magic eye, radio and Mic. inputs. Ext. speaker socket. Tone and Monitor controls. Can be used as an amplifier. £11.11.0  
 Collaro Studio Deck. Very latest model, 3 speeds, 7in. spools £10.19.6  
 Case for above, with 8 x 5in. speaker, two tone grey £5.5.0  
 Complete Kit with Tape and Microphone £29.0.0  
 B.S.R. Monardeck TD2, latest model 5 1/2in spools £9.9.0  
 Tape Amplifier for B.S.R. Deck, printed circuit ready wired with ECC83, ECL82, EM86 and EZ80. Complete with all plugs, sockets, panels, knobs, etc. Mounts under deck making a self-contained unit. £8.5.0

### For QUARTER TRACK

Collaro Studio Deck, Marriott "X" heads £17.10.0  
 Tape Amplifier for Studio Deck, described above, but quarter track £12.13.0  
 Case, with speaker, two tone grey £5.5.0  
 Complete Kit with Tape and Microphone £35.0.0

| Dep. | &  | Mthly. pmts. of |
|------|----|-----------------|
| 24/- | 12 | 19/-            |
| 22/- | 8  | 27/8            |
| 55/- | 12 | 58/-            |
| 20/- | 9  | 21/-            |
| 20/- | 8  | 21/-            |
| 27/6 | 12 | 29/8            |
| 37/- | 12 | 20/8            |
| 70/- | 12 | 58/2            |

B.S.R. TD2 Deck with Marriott "L" Series heads £11.11.0  
 Tape Amplifier for B.S.R. deck, as over, but quarter track £9.9.0

### TAPE PRE-AMPLIFIER

For Studio Deck with power supplies, ECC83, ECL82, EZ80 and EM84. Mic. and Radio sockets, gives an equalised output of 400 m/Volts... Half Track £8.8.0  
 Quarter Track £9.9.0  
 Building Instructions available at 2/6 each Kit (refunded when Kit bought).

### TAPE HEADS

MSS Quarter track. Record/Playback and Erase per set £3.3.0  
 Bradmatic Half track Record/Playback head only £1.12.6  
 Bradmatic Half track Record/Playback and Erase on plate £1.19.8  
 Collaro pressure pad for third head position £4/-

### BRENELL

Mk. 5 Series 2 Deck, Half track 4 speed £32.11.0  
 Mk. 5 Series 2 Tape Amplifier with power pack £28.0.0

| Dep. | &  | Mthly. pmts. of |
|------|----|-----------------|
| 24/- | 12 | 19/-            |
| 20/- | 9  | 21/-            |
| 20/- | 8  | 21/-            |
| 20/- | 9  | 21/-            |
| 65/- | 12 | 54/-            |
| 52/- | 12 | 43/2            |

## GRAMOPHONE UNITS, MOTORS, PICK-UPS

Decca Deram Arm and Plug-in Shell £5.5.0  
 Decca Deram Transcription Cartridge £13.6.6  
 Decca Deram Auto Gartride £13.6.6  
 Garrard SRP10 with GCS cartridge, Mono, single player £5.9.11  
 B.S.R. UA14 with TCS cartridge, Mono, 4-speed changer £6.19.8  
 Garrard Autolism, Mono GCS cartridge, 4 speed changer £17.10.0  
 Garrard AT6 Autolism de Luxe. GCS Mono cartridge £11.9.0  
 Garrard 4H/F with Mono GCS cartridge £17.0.0  
 Garrard Lab Type "A" Transcription auto-changer with GCS cartridge £19.14.9  
 Garrard 301 £20.12.2  
 Garrard 301 Strobe £22.0.0  
 Philips AG1016, Stereo cartridge, will change 2in. records (adaptor 10/- extra) £21.12.0  
 Goldring GL58 with arm, less cartridge £16.19.8  
 Goldring GL70 with arm, no cartridge £26.3.0  
 Goldring GL55X, as GL58 but less pick-up arm £13.17.0  
 Goldring "88" Transcription, no arm £17.14.0

| Dep. | &  | Mthly. pmts. of |
|------|----|-----------------|
| 20/- | 6  | 23/3            |
| 20/- | 7  | 22/6            |
| 26/8 | 9  | 24/9            |
| 34/- | 12 | 28/2            |
| 39/8 | 12 | 32/9            |
| 43/2 | 12 | 34/-            |
| 44/- | 12 | 36/6            |
| 27/- | 12 | 20/8            |
| 35/- | 12 | 26/6            |
| 50/- | 12 | 43/2            |
| 27/7 | 12 | 21/5            |
| 39/- | 12 | 29/-            |

## ARMSTRONG - NEW TUNER AMPLIFIERS

### MONO

AF208 A.M./F.M. Radio chassis, base and treble controls, P.U. inputs, etc. £21.4.0  
 ST3 Mk. 2 A.M./F.M. Self-powered tuner. £25.12.0  
 227M A.M./F.M. Radio chassis 10 watts £33.18.0

| Dep. | &  | Mthly. pmts. of |
|------|----|-----------------|
| 46/- | 12 | 34/10           |
| 33/- | 12 | 42/9            |
| 70/6 | 12 | 56/1            |

### STEREO

Stereo 55 A.M./F.M. Radio chassis, with Stereo gram inputs £29.18.0  
 223 A.M./F.M. Self-powered (Tuner only) £28.15.0  
 224 P.M. only, Self-powered Tuner £29.10.0  
 227 A.M./F.M. Radio chassis, Stereo gram, 10 watts each channel £48.15.0  
 226 A.M./F.M. Radio chassis, Stereogram, 10 watts each channel, Filters, etc. £56.0.0

| Dep.  | &  | Mthly. pmts. of |
|-------|----|-----------------|
| 62/6  | 12 | 48/5            |
| 57/6  | 12 | 47/9            |
| 45/-  | 12 | 37/4            |
| 97/6  | 12 | 81/1            |
| 112/- | 12 | 93/2            |

### OTHER TUNERS

Tripletone P.M. Tuner, less power £13.19.6  
 Tripletone P.M. Tuner, self-powered £15.14.6

| Dep. | &  | Mthly. pmts. of |
|------|----|-----------------|
| 28/- | 12 | 23/2            |
| 31/6 | 12 | 26/1            |

## STEREO AMPLIFIERS

Armstrong 222 Integrated, 10W per channel £27.10.0  
 Dulci AC202, Integrated £12.12.0  
 Dulci GA505, Integrated £18.18.0  
 Rogers Cadet Mk. 2 with pre-amplifier, 4 ECL86 valves £26.15.6  
 Leak Stereo 20, Mic. amplifier £30.9.0  
 Leak Variatone stereo pre-amplifier £25.0.0  
 Quad 22 Stereo Control Unit £25.0.0  
 For Quad Main Amplifiers see Mono section.

| Dep. | &  | Mthly. pmts. of |
|------|----|-----------------|
| 55/- | 12 | 45/8            |
| 27/- | 12 | 30/8            |
| 40/6 | 12 | 31/1            |
| 53/6 | 12 | 44/5            |
| 64/6 | 12 | 50/8            |
| 50/- | 12 | 41/8            |
| 50/- | 12 | 41/6            |

## MONO AMPLIFIERS

Linear L45, 3 watt, 3 valve £5.19.6  
 Linear Distonic, 12 watt, suitable Mic. or Guitar £12.10.0  
 Linear Concord, 30 watt, Ideal Guitar or Amp. with case £18.0.0  
 Dulci GA5, integrated amp., 5 watt, ECL86 valve £13.2.6  
 Dulci DPA15, 15 watt with 2 valve pre-amp. £25.4.0  
 Tripletone Hi-Fi Major with pre-amp. Suitable for Guitar or Mic. etc. £15.18.9  
 Leak TL12, 10 watt Main amp. only £15.15.0  
 Leak Variatone pre-amplifier £15.15.0  
 Quad, 15 watt Main amplifier only £22.10.0  
 Quad pre-amplifier, Mono £19.10.0

## JASON F.M. AND TV SOUND TUNERS

FMT1, complete with 4 EF91 valves £7.4.6  
 FMT2, less power, complete with 4 EF90 valves £9.4.6  
 FMT2, with power, complete with 4 EF80 and 1 EZ80 £11.4.6  
 FMT3, Fringe, complete with valves, less power £10.19.0  
 FMT3, with power, complete with all valves £12.19.0  
 All JTV/2, switched F.M. and TV sound, self powered, all valves £15.12.6  
 Mercury II, as JTV/2 but less power, all valves £11.0.0  
 Instruction book included in all kits. Available separately, 2/6 and 3/6.  
 JTV/2, ready built, state channels £22.5.0  
 Monitor, ready built (as Mercury II) £18.10.0

| Dep. | &  | Mthly. pmts. of |
|------|----|-----------------|
| 21/- | 7  | 20/6            |
| 20/6 | 8  | 20/6            |
| 22/6 | 8  | 24/9            |
| 26/- | 12 | 21/6            |
| 33/8 | 12 | 25/8            |
| 22/- | 8  | 27/3            |
| 44/6 | 12 | 36/11           |
| 33/- | 12 | 27/4            |

## LOUDSPEAKERS

Goodmans Axiote 8 £5.5.7  
 Goodmans Axiom 10 £6.5.11  
 Goodmans SX10/XL £7.0.0  
 Goodmans XO 5000 cross-over £11.9.0  
 Goodmans Axiom 201 12in. Unit £10.7.0  
 Goodmans Axiom 301 12in. Unit £14.10.0  
 Wharfedale Super 8/RS/DD £8.14.2  
 W.B. HF1012 10in. £4.7.6  
 R.T.C. 12in. Unit, 15 watt £5.5.0  
 R.T.C. Hi-Fi Master £8.8.0  
 Wharfedale W12/EG 12in. 15 watt Lead £10.10.0  
 Wharfedale W15/EG 15in. 15 watt Bass Guitar speaker £17.10.0  
 Wharfedale Snper 10/RS/DD 10in. high quality unit £10.19.0  
 Wharfedale RS12/DD 12in. 15 watt Hi-Fi £11.10.0

| Dep. | &  | Mthly. pmts. of |
|------|----|-----------------|
| 21/- | 8  | 25/9            |
| 29/8 | 12 | 24/-            |
| 20/- | 8  | 21/-            |
| 21/- | 12 | 17/5            |
| 35/- | 12 | 29/-            |
| 23/8 | 12 | 17/11           |
| 27/6 | 9  | 24/9            |

EASILY REACHED BY TRAIN FROM WATERLOO TO SURBITON

## SURBITON PARK RADIO LTD.

48, SURBITON ROAD, KINGSTON-ON-THAMES, SURREY


Phone: KIN 5549

- Order for Cash, C.O.D. or Terms
- Hours 9 a.m.-6 p.m. (1 p.m. Wed.)
- Open ALL DAY Saturday
- Established 30 years
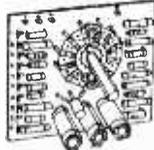
# PARK RADIO LTD.

**YOUR MAIN SUPPLIERS  
FOR THE NEW MARTIN  
10W. AMPLIFIER KITS**

With these ingenious new MARTIN AUDIOKITS you can build an ALL-TRANSISTOR Hi-Fi Assembly to suit your personal requirements exactly. When built, you will have a modern, powerful, high quality assembly. Building is easy, and you will save pounds. Designed for simple panel mounting. Easily doubled up for stereo. Full instructions with every kit. Leaflets free on request.



## UNIT 1 FIVE STAGE SELECTOR

Enables up to 5 inputs to be connected and correctly matched to following pre-amp stage. With transistor, resistors and capacitors mounted on printed circuit board. Long spindle for adding stereo when required.

Size 2 1/2 x 3in. For Magnetic and crystal P.U.s, Radio Tuner, Microphone, and output from tape head. Requires 9-15V.

47/6



## UNIT 4 COMBINED PRE-AMPLIFIER AND TONE CONTROL UNIT


Three stages of audio control—base control operating between -14 to +10 dB; treble control between -16 to +12 dB; volume control with on-off switch to servo supply to complete installation. With transistors, resistors etc. on printed circuit board. 4 1/2 x 2 1/2in. 9-15V.

62/6
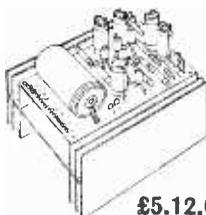
## UNIT 5 MAIN AMPLIFIER

Complete with heat sink on which the 813 transistor printed-circuit amplifier is built. Transformerless output gives maximum of 10 watts into 3ohm speaker operating from 24 volt supply. Pre-tested by makers.

Wharfedale 3:1:5 ohm matching Transformer... 13/6



£5.12.6

## UNIT 6 POWER SUPPLY UNIT

Operates from 200-250 volts A.C. giving D.C. output at 24 volts for main amplifier and tappings for power to other Martin Audiokit Units. Incorporates heavy duty transformer, full smoothing and latest type rectification.



52/6

**ALL 4 ABOVE UNITS £13.15.0 OR 27/6 DEPOSIT AND 12 MONTHLY PAYMENTS OF 22/9**

**● TAPE ENTHUSIASTS — SEE DETAILS OF MARTIN REORDAKITS — Page Opposite**

# Make Your Ability PAY

**UNLIMITED OPPORTUNITIES** exist today for "getting on" . . . but only for the fully trained man. Let ICS tuition develop your talents and help you to success.

**STUDY IS EASY** with ICS guidance. The courses are thorough. Printed manuals, fully illustrated, make study simple and progress sure.

**YOUR ROAD TO SUCCESS** can start from here—today. Complete this coupon and post it to us, for full particulars of the course which interests you. MODERATE FEES INCLUDE ALL BOOKS.

## Take the right course now . . .

### ADVERTISING & ART

Copywriting  
Layout & Typography  
Commercial Illustrating  
Oil & Water Colour

### BUILDING & CIVIL ENG'NG

Architecture, Bricklaying  
Building Construction  
Builders' Draughtsman  
Interior Decoration  
Quantity Surveying  
Heating & Ventilation  
Carpentry & Joinery

### COMMERCE

Book-keeping  
Accountancy & Costing  
Business Training  
Office Training  
Purchasing, Storekeeping  
Secretarialship

### DRAUGHTSMANSHIP

Architectural, Mechanical  
Drawing Office Practice

### ELECTRONICS

Computer & Maintenance  
Electronic Technicians  
Industrial Electronic

### FARMING

Arable & Livestock  
Pig & Poultry Keeping  
Rabbits & Chickens

### GENERAL EDUCATION

G.C.E. subjects at Ordinary & Advanced Level  
Good English  
Foreign Languages

### HORTICULTURE

Home Gardening  
Park Gardening  
Market Gardening

### MANAGEMENT

Business Management  
Hotel Management  
Industrial Management  
Office Management  
Personnel Management  
Works Management  
Work Study  
Workmanship

### MECHANICAL & MOTOR ENG'NG

Engineering Maths.  
Diesel Engines, Welding  
Industrial Instrumentation  
Workshop Practice  
Refrigeration  
Motor Mechanics, etc.

### POLICE

Entrance Examination

### PHOTOGRAPHY

Practical Photography

### RADIO, TV & ELECTRICAL

Servicing & Engineering  
Radio Construction (with Kits)  
P.M.G. Certificate  
Telecommunications  
Electricians' Electrical Contractor

### SELLING

Company Reps.  
Sales Management  
Marketing

### WRITING FOR PROFIT

Short-story Writing  
Free-lance Journalism

**INTENSIVE COACHING** for all principal examinations—G.C.E., Secretaryship, Accountancy, Engineering, Work Study, Management, Radio, Architecture and Surveying. Special course for G.C.E. French Oral Test.

Member of the Association of British Correspondence Colleges

**Start today the ICS way!**

## INTERNATIONAL CORRESPONDENCE SCHOOLS

(Dept. 172)

Intertext House, Parkgate Rd., London, S.W.11

Send FREE book on.....

Name.....

Address.....

Occupation.....

3.64

**INTERNATIONAL CORRESPONDENCE SCHOOLS**

EQUIPMENT FOR RADIO  
"AMATEURS" COMMUNICATIONS



INSTRUMENTS FOR TEST,  
SERVICE AND WORKSHOP

## SAVE MONEY... AND ENJOY YOURSELF BUILDING THE WORLD'S BEST KIT-SETS — THE HEATHKIT WAY!

The clearly written instruction manuals, issued with each kit, show you how.

DEFERRED TERMS ON ORDERS ABOVE £10. ALL MODELS ALSO AVAILABLE ASSEMBLED

### TEST INSTRUMENTS



**5in. OSCILLOSCOPE.** Model 0-12U. Laboratory quality at utility oscilloscope price. Wide band amplifiers essential for T.V. servicing, F.M. alignment, etc. T/B covers 10 c/s-500 kc/s in 5 ranges.

£43.10.0 assembled. **£35.10.0 Kit**

**PORTABLE 'SCOPE.** Model OS-1. A compact portable oscilloscope, ideal for servicing and general work. Printed circuit board. Case: 7½ x 4½ x 12½ in. long. Wt. only 10½ lbs.

£29.8.0 assembled **£21.18.0 Kit**

**ELECTRONIC SWITCH.** Model S-3U. Converts a single beam oscilloscope into double beam operation.

£18.10.0 assembled **£12.18.0 Kit**



**VALVE VOLTMETER.** Model V-7A. The world's best selling VTVM. Measures up to 1,500 volts (d.c. and r.m.s.) and 4,000 pk. to pk. Res. 0.1 Ω 1,000 MΩ. Centre zero dB scale, d.c. input. Resistance 11 MΩ, 4½ in. meter. Complete with test prods, leads and standardising battery.

£19.18.6 assembled **£13.18.6 Kit**

**RF PROBE.** 309-CU extends range to 100 Mc/s. Indication to 300 Mc/s.

**£11.3.6 Kit**

**HV PROBE.** HV-336 measures up to 30,000V d.c.

**£2.19.6 Kit**

**RF SIGNAL GENERATOR.** Model RF-1U. Up to 100 Mc/s fundamental, 200 Mc/s harmonics. Up to 100 mV output on all bands.

£19.18.0 **£13.8.0 Kit**

**MULTIMETER.** Model MM-1U. Ranges: 0-1.5 v. to 1,500 v. a.c. and d.c.; 150µA to 15A d.c.; 0.2Ω to 20MΩ 4½ in. 50µA meter.

£18.11.6 assembled **£12.18.0 Kit**

A wide range of other test instruments available including: R/C Bridge C-3U £10.10.0. AF Voltmeter AV-3U, £16.10.0. Wattmeter AW-1U, £17.5.0. (Capacitance meter) CM-1U £15.15.0. Power supplies. Decade boxes etc. Many other instruments available under American Mail order scheme. Why not send for full details.

### SSU-1 SPEAKER SYSTEM



A practical solution to the problem of a moderately-priced speaker suitable for Stereo/Mono amplifiers, where the equipment has to be compact. Two speakers, balance control, ducted port reflex cabinet.

Horizontal or vertical (without legs)

Incl. P.T. **£10.17.6 Kit**

Horizontal or vertical (with matching legs)

Incl. P.T. **£11.12.0 Kit**

SSU-1

### "AMATEUR" EQUIPMENT

#### AMATEUR BANDS RECEIVER

Model RA-1. Covers all amateur bands from 160-10 m. Half lattice crystal filter. 8 valves, "S" meter, tuned R.F. amplifier stage.

**£39.6.6 Kit**


Assembled **£52.10.0**



RA-1

**AMATEUR TRANSMITTER.** Model DX-100U. Covers all amateur bands 160-10M. 150 w. d.c. input, self contained with power supply. Modulator. VFO.

Assembled **£104.15.0** **£79.10.0 Kit**

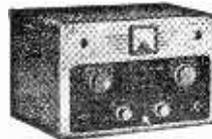

DX-40U

#### AMATEUR TRANSMITTER

Model DX-40U. Covers 80-10 m. Power input 75 w. C.W., 60 w. peak C.C. phone. Output 40 w. to aerial. Prov. for V.F.O.

**£33.19.0 Kit**

Assembled **£45.8.0**

Other kits in the amateur range include: SSB Adaptor SB-10U, £39.5.0. Variable Freq. Oscillator VF-1U, £12.10.0. Balun Coil Unit B-1U, £4.15.6. Grid-Dip Meter GD-1U, £10.19.6. Q Multiplier QPM-1, £8.10.0. Wide range of models under American Mail Order Scheme.

### TRANSISTOR RECEIVERS

#### "OXFORD" LUXURY TRANSISTOR DUAL WAVEBAND RECEIVER.

The ideal domestic, car or personal portable receiver. 10 Semi-conductors. Solid leather case. Send for full details.

Incl. P.T. **£14.18.0 Kit**



**6 TRANSISTOR PORTABLE.** Model UXR-1. Prealigned I.F. transformers. Printed circuit, 7in. x 4in. high flux speaker. Real hide case. Very easy to build.

Incl. P.T. **£12.11.0 Kit**

UXR-1

**7 TRANSISTOR PORTABLE.** Model RSW-1. Two short, trawler and medium wave bands.

Incl. P.T. **£19.17.6 Kit**

**"MOHICAN" GENERAL COVERAGE RECEIVER.** Model GC-1U. Excellent portable or general purpose receiver for "amateur" or short wave listening. See full spec. leaflet.

Assembled **£48.17.6** **£39.17.6 Kit**



GC-1U

SEND FOR FREE BRITISH CATALOGUE  
OVER 50 MODELS TO CHOOSE FROM

# DAYSTROM LTD.

Dept. PW-3.

GLOUCESTER,  
ENGLAND

A member of the Daystrom Group, manufacturers of the WORLD'S LARGEST-SELLING ELECTRONIC KITS

THE WORLD'S BEST  
KIT-SETS OF THE



HIGHEST QUALITY  
AT LOWER COST

Millions of Heathkit models are in use throughout the world because :—

- ★ They are so easy to build. Even for an absolute beginner.
- ★ The manual of instructions is foolproof. Because all manuals are written by the world's experts in kit-set design.
- ★ You get professional appearance and performance with every model.

**HI-FI AMPLIFIERS**



S-33

**6W STEREO AMPLIFIER.** Model S-33. 3 w/chl. Inputs for radio, tape and gram. Stereo/Mono ganged controls. Sensitivity 200 MV.

£18.18.0 Assembled **£13.7.6** Kit

**18W STEREO AMPLIFIER.** Model S-99. Ganged controls. Stereo/Mono gram, radio and tape recorder inputs. P/B selection.

£37.19.0 Assembled. **£27.19.6** Kit



**5W HI-FI MONO AMPLIFIER.** Model MA-5. A low priced amplifier based on the S-33. Printed circuit construction makes it easy to build. £14.19.6 assembled.

**£10.19.6** Kit

**6W DE-LUXE STEREO AMPLIFIER.** Model S-33H. An inexpensive stereo/mono amplifier with high sensitivity. Suitable for use with Decca Deram cartridge

£21.7.6 Assembled **£15.17.6** Kit

**TAPE RECORD/REPLAY AMPLIFIER KITS.** Will operate with most tape decks. Send for details.

TA-1M (Mono), £19.18.0. TA-1S (Stereo), £25.10.0

**HI-FI SINGLE CHANNEL AMPLIFIER.** Model MA-12. Ideal for use with Models USC-1 and UMC-1. O.I X THD at 10 W. Wide freq. range.

£15.18.0 Assembled.

**£11.18.0** Kit

**NEW MODELS**



**PUBLIC ADDRESS AMPLIFIER.** PA-1. For vocal and instrumental groups, guitars, etc. 50 W r.m.s., 100 W pk output. 4 inputs, 2 loudspeakers in one compact unit. Send for full details.

£74.0.0 Assembled **£54.15.0** Kit

Set of 4 Legs 17/6 extra.

**COMMUNICATIONS TYPE RECEIVER RG-1.** A high performance low cost receiver for the discriminating listener. Freq.: cov. 600 kc/s-1.5 Mc/s and 1.7 Mc/s to 32 Mc/s. Send for details.

£53.0.0 Assembled.

**£39.16.0** Kit



**SELF SUPPORTING AERIAL TOWER KIT.** Model HT1. Ideal for Amateur Radio or TV reception, etc. Strong steel construction, height 32 ft. tapered square section 3ft. x 3ft. at base. Kit £29.15.0 Oxide Painted. £35.15.0 Galvanised.

Accessories available. Send for details.

**'COTSWOLD' SPEAKER SYSTEMS**

**STANDARD MODEL**

Acoustically designed enclosure in the white 26 x 23 x 15 1/2 in. 12in. bass speaker, elliptical middle speaker, 2in. pressure unit. Covers 30-20,000 c/s. Complete kit with all controls.



**MFS SYSTEM**

A minimum floor space model for the smaller room. 36in. high x 16 1/2 in. x 14in. deep. Almost identical performance to standard model.

Price either model **£23.4.0** Kit

**HI-FI TUNERS**

**Model FM-4U.** Tuning range 88-108 Mc/s. Tuning unit (FMT-4U) with 10.7 Mc/s I.F. (£2.15.0 inc. P.T.). I.F. Amp (FMA-4U) complete with cabinet and valves.

Total **£15.18.0** Kit



FM-4U

**AM/FM TUNER.** Covers FM 88-108 Mc/s. AM. 16-50, 200-550, 900-2,000 m. Tuning heart (£4.13.6 inc. P.T.), and I.F. Amp.

Total **£26.10.0** Kit



**EQUIPMENT CABINETS**

A large range, in kit form or assembled and finished, available to meet most needs. Illustrated details on request.

Prices from **£7.7.0**

to **£33.12.0**

**MONEY BACK GUARANTEE**

Daystrom Ltd. unconditionally guarantees that each Heathkit product assembled in accordance with our easy to understand instruction manual must meet our published specifications for performance or the purchase price will be cheerfully refunded.

**250**

**AMERICAN HEATHKIT MODELS**

Full details of Direct Mail Order Scheme and fully illustrated catalogue of range can be obtained from us for only 1/- post paid. (FREE to Service Depts.)

**DAYSTROM LTD.**

Dept. P.W.3, GLOUCESTER, ENGLAND

A member of the Daystrom Group, manufacturers of the  
WORLD'S LARGEST-SELLING ELECTRONIC KITS

Please send me **FREE BRITISH CATALOGUE** (Yes/No)

Full details of model(s).....

NAME .....

ADDRESS .....

PW3

Brand new individually checked and guaranteed

VALVES

Table listing various vacuum tube valves with their types, manufacturers, and prices. Columns include valve type (e.g., AC/HL, AC/PA), manufacturer (e.g., E1266, E1415), and price. Includes a section for C.R. Tubes at the bottom right.

MANY OTHERS IN STOCK include Cathode Ray Tubes and Special Valves. U.K. orders below £1 P. & P. 1/-; over £1, 2/-; over £3, P. & P. free C.O.D. 2/6 extra. Overseas Postage extra at cost.

MARCONI COMMUNICATION RECEIVERS. CR.150. Frequency coverage 2-60 Mc/s in 5 bands. Two I.F.s. 1st 1,600 kc/s, 2nd 463 kc/s. Image signal protecting over 40 db up to 30 Mc/s and 20-40 db from 30-60 Mc/s. Self checking calibration (built in calibrator). Stabilisation of supply and temperature compensation. Electrical and mechanical bandspread. Metering and visual tuning indicator. Bandpass from 100c/s to 10kc/s in 5 stages. Acoustic filter associated with 100 c/s. Bandpass position for CW reception. Facilities for diversity reception. In as new guaranteed condition with original mains power supply unit £70 or without power supply unit £60. Carriage 30/-.

Original mains power pack for H.R.O. 110/220 v. A.C. Brand new in original packing. 45/- P. & P. 4/-.

CONNECTORS FOR TCS RECEIVER, TRANSMITTER AND REMOTE CONTROL. with original plugs on both ends. New £1.17.6 each. P. & P. 2/6.

TRANSMITTER RECEIVER. TYPE 68T. 3-5 Mc/s netting facilities. Low power consumption. Requires 150 v. h.t. and 3 v. l.t. dry batteries. In good condition. 35/-. Carriage 8/-.

COMMUNICATION RECEIVER. TYPE SR 40. 540 Kc/s-31 Mc/s in 4 bands. Built-in Sin. loudspeaker. telescopic aerial for SW reception. Calibrated "S" meter, automatic interference limiter. BFO circuit. 220v. A.C. Weight approx. 15 lb. £29, carriage free U.K.

R.209 RECEPTION SET. A 10-valve high-grade Superhet Receiver with facilities for receiving R/T (A.M. or F.M.) and CW frequency 1 Mc/s-20 Mc/s. Hermetically sealed. Built on miniature valves and incorporating its own vibrator power-supply unit driven by a 6 v. battery (2 point connector included). The set provides for reception from rod, open-wire or dipole aerial with built-in loudspeaker

or phone output. Dimensions: Length 12in. width 8in., depth 9in. Weight 23 lb. In as new, tested and guaranteed condition. £23.10.0, including special headphone and supply leads. Carr. £1.

PRECISION WATT METERS made by Weston (USA) for D.C. and A.C. 25-1,000 c/s. Voltage coils 150 and 300 v., current max. 7.5 amps. Mirror dial calibrated up to 1,500 watts. Connecting instructions included. Overall measurements 6 1/2 x 5 1/2 x 3 1/2 in. Brand new £9.19.6.

CARBON INSET MICROPHONE. G.P.O. type, 2/6. P. & P. 1/6.

PANEL METERS (round)

|                      |        |               |      |
|----------------------|--------|---------------|------|
| 0-20 microamps       | 2 1/2" | D.C.          | 79/- |
| 0-50 microamps       | 3"     | D.C.          | 45/- |
| 0-50 microamps       | 2 1/2" | D.C.**        | 40/- |
| 0-100 microamps      | 2 1/2" | D.C.          | 35/- |
| 0-100 microamps      | 2 1/2" | D.C.**        | 35/- |
| 0-100 microamps      | 2 1/2" | D.C.          | 32/6 |
| 0-200 microamps      | 2 1/2" | D.C.          | 21/- |
| 0-500 microamps      | 2 1/2" | D.C.          | 30/- |
| 0-500 microamps      | 2 1/2" | D.C.          | 19/6 |
| 0-1mA*               | 3 1/2" | D.C.          | 35/- |
| 0-1mA                | 3 1/2" | D.C.**        | 35/- |
| 0-5mA                | 3 1/2" | D.C.          | 29/- |
| 150-0-1,500mA        | 3 1/2" | D.C.          | 45/- |
| 0-15v                | 2 1/2" | A.C.          | 17/6 |
| 0-50v                | 2 1/2" | D.C.          | 28/- |
| 0-150v               | 2 1/2" | A.C.          | 24/- |
| 0-500v (shunt)       | 2 1/2" | D.C.          | 20/- |
| 0-5kV                | 3 1/2" | electrostatic | 85/- |
| 0-10kV               | 2 1/2" | D.C.          | 63/- |
| Freq. 0-70 c/Sec/25v | 3 1/2" |               | 52/- |

\*"Weston", as usually used also in H.R.O. as "S" meter. \*\*Projection type.

**P.C. RADIO LTD**  
170 GOLDHAWK ROAD, W.12  
Shepherd's Bush 9496  
Open 9-5.30 p.m. Thursday 9-1 p.m.

# STERN-CLYNE

Incorporating STERN RADIO LTD., PREMIER RADIO, CLYNE RADIO LTD.  
Three well-known names with a reputation for quality and service.



Combined resources, technical knowledge and over 50 years' experience gives you an organisation offering a fully comprehensive specialist service in the rapidly expanding world of electronics.



## MULLARD 3-VALVE PRE-AMPLIFIER TONE CONTROL UNIT

Designed mainly for Mullard Range of Amplifiers, also suitable for any Amplifiers requiring input up to 250mV. Incorporates: 5 Input Channels, including for Tape and Magnetic Pickups. Separate Bass and Treble controls. High pass filter 20 to 150 c/s. low pass filter 5-9 Kc/s. Totally enclosed in case size 11 1/2" x 4 1/2" x 4 1/2".

**KIT OF PARTS £10.00** (Carr. & Ins. 5/-) **ASSEMBLED AND TESTED £13.10**

*Instruction book and detailed price list (free with kit) available separately at 2/- Post Free.*



## PRICE REDUCTIONS

- (a) THE KIT OF PARTS to build both the "5-10" Amplifier and the 2-Valve Pre-Amplifier..... **£15.15.0**
  - (Carr. & Ins. 8/6).
  - (b) Assembled and Tested ..... **£21.10.0**
  - (c) THE KIT OF PARTS to build both the "5-10" Amplifier and the 3-Valve Pre-Amplifier..... **£19.10.0**
  - (Carr. & Ins. 10/-).
  - (d) Assembled and Tested..... **£25.10.0**
- With PARTRIDGE OUTPUT TRANSFORMER **£1.6.0 extra.**

## MULLARD "5-10" MAIN AMPLIFIER

For use with MULLARD 2 or 3 valve pre-amplifiers with which an undistorted power output of up to 10 watts is obtained. SPECIFIED COMPONENTS and MULLARD VALVES including PARTRIDGE MAINS TRANSFORMER and choice of PARMEKO or PARTRIDGE Output Transformer.

**COMPLETE KIT (Parmeko Output Trans.) ASSEMBLED AND TESTED £10.00**

**ASSEMBLED AND TESTED £13.10.0**

Above incorporating PARTRIDGE OUTPUT TRANS. £1.6.0 extra. *Instruction book and detailed price list (free with kit) available separately at 2/- Post Free.*

## THE MULLARD 5-10RC AMPLIFIER

The popular complete "5-10" incorporating Passive Control Unit providing up to 10 watts high quality reproduction with input of 300 mV. Specified components and new MULLARD VALVES. Includes PARTRIDGE MAINS TRANSFORMERS and choice of PARMEKO or PARTRIDGE output Transformers. Surplus Power available for Tuner.

**COMPLETE KIT £12.00**

**ASSEMBLED AND TESTED £16.00** (Carr. & Ins. 7/6) **With PARTRIDGE OUTPUT TRANS. £1.6.0 ex.**

*Instruction book and detailed price list (free with kit) available separately at 2/- Post Free.*



## MULLARD 2-VALVE PRE-AMPLIFIER TONE CONTROL UNIT

Employing two EF86 valves and designed to operate with the Mullard AMPLIFIERS but also perfectly suitable for other makes with input up to 250 mV.

- ★ Equalisation for the latest R.I.A.A. characteristics.
- ★ Inputs for Crystal Pick-ups and variable reluctance magnetic types.
- ★ Input (a) Direct from High Imp. Tape Head. (b) From a Tape Amplifier or Pre-Amplifier.
- ★ Sensitive Microphone Channel. ★ Wide range BASS and TREBLE CONTROLS.

**KIT OF PARTS £6.6.0** **ASSEMBLED AND TESTED £9.10.0** (Carr. & Ins. 5/-).

*Instruction book and detailed price list (free with kit) available separately at 2/- Post Free.*



## THE "TUDOR" STEREO AMPLIFIER

**PRICE £15.0.0** (Pkg. & Carr. 7/6)

A self-contained Shelf-mounting Amplifier designed to provide high quality stereophonic and monophonic reproduction. Each channel provides a rated output of 6 watts and for monophonic operation approx. 12 watts is produced. Separate EASS and TREBLE CONTROLS. The Cabinet is finished in Black Crackle. Size 14 x 8 x 4 1/2 in. Send for full specification.



## THE MULLARD 3-3RC

A HIGH QUALITY AMPLIFIER DEVELOPED FROM THE VERY POPULAR 3-WATT MULLARD "3-3" DESIGN.

**KIT OF PARTS ASSEMBLED AND TESTED £8.8.0**

**ASSEMBLED AND TESTED £11.10.0**

Complete to the MULLARD specification including PARMEKO OUTPUT TRANSFORMER. Switched inputs for 78 and 45.

L.P. records plus a Radio position. Extra power to drive a Radio Tuning Unit is also available. (Carr. & Ins. 8/6). Please state L.S. impedance. *Instruction book and detailed price list (free with kit) available separately at 2/- Post Free.*

## THE SINCLAIR SLIMLINE

A new 2-TRANSISTOR printed circuit pocket radio. Completely portable—the smallest ever—only 2 1/2 in. x 1 1/2 in. x 1 1/2 in. Uses Micro-Alloy Transistors and with built-in ferrite aerial will receive all stations on M.W., B.B.C.—208, etc. Easy to assemble—no adjustment problems. All required components, including earpiece. **ONLY 49/6 P. & P 1/5.**

*All parts sold separately.*

## HI-FI STEREO HEADPHONES

For the connoisseur who requires perfection. Each Earphone consists of a 2" Dynamic Loudspeaker with a full frequency range, fitted with foam rubber Ear Pads for added comfort to keep out noise and to maintain an excellent bass response. The resistance junction box with change-over switch provides simple transfer from Phones to Speaker. Specifications: Frequency Range—25-15,000 c.p.s. Input Impedance—16 ohms. Power rating—1 watt. Weight—13 ozs.

**PRICE 5 Gns. P. & P. 2/6.**

(Junction box 15/- ex.)



## THE "MONO-GRAM"

A small Amplifier of keen high quality performance. Incorporates MULLARD ECL86 Valve, separate BASS and TREBLE controls, PARTRIDGE output Transformer producing up to 3 watts undistorted output. (Carr. & Ins. 3/6).

**Kit of Parts £4.10.0** **Assembled and Tested £6.0.0**

*price list (free with kit) available separately at 2/- Post Free.*

*Instruction book and detailed price list (free with kit) available separately at 2/- Post Free.*

Perfectly suited for Portable Installations for which purpose we offer PORTABLE CASE (£3.10.0), the AMPLIFIER KIT and 8" x 5" SPEAKER (£1.0.0). All for **£9.0.0**

Alternatively with ASSEMBLED AMPLIFIER ..... **£10.0.0** (Carr. & Ins. 6/-).

The Case quoted above will accommodate some 4-speed Single Record Units. Larger model is available for extra 10/-. With this Equipment a COMPLETE PORTABLE RECORD PLAYER can be built for **£14.0.0**



## MONAURAL STETHOSCOPE HEADSETS

Suitable for Radio, Tape Recorders, or monitoring tape recordings, magnetic low impedance or Crystal High Impedance. Complete with 4ft. of lead and miniature Jack Plug. **PRICE 10/6 P. & P 1/6**

## ACOS MONAURAL STETHOSCOPE HEADSETS

Suitable for Tape Recorders, or monitoring tape recordings, 100 ohm impedance magnetic. Complete with 4ft. lead. (Originally 21/-) **OUR PRICE 12/6 P. & P 1/6**

SEE FOLLOWING PAGES FOR ADDRESSES AND DETAILS OF OTHER STERN-CLYNE PRODUCTS

Great Britain's Greatest Electronic Hobbies Organisation

# STERN-CLYNE

## NEW LOW PRICES — NOW YOU CAN AFFORD A CAR RADIO



### THE 'HIGHWAYMAN'

#### OUR QUALITY CAR RADIO TO BUILD YOURSELF AT A NEW LOW PRICE

Look at these features:

- ★ Attractive styling.
- ★ Push-pull output.
- ★ Three latest Mullard transistors plus valves types EBF83 and ECH84.
- ★ No Buzz, high output and sensitivity.
- ★ Printed circuit (latest type), 7 x 4 in. high flux p.m. speaker and baffle.
- ★ Medium and Long Waves.
- ★ Push button for fingertip control.
- ★ Extremely low battery consumption (less than 1 amp).
- ★ Easy to fit any make car. (Positive earth only.)
- ★ 12-volt operation.
- ★ Compact size, measures only 7 x 7 x 2 1/2 in. deep.
- ★ Easy assembly, supplied with dial and drive already mounted.

Special inclusive price of ONLY **£7.19.6** Plus 5/- P. & P.

All parts available separately. Individually priced parts list and comprehensive instruction booklet 2/6 post free. (Deducted from cost if complete parcel purchased later.)



### THE "AIR KING"

Our highly successful six-transistor luxury portable with the "SLIM LINE" look. To build yourself, with printed circuit chassis for reliability and simplicity in construction. May be used as Car Radio, with full MEDIUM wave and LONG wave coverage.

Look at these features:

- ★ 500 milliwatt output to high flux 7 x 3 1/2 in. high fidelity loudspeaker
- ★ Six selected MULLARD TRANSISTORS in latest super-sensitive circuit plus germanium diode.
- ★ Compact size only 9 1/4 x 3 1/2 x 1 1/2 in. high.
- ★ Attractive three-tone cabinet, black, dark grey and silver grey with gilt control knobs and all gilt fittings.
- ★ Coax. socket for car aerial.
- ★ Brand new guaranteed components.
- ★ Push-pull output.
- ★ Automatic volume control
- ★ Long-life battery.
- ★ Super-sensitive internal Ferrite rod aerial.

Special Inclusive price for all required components. ONLY **£7.19.6** (Plus P. & P. 4/-). Alignment service available. Full assembly details and individually priced parts list, all of which are available separately, price 1/6 post free.



### The NEW CHASSIS PUNCH SET

Five of the most used Hole Punches made of the finest hardened steel will save hours of tedious hand labour, suitable for Aluminium, Sheet Metal, Plastic, etc. Punch Sizes 1/16", 1/8", 1/4", 3/8" complete with Tommy Bar, Tapered Reamer, and Zip Fastening Carrying Case. PRICE **49/6** P.&P. 3/6

SEND FOR CURRENT PRICE LIST OF ALL LEADING RECORDING TAPES AND ACCESSORIES

### THE HE30 4-BAND COMMUNICATION RECEIVER



One of the finest general coverage bandspread Receivers available at this price. Covering 550Kc/s—160Kc/s, 4.8Mc/s—14.5Mc/s, 1.6Mc/s—4.8Mc/s, 10.5Mc/s—30Mc/s. Illuminated slide rule dial, calibrated every 5Kc/s on 80 and 40 metres. Edgewise S-meter, 0.100 logging scale, coverage from 0.55—30Mc/s, 8 valve plus Rectifier superhet circuit. RF Stage with

an Aerial Trimmer, 2 IF Stages, B.F.O. control Q-multiplier, Controls: Function Switch, Audio Gain, Selectivity (Q-multiplier), Frequency (B.F.O.), Band Selector, IF Gain, Trimmer, AVC-MVC Switch, Ant Switch, Main Tuning, Bandspread Tuning and Headphone Jack, Selectivity—60dB at 10Kc/s, 0.8Kc/s at 6dB (with Q-Multiplier) IF-45Kc/s. External PM Speaker reqd., 4 or 8 ohms impedance, Output 1.5 watts, 4 modern Miniature B7G Base Valves and 5Y3 Rectifier. Size 15 x 10 x 7 1/2 in. Grey crackle finish. 220/240 volt A.C. mains, 50-60 cycle operation. Full instructions and circuit diagram supplied. Send S.A.E. PRICE **40 Gns.** Carriage for leaflet. Paid.

SEND STAMP FOR COPY OF OUR INTERESTING LITTLE BOOKLET "What is High Fidelity?"

SEE PRECEDING PAGE FOR OTHER STERN-CLYNE PRODUCTS

### THE "TRAVLER" MkII

Introducing our new ready-built transistorised car radio for ONLY **9 1/2 Gns.** P. & P. 5/- including 7 x 4" speaker fitted to baffle, fixing brackets, filter unit, all nuts and bolts with fitting instructions **£2.19.6** H.P. Terms: Dep.



(Plus 5/- P. & P.)

and 7 monthly payments for £12.6. Star Features ★ Handsomely Styled. ★ Mullard Valves and Transistors. ★ Push Buttons. ★ 11 watts Output. ★ Long and Medium Wavebands. ★ Quality Speaker (E.M.I.). ★ Easily Fitted. Radio Luxembourg (and many other foreign stations) 12 volt Positive Earth Only (applies to 99.8% of the cars on the road). ★ Dimensions 7 x 2 x 7" depth.

Optional extras, 3 section chromium plated weatherproof telescopic aerial, type 1 17/44", 19/6; type 2, 27/43", 29/6, both plus P. & P. 2/6 if purchased separately.


### THE MINICO JUNIOR TRANSISTORISED TAPE RECORDER

Record anywhere any time. A truly portable versatile Recorder with a difference, the highly sensitive Crystal Microphone is built into the Zip Carrying Strap which leaves both hands free to operate your Cine Camera, the Microphone can be removed for office use as a Dictating Machine or for Parties. Outstanding quality of reproduction and tone, up to 45 mins. playing time with track and operating on 4 1/2 volt Half-Pen Batteries. Robust metal body, size 6 1/2 x 4 1/2 x 2 1/2", weight 33 ozs. Usual price 16 gns. complete with Microphones. OUR PRICE **£6.19.6** P. & P. 4/- Tape and Battery.


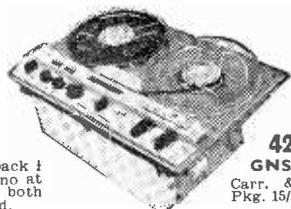
### STEREO TAPE DECK WITH BUILT IN PRE-AMPLIFIER

A professional addition to your Hi-Fi Stereo System consisting of two basic Units, the Tape Deck and Pre-amplifier, which employs 4 Transistors and 4 Valves. The Unit with record and playback 1 track stereo or 1 track mono at either 7 1/2 i.p.s. or 3 1/2 i.p.s. both speeds being fully equalised.



42 GNS. Carr. & Pkg. 15/-

Features: Track System: 1 track 2 channel stereo or mono record and playback. Independent single channel recording on either channel while playback on other channel. Head Type: 1 track 2 channel inline stereo and associated erase heads. Low loss laminated pole pieces. Level Indicators: 2 Meters, 1 per channel. Digital Counter: 3 digit tape position indicator. Automatic Stop: When tape runs out or breaks. Inputs: Microphone 1mV 60K, ohms impedance) Gram/Tuner 50mV (high impedance). Output: (cathode follower). Monitor Sockets: 2 x 5K, ohms impedance. Audio Output: 500mV. Oscillator: Push-pull 80Kc/s. S/N Ratio: —45dB or better at 7 1/2" tape speed. Separation: to 45dB or more between stereo channels. Frequency Response: 40 to 15,000 cycles per sec. at 1 i.p.s., 40 to 9,000 cycles per sec. at 3 1/2 i.p.s. Single Motor: 4 pole heavy duty induction type. Power Supply: 240V A.C. 50 cycles. Size 6 1/2 x 10 1/2 x 15". Tape Size: Up to 7". Line Up: 4-25B173 Transistors, 2-12AT7, 1-1A07, 1-12BH7 Valves.

### THE HE-40 4-BAND COMMUNICATION RECEIVER

Completely built ready to go. High sensitivity Superhet receiver covering 550 Kc/s—1,600 Kc/s, 1.6 Mc/s—4.4 Mc/s, 4.4 Mc/s—11 Mc/s 11 Mc/s—30 Mc/s. Electrical Bandspread tuning. Slide rule type tuning dial. Internal ferrite rod aerial for medium waveband reception and 1 5/8 in. 10 section chromium plated telescopic whip aerial for the short wave bands. Sockets for optional outdoor aerial. Internal high flux monitor loudspeaker. Latest modern miniature B7G base valves. Headphone socket (may also be used for external loudspeaker). A.V.C., B.F.O. built-in "S" meter. 220/240 volt A.C. mains, 50-60 cycle operation. Handsomely styled cabinet with grey crackle finish and handsome front panel, with chrome and satin chrome fittings. Measures 13 1/2 in. x 8 1/2 in. x 5 1/2 in. (high) and weighs only 1 1/2 lbs. A comprehensive instruction manual is supplied. An ideal receiver for the radio amateur and short wave listeners of all ages.



Send S.A.E. for leaflet. PRICE **£24.15.0** Carriage Paid.

**INTRODUCTION OFFER !! Available Shortly**



**FOR ONLY 48 gns.**



Plus 15/- Pkg. & Carr.  
**THE TUDOR STEREO HI-FI SYSTEM**, comprising a Self Powered AM/FM Tuner, Stereo Pre-amplifier, 12 watt per channel Stereo Power Amplifier. The Tuner and Pre-amplifier are housed in matching black crackle finish metal cabinets for shelf mounting, with silver metal dials and matching knobs. Specifications: Tuner—Outstanding quality, providing full VHF/FM long and medium waveband coverage, frequency range FM 87.5-108.5 Mc/s, AM/MW 522-1630 Kc/s, LW 145-270 Kc/s 100mV output mains supply 105/240 A.C. Valve line-up: ECC85, ECH81, EF89, EB91, EM84, ECC83. Multiplex outlet provided. Pre-amplifier—Designed for use with the Tudor Stereo Power Amplifier with inputs for most types of Pickups, direct play from Tape-Heads and ample sensitivity for either Crystal or Moving Coil Microphone. Distortion 0.1%, tape outputs 100mV from 90K ohm source inputs—Microphone 5 mV, Tape 5.3 mV, R.I.A.A. 4.3 mV flat 250 mV, Tuner 100 mV. Valve line-up: 2—EF86, 4—ECC83. Power Amplifier—14 watts per Channel, sensitivity 1 volt g.n.s., for 14 watts output, frequency response  $\pm 0.5dB$  20 c/s. —20 Kc/s. Speaker impedance 4, 8 or 16 ohms, surplus power available for Tape Pre-Amp, mains supply 105/240 v. A.C. Valve line-up: 2—ECC83, 4—EL84, 1—CZ34.

**DOUBLE FEATURE PRE-AMPLIFIER AND JL10 POWER AMPLIFIER**

A new conception in the field of audio engineering by Stern-Clyne development engineers. The most up-to-date circuitry is used in the Double Feature Pre-amplifier. It has matched inputs for microphone, crystal or magnetic pick-ups and radio tuner and in addition offers full facilities for tape recording and high fidelity replay. This unique feature means that should you wish to include tape in your hi-fi system at a later date all that is required is a suitable tape deck. Offers superb reproduction from all sources at low cost. Available shortly. Brief specifications:

**★ J.L.10 POWER AMPLIFIER**



Incorporates the latest triode-pentode ECL86 valves in push-pull. PARTRIDGE ultra linear output transformer, PARTRIDGE mains transformer and smoothing choke. 10 watt power output, surplus power available for tuner. Output impedance 3-7.5-15 ohm.

KIT OF PARTS **11 Gns.** C.&I. 7/-  
 READY BUILT **14 Gns.** 7/-

**★ DOUBLE FEATURE PRE-AMPLIFIER**



Inputs for microphone, crystal or magnetic pick-ups, tuner unit, Push-button switching for 3 tape speeds equalised. Tape erase Bias Oscillator circuit incorporating ferro-cube transformer. Function switch, separate base, treble and volume controls, level control and latest EM87 magic eye level indicator. The pre-amplifier is totally enclosed in a silver hammer finish steel case, and an attractive perspex front panel completes the presentation.

KIT OF PARTS **£17.0.0** READY BUILT **£21.0.0** C. & I. 5/-  
 PRICES: If both above units purchased together:  
 KIT OF PARTS **£27.10.0** READY BUILT **32 Gns.** C.&I. 10/-



**MODEL CR3'S TAPE RECORDER**

MODEL CR3'S incorporates the HF/TR3 Mk. II Tape Amplifier (described below) and the Collaro "Studio" Twin Track 3-speed Deck operating at 1 1/2 in., 3 in., and 7 in. speeds. Complete with microphone and 1,200ft. tape.

KIT OF PARTS **£33.8.0**  
 ASSEMBLED AND TESTED **£43.0.0** (Carr. & Ins. 15/- extra).

**STEREO TAPE PRE-AMPLIFIER**

MODEL STP-1. For use with current TRUVOX, BRENNEL or COLLARO "STUDIO" 1 and 1 track Stereo Decks. Incorporates Ferro-cube Oscillator, 4-speed Equalisation Signal Level Meter and separate Gain Control. Includes separate Power Unit. KIT OF PARTS **£22.0.0** (Carr. & Ins. 8/6) ASSEMBLED **£28.0.0**



Instruction book and detailed price list (free with kit) available separately at 3/- Post Free.

**TAPE PRE-AMPLIFIER MULLARD Type "C"**

Suitable for most 1 track Mono Tape Decks. Incorporates Ferro-cube Push-Pull Oscillator, Treble Inductor and 3-sp. Equalisation. Includes separate Power Unit.



KIT OF PARTS **£14.0.0** (Carr. & Ins. 7/6) ASSEMBLED **£19.10.0**  
 Instruction book and detailed price list (free with kit) available separately at 3/6 Post Free.

**MULLARD TAPE AMPLIFIER**

**MODEL HF/TR3/MK.II**

Based on Mullard's Type "A" design and suitable for most 1 track Mono Tape Decks. Incorporates Ferro-cube Treble Inductor, Gilson Output Transformer, and 3-speed Equalisation. Includes separate Power Unit, using PARTRIDGE Mains Transformer.



KIT OF PARTS **£13.13.0** (Carr. & Ins. 7/6) ASSEMBLED **£19.0.0**  
 Instruction book and detailed price list (free with kit) available separately at 3/- Post Free.

**COMBINATION TAPE UNITS**

All our Tape Units can be supplied specially matched to any Tape Deck such as Collaro, Brennel Mk.5 Series II, also the Wearite. Specimen prices as below.

|   | Kit      | Assembled |
|---|----------|-----------|
| STP-1 Pre-amp with Collaro Studio Tape Deck                 | £36. 0.0 | £42. 0.0  |
| Assembled with track switch fitted, £44.2.0                 |          |           |
| STP-1 with Brennel Mk. 5 series II with Track Switch fitted | £69. 4.0 | £74.15.0  |
| STP-1 with Brennel Mk.5 Series II, 1 Track Deck             | £24.10.0 | £30. 0.0  |
| Type "C" Pre-amp with Collaro Studio Tape Deck              | £24.10.0 | £30. 0.0  |
| Type "C" Pre-amp with Brennel Mk.5 series II Deck           | £46.11.0 | £58. 1.0  |
| Assembled with deck wired and matched, £55.3.0              |          |           |
| HF/TR3 with Collaro Studio Tape Deck                        | £24. 3.0 | £29.10.0  |
| Assembled with deck wired and matched, £31.12.0             |          |           |
| HF/TR3 with Brennel Mk.5 Series II Deck                     | £46. 4.0 | £51.11.0  |
| Assembled with deck wired and matched, £55.13.0             |          |           |

(Carr. & Ins. 15/- on above units. Send S.A.E. for comprehensive price list.

**VISIT YOUR NEAREST STERN-CLYNE BRANCH**


|               |                                    |                   |                    |
|---------------|------------------------------------|-------------------|--------------------|
| WEST END:     | 18 Tottenham Court Road, W.1.      | MUSEum 5929/0095  | Half-day Sat       |
|               | 23 Tottenham Court Road, W.1.      | MUSEum 3451/2     | Half-day Thurs     |
|               | 309 Edgware Road, W.2.             | PADddington 6963  | Half-day Thurs     |
| CITY:         | 109 Fleet Street, E.C.4.           | FLEet St. 5812/3  | Half-day Sat       |
| NORTH LONDON: | 162 Holloway Road, N.7.            | NORTH 8161/5      | Half-day Thurs     |
| SOUTH LONDON: | 9 Camberwell Church Street, S.E.5. | RODney 2875       | Half-day Thurs     |
| CROYDON:      | 12 Suffolk House, George Street.   | MUNicipal 3250    | Half-day Wed       |
| BRISTOL:      | 26 Merchant Street, Bristol 1.     | Bristol 20261     | Half-day Wed       |
| MANCHESTER:   | 10 Withy Grove, Manchester 4.      | BLAck Friars 5379 | Open 6 days a week |
|               | 162 Holloway Road, London, N.7.    | NORTH 8161/5      |                    |

Mail Orders and enquiries to Dept. P.W.

**Great Britain's Greatest Electronic Hobbies Organisation**

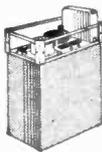**WIRELESS SET NO. 38 AFV**

A lightweight portable transmitter/receiver with transmitting range 5 to 10 miles and frequency covers range 7.4 to 9 Mc/s. Operates from 3 and 120 v external dry batteries. Large, clearly numbered tuning control, with tuning lock, in good condition.



ONLY **39/6** Plus 5/- P. & P. 3d.

**HIGH IMPEDANCE PERSONAL LISTENING EARPIECES**


Suitable for all types of crystal sets and transistor sets. Complete with plug. **5/11** P. & P. 6d.

**PORTABLE MAINS SOLDERING IRON**

30 watts. Features removable handles that cover tin and barrel. Complete with lead and plug. **12/6**

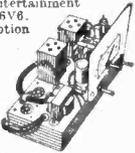**SUPERHET RADIO CHASSIS**

These well-made chassis were made for the Government for Forces entertainment with 6K8, 6K7, 6R7, 6V6. Choke smoothed slow-motion tuning, printing scale, 290-550 metres. BRAND NEW, complete with valves and 6 volt Power Pack. Cabinet with 8 in. speaker to fit. Complete in maker's cartons. **£3.19.11** P. & P. 5/-



**SUPERB STREAMLINE MICROPHONE**

Omal-directional response 60-10,000 c/s. Output level 52 dB. Built in on/off switch. Provision for conversion to hand held, cord suspended or stand mike. Attractive satin chrome finish.

Microphone **37/6** P. & P. 1/9  
Desk Stand **10/-** P. & P. 1/9  
Floor Stands Available

**LIGHTWEIGHT HIGH IMPEDANCE HEADPHONES**

Ideal for crystal sets **12/6** P. & P. 1/6 and Morse practice.

**TODAYS SUPREME VALUE IN AMPLIFIERS!**

BRITISH MADE GORLER TYPE AMPLIFIER GS12005. All-transistor subminiature quality amplifier 60-16,000 c/s  $\pm 3dB$ , 70-14,000 c/s  $\pm 1dB$ , 5mV for 1 watt out at 7v. **92/6** Built and tested.

**EXTENDABLE BELLING AND LEE CAR AERIAL**

Fits any car anywhere. Complete with plug and suction pads. **12/6** P. & P. 1/-

**PORTABLE INTERCOM/ELECTRONIC BABY SITTER**

Amazing Transistor intercom system with approx. 66 ft. connecting flex. 9V Battery 2/6 extra. Every sound relayed. Two way buzzer, call and speak system. Also usable on wall or desk. P. & P. 2/6. **£3.3.0**



**I155 INSTRUCTION HANDBOOK**

**3/11** P. & P. 3d.



**TRANSISTOR SALE**

- Mullard OC 44.....3/11 P. & P. 3d.
- Mullard OC 45.....3/11 P. & P. 3d.
- Mullard OC 71.....2/11 P. & P. 3d.
- Mullard OA 90.....1/11 P. & P. 3d.
- Ediewan X1202 Germanium diodes.....1/11 P. & P. 3d.
- Transistor Holder, 3-pin 11d. each P. & P. 3d.

**MICRO ALLOY TRANSISTORS**

- Mat 100.....7/9
- Mat 101.....8/6
- Mat 120.....7/9
- Mat 121.....8/6
- VHF Transistor ADT140.....15/- Above MAT's Postage Paid.

Ferrite Slab Aerials, suitable for transistor sets. 3/- P. & P. 6d.

**TRANS. RADIO TUBULAR SPEAKER**

Booster Speaker. Plugs into ear-piece socket of most radios and tape recorders. Gives double the volume and a high stereo effect that will amaze you. size Approx. 9 x 2 1/2 in. PRICE **25/-** P. & P. 1/9.



**VALVES**

- 6R8G.....1/11 P. & P. 3d.
- 6K8.....3/6 P. & P. 3d.
- 6V6.....3/6 P. & P. 3d.
- 11L4.....4/- P. & P. 3d.
- 1T4.....4/- P. & P. 3d.
- 184.....5/6 P. & P. 3d.

**METER TEST KITS**


Comprising insulated leads and test prods. insulated croc. clips and meter terminal connectors. All contained in plastic hold-all. P. & P. 1/3  
Meter Test Prods. P. & P. 9d.

**9/11**

**4/11**

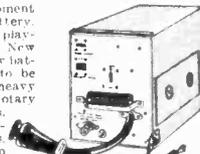**12 VOLTS CONVERTOR TO 240 VOLTS**


Run all your mains a.c.-d.c. equipment from your car battery. shavers, record players, radios, etc. New type vibrator, low battery drain, not to be confused with heavy battery drain Rotary transformers. Spare fuses, vibrator battery clips etc. 12 volts to 240 at 100 m.a.



BRAND-NEW, tested in waterproof cartons. ONLY **35/-** P. & P. 5/-

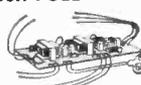**4 TRANSISTOR PUSH-PULL RADIO AMPLIFIER 49/11**

Complete with 3 ohm output transformer working from a standard 0 volt battery. Output in excess of 200 MW.



**TAPE RECORDER**

Fully portable. Twin tracked, 3 in. standard tape. 4-transistor. Wonderful tone from speaker. Complete with mike, batteries and transparent cover. **£8.10.0** Post 5/-



**CRYSTAL CALIBRATOR TEST SET No. 7 MKI**

New in Paxolin cabinet with circuit and instructions on rear panel. Calibrates transmitters AND receivers. 3 choices of calibration points: 10,100, 1,000 kc/s apart, harmonics up to 20 mc/s. Operates from 2v accumulator and 120v dry battery. P. & P. 3/6



**65/-**

**CRYSTAL SET**

Build your own crystal set and hear it work. Easy to build and tune. Picks up main stations. P. & P. 11d. **9/11** With personal 12/11 With head-phones ear-piece. P. & P. 11d **22/11** P. & P. 1/6



**TSL "KITBOARD"**

The newest thing for the transistor constructor. Better than a printed circuit board! Perfect for assembling modern subminiature components into the smallest possible arrangements. Perforated 10 holes to the inch. Strong, light. Suitable for all transistor equipment. Size 1 x 4 1/2 x 4 in. 3/6  
Size 2 x 2 1/2 x 4 in. 2/9

**LEAD ACID ACCUMULATORS (Unspillable)**

2 volt- 16 A.H. Brand New. Size 4 x 7 x 2 in. 4/11 each, 3 for 12/6. P. & P. 3/- per cell.



**OPERATORS' UNITS**

A host of valuable components (block condenser, lock plug, socket, etc.). ONLY 1/11 EACH, P. & P. 1/3

**IDEAL FOR CHILDREN 7 YEARS AND OVER—GENERAL ELECTRIC**

- Electronic construction kits made by General Electric. 4.
- 1. Electronic writing.
- 2. Put a satellite into orbit.
- 3. Build a burglar alarm system.
- 4. Weather Station, state which one one required.



**42/6** EACH P. & P. 2/-

**ELECTRONIC CONSTRUCTION KITS**

8 Radio Circuits, including more practice set. All components and single headphones provided. (No soldering necessary.) Post Free. **49/11**

**SONA SINCLAIR SLIMLINE**

Gives choice of British and European programmes with staggeringly good quality and selectivity. Building is easy and interesting, and as well as providing superb listening through the earpiece, the "Slimline" makes a wonderful radio jack too. FULL coverage of medium wave-band. Extremely robust construction. **49/6**



**HANDY METAL COMPONENT CASES**

Hinged lid. Size 6 1/2 x 6 x 2 in. Padded inside, many uses. 2/6 each, 2 for 4/6. P. & P. 1/- each.



**MORE BARGAINS OPPOSITE**

**RF FIELD INDICATORS**

Designed for checking the radiation from a transmitting antenna. The sensitivity can be controlled by adjustment of panel control; the antenna length, or by increasing distance from the radiator. Frequency range 1-250 mc/s. 200mA D.C. Complete with instruction book.



69/6

**HAWAIIAN PORTABLE RECORD PLAYER**

Uses a unique pick-up unit, burnable and speaker to give amazing volume and reproduction. Battery operated, plays up to 12hr. records at 33 $\frac{1}{3}$  or 45 r.p.m. Separate fine speed and volume controls. 45 r.p.m. adaptor. Plastic cabinet. Fully waterproof with carrying handle and record storage compartment. Size 9in. dia. x 3in. deep. Weight 2 lb. 9 ozs. PRICE **£8.19.6**



**DOUBLE THROAT MICROPHONE**

Can be adapted for use with musical instruments. 4/11 P. & P.

**MORSE KEYS**

Morse Key assembly with base and cover. Complete with lead.



FRAND 6/11 P. & P. NEW

**HOOVER ROTARY TRANSFORMERS**

11.5v. input. 490v. output at 60mA. From 6v. input and approximately 450v. output at 75mA. PRICE 9/11 P. & P.



**BATTERY CHARGE ADJUSTERS**

- Charge Rate Adjuster.
- Government manufacture.
- Easily fitted to charging circuit.

3/6 each. 2 for 6/6. P. & P. 1/- each.

**BELLING & LEE SPARKMASTER**

1. Reduces plug burning.
  2. Eases starting from cold.
  3. Minimises pinking.
- 2/6 each. P. & P. 6d.



**No. 19 TRANSMITTER RECEIVER**

Trans Receiver covers 2-8 Mc/s. (150-37 metres in two bands). Has an intercom amplifier. Designed for 12 and 24 volts operation. Uses a 6-valve superbet receiver, I.F. being 465 Kc/s. and a 6-valve transducer designed for voice and C.W. operation. Incorporates test and tuning meter for voltages, aerial loading and current tests. Panel controls: frequency tuning, P.A. tuning, gain control, MCW, C.W., R.T. switch, Het-tone netting. Off-on quench aerial. AVC. I.T.-HT-drives test. ONLY 47/6 P. & P.

19 SET CONNECTORS 8 pin 10/6 P. & P. 1/6 5/-

19 SET CONTROL BOX. EACH 4/11 P. & P. Single Type. 1/6 5/11 P. & P. Each 1/9

INSTRUCTION HANDBOOK 3/6. With Aerials (U.S.A.) 6 ft. 6 in. 7/6. P. & P. 2/6. 5 ft. 4/- P. & P. 1/3. Canadian Model 10/- Extra.

**COMPONENTS**

SMOOTHING CHOKES. 100 mA. 10-20 H. resistance. 450 ohms. Sturdy construction. 4/11 P. & P. 2/6

SMOOTHING CONDENSERS. T.C.C. metal enclosed block condenser. 47, 24, 12µ, with terminals. 8 mfd. 350 v. working. Suitable for cross-over units. 3/11 P. & P. 1/6

MAINS TRANSFORMER. Mains standard primary 250 0.250 v. 80 mA. 6.3 v. coils at 4 amps. 5 volts at 2 amps. Both tapped at 4 v. 18/11 each P. & P. 2/6

As above 250-0-250 v. sec. 19/11 P. & P. 2/6

FILAMENT TRANSFORMERS. 200/250v. 50 c/s primaries. 6.3 v. at 2 amps. 8/11 P. & P. 1/3

PAXOLIN TAG STRIPS (14 tags). Double wave. 1/3 each P. & P. 6d.

7-WAY TAG STRIP. 5d. each P. & P. 1/3

PANEL MOUNTING FUSE HOLDERS. Beautifully made, plastic sturdy construction. 2/11 each P. & P. 6d.

ELECTROLYTIC CONDENSERS. 0.05 mid. T.C.C. 350 v. working. 1/- each P. & P. 3d.

OCTAL MOULDED VALVE HOLDERS. 6d. 3 for 1/3. 807 valve holders. 9d. 3 for 2/-.

87G valve holder. ceramic moulded with screening skirt. 9d. 3 for 2/- P. & P. on each 3d.

CONDENSERS. Variable condenser solid dielectric. 0.0005 mFd. 3/3, P. & P. 9d.

TRIMMERS. 0.750 mFd. max. 9d. P. & P. 3d.

CONDENSERS 50 mFd. electrolytic reversible. 12 v. working. 1/3, P. & P. 3d.

1 mFd. CONDENSERS. 150 v. working. Suitable as suppressors. 1/11. P. & P. 6d. 470 pf. 10% tolerance. 7/0 v. working. 7d. P. & P. 3d.

**SENSITIVE MULTIMETER**

20,000 ohm per volt. 1% resistor used throughout. Single control system for all ranges. Compact and lightweight. Highly accurate. **£5.10.0** P. & P.



**AMERICAN RECORDING TAPES**

3in. 600ft. Std. 8/- P. & P. 2/-  
 5in. 450ft. Std. 14/6 P. & P. 2/-  
 7in. 1,200ft. Std. 15/- P. & P. 2/-

**Tape Splicer**

Precision made, chrome finish, heavy base. 12/6. P. & P. 1/6.

**TEST SET 253**

Range 20-88 mc/s in 4 bands. Vernier tuning. Optional pulsed output with fine tuning 50 c/s mains operation. Noise generator. Strongly made. With metal carrying case. Contains many valuable components: 9 valves, full wave rectifier unit, 3 crystals, meter, mains transformer, numerous switches, P. & P. chokes, condensers, etc.



52/6 5/-

**HI-FI GT. 50 RADIO JACK**

MAKE A RADIO RECEIVER OUT OF YOUR AMPLIFIER. Full medium wave. Ideal for all tape recorders, amplifiers, etc. No batteries required—just plug in.



29/-

**VARIABLE RESISTORS**

Large sturdy wirewound variable resistors. Diameter 3in. length (with spindle) 3 1/2 in. Made by Marconi. 12/11 P. & P. 1/-



Miniature wire wound variable potentiometers. 6 ohms, 100 ohm, 60 ohm. EACH 2/11

**RESISTORS**

Special offers. High quality 1 and 1/2 watt resistors. All preferred values (state values required). 10Ω-10 meg. ohm. 3rd. each, 6 for 1/6. 12 for 2/9, 24/- for 100.

**HEAVY DUTY RF CHOKES ON STAND**

Suitable for transmitting circuits. P. & P. 1/6 4/11

**MOVING COIL HEADPHONES AND MICROPHONE ATTACHED**

Suitable for 19 set. Not new. P. & P. 2/3 6/11

**TEST SET TYPE 46**

Will radiate a continuous note. Range 1250 Kc/s — 23,500 Kc/s (12-240 meters). 5 switched bands. Contains VR21 valve and as precision slow motion tuning unit enclosed in grey metal case; rod aerial base on side, good condition. Power requirements 2V. 90-120V. Battery 49/6 P. & P. 5/- space provided.



**SIX TRANSISTOR RADIO**

Just arrived! Superb pocket radios. Gives terrific reception, station after station; home and abroad. Attractive finish. Perfect toned speaker. With personal earpiece. **£3.19.11** P. & P. 5/-

PERSONAL CALLERS WELCOME AT OUR NEW BRANCH BELOW:



TRADE SUPPLIED

SONA ELECTRONIC CO. (Dept. PW3), BRIGGATE HSE., 13 ALBION PL., LEEDS

TERMS:  
 CASH WITH  
 ORDER  
 5/- EXTRA ON  
 C.O.D. ORDERS

**FINEST RANGE OF NEW GUARANTEED VALVES AVAILABLE**

*- all these and hundreds more*

**24 HOUR SERVICE**

**TERMS OF BUSINESS C.W.O. or C.O.D.**

**4/2 PACKING CHARGE ON ALL C.O.D.**

**ORDERS. POSTAGE 6d. PER VALVE**

Open 9 - 5.45. e.c. Wednesday

**ORDER**

Please Supply Valve(s) Nos. ....

NAME .....

ADDRESS .....

.....

.....

C.W.O. £                      C.O.D. (+ 4/2) Postage                      X

**R.S.T. VALVE MAIL**  
**211a STREATHAM**

**All Valves Brand New and Fully Guaranteed — Obsolete valves a speciality.**  
**Quotations given on any type not listed. Send S.A.E.**

*Special 24 Hour Express Mail Order Service*

|                           |                |              |                     |              |                   |              |                |              |                  |              |                |              |                  |              |                   |              |
|---------------------------|----------------|--------------|---------------------|--------------|-------------------|--------------|----------------|--------------|------------------|--------------|----------------|--------------|------------------|--------------|-------------------|--------------|
| AC2/PEN<br>19/6           | ECC88<br>ECC91 | 12/6<br>3/-  | EY86<br>EY91        | 7/-<br>3/-   | PABC80<br>PCC84   | 13/-<br>7/-  | SP61<br>T41    | 3/6<br>15/-  | UL85<br>UM80     | 7/6<br>10/6  | 6A7<br>6A8B    | 9/-<br>8/6   | 6L19<br>6N7GT    | 15/-<br>9/6  | 12Q7GT<br>12S7A   | 6/-<br>8/6   |
| AC2 PEN<br>DD             | ECF80<br>ECF82 | 7/6<br>8/6   | EZ35<br>EZ40        | 6/-<br>7/-   | PCC85<br>PCC88    | 9/6<br>12/6  | TDD4<br>TDD13C | 12/6<br>12/6 | URIC<br>U6       | 15/-<br>1/6  | 6A8GT<br>6A7   | 13/6<br>6/-  | 6P25<br>6P28     | 10/6<br>12/6 | 12S7J<br>12SK7    | 8/-<br>6/-   |
| AC/TP1 29/-<br>AC/VP1-5-7 | ECH3<br>ECH21  | 21/6<br>21/- | EZ41<br>EZ80        | 7/-<br>5/6   | PCC89<br>PCF80    | 8/6<br>7/6   | TH41<br>TY86F  | 17/6<br>12/6 | U8<br>U9         | 15/-<br>7/6  | 6A5<br>6A5     | 5/-<br>5/-   | 6Q7<br>6Q7G      | 9/-<br>6/-   | 12S7L<br>12SN7    | 8/-<br>10/-  |
| AZ1<br>AZ31               | ECH35<br>ECH42 | 10/6<br>9/6  | EZ81<br>EZ90        | 5/6<br>4/6   | PCF82<br>PCF84    | 7/6<br>12/6  | U10<br>U11     | 12/6<br>15/6 | UY1<br>UY21      | 12/6<br>15/6 | 6A5<br>6A6     | 5/-<br>6/-   | 6Q7GT<br>6A7     | 8/6<br>7/6   | 12S7Q<br>14H7     | 12/-<br>10/- |
| B36<br>CIC                | ECH83<br>ECL80 | 8/6<br>6/6   | E1148<br>FC2        | 21/-<br>17/6 | PCF86<br>PCL82    | 7/6<br>9/-   | U12<br>U14     | 9/-<br>9/-   | UY41<br>UY85     | 7/6<br>6/-   | 6A6<br>6A6     | 6/6<br>6/-   | 6S7<br>6S7       | 8/6<br>7/6   | 14R7<br>19AQ5     | 10/-<br>8/-  |
| CCH35<br>C33              | ECL81<br>ECL82 | 10/6<br>9/6  | FC4<br>FW4/500      | 15/-<br>9/6  | PCL84<br>PCL85    | 7/-<br>7/6   | U22<br>U24     | 8/-<br>21/-  | YP4<br>YP4A      | 15/-<br>15/- | 6A6<br>6A6     | 6/-<br>6/-   | 6S7<br>6S7       | 7/6<br>6/6   | 19B6G15/-<br>20D1 | 10/-<br>21/- |
| DAF91<br>DAF96            | ECL83<br>ECL86 | 10/6<br>9/6  | FW4/800<br>GZ30     | 9/6<br>10/6  | PCL86<br>PEN4A    | 12/6<br>19/6 | U25<br>U31     | 11/-<br>9/6  | YP4B<br>YR150/30 | 15/-<br>7/6  | 6B6<br>6B6G    | 6/-<br>15/-  | 6S7<br>6S7GT     | 6/6<br>5/6   | 20F2<br>20L1      | 17/6<br>22/6 |
| DK92<br>DK96              | EF6<br>EF9     | 21/-<br>21/- | GZ32<br>GZ33        | 10/6<br>19/3 | PEN4D<br>PEN4A    | 22/6<br>17/6 | U35<br>U37     | 17/6<br>17/6 | W61<br>W76       | 11/-<br>5/-  | 6B7<br>6B7     | 12/6<br>12/6 | 6S7<br>6U4GT     | 10/6<br>10/6 | 20P3<br>20P4      | 24/-<br>20/- |
| DK99<br>DF33              | EF22<br>EF23   | 14/-<br>8/-  | GZ34<br>GZ34        | 19/3<br>13/6 | PEN4A<br>PEN36C   | 17/6<br>20/- | U47<br>U50     | 11/-<br>7/-  | W77<br>W81       | 4/-<br>6/-   | 6B7<br>6B7     | 12/6<br>9/6  | 6U5G<br>6V6GT    | 7/6<br>4/-   | 20P5<br>25A6      | 20/-<br>8/-  |
| DF91<br>DF92              | EF37<br>EF37A  | 8/-<br>8/-   | HABC8010/-<br>HL41  | 8/-<br>8/-   | PEN45<br>PEN45DD  | 20/-<br>10/6 | U52<br>U78     | 4/-<br>4/6   | W81M<br>X41      | 6/-<br>22/6  | 6B7<br>6B7     | 12/6<br>3/6  | 6V6<br>6X4       | 4/6<br>4/6   | 25Y5<br>25Y5G     | 8/-<br>8/-   |
| DF96<br>DH63              | EF40<br>EF42   | 15/-<br>10/6 | HL41DD<br>HL92      | 8/6<br>8/6   | PEN45DD<br>PEN46  | 25/-<br>5/-  | U78<br>U251    | 4/6<br>15/-  | X61M<br>X65      | 10/-<br>12/6 | 6C5GT<br>6C6   | 8/6<br>6/6   | 6X5G<br>6X5GT    | 5/6<br>8/6   | 25Z4<br>25Z5      | 7/6<br>8/-   |
| DH77<br>DK32              | EF50A<br>EF50E | 3/6<br>3/6   | HL133DD<br>HN309    | 9/6<br>25/-  | PEN46<br>PEN453DD | 5/-<br>40/20 | U251<br>U281   | 15/-<br>19/6 | X76M<br>X78      | 12/6<br>26/6 | 6CD6G<br>6CH6  | 25/-<br>16/- | 7B5<br>7C5       | 12/6<br>8/-  | 25Z6<br>275U      | 8/6<br>19/6  |
| DK91<br>DK92              | EF80<br>EF85   | 5/-<br>5/-   | IW4.350<br>IW4.500  | 10/-<br>10/- | PENDD4020<br>PL33 | 20/-<br>15/- | U281<br>U301   | 19/6<br>18/6 | X79<br>Y61       | 40/-<br>10/- | 6CW4<br>6D2    | 16/-<br>10/- | 7C5<br>7C6       | 8/-<br>8/6   | 30C1<br>30C15     | 9/-<br>12/6  |
| DK96<br>DL35              | EF89<br>EF91   | 8/-<br>4/-   | KT33C<br>KT36       | 8/-<br>9/6   | PL33<br>PL36      | 15/-<br>12/6 | U301<br>U329   | 18/6<br>15/- | Y63<br>Y63       | 10/-<br>10/- | 6D6<br>6E5     | 5/6<br>10/6  | 7D5<br>7D6       | 15/-<br>15/6 | 30F1<br>30L1      | 10/6<br>8/6  |
| DL91<br>DL92              | EF92<br>EF95   | 4/-<br>5/-   | KT61<br>KT66        | 9/6<br>15/-  | PL38<br>PL81      | 18/-<br>7/6  | U329<br>U339   | 15/-<br>13/6 | Z63<br>Z66       | 7/6<br>10/6  | 6F1<br>6F6     | 10/6<br>6/6  | 7D8<br>7H7       | 15/-<br>10/6 | 30L5<br>30P4      | 11/-<br>18/- |
| DL93<br>DL94              | EF98<br>EF183  | 5/-<br>8/-   | KT78<br>KTW61       | 8/-<br>8/-   | PL82<br>PL83      | 7/6<br>7/6   | U339<br>U339   | 13/6<br>13/6 | Z77<br>Z152      | 4/6<br>5/-   | 6F2<br>6F13    | 10/6<br>10/- | 7H7<br>7Y4       | 6/6<br>6/6   | 30P4<br>30P12     | 18/-<br>10/- |
| DL96<br>EA50              | EF184<br>EK32  | 8/-<br>8/6   | L63<br>LN152        | 5/-<br>6/6   | PL84<br>PL820     | 7/6<br>18/-  | U339<br>U339   | 13/6<br>13/6 | IA7<br>IC5       | 11/-<br>10/6 | 6F14<br>6F15   | 10/6<br>12/6 | 8D3<br>9BY6      | 4/-<br>12/6  | 30P16<br>30P19    | 17/6<br>17/6 |
| EABC80<br>EAC91           | EL3<br>EL32    | 21/6<br>4/6  | LN152<br>LN309      | 6/6<br>9/6   | PL820<br>PM24M    | 18/-<br>13/6 | U339<br>U339   | 13/6<br>13/6 | ID5<br>ID6       | 8/6<br>10/6  | 6F19<br>6F23   | 12/6<br>10/6 | 10C1<br>10C2     | 12/6<br>12/6 | 30PL1<br>30PL13   | 15/6<br>15/6 |
| EAF42<br>EB34             | EL33<br>EL34   | 10/6<br>14/6 | LZ319<br>LKT4       | 12/6<br>17/6 | PX4<br>PX25       | 15/-<br>25/- | U339<br>U339   | 13/6<br>13/6 | IHS<br>IL4       | 9/6<br>5/6   | 6F25<br>6F26   | 16/6<br>16/6 | 10F1<br>10F9     | 10/6<br>12/6 | 30PL14<br>35A5    | 12/6<br>15/- |
| EB41<br>EB91              | EL35<br>EL37   | 10/6<br>17/6 | MS4B<br>MVS,PEN     | 17/6<br>17/6 | PY31<br>PY32      | 15/-<br>10/6 | U339<br>U339   | 13/6<br>13/6 | INS<br>IS4       | 5/6<br>7/6   | 6F33<br>6H6    | 5/6<br>2/6   | 10LD11<br>10P13  | 15/-<br>15/6 | 35L6GT<br>35W4    | 8/6<br>6/6   |
| EBC3<br>EBC33             | EL38<br>EL41   | 17/6<br>9/6  | MVS,PEN<br>MVS,PENB | 17/6<br>17/6 | PY33<br>PY80      | 10/6<br>7/6  | U339<br>U339   | 13/6<br>13/6 | IS5<br>IT4       | 5/6<br>4/6   | 6H6<br>6J5GT   | 2/6<br>5/6   | 10P14<br>11D5    | 19/6<br>23/6 | 35Z3<br>35Z4      | 15/-<br>6/6  |
| EBC41<br>EBC81            | EL42<br>EL81   | 9/6<br>12/6  | MU14<br>MX40        | 9/6<br>15/-  | PY81<br>PY82      | 7/6<br>5/6   | U339<br>U339   | 13/6<br>13/6 | IUS<br>IP        | 5/6<br>22/6  | 6J5<br>6J7     | 5/6<br>5/6   | 12A6<br>12A8     | 6/6<br>11/-  | 35Z5<br>41STH     | 8/6<br>22/6  |
| EBF80<br>EBF83            | EL84<br>EL85   | 6/9<br>10/6  | N18<br>N37          | 8/-<br>14/-  | PY83<br>PY88      | 8/6<br>10/6  | U339<br>U339   | 13/6<br>13/6 | IR5<br>IS4       | 5/6<br>7/6   | 6K7GT<br>6K7   | 7/6<br>7/6   | 12AT6<br>12AT7   | 7/6<br>5/6   | 50C5<br>50C6      | 11/-<br>11/- |
| EBF89<br>EBL1             | EL90<br>EL91   | 8/6<br>4/-   | N37<br>N78          | 14/-<br>26/- | PY88<br>PY800     | 10/6<br>10/6 | U339<br>U339   | 13/6<br>13/6 | IS5<br>IS4       | 5/6<br>7/6   | 6K7GT<br>6K7GT | 2/6<br>2/6   | 12AU6<br>12AU7   | 17/6<br>5/6  | 50CD6G<br>30/-    | 7/6<br>30/-  |
| ECC21<br>ECC35            | EL95<br>EM80   | 10/6<br>8/6  | N108<br>N308        | 15/-<br>18/- | PZ30<br>QS95/10   | 15/-<br>10/6 | U339<br>U339   | 13/6<br>13/6 | IS5<br>IT4       | 5/6<br>4/6   | 6K8<br>6K8G    | 9/6<br>9/6   | 12AX7<br>12BA6   | 7/6<br>5/6   | 50L6<br>75        | 8/6<br>8/-   |
| ECC40<br>ECC81            | EM81<br>EM84   | 8/6<br>8/-   | N339<br>N369        | 30/-<br>10/6 | R2<br>R16         | 10/-<br>17/6 | U339<br>U339   | 13/6<br>13/6 | IS5<br>IS4       | 5/6<br>7/6   | 6K8GT<br>6L1   | 9/6<br>10/6  | 12BE6<br>12BH7   | 7/6<br>10/6  | 78<br>80          | 7/6<br>7/6   |
| ECC82<br>ECC83            | EM85<br>EY51   | 10/6<br>7/6  | OD3<br>OZ4          | 5/-<br>5/-   | R19<br>R20        | 16/-<br>16/- | U339<br>U339   | 13/6<br>13/6 | IS5<br>IS4       | 5/6<br>7/6   | 6L1<br>6L6     | 10/6<br>10/6 | 12J5GT<br>12J7GT | 4/-<br>8/6   | 85A2<br>185BT     | 12/6<br>30/- |
| ECC84<br>ECC85            | EY81<br>EY83   | 8/6<br>12/6  | P2                  | 10/-         | SP41              | 3/6          | U339           | 13/6         | IS5              | 5/6          | 6L7<br>6L18    | 10/6<br>10/- | 12K7GT<br>12K8GT | 5/-<br>10/-  | 807A<br>807B      | 7/6<br>7/-   |

**COMPLETE VALVE LIST FREE WITH ORDER**  
**METAL RECTIFIERS**

|          |              |              |               |              |
|----------|--------------|--------------|---------------|--------------|
| RM1 7/6  | 14A86        | 23/-         | 16RD 2-2-8-1  | 12/- (FC142) |
| RM2 8/-  | 14A97        | 26/-         | 16RE 2-1-8-1  | 10/- (FC150) |
| RM3 10/- | 14A100       | 28/-         | 18RA 1-1-8-1  | 5/- (FC118)  |
| RM4 17/6 | 14RA 1-2-8-2 | 21/- (FC301) | 18RA 1-1-16-1 | 7/- (FC116)  |
| RM5 19/6 | 14RA 1-2-8-3 | 25/- (FC31)  | 18RD 2-2-8-1  | 16/- (FC124) |

**SETS OF VALVES**

|                               |     |     |                |
|-------------------------------|-----|-----|----------------|
| IR5, IS5, IT4, 35A, 3V4       | ... | ... | Set of 4, 17/- |
| DAF91, DF91, DK91, DL92, DL94 | ... | ... | Set of 4, 17/- |
| DAF96, DF96, DK96, DL96       | ... | ... | Set of 4, 25/- |

**BRAND NEW TRANSISTORS**

|          |          |                |
|----------|----------|----------------|
| OC44 5/- | OC74 8/- | OC81D 5/-      |
| OC45 5/- | OC75 8/- | OC81m/pr. 12/6 |
| OC71 5/- | OC77 8/- | OC82 6/-       |
| OC72 8/- | OC81 5/- | OC82D 6/-      |

**SILICON RECTIFIERS**


400 volts 350 mA ... .. 7/6 each

**ORDER CO.**

Tel: MITcham 6202  
 Open Daily to Callers

**ROAD MITCHAM SURREY**

ARMSTRONG AF208AM,FM RADIOGRAM CHASSIS

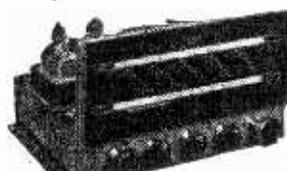

£21-4-0 (carriage free)

- FULL VHF BAND (87-108 Mc/s) and MEDIUM BAND 187-570 m.
- 5 WATTS OUTPUT, 7 VALVES.
- 16 db NEGATIVE FEEDBACK.
- WIDE-RANGE BASS AND TREBLE CONTROLS.
- 2 COMPENSATED PICK-UP INPUTS.
- FREQUENCY RESPONSE 50-22,000 c.p.s., ±2 db.
- TAPE RECORD AND PLAYBACK FACILITIES.
- CONTINENTAL RECEPTION OF GOOD PROGRAMME VALUE.

FOR 3, 7½ and 15 ohm SPEAKERS. Write for free literature.

New Boxed VALVES 90-day Guarantee

|      |     |       |      |        |      |       |      |
|------|-----|-------|------|--------|------|-------|------|
| 054  | 6/- | 8K7G  | 5/-  | E891   | 4/-  | PCF82 | 8/-  |
| 1R5  | 6/- | 6K8G  | 5/-  | E844   | 4/-  | PC182 | 10/- |
| 1R5  | 6/- | 6L6G  | 8/-  | E881   | 8/-  | PC184 | 10/- |
| 174  | 3/- | 6N7M  | 5/-  | E8F80  | 9/-  | PI81  | 10/- |
| 2X3  | 2/- | 607G  | 6/-  | E8H42  | 9/-  | PI83  | 10/- |
| 384  | 7/- | 6N7   | 5/-  | E8C81  | 9/-  | PV33  | 15/- |
| 3V4  | 7/- | 6V6G  | 5/-  | E8C80  | 9/-  | PY80  | 7/-  |
| 3Q4  | 7/- | 6X4   | 5/-  | E8L82  | 10/- | PY81  | 8/-  |
| 3U4  | 6/- | 6X5   | 6/-  | E8F86  | 8/-  | PY82  | 7/-  |
| 5Y4  | 6/- | 12A7  | 6/-  | E8F88  | 10/- | SP41  | 3/-  |
| 5Z4  | 6/- | 12A7  | 6/-  | E8F89  | 8/-  | HP61  | 3/-  |
| 6AC7 | 4/- | 12AX7 | 7/-  | E8L32  | 5/-  | U22   | 7/-  |
| 6AM5 | 4/- | 12BH7 | 7/-  | E8L84  | 7/-  | UB31  | 8/-  |
| 6AT6 | 6/- | 12K7  | 5/-  | EY81   | 9/-  | UB81  | 9/-  |
| 6BA5 | 7/- | 15K8  | 14/- | EY85   | 9/-  | UB89  | 9/-  |
| 6BE6 | 8/- | 12Q7  | 5/-  | EZ40   | 7/-  | UCH81 | 9/-  |
| 6BW6 | 7/- | 25Y6G | 9/-  | EZ80   | 7/-  | UL82  | 10/- |
| 6C4  | 5/- | 3L6G  | 9/-  | EZ81   | 7/-  | UL88  | 12/- |
| 6H6  | 6/- | 3Z54  | 5/-  | EAB300 | 10/- | UF88  | 8/-  |
| 6J6  | 4/- | 9C4   | 2/-  | EV82A  | 5/-  | UL41  | 8/-  |
| 6L6  | 3/- | DAF96 | 8/-  | KT38C  | 8/-  | UX41  | 7/-  |
| 6J5  | 6/- | DF96  | 8/-  | KT76   | 8/-  | UX85  | 7/-  |
| 6J5  | 5/- | DK96  | 8/-  | MU14   | 7/-  | U19   | 7/-  |
| 6L7G | 6/- | DL96  | 8/-  | PCN84  | 8/-  | VH150 | 7/-  |
| 6K6  | 5/- | ELC80 | 8/-  | PC80   | 8/-  | W81   | 6/-  |

NEW ELECTROLYTICS CAN TYPES

|        |     |            |     |               |      |
|--------|-----|------------|-----|---------------|------|
| 1300V  | 2/- | 50/350V    | 5/8 | 8/600V        | 9/-  |
| 2300V  | 2/5 | 100/25V    | 5/8 | 16/450V       | 5/-  |
| 4450V  | 8/5 | 250/5V     | 3/- | 16/600V       | 12/- |
| 4450V  | 8/5 | 500/12V    | 3/- | 16/16500V     | 7/8  |
| 16450V | 8/5 | 1,000/12V  | 3/- | 50/400V       | 6/8  |
| 32400V | 3/8 | 6,000/6V   | 5/8 | 32+32+350V    | 6/-  |
| 25250V | 1/8 | 8+8/450V   | 3/8 | 32+32+32+350V | 7/-  |
| 25500V | 1/8 | 8+16/450V  | 3/8 | 50+50/350V    | 7/-  |
| 50250V | 2/- | 16+16/450V | 4/8 | 64+120/350V   | 11/8 |
| 60500V | 2/- | 32+32/350V | 4/8 | 100+200/275V  | 12/8 |

TELESCOPIC CHROME AERIALS. 13in. extending to 43 in., 8/6 ea.

TRIPLETERS Bands 1, 2, 3, 19/6. COAX PLUG, 1/4-LEAD SOCKET, 2/-; PANEL SOCKETS, 1/-; OUTLET BOXES (Surge or dust), 4/- ea.

BALANCED TWIN FEEDER yd. 6d. 80 or 300 ohms. TWIN SCREENED per yd. 1/-, 80 ohms only.

Wirewound Ext. Speaker Control, 10 Ω 3/-, 25 Ω 6/6.

WIRE-WOUND POT, 3 WATT, Pre-set Min. TV Type. All values to 10 ohms to 25 K, 3/- ea. 30K., 4/- (Carbon 30 K. to 2 meg., 3/-).

WIRE-WOUND 4 WATTS Pots. Long spindle, Value, 50 ohms to 50 K, 6/8; 100 K., 7/6.

PHILIPS TRIMMER, 0.1 pF., 250 pF., 1/-.

TRIMMERS, Ceramic, 30, 50, 70 pF., 9d.; 100 pF., 10 pF., 1/3; 250 pF., 1/8; 500 pF., 750 pF., 1/9.

TV etc. TRIMMER, 1000 pF. with knob, 2/-.

RESISTORS, Preferred values, 10 ohms to 1 meg., 1 w., 5d.; 1 w., 4d.; 1 w., 6d.; 1 1/2 w., 8d.; 2 w., 1 w. High Stability, 1 w., 2/-; Preferred value 10 Ω to 10 meg. Ditto 3/8 to 22 meg., 9d.

BRIMSTORS, CZ1, 3/8; CZ2, 2/8; CZ3, 1/6.

|                    |                      |     |
|--------------------|----------------------|-----|
| 5 watt             | WIRE-WOUND RESISTORS | 1/3 |
| 10 watt            | 10 ohms-10,000 ohms  | 2/- |
| 15 watt            |                      | 3/- |
| 12.5K to 47K 10 w. |                      | 3/- |

**80 ohm COAX** Semi-air spaced 4in. stranded core. 40 yds. 17/6d. yd. 60 yds. 25/- Fringe Quality Air spaced 1/6 yd. Ideal 625 lines.

**Volume Controls** Linear or Log Tracks Long spindles, Midget 5 K ohms to 2 Meg. L.S. 3/-; D.P., 4/6; Stereo L/S 10/8; D.P. 14/6

MAINS TRANSFORMERS 200 250 v. A.C.

Postage 2/- each transformer.

|  |      |
|--|------|
| STANDARD, 250-0-250, 50 mA, 5 v. 2.5 A.  | 2/6  |
| tapped 4 v. 4 a. Rectifier, 6.5 v. 1 a., 5 v. 2 a., or 4 v. 2 a. 22/6  | 2/6  |
| MINIATURE 200 v. 20 mA, 6.5 v. 1 a.  | 10/6 |
| MIDGET, 220 v. 45 mA, 6.5 v. 2 a.  | 15/6 |
| SMALL, 250-0-250, 45 mA, 6.5 v. 2 a.   | 17/6 |
| STD, 250-0-250, 65 mA, 6.5 v. 2 a.   | 17/6 |
| HEATER TRANS., 6.5 v. 1 a. 5.5 v. 2 a.   | 7/6  |
| Ditto, tapped 1.4, 2.5, 4.5, 6.5 v.  | 8/6  |
| Ditto, sec. 6.5 v. 4 amp.  | 10/6 |
| GENERAL PURPOSE LOW VOLTAGE, 2 amp., 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24, 30 v.   | 22/6 |
| AUTO TRANSFORMER, 50 w. v.   | 22/6 |
| 0, 115, 200, 250, 250 v. 300 v.  | 32/6 |
| MULLARD "510" Mains Transformer  | 38/6 |
| PARMEKO MAINS TRANSFORMER. Made for special contract, the ratings can safely be doubled. Guaranteed 2 years. Primary 0-110-210-250-250 v. H.T. 300-0-300 v. 30 mA. L.T. 0.3 v. 1.8 amp. Size 4 x 3 1/2 in. | 17/6 |

INTERVALVE TRANSFORMERS, 5.3:1 or 5:1 9/6.

TRANSFORMERS, Heavy Duty, 5/8. Multi-ratio, 7/6. Multiratio heavy duty push-pull 10 w. 10/6. Battery 4/6. Sub min. 5/8.

10 w. O.P. matching trans. 3 x 1 1/2 12/6.

L.F. CHOKES 15 10H, 500/65 mA 5/-; 10H., 85 mA. 10/6; 10H., 120 mA. 14/6.

TIMED COPPER WIRE 16 to 22 swg., 1 lb., 3/6.

ENAMEL COPPER WIRE 16-22, 2/8; 24-30, 3/6; 32-40, 4/6; D.C.C. 28, 34, 36 swg. 2oz., 3/6.

I.F. TRANSFORMERS 7/6 pair

485 K/s Shug Tuning Miniature Can, 2 x 1 1/2 in. High Q and good bandwidth. Data sheets. STANDARD SIZE WEYRAD, 10/6 pair.

FULL WAVE BRIDGE SELENIUM RECTIFIER: 2, 6 or 12 v. 1 1/2 amp. 8/9; 2 a., 11/3; 4 a., 17/6.

CHARGER TRANSFORMERS. Tapped input 200 v. for charging at 2, 6 or 12 v., 14 amps. 15/6; 2 amps., 17/6; 4 amps., 22/6. Circuit included.

4 AMP CAR BATTERY CHARGER with ammeter leads. Fuse caps, etc., for 6 v. or 12 v. 69/9.

BOOKS list S.A.E.

|  |          |
|--|----------|
| Boys' Book of Crystal Sets               | 2/6      |
| N.W. Radio Valve Data                    | 6/-      |
| High Fidelity Speaker Enclosure          | 5/-      |
| Valve and TV Tube Equivalents            | 9/6      |
| TV Fault Finding                         | 5/-      |
| Mullard Amplifier Manual                 | 8/6      |
| Radio Valve Guide, Books 1, 2, 3, 4 or 5 | 5/- each |
| Transistor Superhet Receivers            | 7/6      |
| Practical Radio Inside Out               | 3/6      |
| Master Colour Code Chart                 | 1/6      |
| Transistor Controlled Models             | 7/6      |
| Principles of Colour TV                  | 16/-     |
| International Radio Stations             | 2/6      |

4 TRANSISTOR PUSH-PULL AUDIO AMPLIFIER

Size 3 x 1 1/2 x 2.

A ready built miniature push-pull amplifier with Driver and output transformers, 4 transistors. Ideal for use with record players, intercoms, B.B.Y. ALARMS, etc. Complete with full TV set, instructions and circuit.

Price 47/6. 6v. Batt. 2/3. 2in. Speaker 15/-.

1964 RADIOGRAM CHASSIS



THREE WAVEBANDS LATEST MULLARD S.W. 200 m. - 550 m. ECH1, EFS9, EBK1, L.A., 800 m. - 2,000 m. E184, EZ80

12-month Guarantee.

Auto 200-250 v. 4-watt switch, short-Medium, Long/Tune, Ferrite Aerial A.V.C. and Negative feedback, 3 ohm output, 5 watts. Glass dial, horizontal winding, size 1 1/2 in. x 4 in. Aligned and calibrated. Isolated Chassis, size 1 1/2 in. x 4 in. high x 3 1/2 in. deep.

£9.15 6 cart. & Ins. 4/6.

BAKERS SELHURST LOUDSPEAKERS



|   |      |
|---|------|
| 12in. Baker, 15w. Stalwart  | 12/6 |
| 8 or 15 ohms, 45-12,000 c.p.s.  | 5/6  |
| 12in. Stereo, Foam Suspension, 12w., 35-16,000 c.p.s.                       | 7/6  |
| 15in. Standard H.D. 20w. 40-14,500 c.p.s.                                   | 7/6  |
| 12in. De Luxe 15w. 25-17,000 c.p.s.   | 9/6  |
| 12in. Bass 25w. 20-18,000 c.p.s.  | 12/6 |
| 15in. Auditorium 35w. Bass, 20 c.p.s. to 12 k/c. Ideal Bass (Tullar), 18/6. |      |

Portable enclosures for 12in. "Stalwart" £8 each.

LOUDSPEAKERS P.M. 3 OHM. 2 1/2, 3, 4 in.; 7 x 4 in.; 15/6; 6 1/2 in. Rola, 18/6; 6 in. Plezacy, 17/6; 8 x 6 in., 21/6; 5 in. 50, 21/6; 10 x 10 in., 22/6; 10 in. STEPHAN HF12, 10in. 3 to 35,000, 10w. 87/6; 5in. HF12, 7/2; Tweeter T359, 30/6; Cross-over CX2000, 30/-.

EXTENSION SPEAKER CABINETS, 5in., 15/6; 6in., 18/6; 8in., 16/6; 10in., 22/6; 12in., 60/-.

C.R.T. BOOSTER TRANSFORMERS for heater cathode short circuit of tubes with falling emission. Full instructions supplied, mains input. Type A optional 25% and 50% boost 2v. or 4v. or 6.3v. or 10.8v. or 12.6v. State voltage required. PRICE 10/6.

TWIN GANG TUNING CONDENSERS. 365 pF. miniature 1in. x 1 1/4 in. 1 1/2 in.; 500 pF. Standard with trimmer, 9/-; uidget, 7/6; with trimmer, 9/-.

500 pF. soft motion tuning, standard or uidget, 9/6. Trimmer gang 208 - 174 pF. with trimmer, 10/6. SMALL 3 gang 500 pF, 17/-, SINGLE 365 pF, 7/6. SINGLE 100 pF, 25 pF, 50 pF, 75 pF, 100 pF, 180 pF, 5/6. Solid dielectric 100, 300, 500 pF, 3/6.

CONDENSERS. New stock, 0.001 mid. 7 kv. Transformer gang 208 - 174 pF. with trimmer, 10/6. Tubular 500 v. 0.001 to 0.05 mid., 9d.; 0.1, 1/2; 0.25, 1/10; 0.5, 250 v., 1/3; 0.1, 250 v., 9d.; 0.1, 2000 v. 3/6.

CERAMIC CONDS. 500 v. 0.2 pF. to 0.01 mid., 9d. SILVER MICA CONDENSERS, 10% 5 pF to 500 pF, 9d.; 500 pF. to 3,000 pF, 1/-, Close tolerance (-1 pF) 22 pF. to 47 pF, 1/2. Ditto 1/2, to 50 pF, to 815 pF, 1/2; 1,000 pF. to 5,000 pF, 1/9.

45, Kv/s SIGNAL GENERATOR Price 10/6 ready made with valve 18S. POCKET SIZE 2 1/4 x 4 x 1 in. One resistor to change, full instructions supplied. Battery 8/6, 60V x 11V. Details Free.

WAVECHANCE SWITCHES

|  |     |
|--|-----|
| 8 p. 4-way 2 water long spindle  | 8/6 |
| 2 p. 2-way, or 2 p. 6-way long spindle   | 3/6 |
| 4 p. 2-way or 4 p. 3-way long spindle  | 3/6 |
| 3 p. 4-way or 1 p. 12-way long spindle   | 3/6 |
| WAVE-CHANGE "MARKETS" Wafers available 1 p. 12 way, 2 p. 6 way, 3 p. 4 way, 4 p. 3 way, 6 p. 2 way, 1 waler switch, 8/6. 2 waler switch, 12/6; 3 waler switch, 16/-; additional wafers up to 12, 3/6 each extra; Toggle Switches, s.p., 2/-; d.p., 3/6; d.p.d.t., 4/-; Min. Slide d.p.d.t., 3/6. |     |

CRYSTAL MIKE INSERTS, 6/8 (High output, Size 1 1/2 in. dia. x 1 in. ACOS Mini-4L insert 1 1/2 in. dia. x 1 in., 8/6)

ACOS 394 DE LUXE STRIKE MIKE 35/-

EMI Q4 ALITY STRIKE MIKE 35/-

TELEPHONE TAPE MIKE 10/6

GUITAR CONTACT MIKE 15/6

Valveholders, EA50, 6d. B12A, CRT 1/3. Engr. and Amer. 3 1/2 and 4 pin. 1/3. Moulded Mazda and int. octal, 6d.; BG7, B8A, B9C, B9A, 9d. B7C with can. 1/6. B9A with can. 1/6. Ceramic EF90, B7C, B9A, int. octal, 1/7. B7C, B9A cans, 1/7 each. Valve plugs B7C, B9A, int. octal 2/8.


HIGH GAIN TV PRE-AMPLIFIERS B.C.C. Bands 1 to 5 Gain 18dB EC84 valve. Kit price 29/6 or 49/6 with power pack. Details 6d. (PC884 valves if preferred). Coils only 9/6. BAND III I.T.A.—Same prices. Tunable channels 8 to 13, Gain 17dB. Circuit and coils only 9/6.

THE ORIGINAL RADIO COMPONENT

Our written guarantee with every purchase NEW COMPONENT LIST 1/-.

Bus 133 or 68 pass door S.R. Station Selhurst

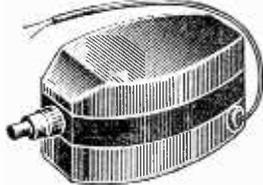**THE "INSTANT" BULK TAPE ERASER AND RECORDING HEAD DEMAGNETIZER**



200/250 v. A.C. **35/-** Leaflet S.A.E.

**PLASTIC RECORDING TAPE**

|             |                          |                     |
|-------------|--------------------------|---------------------|
| Double Play | 7in. reel, 2,400ft. 25/- | Spare Plastic Reels |
|             | 5in. reel, 1,200ft. 12/6 |                     |
| Long Play   | 7in. reel, 1,800ft. 22/6 | 3in. 1/6            |
|             | 5in. reel, 1,200ft. 17/6 | 4in. 2/-            |
|             | 3in. reel, 900ft. 15/6   | 5in. 2/-            |
| Standard    | 7in. reel, 1,200ft. 17/6 | 7in. 2/6            |
|             | 5in. reel, 600ft. 11/6   |                     |

"EASISPLICE" Tape Splicer 5/-.

CRYSTAL SET BOOKLET, 1/-.  
CRYSTAL DIODE (G.E.C., 2/-, 6EX34, 4/-, OA81, 3/-, HIGH RESISTANCE PHONES, 4,000 ohms. 15/-, MOVING COIL PHONES, 100 ohms. 10/-, SWITCH CLEANER. Fluid squirt sprout. 4/6 tin.

**"6+1" TRANSISTOR RADIO MEDIUM AND LONG WAVE KIT**

First class components to make a 6 transistor 2 waveband superhet chassis. Ideal for portable or table radio. All parts including 7VA transistors, ferrite aerial, with car aerial coil, printed circuit, 8 1/2in x 2 1/2in., but EXCLUDING Speaker and cabinet. Speakers, 35 ohms, 7 x 4in. 21/- 5in., 17/6, 3 1/2in., 15/6.

**£4.5.0**

**BULGIN PLUGS AND SOCKETS.** Non-reversible P4, 3-pin, 4/3; P73, 3-pin, 4/6; P194, 3-pin, 6/6. GAKS. English spec. circuit, 2/6. Closed circuit, 4/3. Grundig type, 3-pin, 1/3. Grundig lead jack, 3/6. **JACK PLUGS.** English, 3/-; Screened, 4/-; Grundig, 3-pin, 3/6; Phono Plugs, 1/-; Sockets, 6d.

**LADDIN FORMERS** and cores, 1in., 6d.; 2in., 10d. 0.3in. FORMERS, 2.5/6 or 3 cans. TV 1 or 2; 2in. sq. x 2 1/2in., or 2in. sq. x 1 1/2in., 2/- with cores. **SLOW MOTION DRIVERS.** 6s. 1/4. **SOLENOID.** 25W, 200V or 250V, 24/-. **ATEX SUB-MIN. IRON.** 1in., 2in. or 2 1/2in., 29/8. **BENCH STAND** for above, 12/6. Spares in Stock. 1/15in. Paxolin Panels, 10 x 8in., 2/-.

**Miniature Contact Cooled Rectifiers.** 250V 50mA, 7/6; 250V 60mA, 8/6; 250V 85mA, 9/6; Selenium Rect., 300V 85mA, 5/-; TV, etc., Silicon Sub. Min. Rectifiers, 250V 450mA, 10/-, K3/25, 600V, 5mA, 5/-, RM4, RM5, 14A100, 14A110 10/- each. FC3120/- Coils Wearite "P" Type, 4/- each. Osmor Midget "Q" type, adj. dust core, from 4/- each. All ranges, List S.A.E. **Teletron D.W.R.** L. and Med. T.R.F. with reaction, 4/-; Med. wave D.R., 3/6. **Ferrite Aerials,** M., 8/6; M. and L., 12/6. **Osmor Ferrite Rods,** M., L. and M. for transistor circuits, 10/- each. **Ferrite Rods,** 8 x 1/2in., 6 x 1/2in., 6 x 1/4in., 3/-; H.F. Chokes, 2/6. **Osmor Q1,** 6/9. **T.R.F. Coils,** A/HF, 7/- pair; HAN, 3/6. **Renanco DRS,** 2, 4/6. **DRX1,** 3/- **Screwdriver,** 3in. 6L Test Prods, 2/9. **Neoside Trimming Tool,** 1/9. **Neon Mains Tester Screwdriver,** 5/-. **Multicore Solder,** 4d. yd. Dispenser, 2/6.

Aluminium Chassis, 18 s.w.g. Plain, undrilled, 4 sides, riveted corners, lattice fixing holes, 2 1/2in. sides, 7 x 4in., 4/6; 9 x 7in., 5/9; 11 x 7in., 6/9; 13 x 9in., 8/6; 14 x 11in., 10/6; 15 x 14in., 12/6. **Aluminium Panels,** 18 s.w.g., 12 x 12in., 4/6; 14 x 9in., 4/-; 12 x 8in., 3/-; 10 x 7in., 2/3; 8 in., 2/-; 6 x 4in., 1/6.

**MARTIN TAPE PRE-AMPLIFIERS & DECKS, PLAY-BACK THROUGH YOUR OWN HIFI**

|                                 |                                   |
|---------------------------------|-----------------------------------|
| B.R.S. 2 track Pre-amp, £8.8.0  | B.S.R. TD2 tape deck, £5.5.0      |
| Collaro 2 track Pre-amp, £8.8.0 | Collaro Studio tape deck £10.10.0 |

**COMPLETE RECORDING & PLAY-BACK AMPLIFIERS**

|                                 |                            |
|---------------------------------|----------------------------|
| 2 track B.S.R. amplifier £8.8.0 | Collaro amplifier £11.11.0 |
|---------------------------------|----------------------------|

**MAINS DROPPERS.** Budget adjustable sliders 0.3A, 1,000 ohms, 5/-; 0.2A, 1,200 ohms, 5/-; 0.15A, 1,500 ohms, 5/-; 0.1A, 2,000 ohms, 5/-.

**MIKE TRANSFORMERS.** 50-1, 3/9, P.V.C. Covered Wire, single or stranded, 2d. yd. Sleeving, 1 or 2 mm., 2d.; 4 mm., 3d.; 6 mm., 5d. 3/1.

**SPEAKER-FRET.** Gold, Maroon or Green Cloth, 17 x 2 1/2in., 5/-; 25 x 3 1/2in., 10/-. Tygan, various colours 5 1/2in. wide from 10/- to 26in. wide from 5/- to 3 samples 1/-. Expanded Metal, Gold, 12 x 12in., 6/6. Plastic mounting tube holder, 2/-. Fuses 1 1/2in., 60mA, 5A, 6d. Insulated side cutters, 8/6, Bib Stripper, 3/6.

**RADIO AND TELEVISION SPARES**

All leading makes, volume controls, etc., fine output transformers, etc., B. V. A. valves (current and obsolete types). Send S.A.E. for quotation.

**WEYRAD**

**COILS AND TRANSFORMERS FOR 2-WAVE 6-TRANSISTOR PRINTED CIRCUIT AND FERRITE AERIAL**

Long and Medium aerial—RA2W 6in. rod 208P tuning, with car aerial coil 12/6  
Osc. Coil P50/LAC, 176P tuning 5/4  
1st and 2nd I.F. P50/2CC, 470kcs/15/16in. dia. by 4in. 5/7 each  
3rd I.F. P50/3CC 6/-  
Driver Cores 6d.  
Wavechange Transformer—LFDT4 1/6  
Wavechange Slide Switch 2p x 2 1/2in. 3/6  
Printed Circuit—PCAL, 4d. 8in.  
Ready drilled and printed 9/6  
Volume Control, 5K-DP 4/6  
35 ohm Speakers, 3in., 15/6; 5in., 17/6; 7 x 4in., 21/-  
Tuning Gang with trimmers 10/6  
6 Mullard Transistors and diode 42/6  
Constructor's Booklet 2/-  
3 ohm O.P. Trans. O.P.T.I 10/6


**NEW MULLARD TRANSISTORS**

OC71 6/-, OC72 7/6, OCBD 7/6, OC81 7/6, OC44 8/9, OC45 8/6, OC171 10/6, AP117 9/6, sub Miniature Condensers, 0.1 mF, 30v., 1/3, 1, 2, 4, 5, 8, 16, 25, 30, 50, 100 mF, 15 volt, 2/6 ea. Transistor Holders, 1/3.

**SINCLAIR "SLIMLINE" RADIO**

Med. wave kit, 2 transistors, 2 diodes, earphone, ferrite aerial, Cabinet 8 x 1 1/2 x 4in. 49/6, batt. 3/6.

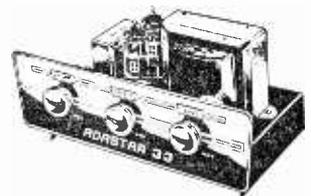**ADASTRA 3-3 AMPLIFIER 3 WATTS HIGH FIDELITY AT LOW COST**



**READY BUILT, WIRED AND TESTED** A.C. only, 200-250 V. Valves EC1, 6E and E280, 3 ohms quality output, Mullard tone circuits, (controls) bass boost, treble and volume. Separate engraved front panel with die lux finish. Quality mains transformer. Stove enamelled chassis size 6in. x 5in. x 3in. Bargain Price £24.19.6 Details S.A.E.  
"Performs agreeably well" (The Gramophone)

**BUILD YOUR OWN RECORD PLAYER**

FROM £9.19.6

AND SAVE POUNDS!!



4 Speed Autotune or Single Player units supplied with Brand New 2-tone deluxe Portable Cabinet 17x15x8 1/2in. Strong carrying handle, gilt finish clips and hinges. As used by Famous Make for 20gns. models. Ready cut-out motor board 14x13in. Front baffle with 7 x 4in. high flux loudspeaker and 3 watt 2 valve UY85, UCL82 2-stage amplifier ready built on metal chassis 12 x 3 x 2 1/2in. Quality 3 ohm output transformer, low hum level circuit. Volume and Tone controls, 3-core safety mains lead. All items fit together perfectly. Special instructions enable assembly in 30 minutes, only 5 wires to join! 12-month written guarantee. Available separately or package deals as below.

**AUTOCHEANGER KITS COMPLETE** (as above)  
B.S.R. Monarch .. £11.10.0 P.P. 5/6  
Garrard Autotism .. £12.18.0 P.P. 5/6

**SINGLE PLAYER KITS COMPLETE** (as above)  
E.M.I. Junior .. £9.19.6 P.P. 5/6  
E.M.I. auto stop/start .. £11.5.0 P.P. 5/6

**OR SEPARATELY**  
Cabinet with board 14 x 13in. cut out to your choice £3.9.6 P.P. 3/6  
Amplifier with 7 x 4in speaker £3.17.6 P.P. 2/6

**AUTOCHEANGERS**  
B.S.R. UA14 .. £5.19.6 P.P. 4/6  
B.S.R. UA15/16 .. £6.17.6 P.P. 4/6  
Garrard Autotism .. £6.17.6 P.P. 4/6

**SINGLE PLAYERS**  
E.M.I. auto stop/start .. £5.10.0 P.P. 4/6  
E.M.I. Junior .. £3.7.6 P.P. 3/6

**TRANSCRIPTION UNITS**  
Garrard 4HF .. £16.10.0 P.P. 5/6  
Philips AG1016 .. £12.5.0 P.P. 5/6  
Garrard AT8 .. £11.0.0 P.P. 5/6

**BARGAIN**  
B.S.R. Autotune UA12 Stereo/Mono .. £7.10.0 P.P. 4/6

Replacement sapphire styli available from 5/3. Replacement Xials from 15/-; Stereo from 31/6.

**BARGAIN SINGLE PLAYER KIT 200/250 v. A.C. (less cabinet)**

**£5.15.0**

Post 5/-

With 2-stage Amplifier; 3 watt; 2 valves, UCL82, UY85; High-flux 5in. speaker; 4-speed E.M.I. Turntable, 16, 33, 45, 78 r.p.m.; Crystal Pick-up for LP/STD. Records, 7in, 10in, 12in.; Cut out Mounting board 12 x 9 1/2in.

**ARDENTE TRANSISTOR TRANSFORMERS**

D3035, 7.3 CT:1 Push-Pull to 8 ohms for OC72, 11/-  
D3034, 1.74:1 C.T. Push-Pull Driver for OC72, 11/-  
D3038, 11.5:1 Output to 8 ohms for OC72, etc., 11/-  
D167, 18.2:1 Output to 3 ohms for OC72, etc., 12/-  
D239, 4.5:1 Driver, 2in. x 2in. x 2in. 11/8  
D240, 8.5:1 Driver, 2in. x 2in. x 2in. 11/8  
**ARDENTE TRANSISTOR VOLUME CONTROLS**  
VC1545, 5K with switch dia., 9in., 5/8  
**DEAF AID EARPIECE.** Xtal or magnetic, 7/8  
**SUB-MIN. JACK AND PLUG** 3/6 pair

**MINIATURE PANEL METERS**

Size 1 1/2in. sq. Precision jewelled bearings, 2% accuracy, silvered dials, black numerals and fine pointers, zero adjustment screw on front of meter.  
0-1 mA .. 27/6 0-50µA .. 39/6  
0-5 mA .. 27/6 0-500µA .. 32/8  
0-300 V .. 27/6 "S" Meter .. 35/-

**CABY MULTIMETER M.1**  
0-1200 v. AC/DC, ohms 0-100k, etc., 54/-


**COMPONENT SHOP SPECIALISTS**

P.P. charge 1/- C.O.D. 2/- extra.


**337 WHITEHORSE ROAD WEST CROYDON**

Telephone: THO 1665  
(Export volume. Send remittance, and extra postage, no C.O.D.)

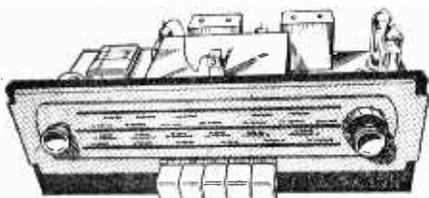**BRAND NEW AM-FM (V.H.F.) RADIO GRAM CHASSIS AT £13.13.0 (Carriage Paid)**



Chassis size 15 x 6½ x 5½in. high. New manufacture. Dial 14½ x 4in. in 2 colours, predominantly gold. 200-250 v. A.C. only. Pick-up, Ext. Speaker, A.C. E., and Dipole Sockets. Five push buttons—O.P.F., L.W., M.W., F.M. and Gram. Aligned and tested. O.P. Transformer. Tone Control. 1000-1900 M.: 200-550 M.: 88-98 Mc.s. Valves: E250 rect., EC181, EF98, EAB/80, EL84, EC182. Speaker 8 x 2in. and cabinet to fit chassis (table model). 4778 (post 3/6). 10 x 6in. FLUORESCENT SPEAKER £12.25/- to purchasers of this chassis. **TERMS:** (Chassis) £3.10.0 down and 5 monthly payments of £2.4.0. (Cheap Room Dipole for V.H.F. 12/6. Feeder 6d. per yard. 1/6in. dia. aluminium 2/6. **ALTERNATIVE DESIGN.** L.W. 1000-1900 M.: 8 W. (9-15 Mc.s.) M.W. 190-475 M.: V.H.F. 87-100 Mc.s. Gram. position. **TERMS:** £3.10.0 down and 6 monthly payments of £2.4.0.

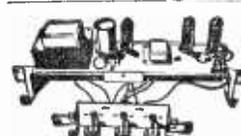

**PUSH-PULL AMPLIFIER £5.5.0**  
(6 Carr.)


Brand new 200-240 A.C. mains. Bass, treble and vol. controls. With valves E250, EC182 and 2-EL84 giving full 8 w. Chassis 12 x 3½ x 3½in. With o.p. trans. for 2-3 ohm speaker. Front panel (normally screwed to chassis) may be removed and used as "flying panel". Stereo version 2 x 4 w. same price. Fixed panel. Tone & Vol. Controls.

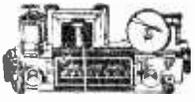**TAPE RECORDER AMPLIFIER**



Type TR3. Fully built, high gain, low noise, printed circuit. Attractive grey and gold front panel 13 x 1½in. Height 9½in. overall. Front to back 5½in. Vol. and on-off tone, Mike, auto and ext. speaker jacks. Valves: 6X4 rect., EC182, E250. Mains trans. Ready to fit to H.S.R. Deck. Complete with switch water-weld. Our Price ONLY £6.16.0 (6/- Packing and Carr.). Also available for Collaro Deck at 5/- extra.

**SELF-POWERED VHF TUNER CHASSIS** (covering 88-95 Mc.s. Multiband portability tuner. Dims. 10½ x 4½ x 5½in. high. Valves EC182 and 2 EF98 plus 2 diodes with E250 rectifier. Mains transformer. Fully wired and tested. ONLY £7.17.6 (car. paid). Room dipole 12/6. Feeder 6d. per yard.



**SPECIAL OFFER PRINTED CIRCUIT AM-FM CHASSIS AT ONLY £9**

A small quantity of Printed Circuit chassis by famous manufacturer. Valves EC182, EC181, EF98, EAB/80, U184 and U185. O.P. trans. for 2-3 ohm speaker. Chassis 14 x 7 x 7in. Front controls concentric left—Vol. and Tone; right—W.C. and Tuning "Gold" tone knobs provided. 2-dial bulb Sockets. A.C. E. Ext. sp. P.T. Mains isolating transformer free. Covers Long, Med., V.H.F. (87-101 Mc.s.). Unused sockets furnished, but not dirty. New Mullard Valves. Dial 14 x 6in. and brown, size 13 x 3½in.



**6-TRANSISTOR PORTABLE—Fully Built**


The "SCALA" for only £7.10.8, car. paid. 8½ x 2 x 3½in. high. Choice of colours. Recharge. M.W. and L.W. Ferrite aerial. Battery 2 1/2 extra. Printed circuit. Nicely styled. A professional job. 3½in. speaker. Fully tunable M.W. and L.W. Superhet circuit.

100 mF. + 200 mF. ELECTROLYTIC. New 275 v. (350 v. surge). 4in. x 1½in. dia. 5/- each. (Post 1/6).

**ALL ITEMS ARE NEW AND FULLY BUILT UNLESS OTHERWISE STATED. TESTED BEFORE DESPATCH.**  
Terms Available on Items over £5. Send 6d. (stamps will do) for 20 page illustrated catalogue. Delivery by return. C.O.D. 2/- extra.  
**ALL ITEMS GUARANTEED 12 MONTHS. VALVES 3 MONTHS**

**GLADSTONE RADIO**  
"SCALA", CAMP RD., FARNBOROUGH, Hants.  
Farnborough 3871 (1.08ED) SATS.

**"REALISTIC" 'SEVEN'**

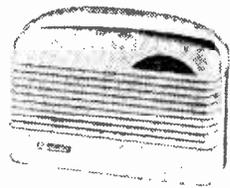


7 Transistor Superhet. 350 Milliwatt output. 4-inch speaker. All components mounted on a single printed circuit board size 3½ x 4½in. in one complete assembly. Plastic cabinet, with carrying handle, size 7 x 10 x 3½in. External Socket for car aerial. Ferrite rod aerial. Price for the complete parcel including Transistors, Cabinet, Speaker, etc., and full Construction Data: **£5.19.6**  
P. & P. 4/6.

PP9 Battery 3/6. Data and instructions separately 2/6. Refunded if you purchase the parcel.  
Any parts supplied separately.

**4 TRANSISTOR MINIATURE PUSH-PULL AUDIO AMPLIFIER**

PRINTED CIRCUIT. 5in. x 2½in. x 1½in. over transformers. Output for 2-ohm speaker. Suitable for microphone, record player, guitar and radio input. 3-12 volt battery required. Frequency range 100 cps. to 25 Kcps. Push/pull output single ended. Instruction sheet provided. Fully wired ready to use. Two types available. 1 watt output, 35/-. 1½ watts 41/-. P & P 2/6.

**THIS SUPERB SET for £9 (Carr. pd.)**

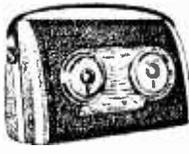

6-transistor radio covered in sponge-clean Duracore lac. in latest two-tone shades, M.W. and L.W. Ferrite rod, provision for car aerial, 2-colour scale. With PP9 battery giving 300 hours use. Weighs under 4 lbs. With carrying handle. 12 x 7in. high x 4½in. at base tapering to 2½in. at top. Brand new, fully guaranteed. 3 push buttons. Superhet circuit, 6in. L.S.


**5 WATT AMPLIFIER**

Our price ONLY 58/- (post 3/-) a new hundred only: valves EF91 and EL84 with metal rectifier, 6 x 4 x 1½in. high (5in. over EL54). Mains trans. and o.p. with vol. and tone controls; on-off; c-o-x. input.

**SPECIAL REDUCTIONS ON GRAMPHONE AMPLIFIERS**

1½ watt type. Save 4/6. With 5in. speaker. Baffle 12 x 6in. 200-240 v. A.C. EL84 and Rectifier. Tone and Volume. On/off switch. Two knobs. Ready to play. Useful for Stereo. 46/-, post 5/-.  
4 watt type. Save 20/-. Valves UY50, UY80 and UL84. 200-240 v. A.C. Covered baffle 12 x 7½in. (6in. speaker). 3 front controls; bass, treble, on-off vol. 54/-, post 5/-. Double wound mains transformer.  
2½ watt type. Save 20/-. 2½ watts. EC182 EC182 and E280. Controls: volume, bass and treble. On/off switch. 200-240 v. A.C. O.P. trans. Size 12 x 8 x 3½in. over valves. Suitable for microphone input and for Guitar. 55/-, post 5/-.

**STEREO CONVERTER UNIT**

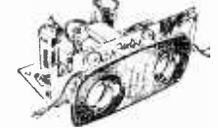

Converts existing Radiogram to play stereo records. Chassis 4½ x 2½ x 4in. overall height. Mains and O.P. trans. Metal Rect. EC182 valve and all screws, panels, etc. Moulded front section. Fully built. Brand new, only extras needed: speaker and stereo cartridge. Full instruction leaflet. Limited quantity at 89/6 (5/6 P. & P.). Stereo Cartridge, 25/-.

**TOP QUALITY RECORDING TAPE (Guaranteed)**

|       |         |                                      |       |         |
|-------|---------|--------------------------------------|-------|---------|
|       |         | (1/- per tape six or more post free) |       |         |
| 4in.  | 600ft.  | 12/6                                 | 3½in. | 1200ft. |
| 5in.  | 600ft.  | 11/3                                 | 3½in. | 1800ft. |
| 5in.  | 900ft.  | 17/-                                 | 4in.  | 1200ft. |
| 5in.  | 1200ft. | 30/-                                 | 7in.  | 1800ft. |
| 5½in. | 850ft.  | 11/6                                 | 7in.  | 2400ft. |
|       |         |                                      |       | 32/6    |

**BATTERY ELIMINATOR**

For 4 Low Consumption Valves (98 ranges) 90v. 15 mA and 1.4v. 125mA. 46/- (4 post). 200-250v. A.C. Also for 250mA. 1.4v. and 90v. 15mA at same price. Two separate units to replace existing batteries. 4 x 2½ x 2½in. and 3 x 2½ x 1½in.

**13 x 8 ins. LOUDSPEAKER**  
Three ohm. Ceramic magnet of latest type. BRAND NEW.  
42/6 (post 3/6)

**HEATER TRANSFORMER**

Mains input giving 4.2v. 2 amp. Size 2½ x 2½ x 1½in. (2½in. over winding). 5/8 ea. L.s. 16/- for 12, or 20/- for 50. P. & P. 2/- for 1 to 3, post free more than six.

# Practical Wireless

Vol. XXXIX No. 685 MARCH, 1964

Editorial and Advertisement  
Offices:

**PRACTICAL WIRELESS**

George Newnes Ltd., Tower House,  
Southampton Street, W.C.2.

© George Newnes Ltd., 1964

Phone: Temple Bar 4363

Telegrams: Newnes, Rand, London,  
Registered at the G.P.O. for trans-  
mission by Canadian Magazine Post.

**SUBSCRIPTION RATES**

including postage for one year

To any part of the world £1.9.0

## Contents

|   | Page |
|---|------|
| Editorial ... ..  | 1021 |
| Round the World of Wireless ...                         | 1022 |
| The "7-20" Stereo Amplifier ...                         | 1024 |
| The "Junior" Crystal Set ...                            | 1030 |
| On Your Wavelength ...                                  | 1036 |
| Basic Stabilised Power Pack ...                         | 1037 |
| All Band Aerial Tuner ...                               | 1040 |
| Audio Testing with the P.W.<br>"Sixteen" ... ..         | 1045 |
| Pocket Signal Tracer ...                                | 1048 |
| Modifications to the Local<br>Station F.M. Receiver ... | 1053 |
| Wow and Flutter ...                                     | 1057 |
| An Advanced Metronome ...                               | 1062 |
| An Inexpensive Stereo Tape<br>Recorder ... ..           | 1066 |
| Trade News ... ..                                       | 1073 |
| Short Wave One ... ..                                   | 1077 |
| Test Gear Accessories ...                               | 1081 |
| Club News ... ..  | 1086 |
| Letters to the Editor ...                               | 1089 |

The Editor will be pleased to consider articles of a practical nature. Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed: The Editor, PRACTICAL WIRELESS, George Newnes, Ltd., Tower House, Southampton Street, London, W.C.2. Owing to the rapid progress in the designs of wireless apparatus and to our efforts to keep readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in PRACTICAL WIRELESS is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. PRACTICAL WIRELESS incorporates "Amateur Wireless."

## Definitions

WHAT is a "wireless" enthusiast? Should he really be called a "radio enthusiast"? And where does "electronics" fit into the picture? In our hobby there are many loose and rather vague demarcation lines and terms of doubtful validity. This comes to mind when occasionally a reader asks why we do not change our title from "Practical Wireless" to "Practical Radio", to "bring it up to date."

One reason is that our present name has been in continuous use for so many years that it has become traditional and universally accepted. For although, in isolation, "wireless" is an outmoded word, everyone knows what it means, even though it is capable of various interpretations.

Mr. X, for instance, is known as a radio enthusiast, but his main interests are test instruments and tape recorders—neither, strictly speaking, wireless or radio. And Mr. Y who likes building amplifiers, though by definition an audiophile is no doubt thought of as a radio enthusiast.

These anomalies have been with us for a long time. The pioneer "wireless enthusiast" was essentially an experimenter, the main preoccupation being to establish and improve methods of long-distance communication by wireless equipment.

When the broadcasting of entertainment material was established in the early 20's, a "wireless enthusiast" was most likely to be a completely non-technical builder of wireless sets using a set of point-to-point wiring diagrams and a kitchen table. Later on, when commercially built sets became more numerous and competitive in price, most of the do-it-yourself builders lost interest, leaving behind the more technically inclined.

In the early 30's, some "wireless" experimenters were working on television equipment, others were interested in circuits to amplify the magnetic pickups which had displaced the acoustic gramophone, and a few were even probing the possibilities of wire recording—little realising how these various offshoots were to develop in the years ahead!


The immense technical strides due to wartime research brought, after the war, a new impetus to old hands and introduced a new generation of enthusiasts. The transistor led to an enormous new interest in set building which can in some ways be likened to the activity of the early 30's, for many of these set builders were almost completely non-technical.

Then there is "electronics." The term is not always clearly understood, is often mis-applied and sometimes awkwardly overlaps radio, audio, video and other spheres.

In other words, the picture of a typical wireless or radio enthusiast changes, often fundamentally, wherever you cut the cake, and at what time period you cut it. This, perhaps, is the key to the continued and always expanding interest, for there can be very few hobbies which offer so many and so varied facets and can give their adherents such a large number of ever-changing spheres to explore.

So the next time you question the use of the word "Wireless", ask yourself if the term "Radio" is more precise. Most likely it won't be!

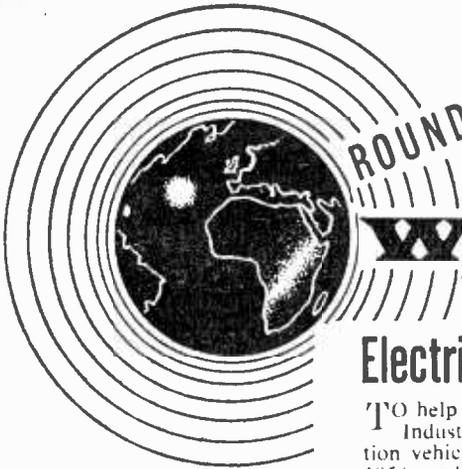Our next issue dated April will be published on March 6th



ROUND THE WORLD

# of WIRELESS

## NEWS AT HOME AND ABROAD

### SOUND SYSTEM FOR NEW THEATRE

**T**he extensive sound and telephone systems of the recently opened Nottingham Playhouse Theatre, have all been installed by Standard Telephones and Cables Limited. A 25-line telephone system links all parts of the theatre and for the producer and key theatre personnel, there is a loudspeaking intercom system.

For the audience, eight loudspeakers in the auditorium carry sound from the stage and from the sound effects console. These loudspeakers are fed by a dual-channel amplification system which, in addition to providing for stereophonic reproduction, may be used to "move" sound from one part of the auditorium to another.

As an integral part of the system, sound from the stage is taken to 27 loudspeakers in dressing rooms and the theatre workshops so that actors and stage assistants can follow the progress of each performance.


## EXTRA TELECOMMUNICATIONS STAFF FLOWN TO HOLY LAND

**D**URING the visit of Pope Paul VI to the Holy Land in January, more than 1,000 journalists and photographers from all over the world arrived in Jordan to cover the Pope's pilgrimage. The needs of the reporters for telecommunication facilities placed unprecedented demands on the Cable and Wire-
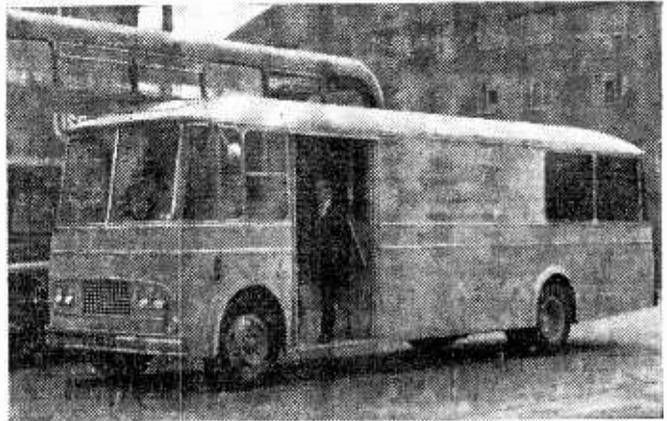
## Electrical Equipment to Tour Europe

**T**O help increase overseas exports, Avo Limited (part of the Metal Industries Group) has commissioned a new mobile demonstration vehicle to replace a similar vehicle which went into service in 1954 and which has helped boost sales abroad by travelling thousands of miles to grind Avo products right to the doors of prospective customers. The new unit will have similar duties and is expected to visit many European and Middle East countries during the year.

The vehicle has been built on to a Bedford public service vehicle chassis, and at 30ft. in length, is longer than a London bus. Inside the unit will be examples of Avo's electrical, electronic and nucleonic measuring instruments and coil winding machinery. Customers will be able to relax in the lounge area which has been provided in the vehicle, which is also fully air conditioned.



*Avo's new demonstration vehicle all set for a tour of Europe and the Middle East.*

less station in Amman. To cope with this extra traffic, the Company flew in additional staff from London, Gibraltar, Malta, Aden, Nairobi and Bahrain. Cable and Wireless Limited co-operated with the Government of Jordan to provide the world press and radio with the essential communication services between

Jerusalem and Amman; between Amman and the rest of the world.

In all, an extra sixty engineers, technicians and operators helped man the station during the visit. They were accompanied at the Amman station by an extra five and a half tons of equipment which had also been flown in specially.

## TRANSMITTERS FOR SWITZERLAND

TO provide private motorists and commercial vehicle users with a reliable and inexpensive communications service, the Post and Telegraph Administration of Switzerland is to commence a public car-calling network which has been operating experimentally until recently. The network calls for ten v.h.f. radio-telephone transmitters each with an output of 1kW and these have been ordered from Standard Telephones and Cables Limited.

These transmitters are to be placed at strategic high points above the valleys and will be used for telephone operators to advise drivers of vehicles when a telephone call awaits them. On hearing such a message on his car radio, the driver will know to stop at the next telephone and contact either the operator or the person wishing to speak to him. This system obviates the need for motorists to install costly transmitter equipment and it further overcomes the disadvantage of a low-power, mobile transmitter, the range of which would be seriously restricted by mountains.

## British Equipment for Tanganyika

BROADCASTING transmission equipment which will cover the whole of East Africa by radio, is to be supplied by the Marconi Company Limited to the newly independent Government of Tanganyika. This order was confirmed by Mr. Paul Bomani, Tanganyikan Minister of Finance, during a recent visit to Britain.

The equipment is for the new radio station at Dar-es-Salaam and will form part of an extension to the country's broadcasting facilities. The order is for two 50kW medium frequency transmitters, together with programme input equipment and ancillaries. Also included in the order is the aerial system, which will consist of directional array.

## Airborne Communications Equipment Ordered

LIGHTWEIGHT v.h.f. airborne communication equipment has been ordered recently from Standard Telephones and Cables Limited by the Ministry of Aviation. The equipment which is the STR.38 transmitter/receiver, will be used to equip medium-light aircraft and rotocraft of the Army and Royal Air Force.

The STR.38 is well suited for this purpose, its weight being less than 14 lb., this being accomplished mainly by the use of transistors.

## Supersonic Airliner to have New Type of Aerial

A DESIGN for an aircraft aerial which makes use of the metal skin of the aircraft as part of the aerial and which has already been used for the Trident


and Vanguard airliners, is to be employed in the Anglo-French Concorde supersonic airliner. The "notch" aerial, as the design is known, was the result of work

done by a team of technicians of Standard Telephones and Cables Limited, and now STC has secured the study contract for the aerial system from Sud Aviation of Paris.

The special h.f. notch aerial unit will be fitted below the skin of the Concorde and covered with glass fibre to restore the original skin contour of the aircraft. The necessity of eliminating projections from the surface of the aircraft (which would produce intolerable drag on the aircraft and affect its performance) makes the notch type of aerial essential, conventional wire aeriels previously used being completely unsatisfactory.


The unit in the notch will couple signals from the Concorde's transmitter to the aircraft's wings, tail and fuselage and vice versa.

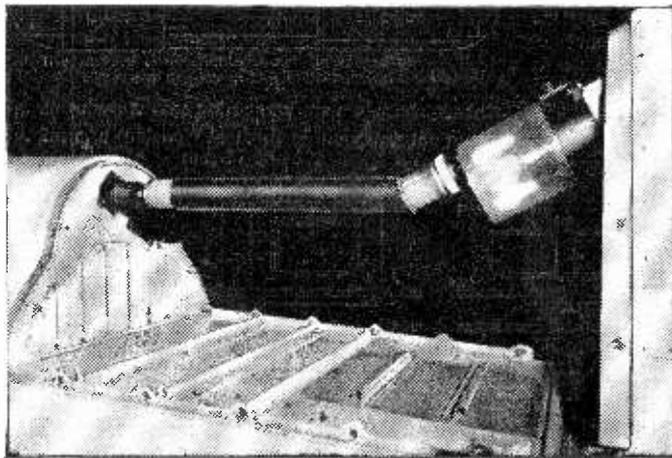*This is the "notch" aerial unit—as used in the Trident airliner—to be used in the new Concorde aircraft.*



# The "7-20"

## stereo amplifier

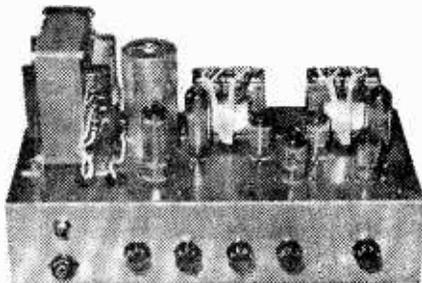

by M. L. Michaelis

### A NEW DESIGN USING THE ECLL800 AUDIO VALVE

**T**HE most modern trend in high power stereophonic amplifiers is presented in this design.

For clubs, schools, dances, parties and similar functions, for open-air use and even for the musical specialist at home some 8 to 10W power output on *each* channel is required.

Push pull operation is virtually essential for any high-power amplifier, as it affords the only really economical method of obtaining sufficient reduction of distortion and tolerable power efficiency. The principle objection to high-power push-pull output stages was formerly the relatively large number of valves required. In place of the single output valve of a single-ended amplifier, a pair of power valves was required, and, furthermore, a phase-splitter valve.

A basically new valve has now appeared on the market which is likely to revolutionise valve-operated audio power amplifiers.

#### Unidrive Push-Pull Output Valve ECLL800

The ECLL800 is, as its type designation implies, a combination of a phase-splitter triode and two power pentodes within a single envelope. It thus contains all the requirements for a push-pull output stage in the form of a single valve which is of the same physical size as a conventional EL84 pentode, and uses the same noval base. Furthermore, a set of Class B operating conditions is possible, under which the ECLL800 takes exactly the same h.t. drain as an EL84. The ECLL800 thus offers many very interesting opportunities for amateur experiments.

The present stereophonic amplifier design shows this valve under normal optimum operating conditions as recommended by the makers (Class AB).

The designation "Unidrive" for the ECLL800 means that the input drive signal required is that from a conventional single-ended voltage amplifier, e.g. from the anode circuit of one section of an ECC83, or from the anode circuit of an EF86. The ECLL800 contains its own phase-splitter, and this is in fact itself a completely new design and not a mere inclusion of a conventional voltage amplifier triode within the same glass bulb.

The tubular cathode of one pentode section is extended upwards beyond the end of the pentode

anode. The protruding section is positioned symmetrically inside a re-entrant half-cylindrical anode. Midway between the extended cathode and this anode, on both sides, are situated flat metal plates with a large rectangular cut-out to allow the electron clouds to pass through. These "rectangular iris windows" are joined together and to the control grid of one pentode system, and connected externally to pin 2 of the noval base. This combination electrode, conventionally termed "triode grid plus pentode No. 1 control grid", is the input electrode of the ECLL800, requiring a single-ended drive signal of 8V r.m.s. for 8.5W push-pull output at 5 per cent distortion.

With the adoption of the usual negative feedback arrangements, as employed in our present design too, the total distortion of the *entire* amplifier is less than 1 per cent at 8W output *per* channel.

The rectangular iris grid of the phase-splitter triode is designed such that the triode has a gain of exactly unity when an anode load of 150k $\Omega$  is employed (R64, R65 in our design). The signal at the triode anode (pin 1) is then of the same amplitude but opposite phase, as the input signal, and can be coupled externally to pin 6, the control grid of the other pentode section.

All three cathodes and both suppressor grids are commoned together to pin 7 of the base, and the screens of the two pentodes are commoned to pin 9. Pins 3 and 8 are the two pentode anode connections going to the two ends of the centre-tapped primary of a push-pull output transformer, the common h.t. supply being fed in, as usual, at the centre tap.

All electrodes of the three valve sections are thus accommodated on seven pins, the remaining two being used for the heater, in the normal position, pins 4 and 5. The total heater consumption of an ECLL800 is only 0.6A at 6.3V, which is astonishingly low for a complete push-pull output stage.

#### Curvature Compensation

The control characteristic of the rectangular irises on the triode has been made such that its residual curvature (non-linearity) is compensatory to that of the pentodes, so that the overall linearity of the ECLL800 is better than for any of its

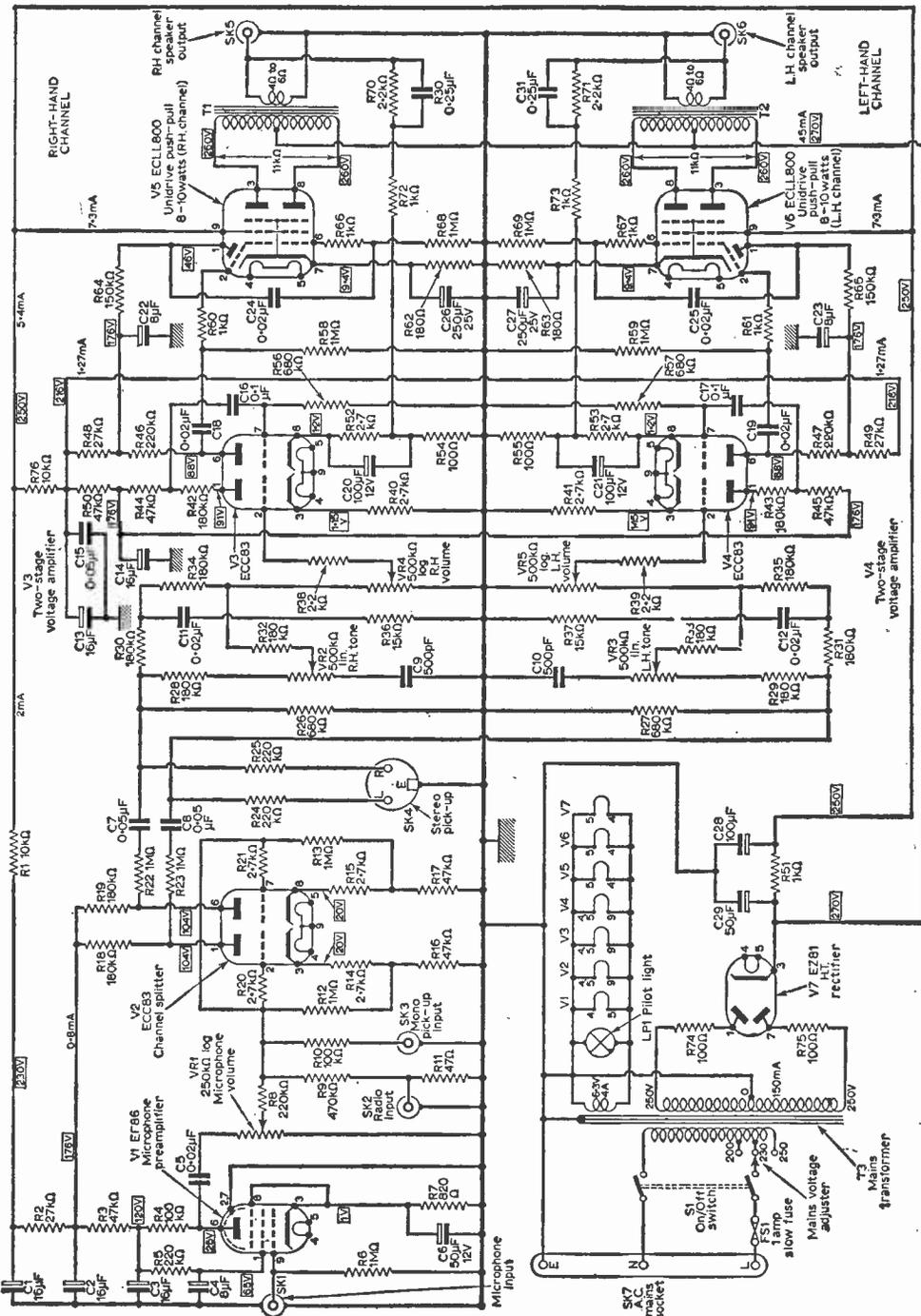


Fig. 1: The circuit. Numbers in circles indicate positive voltages w.r.t. chassis, as measured for prototype, using 20kΩ/V meter and with all volume controls at zero setting (no signal). Values shown against arrows on h.t. feeds are as calculated from above mentioned voltage readings.

sections alone. This is the first deliberate exploitation of this method of compensating distortion known to the author in commercial production practice. Certainly it is in general simpler and more economical to use negative feedback for improving linearity, in the familiar manner, yet the adoption of "compensatory control characteristics" for two or more stages in an amplifier chain offers, in principle, the possibility of driving the amplifier well beyond the linear part of the characteristics of individual stages, without undue overall distortion.

In combination with conventional negative feedback, this leads to greatly improved conversion efficiency of h.t. input power to audio output power. The ECLL800 probably represents nowhere near the ultimate of what may be achievable with such techniques, and valve manufacturers will doubtless bring out new types along these lines in the future.

#### Functions of the "7-20" Stereo Amplifier

This amplifier is designed for universal stereo and monaural (conventional) applications. V2 is here a channel-splitter, for feeding ordinary monaural inputs evenly onto both channels, the amplifier then functioning as 20W power output system for such signals.

The fact that half of this power is fed to each of two speakers or speaker systems, which can be placed some distance apart (ideally in opposite corners of the room, or opposite wings of a stage, for stereo use), enables an impressive projection of the sound into the room to be achieved, even for monaural inputs from ordinary pickups, tape decks or radio tuners. The use of such an amplifier system, employing two channels, is thus definitely worth while even for such signals. The sound appears to stand in the room, and *not* "come out of a hole", as otherwise with single speaker systems. Moreover, the intensity of sound is greater for the same power, and subjective quality and brilliance are improved.

It is, of course, essential to use speakers able to handle 10W peak power. It is not safe to use smaller speakers, even if one keeps the general volume turned low, because transients could still drive the amplifier momentarily to full power and rupture the cone and voice-coil system of a small speaker. Examples of suitable speakers are the WB Stentorian units HF 1016, in any of the makers cabinets or well designed amateur-built cabinets. For outdoor use, suitable horn speakers may be employed.

#### The Pre-amplifier

The pre-amplifier system included in the "7-20" stereo amplifier is quite comprehensive since the public address and entertainment applications require the frequent use of an announcer's or soloist's microphone.

High gain reserves are incorporated, which can be brought into use by internal variation of certain component values (as discussed below), to any extent such as to trim the complete amplifier to simultaneous optimum performance at all inputs for a particular microphone, tape deck, stereo pickup, etc.

The channel-splitter, V2, allows simultaneous monaural and stereophonic operation without

mutual interference. Such requirements arise, for example, if a public stereophonic concert (or an educational stereophonic concert in a school) is being given in a hall, with the two speakers in the wings of the stage, and a commentator wishes to inject explanations or announcements into the amplifier via a microphone. He may do so without any switching whatsoever, and whilst a stereo recording is actually playing, his voice will come equally over both channels, and will thus appear to originate from mid-stage, where he will, in fact, probably be situated.

#### Controls

The arrangement of controls has been designed with such applications in mind. Thus each main channel has been given two controls, a volume control and a treble tone control. Balance controls and other ganged arrangements have been discarded, as they bring added complexity and confusion. It was decided to dispense with a manual bass control too, in order to keep the number of controls down to a very minimum. A treble control is much more important than a bass control, and it is generally satisfactory to run the amplifier with some 15dB fixed bass boost for musical purposes and associated commentaries, as has here been done. Details of varying the degree of fixed bass boost are given below, as well as for the introduction of manual bass controls if required—there is still ample room for such on the chassis.

These considerations led to the use of just four simple controls for the main amplifier, with the addition of a fifth, VR1, the microphone volume control. The commentator can "mix himself in" on to a playing stereo or monaural recording at any desired relative intensity from zero to full power.

#### Monaural Inputs

The microphone input at SK1 may, of course, be used for any other weak signal input requiring greater amplification than a pick-up, e.g. a conventional monaural tape deck. V3 and V4 anode circuits (pin 1) can be adjusted (see below) such that inputs of 1mV or less at SK1 suffice to fully load the amplifier. VR1 is operative only for inputs at SK1. Inputs at SK2 and SK3, as well as stereo inputs at SK4, are controlled only by the four main amplifier controls, which, of course, also control SK1 inputs once again.

The radio input at SK2 is intended to be fed from the extension speaker sockets of a radio (low impedance). R11 is inserted to make this input insensitive to hum pick-up, so that long unscreened twin flex leads can be employed. If the insertion of the appropriate plug in the extension speaker sockets of the radio disconnects the internal speaker, the value of R11 must be reduced to the speaker impedance of the radio receiver, and must be of sufficient power rating to absorb the entire output power of the radio set. This demand can be satisfied by leaving R11 as shown, and wiring the necessary additional parallel resistor in or near the plug fitting SK2, if desired.

The input at SK3 must be screened. The resistors R8, R9 and R10 effect mutual decoupling of the three monaural inputs, so that all three may be left connected even when not operative. Many

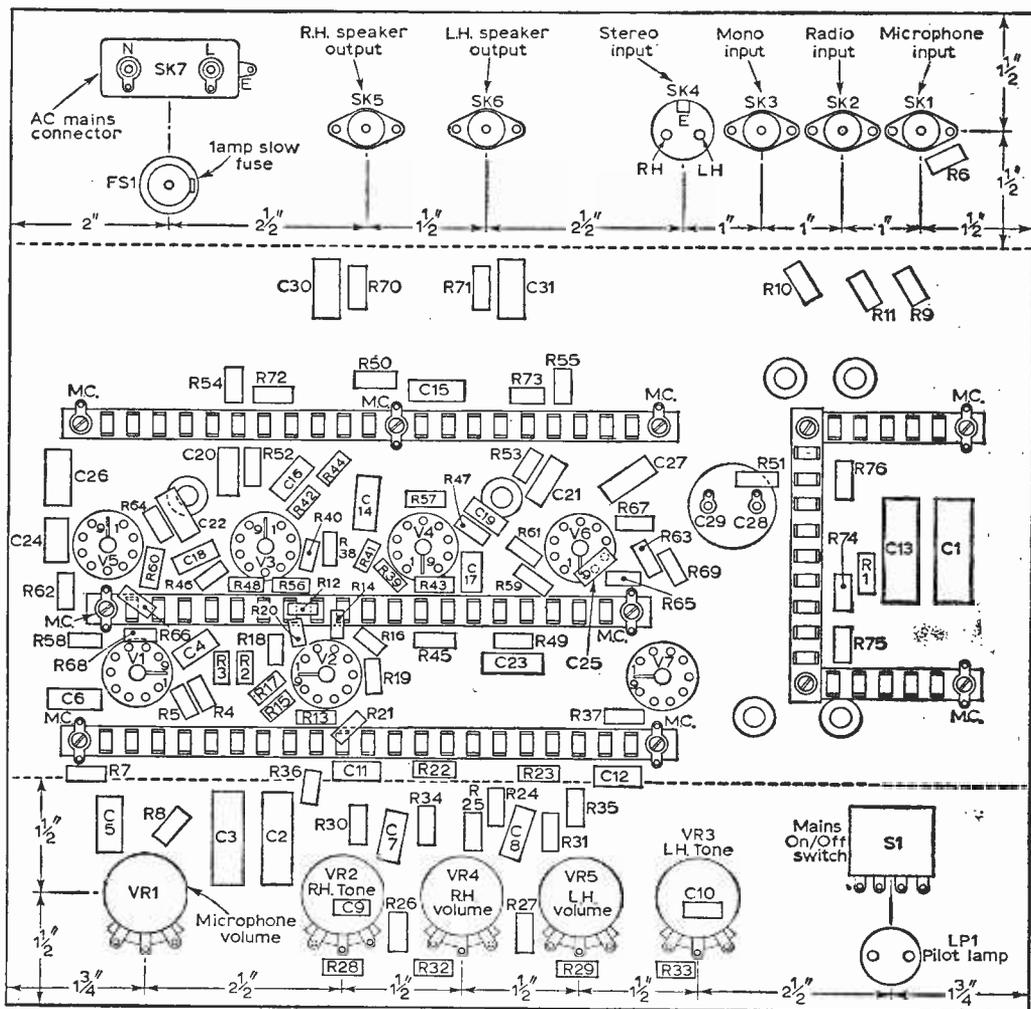


Fig. 2: Underchassis layout diagram.

pick-up units have extra contacts shorting the output when the motor is not running: R10 (and R24, R25 in the case of the stereo input SK4) thereby prevent shorting of other signals in the amplifier. At the same time, these decoupling resistors permit a wide range of fixed adjustments to the relative gains for the various inputs to be made, for optimum performance with a particular set of equipment.

**Hum Removal**

The principal gain reserves of the "7-20" stereo amplifier lie in the anode circuits of V3, V4 at pin 1. Gain can be increased by increasing the values of R44 and R45 and decreasing the values of R42, R43 by the same amount—and vice versa. In the extremes, the gain of the entire amplifier can be raised by a factor of five times, or reduced to zero, by these measures.

When making adjustments, it should first of all be checked whether the arrangement shown, with split anode loads, gives least hum output, or whether it is better to replace R42-R45 by a pair of 220kΩ 1/2W resistors, taking C16 and C17 still to the tops of R56 and R57, but splitting these resistors appropriately for the grid pin 7 feeds. The precise conditions will here depend somewhat on the exact positions of heater wiring, etc.

In general, heater wires should be run low in the chassis, hard up against the metal bottom, and other circuit wiring held well clear. If necessary, heater wires should be in the form of tightly twisted leads, one of which is earthed to chassis in passing each valveholder. It may also prove of advantage to experiment with small aluminium shields (earthed to chassis) between the rectifier (V7) valveholder and the control panel VR1 to VR4.

Gain Adjustments

Having minimised residual hum, the split anode or grid loads (whichever are finally adopted) in V3 and V4 should be adjusted until the desired normal volume of output (not necessarily full power) is obtained from the chosen microphone connected at P1 and whilst speaking at the average intended distance and loudness, VR1 being at mid-track and all other controls at maximum.

Having completed this adjustment, VR1 should be turned down to zero, and all other controls to half-track. The desired radio receiver should then be adjusted to normal intensity on its internal speaker, and then switched over to SK2 of the amplifier, making adjustments to R11 if necessary, as already discussed. R9 should then be adjusted until the amplifier is on the verge of overloading, on both channels.

The radio receiver should then be disconnected from SK2 and the desired monaural pick-up

the producer and his helpers during dances and other functions.

Choice of Components and Alternatives

Specified values of electrolytics should not be reduced, though slightly larger values, if able to be accommodated are permissible.

The main smoothing resistor, R51, may be replaced by a choke of about 10 to 20 henries inductance and about 30mA (not less) current rating. C28 and C29 must be high surge-rating electrolytic cans; whether two separate cans or a single double-value can is used is immaterial. The voltage rating must be 500V, for low leakage current at the operating voltage. All other electrolytics are small tubular items of lower voltage rating, as specified in the parts list.

The mains transformers h.t. windings must be 250-0-250V. Other voltages, lower or higher, are not permissible. The no-signal d.c. current drain from the rectifier cathode is 110mA and rises to

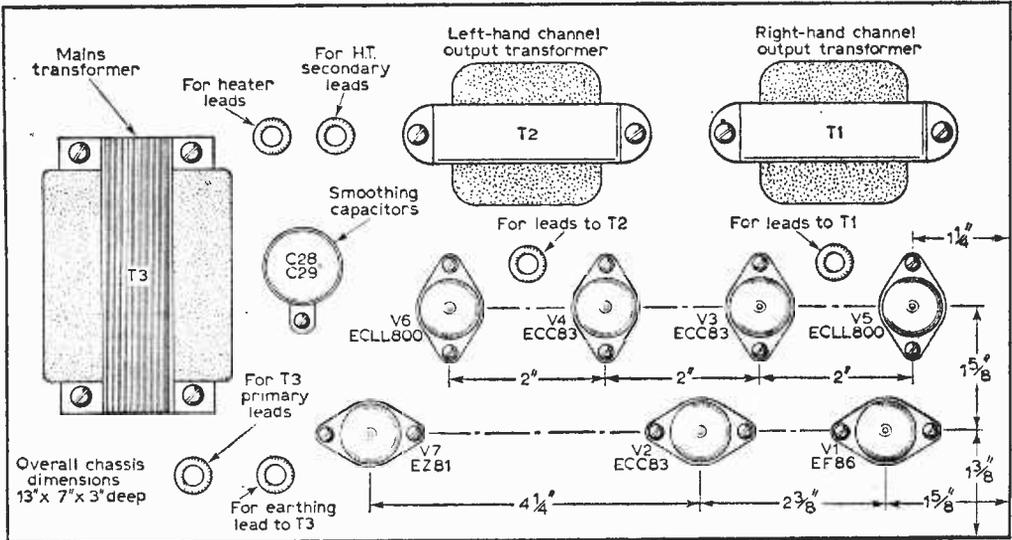


Fig. 3: Above-chassis layout and dimensions.

connected at SK3. If the makers specify a particular pick-up circuit, the additional resistors and capacitors must be included below the pick-up arm mount on the record player.

The four main amplifier controls should be advanced to maximum, and a medium intensity record played. R10 should be adjusted such that the amplifier definitely overloads, to allow a margin of safety for weaker recordings. The same procedure should then be repeated for the stereo input socket, SK4, adjusting the values of R24 and R25 (but always maintaining them equal).

It should be added here that, in general, the use of both monaural and stereo pick-ups, at SK3 and SK4, is not necessary, as all stereo record players will also play normal monaural records (but not vice versa: stereo records are immediately destroyed if played on a normal record player). However, the use of two turntables, only one of which need be stereophonic, gives greater scope for

150mA at full drive. The transformer and rectifier must thus be rated for 150mA.

Regarding output transformers, types standardised for a pair of 6V6 or EL84 valves in push-pull are usable, and should present no difficulty in obtaining. If winding these items oneself, according to general tables and experience, one should aim at an impedance of 11kΩ anode-to-anode, this being the optimum value, but by no means over critical.

An EZ81 rectifier, as specified, is essential. Type EZ80 is not suitable as a substitute, as it has insufficient maximum current rating.

Tone Controls

In the following discussion, component numbers from the right hand channel will be referred to. Similar remarks apply to corresponding components in the left hand channel.

Beyond C7 the feed to V3 is split into a bass branch (via R30) and into a treble branch (via R28). The treble branch is variable, giving maximum (level) treble response with VR2 slider at the top; movement of the slider towards C9 reduces treble response. The action can be made more powerful, if desired, by increasing the value of C9, and vice versa. If rising treble response is desired, a capacitor of between 100pF and 250pF should be inserted between the top end of VR2 and R28.

The bass branch gives about 10dB fixed boost. This can be reduced by increasing the value of R34. Increase of bass boost is achieved in the negative feedback circuit if required (see below).

If a variable bass control is to be added, this

should be in the form of a 500kΩ linear potentiometer whose track is connected across C11, R34 then goes to its slider.

A further (approximately) 5dB of bass boost are obtained by means of R70 and C30, which reduce negative feedback over the main amplifier loop at low frequencies and thus increase gain. The amount of bass boost contributed here can be increased by increasing the value of R70, and vice versa. The turnover frequency for the bass boost can be raised by decreasing the value of C30, and vice versa.

Whatever alterations are made to one channel during all these adjustments *must* be made to the  
 —continued on page 1070

**COMPONENTS LIST**

**Resistors:**

- R1 10kΩ 1W
- R2 27kΩ 1W
- R3 47kΩ 1W
- R4 100kΩ 1W
- R5 220kΩ
- R6 1MΩ
- R7 820Ω
- R8 220kΩ
- R9 470kΩ
- R10 100kΩ
- R11 47Ω 1W
- R12 1MΩ
- R13 1MΩ
- R14 2.7kΩ
- R15 2.7kΩ
- R16 47kΩ
- R17 47kΩ
- R18 180kΩ
- R19 180kΩ
- R20 2.7kΩ
- R21 2.7kΩ
- R22 1MΩ
- R23 1MΩ
- R24 220kΩ
- R25 220kΩ
- R26 680kΩ
- R27 680kΩ
- R28 180kΩ
- R29 180kΩ
- R30 180kΩ
- R31 180kΩ
- R32 180kΩ
- R33 180kΩ
- R34 180kΩ
- R35 180kΩ
- R36 15kΩ
- R37 15kΩ
- R38 2.2kΩ
- R39 2.2kΩ
- R40 2.7kΩ
- R41 2.7kΩ
- R42 180kΩ
- R43 180kΩ
- R44 47kΩ
- R45 47kΩ
- R46 220kΩ
- R47 220kΩ
- R48 27kΩ
- R49 27kΩ
- R50 47kΩ 1W
- R51 1kΩ 2W
- R52 2.7kΩ
- R53 2.7kΩ
- R54 100Ω
- R55 100Ω
- R56 680kΩ
- R57 680kΩ
- R58 1MΩ
- R59 1MΩ
- R60 1kΩ
- R61 1kΩ
- R62 180Ω 2W
- R63 180Ω 2W
- R64 150kΩ
- R65 150kΩ
- R66 1kΩ
- R67 1kΩ
- R68 1MΩ
- R69 1MΩ
- R70 2.2kΩ
- R71 2.2kΩ
- R72 1kΩ
- R73 1kΩ
- R74 100Ω 2W
- R75 100Ω 2W
- R76 10kΩ 1W

All Carbon, ½W, ±10%, unless otherwise stated.

**Capacitors:**

- C1 16μF electrolytic 350V
- C2 16μF electrolytic 350V
- C3 16μF electrolytic 350V
- C4 8μF electrolytic 350V
- C5 0.02μF paper 500V
- C6 50μF electrolytic 12V
- C7 0.05μF paper 500V
- C8 0.05μF paper 500V
- C9 500pF ceramic 500V
- C10 500pF ceramic 500V

- C11 0.02μF paper 500V
- C12 0.02μF paper 500V
- C13 16μF electrolytic 350V
- C14 16μF electrolytic 350V
- C15 0.05μF paper 500V
- C16 0.1μF paper 500V
- C17 0.1μF paper 500V
- C18 0.02μF paper 500V
- C19 0.02μF paper 500V
- C20 100μF electrolytic 12V
- C21 100μF electrolytic 12V
- C22 8μF electrolytic 350V
- D23 8μF electrolytic 350V
- C24 0.02μF paper 500V
- C25 0.02μF paper 500V
- C26 250μF electrolytic 25V
- C27 250μF electrolytic 25V
- C28 100μF } double can electrolytic 500V
- C29 50μF }
- C30 0.25μF paper 500V
- C31 0.25μF paper 500V

**Potentiometers:**

- VR1 250kΩ log
- VR2 500kΩ lin
- VR3 500kΩ lin
- VR4 500kΩ log
- VR5 500kΩ log

**Valves:**

- V1 EF86
- V2 ECC83
- V3 ECC83
- V4 ECC83
- V5 ECLL800
- V6 ECLL800
- V7 EZ81

**Sockets:**

- SK1 Coaxial panel type
- SK2 Coaxial panel type
- SK3 Coaxial panel type
- SK4 Stereo pick-up
- SK5 Stereo speaker
- SK6 Stereo speaker
- SK7 Mains connector, 3 pole

**Transformers:**

- T1, T2 Push-pull output transformer. Primary 11kΩ, secondary to suit speaker. (Allen OPI348). Any conventional transformer for 6V6 or EL84 valves is suitable.
- T3 Mains transformer. Secondaries: 250-0-250V 150mA; 6.3V 4A.

**Miscellaneous:**

- FS1 Panel fuse
- LPI Panel pilot lamp 6.3V
- S1 D.P.S.T./Q.M.B. on/off toggle switch
- Chassis 7in. x 13in. x 3in. approx. Perforated cover. Wire, sleeving, tagstrips, bolts, grommets. Control knobs. Seven noval (B9A) valve holders.

# A New Build-and-Learn Series—I

## The "JUNIOR" Crystal Set

*This series of receivers was designed primarily to give practical aid to students at an Evening Class. The circuits are unusual, but not novel. The final stage receiver is much more sensitive than most two transistor receivers, but is not more difficult to build.*

*The text is written for the young beginner and naturally more advanced readers will find some of the information superfluous. The author is sure that any beginner will be able to make this radio as a result of this article.*

**S**TAGE-BY-STAGE method of construction is adopted in this new series for the beginner. The design develops from a simple basic crystal receiver to an advanced two-transistor regenerative reflexed circuit for operation on long and medium waves. At the end of each stage the constructor will possess a fully-working receiver; he will, furthermore, have acquired a good understanding of the theory involved, since a simple description of how each circuit functions is given in addition to full practical details concerning components and wiring.

Much enjoyment will undoubtedly be obtained from the operation of each receiver in the series and for a time the beginner may be loth to embark on the modifications necessary to convert one model to the next design. However, in his own good time he can follow this series of articles through to the conclusion.

It is not recommended that earlier stages be 'short-circuited' in an attempt to build the final receiver as soon as possible. Beginners should adhere closely to the text and build and test out each stage in succession. In this way full benefit will be obtained from this "build and learn" series.


### The Components

The components and other materials required are given in the components list. All items could be obtained straight away; alternatively just those for the first stage circuit (see Fig. 3) and others acquired as the construction proceeds.
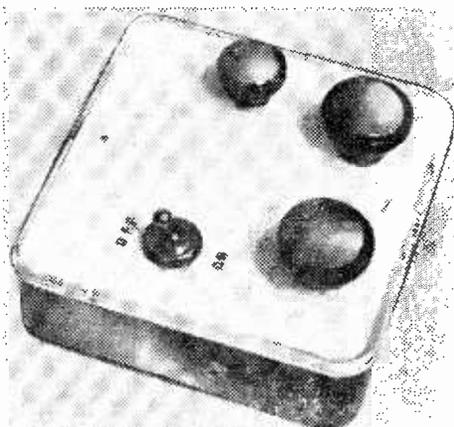
### Commencing the Construction

A piece of Formica or similar plastic board is sawn with a tenon or hack saw to the size shown in Fig. 1. The edges are rounded and it is tried for easy fitting into the clear plastic sandwich box.

The holes for the reaction and the tuning capacitors must be so placed that the capacitors fit inside the plastic board but as near to the top of Fig. 1 as possible. The switch S1 is then measured and the hole drilled to suit (probably



The final stage receiver complete.

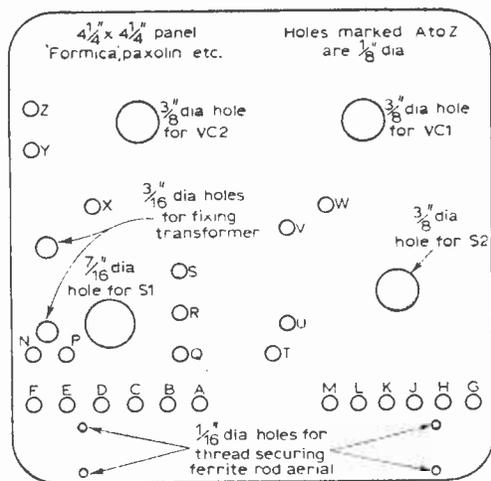


Fig. 1: Drilling details of the plastic board.

$\frac{1}{8}$  in.). A similar ( $\frac{1}{8}$  in.) hole is drilled for the rotary switch (S2).

Numerous small  $\frac{1}{16}$  in. holes and two  $\frac{1}{8}$  in. holes are then drilled as shown; great accuracy is not required. The holes are then lettered in pencil to provide a check when wiring up. The plastic board then appears as in Fig. 1.

**Mounting the First Component**

The tuning capacitor (VC1) is mounted as shown in Fig. 2(a) and secured with a lock washer and nut. A nut and bolt with two solder tags are then fitted to each  $\frac{1}{8}$  in. hole (that is those marked A to Z), three of these being shown in Fig. 2(a). The nuts are on the component side of the sheet and the heads on the "knob" side. The two tags fit together on the component side. Alternatively constructors may prefer to add the nuts, bolts and tags as they proceed stage by stage rather than fitting them all at the commencement.

The first working practical circuit and layout is shown in Fig. 3 and the tags needed are clearly shown.

**Winding the L.W. Coil**

Full details for winding the l.w. coil are given in Fig. 4 but only stage 1 is required now.

A small piece of postcard is cut to make a tube to slide easily over the ferrite rod and is held with Sellotape. Tie an identification knot in the loose

end of a reel of 32s.w.g. enamelled copper wire (do not pull this tight or the wire may break). Leave a few inches spare for connection later and then wind on 65 or 70 turns in as small a pile as possible. Then move over to make another similar pile  $\frac{1}{4}$  in. away wound definitely in the same direction. Wrap lightly with Sellotape to prevent


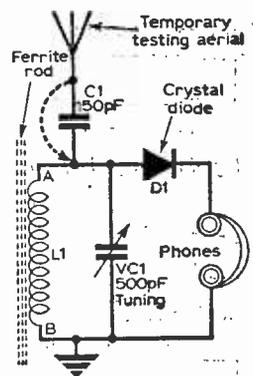


Fig. 3a.(above): The first stage circuit.

Fig. 3b (below): Wiring for the diode receiver.

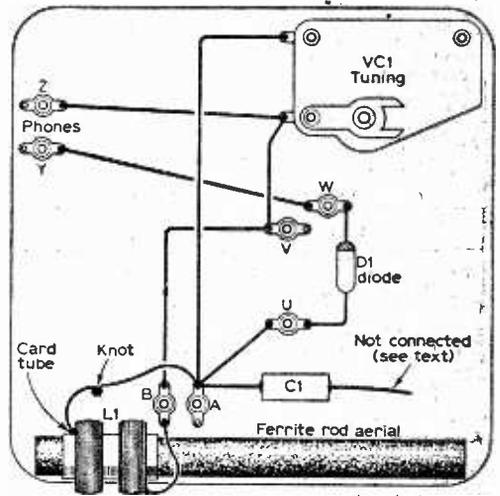

the coils coming loose. The knotted wire is "A" in Fig. 3, the unknotted end being "B". If the coil has been correctly wound the ferrite rod will slip nicely in and out of the coil at will.

**Wiring the First Receiver**

The beginner is advised to use only radio-type multi-cored solder and no other flux than that contained in the solder. Every connection point, both wire or tag, must be scraped absolutely clean and bright with a penknife and then tinned. The iron must be held on the part until enough heat has conducted to make this tinning perfect. Do not make any joint by piling on solder. If the tinning is not done properly a "dry joint" will result and the set will either fail to work or will be very noisy.

Thin covered connecting wire is used and only a  $\frac{1}{16}$  in. to  $\frac{1}{8}$  in. length is bared at the ends. No surplus whiskers of wire must be left sticking out

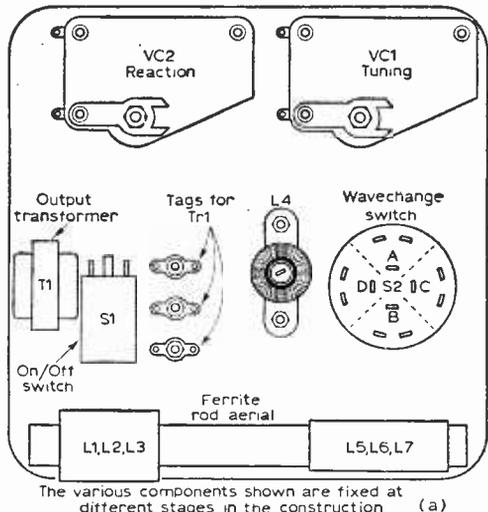


Fig. 2a (above): The positions of the major components.

Fig. 2b, c, d (below): Methods of mounting the ferrite rod, T1 and S2.

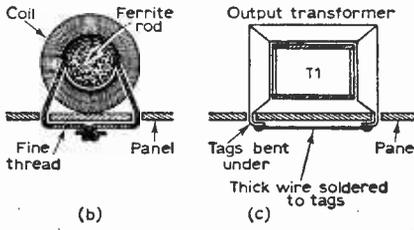




Fig. 4a: Stage 1 of construction of long wave coil.

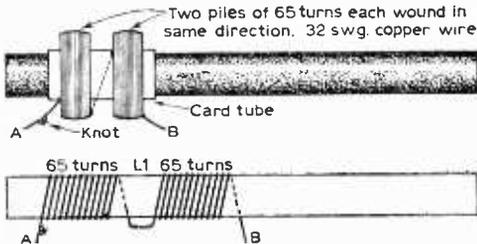


Fig. 4b: Stage 2.

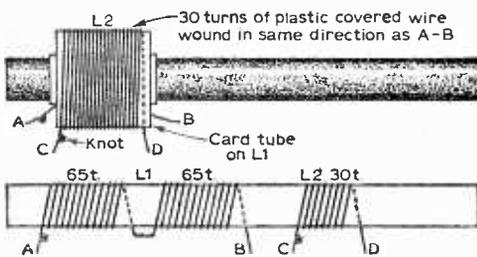


Fig. 4c: Stage 3.

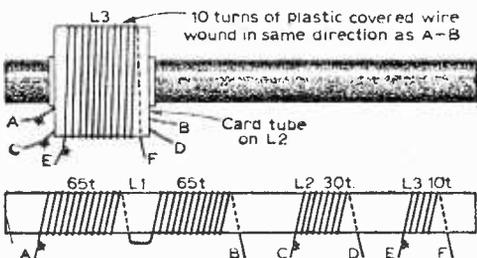


Fig. 4d: Stage 4.

of joints to cause unwanted and annoying shorts.

The following connections are made:

1. Tag B to V and on to moving vanes of VC1 (rotor).
2. A to fixed vanes of VC1 (stator).
3. A to U.
4. Moving vanes VC1 to phones tag Z.
5. W to other phones tag Y.
6. The coil ends are scraped of enamel and soldered to A and B respectively. Join also C1 to A.
7. The diode D1 is soldered in (either way round) between W and U.

#### Soldering Diodes and Transistors

Care is needed when soldering semiconductor devices such as diodes and transistors. Do not shorten the leads on these components to less than about 1in. Use a small instrument-type soldering

iron and when this is fully heated apply the bit to the joint and complete the soldering operation as quickly as possible. It is a good idea to place a metal tool on the diode (or transistor) lead so that this conducts heat rapidly away and thereby

#### COMPONENTS LIST

A complete list of all the components required covering all stages of construction.

##### Resistors:

- R1 150kΩ brown, green yellow
- R2 10kΩ brown, black, orange
- R3 47kΩ yellow, violet, orange
- R4 2.2kΩ red, red, red
- R5 100kΩ brown, black, yellow

Colour code: The colours given above read as follows: 1—band at extreme end of resistor, 2—second band, 3—third band.

All resistors are carbon composition, 10% tolerance, and  $\frac{1}{4}$  or  $\frac{1}{2}$ W.

##### Fixed Capacitors:

- C1 150pF (0.00015μF) ceramic or mica
- C2 0.1μF paper, any working voltage
- C3 150pF (0.00015μF) ceramic or mica
- C4 5μF electrolytic, 12 to 25V working
- C5 25μF electrolytic, 12 to 25V working
- C6 0.01μF paper, any working voltage
- C7 100μF electrolytic, 12 to 25V working

##### Variable (Tuning) Capacitors:

- VC1 500pF (0.0005μF) mica dielectric } (Radio-
- VC2 300pF (0.0003μF) mica dielectric } spares)

##### Ferrite Rod:

Rod, preferably  $\frac{3}{8}$ in. diameter, and at least 4in. long, although the longer the better. A  $\frac{1}{2}$ in. diameter rod could be used, but the results would be somewhat inferior.

##### Inductances (Coils):

- L1, L2, L3 are coils (Long Wave) wound on the ferrite rod.
- L5, L6, L7 are similar Medium Wave coils.
- L4 is a small home-made high frequency choke.

Wire for these coils: 2oz. of 26s.w.g., 2oz. of 32s.w.g. enamelled copper wire, and a few yards of thin plastic covered connecting wire.

Coil Former:  $\frac{1}{2}$ in. diameter by  $1\frac{1}{2}$ in. high, with a few ferrite cores (an old T.V. set will supply this).

##### Transistors:

- Tr1 OC44, first grade, not surplus.
- Tr2 Preferably OC81, but an OC72 will do.
- D1 Germanium diode, OA70, OA81.

##### A.F. Transformer:

- T1 Radiospares T/T3, ratio 3:3:1.

##### Switches:

- S1 Toggle type, on/off.
- S2 Rotary type, single wafer, four-poles, two-ways.

##### Battery:

- B1, 9V Exide DT3 or Ever Ready PP3


##### Miscellaneous Items:

- 3 doz. 6 B.A. nuts and bolts,  $\frac{1}{2}$ in. long is sufficient.
- 3 doz. solder tags to suit. Cored solder. Thin, plastic covered, coloured connecting wire.
- Knobs. Plastic sandwich box, approx. 5in. x 5in. or 5in. x 7in. if a miniature speaker is to be fitted later. Phones: ex-Govt. DLR type (reed type) are best, but crystal insert can be used. Battery connectors. Laminated plastic sheet, 5in. x 5in.
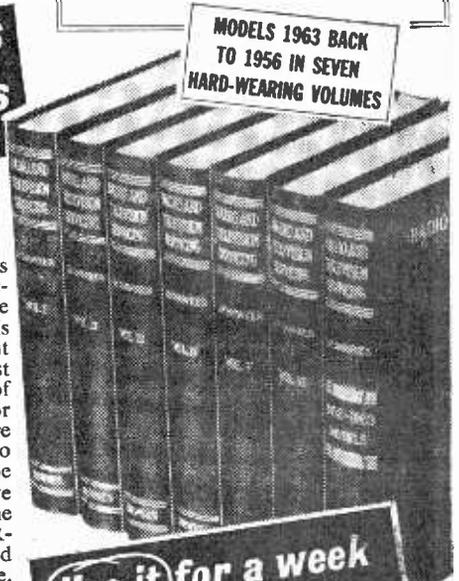
# THIS MAKES MONEY FOR YOU FOR YEARS TO COME!

TELEVISION  
 RADIO • RADIOGRAMS  
 CAR RADIOS  
 TAPE RECORDERS  
 RECORD REPRODUCERS

**CIRCUITS • DATA • SERVICING HINTS**  
 For over **2,900** Models



## Newnes RADIO and TV Servicing

Over 50,000 sold!  
 Now comes the greatest edition of all.

**A REAL MONEY-SPINNER VITAL TO THE SHREWD RADIO MAN**  
 This New 11th Edition of Newnes famous repair set equips you for quicker servicing and more profit! With sets capable of giving longer service you need this data more than ever. It is your constant reference to sets marketed over the past eight years—always at hand instead of loose paper data so easily mislaid or destroyed. To-day there are also more radios and transistor portables, stereo radiograms, record reproducers, tape recorders, car radios than ever before—all needing expert service from time to time. Newnes RADIO & TV SERVICING provides you with data and information needed for years to come. Prove this investment now by 7 days' Free Trial.

Over 4,500 Pages of Circuits, Component Layout Diagrams, Quick-Ref Data and Latest Developments

Use it for a week  
**FREE**  
 NO OBLIGATION TO BUY

### DATA FOR ALL THESE MAKES

Ace, Ajax, Alba, Ambassador, Argosy, Armstrong, Baird, Beethoven, Berec, Brayhead, B.R.C., B.S.R., Bush, Capitol, Champion, Channel, Collaro, Cossor, Cyldon, Dansette, Decca, Defiant, Dynatron, E.A.R., Eddystone, Ekco, Elizabethan, Elpico, Emerson, E.M.I., Emisonic, English Electric, Ever Ready, Ferguson, Ferranti, Fidelity, Ford Motor Co., Garrard, G.B.C., G.E.C., Gramdeck, Grundig, H.M.V., Invicta, K-B, Magnavox, Marconiphone, Masteradio, McCarthy, McMichael, Motorola, Murphy, Pageant, Pam, Perdio, Peto Scott, Philco, Phillips, Pilot, Portadyne, Portogram, Pye, Radiomobile, Raymond, Regentone, R.G.D., Roberts' Radio, Sobel, Sony, Sound, Spencer-West, Stella, Stereosound, Strad, Ultra, Vidor, Volmar, Walter, Webcor, Zenith.

GIVEN WITH EVERY SET  
**Newnes TV ENGINEERS POCKET BOOK**  
 (Value 12/6)

An invaluable companion to your set for on-the-spot repairs. 272 pages of reference data on installing, fault-tracing and repairing, servicing equipment, etc.



FOR EVERY PURCHASER —  
 2 YEARS FREE POSTAL  
 ADVISORY SERVICE.

*Quicker work Builds Goodwill  
 -Makes more Profit!*

Geo. Newnes Ltd.,  
 15-17 Long Acre,  
 London, W.C.2.

Send me Newnes  
 RADIO AND TELEVISION  
 SERVICING (in 7 Volumes) and TV  
 ENGINEERS POCKET BOOK without  
 obligation to purchase. I will return them in 8 days or send 16/- deposit 8 days after delivery, then twenty monthly subscriptions of 16s, paying £16.16s in all. Alternatively, in 8 days I will remit the full cash price of £16.16s.

If under 21 your father must fill up this coupon. If married woman your husband must fill it up.

Full name.....  
 (BLOCK LETTERS) (Mr., Mrs., Miss)


Address.....

Occupation.....

Signature.....  
 (Mr., Mrs., Miss) (RV) 40/95

Tick V where applicable  
 The address on left is—

|                    |                          |
|--------------------|--------------------------|
| My Property        | <input type="checkbox"/> |
| Rented unfurnished | <input type="checkbox"/> |
| Parents' Home      | <input type="checkbox"/> |
| Furnished Accom.   | <input type="checkbox"/> |
| Temporary Address  | <input type="checkbox"/> |

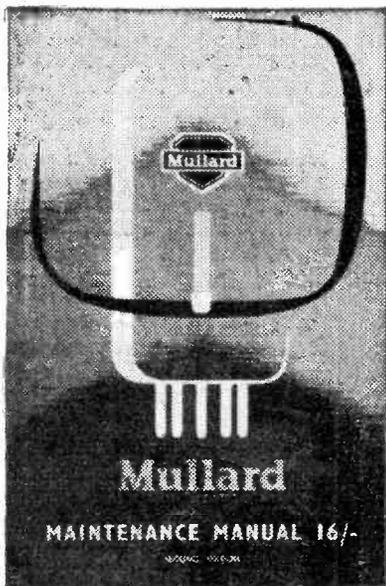

# 6 SIX GOOD REASONS WHY YOU NEED THE NEW EDITION OF THE Mullard MAINTENANCE MANUAL

1. This is a completely new and up-to-date edition including data on all current replacement valves, semiconductors and cathode ray tubes. It contains valuable new material essential as reference for every Service Engineer.
2. Supplementary data sheets will be issued from time to time to provide data on new types. This service is included in the initial price of 16/-.
3. The binding of this edition is specially designed to allow the supplementary data sheets to be inserted simply and without gluing.
4. The manual contains full data on 178 separate types and the equivalents list of current types provides cross-references to 480 types.
5. All devices are listed in alphabetical order for easy reference.
6. The data on each type has been carefully compiled to supply the information which the Service Engineer is most likely to require, including very clear base diagrams for each type.



NOTE: A few copies of the previous edition are still available at 10/6d. each (postage and packing 1/- extra).

Published by Mullard Ltd. U.K. Price 16/- . Get your copy from your radio dealer or order direct from MULLARD LTD., DEPT. B., MULLARD HOUSE, TORRINGTON PLACE, LONDON, W.C.1. (Postage and packing 1s. 0d. extra.)

MVM402

## "THE CONSTRUCTOR'S PARADISE"

### BEAR HUDSON LTD.

63 GOLDHAWK RD, SHEPHERD'S BUSH, LONDON, W. 12  
 Now open at 11 JERDAN PLACE, FULHAM, LONDON, S.W. 6. Phone: FUL3405

#### SPECIAL MICROPHONE OFFERS

##### "Planet" SUPER X-TAL MIKE

Fantastic value. Beautifully made modern styled crystal mike in strong plastic housing. With approx. 5ft. sheathed cable and miniature jack plug. Response 50 to 15,000 c/s. High impedance. Guaranteed. List price 30/-.

##### TSL Mk. II "STUDIO SPECIAL" MOVING COIL

Designed for professional quality reproduction

With improved diaphragm and coil assembly. Complete with 6ft. cable and non-slip base. In elegant "sound-dome" contoured case. Sensitivity—1mV per micro-bar at 1,000 c/s. Completely smooth response from 40 to 15,000 c/s. Output impedance—50KΩ. Pattern—spherical lobe. Leaflet on request.



Grey plastic with plated metal

79/6

##### TSL Mk. 2 THREE CHANNEL MIXER

The most popular low-priced mixer ever made! Can be used with any tape recorder. Complete with colour-coded plugs, modern controls. Gold hammer finished steel case.



47/6

##### H.L.P. 2 CROSSOVER NETWORK

For frequency base and treble speaker systems. Essential to perfect hi-fi reproduction.

47/6



SPECIAL PRICE

12/6

LIST 30/-

#### BEST OF ALL B.H. "HI-FI 14" with integrated tone controls and mix facilities

A real break-through in hi-fi value! This superb amplifier designed by Dr. W. J. May incorporates valuable features including two high gain inputs, each with its own volume control to permit mixing! Multiple neg. feedback loops can be varied. Robust design using quality components means dependability at all times. Frequency response—25-25,000 c/s ± 2dB. Separate bass and treble cut and lift controls. Output—3 or 15 ohms. With punched chassis, valves and instructions.

FANTASTIC VALUE AT THE PRICE!

Complete kit of parts as described

£7.19.6

Built and tested

£9.18.6



#### COMPONENTS - HI-FI - BOOKS - SERVICE

24-HOUR MAIL ORDER SERVICE with all goods guaranteed.

★ FREE POSTAGE on orders over 20/-; add 1/- postage if under.

★ LOWEST PRICES FROM BULK PURCHASING AND MANUFACTURING

#### B. & O. 609 4-WAVE BAND EXPORT TRANSISTOR SET DE-LUXE


INSTANTLY ADAPTABLE TO A TRUE CAR RADIO. SUPER QUALITY 7 x 4in LOUDSPEAKER  
 Reduced from 15 $\frac{1}{2}$  gns. to



4 wavebands (L.M. and 2 Short). Push button control; 7 transistors + 4 diodes; A.V.C. built-in suppressors. Made by world famous B. & O. A truly de-luxe set: speaker and aerial connections. Strong cabinet, covered dove grey.

● ALL SINCLAIR DESIGNS AND MARTIN AUDIOKITS IN STOCK

#### THE TSL CONSTANT VELOCITY EQUALISER

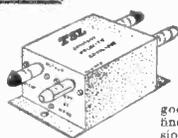

This remarkable new TSL development enables quality almost as good as the finest professional magnetic pick-ups to be obtained from crystal or ceramic types. With it, even cheap record players become first-class instruments. With good equipment results are astonishing. Ideal for B.S.R. Coliario, Garrard and Accos. With plugs for mono or stereo. 3 years' guarantee. Ready for use.

30/- Thousands sold. POST FREE

**TRANSISTOR OPPORTUNITIES**  
 OC.71—special offer, 3/9; OC.45, 5/6; OC.44, 6/-; OC.169, 8/-; MAT 100 or 120, 7/8; MAT 101 or 121, 8/6; ADT.140 with 500 mc/s cut-off, 15/-.

Orders by post to BEAR HUDSON LTD., Dept. PW.3, 63 Goldhawk Rd., London, W. 12

prevents the component becoming heated. *Excessive heat can cause serious damage to semi-conductor devices.* Do not allow the iron to approach near the diode or transistor body.

A pair of pliers can be used as a "heat shunt" in the manner shown in Fig. 5.

**Testing the First Circuit**

At this stage the circuit is a simple diode receiver as shown in Fig. 3(a) and it may be tested as follows. For this test an aerial and earth is required, although when entirely completed the receiver will be fully portable and no external aerial or earth will be needed.

A wire is taken from a water tap (or other good direct earthing point) and connected to tag B. About 100ft of wire is temporarily erected in the garden (or slung backwards and forwards across the loft) and one end is connected to A. A pair of headphones are connected to the labelled tags (Fig. 3). The ferrite rod is placed so that it is almost entirely out of the coil. The tuner capacitor VCI is fitted with a knob and is adjusted so that the vanes are fully open.

component or to one or more of the vanes having become bent.

Another cause of intermittent contact between the two sections of the capacitor could be the presence of dirt and dust containing metallic particles. Second-hand components in particular should be carefully examined and cleaned if necessary with a feather or pipe cleaner.

When the test is applied to the inductance—see Fig. 6(b)—the lamp will light, although maybe not at full brilliance. No light from the lamp indicates an "open-circuit" coil and the break in the wire must be located and repaired if possible.

The tests described are simple yet effective. Furthermore, the principles involved are basic to those more elaborate methods of testing that you are likely to encounter as your experience increases.

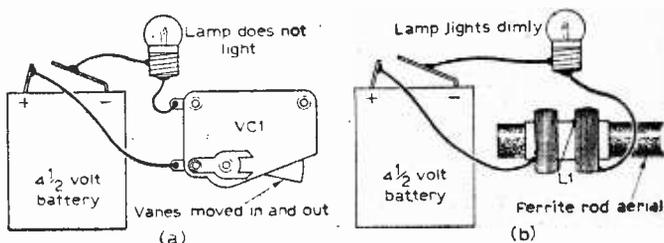


Fig. 6a: Testing the variable capacitor, VCI; b: testing the coils.

**A Further Test of the First Circuit**

When testing you will note that the ferrite rod had to be almost out of the coil and VCI almost open. This means really that the coil L1 has been made too long; this is deliberate because later on no external aerial is to be used.

If reception in the first test was reasonable (and at Bognor Regis in Sussex and in London it was exceptionally good) remove the aerial from A and connect it temporarily to the spare end of C1 (Fig. 3).

Place the coil somewhere near the centre of the ferrite rod and tune with VCI. Now the tuning will be sharper (selectivity better) and the vanes will be almost but not quite in. If they have to be put right in then either you have made L1 too small or VCI is of a lower value than 500pF (sometimes expressed as 0.0005μF).

**Purpose of the Parts in this Circuit**

L1 and VCI form a "tuned circuit" which resonates (like piano strings do) at certain frequencies according to the setting of VCI. The aerial receives most frequencies, the one tuned by VCI will set up oscillations in L1 and these are rectified, i.e. converted into pulsating d.c. by the diode D1. This d.c. "audio" signal is fed to the phones and causes magnetism in them to fluctuate so the diaphragms are moved and produce sound waves.

No r.f. (radio frequency) bypass capacitor is required as the windings on the phones will bypass sufficient r.f. to earth due to their self-capacity.

The ferrite rod increases the inductance of the coil, which would otherwise have to contain many more or larger turns of wire.

**TO BE CONTINUED**

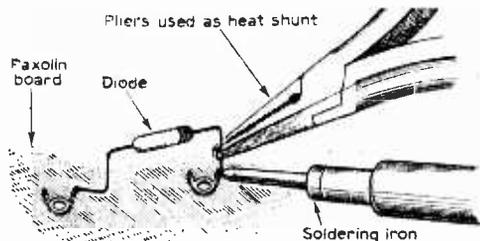


Fig. 5: Using a pair of pliers as a heat shunt during soldering.


If all is well the Light Programme (Droitwich, long wave) will be heard on 1,500m. It may be tuned by moving the capacitor VCI vanes and/or the ferrite rod in the coil L1. If this station is not received the circuit has not been correctly wired or a joint has been incorrectly made or a component is faulty.

**Component Testing**

Simple continuity and installation checks can be performed with the aid of a small battery and a flashlamp bulb. Fig. 6 illustrates the use of such equipment to check a variable capacitor and an inductance.

If the capacitor is in good order no light will appear in the lamp. The spindle should be turned to and fro during the test. If the lamp does light this indicates that the moving vanes (rotor) and the fixed vanes (stator) of the capacitor are touching.

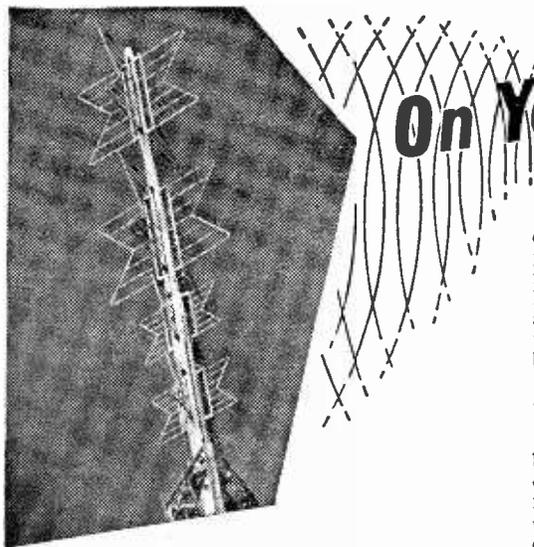This fault will be due either to mechanical misalignment of the two portions of the



# On Your Wavelength

## By THERMION

cases he is eager and willing to solve beginners' problems, but—and this is part of my argument in favour of "shopping around"—it does not take long to learn to discriminate between the obliging and knowledgeable shopkeeper or assistant, and the merely mercenary merchant who can't be bothered.

### The Kit Danger

One does not become a radio constructor merely by wiring up a transistor radio kit, any more than one becomes a carpenter by glueing together a factory prepared set of legs and a piece of plywood to make a coffee table. Here I must make it clear that this does not refer to the "build and learn" type of kit, which is intended for educational purposes and is accompanied with a printed text giving full instructions and explanations. Such kits are generally very useful teaching aids.

A SHORT time ago I commented on the apparent lack of initiative of those beginners who never venture beyond assembling radios bought in kit form, and I suggested that they were missing an awful lot by not shopping around for the individual parts.

Mr. Ken Greenberg, of Chicago, U.S.A., agrees in principle with me and in an interesting letter recalls his own first attempts at radio construction in the mid-thirties. He does, however, suggest (regretfully) that a youngster "... would be foolish to try and build something today by going out and buying the various parts needed from individual parts houses. In this country, anyhow, gone are the helpful clerks and shop owners of years ago. In fact most store owners are noticeably disturbed when a kid comes in for "just a few resistors."

Thus it seems so far as the U.S.A. is concerned the good old days of radio construction are something to be mourned, just another victim of the increasing tempo of present day life. However, I think it would be generally agreed that such a state of affairs has not yet developed in this country. Traditionally we have been more inclined (or perhaps compelled) to build our own equipment; on the other hand it is true that commercial equipment partly assembled, or in kit form is becoming more commonplace, and some will say that already "the writing is on the wall".

### Components for All

Surely, as long as there is a real demand for components, component shops will continue to cater for the individual, even if he only wants a 47k. The abundance of ex-Government and ex-Manufacturers' surplus equipment and components would seem to be an assurance against the disappearance of the component shops through non-availability of cheap parts.

As regards to the attitude of the man behind the counter, it would be idle to pretend that in all

As I see it, a serious objection to the proliferation of kits is that scores of people not having any interest in radio theory or design are induced to purchase a transistor radio kit simply because they hope to save a few pounds as compared with the cost of a commercially made receiver. One hears of the lack of interest, or even hostility of shopkeepers when such a purchaser returns to explain his trouble. I refuse to believe that radio shops nowadays are staffed only by sales automatons. What I think is likely is that the patience and good humour of many radio salesmen has been dissipated over recent years by the vast numbers of uninformed, inexperienced customers they have had to deal with. Such people devoid of any knowledge of electricity or radio take on the construction of, say, a multistage transistor radio of Lilliputian proportions, the set refuses to work first time (nothing particularly unusual here, as every experienced constructor knows) but the clueless ones do not know where to look and what simple tests to apply. Thoroughly disheartened, all they can do is return to the shop and burden the salesman with their tale of woe.

### Prudent Selling

Coming now to the crux of the matter, has not this state of affairs been brought about largely by the retailers who "push" these kits. Perhaps a little advice to the intending purchaser if he seems to be considering something rather too ambitious for his apparent talents would pay in the end. The immediate cash reward for the sale of a simpler and cheaper kit might not be too appealing—but the greater chance of a happy and satisfied customer with no subsequent complaints or bewildering faults to sort out must surely count for something on the credit side.

# A basic stabilised POWER PACK

By P. Cairns

*This unit will provide a steady d.c. supply from either 150 to 260V or 190 to 310V.*

**A**N extremely useful piece of equipment for the amateur workshop is a stabilised power pack. Where any serious experimental work is carried out such a unit is almost a necessity. Stabilised power units are also much used for supplying oscillators, transmitter v.f.o. and buffer stages and any other apparatus where frequency stability is at all dependent upon a constant h.t. voltage.

### *Inexpensive and Reliable*

The unit to be described has the advantage of being both inexpensive and reliable. It may be built up as an entirely new unit or an existing power pack may be modified.

### *Performance Details*

The purpose of any stabilised power unit is to provide a steady d.c. output which remains constant despite any reasonable variation in input voltage or load. This h.t. voltage should also be capable of variation over a specific range and have a low ripple content. In the power unit described the specification is extremely good. The h.t. voltage is variable over the range 150V to 260V or 190V to 310V depending upon the value of R9, with an h.t. stability factor of  $\pm 0.5\%$  for variations in load current between 0-100mA, and a stability factor of less than 1% for variations in supply voltage of  $\pm 10\%$ . Ripple value is less than 25mV at 250V

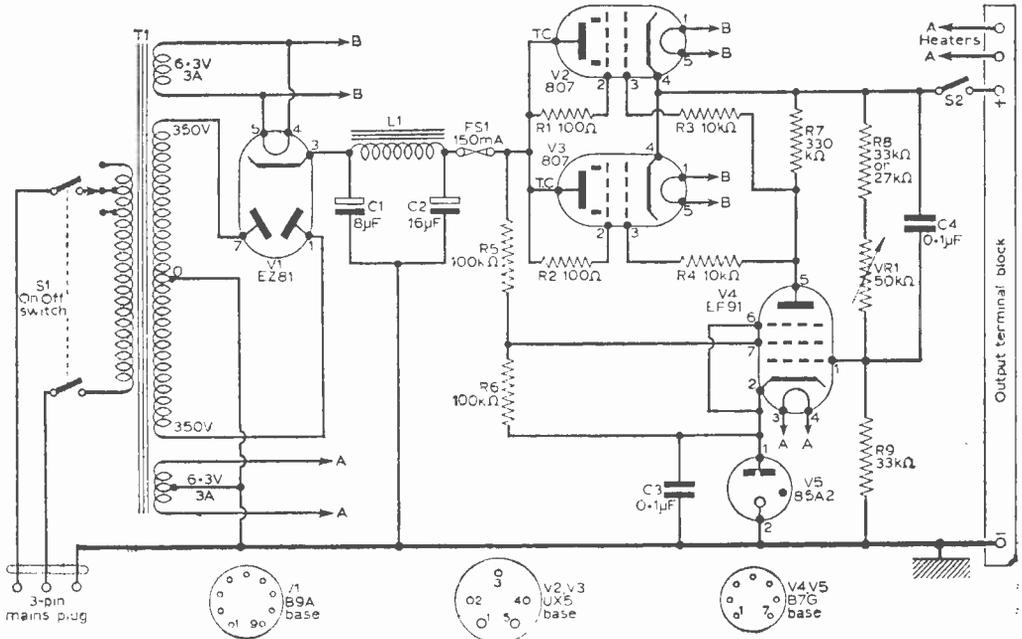


Fig. 1: The circuit diagram of the power pack.

with a 50mA current drain, i.e. ripple factor is better than 0.01%. If a smaller current output is required, that is, if lighter loads are anticipated, a smaller VA transformer can be used and one of the series stabiliser valves omitted. Thus, using a transformer having a 60mA secondary and with V2 omitted the rest of the circuit and

Fig. 2: An above-chassis view of the unit.

specification remains the same except that a load current of only 50mA is available.

As can be seen from the circuit diagram in Fig. 1, the front end of the unit is comprised of a standard mains transformer and full wave rectifier V1. The positive output is taken from the cathode of V1, via the smoothing circuit and fuse, to the stabilising circuit. Switches are included in both mains and h.t. circuits. A conventional type LC smoothing circuit is used, L1, C1 and C2, further smoothing being carried

Fig. 3: The under-chassis layout of components.

out by the stabilising circuit which "sees" the h.t. ripple simply as variations in the mean h.t. voltage level and immediately compensates for these variations. The result is an extremely smooth h.t. supply with a ripple value well below that of the average power unit and LC filter.

**The Stabilising Circuit**

The stabilising circuit is composed of two series stabiliser valves, V2 and V3, in parallel, the amplifier V4 and the neon reference tube V5.

The amplifier V4 is connected as a high-gain pentode, its cathode being maintained at a constant voltage (about 85V) by means of the reference neon V5. The grid of V4 is connected to the lower junction in a chain of resistors, R8, VR1 and R9, the grid voltage being variable over a limited range by means of VR1. The output from V4 anode is taken to the grids of the series stabiliser valves. A closed feedback loop is therefore formed, from h.t. line to V4 grid; from V4 anode to V2, V3

grids, then back to the h.t. line, the common reference point being the cathode voltage of V4 which remains constant despite any changes in h.t. voltage or current.

The action of the stabiliser circuit is self compensating and quite simple to follow.

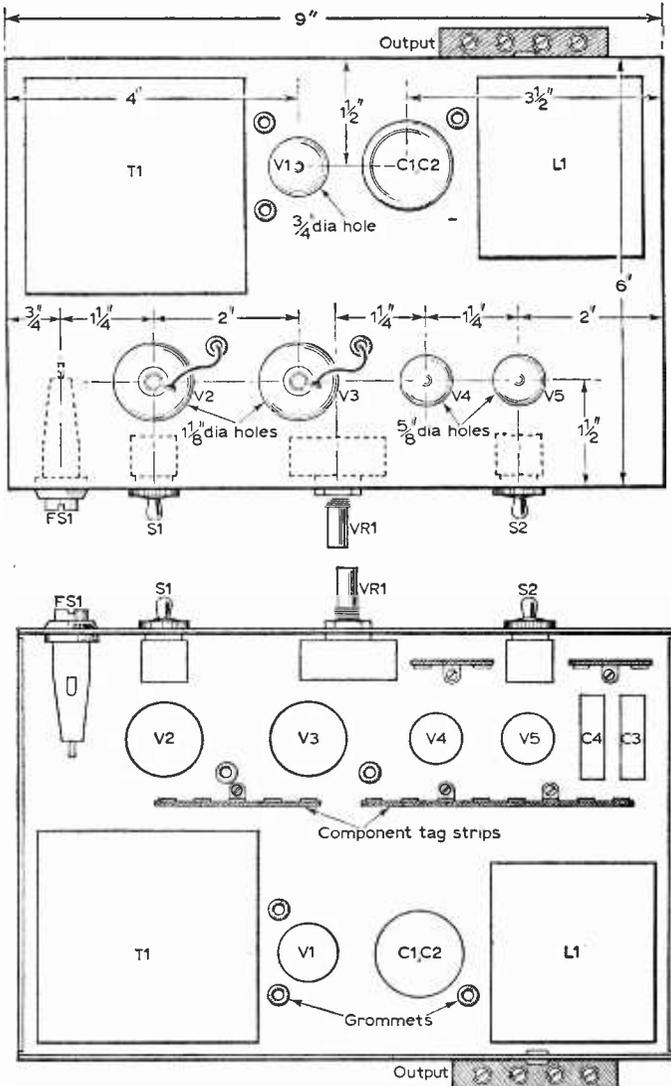


Fig. 4: The front panel of the unit.

Assume a sudden increase in load, the voltage across the resistor chain R8. VR1 and R9 will drop, V4 grid voltage will therefore drop and go more negative with respect to the cathode which is fixed. This tends to cut V4 off, reduces anode current and therefore reduces the voltage drop across the anode load resistor R7. The anode will now go positive (towards h.t.) and as this is d.c. coupled via the grid stoppers R3 and R4 to the grids of V2 and V3, these grids will go positive. The current through these valves will therefore increase and compensate for the extra load being delivered.

The action described is, of course, instantaneous. For a sudden decrease in the load current the action is reversed. Variations in input or mains voltage result in a similar reaction. The cathode of V4 is decoupled by C3 and the grid by C4, this further reducing ripple by increasing the time constant of the grid circuit and also obviating any tendency for V4 to oscillate. The small stopper resistors in the screens of the stabiliser valves are to prevent parasitic oscillation.

**Increasing the Current Supply**

The value of load current which can be taken is limited only by the maximum anode current and dissipation ratings of the series stabiliser valves, assuming, of course, that an adequate transformer is used. If therefore a larger current supply is required, an extra stabilising valve (or valves) is simply connected in parallel with those already in use without any other circuit alterations being necessary, the VA of the transformer being increased to suit.

The writer has used up to ten valves in parallel when a stabilised supply of 500mA was required.

Though there are many types of valve which can be used as series stabilisers, including special types designed for this specific purpose (KT55, 12E1, etc.), most large output valves with a high maximum. The stopper resistors R1 and R2 should be relatively low ra value are suitable, the valves being triode connected as in the circuit shown. Here 807 valves were used as they are a common type used by many amateur constructors and can be bought on the surplus market for a few shillings.

**Practical Layout**

The author's unit was originally designed to be added to an already existing power pack. Should a suitable type of power pack be already available the stabilising circuit can either be built on the existing chassis or if insufficient space is available, built on a separate sub-chassis.

A suitable layout for a complete unit is shown in Figs. 2 and 3, all relevant dimensions and layout being shown. The layout is not at all critical, tagstrips being used at convenient points for mounting components. The amplifier V4 and its associate circuitry should be kept reasonably clear of mains and transformer leads to keep pick-up to a minimum. The stopper resistors R1 and R2 should be connected directly on to the appropriate valve base pins.

Though the prototype unit had the controls mounted on the chassis front plate, a separate front panel can be made if required, this will facilitate rack mounting.

**The Mains Transformer**

Two heater windings, both 6.3V, are required. One is for the rectifier and series stabiliser valves, the other is the main centre-tapped supply for external use, V4 also using this supply.

The separate unearthed heater winding is necessary for the rectifier and series valves as the cathodes of these valves are all up at h.t. potential, and if a common earthed supply were used for all the valves, heater cathode insulation breakdown could occur in the rectifier and series valves.

The output supplies may be brought out to a four-way terminal block or to a multi-pin output plug or socket. Two ranges of voltage output are available, these being dependent upon the value of R8 which simply determines the maximum bias

| COMPONENTS LIST   |                            |
|---|----------------------------|
| <b>Resistors:</b>   |                            |
| R1 100Ω   | R6 100kΩ                   |
| R2 100Ω   | R7 330kΩ                   |
| R3 10kΩ   | R8 33kΩ for 150-260V range |
| R4 10kΩ   | R9 27kΩ for 190-310V range |
| R5 100kΩ  | R9 33kΩ                    |
| All 10% $\frac{1}{2}$ W carbon  |                            |
| VR1 50kΩ wire-wound potentiometer   |                            |
| <b>Capacitors:</b>  |                            |
| C1 8μF electrolytic 500V  |                            |
| C2 16μF electrolytic 500V   |                            |
| C3 0.1μF paper 350V   |                            |
| C4 0.1μF paper 350V   |                            |
| <b>Valves:</b>  |                            |
| V1 EZ81   |                            |
| V2, V3 807  |                            |
| V4 EF91, Z77 or 6AM6  |                            |
| V5 85A2   |                            |
| <b>Switches:</b>  |                            |
| S1 D.P.S.T. toggle  |                            |
| S2 S.P.S.T. toggle  |                            |
| <b>Miscellaneous:</b>   |                            |
| L1 Smoothing choke 10H 100mA  |                            |
| T1 Mains transformer. Secondaries: 350-0-350V 120mA; 6.3V 3A; 6.3V 3A centre tapped   |                            |
| FS1 Cartridge fuse 150mA  |                            |
| Valveholders: one B9A, two UX5; two B7G with screening cans. Four-way terminal block. Pointer knob. Tagstrips and grommets. |                            |

level obtainable on the grid of V4 by means of VR1. Suitable values for R8 are shown in the components list.


When the unit is complete and the wiring checked, the variable voltage control VR1 can be calibrated.

With the unit switched on and an external load connected, connect a d.c. voltmeter across the positive and negative output points. Turn VR1 to its earthy end (maximum output voltage) and mark the value with marking ink on a suitable scale. If a pointer knob is used, the calibration points can be marked on to the chassis itself. The control is then turned in the opposite direction and the voltage calibration points marked at appropriate intervals, say every ten volts, until the minimum value is reached.

The unit is now ready for use and should prove extremely useful and reliable over a long period while requiring but the minimum of attention. ■

# AN ALL BAND AERIAL TUNER

by F. G. Rayer

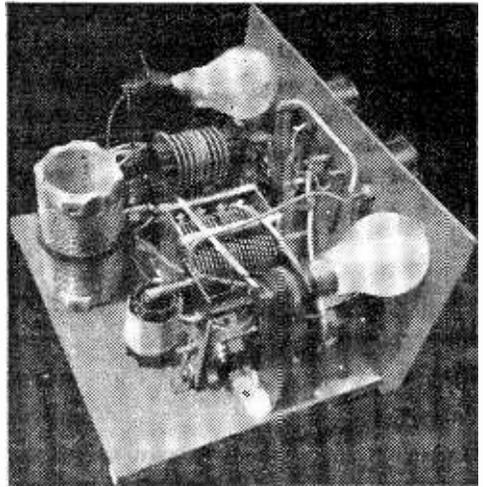

**T**HE simplest form of transmitting aerial capable of being used on all bands from 160 to 10 metres is the end-fed wire, and some type of aerial tuner is practically essential for operating this kind of aerial. The tuning unit described here is suitable for transmitters of up to 150W input on 80—10m, and 10W on 160m.

To facilitate testing without using the aerial, lamp loads are provided, and prove very useful for those checks which can be made with an artificial aerial.

The tuner circuit is shown in Fig. 1, and all types of working are selected with switches. Switch sections S1A and S1B are on a single spindle (2-pole 6-way) and have the following positions:

- (1) Transmitter (or receiver) directly to aerial.
- (2) Link coupling to 10 and 15m coil.
- (3) Link coupling to 20 to 80m coil.
- (4) Link coupling to series tuned 160m coil.
- (5) Transmitter to 75W lamp.
- (6) Transmitter to 15W lamp.

The 15W (LP1) lamp is intended for low power transmitters, and the top band transmitter, where the power limit is 10W. The 75W lamp (LP2) may be replaced by a 40W, 60W or 100W lamp, if preferred, in accordance with the r.f. power expected from the 80—10m transmitter. The lamp loads are suitable for many tests, such as modulation, tuning up exciter and driver, etc. Lamps are not satisfactory when a transmitter is

being keyed, but can, of course, take the output of a c.w. transmitter being tested without keying. Use of the lamps avoids unnecessary interference to other stations.

Switch wafers S2C and S2D are a 2-pole 5-way unit, with the following positions:

- (1) Parallel tuning of 10—15m coil.
- (2) 20m parallel tuned.
- (3) 40m parallel tuned.
- (4) 80m parallel tuned.
- (5) 160m series tuned.


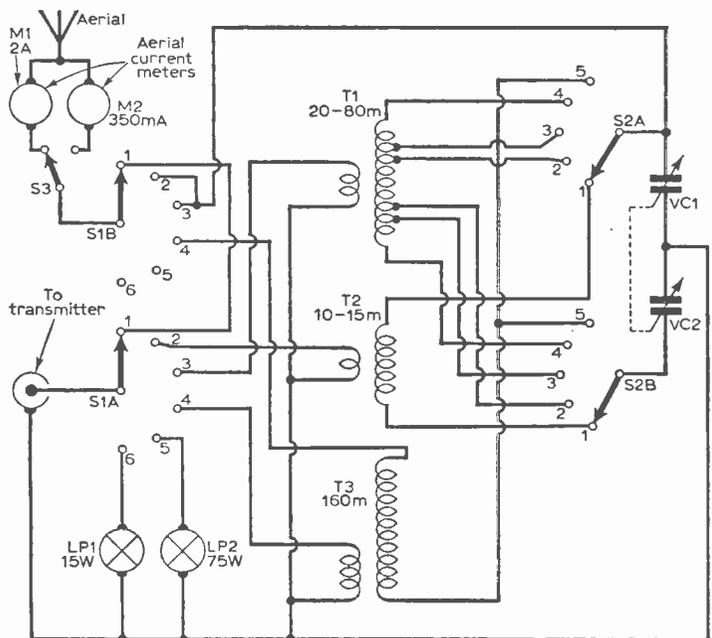
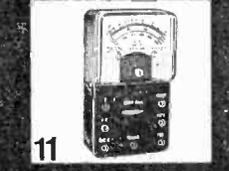
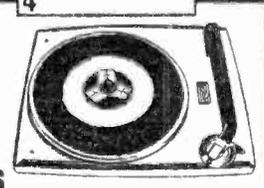


Fig. 1: The circuit of the aerial tuner.

# Just a few of our BARGAINS

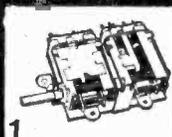

**FREE GIFT OFFER**  
**Electric Soldering Iron**  
 with the  
**Pocket Multi Meter**  
 See item No. 11 for  
 further details

1. **A.M. F.M. PERMEABILITY TUNER FOR ALL TRANSISTOR OPERATION.** Size 2½ x 2½ in. approx. By famous manufacturer. A.M.-I.F. 470 Kc/s. F.M.-I.F. 10.7 Mc/s. A.M. coverage from 1820 Kc/s-825 Kc/s. F.M. coverage 108 Mc/s-88 Mc/s. Circuit diagram 2/6. 2 REE with Tuner. 25/-, 1st, 2nd, 3rd A.M. I.F.'s, 12/8 set. 1st, 2nd, 3rd and 4th P.M. I.F.'s, 12/8 set. V.H.F. Osc. choke, 1/-, A.M. I.F. trap, 1/6, A.F. 114 and A.F. 115, 5/- each. All the above are the RF end of an AM/FM receiver car radio, etc. The above six items purchased together, £2.10.0.

2. **TRANSISTORISED POCKET RADIO** with printed circuit, mini-earpiece, high gain ferrox slab aerial. No aerial or earth required. To build yourself for completely personal listening. 4½ x 3½ x 1½ in. Luxembourg in favourable areas. Only 2½/-. P. & P. 2/6. All parts available separately.

3. **A.C./D.C. POCKET MULTI-METER KIT.** 2in. moving coil meter scale, calibrated in A.C./D.C. volts, ohms and millamps. Voltage range A.C./D.C. 0-50, 0-100, 0-250, 0-500. Millamps 0-10, 0-100. Ohms ranges 0-10,000, 0-100,000, 19/8. P. & P. 2/-. Wiring diagram 1/- free with parts.

4. **SIGNAL GENERATORS:** Cash £7.5.0. P. & P. 6/6. Coverage 100 Kc/s to 100 Mc/s on fundamentals and 100 Mc/s to 200 Mc/s on harmonics. Case 10 x 6½ x 3½ in. Three miniature valves and Metal Rectifier. A.C. mains 200-250v. Internal modulation of 400 c.p.s. to a depth of 30 per cent. Modulated or unmodulated R.F. output continuously variable 100 millivolts. C.W. and mod. switch, variable A.F. output. Magic eyes as output indicator. Accuracy 2 per cent.

5. **SIGNAL GENERATORS:** Cash £5.5.0. P. & P. 6/8. Coverage 120 Kc/s to 84 Mc/s. Case 10 x 6½ x 4½ in. Size of scale 6½ x 3½ in. 2 valves and rectifier. A.C. mains 220-250v. Internal modulation of 400 c.p.s. to a depth of 30 per cent, modulated or unmodulated R.F. output continuously variable 100 millivolts. C.W. and mod. switch variable A.F. output and moving coil output meter. Accuracy ±2 per cent.

6. **STAAR 45 9 v. BATTERY RECORD PLAYER** complete with pick-up and deck. A completely portable player. Head protected by plastic dome with a brush which cleans the stylus as it rises into playing position. 45 r.p.m. Auto on-off switch governed motor, attractive two-tone grey finish, £2.9.6. P. & P. 2/-.

7. **50 MICRO-AMP METER** movement by world famous manufacturer. Size 3 x 2½ in., 25/- plus 1/- P. & P.

8. **ALTITUDE METER.** 270 degree scale. 3in. diameter. Would make ideal car rev.-counter. £1 plus 2/- postage and packing.

9. **CHANNEL TUNER I.F. 16-19 Mc/s.** Continuously tunable from 174-216 Mc/s. Valves required—PCP80 and PCCS4 (in series). Cover BBC and ITA ranges. Also Police, Fire and Taxia, etc. Brand new by famous maker, 10/-, P. & P. 3/-.

10. **B.S.R. MONARCH UA14 WITH FULL-FI HEAD.** 4-speed, plays 10 records, 12in., 10in. or 7in. at 16, 33, 45 or 78 r.p.m. Intermixes 7in., 10in. and 12in. records of the same speed. Has manual play position: colour brown. Dimensions 12½ x 10½ in. Space required above baseboard 4½ in., below baseboard 2½ in. Fitted with Full-FI turnover crystal head, £5.19.6. P. & P. 6/6.

11. **POCKET MULTI-METER.** Size 3½ x 2½ x 1½ in. Meter size 2½ x 1½ in. Sensitivity 1,000 O.P.V. on both A.C. and D.C. A.C. and D.C. volts. 0-15, 0-150, 0-1,000. D.C. current 0-150 mA. Resistance 0-100K Ω. Complete with test leads, battery and full instructions, 35/-, P. & P. 2/6. **FREE GIFT** for limited period only. 30 watt Electric Soldering Iron value 15/- to every purchaser of the pocket multi-meter.

12. **8-watt PUSH-PULL 4 VALVE AMPLIFIER** plus **METAL RECTIFIER.** A.C. mains 200-250 v. Size 10½ x 6½ x 2½ in. 4 valves. For use with all makes and types of pick-up and mike. Negative feed back. Two input, mike and gram, and controls for same. Separate controls for Bass and Treble lift. Response flat, from 40 cycles to 15 kc/s. 2 dB down to 20 kc/s. Output 8 watts at 5 per cent total distortion. Noise level 40 dB down all hum. Output transformer tapped for 3 and 15 ohms speech coils. For use with 8in. or L.P. records, musical instruments such as guitars, etc. Suitable for small halls, £3.19.6. P. & P. 7/6. Crystal mike to suit, 15/-, P. & P. 2/-. 8 x 6in. P.M. Speaker to suit, 12/8. P. & P. 2/-.

**RADIO & T.V. COMPONENTS**  
 [ACTON]  
**LIMITED**

**21b HIGH STREET**  
**ACTON, LONDON, W.3.**

**ALL ENQUIRIES S.A.E.**  
**GOODS NOT DESPATCHED OUTSIDE U.K.**

**SHOP HOURS**  
 9 a.m.—6 p.m.  
 Early Closing  
**WEDNESDAY**

# NEW COMPONENTS SHOP & MAIL ORDER HOUSE

## TRANSISTOR RADIO

**NOW ONLY 39/6** No More To Pay

Highest Quality **READY TO PLAY** pocket transistor radios. Powerful moving coil speaker—3 semi-conductors—2 latest powerful transistors plus semi-conductor ensures clear reception over M.W. Telescope aerial. Only 39/6. Carrying Case, Earpiece and Battery 7/6 extra, plus 3/- & P. C.O.D. 2/6 extra. Money Back Guarantee.



## TAPE RECORDERS

4 Transistor battery portable twin track tape recorders, with loudspeaker. Many extras including microphone, twin track tape, leakproof batteries, personal earphone, carrying strap, etc. Size only 8 x 4 x 3 1/2 in. Fast rewind, record, playback. Simple to operate. **FULLY TESTED. ONLY £5.17.6. NO MORE TO PAY. plus 2/6 P.P. (2/6 c.o.d.)**



## ULTRA-MODERN RECORD PLAYERS

at greatly reduced prices. ALL FAMOUS MAKES

**BSR UA14 4-speed autochanger. £5.19.6**  
**COLLARO C60 4-speed auto. £5.15.0**  
**BSR TU12 Single player £3.12.6**

Beautiful Rexine covered 2-tone cabinets (fits autochange units), 59/6. P. & P. 3/6.



## FULLY TRANSISTORISED 2 WAY INTERCOM

**BABY ALARM** Reduced to only **57/6** no more to pay

An exciting clear toned 2-way intercom which is ideally suited for Office and Home. Many uses as Baby Alarm, Invalid 2-way Phone, Temporary Phone for Garage, Factories, etc. Loud calling signal can be used as alarm. **ONLY 57/6 plus 2/6 P. & P. Full Money Refund Guarantee.**



## METER PRICES SLASHED

Multi range meters with easy read scales. Instructions, leads and batteries included.

**Model EP10K 10,000 o/v. 79/6**  
**20,000 o/v. 97/6**  
**P. & P. 2/6. (C.O.D. 2/6 extra)**



## THE SUPERB HAWK TR-301

Long & medium wavebands fully transistorised. Outstanding little performer—pulls in all stations. Complete with carrying case, ear piece, batteries etc. **Fully Guaranteed—size 3 1/2 x 5 1/2 in. Ivory & Bronze finish. NOW ONLY £8.9.6. P. & P. 2/6 (C.O.D. 2/6 extra).**



**WORLD WIDE MINI-VALVE SHORT WAVE RADIO Only 50/-**  
 Plug in coils—super sensitive circuit—bandspread tuning. Complete set of parts with fully illustrated instructions only 50/-, P. & P. 2/6 extra (C.O.D. 2/6 extra). All parts available separately.

## READY TO PLAY

**SIX TRANSISTOR RADIOS**

Portable six transistor radios in presentation boxes. Powerful loudspeaker reception brings in HOME, LIGHT, LUXEMBOURG & CONTINENTAL STATIONS. Beautifully designed. Finger tip controls. Quality carrying case, personal earpiece, battery, etc. **FULLY TESTED. 75/- NO MORE TO PAY plus 2/6 p. & p. (C.O.D. 2/6 extra).**



## NEW - MODERN

High Performance Telephone Amplifier. The strong clear tone makes telephone conversations a pleasure and leaves both hands free for writing etc. **MODEL 424 65/- plus 2/6 p. & p. (C.O.D. 2/6 extra.) MODEL 425 75/- plus 2/6 p. & p. (C.O.D. 2/6 extra).**



## FABULOUS ELECTRICAL ORGAN

A genuine musical instrument with a remarkable performance. Notes are produced in same way as full sized organ with individually tuned reeds. Measures only 13 x 5 1/2 x 4 1/2 in. Complete with batteries and tutorial booklet for learners. Volume is ample for large rooms. **NOW ONLY 69/6 plus 2/6 p. & p. (C.O.D. 2/6 extra).**



# HEROS RADIO

(Dept. P.W.4)  
 19 GARDNER STREET  
 BRIGHTON 1, SUSSEX

BY RETURN SERVICE

## VALVES SAME DAY SERVICE NEW! TESTED! GUARANTEED!

**SETS** 1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL94 ... Set of 4 for 15/-  
 DAF96, DF96, DK96, DL96 ... 4 for 23/6

|            |             |            |           |             |             |
|------------|-------------|------------|-----------|-------------|-------------|
| 1A7GT 8/-  | 6U4GT 9/6   | DAC32 8/3  | ECL80 6/3 | PCC85 6/9   | U37 17/-    |
| 1D5 6/6    | 6V8GT 3/9   | DAF91 8/9  | ECL12 7/- | PCC89 8/-   | U47 8/6     |
| 1BE2T 6/3  | 6V6GT 6/6   | DAF96 6/-  | FTL36 9/- | PCF80 5/9   | U50 4/6     |
| 1NS5GT 8/- | 6X4 3/9     | DCC90 6/9  | EP1 3/9   | PCF82 6/9   | U73 3/9     |
| 1R5 4/9    | 6X5GT 5/6   | DF33 8/6   | EF41 6/6  | PCF84 8/-   | U191 11/-   |
| 1S5 3/9    | 7B7 8/-     | DF91 2/6   | EF42 4/3  | PCF86 8/-   | U281 9/6    |
| 1T4 2/6    | 7C5 7/9     | DF96 6/-   | EF80 5/9  | PCF906 14/- | U282 12/9   |
| 3A5 8/9    | 7C8 7/6     | DH76 3/6   | EF85 5/-  | PCL82 7/3   | U281 9/-    |
| 5B4 5/6    | 7HT 15/9    | DH77 4/9   | EZ40 5/6  | PCL83 9/-   | U301 12/6   |
| 3S4 4/9    | 7S7 25/-    | DK32 8/6   | EF89 4/9  | PCL84 6/6   | U801 17/-   |
| 3V4 4/6    | 7Y4 5/-     | DK40 15/6  | EF91 3/3  | PCL85 8/6   | UABC80 5/9  |
| 5U4G 4/6   | 10C2 12/3   | DK91 4/9   | EF92 2/6  | PEN4DD      | UAF42 8/-   |
| 5Y3GT 5/-  | 10F9 10/-   | DK92 6/9   | EL33 7/6  | PENA4 19/6  | UBC41 8/3   |
| 5Z4C 7/-   | 12A7S 4/9   | DK96 6/6   | EL41 7/3  | PEN36C 8/6  | UDC81 7/3   |
| 6A8G 5/6   | 12A7T 3/9   | DL33 7/9   | EL42 7/6  | PEN38C 8/6  | UBF80 6/6   |
| 6AL6 2/-   | 12AU7 4/9   | DL35 6/9   | EL84 4/9  | PEN383 10/6 | UBF89 6/9   |
| 6AQ5 6/-   | 12AX7 4/9   | DL92 4/9   | EM34 7/11 | PL36 8/9    | UBL21 9/9   |
| 6AT6 4/9   | 12K7GT 4/3  | DL94 5/6   | EM80 7/9  | PL38 16/6   | UC92 6/6    |
| 6E26 6/-   | 12K9GT 3/9  | DL96 6/3   | EM81 6/9  | PL81 7/6    | UCC84 8/9   |
| 6BE6 5/3   | 12Q7GT 4/3  | EABC90 5/3 | EM84 8/6  | PL82 5/6    | UCB85 6/9   |
| 6BG6G 12/6 | 12Z3 8/6    | EAF42 8/6  | EM87 8/9  | PL83 5/6    | UCF80 8/6   |
| 6BH6 5/-   | 19BG6G 13/6 | EB91 2/-   | EY51 6/-  | PL84 5/9    | UCH42 7/6   |
| 6B76 5/6   | 20F2 11/-   | EBC33 5/9  | EY84 9/-  | PX4 9/-     | UCHA1 6/6   |
| 6CD3G 28/6 | 20P4 14/9   | EBC41 7/3  | EY86 5/6  | PX25 7/9    | UCL82 8/6   |
| 6E5 5/6    | 20P5 14/9   | EBC91 6/9  | EZ40 5/6  | PY32 5/9    | UCL83 9/-   |
| 6F13 4/9   | 25L6GT 5/9  | EBF80 5/6  | EZ41 7/6  | PY33 10/-   | UF4 7/3     |
| 6F14 9/-   | 25U4GT 10/6 | EBF93 7/9  | EZ80 4/6  | PY80 5/3    | UF42 4/9    |
| 6K7G 1/6   | 30FL1 9/6   | EBF89 6/9  | EZ81 4/6  | PY81 5/9    | UF89 6/3    |
| 6K7GT 4/-  | 30PL15 8/6  | EBL21 8/3  | GZ32 8/6  | PY82 4/9    | UL41 7/-    |
| 6K9C 4/3   | 30P1 9/-    | ECC40 7/6  | KT33 5/6  | PY83 5/9    | UL44 19/6   |
| 6K8GT 7/8  | 30P13 3/6   | ECC81 3/9  | KT36 14/- | PY88 7/9    | UC85 4/3    |
| 6L8G 5/9   | 30PL14 12/3 | ECC82 4/9  | KT81 7/6  | R17 15/-    | UL84 8/3    |
| 6LD20 5/3  | 35A5 14/-   | ECC83 7/3  | KT83 3/9  | TDD4 7/9    | UY7 7/6     |
| 6P25 7/-   | 35L6GT 7/9  | ECC84 6/6  | KTW61 4/9 | TR21C 10/6  | UY21 8/6    |
| 6P26 9/6   | 3Z4GT 4/11  | ECC85 6/3  | MU14 5/-  | TY23 14/-   | UY41 4/9    |
| 6Q7G 4/9   | A36 8/6     | ECC86 6/3  | MX40 3/6  | TY86F 11/3  | UY85 4/3    |
| 6Q7GT 7/8  | B36 4/6     | ECF82 6/3  | N18 5/6   | U22 6/-     | UY1321 15/- |
| 6R7GT 9/6  | CCH35 12/9  | ECH35 6/-  | PC95 9/-  | U24 15/-    | W76 3/6     |
| 6S12GT 5/6 | CL33 9/6    | ECH42 8/3  | PC97 7/6  | U25 8/6     | W77 2/6     |
| 6SNTGT 3/9 | CY1 12/6    | ECH81 6/-  | PCC84 6/- | U26 8/6     | X63 5/6     |

## HOW TO BUILD TINY ELECTRONIC CIRCUITS

This work is intended to bring "miniaturized" electronics home to the amateur, experimenter and service technician and to take the mystery out of "making it smaller". In short it is a volume on the "how to do it" of electronic miniaturization without elaborate equipment.

By M. Moses.

- 30/- Postage 1/-
- TAPE RECORDING YEAR BOOK**, 1964. 7/6. Postage 9d.
- AMATEUR RADIO CALL BOOK**, by R.S.G.B., 1964. 4/6. Postage 6d.
- FREQUENCY DIVIDER ORGANS FOR THE CONSTRUCTOR**, by A. Douglas. 25/-, Postage 1/-.
- MODERN TAPE RECORDING AND HI-FI**, by K. Peters. 30/-, Postage 1/-.
- ELECTRONIC ORGAN HANDBOOK**, by H. E. Anderson. 40/-, Postage 1/-.
- TRANSISTOR CIRCUITS FOR RADIO CONTROLLED Models**, Bernard. 7/6. Postage 6d.
- RADIO VALVE DATA**, 7th Ed. Compiled by "WW". 6/-, Postage 10d.
- COMPLETE CATALOGUE** 1/-.

## THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST of British and American Technical Books

19-21 PRAED STREET LONDON, W.2

Phone: PADdington 4185  
 Open 6 days 9-6 p.m.

## READERS RADIO

24 COLBERG PLACE, STAMFORD HILL LONDON N.16

STA. 4587

Post 6d. per valve extra.  
 Any Parcel Insured Against Damage in Transit 6d. extra.  
 Any C.O.D. Parcel 4/3 extra.

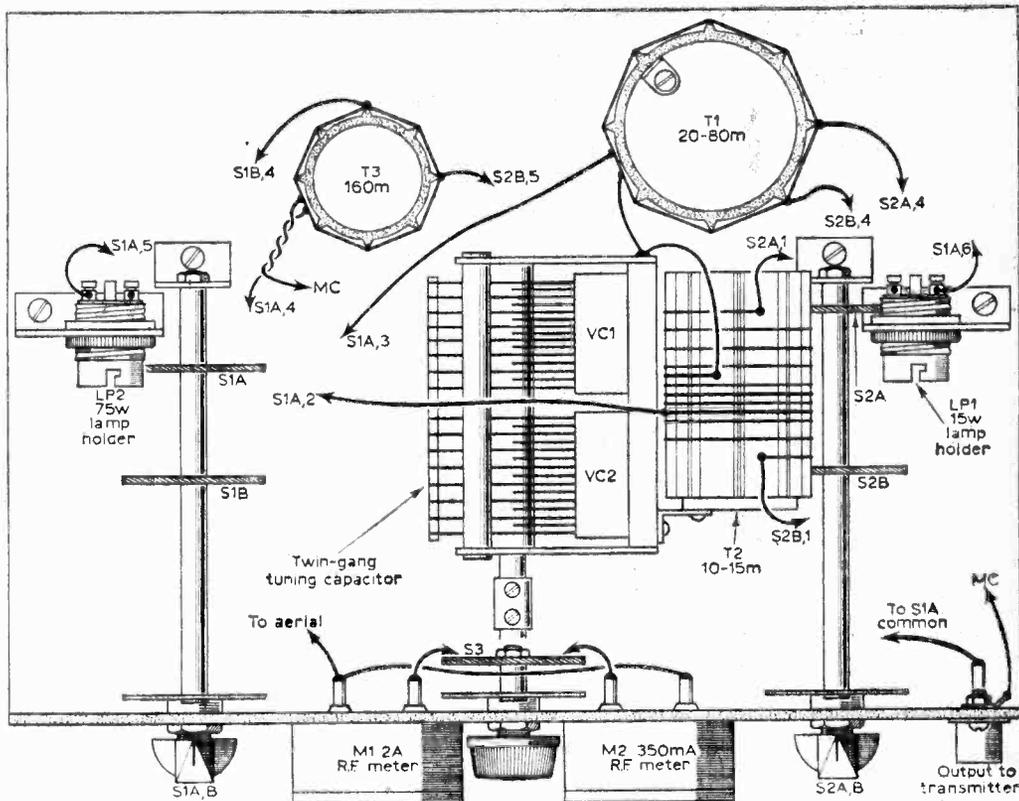


Fig. 2: Above-chassis layout of components.

The 10—15m coil (T2) is separate from the 20—80m coil in order that suitable link windings can be provided, as it is not easy to use a link giving suitable coupling from 10—80m on a single coil. As the aerial was a half-wave on 80, parallel tuning is in order from 10—80m. VC1 and VC2 are sections of a 2-gang 150pF wide-spaced capacitor.

As the aerial length is a quarter-wave on 160m, series tuning is necessary on this band. Position 5 on switch S2 places VC1 and VC2 in parallel, to obtain enough capacity, the capacitor being at the bottom end of the 160m coil (T3), in the usual way.

Switch S3 is a single pole 2-way unit, selecting 2A (M1) and 350mA (M2) r.f. meters, to show aerial current. The purpose of these meters is to give immediate visual indication that the transmitter is radiating its accustomed signal. With a given aerial, any increase in aerial current will correspond to an increase in the radiated signal, so the readings are useful when adjusting drive or other conditions. The use of either meter allows both low and high power transmitters to be connected to the tuner, and also covers those circumstances when the aerial impedance is relatively low on some bands.

The switch S1 is used to select 10—15m, 20—80m,

and 160m links, as appropriate. Position 1 on this switch gives straight through working, which is useful when checking over the bands with the receiver, or listening on frequencies not covered by the coils. With some transmitters and aerials, the transmitter may be loaded directly by the aerial, but with many aerials this is impossible, and will in any case result in more harmonic radiation.

**Layout and Coils**

Fig. 2 shows the layout adopted, which provides quite short leads in the tuned circuits. The switches are large, heavy duty types, unwanted contacts being ignored. Each switch is supported by a bracket at the back, to increase rigidity.

The 2-gang capacitor has a short extension spindle. A hardboard front panel is used, to avoid the need for extra insulation for the meters. A coaxial socket on the panel receives a plug, a few feet of 75Ω coaxial cable being used between transmitter and tuner.

The 10—15m coil (T2) is wound on an 8-ribbed former, 1 1/4 in. in diameter across the ribs. Eight turns of 14s.w.g. wire are used, spaced to occupy 1 1/2 in. The link is two turns of well insulated wire, wound over the centre of the eight turns. The coil

is supported by a paxolin strip held by a bracket to the gang capacitor.

The 20-80m coil (T1) is 2½ in. in diameter, notched to take about 8 turns per inch (Eddystone 2½ in. x 5 in. frequentite). The winding is 26 turns of 20s.w.g. wire. Tappings C3 and D3 are six turns from each end. Tappings C2 and D2 are four turns from tappings C3 and D3. The link is three turns of well insulated wire. This coil is fixed vertically by means of a bracket screwed to the baseboard.

aerial, transmitter, or capacity of VC1 and VC2.

Strips of paxolin 6 in. long and 1½ in. wide are cut to take ordinary pendant holders. Each strip is held vertically by a bracket, so that the bulbs are pressed against 1½ in. holes in the panel.

Terminals are fitted for Earth and Aerial, the latter terminal being supported on an insulated strip. These leads pass out of the back of the tuner cabinet. The complete cabinet was 12 in. wide, 7½ in. high, and 9 in. deep, inside measurements, but dimensions can easily be changed to suit any fairly large case or box available.


Notes on Working

An aerial of about 138ft., this being a single uncut wire, forming both top and down-lead, will be satisfactory. All parts of the aerial should be as far from earthed objects as possible. This, and similar lengths, will take parallel tuning on all bands except 160m. Here, series tuning is used.

If 160m is not required, the 160m coil can be omitted. If space is not available for 138ft. then half this length will give parallel tuning on 40-10m, with series tuning on 80m.

The tuner is in use for reception as well as transmission (except for switch position 1) and this will increase receiver signal strength where the receiver has a 75Ω or similar input. If the tuner is to be omitted for reception, the receiver/transmitter aerial relay or switch is removed from the transmitter side of the tuner, to the aerial side.

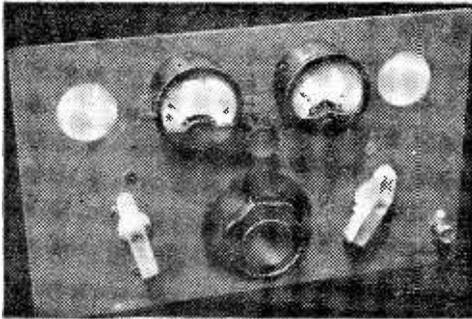If an aerial giving some intermediate impedance is used, this may need tapping down the coils, for correct loading. If so, the switch S2 will need an extra wafer, to avoid moving clips by hand.



The finished aerial tuner.

For 160m (T3) the coil is 1½ in. in diameter, and has 48 turns, side by side, of 24s.w.g. wire. The link is overwound at the "earthed" end of the coil, and consists of eight turns.

Other coils can be satisfactory, and the number of turns can be adjusted as required, to suit the


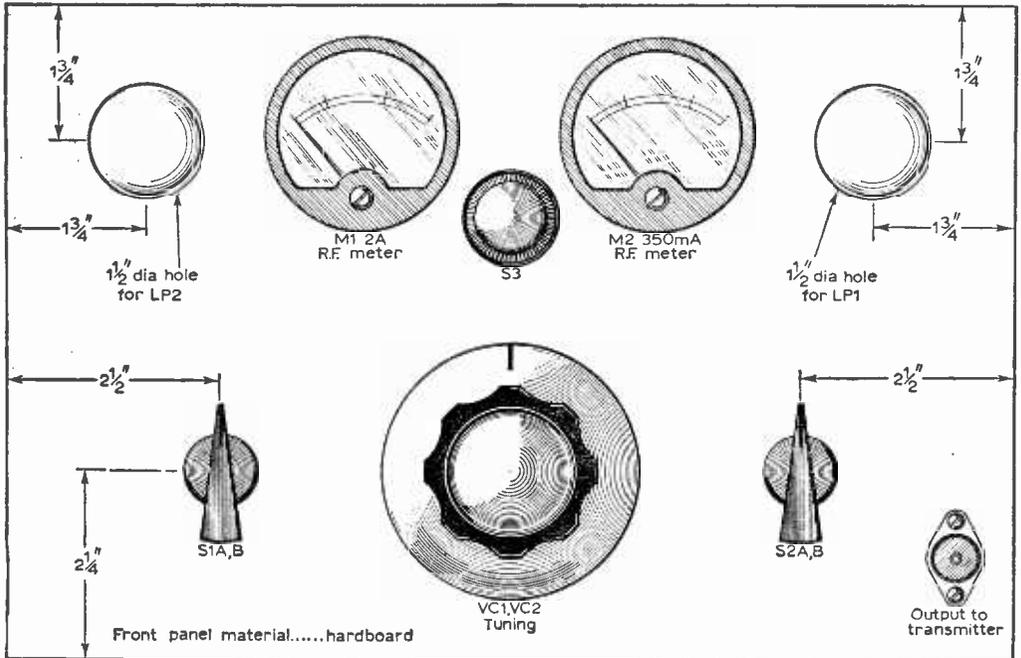


Fig. 3: Layout of controls and meters on the front panel.
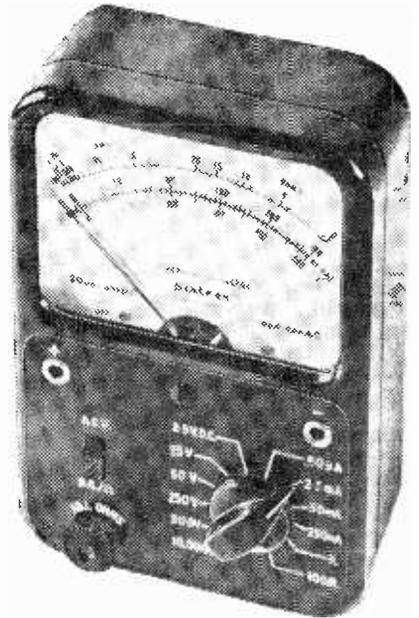
# Audio Testing with the "PRACTICAL WIRELESS" "Sixteen" Multirange METER



WITH the aid of a good meter, practically all the tests for "goodness" can be made on domestic equipment. True, there are a number of specialised measurements, and those involving frequency change, phase comparison, etc., where an oscilloscope is the obvious instrument to use. But, even audio equipment, with its need for stringent frequency response limitations and low hum and distortion figures, can be dealt with, using the high resistance a.c.-d.c. meter, such as the P.W. "Sixteen", and sufficient patient application.

The following notes are practical workshop methods of carrying out operating tests on audio equipment, from the humble record player to the hi-fi, stereo tape recorder. Some of the points are common to most domestic equipment, and will receive only brief mention. Reference should be made to the previous article (February PRACTICAL WIRELESS) and to the "Typical Tests" given on the back of the PRACTICAL WIRELESS "Sixteen" blue-print.

### The Record Player

The simplest type of record player consists of a one-valve amplifier, with the valve heater fed from either a mains dropping resistor, a motor winding, or from a tapping on a transformer. H.T. may be provided by a small, contact-cooled metal rectifier, either half-wave connected through a surge limiting resistor from the mains, or full-wave (or bridge) connected from a transformer winding. A typical circuit of the former type is shown in Fig. 1, with test points arrowed.

First test is for a.c. to both motor and amplifier,

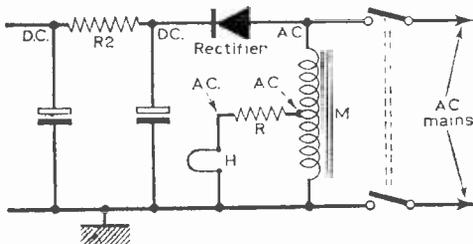


Fig. 1: Power supply circuit of a simple record-player, showing test points.

### IMPORTANT NOTE CONCERNING BATTERIES

Attention is drawn to an error in the battery references on the blueprint of the P.W. "Sixteen" Multirange Meter (included in the January issue).

The theoretical circuit (Fig. 1) shows the batteries correctly: B1 15V battery (B121); B2 1.5V cell (U10).

The circuit references B1 and B2 should be transposed in the Components List, also in Fig. 3, upper portion only relating to S1C tag 9 and tag 10.

The last paragraph but two on page 813 should be amended in a similar manner.

proving the double-pole switch.

Next, the voltage at the tapping point of the motor windings should be checked, and, if a limiting resistor is included, as in Fig. 1, the voltage at the "hot" side of the valve heater. The difference between these last two readings enables us to compute the valve heater current also by using Ohm's Law—having first made a resistance check of the limiting resistor, of course.

From this point, we go to the h.t. from the rectifier, and thence to the h.t. applied to the system. Again, the difference between these two readings gives the voltage drop across R2, and enables us to calculate the h.t. current. Thus, by making two or three quick tests with the multimeter, disturbing nothing in the circuit, we have a pretty good idea of the "health" of the record player. From there fault-finding procedure is a matter of simple elimination.

### Audio Amplifiers

First tests on audio amplifiers are again: h.t. and I.t. voltages.

In general, rectifier circuits will be full-wave with the anodes fed from outer ends of a centre-

tapped secondary winding of the mains transformer. Voltages used on many audio amplifiers are considerably higher than on the average radio or television receiver: a 500-0-500V secondary is by no means unusual. Care must be exercised when taking these measurements, and the highest voltage range must be employed, with one side of the meter returned to chassis, or centre-tap. The basic circuit may be as shown in Fig. 6 of the blueprint published in the January 1964 issue of PRACTICAL WIRELESS.

Quite wide variations may be found, however, and voltage readings can be misleading unless the exact circuit is known. For example, one method of hum reduction is as shown in Fig. 2.

Here, the centre-tap of the h.t. secondary of the mains transformer is not returned directly to chassis, but is applied, via a variable resistor VR to the heaters of pre-amplifier valves, or valves in the early stages of the amplifier. The h.t. current then passes through the heaters and VR is adjusted to provide the correct energising current. The centre-tap is thus negative to chassis. This negative voltage may also be used as a convenient source of bias. The electrolytic capacitor C will invariably be found and acts as a bypass to the low frequencies and as a bias filter component.

When measuring a.c. applied to the rectifier anodes of this type of circuit, one side of the meter should be taken to the centre-tap, rather than to the chassis. A further reading of the d.c. between chassis and centre-tap then gives an indication of the h.t. current being drawn.

**Hum Cancelling Arrangements**  
The circuit of Fig. 2 was used on a number of earlier amplifiers. Modern equipment often employs a different method of heater hum reduction, by energising the heaters from a low-voltage secondary winding of the mains transformer, (a.c.), and applying a slightly positive potential, either from a "bleeder" across the h.t. or from the cathode of an output stage. The purpose of this device is to attract random electrons back to the heater, now at a slightly higher potential than the cathode. Allowance for this positive d.c. voltage must be made when taking a.c. heater voltage measurements on circuits of this nature.

A more usual, hum-reducing circuit is the balanced heater line. A potentiometer, usually consisting of a wire-wound variable resistor with slider connected to chassis, is connected across the heater supply, acting as a "humdinger". Fig. 3, which is an illustration of the power pack of a well-known amplifier, demonstrates this method.

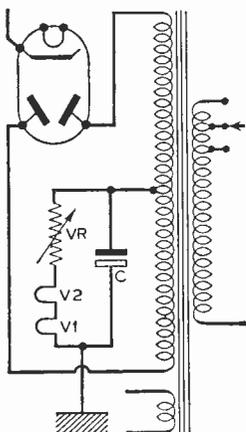


Fig. 2: Full-wave rectifier input to audio amplifier, with hum-reducing heater connection.

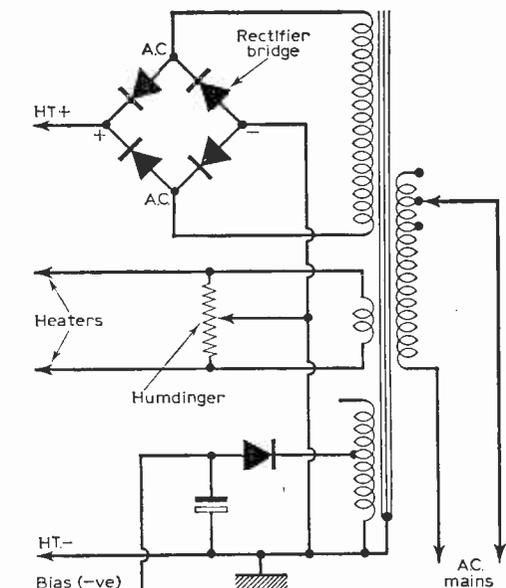


Fig. 3: Amplifier power supply circuit with bridge-connected full-wave rectification, balanced heater supply and separate bias source.

Also notable in this circuit is the use of a bridge-connected metal rectifier for h.t. supply and the rectified negative bias supply from a further secondary tapping.

Hum is a very real problem in audio amplifier design, as most constructors are well aware. One way of checking the filter circuits with the aid of a meter is to use an a.c. meter with an isolating capacitor, as in Fig. 4. The "hot" side is applied to points A, B, and C in turn, with no signal and under maximum signal conditions. A considerable reduction in readings should be noted from A toward C.

**D.C. Balance of Output Stages**

Perhaps the most stringent condition as regards use of the meter apply at the output end of any audio amplifier. Whilst it is important that earlier stages should be in order to eliminate spurious hum pick-up, noise and some distortion, it is in the output section of the amplifier that the greatest care is needed with trouble-shooting. Push-pull output stages of conventional design are especially

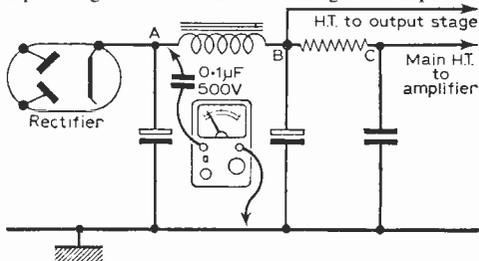


Fig. 4: Rough check for hum level in smoothing circuits.

critical: it is essential that they are exactly balanced, with the current in each half-section of the output transformer primary equal and opposite.

The bias of each valve is adjustable over a limited range by a balance control, so that from the d.c. aspect, this circuit may be considered as a balanced bridge. This is clearly seen in Fig. 5, where it will also be noted that each valve has a separate cathode resistor.

Adjustment of the balance control should enable the d.c. currents through the two valves to be equalised. This can be checked by connecting the meter across the transformer primary, as shown, and adjusting for zero reading. It may be necessary to reverse the meter when making this adjustment, to ensure that the correct zero reading is obtained,

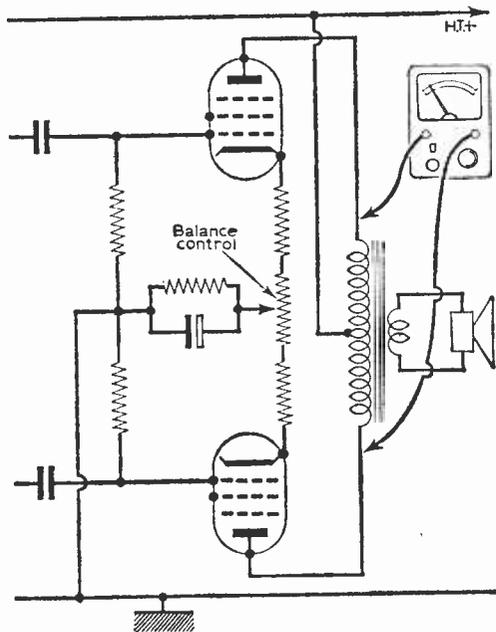


Fig. 5: Push-pull output stage balance adjustment.

If the meter indicates a low standing voltage, this may be caused by a low emission valve, and can be proved by transposing the two valves, when the standing voltage should reverse polarity. If it stays the same, suspect the cathode bias resistor or one of the coupling capacitors from the previous stage. A coupling capacitor with poor insulation resistance will tend to neutralise the negative bias and increase current through the particular valve it feeds. This condition seldom remains static, the usual result being a steady deterioration, increase in distortion and eventual over-running of the valve, which often shows signs of distress by glowing red.

**Loudspeaker Phasing**

Troubles at the output are usually the result of mis-matching of loudspeakers to the transformer,

especially where more than one loudspeaker is used.

A lack of bass will often indicate that speakers have been connected out of phase. This can be checked by first disconnecting the speakers, then applying a d.c. voltage from a low impedance source (a torch battery is sufficient). Note whether the loudspeaker cone pulls in when the connection is made—do not maintain the connection—and mark the polarity. Connect each speaker so that in parallel the polarities match, and in series the positive of one speaker is connected to the negative of the other. The meter comes in handy when a convenient low d.c. has to be identified.

Output power can be checked by first substituting the loudspeaker with a wirewound resistor of equivalent resistance to the given a.c. impedance of the speaker, then measuring the a.c. voltage developed across this resistor with a constant level signal input.

A series of readings taken in this way enables one to make a rough check on the overall response of the amplifier. The curve is produced by plotting audio output against frequency. Accurate readings are not so important here as the need for a constant amplitude input, which must be chosen to avoid overloading the amplifier at certain fre-

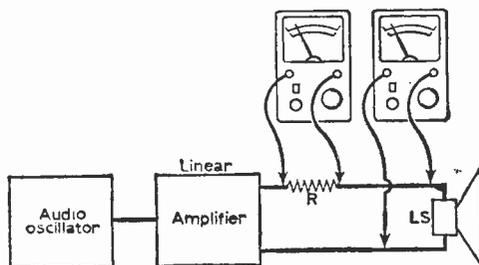


Fig. 6: Loudspeaker impedance check. Low readings only.

quencies. A.C. power is calculated by dividing voltage obtained by resistance.


It is sometimes necessary to determine the impedance curve of a loudspeaker. While this is generally done with the aid of an impedance bridge, it is nevertheless possible, with the aid of our multimeter, to make practical tests.

If an audio oscillator is available, a hook-up such as illustrated in Fig. 6 enables us to take voltage and current readings at various frequencies, and plot a curve. A word or two of warning: the curve produced may look like an Alpine range; this is not at all unusual, as the loudspeaker response and the loading of the enclosure together make for a smooth output.

**Tape Recorders**

Tape recorders testing requires attention to many of the above points, plus the measurement of oscillator voltages and currents. During recording, an h.f. bias voltage of between 45 and 60kc/s is applied to the recording head, the signal being superimposed on this. Correct level of bias is essential for good recordings, and it must be of sufficient amplitude to overcome inherent noise and free from distortion.

—continued on page 1085

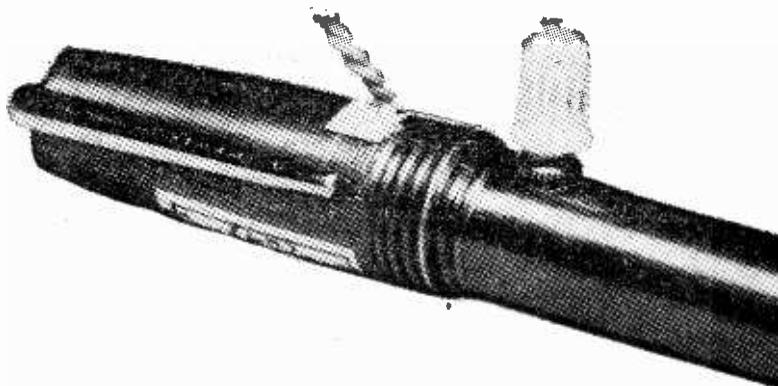

# SIGNAL TRACER-POCKET SIGNAL TRACER-POCKET

**T**HIS signal tracer comprises basically a germanium diode detector circuit feeding into a two-stage transistor amplifier which ultimately feeds its output into a miniature high impedance earpiece. The unit is suitable for tracing r.f., i.f. and a.f. signals but care should be taken when using it not to overload the diode.

All components are mounted on a small paxolin chassis which itself is fitted inside the casing of a small penlight torch casing of the type which can be obtained from Woolworths for 1s. 10d.

This torch casing has a shaped plastic nose cone to shield the bulb and this allows the streamlining of the probe tip to be made really professional, so producing an entirely useful piece of apparatus which has a very commercial appearance.

The power supply for the signal tracer is a leak-proof 1.5V "Ever Ready" type U7 dry cell which is fitted inside the torch casing, so making the unit entirely self contained except for the earpiece, which, of course, of necessity is outside the casing anyway.

The tracer can be clipped into the service man's pocket just like a fountain pen and so is quite portable and takes up very little room.

The resistors and capacitors are of the sub-miniature type which in these days of continued miniaturisation are quite easily come by. C1, however, should be of the paper tubular type and should have a very high working voltage so it can protect the diode if the probe tip accidentally touches a very high voltage point when tracing in mains operated equipment. In the author's model C1 is 2.7kV d.c. working. The transistors used are also sub-miniature and are in fact smaller in size than the resistors or capacitors and are of American manufacture. However, Mullard are now producing a sub-miniature version of the "OC44"—this version being the "OC44M"—and these can be used and it is quite likely that no alteration in the value of the resistors or capacitors will be necessary. Normal size surplus transistors, r.f. or a.f., may also be employed, but if so it is important that the length of their body (not leads) is not longer than about 8mm, otherwise they will impede the fitting of the chassis into the casing when this unit is completed.

The circuit of the signal tracer is given in Fig. 1.

## THE MAIN CHASSIS

The main chassis upon which most of the components of the signal tracer are mounted is made from a small rectangular piece of paxolin  $\frac{1}{8}$ in. thick, 1 $\frac{1}{2}$ in. long and  $\frac{1}{8}$ in. wide.

Such a small piece of paxolin will probably be found in the average constructor's "junk" box and because of this thinness may be trimmed to size with scissors. This chassis is shown in Fig. 2. As can be seen, two small pieces are cut out of the ends of the chassis. The piece out of the left-hand end is  $\frac{1}{2}$ in. wide and  $\frac{2}{10}$ in. deep and the piece cut out of the right-hand end is  $\frac{1}{2}$ in. wide but only  $\frac{1}{8}$ in. deep.

Also, as can be seen, a number of holes are pricked into the chassis. The specific positions of these holes are indicated in Fig. 2. Their positions should first be accurately marked on the paxolin chassis with a needle or pin and then pierced, using a red-hot sewing needle. This process is very quickly done since the paxolin is so thin.

The positive and negative supply lines (+ve and -ve rails) should now be attached to the chassis. These are made of thin gauge bare copper wire and are fixed to the chassis via the holes bored at each end of it in the manner shown in Fig. 3. The negative supply rail should be mounted above the chassis and the positive rail mounted below the chassis. These rails are fixed by passing their ends through their respective holes at the end of the

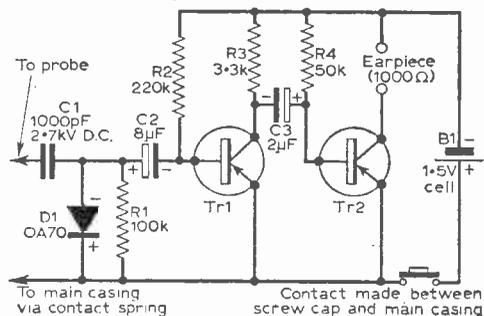


Fig. 1: The circuit of the tracer.



# SIGNAL TRACER-POCKET SIGNAL TRACER-POCKET SI

By R. W. KNEESHAW

chassis as shown in Fig. 3. These ends are then doubled over and passed through the adjacent hole, then snipped off, bent over and soldered to keep the rails permanently fixed in place.

Next the contact spring that carries the connection from the positive battery terminal from the main torch casing to the positive rail should be mounted in place. This contact spring is made from a piece of brass strip such as the brass strip terminals found on the flat 4½V torch batteries. This spring may be cut from such a thin piece of brass strip 1½ in. long and  $\frac{3}{32}$  in. wide and curved to the shape portrayed in Fig. 4.

The bent-over part of the strip should fix over the end of the chassis in the  $\frac{1}{4}$  in. x  $\frac{1}{16}$  in. cutaway piece. This is shown in this drawing. The part where the contact spring is fixed to the chassis should then be lightly squeezed with a pair of pliers, so making a very firm attachment.

The spring contact must be electrically connected to the positive rail and this is done by means of a little piece of brass strip of length  $\frac{1}{8}$  in. and width  $\frac{1}{32}$  in.

This piece of strip bridges the gap under the chassis between the fixed end of the spring contact and the positive rail and is soldered to these points as shown in Fig. 5. The soldering in place of this brass bridging strip enhances the rigidity of the fixing of the spring contact to the chassis.

## WIRING UP THE COMPONENTS

The components of the signal tracer are now to be soldered correctly in place on the chassis.

The position of the components is clearly shown in Fig. 6. Apart from C1 and C2 all components are mounted above the chassis. C1 is mounted in the  $\frac{1}{4}$  in. x 2/10 in. cutaway piece at the end of the chassis as shown. C2 is mounted under the chassis and should be of the sub-miniature electrolytic type. One end of C2 should be soldered to the under-chassis junction of C1. R1 and the diode D1 (indicated "X" in Fig. 6) and its other end should be soldered to the under-chassis connection between the base of Tr1 and R2.

The other outward end of C1 is snipped off quite short and bent over the first two or three

turns of a small spring (about  $\frac{1}{4}$  in. long and 1/10 in. diameter), thus fixing the spring tightly to it. The mounting of this spring is shown in Fig. 6. This spring should be quite gentle in pressure and its function is to complete the connection of the signal input from the probe tip to C1.

Small plastic sleeving should be slipped over the transistor leads to prevent them shorting together. When soldering, heat sinks should be used to conduct the heat of the iron away from the transistors. These heat sinks may be in the form of long pieces of copper wire, twisted round each lead, or may be effected by gripping the transistor leads with a pair of pliers or tweezers when soldering them.


When the soldering is completed on the chassis a small piece of transparent adhesive tape should be stuck over the end of the contact spring where it is attached to the chassis. This is to prevent the spring from shorting on to the earphone socket which is to be connected up later. Another piece of transparent adhesive tape should also be stuck over the diode, so preventing its ends from touching the inside of the torch casing when the chassis is inserted into the casing.

## THE EARPHONE SOCKET

The miniature earphone socket must now be soldered to the chassis. Two of the tags on this socket should be shorted together and lead "A" attached to them. These two tags are depicted in Fig. 8 (it is important the right pair are strapped together), this diagram showing clearly how the earphone socket is connected up to the main chassis. The other soldering tag on this socket must have lead "B" connected to it. Both leads "A" and "B" are about  $\frac{1}{2}$  in. long and lead "A" is connected to the negative rail above the chassis and lead "B" connected to the collector wire of Tr2 below the chassis.

Part of the switch contact arm on the earpiece socket should be snipped off, the portion to be cut off being ascertained by reference to Fig. 7.

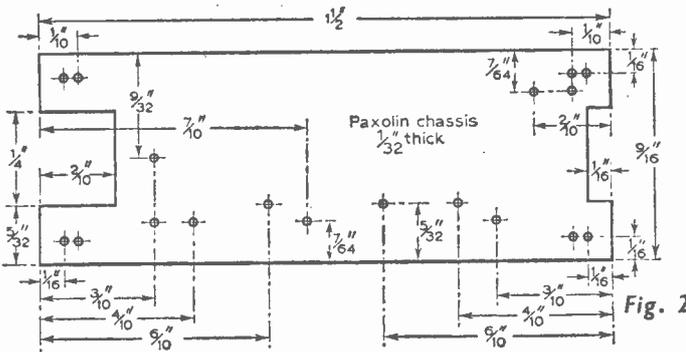A small ebonite collar is slipped over the screwed link of the earphone socket together with a celluloid or mica washer (external diameter  $\frac{1}{4}$  in. and internal diameter  $\frac{3}{32}$  in.). The small ebonite



**COMPONENTS LIST**

**Resistors:**  
 R1 100kΩ      R3 3.3kΩ  
 R2 220kΩ      R4 50kΩ

**Capacitors:**  
 C1 1,000pF paper 2,700kv  
 C2 8μF electrolytic  
 C3 2μF electrolytic

**Semiconductors:**  
 D1 OA70  
 Tr1, 2 OC44M

**Battery:**  
 B1 1.5V cell U7

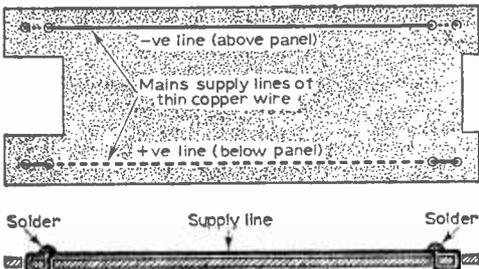


Fig. 3

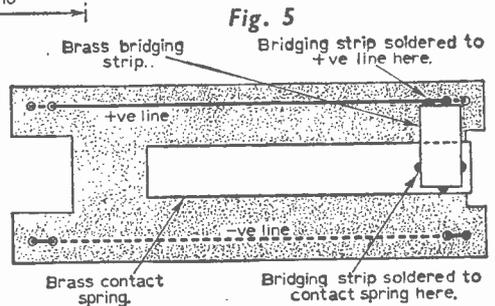


Fig. 5



Fig. 4

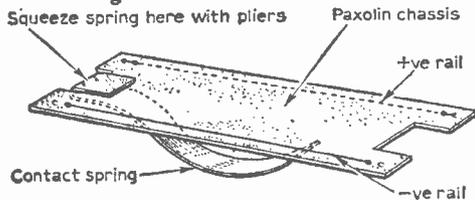


Fig. 6

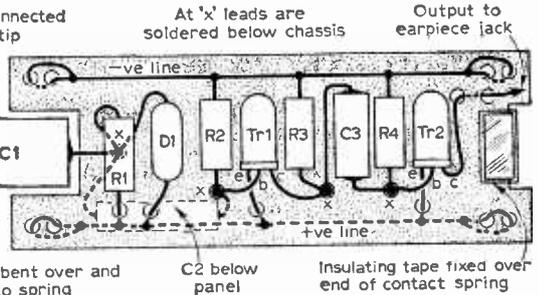


Fig. 7


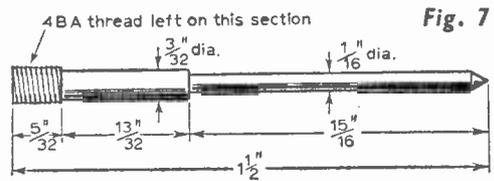


Fig. 8: A sectional view of the completed instrument.

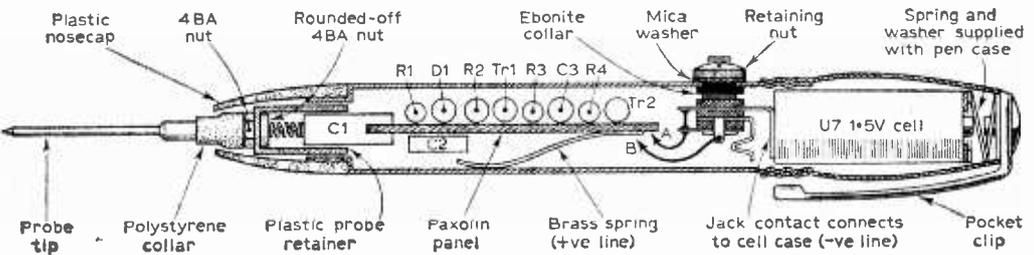

collar was taken from an old headphone jack plug (normal size, not miniature). If an old jack plug isn't handy such an insulating collar will probably be found in some old piece of radio or electrical apparatus such as switches, banana plugs or sockets. A suitable washer can be cut from an old photographic negative.

The only modifications to the penlight torch casing are: (i) The spring (and the washer attached to it) which is found inside the casing when it is bought must be transferred into the screw cap (the spring entering before the washer); (ii) a hole  $\frac{3}{16}$  in. in diameter must be bored in the casing exactly  $\frac{1}{2}$  in. from the end of the casing that screws into the screw cap. It is important that the position of this hole is correct, otherwise the positive pole of the battery will not make contact with the rivet in the end of the screw cap when it is screwed into the casing or it may be found impossible to screw the cap on properly.

The main chassis may now be placed inside the lower half of the torch casing shown. However, before this is done the wiring of components on the main chassis should be checked against the circuit diagram and any errors corrected. Also the inside of the casing should be lightly scraped with a round file to ensure good contact between it and the contact spring attached to the main chassis.

To fit the chassis inside the casing unscrew the retaining nut from the earpiece socket and also take off the celluloid washer, but leave the ebonite collar on, and then push the chassis gently into the casing (C) entering first), making sure that the contact spring enters unimpeded. When the chassis is properly inside C1 should be slightly protruding out of the other end of the casing (the end into which the torch bulb was to be screwed) and the screwed link of the earpiece socket should be located right beneath the hole drilled in the casing. With a pair of tweezers or long-nosed pliers grip this socket and gently push the screwed link through the hole in the casing until the ebonite collar fits into that hole. Then place the celluloid washer over the screwed link (now protruding through the side of the casing and screw the retaining nut tightly on to it. The chassis is then firmly fixed inside the casing. The battery can now be placed inside the casing and the screw cap screwed on. The negative zinc casing of the battery should be resting on the switch contact arm of the earpiece socket. Fig. 7 shows the chassis, battery and socket correctly positioned inside the penlight torch casing.

### THE PROBE TIP

The probe tip is made from a  $1\frac{1}{2}$  in. length of 4B.A. brass screwed rod. It was fashioned by filing it whilst it was being turned in the chuck of a hand drill (the latter was clamped in a vice and so was used as a crude type of lathe). A power drill, of course, would shorten this job immensely but, even so, since the screwed rod is of brass and is fairly soft the job only takes about half an hour using a hand drill.

The rod is fitted down to the dimensions shown in Fig. 7.

As can be seen  $\frac{5}{16}$  in. of length of the rod are untouched and that for  $\frac{13}{16}$  in. of length the rod is

turned down to  $\frac{3}{16}$  in. diameter (i.e. until the screw thread just disappears), and for the remaining  $\frac{1}{16}$  in. of length the rod is filed down to  $\frac{1}{16}$  in. diameter. The thin end should be filed to a fine point.

From an old battery plug or aerial plug retain the plastic portion. In the author's case this was an h.t. plug from a very old battery portable receiver. However, any such insulating piece that can be found in the junk box may be used but it must be of the correct shape, i.e. cylindrical, hollow inside and closed at one end. It must be  $\frac{3}{16}$  in. in length and have an external diameter of  $\frac{3}{16}$  in. Any piece of the correct shape could be sawn and filed to these dimensions and the hole can be drilled in the centre of the closed end. This hole should be just big enough to pass the screwed end of the brass probe.

The inside of this insulating piece should be reamed out with a round file until it just completely fits over the capacitor C1 which is protruding from one end of the main chassis.

Now round off the corners of a flat 4B.A. nut until it just snugly fits right inside the insulating piece. The thread of the brass probe is then passed through the small hole in the closed end of this insulating piece and screwed into the rounded-off nut inside. A locking 4B.A. nut is screwed into the probe tip outside the insulating piece, so rigidly fixing this brass probe tip to it.

From an old polystyrene ink cartridge (of the type used in many makes of ballpoint pen) cut off the portion  $\frac{1}{4}$  in. from the smaller diameter end. The "stepped" portion so cut off should then be slipped over the brass probe. (These ink cartridges are easily obtainable from any stationery store and cost only 4d.)

The finished probe assembly is now attached to the torch casing as follows: Unscrew the plastic nose cone of the penlight casing, exposing the end of C1 and the small spring attached to it. Slip the insulating piece of the probe assembly over C1 such that it slides inside the penlight casing. The plastic nose cone of the torch is then slipped over the probe tip and screwed on to the torch casing. Fig. 8 shows the probe assembly correctly fixed inside the penlight casing.

The input signal to the tracer is applied across the probe tip and the torch casing (positive battery line) and so a lead must be made to connect the torch casing to the earth line of the piece of apparatus being investigated by the signal tracer. This lead should be of thin plastic-covered flex, about 18 in. long, and should have a crocodile clip attached at either end. The crocodile clips used by the author were the miniature type, which seemed more fitting for such a miniature piece of apparatus. One end of this lead is connected to the casing by clipping it on to the pocket clip fixed to the screw cap of the torch and, of course, the other end of the lead should be attached to the earth line of the piece of equipment being tested.

### USING THE TRACER

The signal tracer is now complete and it may be switched on by screwing the screw cap of the torch right on gently as far as it will go. It is thus switched off by unscrewing this cap about half a turn or so in the opposite direction.

Insert the earphone and switch the tracer unit on. A slight click should be heard in the earphone when the probe tip is touched with a metal object.

If no click is heard in the earphone then it is probably due to either—

(i) The positive battery terminal is not connecting properly to the rivet at the inside end of the screw cap when the cap is fully screwed on;

(ii) The contact spring fixed to chassis not making good electrical connection with the inside of the torch casing (This is remedied by withdrawing chassis and scraping inside of casing some more with a round file.);

(iii) The probe tip is not making good contact with the spring attached to the end of C1.

These points should thus be checked in turn and any poor contact remedied where found.

It is unlikely that the circuit wiring is at fault, since this should have been thoroughly checked before the chassis was initially inserted into the casing.

The signal tracer may be further tested by connecting its casing to the positive battery line of a transistor receiver, which is switched on and tuned to a station, and touching the probe tip on to the diode detector of that set and finding whether a signal is heard or not. In fact a signal should be heard at the base or collector leads of all transistors in the set except perhaps at the base of the mixer (where, of course, the incoming signal has received no amplification).

### INSULATING THE CASE

Although originally this device was intended to be used for tracing signals and thus faults in transistorised equipment it can, of course, be equally well used in mains operated valve receivers. However, it should be remembered that since the casing of the tracer must be connected to the chassis of the receiver this casing may be live and the user may suffer a serious shock. This risk, however, can be alleviated by binding the tracer casing with insulating tape before using it (first switching the tracer on, of course), after which it should be perfectly safe to handle.

After the servicing has been completed the binding of the insulation tape can be taken off and the tracer switched off.

The high d.c. working voltage of C1, of course, protects the diode if the probe tip accidentally touches a high voltage point when servicing mains operated receivers.

### MULTI LOCATION

This signal tracer was primarily designed to determine how far a signal is going through a faulty receiver and thus to ascertain the location of the fault. To do this the receiver dial pointer is placed to a position where a strong signal comes in (such as the Light or Home programmes). Then connect the casing of the tracer to the positive battery line of the receiver (if transistorised receiver) or to the earth line (if a valve-operated receiver). Then, starting from the

aerial end of the set, place the probe tip first on the base and then on the collector (if a transistorised set) or control grid and then anode (if a valve receiver) of each stage in turn, working forward towards the loudspeaker until one point is reached where no signal can be obtained. One then knows that the fault lies between this point and the point just previously tested. Further probing at positions between these two points should narrow the fault down until its exact location or nature is realised.

Low-emission valves may be found using this instrument, since the signal heard at their control grid should be quite strong and yet very weak or non-existent at their anode.

Transistors that for some reason have suddenly lost their gain, however, are a different matter, since a transistor, being a completely "solid state" device, does afford a good electrical connection between base and collector, and although the transistor is faulty in this way an equally strong signal sometimes may be louder at the base of and base.

With the transistor receivers the signal heard in the earpiece of the tracer doesn't necessarily increase progressively in strength as one moves successively from base to collector, stage by stage throughout the set. This will probably be due to mismatching between the transistor and the probe assembly at certain test points and as a result the signal sometimes may be louder at the base of some transistors than at its collector, and this may prove misleading when trying to detect a transistor which is not amplifying properly for some unknown reason. However, for locating open circuits in printed circuitry or resistors and capacitors in transistor receivers the device is very useful indeed.

### TRACER AND INJECTOR USED TOGETHER

The author, of course, constructed this signal tracer for use with the "Pocket Signal Injector" which was covered in a constructional article in the July, 1963, edition of PRACTICAL WIRELESS. This being so, servicing of faulty receivers is made even easier by employing the two devices together.

The signal injector is switched on and its signal injected into the aerial socket of the receiver which is faulty. This is done by placing its probe tip into the aerial socket of the receiver (if that receiver requires an external aerial) or placing the probe tip of the injector near to the ferrite rod (if the receiver is portable and has its own internal aerial). In either case a signal is successfully injected into the set and may be followed through the receiver, using the signal tracer as previously explained, until the spot where the injected signal fails to pass through is found.

The two units being constructed in identical penlight torch containers make a very useful "pen and pencil" type of set for the service man and, of course, take up very little room. The author has also added to this pair a torch of similar type, since such a pocket torch is often very useful when trying to ascertain where leads or components are connected to in the more inaccessible parts of a radio receiver chassis, especially in the more miniature receivers found today.

# Modifications to the Local Station F.M. Receiver

By J. G. Ransome

## ALTERING THE COVERAGE OF THIS P.W. DESIGN

SINCE the publication of constructional details for the "Local Station F.M. Receiver" (*Practical Wireless*, July 1963), several enquiries have been received concerning conversion details for using this receiver on frequencies other than those encompassed by the original design. In particular, conversion details have been requested for the 70Mc/s, 144Mc/s and 190Mc/s bands—the latter being required for the sound part of Continental and Irish television f.m. signals. This article, therefore, is presented to give details of suitable conversions to the original circuit in order that the above bands may be received.

### 70Mc/s Band

The 70Mc/s band is extensively used by commercial stations, (taxis, control of mobile services, etc) and by certain mobile amateurs. The modification necessary to receive 70Mc/s transmissions is extremely simple and merely involves alteration to the tuned circuit around L1.

In the original circuit the oscillator ran at about 80Mc/s, this beating with the incoming signal at 90Mc/s to produce the i.f. at 10.7Mc/s. Thus if we have an r.f. signal at 70Mc/s the local oscillator being at 80 Mc/s will again produce an i.f. of 10.7Mc/s. Not only is it convenient to leave the oscillator unmodified but it is preferable from the point of view of possible interference, since if the oscillator were modified to run at 60Mc/s i.e.

below the signal frequency, there may be interference to television signals in the 60Mc/s band (Band I, channel 4).

There are two ways of modifying the input circuit for 70 Mc/s. We can either reduce the resonant frequency of the circuit by padding L1 with a capacitor or by rewinding L1 to the appropriate inductance. Of the alternatives the latter is more elegant from the theoretical standpoint, but the former is more convenient and works quite well.

The converted circuit is shown in Fig. 1 this shows the padding capacitor Cp as being switched—which is useful in that it makes the receiver tunable over both the 70Mc/s and 90 Mc/s bands. If the set is to be used only on 70Mc/s then, of course, the switch is omitted. The set now tunes the 70Mc/s band, L1 being tuned for optimum results.

If the alternative of rewinding L1 is preferred, then L1 is wound with 6½ turns of 20s.w.g. wire wound on a ½in. diameter iron dust cored former, each turn being spaced from the next by a distance equal to the diameter of the wire. The aerial tap is

TABLE I (Coil details)

All coils are wound on 0.3in. dia. iron dust cored Aladdin formers with 22 s.w.g. enamelled wire, each turn being spaced from the next by a distance equal to the diameter of the wire.

|    | 144 Mc/s   | 190 Mc/s   |
|----|--|--|
| L4 | 5½ turns<br>Tap 2 turns<br>from earthy end.        | 4½ turns<br>Tap 2 turns<br>from earthy end.        |
| L5 | 4 turns.   | 4 turns.   |
| L6 | 6 turns.<br>Tap 2½ turns from<br>high tension end. | 5 turns.<br>Tap 2½ turns from<br>high tension end. |

three turns from the earthy end of the coil. L1 is peaked for maximum signal at 70Mc/s.

Either of the modifications will ensure satisfactory reception of 70Mc/s signals.

### 144Mc/s and 190Mc/s Bands

For those readers who are well within the primary service area of transmitters operating on 144Mc/s or 190Mc/s the conversion is almost as easy as that for 70Mc/s just described.

All that is required is that L1 and L2 are rewound to the specifications shown in Table I; in all other respects the original circuit remains the same. Unfortunately the modified circuit as it stands is not very sensitive. The great difficulty here is that as we increase the frequency there is a tendency for the r.f. signal to decrease at the grid of V1A owing to losses due to stray capacitive

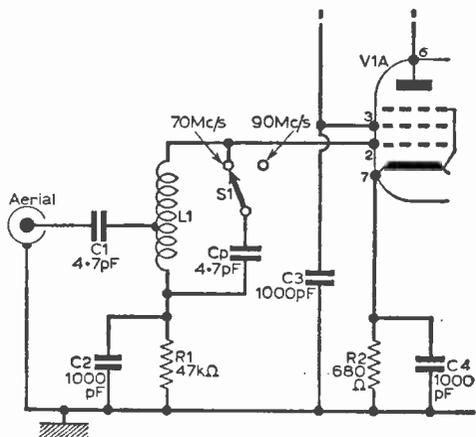


Fig. 1: The modified circuitry of V1 (see Fig. 1, page 220 of the July 1963 issue).

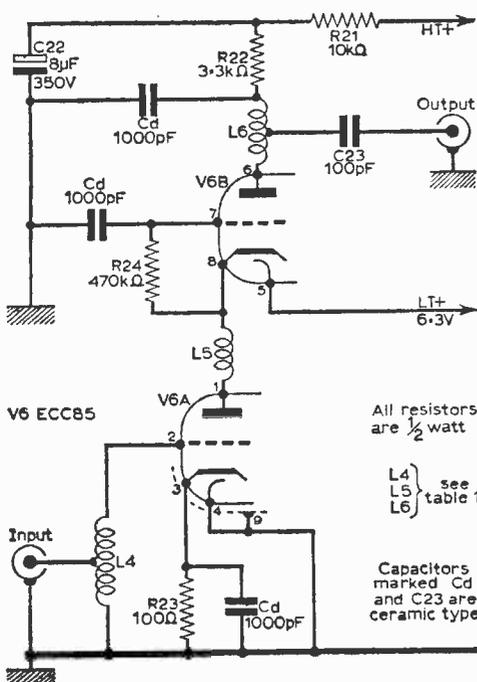


Fig. 2: The circuit of the pre-amplifier for 144Mc/s and 190Mc/s.

and other effects. It is therefore necessary to fit an r.f. amplifier.

An r.f. amplifier is to be preferred to an extra i.f. amplifier (which would be much more convenient) under these conditions for reasons of noise. Most of the noise (noticeable as a general hiss) is generated in the mixer and r.f. stage, (V1A in the original). Now the more we amplify after this first stage the more we increase the noise level in the a.f. signal.

However, if we increase the signal to the grid of V1A the effect of the noise is reduced. Thus we need to have an r.f. amplifier in areas where the signal strength is anything less than strong. It is suggested that the coils L1 and L2 be modified first and the set checked for reception quality and sensitivity, and if these are unsatisfactory the pre-amplifier should be constructed.

**Pre-amplifier**

It was found the insufficient room could be made on the original chassis to accommodate the

**COMPONENTS LIST**

**Resistors:**

- R21 10kΩ
- R22 3.3kΩ
- All 1/2W 10% carbon
- R23 100Ω
- R24 470kΩ

**Capacitors:**

- C22 8µF electrolytic 350V
- C23 100pF ceramic
- Cd 1,000pF ceramic

**Coils:**

- L4, 5, 6 see Table 1

**Valve:**

- V6 ECC85

r.f. amplifier and so it was decided to construct the amplifier as a separate unit.

In the prototype the chassis used was that of a redundant television turret tuner which had been purchased in a brand new condition (less coils) for 2/6d., and since these are quite readily available at many surplus shops the writer would commend to the reader the use of such a chassis as they contain most (if not all) of the components required, together with suitable coil formers.

The circuit of the pre-amplifier is shown in Fig. 2 (mod) and suitable coil-winding details are given in Table 1.

There should be little difficulty in constructing the r.f. amplifier for those who have successfully undertaken the building of the original receiver. As before, the wiring must be kept as short as

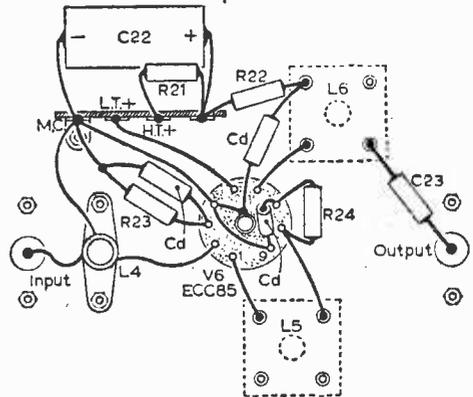


Fig. 3: The pre-amplifier wiring.

possible and an additional desirable feature would be the use of ceramic capacitors for the decoupling capacitors Cd as the lowest possible inductance is required in this part of the circuit.

**Aligning the Circuit**


The peaking of the circuit is extremely simple as L4 and L5 are fairly broadly tuned and so are peaked last. The procedure is as follows:

Switch on the main set and pre-amplifier, and connect the output of the amplifier to the main receiver input by means of a length of coaxial cable. If a suitable signal generator is available inject a 145Mc/s (or 190Mc/s as appropriate) signal at the grid of V6A (pin 2) and adjust L6 for maximum output and then likewise adjust L5. It may then be necessary to readjust L6 again for maximum response. The signal generator is then removed from V6A grid and transferred to the aerial input at the tap on L4 and this is adjusted for maximum response. The aerial may now be connected and L4 readjusted for maximum output.

If no signal generator is available the unit must be aligned on the aerial. A suitable aerial is connected to the set and the coils adjusted in the same manner as above, using a signal which is as strong as possible.

These then are the modifications which may be made to the original set and since they have all been tried and tested the constructor may undertake them with every confidence.

# INCREASE YOUR KNOWLEDGE

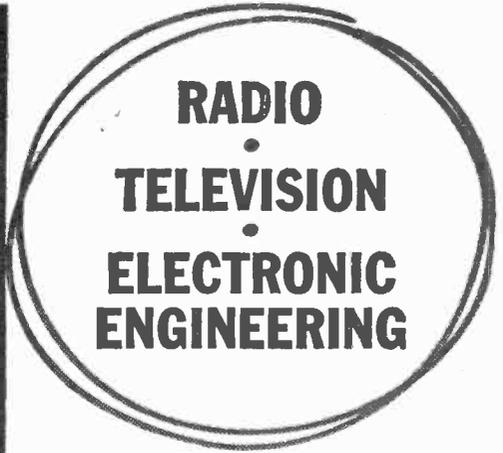

MEMBER OF THE ASSOCIATION  
OF BRITISH CORRESPONDENCE COLLEGES

### CHOOSE THE RIGHT COURSE FROM:

RADIO AND TELEVISION ENGINEERING, INDUSTRIAL TELEVISION, RADIO AND TELEVISION SERVICING, ELECTRONICS, COMPUTERS AND PROGRAMMING, ELECTRONIC TECHNICIANS, SERVOMECHANISMS, TELEMETRY, COLOUR TV, INSTRUMENTATION, AND PRINCIPLES OF AUTOMATION.

### ALSO EXAMINATION COURSES FOR:

A.M.Brit.I.R.E.; City and Guilds Telecom. Technicians, C. & G. Radio and T.V. Servicing (R.T.E.B.), and P.M.G.'s Certificates. C. & G. Radio Amateurs' Certificate.

### LEARN AS YOU BUILD

Practical Radio Courses: Gain a sound knowledge of Radio as you build YOUR OWN 5-valve superhet Receiver and Portable Transistor, Signal Generator and High Quality Multitester. At the end of the course you have invaluable practical equipment and a fund of personal knowledge and skill. ICS Practical Radio Courses open a new world to the keen amateur.

### THERE IS AN ICS COURSE FOR YOU


Whether you need a basic grounding, tuition to complete your technical qualifications, or further specialised knowledge, ICS can help you with a course individually adapted to your requirements.

There is a place for you among the fully-trained men. They are the highly paid men—the men of the future. If you want to get to the top, or to succeed in your own business, put your technical training in our experienced hands.

ICS Courses are written in clear, simple and direct language, fully illustrated and specially edited to facilitate individual home study. You will learn in the comfort of your own home—at your own speed. The unique ICS teaching method embodies the teacher in the text; it combines expert practical experience with clearly explained theoretical training. Let ICS help you to develop your ambitions and ensure a successful future. Invest in your own capabilities.
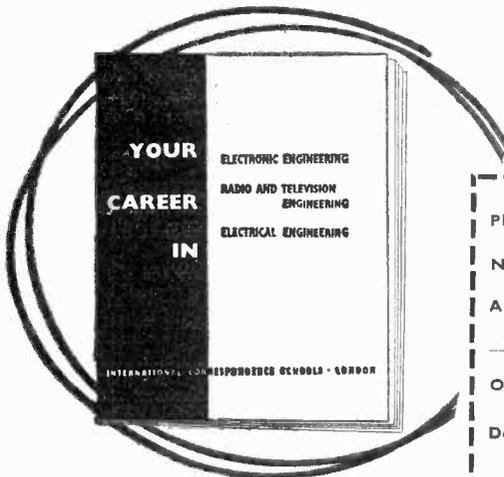
### FILL IN AND POST THIS COUPON TODAY

You will receive the FREE ICS Prospectus listing the examinations and ICS technical course in radio, television and electronics. PLUS details of over 150 specialised subjects.



PLEASE SEND FREE BOOK ON \_\_\_\_\_

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

OCCUPATION \_\_\_\_\_ AGE \_\_\_\_\_

INTERNATIONAL CORRESPONDENCE SCHOOLS  
Dept. 170, INTERTEX HOUSE, PARKGATE RD, London SW11



# WOW AND FLUTTER

by H. W. Hellyer

Tape recorder and gramophone faults likely to cause these audio imperfections in the reproduction.

WHILE the pundits pontificate and fail to agree on a definition for the term "high-fidelity", it is as well to remember that there are other terms, in as general use, that still remain vague and inconclusive. But whereas every audiophile has his personal reservation about the "highness of fi", the terms of our title are very real, measurable, and can be quite disturbing.

Time is the essence of audio matters and rhythm the most vital factor. A sound with no rhythm we dismiss as noise. The physiologists tell us our lives are based on the fundamental rhythms of nature. Regularity is the yardstick by which we judge the audible word. Pitch and intensity can vary by fairly large amounts before our imperfect ear protests. Under ideal conditions, the healthy person can detect a difference of 1% in pitch variation of a signal rich in harmonics, but a pure tone slightly higher than mid-range that is varied only one tenth of this and at a regular rate of variation is immediately apparent.

Intensity enters here, for a note seems to decrease in pitch as it gets louder. This effect is very marked at frequencies below 100c/s.

Since the pitch of the note we hear reproduced by a gramophone or tape recorder depends on the speed at which the disc revolves or the tape passes the head gap, it is obvious that variations in speed are extremely important, and must be avoided. But the dependence upon rhythm makes our ear very intolerant not only of plain changes of pitch but also of the short-term variations caused by cyclic irregularities of the mechanism.

### Distinction Between Wow and Flutter

At low periods of change (as distinct from low frequencies) the effect becomes most disturbing, and the brain registers the sensation of discord. Thus, a pure tone of, say, 1,000 cycles, which varies only 0.04% in pitch regularly every five seconds gives rise to a feeling of greater discomfort than a signal varying twice the

amount but at twice the speed of variation; while a signal varying in pitch and intensity with rapidity allows a tolerance of quite wide limits before the ear takes note.

These relatively low changes of pitch, up to about ten times a second, are called "wow", and variations at a higher rate are known as "flutter". There is no hard and fast division: some German engineers regard cyclic variations up to 20 cycles as wow; some American engineers use the term flutter for all cyclic variations.

The effect of wow, or cyclic variations below 10 cycles, is to impose a tremolo effect upon the signal. This is especially noticeable on a sustained note, such as the playing of a piano or organ. Flutter has the effect of roughening the tone, and is often mistaken for other forms of distortion, and consequently difficult to diagnose and trace. Because of its nature, it may be less regular, thus increasing the difficulty. What sounds like an overloaded amplifier can often be the result of a flutter effect between 40 and 100 cycles which frequency modulates the signal and gives what really amounts to intermodulation distortion.

### Acceptable Standards

There is no standard determining the acceptable amounts of wow and flutter. Indeed British

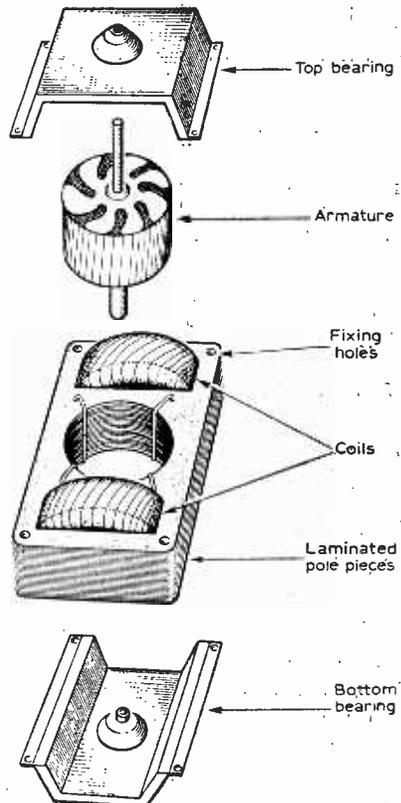


Fig. 1: The construction of an induction motor.

Standard 1988:1953, which deals with these frequency and speed variations, states that it is "not possible to stipulate . . . standards. As a rough indication, 0.05% r.m.s. is considered good, while 0.5% is bad". (This should not be confused with the speed tolerance laid down in BS1568:1960, which recommends a  $\pm 2\%$  maximum speed tolerance for domestic tape recorders. As a matter of interest, very few modern machines are as poor as this, and professional machines are often within  $\pm 0.5\%$  of the nominal speed.)

Wow is caused by irregular rotation of drive mechanisms. This may originate at the motor, belt or idler, flywheel (or turntable, in the case of the gramophone), capstan or pressure wheel. The rhythm of the wow is often a clue to its origin.

### Possible Motor Defects

The modern induction motor is considerably more efficient than its forerunners and, when correctly loaded, runs at a constant speed determined by the mains frequency. The type widely used for turntable drive of gramophone mechanisms, and some of the simpler tape recorders, is the 4-pole shaded-pole variety, as shown in the "exploded view" of Fig. 1. Here, the armature is a solid unit, the laminations form a rigid structure and the bearings are "self-oiling".

This last property is the result of research into metals and plastics which has made possible the use of materials with oil-retaining properties, yet with sufficient hardness to resist the normal wear

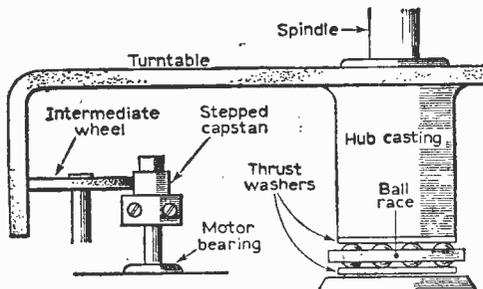


Fig. 2: The usual method of turntable drive for a gramophone.

of a spindle rotating at speeds up to 3,000 r.p.m. when loaded. Nevertheless, excessive heating will cause a drying-out of bearings and, in extreme cases, could result in motor seizure. So the first check must be the correct lubrication of bearings. One or two drops of light oil are generally sufficient at these points—and care must be taken to avoid excess oil being thrown off, in case this surplus should contaminate the rubber of idler wheels or belts. The final state will be worse than the original fault if over-enthusiastic oiling takes place.

Next, ensure that ventilation is sufficient to maintain the motor at a normal and constant temperature. If overheating has occurred, check the insulation of the fine lead-out wires of the field coils, especially where these pass through the coil cheeks. Where plastic coil formers are employed, see that heat has not distorted these. Check also the lamination clamps—loose laminations are a

source of obscure noises, hum and heat. See that the blades of the fan are not distorted, that the bearings are correctly centred and there is no side-thrust. Some bearing clamps use rivets, which tend to work loose. Where this has happened, it may be advisable to drill out the rivets, replacing them with bolts, shakeproof washers and nuts.

Bent motor spindles are a possible source of wow, the frequency being in the order of 20-25c/s with a loaded, synchronous motor. Check by observing the free rotation of the uncoupled motor under a bright, directional light. Little can be done to rectify this fault, apart from motor replacement, unfortunately.

### The Drive System

The usual arrangement for turntable drive is as shown in Fig. 2, where the motor has a stepped capstan fixed to its spindle by compression spring

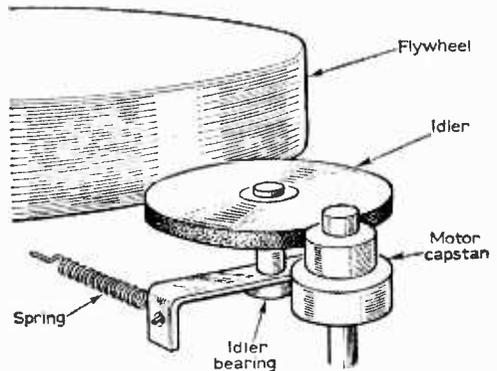


Fig. 3: Providing the drive for a tape recorder flywheel.


or grub-screws. A slipping capstan caused by loose screws is another possible source of irregularity, as is a vertical displacement which results in the rubber intermediate (idler) wheel being driven by the correct diameter step but rubbing on the next largest step of the capstan. The idler itself may become distorted, and here it must be stated that by the most prevalent reason for this fault is a mechanism being left in engagement when switched off. (A similar stricture applies to the idlers and pressure rollers of tape decks.)

Incorrect engagement of the idler with the turntable rim can be caused by the spring that operates the idler arm becoming weak or distorted, and by the arm itself binding, usually as a result of grit between sliding members. The remedy is cleaning and lubrication where appropriate with a medium grease. But take care at this point, also, for some mechanisms use graphite grease only, and any other medium will accentuate the binding.

### Correct Seating of Turntable

The turntable itself must sit correctly on its bearing, and the thrust washers should always be replaced when turntables are removed for service. Bearings, especially the brass ring of the ball-race, should be kept clean, and a close watch should be kept for burrs or grit in the hub cavity. Ensure that the hub is not binding on spindle housing, and

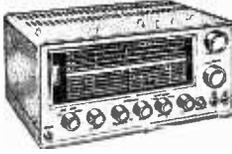
**HE-30 SUPER AMATEUR COMMUNICATION RECEIVER**



4 bands covering 550Kc/s to 30Mc/s continuous. Operation 200/240 volt A.C. Special features include: Easy to read illuminated slide rule dial—Built in Q multiplier—Aerial trimmer—calibrated electrical bandspread on amateur bands—0-100 logging scale—Noise limiter—AVC/MVC selector—stable oscillator and B.F.O. for clear CW and SSB reception—built in edgewise "S" meter. Output for phones or STD speaker. Supplied brand new and guaranteed with manual. £42 carriage paid. S.A.E. for full details.

**CV2193/89D.**  
**DOUBLE-BEAM C.R.T.**  
As used in Cossor 1035 scope etc. Brand new and boxed. 59/6 each. P. & P. 4/6.

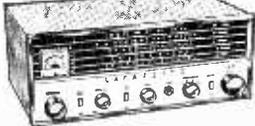**HE-40 DE LUXE 4-BAND COMMUNICATION RECEIVER**



Frequency coverage 550Kc/s to 30 Mc/s continuous. Operation 220/240 volt A.C. The perfect receiver for short wave listening. Special features include: Slide rule bandspread—0-100 logging scale—improved selectivity—built in "S" meter—A.V.C.—Noise limiter—B.F.O.—Phone jack built in 5in. speaker—tone control—standby switch—supplied with three aerials, ferrite loop for broadcast band, adjustable 58in. whip for short wave and wire aerial. Smartly styled durable metal cabinet. Supplied brand new and guaranteed with manual. £24.15.0 carriage paid. S.A.E. for full details.

**NATIONAL H.R.O. RECEIVER**



**SENIOR MODEL.** Supplied complete with full set of nine coils covering 50Kc/s to 30Mc/s. Each receiver thoroughly checked before despatch and available as follows:

Table Model. Good used cond ... £18.18.0  
Rack Model. As new cond. ... £22.18.0  
Rack Model. Good used cond. £18.18.0  
N.B.—Rack model is identical to table model with extended front panel to fit a 19in. rack. Carriage £1 extra.

200/250 volt A.C. power supplied for all the above receivers, also sold separately 59/6, carr. 5/-. S.A.E. for details.

**LAFAYETTE BRAND RECORDING TAPES**

First grade quality American tapes. Brand new and guaranteed. Discounts for quantities.

- 5in. 600ft. std. plastic. . . . 8/6
- 5in. 900ft. L.P. acetate . . . 10/-
- 5in. 1200ft. D.P. mylar . . . 15/-
- 5in. 1200ft. L.P. acetate . . . 12/6
- 5in. 1800ft. D.P. mylar . . . 22/6
- 7in. 1200ft. std. mylar . . . 12/6
- 7in. 1800ft. L.P. acetate . . . 15/-
- 7in. 1800ft. L.P. mylar . . . 20/-
- 7in. 2400ft. D.P. mylar . . . 25/-

**COSSOR DOUBLE-BEAM OSCILLOSCOPE 1035**

4in. tube. Calibrated Y1 amplifier from 50mV to 50V. Bandwidth 100Mc/s. Calibrated Y2 amplifier from 5V to 500V with bandwidth up to 100Kc/s. Directly calibrated X shift providing time measurements from 15 microseconds to 150 milliseconds. Supplied in guaranteed perfect condition. £40 each. Carr. 39/-.

**UNIVERSAL AVOMETER MODEL "7"**



50 ranges. Guaranteed perfect working order. Supplied complete with leads, batteries and instructions. £11 each. Registered post 5/- extra.

**MINE DETECTOR No. 4A**

Will detect all types of metals. Fully portable. Complete with instructions. 39/6 each. Carr. 10/-. Battery 8/6 extra.

**SILICON RECTIFIERS**

- SCR. 400V. P.I.V. 4.7 amp. . . 7/6
- 200V. P.I.V. 1 amp . . . 5/6
- 400V. P.I.V. 500mA . . 5/6
- 400V. P.I.V. 500mA . . 3/6
- 70V. P.I.V. 1 amp . . 3/6

0A292 miniature silicon rectifiers, 1/ each. Discounts for quantities. Please add postage.

**ERSKINE TYPE 13 DOUBLE BEAM OSCILLOSCOPE**

Time base 2c/s—750Kc/s. Calibrators at 100Kc/s and 1Mc/s. Separate Y1 and Y2 amplifiers up to 5.5Mc/s. Operation 110/230 volt A.C. Supplied in perfect working order. £27.10.0, Carr. 20/-.



- 50µA . . . 32/6
- 100µA . . . 29/6
- 200µA . . . 27/6
- 500µA . . . 25/-
- 50-0-50µA . . 29/6
- 100-0-100µA 27/6
- 300mA . . . 22/6
- 1mA . . . 22/6

Calibrated "S" meters 35/-. A full range of larger clear plastic and Bakelite panel meters are available. Send for illustrated leaflet. Trade terms available.

**CLEAR PLASTIC PANEL METERS**

D'Arsonval Movement • Jewelled Movements, 1 1/2 in. Square Fronts, 1 in. Overall Behind Panel, 1 in. Dia. Panel Hole. Accuracy 2% of Full Scale. Silver Dials, Black Numerals and Pointers. Front Zero Adjustment. All types moving coil. Individually boxed and guaranteed. Available as follows:

- 10mA . . . 22/6
- 50mA . . . 22/6
- 100mA . . . 22/6
- 150mA . . . 22/6
- 200mA . . . 22/6
- 500mA . . . 22/6
- 750mA . . . 22/6
- 1A. DC . . . 22/6
- 5A. DC . . . 22/6
- 3V. DC . . . 22/6
- 10V. DC . . . 22/6

**FIELD TELEPHONES**

Type "L". Two line connection, generator bell ringing. Complete telephone in intercom. Supplied in excellent condition, fully tested and complete with batteries. Only 69/6 per pair. Carr. 5/-.



Type "F". As above but moulded bakelite case (as illustrated). Supplied complete with wooden transit case for field use. £4.19.6 per pair. Carr. 5/-.

**MARCONI TF 146G/4 STANDARD SIGNAL GENERATORS**

First release of this late mark. 85Kc/s to 25Mc/s ±1%. Output variable from 1µV to 1 volt. Internal sine wave modulation 400cps up to 75c/s. Operation 200/250 volt A.C. Offered in excellent condition. Ex-ministry, untested without leads £16.10.0 or tested and guaranteed £25. Carriage 30/-.

**TE-20A R.F. SIGNAL GENERATOR**



A precision signal generator of extremely high accuracy and quality. Six ranges from 120Kc/s to 130Mc/s on fundamentals with calibrated harmonics from 120-300 Mc/s. 400 cps INT. MOD. OR EXT. MOD. OUTPUTS MOD. R.F. UNMOD R.F. or 400 c/s audio. R.F. output in excess of 100 mv. Large clear 5 inch dial. Handsome grey metal case with handle. Size 7 1/2 x 10 x 4 1/2 in. Complete with leads. Operation 220/240 volts A.C. Supplied brand new and guaranteed £12.19.6. Carr. 5/-.

**P.C.R.2 COMMUNICATION RECEIVERS**

Excellent 6 valve receiver. Frequency coverage on 3 bands, 800-2300 metres, 190-550 metres and 8-22Mc/s. Output for phone or speaker. Supplied in perfect condition, £25.19.6 each. Carr. 10/-. The receiver can be supplied with an internal power supply to operate on 200/250 volt A.C. at 39/6 extra, or plug in external power supplies are 35/- extra. Full circuit supplied.

**AVO WIDE RANGE SIGNAL GENERATORS**

Frequency coverage 50Kc/s to 80Mc/s in six turret operated ranges. For use on standard A.C. mains. Packed in original transit cases with accessories. Supplied in as new condition. fully checked before despatch. £15. Carr. 10/-.

**MINIFLUX 1 TRACK TAPE HEADS**

Set of three, record, playback, erase. Only 29/6 set. P. & P. 9d.

**MICROAMMETERS**

0-500 microamp. 2 1/2 in. circular flush panel mounting. Dials engraved 0-15, 0-600 volts. Brand new boxed, 15/-, P. & P. 1/6.

**HEAVY DUTY AUTO TRANSFORMERS**

0/115/230 volts step up or step down. Brand new boxed, ex-U.S.A. 3,000 watt. £7.10.0, carr. 10/-; 7,500 watt. £15.0, carr. £1.

**CR.100 COMMUNICATION RECEIVERS**

60Kc/s to 30Mc/s on 6 bands. 200/250 volt A.C. operation. Supplied in perfect working condition. £21 each. Carr. 30/-.

**FIELD STRENGTH METERS**

Frequency coverage 1-250Mc/s. Fitted with 200 microamp meter. Supplied with telescopic aerial, earpiece and instructions 69/6 post paid.

LARGEST STOCK OF COMPONENTS IN THE COUNTRY. OPEN 9 a.m.-6 p.m. EVERY DAY—MONDAY TO SATURDAY.

**G.W. SMITH & CO (RADIO) LIMITED**  
Phone: GERRARD 8204/9155  
Cables: SMITHEX LESQUARE  
3-34 LISLE STREET, LONDON, W.C.2

★ AS SUPPLIED TO Government Departments, Technical Colleges and Universities, Motor and Aircraft Industry, Industrial Research Laboratories, Education Departments, Film Studios. Ideal for all Commercial and Domestic purposes!



Call, write or 'phone

**HORNTONS  
ELECTRONICS**  
1 NAVIGATION STREET  
(next to Queens Hotel)  
**BIRMINGHAM 2**  
Telephone MID 0972

**KEEP AN  ON THINGS**

with another unbelievable offer!

**"CLOSED-CIRCUIT"  
TELEVISION CAMERAS**  
FANTASTIC **£45** COMPLETE  
AT ONLY Carr. & Ins. 18/-  
definitely unrepeatable at this price!

★ **READY ASSEMBLED FOR IMMEDIATE Use** .. Note— These Cameras have been fitted with NEW 2nd Grade Industrial Viticon Tubes, and whilst odd blemishes are existent, picture quality is good. Thoroughly recommended for **EXPERIMENTAL PURPOSES** as well as for **SECURITY, EDUCATION and ENTERTAINMENT**. Simplicity in operation, no technical knowledge required, camera plugs direct into aerial socket of your TV Set. 405 line R.F. output. Horizontal Resolution 2-21 Mc/s. Tunable to any Channel in Band 1, i.e. Channels 1-5. Distance between Camera and Sets can be up to several hundred yards. 4 to 6 TV Sets can be used off one Camera 210-240 v. A.C. 50/60 cycles. Interchangeable lens mounting; "C" mount (16 mm. Cine fitting). Weight only 4 lb. Telephoto lenses can be obtained on request. Service facilities; spares readily available if required.

Get ready to record your own pictures on Video-Tape!

**NOTE**

**1 in. 1/1.9 ANASTIGMAT LENSES at only 12 Gns.**

This lens has varying aperture from 1/1.9 to 1/16 and is fully calibrated in focusing mount from infinity to 18in. Standard "C" mount. Highest quality, bloomed and correctly registered for TV work.

# TIME IS MONEY!

With today's high labour costs, this old saying is particularly true. What has this to do with catalogues? A catalogue that lists all the components you are likely to need — over 5,000 — and indexes them fully and accurately must save you many hours of searching. With our well-known by-return Mail Order Service we save you even more time.

Most of the items we sell are at standard prices. We don't give stamps, but by saving you time we save you money! If you are unconverted send the coupon today, together with 2/6, plus 1/6 postage and packing. You may find it the best investment you ever made.

**SHOP HOURS FROM  
1st MARCH 1964**

|                            |        |
|----------------------------|--------|
| Mon.                       | 9-5.30 |
| Tues.                      | 9-5.30 |
| <b>WED. CLOSED ALL DAY</b> |        |
| Thurs.                     | 9-5.30 |
| Fri.                       | 9-6.30 |
| Sat.                       | 9-5.30 |

PLEASE WRITE YOUR NAME AND ADDRESS IN BLOCK CAPITALS

NAME .....

ADDRESS .....

HOMERADIO LTD., Dept. PW, 187 London Rd., Mitcham, Surrey

that the circlip has its own stand-off washer in place.

**Tape Recorder Drives**

A similar arrangement of drive is sometimes found in tape recorder mechanisms, as shown in Fig. 3. The flywheel is driven by an idler which locates a stepped capstan for speed change. Again, care should be taken in the setting of the capstan, and the bearings of motor, idler and flywheel. Where belt drive is employed, check for hardened portions of rubber or plastic belts, which can cause "bumps" and irregular drive. If a machine has been unused for some time, the belts may tend to harden into their "shape" and can sometimes be cured by slight heating. Perhaps the best method, if the belts can be removed without too much trouble, is to allow them to recover pliability in a bowl of hot water, remembering to dry them thoroughly before replacement, then running the machine for a lengthy test period.

Some causes of wow and flutter on tape mechanisms are not so obvious, and Fig. 4 points out a few of the possible trouble spots. Binding pressure pads can cause irregular tape transport, as can incorrectly aligned guides, pressure rollers

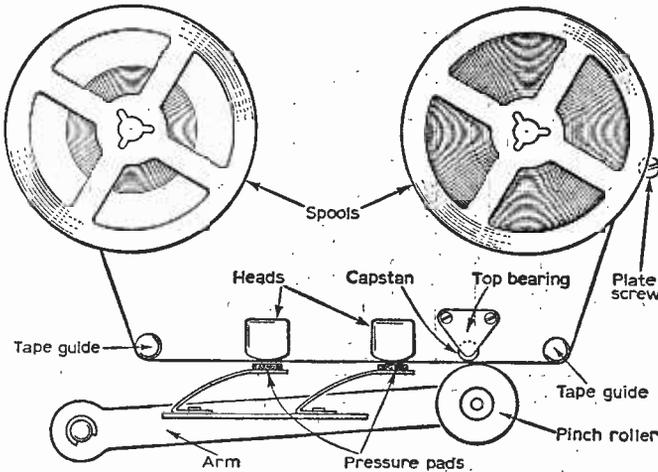


Fig. 4: Possible points on a tape deck where wow or flutter may originate.

and spool carriers. Check that spool carriers are not fouling such things as deck plate screws, that the top plate is firmly in position, that the pressure arm engages cleanly, and the top bearing of the flywheel is in alignment, clean and lubricated.

Flutter is sometimes caused by excessive take-up tension, usually the outcome of a hardened clutch felt or wrongly set spindle, where the inner carrier type of clutch is fitted. Similarly, a braking action of the feed spool, either by excessive reverse torque of the feed brakes can give rise to irregularity..

**Laboratory Measurements**

Testing for wow and flutter has become an exact science in the laboratory, and quite elaborate "fluttergrams" are prepared for the reviews in the specialist magazines. If it is remembered that these faults are a form of frequency modulation, the difficulty of making measurements of the percentage of wow will be realised.

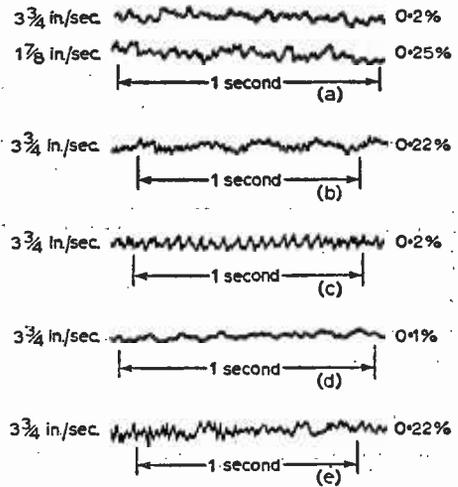


Fig. 5: A selection of "fluttergrams"—see text.

The laboratory method of measurement is to record a steady tone, say 3kc/s, then play back this recording, feeding the output into a "flutter-bridge" which consists of a limiter and f.m. discriminator circuit. This converts the frequency variations into amplitude changes, and these are used to operate a high-speed pen recorder. The result is a very informative record of the continuous output against a time scale. Reduced to one second sections, these fluttergrams give an immediate indication of both the low-periodic wow and the high-speed flutter, as shown in Fig. 5. (The author is indebted to technical consultant A. Tutchings for these fluttergrams, which were prepared for reviews of new equipment in "The Tape Recorder.")

**Study of the Fluttergrams**

Fig. 5(a) shows the random effect of speed variations at 3 3/4 and 1 in/sec of a high quality machine. There is hardly any periodic content of wow and the amount of high-speed flutter would be unnoticeable, even on a sustained piano note.

As a contrast, Fig. 5(b) demonstrates the effect of a 5c/s capstan wow. Fig. 5(c) has an 18c/s wow due to the idler of the machine under test being out of true, and a fair amount of high-speed flutter. Although Fig. 5(d) shows a 7c/s wow, due to the capstan, the total integrated wow and flutter for this machine was as low as 0.1%, and the fluttergram shows an almost total absence of high-speed variation. Fig. 5(e) is included to show the cancelling effect of the 50c/s flutter from a drive motor rotating at 3,000 rev/min where the variation adds

—continued on page 1090

# an advanced metronome

A five valve instrument with provision for accenting the number of beats to the bar.

BY G. J. POPE

THIS article describes a novel metronome circuit evolved by the writer a short time ago. Many readers with musical interests will no doubt find this a useful design to develop into a practical model.

voltage drop across the common cathode resistor is much lower when V2A is triggered.

Diodes D1 and D2 in conjunction with the capacitors C3 and C4 form a diode pump circuit, the voltage across the 2μF capacitor C4 rising in a series of steps whose height will be roughly proportional to the input pulse from the multivibrator

$$\text{reduced in the ratio } \frac{0.02}{2 + 0.02}.$$

Thus the voltage across the 2μF capacitor will rise positively until the potential on the grid of V2A just exceeds the standing cathode voltage due to V2B current. V2A will then switch on, and the cathode voltage will fall to a low value. Thus C4 will be discharged to near earth potential. (See Fig. 2). V4 remains cut off whilst the charge on the 0.1μF (C5) between V2A anode and V2B grid leaks away through the 270kΩ resistor, R7.

A pulse at V2B anode is of considerably lower amplitude than that at the output of the multivibrator, so that a booster amplifier is required to operate V5A and V5B. These latter two triodes operate as a second flip-flop circuit, and are brought into operation via a further staircase circuit from the first flip-flop output.

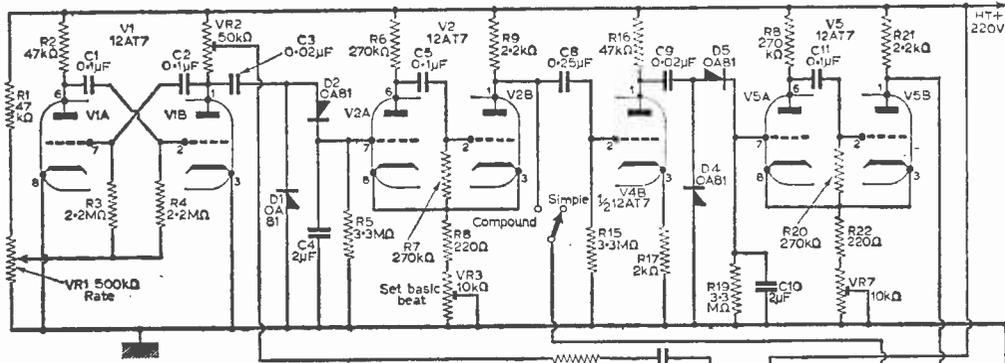



Fig. 1: The circuit.

Valves are used in this design since double triodes were then, and possibly still are, cheaper than a pair of reliable transistors. However, the principle could be extended to transistor circuitry if required.

It was considered that a method of accenting the number of beats in the bar would be desirable. By the use of staircase integrator circuits, it is arranged for the accenting of the first beat which is required for simple or common time marking, and also the accenting of fourth and seventh beats which is required in the case 6/8 and 9/8 time respectively.

Referring to the circuit diagram (Fig. 1) it will be seen that the two triodes V1A and V1B form a multivibrator and this produces the basic beat measure. The rate of this basic beat can be varied by means of potentiometer VR1, thus the time can be adjusted for *Lento*, *Andante* or *Presto*, and for the basic note value—crotchet, quaver or semiquaver etc.

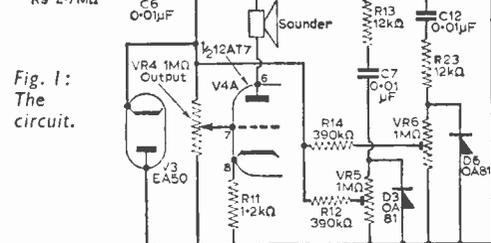Valves V2A and V2B form a flip-flop circuit, where V2B is normally conducting. The current in V2B is much greater than in V2A, so that the



V1A and V1B produce a basic note beat, and the 10kΩ potentiometer VR3 in V2 cathode circuit may be varied so that either two, three or four pulses are counted to V2A grid before this valve triggers. If the potentiometer VR7 in V5A and V5B cathode is set so that V5 also triggers when V2 triggers, then a large coincident pulse will be applied to V4A grid and the waveform will appear as either 2/4 time (Fig. 3a) or 3/4 (Fig. 3b), or as 4/4 time (Fig. 3c).



Compound times are counted by varying the potentiometer VR7 in V5 cathode circuit. Potentiometer

TOP QUALITY—LOW COST **CRC** AMATEUR RADIO EQUIPMENT

**BUILD YOUR SHORT WAVE LISTENING STATION WITH CODAR-KITS.  
CR 66 COMMUNICATIONS RECEIVER**

★ **P.R. 30 R.F. PRESELECTOR** ★

**THE FINEST SUPERHET KIT EVER OFFERED**

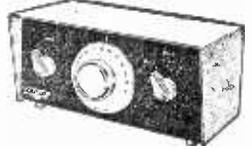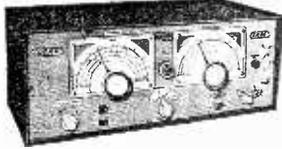

★  
Frequency Range 540 Kc/s to 30 Mc/s in four Band-switched ranges.

Frequency range 1.5-30 Mc/s. Substantially improves the performance of any superhet receiver.

Electrical Bandsread. Coil Unit wired ready and I.F. Transformers factory aligned, no test equipment required. Temperature compensated trimmers. Regenerative I.F. stage for maximum gain and B.F.O. Panel aerial trimmer, separate speaker switch, 3 watts output for external 2-3 ohm speaker. Separate cathode follower for tape recording etc. Valve line-up—ECC81, 6BF9, ECC81, EL84, EZ80, 6EM84 (Optional extra). For 200-250 volt A.C. Cabinet size 16 x 6½ x 8½ in.

G4HZ writes . . . I am delighted with it, it improves my Eddystone 640 in all respects. The difference with the Pre-selector is fantastic, a weak signal on 15 metres about S2 changed to S8. On the L.F. Bands, unwanted noise and mush is cut out.

G3RIA writes . . . The results in conjunction with my Eddystone 888 are amazing. Signals are twice as strong with much higher signal/noise ratio. A first-class product well worth the money. The P.R.30 uses EF183 Frame Grid R.F. Amplifier and provides up to 20 dB gain. Features include vernier tuning, gain control, selector switch for either dipole or end fed antenna. External power supplies (obtainable from Rx). Smart styling in grey and black. Complete, READY BUILT, with all plugs, cables. Now available in two models.

Complete Kit with 17-page Instruction Manual £18.50  
Tuning indicator parts with EM84, 17/6. Carriage 6/-.

P.R.30 for external power supplies 180-250 volts H.T., 6.3 volts 3 amp. L.T. (obtainable from receiver). £4.17.6 Carr. 3/6.


"S" METER CONVERSION KIT NOW AVAILABLE  
H.P. TERMS AVAILABLE

P.R.30X self powered with internal power supply for 200-250 volt A.C. Will provide 200 volts up to 25 M/a. and 6.3 volts 1 amp. for other accessories. £7.2.0 Carr. 3/6.

CAN BE SUPPLIED READY BUILT, PRICE ON REQUEST.

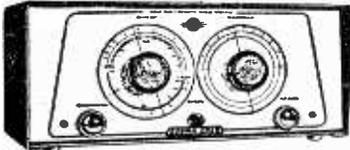**CODAR-KIT CR 45 MAINS T.R.F. SHORT WAVE RECEIVER**

World-wide short wave reception, North-South America, India, Russia, Far East, Australia, amateurs, shipping, etc.



- ★ Separate electrical bandsread.
- ★ Three slow motion vernier drives.
- ★ Low loss polystyrene plug-in coils, factory aligned.
- ★ Dials calibrated in frequencies and degrees.
- ★ Power output 3 watts for 2/3 ohm speaker.
- ★ Valve line-up: ECC81/EL84/EZ80.
- ★ Front Panel Silver and Black, control knobs Grey.
- ★ Provision for panel phone jack.

Superb modern styling and Top quality components throughout. Complete CR 45 CODAR-KIT, with valves and 3 Coils, 10-28, 25-75, 60-176 metres. Instruction Manual 11 pages, less Cabinet

£7.5.0 Carr. 4/6.


CR 45 Cabinet Silver Grey 12 x 5½ x 7 in. with sliding door for easy coil changing and detachable louvered rear panel 28/6  
Instruction Manual only 4/- post free. Extra coils 4/9 each.

★ CAN BE SUPPLIED READY BUILT PRICE ON REQUEST.

★ **THE MINI-CLIPPER**

- ★ Miniature 1 valve short wave receiver.
- ★ Low loss polystyrene plug-in coils, factory aligned.
- ★ Air spaced ball bearing condensers.
- ★ Provision to add two-transistor amplifier.
- ★ Battery lasts months.

36/6

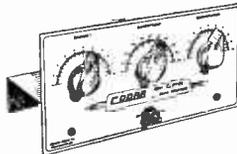

Can be built in one evening, ready to switch on, to bring the fascination of Short Wave listening at very low cost. Complete MINI-CLIPPER CODAR-KIT, valve, and one coil 25-75 metres, Instruction Manual 4 pages, 36/6, carr. 2/6. Extra Coils 4/9 each. Electrical Bandsread available. Instruction Manual only 2/-, post free.

★ **THE SUPER CLIPPER**

- ★ Peak Performance short wave battery receiver.
- ★ Large precision dial, dual slow motion drives.
- ★ Bandsread on all Bands.
- ★ High gain valve/transistor hybrid circuit.
- ★ 2 Mullard transistor amplifiers, pre-assembled and tested.
- ★ Low loss polystyrene plug-in coils, factory aligned.
- ★ Batteries last months.

88/6



Easy to assemble, this famous Short Wave Receiver brings a new world of listening pleasure to your finger tips. Complete SUPER-CLIPPER CODAR-KIT, valve, transistors, 2 Coils 20-60, 55-180 metres. Instruction Manual 7 pages, 88/6, carr. 2/6. Front Panel Silver Grey, 10 x 7½ in. 6/9 extra if required. Extra Coils 4/9 each.

CODAR-KITS are famous for PEAK PERFORMANCE, EASY TO FOLLOW INSTRUCTIONS, CLEAR PICTORIAL DIAGRAMS. Some of the Top Quality names who supply material for CODAR-KITS . . . MULLARD, BRIMAR, JACKSON, DENCO, ELECTRONIQUES, THORN, A.E.I. etc. etc. . . only the best is good enough for the high CODAR standards which make complete success certain. 6d. in stamps brings illustrated leaflets.

**CODAR RADIO COMPANY**

BANK HOUSE, SOUTHWICK SQUARE, SOUTHWICK, SUSSEX G3IRE CANADA: CODAR RADIO OF CANADA, TWEED, ONT. G3HGQ

This is a first-class instrument and 'MADE IN ENGLAND' need we say more!

# POCKET SIZED MULTI-RANGE TEST SET

£11.10.0 complete with leather case ...

## SEE **minitest**



- ★ D.C. SENSITIVITY 20,000 ohms per volt
- ★ A.C. SENSITIVITY 2,000 ohms per volt
- ★ D.C. ACCURACY ± 2% F.S.D.
- ★ A.C. ACCURACY ± 2% F.S.D.

- ★ A.C. ACCURACY maintained up to 20 kc/s.
- ★ EASY TO READ SCALE
- ★ TWENTY RANGES
- ★ ADDITIONAL DECIBEL SCALE
- ★ PRESSED STEEL CASE

**RANGES:**

| D.C. Volts | D.C. Amps. | A.C. Volts | Ohms         |
|------------|------------|------------|--------------|
| 0-1000     | 0-1 Amp.   | 0-1000     | 0-2000       |
| 0-250      | 0-100 mA.  | 0-250      | 0-200,000    |
| 0-100      | 0-10 mA.   | 0-100      | 0-20 Megohms |
| 0-25       | 0-1 mA.    | 0-25       |              |
| 0-10       | 0-50 μA.   | 0-10       |              |
| 0-2.5      | 0-2.5      |            |              |

A modern self-contained multi-range test set of high sensitivity, intended for the measurement of A.C. and D.C. volts, D.C. current and resistance. The pressed steel case not only effectively screens the movement from external magnetic fields but also provides that extra protection against the accidental blow or mishandling that would fracture a completely plastic moulding.

The exterior cover is moulded in grey Melamine and is designed to focus attention on the clear easy-to-read scale.

GENERAL CATALOGUE covering full range of components, send 1/6 in stamps or P.O. PLEASE SEND S.A.E. WITH ALL OTHER ENQUIRIES.

# DENCO (CLACTON) LTD.

(DEPT. P.W.) OLD ROAD, CLACTON-ON-SEA, ESSEX

## ADAMIN- by LITESOLD



These new ADAMIN micro soldering instruments complement the well-known LITESOLD models for special applications and still further extend our very comprehensive range of specialised soldering equipment.

Bit sizes now 1/16 in. to 1/8 in.

### A POPULAR ADAMIN MAINS MODEL

The C10L (shown on bench stand) is probably the smallest mains voltage model in the world. Bit dia. 3/32 in., length 7 in., weight 1/2 oz. (less flex). Heats in 30 secs.

Brochure No. S10 sent free on request.

Sole proprietors and manufacturers:

**LIGHT SOLDERING DEVELOPMENTS LTD**  
28 Sydenham Road, Croydon, Surrey

Phone: CR0ydon 8589

Grams: Litesold Croydon

## EXPRESS ELECTRONICS

32 SOUTH END CROYDON SURREY

TEL. CR0 9186

### VALVES NEW TESTED AND GUARANTEED FOR THREE MONTHS

|       |            |                |      |       |      |       |      |       |      |
|-------|------------|----------------|------|-------|------|-------|------|-------|------|
| IC1   | 5/6 6BE6   | 7/- 12AU7      | 6/9  | DH142 | 5/6  | EF91  | 4/-  | PL83  | 7/-  |
| 1C2   | 7/6 6BB8   | 5/6 12AX7      | 6/9  | DH150 | 10/- | EF93  | 5/6  | PY33  | 10/6 |
| 1C3   | 7/6 6B76   | 6/9 12BE6      | 6/9  | DK91  | 5/6  | EL41  | 9/6  | PV81  | 6/9  |
| 1F1   | 7/6 6BR7   | 8/9 12BH7      | 10/6 | DK96  | 7/6  | EL84  | 7/-  | PV82  | 7/6  |
| 1F3   | 4/- 6BW6   | 6/6 12K8GT11/- | DL93 | 5/6   | EM85 | 10/-  | PV83 | 7/6   |      |
| 1FD1  | 7/6 6BW7   | 7/- 12QGT      | 7/6  | DL94  | 8/-  | EY31  | 7/6  | R19   | 6/6  |
| 1FD9  | 5/6 6D2    | 4/- 12SN7      | 6/9  | DL96  | 7/6  | EY31  | 10/- | SA1   | 9/6  |
| 1P1   | 7/6 6F13   | 1/6 6A5        | 9/-  | EB91  | 4/-  | EZ40  | 5/6  | U93   | 7/6  |
| 1P10  | 5/6 6HG6T  | 2/- 19AQ5      | 9/6  | EBC41 | 7/6  | EZ80  | 6/-  | U76   | 7/6  |
| 1P11  | 6/- 6J7GT  | 7/6 25L6GT     | 7/6  | EBC80 | 8/6  | EZ81  | 6/9  | U78   | 5/-  |
| 1R5   | 5/6 6K74   | 5/6 30C1       | 7/6  | ECC81 | 4/-  | HV R2 | 9/6  | U142  | 7/6  |
| 1R5   | 5/6 6K86   | 6/- 30L1       | 7/6  | ECC82 | 6/9  | KTC30 | 6/-  | UBC41 | 8/6  |
| 1T4   | 4/- 6Q7G   | 5/6 35L6GT     | 7/6  | ECC83 | 6/9  | KT66  | 13/6 | UCH42 | 9/6  |
| 1U5   | 5/6 6SL7GT | 6/- 35W4       | 8/6  | ECC84 | 6/9  | N17   | 5/6  | UF41  | 8/6  |
| 3Q4   | 5/6 6SN7GT | 7/6 35Z4GT     | 8/-  | ECC85 | 7/6  | N18   | 5/6  | OL41  | 8/6  |
| 3R4   | 5/6 6V6G   | 7/6 5763       | 7/6  | ECP80 | 6/9  | N19   | 6/-  | UY41  | 7/6  |
| 3V4   | 6/- 6X4    | 5/- 80         | 8/6  | ECP82 | 7/6  | PD9   | 6/9  | W17   | 4/-  |
| 3Y3GT | 5/- 6X5G   | 5/9 DAF91      | 5/6  | ECH42 | 9/-  | PCC84 | 7/6  | W76   | 4/6  |
| 674G  | 7/6 7Y4    | 6/- DAF95      | 7/6  | ECH81 | 10/- | PCF80 | 7/6  | W142  | 8/6  |
| 6A8   | 5/6 8D3    | 4/- DCC90      | 12/6 | ECL80 | 8/6  | PCF82 | 6/6  | X17   | 5/6  |
| 6AL5  | 4/- 9D7    | 9/6 DF91       | 4/-  | ECL82 | 7/6  | PCF83 | 6/9  | X142  | 9/-  |
| 6AM5  | 4/- 12AD6  | 11/6 DF96      | 7/6  | EF41  | 9/-  | PCL84 | 9/6  | X160  | 9/-  |
| 6AT8  | 5/- 12AH8  | 10/- DH76      | 7/6  | EF80  | 8/-  | PL41  | 9/6  | Z77   | 4/-  |
| 6BA6  | 5/- 12AT7  | 4/- DH77       | 5/-  | EF86  | 7/-  | PL82  | 7/-  | ZD17  | 5/6  |

### ASK FOR RESISTOR AND CAPACITOR COLOUR CODE FREE WITH EVERY PURCHASE

High Stability Resistors 1/4W 5% 50Ω to 1M, 9d. Midget Ceramics 500 v., 9d. Coax. Super Quality 1/4in. 6d. 1/8. Plugs 9d. Sockets 9d. Silicon H.T. Rects. 250 v. 300 mA 1/4in. x 1/2in. 8/6. Contact Coiled 250 v. 50 mA 8/6. 85 mA 8/6. NEW TRANSISTORS BY MULLARD. OC19, OC26, OC56, 25/-; OC24, OC45, 5/-; OC70, 6/-; OC71, 8/-; OC72, 6/-; OC73 Matched pair, 12/-; OC74, OC75, OC78, 7/6; OC81, 8/-; OC81 Matched pair, 12/-; OC170, OC171, 7/6.

### VALVES MATCHED IN PAIRS

EL34 27/6, EL84 18/-, N709 18/-, 6V6G 15/-, 6BW6 14/- per pair. Push-Pull O.P. Transformer for above 3/15G 14/6. P. & F. 1/6 12in. P.M. Speakers 3Ω 24/6. Baker's 'Belhurst' 12in. 15Ω 15W Stewart 80/-, 12in. Stereo Model 86.15.0.

### SETS OF VALVES

DK91, DF91, DAF91, DL92 or DL94... 19/6  
DK96, DF96, DAF96, DL96... 29/6  
8K8, 6K7, 6Q7, 4V6, 5Z4 or 6X5G... 19/6  
1R5, 1T4, 185, 384 or 3V4... 19/6

ECH42, EF41, EBC41, EL41, EZ40... 37/6  
EHC42, EF41, EBC41, EL41, UV41... 36/-

Postage and packing 6d. Over £1 post free. C.O.D. 4/-.



NB Number of steps depends on setting of cathode resistance

Fig. 2: The voltage waveforms at the grids of V2A and V5A.

meters VR5 and VR6 are adjusted so that the appearance of the pulses on a cathode ray tube screen would be as indicated in Fig. 4.

In the 9/8 time case shown above, both V2A and V2B fire on the arrival of a multivibrator pulse. On the receipt of the 4th pulse V2 enlarges this pulse to one of medium height (or loudness).

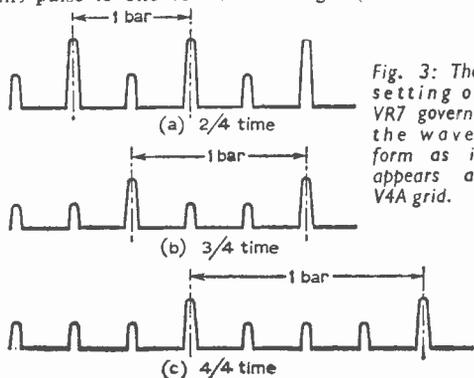


Fig. 3: The setting of VR7 governs the waveform as it appears at V4A grid.

The same thing occurs on the arrival of the 7th pulse; the 10th pulse causes both V2 and V5 to fire.

It was found necessary to connect a diode (V3) across the grid circuit feed of V4A in order to remove the negative-going component of the pulses before amplification.

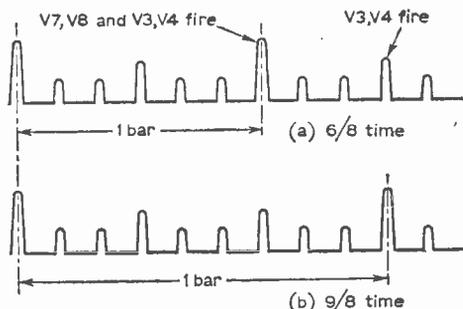


Fig. 4: The waveforms of compound times.

In a finished practical model, tapped resistor chains switched as required would be used to adjust the triggering potential of each flip-flop circuit.


A final point, in order to get reliable operation and a clean waveform (pulse trains as shown were obtained on an oscilloscope) it was found necessary to use a low impedance power supply. ■

# FREE INSIDE NEXT MONTHS ISSUE!
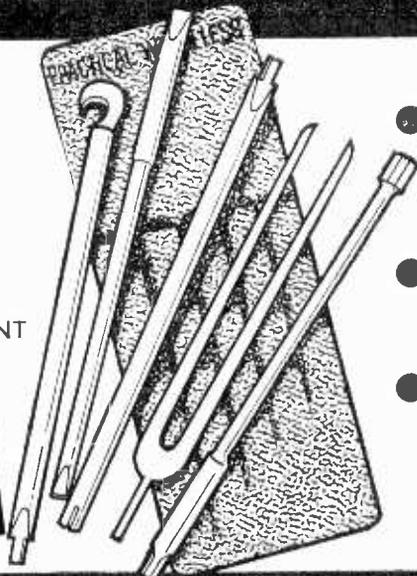
## Set of 5 TRIMMER TOOLS

FOR RECEIVER ALIGNMENT

ALSO  
IN NEXT MONTH'S ISSUE  
"RECEIVER ALIGNMENT  
WITHOUT  
TEST EQUIPMENT"



- ADJUSTS STANDARD COIL CORES AND TRIMMERS
- MOULDED IN LOW-LOSS POLYSTYRENE
- PACKED IN HANDY POCLETTE

APRIL ISSUE ON SALE MARCH 6<sup>TH</sup> - MAKE SURE OF YOUR COPY NOW!

In April last year, the author of this article had a Letter to the Editor published in which he mentioned his home-constructed stereo tape equipment, and in response to requests from many readers, Mr. Hawkins now gives details of the tape recorder he assembled from standard units at low cost.

## An Inexpensive Stereo Tape Recorder

BY R. C. HAWKINS

**T**HERE is now a wide choice of mono and stereo commercial tape recordings and after having experimented for some years with stereo disc equipment I became dissatisfied, for several reasons, with the results. Firstly discs, unless treated with elaborate care both in themselves and in the tracking mechanism have a limited "high quality" life, secondly there is a falling off in response as the speed reduces towards the centre and thirdly it is difficult with L.P.'s to select those items which are "favourites". Another reason is the rather abstract feeling that disc reproduction is only an extension of the horn and sound box era, and that tape has a more versatile future.

Apart from technical reasons there are the obvious advantages of being able to record one's own experimental stereo, to take recordings of the BBC stereo transmissions and to simplify recordings for home cine work.

### Facilities Required

Commercial stereo tape recorders cost from about 85 guineas upwards—well beyond my modest means. Although I have done my "stint" in radio and television construction, I am today a lazy constructor and prefer to take advantage of printed circuits and to use proven and tested designs. In resolving to build my own recorder I decided it must have the following facilities:

- 1 At least two speeds— $3\frac{1}{2}$  and  $7\frac{1}{2}$  in./sec. (to take advantage of all the commercial tape recordings available at present).
- 2 Four-tracks (i.e. two per channel on stereo) to give maximum tape economy and again to cover all present commercial recordings (two-track stereo will reproduce on a four track machine without apparent loss of quality).
- 3 Monitoring devices (almost essential on stereo recording).
- 4 Ability to feed larger separate stereo amplifiers when required.

5 Be sufficiently portable to use in outside locations.

A stereo tape recorder is basically two mono units feeding one deck and it is therefore perfectly feasible to use two standard units with suitable adaptation. After much searching I contacted Martin Recordakits and found this firm extremely interested and helpful (they had already made up a stereo recorder using their standard units). Martins supplied me with two Type 8311 Amplifiers with "ganged" potentiometers instead of the single ones. Loudspeaker monitoring operates with these amplifiers and "record" level is shown by the "magic eye" method. There is no reason why similar units by other manufacturers could not be used.

I chose the Collaro Studio Deck (operating at three speeds) and fitted with Reuter four track record and erase heads. Provided the heads are four track no special "stereo" heads are required. The manufacturers of the amplifiers must be notified of the type of head used so that any mismatch can be avoided.

### The Portable Cabinet

It is now necessary to make the suitcase type cabinet. This is surprisingly easy using the new adhesives. A frame is first made in 1in. by 1in. timber (20in. wide by 19in. and  $6\frac{1}{2}$ in. deep—slightly larger than really necessary to facilitate servicing and to give room for possible later modifications). The top and sides of this frame are filled with 6mm ply and the whole covered in self adhesive plastic cloth. One now has a bottomless box ready for fixing the units. The bottom (screwed on later when the recorder was complete) consists of  $\frac{1}{2}$ in. timber cut 2in. short each side to allow for ventilation; contemporary style legs are fitted to the bottom and these can easily be unscrewed when the recorder is used for outside locations. The lid can be made up of 6mm ply (no framing being necessary although it should be "blocked" at each inner corner for strength).

TRADE ENQUIRIES  
INVITED

# RADIO CLEARANCE LTD.

Telephone: MUSEum 9188  
EST. 35 YRS.

THE OLDEST COMPONENT SPECIALISTS IN THE TRADE  
27 TOTTENHAM COURT ROAD, LONDON W.1

## ANOTHER SCOOP— LIMITED QUANTITY ONLY

Don't miss a chance like this!

### The "Minigram" Transistorised Record Player

**FEATURES**

- Ready-built amplifier with four first-grade Mullard transistors.
- Plays 45 R.P.M. pop records.
- Built-in automatic stop.
- Lightweight and portable.
- Instruction leaflet supplied.
- Crystal pick-up with expendable stylus.
- Operates from a 9V battery (3/9 ext.)
- Available in two colours—cream/red or cream/blue.
- A real "FAMILY FAVOURITE".
- Ideal for Teenagers.
- For use ANYWHERE.
- Hours of amusement for the younger members of the family.
- Assemble one of these amazing Players in less than 30 minutes; supplied in 3 complete units with only 10 connections to make.

Approximate dimensions 9x8x4 in.



- A** Motor and pick-up deck.....(2/6 P. & P.) **39/6** ONLY **79/6**
- B** Ready-built 4-transistor amplifier, complete with volume control and L'speaker (2/- P.&P.) **35/-** the complete pkgs. (plus 5/- P. & P.)
- C** Portable two-tone case with handle, and expanded metal fret. (2/6 P. & P.) **5/-** or any unit sold separately.

## Loudspeaker Bargains Still Available

Enormous purchases of Brand New and Guaranteed Plessey loudspeakers enable us to offer these units at the **LOWEST PRICES EVER!** Don't miss this golden opportunity to obtain a first-grade permanent-magnet **LOUDSPEAKER** off the production line at **LESS THAN THE MANUFACTURER'S COST!** Read carefully the prepared list below and choose just the right speaker for the job—**COMPARE THE PRICES ANYWHERE!** **SELLING FAST—STOCKS CHANGING RAPIDLY.**

**SCHEDULE OF LOUDSPEAKERS AVAILABLE**

| Diameter in inches | Gauss in lines | Imped. in ohms | Price | Diameter in inches | Gauss in lines | Imped. in ohms | Price | Diameter in inches | Gauss in lines | Imped. in ohms | Price | Diameter in inches | Gauss in lines | Imped. in ohms | Price |
|--------------------|----------------|----------------|-------|--------------------|----------------|----------------|-------|--------------------|----------------|----------------|-------|--------------------|----------------|----------------|-------|
| 2 1/2              | 7000           | 30             | 8/-   | 3 1/2              | 9500           | 50             | 10/8  | 4                  | 9500           | 35             | 11/8  | 5                  | 8500           | 3              | 9/8   |
| 2 1/2              | 7000           | 35             | 8/8   | 4                  | 7000           | 25             | 11/8  | 5                  | 6000           | 3              | 8/-   | 5                  | 9500           | 3              | 10/8  |
| 2 1/2              | 7000           | 50             | 8/8   | 4                  | 6000           | 35             | 10/8  | 5                  | 6000           | 5              | 8/8   | 5                  | 9500           | 3              | 10/8  |
| 2 1/2              | 7000           | 80             | 8/8   | 4                  | 7000           | 35             | 11/8  | 5                  | 7000           | 3              | 8/8   | 5                  | 10000          | 3              | 11/8  |
| 3 1/2              | 8500 (E.M.L.)  | 3              | 8/8   |                    |                |                |       | 5                  | 7000           | 5              | 8/8   | 5 1/2              | 7000           | 3              | 11/8  |
| 3 1/2              | 7000           | 35             | 8/8   |                    |                |                |       | 5                  | 7500           | 3              | 9/8   | 5 1/2              | 8500           | 3              | 11/8  |

| Elliptical Size | Gauss in lines | Imped. in ohms | Price | Elliptical Size | Gauss in lines | Imped. in ohms | Price | Elliptical Size | Gauss in lines | Imped. in ohms | Price | Elliptical Size | Gauss in lines | Imped. in ohms | Price |
|-----------------|----------------|----------------|-------|-----------------|----------------|----------------|-------|-----------------|----------------|----------------|-------|-----------------|----------------|----------------|-------|
| 5 x 3           | 8000           | 3              | 7/8   | 5 x 3           | 9000           | 25             | 11/-  | 7 x 3 1/2       | 9500           | 3              | 10/8  | 8 x 2 1/2       | 8500           | 5              | 9/8   |
| 5 x 3           | 7000           | 3              | 8/-   | 6 x 4           | 6000           | 3              | 8/8   | 7 x 4           | 7900           | 3              | 10/-  | 8 x 2 1/2       | 9500           | 3              | 10/-  |
| 5 x 3           | 9000           | 3              | 8/8   | 6 x 4           | 7000           | 3              | 9/-   | 7 x 4           | 8500           | 5              | 10/8  | 8 x 2 1/2       | 9500           | 4              | 10/-  |
| 5 x 3           | 6000           | 25             | 9/8   | 6 x 4           | 8500           | 3              | 9/8   | 8 x 2 1/2       | 8000           | 3              | 8/8   | 8 x 2 1/2       | 9500           | 4              | 10/-  |
| 5 x 3           | 7000           | 25             | 10/-  | 6 x 4           | 8500           | 3              | 10/-  | 8 x 2 1/2       | 7000           | 3              | 9/8   | 8 x 2 1/2       | 9500           | 5              | 10/-  |

ALLOW 2/- each Speaker for postage and packing, and please specify the exact requirements—the nearest available will be sent.

## OVER 50,000 SOLD AND STILL THE DEMAND CONTINUES FOR OUR "HEAVENLY TWINS"

Ask for a demonstration in the shop.

**"CAPRI"**  
Sensitive!  
Super-selective!  
Superb  
Speaker!  
**NOW ONLY 79/6**  
(2/- P. & Pkg.)  
Pocket Super-net MW and Drotswitch LW  
Size 4 1/2 x 2 1/2 x 1 1/2 in.  
Constructional data 1/8 Post free.




The best and easiest transistor build-yourself sets available.

Send S.A.E. for FREE PARTS LIST  
6 First Grade MULLARD Transistors Diode(s) and all components BRAND NEW and GUARANTEED

Choice of a dozen stations in daylight...

**THE "CONTESSA"**  
"QUEEN OF THEM ALL"  
ONLY **£9.19.6**  
(3/6 p. & pkg.)

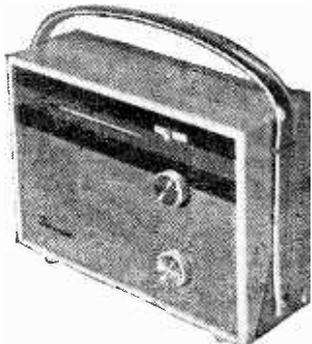PORTABLE and CAR RADIO 2 WAVEBAND SUPERHET Construction manual 2/10 Post Free.



Inclusive price for all associated components, case, battery and instruction Book complete in every detail. ANY PARTS SOLD SEPARATELY ON THE BUILD-AS-YOU-BUY SCHEME

**CONTESSA £9.19.6** (plus 3/6 P. & P.)  
**CAPRI** Battery 2/6 extra. **79/6** (plus 2/- P. & P.)

**SELECTED BARGAINS**

Beautifully geared AM/FM 2 Gang Condensers, 4/8; AM/FM IFT's 465 kc/s and 10.7 Mc/s, 4/8 pair; Magnavox Crystal Tape Recorder Mikes, 12/8; Double-tuned Transistor ferrox IFT's Q120, 470 kc/s, 5/8 pair; transistor sub min 7 mm coil set (4) 4/6, the set; Plessey-Brayhead turret tuners 34/38 Mc/s, valves 8/8 each; 3 watt Stereo Amplifiers, complete, ready to switch on 79/6; Sentercell rectifiers R3/2D-D3-2-1Y, 2/6 each. DIODES—0A70, 0A79, 0A90, CG46H, GD10, 2/- each.

TRANSISTORS: Set of 6 (RF and LF) including 1 watt matched pair; heat sink and diode, 13/6 the set; OC45 4/6, PXA101 3/6, AF115 4/6, Submin. Germanium diode 13, M.1 diode 6d, each. Silicon diodes 200 p.p.v., 200 mA, 1/- each, 400 p.p.v., 350 mA, 2/6 each. Please send STAMPED and ADDRESSED envelope with any enquiry. We regret no catalogues—our stocks move too quickly! Kindly make provision for additional postage and packing charges to avoid delay. Terms: Cash With Order or C.O.D. on Orders over 10/-.

# SPECIAL OFFER! FROM R. & T.V. LTD.

*Elegant Seven*



## COMBINED PORTABLE & CAR RADIO

The Radio with the STAR features

- ★ 7-transistor superhet. Output 350mW.
- ★ Two-tone grey wooden cabinet, fitted handle with silver coloured fittings. Size 12½ x 8½ x 3½in.
- ★ Horizontal tuning scale, size 1½ x 2½in. in silver with black lettering.
- ★ All stations clearly marked.
- ★ Ferrite-rod internal aerial.
- ★ I.F. 470 Kcs.
- ★ Operated from PP9 battery.
- ★ Full comprehensive instructions and point-to-point wiring diagram.
- ★ Printed circuit board, back printed with all component values.
- ★ Fully tunable over medium and long waveband.
- ★ Car aerial socket.
- ★ Full after-sale service.

**ONLY £5.9.6**

Plus 5/6 P. & P. Parts list & circuit diagram 2/6. FREE with parts. 4½in. Speaker also available, 7/6 extra.


Goods not despatched outside U.K.

All enquiries S.A.E. Terms C.W.O.
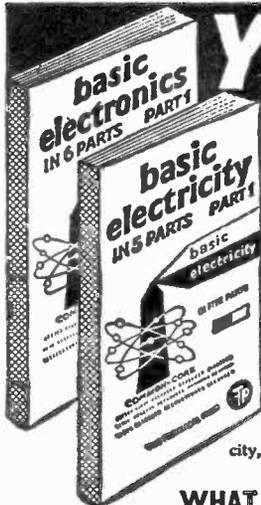
## RADIO & TV COMPONENTS (ACTON) LTD 21C High St., Acton, London, W3

Open 9 a.m.-6 p.m. including Sats. Early closing Wed.

**FREE**—limited period only —  
30-watt **ELECTRIC SOLDERING** Iron, value 15/6, to every purchaser of the parts for the "Elegant Seven".



# YOURS FREE FOR 7 DAYS

## The New 'Picture-Book' way of learning **BASIC ELECTRICITY (5 VOLS.)** **BASIC ELECTRONICS (6 VOLS.)**

You'll find it easy to learn with this outstandingly successful new pictorial method—the essential facts are explained in the simplest language, one at a time; and each is illustrated by an accurate, cartoon-type drawing.

The books are based on the latest research into simplified learning techniques. This has proved that the Pictorial Approach to learning is the quickest and soundest way of gaining mastery over these subjects.

The series will be of exceptional value in training mechanics and technicians in Electricity, Radio and Electronics.

### WHAT READERS SAY

- "Learn more in part 1 than the previous 2 years." L.M.J., Durham.
- "I am convinced that I am on to something really worth while." J.L.P., Fife.
- "Without doubt they are the easiest to follow books I have ever studied." W.J., Aylesbury.
- "Congratulations on a well planned easy to learn series." M.K., Horsham.
- "First class, I cannot praise them too highly." J.J., Taunton.

A TECHNICAL PRESS PUBLICATION

To Selray Book Co.  
60 Hayes Hill, Hayes, Bromley, Kent

Please send me Without Obligation to Purchase, Basic Electricity/Basic Electronics on 7 Days Free Trial. I will either return set, carriage paid, in good condition within 8 days or send down payment of 10/- (Basic Electricity) followed by 6 fortnightly payments of 10/-. Down payment of 12/- (Basic Electronics) followed by 6 fortnightly payments of 12/-. Alternatively, I will send 63/- (Basic Electricity—5 parts), 75/- (Basic Electronics—6 parts) post free. This offer applies to United Kingdom only.

Tick against set required (only one set allowed on free trial).  
**BASIC ELECTRICITY**  **BASIC ELECTRONICS**   
 Signature \_\_\_\_\_

(If under 21, signature of parent or guardian)

**BLOCK LETTERS BELOW**  
 Name \_\_\_\_\_  
 FULL POSTAL Address \_\_\_\_\_

**POST NOW FOR THIS OFFER!!**

The tape deck is fitted next. A template is provided with the Collaro deck so that the aperture may be cut to correct size and fixing holes drilled. More heat is

Fig. 1: A top view of the recorder showing the separate and common controls and sockets.

obviously generated with stereo equipment than mono and it is very advisable to mount the deck slightly raised from the baseboard by rubber grommets—this gives good air space for ventilation.

Stick-on "decorative" templates are provided by Martins for the controls but it must be remembered that only one ganged volume control and one ganged tone control is used. A ganged loudspeaker monitor control was also supplied but for reasons I will give later this was discarded and two separate controls used. There are, of course, two "mike" inputs, two "radio" inputs and two magic eye escutcheons.

The general layout is shown in Figs. 1 and 2.

**Wiring the Equipment**

It is not proposed to describe the amplifiers in detail: they are fairly conventional and a circuit diagram and point to point wiring instructions are supplied with each kit. Wires are already attached to the printed circuit baseboard of the amplifier although it may be necessary to extend these for the stereo set up. Provided one considers a single amplifier at a time it is quite possible for the completely non-technical to wire up the recorder.


It is best to consider the ampli-

Fig. 2: An under side view showing the positions of the amplifiers and mains transformers.

fiers as Channels A and B and to remember that Channel A occupies the left-hand side of the cabinet and is connected to the top connections in the erase and record heads. This will give the correct "phase" of playback on stereo tapes, provided the speakers are similarly placed.

A switch wafer is supplied with each amplifier which is designed to slip on to the speed change control on the Collaro deck. This wafer gives circuit compensation in the amplifier at the various speeds. With spacers ample room will be found to fit both wafers on to the spindle of this speed control.

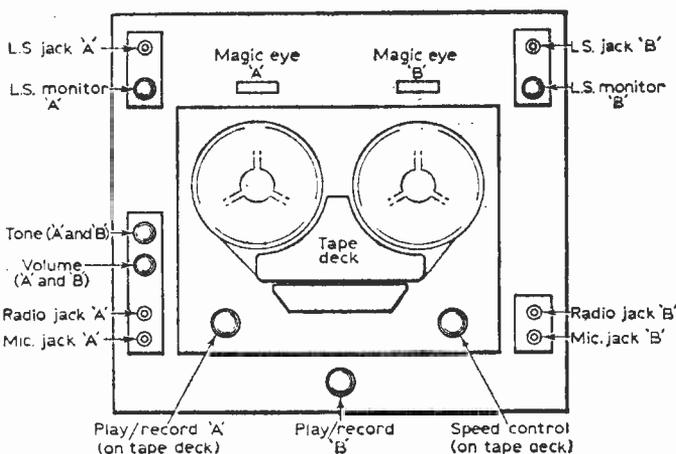
Wiring can now be completed as per the instruction booklet with the usual care exercised on



soldering the leads to the heads (it being essential to provide heat insulation from the heads with a pair of pliers whilst this operation takes place).

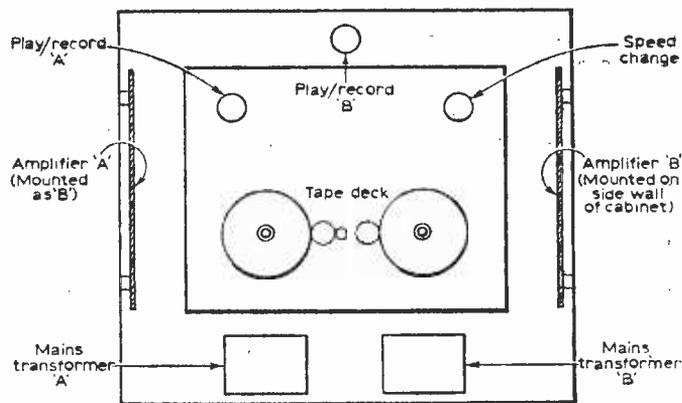**Loudspeakers**

It will be noted that no internal speakers are fitted as my already existing pair of wall mounted speakers provided a far better system for reproduction. The wiring for the amplifiers does provide for an internal speaker (these being connected when the external speaker jack plug is removed). For immediate playback on outside locations two



small 2½ in. speakers could easily be fitted on each side of the cabinet although stereo effect with these speakers would be less evident because of the narrow spacing.

The ganged volume control can be taken out of gang by a pull upwards on the spindle, and is used for "balancing". I achieved this by switching both amplifiers to "record" and feeding a radio signal to each amplifier in turn (this should obviously be done on a tuning signal or an audio signal generator can be used, if available). It is then only necessary to balance on the magic eye

shadow. Once balanced the control should be left in gang (apart from a periodic check) and any further balance compensation for particular commercial recordings carried out by decreasing volume to the appropriate speaker on the "monitor" control.

It was found initially that a "whistle" was recorded and this was traced to a beat note between the two erase oscillators. To cure this, switch to record on both channels and adjust the tuning slug on either one of the erase oscillator coils until the whistle disappears. The oscillators are remarkably stable as I have only had to carry out this operation once and no reappearance of "beat" has manifested in 18 months.

### Mono Operation

For mono operation one amplifier at a time can be used—the other amplifiers being muted by the appropriate "monitor" control (or separate mains switches can be inserted). Ample volume is available for ordinary domestic purposes with only one channel used. Full track mono use is available by this method and "head" switching is avoided.

On home recordings it was found that a disappointing amount of bass was evident. Compensation is made in the circuit to level out the characteristic of the amplifier in the record position; this was altered by removing C16 (in the Martin circuit) from the record/play switch and placing a short across this connection: C16 was

then placed in series with the sliding contact of this switch and the cathode of V2A (thus reducing bass feedback). An immediate improvement was evident and I reported this to Martins assuring them I was not a "boom" addict: they replied that technically I had "messed" up the response and they could not explain the apparent improvement. Constructors may like to try this modification if they are similarly disappointed.

### Stereo Operation

The subject of stereo recording is an enormous one and outside the scope of a constructional article. For some really demonstrative instruction I would recommend the purchase of a four-track stereo tape called "Stereo Confidential" issued by Music on Tape and available in either a 3½ or 7½ in./sec. version.

To feed an external stereo amplifier the outputs from the pre-amplifier in the tape recorder can be taken from the "radio" sockets. Stereo discs can be directly recorded by providing two jack plugs from a stereo pickup (red to Channel A) using the Radio sockets (remember, however, the re-recording of commercial discs is prohibited by the usual copyright regulations).

Quality is extremely good and adjudged superior to quite expensive console stereograms. With the internal output stages it would not be good enough for the hi-fi purist but this recorder is, by comparison, portable and very much cheaper. Cost of the deck and units was about £36 but "careful" buying could possibly reduce this price. ■

## The "7-20" Stereo Amplifier

—continued from page 1029

other one too, in exactly the same position and to the same extent. It is of paramount importance to maintain absolute symmetry between the two channels.

Adjustments of frequency response in the main amplifier should be carried out such that subjectively correct reproduction, with ample bass and treble, results from stereo records over SK4, with VR2 and VR3 set at mid-track. If this does not lead to sufficient speech clarity from a microphone over SK1 (too much bass), reduce the value of C5 until satisfactory performance is obtained. Much will depend upon the type of microphone used. A certain amount of treble boost in the microphone preamplifier, V1, alone is also obtainable by replacing C6 with a paper capacitor of about 0.1µF capacity.

Wherever grid stoppers are specified (resistors directly in series with control grid connections) these must be wired hard up against the respective valveholder pins.

### Loudspeakers

As already mentioned, speakers, or speaker groups, of adequate power rating are essential. The circuit as shown in Fig. 1 is for 4 to 6Ω speakers or groups.

If 15Ω units are to be used, the output transformers must be obtained with the appropriate

secondaries and the components in the main amplifier negative feedback loops must be changed. The correct values for R70, R71 are then 3.9kΩ, for R72, R73 1.8kΩ and for C30, C31 0.15µF. If original values were altered during frequency response adjustments, the above values for 15Ω speakers require alteration in the same proportion.

There is no objection to the use of series-parallel combinations of smaller speakers at different locations, provided that the total power rating remains adequate and the normal rules of matching are observed. Furthermore, with such multiple speaker positions, care should be exercised that stereophonic reproduction (if used) is not thereby confused.

### Final Checks

Upon completion of the amplifier, even if it appears to be working satisfactorily, voltages at all points shown on Fig. 1 should be compared with the prototype figures entered in Fig. 1. A meter of at least 20kΩ per volt sensitivity must be used, or a valve voltmeter.

If a meter of lower sensitivity is used, readings may in some cases be falsified (indicate low). Slight departures from prototype figures are possible, and may be ignored. But large differences—especially if different for corresponding points of the two channels, indicate faulty components or wiring errors, and should be traced and removed. It is advisable to check all wiring very carefully before first switching the completed amplifier on. ■

# RETURN-OF-POST SERVICE

We offer a really efficient Mail Order Service on all items stocked. All cash orders are dealt with on the day of receipt. ★ Hire purchase orders are subject to slight delay but this is kept to the absolute minimum.

## ● ILLUSTRATED LISTS

Illustrated lists are available on LOUDSPEAKERS, TAPE DECKS, TEST GEAR, GRAMOPHONE EQUIPMENT, AMPLIFIERS. Any will be sent free upon request.

## ● AMPLIFIER KITS

We have full stocks of all components for the Mullard 510, Mullard 3-3, Mullard 2 and 3 Valve Pre-amp, Mullard Stereo, Mullard Mixer. Fully detailed list on any of these sent upon request.

Instruction Manual: All Mullard Audio Circuits in "Circuits for Audio Amplifiers". 9/5. Post Free.

## ● MARTIN AUDIO KITS

A range of high quality transistor amplifying equipment is now being produced by MARTIN ELECTRONICS. Included are 3 and 10 watt Amplifiers, Pre-amplifiers, mixer and input switching units. Please write for full details.

## ● ARMSTRONG EQUIPMENT

### TUNER AMPLIFIERS

|                         | Cash Price | Deposit | Hire Purchase Mthly/Pmts. |
|-------------------------|------------|---------|---------------------------|
| Model 22 Stereo         | £48.15.0   | £9.15.0 | 12 of £3.11.6             |
| Model 22 M Mono         | £33.18.0   | £3.18.0 | 12 of £2.8.6              |
| Model 23 De Luxe Stereo | £56.0.0    | £11.0.0 | 12 of £4.2.6              |
| Stereo 55 Stereo        | £29.18.0   | £5.18.0 | 12 of £2.4.0              |

### RADIOGRAM CHASSIS

|                   |         |        |               |
|-------------------|---------|--------|---------------|
| Model AF308 AM/FM | £21.4.0 | £4.4.0 | 12 of £1.11.2 |
|-------------------|---------|--------|---------------|

### TUNERS

|                      |          |        |                |
|----------------------|----------|--------|----------------|
| Model T4B FM         | £20.8.0  | £4.2.0 | 12 of £1.9.11  |
| Model ST3 Mk 2 AM/FM | £25.12.0 | £5.2.0 | 12 of £1.17.11 |

Makers' literature available on any item.

## ● NEW MULLARD CONDENSERS

Mullard Miniature Foil and Polyester condensers as used in the latest TV and Transistor sets.

Miniature Foil, 30 volt working for Transistor sets. .01mfd. 70V; .022mfd. 90V; .047mfd. 90V; .1mfd. 110V.

Polyester Tubular Capacitors. Moulded outer case designed to withstand accidental contact with the soldering iron. Tolerance 10%. 12V, range: .01mfd. .022mfd. .047mfd. all 90V. each. 1mfd. 1/2; .47mfd. 1/8; .1mfd. 3/4; .400V, range: .001mfd. .0022mfd. .0047mfd. .01mfd. .022mfd. all 90V. each. .04mfd. 1/2; .1mfd. 1/3; .22mfd. 1/8; .47mfd. 2/5. Postage extra.

## ● MINIATURE ELECTROLYTIC CONDENSERS

Latest miniature types by Mullard and Radio spares.

RADIO SPARES: All 15 volt. 2mfd. 4mfd. 5mfd. 8mfd. 10mfd. 16mfd. 32mfd. 50mfd. 100mfd. all 2/3 each. Postage extra. MULLARD: 2mfd. 10V; 1/8; 4mfd. 4V; 1/8; 10mfd. 16V; 1/8; 16mfd. 10V; 1/8; 25mfd. 4V; 1/8; 25mfd. 25V; 1/3; 32mfd. 2.5V; 1/8; 32mfd. 4V; 1/8.

## ● "SYNCHROTAPE" RECORDING TAPE

Low priced British tape, all reels fitted with leaders. Standard Play: 600ft. (5") 13/6; 850ft. (5 1/2") 17/-; 1,200ft. (7") 21/-; Long Play: 900ft. (5 1/2") 17/-; 1,200ft. (5 1/2") 20/-; 1,800ft. (7") 30/-; All Post Free.

## ● TAPE RECORDING EQUIPMENT

### TAPE DECKS

|  | Cash Price | Deposit | Hire Purchase Mthly/Pmts. |
|--|------------|---------|---------------------------|
| ALL CARRIAGE FREE  |            |         |                           |
| COLLARO STUDIO, latest model, two track, Bradiatic Heads | £10.19.6   | £2.3.6  | 12 of 16/4                |
| Four Track, Marriott Heads                               | £17.17.0   | £3.12.0 | 12 of 26/2                |

### MARTIN TAPE AMPLIFIER KITS

Tape Amplifiers: For Collaro 8311-V 2-Track £11.11.0 8311-V 4-Track £12.12.0  
Tape Pre-Amplifiers: For Collaro 8312-CP 2-Track £8.8.0 8312-4-CP 4-Track £9.9.0  
Crimp through assembly for mounting 8312 Pre-Amp under Collaro Deck. £11.11.0  
Carrying Cases with speaker. For Collaro Deck and 8311 Amplifier £5.5.0.

H.P. TERMS available on decks, amp. and cases. Ask for quote.

MULLARD TAPE PRE-AMPLIFIER KIT  
We stock complete kits and all separate components for the Mullard Tape Pre-Amplifier. Fully detailed list available.

## ● LOUDSPEAKERS

GOODMANS: Axletree 8in., £5.5.7; Axiom 10in., £6.5.11; 12in., Axiom 301, £10.17.4; 12in., Axiom 301, £15.4.8; 12in., Axiom 51 Bass, £9.2.8; 12in., Axiom 61 Bass, £14.7.8; Trebax Tweeter, £6.10.2; X05000 Crossover unit, £2.0.11.  
WHITFIELD: HF1016 10in., £7.0.0; HF1012 10in., £4.7.6; HF816 8in., £6.0.0; T416 8in., £5.13.6; T16 Tweeter, £4.8.3; T15 Tweeter, £1.10.6; CX3000 Crossover unit, £1.11.3; CX1500 Crossover unit, £2.0.0. H.P. Terms available on all speakers.

## P.W. TEST METER KIT

Send for fully detailed list.

## ● STEREO COMPONENTS

Morganite Ranged potentiometers as specified for the Mullard circuits. ★ Log/Anti-Log, 500k, 1 meg., 2 meg. ★ Log/Log, 50k, 250k, 1 meg., 2 meg. ★ Lin/Lin 250k, 500k, 1 meg., 2 meg. All 10/6 each. Postage extra.

## ● TRANSISTORS

MULLARD. Current production types, not rejects. All in makers' boxes. Postage 3d. on each. AF114, 11/-; AF115, 10/6; AF116, 10/-; AF117, 9/6; OC44, 8/3; OC45 8/-; OC70 and OC71, 6/6; OC72, 8/-; OC72 Matched Pairs, 18/-; OC78, 8/-; OC81, 8/-; OC170, 9/6; OC171, 9/-; Any other Mullard type obtained promptly. Ask for quotation.

## ● JASON F.M. TUNERS

We stock all parts needed for the construction of these excellent tuners. All parts can be supplied separately but we can offer attractive reductions in price if all items are purchased at same time as follows:

|  |
|--|
| FMT1, £6.12.6; FMT2 (less power), £7.15.0.             |
| FMT3 (with power), £9.12.6; FMT3 (less power), £9.9.6. |
| FMT3 (with power), £11.7.6. Mercury 2, £10.14.6.       |
| JTV7, £14.12.6.  |

Hire Purchase Terms available. Ask for list.

## ● P.W. STRAND, MAYFAIR & SAVOY UNITS

We stock parts for the P.W. Strand Amplifier, Mayfair Pre-Amplifier and Savoy FM Tuner. Detailed price lists are available.

## ● LATEST TEST METERS

|                       | Cash Price | Deposit | Hire Purchase Mthly/Pmts. |
|-----------------------|------------|---------|---------------------------|
| AVO Model 8 Mark II   | £24.0.0    | £4.18.0 | 12 of £1.15.2             |
| AVO Model 7 Mark II   | £21.0.0    | £4.4.0  | 12 of £1.10.10            |
| AVO Multimeter Mark 4 | £9.10.0    | £1.18.0 | 12 of 14/4                |
| T.M.K. TPB            | £3.19.6    | £1.3.6  | 3 of £1.2.0               |
| T.M.K. TP58           | £5.19.6    | £1.15.6 | 3 of £1.11.4              |
| T.M.K. Model 500      | £25.19.6   | £1.15.6 | 12 of 13/8                |
| T.M.K. MODEL 47A      | £10.10.0   | £2.2.0  | 12 of 15/8                |

Full details of any of the above supplied free on request. The AVO models 7 and 8 are both latest models from current production—not to be confused with Government Surplus.

## ● OUTPUT TRANSFORMERS

GILSON: W0696A, W0696B, 50/6, post 2/6. W0710, 55/6, post 2/6. W0692, 60/6, post 2/6. W0767, 27/-, post 1/6. W0766A, 57/6, post 2/6. W01922, 84/-, post 3/6.  
PARTIDGE: P3667, 75/-, post 2/6. P4131, 75/-, post 2/6.  
PARMELO: P2629, 47/6; P2642, 45/-; P2643, 47/6. All plus post 2/6; P2641, 29/6, post 2/-; P2628, 17/-, post 2/-; P2632, 41/-, post 1/6.

## ● MAINS TRANSFORMERS

GILSON: W0741A, 63/-, post 4/-; W0830, 48/9, post 2/6; W0132B, 58/6, post 3/6; W0129A, 58/-, post 3/6; W0156B, 80/-, post 4/6; W01341, Choke, 36/-, post 2/-.  
PARMELO: P2631, 35/-, post 2/6; P2630, 54/9, post 3/6; P2644, 76/6, post 4/-; P2630, 41/-, post 3/-; P2631, 56/9, post 3/3.

## ● GRAMOPHONE EQUIPMENT

| ALL LATEST MODELS | Cash Price | Deposit | Hire Purchase Mthly/Pmts. |
|-------------------|------------|---------|---------------------------|
| ALL POST FREE     |            |         |                           |
| RECORD CHANGERS   |            |         |                           |

|                                     |         |          |             |
|-------------------------------------|---------|----------|-------------|
| GARRARD AUTOSLIM (Mono PU)          | £7.2.6  | £1.8.6   | 12 of 11/2  |
| GARRARD AUTOSLIM (Stereo PU)        | £11.9.0 | £2.6.0   | 12 of 16/11 |
| GARRARD AUTOSLIM (ATE Stereo PU)    | £12.5.4 | £2.9.4   | 12 of 18/-  |
| B.S.R. U414 (TC8 Mono PU)           | £6.19.6 | £1.7.6   | 12 of 11/-  |
| B.S.R. U411 Monarch (TC8 Stereo PU) | £7.19.6 | £1.11.6  | 12 of 12/4  |
| B.S.R. U414 (TC8 Mono PU)           | £7.19.6 | £1.11.6  | 12 of 12/4  |
| B.S.R. U416 (TC8 Stereo/LP/78)      | £8.19.6 | £1.15.6  | 12 of 13/8  |
| SINGLE RECORD PLAYERS               |         |          |             |
| B.S.R. T16 (TC8 Mono PU)            | £3.17.6 | £1.4.6   | 3 of £1.1.0 |
| B.S.T. G17 (TC8 Mono PU)            | £4.18.8 | £1.5.3   | 3 of £1.8.8 |
| GARRARD SRP10 (Mono PU)             | £5.9.11 | £1.12.11 | 3 of £1.9.0 |

### TRANSCRIPTION UNITS

GARRARD 4HF (GC8 PU) £16.12.6 £3.6.6 12 of £14.5  
PHILIPS AP1000 (S/M PU) £12.12.0 £2.10.0 12 of 19/6  
Many of the above can be supplied for stereo working. See our Gramophone Equipment List for details.

### ★ TERMS OF BUSINESS

Cash with order or C.O.D. We charge C.O.D. orders as follows: Up to £5, minimum of 4/2. Over £5 and under £10, 2/6. Over £10, no charge. Postage extra on CASH order under £5 except where stated. Postage extra on overseas orders irrespective of price.

# WATTS RADIO

(MAIL ORDER) LTD.

54 CHURCH ST., WEYBRIDGE, SURREY

Telephone: Weybridge 47556

Please note: Postal business only from this address  
Callers welcome by appointment

### ★ HIRE PURCHASE TERMS

Available on any item. Repayments over 3, 6 or 12 months as below. Three months: Deposit 4/- in the £. Service charge 5%. Minimum charge 10/-. Six months: Deposit 5/- in the £. Service charge 7 1/2%. Minimum charge 15/-. Twelve months: Deposit 4 1/2% in the £. Service charge 10%, minimum charge 30/-.

# NOMBREX INSTRUMENTATION

Wide-range Transistorised  
**AUDIO GENERATOR—Model 63**  
 Range 10—100,000 c/s.

- ★ Laboratory Standard Specification
- ★ Sine and Square Wave
- ★ Direct Frequency Calibration
- ★ Accuracy and Low Distortion
- ★ Calibrated Output Voltage
- ★ Battery Operated and Compact

**£16.15.0** complete with test lead  
 Battery 2/3. Post and Packing 3/6.  
 H.P. 4 gns. deposit and 47/- monthly.



Wide-range Transistorised  
**C.R. BRIDGE—Model 62**  
 6 Ranges: 1Ω to 100MΩ  
 1pF to 100μF


- ★ Visual null indicator
- ★ Power factor check
- ★ Electrolytic leakage test
- ★ Battery operated

**£8.7.3**

including battery.  
 Post and Packing 3/6 extra.  
 H.P. 40/- deposit and 24/- monthly.



S.A.E. for full technical leaflets

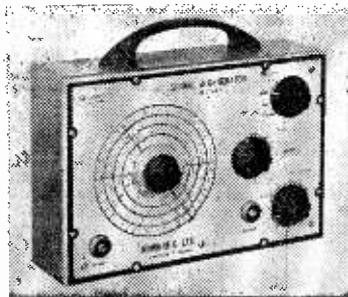

Wide-range Transistorised  
**SIGNAL GENERATOR—Model 27**  
 Range 150 Kc/s to 350 Mc/s.

- ★ Accuracy better than 2%
- ★ Directly calibrated
- ★ Battery operated
- ★ Compact and light

**£9.12.3**


with test lead and battery.  
 Post and Packing 3/6 extra.  
 H.P. 48/- deposit and 27/- monthly.

Trade and Export Enquiries Invited

**NOMBREX LTD.** Instruments Division 73

ESTUARY HOUSE, CAMPERDOWN TERRACE  
 EXMOUTH, DEVON. Phone: 3515.

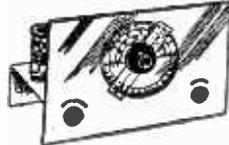
**LISTEN TO THE WORLD on TELSTAR our I-VALVE SHORT WAVE RADIO**



Receives speech and music from all over the world. Price includes valve and one coil covering 40-100 metres. Can be extended to cover 10-100 metres. Can be converted to 2 or 3 valve and all-mains speaker use. Total Building Costs **35/-** P. & P. 2/-.

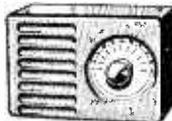**R.C.S. TRANSISTORISED TAPE TUNER**

Wonderful reproduction of all your favourite programmes. Covers full medium wave band. Special circuit incorporating ferrite rod aerial and tuning condenser gives COMPLETE STATION SEPARATION. Attractive case size 3 1/2 x 2 1/2 in. deep. NO EXTERNAL AERIAL OR EARTH REQUIRED. Chassis and components colour coded for easy construction. All parts supplied with step by step instructions.



ONLY **25/-** P. & P. 2/-.  
 (VT3 battery 2/6 extra).

**THE R.C.S. PERSONAL SET For Private Listening**



An amazing little set, with built-in ferrite rod aerial bringing in medium wave at wonderful volume. Sturdy case. Size only 2 1/2 x 3 1/2 x 1 1/2 in. Fits into the palm of the hand. Drilled chassis colour coded for easy assembly. Total Building Costs (including earpiece) **30/-** P. & P. 2/-.

**R.C.S. CRYSTAL RECEIVER**

Covering medium wave band. Ideal for the beginner! All components including case. **8/6** P. & P. (Suitable headphones 9/6). Easily converted to 1-transistor or 2-transistor receiver.



All parts available separately. Send S.A.E. for free layout plans and parts lists of any of the above sets.

**R.C.S. PRODUCTS (RADIO) LTD.**

11 Oliver Rd., London, E.17. (Mail Order only)  
 Export Trade enquiries invited

## ERSIN MULTICORE SOLDERS

for a first class joint every time

Wherever precision soldering is essential, manufacturers, engineers and handymen rely on MULTICORE. There's a MULTICORE SOLDER just made for the job you have in hand. Here are some of them.

**THE NEW HANDY DISPENSER**

Easy to find in the tool box—simple to use. The solder is in a continuous coil which can be used direct from the handy free-standing dispenser—in fact, it is virtually a third hand for those tricky soldering jobs. Containing 15 feet 5-core 18 s.w.g. Ersin Multicore Savbit alloy. **2/6**



**PRINTED CIRCUIT & TRANSISTOR SOLDER**

Designed for soldering High Temperature sensitive components. Plastic re-usable reel contains 250 feet of 60/40 High Tin Quality 22 S.W.G. ERSIN MULTICORE SOLDER with 5-cores of non-corrosive flux. Ask for Size 10. **15/-** each.

For small users, the same specification is available on a 2/6d. reel.



**BIB WIRE STRIPPER AND CUTTER**

Strips insulation without nicking wire, cuts wire cleanly, splits extruding flux. **3/6** each



**MULTICORE SOLDERS LTD**

MULTICORE WORKS, NEMEL HEMPSTEAD, HERTS. (BOXMOOR 3638)

# T N

# rade ews

### Sound Effects Tapes

THE recently issued series of Castle sound effects records is now available as pre-recorded tapes. These tapes have been made of all the Castle records so far released and will be made of future discs.

The tapes are recorded direct from the masters at a speed of 3½ in.p.s., full track, and are accommodated on standard 3in. spools. This means the tapes can be replayed on all standard full track, half track or quarter track recorders, irrespective of track selection.

The tapes have the same coding as the records and follow exactly the effects and timings of the respective discs. The price of a tape is 18s. 6d.

Produced by F. C. Judd (Sound Recording) Limited, the tapes are distributed by *Recorded Tuition Limited, 174 Maybank Road, South Woodford, London, E.18.*



The Hammarlund HQ-170A triple conversion receiver.

### Triple Conversion Receiver

IN the familiar style of Hammarlund receivers, the HQ-170A makes its first appearance with claims of improved stability and overall performance on previous models. The many refinements of this new receiver make for optimum reception of ssb/c.w. and a.m./mcw, and vernier tuning, adjustable band-width, etc, help to make the HQ-170A an attractive set for the amateur.

The 17-valve circuit incorporates an automatic noise limiter and allows triple conversion for i.f. frequencies of 3035kc/s, 455kc/s and 60kc/s. The circuit front end provides tuning over the 6, 10, 15, 20, 40, 80 and 160m bands. *K. W. Electronics Limited, Vanguard Works, 1 Heath Street, Dartford, Kent,* are the U.K. agents for Hammarlund equipment.

### Transistor Tester

A NEW portable transistor tester is being marketed by the Irongate (M.O.) Company Limited, which is capable of accurately testing both general and power transistors and diodes. The tester (model AT-1) is battery-powered and measures only 7½ in. x 4 in. x 3 in.


A large, easy-to-read meter is a feature of the panel of this instrument, as well as the quick-release spring sockets for holding the component under test. The price of the model AT-1 is £9 17s. 6d. and the makers are the *Irongate (M.O.) Company Limited, Irongate Wharf Road, Praed Street, London, W.2.*

### Radio-telephone

ONE of the new radio-telephone equipments recently announced by Rank-Bush Murphy Electronics, is the "Rambler". This is a portable receiver/transmitter designed for two-way communication between fixed or mobile stations.

It employs a fully transistorised circuit and takes its power from a small mercury battery, which provides more than 50 hours operating life.

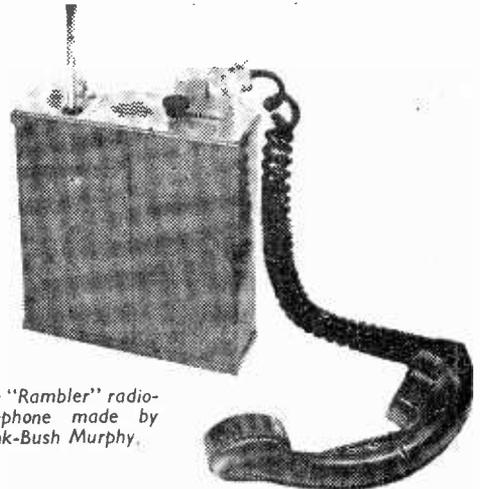Amplitude modulation is employed in the Rambler, which operates in the range 50 to 140Mc/s. A small built-in loudspeaker and telescopic aerial are features of the equipment and provision is made for using either a microphone or lightweight handset. The price of the Rambler is 80 guineas and the manufacturers are *Rank-Bush Murphy Limited, Bessemer Road, Welwyn Garden City, Hertfordshire.*




The "Rambler" radio-telephone made by Rank-Bush Murphy.
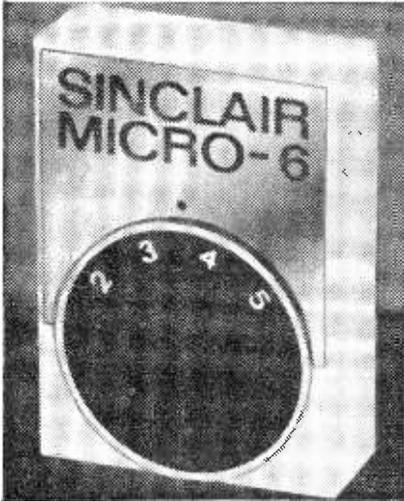
### Miniature Transistor Receiver

A NEW six-stage transistor receiver kit has been announced by Sinclair Radionics Limited. Known as the "Micro-Six", this receiver, when fully assembled, measures only  $1\frac{1}{4}$  in. x  $1\frac{3}{10}$  in. x  $\frac{1}{2}$  in.

Power to operate the receiver is provided by a mercury cell which will last several months. Using an internal ferrite rod aerial, the receiver tunes over the medium wave band and delivers its output through an earpiece which comes complete with the kit of parts. Micro-miniature components and a printed circuit are employed in the construction, and building instructions accompany each kit. The Micro-Six may be obtained from *Sinclair Radionics Limited, 69 Histon Road, Cambridge*, at a cost of 59s. 6d.



This illustration shows, larger than life-size, the Sinclair Micro-Six.



A new portable tape recorder made by Standard.

### Mains Battery Tape Recorder

THE Unicorder model SR-F61RT is a portable tape recorder made by Standard which will operate from a mains supply or from ten torch-type batteries. Despite its small size—8 in. x  $6\frac{1}{2}$  in. x 3 in.—the Unicorder features two-speed, twin-track operation. The recorder takes  $3\frac{1}{2}$  in. tape spools and incorporates most of the facilities of standard-size machines. One unusual feature, however, is its facility for remote-control operation.

The SR-F61RT employs two internal loudspeakers, each 2½ in. in diameter, although a socket for an extension speaker is provided. It is possible to operate the recorder in its leather-carrying case which is included in the price—36 guineas. The U.K. agents for Standard products are *Denham and Morley Limited, Denmore House, 173/175 Cleveland Street, London, W.1.*

## NEED AN AERIAL FOR BBC-2?

Then get the March issue of PRACTICAL TELEVISION which carries a special article giving designs for u.h.f. arrays.

In every issue of *Practical Television*:

- ★ Regular articles on servicing and fault finding
- ★ Monthly commentary and hints on TV DX reception
- ★ Articles on amateur TV transmitting
- ★ Colour TV explained plus other informative articles

Also in the March issue **A Vision Transmitter/Receiver for the 70cm ham band.**

**MAKE SURE OF YOUR COPY OUT ON FEBRUARY 21st 2/-**

# PORTABLE TRANSISTOR RADIOS

## BACKED BY SUPER AFTER SALES SERVICE

### ROAMER SEVEN Mk III

● 9 stages—7 transistors and 2 diodes

Covers Medium and Long Waves, Trawler Band and two Short Waves to approx. 17 metres. Push-pull output for room filling volume from rich toned heavy duty 5in. speaker. Ferrite rod aerial for M & L waves and telescopic aerial for S Waves. Air spaced ganged tuning condenser ensures wonderful stations selection. Simulated hide case with gilt trim and shoulder and hand straps. Size 9 x 7 x 4in. approx. The perfect portable and the ideal car radio. (Uses PP9 battery available anywhere.)


### 5 WAVEBAND PORTABLE OR CAR RADIO

Amazing performance and specification

Total cost of parts now only

**£5.19.6** P. & P. 5/6

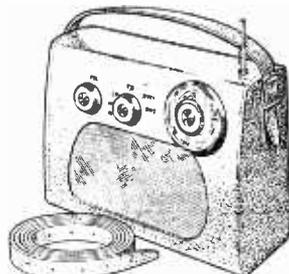Parts Price List and easy build plans 3/-




### TRANSONA FIVE

"Home, Light, & Fun... Lots of good volume..." G.P., Durham.

● 7 stages—5 transistors and 2 diodes.

Fully tunable over medium and Long Waves and Trawler Band. Incorporates Ferrite rod aerial, tuning condenser, volume control, new type fine tone super dynamic speaker, etc. Attractive case. Size 6 1/2 x 4 x 1 1/2in. with red speaker grille. (Uses 1289 battery available anywhere.)

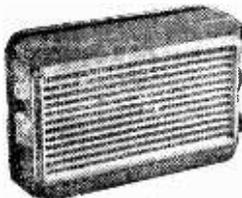Total cost of all parts now only **42/6** P. & P. 3/6.



Parts Price List and easy build plans 2/-

### TRANSONA SIX


NEW!

● 8 stages—6 transistors and 2 diodes.

This is a top performance receiver covering full Medium and Long Waves and Trawler Band. High-grade powerful magnet 3in. speaker makes listening a pleasure. Push-pull transistors for ample power. Ferrite rod aerial. Many stations listed in one evening including Luxembourg loud and clear. Attractive case in grey with red grille. Size 6 1/2 x 4 x 1 1/2in. (Uses PP4 battery available anywhere). (Carrying strap 2/- ex.)

Total cost of all parts now only **59/6** P. & P. 3/6

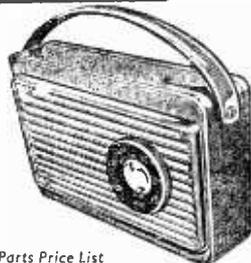Parts Price List and easy build plans 1/6




### SUPER SEVEN

● 9 stages—7 transistors and 2 diodes

Covers Medium and Long Waves and Trawler band. The ideal radio, can be fitted with carrying strap for outdoor use. Completely portable—has built in aerial for wonderful reception. Push-pull output, 3in. speaker (will drive larger speaker). Size 7 1/2 x 5 1/2 x 1 1/2in. (Uses PP6 battery available anywhere.)

Total cost of all parts now only **£3.19.6** P. & P. 3/6

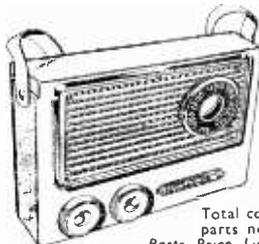Parts Price List and easy build plans 2/-



### MELODY SIX

"... amazed at volume and performance... has really come up to my expectations." S.G., Stockton-on-Tees


FREE! Miniature Earpiece, plug and socket (value 9/6) and details of conversion to private listening.

● 8 Stages—6 transistors and 2 diodes.

Our latest completely portable transistor radio covering medium and long waves. Incorporates pre-tagged circuit board, 3in. heavy duty speaker, top grade transistors, volume control, tuning condenser, wave change slide switch, sensitive tin. ferrite rod aerial. Push-pull output. Wonderful reception of B.B.C. Home and Light, 208 and many Continental stations. Handsome leather-look pocket size case, only 6 1/2 x 3 1/2 x 1 1/2in. approx. with gilt speaker grille and supplied with hand and shoulder straps.

Total cost of all parts now only **£4.9.6** P. & P. 3/-

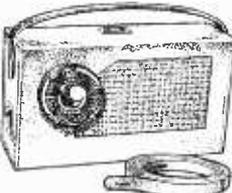Parts Price List and easy build plans 2/-



### ROAMER SIX


FREE! Miniature Earpiece, plug and socket (value 9/6) and details of conversion to private listening.

● 8 stages—6 transistors and 2 diodes.

Listen to stations half a world away with this 5 waveband portable. Tunable on Medium and Long waves, Trawler Band and two Short Waves. Sensitive ferrite rod aerial and telescopic aerial for short waves. Top grade transistors, 3-inch speaker, handsome case with gilt fittings. Size 6 1/2 x 4 1/2 x 1 1/2in.

Total cost of all parts now only **£4.19.6** P.&P.3/6.

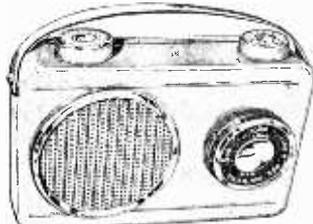Parts Price List and easy build plans 3/-




### POCKET FIVE

● 7 stages—5 transistors and 2 diodes.

Covers Medium and Long Waves and Trawler Band, a feature usually found in only the most expensive radios. On test Home, Light, Luxembourg and many Continental stations were received loud and clear. Designed round supersensitive Ferrite Rod Aerial and fine tone 2 1/2in. moving coil speaker, built into attractive black case with red speaker grille. Size 5 1/2 x 1 1/2 x 3 1/2in. (Uses 1289 battery available anywhere.)

Total cost of all parts now only **42/6** P. & P. 3/-

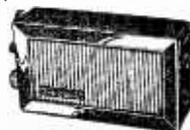Parts Price List and easy build plans 1/6



All components used in our receivers may be purchased separately if desired. Parts price lists and easy build plans supplied free with sets of parts or available separately at prices stated.


## Radio Exchange Co.

27 HARPUR STREET, BEDFORD  
Phone 2367 Opposite Co-op. 9 to 5 p.m. 10-1 p.m. Sats.

# WEYRAD

## 6-TRANSISTOR 2-WAVE SUPERHET RECEIVER MODIFICATIONS NOW AVAILABLE FOR 500 mW OUTPUT

|  |              |
|--|--------------|
| <b>ROD AERIAL—RA2W</b>   |              |
| 6 in. long, 3/8 in. diameter, connections to tags on Coils. For 208pF tuning capacity. Complete with Car Aerial Coil ... .. 12/6 |              |
| <b>OSCILLATOR COIL—P50/1AC</b>   |              |
| M.W. covered with 176pF tuning capacity, L.W. by extra padder ... .. 5/4   |              |
| <b>I.F. TRANSFORMERS</b>   |              |
| 1st and 2nd Stage—P50/2CC ... .. 5/7   | (2 required) |
| 3rd Stage—P50/3CC ... .. 6/-   |              |
| <b>DRIVER TRANSFORMER—LFDT4</b> ... .. 9/6   |              |
| <b>OUTPUT TRANSFORMER—OPT1</b> ... .. 10/6   |              |
| <b>PRINTED CIRCUIT—PCA1</b> ... .. 9/6   |              |

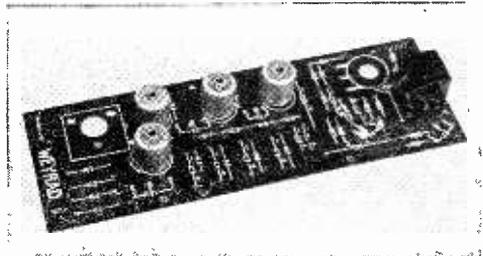

In response to many requests we have redesigned the output stages to give 500 mW and to enable a standard 3 ohm Speaker to be used. Full details of the simple changes are given on a separate leaflet available on receipt of stamp.

|   |
|---|
| <b>CONSTRUCTOR'S BOOKLET WITH FULL DETAILS</b> ... .. 2/-   |
| <b>TRANSISTOR A.F. AMPLIFIER TYPE A.F.1—LOW IMPEDANCE INPUT, 3-TRANSISTOR, 500 mW OUTPUT, FULLY ASSEMBLED WITH VOLUME CONTROL</b> ... .. 63/6 |

**WEYMOUTH RADIO MANUFACTURING CO., LTD.**  
**REGENT FACTORY, SCHOOL STREET,**  
**WEYMOUTH, DORSET**

**THE  
 PEMBRIDGE  
 COLLEGE  
 OF ELECTRONICS  
 PROVIDES TRAINING  
 IN RADIO  
 AND TELEVISION**

### FULL-TIME COLLEGE COURSE IN RADIO AND TELEVISION

Our Course has now been extended to sixteen months' duration to include theoretical and practical instruction on transistor television receivers, U.H.F. television receivers and colour television.

Next course commences 15th April, 1964.

This Course is recognised by the Radio Trades Examination Board (R.T.E.B.) for the Radio and Television Servicing Certificate examinations.

Provides excellent practical experience on valve and transistor radio receivers and all well-known makes of television receivers.

To: **The Pembridge College of Electronics (Dept. P11)**  
**34a Hereford Road, London, W.2.**

Please send, without obligation, details of the Full-time Course in Radio and Television.

Name \_\_\_\_\_

Address \_\_\_\_\_

# Short Wave

## One

A simple, dry battery operated receiver, suitable for the beginner.

BY C. J. MITCHELL

THIS is a simple one-valve regenerative receiver which any beginner should be capable of building. The circuitry is quite standard but a novel form of construction is incorporated. This little set produced quite remarkable results when used with a short aerial (22ft.). Even Radio Australia has been heard at reasonable strength at the author's location (Epsom, Surrey).

The receiver is built on a standard two ounce tobacco tin with removable lid (not hinged type). This tin is extremely easy to make soldered connections to, and even a lightweight iron will suffice. The lid is removed and bolted to the upturned tin. The front can be painted, if desired.

### Major Components

The coil used in the prototype was the Osmor type SWQ2, which covers 3.5Mc/s to 12Mc/s. Alternatively the type SWQ1 which covers 11Mc/s to 30Mc/s could be used. These coils have adjustable dust cores which will slightly vary the band covered.

An acorn triode type 955 was used, however an acorn pentode type 954 with anode, grid 3 and grid 2 strapped together would also be suitable. The author managed to purchase a valve base for the 955. This particular item may prove difficult to obtain, but it is stocked by some surplus dealers. On the other hand it is possible to solder


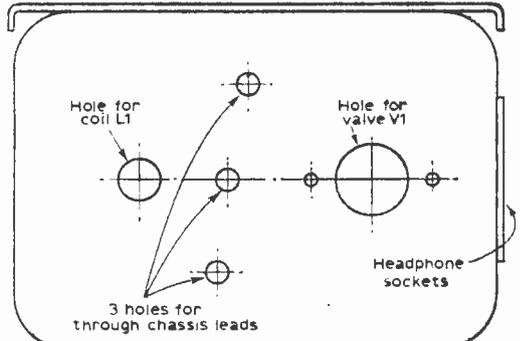


Fig. 2a (above): The tobacco tin chassis; b (below): the tin lid used as the front panel.

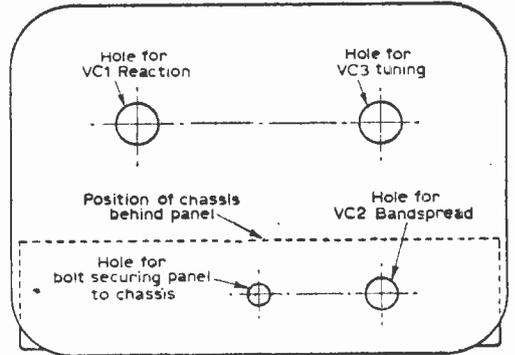

the wires directly to the pins of the valve, and this is the obvious remedy.

Tuning is performed by means of a 100pF solid dielectric variable capacitor VC3. A 300pF small solid dielectric capacitor VC1 suffices for reaction, and for bandspread a 25pF panel mounting trimmer VC2 was used.

This receiver is powered by dry batteries, and is especially convenient for beginners. Two 3V cycle headlamp batteries will be required for the heater and a 90V high tension radio battery for the h.t.

The two 3V batteries are connected in series (positive to negative) to obtain a 6V supply.

Beginners should note that in its existing form this receiver is not suitable for use with an a.c. mains power unit.

### Construction

Having drilled the chassis and lid, as shown in Fig. 2, bolt the front panel in position and mount the three controls—tuning, reaction and bandspread.

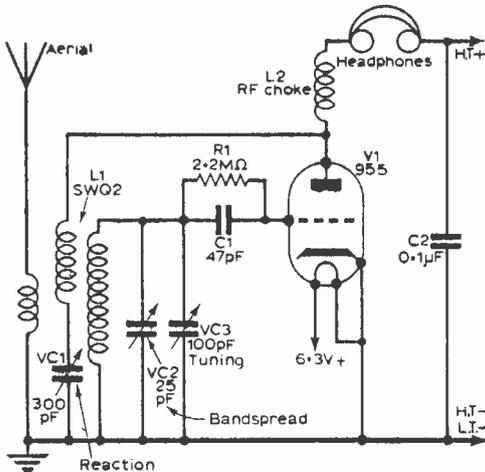


Fig. 1: The circuit of the receiver.

### COMPONENTS LIST

- R1 2.2MΩ carbon
- C1 47pF ceramic or mica
- C2 0.1μF paper
- VC1 300pF solid dielectric variable
- VC2 25pF air dielectric trimmer
- VC3 100pF solid dielectric variable
- L1 Coil 3.5 to 12 Mc/s (Osmor SWQ2)
- L2 R.F. choke 2.5mH
- V1 955 or 954

Next mount the valve holder (if used), using suitable stand-off insulators if necessary. Then follow with the headphone socket, coil and grommet for power lead.

Now start on the soldering by earthing the moving vanes of all the variable capacitors, the cathode and one side of the valve heater, and also the appropriate tags of the coil. Next connect up the tuning, bandspread and reaction capacitors to their respective parts of the coil; then wire the grid leak resistor R1 and capacitor C1 and finally the r.f. choke and the power lead.

**Operating**

Connect an aerial and earth to the set and plug in a pair of medium or high impedance headphones.

Connect up to the l.t. and h.t. batteries and switch on. Adjust the reaction control until the set is *almost* into oscillation then rotate the tuning controls to bring in the signals. The bandspread capacitor is used for fine tuning. The reaction


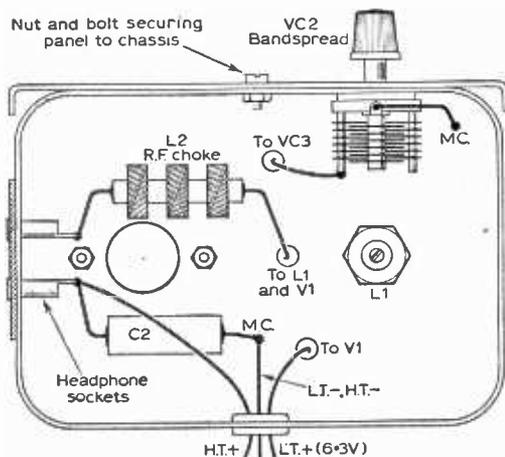


Fig. 3a (above): The underside wiring; b (below): the wiring on the top of the chassis.

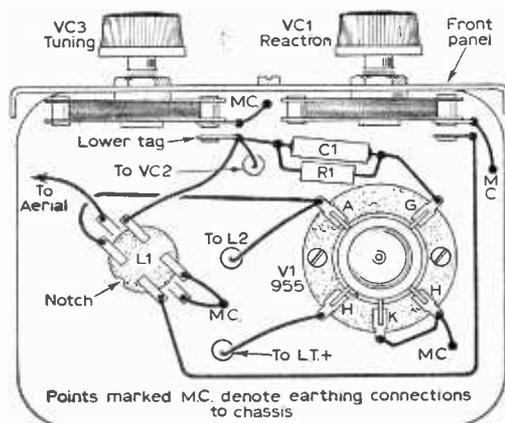

Tobacco tin used as chassis and lid as front panel

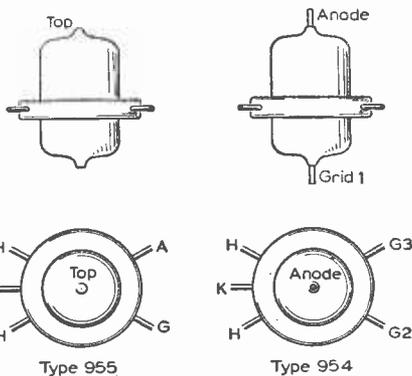


Fig. 4: Connections to two types of acorn valves which may be used in this set.

control will need adjusting occasionally during the tuning as its optimum setting varies from one end of the scale to the other.

If no signals are heard then it is most likely that the connections to the reaction coil need reversing.

Using the reaction control carefully so that the receiver is always operating at the point of maximum sensitivity, it should be possible to receive signals from all parts of the world.

**A MUST FOR HOME HANDYMEN!**

**PRACTICAL HOUSEHOLDER**  
**SPRING ANNUAL 1964**

An Up-to-the-Minute Guide to Improvements in the Home



Special sections on:  
Exterior Improvements, Interior Decoration, Modernisation, Kitchens, Concreting and Brickwork, Furniture and Woodworking, Garden Furniture, Home Workshop.

**ORDER NOW! OUT FEBRUARY 28th—2/6**

To ..... (Name of Newsagent)

Please reserve/deliver my copy of the PRACTICAL HOUSEHOLDER SPRING ANNUAL 1964 (2/6), on sale February 28th.

Name .....

Address .....

● **SCOOP!** Hi-Fi 10 watt Amplifier £7.10.0 complete. Carr. 5/6. Branded manufacturer's model (cartoned). Very latest high efficiency valves. Push-pull output. Separate bass-treble controls, dual input for "mike", 3 or 15 ohm speakers. High sensitivity. Fully guaranteed.

● **SCOOP!** Baby Alarm or Intercomm. Kit. Complete set of parts with diagram, etc. Housed in Two beautiful moulded plastic cabinets of pleasing design. High sensitivity. Fully Controllable. Only 4 gns., carr. 5/6, or Assembled Ready for Use, £5.

● **SCOOP!** 17in., £11; 14in. £7. 12 months' fully written guarantee. Channels for all areas. Insured. Carr. 14in. 20/-; 17in. 30/-. These TV sets are ex-Rental, already well maintained. We regun tubes ourselves. Valves and parts are manufacturers' surpluses. ALL SETS have a written guarantee covering valves, tubes and components.

● **SCOOP!** Set of 6 Transistors and Diode. Brand new. Beautifully Boxed. Complete with Circuit, 15/0, P.P. 1/6.

# DO IT YOURSELF

## Build a Record Player and save Pounds The Cheapest Way The L.K. Way

Famous Autochanger or Single Player Units supplied with brand new, two-tone, de-luxe portable cabinets, 17 x 15 x 8 1/2 in. Strong carrying handle, gilt finish clips and hinges as used by famous make for 22 gn. model. Ready cut out motor board, 14 x 13 1/2 in. Front baffle 7 x 4 in. High flux loudspeaker and 3 watt amplifier. Amplifier ready built on metal chassis with output transformer, volume and tone controls. All items fit together perfectly. Special instructions enable assembly in 30 minutes. Only 5 wires to join. 12 months' written guarantee. Available separately or package deals as below.

### L.K. PRICES FOR COMPLETE KITS:

|  |          |      |     |
|--|----------|------|-----|
| <b>Autochanger Kits as above</b>                             |          |      |     |
| B.S.R. U.A.14  | £11.0.0  | P.P. | 5/6 |
| Garrard Autoslim   | £11.10.0 | P.P. | 5/6 |
| <b>Single Player Kits as above</b>                           |          |      |     |
| Garrard S.R.P.10   | £10.15.0 | P.P. | 5/6 |
| E.M.I. Auto-stop   | £11.0.0  | P.P. | 5/6 |
| Individual Prices for those who wish to purchase separately. |          |      |     |
| Record Player Cabinet with Cut-out Board                     | £2.15.0  | P.P. | 3/6 |
| Amplifier with 7 x 4 in. speaker                             | £3.10.0  | P.P. | 2/6 |
| <b>Auto-changers</b>   |          |      |     |
| B.S.R. U.A.14  | £5.10.0  | P.P. | 5/6 |
| Garrard Auto Slim  | £6.15.0  | P.P. | 4/6 |
| <b>Single Players</b>  |          |      |     |
| E.M.I. Auto-Stop   | £5.7.8   | P.P. | 4/6 |
| Garrard S.R.P.10   | £5.7.8   | P.P. | 4/6 |
| E.M.I. Separate Pick-up                                      | £5.5.0   | P.P. | 3/6 |
| <b>Transcription Units—Stereo—Mono</b>                       |          |      |     |
| Garrard 4 H.F.   | £16.0.0  | P.P. | 5/- |
| Phillips A.G.10/16   | £12.0.0  | P.P. | 5/- |
| Garrard A.T.6  | £10.5.0  | P.P. | 5/- |

● **SCOOP!** 10in. speakers by W. B. of Mansfield. A beautiful H-Fi Speaker in maker's cartons. Fully guaranteed. Our price, 42/-, P.P. 1/10.

● **SCOOP!** A First-Class 2 Wave-Band Superhet Chassis, 6 Transistor. By world famous manufacturer. Fully built, tested, aligned, boxed, guaranteed. Our price only £4.4.0. Suitable speaker 35 ohms, 10/6. A cabinet can be supplied for 22/6 only. Hurry while stocks last. P.P. 2/3.

● **SCOOP!** Record Player Amplifier. 2 valve, A.C. mains. Output 3 watts. Ready built, tested, guaranteed. Complete with valves, output transformer and speaker. Our price 50/- only. Product of national manufacturer. P.P. 1/6.

● **SCOOP!** B.S.R. U.A.14 Auto-changers. Brand new and wired for stereo. Note OUR price £5.10.0 only. P.P. 5/6.

● **SCOOP!** A Short Wave Receiver. Speech and music from all over the world, covering 40-100 metres. Conversion for 10-100 metres if required. This is not a toy but a receiver fully built, tested and guaranteed. Our price 62/-, in kit form 42/-, P.P. 2/3.

● **SCOOP!** Personal Radio. Built in ferrite rod aerial. Medium wave only. Wonderful volume. Size 2 1/2 x 3 1/2 x 3 1/2 in. Fits in the palm of the hand. In kit form only, 32/- complete in every detail. P.P. 1/9.

● **SCOOP!** Top Quality Recording Tape (1/- per tape, 6 or more post free).

|                  |      |                   |      |
|------------------|------|-------------------|------|
| 4in. 600ft.      | 12/6 | 5 1/2 in. 1200ft. | 17/6 |
| 5in. 600ft.      | 12/6 | 5 1/2 in. 1800ft. | 35/- |
| 5 1/2 in. 900ft. | 17/- | 7in. 1200ft.      | 17/6 |
| 5in. 1200ft.     | 30/- | 7in. 1800ft.      | 26/6 |
| 5 1/2 in. 350ft. | 15/- | 7 1/2 in. 2400ft. | 45/- |

A reduction of 6d. per reel for all Hospitals and Professional Users. This tape is fully guaranteed.

● **SCOOP!** The Wiltonia—Pre-assembled for only 75/-, P.P. 2/6 extra. Real call carrying case and earpiece included free of charge. Six transistor superhet miniature personal radio. Ferrite rod aerial. I.F. frequency 470 Kc/s. 3in. speaker. Printed circuit 2 1/2 x 3 1/2 in. Slow motion drive. In beautiful plastic case, size 4 x 2 1/2 x 1 1/2 in. In order to ensure perfect results the Wiltonia is supplied to you with R.F. and I.F. stages. Driver and output stages ready built with all compartments mounted on the printed circuit. The Wiltonia pre-assembled can be completed in half an hour with no soldering and tools whatsoever.

● **SCOOP!** 1964 Radiogram Chassis, 3 wave bands, 5 valves.

|                      |                             |
|----------------------|-----------------------------|
| S.W. 16M to 50M.     | Five Valves.                |
| M.W. 200M. to 350M.  | Latest Mullard.             |
| L.W. 800M. to 2000M. | E.C.H.81. E.F.89. F.B.C.81. |
|                      | E.L.84. E.Z.80.             |

A.C. 200-250 v. 4-way switch, short to medium. 1/gram ferrite aerial A.V.C. Negative feedback, 3 ohm output, 5 watts, glass dial, horizontal wording, size 13in. x 4in. Aligned and calibrated. Isolated chassis, size 13 1/2 in. x 9 1/2 in. x 5 1/2 in. deep. Our price £8.15.0. Carr. 4/6 extra.

● **SCOOP!** "NOTON" Seven Transistor 2 wave-band. Brand new design. For car radio and general purpose giving 1 watt output when connected to any standard 3 ohm speaker. All parts available separately. Size 7 x 5 x 1 1/2 in. Building plans 2/6 (free with kit).

This versatile units has been designed to fit into a variety of cases, and all components down to control knobs and battery clips are supplied together with clear illustrated plans. It gives a superb performance with dozens of stations including Luxembourg when connected to a 9-volt battery and speaker. Only £8.15.0 complete. P.P. 2/6.

● **SCOOP!** "NOTON" Mains Power Pack Kit for Transistor Radios. Boosts and generally extends life of old batteries. In attractive two-tone plastic case. Assembled in one hour. Miniature size, 4 x 2 x 1 1/2 in. Normal output 5 v. 100mA. Full mains transformer. Full wave germanium diodes. Cartridge fuse. Runs radio direct from mains. Complete kit with plans, 33/-, P.P. 1/6. Ready Assembled 42/-, P.P. 1/6.

● **SCOOP!** Transistor Tape Recorder. The best obtainable, by very famous manufacturer. Brand new, boxed and guaranteed. Reduced from £12 kits., Now £7.10.0, complete with microphone, tape, batteries and operational booklet. P.P. 3/6. Features four transistor push-pull amplifier, two motors, single switch operation, pause, speed, wind/rewind, record/pauseback. Can be used in any position, indoor or outdoor.

Remember we are Agents for the Full Range of Brittamer Radiogram Chassis with full stock always available. PLEASE SEND FOR DETAILS.

# ★ L.K. ELECTRONICS ★

27 OLD BOND STREET, LONDON, W.1.

The cheapest, the best, the quickest service

If not advertised it is still in stock

MAIL ORDER ONLY — TO THIS ADDRESS PLEASE

# IMPROVED

Modern styling in light grey with legible black engraving.

Constructed to withstand adverse climatic conditions.

Ever ready case, including leads, prods and clips.

Improved internal assemblies.

Re-styled scale plate for easy rapid reading. 2 basic scales, each 2.5 inches in length.

New standards of accuracy, using an individual calibrated scale plate. d.c. ranges 2.25% f.s.d. a.c. ranges 2.75% f.s.d.

Available accessories include a 2500V d.c. multiplier and 5, 10 and 25A shunts for d.c. current measurement.

## STANDARDS OF



### Mk 4

# MULTIMINOR

# ACCURACY AND RELIABILITY

The Mk. 4 MULTIMINOR is an entirely new version of this famous Avo instrument and supersedes all previous models. It is styled on modern lines, with new high standards of accuracy, improved internal assemblies, and incorporating pancimatic properties.

The instrument is supplied in an attractive black carrying case, which also houses a pair of leads with interchangeable prods and clips, and an instruction booklet. It is packed in an attractive display carton. Robust real leather cases are available, if required, in two sizes, one to take the instrument with leads, clips and prods, and the other to house these and also a high voltage multiplier and a d.c. shunt.

D.C. Current: 100 $\mu$ A f.s.d. — 1A f.s.d. in 5 ranges  
A.C. Voltage: 10V f.s.d. — 1,000V f.s.d. in 5 ranges  
D.C. Voltage: 2.5V f.s.d. — 1,000V f.s.d. in 6 ranges  
D.C. Millivolt range: 0 — 100mV f.s.d.

Resistance: 0.2 M $\Omega$  in 2 ranges using 1.5V cell  
Sensitivity: 10,000 $\Omega$ /V on a.c. Voltage ranges  
1,000 $\Omega$ /V on d.c. Voltage ranges

● For full details of this great new pocket-size instrument, write for descriptive leaflet.

**AVO LTD**

AVOCET HOUSE - 92-96 VAUXHALL BRIDGE ROAD - LONDON, S.W.1 - Tel.: Victoria 3404

**M**  
group

MM17

# HOUSING HI-FI?

This is one of a wide range of cabinets for every hi-fi purpose—speakers, equipment, tapes and records. Soundly designed, superbly finished, sensibly priced. Send for illustrated catalogue and name of local stockist.



Lowline Four: 29 gns.

Now available in Teak at a little extra cost

**RECORD HOUSING**

(Dept. P.W.3), Brook Road, London N22.  
Telephone: BOWes Park 7487/8



**LOWEST EVER PRICES**



|                          |          |     |      |
|--------------------------|----------|-----|------|
| 5in. Std.                | 600ft.   | ... | 8/6  |
| 7in. Std.                | 1,200ft. | ... | 12/6 |
| 5in. L.P.                | 900ft.   | ... | 10/- |
| 5 $\frac{1}{2}$ in. L.P. | 1,200ft. | ... | 12/6 |
| 7in. L.P.                | 1,800ft. | ... | 15/- |
| 4in. D.P.                | 600ft.   | ... | 9/-  |
| 5in. D.P.                | 1,200ft. | ... | 15/- |
| 5 $\frac{1}{2}$ in. D.P. | 1,800ft. | ... | 22/6 |
| 7in. D.P.                | 2,400ft. | ... | 25/- |

**SPECIAL!! "LAFAYETTE"**

7in. Std. 1,200ft., 12/6  
7in. L.P. 1,800ft., 15/-  
7in. D.P. 2,400ft., 25/-

**EXCLUSIVE TO GEE'S "AMERICAN SHAMROCK"**

Professional quality  
7in. L.P. 1,800ft., 15/6

**SPARE SPOOLS, 4in.,**  
5in., 5 $\frac{1}{2}$ in., 2/- each;  
7in. 2/6; 8 $\frac{1}{2}$ in. 5/-.

Obtainable only from—

**GEE BROS. (RADIO) LTD., Dept. P.W.**  
15 LITTLE NEWPORT ST. LONDON W.C.2  
(Adjoining Leicester Sq. Tube) GER 6794/1453

**"GEE'S" ACCESSORY KIT.** 1 "BIB" splicer, 1 splicing Tape, 3 Leader Tapes (3 colours), 10 Retaining Clips. Packed in plastic container. PRICE 32/6. While stocks last.

**GOLLARO "STUDIO" TAPE TRANSCRIBERS.** Brand new in original cartons. 3 speeds. 1 $\frac{1}{2}$ , 3 $\frac{1}{2}$ , 7 $\frac{1}{2}$  i.p.s. 3 motors, digital counter, etc. Complete with instructions and fixings. A.C. 200/250 v. operation. **SPECIAL PRICE 10 GNS.** Carr. paid.

P. & P. 2/- per order (over £3 post free). Other types available. S.A.F. for Bumper Tape and Accessories list.

Special discounts for quantities.

# TEST GEAR accessories

## Part 2

BY C. MACKAY

CONTINUED FROM PAGE 931 OF THE FEBRUARY ISSUE

**L**AST month, the construction details for a dummy aerial unit were given. This month the construction of a diode detector probe will be described and some of the applications of such a probe discussed.

### THE DIODE PROBE

The circuit diagram of this diode detector probe is given in Fig. 4, and the unit was built inside a Denco coil screening can as was the dummy aerial.

The probe section (Fig. 5) consists of a length of 16s.w.g. copper wire inside an equal length of

2mm "Systoflex" insulated sleeving. Both were then placed inside a 4in. length of copper tubing of 6B.A. inside diameter size. A metal wire retainer was used for clamping the lower end (as tightly as possible) and a right-angled bracket is used to bolt this whole sub-assembly to the underside of the screw-on lid so that only the probe part projects through a suitably drilled hole in the centre of the lid (Fig. 6).

A solder tag should be fitted under both sides of the fixing bolt so that a short length of flex with a crocodile clip can be used for making a "chassis" connection, and for an internal "chassis" connection.


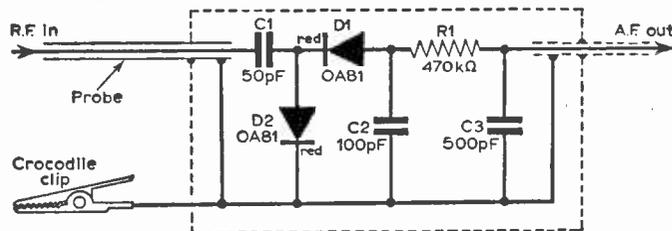


Fig. 4 (above): The circuit of the diode probe unit.


Fig. 5 (right): Details of the probe.

Fig. 6 (below): Construction of the probe unit.

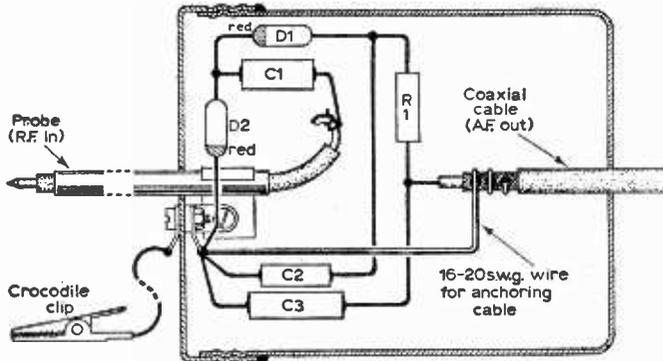
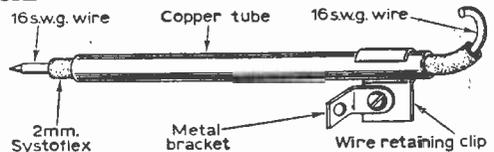
### WIRING UP

Originally a tag strip was used in a manner similar to that used for the dummy aerial, but since things became rather crowded, it was decided that the tagstrip was too much of a liability. Because of this the components were made completely self supporting on their connecting wires as shown in Fig. 6.



Next a hole was drilled in the centre of the base of the can to take the connecting cable. This cable is connected as shown in Fig. 6 and is supported by the cable outer conductor.

The detector probe is used for removing the high-frequency carrier from a modulated wave, and, as will be explained, it can be used for signal tracing in receivers, tracing resonance curves by means of a wobulator and an oscilloscope, and for the testing of modulators.

USE WITH A SIGNAL TRACER

One of the quickest and easiest methods of tracing a fault in a receiver is by means of the "signal-tracer" method.

In this method, only the working part of the receiver next to the aerial is used, the rest of the set being by-passed and temporarily replaced by the signal tracer. Thus, if the fault occurs in an audio stage, only another audio amplifier is required. The audio amplifier need not be very elaborate, and a simple two-valve plus rectifier type is perfectly sufficient. The circuit of a suitable signal tracer is shown in Fig. 7 with component values. Note that all input leads should be completely screened in order to avoid any hum pick-up.

USING THE PROBE

If the fault occurs in a stage handling carrier or intermediate frequency signals, the reader might think that it would be necessary to provide a tuned high-frequency amplifier. This would be, however, rather costly, and instead, the signal is detected and fed into an audio amplifier. This is where the diode detector probe is used.

COMPONENTS LIST FOR DIODE PROBE UNIT

- R1 470kΩ carbon 1W
- C1 50pF ceramic
- C2 100pF ceramic
- C3 500pF ceramic
- D1 OA81 Mullard
- D2 OA81 Mullard

Miscellaneous:

16 s.w.g. wire (about 6 inches). 2 mm Systoflex (about 6 inches). 4 inches of copper (or brass) tubing to take 6 B.A. studding. 2 yards coaxial cable. 2 feet flex. 1 crocodile clip. 1 screening can (Denco (Clacton) Ltd.). 1 wire retaining clip. 1 Meccano right-angled bracket.

number of faults have somehow occurred simultaneously, they can all be systematically detected and cured.

WARNING

If any tests are going to be made on "live" chassis sets, care should be taken to ensure that the chassis is connected to the "neutral" side of the mains, and that all test instruments are isolated from the mains and also are NOT earthed.

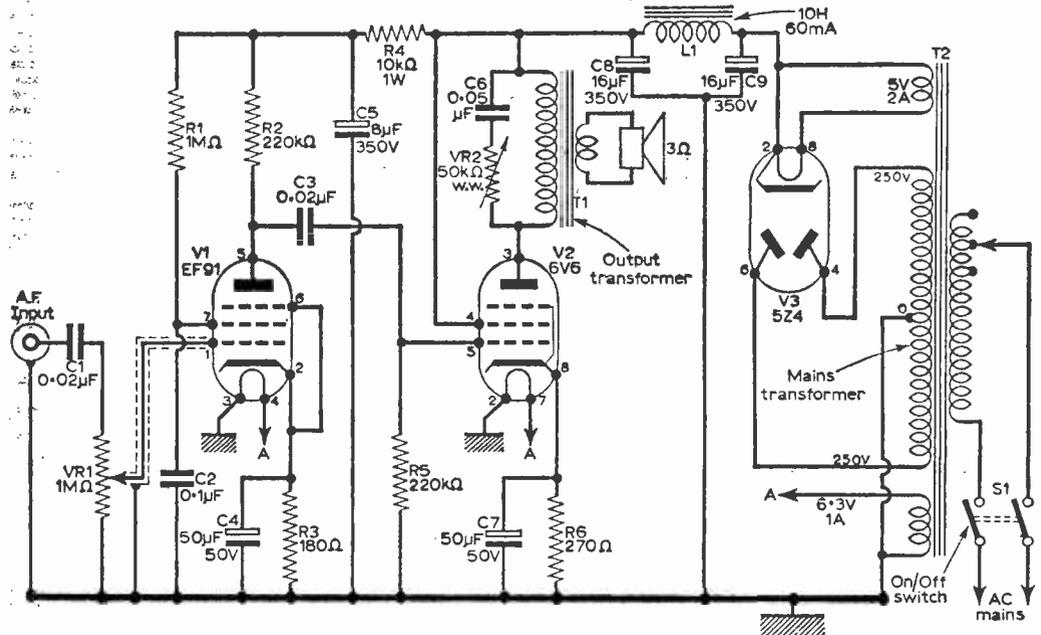


Fig. 7: The circuit of an inexpensive signal tracer.

The modulated carrier is fed into the probe, and the audio output is taken to the amplifier. If the audio signal is heard clearly in the loudspeaker, then that part of the receiver between the aerial and the point where the tapping was taken for the probe must obviously be working properly. By applying this method to various points in the receiver, the faulty region may be quickly found, and the fault eliminated. It can be seen that if a

WOBBULATION

Wobulation is the varying of the frequency of an oscillator above and below its basic frequency at some definite rate. This frequency modulated signal is fed into the apparatus to be examined. The output is detected and rectified by means of the detector probe unit and fed into the Y-amplifier of an oscilloscope, while the

# BRITISH NATIONAL RADIO SCHOOL

ESTABLISHED  
25 YEARS

announces a —

RESIDENT: MR. J. SYKES, M.I.E.E.,  
M. BRIT. I.R.E. G85RK

## COMPLETE DO-IT-YOURSELF TRAINING PROGRAMME IN RADIO • TELEVISION • ELECTRONICS

The demand for good Electronic Engineers is increasing almost daily throughout the world. Electronics is now the most rapidly expanding of all industries with its applications reaching into almost every sphere of human activity. If you are looking for a new career with new opportunities—then now is the time to choose—Electronics. If you are already employed in this field—then now is the moment to seek higher qualifications to secure the top jobs which are waiting to be filled. Most of all, the great potential of electronic development means unlimited scope for the future and will ensure a secure occupation for you—unlikely to be affected by possible future recessions in other industries.

The British National Radio School has had 25 years' experience of HOME STUDY coaching for students wishing to master the fascinating subjects of Electronics—whether the object be career or as a hobby or new interest. The School is entirely independent and specialises ONLY in the teaching of electronic subjects. It employs only fully qualified staff to conduct and supervise each individual course taken by a student and it is this close and personal contact between Tutor and Student which we believe makes possible the successful completion of a course of study.

A special feature of our system is that all courses start right from the beginning and no previous knowledge or experience is necessary or expected. Training is carried out in easy step-by-step stages using the most modern methods of tuition. The great advantage of the home study method is that it provides a complete self-contained course giving everything needed for the subject concerned and enabling work to be done in the comfort of one's own home and over any period of time desired.

What about YOUR OWN BUSINESS IN ELECTRONICS? We have very many students who enrol with us solely to enable them to start up their own business—most commonly in the servicing of radio and television receivers. The large number of such receivers and other electronic apparatus now in use means that there is a continuous and growing demand for people and firms to service such equipment when it proves faulty. Our practical electronics course with equipment as described briefly below is designed to give the complete beginner adequate practical knowledge for this servicing work. It requires practically no capital to start a Servicing business—all the assets are in the skill and knowledge of the owner and there is never any shortage of work—usually far too much! Fees and earnings are high and expansion rapid and you have the satisfaction of working on your own and only for yourself.

Of course, you may only be interested in Electronics as a HOBBY or you may simply wish to widen your knowledge of technical subjects. The spread of electronics today means that it is very useful to know the basic facts that lie behind so many technical processes and equipment. It can be very useful to know how radio and TV receivers and transmitters work; how remote control systems operate (as for model boats, etc.); how 'Hi-Fi' sound equipment should be installed and operated; how transistors really work; what computers are all about and so on...

Many of our students pursue their hobby in a very active way by qualifying as an Amateur Radio Operator or 'Ham'. We have a special and most successful course for the G.P.O. Licence.

Finally we extend a special welcome to students from overseas—they enrol with us from almost every country in the world and present-day fast air mail services mean that we can coach them as efficiently and quickly as if they lived in the U.K.

### EXAMINATION COURSES

- CITY & GUILDS TELECOM. TECHNICIANS CERT.
- CITY & GUILDS FULL TECHNOLOGICAL CERT.
- A.M.Brit.I.R.E. EXAMINATION.
- RADIO AMATEURS' LICENCE EXAMINATION.
- P.M.G. CERTIFICATES FOR RADIO OPERATORS.
- R.T.E.B. SERVICING CERTIFICATES.

### OTHER COURSES

- MATHEMATICS
- TELEVISION
- TRANSISTORS
- SERVO-MECHANISMS
- COMPUTERS
- RADAR & NAVIGATIONAL AIDS

### NEW PRACTICAL & EXPERIMENTAL 'LEARN-WHILST-YOU-BUILD-IT' COURSE IN RADIO & T/V SERVICING

This is a new complete experimental course comprising a mixture of theory and practical work using a very full range of electronic components and apparatus. Starting right from the beginning—or at a later stage if needed—the course enables the student to build up all the basic electronic circuits—amplifier; oscillator; rectifier; detector; etc.—and finally to the design, construction, testing and servicing of a latest design fully transistorised receiver using nine transistors and covering long and medium wave and TWO SHORT WAVEBANDS plus VHF/FM reception. It is of real luxury quality throughout—operates from a 9v. battery and can be used anywhere in the world. Every present-day technique in circuitry is covered and the course also includes multi-range test meter; signal generator and oscilloscope. By the end of the course the student will be able to deal with any type of servicing work with confidence and will also have a very useful workshop of equipment. Nearly 100 interesting and absorbing EXPERIMENTS are carried out enabling anyone to gain full mastery of electronics.

## POST NOW FOR FREE BROCHURE

TO: BRITISH NATIONAL RADIO SCHOOL, RADIO HOUSE, READING, BERKS.

Please send details of your Courses, without any obligation, to:—

NAME.....

ADDRESS.....

I am interested in.....course above.

Block Caps  
Please

PW 3/64



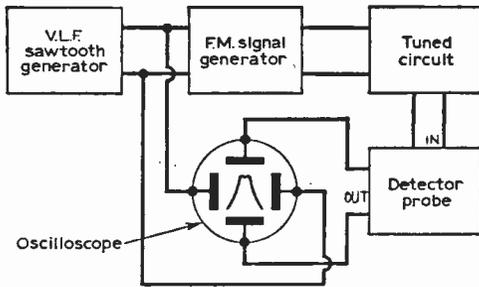


Fig. 8a (above): Using the probe in conjunction with an oscilloscope.

Fig. 8b (right): A graph of attenuation against frequency—see text.


modulating signal is fed into the X-amplifier. Thus a trace is produced on the screen of the oscilloscope which gives a graph of amplification (or attenuation) against frequency. (See Figs. 8a and 8b.)

**TESTING MODULATORS**

The detector probe may be used for testing modulators as follows.

The output of the modulator is rectified and detected by the probe unit, and the output is fed into an audio amplifier. The modulating signal should be faithfully reproduced in the loudspeaker if the modulation is working correctly. Care should be taken not to overload the probe.

*Part 3 appears next month.*

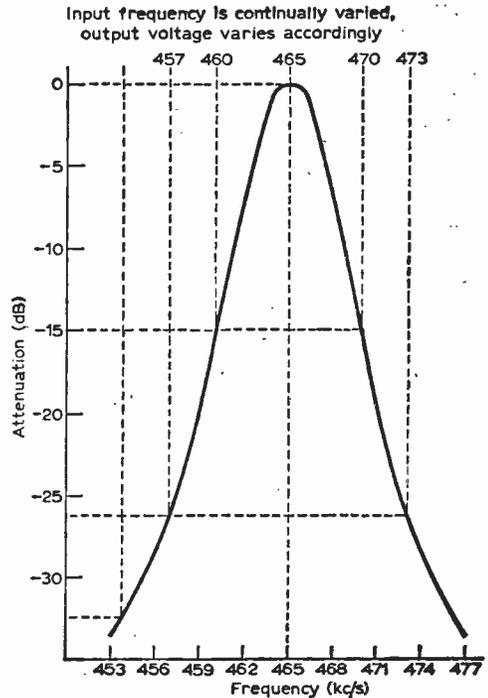

**Audio Testing with the P.W. "Sixteen"**

*—continued from page 1047*

This h.f. bias is supplied by an oscillator, which may be a dual-purpose valve, or section of a valve, doubling as an output stage for playback.

Modern tape recorders also use this circuit as a source of current for erasure. The erase head is fundamentally a power device, and the current is the important factor. The multimeter, switched to the 250V a.c. range, will give an indication of bias by connecting it between chassis and the "live" side of the head connections, on the medium and high impedance heads used on the majority of popular tape recorders.

The actual reading of voltage is not important unless specification tests are being made—in which case a valve-voltmeter is usually stipulated. Fortunately, on the majority of models, it is sufficient to check that a.c. is present: only on the semi-professional machine will an adjustment for frequency be found, and the preset resistor or concentric capacitor found on many other popular models is simply set for near maximum amplitude of bias.

**Low Impedance Heads**

On machines that employ low impedance heads it will be difficult to obtain a satisfactory indication, and a better method of assessing efficiency is to read the current. The model "Sixteen" Multi-

range Meter is not adapted for a.c. current readings—they are seldom required—and a quite simple way of overcoming this is to insert a small resistor, 10-100Ω in the earthy lead of the head being tested and measure the a.c. voltage developed across it.

It is sometimes necessary to check the phase connection of a matched input, such as a stereo tape head or pick-up crystal. This can occur when a four-connection head, for example, has been disconnected and there is some doubt about tag sequence. A meter between the "live"—non-earthly—terminals of the output of each channel should indicate zero volts when phase is correct. In practice there may be some small standing voltage.

To sum up—each user of the "Sixteen" Multirange Meter will have a number of applications to add to the foregoing. A meter is an "individual" instrument, and a good one is invaluable.

**PURCHASING THE COMPONENTS**

All components required for building the PRACTICAL WIRELESS "Sixteen" Multirange Meter should be obtainable from radio component dealers. If any difficulty is experienced in obtaining these items readers are advised to contact Lasky's Radio, 207 Edgware Road, London W.2, who are the main distributors for PRACTICAL WIRELESS "Sixteen" components.

It is again emphasised that the various manufacturers concerned do not normally supply direct to individuals.

# CLUB

## COVENTRY AMATEUR RADIO SOCIETY

Hon. Sec.: A. J. Wilkes, G3PQQ, 141 Overslade Crescent, Coundon, Coventry, Warwickshire.

To encourage members to attend meetings more frequently, the Society's committee has organised an interesting and varied programme of lectures and events for 1964. Added incentive for members to make regular attendances is provided by the new and more desirable club room at the T.A. headquarters, where the Society has permission to erect whatever aerials it requires and has already taken advantage of this by erecting 2m and 160m aerials.

## DERBY AND DISTRICT AMATEUR RADIO SOCIETY

Hon. Sec.: F. C. Ward, G2CVV, 5 Uplands Avenue, Littleover, Derby.

At the open evening of January 8th, the Treasurer collected members' subscriptions for 1964. A film show was given for the meeting of January 15th and a week later, some "Practical Hints and Tips" were given for beginners and junior members of the Society.

The Annual General Meeting was held on February 5th, when a new committee was elected for the forthcoming year.

## GOSPORT COMMUNITY ASSOCIATION AMATEUR RADIO CLUB

Hon. Sec.: R. E. Daw, Troodos, 34 Anglesey Road, Alverstoke, Hampshire.

R.A.E. lectures are currently being given at the Monday evening meetings of this Club and beginners to the hobby can be sure of receiving assistance with their constructional projects from the more learned members.

At most meetings the Club transmitter is on the air.

## GRAFTON RADIO SOCIETY

Hon. Sec.: A. E. Bristow, 37 Tyndale Mansions, Upper Street, London N.1.

All future "Worked All London Town" (WALT) awards—which are made available by this Society—will be made under revised rules. Certificates are awarded to radio amateurs throughout the world who can provide proof of two-way communication—in compliance with set rules—with London amateurs in 65 of the 118 London Postal Districts, and because of the recent increase in mobile activity, a limit on the number of JM contacts acceptable in applicants' lists of contacts claimed has been introduced.

Copies of the revised rules may be obtained on request, from the Society secretary.

## INTERNATIONAL SHORT WAVE CLUB

Sec.: Arthur E. Bear, 100 Adams Gardens Estate, London S.E.16.

As its title suggests, this Society has members in many countries throughout the world and it is pointed out that any readers interested in joining the ISWC can obtain a copy of the Club's news bulletin (International Short Wave Radio) on application to the above address.

## MID-WARWICKSHIRE AMATEUR RADIO SOCIETY

Hon. Sec.: T. Inkester, 13 Dormer Place, Leamington Spa, Warwickshire.

The first event in this Society's calendar of meetings for 1964, was the Annual General Meeting held on January 13th.

## MITCHAM AND DISTRICT RADIO SOCIETY

Hon. Sec.: A. Thurlay, 50 Bruce Road, Mitcham, Surrey.

Recent attendance figures have given promise of continued growth for this Society in 1964.

January's meeting was devoted to a junk sale which was held on the 17th.

## NORTHERN HEIGHTS AMATEUR RADIO SOCIETY

Hon. Sec.: A. Robinson, G3MDW, Candy Cabin, Ogden, Halifax.

This Society's committee met on January 15th, which for other members remained as an informal evening. The film show which was given on January 29th was well received by all present.

February began with a ragweek meeting on the 5th.

## READING AMATEUR RADIO CLUB

Hon. Sec.: R. G. Nash, G3EJA, "Peacehaven", 9 Holybrook Road, Reading, Berkshire.

The Dinner and Social evening held on January 18th was enjoyed by the many members who attended this, the first Club event of 1964.

Another important event in January was the Annual General Meeting held on the 25th. At this meeting the Treasurer's report and a review of the Club's activities during the past year were

given. This meeting also saw the election of a new committee of Club officers and a discussion of the programme of events for 1964.

## RODING BOYS' SOCIETY: RADIO SECTION

R. Marchant, 154 Essex Road, London E.10.

This Society's active efforts to increase membership have been aided by demonstrations at recent exhibitions. As well as a number of new members, this Society has recently obtained its own call-sign: G5SRF.

## SPEN VALLEY AMATEUR RADIO SOCIETY

Hon. Sec.: N. Pride, 100 Raikes Lane, Birstall, Leeds.

The display of members' gear, which was held on January 9th, was attended by members of the Leeds, Bradford, Halifax and Northern Heights Radio Societies. Later in the month, members heard a talk on "Modern Methods of Weather Forecasting", which had been arranged by the Met. Office of the Church Fenton R.A.F. Station.

On February 4th a group of members paid a visit to the Halifax Radio Society and on February 6th, Mr. W. Dougherty lectured on "Noise Problems."

## STOURBRIDGE AND DISTRICT AMATEUR RADIO SOCIETY

Hon. Sec.: R. A. G. MacIntosh, 50 Field Lane, Oldswinford, Stourbridge, Worcestershire.

The January meeting of this Society was held on the 14th when Mr. G. Woollenden gave the first of two talks on v.h.f. and hi-fi entitled "Hi-fi Without Tears."

## UXBRIDGE RADIO SOCIETY

Hon. Sec.: A. Duell, "Treetops", Bakers Wood, Denham, Buckinghamshire.

The first meeting of the New Year was held on January 6th, but the main meeting of the month—the Annual General Meeting—was held on the 13th.

## WEST KENT AMATEUR RADIO SOCIETY

R. Trevitt, 28 Dales Avenue, Tunbridge Wells, Kent.

The meeting for January 10th was devoted to discussions on audio subjects with demonstrations of some audio equipment. On January 24th, members heard the third of H. F. Richards' talks under the title "100 Years of Wireless", his topic this time being "Broadcasting and TV."

The Society was represented in the Affiliated Societies' Contest (February 1st and 2nd) by a number of members who turned out to help with and operate the station.

## THE AMATEUR RADIO CLUB, BANGALORE

Post Box 53, Bangalore-1, India.

Any radio society might envy the record of the Amateur Radio Club of Bangalore, India, which although only three years old, has more than 100 members and claims to be the Country's leading society. The Club's membership includes many licensed amateurs and the Club station—VU2TT—is an active user of South India's amateur bands. It also boasts SWL and YL sections and has its own library.

As impressive as its rapid growth is the Club's quarterly magazine SIRAN (South India Radio Amateurs' Newsreel). This publication has the familiar duplicated style of many British society bulletins, but has the distinction of being eighteen foolscap pages in length and full of Club news, comments, letters, constructional articles, etc.: an admirable production for a completely amateur society.

The Amateur Radio Club, Bangalore is obviously going to continue to be an important factor in the spread of amateur radio in India and we wish it every success.

## HENRY'S RADIO LTD.

### Note to Customers

FOLLOWING a number of complaints concerning the non-delivery of goods ordered by post (due to non-arrival of correspondence) between November 10th and December 31st, the Post Office Special Investigation Department have since discovered, and dealt with, the cause of the losses.

Customers so affected are asked to claim for the loss of postal orders and re-order if necessary.

The Post Office and Henry's Radio Ltd. regret any inconvenience caused to customers by this unfortunate episode.

# HOME CONSTRUCTORS LOOK!



**THE SKYROVER**  
7 TRANSISTOR  
PORTABLE  
RECEIVER

**THE SKYROVER**  
De Luxe  
7 TRANSISTOR PORTABLE



**GENERAL SPECIFICATION FOR BOTH MODELS**

7 transistors and 2 diode superhet—6 waveband portable receiver, covering the full Medium Waveband (180-576 M) and Short Waveband (31-94 M) and in addition 4 separate switched Band Spread Ranges on 13M, 16M, 19M and 25M/bands—with manual Band Spread Tuning for accurate Station selection. I.F. frequency 470 Kc/s. Output 500 Mw. 5in. Ceramic Magnet P.M. Speaker. Telescopic and internal Ferrite Rod Aerial. All Mullard Transistors and Diodes. The coil pack and tuning heart is completely factory assembled, wired and tested. The remaining assembly can be completed in under three hours from our detailed and easy to follow instructions. Operates on four 1.5V Lorch batts. (U2 or equivalent).

**THE SKYROVER**, Individual Details—controls: Waveband Selector. Volume Control with on/off switch. Tuning Control with easy to read Dial Scale. In attractive plastic cabinet, size: 10 x 6½ x 3½in., with metal trim and carrying handle.

**THE SKYROVER De Luxe**, Tone Control Circuit is incorporated with separate Tone Control in addition to Volume and Tuning Controls and Waveband Selector. In sturdy wood cabinets, size: 11½ x 6½ x 3½in. covered in washable material with plastic trim and carrying handle. Also Car Aerial socket.

MAY BE BUILT FOR **£10.19.6**  
All Parts Sold Separately.

MAY BE BUILT FOR **£12.19.6**  
All Parts Sold Separately.

Circuit diagram and data for each set 2/6 extra, free if all parts bought. Four U2 batteries 2/8 extra. Four Leak-Proof Batteries 3/4 extra. Add 5/- P. & P. on each set.

**THE 'REALISTIC' 7**



A fully transistorised Portable Receiver made to the highest professional standards—is now available to the home constructor. Comprises 7 Mullard Trans. OC44, 2 OC45's, OC71, OC81D and 2 OC81's plus OA70 Crystal Diode. Delivers 350 milliwatt output to 4in. high flux speaker. —I.F. frequency 470 Kc/s.—fully tunable over medium and long wavebands. All components mounted on single printed circuit board, size 5½ x 5½in. Attractive two-tone plastic cabinet with carrying handle—size 7 x 10 x 3½in. with easy to read dial and socket for car and aerial, choice of Red/Grey, Blue/Grey or all Grey, complete with full instructions.  
MAY BE BUILT FOR **£5.19.6** All parts sold separately Battery 3/9 extra P. & P. 4/6 extra. (Circuit diagram 2/6, free if all parts bought.)



**THE 'SPRITE'**

A six transistor superhet Miniature Pocket Radio of Commercial Quality. Fully tunable over Long and Medium wavebands. Uses printed circuit and high sensitivity internal ferrite rod aerial. I.F. frequency 470 Kc/s. Transistors: 3-Philco 2067's, 2-Mullard OC81M, OC81D and OA90 diode, 3 inch speaker. Works on single PP3 battery, supplied with the complete RF and IF stages, driver and output stages, ready built and mounted on the printed circuit; for final assembly you have only to fit the wave-change switch, tuning condenser and drive, volume control, earphone socket and aerial rod. In very attractive plastic case, size 4 x 2½ x 1½in. **MAY BE BUILT FOR 79/6**  
All parts sold separately  
Real Calf Leather Case, wrist strap and Personal Earphone with case, and battery 12/6 extra. P. & P. 3/6 extra. (Data and instructions 2/6, free if all parts bought.)

**AND THE 'REALISTIC' 7 DE LUXE**

Now available, with the same specification as the standard model PLUS a re-styled superior wood cabinet covered in attractive washable materials, with chrome trim and carrying handle. AND a full vision circular tuning dial.  
**Only £1.0.0 extra** P. & P. etc. as Standard Model.

**READY BUILT BARGAINS!**

**2 TRANSISTOR POCKET RADIO**

Ready made as illustrated—complete with personal earpiece, telescopic aerial, battery and carrying case! Wonderful value and performance—full medium waveband coverage—built in 2½in. speaker gives full tone reproduction. Works on single PP3 9 v. battery. In attractive plastic case—size only 4 x 2½ x 1½in. All accessories included in the price.

**WIRECOMP'S 42/- POST PRICE COMPLETE FREE**

**ALSO 6 TRANSISTOR POCKET RADIO FULLY BUILT**

Wonderful performance. Tunable over full medium waveband. Built-in 2½in. speaker. In attractive plastic carrying case—size 4 x 2½ x 1½in. Operates on single PP3 9 v. battery. Supplied complete with personal earpiece, leather carrying case and battery.

**WIRECOMP'S 79/6 POST PRICE COMPLETE FREE**



**COLLARO STUDIO TAPE DECKS**

Latest model: 3 speed, 3 motors. Take 7in reels. Fitted with half-track heads. **WIRECOMP'S PRICE £10.10.0**  
New and Unused. Carriage and Packing 7/6.  
As above but fitted with the latest quarter-track heads. **WIRECOMP'S PRICE £13.19.6**  
Carriage and Packing 7/6.

**E.M.I. 4-SPD. RECORD PLAYER**

New, unused and individually boxed, fitted with lightweight pick-up with ACOS G.P. 73/2 stereo cartridge. Cabinet space required 13½ x 12½ x 4½in. A 9-inch metal turntable is fitted. For use on 200/250 volt A.C. mains, with Auto-stop. The stereo cartridge will play all types of Mono Records, 78's, L.P.'s etc., but if desired, a G.P. 87 L.P.7/8 Mono cartridge will be supplied in lieu of the G.P.73 at no difference in cost.



**WIRECOMP'S 79/6 P. & P. PRICE 3/6**

**CRYSTAL PICK-UP CARTRIDGES**

- MONO. All complete with Styl. Add 1/- P. & P.
- Type C.T.1. By well-known manfr., with 2 sapphire styl 9 6
  - Garrard Ceramic G.C.E.A. .... 15 0 Acos G.P.65/3 .. 15 0
  - Garrard Magnetic T.O.M.2. .... 15 0 Acos G.P.65/1 .. 17 0
  - Acos G.P.59 .....
  - STEREO Acostereo 73/1 with 2 sapphires .....
  - Acostereo 73/2 with diamond LP/Stereo and sapphire std. 29 6
  - Collaro type C Turnover with 2 sapphires .....
  - Collie S.C.I. Turnover, with 2 sapphires .....
  - Collie S.C.I. Turnover with diamond LP/Stereo and sapphire std. 25 0
  - Ronette Stereo O.V. Turnover with 2 sapphires .....
  - Ronette Stereo types 105 and 106 with 2 sapphires .....
  - Ronette Stereo types 105 and 106 with diamond LP/ Stereo and sapphire std. .... 39 6

**TAPE FAMOUS MAKE. FULLY GUARANTEED. AT RECORD LOW PRICES.**

- P.V.C. base on latest type plastic spools. New, perfect, boxed.
- 1,200ft. on 7in. spool. .... 12 6 850ft. on 5½in. spool. .... 11 0
- 1,800ft. on 7in. spool. .... 19 6 600ft. on 5in. spool. .... 8 6
- 1,200ft. on 5½in. spool. .... 15 0 225ft. on 3in. spool. .... 4 11
- 2,400ft. Double Play on 7in. spool .....

**WIRECOMP ELECTRONICS**

378 HARROW ROAD LONDON W9.

TEL: CUNNINGHAM 9530

Hours of business: 9 a.m. to 6 p.m. Open all day Saturday. Opposite Paddington General Hospital. Buses 18B and 36 pass the door.

# COULD THIS SMALL INVESTMENT BE THE KEY TO YOUR FUTURE SUCCESS?

**New Radio Training Course now available for 36/- complete!**

How can anyone afford to produce a course for 36/-? Here is the story behind this greatest value radio training and why you get it for so little!

We pictured the average student as an ambitious person, doing some wireless repair work, but needing more training, more practical knowledge to become an expert. We thought of men who just couldn't afford high priced correspondence courses like the four different ones we had for comparison purposes. The answer. Why not put the essential lessons, the sum and substance of practical radio training into manual form? This way we could cut selling expense, letter writing, sending one lesson at a time, cut the cost of tests that do not help learning in any case! Good idea? We thought so. Arrangements were then made with a highly qualified text book publisher who planned and worked out the whole idea, collected all essential up-to-date data, secured co-operation and assistance from leading manufacturers and tested the material on servicing engineers. In addition permission was obtained to use sections of a leading home-study course. Difficult parts were simplified and helpful examples worked out for easy understanding. New sections were added, some lessons enlarged, photographs and drawings obtained to make things easier.

The 22 practical lessons making up this course-manual are easy to follow and apply to actual radio jobs. Use this training to get ahead in radio and as an introduction to television. Radio facts that puzzled you will be quickly cleared up. You will find yourself doing radio repairs in minutes instead of hours—instantly finding faults and making needed adjustments.

Every new radio development of importance and thousands of time saving radio facts are packed into this complete course-manual. For example, there is a large lesson on servicing VHF/EM sets and another full lesson on audio amplifiers.

The course includes easy-to-follow, well illustrated sections on test equipment, circuits, car radio sets, alignment, use of the oscilloscope, and every other topic needed to be an expert in wireless repairing.

The lessons are easy to understand, practical, down to earth. You will enjoy every minute of your training. This could be the key to your future success! If you would like me to reserve a copy of the course for you, please clip the coupon right away.

Yours sincerely,

FRED G. SIMPER

P.S.—You must be convinced that this is the best value you have ever seen in radio training, otherwise you can return the course (or have your money refunded if sent with order) after you have examined it in your own home for a period of seven days.

P.P.S.—Send cash with order and get a 70-page Radio Fault Finding Book at no extra charge. This book covers Basic Fault Finding, Static Tests, Faults causing Distorted Reception, Hum and Noise, Instability, Intermittent Faults, FM Receivers, Transistors and Printed Circuits.

### FREE TRIAL OFFER!

Terms only 5/- per week if you wish.

To FRED G. SIMPER, s/o Sim-Tech Technical Books, Dept. XR.1, West End, Southampton, Hants.

Please send your RADIO COURSE for a full seven days' free trial. If not delighted I may return the course post-paid without further obligation on my part, otherwise I will pay cash price of 37/6 (this is 1/6 postage) OR 5/- weekly until 37/6 plus 2/6 service charge, total 40/- is paid.

Tick here if enclosing full price of 37/6 (same 7-day money back guarantee). NOTE: PLEASE SEND ME THE FREE 70-PAGE (GIFT BOOK ON RADIO FAULT FINDING as described above. Overseas customers please send full amount (including Ireland).


Name .....

Address .....

City..... County.....

## Irongate (M.O.) LTD

### CONSTANT VOLTAGE TRANSFORMER

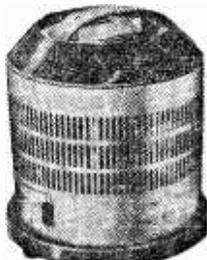


240 & 110 Volts DUAL VOLTAGE MAINS STABILIZER

Will cut out mains interference with TV, Hi-Fi, stereo, tape recorder or any Laboratory equipment by providing perfectly stabilized voltage supply.

★ PERFECT PICTURE & RADIO RECEPTION

- ★ PREVENTS DAMAGE BY POWER SURGES AND CUTS
  - ★ JUST PLUGS IN
  - ★ ATTRACTIVE METAL CASE 8in. HIGH
  - ★ CAPACITY 250VA
  - ★ OUTPUT ACCURACY ±1%
- Ex stock. Carriage free. ONLY **£11.10.0**

### TRANSISTOR TESTER

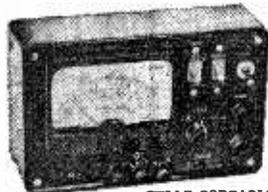

FULLY PORTABLE

Measurement Ranges: Ico (Icbo) and the reverse current of diodes. PNP and NPN—0—50µA (1µA per scale). POWER—0—1mA (200µA per scale). 50-200 (5 per scale). Bias current—(1mA on PNP and NPN), (5µA on POWER).

α.9-0.995 (from β— $\frac{\alpha}{1-\alpha}$ )  
 Terminals: Spring Sockets and Screw Terminals.  
 Meter: 4in. 50µA moving coil. Size and Weight: 8in. x 4in. x 3in., 2½lb. Powered by pen-cells.

MODEL AT-1 ONLY **£9.17.6**  
 Post Free.

### TRANSISTORIZED MEGOHMMETER

BATTERY OPERATED. 500v.—1,000 Megohms.

This most advanced insulation and conductivity tester incorporates these outstanding advantages:

- ★ One-handed push-button operation.
- ★ 4in. A.C.-D.C. Voltmeter with fine Zero adjustment.
- ★ Stable and accurate readings.
- ★ Easy-to-read scaling.
- ★ Metal case 7in. x 5in. x 3in.

Complete with probes and carrying case. Post Free. ONLY **22 Gns.**

ALL ITEMS EX-STOCK

## Irongate (M.O.) LTD

Dept. (P.W.S) IRONGATE WHARF RD., FRAED ST., LONDON, W.2. ADDING TON 2288/4

# JAG ELECTRONIC CABINET MAKERS LTD

2c CHURCH STREET Slough, Bucks.

## CABINETS

We make a complete range of cabinets or will make to your own specification.

**GRAM CABINETS**  
 For single player ..... **£2**  
 For autochanger ..... **£3**  
 P. & P. 5/- per cabinet.

**SPEAKER CABINETS**  
 With sloping fronts, all colours. 5in. 9/-, 6in. 10/6, 8in. 15/-, 10in. 18/-, 12in. 25/- P. & P. up to 8in. 2/6, 10in. 3/-, 12in. 3/6.

Trade enquiries invited for cabinets.

### LINE OUTPUT TRANSFORMERS AND SCAN COILS

FERGUSON: 204, 206, 306 ..... 17/6 ea.  
 PYE: V4, V14, VT17 ..... 17/6 ea.  
 EKCO: 221, 231 ..... 35/- ea.  
 P. & P. 3/6 on each of above L.O.P.T.s.

**FIREBALL TURRET TUNERS**  
 All ex-equipment .. 17/6 ea, P. & P. 3/-

### RECORD PLAYER AMPLIFIER AND SPEAKER

A compact 2w. amplifier with tone and vol. controls. Complete with valves (PCL82 and PY82), on board with o/p transformer and quality 6in speaker. Crisp reproduction! absolutely ready to play. ONLY **39/6**. P. & P. 2/6.

**SPEAKERS**, ex-equipment. 5in. 5/-, 7 x 4in. 7/6, 8in. 7/6. P. & P. 2/- ea.

### 6 TRANSISTOR PORTABLES

A first class, 6 transistor receiver with printed ckt., 3in. speaker, and car aerial socket. Full med. & long wave coverage, with vol. on/off, tuning and wave change controls. Housed in attractive cabinet covered with pastel coloured leathercloth, and complete with carrying handle and gilt trim. A Real Ready to Play Bargain! ONLY 7 gns. (inc. P./Tax) plus 2/- P. & P.

### VALUES

| SURPLUS or EX-EQUIPMENT |     |       |      |       |      |
|-------------------------|-----|-------|------|-------|------|
| EB91                    | 2/- | PCF80 | 4/6  | UCC84 | 7/6  |
| EBF80                   | 4/6 | PCL82 | 4/6  | UCF80 | 7/6  |
| EBF89                   | 5/- | PCL83 | 5/-  | UF42  | 2/6  |
| ECC81                   | 3/6 | PCL84 | 6/6  | GC9   | 10/- |
| ECC82                   | 3/6 | PL33  | 7/-  | 6F1   | 3/-  |
| ECC83                   | 4/- | PL36  | 10/- | 6F12  | 2/-  |
| ECC84                   | 5/- | PL38  | 10/- | 6F13  | 5/-  |
| ECF80                   | 4/6 | PL8   | 6/-  | 6F14  | 5/-  |
| ECF82                   | 5/- | PL82  | 4/6  | 6F15  | 6/-  |
| ECH35                   | 6/- | PL83  | 5/-  | 6L1   | 7/-  |
| ECH42                   | 6/- | PY31  | 6/6  | 6L18  | 6/-  |
| ECL80                   | 4/- | PY32  | 7/6  | 6P25  | 5/-  |
| ECL82                   | 6/- | PY33  | 7/6  | 6P28  | 8/-  |
| EF80                    | 2/- | PY80  | 3/6  | 10C1  | 10/- |
| EF85                    | 4/6 | PY81  | 3/6  | 10C2  | 10/- |
| EF91                    | 1/6 | PY82  | 3/6  | 10F1  | 3/-  |
| EL33                    | 5/- | PY83  | 6/-  | 10P13 | 6/6  |
| EL84                    | 4/6 | PZ30  | 7/-  | 10P14 | 6/3  |
| EY51                    | 3/- | U24   | 6/-  | 20D1  | 4/-  |
| EY86                    | 4/6 | U25   | 6/-  | 20F2  | 6/-  |
| EZ80                    | 4/- | U26   | 6/-  | 20L1  | 8/-  |
| EZ81                    | 4/6 | U191  | 7/-  | 20P1  | 7/-  |
| GZ32                    | 5/- | U90   | 9/-  | 20P3  | 7/6  |
| KT33C                   | 4/- | U801  | 14/- | 20P4  | 12/- |
| KT36                    | 7/- | UAF42 | 5/-  | 20P5  | 7/6  |
| PCC84                   | 4/6 | UBC41 | 5/-  | 30P4  | 7/-  |

Many other types available Post 6d per valve. All enquiries S.A.E. please TERMS: C.W.O.



# LETTERS TO THE EDITOR

Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying commercial or surplus equipment. We cannot supply alternative details for receivers described in these pages. **WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE.** If a postal reply is required a stamped and addressed envelope must be enclosed with the coupon from page iii of the cover.

The Editor does not necessarily agree with the opinions expressed by his correspondents

## DECEPTIVE VOLTAGE MEASUREMENTS

**SIR.**—There must be many high resistance meters (20,000 $\Omega$ /V or more) now in use by amateurs and, of course, they are particularly suited for measuring voltages in high resistance circuits. However, when it is necessary to determine the voltage of a small dry battery, a lower resistance meter is preferable, as this is likely to give a more exact indication of the condition of the battery.

A high resistance meter will show the correct voltage, if the battery is new, with a low internal resistance; but when the battery is partially or nearly exhausted, the voltage registered will be higher than that obtained under ordinary working conditions.

As an example, a nearly exhausted 3V battery gave a reading of about 2.5V on a high resistance meter, but with a lower resistance meter, the voltage was shown to be only a fraction of 1V. This was due to the fact that it only requires a minute current to operate the high resistance meter, and a battery tested by it may be passed as being up to standard when it is actually of no practical use.—**H. IVOR JENKINS** (Bridgend, Glamorganshire).

## TAPE ACCESSORIES

**SIR.**—I should like to pass on a useful tip regarding broken drive belts of tape recorders. A suitable replacement for such a drive belt, if a new one is not available, can be manufactured by neatly cutting the wrist end off a rubber household glove.

This will prove to be a very serviceable substitute and one which I fitted to my tape recorder last May has so far not slipped nor stretched as was the tendency of the original belt. — **R. W. CRAIG** (Bexley, Kent).

## CHROME TAPE SCREENING AGAIN

**SIR.**—Mr. Evans ought really to have checked his facts before writing his letter (December issue) in which he refutes a previous suggestion that chrome tape could be used for screening wires. This tape is, admittedly, made of plastic, but the chrome finish is given by a thin coating of aluminium deposited on the tape under vacuum. The coating is electrically continuous and exactly the same type of coating is used in the manufacture of capacitors.

There is, therefore, no reason why chrome self-

adhesive tape should not be used for screening purposes, provided the practical difficulty of connecting the aluminium to earth (the coating is sandwiched between the body of the tape and the adhesive layer) can be overcome. — **C. E. A. SWINDIN** (Wick, Gloucestershire).

## A LACK OF COURTESY HERE

**SIR.**—On a number of occasions I have replied to requests for back numbers of P.W. appearing on the Letters to the Editor page, and I would like to inform you of some of the results of my efforts to help other readers.

One recipient in Glasgow returned the issue I had sent saying he was over-supplied; another returned two copies a week later saying he no longer needed them and a third returned the copies informing me that he had received what he wanted a month previously through a request he had placed in another magazine!

I have done my best to help these readers and have spent a couple of shillings on postage without recompense. After this I think I shall keep my copies of P.W. to myself and let those who are interested *buy* the magazine, rather than *borrow* it. — **W. W. PERRIN** (Penarth, Glamorganshire).

## CONVERTING CONVERT

**SIR.**—Radio construction has been my hobby for about three years and from the pages of your magazine I have built several pieces of equipment which have, on the whole, operated well. In common with most other constructors I know, the first step I make in building any unit is to collect all the components required. Next the chassis has to be drilled, the components mounted and wired up, any necessary adjustments made and finally a cabinet built. Now your excellent publication provides detailed instructions through all of these stages for each piece of equipment described and although it may provide a good deal of satisfaction when finished, the thought that it was necessary to follow step-by-step plans somewhat dampens the spirit when the latest box-of-tricks is demonstrated before admiring friends. To design one's own equipment would provide an answer to this frustration, but for myself, at least, this presented too many problems. I have, however, struck upon an outlet for my whims which I recommend to other readers who now and again feel the need for independence.

The idea is by no means new, for radio amateurs

have been relying on it to provide their equipment for many years. I refer to the conversion of second-hand commercial and service equipment. For the ham, ex-government equipment is a boon, but for those, like myself, merely seeking amusement from repairs and modifications, it has many disadvantages when it comes to tracing information on which the constructor may base his experiments. Far more satisfaction can be obtained, in my opinion, from second-hand television and radio receivers, radiograms and record players, which may be obtained in their hundreds for ridiculous prices, some in working order. I have bought magnificent specimens of equipment selling for a few pounds in good working order, their only fault being their age, and I have enjoyed many happy hours repairing and converting such equipment, with no feeling of "cheating" by having all the information to hand.—D. G. JENKINS (Guildford, Surrey).

*Sir—I would be grateful if any reader could sell or loan me . . .*

. . . the issues of P.W. giving mains conversion details of the No. 19 set.—T. E. JONES, Red Cow Inn, Penybryn, Wrexham, Denbighshire.

. . . the circuit of the CR.100 communications receiver.—W. EDMONDSON, Arundale, Barrington Road, Letchworth, Hertfordshire.

. . . the manual or any information on the Eddy-stone model B.34 receiver.—Yap Pah Tho, c/o Ministry of Education, Federal House, Kuala Lumpur, Malaysia.

. . . the August and September 1959 issues of P.W.—F. GRIFFIN, 8 Speke Road, Speke, Liverpool 24.

. . . the handbook for an ex-R.N. R/T. pattern 4660.—R. LITTLE, 19 Waterfield Road, East Sleekburn, Bedlington Station, Northumberland.

. . . the February 1963 issue of P.W.—D. M. BILSBY, 31 Hainge Road, Tivdale, Tipton, Staffordshire.

. . . the circuit or any data for the R.1515 receiver.—R. G. W. BARTOCK, 38 Bittell Road, Barnet Green, Birmingham.

. . . the circuits and manuals of the recording bridge type R.B.150 and the receiver R.206.—R. S. MARTIN, 41 Mayheld Road, Northfleet, Kent.

. . . the circuit and data for the R.1155 receiver—H. BRUNKER, 104A Bethune Road, Stoke Newington, London. N.16.

. . . the Air Ministry pamphlet AP2879AF.—S. G. JONES, 393 Manchester Road, Lostock, Northwich, Cheshire.

. . . the service manual for the No. 38 Mk. 11 transceiver.—H. HUMPHRIES, The Old Vicarage, Gazeley, Newmarket, Suffolk.

. . . the circuit and other data on the R.109 receiver.—D. G. VAUGHAN, c/o The London School of Flying, The Aerodrome, Elstree Hertfordshire.

. . . the May 1962 issue of P.W.—A. MILBURN, 27 Chequerfield Road, Pontefract, Yorkshire.

. . . the circuit and/or manual for the Murphy model SA104R receiver.—W. G. PRICE, 228 The Broadway Dudley, Worcestershire.

. . . any circuit details of the R.1132A communications receiver.—A. DIPPER, 50 St. Cuthberts Avenue South Shields, Co. Durham.

**FIRST TIME EVER!**

**PRACTICAL MOTORIST ANNUAL 1964**

**128 Page Guide to Better Motoring at Less Cost**



**Sections on:**

**Tools and their Uses, Car Specifications, Repair, Maintenance, Overhaul, Tuning Made Easy, Electrics, Driving Techniques, plus Road Tests of Popular Models.**

**DEMAND WILL BE TREMENDOUS — TO MAKE SURE OF YOUR COPY—ORDER NOW**

**Wow and Flutter**

*—continued from page 1061*

and subtracts as the record and replay periodic peaks come into and out of phase. As an example, a pressure roller that has a deformation causing a wow twice per revolution could have a resultant effect on replay that varies between one and three peaks per revolution, and this random cancelling greatly reduces the aural effect of the fault.

**Peak-to-Peak Values**

It will be noted that percentage figures are given with each fluttergram. These are integrated readings, at r.m.s. values, and where a machine has a specification of  $\pm$  a certain figure, this must be multiplied by 0.707 to reduce it from the peak-to-peak value.

In certain cases, where a peak-to-peak specification is stated, it is necessary to interpret this to obtain a fair comparison with other machines. Thus, the Grundig TK40, an excellent domestic model, has a specification of  $\pm 0.12\%$  at  $3\frac{1}{2}$  in/sec, which becomes the much more revealing figure of 0.085% r.m.s. For a really pessimistic view of wow and flutter specifications, it may be necessary to multiply the peak reading by  $\sqrt{2}/2$ , or 0.35, where the waveform is sinusoidal, and allowance has to be made for the most stringent conditions.

From the above it can be seen that wow and flutter is a real problem. Its elimination exercises the utmost ingenuity of designers. That the specifications of current models should be so low is a tribute to their labours.

To .....  
 (Name of Newsagent)  
 Please reserve/deliver my copy of the PRACTICAL MOTORIST ANNUAL 1964 (2/6), on sale March 20th.  
 Name.....  
 Address.....  
 .....

**NOW! ANOTHER PURCHASE of the year's keenest TAPE RECORDER BARGAIN!**



A 24 gus. Tape Recorder offered at the bargain price of only 15 gns. plus 10% carr. Supplied in 3 Units already wired and tested. A Modern Circuit for quality recording from Mike, Gram or Radio, using latest B.S.R. Twin Track Monardeck Type T.D.2. Magic-eye recording indicator. Ext. spl., switch super-impose and straight-through amplifier facilities, etc.

- Valve line up EF86, ECL252, 8M84, E230 and Silicon Diode.
- 2 tone Cabinet and 8" x 5" Speaker Size 14" x 10 1/2" x 7 1/2" **£3.10.0** + 5/- Carr.
  - Wired Amplifier complete with 4 Valves, Iron Panel, Knobs **£5.12.6** + 3/6 Carr.
  - B.S.R. Monardeck Type T.D.2 Accessories—Mike, Tape, Screened Lead Plugs, etc. **£7.7.0** + 4/6 Carr.
  - COMPLETE KIT** comprising items above **£10.0.0** + 2/- Carr.
  - Leads, circuits, instructions, 2/- post free. **15 gns.** + 10/- Carr.

**NEW BRITISH RECORDING TAPE**

Famous Manufacturer. Bulk purchase, genuine recommended Tape Bargain. Unconditional Guarantee. Fitted Leader & Stop Foils (except 3in.).

|                      |                         |                         |
|----------------------|-------------------------|-------------------------|
| Standard (PVC base)  | Long Play (P.V.C. base) | D'ble Play (Mylar base) |
| 3in. 150ft. 8/8      | 900ft. 15/-             | 1200ft. 25/-            |
| 5in. 600ft. 11/8     | 225ft. 4/9              | 300ft. 6/6              |
| 5 1/2in. 850ft. 14/8 | 1200ft. 17/8            | 1800ft. 32/6            |
| 7in. 1200ft. 17/8    | 1800ft. 22/8            | 2400ft. 42/8            |

Post and Packing—3in. Reels, 6d. Each additional Reel, 3d. 4in. to 7in. Reels 1/- Each additional Reel, 6d.

**EMPTY TAPE REELS (Plastic):** 3in. 1/3, 4in. 2/-, 5in. 2/-, 5 1/2in. 2/-, 7in. 2/3. **PLASTIC REEL CONTAINERS (Cassettes):** 3in. 1/3, 5in. 1/9 5 1/2in. 2/6, 7in. 2/3.

**Condensers—Silver Mica.** All values 2pF to 1,000pF, 6d. each. Ditto. Ceramic 9d. Tub. 450V T.C.C. etc. 0.001 mFd to 0.01 and 0.1/250V. 9d. 0.02-0.1/500V. 1/-, 0.25 Hunt. 1/6. 0.5 T.C.C. 1/9 etc. etc. Close Top/Micas—10% hpF-500pF 3d. 500-5,000pF 1/1- 1% 3pF-100pF. 9d. 100pF-500pF. 11d. 575pF. 5,000pF. 1/8. Resistors—Full Range 10 ohms-10 meg. ohms 20% type modern ratings 1W, 6d. 2W. 9d. Hi-Stab. 5% 1W, 4/6. 10d. (100 ohms-1 meg). Other values 8d. 1% 1W, 1/6, etc., etc.

**Volume Controls—5K-2 Meg. ohms.** 3in. Spindles. Morganite Midget Type 1 1/2in. diam. Gear. 1 year. LOG or LIN ratios less 5/6. 3/6. DE. Sw. 4/6. Twin Stereo less 5/6. 6/6. DE. Sw. 8/6. Specials to order.

**SPECIAL BARGAIN**

1 Meg. VOL. Controls DP. Sw. 1" gated spindle. Famous Mira. 4/6 for 10/- post free.

**RECORD PLAYER CABINETS 59/6 Carr. & Ins. 5/-**

Contemporary style, resin covered cabinet in two-tone maroon and cream. Size 15 1/2" x 14 1/2" x 9 1/2". Fitted with all accessories including bafile board and Vinar fret. Space available for all modern amplifiers and auto-changers etc. Uncut record player mounting board 14 1/2" x 12 1/2" supplied.

**2-VALVE 2 WATT AMPLIFIER.** E230 and Twin stage ECL252 with vol. and neg. feedback tone control. A.C. 200/250V with knobs, etc., ready wired to fit above cabinet. £2.17.6. P. & P. 1/6. 7" x 4" speaker and trans. £2/-, P. & P. 2/6.

**COMPLETE R/PLAYER KIT.** As ill. inc. BSR UA1A Unit. New Bargain Price Now Only £11.10.0. 7/6 carr. Double wound mains Tr. no live chassis!



**TYGAN FRET (Contem. pat.).** 12 x 12in. 3/6; 12 x 18in. 3/6; 12 x 24in. 4/6, etc.

**EXPANDED ANODISED ZINCAL.** Attractive gilt finish 1/2 in. x 1/2 in. diamond mesh 4/6 sq.ft. Multiples of 6in. cut. Max. size 4 ft. x 3ft., 47/6, plus carr.

**ENAMELLED COPPER WIRE—** 4lb. reels 14g-20g, 2/6; 22g-28g, 3/6; 30g-34g, 3/6; 36g-38g, 4/8; 39g-40g, 4/8, etc.

**JASON FM TUNER UNITS.** Designer-approved kits of parts. FMT1, 5 gns. 4 valves, 20/-; FMT2, 27. 5 valves, 35/-; JTV MERCURY 10 gns. JTVB £13.19.6. 4 valves, 28/6. **NEW JASON FM HANDBOOK** 2/6. 48 hr. Alignment Services. 7/6. P. & P. 2/6.

**TRIMMERS.** Ceramic (Compression Type)—30pF, 50pF, 70pF, 9d; 100pF, 150pF 1/3; 250pF, 1/6; 600pF, 1/9.

**PHILIPS.** Bee Hive Type (conc. air spaced)—2.5pF, 1/-; 3-20pF, 1/-.

**KNOBs—Modern Continental type.** Brown or Ivory with Gold Ring; 1" dia., 9d. each; 1 1/2" dia.; Brown or Ivory with Gold Centre, 1" dia., 10d. each; 1 1/2" dia. each. **LARGE SELECTION AVAILABLE.**

**METAL RECTIFIERS, STC Types—** RM1, 4/6; RM2, 5/6; RM3, 7/6; RM4, 16/-; RM5, 21/-; RM4B, 17/6.

**TUB-ELECTROLYTICS-CAN**

25/25v, 50/12v, 1/9; 8 + 8/450v, 4/6; 50/50v, 100/125v, 2/-; 32 + 32/275v, 4/6; 8/450v, 4/350v, 2/3; 50/50/350v, 6/6; 16 + 16/450v, 5/6; 60/250/275v, 12/6; 32 + 32/450v, 6/6; 100 + 200/275v, 12/6

**MULLARD "3-3" HI-FI AMPLIFIER. 3 VALVES 3 WATT**



3 ohm and 16 ohm Output. A really first-class Amplifier giving Hi-Fi quality at a reasonable cost. Mullard's latest circuit. Valve line up: EF86, EL84, EZ81, Extra HT and LT available for Tuner Unit addition. This is the ideal companion Amplifier for FM tuner units.


**TECHNICAL SPECIFICATION—** Freq. Response: + or - 1 dB 40 c/s-20 Kc/s. Tone control: Max. Treble Cut 20 Kc/s. Sensitivity: 100 Mw for 3 w. output. Output Power (at 400 c/s): 3 w. at 1% total harmonic distortion. Hum and Noise Level: At least 70 dB below 3 w.

**COMPLETE KIT** (incl. valves, all components wiring diagram and special quality sectional Output Trans.). **Ben. Price £6.19.6.** Carr. 4/6. Complete wired and tested, 8 gns. Wired power O/P socket and additional smoothing for Tuner Unit, 10/6 extra.

**Bronze Encutcheon, Printed Vol. Treble, Bass, On-Off, supplied with each Kit.**

**Recommended Speakers—**WB, HF 1012, £4.7.8. Goodmans AX10M, 10, 8.6.5d. 5in. AX10T £5.5.0 or AUDIOM 51, £8.10.0.

**DE-LUXE RECORD PLAYER KIT**

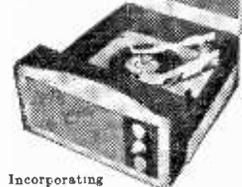

Incorporating 4 Sp. Garrard Auto-Slim unit and Mullard latest 3 w. amplifier (ECL 86 and E2 80), vol. bass and treble controls, with 8" x 5" 10,000 line speaker. Contemporary styled 2-tone cabinet, charcoal-grey and off-white with matching blue reed. Size 17 1/2" x 16" x 8".

**COMPLETE KIT £13.19.6** Carr. and ins. 10s.


**BARGAINS — 4-SP. PLAYER UNITS** Single Players E.M.I. Stereo/Mono ..... £6.10.0 E.M.I. Junior '985' ..... £3.7.8 Auto-changers ..... £8.19.6 BSR UA1A ..... £6.10.0 BSR UA1A ..... £6.10.0

**TRANSISTOR COMPONENTS**

Midget I.F.'s—465 Kc/s 9 1/2in. diam. .... 5/8 Osc. Coil M. & L.W. .... 5/8 Midget Driver Trans. 3.5d 9/6 Midget Output Trans. Push-Pull—3 ohms ..... 6/9 Elect. Condensers—Midget Type 1 mfd.-50 mfd. ea. 1/9, 100 mfd. 2/-, 12V. Condensers 150 v. working: .01 mfd., .02 mfd., .03 mfd., .04 mfd. 6d.; .05 mfd., .1 mfd., 1/6; .25 mfd., 1/3; .5 mfd., 1/8, etc. Midget Tuning Condensers: J.B. "OD" 208 pF and 176 pF, 5/8. ditto with trimmers, 8/6. J.B. 220pF and 105pF conc. slow motion 10/6. 365pF single 7/6. Sub. Mica 5in. Dia. 100 pF, 300pF, 500pF, 7/- each. **FERRITE AERIALS. M. & L.W.** car aerial coil 9/8. Midget Vol. Control with edge control knob, 5 K/ohms, with switch 4/8; Ditto less switch 3/8. Speakers: P.M.: 2in. Plessey 7/8 ohms 15/8. 2 1/2in. Continental 8 ohms 13/8. 7 x 4in. Plessey 3s ohms, 32/6. Ear PIEG Phones—Mira. Continental type 3ft. lead, jack plug and socket. High Imp., 8/-, Low Imp., 7/6. Grand New. Mira. 1st grade. 1 OC44 + 2 OC45. 15/6. 1 OC82 + 2 OC81. 15/6. All above and OA81, 32/6. Post Free.

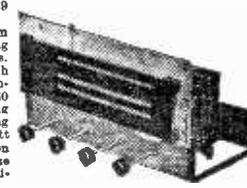**7 VALVE AM/FM RADIOGRAM CHASSIS**

Valve line-up ECC85, ECH81, EF 89 EAC80, EL84, EM81, EZ80. Gram Three Waveband and Switched Gram positions. Mc/s. 200-250 m. Long 1,000-2,000 m. VHF/FM 88-95 Mc/s. Philips Continental Tuning Insert with permeability tuning on FM and combined AM/FM IF transformers. 450 Kc/s. and 10.7 Mc/s. Dust core tuning all coils. Latest circuitry including AVC and Neg. Feedback. Three watt output. Sensitivity and reproduction of a very high standard. Chassis size 13 1/2" x 6 1/2". Height 7 1/2in. Edge illuminated glass dial 1 1/2 x 3 1/2in. Vertical position. Horizontal station names. Gold on brown background. A.C. 200/250v. operation. Magic-eye tuning. Ckt. diagram now available.



**Aligned and tested ready for use £13.10.0 Carr. & ins. 7/6**

Complete with 4 Knobs—walnut or Ivory to choice. Indoor FM aerial 3/6 extra. 8 ohm P.M. Speaker only required. Recommended Quality Speakers 10in. Elac H/D, 30/-; 13 1/2" x 5in. E.M.I. "Fidelity", 25/-; 12in. B.A. with cone. Tweeter, 42/6, Carr. 2/6.

**BONDACOUST Speaker Cabinet Acoustic Wadding (1in. thick approx.) 12in. wide, any length cut, 1/6 ft., 4/- yd. TINED COPPER WIRE. 16-22g 2/8 lb. ERSIN MULTICOORE SOLDER. 60/40 4d. per yard. Cartons 2/6 etc.**

We manufacture all types Radio Mainstays, Chokes, Quality, O/P Trans., etc. Enquiries invited for Specials. Prototypes for small production runs. Quotations by return. Send for detailed bargain lists, 3d. stamp.

**RADIO COMPONENT SPECIALISTS**

70 Bristolock Rd., Thornton Heath, Surrey. Hours: 9 a.m.-6 p.m., 1 p.m. Wed. THO 2188. Terms C.W.O. or C.O.D. Post and Packing up to 13. 9d.; 1 lb. 1/3; 5 lb. 2/3; 5 lb. 2/9; 8 lb. 3/6.



# Lewis have the Cabinet for you

We can supply any cabinet to your own specification

This is only one example of—  
**THE LARGEST RANGE OF CABINETS IN THE COUNTRY**

Equipment is also our speciality.



**The Grosvenor**  
Price 18 gns.



**The Lowboy**  
Price 24 gns.

**LEWIS radio**

100(P24) Chase Side, Southgate London, N.14, Pal 3733/9666

FREE CATALOGUE

Send today for the new Lewis Catalogue

Designed to assist your choice of cabinet.

THE New Lewis Radio Cabinet Catalogue—the most comprehensive ever prepared. Sent absolutely free.

Please send your new free cabinet catalogue.

Name \_\_\_\_\_

Address \_\_\_\_\_

BLOCK CAPITALS PLEASE

## NEW VALVES!

Guaranteed Set Tested  
**24-HOUR SERVICE.**

1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK81, DL92, DL94, SET of 4, 14/-, DAF94, DF96, DK96, DL96, SET of 4, 22/-.

|        |     |       |     |        |      |
|--------|-----|-------|-----|--------|------|
| OA2    | 4/- | DL33  | 6/9 | PCF82  | 6/-  |
| LD5    | 4/9 | DL35  | 6/- | PCL82  | 6/6  |
| 1R5    | 3/9 | DL82  | 4/9 | PCL83  | 6/6  |
| 1S5    | 3/9 | DL94  | 5/6 | PCL84  | 6/6  |
| 1T4    | 2/3 | DL96  | 5/6 | PL36   | 7/9  |
| 3S4    | 4/9 | EB91  | 2/- | PL81   | 6/6  |
| 3V4    | 5/6 | EB041 | 6/3 | PL82   | 5/-  |
| 5U4G   | 4/3 | EBF80 | 5/3 | PL83   | 5/3  |
| 5Y3GT  | 4/3 | EBL21 | 3/- | PL84   | 5/6  |
| 6Z4C   | 6/9 | ECC40 | 7/- | PY31   | 6/-  |
| 6K7G   | 1/3 | ECC81 | 3/3 | PY32   | 3/6  |
| 6R8G   | 3/- | ECC82 | 4/6 | PY33   | 6/3  |
| 6Q7G   | 4/3 | ECC83 | 4/6 | PY80   | 4/9  |
| 6U7G   | 7/6 | ECC84 | 5/6 | PY81   | 5/-  |
| 6X5GT  | 3/6 | ECC90 | 6/- | PY83   | 4/9  |
| 12K7GT | 3/- | ECF82 | 6/- | U65    | 5/6  |
| 12K8GT | 6/6 | ECH42 | 7/6 | U26    | 7/9  |
| 12K7GT | 3/3 | ECL80 | 5/9 | UABC90 | 5/6  |
| 12S7GT | 5/6 | EF56  | 6/6 | UAF42  | 7/3  |
| 2E16T  | 6/6 | EF80  | 4/9 | UBC41  | 4/3  |
| 3816GT | 6/6 | EF85  | 4/9 | UBF90  | 6/6  |
| 3624GT | 4/6 | EF86  | 5/9 | UC095  | 6/6  |
| 8A2    | 6/6 | EF89  | 3/9 | UCH42  | 7/-  |
| CL3    | 8/6 | EF91  | 3/9 | UCH81  | 6/3  |
| DAC33  | 7/6 | EL41  | 7/3 | UCL39  | 7/6  |
| DAF91  | 3/3 | EL84  | 4/6 | UCL83  | 3/-  |
| DAF96  | 5/6 | EY51  | 5/6 | UF41   | 6/9  |
| DF33   | 7/6 | EY86  | 5/- | UF89   | 5/9  |
| DF91   | 2/3 | EZ40  | 5/- | UL41   | 6/9  |
| DF96   | 5/6 | EZ80  | 3/9 | UL84   | 6/3  |
| DB77   | 3/9 | EZ81  | 3/9 | U08    | 11/- |
| DK32   | 7/9 | MU14  | 4/6 | UY21   | 8/3  |
| DK81   | 3/9 | PC084 | 5/6 | UY41   | 4/3  |
| DK82   | 6/9 | PC086 | 7/9 | UY85   | 4/-  |
| DK86   | 6/- | PCF80 | 5/3 |        |      |

Postage 6d. per valve extra. Any Parcel Insured Against Damage in Transit 6d. extra. Any C.O.D. Parcel 4/3 extra. Office address, no callers.

## GERALD BERNARD

63 OSBALDESTON ROAD,  
STOKE NEWINGTON,  
LONDON, N.16

## RADIO BOOKS

- STEREO FOR BEGINNERS 8/6  
The Author explains what Stereo is and how to obtain the best results. Chapters on Purchase, Installation and Maintenance. Well illustrated.
- HI-FI FOR BEGINNERS 8/6  
Chapters on Amplifiers, Loudspeakers, Pick-ups, Turntables, Radio Tuners, Stereo etc. Well illustrated.
- SOUND & CINE FOR BEGINNERS 8/6  
Chapters on Experimental soundtracks, separate tape tracks, Sound Stripe, etc., etc. Well illustrated.

## BASIC ELECTRICITY

- AUDIO & Acoustics by Briggs 11/6
- MORE about Loudspeakers by Briggs 9/6
- CABINET Handbook by Briggs 8/6
- "P.W." RADIO & Television Ref. Data 4/3

ELECTRONICS Pocket Book by Hawley 22/-

TESTED Short Wave Receiver Circuits using M.A.T.s 5/6

TESTED Short Wave S/Het Receiver Circuits using M.A.T.s 6/6

22 TESTED Circuits using M.A.T.s 5/6

AT A GLANCE Valve and T.V. Tube equivalents 4/-

OSCILLOSCOPE Book 5/6

USING an Oscilloscope 7/-

OSCILLOSCOPE Equipment 5/6

MULLARD Transistor Radios 5/6

MULLARD Ref. Transistor Circuits 13/6

EXTRA Equipment Tape Recorder COIL Design and Construction 5/6

TRANSISTOR Circuits for Radio Control of Models 8/-

SERVICING Transistor Receivers 5/9

ELECTRONIC Novelties 5/9

RADIO Valve Data "Wireless World" 7/-

BEGINNER'S Guide to Radio 8/6

MODERN Transistor Circuits for Beginners 8/-

HOW to Receive Foreign T.V. Programmes with Shiple Modifications 5/6

All books include postage. List S.A.E.

## SELWAY BOOK CO.

66 HAYES HILL, HAYES, BROMLEY KENT. Tel. HURSTWAY 1818

## ULTRA VIOLET BULBS

Easy to use soups of UV for dozens of practical and experimental uses. 12 volt 36 watt AC/DC SBC 8/6. P. & P. 11/- 12 volt 60 watt AC/DC SBC 8/6. P. & P. 11/- Transformer to suit the above: input 200-240 A.C. Output 12 Volt A.C. 36 watt 18/6. P. & P. 2/6. Input 200-240 A.C. 12 volt A.C. 60 watt 22/6. P. & P. 3/6.

Set of 4 colours FLUORESCENT Paint. Red, Orange, Green and Blue in 1 oz. tins. Ideal for use with the above Ultra Violet Bulbs 8/6. P. & P. 3/6.

## BUILD AN EFFICIENT STROBE UNIT FOR ONLY 37/6.

The ideal instrument for workshop, lab. or factory. This wonderful device enables you to "freeze" motion and examine moving parts as stationary. We supply a simple circuit diagram and all electrical parts including the NSP2 Strobe tube which will enable you to easily and quickly construct a unit for infinite variety of speeds, from 1 flash in several seconds to several thousands per minute. New modified circuits bring price down to 37/6 plus 3/- P. & P. NSP2 CY299 STROBOTRON FLASH-TUBE made by Philips, brand new L.O. base. Price 15/- P. & P. 1/-.

## MAGNETIC COUNTERS 10 IMPULSES PER SECOND

Very latest High Speed type type P.O. guaranteed. Price 2.300 ohms, type No. 100B, coil 2,300 ohms, for 48 volt D.C. operation (will work on 88 volt), overall size 4 x 1 x 1 in. Also available in type 101A which can be used as an interesting accessory with our Strobe unit. Either type price 15/- P. & P. 1/6.

## VARIABLE VOLTAGE TRANSFORMER £4.10.0

Post Paid. Input 230 v. A.C. Output 0-250 v. at 1 amp., fully shrouded, new. Also available 2.5, 5, 8, 10, 12 and 20 amp. Write for details.

4,000 Ohm Headphones, brand new (imported), 12/6 each, 3 1/2" x 1 1/2". SIEMENS 1A3-RELAY. Very latest type, sealed. H98E, 1,700 ohms plus 1,700 ohms single C/O contacts. Price 16/6 each, plus 1/- P. & P.

A.H. ACCUMULATOR, in metal case with leather carrying handle. New. Price 37/6, carriage 6/-.

3 r.p.m. GEARED MOTOR

24 v. D.C. (will operate from 12 v.). 1000 rev. gear. Consumption 200 mA. Size 3 1/2 x 2 1/2 x 2 ins. Weight 15 oz. Small Powerful. Fully Suppressed. 38/6. P. & P. 3/6. 280 VOLT A.C. GEARED MOTORS. Type B16G 80 r.p.m., 26 lb. inch, £1.19.6. P. & P. 2/- Type D16G 5 r.p.m., 1.7 lb. inch, £2.9.6. P. & P. 3/6. Type D16G 13 r.p.m., 1.46 lb. inch, £2.12.6. P. & P. 3/6.

## LIGHT SENSITIVE SWITCH

Kit of parts, including ORP .12 Cadmium Sulphide Photocell, Relay, Transistor and Circuit, etc., price 85/- plus 2/6 P. & P. ORP .12 including circuit, 10/6 each plus 1/- P. & P.

## MINIATURE UNISELECTOR SWITCH

3 banks of 11 position plus home bank. 40 ohm coil. 24-36 v. operation. Ex-exceptional. Individually tested. 23/6, plus 2/6 P. & P.

## MINIATURE LEAD ACID ACCUMULATORS

(Brand new) 2V, 1.5 A.H. Size 4 x 1 1/2 x 1 1/2 in. Wt. approx. 1 lb. 16/6 for 3. P. & P. 1/6. 12V, 0.5 A.H. Size 4 x 3 x 1 1/2 in. Wt. approx. 2 1/2 lb. (can be used as double 6V.). 15/6 each; P. & P. 1/6.

## TRANSISTORS

|        |     |        |      |        |      |
|--------|-----|--------|------|--------|------|
| OC41   | 7/- | OC84   | 10/- | GET573 | 12/6 |
| OC45   | 5/- | OC139  | 18/- | GC110  | 17/6 |
| OC46   | 5/- | OC148  | 20/- | 2N438  | 20/- |
| OC72   | 7/- | OC171  | 10/6 | 5B845  | 17/6 |
| OC73   | 6/- | OC200  | 10/6 | AC107  | 14/6 |
| OC75   | 7/- | OC201  | 21/- | AF114  | 11/- |
| OC78   | 6/- | OC203  | 14/- | AF115  | 10/6 |
| OC7T10 | 9/- | OC214  | 10/6 | AF116  | 10/- |
| OC81   | 8/- | GET105 | 10/- | AF117  | 9/6  |

\* Available in Matched pairs.

## SERVICE TRADING CO.

All Mail Orders also callers.

47-49 High Street, Kingston on Thames

Tel. KINGSTON 94

Personal callers only

9 Little Newport Street, London W.C.2 (off Leicester Square) Tel: GARRAY 0676

**PCR COMMUNICATION RECEIVERS**

Manufactured by Pye and Philips. One of the Army's most versatile and sensitive sets. RF stage and 2 of IF using 6 British I.O. type valves. Large 180 degrees illuminated and Calibrated Dial. Flivwheel tuning with locking device. Aerial trimmer. Tone and volume controls. Band switch from panel jacks for speaker or phones. In black metal case, size 17" L x 8" H x 10" D. Model PCR2 covers 6-22 Mc/s. 200-550 metres and 850-2,000 metres. £5.19.6. Model PCR3. As PCR2 but has 2 Short Wave Bands. 2.0-7.0 Mc/s and 7.0-23.0 Mc/s and Medium Wave Band 190-550 metres. ONLY £8.8.0. Every receiver aerial tested before despatch. Add 10/6 carr. Both types used, but excellent condition. Designed to operate from bulky external power supply, but any set can be fitted with BRAND NEW COMPONENTS INTERNAL PACK for 200/250 v. A.C. at extra cost of £2. S.A.E. for illustrated leaflet.

**TEST METERS FOR EVERY PURPOSE & POCKET**



**20,000 O.P.V. MODEL TP-10** Reads A.C. & D.C. Volts up to 1,900; D.C. Current to 500 mA; Resistance to 1 Meg; Capacitance to 1µF; Decibels from -20 to +36; Output Jack for Audio Measurements. Size 3 1/2 x 5 1/2 in. **£3.19.6**



**20,000 O.P.V. MODEL TP-5S.** Reads voltage up to 1,000 D.C. at 20,000 ohms per volt and A.C. at 10,000 O.P.V.: D.C. Current to 500mA; Resistance to 10 Megs.; Capacitance to 0.1µF; Decibels from -20 to +36. Size 3 1/2 in x 5 1/2 in. **£5.19.6**



**30,000 O.P.V. MODEL 500.** Volts to 1,000; D.C. at 30,000 O.P.V. A.C. at 20,000; 12 Amps D.C. Current; 60 Megs Resistance; -20 to +56 dBs; Internal buzzer short circuit warning. Size 3 1/2 in. x 6 1/2 in. x 2 1/2 in. **£8.19.6**

All New Stock, with leads, probes and internal batteries. 6 months' guarantee backed by full service facilities. Details S.A.E.

**DOUBLE BEAM OSCILLOSCOPE TUBES, TYPE CV-1596.** Equivalent to COSSOR 09D (as used in Oscilloscopes by Cossor 339 series) and Hartley & Erskine (13 series). Listed £12. BRAND NEW IN MAKER'S CRATES. ONLY 25/- (carriage 5/-).

**LAVOIE UHF WAVEMETER MODEL 103.** Coverage 375/725 Mc/s. Complete with correct Calibration Chart. First-class condition. Battery operated and portable. Size 11 x 8 x 7 1/2 in. ONLY £3.19.6 (carriage 7/6).

**AMERICAN DESK TELEPHONE,** complete with handset. Non-dial type but has internal bell. Ideal for extension or intercom. BRAND NEW. ONLY 30/- (post 4/-).

**ACOS 3 1/2 STICK MIKE** with screened lead and table stand. ONLY 32/6 (post 1/6).

**CRYSTAL DESK MIKE** with screened lead and built-in stand. ONLY 15/- (post 1/6).

**BCM FREQUENCY METERS.** The famous American crystal controlled frequency measuring standard. Coverage 125 Kc/s - 20 Mc/s. With original Calibration Book. Perfect order. Only £16.

**SPRAGUE CONDENSERS.** Metal cased, wire end. New 0.01 mfd. 1,000 volt, and 0.1 mfd. 500 volt, 7/6 per dozen. Special quotes for quantities.


**10 VOLTS AMERICAN DYNAMOTORS.** Deliver 220 volts at 100 mA. Size 5 1/2 in. x 3 1/2 in. diameter. Ideal for running Electric Shaver etc. for Car battery. ONLY 32/6 (post 2/6).

**90/- CONSTRUCTOR'S PARCEL.** Assorted colours wiring wire, solder, resistors, condensers, volume controls, tag panel. ALL NEW (post 2/6).

**RESISTORS.** 100 assorted values our choice. NEW. 7/6.

**CONDENSERS.** 100 assorted mica and silvermica. NEW. 10/-.

**TRANSISTORISED INSULATION TESTERS**

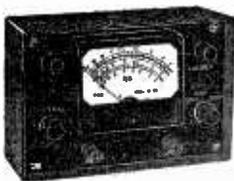


Size 7 in. x 4 in. x 4 in. batteries and test leads.

The latest technique for checking insulation of electrical circuits, appliances and components. One handed operation (no turning of generator) a Transistor DC-DC converter being employed to supply the high potentials. Three Testing voltages, 100 250 and 500, to measure up to 500 megohms. Complete with leather carrying case, internal ONLY **£17.10.0.**

S.A.E. for illustrated details.


**P.W. "CELESTE 7" RECEIVER**

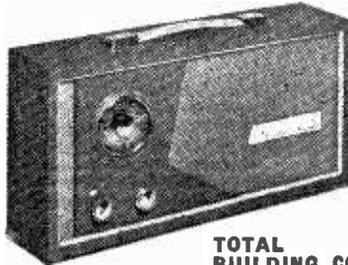

Build this latest P.W. seven transistor portable, as described in June and July issues. Medium and Long waves, with output of 1 watt from large 7 x 4 in. loudspeaker. Internal high gain aerial with car aerial socket. All components sold separately—parts list S.A.E.

**TOTAL BUILDING COST £9.19.6**

**"POCKET 4" TRANSISTOR RECEIVER**

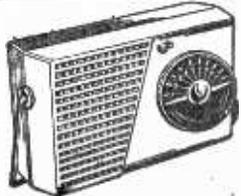

Uses miniature speaker, proper tuning condenser, and volume control. Built-in aerial makes unit efficient and portable. Ideal for the beginner. Full medium wave coverage. All components and case for only 42/6 (P. & P. 2/6). Ten-page constructional book free with parts or separately 1/6. S.A.E. for parts price list.

**BATTERY CHARGER**

6 v. or 12 v. at 2/4 amps. Fused and fitted with Ammeter and Voltage Selector. Louvred metal case finished attractive hammered blue. Ready for use with mains and output leads. ONLY 55/- (Post 3/6).

**PORTABLE A.C. VOLTMETER**

First Grade Moving Iron with 5 in. Mirror Scale. Reads up to 150 volts A.C. 400 and 1200-2400 cycles. In substantial oak case with removable lid. Overall size 8 1/2 x 8 1/2 x 5 1/2 in. BRAND NEW. ONLY 25.

**COSSOR TYPE 1025 DOUBLE BEAM OSCILLOSCOPES.** A few only of these modern scopes, overhauled and in perfect order. ONLY 445. Further details on request.

**PANEL METERS.** 25 microamps D.C. 2 1/2 in. Proj. circular 59/6. 50 microamps D.C. 2 1/2 in. Flush circular, 59/6. 100 microamps D.C. 2 1/2 in. Flush circular, 33/6. 40 amps D.C. 2 1/2 in. Proj. circular, 7/6 500 volts A.C. 2 1/2 in. Flush circular, 25/6.

**RECORD INSULATION TESTERS.** Read up to 20 mega. at 500 volts pressure. Overhauled and in perfect order. ONLY 28.10.0

**TELESCOPIIC AERIAL.** 8 sections 20 in. open, 16 in. closed, with 5 in. projection. Chromium plated and ideal for a variety of uses. ONLY 10/8.

**HARRIS ELECTRONICS (LONDON) LTD**

138 Gray's Inn Road, London, W.C.1

Phone TERminus 7937

Please include carriage costs on all items. (Open until 1 P.M. Saturdays). We are 2 mins. from High Holborn (Chancery Lane Station) and 5 mins. by Bus from King's Cross.

# CRYSTALS & COMPONENTS

LTD.

2-4 EARLHAM ST., W.C.2. Tel. TEM. 1189

Near Cambridge Circus. A few minutes' walk from Leicester Square or Tottenham Court Road Underground Stations. Hours of Business: 9 to 6, Saturdays 9 to 1. Open All Day Thurs.

### TRANSFORMER BARGAINS

Fri: 240 volta. Sec: 17 volta 1 amp. Ideal for small models. 5/-, P. & P. 2/6  
 Fri: 200/240 v. Sec: 6.5 v. 4 amps. 8/8. P. & P. 2/6.  
 Fri: 240 v. Sec: 250 v. 60 ma and 80 v. 100 ma, 5/-, P. & P. 2/6.  
 Fri: 240 v. Sec: 6.5 v. 2 amps. 6/-, P. & P. 2/6.

### E.H.T. TRANSFORMERS

Fri: 200/250 volta. Sec: 2,500 volta, 10 ma, 2 v. 1.5 amps. 6.5 volta, 3 amps, 22/6, plus 5/- P. & P.

### H.T. TRANSFORMERS

Type HT 2. Pri: 200/240 v. Sec: 3500/3500 v. 120 ma and 0-3-12-15 volta. 5 amps. 35/-, plus 5/6 P. & P.  
 Type HT3. Pri: 200/240 volta. Sec: 5000/5000 v. 95 ma and 0-4-6 v. 3 amps, 0-4-5-6 v. 3 amps, 0-4-6.3 v. 2 amps, 27/6, plus 5/6 P. & P.  
 Type HT12. Pri: 110/250 volta. Sec: 225 v. 100 ma and 6.3 v. 5 amp. 6.3 v. 1 amp. 6.3 v. 2.5 amps. P. & P. 5/-.

### TYPE 68 TRANS/RECEIVERS

Brand new. Operating on 7.4 to 9 Mhz. Trans/Receivers. Complete with headphones, throat microphone, junction box and aerial rods. Operate on 150 volta HT & 3 volta LT dry batteries. Complete less batteries and not tested. 47/6 per set plus 5/6 post. Or 84.10.0 per pair plus 12p post and packing.

Send S.A.E. for our NEW CRYSTALS LIST

### WIRELESS SET No. 19

Complete with original power supply unit for 12 volta input. Transmitter/Receiver covering 2-8 Mc/s and V.H.F. 240 Mc/s. 6 valve superhet receiver and 6 valves in Transmitter. Using 1 P. of 465 Kote. For voice and C.W. In good condition not tested. 84.17.8. Plus 1/- packing and carriage. Microphone and headset for this set 17/6 plus 2/6 post and packing. 19 Set Variometers, 17/6, plus 2/6 post and packing. Control box for 19 set, 10/-, plus 2/- post and packing. Lead for Control Box, 12/6. P. & P. 2/-.

### U.H.F. AERIAL

On 10ft. collapsible mast. Spring loaded in 1ft. tubular sections. Complete with 12ft. co-ax lead and rubber covered plug. 3 steel pegs and nylon guys. Can be easily lashed to existing TV aerials for modification to new frequency. 12/6 plus 2/6 P. & P.

TERMS of BUSINESS CASH WITH ORDER

### TV EXTRAS

AERIALS 25/- Indoor combined. Complete with 12ft. co-ax. and plug. P. & P. 2/6.  
 AERIALS 35/6 Loft Combined BBC with 3 element ITA universal fitting. P. & P. 3/6.  
 Co-ax Cable 6d. per yd. Plugs 1/3 ea.  
 LEGS—Complete with fittings for any set, 35/6.



17" £11.10.0

14" & 7.10.0

12 months' Full Written Guarantee.

Channels for all areas.

Demonstrations daily in our Shop, Personal collection advised.

Carr. 14in., 20/- 17in., 30/-.

### TELEVISION TUBES REGUNNED

|  |                    |
|--|--------------------|
| Guaranteed 1 Year Ins. and Carr. 10/6.                 | 21in. 99/6         |
| Add 10/- refundable on OLD TUBE (110' Tubes in stock.) | 17in. 79/6         |
|  | 15, 14, 12in. 59/6 |

### EX-MAINTENANCE TESTED TUBES

15/- Satisfaction Guaranteed. =36/24, 14KP4, 141, 121, 131/74, and others. Carr. 5/-.

### PERSONAL CALLERS

T.V.s 5/-, Type 38 Sets 15/- Large Transmitting Valves 5/- Tape and Record Cabinets 5/- Telephone Multi-line and dial systems 25/-  
 Tubes—Various, 2-6in. BRIT. & U.S.A. from 5/-.

### TELEPHONE 15/6 HANDSET

pair G.P.O. standard pattern. House to Workshop, garage, inter-office, etc. Works off any small battery. P. & P. 4/6.

### SPEAKERS 7/9 each.

6in.8in.7in.x 4in. Money-back guaranteed. Enquire for other sizes. Ex. mid. salvage. P.P. 2/3.

### SPARES

Condensers. 100, 10/-, New Assorted electrolytics & Pfs. Resistances 100—5/- Asst. sizes, watts, grades. VALVES 9d. ea. 40—£1 1,000's of Valves available. P.P. on 1-4 6d., 12 116.

Stamp for Free List **DUKE & CO. (LONDON) LTD.** Phone 621/3 Romford Road, Manor Park, E.12 ILFord 6001/2/3 Liverpool St.—Manor Pk.—10 mins.

# FREE TO AMBITIOUS ENGINEERS

— THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

Have you sent for your copy? ENGINEERING OPPORTUNITIES is a highly informative 156-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronics Courses, administered by our Specialist Electronics Training Division—the B.I.E.T. School of Electronics, explains the benefits of our Employment Dept. and shows you how to qualify for five years promotion in one year.

We definitely Guarantee **"NO PASS—NO FEE"**

Whatever your age or experience, you cannot afford to miss reading this famous book. If you are earning less than £25 a week, send for your copy of "ENGINEERING OPPORTUNITIES" today—FREE.

### WHICH IS YOUR PET SUBJECT?

Mechanical Eng., Electrical Eng., Civil Engineering, Radio Engineering, Automobile Eng., Aeronautical Eng., Production Eng., Building, Plastics, Draughtsmanship, Television, etc.

GET SOME LETTERS AFTER YOUR NAME!

- A.M.I. Mech. E.
- A.M.I.C.E.
- A.M.I. Prod. E.
- A.M.I.M.I.
- A.I.O.B.
- A.F.R.Ae.S.
- B.Sc.
- A.M. Brit. I.R.E.
- City & Guilds
- Gen. Cert. of Education
- etc., etc.

### PRACTICAL EQUIPMENT

Basic Practical and Theoretical Courses for beginners in Radio, T.V. Electronics, Etc., A.M. Brit. I.R.E. City & Guilds Radio Amateurs' Exam. R.T.E.B. Certificate P.M.G. Certificate  
 Practical Radio Radio & Television Servicing Practical Electronics Electronics Engineering Automation

### INCLUDING TOOLS!

The specialist Electronics Division of B.I.E.T. NOW offers you a real laboratory training at home with practical equipment. Ask for details.

### B.I.E.T. SCHOOL OF ELECTRONICS



### POST COUPON NOW!

Please send me your FREE 156-page "ENGINEERING OPPORTUNITIES" (Write if you prefer not to cut page)

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

SUBJECT OR EXAM THAT INTERESTS ME \_\_\_\_\_ SÉ/21

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY (Dept. SE/21), 29 Wright's Lane, London, W.8

THE B.I.E.T. IS THE LEADING ORGANISATION OF ITS KIND IN THE WORLD

# SPRING CLEARANCE SALE — PRICES SLASHED

## STOCK ROOMS MUST BE CLEARED TO MAKE WAY FOR SPRING STOCK

**Stock No. 101—**Few Only **MAINS BURGULAR ALARMS**, with complete set of door and window microswitches and Connecting Wire etc. Advertised at 7 p.m. **OUR PRICE** to clear **39/6**, plus 3/- P. & P.

**Stock No. 106—BRASS RIGHT ANGLE BRACKETS** drilled with 2 holes. Approximately 1 in. square. Only **9/-** a pair.

**Stock No. 104—MINIATURE MEDIUM WAVE TUNING COILS** with reaction winding. Clearance price **2/-** each, plus 6d. P. & P.

**Stock No. 105—39 ONLY PRECISION CAMERAS**, Takes 127 film. To clear **2/6** each, plus 1/6 P. & P.

**Stock No. 106—193 ONLY MINIATURE PLASTIC RADIO CABINETS**, complete with Chrome carrying Handles, Dial and tuning knob. Size 5 1/2 x 3 1/2 x 1 1/2 in. Clearance price only **5/6**, plus 1/- P. & P.

**Stock No. 107—PRINTED CIRCUITS** of 3 Transistor R-Flex Radio made to fit above radio, **2/6**, plus 1/6 P. & P.

**Stock No. 108—MINIATURE PRINTED RADIO CABINETS**, 5 x 3 1/2 x 1 in. **2/6** each to clear, plus 6d. P. & P.

**Stock No. 109—BEAUTIFUL MINIATURE SIZE PLASTIC RADIO CABINETS**, Size 5 x 3 x 1 1/4 in. Printed and ready drilled. **OUR PRICE 3/6**, plus 1/- P. & P.

**Stock No. 110—MINIATURE PLASTIC RADIO CABINETS** unprinted. Size 3 x 2 1/2 x 1 1/4 in. **2/6** each to clear, plus 6d. P. & P.

**Stock No. 111—BEAUTIFULLY MOULDED MINIATURE PLASTIC RADIO CABINETS**, complete with tiny carrying handle and tuning knob. Size 4 x 2 1/2 x 1 1/4 in. Price to clear **3/6**, plus 1/- P. & P.

**Stock No. 111a—Specially Printed Circuits** for above cabinet of two transistor reflex radio **2/6**, plus 6d. P. & P.

**Stock No. 112—EXCEPTIONALLY GOOD LOOKING PLASTIC RADIO CABINETS "SLIM LINE"**, Size 6 x 3 1/2 x 1 1/4 in. Clearance price **3/6** plus 6d. P. & P.

### AMAZING CIGARETTE RADIO only 18/6



Complete set of parts. Amaze your friends — this highly sensitive TRANSISTOR "CIGARETTE" receives all medium wave stations clear and crisp — holds ten cigarettes — weighs less than 6 ozs. with cigarette! Tiny battery inside lasts over three months. This brilliant little novelty personal phone radio is ideal for **Weekend News, Sports, Gossip**. Can be built by anyone from our simple pictorial diagrams in an hour or two. All parts supplied for 18/6 (add 1/6 P. & P.). C.O.D. 2/- extra. (Parts sold separately priced parts list 1/-).

**Stock No. 113a—BEAUTIFUL BLACK & GOLD READY DRILLED FRONT RADIO PANELS TO GO WITH THESE**, 6/-, plus 1/- P. & P.

**Stock No. 114—MINIATURE RADIO CABINETS IN GOLD** but undrilled. Size 4 1/2 x 3 x 1 1/4 in. Give away price of **3/6**, plus 6d. P. & P. Special carrying cases for above at 1/6, plus 6d. P. & P.

**Stock No. 115—RADIO CABINETS** same as specified as above, but upright design, **3/6** each, plus 6d. P. & P.

**Stock No. 115a—Special carrying case** for above at 1/6, plus 6d. P. & P.

**Stock No. 116—ANOTHER TYPE RADIO CABINET**, horizontal, **2/6** each, plus 6d. P. & P.

**Stock No. 116a—BRAND NEW MAGNETIC DEAF AID TYPE EARPIECES**, complete with Plug and Socket, **400 ohms**. **OUR SPECIAL PRICE 6/-**, plus 6d. P. & P.

**Stock No. 126—BRAND NEW CRYSTAL DEAF AID TYPE EARPIECES**. Our price **4/-** plus 6d. P. & P.

**Stock No. 127—DECORATIVE SPEAKER GRILLS** 2 in. diameter, 3 for 1/-, plus 6d. P. & P.

**Stock No. 128—3 in. PLASTIC TAPPING HANDLES** with filing screws, 6d. each, plus 6d. P. & P.

**Stock No. 133—93 ONLY STANDARD PLASTIC CELLING SWITCHES**, two way, cord operated. Clearance price **2/6**, plus 1/- P. & P.

### AMAZING NEW INVENTION AUTOMATIC CAR LIGHTER ONLY 10/-



We have been lucky enough to purchase 1,500 only of these fully automatic Car Cigarette Dispenser/Lighters because of a frustrated export shipment. Originally made to sell at about 45/-! Robust and ingeniously designed in heavy chromium. Holds packet of cigarettes (any make and size) you reach out with one hand, press a button and a lighted cigarette is in your hand! Can be fitted by anyone in 2/8 minutes. For 6 or 12 volts, full connecting details—only one wire to connect! Each one in own coloured box, brand new and untouched. Only **10/-**, add 2/- P. & P. (C.O.D. 2/6 extra).

**Stock No. 117—477 SUB-MINIATURE TRANSISTOR RADIO CASES** (Plastic undrilled). Size only 1 1/2 x 1 1/2 x 1/2 in. To Clear **1/-** each, plus 6d. P. & P.

**Stock No. 118—SPRING TERRY CLIPS** for holding Miniature Valve. Price 10. 3. 1/-, plus 6d. P. & P.

**Stock No. 119—79 ONLY MINIATURE 8 TAG COILS** covering Medium Wave and Long Wave with reaction winding. Price to clear **2/-** each, plus 6d. P. & P.

**Stock No. 120—SIMILAR TO ABOVE** but Medium Wave only **2/-** each plus 6d. P. & P.

### Stock No. 150. "VOLKSRADIO" POCKET VALVE RADIO ONLY 15/-

Take Over Bid makes this Fantastic Offer possible — the beautifully compact "5 Star VolkSRadio" measuring 4 1/2 x 2 1/2 x 1 1/4 in. receives perfectly—in the bedroom, office, garden—over all medium waves (incl. Luxembourg). Under 1d. hour running cost. Anyone can assemble in 1 or 2 hours, given our simple A B C plan. Complete set of parts. Only **15/-**, plus 1/8 P. & P. C.O.D. extra. (Parts can be bought separately.)



**Stock No. 137—BRAND NEW TRIMMERS "CYLDRON"** 200 P.F. To clear 1/- each, plus 4d. P. & P.

**Stock No. 138—MINIATURE AGORN VALVES**. Type 654. 9d. each plus 6d. P. & P.

**Stock No. 139—6K7G BRAND NEW VALVES**, 2/8, plus 9d. P. & P.

**Stock No. 140—6V6G VALVES** 4/8, plus 9d. P. & P.

**Stock No. 141—1L4 BRAND NEW VALVE**, 1/8, plus 6d. P. & P.

**Stock No. 142—BRAND NEW B7G VALVE HOLDERS**, 6d., plus 4d. P. & P.



### THE MINUTE TRANSISTOR RADIO MIAMI ONLY 17/6

Unbelievably small—outrageously cheap! You will be amazed at the fine quality of tone and volume of this great little radio. Only a fantastic 10/- component or months on an 8d. battery. 3 1/2 x 2 1/2 x 1 1/2 in. the MIAMI will bring you great simple assembly plan with each set. **ONLY 17/6**. YES 17/6. Plus 2/6 P. & P. (C.O.D. 2/- extra). Satisfaction Guaranteed. Demonstrations given daily. Parts available separately if required.

**TERMS OF BUSINESS**  
C.O.D. 2/6 extra, regret No C.O.D. under 1/- Add extra postage for overseas. Special prices for quantity and the Trade. All goods guaranteed. Components technical books, Hi-Fi by Leak, Jaxon, Lorenz, Quad, etc. Send S.A.E. for quotation or with any enquiry.

**Stock No. 121—MEDIUM WAVE LOOPSTICK COILS** with Variable Tuning Core, 73 only. To clear **2/8** each, plus 6d. P. & P.

**Stock No. 122—FEW ONLY VARIABLE TUNING CONDENSER** (Mica Dielectric)—.0005 mfd. **8/6**, plus 6d. P. & P.

**Stock No. 123—173 RADIO DIALS**. Printed Medium and Long Wave, Square shape, 3 1/2 x 3 1/2 in. with central hole. Price 1/6, plus 3d. P. & P.

**Stock No. 124—SUB-MINIATURE DIODES** all brand new and tested. Clearance price 3 for 1/- plus 3d. P. & P.

### OUR NEW 4-STAGE MINUETTE

Build this newly designed "MINUETTE" 4-Stage G E Transistor set in very strong ready drilled ULTRA-MODERN CASE. Size only 3 1/2 x 2 1/2 x 1 1/4 in. Uses three transistors and diode and SELF-CONTAINED LOUDSPEAKER. Very sensitive, ideal for office, bedroom, holidays, etc. Months and months of listening off an 8d. battery. Can be built FOR ONLY 30/- including PROPER CASE, miniature speaker, etc. SIMPLE YES A.B.C. PICTORIAL STEP-BY-STEP PLANS etc. plus post and packing 1/6 (C.O.D. 2/- extra). Parts sold separately, priced parts list 1/-.

**Stock No. 125—BRAND NEW ASSORTED CONDENSERS** 30pF to .01 mfd., 25 for 7/6, plus 1/- P. & P.

**Stock No. 124—SPECIAL OFFER OF HOME CONSTRUCTED RADIOS NEEDING ATTENTION**. Filled with components in good condition.

**Stock No. 124a—TYPE (B) 2/8 Transistor**. Size 4 1/2 x 3 x 1 1/4 in. Price 5/- each plus 1/- P. & P.

**Brand new 2 1/2 in. Miniature Coil Speakers**, worth 14/-, given free with every order for free.

**Stock No. 124b—TYPE (D) Miniature Valve Radios** in plastic case. Size approximately 5 x 3 x 1 1/4 in. Price 5/- plus 1/6 P. & P.

**Stock No. 124c—TYPE (E) 20 only**, Valve Radios in small Fibra-Plastic case. Size 7 x 5 x 2 1/4 in. Price 2/8, plus 2/6 P. & P.

**Stock No. 125—SURPRISE PARCEL TYPE (A)**. Assorted components. Price 5/- plus 1/8 P. & P.

**Stock No. 127—GIANT SURPRISE PARCEL TYPE (C)**. Price 15/-, plus 1/6 P. & P.

**Stock No. 128—WANDER PLUGS**. New and unused. 8/- doz., plus 6d. P. & P.

**Stock No. 124—3 in. MOVING COIL LOUD-SPEAKERS**. Brand new, 3 ohms 10/-, plus 2/6 P. & P.

**Stock No. 128—SPECIAL CLEARANCE OF FULLY GUARANTEED BRAND NEW "GOLD FRONT" 6 TRANSISTOR SUPERBET RADIOS**. Complete with real leather carrying case. Personal earpiece, battery. All in beautiful presentation boxes. Only 75/- plus 2/6 P. & P. 74 only. Advertised at 65.6.0 recently. Last 74—no more available.

**Stock No. 143—256 ONLY: MINIATURE PRECISION "MINE PAT" 8 P.V. CAMERAS** complete with 11 rolls of film and real leather carrying case. Size 2 1/2 x 1 1/2 x 1 1/4 in. Price to clear **20/-** each. Post Free.

**Stock No. 144—BRAND NEW 2 1/2 in. MOVING COIL LOUDSPEAKERS**. SPECIAL PRICE 2/8, plus 1/6 P. & P. 50 ohms

**Stock No. 145—BRAND NEW ASSORTED RESISTORS** in packets of 100, 8/-, plus 6d. P. & P.

**Stock No. 151—BRAND NEW "PLESSEY" MOVING COIL SPEAKERS**, 2 1/2 in. 40 ohms. M.C.H.C. Transistor. Direct—No O.P.T. needed. Special prices 2/6, plus 1/6 P. & P.

**CONCORD ELECTRONICS (Dept P.W.5) 210 Church Road, Hove, Sussex**  
PERSONAL CALLERS WELCOME — Open 8.30 a.m. until 1 p.m. and 2 p.m. until 5.30 p.m. Saturdays 8.30 a.m. to 1 p.m.  
Demonstrations Daily.

# HERE'S A LOW COST WAY TO GET INTO T.V. SERVICING FAST!

If you are a man who wants to get ahead in television, you will probably be interested in this new revolutionary type television training programme now being introduced for the first time.

Knowing that early success will usually spur a man on to greater achievement you learn how to make the easiest T.V. repairs first. Since the easiest T.V. repairs are the ones most often found on service calls, you are ready to make money right after the first lesson. Then as you progress you will discover how to handle every kind of trouble found in all makes of T.V. set!

Here for example are some of the items covered in the course:

1. Simple adjustments to correct poor pictures.
2. Circuit faults indicated by a poor pattern.
3. Finding bad valves by observing picture faults.
4. Antenna Principles and Practices.
5. Facts about the T.V. signal to help you in repair work.
6. All about Cathode Ray tubes.
7. How to tell what is at fault.
8. Explanation of television circuits.
9. U.H.F. converters and tuners.
10. Television test equipment and alignment.
11. Advanced trouble shooting by picture analysis.

This is a real home study course that has been bound into one giant 8 x 11in., 192 page manual to reduce cost.

Compares favourably with some courses costing very much more! By creating a mass market through large volume sales and eliminating individual letter writing we are able to pass on these savings directly to you!

The course features over 325 different line drawings, circuits, servicing charts and illustrations to simplify the text and make your study more enjoyable. Soon you will be well on your way to becoming a first-class television repair technician!

## YOU TAKE NO CHANCES WHEN YOU DEAL WITH SIM-TECH

You must be convinced that this is the best value you have ever seen in television training, otherwise you can return the course (or have your money refunded if sent with order) after you have examined it in your own home for a period of seven full days.

The price? Only 38/- per course, plus postage and packing, 1/6.

Free 71-page book on Television Faults will be included if you send cash with order.

### FREE TRIAL OFFER

Terms only 5/- per week if you wish.

To SIM-TECH BOOK COMPANY Dept. BT.4 West End, Southampton, Hants.

Please send your Television Course for a full seven days' free trial. If not delighted I may return the course post-paid without further obligation on my part. Otherwise I will pay cash price of 37/6 or 8/- weekly until 37/6 plus 2/6 service charge, total 40/- is paid.

Tick here if enclosing full price of 37/6. (Same 7-day money back guarantee). NOTE: Customers who send cash with order get in addition a 71-page book on TELEVISION FAULTS. Overseas customers please send full amount (including Ireland).

Name .....

Address .....

.....

City..... County.....

## STAR DXER S.R.-40 £24.15.0

General purpose superhet communications receiver for A.C. mains, 220-240 volts, covering 550 Kc/s to 30 Mc/s in four switched bands. Slide rule tuning dial, electrical band-spread, internal speaker, panel "S" meter, noise limiter, E.F.O. phone jack, Ferrite and whip aeriels. Handsome grey crackle cabinet 13 x 8 1/2 x 5 1/2 in. Wt. 12 lb. Full instruction manual. BRAND NEW CURRENT MODEL.

P.C.R.-3 RECEIVER. 3-wave bands, medium wave and 2 short wave, from 120-13 metres. Good condition, tested, 8 gns. Carr. 10/-. A.C. mains internal power supply £2 extra.

**SILICON RECTIFIERS.** Type IEA2 (4 x 1/2 in.) will handle 250 volts at up to 500 mA. Replaces any TV metal rectifier, 7/6.

**AR-88 VIBRATOR PACKS.** For 6 v. operation. Complete with vibrator and OZ4 rectifier. BRAND NEW in original cartons, 17/6. P. & P. 5/-.

**MOVING COIL PHONES.** Fine quality Canadian with Deamois ear muffs and leather covered headband. With lead and jack plug. Noise excluding, supremely comfortable. BRAND NEW.....22/6 post 1/6.

**AVO WIDE RANGE SIGNAL GENERATORS.** Six turret operated ranges covering 50 Kc/s to 80 Mc/s. For use on standard A.C. mains. Packed in original transit cases with accessories. Post-war type in new condition £15. Carriage 10/-. REAL BARGAIN.

**CRYSTAL CALIBRATOR.** As used in Canadian No. 52 set. Incorporates twin 1Mc/s and 100Kc/s crystal and a multivibrator circuit to give 10Kc/s marker pips. Requires 12V 1 amp. L.T. and 150V. H.T. Complete with 3 valves, circuit of 52 set and operational notes. BRAND NEW 37/6, plus 2/6 P. & P.

**ALMS SPARE VALVES.** Complete Set of BRAND NEW individually boxed original valves (14), 50/-, plus 2/6 P. & P.

**MULLARD CRYSTAL CALIBRATOR.** In neat grey metal case 9 x 7 x 6 1/2 in. Gives 1 Mc/s, 100 Kc/s, and 10 Kc/s, marker pips and harmonics as selected. Optional 400 c/s modulation. Complete 6 valves (1T4 (5), 1R5 (1), and 1Mc/s 37C glass crystal. Requires 60 V. H.T. and 1.5 V. L.T. In original transit case. BRAND NEW, £24.19.6, carr. 7/6.

**MICRO-AMMETER.** 0-500µA. Made by R.C.A. Weston Westinghouse, and other famous American manufacturers. Circular 2 1/2 in. flush panel mounting. Dials are engraved 0-15, 0-600 volts. As used in the American version of the "19 SET". TESTED AND GUARANTEED 15/-.

CHARLES BRITAIN (RADIO) LTD., 11 UPPER SAINT MARTINS LANE, LONDON W.C.2. Temple Bar 0545 Shop hours 9-6 p.m. (9-1 p.m. Thursday). Open all day Saturday.

## PADGETTS RADIO STORES

OLD TOWN HALL, KNOWLER HILL LIVERSEDGE, YORKS. Telephone: Cleckheaton 2868

**New Boxed Tube Unit Type 7301.** With two EF52, three EF91, five 6L6, two CV4025, one 6V6GT. Also Tube Type VCRX 263 with metal screen. Fitted with dimmer unit and lamps Part 7302. A fine unit for only 45/-, Carr. B.R.S. 8/-. No details on this unit.

**New Boxed Drive Unit Type 114.** Complete with 5U4, 6L6 valves, housed in a very nice case. 15/-, Carr. B.R.S. 7/6.

**New Boxed 12 Volt Vibrator Pack with Spare Vibrator.** Type P.C.R. 250 volts at 150 milli. 18/- Carr. 7/6.

**New 12in. Speaker with Built-in Tweeter.** 28/6.

**ARMY SET TYPE 19.** Complete sets 32/-, Less transmitter and valves, 20/-. Less valves for spares, but with 500mc-amp. meter 12/6. Used, but have no dry rot, all untested. Carr. B.R.S. on any set 10/-.

**P.M. Speakers, Guaranteed ex T.V. sets.** 6in. round, 6 x 4in. Rola and Plessey, Philips 5in. round, all at 3/- each. Post 2/-, 6 for 20/-, post paid. Goodmans 7 x 3in., 5/-, post 2/-, 8in. round, 6/-, post 2/-.

**Valves Removed from T.V. sets.** Tested on a Mullard Valve Tester, and are 100% as new. Three months' unconditional guarantee. POST FREE.

|       |     |       |     |       |     |
|-------|-----|-------|-----|-------|-----|
| ECL80 | 2/- | 10P13 | 5/- | PL81  | 5/- |
| ECC82 | 3/- | 10P14 | 5/- | PL82  | 5/- |
| EY51  | 2/6 | 20D1  | 3/- | PL83  | 5/- |
| EF90  | 4/6 | 20L1  | 5/- | PL33  | 4/- |
| EF91  | 8d. | 20P3  | 5/- | PL38  | 5/- |
| EF91  | 9d. | 20P4  | 8/6 | PY80  | 5/- |
| GSN7  | 2/6 | 20P1  | 5/- | PY81  | 4/- |
| 6F1   | 1/- | U801  | 8/6 | PY82  | 5/- |
| 6F14  | 5/- | U281  | 5/- | PCF80 | 4/6 |
| 6F15  | 5/- | U282  | 5/- | PCF84 | 4/6 |
| 6LD20 | 5/- | U282  | 5/- | B36   | 4/- |
| 10C2  | 5/- | U329  | 5/- | N37   | 5/- |
| 10F1  | 1/- | KT36  | 5/- | 6U4   | 5/- |

EF90 1/6, or 10/- per doz. Grade II EF90 for test purposes, 4/- per doz.

**New Valves Ex Units. POST FREE.** 6K7 1/6, doz. 12/-, 6K8 2/6, doz. 22/-, 6V6 2/6, doz. 22/-, 807 U.S.A. 6/-, PP3/250 (PX4) 5/-, AC27EN (PEN44) 2/6, 5U4 3/-, 6SN7 3/-, 6V6GT 4/6, EF91 1/6, EL91 1/6, 6P8 2/-, 5Z4 5/6, 5Y3 4/6, 6X5 4/6, EF50 1/-, 6/- doz. ARP12 1/6, 6 for 5/6, box of 50 18/-, KT66 8/-, ARTP2 2/-, ART4 2/-, APP37 2/-, AR8 2/-, IT4 2/-, 954 new boxed 1/3.

**13 Channel T.V. Sets.** 14in. untested 30/-, Carr. 10/-, 17in. sets untested, 50/-, Carr. 10/-, Well packed sent at owner's risk.

**T.V. Tubes.** Completely rebuilt & refaced. 12 months guar. Sizes up to 17in. Special trade price of 75/-, Carr. and Ins. 7/6.

**Reclaimed Tubes.** 14in., 30/-, Carr. 7/6, 6 months guarantee.

## RES/CAP. BRIDGE 39/6


p. & p. 2/6 Checks all types of resistors, condensers 6 RANGES

Built in 1 hour. Direct reading READY CALIBRATED Stamp for details of this and other kits.

RADIO MAIL (Dept. PV) Raleigh Mews, Raleigh Street, Nottingham

FAMOUS FOR THIRTY YEARS for SHORT-WAVE EQUIPMENT of QUALITY

## H.A.C. SHORT-WAVE KITS

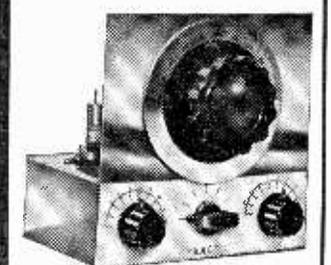

H.A.C. were the original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers - including Technical Colleges, Hospitals, Public Schools, Hams, etc.

### NEW 1964 RANGE NOW READY

1-Valve model "CX", complete kit, Price 34/6

Customers say: "Definitely the best one-valve S.W. kit available at any price." This kit contains all genuine Short-Wave components, a drilled chassis, accessories and full instructions. Ready to assemble and, of course, as all our products, fully guaranteed. FULL RANGE of other kits still available including the famous model "K", price 77/-.

Before ordering call and inspect a demonstration receiver or send for a descriptive catalogue and order form to—

"H.A.C." SHORT-WAVE PRODUCTS (Dept. T.H.), 44 Old Bond St., London W.1

**Infra-Red Heaters**

Make up one of these latest type heaters. Ideal for bathroom, etc. They are simple to make from our easy-to-follow instructions—uses silica enclosed elements designed for the correct infra-red wavelength (8 microns). Price for 750 watt element and metal casing as illustrated 19/6, plus 2/6 post and insurance.



**Limited Quantity Only**

Waterproof heater wire. 15 yds. length. 70 watts. Self-regulating temperature control. 10/-, post free.

**Microphone Inserts**

American made. Dynamic type. Real bargain at 3/6, plus 6d. postage.



Crystal type 5/6.

**Beginner's Superhet**

As supplied to many schools and colleges. A simple basic superhet—easy to understand and which can be progressively extended—ideal for students—components include valves—metal rectifier tuning condenser—I.F. transformer, etc. In fact, complete superhet except speaker. Price 23 plus 3/6 post and insurance. Data included free or 4p. 1/6.



**Copper Clad Element**

Plant this under a reflector to make ideal infra-red heater, also suitable for building into convector, blower heater, drying cabinet, etc. 230/240 v., 1250 watts. 12 ins. long but can be bent to almost any shape. 7/6, plus 2/6 post and insurance.

**Cabinet Snip**

This fine cabinet as illustrated but less control knobs is available this month at the special snip price of 16/6, plus 4/6 post and insurance. Size 13 1/2 in. x 9 in. x 4 in. and it is nicely covered in two tone I.C.I. fabric.



**Yaxley Switches**

- |                     |                     |
|---------------------|---------------------|
| 1 pole, 2 way 2/-   | 1 pole, 3 way 2/-   |
| 1 pole, 4 way 2/6   | 1 pole, 5 way 2/6   |
| 1 pole, 7 way 3/6   | 1 pole, 9 way 3/6   |
| 1 pole, 11 way 3/6  | 2 pole, 12 way 3/6  |
| 2 pole, 2 way 2/6   | 2 pole, 4 way 2/6   |
| 2 pole, 5 way 5/-   | 2 pole, 6 way 3/6   |
| 2 pole, 12 way 5/6  | 3 pole, 3 way 3/6   |
| 3 pole, 5 way 4/6   | 3 pole, 12 way 8/6  |
| 4 pole, 2 way 2/6   | 4 pole, 3 way 3/6   |
| 4 pole, 4 way 3/6   | 4 pole, 6 way 8/6   |
| 4 pole, 6 way 6/6   | 4 pole, 11 way 10/6 |
| 4 pole, 12 way 11/6 | 5 pole, 3 way 4/6   |
| 5 pole, 5 way 8/6   | 6 pole, 12 way 14/6 |
| 6 pole, 3 way 9/6   | 6 pole, 3 way 4/6   |
| 6 pole, 12 way 17/6 | 6 pole, 11 way 16/6 |
| 8 pole, 4 way 6/6   | 8 pole, 2 way 6/6   |
| 8 pole, 4 way 7/6   | 8 pole, 6 way 11/6  |
| 8 pole, 12 way 22/6 | 12 pole, 2 way 8/-  |
| 12 pole, 3 way 16/6 | 12 way ladder 3/6   |

1 pole, 6 way incremental shorting. 3/6

Please add 1/- post and packing for all orders below 23.

**Meter Bargains**


2nd. Moving Coil 500 micro-amp. f.s.d. Brand New, 17/6, plus 1/- packing and insurance.

**CABINET & PICK-UP**

Made for a famous company intending to make a Hi-Fi Record Player but changing their minds. This is an extremely fine looking cabinet, must have cost at least £2 to make. It is complete with handle and fasteners as illustrated. Also included in the parcel is a Cosmocond pick-up with crystal cartridge and sapphire stylus. Both items new and perfect. Only 19/6, plus 4/6 post and insurance.



**GOOD COMPANION Mark III**

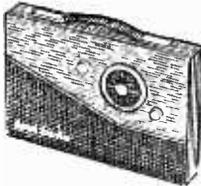

The 6 transistor set with the 8 transistor performance. Incorporating all the latest requirements. Anyone who can solder can make it. Many thousands already in use all over the country. Full coverage of Long and Medium wavebands. Fine looking cabinet, size 11" x 6" x 3". Q.P.P. Output approx. 750 mW. Excellent reception of difficult stations like 208. Variable feed back gives excellent tone. ONLY £5.19.6 3/6 Post and Insurance.

**THIS MONTH'S SNIPS**

**FLOUORESCENT LIGHTING FITTINGS.** All complete and ready to work as soon as tubes are fitted. Unused and guaranteed in perfect working order.

**THE TWIN 20 (Plug in model).** This very popular fitting is two feet long and approx. five inches wide. This makes it ideal for corridors, hallways, kitchens, toilets, etc. Being plug-in it can be quickly changed from room to room as desired. Light output approx. same as 100 watt lamp. White enamel. Brand new and perfect. Uses standard tubes. 19/6, plus 3/6 post and insurance.

**THE TWIN 20 (Batten model).** Similar to above but intended for mounting directly to ceiling or hanging by chains. 18/6, plus 3/6 post.

**THE FOUR FOOT 40.** A white enamelled batten type fitting, extremely popular as a kitchen light but equally suitable for bedroom or office, etc. Complete ready to work when standard bi-pin tube is fitted. 14/6, plus 4/6 carr. and insurance.

**THE FIVE FOOT 80.** Similar to above but for 5 foot 80 watt tube. 27/6 plus 7/6 carr. and insurance.

**CIRCLE-LITE (plug in model).** Straight fittings may look a little plain in some positions but the circular types are just as efficient and have the very modern look. They are ideal in living rooms, shops and offices, in fact anywhere, and being plug-in they can be fitted in a jiffy at no extra expense. Whole shops and offices can be re-lit in minutes and as something like three times the light quantity for the same current is achieved additional wiring is not necessary to create a transactions light increase. 40 watt circular fitting. Complete, requiring only tube. 19/6, plus 2/6 post and packing.

**CIRCLE-LITE (surface mounting).** As above but intended for direct to the ceiling. 27/6, plus 3/6 post and packing.

**NOTE:** Tubes are available to callers from 7/6 each but can only be dispatched in minimum quantities of 0 owing to damage risk.

**"CORONET" Mk. III**

An excellent pocket size set using 3 MAT transistors for the oscillator and I.F. stages and 2 junction types including matched pair for the output stage. It fully covers the medium-wave band and that part of the long-wave band to bring in B.B.C. Light. The circuit includes a highly efficient slab aerial and Plessey tuning condenser incorporating wave change switch. Overall size approximately 4 1/2 x 2 1/2 x 1 1/2 in. Supplied complete with varying case, this two-wave pocket set is available whilst stocks last at the very low price of 23.12.6.



**MULTI-METER BARGAIN**

Model number EP10K. Extra wide scale fitted corner view for compactness, extra accurate as it uses 156 components. Sensitivity 10 000 ohms per volt A.C. and D.C. ranges D.C. voltage up to 1.2kV in 5 ranges. A.C. voltage up to 1.2kV 5 ranges. D.C. current up to 300mA 3 ranges. Resistance up to 2 meg. Capacities 005 to 15 mf and decibels. Complete with full instructions and test prods and battery for ohms range. A real bargain not repeatable once stocks cleared. Price 89/6, Carriage and insurance 5/-.

**Electric Blanket Spares**

We carry a good stock of elements, thermostat and switches etc. for Electric Blankets. Neud S.A.E. for list.

**Timer Kit**


Special offer of all components except metal box to make mains operated interval timer for photography etc. 12/6 plus 2/6 post.

**5000 mFd Condensers**

12 V. working—Plessey—perfect. 2/- each. 18/- doz.

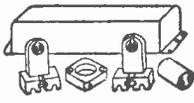**Fluorescent Light Bargain**

For pelmet or window lighting, etc. Kit of parts comprising: choke, two lamp holders.



40 watt, 19/6; 80 watt, 27/6. Plus 2/6 post and insurance.

**Building A 'Scope**



3in. oscilloscope tube. American made type No. 3FP7, 6.3 v. 0.6 amp. heater, electrostatic deflection, brand new and guaranteed with circuit diagram of scope. 15/- each, plus 2/6 post and insurance.

**Adjustable Thermostat**



Suitable for industrial or domestic purposes such as controlling furnace oven, immersion heater, etc. Can also be used as a thermostat or fire alarm. Made by Sunvic these are approximately 17in. long and adjustable over a range 0 to 550 F. The contacts are rated at 15 amps., 230 volts, and the adjustment spindle, which comes to the top, can be fitted with a flexible drive for remote control or just a pointer knob for local control. Listed at 25 or 24 each, these are offered at only 8/6, plus 2/6 postage and insurance.

**Ice-Stat**

This is a small thermostat which cuts on and off at around freezing point. Has many uses, one of which could be an ice warning device to be fitted under your motor car. Price 7/6, post 1/-.

**Refrigerator Thermostat**

Standard type with adjustment for all normal refrigerator temperatures, 7/6, plus 1/- post.

**Simmerstat Heater Regulator**

Suitable to control elements, heater, soldering irons and boiling rings up to 2,500 watts. Complete adjustable, normal price 55/- each, special snip price 12/6, plus 1/6 postage and insurance.

**15 amp. Thermostat**

Adjustable over a fairly wide range of temperatures but set for 70°F., suitable for wall mounting to control room heaters. Exceptional bargain at 9/6, plus 1/- post and insurance.

**ELECTRONICS (CROYDON) LTD**  
266 LONDON ROAD, WEST CROYDON, SURREY,  
(Opposite SAVOY CINEMA)

## SERVICE SHEETS

**SERVICE SHEETS.** Radio and Television, 3/6, post paid. VEST AND EMERY, 17 Halgarth Street, Durham.

**SERVICE SHEETS:** Radio, TV, 5,000 models. List 1/-. S.A.E. inquiries TELRAY, 11 Mauland Bank, Preston.

**SERVICE SHEETS:** Radio and TV, 4/- each. List 2/-. All orders dispatched on day received. Also Manuals for sale and hire. List 1/-. S.A.E. please. SULTAN RADIO, 29 Church Road, Tunbridge Wells, Kent.

**S.P. DISTRIBUTORS** is now under New Management. Try our streamlined service. We supply SERVICE SHEETS for Radios, Televisions, Tape Recorders, Amplifiers, etc. etc. by RETURN OF POST at 4/- each plus postage. Send S.A.E. with inquiries. List 1/6, plus postage. Mail orders only please to S.P. DISTRIBUTORS, 44 Old Bond Street, London W1.

**TRADE SERVICE SHEETS** offered by retired engineer. If I haven't got it you won't get it. All 4/- each by return. Please include large S.A.E. Mail orders only. ETZIONI, 80 Merrion Avenue, Stanmore, Middx.

**S.E.S. SERVICE SHEETS** for all TV, Radio, including Transistors, Tape Recorders, Echo Units, Amplifiers, Record Players and Autochangers, etc., also various domestic appliances. List 1/-. S.A.E. Mail orders only. SUN ELECTRICAL SERVICES, 38 St George's Road, Hastings.

**SERVICE SHEETS** for all makes of Radio and TV, 1925-1963. Prices from 1/- with free fault-finding guide. S.A.E. inquiries. Catalogue of 6,000 models, 1/6. 125 Radio/TV Sheets covering many popular models, 21/-. Valves, modern and obsolete. Radio/TV Books. S.A.E. lists. HAMILTON RADIO, Western Road, St. Leonards, Sussex.

**TELEVISION CHARTS 1/6:** with layout details. 2/8. Makers' Service Manuals from 3/8. TV type valves BTG, B8A, B9A 2/8. All by rapid return post service. Send s.a.e. for lists: Back issues PTV 1/6. All post paid: Send now to Shaw, 64 Standish Street, Burnley, Lancs.

**SERVICE SHEETS** also Current and Obsolete Valves for sale. JOHN GILBERT TELEVISION, 1b Shepherd's Bush Road, London. W12. Phone: SHE 8441.

## BOOKS &amp; PUBLICATIONS

**AUDIO,** America's foremost journal. Year's subscription 43/-. specimen copy 4/-. All American radio journals supplied—list free. WILLEN (Dept. 40), 61a Broadway, London, E15.

**FIND TV SET TROUBLES IN MINUTES** from the great book The Principles of TV Receiver Servicing. 10/6 all book houses and radio wholesalers. If not in stock from Dept. B Secretary, 32 Kidmore Road, Caversham, Reading, Berks.

From **GORDON J. KING LIMITED**  
6 NEW ROAD, BRIGHAM, DEVON.  
Tel: Brigham 2304

**NOW! THE "KING FM-BOOSTER"**  
(Latest VHF Transistor Printed Ckt.)

- ★ For Better Fringe FM Reception.
- ★ Improved Limiting clears Interference.
- ★ For FM DX Reception, etc.
- ★ 6 Times Signal Gain (16dB).
- ★ Battery (7P4) Powered.
- ★ Only 23.18.0 (inc. Battery, P. & P.).


**RATES:** 7/3 per line or part thereof average five words to line, minimum 2 lines, Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertiser Manager "Practical Wireless", Tower House, Southampton St., London W.C.2.

## RECEIVERS &amp; COMPONENTS

## MARGON CANADIAN RECEIVER

No. 52

(Brand New)

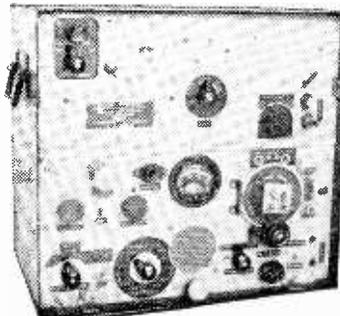

## AMATEUR SHIPPING BROADCAST

**MAGNIFICENT 10 VALVE RECEIVER.** 3 waveband 1.75-16 Mc/s 19-170 metres, with 3 valve xtal calibrator, speaker and phone outputs, complete for 230/240 AC mains and 12V DC. BRAND NEW, £14. Carriage £1.

**USED (less Case) Receiver only, £6.10.0.** Carriage 10/-. All fully tested before dispatch with circuits.

**WS N019 MK III, TXRC.** 2.8 Mc/s with economy power pack 12/24V DC. Excellent condition 80/-. Carriage 25/-. set only 55/-. Carriage 15/-. All parts available.

**TXRC, 12 valve superhet 12V DC operation,** freq. 60-95 Mc/s ideal 2 or 4 metre mobile rig, easily converted, suggested mods. and circuit supplied, internal speaker and phone outputs. Size approx. 14 x 13 x 7in. UNUSED, £8.10.0. Carriage 10/-.

**TRANSMITTER, 1.75-16 Mc/s 3 waveband** tuneable, grid modulation using 613. Used complete with all valves, circuit £7.10.0. Carriage 10/-.

**COMMAND RECEIVERS.** BC455-B 6-9.1 Mc/s each at 60/-. Post 5/-. BRAND NEW.

**ROTARY TRANSFORMERS.** 12V DC input, 300V DC 130mA output, note size only 4 x 2in. 15/-. Post 2/6.

**CONVERTER.** 12 to 230V 100mA vibrator type, complete spare vibrator, battery clips, fuse, etc. UNUSED 25/-. Carriage 5/-.

**MOVING COIL HEADPHONES.** BRAND NEW. Chancels padded, complete with jack plug 15/6. Post 2/-.

**SET OF VALVES** for 52 Receiver. 13 in all with vibrator 12/6. Post 2/6.

**MICROAMMETERS.** 2in. FSD 0-100 moving coil mounted in case 5 x 5 x 3in. with shock mounts, max/min sensitivity switch, 30V, Post 5/-. Many other bargains. List 6d. S.A.E. inquiries.

**TXRC, 1966, 124-156 Mc/s.** Complete 21 valves. Excellent condition. £6.10.0. Carr. 10/-.

A. J. THOMPSON

"ELLING LODGE"

CODICOTE, HITCHIN, HERTS.

Phone: Codicote 242

## RECEIVERS &amp; COMPONENTS

(continued)

**TRANSISTORS** now half-price unmarked but tested packets of 16; unmarked untested packets of 40, duds suitable as diodes, packets of 80. All packets 40/- each, postage 1/-. Four packets post free. C.W.O. K. R. WHISTON (Dept. PWT), New Mills, Stockport.

**REPANCO.** Lists. Circuits to build. 6d. stamps. Poleshill Road, Coventry.

**A.1. POST FREE BARGAINS.** Oriental crystal microphone inserts 6/8 each. Acos type 6/- each. GEX25 diodes 1/3 each. Guaranteed set tested valves, EP80, EB91, 10E1 9d. each, 3 for 1/6. L63, EOL80, 2/- each. PZ30, EL38, PL33, PY31 2/6 each. PY81 3/-. KT36, B36, 20P1, 27SU 4/- each. N37, U281 4/3 each. ECC82 4/6. EB41, EBC41, ECC81, EL42, PL81, 6C13, 10C2, 6LD20, 20L1, EL33 5/- each. 30P4, 53KU, PL36, 6/6 each. PL82, PL83, PY80, PY82, PCF80 3/6 each. Send for full list of valves. A.1. RADIO COMPONENTS, 14 The Borough, Canterbury, Kent.

## NEW VALVES GUARANTEED!

|      |      |        |     |        |     |
|------|------|--------|-----|--------|-----|
| 1D5  | 5/-  | 6X5G   | 4/6 | PEN96C | 5/- |
| 1L4  | 1/11 | 7C5    | 5/- | PCL82  | 7/6 |
| 1T4  | 2/6  | 25L6GT | 4/6 | EZ41   | 5/6 |
| 1R5  | 4/11 | C1C    | 5/- | PCL84  | 5/- |
| 6B3  | 3/11 |        |     | PCL85  | 7/6 |
| 6K7G | 1/3  | CY31   | 5/- | PEN44  | 5/- |
| 6BW7 | 4/6  | ECC85  | 5/- | R19    | 7/- |
| 6X4  | 3/6  | PEN46  | 2/6 | TY86F  | 6/- |

Cash with order only. Postage 6d. per valve. Any parcel insured against damage in transit 6d. extra.

**A.D.A. MANUFACTURING Co.,**  
172 Alfreton Road, NOTTINGHAM.

**WANTED: VALVES, TRANSISTORS, Etc.**  
Bought for Cash.

**DIRECT TV REPLACEMENTS LTD.,** largest stockists of TV Components in the U.K. Line Output Transformers, Frame Output Transformers, Deflector Coils for most makes. Official sole suppliers for many set makers. Same Day Dispatch Service. Terms C.O.D. or C.W.O. Send S.A.E. For quotes. Day and Night Telephone GIPSY Hill 6166, 126 Hamilton Road, West Norwood, SE27.

**STOCK CLEARANCE** Valves, Condensers, Resistors, Transformers. Mail only. Bargain lists. 98 Greenway Avenue, E.17.



**EXPERIMENTERS' BARGAIN**  
Transceiver SC1532, 100 to 150 Mc/s. Crystal controlled (no crystals). Receiver section, valves, 3 of 12G7, 12C6, 12A7, 12J5, 3 of 9003, 9002, 12H6, 30/- post paid. Transmitter, part stripped, valves, 6S57, 3 of 12A6, 6C6, 2 of 832 includes modulation transformer, etc., 25/- post paid. Both units in rack, sent by rail for 50/-. Complete with all valves and in good clean condition. I.X. Police V.H.F. Receivers, approx. 80 to 90 Mc/s. Built in 230 volt A.C. power supply and 6in. speaker. Supplied in good used condition less crystal. Complete with 11 valves, £3, carriage paid. Meter—2in. square 0-500 microamp used, tested, 8/6, post 1/6. Telephone Wire, 500 yards twin plastic covered, only 35/-, carriage paid. Transmitters type 88, no attachments, 50/-, post paid.



**RECEIVERS & COMPONENTS**

(continued)

"WEATHKITS" can now be seen in London and purchased on easy terms. Free brochure. **DIRECT TV REPLACEMENTS LTD.**, Dept. PW7/9, 126 Hamilton Road, West Norwood, SE27. GIPSY Hill 6166.

**SPEAKER REPAIRS**, Cones fitted. Satisfaction guaranteed. L. S. **REPAIRS**, Pluckley, Ashford, Kent.

**100% TUBES!** Famous make Rescreened, rebuilt, £4.15.0. Guaranteed year. 70°, 90°, 110°. Carriage 12/6. Mullard, Mazda, etc. **NEW BOXED VALVES**, 12 months' guarantee! POC84, PY800/1, PCL82, EF183, EF184, BY100, BY101, etc. 7/6 each. PL81, UZ2, EF86, EC1245, PCF80, U191, PL33, etc. 9/- each. PY33, 30P12, 9/8 each.

**PHILIP BEARMAN**

43 Leicester Road, New Barnet

Tel: BAR 1934 (Any time)

LISTS FREE. SAME DAY SERVICE.

**EXCEPTIONAL VALUE:** Picture Tubes, brand new, Mazda 19in., CME901, Mullard 19in., AW47-90-91, £4 10/-; Mullard 23in., AW50 90, £6 10/-; carriage (insured) paid 12 months' guarantee. Note: All brand new. We also supply most other sizes completely regunned at £4/17/6, guaranteed 12 months. **TOMLINS**, 156 Lewisham Way, New Cross, SE14. TID 3857.

**CRYSTAL CALIBRATOR No. 7 MK. 1** using 6 valves, a 1 Mc/s crystal osc. is used to synchronise 2 multi-vibrator osc. operating at 10 Kc/s and 100 Kc/s respectively. Harmonics of 10-100 and 1,000 Kc/s are available up to 20 Mc/s, far beyond this on any sensitive set, modulator also incorporated for receiving. In small Bakelite case with carrying handle, power 2 v. L.T., 80-120 v. H.T. Circuit and instructions supplied. **BRAND NEW, 70/-, Post 5/-.**



**WAVE-METER INDICATOR Type 230.** Using plug-in wave-meter boxes into a 7-valve sensitive amplifier and indicator unit, means operated 100-250 volts. Power unit at rear on a small separate chassis supplying 350V. D.C. at 100mA full wave rectified and 6.3 volts 4 amps I.T. Each supplied new or as new with a V.H.F. or U.H.F. wave-meter box and all connectors in wooden transit case. Wave-meter boxes easily made to all frequencies. Containing coil tuned by variable condenser, output in series with diode to input socket on indicator unit. Price for this essential piece of equipment, only 50/-, carr. 7/6.



**J. T. SUPPLY (Dept. H)**  
159 MEADOW LANE, LEEDS 11  
CALLERS WELCOME

**RECEIVERS & COMPONENTS**

(continued)

**No. 3 BUMPER PARCEL**

- 6 Assorted ex-government valves.
  - 6 Wander plug sockets—sorry no plugs.
  - 6 Pairs of Brass instrument case safety hooks.
  - 1 Electro magnetic counter 10 Imp. per sec.
  - 3 Assorted Mains Dropper Resistances.
  - 3 Yards of insulating sleeving.
  - 1 Post Office telephone fuse box with fuses.
  - 12 Assorted car bulbs, 6 volt and 12 volt.
  - 3 M.E.S. panel lamp bulbs, 6 volt.
  - 12 Sheets of carbon paper.
  - 50 Tubular condensers assorted.
  - 12 High stability resistors, assorted.
  - 12 Assorted valve bases.
  - 6 Valve retainers.
  - 1 Clockwork timing mechanism intended for blowing up rockets?
  - 1 12 Volt vibrator mallery, 4 pin.
  - 2 Red bezels for panel lamps.
  - 3 Telephone cords braided, 90in. long.
  - 1 Speaker, 3 ohm.
  - 2 Crystal adaptors.
  - 4 doz. Cartridge fuses.
  - 6 Transistor clips.
  - 1 Pair test leads with prods and spades.
- (These need cleaning and oiling, new but bad storing)

20/- Post Free, Two Parcels for 35/-

**Signal Generator Type 106.** Made by Salford Electric, 5.5 to 55 Mc/s. With charts, leads, plugs, in original case. **BRAND NEW.** Free delivery. £7.10.0.

**BREAKDOWN UNITS**  
**Transmitter Receiver Control Box** containing 7 instrument knobs, 4 toggle switches, 3 rotary switches, 20 small potentiometers, 2 Plessey Sockets, cases rough but components O.K. 5/- each, post paid or 2 for 10/-.

**19" RACK FITTING CABINET.** 34" high by 21" deep with telescopic drawer slides. Louvred sides, back and top. Brand new Swedish make. £4.0.0 only, plus B.R.S. delivery.

ECR35 Tube with Screen and Base with data, 25/-.

5UP7 Tube with Screen and Base, with data, 30/-.

20ft. Steel Telescopic Mast, 50/-.  
High Stab Resistors, 6d. each.

**MONITOR 56** is a high-speed triggered oscilloscope, comprising indicating Unit Type 248, Power Unit 675 and Follow-up Unit 68, with connecting cables. A minimum 30v. is required to trigger. Amplifier has flat response to 1.5Mc/s. Indicator may be used with external Timebases and Signal Amps. at rear links. Valve heaters run continuously; H.T. only, being switched ON/OFF on front panel. Valve functions: V1(a), V2, V3, V4(a), V5, V6, V7, V17 Trigger stage, V8, V9 Sawtooth Generator, V10, V11, V12 "X" plates paraphase amp, V13, V14 paraphase amplifier for signal (video) "Y" plates. Meter: use 5v. for scale x 20; 20v. for 5; 100v. for Direct; 500v. for divide by 5. With circuit and leads, probe, etc., £8, plus carriage 15/-.

A LIMITED NUMBER OF TRANSMITTERS AND RECEIVERS WITH FULL DETAILS. 19" Rack Fittings to Fit Swedish Cabinets. Send large envelope addressed for details.

Also a good range of Transformers.

**E. R. NICHOLLS**

Mail Order and Retail Shop:

46 LOWFIELD ROAD

off SHAW HEATH, STOCKPORT  
CHESHIRE.

**RECEIVERS & COMPONENTS**

(continued)

**RECEPTION SET R220 MK 2**

14-valve double superhet crystal controlled. From 60 to 100 meg. according to crystal used. Built-in stabilised P.P. internal speaker phone output. Brand new. Supplied with circuit and modification details. For 72-144 meg. etc.

£3.10.0 Post Free.

Separate Circuit and Modification kit, 25/-, Post Free.

Large quantity of H.T. and L.T. Transformers and Smoothing Chokes. Just listed also Jones' Plugs and Sockets, with Leads, Plessey Plugs and Sockets, Co-ax. Plugs, Locking, low loss in Standard and Miniature. Send large addressed envelope for full lists of these and other components on stock.

Copper Laminate Board, single or double sided. 5/- per square foot panels, either type 3 ft. by 4 ft. 33/-.

Mains Neons with moulded base and fixing screws, 3/6 set.

Magslips, Selsyns, Indicators, 50 volts; 115 volts, 230 volts.

Assorted Instrument Knobs, 4/- doz. Valve holders, 5/- per 24.

High Stab Resistors, 5% 6d., 2% 9d., 1% 1/-, Every six packed in 7-compartment linen finish component box. Unmarked.

Assorted Resistors, 50 carbon plus 50 high stab. My choice. 7/6.

Reflected Power Meter or Standing Wave Ratio Indicator Unit, and other kit including 500 micro amp. meters, plugs, sockets, leads, switch, circuit, instructions, 144 meg. Complete 35/-.

144 meg. Harmonic Filter with all plugs, sockets, leads. 25/-.

Speakers, 3 ohm P.M. 5in. 5/-, 6in. 6/-, 7 x 4in. 7/-, 8in. 8/-, 10in. 12/6.

Trade enquiries invited for large quantity OC201 Transistors, Printed Circuit Board, 50 mfd at 70 volts Sub. Min. Condensers.

**E. R. NICHOLLS**


Mail Order and Retail Shop:

46 LOWFIELD ROAD

off SHAW HEATH, STOCKPORT  
CHESHIRE.

## RECEIVERS &amp; COMPONENTS

(continued)

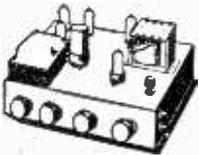GUITAR AMPLIFIERS  
WITH TREMOLO

15 watt Valves  
ECC83, ECC83,  
ECC83, EL84,  
E281, 30  
watt Valves  
ECC83, ECC83,  
ECC83, EL34,  
EL34, GZ34. Four  
jack inputs. Six  
controls: two  
volume, bass,  
treble, tremolo

speed, depth. Remote plug. 3 and 15 ohms  
outputs.

15 watt tremolo kit £9.10.0; Factory built  
£19.10.0. 30 watt tremolo kit £12.10.0;  
Factory built £15.10.0.

## LESS TREMOLO:

15 watt 2 input kit £8; Factory built (illus.)  
£10.10.0. 15 watt 4 input kit £8.10.0; Fac-  
tory built £11.30 watt 4 input kit £11.10.0;  
Factory built £14.

Add carr. 7/6 any amplifier.

Send for free leaflet.

## STROUD AUDIO

FAGANHILL LANE, STROUD, GLOS.

## FOR SALE

LOUDSPEAKERS: 6 1/2 in. round, 7 in. x  
4 in. elliptical 3 ohm. Fully Guarant-  
eed 7/6 Post Free. THE HOUSE OF  
WAX, 141-143 Lake Road, Portsmouth.

**240-ELECTRIC POWER** ADVANCED

ANYTHING from 12 or CAR BATTERY

AMERICAN DYNAMOTOR UNIT

Input 12, 24, 36, 48, 60, 72, 84, 96, 108, 120, 144, 168, 180, 216, 228, 270, 324, 360, 432, 480, 540, 600, 648, 720, 756, 810, 864, 900, 936, 972, 1008, 1044, 1080, 1116, 1152, 1188, 1224, 1260, 1296, 1332, 1368, 1404, 1440, 1476, 1512, 1548, 1584, 1620, 1656, 1692, 1728, 1764, 1800, 1836, 1872, 1908, 1944, 1980, 2016, 2052, 2088, 2124, 2160, 2196, 2232, 2268, 2304, 2340, 2376, 2412, 2448, 2484, 2520, 2556, 2592, 2628, 2664, 2700, 2736, 2772, 2808, 2844, 2880, 2916, 2952, 2988, 3024, 3060, 3096, 3132, 3168, 3204, 3240, 3276, 3312, 3348, 3384, 3420, 3456, 3492, 3528, 3564, 3600, 3636, 3672, 3708, 3744, 3780, 3816, 3852, 3888, 3924, 3960, 3996, 4032, 4068, 4104, 4140, 4176, 4212, 4248, 4284, 4320, 4356, 4392, 4428, 4464, 4500, 4536, 4572, 4608, 4644, 4680, 4716, 4752, 4788, 4824, 4860, 4896, 4932, 4968, 5004, 5040, 5076, 5112, 5148, 5184, 5220, 5256, 5292, 5328, 5364, 5400, 5436, 5472, 5508, 5544, 5580, 5616, 5652, 5688, 5724, 5760, 5796, 5832, 5868, 5904, 5940, 5976, 6012, 6048, 6084, 6120, 6156, 6192, 6228, 6264, 6300, 6336, 6372, 6408, 6444, 6480, 6516, 6552, 6588, 6624, 6660, 6696, 6732, 6768, 6804, 6840, 6876, 6912, 6948, 6984, 7020, 7056, 7092, 7128, 7164, 7200, 7236, 7272, 7308, 7344, 7380, 7416, 7452, 7488, 7524, 7560, 7596, 7632, 7668, 7704, 7740, 7776, 7812, 7848, 7884, 7920, 7956, 7992, 8028, 8064, 8100, 8136, 8172, 8208, 8244, 8280, 8316, 8352, 8388, 8424, 8460, 8496, 8532, 8568, 8604, 8640, 8676, 8712, 8748, 8784, 8820, 8856, 8892, 8928, 8964, 9000, 9036, 9072, 9108, 9144, 9180, 9216, 9252, 9288, 9324, 9360, 9396, 9432, 9468, 9504, 9540, 9576, 9612, 9648, 9684, 9720, 9756, 9792, 9828, 9864, 9900, 9936, 9972, 10008, 10044, 10080, 10116, 10152, 10188, 10224, 10260, 10296, 10332, 10368, 10404, 10440, 10476, 10512, 10548, 10584, 10620, 10656, 10692, 10728, 10764, 10800, 10836, 10872, 10908, 10944, 10980, 11016, 11052, 11088, 11124, 11160, 11196, 11232, 11268, 11304, 11340, 11376, 11412, 11448, 11484, 11520, 11556, 11592, 11628, 11664, 11700, 11736, 11772, 11808, 11844, 11880, 11916, 11952, 11988, 12024, 12060, 12096, 12132, 12168, 12204, 12240, 12276, 12312, 12348, 12384, 12420, 12456, 12492, 12528, 12564, 12600, 12636, 12672, 12708, 12744, 12780, 12816, 12852, 12888, 12924, 12960, 12996, 13032, 13068, 13104, 13140, 13176, 13212, 13248, 13284, 13320, 13356, 13392, 13428, 13464, 13500, 13536, 13572, 13608, 13644, 13680, 13716, 13752, 13788, 13824, 13860, 13896, 13932, 13968, 14004, 14040, 14076, 14112, 14148, 14184, 14220, 14256, 14292, 14328, 14364, 14400, 14436, 14472, 14508, 14544, 14580, 14616, 14652, 14688, 14724, 14760, 14796, 14832, 14868, 14904, 14940, 14976, 15012, 15048, 15084, 15120, 15156, 15192, 15228, 15264, 15300, 15336, 15372, 15408, 15444, 15480, 15516, 15552, 15588, 15624, 15660, 15696, 15732, 15768, 15804, 15840, 15876, 15912, 15948, 15984, 16020, 16056, 16092, 16128, 16164, 16200, 16236, 16272, 16308, 16344, 16380, 16416, 16452, 16488, 16524, 16560, 16596, 16632, 16668, 16704, 16740, 16776, 16812, 16848, 16884, 16920, 16956, 16992, 17028, 17064, 17100, 17136, 17172, 17208, 17244, 17280, 17316, 17352, 17388, 17424, 17460, 17496, 17532, 17568, 17604, 17640, 17676, 17712, 17748, 17784, 17820, 17856, 17892, 17928, 17964, 18000, 18036, 18072, 18108, 18144, 18180, 18216, 18252, 18288, 18324, 18360, 18396, 18432, 18468, 18504, 18540, 18576, 18612, 18648, 18684, 18720, 18756, 18792, 18828, 18864, 18900, 18936, 18972, 19008, 19044, 19080, 19116, 19152, 19188, 19224, 19260, 19296, 19332, 19368, 19404, 19440, 19476, 19512, 19548, 19584, 19620, 19656, 19692, 19728, 19764, 19800, 19836, 19872, 19908, 19944, 19980, 20016, 20052, 20088, 20124, 20160, 20196, 20232, 20268, 20304, 20340, 20376, 20412, 20448, 20484, 20520, 20556, 20592, 20628, 20664, 20700, 20736, 20772, 20808, 20844, 20880, 20916, 20952, 20988, 21024, 21060, 21096, 21132, 21168, 21204, 21240, 21276, 21312, 21348, 21384, 21420, 21456, 21492, 21528, 21564, 21600, 21636, 21672, 21708, 21744, 21780, 21816, 21852, 21888, 21924, 21960, 21996, 22032, 22068, 22104, 22140, 22176, 22212, 22248, 22284, 22320, 22356, 22392, 22428, 22464, 22500, 22536, 22572, 22608, 22644, 22680, 22716, 22752, 22788, 22824, 22860, 22896, 22932, 22968, 23004, 23040, 23076, 23112, 23148, 23184, 23220, 23256, 23292, 23328, 23364, 23400, 23436, 23472, 23508, 23544, 23580, 23616, 23652, 23688, 23724, 23760, 23796, 23832, 23868, 23904, 23940, 23976, 24012, 24048, 24084, 24120, 24156, 24192, 24228, 24264, 24300, 24336, 24372, 24408, 24444, 24480, 24516, 24552, 24588, 24624, 24660, 24696, 24732, 24768, 24804, 24840, 24876, 24912, 24948, 24984, 25020, 25056, 25092, 25128, 25164, 25200, 25236, 25272, 25308, 25344, 25380, 25416, 25452, 25488, 25524, 25560, 25596, 25632, 25668, 25704, 25740, 25776, 25812, 25848, 25884, 25920, 25956, 25992, 26028, 26064, 26100, 26136, 26172, 26208, 26244, 26280, 26316, 26352, 26388, 26424, 26460, 26496, 26532, 26568, 26604, 26640, 26676, 26712, 26748, 26784, 26820, 26856, 26892, 26928, 26964, 27000, 27036, 27072, 27108, 27144, 27180, 27216, 27252, 27288, 27324, 27360, 27396, 27432, 27468, 27504, 27540, 27576, 27612, 27648, 27684, 27720, 27756, 27792, 27828, 27864, 27900, 27936, 27972, 28008, 28044, 28080, 28116, 28152, 28188, 28224, 28260, 28296, 28332, 28368, 28404, 28440, 28476, 28512, 28548, 28584, 28620, 28656, 28692, 28728, 28764, 28800, 28836, 28872, 28908, 28944, 28980, 29016, 29052, 29088, 29124, 29160, 29196, 29232, 29268, 29304, 29340, 29376, 29412, 29448, 29484, 29520, 29556, 29592, 29628, 29664, 29700, 29736, 29772, 29808, 29844, 29880, 29916, 29952, 29988, 30024, 30060, 30096, 30132, 30168, 30204, 30240, 30276, 30312, 30348, 30384, 30420, 30456, 30492, 30528, 30564, 30600, 30636, 30672, 30708, 30744, 30780, 30816, 30852, 30888, 30924, 30960, 30996, 31032, 31068, 31104, 31140, 31176, 31212, 31248, 31284, 31320, 31356, 31392, 31428, 31464, 31500, 31536, 31572, 31608, 31644, 31680, 31716, 31752, 31788, 31824, 31860, 31896, 31932, 31968, 32004, 32040, 32076, 32112, 32148, 32184, 32220, 32256, 32292, 32328, 32364, 32400, 32436, 32472, 32508, 32544, 32580, 32616, 32652, 32688, 32724, 32760, 32796, 32832, 32868, 32904, 32940, 32976, 33012, 33048, 33084, 33120, 33156, 33192, 33228, 33264, 33300, 33336, 33372, 33408, 33444, 33480, 33516, 33552, 33588, 33624, 33660, 33696, 33732, 33768, 33804, 33840, 33876, 33912, 33948, 33984, 34020, 34056, 34092, 34128, 34164, 34200, 34236, 34272, 34308, 34344, 34380, 34416, 34452, 34488, 34524, 34560, 34596, 34632, 34668, 34704, 34740, 34776, 34812, 34848, 34884, 34920, 34956, 34992, 35028, 35064, 35100, 35136, 35172, 35208, 35244, 35280, 35316, 35352, 35388, 35424, 35460, 35496, 35532, 35568, 35604, 35640, 35676, 35712, 35748, 35784, 35820, 35856, 35892, 35928, 35964, 36000, 36036, 36072, 36108, 36144, 36180, 36216, 36252, 36288, 36324, 36360, 36396, 36432, 36468, 36504, 36540, 36576, 36612, 36648, 36684, 36720, 36756, 36792, 36828, 36864, 36900, 36936, 36972, 37008, 37044, 37080, 37116, 37152, 37188, 37224, 37260, 37296, 37332, 37368, 37404, 37440, 37476, 37512, 37548, 37584, 37620, 37656, 37692, 37728, 37764, 37800, 37836, 37872, 37908, 37944, 37980, 38016, 38052, 38088, 38124, 38160, 38196, 38232, 38268, 38304, 38340, 38376, 38412, 38448, 38484, 38520, 38556, 38592, 38628, 38664, 38700, 38736, 38772, 38808, 38844, 38880, 38916, 38952, 38988, 39024, 39060, 39096, 39132, 39168, 39204, 39240, 39276, 39312, 39348, 39384, 39420, 39456, 39492, 39528, 39564, 39600, 39636, 39672, 39708, 39744, 39780, 39816, 39852, 39888, 39924, 39960, 40000.

## GET PLASTERED !! FREE

POWING TROWEL WITH EACH ORDER OVER  
45/-.

RESISTORS, Carbon 10-4 meg. 1/5 watt 2/- doz.  
DROPPERS, 15Ω-20K 1/6. POTENTIOMETERS,  
10Ω-2 meg. 1/6. CONDENSERS, Ceramic (2-1000pF),  
8/Mica (5.2-80,000pF), M/Mica 0.00002-0.1 mfd,  
8/- doz., Ppr Tube (0.001-0.5 mfd), 4/- doz., Block  
Tpr (0.001-8 mfd), 3/6. Metalpack (0.05-4 mfd), 6d.  
ELECTROLYTICS (2-8 mfd), 1/6; (9-900 mfd), 2/8;  
501-14,000 mfd), 3/6. TRIMMERS, 1-6 gang, 5/- doz.  
SWITCHES, Water 1-3 gang, 2/8. Biscuits, 9d.  
Holders, 2/8. Add-ons D/F, 1/8. VALVE HOLDERS,  
3/6; 350, BQ, B2, B4, B5, 6d. (or 3/6 each, doz.,  
Inc. PC Types). TAG STRIPS, 1, 2, 3, 7 way, 1/6 doz.  
9, 10, 11 way, 5/- doz. TENSION SPRINGS, 1 1/2-1 1/2  
inch, 3/- doz., 3 inch 4d., 5 inch 5d. SOCKETS, 2, 3, 4,  
5, 6, 8-pin, 2/- 1 doz. COLLS, Aladdin, 1/-; Wherite  
1/6; Others 4/9 1 doz. Formers, 2d. BULBS, 6-10V  
assort., 4/6 1 doz. COND. CLIPS 1-1 1/2 inch, 1/6 1 doz.  
VERT. 1-1 inch, 2/8 1 doz. 2 inch 6d. KNOBS,  
brown, 2/-, or assort. 3/6 doz. INSULATION BOARD,  
258 sq. in. for 4/6. GROMMETS & SLEEVES, 1/-  
per 100. FELT WASHERS, 25 for 1/- 25 assort.  
CLAMPS & BRACKETS, 3/8. RECTIFIERS 2d.  
POCKET VOLTMETERS 9/6. PULSE GENERATOR  
1/6. VALVE VOLTMETERS (Less Mtr. Memnt.),  
7/8. BC-1094-A CONTROL UNITS, 75/-, 4-Valve  
MODULATOR UNIT, 11/6. AGC P.F. 11/-,  
5-WATT AMPLIFIER KIT 65/6. 5W RADIO KIT  
67/6. RF50A 1/6. CONTROL UNIT No. 3 Mk. I, 5/-  
50 SELF TAP SCREWS, 2/8. SLEEVING, 1 d. yd.  
TEST SET MICROPHONE & RECEIVER No. 4,  
25/-, 8 amp. 2 pin sw. Skis, 1/-, LARGE SELEC-  
TION OF ABOVE COMPONENTS (No. 240)  
GUARANTEED BARGAIN, 10/-, 7 TV POTS on  
Strip, 7/6. Dimmer Switches, 7/6. ALL COM-  
PONENTS ARE NEW. Please add small amount  
for P. & P. S.A.E. for List. 1/- for Catalogue.

## ALBATROSS ENGINEERING COMPANY

Dept. FW12, 75-80 HIGH STREET, GOSBERTON,  
SPALDING, LINCS. (Gen. 458)

## FOR SALE

(continued)

## YOU COULD READ MORSE BY MARCH

By using the RHYTHM METHOD  
of Morse tuition a student, start-  
ing from scratch, has passed his  
Morse Test in just 13 DAYS by  
faithfully following the instruc-  
tions given in this fantastic  
course. You could pass the test  
NEXT MONTH. For explanatory  
booklet please send 6d. in stamps to:  
G3CHS 45 GREEN LANE,  
PURLEY, SURREY

## GUARANTEED TRANSISTORS

2/- each, XA101, XA102, XB103,  
XB104, XA112, OC430.

3/6 each, GET16, GET20, GET  
884, GET873, 250mW ZENER  
DIODES 4 volts to 22 volts,  
OC44, OC45, OC71, OC81D,  
OC81.

4/- each, OC170, OC171, AF117,  
XU611, GET671, GET672, GET  
673, GET691, GET692, GET693,  
GET694, GET884.

5/- each, OC309, OC320, OC703,  
OC800, OC46, OC47, ORP60,  
and many more.

LARGE STOCKS of Mullard,  
Mazda, Bush, G.E.C., Impex,  
A.E.I.

Send 3d. stamp for full list.

## B.W. CURSONS

78 BROAD STREET  
CANTERBURY, KENT

FANTASTIC  
BARGAIN OFFER!ELECTRIC  
SOLDERING IRON

Lightweight Pistol Grip handle,  
40 watt, 240/250v. A.C. Solid  
copper bit. Detachable handle  
forms cover for iron when not in  
use. With 4ft. Safety 3-core  
flex. Indispensable for  
every home handy-  
man. A boon to model  
makers and a necessity  
for every wireless en-  
thusiast. Offered to  
you at this new amaz-  
ing price.

ONLY  
9/6

C. H. SERVICE, Dept. P.W.  
Lusted Hall Lane, Tatsfield, Kent.

## FOR SALE

(continued)

EXCEPTIONAL Transistor Portable  
Tape Recorder, value £5/19/6, com-  
plete with crystal microphone, ear-  
phone, spools, tape, batteries, instruc-  
tions, presentation box (extra tapes  
100ft. 4/6. Ideal gift, £5/19/6. Satis-  
faction guaranteed. Postage, packing  
2/6. TOMLINS, 156 Lewisham Way,  
New Cross, SE14.

## The Wonderful 'DATROLA'

"DATROLA" transistor Electronic  
ORGAN. 2 octave. Complete and ready  
to play, with instructions and music.  
Size 14 1/2 x 5 in.



Special Offer only £4.19.6 post free  
Ideal present for all ages. Can be played  
anywhere (battery operated). Instruc-  
tional aid to music, will give endless  
hours of amusement.

DATA ELECTRONICS LTD.  
6 Hillside Gardens, Edgware, Middx.

## GOVERNMENT SURPLUS

Radio, Radar and Electronic  
Gear for Sale

SEND FOR FREE LISTS

S L A T E R

34 Lifford Street : Sheffield 9  
Yorkshire.

## WANTED

WANTED: TEST GEAR, Meters,  
Valves, Components, Communication  
Sets, Amplifiers, Letters only, HUG-  
GETT'S LTD., 2-4 Pawson's Road,  
West Croydon, Surrey.

WANTED  
VALVES ONLY

Must be new and boxed  
Payment by return.

WILLIAM CARVIS LTD.

103 North Street, Leeds 7

A PROMPT CASH OFFER for your  
surplus brand new Valves and  
Transistors. R.H.S., Beverley House,  
Mannville Terrace, Bradford 7.

## NEW VALVES WANTED

Any type, or quantity

CASH PAID

R.S.T. Valve Mail Order Co.

211A

**MISCELLANEOUS**

**YOUR KIT, Radio. Amplifier** expertly assembled and aligned. Moderate charge, prompt attention. M. JOHNSON, Ivy Cottage, The Ridgeway, Astwood Bk. Redditch, Worcs.

**KITS BUILT, repairs, alignment.** S.A.E. leaflet. KINDER, 6 Hooker Rd., Heartsease, Norwich, Norfolk.

**ELECTRONIC MUSIC?**

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes! It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swing.

Write NOW for free leaflet and further details to C. & S., 29 Maude Street, Darlington, Durham. Send 2d. stamp

**SOUND RECORDINGS**

**A UNIQUE BUY!** Recording Tape, top brand, 5 1/2 in., 1,200ft., 19/6; 7 in., 2,400ft. D.P., 28/6. P and P. 1.6 per spool. Bargains in all sizes. S.A.E. for list. E. C. KINGSLEY AND CO., 32 Tottenham Court Road, London, W1. EUSTON 6500.

**SITUATIONS VACANT**

**A.M.I. Mech. E., A.M.I. Brit. I.R.E.** City and Guilds, G.C.E., etc., brings high pay and security. "No pass—no pay" terms. Over 95% successes. For details of exams, and courses in all branches of Engineering, Building, Electronics, etc., write for 148-page handbook—free. B.I.E.T., (Dept. 242B), 29 Wright's Lane, London, W8.

**ROYAL NAVAL RESERVE**

Men between the ages of 16 and 26 and ex-servicemen with previous communication training up to the age of 40 are invited to train in their spare time as Radio and Tactical Communication Operators in the Royal Naval Reserve.

For details apply: **ADMIRAL COMMANDING RESERVES** Admiralty State Building, London, S.W.5 or ask at your nearest Royal Naval Careers Office.

**RADIO AND TV Exams, and courses** by Britain's finest Home-study School. Coaching for Brit.I.R.E., City and Guilds, Amateur's Licence, R.T.E.B., P.M.G. Cert., etc. FREE brochure from **BRITISH NATIONAL RADIO SCHOOL**, Ruesell Street, Reading.

**SITUATIONS VACANT**

(continued)

**TV AND RADIO, A.M. Brit. I.R.E., City and Guilds, R.T.E.B. Cert., etc.** on "no pass—no fee" terms. Over 95% successes. For details of exams, and courses (including practical apparatus) in all branches of Radio TV and Electronics write for 148-page handbook—free. B.I.E.T. (Dept. 242G), 29 Wright's Lane, London, W8.

**CITY AND GUILDS** (Electrical, etc.) on "no pass—no fee" terms. Over 95% successes. For details of Electrical Engineering, Applied Electronics, Automation, etc., send for our 148-page handbook, free and post free. B.I.E.T. (Dept. 242A), 29 Wright's Lane, London, W8.

**BUSINESS OPPORTUNITIES**

**IF YOU** are a Self-employed TV Service Engineer wishing to increase your profits by at least 25% and receive free technical information, send s.a.e. for details to BOX No 55.

**METAL WORK**

**METAL WORK.** All types cabinets, chassis, racks, etc., to your specifications. **PHILPOTTS METAL WORKS LTD.**, Chapman St., Loughborough.

**Cases, Chassis, Frames, etc., anything in metal.** Send your drawings for quotation. "One-off's" with pleasure. Trade enquiries welcomed.

Stove enamelled any professional finish.

*Moss Watson*

**40 MOUNT PLEASANT STREET OLDHAM, LANCs. MAIN 9400**

**EDUCATIONAL**

**BECOME "TECHNICALLY QUALIFIED"** in your spare time. Guaranteed Diploma and Exam. Home-study Courses in Radio, TV Servicing and Maintenance. R.T.E.B., City and Guilds, etc. Highly informative 120-page Guide—FREE. **CHAMBERS COLLEGE** (Dept. 363), 148 Holborn London, EC1.

**EDUCATIONAL**

(continued)

**RADIO OFFICERS** see the world. Sea-going and shore appointments. Our many recent successes provide additional trainee vacancies during 1964 Day and Boarding students. Grants and Scholarships available. Stamp for Prospectus. **WIRELESS COLLEGE**, Colwyn Bay.

**Radio Television & Electronics**

Learn at home with the world's largest home study organisation, Brit.I.R.E.; City & Guilds; R.T.E.B., etc. Also Practical Courses with equipment.

All books supplied. Write for **FREE prospectus** stating subject to

**I.C.S.**

(Dept. 541), Intertext House, Parkgate Road, London, S.W.11

**THE INCORPORATED PRACTITIONERS** in Radio & Electronics (I.P.R.E.) Ltd., Membership Condition booklet 1/-, Sample copy of I.P.R.E. official Journal 2/- post free. Dept. B Secretary, 32 Kidmore Road, Caversham, Reading, Berks.

$$X = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

**DON'T FUMBLE** with Formulae. Master Mathematics quickly and easily the Understandable Way.

**1st lesson and details FREE**

The Dryden School of **UNDERSTANDABLE MATHEMATICS** 10 C., Dryden Chambers, Oxford St., London, W.1.

Name \_\_\_\_\_  
 Address \_\_\_\_\_  
 \_\_\_\_\_  
 \_\_\_\_\_

**INCREASE YOUR INCOME  
WIDEN YOUR KNOWLEDGE  
MAKE NEW FRIENDS  
JOIN THE  
ARMY EMERGENCY RESERVE  
R.E.M.E.**

Wireless and Telecommunication mechanics with or without previous military service are required as volunteers to train for 15 days in the summer on modern equipments. Generous pay and bounties. For details write:

**HQ AER, REME, BROXHEAD HOUSE, Bordon, Hants.**

**BBC · ITV · F.M. AERIALS**



**B.B.C. (BAND 1).** Telescopic loft, 21/-, External S/D 30/-.

**I.T.V. (BAND 3).** 3 Element loft array, 25/-, 5 Element Wall mounting, 3 Element, 35/-, 5 Element, 45/-.

**COMBINED B.B.C./I.T.V.** Loft 1+3, 41/3; 1+5, 48/9. Wall mounting 1+3, 58/3; 1+5, 63/9. Chimney 1+3, 63/9; 1+5, 71/3.

**F.M. (BAND 2).** Loft S/D, 12/6; "H" 30/-, 3 Element, 52/8. External units available. Coax cable 8ft. rd. Coax plugs 1/3. C.W.O. or C.O.D. P.P. 3/- Send 6d. stamps for illustrated lists. Band IV 625 line Aerials also available.

**K.V.A. ELECTRONICS** (Dept. P.W.) 3a Godstone Road, Kenley, Surrey. CRO 2527

## Lyons Radio Ltd.

3 Goldhawk Road, London W.12

**BATTERY CHARGER or POWER UNIT for MODEL RAILWAY, etc.** Make your own using our top grade transformers and rectifiers; wiring diagram supplied.

**TRANSFORMERS.** Full wave bridge type for outputs up to 12V, D.C. 1 amp. size, 6/3; 2 amp. 8/9; 4 amp. 12/6; 6 amp. 14/6. Postage, see below.


**TRANSFORMERS.** Pri. 200/250V. A.C. mains. Sec. tapped 3t, 9 and 17V. for producing 2, 6 or 12V. D.C. respectively when used with above rectifiers. 1 amp. size 10/-; 2 amp. 14/6; 4 amp. 16/6; 6 amp. (tapped 9 and 17V.) 25/9. Postage (up to 16/3) 2/6, over 3/6.

**BATTERY CHARGERS.** Ready made for charging 6 or 12 volt batteries at 3 to 4 amps. Housed in neat metal case fitted with ammeter, mains lead, battery lead with pull-dog clips and voltage selector socket. Fully guaranteed. Genuine bargain. PRICE ONLY 65/-. post 4/6.

**"PROGRESSIVE" SHORT WAVE RECEIVER.** Specially designed kits to enable even the beginner to construct a 1 valve short wave radio with every confidence of success. A second and then a third valve stage can be added, the chassis supplied being punched to take all three stages. Can be operated from dry batteries or from a simply constructed mains power unit (Kit 32/6). Cost of all parts to make the 1 Valve Radio including 1 plug-in coil (40-100 metres) ONLY 35/-. 1 to 2 valve conversion parts 7/6, 2-3 valve conversion parts 10/-. Extra plug-in coils; 10-20, 20-40, 100-200, 200-450 metres 4/- each. Clear wiring diagrams and instructions supplied free with all parts. 1/6 separately.

**4½ WATT HIGH QUALITY AMPLIFIERS.** For 220/240V. A.C. mains or 8V. car battery. Valve line-up 6SL7, 6SK7, 6V6, 6X5. Separate gram. and mike inputs. Heavy duty output transformer for 3, 8 and 15 ohm speakers. Fully enclosed in metal case 9 x 8 x 8in. Slightly stone soiled externally otherwise as new and unused. Supplied with all valves at greatly reduced price. ONLY 67/6, post 5/6. Vibrator only needed for 8V. input. 7/6 extra if required.

### B.B.C.2 (625 LINE) T.V. AERIALS

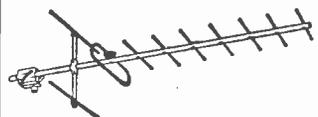

**EXTERNAL MAST MOUNTING ARRAYS**  
5 element, 36/-; 9 element, 45/-.  
**WALL MOUNTING ARRAYS with CRANKED ARM.** 5 element, 51/6; 9 element, 60/-.  
**CHIMNEY ARRAYS with LASHINGS,** etc. 5 element, 63/6; 9 element, 72/-.  
**LOFT ARRAYS.** 3 element, 24/-; 5 element, 32/6. Also available for Window Fixing, 2/6 extra. Co-ax. Plugs, 1/2.  
**Low Loss Co-axial Cable** 1/6 yd. S.A.E. for LISTS. C.W.O. or C.O.D.  
**K.V.A. ELECTRONICS** CRO 2527  
**3B GODSTONE RD. KENLEY SURREY**

## 2 METRES 4

The thrills of VHF Amateur Radio can now be yours for as low as 39/6, complete kit (by post, carriage and packing, 2/6 extra). Tuning range 70-150 Mc/s. Stamped addressed envelope for free copy of literature and full details. Newcomers to Short-Wave Radio ask for details of the famous "Globe-Kings" kits and receivers. Home and Overseas Sales.

**JOHNSONS (Radio)**  
St. Martins Gate, Worcester

## FIRST-CLASS RADIO AND T/V COURSES... GET A CERTIFICATE!

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure a recognised qualification or extend your knowledge of Radio and T.V. Let us show you how.

### FREE GUIDE

The New Free Guide contains 120 pages of information of the greatest importance to both the amateur and the man employed in the radio industry. Chambers College provides first rate postal courses for Radio Amateurs' Exam., R.T.E.B. Servicing Cert., C. & C. Telecoms., Grad. Brit. I.R.E. Guide also gives details of range of diploma courses in Radio/T.V. Servicing, Electronics and other branches of engineering, together with particulars of our remarkable Guarantee of

**SUCCESS OR NO FEE**  
Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

**FOUNDED 1885—OVER 150,000 SUCCESSES**  
**CHAMBERS COLLEGE**  
(Incorp. National Inst. of Engineering)  
(Dept. 461), 148 HOLBORN LONDON, E.C.1



The PUNCH you need!

| HOLE PUNCHES                  |     |     |     |          |
|-------------------------------|-----|-----|-----|----------|
| Instant Type                  | ... | ... | ... | 6/10 ea. |
| 3/8" diameter                 | ... | ... | ... | ...      |
| Screw-up Type                 | ... | ... | ... | ...      |
| 1 1/2" diameter Toggle switch | ... | ... | ... | 8/6 ..   |
| 1 1/2" " " " " "              | ... | ... | ... | 8/6 ..   |
| 1 1/2" " B7G                  | ... | ... | ... | 9/6 ..   |
| 1 1/2" " B8A, B9A...          | ... | ... | ... | 9/6 ..   |
| 1 1/2" " " " " "              | ... | ... | ... | 10/2 ..  |
| 1 1/2" " " " " "              | ... | ... | ... | 10/8 ..  |
| 1 1/2" " " " " "              | ... | ... | ... | 11/8 ..  |
| 1 1/2" diameter Int. Octal... | ... | ... | ... | 13/4 ..  |
| 1 1/2" " " " " "              | ... | ... | ... | 16/2 ..  |
| 1 1/2" " " " " "              | ... | ... | ... | 18/10 .. |
| 1 1/2" " B9G                  | ... | ... | ... | 21/8 ..  |
| 1 1/2" " " " " "              | ... | ... | ... | 24/4 ..  |
| 2 1/2" " Meter                | ... | ... | ... | 33/2 ..  |

Complete Set 49.3.6.  
No extra charge for postage and packing in the U.K.

**Oliver & Randall Ltd**  
Dept. 7  
7 KELSEY PARK ROAD  
BECKENHAM, KENT  
Tel.: Beckenham 8262

## STOP! LOOK!

**TRANSISTORS from 1/3**  
**GREEN SPOTS** 1/3 or 3 for 3/3.  
**RED SPOTS** down to 1/6 or 3 for 4/-.  
**WHITE SPOTS** down to 2/- or 3 for 5/3.  
**MICRO-ALLOY TRANSISTORS**  
**MAT100** 7/9, 101 8/6, 120 7/9, 121 8/6, ADT140 15/-.  
**EARPIECES** with Lead and Plug Crystal Type. 5/-; Low Imp. 4/-.  
**TRANSISTOR HOLDERS** 3 or 5 pin, 1/-.  
**SOLDERING IRONS**, 230 volt A.C., 12/9.  
**REACTION CONDENSERS .0001 3/-**, .0003 3/9, .0005 4/3.  
**J. B. DILEXONS .0001, .0003, .0005** all 4/9 each.

**REPANCO COMPONENTS**  
**DRX1** Crystal Set Coils with Circuit 3/-.  
**DRR2** Dual Range Coil with Reaction Winding and Circuit, 4/6.  
**FR2** Ferrite Rod Aerial, 12/6.  
**CHI** R.F. Chokes, 2/6.  
**TRANSISTOR TRANSFORMERS**  
TT49 5/-, TT46 6/-, TT45 6/-, TT23 22/6, TT24 22/6.

**MULLARD TRANSISTORS AND DIODES**  
OC70 6/6, OC71 6/6, OC44 8/3, OC45 8/-, OC72 8/-, OC81 8/-, OC25 12/-, AF102 27/6, AF114 11/-, AF115 10/6, AF116 10/-, AF117 9/6, AF124 11/-, AF125 10/6, AF126 10/-, AF127 9/6, OC170 8/6, OC171 9/-, OA70 3/-, OA81 3/-.

ALL SENT POST FREE IN U.K. by  
**PETHERICK'S RADIO SUPPLIES**  
22 HIGH STREET  
**BIDEFORD, N. DEVON**  
Tel.: Bideford 1217

## WORLD RADIO & TV HANDBOOK 1964 22/-

By JOHANSEN. Postage 1/-.  
**Amateur Radio Call Book 1964**, by R.S.G.B. 4/6. Postage 6d.  
**All in One Tape Recorder Book**, by Lloyd, 13/6. Postage 9d.  
**Introduction to Lasers and Masers**, by Lytel, 18/-. Postage 1/-.  
**Radio and Line Transmission**, by Danielson, Vol. 1 21/-. Vol. 2 22/6. Postage 1/-.  
**Using an Oscilloscope**, by Easterling, 6/6. Postage 6d.  
**British Transistor Directory**, by Bradley, 8/6. Postage 6d.  
**Transistor Circuits for Radio Controlled Models**, 7/6. Postage 6d.  
**Amateur Radio Handbook**, 3rd Ed., by R.S.G.B. 34/-. Postage 2/6.

**UNIVERSAL BOOK CO.**  
12 Little Newport Street, London, W.C.2 (adjoining Lisle Street)

## Football Pool Computer

A Novel Circuit which is cheap to build. Forecasting made easy!  
**ANALOGUE COMPUTER**  
Multiplies and Divides by electrical analogue methods. Exceedingly simple circuit. Fascinating demonstration of computer principles. Both above circuits for 3/6, post free.  
Noughts and Crosses Machine  
Full circuit of our unbeaten machine. 3/6 post free.

**MULTIMETERS**  
Circuit of 18,000 o.p.v. kit at 65/-. and details of other multimeters from 35/- on request. 1% High Stab. Resistors. Brand new 1W 2%. Many special multimeter values. 100Ω, 1K, 10K, 100K, 1Ω, 1W, 1/6 each.  
**Precision Wirewound Resistors** 1W. 1Ω to 5K, 1%, 3/-; to 20K, 1%, 4/3; 1% add 3d. Your value wound to order.

**PLANET INSTRUMENT CO.,**  
25 DOMINION AVENUE, LEEDS 7

# BENTLEY ACOUSTIC CORPORATION LTD.

Suppliers to H.M. Government. 38 CHALCOT ROAD, LONDON, N.W.1 Telephone: PRIMROSE 9090

**NEAREST UNDERGROUND: CHALK FARM. ALL GOODS LISTED BELOW ACTUALLY IN STOCK ALL GOODS ARE NEW, BEST QUALITY BRANDS ONLY, AND SUBJECT TO MAKERS' FULL GUARANTEE. PLEASE NOTE THAT WE DO NOT SELL ITEMS FROM DISMANTLED EQUIPMENT NOR MANUFACTURERS' SECONDS & REJECTS, WHICH ARE OFTEN DESCRIBED AS "NEW AND TESTED," BUT HAVE A SHORT AND UNRELIABLE LIFE**

|        |       |       |      |        |      |        |       |           |      |     |       |      |       |        |           |        |          |       |       |        |      |
|--------|-------|-------|------|--------|------|--------|-------|-----------|------|-----|-------|------|-------|--------|-----------|--------|----------|-------|-------|--------|------|
| 0A2    | 4/6   | 6BR8  | 8/-  | 6V6G   | 3/0  | 20P1   | 13/6  | AC/PEP/   | EA76 | 6/9 | EL34  | 22/- | K1Z41 | 5/6    | R16       | 29/-   | 752      | 4/6   | AF126 | 10/-   |      |
| 0B2    | 6/-   | 6BR7  | 26/- | 6V6G   | 5/6  | 20P5   | 12/3  | DD        | 23/3 | 1/6 | EL40  | 5/6  | L141  | 7/3    | L63       | 3/-    | R17      | 17/6  | 176   | 4/6    |      |
| 0Z1G   | 4/3   | 6BW6  | 6/0  | 6X4    | 3/0  | 20A6G  | 7/6   | AO/PEP/   | 4/9  | 6/3 | EL42  | 7/8  | LN352 | 6/2    | LN3       | 9/6    | LN8      | 6/78  | 678   | 3/9    |      |
| 1A3    | 2/6   | 6BW7  | 5/-  | 6X5    | 4/6  | 20A1G  | 6/-   | AO/HLLD   | 6/2  | 6/3 | EL43  | 7/6  | LN31  | 8/3    | LN309     | 7/9    | LN9      | 6/6   | LN4   | 10/6   |      |
| 1A5    | 5/-   | 6BX6  | 3/9  | 6V6G   | 9/-  | 25U4G  | 16/2  |           |      | 9/3 | EB31  | 17/- | EL83  | 6/9    | LN319     | 6/6    | R52      | 9/-   | U101  | 19/6   |      |
| 1AGT   | 7/0   | 6C4   | 2/3  | 7B6    | 12/6 | 25V5   | 7/9   | AO/PEP/   |      |     | EB41  | 4/9  | EL84  | 4/9    | LP2       | 9/6    | RLC/240A | 1/07  | 17/6  | U104   | 10/6 |
| 1C1    | 4/-   | 6C5   | 4/-  | 7B7    | 7/-  | 25Y5G  | 7/9   | (5) PEP   | 17/6 |     | EB91  | 2/3  | EL85  | 7/6    | ME41      | 15/2   |          | 1/91  | 9/6   | GET102 | 8/6  |
| 1C2    | 6/9   | 6C6   | 3/-  | 7C5    | 7/3  | 25Z4G  | 8/6   | AO/PEP/   |      |     | EB93  | 20/6 | EL86  | 7/3    | ME91      | 12/6   | KK34     | 7/6   | U201  | 9/6    |      |
| 1C9    | 6/3   | 6C8   | 3/-  | 7C6    | 6/9  | 25Z5   | 7/3   | (7) 17V   |      |     | EB93  | 8/6  | EL91  | 2/6    | M14       | 3/6    | SL30     | 22/6  | U291  | 8/9    |      |
| 1C9    | 6/3   | 6C8   | 10/9 | 7D3    | 15/- | 25Z6G  | 8/-   | AC/SG     | 22/6 |     | EB94  | 6/6  | EL93  | 6/6    | M104      | 8/-    | SP4B     | 19/6  | U292  | 12/3   |      |
| 1C8    | 13/6  | 6C10  | 7/6  | 7D5    | 15/- | 25Z8   | 23/3  | AC/SG/17V |      |     | EB94  | 6/6  | EL96  | 27/-   | M114      | 7/6    | SP13C    | 12/6  | U301  | 11/3   |      |
| 1D5    | 6/6   | 6C12  | 6/-  | 7D6    | 15/- | 25D7   | 6/9   |           |      |     | EB91  | 5/6  | EL20  | 16/4   | M116/12/6 |        | SP41     | 2/-   | U320  | 9/6    |      |
| 1D6    | 6/6   | 6C17  | 12/6 | 7D9    | 15/- | 30C1   | 5/6   | AO/TH     | 15/- |     | EB90  | 5/6  | EL22  | 16/4   | M15       | 5/9    | SP42     | 12/6  | U330  | 9/6    |      |
| 1E1    | 5/9   | 6C16G | 18/- | 7H7    | 5/9  | 30C15  | 9/-   | AO/TP     | 13/- |     | EBF8  | 7/3  | EL30  | 20/5   | M84B      | 10/5   | SP61     | 2/-   | U405  | 9/9    |      |
| 1E2    | 2/3   | 6C16  | 6/-  | 7H7    | 12/6 | 30C18  | 10/6  | AO/TP     | 11/2 |     | EBF8  | 8/3  | EL34  | 7/6    | M815      | 9/6    | SC25     | 27/2  | U404  | 3/7    |      |
| 1E3    | 2/3   | 6C14  | 2/4  | 787    | 14/6 | 30C5   | 5/9   | AO/VP     | 20/5 |     | EBL21 | 8/-  | EL34  | 11/6   | M12       | 11/4/6 | SC61     | 5/9   | U801  | 16/3   |      |
| 1FD1   | 5/9   | 6D1   | 1/6  | 7Y1    | 5/-  | 30FL1  | 9/3   | ATP4      | 2/3  |     | EB52  | 4/3  | EM35  | 12/-   | MX40      | 8/9    | T41      | 9/-   | U420  | 6/9    |      |
| 1FD9   | 3/6   | 6D3   | 9/6  | 8D2    | 2/6  | 30FL11 | 11/2  | AZ1       | 5/9  |     | 30F15 | 12/6 | EM71  | 13/6   | N57       | 23/3   | TH92     | 12/6  | VMP4G | 11/0   |      |
| 1G6    | 6/-   | 6D6   | 3/-  | 9B7W   | 9/6  | 30L1   | 5/6   | A231      | 6/6  |     | EB54  | 6/-  | EM80  | 6/3    | N7        | 26/3   | TH10     | 12/6  | VEK35 | 3/6    |      |
| 1H5GT  | 7/0   | 6D8   | 15/- | 9B7    | 9/6  | 30L14  | 6/6   | CH35      | 12/6 |     | EB51  | 6/6  | EM82  | 6/6    | N20       | 26/3   | TH12C    | 10/6  | VH48  | 12/6   |      |
| 1L4    | 2/3   | 6D3   | 9/6  | 9D7    | 9/3  | 30P1   | 12/3  | BE36      | 4/9  |     | EB41  | 27/6 | EM84  | 6/9    | N39       | 15/-   | TH30C    | 14/6  | VP2B  | 9/6    |      |
| 1L6A   | 16/10 | 6F1   | 9/6  | 10C1   | 9/3  | 30P12  | 7/6   | BL63      | 10/6 |     | EB90  | 2/6  | EM85  | 8/9    | P21       | 2/6    | TH41     | 13/-  | VP4   | 14/6   |      |
| 1LD5   | 4/-   | 6D5   | 5/6  | 10C2   | 12/3 | 30P16  | 6/-   | C1        | 12/6 |     | EB92  | 6/6  | EM87  | 15/2   | PAB80     | 6/9    | TH23     | 6/9   | VPA4  | 14/6   |      |
| 1LNS   | 4/6   | 6E6G  | 3/6  | 10H1   | 7/-  | 30P19  | 12/3  | C1        | 12/6 |     | EB91  | 7/3  | EN31  | 45/-   | PC80      | 10/3   | TP22     | 5/6   | VPA8  | 20/5   |      |
| 1NSGT  | 8/6   | 6E6GT | 7/6  | 10P2   | 12/6 | 30P14  | 12/6  | CH35      | 12/6 |     | EB92  | 6/6  | EN32  | 6/6    | PC81      | 10/3   | TP25     | 5/6   | VP18C | 2/6    |      |
| 1P1    | 5/9   | 6E9   | 9/6  | 10P1   | 10/- | 30P13  | 9/3   | CK506     | 6/9  |     | EB94  | 21/7 | EX51  | 5/9    | PC95      | 11/6   | TP2620   | 17/6  | VP28  | 9/6    |      |
| 1P10   | 5/6   | 6H11  | 17/9 | 10F9   | 9/9  | 30P14  | 12/6  | CL4       | 19/6 |     | EB93  | 5/-  | EX81  | 7/3    | PC97      | 7/9    | TPV6F    | 11/6  | VP41  | 5/6    |      |
| 1P11   | 4/6   | 6F12  | 3/-  | 10H18  | 10/- | 35A5   | 20/9  | LC33      | 11/6 |     | EB40  | 7/-  | EX83  | 9/3    | PC94      | 5/6    | CAB80    | 5/8   | VP13  | 9/6    |      |
| 1R4    | 4/-   | 6F13  | 4/9  | 10L16  | 6/3  | 35L6GT | 6/9   | CG        | 2/6  |     | EB91  | 3/6  | EX84  | 9/6    | PC95      | 5/9    | CAF42    | 1/6   | VH75  | 21/-   |      |
| 1R5    | 5/-   | 6F14  | 28/3 | 10L17  | 6/3  | 35Z4   | 10/6  | CH35      | 12/6 |     | EB93  | 4/6  | EX85  | 14/6   | PC96      | 5/9    | CAF42    | 10/6  | VH85  | 10/6   |      |
| 1R5    | 5/-   | 6F14  | 28/3 | 10L17  | 6/3  | 35Z4   | 10/6  | CH35      | 12/6 |     | EB93  | 4/6  | EX85  | 14/6   | PC96      | 5/9    | CAF42    | 10/6  | VH85  | 10/6   |      |
| 1F2    | 29/-  | 6F16  | 6/9  | 10P14  | 11/6 | 35Z4GT | 4/9   | CV1       | 16/4 |     | EB94  | 5/9  | EX91  | 3/-    | PC189     | 10/6   | CB01     | 6/3   | VT61A | 7/-    |      |
| 1T4    | 2/3   | 6F17  | 12/6 | 11D3   | 17/6 | 35Z5GT | 5/9   | CV1C      | 6/6  |     | EB95  | 6/3  | EX95  | 4/6    | PC98      | 5/6    | CF80     | 5/9   | VT61  | 3/6    |      |
| 114    | 5/6   | 6F18  | 13/5 | 11D5   | 17/6 | 40R1A  | 6/6   | CV1       | 5/9  |     | EB98  | 10/- | EX40  | 5/3    | PC92      | 6/3    | CF89     | 6/9   | VC111 | 5/-    |      |
| 1U5    | 5/3   | 6F19  | 4/9  | 11E1   | 15/- | 41RTH  | 15/-  | D15       | 17/6 |     | EB91  | 1/3  | EX41  | 5/6    | PC92      | 6/3    | CF89     | 6/9   | VC12  | 10/6   |      |
| 2A7    | 12/6  | 6E2   | 12/6 | 12D6   | 10/6 | 41RTH  | 15/-  | D15       | 17/6 |     | EB91  | 1/3  | EX41  | 5/6    | PC92      | 6/3    | CF89     | 6/9   | VC12  | 10/6   |      |
| 2A26   | 2/9   | 6E24  | 9/6  | 12A8   | 2/3  | 43     | 10/-  | D42       | 10/6 |     | EB96  | 22/6 | EZ81  | 4/-    | PC182     | 6/6    | UC94     | 8/9   | VT133 | 7/-    |      |
| 2D13C  | 7/-   | 6E26  | 5/-  | 12A8   | 16/6 | 50A5   | 21/10 | D65       | 5/-  |     | EB90  | 3/9  | EZ90  | 3/9    | PC93      | 6/9    | UC95     | 6/3   | W21   | 5/6    |      |
| 2D21   | 5/6   | 6E32  | 3/-  | 12A6C  | 6/6  | 50B6   | 6/6   | D77       | 2/3  |     | EB92  | 6/3  | FC4   | 9/9    | PC184     | 7/-    | UC92     | 8/9   | W22   | 20/6   |      |
| 2P     | 28/3  | 6E33  | 3/6  | 12A6E  | 9/6  | 50C5   | 6/6   | DA32      | 9/6  |     | EB93  | 11/6 | FC4   | 9/9    | PC185     | 7/6    | UC94     | 8/9   | W24   | 20/6   |      |
| 2X2    | 3/-   | 6E6   | 9/6  | 12C6G  | 8/-  | 50C16G | 4/9   | DA91      | 9/6  |     | EB94  | 24/6 | FC18C | 17/-   | PC186     | 9/6    | UC91     | 8/9   | W21M  | 24/6   |      |
| 3A4    | 3/9   | 6H6   | 1/6  | 12A7H  | 5/-  | 50L6GT | 6/6   | DA96      | 5/9  |     | EB93  | 21/6 | FC4   | 50/6/6 | PC188     | 12/6   | UC81     | 8/6   | W76   | 3/6    |      |
| 3A5    | 3/9   | 6J5G  | 3/-  | 12A83  | 9/-  | 52K1   | 14/6  | DC990     | 6/9  |     | EB91  | 9/9  | FC4   | 80/6/6 | PC188     | 12/6   | UC82     | 7/9   | W77   | 2/6    |      |
| 3B7    | 5/-   | 6J5GT | 4/3  | 12A7H  | 4/6  | 58K1   | 14/6  | D4        | 12/6 |     | EB93  | 22/6 | GC1C  | 9/6    | PC185     | 8/6    | UC83     | 8/6   | W77   | 2/6    |      |
| 3B9    | 3/9   | 6J6   | 3/-  | 12A7H  | 3/6  | 58K2   | 14/6  | D4        | 12/6 |     | EB93  | 22/6 | GC1C  | 9/6    | PC185     | 8/6    | UC83     | 8/6   | W77   | 2/6    |      |
| 3Q3    | 9/3   | 6K7G  | 4/6  | 12A7G  | 5/9  | 58K3   | 14/6  | D4        | 12/6 |     | EB93  | 22/6 | GC1C  | 9/6    | PC185     | 8/6    | UC83     | 8/6   | W77   | 2/6    |      |
| 3Q3GT  | 7/-   | 6K7GT | 7/-  | 12A7G  | 4/6  | 58K4   | 14/6  | D4        | 12/6 |     | EB93  | 22/6 | GC1C  | 9/6    | PC185     | 8/6    | UC83     | 8/6   | W77   | 2/6    |      |
| 384    | 4/6   | 6L8   | 12/6 | 12A7G  | 6/6  | 58K5   | 14/6  | D4        | 12/6 |     | EB93  | 22/6 | GC1C  | 9/6    | PC185     | 8/6    | UC83     | 8/6   | W77   | 2/6    |      |
| 3V4    | 5/3   | 6K6GT | 5/6  | 12A7H  | 4/6  | 58K6   | 14/6  | D4        | 12/6 |     | EB93  | 22/6 | GC1C  | 9/6    | PC185     | 8/6    | UC83     | 8/6   | W77   | 2/6    |      |
| 4D1    | 3/9   | 6K7G  | 1/3  | 12B8B  | 5/9  | 80     | 5/3   | DE72      | 30/- |     | EB90  | 6/-  | GC23  | 14/6   | PC99      | 9/6    | UC84     | 8/6   | W78   | 2/6    |      |
| 3R4G   | 5/6   | 6K7GT | 4/-  | 12B8B  | 5/9  | 88     | 15/6  | DE91      | 2/3  |     | EB92  | 7/-  | H30   | 5/-    | PC94      | 12/-   | UC99     | 9/6   | X24   | 16/6   |      |
| 5T4    | 7/-   | 6K8G  | 3/3  | 12B7H  | 6/9  | 85V    | 8/-   | DE96      | 5/9  |     | EB93  | 8/9  | H63   | 6/9    | PC98      | 10/6   | UC94     | 8/6   | X41   | 15/6   |      |
| 5U4G   | 4/6   | 6K8GT | 7/9  | 1E11   | 16/9 | 85A3   | 8/6   | DE97      | 10/6 |     | EB91  | 8/9  | ELC18 | 8/9    | HAC80     | 9/3    | PC95     | 43/10 | UC46  | 8/6    |      |
| 5V4G   | 7/6   | 6K8Z  | 24/- | 12H6GT | 1/6  | 90A6   | 6/78  | DE30      | 15/6 |     | EB6   | 20/6 | H12   | 7/6    | ELC18     | 6/-    | UC46     | 8/6   | X45   | 4/6    |      |
| 6Y3GT  | 4/6   | 6K7G  | 4/6  | 12A7G  | 5/6  | 90A6   | 6/78  | DE30      | 15/6 |     | EB6   | 20/6 | H12   | 7/6    | ELC18     | 6/-    | UC46     | 8/6   | X45   | 4/6    |      |
| 5Y4    | 9/6   | 6L6G  | 4/6  | 12G7G  | 7/6  | 90C9   | 4/2   | DE78      | 3/6  |     | EB92  | 6/6  | H123  | 3/6    | PC94      | 10/-   | UC44     | 15/2  | UC45  | 10/6   |      |
| 5Z8    | 7/-   | 6L8G  | 4/6  | 12K5   | 10/6 | 90C9   | 4/2   | DE77      | 3/6  |     | EB93  | 3/3  | H123D | 5/6    | PC94      | 10/-   | UC44     | 15/2  | UC45  | 10/6   |      |
| 5Z8    | 7/-   | 6L7GT | 4/6  | 12K7GT | 3/6  | 90C1   | 11/6  | DH81      | 23/3 |     | EB91  | 6/6  | H141  | 3/9    | PC91      | 10/-   | UC46     | 15/2  | UC46  | 10/6   |      |
| 6 30L2 | 8/3   | 6L17  | 12/6 | 12K8GT | 9/-  | 150B2  | 16/6  | DH10      | 25/- |     | EB91  | 3/9  | H141D | 18/6   | PC91      | 10/-   | UC46     | 15/2  | UC46  | 10/6   |      |
| 6A7    | 3/9   | 6L18  | 12/6 | 12K8GT | 9/-  | 150B2  | 16/6  | DH10      | 25/- |     | EB91  | 3/9  | H141D | 18/6   | PC91      | 10/-   | UC46     | 15/2  | UC46  | 10/6   |      |
| 6A6G   | 5/9   | 6L19  | 9/9  | 12K8GT | 6/9  | 11     | 13/6  | DK42      | 7/9  |     | EB91  | 3/9  | H141D | 18/6   | PC91      | 10/-   | UC46     | 15/2  | UC46  | 10/6   |      |
| 6B7    | 4/-   | 6L13  | 6/6  | 12K7   | 4/-  | 1N8BT  | 34/11 | DK40      | 18/6 |     | EB92  | 4/9  | ELF42 | 5/9    | PC91      | 10/-   | UC46     | 15/2  | UC46  | 10/6   |      |
| 6C17   | 3/-   | 6L16  | 6/6  | 12K7   | 4/-  | 215M6  | 6/6   | DK91      | 4/-  |     | EB92  | 2/6  | HN309 | 29/6   | PC91      | 10/-   | UC46     | 15/2  | UC46  | 10/6   |      |
| 6A45   | 2/6   | 6L29G | 5/6  | 12K8GT | 3/-  | 290B   | 10/6  | DK92      | 6/6  |     | EB93  | 3/6  | HVR2A | 9/9    | PC91      | 10/-   | UC46     | 15/2  | UC46  | 10/6   |      |
| 6A97   | 5/9   | 6K7GT | 5/-  | 12K7   | 5/-  | 301    | 20/-  | DR96      | 6/3  |     | EB93  | 5/-  | HVR2A | 9/9    | PC91      | 10/-   | UC46     | 15/2  | UC46  | 10/6   |      |
| 6A15   | 8/6   | 6P1   | 9/3  | 12K87  | 3/-  | 302    | 10/6  | DL33      | 7/3  |     | EB90  | 3/9  | W3    | 5/6    | EL84      | 5/6    | UC21     | 8/6   | Y63   | 5/6    |      |
| 6A5    | 4/9   | 6P25  | 6/9  | 12K87  | 8/-  | 303    | 15/-  | DL35      | 6/3  |     | EB93  | 9/9  | W4    | 35/6   | EL600     | 15/9   | UC41     | 4/6   | Y65   | 5/6    |      |
| 6A6    | 12/6  | 6P26  | 9/-  | 12K87  | 5/9  | 304    | 15/-  | DL63      | 5/9  |     | EB95  | 4/9  | W4    | 35/6   | PM84      | 9/3    | UC55     | 5/-   | Z63   | 4/6    |      |
| 6A58   | 5/6   | 6P28  | 11/6 | 12L15G | 7/-  | 305    | 13/6  | DL68      | 15/- |     | EB95  | 6/-  | W4    | 35/6   | PM        |        |          |       |       |        |      |

We supply from stock most of the components and items specified or circuits published in this and other magazines and radio books. Let us quote for your circuit, first grade components at realistic prices.

# MINIATURE 'SCOPE

MODEL CT84

Features 2½ in. DG7/5 Tube. Level 2dB, 50 c/s to 2 Mc/s. 3½ Sec. to 80½ Sec. Sweep. High sensitivity. Fully portable scopes. Ideal for all transistor and valve design or servicing. 22 to 30 volt D.C. operated. ● LEAFLET ON REQUEST ●

£16-10-0  
CARRIAGE 7/6

## DEAC RECHARGEABLE BATTERIES

- (a) 18 volt 100mA/H 4 x lin. diameter. Brand new sleeved, 30½".
- 3.9 volt 450mA/H. 12½".
- Easily split into any multiple of 1.2 volt. Brand new.



## MULTI-METERS

Multi-range test meters featuring easy to read scales and provided with full operating instructions, lead and batteries. Suitable for amateur, designers, repair shops, all domestic uses. Full details and specification in our catalogue.

- ★ PT34 1 Kohm/volt ..... £2 5 0
- ★ M1 2 " " ..... £2 9 6
- ★ THL33 2 " " (illus.) £3 15 0
- ★ EPIOK 10 " " ..... £4 9 6
- ★ ITI-2 20 " " ..... £5 5 0
- ★ TPSS 20 " " ..... £5 19 6
- ★ EP30K 30 " " ..... £6 19 6
- ★ 500 30 " " ..... £8 19 6
- ★ EP50K 50 " " ..... £9 19 6

## SUBSTITUTION BOXES

- Capacitor Box. Provides 9 standard values from 0.001 to 0.22 mfd at 600 volt working, 29½".
- Resistor Box. Provides 24 standard values at 1 watt, 15 ohms to 10 meg., 37½".

Each box fully calibrated with insulated leads. Invaluable for service and design.

## NOMBREX TEST EQUIPMENT



All transistor portable units supplied with full instructions.

LEAFLETS ON REQUEST

- ★ 150 Kc/s to 350 Mc/s generator. RF, Mod., AF. 8 ranges. Leads, batt., instructions. £7.18.6, P.P. 2/6.
- ★ Resistance/Capacitance Bridge. 1 pF to 100mFd and 1 ohm to 100meg. leakage. PF Tests, with batt. and instructions, £7.2.3, P.P. 2/6.
- ★ Power Supply. Gives any voltage 1 to 15 D.C. up to 0.1 amp. From Mains. £5.17.6, P.P. 2/6.
- ★ Audio Generator, 10 c/s to 100,000 c/s. Sine and square wave. With batt. and instructions. £15.2.3, P.P. 2/6.

## HI-FI SPEAKERS

- CX300 12 inch 25 watt ..... 12 Gns.
- CR12AE 12 inch 20 watt ..... 8 Gns.
- CR30AE 12 inch 20 watt ..... 8 Gns.
- triple range ... .. 10 Gns.
- BA7 8 inch 6 watt ..... 7/6
- 10 watt Horn Tweeter ... .. 2/6

TEST LEAD KIT supplied in Pocket Pouch. Contains probes, leads, clips, etc. 8/6. P.P. 9d.

## RECORDING TAPES

- 5in. 600ft. 12½"; 5in. 900ft. 15½"; 7in. 1,200ft. 18½"; 7in. 1,800ft. 25½"; 7in. 2,400ft. 27½". Excellent quality. P.P. 1/6.


## 100 Kc/s QUARTZ CRYSTALS

- 2 Pin: Octal or 3 Pin ..... 15½ ea.
  - 500 Kc/s 2 Pin ..... 15½
  - 455 Kc/s (AR88) ..... 12/6
  - 5000 Kc/s 2 Pin ..... 10/6
  - 10 Mc/s 2 Pin ..... 15/6
  - 27 Mc/s Radio Control ..... 15/6
  - 456 Kc/s HRO ..... 15/6
- (Over 600 Frequencies in Stock for all purposes).

## MAINS AND BATTERY RECORD AND TAPE DECKS

- All Decks Complete with Cartridges
- ★ BSR UA14 4-speed ..... £5 19 6
- ★ Garrard Autoslim ..... £6 10 0
- ★ Unpluggable Head Version ..... £6 19 6
- ★ Stereo Version ..... £7 19 6
- ★ SRP10 4-speed or GU7 ..... £5 5 0
- ★ Garrard AT6 with Stereo Cartridge ..... £10 19 6
- ★ Collaro 2-track Studio Deck ..... £10 10 0
- ★ 4-track Deck ..... £13 19 6
- P. & P. 3/6 any type above.
- ★ 9 volt Starr 45 r.p.m. .... 39/6
- ★ 45 or 33 r.p.m. Star 9V ..... 92/6
- ★ 45 r.p.m. Garrard, 6V ..... 35/-
- ★ 4-speed B.S.R. 9V ..... 5 gns.
- ★ Garrard 9V. 2-speed, 2-track Tape Deck ..... £12 15 0
- P. & P. 3/6 any of above.

## STEREO AMPLIFIERS

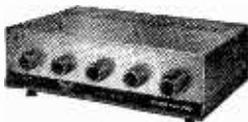

Complete with full function pre-amplifiers and controls.

- ★ SA80 4+4 watts ..... £9 10 0
- ★ SA150 7+7 watts ..... £16 10 0
- ★ SA300 15+15 watts ..... £32 10 0

Each amplifier completely self contained and designed for Mono and Stereo output. Supplied complete with full manual. Leaflets on any type on request. (Full range of Speakers, Tweeters and Decks in stock. see catalogue.)

## STETHOSCOPE HEADSETS

Crystal and Magnetic, 10/6 each.

## CRYSTAL MICROPHONES

- Acos 39-1 Stick Microphone ..... 32/6
- Acos 60-1 Stick Microphone ..... 27/6
- Acos 40 Deck Microphone ..... 15/-
- Acos 45 Hand Microphone ..... 22/6
- Lapel/Hand Microphone ..... 12/6
- MC24 Stick Microphone ..... 25/-
- 100C Stick with Stand ..... 39/6
- BM3 Stick with Stand ..... 32/6
- Lapel/Hand Magnetic ..... 12/6

## MINIATURE PANEL METERS

- \*0/50µA (D.C.) 39/6 \*0/5mA (D.C.) 27/6
  - \*0/500µA (D.C.) 32/6 \*0/300V (D.C.) 27/6
  - \*0/1mA (D.C.) 27/6 "S" Meter 35/-
- All Brand New Boxed. \*Available Clear Plastic Front or Black Moulded.
- 200µA D.C. Edge meter ..... 69/6
  - 1 mA D.C. Edge meter ..... 59/6
- ¾ x 1 inch Front Panel.

POCKET SOLDERING IRON. 30 watts. 220/250 volts A.C. Complete with pointed bit, mains plug, carry pouch. 14/6. P.P. 1/6.

## HEADPHONES

- 2000 ohms 12/6. 4000 ohms 14/-.

## BUILD A QUALITY TAPE RECORDER

- ★ Printed circuit. Record/playback Amplifier Kits. 2 Track 11 gns. 4 Track 12 gns.
- ★ Studio Deck. 2 Track £10.19.6 4 Track £13.19.6
- ★ Cabinet with Speaker 5 gns. Leaflet on Request.

5-Piece Hole Cutter for all chassis work. ½ in. to 1½ in. with pouch 49/6.

Crystal Contact Microphone 12½ P.P. 9d

2K 1-track Tape Head ..... 15/- P.P. 9d.

Telephone Recording Attach. ment ..... 12½ P.P. 9d.

4-Channel Transistor Mixer Unit ..... 59½ P.P. 1/6

Tape Jack Radio Tuner ..... 29½ P.P. 1/6

## BOAC VHF POCKET RECEIVERS

● Complete units with CS 5A VHF Detector, 5-V6/BR (OC44) Transistors. 3.9V. 450mA rechargeable Deac battery 2—OA91, OA 10 rectifiers, 1Kohm stethoscope headset, moulded casing, etc.



- Complete Unit with Full Circuit OR DEAC BATTERY 12/6, P.P. 1/6
- Unit less DEAC & HEADSET 15/-, P.P. 1/6
- Unit less DEAC & HEADSET 12/6, P.P. 1/6

## FIELD STRENGTH METER

Five channels cover 1 Mc to 200 Mc/s. Fitted 200 microamp meter for CW or RF. Indication and Earphone for A.F. Monitoring. Designed for checking all types of transmitters. Size 4 x 2½ x 2½ in. Complete. Ready to Use, with instruction and telescopic aerial, 69/6. Post Free.

## RUN YOUR RADIO OR AMPLIFIER FROM MAINS BATTERY ELIMINATORS AND CHARGERS

1. For PP3 or equivalent 9 volt Pocket Radio Battery, 18/6. P.P. 1/-.
2. For PP4, PP7, PP9, 9 volt Portable Radio Equipment. Supplies up to 300mA, 49/6. P.P. 2/-.
3. De Luxe version of No. 1 also charges PP3 type batteries. 24/-, P.P. 1/-.

## TYPE 38 TRANSMITTER RECEIVER

Complete with 5 valves. In new condition. These sets are sold without guarantee but are serviceable. 22/6 P.P. 2/6

Headphones 7/6 pair. Junction Box 2/6

Throat Mike 4/6. Aerial Rod 2/6

# Henry's Radio Ltd

PADDINGTON 1008/9  
303 EDGWARE RD., LONDON W.2

Open Monday to Sat. 9-6. Thurs. 1 o'clock.

PLEASE TURN TO BACK PAGE

# Practical Wireless

# BLUEPRINT SERVICE

**A**LL of these blueprints are drawn full-size and although the issues containing descriptions of these sets are now out of print, constructional details are available free with each blueprint except for those marked thus (\*).

Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to PRACTICAL WIRELESS, Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, London W.C.2.

## DOUBLE-SIDED BLUEPRINTS

Each blueprint in this series contains details of two separate instruments or items of equipment.

|                                     |   |   |     |
|-------------------------------------|---|---|-----|
| The Strand Amplifier ... ..         | } | * | 5/- |
| The PW Signal Generator ... ..      |   |   |     |
| The Savoy VHF Tuner ... ..          | } | * | 5/- |
| The Mayfair Pre-amplifier ... ..    |   |   |     |
| The Berkeley Loudspeaker Enclosure  | } | * | 5/- |
| The Luxembourg Tuner ... ..         |   |   |     |
| The PW Troubadour ... ..            | } |   | 7/6 |
| The PW Everest Tuner ... ..         |   |   |     |
| The PW Britannic Two ... ..         | } | * | 6/- |
| The PW Mercury Six ... ..           |   |   |     |
| The PW Regency ... ..               | } | * | 5/- |
| The PW International Short Wave Two |   |   |     |

## RECEIVERS

|                                |           |
|--------------------------------|-----------|
| The Tutor * ... ..             | 3/-       |
| The Citizen * ... ..           | 5/-       |
| Junior Crystal Set ... ..      | PW94 2/-  |
| Dual-wave Crystal Diode ... .. | PW95 2/6  |
| Modern One-valver ... ..       | PW96 2/6  |
| All-dry Three ... ..           | PW97 3/6  |
| Modern Two-valver ... ..       | PW98 3/6  |
| A.C. Band-pass Three ... ..    | PW99 4/-  |
| A.C. Coronet-4 ... ..          | PW100 4/- |
| A.C./D.C. Coronet ... ..       | PW101 4/- |
| The PW Pocket Superhet ... ..  | 5/-       |

## MISCELLANEOUS

|   |     |
|---|-----|
| The PW 3-speed Autogram ... ..          | 8/- |
| The PW Monophonic Electric Organ ... .. | 8/- |
| The PW Roadfarer * ... ..               | 5/- |
| The PT Band III TV converter ... ..     | 1/6 |
| The Mini-amp * ... ..                   | 5/- |
| The PT Olympic * ... ..                 | 7/6 |
| The PT Multimeter * ... ..              | 5/- |

## SOME EARLIER DESIGNS

**T**HE following blueprints include some pre-war designs and are kept in circulation for those constructors who wish to make use of old components which they may have in their spares box. The majority of the components for these receivers are no longer stocked by retailers.

|                                     |       |     |
|-------------------------------------|-------|-----|
| Experimenter's Short Wave ... ..    | PW30a | 2/6 |
| Midget Short Wave Two ... ..        | PW38a | 2/6 |
| Simple S.W. One-valver ... ..       | PW88  | 2/6 |
| Pyramid One-valver ... ..           | PW93  | 2/6 |
| BBC Special One-valver ... ..       | AW387 | 2/6 |
| A One-valver for America ... ..     | AW429 | 2/6 |
| Short-Wave World Beater ... ..      | AW436 | 3/6 |
| Standard Four Valve S.W. ... ..     | WM383 | 3/6 |
| Enthusiast's Power Amplifier ... .. | WM387 | 3/6 |
| Standard Four Valve ... ..          | WM391 | 3/6 |
| Listener's 5-Watt Amplifier ... ..  | WM392 | 3/6 |

## QUERY COUPON

This coupon is available until 6th March, 1964, and must accompany all queries in accordance with the notice on our "Letters to the Editor" page.

PRACTICAL WIRELESS, MARCH, 1964.

★ LATEST ILLUSTRATED AND DETAILED CATALOGUE—COMPONENTS—EQUIPMENT—HI-FI. 2/- Postage.

★ NEW 8-PAGE VALVE, CRYSTAL, TRANSISTOR AND RECTIFIER CATALOGUE 1/-.



### "THE CONESSA"

★ COMBINED PORTABLE AND CAR RADIO ★ AMAZING SENSITIVITY AND SELECTIVITY ON MEDIUM AND LONG WAVEBANDS ★ The easiest Superhet Radio to build on the market. Features clearly-marked printed circuit and packaged components with full illustrated building instructions. Full tuning of medium and long wave bands with unbeatable sensitivity and selectivity. Excellent tone and volume with over 600mW push-pull output.

★ Clearly marked horizontal station dial with slow motion tuning. Two colour Blue or Beige cabinets with Gold handles, grilles and fittings. Size 10½ x 7½ x 3½in., includes car aerial sockets, recording sockets.

★ 6 Mullard Transistors and 2 Diodes.

TOTAL COST OF ALL PARTS

**£9.19.6** P.P. 3/6

Fully Detailed and Illustrated Leaflet on request.

All parts sold separately. Guaranteed the Best Obtainable. Attractive Appearance. Reliable Design. Quality Performance.

UNBEATABLE FOR QUALITY AND VALUE

## MINIGRAM TRANSISTOR PORTABLE RECORD PLAYER



● Made by well known British manufacturer. Features ready built 4-transistor printed circuit 1 watt amplifier, elliptical speaker and volume control. Low current Star, constant speed 45 r.p.m. turntable with crystal pick-up. Strong moulded two colour cabinet with handle. Plays anywhere on long life 9 volt battery. Requires less than half an hour's work to connect up using ready built units and easy instructions.

TOTAL COST **79/6** P.P. 5/-

(BATTERY 3/9 EXTRA)  
ALL UNITS

SOLD SEPARATELY

★ READY BUILT AMPLIFIER WITH SPEAKER AND VOLUME CONTROL **35/-** P.P. 2/-


★ TURNTABLE WITH PICKUP. **39/6** P.P. 2/6

★ TWO TONE CASE WITH HANDLE. **5/-** P.P. 2/-

● EXCELLENT QUALITY AND VALUE ●

NEW LOW PRICES
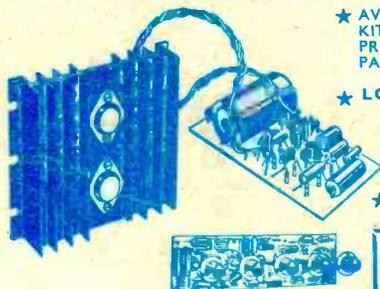
### 10 WATT TRANSISTOR HI-FI AMPLIFIER AND PREAMPLIFIER



★ AVAILABLE IN KIT FORM OR PREBUILT PANELS

★ LOW NOISE

★ LOW POWER REQUIREMENTS


★ MONO OR STEREO

Circuits and details FREE on Request

★ CALL FOR DEMONSTRATION—ANY TIME ★
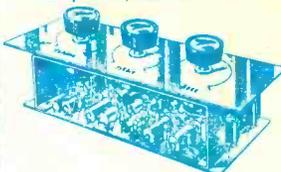
### 7-TRANSISTOR RECORD/PLAYER/RADIOGRAM AMPLIFIER

- 4 watt peak output.
- Full Treble and Bass boost and cut.
- 40 c/s to 20 kc/s  $\pm$  3 dB.
- Inputs for Pick-ups, Radio Tuners, Microphones, mixers.



### ● TWO VERSIONS AVAILABLE

- 12/18 volt for 15 ohm speakers. (mains unit now 60/- extra).
- 9/12 volt for 3 ohm speakers (mains unit 49/6 extra).
- Size only 6 x 2½ x 2in. Ideal for mains or battery, portable or domestic record player, grams, etc. Or car.
- Built Ready **£5.19.6** P.P. To Use 2/-.

BOOKLET FREE ON REQUEST

### TO BUILD YOURSELF

- Mini Ranger Personal Radio. 49/6
- Ranger-3 Personal Radio. 49/6
- Sinclair Slimline Personal Radio. 49/6
- Sinclair Micro Injector 27/6.
- Quintet M/LW-5.....79/6, P.P. 2/-
- PW-6 Superhet.....£7 19 6
- PW Celeste.....£9 19 6
- PW Spinette.....£10 19 6
- PW Shortwave 2.....99/6, P.P. 2/6

Leaflet and details on request

### 4-WAVEBAND COMMUNICATIONS RECEIVER

- 550 kc/s to 30Mc/s.—BFO—AVC—Noise Limiter — Bandsread — "S" Meter — Telescopic Aerial — Full World Wide Coverage. 4 valve. PRICE £24.15.0. With Full Instructions. BRAND NEW IN CARTONS. Detailed Leaflets on request.
- 9 valve version of above 40 gns. Details on request.

### TRANSISTOR MINIATURE AMPLIFIERS

- ★ 3T 125mW 9 v. 30/80 ohm 39/6
- ★ 4T 250mW 9 v. 8/10 ohm 39/6
- ★ 5T 350mW 9 v. 12/16 ohm 57/6
- ★ 4T 1 watt 9 v. 3/5 ohm 59/6
- ★ 4T 1 watt 6 v. 3/5 ohm 92/6
- ★ 4T 1½ watt 12 v. 3/5 ohm 97/6

PERFORMANCE EQUIVALENT TO VALVE AMPLIFIERS OF FOUR TIMES THE PRICE AND MANY TIMES THE SIZE.

★ Power output 10 watts at 400 c/s. Second harmonic distortion 0.1%. Total harmonic distortion 0.25% at 10 watts. Signal to noise ratio at 10 watts 70 dB. Overall response within 3 dB 40 c/s to 20 kc/s.

★ 6-Transistor 10 watt power amplifier. 0.25 ohm output impedance for 3 ohms. 24 volt supply, 300mA average for 10 watts. 100mV into 33 k.ohm sensitivity. 1 dB, 40 c/s to 20 kc/s. Built £5.10.0 P.P. 2/6. Or Kit 99/6 P.P. 2/6. (Mains Unit 69/6 P.P. 2/6).

★ As above but 10 watts for 15 ohm speakers, 40 volt supply, 150mA average for 10 watts. 1 dB, 40 c/s to 20 kc/s. Built £5.19.6 P.P. 2/6. Or Kit £5.10.0 P.P. 2/6. (Mains Unit 69/6 P.P. 2/6).

★ Full function pre-amplifier and control unit on printed circuit. Size 9 x 2½in. Features 6 position input selector for microphones, tuners, tape, pick-ups—treble and bass controls + 12 dB at 50 c/s and 12 kc/s—14 dB at 50 c/s and 12 kc/s. Four-position filter and volume controls. 1.5 mV to 300 mV input sensitivity. Built £5.10.0 P.P. 2/-. Or Kit 99/6 P.P. 2/-. (Front panel 8/6 extra).

## FM TUNER First Again

(As described in December 1963 Edition of "Radio Constructor")

- ★ 5-Transistor
- ★ 4 Diodes
- ★ Full coverage 87 to 105 Mc/s

★ AFC and AVC

Printed circuit design of high sensitivity and quality. Output for valve or transistor amplifiers. Size 3½ x 2½ x 4in. Simplified building instructions. All parts sold separately.



TOTAL **£7.19.6** P.P. COST 2/6

(Cabinet assembly etc. 20/- extra.)

Detailed Circuit Book on Request

### BABY ALARM

Ready to use with microphone and battery. Fully portable. **£5.10.0**

### TELEPHONE AMPLIFIERS

For use with all telephones. Gives speaker output. Battery operated. **£5.10.0.**

## Henry's Radio Ltd.

303 EDGWARE ROAD, LONDON, W.2  
PADDINGTON 1008/9

Open Monday to Sat. 9-6. Thurs. 1 o'clock.