


PRACTICAL WIRELESS

MAY 1964

2⁺



The PW 35 WATT GUITAR AMPLIFIER

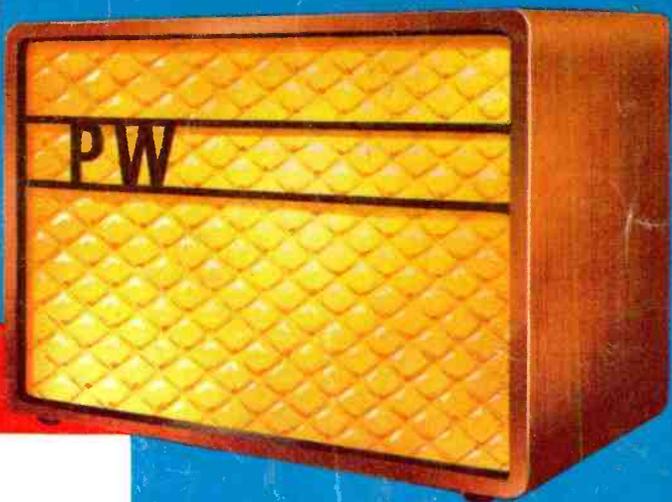

FREE INSIDE

DOUBLE-SIDED

BLUEPRINT

TO BUILD THIS

GUITAR AMPLIFIER

ALSO A SIMPLE
2-STAGE AMPLIFIER

Fringevision Ltd

**ELCOT LANE
MARLBOROUGH · WILTS**

TELEPHONE: 657 and 658



**WIDE BAND
UHF AERIALS
for BBC2 now
and ITV 2**

FIVE STAR QUALITY AERIALS

- ★ Anodised elements for protection. ★ Modern plastic moulding techniques used for convected reflector and parasitic elements giving longer life. ★ Staggered spaced elements for maximum performance with all channel band width. ★ Multi-element reflector giving high back to front ratio ★ Maximum efficiency of matching by using laboratory developed collector plate—without any other matching device.

Model	Description	Gain DB	B/F Ratio DB	Retail Price
UF/H3	3-ELEMENT, HEAD ONLY with CLAMP	7.0	18.0	31/6
UF/H5	5-ELEMENT, HEAD ONLY with CLAMP	8.25	19.5	36/6
UF/H7	7-ELEMENT, HEAD ONLY with CLAMP	10.5	24.5	41/-
UF/H10	10-ELEMENT, HEAD ONLY with CLAMP	12.5	26.0	47/-
UF/H12	12-ELEMENT, HEAD ONLY with CLAMP	13.5	28.0	51/-
UF/H14	14-ELEMENT, HEAD ONLY with CLAMP	15.0	29.0	55/-
UF/H18	18-ELEMENT, HEAD ONLY with CLAMP	16.25	30.0	70/-
UF/H22	22-ELEMENT, HEAD ONLY with CLAMP	17.0	31.0	85/-

PLEASE STATE LARGE OR SMALL CLAMP REQUIRED

ADCOLA
SOLDERING EQUIPMENT

SOLDERING EQUIPMENT


for

TOTAL PERFORMANCE

A COMPLETE RANGE OF EQUIPMENT FOR THE RADIO AMATEUR

ILLUSTRATED

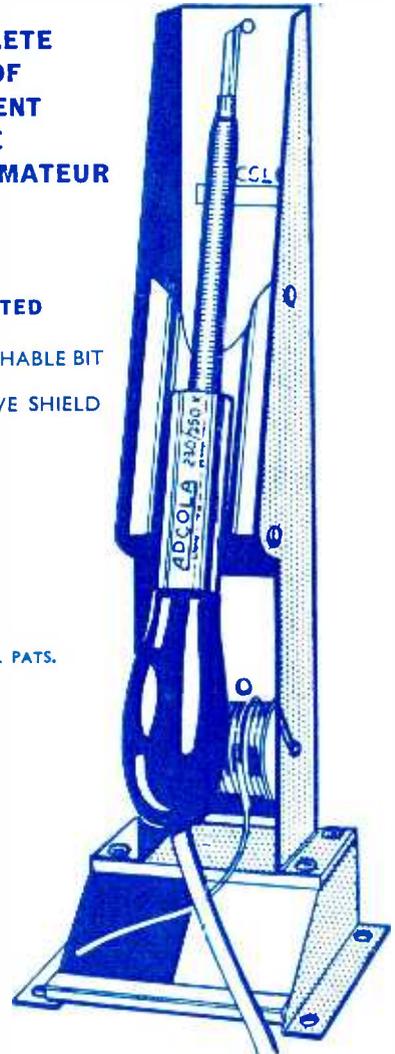- List 64.
- $\frac{3}{16}$ " DETACHABLE BIT IN PROTECTIVE SHIELD
- List 700



BRIT. & FOR. PATS.

Sales & Service

APPLY DIRECT FOR CATALOGUE TO

**ADCOLA PRODUCTS LTD.,
ADCOLA HOUSE,
GAUDEN ROAD, LONDON, S.W.4**

Telephones MACaulay 4272 & 3101 Telegrams SOLJOINT LONDON SW4

EKCO L.O.P.T. Unused replacements for Perspex cased 1954-7 models, complete with E.H.T. rect. 39/1-...

00-AK, low loss, 6d. vol. 25 vds., 11/8, 30 vds., 22/1, 100 vds., 42/6. Co-ax plugs, 1/3. Wall-mount boxes 3/8.

SPECIAL C.R.T. OFFER Due to huge Bulk Special Purchase we are offering MW 31-74 Tubes at...

LOUDSPEAKERS. 3Ω Top Makes 0 1/2 in. 7/6 5 in. 8/6 8 in. 7 x 4 in. 8/6

CONNECTING WIRE P.V.C. Bright colours. Five 2/1 feet, coils only

3 VALVE AMPLIFIERS Kit of new parts, consisting chassis, mains and output transformers, valves (P91, 6X4, 6X5) and all components.

MAINS TRANSFORMERS Excellent Quality Guaranteed. Upright mounting 250-0-250 V 60ma. 6.3V, 3A (80ma) 12/6 611ta semi-shrouded 9/6

13 CHANNEL T.V.s Table Models. Famous Makes. Absolutely Complete. These sets are unequalled in value due to huge purchase direct from source.

LEAK AMPLIFIER SNIPS Due to a fortunate purchase we are able to make the following unrepeatable offers.

★ BULK BARGAINS ★ 12 POTS. Popular values, 2K to 2 Meg. Unused, mixed, pre-set, long sp. switched, etc. 4/6

100 RESISTORS 6 6 Excellent. Sizes 1-3 watt.

100 CONDENSERS 9 6 Miniature Ceramic and Silver Mica Condensers, 3 pF to 5,000 pF. LIST VALUE OVER 4/6

25 TAG STRIPS 4/1- 2, 4, 6, 8 way etc. Unused.

100 HI STABS 9 6 1/2 to 2 1/2, 100Ω to 5MΩ

★ Tubes ★ HIGHEST QUALITY - COMPARE OUR PRICES - GUARANTEED 6 Months 12 Months NEW TYPES

TRANSISTORS GUARANTEED TOP QUALITY

Huge reduction. Red Spot 1/6 standard L.P. type now only White Spot R.F. 2/-

Mullard Matched Output Kits (OC81D and 2-OC81S) 12/6 R.F. Kits (OC44, OC45 (2), 3 transistors) 12/6

Table of transistor types and prices: AF114 8/- OC14 5/6 AF115 7/8 OC45 5/6 AF116 7/8 OC72 5/6 AF117 7/- OC81 5/6 AF127 9/6 OC81D 5/6 OC26 12/6 OC82 6/- OC38 14/- OC170 8/6 OC171 8/6

GERMANIUM DIODES General Purpose miniature detector. A.V.C., etc. 8d.

Gold Bonded highest quality, individually tested. 1/-

SILICON RECTIFIERS Guaranteed performance. Top Make. Tested 250V working.

100mA 3/9 250mA (3 for 9/8) 3/9 18/6 (3 for 18/6) 7/6

NEW SHOP SOUTHAMPTON

Now Open in Large Premises WE LOOK FORWARD TO OFFERING YOU A FIRST CLASS SERVICE. Please note the address.

72 EAST STREET (Tel. 25851)

With widest Stocks, Keenest Prices. T.V.s, Radios, Valves, Transistors, Hi-Hi Equipment, Loudspeakers, Autoconverters, Cables, Components, etc. 4/-

4 watt AMPLIFIER

excellent amplifier with high gain preamp stage, 10F3 driving 10K14 output stage, complete with 8in. speaker. In attractive 2-tone case. Tone control, amazing volume and clarity, ideal for guitars, record players, p.a. in small halls, baby alarms, etc. Easily worth 45/6

ENQUIRIES WELCOMED Quantity Prices or Quotes for items not listed, particularly rare values. TELEPHONE C.O.D. ORDERS DISPATCHED THE SAME DAY.

★ GUARANTEED VALVES ★

by return of post THE MOST ATTRACTIVE COMPETITIVE VALVE LIST IN THE COUNTRY All valves are new and unused unless otherwise advised

Table with 3 columns: POST (1 Valve 6d., 2-11 1/- FREE for 12 or more valves), 3 MONTHS GUARANTEE (In writing with every valve), FREE TRANS IN-SURANCE (Satisfaction or Money back Guarantee on Goods if returned within 14 days)


Main table of vacuum tube types and prices: 0Z4 4/6 6K7G 2/- 20D1 8/9 DL75 6/- EY86 5/6 SU2150 4/6 1A7GT 9/6 6K7GT 4/6 20F2 9/6 DL82 9/1 T41 6/9 1C6GT 7/8 6K8G 5/- 20L1 15/- DL92 5/- E240 5/6 TDD4 7/4 1D5 7/- 6H3GT 8/3 20P1 9/6 DL94 6/6 E241 5/6 U14 7/6 1D6 9/6 6X23 8/1 6B3P3 11/- DL95 17/- E250 5/6 U12 7/6 1H5GT 8/9 6L1 9/6 20P4 15/- EA50 1/3 E281 4/6 U92 6/9 1L4 3/- 6L6 7/6 20P5 11/6 EA50C80 0/- FC4 8/- U24 12/6 1LD5 3/6 6L6G 6/6 25A9G 8/- EA91 4/- FW4/500 7/- U25 8/- 1L8S 4/- 6L18 7/8 25LUGT 8/- EA94 6/9 GT1C 12/6 U26 7/- 1N6GT 8/9 6L19 12/6 25Y5G 8/- EA94Z 8/3 G232 10/- U31 7/- 1R5 5/6 6L2D20 7/8 25Z4G 7/- EB34 9/- G234 9/- U33 13/- 1U5 6/- 6N7 7/6 25Z5 8/- EB41 5/- HK90 9/6 U35 12/6 1S4 7/6 6P1 9/6 25Z6G 8/- EB91 2/- HL41D 8/- U37 26/- 1S5 3/9 6P25 8/6 27SU 17/6 EB93 4/9 HK909 19/6 U50 4/9 1T4 3/9 6P28 9/6 30C1 5/- EB94 6/- HVR2 8/- U52 4/9 2D21 5/6 6Q7G 4/6 30C15 0/6 EB95 6/6 K735 6/9 U76 4/- 3A4 4/- 6Q7GT 8/- 30F5 10/6 EB96 6/6 K736 6/9 U78 4/- 3A5 6/- 6R7G 9/- 30F11 10/6 EB98 7/6 K738 14/- U107 12/6 3Q4 5/- 6SA7 6/9 30L1 5/- EB99 6/9 KT44 8/- U191 9/6 3S4 5/- 6SC7 4/9 30L15 12/6 EB121 11/- K751 10/6 U281 8/6 3V4 5/- 6SQ7 4/9 30B1 9/6 EB131 17/- K752 8/6 U282 14/- 3Y4G 8/- 6SJ7 4/6 30P12 7/- EC52 4/9 U283 4/6 U301 12/- 5Y4G 8/- 6SJ7 4/6 30P14 14/- EC91 4/6 K768 12/- U309 6/6 5Y4G 8/- 6SK7 5/- 30P11 10/6 EC92 8/6 K768 8/6 U329 8/6 5V4G 7/6 6SL7GT 5/9 30P13 12/6 EC93 7/6 K738 10/- U339 11/6 5Y3G 4/9 6SN7GT 4/6 30P14 12/6 EC93C 4/6 K7681 5/9 U342 14/- 5Y3GT 4/- 6SS7 3/6 35L6GT 7/- EC93A 9/- K7683 5/- UAB30 5/- 5Y4G 9/6 6U4GT 8/- 35W4 5/- EC93S 5/- K7423 11/- UAF42 8/- 5Z4G 7/6 6V6G 4/6 35Z4GT 6/- EC94 6/6 L63 3/- UB41 7/- 5Z4GT 9/6 6V6GT 6/- EC95 4/6 EC95A 4/6 LNI52 6/6 UB41 7/- 6Y30L2 9/6 6X5 4/6 6/6 EC96 4/6 U114 7/- UB41 7/- 6Y30L2 9/6 6X5GT 5/- 4/6 EC98 4/6 N37 10/6 UBFO 6/6 6Y30L2 9/6 6X5GT 5/- 4/6 EC98A 6/6 N73 13/- UB99 7/6 6A8G 5/- 7B6 9/- 50C5 8/6 EC98S 6/- N108 13/- UB121 9/- 6A8GT 12/6 7B7 5/6 50LGT 8/6 EC98 11/6 N152 8/6 UB121 9/- 6A67 3/9 7C6 7/6 61B1 17/6 EC98E 6/- P41 3/6 UC94 9/- 6A67 6/9 7H7 5/- 61SPT 11/- EC98I 11/- PAB30 7/- UC96 8/6 6AK5 4/3 7R7 12/- 2B7 13/6 EC98J 6/- PC88 10/- UC97 8/6 6AL5 3/3 757 8/9 75 5/6 EC98K 6/- PC97 7/6 UC98 8/6 6AM6 3/- 7Y4 5/- 80 5/- EC98L 6/- PC98 5/- UC98 8/6 6A05 5/- 8D3 3/- 83 6/6 EC98M 6/- PC98 5/- UC98 8/6 6AT6 6/- 10C1 9/- 135T 19/6 EC98N 6/- PC98 11/6 UC98 10/- 6AV6 5/9 10C2 15/- 185BTA 19/6 EC98P 13/6 PC98 11/6 UC98 10/- 6B7 8/6 10E7 7/6 807A 5/- EC98Q 10/- PC98 11/6 UC98 10/- 6B8G 3/6 10F8 10/6 807E 4/9 EF22 6/- PC98Z 10/- UF85 7/- 6BA6 4/9 10F18 10/6 813 4/9 EF36 3/6 PC98A 10/- UF86 12/- 6BE6 5/- 10LD11 14/6 832 14/- EF37A 6/- PC98B 6/- U141 7/6 6BG6G 15/- 10P13 12/6 866A 12/6 EF39 3/3 PC98E 6/6 UL44 14/- 6BF6 5/- 10P14 9/6 8C4 3/9 EF40 9/6 PC98 6/- U145 7/6 6BR7 8/6 12A8 2/- 956 2/- EF42 4/6 PC98A 7/- UL46 8/- 6BR8 9/6 12A8S 9/- 1025 5/6 EF50-BR18 PC98 9/- UR1C 7/6 6BW6 5/- 12A8H 11/- 5763 7/- EF50A 12/6 PEN25 3/9 U06 8/6 6C4 2/3 12AT7 5/6 9002 2/6 EF54 3/6 PEN46 4/6 U07 9/6 6C5 5/6 12AU6 9/- 9003 5/6 EF55 6/6 PEN45 8/6 U08 11/- 6C6 3/6 12AU7 6/- ATP4 2/6 EF58 6/- PL38 8/- UY21 8/6 6C9 11/- 12AV6 6/3 AZ21 6/- EF59 4/6 PL38 10/- UY41 5/6 6C9G 6/6 12AX7 6/6 AZ41 7/- EF61 3/- PL81 6/- UY42 7/6 6CH6 6/6 12BA6 6/- B36 4/3 EF92 3/- PL82 5/6 UY85 5/6 6D2 3/6 12BE6 6/6 C1C 8/- EF183 8/- PL83 6/- VP4B 9/- 6D3 9/6 12BH7 8/9 C1C35 12/- EF184 8/- PL84 6/- VP4C 9/- 6D6 3/- 12C3 5/6 C1C3 9/- EK32 6/- PL85 6/- VP4D 5/9 6E1 4/9 12C5 7/6 C21 7/6 EL32 3/9 PM8 6/6 VR105 6/6 6F5 7/6 12H6 1/9 D77 3/3 EL33 6/- PX4 8/- VR150 6/6 6F13 4/3 12J56T 3/3 DA30 11/6 EL34 10/- PX25 8/- W76 3/- 6F6G 3/6 12J76T 8/- DAC32 9/6 EL35 6/- PY31 8/- W81 7/3 6F14 6/6 12K7GT 4/6 DAF91 4/6 EL38 12/6 PY32 10/- X65 8/6 6F15 9/6 12K8 9/6 DAF96 8/- EL39 3/- PY81 6/- X65 11/6 6F19 6/- 12K9GT 9/6 DPF33 8/9 EL41 8/- PY80 6/6 X66 7/6 6F32 4/9 12Q7GT 4/6 DFF91 3/- EL42 8/9 PY81 4/9 X81M 9/6 6F33 4/- 12SA7 6/3 DFF6 6/- EL44 4/6 PY82 5/6 Y63 6/6 6H6 1/8 12SG7 4/6 DFF97 7/6 EL55 9/9 PY83 5/6 Y63 4/9 6F15 4/9 12S9 7/6 DFF98 5/6 EL56 8/6 PY84 8/6 Y63 8/6 6J5G 3/- 12SJ7 5/6 DFF98 4/6 EL55 5/- PY80 6/6 6J5GT 4/3 12SK7 2/9 DK32 9/6 EM84 8/9 PY80 6/6 6J6 2/6 12SN7GT 6/9 DK31 5/6 EM86 6/6 PZ30 9/6 6J7 8/6 12SQ7 7/6 DK92 6/6 EM81 6/6 9/9 PY81 9/6 6J7G 4/9 12S9 7/6 DK96 8/6 EM81 6/6 9/9 PY81 9/6 6J7GT 7/6 1457 14/6 DL33 7/6 EM85 8/- SP41 2/3 6K6GT 6/- 19A05 7/9 DL35 7/6 EN31 16/- SP61 2/3 6K7 5/9 19B6G 14/- DL63 9/- EY51 7/- SU25 16/-

Post: 2 lbs. 2/-, 4 lbs. 2/6, 7 lbs. 3/8, 15 lbs. 4/-, etc. (C.O.D.) 2/- extra. ALL ITEMS LESS 5% AND POST FREE IN DOZENS. RETAIL SHOP AND NEW HI-FI ROOM 350-352 FRATTON ROAD, PORTSMOUTH. (Tel: 22064) ALL MAIL ORDER, RETAIL SHOP AND HI-FI ROOM 11-12 NORTH ROAD, BRIGHTON. Tel. 67999

FANTASTIC BUY!**STEREO DYNAMIC MICROPHONE MODEL SM.D100**

A truly revolutionary new stereo dynamic microphone, ideal for the tape recording and audio enthusiast who has an eye for quality and value. Brief specification—Frequency response 60-15,000 c/s. Output impedance 50K ohms, sensitivity—40dB. Size: 2 1/2" high, Mike 2 1/2" dia. Base 4 1/2" dia. Mike can be removed from table stand and used with floor stand if desired. Supplied complete with table stand and 10ft. of screened lead in display carton.

PRICE **9 Gns.** S.A.E. for leaflet.

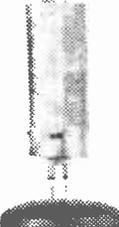**DM.614. 50K DYNAMIC SUPER SENSITIVE DESK OR NECK MICROPHONE**

Never before at such high quality at such low price. Complete with carrying cord and desk stand. Lightweight. PRICE 45/-, Complete in presentation pack.

**CT.10 HORN TWEETER**

For true highidelity reproduction of the upper middle and top frequency ranges in multi-unit speaker installations. Pressure unit type utilizing a spun aluminium diaphragm. Output 10 watts. Frequency response 1500-1800 c.p.s. Impedance 16 ohm.

Finished in matt black, flanged and drilled for baffle mounting.

PRICE **29/6**

MINIATURE PORTABLE TAPE RECORDER MODEL TC.601

★ Fully transistorised.
★ Dual track



★ Combined microphone/speaker.
★ Size only 10 1/2" x 3 1/2" x 2 1/2"

Completely portable, self-contained, full function miniature tape recorder utilising advanced transistor circuitry with 4-transistor push-pull output stage to give you quality reproduction you would only expect from units three times the price. Simple control or rewind/stop/playback/record, and variable volume control. Attractive tan and gold high impact poly-vinyl case with transparent snap-on plexiglas top enabling unit to be operated with top lid position. Complete with dual purpose microphone-speaker. 200 ft. of tape, batteries and instruction book.

PRICE **£8.19.6**

SUBSTITUTION BOXES

Fully calibrated complete with insulated leads. Model O.M.G RESISTANCE BOX provides 24 standard values at 1 watt, 15 ohms to 10 meg. Price 37/6.



Model O.M.B CAPACITANCE BOX provides 9 standard values from 0.001 to 0.22 mfd at 500 volt working. Price 28/6.

4-TRANSISTOR PUSH-PULL AUDIO AMPLIFIER

Model **REG.2004**

Not a kit—a ready built miniature amplifier incorporating 4-transistor 9 volt battery amp coil (or Power) speaker and volume control connection leads. The most useful amplifier ever produced. Complete with instructions and circuit diagram. Ideal for making powerful transistor radios, using battery powered record players, intercom etc. Must be heard to be appreciated.

ONLY **42/6**

AMT.31 3-TRANSISTOR SUB-MINIATURE AM TUNER

Covers full broadcast band 4 transistors—3 IF and 1 Osc. Ferrite rod antenna completely wired and self circuit on printed circuit board. Complete with instructions. Price **84/1**

H402 ULTRA SUB-MINIATURE TRANSISTOR COIL SET.

Smallest 2 gang variable condenser 1 1/2" dia. square x 1/2" deep. 3 1/2" x 1" and Osc. coil 1/2" square x 1/2" high. Ferrite rod with medium wave coil ready wound. All supplied with suggested 6 transistor set circuit and parts list. Matched coils shielded and impregnated high O 455 Kc/s. All slug tuned. Tuning dial and knob fits securely on shaft. ONLY **24/6** complete.

UD.19H UNIDIRECTIONAL DYNAMIC MICROPHONE

The very latest microphone creation, designed to take the professional and enthusiast the last word in unidirectional performance.

Designed to provide the speed component from the periphery, thus eliminating all previous common unidirectional design defects. Exclusive features include high sensitivity and excellent frequency characteristics achieved by use of an aluminium wire voice coil. High stability by use of polyester film for the diaphragm. Extremely effective in minimising feed-back problems. Dual high and low impedance, wind adaptor and shielded cable. PRICE **£14.14.0.**

DS.1 MICROPHONE DESK STAND

5 1/2" dia., grey plastic base. 3 1/2" x 1/2" dia. rod (27 threads). PRICE **10/6**

HAWAIIAN PORTABLE RECORD PLAYER Model HN707


Uses a unique pick-up, turntable and special speaker to give amazing volume and reproduction with the use of valves or transistors. Battery operated, plays up to 12" records at 33 1/3 or 45 c.p.m. Separate line speed and volume control. 4 1/2" wind adaptor and stroboscope. Durable plastic cabinet fully waterproof with carrying handle and record storage compartment. Size 9 1/2" dia. x 3 1/2" deep. Weight 2 1/2 lb. 0 oz.

SPECIAL OFFER ONLY £4.19.6

NOW! HI-FI SOUND

With the **K430 RADIO AMPLIFIER**

Designed for use with transistor radios, valve radio-car radios, amplifiers where quality reproduction of sound is required. Plug into earpiece output socket of nearly all miniature sets. The cabinet is finished in beige leather with contemporary gold buttons at each end. Complete with 12ft. extension cord fitted with miniature plugs, individually cartoned and guaranteed. Size: 9 1/2" x 3 1/2" diameter.

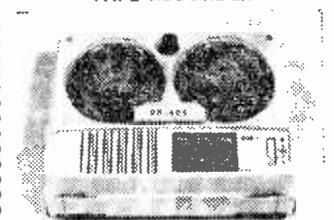NEW! PUSH BUTTON PORTABLE TAPE RECORDER

MODEL **UN.406.**

The latest in transistor portable recorders incorporating 4 transistor amplifier two motors, adjustable speed control, twin track recording, big 2 1/2" dynamic speaker, simple push button stop/record/play and rewind controls. Volume control. Attractive two-tone case with carrying handle and lead. Complete with remote control microphone, 200 ft. of tape. Earphone. Batteries and instruction book.

PRICE **10 Gns.**

HI FI SPEAKER

MODEL **C.R. 12AE.** Two-way true Hi-Fi and super stereo at low cost, response: 30-16,000 c.p.s. 10-watt 16 ohms. PRICE **£8.8.0.**

SF.20 RADIO EARPHONES

Hi-impedance 2,000 ohms general use headset. Black and Ivory plastic cased electro-magnetic units with adjustable headband for comfortable fit. Individual listening for all types of applications. Individually packed, with flexible cord attached.

PRICE **12/-**

R.F. FIELD INDICATOR

RF 40. Designed for checking the radiation from a transmitting antenna. The sensitivity can be controlled by movement of panel control, the antenna length or by increasing distance from the radiator. Freq. range 1-250 Mc/s. S.W.G.A. Ltd.

Complete as illustrated. With instructions. PRICE **69/6**

SIGNAL INJECTION PROBE IT.1

Push button operation. Ideal for making rapid checks on radios, TV Amps, tuners, etc. PRICE **39/6**

THIS MONTH'S SNIP
U.S.A. 12FT. WHIP AERIALS
7/6 POST PAID.




MAIL ORDERS TO: (DEPT. P), 32a COPTIC STREET, LONDON W.C.1.
CALLERS WELCOME AT: 87 TOTTENHAM COURT RD, LONDON W.1. MUS 9606

THE R.S.C. BASS-MAJOR 30 WATT GUITAR AMPLIFIER

A MULTI-PURPOSE HIGH FIDELITY, HIGH OUTPUT UNIT FOR VOCAL AND INSTRUMENTALIST GROUPS

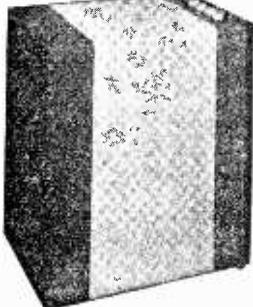Eminently suitable for bass, lead or rhythm guitar and all other musical instruments



- ★ Incorporating two 15in. heavy duty 25-watt high flux (17,000 lines) loudspeakers with 3in. diameter speech coils. Designed for efficiently handling full output of amplifier at frequencies down to 25 c.p.s.
- ★ Dual Cone in second speaker reproduces frequencies up to 17,000 c.p.s.
- ★ Heavily made cabinet of convenient size 24 x 21 x 14in. has an exceptionally attractive covering in two contrasting tones of Vynair.
- ★ For 200-250 v. to 50 c.p.s. A.C. mains operation.
- ★ Four jack socket inputs and two independent vol. controls for simultaneous connection of up to four instrument pick-ups or microphones.
- ★ Separate bass and treble controls providing more than adequate 'Boost' or 'Cut'.
- ★ LEVEL frequency response throughout the audible range.
- ★ SUPERIOR TO UNITS AT TWICE THE COST.

39½ Gns.

Send S.A.E. for leaflet.
OR DEPOSIT of £4.30 and 12 monthly payments of £3.9.11. Carr. 17/6.

R.S.C. JUNIOR GUITAR AMPLIFIER 5-watt high quality output. Separate bass and treble "cut" and "boost" controls. Sensitivity 15 m.v. Two high impedance inputs. 10in. loudspeaker. Handsome strongly made cabinet (size 14 x 14 x 7in. approx.) finished in complementary shades of Rexine/Tygan. 200-250 A.C. mains. **£8.19.6** Or DEPOSIT £1 and 9 monthly payments of 41s. Carr. 7/6.

LINEAR TREMOLO/PREAMP. UNIT Designed for introducing the Tremolo effect to any amplifier which is fitted with a reserve power supply point, for smoothed H.T. and 6.3 v. A.C. L.T. This applies to practically all amplifiers of our manufacture, and to those of several other manufacturers. The unit plugs into power supply point and any input socket or amplifier. Controls are Speed (frequency of interruptions), Depth (for heavy or light effect), Volume and Switch. Three sockets are for two inputs and Foot Switch. **ONLY 4 Gns.**

R.S.C. SENIOR 15 WATT LEAD or RHYTHM GUITAR AMPLIFIER

High-fidelity push-pull output. Separate bass and treble "cut" and "boost" controls. Twin separately controlled inputs so that two instruments or "mike" and pick ups can be used at the same time. Loudspeaker is a heavy duty high flux 12in. 20 watt model with cast chassis. Chassis is well made and finished as Junior Model. Size approx. 18 x 18 x 8in.


Only **18 Gns.** Carr. 10/-

Send S.A.E. for leaflet. Or DEPOSIT 37/9 and twelve monthly payments of 31/6.

R.S.C. B20 BASS GUITAR AMPLIFIER

A highly efficient unit incorporating a massive 15in. high flux loudspeaker specially constructed to withstand heaviest load conditions. Rating 25 watts. Individual bass and treble controls give ample "boost" and "cut". Two high impedance jack socket inputs are separately controlled. All controls are conveniently positioned in a recess on top of the cabinet. Cabinet is of substantial construction and attractively finished in two contrasting tones of Rexine and Vynair. Size approx. 24 x 21 x 13in. Operation from 200-50 c.p.s. A.C. mains.

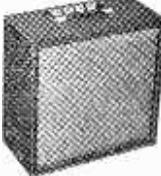Send S.A.E. for leaflet.
29½ Gns. Or Deposit **£3.2.0** and 12 monthly payments of 51/8. Carr. 17/6.



GLASGOW — LONDON — EDINBURGH

326 ARGYLE STREET 238 EDGWARE ROAD 133 LEITH STREET
Three new branches now open

TRANSISTOR SALE. Mullard OC71 3/9, OC45 4/11, OC44 4/11, OC72 4/9, OC81 4/11, OC171 8/9, Ediswan XA101 3/9, XB102 3/9, XA112 3/9, XB113 3/9, XB104 3/9, XC01A 3/9. Postage od. for up to 3 Transistors.

D.C. SUPPLY KIT. 12 v. 1 a. consisting of a partially drilled metal case, mains trans. F.W. Bridge Rectifier, 2 fusesholders and fuses. Change Direction switch, variable speed regulator and circuit. For 200-250 v. A.C. mains. Suitable for Electric Trains. Limited number available at 29/11.

SELENIUM RECTIFIERS
F.W. BRIDGE 24 v. 2 amp. .. 14/9
6/12 v. 1 a. .. 3/11 24 v. 20 amp. .. 89/9
6/12 v. 2 a. .. 6/11 H.T. TYPES H.W.
6/12 v. 3 a. .. 9/9 150 v. 40 mA .. 3/9
6/12 v. 4 a. .. 12/3 250 v. 50 mA .. 3/11
6/12 v. 6 a. .. 15/3 250 v. 60 mA .. 4/11
6/12 v. 10 a. .. 26/9 250 v. 80 mA .. 5/11
6/12 v. 15 a. .. 35/9 250 v. 250 mA .. 11/9
CONTACT COOLED. 250 v. 75 mA. F.W. (Bridge). 10/11. 250 v. 50 mA. F.W. (Bridge) 8/11. H.W. 250 v. 60 mA. 5/11.

HI-FI 10-WATT AMPLIFIERS. Brand New Complete **£7.19.9** Carr. 5/6.

Manufacturers' discontinued Model. Push-Pull output. Latest high efficiency valves. Dual separately controlled inputs for "Mike". Separate Bass and Treble Controls. High sensitivity. Output for 3 or 15 ohm speaker. Guaranteed tested and in perfect working order.

DERBY Now open at 26 Osment Road The Spot

HEAVY DUTY LOUDSPEAKERS IN SUBSTANTIAL REXINE COVERED CABINETS. Type BG1. Suitable for Bass Guitar. Speaker Unit 15in., High Flux, 15 ohms, 30 watts. Cabinet size approx. 24 x 21 x 13in. (only 19s) Carr. Or Deposit 37/9 and 12 monthly payments of 31/6. Type BG32. Suitable Bass and Lead Guitar. Two 12in. high flux 15 ohm 25 watt speakers, one with aluminium speech coil and dual cone to provide smooth frequency response from 25 to 17,000 c.p.s. Cabinet size approx. 30 x 21 x 14in. Covered in two contrasting tones of grey Vynair and Rexine. Rating 50 watts. Only 29 gns. Or Deposit **£3.7.6** and 12 monthly payments of 50/-.

LARGE REXINE COVERED SPEAKER CABINETS. Heavy keyboard construction. Very attractive two tone covering of Rexine and Vynair. Size 30 x 21 x 16in. cut for 15in. or 18in. speaker or for two 12in. units. Or Deposit 25/9 and 9 monthly payments 25/9. Size 30 x 30 x 18in. cut for 15in. or 18in. speaker 13gns. or Deposit 30/4 and 9 monthly payments 30/4. Suitable speakers available.

FANE EXTRA HEAVY DUTY LOUDSPEAKER 15in. TYPE 153 40 watts. Total flux 375,000 lines. Extremely high sensitivity. 15 ohm voice coil. Only 18 gns. or Deposit 37/9 and 12 monthly payments of 31/6.


FANE EXTRA HEAVY L/SPEAKER 18s. 18in., 15 ohms, 60 watts, 3in. diam. Speech Coil. Total Flux 375,000 lines. High sensitivity. ONLY 24 gns. or Deposit 37/9 and 12 monthly payments of 42/9. Send S.A.E. for leaflet on 153 and 183.

EX. GOVT. SMOOTHING CHOKES. 200 mA, 3-5 H, 50 ohms, Parmeko 8/9; 150 mA, 10 H, 50 ohms 9/9; 80 mA, 20 H, 50 ohms 5/9; 120 mA, 12 H, 100 ohms 8/9; 50 mA, 50 H, 1,000 ohms 6/9; 100 mA, 10 H, 100 ohms 6/9; 60 mA, 5-10 H, 250 ohms 2/11.

COMPLETE POWER PACK KIT, 19/11 Consisting of Mains Trans. Metal Rectifier, Double electrolytic, smoothing choke chassis and circuit. For 200-250 v. A.C. mains. Output 250 v., 60 mA, 6.3 v., 2 a.

R.S.C. POWER PACK, 39/9. Louvred metal case only 8 x 5 x 2 1/2in. Stove enamelled. For 200-250 v. A.C. mains. Output at 4 pin plug and socket 250 v. 60 mA, fully smoothed and 6.3 v. 2 a. Suitable for power requirements of almost any Pre-amp. or Radio Tuner.

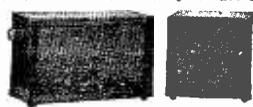R.S.C. BABY ALARM or INTER-COMM. KIT. Complete set of parts with diagrams, etc. Housed in two polished walnut finished cabinets of pleasing design. High sensitivity. For 200-250 v. A.C. mains. Fully isolated. Controllable at both units. An intercomm. of this class would normally cost £20-£30. Only 99/6, carr. 5/- or assembled ready for use 8 gns.



EX. GOVT. SELENIUM RECTIFIERS 12v 15 AMP 19/9 (BRIDGE) F.W. ONLY

R.S.C. (Manchester) Ltd.

LEICESTER 32 High St.	BIRMINGHAM 6 Gt. Western Arcade, Opp. Snow Hill Station	SHEFFIELD 13 Exchange St. (Castle Market Bldgs.) Sheffield	HULL 51 Savile St., Hull	LIVERPOOL 73 Dale St. Liverpool 2	BRADFORD 56 Morley St. (above Alhambra Theatre) Bradford	MANCHESTER 8-10 Brown St. (Market Street) Manchester 2	LEEDS 5-7 County (Mecca) Arcade Briggate, Leeds
Half-day Thursday	No half-day	Half-day Thursday		Half-day Wednesday		No half-day	No half-day

MAIL ORDERS to 54 Wellington St, Leeds 1. Terms: C.W.O. or C.O.D. No C.O.D. under £1. Postage 2/9 extra under £2. 4/6 extra under £5. Trade Supplied. S.A.E. with all enquiries please.

R.S.C. (Manchester) Ltd.

LEICESTER 32 High St.
BIRMINGHAM 6 Gt. Western Arcade, Opp. Snow Hill Station
 Half-day Thursday
 No half-day

MAIL ORDERS to 54 Wellington St, Leeds 1. Terms: C.W.O. or C.O.D. No C.O.D. under £1. Postage 2/10 extra under £2. 4/6 extra under £5. Trade Supplied. S.A.E. with all enquiries please.

SHEFFIELD 13 Exchange St. (Castle Market Bldgs.)
 Half-day Thursday

HULL 51 Savile St., Hull
 Half-day Thursday

LIVERPOOL 73 Dale St. Liverpool 2
 Half-day Wednesday

BRADFORD 56 Morley St. Above Alhambra Theatre) Bradford
 Half-day Wednesday

MANCHESTER 8-10 Brown St. (Market Street) Manchester 2
 No half-day

LEEDS 5-7 County (Mecca) Arcade Briggate, Leeds
 No half-day

DERBY 26 Osmaston Road THE SPOT

FANE HEAVY DUTY HI-FI SPEAKERS

12in. 15 ohms. Cast chassis. Exceptionally robust 2in. diam. Voice Coil Assemblies. 122/10 20watt. 5 gns. 122/10A 20watt. 6 gns. 122/12 20watt. 7 gns. 122/12A 20watt. 8 gns. 122/14 22watt. 9 gns. 122/14A 22watt. 10 gns. 122/17 25watt. £11.17.6 25watt. £12.17.6 15in. 15 ohms. Cast chassis. Exceptionally robust 2in. diam. Voice Coil Assemblies. 152/12 20watt. 12 gns. 152/12A 20watt. 13 gns. 152/14 27watt. 14 gns. 152/14A 27watt. 15 gns. 152/17 35watt. 16 gns. 152/17A 35watt. 17 gns. "A" indicates dual cone type. 30-17000 c.p.s. Send S.A.E. for leaflets. Terms available.

R.S.C. 30-WATT ULTRA LINEAR

HIGH FIDELITY AMPLIFIER A10
 A highly sensitive Push-Pull high output unit with self-contained Pre-amp. Tone Control Stages. Certified performance figures compare equally with most expensive amplifiers available. Hum level 70 dB down. Frequency response ± 3 dB 30-30,000 c/s. A specially designed sectionally wound ultra linear output transformer is used with 807 vacuum valves. All components are chosen for reliability. Six valves are used EF86, EF86, ECC83, 807, 807, GZ34. Separate Bass and Treble Controls are provided. Minimum input required for full output is only 12 millivolts so that ANY KIND OF MICROPHONE OR PICK-UP IS SUITABLE. The unit is designed for CLUBS, SCHOOLS, THEATRES, DANCE HALLS, OUT-DOOR FUNCTIONS, etc. For use with Electronic ORGAN, GUITAR, STRING BASS, etc. For standard or long-playing records. OUTPUT SOCKET PROVIDES L.T. and H.T. for RADIO FEEDER UNIT. An extra input with associated vol. control is provided so that two separate inputs such as Gram and "Mike" can be mixed. Amplifier operates on 200-250 v. 50 c/s. A.C. Mains and has output of 15 ohm 30 watt speakers. Complete kit of parts with fully punched chassis and point-to-point wiring diagrams and instructions. It required perforated cover with carry handles can be supplied

11 Gns. Carr. 10/-

for 19/9. The amplified can be supplied, factory built with EL34 output valves and 12 months' guarantee, for 14 gns. Send S.A.E. for leaflet.

TERMS: DEPOSIT 33/9 and 9 monthly payments of 3/9. Suitable microphones and speakers available at competitive prices.

ARMSTRONG, DULCI, LINEAR, ROGERS, LEAK and JASON EQUIPMENT, GOODMAN'S, W.B. and FANE SPEAKERS, GARRARD and GOLDRING T/ TABLES CASH or H.P.

SUPERHET FEEDER UNIT. Design of a high quality Radio Tuner (specially suitable for use with our Amplifiers). Delayed A.V.C./I.C. Controls are Tuning W/C and Vol. Only 250 v. 15 mA. H.T. and L.T. of 8.5 v. amp. required from amplifier. Size approx. 9 x 6 x 7 1/2 in. Simple alignment procedure. Point-to-Point wiring diagrams, instructions and price parts list with illustrations. 2/6. Total building cost £4.15.0. S.A.E. for leaflet.

R.S.C. BATTERY TO MAINS CONVERSION UNITS

R.S.C. BATTERY TO MAINS TYPE BM1. An all-dry battery eliminator. Size 5 1/2 x 4 1/2 in. approx. Completely replaces battery supplying 1.4 v. and 90 v. where A.C. mains 200-250 v. 50 c/s is available. Suitable for all battery portable receivers requiring 1.4 and 90 v. This includes low consumption types. Complete kit with diagrams. 39/9. or ready to use. 46/6.



P.M. SPEAKERS. 10in. W.B. "Stentorian" 30; 15 ohms type HF 1012 10 watts, hi-fidelity type. Recommended for use with our All Amplifier. £4.7.6. 12in. R.A. 3 ohms 10 watts (12,000 lines). 59/9.

TWEETERS. R.A. 3 ohm. 25/9; 15 ohm 25/9 R.A. 12in. DUAL CONE 3 ohm 8 watt Speakers. Ideal for Stereo. Only 39/9 ea.

JASON FMTI V.H.F./F.M. Radio Tuner design. Total cost of parts including valves, Tuning dial. Eschutecon, etc., £6.19.6.

LINEAR L45 MINIATURE 45 WATT QUALITY AMPLIFIER. Suitable for any record playing unit and most microphoned Negative feedback 10-point Servo Bass and Treble Controls. For mains 200-250 v. 50 c/s. Output for 2-3 ohm speaker. Mullard valves E230, ECC83, EL34. Size only 7 x 5 x 5 1/2 in. high. Guaranteed 12 months. Only £5.19.6. Send S.A.E. for leaflet. Terms: Deposit 22/6 and 5 monthly payments of 2/6.


12in. 16 WATT HIGH QUALITY LOUDSPEAKER



18 x 14 x 10in. Fin. sh. as above. Terms: Deposit 17/9 and 9 monthly payments of 17/9. Only £7.19.6. Carr. 8/6.

For larger types see preceding page. **LINEAR LG34 GRAM AMPLIFIER.** High quality. Separate Bass and Treble Controls. Handsome appearance. Complete kit enclosed. Black/Gold Frontplate 5 gns.

R.S.C. 4-5 WATT A5 HIGH-GAIN AMPLIFIER

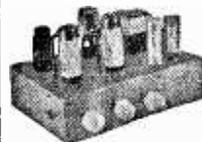

A highly-sensitive 4-valve quality amplifier for the home, small club, etc. Only 50 millivolts input is required for full output so that it is suitable for use with the latest high fidelity pick-up heads, in addition to all other types of pick-ups and practically all "mikes". Separate Bass and Treble Controls are provided. These give full long-playing record equalisation. Hum level is negligible being 71 dB down. 15 dB of Negative feedback is used. H.T. of 300 v. 25 mA and L.T. of 6.3 v. 1.5 A. is available for the supply of a Radio Feeder Unit, or Tape-Deck pre-amplifier. For A.C. mains input of 200-250 v. 50 c/s. Output for 2-3 ohm speaker. Chassis is not alive. Kit is complete in every detail and includes fully punched chassis (with bassplate) and instructions. Exceptional value at only £4.15.0, or assembled ready for use 25/- extra. Plus 3/6 carr., or deposit 22/6 and 5 monthly payments of 22/6 for assembled unit.

GLASGOW — LONDON — EDINBURGH

326 ARGYLE STREET
 Now Open

238 EDGWARE ROAD
 Opening Shortly

133 LEITH STREET
 Now Open

THE SKYFOUR T.R.F. RECEIVER. A design for a 3 valve long and medium wave 200-250 v. A.C. Mains receiver with selenium rectifier. High gain H.F. stage and low distortion detector. Valve line-up 6K7, 5P61, 6V6C. Selectivity and quality excellent. Simple to construct. Point-to-Point wiring diagrams, instructions and parts list 1/9, maximum building costs £4.19.6, inc. attractive walnut veneered wood cabinet 12 x 6 1/2 x 5 1/2 in.

R.S.C. BASS REFLEX CABINETS, JUNIOR MODEL. Specially designed for W.B. HF102 Speaker, but suitable for any good quality 10in. speaker. Acoustically lined and ported. Polished walnut veneer finish. Size 18 x 12 x 10in. Handsome appearance. Ensure superb reproduction for only £3-19.6.

STANDARD MODEL. As above but for 12in. speakers. Size 20 x 15 x 13in. For vertical or horizontal use. £3-19.6. Set of legs with brass ferrules. 19/6.

R.S.C. JUNIOR HI-FI REPRODUCER. The very latest Goodman Axlette 8 High Fidelity loudspeaker (retailing at approx. 5 gns.) fitted in a specially designed Bass Reflex cabinet size 12 x 18 x 10in. Acoustically lined and ported and finished in polished walnut veneer. Matching impedance 15 ohms frequency range 40-15,000 c.p.s. Power handling 6 watts nominal. **8 Gns.** Carr. 4/6. Ideal for Stereo.

MULTI-METER, CABY MI. Sensitivity 2,000 ohms per volt. A.C. and D.C., 54/- A.10. Basic Meter sensitivity 155 microamps A.C. and D.C. ranges £4.17.6. B.20. Sensitivity up to 10,000 ohms per volt A.C. and D.C., £5.10.0. 30,000 ohms per volt, with overload buzzer. £8.18.6.

R.S.C. CORNER CONSOLE CABINETS

Polished walnut veneer finish. Pleasing design. **JUNIOR MODEL.** Size 20 x 11 x 8 in. for 6in. speakers. £25.9. **STANDARD MODEL.** Size 27 x 18 x 12in. for 8 or 10in. speakers £4.11.9. **SENIOR MODEL.** Size 30 x 20 x 15in. for 12in. Speaker Suitable. Speaker systems below. Only 7 gns.



AUDIOTRINE HI-FI SPEAKER SYSTEMS. Consisting of matched 12in. 12,000 line, 15 ohm high quality speaker; cross-over network consisting of choke condenser, etc.) and Tweeter The smooth response and extended frequency range ensure surprisingly realistic reproduction. Standard 10 watt rating £4.19.9. Carr. 5/- or Senior 15 watt. £6.19.9. Carr. 7/6.

AUDIOTRINE EQUIPMENT CABINETS

Size 36 x 15 x 18in. Beautiful walnut veneered finish. Elegant contemporary design. Robust construction. Uncut, removable baseboard. **Denr.** above (only 121 gns. Carr. 15/-) Terms: Dep. 25/9 and 9 monthly pymts. 20/9.



kit of parts with diagrams and instructions. 49/9, or ready for use. 59/6.

AUDIOTRINE HI-FI TAPE RECORDER KIT 25


REALISM AT INCREDIBLY LOW COST. CAN BE ASSEMBLED IN AN HOUR
 Incorporating the latest Collaro Studio Tape Transcriber, The Audiotrine High Quality Tape Amplifier with negative feedback equalisation for each of 3 speeds. High Flux P.M. Speaker, empty Tape Spool, a Reel of Best Quality Tape and a Handsome Portable Carrying Cabinet attractively finished in durable two-tone Polychrome size 14 1/2 x 15 x 8 1/2 in. high and circuit. Total cost if purchased individually approximately £40. Performance equal to units in the 330-330 class. S.A.E. for leaflet.
TERMS: Deposit £2.13.9 and 12 monthly payments of 44/-. Cash price if settled in 3 months.



HIGH FIDELITY 12-14 WATT AMPLIFIER TYPE A11

PUSH-PULL ULTRA LINEAR OUTPUT 'BUILT-IN' TONE CONTROL PRE-AMP STAGES

Two input sockets with associated controls allow mixing of "mike" and gram, as in A10 High sensitivity. Includes 5 valves, ECC83, ECC83, EL84, EL84, EZ81. High Quality specially wound output transformer specially designed for Ultra Linear operation and reliable small condensers of current manufacture. INDIVIDUAL CONTROLS FOR BASS AND TREBLE "Lift" and "Cut". Frequency response ± 3 dB 30-30,000 c/s. Six negative feedback loops. Hum level 60 dB down. ONLY 23 millivolts INPUT required for FULL OUTPUT. Suitable for use with all makes and types of pick-ups and microphones. Comparable with the very best designs for STANDARD or LONG PLAYING RECORDS. FOR MUSICAL INSTRUMENTS such as STRING BASS, LEAD OR RHYTHM GUITARS, etc.
OUTPUT SOCKET with plug provides 300 v, 30 mA, and 6.3 v, 1.5 a. For supply of a RADIO FEEDER UNIT. Size approx. 12 x 9 x 7 in. For A.C. mains 200-250 v, 50 c.p.s. Output for 8 and 15 ohm speakers. Kit is complete to last nut. Chassis is fully punched. Full instructions and point-to-point wiring diagrams supplied. Only **8 Gns.** Carr. 10/-. (Or factory built 51/- extra.)
 If required louvered metal cover with 2 carrying handles can be supplied for 13/9. **TERMS ON ASSEMBLED UNITS.** DEPOSIT 2/9 and 9 monthly payments of 2/9. Send S.A.E. for illustrated leaflet detailing Cabinets, Speakers, Microphones, etc., with cash and credit terms.

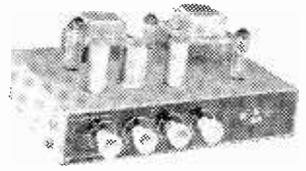

LINEAR TAPE PRE-AMPLIFIER. Type LP/1, Switched Negative feedback equalisation. Positions for Record Lin., 3 1/2 in., 7 in. and Playback. EM84 Recording Level Indicator. Designed primarily as the link between a Collaro Tape Transcriber and a high fidelity amplifier, but suitable for almost any Tape Deck. Only 9 gns. S.A.E. for leaflet.

R.S.C. STEREO/TEN HIGH QUALITY AMPLIFIER

A complete set of parts for the construction of a stereophonic amplifier giving 5 watts high quality output on each channel (total 10 watts). Sensitivity is 50 millivolts. Suitable for all crystal stereo heads. Ganged Bass and Treble Control give equal variation of "lift" and "cut". Provision is made for use as straight (monaural) 10-watt amplifier. Valve line-up ECC83, ECC83, EL84, EL84, EZ81. Outputs for 2-3 ohm speakers. Point-to-Point wiring diagrams and instructions supplied. Send S.A.E. for leaflet. Full constructional details and price list 2/6. Carr. 10/-. ready to use for 59/6 extra.



Kit can be supplied assembled and

ONLY 3 PAIRS OF SOLDERED JOINTS PLUS MAINS

R.S.C. GRAM AMPLIFIER KIT. 3 watts output. Negative feedback. Control Vol., Tone and Switch. Mains operation 200-250 v. A.C. Fully isolated chassis. Circuit, etc., supplied. Only 39/9. Carr. 3/9.
HI-FI CRYSTAL PICK-UP HEADS. (Cartridges.) Acos Standard replacement for Garrard, B.S.R. and Collaro. 16/9. Acos Stereo-Monaural 29/9. Ronette Stereo-Monaural 39/6. B.S.R. Stereo 39/9.
GRAMMITE RECORDING HEADS. High Impedance Record/Playback 22/-. Low Impedance Erase, 12/6.
MARRIOTT RECORDING HEADS. High Impedance. Record/Playback 15/-. Low Impedance. Erase, 10/-.
CRISTAL PICK-UPS. Complete and with latest Acos/Hi-Fi Turnover Cartridge 29/11.
CRYSTAL MICROPHONES. Hand Type NP110 14/9. R.T.C. 19/9. Acos Mic 40 25/9. Acos Mic 45 29/9. Stick Type Acos 39-1 39/9. BM3 with neck band and heavy table stand 59/9. Lapel type 29/9.
COLLARO TUNING. 4-speed Single Player Unit and Crystal Pick-up with hi-fi Turnover head Only 23-19.6.
B.S.R. UA14 4-sp'd AUTO-CHANGERS with hi-fi turnover head. £6-19.6. Carr. 4/6.
GARRARD AUTO-SLIM 4-SPEED AUTO-CHANGERS with high fidelity Pick-up. Latest model. For 200-250 v. A.C. mains. £7-17.6. Carr. 4/6.
GARRARD AT6 AUTO-SLIM DELUXE 4-SPEED AUTO-CHANGERS. Turnover GC8 head, for 200-250 v. A.C. mains. £11-9.0.
GLSA MINIATURE 2-3 WATT GRAM AMPLIFIER. For use with any single or auto-change unit. Output for 2-3 ohm speaker. For 200-250 v. A.C. mains. Size 11 x 2 1/2 x 2 1/2 in. Controls: Vol. and Tone with Switch. Only 59/6.

SENSATIONAL STEREO OFFER

A complete set of parts **4 Gns.** to construct a good quality Stereo amplifier with an undistorted output of total 8 watts. For A.C. mains input of 200-250 v. Sensitivity 130 m.v. Ganged Vol. and Tone Controls. Preset balance control. Full instructions and wiring diagrams supplied. Stereo Pick-up head 19/9 extra with above only.
HEAVY DUTY CHARGER KIT. 6 1/2 v. 6 amps., variable output. Consisting of Mains Transformer, 0-200-230-250 v.; P.W. (Bridge) Selenium Rectifier; Ammeter, Variable Charge Rate Selector Panels, Fuses, Fuses, Fuseholder and circuit. 59/9. Carr. 4/6.



HEAVY DUTY CHARGER KIT. 6 1/2 v. 6 amps., variable output. Consisting of Mains Transformer, 0-200-230-250 v.; P.W. (Bridge) Selenium Rectifier; Ammeter, Variable Charge Rate Selector Panels, Fuses, Fuses, Fuseholder and circuit. 59/9. Carr. 4/6.

R.S.C. MAINS TRANSFORMERS (GUARANTEED)

Interleaved and Impregnated. Primary 200-230-250 v. 50 c/s. Screened TOP SHROUDED "DROP THROUGH"
 250-0-250V. 70mA. 6.3v. 2a. 0-5-6.3v. 2a. 17/9
 350-0-350V. 80mA. 6.3v. 2a. 0-5-6.3v. 2a. 18/9
 250-0-250V. 100mA. 6.3v. 2a. 6.3v. 1a. 21/9
 250-0-250V. 100mA. 6.3v. 3.5a. C.T. 27/9
 350-0-350V. 100mA. 6.3v. 4a. 0-5-6.3v. 3a. 25/9
 300-0-300V. 130mA. 6.3v. 4a. C.T. 1a. for Mullard 510 Amplifier. 29/9
 300-0-300V. 100mA. 6.3v. 4a. 0-5-6.3v. 3a. 26/9
 350-0-350V. 150mA. 6.3v. 4a. 0-5-6.3v. 3a. 26/9
FULLY SHROUDED UPRIGHT
 250-0-250V. 80mA. 6.3v. 2a. 0-5-6.3v. 2a. Midget type 21 x 3 x 3 in. 17/11
 250-0-250V. 100mA. 6.3v. 4a. 0-5-6.3v. 3a. 27/9
 300-0-300V. 100mA. 6.3v. 4a. 5v. 3a. 27/11
 300-0-300V. 150mA. 6.3v. 4a. C.T. 6.3v. 1a. for Mullard Amplifier. 33/9
 300-0-350V. 100mA. 6.3v. 4a. 0-5-6.3v. 3a. 27/11
 350-0-350V. 150mA. 6.3v. 4a. 0-5-6.3v. 3a. 35/9



Kit can be supplied assembled and

R.S.C. BATTERY CHARGING EQUIPMENT

All for A.C. Mains 200-250v., 50 c/s.
ASSEMBLED 6 1/2 v. 6 amp. Fitted Ammeter and variable charge rate selector plug for 6 v. or 12 v. Louvered metal case with stoved grey hammer finish. Fused and ready for use with mains and output leads and battery clips. Carr. 4/6. **59/9**
CHARGER KIT, 12 v. 14 AMP or 24 v. 7 AMP Consisting of mains trans. 200-230-250 v. P.W. (Bridge) selenium Rectifier. Ammeter. Fuses, Variable Resistor, Heavy Steel Stove enamelled case and Circuit. Only £9-19.6. Carr. 15/-. Please state if 12 v. or 24 v. kit required.



ASSEMBLED 6 1/2 v. 6 amp. Fitted Ammeter and selector plug for 6 v. or 12 v. Louvered metal case with stoved grey hammer finish. Fused, ready for use with mains and output leads. Carr. 3/9. **39/9**
 6 1/2 v. 6 amp. 27/9 Less meter.

FULLY SHROUDED (continued)
 425-0-425V. 200mA. 6.3v. 4a. C.T. 5v. 3a. 55/9
 425-0-425V. 200mA. 6.3v. 4a. C.T. 6.3v. 4a. C.T. 5v. 3a. 59/9
 450-0-450V. 250mA. 6.3v. 4a. C.T. 5v. 3a. 69/9
OUTPUT TRANSFORMERS
 Midget Battery Pentode 681 for 3S4, etc. 4/6
 Small Pentode 5,000Ω to 3Ω 4/6
 Small Pentode 75,000Ω to 3Ω 4/6
 Standard Pentode 5,000Ω to 3Ω 5/9
 Standard Pentode 7,000Ω to 3Ω 5/9
 10,000Ω to 3Ω 5/9
 Push-Pull 8 watts, EL84, or 6V6 to 3Ω or matched to 15Ω 9/9
 Push-Pull 10-12 watts to match 6V6 or EL84 to 3-8 to 15Ω 19/9
 Following types for 3 and 15Ω speakers:
 Push-Pull 10-12 watts 6V6 or EL84 18/9
 Push-Pull 15-18 watts 6L6, KT66 22/9
 Push-Pull Mullard 510 Ultra Linear 25/9
 Push-Pull 20 watts, sectionally wound. 6L6, KT66, EL34, etc. 49/9




Kit can be supplied assembled and

Guaranteed 12 months.

BATTERY CHARGER KITS Consisting of Mains Transformer, P.W. Bridge, Metal Rectifier, metal ventilated steel case, Fuses, Fuseholders, Grommets, panels, Heavy Duty Clip, circuit. Carr. 3/6 extra.
 6 v. or 12 v. 1 amp. 22/9
 As above, with Ammeter 25/9
 6 v. or 12 v. 2 amps. 19/9
 6 v. or 12 v. 2 amps. inclusive of Ammeter 35/9
 6 v. or 12 v. 4 amps. with Ammeter and variable charge rate selector 52/9
CHARGER AMMETERS 0-1.5 a. 0-4 a. 0-7 a. 8/9 ea.
CHARGER KIT, 12v. 10 Amp. with variable charge rate adjustment and ammeter. £4-19.6. Carr. 10/-.

MIDGET MAINS Primaries 200-250 v. 50 c/s. 250v. 60mA. 6.3v. 2a. 11/9
 250-0-250V. 60mA. 6.3v. 2a. 12/11
 Both above size 2 1/2 x 2 1/2 in.
FILAMENT TRANSFORMERS
 All with 200-250v. 50 c/s primaries 6.3v. 1.5a. 5/9; 6.3v. 2a. 7/6; 0-4-6.3v. 2a. 7/9; 12v. 1a; 7/11; 6.3v. 3a; 8/11; 6.3v. 6a; 17/6; 12v. 1.5a. wire, etc. 17/6
SMOOTHING CHOKES
 150mA. 7-10 H. 250 ohms. 11/9
 100mA. 10H. 200 ohms. 8/9
 80mA. 10H. 350 ohms. 5/9
 60mA. 10H. 400 ohms. 4/11
CHARGE TRANSFORMERS
 All with 200-230-250v. 50 c/s Primaries:
 0-9-15v. 1a. 12/9; 0-9-15v. 2a. 14/9; 0-9-15v. 3a. 16/9; 0-9-15v. 5a. 19/9; 0-9-15v. 6a. 23/9; 0-9-15v. 8a. 28/9.
Auto (Step up/Step down) TRANS. 0-110-230-250v. 50-80 watts. 13/9;
 250 watts. 39/9; 150 watts. 27/9.
MICROPHONE TRANSFORMERS 120-1 high grade, clamped, 8/9.

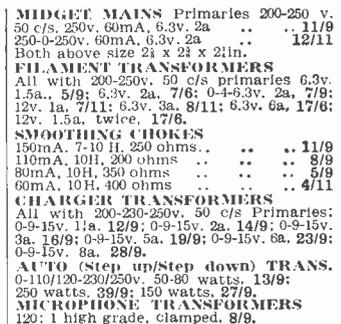

Kit can be supplied assembled and

EQUIPMENT FOR RADIO
"AMATEURS" COMMUNICATIONS



INSTRUMENTS FOR TEST,
SERVICE AND WORKSHOP

SAVE MONEY . . . AND ENJOY YOURSELF BUILDING THE WORLD'S BEST KIT-SETS — THE HEATHKIT WAY!

The clearly written instruction manuals, issued with each kit, show you how.

DEFERRED TERMS ON ORDERS ABOVE £10. ALL MODELS ALSO AVAILABLE ASSEMBLED

TEST INSTRUMENTS



5in. OSCILLOSCOPE. Model 10-12U. Laboratory quality at utility oscilloscope price. Wide band amplifiers essential for T.V. servicing, F.M. alignment, etc. T/B covers 10 c/s-500 kc/s in 5 ranges.

£41.10.0 assembled. **£32.12.6** Kit
PORTABLE 'SCOPE. Model OS-1. A compact portable oscilloscope, ideal for servicing and general work. Printed circuit board. Case: 7½ x 4½ x 12½in. long. Wt. only 10½ lbs.

£29.8.0 assembled **£21.18.0** Kit

10-12U

ELECTRONIC SWITCH. Model S-3U. Converts a single beam oscilloscope into double beam operation.

£18.10.0 assembled **£12.18.0** Kit



VALVE VOLTMETER. Model V-7A. The world's best selling VTVM. Measures up to 1,500 volts (d.c. and r.m.s.) and 4,000 pk. to pk. Res. 0.1Ω 1,000 MΩ. Centre zero dB scale, d.c. input. Resistance 11MΩ, 4½in. meter. Complete with test prods, leads and standardising battery.

£19.18.6 assembled **£13.18.6** Kit

V-7A

RF PROBE. 309-CU extends range to 100 Mc/s. Indication to 300 Mc/s.

£1.13.6 Kit

HV PROBE, HV-336 measures up to 30,000V d.c.

£2.19.6 Kit

RF SIGNAL GENERATOR. Model RF-1U. Up to 100 Mc/s fundamental, 200 Mc/s harmonics. Up to 100 mV output on all bands.

£19.18.0 assembled **£13.8.0** Kit

MULTIMETER. Model MM-1U. Ranges: 0-1.5 v. to 1,500 v. a.c. and d.c.; 150µA to 15A d.c.; 0.2Ω to 20MΩ, 4½in. 50µA meter.

£18.11.6 assembled **£12.18.0** Kit

A wide range of other test instruments available including: R/C Bridge C-3U £10.10.0. AF Voltmeter AV-3U, £16.10.0. Wattmeter AW-1U, £17.5.0. (Capacitance meter) CM-1U £15.15.0. Power supplies. Decade boxes etc. Many other instruments available under American Mail order scheme. Why not send for full details?

SSU-1 SPEAKER SYSTEM



SSU-1

A practical solution to the problem of a moderately-priced speaker suitable for Stereo/Mono amplifiers, where the equipment has to be compact. Two speakers, horizontal control, ducted port reflex cabinet.

Horizontal or vertical (without legs)

Incl. P.T. **£10.17.6** Kit

Horizontal or vertical (with matching legs)

Incl. P.T. **£11.12.0** Kit

"AMATEUR" EQUIPMENT

AMATEUR BANDS RECEIVER

Model RA-1. Covers all amateur bands from 160-10 m. Half lattice crystal filter, 8 valve, "S" meter, tuned R.F. amplifier stage.


£39.6.6 Kit
Assembled **£52.10.0**



RA-1

AMATEUR TRANSMITTER. Model DX-100U. Covers all amateur bands 160-10M. 150 w. d.c. input, self contained with power supply. Modulator, VFO.

Assembled **£104.15.0** **£79.10.0** Kit

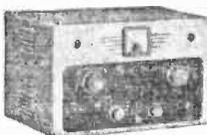

DX-40U

AMATEUR TRANSMITTER

Model DX-40U. Covers 80-10 m Power inputs 75 w. C.W., 60 w peak C.C. phone. Output 40 w to aerial. Prov. for V.F.O.

£33.19.0 Kit
Assembled **£45.8.0**

Other kits in the amateur range include: SSB Adaptor SB-10U, £39.5.0 Variable Freq. Oscillator VF-1U, £12.10.0 Balun Coil Unit B-1U £4.15.6. Grid-Dip Meter GD-1U £10.19.6. Q Multiplier QPM-1, £8.10.0. Wide range of model: under American Mail Order Scheme.

TRANSISTOR RECEIVERS

"OXFORD" LUXURY TRANSISTOR DUAL WAVEBAND RECEIVER.

The ideal domestic, car or personal portable receiver. 10 Semi-conductors. Solid leather case. Send for full details.

Incl. P.T. **£14.18.0** Kit



UXR-1

6 TRANSISTOR PORTABLE. Model UXR-1. Prealigned I.F. transformers Printed circuit, 7in. x 4in. high flux speaker Real hide case. Very easy to build.

Incl. P.T. **£12.11.0** Kit

7 TRANSISTOR PORTABLE. Model RSW-1. Two short trawler and medium wave bands.

Incl. P.T. **£19.17.6** Kit

"MOHICAN" GENERAL COVERAGE RECEIVER. Model GC-1U. Excellent portable or general purpose receiver for "amateur" or short wave listening. See full spec. leaflets.

Assembled **£45.17.6** **£37.17.6** Kit



GC-1U

SEND FOR FREE BRITISH CATALOGUE
OVER 50 MODELS TO CHOOSE FROM

DAYSTROM LTD.

Dept. PW-5.

GLOUCESTER
ENGLAND


A member of the Daystrom Group, manufacturers of the WORLD'S LARGEST-SELLING ELECTRONIC KITS



Millions of Heathkit models are in use throughout the world because:—

- ★ They are so easy to build. Even for an absolute beginner.
- ★ The manual of instructions is foolproof. Because all manuals are written by the world's experts in kit-set design.
- ★ You get professional appearance and performance with every model.

HI-FI AMPLIFIERS

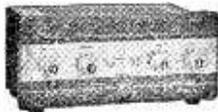

6W STEREO AMPLIFIER. Model S-33. 3 w/chl. Inputs for radio, tape and gram. Stereo/Mono ganged controls. Sensitivity 200mV.
 £18.18.0 Assembled **£13.7.6** Kit



18W STEREO AMPLIFIER. Model S-99. Ganged controls. Stereo/Mono gram, radio and tape recorder inputs. P/B selection.
 £27.19.6 Kit
 £37.19.0 Assembled

S-33
6W DE-LUXE STEREO AMPLIFIER. Model S-33H. An inexpensive stereo/mono amplifier with high sensitivity. Suitable for use with Decca Deram cartridge.
 £21.7.6 Assembled **£15.17.6** Kit

5W HI-FI MONO AMPLIFIER. Model MA-5. A low priced amplifier based on the S-33. Printed circuit construction makes it easy to build. **£14.19.6** assembled. **£10.19.6** Kit

TAPE RECORD/REPLAY AMPLIFIER KITS. Will operate with most tape decks. Send for details.
 TA-1M (Mono), £19.18.0. Kit TA-1S (Stereo), £25.10.0 Kit

HI-FI SINGLE CHANNEL AMPLIFIER. Model MA-12. Ideal for use with Models USC-1 and UMC-1. 0.1% THD at 10 W. Wide freq. range. **£15.18.0** Assembled. **£11.18.0** Kit

OTHER MODELS

DE-LUXE LARGE SCALE VVM KIT. Model IM-13U. a.c. and d.c. volts 0.1-1500v in 7 ranges. Ohms to 1000MΩ in 7 ranges. 6" Meter. Modern styling with unique gimbal mount.



£18.18.0 Kit. **£26.18.0** Assembled



PUBLIC ADDRESS AMPLIFIER, PA-1. For vocal and instrumental groups, guitars, etc. 50 W r.m.s., 100 W pk output. 4 inputs, 2 loudspeakers in one compact unit. Send for full details.

£74.0.0 Assembled **£54.15.0** Kit

Set of 4 Legs 17/6 extra.

COMMUNICATIONS TYPE RECEIVER RG-1. A high performance low cost receiver for the discriminating listener. Freq.: cov. 600 kc s-1.5 Mc/s and 1.7 Mc/s to 32 Mc/s. Send for details.

£53.0.0 Assembled. **£39.16.0** Kit



SELF SUPPORTING AERIAL TOWER KIT. Model HTI. Ideal for Amateur Radio or TV reception, etc. Strong steel construction, height 32 ft. tapered square section 3ft. x 3 ft. at base. Kit **£29.15.0** Oxide Painted. **£35.15.0** Galvanised.

Accessories available. Send for details.

GOTSWOLD SPEAKER SYSTEMS

STANDARD MODEL
 Acoustically designed enclosure in the white 26 x 23 x 15 1/2 in. 12in. bass speaker, elliptical middle speaker, 2in. pressure unit. Covers 30-20,000 c/s. Complete kit with all controls.



MFS SYSTEM

A minimum floor space model for the smaller room. 36in. high x 16 1/2 in. x 14in. deep. Almost identical performance to standard model.

Price either model **£23.4.0** Kit

HI-FI TUNERS

Model FM-4U. Tuning range 88-108 Mc/s. Tuning unit (FMT-4U) with 10.7 Mc/s I.F. (£2.15.0 inc. P.T.). I.F. Amp. (FMA-4U) complete with cabinet and valves.

Total **£15.18.0** Kit

AM/FM TUNER. Covers FM 88-108 Mc/s. AM. 16-50, 200-550, 900-2,000 m. Tuning heart (£4.13.6 inc. P.T.), and I.F. Amp.

FM-4U
 Total **£26.10.0** Kit

EQUIPMENT CABINETS



A large range, in kit form or assembled and finished, available to meet most needs. Illustrated details on request.

Prices from **£6.19.6** to **£29.8.0**

MONEY BACK GUARANTEE

Daystrom Ltd. unconditionally guarantee that each Heathkit product assembled in accordance with our easy to understand instruction manual must meet our published specifications for performance or the purchase price will be cheerfully refunded.

DAYSTROM LTD.

Dept. P.W.5, GLOUCESTER, ENGLAND

A member of the Daystrom Group, manufacturers of the WORLD'S LARGEST-SELLING ELECTRONIC KITS

Please send me FREE BRITISH CATALOGUE (Yes/No)

Full details of model(s)

NAME

ADDRESS

PW5

BENTLEY ACOUSTIC CORPORATION LTD.

Suppliers to H.M. Government. 38 CHALCOT PLACE, LONDON, N.W.1 Telephone: PRIMROSE 9090


NEAREST UNDERGROUND: CHALK FARM. ALL GOODS LISTED BELOW ARE ACTUALLY IN STOCK. ALL GOODS ARE NEW, BEST QUALITY BRANDS ONLY, AND SUBJECT TO MAKERS' FULL GUARANTEE. PLEASE NOTE THAT WE DO NOT SELL ITEMS FROM DISMANTLED EQUIPMENT NOR MANUFACTURERS' SECONDS & REJECTS, WHICH ARE OFTEN DESCRIBED AS "NEW AND TESTED", BUT HAVE A SHORT AND UNRELIABLE LIFE

0A2	4/6	6BR8	2/1	6V6G	3/0	2011	12/6	AC2PEN	EP5CC	10/-	EL32	3/6	K788	28/-	QK150/159/6	CS0	4/6	AF123	10/6	
0B2	6/-	6BR7	26/-	6V6GT	5/0	2011	12/6	DD 12/G	EL10F	10/6	EL33	6/8	K7W01	4/0	R12	5/0	CS2	4/6	AF129	10/-
0Z4C/T	4/3	6BR6	6/0	6X4	8/0	20P3	12/6	AC4PEN	E1148	1/0	EL31	3/6	K7W63	5/0	R16	20/-	CS7	4/6	AF127	9/6
1A3	2/6	6BR7	5/0	6X5	4/0	20P4	12/6		E1149	1/6	EL35	1/0	K7W63	5/0	R17	17/6	CS8	4/0	BY213	11/6
1A3	5/-	6BR6	3/0	6Y94	6/0	20P5	12/3	AC5PEN	E1150	6/0	EL37	12/3	K7Z41	4/0	R18	8/6	CS4	10/6	GB3	9/6
1C1	4/-	6C5	4/-	7A7	12/6	2106T	6/0	AC6PEN	E1151	3/0	EL42	7/6	L1152	6/0	R32	9/6	CS1	10/6	G11	10/-
1C2	6/0	6C9	8/-	7B0	10/6	2146T/12/6	6/0	ACHLD3	E1152	6/0	EL41	8/6	L1309	7/0	R41/240A	6/0	CS1	9/6	GET109	8/6
1C3	6/0	6C8	3/-	7B7	7/-	255 V5	6/0	AC7PEN	E1153	6/0	EL44	1/6	L1319	9/6	64/-	CS1	9/6	GET103	7/6	
1C5	6/0	6C9	10/6	7C5	7/6	255 V3	7/0	AC8PEN	E1154	4/0	EL44	4/0	L1319	9/6	64/-	CS1	9/6	GET104	10/-	
1C7	7/6	6C4	2/3	6Z4	6/0	2646G	7/0	AC9PEN	E1155	6/0	EL45	7/6	L1319	9/6	64/-	CS1	9/6	GET106	10/6	
1D1	4/-	6C5	4/-	7A7	12/6	2106T	6/0	AC6PEN	E1151	3/0	EL42	7/6	L1152	6/0	R32	9/6	CS1	10/6	G11	10/-
1D2	6/0	6C9	8/-	7B0	10/6	2146T/12/6	6/0	ACHLD3	E1152	6/0	EL41	8/6	L1309	7/0	R41/240A	6/0	CS1	9/6	GET109	8/6
1D3	6/0	6C8	3/-	7B7	7/-	255 V5	6/0	AC7PEN	E1153	6/0	EL44	1/6	L1319	9/6	64/-	CS1	9/6	GET103	7/6	
1D5	6/0	6C9	10/6	7C5	7/6	255 V3	7/0	AC8PEN	E1154	4/0	EL44	4/0	L1319	9/6	64/-	CS1	9/6	GET104	10/6	
1D7	7/6	6C4	2/3	6Z4	6/0	2646G	7/0	AC9PEN	E1155	6/0	EL45	7/6	L1319	9/6	64/-	CS1	9/6	GET106	10/6	
1E1	4/-	6C5	4/-	7A7	12/6	2106T	6/0	AC6PEN	E1151	3/0	EL42	7/6	L1152	6/0	R32	9/6	CS1	10/6	G11	10/-
1E2	6/0	6C9	8/-	7B0	10/6	2146T/12/6	6/0	ACHLD3	E1152	6/0	EL41	8/6	L1309	7/0	R41/240A	6/0	CS1	9/6	GET109	8/6
1E3	6/0	6C8	3/-	7B7	7/-	255 V5	6/0	AC7PEN	E1153	6/0	EL44	1/6	L1319	9/6	64/-	CS1	9/6	GET103	7/6	
1E5	6/0	6C9	10/6	7C5	7/6	255 V3	7/0	AC8PEN	E1154	4/0	EL44	4/0	L1319	9/6	64/-	CS1	9/6	GET104	10/6	
1E7	7/6	6C4	2/3	6Z4	6/0	2646G	7/0	AC9PEN	E1155	6/0	EL45	7/6	L1319	9/6	64/-	CS1	9/6	GET106	10/6	
1F1	4/-	6C5	4/-	7A7	12/6	2106T	6/0	AC6PEN	E1151	3/0	EL42	7/6	L1152	6/0	R32	9/6	CS1	10/6	G11	10/-
1F2	6/0	6C9	8/-	7B0	10/6	2146T/12/6	6/0	ACHLD3	E1152	6/0	EL41	8/6	L1309	7/0	R41/240A	6/0	CS1	9/6	GET109	8/6
1F3	6/0	6C8	3/-	7B7	7/-	255 V5	6/0	AC7PEN	E1153	6/0	EL44	1/6	L1319	9/6	64/-	CS1	9/6	GET103	7/6	
1F5	6/0	6C9	10/6	7C5	7/6	255 V3	7/0	AC8PEN	E1154	4/0	EL44	4/0	L1319	9/6	64/-	CS1	9/6	GET104	10/6	
1F7	7/6	6C4	2/3	6Z4	6/0	2646G	7/0	AC9PEN	E1155	6/0	EL45	7/6	L1319	9/6	64/-	CS1	9/6	GET106	10/6	
1G1	4/-	6C5	4/-	7A7	12/6	2106T	6/0	AC6PEN	E1151	3/0	EL42	7/6	L1152	6/0	R32	9/6	CS1	10/6	G11	10/-
1G2	6/0	6C9	8/-	7B0	10/6	2146T/12/6	6/0	ACHLD3	E1152	6/0	EL41	8/6	L1309	7/0	R41/240A	6/0	CS1	9/6	GET109	8/6
1G3	6/0	6C8	3/-	7B7	7/-	255 V5	6/0	AC7PEN	E1153	6/0	EL44	1/6	L1319	9/6	64/-	CS1	9/6	GET103	7/6	
1G5	6/0	6C9	10/6	7C5	7/6	255 V3	7/0	AC8PEN	E1154	4/0	EL44	4/0	L1319	9/6	64/-	CS1	9/6	GET104	10/6	
1G7	7/6	6C4	2/3	6Z4	6/0	2646G	7/0	AC9PEN	E1155	6/0	EL45	7/6	L1319	9/6	64/-	CS1	9/6	GET106	10/6	
1H1	4/-	6C5	4/-	7A7	12/6	2106T	6/0	AC6PEN	E1151	3/0	EL42	7/6	L1152	6/0	R32	9/6	CS1	10/6	G11	10/-
1H2	6/0	6C9	8/-	7B0	10/6	2146T/12/6	6/0	ACHLD3	E1152	6/0	EL41	8/6	L1309	7/0	R41/240A	6/0	CS1	9/6	GET109	8/6
1H3	6/0	6C8	3/-	7B7	7/-	255 V5	6/0	AC7PEN	E1153	6/0	EL44	1/6	L1319	9/6	64/-	CS1	9/6	GET103	7/6	
1H5	6/0	6C9	10/6	7C5	7/6	255 V3	7/0	AC8PEN	E1154	4/0	EL44	4/0	L1319	9/6	64/-	CS1	9/6	GET104	10/6	
1H7	7/6	6C4	2/3	6Z4	6/0	2646G	7/0	AC9PEN	E1155	6/0	EL45	7/6	L1319	9/6	64/-	CS1	9/6	GET106	10/6	
1I1	4/-	6C5	4/-	7A7	12/6	2106T	6/0	AC6PEN	E1151	3/0	EL42	7/6	L1152	6/0	R32	9/6	CS1	10/6	G11	10/-
1I2	6/0	6C9	8/-	7B0	10/6	2146T/12/6	6/0	ACHLD3	E1152	6/0	EL41	8/6	L1309	7/0	R41/240A	6/0	CS1	9/6	GET109	8/6
1I3	6/0	6C8	3/-	7B7	7/-	255 V5	6/0	AC7PEN	E1153	6/0	EL44	1/6	L1319	9/6	64/-	CS1	9/6	GET103	7/6	
1I5	6/0	6C9	10/6	7C5	7/6	255 V3	7/0	AC8PEN	E1154	4/0	EL44	4/0	L1319	9/6	64/-	CS1	9/6	GET104	10/6	
1I7	7/6	6C4	2/3	6Z4	6/0	2646G	7/0	AC9PEN	E1155	6/0	EL45	7/6	L1319	9/6	64/-	CS1	9/6	GET106	10/6	
1J1	4/-	6C5	4/-	7A7	12/6	2106T	6/0	AC6PEN	E1151	3/0	EL42	7/6	L1152	6/0	R32	9/6	CS1	10/6	G11	10/-
1J2	6/0	6C9	8/-	7B0	10/6	2146T/12/6	6/0	ACHLD3	E1152	6/0	EL41	8/6	L1309	7/0	R41/240A	6/0	CS1	9/6	GET109	8/6
1J3	6/0	6C8	3/-	7B7	7/-	255 V5	6/0	AC7PEN	E1153	6/0	EL44	1/6	L1319	9/6	64/-	CS1	9/6	GET103	7/6	
1J5	6/0	6C9	10/6	7C5	7/6	255 V3	7/0	AC8PEN	E1154	4/0	EL44	4/0	L1319	9/6	64/-	CS1	9/6	GET104	10/6	
1J7	7/6	6C4	2/3	6Z4	6/0	2646G	7/0	AC9PEN	E1155	6/0	EL45	7/6	L1319	9/6	64/-	CS1	9/6	GET106	10/6	
1K1	4/-	6C5	4/-	7A7	12/6	2106T	6/0	AC6PEN	E1151	3/0	EL42	7/6	L1152	6/0	R32	9/6	CS1	10/6	G11	10/-
1K2	6/0	6C9	8/-	7B0	10/6	2146T/12/6	6/0	ACHLD3	E1152	6/0	EL41	8/6	L1309	7/0	R41/240A	6/0	CS1	9/6	GET109	8/6
1K3	6/0	6C8	3/-	7B7	7/-	255 V5	6/0	AC7PEN	E1153	6/0	EL44	1/6	L1319	9/6	64/-	CS1	9/6	GET103	7/6	
1K5	6/0	6C9	10/6	7C5	7/6	255 V3	7/0	AC8PEN	E1154	4/0	EL44	4/0	L1319	9/6	64/-	CS1	9/6	GET104	10/6	
1K7	7/6	6C4	2/3	6Z4	6/0	2646G	7/0	AC9PEN	E1155	6/0	EL45	7/6	L1319	9/6	64/-	CS1	9/6	GET106	10/6	
1L1	4/-	6C5	4/-	7A7	12/6	2106T	6/0	AC6PEN	E1151	3/0	EL42	7/6	L1152	6/0	R32	9/6	CS1	10/6	G11	10/-
1L2	6/0	6C9	8/-	7B0	10/6	2146T/12/6	6/0	ACHLD3	E1152	6/0	EL41	8/6	L1309	7/0	R41/240A	6/0	CS1	9/6	GET109	8/6
1L3	6/0	6C8	3/-	7B7	7/-	255 V5	6/0	AC7PEN	E1153	6/0	EL44	1/6	L1319	9/6	64/-	CS1	9/6	GET103	7/6	
1L5	6/0	6C9	10/6	7C5	7/6	255 V3	7/0	AC8PEN	E1154	4/0	EL44	4/0	L1319	9/6	64/-	CS1	9/6	GET104	10/6	
1L7	7/6	6C4	2/3	6Z4	6/0	2646G	7/0	AC9PEN	E1155	6/0	EL45	7/6	L1319	9/6	64/-	CS1	9/6	GET106	10/6	
1M1	4/-	6C5	4/-	7A7	12/6	2106T	6/0	AC6PEN	E1151	3/0	EL42	7/6	L1152	6/0	R32	9/6	CS1	10/6	G11	10/-
1M2	6/0	6C9	8/-	7B0	10/6	2146T/12/6	6/0	ACHLD3	E1152	6/0	EL41	8/6	L1309	7/0	R41/240A	6/0	CS1	9/6	GET109	8/6
1M3	6/0	6C8	3/-	7B7	7/-	255 V5	6/0	AC7PEN	E1153	6/0	EL44	1/6	L1319	9/6	64/-	CS1	9/6	GET103	7/6	
1M5	6/0	6C9	10/6	7C5	7/6	255 V3	7/0	AC8PEN	E1154	4/0	EL44	4/0	L1319	9/6	64/-	CS1	9/6	GET104	10/6	
1M7	7/6	6C4	2/3	6Z4	6/0	2646G	7/0	AC9PEN	E1155	6/0	EL45	7/6	L1319	9/6	64/-	CS1	9/6	GET106	10/6	
1N1	4/-	6C5	4/-	7A7	12/6	2106T	6/0	AC6PEN	E1151	3/0	EL42	7/6	L1152	6/0	R32	9/6	CS1	10/6	G11	10/-
1N2	6/0	6C9	8/-	7B0	10/6	2146T/12/6	6/0	ACHLD3	E1152	6/0	EL41	8/6	L1309	7/0	R41/240A	6/0	CS1	9/6	GET109	8/6
1N3	6/0	6C8	3/-	7B7	7/-	255 V5	6/0	AC7PEN	E1153	6/0	EL44	1/6	L1319	9/6	64/-	CS1	9/6	GET103	7/6	
1N5	6/0	6C9	10/6	7C5	7/6	255 V3	7/0	AC8PEN	E1154	4/0	EL44	4/0	L1319	9/6	64/-	CS1	9/6	GET104	10/6	
1N7	7/6	6C4	2/3	6Z4	6/0	2646G	7/0	AC9PEN	E1155	6/0	EL45	7/6	L1319	9/6	64/-	CS1	9/6	GET106	10/6	
1O1	4/-	6C5	4/-	7A7	12/6	2106T	6/0	AC6PEN	E1151	3/0	EL42	7/6	L1152	6/0	R32	9/6	CS1	10/6	G11	10/-
1O2	6/0	6C9	8/-	7B0	10/6	2146T/12/6	6/0	ACHLD3	E1152	6/0	EL41	8/6	L1309	7/0	R41/240A	6/0	CS1	9/6	GET109	8/6
1O3	6/0	6C8	3/-	7B7	7/-	255 V5	6/0	AC7PEN	E1153	6/0	EL44	1/6	L1319	9/6						

STERN-CLYNE

Great Britain's Greatest Electronic Hobbies Organisation

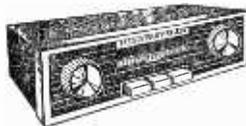NEW LOW PRICES — NOW YOU CAN AFFORD A CAR RADIO



THE 'HIGHWAYMAN'
OUR QUALITY CARRADIO
TO BUILD YOURSELF AT
A NEW LOW PRICE

Look at these features:
★ Attractive styling. ★ Push-pull output. ★ Three latest types EBFB3 and ECHB3. ★ No Buzz, high output and sensitivity. ★ Printed circuit (latest type). 7 x 4in. high flux p.m. speaker and baffle. ★ Medium and Long Waves. ★ Push button for finkertip control. ★ Extremely low battery consumption (less than 1 amp). ★ Easy to fit any make car (Positive earth only). ★ 12-volt operation. ★ Compact size, measures only 7 x 7 x 2in. deep. ★ Easy assembly, supplied with dial and drive already mounted.

Special inclusive price of ONLY **£7.19.6** Plus 5/- P. & P.

All parts available separately. Individually priced parts list and comprehensive instruction booklet 2/6 post free. (Deducted from cost if complete parcel purchased later.)

THE "TRAVLER" MkII
Introducing our new ready-built transistorised car radio for ONLY



9½ Gns. P. & P. 5/-
Including 7 x 4" speaker fitted to baffle, fixing brackets, filter unit, all nuts and bolts with fitting instructions

H.P. Terms: Dep. **£2.19.6** and 7 monthly payments of £1.2.6. (Plus 5/- P. & P.)

Star Features ★ Handsomely Styled. ★ Mullard Valves and Transistors. ★ Push Buttons. ★ 11 watts Output. ★ Long and Medium Wavebands. ★ Quality Speaker (E.M.I.). ★ Easily Fitted. ★ Radio Luxembourg (and many other foreign stations) 12 volt Positive Earth Only (applies to 99.8% of the cars on the road). ★ Dimensions 7 x 2 x 7" depth.

Optional extras, 3 section chromium plated weatherproof telescopic aerials type 1 17/44", 19/6, type 2, 27/43", 29/6, both plus P. & P. 2/6 if purchased separately.

THE WORLD AT YOUR FINGERTIPS!!

THE HE-30 4-BAND COMMUNICATION RECEIVER



One of the finest general coverage bandspread Receivers available at this price. Covering 350Kc/s—1800Kc/s. 4.8Mc/s—14.5Mc/s, 1.6Mc/s—4.8Mc/s. 10.5Mc/s—30Mc/s. Illuminated slide rule dial, calibrated every 5Kc/s on 80 and 40 metres. Edgewise S-meter, 0-100 logging scale, coverage from 0.55—30 Mc/s, 8 valve plus Rectifier superhet circuits. RF Stage with B.P.O. control Q-multiplier. Controls: Function Switch, Audio Gain, Selectivity (Q-multiplier) Frequency (BFO), Band Selector, IF Gain, Trimmer, AVC-MVC Switch, Ant Switch, Main Tuning, Bandsread Tuning and Head-Phone Jack. Selectivity—60dB at 10Kc/s, 0.8Kc/s at 6dB (with Q-Multiplier) IF—65Kc/s. External P.M. speaker reqd. 4 or 8 ohms impedance, Output 1.5 watts, 8 modern Miniature BTG Base Valves and 5Y3 Rectifier. Size 15 x 10 x 7in. Grey crackle finish. 220/240 volt A.C. mains, 50-60 cycle operation. Full instructions and circuit diagram supplied. Send S.A.E. for leaflet.

PRICE **40 Gns.** Carriage Paid.


THE HE-40 4-BAND COMMUNICATION RECEIVER



Completely built and ready to go. High sensitivity Superhet receiver covering 550Kc/s—1,300 Kc/s, 1.6 Mc/s—4.4 Mc/s, 4 Mc/s—11 Mc/s, 11 Mc/s—30 Mc/s. Electrical Bandsread tuning. Slide rule type tuning dial. Internal ferrite rod aerial for medium waveband reception and 1 5/8in. 10 section chromium plated telescopic whip aerial for the short wave bands. Sockets for optional outdoor aerial. Internal high flux monitor loudspeaker. Latest modern miniature BTG base valves. Head-Phone socket (may also be used for external loudspeaker). ANL, BFO, built-in "S" meter, 220/240 volt A.C. mains, 50-60 cycle operation. Handsomely styled cabinet with grey crackle finish and handsome front panel, with chrome and satin chrome fittings. Measures 13 1/2in. x 8 1/2in. x 5 1/2in. (high) and weighs only 11 1/2 lbs. A comprehensive instruction manual is supplied. An ideal receiver for the radio amateur and short wave listeners of all ages. Send S.A.E. for leaflet.

PRICE **£24.15.0** Carriage Paid.

THE NEW HE-80 COMMUNICATION RECEIVER

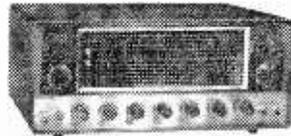


The HE-80 has outstanding sensitivity 0-100 logging scale for instant re-set built-in "S" meter special recording Jack, remote Control Socket allowing simultaneous control with transmitter, 100Kc crystal oscillator circuit providing accurate harmonic signals of either 4 or 8 ohms impedance. Two headphone sockets, one high, one low.

TECHNICAL SPECIFICATIONS.
Frequencies Coverage: Band 1 540—1665Kc; Band 2 1.6—4.8Kc; Band 3 4.8—14.5Mc; Band 4 10.5—30Mc; Band 5 14—146 Mc/s. Band Spread (Ham Band directly read): 80 Metre Band; 40 Metre Band; 20 Metre Band; 15 Metre Band; 10 Metre Band. Sensitivity: 1 micro-volt for 10dB signal to noise ratio. Selectivity: Normal 10Kc at —75dB, 1.25Kc at —6dB. With Q-Multi: variable to 700 e.p.s. at 6dB. Operation: AM, SSB, CW and FM. AM diode detector. SSB/CW product detector (BFO). FM gated band detector. Power Source: 240 volts 50/60 Cycles A.C. Power Consumption: 60 watts. Audio Output: 1.5 watts, 8 or 500 ohms impedance. Auxiliary Circuit: Electrical Bandsread, Q-Multiplier, ANL, AVC-MVC, BFO, 100Kc crystal calibrator. Valve Line-up: 4—6AQ5, 6BE6, 3—6BA6, 2—6BE6, 6AL5, 6AQ5, OA2, 6CA4. Dimensions: 17in. wide, 6 1/2in. high, 10in. deep.

PRICE **59 Gns.** Carriage Paid.

"STARFLITE TRANSMITTER"

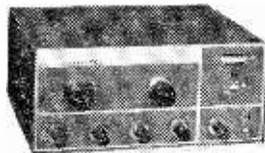

Designed to meet the needs of most amateurs the Starflite has single-knob band-switching, front panel switch to select any of five crystal positions with provision for an external VFO. Controlled carrier modulator permits almost 100% of the CW input to be used on AM peaks. Grid-block keying provides chirp-free operation. A full wave silicon diode power supply effects extremely low output ripple for cleaner CW transmission, electron-coupled Pierce Oscillator, capacitance bridge neutralization of the final and a three-stage low-pass filter. An illuminated edgewise D'Arsonval panel meter. Pi-network output provides the correct impedance match between the plate circuit and any 50-72 ohm co-axial feeder. Easy to follow point-to-point instructions supplied with each set of components. When constructed the Unit is housed in a heavy gauge steel Cabinet finished in grey crackle.

SPECIFICATIONS: Power Input—90 watts peak; Operation: C.W., AM Phone—crystal or VFO Control; Band coverage: 80-10 metres; Coupling: Pi-network; Valve Line-up: 6146, (2) 6CL6, 12AX7, 6DE7 Low Pass Filter. Size 13 1/2in. wide x 12in. deep (inc. knobs) x 6 1/2in. high (inc. rubber feet). Weight 26 lbs. Power Requirements, 220/240 v. 50-60 C/Ps, 225 watts.

MAY BE BUILT FOR **35 Gns.** Carriage & Insurance 15/-

SEE FOLLOWING PAGES FOR ADDRESSES AND OTHER ITEMS

STERN-CLYNE

Great Britain's Greatest Electronic Hobbies Organisation

MULLARD 2-VALVE PRE-AMPLIFIER TONE CONTROL UNIT

Employing two EF86 valves and designed to operate with the Mullard AMPLIFIERS but also perfectly suitable for other makes with input up to 250 mV.

★ Equalisation for the latest R.I.A.A. characteristics. ★ Inputs for Crystal Pickups and variable reluctance magnetic types. ★ Input (a) Direct from High Imp. Tape Head. (b) From a Tape Amplifier or Pre-Amplifier ★ Sensitive Microphone Channel. ★ Wide range BASS and TREBLE controls.

KIT OF PARTS £6.60 AND TESTED £9.10.0 (Carr. & Ins. 5/-)

Instruction book and detailed price list (free with kit) available separately at 2/- Post Free.



MULLARD 3-VALVE PRE-AMPLIFIER TONE CONTROL UNIT

Designed mainly for Mullard Range of Amplifiers, also suitable for any Amplifiers requiring input up to 250mV. Incorporates 5 input Channels, including for Tape and Magnetic Pickups. Separate Bass and Treble controls. High pass filter 20 to 160 c/s. low pass filter 5-9 Kc/s. Totally enclosed in case Size 11 1/2" x 4 1/2" x 4 1/2".

KIT OF PARTS £10.00 (Carr. & Ins. 5/-) AND TESTED £13.13.0

Instruction book and detailed price list (free with kit) available separately at 3/6 Post Free.



MULLARD "5-10" MAIN AMPLIFIER

For use with MULLARD 2 or 3 valve pre-amplifiers with which an undistorted power output of up to 10 watts is obtained. SPECIFIED COMPONENTS and MULLARD VALVES including PARTRIDGE MAINS TRANSFORMER and choice of PARMEKO or PARTRIDGE Output Transformer


COMPLETE KIT £10.00 (Parmeko Output Trans.)

ASSEMBLED AND TESTED £13.10.0

(Carr. & Ins. 6/6).

ABOVE incorporating PARTRIDGE OUTPUT TRANS. £1.6.0 extra.

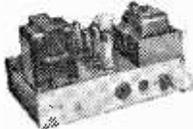Instruction book and detailed price list (free with kit) available separately at 2/- Post Free.



COMBINED PRICE REDUCTION

MULLARD 5-10 Main Amplifier and 2 valve Pre-Amp. Kit £16.15.0. C. & I. 3/6. Built and tested, £21.10.0. C. & I. 10/-

MULLARD 5-10 Main Amplifier and 3 valve Pre-Amp. Kit £19.10.0. C. & I. 8/6. Built and tested, £25.10.0. C. & I. 10/- With Partridge Transformer £1.6.0 extra.

THE MULLARD 5-10RC AMPLIFIER

The popular complete "5-10" incorporating Passive Control Unit providing up to 10 watts high quality reproduction with input of 800 mV. Specified components and new MULLARD VALVES. Includes PARTRIDGE MAINS TRANSFORMERS and choice of PARMEKO or PARTRIDGE Output Transformers. Surplus Power available for Tuner.

COMPLETE KIT £12.0.0

ASSEMBLED AND TESTED £16.0.0 (Carr. & Ins. 7/6).

With PARTRIDGE OUTPUT TRANS. £1.6.0 extra.

Instruction book and detailed price list (free with kit) available separately at 2/- Post Free.



THE MULLARD 3-3RC A HIGH QUALITY AMPLIFIER DEVELOPED FROM THE VERY POPULAR 3-WATT MULLARD "3-3" DESIGN.

KIT OF PARTS £8.8.0

ASSEMBLED AND TESTED £11.10.0 (Carr. & Ins. 6/6).

Complete to the MULLARD specification including PARMEKO OUTPUT TRANSFORMER. Switched inputs for 78 and




L.P. records plus a Radio position. Extra power to drive a Radio Tuning Unit is also available. Please state L.S. impedance.

Instruction book and detailed price list (free with kit) available separately at 2/- Post Free.

THE "MONO-GRAM"

A small Amplifier of genuine high quality performance. Incorporates MULLARD ECL86 Valve, separate BASS and TREBLE controls. PARTRIDGE output Transformer producing up to 3 watts undistorted output. (Carr. & Ins. 3/6).

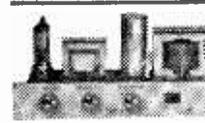Kit of Parts £4.10.0 Assembled and Tested £6.0.0



Instruction book and detailed price list (free with kit) available separately at 2/6 Post Free.

CHASSIS BARGAIN



A 6 valve Superhet Radiogram Chassis of outstanding quality covering MW 200-550 Metres. LW 1200-2000 Metres. VHF 87-100 Mc/s.

Incorporating internal Ferrite Rod Aerial and the famous Gortler Tuning Heart for VHF Pickup input suitable for most modern Record Players. Power output 10 watts, valve line up E200, EABC80, EF86, ECH81, EL84, ECC83. Volume ON/OFF and Tone Control, attractive black Tuning Dial size 15" x 6" with gold lettering and contrasting cream and gold knobs. A.C. 200/250 v. Size 13 x 7 1/2 x 6 1/2". P. & P. 5/-.

PRICE 16 Gns. Or £2.9.0 deposit (plus P. & P.) and 4 monthly payments of 12/6.

MODEL CR3/S TAPE RECORDER



MODEL CR3/S incorporates HF/TR3 Mk. II Tape Amplifier (described below) and the Collaro "Studio" Twin Track 3-speed Deck operating at 1 1/2 in., 3 in., and 7 1/2 in. speeds. Complete with microphone and 1,200ft. tape.

KIT OF PARTS £33.8.0

ASSEMBLED AND TESTED £43.0.0 (Carr. & Ins. 15/- extra)

STEREO TAPE PRE-AMPLIFIER

MODEL STP-1. For use with current TRUVOX, BRENNEL or COLLARO "STUDIO" 1 and 1 track Stereo Decks. Incorporates Ferro-cube Oscillator, 4-speed Equalisation Signal Level Meter and separate Gain Control. Includes separate Power Unit. **KIT OF PARTS £22.0.0** (Carr. & Ins. 9/6) **ASSEMBLED £28.0.0**

Instruction book and detailed price list (free with kit) available separately at 5/- Post Free.



TAPE PRE-AMPLIFIER MULLARD Type "C"

Suitable for most 1 track, Mono Tape Decks. Incorporates Ferro-cube Push-Pull Oscillator, Treble Inductor and 3-sp. Equalisation. Includes separate Power Unit. **KIT OF PARTS £14.0.0** (Carr. & Ins. 7/6). **ASSEMBLED £19.10.0**

Instruction book and detailed price list (free with kit) available separately at 3/6 Post Free.



MULLARD TAPE AMPLIFIER

MODEL HF/TR3/MK.II Based on Mullard's Type 'A' design and suitable for most 1 track Mono Tape Decks. Incorporates Ferro-cube Treble Inductor, Gison Output Transformer, and 3-speed Equalisation. Includes separate Power Unit, using PARTRIDGE Mains Transformer. **KIT OF PARTS £13.13.0** (Carr. & Ins. 7/6). **ASSEMBLED £19.0.0**

Instruction book and detailed price list (free with kit) available separately at 3/- Post Free.



COMBINATION TAPE UNITS

All our Tape Units can be supplied specially matched to any Tape Deck such as Collaro, Brennel Mk.5 Series II, also the Warrite. Specimen prices as below.

Kit Assembled	Kit Assembled
STP-1 Pre-amp with Collaro Studio Tape Deck.....	£26. 0.0 £42. 0.0
Assembled with L.ack switch fitted, £44.2.0.	
STP-1 with Brennel Mk. 5 Series II with Track switch fitted.....	£28. 0.0
STP-1 with Brennel Mk.5 Series II, 1 Track Deck.....	£24.15.0
Type "C" Pre-amp with Collaro Studio Tape Deck.....	£24.10.0 £30. 0.0
Assembled with deck wired and matched, £32.2.0.	
Type "C" Pre-amp with Brennel Mk.5 Series II Deck.....	£46.11.0 £53. 1.0
Assembled with deck wired and matched, £55.8.0.	
HF/TR3 with Collaro Studio Tape Deck.....	£24. 3.0 £29.10.0
Assembled with deck wired and matched, £31.12.0.	
HF/TR3 with Brennel Mk.5 Series II Deck.....	£49. 4.0 £51.11.0
Assembled with deck wired and matched, £53.13.0.	

Carr. & Ins. 15/- on above units. Send S.A.E. for comprehensive price list.

SEND FOR CURRENT PRICE LIST OF ALL LEADING RECORDING TAPES AND ACCESSORIES

SEE PRECEDING PAGE FOR OTHER STERN-CLYNE PRODUCTS

STERN-CLYNE


Great Britain's Greatest Electronic Hobbies Organisation

THE TUDOR STEREO HI-FI SYSTEM



FOR ONLY **48 gns.**
Plus 15/- Pkg. & Carr.

Comprising a Self Powered AM/FM Tuner, Stereo Pre-amplifier, 12 watt per channel Stereo Power Amplifier. The Tuner and Pre-amplifier are housed in matching black crackle finish metal cabinets for shelf mounting, with silver metal dial and matching knobs. Specifications: Tuner—Outstanding quality providing full VHF/FM long and medium waveband coverage (frequency range FM 87.5-108.5 Mc/s, AM/MW 522-1630 Kc/s, LW 145-270 Kc/s, 100mV output mains supply 105/240 A.C. Valve line-up, ECC85, ECH81, EBF89, EB91, EM84; ECC83. Multiplex outlet provided. Pre-amplifier—Designed for use with the Tudor Stereo Power Amplifier with inputs for most types of Pickups, direct play from Tape-Heads and ample sensitivity for either Crystal or Moving Coil Microphone. Distortion 0.1%, tape outputs 100mV from 90K, ohm source inputs—Microphone, 5 mV, Tape 5.3 mV, R.A., 4.3 mV flat 250 mV. Tuner 2—EF86, 4—ECC83. Power Amplifier—14 watts per channel, sensitivity 1 volt r.m.s. for 14 watts output, frequency response $\pm 0.5dB$ 20 c/s., -20 Kc/s. Speaker Impedance 4, 8 or 16 ohms, surplus power available for Tape Pre-Amp, mains supply 105/240 v. A.C. Valve line-up, 2—ECC83, 4—EL84, 1—6X4.

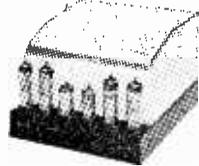

100 mV. Valve line-up: 2—ECC83, 4—EL84, 1—6X4.

DOUBLE FEATURE PRE-AMPLIFIER AND JLI0 POWER AMPLIFIER

A new conception in the field of audio engineering by Stern-Clyne development engineers. The most up-to-date circuitry is used in the Double Feature Pre-amplifier. It has matched inputs for microphone, crystal or magnetic pick-ups and radio tuner and in addition offers full facilities for tape recording and high fidelity replay. This unique feature means that should you wish to include tape in your hi-fi system at a later date all that is required is a suitable tape deck.

★ J.L.I0 POWER AMPLIFIER



Incorporates the latest triode-pentode ECL36 valves in push pull. PARTIDGE ultra linear output transformer, PARTIDGE mains transformer and smoothing choke. 10 watts power output, surplus power available for tuner. Output impedance 3—7.5—15 ohms.

KIT OF PARTS **11 Gns.** C. & I. 7/6.
READY BUILT **14 Gns.**

★ DOUBLE FEATURE PRE-AMPLIFIER



Inputs for microphone, crystal or magnetic pick-ups, tuner unit, Push-button switching for 3 tape speeds equalised. Tape erase Bias Oscillator circuit incorporating ferro-cube transformer. Function switch, separate base, treble and volume controls, level control and latest EM87 magic eye level indicator. The pre-amplifier is totally enclosed in a silver hammer finish steel case, and an attractive perspex front panel completes the presentation.


enclosed in a silver hammer finish steel case, and an attractive perspex front panel completes the presentation.

KIT OF PARTS **£17.0.0** READY BUILT **£21.0.0** C. & I. 5/-.
PRICES: If both above units purchased together: C. & I.
KIT OF PARTS **£27.10.0** READY BUILT **32 Gns.** 10/-

SEND STAMP FOR COPY OF OUR INTERESTING LITTLE BOOKLET "What is High Fidelity?"

MARTIN Fully Transistorised AUDIOKITS

These ingeniously designed sub-assembled kits enable you to build a transistorised Hi-Fi system by simply linking together your choice of units. No technical knowledge or special tools are needed to build with complete success. All units are supplied on printed circuit boards ready to mount and connect. Latest type transistors used in conjunction with the specially developed circuits give you superb reproduction. For battery operation or can be used on A.C. mains with Martin power supply unit.

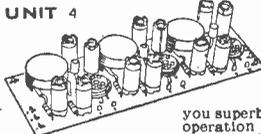

Following Audiokits available:—
Unit 1.—5-Stage Matching Input Selector Unit. 47/6.
Unit 2.—Pre-Amplifier with Master Volume Control. 37/6.
Unit 3.—3-Channel Mixer. 79/6. (Plus in matching adaptors for above, 3/6 each).
Unit 4.—Combined Pre-Amplifier and Tone Control Unit. 62/6
Unit 5.—10 watt Main Amp. (3 ohm o/p imp. only at present). 55/12.6.
Unit 6.—Power Supply Unit. 22/12.6.
P. & P. extra on above items. Full range of attractive perspex enclosures available. Send S.A.E. for fully descriptive literature.

THE NEW CHASSIS PUNCH SET

Five of the most used Hole Punches made of the finest hardened steel will save hours of tedious hand labour suitable for aluminium, Sheet Metal, Plastic, etc. Punch Sizes 1-1/4", 1-1/2", complete with Tommy Bar, Tapered Reamer, Price **49/6** P.&P. 3/6



HI-FI STEREO HEADPHONES

For the connoisseur who requires perfection. Each Earphone consists of a 2" Dynamic Loudspeaker with a full frequency range, fitted with foam rubber Ear Pads for added comfort to keep out noise and to maintain an excellent bass response. The resistance junction box with change-over switch provides simple transfer from Phones to Speaker. Specifications: Frequency Range—25-15,000 c.p.s. Imp. Impedance—16 ohms. Power rating—4 watt. Weight—13 ozs.

PRICE **5 Gns.** P. & P. 2/6.
(Junction box 15/- ex.)



MONAURAL STETHOSCOPE HEADSETS

Suitable for Radio, Tape Recorders, or monitoring tape recordings, magnetic low impedance or Crystal High impedance. Complete with 4ft. of lead and miniature Jack Plug. PRICE **10/6** P. & P. 1/6

AGOS MONAURAL STETHOSCOPE HEADSETS

Suitable for Tape Recorders, or monitoring tape recorders, 100 ohm impedance magnetic. Complete with 12/6 P. & P. 1/6 lead. (Originally 21/-). OUR PRICE

- | | | | |
|-----------------|------------------------------------|-------------------|--------------------|
| WEST END: | 18 Tottenham Court Road, W.1. | MUSEum 5929/0095 | Half-day Sat |
| (Premier Radio) | 23 Tottenham Court Road, W.1. | MUSEum 3451/2 | Half-day Thurs |
| (Premier Radio) | 309 Edgware Road, W.2. | PADddington 6963 | Half-day Thurs |
| CITY: | 109 Fleet Street, E.C.4. | FLEet St. 5812/3 | Half-day Sat |
| NORTH LONDON: | 162 Holloway Road, N.7. | NOrrh 8161/5 | Half-day Thurs |
| SOUTH LONDON: | 9 Camberwell Church Street, S.E.5. | RODney 2875 | Half-day Thurs |
| CROYDON: | 12 Suffolk House, George Street. | MUNicipal 3250 | Half-day Wed |
| BRISTOL: | 26 Merchant Street, Bristol 1. | Bristol 20261 | Half-day Wed |
| MANCHESTER: | 10 Withy Grove, Manchester 4. | BLAck Friars 5379 | Open 6 days a week |
- Mail Orders and enquiries to Dept. P.W. 162 Holloway Rd, London, N.7. **NORTH 8161/5**



CLEAR PLASTIC PANEL METERS

First grade quality. Moving coil panel meters. available in 1 1/2" sq. front. S.A.E. for illustrated leaflet. Discounts for quantity. Available as follows. Type MR. 38P.

100µA 32/6 1A. DC 22/6
200µA 29/6 5A. DC 22/6
500µA 27/6 3V. DC 22/6
50-0-50µA 25/- 10V. DC 22/6
1mA 29/6 50V. DC 22/6
5mA 22/6 100V. DC 22/6
10mA 22/6 150V. DC 22/6
50mA 22/6 300V. DC 22/6
100mA 22/6 500V. DC 22/6
150mA 22/6 750V. DC 22/6
200mA 22/6 15V. AC 22/6
300mA 22/6 50V. AC 22/6
500mA 22/6 150V. AC 22/6
750mA 22/6 300V. AC 22/6
1000mA 22/6 500V. AC 22/6

Type MR. 39 2 1/2" sq. front. 50µA 57/6 1mA 32/6
100µA 47/6 10mA 32/6
500µA 37/6 100mA 32/6
50-0-50µA 37/6 1A. DC 32/6
100-0-100µA 42/6 300V. AC 32/6
300V. AC 32/6

Type MR. 65P. 3 1/4" sq. front. 50µA 59/6 1mA 35/-
100µA 49/6 10mA 35/-
500µA 39/6 100mA 35/-
50-0-50µA 59/6 1A. DC 35/-
100-0-100µA 49/6 300V. AC 35/-
POST EXTRA 300V. AC 35/-

Type MR. 65P. 3 1/4" sq. front. 50µA 59/6 1mA 35/-
100µA 49/6 10mA 35/-
500µA 39/6 100mA 35/-
50-0-50µA 59/6 1A. DC 35/-
100-0-100µA 49/6 300V. AC 35/-
POST EXTRA 300V. AC 35/-

Type MR. 65P. 3 1/4" sq. front. 50µA 59/6 1mA 35/-
100µA 49/6 10mA 35/-
500µA 39/6 100mA 35/-
50-0-50µA 59/6 1A. DC 35/-
100-0-100µA 49/6 300V. AC 35/-
POST EXTRA 300V. AC 35/-

Type MR. 65P. 3 1/4" sq. front. 50µA 59/6 1mA 35/-
100µA 49/6 10mA 35/-
500µA 39/6 100mA 35/-
50-0-50µA 59/6 1A. DC 35/-
100-0-100µA 49/6 300V. AC 35/-
POST EXTRA 300V. AC 35/-

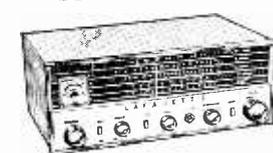HE-40 DE LUXE 4-BAND COMMUNICATION RECEIVER



Frequency coverage 550Kc/s to 30 Mc/s continuous. Operation 220/240 volt. AC/DC. The perfect receiver for short wave listening. Special features include: Slide tuning dial—electrical band-spread—0-100 logging scale—improved selectivity—built in "S" meter—A.V.C.—Noise limiter—B.F.O.—Phone jack built in 5in. speaker—tone control—standby switch—supplied with three aeriels, ferrite loop for broadcast band, adjustable 58in. whip for short wave and wire aerial. Smartly styled durable metal cabinet. Supplied brand new and guaranteed with manual. £24.15.9 carriage paid. S.A.E. for full details. Part exchanges welcome.

control—standby switch—supplied with three aeriels, ferrite loop for broadcast band, adjustable 58in. whip for short wave and wire aerial. Smartly styled durable metal cabinet. Supplied brand new and guaranteed with manual. £24.15.9 carriage paid. S.A.E. for full details. Part exchanges welcome.

MODEL ITI-2 MULTITESTER 20,000 O.P.V.

20,000 o.p.v. D.C. 10,000 o.p.v. A.C. specifications:
D.C. V: 0-5-25-250-500-2500 V.
A.C. V: 0-10-50-500-1000 V.
Current: 0-50µA-25mA-250mA
Resistance: 0-60K-∞M Ω.
Capacity: 0.01-0.3µF (at AC 10 V)
Decibel: -20dB +22dB
Output range: 0-10-50-500-1000V
Battery: 1.5 V U12
Size: 3 1/2 x 4 1/2 in.
Supplied complete with batteries, leads instructions, 82/6. Post 2/6.



MARCONI TF144G 4 STANDARD SIGNAL GENERATORS

First release of this late mark. 85Kc/s to 25Mc/s ±1%. Output variable from 1µV to 1 volt. Internal sine wave modulation 100c/s up to 75%, depth. Operation 200/250 volt A.C. Offered in really excellent condition, like new fully tested and guaranteed. £25. Carr. 30/-.

TE-20 RF SIGNAL GENERATOR

Accurate wide range signal generator covering 120Kc/s—260Mc/s on 8 bands. Directly calibrated. Variable RF attenuator. Operation 200/240 V. A.C. similar in appearance to TE-46 CR Bridge. Brand new with instructions. £12. Carr. 5/-. S.A.E. for details.

COSSOR DOUBLE-BEAM OSCILLOSCOPE 1035

4in. tube. Calibrated Y1 amplifier from 50mV to 50V. Bandwidth 10Mc/s. Calibrated Y2 amplifier from 5V. to 500V. with bandwidth up to 100Kc/s. Directly calibrated X shift providing time measurements from 15 microseconds to 150 milliseconds. Supplied in guaranteed perfect condition. £27.10.0 each. Carr. 30/-. Spare Tubes. TYPE 80D. Brand New. 59/8 each. P. & P. 4/6.


ERSKINE TYPE 13 DOUBLE BEAM OSCILLOSCOPE

Time base 2c/s—750Kc/s. Calibrators at 100Kc/s and 1Mc/s. Separate Y1 and Y2 amplifiers up to 5.5Mc/s. Operation 110/230 volt A.C. Supplied in perfect working order. £27.10.0. Carr. 20/-.

CR.100 COMMUNICATION RCVRs.

60Kc/s to 30Mc/s on 6 bands. 200/250 volt A.C. operation. Supplied in perfect working condition. £21 each. Carr. 30/-.

FIELD TELEPHONES

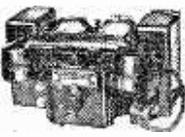

Type "L". Two line connection, generator bell ringing. Complete telephone intercom. Supplied in excellent condition, fully tested and complete with batteries. Only 49/6 per pair. Carr. 5/-. Type "F". As above but moulded bakelite case (as illustrated). Supplied complete with wooden transit case for field use. £4.19.6 per pair. Carr. 5/-.

MICROAMMETERS

0-500 microamp. 2 1/2in. circular flush panel mounting. Dials engraved 0-15, 0-600 volts. Brand new, boxed, 15/-, P. & P. 1/6.

MINE DETECTOR NO. 4A

Will detect all types of metals. Fully portable. Complete with instructions. 39/6 each. Carr. 10/-. Battery 8/6 extra.

GEARED SLIDER RHEOSTAT

1.2 ohms 12 amp. 15/6. P.P. 3/6.

FIELD STRENGTH METERS

Fitted with 200 microamp meter. Supplied with telescopic aerial, earpiece and instructions 69/6 post paid.

9 TRANSISTOR TRANSCIEVERS TWO-WAY RADIOS

Average range up to 5 miles. Frequency 27 Mc/s. Band. Supplied complete with telescopic aeriels. Batteries. Personal Leathers carrying cases and instructions. Brand new, guaranteed. £25. pair. S.A.E. for details.



SEMI AUTOMATIC BUG KEY



Super speed key. 7 speed adjustments, 10 WPM to as high as desired with scale for reproducible settings. Precision tool anti rust nickel plated brass and stainless steel operating parts. Size 6 1/2 x 3 x 2 1/2 in. Brand new. £4.12.6. Post paid.

SILICON RECTIFIERS

SCR. 400V. P.I.V. 4.7 amp 7/6
200V. P.I.V. 6 amp 5/6
800V. P.I.V. 500mA 5/6
400V. P.I.V. 500mA 3/6
70V. P.I.V. 1 amp 3/6
95V. P.I.V. 1 amp 4/6
0A302 miniature silicon rectifiers 1/- each. Special Discounts for quantities. Please add postage.

PLUGS AND SOCKETS

Painton 15-pin in-line printed circuit connectors. 7/6 pair. Large quantities available. Unifers. 4 pin. 2/6 pr; 8 pin 3/6 pr; 12 pin 4/6 pr; 18 pin 4/6 pr. Painton Miniature Jones. 4 pin 3/6 pr; 6 pin 4/6 pr; 8 pin 4/6 pr; 12 pin 5/6 pr; 18 pin 7/6 pr; 24 pin 10/6 pr; 33 pin 12/6 pr. Post extra.

AMERICAN BLOCK PAPER CONDENSERS

Very high quality. 10mF. 600V. 8/6; 10 mF. 1kV 10/8; 12 mF. 1.5kV 15/-. Post extra.

L.T. METAL RECTIFIERS

FULL wave bridge connected. 12/18V 1A 3/9 24/36V 1A 7/3
12/18V 2A 4/3 24/36V 2A 13/6
12/18V 4A 8/6 24/36V 15A 45/6
12/18V 6A 12/6 36/48V 6A 32/6
12/18V 10A 22/8 Post extra.

L.T. TRANSFORMERS

For changers, models etc. All primaries tapped 200/250V. (1) 3.5, 9 or 17V., 1 amp, 9/6; (2) ditto 2A., 14/3; (3) ditto 4A., 16/6; (4) ditto 6A., 26/6; (5) 3, 4.5, 6, 8, 10, 12, 15, 18, 20, 24 or 30V., 2 amp, 18/6; (6) ditto 4A., 30/6; (7) ditto 5A., 37/6; (8) 50V., 1 amp, 13/6; (9) 50V., 1 amp, 15/6. Post extra.

AUTO TRANSFORMERS

Step up or step down. Tapped 0/115/200/230/250V. 20W. 9/1; 60W. 12/6; 75W. 15/6; 150W. 18/6; 200W. 27/6; 300W. 42/6; 500W. 67/6; 1,000W. 90/-; 1,500W. 128.18.6; 3,000W. 177.10.0; 7,500W. £15 (only tapped 0/110/230V.) Post extra.

30,000 O.P.V. TEST METER MODEL 500

Reads voltages up to 1,000 D.C. at 30,000 ohms per volt and A.C. at 15,000 o.p.v., D.C. current to 12 amps. Resistance to 60 Megs; Decibels from -20 to +56. Incorporates internal buzzer for audible warning of direct shorts and blocking condenser for A.F. output measurements. Size 3 1/8 x 6 1/8 x 2 1/2 in. PRICE £8-17.6.



CONSTANT VOLTAGE TRANS.
95/130V. Input. 115V. Output.
500 watts. Can be used in series
for 230V. £4 each. Carr. 10/-.

**DUMONT KIOSIPI DOUBLE
BEAM C.R.T.**
Twin gun. 6.3V. new. boxed.
59/8. P.P. 3/6.

MAINS ISOLATION TRANS.
230V. to 230V. 50V. 10/6. P.P. 3/-.
3/-: 100W. 29/6. P.P. 3/6: 1,000W.
£5. Carr. 10/-.

TM-59 'er 'S' METER



Signal strength meter using VTVM principles. Calibrated in S units. Sensitivity and zero adjustments. For any superhet receiver with AVC. Requires 150/200V. and 6 or 12V. Complete with valve and full instructions. 82/6. P.P. 2/6.

VARIAC TRANSFORMER
24 amp. Pri. 230V. Sec. 185/250V. £12.10.0. Carr. 10/-.

MAINS MOTORS 220 240V
90 watts. 5,000 r.p.m. 4 1/2 in. spindle 22/6. P.P. 2/-.

**MINIATURE LEAD ACID
ACCUMULATORS**
Brand new. 2V. 1.5A. 4 x 1 x 1 1/2 in.
5/8. P.P. 1/3. 12V. 0.75A.
4 x 3 x 1 1/2 in. 15/6. P.P. 1/6.

TWIN MOTOR BARGAIN
200/250V. A.C. Twin concentric spindles. Either motor reversible. 1400 r.p.m. Brand new. 12/6. P.P. 2/6.

MINIFLEX 1/2 TRACK TAPE HEADS
Set of 3, record. playback, erase. ONLY 29/6 set. P. & P. 9d.

**COLLARO/MAGNAVOX. STUDIO
TAPE TRANSCRIBER**
Brand new. 3 speeds. 11. 31. 71
i.p.s. 3 motors, digital counter.
Complete with 2 spools. Instructions.
10 gm. Carr. paid.


**4-CHANNEL TRANSISTORISED
MICROPHONE MIXER**
Add musical lights and additional 3 c.u.n.d. effects to your recordings. The MM-4 permits mixing of four signals such as microphone, records, tuner, etc. into single output. Inputs and output take standard plugs. Fully transistorised and self contained in handsome case. PRICE 59/6 Post Paid.



HEAVY DUTY POWER SUPPLIES
Input 200/250 volt A.C. Three H.T. outputs 2 x 400V. 175mA and 350V. 225mA. All fully smoothed. 2 x 6.3V. 5 amp. 6.3V. 4 amp. 12V. 0.5 amp. Supplied in perfect condition. £5.10.0. Carr. 20/-.


**PRECISION PORTABLE
VOLTMETERS**
Polished wood case. 8in. scale with knife edge pointer. A.C. and D.C. volts: 0-180 volts. 59/8. 0-180-320 volts. £5.18.6. P.P. 3/6.

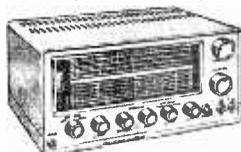HE-30 SUPER AMATEUR COMMUNICATION RECEIVER



4 bands covering 550Kc/s to 30Mc/s continuous. Operation 200/240 volt A.C. Special features include: Easy to read illuminated slide rule dial—Built in Q multiplier—Aerial trimmer—calibrated electrical bandspread on amateur bands—0-100 logging scale—noise limiter—AVC/MVC selector—stable, 1000 Hz multiplier—clear CW and 85b re-p.e.p. meter. Output for phones or STD speaker. Supplied brand new and guaranteed with manual. £42 carr. paid. S.A.E. for full details. Part exchanges welcome.

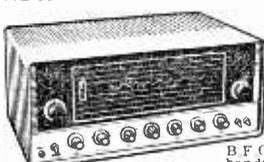HE-80 14-VALVE AMATEUR COMMUNICATION RECEIVER




550Kc/s to 30Mc/s 2 Metre Band. 144 to 146M/c/s. Two receivers in one. Continuous coverage from 550Kc/s to 30Mc/s and 144 to 146M/c/s. Dual conversion on 2 metres, with extra RF and Mix stage. Special features include "S" meter. Crystal calibrator "Q" multiplier. B.F.O. Bandspread on all amateur bands. Large illuminated dial with logging scale. Improved A.N.L. regulated power pack. Output for phones or speaker (8 or 500 ohms). Operation 200/250 volt A.C. Valve line-up 4 x 6AQ8, 3 x 6BA8, 2 x 6BE6, 1 x 6BE1, 8AL5, 8AQA, 6CA4, and OA2. Attractive grey steel cabinet. 17 x 7 x 10in. Supplied brand new and guaranteed complete with instruction manual. 59 gm. Carriage paid. S.A.E. for full details. Part exchanges welcome.

**NATIONAL H.R.O. RECEIVERS
SENIOR MODEL.** Complete with a full set of 9 coils covering 50Kc/s to 30Mc/s. Each receiver thoroughly checked and tested before despatch. Dual purpose rack model for table or phone or speaker. Extremely good used condition. £18.18.0. Carr. £1. 200/250 volt A.C. power supplies for H.R.O. also sold separately. 59/8. Carr. 5/- S.A.E. for full details.

P.C.R.2 COMMUNICATION RECEIVERS

Excellent 6 valve receiver. Frequency coverage on 3 bands. 200-2,000 metres. 100-550 metres and 8-22Mc/s. Output for phone or speaker. Supplied in perfect condition. £5.19.6 each. Carr. 10/- The receiver can be supplied with an internal power supply to operate on 200/250 volt A.C. at 39/6 extra, or plug in external power supplies are 35/- extra. Full circuit supplied.

MODEL PT-34 1,000 O.P.V. MULTI-TESTER

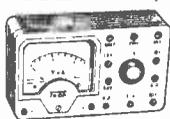

Dependable and Easy to Read SPECIFICATIONS:
D.C. V. ... 0-10-30-250-500-1000 V
A.C. V. ... 0-10-50-250-500-1000 V
Current ... 0-1-100-500mA
Resistance: 0-100K Ohm Battery: 1.5V U12.
Size: 3 1/2 x 2 1/2 x 1 1/2 in.
Supplied complete with batteries, leads, instructions. 39/6. Post 1/6.

MODEL PV-58 VACUUM TUBE VOLTMETERS

Latest design with special circuit for stable and accurate measurements. Resistors used are all within 1% tolerance. Specially designed 8in. 200uA meter. 11 Mcv. inputs. Ranges:
-D.C. V. 0-1.5-5-15-50-150-500-1500V.
+D.C. V. 0-1.5-5-15-50-150-500-1500V.
A.C. V. 0-1.5-5-15-50-150-500-1500V. RMS.
-0-1-4-14-40-140-400-1300-1000 P.P.
Resistance: 2 ohm to 1,000 megohm.
Decibels: -10dB to +65 dB.
Operation 220/240 volt A.C. Size 7 x 4 1/2 x 4in.
Supplied brand new and guaranteed complete with probe and instructions. £13.19.6. P.P. 3/6.



TE-46 CAPACITY-RESISTANCE ANALYSER



* Factory wired and tested.
* Capacitance bridge circuit.
* Direct reading scales for capacitance and resistance.
* Magic eye null indicator and meter.
* Checks opens, shorts, leakage and intermittents.
* Determines power factor of electrolytics.
* 2 Turns ratio scales.
* Measures impedance.
Capacity 4 ranges 2pF-2,000 pF. Resistance 4 ranges 2 ohm-200 meg. ohm. Turns, ratio and impedance ranges. Read insulation resistance direct on meter. 200 meg. Size 10 1/2 x 7 x 5 1/2 in. Operation 200/250 V. A.C. Supplied brand new with instructions. £15. Carr. 7/6.

COMMUNICATION RECEIVER SPEAKER



3 x 5in. speaker in grey steel case to match HE-30 or HE-80. 8 ohm imp. Size 7 1/4 x 3 1/2 x 5 1/2. 55/- each. P.P. 2/6.

**LAFAYETTE BRAND
RECORDING TAPE**

First grade quality American tapes. Brand new and guaranteed. Discounts for quantities.
5in. 600ft. std. plastic 8/8
5in. 600ft. L.P. acetate 10/-
5in. 1200ft. D.P. mylar 15/-
5in. 1200ft. L.P. acetate 12/8
5in. 1800ft. D.P. mylar 22/8
7in. 1200ft. std. mylar 12/6
7in. 1800ft. L.P. acetate 15/-
7in. 1800ft. L.P. mylar 22/-
7in. 2400ft. D.P. mylar 25/-
Postage 2/- Over £3 post paid.

**TRANSISTORISED FIELD
STRENGTH METER**



3 bands 2.5 to 57Mc/s. Permits easy tuning up for max. transmitter output. Ear- phone jack to monitor radio. 200uA meter cal. 0-10
Supplied complete with battery telescopic aerial. £7.7.0 each. P.P. 2/6.

HEADSET & BOOM MICROPHONE
American type, low impedance. padded. 49/6. P.P. 2/6.

R.C.A. HEADSETS
Low imp. Fitted with std. jack plug. 15/6. P.P. 1/6.

ROTARY TRANSFORMERS
12V. D.C. input. Output 310/360V. D.C. 30mA. New boxed. 10/- P.P. 2/-.

200 KΩ INSTRUMENT POTS.
Wirewound. 3/4in. dia. 5/8 each. P.P. 1/3.

R.C.A. PLATE TRANSFORMERS
200/250V. pri. 2,000-1,500-0-1,500-2,000V. 500mA. New, boxed. £6.10.0. Carr. £1.

PHOTO VOLTAGE AMP. UNITS
Fitted with twin selenium photo cells. Tinsley mirror valve. £9.19.6 each. Carr. 7/6.

500 VOLT BRIDGE MEGGERS
Evershed Vignoles series 11. Supplied in as new condition, complete with leather case. £40 each. Guaranteed.

**PRECISION COMBINATION
VOLTMETER AMMETER**
Two separate instruments housed in polished wood case. 6in. scales with knife edge pointers. Ranges as follows: A.C. and D.C. volts: 0-180-300-600 volts. A.C. and D.C. Current: 0-25-50-150-200 amps. Supplied complete with shunts, leads and leather carrying case. Brand new condition. £9.19.6 each. Carr. 7/6.

**LARGEST STOCKS OF
COMPONENTS**
receivers and test equipment in the country. Open 9 a.m. to 6 p.m. Every day, Monday to Saturday. Trade supplied. S.A.E. for Valve Lists, etc.

GW SMITH & CO (RADIO) LIMITED
Phone GERRARD 8204/9155
Cables SMITHEX LESQUARE
3-34 LISLE STREET, LONDON W.C.2

POST HASTE FROM SURBITON

ALL ORDERS DESPATCHED SAME DAY ● WE PAY POSTAGE and INSURANCE ● ALL TRANSACTIONS receive PERSONAL ATTENTION and PROTECTION from our MONEY BACK GUARANTEE

★ MARTIN RECORDAKITS ★

For HALF TRACK

Tape Amplifier for Studio Deck with ready wired printed circuit control and input panels, mains and output transformers, knobs, plans, screws, etc. EP86, ECC83, EZ80, EM85 and 2 EL84. 3 watts output. Magic eye, radio and Mic. inputs. Ext. speaker socket. Tone and Monitor controls. Can be used as an amplifier. £11.11.0
 Collaro Studio Deck. Very latest model, 3 speeds, 7in. spools. £10.19.6
 Case for above, with 8 x 5in. speaker, two tone grey. £5.5.0
 Complete Kit with Tape and Microphone. £29.5.0

B.S.R. Monardeck TD2, latest model 5 1/2in. spools £29.9.0
 Tape Amplifier for B.S.R. Deck, printed circuit ready wired with ECC83, ECL82, EM85 and EZ80. Complete with all plugs, sockets, panels, knobs, etc. Mounts under deck making a self-contained unit. £8.8.0

For QUARTER TRACK

Collaro Studio Deck, Marriott "X" heads. £17.17.0
 Tape Amplifier for Studio Deck, described above, but quarter track. £12.12.0
 Case, with speaker, two tone grey. £5.5.0
 Complete Kit with Tape and Microphone. £35.0.0

Dep.	&	Mthly pmts. of
24/-	12	19/-
22/-	8	27/3
58/-	12	48/2
20/-	9	21/-
37/6	12	28/5
37/-	12	20/8
70/-	12	58/2

B.S.R. TD2 Deck with Marriott "L" Series heads £11.11.0
 Tape Amplifier for B.S.R. deck, as over, but quarter track. £9.9.0

TAPE PRE-AMPLIFIER

For Studio Deck, with power supplies, ECC83, ECL82, EZ80 and EM84. Mic. and Radio socket, gives full equalised output of 400 mV/ohms. Half Track £8.8.0
 Quarter Track £9.9.0
 Building Instructions available at 2/6 each Kit (refunded on purchase Kit).

TAPE HEADS

MSS Quarter track. Record/Playback and Erase per set. £3.3.0
 Bradmatic Half track Record/Playback head only £1.12.6
 Bradmatic Half track Record/Playback and Erase per plate. £1.19.6
 Collaro pressure pad for third head position. 4/-

BRENELL

Mk. 5 Series 2 Deck, Half track 4 speed. £32.11.0
 Mk. 5 Series 2 Tape Amplifier with power pack £26.0.0

Dep.	&	Mthly pmts. of
24/-	12	19/-
20/-	9	21/-
20/-	8	21/-
20/-	9	21/-
65/-	12	54/-
52/-	12	43/2

GRAMOPHONE UNITS, MOTORS, PICK-UPS

Decca Deram Arm and Plug-in Shell. £5.5.0	—	—	—
Decca Deram Transcription Cartridge. £4.14.6	—	—	—
Decca Dram Auto Cartridge. £3.13.6	—	—	—
Garrard SRP10 with GCS cartridge, Mono, single player. £5.9.11	—	—	—
B.S.R. UA14 with TCS cartridge, Mono, 4-speed changer. £6.19.6	20/-	6	23/3
Garrard Autotrim, Mono GCS cartridge, 4 speed changer. £7.17.0	20/-	7	22/6
Garrard A16 Autotrim de Luxe, GCS Mono cartridge. £11.9.0	26/6	9	24/9
Garrard 4H/F with Mono GCS cartridge. £17.0.0	34/-	12	28/2
Garrard Lab Type "A" Transcription auto-changer, with GCS cartridge, mono. £19.14.0	39/6	12	32/9
Garrard 301. £20.12.2	43/2	12	34/-
Garrard 301 Strobe. £22.0.0	44/-	12	36/6
Philips A61016, Stereo cartridge, will change 7in. records (adapter 10/- extra). £12.12.0	27/-	12	29/6
Goldring GL58 with arm, less cartridge. £17.1.9	36/-	12	28/2
Goldring GL70 with arm, no cartridge. £27.9.4	55/-	12	45/8
Goldring "88" Transcription, no arm. £18.18.5	41/-	12	31/1

MONO AMPLIFIERS

Linear L45, 3 watt, 3 valve. £5.19.6	—	—	—
Linear Diatonic, 12 watt, suitable Mic. or guitar. £12.12.0	27/-	12	20/8
Linear Conchord, 20 watt, ideal guitar amp, with case. £18.0.0	38/-	12	29/10
Dulci GA5, integrated amp, 5 watt, ECL86 valve £13.2.6	28/6	12	21/6
Dulci PA15, 15 watt with 2 valve pre-amp. £26.5.0	52/6	12	43/6
Tripletone Hi-Fi Major with pre-amp. Suitable for Guitar or Mic. etc. £15.19.0	35/3	12	28/1
Leak TL12, 10 watt Main amp. only. £18.19.0	40/6	12	31/1
Leak Variotape pre-amplifier. £15.15.0	31/6	12	26/1
Quad, 15 watt Main amplifier only. £22.10.0	45/-	12	37/4
Quad pre-amplifier, Mono. £19.10.0	39/-	12	32/4

ARMSTRONG - NEW TUNER-AMPLIFIERS

MONO

AF208 A.M./F.M. Radio chassis, bass and treble controls, P.V. inputs, etc. £21.4.0	48/-	12	34/10
BT3 Mk. 2 A.M./F.M. Self-powered tuner. £25.12.0	53/-	12	42/4
227M Q.M./F.M. Radio chassis 10 watts. £23.18.0	70/6	12	56/1
225 A.M./F.M. Self-powered (Tuner only). £23.15.0	67/6	12	47/9
224 F.M. only, Self-powered Tuner. £22.10.0	45/-	12	37/4

STEREO

Stereo 55 A.M./F.M. Radio chassis, with Stereo gram inputs. £29.13.0	62/6	12	49/5
227 A.M./F.M. Radio chassis, Stereo gram, 10 watts each channel. £29.15.0	97/6	12	81/1
228 A.M./F.M. Radio chassis, Stereo gram, 10 watts each channel, Filter, etc. £58.0.0	112/-	12	93/2

OTHER TUNERS

Tripletone F.M. Tuner, less power. £13.19.6	28/-	12	23/2
Tripletone F.M. Tuner, self-powered. £15.14.6	31/6	12	28/1

STEREO AMPLIFIERS—VARIOUS

Armstrong 222, Integrated, 10W per channel. £27.10.0	55/-	12	45/8
Dulci GA505, Integrated. £18.18.0	40/6	12	31/1
Rogers Cadet Mk. 2 with pre-amplifier, 4 ECL86 valves. £28.15.0	53/6	12	44/5
Leak Stereo 20, Main amplifier. £30.9.0	64/6	12	50/3
Leak Variotape stereo pre-amplifier. £25.0.0	50/-	12	41/6
Quad 22 Stereo Control Unit. £25.0.0	50/-	12	41/6

For Quad Main Amplifiers see Mono section.

JASON F.M. AND TV SOUND TUNERS

FMT1, complete with 4 EF81 valves. £7.4.6	21/-	7	20/6
FMT2, less power, complete with 4 EF80 valves. £9.4.6	20/-	9	20/6
FMT2, with power, complete with 4 EF80 and 1 EZ40. £11.4.6	22/6	9	24/9
MT3, Surrey, complete with valves, less power. £10.19.0	22/-	8	27/3
FMT3, with power, complete with all valves. £12.19.0	26/-	12	21/6
JTV/2, switched F.M. and TV sound, self powered, all valves. £15.12.6	33/6	12	25/8
Mercury II, as JTV/2 but less power, all valves. £11.0.0	22/-	8	27/3
Instruction book included in all kits. Available separately. 2/6 and 3/6.	—	—	—
JTV/2, ready built, state channels. £22.5.0	44/6	12	36/11
Monitor, ready built (as Mercury II). £16.15.6	33/6	12	27/9

LOUDSPEAKERS

Goodmans Axlette 3. £5.5.7	—	—	—
Goodmans Axiom 10. £5.5.11	—	—	—
Goodmans 5K/20/XL. £7.7.0	—	—	—
Goodmans XO 5000 cross-over. £2.0.11	—	—	—
Goodmans Axiom 291 12in. Unit. £10.17.4	22/5	12	17/11
Goodmans Axiom 301 12in. Unit. £15.4.6	30/6	12	25/3
Wharfedale Super 5/8S/DD. £8.14.2	—	—	—
W.B. HF1012 10in. £4.7.8	—	—	—
R.T.C. 12in. Unit, 15 watt. £5.15.0	—	—	—
R.T.C. Hi-Fi Master. £8.8.0	20/-	8	21/-
Wharfedale W12/EG 12in. 15 watt Lead Guitar speaker. £10.10.0	21/-	12	17/5
Wharfedale W15/EG 15in. 15 watt Base Guitar speaker. £17.10.0	35/-	12	29/-
Wharfedale Super 10/RS/DD 10in. high quality unit. £15.18.0	23/8	12	17/11
Wharfedale RS19/DD 12in. 15 watt. Hi-Fi. £11.10.0	27/6	9	24/9

EASILY REACHED BY TRAIN FROM WATERLOO TO SURBITON

SURBITON PARK RADIO LTD.

48, SURBITON ROAD, KINGSTON-ON-THAMES, ENGLAND

- Order for Cash, C.O.D. or Terms
- Hours 9 a.m.-6 p.m. (1 p.m. Wed.)
- Open ALL DAY Saturday
- Established 30 years

PARK RADIO LTD.

**YOUR MAIN SUPPLIERS
FOR THE NEW MARTIN
10W. AMPLIFIER KITS**


With these ingenious new MARTIN AUDIOKITS you can build an ALL-TRANSISTOR Hi-Fi Assembly to suit your personal requirements exactly. When built, you will have a modern, powerful, high quality assembly with ALL the features of a de-luxe hi-fi assembly. Building is easy, and you will save pounds. Designed for simple panel mounting. Easily doubled up for stereo. Full instructions with every kit. Leaflets free on request.



UNIT 1 FIVE STAGE SELECTOR

Enables up to 5 inputs to be connected and correctly switched to following pre-amp stage. With transistor, resistor and capacitors mounted on printed circuit board. Long spindle for adding stereo when required. With Mazda AC136 Transistor.

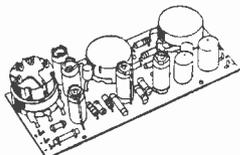Size 3 1/2 x 3in. For Magnetic and crystal P.U.s, Radio Tuner, Microphone, and output from tape head. Requires 9-15 V. **47/6**




UNIT 4 COMBINED PRE-AMPLIFIER AND TONE CONTROL UNIT

Three stages of audio control—base control operating between -10 to +10 dB; treble control between -16 to +12 dB; volume control with on-off switch to serve power supply to complete installation. With all components mounted on printed circuit board. 6 1/2 x 2 1/2in. 9-15V. With Mazda AC176 Transistor. **62/6**

UNIT 5 MAIN AMPLIFIER

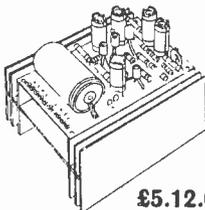
Complete with heat sink, on which the six transistor printed-circuit amplifier is built. Transformerless output gives maximum of 10 watts into 2-ohm speaker, operating from 24 volt supply. Pre-tested by makers. Transistor due-up: Mazda AC136, AC113, AC184, AC157, 2xN KT461, AA120. Wharfedale 3: 15 ohms Matching Transformer. **13/6**



£5.12.6

UNIT 6 POWER SUPPLY UNIT

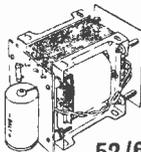Operates from 200-250 volts, A.C., giving D.C. output at 24 volts for main amplifier and tappings for power to other Martin Audiokit Units. Incorporates heavy duty transformer, full smoothing and latest type rectification. Elegant front Control Panel for above ready for fitting. **10/6**



52/6

**ALL 4 ABOVE UNITS £14.5.0 OR 28 6 DEPOSIT
AND 12 MONTHLY PAYMENTS OF 23 7**

**● TAPE ENTHUSIASTS — SEE DETAILS
OF MARTIN RECORDAKITS — Page Opposite**

TECHNICAL TRAINING in radio television and electronics

Whether you plan to have your own business, to become an electronics engineer, to take up a career in industry, or to brush-up your knowledge and study new developments, transistors, etc., an I.C.S. Course will help you to success. You learn at home in your own time, under expert tuition. Moderate fees include all books.

EXAMINATION COURSES FOR:—

**C. & G. Radio
and
TV Servicing Certificate**
(R.T.E.B.)

**C. & G. Radio
Amateurs' Exam.
(Amateurs' Transmitting
Licence)
P.M.G. Certificates in
Radiotelegraphy**

**British Institution of Radio Engineers,
C. & G. Telecom. Technician's Cert.
Gen. Cert. of Education, etc.**

New practical radio construction courses

Learn as you build the I.C.S. way. Learn the theory of radio and electronics. Build a 5-valve, 2-waveband receiver, a transistor portable and an A.F. amplifier. Build a signal generator and a multimeter as well, if you wish—two essential pieces of equipment for those engaged in servicing work. Three courses to choose from.

Post this Coupon TODAY! for FREE book on careers in Radio, and full details of other I.C.S. Courses
Member of the Association of British Correspondence Colleges

INTERNATIONAL CORRESPONDENCE SCHOOLS

(Dept. 171), Intertext House, Parkgate Road,
London, S.W.11.

Please send book on








Name Age

(Block Letters Please) Address

Occupation 5.64

INTERNATIONAL CORRESPONDENCE SCHOOLS

Just a few of our BARGAINS

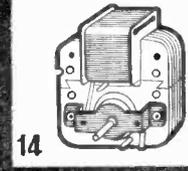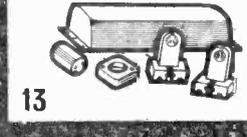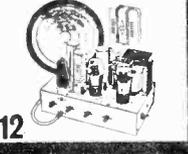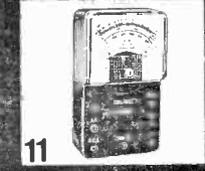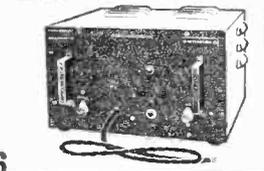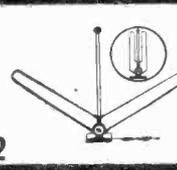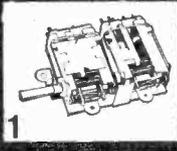

1. A.M. F.M. PERMEABILITY TUNER FOR ALL TRANSISTOR OPERATION. Size 2 1/2 x 2 1/2 in. approx. By famous manufacturer. A.M.-11: 470 Kc/s. P.M.-1: 10.7 Mc/s. A.M. coverage from 1820 Kc/s-825 Kc/s. F.M. coverage 108 Mc/s-88 Mc/s. Circuit diagram 2/6, FREE with Tuner. 25/-, 1st, 2nd, 3rd A.M. 1P's, 12/6 set. 1st, 2nd, 3rd and 4th P.M. 1P's, 12/6 set. V.H.F. Osc. choke, 1/-, A.M. 1.P. trap, 1/6, A.F. 114 and A.F. 115, 5/- each. All the above are the HF end of an AM/FM receiver car radio, etc. The above six items purchased together, £2.10.0.
2. 625 INDOOR AERIAL. Complete with stand, fully extendable, can also be used for 405, T.V. BBC and FM. 10/6, plus 1/- P. & P.
3. A.C./D.C. POCKET MULTI-METER KIT. 2in. moving coil meter scale, calibrated A.C./D.C. volts, ohms and milliamperes. Voltage range A.C./D.C. 0-50, 0-100, 0-250, 0-500. Milliamps 0-10, 0-100. Ohms ranges 0-10,000, 0-100,000, 19/6. P. & P. 2/-. Wiring diagram 1/- free with parts.
4. SIGNAL GENERATORS. Cash £7.5.0. P. & P. 6/6. Coverage 100 Kc/s to 100 Mc/s on fundamentals and 100 Mc/s to 200 Mc/s on harmonics. Case 10 x 6 1/2 x 5 1/2 in. Three miniature valves and Metal Rectifier. A.C. mains 230-250v. Internal modulation of 400 c.p.s. to a depth of 30 per cent. Modulated or unmodulated R.F. output continuously variable 100 millivolts. C.W. and mod. switch, variable A.P. output. Magic eye an output indicator. Accuracy 2 per cent.
5. SIGNAL GENERATORS. Cash £5.5.0. P. & P. 6/6. Coverage 120 Kc/s to 84 Mc/s. Case 10 x 6 1/2 x 4 1/2 in. Size of scale 6 1/2 x 5 1/2 in. 2 valves and rectifier. A.C. mains 230-250v. Internal modulation of 400 c.p.s. to a depth of 30 per cent, modulated or unmodulated R.F. output continuously variable 100 millivolts. C.W. and mod. switch variable A.P. output and moving coil output meter. Accuracy ±2 per cent.
6. FIXED FREQUENCY SIGNAL GENERATOR. Crystal control in metal case, size 10 x 6 x 4 in. Incorporating two PU13 valves, mains transformer, metal rectifier, choke, indicator lamp, crystal and numerous components. Modulated and unmodulated output sockets. Originally used for 1 T.V. frequencies. Brand new. 39/6, plus 6/- P. & P. A.C. Mains 200/250 volts.
7. 50 MICRO-AMP METER movement by world famous manufacturer. Size 3 x 2 1/2 in., 50/-, post free.
8. The MOTORISTS' REV. COUNTER. Kit of parts comprising 270 degree 5in. moving coil movement. Manufacturer's present price of this movement would be at least £7. Complete with full instructions and circuit diagram. Scale calibrated up to 8000 r.p.m. Can be used with any 4 or 6 cylinder car. 29/6, plus 3/6 P. & P. Meter movement only 22/- post paid.
9. CHANNEL TUNER I.F. 16-19 Mc/s. Continuously tunable from 174-216 Mc/s. Valves required—PCP80 and PCC84 (in series). Cover BBC and ITA ranges. Also Police, Fire and Taxia, etc. Brand new by famous maker, 10/-. P. & P. 3/-.
10. B.S.R. MONARCH UA14 WITH FULL-FI HEAD. 4-speed, plays 10 records, 12in., 10in. or 7in. at 18, 33, 45 or 78 r.p.m. Intermixes 7in., 10in. and 12in. records of the same speed. Has manual play position: colour brown. Dimensions: 12 1/2 x 10 1/2 in. Space required above baseboard 4 1/2 in., below baseboard 2 1/2 in. Fitted with Full-Fi turnover crystal head, £5.19.6. P. & P. 6/6.
11. POCKET MULTI-METER. Size 3 1/2 x 2 1/2 x 1 1/2. Meter size 2 1/2 x 1 1/2 in. Sensitivity 1,900 O.P.V. on both A.C. and D.C. A.C. and D.C. volts: 0-15, 0-150, 0-1,000. D.C. current: 0-150 mA. Resistance 0-100K Ω. Complete with test prods, battery and full instructions. 35/-, P. & P. 1/6
12. 8-watt PUSH-PULL 4 VALVE AMPLIFIER PLUS METAL RECTIFIER. A.C. mains 230-250 v. Size 10 1/2 x 6 1/2 x 2 1/2 in. 4 valves. For use with all makes and types of pick-up and mike. Negative feed back. Two input, mike and gram, and controls for same. Separate controls for Bass and Treble lift. Response flat from 40 cycles to 15 kc/s. 2 dB down to 20 kc/s. Output 8 watts at 5 per cent total distortion. Noise level 40 dB below full hum. Output transformer tapped for 3 and 15 ohms speech coils. For use with Std. or L.P. records, musical instruments such as guitars, etc. Suitable for small halls, £3.19.6. P. & P. 7/6. Crystal mike to suit, 15/-, P. & P. 2/-. 8" x 5" P.M. Speaker to suit, 12/6. P. & P. 2/-.
13. FLUORESCENT LIGHT KIT. 40 watt fluorescent lighting kit comprising Siemens Choke, 2 pin holders, starter holder and starter. 11/6, plus 3/- P. & P.
14. A.C. MAINS MOTOR. Silent running by famous manufacturer. A.C. Mains 230-250, shaded pull start. 1440 r.p.m., size 2 1/2 x 5 1/2 x 1 1/2 in. approx. 7/6, plus 1/6 P. & P.

RADIO & T.V. COMPONENTS
[ACTON]
LIMITED

21b HIGH STREET
ACTON, LONDON, W.3.

ALL ENQUIRIES S.A.E.
GOODS NOT DESPATCHED OUTSIDE U.K.

SPECIAL OFFER! FROM R. & T.V. LTD.

Elegant Seven

COMBINED PORTABLE & CAR RADIO

The Radio with the STAR features

- ★ 7-transistor superhet. Output 350mW.
- ★ Two-tone grey wooden cabinet, fitted handle with silver coloured fittings. Size 12½ x 8½ x 3½ in.
- ★ Horizontal tuning scale, size 11½ x 2⅜ in. in silver with black lettering.
- ★ All stations clearly marked.
- ★ Ferrite-rod internal aerial.
- ★ I.F. 470 Kcs.
- ★ Operated from PP9 battery.
- ★ Full comprehensive instructions and point-to-point wiring diagrams.
- ★ Printed circuit board, back printed with all component values.
- ★ Fully tunable over medium and long waveband.
- ★ Car aerial socket.
- ★ Full after-sale service.

ONLY
£5.9.6



Plus 5/6 P. & P. Parts list & circuit diagram 2/6. FREE with parts. 4½ in. Speaker also available. 7/6 extra.

Goods not despatched outside U.K. All enquiries S.A.E. Terms C.W.O.

RADIO & TV COMPONENTS (ACTON) LTD 21C High St., Acton, London, W3

Open 9 a.m.-6 p.m. Including Sats. Early closing Wed.


CRYSTALS & COMPONENTS LTD.

2-4 EARLHAM ST., W.C.2. Tel. TEM. 1189

Near Cambridge Circus. A few minutes' walk from Leicester Square on Tottenham Court Road Underground Stations. Hours of Business: 9 to 6. Saturdays 9 to 1. Open All Day Thurs.

WIRELESS SET No. 19.

Complete with original power supply unit for 12 volts input. Transmitter Receiver covering 28 Mc/s and V.H.F. 240 Mc/s 8 valve superhet receiver and 8 valves in Transmitter. Using I.F. of 165 Kcs. For voice and C.W. In good condition not tested. £4.12.8. Plus £1 packing and carriage. Microphone and headset for this set 17/3 plus 2/6 post and packing. 19 Set Variometers. 17/8 plus 2/6 post and packing. Control box for 19 set. 10/- plus 2/- post and packing. Lead for control box. 12/8. post and packing 2/-.

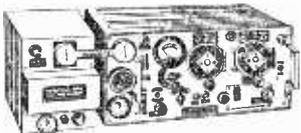

TYPE 38 TRANS/RECEIVERS

Brand new. Operating on 7.4 to 9 Mc/s. Trans-Receiver. Complete with headphones, throat microphone function box and aerial rods. Operate on 150 volts HT and 3 volts LT dry batteries. Complete inc. batteries and not tested. 42/8 per set plus 6/6 post. Or £4.10.0 per pair plus 10/- post and packing.



SEND S.A.E. FOR
NEW
CRYSTALS
LIST

Terms of
Business
Cash With
Order.

1000 p.i.v. silicon diodes 550 m'A 9/- each plus 6d p. & p.

BARGAIN OFFER!

AMPLIFIER. 3 watts, 2 valves, 6X4, ECL82. AC Mains. Mounted on board with 8in. speaker, Pilot light and Tone Control. £3.10.0 complete. Post 4/6.

CONNECTING WIRE. Stranded or Single. Various colours, our selection 100ft. 4/-.

SPEAKER CABINET. THE HAYDON (17 x 15 x 8in.). Designed to take a 12in. heavy duty speaker. Ideal for bass guitar. Covered with Vynide and Vynair in contrasting colours. 50/-, post 7/6 extra.

SPEAKER suitable for above cabinet. R.T.C. 15 ohms 15 watts. Heavy duty 12in. £5, post 4/-.

STEREO Ronette S 106. 25/-.

CARTRIDGES. Monaural. Acos GP59-5 high output. 15/-. Acos GP65-1G medium output, 15/-, to fit most Garrard, Collazo or B.S.R. pick-ups.

EARPIECES with cord and 3.5 mm. plug. Crystal. 4/-; 180 ohms magnetic 6/6; 80 ohm 2.5 plug. 4/-.

HIGH RESISTANCE PHONES: 4,000 ohms. Chinese, 11/6 pair; **TRANSISTOR ELECTROLYTICS:** 1µF, 2µF, 4µF, 5µF, 8µF, 16µF, 32µF, 50µF, 100µF, all 15 volt, 1/3 each.

BARGAINS IN TRANSISTORS. The latest Mullard M Series: OC44M, two OC45M, OC81DM. Two OC81M matched pair; OA90 diode. Complete set. 22/6. OC44, 3/6; OC45, 3/-; OC71 2/6; OC72, 3/-; OA81, 2/3; GEC S6 Good AF General Purposes. 2/-; GET873 RF. 2/3.

McMICHAEL TELESCOPIC TV AERIAL. 23' extending to 45'. Fitted with coaxial plug. Will suit any set. ONLY 7/6.

MAKE your own light-sensitive switch: for parking lights, burglar alarms, model railways, door bells, window lights, etc., etc. The Circuit, Mullard ORP12 Light Cell, two transistors and resistors. 25/- the Set.

TERMS: C.W.O. OR C.O.D.

BROADWAY ELECTRONICS

92 MITCHAM ROAD, TOOTING, S.W.17

(four minutes from Tooting Broadway Underground Station)

COULD THIS SMALL INVESTMENT BE THE KEY TO YOUR FUTURE SUCCESS?

New Radio Training Course now available for 36/- complete!

How can anyone afford to produce a course for 36/-?

Here is the story behind this greatest value radio training and why you get it for so little!

We pictured the average student as an ambitious person, doing some wireless repair work, but needing more training, more practical knowledge to become an expert. We thought of men who just couldn't afford high priced correspondence courses like the four different ones we had for comparison purposes. The answer. Why not put the essential lessons, the sum and substance of practical radio training into manual form? This way we could cut selling expense, letter writing, sending one lesson at a time, cut the cost of items that do not help learning in any case! Good idea? We thought so. Arrangements were then made with a highly qualified text book publisher who planned and worked out the whole idea, collected all essential up-to-date data, secured co-operation and assistance from leading manufacturers and tested the material on servicing engineers. In addition permission was obtained to use sections of a leading home-study course. Difficult parts were simplified and helpful examples worked out for easy understanding. New sections were added, some lessons enlarged, photographs and drawings obtained to make things easier.

The 22 practical lessons making up this course-manual are easy to follow and apply to actual radio jobs. Use this training to get ahead in radio and as an introduction to television. Radio facts that puzzled you will be quickly cleared up. You will find yourself doing radio repairs in minutes instead of hours—instantly finding faults and making needed adjustments.

Every new radio development of importance and thousands of time saving radio facts are packed into this complete course manual. For example, there is a large lesson on servicing VHF/FM sets and another full lesson on audio amplifiers.

The course includes easy-to-follow, well illustrated sections on test equipment, circuits, car radio sets, alignment, use of the oscilloscope, and every other topic needed to be an expert in wireless repairing.

The lessons are easy to understand, practical, down to earth. You will enjoy every minute of your training. This could be the key to your future success.

If you would like me to reserve a copy of the course for you, please clip the coupon right away.

Yours sincerely,
FRED G. SIMPER.

P.S.—You must be convinced that this is the best value you have ever seen in radio training, otherwise you can return the course (or have your money refunded if sent with order) after you have examined it in your own home for a period of seven days.

P.P.S.—Send cash with order and get a 70-page Radio Fault Finding Book at no extra charge. This book covers Basic Fault Finding Static Tests, Faults causing Distorted Reception, Hum and Noise, Instability, Intermittent Faults, FM Receivers, Transistors and Printed Circuits.

FREE TRIAL OFFER!
Terms only 5/- per week if you wish.

To **FRED G. SIMPER**, c/o Sim-Tech Technicians' Books, Dept. XR3, West End, Southampton, Hants.

Please send your RADIO COURSE for a full seven days' free trial. If not delighted I may return the course post-paid without further obligation on my part, otherwise I will pay cash price of 37/6 (includes 1/6 postage) OR 5/- weekly until 37/6 plus 2/6 service charge, total 40/- is paid.

Tick here if enclosing full price of 37/6 (same 7-day money back guarantee). **NOTE: PLEASE SEND ME THE FREE 70-PAGE GIFT BOOK ON RADIO FAULT FINDING** (a descriptive booklet). Overseas customers please send full amount (including Ireland).

Name

Address

City..... County.....

CABINETS???

ASK US FIRST

We manufacture a complete range of all types of cabinets at very competitive prices. Please give exact dimensions of cabinet required. W. will also make to your design.

LINE OUTPUT TRANSFORMERS

BUSH TV26	17/6 ea.
PYE V4, VT14, CTM4, VT17	17/6 ea.
EKCO 221, 231	25/-
FERGUSON 204, 206, 306, 998	17/6 ea.
PHILIPS 1446U, 1458U	17/6 ea.
McMICHAEL MP14	17/6 ea.
SOBELL T346	17/6 ea.

Post and Pack. 3/6 each.

SCAN COILS for above Models 10/- ea. P. & P. 3/- ea.

RECORD PLAYER AMPLIFIERS

2 WATT AMPLIFIER. A compact unit with tone and volume controls. With valves (PC182, PY82) on a board complete with 6p transformer and 6in. speaker. Cheap reproduction. Absolutely ready to play. **ONLY 59/6**, plus 2/6 P. & P. **4 WATT AMPLIFIER.** Valve line up 4B17 or 6F89, E184, E280. Fitted with volume, bass, and treble lift controls. Absolutely complete **ONLY 53.12.6**, plus 4/6 P. & P.

PORTABLE TRANSISTOR RADIOS

QUALITY 6 TRANSISTOR RADIO, giving amplifying reception on medium and short waves, good tone from 3in. speaker, socket for car aerial. In robust, stylish case in mixed colours. **£6.15.0**. **DE LUXE VERSION** of above with 5in. speaker **£7.7.0**. Either set plus 2/6 post and packing.

TURRET TUNERS for:	FERGUSON 204,
EKCO 221, 231,	206, 306,
PHILIPS 1446U, 1458U,	206, 306,
PYE V4, VT14, VT17, CTM4	McMICHAEL MP14
ALL AT 7/6 EACH P. & P. 2/6.	

COMPLETE I4 in. TV SETS—Untested

Choice of **PYE, PHILIPS, EKCO** and **SOBELL**, well packed—but at owners' risk. **£2 EACH**, plus 10/- carriage and packing.

VALVES EX-EQUIPMENT TESTED & GUARANTEED

EB91	2/-	PL36	6/6	6F15	6/-
EBF50	4/-	PL81	5/6	6F19	6/-
EBF82	4/6	PL82	4/-	6H4	6/-
EC81	3/6	PL83	5/-	6L1	6/-
EC82	4/-	PY32	7/6	6P25	5/-
EC85	5/-	PY33	7/6	6P28	7/-
ECH35	6/-	PY80	3/6	7B6	6/-
ECJ42	6/-	PY81	2/6	7G5	6/-
ECJ81	6/-	PY82	3/-	7F7	10/-
EC182	6/-	PY83	6/-	7J7	6/-
EP85	4/6	PZ30	7/-	7V4	5/-
EP91	2/6	U25	6/-	6X4	5/-
EL33	5/-	U26	6/-	6UW7	4/6
EL34	5/6	U191	7/-	4A57	10/-
EY1	3/-	U301	5/-	30F5	5/-
EY86	4/6	UAF42	5/-	35Z3	5/-
EZ80	4/-	U341	5/-	35Z4	5/-
KT32	4/-	U384	7/6	30P11	7/-
KT36	7/-	UCF80	7/6	PL12	5/-
PCX4	4/-	UC42	2/6	30P11.3	6/6
PCF80	4/-	6C9	10/-	30P11	7/-
PCP82	4/6	8X5	4/6	6C01.2	7/-
PC182	5/-	6F1	2/6	6L19	6/6
PL83	5/6	6F12	2/6	50C106	16/-
PL44	6/6	6F13	5/-	6C106G	12/-
PL33	7/-	6F14	5/-		

EB80 in a batch of 12 for 20/-. EC130 in a batch of 6 for 20/-. Postage and Package is 6d. on each valve.

TV TUBES, an ex equipment set tested, CRM14 17/6 each.

MULLARD 14 in. tubes of all types. AW and MW. All 17/6 each. P. & P. 10/6.

SPEAKERS EX EQUIPMENT, 5 in. 5/-, 7 in. 8 4 in. 6/-, 6 in. 6/6, 8 in. 7/-, P. & P. 1/6 each.

JAG ELECTRICS & CABINET MAKERS Ltd

2c Church Street, Slough, Bucks.

TRADE INQUIRIES INVITED

HARVERSON Surplus Co. Ltd.


Also see facing page

SPECIAL OFFER!

MARCONI QUARTZ CRYSTALS TYPES ZHB

Glass encapsulated, 2 wire lead out. Size 1 1/4 in. high x 3/4 in. dia. Following frequencies (Kc/s only available):
139583, 139646, 137088, 137711, 138333, 138966, 139553, 140211, 140833, 141466, 142088, 142711, 143333, 143966, 144599
6/- each. P. & P. 1/- per crystal, 3 or more Post Free.

3-VALVE AUDIO AMPLIFIER. MODEL HA34

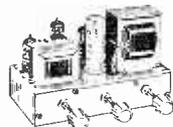

Designed for Hi-Fi reproduction of records A.C. mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2 in. w x 4 in. d x 4 1/2 in. h. Incorporates EC83R, EL84, E280 valves, heavy duty double-wound mains transformer and output transformer matched to 3 ohm speaker, separate Bass, Treble and volume controls. Negative feedback line. Output 41 watts. Front panel can be detached and leads extended for remote mounting of controls.

The HA34 has been specially designed for us and our quantity order enables us to offer them complete with knobs valves. **£45.0 P. & P.** etc., wired and tested for only **£45.0 P. & P.**

TWO VALVE AMPLIFIER, similar to above but using PL182 and E280 with tone and volume controls. Output 3 watts. PRICE 75/-, P. & P. 4/-.

4-SPEED PLAYER UNIT BARGAINS

All Brand New in Makers' original Packing
SINGLE PLAYERS
B.S.R. TU/12..... £3.10.0 Carr. 3/5
B.S.R. GU7 with unit mounted pick-up arm..... £4.18.8 Carr. 4/-

AUTO CHANGERS

B.S.R. UA14..... £6.2.6
Latest B.S.R. UA16..... £7.9.8
LATEST GARRARD AUTO-SLIM. With heavy duty, 4-pole motor. FEW ONLY £7.7.0. (Standard Auto-Slim £6.17.6). Carr. 5/- on each.

NEW CARTRIDGE

BARGAINS!

RONETTE STEREO 105 CARTRIDGE, Stereo/PL178. Complete with two sapphires. Original list price 67/9. **OUR PRICE 24/-**. P. & P. 1/-
COLLARO HI-FI STEREO TO CARTRIDGE, Type "C". Complete with universal bracket and shell for stereo, LP and 78. Original list price 59/8. **OUR PRICE 25/-**. P. & P. 1/-.

SPECIAL TRANSISTOR BARGAINS

ALL BRAND NEW
GET 15 (Matched Pair) 15/-
OC71 5/- OC72 6/- OC76 6/-
PXA101 6/6 XA102 6/6 V15/10p 12/6
Set of Mullard 6 transistors, OC44, 2—OC45
OC81D matched pair OC81, 25/-


EDISWAN MAZDA

R.F.J. Pack: 1—PXA102 Mixer: 2—PXA101 I.F. Amp.; (Equip. OC44 and OC45)..... 10/6
R.F. 2 Pack: 2—PXA101 I.F.;—PXA102 Osc.;—1—PXA102 Mixer..... 12/6
L.F.o Pack: Consisting of PCB113 Driver; Matched pair PCB113 mounted complete with heat sinks (Equip. OC81D and OC81D)..... 12/6
ALL TRANSISTORS POST FREE

STEREO AMPLIFIER

Incorporating 2 EC182s and 1 E280, heavy duty double-wound mains transformer. Output 4 watts per channel. Full tone and volume controls. Absolutely complete.

FEW ONLY

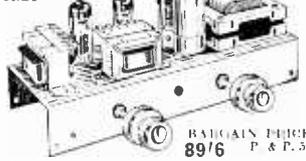

Also available complete with two x 5in. Speakers for only **£5.10.6**. P. & P. 6/6.

SPECIAL PURCHASE!
TURRET TUNERS
 by famous maker
 Brand new and unused. Complete with PC834 and PC830 valves. 34-38 Mc/s I.F. Sections for Channels 1 to 5 and 8 and 9. Circuit diagram supplied.
ONLY 25/- each. P. & P. 26.



F.M. TUNER HEAD
 A personality tuned tuner head by a famous maker, supplied without valve (ECC85) and drum and spindle, 13/6 plus 1/9 P. & P. Valve 8/6 extra. Drum and spindle 3/6 extra.

GÖRLER F.M. TUNER HEADS
 107 Mc/s I.F.P.
 15/- plus 1/9 P. & P. (ECC85 valve, 8/6 extra).

E.M.I. 4-speed Player and P.U.
FURTHER HUGE PURCHASE enables us to offer these **67/6** P. & P. at 4/6.



Heavy 8 1/2 in. metal turntable. Low flutter performance 200/250 v. shaded motor with tap at 45v. for amplifier valve filament if required. Turnover LP/78 head.

RECORD PLAYER AMPLIFIER
 2 valve (E280, E01822, A4), mains, 3 watts output, rosette built, tested and complete with valves and output transformer. Size 7 in. w. x 2 1/2 in. d. x 5 1/2 in. h. 55/6. P. & P. 3/-.
 Suitable speakers: 6 1/2 in. 15/- P. & P. 1/-; 10 x 5 in. 26/-. P. & P. 1/6.

SPEAKER & CABINET FABRICS
 Original, or Red and Gold Vynair for speaker and cabinet covering, also Red BeXine for cabinet covering only. All 4 1/2 in. wide and usually sold at 35/- yard.
OUR 13/6 per yard plus P. & P. 1/9. (Minimum order 1 yard). Send S.A.E. for samples.

HARVERSON'S F.M. TUNER Mk. I

● F.M. Tuner head by famous maker.
 ● Guaranteed non-drift.
 ● Per-tuneability tuning.
 ● Frequency coverage 88-160 Mc/s. ● OAS1 balanced diode output. ● Two I.F. stages and discriminator. ● Attractive m.e.c. and gold dust (7 x 3 in. glass). ● Self powered, using a good quality mains transformer and valve rectifier.
 ● Valves used ECC85, two EBF80s, and E280 (optional). ● Fully drilled chassis. ● Size of completed tuner 8 x 6 x 5 1/2 in. All parts sold separately. Set of parts if purchased at one time £5.19.8, plus 50/- P.P. and inc. Circuit diagram and instructions 1/6 post free. Mark II Version as above but complete with magic eye, front panel and brackets. 26.12.8. P. & P. 8/6.
 Mark III Version as Mark I but with output stage (ECL22) and tone control. 27.7.0. P. & P. 8/6.
 Handsome Metal Cabinets. Choice of Grey, Black or Green. To fit Mark I, 25/-. P. & P. 2/6. To fit Mark II, 17/8. P. & P. 2/6.

6 TRANSISTOR AND DIODE SUPERHET
 A first-class 2 wavebands transistor superhet. ● Printed circuit panel (size 4 1/2 x 2 1/2 in.). ● 3 pre-aligned I.F. transformers. ● High-gain Ferrite and aerial. ● All First-grade transistors. ● Car aerial winding. ● Push-pull output. ● All parts supplied with simple instructions. All parts sold separately. Set of parts if purchased at one time. **ONLY £4.50** P. & P. 2/6

35 OHM SPEAKERS
 Suitable for use with above 2m. Goodmans. Ideal replacement for most pocket portables 8/6. 3 1/2 in. 12/6; 5 in. 17/6; 7 x 4 in. 21/-. P. & P. 1/6 per speaker.

Portable CABINET
 Size approx. 9 1/2 x 6 1/2 x 3 1/2 in. Suitable for above using 3 1/2 in. speaker, 25/-. P. & P. 2/6.

COIL AND TRANSFORMER SET FOR TRANSISTOR SUPERHET
 3 I.F. transformers, one oscillator coil, one driver transformer and wound Ferrite aerial (meat., long, and aerial coupling). 38/6 complete, plus 1/-, 6 transistor printed circuit board to match 8/6 post 9d. Circuit diagram 1/6 extra.

QUALITY RECORD PLAYER AMPLIFIER
 A top quality record player amplifier. Size 7 in. w. x 2 1/2 in. d. x 5 1/2 in. h. This amplifier which is used in a 29 in. record player employs two XLS ELSA E280 valves. Bass, treble and volume controls. Complete with output transformer matched for 3 ohm speaker.
PRICE 69/6 P. & P. 3/6
DITTO. Mounted on board with output transformer and 6 1/2 in. speaker.
Complete at 89/6 P. & P. 4/6.

QUALITY PORTABLE RECORD PLAYER CABINET
 Light motor hood. Will take above amplifier and B.S.R. or GARRARD Autochanger or Single Record Player Unit. Size 18 x 14 x 5 1/2 in.
PRICE £3.9.6. Carr. 5/-.

HIGH GAIN 4-TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT Type TAI


● Peak output in excess of 1 1/2 watts. ● All standard British components. ● Built on printed circuit panel size 5 x 3 in. ● Generous size Driver and Output Transformers. ● Output transformer tapped for 4 ohm and 15 ohm speakers. ● Transistors (GET114 or S1 Mullard OC81D and matched pair of OC81 o/p). ● 9 volt operation. ● Everything supplied, wire battery clips, solder, etc. ● Comprehensive, easy to follow instructions and circuit diagram 1/6 (Free with Kit). All parts sold separately. Also ready built and tested, 52/8. P. & P. 2/6. A pair of TAI's are ideal for stereo.



SPECIAL PRICE 45/- P. & P. 2/6.

10/14 WATT HI-FI AMPLIFIER KIT

A stylish finished monaural amplifier with an output of 14 watts, from 2 EL84s in push-pull. Super reproduction of both music and speech, with intelligible bass, separate inputs for tape and gram, allow records and announcements to follow each other. Fully shielded section wound output transformer to match 3-15 ohm speaker and 2 independent volume controls and separate bass and treble controls are provided giving good cut and cut. Valve line-up 2 EL84s, ECC85, EBF80 and E280 rectifier. Simple instruction booklet 1/6. (Free with parts). All parts sold separately. **ONLY £6.19.6** P. & P. 6/6. Also available ready built and tested complete with standard input jack sockets. **£8.15.0** P. & P. 6/6.

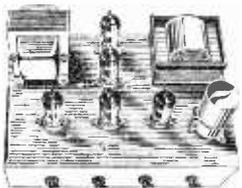

BRAND NEW 3 OHM LOUDSPEAKERS

2 1/2 in. 12/6; 5 in. 12/6; 6 1/2 in. 15/-; 8 in. 21/-; 10 in. 25/-; 12 in. 27/6
 E.M.I. 2 1/2 in. tweeter ... 10/6
 12 in. 15 ohm ... 30/-
 10 in. x 4 in. ... 20/-
 Latest type E.M.I. 1 1/2 x 8 in. with high flux ceramic magnet, 11,000 gauss. Aluminium centre cone. 10 watts. 50 ohm to 10 Kch. 48/- P. & P. up to 6 in. 1 1/2 over 6 in. 2/6 per speaker.

AMPLIFIER CARRYING CASES BRAND NEW

Strongly made wooden construction, tough vinyl covered, complete with carrying handle. Overall size 12 1/2 in. wide x 9 in. deep x 8 in. high with sloping front panel. Weight only 4 1/2 lbs. Ideal for our 10/14 watt amplifier and many others.
BARGAIN PRICE 28/6 P. & P. 4/-

AMPLIFIER ON PRINTED CIRCUIT BOARD



TAPE DECKS COLLARO STUDIO DECK B.S.R. MONARDECK

(single speed) 3 1/2 in. per sec., simple control uses 3 1/2 in. spools, 28.10.0 plus 6/- extra. (Tape extra on both).

Superior CABINET To take 8 x 5 in. speaker, with motor board will accommodate BSR UA14 or UA16. 23.9.6. Carr. 5/6, speaker 10/6 extra. P. & P. 1/6 extra.
LARGE CABINET Similar to above with 3 ohm speaker. 23.9.6. Carr. 5/6.

★ BARGAIN CORNER ★

ACOS CRYSTAL MIKES. High amp. For desk or hand use. High sensitivity. 18/6. P. & P. 1/6.
TSL CRYSTAL STICK MIKE. Listed at 45/-. Our price 18/6. P. & P. 1/6.
CARBON MIKE INSERTS. Brand new. 2 1/2 in. dia. 3/6. P. & P. 3d.
STANDARD COILVERN 50K W W Project Pats. 2 for 4/-. P. & P. 1/6.
T.C.C. SUPPRESSOR CONDENSERS. 250 v. A.C. 0.001 - 0.005 u.F. In tubular can 1 1/2 in. long x 1/2 in. dia. 2 for 3/-. Post free.

MAINS TRANSFORMER
 Drop thru type. Tapped primary 110v., 200v., 240v., 320-0-320v. at 80mA and 6.3v. at 3 amps. Generous core. Stack size 3 1/2 x 2 1/2 x 1 1/2 in. Weight 4 lbs. **ONLY 15/-. P. & P. 3/6.**

SPECIAL SPEAKER BARGAINS!
FEW ONLY 6 x 4 in. 3 ohm Speakers. Only 9/- P. & P. 1/6 per speaker.

8 x 5 in. 3 ohm SPEAKERS BY WELL KNOWN MAKER Unrepeatable at only 10/6 each. P. & P. 1/6 per speaker. A pair of these are ideal for Stereo.
ROLA CELESTION. approx. 9 in. x 6 in. 3 ohm. Middle register speaker. 10/6. P. & P. 2/6.

◀ LOOK OPPOSITE FOR MORE BARGAINS

HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, S.W.19 CHERRYWOOD 3985/6

Open all day Saturday Early closing Wed., 1 p.m.

A few minutes from South Wimbledon Tube Station. (Please write clearly)
PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.
SENTS STAMPED ADDRESS ENVELOPE WITH ALL ENQUIRIES

The
**AMATEUR RADIO
HANDBOOK**

Third Edition

Contents include Fundamentals, Valves, Semi-conductors, H.F. Receivers, V.H.F./U.H.F. Receivers, H.F. Transmitters, V.H.F./U.H.F. Transmitters, Keying and Break-in, Modulation, Single Sideband, Frequency Modulation Propagation, H.F. Aerials, V.H.F. Aerials, Noise, Mobile Equipment, Power Supplies, Interference, Measurements, Operating Technique and Station Layout, the R.S.G.B. and General Data.

Bound in maroon linson buckram - - 544 pages
700 diagrams and 100 half-tones

PRICE 34/- (Postage and packing 2/6)
(£5.50 post paid U.S.A. and Canada)

Obtainable from leading booksellers or
(Dept. P.W.5.)

**RADIO SOCIETY OF
GREAT BRITAIN**

28 Little Russell Street, London, W.C.1

EXPRESS ELECTRONICS

32 SOUTH END CROYDON SURREY

TEL. CRO 9186

VALVES NEW TESTED AND GUARANTEED
FOR THREE MONTHS

1C1	5/8 6BE6	7/-	12AU7	6/9	DH142	8/8	EP91	4/-	PL83	7/6
1C2	7/8 6BH6	5/9	12AX7	6/9	DH150	10/-	EP92	5/8	PY33	8/6
1C3	7/8 6BJ6	5/9	12BE6	4/6	DK91	5/6	EL41	9/8	PY81	6/9
1F1	7/6 6BR7	8/9	12BH7	10/8	DK96	7/8	EL84	7/-	PY82	7/8
1F3	2/- 6BW9	9/8	12K8GT11/-	DL92	5/8	EM85	10/-	PY83	7/8	
1FD1	7/6 6BW7	7/8	12Q7GT	7/8	DL94	6/-	EY31	7/8	R19	6/8
1FD9	5/8 6D2	4/-	12SN7	4/6	DL98	7/8	EY31	10/-	SSA1	9/8
1P1	7/6 6FP12	4/-	16A5	9/8	EH91	4/-	EZ40	5/8	U52	7/8
1P10	5/8 6H6GT	2/-	19A5	9/8	EH41	7/8	EZ80	6/-	U76	7/8
1P11	6/- 6J7GT	7/8	25L6GT	5/-	EBF80	8/8	EZ81	8/9	U78	5/-
1R5	5/8 6K7G	5/8	30C1	7/8	EC81	4/-	HV12	9/8	U142	7/8
1S5	5/8 6K8G	6/-	30L1	7/8	EC82	6/9	KT33C	8/-	UBM1	8/8
1T4	2/- 6Q7G	5/8	35L6GT	7/8	EC83	8/9	KT95	13/6	UC142	8/8
1U5	5/8 6SL7GT	6/-	35W4	8/8	EC84	6/8	N17	5/8	UF41	8/8
3Q4	5/8 6SN7GT	7/8	35Z4GT	8/-	EC85	7/8	N18	5/8	UL41	8/8
384	5/8 6V6G	7/8	5763	7/8	ECF80	6/8	N19	6/-	UY41	8/8
3V4	6/- 6X4	5/8	80	8/-	ECF82	7/8	N709	7/-	W17	2/-
5Y8GT	5/- 6X5G	5/8	19AF91	5/8	ECH42	9/-	PC84	7/8	W78	4/8
EZ40	6/8 7X4	5/-	19AF96	7/8	ECH81	10/-	PCF80	7/8	W142	8/8
6AK6	5/8 8D3	4/-	DC90	12/8	ECL90	6/8	PCF82	6/8	X17	5/8
6AL5	4/- 9Y7	9/8	DF91	2/-	ECL92	7/8	PCL82	6/8	X142	9/8
6AM6	4/- 12AD6	7/8	DF96	7/8	EF41	9/-	PL84	5/8	X150	9/-
6AT6	5/- 13A18	10/-	DH76	7/8	EP80	8/-	PL81	8/8	Z77	4/-
6BA6	5/- 12AT7	4/-	DH77	5/-	EP86	9/-	PL82	7/-	ZD17	5/8

**ASK FOR RESISTOR AND CAPACITOR COLOUR CODE
FREE WITH EVERY PURCHASE**

High Stability Resistors 1W 5% 50Ω to 1M. 9d. Midret Ceramics 500 v. 9d. Coax. Super Quality 1in. 6d. 9d. Plus 9d. Sockets 9d. Silicon H.T. Resist. 250 v. 300 mA 1in. x 1in. 8/6. Contact Cooled 250 v. 50 mA 6/6. 85 mA 8/6. NEW TRANSISTORS BY MULLARD. OC19, OC26, OC66, 25/-; OC34, OC45, 5/-; OC76, 6/-; O77, 5/-; OC72, 6/-; OC72 Matched pair, 12/-; OC74, OC75, OC78, 7/8; OC81, 6/-; D94 Matched pair, 12/-; OC170, OC171, 7/8.

VALVES MATCHED IN PAIRS

FLM4 27/8. EL84, 15/-; N709 15/-; 6V6G 15/-; 6AW6 14/- per pair. Push-Pull O.P. Transformer for above 315Ω 14/6. P. & P. 1/6. 12in. P.M. Speakers 3Ω 24/6. Baker's "Sehurst" 12in. 15Ω 15W Staiwart £5.50. 12in. Stereo Model £8.15.0.

SETS OF VALVES

DR91, DF91, DAF91, DL92 or DL91, 17/6 ECH42, EF41, EBC41, DK96, DF96, DAF96, DL96, 28/8 EL41, EZ40, 37/8
FR8, 6K7, 6Q7, 6V6, 3Z4 or 6X5G, 19/6 EY142, EF11, ER341,
1B2, 1T4, 1S5, 384 or 3V1, 17/6 UL41, 1Y11, 35/-
Postage and packing 6d. Over £1 post free. C.O.D. 4/-

● **SCOOP! Transistor Tape Recorder.** The best obtainable by very famous manufacturer. Brand new, boxed, guaranteed. Reduced from 12 gns. **OUR price £7.10.0.** P.P. 3/6. Complete with microphone, tape, batteries and operational booklet. Features push-pull amplifier, two motors, single switch operation, pause, speed, wind, rewind, record, play back. Can be used in any position, indoor or outdoor.

**DO IT
YOURSELF**

Famous Autochanger or Single Player Units supplied with brand new, two-tone, de-luxe portable cabinets, 17 x 15 x 8½in. Strong carrying handle, gilt finish clips and hinges are used by famous make for 22 gn. model. Ready cut out motor board, 14 x 13in. Front baffle 7 x 4in. High flux loudspeaker and 3 watt amplifier. Amplifier ready built on metal chassis with output transformer, volume and tone controls. All items fit together perfectly. Special instructions enable assembly in 30 minutes. Only 5 wires to join. 12 month's written guarantee. Available separately or package deals as below.

L.K. PRICES FOR COMPLETE KITS:

Autochanger Kits as above

B.S.R. U.A.14 £10.17.6 P.P. 5/6
Garrard Autoslum £11. 7.6 P.P. 5/6

Single Player Kits as above

Garrard S.R.P.10 £10.12.6 P.P. 5/6
E.M.I. Autostop £10.17.6 P.P. 5/6
Individual Prices for those who wish to purchase separately.
Record Player Cabinet with Cut-out Board... £2.15.0 P.P. 3/6
Amplifier with 7 x 4in. speaker £3.10.0 P.P. 2/6

Auto-changers

B.S.R. U.A.14 £5.10.0 P.P. 5/6
Garrard Auto Slim £6.15.0 P.P. 4/6

Single Players

E.M.I. Auto-Stop £5. 7.6 P.P. 4/6
Garrard S.R.P.10 £5. 5.0 P.P. 4/6
E.M.I. Separate Pick-up £3.0.0 P.P. 3/6

Transcription Units—Stereo Head—Mono

Garrard 4 H.F. £14.10.0 P.P. 5/-
Phillips A.G.10/16 £12. 0.0 P.P. 5/-
Garrard A.T.6 £9.19.6 P.P. 5/-

● **SCOOP! Tapes.** We are reducing our huge stocks of Paper, Acetate, Mylar. All sizes. Spare spools also available. Let us quote you at our expense. Special Prices for lots of 1 doz. and over.

● **SCOOP! A Limited Number only. Tape Decks by B.S.R. Latest Model, AC/200/240v.** Brand new and boxed. **Our price £6.10.0 only.** P.P. 4/6.

Please send for complete list of Tape Decks.

THE CHEAPEST, THE BEST, THE QUICK-EST SERVICE.

IF NOT ADVERTISED IT IS STILL IN STOCK

**MAIL ORDER ONLY — TO ADDRESS
OPPOSITE PLEASE**

● **SCOOP! 1964 Radiogram Chassis. Stereo,** 3 wave bands, long medium and short. 5 watts per channel. 6 valves. Latest Mullard. AC 200-250v. Ferrite aerial. Glass dial, horizontal wording, concentric controls. isolated chassis size 13½ x 9in. high x 5in. deep. Product of famous national manufacturer. Brand new and boxed. Maker's guarantee. **OUR price £13.10.0.** List price £19.8.0. P.P.5/6. *Our chassis list quotes prices the keenest in the trade. We are main agents for the complete range of Brittamer chassis and amplifiers. Brittamer makers of radiogram chassis to the top names in radio.*

● **SCOOP! A Stereo Amplifier** by world famous amplifier designers. 5 watts per channel. fascia panel in black and silver. Assembled, tested, guaranteed. Even leads and plugs supplied. Maker's package unopened.

OUR price £7.10.0. List price £15.15.0. P.P. 5/6. *Please send for our Amplifier and Hi-Fi lists they are FREE. Our prices the most competitive in the trade.*

● **SCOOP! Microphones.** Complete Lead Coax Plug, dynamic. Brand New. Our Price, 5/- only. P.P. 1/6.

Build a Record Player and save Pounds

The Cheapest Way The L.K. Way

● **SCOOP! 10in. Speakers** by W.B. of Mansfield. A beautiful Hi-Fi speaker, magnet flux density, 12,000 lines gauss. Brand new in maker's carton. Fully guaranteed. **OUR price 42/- only.** P.P. 1/10. *Please send for our Speaker Lists. Our prices are the most competitive in the trade.*

● **SCOOP! B.S.R. U.A.14 Autochangers.** Brand new and boxed. Wired for stereo. Note **OUR price £5.7.6.** P.P. 5/-.

● **SCOOP! Garrard Autoslims.** Brand new and boxed. Wired for stereo. Note **OUR price £6.0.0 only.** P.P. 5/-.

● **SCOOP! Diodes**—over 1,000,000 in stock—ideal substitute O.A.81 vision detector. Note **OUR price £1.0.0 per 500.** P.P. 2/-. (In 500 lots only). All guaranteed.

● **SCOOP! Now available our Short Wave Receiver Mk. II** in kit form. A wonderful little set, dry battery operated. Radio Australia received in Surbiton, Surrey at reasonable strength. Coverage 3.5Mc/s to 12Mc/s, 11Mc/s to 30Mc/s. Note **OUR price 42/- only.** All components guaranteed. P.P. 2/3.

● **SCOOP! Record Player Amplifier.** Product of national manufacturer. 2 valve, A.C. mains, output 3 watts. Complete with speaker, output transformer, valves, knobs, etc. Fully wired, tested and guaranteed. Mounted on baffle board ready for cabinet. Note **OUR price 50/- only.** P.P. 2/-.

TRANSISTOR SECTION

● **SCOOP! A first-class 2 wave-band 6 transistor superhet chassis** by world famous manufacturer. Fully built, aligned, tested, guaranteed. Full coverage long and medium waves.

Note **OUR price £4.4.0 only.** Suitable speaker 10/6. A few cabinets can be supplied at 22/6 each.

OUR price for the package deal £5.5.0 only.

● **SCOOP! As above, 7 transistor.** **OUR price £4.15.0 only.** Suitable speaker 10/6, Cabinet (very attractive), 22/6.

OUR price for the package deal £5.14.0 only.

● **SCOOP! As above, 8 transistor.** **OUR price £5.4.0 only.** Suitable speaker 10/6 Cabinet (very attractive two-tone), 22/6.

OUR price for the package deal £6.3.0 only.

● **SCOOP! 'Noton' Mains Power Pack Kit** for transistor radios. Boosts and generally extends life of old batteries, in two-tone plastic case. Assembled in 1 hour. Miniature size, 4 x 2 x 1½in. Normal output 9v. 100mA. Full wave germanium diodes. Cartridge fuse. Runs radio direct from mains. Complete kits of parts with full instructions. all parts guaranteed.

OUR price 30/- only. Ready assembled 40/-, P.P. on all the above, 2/-.

● **SCOOP! Set of 6 transistors and diode.** Brand new in presentation case with circuit. **OUR price 15/-.** P.P. 1/-.



L.K. ELECTRONICS

27 OLD BOND STREET, LONDON, W.1.

THE TRIPLETONE HI-FI MAJOR

Price £15.18.9 Complete

Guaranteed for 12 months.

QUALITY AMPLIFIER

- Power Output (R.M.S.) 12 watts
Distortion 0.15%
Negative Feedback 32dB
Inputs for 10 watts: Gram: 250mv. Mic: 10mv.
Bass Control: Variable +18dB to -18dB at 30 c/s.
Middle Control: Variable +15dB to -15dB at 400 c/s.
Trebble Control: Variable +18dB to -18dB.
* Mic. Pre-amp Stage
* Boost on Treble, Middle and Bass
* Mixing on Mic. and Gram
* Power for AM or FM Feeder
* Push-Pull Output Stage
* Plays 78, 45 and 33 1/2 Records
Size: 12" x 5 1/2" x 6 1/2" high.
Valves: 12AX7, 12AX7, EL84, EL84, E281.
Output Impedance 16 or 15 ohms
Frequency Response: 20-20,000 c/s.
Hum and Noise -80dB
Mains: 200-250 volts A.C. Fully isolated.
De Luxe Case: 14" x 9" x 7 1/2", 30/- extra.

New Boxed VALVES 90-day Guarantee

Table with 4 columns: Valve type, Price, Valve type, Price. Includes items like 0Z4, 1R5, 1S6, 1T4, 2X2, 384, etc.

NEW ELECTROLYTICS

Table with 3 columns: Tubular, Tubular, Can Types. Includes items like 1/350V, 2/3 100/25V, 4/350/25V, etc.

TELESCOPIC CHROME AERIALS, 15 to 43in., 8/6.
TRIPLEXERS Bands I, II, III, 12/6. COAX PLUG, 1/-
LEAD SOCKET, 2/-. PANEL SOCKETS, 1/-
OUTLET BOXES (surface or flush), 4/-
BALANCED TWIN FEEDER 78, 6d. 80 or 300 ohms.
TWIN SCREENS, 100 pF, 7d. 80 ohms out.
Wirewound Ext. Speaker Control, 10 Ohm 3/-. 25 Ohm 6/6.
WIRE-WOUND POTS, 3 WATT. Pre-set Min.
TV Types. All values to 10 ohms to 20 K., 3/-
30K., 4/- Carbon 30 K to 2 meg., 8/-.
WIRE-WOUND 4 WATT. Pot. Long spindle.
Value, 30 ohms to 50 K., 6/6; 100 K., 7/6.
PHILIPS TRIMMERS, 0.10 pF., 3.30 pF., 1/-.
TRIMMERS, Ceramic, 30, 50, 70 pF., 9d., 100 pF., 15d.
pF., 1/3; 200 pF., 1/6; 500 pF., 75d. pF., 1/9.
TV etc. TRIMMER, 1000 pF. with knob, 2/-.
RESISTORS, Preferred values, 10 ohms to 10 meg.,
1 w., 4d.; 1 w., 4d.; 1 w., 6d.; 1 1/2 w., 8d.; 2 w., 1/-.
High Stability, 1 w., 1/2; 2/-. Preferred values
100 to 10 meg. Ditto 1/2, 1/3, 1/4, 1/5, 1/10 to 22 meg., 9d.
RESISTORS, C71, 3/6; C72, 2/6; C73, 1/6.
5 watt } WIRE-WOUND RESISTORS } 1/3
10 watt } 10 ohms-10,000 ohms } 2/-
15 watt } }
12.5 K to 25 K 10 w. ... 3/-

Volume Controls 80 ohm COAX Cable
Linear of Log Tracks Semi-air spaced 4in.
Long spindles, 15/6 40 yds. 25/-
5 K ohms to 2 Meg. 6d yds. 25/-
S. 3 1/2 p. 4/6
Stereo L ines, D.P. 4/6
1m. log. + 1m. A. log. 7/8
Ideal 625 lines
Low loss 5dB
100ft. 50 Mc/s 1/6 yd.

MAINS TRANSFORMERS 200/250 v. A.C.
Voltage 2/- each transformer.
STANDARD, 250-0-250, 50 mA, 6.3 v. 3.5 A.
Tapped 4 v. 4 A. Rectifier, 6.3 v. 1 A., 5 v.
2 or 4 v. 2 A. 22/6. ditto, 350-0-350 ... 29/6
MINIATURE 200 v. 20 mA, 6.3 v. 1 A. 10/6
MIDGET, 220 v. 35 mA, 6.3 v. 2 A. ... 15/6
SMALL, 230-0-230, 45 mA, 6.3 v. 2 A. ... 17/6
STD. 250-0-250, 65 mA, 6.3 v. 3.5 A. ... 17/6
HEATER TRANS. 6.3 v. 1 1/2 A. ... 7/6
Ditto, tapped 1.4, 2, 3, 4, 5, 6.3 v. ... 8/6
Ditto, wcc. 6.3 v. 4 amp. ... 10/6
GENERAL PURPOSE LOW VOLTAGE, 2 amp.
3, 4, 5, 6, 8, 10, 12, 15, 18, 24, 30 v. ... 22/6
AUTO TRANSFORMERS, 150 v. ... 22/6
0, 110, 200, 230, 250 v. 500 w. ... 82/6
MULLARD "510" Mains Transformer ... 38/6
PARMCO MAINS TRANSFORMER. The
ratings can safely be doubled. Primary 0-110-
210-230-250 v. H.T. 300-0-300 v. 30 mA. L.T.
6.3 v. 1.8 amp. ... 17/6

INTERVAL TRANSFORMERS, 3:1 or 5:1, 9/-
O.P. TRANSFORMERS Heavy Duty, 5/6. Multi-
plication, 7/6. Multitap heavy duty push-pull, 10 w.,
15/6. Battery 4/6. Sub. min. 5/8.
10w. O.P. matching trans., 3, 7, 15 Q, 12/6.
I.F. CHOKES 15 10H., 50-65 mA. 3/-; 10H., 55 mA.
10H., 130 mA, 10/6.
TINNED COPPER WIRE 16 to 22 swg., 1lb., 3/6.
ENAMEL COPPER WIRE 16-22, 2/9; 24-30, 3/6;
32-40, 4/6. D.C. 25, 34, 30 swg., 2oz., 3/6.

I.F. TRANSFORMERS 7/6 pair
465 Kc/s Slug Tuning Miniature Can, 2 x 1 1/2 in.
High Q and good bandwidth. Data sheets.
Standard size Weyrad, 10/6 pair.

FULL WAVE BRIDGE SELENIUM RECTIFIER:
2, 6 or 12 v. 1 1/2 amp., 8/9; 2 A., 11/3; 4 A., 17/6.
CHARGER TRANSFORMERS. Tapped input 200V,
250 v. for charging at 2, 8 or 12 v. 1 1/2 amps., 15/6;
2 amps., 17/6; 4 amps., 22/6. Circuit included.
4 AMP CAR BATTERY CHARGER with am-
meter, Leads, Fuse Case, etc., for 6 v. or 12 v., 6/9

BOOKS list S.E.A.
Boys' Book of Crystal Sets. ... 2/6
"W.W." Radio Valve Data. ... 6/-
High Fidelity Speaker Enclosure ... 5/-
Valve and TV Tube Equivalents ... 9/6
TV Fault Finding ... 5/-
Mullard Amplifier Manual ... 2/6
Radio Valve Guide, Books 1, 2, 3 ... 8/6
4 or 5 ... 5/- each
Transistor Superhit Receivers ... 7/6
Practical Radio Inside Out ... 3/6
Master Colour Colour Guide ... 7/6
Transistor Controlled Models ... 7/6
Principles of Colour TV ... 16/-
International Radio Stations ... 2/6

4 TRANSISTOR PUSH-PULL AUDIO
size 3 x 1 1/2 in. AMPLIFIER
A ready built miniature push-pull amplifier with
Driver and output transformers, 4 transistors.
Ideal for use with record players, intercoms,
BABY ALARMS etc. Complete with full
Price 47/6. Instructions and circuit.
9v. Batt. 2/3. 2in. Speaker 15/-
Toggle Switches, S.P. 2/-; d.p. 3/6.
d.p.d.t. 4/-. Min. Slide d.p.d.t. 3/6.

1964 RADIOGRAM CHASSIS
THREE WAVEBANDS FIVE VALVES
S.W. 16 m - 30 m. LATEST MCZ80
M.W. 200 m - 200 m. ECR51, EP90, EBC51,
1.W. 800 m - 2,000 m. EL84, EZ80
12-month Guarantee.
A.C. 200/250 v. 4-way Switch-Short-Medium,
Long/Gram. Ferrite Aerial A.V.C. and Negative
feedback, 3 ohm out, 5 watts. (Glass
dial, horizontal wording, size 13in. x 4in.
Aligned and calibrated. Isolated Chassis, size
13 1/2 in. x 9 in. high x 5 1/2 in. deep.
£9.15.6 Carr. & Ins. 4/6

BAKERS SELHURST LOUDSPEAKERS



- 12in. Baker, 15w. 24watt
3 or 15 ohms, 40-15,000
c/s. ... 5.62s.
12in. Stereo, Foam sus-
pension, 12w., 35-16,000
c.p.s. ... 7.62s.
12in. Standard H.D. 20w.
40-14,500 c.p.s. ... 7.62s.
12in. De Luxe 15w. 25-
17,000 c.p.s. ... 9.06s.
12in. Base 25w. 20-18,000
c.p.s. ... 12.82s.
15in. Auditorium, 35w., 20 c.p.s. to 12 kc/s. Idea
Guitars, etc., 15.92s.

LOUDSPEAKERS P.M. 3 OHM. 24, 3, 4, 5in.,
7 x 4in., 15/6; 64in. Rola, 16/6; 8in. Pleacey, 17/6;
9 x 6in., 8 x 5in., 21/-; 10 x 6in., 22/6; 10 in. Rola,
30/-; 12in. R.A., 30/-; EMI double cone, 13 x 1 1/2in.,
45/-
STENTORIAN HF101, 10in. 3 to 15 ohms, 10w. 87/6;
8in. HF42, 72/-; Tweeter, T359, 30/-; Cross-over
CX3000 30/-
EXTENSION SPEAKER CABINETS, 5in., 15/6;
9 1/2in., 18/6; 8in., 19/6; 10in., 26/6; 12in., 30/-

C.R.T. BOOSTER TRANSFORMERS
for heater cathode short circuit, or
tubes with failing emission. Full
instructions supplied, mains input.
Type A optional 25% and 50% boost
2v. or 4v., 6.3v. or 10v., or 12.5v.
State voltage required. PRICE 10/6.

TWIN GANG TUNING CONDENSERS, 385 pF.
miniature 1in x 1 1/2in., 10/-; 500 pF Standard
with trimmers, 9/-; midget, 7/6; with trimmers, 9/-
500 pF slow motion tuning, standard or midget, 9/-
Transistor gang 208 + 176 pF with trimmers, 10/6.
SMALL 3 gang 100 pF, 17/-; SINGLE 300 pF, 7/6.
SINGLE 10 pF, 25 pF, 50 pF, 75 pF, 100 pF, 160 pF
5/6. Mold dielectric 100, 300, 500 pF, 3/6.
CONDENSERS. New stock. 0.001 mfd, 7 kv.
1/3C, 5/6; D20, 20 kv, 9/6; 0.1 mfd, 7 kv, 9/6;
Tubular 330 pF, 0.001 to 0.05 mfd., 9d.; 0.1, 1/-;
0.25, 1/6; 0.5/350 v., 1/6; 0.1/250 v., 9d.; 0.1/2,000 v.,
0.1/1,000 v., 1/8; 0.1 mfd, 2,000 volts, 3/6.
CERAMIC COND. 500 v. 0.3 pF to 0.01 mfd., 9d.
SILVER MICA CONDENSERS, 10% 1 pF to 500 pF,
9d.; 500 pF to 3,000 pF 1/- Close tolerance
(±1 pF) 2.2 pF to 47 pF, 1/- Ditto 1% to 50 pF
to 315 pF, 1/-; 1,000 pF to 5,000 pF, 1/9.

465 Kc/s SIGNAL GENERATOR
Price 10/6, ready made with valve ISS.
DIPKETS SIZE 21 x 4 1/2 x 1 1/2 in. One resistor
to change. Full instructions supplied.
Battery 8/6. 89V +13V. Details Free.

WAVECHANGE SWITCHES
p. 4-way 2 water long spindle ... 6/6
2 p. 2-way or 2 p. 6-way long spindle ... 3/6
3 p. 2-way or 4 p. 3-way long spindle ... 3/6
3 p. 4-way or 1 p. 12-way long spindle ... 3/6
Wavechange MAKITS. Wafers Avail-
able: 1 p. 12 way, 2 p. 6 way, 3 p. 4 way,
4 p. 3 way, 6 p. 2 way, 1 wafer switch, 8/6
2 wafer switch, 12/6; 3 wafer switch, 16/-;
additional wafers up to 12, 3/6 each extra.

CRYSTAL MIKE INSERTS, 9/6
High output. Size 1 1/2 in. dia. x 1 in.
ACOS MIC. 14 insert 1 1/2 in. dia. x 1 in., 8/6
ACOS MIC. DE LUXE STICK MIKE 55/-
TSLI 41 ALPINE STICK MIKE ... 25/-
TELEPHONE TAPE MIKE ... 10/6
GUITAR CONTACT MIKE ... 15/6
MOVING COIL MIKE ... 59/6
FLOOR STANDS ... 57/6


Valveholders, EA50, 6d. B12A, CRT, 1/3.
Engl. and Amer. 4, 5 and 7 pin. 1/1.
MOULDED Mazda and int. oct., 6d.; 6B7,
B8A, B8C, B9A, 9d., 6V7 with can, 1/6. B9A
with can, 1/9. Ceramic EF50, 6V7, B8A,
int. oct., 1/-; 6V7, B9A cans, 1/- each. Valve
plugs BT, B9A, int. cans, 2/3.

HIGH GAIN TV PRE-AMPLIFIERS
B.B.C. Channel 1 to 5. Gain 18dB.
EC93A valve. Kit price 29/6 or 49/6
with power pack. Details 6d. (PC83A
valves 1d preferred). Coils only 9/6.
H.A.N.D. II I.T.A. - Same prices.
Tunable channels 3 to 13. Gain 17dB.
Circuit and coils only 9/6. Chassis 4/9.

RADIO COMPONENT

Our written guarantee with every purchase
NEW COMPONENT LIST 1/-
Bus 133 or 68 pass door
S.R. Station Selhurst

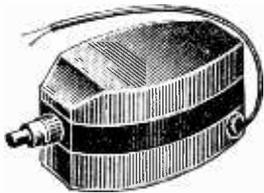THE "INSTANT" BULK TAPE ERASER AND RECORDING HEAD DEMAGNETIZER



200/250 v. A.C. **35/-** Leaflet S.A.E.

PLASTIC RECORDING TAPE

Double Play	7in. reel, 2,400ft. 42/-	Spare Plastic Reels
	5in. reel, 1,200ft. 25/-	
Long Play	7in. reel, 1,800ft. 22/8	3in. 1/6
	6in. reel, 1,200ft. 17/6	4in. 2/-
	5in. reel, 900ft. 15/6	5in. 2/4
Standard	7in. reel, 1,200ft. 17/6	5in. 2/6
	5in. reel, 600ft. 11/6	7in. 2/6

"EASISPLICE" Tape Splicer 5/-.
Leader tape 4/6; Splicing tape 3/-.

CRYSTAL SET BOOKLET 1/-
CRYSTAL DIODE G.E.C. 2/-, GEX 34, 4/-, OA81, 3/-, HIGH RESISTANCE PHONES, 4,000 ohms, 15/-, p. MOVING COIL PHONES, 100 ohms, 10/-, SWITCH CLEANER. Fluid squirt stout, 4/8 tin.

"6+1" TRANSISTOR RADIO MEDIUM AND LONG WAVE KIT

First class components to make a 6 transistor 2 waveband superhet chassis. Ideal for portable or table radio. All parts including BVA transistors, ferrite aerial, with car aerial coil, printed circuit, 8in. x 2 1/2in., but EXCLUDING speaker and cabinet.
Speakers, 35 ohms, 7 x 4in. 21/- **£4.50**
5in., 17/6; 3 1/2in., 15/6.

BULGIN PLUGS AND SOCKETS. Non-reversible P7L, 2-pin, 4/3; P73, 3-pin, 4/6; P194, 6-pin, 6/6. **JACKS.** English open circuits 2/8. Closed circuit, 4/3. Grundig type 3-pin, 1/3. Grundig lead jack 3/6. **JACK PLUGS** English, 3/-; Screened, 4/-; Grundig, 3-pin, 3/6; Photo Plugs, 1/-; Sockets 6d. **ALADDIN FORMERS** and cores, 4in., 8d.; 2in., 10d. 0.3in. FORMERS, 5937 or 8 cans TV1 or 2, 7in. sq. x 2 1/2in., or 4in. sq. x 1 1/2in., 2/- with cores. **SLOW MOTION DRIVES.** incl. 4/3.

SOLENOID IRON. 20V, 200V or 240V, 24/-. **ANEX SUB-MIN. IRON.** 15w, 200 or 240v., 20/6. **BENCH STAND** for above 12/6. Spares in Stock. 1/161in. Paxolin Panels, 10 x 8in., 2/-.
Miniature Contact Cooled Rectifiers. 250, 50mA, 7/8; 250V 60mA, 8/8; 250V 85mA, 9/6; Selenium Rect., 300V 85mA, 5/-, TV etc., Silicon Sub. Min. Rectifiers, 250V 450mA, 10/-, K3/25, 60V, 5mA, 5/-, EM4, RM5, 14A100, 14A116 10/- each, FC51 20/- Coils Wearite "P" type, 4/- each. dust core. Osmor Midket "Q" type, ad. dust core. from 4/- each. All ranges. List S.A.E.
Repanco DRR2. L. and Med. T.R.F. with reaction, 4/6. Osmor G.M., 3/6. **Ferrite Aerials.** M., 8/9; M. and L., 1/6. **Osmor Ferrite Rod Aerials.** L. and M. for transistor circuits, 10/- each. **Ferrite Rods,** 8 x 1in., 6 x 1in., 6 x 1/2in., 3/-, H.F. Chokes, 2/6. Osmor G.M., 6/9. **T.R.F. Coils.** A.H.F. 7/- pair, H.A.X. 3/6. **Screwdriver.** 5in., 6d. Test Prods. 2/9. **Neoside Trimming Tool.** 1/9. **Neon Mains Tester Screwdriver.** 5/-. **Multicore Solder.** 4d. 4in. Dispenser, 2/6.

Aluminium Chassis. 18 s.w.g. Plain, anodized. 18 sided, riveted corners, lattice fixing holes, 2 1/2in. sides, 7 x 4in., 4/9; 8 x 7in., 5/9; 11 x 7in., 6/9; 13 x 9in., 8/8; 14 x 11in., 10/6; 15 x 14in., 12/6. **Aluminium Panels,** 18 s.w.g., 12 x 12in., 4/6; 14 x 9in., 4/-; 12 x 8in., 3/-; 10 x 7in., 2/3; 8 x 6in., 2/-; 6 x 4in., 1/6.

MARTIN TAPE PRE-AMPLIFIERS & DECKS (PLAY-BACK THROUGH YOUR OWN AMPLIFIER)
B.S.R. 2 track B.S.R. TD2 tape Pre-amp, £8.8.0 deck £6.15.0
Collaro 2 track Collaro Studio Pre-amp, £8.8.0 tape deck £10.10.0

COMPLETE RECORDING & PLAY-BACK AMPLIFIERS
2 track B.S.R. Collaro amplifier £8.8.0 amplifier £11.11.0

MAINS DROPPERS. Midget adjustable sliders 0.3A 1,000 ohms, 6/-; 0.2A 1,300 ohms, 6/-; 0.15A 1,500 ohms, 6/-; 0.1A 2,000 ohms, 6/-.
MIKE TRANSFORMERS 50-1. 3/9.
P.V.C. Covered Wire, single or stranded, 2d. yd. Sleeving, 1 or 2 mm., 2d.; 4 mm., 3a.; 6 mm., 5d. yd. **SPEAKER-FEET.** Gold, Maroon or Green Cloth 17 x 2 1/2in., 5/-; 25 x 3 1/2in., 10/-. TYPAN, various colours 52in. wide from 10/- ft., 26in. wide from 6/- ft. Samples 1/-. Expanded Metal, Gold, 12 x 12in., 6/-, Panel mounting fuse holder, 2/-. Fuses (1/2, 60mA) 5A, 6d. Insulated side cutters, 8/6. Bib Stripper, 3/6.

RADIO AND TELEVISION SPARES
All leading makes, volume controls, etc., line output transformers, etc., B. V. A. valves (current and obsolete types). Send S.A.E. for quotation.

WEYRAD

COILS AND TRANSFORMERS FOR 2-WAVE 6-TRANSISTOR PRINTED CIRCUIT AND FERRITE AERIAL.

Long and Medium aerial—RA2W 6in. rod 208 pf tuning, with car aerial coil, 12/6
1st and 2nd I.F. P50/2CC. 470kc/s 11/6in. dia. by fin. 5/7 each
3rd I.F. P50/3CC 6/-
Spare Cores 9/6
Driver Transformer—LFDT4 6/6
Wavechange Slide Switch d.p.d.t. 3/6
Printed Circuit—PCAL. Size 2 1/2 x 8 1/2in. 9/6
Volume Control, 5K-1D 4/6
Ready drilled and printed 4/6
35 ohm Speakers, 3 1/2in., 15/6; 5in., 17/6; 7 x 4in., 21/-.
Tuning Gang with trimmers 10/6
6 Mullard Transistors and diode 4/6
Constructor's Booklet, 2/6
3 ohm O.P. Trans. O.P.T.1 10/6

NEW MULLARD TRANSISTORS
OC71 6/-, OC72 7/6, OC81D 7/6, OC81 7/6, OC48 8/9, OC45 8/6, OC171 10/6, AF117 9/6.
Nip Miniature Condensers, 0.1 mFd. 30v., 1/3, 1, 2, 4, 5, 8, 16, 25, 30, 50, 100 mFd 15 volt, 2/6 ea. Transistor Holders, 1/3.

SINCLAIR "SLIMLINE" RADIO
Med. wave kit, 2 transistors, 2 diodes, earphone, ferrite aerial. Cabinet 3 x 17 x 4in. 49/6, batt. 3/6.

ADAstra 3-3 AMPLIFIER 3 WATTS HIGH FIDELITY AT LOW COST



READY BUILT, WIRED AND TESTED A.C. only, 200-250 V. Valves ECL86 and E280, 3 ohms quality output. Mullard tone circuit. Controls: bass boost, treble and volume. Separate engraved front panel with die fuse finish. Quality mains transformer. Stove enamelled chassis size 6in. x 5in. x 3in. Bargain Price £4.19.6 Details S.A.E.
"Performs agreeably well" (The Gramophone)

BUILD YOUR OWN RECORD PLAYER

FROM £9.19.6

AND SAVE POUNDS!!



4 Speed Autochange or Single Player units supplied with Brand New 24 core de luxe Portable Cabinets 17x15x8 1/2in. Strong carrying handle, gilt finish clips and hinges. As used by Famous Make for 20cans. models. Ready cut-out motor board 14x13in. Front baffle with 7 x 4in. high flux loudspeaker and 3 watt 2 valve UY85, UCL82 2-stage amplifier ready built on metal chassis 12 x 3 x 2 1/2in. quality 3 ohm output transformer, low hum level circuit. Volume and Tone controls. 3-core safety mains lead. All items fit together perfectly. Special instructions enable assembly in 30 minutes, only 5 wires to join! 12 month written guarantee. Available separately or package deals as below. **AUTOCHANGER KITS COMPLETE** (as above)
B.S.R. Monarch .. £11.10.0 P.P. 5/6
Garrard Autoslim .. £12.15.0 P.P. 5/6
SINGLE PLAYER KITS, COMPLETE (as above)
E.M.I. Junior .. £19.16.0 P.P. 5/6
E.M.I. Auto stop/start .. £11.5.0 P.P. 5/6
OR SEPARATELY

Cabinet with board 14 x 13in. cut out to four choice £3.9.6 P.P. 3/6
Amplifier with 7 x 4in. speaker £2.17.6 P.P. 2/6
AUTOCHANGERS
B.S.R. UA14 .. £5.19.6 P.P. 4/6
B.S.R. UA15/16 .. £6.17.6 P.P. 4/6
Garrard Autoslim .. £17.16.0 P.P. 4/6
SINGLE PLAYERS
Garrard SRP10 .. £5.5.0 P.P. 4/6
E.M.I. auto stop/start .. £5.5.0 P.P. 4/6
E.M.I. Junior .. £3.7.6 P.P. 3/6

TRANSCRIPTION UNITS
Garrard 4HF .. £15.15.0 P.P. 5/-
Philips AG1016 .. £12.5.0 P.P. 5/-
Garrard AT76 .. £10.10.0 P.P. 5/-

BARGAIN
B.S.R. Autochange UA12 Stereo/Mono .. £7.10.0 P.P. 4/6

Replacement sapphire styli 5/-, diamond 15/-, Mono GP59 Xtals 15/-; Stereo Ronette 80/-.

BARGAIN SINGLE PLAYER KIT 200/250 v. A.C. (less cabinet)

£5.15.0

Post 5/-.

With 2-stage Amplifier; 3 watt, 2 valves, UCL82, UY85; High-flux 5in. speaker; 4-speed E.M.I. Turntable, 16, 33, 45, 78 r.p.m.; Crystal Pick-up for LP/STD. Records, 7in., 10in., 12in.; Cut out Mounting boards 12 x 9in.

ARDENTE TRANSISTOR TRANSFORMERS

D3035, 7.3 CT:1 Push-Pull to 3 ohms for OC72, 11/-
D3034, 1.74:1 C.T. Push-Pull Driver for OC72, 11/-
D3033, 11.5:1 Output to 3 ohms for OC72 etc., 11/-
D167, 15.2:1 Output to 3 ohms for OC72, etc., 12/-
D239, 4.5:1 Driver, 7in. x 7in. x 7in., 11/6-
D240, 8.5:1 Driver, 7in. x 7in. x 7in., 11/6-

ARDENTE TRANSISTOR VOLUME CONTROLS

VC145, 5K with switch dia. 9in. 5/3
DEAF AID EARPIECE, Xtal or magnets 7/8
SUB.-MIN. JACK and PLUG 3/8 pair

MINIATURE PANEL METERS

Size 1 1/2in. sq. Precision jewelled bearings, 2% accuracy, silvered dials, black numerals and fine pointers, zero adjustment screw on front of meter.

0-1 mA .. 27/6	0-50µA .. 39/6
0-5 mA .. 27/6	0-500µA .. 32/6
0-300 V .. 27/6	"S" Meter .. 35/-

CABY MULTIMETER M1
0-1200 v. A.C./D.C., ohms 0-100K, etc., 54/-.

COMPONENT SHOP 337 WHITEHORSE ROAD WEST CROYDON

Telephone: THO 1665
(L.sport welcome. Send resistance, and extra postage, no C.O.D.)
P.P. charge 1/-. C.O.D. 2/- extra.

ELECTRONICS


LEARN - THE PRACTICAL WAY . . .

your career . . .
hobby . . .
own business . . . ?

The demand for good Electronic Engineers is increasing almost daily throughout the world. Electronics is now the most rapidly expanding of all industries with its applications reaching into almost every sphere of human activity. If you are looking for a new career with new opportunities—then now is the time to choose—Electronics. If you are already employed in this field—then now is the moment to seek high qualifications to secure the top jobs which are waiting to be filled. Most of all, the great potential of electronic development means unlimited scope for the future and will ensure a secure occupation for you—unlikely to be affected by possible future recessions in other industries.

The British National Radio School has had 25 years' experience of HOME STUDY coaching for students wishing to master the fascinating subjects of Electronics—whether the object be career or as a hobby or new interest. The School is entirely independent and specialises ONLY in the teaching of electronic subjects. It employs only fully qualified staff to conduct and supervise each individual course taken by a student and it is this close and personal contact between Tutor and Student which we believe makes possible the successful completion of a course of study.

A special feature of our system is that all courses start right from the beginning and no previous knowledge or experience is necessary or expected. Training is carried out in easy step-by-step stages using the most modern methods of tuition. The great advantage of the home study method is that it provides a complete self-contained course giving everything needed for the subject concerned and enabling work to be done in the comfort of one's own home and over any period of time desired.

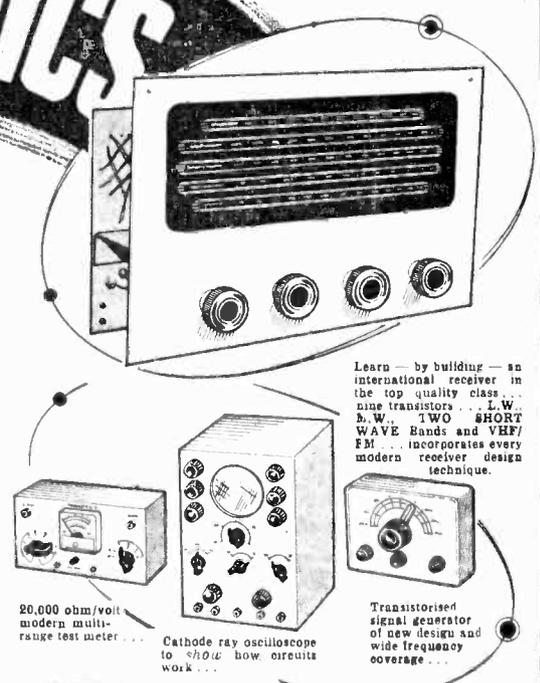

Learn — by building — an international receiver in the top quality class... nine transistors... L.W. h. W. TWO SHORT WAVE Bands and VHF/ FM... incorporates every modern receiver design technique.

20,000 ohm/volt modern multi-range test meter . . .

Cathode ray oscilloscope to show how circuits work . . .

Transistorised signal generator of new design and wide frequency coverage . . .



Complete picture way library of theory books and practical manuals NO MATHEMATICS

EXAMINATION COURSES

- CITY & GUILDS TELECOM. TECHNICIANS CERT.
- CITY & GUILDS FULL TECHNOLOGICAL CERT.
- A.M.Brit.I.R.E. EXAMINATION.
- RADIO AMATEURS' LICENCE EXAMINATION.
- P.M.G. CERTIFICATES FOR RADIO OPERATORS.
- R.T.E.B. SERVICING CERTIFICATES.

OTHER COURSES

- MATHEMATICS
- TELEVISION
- TRANSISTORS
- SERVO-MECHANISMS
- COMPUTERS
- RADA R & NAVIGATIONAL AIDS

BUILD AND EXPERIMENT WITH ALL THE ABOVE—AS—YOU—LEARN . . .

This is a new complete experimental course comprising a mixture of theory and practical work using a very full range of electronic components and apparatus. Starting right from the beginning—or at a later stage if needed—the course enables the student to build up all the basic electronic circuits—amplifier; oscillator; rectifier; detector; etc.—and finally to the design, construction, testing and servicing of a latest design fully transistorised receiver using nine transistors and covering long and medium wave and TWO SHORT WAVE BANDS plus VHF/FM reception. It is of real luxury quality throughout—operates from a 1.5 battery and can be used anywhere in the world. Every present-day technique in circuitry is covered and the course also includes multi-range test meter; signal generator and oscilloscope. By the end of the course the student will be able to deal with any type of servicing work with confidence and will also have a very useful workshop of equipment. Nearly 100 interesting and absorbing EXPERIMENTS are carried out during this comprehensive course enabling anyone to gain full mastery of electronics.

FREE



POST NOW

TO: BRITISH NATIONAL RADIO SCHOOL, RADIO HOUSE, READING, BERKS.
Please send me your free Brochure giving details of your Courses, without any obligation, to:—

NAME _____

ADDRESS _____

I am interested in _____ course above

(We do not employ representatives) PW 5/64

British National Radio School

Practical Wireless

Vol. XL No. 687 MAY, 1964

Editorial and Advertisement
Offices:

PRACTICAL WIRELESS

George Newnes Ltd., Tower House,
Southampton Street, W.C.2.

© George Newnes Ltd., 1964

Phone: Temple Bar 4363

Telegrams: Newnes, Rand, London,
Registered at the G.P.O. for trans-
mission by Canadian Magazine Post.

SUBSCRIPTION RATES

including postage for one year

To any part of the world £1.90

Contents

Editorial	25
Round the World of Wireless ...	26
The Hillingdon Radiogram ...	28
The P.W. Guitar Amplifier ...	32
Test Gear Accessories ...	39
Unit Construction Boards ...	41
On Your Wavelength ...	44
This "J" Business ...	47
Medium Wave Aerial Data ...	50
Six-Band T.R.F. Receiver ...	52
Communications Through the Ground	56
On The Short Waves	58
P.W. Leader Competition ...	61
A Simple 2-stage Amplifier ...	65
Books Reviewed	70
A Mains Distribution Panel ...	73
Club News	74
Trade News	77
The Junior Crystal + 2 ...	81
Letters to the Editor	89

The Editor will be pleased to consider articles of a practical nature. Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed to the Editor, PRACTICAL WIRELESS, George Newnes, Ltd., Tower House, Southampton Street, London, W.C.2. Owing to the rapid progress in the designs of wireless apparatus and to our efforts to keep readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent. Copyright in all drawings, photographs and articles published in PRACTICAL WIRELESS is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. PRACTICAL WIRELESS incorporates "Amateur Wireless."

Leaders Galore!

"THE Editor asks for a leader. He must be slipping!"—thus begins one of the contributions to the Leader Competition. Another suggested that as nobody ever reads the leader, his entry was so much waste of time and effort. From these two comments alone, it will be obvious that readers not only accepted the challenge but took the opportunity to get in a few sly digs at the same time!

The number of entries was much larger than anticipated and we were very impressed with the high general standard—two factors which made the judging extremely difficult. It was doubly gratifying that the response was so good, for the prizes offered were nominal and most readers were obviously stimulated to take part through pure interest and enthusiasm.

And what an extraordinary variety of entries came in! There were unabashed lighthearted leaders and stern censorious ones. There were leaders on the past, the present and the future. Many took the theme of space and electronics. Others looked at valves and transistors. Some concerned themselves with various aspects of design and construction. One was addressed to contributors; another spoke of writing for PRACTICAL WIRELESS. Several developed the richness and variety of our hobby, but another warned of the narrowness of outlook of those too fully wrapped up in radio. Then there were articles on kits, on amateur bands, on home movies, and on many other practical or abstract subjects. Hardly anything or anyone escaped this literary onslaught!


Not only was there a vast range of subjects and attitudes, but participation from all age groups. The youngest and oldest (known) contributors were 14 and 70 years old respectively.

This flood of material presented a formidable task to the judging panel. A process of elimination began. Personal viewpoints of the judges were not, of course, allowed to influence selection or rejection, but some entries were obviously unsuitable subjects for leaders and others failed because the writers did not develop a good original theme or were sidetracked.

This preliminary thinning out still left a considerable number of survivors which was eventually reduced to a final "short list" of ten—and here, the panel ran into trouble for these were all good enough to take the winning positions. The selections finally made are printed on pages 61 and 62, together with a list of "highly commended" entries.

Very many thanks to everyone who co-operated. It was a fine effort. Every entry received was carefully considered and even those which were rejected early on often showed considerable merit. And now that he knows so many readers look at the leader column, your Editor will have to be particularly careful what he writes in future!

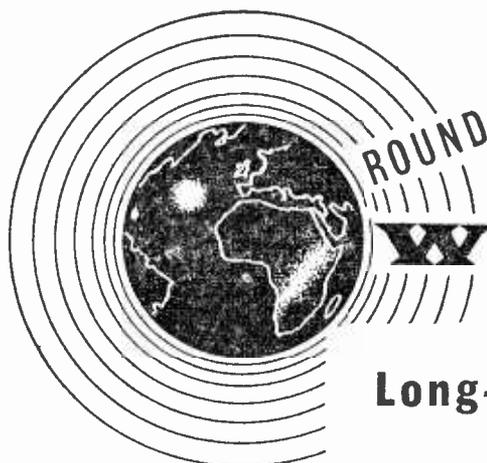Our next issue dated June will be published on May 7th



of WIRELESS

**NEWS AT HOME
AND ABROAD**

New Submarine Cable Links U.K. and Germany

UP until recently, all telephone connections between this country and Western Germany have had to be routed through Belgium and the Netherlands. Now, with the inauguration in February of the first direct, large capacity, submarine telephone cable linking Britain and the Federal Republic, 120 new telephone circuits become available, any one of which will carry 24 telegraph circuits.

The new cable connects Winterton, in Norfolk with Borkum Island, from where it is taken to Leer on the German mainland. Two ships were employed in the 200 nautical mile long, cable laying operation; the G.P.O.'s H.M.T.S. "Monarch" and the Danish cables ship "Peter Faber". The cable was manufactured by Standard Telephones and Cables Limited, who also supplied the repeaters and equalisers.

Apart from British/German traffic, a number of channels in the cable will be allocated to United States/German connections, and by linking up with the existing TAT 3 U.K./U.S.A. cable, will thus provide direct circuits between the U.S.A. and West Germany.


A second Anglo-German cable will be in service later this year.

Long-established Institution Changes Its Title

FROM the very early days of the British Institution of Radio Engineers (founded in 1925) there have been those who advocated the inclusion of "electronic" in its title. After the War the Institution's name again came under discussion with the increasing recognition of the amount of activity in the Institution which was covered by the term "electronics". This fact has steadily become more apparent and now, nearly three years after the Institution was incorporated by Royal Charter, the Queen was pleased, at a Privy Council held by her Majesty on 26th February, 1964, to make an Order in Council allowing amendments to the Charter of The British Institution of Radio Engineers changing its name to "The Institution of Electronic and Radio Engineers".

RADIO TELESCOPE FOR DSIR

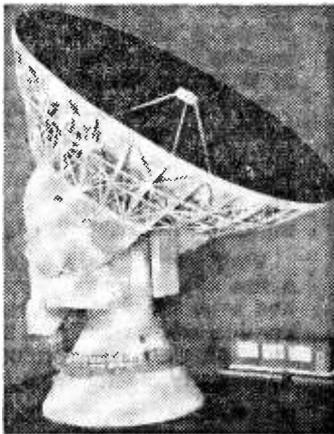THE Ministry of Public Building and Works recently placed a contract with the Electronics Group of Associated Electrical Industries Limited, for the design and installation of a radio telescope for the Department of Scientific and Industrial Research at Chilbolton in Hampshire.




Backed by considerable experience in the design of steerable aeriels, AEI's Electronics Group has designed the new aerial to be steered with a pointing accuracy of two minutes of arc, in winds of up to 45m.p.h. The drive motors which will steer the aerial's 82ft. dish—which together with the rest of the moving structure will weigh approximately 300 tons—will be supplied by AEI's Motor and Control Gear Division.

The DSIR eventually plans to use the new telescope in its study of radiation and radio signals pick-up.

A model of the new 'steerable aerial to be supplied by AEI to the DSIR.

EQUIPMENT FOR CARIBBEAN LINKS

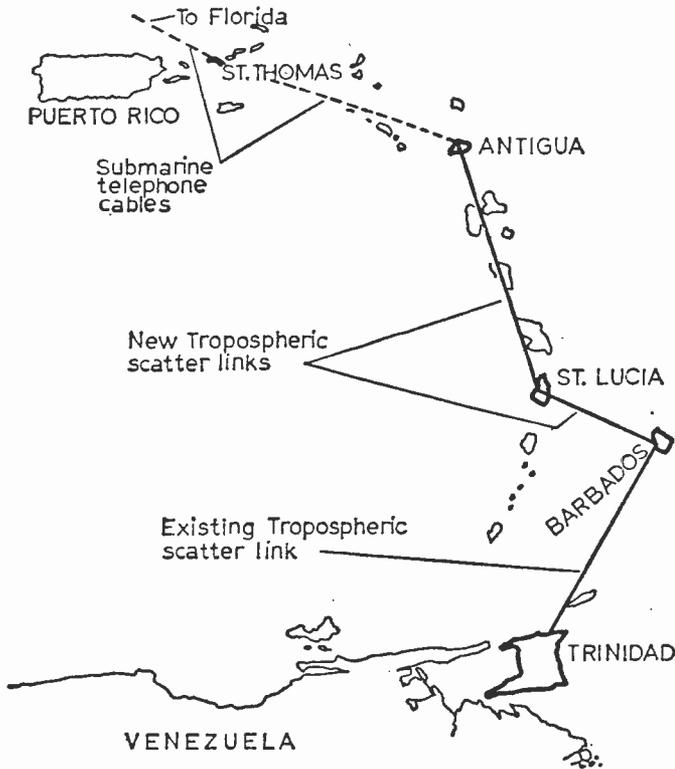

A map of the Eastern Caribbean showing existing and planned tropospheric scatter links and submarine cables.

EQUIPMENT for the multi-channel tropospheric scatter and microwave link system to be established in the islands of the Eastern Caribbean (see Round the World of Wireless last month) is to be the responsibility of the Marconi Company Ltd.

The two new tropospheric scatter links will connect Antigua to St. Lucia and St. Lucia to Barbados, distances of 220 and 112 miles respectively. The Antigua-St. Lucia installation will be a Marconi 900Mc/s tropospheric scatter link, providing 64 telephone channels. At each end of the link, two 30ft. diameter dishes will be erected with parametric amplifiers to give a low noise factor. The 2,000Mc/s tropospheric scatter link between St. Lucia and Barbados, will be of American manufacture by the Radio Engineering Laboratories Inc., and will carry 80 channels. A Marconi 900Mc/s link is already in existence providing communication between the final two terminal islands in the system—Barbados and Trinidad—but under the contract, the capacity of this link will be increased from 12 to 64 channels.

Short overland connections in Antigua, St. Lucia and Barbados will be necessary to complete each section of the system. At Antigua and Barbados these connections will be provided by twin path 7,000Mc/s microwave links manufactured by Pye Telecommunications Limited, carrying 64 and 92 telephone channels respectively, to link, in the first case, the St. Thomas-Antigua submarine cable to the Antigua-St. Lucia 900Mc/s link, and in the latter case to link the Barbados terminals of the second and last legs of the tropospheric scatter link. On St. Lucia will be a short, v.h.f. link, providing a 32 channel path between the first and second legs.

Irish Islands Get Telephone Service

BY linking four islands off the western and southern coasts of Ireland with mainland telephone exchanges, v.h.f. radiotelephone equipment made by the Automatic Telephone and Electric Company Limited, will bring a public telephone service to the islands' inhabitants for the first time.

The equipments—known as "Country Sets"—are capable of operating from 12V battery supplies, providing exactly the same service as a conventional land-line system. Transistorised circuits help minimise power consumption which at the mainland terminals of the links can be provided for by either mains or battery supplies.

The Country Sets operate on 54—88Mc/s or 156—184Mc/s and these particular installations will link Inishmeane with Bunbeg, Inishturk with Cleggan, Achill Beg with Achill Sound and Long Island with Baltimore.


RADIO TELEPHONES FOR DANISH POLICE

THE whole of Denmark is to be covered by a radio telephone network which will link mobile units of the Danish police to fixed stations at their headquarters. The contract for this installation has been awarded to Pye Telecommunications Limited by the Danish State Police after extensive field trials.

Police cars and motorcycles will be equipped with radio telephones employing transistorised receivers and instant heating transmitting valves.

Pye in India

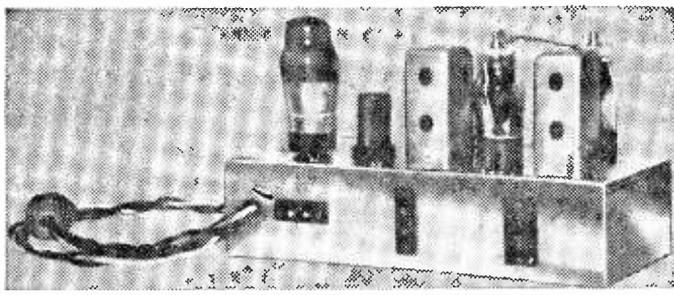A NEW radio receiver factory opened recently in Bombay under the administration of the Tata Group of India and National Ecko Radio and Engineering Limited of Bombay, and the British firm, Pye of Cambridge. Pye will collaborate with the Tata Group to produce eventually more than 200,000 radio receivers a year from this one factory, which will be the largest of its kind in India.



The Hillingdon RADIOGRAM

BY J. B. WILLMOTT

CONTINUED FROM PAGE 1164 OF THE APRIL ISSUE

THE circuit of this switch-tuned a.m. radiogram was described in last month's issue along with details of chassis construction. The next step is to assemble and wire up the two chassis.

MOUNTING THE COMPONENTS

Reference should be made to Fig. 5, which shows the layout of components and wiring underneath the chassis. It is recommended that components be mounted in the following order:

First of all fit a rubber grommet in the $\frac{3}{16}$ in. diameter hole on the rear chassis runner which is to allow for entry of the six-way power supply cable. Using 6B.A. nuts and bolts, the aerial, earth, pick-up and loudspeaker sockets can now be mounted on the rear runner, also the four-way tagstrip TS4 adjacent to the grommeted hole previously referred to.

Now mount the four octal valveholders, noting particularly the orientation of the locating spigots. Again use 6B.A. nuts and bolts and at the same time include the tagstrips TS1 and TS2 on one fixing bolt of V1 and V2 respectively, also the solder tag on fixing bolts of V4 and V3.

The i.f. transformers can next be mounted, not forgetting to include the tagstrip TS3 on one mounting bolt of T2. The output transformer is also mounted beneath the chassis.

The tone control and volume control may now be secured to the front chassis runner and finally the coilpack unit. Handle this component with care and make sure that it is fixed with the "green" and "red" tags nearest the top (open) edge of the chassis runner (see Fig. 5). The fixing nuts of these three components should be screwed up really firmly, preferably using shakeproof washers between the nuts and chassis surface.

Turning now to the power supply chassis, the position of the various components should be easily seen from the drilling diagram (Fig. 3) given last month. The mains transformer is mounted above chassis and the choke and smoothing capacitors below. The power output socket is on the end runner nearest the rectifier valve V5. Rubber grommets should be fitted in all holes marked "B" as in each case these provide for current-carrying leads passing through the chassis.

WIRING UP

It is strongly recommended that the power supply chassis be wired up first in order that when the constructor has completed the more complex wiring of the main chassis he already has the power unit complete and ready to connect up and test the completed job without further delay.

Wiring of the power supply calls for no special comment; reference to the theoretical circuit in Fig. 1 should make it perfectly clear. Extreme care must be used in wiring the power take-off socket, adhering strictly to the pin numbering as shown. It is a good plan to carry out the wiring of the octal plug as the next operation whilst the socket wiring is fresh in the mind.

The exact length of cable required to reach from main chassis to power pack depends on the positioning of the two units in the cabinet, but it is better to allow too much lead rather than "just enough". It is recommended that the six-way cable be made up of a twisted red/black, a twisted yellow/blue (or any other pair of colours differing from red/black) and a flat twin length of plastic insulated flex. These leads are terminated on the octal plug as follows:

Pin 1.—No connection.

Pin 2.—Blue flex (earthed side of 6.3V heater supply).

- Pin 3.—One lead of flat twin flex.
- Pin 4.—Other lead of flat twin flex.
- Pin 5.—No connection.
- Pin 6.—Red flex (h.t. positive line).
- Pin 7.—Yellow flex (live side of 6.3V heater supply).
- Pin 8.—Black flex (h.t. negative and chassis).

The cable can be plaited together or bound at intervals with insulating tape. Thread the end of the cable through the grommets on the rear chassis runner of the main chassis and anchor the leads to the four-way tagstrip TS4 as shown in Fig. 5, again taking extreme care not to make any errors in the colour coding. The remaining leads are connected to the on/off switch on VR2.

valve are earthed to chassis and form the heater supply return. The tagstrips TS1, TS2 and TS3, the volume and tone controls and the coilpack can next be wired up. The various anode, screen and cathode connecting components should be secured to their respective valveholder pins, their other ends being left "free" for later connection to busbar or h.t. rail.

A heater supply for the indicator lamp is connected in parallel with the heater of V2 and taken through the chassis via the ¼ in. hole adjacent to the V2 valveholder. The indicator lamp is not fixed to the chassis but is on a fly-lead long enough to permit its being mounted on the surface panel of the completed radiogram.

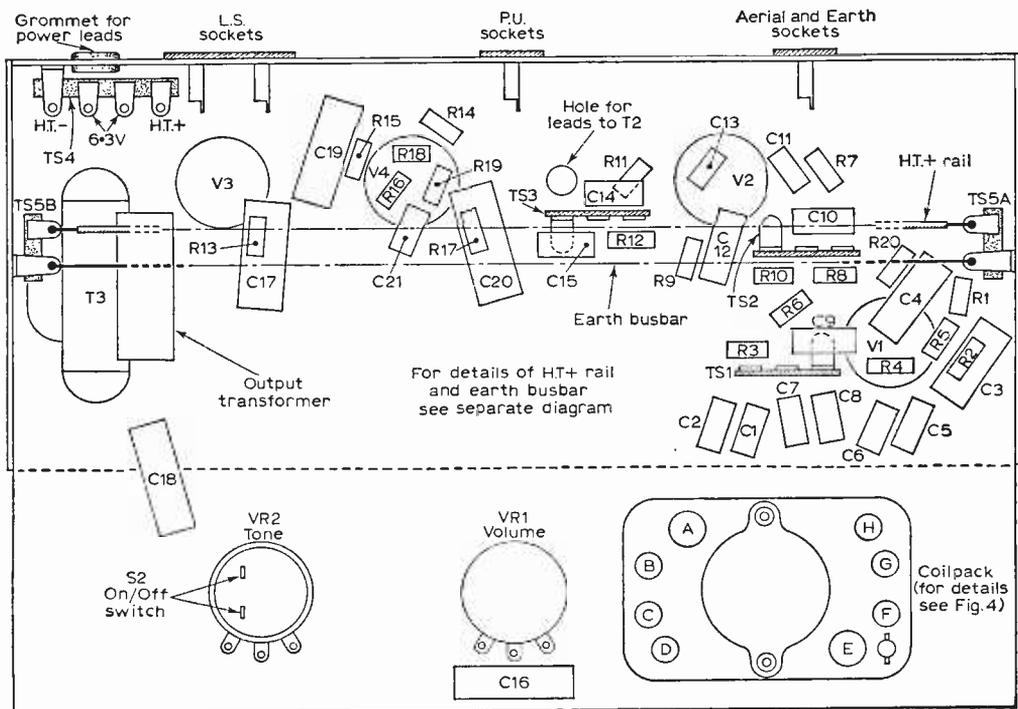


Fig. 5: The relative positions of components mounted beneath the chassis main.

Make a careful check of all wiring and then proceed to the wiring up of the main chassis. A feature to note here is the provision of a main negative busbar and an h.t. positive rail stretched across the full length of the chassis (see Fig. 5). Most of the voltage dropping and cathode bias resistors, together with their associated decoupling capacitors, are anchored at one end to the earth busbar, their other ends going to the appropriate valveholder pins. This makes assembly much simpler and the result is both neat and efficient and greatly facilitates testing and servicing should this prove necessary at some future date.

Before the busbar and h.t. rail are put in position, however, wire up the heater supply to pin 7 of each valveholder. Pins 1 and 2 on each

The negative busbar, comprising a length 14 or 16s.w.g. tinned copper wire, is now stretched tightly across the chassis between the earthed tags of TS5(a) and TS5(b) and the appropriate components soldered to it.

A further length of wire is now measured off to stretch from the insulated tag of TS5(a) to that of TS5(b), but this is provisionally soldered into position at one end only. Short lengths of insulating sleeving are then slid on, leaving gaps at appropriate distances to permit the connection of voltage dropping resistors and "red" leads to T1 and T2 (see Fig. 6). The wire is then secured at its free end and the appropriate connections made to this h.t. rail.

This should complete all wiring and a careful

check should be made. It is a good plan to colour in each wire on the theoretical diagram as it is checked. Make sure that where screened leads are used the screening braid does not foul any nearby tags or components and that where the braid is shown as "earthed" it is securely anchored to the tag in question. A screened lead was used in the prototype for the connection between T51, below chassis, and the top cap grid of V1 as a precautionary measure. It is conceivable that unwanted coupling between this rather lengthy lead and that going from the top of T2 to the grid of V2 might cause instability.

If a multirange testmeter is available routine tests can now be carried out to ensure that there are no short-circuits existing between the h.t. line and chassis or between the live heater line and

driver to the "live" pick-up socket on the rear panel; a loud and healthy "brrrr . . ." from the speaker should result which should vary in intensity with the setting of the volume control.

This test proves the correct working of the audio stages V3 and V4. Now turn the selector switch to any one of the "radio" positions and tap the top cap of V2 with the screwdriver with volume control at maximum position; a sharp "click" should be audible. Repeat this by touching first the top cap of V1, then the aerial socket on the rear panel. If the desired response is obtained it is fair to assume that no serious wiring errors have been made and some attempt can be made to receive a signal.

Actually, when received from the manufacturers, the coilpack will probably be found to have been

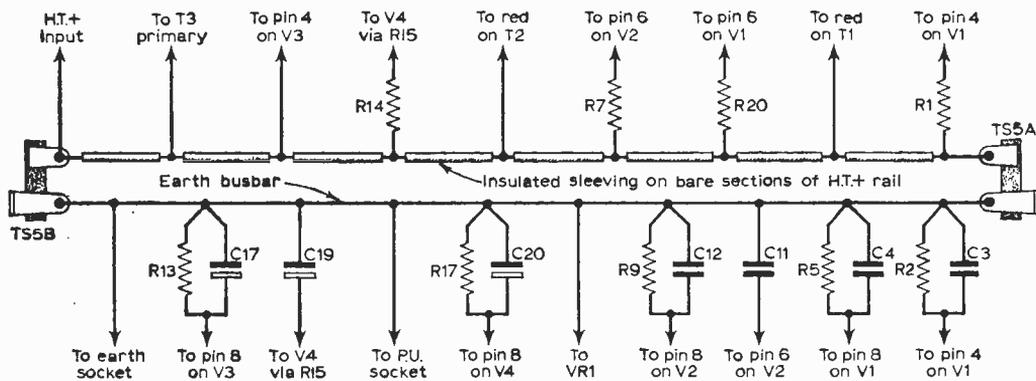


Fig. 6: Component wiring to the earth busbar and h.t. rail.

chassis. If all is in order the completed receiver can now be tested.

TESTING AND ALIGNMENT

Plug the main chassis into the power supply unit (never operate the latter without a suitable "load" on the h.t. supply, in actual fact the inclusion of the on/off switch on the main chassis renders it impossible to switch on the power unit without the two chassis being connected). Insert the valves into their appropriate valveholders, not overlooking the fact that the 6J5, which is V4 on the circuit diagram, actually occupies the position between V2 and V3 on the main chassis, and connect the loudspeaker to the sockets provided on the rear chassis runner.

Set the selector switch on the coilpack to the "gram" position, fully clockwise, and with the volume control at minimum (anticlockwise) switch on by turning VR2 until the "click" of the switch is heard.

Watch and listen carefully for any signs of overheating; the pilot lamp should come on immediately and the valve heaters glow after a few seconds. Gradually advance the volume control to maximum—a slight "breathing" sound should be audible from the speaker or possibly a very faint mains hum. Now advance the blade of a screw-

roughly aligned to the BBC London Home, Light and Third programmes. In the case of the prototype, signals were audible at all four positions of the switch as soon as an aerial was connected up, prealigned 465kc/s i.f. transformers having been used in construction.

However, for those possibly less fortunate here is the procedure for alignment. If a signal generator is available alignment of the i.f. transformers to 465kc/s can be carried out as the first operation. As the method of doing this will almost certainly be already known to anyone possessing a signal generator it will not be repeated here.

Those without such an instrument need not despair as with reasonable care and patience this receiver can be satisfactorily aligned without the use of instruments.

Turn the selector switch fully anticlockwise: this is the position in which the BBC Light Programme (on 247m where coilpack CP4/MG is used or on 1,500m where CP4/LG is used) should be received. Insert a suitable trimming tool through the hole in the front panel giving access to the core of coil "E" and screw slowly in or out until the signal can be heard. Now transfer the trimming tool to the core of coil "A" and adjust for maximum volume.

Next carefully adjust the cores of the i.f. transformers in turn, beginning with T1 primary and

working through to T2 secondary for maximum volume. Not more than one or two turns either way from the setting in which the components were originally supplied (provided prealigned ones have been ordered) should be necessary.

Repeat the adjustments a second time to see if any further improvement can be obtained. Naturally without a signal generator there will be no guarantee that the i.f. transformers will be aligned exactly to 465kc/s, but as no ganging of tuned circuits by a variable capacitor is involved this is not of great consequence.

Now return to the adjustment of cores "E" and "A" as a further improvement will no doubt be now obtainable.

Turn the wavechange switch to position 2 and in this position adjustment of cores "F" and "B" should enable the B.B.C. Third Programme on 464m to be tuned in. Similarly in position 3 the Home Service should be located and on position 4 Radio Luxembourg on 208m, by adjustment of cores "G" and "C" and "H" and "D" respectively.

The position of the various tuning cores is clearly shown on the data sheet supplied with the coilpack (Fig. 4, last month).

INSTALLING THE CHASSIS

When fully satisfied with the alignment the chassis can be fitted into the cabinet.

The screened pick-up lead from the record player unit should be terminated by a red wander plug for the inner lead and a black wander plug for the screening braid; these, of course, plug into the appropriate sockets on the rear panel of the main chassis.

The gramophone motor can be conveniently connected by a length of twin flex across the primary tags of the mains transformer on the power unit chassis. This will then ensure that when the radio receiver switch is in the "off" position the gram motor is simultaneously disconnected from the mains.

It will be found that a very pleasing standard of reproduction will be obtainable from records, with more than adequate volume for all domestic needs. The maximum output obtainable approaches 4W.

Normally the tone control will require setting at the minimum position (anticlockwise) as the V4 stage already provides enhanced bass response, but it may, of course, be advanced slightly to counteract surface noise on the older type 78 records. ■

FREE *INSIDE NEXT MONTH'S* **PRACTICAL WIRELESS**

ANOTHER BIG DOUBLE-SIDED **BLUEPRINT**

1 *to build* **2**

COMPACT SHORT WAVE TRANSCEIVER

Case size 4" x 4" x 2½". Designed for 7 Mc/s wave band. Can be adapted with plug-in coils for other Amateur wave bands.



MAINS POWER PACK
for transistor radios

Converts your battery radio to mains operation. 9 volts d.c. output from 200/230 volts a.c. Compact, same size as 9 volt dry battery.



ORDER FROM YOUR NEWSAGENT TO-DAY!

GUITAR AMPLIFIER

PUBLISHED BY GEO. NEWNES LTD., TOWER HOUSE, SOUTHAMPTON STREET, LONDON W.C.2.

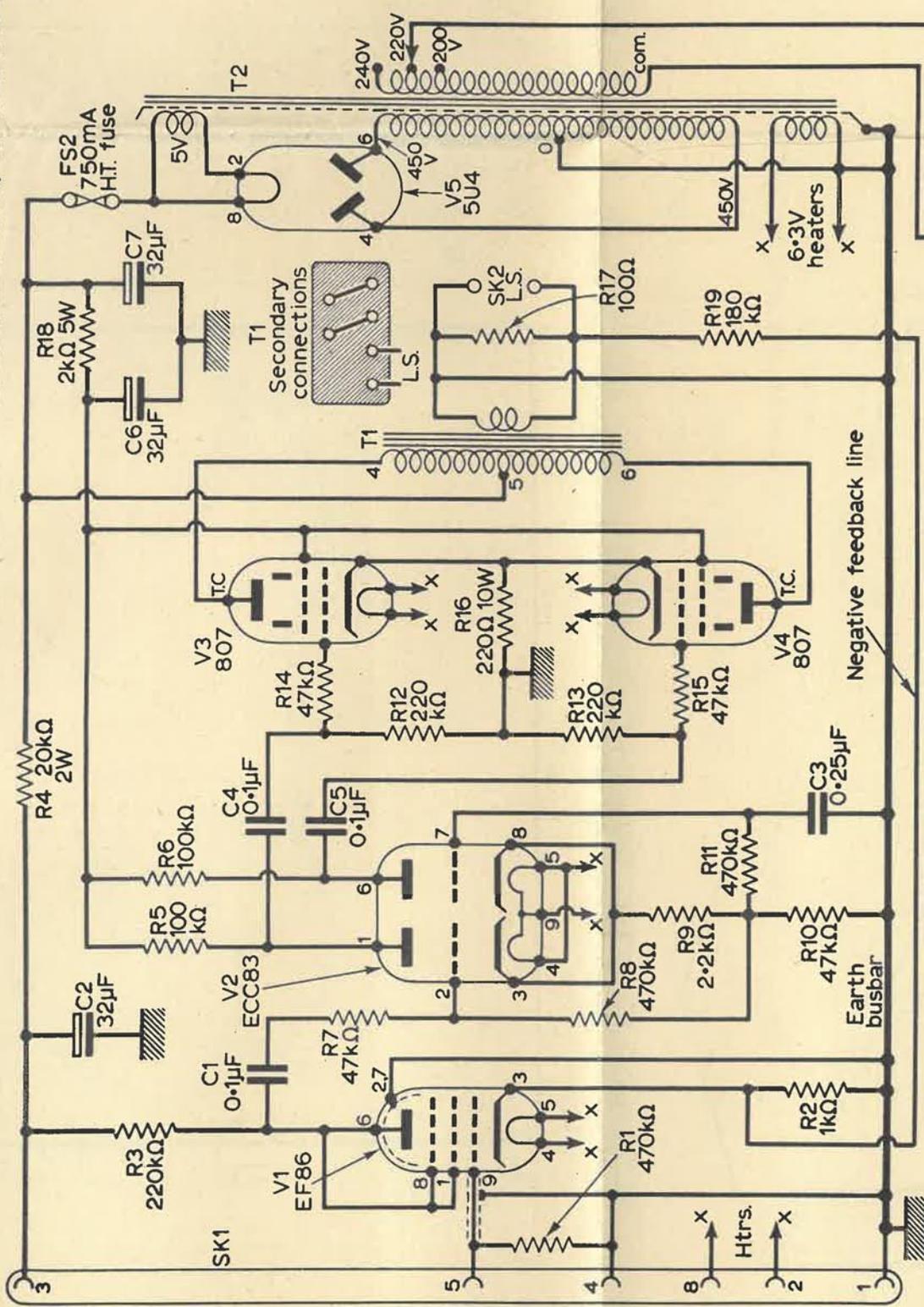


FIG. 1 CIRCUIT DIAGRAM

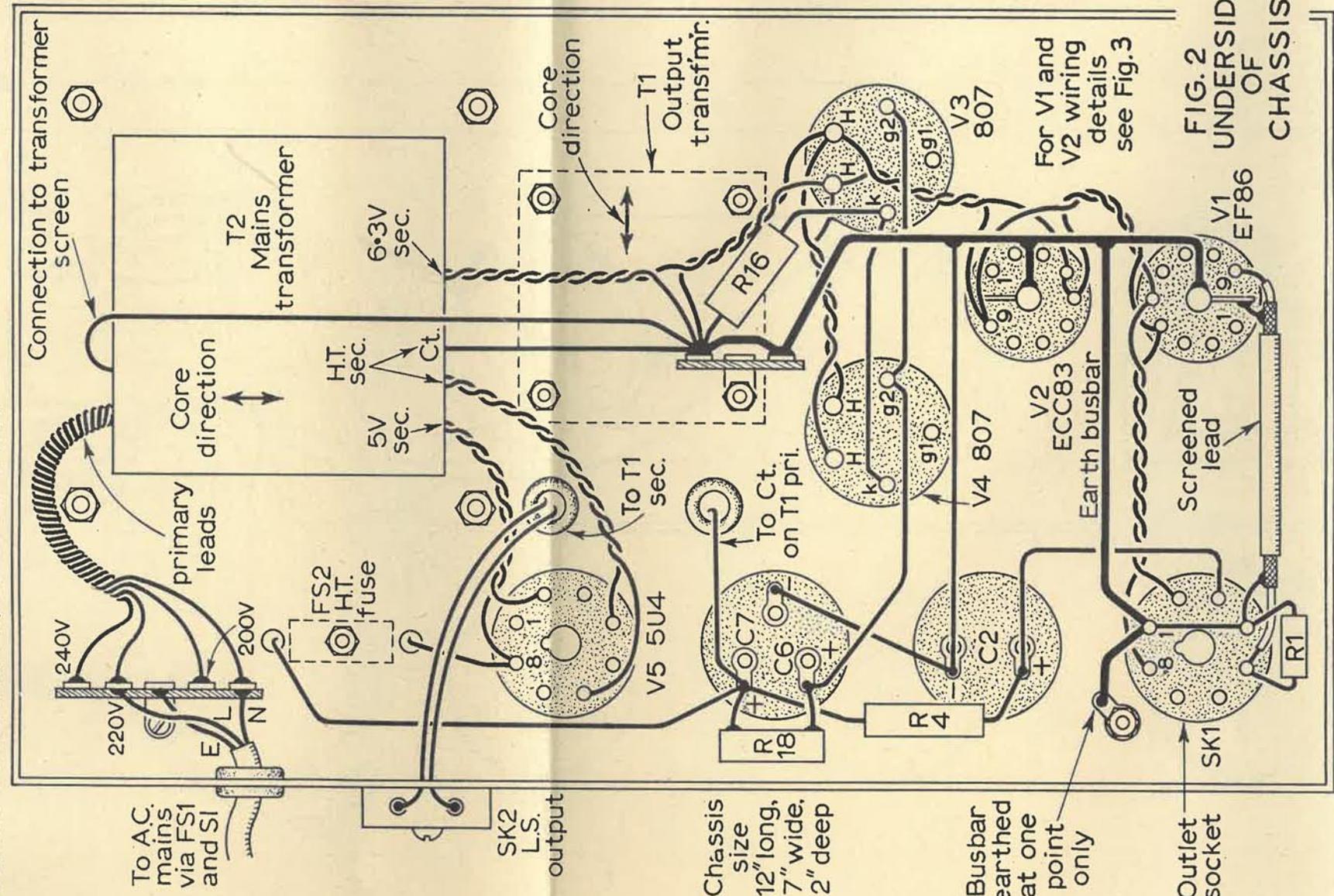


FIG. 2 UNDERSIDE OF CHASSIS


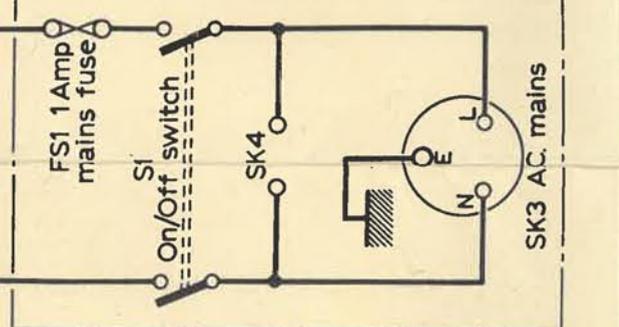


FIG. 3 WIRING AND COMPONENTS

POWER UNIT AND OUTPUT STAGES

PRE-AMPLIFIER Contd.

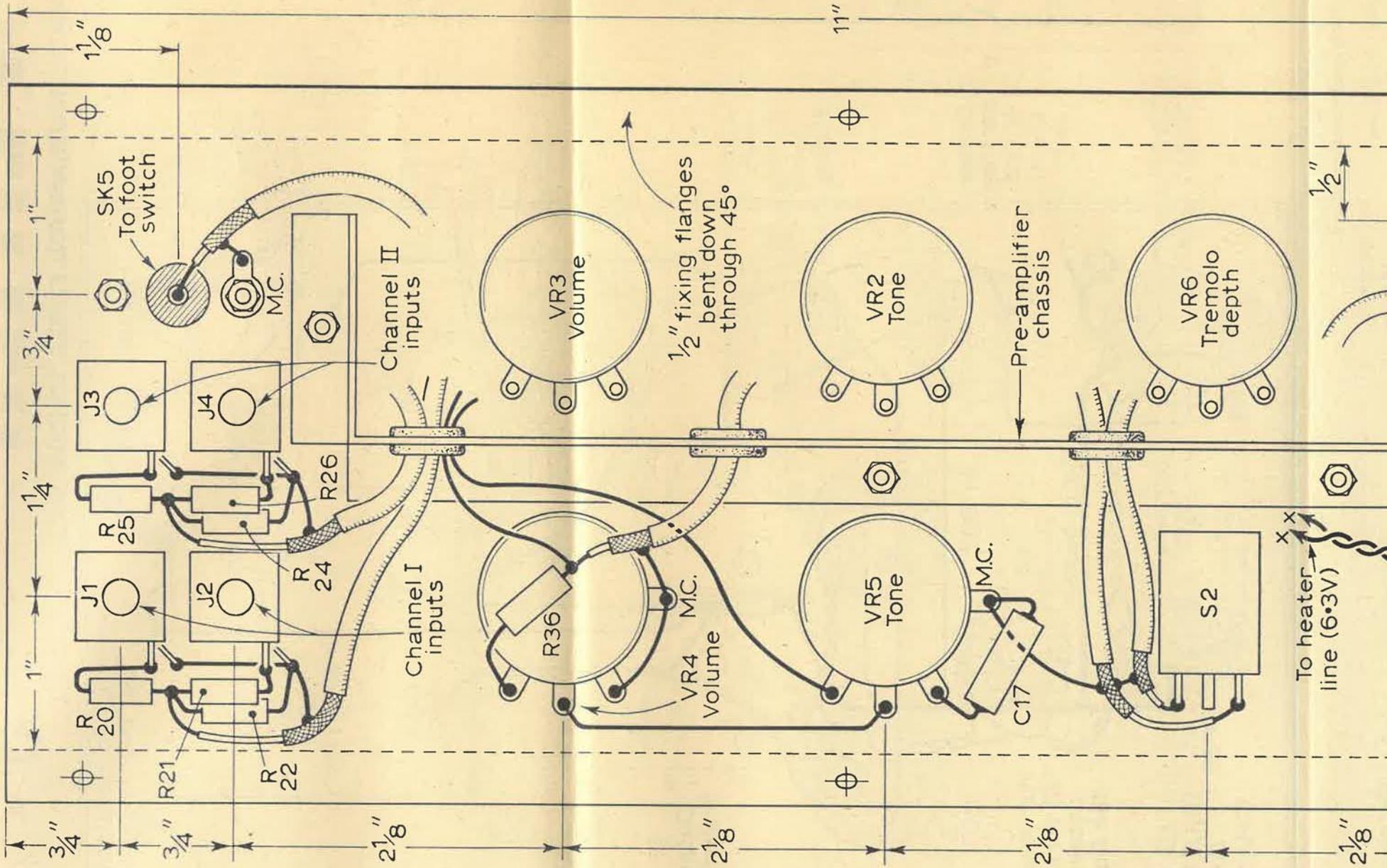

CABINET CONSTRUCTION

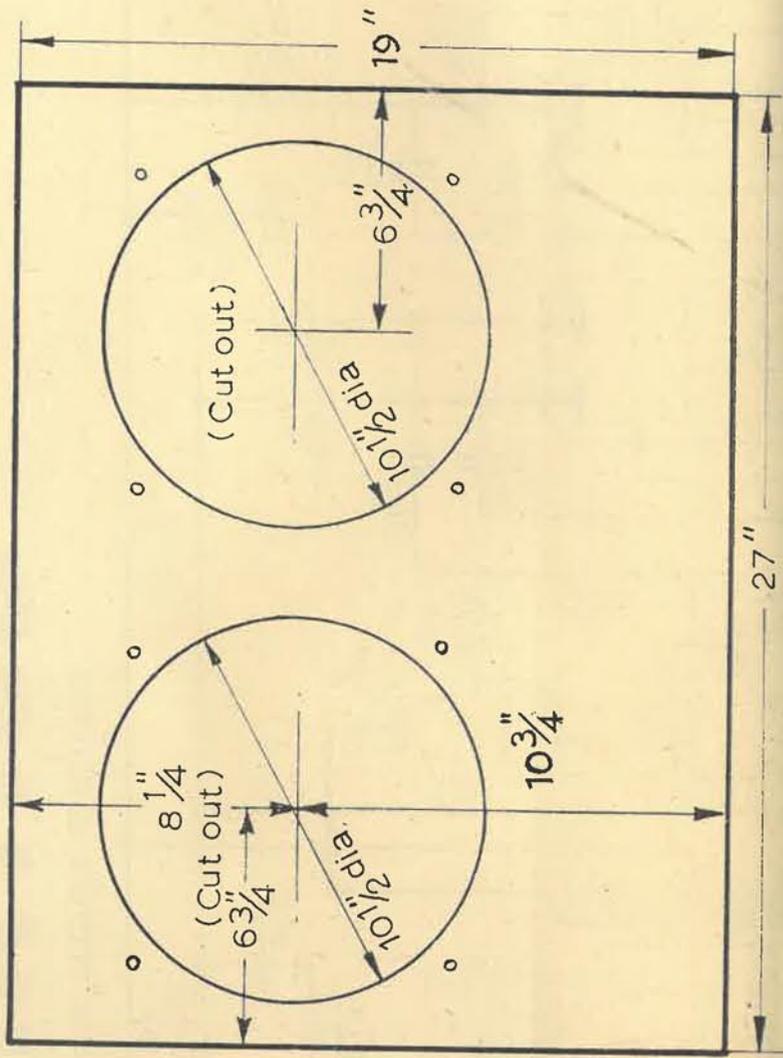


FIG. 8

FRONT CABINET PANEL SHOWING SPEAKER CUT-OUTS

Material 1/2 plywood (Drill mounting holes to suit speakers used)

Cut-out for pre-amp. chassis & panel

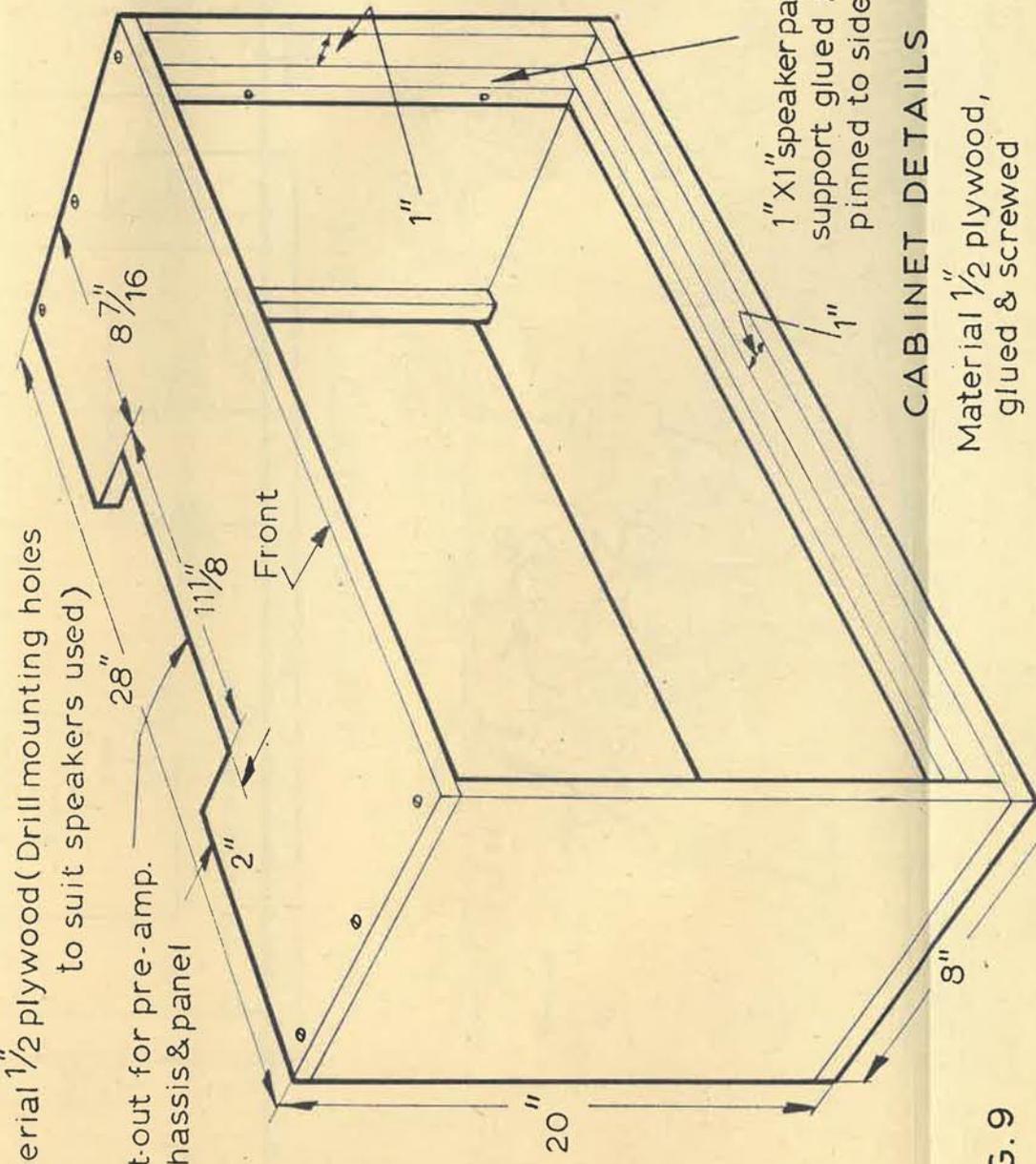


FIG. 9

CABINET DETAILS
Material 1/2 plywood, glued & screwed


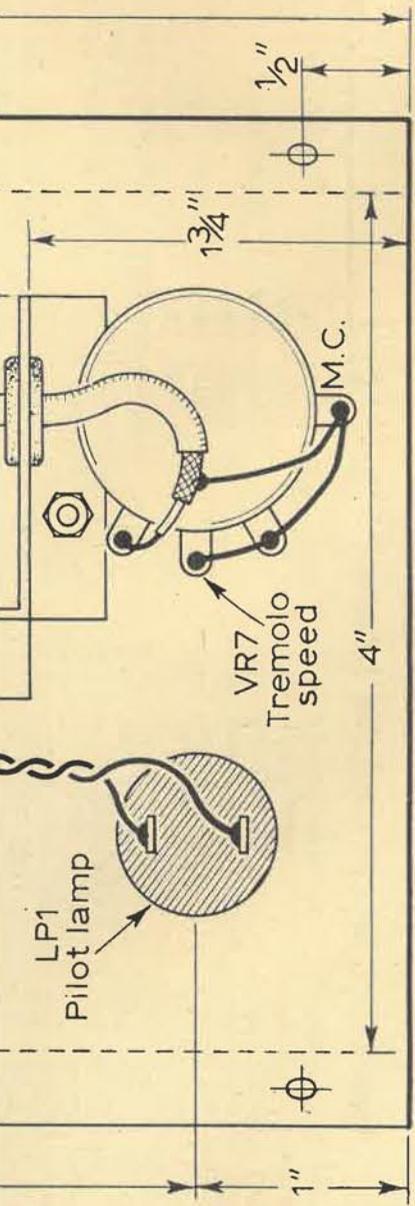
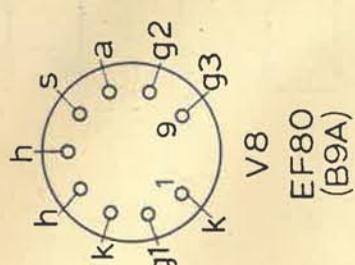
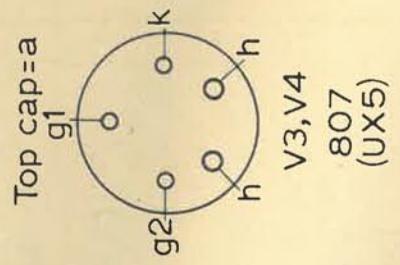
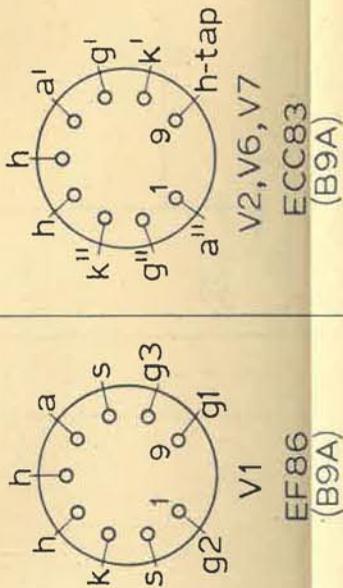


FIG. 6 CONTROL PANEL WIRING

FIG. 7 CHASSIS DRILLING

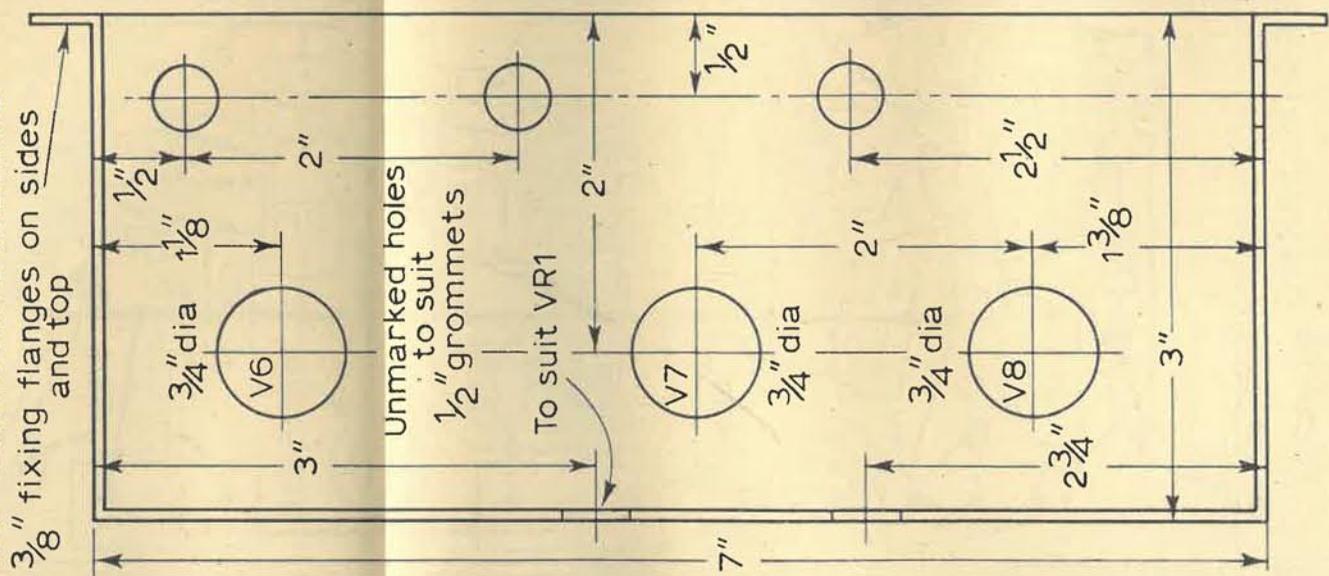

VALVE BASE DETAILS

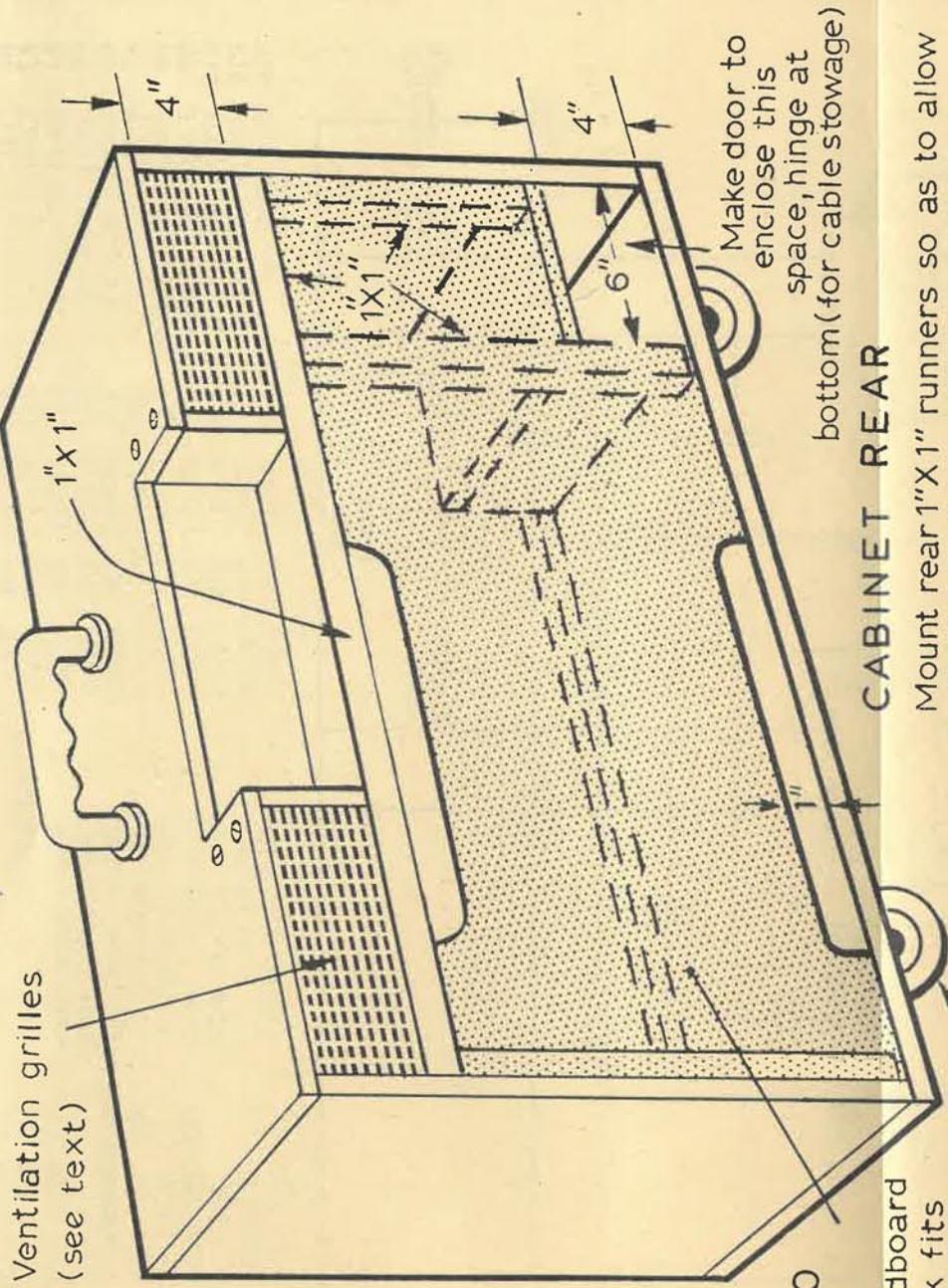


FIG. 10

CABINET REAR

Mount rear 1"X1" runners so as to allow depth of hardboard back to fit flush

Do not forget bottom vent, on hardboard back


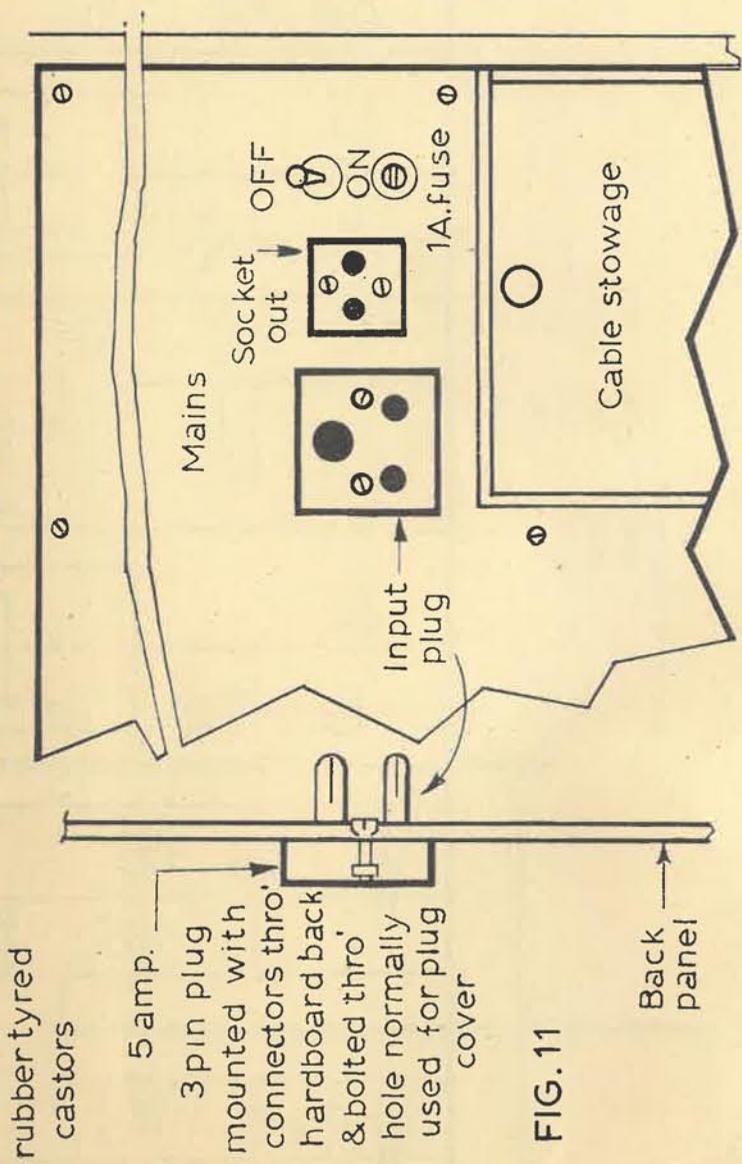


FIG. 11

BACK PANEL showing mains connectors, fuse and switch

Design by
B. L. Phillips

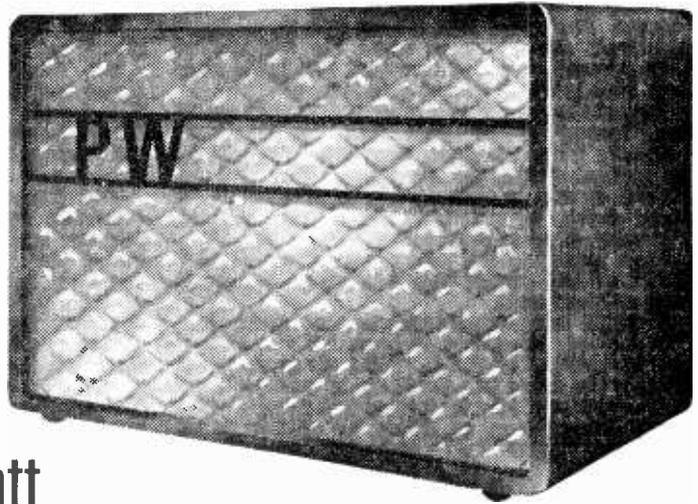

The P.W. 35 Watt GUITAR AMPLIFIER

A QUALITY INSTRUMENT FEATURING
SEPARATE TONE CONTROLS, TREMOLO
FACILITY AND A 20 c/s-20 kc/s RESPONSE

THERE has been a lot of interest shown recently in amplifying equipment for use with the electric guitar and guitar bass. There are, of course, numerous amplifier units available commercially for use with the guitar, but the better types are expensive, and information available to the home constructor is somewhat difficult to obtain, making it rather difficult to build an amplifier from "scratch" unless the constructor has had some experience in this field.

The requirements of an amplifier for use with guitar and guitar bass are rather different in a number of respects to units used exclusively for music or speech reproduction. Using an ordinary amplifier with a guitar invariably gives poor results much to the dismay of the user; apart from the danger of damage to the amplifier itself and the loudspeaker.

Two of the major requirements needed in this application are, a high transient power output over a wide frequency range at low distortion, and an extremely good low frequency response together with high sensitivity. Apart from the amplifier, various electronic "gimmicks" are required, such as the "tremolo" facility, which are not found on ordinary sound amplifying equipment.

Together with the electrical side there is the mechanical layout to consider. The unit must be rugged, the loudspeaker(s) able to handle the full output without distortion or risk of damage, and the whole equipment must be able to stand being run at high outputs for long periods of time. Transportability is another requirement.

After some considerable experimenting and design work, the PRACTICAL WIRELESS Guitar Amplifier was evolved. This amplifier has been compared with the most expensive guitar amplifiers available and will be found as good as anything that can be purchased commercially. Particular attention has been paid to rugged cabinet construction and the use of high quality components—this does tend to make the amplifier somewhat expensive to build, but the final results will more than repay the cost and work involved. *Disappointing results may be caused by using inferior or faulty components that have been lying in the "spares box" some considerable time.*

Most constructors will have no difficulty with building this equipment, for the diagrams with the Blueprint enclosed with this issue of PRACTICAL WIRELESS have been made as clear as possible to enable the amateur to obtain successful results. One point that needs mentioning is that the recommended layouts *must* be used for optimum performance—any old chassis available will just not do. To avoid unwanted feedback, hum, etc., components must be laid out as shown in the diagrams.

It is surprising the number of constructors who cannot get satisfactory results from equipment published in these pages purely because they have not followed the practical layouts given, *The practical layout is as important as the electrical circuit it contains.*

Specification

The PRACTICAL WIRELESS Guitar Amplifier has the following specification:

- 1 Independent twin-channel amplification; separate tone and volume controls; two inputs per channel, four inputs in all.
- 2 Variable speed and depth tremolo facility on one channel, with optional foot switch control.
- 3 A 35W power amplifier with heavy negative feedback and a response of 25c/s to 20,00c/s \pm 3dB.
- 4 Twin heavy duty 12in. loudspeakers, mounted in line.
- 5 Robust cabinet built to allay resonance, even when used at full output with a bass guitar.
- 6 Mains voltage outlet panel for additional attachments such as an echo unit.

Construction of the guitar amplifier will be described step by step, the first part to be dealt with being the power unit and main amplifier.

Power Supply and Output Stages

The power supply and output stages of the amplifier are combined on one chassis entirely separate from the pre-amplifier section. This unit consists of the mains power pack, output stages, the phase inverter and driver valve.

Type 807 valves have been used in the output due to their ease of supply, cheapness and excellent results when used in this circuit. The fact that the anode connections of the 807 are brought out to a top cap, makes amplifier stability easier to arrange as the anode circuits are automatically placed well away from earlier circuit parts.

The complete circuit of the power supply and output stages is given in Fig. 1, and the practical layout of the wiring and components is given in Fig. 2 and Fig. 3. Particular attention should be given to the way the earth busbar is run, with only actual chassis connection being at the outlet socket to the pre-amplifier.

Actual dimensions of the transformers and their mounting feet have not been given as some constructors may wish to use components to hand, the only important point being that the transformers are mounted basically as shown (and, of course, that they are of the correct ratings as specified).

It is suggested that the heater wiring is run first. Only one side of the heater wiring is grounded and this is performed at the earth busbar near the mains transformer. There should be no other earth to the heater wiring. If the heater winding has a centre tap, this should be grounded in place of one side of the supply.

Fig. 3 shows a closer view of the components around the V1 and V2 valveholders, and this layout must be closely followed for stable results. Pay particular attention to the grid stoppers R14 and 15, these are wired close to the 807 grid pins; the wire end from resistor to grid pin not being longer than $\frac{1}{4}$ in.

The cathode bias resistor R16 being a 10W type is rather large in bulk, and if the type with a hole running the entire centre of the component is available, it may be mounted on the chassis by placing a 4BA bolt through it and mounting to the

chassis side. A fibre washer at each end will hold the resistor without damage.

It is rather difficult to show in a simple line drawing such as Fig. 3 the true physical layout of all components exactly as they appear when wired up. Some of the components have, of necessity, been moved further away from their actual positions so their connections can be clearly followed.

The main point to remember when making up this chassis is to keep all signal leads as short as possible, i.e. the signal side of all resistors should be no longer than $\frac{1}{2}$ in., the capacitors being placed so that as little connecting wire as possible is used. All capacitors are wired with the outside foil (usually marked on the component with a black line or the letters "O.S."), towards the earthy side of the circuit. Use plastic or "Systoflex" sleeving over all bare connections, and make sure all soldered connections are well made to avoid dry joints.

All main components such as valveholders, electrolytic capacitors and transformers should be soundly bolted down, preferably with shake-proof washers under all nuts. There is a high level of vibration in the completed cabinet, especially when used with the bass guitar, so all bolted parts need to be very secure.

Transformers

The specified mains transformer is supplied as a double shrouded upright type. For use with this unit, one half of the shroud is removed by undoing the four retaining bolts temporarily. The transformer can then be mounted on the chassis as a half-shrouded, drop through type.

Some mention should also be made about the output transformer. Various types have been tried, and the best one for overall response and power handling qualities was found to be one made by "Radiospares". This particular transformer is known as the "De Luxe" model, and has an excellent specification, and a continuous rated output of 30W. The maximum d.c. current per primary being 125mA. Other output transformers can be used of course, providing they have the correct impedance match and can handle the power. The correct matching in this circuit is a primary impedance of 4k Ω per anode winding, to a 15 Ω secondary.

Testing the Main Chassis

To conduct tests, connect the mains supply to the power and output chassis by coupling direct to the mains transformer primary with a temporary lead.

TESTS:

After all assembly and wiring has been completed, double check all connections with the circuit diagrams, making sure that no earth faults exist on the h.t.+ rail.

Connect a loudspeaker across the output terminals, insert all valves, making sure to clip on the 807 top caps, and switch on.

Check the h.t. voltage, which should be around 450 to 470 volts above chassis. If on warming up a loud howl is heard, switch off and reverse the

negative feedback lead and earth connection to the speaker outlet.

When operating correctly, there should be no background noise heard, apart from just a faint "liveness" in the speaker. *Do not touch the grid input to the EF86, as the resulting intense hum generated may damage the speaker.*

If further tests are required, a crystal gramophone pick-up may be coupled to the valve (via a volume control) for actual sound tests.

DO'S AND DON'TS:

On no account should the amplifier be switched on without having a loudspeaker in circuit. Failure to observe this may destroy the output transformer. If special tests are required without a speaker being operated, then a 15Ω 20W resistor must be wired across the output transformer secondary as a dummy load.

The voltages present (both the mains and the 450V h.t.), are without doubt LETHAL, and the constructor is advised to take great care when running the unit whilst out of its cabinet. *In particular keep well away from the 807 top caps.* High peak voltages of many thousands are present here when a signal is present, and severe burns can be had if they are accidentally touched during use.

The next part to be described will be the pre-amplifier section.

The Pre-amplifier Unit

The pre-amplifier is the most important and critical section of the whole equipment as regards construction and wiring. Poor components or badly arranged wiring can cause untold trouble, such as pronounced hum, crackling and various noises which may take considerable pains to stop.

The inputs of the pre-amplifier are sensitive to about 4mV for a full 30W output, so it will be appreciated that care is needed to keep all noise levels well below this level by at least 40dB.

The worst offender usually in home constructed audio equipment is hum. Special care has been taken to keep this down to a very low level, and providing the instructions given are faithfully followed, the hum present should be negligible.

The circuit diagram is given in Fig 4, and before the construction is commenced, a description of the circuit operation will be given to enable a fuller understanding of the principles involved to be tied up with the practical circuit layout.

The Circuit

On the channel I (normal amplification), the two inputs are coupled to one half of an ECC83 twin triode valve (V6A), the amplified signal being taken via the tone control and volume control to the common outlet lead to the main amplifier unit. The resistive stoppers R20 and R21 in the input jack leads are to prevent interaction between two pick-ups when both are used on one channel.

The more complicated channel is the tremolo channel II. The inputs to this channel are coupled as above to the other half of V6, but in this case the amplified output at V6B anode is coupled to another triode V7A, which is the tremolo modula-

tor stage. Both halves of V7A and V7B are cathode coupled, and a low frequency signal is applied to the second triode from the phase shift oscillator V8.

This low frequency signal causes the cathode voltage on V7 to vary in sympathy, causing the gain of V7 to vary in direct proportion. The time constant of V7 cathode circuit is arranged so that it follows the high relative frequency of the audio signal, but allows the oscillator signal to be developed across the cathode resistor capacitor, R32, C23. At the output of V7A, there is both audio (now tremulant) plus some oscillator fundamental.

The oscillator content must be removed, otherwise a loud "thumping" will be heard in the output. This is accomplished by the high pass filter network C13, C14, C15 and R33, R34.

After filtering, the signal passes to the common outlet as for channel I, via its tone control VR2 or VR5. The variable resistor, VR1, is a preset gain control for V7, and by feeding back some of the output to the grid circuit, the overall gain of both V6 and V7 can be made identical to channel I.

An extra facility incorporated in this design and not often found in commercial amplifiers of this type, is a switch (S2) to remove completely the tremolo facility and make the response curve of the tremolo channel identical to that of channel I. The high pass network used in the tremolo circuit causes the audio response to be rather sharp, and although ideal for guitar use, with a microphone is rather too "toppy", thus this switch enables any channel to be used for high quality reproduction whenever so required.

V8 is the low frequency oscillator stage, and has a range of approximately 5 to 12c/s. The speed is controlled by VR7, and the depth or intensity controlled by VR6. A footswitch socket (SK5) is placed across VR5 and enables an instant on/off control of the tremolo effect remote from the amplifier. The 0.1μF capacitor C18 across this socket removes oscillator harmonics and also makes the switching electrically silent.

Note the rather high values of capacitance in the screen and cathode circuits of V8. This is, of course, for maximum efficiency at these very low frequencies.

Screened Leads

The pre-amplifier is built up from two sub-assemblies, a small chassis and a control panel which are bolted together.

There is, of necessity, a large amount of screened lead in the construction of the pre-amplifier unit, and where screened leads are specified they must be used. All connections must be correctly soldered, and the practical layout shown followed as closely as possible.

Particular attention must be paid to the heater wiring in the pre-amplifier unit, all leads being tightly twisted and kept as far away from the signal circuits as possible. On no account is the heater wiring to be made an "earth return" circuit.

The chassis layout is given in Fig. 5 and the drilling details in Fig. 7. The layout and wiring of the associated control panel is given in Fig. 6.

Cabinet Construction

Figs. 8 to 11 and the drilling details in Fig. 7 give full details of the cabinet. It is suggested that the front panel (Fig. 8) be made first, as this fits *inside* the cabinet, and it is important that adequate clearance be made for this panel to fit against the 1in. x 1in. supports when the speaker fret material is in place.

After drilling and cutting out the speaker apertures, the speaker units should be laid on the rear of the panel, making sure they line up centrally over these holes, and the mounting holes can be marked. Countersink these holes on the front of the panel, and using countersunk bolts, firmly bolt down the speakers, preferably with

the cabinet has been covered with *Vynide* or similar material. The panel is then pushed home and fixed as above. Cover the sides and bottom runner of the pre-amplifier cut-out.

In the connection of the cabinet, the two vertical dimensions in Fig. 8, 8½in. and 10½in. were incorrectly printed on a number of Blueprints as 8¼in. and 11¼in.

When covering is completed, make the hard-board back as shown in Fig. 10, and drill and mount the power input attachments as per Fig 11. When finished, a coat of very dark wood stain gives the back a clean finish.

The top ventilation grills are made from ordinary metal loudspeaker grill material, cut the width of apertures, with a length some 2in. greater

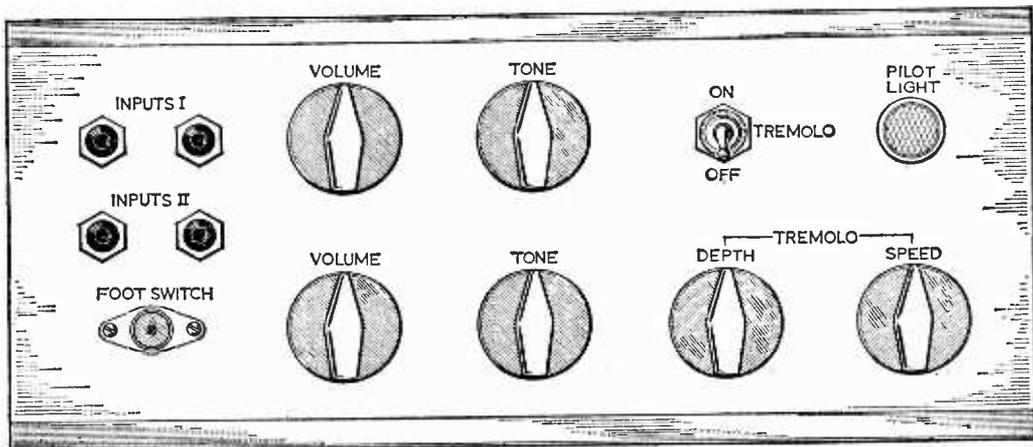


Fig. 12: Layout of the pre-amplifier control panel.

their terminals facing downwards. The next job is to cover the speaker panel front with suitable loudspeaker material such as "TYGAN". Close weave material is not recommended. Use an adhesive such as "EVOSTICK", spreading enough on the panel to produce a thin film (more will creep through the material) and place the material centrally on the panel. Allow about an inch overlap to the back, and keep tension on the edges of the material until dry. Then glue the edges down, removing any overlap at the corners of the panel with a sharp knife when the glue has thoroughly dried.

The remainder of the cabinet construction is not really difficult, apart from possibly the cable stowage compartment. This is a 3-ply box mounted on the cabinet floor on the right hand rear side. All joints should be glued and pinned, a piece of wood, 4in. by 6in. glued to the speaker panel rear makes an easy mounting for the side and top of this compartment. A door is made for the front of this compartment, hinged at the bottom, with a door catch fastener at the top. A small supboard knob completes the job.

Incidentally, the speaker panel may be screwed to the 1in. x 1in. supports, or may alternatively be glued and pinned. The last method gives the best visual effect as no screw heads are visible.

The panel should not be fixed until the rest of

than these openings. Bend one edge of the metal inwards for 1in. and screw to the cabinet side, then bend the other end to fit into the hole correctly. Do not be frightened to bend the material—it is easily straightened. This last edge is then screwed to the pre-amplifier cut-out side pieces. This operation is quite "fiddly" but once done need never be touched again.

Installing Amplifiers

The two loudspeakers must be of the heavy duty type. Several manufacturers produce speaker units specially designed for guitar amplifiers. Both speakers should be 12in. diameter, have 15Ω speech coils and be rated for 20 to 25W power handling capacity.

The first job here is to connect the speaker wiring, and to phase the speakers themselves.

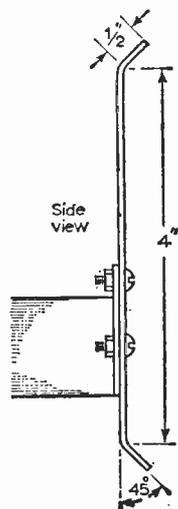


Fig. 13: The method used to fix the control panel to the cabinet.

Temporarily couple a 3V battery to one speaker and note whether the cone moves *in or out*. Mark the speaker terminal connected to the positive battery pole. Now, repeat the procedure on the second speaker, making sure it moves in the same direction as the first, and again mark the terminal which has the battery positive on it. Wire both speakers in parallel, ensuring the marked terminals are coupled together, and test finally with the battery again. Both speaker cones should move together in the same direction.

Place the power amplifier unit in the bottom of the cabinet, with the mains transformer roughly in the centre below the carrying handle. Check the cabinet for carrying balance, and alter the unit until the centre of gravity is as near the centre as practical.

Screw down the chassis mounting feet. Run the mains feed to the hardboard back and connect to the fuse and on/off switch there. Leave about 3ft. of flex between the two so the back can be removed and taken out of the way when servicing. Connect the loudspeaker leads to the outlet strip on the chassis.

After giving the completed pre-amplifier control panel a coat of paint (black gloss is suggested), place the knobs in position and slide the unit in place in the top cabinet cut-out. Screw down securely, and plug the flying lead into the main chassis socket. Make certain that the leads are well away from the power valves, and if necessary cleat to cabinet sides.

At this stage leave the back of the cabinet open to enable final adjustments to be made.

Final Tests

Turn gain controls to OFF and switch on. There should be hardly any noise level under these conditions, if there is, suspect a fault condition.

Make sure S1 is in the NORMAL position, and slowly turn channel II volume up. At maximum a fairly high noise level will be evident—mostly hiss with some hum. This is normal as the inputs are wide open. Shorting one input jack out should remove all the hum content.

Repeat on channel I, checking that tone controls operate.

If the noise level of channel II is far greater than channel I, adjust VR1 carefully (with S1 in tremolo position) until noise levels are identical.

If possible, couple a signal source, such as a radio set, to one input jack via a separate volume control to avoid overloading, and check the amplifier for power output and quality. Keep the input signal very low by adjusting the separate volume control, using the main amplifier controls for level adjustment.

The tremolo controls can be tried on this signal, and as there may be some snags here, some hints are given for curing any slight troubles encountered.

- 1 Tremolo satisfactory, but some "thumping" when depth control full: place additional 100k Ω resistor across R33, increase value of C18 to 0.2 μ F.
- 2 Tremolo depth satisfactory, but oscillator stops towards low end of speed range: check C24, C19 for leakage, change V8, alter R39 to 1M Ω . If possible test the equipment with a guitar and

make sure the gain of channel II is identical to channel I by adjusting VR1.

Fault Finding

It is quite possible some slight faults may exist after completion, and some common faults and possible cures are listed below.

HUM: Most likely induced from heater chain. If mains transformer has no centre tap, remove earth on one side of heater chain and connect "hum-dinger" control across the chain at mains transformer end, with centre slider to chassis. Adjust until hum is at its lowest level. A valve with a heater cathode short will give considerable hum as will faulty smoothing capacitors.

DISTORTION: Obviously, distortion does set in at very high outputs, or if the input signal is overloading the pre-amplifier, but if it is present all the time at low signal levels, suspect instability.

Check that all grid stoppers are the correct value, and that all screened leads are fitted as specified. Metal screens over early valves are not essential, but the fitting of them may assist in removing instability; the ECC83 on the power chassis is worth a try in difficult cases. In some circumstances earthing the loudspeaker frames to chassis can remove awkward and often difficult to cure instability. Generally though, instability is caused by poor layout conditions, unscreened leads, etc., and if the layouts shown are closely followed, no trouble of this nature should occur.

Always ensure that the output valves have similar anode currents, although a difference between them of 5 to 10mA is not important. A large discrepancy between them can, however, cause low output power with severe distortion. ■

INCLUDED IN THE MAY ISSUE OF PRACTICAL TELEVISION

- ★ *A Rotatable Aerial for Improved DX Reception*
- ★ *A TV Baby Alarm*

Plus: Servicing and Fault-finding, Articles, DX-TV Feature, Problems Solved, Amateur TV Transmitting, etc.

**ORDER YOUR COPY NOW—
OUT APRIL 22nd, PRICE 2/-**



Offer the Finest Value to HOME CONSTRUCTORS

We consider our construction parcels to be the finest value on the home constructor market. If on receipt you feel not competent to build the set, you may return it as received within 7 days, when the sum paid will be refunded less postage.



The SKYROVER

Controls: Waveband Selector, Volume Control, with on/off Switch, Tuning Control. In plastic cabinet, size 10 x 6 1/2 x 3 1/4 in. with metal trim and carrying handle.

Can be built for **£10.19.6** P. & P. 5/-
 H.P. Terms: 22/- deposit and 11 mths. at 21/-.

THE SKYROVER and SKYROVER DE LUXE

GENERAL SPECIFICATION:
 7 transistor plus 2 diode superhet, 6 waveband portable receiver. Operating from four 1.5 v. torch batteries. The SKYROVER and SKYROVER DE LUXE covers the full Medium Waveband and Short Waveband 31-94 M., and also 4 separate switched band-spread ranges. RM 15M, RM and 25M, with Band-Spread Tuning for accurate Station Selection. The coil pack and tuning heart is completely factory assembled, wired and tested. The remaining assembly can be completed in under three hours from our easy to follow, stage by stage instructions.


SPECIFICATION:
 Superhet, 470 Kc/s. All Mullard Transistors and Diode. Uses 4-U2 batteries. 5in. Ceramic Magnet P.M. Speaker. Easy to read Dial Scale. Band Spread Tuning. 500 MW Output. Telescopic Aerial & Ferrite Rod Aerial. **WAVEBAND COVERAGE:** 180-576M; 31-94M and Band Spread on 13, 15, 19 and 25 metre Bands.

The SKYROVER DE LUXE

Tone Control Circuit is incorporated, with separate Tone Control in addition to Volume Control, Tuning Control and Waveband Selector. In a wood cabinet size 11 1/2 x 6 1/2 x 3 1/4 in., covered with a washable material with plastic trim and carrying handle. Also car aerial socket fitted.

Can be built for **£12.19.6** P. & P. 5/-.

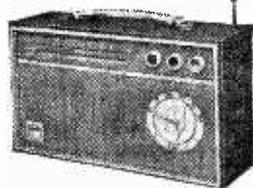H.P. Terms: 26/- deposit and 11 mths. at 24/6. Data for each receiver 2/6 extra. Refunded if you purchase the parcel. Four U2 batteries included FREE All Components Available Separately.



The "REALISTIC" Seven

* 7-transistor Superhet. * 350 milliwatt output into 4in. high flux speaker. * All components mounted on a single printed circuit board, size 5 1/2 x 5 1/2 in. in one complete assembly. * Plastic cabinet with carrying handle, size 7 x 10 x 3 1/4 in. in Red/Grey, Blue/Grey or all Grey. * Easy to read dial. * Externalsocket for car aerial. * I.F. frequency 470 Kc/s. * Ferrite rod internal aerial. Operates from PP9 or similar batteries. * Full comprehensive data supplied with each receiver. * All coils and I.F.'s etc. fully wound ready for immediate assembly. **LASKY'S PRICE** for the complete parcel including Transistors, Cabinet, Speaker, etc., and Full Construction Data. Can be built for **£5.19.6** P. & P. 4/6.

PP9 Batt. 2/6. Data and instructions separately 2/6. Refunded if you purchase the parcel.



REALISTIC Seven DE LUXE

With the same specification as standard model—PLUS a superior wood cabinet in contemporary styling. ALSO a full vision circular dial.

FOR ONLY **£1** EXTRA P. & P. as std. model

The "Sixteen" Multirange METER KIT

This outstanding meter was featured by *Practical Wireless* in the Jan. '64 issue. Lasky's are now able to offer the complete kit of parts as specified by the designer. The "Sixteen" Multirange offers the home constructor and serviceman an instrument that will meet most of his requirements for voltage, current and resistance measurement. There are 16 switched ranges: 9 for voltage measurement, 4 current ranges and 3 resistance ranges. All British components are used throughout. The instrument case is supplied with the meter movement built-in. The two scales are clearly printed in black on white and are very easy to read.

RANGE SPECIFICATION: D.C. volts: 0-2.5-25-50-250-500 at 20,000Ω/V. A.C. volts: 0-25-50-250-500 at 1,000Ω/V. D.C. current: 0-50μA, 0-2.5-50-250 mA. Resistance: 0-2,000Ω, 0-200kΩ, 0-20MΩ. Basic movement: 40μA i.s.d. moving coil. With universal shunt full scale deflection current is 50μA. Size: 1 1/2 in. x 1 1/2 in. x 1 1/2 in. Controls: 12 position range switch; separate slide switch for A.C. volts—D.C. ohms; ohms zero adjustment pot. meter; meter zero. External connections: Two 4mm. sockets for test lead plugs. Power requirements: One 1.5V. and one 1.5V. batteries. Complete with all parts and full construction details. Data and circuit avail. separately 6/-, refunded if all parts bought. Pair of Batts. 2/5 extra.



LASKY'S PRICE
£5.19.6 P. & P. 5/-

H.P. Terms: 21/- deposit and 5 months at 21/-.

TAPE SPlicer OFFER!

By famous manufacturer. All metal nickel plated construction with separate razor blade—securely clamps tape while splicing. Listed at 18/6. **LASKY'S PRICE 14/6 POST FREE.**

HEADPHONES

S. G. Brown Type F earphones, moving iron 2000 ohms, hand-held type but a headband could easily be fitted. **LASKY'S PRICE 14/6. P. & P. 1/6.**

E.M.I. 4-SPEED RECORD PLAYER

New, unused and individually boxed fitted with lightweight pick-up with ACOS G.P. 73/2 stereo cartridge. Cabinet space required 13 1/2 x 12 1/2 x 4 1/2 in. A 9in. metal turntable is fitted. For use on 200/250 volt A.C. Mains, with Auto-stop. The stereo cartridge will play all types of Mono Records, 78's, L.P.s etc., but if desired a G.P. 67 LP/78 Mono cartridge will be supplied in lieu of the GP73 at no difference in cost.



LASKY'S PRICE 79/6 P. & P. 3/6 extra.

AUTO. RECORD PLAYER

H.M.V. 45 T.P.M. AUTOMATIC RECORD PLAYER. Designed to take only 45 r.p.m. 7in. discs. Will play up to 8 automatically. Fitted with lightweight pick-up and crystal cartridge, mounted on a plinth. For 200/250 v. A.C. mains. Size approx. 10 x 10 x 5in. **LASKY'S PRICE 59/6. P. & P. 3/6 extra.**

GUITAR PICK-UP

Crystal-high imp. Size only 1 1/2 x 1 1/2 x 1 in. Clips to finger board—no screws. Complete with cable. **LASKY'S PRICE 15/11. p. & p. 1/-.**

207 EDGWARE ROAD, LONDON, W.2. | 33 TOTTENHAM COURT ROAD, W.1. | 152/3 FLEET STREET, LONDON, E.C.4.
 Near Praed St. PADDINGTON 3271/2 | Nearest Stn., Goodge St. MUSEUM 2605 | Telephone: Fleet Street 2833.
 BOTH OPEN ALL DAY SAT. Early Closing Thurs. Mail Orders to Dept. P.W., Edgware Rd. Open all day Thursday. Early closing Sat.

**SURPLUS UNUSED TRANSFORMERS
BY WELL KNOWN MANUFACTURERS**

- 45 watt P.P. output transformer—suitable KT66's. 22/6
500 ohm secondary
- 50 watt P.P. output transformer—suitable EL34's. 35/-
Secondaries: 500 ohm and 15 ohm
- Mains transformer. 240v Primary. 225v-0-225v 15/-
65mA; 4v 2.3a; 4v 1 1/2a
- Mains transformer. 240v Primary. 290v-0-290v 35/-
260mA; 4v 8v; 4v 2a; 4v 4 1/2a; 6.3v 1 1/2a
- L.T. transformer. 240v Primary. Secondary tapped 19/6
12v, 13v, 14v. 6 amps.
- L.T. transformer. 240v Primary. Secondary tapped 19/6
1 1/2v, 13 1/2v, 15 1/2v. 6 amps. Separate 9v 1 1/2a.
(All prices include post and packing).

RADIO EXPERIMENTAL PRODUCTS LIMITED
33 MUCH PART STREET, COVENTRY

96 pages of factual tabulated data . . .

**"PRACTICAL WIRELESS" RADIO AND
TELEVISION REFERENCE DATA**

Compiled by J. P. Hawker

Contains full details of colour codes; everyday formulae, for calculating the values of biasing components, potential dividers, resonance, gain, etc.; aerial dimensions; a quick frequency-wavelength conversion table; stations and frequencies; common symbols and abbreviations; notes on amateur radio and a list of call-sign prefixes; communication receiver I.F.s; mathematical data including logarithm tables; wire and cable data; battery equivalents; valve, transistor and picture tube pin connections, bases, ratings and equivalents including selected CV types. 96 pages, illustrated, over 62 pages of tables.

10s. 6d. FROM ALL BOOKSELLERS
... or, in case of difficulty 11s. 6d. by post from
GEORGE NEWNES LTD., Tower House,
Southampton Street, London, W.C.2. **NEWNES**

RETURN-OF-POST SERVICE

We offer a really efficient Mail Order Service on all items stocked. All cash orders are dealt with on the day of receipt. ★ Hire purchase orders are subject to slight delay but this is kept to the absolute minimum.

● **SPECIAL OFFER!! STEREO CARTRIDGES**

RONETTE 105 Stereo/Mono Cartridge. Complete with fixing bracket and stylus. List 59/4. OUR PRICE 23/6. Post Free.

● **"P.W." GUITAR AMPLIFIER**

Detailed list available for the amplifier described in this issue.

● **ILLUSTRATED LISTS**

Illustrated lists are available on LOUDSPEAKERS, TAPE DECKS, TEST GEAR, GRAMOPHONE EQUIPMENT, AMPLIFIERS. Any will be sent free upon request.

● **AMPLIFIER KITS**

We have full stocks of all components for the Mullard 510, Mullard 3-3, Mullard 2 and 3 Valve Pre-amp, Mullard Stereo, Mullard Mixer. Fully detailed list on any of these sent upon request.

Instruction Manual: All Mullard Audio Circuits in "Circuits for Audio Amplifiers", 9/5. Post free.

● **LATEST TEST METERS**

	Cash Price	Deposit	Hire Purchase Mthly/Pmts.
AVO Model 8 Mark II	£24. 0/0	£4.16.0	12 of £1.15.2
AVO Model 7 Mark II	£21. 0/0	£4. 4/0	12 of £1.10.10
AVO Multimeter Mark 4	£9.10.0	£1.18.0	12 of 14/4
T.M.K. TP10	£3.18.8	£1. 3/6	3 of £1.2.0
T.M.K. TP5N	£5.19.6	£1.15.6	3 of £1.1.4
T.M.K. Model 500	£8.19.6	£1.15.6	12 of 13/8
RAYLOR MODEL 127 A	£10.10.0	£2. 2/0	12 of 15/8

Full details of any of the above supplied free on request.
The AVO models 7 and 8 are both latest models from current production—not to be confused with Government Surplus.

● **TAPE RECORDING EQUIPMENT**

	Cash Price	Deposit	Hire Purchase Mthly/Pmts.
ALL CARRIAGE FREE			
COLLARO STUDIO, latest model. Two track. Bradmatic Heads.	£10.19.6	£2. 3/6	12 of 16/4
Four Track, Marriott Heads	£17.17.0	£3.12.0	12 of 26/2

MARTIN TAPE AMPLIFIER KITS
Tape Amplifiers
For Collaro 8311-V 2-Track £11.1.0 8311-V 4-Track £12.12.0
Tape Pre-Amplifiers
For Collaro 8312-CP 2-Track £9.8.0 8312-4-CP 4-Track £9.9.0
Drop through assembly for mounting 8312 Pre-Amp under Collaro Deck, £11.1.6.
Carrying Cases with speaker. For Collaro Deck and 8311 Amplifier, £5.5.0.

H.P. TERMS available on decks, amp. and cases. Ask for quote.
MULLARD TAPE PRE-AMPLIFIER KIT
We stock complete kits and all separate components for the Mullard Tape Pre-Amplifier. Fully detailed list available.

● **HI-FI LOUDSPEAKERS**

GOODMANS: Axiette 8in., £5.5.7; Axiom 10in., £6.5.11; 12in. Axiom 201, £10.17.4; 12in., Axiom 301, £15.4.8; 12in., Audion 51 Bass, £9.2.8; 12in., Audion 61 Bass, £14.7.8; Treobax Tweeter, £6.10.2; X05000 Crossover unit, £2.0.11.
WHITELEY: HF1016 10in., £7.0.0; HF1012 10in., £4.7.6; HF816 8in., £6.0.0; T16 8in., £5.13.6; T10 Tweeter, £5.3.3; F33 Tweeter, £1.10.6; CX3000 Crossover unit, £1.11.6; CX1500 Crossover unit, £9.0.0. H.P. Terms available on all speakers.

● **SPECIAL LOUDSPEAKER BARGAINS**

E.M.I. 13 x 8in. Elliptical. 10 watts. 3 ohms. 38/6. P. & P. 2/6.
RICHARD ALLAN 12in. Round. 5 watts. 3 ohms. 27/6. P. & P. 2/6.

● **STEREO COMPONENTS**

Morganite lagged potentiometers as specified for the Mullard circuits. ★ Log/Anti-Log, 500k, 1 meg., 2 meg. ★ Log/Log, 50k, 250k, 1 meg. ★ Lin/Lin 250k, 500k, 1 meg., 2 meg. All 10/6 each. Postage extra.

● **GRAMOPHONE EQUIPMENT**

ALL LATEST MODELS Hire Purchase
ALL POST FREE Cash Price Deposit Mthly/Pmts.

	Cash Price	Deposit	Mthly/Pmts.
RECORD CHANGERS			
GARRARD AUTOSLIM (Mono PU)	£6.17.6	£1.12.6	6 of £1
GARRARD AUTOSLIM (Mono PU)	£11. 9/0	£2 6/0	12 of 16/11
GARRARD AUTOSLIM AT6 (Stereo/Mono PU)	£12. 5/4	£2. 9/4	12 of 18/-
B.S.R. UA14 (TC8 Mono PU)	£6.15.0	£1.10.0	6 of £1
B.S.R. UA14 Monoreh (TC8 Stereo/LP78)	£7.15.0	£1.18.0	6 of £12.0
B.S.R. UA15 (TC8 Mono PU)	£7.15.0	£1.18.0	6 of £12.0
B.S.R. UA5 (TC8 Stereo/LP78)	£8.15.0	£2.6.0	6 of £14.0

● **SINGLE RECORD PLAYERS**

B.S.R. TU12 (TC8 Mono PU)	£4.1.3	£1. 8/3	3 of £12.0
B.S.R. GU7 (TC8 Mono PU)	£4.18.3	£1. 8/3	3 of £18.8
GARRARD SK10 (Mono PU)	£5. 9/11	£1.12.11	3 of £19.0

● **TRANSCRIPTION UNITS**

GARRARD HF (GC8 PU)	£16.12.6	£3. 6/6	12 of £14.5
PHILIPS AG1016 (SM/PU)	£12.12.0	£2.10.0	12 of 18/6

Many of the above can be supplied for stereo working. See our Gramophone Equipment List for details.

● **JASON F.M. TUNERS**

We stock all parts needed for the construction of these excellent tuners. All parts can be supplied separately but we can offer attractive reductions in price if all items are purchased at same time as follows.

- FMT1, £f.12.6; FMT2 (less power), £7.15.0.
- FMT2 (with power), £9.12.6; FMT3 (less power), £9.9.6.
- FMT3 (with power), £11.7.6; Mercury 2, £10.14.6.
- JTY, £f.12.6.

Hire Purchase Terms available. Ask for list.

● **OUTPUT TRANSFORMERS**

GILSON: W0696A, W0696B, 50/6, post 2/6. W0710, 55/6, post 2/6. W0892, 62/3, post 2/9. W0767, 27/-, post 1/6. W0796A, 57/6, post 2/6. W01932, 84/-, post 3/-.
PARTRIDGE: P3667, 75/-, post 2/9. P4131, 75/-, post 2/9.
PARMEKO: P2627, 49/9; P2642, 47/3; P2643, 49/9. All plus post 2/9; P2641, 30/9, post 2/-; P2926, 16/9, post 2/-; P2932, 43/-, post 2/6.

● **MAINS TRANSFORMERS**

GILSON: W0741A, 63/-, post 4/-; W0839, 48/9, post 2/9; W01328, £0/6, post 3/6; W01288, 58/-, post 3/6; W01566, 80/-, post 4/6; W01341 Choke, 36/-, post 2/-.
PARTRIDGE: P2341, 37/-, post 2/9; P2830, 57/3, post 3/3; P2644, 80/-, post 4/-; P2930, 43/-, post 3/-; P2931, 59/6, post 3/3.

★ **TERMS OF BUSINESS**

Cash with order or C.O.D. We charge C.O.D. orders as follows: Up to £5, minimum of 4/2. Over £5 and under £10, 2/8. Over £10, no charge. Postage extra on CASH order. Under £5 except where stated. Postage extra on overseas orders irrespective of price.

WATTS RADIO

(MAIL ORDER) LTD.

54 CHURCH ST., WEYBRIDGE, SURREY

Telephone: Weybridge 47556

Please note: Postal business only from this address
Callers welcome by appointment

★ **HIRE PURCHASE TERMS**

Available on any item. Repayments over 3, 6 or 12 months as below. Three months: Deposit 6/- in the £. Service charge 5%, minimum charge 10/-. Six months: Deposit 3/- in the £. Service charge 7 1/2%, minimum charge 15/-. Twelve months: Deposit 4/- in the £. Service charge 10%, minimum charge 20/-.

TEST GEAR accessories

Part 4

BY C. MACKAY

CONTINUED FROM PAGE 1186 OF THE APRIL ISSUE

THIS month, the construction of an amplifier probe will be discussed. Reference to the circuit diagram given in Fig. 12 will show that the amplifier is quite conventional.

The anode load of the EF91 valve (R4) has a rather lower value than usual (10,000Ω), but this considerably improves the high-frequency response. The cathode decoupling capacitor, C4, is itself shunted by another capacitor, C3, to improve the high frequency decoupling.

The grid leak resistor R1 has the rather high value of 10MΩ. This gives a very high input

HIGH-FREQUENCY RESPONSE

The high-frequency response is excellent, and is substantially flat (± 3 dB) up to at least 40kc/s. The probe will pass a 30kc/s square wave with negligible distortion. This makes this unit particularly valuable for the testing of audio equipment with square waves and an oscilloscope.

Also, the overall voltage gain of the unit is 15 times approximately (about 25 decibels). As a d.c. battery is used for the heater supply and no other mains voltage is present inside the screening can, there is no hum pick up, and thus any low level phenomena which are being investigated will not be masked by hum.

The gain provided by this unit is still useful at 4Mc/s. and no sine wave distortion was observed at this frequency. This top frequency limit is fixed by the capacitance across the output due to the self capacitance of the coaxial feeder cable to the oscilloscope or measuring instrument.

BUILDING THE PROBE

This probe unit was built inside an old i.f. transformer screening can, similar to that used last

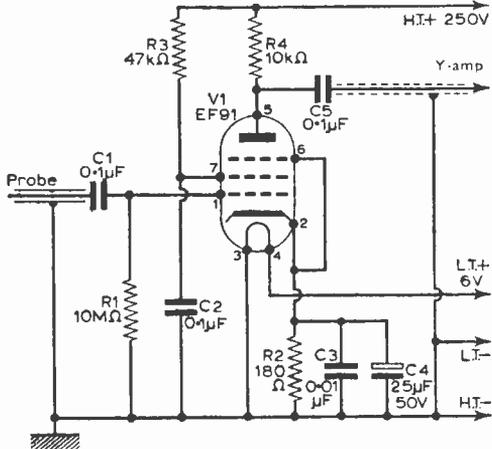


Fig. 12: The circuit of the amplifier probe unit.

impedance, but at the expense of low-frequency response. This is because, at low frequencies, the impedance of C1 becomes greater and since C1 and R1 form a potentiometer attenuator, the fraction of the input voltage which is applied to the grid is reduced whenever the frequency is reduced to the point where the impedance of C1 becomes comparable with that of R1. Thus, the response begins to drop off noticeably at about 40c/s.

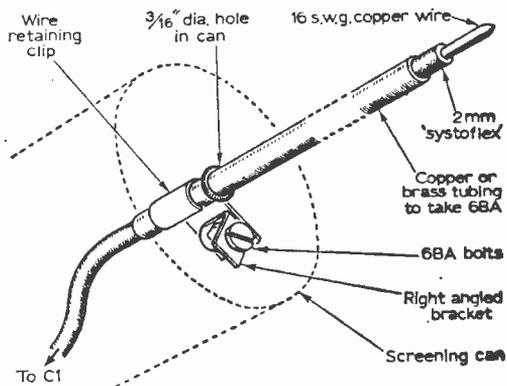


Fig. 13: Details of the probe assembly.

**COMPONENTS LIST
FOR AMPLIFIER PROBE UNIT**

- R1 10M Ω (may be reduced to 1M Ω)
- R2 180 Ω
- R3 47,000 Ω
- R4 10,000 Ω
- C1 0.1 μ F
- C2 0.1 μ F
- C3 0.01 μ F
- C4 25 μ F 50V
- C5 0.1 μ F
- V1 EF91 Mullard

Miscellaneous:

One B7G valveholder. Screening can. Paxolin or printed circuit board. 2 yards of coaxial cable. 2 yards of 3-core cable (for power supply). Systoflex, nuts, bolts.

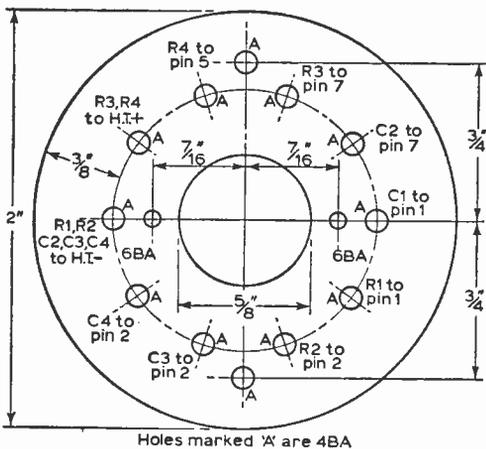


Fig. 15 (right): A suggested printed circuit layout for the panel.

month for the cathode follower probe, and the actual probe section was made in exactly the same way. The reader is therefore referred to last month's issue for further details if those shown in Fig. 13 are inadequate.

The main wiring is again built on to a circular piece of paxolin suitably drilled as in Fig. 14a.

PRINTED CIRCUIT TECHNIQUE

This method of construction lends itself easily to the use of a printed circuit board, and a suggested pattern is given in Fig. 15 for those interested in using copper clad board.

Drilling of the etched circuit should be very carefully carried out, and all drilling should be done from the laminated (copper) side of the printed circuit board. All large holes should be first drilled with a small bit, and progressively larger bits should be used to enlarge the hole until it is the correct size.

The board should, on no account, be bent or subjected to any stress or strain as the laminated copper may crack minutely giving either an open circuit or a very noisy contact.

The connecting cables should be connected


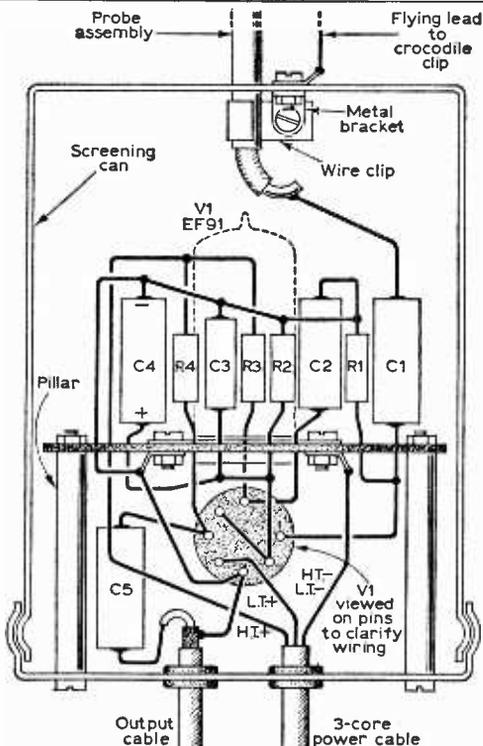


Fig. 14a (left): Drilling details of the paxolin panel for the amplifier probe.

Fig. 14b (above): Component layout and wiring inside the can.

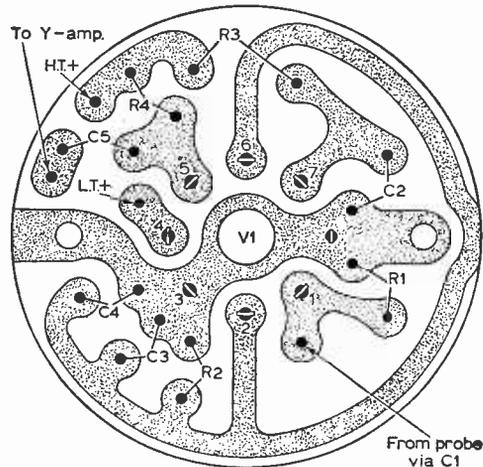

directly to the printed circuit conductors. The whole unit is mounted within the screening can as shown in Fig. 14. No trouble was experienced with microphony, but in the event of such trouble

—continued on page 43

UNIT CONSTRUCTION BOARDS

A MODERN METHOD OF
"BREADBOARD" WIRING

BY R. R. SLANEY

MANY constructors, before finally assembling a circuit utilising transistors, prefer to build it temporarily in "breadboard" fashion in order to facilitate testing and experiment. This procedure has many advantages both for the beginner and the more experienced constructor, especially if it is desired to experiment with component values and circuit variations, apart from the basic need to determine whether the circuit as constructed will function correctly.

For the novice in particular, much disappointment and frustration can be avoided by following this method and much can be learned if the opportunity is taken of laying out the simpler circuits more in accordance with the theoretical rather than the space-saving necessities of the practical diagram.

There are, however, certain disadvantages and in the writer's experience these have been mainly due to the difficulties of providing convenient and satisfactory anchorage points for components and point-to-point connections. On-the-spot improvisations with whatever materials are handy tend to make for untidy work and unnecessary complications in layout and create conditions in which mistakes can easily be made.

Pre-drilled Insulating Board

It was considerations such as these that led the writer to experiment with the idea of unit

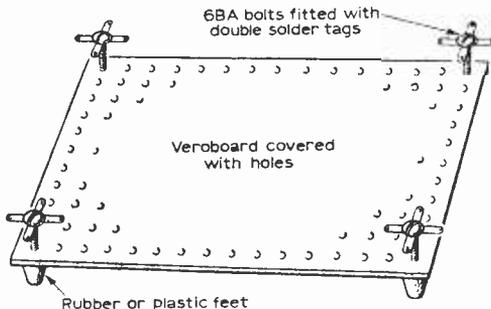


Fig. 1: The basic construction board with the positive and negative rails supports at each corner.

construction boards. In the first instance experimental boards were made from laminated plastic sheets (paxolin) obtained on the surplus market. Whilst these were satisfactory in every way their preparation involved a considerable amount of drilling. It is therefore suggested that Veroboard is used instead. As readers are no doubt aware this is a pre-drilled insulating board obtainable in a variety of sizes. The existing holes can easily be enlarged as required with a 6B.A. clearance drill.

The construction boards are simply prepared. The four corner holes are enlarged to take 6 B.A. bolts to which double solder tags are fitted. These bolts also hold in place four small rubber feet to allow components and wiring to be taken beneath the board of required, see Fig. 1. Heavy gauge wire is soldered lengthways between each pair of bolts to serve as positive and negative rails, although the position of these can be varied to suit any particular layout.

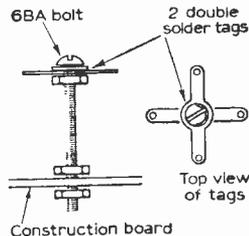


Fig. 2: The construction of a component anchorage point.

Anchorage Points

For supporting the smaller components and providing anchorage points, a number of 1/4 in. 6B.A. bolts should be prepared by fitting two double solder tags crosswise under the head, thus providing a four-way connecting point, see Fig. 2. A nut can also be run a short way up each bolt which is then ready for fixing to the board wherever it is needed by the addition of one nut, the appropriate hole or holes having been enlarged as described.

To allow transistors to be interchanged or different types to be tried experimentally in circuits, the small plastic holders now available are used. These are mounted on a paxolin bracket as shown in Fig. 3. Thin paxolin sheet 1/4 in. thick is used and each holder requires a piece approximately 1/4 in. x 1/4 in. The hole for the holder is cut


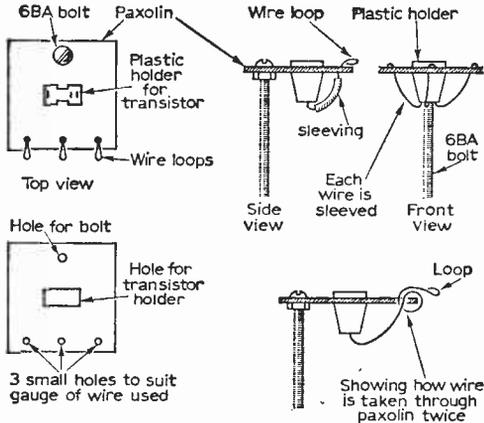


Fig. 3: Diagrams to illustrate the construction of transistor mounts, using plastic holders.

out with a penknife. It is better to start with a piece of paxolin somewhat larger than the finished size and cut it down afterwards. The plastic holder can either be glued or held in place with the metal clip provided.

To each of the three tags on the plastic holder a short length of tinned wire is soldered with a piece of sleeving

Fig. 4: A transistor holder for mounting directly into the construction board.

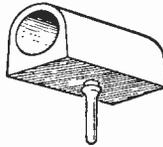

as shown in the diagram (Fig. 3). This is then taken up through one of the small holes previously made in the paxolin bracket, over the edge and up through the hole again to provide a firm anchor-

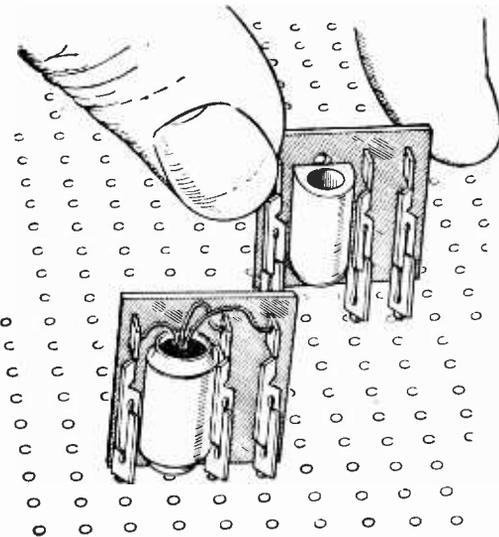


Fig. 5: Commercially available transistor mounts which plug into special sockets.

age. The end of each piece of wire is terminated in a flat loop. All soldered connections are made to these loops which, in effect, are solder tags.

Mountings for Transistors

For those who prefer to solder transistors directly into the circuit the *Lektrokitt* mounting in moulded p.v.c. is available. These holders make a push fit into the standard *Veroboard* holes, see Fig. 4. Alternatively a rather more professional and expensive design which plugs into sockets inserted into the *Veroboard* holes is available. As

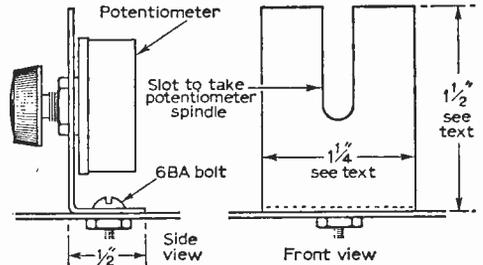


Fig. 6: Details of a suitable potentiometer mounting bracket.

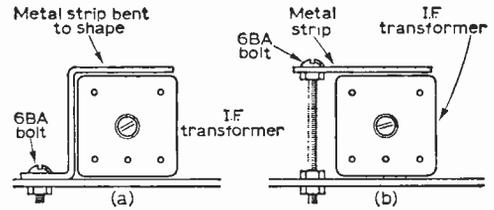


Fig. 7: Three methods of securing i.f. transformers.

will be seen from the illustration (Fig. 5) a diode holder is also available.

Simple brackets for mounting standard potentiometers can be made from aluminium as shown in Fig. 6. If necessary the upright member can be made longer to accommodate two potentiometers one above the other. The same brackets can also be used for standard 365pF tuning capacitors if suitable holes are drilled to enable the capacitor to be bolted to the bracket. If separate brackets are made for each of these components the one intended for potentiometers need be only 1/4 in. wide.

Coils, inter-stage and output transformers are bolted direct to the board, one bolt usually sufficing. Transformers which cannot be bolted

direct can be fixed to the board using one of the simple brackets described below.

Fig. 7a illustrates a bracket for securing i.f. transformers to the board. It will be noted that the transformers lie on their sides. This method permits of access to the pins for soldering and to the core for adjustments. An alternative bracket is shown in Fig. 7b. With a longer bolt the horizontal member can be adjusted up or down to accommodate different sizes of transformers. A further and effective alternative, using a Terry clip, is shown in Fig. 7c.

Clips for Rod Aerials

Terry clips, which are available in a comprehensive range of sizes, make excellent holders for varying shapes and sizes of ferrite rod aerials. The clips may be bolted direct to the board in any convenient position or stood off from the edge as shown in Fig. 8.

To complete the list of basic accessories a small but indispensable item is the soldering pin made by *Lektrokit*. These are used for simple point-to-point connections. Made of metal, they are $\frac{1}{16}$ in. tapered pins which will push securely into the standard *Veroboard* holes wherever they may be needed. One of these pins, greatly enlarged, is shown in Fig. 9a.

With regard to the construction boards themselves, their size will depend, of course, on individual requirements and some constructors may prefer to make several of different sizes. For others it may be a better plan to use boards of one standard size which can, if required, be joined to one another. This can be done quite simply

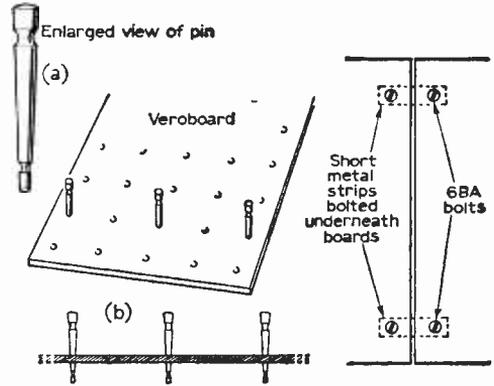


Fig. 9 (left): The soldering pins made specifically to fix into *Veroboard*.

Fig. 10 (right): The method of joining two construction boards.

to isolate one part of the strip from another by lightly drilling through.

Finally, in order to protect transistors from the possibly disastrous results of applying incorrect battery polarity during experiments the following procedure is suggested. A miniature jack plug and socket should be fitted with red and black flying leads, ensuring that when connected together the red goes to red. All that is then required is for the plug to be soldered direct to the circuit and the socket to the battery, correct polarity being observed in both cases. Once this is done complete protection is ensured, coupled with an effective and simple switching arrangement. ■

TEST GEAR ACCESSORIES

—continued from page 40

occurring, a special, antimicrophonic B7G type valveholder should be used.

POWER SUPPLY

The power supply required by this unit is:
250V d.c. at 15mA max.
6.3V at 0.3A.

The power unit described last month for use with the cathode follower probe is perfectly suitable for use with the amplifier probe. The no-hum advantage obtained by using a 6V battery for the heater supply is thought to be very necessary, as this completely eliminates the possibility of hum being introduced into the output.

COOLING THE UNIT

Several $\frac{1}{16}$ in. diameter holes should be drilled in the side of the screening can so that the valve can be well ventilated, and it should be found that the unit does not become unduly warm during operation.

The output cable should be of the screened, coaxial type, and the power cable should be well insulated.

This unit will work efficiently for long periods, and no trouble should be encountered in its operation.

Next Month Part 5


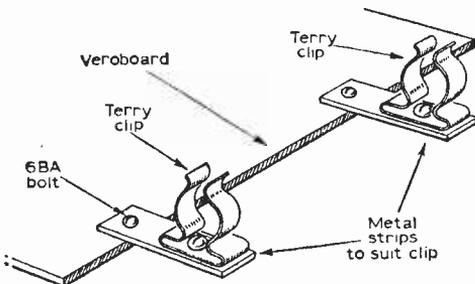


Fig. 8: A method of mounting ferrite rod aerials using Terry clips.

with two short metal strips drilled to take 6BA. bolts. The boards are then butted together as shown in Fig. 10. There is, of course, no reason why the boards should not be joined simply by overlapping one edge with another and bolting through. It is suggested that the two sides of each board should be clearly and permanently marked "positive" and "negative".

Copper Bonded Board

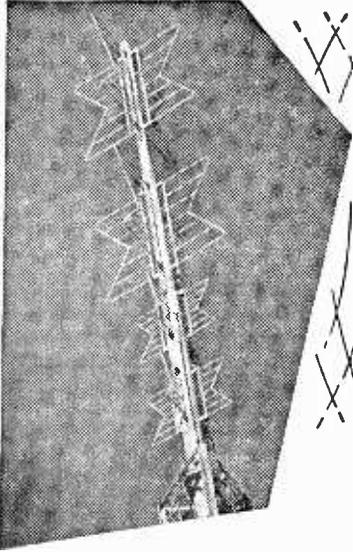It will no doubt be of interest to many readers to know that *Veroboard* is also available with a series of copper strips bonded to it. Thus when a prototype circuit has been built and tested on a construction board it can be reduced to a more permanent and compact form, using the copper bonded *Veroboard* as a type of printed circuit. The lengths of copper strip can easily be broken



On Your Wavelength

By THERMION

THE expression "free as the air" conjures up a sense of absolute freedom perhaps more vividly than any other phrase. It is, of course, a quite fanciful image as far as we highly organised humans are concerned. How often do we learn to our amazement, and perhaps disgust, that some particular seemingly innocent activity is in fact "agin the law"?

This apart I don't doubt that there are those who would consider this a singularly inappropriate choice of words to signify freedom and liberty as they recall how their hopes of using the air wireless-wise have been balked by officialdom. Our "Letters to the Editor" page certainly has on occasions borne witness to the frustrations experienced by those unable for some reason or another to obtain the requisite licence to radiate electromagnetic waves in free space.

The medium through which radio waves are propagated may indeed be "free" in the unconfined sense, but the use of this medium for transmission or reception is at all times subject to governmental sanction. Or, to put it more plainly, you cannot legally operate any kind of wireless transmitter or receiver unless you hold the appropriate licence issued by the authority concerned, this being in the U.K. the Postmaster-General.

Receiving Licences

I imagine that to many the position regarding wireless licences is rather perplexing. This may be particularly so on the receiving side, where it is impossible or impractical to enforce any restriction on the tuning range of receiving apparatus in the possession of private individuals. The Broadcast Receiving Licence permits one to install and operate equipment for the sole or prime purpose of receiving matter sent from authorised broadcasting stations for general reception and from licensed amateur stations, as you can verify by looking at your licence. The holder of an Amateur Transmitting Licence is automatically

covered for the reception of signals from other amateur stations but not for the reception of broadcast programmes. The latter is, however, covered by any broadcast wireless licence issued to the same household.

The fact that we have no legal right to listen in to all and sundry in the way of wireless transmissions has been clearly demonstrated quite recently in the case relating to police radar. Some "enterprising" person or persons proposed to put on the market a device intended to give warning to the driver of a vehicle when he was approaching a police radar trap. The G.P.O. promptly squashed this by declaring such a device to be by definition a receiver and that they would not grant a licence for the installation and use of this kind of receiver.

An interesting point arises concerning communications receivers. These are presumably covered in the normal way by a broadcast receiving licence, although most of the receiver coverage might be outside the normal broadcasting bands. Supposing a communications receiver happens to have a range covering, let us say, this police radar, how can its use be prevented?

The answer is, I suspect, that the act of tuning in and listening to a non-broadcast transmission is not in itself an offence but that an offence would be committed immediately any use was made of information gleaned in this manner. It is obviously impossible to prevent people tuning in to any frequency, but the law does jump down heavily whenever anyone is discovered making use of intercepted signals and this includes the passing on to a third party of details of such transmissions.

This would then explain the ban on the anti-radar device since the sole purpose of this device was to make use of the information (i.e. radar signals) received.

Mention of cars brings to mind the questions that often arise regarding licences for car radios.

A separate licence (that is, additional to the household licence) is needed if the radio makes use of the car battery—this is regardless of whether the receiver is a permanent installation or not. The type of aerial used does not enter into the question. One of our readers inquired if it would be in order to couple a miniature transistor receiver to an audio amplifier and loudspeaker unit installed in the car, the a.f. amplifier only being powered from the car battery. I understand that the Post Office rule that such an arrangement would definitely require a separate licence. Anyhow a brave try . . .

Any other bright suggestions, legal, of course? The ingenuity of some of our readers often fills me with admiration but I am afraid that in a battle of wits the odds are very much on the G.P.O. boys!

THIS MAKES MONEY FOR YOU FOR YEARS TO COME!

TELEVISION
RADIO • RADIOGRAMS
CAR RADIOS
TAPE RECORDERS
RECORD REPRODUCERS

CIRCUITS • DATA • SERVICING HINTS
For over **2,900 Models**

A REAL MONEY-SPINNER
VITAL TO THE SHREWD RADIO MAN

Newnes RADIO and TV Servicing

Over 50,000 sold!
Now comes the greatest
edition of all.

This New 11th Edition of Newnes famous repair set equips you for quicker servicing and more profit! With sets capable of giving longer service you need this data more than ever. It is your constant reference to sets marketed over the past eight years—always at hand instead of loose paper data so easily mislaid or destroyed. To-day there are also more radios and transistor portables, stereo radiograms, record reproducers, tape recorders, car radios than ever before—all needing expert service from time to time. Newnes RADIO & TV SERVICING provides you with data and information needed for years to come. Prove this investment now by 7 days' Free Trial.


Over 4,500 Pages of Circuits, Component Layout Diagrams, Quick-Ref Data and Latest Developments

DATA FOR ALL THESE MAKES

Ace, Ajax, Alba, Ambassador, Argosy, Armstrong, Baird, Beethoven, Berc, Brayhead, B.R.C., B.S.R., Bush, Capitol, Champion, Channel, Collaro, Cossor, Cydon, Dansette, Decca, Defiant, Dynatron, E.A.R., Eddystone, Ekco, Elizabethan, Elpico, Emerson, E.M.I., Emisonic, English Electric, Ever Ready, Ferguson, Ferranti, Fidelity, Ford Motor Co., Garrard, G.B.C., G.E.C., Gramdeck, Grundig, H.M.V., Invicta, K-B, Magnavox, Marconiphone, Masteradio, McCarthy, McMichael, Motorola, Murphy, Pageant, Pam, Perdio, Peto Scott, Philco, Philips, Pilot, Portadyne, Portogram, Pye, Radiomobile, Raymond, Regentone, R.G.D., Roberts' Radio, Sobel, Sony, Sound, Spencer-West, Stella, Stereosound, Strad, Ultra, Vidor, Volmar, Walter, Webcor, Zenith.

FOR EVERY PURCHASER —
2 YEARS FREE POSTAL
ADVISORY SERVICE

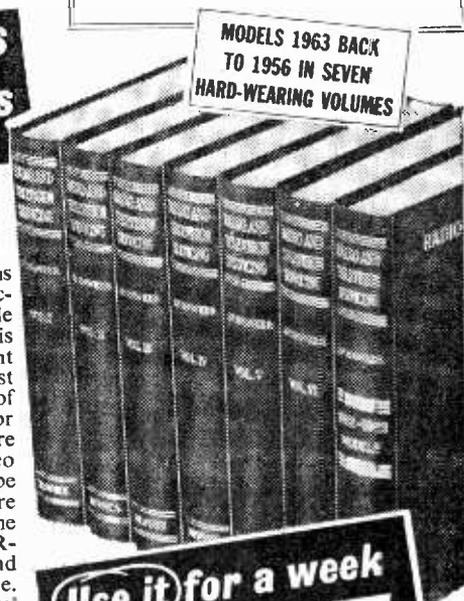*Quicker work Builds Goodwill
-Makes more Profit!*



Use it for a week
FREE
NO OBLIGATION TO BUY

GIVEN WITH EVERY SET
Newnes TV ENGINEERS POCKET BOOK
(Value 12/6)

An invaluable companion to your set for on-the-spot repairs. 272 pages of reference data on installing, fault-tracing and repairing, servicing equipment, etc.



George Newnes Ltd.,
15-17 Long Acre
London, W.C.2.

If under 21 your father must fill up coupon.
If married woman your husband must fill it up.

Please send Newnes
RADIO AND TELEVISION SERVICING
(7 Volumes) and TV
ENGINEERS POCKET BOOK without
obligation to buy. In
8 days I will return
them or post only 16/-
deposit, then 16/-
monthly for 20 months,
paying £16.16s. in all.
Cash in 8 days £16.16s.
Free Trial applies G.B.
For Ireland send cash
price (refundable if
title returned in 8 days).


Full Name (Mr., Mrs., Miss)
(BLOCK LETTERS)
Address

Occupation

Signature

(Mr., Mrs., Miss)
(RV)40/610

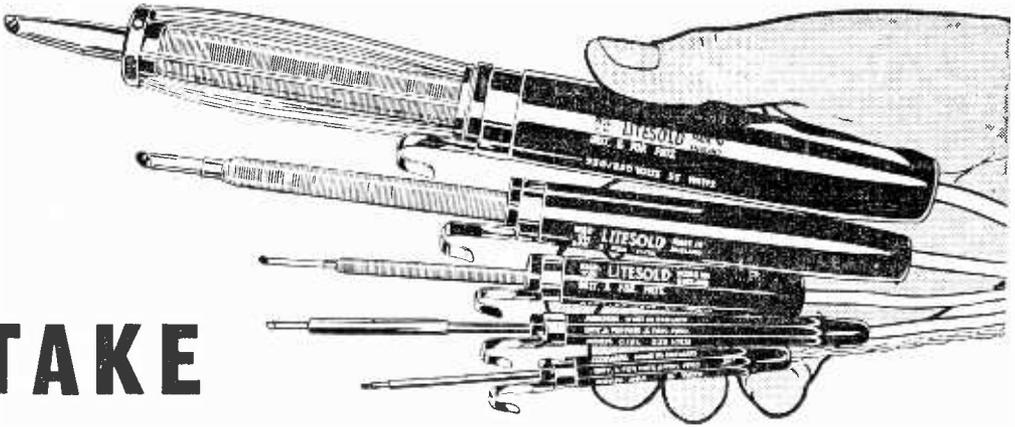Tick ✓ where applicable
The address on left is—
My Property
Rented unfurnished
Parents' Home
Furnished Accom.
Temporary Address



TAKE FIVE!

There are 30 other models, too. There ARE several other makes of soldering instruments. Big ones. Small ones. Good ones. We've seen them. We don't make the biggest ones. Or the most expensive ones. Or the most elaborate ones. We DO make the 'smallest ones. And the widest range. We make the best. Always have. May we send you details?

Brochure P.W.10 post free on request.

LIGHT SOLDERING DEVELOPMENTS LTD., 28, Sydenham Road, Croydon, Surrey.

Telephone: CROydon 8589.

The New NOMBREX

TRANSISTORISED WIDE-RANGE

Inductance Bridge

1 μ H to 100H

Model 66

Laboratory

Specification:

Inductance

Measurements within
5% Accuracy


Measures Q and tan δ

Balance indication by
miniature meter

Compact, only 6½ x 4½ in.

Direct calibration

Portable, weight 2 lb.

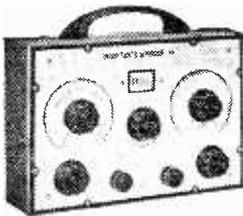

PRICE £18.0.0.

Battery 2/3

Post & pkg. 3/6

Release date 10th April

ORDER NOW

TRADE & EXPORT

enquiries invited

H.P. £5 deposit

and 49/- monthly

S.A.E. for full

technical leaflet

NOMBREX LTD. (Instruments Division 77)

Estuary House, Camperdown Terrace, Exmouth, Devon,
England. Tel. 3515.

OSMOR

CHANGE OF ADDRESS

To

540 PURLEY WAY

CROYDON

(NEAR AIRPORT)

SURREY

Telephone


CROydon 5148-9

this “j” business


HAVING by now got some idea of what operator “j” is, let us see the kind of things we can do with it, especially with regard to circuit theory problems.

When we first learnt arithmetic at school, we were taught that $1+1=2$. Maybe it always does in the mathematics of *things*, but not in the mathematics of *measurement*. One foot forwards plus one foot backwards doesn't equal two feet in any direction. Neither does one foot up plus one foot across. This is where our labels, plus and minus, and j, come in. They are the symbols for direction, just as ordinary numbers are symbols for size.

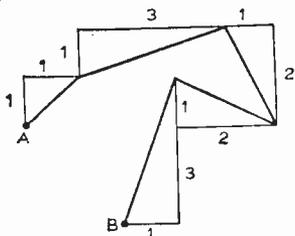Suppose you had to work out the distance between A and B in the sketch below. Would you find it easy or difficult?



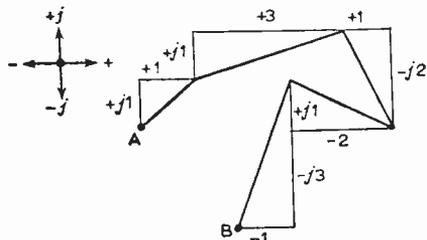Let us draw the figure again, and use labels in front of all the sizes to indicate their direction. To the right is +; to the left is -; up is +j; and down is -j. We now have a sketch like this:



To find the distance from A to B we simply add all the numbers together, like this:

$$\begin{array}{r}
 +1+j1 \\
 +3+j1 \\
 +1-j2 \\
 -2+j1 \\
 -1-j3 \\
 \hline
 \text{Total} \quad +2-j2
 \end{array}$$

Following on the general introduction given in last month's article, this final article shows how the “j” notation can be applied to problems relating to a.c. circuit theory.

By Roy Hartkopf

CONTINUED FROM PAGE 1194 OF THE APRIL ISSUE

We have written $j1$ instead of “j” to make it clearer. Actually $1j$ or $j1$ is exactly the same thing as j .


So the distance from A to B is two units to the right plus two units down. Simple, isn't it? You can check the result by drawing it on a piece of graph paper.

These double-barrelled quantities, which have direction as well as distance, are called vectors, and what we have just been doing is an example of vector algebra.

So far we have been talking about distances and directions in space, on a flat surface. But we can also have—though it sounds Irish—different “directions” in time. And it is here that the j notation is particularly useful to radio and electrical engineers.

The rotating vector

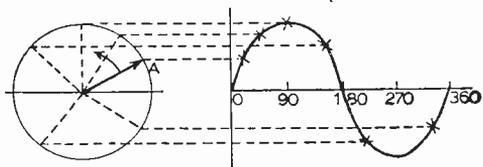
We all have a fair idea of what one cycle of a sine wave looks like, and we also know that this cycle repeats over and over again. Many will remember that it is called a sine wave because it can be shown to be the projection of a rotating line or rotating vector. The sketch below illustrates how this comes to be so.



The sine wave is really a picture of the height of the point A above or below the base line as the rotating line is swung round like the hand of a clock. When it has swung round 90° and is at right angles to the base line, the point A is as high as it can go. At 180° it is level again with the base line. At 270° it is at its lowest position, and at 360° it is back where it started from, having completed one cycle.

Suppose we have a second sine wave, of the same frequency but 90° out of phase with the first. The diagram below shows how these two waves could be represented by two rotating lines, 90° apart from each

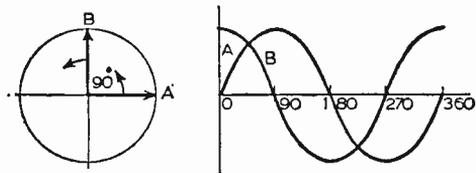
other, the one chasing the other like the wooden horses on a merry-go-round.




If we get this picture clearly in our minds we can begin to see where the "90° out of phase" fits in.

As far as the actual waves are concerned, it would be more correct to say they were a quarter of a cycle out of phase. But it is customary to talk about degrees out of phase, and it is a handy way so long as we remember they really represent fractions of a cycle, and not an actual angle.

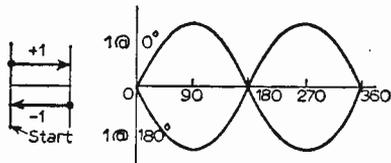We have already mentioned that in the mathematics of measurement, one plus one does not necessarily make two at all. The following sketches show how this happens both in ordinary vectors and in sine waves.



In the first case, when the directions are opposite they cancel out because they represent equal amounts in opposite directions. Another way of putting it would be to say that one line has been swung through 180°. And exactly the same thing happens with the sine waves. At each instant the one is equal and in the "opposite direction" to the other, they are 180° out of phase and so they cancel out. Let us take a second case where the vectors and the sine waves are 90° apart. They look like this:

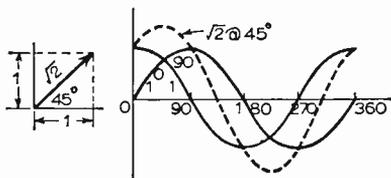


Here we find that the two vectors at right angles give us a resultant which is $\sqrt{2}$ or 1.4 units long at an angle of 45°. And if we plot the two sine waves and add them we will get exactly the same effect, another sine wave 1.4 times the amplitude and 45° out of phase with the two original waves.

All this boils down to the fact that we can treat sine waves in exactly the same way as we can treat distances and directions; that is label them with plus, or minus, or j, to indicate if and when they are out of phase, and just what their phase relationship is.

R, C and L in parallel

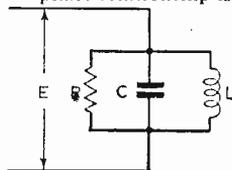Let us take a case where we have a resistor, capacitor and inductor in parallel across an alternating voltage E.



We know that the impedance of the resistor is R, the impedance of the capacitor is:

$$\frac{1}{2\pi fC}$$


and the impedance of the inductor is $2\pi fL$.

By Ohm's Law:

$$I = \frac{E}{R} \text{ so } I_R = \frac{E}{R}, I_C = \frac{1}{2\pi fC} = 2\pi fCE, \text{ and } I_L = \frac{E}{2\pi fL}$$

We also know that the capacitive current is leading by 90° on the resistive current and the inductive current is lagging by 90°.

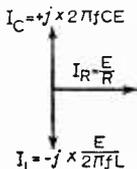So we can draw a diagram of our currents like this, putting the appropriate label in front of them.



In working with j there is one fact which we must always remember for it crops up time and time again in calculations. This is that, since $j^2 = -1$, we can write $-j$ as:

$$-\frac{j^2}{j}, \text{ which is } -\frac{-1}{j}, \text{ which is } +\frac{1}{j}. \text{ So } \frac{1}{j} \text{ is equal to } -j, \text{ and also } j \text{ is equal to } -\frac{1}{j}.$$

Because of this we can write our inductive current, which is:

$$-j \frac{E}{2\pi fL} \text{ as } + \frac{E}{j2\pi fL}.$$

It is exactly the same thing.


So, taking into account our j notation, the inductive impedance is $j2\pi fL$ and the capacitive impedance is

$$\frac{1}{j2\pi fC}, \text{ or if we prefer it, } -j \frac{1}{2\pi fC}$$

which again is exactly the same thing.

A Series Circuit

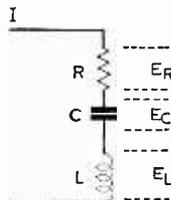Let us see if these j labels automatically give us a sensible result in a series circuit containing R, C and L.




In this case, since the current can't disappear into thin air, the same current must flow through the three. Here we use Ohm's Law in the form $E = IR$,

to find the voltages across the three impedances.


Thus $E_R=IR$, $E_C = -j \frac{1}{2\pi fC}$, $E_L=j2\pi fLI$

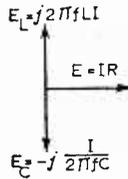So E_R is plain, E_C has a $-j$ label, and E_L has a $+j$ label. The diagram would look like this.



At first sight things seem to be back to front. But if we look carefully we see it is the inductive voltage which is leading and the capacitive voltage which is lagging. This makes sense because if the inductive current is 90° behind the voltage, then the voltage is 90° ahead of the current. A similar argument applies to the capacity.

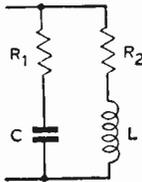As a final example of what we can do with j notation let us consider the circuit shown below. It consists of resistance and capacity in parallel with resistance and inductance.



The impedance of the resistor-capacitor arm is

$$Z_{R1-C} = R_1 + \frac{1}{j2\pi fC} \quad \left(\text{or } R_1 - j \frac{1}{2\pi fC} \right)$$

The impedance of the resistor inductor arm is:

$$Z_{R2-L} = R_2 + j2\pi fL$$

As most of us know, the formula for two impedances in parallel is:

$$\frac{1}{Z_{total}} = \frac{1}{Z_1} + \frac{1}{Z_2}$$

$$\text{Which equals } \frac{Z_1 \times Z_2}{Z_1 + Z_2}$$

And turning it upside down we have:

$$Z_{total} = \frac{Z_1 \times Z_2}{Z_1 + Z_2}$$

Applying this directly to our case, we have,

$$Z_{total} = \frac{\left(R_1 + \frac{1}{j2\pi fC} \right) \times \left(R_2 + j2\pi fL \right)}{R_1 + \frac{1}{j2\pi fC} + R_2 + j2\pi fL}$$

Normally this would be the answer; and if we substituted numbers it would simplify down to a number plus (or minus) another number with a j label in front of it. (If it was pure resistance the j part would be zero and if it was purely inductance or capacitance the other part would be zero.)

In the case of our circuit we can simplify the formula if we make the two resistors equal. The formula now looks like this:

$$Z_{total} = \frac{\left(R + \frac{1}{j2\pi fC} \right) \times \left(R + j2\pi fL \right)}{2R + \frac{1}{j2\pi fC} + j2\pi fL}$$

Multiplying out the top we get:

$$\frac{R^2 + j2\pi fLR + \frac{R}{j2\pi fC} + \frac{j2\pi fL}{j2\pi fC}}{2R + \frac{1}{j2\pi fC} + j2\pi fL}$$

Rearranging the formula we get:

$$\frac{\frac{L}{C} + R^2 + j2\pi fLR + \frac{R}{j2\pi fC}}{2R + j2\pi fL + \frac{1}{j2\pi fC}}$$

Looking at this we see that, except for the term $\frac{L}{C}$ in the top line, there is a striking similarity between

the top and bottom lines. If we make $\frac{L}{C}$ equal to R^2 the formula looks like this.

$$Z_{total} = \frac{R^2 + R^2 + j2\pi fLR + \frac{R}{j2\pi fC}}{2R + j2\pi fL + \frac{1}{j2\pi fC}}$$

$$= \frac{2R^2 + j2\pi fLR + \frac{R}{j2\pi fC}}{2R + j2\pi fL + \frac{1}{j2\pi fC}}$$

$$= \frac{R \times \left(2R + j2\pi fL + \frac{1}{j2\pi fC} \right)}{2R + j2\pi fL + \frac{1}{j2\pi fC}}$$

$$= R.$$

So we have the very interesting result that in this circuit, if the two resistors are equal and the ratio of $\frac{L}{C}$ is made equal to R^2 , the circuit behaves like a simple resistance regardless of whatever the frequency may be. This example shows how the use of j notation can help us to see new possibilities in circuits as well as making practical calculations easier.

Now we should be in business—the j business. If in future we read an article splattered with j 's we shouldn't feel they represent some mathematical magic that we'll never be able to understand. Even if the detailed workings are too involved to follow, at least we'll have a solid general idea of what it's about. And this after all is the important aspect of understanding. ■

Medium Wave Aerial Data

COIL DESIGN DETAILS FOR FERRITE ROD AERIALS

By **RICHARD MARSH**

IT is well known that a ferrite rod with a suitable coil makes a very good aerial for small portable receivers. A great feature is their compactness coupled with efficiency.

The design of a suitable coil depends on complicated formulae but the average amateur need not be put off by this. Instead of using formulae the accompanying graph may be used for quickly deciding upon a suitable coil.

This graph relates to a standard round ferrite rod $\frac{3}{8}$ in. diameter, 8in. long. The coil must be close-wound on a low-loss former but about six layers of good, clean writing paper will do (with a

band with a 500pF variable capacitor and similarly for a 16-turn coil placed 0.65in. from the end of the rod.

(2) With a 300pF variable capacitor the centre of a 20-turn coil would be about 0.8in. from the end of the rod.

(3) With a 40pF variable trimmer used as a tuning capacitor coils of 60 or 70 turns could be used with their centres 1in. or 0.65in. respectively from the end of the rod.

(4) Push-button tuning. With, say, a 60-turn coil about 1in. from the end of the rod select a number of capacitors with a suitable trimmer for



few drops of gum in the last three layers to hold it together). Cover the outside with Durafix and wind on the wire, using Litz or bunched conductor wire.

Each curve on the graph is for a different number of turns from 10 to 100. A coil may occupy any position on the rod from the middle right out to the end. The distance "L" is the distance between the middle of the coil and the end of the rod. Note that the inductance of any coil may be reduced to almost half its maximum value by sliding it right to the end of the rod. This provides some useful adjustment that could enable a trimming capacitor to be omitted in some instances.

On the right there is a vertical scale with pairs of numbers at various intervals. These pairs of numbers represent the range of total capacitance required to provide tuning over the whole medium wave band (taken as 550kc/s to 1,500kc/s) for each coil. The way to use this scale is best illustrated with a number of examples thus:

(1) Suppose we have available a 500pF tuning capacitor. Take a horizontal line from 500 in the right-hand scale and note that it crosses the 20-turn coil and the 16-turn coil lines at points corresponding to distances 0.265in. and 0.65in. respectively. This means that a 20-turn coil placed so that its centre is 0.265in. from the end of the ferrite rod may be turned over the whole of the medium wave


each and a suitable low-loss wafer or push-button switch with as many positions as needed for the stations chosen. Start with one station and adjust the coil position for best results, then fix the coil in that position with Durafix, etc., and for other stations adjust the capacitors.

The rod used is one commercially available and allowances must be made for possible variations of performance from one rod to another and also for the capacitance of the circuit. Rather than push a coil right to the very end of its rod it would be better to remove one or two turns and have it some $\frac{1}{8}$ in. or more further on the rod.

The Q of all coils tested was good. The 100-turn coil had the highest value, 262. The 50, 20 and 10 turn coils had 260, 202 and 130 respectively. These values for Q vary slightly with coil position and are a maximum with the coil centres in the region 1in. to 1 $\frac{1}{4}$ in. from the end of the rod.

Other Diameter Rods

As previously stated, this graph is directly applicable to a $\frac{3}{8}$ in. diameter ferrite rod. Other rods in common use have diameters of $\frac{1}{4}$ in., $\frac{5}{16}$ in. and $\frac{1}{2}$ in. When using any of these rods the data obtained from the graph should be considered as subject to slight modification. However, the optimum position for the coil will be readily ascertained when receiver alignment is performed. ■

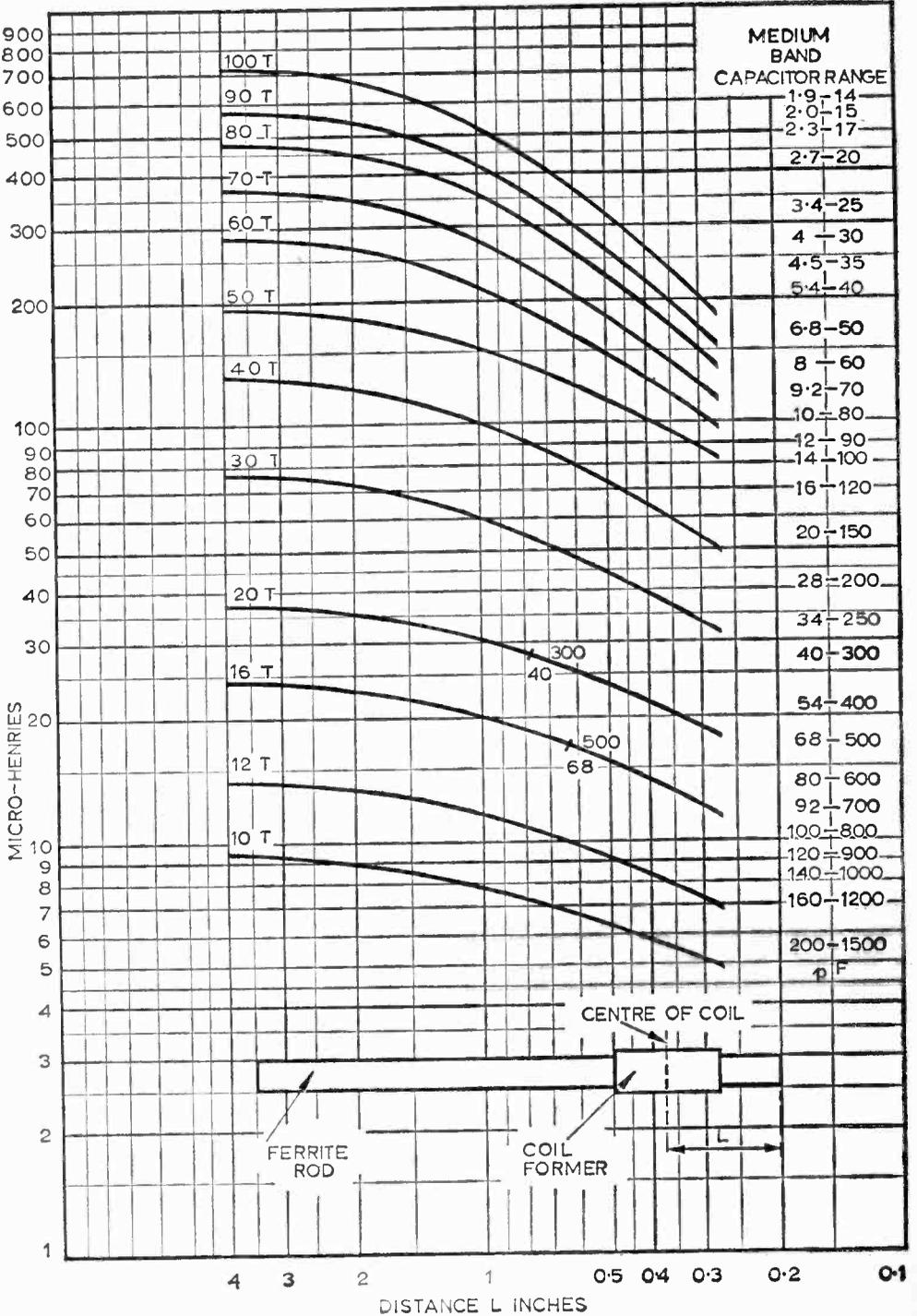

THIS receiver is mains operated, and is constructed in an easily obtainable aluminium case measuring 12in. x 7in. x 3in., a small speaker being included. It operates from a telescopic aerial, and can thus be used anywhere where mains are available. An external aerial can be used in the normal way, though very good results are achieved with the telescopic aerial.

The receiver has six wavebands, covering medium waves, shore and shipping, amateur and short waves. The band coverage is approximately as follows:

Band	Frequency	Wavelength
1	30—20Mc/s	10—15 metres
2	21—10Mc/s	14—30 metres
3	10—4.5Mc/s	30—65 metres
4	4.5—2Mc/s	65—150 metres
5	2—0.9Mc/s	150—330 metres
6	900—450kc/s	330—650 metres

Reference to the circuit diagram (Fig. 1) shows that a single coil is used for each band. There is thus no trimming or aligning whatever to be performed, and any slight changes in the coils will have no effect on efficiency.

Circuit Description

Regeneration is used in the detector stage (V2), and this results in very high sensitivity. The r.f. stage is untuned, and serves to isolate the aerial, to avoid troublesome hand-capacity effects. VC1 is the band-setting capacitor, while VC2 is used for fine tuning. This arrangement has the effect of dividing each waveband into ten or more smaller bands, each of which is "spread" by VC2, thus allowing easy tuning.

The third valve, V3, provides two stages of audio amplification, giving sufficient volume for the 2½in. speaker. An external speaker can be used if a self contained, portable set is not required. V4 is the usual full-wave h.t. rectifier.

Latitude in Component Values

There is some latitude in component values, so items to hand may be fitted in some cases, for example: the 0.05μF by-pass capacitors may be 0.1μF; VR1 may be 20kΩ or 25kΩ; VR2 may be 50kΩ with R5 47kΩ or 68kΩ; or VR2 may be 200kΩ, with R5 220kΩ; VR3 may be 0.5MΩ. VR3 incorporates the mains on/off switch, but this could be in VR1 and VR2, or a separate toggle switch could be employed. C11 may be 50μF; C13 may be 32μF; C13 and C14 may be separate components, instead of a twin capacitor, and C7 may equally well be 8μF. C9 and C10 must be mica, or good quality high voltage paper, as leakage here will upset the 12AT7 grid bias values. C12 may be as large as 0.01μF.

SIX-BAND T.R.F. Receiver


BY F.G. RAYER

There is no reason why the receiver should not be adjusted to suit any other metal case to hand. A wooden panel, or one of any kind of insulating material, is not recommended, unless it is backed by metal for screening purposes.

Wiring-up the Receiver

Fig. 2 shows the top of the chassis, and Fig. 3 is the underside. Heaters are wired first, the heater circuit wiring being against the chassis, and clear of grid leads. With V3, tags 4 and 5 are joined and taken to chassis.

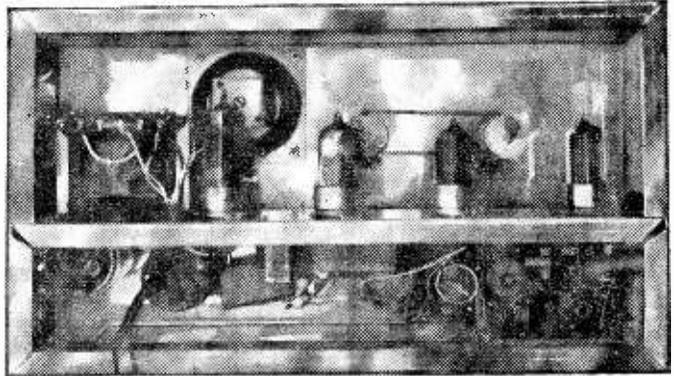All connections associated with V2 must be as short as possible. R4 and C5 should have very short leads to tag 1. C6 and C8 are earthed to a tag near V2. The same



An interior view of the finished receiver.

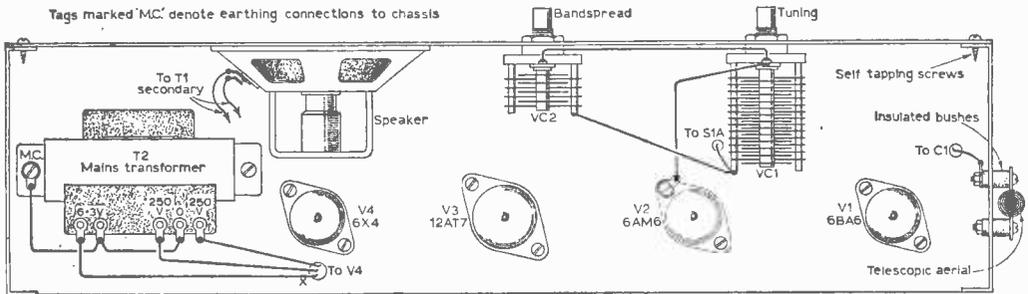


Fig. 2: The layout of the major components on the chassis.

bolt secures a tag on top of the chassis, and a lead goes directly from this tag to the moving plates tag of VC1, and from there to VC2. Switch leads must be short and direct, especially for bands 1 and 2. The telescopic aerial is fixed with 3/4 in. 6BA bolts insulated from the metal cabinet by means of fibre

near wires carrying a.c.

If a small smoothing choke is to hand this can be used instead of R13. If the set is used in an earthed situation, a 3-core mains cord is preferable, the metal chassis being earthed to the large pin of a 3-pin plug. A low rating fuse can be inserted in

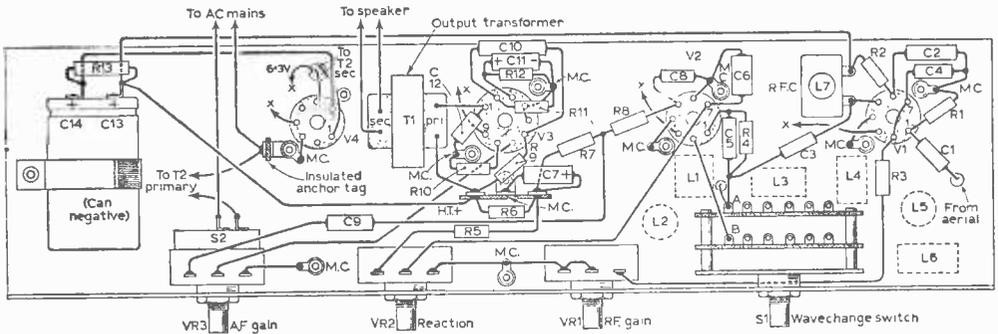


Fig. 3: An underchassis wiring diagram.

pillars and washers. If this type of aerial is not required, an insulated socket or terminal may be connected to C1.

The mains transformer and speaker leads pass through a hole in the chassis. An insulated tag forms an anchor point for the mains lead. Grid and anode leads must not be near each other, or

13A type plugs. If any tests are required, V1 may be eliminated by temporarily taking a short aerial to C3. This will allow the detector and a.f. stages to be checked.

Details of the Coils

Fig. 1 shows one coil only, but the coils for

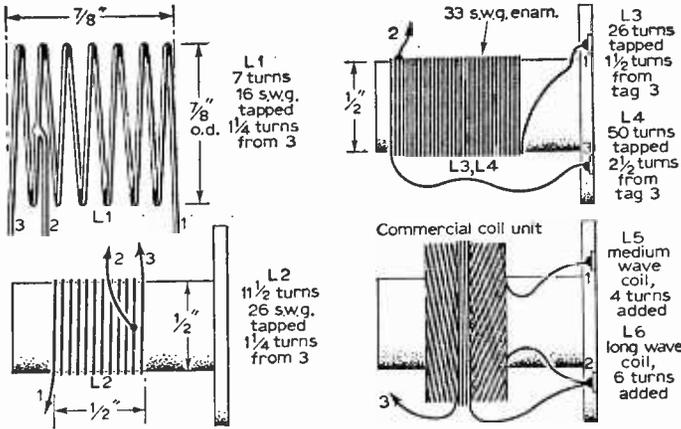


Fig. 4: Construction details of the coils.

other bands are connected in the same way, to consecutive tags on the switch. Medium wave coverage is useful for general listening, but band 6 may be omitted, if this is not required. The set is best tested with a single coil, then checked on other bands as the other coils are added.

Fig. 4 shows details of the coils, and with each the cathode tap 2 is very near the earthed end of the coil, 3. The exact position of this tap has an important effect. If the tapping is too near point 3, there will be insufficient regeneration. If the tapping is too far from point 3, oscillation will begin before V2 is providing anything like maximum gain. It may thus be worth while experimenting with the cathode taps, to suit the actual valve employed as a detector, though the tappings given below should generally be satisfactory.

The small coils are easily wound, as they have few turns. The larger coils, however, require many more turns, so can best be ready made, a few extra turns being added between points 2 and 3. Coupling or other unrequired windings should generally be removed, to avoid absorption, as the coils need only a single winding.

For range 1, 7 turns of 16s.w.g. wire are used, point 2 being $1\frac{1}{4}$ turns from point 3. The coil is self supporting, with the shortest possible leads, and is $\frac{3}{8}$ in. outside diameter, and $\frac{7}{8}$ in. long.

Ranges 2, 3 and 4 are wound on $\frac{1}{8}$ in. diameter coil formers. Range 2 has $11\frac{1}{2}$ turns of 26s.w.g. enamelled wire, occupying $\frac{1}{2}$ in. and tap 2 is $1\frac{1}{4}$ turn from point 3. Coil 3 has 26 turns of 33s.w.g. enamelled wire, close wound, the tapping being $1\frac{1}{2}$ turn from point 3. Coil 4 is also of 33s.w.g. enamelled wire, and has 50 turns side by side, the tapping 2 being $2\frac{1}{2}$ turns from point 3. A dust iron core is fitted in this coil.

Range 5 uses a medium wave coil. This coil would normally tune about 200-550m., but with the low capacity present the range is about 150-330m. Adjustment of the core allows the range to be modified as required.

On range 6 a long wave coil is used, turns being removed until suitable coverage can be obtained by adjusting the core position.

With range 5, 4 turns are provided between points 2 and 3. This is arranged by winding 4

extra turns of thin insulated wire on the original coil, point 2 being the junction of the original winding and new winding. With coil 6, 6 turns are required between points 2 and 3.

The coils are placed as in Fig. 3 and all switch connections are shown in Fig. 5.

Tuning Scales

Six scales are drawn on thin card and a wire pointer is fitted to VC1 to read against these. Scales and switch positions are numbered to agree. Markings may be in frequency or wavelength as preferred. VC2 being set at half capacity during this operation. Some type of signal generator is convenient, or the harmonics of a fixed frequency oscillator may be counted off, and the scales marked to agree. If preferred, the usual short wave bands may be marked, other markings being omitted.

A Bulgin 0-100 scale was fitted under the

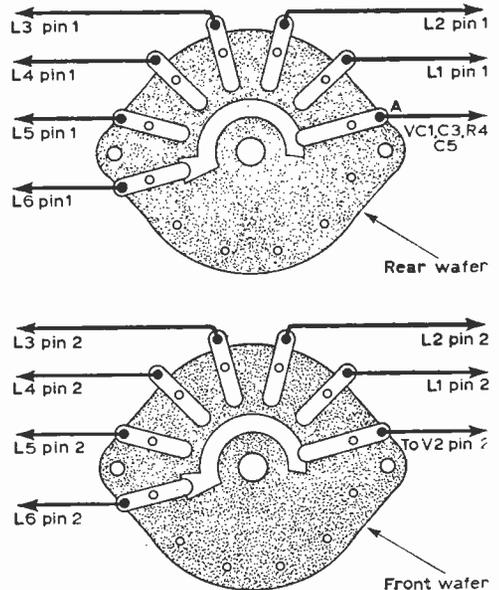


Fig. 5: S1 switch connections.

securing nut of VC2, and bandspreading can be read against this. All normal tuning on short wave bands is carried out by means of this control.

Operating Notes

VR3 is the audio gain control and is used in the normal manner. VR2 controls regeneration, and adjustment here is critical, for best possible long

—continued on page 90

communications

THROUGH THE GROUND

An interesting idea
for the experimenter

By C. R. Bradley

IT is well known that the ground is conductive—direct connection is often made to it and used as an “earth” or reference point for electrical equipment. Equipment is often earthed for safety and voltages are usually measured with respect to ground.

It is possible to send a morse or voice signal from one point to another by arranging to have either a direct or alternating current flowing between the different points. However, to achieve this two conductors are needed between the two points. For this reason, telephones are connected to the central exchange by a pair of wires (Fig. 1a).

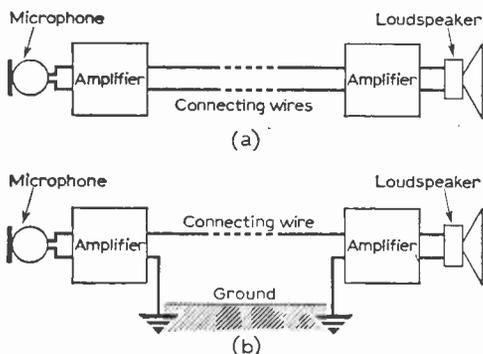


Fig. 1(a): A simple two-wire intercom; (b): a modified version which dispenses with one of the wires.

As the ground is conductive, one of the wires may be dispensed with and the terminals at each end of it earthed. Over long runs where wire is expensive, this reduces cost although the received signal may be weaker because of the resistance of the ground.

The system to be described makes use of the fact that the ground is not a perfect conductor and will show a resistance between any two points. The ground is in fact used to replace *both* conductors.

Consider a pair of earthing rods, A and B sunk several feet apart. A voltage X is applied between them. (Fig. 2).

The resistance of the ground may be regarded as an infinite number of “paths” between A and B. The shortest path AB (R_1) will have the lowest resistance and all the other paths will have a resistance proportional to their lengths. In theory, the voltage X would drive a current through each one of the paths.

If another pair of earthing rods are sunk, Y and Z, there will be a small current flowing through the ground between Y and Z, produced by the voltage X. If Z and Y are a mile or more from A and B, then this current will only be a tiny fraction of that flowing through R_1 . However, with sensitive equipment it may be detected.

There will be a certain voltage drop across the resistance YZ and this will be shown on a sensitive voltmeter.

PRACTICAL SYSTEM

If a strong audio signal is fed in at A and B, it may be received at Y and Z. The audio signal may be produced by an ordinary audio amplifier with microphone. A suitable receiver is a pair of headphones connected between Z and Y. In practice two, not four earthing rods are needed as the cold water main is used for earthing points A and Z.

It is most important that the earths B and Y

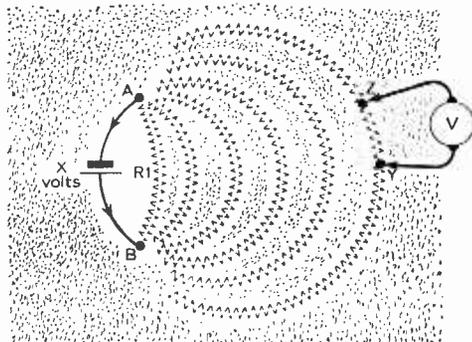


Fig. 2: Illustrating imaginary paths of resistance through which current produced by voltage X would flow.

make a good contact with the ground. An earthing rod may be used or a large piece of aluminium, copper or brass (not lead or iron since both will corrode). A piece of scrap piping or sheet is suitable; the only requirement is that the object should have as large a surface area as possible.

The earths B and Y at the transmitting and receiving ends respectively should be placed as far away from any water pipes as possible. As these usually follow the roads, the far end of a back garden is usually a good position.

The resistance between the earths and the water pipes is then measured at each end.

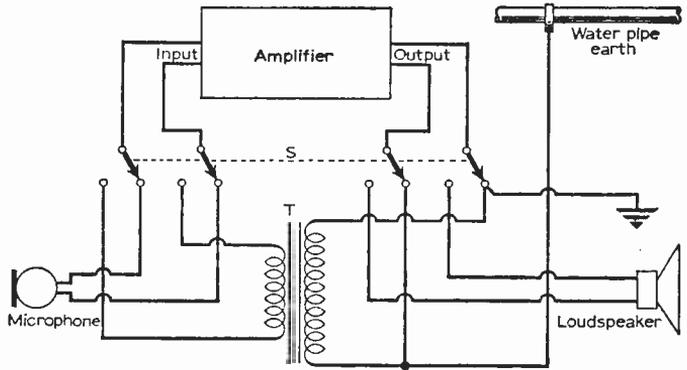


Fig. 4: A two-way station. The 4-pole switch S is shown in the send position. T is an output transformer with its primary connected to the amplifier input.


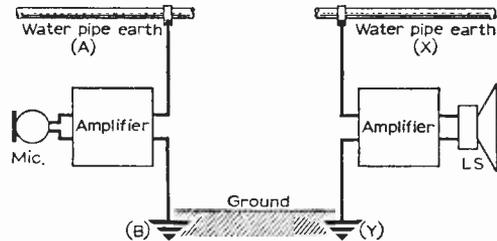


Fig. 3a (above): Diagram of a practical set up. Note that the water pipes are not used simply as conductors (the system would work even if the pipes at the transmitting and receiving ends were separate) but as convenient earthing points.

Fig. 3b (below): This shows how the resistance of the ground is used in the system of Fig. 3a. Only the current which flows in the direction AXYB is used; a much larger current flows through R1.

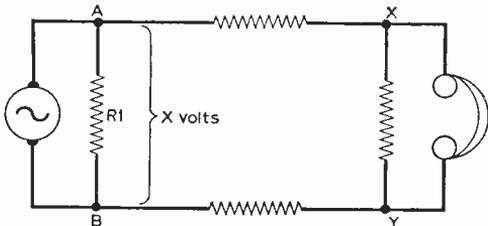

Depending on many factors, it may be anywhere between 100 and 3Ω.

If a pair of headphones are connected between the earth and the water pipes, a slight mains hum and an assortment of clicks and buzzes will be heard. This is all the equipment required at the receiving end. Both high and low impedance headphones work equally well.

An ordinary audio amplifier is used to provide the transmitted signal. The speaker output may be connected directly to the earth and the water pipes. The amplifier should be as powerful as possible; ranges of over a mile can be achieved with 8W amplifiers. Small low wattage transistor amplifiers

are no good for long distances. In spite of the mismatch at the transmitter, a clear signal should be received.

LONG DISTANCE RECEPTION

The received signal may be amplified if desired. Some kind of rough matching to the high input impedance of the amplifier would be required, and a loudspeaker output transformer connected in reverse would be suitable for this purpose.

EQUIPMENT REQUIRED FOR 2-WAY STATION

- 1 Audio amplifier, preferably 8 or more watts.
- 1 Output transformer, ratio unimportant.
- 1 Four-pole, two-way send/receive switch.
- 1 Earthing rod or substitute, see text.
- 1 Microphone.
- 1 Loudspeaker.
- 1 Water pipe earthing clip.
- 1 Long wire for connection to outside earth.

In case of difficulty, all these can be obtained from Electronic Constructors, Sutton Montis, Somerset.

Theoretically, for the best reception the earthing rod should be as far away from the nearest water pipes as possible at each end. Two earthing rods, as far apart as possible could be used instead of the earth-and-water pipe arrangement; this might reduce hum.

This method of communication is by no means a new idea but one that has been much neglected. There is much room for experimentation with multiple earth systems and tuned filters.

The writer hopes that anybody interested in this subject will write to him*; it would be interesting to start a "ground ham" club. This is an excellent medium for code practice as the received signal is very similar to that received on the short waves. ▀

* C. R. Bradley,
132 Horton Road,
Datchet,
Bucks.

on the Short Waves

A MONTHLY COMMENTARY BY J. GUTTERIDGE

AT some time or another when tuning around the short wave bands newcomers hear programmes mentioning DX, reception reports, short wave listeners and transmitting amateurs. The purpose of this feature is to help readers to get the best out of their short wave receivers.

The more experienced listeners will not be overlooked either. For them the latest information of frequency changes, new stations and unusual DX will be given. So that this feature can be as useful as possible we hope readers will write in and tell us of any news of interest and details of listening activities.

Where to listen

The first thing to know is where to listen. Bands of frequencies are allocated to different forms of broadcasting by international agreement. Amateur's operate in the 160 metre band (1,715—2,000kc/s); 80m band (3,500—3,800kc/s); 42m band (7,000—7,100kc/s); 20m band (14,000—14,350kc/s); 14m band (21,000—21,450kc/s); and 10m band (28,000—29,700kc/s).

On the short waves, broadcasting stations operate in the 125m band (2,300—2,498kc/s); 90m band (3,200—3,400kc/s); 75m band (3,950—4,000kc/s); 60m band (4,750—4,995kc/s and 5,005—5,060kc/s); 49m band (5,950—6,200kc/s); 41m band (7,100—7,300kc/s); 31m band (9,500—9,775kc/s); 25m band (11,700—11,975kc/s); 19m band (15,100—15,450kc/s); 16m band (17,700—17,900kc/s); 13m band (21,450—21,750kc/s); and 11m band (25,600—26,100kc/s). Not all stations adhere to these bands, however, and a number of stations can be heard outside them.

With a few minor variations, these bands are the same all over the world. These two main variations occur in North and South America. Here there are no 75 and 41 metre bands for general broadcasting. As a result the 80 and 42 metre bands have been extended to cover these frequencies.

Broadcasting Bands

Because of changes—daily, monthly and annually—in ionospheric conditions, the stations which can be heard in these bands are continuously changing. Here then is a run down on the present general situation in the various broadcasting bands. Amateur bands will be dealt with next month.

The 120, 90 and 60 metre bands are sometimes called tropical bands as they are mainly used for local domestic broadcasting by tropical countries. You will be extremely lucky to find a readable station on 120 and 90 metres. In the 60 metre band after dark careful tuning should find a number of South American stations and, particularly in the early evening, African stations. Morse (c.w.) interference usually makes things difficult.

Most of the stations in the 75 metre band are situated in Europe. They are at their best after dark. Long distance reception can also be achieved then.

During daylight hours 49 metres will produce mainly Europeans. After darkness almost anything can be heard. With the present night-time closure of most of the higher frequency bands many stations are using at least one outlet in this band. The result is a morass of stations broadcasting on top of each other. Freak things are happening and you may find the more unexpected stations coming out on top.

Worldwide Reception on 31 metres

Conditions on 41 metres are similar to those on 49, although the range of stations is slightly wider during daylight hours. World-wide reception is possible during the day on 31 metres. After dark this band is also giving good DX.

Conditions on 25, 19, 16 metres are basically similar. Good long distance DX during the daytime, North America being the most predominant continent in the 19 and 16 metre bands. As darkness falls 16 metre stations quickly disappear to be followed shortly by 19 metres. Twenty-five metres is now lasting well, many South American stations being audible during the evening.

The 13 metre band at present gives a very limited amount of long distance reception. As soon as darkness falls the band becomes useless. At present the 11 metre band is not worth bothering with at all.

Stations to watch for

Now to some news of stations. All times given here are G.M.T. The Radio Voice of the Gospel, P.O. Box 654, Addis Ababa, Ethiopia (call ETLF), says it is currently operating two 100kW transmitters. Although no programmes are beamed to Europe watch out for it after 1700 G.M.T. on 9,705kc/s when it has programmes to the Middle East and South Africa. Best chance of identification is from 1900-1930 when the programme is in English. You may also hear the English transmission to West Africa from 1830-1930 on 15,440kc/s. Full QSL verification is given for correct reports.

If you want to hear the latest in U.S.A. light and popular music try Radio New York World-wide, 4 West 58th Street, New York 19, N.Y., U.S.A. (call WRUL). Transmission to the British Isles is from 1230-1930 on 15,440kc/s and 1930-2145 on 9,710kc/s. If these frequencies are blocked try the continental European ones. These are 1230-1530 on 15,370kc/s; 1530-1830 on 15,385kc/s; 1830-2145 on 9,520kc/s. Finally, a good DX station in the 75 metre band. Watch out on 3,940kc/s after 2200 for the Voice of America relay station at Okinawa.

TRADE ENQUIRIES
INVITED

RADIO CLEARANCE LTD.

Telephone: MUSEUM 9188
EST. 35 YRS.

THE OLDEST COMPONENT SPECIALISTS IN THE TRADE
27 TOTTENHAM COURT ROAD, LONDON W.1


ANOTHER SCOOP— LIMITED QUANTITY ONLY

Don't miss a chance like this!

The "Minigram" Transistorised Record Player

FEATURES

- Ready-built amplifier with four first-grade Mullard transistors.
- Plays 45 R.P.M. pop records.
- Built-in automatic stop.
- Lightweight and portable.
- Instruction leaflet supplied.
- Crystal pick-up with expendable stylus.
- Operates from a 9V battery (3/6 ext.)
- Available in two colours—cream/red or cream/blue.
- A real "FAMILY FAVOURITE".
- Ideal for Teenagers.
- For use ANYWHERE.
- Hours of amusement for the younger members of the family.
- Assemble one of these amazing Players in less than 30 minutes; supplied in 3 complete units with only 11 competitors to make. Approximate dimen—lens 9x3 1/2 x 4in.

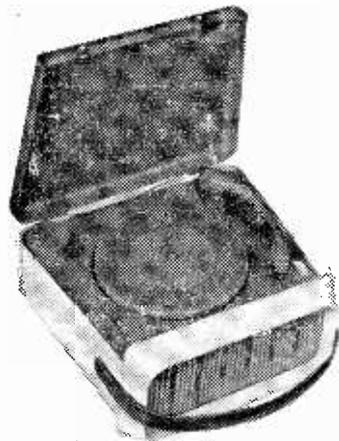

- A** Motor and pick-up deck.....(2/6 P. & P.) **39/6** ONLY **79/6**
- B** Ready-built 4-transistor amplifier, complete with volume control and L's peaker (2/- P. & P.) **35/-** the complete Pckgs. (plus 5/- P. & P.) or any unit sold separately.
- C** Portable two-tone case with handle, and expanded metal fret. (2/- P. & P.) **5/-**

Loudspeaker Bargains Still Available

Enormous purchases of Brand New and Guaranteed Plessey loudspeakers enable us to offer these units at THE LOWEST PRICES EVER! Don't miss this golden opportunity to obtain a first-grade permanent-magnet LOUDSPEAKER off the production line at LESS THAN THE MANUFACTURER'S COST! Read carefully the prepared list below and choose just the right speaker for the job—COMPARE THE PRICES ANYWHERE! SELLING FAST—STOCKS CHANGING RAPIDLY.

SCHEDULE OF LOUDSPEAKERS AVAILABLE

Diameter in inches	Gauss in lines	Imped. in ohms	Price	Diameter in inches	Gauss in lines	Imped. in ohms	Price	Diameter in inches	Gauss in lines	Imped. in ohms	Price	Diameter in inches	Gauss in lines	Imped. in ohms	Price
2	7000	80	8/-	3 1/2	9500	50	10/6	4	9500	35	11/6	5	8500	3	9/6
2 1/2	7000	35	8/8	4	7000	25	11/6	5	6000	3	8/-	5	9500	3	10/8
2 1/2	7000	50	8/8	4	6000	35	10/6	5	6000	3	8/8	5	9500	3	10/8
2 1/2	7000	80	8/8	4	7000	35	11/-	5	7000	3	8/8	6 1/2	7000	3	11/-
3 1/2	8500(E.M.L.)	3	8/8					5	7000	5	8/8	6 1/2	8500	3	11/6
3 1/2	7000	35	8/8					5	7500	3	9/-				

Elliptical Size	Gauss in lines	Imped. in ohms	Price	Elliptical Size	Gauss in lines	Imped. in ohms	Price	Elliptical Size	Gauss in lines	Imped. in ohms	Price	Elliptical Size	Gauss in lines	Imped. in ohms	Price
5 x 3	6000	3	7/8	5 x 3	9000	25	11/-	7 x 3	9500	3	10/6	8 x 2 1/2	8500	3	9/6
5 x 3	7000	3	8/8	6 x 4	6000	3	8/8	7 x 3 1/2	9500	3	10/6	8 x 2 1/2	9500	3	10/-
5 x 3	9000	3	8/8	6 x 4	7000	3	9/8	8 x 2 1/2	6900	3	8/8	8 x 2 1/2	9500	4	10/-
5 x 3	6000	25	9/8	6 x 4	8500	3	9/8	8 x 2 1/2	7000	5	9/8	8 x 2 1/2	9500	4	10/-
5 x 3	7000	25	10/-	6 x 4	9500	3	10/-								

ALLOW 2/- each Speaker for postage and packing, and please specify the exact requirements—the nearest available will be sent.

OVER 50,000 SOLD AND STILL THE DEMAND CONTINUES FOR OUR "HEAVENLY TWINS"

Ask for a demonstration in the shop.

"CAPRI"
Sensitive!
Super-selective!
Superb
Speaker!
NOW ONLY 79/6



(2/- P. & PKG.)
Pocket Superbet MW and Drotwich LW
Size 4 1/2 x 2 1/2 x 1 1/2 in.
Constructional data 1/9 Post free.

The best and easiest transistor build-yourself sets available.


Send S.A.E. for FREE PARTS LIST

6 First Grade MULLARD Transistors
Diode(s) and all components BRAND NEW and GUARANTEED

Choice of a dozen stations in daylight...

THE "CONTESSA"
"QUEEN OF THEM ALL"
ONLY **£9.19.6**
(3/6 p. & pkg.)

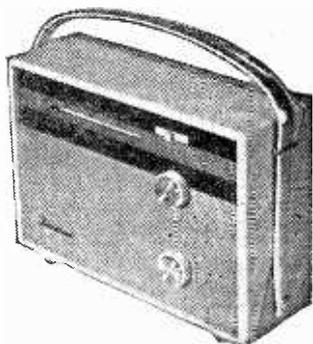PORTABLE and CAR RADIO 2 WAVEBAND SUPERBET
Construction manual 2/10 Post Free.



Inclusive price for all associated components, case, battery and instruction Book complete in every detail.
ANY PARTS SOLD SEPARATELY ON THE BUILD-AS-YOU-BUY SCHEME

CONTESSA £9.19.6 (plus 3/6 P. & P.)
CAPRI Battery 79/6 (plus 2/- P. & P.)

SELECTED BARGAINS

Beautifully geared AM/FM 2 gang Condensers. 4/8; AM/FM IFT's 465 kc/s and 10.7 Mc/s. 4/6 pair; Magnavox Crystal Tape Recorder Mikes. 12/6; Double-tuned Transistor ferrux IPT's Q120. 470 kc/s. 5/6 pair; transistor sub min. 7 mm coil set (4) 4/6, the set; Plessey-Brayhead turret tuners 34/38 Mc/s. valves 8/6 each; 3 watt Stereo Amplifiers, complete, ready to switch on 79/6; Sentercell rectifiers R3/2D-D3-2-1Y. 2/6 each. DIODES—OA70, OA79, OA90, CG46H, GD10. 2/- each.
TRANSISTORS: Set of 6 (RF and LF) including 1 watt matched pair, heat sink and diode, 13/6 the set; OC45 4/6, PXA101 3/6, AF115 4/6. Submin. Germanium diode 1/3. M.1 diode 6d. each. Silicon diodes, 200 p.i.v. 200 mA. 1/- each. 400 p.i.v. 330 mA. 2/6 each.
Please send STAMPED and ADDRESSED envelope with any enquiry. We regret no catalogues—our stocks move too quickly! Kindly make provision for additional postage and packing charges to avoid delay. Terms: Cash With Order or C.O.D. on Orders over 10/-

IMPROVED

STANDARDS OF

ACCURACY AND RELIABILITY

Modern styling in light grey with legible black engraving.

Constructed to withstand adverse climatic conditions.


Ever ready case, including leads, prods and clips.

Improved internal assemblies.

Re-styled scale plate for easy rapid reading. 2 basic scales, each 2.5 inches in length.

New standards of accuracy, using an individual calibrated scale plate. d.c. ranges 2.25% f.s.d. a.c. ranges 2.75% f.s.d.

Available accessories include a 2500V d.c. multiplier and 5, 10 and 25A shunts for d.c. current measurement.

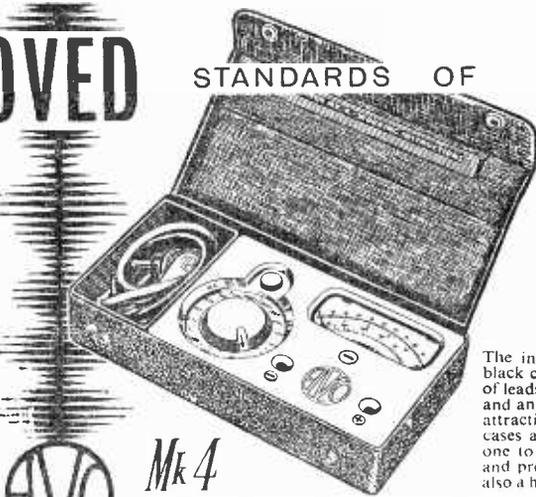

Mk 4

MULTIMINOR

The Mk. 4 MULTIMINOR is an entirely new version of this famous Avo instrument and supersedes all previous models. It is styled on modern lines, with new high standards of accuracy, improved internal assemblies, and incorporating panclimatic properties.

The instrument is supplied in an attractive black carrying case, which also houses a pair of leads with interchangeable prods and clips, and an instruction booklet. It is packed in an attractive display carton. Robust real leather cases are available, if required, in two sizes, one to take the instrument with leads, clips and prods, and the other to house these and also a high voltage multiplier and a d.c. shunt.

D.C. Current: 100µA f.s.d. — 1A f.s.d. in 5 ranges
 A.C. Voltage: 10V f.s.d. — 1,000V f.s.d. in 5 ranges
 D.C. Voltage: 2.5V f.s.d. — 1,000V f.s.d. in 6 ranges
 D.C. Millivolt range: 0 — 100mV f.s.d.

Resistance: 0-2 MΩ in 2 ranges using 1.5V cell.
 Sensitivity: 10,000Ω/V on d.c. Voltage ranges.
 1,000Ω/V on a.c. Voltage ranges.

For full details of this great new pocket-size instrument, write for descriptive leaflet.

AVO LTD AVOCET HOUSE - 92-96 VAUXHALL BRIDGE ROAD - LONDON, S.W.1 - Tel: Victoria 3404 (12 lines)




MM17

FORMULA 1456

THE NEW WAY TO BUILD HI-FI SAVES SPACE, TIME AND MONEY

Formula 1456 is the most popular combination of units in the brilliant new Martin Audiokit range, for it builds into a 10 watt hi-fi amplifier system complete with selector switch, tone-controls, power amp. and power supply. There are other units in the range, including a versatile 3-channel mixer, and all these units are adaptable to use in a great variety of applications. Performance standards are high, building is simple, costs are low—and once installed it is easy to add further Audiokits eventually up to stereo.

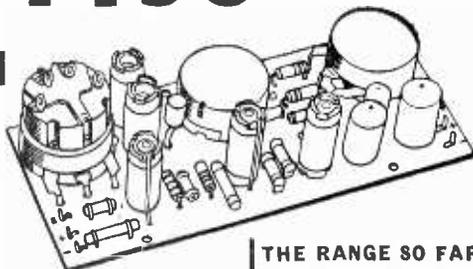

- ★ FULLY TRANSISTORISED
- ★ THE MOST FLEXIBLE KIT SYSTEM EVER

THE RANGE SO FAR

UNIT 1 5-stage input selector	£2 7 6
UNIT 2 Pre-amp with vol. control	£1 17 6
UNIT 3 3-channel mixer	
Matching adaptors for same, each	8 6
UNIT 4 Pre-amp and tone control	£3 2 6
UNIT 5 10 watt power amplifier	£5 12 6
UNIT 8 Mains power supply unit	£2 12 6

Kits complete with knobs, instructions, etc. Escutcheons available to requirement at 10/6 each.

MARTIN AUDIOKITS

KITS FOR TAPE ENTHUSIASTS, TOO

MARTIN RECORDKITS enable you to build a complete tape recorder (2 or 4 track) or pre-amp and deck assembly for use with hi-fi. LEAFLETS ON REQUEST.

TRADE ENQUIRIES INVITED

MARTIN ELECTRONICS LTD. 154-155 HIGH STREET, BRENTFORD, MIDDLESEX ISLeworth 5885/161

MARTIN ELECTRONICS, 154/5 HIGH STREET, BRENTFORD, MIDDLESEX

Please send details of MARTIN AUDIOKITS

Please send details of MARTIN RECORDKITS

NAME.....

ADDRESS.....

BLOCK LETTERS P.W.5

P.W.

Leader Competition

As already mentioned in this month's leader, page 25, the large number of entries to this competition and the high standard of many of them made the task of selecting the winners extremely difficult. Eventually, a short list of ten possible winners was drawn up. From these the winners were chosen; in fact the various contenders were so close that it was decided to add an extra prize for good measure. The winning two entries are reproduced on this page—they are printed as received and have not been altered in any way.

Debts of Gratitude

1

HOW often, I wonder, do any of our readers pause from slide-rule or soldering iron manipulation to hark back to their youth to recall the origin of the interest in radio and electronics that we all share? When I did this, recently, I came to realise that I probably owe unsettled debts of gratitude to a number of men whose names are now regrettably forgotten.

Submitted by

They lent or gave me wireless textbooks and magazines, taught me how to solder, allowed me into their "shacks", made my first "tatty" one-valver work, gave advice—in other words they fostered my interest. This did not cost them a great deal, in either time or money; however, the value of their help cannot be calculated—it grew to the extent of becoming my livelihood!

R. T. Pretty
Farnham
Surrey

In place of preoccupation with the problems of youth and public recitals of its shortcomings, would it not be a more positive step if some of us tried to repay our individual debts in this simple way? Merely letting the lad next door look over your shoulder while you set up one of the units you have built from a PRACTICAL WIRELESS circuit may give a youngster a glimpse of the career he wants, or bring him to one of the most satisfying hobbies there is.

Youth, Electronics and Educational Reform

FROM reading PRACTICAL WIRELESS and other publications it appears that large numbers of young people are actively interested in various branches of radio and electronics. In the towns and cities there are often radio clubs where the younger generation can benefit from the knowledge and experience of other older enthusiasts, but there are also large numbers who, because of isolation or other factors, work, read and acquire knowledge on their own. Thus the achievements of these individuals are limited.

All of these young people are potential electrical and electronics engineers. With new advances and developments in electronics, society will come to depend more on those qualified people than at present, and youth, with its assets of enthusiasm and talent, will have to meet the demand. Recent Government reports have indicated that there is a real shortage of engineers and technologists.

But is the educational system taking account of this? Most types of schools do not provide for modern sciences such as electronics at all, and often too much time is devoted to what are (to the prospective engineer) irrelevant subjects. If electronics was made a school subject the large numbers of teenage "lone wolves" of radio construction, as well as those belonging to radio clubs and societies, could broaden their knowledge and experience of electronics considerably and would be better fitted to pursue a career in this field.

More time must be given to practical work in schools because electronics, like almost all other modern sciences, demands the skilful co-ordination of hand and brain. It is the responsibility of teachers, parents and others who have influence in these matters to act immediately and prevent more time and talents being wasted, for this is a waste we can ill afford.

2

Submitted by

Charles Forbes
Strabane
Co. Tyrone
N. Ireland

And here is the extra prizewinner, awarded for being so close to the first and second entries.

Facts of Life

3

WE'RE a mixed bunch with many different interests in the various fields of electronics, but let us take another look at that little chappie who is the common denominator of all our activities.

Individually he's a pretty insignificant fellow, our mutual friend the Electron, but with his numerous pals he lights the world, broadcasts our views, entertains us, helps us run our trade and commerce and very often does our thinking for us.

Do we think enough about his reactions when he is pulled along under the influence of d.c., only to find himself suddenly squashed against the plate of a condenser, or again when being hurled across the vast space between cathode and anode? What are the effects as he struggles through the narrow confines of a resistor?

If we are to really enjoy and understand our hobby, whether it be amateur transmission, hi-fi, model control or any other of the sidelines catered for in this magazine a knowledge of what makes him tick is essential.

A number of people such as Ohm and Kirchoff spent their lives following his movements, checking on his relationships until at last a basic pattern of his behaviour was established.

These basic principles make up the common base from where all our separate paths lead. Let us remember to go back to base occasionally to replenish our store of knowledge and to meet again the hero of our story, the Electron.

Submitted by

Cyril M. Parry
Tonyrefail
Porth
Glamorgan

The judges felt that as the last ten to be considered were all serious contenders, some recognition of their merit should be given. Accordingly, here is a list of those entries—in no particular order—which came so close to winning one of the prizes:

Back to Basics: by A. S. Hussey, South Ockenden, Essex.

Endeavour: by K. L. Smith, London, E.17.

Satellites and the Ham: by F. Dawson, London, S.E.3.

Your Motive and Ours: by F. P. Mason, Sutton, Surrey.

Are We Becoming Earthbound?: by W. F. Clark, Chelmsford, Essex.

The Magic of Tomorrow: by R. Hodges, London, N.15.

Contributors: by R. A. Bower, Dunfermline.

Congratulations to the winners and to those with a "near miss", and many thanks to all those other readers who sent along entries for the competition. Space does not permit mentioning everyone by name but we hope that you will accept our appreciation for entering into the spirit of the contest.

Finally—

We thought readers would be interested in the entry published below. It could not be considered in the contest as the approach and viewpoint are not appropriate to a leader. However, it was so unusual—and the only one received from the wife of a reader—that we think it worth reproducing. After reading this, we ask married readers to search their consciences!

Grounds?

I AM a widow, a wireless widow. There are times when I wish Marconi had never been born. Still I suppose if it hadn't been Marconi it would have been someone else. When I sue for divorce I wonder what the Judge will say when I claim grounds for desertion and cite a radio as co-respondent.

I sit busy knitting or reading and then my better half looks up from the magazine he has been reading. "I say, do you know this firm only charges 1s. 9d. for a ferrite rod." Now what that is I have no idea, but murmur something appropriate. I needn't have bothered, he is already immersed in the magazine again.

We went to the local flower show last week or at least I thought that's where we were going. I might have guessed it. The first stop was the Amateur Radio Tent! The postman called yesterday. Ah! I thought, the magazine I was expecting. What a hope! it was the valves he had sent for.

This morning when I went to the door expecting to see the baker, it was a young girl. "Please can Mr. B. mend my radio, it is making funny noises." I make funny noises, only they are insides where no-one can hear them.

I settle at the sewing machine to make my new dress, and then pandemonium breaks out. The baby has got hold of a couple of valves and is busy banging them on the piano.


It's strange, but whenever I need to work in the kitchen there is always just one little wire which needs soldering! Thank goodness he knows nothing about TV. There are enough bits and pieces about now, not to mention the magazines and diagrams which I am constantly tidying up.

Submitted by


Mrs. Joyce Burdett
Leicester

4

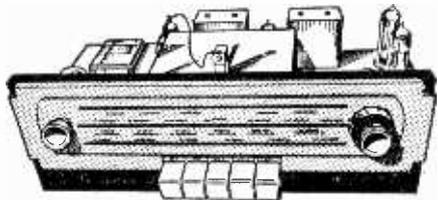BRAND NEW AM/FM (V.H.F.) RADIO GRAM CHASSIS AT £13.13.0 (Carriage Paid)



Chassis size 15 x 6 1/2 x 5 1/2 in. high. New manufacture. Dia. 14 1/2 x 4 in. in 2 colours, predominantly gold. 200-250 v. A.C. only. Pick-up, Ext. Speaker, Acc. F., and Dipole Speakers. Five push buttons—OFF, L.W., M.W., F.M. and Gram. Aligned and tested. O.P. Transformer. Tone Control. 1000-1900 Mc.: 200-650 Mc.: 88-98 Mc/s. Valves EZ80 rect.; ECH81, EF89, BABC80, EL84, ECC85. Speaker 8 x 5 in. and Cabinet to fit chassis (table model), 47/6 (post 5/-). 10 x 6 in. ELLIPTICAL SPEAKER 25/- to purchasers of this chassis. TERMS: (4 chassis) £3.10.0 down and 5 monthly payments of £2.4.0. cheap Room Dipole for V.H.F. 12/6. Feeder 6d. per yard. Circuit diagram 2/6. ALTERNATIVE DESIGN. L.W. 1000-1900 M. S.W. (9-15 Mc/s): M.W. 190-475 Mc.; V.H.F. 87-100 Mc/s: Gram. position. Otherwise similar to above chassis. Price £15.15.0 (carr. paid). TERMS: £3.10.0 down and 6 monthly payments of £2.4.0.

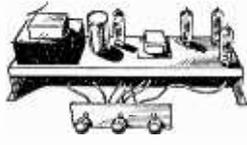

PUSH-PULL AMPLIFIER £5.5.0
(6/- Carr.)

Brand new 200/240 A.C. mains. Bass, treble and vol. controls, with valves EZ80, ECH83 and 2-EL84 giving full 8 w. Chassis 12 x 3 1/2 x 3 1/2 in. With o.p. trans. for 2-3 ohm speaker. Front panel (normally screwed to chassis) may be removed and used as "flying panel".

LAFAYETTE BRAND TAPES FULLY GUARANTEED AT RECORD LOW PRICES

MYLAR BASE	ACETATE BASE
5in. Double play, 1,200ft. . . . 16/-	5in. Long play, 900ft. . . . 10/-
5 1/2in. Long play, 1,200ft. . . . 16/-	5 1/2in. Long play, 1,200ft. . . . 12/6
5 1/2in. Double play, 1,800ft. . . . 22/6	7in. Long play, 1,800ft. . . . 15/-
7in. Stand. play, 1,200ft. . . . 12/6	MESSAGE TAPES
7in. Long play, 1,800ft. . . . 10/6	3in.—150ft. 3/6
7in. Double play, 2,400ft. . . . 25/-	3in.—225ft. 4/11
F.V.G. BASE	3in.—300ft. 7/6
5in. Standard play, 600ft. 8/6	P. & P. 1/- extra per reel; 4 reels
5 1/2in. Standard play, 800ft. 11/6	and over Post Free.

Full range of triple play Lafayette tape now available on all size spools—prices on request.

SELF-POWERED VHF TUNER CHASSIS. Covering 88-95 Mc/s. Mullard permeability tuner. Dims. 10 1/2 x 4 1/2 x 5 1/2 in. high. Valves ECC85 and 2-EF89's plus 2 diodes with EZ80 rectifier. Mains transformer. Fully wired and tested. ONLY £7.17.6 (carr. paid). Room dipole 12/6. Feeder 6d. per yard.



SPECIAL OFFER PRINTED CIRCUIT AM-FM CHASSIS AT ONLY £9

A small quantity of Printed Circuit chassis by famous manufacturer. Valves UY85, UCH81, UF89, UAB80, UL84 and UCC85. O.p. trans. for 2-3 ohm speaker. Chassis 14 x 7 x 7 in. Front controls concentric, left—Vol. and Tone; right—W/e and Tuning "Gold" centre knobs provided. 2-dial Bulb Sockets. Acc. F. Ext. sp. P.L. Mains isolating transformer free. Covers Long, Med., VHF (87-101 Mc/s). Unused slightly tarnished, but not dirty; New Mullard Valves. Dial in gold and brown, size 13 x 3 1/2 in.



6-TRANSISTOR PORTABLE — Fully Built


The "SCALA" for only £7.10.6, carr. paid. 8 1/2 x 2 x 5 1/2 in. high. Choice of colours. Resine. M.W. and L.W. Ferrite aerial. Battery 219 extra. Printed circuit. Nicely styled. A professional job. 3 1/2 in. speaker. Fully tunable M.W. and L.W. Superhet circuit.

100 mF. + 200 mF. ELECTROLYTIC. New 275 v. (350 v. surge). 4in. x 1 1/2 in. dia., 5/- each. (Post 1/-).

ALL ITEMS ARE NEW AND FULLY BUILT UNLESS OTHERWISE STATED. TESTED BEFORE DESPATCH. Terms Available on Items over £5. Send no. (stamp will do) for 20 page illustrated catalogue. Delivery by return. C.O.D. 2/- extra. ALL ITEMS GUARANTEED 12 MONTHS. VALVES 3 MONTHS

GLADSTONE RADIO
"SCALA", CAMP RD., FARNBOROUGH, Hants.
Farnborough 3871 CLOSED SATS.

"REALISTIC" 'SEVEN'

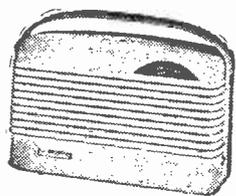

7 Transistor Superhet. 350 Milliwatt output, 4-inch speaker. All components mounted on a single printed circuit board size 5 1/2 x 5 1/2 in. in one complete assembly. Plastic cabinet, with carrying handle, size 7 x 10 x 3 1/2 in. External Socket for car aerial. Ferrite rod aerial. Price for the complete parcel including Transistor, Cabinet, Speaker, etc., and full Construction Data: **£5.19.6** P. & P. 4/6.


PP9 Battery 3/6. Data and instructions separately 2/6. Refunded if you purchase the parcel.
Any parts supplied separately.

4 TRANSISTOR MINIATURE PUSH-PULL AUDIO AMPLIFIER

PRINTED CIRCUIT. 5in. x 2in. x 1 1/2 in. over transformers. Output for 3-ohm speaker. Suitable for microphone, record player, guitar and radio input. 12 volt battery required. Frequency range 100 cps. to 25 Kcps. Push/pull output single ended. Instruction sheet provided. Fully wired ready for use. Three types. 200mW, 29/6; 500mW, 35/-; 1 watt, 41/- P. & P. 2/6.

THIS SUPERB SET for £9 (Carr. pd.)

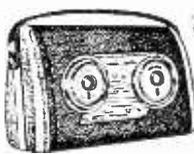6-transistor radio covered in provision-clean Duracour fabric, in latest two-tone shades, M.W. and L.W. ferrite rod, sponge for car aerial, 2-colour scale. With PP9 battery giving 300 hours use. Weighs under 4 lbs. With carrying handle. 12 x 7 in. high x 4 1/2 in. at base tapering to 2 in. at top. Brand new, fully guaranteed. 3 push buttons. Superhet circuit, 5in. L.S.



5 WATT AMPLIFIER

Our price ONLY 58/- (post 5/-); a few hundred only; valves EF91 and EL84 with metal rectifier; 6 x 4 x 1 1/2 in. high (5in. over EL84). Mains trans. and o.p. with vol. and tone controls; on-off; co-ax. input.

GRAMOPHONE AMPLIFIERS

1 1/2 watt type. With 5in. speaker. Baffle 12 1/2 x 6 in. 200-240 v. A.C. EL84 and Rectifier. Tone and Volume. On/off switch. Two knobs. Ready to play. Useful for Stereo, 49/6, post 5/-.
4 watt type. Valves UY85, UF80 and UL84. 200-240 v. A.C. Covered baffle 13 1/2 x 7 1/2 in. (6in. speaker), 3 front controls; bass, treble, on-off/vol., 60/-, post 5/-. Double wound mains transformer.

HIGH QUALITY PUSH-PULL OUTPUT AMPLIFIER

Chassis 10 x 7 1/2 x 7 1/2 in. high over trans. Used, guaranteed and in excellent order. New valves EZ40, ECC83 and 2 x EL81; 8 watts. Mains trans. tapped 200-250 volts. O.p. Trans. for 3, 8 and 15 ohm. Choke smoothing. On-off/vol., and tone controls. For tuners, Record Players, etc., £8.15.0. P. & P. 6/-. We can modify for Guitar input for 15/- extra.

TRIPLE-FOUR STEREO PUSH-PULL OUTPUT AMPLIFIER

Chassis 10 1/2 x 4 1/2 x 4 1/2 in. high. New production. Valves 4 x ECL83 and 1—ECC83. Two metal rect. Mains trans. and 2 o.p. trans. Separate control panel 7 1/2 x 4 in. containing Mono/Stereo switch; balance; vol.; treble; bass. Brand new. £7.17.6. P. & P. 6/-.
4-SPEED AUTOCHANGERS

BRR-UA14	£5.19.6
GARRARD AUTOSLIM	£8.10.0
STEREO	£7. 5.0
AUTOSLIM DE LUXE A76	£10.19.6
STEREO	£11.10.0

Carr. 5/- each.

BATTERY ELIMINATOR

For 4 Low Consumption Valves (96 ranges) 90v. 15 mA and 1.4v. 125mA, 45/- (4/- post). 200-250v. A.C. Also for 250mA, 1.4v. and 90v. 15mA at same price. Two separate units to replace existing batteries. 4 x 2 1/2 x 2 1/2 in. and 3 x 2 1/2 x 1 1/2 in.

13 x 8 in. LOUSPEAKER
Three ohm. Ceramic magnet of latest type. BRAND NEW.
42/6 (post 3/6)

HEATER TRANSFORMER

Mains input giving 6.3v. 2 amp. Size 2 1/2 x 2 x 1 1/2 in. (2 1/2 in. over winding) 5/8 ea. Loss 10% for 12, or 20% for 50. P. & P. 2/- for 1 to 6, post free more than six.



THE SKYROVER AND SKYROVER De Luxe

General Specification for both models

7 transistors and 2 diode superhet—6 waveband portable receiver, covering the full Medium Waveband (180-576M) and Short Waveband (31-94M) and in addition 4 separate switched Band Spread Ranges on 13M, 16M, 19M and 25M/bands—with manual Band Spread Tuning for accurate Station selection, I.F. frequency 470Kc/s. Output 300MW, 5in. Ceramic Magnet P.M. Speaker, Telescopic and internal Ferrite Rod Aerial. All Mullard Transistors and Diodes. The 301i Pack and tuning head is completely factory assembled, wired and tested. The remaining assembly can be completed in under three hours from our detailed and easy to follow instructions. Operates on four 1.5V torch batts. (U2 or equivalent).

THE SKYROVER. Individual Details—controls: Waveband Selector, Volume Control with on/off switch, Tuning Control with easy to read Dial Scale. In attractive plastic cabinet, size: 10 x 6 1/2 x 3 1/2 in., with metal trim and carrying handle.

MAY BE BUILT FOR £10.19.6 All Parts Sold Separately.

H.P. Terms 22/- deposit and 11 monthly payments of 21/-

THE SKYROVER De Luxe. Tone Control Circuit is incorporated with separate Tone Control in addition Volume and Tuning Controls and Waveband Selector. In sturdy wood cabinets, size: 11 x 6 1/2 x 3 in. covered in washable material with plastic trim and carrying handle. Also Car Aerial socket.

MAY BE BUILT FOR £12.19.6 All Parts Sold Separately.

H.P. Terms 22/- deposit and 11 monthly payments of 24/6

Circuit diagram and data for each set 2/6 extra, free if all parts bought. Free U2 batteries included FREE. Add 5/- P. & P. on each set.

THE PETIT FULMITER A.C. ELIMINATOR and BATTERY CHARGER 18/6 P. & P. 1/6. (approx. same size as PP3 battery).

MORE TRANSISTOR RADIOS FOR HOME CONSTRUCTION

THE "REALISTIC" 7

Seven transistor portable receiver—full L. and M. waveband coverage. 4in. speaker. Full description last appeared April '64. **MAY BE BUILT FOR £5.19.6** Battery 3/6 extra. P. & P. 4/6

Also De Luxe Model with superior PVC covered wood cabinet and full view tuning dial. **MAY BE BUILT FOR £6.19.6.** All parts sold separately. Battery 3/6 extra. P. & P. 4/6

THE "SPRITE"

6 transistor mini pocket receiver. Full L. and M. waveband coverage. Size only 4 x 2 1/2 x 1 1/2 in. In sub assemblies. 3in. speaker. **CAN BE BUILT FOR 7/9.6** phone and battery. Post carrying case. All parts sold separately. P. & P. 3/6.

READY BUILT BARGAINS

2 transistor pocket radio—complete with earpiece, telescopic aerial, battery and case. Medium waveband. **42/-** Post Size 4 x 2 1/2 x 1 1/2 in. Complete with accessories. **Free**

Also 8 transistor model. Long and medium waveband. Fully built complete with earpiece, battery and leather 7/9.6 **Free** Post carrying case.

SUPER AMERICAN TAPE

LAFAYETTE B-BAND, FULLY GUARANTEED RECORD LOW PRICES

MYLAR BASE	ACETATE BASE
5in. Double play, 1,200ft. 15/-	5in. Long play, 900ft. 10/-
5 1/2in. Long play, 1,200ft. 15/-	5 1/2in. Long play, 1,200ft. 12/6
5 1/2in. Double play, 1,800ft. 22/6	7in. Long play, 1,800ft. 15/-
7in. Standard play, 1,200ft. 12/6	7in. Standard TAPE 7/-
7in. Long play, 1,800ft. 21/6	3in.—150ft. 3/6
7in. Double play, 2,400ft. 25/-	3in.—25ft. 4/11
P.V.C. BASE	3in.—300ft. 7/6
5in. Standard play, 600ft. 9/6	All other makes, types and sizes in stock
5in. Standard play, 850ft. 11/6	
P. & P. 1/- extra per reel. 4 reels and over Post Free.	

WIRECOMP ELECTRONICS

378 HARROW ROAD, LONDON W9
 TEL: CUNNINGHAM 9330
 Hours of business: 9 a.m. to 6 p.m. Open all day Saturday. Opposite Paddington General Hospital. Buses 181 and 36 pass the door.

Z & I AERO SERVICES LTD.

Head Office and Warehouse: 44A WESTBOURNE GROVE, LONDON W.2, Tel: PARK 5641/213

FIRST QUALITY ELECTRONIC VALVES FOR EX-STOCK DELIVERY																		
0A2	4/-	6AM4	15/-	68N7GT	4/6	25Z25	7/-	DAF96	5/8	EF37A	6/-	GZ32	10/-	PL82	6/8	UBA80	5/-	
0A3	11/-	6AM6	4/-	68Q7GT	5/-	35Z26GT	3/8	DD141	7/8	EF39	5/-	GG24	10/-	PL83	6/8	CAF42	8/6	
0A81	2/-	6AA5	6/-	68Q8T	6/8	68D17	6/-	DF98	6/-	EP40	6/-	GZ34	8/6	PL84	6/8	UBC41	6/6	
0B2	6/-	6AS6	5/-	6U7G	10/-	30C15	5/8	DF96	5/8	EF41	6/8	HYR2	7/-	PL50	13/-	UBC81	7/6	
0C3	5/8	6AS7G	22/6	6V6	9/-	30F5	6/8	DK40	11/-	EF42	6/-	K78C	25/-	PM44	8/-	EPF80	6/6	
0D3	5/-	6AT5	4/-	6V6G	3/8	30FL1	9/-	DK92	6/8	EP80	5/-	K786	15/-	PY33	10/-	UBC90	7/6	
1A5	4/8	6A06	5/-	6V6GT	5/-	30PL14	12/6	DK96	6/8	EP83	9/8	K788	20/-	PY40	4/8	UBL21	11/-	
1A7GT	7/-	6AV6	5/-	6X4	4/-	30P19	12/-	DL89	10/-	EP85	6/-	K7W92	7/-	PY51	6/8	UBA84	8/6	
1D6	7/8	6B7	5/-	6X5G	3/8	30PL1	10/8	DL96	6/-	EP86	5/8	ME47	7/8	PY92	5/-	UCS5	6/6	
1G6GT	7/8	6B8G	2/6	6X5GT	5/8	35A5	11/8	DM70	5/-	EP89	4/8	MHL86	11/8	PY93	6/-	UCF80	9/8	
1H5GT	7/8	6BA	4/8	7C6	6/-	35L6GT	6/8	DY88	7/-	EP95	5/-	MU14	4/-	PY88	7/8	UCH21	8/6	
1R5	5/8	6B2F	5/-	7Y4	7/-	33V4	4/8	EB88C	15/-	EP98	9/-	N73	15/-	PY89	6/8	UCH72	7/6	
184	4/8	6BRH6	7/-	9BW6	7/-	33Z4T	7/-	EB83	6/-	EP83	2/6	OP71	2/6	PY90	6/8	UCH81	7/6	
185	4/8	6BRH6	7/-	1011	7/-	33Z5GT	5/-	EB10F	15/-	EM87	8/8	PAB30	7/-	QQV02	10/-	UCR3	8/6	
174	3/-	6B1K4	20/-	10114	12/-	50B55	6/-	EB10CC	10/-	EN90	7/8	PC46	12/-	45/-	UF42	7/6		
1U4	6/-	6BQ7A	7/-	11B5	7/-	50C6	6/-	EB1C90	8/-	EL34	10/-	PC97	8/6	QQV03	10/-	UF42	7/6	
1U5	5/-	6B17	11/-	11B5	7/-	50C19G	25/-	EB1C92	6/-	EL36	9/8	PC84	8/6	35/-	UF80	6/6		
1X2A	7/-	6BR8	5/-	12AC6	6/-	201AGT	6/-	EB1C3	13/-	EL37	17/6	PC86	7/-	R10	15/-	UF85	6/6	
1X2B	7/-	6BR6	9/-	12A18	11/-	58K4	9/-	EB1C33	7/-	EL38	17/6	PC88	10/-	R15	7/8	UF86	8/6	
20W4	14/-	6BW7	9/-	12AT6	9/-	83	8/-	EB1C41	6/8	EL41	7/8	PC99	10/-	R19	6/-	UF89	6/6	
2D21	6/-	6CSGT	6/-	12AT7	9/-	85A2	8/8	EB1C81	6/8	EL42	7/8	PCU18	10/-	R118	12/6	UL4	6/6	
3A4	8/8	6C8G	7/-	12AT6	6/-	90A4	15/-	EBP90	6/8	EL81	6/8	PCF80	6/8	R23	12/6	UBA	6/6	
3A5	7/-	6C86	5/-	12AU7	5/-	90C1	13/-	EBP83	7/-	EL83	7/8	PCF82	6/8	TH41	10/-	UM10	8/6	
3B7	4/8	6CDD6G	17/6	12AV7	8/-	807	9/-	EBP89	6/-	EEL84	5/-	PCF84	10/-	TH233	6/8	UM80	7/6	
3D6	3/-	6CL6	10/-	12AX7	6/-	832	20/-	EB1L1	11/-	L85	7/-	PCF86	8/-	TH2321	7/8	UY21	8/6	
3E29	50/-	6CW4	14/-	12AX7	10/-	86A4	14/6	EB1L21	11/-	EL86	7/8	PCF80	10/-	TH22	4/8	UY41	5/8	
3E4	6/8	6D15	7/8	12BA6	6/-	884	10/-	EBP82	6/8	EL87	8/8	PCP02	10/6	TH25	5/8	UY45	5/8	
3Q5GT	6/8	6D14	15/-	12BA6G	6/8	95A4	5/-	EBP84	5/-	EL92	6/-	PCL81	9/-	TH2620	7/8	YCR139A	25/-	
384	5/-	6D8A	15/-	12BH6	6/8	95A4	5/-	EBP84	5/-	EL822	8/-	PCL83	6/8	TT15	36/-	525/-		
3V4	5/8	6E7	4/8	12B17	6/8	95E7	5/-	EBP84	6/8	EM34	9/8	PCL84	8/8	TT21	32/-	YP4	12/6	
584GY	9/-	6E17	6/-	12E1	20/6	988A	4/8	EBP85	6/8	EM80	6/8	PCL84	6/8	U12/14	7/8	YH18	9/8	
5U4G	5/-	6E23	8/8	12CA6	10/8	989	4/8	EBP85	6/8	EM81	7/8	PCL85	8/8	Y22	5/8	X63	5/6	
5U4GB	6/-	6E14	9/-	12C6T	9/8	95E70	10/-	EBP86	7/8	EM84	8/8	PCL86	8/8	U24	12/-	X79	15/6	
5V4G	6/-	6E15	5/-	12C6T	3/8	95E73	10/-	EBP87	7/8	EM85	9/-	PCN45	6/8	U25	11/-	Z69	7/6	
5Y3G	4/8	6E7G	4/-	12B7	5/-	9599	6/-	EBP86	11/-	EN31	10/-	PCN45DD	U31	6/8				
584GT	6/-	6E8GT	6/-	12BQ7	10/-	6146	27/6	EBP87	9/-	EN32	10/-	11/-	U60	5/8	Valve Bases			
5Z4	9/-	6E7	5/-	13B16	6/-	AC7E/TH14	6/8	EBP88	10/-	EN31	7/-	PCN38	10/6	U76	5/8	USM4	1/6	
5Z4GT	8/-	6E8G	4/-	12AQ5	6/-	AC7E/PC6	6/8	EBP88	7/-	EN81	7/8	PCN384	7/-	U91	9/-	USM4	1/6	
6A8G	6/-	6E6	9/-	130B6G/10	6/-	91	6/8	EBP88	6/-	EY84	7/8	PCN45	12/6	U251	12/6	USM5	1/6	
6A8A	6/8	6E6G	9/-	20L1	12/-	A21	5/8	EBP88	7/8	EY85	5/8	PCN45	9/8	U281	13/6	BSA	1/-	
6A4P	21/6	6E18	8/-	20P1	14/-	AZ31	8/-	EY86	6/8	EZ40	5/8	PENDD	U282	12/6	HTA	1/6		
6A15	5/-	6E7	6/8	20P1	12/6	AZ41	6/8	EY87	6/8	EZ41	6/8	4020	U283	17/6	BBG	1/8		
6A15	11/-	6E7G	6/-	25AG6	8/-	41E1	6/8	EY88	6/8	EZ40	3/8	PL36	8/8	U408	7/8	41	25/6	
6A8E	5/-	68E7	5/-	25L6T	4/-	E1C33	9/-	EY86	6/8	EZ81	4/8	PL38	16/8	U801	20/-	BBA	1/6	
6A8E	7/-	68L7GT	4/8	25Z4G	6/8	EY31	5/8	EY89	12/-	GZ30	10/-	PL81	7/8	U4020	5/-	B9G	2/6	

TRANSISTORS

OC28	..	17/6	OC75	..	6/-
OC35	..	15/-	OC78	..	6/-
OC44	..	8/-	OC78	..	7/6
OC45	..	6/6	OC79	..	7/6
OC70	..	5/6	OC189	..	12/-
OC71	..	5/6	OC170	..	8/6
OC72	..	8/-			

Set of two matched OC81 and one OC81D, 12/6.

GET115 .. 7/- GET575 .. 20/-

Matched pair of GET375 .. 35/-

R.O.A. 2N410 (OC45) .. 3/-

R.O.A. 2N412 (OC44) .. 3/-

Spot Marked:

Red	1/8	White	2/8
Yellow	2/8	Green	1/6

SILICON SEMICONDUCTOR RECTIFIERS

2E8	500 p.p.t.v.	200mA	..	3/6
BY100	700 p.p.t.v.	450mA	..	8/6
Lucas DD088	800 p.p.t.v.	12/6
500mA

CATHODE RAY TUBES

1D7-5	55/-
DG7-6	85/-
DG13-2	80/-
VC97	40/-
VC138A	50/-
VC138A	60/-
VC138A	25/-
VC817 V or C	40/-
8M1	40/-
89J	80/-

SIGNAL DIODES

GA81	2/-
Y442	1/8
OC10E	1/8

All our valves carry full manufacturers' guarantee. Any faulty item is replaced immediately free of charge. Please add 2/6 2 for postage and handling.

A SIMPLE 2-stage Amplifier

**A ONE-VALVE RECORD PLAYER AMPLIFIER DELIVERING UP TO 3.5W OUTPUT
BY G. J. KING**

THIS amplifier is designed to give good quality reproduction of disc records for the smallest possible outlay. Although it features a simple, single-ended output stage and a modest one valve, it is nevertheless capable of delivering a maximum of 3.5W of audio.

At 2W output the total distortion is less than 0.5%, but as with any small amplifier of this nature the distortion tends to rise rapidly towards full output. At 3W the distortion is a little below 3% and gets up to the 10% mark at full output of the valve.

For many domestic applications the peak power rarely exceeds 1 to 2W, for this is quite a loud noise from a sensitive speaker system, and within

($\mu = 100$) and the high slope of the pentode ($gm = 10mA/V$ at an anode current of 36mA) provide a remarkably high overall sensitivity. In a normal circuit the pentode section is fully driven from a 50mV signal applied to the grid of the triode section.

Thus, by the use of a crystal or ceramic pick-up, quite a large degree of negative voltage feedback can be applied overall and still the valve can be driven to full output. Hitherto such circuit technique has demanded the employment of a separate pre-amplifier valve or very little or zero negative feedback. This is one of the reasons why previous single-stage record reproducing amplifiers, such as those used in certain commercial instru-

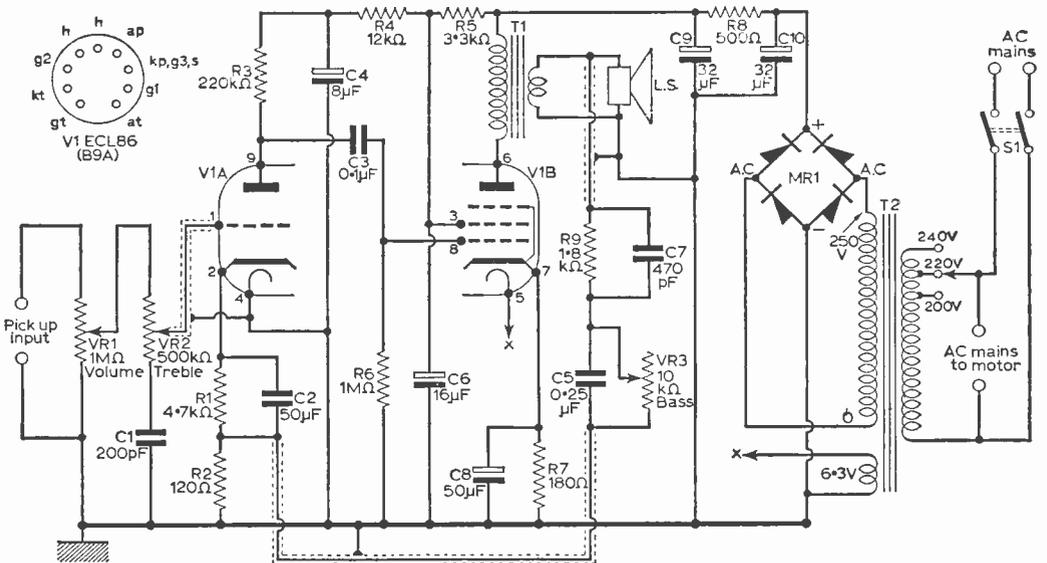


Fig. 1: The complete circuit of the amplifier.

this range of power the amplifier has several hi-fi attributes.

Audio Triode-Pentode Valve

The design is based on the Mullard ECL86, which is a fairly recent triode-pentode valve evolved specifically for audio applications. The high amplification factor of the triode section

ments of the popular price range, having quite a long way to go to give anything approaching hi-fi quality.

Apart from the valve, the quality of reproduction is tied closely to the design of the output or speaker transformer. The goodness of this component governs the amount of negative feedback which can be applied before the amplifier goes

unstable at certain frequencies where the phase shift is excessive. Preferably, the transformer should be free of resonances well above the audible spectrum. Bad resonances at the top end of the a.f. spectrum will tend to incite instability with full treble lift.

The Circuit

The circuit is based on a design by Mullard Limited, but with small alterations to suit the application in mind. As shown in Fig. 1, a completely isolated mains transformer is employed. It was decided to adopt this safer method rather than trying to cut costs by the use of an a.c.-d.c. arrangement, for it was thought that experimenters may wish to use the amplifier in conjunction with some other equipment, such as a tape recorder, in which case a "live" chassis would prove somewhat of an embarrassment.

To facilitate smoothing and to maintain the lowest possible hum level a bridge h.t. rectifier circuit was chosen. The bridge rectifier is a contact-cooled type with a current rating of 50-75mA. The power section, in fact, has a very wide safety margin, for the amplifier takes little more than 40mA. But this was thought desirable as it not only allows the amplifier to be operated continuously over long periods without heating up, but it also gives a bit of spare power should it be required to fit a pre-amplifier stage for a tape head.

The triode section is arranged as a voltage amplifier, with feedback applied to the cathode circuit from the output of the pentode section. The gain of the triode section is approximately 50 times. The pick-up signal is applied across the volume control VR1, and from here it goes to the treble control VR2 which, in conjunction with C1, forms a passive RC network, giving continuous treble cut from about 300c/s.

R3 is the triode anode load which is fed from the h.t. line through a two-stage filter R5, C6 and R4, C4. V1A is biased by the voltage drop across R1 and R2 in series, and R3 is bypassed by C2 to avoid degeneration due to negative current feedback. The feedback voltage is effectively applied across R2.

The signal at the anode of V1A is coupled to the control grid of V1B via C3, with R6 as the grid-leak. The screen of the pentode is energised at R5, C6 filter, while the valve is biased by the voltage dropped across the cathode resistor R7, with C8 as the bypass.

The pentode operates with an anode load of 7k Ω , so an impedance of this value must be reflected across the primary winding of the output transformer when the required speaker is connected (see List of Components). One side of the secondary is connected to chassis and the other side to the negative feedback and bass control loop. The secondary, of course, also connects across the speaker.

Negative feedback is taken through the network C5, C7, VR3 and R9. The parallel combination C5 and VR3 forms the bass control proper. This provides continuously variable bass boost from about 1,500c/s.

The main h.t. smoothing is achieved by C9 and C10 and R8. Note that it may be necessary to

adjust the value of R8 to give 275V on the h.t. line, relative to chassis.

Construction

A prototype amplifier was constructed in two sections—the amplifier proper and a separate control panel. This was considered desirable for it allows the control panel to be mounted almost anywhere in a cabinet, for accessibility of the controls, without having to bother too much about the positioning of the amplifier chassis.

The control panel is connected to the amplifier chassis through three cables, two of which are screened. A screened single conductor is employed to couple the grid of the triode to the treble control VR2, a screened double conductor for the negative feedback and bass control VR3, and a

COMPONENTS LIST

Resistors:

R1	4.7k Ω 5%	R6	1M Ω 10%
R2	120 Ω 5%	R7	180 Ω 2W ww 5%
R3	220k Ω 5%	R8	500 Ω 2W 10%
R4	12k Ω 10%	R9	1.8k 5%
R5	3.3k Ω 10%		

All 1W carbon unless otherwise indicated

Potentiometers:

VR1	1M Ω log. with two-pole on/off switch
VR2	50k Ω linear
VR3	10k Ω log.

Capacitors:

C1	200pF ceramic 10%
C2	50 μ F electrolytic 12V
C3	0.1 μ F paper 350V
C4, 6	8 + 16 μ F electrolytic 350V
C5	0.25 μ F paper 350V
C7	470pF ceramic 10%
C8	50 μ F electrolytic 25V
C9, 10	32 + 32 μ F electrolytic 350V

Miscellaneous:

- T1 Speaker transformer. Ratio 46 : 1 for 3 Ω speaker, or 21 : 1 for 15 Ω speaker. Primary inductance 10H. (Radiospares "Hygrade").
- T2 Mains transformer. Secondaries 0-250V 75mA; 6.3V 1.5A (Radiospares "Bridge" type).

V1 ECL86

MRI Bridge rectifier, 250V 75mA

One B9A valveholder, nylon loaded and with screening skirt. One two-way and one four-way tag strips. One two-way speaker socket. Soldering tags, 6 and 4 BA nuts and screws. Screened cable, single conductor and also double conductor. Connecting wire and flex. Three control knobs. Metal for chassis.

length of plastic flex for the circuit between the mains primary of T2 and the on/off switch S1, which is ganged to the volume control VR1.

The inter-connecting cables should not exceed about 18in. in length owing to the high impedance of the input circuit, and because of the high sensitivity of the ECL86 the utmost of care must be taken to avoid stray capacitive coupling between the grid of the triode section and the anode circuit of the pentode section. Excessive unwanted coupling here will result in instability which will increase in severity as the treble control is turned up. The negative feedback will also be adversely affected due to phase shift effects.

The connection to Pin 1 should, therefore, have

PORTABLE TRANSISTOR RADIOS

BACKED BY SUPER AFTER SALES SERVICE

ROAMER SEVEN Mk III

● 9 stages—7 transistors and 2 diodes

Covers Medium and Long Waves, Trawler Band and two Short Waves to approx. 17 metres. Push-pull output for room filling volume from rich toned heavy duty 5in. speaker. Air spaced ganged tuning condenser. Ferrite rod aerial for M & L waves and telescopic aerial for S Waves. Simulated hide case with gilt trim and shoulder and hand straps. Size 9 x 7 x 4in. approx. The perfect portable and the ideal car radio. (Uses PP9 battery available anywhere.)


5 WAVEBAND PORTABLE OR CAR RADIO

Amazing performance and specification

Total cost of parts now only

£5.19.6 P. & P. 5/6

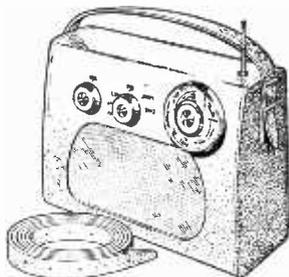Parts Price List and easy build plans 3/-.




TRANSONA FIVE

Home, Light, AFN, Lw, all other stations, G.P., Busham

● 7 stages—5 transistors and 2 diodes.

Fully tunable over medium and Long Waves and Trawler Band. Incorporates Ferrite rod aerial, tuning condenser, volume control, new type fine tone super dynamic 2 1/2in. speaker etc. Attractive case. Size 6 1/2 x 4 1/2 x 1 1/2in. with red speaker grille. (Uses 1289 battery available anywhere.)

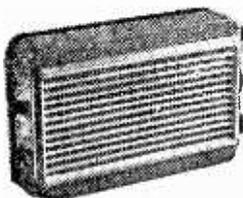Total cost of all parts now only **42/6** P. & P. 3/6.



Parts Price List and easy build plans 2/-.

TRANSONA SIX

NEW!

● 8 stages—6 transistors and 2 diodes.

This is a top performance receiver covering full Medium and Long Waves and Trawler Band. High-grade Ferrite magnet 3in. speaker makes listening a pleasure. Push-pull transformers for ample power. Ferrite rod aerial. Many stations listed in one evening including Luxembourg loud and clear. Attractive case in grey with red grille. Size 6 1/2 x 4 1/2 x 1 1/2in. (Uses PP4 battery available anywhere). (Carrying strap 2/- ex.)

Total cost of all parts now only **59/6** P. & P. 3/6



Parts Price List and easy build plans 1/6


SUPER SEVEN

● 9 stages—7 transistors and 2 diodes

Covers Medium and Long Waves and Trawler band. Completely portable—has built-in Ferrite rod aerial for wonderful reception. Push-pull output, 3in. speaker (will drive larger speaker). Size 7 1/2 x 5 1/2 x 1 1/2in. (Uses 9v. battery, available anywhere.) (Telescopic Aerial for Trawler Band (optional) extra. 6/11.

Total cost of all parts now only **£3.19.6** P & P. 3/6

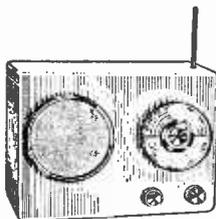Parts Price List and easy build plans 2/-.



MELODY SIX

FREE!

... amazed at volume and performance... has really come up to my expectations." S. G., Stockton-on-Tees

Miniature Earpiece, plug and socket (value 9/6) and details of conversion to private listening.

● 8 Stages—6 transistors and 2 diodes.

Our latest completely portable transistor radio covering medium and long waves. Incorporates pre-tuned circuit board, 5in. heavy duty speaker, top grade transistors, volume control, tuning condenser, wave change slide switch, sensitive 6in. ferrite rod aerial. Push-pull output. Wonderful reception of B.B.C. Home and Light, 208 and many Continental stations. Handsome leather-look pocket size case, only 6 1/2 x 3 1/2 x 1 1/2in. approx., with gilt speaker grille and supplied with hand and shoulder straps.



Total cost of all parts only **£4.9.6** P. & P. 3/-.

Parts Price List and easy build plans 2/-.

ROAMER SIX

FREE! Miniature Earpiece, plug and socket (value 9/6) and details of conversion to private listening.


● 8 stages—6 transistors and 2 diodes.

Listen to stations half a world away with this 5 waveband portable. Tunable on Medium and Long waves, Trawler Band and two Short waves. Sensitive ferrite rod aerial and telescopic aerial for short waves. Top grade transistors, 3-inch speaker, handsome case with gilt fittings. Size 6 1/2 x 4 1/2 x 1 1/2in.

POCKET FIVE

● 7 stages—5 transistors and 2 diodes.

Covers Medium and Long Waves and Trawler Band, a feature usually found in only the most expensive radios. On test Home, Light, Luxembourg and many Continental stations were received loud and clear. Designed round supersensitive Ferrite Rod Aerial and fine tone 2 1/2in. moving coil speaker, built into attractive black case with red speaker grille. Size 5 1/2 x 1 1/2 x 3 1/2in. (Uses 1289 battery available anywhere.)

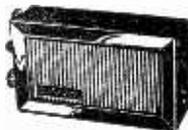

Total cost of all parts now only **42/6**

P. & P. 3/-

Parts Price List and easy build plans 1/6

Total cost of all parts now only **£4.19.6** P. & P. 3/6.

Parts Price List and easy build plans 1/-.

All components used in our receivers may be purchased separately if desired. Parts price lists and easy build plans supplied free with sets of parts or available separately at fixed prices stated.


Radio Exchange Co.

27 HARPUR STREET, BEDFORD
Phone 2367 Opposite Co-op. 9—5 p.m. 10—1 p.m. Sats.

WEYRAD

6-TRANSISTOR 2-WAVE SUPERHET RECEIVER MODIFICATIONS NOW AVAILABLE FOR 500 mW OUTPUT


ROD AERIAL—RA2W 6 in. long, 3/8 in. diameter, connections to tags on Coils. For 208pF tuning capacity. Complete with Car Aerial Coil	12/6
OSCILLATOR COIL—P50/1AC M.W. covered with 176pF tuning capacity, L.W. by extra padder	5/4
I.F. TRANSFORMERS 1st and 2nd Stage—P50/2CC	5/7 (2 required)
3rd Stage—P50/3CC	6/-
DRIVER TRANSFORMER—LFDT4	9/6
OUTPUT TRANSFORMER—OPT1	10/6
PRINTED CIRCUIT—PCA1	9/6

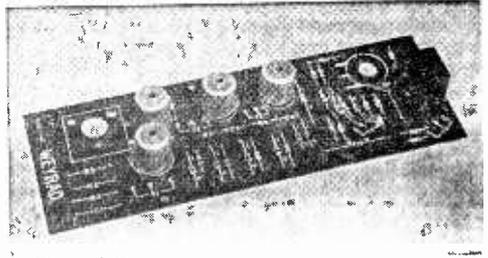

In response to many requests we have redesigned the output stages to give 500 mW and to enable a standard 3 ohm Speaker to be used. Full details of the simple changes are given on a separate leaflet available on receipt of stamp.

CONSTRUCTOR'S BOOKLET WITH FULL DETAILS	2/-
TRANSISTOR A.F. AMPLIFIER TYPE A.F.1—LOW IMPEDANCE INPUT, 3-TRANSISTOR, 500 mW OUTPUT, FULLY ASSEMBLED WITH VOLUME CONTROL	83/6

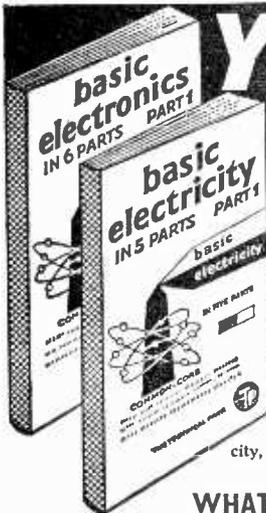WEYMOUTH RADIO MANUFACTURING CO., LTD.
REGENT FACTORY, SCHOOL STREET,
WEYMOUTH, DORSET



YOURS FREE FOR 7 DAYS

The New 'Picture-Book' way of learning **BASIC ELECTRICITY (5 VOLS.)** **BASIC ELECTRONICS (6 VOLS.)**

You'll find it easy to learn with this outstandingly successful new pictorial method—the essential facts are explained in the simplest language, one at a time; and each is illustrated by an accurate, cartoon-type drawing.

The books are based on the latest research into simplified learning techniques. This has proved that the **Pictorial Approach** to learning is the quickest and soundest way of gaining mastery over these subjects.

The series will be of exceptional value in training mechanics and technicians in Electricity, Radio and Electronics.

WHAT READERS SAY

"Learnt more in part 1 than the previous 2 years." L.M.J., Durham. "I am convinced that I am on to something really worth while." J.L.P., Fife. "Without doubt they are the easiest to follow books I have ever studied." W.J., Aylesbury. "Congratulations on a well planned easy to learn series." M.K., Horsham. "First class, I cannot praise them too highly." J.J., Taunton.

A TECHNICAL PRESS PUBLICATION

To Selray Book Co.

60 Hayes Hill, Hayes, Bromley, Kent

Please send me **Without Obligation to Purchase**, Basic Electricity/Basic Electronics on **7 Days Free Trial**. I will either return set, carriage paid in good condition within 8 days or send down payment of 10/- (Basic Electricity) followed by 6 fortnightly payments of 10/-. Down payment of 12/- (Basic Electronics) followed by 6 fortnightly payments of 12/-. Alternatively, I will send 63/- (Basic Electricity—5 parts), 75/- (Basic Electronics—6 parts) post free. This offer applies to United Kingdom only.

Tick against set required (only one set allowed on free trial).
BASIC ELECTRICITY **BASIC ELECTRONICS**
Signature _____
(If under 21, signature of parent or guardian)

BLOCK LETTERS BELOW
Name _____
FULL POSTAL Address _____

POST NOW FOR THIS OFFER !!

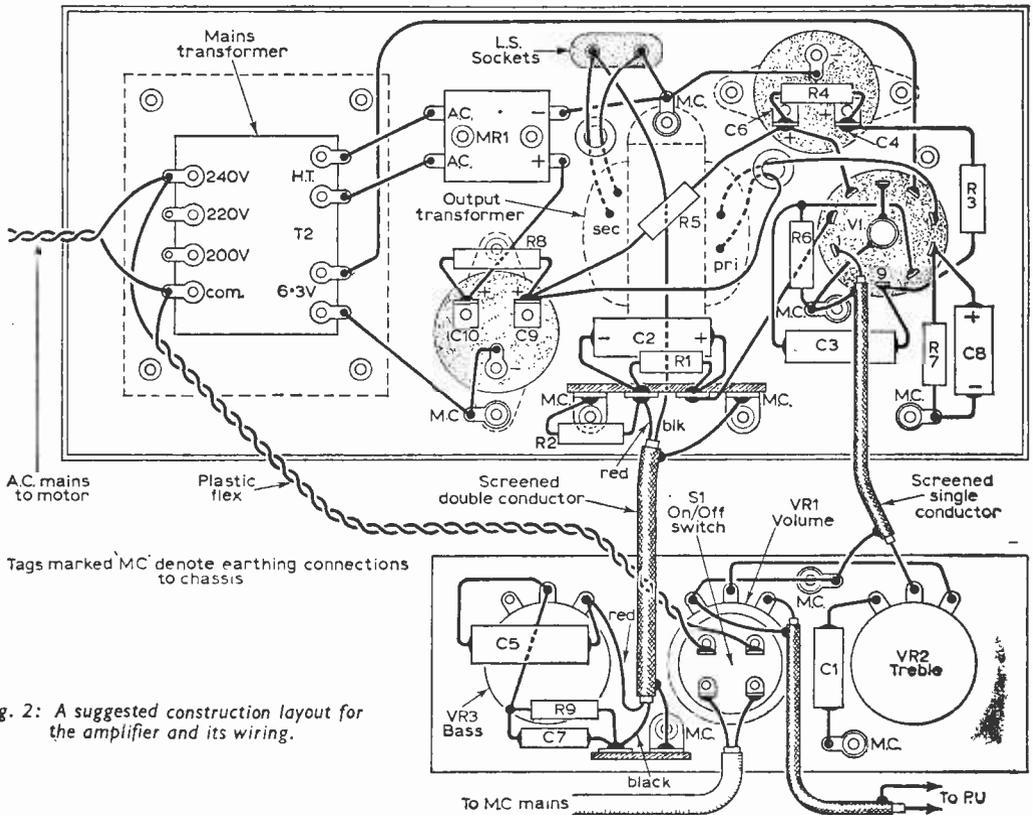


Fig. 2: A suggested construction layout for the amplifier and its wiring.

the shortest possible length of inner conductor exposed from the screened lead, while the screen itself must be bonded to chassis at the solder tag clamped underneath the valveholder securing nut. Further, the anode lead to pin 6 should be routed round the far side of the valveholder, as shown in Fig. 2.

Care must be taken to ensure that the inner conductors of the negative feedback and bass screened coupling are not inadvertently reversed during the construction. This can be avoided by the use of a screened double conductor in which the conductors are coloured red and black. Both screened cables must be bonded to chassis at their screens at both ends—at the amplifier and the control panel. Inefficient "earthing" will cause instability and a high hum level.

If the interconnecting cables are extra long the hum level may be higher than necessary, and in some cases it may be possible to minimise it by connecting a separate, fairly large diameter flexible conductor from a soldering tag on the amplifier (as close as possible to V1) to a similar tag on the control panel (as close as possible to the volume control). The screened outer conductor of a length of coaxial cable is highly suitable for this application, after first pulling out the polythene-covered inner conductor.

Component Layout

The layout of the components and the point-to-point wiring are given in detail in Fig. 2. The dimensions of the amplifier chassis will depend very much on the size of the mains transformer and output transformer, while the control panel can be any size to suit the application which the experimenter may have in mind. The controls on the latter, however, should be grouped as closely as possible together to avoid extra-long inter-connecting wires.

Both the chassis and the control panel can be made of 16s.w.g. aluminium sheet and, although the main amplifier can be built direct on to a flat piece of aluminium, for the sake of rigidity the sides of the chassis are best bent at right-angles to form a very shallow chassis with quarter-to-half-inch sides. In application, the chassis may then be mounted on pillars or wood strips.

In the prototype a through-chassis type of mains transformer was employed, as Fig. 2 shows, but there is no reason at all why a chassis-mounted type of transformer could not be used. Rubber grommets would then be employed to feed the transformer connections through the chassis.

The output transformer is mounted on the top

—continued on page 78

BOOKS REVIEWED

DISC RECORDING AND REPRODUCTION

By P. J. Guy. 256 pages, 5½ x 8½ ins. Price 42s.

RADIO RECEPTION

By H. Henderson. 256 pages, 5½ x 8½ ins. Price 42s.

Both published by Focal Press Ltd.

THE idea of a series of books, each one self contained, which dovetail to form a single authoritative work is an excellent one. Such a series is *The Technique of Sound Reproduction* which, edited by John Borwick, comprises six works covering the whole field of hi-fi sound recording and reproduction. Each book is written by a specialist and a uniform technical level has been aimed at throughout the series. Two books in this series are reviewed this month; we hope to review others in due course.

DISC RECORDING devotes the first six chapters (80 pages) to definitions of the nature of sound and to the theory and practice of modern disc recording from the microphone to the processing of records. The bulk of the book covers the component constituents of disc reproduction—stylus, pick-ups, motors, amplifiers, etc. Supplementary chapters deal with such aspects as stereo reproduction, hum and motor troubles, equalisers, response measurements, etc.

A valuable section is made up of five appendices which provide a wealth of design facts and formulae on such things as negative feedback, recording and reproducing equalisation, constant resistance faders, etc. This arrangement of grouping the mathematical material at the end of the book not only makes it a very useful reference section but permits the author to develop his main chapters without having to digress with formulae and calculations.

To sum up: For those who have progressed beyond the stage of simple amplifiers or wish to fill out their knowledge of the many factors involved in modern recording and reproduction of discs this will find a welcome place on the bookshelf.

RADIO RECEPTION is perhaps the "odd man out" in this series, for it is the only one not dealing exclusively in purely audio matters. Its inclusion, however, is justified in that radio tuners are needed to receive the high-quality v.h.f.-f.m. broadcasts.

The first three chapters deal with basic theory and your reviewer cannot quite decide whether this is to be applauded or condemned! There are so many books available covering these aspects in much greater detail that the space could well have been used to elaborate on more practical matters.

However, the chapters are very well written and will serve as a general "refresher" for those already conversant with basic theory. They also serve to point to the overall level at which the following chapters are aimed. These chapters deal with the r.f. amplifier, frequency changing, i.f. amplification, demodulation.

No audio circuitry is described, this being dealt with in a separate volume. These sections give data for both valve and transistor circuitry and practical values are given in many instances.

Alignment and Performance has just over five pages and, although it cannot be faulted as such, perhaps a more extensive and more practical treatment would have been beneficial. This is followed by a section on commercial receivers and tuners with circuit diagrams and descriptions. Here again some criticism: the circuit diagrams are obviously reprinted copies from manufacturers' literature and consequently they are all in different styles and in some cases are so small as to present a decided strain on the eyes. For the price of this book it would surely not be unreasonable to expect circuits to be redrawn to suit the space available. And one circuit has no component values shown at all!

Two good chapters follow—Receiving Aerials and Stereo Reception and Transmission. The book concludes with a short glossary and a bibliography.

A useful feature (both books) is the listing of main headings at the beginning of each chapter.—*D.C.*

SILICON CONTROLLED RECTIFIER DESIGNERS' HANDBOOK

Published by Westinghouse Electric Corp. Pennsylvania. 274 pages, 5½ in. x 8½ in. Price 16s.

THE purpose of this handbook is to familiarise circuit design engineers with the characteristics of npnp four-layer semiconductor devices such as the conventional silicon-controlled rectifier (SCR) and the gate-controlled switch (GCS).

Principles of operation, methods of construction, ratings and characteristics of these devices are described. In the large section dealing with applications of the SCR and the GSC the following are among the subjects treated to detailed analysis: switching circuits, d.c. to a.c., power inverters, ultrasonic generators, servo amplifiers, d.c. choppers and ignition systems.


The section Design Data, or "working tool" information, as it is aptly sub-titled, comprises 40-odd pages of tables and curves all relevant to SCR, GCS and other rectifier circuits—a valuable compilation of data from widely scattered sources.

The handbook includes specifications giving the mechanical, electrical and thermal characteristics of each Westinghouse type currently available.

Distributors of this handbook in the U.K. are the Westinghouse Brake and Signal Co. Ltd., 82 York Way, King's Cross, London, N.1.—*F.E.B.*

WIRELESS SET NO. 38 AFV

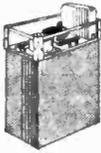A lightweight transmitter with transmitting range 5 to 10 miles and frequency coverage 7.4 to 9 Mc/s. Operates from 3 and 120 v. external dry batteries. Large, clearly numbered tuning control, with tuning lock. In good condition.



ONLY **39/6** Plus 7/6.
2 for £3.15.0. P. & P.

TAMPER PROOF CAR AERIAL

Wing mounting, cannot be extended without key. Chrome finish. Max. size fully extended 42in. Required clearance below wing 10in. PRICE **39/6** Post free.

BALANCED ARMATURE DLR HEADPHONES

Brand new and boxed. 10/6 per pair or 2 pairs for 17/6. P. & P. 1/6 per pair.

MINNETTE GRAMOPHONE AMPLIFIER


The "Minnette" is a compact Two Stage Amplifier designed primarily for use in small, portable self-contained Record Player Units. The circuit consists of a single triode-pentode valve, Mullard ECL82 valve is such that relatively small input at the grid of the triode section will produce maximum power from the pentode section. Thus the output derived from most crystal pick-ups is ample to produce maximum output from the valve. The power supply is conventional and utilises a Mullard ECL82 valve rectifier with adequate capacitive resistive filtering. Dimensions—Amplifier 6 inches by 3 inches by 4 inches. Front panel 6 1/2 inches by 1 1/2 inches. For operation on A.C. mains 250/250 volts. **£3.19.6** Post free.



The sensitivity of the valve, Mullard ECL82, is such that relatively small input at the grid of the triode section will produce maximum power from the pentode section. Thus the output derived from most crystal pick-ups is ample to produce maximum output from the valve. The power supply is conventional and utilises a Mullard ECL82 valve rectifier with adequate capacitive resistive filtering. Dimensions—Amplifier 6 inches by 3 inches by 4 inches. Front panel 6 1/2 inches by 1 1/2 inches. For operation on A.C. mains 250/250 volts. **£3.19.6** Post free.


HOOVER ROTARY TRANSFORMERS

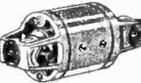11.5 input, 480 v output, at 65mA, from 9 v. input, approx. 250 v. output at 72mA. Price **9/11** P. & P. 3/6.




RF FIELD INDICATORS

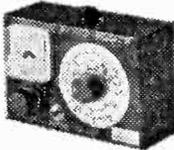Designed for checking the radiation from a transmitting antenna. The sensitivity can be controlled by adjustment of panel control, the antenna length, or by increasing distance from the radiator. Frequency range 1-25 Mc/s, 200mA. D.C. Complete with instruction book. **69/6**




4 TRANSISTOR PUSH-PULL RADIO AMPLIFIER 39/6

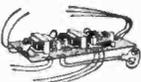Complete with 3 ohm output transformer working from a standard 9 volt battery. Output in excess of 200 MW.



NO. 19 TRANSMITTER RECEIVER

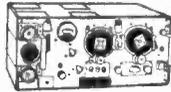

Trans./Receiver covers 2-8 Mc/s. (150-37 metres in two bands)—has an intercom, amplifier. Designed for 12 and 24 volts operation. Uses a 6-valve transmitter designed for voice and C.W. operation. Incorporates test and tuning meter in voltages, aerial loading and current tests. Panel controls, frequency tuning, P.A. tuning, gain control, MCW, CW, R/T switch. Hit-tone netting. OB-on quench aerial. AVC, LT-BT drives test. P. & P. 5/- 2 for £4.10.0. ONLY **47/6** Post free.

Canadian Model, 10/- each, extra. Instruction Handbook, 8/6. Whip Aerials 8 (t. 0in.), 7/6. P. & P. 2/6. 5ft. 0in., 4/- P. & P. 2/6. Control Box Single Type 4711, P. & P. 1/6. Double Type 6711, P. & P. 2/6. 19 Set Receiver Power Unit Kit, 200-250 v. A/C to 275 v. D.C. Choke smoothed 12 v. L.T. Complete with connector to set (state which required 6 or 12 pin), 39/6, P. & P. 6/-.

TRANSISTOR SALE

- Mullard OC44 (P. & P. 3d.)..... 3/11
- Mullard OC46 (P. & P. 3d.)..... 3/11
- Mullard OC71 (P. & P. 3d.)..... 2/11
- OA79 (P. & P. 8d.)..... 1/11
- Ediswan XD202 Germanium diodes (P. & P. 8d.)..... 2/11
- Transistor Holder, 3-pin, (P. & P. 3d.) 11d. each.

MICRO ALLOY TRANSISTORS

- Mat 100 7/9
- Mat 101 8/8
- Mat 120 7/9
- VHF Transistor, A DTF140 15/-

Above MAT's postage paid. Ferrite Smb Aerials, suitable for transistor sets..... 3/- P. & P. 6d.

TEST SET TYPE 46

Will radiate a continuous note. Range 1,250 Mc/s-23,000 Kc/s (12-24 Metres). 5 switched bands, contains V121 valve and has a precision slow motion tuning unit enclosed in grey metal case, rod aerial base on side, good condition. Power requirement, 2 v., 90-120 v. Battery space provided. **35/-** P. & P. 5/-.



TRANSISTOR SIGNAL INJECTOR

Produces an audio signal rich in harmonics through the R.F. range. Ideal for fault testing in Radio circuits. Push button operation. Powered by four pen light cells. No bigger than a small hand torch. Made by Eagle products. Just the job for the service man. **39/6** Post free.

1155 INSTRUCTION HANDBOOK


3/11. P. & P. 3d.

HANDY METAL COMPONENT CASES

Hinged lid. Size 6 1/2 x 6 x 2in. Padded inside many uses. 2/6 each. 2 for 4/6. P. & P. 1/6.

SUPERHET RADIO CHASSIS

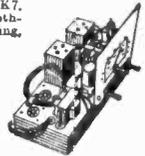These well-made chassis were made for the Government for Forces entertainment with 6K8, 6K7, 6Q7, 6V6. Choke smoothing slow-motion tuning, metres. Complete with 6v power pack.



BRAND NEW. Cabinet with 8in. speaker to fit. Complete in maker's cartons. **£3.19.11** P. & P. 3/-.

FOSTER MIKE (Dynamic type)

Output impedance 600 Ω, 10 Ω, 50 K Ω, ± 30%. Effective output level: 56 dB (60 H Ω) ± 3 dB at 1,000 c/s (0 dB=1 v/p bar). Response: 100-1,200 c/s ± 5 dB non directional. Attractive plastic and chrome finish. All necessary accessories for adaptation as band, table or suspended mike, 50/- P. & P. of PVC cable. 1/-.

PLANET CRYSTAL MICROPHONE

List Price one 35/-. Beautifully made in strong plastic case with approx. 5ft. of cable and jack plug. Response 60-18,000 c/s. **11/6** P. & P. 2/-.



SPECIAL OFFER WHILE STOCKS LAST

4-speed Record Player deck B&E. UA14 With latest HI-FI turnover head. ONLY **£5.19.6** P. & P. 6/-.

LEAD ACID ACCUMULATORS

(Unspillable) 2 volts 16 A.H. Brand new. Size 4 x 7 x 2in. 4/11 each. 3 for 12/6. P. & P. 3/- per cell.



TODAY'S SUPREME VALUE IN AMPLIFIERS. BRITISH MADE GORLER TYPE AMPLIFIER

G812005 All-transistor subminiature quality amplifier. 60-18,000 c/s ± 3 dB, 70-14,000 c/s ± 1 dB, 5mV for 1 watt out at 6 v. Built and tested, 92/6.

LUXEMBOURG EXPANDING AERIALS

Complete with instructions. 3/6. P. & P. 7d.


PICK-UP ARM

COMPLETE WITH LATEST Acco/Hi-Fi turnover cartridge. 25/-. P. & P. 1/-.

TEST OSCILLATOR TYPE 4

Frequency range 20 to 100 Mc/s. in two bands selected by plugging in the appropriate loop aerial, two of which are supplied with the set. Operates from a 6 v. D.C. supply which is converted by an internal vibrator pack to 280 v. and 6 v. L.T. The unit is in good condition, and a clear circuit drawing is mounted on the interior of the rear panel. The equipment contains many useful components, e.g. twin gang tuning, condenser, valves, transformer, chokes, resistors, etc. A neat compact unit in grey enameled case 1 1/2 x 7 x 6 1/2. **39/6** 5/- with carrying handle.

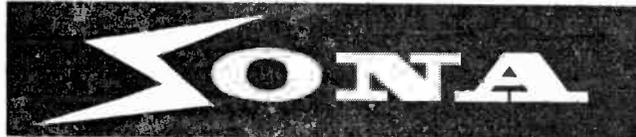TERMS:
CASH WITH ORDER
5/- EXTRA ON C.O.D.
ORDERS
No C.O.D. under 30/-.



**TRADE SUPPLIED
ORDERS FROM
ABROAD WELCOME**

SONA ELECTRONIC CO. (Dept. PW5), BRIGGATE HSE., 13 ALBION PL., LEEDS

"THE CONSTRUCTOR'S PARADISE"
BEAR HUDSON LTD.

63 GOLDHAWK RD, SHEPHERD'S BUSH, LONDON, W.12 PHONE: SHE 2581
 Now open at 11 JERDAN PLACE, FULHAM, LONDON, S.W.6. Phone: FUL 3405

MICROPHONE OPPORTUNITIES

"Planet" SUPER X-TAL MIKE

Fantastic value. Beautifully made modern styled crystal mike in strong plastic housing. With approx. 5ft. sheathed cable and miniature jack plug. Response 50 to 13,000 c/s. High impedance. Guaranteed. List price 30/-.



SPECIAL PRICE 12/6 LIST 30/-

TSL "AUDIO HEART"

A VERSATILE HI-FI TRANSISTOR AMP.

Uses 2 x 81D transistors with 2 x OC81 in push pull to give full watt output at 3-5 ohms. Input sensitivity 5 to 10mV for 1 w. out. Operating voltage—6V. 8" x 2 1/2" x 1 1/2". Response 10-10,000 c/s. ± 3 dB. This superb amplifier is characterised by exceptional stability, providing full output at up to 112°F. Available ready built or for building yourself. Guaranteed. With transistors, transformers, etc., etc. and instructions. **52/6**
 BUILT IT FOR Ready built and tested **59/6**


TSL Mk. 2 THREE CHANNEL MIXER

The most popular low-price mixer ever made! Can be used with any tape recorder. Complete with colour-coded plugs, modern controls. Gold hammer finished steel case. **47/6**



HLP.2 CROSSOVER NETWORK

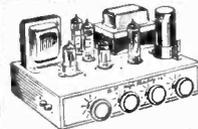For use between bass and treble speaker units. Ensures smooth response over entire audio spectrum and is essential to perfect hi-fi reproduction. **47/6**



A real break-through in hi-fi value! This superb amplifier designed by Dr. W. J. May incorporates valuable features including two high gain inputs, each with its own volume control to permit mixing! Multiple neg. feedback loops can be varied. Robust design using quality components means dependability at all times. Frequency response—20-25,000 c/s. ± 2dB. Separate bass and treble cut and lift controls. Output ± 3 or 15 ohms. With punched chassis, elegant escutcheon plate, valves and instructions. **FANTASTIC VALUE AT THE PRICE!**
 Complete kit of parts as described. Fitting metal cover with handle. **32/8**. **£9.90** Built and tested **£11.11.0**

COMPONENTS - HI-FI - BOOKS - SERVICE

24-HOUR MAIL ORDER SERVICE with all goods guaranteed.
 ★ FREE POSTAGE on orders over 20/-; add 1/- postage if under.
 ★ LOWEST PRICES FROM BULK PURCHASING AND MANUFACTURING

BERNARDS BOOKS FOR TRANSISTOR CONSTRUCTORS

- 183** How to receive foreign TV programmes on your TV set using simple circuits using Modules. **5/-** Post free
 - 184** Tested Transistor Circuits using Modules. **2/6** Post free
 - 185** Tested Shortwave Receiver Circuit using MATs. **5/-** Post free
 - 186** Tested Superhet Shortwave and Communication Receiver Circuits using MATs. **6/-** Post free
- Send 6d. for full catalogue of Bernards Radio Books. We stock the Parts You Need for the Circuits too!

SINCLAIR MICRO-6

The world's smallest and most amazing radio. All parts to build, inc. earpiece and instructions come to **59/6**

We supply all Sinclair designs

MAKE YOUR CRYSTAL P.U. REAL HI-FI WITH THE TSL CONSTANT VELOCITY EQUALISER



This remarkable new TSL development in quality almost as good as the finest professional magnetic pick-ups to be obtained from crystal or ceramic types. With it, even cheap record players become first-class instruments. With good equipment results are astonishing. Ideal for B.S.R., Colliari, Garrani and Acos. With plugs for mono or stereo. 3 years' guarantee. Ready for use. **30/-** Post Free
 Thousands sold.

TRANSISTOR OPPORTUNITIES

OC.71—special offer, 3/9; OC.35, 5/6; OC.44, 6/-; OC.169, 8/-; MAT 100 or 120, 7/9; MAT 101 or 121, 8/6; ADT.140 with 500 mc/s cut-off, 15/-.

Orders by post to BEAR HUDSON LTD., Dept. PW5, 63 Goldhawk Rd., London, W.12

This is a page from our Catalogue, LTD.
 If you think that the other 199 pages would interest you, send Coupon below, with 4/- P.O.

continued

Price £ s. d.

fully transistorised signal generator (size only 6 1/2 in. x 4 1/2 in.) (weight under 2 lb.). Frequency range 200 kc/s-220 Mc/s. **9 10 0**
 Battery (extra) **2 3**

Maker: NOMBREX. Resistance Capacity Bridge

Cat. No. Maker's No. Description

TG18 62 RANGES 1. 1 ohm-10K ohms 2. 100 ohms-1 Megohm. 3. 10K ohms-100 Megohms. 4. 1pF-0.1uF. 5. 100pF-1uF. 1. 0.01uF-100uF.

ACCURACY. All the ranges employ close tolerance internal standards, permitting measurement to an accuracy of 2 1/2% or better at mid-scale.

POWER FACTOR. This control operates on the high range, permitting power factor

est cap meas
 LEAKAGE provi
 tors of
 SIZE.

Maker: NOMBREX.

Cat. No. Maker's No. Description

TG20 63 RANG
 OUT
 OUT
 sq
 it
 1
 Dis
 Ac

Please write your name and address in block capitals


NAME _____

ADDRESS _____

HOME RADIO LTD., DEPT. PW, 187 LONDON ROAD, MITCHAM.

A Mains Distribution Panel

BY G. R. SIMPSON

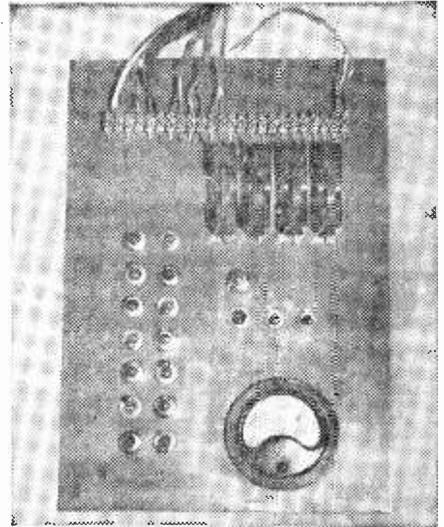

THE circuit diagram (Fig. 1) shows a simple mains distribution panel consisting of one fused mains input and three switched mains outputs with a neon indicator to signify that the board is alive, and a 0-300V a.c. voltmeter.

The purpose of the panel is to accept the current from one mains input and to redistribute it


through switches to the three output terminals. More output terminals can be built in if desired.

Not only does the panel eliminate the need for double-adaptors, but enhances the appearance of the work-room layout and provides a central panel from where any piece of equipment can easily be switched on.

The chassis construction of the mains distribution panel is very simple. A small biscuit tin could be used, or alternatively, a laminated plastic on

plywood face, with 2in. x 1in. wood for the edges faced with laminated plastic and a plywood base-board with four small rubber feet.

A d.p.s.t. switch is used for the mains input while the output switches are s.p.s.t. The input and output terminals are provided by a row of 5A block connectors mounted on the surface of the panel. This row of connectors should be covered by means of a strip of plastic material to prevent the possibility of the live terminals being touched by hand. The fuse can either be the Sylok type or the flush panel mounting, and should be rated in such a way that if a short should occur, the panel fuse would be blown and not the house fuse.

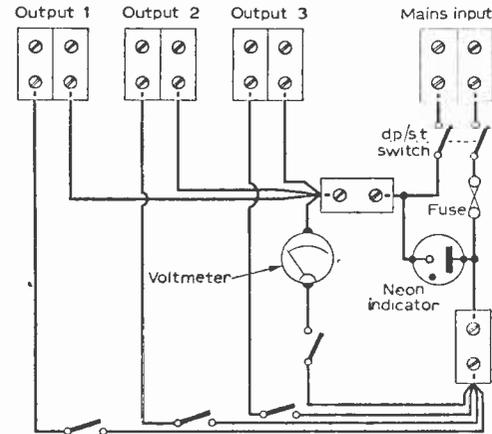

through switches to the three output terminals. More output terminals can be built in if desired.

Not only does the panel eliminate the need for double-adaptors, but enhances the appearance of the work-room layout and provides a central panel from where any piece of equipment can easily be switched on.

The chassis construction of the mains distribution panel is very simple. A small biscuit tin could be used, or alternatively, a laminated plastic on


Fig. 1: The simple circuit of the unit.

plywood face, with 2in. x 1in. wood for the edges faced with laminated plastic and a plywood base-board with four small rubber feet.

A d.p.s.t. switch is used for the mains input while the output switches are s.p.s.t. The input and output terminals are provided by a row of 5A block connectors mounted on the surface of the panel. This row of connectors should be covered by means of a strip of plastic material to prevent the possibility of the live terminals being touched by hand. The fuse can either be the Sylok type or the flush panel mounting, and should be rated in such a way that if a short should occur, the panel fuse would be blown and not the house fuse.

JOIN THE PRACTICAL GROUP

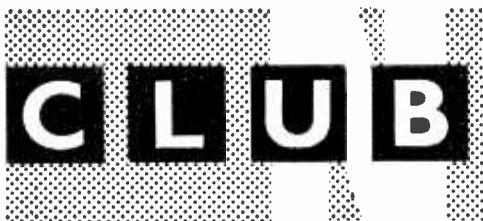- PRACTICAL TELEVISION 2/-
Every Month
- PRACTICAL MOTORIST 1/9
Every Month
- PRACTICAL HOUSEHOLDER 1/6
Every Month



ACTON, BRENTFORD AND CHISWICK RADIO CLUB
 Hon. Sec.: G3GEH, 188 Gunnersbury Avenue, Acton, London, W.3.

Any local radio enthusiasts interested in joining this society are invited to attend the monthly meetings which are held at the A.E.U. Club, 66 High Road, Chiswick.

When the Club assembles for its next meeting—on 14th April—members will be carrying out some comparison tests on receivers.

BRADFORD RADIO SOCIETY

Hon. Sec.: E. G. Barker, G3OTO, 63 Woodcot Avenue, Baildon, Shipley, Yorkshire.

Society activities for March began with a junk sale on the 10th. A fortnight later however, came the more formal occasion of the Annual General Meeting, held on the 24th.

CLIFTON AMATEUR RADIO SOCIETY

Hon. Sec.: J. Rose, G3OGE, 63 Broomfield Road, Beckenham, Kent.

On 6th March members were entertained by G3IEQ, who was talking about his portable operation from Scotland.

Later in the month a number of members made a visit to Crystal Palace Amateur Radio Society in the first round of the inter-club quiz. On 3rd April it was the turn of Clifton to play hosts to Crystal Palace members, in the return half of the match.

FLINTSHIRE RADIO SOCIETY

Hon. Sec.: A. Antley, Fairholme, Fairfield Avenue, Rhyl, Flintshire.

After the usual practice period of slow Morse, the March meeting of this Society—held on the 31st—continued with the main part of the evening's programme which proceeded under the title "Animal, Vegetable or Mineral".

MELTON MOWBRAY AMATEUR RADIO SOCIETY

Hon. Sec.: D. W. Lilley, G3DFD, 23 Melton Road, Asfordby Hill, Melton Mowbray, Leicestershire.

At the meeting on 26th March, junior members of the Society brought along problems they had met as beginners to amateur radio, for discussion amongst other members at this open evening.

LIVERPOOL AND DISTRICT AMATEUR RADIO SOCIETY

Hon. Sec.: H. James, G3MCN, 448 East Prescott Road, Knotty Ash, Liverpool 14.

The Society's annual Hamfest was held on 7th March. This took the form of a dinner and dance and proved to be a memorable occasion for all members who attended. Three days after this members met to hold a Hamfest "post mortem".

The next two meetings were held on the 17th and 24th of the month and were respectively, a film show and a junk sale. Activities for the month ended with members taking part in a two-team quiz on the 31st.

NORTHERN HEIGHTS AMATEUR RADIO SOCIETY

Hon. Sec.: A. Robinson, G3MDW, Candy Cabin, Ogdon, Halifax, Yorkshire.

On 18th March, a group of members visited the Tape Recorder Centre in Halifax, where they were entertained by an interesting demonstration of hi-fi equipment.

A ragchew began the programme for the new month on 1st April.

READING AMATEUR RADIO CLUB

Hon. Sec.: R. G. Nash, G3EJA, "Peacehaven", 9 Holybrook Road, Reading, Berkshire.

The only meeting for March was held on the 28th and was devoted to gear for mobile operation.

SALOP AMATEUR RADIO SOCIETY

Hon. Sec.: K. E. Jones, G3RRN, Greystones, Shrewsbury Road, Church Stretton, Shropshire.

The lecturer at the meeting on 12th March was the Society's secretary, Dr. K. E. Jones, whose subject that evening was "Man, Medicine and Electrons".

SCARBOROUGH AMATEUR RADIO SOCIETY

Hon. Sec.: P. B. Briscoe, G8KU, "Roseacre", Irton, Scarborough, Yorkshire.

The full programme of events for March included a film show given on the 12th. This was followed a week later by a talk concerning simple formulae for the Radio Amateur's Examination.

At the final meeting for March, on the 26th, members were invited to deliver a five-minute address on any radio subject of their choice.

April began with a surplus sale on the 2nd.

SOUTH BIRMINGHAM RADIO SOCIETY

Hon. Sec.: T. W. Legg, Flat 3, 80 Alcester Road, Birmingham 23.

The March meeting of this Society was held on the 19th, when members who attended heard a tape recorded lecture.

SPEN VALLEY AMATEUR RADIO SOCIETY

Hon. Sec.: N. Pride, 100 Raikes Lane, Birstall, Leeds.

Members who attended the meeting on 7th March heard a lecture entitled "Communication Satellites". This was followed at the next meeting by a talk on "Silicon Semiconductors" given on 18th March.

STOCKPORT RADIO SOCIETY

Hon. Sec.: R. R. Diamond, G3SFN, 102 Chatsworth Road, Hazel Grove, Cheshire.

A recent innovation at meetings of this Society is the opportunity given to all junior members to discuss with a senior member, any questions or problems they have concerning their hobby. These discussions are held for 15 minutes before each meeting begins.

The highlight of the programme for March was the Ladies' Evening held on the 11th. At this event, members brought along their Y.L.'s and X.Y.L.'s for an evening's entertainment which had been organised for them, and for the opportunity to meet other members.

One of the oldest members of this Society, G2ARX, announced recently that he would present to the Society a Cup, to be awarded annually to the winner of an equipment construction competition.

STOURBRIDGE AND DISTRICT AMATEUR RADIO SOCIETY

Hon. Sec.: R. A. G. MacIntosh, 50 Field Lane, Oldswinford, Stourbridge, Worcestershire.

The Annual General Meeting of this Society was held on 10th March, when official Society business was reviewed.

UNIVERSITY OF KEELE RADIO SOCIETY

V. J. Reynolds, G3COY, 90 Prince's Road, Hartshill, Stoke-on-Trent, Staffordshire.

This Society is currently engaged with plans for its participation in the Midlands Mobile Rally, to be held at Trentham Gardens on 19th April. On this date, the Society will perform the duty of an out-station on the talk-in network on 160m. During the Rally the station will be on the air under call sign G3COY on 1960kc/s.

WEST KENT AMATEUR RADIO SOCIETY

R. Trevitt, 28 Dales Avenue, Tunbridge Wells, Kent.

Because of the Easter holiday, only one meeting was held during March, this being on the 13th. At this meeting members saw a demonstration of various pieces of test equipment.

MIDLAND MOBILE RALLY

This year's rally is to be held on 19th April at Trentham Gardens, Trentham, Nr. Stoke-on-Trent, Staffordshire. Talk-in stations will be provided on 160m, 80m and 2m.

Organised jointly by the Midland Amateur Radio Society and the Stoke-on-Trent Radio Society, this event should prove to be an enjoyable occasion for all those who attend. In addition to the rally of mobiles from all over the country, an exhibition of radio society and trade stands will be staged, and of special interest will be a display of amateur television.


In the grounds, the R.A.F. mountain rescue unit will give demonstrations and there will be water skiing on the lake.

TOP QUALITY—LOW COST  **AMATEUR RADIO EQUIPMENT**

BUILD YOUR SHORT WAVE LISTENING STATION WITH CODAR-KITS.
CR 66 COMMUNICATIONS RECEIVER

THE FINEST SUPERHET KIT EVER OFFERED

Hundreds of testimonials (can be seen at our offices) prove this highly sensitive top quality receiver to be the finest value ever offered. No technical knowledge or equipment is required. Assembled Coil Unit and I.F. Transformers are factory aligned. Frequency range 540 Kc/s to 30 Mc/s in 4 bandswitched ranges. Separate Electrical Bandspeed, Regenerative I.F. stage for maximum gain and B.F.O. Panel aerial trimmer, AVC, Standby, Speaker switches. 3 watts output for 2-3 ohm external speaker. Valve line-up: ECH81, EBF89, ECC81, EL84, EZ80, EM84. Tuning indicator. Modern styling in Silver Grey Cabinet 16 x 6½ x 8½ in.

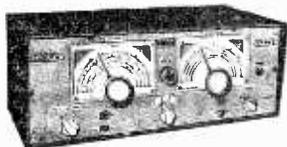

- Complete Kit, 17-page Instruction Manual ... £19. 2.6
- Ready Built..... £21.12.6
- "S" Meter Model Kit £21. 2.6
- Ready Built..... £23.15.0

Carriage on all models 6/- . H.P. Terms available on request.

★ **P.R. 30 R.F. PRESELECTOR** ★

Frequency range 1.5-30 Mc/s. Substantially improves the performance of any superhet receiver

G4HZ writes . . . I am delighted with it, it improves my Eddystone 640 in all respects. The difference with the Pre-selector is fantastic, a weak signal on 15 metres about S2 changed to S8. On the L.F. Bands, unwanted noise and mush is cut out.




G3RIA writes . . . The results in conjunction with my Eddystone 888 are amazing. Signals are twice as strong with much higher signal/noise ratio. A first-class product well worth the money. The P.R.30 uses EF183 Frame Grid R.F. Amplifier and provides up to 20 dB gain. Features include vernier tuning, gain control, selector switch for either dipole or end fed antenna. External power supplies (obtainable from Rx). Smart styling in grey and black. Complete, READY BUILT, with all plugs, cables.

Now available in two models.
 P.R.30 for external power supplies 180-250 volts H.T., 6.3 volts 3 amp. L.T. (obtainable from receiver). **£4.17.6** Carr. 3/6.

P.R.30X self powered with internal power supply for 200-250 volt A.C. Will provide 200 volts up to 25 mA and 6.3 volts 1 amp. for other accessories. **£7.2.0** Carr. 3/6.

CODAR-KIT CR 45 MAINS T.R.F. SHORT WAVE RECEIVER

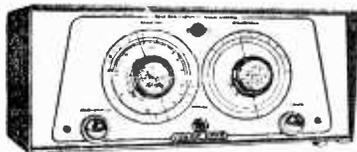World-wide short wave reception, North-South America, India, Russia, Far East, Australia, amateurs, shipping, etc.



- ★ Separate electrical bandspeed.
- ★ Three slow motion vernier drives.
- ★ Low loss polystyrene plug-in coils, factory aligned.
- ★ Dials calibrated in frequencies and degrees.
- ★ Power output 3 watts for 2/3 ohm speaker.
- ★ Valve line-up: ECC81/EL84/EZ80.
- ★ Front Panel Silver and Black, control knobs Grey.
- ★ Provision for panel phone jack.

Superb modern styling and Top quality components throughout. Complete CR 45 CODAR-KIT, with valves and 3 Coils, 10-28, 25-75, 60-176 metres. Instruction Manual 11 pages, less Cabinet.....

£7.5.0 Carr. 4/6

CR 45 Cabinet Silver Grey 12 x 5½ x 7in. with sliding door for easy coil changing and detachable loured rear panel **28/6**
 Instruction Manual only 4/- post free. Extra coils 4/9 each.

★ CAN BE SUPPLIED READY BUILT PRICE ON REQUEST.

★ **NOW AVAILABLE** ★
RQ 10 "Q" MULTIPLIER/FILTER

The new CODAR RQ 10 "Q" Multiplier can be used with any superhet receiver employing an I.F. between 450 and 470 Kc/s. It provides a considerable increase in selectivity for either peaking or rejecting a signal on AM, CW or SSB. Both PEAK and NULL functions are tunable over the receiver I.F. passband. Model RQ 10 for external power supplies 180-250 volts at 5 Ma, 6.3 volts .3 amp (obtainable from receiver). £6.15.0. Carr. 3/-. Model RQ 10X self-powered version for 200-250 volts AC. This model has accessory socket to provide up to 25Ma at 200 volts H.T. and 6.3 volts 1 amp AC for other accessories. £8.0.0. Carr. 3/6

★ Both models are ready built with all cables, instructions.
CODAR AERIAL KIT. 50ft. of high quality stranded copper aerial wire. 4 porcelain insulators. Instruction leaflets giving details of 5 simple aerial systems suitable for general coverage or the Short Wave Listener. 8/6 post free.

CODAR-COIL AIR SPACED COILS. A range of over 45 different air wound coils from ½ to 3in. diameter, suitable for all applications, receivers, transmitters, aerial tuner units, etc. Full data on request.

Coming shortly. Miniature low power Transmitter, 10 watts for 160/80 metres. Cat. No. A.T.5.

★ **THE SUPER CLIPPER** ★

- ★ Peak Performance short wave battery receiver. **88/6**
- ★ Large precision dial, dual slow motion drives.
- ★ Bandspeed on all Bands.
- ★ High gain valve/transistor hybrid circuit.
- ★ 2 Mullard transistor amplifiers, pre-assembled and tested.
- ★ Low loss polystyrene plug-in coils, factory aligned.
- ★ Batteries last months.



Easy to assemble, this famous Short Wave Receiver brings a new world of listening pleasure to your finger tips. Complete SUPER-CLIPPER CODAR-KIT, valve, transistors, 2 Coils 20-60, 55-180 metres. Instruction Manual 7 pages, 88/6, carr. 2/6. Front Panel Silver Grey, 10 x 7½in. 6/9 extra if required. Extra Coils 4/9 each.

CODAR-KITS are famous for PEAK PERFORMANCE, EASY TO FOLLOW INSTRUCTIONS, CLEAR PICTORIAL DIAGRAMS. Some of the Top Quality names who supply material for CODAR-KITS . . . MULLARD, BRIMAR, JACKSON, DENCO, ELECTRONIQUES, THORN, A.E.I. etc. etc. . . only the best is good enough for the high CODAR standards which make complete success certain. 6d. in stamps brings illustrated leaflets.

CODAR RADIO COMPANY

BANK HOUSE, SOUTHWICK SQUARE, SOUTHWICK, SUSSEX


G31RE

CANADA: CODAR RADIO OF CANADA, TWEED, ONT.

G3HGQ

LATEST HIGH QUALITY COMPONENTS FROM THE MAXI-Q RANGE

TESTED AND TRIED OVER 5 FREQUENCY RANGES

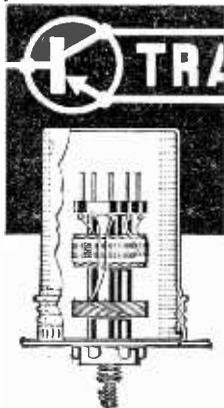

TRANSISTOR TUNING COILS

- Coils for transistor superhets or converters, with or without an R.F. stage and using 465 Kc/s or 1.6 Mc/s I.F.
- ★ Noval B9A Based for Plug-in application—Screw threaded for Chassis application.
 - ★ Formers moulded in low-loss polystyrene for best results.
 - ★ Each coil is packed in an aluminium container which may be used as a screening can.
 - ★ Brass threaded adjustable iron-dust cores.

The following colour code identifies the coils:
BLUE — Aerial coil with base input winding.
YELLOW — Interstage R.F. coil with couplings.
RED — Oscillator coil for 465 Kc/s I.F.
WHITE — Oscillator coil for 1.6 Mc/s I.F.

PRICE 4/9d. each

Coverages: Range 1T—15.4 Mc/s; 2T—515/1.545 Mc/s; 3T—1.67/5.3 Mc/s; 4T—5/15 Mc/s; 5T—10.5/31.5 Mc/s.

Full technical details now included in Technical Bulletin DTB.4—1/6d.

- IFT.13 Miniature 465 Kc/s. I.F. Transformer..... 7/6d. each
- IFT.14 Miniature 465 Kc/s. Last I.F. Transformer 7/6d. each
- IFT.16 Miniature 1.6 Mc/s. I.F. Transformer 6/6d. each
- IFT.17 Miniature 1.6 Mc/s. Last I.F. Transformer 6/6d. each

GENERAL CATALOGUE covering full range of components, send 1/6d. in stamps
PLEASE SEND S.A.E. WITH ALL OTHER ENQUIRIES.

DENCO (CLACTON) LTD. (DEPT. P.W.), 357/9 Old Road, Clacton-on-Sea Essex



TRANSISTORS

AD140 25/-	GET115 6/9	OC41 8/-	OC77 12/-
AF102 27/6	GET114 6/8	OA81 2/-	OC42 6/-
AF114 11/-	GET115 9/6	OA85 3/-	OC43 12/6
AF115 10/6	GET116 17/-	OA86 4/-	OC44 5/-
AF116 5/-	GET120 80/-	OA90 3/-	OC45 5/-
AF117 9/6	OA5 6/-	OA91 3/-	OC46 27/6
AF118 20/-	OA8 5/8	OA95 3/6	OC47 30/-
AF124 11/-	OA7 6/-	OA200 5/-	OC57 16/-
AF125 10/6	OA10 8/-	OA202 6/6	OC58 17/6
AF126 10/6	OA70 3/-	OA210 9/6	OC59 18/6
AF127 9/6	OA73 3/-	OC16W 35/-	OC60 17/6
		OC19 25/-	OC65 22/6
		OC22 25/-	OC66 25/-
		OC23 33/6	OC70 6/6
		OC24 29/-	OC71 4/3
		OC25 12/-	OC72 5/6
		OC26 25/-	2xOC73
		OC28 24/6	OC201 29/-
		OC29 25/6	OC202 24/6
		OC30 40/-	OC203 13/-
		OC35 12/-	OC204 18/-
		OC38 21/6	OC205 30/-
		OC78 8/6	OC206 30/-

SETS OF TRANSISTORS

Set No. 1. Comprising OC41, 2 x OC43, OC81 Driver, matched pair OC81, 20/-
 Set No. 2. Comprising OC81 Driver, matched pair OC81, 10/-.

GRAMOPHONE UNITS

BSR TU12 unit, with Mono TCSH cartridge.....	£3.19.6
BSR GU7 unit, with TC8M and TCSH cartridge, Mono.....	£4.15.0
BSRGU7 unit, with TC8S cartridge, Stereo.....	£5.5.0
Garrard Autoilm, automatic, with GC8 Mono cartridge.....	£7.15.0
Garrard Autoilm, automatic, with EV26 Stereo cartridge.....	£8.10.0
Garrard Autoilm, de luxe, with GC8 Mono cartridge.....	£11.5.0
Garrard Autoilm de luxe, with EV26 Stereo cartridge.....	£12.0.0
BSR Monarch UA14, with TC8 Mono cartridge.....	£6.6.0
BSR Monarch UA14, with TC8S Stereo cartridge.....	£7.7.0
BSR Monarch UA16, with TC8 Mono cartridge.....	£6.19.6
BSR Monarch UA16, with TC8S Stereo cartridge.....	£7.19.6

CATALOGUE

Our 1964 56-page Catalogue is now available. Please send 1/- in stamps for your copy. Trade catalogue also available, for which please attach your business letter heading. Catalogue supplied FREE with all orders received.

TERMS

Cash with Order or C.O.D. Postage and Packing Charges extra. Single valves 9d., Minimum Parcel Post charges 2/-. Please include sufficient postage with your order. Minimum C.O.D. fees and postage 3/6. These Postal Rates apply to U.K. only. For full terms of business see inside cover of catalogue. Personal shoppers 9 am to 5 p.m. Mon. to Friday, Saturday 10 a.m. to 1 p.m.

ALPHA RADIO SUPPLY CO.

103 LEEDS TERRACE, WINTOUN STREET, LEEDS 7

TV EXTRAS AERIALS 25/-
 Indoor combined. Complete with 12ft. co-ax. and plug. P. & P. 2/6.



17" £11.10.0

14" £7.10.0

12 months' Full Written Guarantee

Channels for all areas.

Demonstrations daily in our Shop. Personal collection advised.

Carr. 14in., 20/-, 17in., 30/-.

AERIALS 35/6
 Loft Combined BBC / ITA with 3 elements universal fitting. P. & P. 3/6.
 Co-ax. Cable 6d. per yd. Plugs 1/3 ea
LEGS—Complete with fittings for any set. 35/6.

VALVES 9d. each
 1,000's available. P. & P. on 1-4 6d.,

B.B.C. 2/625 AERIALS
 U.H.F. / COLOUR. 6 elements. Famous manufacturer. New and boxed. Instructions enclosed

TELEPHONE 15/6 HANDSET
 pair G.P.O. standard pattern. House to Workshop, garage, inter-office, etc. Works off any small battery. P. & P. 4/6.

SPEAKERS 7/9 EACH.
 6in. 8in. 7in. x 4in. Money-back guaranteed. Enquire for other sizes. Ex. mfd. salvage. P.P. 2/3.

37/6
5 ELEMENT add on **13/6**
 P.P. 2/6 either type.

REGUNNED TUBES 21 in. 99/6
 Guaranteed 1 Year Ins. and Carr. 10/6. Add 10/- refundable on OLD TUBE (110° Tubes in stock.)

17 in. 79/6
15, 14, 12 in. 59/6
EX-MAINTENANCE TESTED TUBES
 Satisfaction Guaranteed. 36/24, 14KP4, 141, 121, 31/74, and others. Carr. 5/-.



Phone 11, Ford 60017/2/3

DUKE & CO. (LONDON) LTD.
 621/3 Romford Road, Manor Park, E.12
 Liverpool St.—Manor Pk.—10 mins. Stamp For Free List

T N


rade ews

Hi-Fi Tuner

THE new a.m./f.m. tuner, just released by

Grundig Limited, employs twelve valves and fifteen semi-conductors in its circuit, providing a.m. coverage from 510kc/s to 1,620kc/s and f.m. coverage from 87Mc/s to 104Mc/s. The circuit features switchable automatic frequency control and a stereo decoder stage on f.m., and switchable bandwidth selection on a.m. Several other worthwhile facilities are provided.

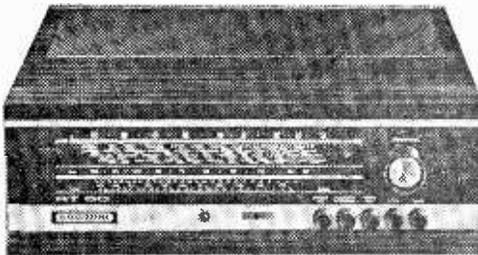Finished in a smart teak case, the tuner (model RT50) comes from Grundig (Great Britain) Limited, 40 Newlands Park, Sydenham, London, S.E.26.



The Grundig a.m./f.m. tuner model RT50.

Automatic Record Changer

THE model 3000LM is a new automatic record changer produced by Garrard Engineering Limited. This deck will take up to eight records of various sizes at four speeds, but it can also be used as a single play deck, when the record spindle is replaced by a special short spindle, supplied with each deck.

Another feature of Garrard's new changer, is the low mass pick-up arm incorporated into the design. This design technique eliminates the mass and resonance of the pick-up arm, thus ensuring

that the best possible performance is obtained from the pick-up cartridge. Reduced record wear is also achieved through this arrangement.

The manufacturers of the 3000LM record changer are Garrard Engineering Limited, Newcastle Street, Swindon.




This is the 3000LM record changer made by Garrard.

100,000 Ω /V Multimeter

A NEW multimeter from Taylor's has a sensitivity of 100,000 Ω /V. This instrument—the model 101—should find many applications in radio and television servicing and in transistor radio and television measurements. In many applications, the model 101 can be used in place of a valve voltmeter, but without the inconvenience of zero drift, valve replacement, and a.c. supply connections inherent in valve voltmeters. The instrument incorporates a rugged 7 μ A centre pole movement which features a mirror arc on the scale to assist readings.

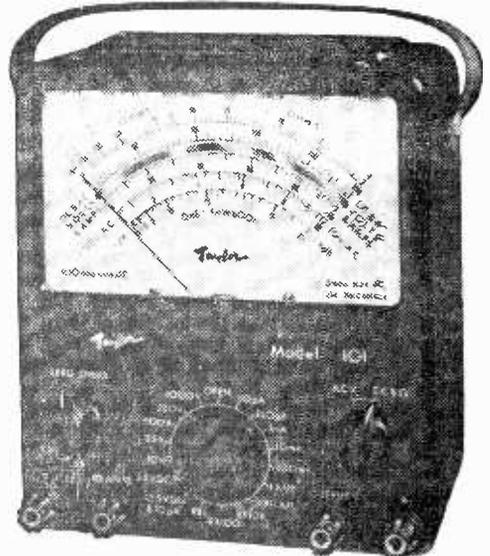Ranges of the 101 include a 10 μ A range and resistance measurements to 200M Ω . The manufacturers of this instrument are Taylor Electrical Instruments Limited, Montrose Avenue, Slough, Buckinghamshire.




The model 101 multimeter from Taylor Limited.

7-Transistor Portable

RECENTLY introduced into the range of Bush radios is the TR112 transistor portable. This receiver covers the long and medium wave bands and provides a power output of 300mW through a 6in. x 4in. elliptical loudspeaker.

The 7-transistor circuit has an average power consumption of 20mA which is supplied by the usual 9V battery. Tone control is provided and wave band selection is accomplished by push-button switches.

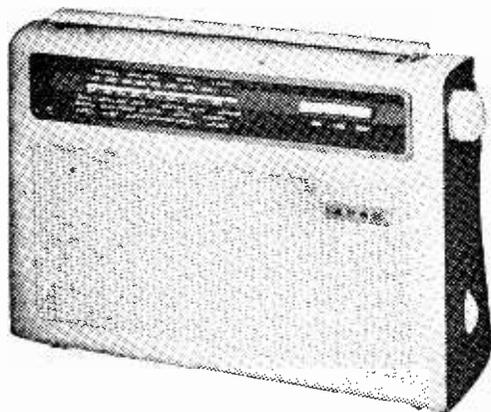The wooden cabinet is covered mainly in calf vynide material with walnut veneer end panels. **Bush Radio, Power Road, Chiswick, London, W.4, make the TR112, which costs 21 guineas.**



This new 7-transistor portable joins the range of Bush radios.

A Simple 2-stage Amplifier

—continued from page 67

of the chassis, as revealed by the broken-line in Fig. 2, and the connecting leads are directed through grommets to the various circuits underneath the chassis.

The smoothing and filter electrolytics on the h.t. line comprise two dual units C9/10 and C4/6. These are of the metal case variety and are mounted by clips on the top of the chassis, with chassis cut-outs to allow connection to the tags. The bridge rectifier is clamped on to the chassis to balance with C9/10.


The speaker circuit is terminated at a two-point socket, but if preferred the speaker leads may be soldered directly into the circuit. Note that negative feedback will occur only when the "earth" and feedback connections on the secondary of the output transformer are correctly phased. If the connections are the wrong way round positive feedback will take place. This is exhibited by very bad instability which is completely uncontrollable. Should this happen, the black inner conductor of

14W Amplifier

TECHNICAL SUPPLIERS LIMITED have announced a new 14W high fidelity amplifier available either ready assembled or in kit form. The amplifier which is known as the B.H. High Fidelity 14, offers separate mixing facilities and full range bass and treble cut and lift controls. As a kit, the amplifier sells for nine guineas; manufactured and fully tested it costs eleven guineas.

Three or 15Ω outputs are provided and with an input sensitivity of 5 and 40mV respectively, 14W output is obtained. Frequency response is 30c/s to 16kc/s ± 2dB at 10W output.

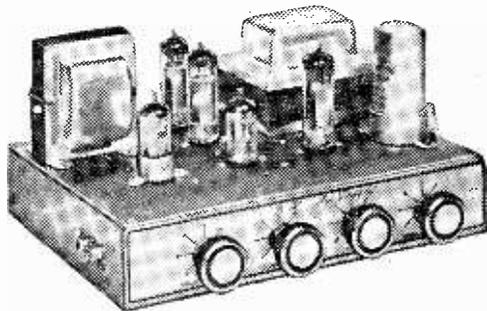Technical Suppliers Limited, Hudson House, 63 Goldhawk Road, London, W.12 are the makers of this amplifier.



T.S.L.'s new 14W amplifier.

Trade Note Correction

We wish to bring to the attention of readers the fact that the Irongate (M.O.) Company Limited are the *sole U.K. stockists* of the transistor tester featured in the Trade News page of the March issue, and *not* as stated in that item, the manufacturers of this equipment.

the screened negative feedback cable and the chassis connection to the speaker socket should be reversed.

Provided the layout is adhered to there should be no problems in getting the amplifier to work correctly. For full output the amplifier requires in the order of 400mV of input signal, and this is readily available from a crystal or ceramic type of pickup. ■

ECLL800 Audio Valve

THIS new valve used in the "7-20" Stereo Amplifier which was described in the March issue of PRACTICAL WIRELESS, consists of a triode and two power pentodes within one envelope and has a novel (B9A) base.

Developed and manufactured by Standard Electric Lorenz A.G., West Germany, the ECLL800 is now available in the U.K. from *Messrs Lugton and Co., 209-212 Tottenham Court Road, London W.1.*

NOW! ANOTHER PURCHASE of the year's keenest TAPE RECORDER BARGAIN!



A 24 gns. Tape Recorder offered at the bargain price of only 15 gns. plus 10/- carr. supplied in 3 Units already wired and tested. A modern Circuit for quality recording from Mike, Gram or Radio, using latest B.S.R. Twin Track Monardeck Type T.D.2. Magic-eye recording indicator. Ext. spkr., switch super-tupose and straight-through amplifier facilities, etc.

- Valve line up EF86, ECL82, EM84, EZ8u and Silicon Diode.
- 2 tone Cabinet and 8" x 5" Speaker Size 14" x 10 1/2" x 7 1/2" Wired Amplifier complete with 4-Valves, front Panel, Knobs **\$5.12.6** + 5/- Carr.
 - B.S.R. Monardeck Type T.D.2 **\$7.7.0** + 4/6 Carr.
 - Accessories—Mike, Tape, Screened Lead Plugs, etc. **\$1.0.0** + 2/- Carr.
 - COMPLETE KIT comprising Items above **15 gns.** + 10/- Carr.
- Leads, circuits, instructions. 2/- post free.

NEW BRITISH RECORDING TAPE

Famous Manufacturer. Bulk purchase, genuine recommended Tape. Bargain. Unconditional Guarantee. Fitted Leader & Stop Posts (except 3in.).

Standard (PVC base)	Long Play (P.V.C. base)	D'bie Play (Mylar base)
3in. 150ft. 8/9	225ft. 4/8	300ft. 6/8
5in. 800ft. 11/8	900ft. 35/-	1200ft. 25/-
5 1/2in. 850ft. 14/8	1200ft. 17/8	1800ft. 32/8
7in. 1200ft. 17/8	1800ft. 22/8	2400ft. 42/8

Post and Packing—3in. Reels, 6d. Each additional Reel, 3d. 4in. to 7in. Reels 1/- Each additional Reel, 10d.

EMPTY TAPE REELS (Plastic): 3in. 1/3, 4in. 2/-, 5in. 2/-, 5 1/2in. 2/-, 7in. 2/3
 PLASTIC REEL CONTAINERS (Cassette): 3in. 1/3, 5in. 1/3, 5 1/2in. 2/-, 7in. 2/3

Condensers—Silver Mica. All values 2pF to 1000pF 6d. each. D'bies Ceramics 9d. Tub. 450V T.C.C. etc. 0.001 mFd to 0.01 and 0.1/350V. 49. 0.02-0.1/600V. 1/- 0.25 Hunt, 1/8, 0.5 T.C.C. 1/9, etc. etc. Close Tol. 8/Micas—10% 5pF-500pF 6d. 600-5,000pF. 1/-, 2% 2pF-100pF. 9d. 100pF-600pF. 1ld. 575pF. 5,000pF. 1/6. Resistors—Full Range 10 ohms-10 meg. ohms 20% 1/4 and 1/2 W. 8d., 1W. 9d. (Midget type modern rating) 1W. 6d., 2W. 9d. Hi-Stab. 5% W. 4W. 6d. (100 ohms-1 meg). Other values 9d. 1% 1/2 W. 1/8, etc., etc.

Volume Controls—5K-2 Meg. ohms. 3in. spindles. Morganite Midget Type 1 1/2in. diam. Guar. 1 year. LOG or LIN ratio less Sw. 3/-, DP. Sw. 4/8. Twin Stereo less Sw. 8/8. DP. Sw. 8/-. Specials to order.

SPECIAL BARGAIN

1/2 Meg. VOL. Controls DP. Sw. 4 ratted spindle. Famous Mfrs. 4 for 10/-, post free.

RECORD PLAYER CABINETS 59/6 Carr. & Ins. 5/-

Contemporary style, resin-coated cabinet in two-tone maroon and cream. Size 16 1/2" x 14 1/2" x 9 1/2", fitted with all accessories including battle board and Vinylart fret. Space available for all modern amplifiers and auto-changers etc. Uncut record player mounting board 14 1/2" x 12 1/2" supplied.

2-VALVE 2 WATT AMPLIFIER. EZ80 and Twin stage ECL82 with vol. and neg. feedback tone control. A.C. 200/250V with knobs etc. ready wired to fit above cabinet. £217.6. P. & P. 1/6. 7" x 4" speaker and trans. 22/-, P. & P. 2/-.

COMPLETE R/PLAYER KIT. As ill. inc. BSR UA14 Unit. New Bargain. Price Now Only £11.10.0. 7/6 carr. Double wound mains Tr. no live chassis!




TYGAN FRET (Contem. pat.). 12 x 12in. 2/-; 12 x 18in. 3/-; 12 x 24in. 4/-, etc.

EXPANDED ANODISED METAL Attractive gilt finish 1/2 in. x 1/2 in. diamond mesh 4/8 sq.ft. Multiples of 6in. cut. Max. size 4 ft. x 3ft., 4/8, plus carr.

ENAMELLED COPPER WIRE— 1/4lb. reels 14g-20g. 2/4; 22g-28g. 3/-; 30g-34g. 3/8; 36g-38g. 4/3; 39g-44g. 4/8, etc.



Est. 1949

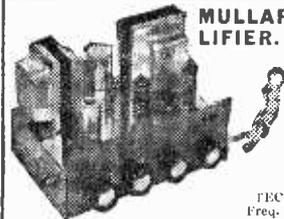

MULLARD "3-3" HI-FI AMP-LIFIER. 3 VALVES 3 WATT

3 ohm and 15 ohm Output. A really first-class Amplifier giving Hi-Fi quality at a reasonable cost. Mullard's latest circuit. Valve line up: EF86, ECL84, EZ81. Extra HT and LT available for Tuner Unit addition. This is the ideal companion Amplifier for FM tuner units.

TECHNICAL SPECIFICATION— Freq. Response: + or - 1 dB 40 c/s-25 Kc/s. Tone controls: Max. Treble 100 Mv at 400 cps; 3 w. at 1% total harmonic distortion. Hum and Noise Level: At least 70 dB below 3 w.

COMPLETE KIT (incl. valves, all components wiring diagram and special quality sectional Output Trans.). Bgn. Price £6.19.6. Carr. 4/6. Complete wired and tested, 3 gns. Wired power O/P socket and additional smoothing for Tuner Unit, 10/8 extra.

3 ohm and 15 ohm Output. A really first-class Amplifier giving Hi-Fi quality at a reasonable cost. Mullard's latest circuit. Valve line up: EF86, ECL84, EZ81. Extra HT and LT available for Tuner Unit addition. This is the ideal companion Amplifier for FM tuner units.

TECHNICAL SPECIFICATION— Freq. Response: + or - 1 dB 40 c/s-25 Kc/s. Tone controls: Max. Treble 100 Mv at 400 cps; 3 w. at 1% total harmonic distortion. Hum and Noise Level: At least 70 dB below 3 w.

COMPLETE KIT (incl. valves, all components wiring diagram and special quality sectional Output Trans.). Bgn. Price £6.19.6. Carr. 4/6. Complete wired and tested, 3 gns. Wired power O/P socket and additional smoothing for Tuner Unit, 10/8 extra.

Bronze Escutcheon, Printed Vol. Treble, Bass, On-Off, supplied with each kit.
 Recommended Speakers—WB XF1012, £4.7.8. Goodmans AXIOM 10, £6.5.0. 8in. AXIETTE £5.5.0 or AUDIOM 61, £8.10.0.

DE-LUXE RECORD PLAYER KIT



Incorporating 4 Sp Garrard Auto-Slim unit and Mullard latest 3 w. amplifier (ECL 88 and EZ 80), vol., bass and treble controls, with 8" x 5" 10,000 line speaker. Contemporary styled 2-tone cabinet, charcoal-grey and off-white with matching blue relief. Size 17 1/2" x 15" x 3"


COMPLETE KIT £13.19.6
 Carr. and ins. 10s.
 Cat. & Const. details 2/6 (free with kit).
BARGAINS—4-SP. PLAYER UNITS
 Single Players **carr. 3/6**
 E.M.I. Stereo/Mono £21.0.0
 E.M.I. Junior "988" £27.6
 Auto-changers **carr. 5/-**
 BSR UA16 £21.8.0
 BSR UA13 £21.0.0
 GARRARD Autostim £21.8.0

TRANSISTOR COMPONENTS

Midget 1.F.F.s—465 Kcs 9/16in. diam. 5/3
 Osc. Coll. 4. L.W. 5/9
 Midget Driver Trans. 3.5c1 6/9
 Midget Output Trans. Push-Pull—3 ohms 6/9
 Elect. Condensers—Midget Type 1 mfd-50 mfd. ea. 1/9, 100 mfd. 2/-, 10V.
 Condensers 150 v. working: .01 mfd., .02 mfd., .03 mfd., .04 mfd. 8d.; .05 mfd., .1 mfd., 1/- .35 mfd., 1/3; .5 mfd., 1/8, etc.
 Midget Tuning Condensers. J.B. "OC" 208 pF and 176 pF. 8/8 ditto with trimmers, 9/8. J.B. 220pF and 105pF conc. slow motion 10/8. 36pF single 7/8. Sp. Min. 4in. Dielein 100 pF, 300pF 500pF 7/- each.
FERRITE AERIALS. M. & L.W. car aerial coil 9/3.
Midget Vol. Control with edge control knob, 5 K/ohms, with switch 4/9; Ditto less switch 8/9
 Speakers: P.M.I. 2in. Plessey 7.5 ohms 15/8. 2 1/2in. Continental 8 ohms, 13/8. 7 x 4in. Plessey 36 ohms. 23/6.
 Exp. Tuning Phones—Min. Continental type 3in. lead, jack plug and socket. High Imp., 8/-, Low Imp., 7/6.
 Brand New, Mfrs. 1st grade. 1 OC45 & 2 OC45, 15/8; 1 OC81 & 2 OC81, 15/8. All above and OAS1, 32/6 Post Free.

7 VALVE AM/FM RADIOGRAM CHASSIS

Valve line-up ECC85, ECH81, EF89, EABC80, EL34, EM81, EZ80. Three Waveband and Switched Gram positions. Med. 200-550 m. 100K 1,000-2,000 m. VHF/FM 88-95 Mc/s. Philips Continental Tuning Insert with permeability tuning on FM and combined AM/FM IF transformers. 460 Kc/s. and 10.7 Mc/s. Dust core tuning all coils. Latest circuitry including AVC and Neg. Feedback. Three watt output. Sensitivity and reproduction of a very high standard. Chassis size 13 1/2 x 6 1/2in. Height 7 1/2in. Edge illuminated glass dial 1 1/2 x 3 1/2in.

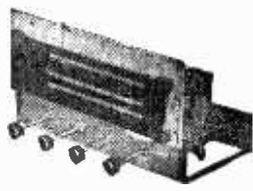

Vertical pointer. Horizontal station names. Gold on brown background. A.C. 200/250v. operation. Magic-eye tuning. Cct. diagram now available.

Aligned and tested ready for use £13.10.0 Carr. & Ins. 7/6
 Complete with 4 Knobs—walnut or ivory to choice. Indoor FM aerial 3/6 extra. 3 ohm P.M. speaker only required. Recommended Quality Speakers 19in. Elac B/D, 30/-; 13 1/2 in. E.M.I. "Fidelity", 37/8; 12in. R.A. with concentric Tweeter 42/8. Carr. 2/6

BONDACOUST Speaker Cabinet Acoustic Wadding (lin. thick approx.) 12in. wide, any length cut, 1/8 ft., 4/- yard. **TINNED COPPER WIRE.** 16-22g. 2/6 lb. **ERSIN MULTICORE SOLDER.** 60/40. 4d. per yard. Cartons 2/8, etc.

We manufacture all types Radio Mains Trans., Chokes, Quality O/P Trans. etc. Enquiries invited for Specials. Prototypes for small production runs. Quotations by return. Send for detailed bargain lists, 3d. stamp.


RADIO COMPONENT SPECIALISTS
 70 Bristock Rd., Thornton Heath, Surrey. Hours: 9 a.m. - 6 p.m., 1 p.m. - 7 p.m. T110 2188. Terms C.W.O. or C.O.D. Post and Packing up to 1 lb. 9d., 1 lb. 1/3, 3 lb. 2/3; 5 lb. 2/9; 8 lb. 2/6.

SAVE THOSE BATTERIES

WITH THE
"Pee-Pee Battery Eliminator"

Now you can run your transistor portable radio, record player, amplifier etc., direct from A.C. mains. This compact unit replaces PP3, PP4, PP7, PP9, etc. 9 volt. batteries. Price 35/- P. & P. 2/9. Also available "Pee-Pee" Twin Pack for equipment requiring two separate 9 volt outputs. Price 42/6. P. & P. 2/9. Special adaptor available for sets using 41 volt type batteries. 2/6 extra.

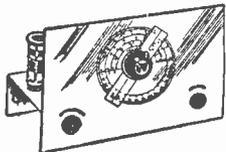LISTEN TO THE WORLD ON TELSTAR our I-VALVE SHORT WAVE RADIO



Receives speech and music from all over the world. Price includes valve and one coil covering 40-100 metres. Can be extended to cover 10-100 metres. Can be converted to 2 or 3 valve and all-mains speaker use. Total Building Costs 35/- P. & P. 2/-.

THE R.C.S. PERSONAL SET

For Private Listening



An amazing little set, with built-in ferrite rod aerial bringing in medium wave at wonderful volume. Sturdy case. Size only 2 1/2 x 3 1/2 x 1 in. Fits into the palm of the hand. Drilled chassis colour coded for easy assembly. Total Building Costs (including earpiece) 30/- P. & P. 2/-.

R.C.S. CRYSTAL RECEIVER

Covering medium wave band. Ideal for the beginner! All components including case. 8/6 P. & P. 1/6. (Suitable headphones 9/6). Easily converted to I-transistor or 2-stage transistor receiver.



All parts available separately. Send S.A.E. for free layout plans and parts lists of any of the above sets.

R.C.S. PRODUCTS (RADIO) LTD.

11 Oliver Rd., London, E.17. (Mail Order only)

Export Trade enquiries invited

AN AEI PRODUCT

Anatomy of a Superior Soldering Iron

The Solon range of electric soldering irons includes 15 and 25 watt models for radio, TV and electronic equipment; 65 watt models for household and workshop use. Larger models up to 240 watt also available.

Select a SOLON

TRADE MARK

Used in industry for over 30 years

Obtainable from your usual radio or electrical supplier



6 ft. flexible lead with cord grip

Heats up from cold in 1 1/2 mins.

Will give a lifetime of service

25 watt model for radio work

Heat concentrated in bit

THE PEMBRIDGE COLLEGE OF ELECTRONICS PROVIDES TRAINING IN RADIO AND TELEVISION

FULL-TIME COLLEGE COURSE IN RADIO AND TELEVISION

Our Course has now been extended to sixteen months' duration to include theoretical and practical instruction on transistor television receivers, U.H.F. television receivers and colour television.

Next course commences 2nd September, 1964.

This Course is recognised by the Radio Trades Examination Board (R.T.E.B.) for the Radio and Television Servicing Certificate examinations.

Provides excellent practical experience on valve and transistor radio receivers and all well-known makes of television receivers.

To:

The Pembridge College of Electronics (Dept. P11)
34a Hereford Road, London, W.2.

Please send, without obligation, details of the Full-time Course in Radio and Television.

Name _____

Address _____

A New Build-and-Learn Series—3

The "JUNIOR" Crystal + 2

This series of receivers was designed primarily to give practical aid to students at an Evening Class. The circuits are unusual, but not novel. The final stage receiver is much more sensitive than most two transistor receivers, but is not more difficult to build.

The text is written for the young beginner and naturally more advanced readers will find some of the information superfluous. The author is sure that any beginner will be able to make this radio as a result of this article.


CONTINUED FROM PAGE 1181 OF THE APRIL ISSUE

BY E. V. KING

IT may seem odd that having described in last month's issue, how to make the OC44 transistor Tr1 operate as an a.f. amplifier, we should now convert it to an r.f. amplifier! Actually in the final version of this receiver it acts as both! This is known as reflexing and since the circuit for this arrangement is rather difficult for the beginner to understand we are building it bit by bit and testing at each stage.

Fig. 9 shows the next modification with all wiring. The following wires (see Fig. 8) are removed or altered:

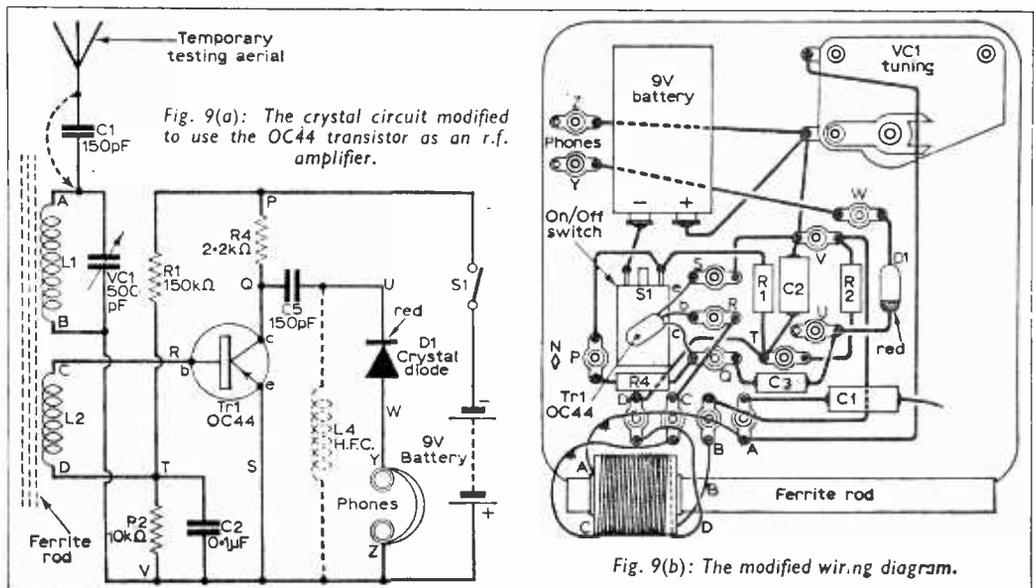1. Disconnect from the phones the lead which goes to R4. Connect this lead to the switch S1.
2. Remove entirely the other phone lead.
3. Remove both ends of the coil L2 (plastic-covered leads), then connect the knotted end to tag "C" and the other end to tag "D".
4. Disconnect from the base of Tr the lead which goes to D1. Connect this lead to one phone terminal.
5. Connect the other phone terminal to the rotor of VC1.



- Connect C3 (150pF) between the collector of the transistor and the red end of the diode.
- Join coil tag "C" to the base of the transistor.
- Join coil tag "D" to the junction of R1, R2 and C2 (at tag T).

Testing the R.F. Amplifier

The circuit is now as in Fig. 9 (without L4) and the wiring should all be carefully checked. The aerial is placed on tag "A", the lead earth on tag "B" and the ferrite rod moved almost completely out of the coil. The Light Programme should now be heard, heavily damped over most of the scale. If the aerial is removed from C1 the station will be very weak but should be tunable with the ferrite rod positioned midway in the coil.

The r.f. choke L4 is next made and temporarily connected.

Making the R.F. Choke

An ordinary $\frac{1}{4}$ in. coil former with dust-iron slugs is required. Four pieces of $\frac{1}{4}$ in. rubber tube are then cut as shown in Fig. 10 and they are slid over the former to make slots. Some fine wire, the gauge of which is not critical, is then wound on, all in one direction, so that every slot has exactly 200 turns in it. If there is room in the slots it is advantageous to put on 300 turns but the number of turns in each slot must be the same. The ends of the wires are scraped clean and taken to tags which are conveniently fitted to screws used for fixing the choke.

Fitting and Testing the Choke

The receiver is working as explained with the circuit of Fig. 9. The r.f. choke is now wired temporarily between the red end of the diode and the rotor of the tuning capacitor. The volume of the receiver will now be as loud as it was when the OC44 transistor was employed as an a.f. amplifier. Tuning will be sharp and adequate. Only in very strong signal areas, however, will the receiver work without an aerial.

The choke is now fitted carefully, using tags U and V. This will automatically put it in circuit if the coil ends go also to these tags.

Combined A.F. and R.F. Amplifier

The next stage in the development of this receiver is the conversion to "reflex operation".

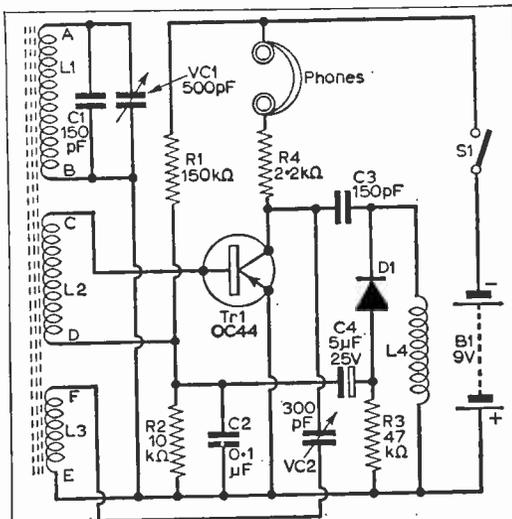


Fig. 11a (above): The reflex circuit (long waves only) with reaction.

Fig. 11b (below): The wiring of the regenerative receiver.

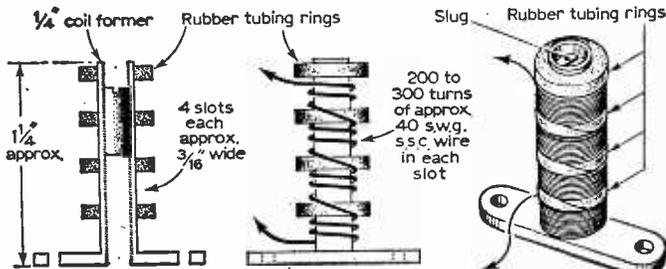
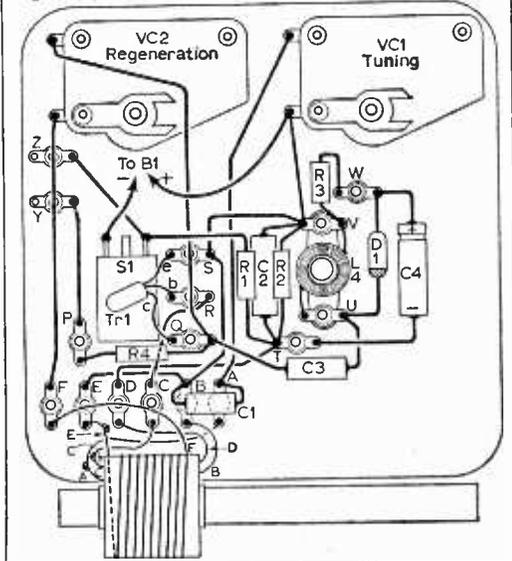


Fig. 10: Winding details of the r.f. choke, L4.

This means that the transistor Tr1 will function as an r.f. amplifier as well as an a.f. amplifier.

The operative circuit will be as in Fig. 11 (except that VC2 and L3 will not initially be connected. L1 tunes to the desired station; it is transformer-coupled to L2 which feeds r.f. into the OC44 transistor. The amplified r.f. is "choked" off by R4 and the phone windings (these act as a r.f. choke) and is thus forced

PCR COMMUNICATION RECEIVERS

Manufactured by Pye and Philips. One of the Army's most versatile and sensitive sets. RF stage and 2 of 1F using 6 British I.O. type valves. Large 180 degrees illuminated and Calibrated Dial. Flywheel tuning with locking device. Aerial trimmer. Tone and volume controls. Band switch from panel lacks for speaker or phones. In black metal case. size 17" L x 8" H x 10" D. Model PCR3 covers 6-22 Mc/s, 200-550 metres and 850-2,000 metres. **£5.19.6.** Model PCR3. As PCR2 but has 2 Short Wave Bands. 2.0-7.0 Mc/s and 7.0-23.0 Mc/s and Medium Wave Band 190-550 metres. **ONLY £8.8.0.** Every receiver aerial tested before despatch. Add 10/6 carr. Both types used, but excellent condition. Designed to operate from bulky external power supply, but any set can be fitted with BRAND NEW COMPONENTS INTERNAL PACK for 200/250 v. A.C. at extra cost of **£2.** S.A.E. for illustrated leaflet.

TEST METERS FOR EVERY PURPOSE & POCKET



2,000 O.P.V. MODEL TP-10
Reads A.C. & D.C. Volts up to 1,000; D.C. Current to 500 mA; Resistance to 1 Meg; Capacitance to 1µF; Decibels from -20 to +36; Output Jack for Audio Measurements. Size 3 1/2 x 5 1/2 in. **£3.19.6**



20,000 O.P.V. MODEL TP-58.
Reads voltage up to 1,000 D.C. at 20,000 ohms per volt and A.C. at 10,000 O.P.V.; D.C. Current to 500mA; Resistance to 10 Megs.; Capacitance to 0.1µF; Decibels from -20 to +36. Size 3 1/2 in. x 5 1/2 in. **£5.19.6**



30,000 O.P.V. MODEL 500. Volts to 1,000; D.C. at 30,000 O.P.V. A.C. at 20,000; 12 AMPS D.C. Current; 60 Megs Resistance; -20 to +56 dBs; internal buzzer short circuit warning. Size 3 1/2 in. x 6 1/2 in. x 2 1/2 in. **£8.19.6**

All New Stock, with leads, prods and internal batteries, 6 months' guarantee backed by full service facilities. Details S.A.E.

DOUBLE BEAM OSCILLOSCOPE TUBES, TYPE CV-1596. Equivalent to COSSOR 09D (as used in Oscilloscopes by Cossor 338 series) and Hartley & Erskine (13 series). Listed £12. BRAND NEW IN MAKER'S CRATES. **ONLY 25/-** (carriage 5/-).

LARGE CUP WAVEMETER MODEL 105. Coverage 375/725 Mc/s. Complete with correct Calibration Chart. First-class condition. Battery operated and portable. size 11 x 8 x 7 1/2 in. **ONLY £3.19.6** (carriage 7/6).

AMERICAN DESK TELEPHONE, complete with handset. Non-dial type but has internal bell. Ideal for extension or intercom. BRAND NEW. **ONLY 30/-** (post 4/-).

ACOS 35/1 STICK MIKE with screened lead and table stand. **ONLY 32/6** (post 1/6).

CRYSTAL DESK MIKE with screened lead and built-in stand. **ONLY 15/-** (post 1/6).

PORTABLE A.C. VOLTMETER. First Grade Moving Iron with 6in. Mirror Scale. Reads up to 150 volts A.C. 400 and 1200-2400 cycles. In substantial oak case with removable lid. Overall size 8 1/2 x 8 1/2 x 5 1/2 in. BRAND NEW. **ONLY 25/-**.

COSSOR TYPE 1035 DOUBLE BEAM OSCILLOSCOPES. A few only of these modern scopes, overhauled and in perfect order. **ONLY £45.** Further details on request.

SPRAGUE CONDENSERS. Metal cased, wire end. New 0.01 mfd. 1,000 volt, and 0.1 mfd. 500 volt, 7/6 per dozen. Special quotes for quantities.

12 VOLTS AMERICAN DYNAMOTORS. Deliver 220 volts at 100 mA. Size 5 1/2 x 3 1/2 in. diameter. Ideal for Running Electric Shaver etc. for Car Battery. **ONLY 32/6** (post 2/6).

20/- CONSTRUCTOR'S PARCEL. Assorted colours wiring wire, solder, resistors, condensers, volume controls, tag panel. ALL NEW (post 2/6).

RESISTORS. 100 assorted values our choice. NEW. 7/6.

CONDENSERS. 100 assorted mica and silvermica. NEW. 10/-.

TRANSISTORISED INSULATION TESTERS




Size 7in. x 4 1/2 in. x 4in.

ONLY £17.10.0
S.A.E. for illustrated details.

The latest technique for checking insulation of electrical circuits, appliances and components. One handed operation (no turning of generator), a Transistor DC-DC converter being employed to supply the high potentials. Three Testing voltages, 100, 250 and 500, to measure up to 500 megohms. Complete with leather carrying case, internal batteries and test leads.

P.W. "CELESTE 7" RECEIVER

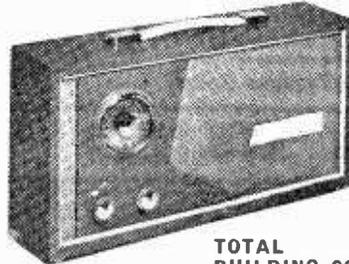

Build this latest P.W. seven transistor portable, as described in June and July issues. Medium and Long waves, with output of 1 watt from large 7 x 4in. loud speaker, internal high gain aerial with car aerial socket. All components sold separately - parts list S.A.E.

TOTAL BUILDING COST £9.19.6

VARIABLE VOLTAGE TRANSFORMERS

Fully shrouded, input 230 v. A. 50/60 cycles, output 0-250 v.
2.5 amps type..... **£5 17 6**
5 amps type..... **£9**
10 amps type **£16 10 0**



Brand new Import, fully guaranteed. Immediate delivery and service. Illustrated details on request.

BATTERY CHARGER

6 v. or 12 v. at 3/4 amps. Fused and fitted with Ammeter and Voltage Selector. Louvred metal case finished attractive hammered blue. Ready for use with mains and output leads. **ONLY 55/-** (Post 3/6).

PANEL METERS. 25 microamps D.C. 2 1/2 in. Proj-circular 59/6-50 microamps D.C. 2 1/2 in. Flush circular 59/6. 40 amps D.C. 2 in. Proj-circular 7/6. 300 volts A.C. 2 1/2 in. Flush circular 25/- . 500 volts A.C. 2 1/2 in. Flush circular 25/-.

TELESCOPIC AERIAL. 8 sections 30in. open, 5in. closed, with 4in. projection. Chromium plated and ideal for a variety of uses. **ONLY 10/8.**

HARRIS ELECTRONICS (LONDON) LTD

138 Gray's Inn Road, London, W.C.1

Phone TERm us 7937

Please include carriage costs on all items (Open until 1 p.m. Saturdays). We are 2 mins from High Holborn (Chancery Lane Station) and 6 mins. by Bus from King's Cross.

through C3, where it sets up oscillations across L4, which may be assumed to be a very broadly tuned circuit.

The r.f. signal across L4 is rectified by the diode D1 and generates a voltage across R3, the diode load resistor. L.F. audio frequency variations (i.e. vibrations caused by speech or music) can pass C4, which is of high capacity, and this a.f. or audio signal is fed back to the transistor base via the coil L2.

The OC44 transistor amplifies these audio vibrations but they cannot pass the small capacitor C3 and thus are fed along R4 into the phones. This process is known as "reflexing" and it gives the gain of two transistors with only one being actually used.

Resistors R1 and R2 form a bias network splitting the battery voltage in the ratio 15:1, giving the coil L2 a potential of approximately 0.5V negative relative to the positive line. This will give a collector current of about 2mA in the transistor.

Later a feedback coil (L3) will be fitted and also a feedback capacitor VC2. These two components together will give reaction and the receiver will then work anywhere in the British Isles without an external aerial.

Reflex Wiring (Fig. 11)

The wiring modifications are as follows.

1. Test the receiver as working at stage of Fig. 9 with the choke L4 fitted.
2. Remove both phone wires.
3. Remove the wire from R4 to switch S1 and connect one from R4 to phones.
4. Connect the other phone tag to switch S1.
5. Connect C4 with positive end to diode black.
6. Connect negative end of C4 to tag "T".
7. Connect black of diode to R3 and other end of R3 to rotor of tuning capacitor VC1 or tag V.
8. The choke L4 is now fitted. This is easy but great care is required to keep the wiring correct. The tags labelled U and V are made the choke terminals (or tags) and may usually be conveniently made the fixing screws as well. Check the wiring carefully with Fig. 11.
9. Make sure the small capacitor C3 is between the diode side of the choke and the collector of the OC44 transistor.

Testing the Reflexing

The receiver is fixed as before and this time the volume will be so great that in most places the Light Programme will come in at an uncomfortable volume which is easily audible two yards or more away from good phones (reed type). The current taken is still only about 2mA. The tuning will be somewhat flat and unselective.

The choke has an appreciable effect in this circuit: if wound as in the instructions all is well, if a purchased one is used the ordinary TV-type h.f. choke is *not* suitable and readers must specify that the choke is for medium and long waves only.

Adding Regeneration

When regeneration (or "reaction") is added the set will work without an external aerial, the ferrite rod being sufficient. The tuning will be more selective but somewhat more difficult, since the variable regeneration control VC2 has some effect on the settings of the tuning capacitor VC1.

For regeneration an additional coil, L3, is wound on the two coils already wound. This is done as shown in Fig. 4, stage 4. (See March issue.) The directions of winding are most important.

The following wiring is then carried out:

1. Solder aerial reaction coil L3 ends E and F to their respective tags.
2. Join tag F to reaction capacitor VC2 rotor and tag E to tag B (battery+ line).
3. Wire stator of VC2 to the collector of the OC44.
4. Wire spare end of C1 to tag B.
5. Inspect carefully for any shorts, especially between tags for anchoring the aerial coil connections.

These connections are already shown in Fig. 11.

Testing with Regeneration

No aerial is required. Place the ferrite rod in the coil and switch on. Adjust VC1 so that the vanes are fully opened and then close VC2 until oscillation at audio frequency is heard. If it is not then something is wrong. The trouble in this event may be due to a poor, insensitive transistor or the r.f. choke L4 may be at fault. The direction of the coil windings is all-important. Remember, the aerial is directional.

Assuming oscillations are heard, reduce the capacity of VC2 until they just cease. This point is the most sensitive and when tuning VC1 the reaction control VC2 must be constantly adjusted so that the oscillations are *just* on the point of commencing. This will take some getting used to as VC2 is not a volume control but a sensitivity control.

The Light Programme will come in at good strength (say three times as loud as a crystal set with a long aerial), although no external aerial is required.

With this station tuned in VC1 will be about halfway out and VC2 may be anywhere, but we want now to get the reaction adjusted for optimum ease of adjustment. This is performed as follows: Fully close VC1 and adjust VC2 until oscillation just occurs. If this occurs with VC2 nearly fully in all is well. On the other hand, if this control is opened to any great degree then one turn at a time must be taken off L3 (the last coil wound) until oscillation occurs only when VC2 is almost fully in. In this way the reaction adjustment will be found to be much finer, steadier and easier.

The long wave section is now complete. The receiver should now be thoroughly tested as working and then every wire and component should be laid out carefully and methodically so that further modifications may be carried out without any mishaps to the part already done.

Some younger readers may feel that they have done enough for now and the unit may now, if desired, be housed in a plastic sandwich box and it will give good service in this way.

How the Reaction Works

The r.f. oscillations are choked off after leaving the collector of the OC44 by R4 and the phone windings, some pass C3 to the diode and are rectified but some pass through VC2 to the feedback coil L3. Here, provided the coil is wound the correct way, magnetic coupling will feed additional r.f. into L2. additional, that is, to the r.f. being fed into L2 by L1 (and the ferrite rod). If L3 winding direction is correct the r.f. will be in phase (will increase amplification), but the reverse is also true. The number of turns suggested for L3 will suit the worst OC44 but a good one will probably only need five or six turns. The less the better as long as feedback is sufficient, since the less turns on L3 the less the tuning of L1 will be affected.

Adding Another Transistor

The receiver is now as shown in Fig. 11. It is proposed now to fit a second transistor, a

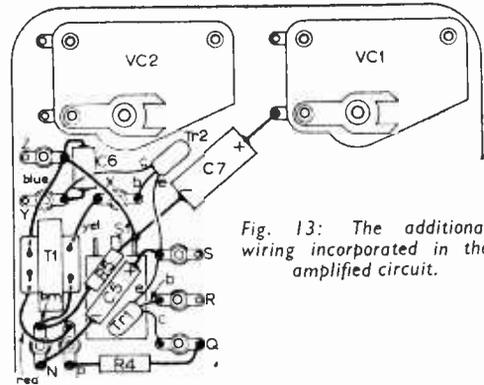


Fig. 13: The additional wiring incorporated in the amplified circuit.

this resistor. The other phone tag is left wired to the switch and the blue transformer wire is also soldered to it. The yellow lead is soldered to the tag marked "X" and it must be checked that this tag is not fouled by the capacitor vanes when they open.

The brown lead is soldered to a small tag labelled "N" and is coupled to the switch via R5. From the "N" side of R5 connect C5 with the positive end to the emitter of the OC44. Connect C6 across the phone terminals. Carefully sleeve the leads of the OC81 and solder the emitter to the emitter of the OC44, the base to tag "X" (yellow transformer lead) and the collector to the open-circuit phone tag. Check that the circuit complies with Figs. 12 and 13.

Testing the Amplifier Circuit

The phones and battery are re-connected and on test the receiver will now be much more powerful and Droitwich should be heard easily with the phones laid on the table. Remember to set the reaction control almost on the point of oscillation. If a milliammeter is available the current should be about 8mA, but this is not very critical as long as it is not creeping up. Good volume can be obtained with a current of only 3mA and adjustment of this current is possible by carefully altering the value of R5. If it is made of lower resistance the current will increase, not necessarily with any increase in volume. Good results with low consumption of battery current may be obtained with R5 at 200kΩ.

Check now that the vanes of VC2 cannot foul the OC81 leads.

In the concluding part of this series next month, the receiver circuit will be modified, once again, to include medium as well as long waves in its coverage.

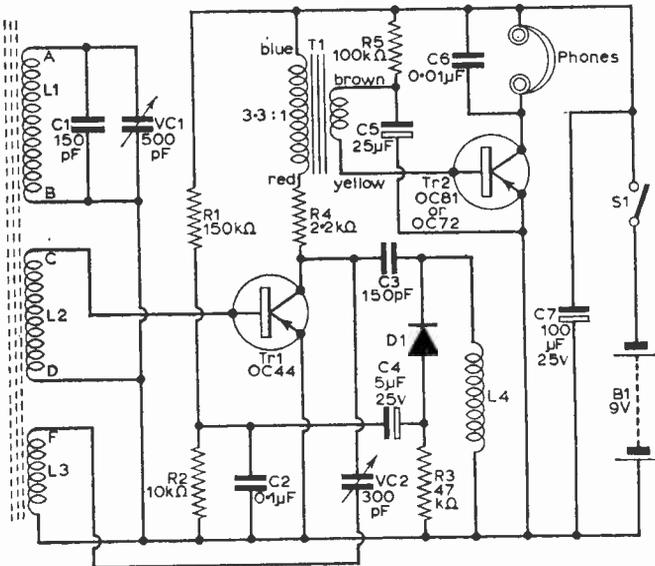


Fig. 12: An amplified version of the reaction circuit.

type OC81, as shown in Figs. 12 and 13.

The audio frequency transformer T1 is fairly critical and the correct one should be obtained and fitted through the two holes indicated in Fig. 1. (Radiospares type T/T3, ratio 3:3:1.) The tags are soldered to a thick wire as shown in Fig. 2(b)—see March issue.

Wiring the OC81

The circuit of Fig. 12 is now to be completed, the new wiring being shown in Fig. 13.

The lead from R4 to the phones is removed entirely and the red transformer lead attached to

Waterproof heater wire

16 yds. length, 70 watts, self regulating temperature control. 10/- post free.

Refrigerator Thermostat

Standard type with adjustment for all normal refrigerator temperatures, 7/6 plus 1/- post.

Simmerstat Heater Regulator

Suitable to control elements, heater, soldering irons and boiling rings up to 2,500 watts. Complete adjustable, normal price 55/- each, special snip price 12/6, plus 1/6 postage and insurance.

Pre-Amplifier. Made to Mullard design to suit the 10 watt amplifier, made to specification. New Unit. Simply needs valves. Type EF86. 3/6 each.

48 Sets (Receiver/Transmitter) pack set. Unused sets complete except for crystals. Packed with parts and easily rebuildable into other gear. 19/6 each. Post 3/-.

Battery Charger Kit. Comprises 5 amp transformer, 5 amp rectifier, metal case and meter to charge 6 or 12 volt batteries up to 5 amps. With variable charge rate. 39/6 each. Post and insurance, 3/6.

Leins Transformer. 250-0-250 at 80 mA, 6.3 volts 5 a. (normal mains input). 12/6 each. Carriage 2/6.

Output Transformer. Standard pentode matching type. 4/6 each. 48/- per doz. **Vibrator Transformer.** Suitable for 6 or 12 volts input. 5/9 each. 23 per doz.

Slide Switch. Sub-miniature but dup'd. 2/6 each. 18/- per doz.

Smoothing Choke. H, 200 mA. 5/6 each. 54/- per doz.

TV Mains Dropper. With tappings as follows: 25 ohm, 25 ohm, 80 ohm, 60 ohm, 80 ohm. 2/6 each. 24/- per doz.

TV Metal Rectifier. 250 mA, 250 volts. 11/6 each. 26 per doz.

TV Control Panel. With two fuses, mains input plug, and two voltage adjusting screws. 1/6 each. 12/- per doz.

T.C.C. or Dubilier Tubular Condensers.

.5 mf 500 v. 10/- doz.
 .25 mf 500 v. 7/6 doz.
 .25 mf 350 v. 6/- doz.
 .05 mf 500 v. 5/- doz.
 .04 mf 500 v. 4/- doz.
 .0001 mf 1,000 v. 5/- doz.

Battery Charger Rectifier—selenium 12-15 v. 5 amp. 9/6.

Metal Chassis—punched for Mullard 510 Amplifier, complete with inner screening sections and stove enamelled. 12/6 set.

Geiger Counter Tubes—20th century type, Type No. G24, with circuit of geiger counter, 29/6.

Twin Twisted Lighting Flex—equivalent 14/36, rubber insulated, cotton covered 12/6 per 100 yard coil.

Moving Coil Meters

0-500 microamp, 2 1/2 in. flush . . . 17/6
 250-0-250 microamp, 2 1/2 in. surface . . . 27/6
 750 microamp, 2 1/2 in. surface . . . 17/6
 5-0-5 microamp, 2 1/2 in. flush . . . 17/6
 0-30 milliamp, 2 1/2 in. flush . . . 15/-
 0-100 milliamp, 2 1/2 in. flush . . . 15/-
 0-300 milliamp, 2 1/2 in. flush . . . 15/-
 0-500 milliamp, 2 1/2 in. flush . . . 15/-

Filament Transformer. 6.3 v., 1 1/2 amps., 6/6. 3 amp. Dropper—tappings marked 200/220/250, 3/6.

Output Transformer—standard pentode, 4/6.

Neon Lamp—midjet wire ended, ideal mains tester—etc., 2/-. Ex. Govt. 1/6.

Philips Trimmers—0-30pF, 1/- ea. 9/- doz.

Heavy Duty Test Prods—red and black with plug-in lead attachments, 8/6.

Install those extra points. 3.029 twin flat T.R.S. cable. Big purchase enables us to sell this at 45/- per 100 yards, carriage 3/6.

Low Resistance Head Phones. Ideal crystal sets, etc., 7/6, plus 2/6.

Cold Cathode Valve CV413. Voltage regulator or trigger switch—nursed but ex-equipment. 2/- each.

Tag Panels. Ideal for constructors, experimental circuits, etc. 3 of each of 12 different types. 5/-.


Slydlok Panel Mounting Fuses with carrier, 5 amp. 2/- each. 15 amp. 2/6 each. **1mfA 350 v.** Small tubular metal cased condensers made by Dubilier. 2/6 per doz.

5,000 Mfd Condensers

12 v. working by Electro. new and perfect 2/- each. 18/- doz.

GOOD COMPANION Mark III

The 6 transistor set with the 6 transistor performance. Incorporating all the latest requirements. Anyone who can solder can make it. Many thousands already in use all over the country. Full coverage of Long and Medium wavebands. Fine looking cabinet, size 11" x 8" x 3". Q.P.P. Output approx. 750 mW. Excellent reception of difficult stations like 208. Variable feed back gives excellent tone. **ONLY £5.19.6**

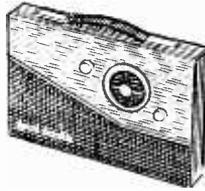


CABINET & PICK-UP

Made for a famous company intending to make a Battery Record Player but changing their minds. This is an extremely fine looking cabinet, must have cost at least £2 to make. It is complete with handle and fasteners as illustrated. Also included in the parcel is a 'Cosmocord pick-up' with crystal cartridge and sapphire styrene. Both items new and perfect. **Only 19/6, plus 4/6 post and insurance.**



**THIS MONTH'S SNIP
Fluorescent Light Bargain**

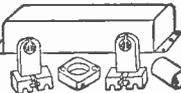Kit of parts comprising: choke, two holders, starter, 40 watt, 19/6; 60 watt, 27/6. Plus 2/6 post and insurance.



The white enamelled metal work to make a complete battery fitting given FREE with every Kit ordered this month. Add only carriage 5/-.


VALVE BARGAINS

3J115	4/3	6J5G	3/-	35L6GT	8/-
184	3/6	6K5G	6/-	37	5/6
2X2	3/-	6K7GT	4/3	30L6G	10/-
6A47	3/-	6K7G	2/-	72	8/6
6B7G	5/-	6S47	5/9	843	7/-
6BSG	2/6	6SK7GT	4/6	860	25/-
6C4	2/3	6V15G	3/9	951	3/6
6C6	3/-	6Q7G	4/6	9004	3/-
6D6	3/-	6X5G	4/6	1625	5/-
6F6G	4/-	7A7	7/-	1DD4	8/6
6FN4	5/-	7B7	7/6	EDF52	7/6
6H4	2/6	7C5	10/-	627	6/6
6H6	3/6	7J4	5/-	1D5	7/-
6H6GT	1/6	12SK7GT	3/6	MU12	5/-
6J5	7/-	12YA4	3/-	PCPN1	6/6
6J5GT	4/-	28D7	2/3	VR105	5/6

25% discount where 12 or more valves ordered.

MOTOR BARGAIN

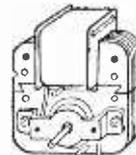Silent running mains motor by very famous maker. Ideal for gramophone, tape recorder, fan etc. etc. 200-250 volts, A.C., shaded pull start. Size approximately 2 1/2 x 2 1/2 x 1 1/2 in. 2.750 i.p.m. Spindle diameter 5/32 in. Spindle length 1 in. Brand new guaranteed. Price 12/6, plus 1/- post.



YAXLEY SWITCHES

By return service—you need not be held up with that prototype or experiment. Please add 1/- postage to all switch orders.

POLES	2 Way	3 Way	4 Way	5 Way	6 Way	7 Way	8 Way	9 Way	10 Way	11 Way	12 Way	13 Way
1.	2/8	2/10	3/1	3/3	3/9	3/8	3/10	4/1	4/3	4/6	4/8	4/8
2.	3/3	3/8	4/1	4/6	4/11	5/4	5/8	6/2	6/5	7/-	7/6	7/6
3.	3/11	4/6	5/2	5/9	6/5	7/-	7/6	8/3	8/6	9/6	10/1	10/1
4.	4/6	5/4	6/2	7/-	7/10	8/8	9/5	10/4	10/10	12/-	12/6	12/6
5.	5/2	6/2	7/3	8/3	8/9	10/1	11/3	12/5	13/1	14/6	15/6	15/6
6.	5/9	7/-	8/3	9/6	10/9	12/-	13/2	14/6	15/8	17/-	18/3	18/3
7.	6/5	7/10	9/4	10/9	12/3	13/8	15/1	16/1	17/6	19/6	20/11	20/11
8.	7/-	8/8	10/4	12/-	13/8	15/4	17/-	18/8	19/8	22/-	23/5	23/5
9.	7/8	9/6	11/5	13/3	15/4	17/-	18/10	20/9	21/11	24/6	26/4	26/4
10.	8/3	10/4	12/5	14/6	16/9	18/8	20/10	22/10	24/1	27/-	29/1	29/1
11.	8/11	11/2	13/6	15/9	18/3	20/4	22/7	24/11	26/4	29/8	31/9	31/9
12.	9/6	12/-	14/6	17/-	19/8	22/-	24/6	27/-	29/1	32/-	34/-	34/-

Speaker Bargain


12in. High-fidelity loud speaker. High flux permanent magnet type with standard 3 ohm speech coil. Will handle up to 12 watts. Brand new, by famous maker. Price 27/6 plus 3/6 post and insurance.



Hi-Fi Speakers

E.M.I. Ceramic magnet 12,000 lines, size 13 x 8 in. (roughly equivalent to 12in. round speaker). Bass frequency 40-50 c/s. Handles up to 10 watts. Price 55/6, plus 5/- carriage and ins. State whether 15 ohm or 3 ohm.

Building A 'Scope

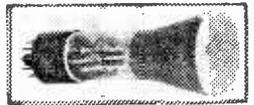

3in. oscilloscope tube. American made type No. 3PFT. 6.3 v. 0.6 amp. heater electrostatic deflection, brand new and guaranteed with circuit diagram of scope 15/- each, plus 2/6 post and insurance.

Timer Kit

Special offer of all components except metal box to make mains operated interval timer for photography etc. 12/6 plus 2/6 post.

Transistorised Thermostat

for controlling temperature where a very high order of accuracy is required—regulation in an egg incubator of .1% was claimed. Complete kit including relay and full data 29/6.

ALWAYS USEFUL ITEMS

Nylon Drive Cord. 5ft. lengths, 1/8 ea. 15/- per doz. 3in. Spindle Coupler with grub screws, 7d. ea. 6/- per doz. Trimming Tool for Insulator 1P8a, 8d. ea. 7/- per doz. Insulated Spindle 3in. polystyrene 5in. length, 1/- ea. 11/- doz. Neon Lamp Midget type as in screwdrivers etc., 2/- ea. 21/- doz. Ebonite Tubing 2 od for making test prods etc. 6in. length 1/- ea. 10/- doz.

Beginner's Superhet

As supplied to many schools and colleges. A simple basic superhet—easy to understand and which can be progressively extended—Ideal for students—components include—valves—metal rectifier tuning condensers—1.5 transformers, etc. In fact complete superhet except speaker. Price 28 plus 1/- post and insurance. Data include free or sep., 1/6.



ELECTRONICS (CROYDON) LTD

Personal shoppers to:

266 LONDON ROAD, WEST CROYDON, SURREY

Post orders to: 43 Silverdale Road, Eastbourne, Sussex.



SAVBIT ALLOY
saves wear on
soldering iron bits

The world-famous copper loaded alloy containing 5 cores of non-corrosive flux, that saves the soldering iron bit. Ersin Multicore Solder is also available in high tin quality alloys. 60 40 in 22 s.w.g. for printed circuits, transistors, etc.

SAVBIT SIZE 1 CARTON

Contains approximately 7 feet of 18 s.w.g. SAVBIT. It is also supplied in 14 s.w.g. and 16 s.w.g. Obtainable from radio and electrical stores.



5/- each

THE HANDY DISPENSER



Easy to find in the tool box—simple to use. Virtually a third hand for tricky soldering jobs. 1-1/2 feet 5-core 18 s.w.g. **ERSIN MULTICORE SAVBIT** alloy in a continuous coil used direct from free-standing dispenser. 2/6 each

BIB WIRE STRIPPER AND CUTTER

Strips insulation without nicking wire cuts wire cleanly, adjustable to most thicknesses. Splits extruded plastic twin flex. 3/6 each



MULTICORE SOLDERS LTD.

MULTICORE WORKS · HEMEL HEMPSTEAD · HERTS. (BOXMOOR 3636)

CHMS 24

CANADIAN RECEIVERS No. 9. Similar to 52 Set, but cover 1.5 to 5 Mc/s. Tip-top condition, complete with crystal calibrator, valves, etc. **BARGAIN FOR CALLERS ONLY. 79/6. PCR-3 RECEIVERS.** 3 wave bands, medium wave and 2 short wave, from 120-13 metres. Good condition, tested. 8 gns. Carr. 10/- A.C. mains internal power supply £2 extra.

SILICON RECTIFIERS. Type BY101 (4in. x 1in.) will handle 250 volts at up to 500 m.A. Replaces any TV metal rectifier, BRAND NEW—not seconds. 7/6.

AR-88 VIBRATOR PACKS. For 6V. operation. Complete with vibrator & OZ4 rectifier, NEW in original cartons. 17/6. P. & P. 2/6.

AR-84 SPARE VALVES. Complete Set of BRAND NEW Individually boxed original valves (14). 50/- plus 2/6 P. & P.

MOVING COIL PHONES. Finest quality Canadian with Chamolix ear muffs and leather covered headband. With lead and jack plug. Noise excluding, supremely comfortable. BRAND NEW.....92/6, post 1/6.

MAGNETIC COUNTERS (EX-G.P.O.). 4 figures to 9,999. Coils 500 Ω for 24V. operation. Tested. (No reset). 5/- each. P. & P. 1/6. **SPECIAL OFFER!** 10 for 30/- P. & P. 7/-.

PRECISION WIRE-WOUND RESISTORS manufactured by Alma. Rivlin, etc. Values available 200 Ω, 1K, 2.5K, 5K, 10K, 25K, 50K, 60K, 100K, 200K, 250K, 500K and 1M Ω. 1%—1/3, 0.1%—2/-, 0.05%—7/6. Please add Post.

CRYSTAL CALIBRATOR. As used in Canadian No. 52 set. Incorporates twin 1Mc/s and 100Kc/s crystal and a multi-vibrator circuit to give 10Kc/s marker pips. Requires 12V, 1 amp. L.T. and 150V. H.T. Complete with 3 valves, circuit of 52-set and operational notes. BRAND NEW 79/6, plus 2/6 P. & P.

MULLARD CRYSTAL CALIBRATOR. In neat grey metal case 9 x 7 x 6 1/2 in. Gives 1 Mc/s, 100 Kc/s, and 10 Kc/s marker pips and harmonics as selected. Optional 400 c/s modulation. Complete 3 valves 17H (5), 18B (1) and 1 Mc/s BT3 glass crystal. Requires 0V. H.T. and 150V. L.T. in original transit case. BRAND NEW. 94.19.6. Carr. 7/6.

MICRO-AMMETER. 0-500 μA. Made by R.C.A., Weston Westinghouse, and other famous American manufacturers. Circular 2 1/2 in. flush panel mounting. Dials are engraved 0-15, 0-600 volts. As used in the American version of the "19 SET". TESTED AND GUARANTEED 15/-.

CHARLES BRITAIN RADIO LTD
11 UPPER SAINT MARTINS LANE, LONDON W.C.2

TEmple Bar 0545

Shop hours 9-6 p.m. (9-1 p.m. Thursdays). Open all day Saturday.

FREE TO AMBITIOUS ENGINEERS
— THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

Have you sent for your copy?
ENGINEERING OPPORTUNITIES is a highly informative 156-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronics Courses, administered by our Specialist Electronics Training Division—the B.I.E.T. School of Electronics, explains the benefits of our Employment Dept. and shows you how to qualify for five years promotion in one year.

We definitely Guarantee
“NO PASS — NO FEE”
Whatever your age or experience, you cannot afford to miss reading this famous book. If you are earning less than £25 a week, send for your copy of “ENGINEERING OPPORTUNITIES” today—FREE.

WHICH IS YOUR PET SUBJECT?

- Mechanical Eng..
- Electrical Eng..
- Civil Engineering.
- Radio Engineering.
- Automobile Eng..
- Aeronautical Eng..
- Production Eng..
- Building, Plastics, Draughtsmanship.
- Television, etc.

GET SOME LETTERS AFTER YOUR NAME!

- A.M.I.Mech.E.
- A.M.I.C.E.
- A.M.I.Prod.E.
- A.M.I.M.I.
- A.I.O.B.
- A.F.R.Ae.S.
- B.Sc.
- A.M.Brit.I.R.E.
- City & Guilds
- Gen. Cert. of Education
- Etc., etc.

PRACTICAL EQUIPMENT

Basic Practical and Theoretical Courses for beginners in Radio, T.V., Electronics, Etc., A.M.Brit.I.R.E. City & Guilds Radio Amateurs' Exam. R.T.E.B. Certificate P.H.G. Certificate Practical Radio Radio & Television Servicing Practical Electronics Electronics Engineering Automation

INCLUDING TOOLS!

The specialist Electronics Division of B.I.E.T. NOW offers you a real laboratory training at home with practical equipment. Ask for details.

B.I.E.T. SCHOOL OF ELECTRONICS



POST COUPON NOW!

Please send me your FREE 156-page "ENGINEERING OPPORTUNITIES"
 (Write if you prefer not to cut page)
 NAME

ADDRESS

SUBJECT OR EXAM THAT INTERESTS ME **SE 21**

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY
(Dept. SE/21), 29 Wright's Lane, London, W.8

THE B.I.E.T. IS THE LEADING ORGANISATION OF ITS KIND IN THE WORLD



LETTERS TO THE EDITOR

A MEETING GROUND FOR THE RADIO ENTHUSIAST

SIR.—Every month your magazine devotes a page to the activities of the amateur radio societies. As readers will have noticed, much of the activity is concerned with what we pithily refer to as “ham” radio and the impression is that club members are a bunch of technically informed gentlemen with a good deal of expensive and complicated equipment. There is, however, a huge army of radio enthusiasts throughout the country who regularly subscribe to P.W. but who are deterred from joining the local radio society because of the fear that their lack of technical knowledge would deprive them of the enjoyment of full participation.

For them, the more novice yet nonetheless enthusiastic readers of this journal, there are in most districts, particularly in London and the bigger towns, the local Evening Institute which provides classes in radio and television. There are, of course, special courses organised by Technical Colleges for those with the serious intention of taking up radio as a career, but the general Institutes hold classes for the radio enthusiast who regards his interest as his hobby.

The accent of these classes is on the practical side and those who attend are encouraged to build equipment or even to take along their own faulty receivers so that they can be shown how to repair them.

The feature of these radio classes which should be especially attractive to young P.W. readers, is that they provide an organised meeting ground for all who are interested in practical radio and who wish to enlarge their knowledge of their favourite hobby in a social atmosphere.—H. NAYLOR CALEY (London).

POCKET SIGNAL INJECTOR CASE

SIR.—Last year I began construction of the Pocket Signal Injector by Mr. R. W. Kneeshaw, described in the July issue of P.W. All the parts were easy to obtain, but for one item—the penlight torch case. I searched every Woolworth store in Cardiff only to be told that it was out of stock and would not be renewed.

Now again, I am unable to obtain the same case for the Pocket Signal Tracer which appeared in the March '64 edition. I would therefore be glad of your advice in this matter.—G. L. DAVIS (Gabalra, Cardiff).

SIR.—With reference to the availability of the penlight torch cases specified in my articles on the Pocket Signal Injector and Signal Tracer, it

Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying commercial or surplus equipment. We cannot supply alternative details for receivers described in these pages. **WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE.** If a postal reply is required a stamped and addressed envelope must be enclosed with the coupon from page iii of the cover.

The Editor does not necessarily agree with the opinions expressed by his correspondents

does appear that Woolworths no longer sell these but I suggest that an alternative “penlight” casing that could easily be adapted, is readily obtainable from Boots Chemists.

In my opinion this case would produce an even more professional looking unit than the original. No circuit alterations are required but, because of its slightly greater length, the inner chassis of either unit would have to be slightly longer with the width remaining the same. This, of course, will present no special problems. A slightly modified method of attaching the probe tip may also have to be evolved, but again this should not prove difficult for the constructor.

The Boots case also has the advantage of a push-button on/off switch incorporated at its end, this being a great improvement on the original.

I trust that this information will prove useful to any of your readers contemplating the construction of either of these units. — R. W. KNEESHAW (Bristol 6).

MODE OF OPERATION

SIR.—Being interested in transistor gadgets, I recently constructed Mr. P. Rowe's Thermostat described in your December 1963 issue. I find this device very sensitive, but the mode of operation is the reverse of that given in the text, i.e. a rise in temperature causes the relay to operate. I therefore suggest that a relay with normally closed contacts be used instead of the type specified.—D. H. COX (Leeds, 17).

[In reference to this letter, the author has verified Mr Cox's remarks and observes that the sentence on page 761 beginning “When the temperature of the sensing transistor Tr1 rises . . .” should read “When the temperature of the sensing transistor Tr1 falls, . . .” A relay with normally closed contacts should, of course, be used.—Ed.]

NOT SUCH A GOOD THING

SIR.—At the risk of offending your Scots readers I feel I must, as a music-loving Englishman, protest the suggestion of your correspondent, Mr. J. F. Jameson (April P.W.) that you should publish a bagpipe amplifier design. However, his comments, apart from this, I agree with. Perhaps too much space is being devoted to musical applications of electronics in your pages. I feel there must be other outlets for your contributors who find insufficient inspiration in superhets and radio-grans.

Now that your guitar-playing readers have been catered for, how about getting back to conventional designs?—S. D. STEBBINGS (Bournemouth, Hampshire).

FOREIGN CORRESPONDENTS

SIR—I have just acquired a tape recorder and I would like to "tapespond" with readers of P.W. I am interested in learning Esperanto and so would especially welcome tape correspondence from readers with similar interests.—**M. L. VAN DE LINDE**, 2 Cowie Street, Sidwell, Port Elizabeth, South Africa.

SIR—I would like to hear from readers in any country, who have an interest in electronics and are of my own age—16. I will answer all letters received.—**MICHAEL ALKALAY**, 37 Prince Street Gardens, Cape Town, South Africa.

SIR—As a regular reader of P.W. and an enthusiast of transistor circuits, I would like a correspondent of my own age (14) in Great Britain. I will answer all correspondence.—**D. PURTON**, "Mount Pleasant", Pakenham, Victoria, Australia.

SIR—I am an enthusiast of amateur radio and I would like a correspondent in England having similar interests.—**M. MAHADEVA RAJU**, B.Sc., 4 Cubbon Pet, 12th Cross, Bangalore 2, South India.

SIR—I am interested in radio and electrical service technology and I would like to correspond with radio servicemen from any country. I will answer promptly all letters received.—**N. O. AZUBUINE**, P.O. Box 359, Port Harcourt, Nigeria.

Sir—I would be grateful if any reader could sell or loan me . . .

. . . the circuit and servicing manual of the Marconi receiver CR 150. If required I will return any data by registered mail.—**V. SAMMUT**, 158 Old Theatre Street, Valletta, Malta.

. . . the instruction manual for the Eddystone receiver model S.750.—**E. RAWSTRON**, 146 Partington Street, Castleton, Rochdale, Lancashire.

. . . the October and November 1960 issues of P.W.—**J. G. WOODLEY**, 6 Perry Avenue, Cullercoats, Northumberland.

. . . the February and April 1962 issues of P.W.—**J. F. MOYNIHAN**, 4 Leeson Park, Dublin, 6, Irish Republic.

. . . E. M. Squire's "Radio Questions and Answers", volume 2, Radio Receivers.—**Rev. E. A. MCCARTHY**, The Vicarage, East Ruston, Stalham, Norwich, Norfolk. **NOR 18Z**.

. . . the issues of P.W. dealing with the No. 19 Set.—**J. F. ROWLES**, 5 Tower Road, Southsea, Hampshire.

. . . the February 1961 issue of P.W.—**A. SLADI**, 12 Greywethers Avenue, Swindon, Wiltshire.

. . . information on the indicating unit type 221.—**S. FOWLER**, 66 Chiltern View Road, Uxbridge, Middlesex.

. . . the circuit of the Bendix aircraft receiver type RA 1B.—**D. W. HANNANT**, 6 Recreation Road, Gorleston, Great Yarmouth, Norfolk.

. . . the June 1961 and March 1963 issues of P.W.—**C. HARGIS**, "Loddington Grange," 13 Knole Road, Boscombe Bournemouth, Hampshire.

. . . the handbook or any information for the Halli-crafter BC669 transmitter/receiver, and the Bendix BC 433 radio compass.—**P. L. MOGFORD**, 27 Ynysmaerdy Road, Briton Ferry Neath, Glamorganshire.

. . . the July, August and September 1963 issues of P.W.—**M. J. CHELL**, 13 Hampden Road, Leicester.

. . . conversion data for the R1155 receiver.—**P. HUGHES**, 4 Ingram Road, Beechwood Gardens, Coventry, Warwickshire.

CORRIGENDA

The Malvern Tape Recorder

When this article was published in the July 1963 issue of PRACTICAL WIRELESS, a number of readers found difficulty in obtaining Mullard or G.E.C. ferrite cores LA1 and LA2 as specified. At that time it was not possible to recommend a supplier for these components. Now, however, we can inform readers that Henry's Radio keep a complete range in stock.

The Euphon

This article was published in the October 1963 issue of PRACTICAL WIRELESS and we bring to the attention of readers the following point which was omitted from the text and which, although perhaps obvious to experienced readers, might not have been apparent to any beginners attempting the construction.

Any other loudspeakers in operation should be cut out to obtain the required effect with the Euphon, the two it feeds *only* being alive.

Another observation which would best be pointed out is that if a high volume is required, the h.f. speaker must not be *too* small or it will not handle the volume. The l.f. speaker must always be considerably larger than the h.f. unit; but it must also be remembered that too large a base loud-speaker will emphasise bass more than is required.

Six-band T.R.F. Receiver

—continued from page 55

distance results. Local transmissions may overload V2, so the gain of V1 must then be reduced by means of VR1.


Quite a good degree of selectivity is obtainable when VR2 is adjusted to bring the detector near the oscillation point. If VR1 and VR3 are both at maximum volume, and VR2 is turned back, to reduce volume, tuning will be flat, and sensitivity poor. It is thus frequently necessary to keep VR2 carefully adjusted so that the detector is nearly oscillating, and reduce gain by VR1. In these circumstances, selectivity is surprisingly good, even for congested s.w. bands, and distant stations can be received.

Loose wiring, or a microphonic valve, can result in a ringing or continuous noise commencing whenever the regeneration control is critically adjusted. A screening can over V2 will help prevent this trouble.

If mains interference is bad, a r.f. choke may be wired from the telescopic aerial to chassis. By-pass capacitors (about 0.01 μ F) can also be wired in parallel with the mains transformer primary, or from mains leads to earth.

If desired, an external aerial tuner can be constructed. This consists of a suitable coil, with parallel capacitor, tunable to the band required. This tuner unit which is simply wired from aerial to chassis, will be found to increase the volume of weak transmissions, and help eliminate possible breakthrough of strong, local stations.

ADVERTISEMENT

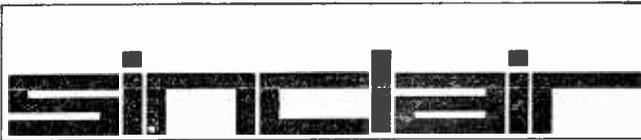

NEWS

No. 1

APRIL/MAY 1964

This is what Sinclair service means to you

WORLD LEADERSHIP

Within an amazingly short time, Sinclair Radionics has leapt forward to become a world-leader in its own specialised field of micro-electronic designs for the home constructor. The reasons for this are not hard to find, and even if, at first, they appear simple, they represent as much of a breakthrough in relations between customer and supplier as do the designs which we have introduced with such success.

SPECIALIST TEAMS

Our object is to produce micro-electronic transistor designs which are not simply interesting to build, but which are well ahead of anything offered by our competitors. They are also technically ahead of any available manufactured products. To achieve these standards, we employ our own highly qualified team of electronic engineers, and when they have contributed their share to a design, we "marry" it to the services of an industrial design group to ensure that our cases are both elegant and functionally right. Developments on these lines are going on all the time in the carefully planned Sinclair programme.

INSTRUCTIONS

Presentation of instructions is another Sinclair feature in which we naturally take pride. The experienced builder will readily recognise and appreciate the quality of the circuits shown in the Instructions. Equally important, however, is that *anyone* with or without technical knowledge can build a Sinclair design with 100% success from the word "Go". With the Micro-6, for example, building is actually proving easier than even we believed at first, and already there are thousands of these sets in use.

SATISFYING THE CUSTOMER

How about you, the customer? We insist on your being completely satisfied in all your dealings with us.

In fact, we have a special service department run solely to help and advise customers and to correct any errors in assembly which may have inadvertently been made. So you need never feel we will not be interested in your particular problem, no matter how slight it might appear to you. That we are genuinely willing and glad to be of help is something extra which even we cannot properly convey in the unique guarantee offered in our advertisements. We can only tell you of the hundreds of letters we receive every week from all over the world praising both our service and our designs. We have already published many in our previous ads. Here is another typical example which reached our office in February:—

"I very much enjoyed the four or five hours work necessary to complete it (Micro-6). It was easier to make than many bigger sets and when finished, worked at once. I consider the conception brilliant and I am very pleased with it. I found your instructions very well produced and easy to follow with no puzzles or omissions.

G. J., Nottingham."

More News next month!

FEATURED ON THE FOLLOWING PAGES

SINCLAIR MICRO-6
The smallest set in the world

SINCLAIR SLIMLINE
Designed for high-speed assembly

SINCLAIR MICRO INJECTOR PROBE
A better instrument for fault tracing

SINCLAIR AMPLIFIERS

SINCLAIR TRANSISTORS

CONSTRUCTIONAL BOOKS

Introducing

MIKE FARRAD

created specially for Sinclair Radionics by Ken Ward



YOU CAN BUILD THE WORLD'S SMALLEST SET IN A SINGLE EVENING!

SIZE ONLY

$1\frac{4}{5}$ x $1\frac{8}{10}$ x $\frac{1}{2}$ in.


REQUIRES NO
SPECIAL
BUILDING
EXPERIENCE
OR TOOLS

OUR UNIQUE GUARANTEE
PROTECTS YOU COMPLETELY

A WORLD-BEATING
BRITISH DESIGN

We knew that really efficient micro-size radio sets were always wanted; we knew how to get the very best out of modern transistors. After we had designed and field-tested the Micro-6 to our complete satisfaction, we released it for constructors only a few weeks ago. What even we hardly expected was the absolutely fantastic performance reports that are daily reaching us in ever growing numbers from all over the country (and abroad too). Range, selectivity, power and quality—the four essentials to any good radio are here in more than generous measure—and being able to build this set yourself will give you the greatest thrill in radio since the invention of the transistor.

SINCLAIR MICRO 6

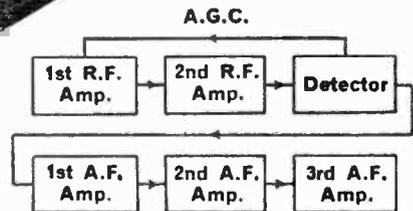

UNIQUE 6-STAGE CIRCUITRY

The key to the success of the Micro-6 is in its brilliantly developed circuitry brought to a stage that only a thorough understanding of transistor behaviour could ever hope to make possible. The result is that within this minute assembly you have a set actually better in performance than that of most transistor superhets many times larger and costlier.

ALL FOR
ONLY **59/6**


Price includes cost of all parts, elegant case, lightweight earpiece and plug, and instructions
MALLORY ZM312 Mercury Cells, 1/11 each

INSTRUCTIONS MANUAL

You will be delighted with the way in which this is presented. The illustrations are exceptionally easy to follow, and stage by stage details show just how simple this set is to build.



sinclair

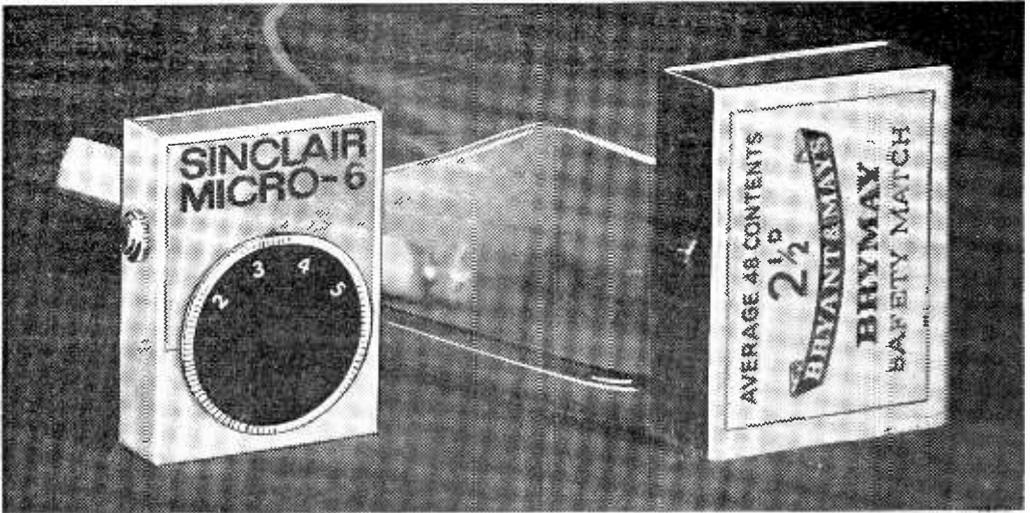


the world's smallest radio

PERFORMANCE BEYOND ALL EXPECTATION

TECHNICAL DESCRIPTION

The Micro-6 uses Micro-Alloy Transistors (MATs) in a completely new circuit comprising six stages. Two stages of R.F. amplification are followed by an efficient double-diode detector which drives a high gain three stage A.F. amplifier. Powerful A.G.C. is applied to the first R.F. stage to ensure fade-free reception of the most distant station, and tuning covers the entire medium waveband. This is widened out at the high frequency end to provide improved separation of Continental stations. The tiny ferrite rod aerial and earpiece socket were both specially designed for this set. This socket incorporates a switch which operates automatically on inserting the earpiece plug, and switches off when the plug is withdrawn. Listening is by means of the high-impedance lightweight earpiece provided. Quality of reproduction is outstandingly good.

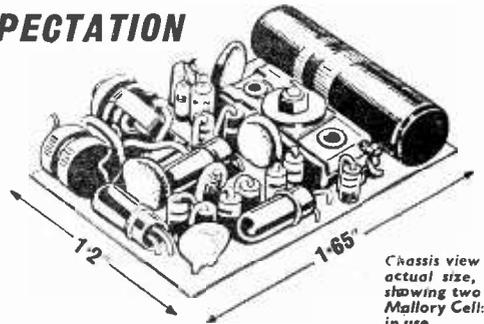

All parts necessary to build this set including case, lightweight earpiece and instructions manual come to

59/6

- IMMENSE POWER AND QUALITY
- PLAYS IN CAR, TRAIN, BUS, PLANE
- COMPLETELY SELF CONTAINED

UNIQUE SINCLAIR GUARANTEE

If you are not completely satisfied with your purchase (we are confident that you will be delighted) your full purchase price will be refunded instantly and without question

FULL SERVICE FACILITIES AVAILABLE TO ALL SINCLAIR CUSTOMERS

SINCLAIR RADIONICS LTD.
69 HISTON ROAD, CAMBRIDGE

If you do not wish to cut coupon from page, please mention "Practical Wireless," May issue, when ordering.

PROFESSIONALLY STYLED IN EVERY DETAIL

Outside — a compact, elegant case only 1 1/2 x 1 1/10 x 1/2 in. with positive drive vernier-action tuning dial, the whole trimmed with gold and black.

inside — beautifully designed printed circuit assembly, a master piece of compactness and electronic efficiency, yet building could not be easier.

MORE SINCLAIR DESIGNS ON NEXT PAGE

SINCLAIR RADIONICS LTD., 69 Histon Rd., Cambridge
Please send parts for.....Micro-6 Receiver(s) and
.....Mallory Mercury Cells at 1/11 each., for which I
enclose £.....s.....d.

NAME _____
ADDRESS _____

PW5

sinclair

DESIGNS THAT ARE YEARS AHEAD

The triumph of Sinclair designs is two-fold— firstly they embody advanced techniques using transistors and micro-miniature components in a fascinating variety of attractive applications; secondly they make it possible for anyone to build with assured ease and success and thereby enjoy using really advanced equipment. All designs are provided with well-presented instructions.

- FULL SERVICE FACILITIES AVAILABLE TO ALL SINCLAIR CUSTOMERS
- PROMPT ATTENTION TO ALL ORDERS

FIRST OF THE SINCLAIR MICRO-RECEIVERS

This is the set that gives you Europe in the palm of your hand. It has self-contained ferrite rod aerial and accommodation for a standard PPS battery, yet measures only 3 1/2" x 1 1/4" x 1/2" in. Tunes over the entire medium wave-band and can be used in cars, trains, buses. Using Sinclair MAT Transistors and special circuitry it provides remarkable power and quality—listening is by means of the lightweight earpiece provided. Building is particularly easy. The Slimline is contained within its neat royal blue and gold case, and is switched on by plugging in the earpiece.



SINCLAIR SLIMLINE

All parts inc. case, earpiece and instructions come in

49/6

SINCLAIR MICRO-AMPLIFIER AS USED IN LABORATORIES, RESEARCH ESTABLISHMENTS, ETC.



Actual size—it's smaller than a 3d piece!

28/6


inc. all parts and instructions.

This fantastically powerful amplifier, smaller than a 3d. piece, makes an excellent broadband R.F. amplifier. With a frequency response from 30 to 50,000 c/s. \pm 1 dB, and power gain of 80 dB (1,000,000 times) it can also be used as a sub-miniature hi-fi amplifier with an output suitable for any earpiece or even loudspeaker. Also makes an invaluable tool in the hands of the keen experimenter.

With MAT Transistors, micro-miniature quality components and micro-printed circuit, inc. instructions for building and many uses.

SINCLAIR MICRO-INJECTOR THE SMALLEST AND MOST EFFICIENT OF ALL SIGNAL INJECTORS

Here is the modern and efficient way to trace faults in valve and transistor audio and radio equipment of all kinds, and you can build it for yourself or buy it ready made. This precision sub-miniature instrument generates and injects a signal into any part of the equipment to be tested at a frequency from 1 Kc/s to 30 Mc/s. The 6d. standard battery which it uses will last for about 6 months. Building is extremely easy with the help of the instructions provided. In neat, well-made plastic case.

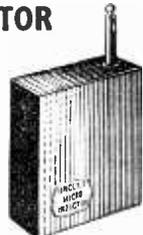

All parts, with case, probe and instructions.

27/6

Ready built and tested **32/6**


3 VALUABLE BOOKS FOR THE CONSTRUCTOR



- GENERAL—"22 Tested Circuits using Micro-Alloy Transistors" Post free **5/6**
- SHORT WAVES—"Tested Short Wave Receivers, Using MATs." Post free **5/6**
- S.W. & COMMUNICATIONS—"Tested Superhet Circuits for Short Wave Communication Receivers, using MATs." Post free **6/6**

SPECIAL PRICE FOR 3 TOGETHER **16/-**

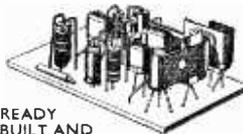SINCLAIR TR.5 QUALITY AMP WITH COMBINED PRE-AMP AND 1/2 WATT POWER AMPLIFIER



READY BUILT AND TESTED

Supplied ready with and tested, with application instructions.

59/6

For a perfectly clean 1/2 watt of audio power, even from very low inputs such as tape heads, modern P.U.s, mics, etc. 500mW transformerless output at 13 ohms: input sensitivity 0.5mV. Power gain 40 dB (100,000,000 times). Size 2 1/2 x 1 1/2 x 1/2 in. Frequency 50 c/s to 20Kc/s \pm 3 dB.

SINCLAIR GUARANTEED TRANSISTORS

- MAT 100 High gain low level 7/9
- MAT 101 Extra high gain, low level 8/6
- MAT 120 High gain, medium and high level 7/9
- MAT 121 Extra high gain, medium and high level 8/6
- ADT.140 FOR V.H.F., U.H.F., TV, etc. 16/-

UNIQUE SINCLAIR GUARANTEE

As described on previous page, this ensures your complete satisfaction with all you buy from Sinclair or your money is refunded without question.

FULL SERVICE FACILITIES AVAILABLE TO ALL SINCLAIR CUSTOMERS

SINCLAIR RADIONICS LTD.
69, HISTON ROAD, CAMBRIDGE

If you do not wish to cut output, please mention "Practical Wireless" Mag. when ordering.

SINCLAIR MICRO-6, SEE PRECEDING PAGES

SINCLAIR RADIONICS LTD., 69 Histon Rd., Cambr.dge

Please send.....

for which I enclose £.....s.....d.

NAME

ADDRESS

PV3

SERVICE SHEETS

SERVICE SHEETS. Radio and Television 3/6 post paid. VEST AND EMERY, 17 Halgarth St., Durham.

SERVICE SHEETS: Radio, TV, 5,000 models. List 1/-. S.A.E. Inquiries TELRAY, 11 Maudland Bank, Preston.

SERVICE SHEETS: Radio and TV, 4/- each. 1964 List now available, 1/6. All orders dispatched on day received. Also Manuals for sale and hire. List 1/-. S.A.E. please. SULTAN RADIO, 29 Church Road, Tunbridge Wells, Kent. Phone: 30523.

S.E.S. SERVICE SHEETS for all T.V., Radio and Tape Recorders, etc. List 1/6 plus S.A.E. SUN ELECTRICAL SERVICES, 38 St Georges Road, Hastings, Sussex.

SERVICE SHEETS for all makes of Radio and TV, 1925-1963. Prices from 1/- with free fault-finding guide. S.A.E. inquiries. Catalogue of 6,000 models. 1/6. 125 Radio/TV Sheets covering many popular models. 21/-. Valves, modern and obsolete. Radio/TV Books. S.A.E. lists. HAMILTON RADIO, Western Road, St. Leonards, Sussex.

SERVICE SHEETS also Current and Obsolete Valves for sale. JOHN GILBERT TELEVISION, 1b Shepherd's Bush Road, London, W.12. Phone: SHE 8441.

SERVICE SHEETS

4/- ea., plus postage.

We have the largest supply of Service Sheets for all makes and types of Radios, Televisions, Tape Recorders, etc. in the country, and can supply by return of post.

To obtain the Service Sheet you require, please complete the attached coupon:

From:

Name: _____

Address: _____

To S.P. DISTRIBUTORS

44 Old Bond St., London, W.1

Please supply Service Sheets for the following:

Make: _____

Model No.: _____ Radio/TV

Make: _____

Model No.: _____ Radio/TV

Make: _____

Model No.: _____ Radio/TV
I also require list of Service Sheets at 1/6.

I also require list of Manuals at 1/- (please delete items not applicable)

I enclose remittance of _____

MAIL ORDERS ONLY

SOUND RECORDING

A UNIQUE BUY! Recording Tape, top brand, 5 1/2 in., 1,200ft., 19/6; 7 in., 2,400ft. D.P., 28/6, P and P 1/6 per spool. Bargains in all sizes. S.A.E. for list. E. C. KINGSLY AND CO., 132 Tottenham Court Road, London, W.1. EUSTon 6500.

RATES: 7/3 per line or part thereof, average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisement must be prepaid and addressed to Advertisement Manager, "Practical Wireless," Tower House, Southampton St., London, W.C.2.

RECEIVERS & COMPONENTS

EXCEPTIONAL VALUE: Picture Tubes, brand new, Mazda 19in., CME 901, Mullard 19in. AW47-90/91, £6/10. carriage (insured) paid 12 £4/0/0; Mullard 23in., AW59/90, months guarantee. Note: All brand new. We also supply most other sizes completely regunned at £4/17/6, guaranteed 12 months. TOMLINS, 156 Lewisham Way, New Cross, SE14. TEL 2857.

"HEATHKITS" can now be seen in London and purchased on easy terms. Free brochure. DIRECT TV REPLACEMENTS LTD. Dept. PW7/9, 125 Hamilton Road, West Norwood, SE27. GIPsy Hill 6166.

TRANSISTORS

A.F. ALL TESTED BEFORE DISPATCH NEW-BRITISH, 8 for 10/- or 20 for £1. P. & P. 1/-.

PERSONAL EARPIECES with Lead and Plug. Low Impedance for Transistor Radios, 3/6 each. P. & P. 1/-.

TRANSISTOR TUNING UNITS Medium Wave—printed circuit. Ideal for Tape Recorders, Amplifiers, etc. Convert your Record Player to Radiogram. Works on 9 volt battery. 59/6. P. & P. 2/-.

625 LINE AERIALS, Indoor. 27/6. P. & P. 2/6.

Cash with Order on all Goods for prompt dispatch. Callers welcomed at

P.X. ELECTRONICS

221 NORTHFIELD AVENUE


EALING, LONDON, W.13.

Phone: EAL 5112

TRANSISTORS now half-price unmarked but tested packets of 16; unmarked untested packets of 40, duds suitable as diodes, packets of 80. All packets 10/- each, postage 1/-. Four packets post free C.W.O. K. R. WHISTON (Dept. PWT). New Mills, Stockport.

SPEAKER REPAIRS. Cones fitted. Satisfaction guaranteed. L. S. REPAIRS, Pluckley, Ashford, Kent.

GUITAR AMPLIFIERS WITH TREMOLO

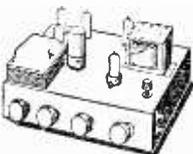

15 watt Valves ECC83, ECC83, EL84, EL84, EZ81. 30 watt Valves ECC83, ECC83, EL34, EL34, GZ34. Four Jack Inputs. Nine controls: four volume, master volume, bass, treble

tremolo speed, depth. Remote plug. 3 and 15 ohms outputs. 15 watt tremolo kit, £9.10.0; Factory built £12.10.0. 30 watt tremolo kit £12.10.0; Factory built £15.10.0.

LESS TREMOLO: 15 watt 2 input kit £8; Factory built (illus.) £10.10.0. 15 watt 4 input kit £8.10.0; Factory built £11. 30 watt 4 input kit £11.10.0; Factory built £14.

Add cart. 7/6 any amplifier. Send for free leaflet.

STROUD AUDIO
PAGANHILL LANE, STROUD, GLOS.

RECEIVERS & COMPONENTS

No. 3 BUMPER PARCEL

- 6 Assorted, ex-government valves.
- 6 Wander plug sockets—sorry no plugs.
- 6 Miscellaneous items.
- 1 Electro magnetic counter 19" mp. per sec.
- 3 Assorted Mains Dropper Resistances.
- 3 Yards of insulating sleeving.
- 1 Post Office telephone fuse box with fuses.
- 12 Assorted car bulbs, 6 volt and 12 volt.
- 3 M.E.S. panel lamp bulbs, 6 volt.
- 12 Sheets of carbon paper.
- 50 Tubular condensers assorted.
- 12 High stability resistors, assorted.
- 12 Assorted valve bases.
- 6 Valve retainers.
- 1 Clockwork timing mechanism intended for: blowing up rockets?
- 1 12 Volt vibrator motor, 4 pin.
- 24 Red bezels for panel lamps.
- 1 Altitude switch in case.
- 1 Speaker, 3 ohm.
- 2 Crystal adaptors.
- 4 doz. Cartridge fuses.
- 12 Assorted Coils, Inductances, Chokes.
- 20/- Post Free, Two Parcels for 35/-.

19" RACK FITTING CABINET. 34" high by 21" deep with telescopic drawer slides. Louvred sides, back and top. Brand new Swedish make, £4.0.0 only, plus B.R.S. delivery.

ECR Tube with Screen and Base with data, 25/-.

5UP7 Tube with Screen and Base, with data, 30/-.

20ft. Steel Telescopic Mast, 50/-.

RECEPTION SET R220 MK 2

14-valve double superhet crystal controlled. From 60 to 100 meg. according to crystal used. Built-in stabilised P.P. internal speaker phone output. Brand new. Supplied with circuit and modification details. For 72-144 meg. etc.

£3.10.0 Post Free.

Separate Circuit and Modification kit, 25/- Post Free.

Copper Laminate Board, single or double sided, 5/- per square foot panels, either type 3 ft. by 4 ft. 33/-.

High Stab Resistors, 5% 6d., 2% 9d., 1% 1/-, Every six packed in 7-compartment linen finish component box. Unmarked.

Assorted Resistors, 50 carbon plus 50 high stab. My choice 7/6.

Reflected Power Meter or Standing Wave Ratio Indicator Unit, and other kit including 500 micro amp. meters, plugs, sockets, leads, switch, circuit, instructions, 144 meg. Complete 35/-.

144 meg. Harmonic Filter with all plugs, sockets, leads. 25/-.

Speakers, 3 ohm P.M. 5in. 5/-, 6in. 6/-, 7 x 4in. 7/-, 8in. 8/-, 10in. 12/6.

Trade enquiries invited for large quantity OC201 Transistors. Printed Circuit Board, 50 mid at 70 volts Sub. Min. Condensers.

U.K. ONLY.

E. R. NICHOLLS


Mail Order and Retail Shop:
46 LOWFIELD ROAD
off SHAW HEATH, STOCKPORT
CHESHIRE.

RECEIVERS & COMPONENTS
(continued)

A.1. POST FREE BARGAINS. Guaranteed set tested valves EF80, EB91, 10P1. 9d. each, 3 for 1/6. L36, ECL80, 2. each. PY31, PZ30, 3/4. PY80, PY82 3/3, ECC81, ECC82, 3/6. PL82 3 9. B36. PCF80, PL83, 20P1. 4. EB780, N37, 4/3. PL33, 4/6. PL81, 4/9. 30F5, 6/1. 53K4 6/6. 185B17/1. Send for full list of cheap valves. A.1. RADIO COMPONENTS, 14 The Borough, Canterbury, Kent.

FANTASTIC BARGAINS! Condensers, Miniature Paper, 7/6d. per 100. Resistors, assorted, 100 cards of 10 for £2/10/-. Transistors, Output, NKT 124/5, 6 for 40/-. Texas transistors, NPN type, 28C17, 4W, only 5/1 each. Pocket containing: 3 AF17, 1 OC81, 2OC71, 1 AC127, 1 Y21. Give-away priced! Complete set of transistors for transformerless line-up! £1 only. Sub-miniature Crystal diodes 1/- each. Miniature earphones complete with plug and lead 2/6 each. Multimeters, a.c. volts and current, d.c. volts and current, Ohms. Complete with battery and leads. Handy pocket size, 39/6 each. 4-transistor printed-circuit amplifiers 39/6 each. Transistor Electrolytics, 1u.f., 2u.f., 4u.f., 8u.f., 10u.f., 16u.f., 25u.f., 32u.f., -all 15V; 64u.f., -10V. All 1/6 each. Acos microphones Mic 40-19/6 only. Telephone tape pick-ups 9/- each. Tape Recorders, complete with Batteries, Tape, Spare Spool, Micro phone, Earphone for monitoring. Lid etc. £4/19/6. G. F. MILLWARD, 17 Peel Close, Draxton Bassett, Staffs. Tel: Tamworth 2321.

Wheatstone Bridge

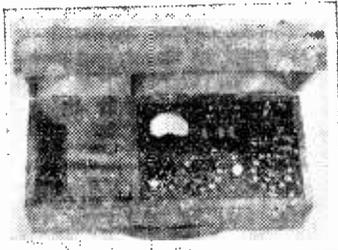

Centre Zero Galvanometer scaled 20-0-20 21in. movement 2.6mA FSD, 3 stud switch controls 0-10, 0-100 ohms and 0-Inf. Complete in carrying case with instructions 45/- Post 3/-.

MARCONI CANADIAN No. 52. As previously advertised, till a number left. Used less case, complete for 15/20 A.C. mains and 12V D.C. Fully tested. Only £9-10-0. Carr. 1/-.

POWER UNIT, Type ZER2. Designed for the above receiver, 52/6, carr. 5/- Moving Coil Headphones, chamols padded with lead and plus, 15/- Post 2/6.

WS. NO19 MK3 TXRC 2.4 Mc/s with economy power pack, 12/24V D.C., 50/-, Carr. 25/- Set only 55/-, Carr. 15/- All parts available

A. J. THOMPSON

'FILING LODGE'
CODICOTE, HITCHIN, HERTS.

Phone: Codicote 242

RECEIVERS & COMPONENTS
(continued)

STOCK CLEARANCE. Valves, Condensers, Resistors, Transformers. Mail only. Bargain lists, 98 Greenway Avenue, E.17.



RECEIVERS

V.H.F. RECEIVERS, P 104, 100-150Mc/s. 13 valves, B.F.O., A.G.C., R.P. and L.F. Gains Tuning Meter. In good condition, £3/10/-. carriage 15/- Matching 230V a.c. power unit, £2 5/-, carriage 10/- Receiver Section of Walkie-Talkie 68T, 3-6Mc/s, contains 4 valves, 3 of ARP12, 1 AR8, 25/- each post paid. Spare valves 1/- each post 3d. Part-stripped matching transmitter chassis, contains many useful parts, coils, condensers, switches, resistors etc. 10/- post paid. 1mA 2in. round meter, 8/6 post: 1/6. Tested and working. Power units, 12V d.c. input for WS19 or WS22, good clean condition, 25/-, either type, carriage paid.



DIRECT TV REPLACEMENTS LTD., largest stockists of TV Components in the U.K. Line Output Transformers, Frame Output Transformers, Deflector Coils for most makes. Official sole suppliers for many set makers. Same Day DieBatch Service. Terms C.O.D. or C.W.O. Send S.A.E. For quotes, Day and Night Telephone GIPSY Hill 6166, 126 Hamilton Road, West Norwood, SE27.

V.H.F. TX-Rx B44 Mk. II

60-65 Mc/s, using 14 midgeet valves (EP61 series). Rx is a double-superhet, internal speaker 6in., also 1/2 volt power unit, voltage meter on front panel. Crystal controlled, all alloy chassis. BRAND NEW with handbook at the low price of 55/-, carr. 7/6. Alloy case 10/- extra. EXPORT ENQUIRIES WELCOME.

NOTE THE NEW ADDRESS FOR LEEDS ONLY WALK AROUND GOV. SURPLUS RADIO SHOP

J. T. SUPPLY

(Dept. H)
150 Meadow Lane, Leeds 11

FOR SALE

240th ELECTRIC POWER ANYWHERE
ANYTIME from 12th CAR BATTERY
with the AMERICAN DYNAMOTOR UNIT
INPUT 12V, OUTPUT 200-250V at 150 to 220 watts
Perfect for TELEVISION, POWER TOOLS and all universal A.C. ELECTRICAL EQUIPMENT, gives wonderful results. Price ONLY 6/- + 1/- carriage
Send stamped envelope for full illustrated details
SCIENTIFIC PRODUCTS, CLEVELAND, OHIO

FOR SALE
(continued)

MORSE EASY!

The famous RHYTHM RECORDED COURSE cuts practice time down to an absolute minimum!
One student, aged 20, took only 13 DAYS and another, aged 71, took 6 WEEKS to obtain a G.P.O. pass certificate. If you wish to read Morse easily and naturally enclose 6d. in stamps please for full explanatory booklet.
To GCCHS 45 GREEN LANE FURLEY, SURREY

WORLD'S SMALLEST

BABYVAR 3-GANG. Variable capacitor size 1in. square by 2in. deep. Will out perform the largest air spaced variable condenser. Ideal for building medium and long wave match box radios. 17/6. P. & P. 9d.
T.S.L. 500 of SINGLE GANG. Tuning capacitor size 1in. sq. x 1in. deep. 18/6. P. & P. 9d. Both complete with trimmers, circuits and full data.
P.S.L. 1000, 8XNOB. To fit Babyvar cond. Back and Gold styling. 14in. dia. 1/1. P. & P. 6d.
Send 3d. stamp for detailed lists.
ELECTRON SUPPLIES (DARVEN).
Dept. B, 46 Hindley Street, DARVEN, Lancs.

SEND S.A.E. for latest lists of RADIO gear etc. for disposal. MAZEL RADIO SERVICE STATION, (Dept. ML), 124/138 London Rd, Manchester 11.

TAKE YOUR PICK 2/6 ANY PACK FOR:-

NEW - ASSORTED - COMPONENTS (Pre-f Value)

- | | |
|---------------------------|---------------------|
| 20 Carbon Resistors | 35 Springs |
| 8 Trimmers, Stamp type | 12 Knobs Rad/TV |
| 15 Ceramic Condensers | 15 Tag Strips |
| 250 Sleeves & Brackets | 10 Valve Holders |
| 550 sq in Insulating Bird | 15 Socket panels |
| 24 Clamps & Brackets | 15 Coil Formers |
| 6 Equipment Handles | 3 Radio Coils |
| 8 Wafers w w Bluecuts | 6 R.F. Chokes |
| 8 Adaptor I.P.F. Switches | 3 Potentiometers |
| 3 Dropper Resistors | 16 Valve Top Caps |
| 240 sq in. Resin Cloth | 60ft. sleeving |
| 12 Paper Tube Conds | 7 Metalpack cond |
| 72 800 Tap. Resps | 3 1/2 GP Sw Kits |
| 200 500k. A.M.P. Switches | 27 Cond Clips |
| 1 Gram Mounting Kit | 75 Feat Washer |
| 4 1/2 D.C. Brushes | 10 Fuse Holders |
| 11 Indes. (Rectets) | 40 Mounted Tags |
| 6 17.5V. Valve Fans | 12 Equipment Feet |
| 45ft Pre-tie Compound | 10 Plug |
| 3 2A 2-pin sw Sockets | 6 T.V. Coils |
| 6 Sub-min Trimmers | 40 Cable Cleats |
| 24 Loudspeaker Ganes | 15 Pch/Btn Knobs |
| 12 Anti-vibration Mounts | 12 R.F. Switches |
| 200 500k. A.M.P. Switches | 1 Slider Switch |
| 60 Nuts/ Bolts/ Washers | 6 Motorcar Bulbs |
| 3 Erectory Coils | 72 Terminal Cover |
| 3 Block Paper Conds | 3 Printed Circuits |
| 1 T.V. Tuner Chassis | 1 Twin Ion Traj |
| 1 1/2 Wave Rectifier | 10 8ES Lamp/Phil |
| 1 Plastering Trowel | 24 sq.in. felt Tape |

New & Used Govt. Equipment, etc.
New Generator No. 2, 21B. Modulator No. 28, 211. Test Set Mic Receiver No. 4, 227. 4 Valve Modulators, 11/6. A.C./D.C. Power Units, 11/6. No. 19 Control Units, 5/6. Dimmers, 7/6. 7 TV Pots 7/6. 8 Probe Generators, 30/- 12a Main Switches, 7/6. 6V 6-pin Motors, 7/6. 6V 400k Accentiometers, 25/- Wide-Band Amplifiers, 30/-, Radio Cabinets, 19/- EP50 Valves 1/3. Regret all V/Volts meters SOLD. Large range of Radar Equipment to callers only. Please send small amount P. & P. Cost, 1/-, List S.A.E. FREE—Foreign Stamps if requested with orders. (See advts in W/W P/T, etc. for other lines.)

ALBATROSS ENGINEERING CO.

Dept. FWS 78-80 HIGH STREET, GOSBERTON SPALDING, Lincs. (Tel. Gos 458)

(continued overleaf)

FOR SALE
(continued)

PRINTED CIRCUIT BOARD, 6in. x 6 1/2in. 3 for 9/6. 1,000 item list 3d. **ROGERS**, 31 Nelson St., Southport.

FANTASTIC BARGAIN OFFER?



ELECTRIC SOLDERING IRON

Lightweight Pistol Grip handle 40 watt. 240/250v. AC. Solid copper bit. Detachable handle forms cover for iron when not in use. With 4ft. Safety 3-core flex. Indispensable for every home handyman. A boon to model makers and a necessity for every wireless enthusiast. Offered to you at this new amazing price.

ONLY
9/6

P. & P. 1/-

C. H. SERVICE, Dept. P.W.
Lusted Hall Lane, Tatsfield, Kent.

Lapel type microphones 7/6
Transistor personal earphones . . . 5/-
Reclaimed 6in. elliptical speakers . 6/-
T/V slot meters 35/-
Cossor mini-scope £8
Call or write:

HOLMES-SMITH ELECTRONICS.
195 New Road,
Portsmouth,
Hants.

FOR SALE
(continued)

EXCEPTIONAL Transistor Portable Tape Recorder, value £5/19/6, complete with crystal microphone, earphone, spools, tape, batteries, instructions, presentation box (extra tapes 100ft. 4/6). Ideal gift. £5/19/6. Satisfaction guaranteed. Postage, packing 2/6. **TOMLINS**, 156 Lewisham Way, New Cross, SE14.

The Wonderful 'DATROLA'

"DATROLA" transistor Electronic ORGAN, 2 octave. Complete and ready to play, with instructions and music. Size 14 1/2 x 5 in.



Special Offer only £4.19.8 post free. Ideal present for all ages. Can be played anywhere (battery operated). Instructional aid to music, will give endless hours of amusement.

DATA ELECTRONICS LTD.
6 Hillside Gardens, Edgware, Middx.

WANTED

WANTED: TEST GEAR. Meters Valves, Components, Communication Sets Amplifiers. Letters only. **HUGGETT'S LTD.**, 2-4 Pawson's Road, West Croydon, Surrey.

WANTED VALVES ONLY

Must be new and boxed
Payment by return.

WILLIAM CARVIS LTD.
103 North Street, Leeds 7

A PROMPT CASH OFFER for your surplus brand new Valves and Transistors. **R.H.S.**, Beverley House, Mannville Terrace, Bradford 7.

WE BUY new valves and transistors, amplifiers, short wave receivers and components, etc. **A.D.A. MANUFACTURING CO.**, 116 Alfreton Road, Nottingham.

NEW VALVES WANTED

Any type, or quantity

CASH PAID

R.S.T. Valve Mail Order Co.
211A Streatham Road
Mitcham, Surrey
Telephone: **MITCHAM 6202**

WANTED Service Sheets and Manuals. No quantity too large, highest prices paid. **SULTAN RADIO**, 29 Church Road, Tunbridge Wells, Kent.

MISCELLANEOUS

PLASTICS MOULDINGS without tool cost. Send your drawing or sample for our immediate quotation, minimum quantities 5,000, to: **BRUCE & PARTNERS**, 4 Bramleys, Rochford.

ELECTRONIC MUSIC?

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes! It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swing

Write NOW for free leaflet and further details to **C. & S.**, 20 Maude Street, Darlington, Durham. Send 2fd. stamp.

BOOKS & PUBLICATIONS

FIND TV SET TROUBLES IN MINUTES from the great book *The Principles of TV Receiver Servicing*. 10/6 all book houses and radio wholesalers. If not in stock from Dept. B Secretary, 32 Kidmore Road, Caversham, Reading, Berks.

AUDIO, America's foremost journal. Year's subscription 43/-, specimen copy 4/-. All American radio journals supplied—list free. **WILLEN** (Dept. 40), 61a Broadway, London, E15.

BUSINESS OPPORTUNITIES

IF YOU are a Self-employed TV Service Engineer wishing to increase your profits by at least 25% and receive free technical information, send s.a.e. for details to Box No. 55.

SITUATIONS VACANT

RADIO AND TV Exams, and courses by Britain's finest Home-study School. Coaching for **Brit.I.R.E.**, City and Guilds, Amateur's Licence, **R.T.E.B.**, P.M.G. Cert., etc. **FREE** brochure from **BRITISH NATIONAL RADIO SCHOOL**, Russell Street, Reading.

TV AND RADIO, **A.M.Brit.I.R.E.**, City and Guilds, **R.T.E.B. Cert.**, etc. on "no pass—no fee" terms. Over 95% successes. For details of exams and courses (including practical apparatus) in all branches of Radio TV and Electronics write for 148-page handbook—free. **B.I.E.T.** (Dept. 242G), 29 Wright's Lane, London, W8.

A.M.I. Mech.E., **A.M.I. Brit. I.R.E.** City and Guilds. **G.C.E.**, etc., brings high pay and security. "No pass—no pay" terms. Over 95% successes. For details of exams, and courses in all branches of Engineering, Building, Electronics, etc., write for 148-page handbook—free. **B.I.E.T.** (Dept. 242B), 29 Wright's Lane, London, W8.

ROYAL NAVAL RESERVE

Men between the ages of 16 and 26 and ex-servicemen with previous communication training up to the age of 40 are invited to train in their spare time as Radio and Tactical Communication Operators in the Royal Naval Reserve.

For details apply:
ADMIRAL COMANDING RESERVES
Empress State Building, London, S.W.5
or ask at your nearest Royal Naval Careers Office.

GUARANTEED TRANSISTORS

2/- each, XA101, XA102, XB103, XB104, XA112, OC430.

3/6 each, GET16, GET20, GET 884, GET873, 250mW ZENER DIODES 4 volts to 22 volts, OC44, OC45, OC71, OC81D, OC81.

4/- each, OC170, OC171, AF117, XU611, GET671, GET672, GET 673, GET691, GET692, GET693, GET694, GET884.

5/- each, OC309, OC320, OC703, OC800, OC46, OC47, ORP60, and many more.

LARGE STOCKS of Mullard, Mazda, Bush, G.E.C., Impex, A.E.I.

Send 3d. stamp for full list.

B.W. CURSONS

78 BROAD STREET
CANTERBURY, KENT

METAL WORK

Cases, Chassis, Frames, etc..

anything in metal. Send your drawings for quotation. One-off's with pleasure. Trade enquiries welcomed.

Stove enamelled any professional finish.

Moss Watson

40 MOUNT PLEASANT STREET OLDHAM, LANCs. MAIN 9400

METAL WORK. All types cabinets, crassis, racks, etc., to your specifications. PHILPOTTS METAL WORKS LTD., Chapman St., Loughborough.

EDUCATIONAL

BECOME "TECHNICALLY QUALIFIED" in your spare time. Guaranteed Diploma and Exam. Home-study Courses in Radio, TV Servicing and Maintenance. R.T.E.B., City and Guilds, etc. Highly Informative 120-page Guide - FREE. CHAMBERS COLLEGE Dept. 3637, 148 Holborn London, EC1.

RADIO OFFICERS see the world. Sea-going and shore appointments. Our many recent successes provide additional trainee vacancies during 1964. Day and Boarding students. Grants and Scholarships available. Stamp for Prospectus. Wireless College, Colwyn Bay.

THE INCORPORATED PRACTITIONERS in Radio & Electronics (I.P.R.E.) Ltd., Membership Condition booklet 1/- Sample copy of I.P.R.E. official Journal 2/- post free. Dept B Secretary 32 Kidmore Road, Caversham, Reading, Berks.

Radio Television & Electronics

Learn at home with the world's largest home study organisation, Brit.I.R.E.; City & Guilds; R.T.E.B., etc. Also Practical Courses with equipment.

All books supplied. Write for FREE prospectus stating subject to

I.C.S.

(Dept. 541), Intertext House, Parkgate Road, London, S.W.11

RES/CAP. BRIDGE 39/6

Checks all types of resistors, condensers & RANGES

Built in 1 hour. Direct reading READY CALIBRATED Stamp for details of this and other kits.

RADIO MAIL (Dept. PX)

Raleigh Mews, Raleigh Street, Nottingham

STOP! LOOK!

TRANSISTORS from 1/3

GREEN SPOTS 1/3 or 3 for 3/3. RED SPOTS down to 1/6 or 3 for 4/-. WHITE SPOTS down to 2/- or 3 for 5/3. MICRO-ALLOY TRANSISTORS MAT100 7/9, 101 8/6, 120 7/9, 121 8/6, ADT140 15/-. EARPIECES with Lead and Plug. Crystal Type, 5/-; Low Imp., 4/-. TRANSISTOR HOLDERS 3 or 5 pin, 1/-. WIRELESS WORLD VALVE DATA 6/-. REACTION CONDENSERS .0001 3/-. .0003 3/9, .0005 4/3. J. B. DILECONS .0001, .0003, .0005 all 4/9 each.

REPANCO COMPONENTS

DRX1 Crystal Set Coils with Circuit 3/-. DRR2 Dual Range Coil with Reaction Winding and Circuit, 4/6. FR2 Ferrite Rod Aerial, 12/6. CHI R.F. Chokes, 2/6. TRANSISTOR TRANSFORMERS TT49 5/-. TT46 6/-. TT45 6/-. TT23 22/6, TT24 22/6. MULLARD TRANSISTORS AND DIODES OC70 6/6, OC71 6/6, OC44 8/3, OC45 8/-. OC72 8/-. OC81 8/-. OC25 12/-. AF102 27/6, AF114 11/-. AF115 10/6, AF116 10/6, AF117 9/6, AF124 11/-. AF125 10/6, AF126 10/6, AF127 9/6, OC170 8/6, OC171 9/6, OA70 3/-. OA81 3/-. ALL SENT POST FREE IN U.K. by

PETHERICKS' RADIO SUPPLIES

22 HIGH STREET BIDEFORD, N. DEVON

Tel: Bideford 1217

NEW VALVES!

Guaranteed Set Tested 24-HOUR SERVICE

Table listing various vacuum tube types and their prices, including 1R5, 1S5, 1T3, 354, 3V4, DAF91, DF91, etc.

Postage 6d. per valve extra. Any Parcel Insured Against Damage in Transit 6d. extra. Any C.O.D. Parcel 4/3 extra. Office address, no callers.

GERALD BERNARD 83 OSBALDESTON ROAD, STOKES NEWINGTON, LONDON, N.15

HERE'S A LOW COST WAY TO GET INTO T.V. SERVICING FAST!

If you are a man who wants to get ahead in television, you will probably be interested in this new revolutionary type television training programme now being introduced for the first time. Knowing that early success will usually spur a man on to greater achievement you learn how to make the easiest T.V. repairs first. Since the easiest T.V. repairs are the ones most often found on service calls, you are ready to make money right after the first lesson. Then as your progress you will discover how to handle every kind of trouble found in all makes of T.V. set!

Here for example are some of the items covered in the course:

- 1. Simple adjustments to correct poor pictures. 2. Circuit faults indicated by a poor pattern. 3. Finding bad valves by observing picture faults. 4. Antenna principles and practices. 5. Facts about the T.V. signal to help you in repair work. 6. All about Cathode Ray tubes. 7. How to tell what is at fault. 8. Explanation of television circuits. 9. U.H.F. converters and tuners. 10. Television test equipment and alignment. 11. Advanced trouble shooting by picture analysis.

This is a real home study course that has been bound into one giant 3 x 11 in. 192 page manual to reduce cost.

Compares favourably with some courses costing very much more! By creating a mass market through large volume sales and eliminating individual letter writing we are able to pass on these savings directly to you!

The course features over 325 different line drawings, circuits, servicing charts and illustrations to simplify the text and make your study more enjoyable. Soon you will be well on your way to becoming a first-class television repair technician!

YOU TAKE NO CHANCES WHEN YOU DEAL WITH SIM-TECH

You must be convinced that this is the best value you have ever seen in television training, otherwise you can return the course (or have your money refunded if sent with order) after you have examined it in your own home for a period of seven full days. The price? Only 36/- per course, plus postage and packing. 1/6.

Free 71-page book on Television Faults will be included if you send cash with order.

FREE TRIAL OFFER

Terms only 5/- per week if you wish

To SIM-TECH BOOK COMPANY Dept. BT.C West End, Southampton, Hants.

Please send your Television Course for a full seven days' free trial. If not delighted I may return the course post-paid without further obligation on my part. Otherwise I will pay cash price of 37/6 or 4/- weekly until 37/6 plus 2/6 service charge, total 40/- is paid.

Tick here if enclosing full price of 37/6. (Same 7-day money back guarantee). NOTE: Customers who send cash with order get in addition a 71-page book on TELEVISION FAULTS. Overseas customers please send full amount including Ireland.

Name

Address

City..... County.....

ULTRA VIOLET BULBS

Easy to use source of UV for dozens of practical and experimental uses. 12 volt 36 watt AC/DC SBC 6/6. P. & P. 1/- 12 volt 60 watt AC/DC SBC 8/6. P. & P. 1/- Transformer to suit the above: Input 200-240 A.C. Output 12 Volt A.C. 36 watt. 16/6. P. & P. 2/6. Input 200-240 A.C. 12 volt A.C. 50 watt. 22/6. P. & P. 3/6. Set of 4 colours FLUORESCENT Paint. Orange, Yellow, Green and Red, in 1 oz. tins. Ideal for use with the above Ultra Violet Bulbs. 9/6. P. & P. 1/6.

BUILD AN EFFICIENT STROBE UNIT FOR ONLY 37/6.

The ideal instrument for workshop, lab. or factory. This wonderful device enables you to "freeze" motion and examine moving parts as stationary. We supply a simple circuit diagram and all electrical parts including the NSP2 Strobe tube which will enable you to easily and quickly construct a unit for infinite variety of speeds, from 1 flash in several seconds to several thousands per minute. New modified circuits bring price down to 37/6 plus 3/- P. & P. NSP2 CV7296 STROBOTRON FLASH-TUBE made by Philips brand new, I.O. base. Price 15/- P. & P. 1/-.

MAGNETIC COUNTERS 10 IMPULSES PER SECOND

High Speed Magnetic Counter, for impulses per second. Type 100D 4.1 ohm coil. 3-6V. D.C. operation. Type 100B 2,300 ohm coil. 36-48V. D.C. operation. Either type, 15/-, plus P. & P. 1/6.



VARIABLE VOLTAGE TRANSFORMER £4-10-0

Post Paid. Input 230 v. A.C. Output 0-260 v. at 1 amp., tully shrouded, new. Also available 2.5, 5, 8, 10, 12 and 20 amp. Write for details.

SIEMENS H.S. H.I.L.A. Very latest type, sealed. H98E. 1,700 ohms plus 1,700 ohms single C/O contacts. Price 16/6 each, plus 1/- P. & P.

SLIDER RESISTANCES Geared Drive, New.

1.2 ohm 14 amp. 27/6
36 ohm 6.5 to 2.8 amp., tapered windings, geared drive (less knob) 45/-
7.5 ohm 2 amp. 37/6
200 ohm 1.25 amp. 37/6
P. & P. 3/6.



12 v. D.C. Reversible Motor with tremendous power weight ratio. 3 position switch. Weight 2.1 ounces. Size 1 1/2 x 1 1/2 in. dia. Speed 7,000 r.p.m. Self lubricating. 15/-, plus 1/- P. & P.

230 VOLT A.C. GEARED MOTORS. Type B16G 80 r.p.m., .26 lb. inch, £11.96. P.P. 2/-. Type D16G 5 r.p.m., 1.7 lb. inch, £22.6. P. & P. 2/6. Type D16G 13 r.p.m., 1.45 lb. inch, £2.12.6. P.P. 2/6.

LIGHT SENSITIVE SWITCH
Kit of parts, including ORP, 12 Cadmium Sulphide Photo cell, Relay, Transistor and Circuit, etc., price 25/- plus 2/6 P. & P. ORP, 12 including circuit, 10/6 each plus 1/- P. & P.

MINIATURE UNISELECTOR SWITCH

3 banks of 11 position plus homing bank, 40 ohm coil, 24 position operation. Ex-equipment. Individually tested. 22/6, plus 2/6 P. & P.



TRANSISTORS

OC41	7/-	OC84*	10/-	GET573*	12/6
OC45*	5/-	OC139	12/-	2G110	17/6
OC71	5/-	OC140	19/-	2N458	20/6
OC72*	7/-	OC71	10/6	SB345	7/6
OC73	6/-	OC200	10/6	AC10	14/6
OC75	7/-	OC201	21/6	AF114	11/6
OC78	6/-	OC203	14/-	AF115	10/6
OC77	9/-	GET104	6/-	AF116	10/6
OC81*	8/-	GET105	10/-	AF117	9/6

* Available in matched pairs

SERVICE TRADING CO.

All Mail Orders also callers, 47-49 High Street, Kingston on Thames Tel: KINGSTON 9450

Personal callers only

9 Little Newport Street, London W.C.2 (off Leicester Square) Tel: GERRARD 0576

PADGETTS RADIO STORES

OLD TOWN HALL, KNOWLER HILL, LIVERMIDLE, YORKS. Telephone: Cleckheaton 2866

Tube Unit Type 7301. With two EF32, three EF91, five 6X4, two CV4025, one 6V8GT. Also Tube Type VCRX263 with mu-metal screen. Fitted with dimmer unit and lamps Part 7302. A fine unit for only 35/-. In good condition. Carr. B.R.S. 8/-. No details on this unit.

New Boxed Drive Unit Type 114. Complete with 5U4, 6L6, VS210 two EF50, one VR92 valves. Also 25 cycle tuning fork. Housed in very nice case. 15/-, Carr. B.R.S. 7/6.

New 12in. Speaker with Built-in Tweeter, 28/6, 3 or 15 ohms. Post free. Army Set, Type 19. Receiver side bench tested on phones. Sets as new. 50/- Clean condition. 32/-. Carriase B.R.S. 10/-. Simple drawing with each set explaining pin connections for mains operated power pack.

New Valves Ex Units, POST FREE. 6K7 1/6 each, doz. 12/-. 6X3 2/6 each, doz. 22/-. CV5 2/6 each, doz. 22/-. 807 U.S.A. 6/- PP3250 (PX4) 5/-. AC2PEN (PENA4) 2/6. 5U4 3/-. 6V8GT 4/6. EF91 1/9. EL91 1/9. 6F6 2/-. 5Z4 5/6. 5Y3 4/6. 6X5 4/6. EF50 1/7. 6J7 doz. ARP12 1/6. 6 for 5/6. box of 50 18/-. KT92 2/-. ART12 2/-. ART14 2/-. APP37 2/-. AR8 2/-. IT4 2/-. G54, new boxed, 1/3. 13 Channel TV Sets, 14in. untested 30/-. carr. 10/-. Well packed, sent at owner's risk. T.V. Tubes. Completely rebuilt and re-tested. 12 months guarantee. Sizes up to 17in. Special trade price of 75/-, Carr. and Ins. 7/6.

RECLAIMED TUBES

Mullard 12 and 14. Mazda CRM141-2 at 17/-. carr. 7/6. Mullard and Mazda 17in., 30/6. 6 months guarantee.

P.M. Speakers, Guaranteed ex T.V. Sets. 8in. round, 6 x 4in. Rola and Plessey, Philips 5in. round, all at 3/- each. Post 2/-, 6 for 20/-, post paid. Goodman 4 x 4in., 5/-, post 2/-, 6 for 20/-, post paid. 8 in. round, 6/-, post 2/-.

Valves Removed from T.V. Sets. Tested on a Mullard Valve Tester and are 100% as new. Three months' unconditional guarantee. POST FREE.

ECL80	2/-	20L1	3/-	PL33	4/-
ECC82	2/-	20L1	5/-	PL88	8/-
EY51	2/6	20P3	5/-	PY80	5/-
EBF80	4/8	20P4	8/6	PY81	4/-
EB91	9/4	20P1	5/-	PY82	5/-
EF91	9/6	20P2	5/-	PCF80	4/6
6SM7	2/6	U801	8/6	PCC84	4/6
6F1	1/-	U261	5/-	B36	4/-
6F11	5/-	U282	5/-	N37	5/-
6F15	5/-	U329	5/-	6U4	5/-
6L6D20	5/-	KT36	5/-	6P25	3/6
10C9	1/-	PL81	5/-	6K25	5/-
10F1	1/-	PL82	5/-	6P28	3/6
10P13	5/-	PL83	5/-	PZ30	5/-
10P14	5/-	PL83	5/-	PZ30	5/-

EF80 1/6, or 10/- per doz. Grade II EF80 for test purposes 4/- per doz.

RADIO BOOKS

STEREO FOR BEGINNERS	8/6
HI-FI FOR BEGINNERS	8/6
SOUND & CINE FOR BEGINNERS	8/6
BASIC ELECTRICITY	
AUDIO & ACOUSTICS by Briggs	11/6
MORE about Loudspeakers by Briggs	9/6
CABINET Handbook by Briggs	8/6
"P.W." RADIO & Television Ref. Data	11/6
22 TESTED Circuits using M.A.T.s AT A GLANCE Valve and T.V. Tube equivalents	4/-
OSCILSCOPE Book	5/6
USING an Oscilloscope	5/6
OSCILSCOPE Equipment	5/6
MULLARD Transistor Radios	5/6
MULLARD Ref. Transistor Circuits	13/6
EXTRA Equipment Tape Recorder	8/6
COIL Design and Construction	5/6
TRANSISTOR Circuits for Radio Control of Models	8/-
SERVICING Transistors Receivers	8/6
ELECTRONIC Novelties	5/6
ELECTRONIC Gadgets	5/6
RADIO Valve Data "Wireless World"	7/-
BEGINNER'S Guide to Radio	8/6
MODERN Transistor Circuits for Beginners	8/-
HOW to Receive Foreign T.V. Programmes with Simple Modifications	5/6
All books include postage. List S.A.E.	

SELRAY BOOK CO.

60 HAYES HILL, HAYES, BROMLEY KENT. Tel. HURSTWAY 1818



FAMOUS FOR THIRTY YEARS for SHORT-WAVE EQUIPMENT of QUALITY

H.A.C. SHORT-WAVE KITS

H.A.C. were the original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, Halls, etc.

NEW 1964 RANGE NOW READY

1-Valve model "CX", complete kit, Price 34/6
Customers say: "Definitely the best one-valve S.W. kit available at any price." This kit contains all genuine Short-Wave components, a drilled chassis, accessories and full instructions. Ready to assemble and, of course, as all our products, fully guaranteed. FULL RANGE of other kits still available including the famous model "K", price 77/-.

Before ordering call and inspect a demonstration receiver or send for a descriptive catalogue and order form to—

"H.A.C." SHORT-WAVE PRODUCTS (Dept. T.H.), 44 Old Bond St., London W.1

FIRST-CLASS RADIO AND T.V. COURSES... GET A CERTIFICATE!

After brief, interesting study course—undertaken at home in your spare time—YOU can secure a recognised qualification or extend your knowledge of Radio and T.V. Let us show you how.

FREE GUIDE

The New Free Guide contains 120 pages of information of the greatest importance to both the amateur and the man employed in the radio industry. Chambers College provides first rate postal courses for Radio Amateurs' Exam., R.T.E.B. Servicing Cert., C. & C. Telecoms., Grad. Brit. I.R.E. Guide also gives details of range of diploma courses in Radio/T.V. Servicing, Electronics and other branches of engineering, together with particulars of our remarkable Guarantee of

SUCCESS OR NO FEE

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER 150,000 SUCCESSSES

CHAMBERS COLLEGE
(Incorp. National Inst. of Engineering)
(Dept. 461), 148 HOLBORN LONDON, E.C.1

SPRING CLEARANCE SALE — PRICES SLASHED

STOCK ROOMS MUST BE CLEARED TO MAKE WAY FOR SPRING STOCK

Stock No. 101—Few Only **MAINS BURGULAR ALARMS**. With complete set of door and window interlocks and Connecting Wire etc. Advertised at 7.50. **OUR PRICE** to clear 39/8, plus 3/- P. & P.

Stock No. 102—**BRASS RIGHT ANGLE BRACKETS**, drilled with 2 holes. Approximately 1/4 square. Only 6d. a pair.

Stock No. 104—**MINIATURE MEDIUM WAVE TUNING COILS** with reaction winding. Clearance price 2/- each, plus 6d. P. & P.

Stock No. 105—**35 ONLY PRECISION CAMERAS**. Takes 127 films. To clear 8/6 each, plus 1/6 P. & P.

Stock No. 108—**185 ONLY MINIATURE PLASTIC RADIO CABINETS**, complete with Chrome carrying Handles. Dial and tuning knob. Size 3 1/2 x 3 1/2 x 1 1/2 in. Clearance price only 5/6, plus 1/- P. & P.

Stock No. 107—**PRINTED CIRCUITS** of 3 Transistor Reflex Radio made to fit above radio, 2/6, plus 1/6 P. & P.

Stock No. 108—**MINIATURE PRINTED RADIO CABINETS**, 5 x 3 1/2 x 1 1/2 in., 3/6 each to clear, plus 6d. P. & P.

Stock No. 109—**BEAUTIFUL MINIATURE SIZE PLASTIC RADIO CABINETS**. Size 3 x 3 x 1 1/2 in. Printed and ready drilled. **OUR PRICE** 3/6, plus 1/- P. & P.

Stock No. 110—**MINIATURE PLASTIC RADIO CABINETS** unprinted. Size 3 x 2 1/2 x 1 1/2 in., 2/6 each to clear, plus 6d. P. & P.

Stock No. 111—**BEAUTIFULLY MOLDDED MINIATURE PLASTIC RADIO CABINETS**, complete with tiny carrying handle and tuning knob. Size 4 x 2 1/2 x 1 1/2 in. Price to clear 3/6, plus 1/- P. & P.

Stock No. 111a—**Specially Printed Circuits** for above cabinet of two transistor reflex radio, 2/6, plus 6d. P. & P.

Stock No. 112—**EXCEPTIONALLY GOOD LOOKING PLASTIC RADIO CABINETS** "SLIM LINE". Size 6 x 3 1/2 x 1 1/2 in. Clearance price 5/6, plus 9d. P. & P.

AMAZING CIGARETTE RADIO only 18/6



Amass your friends! —This highly sensitive **TRANSISTOR "CIGARETADIO"** receives all medium wave stations clear and crisp—holds ten cigarettes—weighs less than 3 ozs. with cigarettes! Tiny battery inside cost 3d. and lasts over three months. This brilliant little novelty personal phone radio is ideal for Bedside, News, Sports, Office. Can be built by anyone from our simple pictorial diagrams in an hour or two. All parts supplied for 18/6 (add 1/6 P. & P.). C.O.D. 2/- extra. (Parts sold separately, priced parts lists 1/-).

Stock No. 113—**BEAUTIFUL BLACK & GOLD READY DRILLED FRONT RADIO PANELS** TO GO WITH THESE, 5/-, plus 1/- P. & P.

Stock No. 114—**MINIATURE RADIO CABINETS** IN GOLD but unprinted. Size 4 1/2 x 3 x 1 1/2 in. five away price of 2/6, plus 6d. P. & P. Special carrying cases for above at 1/6, plus 6d. P. & P.

Stock No. 115—**RADIO CABINETS** same as specified as above, but upright design, 2/6 each, plus 6d. P. & P.

Stock No. 115a—**Special carrying case** for above at 1/6, plus 6d. P. & P.

Stock No. 116—**ANOTHER TYPE RADIO CABINET**, horizontal, 2/6 each, plus 6d. P. & P.

Stock No. 125—**BRAND NEW MAGNETIC DEAF AID TYPE EARPIECES**, complete with Plug and Socket. 300 ohms. **OUR SPECIAL PRICE** 5/- plus 6d. P. & P.

Stock No. 126—**BRAND NEW CRYSTAL DEAF AID TYPE EARPIECES**. Our price 4/- plus 6d. P. & P.

Stock No. 127—**DECORATIVE SPEAKER GRILLS** 2 1/2 in. diameter, 3 for 1/-, plus 6d. P. & P.

Stock No. 128—**4 in. PLASTIC CARRYING HANDLES** with fixing screws, 6d. each, plus 6d. P. & P.

Stock No. 135—**93 ONLY STANDARD PLASTIC CEILING SWITCHES**, two way, cord operated. Clearance price 2/6, plus 1/- P. & P.

AMAZING NEW INVENTION AUTOMATIC CAR LIGHTER ONLY 10/-



We have been lucky enough to purchase 1,600 only of these fully automatic Car Cigarette Dispensers/Lighters Originally made to sell at about 45/-! Robust and ingeniously designed in heavy chromium. Holds packet of cigarettes (any make and size) you reach out with one hand, press a button and a lighted cigarette is in your hand! Can be lit by anyone in 2/3 minutes. For 6 or 12 volts, full connecting details—only one wire to connect! Each one in own coloured box, brand new and untouched. Only 10/-, add 2/- P. & P. (C.O.D. 2/6 extra).

Stock No. 117—**477 SUB-MINIATURE TRANSISTOR RADIO CASES** (Plastic unprinted). Size only 1 1/2 x 1 1/2 x 1/2 in., to clear 1/6- each, plus 6d. P. & P.


Stock No. 118—**SPRING TERRY CLIPS** for holding Miniature Valves. Price for 3, 1/-, plus 6d. P. & P.

Stock No. 119—**72 ONLY MINIATURE 6 TAG COILS** covering Medium Wave and Long Wave with reaction winding. Price to clear 3/6- each plus 6d. P. & P.

Stock No. 120—**SIMILAR TO ABOVE** but Medium Wave only, 2/- each plus 6d. P. & P.

Stock No. 188 "VOLKSRADIO" POCKET VALVE RADIO ONLY 15/-

Take-Over Bid makes this Fantastic Offer possible —the beautifully compact "5 Star Volkstradio" measuring 4 1/2 x 2 1/2 x 1 1/2 in. receives perfectly—in the bedroom, office, garden—over all medium waves (incl. Luxembourg). Under 1 1/2 hour running (incl. Luxembourg). Anyone can assemble it in 1 or 2 hours, using our simple A B C plan. Only 15/-, plus 1/6 P. & P. C.O.D. extra. (Parts can be bought separately).

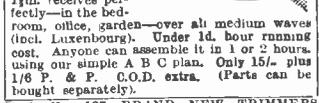

Stock No. 137—**BRAND NEW TRIMMERS "CLYDON"**, 250 pF. To clear 1/- each, plus 4d. P. & P.

Stock No. 138—**MINIATURE ACORDE VALVES**. Type 954, 9d. each, plus 6d. P. & P.

Stock No. 139—**6K7G BRAND NEW VALVES**, 2/6, plus 9d. P. & P.

Stock No. 140—**6V6G VALVES**, 4/8, plus 9d. P. & P.

Stock No. 141—**1L4 BRAND NEW VALVES**, 1/9, plus 6d. P. & P.

Stock No. 142—**BRAND NEW 6Z6 VALVE HOLDERS**, 6d., plus 4d. P. & P.



THE MINUTE TRANSISTOR RADIO MIAMI ONLY 17/6
Unbelievably small—outrageously cheap. You will be amazed at the fine quality of tone and volume of this great little radio. Only a fantastic 2 1/2 x 2 1/2 x 1 1/2 in. The Miami will bring you great entertainment for months on an 8d. battery. Simple assembly plan with each set. Only 17/6. YES 17/6. Plus 2/6 P. & P. (C.O.D. 2/- extra). Satisfaction Guaranteed. Demonstrations given daily. Parts available separately if required.

TERMS OF BUSINESS
C.O.D. 2/6 extra. refund No. C.O.D. under 21. Add extra postage to overseas. Special prices for quantity and the Trade. All goods guaranteed. Components, technical books, Hi-Fi by Leak, Jason, Lorenz, Quad, etc. Send S.A.E. for quotation or with any enquiry.

Stock No. 121—**MEDIUM WAVE LOOPSTOCK COILS** with Variable Tuning Core, 73 only. To clear 2/6 each, plus 6d. P. & P.

Stock No. 122—**FEW ONLY VARIABLE TUNING CONDENSER** (Mika Electric)—4005 mfd., 3/6, plus 6d. P. & P.



Stock No. 170, TRANSISTOR POCKET RADIOS ONLY 28/6
No More To Pay
BULK PURCHASE ENABLES US TO MAKE THIS FANTASTIC OFFER —AND WITH MONEY BACK GUARANTEE!
The "M.A. REMO" — so named that it brings the voice of star entertainers and vocalists dramatically to you—our home, office, etc. Only 47 x 2 1/2 x 1 1/2 in. Fits easily into your pocket or handbag. Works for months on one 1/2 battery. Shouldn't just a few minutes that you can assemble it in an hour or two with our easy plan. Complete set of part including miniature speaker, carrying case—everything only 28/6, 2/6 P. & P. C.O.D./2/6 ext. (Parts can be bought separately.) Limited period—so rush your order before it's too late. DEMONSTRATIONS DAILY.

Stock No. 163—**BRAND NEW ASSORTED CONDENSERS** 30 pF to .01 mfd., 25 for 7/6, plus 1/- P. & P.

Stock No. 164—**SPECIAL OFFER OF HOME CONSTRUCTED RADIOS** needing "ATTENTION". Filled with components in good condition.

Stock No. 164a—**TYPE (B) 2/2 Transistor**. Size 4 1/2 x 3 x 1 1/2 in. Price 6/- each plus 1/- P. & P. Brand new 2 1/2 in. Miniature Coil speakers worth 14/- given free with every order for five.

Stock No. 164b—**TYPE (E) 2/0** Miniature Valve Radios in plastic case. Size approximately 5 x 3 x 1 1/2 in. Price 5/- plus 1/6 P. & P.

Stock No. 164c—**TYPE (E) 2/0 only**. Valve Radios in small fibre airtight cases. Size 7 x 5 x 2 1/2 in. Price 2/6, plus 2/6 P. & P.

Stock No. 165—**SURPRISE PARCEL TYPE (a)** Assorted components. Price 5/-, plus 1/6 P. & P.

Stock No. 167—**GIANT SURPRISE PARCEL TYPE (c)**. Price 15/-, plus 2/- P. & P.

Stock No. 168—**WANDERFLUX**. New and unused. 2/- doz. plus 6d. P. & P.

Stock No. 134—**3 in. MOVING COIL LOUD-SPEAKERS**. Brand new, 3 ohms. 10/-, plus 2/6 P. & P.

Stock No. 168—SPECIAL CLEARANCE OF FULLY GUARANTEED BRAND NEW "GOLD FRONT" 6 TRANSISTOR SUPER-HET RADIO. Complete with real leather carrying case. Personal earpiece, battery. All in beautiful presentation boxes. Only 75/- plus 2/6 P. & P. 74 only. Advertised at 66.0 recently. Last 74—no more available.



Stock No. 143 MINIATURE SPY CAMERA ONLY 18/6 NO MORE TO PAY

World shattering Purchase by our FOREIGN AGENTS makes this exclusive scoop yours for ONLY 18/6. This exciting little 2 speed camera is not a toy but a precision instrument. Instrument in chrome, steel, and leather with minute multi-Magnifying Lens—each 14mm. film takes 10 pictures—size 1 1/2 x 1 1/2 in.—Only 18/6 P. & P. 1/6 ex. FREE Leather Carry-case. Six Rolls of F1

Stock No. 144—**BRAND NEW 2 1/2 in. MOVING COIL LOUD-SPEAKERS**. SPECIAL PRICE 8/6, plus 1/6 P. & P. 30 only.

CONCORD ELECTRONICS (Dept. P.W.7) 210 Church Road, Hove, Sussex
PERSONAL CALLERS WELCOME:— Open 8.30 a.m. until 1 p.m. and 2 p.m. until 5.30 p.m. Saturdays: 8.30 a.m. to 1 p.m.
Demonstrations Daily.

Lewis have the Cabinet for you

We can supply any cabinet to your own specification

This is only one example of—
THE LARGEST RANGE
OF CABINETS IN THE
COUNTRY

Equipment is also our
speciality.



The Grosvenor
Price 18 gns.



The Lowboy
Price 27 gns.

LEWIS radio

100(P54) Chase Side, Southgate
London, N.14, Pal 3733/9666

FREE CATALOGUE

Send today for the new
Lewis Catalogue

Designed to assist your choice of
cabinet.

THE New Lewis Radio Cabinet Cata-
logue sent absolutely free—the most
comprehensive ever prepared. Choose
from 49 different Models.

Please send your new free 24 page colour
cabinet catalogue.

Name

Address.....

BLOCK CAPITALS PLEASE

B.B.C.2 (625 LINE) TV AERIALS



EXTERNAL MAST MOUNTING ARRAYS
5 element, 36/-; 9 element, 45/-.
WALL MOUNTING with CRANKED
ARM. 5 element, 51/6; 9 element, 60/-.
CHIMNEY ARRAYS with LASHINGS,
etc. 5 element, 63/6; 9 element, 72/-.
LOFT ARRAYS. 3 element, 24/-.
7 element, 32/6. Also available for
Window Fixing, 2/6 extra. Co-ax. Plugs,
1/3. Low Loss Co-axial Cable, 1/6 yd.

BBC • ITV • F.M. AERIALS

B.B.C. (BAND 1). Tele-
scopic loft, 21/-. External
S/D 30/-.

I.T.V. (BAND 3). 3 Ele-
ment loft array, 25/-; 5
Element, 35/-; Wall
mounting, 3 Element, 35/-;
5 Element, 45/-.

COMBINED B.B.C./I.T.V.
Loft 1+3, 41/3; 1+5, 48/9.
Wall mounting 1+3, 56/3;
1+5, 63/9. Chimney 1+3,
63/9; 1+5, 71/3.

F.M. (BAND 2). Loft S/D, 12/6. "H",
30/-; 3 Element, 52/6. External units
available. Co-ax. cable 8d. yd. Co-ax.
plugs 1/3. Outlet Boxes 4/6. Diplexer
Crossover Boxes 12/6. C.W.O. or C.O.D.
P.P. 3/-. Send 6d. stamps for illustrated
lists.

K.V.A. ELECTRONICS (Dept. P.T.)
3B, Godstone Road, Kenley, Surrey,
CRO. 2527

2 METRES 4

The thrills of VHF Amateur Radio
can now be yours for as low as 39/6,
complete kit (by post, carriage and
packing. 2/6 extra). Tuning range
70-150 Mc/s. Stamped addressed
envelope for free copy of literature
and full details. Newcomers to
Short-Wave Radio ask for details of
the (amous "Globe-King" kits and
receivers. Home and Overseas Sales.

JOHNSONS (Radio)
St. Martins Gate Worcester

A.R.R.L. RADIO AMATEURS HANDBOOK 1964

New Edition 36/-. Postage 2/6.

World Radio and T.V. Handbook 1962,
by Johansen, 22/-. Postage 1/-.

British Transistor Directory, by Bradley,
8/6. Postage 6d.

Mullard Reference Manual of Transistor
Circuits, 12/6. Postage 1/-.

Radio Servicing Pocket Book, by Hawker,
12/6. Postage 9d.

Model Boat Radio Control, by Casebrook,
7/6. Postage 9d.

Introduction to Lasers and Masers,
by Lytel, 16/-. Postage 9d.

Diode Circuits Handbook, by Turner,
19/-. Postage 1/-.

Oscillator Circuits, by Adams, 24/-,
Postage 1/-.

UNIVERSAL BOOK CO.

12 Little Newport Street, London, W.C.2
(adjoining Lisle Street)

Lyons Radio Ltd.

3 Goldhawk Road
LONDON W.12

ELECTRIC CHECK METERS. 230/250 v.
40 amps for checking electricity consump-
tion. Reconditioned and perfect. PRICE
ONLY 35/-, post 3/6.

TELEPHONE AMPLIFIERS. Transis-
torised, operating from a PP3 type battery
with small induction coil with suction pad
to press on side of telephone, absolutely no
interference with instrument. Eliminates
for ever that time wasting "Holding-on",
loud and clear conversation being repro-
duced by the built-in speaker. Your two
hands can be free if you wish to take notes.
Instead of waiting by the phone. If your
call is not ready to answer, you are at
liberty to carry on with other work, move
around the room etc. Has volume control
and on/off switch, housed in a smart ivory
coloured plastic case 4 1/2 x 3 x 1 1/2 ins. battery
included. PRICE ONLY 65/-, post 2/6.

**CRYSTAL SET/TRANSISTOR RECI-
VER.** Parts to enable the beginner to have
fun and know the thrill of constructing
his own working radio, which can be made
without soldering. Parts supplied are:—
Crystal, coil, tuning condenser, resistors,
transistor, 50ft. coil of aerial wire plus
instructions and wiring diagrams. ALL
for ONLY 13/6. Optional extras. Personal
earphone 6/6, headphones 12/6 pair, case
3/6. Postage 2/-.

NEW 1/4 H.P. ELECTRIC MOTORS. 200/
250 v. A.C. mains split phase induction
type by Crompton Parkinson. Spindle
2 x 1/2 in. dia., 1440 r.p.m., reversible, with
mounting plate and bosses for vertical or
horizontal mounting. BARGAIN PRICE
ONLY 75/-, carriage 9/-.

AERIAL RODS. Set consists of 3 co-
perised tapering steel sections, each 4ft.,
making up a 12ft. aerial or the ever popular
fishing rod. PRICE ONLY 7/6 or with
mounting base. PRICE ONLY 10/6. Car-
riage 3/6



WIRE STRIPPER

A tool designed for home and work-
shop use. Easily adjustable for a
large range of wires. Heavily plated
with plastic coated grip end.

Price 4s. 6d. plus post & pkg. 9d.

MONEY BACK GUARANTEE

HOWLEY TOOL TRADING Co. Ltd
Howley Tannery, Howley Lane,
Warrington, Lancashire, England

MINIKIT

A precision set of tools
comprising of side cutter,
round, snipe and flat nose
4 1/2" tools. Handles P.V.C.
coated for comfort.

Complete in plastic
wallet 30s. plus post and
packing 2s. 6d.



High Stability Resistors. 1W 1% 2/- each.
Full standard range 10Ω to 10MΩ stocked,
many special values for multimeters, etc.
Surplus High Stab. Resistors. 1/2W,
1% 9d., 2% 7d., 5% 5d. each. List available.
Precision Wirewound Resistors 1W.
1 ohm to 5K, 3/- to 20K 4/-; 4% add 3d.
Your value wound to order.

Multimeter Kit. ● Multimeter scale
fixed to meter. ● 25 ranges. ● 18,000 ohms
per volt. ● Sturdy British movement
(Weston) with shock mounted jewels. ●
Shunts ready adjusted to 1%. ● Multiplier
are 1% accuracy (and of 1% stability where-
ever possible). ● Individual zero control for
each ohms range. ● Spares readily available
at listed prices. ● Ranges 0-2500 A-2.5mA-
25mA-250mA DC 0-0.25-2.5-10-25-100-250-500-
1000V DC; 0-10-25-100-250-500-1000V AC;
0-10-25-100-250-500 O.P. volts; 0-10KΩ &
0-10MΩ. 65/- post free. ● Circuit S.A.E.
FREE with kit this month—Parts for third
resistance range 0-10 ohms.

Multimeters. TK20A 35/-, post 1/6; EP10K
69/6, post 1/6; EP30K, post 2/-; EP50K
86/10.0, post 2/6. Illustrated leaflet free.

PLANET INSTRUMENT CO.,
25 DOMINION AVENUE, LEEDS 7

- all these and hundreds more

Mon.—Sat. 9 a.m.—5.45 p.m.
Wednesday 1 p.m.

Special 24 Hour Express Mail Order Service

AC2/PEN 19/6	ECC85 7/6	EY81 8/6	PABC80 13/-	T41 15/-	UM80 10/6	6ABGT 13/6	6L19 15/-	12SA7 8/6
AC2/PEN DD 19/6	ECC88 12/6	EY83 12/6	PCC84 7/-	TDD4 12/6	URIC 15/-	6AC7 6/-	6N7GT 9/6	12S17 8/-
AC TP 29/-	ECC91 3/-	EY86 7/-	PCC85 9/6	TDD13C 17/6	UU6 17/6	6AK5 5/-	6P25 10/6	12SK7 6/-
AC VPI-5-7 15/-	ECCF80 7/6	EY91 3/-	PCC88 12/6	TH41 20/-	UU8 15/-	6ALS 4/-	6P28 12/6	12SL7 8/-
AZ1 15/-	ECH21 21/6	EZ35 6/-	PCC89 8/6	TY86F 12/6	UY9 7/6	6AM5 5/-	6Q7 9/6	12SN7 10/-
AZ31 13/6	ECH35 10/-	EZ40 7/-	PCF80 7/6	U10 9/-	UY19 12/6	6AM6 4/-	6Q7GT 8/6	14H7 10/-
B36 9/-	ECH42 9/6	EZ80 5/6	PCF84 12/6	U12 9/-	UY41 7/6	6AT6 6/-	65A7 7/-	14R7 10/-
CIC 10/-	ECH81 7/-	EZ90 4/6	PCF86 12/6	U14 9/-	UY85 6/-	6AU6 9/-	65C7 8/6	19AQ5 15/-
CCH35 20/6	ECH83 8/6	E1148 2/-	PCL82 7/6	U22 8/-	VP4 15/-	6BBG 2/6	65F5 10/-	19BGG6 8/-
CL33 12/6	ECL80 6/6	E148 2/-	PCL83 9/-	U24 21/-	VP4A 15/-	6BA6 6/-	65G7 7/-	20D1 10/-
CY1 15/-	ECL81 10/-	FC2 15/-	PCL84 7/-	U25 11/-	VP4B 15/-	6BE6 6/-	65H7 6/-	20D2 21/-
CY31 12/6	ECL82 9/6	FC2A 17/6	PCL85 7/6	U26 11/-	VR 105/307/-	6BG6G 15/-	65J7 6/6	20F2 17/6
D77 4/-	ECL83 10/6	FC4 15/-	PCL86 12/6	U31 9/-	VR 150/307/-	6B16 6/-	65K7 5/6	20L1 22/6
DAC32 9/6	ECL86 9/6	FW4/500 9/-	PEN4A 19/6	U35 17/6	W61 11/-	6BQ7A 12/6	65L7GT 5/6	20P1 15/-
DAF91 5/6	EF6 21/-	FW4/800 9/-	PEN4DD 22/6	U37 17/6	W76 5/6	6BR7 10/6	65N7GT 5/-	20P3 24/-
DAF96 6/6	EF9 21/-	GZ30 10/6	PEN4VA 17/6	U47 11/-	W77 4/-	6BS7 12/6	65Q7 8/6	20P4 20/-
DCC90 12/6	EF22 14/-	GZ32 10/6	PEN36C 20/-	U52 4/-	W81M 6/-	6BW6 9/-	64UGT 10/-	20P5 20/-
DF33 9/6	EF36 4/-	GZ33 13/6	PEN45 20/-	U76 6/6	X41 22/6	6BW7 9/-	6U5G 7/6	25A6 8/-
DF91 3/6	EF37 8/-	GZ34 19/3	PEN45DD 25/-	U78 4/6	X61M 10/-	6C5GT 8/-	6V6G 4/-	25L6 8/-
DF92 7/6	EF37A 8/-	HABC80 10/-	PEN46 25/-	U88 4/6	X65 12/6	6C6 3/6	6V6GT 8/-	25Y5G 8/-
DH63 6/6	EF40 15/-	HL41 8/-	PEN45DD 25/-	U91 13/6	X76 12/6	6C9 12/6	6X5G 5/-	25Z4 7/6
DH77 7/6	EF41 8/-	HL41DD 8/6	PEN46 25/-	U91 13/6	X76M 12/6	6CD6G 25/-	6X5GT 8/6	25Z5 8/-
DK32 11/6	EF42 10/6	HL92 8/6	PEN45DD 20/-	U281 15/-	X78 24/-	6CH6 10/-	6/30L2 12/6	25Z6 8/6
DK91 5/6	EF50A 3/6	HL133DD 20/-	PENDD4020 40/20	U282 19/6	X79 40/-	6CW4 16/-	785 12/6	27SU 19/6
DK92 7/6	EF80 3/-	HN309 25/-	PL33 15/-	U301 18/6	Y61 10/6	6D2 4/-	787 8/6	30C1 9/-
DK96 7/6	EF85 5/-	IW4/350 10/-	PL36 12/6	U329 15/-	Y63 10/-	6D6 5/6	7C5 8/6	30C15 12/6
DL33 8/6	EF86 7/-	IW4/500 10/-	PL38 18/-	U339 13/6	Z63 7/6	6E5 10/-	7C6 8/6	30F5 10/-
DL35 10/-	EF89 8/-	K733C 8/-	PL81 7/6	U403 10/-	Z66 10/-	6F1 10/6	7D5 15/-	30FL1 10/6
DL91 7/6	EF91 4/-	K736 17/6	PL82 7/6	U404 10/-	Z77 7/-	6F6 6/9	7D6 15/-	30L1 8/6
DL92 5/6	EF92 4/-	K766 15/-	PL87 7/6	U801 19/6	Z152 5/-	6F12 4/-	7D8 15/-	30L15 11/-
DL93 7/6	EF95 5/-	K776 10/-	PL88 8/-	UABC80 5/6	1A7 11/-	6F14 10/6	7H7 6/-	30P4 18/-
DL94 7/6	EF98 10/-	K781 8/-	PL820 18/-	UBC41 8/6	1D6 10/-	6F15 12/6	757 17/6	30P12 10/-
DL96 6/6	EF183 8/-	K7W6 8/-	PL820 18/-	UBC81 10/-	1H5 9/6	6F19 12/6	7Y4 6/6	30P16 9/-
EAS0 2/6	EF184 8/-	L63 5/-	PM24M 13/6	UBF80 7/6	1L4 5/6	6F23 10/6	8D3 4/-	30P19 17/6
EABC80 5/6	EK32 8/6	LN152 6/6	PX4 15/-	UBF89 7/-	1N5 9/6	6F25 16/6	9BV6 12/6	30PL1 15/-
EAC91 4/6	EL3 21/6	LN309 9/-	PX25 25/-	UBL21 20/-	1R5 5/6	6F26 13/6	10C1 12/6	30PL13 12/6
EAF42 9/6	EL32 4/6	LZ319 12/6	PY31 15/-	UCC84 11/6	1R4 3/6	6F33 5/6	10C2 17/6	30PL14 12/6
EB34 2/6	EL33 10/-	MKT4 17/6	PY32 10/6	UCC85 7/-	1S5 5/6	6H6 2/6	10F1 10/6	35A5 15/-
EB41 6/6	EL34 14/-	MS4B 17/6	PY80 7/6	UCC80 12/6	1T4 3/6	6J5 5/6	10I4 19/6	35Z3 15/-
EB91 4/-	EL35 10/-	MVS'PEN 17/6	PY81 6/6	UCH21 20/-	1U5 5/9	6J5GT 4/6	10I5 23/6	35Z4 6/6
EBC3 21/6	EL37 17/6	MVS/PENB 15/-	PY82 5/6	UCH22 8/6	2P 22/6	6J7 7/6	12A6 6/6	35Z5 8/6
EBC33 4/6	EL38 17/6	MU14 9/6	PY83 8/-	UCH81 7/-	3A4 5/-	6J7GT 5/-	12A8H 11/-	41STH 22/6
EBC41 8/6	EL41 9/6	MU14 9/6	PY88 10/-	UCL82 9/-	3A5 10/6	6J7GT 7/6	12AT6 7/6	50C5 10/-
EBC81 10/-	EL42 9/6	MU14 9/6	PY800 10/-	UCL83 11/6	3Q4 8/-	6K7 7/6	12AT7 5/-	50CD6G 30/-
EBF80 7/6	EL81 12/6	MX40 15/-	PZ30 10/-	UF41 7/6	3Q5 9/-	6K7GT 2/-	12AU6 17/6	50L6 8/6
EBF83 8/-	EL84 6/-	N18 8/-	Q595 10/10/-	UF42 7/6	3S4 5/6	6K8 9/6	12AU7 5/-	75 8/6
EBF89 7/6	EL85 10/-	N37 14/-	Q5150 15	UF80 7/-	3V4 7/-	6K8GT 9/6	12AX7 5/-	78 7/6
EBL1 21/6	EL90 8/6	N78 22/6	R2 10/-	UF85 7/6	3U4 4/-	6K8GT 9/6	12BA6 7/6	80 7/6
EBL21 21/6	EL91 4/-	N108 26/-	R2 10/-	UF86 12/6	5V4G 7/9	6K8GT 9/6	12BE6 7/6	85A2 12/6
ECC35 8/-	EL95 10/6	N308 18/-	R16 17/6	UF89 6/-	5Y3G 4/6	6K25 17/6	12B87 10/-	18SBT 30/-
ECC40 15/-	EM80 8/6	N339 30/-	R19 16/-	UL41 8/-	5Y3GT 5/6	6L1 10/-	12J7GT 8/6	807A 7/6
ECC81 4/6	EM81 8/6	N369 10/6	R20 16/-	UL44 20/-	5Z4G 7/6	6L6 7/6	12K7GT 5/-	807B 7/-
ECC82 5/-	EM84 8/-	OD3 5/-	SP41 3/6	UL46 14/6	5Z4GT 8/6	6L7 10/-	12K8GT 10/-	12Q7GT 6/-
ECC83 5/-	EM85 10/-	OZ4 5/-	SP61 3/6	UL84 6/-	6A7 9/6	6L8 10/-		
ECC84 6/6	EY51 7/6	P2 10/-		UL85 7/6	6A8G 8/6			

COMPLETE VALVE LIST FREE WITH ORDER

METAL RECTIFIERS

RM1 7/6	14A86	23/-	16RD 2-2-8-1	12/- (FC142)
RM2 8/-	14A97	26/-	16RE 2-1-8-1	10/- (FC150)
RM3 10/-	14A100	28/-	18RA 1-1-8-1	5/- (FC118)
RM4 17/6	14RA 1-2-3-2	21/- (FC301)	18RA 1-1-16-1	7/- (FC116)
RM5 19/6	14RA 1-2-8-3	25/- (FC31)	18RD 2-2-8-1	16/- (FC124)

BRAND NEW TRANSISTORS			
OC44 5/-	OC74 8/-	OC81D	5/-
OC45 5/-	OC75 8/-	OC81m,pr	12/6
OC71 5/-	OC77 8/-	OC82	6/-
OC72 8/-	OC81 5/-	OC82D	6/-

SILICON RECEIVERS

400 volts 350 mA 7/6 each

TERMS OF BUSINESS C.W.O. OR C.O.D.
4/2 PACKING CHARGE ON ALL C.O.D.
ORDERS. POSTAGE 6d. per VALVE

SETS OF VALVES			
1R5, 1S5, 1T4, 3S4, 3V4	Set of 4, 17/-
DAF91, DF91, DK91, DL92, DL94	Set of 4, 17/-
DAF96, DF96, DK96, DL96	Set of 4, 25/-

R.S.T. VALVE MAIL ORDER CO.

211a STREATHAM ROAD MITCHAM SURREY

Tel: MITcham 6202
Open Daily to Callers

We supply from stock most of the components and items specified or circuits published in this and other magazines and radio books. Let us quote for your circuit, first grade components at realistic prices.

MINIATURE 'SCOPE

MODEL CT84

Features 2½in. DG7/5 Tube. Level 2dB, 50 c/s to 2 Mc/s. 3½ Sec. to 80µ Sec. Sweep. High sensitivity. Fully portable scopes. Ideal for all transistor and valve design or servicing. 22 to 30 volt D.C. operated. Mains transformer for 220/250 volts A.C. conversion 22/6.

£16-10-0
CARRIAGE 7/6

DEAC RECHARGEABLE BATTERIES

18 volt 100mA/H 4 x 1in. diameter. Brand new sleeved, 30%.
3.9 volt 450mA/H, 12/6.
All types easily split into any multiple of 1.2 volt. Brand new.



MULTI-METERS

Multi-range test meters featuring easy to read scales and provided with full operating instructions, lead and batteries. Suitable for amateurs, designers, repair shops, all domestic uses. Full details and specifications in our catalogue.

- ★ PT34 1 Kohm/volt £2 5 0
- ★ M1 2 " " £2 9 6
- ★ THL33 2 " " (illus.) £3 15 0
- ★ EPI0K 10 " " £4 9 6
- ★ ITI-2 20 " " £5 5 0
- ★ TP55 20 " " £5 19 6
- ★ EP30K 30 " " £6 19 6
- ★ 500 30 " " £8 19 6
- ★ EP50K 50 " " £9 19 6


SUBSTITUTION BOXES

- Capacitor Box. Provides 9 standard values from 0.001 to 0.22 mfd at 600 volt working. 29/6.
- Resistor Box. Provides 24 standard values at 1 watt, 15 ohms to 10 meg., 37/6.

Each box fully calibrated with insulated leads. Invaluable for service and design.

NOMBREX TEST EQUIPMENT

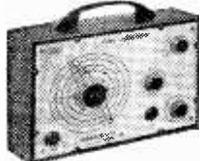All transistor portable units supplied with full instructions.



LEAFLETS ON REQUEST

- ★ 150 Kc/s to 350 Mc/s generator. RF, Mod., AF. 8 ranges. Leads, batt., instructions, £9.10.0.
- ★ Resistance/Capacitance Bridge. 1 pF to 100mF and 1 ohm to 100meg. leakage. PF Tests, with batt. and instructions, £8.5.0.
- ★ Transistorised Power Supply. Gives any voltage 1 to 15 D.C. up to 0.1 amp. From Mains. £6.10.0.
- ★ Audio Generator, 10 c/s to 100,000 c/s. Sine and square wave. With batt. and instructions. £16.15.0.
- ★ Inductance Bridge. 1 micro Henry to 100H, in 4 ranges. Q and tan measurements. With batt. and instrs. £18.

HI-FI SPEAKERS

- CX300 12 inch 25 watt 12 Gns.
- CR12AE 12 inch 20 watt 8 Gns.
- CR30AE 12 inch 20 watt triple range 10 Gns.
- 8A7 8 inch 6 watt 79/6
- 10 watt Horn Tweeter 29/6
- 20 watt Rect. Horn Tweeter 69/6

RECORDING TAPE

5in. 600ft., 12/6; 5in. 900ft., 15/-; 7in. 1,200ft., 18/6; 7in. 1,800ft., 25/-; 7in. 2,400ft., 27/6. Excellent quality.

QUARTZ CRYSTALS

- 100 Kc/s 3 Pin 15/- ea.
 - 500 Kc/s 2 Pin 15/-
 - 455 Kc/s (AR88) 12/6
 - 5000 Kc/s 2 Pin 10/-
 - 10 Mc/s 2 Pin 15/-
 - 27 Mc/s Radio Control 15/-
 - 456 Kc/s HRO 15/-
- (Over 600 Frequencies in Stock for all purposes. Catalogue on request.)

MAINS AND BATTERY RECORD AND TAPE DECKS

- All Decks Complete with Cartridges
- ★ BSR UA14 4-speed Auto. £5 16 9
 - ★ BSR UA15 4-speed Auto. £5 19 6
 - ★ Garrard Autoslim Auto. £6 10 0
 - ★ Unpluggable Hfd. Versn. Auto. £6 19 6
 - ★ Stereo Version Auto. £7 19 6
 - ★ SRP10 4-speed Single Player £5 5 0
 - ★ BSR GU7 4-speed Single Player 5 gns.
 - ★ Garrard AT6 with Stereo Cartridge Autochanger £10 19 6
 - ★ AT6 Mono 10 gns.
 - ★ Collaro 2-track Studio Deck £10 10 0
 - ★ 4-track Deck £13 19 6
- P. & P. 3/6 any type above.
- ★ 9 volt Starr, 45 r.p.m. 39/6
 - ★ 45 or 33 r.p.m. Starr 9V 92/6
 - ★ 45 r.p.m. Garrard, 6V 35/-
 - ★ 4-speed B.S.R. 9V 5 gns.
 - ★ Garrard 9V. 2-speed, 2-track Tape Deck £11 15 0
- P. & P. 2/6 any of above.

TO BUILD YOURSELF

- Ranger-3 Personal Radio 49/6
 - Sinclair Slimline Personal Radio 49/6
 - Sinclair Micro-6 59/6
 - Sinclair Micro Injector 27/6
 - Quintet M/LW-5 79/6. P.P. 2/-.
 - PW-6 Superhet £7 19 6
 - PW Shortwave 2 99/6. P.P. 2/6.
- Leaflet and details on request

ALL PARTS IN STOCK FOR PW SHORTWAVE TRANSISTOR CONVERTER. As per Feb. Edition 1964.

CRYSTAL MICROPHONES

- Acos 39-1 Stick Microphone 32/6
- Acos 60-1 Stick Microphone 27/6
- Acos 40 Deck Microphone 15/-
- Acos 45 Hand Microphone 22/6
- Lapel/Hand Microphone 12/6
- 100C Stick with Stand 39/6
- BM3 Stick with Stand 49/6
- Lapel/Hand Magnetic 8/6

MINIATURE PANEL METERS

- *0/50µA (D.C.) 39/6 *0/5mA (D.C.) 27/6
 - *0/500µA (D.C.) 32/6. *0/300V (D.C.) 27/6
 - *0/1µA (D.C.) 27/6 "5" Meter 35/-
- All Brand New Boxed. *Available Clear Plastic Front or Black Moulded.
- 200µA D.C. Edge meter 69/6
 - 1 mA D.C. Edge meter 59/6
- 3½ x 1 inch Front Panel.

POCKET SOLDERING IRON. 30 watts. 220/250 volts A.C. Complete with pointed bit, mains plug, carry pouch. 14/6. P.P. 1/6.

HEADPHONES

2000 ohms 12/6. 4000 ohms 14/-.

All parts in stock for PW "Build and Learn." Quotations by return.

- Stereo Stethoscope Headset 25/-
- Mono Stethoscope Types. Crystal 10/6. Magnetic 12/6.
- Fully Retractable Car Aerial—Thief Proof 35/-.
- PP3 Battery Eliminator 18/6.
- Tape Demagnetiser, 29/6.
- 1K ohm Dynamic Microphone 12/6.
- 8+8ohm Stereo Headphones 62/6.
- Transistor Signal Injector 39/6.
- Crystal Ovens, 6/12 volt 22/6.
- 12 inch 15 ohm Speaker, 35/-.
- DFI dynamic Mic. 50 k. with stand, 52/6
- New range in stock. See catalogue.
- 5-Piece Hole Cutter for all chassis work ½in. to 1½in. with pouch 49/6.
- Crystal Contact Microphone 12/6 P.P. 9d.
- 2K, ½-track Tape Head 15/- P.P. 9d.
- Telephone Recording Attachment 12/6 P.P. 9d.
- 4-Channel Transistor Mixer Unit 59/6 P.P. 1/6
- Tape Jack Radio Tuner 29/- P.P. 1/-.

MARTIN TRANSISTOR AUDIO KITS

- Unit 1. Input Selector 47/6
- Unit 2. Pre-amplifier 37/6
- Unit 3. 3-Channel Mixer 79/6
- Unit 4. Pre-amp. and Tone Control 62/6
- Unit 5. 10 watt Amplifier £5.12.6
- Unit 6. Mains Unit 52/6
- 4 Transistor 9 volt, 3 ohm, 1 watt Amplifier. Built 49/6 Kit 39/6

FIELD STRENGTH METER

Five channels cover 1 Mc to 200 Mc/s. Fitted 200 microamp meter for CW or RF. Indication and Earphone for A.F. Monitoring. Designed for checking all types of transmitters. Size 4 x 2½ x 2½in. Complete. Ready to Use, with instruction and telescopic aerial, 69/6. Post Free.

RUN YOUR RADIO OR AMPLIFIER FROM MAINS BATTERY ELIMINATORS AND CHARGERS

1. For PP3 or equivalent 9 volt Pocket Radio Battery, 18/6. P.P. 1/-.
2. For PP4, PP7, PP9, 9 volt Portable Radio and Equipment. Supplies up to 300mA, 49/6. P.P. 2/-.
3. De Luxe version of No. 1 also charges PP3 type batteries. 24/- P.P. 1/-.

TEST LEAD KIT supplied in Pocket Pouch. Contains probes, leads, clips, etc. 8/6. P.P. 9d.

- Full range of Goodmans, WB and Eagle Speakers and Tweeters in stock

Henry's Radio Ltd.

PADDINGTON 1008/9
303 EDGWARE RD., LONDON W.2
Open Monday to Sat. 9-6. Thurs. 1 o'clock.

PLEASE TURN TO BACK PAGE

Practical Wireless

BLUEPRINT SERVICE

ALL of these blueprints are drawn full-size and although the issues containing descriptions of these sets are now out of print, constructional details are available free with each blueprint except for those marked thus (*).

Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to PRACTICAL WIRELESS, Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, London W.C.2.

DOUBLE-SIDED BLUEPRINTS

Each blueprint in this series contains details of two separate instruments or items of equipment.

The Strand Amplifier	}	*	5/-
The PW Signal Generator			
The Savoy VHF Tuner	}	*	5/-
The Mayfair Pre-amplifier			
The Berkeley Loudspeaker Enclosure	}	*	5/-
The Luxembourg Tuner			
The PW Troubadour	}	*	7/6
The PW Everest Tuner			
The PW Britannic Two	}	*	6/-
The PW Mercury Six			
The PW Regency	}	*	5/-
The PW International Short Wave Two			

RECEIVERS

The Tutor *	3/-
The Citizen *	5/-
Junior Crystal Set	PW94 2/-
Dual-wave Crystal Diode	PW95 2/6
Modern One-valver	PW96 2/6
All-dry Three	PW97 3/6
Modern Two-valver	PW98 3/6
A.C. Band-pass Three	PW99 4/-
A.C. Coronet-4	PW100 4/-
A.C. D.C. Coronet	PW101 4/-
The PW Pocket Superhet	5/-

MISCELLANEOUS

The PW 3-speed Autogram	8/-
The PW Monophonic Electric Organ ...	8/-
The PW Roadfarer *	5/-
The PT Band III TV converter	1/6
The Mini-amp *	5/-
The PT Olympic *	7/6
The PT Multimeter *	5/-

SOME EARLIER DESIGNS

THE following blueprints include some pre-war designs and are kept in circulation for those constructors who wish to make use of old components which they may have in their spares box. The majority of the components for these receivers are no longer stocked by retailers.

Experimenter's Short Wave	PW30a	2/6
Midget Short Wave Two	PW38a	2/6
Simple S.W. One-valver	PW88	2/6
Pyramid One-valver	PW93	2/6
BBC Special One-valver	AW387	2/6
A One-valver for America	AW429	2/6
Short-Wave World Beater	AW436	3/6
Standard Four Valve S.W.	WM383	3/6
Enthusiast's Power Amplifier	WM387	3/6
Standard Four Valve	WM391	3/6
Listener's 5-Watt Amplifier	WM392	3/6

QUERY COUPON

This coupon is available until 7th May, 1964, and must accompany all queries in accordance with the notice on our "Letters to the Editor" page.


PRACTICAL WIRELESS, MAY, 1964.

NEW! 84 PAGE FULLY DETAILED AND ILLUSTRATED CATALOGUE. HUNDREDS OF NEW ITEMS AND PRICE REDUCTIONS. PRICE 2/-.

- COMPONENTS — TRANSISTORS
- HI-FI EQUIPMENT — VALVES
- TEST GEAR — CRYSTALS

10 WATT TRANSISTOR HI-FI EQUIPMENT

RESULTS WILL AMAZE YOU!

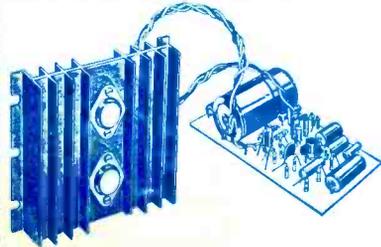

● **POWER AMPLIFIERS.** Two versions. ± 1 dB 40 c/s to 20 kc/s. 60dB Feedback. 100mV input and less than 0.25% distortion for 10 watts output. 3 and 15 ohm versions. Very low current. 6-Transistors and Rectifier.

★ 3 ohm 10 Watt. BUILT **£5.10.0** P.P. 2/6.
★ 15 ohm 10 Watt. BUILT **£5.19.6** P.P. 2/6.

★ **MAINS UNIT**—will run 2-amplifiers for 3 ohm and 15 ohm. 6/6, P.P. 2/6. Each type.

● **PREAMPLIFIER AND CONTROL UNIT.** For use with either of above amplifiers or valve amplifiers — Hum Free — High Sensitivity — 8 Inputs between 1.5mV and 300mV. For all pick-ups — Microphones, Tuners — Tape Replay. Separate treble and bass with cut and boost — 4 position Low Pass Filter — Volume etc. Panel size 9 x 2½ in. Battery operated or from power supply.

● **CALL IN FOR DEMONSTRATION**

★ **Preamplifier Built.**
£5.10.0 P.P. 2/-.

COMPLETE CIRCUITS WITH FULL DETAILS ON REQUEST



PERFORMANCE EQUAL TO VALVE UNITS OF FOUR TIMES THE PRICE AND VERY MUCH LARGER.

- ★ Low Distortion.
- ★ High Performance.
- ★ Mains or Battery.
- ★ Low Noise Design.
- ★ Mono or Stereo.

Dark Brown and Gold Panel Plate. 8/6.

GUARANTEED HIGH PERFORMANCE UNITS.

● Trade Discounts Available. Send For Details.

MINIGRAM TRANSISTOR PORTABLE RECORD PLAYER



● Made by well known British manufacturer. Features ready built 4-transistor printed circuit 1 watt amplifier, elliptical speaker and volume control. Low current Star, constant speed 45 r.p.m. turntable with crystal pick-up. Strong moulded two colour cabinet with handle. Plays anywhere on long life 9 volt battery. Requires less than half an hour's work to connect up using ready built units and easy instructions.

TOTAL COST 7/9 6 P.P. 5/- (Battery 3/9).

MARTIN RECORDAKIT BUILD A QUALITY PORTABLE TAPE RECORDER

Complete in every detail.
● Pre-built units—Collaro Studio Decks—Portable Cabinets with speakers. 6 valve designs.

TWO TRACK

Total Cost £26 P.P. 8/6.

FOUR TRACK

Total Cost £30 P.P. 8/6.
ALL AUDIOKITS IN STOCK

★ Leaflets on Request ★

VHF FM TRANSISTOR TUNER

(As described in December 1963 Edition of "Radio Constructor").

- ★ 5-Transistor.
- ★ 4 Diodes.
- ★ Full coverage 87 to 105 Mc/s.

★ **AFC and AVC.** Printed circuit design of high sensitivity and quality. Output for valve or transistor amplifiers. Size 3½ x 2½ x 4in. Simplified building instructions. All parts sold separately.



TOTAL COST £7.19.6 P.P. 2/6.
(Cabinet assembly 20/- extra.)

Detailed Circuit Book on Request.



"THE CONTESSA"

★ **COMBINED PORTABLE AND CAR RADIO** ★ **AMAZING SENSITIVITY AND SELECTIVITY ON MEDIUM AND LONG WAVEBANDS**

★ The easiest Superhet Radio to build on the market. Features clearly-marked printed circuit and packaged components with full illustrated building instructions. Full tuning of medium and long wave bands with unbeatable sensitivity and selectivity. Excellent tone and volume with over 600mW push-pull output.

★ Clearly marked horizontal station dial with slow motion tuning. Two colour Blue or Beige cabinets with Gold handles, grilles and fittings. Size 10½ x 7½ x 5½ in., includes car aerial sockets, recording sockets.

★ 6 Mullard Transistors and 2 Diodes.


TOTAL COST OF ALL PARTS £9.19.6 P.P. 3/6

Fully Detailed and Illustrated Leaflet on request. All parts sold separately. Guaranteed the Best Obtainable. Attractive Appearance. Reliable Design. Quality Performance.

UNBEATABLE FOR QUALITY AND VALUE

7-TRANSISTOR RECORD/PLAYER/RADIOGRAM AMPLIFIER

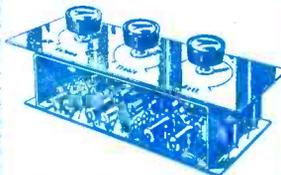- 4 watt peak output.
- Full Treble and Bass boost and cut.
- 40 c/s to 20 kc/s ± 3 dB.
- Inputs for Pick-ups, Radio Tuners, Microphones, mixers.



TWO VERSIONS AVAILABLE

- 12/18 volt for 15 ohm speakers. (mains unit now 60/- extra).
- 9/12 volt for 3 ohm speakers (mains unit 49/6 extra).
- Size only 6 x 2½ x 2in.

Ideal for mains or battery, portable or domestic record player, grams, etc. Or car.

Built Ready To Use **£5.19.6** P.P. 2/-.

4-WAVEBAND COMMUNICATIONS RECEIVER

● 550 kc/s to 30 Mc/s.—BFO — AVC — Noise Limiter — Band spread — "S" Meter — Telescopic Aerial — Full World Wide Coverage. 4 valve. PRICE **£24.15.0** With Full Instructions. BRAND NEW IN CARTONS. Detailed Leaflets on request.

● 9 valve version of above 40 gns. Details on request.

HENRY'S RADIO LTD

PADDINGTON 1008/9
303 EDGWARE RD.
LONDON W.2
Open Monday to Sat.
9-6, Thurs. 1 o'clock.

PLEASE TURN TO INSIDE PAGE